



# Wireless World


January 1970 Three Shillings

Electronic ignition system  
Microcircuit rationalization



**IT'S** Relays in all shapes and sizes to cover the whole industrial/electronic field—that's the measure of the Keyswitch product range  
**KEYSWITCH-** which includes the whole set of Omron miniatures. All Keyswitch Relays are winners because they each combine competitive price and high quality. When you go for Keyswitch quality and economy  
**WINNING** you'll get speedy service too—Keyswitch will produce a prototype relay in 24 hours, deliver a large order of standards in under a week and any specialist order within a month. So whatever type of relays you need, when  
**RELAYS ON** you want quality, good prices and prompt delivery, contact Keyswitch Relays Limited, Cricklewood Lane, London NW2; telephone 01-452 3344; telex 262754.  
**EVERY**  
**CIRCUIT**

KEYSWITCH RELAYS—WHERE THE ACTION IS

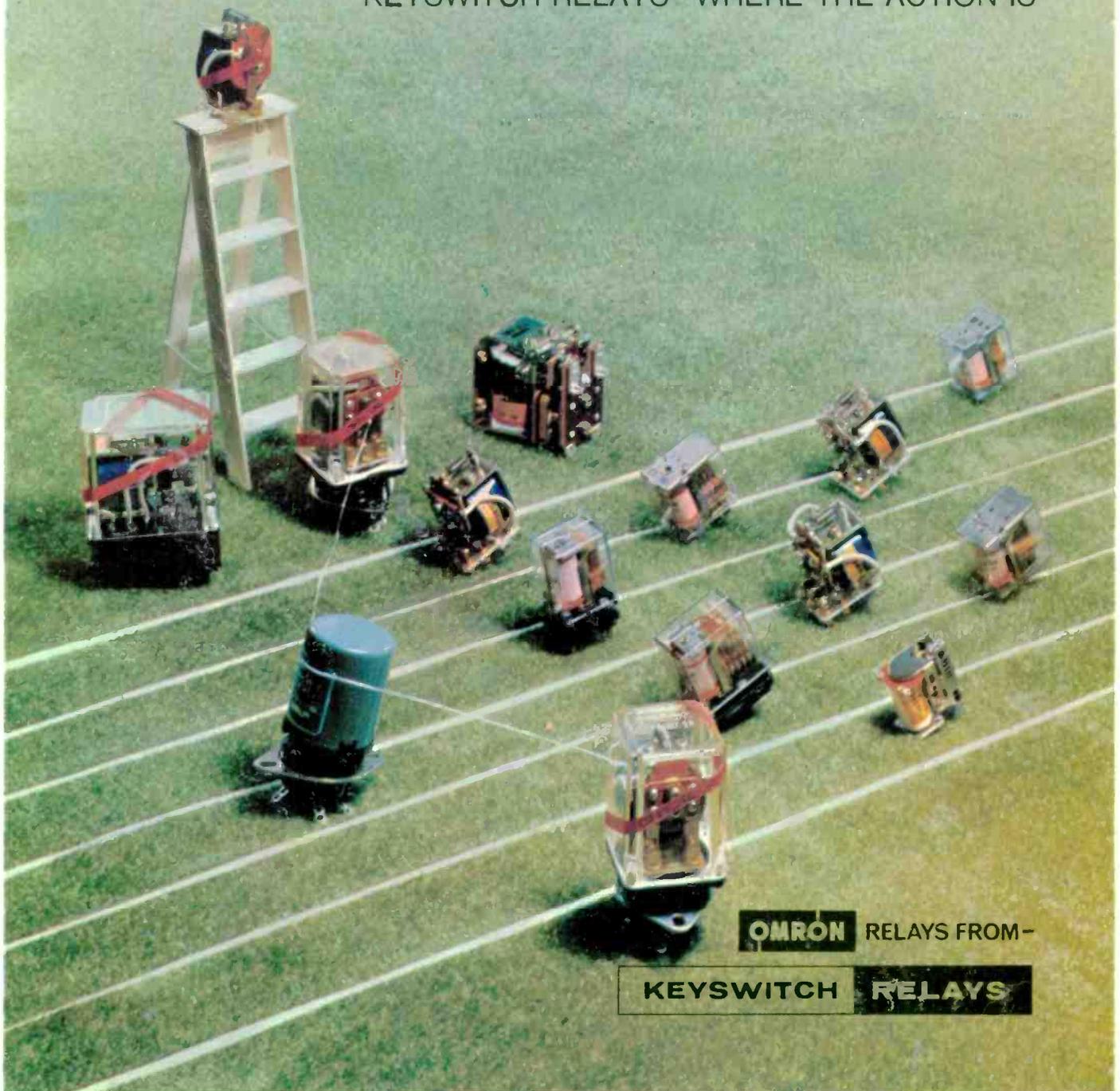

**OMRON** RELAYS FROM—

**KEYSWITCH RELAYS**

WW—001 FOR FURTHER DETAILS

# why the MULTIMINOR is still the best mini-meter

- It's still an Avometer yet fits in the pocket/held easily in one hand
- Has a d.c. sensitivity of  $10,000\Omega/V$
- Measures up to 25kV and 25A with optional accessories
- Accuracy conforms to B.S.S. 89/54.

Get your own Multimeter today (complete with plastic case, leads, instruction booklet and a full year's guarantee) from your local supplier, or ask for details direct from Avo.



**THORN**  
A Member of  
the Thorn Group

Avo Limited  
Avocet House, Dover, Kent  
Telephone: Dover 2626  
Telex: 96283

WW-006 FOR FURTHER DETAILS

# TRIO's New JR-310 SSB Professional Perfection for Amateur Enjoyment



## JR-310 SSB COMMUNICATIONS RECEIVER

\* High-stability VFO of 2 FET's and 2 transistors and easily handles QSO's for hours. \* Precision double gear dial—a TRIO innovation—with linear frequency variable capacitor. Possible to get finer reading 1KHz. One dial rotation covers 25KHz, makes SSB demodulation easier. \* Frequency range covers entire amateur band from 3.5MHz to 29.7MHz. One-touch selection system switches bands. WWV reception of 15MHz possible. \* MHz band circuit structure patterned on Collins type double conversion system so first oscillation is by crystal control, second local oscillation by VFO.

### SPECIFICATIONS OF JR-310

- \* FREQUENCY RANGE: 3.5-29.7 MHz (7 Bands)
- \* SENSITIVITY:  $1\mu\text{V}$  (at 10 dB S/N)
- \* IMAGE RATIO: More than 50 dB
- \* FREQUENCY STABILITY:  $\pm 2\text{KHz}$  in 1-60 min. after switching on, subsequently within 100Hz per 30 min.
- \* Dimensions: 13"(W), 7-3/32"(H), 12-3/16"(D).



### Model SP-5D COMMUNICATION SPEAKER

- \* Communications Speaker which has been designed for use with the 9R-59DE.
- \* Dimensions: 3-9/16"(W), 7-1/8"(H), 5-3/16"(D).



### Model 9R-59DE BUILT IN MECHANICAL FILTER 8 TUBES COMMUNICATION RECEIVER

- \* A mechanical filter enabling superb selectivity with ordinary IF transformers. \* Frequency Range: 550KHz to 30MHz (4 Bands) \* Sensitivity:  $2\mu\text{V}$  for 10dB S/N Ratio (at 10MHz) \* Selectivity:  $\pm 5\text{KHz}$  at -60dB ( $\pm 1.3\text{KHz}$  at -6dB). When using the Mechanical Filter \* Dimensions: Width 15", Height 7", Depth 10"



*the sound approach to quality*

**TRIO**  
TRIO ELECTRONICS, INC.

TO: B.H. Morris & Co., (Radio) Ltd. WW

Send me information on TRIO COMMUNICATION RECEIVERS & name of nearest TRIO retailer.

NAME: \_\_\_\_\_ AGE: \_\_\_\_\_

ADDRESS: \_\_\_\_\_

**TRIO-KENWOOD ELECTRONICS S.A.** 160 Ave., Brugmann, Bruxelles 6, Belgium

Sole Agent for the U.K. **B. H. MORRIS & CO., (RADIO) LTD.** 84/88, Nelson Street, Tower Hamlets, London E. 1, Phone: 01-790 4824

WW-007 FOR FURTHER DETAILS

# If you need power tetrodes at the right price look at this EEV range

## Forced-air Cooled

Type	Service type	Anode dissipation max. (kW)	Output power (kW)	Anode voltage max. (kv)	Frequency (MHz)	Filament ratings	
						(V)	(A)
4CX1000A 4CX1000K	—	1.0	3.2	3.0	110	6.0	9.0
4CX1500B	—	1.5	2.7	3.0	30	6.0	9.0
4CX5000A	CV8295	5.0	16.0	7.5	30/110	7.5	75
4CX10,000D	CV6184	10.0	16.0	7.5	30/110	7.5	75
4CX35,000C	—	35.0	82.0	20.0	30	10	300
CR192A (6166A)	CV8244	10.0	9.0	6.9	60/220	5.0	175

## Vapour Cooled

Type	Anode dissipation max. (kW)	Output power (kW)	Anode voltage max. (kv)	Frequency (MHz)	Filament ratings		Boiler unit
					(V)	(A)	
CY1170J	60	82	15	30	10	300	Integral
CY1172 (RS 2002V)	150	220	15	30	21	350	CY4120



**4CX1000K**

For audio or linear single sideband amplifiers. 4CX1000K has a solid disc screen contact to permit use up to 400MHz.



**4CX10,000D**

For audio, linear, single sideband or screen modulated r.f. amplifiers.




**4CX35,000C**

For audio amplifiers, r.f. linear amplifiers or Class C amplifiers or oscillators.



**CY1170J**

For audio amplifiers, r.f. linear amplifiers or Class C amplifiers or oscillators. Both types have a coaxial metal-ceramic envelope. A range of glass envelope types is also available.

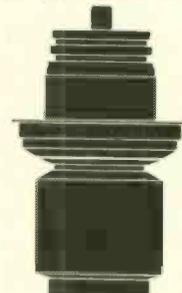

**CY1172**



**English Electric Valve Co Ltd**  
Chelmsford Essex England Telephone : 61777  
Telex : 99103 Grams : Enelectico Chelmsford



Send for full details of EEV tetrodes

Please send me full data on your range of forced-air cooled and vapour cooled tetrodes. I am also looking for a power tetrode with the following parameters.

Output power (kW)

Anode voltage max (kV)

Frequency (MHz)

NAME

POSITION

COMPANY

ADDRESS

TELEPHONE NUMBER

EXTENSION

ww39

WW—008 FOR FURTHER DETAILS

AP 358

**QUAD 50** is a single channel 50 Watt amplifier designed for Broadcast, Recording and other applications in the Audio industry, completely proof against misuse and giving the highest quality of reproduction.



**INPUTS** - 0.5 Vrms unbalanced with provision for an optional plug-in transformer for bridging 600 ohms lines.

**OUTPUTS** - isolated providing 50 watts into almost any impedance from 4 to 200 ohms.

**DIMENSIONS** - 12 $\frac{3}{4}$ " x 6 $\frac{1}{4}$ " x 4 $\frac{1}{2}$ "

*Complete the coupon and post today.*

**QUAD**  
for the  
closest approach  
to the  
original sound

Please send me full details of the QUAD 50 Amplifier

NAME .....

POSITION .....

COMPANY .....

ADDRESS .....



.....

(BLOCK CAPITALS)

**ACOUSTICAL MANUFACTURING CO. LTD.,**  
HUNTINGDON. Telephone: Huntingdon (0480) 2561/2

W W

WW-009 FOR FURTHER DETAILS

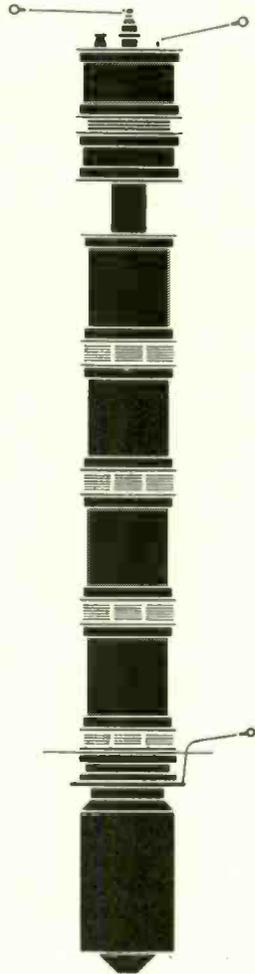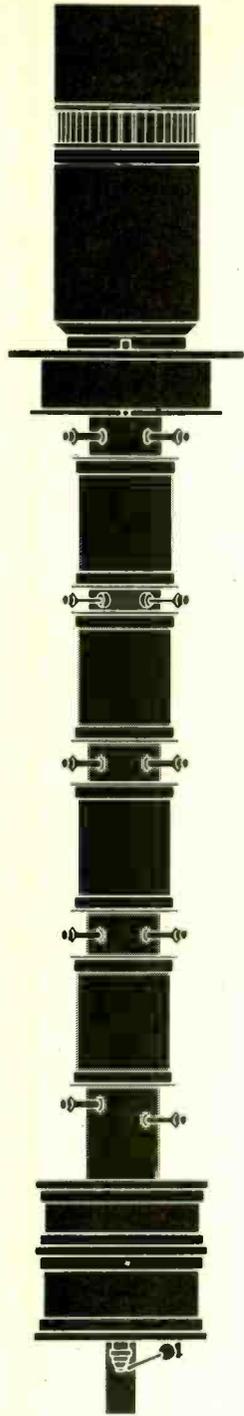

5 7 10 25 40 kW

# EEV klystrons – a wide and flexible range for UHF TV

Send for full details of the complete range of EEV amplifier klystrons.



EEV make amplifier klystrons for UHF TV at power levels 5, 7, 10, 25 and 40kW into the aerial. Their reliability is established, their operating efficiency is good and their design provides a high degree of operational flexibility. A 40kW tube can, for example, be operated at the same efficiency at any power level between 20kW and 40kW. When operated at 40kW the tube needs only 135kW d.c. input.

**English Electric Valve Co Ltd**  
Chelmsford Essex England Telephone: 61777  
Telex: 99103 Grams: Enelectico Chelmsford



Please send me full details of your range of UHF TV amplifier klystrons. I am interested in a klystron with the following parameters:

Frequency Range	Bandwidth	Power Level
<hr/>		
NAME	POSITION	
<hr/>		
COMPANY		
<hr/>		
ADDRESS		
<hr/>		
TELEPHONE NUMBER	EXTENSION	
<hr/>		

WW—010 FOR FURTHER DETAILS



# A New Kind of instrument case

## CONTIL MOD-2


### ideal for development.. cheaper for production

- PVC coated materials = No outside paint to be scratched. PVC easy to clean, surface is scuff resistant.
- PVC/aluminium for front and back panels = Easy cutting with rigidity.
- PVC/steel for sides, top and bottom = Rigidity, low cost and ease of assembly.
- 3 heights of case, 4 widths, 2 depths = 24 cases with screws on top and 24 cases with screws on side, that's 48 cases.
- Low cost = Prices include chassis.
- Modern design = Metal work on front and back and chassis is made easier by aluminium, with PVC steel cladding for strength.
- Good delivery = Believed to be the first off the shelf range of all PVC coated material cases.
- Easy ordering by code letter = Return of post service.
- Economy of size, 24 sizes, 48 shapes = 70 cubic inches to 2200 cubic inches for convenient sizing or layout, no wasted space.
- Genuine modular design = Cases may be mounted together as height includes feet.
- Stainless steel screws used throughout = Modern Pozidrive screws for good appearance and ease of use. Screw-driver cannot slip.
- 6 chassis sizes and many chassis positions on 1/2" centres = Easier planning and 1 to 4 or more chassis can easily be used.

	X	Y	Z	COST 1 off	5 off	10 off	P. & P.
A	4.5	3	6.5	29/6	29/-	28/9	3/-
B	4.5	7	6.5	36/6	35/6	34/6	4/6
C	4.5	10	6.5	46/6	45/6	44/6	4/6
D	9	3	6.5	46/6	45/6	44/6	4/6
E	9	7	6.5	49/6	48/6	47/6	4/6
F	9	10	6.5	58/6	57/6	56/6	4/6
G	13	3	6.5	49/6	48/6	47/6	4/6
H	13	7	6.5	58/6	57/6	56/6	4/6
I	13	10	6.5	69/6	68/6	67/6	6/-
J	18	3	6.5	58/6	57/6	56/6	4/6
K	18	7	6.5	79/6	77/6	76/6	6/-
L	18	10	6.5	106/-	104/-	103/-	6/-
M	4.5	3	13	36/6	35/6	34/6	4/6
N	4.5	7	13	49/6	48/6	47/6	4/6
O	4.5	10	13	69/6	68/6	67/6	6/-
P	9	3	13	49/6	48/6	47/6	4/6
Q	9	7	13	69/6	68/6	67/6	6/-
R	9	10	13	79/6	77/6	76/6	6/-
S	13	3	13	58/6	57/6	56/6	6/-
T	13	7	13	79/6	77/6	76/6	6/-
U	13	10	13	99/6	98/-	97/-	7/6
V	18	3	13	79/6	77/6	76/6	6/-
W	18	7	13	106/-	104/-	103/-	7/6
X	18	10	13	129/6	127/6	126/-	7/6

Sizes in inches Ex-stock. Return of post

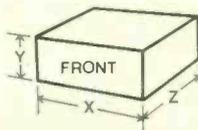For other West Hyde products please see previous advertisements



**LOW COST—FROM 29/6d. TO 129/6d. Laminated PVC Aluminium and PVC Steel.**

Printed circuit chassis will fit into H, I, K, L, T, U, W, X.




**WEST HYDE DEVELOPMENTS LTD.**  
30 HIGH STREET NORTHWOOD MIDDXX.  
Telephone: Northwood 24941

**PLEASE NOTE**  
All products ex-stock for normal quantities. Return of post service. Minimum order £1. Fully detailed leaflets available.

WW-011 FOR FURTHER DETAILS

# Heathkit for Instrumentation

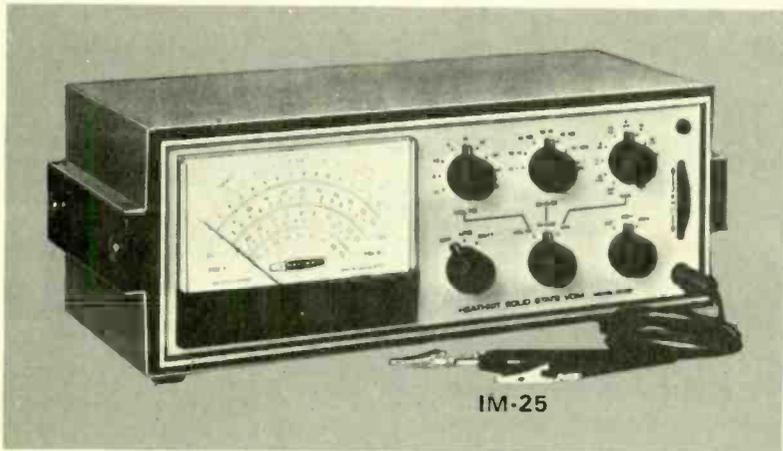


IM-25

The Heathkit range of scientific and electronic test instruments including the latest advances in solid state instrumentation has been especially prepared for the industrial and scientific laboratory instrument user. Whatever your requirements, be they Potentiometric Chart Recorders, Monochromators, Universal Digital Instruments as well as VVMs and general test instruments, substantial savings against similar specifications of other manufacturers can be made by using Heathkit instrumentation.

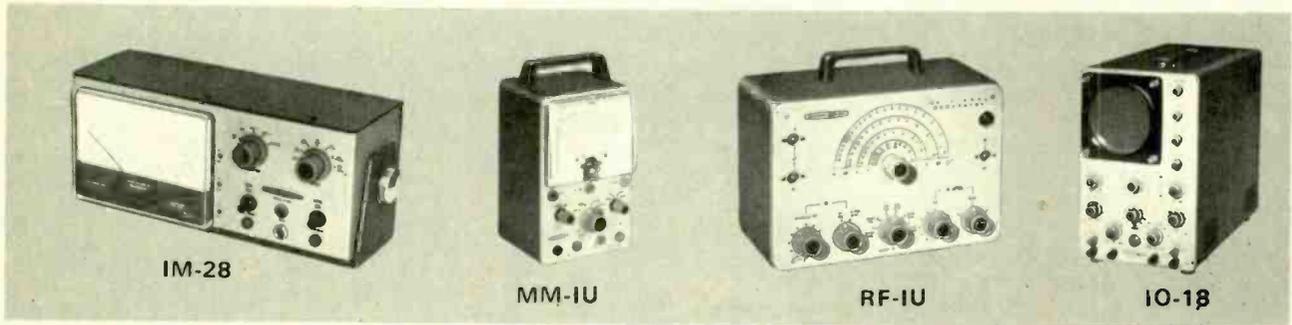**THE LATEST SOLID-STATE 'VVM' PLUS AC AND DC CURRENT, Model IM-25 is typical of the Heathkit ultra-functional instrumentation styling.**

- 9 AC and 9 DC voltage ranges from 150 millivolts to 1500 volts full scale.
  - 7 resistance ranges, 10 ohms centre scale with multipliers X1, X10, X100, X1K, X10K, X100K, and X1 Meg measures from 1 ohm to 1000 M ohms.
  - 11 current ranges from 15 $\mu$ A full scale to 1.5A full scale.
  - 11 M ohm input impedance on DC.
  - 10 Megohm input impedance on A.C.
  - A.C. response to 100 kHz.
  - 6in. 200 $\mu$  A meter with zero-centre for positive and negative voltage measurements without switching.
  - Internal battery power for 120/240 volt A.C. 50Hz.
  - Circuit board construction for extra rugged durability.
- Ready to Use A/IM-25 £47.6.0 Carr. 11/-  
Kit K/IM-25 £36.16.0 Carr. 11/-



IM-28

MM-IU

RF-IU

IO-18

**NEW RESTYLED TEST, SERVICE AND WORKSHOP INSTRUMENTS**

The Heathkit range of instrumentation can adequately provide engineers with quality instruments at lowest cost, whatever your requirements, be they VVMs, Generators, Oscilloscopes, Transistor Testers or Power Supplies.

**FOR THE HOME WORKSHOP**

The householder and hobbyist can, by purchasing easy-to-build Heathkits, obtain low cost models for testing household appliances, automobile circuitry, electrical/electronic models.



SEND FOR THE 1970  
FREE HEATHKIT CATALOGUE  
and see for yourself the wide range of instruments,  
Hi-Fi, Amateur and Leisure products

To: **DAYSTROM LTD.**, Gloucester, GL2 6EE, England  
 Please send me full details of Heathkit models  
 Send me FREE CATALOGUE

NAME .....  
ADDRESS .....


WW 1A



DAYSTROM LTD, Gloucester GL2 6EE, England.  
Tel: Glos 29451. Telex: 43216

WW-012 FOR FURTHER DETAILS
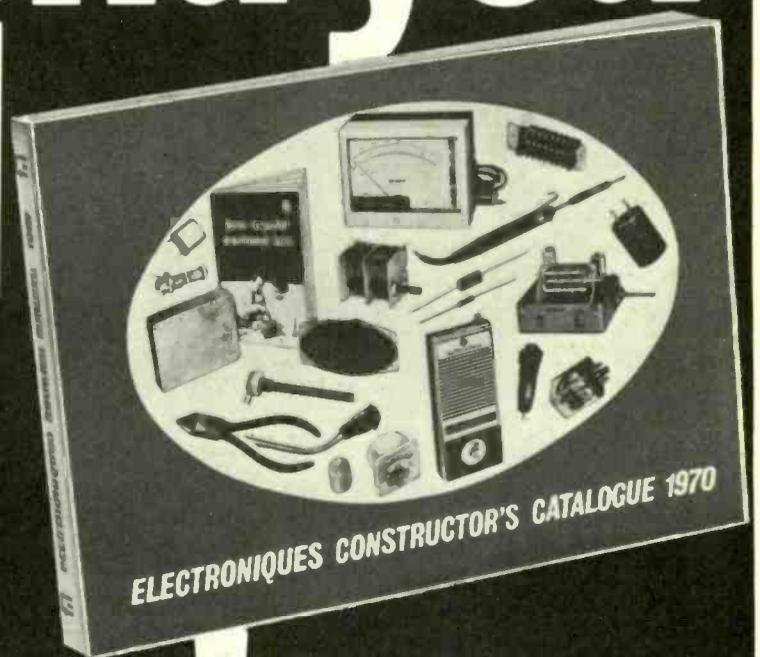
# This book will send you mad with desire!



Don't read on unless you're feeling really strong. This book will start you on a mad, crazy spending spree. It's got everything, but everything for the do-it-yourself radio and hi-fi man.

Everything from a vast range of electronic components available to the home electronics constructor, to a complete range of equipment for the radio "ham". What's the book?

The Electroniques Constructor's Catalogue. Only the most exciting, mouth-watering items are there. Carefully placed in 6 sections for easy reference. And backed by truly efficient sales service. So if you order any of the vast selection of goods, you're sure to get it pretty soon.

All you have to pay for this great big hunk of temptation is 13/- (including packaging and postage).

**So fill in the coupon now. If you dare.**

Enclose PO/cheque made out to:  
Electroniques (proprietors Standard Telephones  
and Cables Limited), Edinburgh Way, Harlow,  
Essex. Telephone: Harlow 26811.


Name .....

Address .....



ww1


WW—013 FOR FURTHER DETAILS

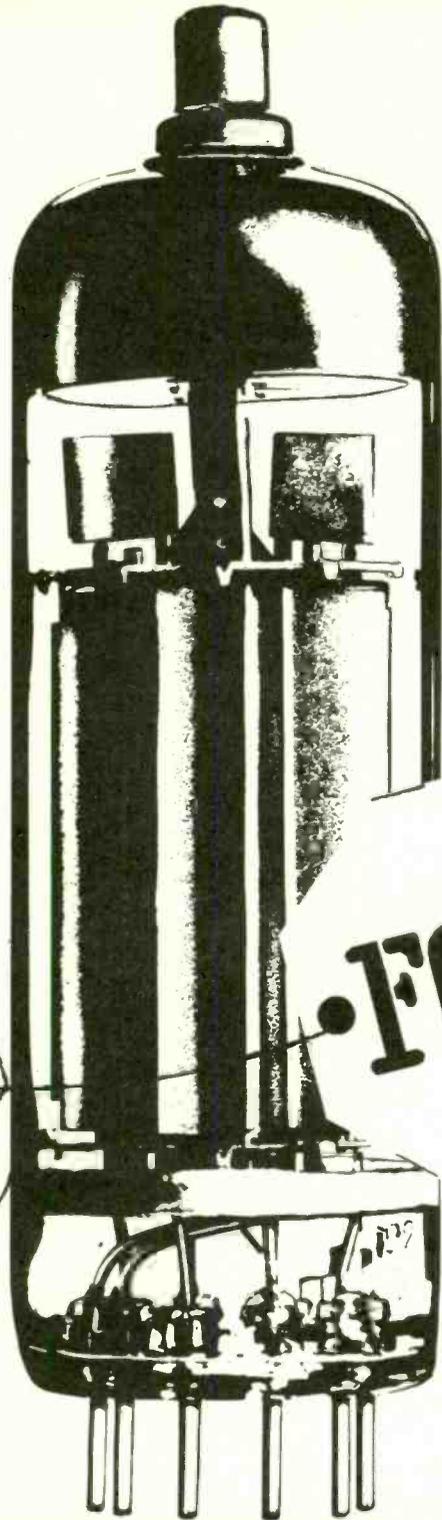

**Over 3,500  
specific  
types**

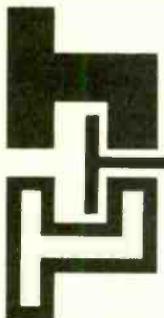**• FOR EXPORT**

For quality, reliability  
and world-wide  
availability you can  
rely on Haltron valves . . .  
and on Hall Electric's speed,  
intelligence and reputation.  
*Ministry of Technology EID approval  
Air Registration Board approval.*



**HALTRON**  
**Radio Valves and Tubes**


Hall Electric Limited  
Haltron House, Anglers Lane  
London, N.W.5.  
Telephone: 01-485 8531 (10 lines) Telex: 2-2573  
Cables: Hallectric, London, N.W.5.

WW—014 FOR FURTHER DETAILS



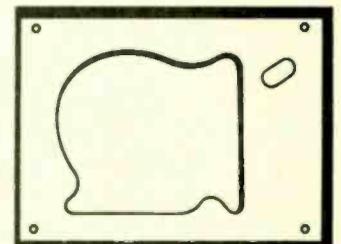
## MODEL 2000 PLINTH SYSTEM

The SME model 2000 plinth system is more than a handsome and convenient housing for your turntable and SME precision pick-up arm. It meets the mechanical requirements under which the best performance will be obtained. High-quality workmanship is combined with ease of assembly. The basic unit is finished in selected veneers of teak, straight-grained walnut, or rosewood. A one-piece hinged lid in heavy acrylic is reinforced with a polished stainless-steel trim.



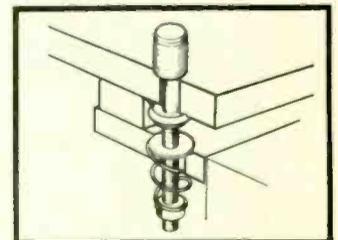*Motor boards in matching veneers are ready cut and drilled for screwdriver assembly with the appropriate pick-up arm and turntable. An uncut board is also available.*



*Four-point spring suspension adjustable for height and damping protects the motor board from acoustic feedback and external vibration.*

# SME

Write for details to: **SME LIMITED · STEYNING · SUSSEX · ENGLAND**

WW—015 FOR FURTHER DETAILS

## Our valves' statistics are vital!

We worry about the vital statistics of our special quality valves. Vital? The screen grid wire in Mullard industrial receiving valves is the thickness of a human hair (9.2 microns)—not much room for error. To ensure this standard of accuracy, we set up a special measurements department—one of the finest in Britain—making measurements down to one millionth of an inch. That's the sort of accuracy that ensures Mullard valves' built-in reliability.


**The time we spend on measurement control cuts your equipment down-time—another reason it pays to ask your supplier for Mullard**

# Mullard

Mullard Limited, Industrial Electronics Division,  
Mullard House, Torrington Place, London WC1. 01-580 6633
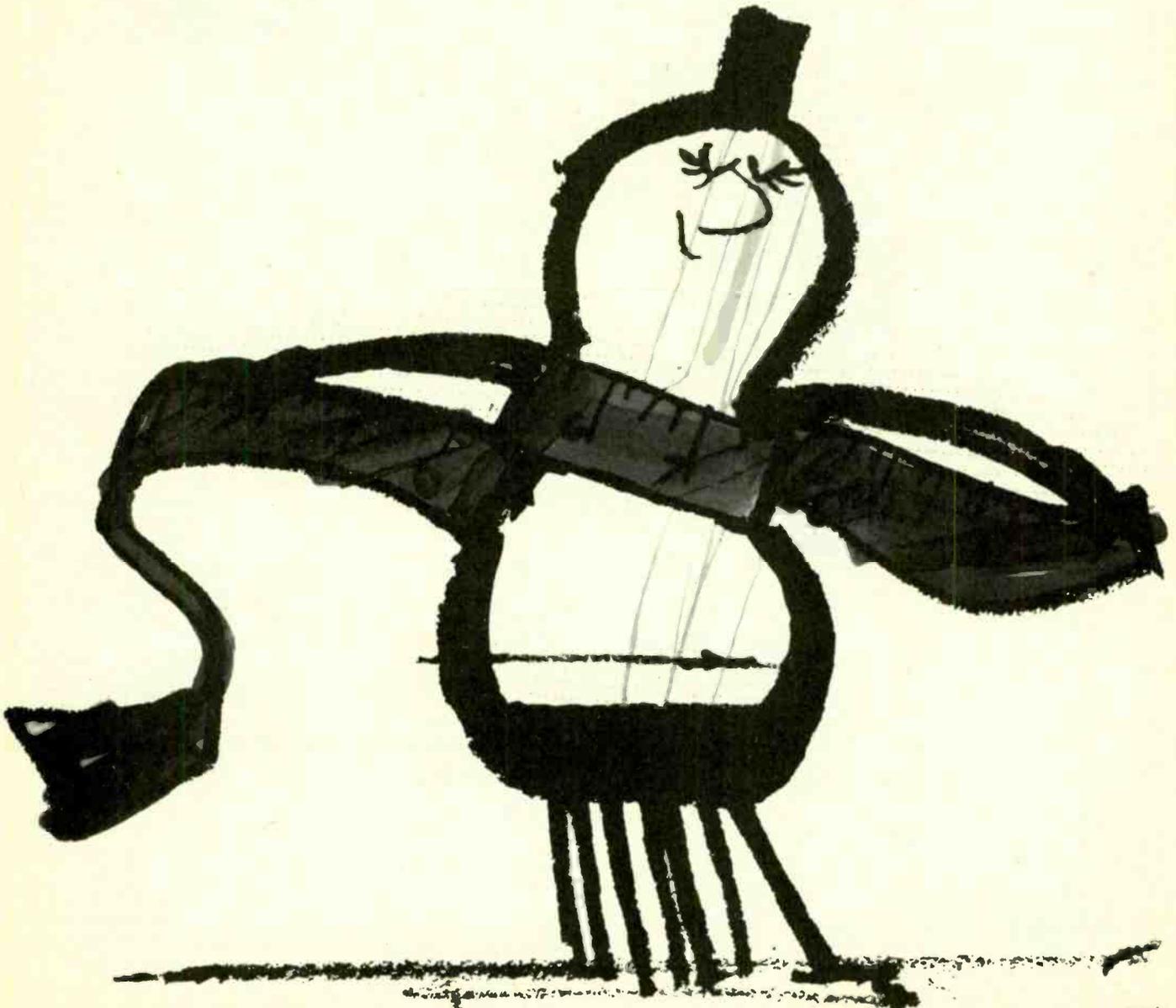
### New Buyers' Guide

There's a new wallchart on Mullard special quality receiving valves. It gives comprehensive equivalents information, and it's free from any Mullard Industrial Distributor, or just use the reader enquiry service.



# Tektronix Type 556 DC-to-50 MHz, dual-beam, sweep-delay oscilloscope

The Type 556 and rack-mount Type R556 use any combination of Tektronix letter or 1-series plug-ins

The UPPER BEAM can display a signal from either *left* or *right* plug-in; with either Time Base A, Time Base B, or external signals; triggered from a composite vertical signal, plug-in single channel signal (with 1A1 or 1A2), external, or line.

*Independent Vertical Systems* use Type 1A1 or 1A2 Plug-in Units for 50 MHz operation; also accept any other 1-series or letter-series plug-in units.

*Independent Sweep Systems* provide 24 calibrated steps from 0.1  $\mu\text{s}/\text{cm}$  to 5s/cm; the X10 Magnifier extends the fastest sweep rates to 10ns/cm.

*Calibrated Sweep Delay* extends continuously from 0.1 microsecond to 50 seconds.

*Signal-Sweep Operation* enables one-shot displays of normal or *delayed* sweeps.


*Independent Triggering Systems* provide

stable displays to beyond 50MHz. Either input signal can be used to trigger either or both time-bases.


*New Dual-Beam CRT* (with illuminated internal graticule) provides "zero-parallax" viewing of small spot size and uniform focus over the 8cm by 10cm display area. Each beam has 6cm vertical scan, with overlap scan of 4cm by 10cm.

*EMI (RFI) Suppression* — meets interference specifications of MIL-I-6181D over these frequency ranges: 150kHz to 1GHz — Radiated (with CRT mesh filter installed), and 150kHz to 25MHz — Conducted (power line).

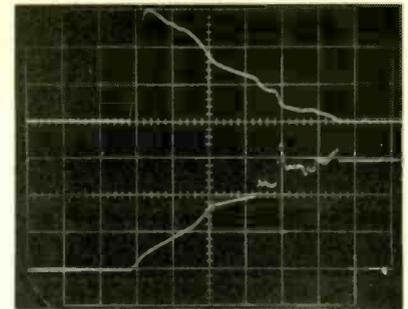stable displays to beyond 50MHz. Either input signal can be used to trigger either or both time-bases.



**Simultaneous Single-shot Displays.** Current versus voltage display of a 0.75 ampere, fast-blow fuse during destructive overload. Both beams are driven by B Time-Base at 50  $\mu\text{s}/\text{cm}$  which is delayed by pre-triggered A Time-Base to provide base reference lines before and after the event. The upper beam shows the current waveform at 30A/cm while the lower beam shows the corresponding voltage across the fuse at 100V/cm.

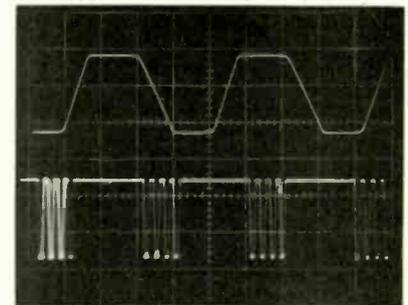

**Single-input Dual-beam Displays.** Upper beam shows bursts of 2.5MHz pulses on Time Base A with time variation between bursts. This shows up as increasing time-jitter between the first and successive bursts. The lower beam shows B Sweep (0.1  $\mu\text{s}/\text{cm}$ ) delayed by A Sweep and triggered on the second pulse of the last burst to provide a jitter-free expanded display of the A Sweep intensified zone. The use of only one probe and one plug-in input simplifies signal connection and provides minimum loading on the source.


#### Plug-in units shown

Type 1A1 Dual-trace Unit (Dual-Trace—50mV/cm at DC-to-50 MHz, 5mV/cm at DC-to-28 MHz. Single-Trace—500  $\mu\text{V}/\text{cm}$  at 2Hz-to-15 MHz. 5 Display Modes—Channel 1, Channel 2, Alternate, Chopped, Added Algebraically. Front-panel signal output.)

#### Type W Differential

Comparator Unit (Conventional Pre-amplifier—50mV/cm at DC-to-23MHz to 1mV/cm at DC-to-8MHz. Decade Input Attenuator to X1000. Differential Input Pre-amplifier—CMRR of 20,000 to 1, DC-to-20kHz. Max Peak Input of  $\pm 15\text{V}$ , XI Attenuation. Calibrated Differential Comparator—Vc Supply of 0 to  $\pm 11\text{V}$ . Accuracy of  $\pm 0.15\%$  of output  $\pm 0.05\%$  FS.)

Price without plug-in units—£1,560

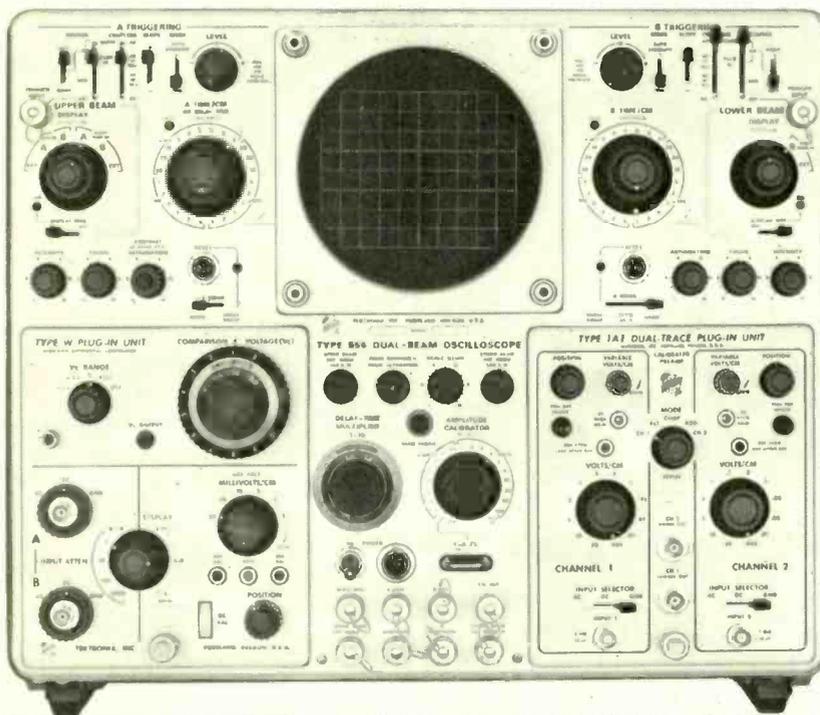

For detailed information on any of our products, please fill in reader reply card or write, telephone or telex.



## Tektronix U.K. Ltd.

Beaverton House · P.O. Box 69 · Harpenden · Herts  
Telephone: Harpenden 61251 · Telex: 25559

#### For overseas enquiries:

**Australia:** Tektronix Australia Pty. Ltd., 4-14, Foster Street, Sydney, N.S.W. **Canada:** Tektronix Canada Ltd., Montreal, Toronto & Vancouver. **France:** Relations Techniques Intercontinentales, S.A., 91, Orsay, Z.I. Courtaboeuf, Route de Villejust (Boite Postale 13). **Switzerland:** Tektronix International A.G., P.O. Box 57, Zug, Switzerland. **Rest of Europe and the Middle East:** Tektronix Ltd., P.O. Box 36, St. Peter Port, Guernsey, C.I. **All other territories:** Tektronix Inc., P.O. Box 500, Beaverton, Oregon, U.S.A.

WW—016 FOR FURTHER DETAILS

# VALUABLE NEW HANDBOOK FREE TO AMBITIOUS ENGINEERS

Have you had *your* copy of "Engineering Opportunities"?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

### On 'SATISFACTION OR REFUND OF FEE' terms

This remarkable book gives details of examinations, and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

### WHICH OF THESE IS YOUR PET SUBJECT?

#### ELECTRONIC ENG.

Advanced Electronic Eng. — Gen. Electronic Eng. — Applied Electronics — Practical Electronics — Radar Tech. — Frequency Modulation — Transistors.

#### ELECTRICAL ENG.

Advanced Electrical Eng. — Gen. Electrical Eng. — Installations — Draughtsmanship — Illuminating Eng. — Refrigeration — Elem. Electrical Science — Electrical Science — Electrical Supply — Mining Electrical Eng.

#### CIVIL ENG.

Advanced Civil Eng. — Gen. Civil Eng. — Municipal Eng. — Structural Eng. — Sanitary Eng. — Road Eng. — Hydraulics — Mining — Water Supply — Petrol Tech.

#### RADIO ENG.

Advanced Radio — Gen. Radio Radio & TV Servicing — TV Eng. — Telecommunications — Sound Recording — Automation — Practical Radio — Radio Amateurs' Exam.

#### MECHANICAL ENG.

Advanced Mechanical Eng. — Gen. Mechanical Eng. — Maintenance Eng. — Diesel Eng. — Press Tool Design — Sheet Metal Work — Welding — Eng. Pattern Making — Inspection — Draughtsmanship — Metallurgy — Production Eng.

#### AUTOMOBILE ENG.

Advanced Automobile Eng. — Gen. Automobile Eng. — Automobile Maintenance — Repair — Automobile Diesel Maintenance — Automobile Electrical Equipment — Garage Management.

WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS INCLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRUMENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.

Which qualification would increase your earning power?  
 A.M.I.E.R.E., B.Sc. (Eng.), A.M.S.E., R.T.E.B., A.M.I.P.E.,  
 A.M.I.M.I., A.R.I.B.A., A.I.O.B., P.M.G., A.R.I.C.S.,  
 M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., C.ENG., CITY & GUILDS,  
 GEN. CERT. OF EDUCATION, ETC.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY  
 446A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

### THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointments Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

164 PAGES OF EXPERT CAREER-GUIDANCE

#### PRACTICAL EQUIPMENT

Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, etc. A.M.I.E.R.E. City & Guilds Radio Amateurs' Exam., R.T.E.B. Certificate, P.M.G. Certificate, Practical Radio, Radio & Television Servicing, Practical Electronics, Electronics Engineering, Automation.

#### INCLUDING TOOLS

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.

## B.I.E.T.

You are bound to benefit from reading "ENGINEERING OPPORTUNITIES." Send for your copy now—FREE and without obligation.



## POST COUPON NOW!

TO B.I.E.T., 446A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE.

Please send me a FREE copy of "ENGINEERING OPPORTUNITIES." I am interested in (state subject, exam., or career).

NAME .....

ADDRESS .....


WRITE IF YOU PREFER NOT TO CUT THIS PAGE

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

WW-017 FOR FURTHER DETAILS

# PURE 100 WATT POWER

TRY IT AND SEE!

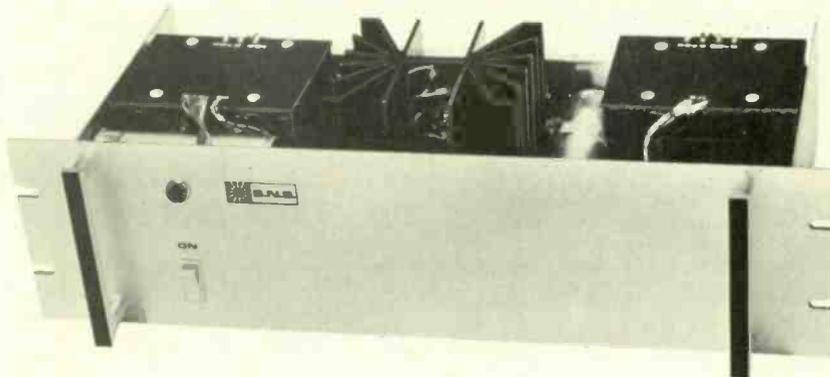

None of this "see if you can squeeze it up to 100 watts". "Well it gets there at 2.875 KHz — anyway this is P.A., not HiFi — so who cares what the distortion is so long as it is not more than 6 or 7 per cent." **The S.N.S. CD.100 amplifier gives a pure, fully transistorised power output of 100 watts at 1 KHz with distortion less than 1 per cent.** You are probably saying "I've heard it all before". So have we! That is why we have built an amplifier which will set new standards in craftsmanship and performance. To prove it we will loan you one for a seven day free trial.

The CD.100 illustrated is a single input unit giving 100 watts RMS output for 25 mV input at 1 KHz so it can be driven by any tuner or tape machine or, of course, the output of a mixer. 50/100 volt line output (0-50-0-50) \*Distortion less than 1 per cent at 1 KHz. \*Full short circuit protection with the exclusive S.N.S. Current Lok circuit. \*Ample thermal capacity to ensure the transistors run within their limits at 100 watts continuous Sine Wave. All these plus points, and many more, make the CD.100 yet another S.N.S. success.




## S.N.S. COMMUNICATIONS LTD.

851 RINGWOOD ROAD — WEST HOWE — BOURNEMOUTH — HANTS — ENGLAND  
Telephone Northbourne 4845/2663. Telegrams: Flexical Bournemouth — Telex: 41224

Manufacturers of: Transistor Amplifiers, Crystal AM and FM Tuners, Radiomicrophones, Cabinet and Line Source Loudspeakers, Loudspeaking Intercom Systems, Hotel Radio and Intercom Systems.

WW—018 FOR FURTHER DETAILS

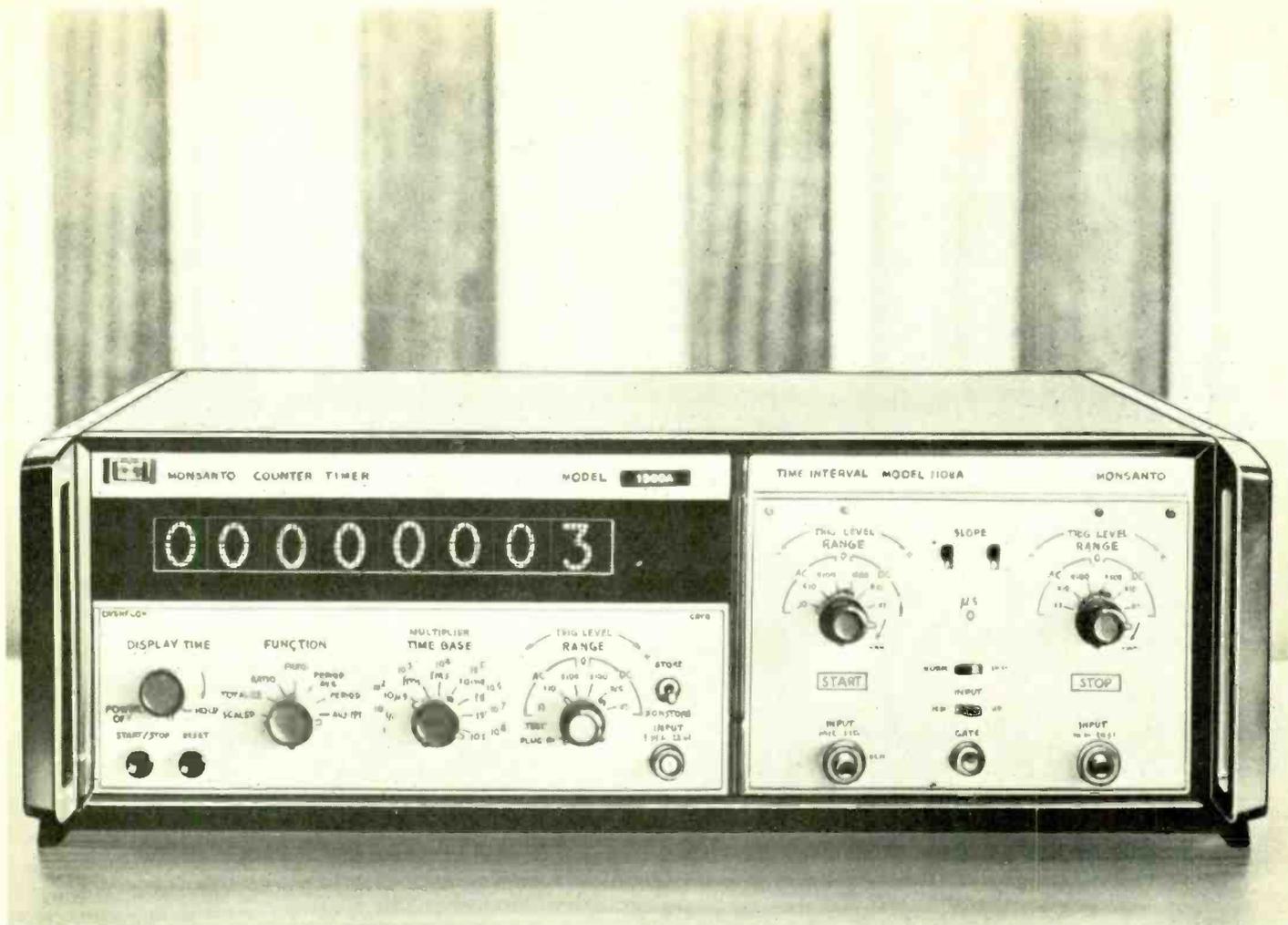

**This new "4th generation" I-C plug-in counter/timer outperforms all others . . . including from d.c. to 3 GHz with only one plug-in . . .**

Why compromise for less? The Model 1500A has a main frame counting range from dc to 125 MHz (to 3 GHz with a single plug-in). This instrument is fully programmable, has provision for external time base up to 10 MHz, and many other significant features, including the well recognised advantages of Monsanto's "4th generation" 90% integrated circuit design. The Model 1104B frequency converter unit covers the range dc to 3 GHz with only one plug-in. Also available: Model 1100A uncommitted plug-in; Model 1101A 500 MHz prescale plug-in; Model 1102A 6-digit preset plug-in; Model 1103A 500 MHz frequency converter plug-in; Model 1107A time interval plug-in; Model 1201A DVM plug-in. Unparalleled performance plus award-winning design make the Model 1500A the ultimate counter for the no-compromise engineer.

Most engineers take Monsanto's reliability for granted because of our 2-year warranty.

For a demonstration, or for full technical details, call 01-450 7811 or write to our exclusive agents:

**G. & E. BRADLEY LTD.**

Electral House, Neasden Lane, London, N.W.10.

# Monsanto

WW-019 FOR FURTHER DETAILS



# Hybrids?

We make them by the million!

That's our Jo\*. . . We gave her seven words and a daisy; and the wall came tumbling down.

The wall of silence. Distinct among the major suppliers of hybrid IC's and passive networks, we at Erie soft-pedalled our publicity. We had to. Because keen commercial minds in UK and Continental companies snapped at the fact that Erie hybrids give complete circuit functions *in less time, at less cost*, than if you select, buy and assemble your own discrete components . . . and give you a hefty bonus in increased reliability. So our order books were

full. And stayed full; even with output rates of 2.5 million units a year.

But now we are coming to you with all this experience. Because now we can give you the only kind of service our reputation will permit. Prompt, personal service. With teams of physicists, chemists, microelectronics specialists, waiting to tackle your problem. With an advanced manufacturing capability that will lift output to the multi-million level, raise reliability even higher, make prices even more competitive. A capability backed by a Quality Assurance laboratory approved

to BS 9000, and all of Erie's world-wide experience.

Send for Publication No. 1. It gives you all the facts. Better still, send for an Erie sales engineer. He will understand your problem.

**ERIE  
ELECTRONICS  
LIMITED**

\* Short for Joshua??



**ERIE ELECTRONICS LTD.,**  
Great Yarmouth, Norfolk.  
Tel: 0493 4911.  
Telex: 97421

**ERIE THICK FILM INTEGRATED CIRCUITS**

WW—020 FOR FURTHER DETAILS

# Three good ideas shelved

# by JJ Instruments



### Decade Capacitors


Accuracy  $\pm 1\%$  alternatively  $\pm \frac{1}{2}\%$ .  
500 volts d.c. working.

- 3 Decade - Cat. Ref. C3 - 100 pf. to 0.111 mfd. in 100 pf. steps.
- 4 Decade - Cat. Ref. C4 - 100 pf. to 1.111 mfd. in 100 pf. steps.
- 4 Decade plus Air Spaced Capacitor - Cat. Ref. VC5 - 50 pf. to 1.1115 mfd. infinitely variable.
- 3 Decade - Cat. Ref. C3 - 100 pf. to 1.111 mfd. in 100 pf. steps.
- 3 Decade plus Air Spaced Capacitor - Cat. Ref. VC4 - 50 pf. to 0.1115 mfd. infinitely variable.
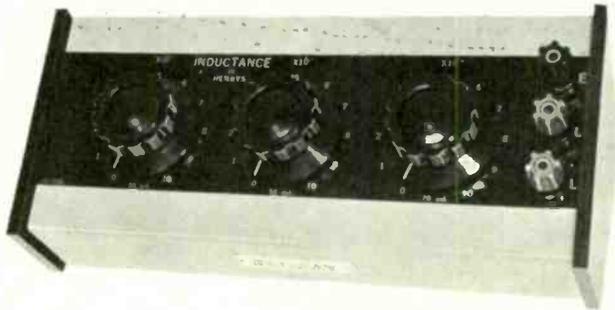
### Switched Capacitor Boxes

Accuracy  $\pm 5\%$  or alternately  $\pm 1\%$ .  
Cat. Ref. C.60 0 to 61 mfd. in 0.1 mfd. steps.  
C.100 0 to 100 mfd. in 1 mfd. steps.  
C.140 0 to 140 mfd. in 1 mfd. steps.

All instruments calibrated in absolute units so that no correction has to be made for strays.




### Decade Resistance

Average Accuracy 0.1%. Residual resistance:

4 Decade - 12 milliohms, 5 Decade - 15 milliohms.

Decade	X 100,000 ohms	X 10,000 ohms	X 1,000 ohms	X 100 ohms	X 10 ohms	X 1 ohm	< 0.1 ohm
Max. Cont. Current	3 mA	7 mA	20 mA	70 mA	200 mA	700 mA	1 A
Short time current rating	3.2 mA	10 mA	32 mA	100 mA	320 mA	1 A	1 A

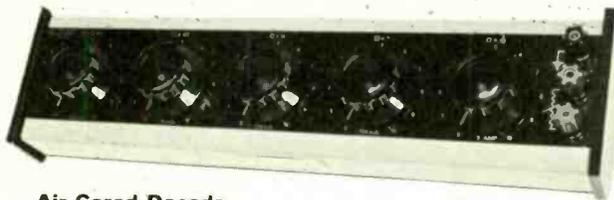Precision Metal film decade resistance box suitable for use both on d.c. and at high frequencies. Accuracy actually improves with use and age.



### Air Cored Decade Inductor

Accuracy  $\pm 5\%$

- 3 decade model Cat. Ref. L1 1 mH to 1 Henry
- 2 decade model Cat. Ref. L2 1 mH to 100 mH
- 2 decade model Cat. Ref. L3 10 mH to 1 Henry

Also available precision Air Spaced Capacitors, Conductance Boxes, Loading Resistors, standard Resistors and Capacitors, Potentiometers, Resistance Bridges and Solid State d.c. Null Detectors.

All Instruments Available from Stock

- 5 Decade Cat. Ref. R7 1,111,100  $\Omega$  by 10  $\Omega$  steps
- Cat. Ref. R9 111,110  $\Omega$  by 1  $\Omega$  steps
- Cat. Ref. R10 11,111  $\Omega$  by 0.1  $\Omega$  steps
- 4 Decade Cat. Ref. R5 111,100 by 10  $\Omega$  steps
- Cat. Ref. R4 11,110 by 1  $\Omega$  steps
- Cat. Ref. R3 1,111 by 0.1  $\Omega$  steps




And Our Sales Engineers always carry a wide range


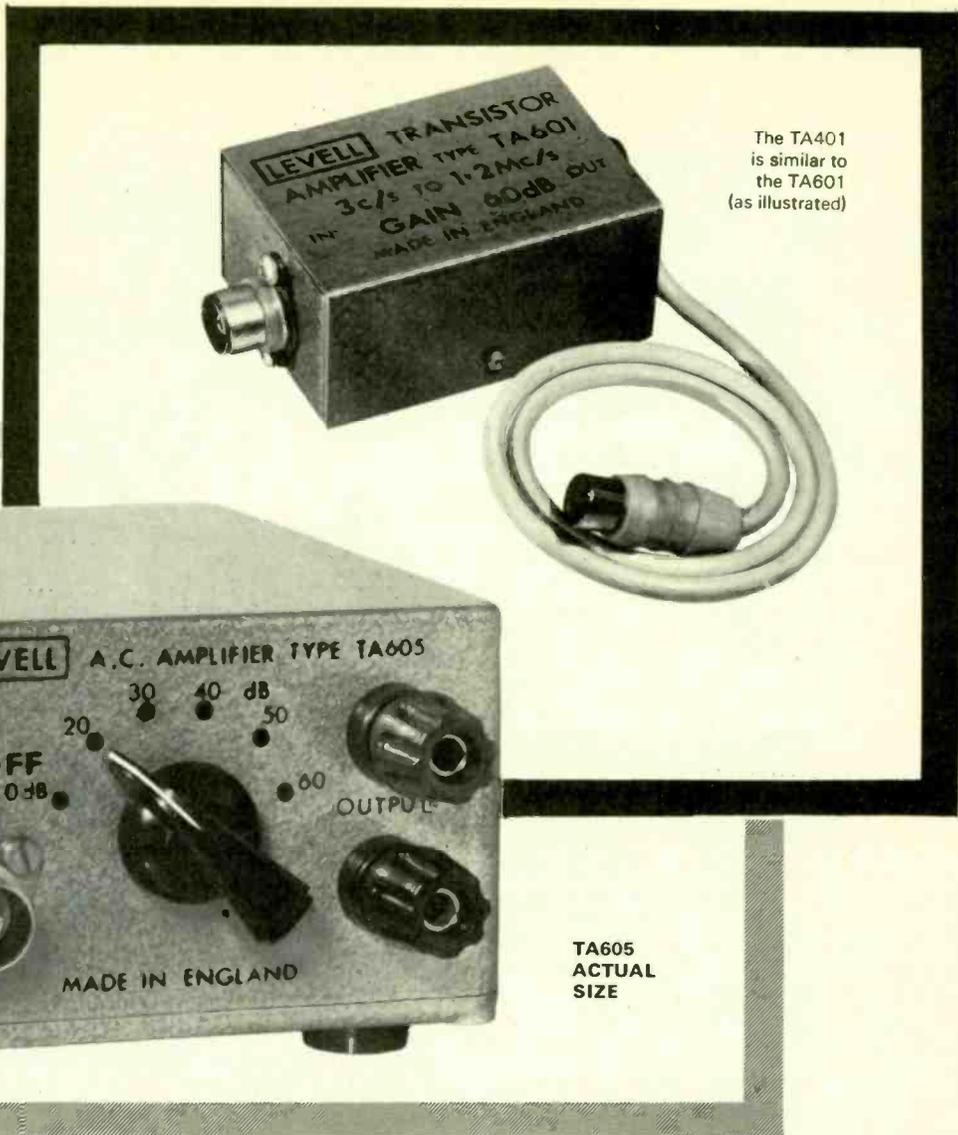
## J.J. Lloyd Instruments Limited

Brook Avenue, Warsash, Southampton SO3 6HP Tel: Locks Heath 84221

**INCREASE  
THE SENSITIVITY OF  
YOUR OSCILLOSCOPE,  
VOLTMETER  
OR  
COUNTER**



The TA401 is similar to the TA601 (as illustrated)

TA605 ACTUAL SIZE

**SPECIFICATIONS**

	TYPE TA401	TYPE TA601	TYPE TA605
<b>GAIN</b>	40dB ±0.1dB	60dB ±0.1dB	20, 30, 40, 50 and 60dB ±0.2dB.
<b>BANDWIDTH ±3dB</b>	1 Hz-3MHz	3Hz-1.2MHz	20-40dB, 1Hz-3MHz; 50dB, 2Hz-2MHz; 60dB, 4Hz-1.5MHz.
<b>BANDWIDTH ±0.3dB</b>	4Hz-1MHz	10Hz-300kHz	20-40dB, 4Hz-1MHz; 60dB, 10Hz-300kHz.
<b>INPUT IMPEDANCE</b>	>5MΩ, <40pF from 100Hz to 1MHz	>1MΩ, <50pF from 100Hz to 300kHz	>5MΩ, <40pF from 100Hz to 300kHz.
<b>INPUT NOISE</b>	<15 μV, zero source; <50 μV, 100k Ω source	<15 μV, zero source; <40 μV, 100k Ω source	As TA401 and TA601 at 40dB and 60dB.
<b>POWER SUPPLY</b>	PP3 battery, life 100 hours		PP9 battery, life 1,000 hours, or A.C. Power Unit.
<b>AVAILABLE OUTPUT</b>	1V up to 1MHz, 300mV at 3MHz, into load of 100kΩ and 50pF		1.5V up to 2MHz, 1V at 3MHz, into 100kΩ and 50pF.
<b>OUTPUT IMPEDANCE</b>	100 Ω in series with 6.4 μ F		
<b>SIZE AND WEIGHT</b>	3" x 1½" x 1½" 7 oz.		2½" x 4" x 5½" 2½ lb.
<b>PRICE with Battery and input lead</b>	£17.0.0	£17.0.0	£27.0.0 (Optional A.C. Power Unit £7.10.0 extra).



Fully detailed leaflets are available on our complete range of portable instruments

**LEVELL ELECTRONICS LIMITED**

Park Road, High Barnet, Herts. Telephone: 01-449 5028  
WW-022 FOR FURTHER DETAILS

*Years* of research...

**"STETOMIKE"**  
**THE NEW STETOCLIP**  
**HEADSET**  
**WITH**  
**BOOM MICROPHONE**



STETOMIKE is the new revolutionary Stethoscope type headset fitted with a Boom-arm Microphone.

STETOMIKE is practically weightless (approx 1½ oz) compared with the usual conventional cumbersome heavy headphones (with Boom-arm Microphone) at present being used.

STETOMIKE is ideal for children and adults, and due to its lightness can be worn for long periods without discomfort and numbness.

STETOMIKE is constructed of pale grey high tensile plastic parts of advanced design. It uses the latest Danavox sensitive balanced armature microphone capsule and magnetic earphones.

STETOMIKE employs a simple unit construction and in the event of unavoidable damage, all items are quickly replaceable on the spot, by the readily available Danavox spare parts service.

STETOMIKE is competitively priced and is directly available to manufacturers and relevant wholesalers.


STETOMIKE is ideal for many projects including speech trainers, telecommunications, walkie-talkies, centralised dictation systems, educational and industrial training equipment, audio equipment and with C.C.T.V. cameras.

**OTHER**  
**DANAVOX**  
**PRODUCTS**

Stetoclip Headsets, Dictating Machine Headsets, Hospital Patients' Headsets, Headphones, Industrial and Hearing Aid type Earphones and Cords, Earhangers, Pillow Speakers, Foot Switches, Throat Microphones, Microphone Capsules, Jack Plugs and Sockets, micro-miniature switches etc.

**Danavox**  
INTERNATIONAL

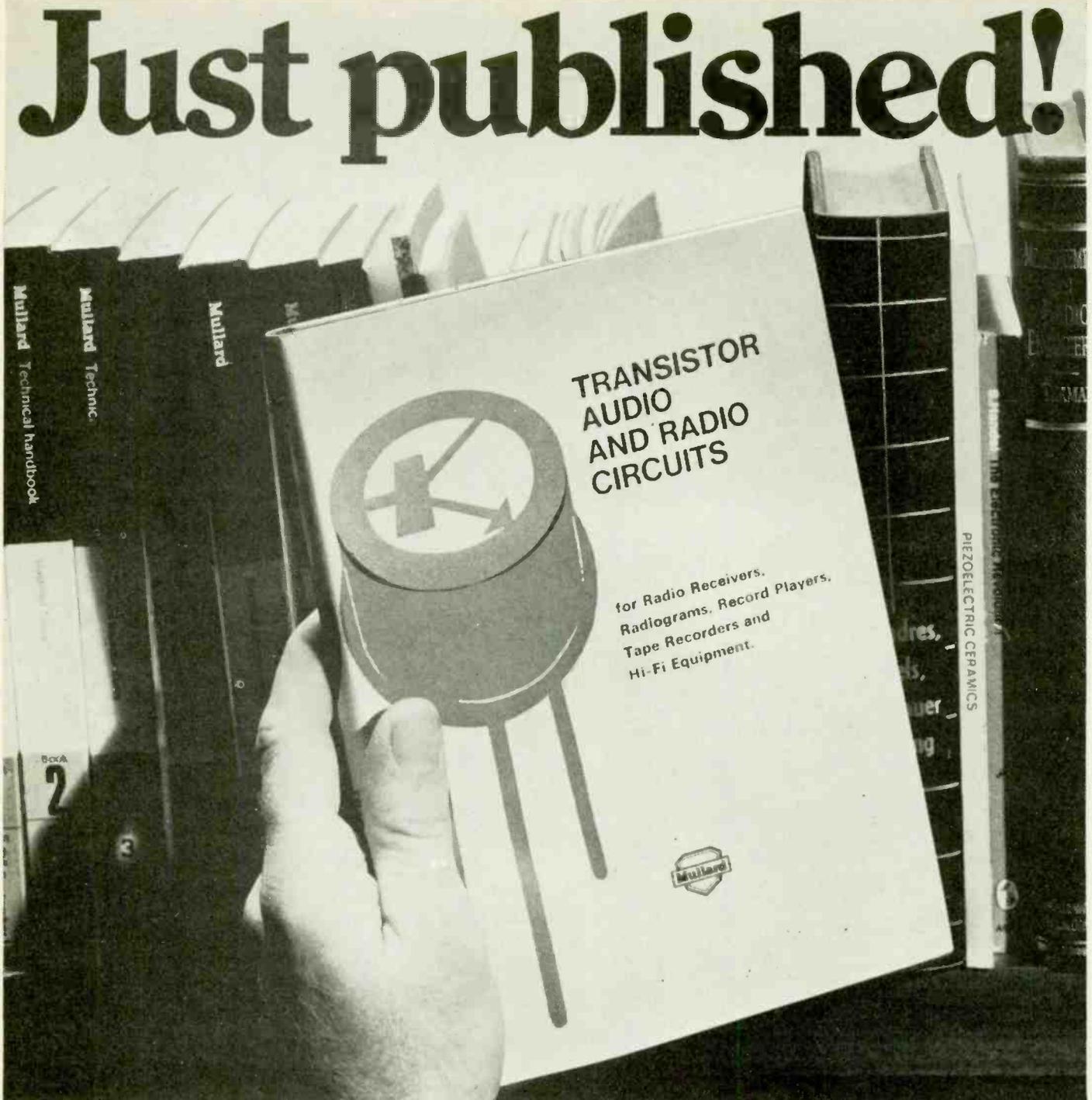**DANAVOX (GT. BRITAIN) LTD.**  
*Electro-Acoustic Components and Hearing Aids*  
"BROADLANDS", SUNNINGHILL, ASCOT, BERKS.  
Telephone: ASCOT 23732/6



## Produced by experts for Engineers, Students and Enthusiasts

This is the book you've been waiting for! Over 200 information-packed pages. Circuits for audio amplifiers, record players, tape recorders, f.m. tuners and portable radio receivers up to hi-fi standards, all designed and proven in Mullard laboratories.

Mullard publications are renowned for the technical authority of their contents and the clarity and style of their presentation.

'Transistor Audio and Radio Circuits' is another outstanding example — there's bound to be a big demand.

It's handy sized and strongly bound. Tremendous value at 30/-.

Get your copy from your local radio retailer, bookshop or direct from Mullard (cash with order) 32/- per copy including postage and packing.

# Mullard

Mullard Limited, Distributor Sales Division,  
Mullard House, Torrington Place, London W.C.1.

CED91

# Heathkit Stereo Hi-fi . . .



STEREO 'COMPACT' AD-27

Are you a do-it-yourself man? Would you like to own a first-class Hi-fi outfit at a do-it-yourself price? The wide range of world-famous Heathkit products offers something for everyone.

## STEREO 'COMPACTS'

The newest additions to the Heathkit range are two "stereo compacts". The AD-27, pictured left includes a turntable unit with a Shure magnetic cartridge, an FM stereo tuner and a 30 watt stereo amplifier. The whole is built into an attractive compact teak or walnut veneered cabinet - all for a kit price of only £82! The AD-17 compact is similar but does not have the FM radio facility and uses a simpler but still attractive cabinet. This kit only costs £54.



STEREO TUNER/AMPLIFIER, AR-14

## STEREO TUNER AMPLIFIERS

If you need a Tuner-Amplifier, we can offer models to suit any pocket. Pictured on the left is the very popular Heathkit AR-14. This is a solid-state stereo Tuner-Amplifier with a sensitive FM tuner, a built-in stereo decoder and a 30 watt stereo amplifier (15 watts I.H.F.M. per channel). It is wonderful value at a kit price of £54.



STEREO TUNER TFM-15

STEREO AMPLIFIER, TSA-12

## STEREO 'SEPARATES'

If your preference is "separates", or perhaps you want just a stereo amplifier without a tuner, again Heathkit offers a selection. Typical is the TSA-12 stereo amplifier, illustrated. This is a solid state stereo amplifier (15 watts I.H.F.M. per channel) at a kit price of only £32 16 0. We have radio tuners to match either for FM reception only, or for FM and Long and Medium wave. The Stereo Tuner, model TFM-15 costs only £28 14 0 in kit form.


## LOUDSPEAKER SYSTEMS

All the units described above can be used with any good hi-fi loudspeakers. To cover this need, the Heathkit range includes several hi-fi loudspeaker kits. The Berkeley kit features a 12 in. bass loudspeaker and a 4 in. high-frequency unit, a ready finished teak or walnut veneered cabinet, and the kit price is only £21 4 0. The 'Avon' mini kit is only £13 8 0.

A WIDE CHOICE OF SPEAKER SYSTEMS



BERKELEY

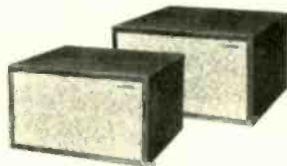

AVON

See the complete range in the FREE CATALOGUE!

TO DAYSTROM LTD, GLOUCESTER, GL2-6EE.

Please send me details of Heathkit Hi-Fi.  
 Send me FREE CATALOGUE

NAME

ADDRESS

WWW-1B



DAYSTROM LTD, GLOUCESTER, GL2-6EE.  
 Tel: Glos 29451. Telex 43216.

WW-024 FOR FURTHER DETAILS

# audix PORTABLE D.J. CONSOLE



#### Specification

Power Output: 25-30 watts at 100V line.  
 Inputs: Two microphones 30-50  $\Omega$  balanced.  
 Auxiliary switched gram, tape, or medium impedance microphone.  
 Master Gain Control, Tape Record Socket,  
 Bass Tone Control: + 10 db - 12 db @ 100 cps.  
 Treble Tone Control: + 8.5 db - 10 db @ 10 Kc/s.  
 Frequency Response:  $\pm$  .5 db 25 c/s - 12 Kc/s.  
 Dimensions: Length: 3' 4". Depth: 1' 6". Height: 2' 6".  
 Height less legs: 1' 0".

Meets the ever growing demand for well presented music and speech at private and public functions—dances, receptions, parties etc. where there is no permanent sound installation. The Audio Portable D.J. Console incorporates the A.25 silicon transistorised power amplifier with three input channels each with separate volume control. The two Garrard SP.25 single play turntable units each have continuously variable fader controls. Monitor loudspeaker, socket for headset and dynamic cardioid microphone completes the equipment which is attractively housed in solid afromosia cabinet with detachable legs.

- HIGH QUALITY REPRODUCTION
- READILY PORTABLE
- QUICKLY SET UP
- SIMPLE TO OPERATE
- STYLISH PRESENTATION

Full information available on request—ask for details of Audio Sound Control Consoles, Integrated Mixer Amplifiers and Complete Sound Systems.

# audix SOUND SYSTEMS

STANSTED, ESSEX.

Telephone: 027-971 3132/3437

WW—027 FOR FURTHER DETAILS


# You're on the right track— with Goldring 800 magnetic cartridges

Goldring 800 magnetic cartridges track unerringly. Because that's the way we make them. They're designed to translate even the most delicate information stored in the groove back into an identical electrical signal. We call it the sound of true transduction.

Hear it for yourself. You'll know you're on the right track.

**Goldring 800/H**... the 800/H is designed for inexpensive changers to track between 2½–3½ grams and has a high output of at least 8mV. £10.13.6 tax paid.

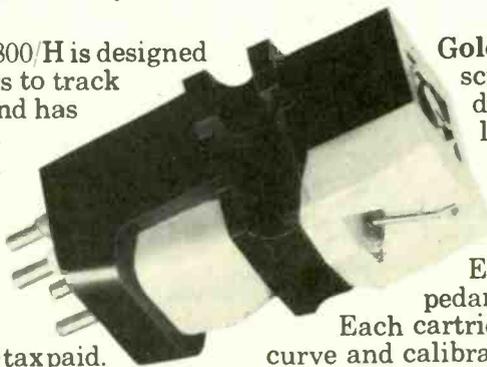**Goldring 800**... the 800 is designed for standard arms and changers where the requirements of high fidelity and robustness usually conflict. £13.0.0 tax paid.



**Goldring 800 E**... is designed for transcription arms and a micro-elliptical diamond is fitted to a finer cantilever, end damped against natural tube resonance £18.17.1 tax paid.

**Goldring 800 Super E**... the 800 Super E is for those to whom perfection is barely good enough. Extraordinarily low mechanical impedance for superb tracking capabilities. Each cartridge is supplied with its individual curve and calibration certificate. £26.0.0 tax paid.



Send for details and complete range of Goldring Hi-Fi equipment  
**Goldring Manufacturing Co. (Great Britain) Ltd.**  
 486-488 High Road, Leytonstone, London, E.11. Tel: C1-539 8343.


WW—028 FOR FURTHER DETAILS

People  
keep  
talking  
about...

Solid State  
Microcircuits  
Integrated circuits  
Semiconductors  
Integrated circuits  
Microcircuits  
Semiconductors  
Solid State  
etc etc etc



We  
talk  
valves!

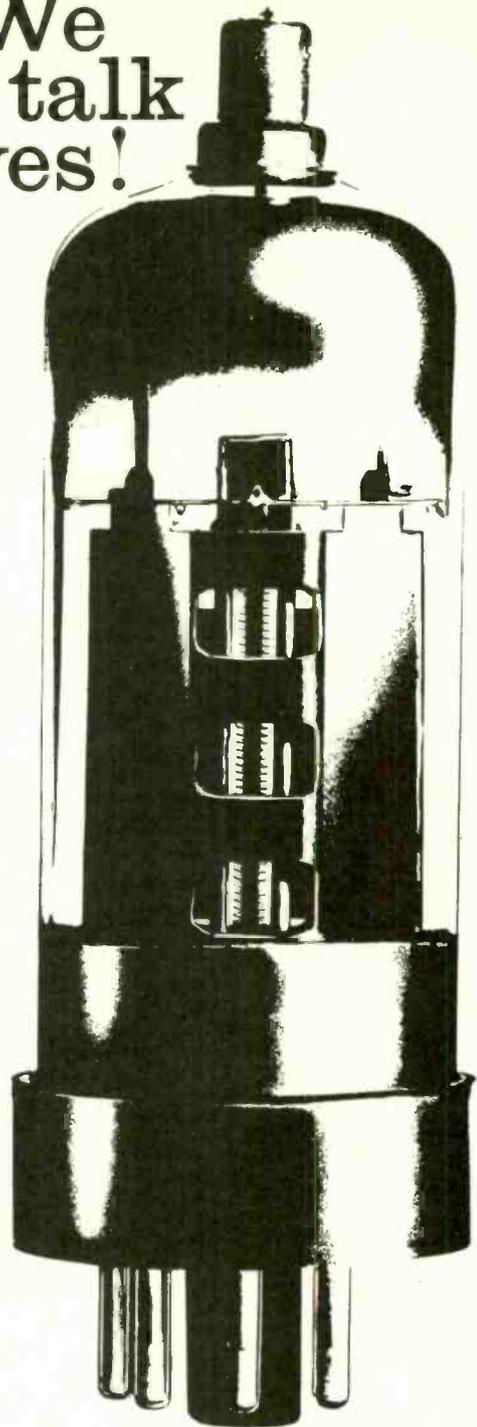


We can't, and don't,  
disregard current advancements  
in sophisticated electronics  
We can, and do,  
cater to an undiminishing requirement  
for replacement valves from all quarters of  
Industry, Education and Research.  
This requirement has been built up over  
many years past.  
So has Pinnacle

**Pinnacle**

**Pinnacle Electronics Limited**  
Achilles Street, New Cross, London, S.E.14.  
Phone: All departments 01-692 7285  
Direct orders: 01-692-7714

WW-029 FOR FURTHER DETAILS

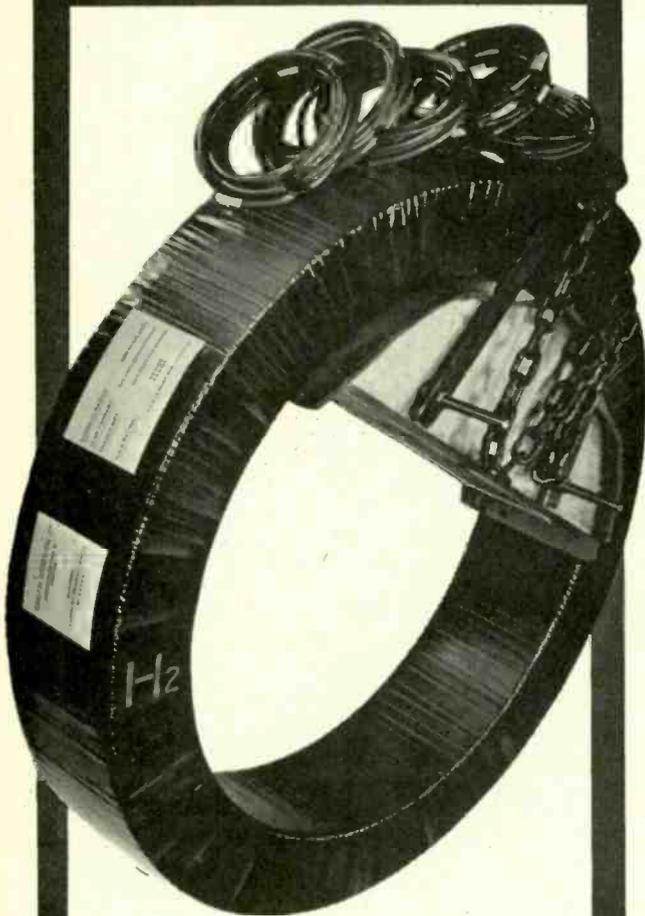**Telcon**  
soft magnetic  
materials give  
today's circuits  
*tomorrow's*  
performance



Telcon Mumetal used in a large bushing current transformer, manufactured by Smith Hobson Ltd., which was one of several for the Niagara Falls Generating Station.



Please send for further details of Telcon soft magnetic materials.

*look ahead with-*  
**T M TELCON**

TELCON METALS LTD., Manor Royal, Crawley, Sussex.  
Telephone: Crawley 28800 Member of the **BICC** Group of Companies.

WW-030 FOR FURTHER DETAILS

From laboratory to  
full industrial duties -  
**COVERED!**

## THE GENEVAC KINNEY RANGE

Exceptionally compact,  
oil sealed rotary piston high vacuum pumps  
providing pressures of 1 torr or below




### GKT, GKC SERIES - INDUSTRIAL TYPE

Four single-stage pumps with speeds up to 500 ft<sup>3</sup>/min. Special patented balancing techniques eliminate harmful vibration - so you needn't bolt them down if you don't want to. Which makes this series ideal for both static and mobile applications.


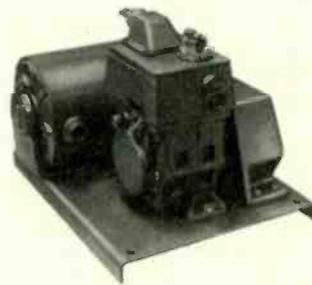
### GHS, GHD SERIES - DUAL PURPOSE

For laboratory or industrial use. Capable of achieving ultimate pressures down to  $5 \times 10^{-4}$  And giving a 50% increase in pumping speed over previous models.



### NRD - NRS SERIES - LABORATORY TYPE

Provide a high vacuum testing facility down to  $5 \times 10^{-4}$  ultimate pressures, plus the ability to remove water vapour and gases from test environments.

All pumps are vibration-free, with low noise levels and full gas ballast facilities. Cost is low, design is compact and construction robust. Efficiency rating is very high and reliability is absolute.

Write for the Genevac Kinney publications . . .

Vacuum Products Division,  
**GENERAL ENGINEERING CO. (RADCLIFFE) LTD.**  
Station Works, Bury Road, Radcliffe, Manchester.  
Telephone 061-723 3271/3041 Telex 66200 Generalrad Manchester.

WW-031 FOR FURTHER DETAILS


PYE SPANS THE WORLD



Pye Telecommunications is the world's largest exporter of radiotelephone equipment. Pye Radiotelephones are used all over the world to ensure *instant* contact. Pye research development and quality control really *do* keep in touch with tomorrow.

rely on

the vital contact

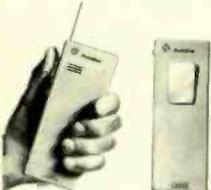

**Pye 'Pocketfone' Personal Radiotelephone**  
 New battery economy circuit - Extremely light-weight and compact - Reception free from noise and interference - Minimum of controls - Transmit button automatically extends antenna - Hearing aid socket - Easily accessible batteries.



**Pye 'Bantam' Portable VHF Radiotelephone**  
 Fully transistorised transmitter and receiver - Very high performance receiver - Crystal filter selectivity - 0.5W transmitter output - 250mW audio power - Long endurance with rechargeable or dry batteries - Can be used with external antenna to give greater range - Weatherproof.




**Pye VHF Radiotelephone Fixed Station**  
 Solid-state receiver and transmitter - 10-15W R.F. output - Field-effect transistors used in receiver - Suitable for all climates - Electronic squelch - Designed to meet all relevant specifications.



**Pye UHF Radiotelephone Fixed Station**  
 Solid state receiver and transmitter - 8-10W R.F. output - Very high R.F. selectivity using field-effect transistors - Very low noise factor - Electronic squelch - A. C. or 24V d.c. operation - Suitable for all climates - Designed to meet all relevant specifications.



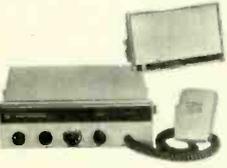**Pye 'Westminster' Remote Mounted Radiotelephone**  
 Completely solid state - 5-8W R.F. output - 1-10 channels with solid state switching - Illuminated channel indicator - Suitable for all climates - Meets all relevant specifications.



**Pye 'Westminster' Front Mounted Radiotelephone**  
 Completely solid state - 5-8W R.F. output - 1-10 channels with solid state switching - Suitable for all climates - Meets all relevant specifications.



**Pye Single-Sideband Radiotelephone**  
 125W (p.e.p.) R.F. output - Fully transistorised receiver - C.W. facilities provided - Sideband selection by crystal filter - Carrier insertion for a.m. compatibility - Fixed or mobile application - Advanced transmitter design.



**Pye 'Pioneer' Radiotelephone**  
 Fully transistorised - For use with automatic, CB manual, or magneto exchanges - Weatherproof cabinet - Unattended operation over long periods - Facility for fitting privacy equipment - Optional single antenna operation.



**Pye 5-Circuit UHF Radiotelephone**  
 Compact 5-circuit radio terminal - Fully - transistorised channelling equipment - Frequency-shift signalling - Continuous unattended operation in all parts of the world - Twelve standard plans for terminals and repeaters.

**PYE**  
 equipment gives you instant-contact with mobility

**PYE TELECOMMUNICATIONS LTD.** Cambridge England Telephone: Cambridge (0223) 61222 Telegrams: Pyetelecom Cambridge Telex: 81166

WW-032 FOR FURTHER DETAILS





NEW

# Litestat


## TEMPERATURE CONTROLLED SOLDERING INSTRUMENTS

- Control within  $\pm 2\frac{1}{2}^{\circ}\text{C}$
- Temperature infinitely adjustable while running
- Available for all voltages
- Built-in indicator lamp
- Cool, comfortable, unbreakable Nylon handle
- Range of bit sizes, Copper or Philips iron-coated


Please ask for leaflet LT.5
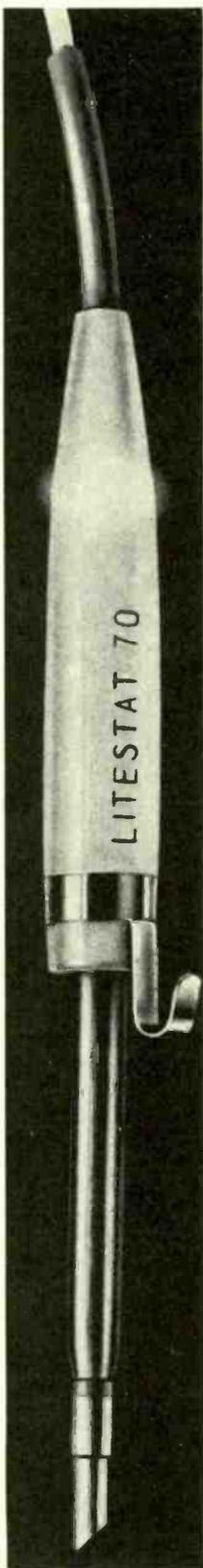
## LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road, Croydon, CR9 2LL  
Telephone: 01-688 8589 and 4559



# CHASSIS and CASES

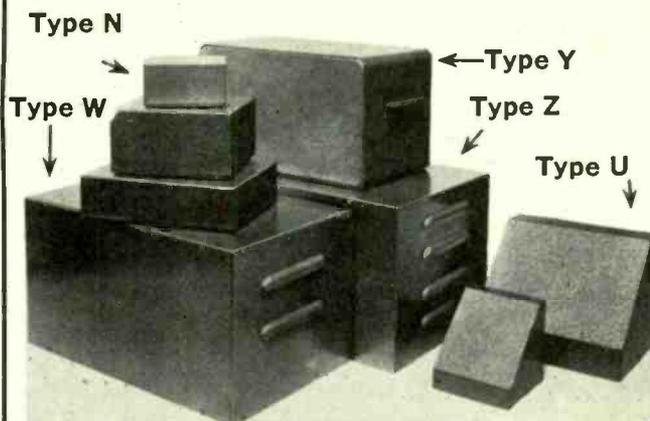

## CASES

ALUMINIUM, SILVER HAMMERED FINISH

Type	Size	Price	Type	Size	Price
N	8 x 6 x 2*	18/-	W	12 x 7 x 7*	37/6
N	6 x 6 x 3	17/6	W	15 x 9 x 8	48/6
N	4 x 4 x 2	11/-	Y	8 x 6 x 6	29/-
U	4 x 4 x 4	11/-	Y	12 x 7 x 7	45/-
U	5½ x 4½ x 4½	17/-	Y	13 x 7 x 9	50/6
U	8 x 6 x 6	23/-	Y	15 x 9 x 7	53/6
U	9½ x 7½ x 3½	24/-	Z	17 x 10 x 9	72/6
U	15 x 9 x 9	49/-	Z	19 x 10 x 8½	78/-
W	8 x 6 x 6	23/-			

\*Height  
Plus post and packing.

Type N has a removable bottom, Type U removable bottom or back, Type W removable front, Type Y all-screwed construction, Type Z removable back and front.

## BLANK CHASSIS

FOUR-SIDED 16 SWG ALUMINIUM

Size	Price	Base	Size	Price	Base
6 x 4 x 2"	6/3	2/11	10 x 8 x 2½"	12/-	5/6
7 x 4 x 1½"	6/-	3/2	12 x 7 x 2½"	12/-	5/11
7 x 5 x 2"	7/6	3/5	12 x 9 x 2½"	13/9	7/-
8 x 4 x 2"	7/-	3/4	13 x 8 x 2½"	13/9	6/11
8½ x 5½ x 2"	8/-	3/9	14 x 7 x 3"	14/6	6/6
9 x 7 x 2"	9/3	4/10	14 x 10 x 2½"	16/-	8/7
10 x 4 x 2½"	9/-	3/9	15 x 10 x 2½"	16/6	9/1
12 x 4 x 2½"	10/-	4/3	17 x 10 x 3"	19/6	10/1
12 x 5 x 3"	12/-	4/9			

## TO FIT OUR CASES

Size	Price	Base	Size	Price	Base
7 x 5½ x 1½"	7/-	3/9	12 x 6½ x 2"	10/9	5/11
7 x 5½ x 2"	7/9	3/9	14 x 8½ x 2"	13/6	7/11
11 x 6½ x 1½"	10/-	5/6	15½ x 9½ x 2½"	17/-	9/6
11 x 6½ x 2"	10/-	5/6	17½ x 9½ x 2½"	18/6	10/6

## WITH BASES

Size	Price	Size	Price
5 x 4 x 2½"	9/3	3½ x 3½ x 2½"	6/6
4 x 2½ x 1½"	6/-	3 x 2 x 1"	5/6
3½ x 3½ x 2½"	7/3	6½ x 2½ x 1½" (18SWG)	8/3

Plus post & packing.

PANELS: Any size up to 3ft. at 6/- sq. ft. 16 s.w.g. (18 s.w.g. 5/3). Plus post and packing.

## H. L. SMITH & CO. LTD.

Electronic Components • Audio Equipment

287/289 EDGWARE ROAD, LONDON, W.2  
Tel: 01-723 5891

We shall be pleased to quote for all your component requirements.

# World Travellers pose for their passports

The Teonex family is big - 2,000 odd members, exclusive of semi-conductor relatives! Like every family, they come in many shapes and sizes. Slim or fat, tall or squat, bigger or smaller, and in many ages: very young to very old.


But there are two common characteristics. They are very reliable and they all have to travel.

Nearly 60 countries now welcome Teonex, on Government and private contract. The family album is as comprehensive as you can get and most members are available from stock.

For technical specifications and price lists please write to Teonex Limited  
2a Westbourne Grove Mews · London W.11 · England  
Cables: Tosupply London W.11

# TEONEX

electronic  
valves &  
semi-conductors

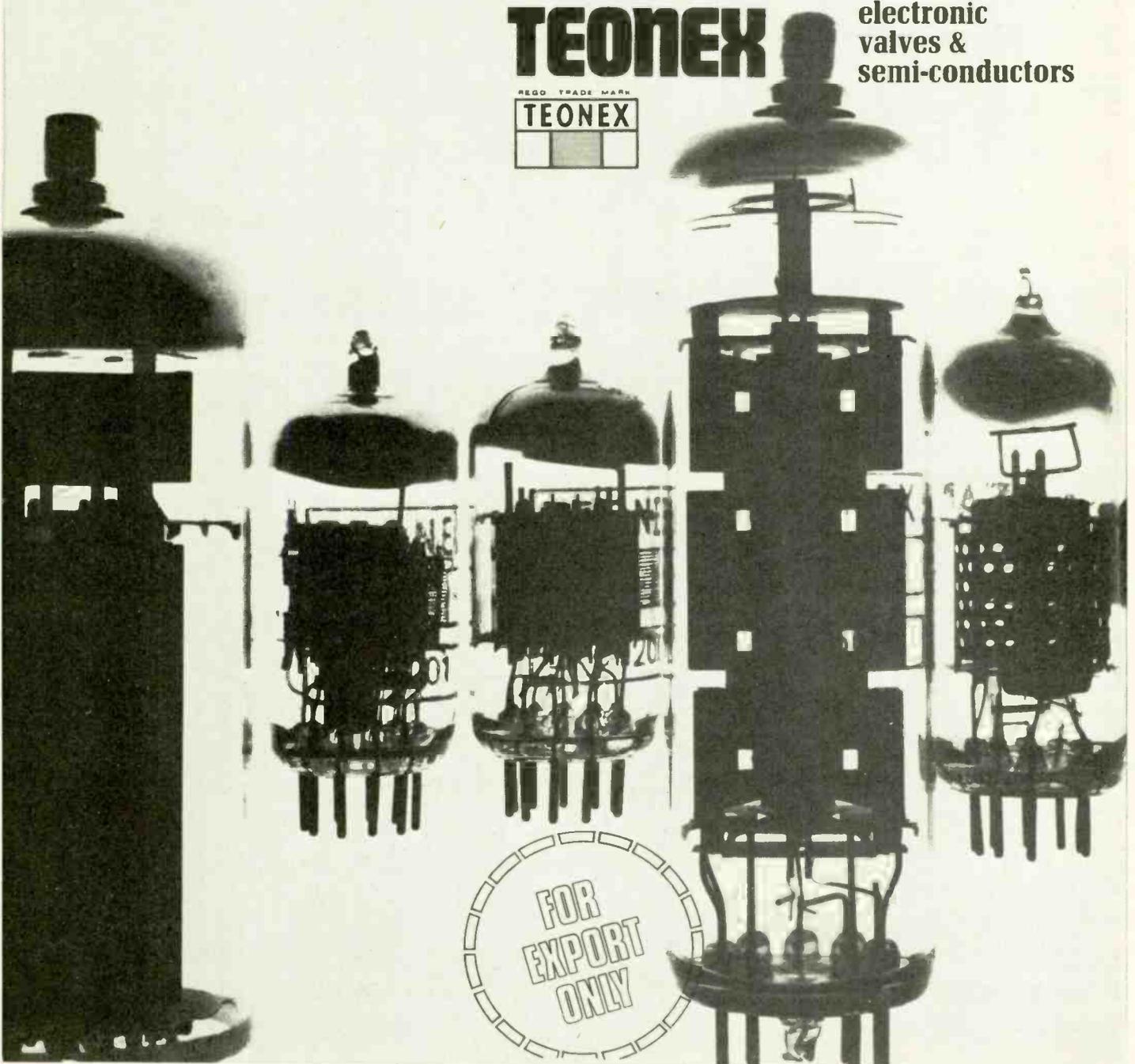


WW—035 FOR FURTHER DETAILS

peak sound



englefield

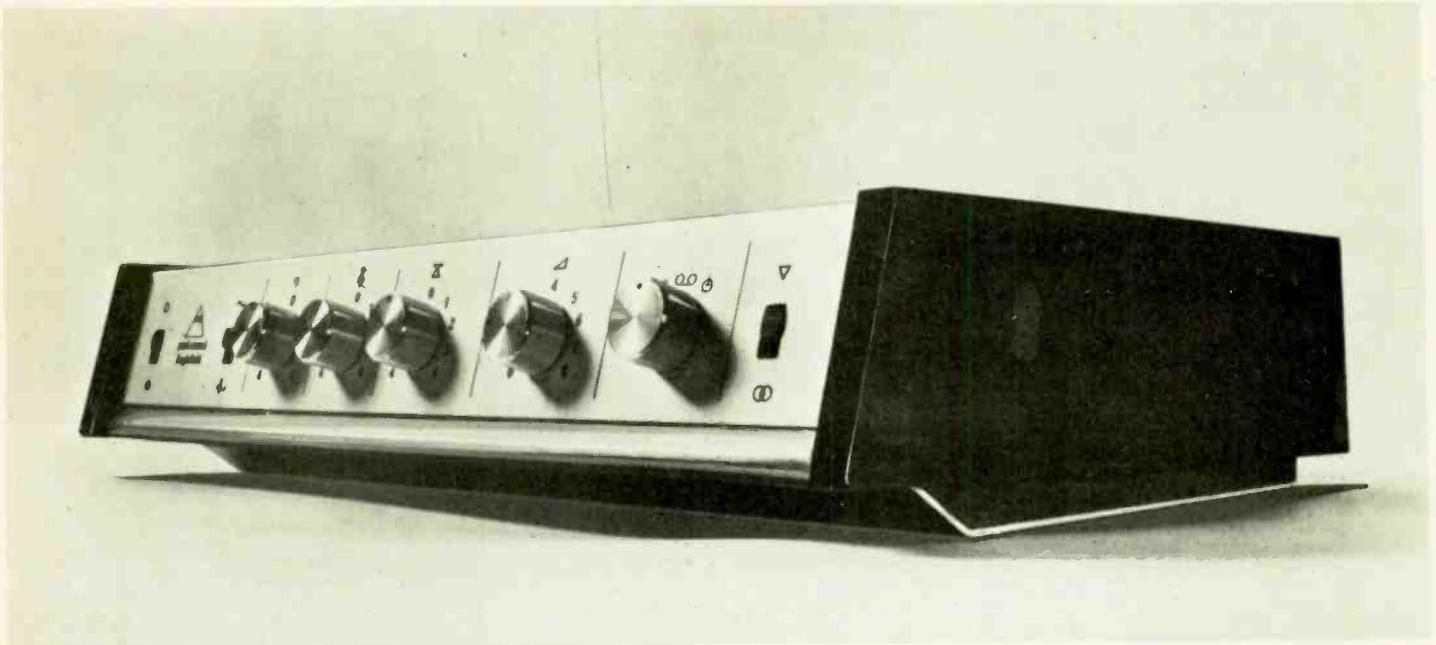

NEW DESIGN FROM PEAK SOUND

Proved-performance high fidelity with specification guarantee

The Peak Sound Englefield is a new system which assembles from laboratory designed modules to provide a cost-performance ratio which has never been bettered in high fidelity. Here is top-flight circuitry housed in a cabinet of elegantly original design which is both beautiful and completely practical back and front. By assembling these Peak Sound units, you can own one of the best high fidelity instruments you have ever heard or seen and all for a cost of about £38. The assembly is supplied complete down to the necessary connecting wires supplied colour coded, cut to length and stripped at the ends for soldering. You can use the Englefield Cabinet design to house either the 12 + 12 system as published in *Practical Wireless*, or the 25 + 25 watt system as approved for the *Hi-Fi News* Twin Twenty by Reg Williamson. Go to your stockist and ask to see and hear Peak Sound equipment now.

Matching F.M. Tuners will be available very shortly.

and this is the Peak Sound Specification Guarantee

Peak Sound guarantee that their equipment meets all specifications as published by them and that these are written in the same terms as are used in equipment reviews appearing in this and other leading high fidelity journals. Audio output powers are quoted at continuous sine wave power in terms of Root Mean Square values (R.M.S.) into stated loads at stated frequencies.

THE SPECIFICATION

Using two Peak Sound PA.12-15's, driven simultaneously at 1 KHz from 240 V. mains supply.  
 Output per channel: 11 watts into 15Ω; 14 watts into 8Ω. (see spec. guarantee).  
 Frequency bandwidth: 10Hz to 45 KHz for 1dB at 1 watt.  
 Total Harmonic Distortion at 1 KHz at 10 watt into 15Ω—0.1%.  
 Input sensitivities: Mag. PU.3.5 mV imp. R.I.A.A. equalized into 68 KΩ; Tape, 100 mV linear into 100 KΩ; Radio, 100 mV linear into 100 KΩ.  
 Overload factor: 29 dB on all input channels.  
 Signal/noise ratio: -65 dB on all inputs. Vol. control max.  
 Controls: Volume, Treble, Bass, Low-pass Filter. Mono/Stereo: On/off; Balance.  
 Using two PA.25-15 amplifiers, output is then 25 watts into 15Ω or 8Ω per channel at 1 KHz.  
 Power bandwidth for -1 dB at 20 watts R.M.S. into 15Ω at less than 0.25% distortion is 20 Hz to 20 KHz.

THE MODULES

Englefield Amplifier Cabinet with front panel, knobs, sockets, cut and stripped wire, fuses, edge connectors, etc. ....	£6 0 0
Two PA. 12-15 power amp. built modules .....	£11 19 0
SCU/400 Pre-amp/Control module, built .....	£15 15 0
PS/45 Power Supply kit .....	£4 10 0
	£38 4 0

Using two PA.25-15 modules at £11/15/- each and PS/68S Stabilized Power Supply Unit at £13/10/-, total price for complete system comes to £58 15 0



Go to your Stockist. Peak Sound products are already available from dealers in many parts. If your own local stockist is not yet ready with the Peak Sound items you require, please send direct together with your supplier's name and address and your requirements will be dealt with without delay.

TRADE ENQUIRIES INVITED.  
**PEAK SOUND (HARROW) LTD.,**  
 32 St. Jude's Road, Englefield  
 Green, Egham, Surrey

Telephone: EGHAM 5316

To Peak Sound, 32 St. Jude's Rd., Englefield Green, Egham, Surrey.

Details of Englefield systems, please and .....

Name .....

Address .....

WW1

Write your stockists name and address in margin below and cut out with coupon if necessary.

WW—036 FOR FURTHER DETAILS

# Some notes on Bridge Measurement by WAYNE KERR

## Number 6

### Radio-Frequency Bridges


The first five issues in this series of notes have described some of the basic principles of low frequency bridges and also their application to the measurement of components using two, three and four terminal techniques.

Transformer Ratio Arm bridges can be designed to operate at radio frequencies up to about 250MHz where other forms of bridge based on transmission lines become practicable.

The design of a bridge required to operate at high frequencies demands careful attention to every aspect of the layout, and in particular to the series inductance introduced by connections between component parts of the bridge. Short lengths of conductor which are insignificant at low frequencies can resonate and introduce immense errors as the frequency is increased.

However, the neutral connection which is available from transformer ratio arms can be used to effectively cancel the series inductance of conductors in the following manner. If two strip connections are made to, say, a bridge standard, these are placed side by side and mounted above a plate connected to neutral. The loop current flowing in the strips will induce, in the plate, an equal and opposite current which cancels the magnetic field, thus reducing the loop inductance.

Figure 1 illustrates a practical circuit for a bridge capable of operating at frequencies up to 100MHz.

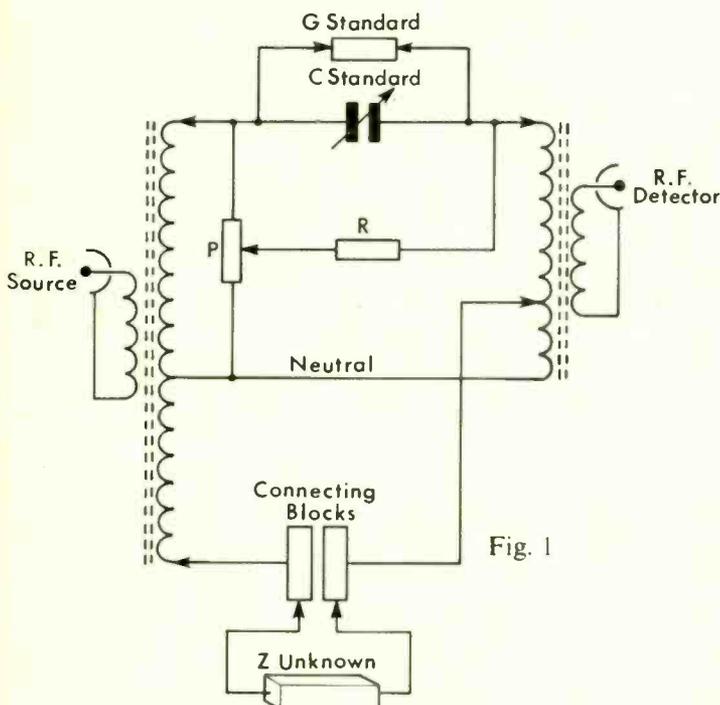


The transformers are formed by winding thin silver tapes on to ferrite or ferrous dust ring cores which are mounted inside individual screening cans.

The unknown impedance is connected to the blocks shown in the diagram which represent a shunt capacitance on the unknown side of the bridge. This capacitance is balanced by the standard variable capacitor and its value is so chosen that the capacitor is half engaged when the dials are at zero. An unknown reactance can therefore be balanced either by increasing the setting of the capacitor or decreasing it in the case of an inductive reactance. This feature is of particular value when transmission lines or aerial arrays are being evaluated.

Drums of low inductance resistors forming fixed conductance standards are arranged to engage with spring contacts. A variable conductance for interpolation is formed by means of a resistor R which is fed with a voltage derived from a resistive potential divider P.

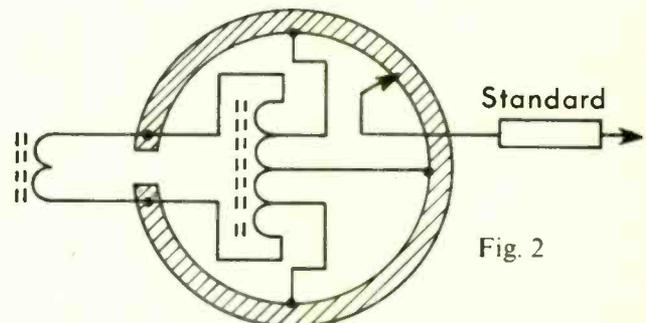Recently, a continuously variable potential divider has been developed which enables voltage division to be effected with great precision. This device is based on the magnetic field in a single turn loop and is illustrated in Figure 2.



The loop is connected to a winding which forms part of the left hand transformer shown in Figure 1. An auto-transformer is connected across the loop and several taps are connected to give a predetermined voltage distribution round the loop. Separate loops can be used to drive resistive and reactive standards and one interesting feature of the arrangement is its ability to create a continuously variable inductance standard. In this case an air cored toroid can be employed whose external field is so small that the presence of metal objects near the coil has no measurable effect.

Radio-frequency bridge measurements require that considerable care should be taken in setting-up the apparatus. Any leakage of power from the source to the detector which by-passes the bridge network will give errors. Furthermore, if an aerial assembly is being measured, radiation from the aerial may be picked up by a badly screened detector and subsequently cancelled by a voltage of opposite phase in the operation of the bridge which will now balance at a false point on its scales. However, with a well screened detector and with soundly constructed connecting cables coupling the source and detector to the bridge, highly accurate measurements can be performed on both active and passive assemblies.

THE WAYNE KERR COMPANY LIMITED  
NEW MALDEN · SURREY · ENGLAND

Telephone: 01-942 2202  
Cables: Waynkerr Malden  
Telex: 262333

WW-037 FOR FURTHER DETAILS

# NKT

FOR

## BS 9000

### ASSURED RELIABILITY

**BRITISH STANDARDS INSTITUTION**

INCORPORATED BY ROYAL CHARTER  
BRITISH STANDARDS HOUSE  
2 PARK STREET, LONDON W1Y 4AA

Newmarket Transistors Ltd.,  
Ering Road,  
Newmarket,  
Suffolk.

For the attention of Mr. R.G. MacLagan,  
Managing Director.

Dear Sirs,

British Standards Institution Approval of  
Manufacturer under BS. 9000

I have to inform you that the arrangements at your Works at

Ering Road,  
Newmarket,  
Suffolk.

are approved by the British Standards Institution as satisfying the requirements  
of BS. 9000.

The inspection arrangements are to be under the control of your approved  
Chief Inspector, Mr. R.W. Rushmore  
and your approved Deputy Chief Inspector, Mr. H.R. Harvey.

This approval covers the following:

Manufacture of electronic parts of assessed quality to the  
BS. 9000 series of specifications as follows:-

Generic Specification BS. 6300  
(1) Transistors, excluding FETs

The British Standards Institution Approval Number allocated to your Works  
identified above is:-

BS. 9000 Approval 1014/M

and this should be quoted on all relevant documents.

The BS. 9000 Manufacturer's Factory Identification Code letters allocated  
to your Works identified above are:-

00

You are hereby authorised to use only the following reference to approval  
on letter headings, advice notes invoices etc.


BS. 9000 Approval 1014/M

This approval, which is subject to the conditions of BS. 9000, may be suspended  
or withdrawn by British Standards Institution in accordance with those conditions  
and is subject to supervision by the Supervising Inspectorate of the Institution,  
which until further notice will be:-

Electrical Quality Assurance Directorate,  
Components Department,  
Ministry of Technology,  
Aquila,  
Bromley,  
Kent.

Will you please acknowledge receipt of this letter (with a copy to the  
Supervising Inspectorate) on the enclosed form.

Yours faithfully,

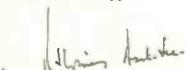

C.G. Usher,  
Senior Administrative Officer.


U.K. Member of International Organization for Standardization  
International Electrotechnical Commission

G. H. BEEBY Chairman of Executive Board

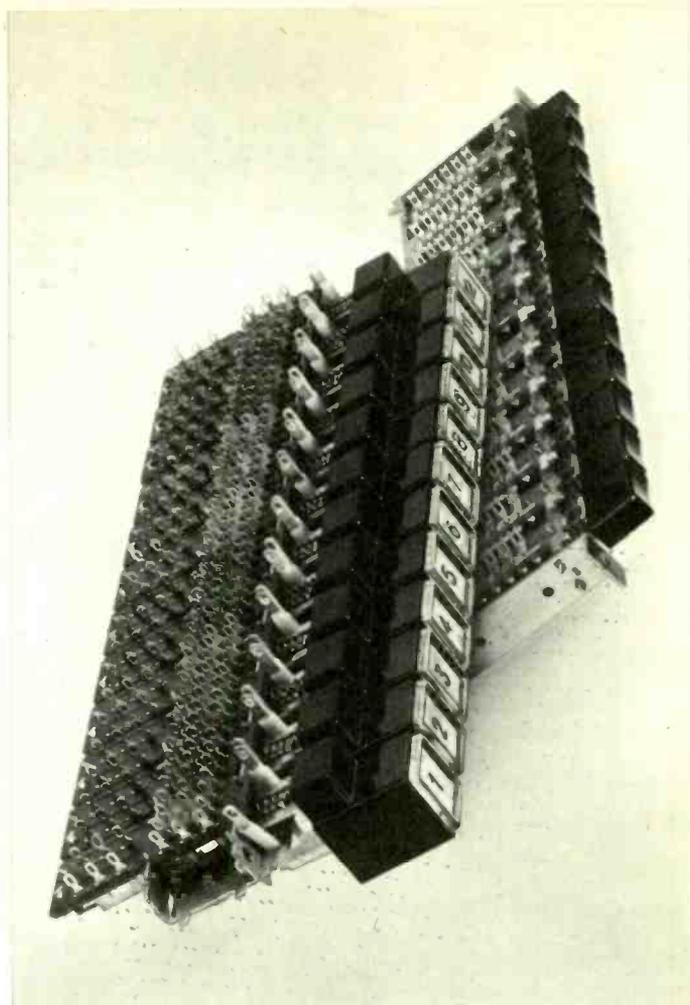H. A. B. SINNEY, C.B., Director General

Telephone: 01-479 9000  
Telex: 264513 (Head Office)  
21228 (Sales & Accounts)  
Teletype: STANDARDS LONDON W1

Your reference: OC/33/1 - 1014/M  
Our reference: 15th September, 1969  
Date



# Push Button Switches

Switches with a diverse range of contact configurations. Any combination of complex latching and interlocking function in single, and between twin bank assemblies. Available with illuminated buttons and choice of five colours, individual legends can be engraved. These, with rotary, slide and lever switches are available from IMPECTRON LIMITED, write or phone for illustrated literature to 23-31, King Street, London, W.3., Telephone: 01-992 5388.



# WORLD FAMOUS **I.M.O.** (ELECTRONICS) LTD. VARIABLE VOLTAGE CONTROLS



## VARIABLE TRANSFORMERS

- ★ Output 0-260V
- ★ Input 230V 50/60CPS
- ★ Shrouded for Bench or Panel mounting

Inset shows latest pattern Brush gear ensuring smooth continuous adjustment.



**£5.10.0** 1 amp      2.5 amp £6.15.0      8 amp £14.10.0      12 amp £21.0.0  
 5 amp £9.15.0      10 amp £18.10.0      20 amp £37.0.0

### CONSTANT VOLTAGE TRANSFORMER.



Maintain spot-on test gear readings with Automatic Mains stabilizer.

Specification:

- ★ Output 240V
- ★ Accuracy ± 1%
- ★ Input 190-260V
- ★ Capacity 250 watts
- ★ Corrected wave

**£12.10.0** C & P 20/-

### 20 AMP LT SUPPLY UNIT



- ★ Input 240V
- ★ Output 20 amps at 24V and 12V fully adjustable
- ★ Size 16" x 12" x 20" high
- ★ Weight 50 lbs.

**£35.0.0**

### SOLID STATE VARIABLE VOLTAGE CONTROL



- ★ Output 25-240V
- ★ Input 240V 50 CPS
- ★ 5 amp & 10 amp models
- ★ Completely sealed

5 amp model **£8.7.6**  
 10 amp model **£13.15.0**

### UNIVERSAL MICRO SWITCH




MLC-3  
 5 amp C/O  
**1/6**  
 each in quantity

10 amp C/O PUSH-BUTTON MICRO-SWITCH panel mounting. Buttons in Red, Green, White & Black Type SS-1. **4/8** each per 1,000

**IMMEDIATE DESPATCH**  
 FULL SPARES AND SERVICE AVAILABLE
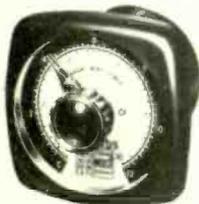
## PROCESS TIMERS

- ★ SYNCHRONOUS MOTOR & CLUTCH
- ★ 10 MILLION OPERATIONS
- ★ Instantaneous & Timed out 3 AMP contacts
- ★ Repeat Accuracy ± 1/2%
- ★ Dial ranges 0-10 secs up to 0-28 hrs. May also be used as impulse start



**SYS TIMER**

**£11**  
 dependent on quantity

- ★ FULLY ADJUSTABLE UP TO 200 SECONDS. FITTED WITH 6AMP S.P.D.T. SWITCH.
- ★ ONE MODEL PROVIDES DELAY AFTER ENERGISE OR DELAY AFTER DE-ENERGISE.



**PNEUMATIC TIMER TYPE ATS**

**£6**  
 approx. dependent on quantity

- ★ SYNCHRONOUS MOTOR & CLUTCH Matchbox size frontal area Automatic re-set
- ★ PLUG-IN OCTAL BASE
- ★ INSTANTANEOUS AND TIMED OUT 2 AMP CONTACTS
- ★ RANGES: 0-10 SECS TO 0-36 MINS



**STP TIMER**

**£5**  
 dependent on quantity

PROXIMITY SWITCHES, LIMIT SWITCHES AND LIQUID LEVEL CONTROLS  
 MANUFACTURERS AND IMPORTERS FOR MINISTRY OF DEFENCE, G.P.O.

## OMRON PRECISION CONTROLS

DIVISION OF IMO PRECISION CONTROLS LTD.

(Dept. WWX) 313 EDGWARE ROAD, LONDON, W2. TEL: 01-723 2231

# BOOKS BY G.A. BRIGGS

OVER A QUARTER OF A MILLION COPIES SOLD SINCE 1948

**AERIAL HANDBOOK** (second edition)  
176 pages, 144 illustrations.  
PRICE (semi-stiff cover) 15/- (16/6 post free).  
Cloth bound 22/6 (24/- post free).



**CABINET HANDBOOK**  
112 pages, 90 illustrations. PRICE 7/6 (8/6  
post free.) Semi-stiff cover. Cloth bound 15/- (16/6  
post free).



**AUDIO BIOGRAPHIES**  
344 pages, 64 contributions from pioneers and  
leaders in Audio. Cloth bound.  
PRICE 25/- (27/- post free).



**MUSICAL INSTRUMENTS AND AUDIO**  
240 pages, 212 illustrations. Cloth bound.  
PRICE 32/6 (34/6 post free).



**LOUDSPEAKERS**  
Fifth edition—336 pages, 230 illustrations.  
cloth bound.  
PRICE 30/- (32/6 post free).



**A TO Z IN AUDIO**  
224 pages, 160 illustrations. Cloth bound.  
PRICE 15/6 (17/- post free).



**PIANOS, PIANISTS AND SONICS**  
190 pages, 102 illustrations. Cloth bound.  
PRICE 18/6 (20/- post free).



**ABOUT YOUR HEARING**  
132 pages, 112 illustrations.  
PRICE (semi-stiff cover) 15/6 (16/6 post free).  
Cloth bound 22/6 (24/- post free).



## READERS OPINIONS

I have recently been going through eight of your books and they have been a feast of information. I have been like a dog with eight tasty dishes, not knowing which one to tackle first but nipping about and sampling each one.

Somerset, Sept., 1969

Having read the majority of your 'Bibles on Hi Fi,' of such a remarkably 'hi' standard, I eagerly await a copy of your Cabinet Handbook.

London N22, November, 1969

Please send orders and enquiries to:

**RANK WHARFEDALE BOOK DEPT. B.W.S.**  
**13 WELLS ROAD ILKLEY YORKS**

Telephone: ILKLEY 4246

Published by  
RANK WHARFEDALE LIMITED IDLE BRADFORD YORKSHIRE

WW-041 FOR FURTHER DETAILS

# YOU WANT PARTS URGENTLY

—almost  
immediately!

### So what do you do?

You reach for the 'phone and dial ONO 239 8072, if it is anything made by the United-Carr Group. You will be surprised how soon you'll get what you want.

### Your immediate needs are our business

We exist to supply the small user quickly with *standard* parts made by these Companies and carry large stocks of their fasteners and clips and a wide range of Radio, Electronic and Electrical components. We're geared to speedy handling and dispatch.

### But you will need our latest catalogue

For quick and accurate ordering you should keep our comprehensive catalogue by you. This useful reference book gives full details of the wide range of parts we stock—nearly everything of the kind that you are likely to require. Even though not ordering anything immediately, you should write now for this useful publication and so be ready to handle rush jobs whenever they arise.


United-Carr Supplies Ltd.,  
Frederick Road, Stapleford, Nottingham.  
Sandiacre 8072 STD ONO 239 8072



UNITED-CARR  
SUPPLIES

UNITED-CARR GROUP

WW-042 FOR FURTHER DETAILS

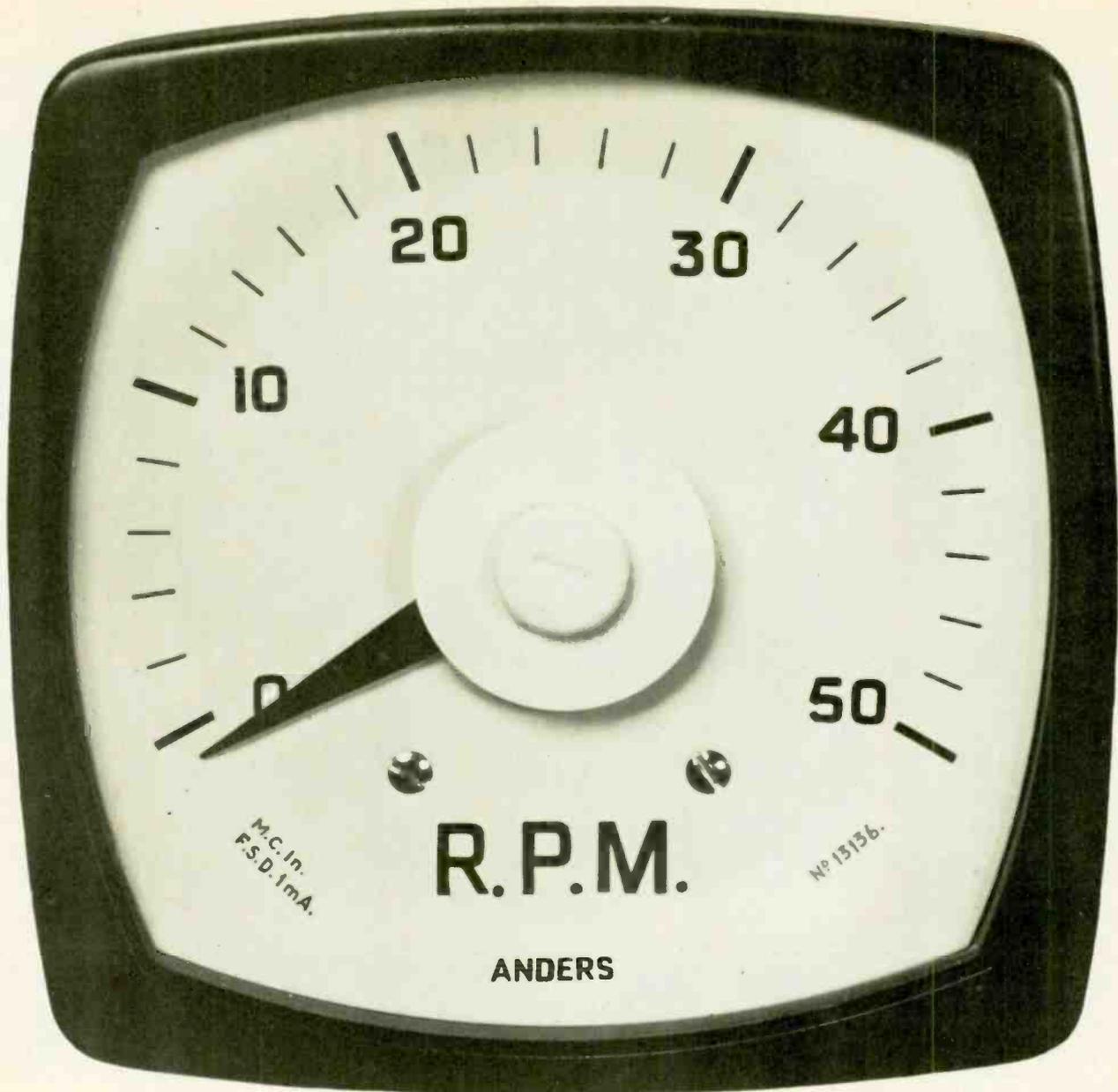

# let's face it

Not everybody's dial is all it should be, so we at Anders specialise in changing our customers' faces to order. Our experienced team of Dial Printers is ready to perform the most complex Face Change with promptness and efficiency. As well as holding the largest stock of off-the-

shelf meters and associated accessories in the United Kingdom, Anders offer a really fast service for supplying non-standard range instruments with special readings. Let's face it, if you have problems with your dial it pays to let Anders face it.

**Anders means meters**


## **ANDERS ELECTRONICS LIMITED**

48/56 Bayham Place, Bayham Street, London, N.W.1  
Telephone 01-387 9092.

Manufacturers and distributors of Electrical Measuring Instruments and Electronic Equipment. Sole U.K. distributors of FRAHM Resonant Reed Frequency meters and Tachometers.

WW-043 FOR FURTHER DETAILS

# EAGLE SERVICE & TEST EQUIPMENT

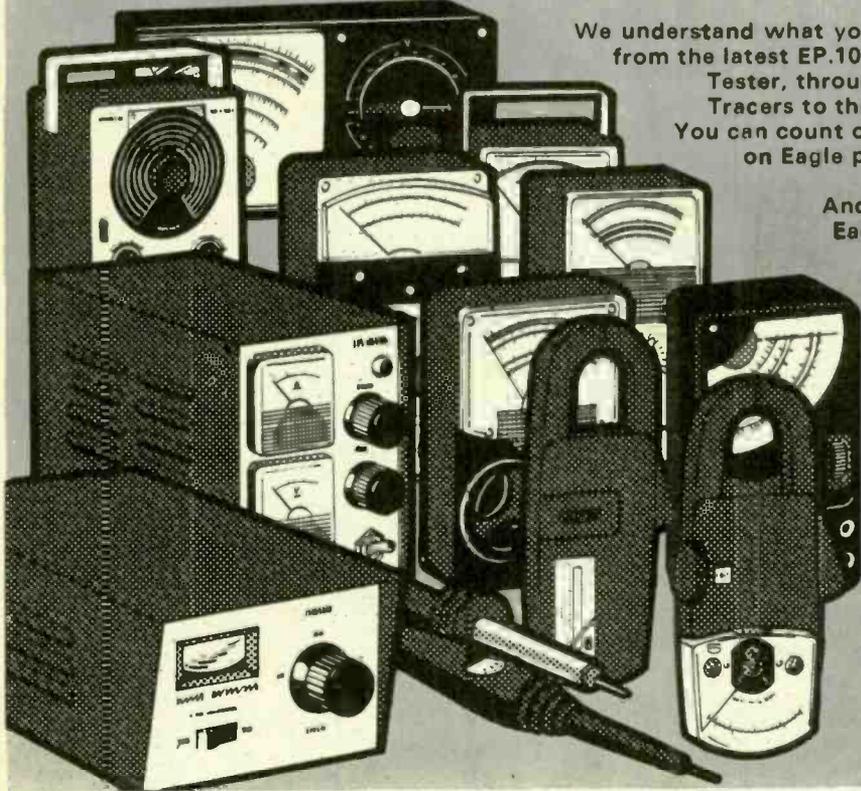

We understand what you need and we make sure that you get it — from the latest EP.100LN Band Suspension Multimeter/Transistor Tester, through Signal Generators, KV Probes and Circuit Tracers to the KEW.7 Pocket-Size Tester — Eagle have it. You can count on Eagle quality. What's more, you can count on Eagle prices. And above all — you can count on the quickest possible delivery!

And another attractive thing about the range of Eagle Products is the rate at which fast-selling new items are added! See our new catalogue, which proves the point! Send the coupon to the Sole Distributors of Eagle Products — B. Adler and Sons (Radio) Limited, Coptic Street, London, W.C.1 or quicker still, dial 01-636 9606, ask for Carol Hill, she'll send you one today!



CATALOGUE PLEASE - BY RETURN OF POST

NAME \_\_\_\_\_

COMPANY \_\_\_\_\_

ADDRESS \_\_\_\_\_

30

WW-044 FOR FURTHER DETAILS

## M. R. SUPPLIES (London) LTD., (Established 1935)

Universally recognised as suppliers of UP-TO-DATE MATERIAL, which does the job properly. Instant delivery. Satisfaction assured. Prices nett.

**ROOM THERMOSTATS.** Danfoss wall-mounted Thermostats, 40 deg. F.-80 deg. F., 380 v. A.C., 4 amps.; 240 v. A.C., 6 amps. Our nett price £1/12/6 (des. 2/-).

**MINIATURE RUNNING TIME METERS (Sangamo).** We have great demands for this remarkable unit and now can supply immediately from stock, 200/250 v. 50 c. synchronous. Counting up to 9,999 hours, with 1/10th indicator. Only 1½ ins. square, with cyclometer dial, depth 2 ins. Many industrial and domestic applications to indicate the running time of any electrical apparatus, easy to install, 63/- (des. 1/6).

**SYNCHRONOUS TIME SWITCHES.** (Another one of our popular specialities) 200/240 v. 50 c., for accurate pre-set switching operations. Sangamo 8.254, providing up to 3 on-off operations per 24 hours at any chosen times, with day-omitting device (use optional). Capacity 20-amps. Compactly housed 4 in. dia., 3½ in. deep. £6/4/6 (des. 4/6).

**ELECTRIC FANS (Papet),** for extracting or blowing. The most exceptional offer we have yet made. 200/250 v. A.C. Induction motor—silent running. 2,800 r.p.m. duty 100 C.F.M. Only 4½ in. square and 2 in. deep. Ideal for domestic or industrial use. Easy mounting, £3/5/- (des. 3/6).

**SMALL GEARED MOTORS.** In addition to our well-known range (List G.M.169), we offer small open type S.P. Units 200/250 v. A.C., 1, 6, 12, 24, 60 r.p.m., approx. 5 in. long, with 1 in. shaft projection each side and enclosed gearbox. Suitable for display work and many industrial uses. Only 75/- (des. 5/-).

**MINIATURE COOLING FANS.** 200/250 v. A.C. With open type induction motor (no interference). Overall 4 in. x 3½ in. x 2½ in. Fitted 6-bladed metal impeller. Ideal for projection lamp cooling, light duty extractors, etc., still only 31/6 (des. 5/-).

**AIR BLOWERS.** Highly efficient units fitted induction totally enclosed motor 230/260 v. 50 c. 1 ph. Model SD.28, 60 CFM (free air) to 11.5 CFM at 1.5 WG (size approx.) 6 x 6 x 7 in. Outlets 2½ in. square. £8/10/- (des. 5/-). Model SD27, 120 CFM (free air) to 40 CFM at 1.2 WG, 8 x 7 x 9 in. outlet 2½ in. sq., £11/15/6 (des. 5/-). Model SD28, 260 CFM (free air) to 127 CFM at 1.5 WG, 11 x 8 x 9 in., outlet 3 in. sq., £13/17/6 (des. U.K. 7/6).

**SYNCHRONOUS ELECTRIC CLOCK MOVEMENTS** (as mentioned and recommended in many national journals). 200/250 v. 50 c. Self-starting. Fitted spindles for hours, minutes and central sweep second hands. Central one-hole fixing. Dia. 2½ in. Depth behind dial only 1 in. With back dust cover, 39/6 (des. 2/-). Set of three brass hands in good plain style. For 5/7 in. dia. 2/6 For 8/10 dia. 3/6 set.

**SYNCHRONOUS TIMER MOTORS (Sangamo).** 200/250 v. 50 c/s. Self-starting 2 in. dia. x 1½ in. deep. Choice of following speeds: 1 r.p.m., 12 r.p.h., 1 r.p.h., 1 rev. 12 hours, 1 rev. per day. Any one 42/- (des. 3/-). Also high-torque model (G.E.C.), 2½ in. x 2 in. x 1½ in. 6 r.p.m., 57/6 (des. 2/-).

**SMITHS TIMER MOTORS.** Synchronous, self-starting 200/250 volts, 1 ph., 50 c. Clockwise. 4 r.p.m. only. Only 25/- (des. 2/-).

**MINIATURE D.C. MOTORS.** 6/12 volts D.C. Ideal model makers. 4,000/9,000 r.p.m. no load. 1½ in. x 1½ in. diameter. Flange fixing. Only 5/- (des. 1/6).

**EXTRACTOR FANS.** Ring mounted all metal construction. T/E induction motor, silent operation. 8 in. blade, 10 in. max. dia., 400 CFM. £8/10/0 (des. 5/-) Same model 10 in. blade, 12 in. max. dia., 500 CFM. £8/18/0 (des. 6/-).

**IMMEDIATE DELIVERY** of Stuart Centrifugal Pumps, including stainless steel (most models).

**OFFICIAL STOCKIST:** "PARVALUX" Electric Motors (List G.M. 169)

M. R. SUPPLIES (LONDON) LTD., 68 New Oxford Street, London, W.C.1  
(Telephone: 01-636 2958)

## Valradio DC to AC TRANSVERTORS (transistorised DC Invertors/Convertors)

Carry out your field tests using standard AC equipment.

A VALRADIO TRANSVERTOR will enable you to use all types of test instruments in the field or in motor vehicles.

Standard models are available for loads of 20W to 1000W for battery inputs of 12V & 24V and equally important to you most types are available from stock.

Prices range from £5 to £170.

The range is covered by three basic groups, having distinct characteristics.

T series—Square wave, frequency tolerance ± 3Hz

Q series—Square wave, frequency tolerance ± 1Hz

S series—Sine wave, frequency tolerance ± 1Hz

Typical model B12/200S input 12V output 115-230V 200W.


Price £67-12-0



Type B12/200S

Send for full information and technical details:  
VALRADIO LTD., Dept. W.C.4,  
Browell's Lane, Feltham, Middlesex, England. Tel.: 01-890 4242

WW-045 FOR FURTHER DETAILS

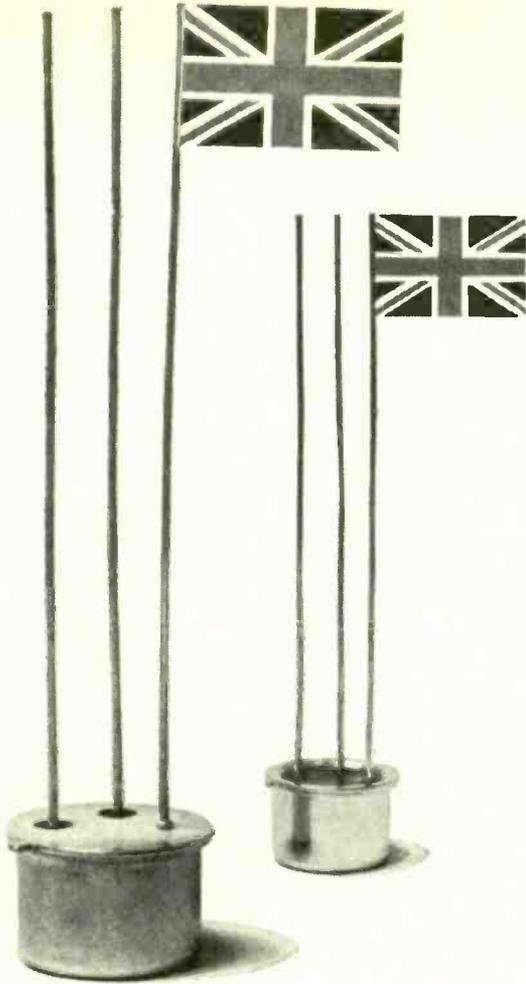

# TO-5 Thyristors are made in Britain by AEI Semiconductors

Which means delivery and quality of this low cost thyristor are guaranteed.

## Features

- All voltage grade available, from 50 to 600V
- Three grades of maximum gate sensitivity 200µA 1mA 10mA, allow selection to give the best performance for every application
- Meets BS9300 Quality Assurance Requirements
- Fully diffused

Write for full details to:

AEI Semiconductors Ltd, Carholme Road,  
Lincoln. Telephone: Lincoln 26435



# AEI

## SEMICONDUCTORS

Member of GEC Semiconductors Ltd.

WW-046 FOR FURTHER DETAILS

# ORYX

## are trumps!

**ORYX**

**MODEL SR1**  
Instant solder remover  
Ideal for printed circuit work  
and integrated circuits.  
79/6

**MODEL SR2**  
with non recoil  
action  
82/6

**ORYX**

**MINIATURE  
SOLDER POT**  
60/-

For rapid  
tinning of  
small tags  
and com-  
ponents.

**ORYX**

**MODEL ST-60**  
90/-

'Hot' wire  
stripper for  
P.T.F.E.  
Insulation.  
24 v operation.

**ORYX**

**MODEL 6A**  
27/6

The smallest  
low voltage  
soldering iron,  
ideal for Printed  
Circuit work.  
6v. 6 watts.

**ORYX**

**MODEL WG50**  
59/6

Thermostatically  
controlled miniature  
soldering iron. 50 watts.  
5 bit sizes  $\frac{1}{16}$ " -  $\frac{1}{4}$ "  
Available for 12v.  
24v. 110v and  
210/250v. operation

**ORYX**

**MODEL M1**  
35/-

A miniature  
mains voltage  
soldering iron  
10 watts. 5 bit  
sizes  $\frac{1}{16}$ " -  $\frac{1}{4}$ "  
210/250v  
operation

Full details of  
these and other  
instruments  
from the Sole  
U.K. and Export  
distributors.

**W. GREENWOOD ELECTRONIC LTD.**

21, GERMAIN STREET, CHESHAM, BUCKS  
TELEPHONE: CHESHAM 4808/9.

WW-047 FOR FURTHER DETAILS

# SIMPLY SUPERB!

# the new brenell...

## MODEL ST STEREO

Probably the most important new recorder of the year!

The new ST400/200 recorders are different from all previous Brenells. All transistorized electronics; shelf-mounting cabinet; simplified controls. Sound quality is even better than ever—as good as you can hear. Three-motor deck performance and reliability; quality components throughout. All usual facilities are available.

ST400/200 recorders are designed to give you exactly what you expect from a Brenell today.

Only the price is less than you may expect... £145 recommended. You pay no import duties... no high selling costs... only for a top-quality recorder, well made. It's a fine formula!

- Mono or stereo operation
- Choice of 2 or 4-track models
- 3 outer-rotor motors
- 3 tape speeds
- 2 recording level meters
- Full input/output and control facilities

A range of Brenell mono and stereo recorders is available, together with Brenell deck and tape-link.



## brenell


BRENELL ENGINEERING COMPANY LTD. 231/5 Liverpool Road, London, N.1. Telephone: 01-607 8271

GD 730

WW—048 FOR FURTHER DETAILS

## DC300

## DUAL-CHANNEL POWER AMPLIFIER

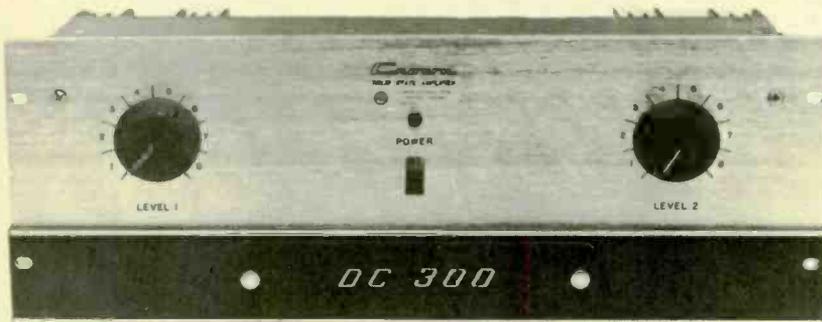

Frequency Response	± 0.1db Zero-20KHz at 1 watt into 8 ohms, ± 0.6db Zero-100K Hz.
Phase Response	Less than 5°, 0-10KHz.
Power Response	± 1db Zero-20KHz at 150 watts RMS into 8 ohms.
Power at Clip Point	Typically 190 watts RMS into 8 ohms, 340 watts RMS into 4 ohms per channel.
Total Output (IHF)	Typically 420 watts RMS into 8 ohms, 800 watts RMS into 4 ohms.
I.M. Distortion (60-7KHz 4:1)	Less than 0.1% from 0.01 watt to 150 watts RMS into 8 ohms, typically below 0.05%. (max 0.05%.)
Damping Factor	Greater than 200 (Zero to 1KHz into 8 ohms at 150 watts RMS).
Hum and Noise (20-20KHz)	100db below 150 watts RMS output (unweighted, typical 110db).
Slewing Rate	8 volts per micro-second. S-R is the maximum value of the first derivative of the output signal.
Dimensions	19in. standard rack mount (W.E. hole spacing), 7in. height, 9½in. deep (from mounting surface).
Weight	40 pounds net weight.
Finish	Bright-anodized brushed-aluminum front-panel with black-anodized front extrusion, access door, and chassis.

★ DC-Coupled throughout!

★ Short Circuit proof!

★ 500 Watts RMS Mono.

★ 70 Volt Balanced line out!

★ Only £320 inc. duty!

**CARSTON ELECTRONICS LTD.**

71 OAKLEY ROAD  
CHINNOR, OXON.

Telephone: Kingston Blount 8561.

WW—049 FOR FURTHER DETAILS

# NAGRA

## The world's best portable professional audio tape recorder



MODEL IVA Automatic, single speed



MODEL IVB Manual, single speed



MODEL IVD Automatic/Manual, three speeds



MODEL IVL Neopilot, three speeds, Automatic/Manual

\* Lids of transparent, shock resistant plastic, have been removed for clarity of illustration.

These models plus eight variants give the professional user a choice of twelve basic Nagra IV tape recorders. Modular plug-in electronic circuit boards, available for each machine, allow unique flexibility in the choice of recording functions.

Study the Nagra IV brochure and see how you can select precisely the facilities you need, built in to one compact machine of outstanding performance and reliability.

Write or telephone for technical information.

**HAYDEN LABORATORIES LIMITED,**

East House, Chiltern Avenue, Amersham, Bucks., England

Tel: 02403 5511 Telex: 83251 Cables: Haylab Amersham.




WW—050 FOR FURTHER DETAILS

# 30 YEARS EXPERIENCE

IN THE DESIGN AND MANUFACTURE OF SOUND SYSTEMS  
WHY NOT LET US SERVE YOU

PRINTED CIRCUIT SOLDERING PLANT

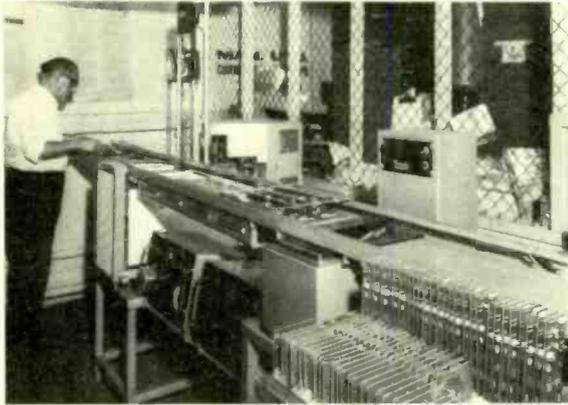

MODULE TEST AND INSPECTION BAY



## "Astronic"

All enquiries to:—

### ASSOCIATED ELECTRONIC ENGINEERS LTD.

DALSTON GARDENS, STANMORE, MIDDLESEX. HA7-1BL  
TELEPHONE 01-204 2125 4 LINES.

All types of Public Address equipment from 10-2,000 watts.  
Custom built mixers.  
Transformers and chokes.

WW—051 FOR FURTHER DETAILS



R.F. SIGNAL GENERATOR  
MODEL 29  
Spin Wheel Tuning £1-0-0 extra

### INSTRUMENTATION BY NOMBREX (1969) LTD. TRANSISTORISED—COMPACT—MODERN STYLING

#### STANDARD MODEL 29-S

- 150 KHz-220 MHz on fundamentals
- Eight clear scales. Total length 40"
- Smooth vernier tuning—ratio 7½ : 1
- Spin wheel tuning—optional extra
- Magnifier cursor—precision tuning
- Unique electronic scale calibration
- Overall accuracy, better than 1.5%
- Modulation, variable depth and frequency

Price £20-0-0

- Weight of instrument with spin tuning 3 lb.
- Size: Height 5¾". Depth 3¾". Width 7½".

#### XTAL CHECK MODEL 29-X

- All the features of the Model 29-S
- AND
- Integral Crystal Oscillator providing calibration check points throughout all ranges. For adjustment of scale accuracy to ±0.02%.

Price £27-10-0

Trade & Export enquiries welcome

NOMBREX (1969) LTD., EXMOUTH, DEVON

Send for full technical leaflets.  
Post and Packing 6/6 extra.

WW—052 FOR FURTHER DETAILS




For  
electronic  
components  
fast...

**Radiospares**

13-17 Epworth St., London E.C.2.  
Tel: 01-253 9561. Telex: 262341.


WW—053 FOR FURTHER DETAILS
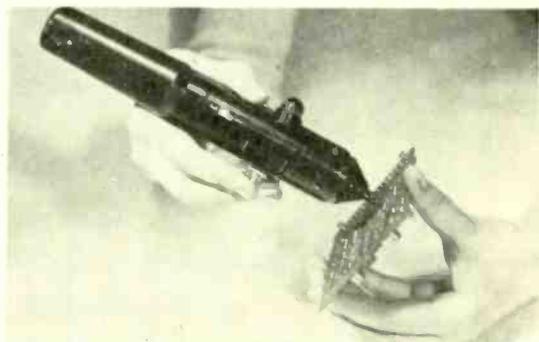
### DIOTESTOR IN-CIRCUIT TRANSISTOR TESTER



**BRITEC LIMITED, 17 Charing Cross Road, London, W.C.2**  
Tel: 01-930-3070

WW—054 FOR FURTHER DETAILS

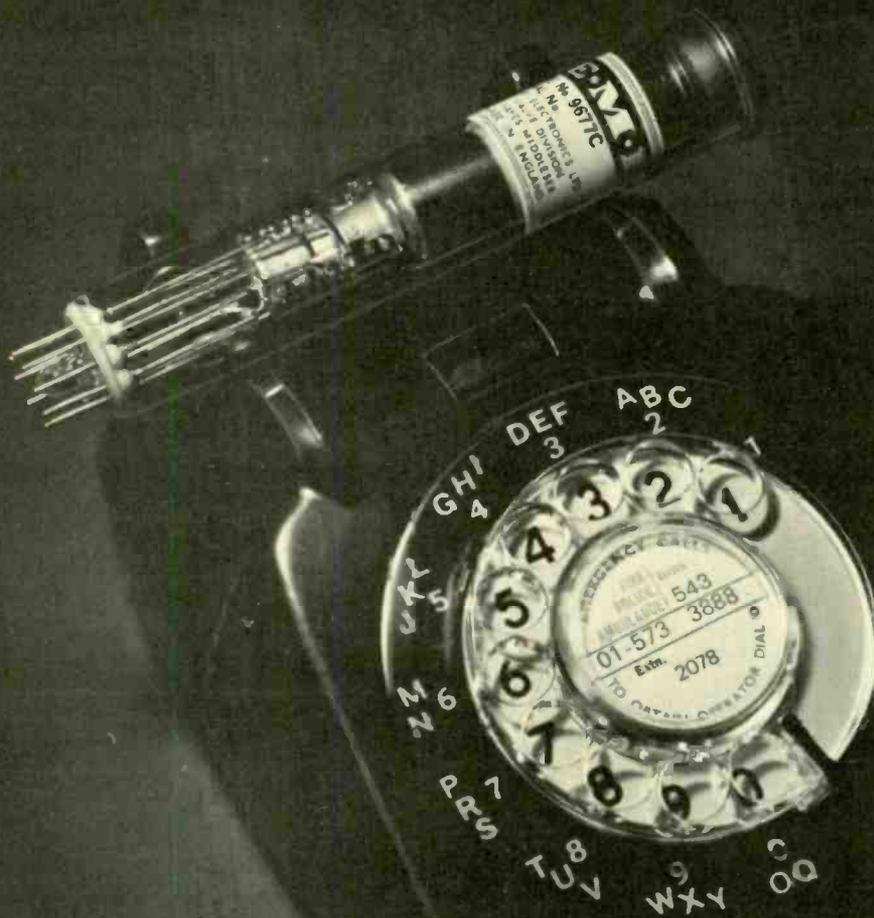**Edmundsons Electronics Ltd.**

60-74, Market Parade, Rye Lane,  
Peckham, London, S.E.15.  
Tel: (01) 639 9731

**Hawnt & Co. Ltd.**

112-114, Pritchett Street,  
Birmingham, 6.  
Tel: (021)-359 4301

**South Wales Wireless**

**Installation Co. Ltd.**  
121, City Road, Cardiff.  
Tel: (0222)-23636

**Smith & Cookson Ltd.**

49-57, Bridgewater Street,  
Liverpool 1.  
Tel: (051)-709 3154

**The Needham  
Engineering Co. Ltd.**

P.O. B. 23, Townhead Street,  
Sheffield S1 1YB  
Tel: (0742)-27161

**J. Gledson & Co. Ltd.**

Newbiggin Lane, Wasterhope,  
Newcastle Upon Tyne, NE5 1PM  
Tel: (0632)-860955

## Sooner or later you'll need both these devices!

At some time, every user of closed circuit t.v. needs a replacement vidicon tube. That's when you need a service organisation that can really perform. Just pick up the phone and contact your nearest EMI distributor. EMI research has produced a range of tubes with reliability, good resolution and high sensitivity. Our distribution organisation has been expanded and streamlined. This ensures that everyone using closed circuit t.v. has access to the best professional advice and a fast replacement service. For further details of the EMI vidicon range contact your distributor or:-

**EMI ELECTRON TUBE DIVISION**


EMI Electronics Ltd., Hayes, Middlesex. Tel. 01-573 3888. Ext. 2078 Telex. 22217 Cables EMIDATA London.

WW-059 FOR FURTHER DETAILS

# Farnell
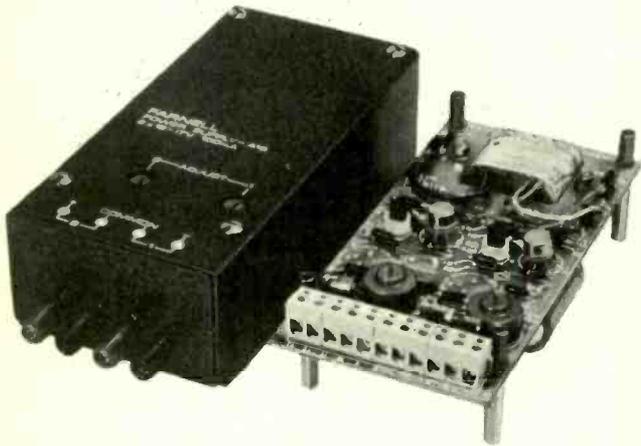
## A15 Operational Amplifier Power Supply

- \* 15-0-15V at 100mA
- \* Employs operational amplifiers
- \* Overload protection
- \* Available as card or sub-unit



The A.15 is intended for driving operational amplifiers and the twin output, nominally 15V, can be varied between 12-17V or connected in series to provide 24-34V. Both ganged control and independent adjustment of one output enable precise setting of output voltages.

### DIMENSIONS:

#### Card


Height 38.1 mm (1.5")  
Width 64 mm (2.52")  
Depth 130 mm (5.12")

#### Complete Sub-Unit

Height 47 mm (1.85")  
(including feet)  
Width 67.5 mm (2.66")  
Depth 153 mm (6.02")  
(including terminals)
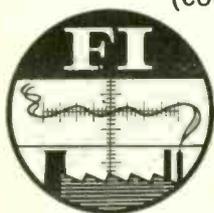
#### Price:

£18. 0. 0. — card  
£20. 0. 0. — modular sub-unit  
(cover, mains lead and terminals)



**FARNELL INSTRUMENTS  
LIMITED,**  
Sandbeck Way,  
Wetherby, LS22 4DH.  
Telephone: 0937-3541/6.  
London Office:  
Telephone: 01 802/5359



STOCKISTS



MULTIMINOR MK. IV

**REPAIR SERVICE  
7-14 DAYS**

We specialise in repair, calibration and conversion of all types of instruments, industrial and precision grade to BSS.89.

Release notes and certificates of accuracy on request.



MODEL 8 MK. III

Suppliers of Elliott, Cambridge and Pye instruments

## LEDON INSTRUMENTS LTD

76-78 DEPTFORD HIGH STREET, LONDON, S.E.8


Tel.: 01-692 2689

E.I.D. & G.P.O. APPROVED

CONTRACTOR TO H.M. GOVT.

WW-061 FOR FURTHER DETAILS

## METER PROBLEMS?

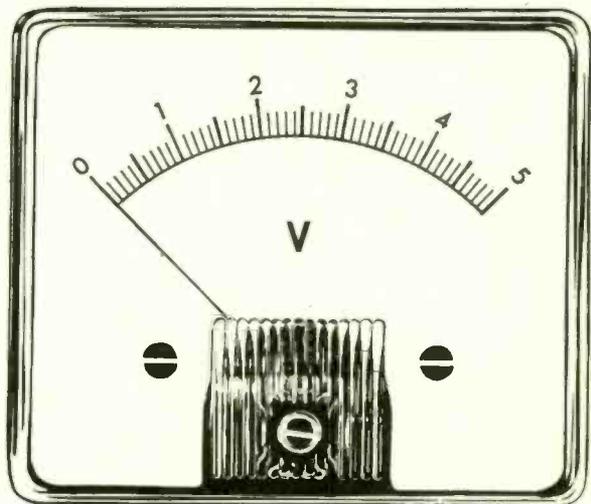

A very wide range of modern design instruments is available for 10/14 days' delivery.

Full Information from:

## HARRIS ELECTRONICS (London)

138 GRAYS INN ROAD, W.C.1

Phone: 01/837/7937

WW-062 FOR FURTHER DETAILS

WW-060 FOR FURTHER DETAILS

# You could be doing things on a much bigger scale



Right now the Selectest Mk2 multi-range test meter meets the requirements of all recent and immediately foreseeable developments in the electric and electronics industries. Accuracy and sensitivity are maximal and these major characteristics are complemented by the extra robustness that withstands modern working conditions and gives longer life. The case is modularly constructed in wipe-clean, tough—but lightweight—melamine. The terminals accept 4mm push-in-plugs and are arranged on the front panel so that the Selectest Mk2 can be used vertically or horizontally. The scale is 25% longer than that on any comparable meter and incorporates an inset mirror and knife thin pointer. Range selection permits continuous rotation. The ultimate are S.E.I. high voltage probes which extend the Selectest's range to 25 or 30kV d.c. for the testing of equipment where the source of impedance is high. These probes can be used with any reputable meter of the required sensitivity but only a Selectest will last as long as the probes.

We manufacture a wide range of portable instruments... write today for full information.

## selectest MARK 2 multi-range test meter



SALFORD ELECTRICAL INSTRUMENTS LIMITED

Peel Works, Barton Lane, Eccles, Manchester M30 0HL


Telephone: 061-789 5081 Telex: 66711

A Member Company of G.E.C. Electrical Components Ltd.

WW—063 FOR FURTHER DETAILS
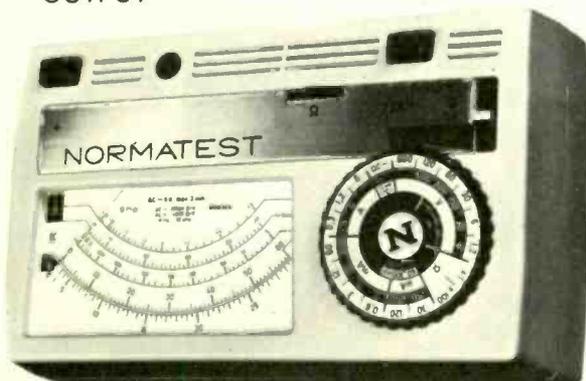
## NORMATEST

- ★ **MODEL 785**
- 40 RANGES FOR—**
- D.C. CURRENT & VOLTAGE
- A.C. CURRENT & VOLTAGE TO 30 kc/s
- RESISTANCE TO 5 MEGOHMS
- TEMPERATURE
- OUTPUT



The newest small Multirange Meter obtainable with a specification comparable to standard-size multirange meters.

- ★ Sensitivity of 20,000 Ohms/volt D.C.
- ★ Accuracy of 2.5% D.C.
- 4,000 Ohms/volt A.C.
- 3.5% A.C. to 500 c/s

★ Robust Taut Suspended Meter Movement

### CROYDON PRECISION INSTRUMENT COMPANY

HAMPTON ROAD : CROYDON : SURREY : Telephone: THORNTON HEATH 4025 & 4094

WW—064 FOR FURTHER DETAILS

## F.A.L. 'PHASE 100'

### Public Address Amplifier



A superb solid state A.C. Mains unit for vocal and instrumental groups and General Public Address use

**59 GNS.**  
Recommended Retail price

- ★ 70 Watts RMS Output
- ★ Output matching for speakers from 3-30 ohms
- ★ 4 separately controlled inputs plus master
- ★ Separate Bass and Treble Controls
- ★ Frequency Response 20 c.p.s. to 30 Kcs.
- ★ High Sensitivity

AVAILABLE FROM YOUR LOCAL DEALER  
Wholesale and Retail enquiries to Manufacturers

SEND S.A.E. FOR FULLY DESCRIPTIVE LEAFLET

FUTURISTIC AIDS LTD., 103 Henconner Lane, Leeds 13

# 16 lbs of high quality performance for only £62

The S51B is the answer for a low cost, easy to use single-beam oscilloscope.

Here are some of the reasons why:

- Small size—light weight  
8" x 7" x 15". 16 lb.
- 5" flat-faced P.D.A. tube.
- Bandwidth DC-3MHz.
- Auto sync and trigger level control.
- Proven performance of over 20,000 S51's in use throughout the world.
- Send for full specification now !!!



WW-065 FOR FURTHER DETAILS

## TELEEQUIPMENT



A member of the Tektronix Group

### TELEEQUIPMENT LTD

313 Chase Road, Southgate, London, N.14  
Telephone: 01-882 1166

For Overseas enquiries write to: Tektronix Limited, P.O. Box 48, Guernsey, C.I.


# Wireless World

Electronics, Television, Radio, Audio

Fifty-ninth year of publication

January 1970

Volume 77 Number 1411

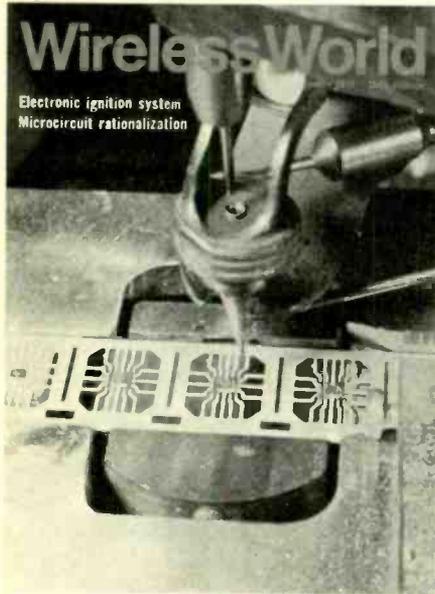

The macrophotograph on this month's cover shows wires being bonded on to integrated circuits at the Mullard Southampton works. On page 6 the future of linear i.c.s is discussed.

## OUR NEXT ISSUE

**Loudspeaker performance:** Paul Klipsch, originator of the Klipsch horn, compares horns and direct radiators

**Ceramic pickups and transistor pre-amplifiers:** are they incompatible? **Matching:** what is meant by this term?

**ibpa**


INTERNATIONAL BUSINESS  
PRESS ASSOCIATION

I.P.C. Electrical-Electronic Press Ltd  
 Managing Director: Kenneth Tett  
 Editorial Director: George H. Mansell  
 Advertisement Director: George Fowkes  
 Dorset House, Stamford Street, London, SE1  
 © I.P.C. Business Press Ltd, 1969  
 Brief extracts or comments are allowed provided  
 acknowledgement to the journal is given.
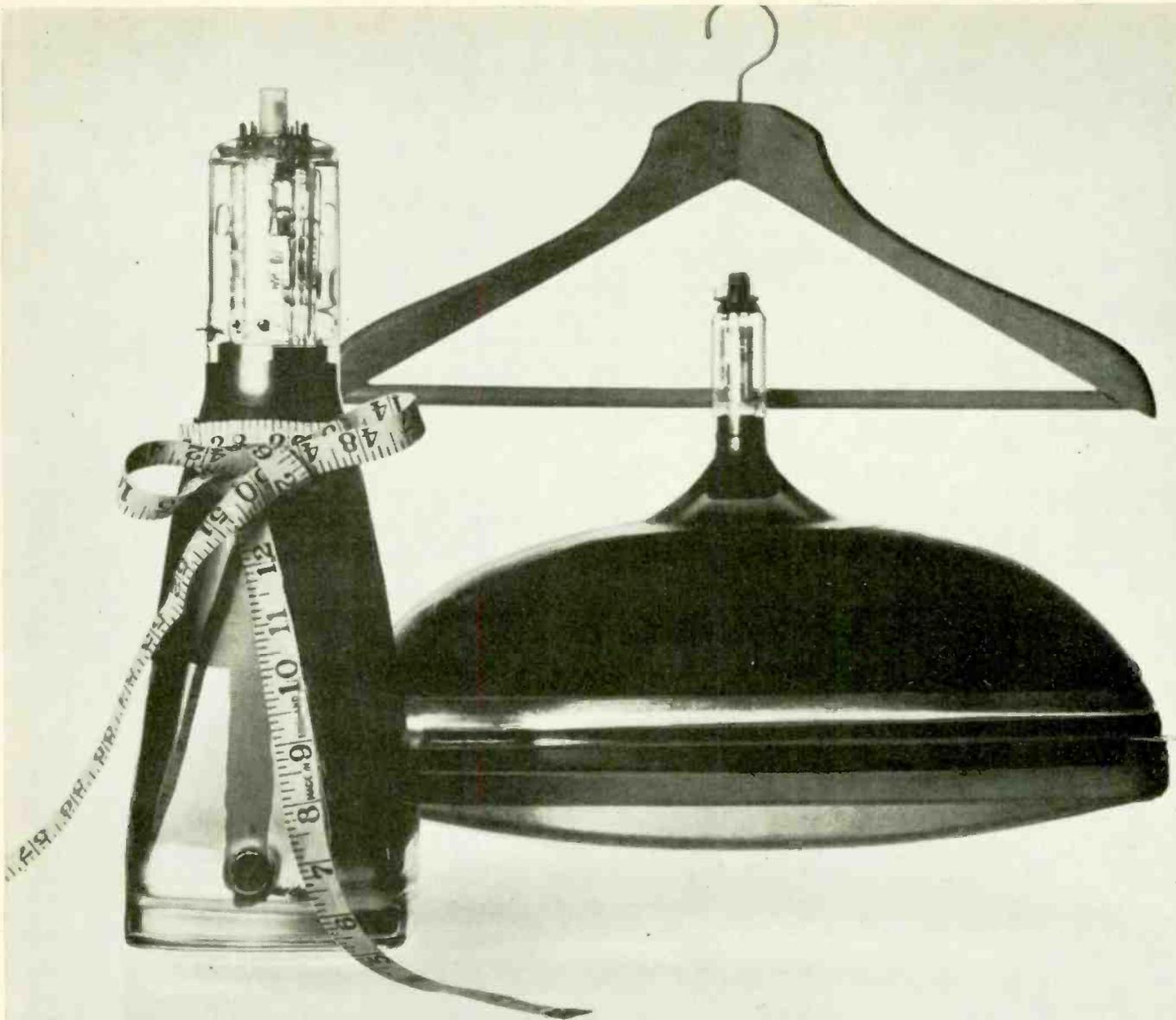
## Contents

- 1 Editorial Comment
- 2 Capacitor-discharge Ignition System by R. M. Marston
- 6 The Future of Linear I.C.s by R. Hirst
- 8 News of the Month
- 10 Letters to the Editor
- 11 Circuit Ideas
- 13 Amorphous Semiconductors by J. E. Carroll
- 16 Application Notes
- 17 Magnetoresistance by B. E. Jones
- 19 Announcements
- 20 Low-distortion Bias and Erase Oscillator by D. Griffiths
- 23 Industrial Telemetry by R. E. Young
- 27 Active Filters—6 by F. E. J. Girling and E. F. Good
- 32 Personalities
- 33 Progress in Tape-recording Techniques by S. Feldman
- 34 World of Amateur Radio
- 35 Electronic Metronome by D. T. Smith
- 35 A Digital Christmas Tree
- 36 D.C. Bias in Push-pull Power Amplifiers by R. A. Smith
- 38 1970 U.K. Conferences & Exhibitions
- 39 New Products
- 44 Meetings
- 45 Test Your Knowledge questions and answers devised by L. Ibbotson
- 46 Literature Received
- 46 H.F. Predictions
- 48 Real & Imaginary by "Vector"
- A95 SITUATIONS VACANT
- A114 INDEX TO ADVERTISERS

**PUBLISHED MONTHLY** (3rd Monday of preceding month). Telephone: 01-928 3333 (70 lines). Telegrams/Telex: Wiworld Hiffepres 25137 London. Cables: "Ethaworld, London, S.E.1." Annual Subscriptions: Home; £2 15s 0d. Overseas; 1 year £2 15s 0d. (Canada and U.S.A.; \$6.75). 3 years £7 0s 0d. (Canada and U.S.A.; \$17.50). Second-Class mail privileges authorized at New York N.Y. Subscribers are requested to notify a change of address four weeks in advance and to return wrapper bearing previous address. BRANCH OFFICES: BIRMINGHAM: 202, Lynton House, Walsall Road, 22b. Telephone: 021-356 4838. BRISTOL: 11, Elmdale Road, Clifton, 8. Telephone: OBR2 21204/5. GLASGOW: 2-3 Clairmont Gardens, C.3. Telephone: 041-332 3792. MANCHESTER: Statham House, Talbot Road, Stretford, M32 0EP. Telephone: 061-872 4211. NEW YORK OFFICE U.S.A.: 205 East 42nd Street, New York 10017. Telephone: 867-3900.



# made to measure- or off the peg?

Open the BRIMAR Industrial Cathode Ray Tube catalogue and you will find just about the widest range of tubes in the business, one of which is likely to be a 'perfect fit' for your requirement. But, if you have something unusual in mind, talk it over with us. BRIMAR can provide the tube you need, either 'made to measure' or 'off the peg', whether it be for measuring instruments, picture monitors, radar, alphanumeric or graphical displays.

Through the unparalleled BRIMAR capability in chemistry, electron optics and vacuum physics the widest design diversity is offered, backed by a personalised customer service.

This service, provided by engineers with extensive

experience of the electronics industry covers advice on tube characteristics, operating conditions and associated components.

Tailored packaging and reliable delivery to meet production schedules are also part of the BRIMAR Service.

Want to know more about the BRIMAR range of Industrial Cathode Ray Tubes? - send for our latest catalogue.



**Thorn Radio Valves  
and Tubes Limited**

7 Soho Square, London, W1V 6DN.  
Telephone: 01-437 5233



# Wireless World

## “Explosion in communications”

**Editor-in-chief:**

W. T. COCKING, F.I.E.E.

**Editor:**

H. W. BARNARD

**Technical Editor:**

T. E. IVALL

**Assistant Editors:**

B. S. CRANK

J. H. WEADEN

**Editorial Assistant:**

J. GREENBANK, B.A.

**Drawing Office:**

H. J. COOKE

**Production:**

D. R. BRAY

**Advertisements:**

 G. BENTON ROWELL (*Manager*)

J. R. EYTON-JONES

 R. PARSONS (*Classified Advertisement Manager*)

Telephone: 01-928 3333 Ext. 538

This was the expression used by Mr. Stonehouse, Minister of Posts and Telecommunications, when he announced in the House of Commons that he was considering setting up an independent enquiry into the long-term future of broadcasting in the U.K. He referred to the need to examine the implications of new technologies, e.g. the possibility of 100 or more communication channels going into every home in Britain via a single wire or microwave link, “which would bring about an explosion in telecommunications”.

One’s immediate reaction to the proposed broadcasting enquiry is “what, another one!” It will be recalled that very few of the recommendations in the Pilkington report of 1962 were implemented and over the years there have been many proposals made by the various committees of enquiry or commissions which, maybe because they were too sweeping, have been turned down. It would, however, appear from the Minister’s latest statement that if the proposed committee is set up it will be asked to look at the long-term future of internal telecommunications generally and not just broadcasting. If so, this is going to be a gargantuan task calling for technological forecasting. Incidentally, Professor W. H. G. Armytage, of the University of Sheffield, speaking recently to members of the Institution of Mechanical Engineers, said it now seems that “technological forecasting is, like weather forecasting, very respectable”. He pointed out, however, that technological forecasting must not be confused with “the inspired doodling that has characterized science and engineering through its history . . . nor the intuitive forecasts that enabled writers like . . . Hugo Gernsback to predict radar or Arthur C. Clarke to predict the earth satellite”. Professor Armytage defined it as “the application of scientific method—or objective, almost clinical method—to the analysis and forecasting of technological change”.

Bearing this in mind the proposed committee could produce a really far-seeing forecast of telecommunications into the ’80s and beyond; but the members will need to be supermen or they will find themselves bogged down by tradition and vested interests.

What are the prospects? The idea of a super telecommunications grid covering the whole country has frequently been suggested and with the growing use of telemetry and control systems, as evidenced by a contribution in this issue, it is fast becoming a necessity.

Such a super grid will be an amalgam of radio and cable techniques. Despite our title we are not so bigoted as to be blind to the potentialities of cable for distribution networks. It is, however, worth recalling that in the early days of this journal there was a fierce war waged between cable and wireless (apocryphal stories are told of the sabotage of cable systems in order to show that wireless was inviolable!) but a marriage was arranged. It is, of course, true to say that without radio devices (amplifiers, repeaters, and the like) the present cable networks could not have materialized.

We do not intend to gaze into our crystal ball, engage in inspired doodling or make intuitive forecasts, but the future for the electronics and radio engineers is certainly exciting.

# Capacitor-discharge Ignition System

An electronic ignition system, suitable for any car, which offers a large number of advantages over conventional ignition

by R. M. Marston

When this unit is wired up to a car's existing ignition system it greatly improves the shape of the ignition voltage wave-forms, and enables a more stable flame-front to be generated in the engine's cylinders. Better combustion is thus obtained, and engine performance is considerably improved.

The unit, which is known as a capacitor-discharge ignition system, confers an impressive list of benefits in terms of engine performance. It gives easy starting, even under sub-zero conditions, and also gives immunity to performance deterioration due to contact-breaker bounce. In addition it gives quicker engine warm-up, improved acceleration, better high-speed performance, and improved fuel economy (2 - 5%). Even more important, it virtually eliminates contact-breaker point burning and wear, gives greatly improved spark-plug life (typically 3 to 5 times longer than in conventional ignition systems), and overcomes the need to adjust contact-breaker and spark-plug gaps with precision.

The ignition unit can be added to any car fitted with a conventional 12-V coil ignition system irrespective of the number of engine cylinders.

Fig. 1 shows the circuit of a conventional, or inductive-discharge ignition system. The contact-breaker (c.b.) points are opened and closed by an engine-driven cam. When the points are closed, current from the battery builds up in the coil primary, to a maximum value of about 4.5A exponentially, with a time constant of  $L/R$  seconds, typical time constants are between 2 and 10ms. As the current builds up, it stores an energy 'packet' of  $(LI^2)/2$  joules, or watt-seconds, in the coil primary.

When the points open, the primary current collapses rapidly via  $C_1$ , and induces a peak potential of about 300V across the coil primary; this voltage is increased to about 30kV at the secondary winding, and this energy is transferred to the spark-plugs by the vehicles distributor.  $C_1$  and the coil form a resonant circuit when the points are open, and the secondary voltage takes about 125 $\mu$ s to build up to its peak value.

Fig. 2 shows typical inductive discharge ignition performance characteristics and ignition requirements at different engine speeds; the early part of the graph, up to about 100 r.p.m., indicates typical sub-zero starting conditions, when battery voltage falls to about 10 V, compared to a normal value of 13.5 V when under dynamo charge. Note that the system operates with very little safety margin under cold-start conditions, and that the available secondary energy becomes inadequate when engine speeds reach 5,900 r.p.m., so that misfiring starts to occur above this speed.

Finally, the relatively long secondary voltage rise times of the inductive system (typically about 125 $\mu$ s) make the ignition system very vulnerable to high energy losses due to

fouling of the spark-plug gaps by carbon and oil deposits. These deposits act as a resistance (typically about 2M  $\Omega$  in cases of bad fouling) across the points. These deposits inevitably absorb some of the applied energy (power-time), and total energy absorption increases in proportion to voltage rise time and fouling resistance.

Capacitor-discharge ignition systems, on the other hand, suffer from hardly any of the snags outlined above. Fig. 3 shows the block diagram of the particular ignition system described here. A self-regulating voltage converter is used to charge storage capacitor  $C_1$  to 400 V, almost irrespective of actual battery potential. When fully charged, this capacitor stores 0.08 joule.

When the c.b. is closed, zero input is applied to the pulse shaper, and the thyristor is off; a standing current of about 250mA is passed through the c.b. via  $R_1$  under this condition, to keep the points 'clean'. The converter is operating, and charges  $C_1$  to 400 V; the capacitor has a charging time constant of about 1.6ms.

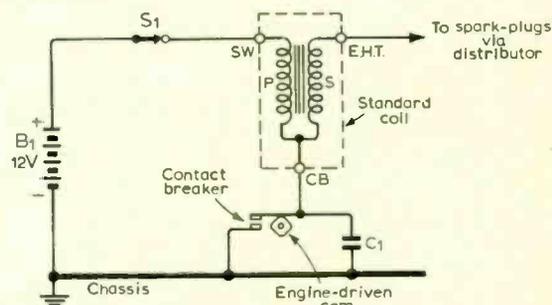


Fig. 1. Circuit of a conventional inductive discharge ignition system.

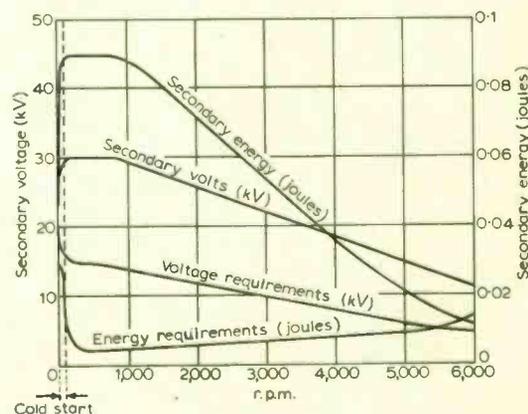


Fig. 2. Typical performance of the circuit of Fig. 1 together with engine energy requirements. The curves assume that battery voltage is normally 13.5V falling to 10V at cold start.

When the c.b. points first open, the pulse shaper operates and turns the thyristor on in about  $2\mu s$ . This short circuits the output of the converter, and turns it off. Simultaneously, one side of  $C_1$  is connected to ground and discharges rapidly into the primary of the coil; the coil steps the resulting primary voltage up to about 40kV, and the stored energy of  $C_1$  is transferred to the spark-plugs. The secondary voltage has a rise time of only a few microseconds.  $C_1$  and the coil form a resonant circuit when the thyristor is on, and have a typical resonant frequency of 1600Hz, giving a period of roughly  $600\mu s$ . At the instant the thyristor fires, the coil's primary voltage rises (in about  $2\mu s$ ) to 400 V, but  $300\mu s$  later the voltage falls to zero as the circuit oscillates and the thyristor turns off, preventing further oscillation. Once this happens the voltage converter re-starts and begins to re-charge  $C_1$ , even though the c.b. points may still be open. The process is repeated when the c.b. opens initially again. Note that the primary coil voltage is isolated from the vehicle's c.b. terminals, which are thus subjected only to the moderately low voltages and currents.

Fig. 4 (a) shows the actual spark voltage performance of

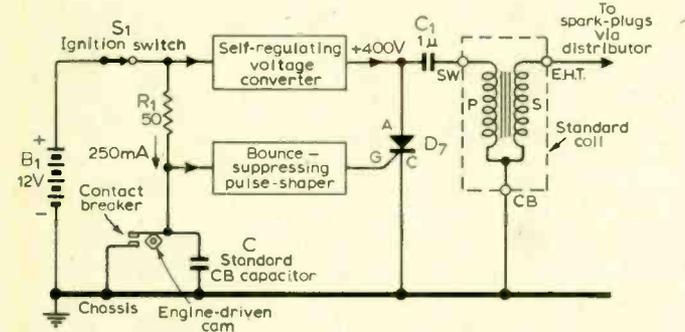


Fig. 3. Block diagram of the capacitive discharge ignition system described in the article.

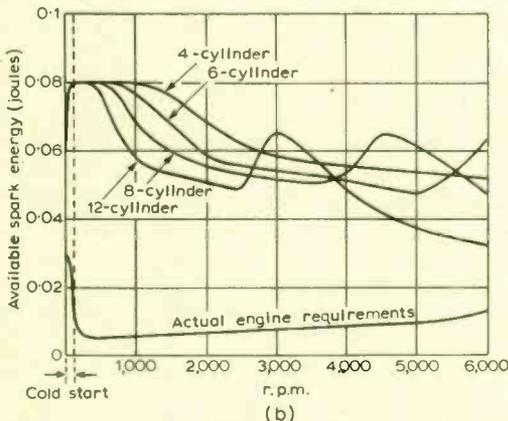
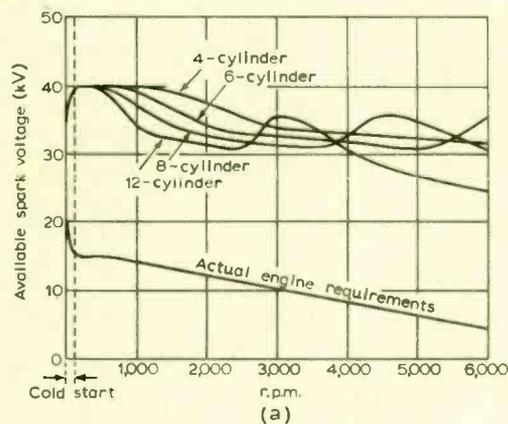


Fig. 4. Curves showing the measure performance of the capacitive discharge ignition system with the same battery voltage conditions as Fig. 2.

the prototype system at different engine speeds, when fitted to different types of engine, together with worst-case ignition voltage requirements, and Fig. 4 (b) shows the system's energy generating performance. Note that both the available voltage and energy are well in excess of engine needs under all operating conditions.

The full circuit of the negative ground version of the ignition system is shown in Fig. 5.  $C_{1a}$  and  $C_{1b}$  form the  $1\mu F$  energy storage capacitor.  $Tr_1-Tr_2$ ,  $T_1$  and the  $D_3-D_6$  bridge form the self-regulating voltage converter.  $Tr_3$  and its associated network form the bounce-suppressing pulse shaper, which fires the thyristor via  $C_3$ .

The voltage converter section operates as follows:  $Tr_1$ , and  $Tr_2$  are an astable multivibrator which uses the halves of the centre-tapped primary of  $T_1$  as collector loads and which generates a series of 24 V (approximately) square waves at each collector, at a frequency of roughly 50Hz. The inductive nature of  $T_1$  causes the early part of each square wave to shoot above the normal flat top;  $R_{11}-R_{12}$  and zener diodes  $ZD_1$  and  $ZD_2$  are used to limit this overshoot to 28 V peak.  $T_1$  steps the square waves up to 400 V peak at the secondary winding. This voltage is then converted to d.c. via the  $D_3-D_6$  bridge rectifier, and used to charge  $C_1$ . It is this overshoot regulation that gives the ignition system its good cold-starting characteristics.  $R_6$  gives the circuit a degree of protection in the event of the battery voltage (under dynamo charge) rising above 15 V, and at the same time reduces the  $C_1$  voltage at high engine speeds.

It should be noted that, although the converter oscillates at a natural frequency of only 50Hz, it is in fact capable of giving good spark generation at c.b. frequencies in excess of 660Hz, i.e., above 20,000 r.p.m. in a four-cylinder, and above 10,000 r.p.m. in an eight-cylinder engine.

At the moment that the c.b. points first open in each ignition cycle the thyristor is triggered, so  $Tr_1$  and  $Tr_2$  stop oscillating;  $300\mu s$  later, the thyristor then turns off, so the multivibrator starts oscillating again. The start of the first half cycle of each converter operation is thus synchronized by the c.b. At c.b. frequencies above about 100Hz, therefore, the converter starts into a half cycle each time the thyristor turns off, but the half cycle is ended prematurely when the thyristor goes on again as the c.b. opens.

The operating frequency of the converter thus synchronizes automatically to half that of the c.b. under this condition. Only a fraction of one natural half cycle is needed to charge  $C_1$  to a useful value, so good sparks are generated up to very high engine speeds.

The c.b. bounce-suppressing and pulse shaping section of the unit operates as follows: When the c.b. points are closed, a standing current of about 250mA is passed through

COMPONENTS LIST

- Resistors  
In the list below the prefix R and the suffix  $\Omega$  have been omitted for clarity.
- |       |        |                |        |
|-------|--------|----------------|--------|
| 1—50* | 4—470  | 7—270 $\Omega$ | 10—220 |
| 2—68k | 5—3.3M | 8—270 $\Omega$ | 11—100 |
| 3—1k  | 6—1*   | 9—220          | 12—100 |
- \* 5-watt wire-wound  
† 2-watt  
remainder all 0.5 watt
- Capacitors  
 $C_{1a}$  and  $C_{1b}$ — $0.5\mu F$ . 600V working, paper or Mylar.  
 $C_2$ — $0.02\mu F$ . 50V working, Mylar.  
 $C_3$ — $0.22\mu F$ . 50V working, Mylar.
- Semi-conductors
- |             | positive earth | negative earth |
|-------------|----------------|----------------|
| $Tr_1$      | —              | 2N3055         |
| $Tr_2$      | —              | 2N3055         |
| $Tr_3$      | —              | 2N3702         |
| $D_1$       | —              | 1N4001         |
| $D_2$       | —              | 1N4001         |
| $D_3-D_6$   | —              | 1N4005         |
| $D_7$       | —              | 2N3525         |
| $ZD_1-ZD_2$ | —              | 2N3525         |
- 27V, 5%, 400mW zener diodes.
- Transformer  $T_1$   
Modified I.T. or battery charger transformer rated at least 30VA. A 240V primary, 17V secondary, 2A transformer is suitable when modified as per text.


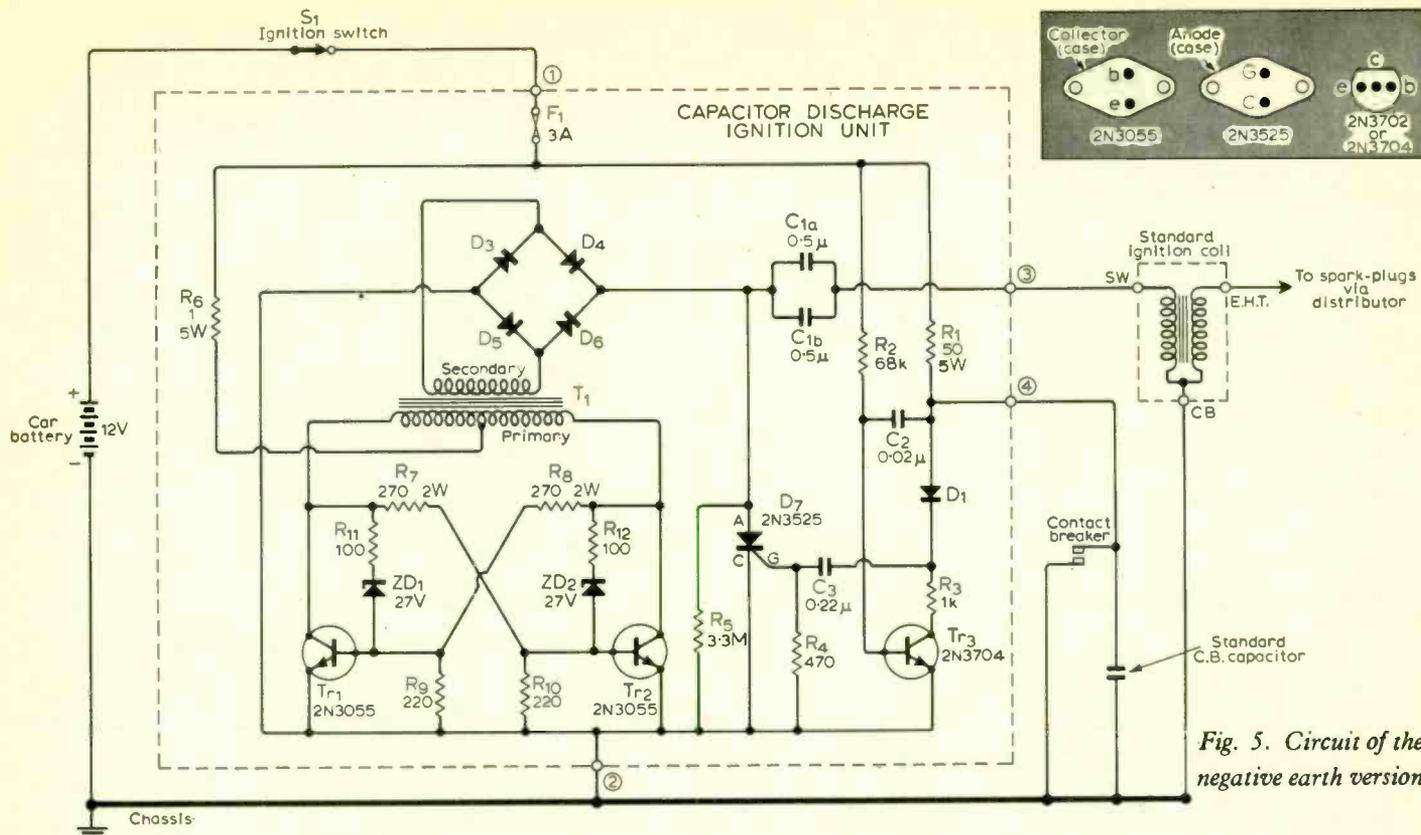


Fig. 5. Circuit of the negative earth version.

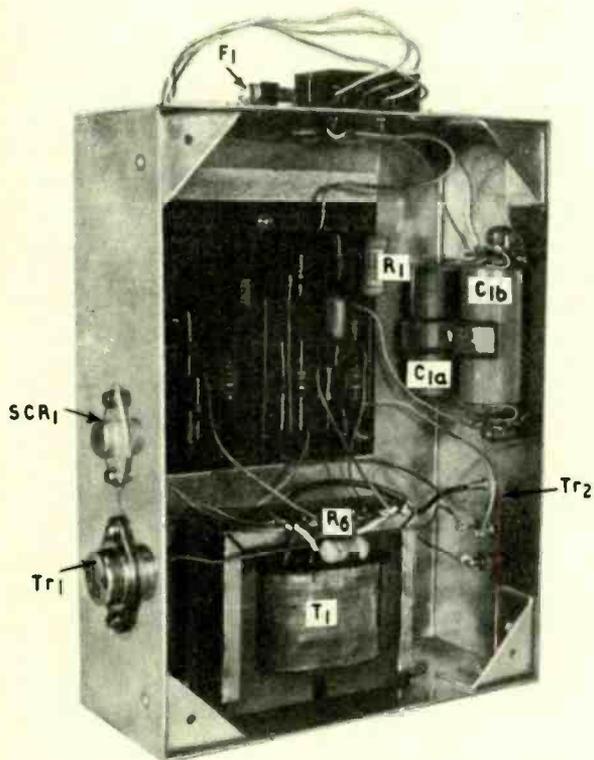

Two views of the prototype positive earth version.

the points via  $R_1$ ; the  $R_1$ - $D_1$ - $C_2$  junction is at ground, and the  $R_2$ - $C_2$  junction is grounded via  $Tr_3$  base-emitter junction. Assume that  $C_2$  and  $C_3$  are fully discharged.

At the instant that the c.b. points open, 12 V appear across the points, and  $C_3$  charges rapidly via  $R_1$ - $D_1$  and the thyristor gate which turns on. Simultaneously,  $C_2$  charges rapidly via  $R_1$  and  $Tr_3$  base so that  $Tr_3$  turns on.

At the instant that the points close again, the  $R_1$ - $D_1$ - $C_2$  junction once more drops to ground volts;  $C_3$  is still fully charged, however, and remains so, since  $D_1$  is reverse biased under this condition;  $C_2$  is also fully charged, but, since its  $R_1$ - $D_1$  side has been pulled down to ground volts, it drives

$Tr_3$  base sharply negative, so  $Tr_3$  is cut off.  $C_3$  thus has no discharge path at this stage, and retains full charge. Consequently, should the points bounce open again at this stage (point bounce only occurs within the first two or three hundred micro-seconds of initial point closure), the thyristor will not be triggered back on again. Now, as soon as the points close, the  $C_2$  charge starts to leak away via  $R_2$ , and eventually, after about  $600\mu s$ , the charge falls to near-zero and  $Tr_3$  is biased on via  $R_2$ . Once it is turned on,  $Tr_3$  provides a discharge path for  $C_3$  via its collector and  $R_3$  and  $R_4$ ;  $C_3$  then discharges rapidly, with a time constant of about  $35\mu s$ . At the end of this period,  $C_2$  and  $C_3$  are once more fully discharged, and the thyristor is ready to be triggered on again.

Thus, the thyristor is triggered on as soon as the points open, but can not be operated again until the points open again after being fully closed for at least  $600\mu s$ . The thyristor is thus immune to false triggering by c.b. point bounce.

The positive ground version of the ignition system is shown in Fig. 6. This is similar to that described above, except that a few circuit polarities are changed and the thyristor is triggered on with a negative pulse applied to its cathode via  $D_2$ .

The only problem involved in the construction of the unit is that of finding transformer  $T_1$ . This is an iron-cored unit with a turns ratio of 15:1 at a power rating of 30VA or greater, and with a centre-tapped low-voltage winding. The easiest way to obtain this unit is to re-wind an existing l.t. or battery-charger transformer. The winding procedure is very simple, and the following is an account of that used on the prototype:—

The transformer is required, before modification, to have a basic turns ratio of 15:1 or less. Any l.t. or battery-charger transformer that meets this and the 30VA power requirement can thus be used. The prototype unit started life as a 240 V:17 V, 2 A battery-charger transformer, and thus satisfied the above specification. Once selected, the low-voltage winding of the unit must be re-wound and centre-tapped to give an exact 15:1 ratio, i.e., a ratio of 240 V:16 V

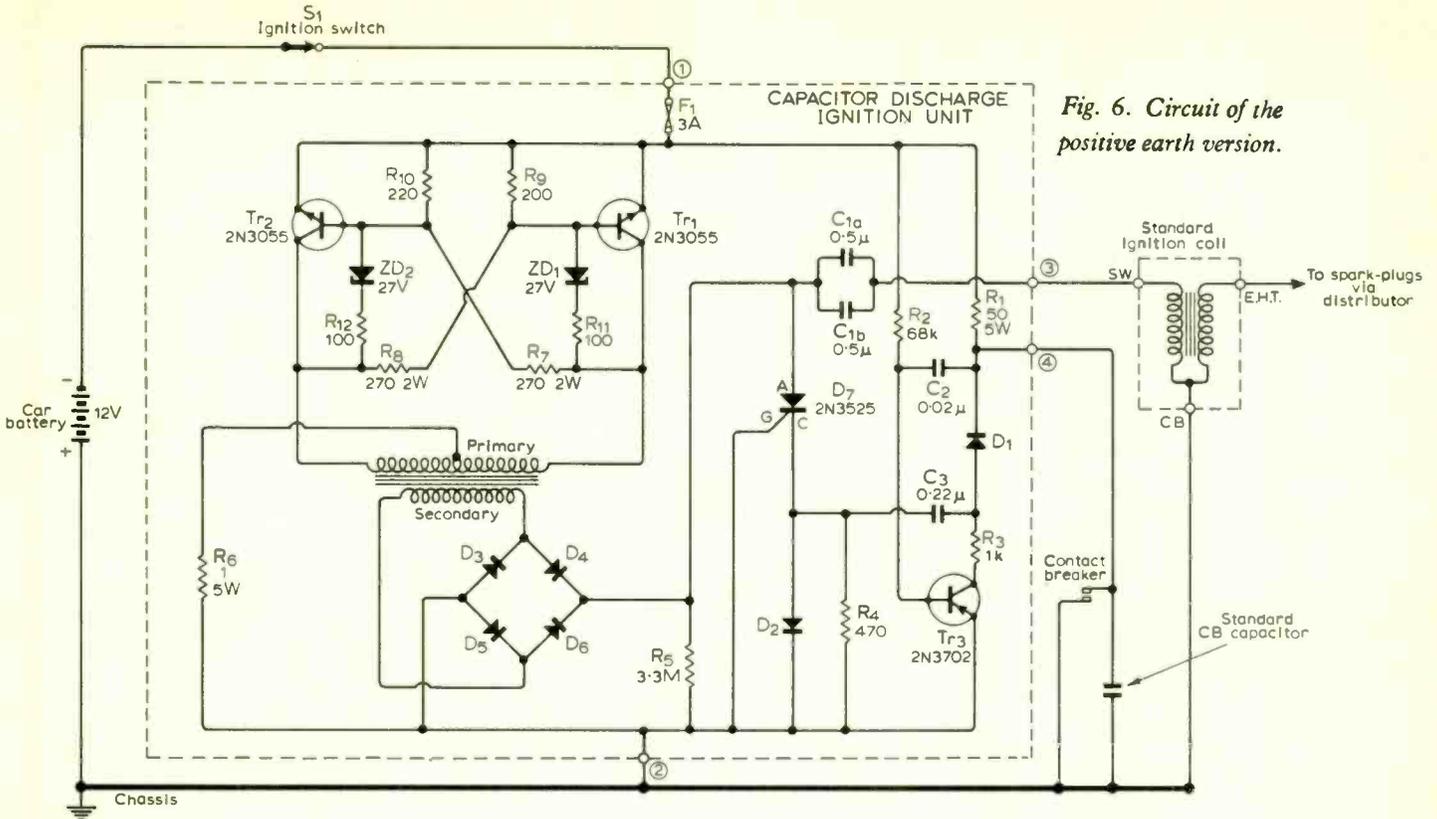


Fig. 6. Circuit of the positive earth version.

in this particular case.

To rewind the transformer, remove its securing clamp and dismantle its iron core laminations (making note of their method of assembly), and then remove the coil bobbin. Next, unwind the entire low-voltage winding (which is invariably the outer winding on the bobbin), and carefully note the total number of turns used; now divide the number of turns by the original value of l.t. voltage, to give the transformers basic turns-per-volt value. On the prototype, total turns were 134, and the original voltage was 17, giving a turns-per-volt value of 7.9. Now calculate the l.t. voltage needed to satisfy the 15:1 final turns ratio of the transformer (16 V in this case) and multiply by the turns-per-volt value (7.9) to give the total number of turns to be rewound (128); now re-wind this number of turns on the bobbin to form the primary of the ignition unit transformer, taking care to make a tap at the half way mark. Finally, re-assemble the core laminations and re-fit the transformer clamp; the transformer is then complete and ready for use. The original mains primary is now of course the secondary of the new transformer.

Construction of the rest of the unit should present no problems, and it can be wired-up direct from the circuit diagram. The prototype positive ground version of the unit (see photographs) is mounted in an 8 x 6 x 2½-in metal box; the two power transistors (Tr<sub>1</sub> and Tr<sub>2</sub>) and the thyristor are mounted, via insulating washers, to the box surface (which acts as a heat sink); most of the remaining components are mounted on a piece of Veroboard Panel; external connections to the unit are made via a 4-way terminal block.

When construction is complete, give the unit a simple functional check by connecting terminal ② to chassis and terminal ① to the 'hot' side of the car's battery; a "humming" noise should now come from the unit, indicating that the converter section is operating, and total current consumption should be roughly 800mA; approximately 400 V should be available between the anode and cathode of the thyristor when tested with a 20,000 Ω/volt meter. If this test is satisfactory, the unit can now be fitted to the car.

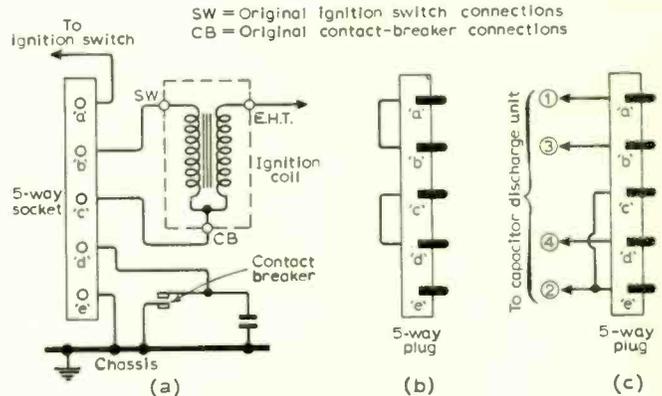


Fig. 7. Plug and socket connections required for fitting the unit to a vehicle. Unplugging the plug (c) and inserting the plug (b) into socket (a) changes from conventional to capacitive discharge ignition system.

The complete unit can be either mounted in the glove compartment (as in the case of the prototype), or can be fixed to the rear fire-wall of the engine compartment (but not close to the exhaust system). The unit can be either wired directly to the existing coil and c.b. assembly, or, preferably, can be wired to these components via a 5-way plug and sockets (Fig. 7), in which case the driver can change from conventional to capacitor discharge ignition by simply fitting an alternative plug into the socket.

Once wiring is complete, turn on the ignition, operate the starter, and check that the system functions well under actual driving conditions; there is no need to re-adjust c.b. or spark-plug gaps, etc.

Results vary from one car to another, but improvements are particularly evident in cars that have covered a considerable mileage since their last tune-up.

Finally, once the unit has been found to perform satisfactorily over a reasonable mileage, it is recommended that the entire circuit be covered with an electrically insulating coat of water-proof paint or varnish, to exclude the harmful effects of moisture. The unit can then be expected to operate correctly for the life of the vehicle.

# The Future of Linear I.C.s

A few simple integrated circuits, with guaranteed long-term availability, could meet nearly all the needs of the industrial manufacturer

by R. Hirst\*

Linear integrated circuit packages have been available for a relatively short period in Britain. By virtue of the techniques employed and the expense incurred in developing and manufacturing monolithic circuitry reasonably large production quantities are required to make the selling price compatible with circuits manufactured from discrete components. This fact in itself restricts the market to which the initial product may be tendered as the industrial design engineer, with a relatively small piece-part requirement, is unable to incorporate devices that are essentially made for the domestic sphere. While the majority of linear integrated circuits will meet industrial requirements, it is the fear of an abrupt cessation in supply at the end of two or three years, due to the biennial change in the requirements of the mass radio and television market, that causes the main concern to the long-term industrial user.

Linear integrated circuit manufacturers seem unable to grasp this situation and continue to pour into the market complex, incompatible and non-interchangeable units mounted in a multitude of mechanical assemblies as can be seen from Table 1.

Based upon a simple survey it would seem reasonable to maintain production of one or two devices that at the present time have more than paid for their tooling costs by virtue of large-scale distribution. It would be necessary to inform the industrial equipment manufacturer which devices would be available for a relatively long time. The consumption, based upon this type of selling, could be surprisingly large and the risk to semiconductor manufacturers spread over a much greater number of customers.

To show how simple linear integrated circuitry could be, the following excursionary appraisal of the requirements of a substantial portion of the industrial consumer has been presented. There would appear to be four main areas in which integrated circuitry could be used to great advantage, these are: switching, l.f. amplification, h.f. amplification, frequency conversion.

**Switching:** This appears to have been adequately covered by the majority of

TABLE 1  
Characteristics of some i.c. amplifiers

type	response at -3dB	gain (dB)	supply volts	pack
SN777	d.c. — 100kHz	70	4.5	*
SN7510	d.c. — 40MHz	42	+8 & -8	*
SN7510L	d.c. — 40MHz	42	+8 & -8	TO-99
TAA111	d.c. — 150kHz	62	7	TO-76
TAA121	d.c. — 150kHz	74	7	TO-76
TAA131	d.c. — 20kHz	56	5	*
TAA141	d.c. — 20kHz	56	5	TO-76
TAA300	d.c. — 25kHz	50	9	TO-74
TAA310	d.c. — 15kHz	100	7	TO-74
TAA293	d.c. — 600kHz	80	6	TO-74
TAA263	d.c. — 600kHz	77	8	TO-72
TAA350	d.c. — 12MHz	80	6	TO-74
TAA231	d.c. — 30MHz	20	12	TO-78
F104A	d.c. — 35MHz	20	20	TO-74
F104B	d.c. — 45MHz	20	20	TO-74
CA3011	0.1 — 20MHz	60	10	TO-74
CA3020	d.c. — 6MHz	58	9	TO-74
CA3021	d.c. — 2.4MHz	56	+18 & -6	TO-74
CA3023	d.c. — 16MHz	53	+18 & -6	TO-74

\* Flatpack

semiconductor manufacturers and it is possible to obtain devices from different manufacturers that are directly interchangeable. The presentation has stabilized in the shape of fourteen-lead dual-in-line packages, usually epoxy encapsulated. The cost of the pack approaches or improves upon the cost that may be achieved by discrete techniques and the only aspect that now remains is to have more standardization and interchangeability.

**L.F. amplification:** As the majority of integrated circuits are d.c.-coupled, it would seem reasonable to lump together the l.f. and h.f. requirements thus reducing the consideration of linear amplification to a single unit. This device is described under the heading of h.f. amplification.

**H.F. amplification:** There is an integrated circuit available on the market with a flat frequency response up to 45MHz which is entirely d.c.-coupled. This device is being used in large quantities in the manufacture of domestic radio and television. It is a Mullard unit type F104B and is mounted in a 12-pin TO-5 can. The internal circuit of this device is shown at the left-hand-side of Fig. 1 and it can be seen to be very simple in design but nevertheless adequate in performance. A variety of response curves may be obtained by changing the value of

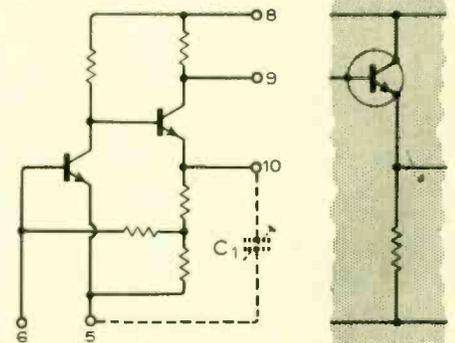


Fig. 1. The Mullard F104A/B is shown on the left which can fulfil nearly all the industrial manufacturers needs for l.f. and h.f. amplification. The shaded area contains an emitter-follower circuit which can be added so that the circuit can be made to drive long coaxial lines.

$C_1$  as shown in the graph of Fig. 2. The circuit in the shaded portion of Fig. 1 is a directly coupled emitter-follower which can be used to reduce the output impedance so that the unit may be terminated in a coaxial lead to feed a further unit which could be some distance from the amplifier.

This circuit has been used in a number of assemblies operating from 100Hz to 30MHz and it was found that by substantially increasing the value of  $C_1$  that the gain at 100kHz could be

increased from 20dB to 30dB if some increase in harmonic distortion could be tolerated. From the curves in Fig. 2 it is obvious that, if the amplifier is used in a relatively narrow band, the value of  $C_1$  may be altered to accurately provide a given level of gain. For instance with  $C_1$  in the order of 25pF the gain at 50MHz would be approximately 26dB. However, if the value of  $C_1$  was reduced to 12pF the gain would have decreased to something in the order of 19dB. As  $C_1$  is an external component it is an easy task to use a ceramic trimmer adjustable from 5pF to 25pF to take up the gain spreads of the integrated circuit.

Obviously this package does not deliver a great deal of power but it may be terminated in one or more stages to give the required output level. It may also be preceded by an emitter-follower in order to increase the input impedance should the need arise. At frequencies below 10MHz the small value of  $C_1$  is unlikely to promote sufficient change in gain to enable the variable capacitor to take up the spreads from circuit to circuit and it is probable that if a considerable gain change is required at the lower frequencies it will be necessary to alter the value of the series input resistor. However, as previously indicated, if  $C_1$  is replaced by a fixed large value of capacitor the gain can be adjusted over a considerable range, but it then becomes necessary to change a capacitor physically, rather than make a simple adjustment. This amplifier has now been produced by Newmarket Transistors Ltd, under the title MC 809 and is a thick film device mounted in a dual-in-line package.

**Frequency conversion:** Fig. 3 shows a simple ring modulator circuit using four diodes and two transformers. This unit may be manufactured from discrete components but the degree of balance required for industrial applications, over a wide temperature range, cannot be easily achieved unless the diodes are carefully matched and mounted in a common heat-simulating device. With the aid of standard monolithic techniques this type of modulator may be readily presented on one chip thus ensuring that the elements have a similar temperature coefficient and are mounted in close proximity.

At the present time transistor monolithic ring modulators are available on the market as standard units but unfortunately the frequency range is very limited and cannot be considered for high-frequency work.

The circuit of Fig. 3 is not the only method of obtaining balanced frequency conversion but it is a simple device that can have a very wide and flat frequency response providing that the transformers are designed correctly. A unit of this nature has a considerable field of application throughout the military and industrial manufacturing industry.

**Conclusion:** Little has been done to establish the needs of industrial manufacturers as far as integrated circuits are

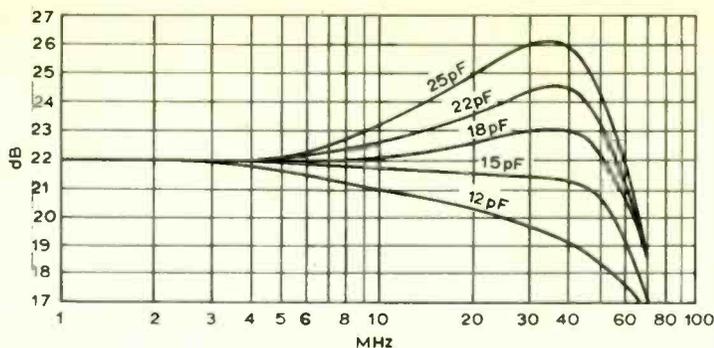


Fig. 2. Frequency response of the F 104 B with different values for  $C_1$ .

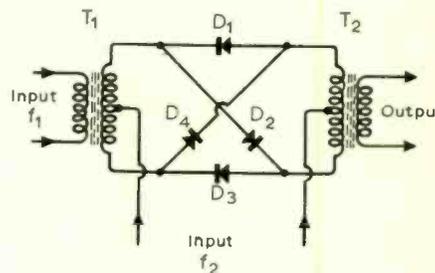


Fig. 3. Basic ring modulator circuit.

concerned. If just one or two of the more simple integrated circuits, at present available to the domestic consumer, were to be classified as devices with long-term availability, the military and industrial manufacturer would undoubtedly respond by including such units in future designs.

During some recent observations into designs promoted by just one industrial manufacturing company it was noted that during the past three years, sixteen totally different amplifiers had been designed to achieve a small signal gain of between 20 and 30dB at 100kHz. Each one of these amplifiers could easily have been replaced by the circuit indicated in Fig. 2 without any detriment to the performance. Some startling but accurate conclusions were reached when cost estimates were prepared for the development and manufacturing cost of the discrete assembly on one hand, and the integrated assembly, on the other.

In the instance of the sixteen amplifiers designed around discrete components, it was ascertained that a total of 2 man-years were involved in the engineering, drawing and planning. The total annual consumption of the final amplifiers was small in the order of 500 units, costing approximately £5 each. The total cost over a manufacturing period of five years was as follows: development—£8,000; 2,500 units—£12,500; giving a total expenditure of £20,500.

Replacing these sixteen different designs with a common integrated circuit the development period could be reduced to one half man-year costing about £2,000 leaving a total of £18,500 to be spread over 2,500 integrated units giving a unit price of £7 8s for a simple three-stage device. There is no reason why a semiconductor manufacturer could not make a substantial profit at such an elevated unit price. The advantage to be gained by the industrial manufacturer at such a price would not be directly financial but a reflection in the substantial

period of time that a skilled engineer would now have to devote to the more elaborate task of system design.

The modern circuit engineer is now likely to find that his services are more and more in demand in the laboratory of the semiconductor manufacturer where, chemistry, physics and electronics come close together. There is a vast shortage of skilled engineers in every country and it has to come that the majority of skills available will be employed in the design of systems using integrated circuitry as the basic building blocks. This does not detract from the skill of the circuit engineer but to the contrary indicates that a much higher degree of skill must be used in planning the minimum number of configurations to be used over a very wide and varied market.

\* Communication Division, S.T.C. Ltd.

## Corrections

J. Dinsdale, author of "A Design in Retrospect" in the November issue, writes: "There is an unfortunate ambiguity in Fig. 5 which does not make it clear whether the mk I or mk II design is being discussed. It is important that the earphone-loading network (shown in the dotted box) is connected in place of the loudspeaker in whichever design is being used. On no account should there be a direct d.c. path from the collector of  $T_{r_6}$  to ground, as Fig. 5 could imply." Also for May read April in ref. 9.

The values of two resistors in the Wien Bridge Oscillator on page 575, December issue, were incorrect in the diagram. For 68k and 33k, read 6.8k and 3.3k. See also page 11 for addendum to last month's "Letters".

# News of the Month

## American radio and TV production

It would appear from the latest figures issued by the U.S. Electronic Industries Association that there is a grave decline in the indigenous radio industry. Not that the sales of domestic receivers have declined but that there has been a growing influx of imported sets while the number of home-produced models has decreased.

The total sales of domestic a.m. and f.m. receivers produced in the U.S. during the first nine months of 1969 was 3.58M compared with 4.15M during the same period in 1968. Imports, however, rose by about 5M to 24.6M of which some 4M eventually bore U.S. company labels. The picture in car radio is very different. Of a total of 8.87M units (a slight increase on the 1968 figure for the same period) just over 1.2M were imported.

Of a total of 9.85M television receivers sold during January-September 1969 (of which over 4.6M were colour) 1.23M imported sets bore U.S. labels and a further 1.58M carried foreign labels. Incidentally, about 13% of the colour receivers sold in the U.S.A. during the first nine months of 1969 were imported.


Figures for the disposal of receivers in the U.K. (supplied by the British Radio Equipment Manufacturers' Assoc.) do not show imported equipment. Disposals of domestic radio receivers declined from 762,000 for the first nine months of 1968 to 547,000 for the same period in 1969. Car radio sets dropped from 309,000 to 262,000. Monochrome television receiver deliveries declined from 1,220,000 in 1968 to 1,172,000 in 1969 and colour sets from 89,000 to 77,000.

## German satellite earth station

Germany's earth station at Raisting, near Munich, now has a second paraboloid aerial. This, like its counterpart at the U.K. Goonhilly station, will enable communication to be maintained via satellites in both the eastern and western hemispheres.

The main physical difference between Raisting's aerials I and II is that the designers have dispensed with the use of

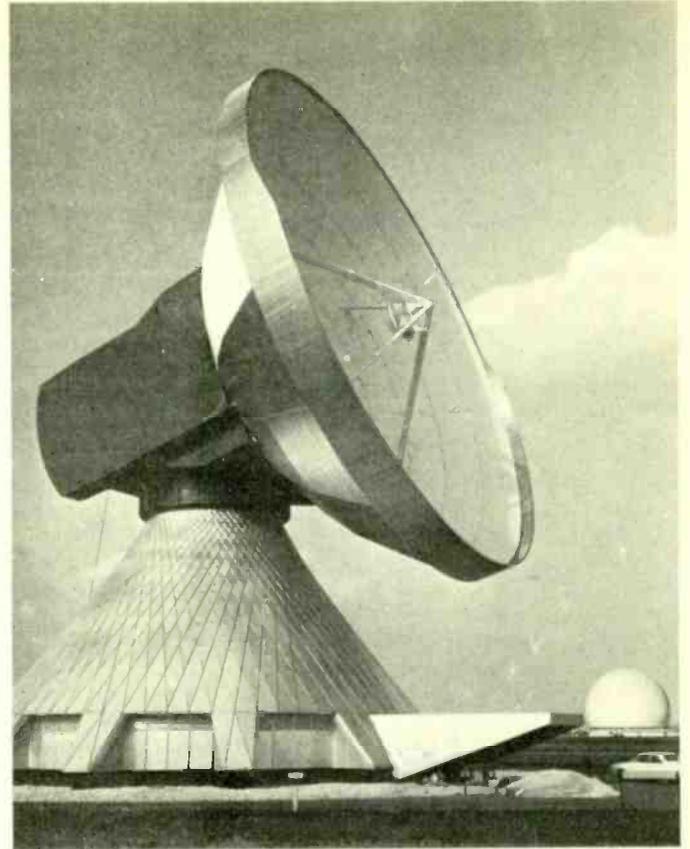*Raisting's second paraboloid. In the background is the radome of the first aerial*



the radome cover in the latest installation. Although this gave protection from the weather it also created a problem—a film of water or ice on the radome caused background noise. Aerial II is fitted with 5000 infra-red radiators to prevent icing. The dish is 28.5m in diameter and the gain 60dB which corresponds to a power gain of one million as compared with an isotropic radiator operating at 4GHz. Maser pre-amplifiers with a 25-MHz bandwidth were originally used in the receiving section of the earth station, but parametric amplifiers with a 500-MHz bandwidth and a gain of 10,000 have now been installed by Siemens who undertook the refurbishing of the station.

## Information service for engineers

INSPEC the Institution of Electrical Engineer's information service in physics, electrotechnology and control, is to launch a selective dissemination of information (SDI) service in electronics in January. It will be available on an individual or group subscription basis in the United Kingdom only. Periodical articles on all aspects of electronics, published in English or English translation, will form the basis of the service. The institution plans to start a comprehensive SDI service covering all languages and the complete subject range of INSPEC in 1971. This service is part of the overall plan for the development of a comprehensive information service, which is being supported by the Office for Scientific & Technical Information of the Department of Education & Science. For the past year the SDI service in electronics has been limited to some 600

research workers as part of a government-supported information research project. Further information and details may be obtained from the manager, INSPEC SDI Investigation, I.E.E. 26 Park Place, Stevenage, Herts.

## Cranfield Institute of Technology

Cranfield College of Aeronautics, which was founded at Cranfield, Bedford, in 1947, has been granted a Royal Charter to become the Cranfield Institute of Technology with power to award its own higher degrees. As its original title implies it has been concerned principally with aeronautics but in future its object will be "to advance, disseminate and apply learning and knowledge in the disciplines of the sciences, engineering, technology and management". The Institute will also pay particular attention to "the educational needs of industry, commerce and the public services".

## Laser space communication

The first laser communications system to be used in a satellite is to be developed by Aerojet-General Corp., of Azusa, Calif., under contract to NASA. The equipment is to be used aboard the Applications Technology Satellite—F (ATS) which is scheduled for launching from Cape Kennedy into a synchronous orbit in 1972. The contractors will develop both the spacecraft equipment and the associated ground equipment. When ATS—G is launched in 1974 the laser

communications experiment may be extended to include spacecraft-to-spacecraft links.

## Conferences on tape

"Cassette Colloquia" is the name of a programme begun by the Institute of Electrical and Electronics Engineers to keep its members technically up to date. Cassette recordings of special seminars, workshops, sessions etc, conducted by the I.E.E.E. will be available to members and non-members. The recording technique for the cassettes involves speech compression without pitch change. This, in conjunction with editing, allows 2½ hours of material to be converted to 75 minutes in the cassette of a recent meeting. A cassette containing this length of recording costs \$10.

## V.H.F. complaints

The B.B.C. has completed an analysis of reports of unsatisfactory v.h.f. reception (during 1968/69) which shows that more than 50% of the complaints were due to the use of inadequate aerials or to faulty or maladjusted receivers. A great deal of dissatisfaction could be avoided, it is said, if dealers would advise when an external aerial is necessary and would also make sure that customers know how to tune their receivers.

## Full colour spectrum from infra-red

New phosphors, employing rare earth elements in crystals, have been found by workers at Bell Telephone Laboratories to convert infra-red radiation into any colour of the rainbow. The source of infra-red energy is a gallium arsenide diode. The initial use of the combination of GaAs diodes and infra-red-to-visible phosphors was reported by General Electric. The phosphors can be painted on the diodes—green or red light is produced by certain crystals containing erbium or holmium, and blue light using thulium. With one of the phosphors, colours gradually change from green through yellow, off-white, and orange, and finally to red, as power is increased. The red light so produced is as bright as that emitted directly by other solid-state lamps.

## WWV standard frequency transmissions

The National Bureau of Standards (U.S. Department of Commerce) in Boulder, Colo., is responsible for the operation of four radio stations (WWV, WWVB and WWVL at Fort Collins, Colo., and WWVH, Hawaii) that transmit accurate time and frequency information. The formats of two of these stations, WWV and WWVH, are being reviewed for possible changes and modification. A questionnaire has been sent to many known users of the broadcast services and

any other users (government, military, industrial, scientific or private individuals) who wish to receive the questionnaire are asked to write to WWV 1969, National Bureau of Standards, Boulder, Colo. 80302.

For the record, station WWV has been transmitting standard radio frequencies on a regularly announced schedule since March 1923 and WWVH began supplementing the broadcast services of WWV from a site on Maui, Hawaii, in 1948. Both stations broadcast the same services on high-frequency carrier waves. Stations WWVB and WWVL at Fort Collins transmit on l.f. and v.l.f. The services of all four stations are described in publication 236, NBS Frequency and Time Broadcast Services, available from the Superintendent of Documents, U.S. Government Printing Office, Washington, D.C. 20402, for 25 cents.

## TV camera for low-light levels

A television camera, type GTNV-1 capable of producing pictures from scenes illuminated at light levels equivalent to starlight, has been introduced by STC. Minimum scene-illumination requirement for the camera, is about  $2 \times 10^{-5}$  ft. candles so that it can respond to scenes that are invisible to the human eye. A vidicon tube is used in conjunction with a three-stage image intensifier having a very high overall gain. Typical brightness magnification is 35,000 times. No especially contrived illumination such as infra-red beams, or reliance on self-emitted infra-red is necessary. For use underwater, where there is very little light, a clearer picture is obtained by using the natural light available rather than an artificial source, the light from which tends to be scattered back to the camera and so degrading the picture.



The STC low-light television camera with cover removed

## W.W. Diary

The larger-page size 1970 *Wireless World* Diary (5 × 3 inches) has enabled a more readable type to be used for the information section which includes those features found to be most acceptable to users. They include formulae, circuits, aerial data, colour television and stereo broadcasting characteristics, transistor data, frequency allocations, addresses of organizations and many other facts and figures.

The Diary, which has a week-at-an-opening, costs 10s (leather) or 7s (rexine).

## American incentive licensing allocations

Although the U.S. Federal Communications Commission recently suspended the application of proposals for increasing the sub-allocations of h.f. bands available only to amateurs holding Extra Class licences, there remain substantial portions of the bands available only to those holding Extra Class and Advanced Class licences, as part of the policy of encouraging American amateurs to study for the more advanced licence examinations, in a scheme introduced in November 1969. The first 25 kHz of the 3.5, 7, 14 and 21-MHz bands are available only to Extra Class telegraphy; the frequencies 3.8 to 3.9, 7.2 to 7.25, 14.2 to 14.275 and 21.25 to 21.35MHz are now all subject to reservations for either Extra Class only or for Extra Class and Advanced Class telephony. Our correspondent Pat Hawker says British amateurs have expressed opposition to an A.R.R.L. proposal that American telephony operation should be authorized in the band 14.1 to 14.2MHz.

## Mysterious generation of u.h.f. exploited

An unexplained phenomenon, discovered at RCA Laboratories in 1967, has been harnessed by RCA to produce the most powerful pulses of radio energy in the u.h.f. range yet achieved by a solid-state device. The effect occurs in avalanche diodes, when they are placed in a circuit tuned to oscillate at frequencies lower than those at which the diodes are supposed to be able to oscillate. For reasons that are still not fully understood, when electrical pulses are now applied to the diodes, they abruptly enter an "anomalous mode" of operation and begin to produce microwave oscillations with powers and efficiencies substantially higher than normal. It is reported that by combining five such devices in a single tiny package and operating them in the anomalous mode, microwave pulses with peak powers above 1,200W have been produced with efficiencies above 25%.

# Letters to the Editor

*The Editor does not necessarily endorse opinions expressed by his correspondents*

## Transistor Distortion Characteristics

Mr. Linsley Hood's results (given in his November article) are rather unexpected, in one respect. A perfect transistor would exhibit a voltage gain independent of  $h_{fe}$ , and, in his particular test circuits, independent of the load resistance as well. Yet the reported figures, even allowing for the imperfections of the transistors, are at variance with this expectation. They are also at variance with my own measurements.

In a practical circuit, the voltage gain is very nearly  $g_m \cdot R_L$  for a planar transistor with low "extrinsic base resistance". Now  $g_m$  is a function of the collector current, not the current amplification factor. It is about  $40 I_C$ . Thus a transistor operating at  $I_C = 1\text{mA}$  has a  $g_m$  of about  $40\text{mA/V}$ .

The voltage gain is therefore  $40 \cdot I_C \cdot R_L$ . In Mr. Hood's tests,  $I_C \cdot R_L$  was kept constant, so one would have expected the voltage gain to be constant, to a first approximation, irrespective of the variations in  $h_{fe}$ ,  $I_C$ , and  $R_L$ . In circuit A, for example,  $I_C \cdot R_L$  was fixed at 5, so the expected voltage gain is 200, not 40-140 as reported.

My own quick tests on a silicon planar transistor (BFY51) produced the expected results: the voltage gain with 5V dropped across the load was 185-210 for loads of 1-8.2k $\Omega$ ; i.e., and 8 to 1 variation in collector current. There is clearly something wrong somewhere.

In the case of alloy transistors, the extrinsic base resistance is comparatively high, and changes the performance appreciably. At the higher collector currents and lower values of  $h_{fe}$ , this resistance (perhaps a few hundred ohms) is comparable with the "true" input resistance  $25 \cdot h_{fe} / I_E$ . Its effect is to reduce the apparent  $g_m$  and also to make the transistor operate, not as a purely voltage-driven stage, but in a mode between voltage drive and current drive. This latter effect improves the linearity. It follows that the linearity of any voltage amplifier stage can be improved by inserting base resistance. The price you pay is in reduced gain and increased

noise. (Much the same effects are obtained by the use of an unbypassed emitter resistance.)

If large output voltage swings are taken, distortion due to Early Effect may become important. (This was reported by Dr. Bailey in connection with one of his power amplifiers, where the driver stage had to deliver large swings.) It may well be that a low- $h_{fe}$  transistor shows less of this distortion than a high- $h_{fe}$  one, though correct selection of types is perhaps better than selecting for low  $h_{fe}$ .

G. W. SHORT,  
South Croydon,  
Surrey.

### The author replies

I was pleased to read Mr. Short's letter, and I note with interest, his argument that a transistor should, ideally, always give an identical stage gain, as a voltage amplifier. However, this is not the situation one finds in practice, nor is it the conclusion one draws from gain calculations made using the classical formula,<sup>1</sup> using the conventional  $h$  parameters, for a common emitter configuration.

$$M = \frac{1}{h_{re} - \frac{h_{ie}}{Z_L} \left( \frac{1 + h_{oe} Z_L}{h_{fe}} \right)}$$

assuming  $Z_{gen} = 0$ .

Taking the transistor type which he quotes, and obtaining the typical values for the  $h$  parameters,  $h_{ie}$ ,  $h_{oe}$ ,  $h_{re}$  and  $h_{fe}$  from the Mullard data sheets, the calculated stage gains for a BFY51, under ideal conditions of zero source and emitter impedance, vary from 210 to 319 over the range of collector loads 1 to 10k $\Omega$ .

However, there is a less complex formula quoted by Manasse<sup>2</sup>, using the concept of the "h determinant"  $\Delta_h$ , ( $\Delta_h$  is equal to  $h_{ie} \cdot h_{oe} - h_{fe} \cdot h_{re}$ ),

$$M = \frac{h_{fe} \cdot R_L}{R_L \cdot \Delta_h + h_{ie}}$$

Since over the range of loads in question with a BFY51,  $\Delta_h$  is very small, this

approximates to—

$$M \approx \frac{h_{fe} \cdot R_L}{h_{ie}}$$

So, if the input impedance of the transistor increases linearly with the product  $h_{fe} \cdot R_L$  (and  $h_{fe}$  may remain nearly constant), the theoretical condition could be met. Normal device shortcomings, such as doping inhomogeneity, carrier trapping and the base-emitter spreading resistance presumably give rise to the failure of the theoretical model.

However, with regard to the gain figures I quoted for the devices I examined, it had not been my intention that these values for gain should be taken as the voltage gain of such devices under ideal voltage amplifier conditions. Alas, low-distortion signal generators do not have zero output impedance. My intention was, rather, to establish a form of "figure of merit" for such devices, and to determine the comparative performance, say, of germanium versus silicon and n-p-n versus p-n-p. In this context the fact that the signal generator had not a zero impedance output was not of importance.

In fact, the apparatus used was a Solartron VF252 precision millivoltmeter, a Radiometer BKF5H distortion meter and a Marconi TF1101 low-distortion oscillator, with 1kHz output filter. (The modulus of the output impedance of the Marconi oscillator is 660 ohms, which accounts for the actual stage gain being lower than the calculated zero input impedance value.) It was remiss of me not to mention in the article the source impedance used, but, surely, if one really wanted to know what the typical stage gain of a particular device would be under zero input and zero emitter resistance conditions, one would calculate it from the formulae, rather than try to measure it with a possibly very untypical component.

With regard to the point raised by Mr. Engstrom in his letter in the December issue, may I say that the points he raises are agreed. The treatment of transistor voltage amplifier non-linearities on the basis of variation in the input admittance is, indeed, the classical approach. However, I quote Mr. P. J. Baxandall's observation that in transistor circuit design it is much more fruitful to consider the devices as voltage amplifiers; and treat their non-linearities on that basis, rather than to endeavour to swamp the input impedance changes by the inclusion of massive input or emitter circuit impedance.

J. L. LINSLEY HOOD

### References

1. "Transistor Circuit Design", Walston and Miller, pp. 98-99.
2. "Modern Transistor Electronics, Analysis and Design", Manasse *et al*, (Prentice Hall), pp. 46-49.



# Circuit Ideas

## Constant current generator

Dual transistors are used to ensure cancellation of thermally variant transistor parameters in the simple constant current generator shown.

By suitably proportioning the resistor values the drift of the constant current due to variation of transistor base-to-emitter junction voltage, collector-to-base leakage current, and current gain are cancelled out.

For cancellation of base-to-emitter voltages the necessary circuit relationship is:

$$R_3 = R_4.$$

To assist stable operation with change of leakage current and gain the remaining resistors are proportioned to satisfy the equality:


$$R_5 = \frac{R_1 R_2}{R_1 + R_2}.$$

The output current is given, with good accuracy, by:

$$I_{cc} = \frac{V_{cc}}{R_5} \left( 1 - \frac{R_2}{R_1 + R_2} \right)$$

The transistors should be operated with equal emitter currents to ensure tracking of the two base-to-emitter voltages with temperature.

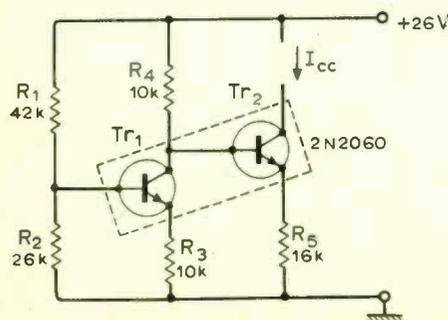The resistors should be wire-wound types with low temperature coefficients. The differential temperature coefficient of the resistor pairs  $R_1, R_2$  and  $R_3, R_4$  is more important than the absolute temperature coefficient.




The measured temperature coefficient of  $I_{cc}$  is typically 0.0015%/°C over the temperature range 0 to 100°C.

As shown the constant current is directly proportional to the supply voltage. To make the constant current independent of the supply, resistor  $R_1$  may be replaced by a temperature-compensated zener diode. An additional resistor ( $R_b$ ) is then required in series with the base of transistor  $Tr_1$ , such that  $R_b = R_5$ .

M. CADWALLADER,  
London N.W.3
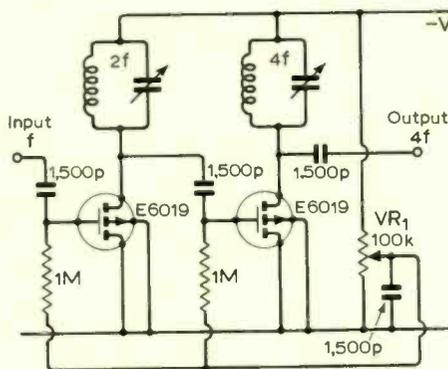
## A M.O.S.T. frequency-doubler chain

The high impedance of m.o.s. transistors allows tuned frequency doublers to be cascaded without requiring impedance transformation. The use of enhancement devices eliminates the need for a separate bias supply. The arrangement is shown in the diagram. The potentiometer is adjusted to provide the required bias



for maximum efficiency. Since  $C_{iss}$  is not highly dependent on the applied gate voltage, adjustment of  $VR_1$  does not detune the preceding circuit. Doublers are not prone to feedback and interaction problems so that dual m.o.s. devices such as the Marconi-Elliott E6029 could be used. The circuit will operate up to 150MHz with the high  $g_m$  devices of the E6019, E6029 series.

J. A. ROBERTS,  
University College,  
Swansea.

## Negative resistance of transistor junction

If the emitter-base junction of a silicon planar transistor is reverse biased, it behaves as a zener diode, with a typical breakdown voltage of 7-10V. If the base is left open-circuit and connection is made to the collector instead, the "zener diode" has a negative resistance characteristic. The effect is exhibited by most


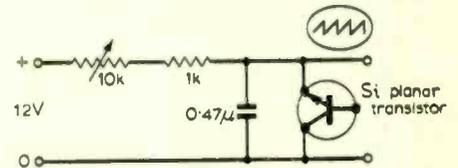


Fig. 1. Test circuit giving ramp waveform.

Fig. 2. Thyristor firing circuit.

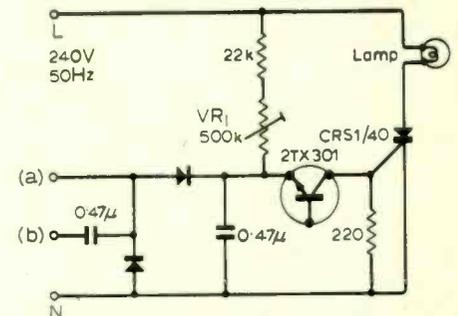

n-p-n silicon planar transistors, but by few p-n-p types. The relaxation oscillator in Fig. 1 can be used as a test circuit.


The device is also useful for firing thyristors. Fig. 2 shows a simple half-wave lamp-dimming circuit which can be controlled manually, by  $VR_1$ , or by a d.c. input 0 and 10V at (a) or an a.c. input 0 to 10V peak-to-peak at (b).

J. A. H. EDWARDS,  
Leicester.

## Low-distortion 30Hz-20kHz oscillator

The circuit is a Wien bridge oscillator employing an f.e.t. to reduce damping on the bridge and allow the use of a 500kΩ twin potentiometer. Harmonic distortion of the prototype was reduced to less than 0.05% over the whole band with the aid of the 22kΩ preset resistor.

C. A. PYE,  
Exhall,  
Warwickshire.

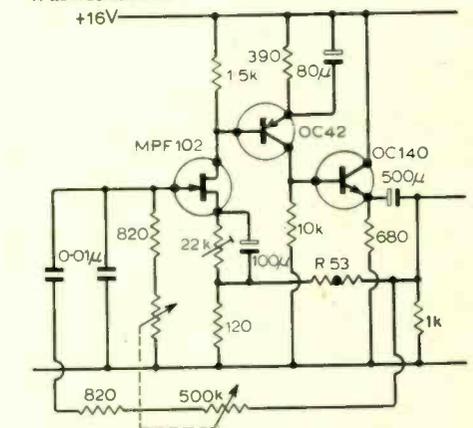

Wien bridge oscillator covering audio range with no capacitor switching.  
(C. A. Pye)

# Amorphous Semiconductors

## An electronic engineer's view after a recent conference at Cambridge

by J. E. Carroll. Ph.D.

About 350 pure and applied physicists with a sprinkling of electronic engineers were in the Cavendish Laboratory, Cambridge, from September 24th to 27th,\* to discuss the amorphous and liquid state. Amorphous materials with their lack of obvious structure have for a long time posed fundamental problems of description to the pure physicist, but the applied physicist and engineer are not attracted to a field unless they have a whiff of a practical application. Although negative resistance and switching effects have been reported as long ago as 1962<sup>1</sup>, this whiff of practical utility was not scented by the technical hounds until 1968 when Ovshinsky<sup>2</sup> published a letter entitled 'Reversible electrical phenomena in disordered structures'. The title appears harmless but the contents suggested the use of amorphous semiconductor material in the application of switches with a high ratio of 'on' to 'off' impedance and also in the application of memory devices. Applications to the communications industry and logic functions in computers are then obvious if the device is a success. At first sight there appear to be several useful technological features: apparent lack of sensitivity of the material to small amounts of impurity, the devices can be used in thin film form that would be compatible with modern integrated circuit technology, no power consumption to maintain the memory, to name a few of the more obvious advantages. This then accounts for a small technical explosion of interest in this field. This article attempts to give a simple account of these amorphous semiconductors and their associated potential devices in the light of the recent Cambridge conference.

### The amorphous state

First, let us ask the question, what is an amorphous material? An initial definition would be a material that exhibited no structure or order. So no matter where we looked, we should see a random spacing of atoms in the material.

Although partially true, this is too naive. The solid material has to be bound together by some cohesive force. This cohesive force can then impose constraints on the extent of the disorder. It is well known that the outermost electrons (valence electrons) of any atom determine the chemical properties of the atom, or in other words determine how one atom binds itself to any other. One type of binding together of atoms is called *covalent* binding. The valence electrons are shared between pairs of neighbouring atoms, lowering the potential energy of the pair and so binding them together. This binding can extend throughout the crystal. Fig. 1(a) indicates such a scheme for say crystalline germanium. Each atom shares four electrons with neighbouring atoms and this completes a relatively stable configuration. In Fig. 1 (b) the same scheme is shown in a disordered array but to preserve the binding the bonds are still linked. The technical jargon says that the co-ordination number of each atom is preserved. This imposes constraints on the short-range order (say over a couple or so of atoms spacing). To appreciate

this fully one needs to go to quantum theory of electron orbitals, but this is not necessary here. However, over larger distances disorder prevails and the atom spacing and positioning become quite random. A slightly more realistic model is obtained by allowing for several of the valence bonds to be broken, or dangling as they are often referred to. This is shown schematically in Fig. 1(c). It is such covalent amorphous materials, but with more complex structures, that have been causing most interest since in many ways they behave like intrinsic conventional semiconductors. There are, of course, other amorphous materials such as amorphous metals. In this latter case the atoms are bound together by a sea or jellium of almost free electrons shared between a large number of atoms. The binding imposes no long- or short-range order and the conduction is not significantly changed between the crystalline and amorphous states. At present these latter materials are not of interest.

Returning to the covalent amorphous semiconductors, we find further evidence for the short-range order in the absorption of certain wavelengths of light. If a

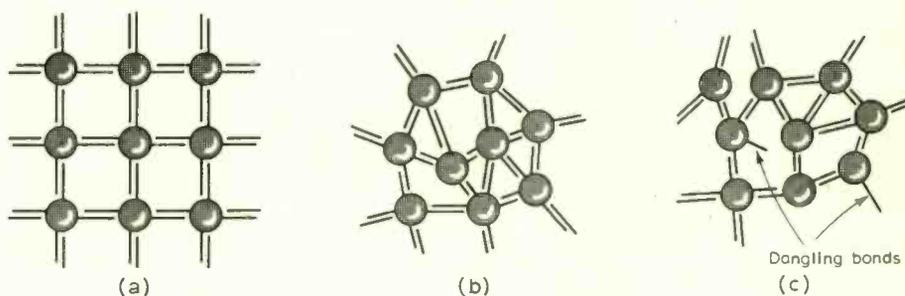


Fig. 1. Covalent binding (schematic) (a) crystalline state (b) amorphous state (c) amorphous state indicating dangling bonds.


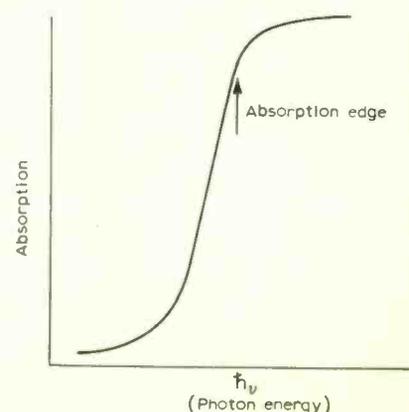



Fig. 2. Absorption edge (schematic). Absorption of light by a crystal against light frequency.

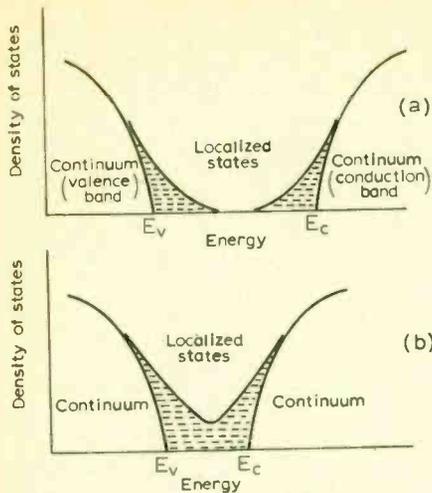\* International Conference on Amorphous and Liquid Semiconductors, sponsored by the Royal Society. The proceedings to be published in a special volume of the *Journal of Non-crystalline Solids*, published by North-Holland Publishing Company, Amsterdam.



(Left). Fig. 3. Density of electron states in amorphous semiconductor (a) non-overlapping localized states (b) overlapping localized states.

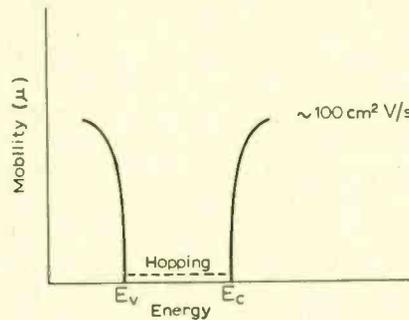(Below). Fig. 4. Electron mobility against energy.



density of electron states throughout the energy 'gap' in amorphous materials, none the less the mobility of any electrons filling those states can probably be ignored. The idea is shown schematically in Fig. 4.

Since any free electrons become trapped by the unfilled valence bonds one is not surprised to find that these semiconductors only exhibit what is termed an intrinsic conduction. Conduction only occurs in proportion to the amount that the thermal agitation can free electrons from their bonds. The addition of impurities makes little effect on this process. The classical behaviour of an intrinsic semiconductor's conductivity is given by  $\sigma = \sigma_0 \exp. -(\Delta E/2kT)$  where  $\Delta E$  is the band gap energy, or close to this value. This result is also found for amorphous semiconductors of the covalent type. An important consequence of this intrinsic behaviour is that the resistance of any specimen decreases as the temperature increases (more electrons produced to conduct electricity by more bonds breaking). This leads to thermal runaway under some conditions and in turn can lead to negative resistance and switching.

### Practical devices

Let us now describe two types of device that were being demonstrated in experimental form by Energy Conversion Devices at the Cambridge conference. They both use films (circa 1 micrometre thick) of an amorphous semiconductor known as a chalcogenide glass. The first type of device is the Ovonic Threshold Switch, or O.T.S., named after Ovshinsky who first reported it in 1968. The threshold voltage is around ten volts and the off resistance can be as high as tens of megohms. As the threshold voltage is reached so the current rises to a few microamps and then switches to many milliamps. The switching time can be extraordinarily fast and this leads to problems in surge currents through the device that can degrade the performance if they are not limited. In the 'on' state the device impedance drops to around 100 ohms (all these figures depend on geometry and so must only be taken as indicating orders of magnitude). The device then remains in the on state provided that the current is above a minimum sustaining value of around 10 mA, or equally the device voltage does not fall below about a volt. If the current does fall below this sustaining level then the device reverts to its high resistance state. Provided that surge currents are limited it is claimed that these switches can be recycled almost indefinitely. The characteristics for the O.T.S. are shown schematically in Fig. 5(a). It should be pointed out that there is evidence against the existence of a closely defined threshold voltage since some workers find that this varies statistically from one switching operation to another<sup>6</sup>. This point was hardly made at the Conference.

photon of light has sufficient energy to break a valence electron bond in a semiconductor then it can become strongly absorbed by the material. Thus if the absorption of light shows a marked edge to it as the wavelength of light is changed (Fig. 2) then this is evidence of a uniform binding energy throughout the body of the crystal. Qualitatively similar optical effects are found in amorphous and crystalline material, though often with different magnitudes. From the existence of these effects it can be inferred that there is considerable uniformity of the electronic structure close to each atom. In other words there is indeed a short-range order in the amorphous material. Now as one of the speakers at the conference asked 'what is a forbidden gap but the binding energy of the valence electrons?' The absorption edge energy is indeed one of the ways of measuring the gap between the valence and conduction band energies in conventional semiconductors. Thus we still expect to find a similar gap in amorphous semiconductors. However, although all gaps are forbidden, some are more forbidden than others! In amorphous material there are lots of broken valence bonds. Although annealing the material can reduce their number, their density is still very high. It is so high in fact that any 'free' electrons, introduced by impurities (on the classical semiconductor basis of creating electrons) become trapped in these dangling bonds. As a consequence the conductivity of the material is not altered even by an appreciable amount of impurity in the material. This is in complete contrast to conventional semiconductors. These traps have a continuum of energies and can in some cases fill up the conventional energy gap. Thus the density of electron states available to electrons with different energies can be drawn schematically as in Fig. 3(a). There is a continuum of states as found in conventional semiconductors but also a high density of localized states forming tails to the continuum. These localized states are in effect the broken valence bonds discussed above. To the electrical engineer who uses frequency filters these tails (or tales) appear most plausible! If one randomly alters the inductances and capacitances of the periodic chain

of these elements that form a frequency filter, then one finds that the cut-off frequencies become diffuse and propagation is possible for regions extending into the formal stop band of the filter. Thus changing the periodic structure of the crystal in a random way would be expected to allow a certain amount of propagation of the quantum electron waves outside their normal permitted range of frequencies or energies. The farther away from the formal permitted energies the more likely are the states to be localized (in the filter analogy the states are a result of local resonances in the filter structure). These tails of localized states extend both from the band of valence electron energies and the conduction band energies. In some materials these tails can overlap (Fig. 3(b)) so that the whole gap is filled with traps. This latter picture is believed to be the relevant one for the glasses that exhibit switching and memory<sup>3</sup>.

Conduction can occur as in a conventional semiconductor. The electron moves in an electric field and gains energy, thus moving to a higher energy state. This is readily possible for electrons in the conduction band where there is a continuum of empty states above the electrons' particular state. It is also possible in the valence band provided that there are vacancies, or holes as they are called, in the occupation of the upper electron states in that band. These holes then permit the electrons to gain energy in an electric field and so allow conduction. An important difference between the amorphous and crystalline state is the magnitude of the mobility. The increase in disorder implies that the electrons have many more collisions as they move. For a given field the electrons' drift velocity is a good order of magnitude lower than in the useful crystalline semiconductors. The mobility is then around 100 cmV/s<sup>2</sup> for these amorphous materials. There is a second mechanism that is called 'hopping'. In the high density of localized electron states in the gap, electrons can hop from one state to another under the action of an electric field. However, this hopping process results in a negligible mobility. We therefore arrive at the picture of a 'mobility gap'. Although there may be a high

Closely allied to the O.T.S. is the O.M.S. or Ovonic Memory Switch. Energy Conversion Devices were exhibit-

ing an experimental thin film array of these devices. In this type of device the conducting state of the glass is permanently, although reversibly, changed by the application of the switching voltage, which must be maintained for a time measured in milliseconds. The switch will then move to its low resistance state and remain in this state even though the current and voltage are removed. The device can then form part of a memory store. The low resistance state may be changed back by applying a current of around an ampere for about 100 microseconds. This then restores the device to its high impedance state. Fig. 5(b) indicates schematically the action of this device. To read the state of the memory one applies a voltage from a source with a medium impedance. In the low impedance state the fraction of the voltage dropped across the switch is negligible and so a voltage sensor across the switch can register zero. In the off state the full voltage appears across the switch so the voltage sensor indicates a unity value. This 'read' process can be made extremely rapid so that at present the memory could find applications in a 'read mostly' or 'read only' type of memory store. Ovshinsky used a material with a composition of  $Te_{4.8}As_{3.0}Si_{1.2}Ge_{1.0}$  for his switches and reduced the arsenic content to around 5% for the memory devices. However, it is not known or, at least, reported what determines whether a device will be a memory, a threshold switch, both or neither!

The chalcogenide glasses used for these devices are covalent amorphous semiconductors and so exhibit a negative temperature coefficient for their resistivity. It is natural to think of the switching as possibly being caused by thermal runaway. Indeed at the Cambridge conference evidence was presented that showed the thermal runaway model fitted several experimental facts. It may, at first sight, be thought that such a mechanism could not account for switching in the subnanosecond speeds that are observed with these devices. However, although the speed of switching is fast, there is a delay of the order of a microsecond before the actual switching occurs. Moreover, it is known that a device with a negative temperature coefficient of resistivity will form a current-controlled negative resistance and in these types of negative resistances the current tends to flow in filaments. This bit of physics can be qualitatively understood by considering a set of parallel and equal negative value resistors. If one resistor takes slightly more than its fair share of current then its resistance falls and it will take more current and so on until all the current is going into the one resistor. Filament formation can imply that the heat required for increasing the conductivity in the filament need only be very small. However, although the thermal runaway theory fits many facts, Professor H. Fritzsche maintained that even with filament formation there was not enough heat for the filament to reach the

required temperature to explain its low resistance, as measured experimentally. It may be that heat causes some slight reversible structural change so that the conduction is no longer intrinsic. Professor H. K. Henisch in another paper suggested that electrical charge effects of the carriers could account for the switching with the current maintaining a plasma in the switch when in the on state. The neutral plasma of charge carriers could imply a high current but low voltage while recombination of the holes and electrons would imply that a minimum sustaining current was required for the plasma. Elsewhere Professor Sir Nevill Mott<sup>4,5</sup> has suggested that tunnelling of charge carriers through Schottky barriers set up at the electrodes could result in switching. It is safe to say that at present there is no definitive theory on the switching effects in these glasses and indeed it may be a combination of effects is required to explain the facts.

The memory type of device is almost certainly connected with a structural change of the amorphous material caused by heating in a filament. A very beautiful bit of evidence for this theory was given by Dr. C. Sie of Energy Conversion Devices in a film shown to the conference delegates. In a particular material ( $As_{55}Te_{35}Ge_{10}$ ) the switching time is very slow and Dr. Sie filmed the device under a microscope and showed the filament growing from the anode towards the cathode contact of the device. As the filament moved towards the cathode the threshold voltage for current switching decreased until, when the filament had fully formed, the threshold voltage was zero and the device was perfectly ohmic in a low resistance state. A microprobe analysis of the composition of the filament showed that it had changed its composition from  $As_{55}Te_{35}Ge_{10}$  to  $As_{38}Te_{58}Ge_4$ . Temperature analysis with a micro-radiometer showed that the material heated as the current initially started but that as the filament passed under the radiometer the temperature dropped. The velocity of propagation of these filaments could vary depending on material. Rough orders of magnitude suggested the variation was between 100 cm/sec to  $10^{-2}$  cm/sec.

**Conclusions**

It is clear that much technical, technological, and theoretical work remains to be done with many elegant experiments along the way. Some elementary ideas are clear for the amorphous semiconductors but the rigorous theory on which to base quantitative work is lacking. For the practical devices the mechanisms by which they work are only just emerging. The memory device is almost certainly made possible by a change of phase along

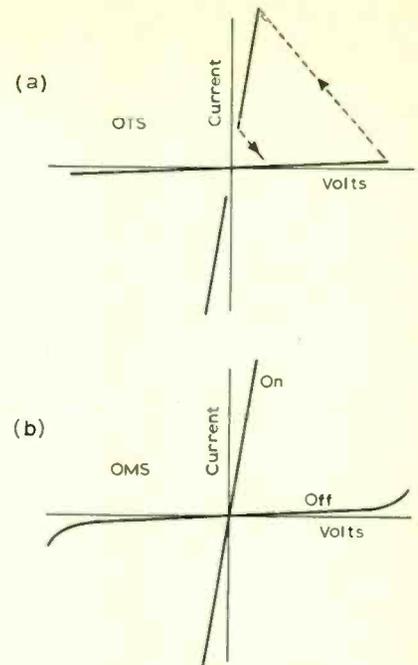


Fig. 5. Ovonic switches (a) the ovonic threshold switch: O.T.S. (b) the ovonic memory switch: O.M.S.

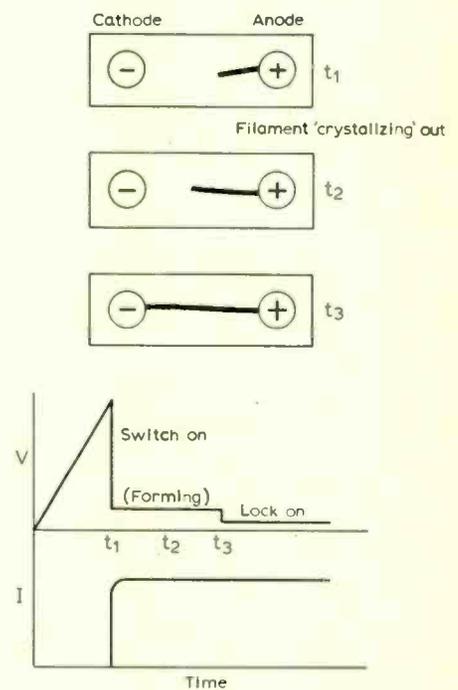


Fig. 6. Schematic of filament formation in memory device. When the voltage exceeds the threshold the current increases (switches on) but the filament takes time to form travelling from the anode. When fully formed the device resistance is lowest. This is termed locked on.

a filament; this change being induced by heating. The switching device is possibly tied up with a number of effects such as space charge, heating and contact conditions. But as one speaker at the conference said 'although we look through a glass, we look through a glass darkly'. This leaves lots of fascinating questions to be answered. Indeed switching and memory devices may not be the only uses that more knowledge about these materials could bring. It may be possible to develop specific glasses to absorb

harmful wavelengths of radiation or indeed respond electrically to other wavelengths of light that existing technology does not permit. The biggest question for the industrialist is perhaps whether it will be worth the cost. The Cambridge conference probably ensured that firms with a current programme will maintain a holding programme of work. Then at least they have a hand in the field to pluck the flowers if they suddenly bloom in the spring. The lack of technological know-how is unlikely to encourage many new firms to undertake their own research.

**Acknowledgements**

The author is indebted to Professor Sir Nevill Mott for allowing him to attend the conference at the last moment in spite of a full house.

**References**

1. A. D. Pearson, J. F. Dewald, W. R. Northover and W. F. Peck Jr. "Advances in Glass Technology" (Plenum Press Inc., New York) 1962, p.357.
2. S. R. Ovshinsky, "Reversible electrical phenomena in disordered structures", *Phys. Rev. Letters*, Vol. 21, pp.1450-53, 1968.
3. M. H. Cohen, H. Fritzsche, and S. R. Ovshinsky, "A simple band model for amorphous semiconducting alloys", *Phys. Rev. Letters*, Vol. 22, pp.1065-1068, 1969.
4. N. F. Mott, "Charge transport in non-crystalline semiconductors", *Festkorperprobleme*, Vol. 9, pp.22-45, 1969.
5. N. F. Mott, "Conduction and switching in non-crystalline materials," *Contemp. Phys.*, Vol. 10, pp.125-138, 1969.
6. C. F. Drake, I. F. Scanlan and A. Engle, "Electrical switching phenomena in transition metal glasses under the influence of high fields", *Phys. Stat. Sol.* Vol. 32, pp.193-208, 1969.

**Amateur h.f. band**


For many years, amateurs in Europe and Africa have been encouraged by the I.A.R.U. Region 1 Bureau to observe voluntarily an international "band plan" on the h.f. bands in order to reduce mutual interference between amateurs using different modes. While, at times, infringements of the plan can be heard (particularly the intrusion of 'phone operation into the c.w. segments), the plan has undoubtedly played a major role in maintaining orderly operation. The band plan was modified slightly at the Brussels I.A.R.U. Conference a few months ago, and is now as follows: 3.5 to 3.6MHz c.w. only; 3.6 to 3.8 c.w. and 'phone; 7.0 to 7.04 c.w. only; 7.04 to 7.1 c.w. and 'phone; 14.0 to 14.1 c.w. only; 14.1 to 14.35 c.w. and 'phone; 21.0 to 21.15 c.w. only; 21.15 to 21.45 c.w. and 'phone; 28.0 to 28.2 c.w. only; and 28.2 to 29.7 c.w. and 'phone. Radio teleprinter operation is recommended around 14.09 MHz.

**Application Notes**

**Circuitry selected from device manufacturers' literature**

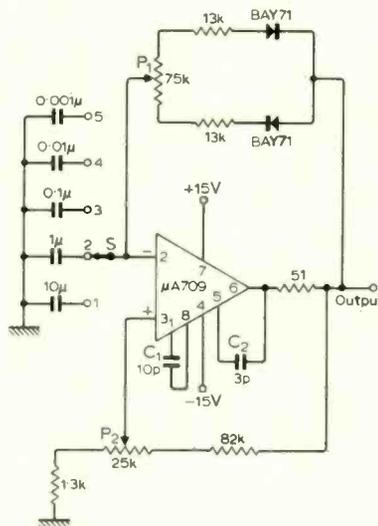**Square-wave generator**


The circuit given below operates over the following five frequency ranges: 2-20Hz, 20-200Hz, 200Hz-2kHz, 2-20kHz, and > 20kHz.  $P_2$  is a coarse frequency control and  $P_1$  is a fine frequency control



which operates by varying the hysteresis cycle. Extracted from "The Application of Linear Microcircuits", Vol.1, SGS Ltd.

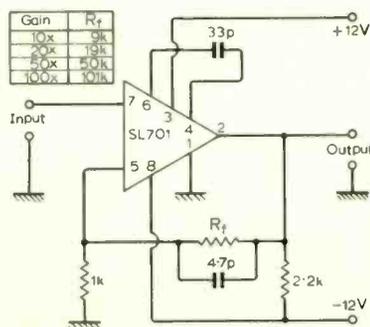**General-Purpose Amplifier**


The gain of this amplifier is set by the resistor  $R_f$ .  $10, R_f = 9k \Omega$ ;  $\times 20, R_f = 19k \Omega$ ;  $\times 50, R_f =$



$50k \Omega, \times 100, R_f = 101k \Omega$  Typical drift is quoted as  $15\mu V/^\circ C$ . Extracted from Plessey Technical Communication No. 7.

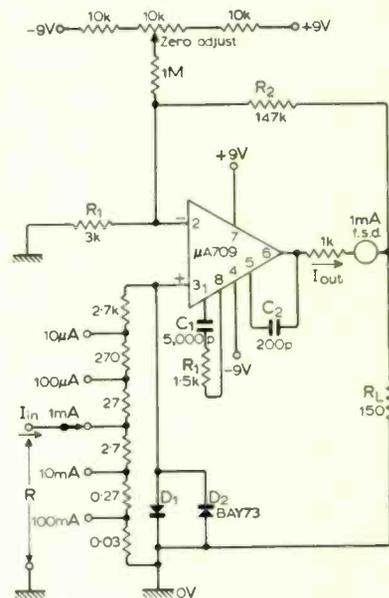**D.C. microammeter**

Below is the circuit of a low voltage-drop microammeter which will give an accuracy of 1% at ambient temperature if a good quality meter and accurate resistor values are used. Variation



of accuracy with temperature is given as  $0.2\% / ^\circ C$ . Extracted from: "The Application of Linear Microcircuits", Vol.1, SGS Ltd.

# Magnetoresistance and its Application

## Mean-square ammeter and d.c. transformer

by B. E. Jones\*, M.Sc., Ph.D.

The magnetoresistance effect and the related Hall effect displayed by a semiconductor under a magnetic field have become of interest in recent years with the advent of extremely high-mobility materials.<sup>1,2</sup> Both effects arise from the action of the externally-applied magnetic field in producing a sideways deflection of the mobile carriers taking part in the conduction process.

The magnetoresistance effect is a phenomenon in which the resistivity of a semiconductor material is considerably increased by a magnetic field whenever the carrier mobility has a large value, for example in indium antimonide or indium arsenide intermetallic compound semiconductors. It has been shown that the total resistance of a rectangular specimen of such a semiconductor shows a square-law increase at small magnetic fields (up to about 0.3 T†) and a linear increase at high magnetic fields (Fig. 1 and Table 1). The magnitude and characteristics of the effect depend largely on the geometry as well as the material itself.<sup>3</sup> For suitably designed components the typical dependence of  $R_B/R_0$  on magnetic flux density  $B$  applies to frequencies well into the gigahertz range. Wafer-shaped configurations exhibit their greatest sensitivity with the field perpendicular to the plane surface.

The electrical properties of a semiconductor are usually sensitive to temperature, and the magnetoresistance effect is no exception. Resistivity usually decreases with temperature and the larger the semiconductor surface area, the smaller the temperature coefficient. In Table 1, one device has a temperature coefficient of  $-1.8\%/^{\circ}\text{C}$ , while a slightly bigger and less sensitive device has a smaller temperature coefficient of  $-0.12\%/^{\circ}\text{C}$ , both figures at  $B = 0$ , and temperature  $25^{\circ}\text{C}$  (these coefficients increase with  $B$ ).

The linear magnetoresistance effect at relatively high magnetic fields has been used to produce a multiplying action, particularly for power measurement from direct current to microwaves.<sup>3</sup> A transducer for displacement measurement based on the effect gave a large output of 5 V d.c. at  $500\ \mu\text{m}$  displacement, without using electronic amplifiers, over a working temperature range  $-320^{\circ}\text{F}$  to  $+200^{\circ}\text{F}$ .<sup>2</sup> A magnetoresistance can obviously be used for magnetic-field measurement, particularly weak fields, and has been employed as a modulator of d.c. currents and voltages, as a contactless variable resistor and been applied to a brushless d.c. motor.<sup>1</sup>

Two further applications of magnetoresistances are described below. In the first case use is made of the square-law characteristic at low values of magnetic-flux density, to produce a simple clip-on mean-square ammeter (0–25 A) of very low input impedance suitable for measuring practically any current waveform. In the

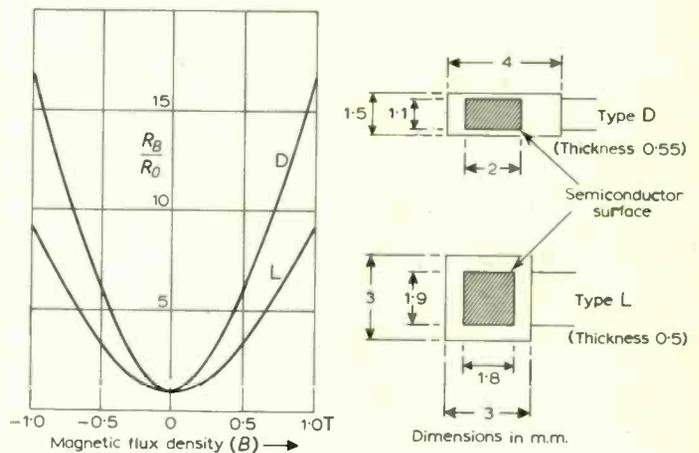


Fig. 1. Magnetoresistance relation  $R_B/R_0$  as a function of the magnetic flux density  $B$  for two commercial devices.

second case, magnetoresistance is used as a magnetic-flux error detector in a feedback circuit to provide a simple d.c. transformer (0–1 A) for clip-on purposes.

### Mean-square ammeter

The circuit used to test the mean-square ammeter scheme employing magnetoresistance is shown in Fig. 2. A gap is cut in one half of the small ferrite ring sufficient to take magnetoresistance  $R_1$  mounted with silicon grease on a thin copper plate (the airgap also linearises the relation between magnetic flux and cable current; actually flux density in the ring

$$B = \frac{1.26 I}{(l_i/\mu + l_g)} \mu T,$$

where  $I$  is cable current,  $l_i$  and  $l_g$  are mean length of magnetic circuit and airgap width respectively in metres, and  $\mu$  is the ferrite magnetic relative permeability). To allow temperature compensation a second magnetoresistance  $R_2$  is similarly mounted on the plate, but situated outside the magnetic circuit. To provide a meter deflection linearly related to change in  $R_1$  caused by flux changes, both  $R_1$  and  $R_2$  are connected in a bridge circuit whose other two arms are current sources and the choice of out-of-balance detector (resistance  $R_d$ ) depends on accuracy and ruggedness required. The current sources are provided by two silicon transistors in a long-tailed pair arrangement with a well-defined voltage on the bases. With flux at zero ( $I = 0$ ), potentiometer  $P_1$  can be adjusted to balance the bridge.

For low flux densities  $R_1 = R_0 + KI^2$ , and for the case  $I = i \sin \omega t$ , it has been shown<sup>4</sup> that, considering only first-order terms, the mean detector current is given by the expression

$$I_d \approx \frac{KI_1}{R_d + R_2 + R_0} \frac{i^2}{2} \left[ 1 - \frac{3K}{2} \frac{i^2}{2(R_d + R_2 + R_0)} \right]$$

assuming  $I_1 = I_2 R_2 / R_0$ , where  $I_1$  and  $I_2$  are the collector currents of transistors  $T_{r1}$  and  $T_{r2}$  respectively. It is evident that the detector current is proportional to the mean-square current  $i^2/2$  in the

\*Electrical Engineering Laboratory of Manchester University

†T is the symbol of the tesla, the SI unit for magnetic flux density ( $= 10^4$  gauss)

Table 1

Characteristics of Magnetoresistance Elements

Type	$R_0$ at $25^{\circ}\text{C}$ ( $\Omega$ )	$R_B/R_0$ factor $B = \pm 0.3\ \text{T}$ , $25^{\circ}\text{C}$	Temp. coeff. at $B = 0$ , $25^{\circ}\text{C}$ ( $\%/^{\circ}\text{C}$ )
FP28D470	470	3	-1.8
FP17L100	100	1.9	-0.12

Note. The magnetoresistance elements are indium antimonide type made by Siemens & Halske A.G. and are obtainable in the U.K. from R. H. Cole Electronics Ltd., 7-15 Lansdowne Road, Croydon, CR9 2HB.

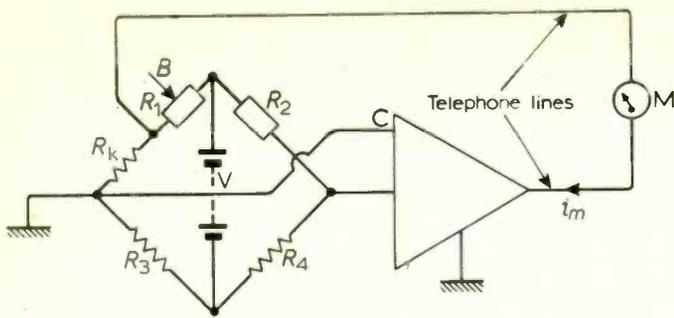


Fig. 2. Mean-square ammeter circuit.  $F_1$  = type A<sub>1</sub> manganese zinc ferrite (Ferroxcube toroid FX 1322) ( $i.d.$  = 6.35 mm,  $l_i$  = 2.76 cm,  $l_g$  = 0.59 mm,  $\mu_{min}$  = 100).  $T_{r1}$ ,  $T_{r2}$  = type C444 transistors (SGS Fairchild).  $R_1$ ,  $R_2$  = type FP28D470 magnetoresistances (see Fig. 1 and Table 1).

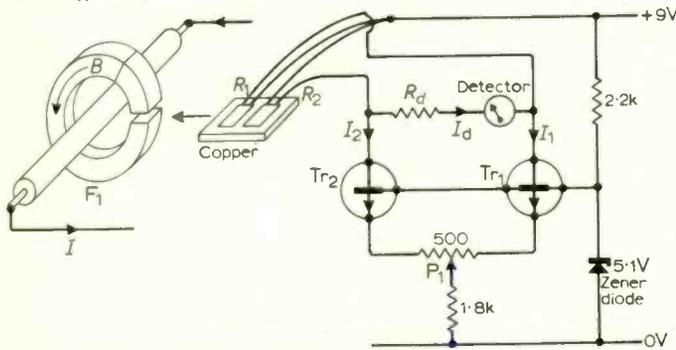


Fig. 3. Bridge containing compensating resistor  $R_k$ .

cable, provided the term after the minus sign in the expression for  $I_d$  is small. With  $R_2 \approx R_0 \approx 470 \Omega$ ,  $K \approx 0.04 \Omega/A^2$ , so that for 2% accuracy when  $i^2/2 = 25 A$ ,  $R_d$  should have a value of about 900  $\Omega$  and  $I_d \approx 15 \mu A$  if  $I_1 \approx 1 mA$  (this value for  $I_1$  restricts magnetoresistance dissipation to about 1/2 mW).

To check accuracy and linearity of the magnetic circuit a high impedance d.c. galvanometer ( $R_d = 12 k\Omega$ ,  $2 \mu A$  f.s.d.) was used as detector in the circuit of Fig. 2. There was less than 1% inaccuracy in the overall square-law characteristic for full-scale deflection when  $I_{r.m.s.} = 25 A$  at 50 Hz (the maximum flux density was only 0.07 T). The impedance of the ammeter is inductive, given by that of a single-turn on the magnetic core. With the core of Fig. 2, at 50 Hz,  $X_m \approx 6 \mu\Omega$ .

**Alternative arrangement**

If it was desired to use a cheap standard rugged moving-coil meter as indicator at some distance from the point of measurement, the arrangement of Fig. 3 could be used. In this,  $R_k$  is a fixed compensating resistor in the branch of the bridge which contains the active element  $R_1$ ;  $R_k$  is also connected to the output circuit of the d.c. amplifier. The input of this amplifier is connected to the output of the bridge and the amplifier output current  $i_m$  passes through  $R_k$ .

When a cable current ( $I$ ) is present, the bridge is unbalanced, a voltage  $e$  is produced at the amplifier input and generates the current  $i_m$ . This current causes a compensating voltage at the terminals of  $R_k$  which is opposed to the error voltage generated by the change of resistance  $R_1$ . The current  $i_m$  increases until these two voltages balance. It has been shown<sup>4</sup> that

$$i_m = VKI^2/2R_k(R_k + R_0)$$

provided

$$[2(R_k + R_0) + KI^2]/A \ll R_k(R_k + R_0)$$

$R_1 = R_0 + KI^2$ ,  $V$  is the battery voltage across the bridge and  $A = i_m/e$  is the amplifier gain. Thus  $i_m$  is independent of  $A$  and linearly related to  $I^2$  so that a millimeter  $M$  will indicate the mean-square of the cable current. It is clear that  $R_k$  can be used as a range change control.

**D.C. transformer**

The alternating current transformer employs a large number of turns to keep small the magnetizing current required to produce the magnetic flux that opposes the flux produced by the current to be

measured. Thus overall the current ratio of the transformer is accurately defined in terms of the turns ratio of the windings. The principle of minimum flux change has the advantage of operating the magnetic core material in a small fixed region of its magnetic characteristic, so that nonlinearity in this characteristic has negligible effect on performance. The principle has been used for direct-current measurement by employing magnetoresistance to measure d.c. flux.

The basic circuit employed to test the idea is shown in Fig. 4. A square ferromagnetic circuit containing an airgap and winding surrounds the insulated cable whose direct current is to be measured. Two magnetoresistances ( $R_e'$  and  $R_e$ ) are attached with silicon grease to a thin copper plate to equalize their temperatures. They are connected in series and driven by a diode low-voltage source ( $V_d$ ) to restrict dissipation. The active resistance  $R_e'$  is in the airgap, while the temperature compensating resistance  $R_e$  remains outside the gap. Because of the square-law characteristic of  $R_e'$  it is necessary to operate it at a constant bias flux density ( $B_k$ ), and this is produced by a stable fixed current ( $I_k$ ) in the feedback winding (W).

If a direct current ( $I$ ) occurs in the cable, a change of flux will occur in the magnetic circuit,  $R_e'$  resistance will change, as will the voltage ( $V$ ) at the connecting point of  $R_e'$  and  $R_e$ . This voltage on being amplified by  $A$  and applied to resistance  $R_m$ , will produce a current ( $I_f$ ) in the feedback winding (W) so as to produce a flux in the magnetic circuit to oppose the original flux produced by  $I$ . If the gain in the flux detector circuit and the voltage gain ( $A$ ) are high, then the resultant flux change in the magnetic circuit will be very small, and  $I$  and  $I_f$  will be simply connected by the expression  $I = NI_f$ , where  $N$  is the number of turns of the feedback winding. The current  $I_f$  can be measured by means of a d.c. ammeter in series with the output of the amplifier.

The integrated amplifier has high gain (about 45,000) and produces a noise voltage of about 0.5  $\mu V$  referred to its input, so it is necessary to use a 0.50  $\mu A$  meter in a low-pass filter circuit. When  $I = 0$ , zero meter deflection is obtained by adjustment of a stable offset current  $I_0$ .

It has been shown<sup>4</sup> that  $I$  and  $I_f$  are in fact related by the expression


$$\frac{I_f}{I} = \frac{1}{N[1 + 1/K]}$$

where

$$K = \frac{NAR_ePB_k}{V_dR_mR_e'(l_i/\mu + l_g) \times 397}$$

the open-loop gain,  $P$  is the dissipation in  $R_e'$ ,  $l_i$  and  $l_g$  are mean magnetic-circuit length and airgap width respectively, and  $\mu$  is the ferrite magnetic relative permeability. With values  $N = 500$ ,  $A \approx 45,000$ ,  $R_e \approx R_e' \approx 100 \Omega$ ,  $P \approx 1$  mW,  $B_k \approx 0.06$  T,  $V_d \approx 0.7$  V,  $R_m \approx 500 \Omega$ ,  $l_i = 18.7$  cm,  $l_g = 0.89$  mm and  $\mu \approx 1,000$ ,  $K$  has a value of about 10.

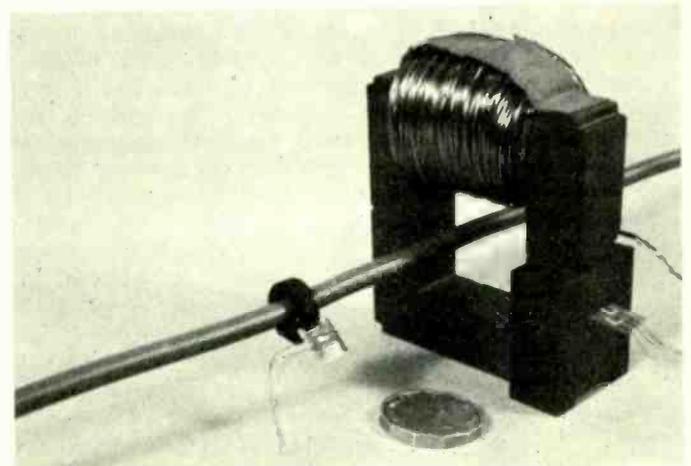The amplifier gain fall-off is arranged to start at about 20 Hz



The magnetic circuits for the mean-square ammeter (left) and the d.c. transformer (right) are shown here. The magnetoresistances are also visible, but in operation one would be in the air gap.

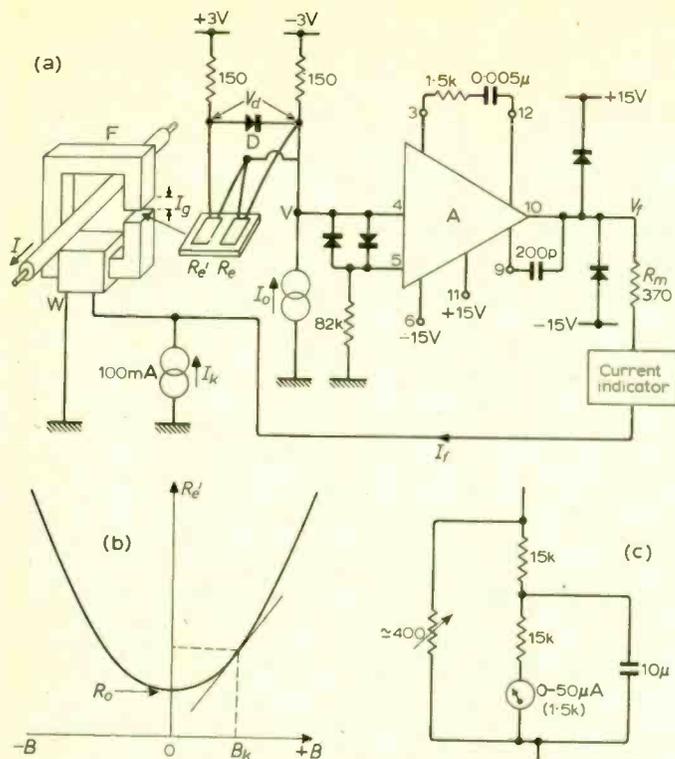


Fig. 4. Direct-current transformer. The basic circuit diagram (a) has  $R_{e'}$ ,  $R_e$  = type FP17L100 magnetoresistances (see Fig. 1 and Table 1). All diodes = silicon, type ZS72 (Ferranti).  $F$  = manganese-zinc ferrite, grade A5 ( $l_g = 0.89$  mm,  $l_l = 18.7$  cm,  $\mu = 1,000$  (Ferroxcube U-cores FX1795)).  $W = 500$  turn (N) winding of 24 s.w.g.  $A = 45,000 \pm 50\%$  (MC1709CP integrated amplifier, Motorola).

to reduce noise and avoid instability problems. With full-scale deflection on the meter when  $I = 1$  A, linearity is much better than 1% above  $I = 0.2$  A; below this value amplifier nonlinearity at low signal levels has some effect. Wide variation in the cable diameter and position of cables in the magnetic circuit has no noticeable effect on readings. The input impedance of the transformer is very low by virtue of the effective high reluctance of the magnetic circuit. The current indicator could be at a considerable distance from the rest of the circuits.

**Temperature effects**

In both the experimental circuits utilizing magnetoresistances described above, the limit to current sensitivity and measurement accuracy is primarily fixed by drift, due to amplifier drift and magnetoresistance temperature dependence. Low temperature coefficient magnetoresistances, operated with minimum self-heating in compensating balanced arrangements should be used, and if necessary further temperature compensation can be achieved by a series thermistor or a parallel metal resistor. Amplifier drift can be reduced by using a d.c. chopper amplifier arrangement.

The experimental circuits described indicate two further useful applications of magnetoresistances. Both circuits are relatively simple and are useful for measuring currents in insulated cables by clipping a measuring head on to the cable. The mean-square ammeter is suitable for measuring practically any current waveform, while the direct-current transformer will measure low-frequency currents (for example, less than 10 Hz) where ordinary current transformers are inadequate.

**REFERENCES**

<sup>1</sup> Weiss, H.; "Die feldplatte—ein neues magnetisch steuerbares halbleiterbauelement", *Solid State Electronics*, 1966, Vol. 9, pp. 443-451.  
<sup>2</sup> Yuan, L. T.; "Magnetoresistive transducer", *Solid State Electronics*, 1966, Vol. 9, pp. 497-502.  
<sup>3</sup> Kataoka, S.; "Multiplying action of the magnetoresistance effect in semiconductors and its application to power measurements", *Proc. I.E.E.*, 1964, Vol. III, No. 11, pp. 1937-1947.  
<sup>4</sup> Jones, B. E.; Ph.D. thesis, Manchester University, 1969.

# Announcements

"U.H.F./S.H.F. Techniques" is the title of a course of six evening lectures to be held at Norwood Technical College, Knight's Hill, London S.E.27, commencing February 3rd. Fee 15s.

**M.E.C.-Electrosil Merger.** Miniature Electronic Components Ltd, of Woking, has been merged with the Electrosil Group and all future enquiries and orders should be placed with Electrosil Ltd, P.O. Box 37, Pallion, Sunderland, Co. Durham.

**Compat Telecommunications**, a wholly owned subsidiary of Compat Corporation of New York, has established offices in Woolmead House, Woolmead, Farnham, Surrey, to handle all of the business of its parent company outside the U.S.A. Compat are manufacturers of computer-controlled data communications equipment.

**Radiatron Components Ltd** has been formed to operate in association with Radiatron Ltd and to deal with a wide range of components. It will handle the Elma range of collet knobs, stud switches, Elmaset instrument cases and readout counters. Both companies will operate from 76 Crown Road, Twickenham, Middx.

**Racal Electronics and Kelvin Hughes** have agreed to work in partnership on a range of h.f., s.s.b. marine radiotelephones. Racal have a contract from Kelvin Hughes for the design and manufacture; Kelvin Hughes the world-wide marketing of the products.

**Industrial Control Systems Ltd** have moved to 78-90 Clarke Road, Northampton. (Tel: Northampton 32417).

The Crawley offices and laboratories of **Pye Unicam Ltd** have been transferred to the company's head office at York Street, Cambridge, CB1 2PX.

**Microwave & Electronic Systems Ltd**, of Midlothian, Scotland, has moved its sales office to 66 Tilehurst Road, Reading, Berks. (Tel: Reading 581937/8.)

G. A. Stanley Palmer Ltd have been appointed sole **U.K. agents** for the range of miniature electrolytic aluminium capacitors manufactured by the International Electronics Corporation of Long Island, N.Y.

Hayden Laboratories Ltd, East House, Chiltern Avenue, Amersham, Bucks, have been appointed exclusive U.K. agents for **Spinner GmbH**, of Munich, W. Germany, manufacturers of radio frequency connectors, directional couplers and other specialized items associated with radio-frequency cables and waveguides.

Nobel Electronics, of Welling, Kent has signed a three-year agreement as sole **U.K. and European agents** for Plastic Capacitors Ltd, Maydown, Co. Londonderry, N. Ireland.

Montclair Electronics Inc, of New York, have appointed G. A. Stanley Palmer Ltd as sole U.K. agents for a range of **magnetic reed relays** and switches from the General Reed Company.

# Low-distortion Bias and Erase Oscillator

## Evolving a current switching design to give a predictable and stable output level and with no trimming requirement for low distortion

by D. Griffiths, Ph.D.

The design of a good bias and erase oscillator for a tape recorder is not easy. For stable biasing a constant output voltage is required, yet any limiting action in the oscillator must not be allowed to distort the sine-wave drive since this would increase the background tape noise. The circuit should be efficient so that the least expensive semiconductors can be used and, ideally, it ought to be designed to work straight off without any complex setting-up procedures, especially those required to minimize the distortion.

The oscillator was required to operate a Ferrograph Series 6 tape deck but using the procedure outlined below it should be possible to alter the component values to make it suit almost any other recorder.

### Specification

The Ferrograph handbook gives the inductance of the two-track FE16 erase head as 1.5mH (per track), requiring 80mA at 27-30V and 68kHz; the record head only requires about 5mA at 15V. The power required from the drive circuit is fortunately not  $0.08 \times 30 = 2.4$  watt but depends only on the losses in the heads; a perfect inductor can not have a net dissipation of energy. Since the erase head has a mu-metal core it is only useful to measure its loss under actual working conditions, for it is quite hopeless to try to extrapolate data on iron-cored inductors.

In the absence of a suitable measuring bridge the losses in this head were assessed by observing their damping effect on a tuned circuit resonating at 68kHz with 30V across it.

The inductance of this test circuit should be less than, say, one fifth of that of the tape head so that the resonant frequency is not too greatly changed by the extra head inductance, but the waveform need only be roughly sinusoidal.

It was found that each winding of the FE16 head introduced the same damping effect on the test circuit as did a 3.3k $\Omega$  resistor. Under operating conditions in a parallel resonant circuit the head could thus be thought of as a perfect 1.5mH inductor in parallel with a 3.3k $\Omega$

resistor, resulting in power dissipation of about 0.25 watt.

At this point one has to face firmly the problem of ensuring a constant output voltage. The necessary limiting action can use the "curvature of the characteristics" of the active circuit elements but designability is sacrificed and well stabilized power supplies are required to maintain operation in the critical region. Some form of a.g.c. could be employed but amplitude overshoot at switch on must be avoided. This is also a problem with thermistor stabilization. The alternative scheme chosen here is to send constant current pulses of a suitable shape through a tuned circuit coupled to the tape heads and rely on a reasonable  $Q$  value to reduce the harmonics sufficiently. This filtering is more effective than one might imagine since the harmonic amplitudes decrease with increasing order, while the attenuation of the tuned circuit also rapidly increases with rising frequency. With transistors or valves it is a simple matter to generate well enough regulated driving pulses for this application but the feasibility of the scheme depends entirely on maintaining a good  $Q$  in the filter despite the loading of the losses in the tape heads.

### Current switching

Ideally the reader should now turn up *Wireless World* for November and December 1962 to an article by R. C. Foss and M. F. Sizmur which gives an admirably lucid account of current

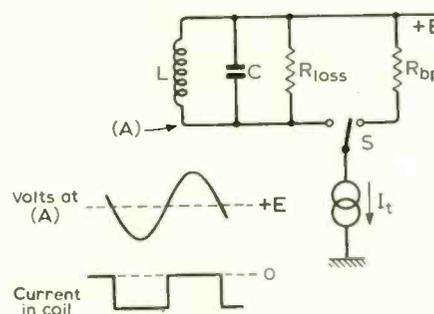


Fig. 1. Principle of a current switched LC oscillator.

switching sine wave oscillators. Their first diagram is reproduced here as Fig. 1 and is a good starting point. When the current generator is first connected to the tuned circuit the voltage at point (A) will swing below  $+E$  with a period governed by the resonant frequency. The size of this swing depends on the losses in the LC circuit, as well as the magnitude of the drive current. Eventually the voltage at (A) swings back up towards  $+E$ , even with the constant current generator still connected. When the voltage across the resonant circuit is zero (i.e. when the point (A) is at  $+E$  again) we choose to switch the current supply into a bypass resistor  $R_{bp}$ . The point (A) then continues its upward voltage swing and but for the losses this would take it as far positive above  $+E$  as it had been below  $+E$  half a cycle earlier; the current generator has infinite output impedance and cannot load the LC circuit. When the voltage at (A) eventually falls to  $+E$  again we reconnect the current supply to the tuned circuit and the cycle repeats.

As a step to a practical realization Fig. 2 shows the next stage of complication and is also from Foss & Sizmur's article. Here the tail current  $I_t$  is alternately switched between the transistor and the diode by the action of the voltage induced in the base winding  $N_b$  which is coupled to the tuned circuit. As indicated, a phase reversing connection is necessary so that when the point (A) is below  $+E$  the base end of  $N_b$  is positive with respect to ground and the transistor conducts as required. But for this base winding voltage and

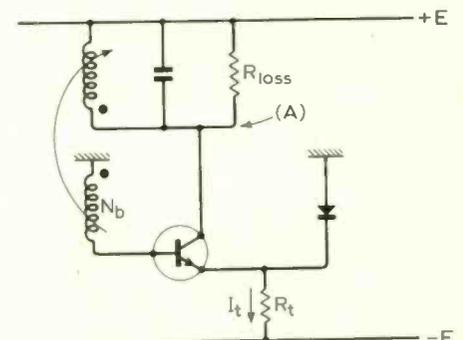


Fig. 2. Tail current is switched between the transistor and the diode.

$V_{be}$ , the tail current driving the LC resonator would be  $E/R_t$ . The tuned circuit is only lightly damped by the transistor as the collector is a high impedance point.

In Fig. 3 the diode is replaced by another transistor with its collector connected to a similar LCR circuit as that on the left hand side. Except for the brief instant of current changeover, the tail current flows only through either  $Tr_1$  or  $Tr_2$ . Whichever transistor is off will have its collector above  $+E$  while the other collector is equally below  $+E$ . That is, the voltages at (A) and (B) see-saw about the positive supply rail.

It is now only a small step to the final arrangement shown in Fig. 4. A single tuning capacitor is employed across a centre tapped inductor which has an additional winding to provide the required bias and erase voltages. As only a positive supply rail was available, the bottom of the tail resistor is connected to ground and the centre tap of the base winding supplied with a suitable potential stabilized with a zener diode. A pair of plastic encapsulated transistors is used for each switch to give the collector dissipation required when both erase heads are simultaneously connected in two channel operation. The 15Ω emitter resistors help to equalize the current in each pair and are useful inspection points at which to observe the individual current waveforms. The 2.2kΩ base resistors are a personal whim to reduce possible excessive base currents when trying out the prototype.

We choose to make the reference voltage defining the tail current about 2.5V above common. There are two reasons for using such a small value. First, that the collector voltages can have a large excursion which will entail a lower step-up ratio to achieve the desired output volts and hence a lower reflected loss from the heads, giving a better Q factor in the filter. The second reason is connected with reducing the output distortion, as discussed later.

To see if the negative going excursions are bottoming the transistors one does not check the voltage waveform at the collectors (!) since the flywheel effect of the high Q tuned circuit dominates the response; it is more useful to examine the tail voltage across  $R_t$  as shown in Fig. 5 and look for the 'dents' indicated. It must be remembered that during the off half cycle the transistor experiences a maximum collector voltage equal to the supply plus the amplitude of the downward swing. 12V r.m.s. is about the maximum reasonable collector excursion with the circuit values shown in Fig. 4. The maximum collector voltage is thus about  $22 + (12 \times 1.4)$  V. Even allowing for a peak emitter voltage of 3V (see Fig. 5), this uncomfortably exceeds the maximum recommended  $V_{ce} = 30$ V of the 2N3704 transistors used in the prototype.

If the tail current is assumed to be constant during each cycle, the collector dissipation can be easily calculated once

the mean collector-emitter voltage is known over the conducting half cycle. Since the average value of a half-sine wave is 0.64 times its peak value and if the collector peak swing is  $12 \times \sqrt{2}$  volts, then the collectors are on average  $12 \times \sqrt{2} \times 0.64 = 11$ V below 22V when conducting, i.e. 11V. When operating, an Avo indicated 2.6V d.c. across the tail resistor, giving a tail current of 52mA. On average,  $V_{ce} = 11 - 2.6 = 8.4$ V and if the current is equally shared between each pair of transistors, the mean collector dissipation is  $8.4 \times 0.052 \times 0.5 \times 0.5 \approx 110$ mW, with the second factor of 0.5 arising from the on-off time ratio.

If the two erase tracks are in use together, the extra drive can be achieved by suitably reducing the tail resistor and there is still a reasonable margin of collector dissipation in hand. This circuit is not very efficient in terms of power consumption; the four transistors dissipate  $\approx 450$ mW to overcome a head loss of 250mW.

Although a good L/C ratio is needed to minimize losses in the tuned circuit primary, the maximum allowable primary inductance is set by the Q value which has to be maintained in spite of the damping effect of the tape head losses. With a 1:2 step-up ratio between primary and secondary the equivalent loss resistance of 3.3kΩ looks like 820Ω across the primary circuit. If the circuit

shows a Q value of  $Q_f$  at resonant frequency  $\omega_f$ , the dynamic resistance of the circuit is  $Q_f \omega_f L$ . Clearly, in this case, we need  $Q_f \omega_f L \leq 820\Omega$ .

Now how much  $Q_f$  is needed? Foss and Sizmur show that with square current pulses the ratio of the  $n^{\text{th}}$  harmonic voltage  $V_n$  to the fundamental  $V_1$  is given by:

$$\frac{V_n}{V_1} = \frac{1}{(n^2 - 1) \cdot Q_f}$$

As a square wave can only generate odd harmonics, the third order one will be the principal component and with  $Q = 10$  its amplitude will be 1.25% of the fundamental. Since it is planned to use something a little less brutal than square driving pulses, this Q value should suffice. For operation at 68kHz this fixes L at 0.25mH. A 30mm diameter ferrite pot core, Mullard LA 2202, was used (with a permeability of 63) giving 1mH for 60 turns. The primary was wound in bifilar fashion to give 30 turns centre-tapped, with 60 turns on the secondary. 28 s.w.g. enamelled copper wire was used for both windings. The working flux density in this application is in the region of 50-100 gauss.

The tuning capacitor has to be larger than the value required to tune the 0.25mH primary inductance to 68kHz since the inductance of the tape head is reflected into the resonant circuit with a magnitude reduced by the square of the

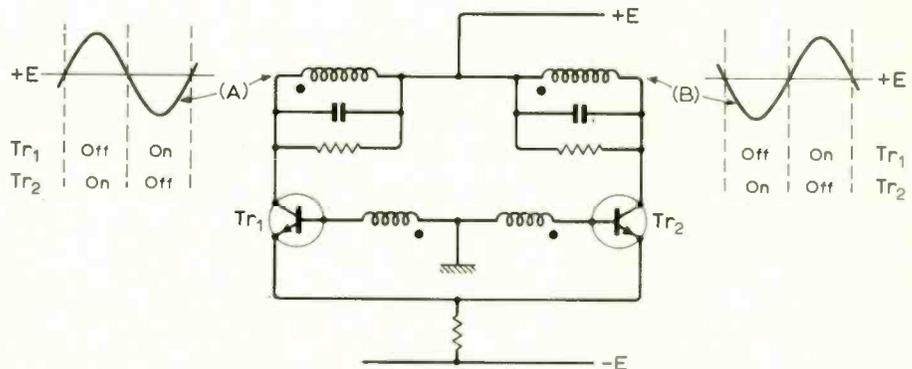


Fig. 3. Diode of Fig. 2 replaced by second transistor.

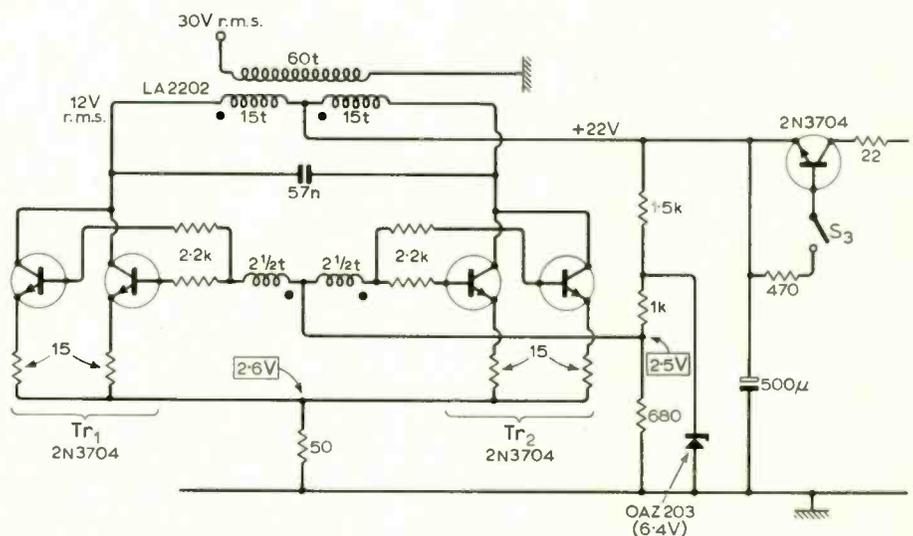


Fig. 4. Practical oscillator circuit.

step-down turns ratio; the total inductance is thus lowered since "inductors in parallel add like resistors in parallel". The secondary winding itself does not behave as a separate inductor since the induction in it is solely determined by that needed to balance the primary applied voltage. If the a.c. voltage across a coil does not depend on the rate of current change through it, then it does not have inductive properties.

Although Ferrograph quote a nominal erase inductance of 1.5mH, their suggested operating point of 80mA and 30V r.m.s. indicates a working inductance more like 0.9mH. As the Vinkor pot core was used without an adjuster, its inductance would be about 10% below nominal. Together with the slight contribution from the recording head, the total effective inductance would thus require about 51,000pF to tune it to 68kHz; in practice 10% tolerance 47,000pF and 10,000pF capacitors were used in parallel. If tuned filters are used as bias rejectors in the recording amplifiers, it will be important to keep the same bias frequency on single and two track operation. The extra inductance of the second head would lower the frequency further and a suitable extra tuning capacitor would have to be switched in.

It must be confessed that there is a little bit more complication in Fig. 4 than was admitted in earlier paragraphs and this concerns the shape of the current pulses. A square pulse with its sharp edges is obviously a rather poor approximation to the required output waveform and something a little more sinewave-like would ease the filtering problem. Now one cannot go to the limit and use an exactly sinewave current drive derived from the output waveform as there is then no limiting action, other than unintentional clipping and bottoming, etc. As a compromise we use a current pulse which is "partly square and partly sine". This is illustrated in Fig. 5 which shows the alternating voltage waveform across the 50Ω resistor, superimposed on the calculated d.c. level which could not be observed with the a.c. coupled scope available.

The squarewave part of the current waveform is developed by the long tail switching action; the sinewave part has a similar amplitude and is derived from the filtered output. This is achieved by giving the base windings a suitable number of turns so as to inject an appropriate amount of sinewave signal in series with the steady d.c. reference level. However, one must be careful in selecting the amplitude of this a.c. component otherwise the maximum reverse bias rating of the emitter-base junctions will be exceeded and extra protective diodes will be needed; the reverse emitter-base rating for the 2N3704 is given as 5 volts. It is important to recognize that the 'off' base junction sees both base windings in series generating the reverse voltage.

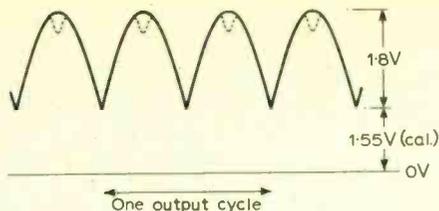


Fig. 5. Waveform across tail resistor. 'Dents' in the peaks indicate that the collectors are bottoming.

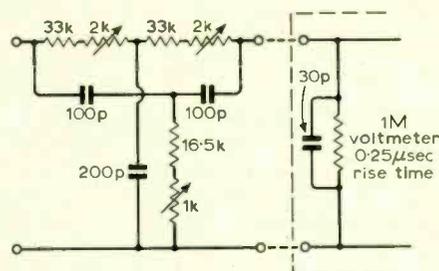


Fig. 7. Twin-T filter for 68kHz.

Fig. 6 shows the base of  $Tr_2 + V_b$  above  $V_{ref}$  derived from the zener diode. But for the  $V_{be}$  of this 'on' transistor and the voltage drop across its 15Ω emitter resistor the top of the tail resistor would also be  $+V_b$  above its d.c. level, taking the emitter of  $Tr_1$  with it (in the positive going direction). Meanwhile the voltage  $-V_b$  on the left hand base winding is holding the base of this transistor down  $-V_b$  below  $V_{ref}$ .

The 1.55V d.c. level in Fig. 5 assumes a  $V_{be}$  of 0.7V and allows for the two 15Ω resistors in parallel. The mean level of the a.c. component is  $1.8 \times 0.64 = 1.15V$  and thus an Avo on a d.c. range across the tail resistor should register  $(1.55 + 1.15) = 2.7V$ . This agrees well with the 2.6V observed. Evidently the steady current component is 32mA and the r.m.s. a.c. contribution is 25mA. In a Fourier representation of a square wave, the first harmonic has an amplitude of  $4/\pi$  times the amplitude of the square wave. Adding these two contributions to the voltage developed across the dynamic resistance seen in the primary circuit, one can estimate the loss resistance at 570Ω, corresponding to a working Q of 6—which is rather below the design figure.

The 500μF reservoir capacitor in Fig. 4 ensures that the oscillations decay smoothly when the circuit is switched off, thus helping to keep the tape heads demagnetized. The decay time is 0.5-1s. Switch  $S_3$  is controlled by the deck selector knob and operates via the series 2N3704 to minimize peak current through the switch contacts. The 22Ω resistor ensures that the initial charging current of the 500μF capacitor does not greatly exceed the maximum transistor current rating of 800mA.

**Performance**

After all that story, how does it do its job? The amplitude of the output

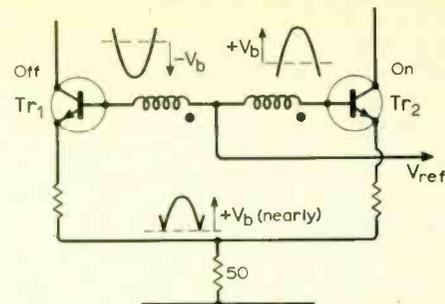


Fig. 6. How base-winding voltages add to build up reverse emitter-base voltage.

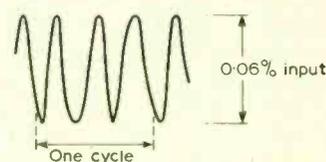


Fig. 8. Residual waveform at the base winding after passing through the twin-T filter.

slowly increases by 2-3% during the first half minute or so after switch on and this is probably due to heating of the transistors. A 40°C rise in junction temperature would lower  $V_{be}$  by about 90mV and thus increase the standing tail current enough to account for this observed rise in output. This effect could be reduced by increasing the tail voltage, remembering to add diodes to protect the base-emitter junctions from excessive reverse voltages arising from the necessary accompanying increase in sine wave drive. It is doubtful if the present small change in biasing could possibly be detected by its effect on the recorded signal. Changes in the supply voltage only slightly affect the oscillator output as might be expected; a 10% reduction in supply potential reduced a 28V output by just under 1.5%.

In the absence of a wave analyser, a simple passive twin-T rejector was used to filter out the fundamental to see what was left. Fig. 7 shows the filter circuit, and Fig. 8 shows a sketch of the residual signal from the 16V bias at a recording head on single channel operation. The amplitude of this residual is 0.06% of the input level and appears to be largely 3rd harmonic as expected. A sine wave input of  $3 \times 68kHz$  to the filter was attenuated by about 7dB as seen on the voltmeter, so it seems likely that these distortion products do not have an amplitude exceeding, say, 0.2% of the fundamental. This seems quite satisfactory and shows that the idea of using current pulses with the "edges rounded off" does indeed greatly reduce the output distortion while still retaining an adequate stability of output level. With a working Q of 6, square drive pulses would have given a 3rd harmonic component an order of magnitude greater at 2% of full output. Judged audibly, the tape hiss is very low and BASF double play tape on the Ferrograph appears to give a peak signal-to-hiss ratio in the upper fifties of decibels.

# Industrial Telemetry

## Some recent supervisory and control schemes

by R. E. Young

The early 1960s saw major developments take place in industrial telemetry<sup>1</sup>, largely as the result of the wide introduction of solid-state equipment and digital techniques. Rapid expansion then followed in step with the accelerating demand for these forms of automation backed by the extremely high reliability that they had been shown to give.


Much of this expansion occurred in the public utility field, authorities being strongly influenced in their policy by the almost overwhelming growth of "service" distribution networks, e.g. for electricity and water, and the increasing cost of manning them in the conventional way.

In general, the economy shown by the adoption of supervisory telemetry methods increases with the size and complexity of the project. Furthermore, the most favourable conditions for setting up such remote control systems are usually found with high concentrations of population and industry.

Thus in a large scale installation for electricity supply in the Far East control is exercised over the distribution network for the urban area of Kuala Lumpur<sup>2</sup>, three bulk supply stations and a total of fifteen substations being covered by the first phase of the scheme.

Recently commissioned, this is a classical digital supervisory system with time-division multiplexed telemetering and telecontrol, and employing the interrogation/reply, or responder, techniques which are used almost exclusively for this work<sup>3</sup>. With time-division operation, each information source is scanned in turn, and in these systems this is achieved by interrogating each source in terms of the unique (digital) address allocated to it.

Measurement or equivalent data points are grouped in blocks of addresses according to priority, so that the period which elapses between successive scans of a given point represents the "updating" time for its particular address block. With the exception of control functions, the various groups of addresses are interrogated in accordance with a pre-determined scan cycle, system programming being arranged to interlace these addresses within the overall scan period. Typically, an updating period of 11 seconds is realized for some 80

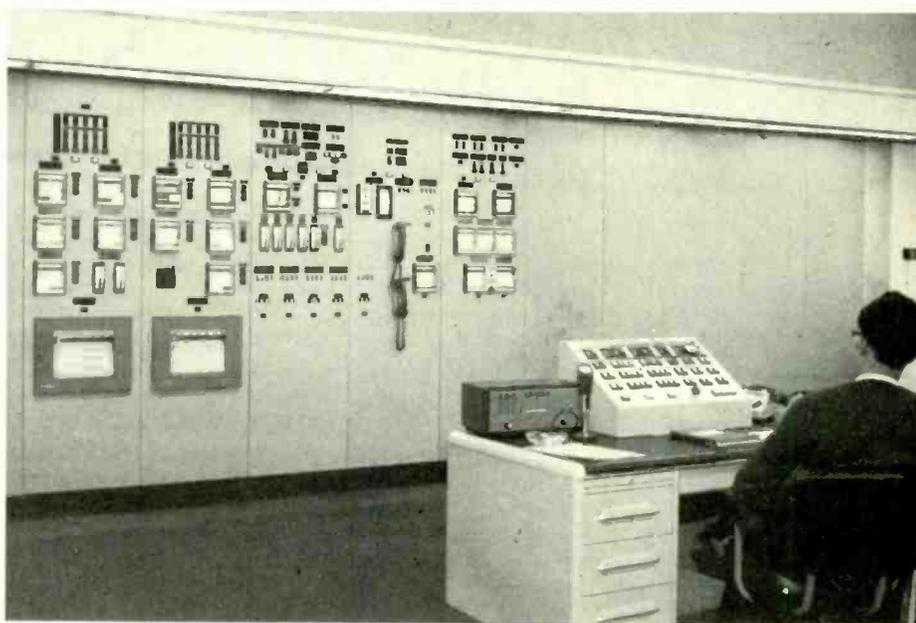

Control room at the Shell shore terminal at Bacton for their North Seas gas project.

measurement addresses; while alarm indication (e.g. for abnormal transformer oil temperature), carrying more urgency, is given a block updating time of 5 seconds.

Control instructions are also sent out by interlacing, but this is done by interrupting the routine scan cycle and thereby extending it for the additional time-sharing to take place. The same system word format is used for the control "way" addresses as for monitoring, and also in both cases the encoded replies sent back from the outstation follow the same pattern.


Obviously, measurements and monitoring information generally must be presented as far as is possible without any likelihood of there being any ambiguity or misinterpretation of the intelligence. It is of interest that the network electrical measurements, viz. voltage, power, reactive power and current, are displayed in analogue form on conventional d.c. moving-coil meters. This involves the use of an individual digital-analogue convertor for each meter as the incoming signals are handled digitally throughout the logic system. It may be taken that the factor of additional cost is considered

more than offset by the advantages accruing from working with a familiar form of display. Also it may be noted that the eight-bit binary number d.a.c.s which are employed, and are of the "successive approximation" type, act as information stores over the measurement updating period.

Communication between master and outstations is by "four-wire" working using special modems\* developed to give maximum speed data transmission over nominal 3kHz bandwidth circuits. These links are set up either in existing pilot cables where suitable spare cores are available or in the main communication cables run along the power network routes. Protection against extraneously induced high voltages is provided at all station line terminations by lightning arrestors and isolation transformers.

The other main area of application for supervisory telemetry systems is the monitoring and control of oil and natural gas pipe line schemes. Here inaccessibility of wellheads and pumping stations is a

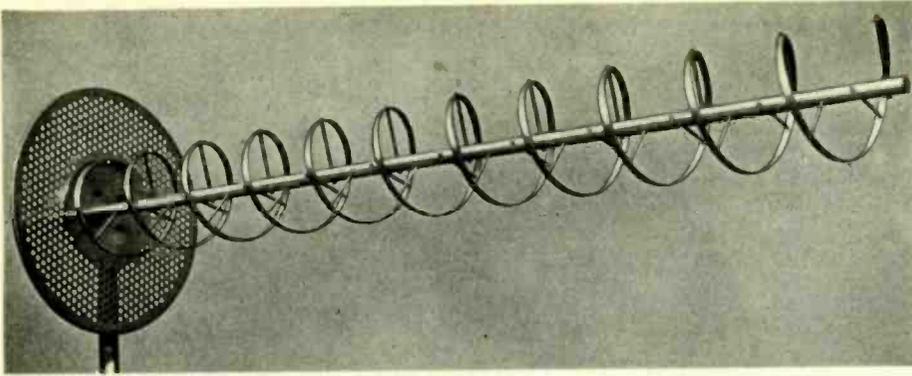\* modulator-demodulator (unit), "four-wire" working demands two conductor pairs, one for "go", one for "return".



*Helical aerial supplied by C & S Antennas Ltd for the North Sea gas radio links.*

major driving force in the adoption of such schemes; these conditions, compared with those associated with most public utility networks, tend to impose more severe restrictions on the choices open to the telemetry system designer. Thus with projects such as the North Sea installations, the virtually inescapable use of radio links produces a "design constraint" which affects the whole system.

The same basic time-division digital techniques are employed, however, for these installations as for the public utility networks; and logic circuit blocks and address-reply methods are essentially the same. The telemetry installation for the B.P. group of wells in the West Sole field<sup>d</sup> is typical of such practice for North Sea operations, the outstations on the project's three wellhead platforms—"A", "B" and "E1"—being under the supervisory control of the shore station at Easington, Yorks. As commissioned, the system capacity is 22 measurements, 120 monitor and alarm indications, together with 41 well control functions; the routine scan updating time is 25 seconds.

One of the main system operational requirements arising from its production control function is the calculation of mass flow for each of the eleven wellheads involved. These corrected values have to be obtained in terms of differential pressure type flow measurements and corresponding manifold pressures; and initially a study was made of using an individual analogue computer at each wellhead. However, it proved possible to centre this function on a single digital computer which is fed with the data in digitized form, and which gives flow rates as a 3-digit numerical indication up to a maximum per wellhead of 59.9 million cu.ft./day.

In general, measurements are displayed on the mimic control panel with three-digit representation for temperature and four for pressure, a "scaling" facility being incorporated in the transfer from binary code input to the decimal reading output. Accompanying this implied degree of resolution, a 12-bit format is used for both addresses and replies, each carrying three additional parity bits for error checking. With the system parameters obtaining in this case, the address/reply cycle time becomes 570 milliseconds. For transmission over the radio links, the address and reply pulse

trains are converted in a frequency shift keying modem to a "tone" input for the transmitter—2.3kHz for binary '0' and 2.7kHz for binary '1'.

The u.h.f. radio link scheme adopted for this project operates in the 460-MHz band and inevitably invites comparison with the offshore wellhead control scheme at Das Island in the Arabian Gulf (Umm Shaif oilfield). Described originally in 1964<sup>5</sup>, this employs a microwave, 3cm ('X' band) link based on a commercially available transmitter magnetron with a rated peak power output of 2.5 kW in the centre of the band. The main point of interest in the present context is that in this earlier scheme a single transmitter is used with radiation from a "cheese" reflector giving a half power beamwidth of about 40° in azimuth to cover the fan-like sector in which the wellheads are grouped.

In contrast the North Sea u.h.f. system utilizes a two stage "hand-on" arrangement for signal transmission between wellhead platforms. The primary link is established between the Easington master and the outstation on platform A, working between this platform and both platforms B and E1 being on a "broadcast" as distinct from a beamed mode. Thus the transmitters on B and E1 operate on a shared frequency, and, in order to avoid radiating together, "come on the air" only when their own plant addresses are received.

Helical aeriels mounted on 200-ft towers are used for transmission and reception on shore and at the platforms. The 11-turn helical elements, made by C & S Antennas Ltd, have a rated beamwidth of 30° to half power points with a v.s.w.r. of 1.5 over the operating bandwidth of 400-500 MHz.

The radio link equipment itself is solid-state throughout; Standard Telephones and Cables type HTR20 f.m. transmitter/receivers being employed with a nominal transmitter power output of 5 watts. This output is obtained from a varactor tuned to act as a trebler stage fed at 133.3—163.3MHz from two preceding trebler stages which have a modulated input at 14.8—17.8MHz. This latter input is obtained from a two-stage phase modulator with crystal oscillator reference drive. Two stages of amplification are interposed between the modulator and the first set of treblers which is followed by three more stages of

amplification to give the input to the final varactor trebler. A tunable bandpass filter is placed in the output from this varactor stage to act as a harmonic suppressor.

In the double superheterodyne receiver the first mixer is preceded by a two section bandpass filter and two stages of r.f. amplification. The bandpass filter is largely responsible for the degree of r.f. selectivity and second channel rejection achieved. A single crystal oscillator feeds both mixer stages, the higher local oscillator frequency required for the first mixer being obtained by multiplication by six (doubler followed by trebler). This avoids the production of spurious beats which is possible with two separate oscillators, "spurious responses" being given as below —80dB. Intermediate frequencies are 70MHz and 10.7MHz with an initial local oscillator frequency of 55—68MHz, fed to the second mixer, and multiplied to 330—408MHz for the first mixer. The output of the second mixer, nominally at 10.7MHz, is fed into a crystal filter to give selectivity at this frequency and thence to a wideband amplifier which provides the input to the limiter and discriminator stages. Both the wideband amplifier and these stages are constructed as linear integrated circuits. Performance criteria are based on a minimum acceptable signal/noise ratio of 20dB; while, for the individual radiation requirement of the broadcast mode, carrier "on" switching time is given as not more than 1ms.

#### **"Telegrid" master programming control System**

As already indicated for the two schemes described, system working speed (data handling speed) is kept relatively low, i.e. the equivalent of a narrow-band telephony channel is generally employed for communication in present generation supervisory telemetry projects. Nevertheless, these communication links must be highly "secure" and, equally important, economic in the full sense of the word; and with the ever growing demand for telecommunication channels, this latter condition is becoming increasingly difficult to meet. This difficulty is encountered whether line or radio working is adopted because of limited capacity—scarcity of installed cables, particularly in built-up areas, and on the radio side, severely restricted channel allocations for such applications.

It is with this background that the Telegrid proposals were put forward as a means of "multiplying" the number of existing communication channels by what may be called supra-multiplexing under the control of a master programming source. The scheme, proposed by G. S. Kermack, managing director of Serck Controls, makes specific communication channels available to users, grouped on a network basis, in accordance with a time sharing schedule held in sequence by narrow band synchronizing signals. Planning of such a scheme would have to be on a national scale, although operation might be on a regional basis within the national framework.

In one suggested embodiment of the scheme (Figs. 1 and 2), four networks are time multiplexed under the control of broadcast synchronizing signals. Network allocation, as shown, would be electricity, gas and water for a distribution group, together with an emergency or stand-by network available to take over from any one of the other three. Alternatively, network 4 could be utilized to give a low speed data transmission facility over a large area in the event of, say, major floods occurring.

The programming of these networks is carried out by a combination of imposed synchronization and delay timing. For this the networks are grouped into two pairs, with the first member of the pair taking the external synchronizing signals, and the second becoming operative after a predetermined time delay following the commencement of the first network scanning cycle or sub-programme.

The main technical feature of the system is the form of coded signals used for programming the networks. These signals are built up from "pips", i.e. short bursts, of tone which can be broadcast from a low-frequency (say 300kHz) transmitter to cover a regional area. In addition to their task of time division synchronization, these master programming signals perform two other functions:—

- (i) Designation and identification of the network to be activated;
- (ii) "Start" the individual network scanning cycle after receipt of the correct combination of signals.

The latter provision is achieved by arranging that the five pips must have been preceded by the six pips before the "five-pip" group is opened up, and conversely. If this sequence is not maintained owing to the absence of a signal or the presence of spurious signals, then the networks are not activated until the correct sequence is re-established, i.e. the system has been made to "fail-safe".

From the diagram it will be seen that guard spaces form part of the timing pattern. These take care of short-term variations and fault condition in individual sub-programmes.

Other developments employing these techniques can be envisaged, as, for example to arrange for each pip or burst of tone to contain a predetermined number of cycles, and, by counting at the

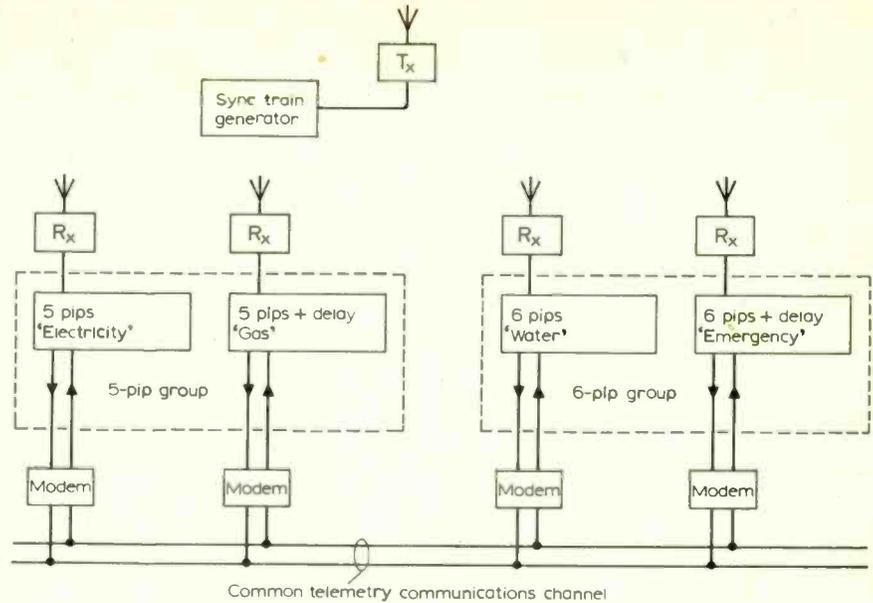


Fig. 1 "Telegrid" diagrammatic network arrangement.

receiving end, to obtain further complementary checking and possibly more precise synchronization.

One of the main advantages of the system is that with an accurately maintained pip (tone) frequency, say at 400 Hz, the signal extraction band-pass filters can be made extremely sharp and only a "crevasse" is required within the synchronizing channel transmission spectrum. Furthermore, with such band-pass filters (e.g. crystal or mechanical type) high rejection of spurious signals is obtained.

### Television Link on Low Bandwidth Cable

Television, as a time-division system, is part of the telemetry family; and in presenting visually inaccessible conventional gauges and similar instruments fulfils a specific telemetering function. One of the main attractions of such presentation is that effectively there is no updating delay, and—often of more importance—rapid changes in quantities can be seen on analogue displays via a television link, whereas they are beyond the capability of the comparatively slow scanning telemetry system.

To speed up these telemetry scanning

rates to give the equivalent of a television system, though theoretically possible, becomes prohibitive in cost. There are instances, therefore, when a television scheme provides the most economic way of tackling an unconventional instrumentation problem, this being much more marked when it can be used for other monitoring duties as well.

A variant of such a scheme is represented by the East Anglian Water Company's closed-circuit television installation at Lowestoft where the emphasis is on surveillance rather than instrument monitoring. The outstanding feature of this project is the video link. As far as is known, this is the first time that a link has provided operationally acceptable picture quality over a 5.2 mile (8.35 km) length of "telephone grade" cable without intermediate repeaters.

This link is of interest on two counts. The first is the potential offered by the equalization and allied techniques which have been developed and shown to be effective under these conditions for high-speed pulse transmission. This aspect bears directly on the problem of obtaining maximum data transmission speed on restricted bandwidth circuits, and also on the improvement in error rate produced by equalizer correction of signal distortion.

The second point is that compromise on picture standards had to be reached but that it proved possible to use a field rate of 50 per second instead of the much lower rate proposed at first in view of the "no-repeater" and other limitations. It was clear that a 405-line interlaced structure was the absolute maximum that could be attempted in terms of frequency and this had the advantage that comparatively low-cost U.K. standard camera and monitor equipment could be employed.

The S.T.C. ten-pair cable installed by the water company between its intake and borehole station at Belough and the Horning master control for both


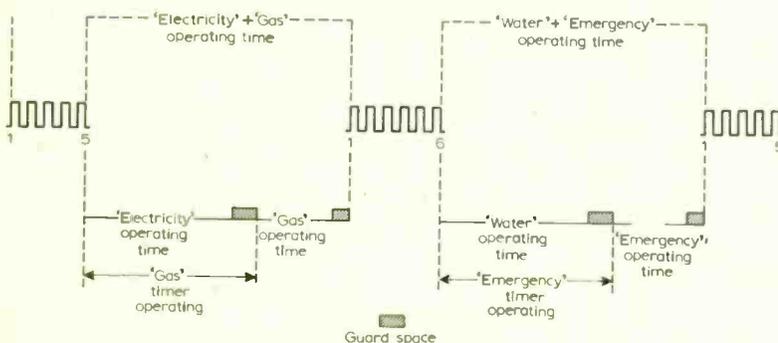


Fig. 2 Overall timing pattern of "Telegrid".

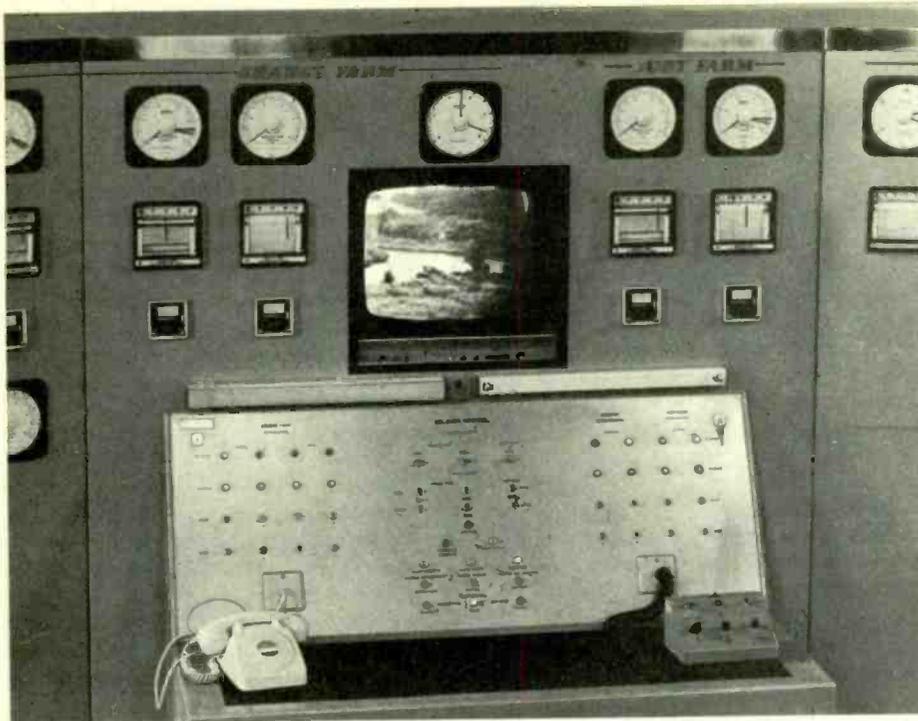

Telemetry and television supervisory control position at the Horning master station of the East Anglian Water Company showing monitor picture as received over the low bandwidth cable link.

telemetry and television signal transmission is of the polythene insulated type with outside steel tape armouring acting as a screen. Diameter overall is some 22mm, individual conductors being of 0.9mm diameter. Conductor resistance is given as 44.2 ohms per mile at 15°C, with attenuation at audio frequencies of 1.20 dB/mile and crosstalk between pairs better than -80dB measured on site. Attenuation reaches a value of some 80dB down at 1.2MHz with an unequalized frequency response approximating to the form  $1/\sqrt{\text{frequency}}$ .

In the final solution, the video circuit was established as two conductor pairs diametrically opposite each other in the cable and connected in parallel. This was found marginally better than a single pair circuit; and at the output of the receiving end equalizing amplifier a uniform response within 2dB is obtained up to 1MHz. The overall response is about 6dB down at 1.2MHz with relatively sharp cut-off thereafter.

It should be noted that a contribution to improved high-frequency response is made by including pre-emphasis in the transmitting characteristic. This amounts to 10dB with a 3dB point at 200kHz. The necessary phase equalization is carried out at the receiving end, some 0.5 microsec. correction being given at 1MHz.

Finally a "crispener" is incorporated to sharpen up fast edges in the video waveform by speeding up their rise times in a non-linear network. The crispener unit embodies an input filter to extract the fast edges from the equalized video waveform for feeding to the non-linear system. This filter operates by signal subtraction referred to a wideband delay line to give a Gaussian type response. After leaving the non-linear network, the

artificially sharpened edges are recombined with the original video waveform, the delay time in the filter being compensated by introducing a corresponding delay in the main video path.

The results obtained in respect of signal/noise ratio, better than "dusk" camera input level (10 foot-candles), can be ascribed to the precautions taken, e.g. with regard to common mode rejection (receiving head amplifier rejection ratio of 70dB), and to the maintenance of electrical balance about earth at the appropriate points in the system. The picture reproduction gains considerably from the crispening technique, although quite acceptable without it; a rise time of less than 800 nanosec being obtained on a 10kHz square wave as measured at the input to the crispener. The overall picture quality also benefits from the use of a monitor with a black level clamp.

Acknowledgement must be made to L. G. Davis, of Glenn Sound Services, who was responsible for the special television link equipment described, and to Serck Controls for supplying details of the two supervisory schemes covered in the first part of the article.

#### REFERENCES

1. "First international telemetering conference", *Wireless World*, Vol. 69, No. 11, November, 1963.
2. "The remote control and supervision of urban power Distribution in Kuala Lumpur", by P. J. White, to be published in *Electrical Review*.
3. "Telemetry engineering", by R. E. Young, Iliffe Books Ltd., 1968.
4. "How a sophisticated telemetry system supervises North Sea gas production", by J. E. Gleave and R. I. Williams, *Oil and Gas International*, October, 1968.
5. "A technical description of the microwave telemetering control system for the Umm Shaif off-shore oilfield, Arabian Gulf", by C. Bedwell, *B.P. Magazine* 12 (1964).

## Reprints from W.W.

We regret the delay in the publication of the reprint of the articles covering the Bailey 30-W and 20-W amplifiers and pre-amplifier. This is now available. For the convenience of new readers we give below the full list of *W.W.* reprints obtainable from the Trade Counter, Dorset House, Stamford Street, London S.E.1. Prices include postage and packing.

No. 1. **High-fidelity Amplifiers** by A. R. Bailey (Nov. and Dec. 1966, and May, June and Nov. 1968). Contains articles on 20- and 30-W amplifiers; a pre-amplifier; and an output transistor protection plus modifications and relevant correspondence. Price 5s.

No. 2. **Stereo Decoder and Simulator** by D. E. O'N. Waddington (Jan. and Oct. 1967). Describes the construction of a stereo decoder for positive or negative power supplies and contains details of an instrument for producing a stereo multiplex signal. Price 3s.


No. 3. **Portable 1-MHz Frequency Standard** by L. Nelson-Jones (Feb. 1968). Presents a design for a frequency standard which is phase locked to the 200kHz Light Programme transmissions. Price 3s.

No. 4. **Wide-range General Purpose Signal Generator** by L. Nelson-Jones (April 1968). Range 150kHz to 120MHz in five bands; output attenuator range 100dB in 20dB steps ( $\pm 0.5$ dB); modulation depth 0 to 50% (can be set to within  $\pm 5\%$  of meter indication); max. output 100mV (from 75 ). Price 3s.

No. 5. **Low-cost High-quality Loudspeaker** by P. J. Baxandall (Aug. and Sept. 1968). Can be built for a few pounds! Excellent performance above 100Hz but is improved if used with a woofer for the low frequencies. Price 5s.

No. 6. **Wireless World Cross-hatch and Dot Generator** (Sept. 1968). A pocket sized instrument using digital integrated circuits. Price 3s.

In addition, the following reprints from earlier issues are still available: **Wireless World Oscilloscope:** Main frame, X amplifier, E.H.T. unit (March, June, July and August 1963), price 5s; No. 1 (audio) Y amplifier (April 1963), price 2s 6d; No. 1 (audio) Timebase Unit (May 1963), price 2s 6d; Calibration — Alternative E.H.T. Unit (Feb. and Oct. 1964), price 2s 6d; and Wide-band Amplifier (March and April 1964), price 2s 6d. **Wireless World Audio Signal Generator** (Nov. and Dec. 1963). Price 3s.

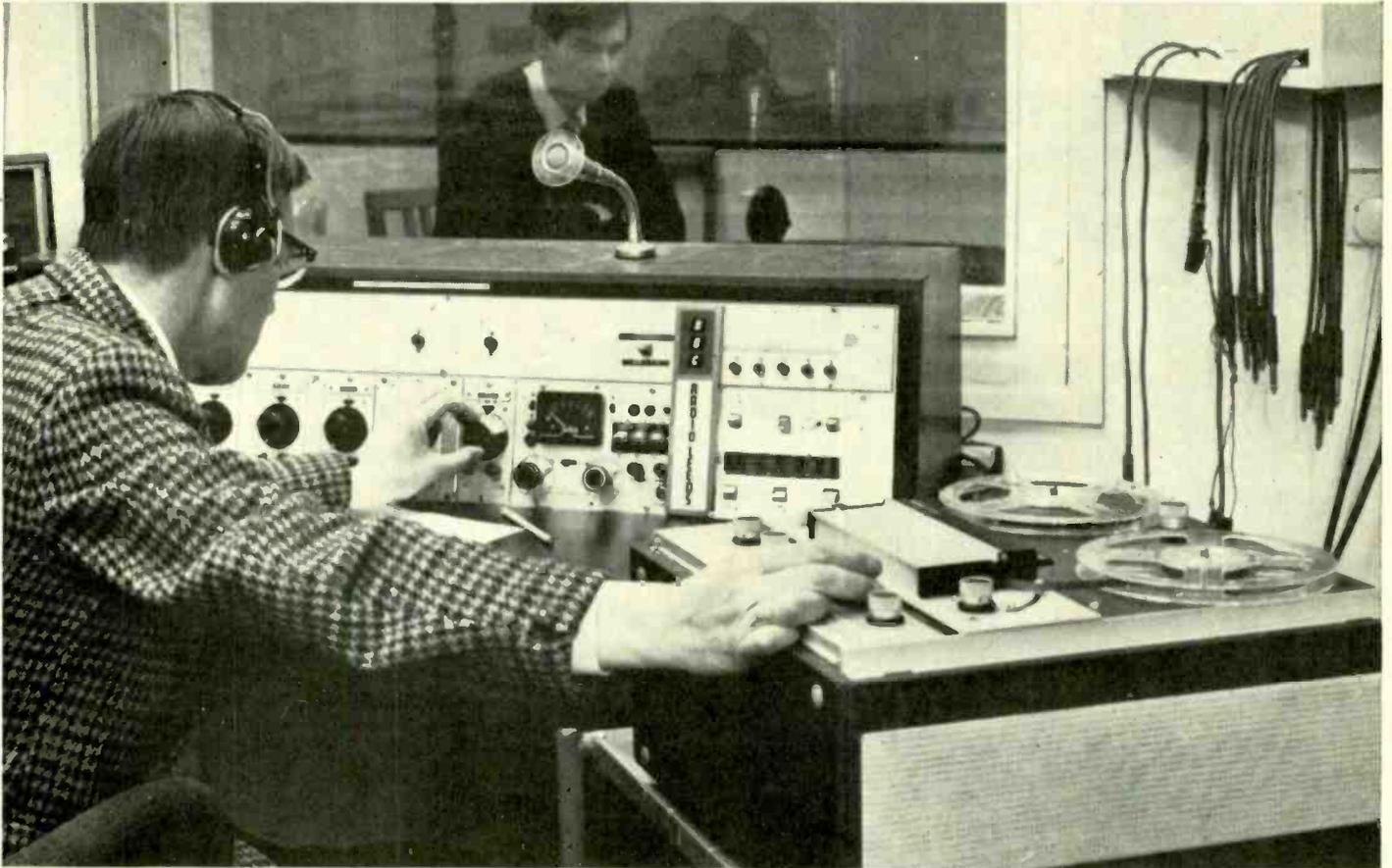

# Radio Leeds: Where a tape recorder must be good and reliable you'll find a Ferrograph.

In a radio station, the tape recorder is in constant use. Technical performance is all-important; absolute dependability and split-second control are essential. So Radio Leeds uses the Ferrograph Series 7 tape recorder.

Ferrograph Series 7 recorders are British-made, available in Mono and Stereo, with and without end amplifiers, in two versions: in elegant hardwood case, or in grey vinyl case. All solid state, three speed, two inputs per channel with independent mixing, all incorporate a range of facilities

unparalleled in any other recorder. Retail prices are from £175 incl. P.T.

Follow the professionals; choose the recorder you know will serve you best at home or in your work: Ferrograph—it makes sound sense. See your nearest stockist or send the coupon for details and address of nearest Ferrograph specialist or ring 01-589 4485.

## Ferrograph

*A member of the Wilmot Breeden Group*

To the Ferrograph Co Ltd,  
Mercury House, 195 Knightsbridge,  
London, S.W.7.

Please send me a free brochure  
on the Ferrograph Series 7   
or the Ferrograph Manual   
for which I enclose £1.

Name \_\_\_\_\_

Address \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

ww

# EMITAPE Afonic low-noise recording tape

quiet as a mouse!



don't buy any tape – buy **EMITAPE**

## THE RANGE OF EMITAPE AFONIC LOW-NOISE TAPE

### 88

#### STANDARD PLAY

The best general purpose tape, giving maximum durability at all professional speeds. Pre-stretched polyester base film of super strength.

### 99

#### LONG PLAY

50% longer recording time – specially designed for multi-track recorders – pre-stretched polyester base film of super strength.

### 100

#### DOUBLE PLAY

Twice the recording time for a given size of spool – the perfect film for low speed, multi-track recorders – superflex polyester base film.

### 300

#### TRIPLE PLAY

Maximum playing time on spools up to 5" dia. – extended dynamic range – specially suitable for battery operated recorders – extra tensile polyester base.

EMITAPE IS AN EMI GROUP PRODUCT



WW—068 FOR FURTHER DETAILS

# Active Filters

## 6. Lead-Lag network and positive gain

by F. E. J. Girling\* and E. F. Good\*

The well-known Sallen-and-Key low-pass and high-pass circuits provide two of the most useful building bricks for applications where only low or moderate values of  $Q$  factor are needed. They are practical examples of the second type of active system analysed in Part 4, a lead-lag or lag-lead network and positive gain, with input connections changed to give low-pass or high-pass response as the case may be.

A notch (or zero) in the stop band is easily obtained by adding a parallel path. This gives a section with a characteristic useful in the realisation of a high-order filter as a cascade (or product) of factors.

Adaptations which give "tuned-circuit" response are also described.

### The Sallen-and-Key circuit

The lead-lag network in a loop with positive gain,  $K$ , has been analysed in general terms in Part 4. This analysis can be applied to the Sallen-and-Key low-pass circuit, Fig. 1(a), by reference to Fig. 1(b), which shows the same circuit with the input  $V_1$  shorted out and a floating generator  $V_2$  introduced into the feedback path. If now the loop is supposed opened at X and the freed end of  $V_2$  earthed, it can be seen that  $\mu$  is given by the transfer function of the lead-lag network, eqn. (19), Part 3, multiplied by  $K$ , i.e.

$$\mu = \frac{KpT_2/b}{1 + p(T_1 + T_2/b) + p^2T_1T_2} \quad (1)$$

where

$$T_1 = C_1(R_1 + R_2),$$

$$T_2 = C_2R_2R_1/(R_1 + R_2).$$

With the loop closed, therefore, since  $\beta = 1$ ,

$$\frac{V_{out}}{V_2} = \frac{\mu}{1 - \mu} = \frac{KpT_2/b}{1 + p\{T_1 + (1 - K)T_2/b\} + p^2T_1T_2} \quad (2)$$

Now the argument used in Part 4 for

deriving eqn. (39) from eqn. (38) gives, if proper note is taken of the change of suffixes as between Fig. 11(b), Part 4, and the present Fig. 1,

$$\frac{V_2}{V_1} = \frac{1}{pC_2R_2} = \frac{b}{pT_2} \quad (3)$$

Hence

$$\frac{V_{out}}{V_1} = \frac{K}{1 + pT/q + p^2T^2} \quad (4)$$

where

$$T^2 = T_1T_2 \quad (5)$$

and

$$\frac{1}{q} = \left(\frac{T_1}{T_2}\right)^{\frac{1}{2}} + \frac{1 - K}{b} \left(\frac{T_2}{T_1}\right)^{\frac{1}{2}} \quad (6)$$

### Alternative analysis as a series-feedback system

The Sallen-and-Key circuits are commonly used with  $K = 1$  (nominally), obtained from an amplifier controlled by 100% series negative feedback. Such an amplifier is most simply represented by the cathode follower, as explained in Part 1 and as used again in the present Part in Fig. 4. Figs. 2(a) and (b) are a reminder of the identity between a cathode follower and a high-gain sign-inverting amplifier with 100% series feedback, and show that essentially the only difference is in the practical matter of where the circuits are earthed. To clarify the identity the output-current circuit in each case is completed by including  $R_L$  and by drawing a short circuit through the h.t. batteries X and any other bias supplies, since it must be assumed that they show negligible impedance to signal frequencies. Ordinarily, of course, the cathode follower, Fig. 2(b), is drawn with the "earthed", or common, line at the bottom. Since

$$K = A/(A + 1) \quad (7)$$

$K \rightarrow 1$  only as  $A \rightarrow \infty$ .

By using the enhanced emitter follower, Fig. 3(a), values of  $A$  of several

hundreds are readily obtained; and it may sometimes be useful to extend this type of connection to triples, etc. If an operational amplifier is to be used, one with differential input and which can take 100% feedback is needed, Fig. 3(b). An operational amplifier should give the low voltage drift obtainable from a long-tailed-pair input stage, which would be useful in an l.p. filter required to pass zero-frequency (d.c.) signals.

In the ideal case,  $K = 1$ , eqn. (6) reduces to  $q = (T_2/T_1)^{\frac{1}{2}}$ , and hence  $T_2 = qT$  and  $T_1 = T/q$ . For finite  $A$ , substitution from eqn. (7) into eqn. (6) gives

$$\frac{1}{q} = \left(\frac{T_1}{T_2}\right)^{\frac{1}{2}} + \frac{1}{b(A + 1)} \left(\frac{T_2}{T_1}\right)^{\frac{1}{2}} \quad (8)$$

This is the same as eqn. (39) of Part 5, and is algebraic proof of the identity of

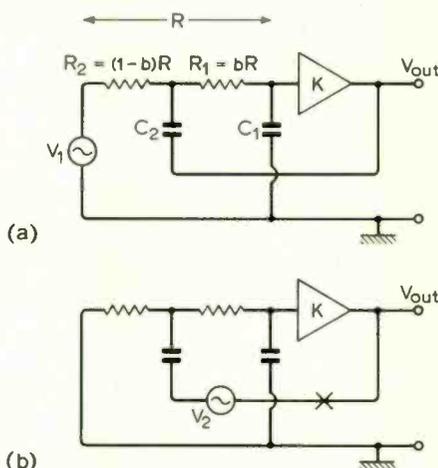


Fig. 1. (a) Sallen-and-Key low-pass filter; (b) the same with  $V_1$  short-circuited and a new source  $V_2$  introduced to facilitate analysis as a lead-lag loop with positive gain.

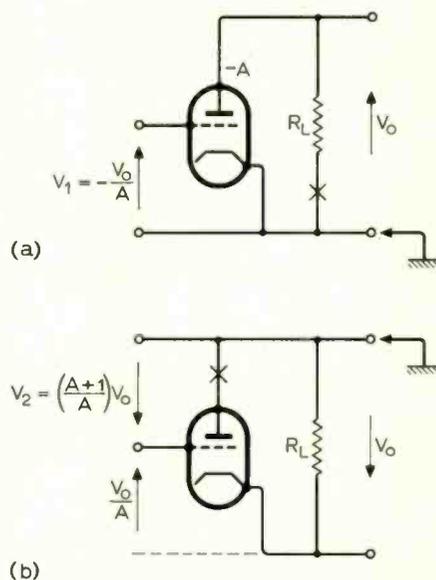


Fig. 2. Example of an active device—a valve: (a) in common-cathode connection, i.e. as a high-gain amplifier,  $V_o/V_1 = -A$ ; (b) in common-anode (cathode-follower) connection, i.e. with 100% series negative feedback,  $V_o/V_2 = A/(A + 1)$ .

\* Royal Radar Establishment.

the Sallen-and-Key circuit and the lag-and-integrator loop with series feedback (Fig. 15 of Part 5), which was mentioned in Part 1. The identity may also be demonstrated graphically as shown in Fig. 4. This is an application of the identity shown in Fig. 2. The only difference between the two circuits is that in (a) terminal 2 of the output is shown earthed, and in (b) terminal 1. But since in neither—in so far as the diagrams tell the whole truth about the circuits—does any current flow in the earth lead, the change makes no essential difference and may be regarded as only a device for marking the node which is to be taken as the reference point of potential.

The triode valve in Fig. 4, as elsewhere, is intended as a universal symbol for a three-terminal amplifier. When more complex amplifiers are used, the identity may not be seen so clearly. A multistage amplifier used as a voltage follower will be wired up somewhat differently from when it is used as a high-gain sign-inverting amplifier, because of the practical requirement in each case for operation from an earthed power supply. Similarly if an operational amplifier with differential input is used, the internal workings are somewhat different in the two connections. But as all are close approximations to an ideal three-terminal amplifier the essential identity remains. The two separate drawings of Fig. 4 are, moreover, not really needed. The change of earth point can be made by the disconnection marked X and the reconnection marked with an arrow head.

**Compensation for finite internal gain**

If  $A$  is finite and positive, application of 100% feedback gives  $K < 1$ , since  $K = A/(A + 1)$ . The theoretically best way of making  $K \rightarrow 1$  very closely is to make  $A \rightarrow \infty$ . But in some situations it may be helpful to use an amplifier of moderate internal gain and reduce the feedback, Fig. 5(a), so that

$$K = \frac{A}{A + 1} \cdot \frac{r_2 + r_1}{r_2} = 1, \tag{9}$$

which is obtained when

$$r_2 = r_1/A. \tag{10}$$

This artifice, which is easily applied when the amplifier is, for example, an enhanced emitter follower, Fig. 5(b), allows the use of the ideal design values. It is important to remember, however, that  $K$  (and consequently  $q$ ) is just as sensitive to changes in  $A$  as before. Caution is needed, therefore, if this method is used to obtain values of  $q$  much beyond the reach of the same amplifier without compensation. There is no complete substitute for high internal gain.

In the alternative analysis (or synthesis) (i.e., as a lag and an integrator in a

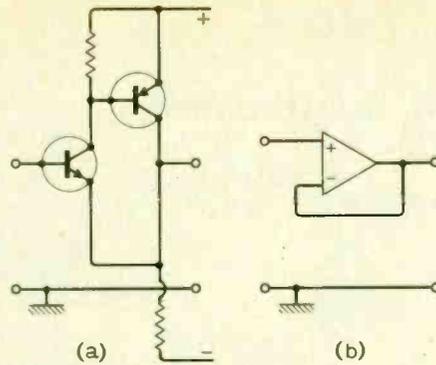


Fig. 3. Possible amplifier configurations for  $K \rightarrow 1$ .

negative-feedback loop) the parallel argument is that finite gain,  $A$ , in the integrating amplifier can be compensated by applying positive feedback (feedback fraction  $1/A$ ) to the amplifier to make its gain apparently infinite, and further that the adjustment is no more critical in the one case than in the other.

In both methods of analysis over compensation produces a regenerative term (negative damping) which subtracts from the positive damping designed into the circuit, and  $q$  is higher than intended; but only if the magnitude of the negative term exceeds the positive will the system oscillate, although, of course this is no criterion of satisfactory performance.

It follows also that working the Sallen-and-Key circuit with  $K > 1$  is equivalent to working the integrating amplifier in the lag-and-integrator circuit with  $A > \infty$  (if mathematicians will allow the statement), meaning that the amplifier gain at zero frequency,  $-A$ , has gone positive, since  $A = K(1 - K)$ , and that the circuit is working in the region above the diagonal in Fig. 9, Part 5. This further emphasises the regenerative nature of the situation when  $K > 1$ .

**Use of Sallen-and-Key circuit with  $K > 1$**

When  $K = 1$ ,  $T_2/T_1 = q^2$ . Hence when  $R_1 = R_2$ ,  $C_2/C_1 = 4q^2$ . This may give an inconveniently large value for  $C_2$ . By using  $K > 1$  a lower value for the ratio  $T_2/T_1$ , and hence of  $C_2/C_1$ , is needed for a given  $q$ .

Let  $C_1 = C/x$ , and  $C_2 = xC$ . Then  $T_1 = CR/x$ ,  $T_2 = xb(1 - b)CR$ , and substitution in eqn. (6) gives

$$\frac{1}{q} = \frac{1}{x} \left( \frac{1}{b(1 - b)} \right)^{\frac{1}{2}} + x(1 - K) \left( \frac{1 - b}{b} \right)^{\frac{1}{2}}, \tag{11}$$

which can be rearranged to give  $K$  in terms of  $x$ ,  $q$ , and  $b$ . Thus, for example, the circuit may be designed for  $C_2 = C_1$ , but at the cost of providing components (both Cs and Rs) of sufficient accuracy in initial selection and in long-term stability to meet the increased sensitivity to errors in component values (Fig. 9,

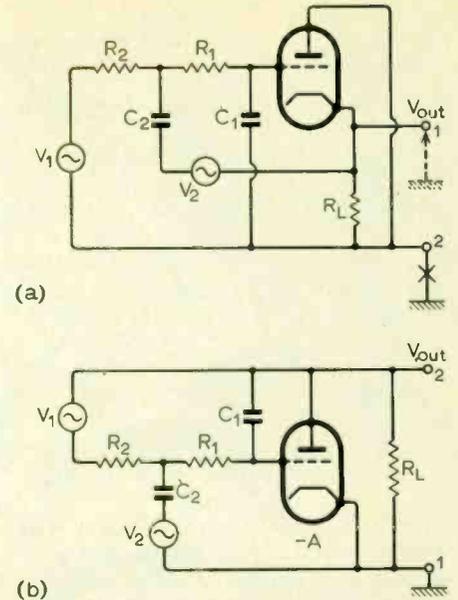


Fig. 4. By changing only the earth point, a Sallen-and-Key l.p. filter is shown to be a lag-and-integrator loop. Also, as the alternative input,  $V_2$ , has one side earthed, the circuit is now suitable for use as a 1st-order band-pass filter.

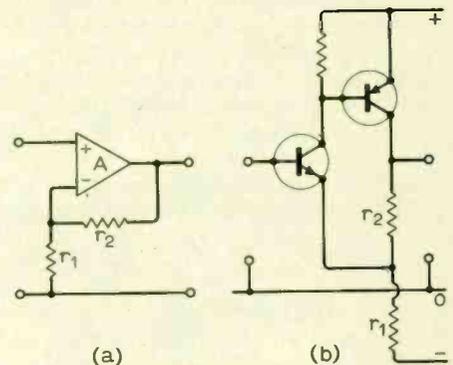


Fig. 5. Feedback less than 100%.

Part 4), which can be interpreted as the result of balancing negative and positive resistance.

**Lead-lag network with resistive loading**

The network in the feedback path (Fig. 1) is as shown in Part 3, Table 1, diagram (a). As the ratio  $C_2/C_1$  is increased,  $k \rightarrow 1$ . Hence, when  $K = 1$ , the loop gain at  $\omega_c$  also tends to unity, (i.e.,  $kK \rightarrow 1$ ), and  $q \rightarrow \infty$  (theoretically without limit) as shown by the diagonal straight line in Fig. 9 of Part 5,  $q$  being proportional to  $\sqrt{(C_2/C_1)}$ .\* Up to this limit the active circuit behaves like a passive circuit: no matter what the component values the circuit cannot become unstable (oscillate), and errors in component values are not magnified.

When the network is loaded by resistance  $R_3$  as shown in Fig. 6,  $k \rightarrow R_3/(R_3 + R_1)$ , and the limiting case

\* It is interesting to notice that increasing  $C_2/C_1$  reduces  $q_0$ , the  $Q$  factor of the passive network. However, over the useful working region (i.e., to the left of the points of maximum  $Q$ ) and always when  $K > 1$ , the increase in  $k$  dominates.

is therefore reached when  $K = (R_3 + R_1)/R_3$ . This may then be considered as a practical maximum value for  $K$ , since in general magnification of errors is to be avoided. The presence of  $R_3$  also alters  $\omega_c$ , and design equations are given in the appendix. This compensation for resistance loading by increasing  $K$  will be most useful when the resistances are effectively accurate and stable, and the ratio  $k$  is therefore accurately known. If  $R_3$  is the input resistance of the amplifier, it may be subject to considerable uncertainty. It is then desirable that  $R_3 \gg R_1$  (and  $\gg R_2$ ), so that if compensation is attempted  $K$  will be only slightly  $> 1$  (Fig. 7).


**High-pass filters**

Any low-pass filter can in principle be transformed into a high-pass filter by substituting  $1/pT$  for  $pT$ ; which means changing a lag into a lead, an integrator into a differentiator, and so on. Operating thus on eqn. (4) of Part 5 gives

$$\mu = \frac{pT/q}{1 + pT/q} \cdot pqT \quad (12)$$

and the schematic shown in Fig. 8. The transformation does not necessarily yield a practical filter however. Fig. 9 is formally the h.-p. counterpart of Fig. 13, Part 5, and if checked by conventional linear circuit analysis gives the expected h.-p. transfer function. As it stands, however, it is unlikely to give a satisfactory performance. At high frequencies it is a shunt feedback system with ratio arms  $C_1$  and  $C_1'$ . As the impedances of these fall indefinitely with increasing frequency, and as the response is required to remain level, indefinitely increasing current is called for. An upper limit to these currents can be set by padding out  $C_1$  and  $C_1'$  with  $r$  and  $r'$  inserted at the points X, making  $C_1'r' = C_1r$ . The presence of these resistors must however to some extent reduce both loop gain and loop phase shift in the region of  $\omega_c$ , and the circuit is now better treated as a two-lead loop, time constants  $C_1r$  and  $C_2R_2$ , with negative gain ( $R_1/r$  if  $A \rightarrow \infty$ ), to which the formulae for two lags and negative gain derived in Part 4 can easily be adapted.

The theoretical schematic of Fig. 8 does not show the same difficulty. At high frequencies (well above  $\omega_c$ )  $V_{out} \rightarrow V_{in}$ , and the "error"  $(V_{in} - V_{out}) \rightarrow 0$ . There is therefore no call for indefinitely increasing current through  $C_1$  with increasing  $\omega$ ; and the same is true for the series-feedback arrangements shown in Fig. 10. Fig. 10(a) shows the functional schematic of a straight-forward circuit with no buffer between the lead and the differentiator; c.f. Fig. 15, Part 5. The design values given are for the ideal case  $A \rightarrow \infty$ . Reversing the procedure shown in Fig. 4, we redraw the circuit with change of earth point and obtain the Sallen-and-Key high-pass circuit shown in Fig. 10(b). The only serious doubt the

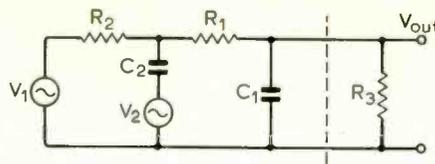

$$T_2 = \frac{C_2 R_2 R_1}{R_1 + R_2}, \quad T_1^* = k_1 C_1 (R_1 + R_2)$$

$$k_2 = \frac{R_3}{R_1 + R_3}, \quad k_1 = \frac{R_3}{R_1 + R_2 + R_3}$$

Fig. 6. CR network with resistance loading.

designer should have about these circuits is that in theory the amplifier should have a level response up to infinite frequency. As, however, it can be of the voltage-follower type, and as high internal gain is of importance only in the vicinity of  $\omega_c$ , it will generally not be difficult to give the amplifier a satisfactory performance up to the highest intended signal frequency. It may, indeed, be thought desirable in these and other active high-pass systems, especially when the internal gain is high, to define the final high-frequency cutoff (with added components) rather than leave it to the chance values of stray capacitances.

For finite values of  $A$

$$\frac{1}{q} = \left(\frac{T_2'}{T_1'}\right)^2 + \frac{1}{b(A+1)} \left(\frac{T_1'}{T_2'}\right)^2 \quad (13)$$

The notation is in conformity with Part 3, Fig. 8 and eqns. (28) to (31), and the primes serve to draw attention to the inversion of the positions of the suffixes compared with the low-pass case, eqn. (8). For  $K > 1$  the appropriate substitutions can be made in the low-pass results.

**Input impedance**

For low  $q$  (say  $\leq 1$ ) the input impedance of a Sallen-and-Key filter is not very different from that of the network when passive. At higher values of  $q$ , because  $T_2/T_1$  or  $T_1'/T_2'$  become  $\gg 1$ , at the resonant frequency the voltage across the element behind the input terminal is equal to  $q$  times the input voltage approximately, and it is necessary to take account of the relatively heavy current that will flow if the filter itself and the preceding circuit are to operate satisfactorily.

**Notch factors**

A notch filter with a symmetrical amplitude vs. frequency response may be used to reject a particular frequency, or be combined with others to form a broader band-stop filter. One with an asymmetrical response may be used as a section of a higher-order filter (e.g., Fig. 1 of Part 1) to give a sharper transition from pass band to stop band. In either case the notch is associated with a quadratic factor with a numerator zero.

Passive CR notch networks, with and without buffer amplifiers, have been


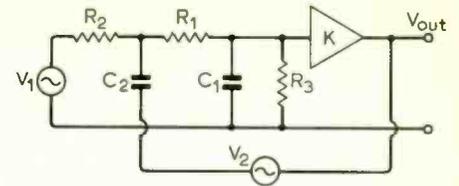


Fig. 7. Resistance-loaded network in active filter.

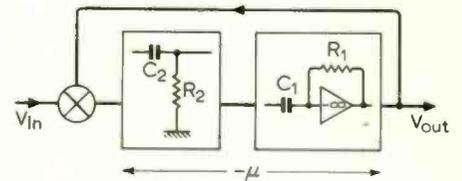

$$T_2' = C_2 R_2 = \frac{1}{q}, \quad T_1' = C_1 R_1 = qT$$

$$\frac{V_{out}}{V_{in}} = -\frac{p^2 T_1' T_2'}{1 + p T_2' + p^2 T_1' T_2'} \quad (A = \infty)$$

Fig. 8. Lead-and-differentiator loop as h.p. filter.

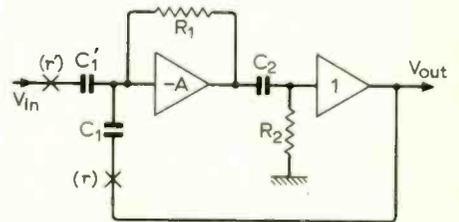


Fig. 9. Practical difficulty in high-pass circuit obtained by direct transformation of low-pass circuit (Part 5, Fig. 13).

described in Part 3. For such networks  $q \gg \frac{1}{2}$ ; and Fig. 11(a) shows an example which gives a symmetrical notch,

$$\frac{V_{out}}{V_{in}} = \frac{1 + p^2 T_1 T_2}{1 + p(T_1 + T_2/b) + p^2 T_1 T_2} \quad (14)$$

with a zero at  $\omega_\infty = 1/(T_1 T_2)^{1/2}$ , if the necessary equal-time-constant condition is met,  $T_3 = T_2$ ; i.e.,

$$C_3 R_3 = C_2 R_1 R_2 / (R_1 + R_2) \quad (15)$$

For  $q > \frac{1}{2}$  the circuit can be made active (i.e., feedback can be applied) as shown in Fig. 11(b). The part of the circuit above and to the right of the dotted line through  $X_1$  is the standard Sallen-and-Key l.p. circuit (Fig. 1), if the assumption is made that the output impedance of the buffer amplifier (1) is negligible; while the circuit to the left of the dotted line through  $X_2$  is the circuit of Fig. 11(a), unaltered if the assumption is made that the output impedance of the amplifier ( $K$ ) is also effectively zero. There must therefore be zero transmission at the same frequency as for eqn. (14); while signals once injected into the upper part of the circuit, whether through  $R_2$  or through  $C_1$ , are subjected to the  $q$  of this active part of the circuit. The complete transfer function is, therefore,

$$\frac{V_{out}}{V_{in}} = \frac{1 + p^2 T^2}{1 + pT/q + p^2 T^2} \quad (16)$$

where  $T^2 = T_1 T_2$ , and  $q$  is given by equn. (6). Preferably the amplifier  $K$  is a high-gain amplifier with 100% feedback. Then, as before,  $K = A/(A + 1)$ , and  $q$  is given by equn. (8).

For an asymmetrical notch, low-pass type, the numerator becomes  $(I + a'p^2T^2)$ , where  $a' < 1$ , and

$$\omega_\infty = 1/\sqrt{a'T^2} = \omega_0/\sqrt{a'} \quad (17)$$

( $\omega_\infty$  is the frequency of the notch,  $\omega_0$  the undamped natural frequency of the system.) The required attenuation in the high-pass path is easily added by connecting the buffer amplifier 1 to a tap on  $R_3$ ; i.e., the network in box  $B_1$  is replaced by the network shown in Fig. 11(d), which has the transfer function  $a'pC_3R_3/(I + pC_3R_3)$ .  $T_3 = C_3R_3$  must of course still  $= T_2$ , equn. (15). For an asymmetrical notch of high-pass type, attenuation can be introduced into the low-pass path as in Fig. 19 of Part 3, so that, as for the passive network,

$$\omega_\infty = \sqrt{a/T} = \omega_0\sqrt{a} \quad (18)$$

Fig. 11(b) is the standard Sallen-and-Key l.p. filter with an added h.p. path. A notch can just as easily be obtained by taking a standard Sallen-and-Key h.p. filter and adding a l.p. path, in other words by starting from Fig. 15 of Part 3, and turning the lower tee into an active filter. The result is shown in Fig. 11(c). As (theoretically) the gains at zero frequency and at infinite frequency are equal, the response is a symmetrical notch. Fig. 11(e) shows attenuation added into box  $B_2$  of Fig. 11(c) (i.e., into the low-pass path) to give asymmetrical notch response, high-pass type. This arrangement may be slightly preferable to that described in the previous paragraph, as high-frequency signals need to pass through only one amplifier.

It is not essential to have a buffer amplifier in the added parallel path. The networks of Fig. 22 of Part 3 can be turned into active filters (e.g., Fig. 12) and the transfer functions are easily derived by making use of those for the passive networks. It is found, however, that for  $K = 1$ ,  $q = b'(T_2/T_1)^2$  or  $q = b(T_1/T_2)^2$ . This results in a greater spread of component values, since  $b'$  and  $b$  are  $< 1$  (often  $\frac{1}{2}$ ). Also  $q_{max}$  is smaller for a given internal gain  $A$  when  $K = 1$  nominally. It seems likely, therefore, that the circuits with the buffer amplifiers will usually be preferred.

In the filters with a buffer amplifier,  $q$  is a function of the active part of the circuit only, and, as in the simple l.p. and h.p. filters, depends on the ratio of two time constants ( $T_1$  and  $T_2$ ) and on the amplifier gain  $K$ .  $T_3$  is isolated from the active part of the circuit, and so errors in  $T_3$  do not affect  $q$ , although they do affect the accuracy of the required match ( $T_3 = T_2$ ) and hence the depth of the notch. If the gain of the buffer amplifier (1) is appreciably  $>$  or  $<$  1,  $\omega_\infty$  is moved accordingly, equns. (17)

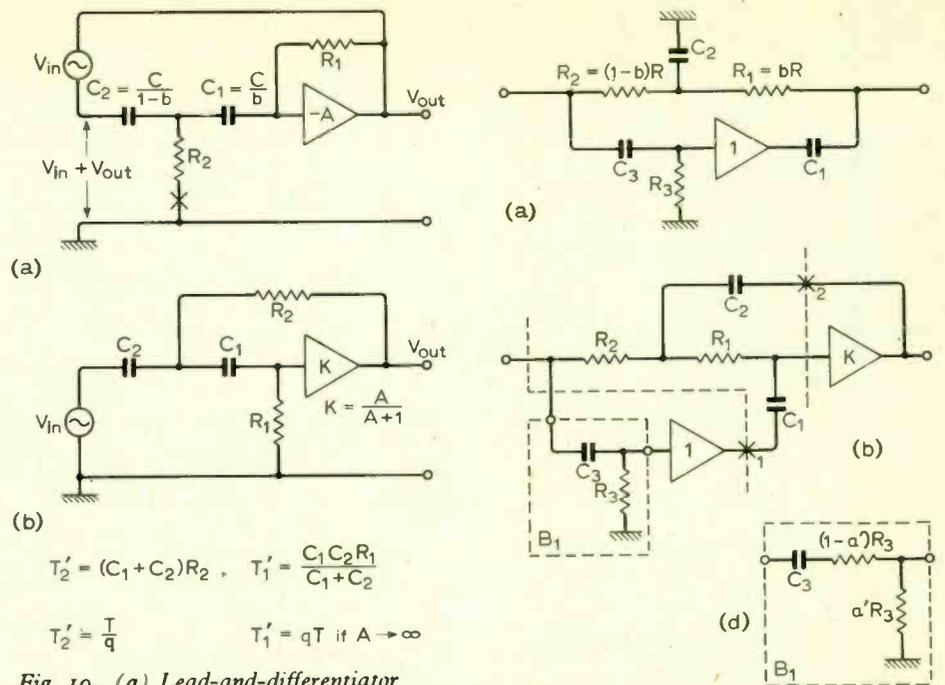


Fig. 10. (a) Lead-and-differentiator loop with series feedback; (b) the same converted by change of earth point to Sallen-and-Key h.p. filter.

and (18), but its gain affects neither  $q$  nor the depth of the notch (as long as its output impedance is effectively zero). So in this sense its internal gain is not a critical factor. And in the notch filters without a buffer amplifier, although  $T_3$  cannot vary independently, still  $q$  does not depend critically on the balance of components or of time constants, at least for  $K \leq 1$ . This contrasts with the behaviour of some rather similar-looking circuits based on the CR parallel-tee network, which can give higher values of  $q$  for a given value of the internal gain,  $A$ , when  $K = 1$  nominally, and which will be the subject of a later article.

**Simple bandpass (tuned-circuit) response**

As shown at the beginning of this article, Fig. 1(b) and equn. (1), the standard Sallen-and-Key l.p. filter can be arranged to give tuned-circuit (1st-order band-pass) response by injecting the signal voltage in series with  $C_2$ ; and, as shown in Fig. 4, for the case  $K = A/(A + 1)$ , (i.e.,  $K \leq 1$ ), by moving the earth point a more convenient arrangement with one side of  $V_2$  earthed is obtained. Similarly the h.p. filter, Fig. 10, is converted to band-pass by injecting the input at the point X. The strange appearance of the circuits is partly remedied by a change of layout as shown in Figs. 13(a) and 14(a), which show the circuits as having feedback networks of familiar form (e.g., Fig. 3, Part 1), only the input connections being unusual.

Because of the limitation

$$q_{max} = \frac{1}{2}\sqrt{b(A + 1)} \text{ or } \frac{1}{2}\sqrt{b'(A + 1)}$$

the circuits are likely to be of limited application; for band-pass filters usually require higher  $Q$  factors than low-pass or

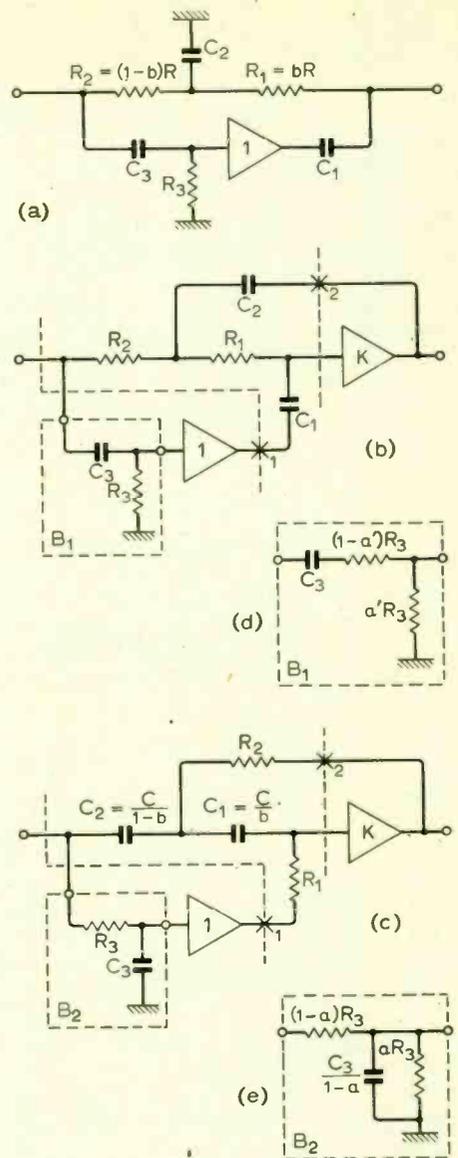


Fig. 11. Modifications for obtaining a notch (or zero): (a) Effectively passive symmetrical notch filter with buffer amplifier in h.p. path; (b) the same made active; (c) similar circuit with buffer in the l.p. path; (d) a method of putting attenuation in the h.p. path of (b); (e) in the l.p. path of (c).

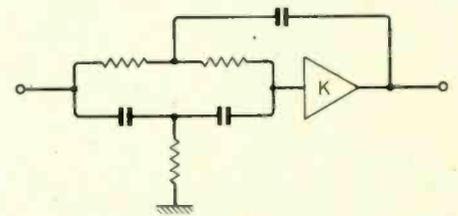


Fig. 12. Notch filter without buffer.

high-pass. For values of  $q$  well below  $q_{max}$ , however, the circuits are interesting in being fully "designable" while using the minimum possible number of components, one amplifier, two capacitors, and two resistors. This very economy, however, makes the circuits unaccommodating; e.g. the gain at resonance which for  $K = 1$  is equal to  $q^2/b$  or  $q^2/b'$  (i.e.,  $2q^2$  when  $b$  and  $b' = \frac{1}{2}$ ) cannot be varied independently of  $q$ ;

and to overcome this inflexibility additional components must be added.

An *ab initio* analysis of the circuits, for  $A = \infty$ ,  $K = 1$ , could be made as follows: (a) write down the current flow caused by  $V_2$ , assuming both the input of the amplifier (the virtual earth) and the output are shorted to ground; (b) write down the current flow caused by  $V_{out}$ , assuming that both the virtual earth and  $V_2$  are shorted to ground; (c) set the sum of the currents converging on the virtual earth to zero.

The useful part of the current flow (a), i.e. the equivalent exciting current, is the current through  $R_1$  (in Fig. 13) and through  $C_1$  (in Fig. 14), i.e.

$$I_{equiv} = \frac{V_2 p T_2}{R_1(1 + p T_2)} \quad (19)$$

and 
$$I_{equiv} = \frac{V_2 p_1 C_1}{1 + p T_2'} \quad (20)$$

where  $T_2$  is the time constant given by  $C_2$  in combination with  $R_1$  and  $R_2$  in parallel (Fig. 13), and  $T_2'$  the time constant given by  $R_2$  in combination with  $C_1$  and  $C_2$  in parallel (Fig. 14).

These equations, as could be foreseen, represent the current a voltage source would drive through a series CR branch; and so the same response will be obtained if the source  $V_2$  is replaced by the source  $V_2''$  feeding in through a branch  $C_3$ ,  $R_3$ , of time constant as specified, Figs. 13(c), 14(c). For the magnitude (gain) to be the same,  $R_3$  should equal  $R_1$ , or  $C_3$  should equal  $C_1$ , for the two cases respectively. But the advantage of having the added branch is that now the gain can be varied independently by varying the impedance of the branch while keeping the product  $C_3 R_3$  constant.

Alternatively the response to an input  $V_2'$  may be calculated. Thus, for Fig. 13,

$$\frac{V_{out}}{V_2'} = - \frac{R_1 + R_2}{R_3} \cdot \frac{1 + qpT}{1 + pT/q + p^2T^2} \quad (21)$$

whence by equating currents the response to  $V_2''$  can be obtained,

$$\frac{V_{out}}{V_2''} = - \frac{R_1 + R_2}{R_3} \cdot \frac{qpT}{1 + pT/q + p^2T^2} \quad (22)$$

if  $C_3 R_3 = qT = T_2 = C_2 R_1 R_2 / (R_1 + R_2)$ . By the same type of argument it is easily shown, Fig. 13(d), that low-pass response may be obtained by feeding in a signal  $V_2''$  through a low-pass (simple-lag) tee network, again of the same time constant,  $T_2 = qT$ .

From the other circuit similar derivations can be made as indicated in Fig. 14. Here it is found that

$$\frac{V_{out}}{V_2'} = - \frac{R_1}{R_3} \cdot \frac{1 + pT/q}{1 + pT/q + p^2T^2} \quad (23)$$

and consequently that  $C_3 R_3$  should now equal  $T/q = T_2' = (C_1 + C_2) R_2$ .

Although all these derived circuits are extravagant in the number of components used, they can be a convenient practical choice. The extra components cause some reduction in  $q_{max}$ , but usually the effect is slight. Component values for  $C_3 R_3$  are not critical, since the input branch is effectively isolated from the resonant feedback loop by the virtual earth and has almost no effect on  $q$ .

**Appendix**

The transfer function giving  $V_{out}/V_2$  for Fig. 6 is readily obtained from equn. (1) by substituting the impedance of the parallel combination of  $R_3$  and  $C_1$ , i.e.  $R_3/(1 + pC_1R_3)$ , for  $1/pC_1$ ; and by making the following convenient substitutions:

$$k_1 = R_3/(R_1 + R_2 + R_3),$$

$$k_2 = R_3/(R_1 + R_3),$$

$$T_1^* = k_1 T_1,$$

i.e.,  $T_1^*$  is the CR product formed from  $C_1$  and  $(R_1 + R_2)$  in parallel with  $R_3$ . [Note:  $k_1/k_2 = k_1(1 - b) + b$ ]. Thus it is found that

$$\frac{V_{out}}{V_2} = \frac{k_1 p T_2 / b}{1 + p(T_1^* + \frac{T_2 k_1}{b k_2}) + p^2 T_1^* T_2} \quad (24)$$

From this, proceeding as before, equns. (1) to (4), the l.p. transfer function for the active circuit, Fig. 7, is obtained as

$$\frac{V_{out}}{V_1} = \frac{k_1 K}{1 + pT/q + p^2T^2} \quad (25)$$

where

$$T^2 = T_1^* T_2, \quad (26)$$

$$1/q = (T_1^*/T_2)^{\frac{1}{2}} + (k_1/k_2)(1 - k_2 K)(T_2/T_1^*)^{\frac{1}{2}} \quad (27)$$

In the special case  $K = 1/k_2$ ,  $1/q = (T_1^*/T_2)^{\frac{1}{2}}$  and  $T_1^* = T/q$ ,  $T_2 = qT$ , which have the ideal form of the corresponding equations for a simple LCR passive prototype. Thus the sensitivity to errors in capacitor values is the same as that of the circuit with an unloaded network, although, since  $K > 1$ , there is additional sensitivity to errors in the values of the resistors that determine  $K$  and  $k_2$ .

**Corrections to Parts 3 and 4**

In Part 3, October issue, in the caption to Fig. 16  $CT_2$  was printed instead of  $CR_2$ .

In Part 4, November issue, the following have been noticed. In Fig. 2, in the box representing the passive network, only the denominator of the transfer function appears. This should read  $1/(the expression printed)$ . In Fig. 5(a),  $1 +$  has been omitted from the

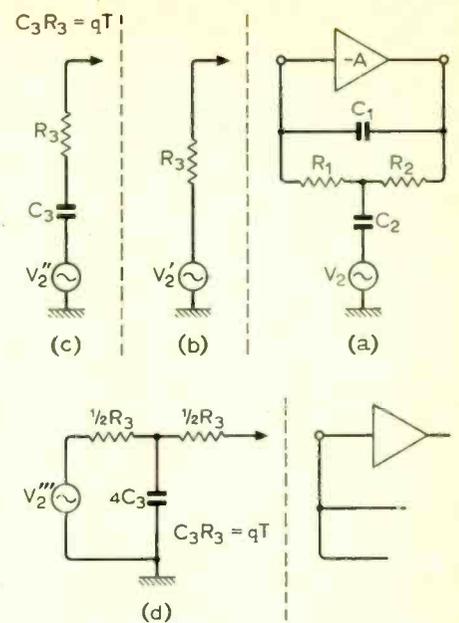


Fig. 13. Derivation of band-pass filter and an alternative form of low-pass filter from the standard l.p. filter (Fig. 4).

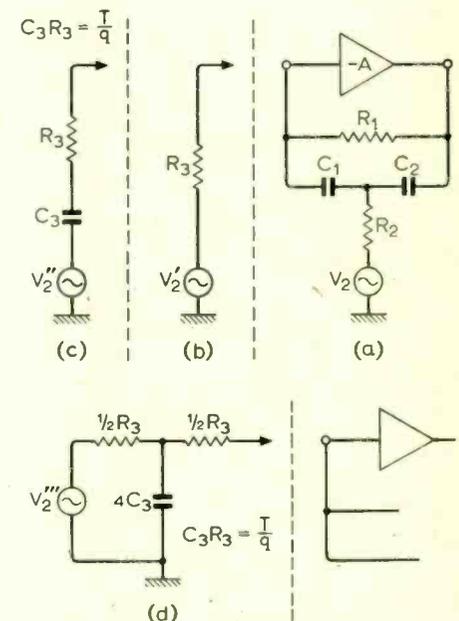


Fig. 14. Similar derivations from the standard h.p. filter (Fig. 10).

denominator of the transfer function in the box representing the passive network; and in the last full column (p. 525) references to Figs. 10(a) and 10(b) should read 11(a) and 11(b) respectively.

# Personalities

**Professor C. W. Oatley, O.B.E., F.R.S.**, professor of electrical engineering in the University of Cambridge, has been awarded one of the Royal Society's three Royal Medals for 1969/70 "for his distinguished work in the wartime development of radar and latterly for the design and development of a highly successful scanning electron microscope." Professor Oatley has occupied the chair of electrical engineering at Cambridge since 1960. He was in charge of basic work on radar transmitters and receivers at the Government Radar Research & Development Establishment during the war and from 1945 until receiving his professorship was lecturer in electrical engineering at the University.

The University of Edinburgh has appointed **P. L. Kirby, D.Sc., F.Inst.P.**, who is research director of Welwyn Electric Ltd, of Bedlington, Northumberland, as its second visiting industrial professor in the newly established Microelectronics Liaison Unit within the School of Engineering Science. Dr. Kirby graduated from Durham University during the war and after two years working on radar systems at T.R.E., Malvern, returned to the North East where he worked on the physical properties of glasses. During this period in industry he took the further degrees of M.Sc., and D.Sc. from Durham and then in 1956 moved to Welwyn Electric Ltd. Professor Kirby has maintained a personal interest in the measurement and interpretation of noise and non-linearity effects in resistive materials.

**Peggy Lilian Hodges**, head of Guided Weapon Simulation and System Analysis at the Stanmore Laboratories of GEC-AEI (Electronics), has been elected to the Fellowship of the Royal Aeronautical Society in recognition of the contribution she has made to avionic and guided weapon technology. Miss Hodges was born in 1921 and educated at Westcliff High School, Essex, and Girton College, Cambridge. She joined GEC-AEI (Electronics) in 1950,

and her work at Stanmore has been centred largely on the performance of guided weapons. She has worked on many projects, notably Seaslug and Sea Dart, with a particular interest in weapon simulation techniques. Miss Hodges is a senior vice-president of the Women's Engineering Society.

**Charles Kao, B.Sc. (Eng.), Ph.D., M.I.E.E.**, has been appointed an honorary senior research fellow at Queen Mary College, University of London. This is the second such appointment from Standard Telecommunication Laboratories in recent months with a view to bringing industrial experience to University affairs. From time to time Dr. Kao will lecture on his specialist subjects including topics in optical communications, coherent wave optics, and electromagnetic problems. Dr. Kao, who is 36, has been with S.T.L. since 1961, where latterly he has been mainly concerned with problems associated with the transmission of coherent light down optical waveguides for future telecommunication systems.

**Alan Hall** has joined Oxley Developments Company, of Ulverston, Lancs, as promotional sales manager. He was until recently in the electronic component division of Johnson Matthey, prior to which he was with Muirhead. Mr. Hall operates an amateur radio station with the call G3UWA.



Alan Hall

**John L. Carroll**, who joined Data Recognition Ltd in 1966 as general manager and has been responsible for the development of their current range of optical document readers, has been appointed technical director. Prior to joining Data Recognition, Mr. Carroll was with English Electric Computers where he was responsible for the development of document handling peripheral equipment; and before that he worked for Solartron on the development of character recognition equipment.

**G. Ross Watson** appointed by the Video Systems Division of Bell & Howell as international marketing manager, was until recently sales engineer responsible for marketing television camera tubes with the English Electric Valve Company. For three years from 1958 Mr. Watson, who is 44, was manager of a mobile television unit frequently used to demonstrate the value of closed-circuit colour TV at surgical operations.

**Peter Smitham** who joined ITT Electronic Services, Harlow, Essex, in July 1967 has been appointed manager. He was previously materials manager. He studied at University College Swansea and spent a post-graduate year at Salford University.

**William J. Charnley**, appointed deputy controller of guided weapons in the Ministry of Technology, was educated at Oulton High School, Liverpool, and at Liverpool University where he obtained a first class honours degree in engineering. Mr. Charnley, who is 47, joined the Civil Service in 1943 at the Royal Aircraft Establishment, Farnborough. He was appointed superintendent of the Blind Landing Experimental Unit in 1955. Six years ago he became head of the Instruments and Electrical Engineering Department at R.A.E. and two years later was appointed head of the Weapons Department. Since 1968 he has been head of the Establishment's Research Planning Division where he is succeeded by **Harold G. Robinson, O.B.E.**, who has been head of the Avionics Department since 1965. Mr. Robinson, who is 45, was educated at H.M. Dockyard School, Portsmouth, where he was awarded a Whitworth Scholarship to Imperial College, London University. He obtained a 1st class honours degree in electrical engineering, and after joining the Civil Service at the R.A.E. in 1948 continued his post-graduate studies during 1951-52 at the Californian Institute of Technology. In 1955 he took charge of the Black Knight research rocket project. From 1960 until 1965 he was in charge of the satellite launcher division at Farnborough.

**Tudor Jones, M.I.E.E.**, aged 42, has joined Cambion Electronic Products Ltd, manufacturers of electronic components, as sales manager. He joins Cambion from the English Electric Co., Stafford, where he was manager of the Production Systems Department.

**Peter L. Mothersole, F.I.E.R.E., M.I.E.E.**, has joined Pye T.V.T. Ltd, Weybridge, as engineering manager of the Audio & Vision Division. Mr. Mothersole, who is 40, has been with the Mullard



Peter Mothersole

Research Laboratories since 1953, where he was for some time leader of the television receiver group. During his National Service he was a radar theory instructor at R.A.F. Yatesbury and then spent a year with E. K. Cole Ltd at Malmesbury as a design engineer on airborne radar equipment.

**Paul Spring**, who joined Grundig (Great Britain) Ltd on its formation in 1952, has been appointed managing director. Mr. Spring has successively been chief engineer, general works manager and, since 1964, technical director.

**Geoffrey E. Beck, B.Sc., F.I.E.E.**, for the past two years chief engineer of Marconi's Electronics Group is appointed technical manager of its Aeronautical Division, based at Basildon, Essex. Mr. Beck, who is 53, graduated at Birmingham University in 1938 and joined the Marconi Research Division, where he worked on the design of naval radar equipment throughout the war. In 1949, Mr. Beck began his long association with the pioneering work into the development of Doppler navigation equipment, which provides pilots with continuous positional information without the use of ground-based aids. In 1962, Geoffrey Beck and Mervyn Morgan, who were jointly responsible for this work, were awarded the Johnston Memorial Trophy by the Guild of Air Pilots and Air Navigators in recognition of their service to aerial navigation. From 1965 to 67, Mr. Beck was manager of the group responsible for the development of the television guidance system for the Martel guided missile. He is vice-president of the Institute of Navigation.

# Progress in Tape-recording Techniques

by Sidney Feldman

Exhibits at the Audio Engineering Society's 37th Convention, held in New York City in October, were predominantly of interest to recording studio engineers. Several 8-track one-inch and 16-track two-inch studio recorders were on operational display. Two machines (Gauss and Magnetic Recording Systems) employed d.c. capstan-drive systems, with the motor-speed controlled precisely by a magnetic tachometer referred to a high stability oscillator. Thus the recorder is not affected by power line frequency variations. The Magnetic Recording machine has a switch-selected speed-range of 32 to 1, permitting operation from  $1\frac{7}{8}$  i.p.s. to 60 i.p.s., and also allows any intermediate speed to be obtained using an external variable-frequency source. Fig.1 shows the basic servo-system employed.

In the Gauss recorder, external synchronization is possible for variable-speed operation, with possible pitch changes of  $\pm 75\%$ . This tape machine utilizes the "focused gap" system of recording, which was marketed, under licence, by Fairchild Recording several years ago, in a series of tape recorders. The bias frequency is approximately 1MHz, and specifications call for a signal-to-noise ratio of 70dB, record input to reproduced output, measured with ASA curve A; peak record level set for 1% distortion on 3M Company 201 tape, at 15 i.p.s.

Of the high-speed tape duplication equipment, Gauss utilizes an endless-loop tape bin, "focused-gap" head, and a bias frequency of 10MHz. Duplication takes place at speeds to 240 i.p.s. Running from a 1200ft master tape at the highest speed, this system can produce 55 copies/hour/slave, utilizing the "stagger loading" system at the slaves. These copies would be at  $1\frac{7}{8}$  i.p.s. The tape would then have to be loaded into the appropriate cassette or cartridge. Console designers are now using, mainly, operational amplifiers in their modules. The modules are completely wired by the manufacturer, saving labour and inter-wiring when a system is built-up. These console "building-blocks" are usually strips 1.5in wide and about 14in long, and they provide functions of equalization, reverberation level control, main-channel level control, input attenuator, and microphone/

line input switching. A typical module will accept microphone level at the input and provide up to +24dBm output with less than 0.5% t.h.d. from 20Hz to 20kHz.

The large recording consoles in use today with loss-less mixing, are only possible using operational amplifiers. A typical mixing circuit, as shown by Melcor (Fig. 2), provides 114dB of isolation between inputs at 20kHz, rising to 134dB at 1kHz. Distortion is 0.25% from

20Hz to 20kHz, at full output of +20dBm. Gain can be adjusted to a maximum of 10dB.

Most tape recorders for the professional market are using transistors for switching functions, and the Quad-Eight Company even have a logic system for track switching on their large console designs. This logic switching can also be interlocked with the tape recorder and the monitoring system, so that operating one button will switch all functions simultaneously.

## Distortion analyser

Crown International have developed an i.m. distortion analyser to test, on a production basis, the Crown DC-300 dual-channel amplifier. Typical i.m. distortion, per channel, (60Hz-7kHz, mixed 4:1) is below 0.05% from 0.01 watt to 150 watts r.m.s. into  $8\Omega$ . The analyser permits rapid measurements of i.m. distortion over a wide range of input levels and power ratings. Active Butterworth filters replace conventional hum-sensitive LC filters. The residual distortion in the analyser itself is typically 0.003%. Ganged input and output controls are employed to facilitate production line testing of amplifiers and other equipment.

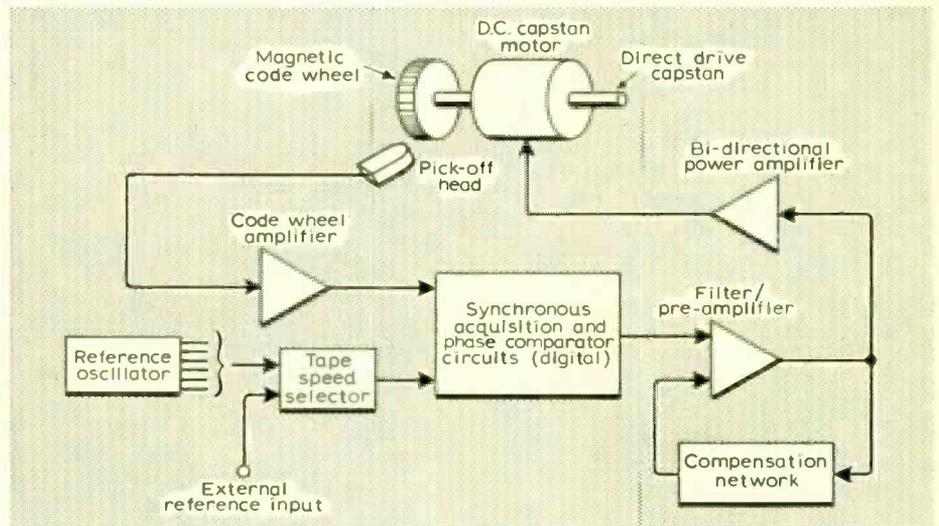


Fig. 1. Speed control system employing magnetic tachometer.

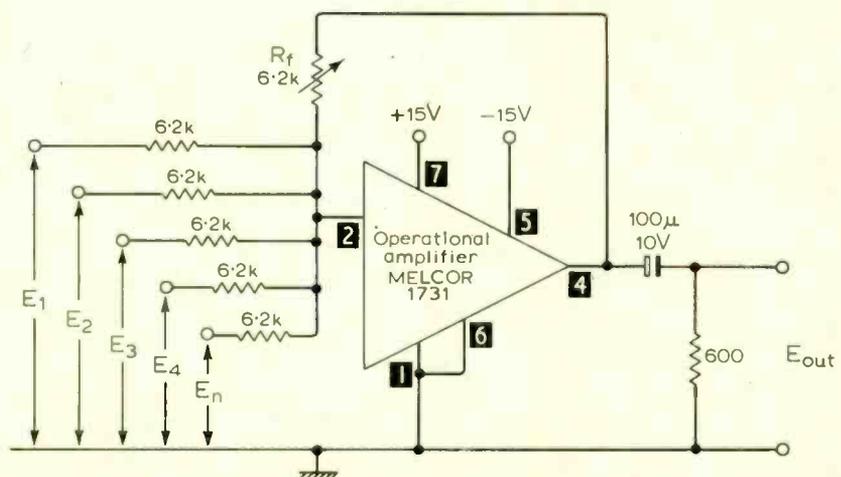


Fig. 2. Mixer using operational amplifier.

# World of Amateur Radio

## Licences and "pirates"

Of every five new British amateur licences now being issued, rather more than three are for Class B operation on v.h.f. telephony only. The licence statistics to the end of October show that in the previous six months there was an increase of 311 Class B licences to a total of 1841, compared with an increase of 198 Class A licences (permitting h.f. operation and requiring the passing of a Morse test) to a total of 13,373. Taking into account the 180 amateur television licences British amateurs now total nearly 15,400.

That there is still an appreciable number of people who attempt to operate in the amateur bands without the formality of a licence is shown by the fact that, in the first nine months of 1969, the Post Office successfully prosecuted more than 70 persons and warned 50 others for offences involving wireless transmitting apparatus being used contrary to Section 1 of the Wireless Telegraphy Act. The fines imposed on these "pirate" stations ranged up to about £100 and the penalties often included forfeiture of the apparatus. The Post Office has indicated that some of the illicit transmissions are regarded as representing a potential hazard to safety of life; they are equally unpopular with licensed amateurs who have sometimes been subjected to deliberate interference and embarrassed by such tricks as the tape recording of genuine amateur "contacts" which are then replayed on transmissions outside the limits of the amateur bands. The Post Office welcomes information which would help in tracing and apprehending the pirates.

## Good tropospheric "openings"

During the spell of pronounced tropospheric propagation in mid-October—conditions which brought many complaints of co-channel interference to broadcasting organizations—large numbers of amateur v.h.f. contacts were made between stations in the U.K. and many countries of Western Europe. The contacts extended from Sweden and Finland to Austria and Switzerland as well as the almost routine links with France, Holland and West

Germany. While most of the contacts were made in the 144-MHz (two-metre) band, the conditions extended also to the 432-MHz (70 cm) band; many of the contacts exceeded 1000 miles. Some amateurs believe that the "tropo" conditions of the 1969 Indian summer were among the most pronounced yet recorded. Peter Blair, G3LTF, of Chelmsford, has raised his total of countries worked on 144 MHz to 28 and on 432 MHz to 19. From January 1st the new voluntary divisions of the 144-MHz band are: 144.0—144.5 telegraphy only; 144.15—144.5 south-west region; 144.5—145.1 south-east region; 145.1—145.5 midlands; 145.5—145.95 north, Scotland and Northern Ireland; and 145.95—146 beacon transmissions.

## R.S.G.B. president for 1970

Dr. John Saxton, director of the Science Research Council's Radio and Space Research Station (Slough) and this year's chairman of the I.E.E. Electronics Division, is to be installed as the 36th president of the Radio Society of Great Britain during the course of a social evening at the Bonnington Hotel, London, on Friday, January 16th. Dr. Saxton, although not himself the holder of an amateur licence, has a keen interest in the relationship between meteorology and radio propagation, and for a number of years has attended many amateur v.h.f. functions.

It is clear from the latest Society accounts that the 1970 Council, despite

the recruitment in recent years of several thousands of additional members, faces problems of the type which are seriously affecting many national and local societies. In each of the past four years expenditure has exceeded income: to a total in the four years of some £8500. Fortunately, the Society has substantial reserves but nevertheless it faces acutely the paradox that even with the present record membership, costs are still rising faster than revenue.

**In Brief:** There has been a good response from British amateurs to a proposal—"Project Trident"—to design and build in the U.K. an amateur radio communications satellite capable of receiving on the 144-MHz band and retransmitting the signals on the 432-MHz band; it is recognized that such a project will take a considerable time to complete . . . It is now hoped that the Australian-built amateur satellite "Australis—Oscar 5" will be launched during December or early January on the Thor-Delta rocket used to put a Tiros weather satellite into orbit; Australis is expected to radiate on 144.050MHz and 29.450MHz for a number of weeks . . . The R.S.G.B. 1.8 MHz Affiliated Societies' Contest is due to be held on January 10th and 11th between 18.00 and 22.00 G.M.T. each day . . . This season's 1.8MHz "Transatlantic Tests" will be continued between 05.00 and 07.30 G.M.T. on December 28th, January 11th and February 1st and 15th . . . A Boy Scouts station on the Caribbean Island of Anguilla, with the callsign VP2EQ, is being operated in the 14-MHz band . . . Indian stations have recently been using the special prefix VU0 instead of VU2 as part of the Ghandi centenary celebrations . . . Mike Matthews, G3JFF, is operating as a maritime mobile station on board the Far East flagship H.M.S. *London* and is expected to visit many Far East and Pacific areas during the next 15 months. . . The Royal Naval Amateur Radio Society, with the callsign G3BZU, transmits a monthly Morse proficiency test at 19.00 G.M.T. on the first Tuesday of each month on 1.875MHz for practice runs and 3.520 MHz for speed proficiency tests.

PAT HAWKER, G3VA

*Since the war, amateur radio in Japan has developed greatly. Station of Yoshio Sameshima, JA2CLI, has many 1.8MHz ("Top Band") achievements to its credit; contacts include the U.S., Hawaii, Canada and Australia (photo. courtesy of Stewart Perry W1BB).*




# Electronic Metronome

## An efficient circuit giving a speed range of 30 to 240 beats per minute

by D. T. Smith

The timing pulses are generated by a complementary-pair form of multivibrator  $Tr_1, Tr_2$ . Both transistors conduct or are cut off together and the conduction time can be made a very small part of each cycle. The conduction time (about 10ms) is used to generate the "tick" and the off time (0.25 to 2s) the interval

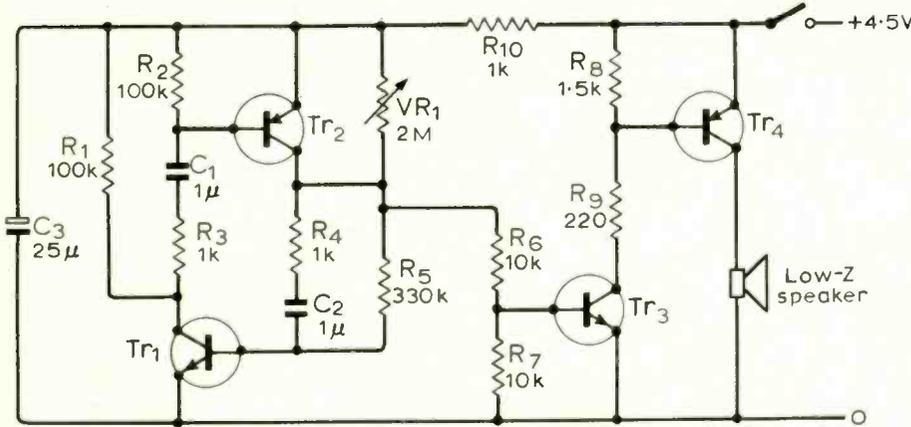As this form of multivibrator may be unfamiliar to some readers, its operating cycle is described. During the conduction period the base of  $Tr_1$  is forward biased and therefore held near zero volts, while  $Tr_2$  is conducting hard and charging  $C_2$  via  $R_4$  towards +4.5V. The conduction period of  $Tr_2$  is limited by the time  $C_1$  can



Complete circuit of metronome.

between ticks. This form of multivibrator is useful in many applications where short pulses, relative to their separation, are required. Low frequencies can be obtained with relatively low capacitor values, and a good range of frequencies obtained by varying a single resistor.

supply enough base current to drive  $Tr_2$ . This time is set primarily by  $C_1$  and  $R_3$ . When  $Tr_2$  is cut off  $R_6$  and  $R_1$  pull the collector of  $Tr_2$  down to zero so that the charge on  $C_2$  gives a negative voltage on the base of  $Tr_1$ .  $Tr_1$  is thus cut off, and no base current flows. The off time is that

taken for  $VR_1$  and  $R_3$  to discharge  $C_2$  and then generate a forward bias at the base of  $Tr_1$  to start conduction. As current starts to flow in  $Tr_1$  it feeds current via  $R_3$  and  $C_1$  to the base of  $Tr_2$  which in turn feeds current via  $R_4$  and  $C_2$  to the base of  $Tr_1$  and so closes a regenerative feedback loop. Both transistors are switched hard on, and the cycle is repeated.


There is no point in having a good quality amplifier to drive the loudspeaker, so a simple two-stage amplifier  $Tr_3$  and  $Tr_4$  is used. This is direct coupled with both transistors cut off when the multivibrator transistors are off, and both conducting hard when the multivibrator transistors are conducting. Any medium- or high-gain silicon planar transistors can be used for  $Tr_1, Tr_2$  and  $Tr_3$ . A medium or high power germanium p-n-p transistor capable of switching about 1A—AC128, OC83, OC25 etc.—can be used for  $Tr_4$ .

There are no special precautions necessary in wiring the circuit, and Vero-board is convenient to use.  $C_2$  should be a paper or polyester type and not electrolytic, as variations of capacitance with age or leakage would upset the calibration. The circuit with loudspeaker and battery are fitted in a suitable box. A low value variable resistor, say 25Ω, may be included in series with the speaker to act as a volume control.

### A Digital Christmas Tree

Using a large number of many coloured lamps switched in pseudo-random sequence, an elegant and fascinating twinkling effect is produced which can be exploited by arranging the lamps around a Christmas tree. In the prototype a 7-stage shift register is used to generate the 'M' sequence, an exclusive OR gate being used to provide feedback to the input from stages 6 and 7. The length of the sequence is 127 clock periods ( $2^7-1$ ). It is arranged that fourteen lamps are controlled by transistor switches from the shift register stages (7 from the Q and 7 from the  $\bar{Q}$  outputs). Transistors can, of course, replace the micrologic elements in the sequence generator. Small pea lamp bulbs (model railway type) are used in the original.

H. N. GRIFFITHS

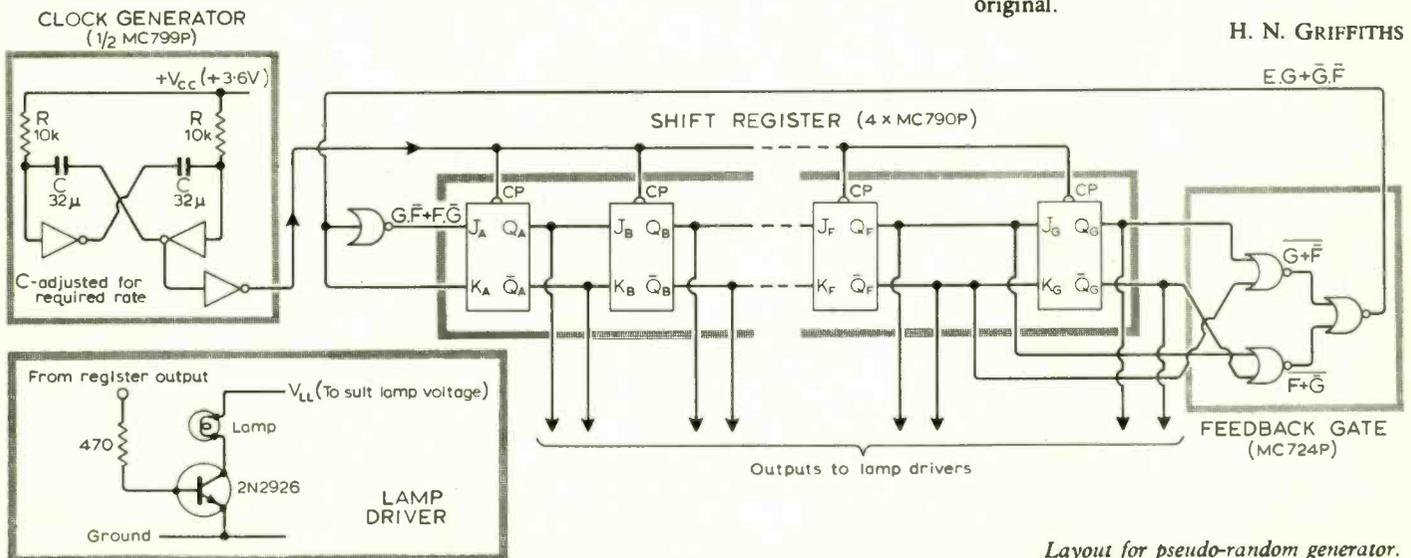

Layout for pseudo-random generator.

# D.C. Bias in Push-Pull Power Amplifiers

## A feedback amplifier controls the working point of a directly coupled driver and output pair

by R. A. Smith

A bias circuit, conventional to many amplifiers, and consisting of d.c. feedback from the collector to the base of the driver transistor, is shown in Fig. 1. A typical practical arrangement is given in Fig. 2. However, the circuit is very sensitive to changes in the current gain of the driver transistor, and hence  $R_f$  must be adjusted for the particular driver transistor used.

Since the prices of suitable transistors are now very low, extra low-current transistors in a circuit present no problem. Hence a transistor can be used whose sole purpose is to stabilize the d.c. level of the output. The requirements of this transistor are:—

(i) High output impedance, so as not to shunt the a.c. signal at the base of the driver transistor.

(ii) A positive current gain to ensure that the d.c. feedback is negative. (The driver transistor changes the sign of the signal).

Its input impedance is not important since it is to be driven through a filter from the low-impedance output of the voltage amplifier, which is capable of supplying large currents; i.e., its loading effect on the amplifier output will be negligible even if the extra transistor has a low input impedance.

In order to satisfy (i), the collector of the stabilizer transistor must be connected to the driver's base; in order to satisfy (ii) a common base circuit must be used. For such a transistor to conduct at all, it must be of opposite polarity to the driver transistor. Also, the a.c. level of the output must be filtered from the d.c. to prevent excessive a.c. feedback. Using a simple RC circuit for this, we obtain the arrangement shown in Fig. 3.

$R_2$  must be chosen so that the potential across it is small compared with the supply voltage. The current passing through this resistor is approximately the base current of the driver transistor, i.e.  $I/\beta$  multiplied by driver transistor collector current which is approximately  $V/2R_L\beta$ .

Thus  $V \gg V_{R_2} = iR_2 = R_2V/2R_L\beta$   
 $2R_L\beta/R_2 \gg 1$  and  $R_2 \ll 2R_L\beta_{min}$  in the worst case.

With  $R_L$  as  $2k\Omega$ ,  $\beta_{min} = 20$  and a factor 20 for " $\ll$ ", this gives  $R_2 = 4k\Omega$ . The  $R_2C$  time constant must be long compared with the lowest frequencies being used.

Fig. 4 shows a circuit used as an a.f. power amplifier. The values given are for a  $3\Omega$  speaker and 25-V power supply.

### High output impedance amplifier

With high output impedance amplifiers we are trying to drive a current in a load irrespective of the potential across it. In an inductive load, for example, the potential may vary considerably depending on the waveform of the input. For the output to be at high impedance, the drive should be from the collectors of the

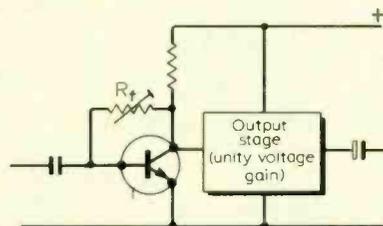


Fig. 1. Arrangement where driver stage  $Tr_1$  controls d.c. level of output pair.

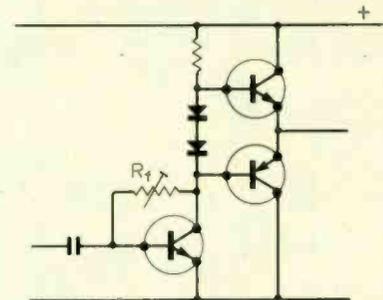


Fig. 2. Typical low-to-medium power output stage.

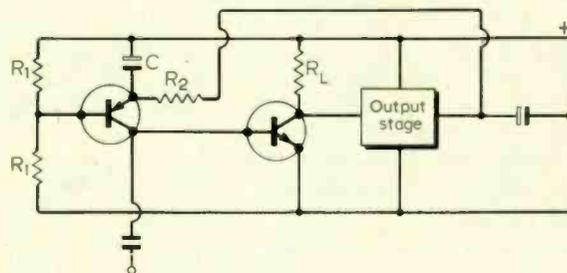


Fig. 3. Use of common-base stage to control d.c. level of amplifier output.

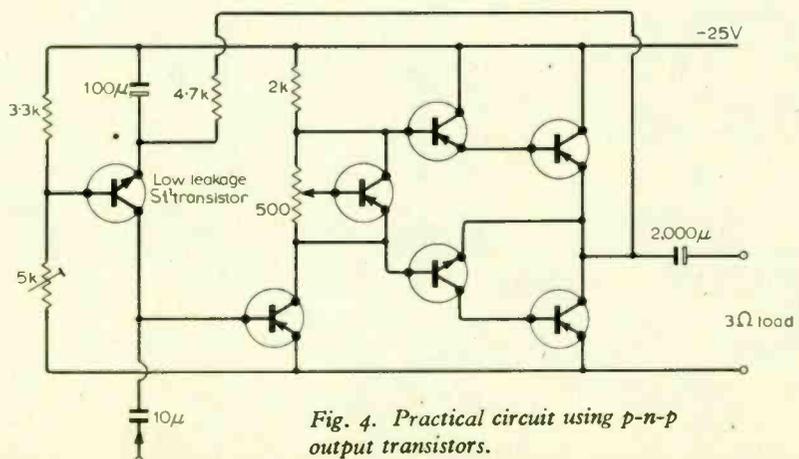


Fig. 4. Practical circuit using p-n-p output transistors.

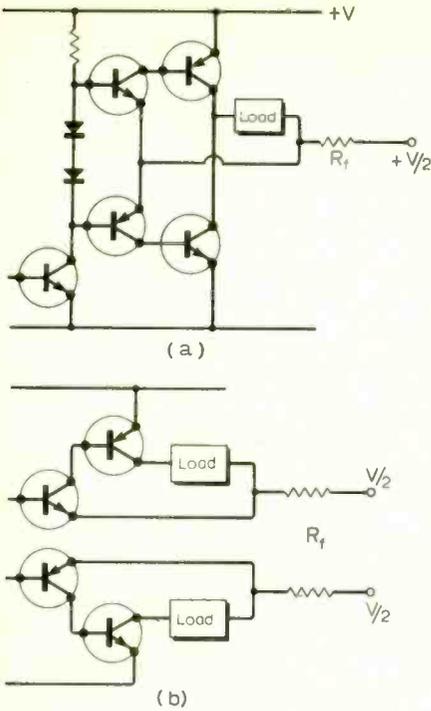


Fig. 5. High output impedance power stage. (a) Actual configuration, (b) Convenient bisection for analysis.

Fig. 6. Application of bias transistor to circuit of Fig. 5.

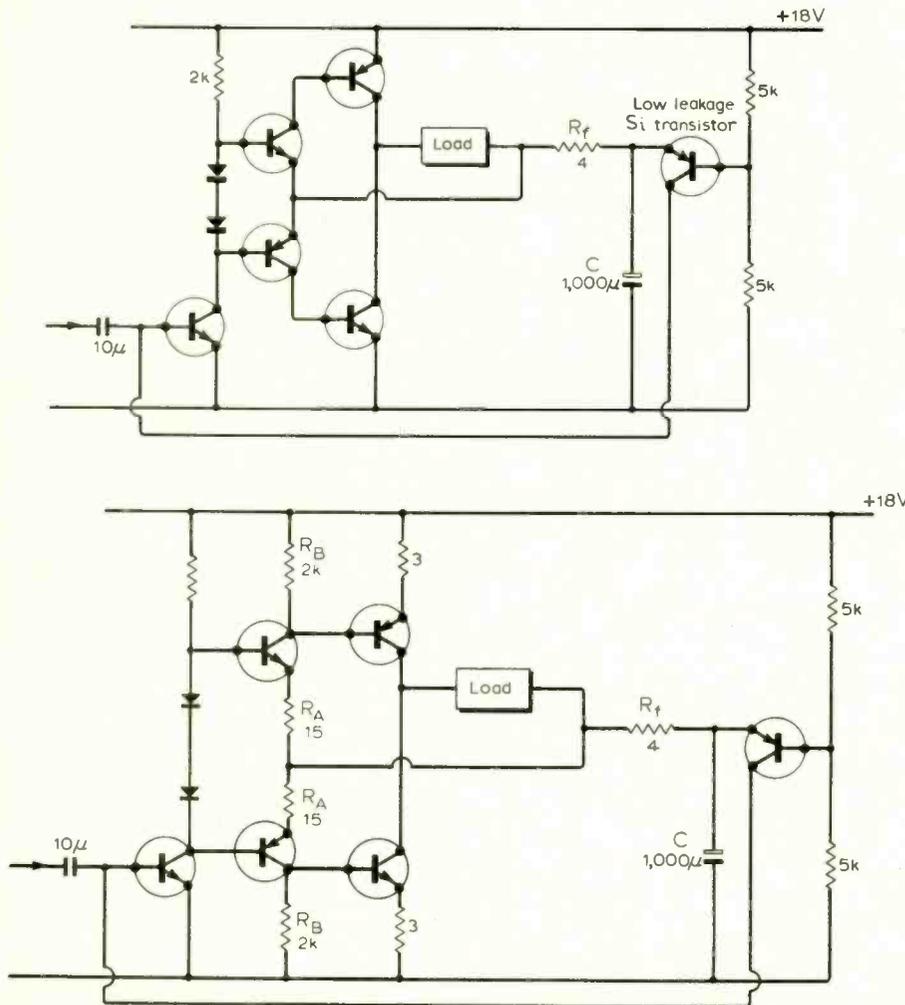


Fig. 7. Modification of the previous circuit to limit standing current in the output stage.

transistors, since the currents in these are the least sensitive to variations of potentials across them.

To apply feedback, the current in the load is passed through a resistor in series with the load, as shown in Figs. 5(a) and 5(b), and hence converted into a voltage which is compared with the input voltage to the amplifier at the emitter-base junctions of one of the driver transistors, depending upon which half of the circuit is conducting.

As will be seen from Fig. 5(b) each part, upper and lower, is an emitter follower across  $R_f$ ; however, the largest part of the current in  $R_f$  comes from the collector of the output transistors (high impedance). There is also a small current in  $R_f$  which flows in the emitter of whichever driver transistor is conducting and this current is approximately the same as the collector current, i.e.  $1/\beta$  times the current through the load in series with  $R_f$ .

$R_f$  should be chosen so that the maximum current in the load (and hence also in  $R_f$ ) produces a voltage across  $R_f$  of, say, a tenth of the power supply voltage. In this case, there is a maximum potential swing of approximately  $\pm 0.4$  of the supply voltage across the load, and the back e.m.f. of an inductive load must not exceed this value if the amplifier is to work in its linear region.

The bias circuit described above can

be incorporated in the circuit as shown in Fig. 6.

In a practical circuit, the standing current in the output transistors can become intolerably large if bias resistors are not included as shown in Fig. 7. Resistors  $R_A$  reduce the quiescent current of the driver transistors and resistors  $R_B$  bleed much of the remaining driver transistors' current to the supply rails rather than through the bases of the power transistors. Values shown are for an amplifier driving 0.25A into an inductive load; it was for driving the scan coils of a magnetically deflected c.r.o.

## More Announcements

(see also p.19)

Hewlett-Packard Ltd have installed a £20,000 patient monitoring system at Walsgrave General Hospital, Coventry. The system includes a cardiac catheterization unit, bedside monitors for coronary care, defibrillator trolleys and two nurse's central stations.

Pye Telecommunications Ltd, has received contracts worth £575,000 for radio telephone equipment to be supplied to Government departments. The orders include u.h.f. fixed and mobile f.m. equipment for airports, v.h.f. motorcycle and personal transmitter/receivers, and v.h.f., h.f. and m.f. marine transmitter/receivers.

STC Mobile Radio Telephones Ltd has been awarded a contract valued at approximately £700,000 by the Home Office for the supply of several thousand mobile a.m. radio telephones for police use.

Plessey Electronics Group has received an order from the North of Scotland Hydro-Electric Board for the supply of radio relay equipment. Operating in the 1500MHz band, the equipment will link the Board's head office in Edinburgh with its main control room at Port-na-Craig, Pitlochry, and communications centres at Burghmuir, Perth and Tealing near Dundee.

**A telecommunications project.** A contract worth £1.4M has been awarded to S.T.C. by the Ministry of Posts, Telegraphs and Telephones of Kuwait for the provision of a number of broadband microwave and coaxial cable links from Basra, Iraq, into the telecommunications centre at Kuwait City.

**Microwave Associates Ltd,** have announced an agreement whereby they will provide a complete marketing service for the products of Microwave Semiconductor Corporation, Somerset, New Jersey, U.S.A.

**Electron microscopes** worth more than \$½M have been ordered from AEI Scientific Apparatus Ltd for the United States and Canada. These orders have been placed by Picker Nuclear, the company's associates in the United States.

# 1970 U.K. Conferences and Exhibitions

*Further details are obtainable from the addresses in parentheses*

## LONDON

- Jan. 19-23 Bloomsbury Centre Hotel  
**American Data Communications Equipment**  
(U.S. Embassy, Grosvenor Sq., London W1A 1AE)
- Mar. 2-5 Alexandra Palace  
**Physics Exhibition**  
(I.P.P.S., 47 Belgrave Sq., London S.W.1)
- Mar. 10-12 Camden Town Hall  
**Sound '70 International**  
(Association of Public Address Engineers, 394 Northolt Rd., South Harrow, Middx.)
- Mar. 17-19 Savoy Place  
**Electrical Methods of Machining, Forming and Coating**  
(I.E.E., Savoy Pl., London W.C.2)
- Apr. 8-15 Earls Court  
**Electrex '70**  
(Electrical Engineers A.S.E.E. Exhibition, Museum St., London W.C.1)
- Apr. 13-16 University College  
**Atomic and Molecular Physics**  
(I.P.P.S., 47 Belgrave Sq., London S.W.1)
- Apr. 23-26 Skyway Hotel  
**High Fidelity Exhibition**  
(Federation of British Audio, 49 Russell Sq., London W.C.1)
- Apr. 28 & 29 Royal Garden Hotel  
**Microelectronics Conference**  
(Business Conferences & Exhibitions, Mercury House, Waterloo Rd., London S.E.1)
- May 4-7 Royal Festival Hall  
**London Engineering Congress (LECO 70)**  
(Council of Engineering Institutions, 2 Little Smith St., London S.W.1)
- May 5-15 Earls Court  
**Mechanical Handling Exhibition**  
(Iliffe Exhibitions, Dorset House, Stamford St., London S.E.1)
- May 11-13 Middlesex Hosp. Med. School  
**Television Measuring Techniques**  
(I.E.R.E., 8-9 Bedford Sq., London W.C.1)
- May 11-16 Olympia  
**Instruments, Electronics & Automation Show**  
(Industrial Exhibitions, 9 Argyll St., London W.1)
- May 19-21 Savoy Place  
**Signal Processing Methods for Radio Telephony**  
(I.E.E., Savoy Pl., London W.C.2)
- June 9-11 Savoy Place  
**Electrical Interference in Instrumentation**  
(I.E.E., Savoy Pl., London W.C.2)
- July 13-17 Olympia  
**Ships' Gear International Show**  
(Brintex Exhibitions, 3 Clements Inn, London W.C.2)
- Sept. 7-11 Grosvenor House  
**International Broadcasting Convention**  
(International Broadcasting Convention, Savoy Pl., London W.C.2)
- Sept. 15-18 Olympia  
**Bio-Medical Engineering Exhibition**  
(U.T.P. Exhibitions, 36-37 Furnival St., London E.C.4)
- Sept. 15-18 Savoy Place  
**Electrical Discharges in Gas**  
(I.E.E., Savoy Pl., London W.C.2)

- Sept. 29-Oct. 2 Savoy Place  
**Trunk Telecommunications by Guided Waves**  
(I.E.E., Savoy Pl., London W.C.2)
- Oct. 15-21 Olympia  
**Audio Festival & Fair**  
(International Audio Festivals and Fairs, 42 Manchester St., London W.1)
- BANGOR**  
July 6-10 University College  
**Microwave Spectroscopy**  
(I.P.P.S., 47 Belgrave Sq., London S.W.1)
- BIRMINGHAM**  
Apr. 14-16 The University  
**Automatic Test Systems**  
(I.E.R.E., 8-9 Bedford Sq., London W.C.1)
- BRIGHTON**  
Mar. 2-6 Exhibition Halls  
**Engineering Design Show**  
(Business Conferences & Exhibitions, Mercury House, Waterloo Rd., London S.E.1)
- CAMBRIDGE**  
Mar. 19-22 Churchill College  
**Television Tomorrow**  
(Royal Television Society, 166 Shaftesbury Ave., London W.C.2)
- CRANFIELD**  
Mar. 23-26 College of Aeronautics  
**Aerospace Instrumentation Symposium**  
(N. O. Matthews, Dept. of Flight, College of Aeronautics, Cranfield, Beds.)
- EDINBURGH**  
Mar. 17-20 The University  
**Management and Economics in the Electronics Industry**  
(D. J. T. Williams, Ferranti Ltd., Ferry Rd., Edinburgh 5)
- HARWELL**  
Apr. 2-3 A.E.R.E.  
**High Voltage Electron Microscopy**  
(I.P.P.S., 47 Belgrave Sq., London S.W.1)
- MANCHESTER**  
Jan. 6-8 The University  
**Solid State Physics**  
(I.P.P.S., 47 Belgrave Sq., London S.W.1)
- Feb. 23-27 Belle Vue  
**Labex Northern**  
(U.T.P. Exhibitions, 36-37 Furnival St., London E.C.4)
- May 19-22 Belle Vue  
**Industrial Training Exhibition & Symposium**  
(John Clarke (P.R.) Ltd., St. James House, 44 Brazennose St., Manchester 2)
- OXFORD**  
Apr. 6-11 The University  
**Biological Engineering Conference**  
(J. Gasking, Dept. of Pharmacology, St. Bartholomews Hospital Medical School, Charterhouse Sq., London E.C.1)

Sept. 14-16 The University  
**Photo-electron Spectroscopy**  
(I.P.P.S., 47 Belgrave Sq., London S.W.1)

## READING

- Apr. 6-8 The University  
**Thin Films Conference**  
(I.P.P.S., 47 Belgrave Sq., London S.W.1)
- Apr. 15-17 The University  
**Defects in Semiconductors**  
(I.P.P.S., 47 Belgrave Sq., London S.W.1)

## TEDDINGTON

- Feb. 25-26 N.P.L.  
**Trends in Diffusion Conference**  
(I.P.P.S., 47 Belgrave Sq., London S.W.1)

## UXBRIDGE

- Apr. 14-16 Brunel University  
**Computer Graphics International Symposium**  
(R. Elliot Green, Brunel University, Uxbridge, Middx.)

## Overseas

### JANUARY-APRIL

- Jan. 14-16 Honolulu  
**System Sciences Conference**  
(Dr. R. H. Jones, 2565 The Mall, University of Hawaii, Honolulu, Hawaii 96822)
- Jan. 20 & 21 Chicago  
**Soldering Technology Seminar**  
(W. R. Dunbar, Grover M. Hermann Hall, Illinois Inst. of Technology, 3241 S. Federal St., Chicago, Illinois 60616)
- Feb. 6-11 Paris  
**Audiovisual Techniques, Electroacoustics & Electronics Show**  
(Fed. Nat. des Ind. Electroniques, 16 rue de Presles, Paris 15)
- Feb. 16-19 Tampa Fla.  
**Computer-Aided Circuit Optimization**  
(Dr. G. W. Zobrist, Dept. of Elect. Eng., University of South Florida, Tampa, Florida 33620)
- Feb. 18-20 Philadelphia  
**Solid-State Circuits Conference**  
(I.E.E.E., 345 E. 47th St., New York, N.Y. 10017)
- Feb. 24-Mar. 5 Tampa, Fla.  
**Applied Communication Systems Analysis**  
(Dr. G. W. Zobrist, Dept. of Elect. Eng., University of S. Florida, Tampa, Fla. 33620)
- Mar. 5-10 Paris  
**Audio Festival**  
(Fed. Nat. des Ind. Electroniques, 16 rue de Presles, Paris 15)
- Mar. 11-13 Washington  
**Scintillation and Semiconductor Counter Symposium**  
(Louis Costrell, Radiation Physics Inst. Section, N.B.S., Washington, D.C. 20234)
- Mar. 18-21 Nairobi  
**Electro 70 Show**  
(Electronics Institution of East Africa, P.O. Box 9690, Nairobi, Kenya)
- Apr. 3-8 Paris  
**Electronic Components Show**  
(Fed. Nat. des Ind. Electroniques, 16 rue de Presles, Paris 15)
- Apr. 6-10 Paris  
**Advanced Microelectronics Conference**  
(Fed. Nat. des Ind. Electroniques, 16 rue de Presles, Paris 15)
- Apr. 14-17 Washington  
**Geoscience Electronics Symposium**  
(I.E.E.E., 345 East 47th St., New York, N.Y. 10017)
- Apr. 21-24 Budapest  
**Microwave Communication Colloquium**  
(Microcoll—Technica Háza Budapest, V. Szabadsag tér 17, Hungary)
- Apr. 27-29 Atlantic City  
**Frequency Control Symposium**  
(Electronic Components Lab., U.S. Army Electronics Command, Fort Monmouth, New Jersey 07703)

# Vortexion


## STEREO MIXERS

These electronic Stereo Mixers range from 2+2 to 5+5 input channels, with left and right outputs at 500 millivolts into 20K ohms up to infinity.

Separate control knobs are provided for L & R signals on each stereo channel so that a Mono/Stereo changeover switch provided can give from four to ten channels for monaural operation, in which state the L & R outputs provide identical signals.

A single knob ganged Master Volume control is fitted, plus a pilot indicator.

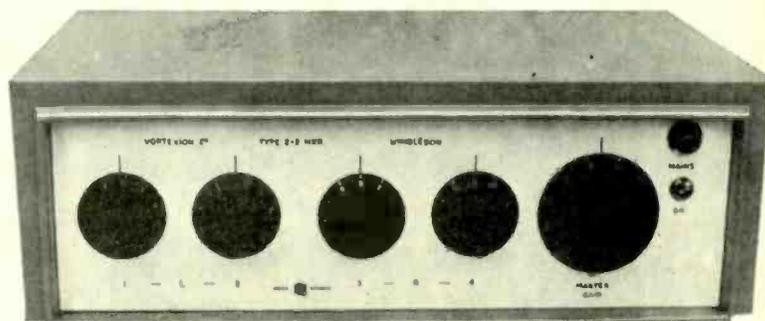The units are mains powered and have the same overall dimensions as monaural mixers.



Also available Monaural Electronic Mixers:—

- |                        |                                   |
|------------------------|-----------------------------------|
| 4 Way Monaural Mixers  | 3 Way Monaural Mixers with P.P.M. |
| 6 Way Monaural Mixers  | 4 Way Monaural Mixers with P.P.M. |
| 8 Way Monaural Mixers  | 6 Way Monaural Mixers with P.P.M. |
| 10 Way Monaural Mixers | 8 Way Monaural Mixers with P.P.M. |

**50/70 WATT ALL SILICON AMPLIFIER WITH BUILT-IN 4 WAY MIXER USING F.E.T.'s.** This is a high fidelity amplifier (0.3% intermodulation distortion) using the circuit of our 100% reliable 100 Watt Amplifier (no failures to date) with its elaborate protection against short and overload, etc. To this is allied our latest development of F.E.T. Mixer amplifier, again fully protected against overload and completely free from radio breakthrough. The mixer is arranged for 3-30/60Ω balanced line microphones, and a high impedance line or gram. input followed by bass and treble controls. Since the unit is completely free from the input rectification distortion of ordinary transistors, this unit gives that clean high quality that has tended to be lost with most solid state amplifiers. 100uV on 30/60 ohm mic. input. 100mV to 100 volts on gram/auxiliary input 100 KΩ.

**CP50 AMPLIFIER.** An all silicon transistor 50 watt amplifier for mains and 12 volt battery operation, charging its own battery and automatically going to battery if mains fail. Protected inputs, and overload and short circuit protected outputs for 8 ohms—15 ohms and 100 volt line. Bass and treble controls fitted. Models available with 1 gram and 2 low mic. inputs. 1 gram and 3 low mic. inputs or 4 low mic. inputs.

**100 WATT ALL SILICON AMPLIFIER.** A high quality amplifier with 8 ohms—15 ohms and 100 volt line output for A.C. Mains. Protection is given for short and open circuit output over driving and over temperature. Input 0.4v on 100K ohms.

**200 WATT AMPLIFIER.** Can deliver its full audio power at any frequency in the range of 30 c/s—20 Kc/s  $\pm$  1 db. Less than 0.2% distortion at 1 Kc/s. Can be used to drive mechanical devices for which power is over 120 watt on continuous sine wave. Input 1 m W 600 ohms. Output 100-120v or 200-240v. Additional matching transformers for other impedances are available.


**30/50 WATT AMPLIFIER.** With 4 mixed inputs, and bass and treble tone controls. Can deliver 50 watts of speech and music or over 30 watts on continuous sine wave. Main amplifier has a response of 30 c/s-20Kc/s  $\pm$  1db. 0.15% distortion. Outputs 4, 7.5, 15 ohms and 100 volt line. Models are available with two, three or four mixed inputs for low impedance balanced line microphones, pick-up or guitar.

**VORTEXION LIMITED, 257-263 The Broadway, Wimbledon, London, S.W.19**

Telephone: 01-542 2814 & 01-542 6242/3/4

Telegrams: "Vortexion London S.W.19"

WW—069 FOR FURTHER DETAILS

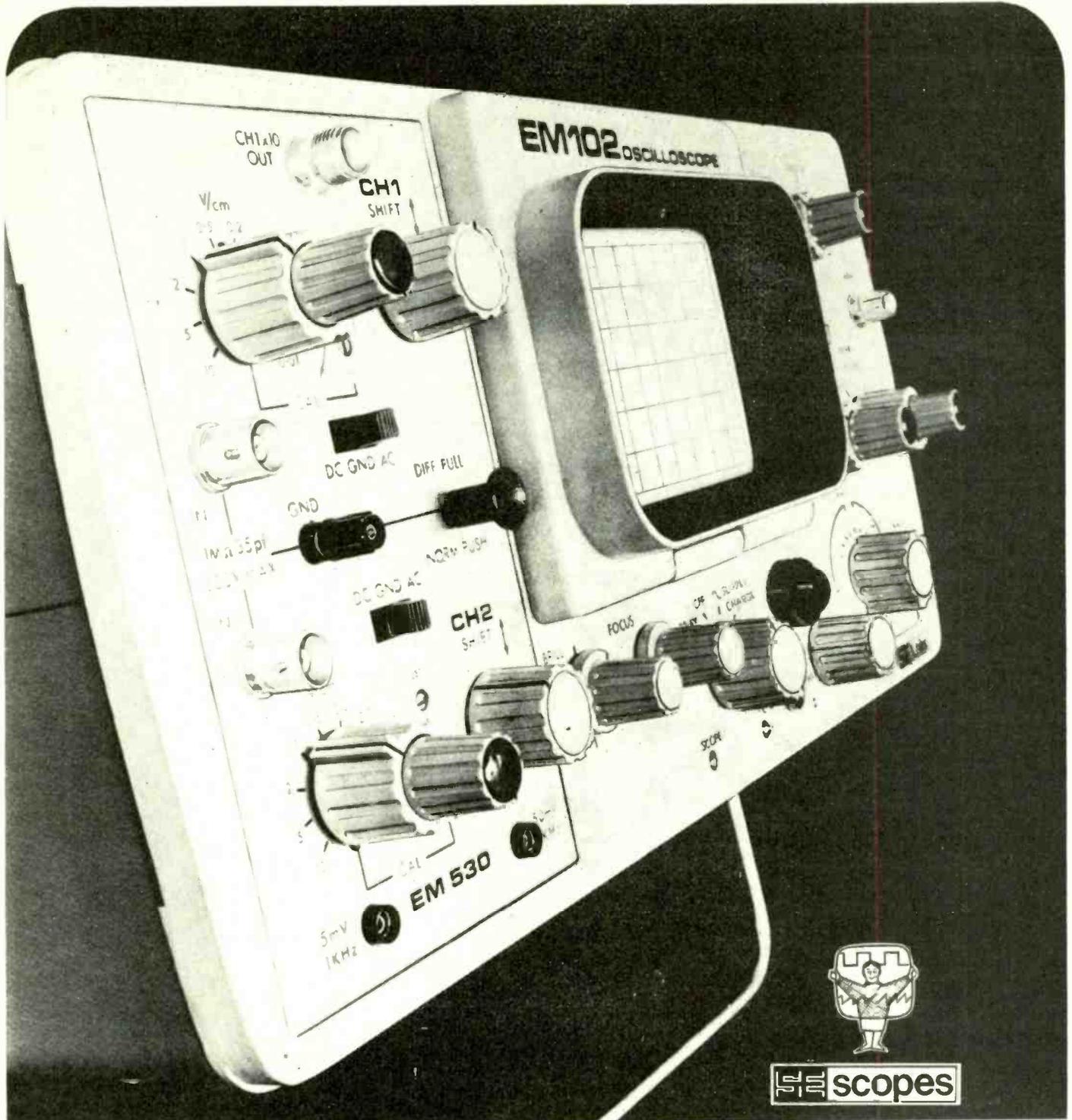

## Scope for Going Places

The EM102 offers you a portable oscilloscope with an ideal performance at a realistic price. Just check its specification (10kV, 20nS/cm. writing speed plus sweep delay). It's designed for laboratory applications but fulfills the role of a completely self-contained unit for servicing purposes. Take it anywhere - it's mains or battery powered with a built-in battery option.

Plug-in units are available with bandwidths from d.c. to 30MHz, voltage sensitivity down to 1mV/cm. If you have an application for an Oscilloscope for use in the laboratory, in the field, or in any unusual environment, write or ring today for information, details or an immediate demonstration.

From £315.



**SE Laboratories (Engineering) Limited.** North Feltham Trading Estate, Feltham, Middlesex.  
Telephone: 01-890-1166 & 5246 (sales); 01-890-5876 (works); Telegrams: Selab, Feltham. Telex: 23995.  
Northern Sales Office, Bessell Lane, Stapleford, Nottingham. Telephone: Sandiacre 3255.

WW—070 FOR FURTHER DETAILS

# New Products


## General Purpose Audio Amplifier

The Elcom GPA general purpose amplifier module—available in two different supply voltage versions—is a low-power high-quality amplifier intended for rack mounting and capable of driving a speaker to 4W mean power. Output is unbalanced, but an external transformer is available for balanced loads. Power supplies required are 50V for the GPA50 and 24V for the GPA24. The a.c. coupled output has an impedance of 7.5  $\Omega$  (GPA24) and 15  $\Omega$  (GPA50). The transformer coupled output has an impedance of 3  $\Omega$ , 7.5  $\Omega$  and 15  $\Omega$  for both voltage versions. At 4W output, sensitivity is quoted as 20dBm maximum, noise level 100dB, and distortion 0.3% (GPA24) and 0.1% (GPA50). Frequency response from 30Hz to 20kHz is within  $\pm 1$ dB, and the amplifier is provided with remote or local gain control facilities. Elcom (Northampton) Ltd, Weedon Road Industrial Estate, Northampton.

**WW 310 for further details.**
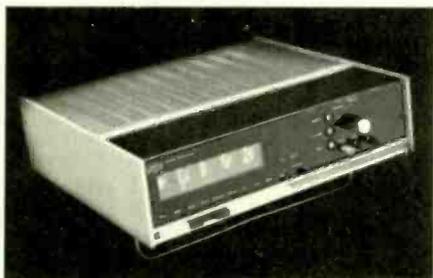
## Auto-range Digital Voltmeter

The SM 212/C digital voltmeter from S.E. Laboratories is designed specifically for data logging and the automatic testing of equipment systems. Selecting "auto" on




the front panel gives complete automatic continuous monitoring over the full range of the instrument (from 10  $\mu$ V to 1kV). The instrument up-ranges at a reading of 9,000 and down-ranges at a reading of 800. All control switches are front-mounted push-buttons. As well as having automatic selection, the instrument's ranges can be selected manually by five push-buttons, and remote ranging for external programming via the B.C.D. output socket. Maximum resolution is 10  $\mu$ V, input impedance > 1000M  $\Omega$  on direct ranges, and accuracy

$\pm 0.01\%$ . Reading rate is 25 per sec. synchronized to mains frequency. Series-mode rejection is > 60dB without filter, and common-mode rejection > 140dB. S.E. Laboratories (Engineering) Ltd, North Feltham Trading Estate, Feltham, Middx.

**WW 315 for further details.**
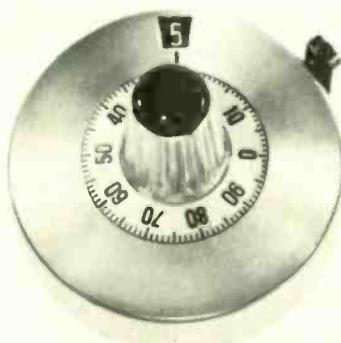
## Turns-counting Dial

R. C. Knight Ltd introduce a range of turns-counting dials for use with multi-turn potentiometers. The model 33-30 illustrated can be used on 10-, 20-, or 30-turn potentiometers. Mating with the potentiometer shaft is accom-



plished using a tapered collet arrangement. Small quantities of up to 100 off are available from stock and prices range from 41s 9d to 47s 3d each, depending on the quantity ordered. R. C. Knight Ltd, 20 Solent Avenue, Lymington, Hants.

**WW 336 for further details**

## Constant-current Power Sources

Direct currents as small as 1  $\mu$ A and as large as 500mA are supplied with extreme accuracy by two constant-current power sources—models 6177B and 6181B—from Hewlett-Packard. Current regulation is such that the output current changes less than 25 p.p.m. ( $\pm 5$  p.p.m. of range setting) with a load change that swings the output voltage from zero to maximum. Current-setting and voltage-limiting controls are independent and can be preset before the load is connected. Maximum output for Model 6177B is 500mA, with voltage limiting continuously adjustable between 0 and 50V. Model 6181B has a maximum output of 250mA with 0-100V limiting. Current output is selected with high resolution (0.2% of range) by a 10-turn control and 3-position  $\times 10$  range switch. Either of the floating output terminals may



be grounded to provide current of either polarity. For systems use, these instruments can be programmed by either external voltage or resistance changes. Extremely high output impedance is maintained without use of reactive elements, resulting in fast programming speed: 500 s from 0 to 99% of programmed output. Hewlett-Packard Ltd, 224 Bath Road, Slough, Bucks.

**WW 316 for further details**


## Light-emitting Diode

The MV50 from Monsanto, is a diffused planar gallium arsenide phosphide light-emitting diode which peaks at 6,500Å. It can be used in place of incandescent lamps as small as the T3/4 size. The life-time of the unit is said to approach 100 years. Light output is 750ft lamberts with a forward current of only 20mA. Turn-on time is 1ns. The MV50 is available in the U.K. from Semiconductor Specialists Inc, Airpark House, 127 Station Road, West Drayton, Middx.

**WW 330 for further details**
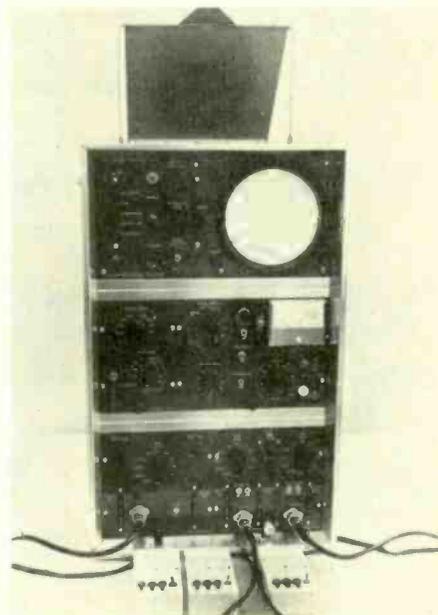
## Electromyograph

Isleworth Electronics have developed an electromyograph suitable for use in clinical medicine practice. The type 7 Electromyograph is a solid-state design, with plug-in units. Four plug-in positions are provided: two amplifiers, a timebase and a stimulator. Two types of amplifier are available—a single channel and double channel. With various combinations, between two and four signals may be displayed simultaneously on the cathode-ray tube. Each channel carries its own built-in calibration signal. Comprehensive camera recording facilities are




provided by a second cathode-ray tube at the rear of the instrument. The remote cable-operated camera shutter is synchronized electrically with the machine. Five modes of operation are possible: single sweep, continuous, superimpose, scan, and autograph. All modes are electrically interlocked to prevent overlapping exposure. Film wind-on after each exposure is automatic. Outputs are provided for data recorder, external loudspeaker (to supplement the unit's own internal sound channel), and trigger pulses to synchronize peripheral equipment. Isleworth Electronics, Frederick Street, Waddesdon, Bucks.

**WW 320 for further details.**
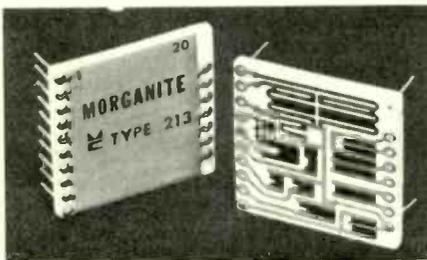
## Binary Ladder Networks

Morganite Resistors have produced two binary ladder networks. Model 215 is an eight-bit high-speed ladder with a standard resistance of 10k $\Omega$  in the binary R-2R configuration. Settling time is less than 100ns with a maximum output voltage ratio error of +0.25 bit over the temperature range -55 to +125°C. Three application resistors, ratioed to the ladder, are also included for bipolar operation and ampli-



fier summation. Model 213 is a 10-bit binary resistor array designed to be compatible with the Fairchild  $\mu$ A 722 current source for D/A and A/D applications. Resistance values correspond directly with those specified on the A 722 data sheet. The resistance temperature coefficient is 0 to -200 p.p.m./°C with resistance tolerance of  $\pm 2\%$  over the temperature range -20 to +85°C. Morganite Resistors Ltd, Bede Industrial Estate, Jarrow, Co. Durham.

**WW 334 for further details.**

## Analogue Computer Teaching System

Analogikit is a system which combines digital and analogue techniques and is intended for the designer, technician and university graduate. The equipment includes operational amplifiers, feedback, summing, scaling and initial condition elements. An introductory handbook explains

the arithmetical aspects of summing, scaling and integration with simple illustrative experiments leading to the construction of differential equations with practical examples of simulated systems. An advanced book deals with the mathematical aspects for degree course students. A complete teaching kit for analogue work, including a mounting deck with power supplies, costs £165 in the U.K. Feedback Ltd, Park Road, Crowborough, Sussex.

**WW 308 for further details.**

## Automatic Counter

All models in the Dana series 8100 automatic counters measure frequencies from 0.05Hz to 50 MHz (d.c. coupled) and 5Hz to 50MHz (a.c. coupled), but models 8120, 8130, 8124 and 8134 have an additional a.c. coupled range from 10 MHz to 500MHz. Models 8110, 8130, 8114, 8134 have a facility for time interval measurement in the range 0.1 s to 10s (up to 100s as an option). When using one of these automatic counters, all that is necessary is to connect the input signal, and set an input voltage range switch to PRESET. The remainder of the measurement process is then controlled by computer logic. Automatic resolution during the reading time is effected, and decimal points and units are automatically indicated. In one second, reading accuracy approaches  $\pm 2 \times 10^{-7}$ . It is claimed the accuracy of the 8100 is better without operator adjustment than that of a manually controlled counter which requires function selection and period-to-frequency calculation. Dana Electronics Ltd, Bilton Way, Dallow Road, Luton, Bedfordshire.

**WW 305 for further details.**

## 32-MHz Counter

The GR 1192 counter measures time intervals, frequency and period from d.c. to 32MHz to a resolution of 0.1  $\mu$ s, and frequency ratio. If the 1157-B scaler is used, the frequency range can be extended to



500MHz. Models are available with 5, 6 or 7 digit presentation. When measuring frequency from d.c. to 32MHz, the counting gate times are 100 $\mu$ s to 10s, and Hz, kHz and MHz can be displayed with positioned

decimal point. Accuracy is  $\pm 1$  count  $\pm$  time base accuracy. The stability of the 10MHz time base is less than  $\pm 2$  parts in  $10^{-6}$  per month. Measurement of period is limited by the digit presentation and is up to 100s, 10s and 1s in the 7-, 6- and 5-digit models, respectively. Single and multiple periods up to  $10^3$  are covered, and time periods can be displayed in ms,  $\mu$ s and ns with positioned decimal point. The ratio of two frequencies, A and B, can be measured from 1 to  $10^3$ . Frequency A from d.c. to 32MHz is measured over 1 to  $10^5$  periods of frequency B, 50Hz to 10MHz. Trigger error in time measurements is defined at  $\pm 0.3\%$  of one period divided by the number of periods averaged for a 40dB input signal-to-noise ratio, and assumes no noise internal to the counter. For input signals of extremely high signal-to-noise ratio, the trigger error in  $\mu$ s is less than 0.0003 divided by the signal slope in V/ $\mu$ s. Price of the three models is £326 (5 digit); £382 (6 digit) and £437 (7 digit). General Radio Company (U.K.) Ltd, Bourne End, Buckinghamshire.

**WW 303 for further details.**

## 3mm Jack Receptacle

Sealectro have developed a 3mm s.r.m. series jack receptacle which prevents r.f. radiation. Designated part number



50-645-4520-31, the receptacle is constructed of gold plated stainless steel, Teflon, and gold-plated beryllium copper. It meets all requirements of MIL-C-39012 regarding contact and dielectric torque and captivation. R. F. Components Division, Sealectro Ltd, Walton Road, Farlington, Portsmouth, PO6 1TB.

**WW 317 for further details.**


## DC/DC Converters


A range of d.c./d.c. converters for changing an available low d.c. voltage (between six and sixty volts in multiples of six volts) to a much higher d.c. voltage is available from Plessey. General use of the component is in transistor instruments incorporating a cathode-ray tube for display purposes. Normal voltages up to 8kV with power up to 0.5W are available in the unit size of 12.7  $\times$  5.1  $\times$  3.8cm, and ranging up to 10kV and 2W in a unit measuring 13.4  $\times$  5.9  $\times$  4.5cm. Plessey Wound Components Division, Titchfield, Hants.

**WW 321 for further details.**
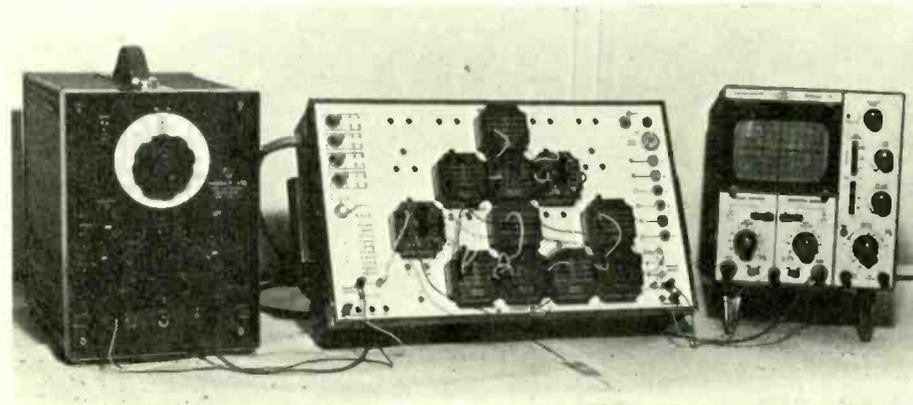
## Portable Instrumentation Recorder

A portable instrumentation magnetic tape recorder, especially designed for use by non-skilled personnel, has been introduced by Bell & Howell. Suitable for a wide range of industrial and research applications, the VR-3200 is available in both 4-track and 6-track versions with speed ranges of  $1\frac{1}{8}$  to 15 i.p.s. and  $3\frac{1}{4}$  to 30 i.p.s. respec-



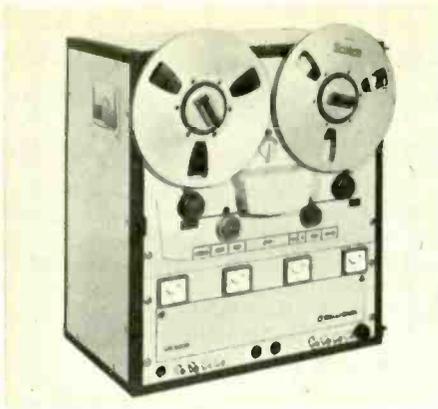

tively. Both versions use  $\frac{1}{2}$  in tape on a 10  $\frac{1}{2}$  in diameter standard N.A.B. spool. F.M. circuitry gives a frequency response of d.c. — 10kHz at 30 i.p.s. with a signal-noise ratio of 44dB. Recording and playback are possible at any speed, the correct centre frequency and filter being automatically selected from the tape transport speed selection switch. Peak detection monitor meters are fitted which enable the correct modulation to be adapted for any input signal level in the range 100mV to 30V. A test facility is incorporated to allow setting up without running tape. Operation is from 230V a.c. (50Hz). A remote control unit is available as an optional extra. Price from £1,456. Bell & Howell Ltd, Consolidated Electrodynamics Division, Lennox Road, Basingstoke, Hants.

WW 325 for further details.

## Marine Communications Receiver

Marine general-purpose/s.s.b. communications receiver type R551, from Redifon, is designed to meet the British Post Office specification and international requirements for a ship's main and s.s.b. receiver. All-solid-state it provides unbroken frequency coverage from 60kHz to 30MHz. It incorporates a frequency synthesizer as well as continuously variable of "free" tuning.



Frequency of the basic receiver is set on three in-line direct-reading decade dials which select the digits for MHz tens, MHz units and kHz hundreds (e.g. 27.2MHz). The tuning process is then completed by a continuously variable control which sweeps a range 100kHz wide. This control is geared to a counter in the same line as the decade dials to give a direct read-out of frequency down to 100Hz (e.g. 27.2796MHz, or 27,279.6kHz). Complete frequency synthesis, using the ARU11, provides the additional decades to enable operators to select precisely the digits for kHz tens, kHz units, and Hz hundreds. This permits immediate direct setting of known frequencies down to increments of 0.1kHz, with instant

switch selection of free tuning or of complete synthesis. Another feature is a dynamic range of over 120dB. This accommodates a correspondingly wide variation in levels of input signals. The use of two inter-coupled a.g.c. systems enables the R551 to receive wanted signals at sensibly constant level despite adjacent unwanted signals. A high degree of front-end protection, independent of whether the receiver is switched on or off, permits the R551 to be installed and operated in close proximity to high-power transmitters. Redifon Ltd, Broomhill Road, London S.W.18.

WW 312 for further details.

## S.S.B. Manpack

The TRA.6929 Minical s.s.b. manpack from Racal-BCC has a power output of 1W p.e.p. and six operating channels covering frequencies from 2 to 7MHz or 2.6 to 9MHz. Complete with batteries, handset, aerial and haversack, the manpack measures 190 x 76 x 210 mm and weighs 3.6 kg.



Intended for military use, Minical has been specifically designed for simplicity of operation with a minimum number of controls. Changing channel takes only a few seconds, and it is claimed that unskilled operators are able to use it after a few minutes instruction. Tuning is effected with the aid of an internal noise generator. By this means, the possibility of radiation during tuning is avoided. The manpack operates from either U2/D type dry cells or rechargeable NiCad cells. If required, a vehicle 12V supply can be used to power the manpack or for recharging the NiCad cells. Racal-BCC Ltd, Western Road, Bracknell, Berkshire.

WW301 for further details

## R.F./U.H.F. Millivoltmeters

Millivac r.f. millivoltmeters types MV-828A and MV-928A are solid-state instruments with full-scale ranges from 1mV to 3V, extended to 300V by a capacitive divider. Frequency range is 10kHz to 1,200MHz. Both instruments operate on 115/230V, 50-450Hz supplies, whilst the MV-928A also operates on internal nickel-cadmium batteries and has a built-in battery charger. Features of the instruments include temperature-compensated probe with replacement diode cartridge and recorder output. Avail-



able through Millivac's U.K. agents, Lyons Instruments Ltd, Hoddesdon, Herts, the MV-828A is priced at £337 10s and the MV-928A at £387 10s. (Duty free). WW 326 for further details.

## Integral-cycle Zero-voltage Switch

The CA3059 integral-cycle zero-voltage switch is contained within a 14-lead dual in-line plastic package and operates direct from the a.c. line. This RCA device is capable of driving triac gates directly, and by providing a triac gating signal at zero-voltage crossings minimizes r.f. interference. A fail-safe circuit is incorporated to guard against an accidentally opened or shorted sensor, and an optional output control is available. Electrical characteristics include; d.c. gate-trigger current of 40mA for  $V_{GT}$  of 3V and  $R_{GT}$  of 70  $\Omega$  gate-trigger pulse width of 80  $\mu$ s before and after 'O' for  $C_X = 0$ ; a gate-trigger pulse width of 20  $\mu$ s before 'O' and 170  $\mu$ s after 'O' for  $C_X$  of 0.015  $\mu$ F; an on-off accuracy of 1% and 3% for sensors of 5k $\Omega$  and 100k $\Omega$ , respectively. RCA Ltd, Sunbury-on-Thames, Middlesex.

WW 309 for further details.

## Dual-trace 10-MHz Oscilloscope

The D54 is a solid-state-circuit oscilloscope. Intended for general purpose laboratory and production line testing applications the Tequipment D54 solid-state oscilloscope has a vertical amplifier bandwidth of d.c. to 10 MHz within -3dB when d.c. coupled,



and 2Hz to 10MHz within  $-3\text{dB}$  when a.c. coupled. A 12-position frequency compensated input attenuator calibrated direct in V/cm can be set for sensitivities of  $10\text{mV/cm}$  to  $50\text{V/cm}$  in a 1-2-5 sequence. The range of timebase sweep speeds is  $200\text{ns/cm}$  to  $2\text{s/cm}$  covered in 22 calibrated steps. A variable uncalibrated control provides continuous overlap between steps and reduces slowest sweep speed to approximately  $5\text{s/cm}$ . The D54 can be operated in the following four modes: channel 1 only; channel 2 only; alternate during which the input to the vertical output amplifier is synchronously switched between channel 1 and channel 2 during flyback; and chopped during which the input to the vertical output amplifier is continuously switched between channel 1 and channel 2 at approximately  $100\text{kHz}$ . Telequipment Ltd, 313 Chase Road, Southgate, London N.14.

WW 302 for further details.

### Over-voltage Protection Unit

New from ITT is an over-voltage protection unit designed to give semiconductor devices protection against voltage surges of  $1\ \mu\text{s}$  or greater duration. The unit employs a reference amplifier and variable potential divider to sense applied voltage. The trip point is continuously variable between  $4.5$  and  $60\text{V}$ , with resolution better than  $0.1\text{V}$ . An excess voltage triggers a crowbar




s.c.r. across the supply. In the event of a fault the unit will handle  $500\text{A}$  peak— $250\text{A}$  mean half cycle. Provision is made for limiting the surge current to lower values if desired. Connected across the two supply terminals, the unit takes less than  $10\text{mA}$  drain at all voltages. The unit is compact—approximately  $65 \times 40 \times 50\text{mm}$ . Access to the voltage adjustment potentiometer is through a hole adjacent to the terminals. The unit will operate in an ambient temperature range from  $-40^\circ$  to  $+65^\circ\text{C}$ . ITT Components Group Europe, Rectifier Product Division, Edinburgh Way, Harlow, Essex.

WW 319 for further details.
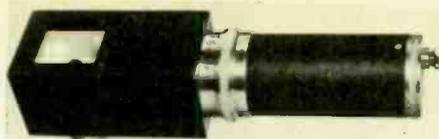
### Colour Monitor Calibrator

The Grafikon calibrator is a hand-held optical instrument that enables the white point of a colour monitor or receiver to be visually set. The instrument is offered up to the tube face and the monitor controls are adjusted to make the colour picture match the instrument's reference colour. The comparison between the monitor and the reference is seen in a Lummer Brodhun photometer cube. The reference colour is obtained from a tungsten halogen lamp and glass filter and is diffused to form a very even reference field. The lamp current is electronically stabilized to ensure that its col-



our is the same each time it is switched on while the tungsten halogen cycle in the lamp maintains its long-term colour stability. A mechanical iris is incorporated to adjust the brightness of the reference field to any grey scale step. This ensures that the reference colour remains the same for all values of brightness. Grafikon Engineers Ltd, 75 South Western Road, Twickenham, Middx.

WW 331 for further details.

### Transportable Insulation Tester

Miles Hivolt offer a transportable insulation test set for measuring leakage currents down to  $0.01\ \text{A}$  at up to  $30\text{kV}$  d.c. It can be driven from the mains or from rechargeable  $24\text{V}$  batteries which give four hours' use at full load, the equivalent of many days' normal use. Mains input is  $100\text{-}125\text{V}$  or  $200\text{-}250\text{V}$  at  $45\text{-}66\text{Hz}$ . The output voltage is available in two ranges  $0.5\text{-}5\text{kV}$  and  $3\text{-}30\text{kV}$ . The output voltage is measured at two ranges  $5\text{kV}$  and  $30\text{kV}$  with full-scale deflections. Maximum output current is  $200\ \text{A}$  at full voltage with higher currents at lower voltages. The equipment weighs  $11.5\text{kg}$  with either battery or mains power unit fitted. Miles Hivolt Ltd, Riverbank Works, Old Shoreham Road, Shoreham-by-Sea, Sussex.

WW 313 for further details.

### 40-MHz Counter/Timer

A solid-state  $40\text{-MHz}$  counter/timer, the TF2414A, with  $10\text{mV}$  sensitivity is available from Marconi Instruments. Advantages include time interval measurement down to  $1\ \mu\text{s}$ , period and multi-period measurement,  $1\text{M}\ \Omega$  input impedance and display memory. Direct frequency measurement is provided up to  $40\text{MHz}$ . A special version TF2414A/2M is designed for use with the M.I. frequency converters (TF2400 series) which extend the frequency range up to  $500\text{MHz}$ . Another version, TF2414A/1 provides a printer output facility supplying a 1-2-4-8 b.c.d. output code for each digit displayed. Stability and accuracy are determined by an oven-controlled crystal oscillator. Circuits incorporate discrete and integrated silicon semiconductors on plug-in printed boards. The display memory maintains the readout while the count is in progress, thus giving a continuous coherent readout. The crystal oscillator has stability of typically  $1 \times 10^{-6}$  over three months and temperature co-efficient of  $\pm 5 \times 10^{-7}$  per  $^\circ\text{C}$ . A standard frequency output is available from the internal reference



oscillator through a front panel socket over a range from  $0.1\text{Hz}$  to  $1\text{MHz}$  (selected by the range switch). Price  $\pounds 298$  f.o.b. U.K. Marconi Instruments Ltd, Longacres, St. Albans, Herts.

WW 311 for further details.

### Add-on Transmitter Amplifier

A wideband untuned solid-state linear transmitting amplifier covering the frequency range  $2\text{-}30\text{MHz}$ , intended as an add-on unit to a low-power transmitter/receiver such as a packset, has been developed by The M.E.L. Equipment Company Ltd. It has an output of  $100\text{W}$  p.e.p. and is designed for a transmitter, the




output of which is not less than  $5\text{W}$  p.e.p. It operates from d.c. supplies of  $10\text{-}30\text{V}$  without need for voltage adjustment. The power supply is self-contained, and provides a supplementary output of  $20\text{W}$  at  $24\text{V}$  d.c. for the associated packset. It is sealed, operable at ambient temperatures from  $-15^\circ\text{C}$  to  $+55^\circ\text{C}$  and meets the durability requirements of DEF 133 (L3). Designated type BA.1013/01 the amplifier measures  $310\text{mm}$  wide by  $300\text{mm}$  deep by  $116\text{mm}$  high. The M.E.L. Equipment Company Ltd, Manor Royal, Crawley, Sussex.

WW 335 for further details.
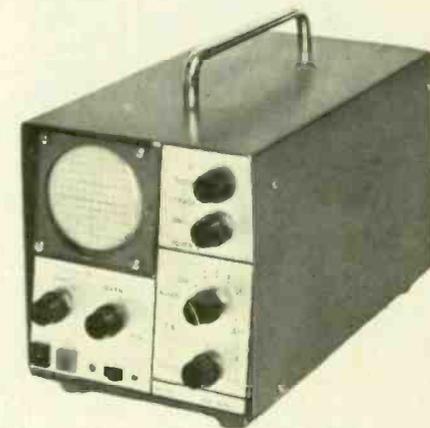
### Educational oscilloscope

An oscilloscope, Mitre type EA0699-1, intended for use in schools, in service workshops and in other equipment as a built-in monitor, has a Y bandwidth of d.c.




to  $100\text{kHz}$ . The instrument costs  $\pounds 24.10\text{s}$ . (discount for schools) and features a Y sensitivity of approximately  $100\text{mV/cm}$  at maximum gain with full Y shift. The timebase range covers approximately  $100\text{ms/cm}$  to  $10\ \mu\text{s/cm}$  and is automatically synchronized. The X input required is  $1\text{V/cm}$  with full X shift when the timebase is switched off. Flyback suppression and access to Y plates

are also featured. Power supply required is 25W at 200 to 250V, 50 to 60Hz. Mitre Electronic Products, 22 Powis Terrace, London W.11.

**WW 304 for further details.**
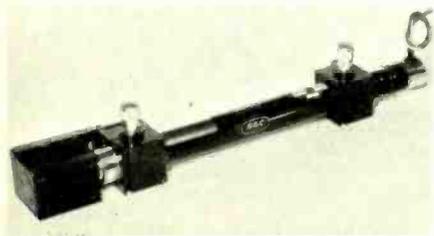
## Broad-band Travelling-wave Amplifier

The TWS23 travelling-wave amplifier from the M-O Valve Company has an output of greater than 10W flat to better than 3dB and at a gain of at least 26dB in the frequency range 2.0 to 4.0GHz, whilst, by adjusting helix voltages, it is possible to




obtain power outputs of over 20 watts at spot frequencies. The tube is packed in a permanent magnet focusing mount, and r.f. coupling is by means of a type N 50 connector. Cooling may be by either conduction or convection, according to specification. The M-O Valve Co. Ltd, Brook Green Works, London W.6.

**WW 322 for further details.**
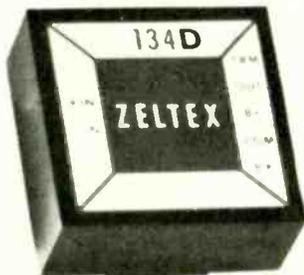
## F.E.T.—input Op. Amp.

Advance Industrial Electronics have available a low-cost general purpose Zeltex operational amplifier, Model 134D which can be used in differential, inverting and non-inverting circuits. Typical voltage drift is 50  $\mu$ V/ $^{\circ}$ C. Typical input bias current is 50pA. Initial offset voltage can be adjusted to zero with an external potentiometer. The unit is short-circuit proof to ground. The amplifier housed in a



plastic/epoxy case can be mounted directly on a p.c. board or plugged into a mating connector. Specification includes an output of  $\pm$ V at 4mA, a d.c. gain of 50,000, and a gain/bandwidth product of 1.3 MHz. Frequency at full output is 100kHz. The slew rate is 6V/s and operating temperature  $-25$  to  $+85^{\circ}$ C. Price is £8 5s. Advance Institute Electronics, Raynham Road, Bishops Stortford, Herts.

**WW 333 for further details**

## V.L.F. Third-octave Analyser

AIM Electronics have announced a third-octave frequency analyser (TOF 260A) with a frequency range extending from 0.5Hz up to 100kHz and covering any eight octaves in this frequency range. The octaves

covered are pre-set to customer requirements. The unit consists of twenty-four filters, each covering one-third of an octave, designed in accordance with BS2475:1964 (which recommends centre frequencies and equivalent bandwidth of the filter elements). Each filter may be attenuated by 0-100% by adjustment of a ten-turn calibrated potentiometer. The outputs from all the filters are combined at the output socket. Thus any combination of filters may be selected by adjustment of the attenuators. Typical applications include extraction of third-octave information from unknown waveforms and simulating the characteristic noise of any low-frequency excitation (e.g. vibrations) by selective filtering of white noise. Price £600. AIM Electronics Ltd, Bar Hill, Cambridge, CB3 8EZ.

**WW 323 for further details.**

## Transistor Amplifier for 1–2 GHz

Electro/Data Inc. have developed a broad-band transistor amplifier for the range 1 to 2 GHz. The new amplifier, designated Model A-12, has a 15dB gain response from 1 to 2 GHz with greater than 10dB of gain from 700 MHz to 2.2 GHz. The



amplifier's noise figure is 6dB typical with a maximum value of 8dB. It has miniature 50  $\Omega$  input and output connectors and a shielded d.c. bias input. A single, negative 12V, 14mA source is required for biasing. Two or more units can be cascaded to provide increased gain, with minor changes in passband ripple and bandwidth. The amplifier has linear gain for output signals up to  $-10$ dBm. Electro/Data Inc., 1621 Jupiter Road, Garland, Texas 75040, U.S.A.

**WW 314 for further details.**

## Modulation Meter

Type 785 modulation meter from Dymar is a solid-state instrument for the measurement of the depth of modulation in a.m. transmitters or the frequency deviation in the case of f.m. transmitters. It is specifically designed for narrow deviation transmitters in mobile and portable v.h.f. radiotelephones, the most sensitive deviation range being 3kHz f.s.d. The frequency range covered is 30-480 MHz and the sensitivity over the whole of this range is better than 2.5mV in 50 ( $-40$ dBm) which permits loose coupling to the transmitter under test. The residual f.m. noise of the local oscillator is typically  $-44$ dB below 3kHz deviation with



the a.f. "voice" filter switched in. Auxiliary outputs are provided at the i.f. (500kHz) and the demodulation audio frequency. This permits viewing of the modulation waveforms on an oscilloscope or applying it to distortion analyzers. Price £240. Dymar Electronics Ltd, Colonial Way, Radlett Road, Watford, Herts.

**WW 327 for further details.**

## Analogue Switches

A range of m.o.s.a.i.c. analogue switches, the ML150 series, has been introduced by Plessey. The switches, with full gate-control isolation and gate-oxide protection, are available in 6-way multiplexer, dual sample/hold and 3-bit digital-to-analogue configurations. The MPI30 series provide matching drive circuits for ML150. The large negative output voltage swings of these circuits (30V) are particularly suited to driving m.o.s. analogue switches. Plessey Microelectronics, Cheney Manor, Swindon, Wilts.

**WW 324 for further details.**

## Continuous Tape-Transport System

A continuous magnetic tape-transport system—MTD 10500—is announced by Recording Designs Ltd. The system comprises three basic models, write only, read only and write/read. Each has variants to suit a range of requirements. The same tape-transport technique is used for each with modular electronics to give particular system characteristics. Seven- and nine-track versions are available each with bi-directional transport speeds from 4 to 37.5 i.p.s. as standard, and an optional speed-range of between 1 and 75 i.p.s., if required. Slew-mode speed (for high-speed inter-block gap detection) is 120 i.p.s. Start and stop speed times are less than 20ms in the standard speed range. Recording densities of 200, 556 and 800 b.p.i. are available. Recording Designs Ltd, Blackwater Station Estate, Camberley, Surrey.

**WW 332 for further details.**

## Low-pass Active Filters

Lionmount are manufacturing low-pass active filters which can be varied continuously throughout the passband. Two types are available; one of which covers the range 1 to 10kHz in one band; the other covering the frequency range 1Hz-10kHz in four switched bands. The designs are based on



9th order Butterworth or Chebychev configuration and can realize 80dB/decade attenuation at cut off. The filters will accept an input voltage of  $\pm$ 10V peak and may be loaded with a minimum of 2,000  $\Omega$ . Lionmount & Co. Ltd, Bellevue Road, New Southgate, London N.11.

**WW 318 for further details.**

# January Meetings

*Tickets are required for some meetings: readers are advised, therefore, to communicate with the society concerned*

## LONDON

6th. I.E.E. "Marketing and the component engineer" by R. H. W. Burkett at 17.30 at Savoy Pl., W.C.2.

6th. I.E.E.—Discussion on "The Haslegrave report on technician courses and examinations" at 18.00 at the London School of Hygiene and Tropical Medicine, Keppel St., W.C.1.

7th. R. Soc.—Juvenile lecture "Television at school" by Dr. R. C. G. Williams at 14.30 at John Adam St., W.C.2.

7th. I.E.E.—"Positional transducers and precision electronic measurements" by P. C. F. Wolfendale at 18.00 at 9 Bedford Sq., W.C.1.

9th. I.E.E. "Tellegen's Theorem: an unusual theorem of wide circuit application" by Dr. R. Spence at 17.30 at Savoy Pl., W.C.2.

12th. I.E.E.—"Phasor diagrams". Discussion led by M. G. Scroggie at 17.30 at Savoy Pl., W.C.2.

13th. I.E.E.—Discussion on "Prospects for ultra-high-frequency f.e.t.s" at 17.30 at Savoy Pl., W.C.2.

13th. I.E.E./I.E.E.—"Physiology for engineers—control of circulation" by Dr. I. Gabe at 18.00 at St. Bartholomew's Hospital Medical Coll., E.C.1.

14th. I.E.E.—"Changing relations between science and technology and their effect on international co-operation" by Dr. A. P. Speiser at 17.30 at Savoy Pl., W.C.2.

14th. I.E.E.—"U.H.F. television transposer equipment" by W. L. Gregory at 18.00 at 9 Bedford Sq., W.C.1.

20th. I.E.E.—"The British Calibration Service" by H. E. Barnett at 17.30 at Savoy Pl., W.C.2.

20th. I.E.E.—"Power semiconductor electronics" by R. G. Dancy at 18.30 at the London School of Hygiene, Keppel St., W.C.1.

21st. S.E.R.T.—"The new I.V.C. colour video tape recorder" by R. A. Calaz at 19.00 at London School of Hygiene, Keppel St., W.C.1.

22nd. J.E.E.—"Devices using tunnelling super-currents" by Dr. B. D. Josephson at 17.30 at Savoy Pl., W.C.2.

23rd. Brit. Acous. Soc.—Symposium on "Electroacoustics in air and water" at 10.00 at 1 Birdcage Walk, S.W.1.

26th. I.E.E.—"Satellite television distribution" by A. K. Jeffris, D. G. Pope and P. C. Gilbert at 17.30 at Savoy Pl., W.C.2.

28th. I.E.E.—Colloquium on "Systems engineering and its educational impact" at 18.00 at 9 Bedford Sq., W.C.1.

30th. I.E.E.—"Radar echoes from clear air in relation to refracting-index variations in the troposphere" by J. A. Lane at 17.30 at Savoy Pl., W.C.2.

## BELFAST

21st. I.E.E.—"Air traffic control" by David Evans at 18.30 at Ashby Institute, Queens University, Stranmillis Road.

## BIRMINGHAM

26th. I.E.E./I.P.O.E.—"Operational experience with p.c.m. systems" by D. Cleobury at 18.00 at M.E.B., Summer Lane.

## BOLTON

12th. I.E.E.T.E.—"The origins of electrical communications" by J. Dalton at 19.30 at Institute of Technology, Deane Rd.

## BRISTOL

15th. I.E.E./R.Ae.S./I.E.E.—"B.A.C. satellites" by G. Crowder at 19.00 at Filton House Conference Room, Filton.

## CAMBRIDGE

29th. I.E.E./I.E.E.—"Tuning of Gunn effect oscillators" by P. W. Crane at 18.30 at University Engineering Laboratories, Trumpington Street.

## CARDIFF

14th. I.E.E.—"Electronics for process control instrumentation" by J. Seers at 18.30 at University of Wales Institute of Science and Technology.

16th. S.E.R.T.—"Educational use of C.C.T.V." by T. Evans at 19.30 at College of Further Education, Cyncoed.

22nd. R.T.S.—"Television transmission equipment in education" by W. D. Kemp at 19.00 at B.B.C., Llandaff.

## CHATHAM

15th. I.E.E.—"The engineer in management" by F. Oakes at 19.00 at Medway College of Technology.

## CHELMSFORD

19th. I.E.E./I.E.E.—"Radar ornithology" by Dr. E. Eastwood at 18.30 at the Civic Centre, Duke Street.

## EDINBURGH

7th. I.E.E.—"Pulse code modulation for point-to-point music transmission" by E. Rout at 19.00 at Napier College of Science and Technology, Colinton Road.

20th. I.E.E.—"The electronics industry in Scotland—past, present & future" by I. MacDonald at 18.00 at the Carlton Hotel.

## FARNBOROUGH

22nd. I.E.E./I.E.E.—"Speech and vocoders" by L. C. Kelly at 19.00 at the Technical College.

## GLASGOW

8th. I.E.E.—"Pulse code modulation for point-to-point music transmission" by E. Rout at 19.00 at the Institution of Engineers and Shipbuilders, 183 Bath St., C.2.

## LEEDS

6th. I.E.E.—"The automatic landing of aircraft" by S. A. W. Jolliffe at 18.30 at the University.

## LEICESTER

20th. I.E.E.—"Static inverters and their applications" by E. W. Porter and R. J. Green at 18.30 at the University.

29th. I.E.E.—"The latest techniques in computer-aided electronic design" by E. Wolfendale at 18.30 at the City Polytechnic.

## LIVERPOOL

5th. I.E.E.—"Communications for people at work and at play" by D. G. Holloway at 18.30 at the University.

7th. I.E.E. (Grads.)—"Low and medium frequency noise in transistors" by Dr. K. F. Knott at 18.30 at M.A.N.W.E.B. Elec. Indus. Development Centre.

19th. I.E.E.—"Electronics in automobiles" by W. G. Hill at 18.30 at the University.

22nd. I.E.E. (Grads.)—"Developments in radio control" by J. R. Francis and R. T. King at 18.30 at M.A.N.W.E.B. Elec. Indus. Development Centre.

29th. I.E.E.—Faraday Lecture "People, communications and engineering" by J. H. H. Merriman at 10.15 and 14.30 (students) and 18.45 (public) at the Philharmonic Hall.

## MANCHESTER

7th. I.E.E./I.E.E.—"On the future of world communications" by Prof. C. Cherry at 18.15 at U.M.I.S.T.

28th. I.E.E. (Grads.)—"Radio interference from high-voltage transmission line conductors" by M. G. Faulkner at 18.45 at U.M.I.S.T.

## NEWCASTLE-UPON-TYNE

7th. S.E.R.T.—"Tandberg audio" by A. W. Dakin at 19.30 at Charles Trevelyan Technical College, Maple Terrace.

14th. I.E.E.—"Electronic telephone exchanges" by V. E. Mann at 18.00 at Dept. of Physics and Physical Electronics, Rutherford Coll., Ellison Pl.

14th. I.E.E.T.E.—"Decca navigational system" by A. Brooker-Carey at 19.30 at Rutherford College of Technology, Ellison Place.

26th. I.E.E.—"The application of electronic engineering to road safety" by D. G. W. Mace and S. Penoyre at 18.30 at the Polytechnic.

## NEWPORT

21st. I.E.E.T.E.—"Change to metric" by G. Esplin at 19.30 at College of Technology, Allt-Yr-Yn Avenue.

## NOTTINGHAM

13th. I.E.E.—Faraday Lecture "People, communications and engineering" by J. H. H. Merriman at 14.30 (students) and 19.15 (public) at Albert Hall.

## OXFORD

14th. I.E.E.—"Tomorrow's world—use of satellites for communication" by W. J. Bray at 19.00 at College of Technology, Headington.

## PRESTON

14th. I.E.E.—"Metrication" by T. C. Campbell at 19.30 at Yorella Restaurant.

## READING

22nd. I.E.E.—"M.O.S. devices in l.s.i." by G. E. Stevenson at 19.30 at J. J. Thomson Physical Laboratory, the University, Whiteknights Park.

## RUGBY

20th. I.E.E. (Grads.)—"Brain cell to microcircuit (pattern recognition)" by Dr. I. Aleksander at 18.15 at the College of Engineering Technology.

## SOUTHAMPTON

27th. S.E.R.T.—"Field effect transistors" by G. A. Allcock at 19.30 at the College of Technology, East Park Terrace.

28th. I.E.E.—"Electronic character recognition" by R. H. Britt at 18.30 at the Lanchester Theatre, University.

## STEVENAGE

12th. I.E.E.—"Current electronic developments in the deep sea fishing industry" by P. J. Hearn at 19.30 at the College of Further Education.

## STOKE-ON-TRENT

15th. I.E.E.—Faraday Lecture "People, communications and engineering" by J. H. H. Merriman at 14.30 (students) and 19.30 (public) at Victoria Hall, Hanley.

## SUNDERLAND

22nd. I.E.E. (Grads.)—"Pulse code modulation" by J. Hutton at 18.30 at the Polytechnic.

## WEYMOUTH

29th. I.E.E.—"Applications of integrated circuits" at 18.30 at South Dorset Technical College.

## WOLVERHAMPTON

7th. I.Prod.E./I.Mech.E.—"C.E.I. as a professional union" by K. M. Platt at 19.15 at Stafford College of Technology, Beacon Side.

# Test Your Knowledge

Series devised by L. Ibbotson\*, B.Sc., A.Inst.P., M.I.E.E.,

M.I.E.R.E.

## 20. Colour

In all the questions it is assumed that the viewer has normal colour vision.

1. Select from the colours quoted below the one which does not appear in the spectrum of white light:
  - (a) orange
  - (b) yellow
  - (c) purple
  - (d) violet.
2. From the spectral colours below select the one which is associated with the highest frequency of radiation:
  - (a) red
  - (b) blue
  - (c) green
  - (d) blue-green.
3. Three light sources of the same area give monochromatic radiation of colours red, green and blue respectively, and have equal luminosity (appear equally bright). The intensity of radiation:
  - (a) is the same for all three
  - (b) is least for the red
  - (c) is least for the green
  - (d) is least for the blue.
4. Evidence suggests that the human brain distinguishes between different colours by the relative stimulation of optical receptors having different frequency responses, in the eye. The theory is that:
  - (a) each "cone" in the retina has a frequency response curve which is slightly different from all the others
  - (b) a separate type of receptor responds to each spectral colour
  - (c) only three distinct frequency-response characteristics are involved
  - (d) only two distinct frequency-response characteristics are involved
5. Monochromatic light of wavelength  $580m\mu$  is seen as yellow. It therefore follows that any light entering the eye which appears to have the same hue:
  - (a) must consist of monochromatic light of wavelength  $580m\mu$
  - (b) may contain many frequencies, but must have maximum energy flux at  $580m\mu$
  - (c) must contain some energy at wavelength  $580m\mu$ , but not necessarily have maximum energy flux at this wavelength
  - (d) need not contain any energy at  $580m\mu$  wavelength
6. True white light is:
  - (a) light with equal energy at all frequencies in the visible range
  - (b) light with a spectral distribution the same as that emitted by the sun
  - (c) the light emitted by a "black body" at a temperature of  $5200^{\circ}\text{K}$
  - (d) an inexact concept which is defined differently in different circumstances.
7. A single monochromatic light can be rendered colourless (giving the sensation of white) by the addition of a suitable quantity of another monochromatic light:
  - (a) whatever the colour of the original light
  - (b) unless the original light is in the red region of the spectrum
  - (c) unless the original light is in the green region of the spectrum
  - (d) unless the original light is in the blue region of the spectrum.
8. White light falls on an object which absorbs in the blue, but reflects other frequencies. The colour of the object will be seen to be:
  - (a) yellow
  - (b) green
  - (c) red
  - (d) purple.
9. Monochromatic yellow light from a sodium lamp falls on an orange (fruit). The colour of the orange when viewed in this light will be:
  - (a) very pale orange
  - (b) low intensity orange
  - (c) yellow
  - (d) black.
10. If white light is added to light of any given colour the result is:
  - (a) a change in hue, but no change in saturation of the colour
  - (b) a change in saturation, but no change in hue
  - (c) a change in both hue and saturation
  - (d) if the original light was monochromatic a change of saturation only, otherwise a change of both hue and saturation.
11. A particular green light has a radiant flux density of 1 watt per square metre. To this light is now added 1 watt per square metre of pure violet light. The effect will be:
  - (a) a considerable change in colour, but little change in luminance
  - (b) a large increase in luminance, but little change in colour
  - (c) little change in either colour or luminance
  - (d) a large change in both colour and luminance.
12. Discounting luminance information, the colour of a light can be specified entirely using:
  - (a) one variable
  - (b) two variables
  - (c) three variables
  - (d) seven variables.
13. If three colours are located on the chromaticity diagram, then mixtures of varying (positive) quantities of light of these three colours will produce only:
  - (a) all colours within the spectral locus (all realisable colours)
  - (b) all colours inside the triangle having the given three colours at the corners
  - (c) all colours outside the triangle having the given three colours at the corners
  - (d) all colours on straight lines joining the three given colours.
14. By mixing, in appropriate quantities, fully saturated red, green and blue light it is possible to produce light:
  - (a) of all colours (all hues and saturations)
  - (b) of every hue, but not all saturations
  - (c) over a restricted range of hues, but with all saturations in that range
  - (d) over a restricted range of both hues and saturations.
15. If ideal phosphors could be developed which produced monochromatic red ( $700m\mu$ ), green ( $520m\mu$ ) and blue ( $450m\mu$ ) light, these could be used, with advantage, at the output of a colour television system. The camera filters at the input of the system would require:
  - (a) to pass bands of frequencies, as narrow as possible, at the quoted wavelengths
  - (b) to have broad overlapping frequency transmission characteristics with maximum transmissions at the quoted wavelength values
  - (c) to have pass-bands which met but did not overlap, so as to divide the visible spectrum into three bands centred on the three quoted wavelengths
  - (d) to have pass-bands between the quoted wavelength values.

\*West Ham College of Technology, London E.15.

# Literature Received

"Gramophone-record reproduction: development, performance and potential of the stereophonic pickup" is the title of an article reprinted from *Proceedings I.E.E.*, Vol. 116, No. 8, August 1969, which is available from Shure Electronics Ltd, 84 Blackfriars Road, London S.E.1 .....**WW434**

Photain Controls Ltd, Radalls Road, Leatherhead, Surrey, have produced a leaflet which describes their range of photocell lamp modules intended for use in automatic gain control circuits, stepless speed control for motors and modulation circuits, etc .....**WW435**

The eight digital electronic counters in the Dana series 8100 range of automatic counters are described in a brochure from Dana Electronics Ltd, Bilton Way, Dallow Road, Luton, Bedfordshire .....**WW436**

The new 7000-series of oscilloscopes from Tektronix, which includes two oscilloscope main-frames with a choice of six vertical amplifiers, four timebase units and three sampling units, are described in a booklet which may be obtained from Tektronix UK Ltd, Beaverton House, Harpenden, Herts .....**WW437**

We have received the following publications from Marconi Instruments Ltd, Longacres, St. Albans, Herts.

- Catalogue 1969-70. A very large catalogue which lists a vast range of electronic measuring equipment .....**WW438**
- "MI Bargain Buys". This month's special offers .....**WW439**

## ACTIVE DEVICES

"The use of Coaxial-Package Transistors in Microstripline Circuits" is the title of Application Note AN-4025 which has been published by RCA Electronic Components, Harrison, New Jersey 07029, U.S.A. ....**WW401**

Dickson Electronic Corp's field-effect and bipolar transistors in l.i.d. chip assemblies are described in a 19-page brochure which may be obtained from Dage (Great Britain) Ltd, 1 Penn Place, Rickmansworth, Herts. ....**WW403**

"Semiconductor Summary 1969/70" is the title of a short-form catalogue available from ITT Electronic Services, Standard Telephones and Cables Ltd, Edinburgh Way, Harlow, Essex. ....**WW404**

Ferranti Ltd., Gem Mill, Chadderton, Oldham, Lancs, have produced some additions for their Microspot c.r.t. manual. This includes a contents sheet and provisional data on the types 1B/97, 12H/40, 14/08, 16A/19, 16A/40, 21B/10 cathode-ray tubes, the DY605 electronic display equipment and the PD5002 solid-state light source. ....**WW405**

The semiconductor products of SGS (UK) Ltd, Planar House, Walton Street, Aylesbury, Bucks, are listed in two catalogues which are available price 21s each.  
Consumer devices. Professional discrete devices

## PASSIVE COMPONENTS

Airpax Electronics, of Cambridge, Maryland 21613, U.S.A., have produced the following two leaflets.

- "The Choice of Protection" discusses the use of mechanical methods of protecting electrical and electronic circuits from the effects of short circuits .....**WW411**
- A catalogue listing semiconductor fuses .....**WW412**

A new edition of the Amphenol catalogue describing miniature circular connectors has just been released. It is available from Amphenol Ltd, Thanet Way, Whitstable, Kent .....**WW413**

Programming systems produced by Oxley Developments Co., Priory Park, Ulverston, Lancs, are the subject of a new catalogue .....**WW414**

"Professional Communications Antenna Systems" is the title of a catalogue available from Antenna Specialists UK Ltd, 1 Euston Road, London N.W.1 .....**WW415**


Full details of a range of edge connectors are given in the well illustrated catalogue "Metal Plate Connector Guide", available from Elco Corporation, Willow Grove, Pa. 19090, U.S.A. ....**WW416**

An article entitled "Understanding Thermocouples" that originally appeared in our sister journal *Instrument and Control Engineering* has now been reprinted and is available from IPC Business Press (Sundry Sales Department), 161-166 Fleet Street, London E.C.4. Price 6s 9d, including postage.

## EQUIPMENT

An effects generator which can be used to produce sound effects for radio and TV programme inserts, and public address announcements is described in a leaflet from the manufacturers Mellotronics Ltd, 28-30 Market Place, London W.1 .....**WW433**

## H.F. Predictions—January

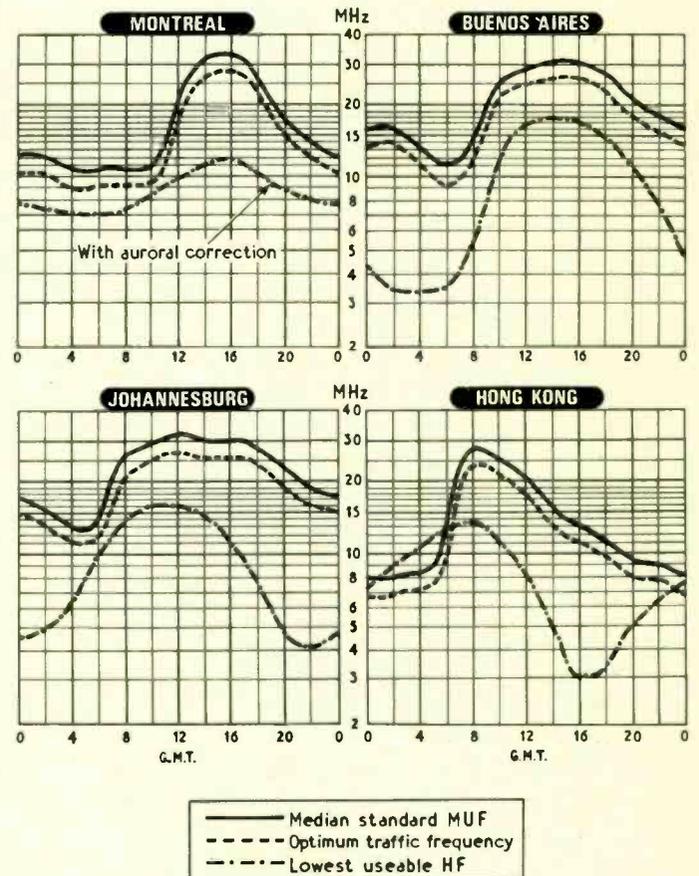

Winter season conditions will continue with a large differential between day and night frequencies except on some routes which show a secondary peak a few hours before dawn. At sunrise and sunset, therefore, the rate of change of MUF is at its greatest and it becomes difficult to maintain satisfactory communication over these periods. On shorter routes, generally less than 2000 km, the daytime MUFs in winter may be lower than in summer when propagation is via the E layer.

The LUFs shown were calculated by Cable and Wireless Ltd for reception in the United Kingdom of point-to-point telegraph services. For other services the curves would be displaced vertically, the exact amount depending on service and equipment parameters.

# Answers to "Test Your Knowledge"

## Questions on page 45

1. (c) No single monochromatic radiation produces the sensation purple; it requires a mixture from the two ends of the spectrum. If monochromatic red light of wavelength 700  $m\mu$  and monochromatic violet of wavelength 400  $m\mu$  (the normally accepted ends of the spectrum) are mixed in various proportions, then the range of "pure" purples is produced.

2. (b)

3. (c) Since the eye is most sensitive to light in the green part of the spectrum, far less energy-flux density is required to produce a given luminance of green light than is required for the same luminance of red or blue. Note that the term "monochromatic" is used to describe radiation of one single wavelength (or, in practice, since this is impossible, over a very narrow band) even though in the present context it may seem inappropriate.

4. (c) The details of the mechanism are still not known.

5. (d) Suitable quantities of light of other wavelengths can produce a similar stimulus in the colour receptors. If spectral green and red are used the result will have the same saturation as well as the same hue.

6. (d) The lights described in (a), (b) and (c) are all forms of white light, although their spectral energy distributions are somewhat different. The standard of white used in television is the colour of a light produced by a particular combination of a tungsten lamp and a filter, known as "standard illuminant C".

7. (c) The complementary of green is purple, which is non-spectral.

8. (a) Yellow is the complementary of blue, so that removing blue from white leaves yellow.

9. (c) The orange, like most natural coloured objects, reflects light over a range of wavelengths, so that its colour, when illuminated by white light, is determined by the total effect of these on the eye. Since the orange is here illuminated with pure yellow it can only reflect yellow.

10. (b) This, and most other properties of colour, are well illustrated by the chromaticity diagram.


11. (a) Although wavelengths at the blue end of the spectrum contribute very little to the brightness of a light they have a very significant effect on its colour.

12. (b) These can be dominant wavelength and purity, or chromaticity co-ordinates (as in the chromaticity diagram). This is why colour information in colour television can be carried by two signals.

13. (b)

14. (b) Reference to the chromaticity diagram shows that no triangle with its corners on realisable colours, even on the spectral locus, can include the whole diagram.

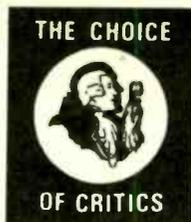15. (b) The total transmission characteristics for each of the three colour channels in the camera would require to be such that any incident radiation would produce relative responses in the three channels equal to the relative outputs from the three phosphors at the receiver required to produce its colour as nearly as possible.



# BULGIN PRECISION COMPONENTS

## PIONEERS FOR NEARLY 50 YEARS AND TODAY LEADING THE WORLD IN NEW ESSENTIAL COMPONENTS

The Bulgin policy of continued research and development has resulted in the introduction of many unique new Electronic Components during the past year. A few are illustrated here. B. 16, 17, 18 three-panel mounting Battery Holders accepting 1, 2, or 3 U2-sized cells respectively. SM. 257/2 + K. 515. Semi-rotary shaft operated D.P.C.O. moulded body switch rated 2A. at 250V A.C. D/S. 941/1 and /2. Illuminated Switch with a normally biased push action which can be locked in the depressed position. L.E.S. lamps, single (1/1) or twin (1/2) S.P.C.O. switch unit. SM. 301/2/PD moulded body. D.P.C.O. 8-contact switch for double-pole alternative circuit switching. Rated 3A. at 250V A.C. P. 537/Chrome or /Gold. Three pole side entry. BS. 666. jack plugs. K. 556/Legend. Collet fixing knob, dial and escutcheon unit which can have dial legending to customers' requirements.

B. 16-18

SM. 257/2 + K. 515 Knob

D/S. 941/1 & /2

SM. 301/2/PD.

P. 537/Chrome or /Gold

D/S. 890/SA. 2419

F. 316/S

D. 965, 966

K. 556/Legend

Example of Edge Legending

F. 296/S

F. 317, 318

P. 550

D/S. 890/SA. 2419 Switched. Legended Indicator. L.E.S. Lamps, with a choice of five lens colours which can be legended. Switching is D.P.C.O. push-push successive action rated 2A. 250V A.C. Other models have different switching arrangements. D. 965, 966 New L.E.S. Signal Lamps for direct connection to printed circuit boards with choice of five lens colours. transparent or translucent. F. 316/S Panel mounting fuseholder for 1" x 1/2"  $\phi$  fuses 15A. rating. F. 296/S Miniature panel mounting fuseholder for 5 x 20 mm. fuses. 5A. rating. SM. 324/2 Key operated D.P.C.O. moulded switch 2A. 250V A.C. rating. P. 550 unique 7 pole + earth inlet/outlet connector rated 6A. 250V A.C. F. 317, 318 Flush-fitting panel mounting fuseholder 5A. rating. F.317 1" x 1/4". F. 318 1 1/4" x 1/4" fuses. Edge Legending. All transparent knobs. K. 436-7 and 472-4 can have legending around the edges as well as on top surface.

FOR DETAILS OF THE COMPLETE RANGE SEND FOR BROCHURES REF. W.W./1.

**A. F. BULGIN & CO. LTD.,**  
Bye Pass Rd., Barking, Essex.  
Tel: 01-594 5588 (12 lines)

MANUFACTURERS AND SUPPLIERS OF RADIO AND ELECTRONIC COMPONENTS TO

ADMIRALTY	MINISTRY OF AVIATION	B.B.C.
WAR OFFICE	MINISTRY OF WORKS	G.P.O.
AIR MINISTRY	MINISTRY OF TECHNOLOGY	I.T.A.
HOME OFFICE	RESEARCH ESTABLISHMENTS	N.P.L.
CROWN AGENTS	U.K.A.E.A.	D.S.I.R.

WW-071 FOR FURTHER DETAILS

# Real & Imaginary

by Vector

## “Yellow, and black, and pale and hectic red,”

As I write, the persuaders have just begun their honeyed blandishments in the Press, on sound radio and on television.

Like those purposeful citizens who make a crust by robbing strongrooms, the colour vendors use an oblique approach. Just as cracksmen traditionally begin operations in the cellars of the house next door to the bank, so do our persuaders tunnel into your private strongroom at your weakest point, namely the Little Woman and to some extent the kids, because these, as a generalization, look at the box a lot more than you do.

At present several of the channels are hard at it, backed by powerful newspaper and magazine campaigns—‘it’ in this case being the task of making you feel a second-class citizen if you are still viewing in unnatural monochrome.

Every day now, and far into the night, the B.B.C. and I.T.A. are firing continual salvos extolling the merits of colour. What does astonish me is that, at the time of writing, I haven’t seen any advertisement emanating from a radio manufacturer on any of the channels.

Should any reader be reaching for his pen to remind me that the I.T.A. is the only organization permitted to carry advertising, stay your hand. While it is true that the B.B.C. does not lend itself to the sordid business of raking in money in return for advertising time, there are other, and more gentlemanly, ways of going about it, as any press relations officer worth his salt could tell you.

One such is for the would-be advertiser to latch on to some national sport or cult. One of your first acts is to present a handsome trophy which has the name of your product indissolubly attached to it; all you have to do then is to sit back and wait for the event to be televised.

Another method is to plaster the railings of the more dynamic association football clubs with advertisements of your product. Try as he may, the cameraman will have to have the railings in the picture for a good deal of the time and so, given a little luck, you have a free plug both on B.B.C. and I.T.A. for about nine months in any given year.

I see the B.B.C. is making a platform of ‘natural television’. They did something similar some years ago in a drive to popularize the v.h.f. sound service. ‘High

quality’ was the torch carried then, but this was soon extinguished by the radio manufacturers, who shoved cheese-pared circuits into a small box, together with a tinpot loudspeaker, and tried to sell it as hi-fi.

And what *is* natural television, pray? If the term means anything it signifies that, colour-wise, the picture on the home screen is identical with the scene in the studio. That being so, I must say that I’m surprised that the B.B.C.’s technical boys have allowed their advertising colleagues to get away with it. For, given an additive system with all its registration problems, the inclusion of band-saving techniques, and colour filters with transmission characteristics which only approximate to those of the home receiver’s phosphors, then even the best colour monitors will not stand comparison with the actual scene.

It’s a pity to have selected such a sales story because it looks as if the experience of v.h.f. sound is going to be repeated with colour television, if the criminally maladjusted receivers to be seen all too often in dealers’ showrooms are anything to go by.

The public will swallow it of course for the same reason that, in 1922, it subscribed to the belief that an unbiased three-valve receiver feeding a ‘sugar-loaf’ horn loudspeaker was giving perfect quality. They believed it because the only standard of comparison was the acoustic gramophone and the quality of the ‘wireless’ was, in its day, marginally better than that. By the same token, today’s standard of comparison with a colour set is the monochrome receiver and therefore any colour, however unreal, is better than no colour at all. Provided that the sky is some shade of blue and the grass approximates to green, who cares about fidelity? Electronics engineers, certainly, and artists, perhaps, but precious few else. So there was really no need for the B.B.C. to oversell on fidelity.

Sticking my neck into the prophet’s noose, my guess is that colour television will take several years to become the norm in the average home and that not a few manufacturers will catch colds in the process.

What, I wonder, would happen if

someone came up with a colour system that was miles ahead of PAL? If there is any such lone inventor reading this, I would advise him that he is most unlikely to see his brain-child come into general use. For, with about £150M already invested in the present system, nobody is going to look kindly upon an invention that sets everyone back to square one.


What are the prospects of such a happening? Who knows? What would it be like, this super system? This also is anybody’s guess. Almost certainly, I would think, it would embody a subtractive colour system. It would also employ a translating interface which is much more in accord with the human eye-brain complex than is today’s television camera.

Our present system is a hangover from Clerk Maxwell, who was the first to show that three black-and-white transparencies can, under certain conditions, provide a picture in full colour. This is an application of the Young-Helmholtz trichromatic theory which is generally believed to form the basis of human colour vision in spite of some anomalies which cannot easily be explained away. No one, for instance, has positively identified three types of cone structure in the eye, one red-detecting, one green and one blue; all the cones seem pretty much the same. Then, a few years ago Dr. Edwin (“Polaroid”) Land demonstrated that two colours, or even one red light and one white, can interact to provide a gamut of colour. Even two monochromatic light sources will produce a wide variety of diluted colours. (This in fact was no new discovery; colour film processes, using two colours only, have been patented since the turn of the century.)


There is a growing awareness of the extreme complexity of the human eye and it is possible that further discoveries in this area may provide the electronics industry with important new thinking about television. We are moving away from comfortable concepts where, for instance, 500 m $\mu$  always equates with green light to quicksands where a body radiating at 500m $\mu$  appears to the eye as brilliant red. (Yes, I know it sounds daft but it can be done by interfering with the signals which trigger the brain into registering colour.) These coded signals are the core of the matter; if only the code could be broken, all sorts of possibilities exist. It might even be feasible to dispense with conventional displays and, instead, feed signals to the area behind the retina.

This sounds crackpot until we come to terms with the thought that colour sensations needn’t derive from incident light-frequency radiation. The coded signals to the brain can be affected in various ways; by mechanical vibration; by the application of external voltages or currents or by hallucinatory drugs. In the last-mentioned case manifestations occur which have every semblance of three-dimensional reality. Given an exact control of the input signals, what might not be possible? Even a degree of sight to the blind seems to be feasible.

# SINCLAIR IC-10

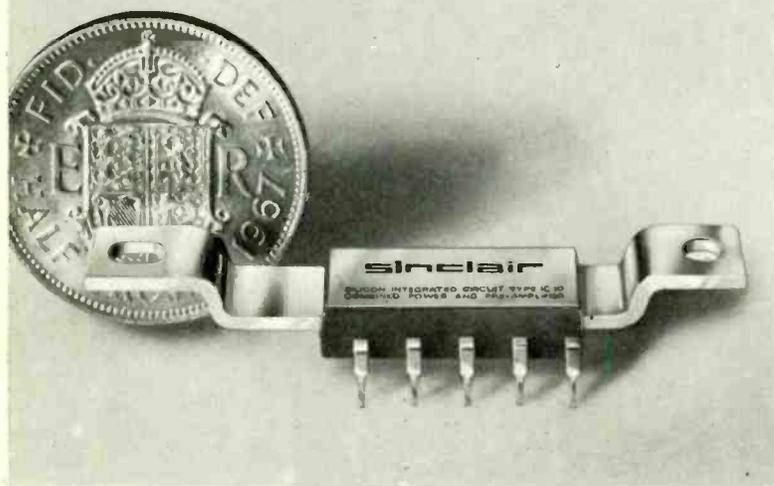
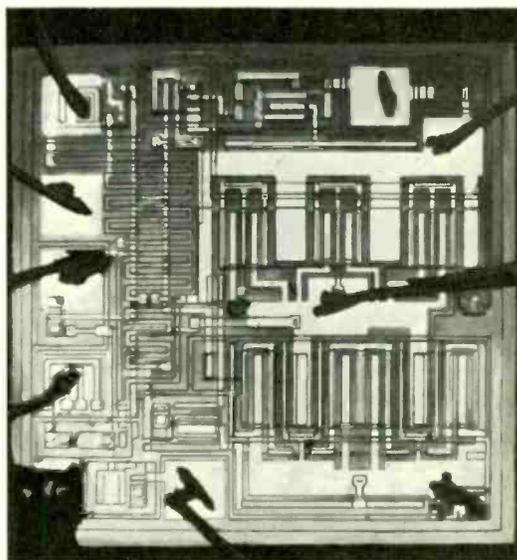
## MONOLITHIC INTEGRATED CIRCUIT AMPLIFIER AND PRE-AMP



*A 13 transistor circuit measuring only one twentieth of an inch square by one hundredth of an inch thick!*

# the world's most advanced high fidelity amplifier

The Sinclair IC-10 is the world's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself, a chip of silicon only a twentieth of an inch square by one hundredth of an inch thick, has 5 watts R.M.S. output (10w. peak). It contains 13 transistors (including two power types), 2 diodes, 1 zenor diode and 18 resistors, formed simultaneously in the silicon by a series of diffusions. The chip is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins. This exciting device is not only more rugged and reliable than any previous amplifier, it also has considerable performance advantages. The most important are complete freedom from thermal runaway due to the close thermal coupling between the output transistors and the bias diodes and very low level of distortion.

The IC-10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of such components as tone and volume controls and a battery or mains power supply. However, it is so designed that it may be used simply in many other applications including car radios, electronic organs, servo amplifiers (it is d.c. coupled throughout), etc. Once proven, the circuits can be produced with complete uniformity which enables us to give a 5-year guarantee on each IC-10, knowing that every unit will work as perfectly as the original and do so for a lifetime.

MORE SINCLAIR DESIGNS ON PAGES FOLLOWING



SINCLAIR RADIONICS LTD. 22 NEWMARKET ROAD, CAMBRIDGE  
Telephone: 0223 52731

### ■ SPECIFICATIONS

Output: 10 Watts peak, 5 Watts R.M.S. continuous  
 Frequency response: 5 Hz to 100 KHz  $\pm$  1dB  
 Total harmonic distortion: Less than 1% at full output.  
 Load impedance: 3 to 15 ohms.  
 Power gain: 110dB (100,000,000,000 times) total.  
 Supply voltage: 8 to 18 volts.  
 Size: 1 x 0.4 x 0.2 inches.  
 Sensitivity: 5mV.  
 Input impedance: Adjustable externally up to 2.5 M ohms.


### ■ CIRCUIT DESCRIPTION

The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. Class AB output is used with closely controlled quiescent current which is independent of temperature. Generous negative feedback is used round both sections and the amplifier is completely free from cross-over distortion at all supply voltages, making battery operation eminently satisfactory.
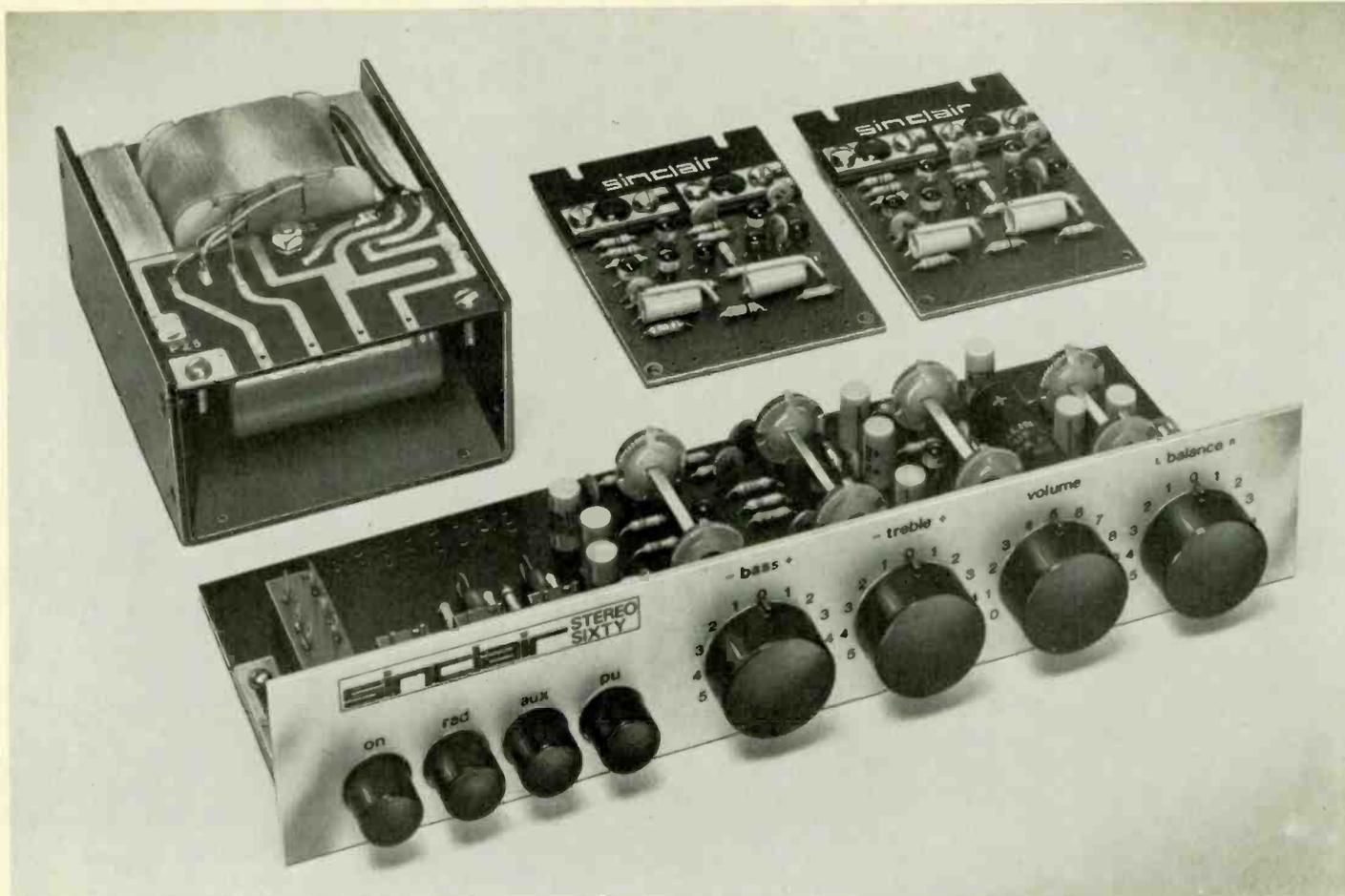
### ■ APPLICATIONS

Each IC-10 is sold with a very comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include stabilised power supplies, oscillators, etc. The pre-amp section can be used as an R.F. or I.F. amplifier without any additional transistors.

**SINCLAIR**  
**IC-10** with IC-10 manual and 5-year guarantee **59/6**  
 Post free.



## Project 60 an exciting alternative

The buyer of an amplifier today has a remarkably wide variety to choose from. It is unlikely that a purchaser would have real difficulty in finding a unit that met all his requirements, although the price might not be as low as could be wished. The only snags are that one's needs can change and that the technically correct amplifier may be physically inconvenient. If you are confident that there is an amplifier available, of the right size and price, which will meet all your needs for the foreseeable future, then that is your best buy. If not, however, we can offer you another possibility which we believe to be an exciting alternative approach. That alternative is **Project 60**.

Project 60 is a range of modules which connect together simply to form a complete stereo amplifier with really excellent performance. So good, in fact, that only 2 or 3 amplifiers in the world can compare with it in overall performance.

The modules are: 1. The Z-30 high gain power amplifier, which is an immensely flexible unit in its own right. 2. The Stereo 60 preamplifier and control unit. 3. The PZ.5 and PZ.6 power supplies. A complete system comprises two Z-30's, one Stereo-60 and a PZ-5 or PZ-6. The power supplies differ in that the PZ-6 is stabilised whilst the PZ-5 is not. This means that the former should be used where the highest possible

continuous sine wave rating is required. In a normal domestic application there will not be a significant difference between using either power unit unless loudspeakers of very low efficiency are being used.

All you need to assemble your system is a screwdriver and a soldering iron. No technical skill or knowledge whatsoever is required and, in the unlikely event of you hitting a problem, our customer service and advice department will put the matter right promptly and willingly.

Perhaps the greatest beauty of the system is that it is not only flexible now but will remain so in the future. We shall shortly be introducing additional modules which will include a comprehensive filter unit, a stereo F.M. tuner and an even more powerful amplifier for very large systems. These and all other modules we introduce will be compatible with those shown here and may be added to your system at any time.

Project 60 modules have been carefully designed to fit into virtually every known type of plinth or cabinet and templates provided enable you to position them. Only holes have to be drilled into the wood of the plinth and any slight slips here will be covered completely by the aluminium front panel of the Stereo 60. The Project 60 manual gives all the instructions you can possibly want clearly and concisely.

# sinclair

SINCLAIR RADIONICS LTD · 22 NEWMARKET ROAD · CAMBRIDGE  
Telephone: 0223 52731

WW—073 FOR FURTHER DETAILS

# Z-30 TWENTY WATT R.M.S. (40 WATT PEAK) POWER AMPLIFIER

The Z-30 is a complete power amplifier of very advanced design employing 9 silicon epitaxial planar transistors. Total harmonic distortion is incredibly low being only 0.02% at full output and all lower outputs. As far as we know, no other high fidelity amplifier made can match this specification, no matter what the price. Thus you can be utterly certain that your Project 60 system will do full justice to your other equipment however good it may be. The Z-30 is unique in that it will operate perfectly, without adjustment, from any power supply from 8 to 35 volts. It also has sufficient gain to operate directly from a crystal pickup. So in addition to its use in a high fidelity system you can use a Z-30 to advantage in your car or a battery operated gramophone for your children, for example. These, and many other applications of the Z-30, are covered in the Project 60 manual.

## SPECIFICATIONS

Power output—15 watts R.M.S. (30 watts peak) into 8 ohms using a 35 volt supply; 20 watts R.M.S. (40 watts peak) into 3 ohms using a 30 volt supply.

Output—Class AB.

Frequency response: 30 to 300,000 Hz  $\pm$  1dB.

Signal to noise ratio: better than 70dB unweighted.

Distortion: 0.02% total harmonic distortion at full output into 8 ohms and at all lower output levels.


Size: 3½ x 2½ x ½ inches.  
Input sensitivity: 250mV into 100 Kohms.  
Damping Factor: > 500.

Loudspeaker impedances 3 to 15 ohms.


Power requirements: 8 to 35 V.d.c.
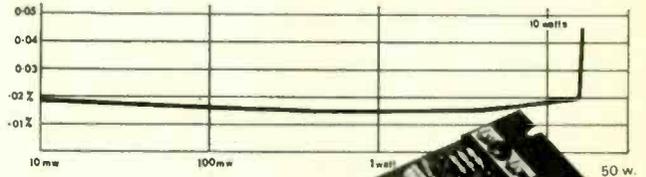
## APPLICATIONS

High fidelity amplifier; car radio amplifier; record player fed direct from pick-up; intercom; electronic music and instruments; P.A., laboratory work, etc. Full details of these and many other applications are given in the manual supplied with your Z.30.



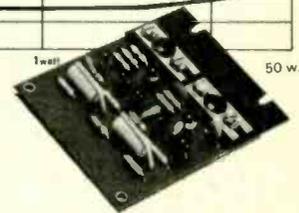Power versus distortion curve of Sinclair Z.30.



Z.30

Ready built, tested and guaranteed, with Z.30 manual.

89/6


# STEREO SIXTY PREAMPLIFIER AND CONTROL UNIT

The Stereo 60 is a stereo preamplifier and control unit designed for the Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout and great attention has been paid to achieving a really high signal-to-noise ratio and excellent tracking between the two channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs. The tone controls are also very carefully designed and tested.
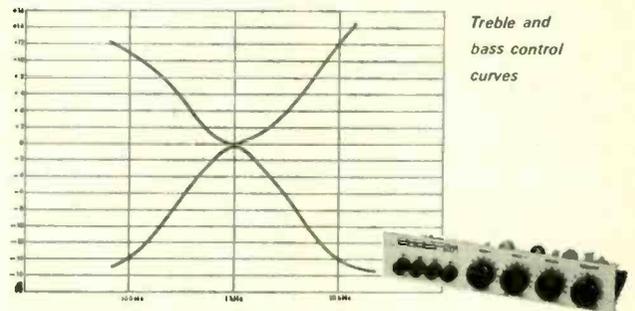
## SPECIFICATIONS

- Input sensitivities—Radio—up to 3mV; Magnetic Pickup—3mV Correct within  $\pm$  1dB on R.I.A.A. curve. Ceramic Pickup—up to 3mV; Auxillary—up to 3mV.
- Output—1 volt.
- Signal-to-noise ratio—better than 70dB.
- Channel matching—within 1dB.
- Tone Controls—TREBLE +15 to -15dB at 10 KHz; BASS +15 to -15dB at 100 Hz.

- Power consumption 5mA.
- Power requirement—PZ.5 or PZ.6.
- Finish—brushed aluminium front panel with black knobs.
- Mounting—on cabinet front by spindle bushes and adjustable brackets.




Treble and bass control curves



STEREO SIXTY

Ready built, tested and guaranteed £9.19s. 6d.

# SINCLAIR POWER SUPPLY UNITS

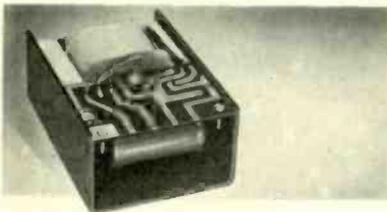

**PZ-5** 30 volts unstabilised—sufficient to drive two Z-30's and a Stereo 60 for the majority of domestic applications.

Price: £4. 19s. 6d.

**PZ-6** 35 volts stabilised—ideal for driving two Z-30's and a Stereo 60 when very low efficiency speakers are employed.

Price: £7. 19s. 6d.

## GUARANTEE

If at any time within 3 months of purchasing Project 60 modules from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter.

**SINCLAIR RADIONICS LIMITED**  
22 NEWMARKET ROAD, CAMBRIDGE  
Telephone 0223 52731

**sinclair**

To: SINCLAIR RADIONICS LTD., 22 NEWMARKET RD., CAMBRIDGE

Please send

NAME

ADDRESS

for which I enclose cash/cheque money order

WW7013

WW—074 FOR FURTHER DETAILS

# 'WATTS' THE NAME FOR RECORD MAINTENANCE



## HI-FI PARASTAT (Reg'd.) Pat. App. 58216/67.



### Gramophone Record Maintenance and Stylus Cleaning Kit

Designed for use on NEW records or records in new condition which are to be played with pick-ups requiring very low tracking pressures. The 30,000 finely pointed tips of the Hi-Fi Parastat Brush positively explore every detail in the record groove to provide the high degree of record cleanliness necessary when

### STYLUS CLEANER

Available separately complete with instructions.



Price 5/- Plus 1/3 P.T.

using ultra lightweight pick-ups tracking at 2 grammes or less. The cover pad in the lid of the case is provided for the purpose of cleaning and activating the brush which when enclosed within the case is kept at the correct level of humidity required to control all static at the working surface. Perfectly clean records must be played with a perfectly clean stylus and an integral part of the kit is the new Watts Stylus Cleaner which provides a safe and efficient method of cleaning the stylus. Supplied complete with instructions, 1 oz. New Formula dispenser, Distilled Water dispenser, spare pad cover and ribbons. Price 42/6 plus 1/3 P.T. Replacements: 1 oz. New Formula dispenser 4/6 Distilled Water Dispenser 4/- Pad Cover and Ribbons 1/9.

### 'PARASTAT' Reg'd. Manual Model Mk.IIA



A dual purpose record maintenance device. Keeps new records in perfect condition. Restores fidelity to older discs. Complete with 1 oz. New Formula dispenser and instructions. Price 45/- Replacements: Pad Covers 2/- each. Brush 12/6. Sponge Cover Pad 1/-, 1 oz. New Formula Dispenser 4/6. **HUMID MOP.** Recommended for use in conjunction with the Manual Parastat and Preener. Cleans and conditions the bristles and velvet pads. Ensures correct degree of humidity at the time of use. Complete with spare sponges and instructions. Price 4/6. Replacements: Set of Sponges 2/6.

### The original DUST BUG Reg'd. (Patent No. 817598)



Automatic Record Cleaner. Easily fitted to any transcription type turntable. Provides a simple and effective method of removing static and dust while the record is being played. Surface noise and record and stylus wear is reduced. resulting in cleaner reproduction. Complete with 1/2 oz. New Formula Dispenser and instructions. Price 18/9 plus 4/5 P.T. Replacements: Nylon Bristle and Plush Pad 1/9. 1/2 oz. New Formula Dispenser 2/6.

### A GUIDE TO THE BETTER CARE OF L.P. AND STEREO RECORDS

Completely revised. 48 pages, fully illustrated, providing all necessary information on Record Care. 2/6 Post Free.

### 'PARASTATIK' Reg'd. DISC PREENER (Patent No. 982599)



Keeps new records like new. Expressly designed for use with records which have not had previous antistatic treatment. Complete with instructions. Price 6/9. Replacements: Packet of 4 wicks 2/-.

All obtainable from your local specialist or direct:

To CECIL E. WATTS LTD. DARBY HSE, SUNBURY ON THAMES, MIDDX.

Please send (Post Free U.K. and Commonwealth)

..... Disc Preeners @ 6/9 ..... Hi-Fi Parastats @ 42/6 plus 1/3 P.T.  
 ..... Dust Bugs @ 18/9 plus 4/5 P.T. .... Manual Parastats @ 45/-  
 ..... 48 page Booklets @ 2/6 ..... Stylus Cleaners @ 5/- plus 1/3 P.T.

Replacement Parts:  
 I enclose cheque/P.O. value £ ..... (Do not send postage stamps)

Name .....  
 Address .....

## TRANSFORMERS

DESIGNED TO CUSTOMER'S OWN SPECIFICATIONS FOR ALL APPLICATIONS UP TO 100 KVA. "C" CORE, PULSE, 3 PHASE, TOROIDS, HIGH TEMPERATURE, ETC.

This month we are adding two new types of Transformers to our existing standard ranges.

**1. THE 1200 SERIES**  
 This series covers 150VA Transformers and gives a voltage range up to 110 volts at various loads.

**2. THE DB SERIES**  
 These Transformers have a high VA density (approximately 2.5VA per cu. inch) and cover a VA range up to 40VA.

Please write for further details.

Samples from our standard production ranges:

### \*Low Voltage

30-0-30V. 4A.	..	..	..	..	..	..	..	..	..	3 12 6
28V. 1A., 28V. 1A., 28V. 1A., 28V. 1A., 30V. 250mA.	..	..	..	..	..	..	..	..	..	4 15 0

\*Primaries 10-0-200-220-240V.

### 20W Transistor Amplifier (W.W. Nov. 1966)

Driver	..	..	..	..	..	..	..	..	..	1 4 6
Mains	..	..	..	..	..	..	..	..	..	1 19 6
L.P. Filter, Chassis Mounting	..	..	..	..	..	..	..	..	..	12 6
L.P. Filter, Printed Circuit Mounting	..	..	..	..	..	..	..	..	..	15 6

### 70V & 100V Line Matching

Fitted with terminal panel, taps at 0.5, 2, 4 and 8W. into 15 ohms 9/- each in 100 Lots  
 Flying leads, taps at 1/2, 1, 2 and 4W. into 3 ohms .. 7/3 each in 100 Lots

Prices inclusive of postage and packing, each.  
 For small quantities, cash with order, please.

## HOWELLS RADIO LIMITED

CARLTON ST., MANCHESTER, M14 4GT 061-226 3411

WW-075 FOR FURTHER DETAILS

# TRANSIPACK®

STATIC

400HZ SUPPLIES

## Inverters-Frequency Changers

FOR

- SERVOS
- SYNCHROS
- SIMULATORS



TYPICAL 500VA FREQUENCY CHANGER


FOR LEAFLET & IMMEDIATE QUOTATION CONTACT:-

**INDUSTRIAL INSTRUMENTS LIMITED**  
 STANLEY RD., BROMLEY, KENT  
 Tel: 01-460 9212  
 Grams: Transipack Bromley

Transipack Factory:  
 PONSWOOD INDUSTRIAL ESTATE  
 THEAKLEN DRIVE,  
 ST. LEONARDS ON SEA, SUSSEX  
 Tel: Hastings 7344

WW-076 FOR FURTHER DETAILS

# 'TRI-BOARD'

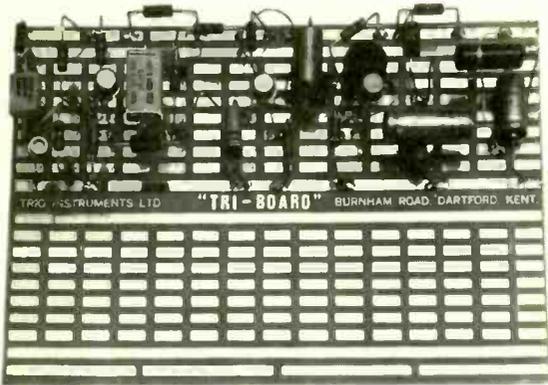

The ideal "Breadboard" material for rapid construction of electronic circuits at the design and prototype stages of development programmes.

TRI-BOARD is supplied in Fibreglass which is suitable for cold punching or cutting. Board size is  $7\frac{1}{2}'' \times 5\frac{3}{8}'' \times \frac{1}{16}''$  thick with 1 oz. copper A roller tinned finish is standard.

**PRICE** 15/- net per board.


Quantity discounts apply:

TRIO INSTRUMENTS LTD.,  
BURNHAM ROAD,  
DARTFORD, KENT.

Telephone: Farningham 2082

WW-077 FOR FURTHER DETAILS
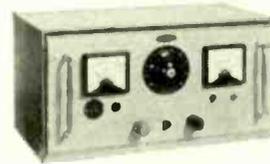
## SMOOTHED POWER UNITS WITH THE ACCUMULATOR PERFORMANCE.



Type 250VRU/30/20

Versatile power units providing all the usual voltages and currents normally required for development, servicing and production testing of practically all domestic and industrial equipment, up to a loading of 600W DC or AC.

### APPLICATIONS

- ★ Production testing and servicing of battery operated equipment.
- ★ Testing fuel pumps—DC motors—relays—windscreen wipers—car radios—and other types of battery equipment.
- ★ Multiple outputs.
- ★ Continuously variable DC voltage.
- ★ Continuously variable AC voltage.

### FEATURES

- ★ Output stabilised to accumulator performance.
- ★ Very low ripple.
- ★ Incorporating silicon rectifiers.
- ★ All models incorporating surge current limiting.
- ★ Low voltage outputs completely isolated from mains.
- ★ Quick delivery.


Type 250VRU/30/20. Output 1, 0-30V 20A DC. Output 2, 0-60V 10A AC. Output 3, 0-250V 4A AC. Price £131-5-0. Input 200/250V 40/60 Hz. Also available for 60V, 120V, 240V outputs.

### VALRADIO LTD.

Dept. WPU4, BROWELL'S LANE, FELTHAM, MIDDLESEX, ENGLAND

Telephone: 01-896 4242

WW-078 FOR FURTHER DETAILS

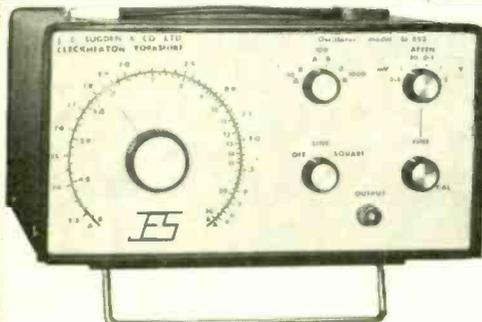

Si451 Millivoltmeter

- ★ 20 ranges also with variable control permitting easy reading of **relative** frequency response

£30.0.0

## JES AUDIO INSTRUMENTATION

Illustrated the Si453 Audio Oscillator

### SPECIAL FEATURES:

- ★ very low distortion content—less than .05%
- ★ an output conforming to RIAA recording characteristic
- ★ battery operation for no ripple or hum loop
- ★ square wave output of fast rise time

£35.0.0

also available

### Si452 Distortion Measuring Unit

- ★ low cost distortion measurement down to .01% with comprehensive facilities including L.F. cut switch, etc.

£25.0.0

J. E. SUGDEN & CO. LTD., BRADFORD ROAD, CLECKHEATON, YORKS.

Tel: Cleckheaton (DWR62) 2501

WW-079 FOR FURTHER DETAILS



MODEL A-303TRD

## SANWA MULTI TESTERS

USED THROUGHOUT THE WORLD. SANWA'S EXPERIENCE OF 30 YEARS ENSURES ACCURACY. RELIABILITY. VERSATILITY. UNSURPASSED TESTER PERFORMANCE COMES WITH EVERY SANWA

6 Months' Guarantee. Excellent Repair Service

Model P-1B	£3 7 6	Model K-30THD	£12 0 0
Model U-500	£5 10 0	Model 380-CD	£13 5 0
Model 380-YTR	£7 17 6	Model F-80TRD	£13 15 0
Model A-303TRD	£10 10 0	Model 430-ES	£19 0 0
Model AT-1	£11 7 6	Model EM-700	£51 0 0

Cases available for all meters

PLEASE WRITE FOR ILLUSTRATED LEAFLETS OF THESE SANWA METERS

SOLE IMPORTERS IN U.K.;  
**QUALITY ELECTRONICS LTD.**


47-49 HIGH STREET, KINGSTON-UPON-THAMES, SURREY. Tel: 01-546 4585

WW-080 FOR FURTHER DETAILS
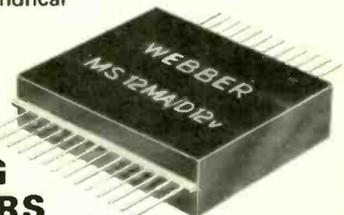
## ENCAPSULATION -

low tool cost method for cylindrical coils and potting. Enquiries also for—

**REED RELAYS  
SOLENOIDS  
COIL WINDING  
TRANSFORMERS  
to 8 K.V.A.**



Relay module 12-way "MS" range

**R. A. WEBBER LTD.**

Knapps Lane, Bristol 5. 0272 657228

WW-081 FOR FURTHER DETAILS



## OXLEY INDUCTORS

Illustrated above are a variety of high quality examples of our work in this field.

The inductor coils are uniquely designed and feature a silver conductor fired to a low expansion glass.

The coils:—

- ★ resist shock
- ★ resist temperature cycling
- ★ have a minimum temperature coefficient
- ★ have negligible frequency drift
- ★ have low self-capacitance

If a unique, perfectly designed, characteristically perfect inductance coil is what you require why not contact our Sales Department.

Enquiries to:

**OXLEY DEVELOPMENTS COMPANY LTD.**  
Priory Park, ULVERSTON, N. Lancs.  
Tel. ULVERSTON 2621 Telex. 6541




WW—082 FOR FURTHER DETAILS

# Sub-miniature DESIGN



Jack Socket R 32307


Threepenny Piece for Comparison of Size

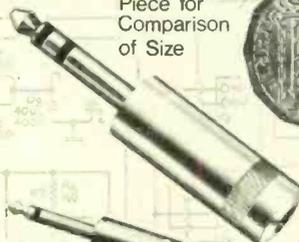

Screened Jack Plug R 22301



Jack Socket R 32400

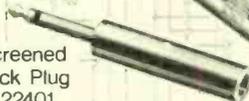

Screened Jack Plug R 22401

Presenting part of a wide range of components used throughout the world by the electronics engineer in search of quality and reliability.

Further information available.



## RENDAR

INSTRUMENTS LTD  
BURGESS HILL, SUSSEX, ENGLAND  
TELEPHONES: BURGESS HILL 2642-3  
CABLES: RENDAR, BURGESS HILL

WW—083 FOR FURTHER DETAILS



**W.H.M.**  
WOW AND  
FLUTTER  
METER  
(R.M.S)  
MODEL 111

**SYDNEY HOUSE, 35 VILLIERS ROAD, WATFORD**  
**WDI-4AL**

WW—084 FOR FURTHER DETAILS

## TRANSFORMERS

### COILS

LARGE OR SMALL QUANTITIES

### CHOKES

TRADE ENQUIRIES WELCOMED

SPECIALISTS IN

### FINE WIRE WINDINGS

MINIATURE TRANSFORMERS  
RELAY AND INSTRUMENT COILS, ETC.  
VACUUM IMPREGNATION TO APPROVED STANDARDS

### ELECTRO-WINDS LTD.

CONTRACTORS TO G.P.O., A.W.R.E., L.E.B., B.B.C., ETC.

123 PARCHMORE ROAD, THORNTON HEATH, SURREY  
01-653 2261 CR4.8LZ EST. 1933

WW—085 FOR FURTHER DETAILS

# better baluns...

Hatfield Baluns provide a simple and effective solution to the problem of matching unbalanced to balanced impedances of different values. Illustrated are two examples from the Hatfield range of RF Power Transformers, which includes 100W, 500W, 1kW and 3kW types, all available on short delivery. These units are weatherproof, capable of being pressurised where required and completely resistant to corrosion. A wide range of impedance ratings is also available.

The range is comprehensive and is backed by many years experience in the design and manufacture of RF Power Transformers and incorporates the newest developments for high efficiency and low insertion loss.

Ask for Folder B4/4 and for the latest edition of the Hatfield Short Form Catalogue.

## HATFIELD BALUN



Dept. WW, HATFIELD INSTRUMENTS LTD., Burrington Way, Plymouth, Devon  
Telephone: Plymouth 72773/5. Telex: 45592 Cables: Sigjen Plymouth  
SOUTH-EAST ASIA—for prompt service and deliveries contact  
HATFIELD INSTRUMENTS (NZ) LTD., P.O. Box 561, Napier, New Zealand.

WW—086 FOR FURTHER DETAILS

**IT TAKES  
A SHORT TIME  
TO TELL  
A LONG STORY**



**CALAN TRACE SHIFTER C501D**

- ★ A TRACE (9,600 MILLIMETRES LONG ON A 5 INCH TUBE!)
- ★ A THREE DIMENSIONAL DISPLAY!
- ★ VERTICAL COMPARISON OF SUCCESSIVE SCANS!

Add these facilities to your oscilloscope. They will help you to examine the functional waveforms of heart or combustion engine or for that matter any other long waveform phenomena.

Price £68 Export and Agency Enquiries Invited.

**Calan Electronics Limited,**

6 Croft Street, Dalkeith, Scotland  
Tel. 031-663-2344

WW-087 FOR FURTHER DETAILS

**SPECIALIST SWITCHES  
are again giving  
the fastest switch  
service in the world**

**FROM THEIR NEW AND LARGER  
PREMISES IN CHARD, SOMERSET**

Specialist Switches make **Rotary and Lever switches, types H, DH, HC, and LO, to specification.** There is one limitation (standard 2 in. long spindles), but this is not important when you are getting the **fastest switch service in the world.**

*Delivery of 1-20 switches: 24 hours.  
Up to 50 or so: 72 hours.  
If you want around 250 or so: 7-10 days.*


Please note our address:  
**SPECIALIST SWITCHES**  
P.O. Box 3,  
**CHARD, SOMERSET**

Write for design charts and prices or  
**TELEPHONE-CHARD 3439**

WW-088 FOR FURTHER DETAILS


**AHUJA  
P.A. SYSTEM**

**PRESENTS - 1969 - RANGE  
PROFESSIONAL QUALITY  
PUBLIC ADDRESS AT AMAZINGLY  
COMPETITIVE PRICES.**

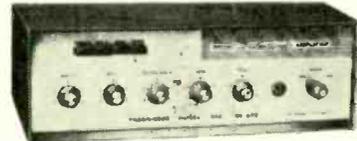

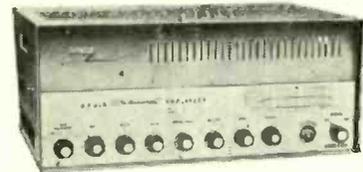
**Model 50 - ATR - 50 Watts**

8 Models in all Transistor A. C. Mains and Battery Operation, Power Output from 15 - Watts to 50 - Watts. Built to International Standards. Also Mixer & Pre - Amplifiers.




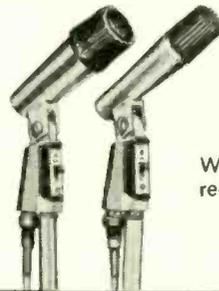**Model A - 100**

6 Models in AC-operated Tube Amplifiers. Power Outputs from 20 - Watts to 100 - Watts. High Fidelity Performance. Absolute reliability in extreme working conditions.



Wide Range of unidirectional Microphones

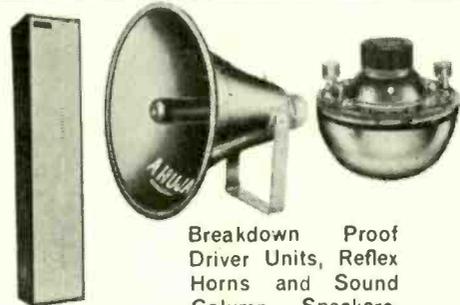

Breakdown Proof Driver Units, Reflex Horns and Sound Column Speakers.


AHUJA P. A. SYSTEM are manufactured in India's largest and most well equipped Plant. These are highly popular in over 25 countries on account of high quality and rugged construction and most competitive international prices.

**AHUJA RADIOS, 13 - DARYA GANJ  
DELHI-6. (INDIA)**

Issued by Engineering Export Promotion Council  
Calcutta (India)

WW-089 FOR FURTHER DETAILS

# FAULT LOCATION

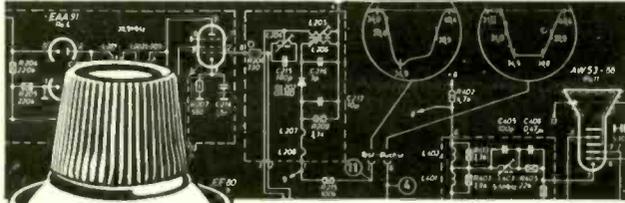

## KONTAKT "Cold Spray 75"

For rapid and effective fault location

Non-toxic, non-inflammable, Cold Spray 75 is a chemically inert coolant capable of producing temperatures of down to -42 centigrade. It can also be used to prevent heat damage during soldering processes, for the rapid freezing of small articles for biological and technical purposes and the prompt location of hairline cracks and other faults in temperature dependent components.

**Other Kontakt products:**

- Kontakt 60 and Kontakt 61 for relay contact cleaning.
- Plastic Spray 70, transparent protective lacquer.
- Insulating Spray 72.
- Kontakt WL. Spray Wash.
- Antistatic Spray 100. Antistatic agent for plastics.
- Politur 80. Polish and cleaner.
- Fluid 101. Dehydrating Fluid.

Details from UK distributors.

## SPECIAL PRODUCTS DISTRIBUTORS LTD.

81 Piccadilly, London, W.1

Tel: 01-629 9556

WW—090 FOR FURTHER DETAILS



6mm tubular midjet flange S6/8 cap over-all length 14.5 mm.

It is one of the many Vitality Instrument and Indicator Lamps that are made in an unusually large number of types, ratings and sizes. It may be just what you need for an existing or new project. If not, another from the hundreds of types and ratings detailed in the Vitality Catalogue may well be.

*\*Many a product owes its success to the intelligent addition of an indicator light.*

## VITALITY BULBS

VITALITY BULBS LTD MINIATURE AND SUB-MINIATURE LAMP SPECIALISTS  
BEETONS WAY, BURY ST. EDMUNDS, SUFFOLK. TEL. BURY 2071. S.T.D. 0284 2071  
A member of the General Instrument Group

WW—092 FOR FURTHER DETAILS

## PRECISION PRESSINGS

**Accurate components at competitive prices**

**produced by progressive tooling and multiform methods**

**JOHN SMITH LTD.**

209 SPON LANE · WEST BROMWICH · STAFFS. TEL. 021-553 2516 (3 LINES)  
WOODS LANE · CRADLEY HEATH · WARLEY · WORCS. TEL. CR 69283 (3 LINES)

WW—091 FOR FURTHER DETAILS

**Ballistics Computers by Westinghouse. Nine servo amplifiers with associated motors. Brand new in sealed containers. £95, delivered.**

**Automatic Numbering Machine by Western Union. Four Uniselectors and 30 neons. Ideal amateur computer. Application leaflet. £12.10s. post free.**

**PUNCHES, READERS, VERIFIERS AND TELEPRINTERS AT REALISTIC PRICES TO EDUCATIONISTS. MOBILE SHOWROOM CALLS ON REQUEST.**

## COMPUTER TRAINING PRODUCTS

2 Lordship Lane, LETCHWORTH, HERTS. Tel: 4536 0462/6

WW—093 FOR FURTHER DETAILS

**CONVERTOR/BATTERY CHARGER.** Input 240v 50 c/s, output 12v 5 amp DC. Input 12v DC, output 240v AC. 170 watt max. With fuse and indicator lamps. Size 9 1/2 x 10 x 4 1/2 in. Weight 19lb. An extremely compact unit that will give many years' reliable service. Supplied with plug and lead. Only £4/10/-. P. & P. 15/- extra.

As above—fully serviceable—perfect interior but soiled exterior cases. £3. P. & P. 15/-.

**G.P. TUBES.** Brand new. G24/G38/G60 at 27/6 ea. G53/1, brass cased. £6 ea.

**PHOTOMULTIPLIERS.** EMI 6097X at £8/10/- ea.

**TRANSISTOR OSCILLATOR.** Variable frequency 40 c/s to 5 kc/s. 5 volt square wave o/p. for 6 to 12v DC input. Size 1 1/2 x 1 1/2 x 1 1/2 in. Not encapsulated. Brand new. Boxed. 11/6 ea.

**TIMER UNIT.** Standard primary transformer giving 18V 4 amp., G.E.C. bridge rectifier in bench or wall mounting case 10 x 10 x 5 in. Complete with internal one second timer sub-chassis. Checked and tested £2/15/0. P. & P. 15/-.

**COUNTENAY TIMER** sub-chassis with 2-12AU7, transistor, relay etc. Requiring 12V. A.C. or D.C. to operate 22/6.

**50 Watt AUDIO AMPLIFIERS** by GEC—4KT 60's 4/8/25 or high impedance inputs 15 ohm out. Standard mains in; metered output etc. No electrolytics. Absolute reliability £20 only. Carr. 30/-.

**AMPLIFIERS.** Compact unit by Parmeko—rated 17 watts, capable of double. 2-KT66/2B254M; ECC81; 2-EF86; 5U4, matching to 15 ohms. High impedance or transformer input. Size 1 1/2 x 8 1/2 x 8 1/2 in. high. Standard mains input. Fully tested £8/10/-. Including carriage.

#### RELAYS

Omron/Schrack octal based plug-in relays. 2 pole c/o 5A, 6v only. Brand new. Boxed. 12/6 ea.

G.E.C. 4 pole c/o 6/12v operation 180 ohms. Platinum contacts. Brand new. Boxed 12/6 ea.

Min. VARLEY type VP4. 4 pole c/o 430 ohm or 15 K/ohm. Brand new 6/6 ea.

Min. SIEMENS. 4 pole c/o. 24V operation. Brand new 8/- ea.

S.T.C. sealed 2 pole c/o 48V. 2.500 ohm 48v. 3/6 ea. 12v 7/- ea.

**CARPENTERS** polarised Single pole c/o 20 and 65 ohm coil as new, complete with base 7/6 ea. Single pole c/o 680, 1.110 and 1.570 ohm coil. As new 6/6 ea.

#### POTENTIOMETERS

**COLVERN** Brand new. 5; 10; 50; 100; 250; 500 ohms; 1; 2.5; 5; 10; 25; 50K at 2/6 ea. Special Brand new **MORGANITE** 250K 1 in. sealed. Normal price 9/-, our price 3/6 ea.

**INSTRUMENT** 3" Colvern. 5; 25; 50; 100 ohms; 2.5; 25K. All at 7/- ea.

**TRIM POTS.** Palantion-solder lugs 5, 10 & 25K at 7/6 ea.; Plus: 10; 20; 50; 100; 200; 250; 500 ohms; 2.5; 25 and 50K at 15/- ea.

**DARSTAN**—preset-sealed 1/2" dia. 1 high. 1; 2 and 5K 2/- HIGH RESOLUTION 25K 80 turns. Complete with knob 6/6

**COLVERN** 50K Ten turn complete with dial £1 P. & P. 2/8 ea.

**GENERAL CONTROLS.** 100K Ten turn. Brand new. Boxed 25/- ea.

**ALMA** precision resistors 100K; 400K; and 998K—0.1% 5/6 ea.; 3.25K—0.1% 4/- ea.

**DALE** heat sink resistors, non-inductive 50 watt. Brand new. 15 ohms—6/6 ea.; 8.2K—5/-. Excellent dummy load

#### CAPACITORS

**ERIE** feed through ceramics 100 pf—9d. ea. Sub-min. **TRIMMER** 1 square. 8, 5pf. Brand new 2/6 ea. Concentric **TRIMMER** 3/30 pf. Brand new 1/6 ea.

**DUBILIER** Electrolytic. 32mfd 350v D.C. Brand new 1/9 ea.

**EHT** 1000pf 20KV working. Ideal transmitter blocking capacitors 6/6 ea.

**VISCONC** EHT. Brand new 0.002 15kV 8/6 ea.; 0.0005 25 kV. 16/- ea.

**E.H.T.** 7.5kV working 0.25 mfd 8/6 ea.; Brand new 5 kV 0.25mfd 10/6 ea.; 10kV 0.05mfd 7/6 ea.

**GEARED MOTORS** 240v 50 c/s synchronous. Geared down to 60 rpm. Brand new 37/6 ea. P. & P. 7/6.

**DIODES** 1N914. Brand new 1/3 ea.; 12/- doz.; £4—100; £25—1,000.

**PHOTOCELL** equivalent OCP 71 2/6 ea.

**BURGESS** Micro Switches V3 5930. Brand new 2/6 ea.

**BULGIN** panel mounting Lamp holders. Red. Brand new 2/3 ea.

**PLUGS & SOCKETS.** New & ex. eq. Plessey; Paignton Cannon; Electromethods; Belling & Lee; Bulgin etc. Write for lists.

**MINIATURE SPEAKERS** 15 ohm 100 MW 2in. diameter. Brand new 10/6 ea.

**TRANSISTORS** BC 114; BC 116. Ex brand new equipment. Guaranteed perfect. Good lead length 2/- ea. Also RT Micrologic L 9914 I.C. 8 lead TO-5 can. Fan out 16 dual 2 input nand nor gate, capable of F/F action at 20 mc/s or non inverting gate or gate + invert. Good length leads. Guaranteed perfect 7/6 ea.

## TEST GEAR

#### OSCILLOSCOPES

**E.M.I.** WM 8 DC—15 mc/s £65  
**E.M.I.** WM 2 DC—18 mc/s £35  
**E.M.I.** 3794 DC—5 mc/s £15  
**SOLARTRON** QD 910. Storage scope £170—£315  
**SOLARTRON** 7118.2 D.B. DC—9 mc/s £60  
**SOLARTRON** 643 DC—15 mc/s £80  
**SOLARTRON** 513/523 DC—10 mc/s £35  
**SOLARTRON** 568 DC—6 mc/s £18  
**COSSOR** 1035 D.B. £20  
**COSSOR** 1049; 1049 Mk. 3. D.B. £22/10 and £30  
**HARTLEY** 13A DB. £18/10/-  
 All carefully checked and tested. Carriage 30/- extra.

#### MARCONI

TF 956 Audio Frequency Wattmeter £15 Carr. 10/-  
 TF 886 Magnification Meter £45 Carr. £1  
 TF 762C UHF Generator £40 Carr. £1  
 TF 995 AM/FM Generator 1.5—200 mc/s £120 Carr. £1  
 TF 369 N. 5 Impedance Bridge £75 Carr. 30/-  
 TF 144G Signal Generator. Serviceable. Clean £18 In Exceptional condition £30 Carr. 30/-  
 TF 885 Video Oscillator Sine/Square £40 Carr. 30/-  
 TF 899 Millivolt meter £8 Carr. 10/-  
 TF 195M Sine wave oscillator 0/40kc/s £14 Carr. £1  
 TF 517 VHF Generator 10 mc/s—300 mc/s £6 Carr. £1  
 TF 428B/1 Valve voltmeter £4 Carr. 10/-  
 TF 428B/2 Valve voltmeter £10 Carr. 10/-  
 TF 388B Attenuator £5 Carr. 10/-  
 TF 791B Carrier Deviation Meter £45 Carr. 30/-

#### SOLARTRON

Pulse generator POS 100C 50 c/s—1 mc/s £25 Carr. £1  
 Laboratory amplifier AWS51A. 15c/s—350kc/s £35 Carr. £1  
 Stabilised P.U. SRS 151A £20 Carr. 30/-  
 Stabilised P.U. SRS 152 £15 Carr. 30/-  
 Stabilised P.U. AS 516 & AS 517 £3, and £6 Carr. 10/-

#### AVO

Generator type TFN AM/FM 5—220mc/s £45 Carr. 15/-  
 Generator CT 368 2—225 mc/s £50 Carr. 15/-  
 Generator 50kc/s—80 mc/s £16 Carr. 15/-  
 Testmeter No. 1 £14 Carr. 15/-  
 Electronic Testmeter CT 38. Complete £18 Carr. £1

**SPECIAL.** Multimeter CT471A. Battery operated, fully transistorised, sensitivity 100 M ohm/V. measures a.c./d.c. voltage (12mV-1200V scales, +/- 3% / +/- 2% f.s.d.) a.c./d.c. current (12 microA-1.2A scales, +/- 3% / +/- 2% f.s.d.) resistance (12 ohm-120M ohm scales, +/- 3% m.s.d.), h.f./v.hf/uhf. voltage with multiplier (4V-400V scales up to 50 MHz; 40 mV-4V up to 1000 MHz). Brand new £75 Carr. 30/-  
 CT 471B, as above by G. & E. Bradley £75 Carr. 30/-

#### CINTEL

Transistorised Nucleonic Scalers with adjustable discriminator. 6 meters display 0-9 giving count of 10 to the 5. In a new condition £30 Carr. 15/-  
 Wide Range Capacitor Bridge £25 Carr. 15/-  
 Sine and Pulse Generator type 1873 £25 Carr. 15/-

#### AIRMEC

Valve Millivoltmeter type 264. 3MV-1V £20 Carr. £1  
 Counter type 865. 6 decades. Bright vertical display gate facilities. Very good condition £30 Carr. 30/-  
 Klystron Power Supply 698B £25 Carr. £1

**SIGNAL GENERATOR/WAVEMETER** type 61. 90 to 160 mc/s. Built in crystal markers. Standard mains input. Excellent condition £12/10/-. Carr. 30/-.

**SIGNAL GENERATOR** type CT 478 by W. H. Sanders. Feet. range 1-3 kmc/s to 4-2 kmc/s. Output power calibrated dbb. New £40. Carr. £2/10/-.

**AM/FM OSCILLATOR** Type 1 CT 212. 85 kc/s to 32 mc/s. As new £35. Carr. £1

**HEINZ GUNTHER** AM/FM Generator 9—200 mc/s. £30 Carr. £1

**SIGNAL Generator** CT 53. Complete with leads. Good condition. £10 Carr. 15/-

**FREQUENCY Meter** BC 221. £17/10/0. with built-in stab. P.U. £22/10/0 Carr. 15/- With Charts.

**DIGITAL VOLTMEETER** type BIE 2114. 1 mV to 1kV DC. Auto decimal change. Excellent condition £65

**MIC-O-VAC** type 22 (CT54) Volts; Current; Ohms, D C to 300 mc/s with probe, leads etc. As new £8/10/0 P. & P. 10/- Plug-in MAINS PACK for Mic-ovac type CT 54. £2/10/0 P. & P. 6/-

**VIBRATING REED ELECTROMETER** type N 572 by ECKO. Range 10 to the -14. Max sensitivity FSD for 1 of 0.03 Micro-microamps. £25 ea. Carr. £1

**RACAL FREQUENCY COUNTERS**  
 SA 20 4 decades 100 kc/s £20 ea.  
 SA 21 6 decades 10 mc/s £45 ea.

SA 28 as SA 21 with converter extending range to 30 mc/s £65 ea.

**GRAUMONT-KALEE** Flutter meter type 564 £35

**GENERAL RADIO** Precision Capacitor type 722. 50 pf to 200 pf. £75 Model 222F at £55

Miniature **SCOPE** type 1200B. Ideal TV servicing etc. Checked and tested £10 P. & P. £1

**ADVANCE** Sinal Generator type D1. 2 mc/s to 190 mc/s. Sine and square mod. With original charts. Excellent condition £12/10/0 P. & P. £1

**SERVOMEX.** Stabilized D.C. Power supplies type DC3. 0-30 Volts, 0-7 amps. Separate voltage and current meters. £35. Type 38, bench mounting, 0-15 Volts, 0-2.5 amps. Separate voltage and current meters £25

**TRANSISTOR** Stabilised Power Unit. 48v, 4 amp. Manufactured by E.M.I. Open chassis. Brand new. Highest quality. Size 10 1/2 x 5 1/2 x 6 1/2 in. £6 ea.

**RACAL** stabilizer unit 24V. raw DC in 20 volts lamp stab and 12V. 5 MA Zener stab out. Brand new condition. Size 5 x 3 x 6 in. Complete with circuit diagram. 35/- ea.

**MAINS FREQUENCY METERS** with large 270 deg. Dial calibrated 45 to 65 cycles 4in. diameter. In original service carton. £3/10/-. P. & P. 7/6.

19in. Rack Mounting **CABINETS** 6ft. high 2ft. deep. Side and rear doors. Fully lapped, complete with base and wheels. £12/10/0 Carriage at cost.

**V.H.F. RECEIVER TYPE 715** by BCC. Complete, tested and working (Less crystal). 12v DC input. Ideal conversion 2 and 4 metres. In good condition. Supplied with conversion data. Only £3/10/0 P. & P. 7/6 ea.

**MULLARD** Transistorised Analogue to Digital Converter Model I. 281. As new. £20 Carr. 15/-

**SUNVIC** DC chopper Amplifier type DCA 1. Superb condition. £22/10/0 ea. Carr. 20/-

**SEQUENTIAL TIMERS** 8 individual timer circuits each with 0-100 sec calibrated dials. Ideal displays, processes, etc. Standard mains input £25 Carr. 25/-

**Ex-SOUTHERN ITV CAMERA** with image orthicon tube and single lens. Mounted on tripod. Sold as seen. £40

**ISOLATING TRANSFORMERS** 240V in 240V 7 KVA out. As new. £25 ea. Carr. £2/10/0

**DESK** Telephones. Current type. 3 wire red, green, white. Ideal extensions etc. As new £3 ea.

**MODERN** Transistorised 10 line automatic desk top exchange. Complete with 10 A.E.I. Telephones, standard G.P.O. type dialling to call any other line. Exchange size 16 x 5 x 6 housed in attractive mahogany case. Complete set. £55

#### METERS

**ELLIOTT** Portable Reflecting Voltmeter. 6" dial scaled 0 to 12.5 Volts 12.5—25—37.5 Frequency range DC to 2.5 kc/s. Accuracy 0.5 fad. Adjustable feet, built in level, magnetic shield, movement lock. In fine quality wood case. £20 P. & P. 15/-

**EHT ELECTROSTATIC** Ernest Turner etc. 0-750V £2 ea.; 0-3.5 KV £2/15/0 ea.; 0-5 KV £3/10/0 ea.; 0-7.5 KV £4/5/0 ea.

**TAYLOR** 100-0-100 Micro amp scaled size 4 x 2" with internal lamp scaled 6-0-6 1/10/0 ea.

**GRIFFIN & GEORGE** 3" round in sloped open ended case with terminals 3 types 0/20; 0/100 and 0/250. All 50 c/s. £1 ea.

#### TRANSFORMERS.

All standard inputs.  
 18v 6 amp and 12v 1 amp. Sep. windings, 18/6 ea.  
 18v 12 amps at £3 ea.  
 3kv 4-5mA. 4v 0.5 amp x 2, 4v 1.1 amp. £3/10/- ea.  
 350-0-350 75mA. 5v 2 amps x 2, 21/- ea.

Gardners 6-3v 2A; 6-3v 1.5A; 6-3v 0.1A. Size 3 x 1 1/2 x 4 1/2 in. As new. 14/- ea.

Gardners. Potter. Multi 6-3's combine to give 48v at 4 amps or 6-3 at 45A. With 350-0-350 at 50mA. £2/10/- ea.

Parmeko/Gardners. Potted. 475-60-0-60-475 at 160 mA; separate winding 215-0215 at 45mA; 6-3v 5A; 6-3v 0.75A; 5v 3A. As new. £3 ea.

Gardners 400-350-0-350-400 at 250MA; 0/4/6-3v 4 amp x 2; 0/4/6-3 2 amp; 0/4/5 3-5A. In original boxes. £4/10/- incl. post. Gardners 2kv 10MA. As new. £3 incl. post. Gardners 2kv 10MA and 4 volts x 2. £4/10/- ea incl. postage.

Parmeko 6-3v at 2 amp x 4. 22/6 ea.  
 Parmeko 65v 1 amp. Separate 0-18-24v at 0.5 amp. 30/- ea.  
 Gard/Parma/Part. 450-400-0-400-450. 180 MA. 2 x 6.3v. £3 ea.

**E.H.T.** Brand new 5kV 5MA with rectifier heater winding. Size 3 x 3 x 3 1/2 in. 27/6 ea.

**ADVANCE** Constant Voltage Trans. 6 volts 50 watt. As new £3 P. & P. 10/-  
 Gardners 4v 30 amp. Brand new £1/10/0 incl. postage. 3 for £3/10/0 incl. postage.  
 Gardners 5v 30amp. Brand new £2 ea. incl. postage.

**CHOKES.** 5H; 10H; 15H; up to 120MA. 8/6 ea. Up to 250MA 12/6 ea.  
 Large quantity LT. HT. EHT transformers. Your requirements, please.

Panel switches DPDT ex eq. 2/6 ea.; DPST Brand new 3/6 ea.; DPDT twice, brand new 6/-; heavy duty DPST brand new 6/- ea.

**PRECISION** continually rotatable stud switches. Single pole. 80 way, can be stacked if required. £3 ea.

**PRECISION** rotary stud switches 2 pole 12W size 2" sq., 1" shaft. £2/10/0 ea.  
 Min. SEALED 4 pole 3 way and 3 pole 4 way rotary switches. 1" shaft 1" dia. x 1" 10/- ea.

## CASH WITH ORDER

**FOR CALLERS.** Always a large quantity of components, transformers, chokes, valves, capacitors, odd units, etc., at 'Chiltmead' prices. Callers welcome 9 a.m. to 10 p.m. any day.


# CHILTM EAD LTD.

22 SUN STREET · READING · BERKS

Off Cumberland Road (Cemetery Junction)

Tel. No. Reading 65916 (9 a.m. to 10 p.m.)

# ELECTRONIC BROKERS

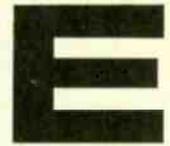


## MEASURING INSTRUMENTS AND RECORDERS

### NEW

6 Pen Event Recorder, 6 in. Chart width. Available in wide range of chart speeds. Rack mounted £79/10/0. Case to suit extra.
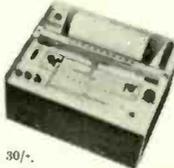
### NEW AMERICAN 5" CHART RECORDER

Good general purpose potentiometric recorder. Suitable for research and laboratory work. Range 0-10 m.v. Variable zero set, Zenor divide reference. Input impedance. Max 100 Kohms. Price £69.10.0, P. & P. 30/-.



### PORTABLE AC/DC PEN RECORDER

A most versatile pen recorder. Produces a trace on a curvilinear 3 1/2 in. strip chart. Two speeds 1 in. and 6 in./hr. Limiting contacts to give alarm, and limits the current when it exceeds the high and/or low preset values. Range: 0 - 1MA D.C. Meter Resistance 400 ohms; 0 - 1MA A.C. Meter Resistance 1800 at 50 Hz; -10 to +5 dB into 600 ohm Impedance Source. Chart speed; 1 in. and 6 in./hr. Chart width: 3 1/2 in. curvilinear. Power supply: 230V 50 Hz driving Synchronous Motor. Price: £52.10.0. Postage and packing £1 5s. 0d.




### STRIP-CHART INDICATING RECORDER

Chart width 9 1/2 in. 10 m.v. Sensitivity ± 0.17 of full scale. Source Impedance 100 ohms. Speed of operation 33 sec. for full-scale travel. Chart speed 1/2 in., 3 in., 6 in. per hour. Single point. £49.10.0. P. & P. 30/-.



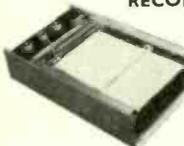
### RECORDER SP 20 Series

General Purpose Single Pen potentiometric instrument for continuous recording for any input signal from 0-10mV D.C. Suitable for use with Spectrophotometer and other laboratory instruments. Chart speed 0.5 to 8.4 cm/min. Linearity ± 0.25%. Fully transistorised. Chart width 200 mm. Input Impedance 10K ohms max. Available 8.P. 20 Plain Linear. 8.P. 21 Flat Bed. 8.P. 22 Linear/Log. From £135 each. P. & P. 40/-.



### PEN RECORDER

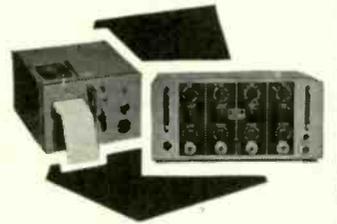

Portable 1, 2 and 4 channel pen recorders by Kelvin Hughes. General purpose recorders providing clear instantaneous and permanent records of phenomena with comparatively high rates of change. The torsion-strip suspension of the moving-coil renders the instrument immune to the effects of vibration and acceleration. Six possible chart speeds, chart width 55 mm. length 150 ft., linearity 8 v. at 3 m.A. response D.C. to 100 c/s. Single pen with amplifier £29; 2 pen recorder £25; 4 pen with amplifier £149. Also 5 pen recorder complete with amplifiers, specification as above but housed in cabinet £225. P. & P. extra.


**ULTRA VIOLET RECORDER** 12 Channel NEP 1050 with 6 galvanometers £280.  
**ULTRA VIOLET PHOTOGRAPHIC RECORDER** 12 Channel mirror Galvanometer Honeywell 1000 with 6 galvos £280.  
 24 Channel Slemic Recorder by Film & Equipments £325. Carriage extra.

**E H T INSULATION TESTER**  
 From 1 - 5 Kv A.C. and D.C. Complete with probes. New equipment. Price £52/10/0. Carr. £2/10/0.
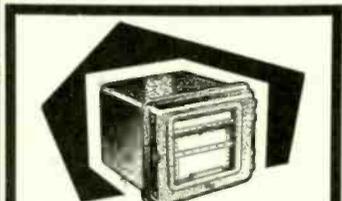
## NEW PORTABLE RECORDING AMMETER



Specification: Type: Moving Coil, D.C. Range: 0-5 amp. D.C. Chart Width: 100 mm. Scale Length: 127 mm. Chart Speeds: 20, 60, 180, 600, 1800 and 5400 mm/hr. Dimensions: 190h x 163 w x 245mm. Weight: 5.5kg. List price £65. Our price £35.



### POTENTIOMETRIC 6 POINT STRIP CHART RECORDER BRAND NEW


For use with thermocouples, pyrometers and other e.m.f. sources. 6 point. Range (-100) - 0 - (+100) mV; 0 - 1,600 deg. C. 6 1/2 in. chart width; pen speed 8 secs. Accuracy ± 0.5%; 10 chart speeds 20-720mm/hr. Tropicalised. Including tools and spares. Listed at over £200. Our price £79.10.0. Also available 0-100mW P.S.D. £89.10.0.

## POWER SUPPLIES

### AIRMEC 698B KLYSTRON POWER SUPPLY

Rack mounted (19 in.). Mains operated. Cathode volts from 1.0 to 2.4 kv. negative. Grid Volts, 0 to 220V negative. Reflector Volts, 0 - 600V negative. Cathode Current, 0.18mA max. Heater 4V at 1.5A. Internal Modulation—Square wave 2 - 4 KHz 7V p-p. Raw Tooth 160 - 600 Hg 0 - 30V peak. Price £45. P. & P. 40/-.
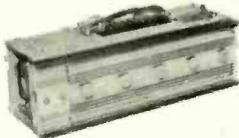
### HIGH PRECISION FULLY STABILISED TRANSISTORISED LOW VOLTAGE POWER SUPPLIES



Incorporating  
 • S.C.R. Panel for overload protection.  
 • OVERLOAD & CIRCUIT BREAKER WITH MANUAL RESET button.  
 • RIPPLE better, better than 3000 : 1.  
 • CHOKE OF CAPACITOR transistorised 120/130 volt A.C. INPUT.  
 Available in the following types:

6 Volt 9 Amp	£12.10.0
6 Volt 12 Amp	£17.10.0
6 Volt 18 Amp	£22.10.0
12 Volt 8 Amp	£22.10.0
12 Volt 16 Amp	£25. 0.0
12 Volt 22 Amp	£25. 0.0
20 Volt 16 Amp	£25. 0.0
24 Volt 4 Amp	£22.10.0
30 Volt 8 Amp	£18.10.0
66 Volt 7 Amp	£25. 0.0

Ex-equipment but fully tested in our laboratory. Carr. 30/-

### ADVANCE TRANSISTORISED DC POWER UNITS

Input Volts	Output Volts	Amps	Price	
DO 4	200-245 ± 15%	12	4	£17/10/-

## METERS

2 in. dia. mounting A.C. voltmeter 0-300 V. A.C. £115.0.  
 Carriage 6/-.  
 3 1/2 in. dia. Electrostatic Kilo Voltmeter in wooden case. £215.0. Carriage 10/-.

Precision A.C. & D.C. Wattmeter. Model 8.67 certified. Accuracy to 1% up to 133 c/s. Range 250/450 V. and 0.5 to 1 A. £29.10.0. Carriage 30/-.

**INDICATING MEASURING AMPLIFIER PR 7410**  
 Suitable for vibration and frequency analysis. Frequency response 10-1,000 Hz. £45. Carr. 40/-.

**BRAND NEW S.E. LABORATORIES TRANSDUCER** complete with encapsulated Amplifier/demodulator S.E. 441/2 Frequency D.C.—60 c.p.s.  
 Available in the following ranges:  
 SE160, SE50 or SE165A. u - 3000 p.s.i.  
 0 - 50 p.s.i. 0 - 500 p.s.i. 0 - 2000 p.s.i.  
 0 - 200 p.s.i. 0 - 750 p.s.i. 0 - 4000 p.s.i.  
 0 - 350 p.s.i. 0 - 2000 p.s.i.  
 Also available differential types ± 10 p.s.i.  
 Also available differential types, + 10 p.s.i.  
 List price £70+-. Our price £15

## COMPUTER AND PERIPHERAL EQUIPMENT




### 7 TRACK DIGITAL MAGNETIC TAPE STORAGE DECK

These machines originally ex-computer, are multi-track recording units. Ideal for data storage. Record and Replay heads encased in one common unit. Low resistance heads. Frequency response approximately 30 Kc/s. to 50 Kc/s. Bit density 557 b.p.i. 1/2 in. 10 1/2 in. spools 230 V. to 380 V. A.C. Capstan Motor speed 1,500 r.p.m. 48 V. D.C. Rewind motor complete with vacuum Assembly. Finished in brush aluminium and matt-black. Size 27 in. x 26 in. x 8 in. Weight 90 lb. Price £72.10.0. Carriage extra.
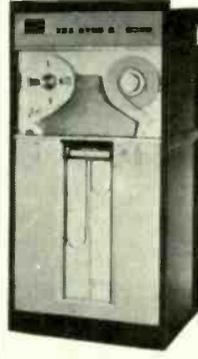
### MODEL 72 MAGNETIC TAPE DATA STORAGE UNIT

This unit consists of 1/2 in. 8 channel read-write heads, can be used to record any 6 bit code. Data can be read in either a forward or backward direction plus giving search facilities. The unit consists circuits for receiving and storing instruction signals. Recording density 250 characters per inch. Tape speed 100 in. per second, price £180. Excellent condition.



**7 TRACK**  
 Ex-computer record/replay head complete with guides. Little used. Price £12.10.0 Carriage 15/-.

### BRAND NEW

Gresham Lion 1 in. 1 + 7 track record/replay heads. Of the highest professional quality. Cost £100 plus price £12.10.0. Carr. 15/-.

### BRAND NEW COMPUTER TAPES AND EMPTY SPOOLS

Made by well known manufacturers	
1/2 in. certified 2,400 ft. 800 b.p.i.	£8.10.0
1/2 in. 2,400 ft.	£8.10.0
1/2 in. Highest grade 2,400 ft.	£3. 0.0
1/2 in. 10 1/2 in. dia. spool and cassette.	£1.10.0
1/2 in. 8 1/2 in. dia. spool and cassette.	£1.10.0
1 in. metal 10 1/2 in. dia. spool and cassette.	£2.10.0
1 in. N.A.B. centres 10 1/2 in. spool only.	£1. 0.0

### TAPE PUNCH MODEL 25 7 HOLE

A multiwire tape punch designed for general application involving the conversion of parallel wire electrical impulses into punched paper tape at 33 characters per second. Unit completely self-contained requiring only motor power and signal supplies. Price £45.

### 7 HOLE NON PARITY TAPE PUNCH

New condition £45.

### LOW SPEED 7 HOLE TAPE PUNCH

80 characters per second by well-known manufacturer. Price £45.

### TELETYPE 8 HOLE PAPER PUNCH MU27 PRICE £75.

Also available 5 hole punch BRPE2 as above. This model has interchangeable heads. Complete with spooler. Price £35.

### HIGH SPEED 5/7 HOLE OPTICAL READER

20 characters per second. £19.10.

### CARD READERS

80 column 1500/80 model, punch } £325  
 80 column 1400/80 model verifier. }  
 Excellent condition.

### HOLLERITH 80 COLUMN CARD PUNCH TYPE HO29 & VERIFIER H129 £225.

### DECODER 4 DIGIT READOUT

Can be used in constructing frequency counter or Digital Voltmeter. Consists of 4 transistorised cards each containing 10 NOR gates £19.10.0. Circuits supplied with Decoder. 5 Digit £25. P. & P. 15/-.

## PROGRAMME BOARDS BY SEALECTRO

These boards are basically a multi pole multi throw switch device consisting of a X-Y Matrix with two contact decks in the Z Plane running at 90 degrees to each other. Contact is made by either, aborting or plugging in pins. Ideal for prototype work, etc. Boards available in 24 x 60 2 plane £12.10.0. Pins available 1/3 each.



## MEMORY PLANES

Ferrite core memory planes with wired Ferrite cores. Used for building your own computer or as an interesting exhibit in the demonstration of a computer. Mounted on plastic material, frame 5 x 8 in. Consisting of matrices 40 x 25 x 4 cores each one individually addressable and divided into 2 halves with independent sense and inhibit wires. £8.10.0. P. & P. 3/-.

## MULLARD MATRIX CORE STORE STACKS

A.W. 510 5 planes 8x16 cores/per plane	£12/10
A.W. 511 6 planes 18x32 cores/per plane	£25
A.W. 534 20 planes 64x64 cores/per plane	£89/10
A.W. 537 8 planes 32x32 cores/per plane	£55
Single plane 40 x 25 x 4	£8/10
Flexi-writer 7 hole punch and keyboard	£199/10

## MEMORY STORE

M. M. 1044 complete with logic circuits mounted in Inhof cabinet £400

## COMPUTERS Burroughs E 201

225 words store. £450  
**COMPUTER.** 802B Hybrid computer with 1K store, in full working order. Complete with paper tape punches, and compatible for Hollerith 80-hole card-periphery. Numerous programmes available including test programmes. Full supporting literature. PRICE ON APPLICATION

## SYNCHRONOUS MOTORS

Model 87 1 r.p.m. and 1/60 r.p.m. Self starting complete with gearing shaft 1/2 in. dia. 1/2 in. long. 200/250 V. 50 Hz. New Condition Ex. Equipment. 30/- P. & P. 3/-.

## TRANSFER CASE



For sending data by personal carrier, GPO post, passenger train, etc. ideal. Suitable for despatching tape 20/- P. & P. 5/-.

## EICHNER 8 Hole Punch £49/10/0.

## EICHNER 8 Hole Reader £29/10/0.

## CANCELLED EXPORT ORDER

90 Column card sorter and punch type 425/0 price on application.

## SPOOLERS 1" and 1/2"

Both hand and motor drives available at £3.0.0 and £5.0.0 respectively.

## BRAND NEW TAPE SPOOLER


Suitable for 1 in., 1/2 in. and 3/4 in. tapes. Fully self-contained £99.10.0.

## 5" TAPE PUNCH

Suitable for machine control complete with 50 reels of tape £35.

# LOW COST ELECTRONIC AND SCIENTIFIC EQUIPMENT AND COMPONENTS

## CONTINUOUS TAPE CASSETTE

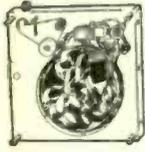


Suitable for sleep-learning, teaching programmes, programming machine tools, telephone answering etc. Complete with replay/record head and separate erase head. 1/2" tape twin track. Speed 3 1/2" per sec. Length of tape 88 feet, but will hold three times this amount. 230V. 50 Hz supply. £3-9.8. p. & p. 10/-.

## 802D DIGITAL DESK COMPUTER

Complete with punches and reader. Compatible for 80 columns punch card system. Storage magnetic core 1,020 word. Suitable for all types of work. Price on application.

## VEEDER ROOT 6 DIGIT COUNTER

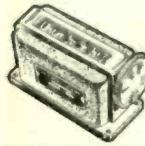

Suitable for counting all kinds of production runs, business machine operation. Mechanically driven. Type KA1337. Reset manual knob. Ex-equipment but new condition. Special price 25/- plus 5/- p. & p.

## MINIATURE SQUARE COUNTER 6 DIGIT



by Veeder Root. Rotary ratchet type, adds 1 count for each 36° movement of shaft 9/8 + 2/8 p. & p.

## HI-SPEED QUICK RESET ELECTRO MAGNETIC COUNTERS

Push button reset 6 digits. 48 v. D.C. 3.5 watts. 20 counts per second. Size 3.875 x 2.625 in. Panel mounting. List £3. Our price 50/8.




## 6 DIGIT ELECTRICAL IMPULSE COUNTER

With electrical and mechanical reset. Counter driven by a 110V D.C. 4.400 ohms coil. Reset 110V D.C. 800 ohm coil. Housed in plastic-alloy case. The units can be interlocked with each other to give vertical or horizontal displays. Price 79/6 p. & p. 5/-.


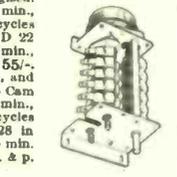
## REPEAT CYCLE TIMERS

These timers repeat a set cycle of switching operations via a cam and micro switch, for as long as the motor is energised. Single Cam RB 21 in 2 min., 4 min., 5 min., 6 min. cycles @ 45/-. Twin Cam RD 22 in 1 min., 2 min., 3 min., 4 min., 5 min. cycles @ 55/-. 4 Cam RD 24 in 4 min., and 5 min. cycles @ 75/-. 6 Cam RD 28 in 1 min., 2 min., 3 min., 4 min., 5 min. cycles @ 95/-. 8 Cam RD 28 in 2 min., 3 min., 4 min., 5 min. cycles @ 115/-. All + p. & p. 5/-.



## UNISELECTOR

8 and 4 Banks, 25 contact per bank, 2 sets of wipers 2 in. radius. Complete with surge capacitor. 25/- and 45/- respectively.

## MINIATURE DIGITAL DISPLAY

Operates on a rear projection 6.3 pilot lamp. The lamp projects the corresponding digit on the condensing lens through a projector lens, on to the viewing screen at the front of the unit. 1 in. width, 3 1/4 in. deep, 1 1/4 in. high. Weight 3 1/2 oz. Character size 1/4 in. high, 0.9 with 8 right hand decimal point and degree. Available to special order, words or other characters or colour, at cost of artwork or plates. List price 6 gns. Our price 49/6.



## LOW OHM SAFETY METER

12 milliamps 5 ohms, suitable for testing circuits where currents must be limited £12/10/- p. 17/6.

ALL ORDERS ACCEPTED SUBJECT TO OUR TRADING CONDITIONS A COPY OF WHICH MAY BE INSPECTED AT OUR PREMISES DURING TRADING HOURS OR WILL BE SENT ON APPLICATION THROUGH THE POST.

## MOTORS

### HYSTERESIS REVERSIBLE MOTOR

Incorporating two coils. Each coil when energised will produce opposite rotation of output shaft. 240V 50 Hz. 1/2 r.p.m., 1 r.p.m., 1/6 r.p.m., 120V 60 Hz, 1/10 r.p.m., 6 r.p.m. 30/- each. P. & P. 3/-.

### HIGH TORQUE INDUCTION MOTOR

3-30 oz/inch. Available in the following speeds only 240V 50 Hz 1/2 r.p.m., 1 r.p.m., 2 r.p.m., 120 V 50 Hz 20 r.p.m. 30/- each. P. & P. 3/-.

### LOW TORQUE HYSTERESIS MOTOR MA23

Ideal for instrument chart drives. Extremely quiet, useful in areas where ambient noise levels are low. High starting torque enable relative high inertia loads to be driven up to 6-oz/in. Available in the following speeds and ranges: 240V 50 Hz 15 r.p.m., 4 r.p.m., 2 r.p.m., 1 1/2 r.p.m., 1 r.p.m., 1/2 r.p.m., 1/3 r.p.m., 1/5 r.p.m., 1/6 r.p.m., 1/10 r.p.m., 1/12 r.p.m., 1/20 r.p.m., 1/40 r.p.m., 1/45 r.p.m., 1/60 r.p.m., 1/75 r.p.m., 1/120 r.p.m., 1/180 r.p.m., 1/360 r.p.m., 1/720 r.p.m., 1/1440 r.p.m., 1/2880 r.p.m., 1/120, 1/45 r.p.m., 120V 50 Hz 1/8 r.p.m., 1/5 r.p.m., 1/15 r.p.m., 1/16 r.p.m., 1/20 r.p.m., 1/30 r.p.m., 1/60 r.p.m., 1/120 r.p.m., 1/240 r.p.m., 1/300 r.p.m., 1/720 r.p.m., 1440 r.p.h. 25/- each. P. & P. 3/-.




### HYSTERESIS CLUTCH MOTOR

with integral clutch allowing the motor to drop out of engagement with the gear train, thereby facilitating easy resetting when used in timers or in conjunction with a light spring. 6 oz. torque at 1 r.p.m. 240 v., 50 c/s. L=left. R=right. 1/5 r.p.m. L, 8 r.p.m. R & L, 6 r.p.m. L, 4 r.p.m. L, 1/2 r.p.m. L, 1/5 r.p.m., 1/8 r.p.m., R & L, 1/10 r.p.m., 1/12, 1/15 r.p.m. L. Also 120 v. 50 c/s 2, 1/6, 1/12, 5/12, 4/11, 1/10 r.p.m. 25/-, P. & P. 3/-.

### HIGH PRECISION MAINS MOTOR

230V 50 Hz 1/8 h.p. continuously rated, 3000 r.p.m. Made by Croydon Engineering Model KA 60 JPB. Suitable for capstan motor. Size 8 in. long, 4 1/2 in. diameter with 6 in. diameter flange and 4 fixing holes. £4-10.0 each. £15.0 postage and packing.

## OSCILLOSCOPES

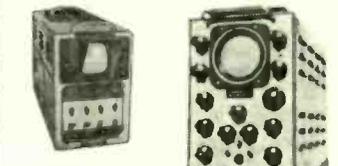

Cosnor 1035. £25.  
Cosnor 1035 Mk. III. £35.  
Cosnor 1049 Mk. III. £40.  
Solortron AD 513.2 L.F. & Servos & CD 5238.2 Long Persistent Tube. £49.10.  
Furzehill 0.100. £25.  
Airmec 249. £25.  
Solortron AD 557 Pulse & Radar Field. £55.  
Solortron Portable CD 1014 £30.  
Solortron CD 7118.2 Double Beam DC.7 Mtg. £65. Calibration extra.  
Mullard L101 Double Beam £98.10.  
Airmec 723. £19.10.  
Solortron Portable CD 1014 £30.

1200C Stroboscope for measuring rotational speeds of fans and moving mechanisms, etc. Speed Range: 600 r.p.m. - 14,500 r.p.m. PRICE: £45. CARRIAGE: 30/-.

### UNUSED MINIATURE 1/2 MILLION MAGNETIC STORAGE DRUM

Type N.S. 1389 16 write and 16 read heads 256 tracks magnetic storage drum. Each track at 800 r.p.m. Holds 1024 bits (32 words of 32 bits). Total storage 250,000 bits. Suitable for many data storage problems. 8" high, 10" dia., 2 1/2" base. £290, carr. extra.

### A.F. GENERATOR TYPE H MODEL I

High impedance, output from 20V. R.M.S. to 200 micro volts. Frequency Range 10c/s to 50kc/s. Distortion less than 1%. Square wave output 800 micro volts to 80 volts peak.

### PULSE AMPLITUDE ANALYSER £105

## PRECISION POTENTIOMETERS

### TEN TURN 360° ROTATION BRAND NEW

Res. Ohms	Linearity Per cent	Manufacturer	Model	Price
100/100/100	.....	Beckman	A	180/-
100	0.5	Beckman	A.8	80/-
200	0.1	Beckman	A	80/-
500	0.5	Beckman	A	80/-
500	0.1	Colvern	2501	48/-
500	0.5	Foxes	PX4	40/-
500	0.5	Colvern	2610	50/-
2K	0.5	Beckman	8A1101	80/-
2K	0.1	Beckman	7215	80/-
10K	0.5	Beckman	2402	30/-
10K	0.1	Beckman X	A	80/-
15K	0.1	Foxes	GPM15	50/-
18K	0.5	Beckman	A	80/-
20K	0.5	Beckman	A	80/-
30K	0.5	Colvern	A	80/-
30K	0.1	Beckman	8A95C	80/-
30K	0.1	Beckman	A.88	70/-
30K	0.5	Beckman	8A 1692	60/-
30K	0.25	Beckman	8A 1692	65/-
50K	0.5	Beckman	2402	30/-
50K	0.1	Beckman	A	80/-
50K	0.5	Beckman	A	80/-
50K	0.1	Beckman	A	80/-
100K	0.1	Beckman	A	100/-
100K	0.5	Beckman	A	70/-
100K	0.1	Colvern	2501	45/-
100K	0.5	Colvern	2610	50/-
298K	0.1	Beckman	8A3902	70/-
300K	0.1	Beckman	A	70/-

### THREE TURN 780° ROTATION

100/100	0.5	Beckman	A	60/-
300	0.5	Beckman	8303	45/-
10K	0.5	Beckman	C.8	45/-
20K/20K	0.1	Beckman	C.8	60/-
10K/10K	0.1	Beckman	C	60/-
50K	0.5	Beckman	C.8	35/-

### FIFTEEN TURN 5400° ROTATION

25K/25K	Beckman B	10 watts	£8.10
46K/46K	Beckman B	10 watts	£8.10

### TWENTY TURN 7200° ROTATION

250 ohms	General Controls	PXM130	80/-
1 Meg	General Controls	PXM130	80/-
50K	Reliance		40/-

### 156 TURN 56, 160° ROTATION

460 ohms	Kevin Hughes	KTP0701	£9.10s.
----------	--------------	---------	---------

### FIVE TURN 1800° ROTATION

500 ohms	Colvern	CLR 2505	40/-
U1.5K	Colvern	CLR 2605	40/-

### SINE COSINE


Keivin & Hughes SCP5. 14-4K	.....	£17.10.0
Colvern 8601	30K	£17.10.0
CLR 9602 - Cam Corrected 25K	.....	£17.10.0
SCP4	32K	£17.10.0
SCP1	38K	£17.10.0

### PRECISION BECKMAN 40 TURN 14,400° ROTATION

Wirewound Precision Potentiometer. SE 107A 20 watts at 40°C. 3 1/4" Diameter. Servo Mounting. 200 K. Brand New £12.10s. List Price £30.

## BRAND NEW LABORATORY TEST EQUIPMENT AT LESS THAN HALF PRICE
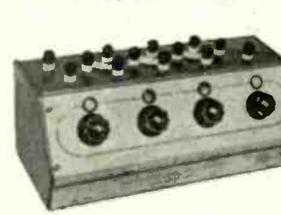
### HIGH VALUE RESISTANCE BOX TYPE R.7003



Specification. Range: 0.01-111 Meg. in 0.01 Megohm divisions. Accuracy: 0.05%. Maximum power rating: 0.1W per step. Case: Hammer finished stove enamel. List price £60. Our price £22/10/-.

### PORTABLE WHEATSTONE BRIDGE



Specification. Type: Moving Coil Galvanometer. Ranges: 1. 0.05 to 5 ohms. 2. 0.5 to 50 ohms. 3. 5 to 500 ohms. 4. 50 to 5,000 ohms. 5. 500 to 50,000 ohms. Scales: Switched. Bidetwivel: 0.5 to 50. Galvanometer Scale: 100-10. Case: Moulded plastic. Internal Source: 4V. Dry battery. Dimensions: 200 x 110 x 65mm. Weight: 0.9 kg. List price £25. Our price £20/18/6.

### MUTUAL INDUCTANCE BOX TYPE R.7005

Specification Range: 0 - 11.100 mH in 0.002 mH divisions. Accuracy: ±(0.3 x M^-0.012) % where M = value of mutual inductance in mH set on the box. Frequency range: 0 - 3.5 K/c/s for all decades except X1=0-15 K/c/s. Maximum current: 0.5A for decades 1A for variometer (both primary and secondary windings). Case: Polished teak. List price £65. Our price £26.10.




### MUTUAL INDUCTANCE COIL TYPE R.7006

Specification. Value: 0.001 H. Accuracy: ±0.3%. Operating Frequency: 5 Kc/s, 10 Kc/s. Maximum current: 1A, 3A. Resistance of coils: 4 ohm, 1 ohm. Case: Moulded plastic. List price 8 gns. Our price 50/-.

CARRIAGE EXTRA

ELECTRONIC BROKERS LTD., 49-53 PANGRAS ROAD, LONDON, N.W.1. Tel: 01-837 7781/2 Cables: SELELECTRO
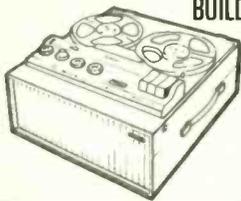
# HENRY'S RADIO LTD. ENGLAND'S LEADING COMPONENT AND EQUIPMENT CENTRES




## BUILD A QUALITY 4 TRACK TAPE RECORDER

To get the best out of your MAGNAVOX DECK, you need a MARTIN RECORAOKIT. This comprises a special high quality 6 valve amplifier and pre-amplifier which comes to you assembled on its printed circuit board — in fact everything for making a superb Tape Recorder. You need no experience or technical skill to bring this about. THE INSTRUCTIONS MANUAL MAKES BUILDING EASY, AND SUCCESS IS ASSURED. Kit comprises: Deck, Amplifier, Cabinet and speaker, with microphone, 7" 1200 ft. tape, and spare spool. ASK FOR BROCHURE 6. TODAY'S VALUE £60. PRICE 39 gns. p.p. 22/6. NOTHING ELSE TO BUY
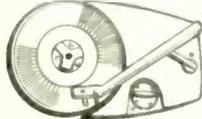
## SCOOP! STAAR RECORD PLAYER

Deck plays 33, 45, 78, R.P.M. records 9 volt operated, with mono cartridge. BRAND NEW... as illustrated.



PRICE 59/6. p.p. 3/6. Send for leaflet No. 2.




## MULLARD 1 WATT AMPLIFIER

Portable Transistor Unit—ideal for Intercoms, Baby Alarms, Telephone, Record Players or Guitar Practice. 9 Volt 5 transistors with volume control, output 3 ohms. Ideal for use with STAAR RECORD DECK. PRICE 45/- p.p. 2/6.

OTHER ITEMS: Suitable 7 x 4 Inch. 3 ohm speaker 17/6 p.p. 1/6. Reaxine covered cabinet 12 x 9 x 4 12/6 p.p. 2/6. P.P. 9 volt battery 3/9. Write for leaflet No. 2.


## GARRARD RECORD DECKS

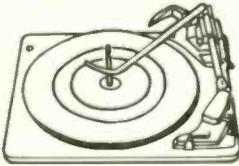

All the latest models BRAND NEW and guaranteed — TERRIFIC SAVINGS!

- \*2025 STEREO £ 7.19.6
- \*2025TC DIAMOND, STAH.C. £ 9.19.6
- \*3000 STEREO 9TAH.C. £ 9.19.6
- \*SP 25 Mk.II £11.19.6
- \*SL 55 £11.19.6
- \*A70 Mk.II £12.10.0
- \*AT 60 K.II. £13.10.0
- \*SL 65 £14.10.0
- AP 75 £19.0.0
- 401 £28.7.6
- SL 75 £29.0.0
- SL 95 £35.0.0
- GL 75 COLORING £33.0.0
- GL 75 P £46.15.0

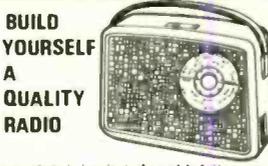ALSO IN STOCK — THORENS — Lenco — B.S.R. Carriage/insurance 7/6 extra on any model. WB4 BASES £9.19.6. PERSPEX COVERS £3.10.0. \*Special offer base and cover available for these models at £4.15.0. Carriage 5/-. Complete range of Cartridges/Plinths/Covers. SEND FOR 8 PAGE BROCHURE 16/17 TODAY.



## BUILD YOURSELF A QUALITY RADIO

New printed circuit design with full power output. Fully tuneable on both mw/lw. bands. 7 Mullard transistors, Fitted 5" speaker, Room Filling Power. Easy to build with terrific results. All local and continental stations. Complete detailed instructions.

TOTAL COST £6.19.6. p.p. 4/6. Ask for Leaflet No. 1.

## TRANSISTORS DIODES RECTIFIERS

WE HAVE THE MOST COMPREHENSIVE STOCK IN GREAT BRITAIN. NEW 1969 LIST OF 1000 TYPES. SEND FOR FREE COPY TODAY (LIST 36) Whether you require one or 1000, devices we can fulfil your order from stock! For quantity quotations telephone: (011) 723 0401 Ex. 4. or (011) 402 6823.

## HENELEC 5-5 STEREO AMPLIFIER

Excellent low priced British designed Stereo Amplifier for use with Record Decks, Mike, Tuners. 16 transistor mains operated. Output 545 watts for 8-15 ohm speakers. Black, silver and wood finish, size 13" x 3" x 6". PRICE £13.10.0. p.p. 7/6. (Leaflet on request). Complete Stereo System 5-5. Garrard 2025 stereo, 5-5 Amplifier, Plinth/Cover, Two 10 watt speakers with tweeters in polished cabinets. Usual price £47.0.0. OUR PRICE £39.10.0. p.p. 20/- ASK FOR BROCHURE 13



## SINCLAIR EQUIPMENT

The SINCLAIR IC-10 is the worlds first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself has an output power of 10 watts, yet with an overall size of 1 x 0.4 x 0.2 in.

IC-10 Integrated Circuit Amplifier	59/6	OTHER TYPES OF INTEGRATED CIRCUITS			
Z30 Stereo 60	89/6	RCA. CA 3014	29/6	G.E. PA246*	52/6
P25 Power Supply	£4.19.6	RCA. CA 3018	22/6	SL402 Plessey	45/0
O16 Loud Speaker	£8.19.6	RCA. CA 3020	29/6	SL403 Plessey	49/6
Z12 Amplifier	89/6	RCA. CA 3036	18/6	S.G.S. UL910	10/0
PZ 4 Power unit	99/6	Sinclair I.C.10.	59/6	S.G.S. UL914	11/0
Stereo 25	£9.19.6	G.E. PA230*	22/6	Mullard TAA263	15/0
O14 Speaker system	£7.19.6	G.E. PA234*	20/0	*Data sheets 3/6 set for these, for others see catalogue.	
		G.E. PA237*	37/6		

## BUILD THIS VHF FM TUNER

5 MULLARD TRANSISTORS. 300 kc/s BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION MONO & STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it — VHF FM gives the REAL sound.

PARTS TOTAL COST £6.19.6. DECODER £5.19.6. ASK FOR LEAFLET No. 3. (FOR STEREO)



## HENRY'S RADIO Fully Illustrated CATALOGUES

ALL TYPES OF ELECTRONIC COMPONENTS TEST EQUIPMENT KITS BUILT UNITS



B HIGH FIDELITY & GENERAL AUDIO EQUIPMENT CATALOGUE

COMPREHENSIVE · CLEAR · CONCISE · CATALOGUES

A Over 300 pages fully detailed and illustrated with more than 6,000 stock items. Everything for amateur and professional use. Complete with 5 vouchers 10/- value, for use with purchases.

ORDER AS CATALOGUE A PRICE 7/6. p.p. 2/-

B New audio and high fidelity catalogue. 120 pages containing ideas and equipment for every application. Special low prices for all leading makes. Plus 12/6 extra discount voucher.

ORDER AS CATALOGUE B. PRICE 7/6. p.p. 1/-

WHY NOT SEND AWAY TODAY!


## AUDIO EQUIPMENT

Mono or Stereo Audio equipment developed from Dinsdale Mk. II — each unit or system will compare favourably with other professional equipment selling at much higher prices.

£11.12.6. to £38.17.6. (all units available separately).

THE FINEST VALUE IN LOW COST HIGH FIDELITY — CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE YOURSELF POUNDS.

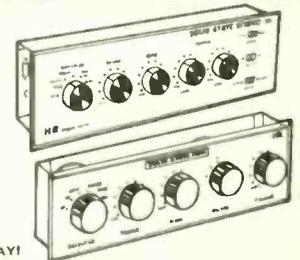SEND FOR BROCHURES No. 12/14 and 21 TODAY!



## HI-FI equipment to suit EVERY POCKET

HIGH FIDELITY AUDIO EQUIPMENT CATALOGUE 5/- p.p. 1/-



VISIT OUR NEW HI-FI CENTRE AT 309 EDGWARE ROAD, for all leading makes of — AMPLIFIERS, TUNERS, DECKS, SPEAKERS, MICROPHONES, TEST EQUIPMENT. ALL WITH DISCOUNTS — IT WILL PAY YOU TO PAY US A VISIT. AUDIO SYSTEMS £40 — £300 TO SUIT EVERY POCKET. DEFERRED TERMS AVAILABLE. SEND FOR ILLUSTRATED BROCHURE 16/17. TWO DEMONSTRATION ROOMS

## ELECTRONIC ORGANS

COMPLETE KITS FOR THE HOME CONSTRUCTOR

STAR FEATURES: \*ALL TRANSISTOR PRINTED CIRCUIT DESIGNS. \*BRITISH DESIGN. \*STEP BY STEP DETAILED INSTRUCTIONS. \*GIVES UP TO 50% ON COMMERCIAL EQUIVALENT. \*EVERYTHING SUPPLIED DOWN TO THE LAST ITEM. \*FULL AFTER SALES SERVICE & ADVICE. \*CREDIT SALE & H.P. TERMS AVAILABLE.

We are pleased to offer the choice of FOUR British designs from a single manual portable at £99 THE MAYFAIR for light or classical music — to a two manual five octave de-luxe model with OAK CONSOLE from £265 for the serious musician.

These kits are the result of years of research and design and offer the best that is essential to good organ designs, coupled with excellent value are within the reach of most pockets. No technical skill or knowledge is required in construction, with the aid of the STEP BY STEP illustrated manuals will produce an instrument that will be a delight to own and use and will give years of trouble free entertainment for the whole family. SEND FOR ILLUSTRATED BROCHURES 9/10/11 TODAY! When in LONDON call in—SEE, HEAR, PLAY FOR YOURSELF.

Organ Demonstration Room 1st Floor, PRACTICAL ELECTRONICS ORGAN — ORGAN COMPONENTS

We are able to supply all items for this series, details on request.

Start building for as little as £10

MODELS FROM £99 — £350.



ILLUSTRATION OF GROSVENOR ELECTRONIC ORGAN

Built models available from £124.

# HENRY'S RADIO LTD.

Mail Order Dept. Components, Organ Dept. 303 EDGWARE ROAD, LONDON W.2. Telephone: 01-723 1008 9

High Fidelity and Equipment Centre 309 EDGWARE ROAD, LONDON W.2. Telephone: 01-723 6963

OPEN MON-SAT 9am-6pm THURS 9am-1pm



# QUALITY COMPONENTS AND EQUIPMENT

## NEW RANGES FOR THE AMATEUR AND PROFESSIONAL USER




**\* QUALITY PANEL METERS**  
 18 Series. Face size 42 x 42mm (1 1/2 x 1 1/2 in). 50µA, 37/6; 100µA, 35/-; 200µA, 32/6; 500µA, 37/6; 1mA, 5mA, 10mA, 50mA, 100mA, 500mA, 25/- each; 10V, 20V, 50V, 100V, 300V and 500V, 25/- each; 1A and 5A, 25/- each. "S" meter, 1mA, 29/6. VU meter, 37/6. 65 Series. Face size 86 x 78mm (3 1/4 x 3 in). 50µA, 62/6; 100µA, 52/6; 200µA, 47/6; 500µA, 45/-; 1mA, 5mA, 10mA, 50mA, 37/6 each. "S" meter, 1mA, 42/6. Other ranges and sizes available. List on request with full details.



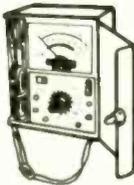**\* 50,000 OHMS PER VOLT MULTIMETER**

Recommended quality instrument with mirror scale and overload protection. Large 3 1/2" x 1 1/2" d.c. (50KΩ/V); 0/6/30/120/300/600/1200V a.c. (10KΩ/V); 0/30µA/6/60/300mA, 0/12Ω resistance 0/10kΩ/1/10/100MΩ. Meter movement 20µA. Polarity reversing switch. Complete with batteries, leads and instructions.  
**AF105 Price £8.10.0 p.p. 2/6 Leather case 28/6**




**\* SINE/SQUARE WAVE AUDIO GENERATOR**



Provides audio output on 4 bands. Sine wave 20c/s to 200kc/s, output up to 7V; square wave 60c/s to 20kc/s, 7V p.p. Distortion under 2%. Output impedance 1kΩ. Variable output amplitude control. Supplied with leads and instructions. A.C. mains operated.  
**TE22 Price £16.10.0.**

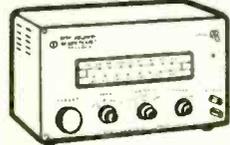**\* DELUXE SINE-SQUARE WAVE RC AUDIO GENERATOR**



Weinbridge RC Audio oscillator featuring four overlapping scales covering 180c/s to 200 Kc/s. Output waveforms are sine, square and complex. Mirrored scale with smooth geared tuning control. Output 5 volts RMS or 10 volts P.P. Sinewave response ±0.5dB. Distortion under 1% at 1Kc/s. Stability ±1%. Accuracy ±2%. 0/P impedance under 3kΩ. Variable Attenuator. Mains operated. With Handbook.  
**ORC 27A Price £28 10 0 pp.10/-**

**\* VACUUM TUBE VOLTMETER**



Features low price for such an instrument. Large 6 in full view scale meter. 28 ranges. D.C. volts: 0/1/15/150/1500/500/1500. A.C. volts: 0/1/15/150/500/1500 r.m.s.; 0/1/4/4/14/40/140/400/1400/4000 p.p. Resistance: R x 10-100-1k-10k-100k-1M-10M. Range 0.2 ohm to 1,000MΩ. dB scales: -10 volts: 0/1/15/150/500/1500. Complete with instructions and leads.  
**MODEL TE65 £17.10.0 p.p. 7/6 HV Probe 50/- R.F. Probe 42/6**

**\* 20,000 OHMS PER VOLT MULTIMETER**




Popular model but with extra scale range. 20,000 ohms per volt. 0/5/25/50/250/500/2500V d.c., 0/1/10/50/100/500/1000V a.c., 0/50µA, 0/21/250mA. Resistance 0-6kΩ and 6MΩ. Also dB scales or capacitance.  
**Model 200H ... 77/6 pp.2/- (Leather case, Price 15/-)**

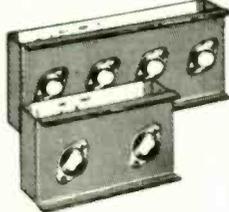**\* PORTABLE OSCILLOSCOPE**



Features 3 in clear view tube, easy to use controls and good stability. Y amp. Sensitivity, 1V p.p./CM. Bandwidth 1.5 cps-1.5 MHz. Input Imp. 2 meg Ω. 25 PF. X amp sensitivity, .9V p.p./CM. Bandwidth 1.5 cps-800 KHz. Input Imp. 2 meg Ω. 20 PF. Time base, 5 ranges 10 cps-300 KHz. Synchronisation. Internal/external. Illuminated scale, 140 x 215 x 330 MM. Weight 15 lbs. 220/240V. A.C. Supplied brand new with handbook.  
**TO3 Price £35 p.p. 10/-**



**\* TRANSISTOR POWER AMPLIFIERS**

12 watt 3 ohm 100mV Input 24 volt supply. Model MPA 12/3 £4.10 p.p. 3/-  
 12 watt 12-16 ohm 100mV Input 40 volts supply. Model MPA 12/15 £5.3 p.p. 13/-  
 25 watt 8-16 ohm 180mV Input 50/60 volt supply. Model MPA 25 £7.10 p.p. 4/6  
 Power Supplies 24 40 volt 90/ p.p. 3/6 50-60 volt 97/6 p.p. 4/6  
 Model PA7. 7 watt Amplifier 3 ohms O.P. 7mV Input, operates 12-18 volts D.C. Price 72/6 p.p. 2/6

\* 100 WATT AMPLIFIER—details on request.

**\* GRID DIP METER**

All transistor grid dip meter, absorption wavemeter and osc. detector. Frequency range 440kc/s to 280Mc/s in 6 coils. Uses 3 transistors plus diode with 500µA meter. Internal battery.  
**TE15 Price £11.10.0 pp.3/6**



**\* DC STABILISED POWER SUPPLY**



Switched DC Stabilised Outputs UP TO 1AMP. 3-6-9 & 12 VOLTS. Indicator lamp for each voltage. Fully fused mains operated. Negligible ripple. Regulation 1%.  
**SE101A Price £8 15 0**

**\* FIELD STRENGTH METER**

5-Ranges 1-250 mc/s. Fitted 200µA meter. Earphone output. Calibrated tuning scales.  
**FL30HA Price 72/6 pp.2/-**  
 Also non-calibrated type peaking F/S meter. FSI Price 45/- pp.2/6

**\* TRANSISTORISED INTERCOMMS**

2-station, £3.10.0; 3-station, £5.15.0; 4-station, £6.12.6 (2-station uses no wires) mains operated, £11.19.6. Telephone amplifier, 59/6.

**\* SIGNAL INJECTOR**

New model for checking all audio and RF up to VHF. Simple to use. Battery operated. Output approx. 1kc/s. 1-4V pp. Harmonics up to VHF.  
**SE250B Price 35/- p.p. 1/6**

**\* MATCHING SIGNAL TRACER**

SE 500 Price 27/6 p.p. 1/6

Suppliers of quality components and equipment for over 25 years

AUDIO — HIGH FIDELITY Complete range in stock to suit all Hi-Fi and Public Address requirements.  
 COMPONENTS UK's largest supplier of components. EVERYTHING YOU NEED  
 SEE CATALOGUE ON FACING PAGE



**\* TRANSISTOR CHECKER**

Complete capacity for checking all transistors npn and pnp for alpha, beta and German. Also diodes complete with leads and instructions. ZQM-2. Price £5.19.6, p.p. 3/6.



**EXPERIMENTER'S MODULE**

Terrific offer of brand new STC time delay electronic units. Adjustable 3-15 recs. 9-12V operated. Supplied complete with suggested uses circuits. STC Module Price 35/-.

**9 & 12V 100mA STABILISED SUPPLY**

Size 3" x 2" x 1 1/2". Fused ready to use. U.K. made Transistorised.  
**9V 45/- pp.2/6 12V 47/6 pp.2/6**

**Transistors**

Huge quantities in stock for industrial users—Write for Industrial Price List. Includes all types of Semiconductor Device.

**PORTABLE GEIGER COUNTERS**



FOR MEASUREMENT OF RADIO-ACTIVITY. Supplied complete with instructions, harness, cables and probe. List price £70. **OUR PRICE, NEW, TESTED COMPLETE WITH BATTERIES £7.10.0** POST 10/- SPARE BATTERIES 15/- PAIR. POST 5/-

**DOSIMETER POCKET-TYPE 0-50r 12/6**



**NOMBREX TRANSISTORISED Test Equipment**

MODEL	PRICE	Leaflet
29a RF. Gen.	21 0 0	35
29x Xtal RF Gen.	29 10 0	35
30 Audio Generator	19 10 0	24
31 R.F. Generator	12 10 0	25
32 C.R. Bridge	10 10 0	26
33 Inductance Bridge	20 0 0	29

**STEREO HEADPHONES**

Featuring soft Padded Headsets, wide frequency response, Adjustable Headbands. Fitted Jack plugs.



DHO 2/5 Recommended 25C/5-15KC/S .. £2.19.6  
 SE28 Built in Tweeters and Volume Controls £9.19.6  
 KOSS. KO727 £16.10.0. PRO-4A .. £3.0.0  
 SP-3KC .. £11.15.0

**CALL FOR DEMONSTRATION**

Mono Switched 8/16 ohms and 4K ohms Price £4.4.0  
**Stereo Headphone Amplifiers**  
 Inputs for PU/Tuner, Battery Model Mains Operated High Quality  
 Eagle MA10 .. £8.19.6  
 Shure SA2/E .. £16.16.0

**The Detector Unit consists essentially of a highly sensitive 931A photo-electric cell combined with a firing circuit. Incorporates a single cold cathode electronic relay, capacitors and resistors designed to fail to safety if external wiring is open or short circuited. Encapsulated in a resin which fully insulates the unit electrically and provides a high degree of mechanical and thermal shockproofing. Original price £74. OUR PRICE BRAND NEW £6 each, with data sheet**


**GRAVINER FIRE DETECTOR UNIT**



SIZE 4 x 3 x 2 1/2 in. Limited quantity available.

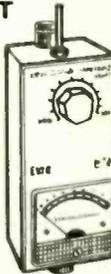**\* SWR ALIGNMENT METER**

Ideal for all transmitter alignment. Built-in field strength meter 100µA. Complete. Ready to use. SWR 1:1 to 1:3.  
**SWR 3 .. Price 69/6 p.p. 2/6**



**WELLER SOLDERING SUPPLY IRONS**

8200 Gun & Iron .. 59/6  
 8200D PK Gun Kit .. 79/6  
 ANTEX CN Iron .. 29/6  
 ANTEX Iron Kit .. 42/6

**\* MULTIMETER**

Return of a popular model. 2000 ohms/V. 0/10/50/500/1000V a.c./d.c. 0/50µA. 0/10/250µA d.c. 0/10/100kΩ/2/1MΩ resistance. dB and capacitance scales. Size 5 in. x 3 1/2 in. x 1 1/2 in. Robust and easy to use. Complete with leads, batteries and instructions.  
**THL 33A 82/6 p.p. 2/6 Leather case Price 22/6**



**\* ALL ITEMS OFFERED ARE BRAND NEW STOCK — ALWAYS IN STOCK \***

**HENRY'S RADIO LTD.**  
 303 & 309 Edgware Rd, London W2

'303' Components/Equipment/Organ. Parts also MAIL ORDER DEPT. 01-723-1008/9  
 '309' Test Gear/High Fidelity etc. 01-723 6963

ALL MAIL ORDERS TO '303'  
 SHOP HOURS 9 a.m.—6 p.m. THURSDAY 1 p.m.  
 OPEN ALL DAY SATURDAY.





2kW FAN HEATER

Three position switching to suit changes in the weather. Switch up for full heater (2kW), switch down for half heat (1kW), switch central blower cold for summer cooling—adjustable thermostat acts as auto control and safety cut-out. Complete kit £3.15.0. Post and ins. 7/6. Made-up model £4.5.0. Post and ins. 7/6.

FLUORESCENT CONTROL KITS

Each kit comprises seven items—Choke, 2 tube ends, starter, starter holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Grolux" tubes for fish tanks and indoor plants. Chokes are super-silent, mostly resin filled. Kit A—15.20 w. 19/6. Kit B—30.40 w. 19/6. Kit C—80 w. 23/6. Kit E—65 w. 19/6. Kit MF1 is for 6in., 9 in. and 12in. miniature tubes, 19/6. Postage on Kits A and B 4/6 for one or two kits then 4/6 for each two kits ordered. Kits C, D and E 4/6 on first kit then 3/6 for each kit ordered. Kit MF1 3/6 on first kit then 3/6 on each two kits ordered.

BLANKET SWITCH

Double pole with neon let into side so luminous in dark, ideal for dark room light or for use with waterproof element—new plastic case. 5/6 each. 3 heat model 7/6.

BLANKET SIMMERSTAT

Although looking like, and fitted as, an ordinary blanket switch, this is in fact a device for switching the blanket on for varying time periods, thus giving a complete control from off to full heat. Also suitable for controlling the temperature of any other appliances using up to 1 amp. Listed at 27/6 each, we offer these while our stocks last at only 12/6 each.

REED SWITCHES

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types: Miniature. 1in. long x approximately 1/4in. diameter. Will make and break up to 1A up to 300 volts. Price 2/6 each. 24/- dozen. Standard. 2in long x 3/16in. diameter. This will break currents of up to 1A, voltages up to 250 volts. Price 2/- each. 18/- per dozen. Flat. Flat type, 2in. long. Just over 1/16in. thick, approximately 1/4in. wide. The Standard Type flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1 amp 200 volts. Price 6/- each. £3 per dozen. Small ceramic magnets to operate these reed switches 1/3 each. 12/- dozen.

HIGH CAPACITY ELECTROLYTICS

Brand new, not ex-equipment. 100 mfd. 25v., 1/3 each 12/- doz. 200 mfd. 25v., 1/6 each 15/- doz. 500 mfd. 12v., 2/- each £1.1.0 doz. 1000 mfd. 12v., 3/- each £1.10.0 doz. 5000 mfd. 12v., 4/9 each £2.8.0 doz. 10,000 mfd. 6v., 8/9 each £3.0.0 doz. 10,000 mfd. 15v., 8/6 each £4.10.0 doz. 15,000 mfd. 10v., 10/8 each £5.0.0 doz. 60,000 mfd. 8v., 22/- each £10.0.0 doz. 70,000 mfd. 13v., 40/- each £20.0.0 doz.

TELESCOPIC AERIAL

For portable, car radio or transmitter. Chrome-plated—six sections extends from 7 1/2 to 47in. Hole in bottom for 6BA screw. 7/6.

TOGGLE SWITCH

3 amp 230v. with fixing ring. 1/6 each 15/- dozen.

80 OHM BALANCED ARMATURE EAR PIECE

Usable as microphone or loudspeaker. 4/6 each.

MINIATURE EAR PIECE

As used with imported pocket radios. 1/6 each 15/- doz.

ISOLATION SWITCH

20 Amp D.P. 250 Volts. Ideal to control Water Heater or any other appliance. Neon indicator shows when current is on, 4/6 48/- per dozen.

FLEX BARGAINS

Screened 3 Core Flex. Each core 14/0076 Copper PVC insulated and coloured, the 3 cores laid together and metal braided overall. Price £3.15.0 per 100 yds. coil. 15A 3 Core Non-kink Flex. 76/0076 insulated coloured cores, protected by tough rubber sheath, then black cotton braided with white tracer. A normal domestic flex as fitted to 3kW fires. Regular price 3/6 per yd. 50 yd. coil £4, or cut to your length 2/- per yard. 10A 3 Core Non-kink Flex. As above but cores are 28/0076 Copper. Normal price 2/6 per yd. 100 yd. coil £7.10.0, or cut to your length 1/9 per yard. 6A 2 Core Flex. As above, but 2 cores each 23/0076 as used for Vacuum Cleaners, Electric Blankets, etc. 39/6 100yd. coil.

15/20 AMP CONNECTORS

Polythene insulated 12-way strip. 2/6 each 24/- doz.

13 AMP FUSED SWITCH

Made by G.E.C. For connecting water heater etc., into 13 amp ring main. Flush type 3/6 each 30/- doz. Metal boxes for surface mounting 1/6 each 15/- doz.

MICRO SWITCH

5 amp. changeover contacts. 1/9 each 18/- doz.

SUPPRESSOR CONDENSER TCC

1 mfd. 250v. A.C. working metal cased with fixing lug. 1/9 each 18/- doz.

HEAT & LIGHT LAMP

275W. Internally mirrored bulb, with b.c. end for plugging into lamp holder. 19/6 each plus 4/6 post and insurance.

TUBULAR TYPE BY PHILLIPS

500W. 29/6 plus 4/6 post and insurance. 750W. MICRO AMP MOVING COIL METER 2 1/2in. flush mounting, ex-W.D. 15/- each plus 3/6 post and insurance for any quantity.

DIGITAL CLOCK

An imposing instrument ideal for modern reception centre or for Managing Director's office—definitely a showpiece to create interest and efficiency—main frequency controlled so always keeps right time without adjustment—in black semi-matt perspex case—made up, tested and guaranteed—offered for only the cost of components £29.10.0, post and insurance 10/-.



SOLDER GUN

A must for every busy man, gives almost instant heat; also illuminates showpiece to create interest and efficiency—main frequency controlled so always keeps right time without adjustment—in black semi-matt perspex case—made up, tested and guaranteed—offered for only the cost of components £29.10.0, post and insurance 10/-.

MINIATURE EXTRACTOR FAN

Beautifully made by famous German Company. PAPST System, 230/240 A.C. Mains operated, size 3 1/2in. x 3 1/2in. x 2in. Made for instrument cooling but ideal to incorporate in a cooker hood, etc. 65/- P. & p. 2/9.

HORSTMANN 'TIME & SET' SWITCH

(A 30 Amp Switch). Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost on period of up to 3 hours. Equally suitable to control processing. Regular price probably around £5. Special snip price 29/6. Post and ins. 4/6.

DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs. Supplied complete with 6 feet of heavy cable and 13 amp plug. Similar panels advertised at £5. Our price: Kit of parts 39/6, plus 3/6 post and insurance. Made up 45/- plus 4/6 P. & I.

24 HOUR TIME SWITCH

Mains operated. Adjustable Contacts give on/off per 24 hours. Contacts rated 20 amps, repeating mechanism so ideal for shop window control, or to switch hall lights (anti-burglar precaution) while you are on holiday. Made by the famous Smiths Company. This month only 39/6 complete with perspex cover, new and unused, plus 3/6 postage and insurance, a real snip which should not be missed.

DOUBLE ENDED MAINS MOTOR

On feet with holes for screw-down fitting. To drive models, oven, blower heater, etc. 10/- each, plus 3/6 post and insurance. 6 or more post free.

DIAMOND H OVEN THERMOSTAT

Type 20 TH with capillary tube and sensor, 20 amp A.C. type as fitted to many cookers adjustable by control knob (not supplied). 12/6 each.

BATTERY OPERATED TAPE DECK

With Capstan control. This unit is extremely well made and measures approx. 6 x 5 x 2in. deep. Has three piano key type controls for Record, Playback and Rewind. Motor is a special heavy duty type intended for operation off 4.5 volts. Supplied complete with 2 spools ready to install. Record Replayhead is the sensitive M4 type intended for use with transistor, amplifier. Price 79/6. Post and insurance 4/6.

PROTECT VALUABLE DEVICES

From thermal runaway or overheating. Thyristors, rectifiers, transistors, etc., which use heat-sinks can easily be protected; simply make the contact thermostat part of the heat sink. Motors and equipment generally can also be adequately protected by having thermostats in strategic spots on the casing. Our contact thermostat has a calibrated dial for setting between 80°-190°F, or with a dial removed range setting is between 80° to 800°F. Price 10/-.

ATLAS SLIMLINE FLUORESCENTS—THE TWENTYLITE AND TWIN FORTY

A Fluorescent lighting unit made by the famous Atlas company, with super silent polyester filled choke and radio suppressed starter. The tube springs in and out and the whole unit is beautifully made and finished white enamel. Amazingly economical. If left on all the time costs only one penny per day (uses 1 unit). Measures 2ft. long. Is ideal Kitchen, Bedroom, Hallway, Porch, Loft, etc. Don't miss this amazing offer, 39/6 with tube. Assembled ready to install. 4 ft. twin model 59/6. Post and ins. 6/6 extra.

1 WATT AMPLIFIER & PRE-AMP

5 transistors—highly efficient made for use with tape-head £4 but equally suitable for microphone or pick up. Limited quantity 29/6. Full circuit diag. also shows tape controls 5/-.

VARYLITE

Will dim incandescent lighting up to 600 watt from full brilliance to out. Fitted on M.K. flush plate, same size and fixing as standard wall switch so may be fitted in place of this, or mount on surface. Price complete in heavy plastic box with control knob £3.19.6.

HI FI BARGAIN

FULL F1 12 INCH LOUDSPEAKER. This is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi load and Rhythm Guitar and public address. Flux Density 11,000 gauss—Total Flux 44,000 Maxwell—Power Handling 15 watts R.M.S.—Cone Moulded fibre—Freq. response 30-10,000 c.p.s.—specify 3 or 15 ohms—Main resonance 60 c.p.s.—Chassis Diam. 12in.—12in. over mounting lug—Baffle hole 11in. Diam.—Mounting holes 4, holes—1in. diam. on pitch circle, 1 1/2in. diam.—Overall height 5 1/2in. A 26 speaker offered for only £3.9.6 plus 7/6 p. & p. Don't miss this offer. 10in. 30 watt £7.19.6. 18in. 100 watt £24.10.0.

TANGENTIAL HEATER UNIT

Winter is coming but act today and you won't dismay. This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW. element and 1kW. element allowing switching 1, 2 and 3kW. and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only need on/off switch. 79/6. Postage and insurance 6/6. Don't miss this.

Where postage is not stated then orders over £3 are post free. Below £3 add 2/9. Semi-conductors add 1/- post. Over £1 post free. S.A.E. with enquiries please.

MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 6 way—1 pole, 12 way. All at 3/6 each. 36/- dozen, your assortment.

WATERPROOF HEATING ELEMENT

26 yards long 70W. Self-regulating temperature control. 10/- post free.

INSTRUMENT MOTOR WITH GEARBOX

Made by famous Smiths Company. Very powerful, although only quite small. Overall dimensions approx. 1 1/2in. deep by 2in. dia. Available with the following speeds: Revs. per day 2—8—12. Revs. per hour 1, 2, 4, 6, 12, 20, 30. Revs. per minute 1, 2, 3, 4, 6, 8, 15, 30, 60. 17/6 each.

CONTROL DRILL SPEEDS

DRILL CONTROLLER

Electronically changes speed from approx. 10 revs. to maximum. Full power speeds by finger-tip control. Kit includes all parts, tools, etc. plus full instructions. Made up available 37/6 plus 2/9.

MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fans, blower, heater etc. New and perfect. Snip at 9/6. Post 3/- for first one then 1/- for each ordered. 12 and over post free.

ELECTRIC CLOCK WITH 25 AMP SWITCH

Made by Smith's, these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The 20 amp dual enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only 39/6, less than the value of the clock alone—post and insurance 2/9.

THERMAL CUTOUT

A miniature device 1/2in. dia. on one screw fixing mount—can be used for motor over-load protection, fire alarm, soldering iron switch off, etc., etc.—15 amp contacts open with flame radiant or conducted heat. 1/6 each, 15/- doz. £5.10.0.

COPPER CLAD ELEMENT

1250 watts—4ft. long but bent to U shape, ideal for overhead heater—just mount reflector above. 12/6 each, plus 4/6 post. £8 doz. post paid.

0.0005mFd TUNING CONDENSER

Proved design. Ideal for straight or reflex circuits 2/6 each. 24/- dozen.

Battery Record Player. Made by Collaro. This is made up on a unit plate with speed selector and pick-up. The turntable is a heavy one and measures approximately 9 1/2in. Pick-up is fitted with the famous "Studio" cartridge. Price 69/6, post and insurance 6/6.

E.H.T. Condenser, 28kV, 0.001 mfd. Suitable for transmitting test conditions 6A at 300k/c. Bakelite case. 18/6 each.

85 Watt Tubular Element. Very well made unit. The element is wound on a porcelain former then encased in a brass tube terminated with beaded leads 12in. long. Normal mains voltage. Price 5/- each or 54/- per doz.

Press to Make Switch. Double pole, 5 amp contacts can be used as single pole, 10 amp, contacts 250 volt working. Single hole fixing. 2/6 each, 24/- doz.

Door Switch. Contacts open when plunger is depressed. Prevents lights being left on. 15 amp contacts, 230 volt working. Made by Arrow. 3/6 each, 36/- per doz.

Rotary Appliance Switch. 16 amp, 230 volt on moulded ceramic base. Operated by pointer knob (not supplied). 2/- each, 18/- per doz.

1/40th h.p. Motor. Made by the French (Casoro) Company. This is an excellent totally enclosed motor, powerful enough to operate small lath, drilling machine, washing machine, etc. Its speed is 1,450 r.p.m. Made for normal 50 cycle, 230/250 volts mains, totally enclosed, size 2 1/2 x 3 1/2in. dia. with 1in. of 1/4in. spindle. Price 19/6 plus 4/6 postage and insurance.

Burglar Alarm Kit. Protect your home and family by frightening away the intruder. With our circuit a mains operated bell rings loudly directly the door or window is opened. Kit comprises 12 reed switches, 12 magnets, relay, mains transformer and bell with circuit. Price 49/6.

THERMOSTATS

Type "A" 15 amp, for controlling room heaters, greenhouses, airing cupboard. Has spindle for pointer knobs. Quickly adjustable from 30-80°F. 9/6 plus 1/- post. Suitable box for wall mounting. 5/- Post and packing 1/-.

Type "B" 15 amp. This is a 17in. long rod type made by the famous Bunnik Co. Spindle adjusts this from 50-550°F. Internal screw alters the setting, so this could be adjustable over 30° to 1000°F. Suitable for controlling E.H.T. (tube), oven, kiln, immersion heater or to make flame-stat or fire alarm. 8/6 plus 2/6 post and insurance.

Type "D". We call this the Ice-stat as it cuts in and out at around freezing point. 2/3 each. Has many uses one of which would be to keep the loft pipes from freezing. If a length of our blanket wire (16yd. 10/-) is wound round the pipes. 7/6 Post and packing 1/-.

Type "E". This is standard refrigerator thermostat. Spindle adjustments cover normal refrigerator temperature. 7/6, plus 1/- post.

Type "P". Glass encased for controlling the temp. of liquid—particularly those in glass tanks, vats or sinks—thermostat. E head (half submerged) by rubber sucker or wire clip—ideal for fish tanks—developpers and chemical baths of all types. Adjustable over range 50° to 150°F. Price 18/-, plus 2/- post and insurance.

ELECTRONICS (CROYDON) LTD Dept. WW, 266 London Road, Croydon CRO-2TH Also 102/3 Tamworth Road, Croydon

### 4-STATION INTERCOM



Our Price Only  
**£7/15/0**

Solve your communication problems with this new 4-Station Transistor Intercom system (1 master and 3 subs), in de luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Operates on one 9 v. battery. On/off switch. Volume control. Ideally suitable to modernise Office, Factory, Workshop, Warehouse, Hospital, Shop, etc., for instant inter-departmental contacts. Complete with 3 connecting wires, each 66ft. and other accessories. Nothing else to buy. P. & P. 7/6 in U.K.

### INTERCOM/BABY ALARM



OUR PRICE ONLY  
**3 gns.**

Same as 4-Station Intercom for two-way instant conversation from MASTER to SUB and SUB to MASTER. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 2/6. P. & P. 4/6.

### 7-STATION INTERCOM

(1 MASTER & 6 SUB-STATIONS) in strong metal cabinets. Fully transistorised. 3 1/2 in. Speakers. Call on Master identified by tone and Pilot lamp. Ideally suitable for Office, Hotel, Hospital and Factory. Price 27 gns. P. & P. 14/6 in U.K.

### Transistor TELEPHONE AMPLIFIER



**59/6**

Why not increase efficiency of Office, Shop and Warehouse with this incredible De-Luxe Portable Transistor TELEPHONE AMPLIFIER which enables you to take down long telephone messages or converse without holding the handset. A useful office aid. A must for every telephone user. Useful for hard of hearing persons. On/off switch. Volume Control. Operates on one 9 v. battery which lasts for months. Ready to operate. P. & P. 3/6 in U.K. Add 2/6 for Battery.

Full price refunded if returned in 7 days.

WEST LONDON DIRECT SUPPLIES (W.W.),  
169 Kensington High Street, London, W.8

# NEW PRICES ON NEW COMPONENTS

#### RESISTORS

High stability, carbon film, low noise. Capless construction, molecular termination bonding.

Dimensions (mm.): Body: 1/2W: 8 x 2.8  
1W: 10 x 4.3

Leads: 35

10% ranges; 10 Ohms to 10 Megohms (E12 Renard Series).

5% ranges; 4.7 Ohms to 1 Megohm (E24 Renard Series).

Prices—per Ohmic value.

	each	10 off	25 off	100 off
1/2W 10%	2d.	1/6	3/3	10/4
1W 5%	2 1/2d.	1/9	3/8	11/8
1W 10%	2 1/2d.	1/9	3/8	11/7
1W 5%	3d.	2/-	4/-	12/10

#### CAPACITORS

Subminiature Polyester film, Modular for P.C. mounting. Hard epoxy resin encapsulation. Radial leads.

±10% tolerance. 100 Volt working.

Prices—per Capacitance value (µF)

	each	10 off	25 off	100 off
0.001, 0.002, 0.005, 0.01, 0.02 ..	6d.	4/3	8/4	30/-
0.05 .. .. .	8d.	6/-	12/6	41/8
0.1 .. .. .	10d.	7/1	15/6	51/-
0.2 .. .. .	1/2	10/-	20/10	68/6

Polystyrene film, Tubular, Axial leads. Unencapsulated ±5% or ±1pf tolerance, 160 Volt Working.

Prices—per Capacitance value (µF)

	each	10 off	25 off	100 off
10, 12, 15, 18, 22, 27, 33, 39, 47, each		10 off	25 off	100 off
56, 68, 82, 100, 120, 180, 220,				
270, 330, 390 .. .. .	5d.	3/7	7/9	24/-
470, 560, 680, 820, 1,000, 1,500	6d.	4/-	8/8	26/8
2,200, 3,300, 4,700, 5,600 .. .. .	7d.	5/-	10/10	33/4
6,800, 8,200, 10,000, 15,000 .. .. .	8d.	6/-	13/-	40/-
22,000 .. .. .	9d.	6/9	18/-	45/4

#### POTENTIOMETERS (Carbon)

Superior grade enclosed controls. Low rotational noise. Body dia., 1in. Spindle, 2in. x 1/4in. Tolerance, 20%.

Linear: 1K to 2M. (1W at 40°C).

Logarithmic: 5K to 2M. (1W at 40°C).

Prices per ohmic value	each	10 off	25 off	100 off
	2/-	18/4	41/8	150/-

#### GANGED STEREO POTENTIOMETERS (Carbon)

1W at 70°C. Long Spindle.

Logarithmic and Linear: 5k + 5k to 1M + 1M.

Prices per ohmic value	each	10 off	25 off	100 off
	8/-	70/-	162/6	575/-

#### SKELETON PRE-SET POTENTIOMETERS (Carbon)

High quality pre-sets suitable for printed circuit boards of 0.1in. P.C.M. 100 ohms to 5 Megohms (Linear only). Miniature: 0.3W at 70°C. ±20% below 1M, ±30% above 1M.

Horizontal (0.7in x 0.4in. P.C.M.) or Vertical (0.4in. x 0.2in. P.C.M.). Subminiature:

0.1W at 70°C. ±20% below 2.5M. ±30% above.

Prices—per ohmic value	each	10 off	25 off	100 off
Miniature (0.3W) .. .. .	1/-	8/9	18/9	66/8
Subminiature (0.1W) .. .. .	10d.	7/1	14/7	46/8

#### ELECTROLYTIC CAPACITORS (Mullard.) —10% to +50%.

Subminiature (all values in µF)	each	10 off	25 off	100 off
4V .. .. .	8	32	64	125
6.4V .. .. .	6.4	25	50	100
10V .. .. .	4	16	32	64
16V .. .. .	2.5	10	20	40
25V .. .. .	1.6	6.4	12.5	25
40V .. .. .	1	4	8	16
64V .. .. .	0.64	2.5	5	10
Price .. .. .	1/4	1/3	1/2	1/-

Small (all values in µF)	each	10 off	25 off	100 off
4V .. .. .	800	1,250	2,000	3,200
6.4V .. .. .	640	1,000	1,600	2,500
10V .. .. .	400	640	1,000	1,600
16V .. .. .	250	400	640	1,000
25V .. .. .	160	250	400	640
40V .. .. .	100	160	250	400
64V .. .. .	64	100	160	250
Price .. .. .	1/6	2/-	2/6	3/-

#### POLYESTER CAPACITORS (Mullard)

Tubular 10%, 160V: 0.01, 0.015, 0.022 µF, 7d. 0.033, 0.047 µF, 8d. 0.068, 0.1 µF, 9d. 0.15 µF, 11d. 0.22 µF, 1/- 0.33 µF, 1/3. 0.47 µF, 1/6. 0.68 µF, 2/3. 1 µF, 2/8.

400V: 1,000, 1,500, 2,200, 3,300, 4,700 µF, 6d. 6,800 µF, 0.01, 0.015, 0.022 µF, 7d. 0.033 µF, 8d. 0.047 µF, 9d. 0.068, 0.1 µF, 11d. 0.15 µF, 1/2. 0.22 µF, 1/6. 0.33 µF, 2/3. 0.47 µF, 2/8.

SEMICONDUCTORS: OA5, OA81, 1/9. OC44, OC45, OC71, OC81, OC81D, OC82D, 2/-, OC70, OC72, 2/3. AC107, OC75, OC170, OC171, 2/6. AF115, AF116, AF117, ACY19, ACY21, 3/3. OC140, 4/3. OC200, 5/-, OC139, 5/3. OC25, 7/-, OC35, 8/-, OC23, OC28, 8/3.

SILICON RECTIFIERS (0.5A): 170 P.I.V., 2/9. 400 P.I.V., 3/-, 800 P.I.V., 3/3. 1,250 P.I.V., 3/9. 1,500 P.I.V., 4/-, (6A): 200 P.I.V., 3/-, 400 P.I.V., 4/-, 600 P.I.V., 5/-, 800 P.I.V., 6/-.

PRINTED CIRCUIT BOARD (Vero).

0.15in. Matrix: 3 1/2in. x 2 1/2in., 3/3. 5 1/2in. x 2 1/2in., 3/11. 3 1/2in. x 3 1/2in., 3/11. 5in. x 3 1/2in., 5/6.

0.1 Matrix: 3 1/2in. x 2 1/2in., 4/-, 5in. x 2 1/2in., 4/6. 3 1/2in. x 3 1/2in., 4/6. 5in. x 3 1/2in., 5/3.

SEND S.A.E. FOR 1969 CATALOGUE

## DUXFORD ELECTRONICS

97/97A MILL ROAD, CAMBRIDGE

Telephone: CAMBRIDGE (0223) 63687

(Visit us at our new Mail Order, Wholesale and Retail Premises)

MINIMUM ORDER VALUE 5/- C.W.O. Post and Packing 1/6

# HIRE

## ELECTRONIC TEST GEAR

— calibrated and ready to plug in

# Livingston Hire

## 01-267 0414

# OPTOELECTRONICS from PROOPS

New Science Projects combine fascination of Optics with Electronics.

## INFRA-RED TRANSMITTERS & RECEIVERS

### INFRA-RED PHOTO RECEIVER — MSP3

Ultra sensitive detector/amplifier for infra-red (Gallium Arsenide) or visible light optical links reception. Spectral response 9500 A. Robust, cylindrical package is coaxial with incident light to facilitate optical alignment and heat sinking.

85/- post free



**MAX RATINGS**

Total dissipation (in free air,  $T_{amb} = 25^{\circ}C$ ).....100mW. Derating Factor.....2mW/ $^{\circ}C$ .  
Output Current Intensity.....100mA. Voltage.....25V. Operating Temperature.....from  $-30^{\circ}$  to  $+125^{\circ}C$ .

Supplied complete with suitable lenses, full Technical Data and Application Sheets, including Line of Sight Speech Link.

Unique devices in a brand new electronic field that can be exploited in a wide range of applications. Miniaturized construction and solid state circuit design is combined with outstanding modulation and switching capabilities to provide infinite possibilities as short distance speech and data links, remote relay controls, safety devices, burglar alarms, batch counters, level detectors, etc., etc.

### GALLIUM ARSENIDE LIGHT SOURCE—MGA 100

Filamentless, infra-red emitter in a robust, sealed cylinder coaxial with beam to facilitate optical alignment and heat sinking.



35/- post free

**MAX RATINGS**


Forward current  $I_f$  max.\* D.C.....400mA. Forward peak current  $I_f$  max.\* (pk).....6A  
Power dissipation\*.....600mW. Derating factor for  $T_{amb}$  greater than  $25^{\circ}C$ .....7.5mW/ $^{\circ}C$ .  
Reverse voltage  $V_R$  max.....1.0V.

\*When mounted on an aluminium heat sink 1 in. x  $\frac{1}{2}$  in. x  $\frac{1}{2}$  in.  
Supplied complete with suitable lenses, full Technical Data and Application Sheets, including Line of Sight Speech Link.

## PHOTOCONDUCTIVE CELLS

### CADMIUM SULPHIDE CELLS (Cds)

Inexpensive light sensitive resistors which require only simple circuitry to work as light triggering units in a wide range of devices, such as: flashing or breakdown lights, exposure meters, brightness controls, automatic porch lights, etc. Not polarity conscious — use with A.C. or D.C. Spectral response covers whole visible light range.

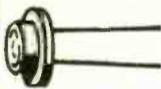

**MKY101-C**

Epoxy sealed.  $\frac{1}{8}$  in. diam. x  $\frac{1}{4}$  in. thick. Resistance at 100 Lux — 500 to 2,000 ohms. Maximum voltage 150 A.C. or D.C. Maximum current 150 mW. **10/6 post free**



**MKY71**


Glass sealed with M.E.S. base. Glass envelope  $\frac{1}{8}$  in. diam., overall length 1 in. Resistance at 100 Lux — 50 Kohms to 150 Kohms. Maximum voltage 150 A.C. or D.C. Maximum current 75 mW. **8/6 post free**

## PHOTOGENERATIVE CELLS

Selenium cells in which light energy is converted into electricity directly measurable on microammeter or used with amplifier as light trigger for alarm and counting devices, luminous fluxmeters, exposure meters, colorimeters, etc.. Spectral response covers visible light range.

Type 1— $1\frac{1}{2}$  x  $1\frac{1}{8}$  in. Output 1 mA at 0.6 volts at 1,000 Lux **5/- post free**

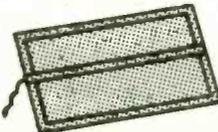Type 3—100 x 50 mm. Output 4 mA at 0.6 volt at 1,000 Lux **22/6 post free**




## REED SWITCH COILS & CAPSULES



R/C6



R/C4

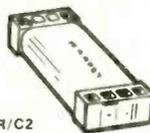

R/C2

Compact assemblies of reed switches and operating coils that permit the design of an infinite variety of multiple switch circuits in an extremely small space. They eliminate the bulk and open contact disadvantage of electro-mechanical relays; hermetically sealed contact isolation ensures long life reliability. Small enough to combine with solid-state components on printed circuit boards. Ideal for switching matrices, binary kits, control systems, etc. These were removed intact from highly expensive computer mechanisms and are guaranteed to be in perfect working order. Each capsule consists of a rare-metal screened, 24 volt DC operating coil on a nylon former with one detachable end for the removal and replacement of reed switches.

**Types available:**

R/C2 Two reed switches, contacts normally open. Size overall:  $1\frac{1}{2}$  x  $\frac{1}{2}$  x  $\frac{1}{2}$  in. **5/- post free**


R/C4 Four reed switches, contacts normally open. Size overall:  $1\frac{1}{2}$  x  $\frac{1}{2}$  x  $\frac{1}{2}$  in. **10/- post free**

R/C6 Six reed switches, 4 contacts normally open, 2 normally closed. Size overall:  $1\frac{1}{2}$  x  $1\frac{1}{2}$  x  $\frac{1}{2}$  in. **15/- post free**

# PROOPS
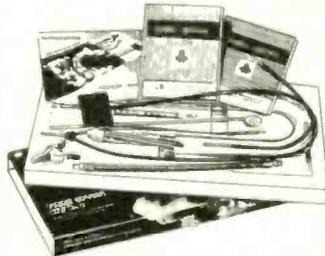
## FIBRE OPTICS

Highly flexible light guides that transmit light to inaccessible places as easily as electricity is conducted by copper wires. Fibre optics make it possible to control, miniaturize, split, reflect or transfer light from one source to many places at once and to operate photo devices, logic circuits, or illuminate in ways never before possible. Proops offer both glass fibre optics or inexpensive Crofon plastic fibres for hundreds of experiments or serious applications in a fascinating new science.



### RANK TAYLOR-HOBSON ENGINEERS KITS

Basic fibre optic components that demonstrate new ways of employing light in serious applications. Two kits are available: each contains high-grade glass-fibre light guides consisting of thousands of fibres tightly bundled in flexible sheaths with ferruled, optically polished ends, together with connecting and light source components. Each is supplied complete with card wallets containing technical and application data.

**KIT 2 £28 Post Free**

Contains: 3 mm. x 18 in., 6 mm. x 12 in. light guides; 1.5 mm. 'Y' guide with two 12 in. long tails; 24 in. long 12 exit component for coding or punched card applications, 24 in. lengths of Crofon 64 filament and monofilament plastic light guide. Also, coherent solids consisting of 25 mm. diam. field flattening lens, 6 mm. x 12 in. image conduit with polished ends, 4 mm x 25 mm. image inverter. Complete with 2-way adaptor, fibre optic torch and batteries, 3 mm./3 mm. and 3 mm./1.5 mm. connectors.

**KIT 1 £16 Post free**

Contains: 1.5 mm. x 24 in., 3 mm. x 18 in., and 6 mm. x 12 in. light guides, plus 24 in. long x 2 exit component for punched card or coding applications. Also battery operated light source, 2-way 'Y' adaptor with non-random separation, and 3 mm./3 mm. and 3 mm./1.5 mm. connectors.

● **Special offer of IMAGE FIBRESCOPIES £5 Post Free** ●

Between 50,000 and 60,000 coherently arranged, 15 micron glass fibres that provide (with appropriate optics) perfect visual inspection into otherwise inaccessible areas. Originally made by Rank Taylor-Hobson for use in industrial and medical fibrescopes at £72 each, these have slight, superficially imperceptible faults and are assembled in transparent, lay-flat tubing instead of opaque, flexible conduit, as usual. Ends are ground, polished and metal capped. Absolutely ideal for demonstration in Schools and Technical Colleges and for many other applications that require highly sophisticated means of access to enclosed, difficult to get at places. Length overall: 3 ft. Cross sectional area: 3 x 3 mm. Resolution: 10 LP/mm. to 20 LP/mm.

### LOW COST CROFON FLEXIBLE LIGHT GUIDES

Newly developed plastic light transmitting media by Dupont, which can be used for both serious projects and inexpensive prototype work. Ends can be ground flat, dyed or capped with epoxy resin. Temperature range:  $-40^{\circ}$  to  $+170^{\circ}F$ . No loss of light through bending. 12 page Data and Applications booklet supplied free with each order. Types available:

**Multi-strand**— 64 special plastic fibres, tightly bundled together in a tough, flexible conduit, 8/6 per foot. Minimum order two feet, 17/- p & p 1/6.

**Monofilament**— single 0.040" plastic fibre which is specially useful for light indication in confined spaces. 4/- per foot. Minimum order three feet, 12/- p & p 1/-.



### RCA TRIAC — CA40432 45/- post free

Suitable for light dimming and motor control circuits. Gate-controlled, full-wave, A.C. silicon switch with integral trigger that blocks or conducts instantly by applying reverse polarity voltage. Suitable for A.C. operation up to 250 volts, controls currents up to 1440 watts. Size only  $\frac{1}{2}$  in. diam. x  $\frac{1}{8}$  in. high. Complete with heat sink, data and applications information.



Proops Bros. Ltd., 52 Tottenham Court Road, London W1P 0BA  
Telephone: 01-580 0141

**KING OF THE PAKS** Unequalled Value and Quality  
**SUPER PAKS** NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U1	120 Glass Sub-min. General Purpose Germanium Diodes	10/-
U2	60 Mixed Germanium Transistors AF/RF	10/-
U3	75 Germanium Gold Bonded Diodes slm. OA5, OA47	10/-
U4	40 Germanium Transistors like OC81, AC128	10/-
U5	60 200mA Sub-min. Sil. Diodes	10/-
U6	40 Silicon Planar Transistors NPN slm. BSY95A, 2N706	10/-
U7	16 Silicon Rectifiers Top-Hat 750mA up to 1,000V	10/-
U8	50 Sil. Planar Diodes 250mA OA/200/202	10/-
U9	30 Mixed Volta 1 watt Zener Diodes	10/-
U11	30 PNP Silicon Planar Transistors TO-5 slm. 2N1192	10/-
U12	12 Silicon Rectifiers EPOXY BY126/127	10/-
U13	30 PNP-NPN Sil. Transistors OC200 & 28104	10/-
U14	150 Mixed Silicon and Germanium Diodes	10/-
U15	30 NPN Silicon Planar Transistors TO-5 slm. 2N867	10/-
U16	10 3-Amp Silicon Rectifiers Stud Type up to 1000 PIV	10/-
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	10/-
U18	8 6-Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	10/-
U19	30 Silicon NPN Transistors like BC108	10/-
U20	12 1.3-amp Silicon Rectifiers Top-Hat up to 1,000 PIV	10/-
U21	30 A.F. Germanium alloy Transistors 2G300 Series & OC71	10/-
U22	10 1-amp Glass Min. Silicon Rectifiers High Volta.	10/-
U23	30 Madu's like MAT Series PNP Transistors	10/-
U24	20 Germanium 1-amp Rectifiers GJM up to 300 PIV	10/-
U25	25 300Mc/s NPN Silicon Transistors 2N708, BSY27	10/-
U26	30 Fast Switching Silicon Diodes like IN914 Micro-min.	10/-
U28	Experimenters' Assortment of Integrated Circuits, untested Gates, Flip-Flops, Registers, etc. 8 Assorted Pieces	20/-
U29	10 1 amp SCR's TO-5 can up to 600 PIV ORR1/25-600	20/-
U30	15 Plastic Silicon Planar trans. NPN 2N2924-2N2926	10/-
U31	20 Sil. Planar NPN trans. low noise Amp 2N3707	10/-
U32	25 Zener diodes 400mW D07 case mixed Volta. 3-18	10/-
U33	15 Plastic case 1 amp Silicon rectifiers 1N4000 series	10/-
U34	30 Sil. PNP alloy trans. TO-5 BCY26, 28302/4	10/-
U35	25 Sil. Planar trans. PNP TO-18 2N2906	10/-
U36	25 Sil. Planar NPN trans. TO-5 BFY50/51/52	10/-
U37	30 Sil. alloy trans. 80-2 PNF, OC200 28322	10/-
U38	20 Fast Switching Sil. trans. NPN, 400Mc/s 2N3011	10/-
U39	30 RF Germ. PNP trans. 2N1303/5 TO-5	10/-
U40	10 Dual trans. 6 lead TO-5 2N2060	10/-
U41	30 RF Germ. trans. TO-1 OC45 NKT72	10/-
U42	10 VHF Germ. PNP trans. TO-1 NKT667 AF117	10/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

**BI-PAK SEMICONDUCTORS**  
 (DEPT. WW)

**TESTED SCR'S**

PIV 1 A	7A	16A	30A
25	7/8	7/8	30/-
50	7/8	7/8	30/-
100	8/8	15/-	45/-
200	12/8	20/-	55/-
300	15/-	25/-	-
400	17/8	25/-	80/-
500	30/-	40/-	95/-
600	-	40/-	50/-

**SIL. RECTS TESTED**

PIV 750mA 3A	10A	30A
50	1/-	2/3
100	1/3	3/3
200	1/9	4/-
300	2/3	4/8
400	2/8	5/8
500	3/3	6/-
600	3/3	6/9
800	3/6	7/8
1000	5/-	9/3
1200	6/6	11/6

**FULL RANGE OF ZENER DIODES**  
 VOLTAGE RANGE 2-16V.  
 400mV (DO-7 case) 3/8 ea.  
 1.5W (Top-Hat) 3/8 ea.  
 10W (80-10 Stud) 5/- ea.  
 All fully tested 5% tol. and marked. State voltage required.

**BRAND NEW TEXAS GERM. TRANSISTORS**

Code and Guaranteed	Pak No.	EQVT
T1	8	2G371A OC71
T2	8	2G374A OC75
T3	8	2G374A OC81D
T4	8	2G381A OC81
T5	8	2G392T OC82
T6	8	2G344A OC44
T7	8	2G345A OC45
T8	8	2G378 OC78
T9	8	2G398A 2N1302
T10	8	2G417 AF117

All 10/- each PAK  
 2N2060 NPN SIL. DUAL TRANS. CODE D1699 TEXAS. Our price 5/-

120 VCB NIXIE DRIVER TRANSISTOR. 8im. BSX21 & 207. 2N1893 FULLY TESTED AND CODED ND120. 1-24 3/8 each. TO-5 N.P.N. 25 up 3/- ea.

**OTHER MONOLITHIC DEVICES**

BP424, Zero voltage switch, 8/6 each.  
 This device is a monolithic I.C. that acts a combined threshold detector and trigger circuit for controlling a triac. It is designed to pulse the gate of a thyristor at the point of zero supply voltage, and therefore eliminate radio frequency interference when used with resistive loads.  
 D13D1 Silicon Unilateral switch 10/- each.  
 A Silicon Planar, monolithic integrated circuit having thyristor electrical characteristics, but with an anode gate and a built-in "Zener" diode between gate and cathode. Full data and application circuits available on request.

**CA3020 RCA (U.S.A.) LINEAR INTEGRATED CIRCUITS**

Audio Power Amplifier, 30/- each.

**FREE**  
 One 10/- Pak of your own choice free with orders valued £4 or over.

**PLEASE NOTE.** To avoid any further increased Postal Charges to our Customers and enable us to keep our "By Return Postal Service" which is second to none, we have re-organized and streamlined our Despatch Order Department and we now request you to send all your orders together with your remittance, direct to our Warehouse and Despatch Department, postal address: BI-PAK SEMICONDUCTORS, Despatch Dept., P.O. Box 6, WARE, HERTS. Postage and packing still 1/- per order. Minimum order 10/-.

**INTEGRATED CIRCUIT AMPLIFIER AS USED IN 'P.E.' PROJECTS**

Identical encapsulation and pin configuration to the following: 8L402-3, IC10 and IC403. Each circuit incorporates a pre-amp and class A.B. Power amp stage capable of delivering up to 3 watts RMS. Fully tested and guaranteed. Supplied complete with circuit details and data.

**BI-PAK MONOLITHIC AMPLIFIERS (TO-5 8 lead)**

BP709C, Operational amplifier, 15/- each.  
 BP701C, Operational amplifier (with Zener output), 12/6 each.  
 BP702C, Operational amplifier (with direct output), 12/6 each.  
 BP501, Wide band amplifier, 15/- each.  
 BP501, Logarithmic wide band amp., 14/- each.  
 BP210C, General purpose amplifier (TO-5 8 lead), (voltage or current amp.), 12/6 each.  
**FAIRCHILD (U.S.A.) TTL MICROLOGIC**  
**INTEGRATED CIRCUITS**  
 Epoxy case T8-5 lead temp. range 15°C to 55°C.  
 UL914, Dual two-input gate, 10/6 each.  
 UL923 J-K-Flip-Flop, 14/- each.  
 Complete data and circuits for the Fairchild I.C.'s available in booklet form priced 1/6.

**MULLARD I.C. AMPLIFIERS**

TAA243, Operational amplifier, 70/- each.  
 TAA263, Linear AF amplifier, 18/6 each.  
 TAA293, General purpose amplifier, 21/- each.

**QUALITY-TESTED PAKS**

6 Matched Trans. OC44/45/81/81D	10/-
20 Red Spot AF Trans. PNP	10/-
16 White Spot RF Trans. PNP	10/-
5 Silicon Rects. 3 A 100-400 PIV	10/-
2 10 A Silicon Rects. 100 PIV	10/-
2 OC140 Trans. NPN Switching	10/-
1 12 A, 800 100 PIV	10/-
3 Sil. Trans. 28303 PNP	10/-
4 Zener Diodes 250mW 3-12V	10/-
3 200 Mc/s Sil. Trans. NPN BSY26/27	10/-
3 Zener Diodes 1W 33V 5% Tol.	10/-
4 High Current Trans. OC42 Eqvt.	10/-
2 Power Transistors 1 OC26 1 OC35	10/-
6 Silicon Rects. 400 PIV 250mA	10/-
4 OC75 Transistors	10/-
1 Power Trans. OC20 100V	10/-
10 OA202 Sil. Diodes Sub-min.	10/-
2 Low Noise Trans. NPN 2N929/30	10/-
1 Sil. Trans. NPN VCB 100 ZT86	10/-
6 OA81 Diodes	10/-
4 OC22 Transistors	10/-
4 OC77 Transistors	10/-
4 Sil. Rects. 400 PIV 500mA	10/-
5 GET884 Trans. Eqvt. OC44	10/-
5 GET883 Trans. Eqvt. OC45	10/-
2 2N708 Sil. Trans. 300 Mc/s. NPN	10/-
3 GT51 LF Low Noise Germ Trans. PNP	10/-
6 IN914 Sil. Diodes 75 PIV 75mA	10/-
8 OA95 Germ. Diodes Sub-min. IN69	10/-
3 NPN Germ. Trans. NKT773 Eqvt. AC130	10/-
2 OC22 Power Trans. Germ.	10/-
2 OC25 Power Trans. Germ.	10/-
4 AC128 Trans. PNP High Gain	10/-
7 OC62H Germ. Diodes Eqvt. PNP/NPN	10/-
3 2N1307 PNP Switching Trans.	10/-
7 OC62H Germ. Diodes Eqvt. OA71	10/-
3 AF116 Type Trans.	10/-
12 Assorted Germ. Diodes Marked (voltage or current amp.), 12/6 each.	10/-
4 AC126 Germ. PNP Trans.	10/-
3 Silicon Rects. 100 PIV 750mA	10/-
3 AF117 Trans.	10/-
7 OC81 Type Trans.	10/-
3 OC71 Trans.	10/-
5 2N2928 Sil. Epoxy Trans.	10/-
7 OC71 Type Trans.	10/-
2 28701 Sil. Trans. Texas	10/-
3 12 Volt Zeners 400mW	10/-
2 10 A 800 PIV Sil. Rects. IS45B	10/-
3 BC108 Sil. NPN High Gain Trans.	10/-
1 2N910 NPN Sil. Trans. VCB 100V	10/-
2 1000 PIV Sil. Rect. 1.5 A R53310 AF	10/-
3 BSY95A Sil. Trans. NPN 200 Mc/s.	10/-
3 OC200 Sil. Trans.	10/-
2 Sil. Power Rects. BYZ13	15/-
1 Sil. Power Trans. NPN 100mc/s. TK201A	15/-
6 Zener Diodes 3-15V Sub-min.	15/-
1 2N132 PNP Epitaxial Planar Sil.	15/-
3 2N897 Epitaxial Planar Trans. Sil.	15/-
4 Germ. Power Trans. Eqvt. OC16	15/-
1 Unijunction Trans. 2N2646	15/-
2 Sil. Trans. 200 Mc/s. 60Vcb ZT83/84	15/-
1 Tunnel Diode AEY11 1050 Mc/s.	15/-
2 2N2712 Sil. Epoxy Planar HFE225	15/-
8 BY 100 Type Sil. Rects.	20/-
25 Sil. and Germ. Trans. Mixed, all marked. New	30/-

**BI-PAK GUARANTEE SATISFACTION OR MONEY BACK**

**NO EXCUSES! NO DELAYS! FROM STOCK!**  
**VARIABLE VOLTAGE TRANSFORMERS**

**INPUT 230 v. A.C. 50/60 OUTPUT VARIABLE 0/260 v. A.C.**

**BRAND NEW.** Keenest prices in the country. All Types (and spares) from 1/2 to 50 amp. available from stock.

0-260 v. at 1 amp.	£5 10 0
0-260 v. at 2.5 amps.	£6 15 0
0-260 v. at 5 amps.	£9 15 0
0-260 v. at 8 amps.	£14 10 0
0-260 v. at 10 amps.	£18 10 0
0-260 v. at 12 amps.	£21 0 0
0-260 v. at 15 amps.	£25 0 0
0-260 v. at 20 amps.	£37 0 0
0-260 v. at 37.5 amps.	£72 0 0
0-260 v. at 50 amps.	£92 0 0

**20 DIFFERENT TYPES AVAILABLE FOR IMMEDIATE DELIVERY.**

**Double Wound Variable Transformers**

Fully isolated, low tension Secondary winding. Input 230 v. A.C. OUTPUT CONTINUOUSLY VARIABLE 0-36 v. A.C.

0-36 v. at 5 amp.	£9.12.6—
	p. & p. 8/6
0-36 v. at 20 amp.	£21.0.0—
	15/- p. & c.

These fully shrouded Transformers, designed to our specifications, are ideally suited for Educational, Industrial and Laboratory use.

**INSULATION TESTERS (NEW)**

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L. 8in. W. 4in. H. 6in. Weight 6lb.

**500 VOLTS, 500 megohms.**  
 Price £28 carriage paid.

**1,000 VOLTS, 1,000 megohms.**  
 £34 carriage paid.

**OPEN TYPES**  
 Designed for Panel Mounting.  
 Input 230 v. A.C. 50/60 Output variable.  
 0-260 v.  
 1/2 amp ..... £3 10 0  
 1 amp ..... £5 10 0  
 2 1/2 amp ..... £6 12 6  
 P. & P. 7/6  
 1 AMP. 1 AMP.

**VAN DE GRAAF ELECTROSTATIC GENERATOR**  
 fitted with motor drive for 230 v. A.C. giving a potential of approx. 50,000 volts. Supplied absolutely complete including accessories for carrying out a number of interesting experiments, and full instructions. This instrument is completely safe, and ideally suited for School demonstrations. Price £77/-, plus 4/- P. & P. Lt. on req.

**CONSTANT VOLTAGE TRANSFORMER**

Input 185-250 v. A.C. Output constant at 230 v. A.C. Capacity 250 watt. Attractive metal case. Fitted red signal lamp. Rubber feet. Weight 17lbs. Price £11/10/-, P. & P. 10/-.

**LATEST TYPE SOLID STATE VARIABLE LIGHTING CONTROLLER**

Ideal for lighting and heating circuits, compact panel mounting. Built in fuse protection. CONTINUOUSLY VARIABLE.  
 Input 230v AC output 25-230v AC  
 5 amp model £8. 7. 6  
 10 amp model £13. 5. 0

**SPEEDIVAC HIGH VOLTAGE HIGH FREQUENCY GENERATOR**

Input 100/110 volts or 200/250 volts AC/DC Output 19KV variable. Ideal for testing insulation, vacuum, leakage path, gas discharge lamps, neon etc. A useful ozone and HF supply. Manufactured by Edwards High Vacuum Ltd. Brand new in maker's polished wooden carrying case. Offered at fraction of maker's price. £10.0.0 plus 7/6 p. & p.

**36 volt 30 amp. A.C. or D.C. Variable L.T. Supply Unit**

INPUT 220/240 v. A.C. OUTPUT CONTINUOUSLY VARIABLE 0-36 v.

Fully isolated. Fitted in robust metal case with Voltmeter, Ammeter, Panel Indicator and chrome handles. Input and Output fully fused. Ideally suited for Lab. or Industrial use. £55 plus 40/- p. & c.

**SERVICE TRADING COMPANY**

# SERVICE TRADING CO

Postage and Carriage shown below are inland only. For Overseas please ask for quotation. We do not issue a catalogue or list.

## LIGHT SENSITIVE SWITCHES

Kit of parts including ORP.12 Cadmium Sulphide PhotoCell. Relay Transistor and Circuit. Now supplied with new Siemens High Speed Relay for 6 or 12 volt operations. Price 25/-, plus 2/6 P. & P. ORP. 12 and Circuit 10/6 post paid.



**220/240 A.C. MAINS MODEL**  
incorporates mains transformer rectifier and special relay with 2 x 5 amp. mains c/o contacts. Price inc. circuit 47/6, plus 2/6 P. & P.

## LIGHT SOURCE AND PHOTO CELL MOUNTING

Precision engineered light source with adjustable lens assembly and ventilated lamp housing to take MBC bulb. Separate photo cell mounting assembly for ORP.12 or similar cell with optic window. Both units are single hole fixing. Price per pair £2/15/0 plus 3/6 P. & P.



## PRECISION INTERVAL TIMER

From 0-30 seconds (repetitive). Jewelled balanced movement. Lever reset. Operates 230 v. A.C. 5 amp. c/o micro-switch. Ex. equipment; tested. 17/6, plus 2/6 P. & P.



## A.C. CONTACTOR

2 make and 2 break (or 2 c/o) 15 amp. contacts. 230/240 v. A.C. operation. Brand new. 22/6 plus 1/- P. & P.



## SEMI-AUTOMATIC "BUG" SUPER SPEED MORSE KEY

7 adjustments, precision tooled, speed adjustable 10 w.p.m. to as high as desired. Weight 2½lb. £4/12/6 post paid.



## DRY REED SWITCHES

2 x lamp Dry Reeds (makes contacts) mounted in 870 ohm 9-18v coil. Size 3¼in. x 3¼in. x ¼in. New. Price 8/6 per pair. Post Paid.  
6 of the above mentioned units (12 Reeds, 6 coils) fitted in metal box. Size 4in. x 3¼in. x 1¼in. Mfg. by Elliott Bros. New 45/- each. Post Paid.

## Telephone Dials (New) 14'6d. Post Paid.

## 34R SILICON SOLAR CELL

4 x 5 volt unit series connected, output up to 2 v. at 20 mA. in sunlight, 30 times the efficiency of selenium. As used in power Earth Satellites, 45/- P. & P. 1/6d.

**AUTO TRANSFORMERS.** Step up, step down. 110-200-220-240 v. Fully shrouded. New. 300 watt type £3/10/- each, P. & P. 4/6. 500 watt type £4/12/6 each, P. & P. 6/6. 1,000 watt type £5/15/- each, P. & P. 7/6.


## RING TRANSFORMER

Functional Versatile Educational  
This multi-purpose Auto Transformer, with large centre aperture, can be used as a Double wound current Transformer, Auto Transformer, H.T. or L.T. Transformer, by simply hand winding the required number of turns through the centre opening. E.g. Using the RT.100 V.A. Model the output could be wound to give 8V. @ 12½a., 4V. @ 25a., 2V. @ 50a., etc.  
Price: RT.100VA 3.18 turns per volt, £2 5 0+3/6 p. and p.  
RT.300VA 2.27 turns per volt, £4 4 0+5/6 p. and p.  
RT.1KVVA 1.82 turns per volt, £6 10 0+6/6 p. and p.


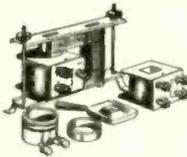
## DEMONSTRATION TRANSFORMER (STENZYL TYPE)

Two removable coils are tapped at 0, 110, 220 volts, and 6, 12, 36 volts respectively. A composite apparatus designed for class demonstration. Electro magnetic induction, jumping ring, induction lamp, relationship between field intensity and ampere turns, induction melting, are just a few of the possible experiments. New modified model. £14/10/- P. & P. 10/-.



## L.T. TRANSFORMERS

Type No.	Sec. Taps	Price	Carr.
1	30, 32, 34, 36 v. at 5 amps.	£4 5 0	6/-
2	30, 40, 50 v. at 5 amps.	£6 5 0	6/6
3	10, 17, 18 v. at 10 amps.	£4 10 0	4/6
4	6, 12 v. at 20 amps.	£5 17 6	6/6
5	17, 18, 20 v. at 20 amps.	£6 12 6	6/6
6	6, 12, 20 v. at 20 amps.	£7 5 0	7/6
7	24 v. at 10 amps.	£4 15 0	5/6
8	4, 6, 24, 32 v. at 12 amps.	£6 10 0	6/6

**CONDENSERS**  
New at a fraction of maker's price.  
2,500 mfd. 100 v. ... 12/6  
10,000 mfd. 35 v. ... 15/-  
4,000 mfd. 25 v. ... 10/-  
4,000 mfd. 50 v. ... 15/-

## LARGE DIGIT 12-18 v. D.C. MAGNETIC COUNTER

4in. drum, calibrated 0-9. Figures 1¼in. high ¼in. wide. Set of 1m, 1b, 1c/o contacts operated by drum cam. The units which can be used in multiples are ideally suited for batch or lap recording or for the many purposes where large easily read numerals are required. Price 18/6, P. & P. 2/6.



## VEEDER ROOT COUNTER

230 v. A.C. 50 cycle 5 figure counter (non resetable). 18/6, P. & P. 1/6.



## POWER RHEOSTATS


(NEW) Ceramic construction, winding embedded in Vitreous Enamel, heavy duty brush assembly designed for continuous duty. AVAILABLE FROM STOCK IN THE FOLLOWING II VALUES:  
100 WATT 1 ohm 10a., 5 ohm 4.7a., 10 ohm 3a., 25 ohm 2a., 50 ohm 1.4a., 100 ohm 1a., 250 ohm .7a., 500 ohm .45a., 1k ohm 280mA., 1.5k ohm 230mA., 2.5k ohm 2a., 5k ohm 140mA., Diameter 3¼in. Shaft length ¼in. dia. ¼in., 27/6, P. & P. 1/6.  
50 WATT 1/5/10/25/50/100/250/500/1K/1.5K/2.5K/5K ohm. All at 21/-, P. & P. 1/6.  
25 WATT 10/25/50/100/250/500/1K/1.5K/2.5K ohm. All at 14/6, P. & P. 1/6.  
Black Silver Skirted knob calibrated in Nos. 1-9. 1¼ in. dia. brass bush. Ideal for above Rheostats, 3/6 each.

## STROBE! STROBE! STROBE!

★ THREE EASY TO BUILD KITS USING XENON WHITE LIGHT FLASH TUBES. SOLID STATE TIMING + TRIGGERING CIRCUITS. PROVISION FOR EXTERNAL TRIGGERING. 230-250v. A.C. OPERATION.  
★ The Strobe is one of the most useful and interesting instruments in the laboratory or workshop. It is invaluable for the study of movement and checking of speeds. Many uses can be found in the psychiatric and photographic fields, also in the entertainment business. It is used a great deal in the motor industry and is a real tool as well as an interesting scientific device.  
★ EXPERIMENTERS "ECONOMY" KIT  
1 to 36 Flash per sec. All electronic components including Veroboard S.C.R. Unijunction Xenon Tube + instructions £5.5.0 plus 5/- P. & P.  
★ NEW INDUSTRIAL KIT  
Ideally suitable for schools, laboratories etc. Roller tin printed circuit. New trigger coil, plastic thyristor 1.80 f.p.s. Price 9 gns. 7/6 P. & P.  
★ HY-LIGHT STROBE  
This strobe has been designed for use in large rooms, halls and the photographic field. It has 4 times the light output at 30 f.p.s. and utilizes a silica tube for longer life expectancy, printed circuit for easy assembly, also a special trigger coil and output capacitor. Light output approx 4 joules. Price £10.17.6 P. & P. 7/6.  
★ 7-INCH POLISHED REFLECTOR. Ideally suited for above Strobe Kits. Price 10/6 + 2/6 p. & p. or post paid with kits.
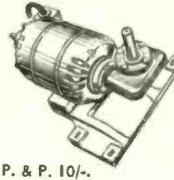
## PARVALUX TYPE SD19 230/250 VOLT AC REVERSIBLE GEARED MOTORS

30 r.p.m. 40 lb. ins. Position of drive spindle adjustable to 3 different angles. Mounted on substantial cast aluminium base. Ex-equipment. Tested and in first-class running order. A really powerful motor offered at a fraction of maker's price. 6 gns. P. & P. 10/-.



## BODINE TYPE N.C.1 GEARED MOTOR

(Type 1) 71 r.p.m. torque 10 lb. in. Reversible 1/70th h.p. 50 cycle 38amp.  
(Type 2) 28 r.p.m. torque 20 lb. in. reversible 1/80th h.p. 50 cycle 28 amp.  
The above two precision made U.S.A. motors are offered in 'as new' condition. Input voltage of motor 115v A.C. Supplied complete with transformer for 230/240v A.C. input  
Price, either type £2.17.6 plus 6/6 P. & P. or less transformer £2.2.6 plus 4/6 P. & P.  
These motors are ideal for rotating aerials, drawing curtains, display stands, vending machines etc. etc.



## 230 v. GEARED MOTOR

(as illustrated)  
6 R.P.M. or 10 R.P.M.  
230 v. A.C. non-reversible, approx. 1.7lb.in. Price 45/-, plus 3/6 P. & P.



## MINIATURE UNISELECTOR

3 banks of 11 positions, plus homing bank. 40 ohm coil. 24-36 v. D.C. operation. Carefully removed from equipment and tested. 22/6, plus 2/6 P. & P.

**UNISELECTOR SWITCHES NEW**  
**4 BANK 25 WAY FULL WIPER**  
25 ohm coil, 24 v. D.C. operation. £5.17.6, plus 2/6 P. & P.  
**6 BANK 25 WAY FULL WIPER**  
25 ohm coil, 24 v. D.C. operation. £6.10.0, plus 2/6 P. & P.  
**8-BANK 25-WAY FULL WIPER**  
24 v. D.C. operation, £7/12/6, plus 4/- P. & P.

## RELAYS

BULK PURCHASE ENABLES US TO OFFER THE FOLLOWING NEW SIEMENS PLESSEY, etc. MINIATURE RELAYS AT A HIGHLY COMPETITIVE PRICE

COIL	WORKING D.C. VOLT	CONTACTS	PRICE
170	9-12	4 c/o H.D.	14/6
170	9-12	3 c/o + 1 H.D. c/o	12/6
280	6-12	2 c/o incl. base	14/6
700	12-24	2 c/o incl. base	12/6
700	16-24	4 c/o incl. base	15/6
700	16-24	4M 2B incl. base	12/6
1250	20-40	2 c/o H.D. incl. base	12/6
9000	40-70	2 c/o incl. base	10/-

H.D. = Heavy Duty POST PAID

## MINIATURE RELAYS

9-12 volt D.C. operation. 2 c/o 500 M.A. contacts. Size only 1in. x 7/8 x 1/8 in. Price 11/6 Post paid.  
30-36 v. D.C. operation. 2 c/o 500 M.A. contacts. 3.200 ohm coil. Size only 1 x 7/8 x 1/8 in. 8/6 post paid.

## 230 VOLT AC RELAYS

230 volt AC Coil. Three c/o 5 amp. contacts, 17/6 Post Paid. (illustrated)  
LONDEX four c/o 3 amp. contacts. 18/6, incl. base. Post Paid.



A.C. AMMETERS 0-1, 0-5, 0-10, 0-15, 0-20 amp. F.R. 2¼in. dia. All at 21/- each.  
A.C. VOLTMETERS 0-25 v., 0-50 v., 0-150 v. M.I. 2¼in. Flush round all at 21/- each. P. & P. extra.  
0-300 v. A.C. Rect. M-Coil 2¼in. .... 29/-  
0-300 v. A.C. Rect. M-Coil 3¼in. Type W23 ..... 55/-

## SANWA MULTI RANGE TESTERS

NEW MODEL UD-50 MULTI TESTER, 20,000 O.P.V. MIRROR SCALED WITH OVERLOAD PROTECTION. Ranges: D.C. volts: 100mV., 0.5 v., 5 v., 250 v., 1,000 v. A.C. volts. 2.5 v., 10 v., 50 v., 250 v., 1,000 v. D.C. current: 5µA. 0.5 mA., 5 mA., 50 mA., 250 mA. Size: 5¼ x 3¼ x 1¼ in. Complete with batteries £7.5.0 and test prods. Post paid



## 'AVO' MODEL 48A

Ex-Admiralty in good condition with instructions, leads, plus D.C. Shunts for 120 Amp and 480 Amp. A.C. Transformer for 60 Amp and 240 Amp. Multiplier for 3600 volt. Complete outfit in fitted case. £15/0/0, P. & P. 10/-.



## SANGAMO WESTON

Ex W.D. Dual range voltmeter. 0-5 and 0-100 v. D.C. FSD 1 mA. In carrying case with test prods and leads. 32/6. P. & P. 3/6.



250 v. A.C. SOLENOID Heavy duty type. Approx. 3lb. pull. 17/6 plus 2/6 P. & P. 12 v. D.C. SOLENOID. Approx. 1lb. pull. 10/6, P. & P. 1/6.  
50 v. D.C. SOLENOID. Approx. 1lb. pull. 10/6, P. & P. 1/6.  
50 v. D.C. SOLENOID. Approx. 2lb. pull. 12/6, P. & P. 1/6.



## NEW MODEL HIGH FREQUENCY TRANSISTORISED MORSE OSCILLATOR

Adjustable tone control. Fitted with moving coil speaker, also earpiece for personal monitoring. Complete with morse key, 45/- plus 3/6d. p. & p.

## NICKEL CADMIUM BATTERY

1.2 v. 35 AH. Size 8½ high x 3 x 1½. 30/- each, plus 4/- P. & P.  
Sintered Cadmium Type 1.2 v. 7AH. Size: height 3½ in., width 2¼ in. x 1½ in. Weight: approx. 13 ozs. Ex-R.A.F. Tested 12/6. P. & P. 2/6.

R.C.A. plastic triac 400 PIV 8 amp. Price 8/6. R.C.A. Diac for above, price 6/-. Price includes data sheet and circuit. G.E. P.U.T. D13, T1, 12/-, Texas F.E.T. 2N3819, 7/6. New plastic Thyristor 400 PIV 8 amp. 18/6 incl. data sheet. All above prices plus 1/6 P. & P.

ALL MAIL ORDERS. ALSO CALLERS AT:  
57 BRIDGMAN ROAD,  
LONDON, W.4. Phone: 995 1560  
Closed Saturdays.

# SERVICE TRADING CO.

SHOWROOMS NOW OPEN  
AMPLE PARKING

PERSONAL CALLERS ONLY

9 LITTLE NEWPORT STREET,  
LONDON, W.C.2.  
Tel.: GER 0576

# L.S.T. ELECTRONIC COMPONENTS LTD.

AA119 2/-	BC137 8/6	BY25 31/9	NKT221 5/6	OC26 12/-	IN4001 2/-	2N2160 14/9
AA119 2/1	BC138 12/-	BY142 3/9	NKT222 4/-	OC28 12/-	IN4005 4/6	2N2218 12/-
AA212 17/6	BC142 15/-	BY210 9/-	NKT223 3/6	OC39 15/-	1N4007 5/6	2N2243 23/7
AC107 14/6	BC143 15/-	BY212 6/-	NKT224 4/6	OC35 9/6	2G302 3/9	2N2369 5/6
AC126 6/6	BC147 4/7	BY213 5/-	NKT225 3/6	OC36 13/-	2G339A 5/6	2N2369A 6/-
AC127 6/-	BC148 3/3	C106F1 9/-	NKT226 10/-	OC41 3/6	2G374 5/-	2N2432 58/4
AC127Z 8/6	BC149 8/-	C111 18/-	NKT227 5/6	OC42 4/-	2G371 5/-	2N2477 18/-
AC128 4/-	BC154 12/-	C111E 12/-	NKT228 6/-	OC43 4/-	2G371B 3/6	2N2484 14/-
AC151 8/8	BC158 7/6	C400 9/-	NKT229 6/-	OC44 4/-	2N301 8/-	2N2613 8/3
AC176 7/6	BCY12 7/6	C426 8/8	NKT261 4/3	OC45 3/-	2N174 24/-	2N2614 7/6
AC187 12/-	BCY30 7/2	C444 9/3	NKT270 3/6	OC70 3/-	2N301 8/-	2N2646 10/-
AC188 12/-	BCY31 7/2	C666 4/-	NKT271 5/4	OC71 3/-	2N109 13/6	2N2894 13/9
AC191 12/-	BCY32 2/3	C666 4/-	NKT272 5/-	OC72 4/6	2N217 7/6	2N2904A 15/6
ACY18 3/6	CRS3 4/11	CRS3/40AF 12/6	NKT273 4/-	OC73 4/-	2N352 15/-	2N2924 5/-
ACY19 4/5	BCY34 6/6	D1371 10/-	NKT274 5/-	OC75 5/-	2N386 12/-	2N2925 5/6
ACY20 3/7	BCY38 8/-	E-403 3/6	NKT275 5/6	OC76 2/6	2N384 17/-	2N3036 39/2
ACY21 4/-	BCY39 28/-	EC401 5/-	NKT276 3/6	OC77 9/3	2N385A 15/-	2N3038 8/8
ACY22 2/11	BCY40 16/-	EC402 4/8	NKT279A 2/6	OC81D 3/-	2N388A 15/-	2N3054 15/-
ACY30 9/-	BCY42 4/-	EB383 3/6	NKT281 5/-	OC81 4/6	2N370 15/-	2N3055 15/-
AD140 15/-	BCY43 17/6	GET102 6/-	NKT301 16/6	OC82 4/6	2N370A 4/2	2N3055 15/-
AD141 11/8	BCY54 17/6	GET103 4/6	NKT302 11/2	OC82D 3/-	2N410 6/-	2N3525 25/-
AD161 6/-	BCY70 4/4	GET104 5/-	NKT303 10/2	OC83 4/-	2N456A 20/-	2N3702 3/6
AD162 6/-	BCY71 8/8	GET105 8/-	NKT304 9/8	OC84 4/-	2N456A 20/-	2N3703 3/3
ADT140 12/6	BCY72 4/8	GET114 5/-	NKT351 8/-	OC84 4/-	2N511A 50/3	2N3704 3/9
AF102 18/-	BCZ11 8/9	GET115 6/-	NKT352 7/6	OC139 8/-	2N513A 118/5	2N3705 3/4
AF106 7/6	BCZ11 10/8	GET123 7/6	NKT402 24/-	OC140 12/-	2N514B 192/-	2N3706 3/10
AF114 4/4	BD119 15/-	GM0290 13/5	NKT403 16/-	OC169 6/-	2N599 12/-	2N3707 2/5
AF115 4/4	BD121 18/6	GM0378 11/-	NKT404 13/8	OC171 6/-	2N599 12/-	2N3709 3/9
AF116 4/4	BD123 13/6	NK451 5/6	NKT405 15/-	OC171 6/-	2N657 5/3	2N3710 3/10
AF117 4/4	BD124 15/-	MAT100 5/6	NKT451 13/8	OC200 6/3	2N696 15/4	2N3711 3/3
AF118 16/6	BF152 13/6	MAT101 5/6	NKT452 13/4	OC201 10/-	2N697 5/3	2N3819 8/-
AF121 4/-	BF154 9/-	MAT120 5/6	NKT453 12/-	OC202 18/10	2N698 4/6	2N3820 18/9
AF124 6/-	BF159 15/-	ME4103 6/-	NKT674 6/-	OC203 8/3	2N706 3/-	2N3820 18/9
AF126 3/9	BF163 9/-	MJES20 15/-	NKT675 5/-	OC204 8/3	2N706A 3/-	2N3826 6/-

PRICES FOR QUANTITIES IN EXCESS OF 100 PIECES ON APPLICATION

## FIRST GRADE + FAST SERVICE

When enquiring for types not listed please enclose a STAMPED ADDRESSED ENVELOPE

AF127 4/-	BF167 6/6	MPF102 9/-	NKT676 5/-	OC205 9/-	2N708 4/-	2N3906 7/6
AF139 8/-	BF173 6/2	MPF103 9/-	NKT677 5/-	OC206 10/6	2N711 7/6	2N4037 18/-
AF181 12/-	BF178 14/-	MPF104 9/-	NKT703 7/6	OC207 7/6	2N711A 7/6	2N4058 7/9
AF186 11/-	BF179 12/-	MPF105 9/-	NKT713 7/6	ORP12 9/6	1S44 1/6	2N4284 3/6
AF239 12/-	BF180 6/-	MPS3638 21/-	NKT773 6/-	ORP60 8/-	2N715 7/6	2N4285 3/6
AFZ11 14/-	BF181 7/-	MJ480 6/-	NKT774 6/-	ORP61 8/-	2N716 7/6	2N4286 3/6
AS172 11/8	BF183 11/8	NK1001 27/-	NKT001 12/6	ORP63 9/-	2N718 7/6	2N4286 3/6
ASV26 4/3	BFX13 4/10	MJ491 30/3	NKT10419 13/-	ORP93 24/-	2N743 5/-	2N4287 3/6
ASV27 6/-	BFX29 8/-	NKT121 10/11	NKT10519 12/6	OC309 12/-	2N744 5/6	2N4288 3/6
ASV28 4/5	BFX44 6/5	NKT122 7/9	NKT10339 10/3	P346A 6/-	2N753 5/-	2N4291 3/6
ASV29 6/-	BFX07 10/6	NKT123 6/2	NKT10429 11/3	RAS310AF 6/-	2N863 6/-	2N4292 3/6
ASZ21 11/-	BFY50 4/6	NKT124 9/8	NKT20329 12/6	RAS508AF 15/-	2N911 7/6	2N4303 15/-
ATZ10 40/-	BFY51 3/9	NKT125 6/2	NKT16229 11/-	SC41D 37/6	2N914 4/3	2N4871 6/9
AU10 39/6	BFY52 4/6	NKT127 5/8	OAS 3/8	ST2 9/9	2N918 15/-	2S02 15/-
AFY19 16/10	BFY55A 3/2	NKT128 6/-	OA10 6/-	ST140 3/-	2N929 5/6	2S004 23/-
BA110 6/-	BSX20 3/4	NKT129 5/10	OA47 1/6	ST141 5/-	2N930 6/8	2S017 15/-
BA111 6/-	BSX21 8/-	NKT141 6/11	OA70 1/6	T1544 1/7	2N1131 9/6	2S018 12/6
BA112 18/-	BSY27 4/-	NKT142 5/10	OA73 1/6	T1543 6/9	2N1132 7/6	2S020 15/-
BA115 18/-	BSY95A 3/4	NKT143 5/4	OA79 1/6	U23AAA 15/-	2N1143 26/2	2S024 25/-
BA130 3/-	BTX39/1 8/-	NKT144 8/-	OA81 1/6	V205 20/-	2N1177 14/6	2S034 12/6
BA132 2/6	600R 120/-	NKT152 3/4	OA85 1/6	V405A 9/3	2N1302 4/6	2S102 10/-
BA338 3/-	BTX40/1 120/-	NKT161 5/8	OA90 1/6	X4102 6/6	2N1303 4/6	2S104 12/6
BC107 2/9	BTY87 120/-	NKT162 5/8	OA91 1/6	X4702 15/-	2N1304 5/-	2S301 7/7
BC109 2/9	ISOR 31/-	NKT163 5/4	OA95 1/6	Z12V7 3/6	2N1305 5/-	2S302 6/-
BC114 7/5	BY100 5/-	NKT164 5/4	OA200 2/-	ZT22 19/-	2N1306 6/6	2S304 15/-
BC115 7/11	BYX10 3/-	NKT165 5/8	OA205 2/-	ZT66 27/6	2N1307 6/6	2S326 12/6
BC116 9/-	BYX36/150 2/6	NKT213 6/-	OA210 6/4	ZT2270 19/6	2N1308 8/-	2S322 8/-
BC118 5/-	BYX36/300 2/10	NKT214 4/-	OA211 9/-	IN23A 20/-	2N1309 8/-	2S701 8/-
BC125 12/-	BYX36/600 3/8	NKT215 4/-	OC19 5/-	IN34A 4/-	2N1507 4/8	2S702 12/-
BC126 12/-	BYX36/600 3/8	NKT216 10/5	OC20 33/6	IN613 6/6	2N1613 6/6	2S711 23/3
BC134 5/-	BY21 25/-	NKT217 10/5	OC22 13/6	IN64 4/-	2N1496 3/6	2S712 30/3
BC136 7/11	BY23 26/3	NKT218 5/3	OC23 15/-	IN82A 9/6	2N1711 7/6	2S733 9/9
			OC24 10/-	IN87A 4/6	2N2147 17/4	40361 13/3
			OC25 6/9	IN191 5/-	2N2148 12/6	40362 16/3

**2N3819** Texas FET 8/-  
25 + 6/9 100 + 5/9

**MICRO-LOGIC**  
These are new Prices.  
1-6 7-11 12+  
uL900 9/9 9/- 8/-  
uL914 9/9 9/- 8/-  
uL923 13/- 12/- 11/-  
Five Page Data and Circuits article 2/6  
Larger quantity prices (100+ and 1,000+) on application.  
Plastic Spreader 1/6

**SILICON RECTIFIERS**

PIV	200mA	750mA	2 Amp	10 Amp
50	6d	1/-	2/3	4/-
100	9d	1/6	2/3	4/-
200	1/3	2/-	2/9	5/-
400	—	2/6	4/-	8/-
600	—	3/-	4/6	9/6
800	—	3/9	5/-	11/3
1000	—	6/-	6/6	14/-

**ULTRASONIC TRANSDUCERS**  
Operate at 40kc/s. Can be used for remote control systems without cables or electronic links. Type 1404 transducers can transmit and receive.  
FREE: With each pair our complete transmitter and receiver circuit.  
PRICE £5.18.0 Pair (Sold only in pairs)

**2N4871** MOTOROLA Unijunction 6/9  
25 + 5/9 100 + 4/9

**BF180** MULLARD UHF AMPLIFIER 6/-  
25 + 4/11 100 + 4/3

**THYRISTORS-SCRs**

PIV	1A	3A	10A	30A	100A
50	7/6	9/-	7/6	25/-	20/-
100	—	10/-	10/-	30/-	22/-
200	8/6	—	12/6	42/-	35/-
300	—	11/-	—	51/-	—
400	9/6	12/6	15/-	60/-	45/-
600	—	—	20/-	84/-	120/-
800	—	—	—	—	—

**56CA4** Gallium Arsenide Infra-Red emitter 29/6 each. (Incl. data)

**2N3055** 115 WATT POWER 15/-  
25 + 13/- 100 + 11/-

**2N2614** RCA LOW NOISE AUDIO 4/9  
25 + 4/- 100 + 3/-

**NEW SPECIAL ITEMS!!**  
40602— Dual Gate MOS-FET 9/- each  
1148— Photo-Darlington Amplifier 26/6  
MGA100— Gallium Arsenide Infra Red Light Source 35/-  
31F2— Infra Red Detector Diode 28/6  
3N84— Silicon Controlled Switch 29/6  
TAA320— Monolithic IC with MOS-FET input followed by Bi-Polar transistor 13/6  
Data sheets 1/- on request—free with above items.

**BC107/8/9** Planars 2/9

**SL403** PLESSEY 3 WATT IC AMPLIFIER 49/6

**ADIGI/2** 10/-  
NPN/PNP PAIR COMPLEMENTARY PAIRS

**2N2926** LOW COST NPN PLANAR 2/-  
25 + 1/8 100 + 1/6

**BY127** 5/-  
MULLARD 800 PIV 1 AMP PLASTIC RECTIFIER 25 + 4/3 100 + 3/-

**"YOU'LL BE KNOCKED OUT BY OUR NEW CAT."**



Prices quoted are current at time of going to press and may be subject to variation. Semiconductors offered bear Manufacturers' original markings and are subject to our full replacement guarantee if not to published specifications. WE DO NOT offer "Re-marked" Semiconductors. Our 1969/70 Catalogue is available FREE on request. Please enclose a stamped addressed envelope with any queries. Quantity Prices on application. Retail: Cash with order, please. Trade: Please furnish useful references if Credit facilities required. Post & Packing 1/- per order (FIRST CLASS).

**MAIL ORDER DEPT. & RETAIL SHOP:—**  
**LST, 7 Coptfold Road, Brentwood, Essex**  
Telephone: 226470/1 (Sales Department)  
**EXPORT ENQUIRIES PARTICULARLY WELCOME**

# Lasky's

## TMK METER KITS ANOTHER LASKY'S EXCLUSIVE

These two new meter kits by TMK offer the professional, electronics hobbyist and student the unique opportunity of building a really first class precision multimeter at a worthwhile saving in cost. The impact resistant bakelite cabinets are supplied with the meter scale and movement mounted in position; the model 200 also has the rotary range selector in position. The highest quality in components and 1% tolerance resistors are used throughout. Both offer professional standards of accuracy. Supplied complete in every detail with full constructional, circuit and operating instructions.

### MODEL 200

20,000 O.P.V. Multimeter. Features 24 measurement ranges with mirror scale. Large 3 x 2 1/2 in. meter, full scale accuracy: DCV and current,  $\pm 2\%$ ; ACV:  $\pm 3\%$ ; resistance  $\pm 3\%$ . Special 0.6V DC range for transistor circuit measurements.



**SPECIFICATION:**

- DCV: 0-0.6 6-30-120-600-1,200V at 20K/OPV.
- ACV: 0-6-30-120-600-1,200V at 10K/OPV.
- DC Current: 0-0.06 6-60-600mA.
- Resistance: 0-10K 100K 1M 10M/ohms (58-580-5.8K-58K at mid-scale).
- Capacitance: 0.002 0.2  $\mu$ F 100  $\mu$ F range.
- Decibels: -20 to +63dB.
- Output: 0.05  $\mu$ F blocking capacitor. Uses two 1.5V (U7 type) batteries. Black bakelite cabinet, size 5 1/2 x 3 3/8 x 1 1/2 in. Complete with test leads.


**LASKY'S KIT PRICE 85/-** Post 3/6

### MODEL 5025 50,000 O.P.V. FEATURING 57 MEASUREMENT RANGES

A highly reliable instrument using an entirely new range selection mechanism which permits the use of a really large meter in a more compact cabinet. The range selected is clearly indicated on the actual meter face facilitating instant identification without taking your eyes from the meter. High speed rotary range selection knob; also features polarity reversal switch, shielded meter movement with overload protection circuit. Special A and mA measurement ranges.

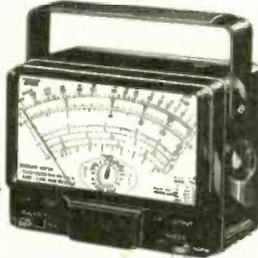**SPECIFICATION:**

- DCV: 0.025-2.5-10-50-250-1,000V at 25K/OPV 0.025-1.25-5.0-25-125-500V at 50K/OPV.
  - ACV: 0-3-10-50-250-1,000V at 2.5K/OPV 0-1.5-5-25-125-500V at 5K/OPV.
  - DC  $\mu$ A: 0-25  $\mu$ A at 125mV; 0-50  $\mu$ A at 250mV.
  - DC mA: 0-2.5-25-250mA at 125mV; 0-5-50-500mA at 250mV.
  - DC Amps: 0-5A at 125mV; 0-10A at 250mV.
  - Resistance: 0-10M/ohms (13, 65, 650, 6.5K and 65K/ohms at centre scale).
  - Output Capacitor: 0.1  $\mu$ F, 400VW in series with ACV ranges.
  - Decibels: -20 to +81.5dB in 10 ranges.
- Operates on two 1.5V (U7 type) batteries. Black bakelite cabinet, size 5 1/2 x 6 x 2 1/2 in. Strong resilient plastic handle. Complete with test leads.



**LASKY'S KIT PRICE £10.10.0** Post 5/-  
ALSO AVAILABLE READY-BUILT AND TESTED £12.10.0. Post 5/-

## TMK 100K "LAB" MULTIMETER

FULLY BUILT AND TESTED

A highly accurate Multimeter using a 10  $\mu$ A. Meter hand calibrated to a DC accuracy of  $\pm 3\%$  of full scale. Special features: ultra large meter scale; 6 1/2 x 3 1/2 in., incorporating an entirely new type of range selection panel which gives instant identification without taking your eyes from the meter. An audible buzzer is provided for easy short testing. SPEC. DCV ranges: 0.5, 2.5, 10, 50, 250, 500, 1,000V at 100K/OPV. ACV ranges: 3, 10, 50, 250, 500, 1,000V at 5K/OPV. DC current: 0-10, 100 A, 0-10, 100mA 0-2.5, 10Amps. Resistance: 0-1K, 10K, 100K, 10M, 100M/ohms. Decibels: -10 to +49.4dB. Continuity test/Audible buzzer. Operates on 1x1.5V U2 and 1x1.5V 8.154 type batts. Cabinet size 7 1/2 x 6 1/2 x 3 1/2 in. Weight 4lb.



**LASKY'S PRICE £19.10.0** Post 5/-

## TMK Model PL-436

FULLY BUILT AND TESTED

20,000 O.P.V. Multi-tester for the amateur or professional. Features mirror scale and wood grain finish front panel. SPEC.: DCV ranges: 0.6, 3, 12, 30, 120, 600V at 20K/O.P.V. ACV ranges: 3, 30, 120, 600V at 8K/O.P.V. DC current: 50  $\mu$ A, 0.6, 60, 600mA. Resistance: 10K, 100K, 1M and 10M ohms end scale (65, 650, 6.5K and 65K ohms centre scale). Decibels: -20 to +57dB in four ranges. Operates on 2 x 1.5V U7 type batts. Size: 5 1/2 x 4 1/2 x 2 1/2 in. Complete with batteries and operating instructions.



**LASKY'S PRICE £6.19.6** Post 5/-

**GET YOUR LASKY'S AUDIO-TRONICS PICTORIAL FREE** 16 colour pages in large 16x11in format packed with 1,000s of items from our vast stocks: Hi-Fi, Radio, Electronics, Test Equipment, Components, Communications, etc. Send 1/- for post only and inclusion on our regular mailing list.

# Lasky's Radio Limited

Branches

207 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 3271  
33 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-636 2605  
Open all day, 9 a.m.—6 p.m. Monday to Saturday  
152/3 FLEET STREET, LONDON, E.C.4. Tel.: 01-353 2833  
Open all day Thursday, early closing 1 p.m. Saturday

High Fidelity Audio Centres


42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-580 2573  
Open all day, 9 a.m.—6 p.m. Monday to Saturday  
118 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 9789  
Open all day Saturday, early closing 1 p.m. Thursday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E.1 Tel.: 01-790 4821



## TTC Model C-1051

POCKET MULTIMETER

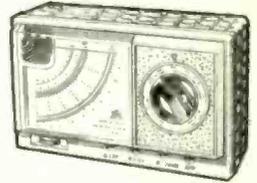

A completely new design 20,000 O.P.V. pocket multimeter with mirror scale and built-in thermal protection. Exceptionally large easy to read meter with 0.1 division movement. Colour coded scales. Single positive click-in, recessed selection switch for all ranges. Ohms zero adjustment. Range spec. a.c. volts: 0-6-30-300-1,200V at 10K/ohms/V. DC volts: 0-3-15-150-300-1.2KV at 20K/ohms/V. Resistance: 0-60K-6mega. DC current: 0-80  $\mu$ A—300mA. Decibels: -20dB to +17dB. Hand calibration gives extremely high standard of accuracy on all ranges. Uses one 1 1/2V penlight battery. Strong impact resistant plastic cabinet—size only 4 1/2 x 3 1/2 x 1 1/2 in. Two colour buff/green fresh. Complete with test leads and battery.

**LASKY'S PRICE 75/-** Post 2/6  
ALSO AVAILABLE C-1052 3 KOPV METER £5.19.6

## TTC MODEL C-1000




A really tiny 1,000 O.P.V. pocket multi-tester with "big" meter performance. Precision 2 jewel meter movement. Hand calibrated to  $\pm 3\%$  accuracy on full scale of DC ranges. 4% on AC ranges. 2 1/2 in. square meter. SPECIFICATIONS: ACV ranges: 0-10, 50, 250, 1,000V at 1K/O.P.V. ACV ranges: 0-10, 50, 250 100V at 1K/O.P.V. DC current: 0-1-100mA. Resistance: 0-150K/ohms (3,000 ohms centre scale). Decibels: -10 to +22dB. Operates on one penlight cell. Two colour buff/green case size only 3 1/2 x 2 1/2 x 1 in. Click stop range selection switch. Ohms zero adjustment. Complete with test leads, battery and pins.

**LASKY'S PRICE 39/6** Post 2/6

## AVAILABLE NOW! THE IC-403

INTEGRATED CIRCUIT AMPLIFIER MODULE

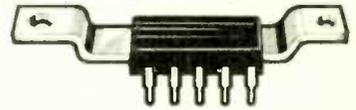


Originally developed for computer and space projects—these tiny modules—size only 25x10x5 millimetres—represent the most amazing breakthrough in circuit design since the introduction of the transistor. The IC 403 is an integrated power and pre-amplifier requiring only the addition of tone and volume controls, power source and speaker to form a complete audio amplifier of 3W output. SPECIFICATION (ratings at 25°C): Output power typically 3W from 250mV input. Frequency response 20Hz to 80KHz +3dB Max. operating voltage 21V. Min operating load 7.5 ohms. Pre-amp. input Imp. 2M/ohms. Pre-amp. O.C. input current 50nA. THE IC-403 IS AVAILABLE FROM STOCK EXCLUSIVELY FROM LASKY'S—COMPLETE WITH INSTRUCTION DATA AND SUGGESTED CIRCUIT APPLICATIONS. FREE INSTRUCTION DATA LEAFLET ON REQUEST. JUST SEND S.A.E.

**LASKY'S PRICE 49/6** Post 1/6, 2 for 95/- post free.  
Also available from stock Sinclair IC-10. 59/6 post free.
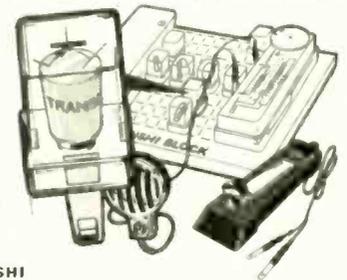
## DENSHI BOARD KITS EDUCATIONAL CIRCUIT SYSTEM

The DENSHI BOARD system enables the young experimenter and electronics hobbyist to produce a wide range of transistor circuits of increasing sophistication—without soldering or the use of any tools at all! Basically the system comprises a slotted circuit board into which plug-in components and bridge pieces are set to produce up to 30 different circuits. The components are encapsulated in transparent plastic blocks bearing the appropriate circuit symbol and value, thus enabling even the complete novice to visually grasp the fundamentals of circuitry after only a few moments study. Each DENSHI



BOARD KIT comes complete with 80-page manual of circuits and data. THESE ARE JUST A FEW OF THE CIRCUITS YOU CAN BUILD IN MINUTES: VARIOUS RADIO RECEIVERS, AMPLIFIERS, MORSE CODE PRACTICE DEVICE, SIGNAL INJECTOR, SIGNAL TRACER, WIRELESS MICROPHONE, ETC. DENSHI BOARD KIT SR-1A comprises: Base board; tuner block; 4 resistors; choke coil transformer; 2SA transistor for RF; 2 diodes; 3 capacitors; battery block; Morse key; antenna lead; crystal earphone; various bridge and connecting pieces and 80 page manual. This kit permits the building of 16 basic circuits.

**LASKY'S PRICE £4.19.6** POST 3/6

DENSHI BOARD KIT SR-2A as SR-1A plus: 2SB transistor for AF; 2 resistors; 1 capacitor; crystal microphone; test probes; electrode; additional connecting pieces; 9V battery. This kit permits the building of 30 circuits.


**LASKY'S PRICE £7.2.6** POST 3/6

**ADMIRALTY B.40 RECEIVERS**



High quality 10 valve receiver manufactured by Murphy. Coverage in 5 bands 680 Kc/s-30 Mc/s. I.F. 500Kc/s. Incorporates 2 R.F. and 3 I.F. stages, bandpass filter, noise limiter, crystal controlled B.F.O. calibrator I.F. output, etc. Built-in speaker, output for phones. Operation 150/250 volt A.C. Size 19 1/2 x 13 1/2 x 1 1/2 in. Weight 114lb. Offered in good working condition. £22/10/0. Carr. 30/- With circuit diagrams. Also available B41 L.F. version of above. 15 Kc/s-700 Kc/s. £17/10/- Carr. 30/-.

**R209 Mk. II COMMUNICATION RECEIVER**

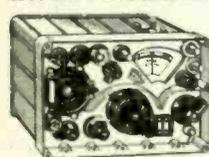

11 valve high grade communication receiver suitable for tropical use. 1-20 Mc/s. on 4 bands. AM/CW/FM operation. Incorporates precision vernier drive. B.F.O. Aerial trimmer, internal speaker and 12v. D.C. internal power supply. Supplied in excellent condition, fully tested and checked. £15.0.0 Carr. 20/-.

**TYPE 13A DOUBLE BEAM OSCILLOSCOPES BARGAIN**



An excellent general purpose D/B oscilloscope. T.B. 2 cps-750 Kc/s. Bandwidth 5.5 Mc/s. Sensitivity 33 mV/cm. Operating voltage 0/110/200/250 v. A.C. Supplied in excellent working condition. £22/10/- Or complete with all accessories, probe, leads, lid, etc. £25. Carriage 30/-.



**MARCONI CT44 TP956 AF ABSORPTION WATTMETER**  
1 μwatt to 6 watts. £20. Carr. 20/-.

**PLESSEY 5L 403A**  
3-watt. integrated amplifier circuit. 48/8 post paid.

**CLASS D. WAVEMETERS**

A crystal controlled heterodyne frequency meter covering 1.7-8 Mc/s. Operation on 6 v. D.C. Ideal for amateur use. Available in good used condition £5.19.8 Carr. 7/6. Or brand new with accessories £7.19.6 Carr. 7/6.

**CLASS D WAVEMETERS No. 2**  
Crystal controlled. 1.2-19 Mc/s. Mains or 12v. D.C. operation. Complete with calibration charts. Excellent condition £12/10/0. Carr. 30/-.

**EDDYSTONE V.H.F. RECEIVERS**  
770r. 19-165 Mc/s. £150. Both types in excellent condition.

**LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS**  
0-20 Kc/s. Output 5K or 600 ohms. 200/250 v. A.C. Offered in excellent condition. £12/10/- Carriage 10/-.

**RACAL MA.168 TRANSISTORISED DIVERSITY SWITCH**  
Brand new condition £15. Carriage 10/-.

**TO-2 PORTABLE OSCILLOSCOPE**

A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth 2 cps-1 MHz. Input Imp. 2 meg Ω. 25 PF. Illuminated scale. 2" tube. 115 x 180 x 230 mm. Weight 8lbs. 220/240v. A.C. Supplied brand new with handbook. £22/10/- Carr. 10/-.

**TO-3 PORTABLE OSCILLOSCOPE. 3" TUBE**

Y amp. Sensitivity. 1v p-p/CM. Bandwidth 1.5 cps-1.5 MHz. Input Imp. 2 meg Ω. 25 PF. X amp. sensitivity. 1v p-p/CM. bandwidth 1.5 cps-800 KHz. Input Imp. 2 meg Ω. 20 PF. Time base. 5 ranges 10 cps-300 KHz. Synchronisation. Internal/external. Illuminated scale. 140 x 215 x 330 mm. Weight 15 1/2 lbs. 220/240 v. A.C. Supplied brand new with handbook. £35/- Carr. 10/-.

**SOLARTRON MONITOR OSCILLOSCOPE TYPE 101**

An extremely high quality oscilloscope with time base of 10 μsec. to 20 m/sec. Internal Y amplifier. Separate mains power supply, 200/250 v. Supplied in excellent condition with cables, probe, etc., as received from Ministry. £8/19/6. Carr. 30/-.

**FIELD TELEPHONES TYPE L** Generator/Ringing, metal case. Operates on 2 1.5 v. batteries (not supplied). Excellent condition. £4.10.0 per pair. Carr. 10/-.

**UNR-30 4 BAND COMMUNICATION RECEIVER**  
Covering 550 Kc/s-30 Mc/s. Incorporates BFO. Built-in speaker and phone jack. Metal cabinet. Operation 220/240 v. A.C. Supplied brand new, guaranteed with instructions. 13gns. Carr. 7/6.

**HAMMARLUND SP600 JX COMMUNICATION RECEIVER**  
Frequency range 540 Kc/s to 54 Mc/s in 6 Bands. Few available in excellent condition, tested and checked. £100 each.



**LAFAYETTE SOLID STATE HA600 RECEIVER**  
5 BAND AM/CW/SSB AMATEUR AND SHORT WAVE. 150 kc/s-400 Kc/s AND 550 Kc/s-30 Mc/s. F.E.T. front end ● 2 mechanical filters ● Hnse dial ● Product detector ● Variable BFO ● Noise limiter ● 8 meter ● 24 1/2 in. Bandspread ● 230 v. A.C./12 v. D.C. neg earth operation ● RF gain control. Size 15in. x 9 1/2 in. x 6 1/2 in. Wt. 18 lbs. EXCEPTIONAL VALUE £45. CARR. 10/- S.A.E. FOR FULL DETAILS.

**TRIO COMMUNICATION RECEIVER MODEL 9R-59DE**


4 band receiver covering 500 Kc/s to 30 Mc/s, continuous and electrical bandspread on 10.15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 48 ohm output and phone jack. SSB-CW ● ANL ● Variable BFO ● 8 meter. ● Sep. Bandspread dial ● IP 455 Kc/s ● audio output 1.5 w. ● Variable BP and AP gain controls. 115/250 v. A.C. mains. Beautifully designed. Size 7 x 15 x 10in. With instruction manual and service data. £42. Carriage Paid. Trio Communication Type Headphones. Normally £5.19.6. Our price £3.15.0 if purchased with above receiver.

**TRIO TS 510 Amateur Transceiver with speaker and mains P.S.U. £212 0**  
**TRIO JR 500SE 10-80 Metre Amateur Receiver £69 10**

**LAFAYETTE HA.800 SOLID STATE AMATEUR COMMUNICATION RECEIVER SIX BANDS 3.5-4, 7-7.3, 14-14.35, 21-45, 28-29.7, 50-54 Mc/s.**

Dual conversion on all bands. 2 x 455 Kc/s mechanical filters. Product detector. Variable B.F.O. 100 Kc/s crystal calibrator. '8' meter. Huge slide rule dial. Operation 230v AC or 12v DC. Size 15" x 8 1/2" x 8 1/2". Complete with instruction manual. £57.10.0. Carr. Paid. (100 Kc/s Crystal 39/6 extra).

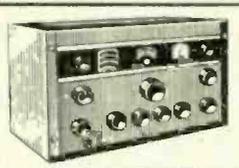**TRIO JR-310 NEW AMATEUR BAND 10-80 METER RECEIVER IN STOCK £77.10.0**



**RCA COMMUNICATIONS RECEIVERS AR88D**  
Latest release by ministry BRAND NEW in original cases. 110-250v. A.C. operation. Frequency in 6 Bands. 635 Kc/s-32 Mc/s continuous. Output impedance 2.5-600 ohms. Incorporating crystal filter, noise limiter, variable BFO, variable selectivity, etc. Price £87.10.0. Carr. £2.

**LAFAYETTE PF-60 SOLID STATE VHF FM RECEIVER**

A completely new transistorised receiver covering 152-174 Mc/s. Fully tuneable or crystal controlled (not supplied) for fixed frequency operation. Incorporates 4 INTEGRATED CIRCUITS. Built-in speaker and illuminated dial. Squelch and volume controls. Tape recorder output. 75 Ω aerial input. Headphone jack. Operation 230 v. A.C./12 v. D.C. Neg. earth. £37/10/- Carr. 10/-.

**SOLARTRON CD711S.2 DOUBLE BEAM OSCILLOSCOPE**

An extremely high quality oscilloscope originally costing £400. Switched beam. Identical Y1, Y2 Amplifiers D.C. to 9 Mc/s. Sensitivity 3mV/CM to 100 V/CM. Time base 10μsec. to 10 M/sec. Calibrator. X amplifier D.C. to 2.5 Mc/s. Z Modulation. 110/250 v. A.C. Supplied in good working order. £85. Carriage 50/-.

**CRYSTAL CALIBRATORS NO. 10**  
Small portable crystal controlled wavemeter. Size 7in. x 7 1/2 in. x 4in. Frequency range 500 Kc/s-10 Mc/s (up to 30 Mc/s on harmonics). Calibrated dial. Power requirements 300 V.D.C. 15mA and 12 V.D.C. 0.3A. Excellent condition. 89/8 Carr. 7/6.

**SEW PANEL METERS**

Type MR.38P. 1 21/32in. square fronts.

50μA.....	40/-	50mA.....	27/6	100V. D.C. ....	27/6
100-0-50μA ..	37/8	100mA.....	27/8	150V. D.C. ....	27/8
500μA.....	37/8	150mA.....	27/8	300V. D.C. ....	27/8
1000-100μA ..	35/-	200mA.....	27/8	500V. D.C. ....	27/8
2000μA.....	35/-	300mA.....	27/8	750V. D.C. ....	27/8
5000μA.....	30/-	500mA.....	27/8	15V. A.C. ....	27/8
5000-0-500μA	27/8	750mA.....	27/8	50V. A.C. ....	27/8
1mA.....	27/8	1 amp.....	27/8	180V. A.C. ....	27/8
1-0-1mA.....	27/8	2 amp.....	27/8	300V. A.C. ....	27/8
2mA.....	27/8	5 amp.....	27/8	500V. A.C. ....	27/8
5mA.....	27/8	2V. D.C. ....	27/8	8 meter 1mA ..	32/-
10mA.....	27/8	10V. D.C. ....	27/8	VU meter.....	42/-
20mA.....	27/8	20V. D.C. ....	27/8		

FULL RANGE OF OTHER SIZES IN STOCK—SEND SAE FOR LEAFLET


**LAFAYETTE STEREO AMPLIFIER MODEL STEREO 10**

Completely transistorised 5 watt per channel I.E.F. music power. Inputs for gram and tuner. Separate volume controls and variable tone control for Bass and Treble. A compact size, high performance stereo amplifier ideal for limited space systems. Beautifully finished in grey and aluminium. Size 7 1/2 in. x 2 1/2 in. x 5 1/2 in. AC. 220/240v. Price £11.19.6 Carr. 7/6.

**POWER RHEOSTATS**

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush sliper. Continuous ratings. Wide range available ex-stock. Single hole fixing. 1/2 in. dia. shafts. Bulk quantities available. 25 WATT. 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms. 14/6. P. & P. 1/6. 50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. 21/- P. & P. 1/6. 100 WATT. 1/5/10/25/50/100/250/500/1000 or 2500 ohms. 27/8. P. & P. 1/6.

**AVOMETER MOVEMENTS**

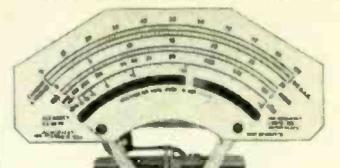

50μA 20KΩ/V. Spare movements for Model 8 or 9. (Fitted with Model 9 scale) or basis for any multimeter. Brand New and Boxed 69/6 P. & P. 3/6

**AVO 48A**  
Perfect order with set of shunts and resistances £12.10.0. P. & P. 7/6.

**T.E.40 HIGH SENSITIVITY A.C. VOLTMETER**

10 meg. input 10 ranges: .01/.03/.1/.31/1/3/10/30/100/300 v. R.M.S. 4 cps.-1.2 Mc/s. Decibels -40 to +80 dB. Supplied brand new complete with leads and instructions. Operation 230 v. A.C. £17/10/- Carr. 5/-.

**TE-65 VALVE VOLTMETER**

High quality instrument with 28 ranges. D.C. volts 1.5-1,500 v. A.C. volts 1.5-1,500 v. Resistance up to 1,000 megohms. 220/240v. A.C. operation. Complete with probe and instructions £17/10/0. P. & P. 6/- Additional Probes available: R.F. 35/- H.V. 42/6.

**COSSOR 1049 DOUBLE BEAM OSCILLOSCOPES**  
D.C. coupled. Band width 1 Kc/s. Perfect order. £25. Carr. 30/-.

**AM/FM SIGNAL GENERATORS**

Oscillator Test No. 2. A high quality precision instrument made for the Ministry by Alrmec. Frequency coverage 20-80 Mc/s. AM/OV/FM. Incorporates precision portables precision dial, level meter, precision attenuator 1μV-100mV. Operation from 12 volt D.C. or 0/110/200/250 v. A.C. Size 12 x 8 1/2 x 9 1/2 in. Supplied in brand new condition complete with all connectors, fully tested. £45. Carr. 20/-.

**GEARED MAINS MOTOR**  
Farlux type RD19 230/250 v. A.C. Reversible. 30 r.p.m. 40 lb. ins. Complete with capacitor. Excellent condition. 89/8 Carr. 10/-.

**TE-16A TRANSISTORISED SIGNAL GENERATOR**

5 Ranges 400 KHz-30 MHz. An inexpensive instrument for the handyman. Operates on 9v. battery. Wide easy to read scale. 800 KHz modulation. 5 1/2" x 5 1/2" x 3 1/2". Complete with instructions and leads. £7/19/6. P/P 4/-.

**TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE**

A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-11.1 MEG Ω. 6 Ranges ± 1%. L. 1μF-111 HENRIES. 6 Ranges -2%. C. 10PF ± 1110MFD. 6 Ranges ± 2%. TURNS RATIO 1:1/1000-1:1100. 6 Ranges ± 1%. Bridge voltage at 1,000 CPS. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2" x 6" x 2". £20. P. & P. 5/-.

**AUTO TRANSFORMERS**

0/115/230v. Step up or step down. Fully shrouded 150 W. 42/6. P. & P. 3/6  
300 W. 59/6. P. & P. 4/6  
500 W. 24/10/0. P. & P. 6/6  
1,000 W. 88/10/0. P. & P. 7/6  
1,500 W. 27/19/6. P. & P. 8/6  
7,500 W. £15/10/0. P. & P. 20/-.

**G. W. SMITH & Co. (Radio) Ltd.**

ALSO SEE OPPOSITE PAGE

**ARF-100 COMBINED AF-RF SIGNAL GENERATOR**



**AF. SINE WAVE**  
20-200,000 cps. Square wave 20-30,000 cps. O/P HIGH IMP. 21 v. P/P 600 Ω 3.8 v. P/P R.F. 100 kc/s-300 Mc/s. Variable R.F. attenuation. Int./Ext. Modulation. Incorporates dual purpose meter to monitor AF output and % mod. on R.F. 220/240 v. A.C. £30. Carr. 7/6.

**VOLTAGE STABILISER TRANSFORMERS.** 180-260v. input. Output 230v. Available 150w or 225w. £12-10.0. Carr. 5/-.

**TE-20RF SIGNAL GENERATOR**



Accurate wide range signal generator covering 120 kc/s-200 Mc/s. on 6 bands. Directly calibrated. Variable R.F. attenuator. Operation 200/240 v. A.C. Brand new with instructions. £15.

P. & P. 7/6. S.A.E. for details.

**PEAK SOUND PRODUCTS**

Full range of Amplifiers, Kits, Speakers in stock.

**TE22 SINE SQUARE WAVE AUDIO GENERATORS**

Sine: 20 cps to 200 kc/s. on 4 bands. Square 20 cps to 30 kc/s. Output Impedance 5,000 ohms, 200/250 v. A.C. operation. Supplied brand new and guaranteed with instructions manual and leads. £18-10.0. Carr. 7/6.



**MARCONI TF885 VIDEO OSCILLATORS**

0-5 mc/s Sine Square Wave £45. Carr. 20/-.

**LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER**



2 pf-2,000 mfd. 2 ohms-200 meg-ohms. Also checks impedance, turns ratio, insulation, 200/250 v. A.C. Brand New, £17-10. Carr. 7/6.

**MARCONI TF142E DISTORTION FACTOR METERS**

Excellent condition. Fully tested £20. Carr. 15/-.

**TY75 AUDIO SIGNAL GENERATOR**

Sine Wave 20 CFS-200 Kc/s. Square Wave 20 CFS-30 Kc/s. High load impedance output. Output variable up to 6 volts. 220/240 volts A.C. Brand new with instructions. £18. Carr. 7/6. Size 210 x 150 x 120 mm.



**MARCONI TF195M BEAT FREQUENCY OSCILLATORS**

0-40 kc/s. £20. Carr. 30/-.

**TE-20D RF SIGNAL GENERATOR**



Accurate wide range signal generator covering 120 Kc/s-500 Mc/s on 6 bands. Directly calibrated. Variable R.F. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions. £15. Carr. 7/6. Size 140 x 215 x 170 mm.

**ADVANCE TEST EQUIPMENT**

Brand new and boxed in original sealed cartons. **VM.76. VALVE VOLTMETER.** R.F. measurements in excess of 100 Mc/s and D.C. measurements up to 1000 v. with accuracy of ±2%. D.C. range 300 MV to 1 KV. A.C. range 300 MV to 300 V R.M.S. Resistance 0.02-500 M. Price £72. **VM.78. UHF MILLIVOLT METER.** Transistorised. A.C. range 10 MV-3V. D.C. current range 0.01/1A-0.3 mA. Resistance 1 ohm-10 megohms. £125. **H1B. AUDIO SIGNAL GENERATOR.** 15 c/s-50 Kc/s. sine or square wave. Price £30. **J1B. AUDIO SIGNAL GENERATOR.** 10 c/s-30 Kc/s. Price £30. **TT15. TRANSISTOR TESTER.** £37/10/- Carrriage 10/- per item.

**MODEL ZGM TRANSISTOR CHECKER**



It has the fullest capacity for checking on A, B and Ic. Equally adaptable for checking diodes, etc. Spec: A: 0.7-0.9987. B: 5-200. Ic: 0/50 micro-amps. 0.5 mA. Resistance for diode 200Ω + 1 MEG. Supplied complete with instructions, battery and leads. £5/19/6. P. & P. 2/6.

**Latest Catalogue**

The latest edition giving full details of a comprehensive range of HI FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT AND COMMUNICATIONS EQUIPMENT. . . . Nearly 200 pages, fully illustrated and detailing thousands of items - many at bargain prices. FREE DISCOUNT COUPONS VALUE 10/-.



SEND NOW - ONLY 7/6 P & P!!

**GARRARD**


Full current range offered brand new and guaranteed at fantastic savings

- \*1025 Mono £6.19.6
- \*1925 Stereo £6.19.6
- \*2025 Stereo £7.18.6
- \*2025T/C Mono/Stereo £5.17.6
- \*3000 Stereo £9.19.6
- \*8P25 MKII £11.19.6
- \*8L55 £11.19.6
- \*A70 MKII £11.19.6
- \*8L65 £14.4.6
- AP75 £17.17.0
- 401 £28. 7.8
- 8L75 £28.10.0

Carriage/insurance 7/6 extra any model. WB4 Bases £3/19/6. Perspex cover £3/10/0. \*Special offer base and cover available for these models at £4.15.0. Carr. 5/-. Full range of Garrard accessories available



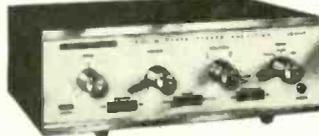**LAFAYETTE LA-224T TRANSISTOR STEREO AMPLIFIER**



19 transistors, 8 diodes, IHP music power 30 watts at 8 ohms. Res. 30-20,000 ±2 dB at 1 w. Distortion 1% or less. Inputs 3 mV and 250 mV. Output 3-16 ohms. Separate L and R volume controls. Treble and bass controls. Stereo phone jack. Brushed aluminium, gold anodised extruded front panel with metal case. Size 10 1/2 in. x 3 1/2 in. x 7 1/2 in. Operation 115/230 volt A.C. £28. Carr. 7/6.

**Variable Voltage Transformers**

Brand new, guaranteed and carriage paid. High quality construction. Input 230 v. 50-60 cycles. Output full variable from 0-260 volts. Bulk quantities available. 1 amp. - £5/10/-; 2.5 amp. - £6/15/-; 5 amp. - £9/15/-; 8 amp. - £14/10/-; 10 amp. - £18/10/-; 12 amp. - £21/-; 20 amp. - £37



**MULTIMETERS for EVERY purpose!**



**TE-900 20,000 Ω/VOLT GIANT MULTIMETER**  
Mirror scale and overload protection. 6in. full view meter. 2 colour scale. 0/2.5/10/250/1,000/5,000 v. A.C. 0/25/12.5/110/50/250/1,000/5,000 v. D.C. 0/50μA/110/100/500mA/10 amp. D.C. 02K/200K/20 MEG. Ohm. £15/- P. & P. 5/-.

**MODEL AS-100D. 100K Ω/Volt. 5in. mirror scale. Built-in meter protection 0/3/12/60/120/300/600/1,200 v. D.C. 0/6/30/120/300/600 v. A.C. 0/10μA/0/60/300MA. 12 Amp. 0/2K/200K/2M/200M Ω. -20 to +17.6. £12/10/- P. & P. 3/6.**




**MODEL TE-90 50,000 O.P.V.**  
Mirror scale overload protection. 0/3/12/60/300/600/1,200 v. D.C. 0/6/30/120/300/600 v. D.C. 0/3/6/60/600 MA. D.C. 16K/160K/1.6/16 MEG Ω. -20 - + 63db. £7/10/0. P. & P. 3/-.



**MODEL TE-78 30,000 O.P.V.**  
0/3/15/60/300/600/1,200 v. D.C. 0/6/30/120/600/1,200 v. A.C. 0/30μA/3/30/300mA. 0/16K/160K/1.6M/16 Meg Ω. £5/10/- P. & P. 3/-.



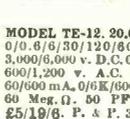**MODEL TE-80 20,000 O.P.V.**  
0/10/50/100/500/1,000 v. A.C. 0/5/25/50/250/500/1,000 v. D.C. 0-50μA. 2/50/500mA. 0/6K/60K/600K/6 meg. £4/17/6. P. & P. 3/-.



**MODEL TE-12 20,000 O.P.V.**  
0/0.6/6/30/120/600/1,200/3,000/6,000 v. D.C. 0/6/30/120/600/1,200 v. A.C. 0/60μA/6/60/600 mA. 0/6K/60K/6Meg/60 Meg Ω. 80 PFD £5/19/6. P. & P. 3/6.



**TE-51. NEW 20,000 Ω/VOLT MULTIMETER,** with overload protection and mirror scale, 0/6/60/120, 1,200 v. A.C. 0/3/30/60/300/600/3,000v. D.C. 0/60μA/12/300mA. D.C. 0/60K/6 meg. ohm. £2/6. P. & P. 2/6.



**MODEL PT-34 1,000 O.P.V.** 0/10/50/250/500/1,000V. a.c. and d.c. 0/1/100/500 mA. d.c. 0/100 K Ω 39/6. P. & P. 1/6.



**MODEL TE-10A 20k Ω/Volt 5/25/50/250/500/2,500 v. A.C. 10/50/100/500/1,000 v. A.C. 0/50μA/2.5 mA/250 mA D.C. 0/6K/6 meg. ohm. -20 to +22 dB. 104, 100 mid. 0.100-0.1 mid. 68/6. P. & P. 2/6.**



**LAFAYETTE 67 Range Super 50K Ω/V. Multimeter.** D.C. voltage 125mv-1000v. A.C. volts 1.5v-1000v. D.C. Current 25μA-10 Amp. Ohms 0-10 Meg Ω. D.B.-20 to +81 db. Overload protection. £12/10/- P. & P. 3/6.

**TRANSISTOR FM TUNER**



6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 9in. x 4in. x 2 1/2in. 3 I.F. stages. Double tuned discriminator, ample output to feed most amplifiers. Operates on 9 volt battery. Coverage 88-108 Mc/s. Ready built ready for use. Fantastic value for money. £26/7/6. P. & P. 2/6.

**SINCLAIR EQUIPMENT**

Z12. 12 watt amplifier 89/6. PZ4. Power supply Unit 89/6. STEREO 25. Pre-amplifier £9/19/6. Q.14 Speakers £7/19/6. Micromatic Radio Kit 40/6. Built 50/6. **NOW AVAILABLE IC10. 59/6 ALL POST PAID.**  
**SPECIAL OFFER**  
2 Z12 amps. PZ4 Power Supply, Stereo 25, Pre-amplifier ..... £22  
or with two Q.14 Speakers. .... £37  
**NEW SINCLAIR 2000 SYSTEM**  
35 watt Integrated Amplifier, £29. Carr. 5/-  
Self-powered FM Tuner, £25. Carr. 5/-.

**ECHO HS-606 STEREO HEADPHONES**



Wonderfully comfortable. Lightweight adjustable vinyl headband, 6ft. cable and stereo jack plug. 25-17,000 cps. 8 Ω Imp. 67/6. P. & P. 2/6.

**HOSIDEN HD4S 2-WAY STEREO HEADPHONES**




Each headphone contains a 2 1/2in. woofer and a 1in. tweeter. Built in individual level controls. 25-18,000 cps. 8 Ω Imp. with cable and stereo plug. £5/19/6. P. & P. 2/6.

**TRANSISTORISED TWO-WAY TELEPHONE INTERCOM**



Operative over amazingly long distances. Separate call and press to talk buttons. 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £8/19/6 pair. P. & P. 3/6.

**TE111 DECADE RESISTANCE ATTENUATOR**

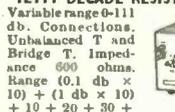

Variable range 0-111 db. Connections. Unbalanced T and Bridge T. Impedance 600 ohms. Range (0.1 db x 10) + (1 db x 10) + 10 + 20 + 30 + 40 db. Frequency: DC to 200 KHz (-3db). Accuracy: 0.05 db. + Indication dB x 0.01. Maximum input less than 4 watts (50 volts). Built in 600 Ω load resistance with internal external switch. Brand new £27/10/- P. & P. 5/-.

**CAR LIGHT FLASHERS**



Heavy duty light flasher employs a condenser discharge principle operating on electro mechanical relay. (As inset.) Housed in strong plastic case. Flashing rate between 60-120 per minute. 15 volt D.C. operation. Maximum load 6 amps. Size 2 1/2 in. dia. by 4in. Supplied brand new at a fraction of original cost. 6/8 each. P. & P. 2/6. (3 for 17/6. P. & P. 4/6.)

**RECORDING HEADS**

Cosmoord & track heads: Post extra.  
Record/Replay High Imp. .... 65/-  
Erase, Low Imp. .... 20/-  
Marriott & track heads. Post extra.  
Record/Playback, high Imp. .... 65/-  
Erase, low Imp. .... 20/-

**AMERICAN RECORDING TAPES**

3in. 225ft. L.P. Acetate 3/6  
3 1/2in. 600ft. T.P. Mylar. 10/-  
5in. 600ft. Std. plastic. 8/6  
American 6in. 900ft. L.P. acetate. 10/-  
tapes.  
Brand new and guaranteed.  
Discounts for quantities.  
Postage 2/-  
Over £3 post paid.  
7in. 1,800ft. L.P. acetate 15/-  
7in. 1,800ft. L.P. Mylar 25/-  
7in. 2,400ft. L.P. Mylar 25/-  
7in. 3,600 ft. T.P. Mylar 45/-

**MAXELL TAPE CASSETTES**

C60-10/3; C90-14/3; C120-19/6. Post extra.

**G.W.SMITH & CO. (RADIO) LTD**

All Mail Orders to -  
147, Church Street, London, W.2  
Tel: 01-262 6562 (Trade subject)  
3, LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204  
34, LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155  
311, EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387  
OPEN 9-6 MONDAY TO SATURDAY (EDGWARE ROAD 1/2 DAY THURSDAY)

# ELECTROVALUE

EVERYTHING BRAND NEW AND TO SPECIFICATION • LARGE STOCKS


## BARGAINS IN NEW TRANSISTORS

ALL POWER TYPES SUPPLIED WITH FREE INSULATING SETS

2N696	5/6	2N3707	4/-	BA102	9/-
2N697	5/6	2N3708	2/9	BC107	2/9
2N706	2/9	2N3709	3/-	BC108	2/6
2N1132	9/9	2N3710	3/3	BC109	2/9
2N1302	4/-	2N3711	3/11	BC147	4/3
2N1303	4/-	2N3904	7/6	BC148	4/3
2N1304	4/6	2N3906	7/6	BC149	4/3
2N1305	4/6	2N3731	23/-	BC153	10/-
2N1306	6/9	2N3820	25/6	BC157	11/-
2N1307	6/9	2N3325	10/6	BC158	3/9
2N1308	8/9	2N3794	3/3	BC158	3/6
2N1309	8/9	2N4286	3/3	BC159	3/9
2N1613	6/-	2N4289	3/3	BC167	2/6
2N1711	7/-	2N4291	3/3	BC168	2/3
2N2218	9/3	2N4292	3/3	BC169	2/6
2N2147	18/9	2N4410	4/9	BC177	6/3
2N2369A	6/9	2N5192	25/-	BC178	5/8
2N2646	10/9	2N5195	29/3	BC179	6/-
2N2924	4/3	40406	16/3	BD121	18/-
2N2925	5/3	40408	14/6	BD123	24/3
2N2926R	2/3	AC126	6/6	BF178	10/6
2N2926O	2/3	AC127	6/-	BFX29	10/9
2N2926Y	2/3	AC128	6/-	BFX85	8/3
2N2926G	2/6	AC176	11/-	BFX88	7/9
2N3053	5/6	ACY22	3/9	BFY50	4/6
2N3054	14/3	ACY40	4/-	BFY51	3/9
2N3055	16/6	AD140	19/-	BSX20	3/3
2N3391A	5/6	AD149	17/6	MJ480	21/-
2N3702	3/6	AD161	16/- pr.	MJ481	27/-
2N3703	3/3	AD162		MJ491	30/-
2N3704	3/9	AF118	16/6	P346A	5/9
2N3705	3/5	AF124	7/6	V405A	7/9
2N3706	3/3	AF127	7/-		

## PEAK SOUND AMPLIFIER KITS

The new Englefield Kits

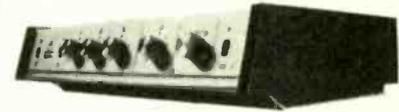

Build it  
12+12  
or  
25+25

Brilliant new styling and available in two forms:  
**STEREO 15 WATTS PER CHANNEL**  
Supplied in kit form with complete amplifier and pre-amplifier modules and power supply components. Output per channel into 15Ω —13 watts R.M.S. Price £38.4.0 Net

**STEREO 25 WATTS PER CHANNEL**  
Supplied in kit form with complete amplifier, pre-amplifier and regulated power supply modules. Output per channel into 15Ω —28 watts R.M.S. Price £58.15.0 Net

Specifications on these amplifiers in accordance with the Specifications in Guarantee published in Peak Sound advertisements.

**Inputs:**  
Magnetic, RIAA 3.5mV  
Ceramic 35mV  
Tape 100mV  
Radio 100mV  
Signal to noise ratios: Better than 60dB all inputs.

**ENGLEFIELD CABINET** to house either above assemblies (as illustrated) £6.0.0.  
Other Peak Sound Products as advertised.  
Mainline Kits as advertised.

## RESISTORS

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	100Ω-220KΩ	E12	18	16	15
C	1/8W	5%	4.7Ω-1MΩ	E24	2.5	2	1.75
C	1/4W	10%	4.7Ω-10MΩ	E12	2.5	1.75	1.5
C	1/2W	5%	4.7Ω-10MΩ	E24	3	2.25	2
MO	1/2W	2%	10Ω-1MΩ	E24	9	8	7
C	1W	10%	4.7Ω-10MΩ	E12	4	3.25	3
WW	1W	10% ± 1/20Ω	0.22Ω-3.3Ω	E12		15d. all quantities	
WW	3W	5%	12Ω-10KΩ	E12		15d. all quantities	
WW	7W	5%	12Ω-10KΩ	E12		15d. all quantities	

Codes: C = carbon film, high stability, low noise.  
MO = metal oxide, ElectroSil TR5, ultra low noise.  
WW = wire wound, Plessey.

Prices are in pence each for each ohmic value and power rating. (Ignore fractions of one penny on total resistor order.)

**Values:**  
E12 denotes series: 1, 1.2, 1.5, 1.8, 2.2, 2.7, 3.3, 3.9, 4.7, 5.6, 6.8, 8.2 and their decades.  
E24 denotes series: as E12 plus 1.1, 1.3, 1.6, 2, 2.4, 3, 3.6, 4.3, 5.1, 6.2, 7.5, 9.1 and their decades.

**NEW PLESSEY INTEGRATED CIRCUIT POWER AMPLIFIER TYPE SL403A.** Only 57/- each. Operates with 18V power supply. Sensitivity 20mV into 20MΩ, 3 watts into 7.5Ω. Supplied complete with application Data on orders for 2 or more.

**PE NOV. 69 STEREO AMPLIFIER KIT** less metalwork £11/18/- NET complete

**CARBON SKELETON PRE-SETS**  
Small high quality, type PR: Linear only: 100Ω, 220Ω, 470Ω, 1KΩ, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1MΩ, 2M2, 5M, 10MΩ vertical or horizontal mounting 1/- each

**S-DeCs: PUT AN END TO "BIRDS-NESTING".** Components just plug in. Saves valuable time. Use components again and again.  
S-DeC ... Only 30/6 post free  
Compact T-DeC, increased capacity, may be temperature-cycled.  
T-DeC ... only 51/- post free

**WAVECHANGE SWITCHES**  
1P 12W; 2P 6W; 3P 4W; 4P 3W—long spindles ... 4/9 each

**SLIDER SWITCHES**  
Double pole, double throw ... 3/- each

**MULLARD SUB-MIN ELECTROLYTICS C426 RANGE** ... Price 1/3 each  
Axial leads. Values (µF/V): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5/64; 6.4/6.4; 6.4/25; 8/4; 8/40; 10/2.5; 10/16; 10/64; 12.5/25; 16/40; 20/16; 20/64; 25/6.4; 25/25; 32/4; 32/10; 32/40; 32/64; 40/16; 40/2.5; 50/6.4; 50/25; 50/40; 64/4; 64/10; 80/2.5; 80/16; 80/25; 100/6.4; 125/4; 125/10; 125/16; 160/2.5; 200/6.4; 200/10; 250/4; 320/2.5; 320/6.4; 400/4; 500/2.5.

**LARGE CAPACITORS. ALL NEW STOCK**  
High ripple current types: 2000µF 25V 7/4; 2000µF 50V 11/4; 5000µF 25V 12/6; 5000µF 50V 21/11; 1000µF 100V 16/3; 2000µF 100V 28/9; 5000µF 70V 36/-; 5000µF 100V 58/3; 1000µF 50V 8/2; 2500µF 64V 15/5; 2500µF 70V 19/6.

**MEDIUM RANGE ELECTROLYTICS**  
Axial leads. Values (µF/V): 50/50 2/-; 100/25 2/-; 100/50 2/6; 250/25 2/6; 250/50 3/9; 500/25 3/9; 1000/10 3/-; 500/50 6/-; 1000/25 4/-; 1000/50 7/-; 2000/25 6/-.

**SMALL ELECTROLYTICS**  
Axial leads: 5/10, 10/10, 25/10, 50/10 1/- each  
25/25, 47/25, 100/10, 220/10 ... 1/3 each

**COMPONENT DISCOUNTS**  
10% on orders for components for £5 or more.  
15% on orders for components for £15 or more.  
(No discount on net items)

**POSTAGE AND PACKING**  
Free on orders over £2.  
Please add 1/6 if order is under £2.  
Overseas orders welcome: carriage charged at cost.

**COLVERN 3 WATT WIRE-WOUND POTENTIOMETERS:** 10Ω, 15Ω, 25Ω, 50Ω, 100Ω, 150Ω, 250Ω, 500Ω, 1KΩ, 1.5KΩ, 2.5KΩ, 5KΩ, 10KΩ, 15KΩ, 25KΩ, 50KΩ.  
Price ... only 5/6 each

**CARBON TRACK POTENTIOMETERS**  
Double wiper ensures minimum noise level. Long plastic spindles.  
Single gang linear ... 220Ω, 470Ω, 1K, etc. to 2.2MΩ 2/6  
Single gang log. ... 4K7, 10K, 22K, etc. to 2.2MΩ ... 2/6  
Dual gang linear ... 4K7, 10K, 22K, etc. to 1MΩ ... 8/6  
Dual gang log. ... 4K7, 10K, 22K, etc. to 2M2Ω ... 8/6  
Log/Anti-log. ... 10K, 47K, 1MΩ only ... 8/6  
Dual anti-log ... 10K only ... 8/6  
Any type with ½ amp double pole mains switch ... extra 2/3

**FETS n-channel**  
Low cost general purpose 2N5163, 25 volt ... only 5/- each  
Audio/r.f. Texas 2N3819 ... 9/- each  
Motorola 2N5459 (MPF105) ... 9/6 each

**30 WATT BAILEY AMPLIFIER COMPONENTS:**  
Transistors for one channel £7/5/6 list, with 10% discount ... only £6/11/-  
Transistors for two channels £14/11/- list, with 15% discount ... only £12/7/5  
Capacitors and resistors for one channel, list £2.  
Printed circuit board free with each transistor set.  
Complete unregulated power supply kit £4/17/6 mono or stereo, subject to discount.  
Complete regulated power supply kit £9/5/- subject to discount.  
Further details on application.

**MAIN LINE AMPLIFIER KITS AS ADVERTISED. PRICES NET AUTHORIZED DEALER**

**SINCLAIR IC.10 INTEGRATED CIRCUIT AMPLIFIER AND PRE-AMPLIFIER**  
This remarkable monolithic integrated circuit amplifier and pre-amplifier is now available for despatch from stock. It is the equivalent of 13 transistor/18 resistor circuit plus 3 diodes and the first of its kind ever. It is d.c. coupled and applicable to an unusually wide range of uses all of which are detailed in the manual provided with it.  
Sinclair IC.10 as advertised, post free ... 59/6 NET

# ELECTROVALUE

DEPT. WW.701, 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY,  
Hours: 9-5.30 daily; 1.0 p.m. Saturdays. Telephone: Egham 5533 (STD 0784-3)



**CURRENT RANGE OF BRAND NEW LT. TRANSFORMERS. FULLY SHROUDED (\*excepted) TERMINAL BLOCK CONNECTIONS. ALL PRIMARIES 220/240v.**

No.	SEC. TAPS	AMPS	PRICE	CARR.
1A	25-33-40-50	15	£10 10 0	12/6
1B	25-33-40-50	10	£7 12 6	9/6
1C	25-33-40-50	6	£6 15 0	9/6
1D	25-33-40-50	3	£4 0 0	7/6
2A	4-16-24-32	12	£7 2 6	8/6
2B	4-16-24-32	8	£5 7 6	8/6
2C	4-16-24-32	4	£3 12 6	7/6
2D	4-16-24-32	2	£2 7 6	5/-
3A*	25-30-35	40	£16 10 0	12/6
3B*	25-30-35	20	£10 5 0	10/6
3C*	25-30-35	10	£7 5 0	8/6
3D	25-30-35	5	£4 2 6	7/6
3E	25-30-35	2	£3 2 6	7/6
4A*	12-20-24	30	£13 0 0	12/6
4B	12-20-24	20	£8 5 0	9/6
4C	12-20-24	10	£4 5 0	8/6
4D	12-20-24	5	£3 12 6	7/6
5A	3-12-18	30	£9 12 6	9/6
5B	3-12-18	20	£7 2 6	8/6
5C	3-12-18	10	£4 5 0	7/6
5D	3-12-18	5	£2 17 6	7/6
6A	48-56-60	2	£3 12 6	6/6
6B	48-56-60	1	£2 12 6	6/6
7A*	6-12	50	£10 7 6	10/6
7B	6-12	20	£6 2 6	8/6
7C	6-12	10	£3 17 6	7/6
7D	6-12	5	£2 15 0	6/6
8A	12-24	1	£1 12 6	6/6
9A	17-32	8	£6 5 0	8/6
10A*	9-15	2	£1 9 6	6/6
11A*	6-3	15	£2 10 0	7/6
12A*	30-25-0-25-30	2	£3 12 6	6/6

**AUTO TRANSFORMERS**

240v.-110v. or 100v. Completely Shrouded fitted with Two-pin American Sockets or terminal blocks. Please state which type required.

Type	Watts	Approx. Weight	Price	Carr.
1	80	2½ lb	£1 19 6	5/6
2	150	4 lb	£2 12 6	6/6
3	300	6½ lb	£3 12 6	6/6
4	500	8½ lb	£5 2 6	8/6
5	1000	15 lb	£7 2 6	9/6
6*	1500	25 lb	£9 15 0	10/6
7*	1750	28 lb	£14 15 0	12/6
8*	2250	30 lb	£17 17 6	15/-

\*Completely enclosed in beautifully finished metal case fitted with two 2-pin American sockets, neon indicator, on/off switch, and carrying handle.

**WE REGRET WE HAVE TO INCREASE ALL THE ABOVE TRANSFORMER PRICES BY 10 PER CENT OWING TO THE HIGH COST OF COPPER.**

# Samson's

(ELECTRONICS) LTD.

9 & 10 CHAPEL ST., LONDON, N.W.1  
01-723-7851 01-262-5125

**HIGH GRADE POTTED CHOKES**

**BY FAMOUS MAKERS. NEW. GUARANTEED**  
20 H. 200 m/a. 30/-, P. & P. 7/6. 20 H. 180 m/a. 27/6. P. & P. 7/6. 15 H. 180 m/a. 25/-, P. & P. 7/6. 12 H. 200 m/a. 25/-, P. & P. 7/6. 10 H. 180 m/a. 22/6. P. & P. 7/6. 5 H. 300 m/a. 15/-, P. & P. 6/6. 30 H. 50 m/a. 25/-, P. & P. 7/6. 10 H. 75 m/a. 10/6. P. & P. 2/6. 50 H. 25 m/a. 8/6. P. & P. 2/-, 10 H. 120 m/a. 12/6. P. & P. 3/6. 15 H. 75 m/a. 12/6. P. & P. 3/6. 5 H. 100 m/a. 6/6. P. & P. 2/-, 0-75 H. 450 m/a. 15/-, P. & P. 4/6.

**PARMEKO NEPTUNE SERIES EHT TRANSFORMERS**

Pri Tapped 200-250v. Sec. 3 kV 58 m/a. 4v. 1-1 A. 10 kv r.m.s. test and 4v. 0-5 A. 75/-, P. & P. 10/-.

**GRESHAM POTTED TRANSFORMERS**

Pri Tapped 200-250v. Sec. 475-0-475v. 160 m/a. 215-0-215v. 60 m/a. 6-3v. 8-2 A. 6-3v. 5 A. 6-3v. 0-75 A. 5v. 3 A. 85/-, P. & P. 10/-.  
Pri Tapped 200-250v. Sec. 415-0-415v. 160 m/a. 165v. 155 m/a. 6-3v. 3 A. 6-3v. 1-6 A. 6-3v. 1-6 A. Sv. 2-8 A. 75/-, P. & P. 10/-.  
Pri Tapped 200-250v. Sec. 6-3v. 2-5 A. twice. 6-3v. 1-5 A. 6-3v. 1 A. 6-3v. 0-5 A. 17/6. P. & P. 4/6.  
Pri Tapped 200-250v. Sec. 27-0-27v. 0-3 A. 28-27-26-0-26-27-28v. 0-3 A. 6-3v. 1 A. 6-3v. 0-3 A. 6-3v. 0-6 A. 30/-, P. & P. 4/6.  
Pri Tapped 200-250v. Sec. 350-0-350v. 25 m/a. 6-3v. 1 A. 15/-, P. & P. 4/-.  
Pri Tapped 205-245v. Sec. 300v. 37 m/a. twice. 4v. 1 A. 4v. 0-3 A. 27/6. P. & P. 5/-.  
Pri Tapped 200-250v. Sec. Tapped 370-390-410v. 6 m/a. 10/-, P. & P. 3/-.  
Pri Tapped 200-245v. Sec. 300-0-300v. 66 m/a. 6-3v. 4A. 17/6. P. & P. 5/-.  
Pri Tapped Sec. 125v. 265 m/a. twice. 35/-, P. & P. 5/-.  
Pri Tapped 200-250v. Sec. 130v. 185 m/a. twice. 200v. 350 m/a. twice. 57/6. P. & P. 8/6.  
Pri Tapped 200-240v. Sec. 130v. 450 m/a. three times. 79/6. P. & P. 10/6.  
Pri Tapped 200-240v. Sec. 400v. 290 m/a. 75/-, P. & P. 10/6.  
Pri Tapped 200-250v. Sec. 45v. 25 m/a. 1v. 0-5 A. 12/6. P. & P. 4/6.  
Pri Tapped 200-240v. Sec. Tapped 760-700-40-20v. 50 m/a. 6-3v. 1-5 A. 25/-, P. & P. 5/-.

**ONE ONLY DAVENSET TRANSFORMER**  
Pri 400-415-440v. Sec. 270v. 1,500 watts. £12/10/- Carr. 15/-

**SMITHS SYNCHRONOUS MOTORS**  
A.C. 200-240v. 4 r.p.m. 3in. dia. Length of spindle 2½in. 22/6. P. & P. 2/6. As above, 1 r.p.m. 22/6. P. & P. 2/6.

**AMERICAN SYNCHRONOUS MOTORS**  
A.C. 230v. 50 cycles, 6 r.p.h. 2½in. dia. cog spindle. 12/6. P. & P. 2/6.

**VENNER SYNCHRONOUS MOTOR**  
A.C. 240v. 50 cycles, 40 r.p.m. 2½in. dia. Length of spindle ½in. 12/6. P. & P. 2/6.

**BERCO SLIDING RESISTORS**  
1004 ohms 1 amp. Single Tube Slider. Length 18ins. 45/-, P. & P. 7/6. 30 ohms 1-25 amps 5-T. Right angle geared drive. 19/6. P. & P. 5/6. 45+12 ohms 6-5/4 amps Single Tube Fixed Length 22ins. 25/-, P. & P. 7/6.

**G.P.O. 3000 TYPE RELAY (New and Boxed)**  
20,000 ohms Heavy Duty Contacts. 2CO, 2M. 15/-, P. & P. 2/-, 75 ohms Normal Contacts. 3M, 1B, 1CO. 6/-, P. & P. 2/-, 500 ohms Heavy Duty Contacts. 3M, 3B. 8/6. P. & P. 2/-, 150 ohms Heavy Duty Contacts. 2M. 6/-, P. & P. 2/-.

**SUNVIC TANK THERMOSTATS**  
Type TQP. 250v. 15 amps NC. 5 amps NO. 190-70 deg. F. Length of stem 10½ins. 25/-, P. & P. 5/-.

**AC 220-240v. SHADED POLE MOTORS**  
1,500 r.p.m. Double spindle. Length 0-9in. and 0-6in. Overall size 3x3½x2ins. New and Boxed. 10/6. P. & P. 3/6.

**BURGESS MICRO SWITCHES**  
Type MK 3BR/74. Norm closed or Norm open. ½in. raised Press Button. 8/6 for three. P. & P. 2/6.


**SIEMENS MINIATURE RELAY BASES**  
Type T.STV 24 C. 6 Contact pln. 4 Coil pins. Cartons of 20, inc. spring clips. 15/-, P. & P. 2/-.

**PULLEN SHUNT WOUND 24v. DC REVERSIBLE MOTORS**  
Type 610 H.P. 1/75 r.p.m. 3,500 Cont/R. New and boxed. 15/-, P. & P. 3/6.

**MAINS ISOLATION TRANSFORMERS**  
Pri tapped 240-220-110v. Sec. 240v. 1200 watts. Built into metal case with twin 13 amp Socket outlet, on/off switch, neon indicator and carry handle. £16.10.6. Carr. 15/-.

**GARDNER'S POTTED TRANSFORMERS**  
Pri Tapped 200-240v. Sec. 35v. 7-2 amps. conservatively rated. 57/6. Carr. 6/6.

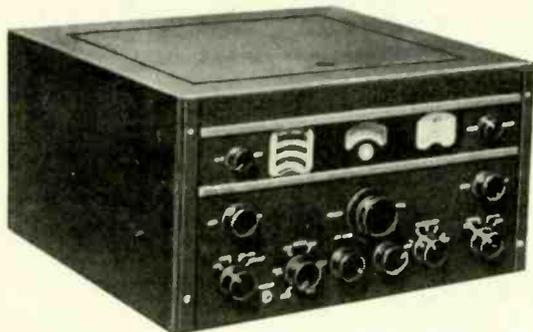**LATEST RELEASE OF RCA COMMUNICATION RECEIVERS AR88**



**BRAND NEW** and in original cases—A.C. mains input. 110V or 250V. Freq. in 6 bands 535 Kc/s-32 Mc/s. Output impedance 2.5-600 ohms. Complete with crystal filter, noise limiter, B.F.O., H.F. tone control, R.F. & A.F. variable controls. Price £87/10/- each, carr. £2.


Same model as above in secondhand cond. (guaranteed working order), from £45 to £60, carr. £2.

**\*SET OF VALVES:** new, £3/10/- a set, post 7/6; **SPEAKERS:** new, £3 each, post 10/-; **\*HEADPHONES:** new, £1/5/- a pair, 600 ohms impedance. Post 5/-.

**AR88 SPARES.** Antenna Coils L5 and 6 and L7 and 8. Oscillator coil L55. Price 10/- each, post 2/6. RF Coils 13 & 14; 17 & 18; 23 & 24; and 27 and 28. Price 12/6 each. 2/6 post. By-pass Capacitor K.98034-1, 3x0.05 mfd. and M.980344, 3x0.01 mfd., 3 for 10/-, post 2/6. Trimmers 95534-502, 2-20 p.f. Box of 3, 10/-, post 2/6. Block Condenser, 3x4 mfd., 600 v., £2 each, 4/- post. Output transformers 901666-501 27/6 each, 4/- post.

\* Available with Receiver only.

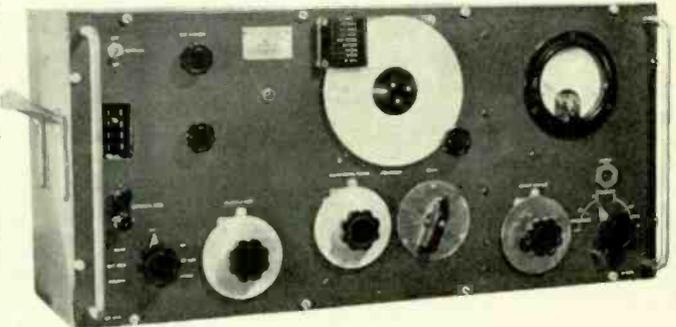S.A.E. for all enquiries. If wishing to call at Stores, please telephone for appointment.



**MARCONI SIGNAL GENERATORS TYPE TF-144G**

Freq. 85Kc/s-25Mc/s in 8 ranges. Incremental: +/— 1% at 1Mc/s. Output: continuously variable 1 microvolt to 1 volt. Output Impedance: 1 microvolt to 100 millivolts, 10 ohms 100mV-1 volt-52.5 ohms. Internal Modulation: 400 c/s sinewave 75% depth. External Modulation: Direct or via internal amplifier. A.C. mains 200/250V, 40-100 c/s. Consumption approx. 40 watts. Measurements: 19¼x12¼x10 in. The above come complete with Mains Leads, Dummy Aerial with screened lead, and plugs. As New, in Manufacturer's cases, £40 each. Carr. 30/- **DISCOUNT OF 10% FOR SCHOOLS, TECHNICAL COLLEGES, etc.**

**W. MILLS** 3-B TRULOCK ROAD, TOTTENHAM, N.17  
Phone: Tottenham 9213

**HRO RECEIVER.** Model 5T. This is a famous American High Frequency superhet, suitable for CW, and MCW, reception crystal filter, with phasing control. AVC and signal strength meter. Complete HRO 5T SET (Receiver, Set of 5 Coils & Power Unit) for £27/10/-, carr. 30/-.

**COMMAND RECEIVERS;** Model 6-9 Mc/s., as new, price £5/10/- each, post 5/-.

**COMMAND TRANSMITTERS,** BC-458: 5.3-7 Mc/s., approx. 25W output, directly calibrated. Valves 2 x 1625 PA; 1 x 1626 osc.; 1 x 1629 Tuning Indicator; Crystal 6,200 Kc/s. New condition—£3/10/- each, 10/- post. (Conversion as per "Surplus Radio Conversion Manual, Vol. No. 2," by R. C. Evenson and O. R. Beach.)

**AIRCRAFT RECEIVER ARR. 2:** Valve line-up 7 x 9001; 3 x 6AK5; and 1 x 12A6. Switch tuned 234-258 Mc/s. Rec. only £3 each, 7/6 post; or Rec. with 24 v. power unit and mounting tray £3/10/- each, 10/- post.

**RECEIVERS:** Type BC-348, operates from 24 v D.C., freq. range 200-500 Kc/s, 1.5-18 Mc/s. (New) £35.0.0 each; (second hand) £20.0.0 each, good condition, carr. 15/- both types.

**MARCONI RECEIVER 1475** type 88: 1.5-20 Mc/s, second-hand condition £10.0.0 each. New condition £25.0.0 each, carr. 15/-.

**RACAL EQUIPMENT:** Frequency Meter type SA20: £35 each, carr. £1. Frequency Counter type SA21: £65 each, carr. 30/-. Diversity Switching Unit type MA168: £35 each, post 10/-. Converter Frequency Electronic VHF Type SA.80 (for use with the SA.20): 25 Mc/s-160 Mc/s, £40 each, carr. £1.

**ROTARY CONVERTERS:** Type 8a, 24 v D.C., 115 v A.C. @ 1.8 amps, 400 c/s 3 phase, £8/10/- each, 8/- post. 24 v D.C. input, 175 v D.C. @ 40mA output, 25/- each, post 2/-.

**CONDENSERS:** 150 mfd, 300 v A.C., £7/10/- each, carr. 15/- 40 mfd, 440 v A.C. wkg., £5 each, 10/- post. 30 mfd, 600 v wkg. D.C., £3/10/- each, post 10/- 15 mfd, 330 v A.C. wkg., 15/- each, post 5/- 10 mfd, 1000 v, 12/6 each, post 2/6 10 mfd, 600 v, 8/6 each, post 5/- 8 mfd, 1200 v, 12/6 each, post 3/- 8 mfd, 600 v, 8/6 each, post 2/6 4 mfd, 3000 v wkg., £3 each, post 7/6 2 mfd, 3000 v wkg., £2 each, post 7/6 0.25 mfd, 2Kv, 4/- each, 1/6 post. 0.01 mfd. MICA 2.5 Kv. Price £1 for 5. Post 2/6. Capacitor: 0.125 mfd, 27,000v wkg. £3.15.0 each, 10/- post.

**AVO MULTIRANGE No. 1 ELECTRONIC TEST SET:** £25 each, carr. £1.

**OSCILLOSCOPE Type 13A,** 100/250 v. A.C. Time base 2 c/s.-750 Kc/s. Bandwidth up to 5 Mc/s. Calibration markers 100 Kc/s. and 1 Mc/s. Double Beam tube. Reliable general purpose scope, £22/10/- each, 30/- carr.

**COSSOR 1035 OSCILLOSCOPE,** £30 each, 30/- carr.

**COSSOR 1049 Mk. 111,** £45 each, 30/- carr.

**RELAYS:** GPO Type 600, 10 relays @ 300 ohms with 2M and 10 relays @ 50 ohms with 1M., £2 each, 6/- post. 12 Small American Relays, mixed types £2, post 4/-.

Many types of American Relays available, i.e., Sigma; Allied Controls; Leach; etc. Prices and further details on request 6d.

**GEARED MOTORS:** 24 v. D.C., current 150 mA, output 1 r.p.m., 30/- each, 4/- post. Assembly unit with Letcherbar Tuning Mechanism and potentiometer, 3 r.p.m., £2 each, 5/- post.

**Actuator Type SR-43:** 28 v. D.C. 2,000 r.p.m., output 26 watts, 5 inch screw thrust, reversible, torque approx. 25 lbs., rating intermittent, price £3 each, post 5/-.

**SYNCHROS:** and other special purpose motors available. British and American ex stock. List available 6d.

**TCS MODULATION TRANSFORMERS,** 20 watts, pr. 6,000 C.T., sec. 6,000 ohms. Price 25/-, post 5/-.

**AUTOMATIC PILOT UNIT Mk. 2.** This complex unit of diodes and valves, relays, magnetic clutches, motors and plug-in amplifiers, with many other items, price £7/10/-, £1 carriage.

**FOR EXPORT ONLY:** B.44 Trans-ceiver Mk. III. Crystal control, 60-95 Mc/s. **AMERICAN EQUIPMENT:** BC-640 Transmitter, 100-156 Mc/s., 50 watt output. For 110 or 230 v. operation. ARC 27 trans-ceivers, 28 v. D.C. input. Also have associated equipment. BC-375 Transmitter, BC-778 Dinghy transmitter, SCR-522 trans-ceiver. Power supply, PP893/GRC 32A; Filter D.C. Power Supply F-170/GRC 32A; Cabinet Electrical CY 1288/GRC 32A; Antenna Box Base and Cables CY 728/GRC; Mast Erector Kits, 1186/GRC; Directional Antenna CRD.6; Comparator Unit, CM.23; Directional Control CRD.6, 567/CRD and 568/CRD; Azimuth Control Units, 260/CRD. Test Set URM.44, complete with Signal Generator TS.622/U.

**SOLENOID UNIT:** 230 v. A.C. input, 2 pole, 15 amp contacts, £2/10/- each post 6/-.

**CONTROL PANEL:** 230 v. A.C., 24 v. D.C. @ 2 amps., £2/10/- each, carr. 12/6.

**AUTO TRANSFORMER:** 230-115 v.; 1,000 w. £5 each, carr. 12/6. 230-115 v.; 300VA, £3 each, carr. 10/-.

**OHMITE VARIABLE RESISTOR:** 5 ohms, 5½ amps; or 2.6 ohms at 4 amps. Price (either type) £2 each, 4/6 post each.

**POWER SUPPLY UNIT PN-12B:** 230 v. A.C. input, 395-0-395 v. output @ 300 mA. Complete with two x 9H chokes and 10 mfd. oil filled capacitors. Mounted in 19in. panel, £6/10/- each, £1 carr.

**TX DRIVER UNIT:** Freq. 100-156 Mc/s. Valves 3 x 3C24's; complete with filament transformer 230 v. A.C. Mounted in 19in. panel, £4/10/- each, 15/- carr.

ALL GOODS OFFERED WHILST STOCKS LAST IN "AS IS" CONDITION UNLESS OTHERWISE STATED

**POWER UNIT:** 110 v. or 230 v. input switched; 28 v. @ 45 amps. D.C. output. Wt. approx. 100 lbs., £17/10/- each, 30/- carr. **SMOOTHING UNITS** suitable for above £7/10/- each, 15/- carr.

**DE-ICER CONTROLLER MK. III:** Contains 10 relays D.P. changeover heavy duty contacts, 1 relay 4P, C/O. (235 ohms coil). Stud switch 30-way relay operated, one five-way ditto, D.C. timing motor with Chronometric governor 20-30 v., 12 r.p.m.; geared to two 30-way stud switches and two Ledex solenoids, 1 delay relay etc., sealed in steel case (4 x 5 x 7 ins.) £3 each, post 7/6.

**MODULATOR UNIT:** 50 watt, part of BC-640, complete with 2 x 811 valves, microphone and modulator transformers etc. £7/10/- each, 15/- carr.

**ADVANCE TEST EQUIPMENT:** TT1S Transistor Tester (CT472) £37/10/- each; VM77C Valve Voltmeter £40 each. Carr. 10/- extra per item.

**NIFE BATTERIES:** 4 v. 160 amps, new, in cases, £20 each, £1 10/- carr.

**FUEL INDICATOR Type 113R:** 24 v. complete with 2 magnetic counters 0-9999, with locking and reset controls mounted in a 3in. diameter case. Price 30/- each, postage 5/-.

**UNISELECTORS (ex equipment):** 5 Bank, 50 Way, 75 ohm Coil, alternate wipe, £2/5/- each, post 4/-.

**FREQUENCY METERS:** BC-221, meter only £30 each, BC-221 complete with stabilised power supply £35 each, carr. 15/-. LM13, 125-20,000 Kc/s., £25 each, carr. 15/-. TS.175/U, £75 each, carr. £1. TS323/UR, 20-450 Mc/s., £75 each, carr. 15/-. FR-67/U: This instrument is direct reading and the results are presented directly in digital form. Counting rate: 20-100,000 events per sec. Time Base Crystal Freq.: 100 Kc/s. per sec. Power supply: 115 v., 50/60 c/s., £100 each, carr. £1.

**CT.49 ABSORPTION AUDIO FREQUENCY METER:** freq. range 450 c/s-22 Kc/s., directly calibrated. Power supply 1.5 v.-22 v. D.C. £12/10/- each, carr. 15/-.

**CATHODE RAY TUBE UNIT:** With 3in. tube, colour green, medium persistence complete with nu-metal screen, £3/10/- each, post 7/6.

**APNI ALTIMETER TRANS./REC.,** suitable for conversion 420 Mc/s., complete with all valves 28 v. D.C. 3 relays, 11 valves, price £3 each, carr. 10/-.

TEST EQUIPMENT

<b>MARCONI</b>	TF-1274	VHF Bridge Oscillator	£75 each
	TF-1275	VHF Bridge Detector	£75 each
	TF-1067/1	Heterodyne Frequency Meter	£85 each
	TF-899	Valve Millivoltmeter	£35 each
	TF-978	VHF Admittance Bridge	£85 each
	TF-894A	Audio Tester	£55 each
	TF-329G	Circuit Magnification Meter	£45 each
	TF-428/2	Valve Voltmeter	£12/10/- each
	TF-428/1	Valve Voltmeter	£8/10/- each
	TF-726C	UHF Signal Generator	£65 each
	TF-934	Deviation Test Meter	£35 each
	6075A	Deviation Test Meter	£65 each
	TF-987/1	Noise Generator	£20 each
	TF-956	(CT.44) A.F. Absorption Wattmeter	£20 each
<b>FIRZ HILL</b>	V.200	Sensitive Valve Voltmeter	£35 each
	B.810	Incremental Inductance Bridge	£75 each
<b>SOLATRON</b>	CD-513	Oscilloscope	£45 each
	CD-513-2	Oscilloscope	£47/10/- each
	AW-553	Power Amplifier	£30 each
<b>AIRMEC</b>	Type 701	Signal Generator	£50 each
<b>PHILLIPS</b>	Type GM-6008	Valve Voltmeter	£35 each
<b>DAWE</b>	Type 402C	Megohm Meter	£12 each

**CANADIAN C52 TRANS/REC.:** Freq. 1.75-16 Mc/s on 3 bands. R.T., M.C.W. and C.W. Crystal calibrator etc, power input 12V. D.C., new cond., complete set £50. Used condition working order £25. Carr. on both types £2/10/- Transmitter only £7/10/- (few only) Carr. 15/- Power Unit for Rec., new £3/5/-. Used power units in working order £2/5/- Carr 10/-.

**AVOMETERS:** Model 47A, £10 each, 10/- post. Excellent secondhand cond. (meters only).

**DECADE RESISTOR SWITCH:** 0.1 ohm per step. 10 positions. 3 Gang, each 0.9 ohms. Tolerance ±1% £3 each, 5/- post. 90 ohms per step. 10 positions, total value 900 ohms. 3 Gang. Tolerance ±1% £3/10/- each, 5/- post.

**TELESCOPIC ANTENNA:** In 4 sections, adjustable to any height up to 20 ft. Closed measures 6 ft. Diameter 2 in. tapering to 1 in. £5 each + 10/- carr. Or £9 for two + £1 carr. (brand new condition).

**COAXIAL TEST EQUIPMENT: COAXSWITCH—**Mnfrs. Bird Electronic Corp. Model 72RS; two-circuit reversing switch, 75 ohms, type "N" female connectors fitted to receive UG-21/U series plugs. New in ctns., £6/10/- each, post 7/6. **CO-AXIAL SWITCH—**Mnfrs. Transco Products Inc., Type M1460-22, 2 pole, 2 throw. (New) £6/10/- each, 4/6 post. 1 pole, 4 throw, Type M1460-4. (New) £6/10/- each, 4/6 post.

**PRD Electronic Inc. Equipment: FREQUENCY METER:** Type 587-A, 0.250-1.0 KMC/SEC. (New) £75 each, post 12/6. **FIXED ATTENUATOR:** Type 130c, 2.0-10.0 KMC/SEC. (New) £5 each, post 4/-. **FIXED ATTENUATOR:** Type 1157S-1, (new) £6 each, post 5/-.

CALLERS BY TELEPHONE  
APPOINTMENT ONLY

W. MILLS

3-B TRULOCK ROAD, TOTTENHAM, N.17

Phone: Tottenham 9213

# 4! brings you a mountain of components at manufacturers' prices



The serious amateur should never be without this comprehensive price list and guide to semiconductors and electronic components from RCA, IR, SGS, Emihus, Semitron, Keyswitch, Plessey, Morganite, Litesold and others (together with manufacturers' application data) which you can buy direct from us at manufacturers' prices e.g. IN914 1/3d.  
 IN916 1/11d.  2N697 4/5d.  2N706 2/3d.  2N706A 2/9d.  2N929 5/8d.  
 2N1613 4/8d.  2N3011 9/1d.  2N3053 6/2d.  2N3055 15/9d.  3N140 15/3d.  BFY50 4/8d.  BFY51 3/9d.  BSY27 18/-  BSY95A 3/3d.  C407 4/6d.  CA3012 18/3d.  CA3014 25/6d.  CA3020 25/9d.  OA200 1/9d.  OA202 1/11d.

## Build the NEW Mainline Audio Amplifier kits - UP TO 70 WATTS

The result of the combined resources of SGS and RCA, these quasi circuits set new standards in quality and performance. Each kit is complete with circuit diagram, all semiconductors, resistors, capacitors and printed circuit board.

12A .....	£7. 0. 0.
25A .....	£8. 5. 0.
40A .....	£9. 0. 0.
70A .....	£10.10. 0.

Any two will make an outstanding stereo equipment.



To: Mainline Electronics Limited, Thames Avenue, Windsor, Berkshire

I enclose 4/-. Please send me your price list and guide

I am interested in ..... Amp Mainline Audio Amplifier Kits. Please send me full data

I am interested in receiving data on preamplifier & power supply kits

NAME \_\_\_\_\_ ADDRESS \_\_\_\_\_

(A member of the ECS Group of Companies)

ww170

# SUPER-BARGAIN STOCKTAKING SALE!!

Use form below for your order. CONDENSERS MUST BE ORDERED BY STOCK NUMBER ONLY.  
If any sale item is 'sold-out' when order received we shall substitute items of equal value.

## ELECTROLYTIC CAPACITORS

Stock No.	Capacity	Voltage	Price s. d.	No. Required	£ s. d.	Stock No.	Capacity	Voltage	Price s. d.	No. Required	£ s. d.
1	1 uf	6	4			42	16 uf	50 REV	2 0		
2	4 uf	25	4			43	16/16	275	2 0		
3	4 uf	4	4			44	16	275	1 0		
4	6 uf	6	4			45	350	12	1 9		
5	3 uf	25	4			46	20/4	275	1 0		
6	64 uf	9	4			47	250	50	2 0		
7	20 uf	6	4			48	500	25	1 6		
9	30 uf	15	6			49	400	15	1 0		
10	8 uf	12	4			50	400	2.5	1 3		
11	8 uf	6	4			51	64	275	1 9		
12	1 uf	350	6			52	32/32	350	2 6		
13	8/8/8	350	1 0			53	8/8/8	275	1 9		
14	50 uf	6	4			54	500	6	6 6		
16	32	150	9			55	64	275	1 3		
17	64	2.5	3			56	25	6	6 6		
18	100/200/200/50	275	7 6			57	100	9	3 6		
19	50/80	300	3 0			58	400	50	2 0		
21	24	275	1 0			59	400	30	1 6		
22	10	25	3			60	500	4	1 3		
23	125	2.5	3			61	150	30	1 6		
24	2	150	3			62	64/32/8	275	2 6		
25	16/32	350	2 6			64	40	6.4	3 3		
26	32	275	1 6			65	50	25	6 6		
28	75/75/75/75	150	2 6			66	250	50	1 9		
30	12.5	40	9			67	30	6	3 3		
31	640	2.5	3			68	100/100/50	275	5 0		
32	3,000	35	7 6			69	50/50/50	350	4 0		
33	3,000	15	3 0			70	40/40/20	275	2 0		
34	3,000	30	7 0			71	400	6.4	3 3		
35	250	70	2 0			72	320	10	3 3		
36	2,500	9	2 0			73	32/32	275	2 6		
38	750	12	1 9				+ 25	25			
39	100 uf	275	2 6								
40	30 uf	10	3								

Total:

## RESISTORS. 5% EXCELLENT QUALITY.

Tick the values required.

7/6d. per 100 of any one value.

2/- per dozen of any one value.

13 ohms	560 ohms	3.3 k ohm	10 k ohm	39 k ohm	91 k ohm	1.2 meg ohm	8.2 meg ohm
22 ohms	750 ohms	3.6 k ohm	16 k ohm	43 k ohm	130 k ohm	1.5 meg ohm	9.1 meg ohm
36 ohms	1 k ohm	4.3 k ohm	18 k ohm	47 k ohm	360 k ohm	1.8 meg ohm	10 meg ohm
47 ohms	1.5 k ohm	4.7 k ohm	22 k ohm	51 k ohm	430 k ohm	3.6 meg ohm	
91 ohms	1.8 k ohm	5.6 k ohm	24 k ohm	62 k ohm	470 k ohm	5.1 meg ohm	
220 ohms	2.2 k ohm	6.8 k ohm	27 k ohm	75 k ohm	560 k ohm	6.2 meg ohm	
470 ohms	2.4 k ohm	7.5 k ohm	30 k ohm	82 k ohm	620 k ohm	7.5 meg ohm	

or our selection (mixed) 6/6d. per 100.

Total:

## SILVER MICA/CERAMIC/POLYSTYRENE CONDENSERS

Available in following values. Tick those required

10/- per 100 of any one value.

3/- per dozen of any one value.

2 pf	5 pf	12 pf	25 pf	50 pf	80 pf	135 pf	180 pf	250 pf	680 pf	1,000 pf	2,500 pf
3.9 pf	6 pf	15 pf	27 pf	58 pf	82 pf	140 pf	190 pf	330 pf	800 pf	1,100 pf	2,700 pf
4 pf	8 pf	18 pf	30 pf	62 pf	100 pf	158 pf	200 pf	420 pf	820 pf	1,500 pf	3,000 pf
4.7 pf	10 pf	22 pf	39 pf	72 pf	125 pf	170 pf	240 pf	600 pf	900 pf	2,200 pf	6,200 pf

Total:

# COMPARE THESE PRICES!!

## MULLARD POLYESTER CONDENSERS

Capacity	Price	No.	Price
1,000 pf	3d. each	400V	
1,500 pf	3d. each		
1,800 pf	3d. each		
2,200 pf	3d. each		
.15 uf	6d. each	160V	
.22 uf	6d. each	160V	
.27 uf	6d. each	160V	
1 uf	1/- each	125V	

Total:

25% discount lots of 100 per type.  
50% discount lots of 1,000 per type.

## GANGED STEREO POTS. 250K 2/6d. each.

## SKELETON PRESETS. Mixed. 6/- dozen.

## VOLUME CONTROLS. 1/2 meg. 1 meg. with D.P. switch. 2/- each.

## TELEVISION REMOTE CONTROLS. Philips. Contain 11' 7-way cable, 1 double pot., 5 resistors, two condensers, 10/- each. (Cost £3/3/-.)

## THIN CONNECTING WIRE. 10 yds 1/-, 100 yds 7/6d., 1,000 yds. 50/-.

## CO-AXIAL CABLE. Black. 6d. yard, £1 50 yds.

## CRYSTAL MIKES. 10/- each.

## TRANSISTOR BARGAIN! THEY CAN'T GET ANY CHEAPER! !!!

P.N.P. Audio. Untested, unmarked. MAINLY O.K. 10/- per 100  
N.P.N. Silicon. R.F. types unmarked ALL USEABLE 10/- per 50  
POWER OUTPUT (Similar OC35) ALL TESTED 4/- each £2 dozen

## SILICON PLANAR TRANSISTORS. ALL TESTED. NO LEAKS OR SHORTS.

Gain of 20/50 6d. each, 50/100 9d. each, 100/200 1/- each.  
Transistors similar to OCP 71 (Light sensitive) 2/- each.

## THYRISTORS. 400 volt BTY 79 7/6d. each. SCR 51 (10 amp) £1 each.

RECTIFIERS. Latest type. All marked. 800 volt peak, 1 amp mean current type 1N4006. 2/6 each, 24/- dozen, £7/10/- 100. S.T.C. 3/4 (400 volt) 2/6 each, 24/- dozen, £7/10/- 100. BYZ 13 or 19 (6 amp) 2/6 each, 24/- dozen, £7/10/- 100.

## RECORDING TAPE GIVE-AWAY!

ALL BRITISH MADE, BEST QUALITY. 5" 600' 7/3d. 5 1/2" 900' 9/-, 7" 1,200' 12/-, 3" 'odd-ends'—may be standard, long or double play—but minimum 150'—2/3d.

MAINS DROPPER TYPE RESISTORS. Hundreds of types from .7 ohm upwards. 1 watt to 50 watts. A large percentage of these are Multi-tapped droppers for radio/television. Owing to the huge variety these can only be offered "assorted", 10/- per dozen.

GIANT SELENIUM SOLAR CELLS. Last few to clear at half price! Circular, 67 mm. diameter 5/- each. 50 mm. x 37 mm. 3 for 10/-.

## RECORD PLAYER CARTRIDGES

ACOS GP67/2 15/- (Mono) GP94/1 30/- (Stereo, ceramic)  
ACOS GP91/3 20/- (Compatible) ACOS GP93/1 with diamond needle 32/6d.  
ACOS GP93/1 25/- (Stereo) ACOS GP94/1 with diamond needle 37/6d.

## TRANSISTORISED FLUORESCENT LIGHTS. 12 VOLT

8 watt 12" tube, Reflector type 59/6 15 watt 18" tube, Batten type 79/6  
Complete with tube. Postage 3/-

## TRANSISTORISED SIGNAL INJECTOR KIT .. .. . 10/-

## TRANSISTORISED SIGNAL TRACER KIT .. .. . 10/-

## TRANSISTORISED REV. COUNTER KIT (CAR) .. .. . 10/-

## VERO-BOARD

2 1/2" x 1" x .15	.. .. . 1/3	17" x 3 1/2" x .15	.. .. . 14/8
3 1/2" x 2 1/2" x .15	.. .. . 3/3	3 1/2" x 2 1/2" x .1	.. .. . 4/2
3 1/2" x 2 1/2" x .15	.. .. . 3/11	3 1/2" x 3 1/2" x .1	.. .. . 4/9
5" x 2 1/2" x .15	.. .. . 3/11	5" x 2 1/2" x .1	.. .. . 4/7
5" x 3 1/2" x .15	.. .. . 5/6	5" x 3 1/2" x .1	.. .. . 5/6
17" x 2 1/2" x .15	.. .. . 11/-		

Spot Face Cutter 7/6d. Pin Insert Tool 9/6d. Terminal Pins 3/6d. for 36. Spot Face Cutter and 5 2 1/2" x 1" boards 9/9d.

These prices cannot be repeated. Order now. Don't forget to add your name and address!  
Please include suitable amount to cover post and packing. Minimum 2/-.

**G. F. MILWARD, DRAYTON BASSETT, near TAMWORTH, STAFFS. Phone: TAMWORTH 2321**

# BETTER BARGAINS SERVICE FROM T.R.S.

## Amplifier Kits

Styled and kitted by T.R.S., using quality components, including valves or transistors and excellent instructions. Backed by T.R.S. service.

**MULLARD 5-10.** Mono. Basic kit (requires pre-amp or passive controls £2 extra.) Input Sensitivity—40 mV; Response 20Hz-15KHz + 1dB; Output 10 watts R.M.S. at 3 or 15 ohms. KIT £10.10.0; BUILT £13.0.0 (Carr. either, 7/6).

**MULLARD 2-VALVE PRE-AMP** with switching for 5 inputs; bass/treble/volume controls, etc. Sensitivity at Input—4mV max. to 330 mV into 80K-1 Megohm; Response 20-25,000 Hz +1dB. KIT £6.19.6; BUILT £9.10.0 (Carr. either, 5/6).

**MULLARD 10-10 STEREO AMPLIFIER.** Input sensitivity—210 mV per ch.; Response 12 Hz—35KHz + 3dB; 10 watts R.M.S. output per channel into 3 or 15 ohms. KIT £18.10.0; BUILT £22.10.0 (Carr. either, 12/6).

As above, less controls and panel. Kit £17.0.0; Built £21.0.0 (2+2 pre-amp. essential).


**2+2 STEREO PRE-AMP** similar to Mullard 2-valve pre-amp, but doubled with gang controls and balance. BUILT £13.19.6 (Carr. 7/6).

**T.R.S. 4+4 STEREO AMP**  
Low cost transistor amplifier based on Mullard modules. 4+4 watts output. For B-15 ohm speakers. Input switching, etc. Bass and treble controls. Simple module assembly. Amp and pre-amp with front panel and knobs.

Kit £7.19.6 (Carr. 3/6); Teak sided cabinet £1.17.6 (Carr. 2/6); 24V. Power pack £2.5.0 (Carr. 2/6); Complete kit inc. DIN plugs and sockets £12.10.0 (Carr. 7/6).
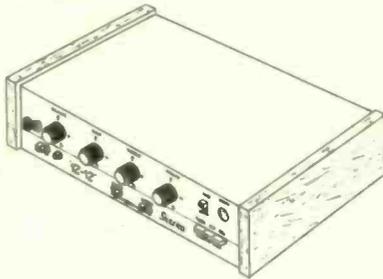
## THE NEW T.R.S. P.W. 12-12

T.R.S. have produced their own kit version of this outstandingly good combined stereo amp and pre-amp. It conforms closely to Practical Wireless's excellent circuit but is styled for a flatter, more conventional cabinet which will be shortly available. Kit includes two-tone front panel and control knobs.



Complete Kit of parts less cabinet (carr. 7/6) **£24.10**

Inputs—Mag. P.U. (R.I.A.A.) 2.5mV into 68 Kohms; Ceramic—Radio: Response—20Hz to 30KHz + 1dB. Output—12 watts per ch. R.M.S. into 15 ohms.

Power/Amp/Pre-amp Kits available separately.

**VINAIR**—Latest I.C.I. Cabinet and Speaker covering. Mottled Light-Grey, Off-White, Fawn, Black, etc., 2/6 per sq. ft. Multiple 1.6 in. cut. 27/6 per yd. Maximum width 48 in.

Send 1/- for Samples—Refundable.  
**BONACOUST**—Speaker Cabinet Acoustic Wadding (as used by leading Hi-Fi Speaker mfrs.), 18 ins. wide. Any length cut. 2/6 per ft.; 7/- per yard

**ENAMELLED COPPER WIRE**  
New 2 oz. reel prices  
14g-20g. 3/-; 22g-28g. 3/6; 30g-34g. 4/3; 36g-38g. 4/9; 39g-40g. 5/-.

Other gauges quoted for.  
**TINNED COPPER WIRE**  
16g-22g. 4/6 per 2 oz.

**EXCLUSIVE T.R. TAPE BARGAIN**  
Professional quality full frequency Mylar Tape by famous mfr. Attractively presented in coloured simulated leather wallets with space for spare reel.  
5 in. 900 ft. 12/6 5 1/2 in. 1200 ft. 17/6  
7 in. 1200 ft. 17/6 7 1/2 in. 1800 ft. 22/6  
Post and packing 1/6 per reel, plus 6d. each for extra reels.

**VEROBOARD**—All standard sizes stocked.  
2 1/2 x 3 1/2, 3/-; 2 1/2 x 5, 3/8; 3 1/2 x 3 1/2, 3/9;  
3 1/2 x 5, 5/2; 17 x 2 1/2, 12/6; 17 x 3 1/2, 15/-.  
Accessories—Term Pins, 1/- doz., 3/- pkt. Face Cutter, 7/3. Pin inserting tool 9/6.  
"CIR-KIT"—Adhesive copper strip 5 ft. by 1/16 in. spool 2/-

**PLUGS AND SOCKETS**  
Phono plugs, 1/-; sockets, 1/-, twin, 1/6  
DIN 5-pin plugs, 3/-; 5-pin sockets, 1/6;  
3-pin plugs, 3/3; 3-pin sockets, 1/6.

**VOLUME CONTROLS**  
1 1/2 in. dia. Long Spindles. Famous make. All values 5000 ohms-2 Megohms. Guaranteed 12 months.

Log or Linear tracks  
Less Sw. 3/6; DP Sw. 5/-  
ditto Centre Tapped 1 Megohm Log. 1 Megohm  
Twin Ganged Stereo controls 1 1/2 in. dia. Long Spindles.

All values 5000 ohms to 2 Megohms. Less Sw. Each 8/6  
ditto 100K to 2 Megohms  
With DP Sw. Each 10/6

**STEREO BALANCE CONTROLS**  
Log/Anti-Log 5K, 10K, 1/2 Meg., 1 Meg., 2 Meg. Each 9/6

**RESISTORS**  
Full Range 10 ohms-10 Megohms. (Midget type, modern ratings.)  
10% 1w, 1w, 4d; 1w, 6d.  
20% 1w, 8d; 2w, 1/-

5% Hi Stab (Cracked Carbon) all pref. values.  
10 ohms-1 Meg. 1w, 6d.; 1w, 6d.  
ditto 10% 3w, 5d; 1w, 6d.

1% Hi Stab 1w, 2/- (10 ohms-100 ohms, 2/3).  
**SKELETON PRE-SETS** for P/circuit use. 100 ohms-2.5 Meg., 2/-.

## GRAMO UNITS, PLINTHS, ETC.

**GARRARD SP.25 Mk. II**  
10 1/2 in. die-cast t/table, cueing device and counterbalance. Less cartridge. In maker's carton £12.7.6 (Carr. 7/6)

**GARRARD LM.2025**  
With latest stereo cartridge and lift control £10.19.6 (Carr. 7/6)

**PLINTHS**  
Garrard WB.1 £3.7.6 (Carr. 5/-)

**SINCLAIR PRODUCTS AS ADVERTISED**

Also T.R.S. 6-valve AM/FM Tuner Kit, £12.10.0 (Carr. 7/6). T.R.S. FM Transistor Tuner, parts £15.15.0 (Carr. 7/6).

Garrard Clearview Cover SCP.1 £3.5.0 (Carr. 4/6)  
Garrard Scandinavian type plinth and cover £5.5.0 (Carr. 5/-)

**CARTRIDGES**  
When bought together with playing units. Decca Deram, £5.5.0; BSR TC8/H (Stereo compatible), 25/-; BSR Stereo TC.85, 28/6; Sonotone 9TA/HC, with diamond 60/-; Acos GP.93-1, 30/-.

**T.R.S. FOR TRANSFORMERS.**  
Mains and output supplied to spec. for single or short production runs. Also comprehensive service in replacement line O/P transformers. Enquiries invited. S.A.E. from private individuals please.

# T.R.S. RADIO COMPONENT SPECIALISTS



70 BRIGSTOCK RD., THORNTON HEATH, SURREY

Open Saturday all day.  
Wednesday 1 p.m.

Next to Thornton Heath Station (S.R.)

Phone: 01-684 2188

# Buying a scope

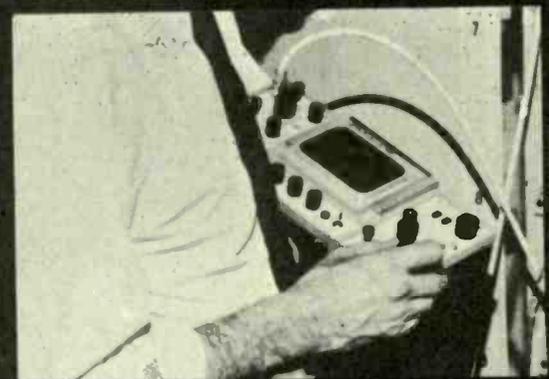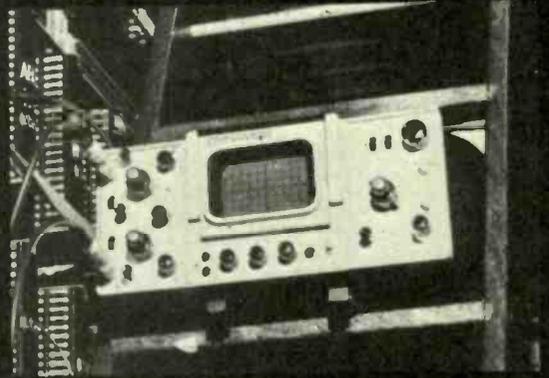

# First ask DYNAMCO

Save yourself time by talking about your applications (PCM, TV, pulse, HF, etc) to our specialist engineers. If we can't meet your requirements from our own extensive range, then we'll tell you who can. Call Chertsey 2636 — and ask for Barrie Newman.

# The scope specialists

World Wide Sales & Service




DYNAMCO

Dynamco Limited Hanworth Lane Chertsey Surrey England

# VALVES

CY31 7/-	PIA4 6/6	6K80T 7/3	8K200 14/-
DAP96 7/9	PL-500 14/8	8L2 14/8	8L6A 9/6
DF96 7/8	PL009 30/-	6P25 11/-	6B4 7/-
DL96 7/6	PX4 14/-	6B47GT 6/6	6B47GT 6/-
DL92 6/6	PX25 12/8	6B47GT 6/-	6B47GT 6/-
DM70 6/6	PY33 12/-	6B47GT 6/-	6B47GT 6/-
DM71 7/6	PY80 8/6	6B47GT 6/-	6B47GT 6/-
DY86 6/6	PY81 8/6	6B47GT 6/-	6B47GT 6/-
DY87 6/6	PY82 8/6	6B47GT 6/-	6B47GT 6/-
DY802 9/9	PY83 7/-	6B47GT 6/-	6B47GT 6/-
EABC80 6/6	PY88 7/6	6B47GT 6/-	6B47GT 6/-
EAF42 10/-	PY800 9/6	6B47GT 6/-	6B47GT 6/-
EBF91 2/-	PY801 9/6	6B47GT 6/-	6B47GT 6/-
EBC31 6/6	PY802 13/8	6B47GT 6/-	6B47GT 6/-
EBC41 10/6	QQV03 10/-	6B47GT 6/-	6B47GT 6/-
EBC81 6/6	QQV05 10/-	6B47GT 6/-	6B47GT 6/-
EBC82 6/6	QQV06 40/-	6B47GT 6/-	6B47GT 6/-
EBC83 6/6	QQV06-40A	6B47GT 6/-	6B47GT 6/-
EBC84 6/6	R10 100/-	6B47GT 6/-	6B47GT 6/-
EBC85 6/6	R10 17/6	6B47GT 6/-	6B47GT 6/-
EBC86 6/6	R17 8/-	6B47GT 6/-	6B47GT 6/-
EBC87 6/6	R19 7/6	6B47GT 6/-	6B47GT 6/-
EBC88 6/6	8TV280/80	6B47GT 6/-	6B47GT 6/-
EBC89 6/6	U25 14/6	6B47GT 6/-	6B47GT 6/-
EBC90 6/6	U26 14/6	6B47GT 6/-	6B47GT 6/-
EBC91 6/6	U27 8/-	6B47GT 6/-	6B47GT 6/-
EBC92 6/6	U191 14/-	6B47GT 6/-	6B47GT 6/-
EBC93 6/6	U201 11/6	6B47GT 6/-	6B47GT 6/-
EBC94 6/6	U201 20/-	6B47GT 6/-	6B47GT 6/-
EBC95 6/6	UABC80 6/6	6B47GT 6/-	6B47GT 6/-
EBC96 6/6	UAC42 10/6	6B47GT 6/-	6B47GT 6/-
EBC97 6/6	UAC43 11/6	6B47GT 6/-	6B47GT 6/-
EBC98 6/6	UBF80 7/-	6B47GT 6/-	6B47GT 6/-
EBC99 6/6	UBF89 7/-	6B47GT 6/-	6B47GT 6/-
EBC100 6/6	UCF80 10/-	6B47GT 6/-	6B47GT 6/-
EBC101 6/6	UCH42 12/6	6B47GT 6/-	6B47GT 6/-
EBC102 6/6	UCH81 7/-	6B47GT 6/-	6B47GT 6/-
EBC103 6/6	UCL82 7/6	6B47GT 6/-	6B47GT 6/-
EBC104 6/6	UCL83 12/-	6B47GT 6/-	6B47GT 6/-
EBC105 6/6	UF41 9/6	6B47GT 6/-	6B47GT 6/-
EBC106 6/6	UF80 7/3	6B47GT 6/-	6B47GT 6/-
EBC107 6/6	UF89 6/8	6B47GT 6/-	6B47GT 6/-
EBC108 6/6	UL44 6/6	6B47GT 6/-	6B47GT 6/-
EBC109 6/6	UL44 6/6	6B47GT 6/-	6B47GT 6/-
EBC110 6/6	UL44 6/6	6B47GT 6/-	6B47GT 6/-
EBC111 6/6	UL44 6/6	6B47GT 6/-	6B47GT 6/-
EBC112 6/6	UL44 6/6	6B47GT 6/-	6B47GT 6/-
EBC113 6/6	UL44 6/6	6B47GT 6/-	6B47GT 6/-
EBC114 6/6	UL44 6/6	6B47GT 6/-	6B47GT 6/-
EBC115 6/6	UL44 6/6	6B47GT 6/-	6B47GT 6/-
EBC116 6/6	UL44 6/6	6B47GT 6/-	6B47GT 6/-
EBC117 6/6	UL44 6/6	6B47GT 6/-	6B47GT 6/-
EBC118 6/6	UL44 6/6	6B47GT 6/-	6B47GT 6/-
EBC119 6/6	UL44 6/6	6B47GT 6/-	6B47GT 6/-
EBC120 6/6	UL44 6/6	6B47GT 6/-	6B47GT 6/-
EL34 10/6	1X2A 7/6	6B47GT 6/-	6B47GT 6/-
EL41 11/6	1X2B 7/6	6B47GT 6/-	6B47GT 6/-
EL42 10/6	3D4 3/-	6B47GT 6/-	6B47GT 6/-
EL84 4/9	3Q4 7/6	6B47GT 6/-	6B47GT 6/-
EL85 8/6	3B4 6/9	6B47GT 6/-	6B47GT 6/-
EL86 8/6	3V4 8/-	6B47GT 6/-	6B47GT 6/-
EL90 8/6	5B254M36/-	6B47GT 6/-	6B47GT 6/-
EL91 5/6	5B255M3	6B47GT 6/-	6B47GT 6/-
EL95 7/6	5R4G Y 10/6	6B47GT 6/-	6B47GT 6/-
EL900 12/-	5U4G 5/6	6B47GT 6/-	6B47GT 6/-
EL903 17/-	5V4G 7/6	6B47GT 6/-	6B47GT 6/-
EM31 5/6	5Y3GT 6/-	6B47GT 6/-	6B47GT 6/-
EM80 7/6	6Z4 14/-	6B47GT 6/-	6B47GT 6/-
EM84 7/6	6Z4G 7/6	6B47GT 6/-	6B47GT 6/-
EM87 11/6	6AB7 4/6	6B47GT 6/-	6B47GT 6/-
EY81 8/6	6AC7 3/-	6B47GT 6/-	6B47GT 6/-
EY86 7/6	6AH6 11/6	6B47GT 6/-	6B47GT 6/-
EY88 8/6	6AK5 5/6	6B47GT 6/-	6B47GT 6/-
EZ41 8/6	6AL5 3/-	6B47GT 6/-	6B47GT 6/-
EZ80 5/6	6AL5W 7/-	6B47GT 6/-	6B47GT 6/-
EZ81 6/6	6AM6 5/-	6B47GT 6/-	6B47GT 6/-
EZ82 6/6	6AM6 3/-	6B47GT 6/-	6B47GT 6/-
EZ83 10/6	6AN5 20/-	6B47GT 6/-	6B47GT 6/-
EZ84 27/6	6AN5 10/-	6B47GT 6/-	6B47GT 6/-
EZ85 32/6	6AQ5 6/-	6B47GT 6/-	6B47GT 6/-
EZ86 25/6	6AQ5W 9/-	6B47GT 6/-	6B47GT 6/-
EZ87 25/6	6B2G 5/-	6B47GT 6/-	6B47GT 6/-
EZ88 25/6	6B6 8/6	6B47GT 6/-	6B47GT 6/-
EZ89 25/6	6B6Q 6/9	6B47GT 6/-	6B47GT 6/-
EZ90 25/6	6B7 16/-	6B47GT 6/-	6B47GT 6/-
EZ91 25/6	6B7W 18/-	6B47GT 6/-	6B47GT 6/-
EZ92 25/6	6B7W 13/-	6B47GT 6/-	6B47GT 6/-
EZ93 25/6	6C4 5/9	6B47GT 6/-	6B47GT 6/-
EZ94 25/6	6C5 4/-	6B47GT 6/-	6B47GT 6/-
EZ95 25/6	6C6 4/-	6B47GT 6/-	6B47GT 6/-
EZ96 25/6	6C6B 7/-	6B47GT 6/-	6B47GT 6/-
EZ97 25/6	6C6L 9/9	6B47GT 6/-	6B47GT 6/-
EZ98 25/6	6D6 3/-	6B47GT 6/-	6B47GT 6/-
EZ99 25/6	6E8 9/-	6B47GT 6/-	6B47GT 6/-
EZ100 25/6	6E8W 13/-	6B47GT 6/-	6B47GT 6/-
EZ101 25/6	6F23 15/-	6B47GT 6/-	6B47GT 6/-
EZ102 25/6	6F3 20/-	6B47GT 6/-	6B47GT 6/-
EZ103 25/6	6H6M 3/-	6B47GT 6/-	6B47GT 6/-
EZ104 25/6	6J4WA 12/-	6B47GT 6/-	6B47GT 6/-
EZ105 25/6	6J5 7/-	6B47GT 6/-	6B47GT 6/-
EZ106 25/6	6J5GT 7/-	6B47GT 6/-	6B47GT 6/-
EZ107 25/6	6J6 6/6	6B47GT 6/-	6B47GT 6/-
EZ108 25/6	6J7 8/-	6B47GT 6/-	6B47GT 6/-
EZ109 25/6	6J7M 8/-	6B47GT 6/-	6B47GT 6/-
EZ110 25/6	6K6GT 8/-	6B47GT 6/-	6B47GT 6/-
EZ111 25/6	6K7 6/6	6B47GT 6/-	6B47GT 6/-
EZ112 25/6	6K7G 2/-	6B47GT 6/-	6B47GT 6/-
EZ113 25/6	6K8 4/-	6B47GT 6/-	6B47GT 6/-

## MARCONI TEST EQUIPMENT

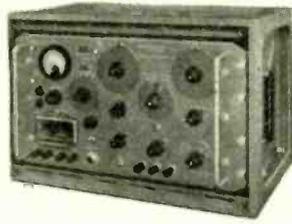

**VALVE VOLTMETER TYPE TF 958.** Measures AC 100mV; 20 c/s to 100 Mc/s, DC 50mV to 100V, multiplier extends ac range to 1.5kV. Balanced input and centre-zero scale for DC. AC up to 100MHz. £32.10.0.

**PRECISION VHF FREQUENCY METER TYPE 183.** 20-300 Mc/s with accuracy 0.03% and 300-1,000 Mc/s with accuracy 0.3%. Additional band on harmonics 5.0-6.25 Mc/s with accuracy + -2x10<sup>-4</sup>. Incorporating calibrating quartz 100 kc/s + -5x 10<sup>-8</sup> 120/220V. A.C. mains. £85. Carr. £2. 4, 5 and 8 bank 25 way uniselectors, 24V, guaranteed perfect, £3.15.6; £4.10.0; £6.17.6 respectively.

**FOR EXPORT ONLY**  
53 TRANSMITTERS. All spares available. COLLINS TCS. Complete installations and spare parts. 62 WIRELESS SETS. Complete installations and spare parts. P.S.U. for C42 & C45 12v and 24v R.C.A. TRANSMITTERS ET 4336. Complete installations and all spares. BC 610E & I TRANSMITTERS. Complete installations and all spares. No. 19 WIRELESS SETS. H.P. SETS and all spares R.210 RECEIVERS with all necessary accessories.  
**PYE RANGER F.M. MOBILE RADIO TELEPHONE.** Transmitter output 7-10W; double superhet receiver, 12v DC positive or negative earth. Full details and specification on request.

**IMPEDANCE BRIDGE TYPE TF 369 (No. 5).** Measures L & C at 80Hz, 1kHz, 10kHz. Ranges—L: 1µH-100H. C: 1mF-100µF. R: 0.1ohms-100ohms. Bridge volts monitored and variable. Automatic detector sensitivity control. £105. Carriage 30/-.

**DISTORTION FACTOR METER TYPE TF 142E.** Frequency range: 100-8,000Hz in four ranges. Distortion range: 0.05 to 50%. Input impedance 600Ω, attenuation 0-60db continuously variable. Sensitivity 1mV. £42.10.0. Carriage 20/-.

**FM DEVIATION METER TYPE TF 791B.** Frequency range: 4-250MHz, deviation 1-75kHz. Specification and price on application.

**PULSE GENERATOR TYPE TF 675F.** Repetition frequency: 50Hz to 50kHz. Pulse duration: 0.15 to 100µ sec; built in 0.1 and 0.5µ sec delay lines. £40.10.0. Carriage 20/-.

**SIGNAL GENERATOR TF 801/A.** 10-300 Mc/s. in 4 bands. Internal at 400 c/s. 1 kc/s. External 50 c/s to 10 kc/s. Output 0-100 db below 200 mV from 75 ohms source. £85. DITTO but 801/A/I with additional high level output. £89. Both P. & P. 20/-, including necessary connectors, plugs, and instruction manual.

**CIRCUIT MAGNIFICATION METER TYPE TF 329F.** Frequency range: 50kHz to 50MHz. Magnification 10 to 500 Q. Tuning Capacitor: 40 to 450pF with ±3pF vernier. Fully overhauled and calibrated. £70. Carriage 30/-.

**TF 899 VALVE VOLTMETER, 10mV to 2V. £17.10.0. Carriage 30/-.**

**F.M. DEVIATION METER TF 934, £57.10.0. Carriage 30/-.**  
**VIDEO OSCILLATOR TF 885A & 885A/I, £55 and £85 resp. Carr. 30/-.**

**SPARES FOR AR.88D. RECEIVERS.** Ask for your needs from our huge selection.

**29/41FT. AERIALS** each consisting of ten 3ft., 7in. dia. tubular screw-in sections. 11ft. (6-section) whip aerial with adaptor to fit the 7in. rod, insulated base, stay plate and stay assemblies, pegs, reamer, hammer, etc. Absolutely brand new and complete ready to erect, in canvas bag, £3/9/6. P. & P. 10/6.

**HARNES "A" & "B"** control units, junction boxes, headphones, microphones, etc.

**FIELD TELEPHONE TYPE "F"** Housed in portable wooden cases. Excellent for communication in and outdoors for up to 10 miles. Pair including batteries, fully tested. £6.10.0, or with 220 yds field cable in drum £7.10.0.

**END OF RANGE ITEMS** in 'as seen' condition: CR-£10; H.R.O.—£10; Coils at 15/-; TF 144 Signal Generator (Rack Models) £20; Furzhill VTVM 10mV to 100V—£15.

## HEWLETT-PACKARD TEST EQUIPMENT


**MODEL 524B ELECTRONIC COUNTER WITH MODEL 525B PLUG IN UNIT.** Basic counter measures frequencies from 10Hz to 10MHz and time from 0 to 10 kHz. Automatic positioning of decimal point, eight place registration. Full self check facility from built in frequency standards. Plug in unit extends frequency range of basic counter to 100 to 220MHz. Full specification and price on request.

**MODEL 400D VALVE MILLIVOLT-METER.** Voltage range: 1mV to 300v F.S.D. in 12 ranges. Frequency range: 10Hz to 4MHz. Input impedance 10MΩ and 15pF. Accuracy 2%. £38.10.0. Carriage 12/-.

**MODEL 430C MICROWAVE POWER METER.** Power range: 0.1 to 10mW F.S.D. in five ranges, also calibrated in DBM from -20 to +10. Frequency range: 10MHz to 'R' Band, depending on Bolometer mount. £58.10.0. Carriage 30/-.
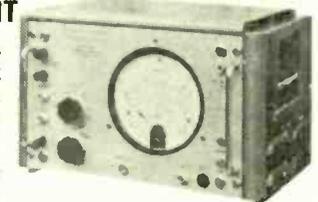
## SOLARTRON EQUIPMENT

**VF 252 VALVE VOLTMETER.** Voltage range: 1.5mV to 15v F.S.D. In nine ranges. 10:1 attenuator input; accuracy 1%. Frequency range: 10Hz to 100kHz. Input impedance: Greater than 50MΩ with 20pF. Full specification upon request. £33.10.0. Carriage 15/-.



Model, DC to 14MHz price upon application. QD 910. Storage Oscilloscope, as new. Price on request.

**ENGLISH ELECTRONIC INSULATION TESTERS 0-10KV** with built-in ionisation amplifier, £35.  
**AIRMEC INSULATION TESTER 0-15KV** built-in ionisation amplifier, £28.  
**KELVIN & HUGHES PEN RECORDERS £35.** Carriage 15/-.  
**BOONTON SIGNAL GENERATOR TS 497/U/R/R, 2-400MHz. £95.**  
**TS 418 B/U SIGNAL GENERATOR, 400-1000MHz. £105.** Carr. 30/-.  
**AVO SIGNAL GENERATOR CT 378, 2-225MHz. £58.10.0.** Carr. 18/-.

## TELEPHONE ENQUIRIES

relating to TEST EQUIPMENT should be made to 01-748 8006 Extension 23. To view TEST EQUIPMENT please phone for appointment

**INTEGRATED CIRCUITS**  
RCA CA 3005 wide band RF Ampl 300mW diss ..... 27/-  
CA 3012 wide band ampl 150mW diss ..... 22/-  
CA 3020 Audio power ampl ..... 30/-  
CA 3036 Audio pre-ampl ..... 19/-  
STC MIC 9301B Digital dual 4 input gates ..... 86/-  
MIC 709-1C Linear operational ampl ..... 190/-  
MIC 9005D Highspeed flip-flop ..... 54/-  
and many others.

## TRANSISTORS, ZENER DIODES etc.

OA5 2/6	OAZ223 to	OC83 5/-	28303 10/-	BYZ16 15/-	MPP10211/-
OA10 3/-	OAZ225 10/-	OC82DM 3/-	AC126 6/6	CR81/10 5/-	MPP103 9/6
OA70 2/-	OC16 15/-	OC83 4/6	AC127 7/6	CR81/20 9/6	MPP104
OA71 2/-	OC22 10/-	OC83B 3/-	AC128 6/6	CR81/30	10/-
OA79 1/9	OC25 7/6	OC84 8/-	AC174 7/6	CR81/10	10/-
OA81 1/8	OC28 5/-	OC122 10/-	ACY28 4/-	CR81/35	10/6
OA200 1/8	OC28 2/8	OC139 6/6	AD140 13/-	CR81/40	11/6
OA202 2/-	OC29 18/-	OC140 9/6	AP117 5/-	CR81/40	12/8
OA210 7/8	OC35 10/-	OC170 5/-	AP127 5/-	CR83/05 6/-	3/6 ea.
OA211 9/6	OC38 8/8	OC171 6/-	AP139 10/-	CR83/20	7/8 ea.
WLA17A	OC45 2/6	OC290 7/6	AP178 12/6	CR83/30	11/8
OAZ20110/-	OC45 2/6	OC201 7/6	APY19 22/6	CR825/025	15/-
OAZ20110/-	OC71 2/6	OC206 10/-	AR26 5/6	CR83/40	12/8
OAZ206 8/6	OC72 4/8	IN21 3/8	AR28 5/6	GET103 4/-	12/8
OAZ207 9/6	OC73 11/-	IN21B 5/-	BC107 3/6	GET115 9/-	12/8
OAZ208 2/6	OC75 6/-	IN25 12/-	BFY51 4/8	GET116 8/-	12/8
OAZ213 6/6	OC78 5/-	IN43 4/-	BFY27 5/-		
	OC81 4/-	IN70 4/-	BVZ13 5/-		
	OC81D 3/-	2N1306 6/6			
	OC81DM 3/-	2N1307 6/6			

MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. U.K. P. & P. up to 10/- 1/-; to £1 2/-; over £1 2/- in £, over £3 post free. C.O.D. 4/- extra.

**P. C. RADIO LTD.**  
170 GOLDHAWK RD., W.12  
01-743 4946

All overseas enquiries & orders please address to:  
**COLOMOR (ELECTRONICS) LTD.**  
170 Goldhawk Rd., London, W.12  
Tel. 01 - 743 0899

# TECHNICAL TRAINING

## in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- P.M.G. Certs. in Radiotelegraphy
- General Certificate of Education, etc.

Examination Students coached until successful

## NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, incl. professional-type valve volt meter—all under expert tuition. Transistor Portable available as separate course.

### POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

#### INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 222, Intertext House, Stewarts Road, London, S.W.8

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.)

NAME

ADDRESS

1/70

INTERNATIONAL CORRESPONDENCE SCHOOLS

## R.S.T. VALVE MAIL ORDER CO.

BLACKWOOD HALL, 16A WELLFIELD ROAD  
STREATHAM, S.W.16

A61 9/6	ECLL800	PL509 37/6	XE13/200	12AC8 10/-	2G402 6/-
ACT9 500/-	PL802 16/6	PT15 15/-	Z66 15/-	12AD6 11/-	2G414 6/-
ARP38 13/-	EP9 30/-	PX4 14/-	Z319 25/-	12AE8 9/6	2G416 6/-
AZ31 10/-	EP37A 7/-	PX25 14/-	Z759 23/-	12AT7 6/-	2G417 6/-
BT19 80/-	EP41 12/-	PY32 10/9	Z800 20/-	12AU7 5/9	2N247 9/6
BT79 67/-	EP50 5/-	PY33 10/9	Z801 30/-	12AX7 8/3	2N555 12/6
C1C 20/-	EP80 4/3	PY81 5/9	Z803U 15/-	12BA6 6/-	AC107 10/-
CBL31 16/-	EP86 6/8	PY82 4/9	OA2 6/3	12BE8 6/8	AC127 7/6
OCH35 15/-	EP89 5/8	PY83 7/-	OB2 6/-	12E1 20/-	AC128 6/8
CV5 95/-	EP91 2/9	PY500 25/-	OC4 4/8	12K6GT 8/-	ACT10 6/6
CV74 80/-	EP92 2/6	PY80 9/5	1CP31 120/-	12K8GT 8/-	ACV21 6/-
CV82 50/-	EP98 15/0	PY801 9/6	1B3GT 7/3	12Q7GT 6/-	AD140 13/6
CV315 80/-	EP183 6/8	PZ30 10/-	1Z2 25/-	13E1 190/-	AF114 7/-
CV354 110/-	EP184 7/-	QF41 400/-	2D21 6/6	20P4 20/-	AF115 7/-
CV370 300/-	EP804 21/-	QQV02/6	2C38A 140/-	24B1 110/-	AF116 7/-
CV372 57/-	EPF80 10/-	QQV03/10	2C43 70/-	25Z4 9/3	AF117 7/-
CV408 50/-	EL90 7/8	QQV03/20	2E26 20/-	25Z6GT 8/6	BY100 5/8
CV428 45/-	EL33 12/6	105/-	2K25 180/-	25Z6GT 8/6	GET571 5/-
CV429 350/-	EL34 10/8	QQV04/15	3A/167M	27M1 72/6	GET875 6/-
CV450 25/-	EL36 9/3	105/-	3A5 20/-	30C15 15/-	GET875 6/-
CV1144 60/-	EL38 26/-	QQV04/15	3B24 70/-	30C17 16/-	NK211 5/-
CV1385 140/-	EL41 10/8	QQV06/40A	3B24M 110/-	30FL1 16/-	NK214 4/-
CV1522 180/-	EL81 9/-	QQV06/40	3E241M 110/-	30FL1 16/-	NK216 7/6
CV1526 30/-	EL84 4/9	QQ05/10	3E241M 110/-	30L15 17/-	NK217 8/-
CV2155 32/6	EL85 7/9	80/-	3E24 40/-	30P4 15/-	NK228 6/-
CV2306 350/-	EL86 8/3	70/-	3E24 40/-	30P19 15/-	NK2404
CV2312 35/-	EL90 6/3	Q870/20 5/8	3C45 65/-	30FL13 18/6	NK2475 6/-
CV4003 10/-	EL360 24/-	Q875/20 5/8	3E24 15/-	30PL14 15/-	NK2775 6/-
CV4004 10/-	EL820 6/-	Q875/60	4C35 300/-	35L6T 9/-	NK1713 7/6
CV4006 8/-	EL821 7/8	Q883/3 7/3	4CX250B	35L6GT 9/-	OC19 17/8
CV4006 18/-	EL822 16/-	Q892/10 4/-	240/-	35W4 4/8	OC20 15/-
CV4007 7/-	EL180 20/-	Q895/10 5/8	4X150A	35Z40T 8/6	OC24 15/-
CV4014 7/-	EM34 21/-	Q8108/45	4X150D 95/-	4X150D	OC25 11/-
CV4015 10/-	EM81 8/3	Q8180/15	200/-	50C5 200/-	OC26 7/6
CV4024 6/-	EM84 7/6	8/-	4X250B	50CD6G	OC28 16/-
CV4025 7/-	EN32 25/-	Q8150/30	80 31/-	80 7/6	OC29 15/-
CV4031 7/-	EY01 8/-	8/-	85A1 25/-	85A2 7/3	OC35 11/8
CV4033 7/-	EY81 7/-	Q8150/36	88L 160/-	90AG 45/-	OC45 4/-
CV4044 12/-	EY83 8/5	20/-	90AV 45/-	90C1 12/-	OC74 6/-
CV4045 10/-	EY84 8/-	Q8150/45	90C12 12/-	90C2 25/-	OC75 6/-
CV4046 90/-	EY86 7/-	20/-	90C3 25/-	160B2 11/6	OC77 8/-
CV4048 12/6	EZ40 8/9	Q8150/60	90C4 5/8	150B3 8/6	OC81 4/-
CV4062 17/8	EZ41 9/8	20/6	90C5 25/-	801 9/8	OC81D 4/-
CV4064 30/-	EZ80 5/8	Q8109/73	90C6 25/-	801 35/-	OC81M 5/8
CY30 12/8	EZ81 5/8	Q8109/45	90C7 8/-	811 35/-	OC81M
DAF91 4/8	GU20 100/-	QV04-7 12/6	90C8 7/6	813 75/-	OC82 6/-
DAF96 7/6	GU21 100/-	QV05-25 9/6	90C9 25/-	813 USA	OC82D 6/-
DOC90 20/-	GT32 10/-	QV06-20 27/8	90C10 25/-	705A 10/-	OC169 5/6
DETS 1,000/-	GT33 11/-	QV07-12 27/8	90C11 25/-	723A/B	OC170 7/-
DET19 6/8	GT34 11/-	QV08-12 27/8	90C12 25/-	725A 160/-	OC171 7/-
DET20 2/6	H63 18/-	R10 15/-	90C13 25/-	829B 60/-	OC200 7/6
DET22 110/-	HL4DD	R17 35/-	90C14 25/-	829C 60/-	SX42 3/6
DET23 110/-	KT8 13/6	R18 7/8	90C15 25/-	829D 60/-	XA101 3/6
DET24 50/-	KT6 21/-	R19 7/9	90C16 25/-	833A 380/-	XA111 3/6
DF91 4/-	KT7 45/-	RG5/500	90C17 25/-	833B 380/-	XA112 4/6
DF96 7/8	KT8 15/-	120/-	90C18 25/-	833C 380/-	XA115 5/6
DI63 5/-	KT9 15/-	81M9 30/5	90C19 25/-	833D 380/-	XA117 3/6
DH77 4/9	KT91 (7C5)	81M12 7/6	90C20 25/-	833E 380/-	XA125 5/6
DK32 7/9	KT92 (7C5)	81P 40/-	90C21 25/-	833F 380/-	XA141 7/6
DK91 6/-	KT93 35/-	81P41 5/8	90C22 25/-	833G 380/-	XA142 8/6
DK92 9/-	KT94 34/-	81P61 5/-	90C23 25/-	833H 380/-	XA143 8/6
DK96 9/-	KTW62	81TV280/45	90C24 25/-	833I 380/-	TUBES
DL68 2/6	M805 800/-	25/-	90C25 25/-	833J 380/-	1CP31 120/-
DL92 5/3	M813 800/-	95/-	90C26 25/-	833K 380/-	2A11 80/-
DL94 6/9	ME140015/-	80/-	90C27 25/-	833L 380/-	3B1 65/-
DL96 7/9	ME150125/-	80/-	90C28 25/-	833M 380/-	3DP1 40/-
DL810 12/6	M14 17/6	80/-	90C29 25/-	833N 380/-	3E01 65/-
DL816 30/-	N37 17/6	80/-	90C30 25/-	833O 380/-	3F77 29/-
DL819 30/-	N78 19/-	80/-	90C31 25/-	833P 380/-	3G1 40/-
DY88 5/-	PC86 11/6	80/-	90C32 25/-	833Q 380/-	3G11 40/-
DY87 5/-	PC88 11/6	80/-	90C33 25/-	833R 380/-	3G12 40/-
DY802 9/8	PC97 8/9	80/-	90C34 25/-	833S 380/-	3G13 40/-
E880C 12/-	PC900	80/-	90C35 25/-	833T 380/-	3G14 40/-
R180F 17/8	PC94 8/6	80/-	90C36 25/-	833U 380/-	3G15 40/-
EA101P 50/-	PC96 8/-	80/-	90C37 25/-	833V 380/-	3G16 40/-
E1820C 22/6	PC98 10/8	80/-	90C38 25/-	833W 380/-	3G17 40/-
EABC80 6/8	PC189 10/6	80/-	90C39 25/-	833X 380/-	3G18 40/-
EAF42 10/-	PCF80 6/9	80/-	90C40 25/-	833Y 380/-	3G19 40/-
EB91 3/-	PCF86 9/-	80/-	90C41 25/-	833Z 380/-	3G20 40/-
EB93 8/8	PCF87 9/-	80/-	90C42 25/-	833AA 380/-	3G21 40/-
EBC41 10/8	PCF88 9/-	80/-	90C43 25/-	833AB 380/-	3G22 40/-
EBC90 4/9	PCF89 9/-	80/-	90C44 25/-	833AC 380/-	3G23 40/-
EBF80 7/6	PCF90 9/-	80/-	90C45 25/-	833AD 380/-	3G24 40/-
EBF83 9/-	PCF91 9/-	80/-	90C46 25/-	833AE 380/-	3G25 40/-
EBF89 6/8	PCF92 9/-	80/-	90C47 25/-	833AF 380/-	3G26 40/-
EEL21 12/-	PCF93 9/-	80/-	90C48 25/-	833AG 380/-	3G27 40/-
ECC33 15/-	PCF94 9/-	80/-	90C49 25/-	833AH 380/-	3G28 40/-
ECC40 17/6	PCF95 9/-	80/-	90C50 25/-	833AI 380/-	3G29 40/-
ECC70 15/-	PCF96 9/-	80/-	90C51 25/-	833AJ 380/-	3G30 40/-
ECC81 6/-	PCF97 9/-	80/-	90C52 25/-	833AK 380/-	3G31 40/-
ECC82 9/9	PCF98 9/-	80/-	90C53 25/-	833AL 380/-	3G32 40/-
ECC83 6/3	PCF99 9/-	80/-	90C54 25/-	833AM 380/-	3G33 40/-
ECC85 5/-	PCF100 9/-	80/-	90C55 25/-	833AN 380/-	3G34 40/-
ECC88 7/6	PCF101 9/-	80/-	90C56 25/-	833AO 380/-	3G35 40/-
ECC90 6/6	PCF102 9/-	80/-	90C57 25/-	833AP 380/-	3G36 40/-
ECC95 11/6	PCF103 9/-	80/-	90C58 25/-	833AQ 380/-	3G37 40/-
ECH42 12/6	PCF104 9/-	80/-	90C59 25/-	833AR 380/-	3G38 40/-
ECH81 5/9	PCF105 9/-	80/-	90C60 25/-	833AS 380/-	3G39 40/-
ECH83 8/8	PCF106 9/-	80/-	90C61 25/-	833AT 380/-	3G40 40/-
ECL80 5/9	PCF107 9/-	80/-	90C62 25/-	833AU 380/-	3G41 40/-
ECL82 7/-	PCF108 9/-	80/-	90C63 25/-	833AV 380/-	3G42 40/-
ECL83 10/3	PCF109 9/-	80/-	90C64 25/-	833AW 380/-	3G43 40/-
ECL86 9/-	PCF110 9/-	80/-	90C65 25/-	833AX 380/-	3G44 40/-
	PL36 10/9		90C66 25/-	833AY 380/-	3G45 40/-
	PL81 8/-		90C67 25/-	833AZ 380/-	3G46 40/-
	PL82 8/8		90C68 25/-	833BA 380/-	3G47 40/-
	PL84 7/-		90C69 25/-	833BB 380/-	3G48 40/-
	PL85 29/-		90C70 25/-	833BC 380/-	3G49 40/-
	PEN45DD 12/-		90C71 25/-	833BD 380/-	3G50 40/-
	PFL200		90C72 25/-	833BE 380/-	3G51 40/-
	PL36 10/9		90C73 25/-	833BF 380/-	3G52 40/-
	PL81 8/-		90C74 25/-	833BG 380/-	3G53 40/-
	PL82 8/8		90C75 25/-	833BH 380/-	3G54 40/-
	PL84 7/-		90C76 25/-	833BI 380/-	3G55 40/-
	PL85 29/-		90C77 25/-	833BJ 380/-	3G56 40/-
	PEN45DD 12/-		90C78 25/-	833BK 380/-	3G57 40/-
	PFL200		90C79 25/-	833BL 380/-	3G58 40/-
	PL36 10/9		90C80 25/-	833BM 380/-	3G59 40/-
	PL81 8/-		90C81 25/-	833BN 380/-	3G60 40/-
	PL82 8/8		90C82 25/-	833BO 380/-	3G61 40/-
	PL84 7/-		90C83 25/-	833BP 380/-	3G62 40/-
	PL85 29/-		90C84 25/-	833BQ 380/-	3G63 40/-
	PEN45DD 12/-		90C85 25/-	833BR 380/-	3G64 40/-
	PFL200		90C86 25/-	833BS 380/-	3G65 40/-
	PL36 10/9		90C87 25/-	833BT 380/-	3G66 40/-
	PL81 8/-		90C88 25/-	833BU 380/-	3G67 40/-
	PL82 8/8		90C89 25/-	833BV 380/-	3G68 40/-
	PL84 7/-		90C90 25/-	833BW 380/-	3G69 40/-
	PL85 29/-		90C91 25/-	833BX 380/-	3G70 40/-
	PEN45DD 12/-		90C92 25/-	833BY 380/-	3G71 40/-
	PFL200		90C93 25/-	833BZ 380/-	3G72 40/-
	PL36 10/9		90C94 25/-	833CA 380/-	3G73 40/-

# R+TV

**RADIO & TV COMPONENTS (Acton) LTD**

**21a High Street, Acton, London, W.3.**

also 323 Edgware Road, London, W.2.

Goods not dispatched outside U.K. Terms C.W.O. All enquiries S.A.E.

## Complete stereo system—£29 10s.

The new Duo general-purpose 2-way speaker system is beautifully finished in polished teak veneer, with matching vynair grille. It is ideal for wall or shelf mounting either upright or horizontally.

**Type 1 SPECIFICATION**

Impedance 10 ohms. It incorporates Goodmans high flux 6" x 4" speaker and 2 1/2" tweeter. Teak finish 12" x 6 1/2" x 5 1/2". 4 guineas each. 7/6d. p. & p.

**Type 2** as type 1. Size 17 1/2" x 10 1/2" x 6 1/2". Incorporating 10 1/2" x 6 1/2" bass unit and 2 1/2" tweeter. 3 ohms impedance 5 1/2 guineas plus 15/- p. & p.

Garrard Changers from £7.19.6d. p. & p. 7/6d.

Cover and Teak finish Plinth £4.15.0d. 7/6d. p. & p.



These 5 items can be purchased together for £29 10s+£1 10s p. & p.

*Duetto* Integrated Transistor Stereo Amplifier **£9 10s.**  
plus 7/6d. p. & p.

The Duetto is a good quality amplifier, attractively styled and finished. It gives superb reproduction previously associated with amplifiers costing far more.

**SPECIFICATION:**

R. M. S. power output: 3 watts per channel into 10 ohms speakers  
**INPUT SENSITIVITY:** Suitable for medium or high output crystal cartridges and tuners. Cross-talk better than 30dB at 1Kc/s.  
**CONTROLS:** 4-position selector switch (2 pos. mono and 2 pos. stereo) dual ganged volume control.  
**TONE CONTROL:** Treble lift and cut. Separate on off switch. A preset balance control.



*The Classic*  
TEAK FINISHED CASE  
**£9**  
plus 7/6 p. & p.  
Built and tested.

**SPECIFICATION**

Sensitivities for 10 watt output at 1 KHz into 3 ohms. Tape Head: 3mV (at 3 1/2" i.p.s.). Mag. P.U.: 2 mV. Cer. P.U.: 80 mV. Tuner: 100 mV. Aux. 100 mV. Tape/Rec. Output: Equalisation for each input is correct to within ±2dB (R.I.A.A.) from 20 KHz to 20KHz. Tone Control Range: Bass ±13 dB at 60 Hz. Treble ±14 dB at 15 KHz. Total Distortion: (for 10 watt output) <1.5%. Signal Noise: <-60dB. AC Mains 200-250v. Size 12 1/2" long. 4 1/2" deep. 2 1/2" high.




*The Viscount*  
INTEGRATED HIGH FIDELITY TRANSISTOR STEREO AMPLIFIER  
**£14 5s.** + 7/6 p. & p.

SIZE: 12 1/2" x 6" x 2 1/2" In teak-finished case. Built and tested.

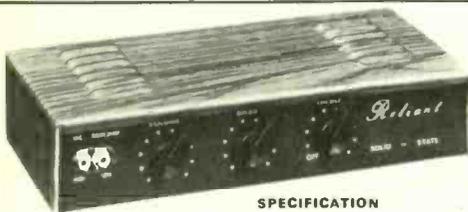**SPECIFICATION**

OUTPUT: 10 watts per channel into 3 to 4 ohms speakers (20 watts) monaural.  
**INPUT:** 6-position rotary selector switch (3 pos. mono and 3 pos. stereo). P.U. Tuner. Tape and Tape Rec. out Sensitivities: All Inputs 100 mV into 1.8M ohm.  
**FREQUENCY RESPONSE:** 40Hz-20KHz ±2DB.  
**TONE CONTROLS:** Separate bass and treble controls. TREBLE 13dB lift and cut (at 15KHz) BASS: 15dB lift and 25dB cut (at 50Hz).  
**VOLUME CONTROLS:** Separate for each channel. AC MAINS INPUT: 200-240v. 50-60Hz.  
**Viscount Mark II** for use with magnetic pick ups specification as above. Fully equalised for magnetic pick ups. Suitable for cartridges with minimum output of 4mV/cm/sec. at 1kc. Input Impedance 47k. **£15 15s.** plus 7/6 p. & p.



**THE RELIANT MK.II**  
Solid State  
General Purpose Amplifier  
In teak-finished case  
**£6 16s.**  
+7/6 p. & p.

**SPECIFICATION**

OUTPUT: 10 watts into a 3 ohms speaker.  
**INPUTS:** (1) for mike (10 m.v.). Input (2) for gram. radio (250 m.v.) Individual bass and treble control.  
**TRANSISTORS:** 4 silicone and three germanium.

MAINS INPUT: 220/250 volts.  
 SIZE: 10 1/2" x 4 1/2" x 2 1/2"  
**MIKE TO SUIT (CRYSTAL):** 12/6d. 1/6d. p. & p.  
 8" x 5" speaker 14/6d. + 3/ p. & p.  
**Mk. 1** £5 15s. + 7/6d. p. & p. less Teak-finished case.


**X101 10w. SOLID-STATE HI-FI AMP**  
With Integral Pre-amp.



Specifications: Power Output (into 3 ohms speaker) 10 watts. Sensitivity (for rated output): 1mV into 3K ohms (0.33 microamp) Total Distortion (at 1 KHz): At 5 watts 0.35%; At rated output 1.5%. Frequency Response: Minus 3 dB points 20 Hz and 40 KHz. Speaker: 3-4 ohms 13-15 ohms may be used! Supply voltage: 24v D.C. at 800 mA. (6-24v may be used).

**69/6** plus 2/6 p. & p.

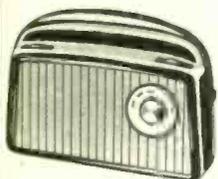**CONTROL ASSEMBLY:** (including resistors and capacitors). 1. Volume: Price 5/-. 2. Treble: Price 5/-. 3. Comprehensive bass and treble: Price 10/-. The above 3 items can be purchased for use with the X101. **POWER SUPPLIES FOR X101:** P101 M (mono) 35/- p. & p. 4/6; P101 (stereo) 42/6 p. & p. 4/6.



**THE DORSET**  
(600mW Output)  
**£5.5.0**  
plus 7/6 p. & p.  
Circuit 2/6. FREE WITH PARTS  
**MAINS POWER PACK KIT:**  
9/6 extra.

7-transistor fully tunable M.W.-L.W. superhet portable—with baby alarm facility. Set of parts. The latest modularized and pre-alignment techniques makes this simple to build. Sizes: 12" x 8" x 3".



**ELEGANT SEVEN**  
MK. III  
(350mW Output)  
**£4.9.6**  
plus 7/6 p. & p.  
Circuit 2/6. FREE WITH PARTS  
**MAINS POWER PACK**  
KIT: 9/6 extra.

7-transistor fully tunable M.W.-L.W. superhet portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.

**50 WATT AMPLIFIER**



AC MAINS 200-250V  
**£28 10s.**  
plus 20/- p. & p.

An extremely reliable general purpose valve Amplifier—with six electronically mixed inputs. Suitable for use with: mics, guitars, gram, tuner, organ, etc. Separate bass and treble controls. Output impedance 3, 8 and 15 ohms.

**NEW COMPLETE HI-FI STEREO SYSTEM £39**

comprising SP25 Garrard MkII with diamond stereo cartridge, Viscount amplifier MkI. Two type 2 speakers, plinth and cover.  
**£39** plus £2 p. & p.

**STEREO PRE-AMPLIFIER**

Inputs—6 position rotary switch (3 position mono, 3 position stereo). Tuner 150 mV into 880k. Magnetic pick-up fully equalised and suitable for magnetic cartridges with minimising output of 4mV/cm/sec. Load 47k. Ceramic pickup 150 mV into 680k. Sensitivities taken for 200mV output. Controls—separate volume controls for each channel. Twin ganged bass. 12dB lift and 15dB cut at 60Hz. Twin ganged treble. 10dB lift and 15dB cut at 10KHz. Voltage required 23-30v DC at 5mA. Size 12 1/2" x 3 1/2" x 2 1/2". In teak finished case, complete with front panel and knobs. Built and tested £7.7.0 plus 5/- p. & p.

**SPECIAL OFFER**

Complete stereo systems comprising BALFOUR 4 speed auto player with stereo head 2 DUO speaker systems size 12 x 6 1/2 x 5 1/2. Plinth (less cover) and the DUETTO stereo amplifier. All above items  
**£20** plus 20/- p. & p.

**AMATRONIX LTD (WW)**

**TRANSISTORS—MINT, NO SECONDS, NO RE-MARKS. GUARANTEED TO SPEC.**

AD161/162	12/-	BFY51	4/-	2N3055	16/8
AF239	10/-	IS44	1/4	2N3707	4/-
B-5000Q	11/3	IS557	3/-	2N3794	3/-
BD121	18/-	MC140	4/-	2N3983	5/8
BC107B	3/-	MEM584C16-	2N4058	4/8	
BC168B	2/3	SF115	3/-	2N4285	3/-
BC169C	2/6	TI407	5/8	2N4289	3/-
BF167	5/3	TIS60M	4/8	2N4291	3/-
BF178	9/-	TIS61M	4/11	2N4292	3/-
BF224	4/-	2N706	2/7	2SB187	2/-
BF225	4/-	2N2926Q	2/6	40468A	7/8

**CERAMIC I.F. RESONATORS.** Tailor-make 455kHz i.f. selectivity to your own requirements. New Brush Cleveite Identical Resonators need only the addition of fixed capacitors of standard values to create superb filters with a wide range of bandwidth options. Makers' data gives capacitor values for filters with 2-8 resonators. Example: 4-resonator filter, -6dB @ 1.9kHz off tune; -60dB @ 10kHz. Resonators Type TF04-442, 10/- each, 4 for 30/-.

**INTEGRATED CIRCUITS—PA234**, new dual-in-line 1W audio amp, with data, 24/-; CA3020, TO-5 push-pull amp, usable to 6MHz, 28/-; TAB101, transistor quad for ring modulator, 21/-.

**AMPLIFIER PACKAGES—**Component kits for efficient transformerless class B power amps. Low standby current, simple circuitry, no adjustments. AX2 9V, 300mW in 10-20 ohms, other loads usable, 12/8; AX3 9V, 800mW in 8 ohms, 20mV in 20K input, 22/8; AX4 24V, 5W in 8 ohms, 4W in 15 ohms, input 100mV in 40K. Operable 18V with 12mA standby current and 2-3W output. Uses AD161/2 output pair with silicon low-level stages. Still only 30/-. AX5, 12V, 3W in 3 ohms, 35/-.

**MINI MAINS TRANSFORMERS—1" x 1" x 11"** Osmor MT9, 9.0-0V 80mA, 12/8. MT6, 6.0-0V, 100mA, 13/6; MT12, 12.0-12V, 50mA, 13/6. Mail order only. Cash with order. List 6d., free with orders. U.K. post free on orders over 10/-.

396 Selsdon Road, South Croydon, Surrey, CR2 0DE

**BAILEY PRE-AMPLIFIER**

High quality pre-amplifier circuit described by Dr. A. R. Bailey in the December, 1966, "Wireless World". This is a low distortion circuit of great versatility with a maximum output of 2 volts making it suitable for driving Bailey 20W and 30W Amplifiers, Linsley Hood Class A Amplifier and many others. All normal pre-amplifier facilities and controls are incorporated. A new Printed Circuit Board containing latest modifications 7in. by 3 1/2in. features edge connector mounting, roller tinned finish and silk screened component locations. This board is available in S.R.B.P. material or fibreglass and the complete kit for the unit contains gain graded BC109 transistors, polyester capacitors and metal oxide resistors where specified.

**BAILEY 30W AMPLIFIER**

All parts are now available for the 60-volt single supply rail version of this unit. We have also designed a new Printed Circuit intended for edge connector mounting. This has the component locations marked and is roller tinned for ease of assembly. Size is also smaller at 4 1/2in. by 2 1/2in. Price in SRP material 11/6d. in Fibreglass 14/6d.

**BAILEY 20W AMPLIFIER**

All parts in stock for this Amplifier including specially designed Printed Circuit Boards for pre-amp and power amp. Mains Transformer for mono or stereo with bifilar wound secondary and special 218V primary for use with CZ6 Thermistor, 35/6d., post 5/-.

Trifilar wound Driver Transformer, 22/6d., post 1/-. Power Amp., 12/6d., post 9d.  
Reprint of "Wireless World" articles, 5/6d. post free.

**DINSDALE 10W AMPLIFIER**

All parts still available for this design.  
Reprint of articles 5/6d., post free.

**LINSLEY HOOD CLASS A AMPLIFIER**

Parts now available for this unit including special matt black anodised Metalwork and all power supply components.

PLEASE SEND S.A.E. FOR ALL LISTS.

**HART ELECTRONICS,**

321 Great Western St., Manchester 14

The firm for quality.

Personal callers welcome, but please note we are closed all day Saturday.

**OSMABET LTD.**

WE MAKE TRANSFORMERS AMONGST OTHER THINGS

**AUTO TRANSFORMERS.** 0-110-200-220-240 v a.c. up or down, fully shrouded fitted terminal blocks. 50 v 31/-; 75 v 37/-; 100 v 45/-; 150 v 57/8; 200 v 71/8; 300 v 90/-; 400 v 112/8; 500 v 127/8; 600 v 135/-; 750 v 172/8; 1000 v 210/-; 1500 v 345/8; 2000 v 400/-; 3000 v 560/-; 4000 v 750/-.

**MAINS ISOLATION TRANSFORMERS.** Input 200-240 v a.c., 1 : 1 ratio, 50 v 60/-; 100 v 90/-; 200 v 150/-; 500 v 300/-.

**MAINS TRANSFORMERS.** Prim 200-240 v a.c. TX1. 425-0-425 v 250 Ma, 6.3 v 4 a, CT, 6.3 v 4 a, CT, 0-5-6.3 v 3 a, 135/-; TX2 250-0-250 v 150 Ma, 6.3 v 4 a, CT, 0-5-6.3 v 3 a, 67/8; TX3 250-0-250 v 100 Ma, 6.3 v 4 a, CT, 6.3 v 1 a, 56/8; TX4 300-0-300 v 90 Ma, 6.3 v 2 a, CT, 6.3 v 1 a, 56/8; TX5 300-0-300 v 120 Ma, 6.3 v 1 a, 6.3 v 2 a, CT, 6.3 v 2 a, 67/8; TX8 250-0-250 v 65 Ma, 6.3 v 1.5 a, 32/8; MT2 230 v 45 Ma, 6.3 v 1.5 a, 25/-.

**INSTRUMENT TRANSFORMERS.** Prim 200/250 v a.c., OMT4/1 tapped sec, 5-20-30-40-60 v, giving 5-10-15-20-25-30-35-40-55-60, 10-0-10, 20-0-20, 30-0-30 v a.c. 1 amp 40/-; ditto tran 2 amp OMT4/2 60/-; OMT5/1 tapped sec, 40-50-60-80-100-110 v, giving 10-20-30-40-50-60-70-80-90-100-110, 10-0-10, 20-0-20, 30-0-30, 40-0-40, 50-0-50 a.c. 1 amp, 60/-.

**HEATER TRANSFORMERS.** Prim 200/250 v a.c. 6.3 v 1.5 a 11/8; 3 a 18/9; 6 a CT 30/-; 12 v 1.5 a 18/9; 3 a CT 30/-; 6 a 56/-; 24 v 1.5 a 27/8; 3 a 56/-; 5 a 75/-; 6 a 108/-; 12 a 150/-; 12-0-12 v 1 a 19/8; 20-0-20 v 0.7 a 19/8.

**MIDGET MAINS TRANSFORMERS.** PW rectification, size 2 x 1 1/2 x 1 1/2 in. prim 200/250 v a.c., output PT1 9-0-9 v 0.5 a; PT2 12-0-12 v 0.25 a; PT3 20-0-20 v 0.15 a, all at 19/8 each.

**OUTPUT TRANSFORMERS.** Mullard 8/10 UL 67/8; 7 watt stereo UL 59/-; 3 watt P3 30/-; PP 11K/7-7.5 ohm 21/-; Multi ratio 7/10 watt 30/-; 30 watt (KT66 etc.) 3-15 ohm 75/-; 50 watt (KT88 etc.) 135/-; 100 watt 225/-; auto matching transformer 10 watt, 3-7.5-15 ohm, up or down 11/8.

**CHOKES.** Inductance 10 H. 65 Ma 12/-; 85 Ma 15/-; 150 Ma 21/-; Flying leads, clamp construction.

**W.W. COLOUR TELEVISION RECEIVER**

Transformers and choke as specified.  
Choke L1 60/-; Transformer T1 57/8; Field O/P transformer 80/-.

Carriage extra on all transformers 4/6 minimum.

**BULK TAPE ERASERS.** 200/250 v a.c. immediate and complete erasure of any size spool of magnetic tape, also suitable for tape head demagnetization, 42/8. P. & P. 3/-.

**FLUORESCENT LIGHTING.** 12 v LT, complete fittings, 12 in. 8 watt 11/0/-; 21 in. 13 watt 13/0/-; special offer 18 in. 15 watt 95/-; Transistor ballast 12 v for single 40 watt or twin 20 watt tubes, 150/-; single 20 watt, 100/-.

**LOUDSPEAKERS.** Complete range, famous make, '25 watt 107/-; 35 watt 130/-; 50 watt 320/-, etc., etc., all at discounts while stock lasts, illustrated lists. P. & P. 6/-.

**LOUDSPEAKERS.** Ex-equipment, perfect, 3 ohms. Elac, Goodman, etc. 8 in. 15/-; 6 in. 10/-; 5 in. 7/6. P. & P. 3/6 min.


**S.A.E. ALL ENQUIRIES PLEASE MAIL ORDER ONLY**

46 KENILWORTH ROAD, EDGWARE, MIDDX. HAS 8YG. Tel: 01-958 9314

WW-095 FOR FURTHER DETAILS

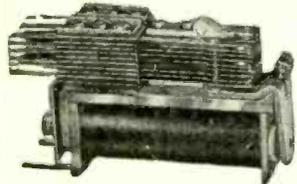**Wilkinsons FOR RELAYS**

**P.O. TYPE 3000 AND 600**  
BUILT TO YOUR REQUIREMENTS—QUICK DELIVERY  
COMPETITIVE PRICES—VARIOUS CONTACTS  
DUST COVERS—QUOTATIONS BY RETURN  
LARGE STOCKS HELD OF MINIATURE SEALED RELAYS



**EQUIPMENT WIRE.** 7/0076, 1/024, 14/0048 P.V.C. type 1 and 2 various colours 80/- per 1,000 yards. 14/0076 type 11 colours only Red and Natural available £15 per 1,000 yards

**MINIATURE SILVER ZINC ACCUMULATOR.** 1.5 volt, 1.5 amperes. Size 2x1.13x0.63in. Weight 1 1/2 oz. Ideal for model work, 12/6 each, 120/- doz., post 1/6.

**STROBOSCOPE FORK.** 125 cycles. P.O. No. 5, 30/- each, post 2/6.

**LEDEX ROTARY SOLENOIDS AND CIRCUIT SELECTORS.** SIZE 5s. 4 pole, 11 way and off 110/-, 4 pole 12 way 110/-, 24 pole, 11 way and off 210/-, 54 pole On Off 150/-.

**N.S.F. SOLENOIDS** type 3E 115.2 ohms 48v. D.C. 17/6 ea. CERAMIC AND PAXOLIN WAFER SWITCHES available from stock at keen prices, send for list. 24 way Double Pole Pax Wafer Switches 12/6 each, post 2/6.

**P.O. STANDARD RACKS** 6ft. U channel sides drilled for 19in. panels heavy angle base, 150/-, cge 20/-; Desk Units for Racks 30/-, cge 7/6.

**MINIATURE BUZZERS.** 12v. with tone adjuster, 7/6.

**PLASTIC-FILM CONDENSERS** TMC S125017LM 0.9+0.1 mfd. 500v. also 1 mfd. 15v. 150v. TCC 20/- each.

**AIR BLOWERS.** 200/250 volt. A.C. cylindrical 7in. 7in. suitable for intake or extraction. 1/50th h.p. £10. 1/15th h.p. £11. 1/10th h.p. £14.

**ELCOM STUD SWITCHES.** 12 pole 2 way or 3 way types on 3 Banks, break before make action, 50/- each.

**GEARED MOTORS.** 1 r.p.m. or 3 r.p.m. 4 watts very powerful, reversible 24v. A.C. 35/-, post 2/6, can be operated from 230v. with our 20/- Transformer. Post 5/-.

**VACUUM GAUGES.** 2in. scaled. 0/30 inches of mercury, 20/- each, post 2/6.

**STANDARD LEVER KEYS 3 POSITION**  
4C lock/4C lock 17/6 each.  
Stop/6C 15/6 each.  
2C 2M non-lock 2C 2M non-lock 14/6 each.  
4C non-lock/6C lock 20/- each.

**ONE HOLE FIXING.** Stop/4 C.O. non-locking 2 position 10/6. 6 C.O. lock/2 C.O. lock 3 position 17/6.

**TRANSFORMER.** 200/240v., tapped 6.3v., 8.3v., 10.3v. 17 amps, 70/-, post 6/-.


**LAMP HOUSES** with pair of 6in. lenses mounted in a 9in. square case. Ideal spotlight 70/- each, post 10/-.

**BATTERY CHARGERS** at special price made by Westinghouse, worth £35. Input 200/250v. A.C. output 6v. 15 amps D.C. with ammeter, fuses; regulated by a 4-position switch and sliding resistance. OUR PRICE 170/-. Cge. 15/-.

**MINIATURE DIGITAL DISPLAY SERIES 661** Counting Insts. Ltd., an assembly of five units each displaying 11 messages in numbers with decimal point, and letters £25 complete, send for details.

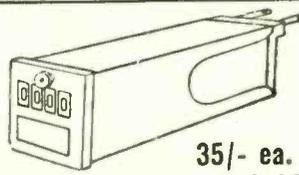**HIGH SPEED COUNTERS**

3 1/2 x 1 1/2 in. 10 counts per second with 4 figures. The following D.C. voltages are available, 6v., 12v., 24v., 50v. or 100v.



35/- ea.

**SUB-MINIATURE** Microswitch Honeywell S.P.D.T. type 11 SMI TN 13 size 3in. x 1in. x 1in. 6/6 each, or mounted in fives for 22/6 post free.

**JACK PLUGS.** 2 Point with screw-on cover, 2/6, post 9d.  
PO 201 on headphone cord 3/-, post 1/6.

**PLUG-IN RELAYS.** Linsley 4 change-over HD contacts 28v. D.C. or 240v. A.C. with base and cover, 35/- each.

**RELAYS.** 24 volt D.C., 4 make, 4 break heavy duty contacts with dust cover, 12/6 each, quantities available.

**MINIATURE BUZZERS.** 12 volts with tone adjuster, 7/6 each as illustrated

**MIRROR GALVANOMETER** BB 3000. N.E.P. Focal length 20 cm £15 each.

**ROOM THERMOSTAT.** Adjustable between 45 and 75 deg. Far., 250v. 10 amp. A.C. ideal for greenhouses, 35/- Post 4/6.

**TERMINAL BLOCKS.** 2 way 5C/430 or 3 way 5C/432 50/- per 100 or £20 per 1,000. (As Illustrated.)

**ROBUST AIRCRAFT PUSH.** SC/898 of bakelite barrel type construction, with 1 1/2in. square hole fixing top with actual push below the level of a 1in. bakelite circle to prevent it being used accidentally. Samples 5/- each large quantities available.

**MAGNETIC COUNTERS.** Veeder Root with zero reset. 800 counts per minute, counting to 999,999, 110 or 125 volts A.C. or 110 volts D.C. 65/- each, post 3/-.

**VACUUM CONDENSERS.** 25 pf., 31 KV, 27/6, post 3/-.

**METERS GUARANTEED.** Complete list available.

Microamps 0/500 2in. MC... 25/-  
Microamps 0/500 2 1/2in. MC... 37/6  
Milliamps 0/50 2in. MC... 35/-  
Milliamps 0/500 3 1/2in. MC... 54/-  
Amps 50-0-50 2in. MC... 17/6  
Amps 0/5 2in. MC... 42/6  
Volts 5/0/5 2in. MC... 25/-  
Volts 0/20 2in. MC... 42/6  
Volts 0-40 2in. MC... 42/6  
Volts 0/10 A.C. 3 1/2in. MCR... 70/-

**MICROAMPS 0/50** scaled in Rontgens 2 1/2in. MC 45/-

**PORTABLE VOLTMETERS** 0/250 Moving Iron A.C./D.C. 6in. scale, in polished wood case, £7/10/-.

**ONE HOLE FIXING SWITCHES DOUBLE POLE ON/OFF**

3 amp 250 volt A.C. 1 1/2in. x 1 1/2in. x 1 1/2in. 30/- per dozen, 200/- per 100. Post 3/- per dozen, 6/- per 100.



**MASTER CONTACTOR.** Precision made. Contacts making and breaking twice per second in sound proof case, thermostat controlled heating, 12 or 24v., 18/6, post 6/-.

**VISCONOL CATHODRAY CONDENSERS.** .001 mfd. 10 kv, 5/-; .002 mfd. 15 kv, 9/-; .02 mfd. 10 kv, 10/-; .025 mfd. 2.5 kv, 5/-; .05 mfd. 5 kv, 9/-; .01 mfd. 4 kv, 9/-; 6 kv, 17/6; 0.5 mfd. 2.5 kv, 17/6; 1 mfd. 2 kv, 17/6.


**RESISTORS,** wire wound or carbon, potentiometers, condensers, quantities ex-stock at low prices.

**BROADBAND MEGGER** series 1, 100 v. with resistance box 1,000 volts, range 0/100 megohms-infinity, usual price £189, our price £60.

**L. WILKINSON (CROYDON) LTD.**  
LONGLEY HOUSE LONGLEY RD. CROYDON SURREY  
Phone: 01-684-0236 Grams: WILCO CROYDON
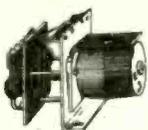
# Electro-Tech Sales

**Motor Driven Variable Voltage Transformers by Ohmite (U.S.A.).** Input 120/240v., 50/60. c.p.s. Output 0-240v. at 480 v.a. A reversible 115v. a.c. geared motor drives the contact sweep arm in the direction required. There is a micro switch mounted at each end of the track which is cam-operated and intended to be connected as a safety-stop. First class condition. £8.15.0. Carriage 15/-.




**New "Croydon" 1/50th HP, cont. rating 240v. A.C. motor, 1500 RPM, foot mounted.** Size: 3 3/8" high x 5" long + spindle length 1 1/2" x 1/2" dia. A really beautiful motor at less than half maker's original price. £6.10.0 each. P. & P. 5/-.



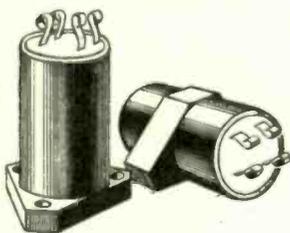**MINIATURE "LATCHMASTER" RELAY**

6, 12, or 24v. D.C. operation. One make one break, contacts rated 5 amps at 30 volts. Once current is applied, relay remains latched until input polarity is reversed. Manufactured for high acceleration requirements by Sperry Gyroscope Co. Size: Length 7/8", dia. 9/16" (including mount). Actual size as illustrated. Please state vertical or horizontal mount and voltage. £3.10.0 each. P. & P. free.



**Brand new "Discus" Centrifugal Blower by Watsons & Watson, 240v.** A.E.I. motor, cont. 2,850 r.p.m., overall diam. 10", outlet flange 2" I.D. additional coupling mounting flange supplied. Limited supply. £9.10.0. Carriage £1.0.0.



**Victoreen "Hi-Meg" Resistors.** One value only 50,000 meg ± 2%, glass encapsulated 15/- post free.

**Welwyn high value Resistors Type GA 36501.** Values between 9.4 and 10.9 kilo-meg ± 1%, glass encapsulated 15/- post free.

We have in stock a large, range of new laboratory equipment, Glassware and Filter Paper all below makers prices! It should pay you to pay us a visit when in our vicinity. We list here just a few selected items:

**Griffin-Grundy, Incubator-Steriliser Type I/200.** Heating chamber 12" x 12" x 14" high, 2 x 300 watt elements, aluminium case, variable up to 200° C. Thermostat setting ± 0.5%, 240v., £27.10.0.

**Griffin-Grundy Drying Oven. Model C2/105.** Designed to meet B.S.1377 spec. for soils drying, very useful as a general purpose drying oven. Outer casing zinc/steel in grey enamel. External size 40" x 21" x 35" high. The heated chamber constructed of compressed asbestos sheet. Internal size 36" wide 19" deep 20" high, four shelf runners, three perforated shelves supplied, heating by 6 x 300 Watt elements, thermostat setting 105°-110° C. Two doors hinged at outer edges. £97.10.0, one only.

**Copper, gas heated hot air drying Ovens.**  
 Internal size 20 x 20 x 20 cm. .. £10. 0.0  
 25 x 25 x 25 cm. .. £11.10.0  
 30 x 30 x 30 cm. .. £12.10.0

Similar to above but hot water, double walled.  
 20 x 20 x 20 cm. .. £15.10.0  
 25 x 25 x 25 cm. .. £16.15.0  
 30 x 30 x 30 cm. .. £18.18.0

**SPEEDIVAC Vacuum Pump Type ES35** .. £30. 0.0  
**SPEEDIVAC Diffusion Pump Type E01** .. £25. 0.0

**Roberval Balance, double pan, counter scale balances, capacity 4 lb., brass pans, 20 cm. diam. £25.0.0.**

**Griffin Flask Shaker.** For up to eight bolthead or standard flasks 240v. AC/DC. £25.0.0.  
 Also in stock various centrifuges, balances, flask heaters, de-ionisers, etc.

**BRAND NEW ALTERNATORS MANUFACTURED BY ENGLISH ELECTRIC CO.**

Type	Motor	Input V.	Ph.	C.P.S.	R.P.M.	Output V.	Ph.	C.P.S.	V.A.
1	220	3	50	3000	115	3	400/20	50	85
2	380/440	3	60	3600	115	3	400/20	50	85
3	115	3	60	3600	115	3	400/20	50	85
4	220	3	60	3600	115	3	400/20	50	85
5	220 D.C.								
6	110 D.C.								



All types give the same Dual outputs as below.  
 £47.10.0 Each

**NEW HYSTERESIS MOTORS BY WALTER JONES.** Type 14050/12. 240v. 50 c/s 1500 RPM cont. rating, output 2.0 oz./in.

Size: Length (less spindle) 3 1/2". Width 2 1/2" x 2 1/2". Spindle 1" x 3/16". Weight 3 lb. Maker's price in region of £22.10.0. Our price £7.15.0 each. P. & P. 5/-.



**English Electric 1/2 h.p. Motors.** 240v. single-phase, standard foot mounted, 1,425 r.p.m., continuous rating. £4.15.0. Carriage 20/-.

**Isolation Transformers.** 1 to 1. 250v. input, 250v. centre tapped out, at 2 K.V.A., mounted in metal case measuring 8 1/2" x 8 1/2" x 11" high. Weight 65lb. £18.10.0. P. & C. 25/-.

**K.L.G. Sealed Terminals.** Type TLS1 AA, overall length 1 1/16", box of 100, 25s. Type TLS1 BB, overall length 1", box of 100, 35s. P. & P. Free.



**Mullard Geiger Muller Tubes Type MX115 (new).** Max. threshold voltage 370. Min. plateau length (volts) 100. Active length 45mm. Wall thickness 375 M.G./sq. cm. Two-pin base. £3.10.0. Post free.

**Dubilier Nitrogol Capacitors.** 24 mfd. at 350 V.D.C. Size (approx.) 4 1/2" high x 3 3/4" x 2 1/2". 10/- each. P. & P. 2/6.

**Muirhead S.M. Drive Type B902C.** 3" dia. (not calibrated). 180 deg. sweep. 10/- each. P. & P. 1/6.

**Berco Rotary "Regavolt,"** variable voltage transformers input 240v. 50/60 cps., output 120-0-120v. at 6 amps. Not new, but in 1st class condition. Few only, £9.10.0. P. & C. 10/-.

**Gardner Transformer Type I.T.N. 876 (new).** Enclosed in ventilated metal case. Prim 200/250, sec. 2 x 12v. windings rated 4 amps each (96 v.a. in series/parallel). £3.2.6. P. & P. 7/6.

**American "Powerstat" Variable Voltage Transformer by Superior Electric Co.** Input 120v. 50/60 c.p.s. Output 0-120v. at 2.25 amps. 1/2" spindle with alternative pre-set locking device. Size (approx.) 3" dia. x 2" long. First class condition. £2.15.0. P. & P. 5/-.

**Mallory Tubular Capacitor,** with mounting clip. 1,000 mfd. 45 V.D.C. Size 2 1/2" long by 1 1/2" dia. 7/6 each. P. & P. 1/6.

**S.T.C. Midget Relay Type 4190 GC. (new).** 2 change-overs, 12v. 40 m.a. coil (170 ohms). 10/6 each. P. & P. 1/6.

**Jackson Air-Spaced Trimmers Type C803.** Pre-set locking type, ceramic end-plate, 2-hole fixing. 3-10 p.f., 2/6. 4-20 p.f., 2/6. 4-60 p.f., 4/-, 5-100 p.f., 4/- (Minimum order any 4 pieces.) P. & P. 1/6.


**Advance Constant Voltage Transformer (new).** Input 190-260v. Output volts 12 R.M.S. at 50 v.a. £4.19.6. Carriage 10/-.

**Robust M.E.S. Dual-circuit Panel Lamp by Thorne,** adjustable length with press-to-test dome. 1" fixing hole. Available red, green, amber. 10/6 each. P. & P. free.



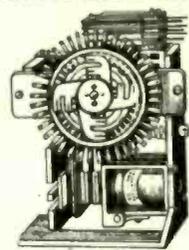
**SCHRACK ROTARY STEPPING RELAY RT304**

48v. coil (28 ohm). The relay has 48 basic segments shorted in step by the 4 sweep contacts to 4 pole-plates (banks of 12). There are 2 secondary switches: (1) one c/o H/Duty contact set which changes over and back with each step; (2) two H/Duty changeovers which changeover on each 12th step and return on the following pulse. Size: Base 3 1/2" x 1 1/2" x 4 1/2" high. New in maker's packing, limited supply, also few only, as above, but 110v. (1,290 ohm coil), £6.10.0 each. P. & P. free.



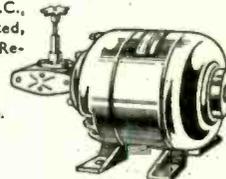**"Parvalux" Reversible 100 RPM Geared Motor**

Type S.D.14, 230/250v. A.C., 22 lb./in. Standard foot mounted, variable angle final drive. Removable 9-tooth chain spigot on 3/16" spindle. 1st class condition. £7.10.0 each. P. & P. 10/-.




**Precision Motor-driven Potentiometer**

By "Precision Line" (U.S.A.). Continuous track with 2 platinum contact wipers set at 90° C.W. resistance 300 ohm only, ± 5% LIN ± 0.5%, ball bearing spindle column. Size: dia. 1 1/32", height 1 1/32", spindle length 1 1/32" by 1/2" dia. These potentiometers were purchased by the importer at a cost of approx. £25 each. Our price £6.15.0 each. P. & P. free



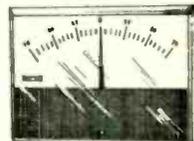
**New 75-0-75 Micro-ammeter by Sifam.**

750 ohm movement, clear reading, 5 1/2 divisions x 1/2"; plastic front, projection 1/2" (tapering forward). Size: 4 1/2" x 3 1/2". 57/6 each. P. & P. 2/6.




**MINIATURE B.P.L. 500-0/500 Micro-Ammeter.** 13/16" Diam. scale. Through-Panel mounting. 45/- P. & P. free.

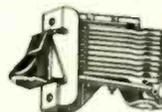**New beautifully-made 3 change-over Key-Switch.** Neat action, either locking or spring-return, as required determined by reversing fixing-plate. Attractive plastic prestle. Available red, green, grey, cream. Limited number only. 17/6 each. P. & P. 1/6.



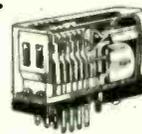**"AUTOMATIC ELECTRIC" ENCLOSED RELAYS**


6v. 50Ω 2 c/o, 14/6  
 24v. 470Ω 4 c/o, 15/6  
 48v. 2.780Ω 4 c/o, 15/6  
 48v. 1.260Ω 6 c/o, 18/6  
 P. & P. free.



**New "Magnetic Devices" solenoid 240v. A.C. Type 42117,** 1 to 3 lb. pull, frame size 1 1/2" x 1 1/2" x 1". 20/- each. P. & P. free.



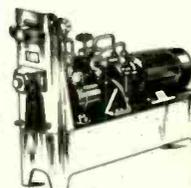**VICKERS-SPERRY-RAND Hydraulic Power Units as illustrated.** Full details upon request. Approx. 60% below makers price at £150.00 each.



**ELECTRO-TECH SALES**

**DEPT. E.W. 101, 264 PENTONVILLE ROAD, LONDON, N.1**  
 (ONE MIN. FROM KINGS X STATION) Tel. 01-837 7401

# SPECIAL MONEY SAVING DISCOUNTS

on the Best Hi-Fidelity Equipment on the Market Today


AMPLIFIERS	Rec. Retail Price	Discount Price	WHARFEDAILE UNIT 3 Speaker Kit	Rec. Retail Price	Discount Price
ARENA F210 2x10 watts Stereo Amplifier teak case	£34 13 0	£29 10 0		£10 17 6	£9 5 0
PHILIPS RH580 stereo amplifier magnetic input	£26 0 0	£21 5 0	<b>PLAYING DECKS</b>		
DULCI 207M as above but accepts magnetic cartridge	£30 0 0	£21 15 0	GARRARD 401	£31 14 2	£27 0 0
GOODMANS Maxamp teak or walnut	£54 0 0	£42 15 0	GARRARD AP75	£23 16 7	£17 15 0
LEAK Stereo 30 plus chassis model	£53 0 0	£43 10 0	GARRARD SP25 Mark II	£15 11 11	£11 5 0
LEAK Stereo 30 plus teak case	£59 10 0	£48 12 6	GARRARD SP22	£6 12 10	£5 10 0
LEAK Stereo 70 chassis model	£63 0 0	£50 15 0	GARRARD SL05	£45 9 1	£34 10 0
LEAK Stereo 70 plus teak case	£69 10 0	£55 15 0	GARRARD SL75	£35 12 5	£30 10 0
NIKKO TRM 40B	£46 10 0	£39 10 0	GARRARD SL65	£18 8 4	£14 17 6
NIKKO TRM 120	£95 0 0	£84 10 0	GARRARD SL55	£13 17 9	£11 12 6
ROGERS RAVENS-BOURNE teak case	£64 0 0	£54 10 0	GARRARD 60 Mark II	£17 5 10	£14 19 6
ROGERS RAVENS-BROOK chassis model	Limited Quantity	£34 10 0	GARRARD 3500	£12 4 10	£10 19 6
ROGERS RAVENS-BROOK in teak case	£46 10 0	£39 10 0	GARRARD 2025 T/C	£11 3 11	£10 10 0
SANSUI AU 222	£62 17 7	£56 10 0	GARRARD 1025	£10 6 2	£9 10 0
SANSUI AU 555	£80 9 7	£69 10 0	GOLDRING GL68	£22 7 2	£17 15 0
TRUVOX TSA200 teak case	£54 12 0	£45 0 0	GOLDRING GL75	£35 15 5	£28 15 0
ROGERS Cadet Mark III teak case	£37 10 0	£34 10 0	GOLDRING GL75P	£46 18 8	£37 10 8
QUAD 33 Control Unit and 303 Power Amplifier	£98 0 0	£92 10 0	THORENS TD150	£29 8 1	£26 10 0
TELETON 203E	£28 7 6	£22 10 0	THORENS TD150A	£35 14 6	£31 10 0
			THORENS TD150AB	£39 16 9	£35 10 0
			THORENS TD125	£63 4 9	£54 5 0
<b>FM TUNERS</b>			Plinths, tops and accessories of above available at 10% discount on retail price.		
ARENA F211 with Decoder	£39 18 0	£34 15 0	<b>STEREO CARTRIDGES</b>		
DULCI FMT7 Mono tuner	£22 1 0	£18 10 0	AUDIO TECHNICA AT66	£6 6 0	£5 10 0
DULCI FMT7S Stereo tuner	£29 8 0	£23 10 0	SHUR M3DM	£7 8 3	£6 2 6
GOODMANS Stereomax teak stereo tuner	£82 10 5	£70 10 0	SHURE 31E	£12 19 5	£11 10 0
LEAK Stereo Troughline tuner chassis mounting	£51 10 6	£39 10 0	SHURE 32E	£12 0 11	£10 15 0
LEAK Stereo Troughline teak case	£59 13 10	£48 10 0	SHURE 55E	£16 13 6	£13 19 0
QUAD Stereo Tuner	£51 0 0	£45 15 0	SHURE 44E	£14 16 6	£12 19 6
TRUVOX FM200 less Decoder	£37 12 11	£32 10 0	SHURE M75E	£25 18 10	£23 5 0
			SHURE V15 Mk II	£40 15 3	£35 0 0
			GOLDRING C890	£5 4 0	£4 2 6
			GOLDRING 800	£13 0 0	£11 12 6
<b>TUNER AMPLIFIERS</b>			<b>STEREO TAPE DECKS AND RECORDERS</b>		
ARENA T1500 teak only	£64 1 0	£57 10 0 (add 7 gns. for decoder)	AKAI Model 4000D 3-head stereo tape deck	£99 19 6	£84 10 0
ARMSTRONG 425	£79 14 9	£71 10 0	AIWA TP 1011 professional stereo 3 head tape deck	£164 6 0	£139 10 0
ARMSTRONG 426	£88 19 0	£79 10 0	SANYO MR910 4 track stereo tape recorder	£83 10 0	£74 10 0
B & O Beomaster 1000	£101 15 0	£94 10 0	SANYO MR920 4 track stereo tape recorder, 2 detachable speakers	£100 16 0	£89 10 0
GOODMANS 3000	£77 14 7	£67 10 0	SANYO MR801 stereo tape deck	£79 0 0	£67 10 0
			REVOX model 1104 4-track tape deck	£187 19 0	£169 10 0
			GRUNDIG TK247 de-luxe stereo tape recorder	£139 18 9	£102 10 0
			<b>MONAURAL MAINS TAPE RECORDERS</b>		
			GRUNDIG TK120 continental twin-track tape recorder	£39 5 0	£29 10 0
			GRUNDIG TK144 4-track tape recorder	£47 13 1	£41 10 0
			GRUNDIG TK149 Automatic 4-track tape recorder	£55 18 10	£49 10 0
			PHILIPS 4307 4-track tape recorder	£48 11 0	£41 10 0
			PHILIPS 4308 2-speed 4-track tape recorder	£60 0 10	£51 10 0
			<b>COMPLETE HI-FI SYSTEMS</b>		
			PHILIPS GF818 Philips autochange player, integrated 2x4 watts amplifier, 2 separate speakers, all in teak finish	£51 9 0	£45 0 0
			RADON 404 SYSTEM Garrard SP25, separate 2x8 watt amplifier, 2 bookshelf type speakers teak or blond oak	£57 4 0	£49 10 0
			WINDSOR 1500 Garrard 2025 T/C, integrated 2x4 watt amplifier, 2 separate speakers, all finished in teak	£57 15 0	£49 19 6
			TOSHIBA SOPHIA Transcription turntable, magnetic cartridge, integrated tuner amplifier, with stereo decoder, fitted hinged perspex top, 2 separate speakers, walnut finish	£82 19 0	£75 0 0
			SANYO DC534E Transcription turntable, magnetic cartridge, integrated tuner/amplifier, 2x12 watts rms, decoder, fitted hinged perspex top	£132 10 0	£119 10 0
			Matching SANYO SX/X speakers per pair	£37 16 0	£32 10 0
<b>SPEAKERS</b> (Prices quoted for single speaker unless otherwise specified)					
ARENA HT14 bookshelf type in teak	£14 3 0	£12 10 0			
ARENA HT10 teak or rosewood	£19 19 0	£17 10 0			
CELESTION Ditton 10	£21 13 1	£17 15 0			
CELESTION Ditton 15	£31 3 7	£26 5 0			
GOODMANS Maxim	£20 15 6	£16 15 0			
GOODMANS Marimba	£24 0 5	£19 15 0			
GOODMANS Mezzo II	£30 18 0	£25 10 0			
GOODMANS Magnum K	£40 2 0	£29 15 0			
LEAK Sandwich	£43 10 0	£37 10 0			
LEAK Mini Sandwich	£29 15 0	£25 5 0			
LOWTHER Accousta PM6	£45 10 0	£40 10 0			
LOWTHER Accousta PM7	£55 10 0	£50 10 0			
KF Cresta	£22 3 7	£18 10 0			
KF Celeste	£29 0 0	£25 0 0			
KF Concord	£43 10 0	£37 10 0			
KF Concerto	£53 10 0	£45 0 0			
QUAD Electrostatic	£66 0 0	£59 10 0			
WHARFEDAILE Denton per pair	£33 12 0	£29 10 0			
WHARFEDAILE Super Linton per pair	£42 0 0	£37 10 0			
WHARFEDAILE Dovedale III	£39 10 0	£32 19 6			

All goods are in manufacturer's sealed cartons and are insured against loss or damage in transit. Guaranteed "by return" service. Add 7/6 to all orders for p. & p. Send cash/cheque with order. Personal Callers Welcome—Business Hours.


**SMITH'S RADIO SERVICE (Wolverhampton) LTD.**  
Mail Order Department, 26 Victoria Street, Wolverhampton, Staffs. Tel: Wolv. 29246

## THERE ARE GEMS IN IRELAND

This is one

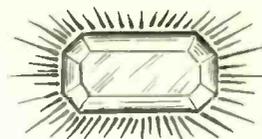

THIS is another

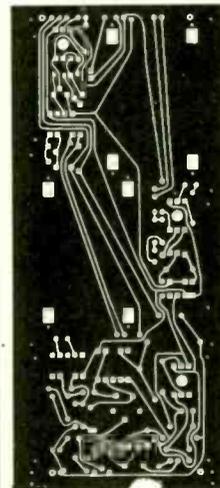

IF YOU WANT A REAL GEM CONTACT




**T ECLARE LTD**  
ENNIS, CO. CLARE. Phone: 21559

AFTER ALL, WE'RE IN THE EMERALD ISLE

## SURPLUS BARGAINS

(EX GOVT.)

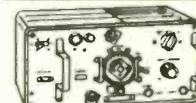


**AMPLIFIER RF No. 2 MK III.** Increases output of 19 set to 25 watts. Brand New. 12v operation. 75/- Carr. 15/- No. 19 Sets and Ancillary Equipment Available. 12v D.C. Power Units 50/- Carr. 10/- 12/24v D.C. Power units with Vibrator Mk. II No. 2 70/- Carr. 10/- H/MIC SETS. Used 15/- New 22/8. P & P 5/-. Mains P.E.U.'s for 19 TM/RC £8.15.0. Carr. 10/-. R.F. Antenna Tuner (ATU) 25/- P. & P. 5/-.  
**COLLINS TCS RECEIVER.** 7 valve Int. Octal Covers 1.5-12 Mc/s Tunable E.F.A.F.F.O. Power required 240v D.C. 80 MA 12v 1.25A. £8.10.0. Carr. 15/-  
**CR 100 RECEIVERS.** Amateur Shipping Broadcast. 60Kc/s-30Mc/s A.C. or D.C. Mains operation. Fully tested. £23.10.0. Carr. 50/-  
**R.41 RECEIVER LF** Version of B.40. Coverage 15Kc/s-700Kc/s. Mains Operation. As new £8.10.0. Carr. 30/-  
**R.209 MK II COMMUNICATION RECEIVERS.** 11 valve. Covers 1-20 Mc/s. 4 bands. AM/FM. CW. BFO. 12v D.C. Internal Power Supply. Tested. £13.10.0. Carr. 15/-



**TELESCOPIC MASTS.** 20ft. Closest to 5ft. 9in. 70/- Carr. 15/- 34ft. Ditto 80/- Carr. 15/-  
**35ft. AERIAL MASTS.** Seven 2in. dia. sections. Interlock 8in. Complete with Base, Nylon Guys. £12.10.0. Carr. 50/-



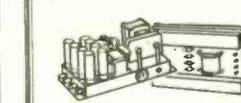**TELE 'F' FIELD TELEPHONES.** Communication up to 10 miles. Tested with batteries. £5.15.0. pair. Carr. 20/-



**LIVINGSTONE LAB TRANSISTOR AMPLIFIER.** 50 watts R.M.S. Size 14 1/2in. x 9in. x 4in. With mains p.a.u. size 16in. x 9 1/2in. x 6 1/2in. 22 Gns. Carr. 20/-

**A.J. THOMPSON (Dept. W)**

"Eiling Lodge," Codicote, Hitchin, Herts. Phone: Codicote 242  
C.W.O. Carriage charges apply to mainland only.

BRAND NEW

SEMICONDUCTORS & COMPONENTS

GUARANTEED

TRANSISTORS Brand new and fully guaranteed. PLEASE NOTE:—A large number of our transistors have now been reduced in price. Many more semi-conductors in stock. Please enquire for types not listed.

Table listing various semiconductor components including transistors (e.g., 2G301, 2G302, 2G303), diodes (e.g., BC126, BC140), and other parts with their respective part numbers and prices.

Table listing other components such as PANEL METERS (38 Series—FACE SIZE 42 x 42 mm), SPEAKERS (3ohm), PRESETS, CARBON POTENTIOMETERS, and SPECIAL OFFERS.

SILICON RECTIFIERS table listing various diode types (PIV, 1A, 3A, 6A, 10A, 17A) and their specifications for different current ratings (50, 100, 200, 400, 600, 800, 1000, 12000).

DIODES & RECTIFIERS table listing various diode types (IN461, IN914, IN916, IN4007, IS010, IS021, IS025, IS113, IS120, IS121, IS130, IS131, IS132) and their specifications.

ACA INTEGRATED CIRCUITS table listing various IC types (CA3005, CA3011, CA3012, CA3013, CA3014, CA3018, CA3019, CA3020) and their specifications.

PLESSEY table listing various IC types (SL402, SL403A) and their specifications.

FAIRCHILD table listing various IC types (L900 Buffer, L914 Gate, L702C, L923 JK Flip, L709 Op Amp) and their specifications.

MULLARD I.C.'s table listing various IC types (FCH 211, FCH 221, FCJ 101, TAA 241, TAA 243, TAA 263, TAA 320) and their specifications.

GENERAL ELECTRIC table listing various IC types (PA230, PA234, PA237, PA246) and their specifications.

THYRISTORS table listing various thyristor types (PIV, 1A, 3A, 5A, 7A, 25A) and their specifications.

VEROBOARD table listing various board types (2 1/2 x 3 1/2, 2 1/2 x 5, 3 1/2 x 3 1/2, 3 1/2 x 5, 3 1/2 x 17, 5 1/2 x 17) and their specifications.

RESISTORS table listing various resistor types (Carbon Film, Wire Wound) and their specifications.

CAPACITORS table listing various capacitor types (Polyester, ceramics, Polystyrene, silver mica, tantalum, trimmers etc.) and their specifications.

THERMISTORS (MULLARD) table listing various thermistor types (VA1005, VA1010, VA1015, VA1033, VA1034, VA1037, VA1038, VA1039, VA1040, VA1066, VA1074, VA1075, VA1077) and their specifications.

SPECIAL OFFER (Limited to last Saturday in January) To encourage personnel callers we are happy to offer a discount of 5% to all our customers on Saturdays only. We are happy to quote for quantity supplies to manufacturers etc. Post and Packing in U.K. 1/6; Europe 5/-; Commonwealth (Air) 13/-.

Telephone: 01-452 0161/2/3 A. MARSHALL & SONS LTD CALLERS WELCOME Hours 9-5.30 Mon.-Sat. 28 CRICKLEWOOD BROADWAY, LONDON, N.W.2

High grade of stability of electric parameters  
Resistance and durability  
Long operational life

# Polish

electronic tubes for radio receiver sets  
electronic tubes for TV receiver sets  
and  
electronic components  
are offered by



## UNIVERSAL


Foreign Trade Enterprise  
Warszawa, Al. Jerozolimskie 44, Poland  
P.O. Box Warszawa 1 No. 370.  
Telex No. 81437

To persons interested we forward detailed information,  
catalogues and tenders.


WW—096 FOR FURTHER DETAILS
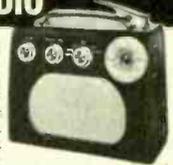
### BUILD YOURSELF A TRANSISTOR RADIO


**RODMEYER EIGHT Mk 1 WITH TONE CONTROL SEVEN WAVEBANDS—MWT, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND.** 8 transistors and 3 diodes. Ferrite rod aerial and telescopic aerial. Socket for car aerial, 7 x 4 in. Speaker. Airspaced ganged tuning condenser. Earpiece socket and earpiece. Selectivity switch. Size 9 x 7 x 4 in. Total Building Costs £6.19.5. P & P 7/6. Plans and Parts list 5/- (free with parts).



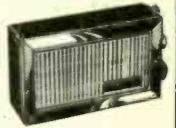
**POCKET FIVE. MED. AND LONG WAVES & TRAWLER BAND WITH SPEAKER AND EARPIECE.** 5 transistors and 2 diodes. ferrite rod aerial, tuning condenser, moving coil speaker, etc. 5 1/2 x 1 1/2 x 3 1/2 in. Total Building Costs 44/6. P. & P. 3/6. Plans and Parts list 1/6 (free with parts).



**RODMEYER SEVEN Mk 4. 7 WAVEBANDS MWT, MW2, LW, SW1, SW2, SW3, AND TRAWLER BAND.** 7 transistors and 2 diodes. Ferrite rod aerial and telescopic aerial. Socket for car aerial, 7 x 4 in. speaker. Airspaced ganged tuning condenser etc. Size 9 x 7 x 4 in. Total Building Costs £5/19/6. P. & P. 7/6. Personal earpiece with switched socket for private listening 5/- extra. Plans and Parts list 3/- (free with parts).

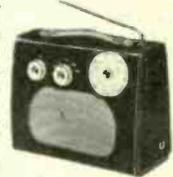

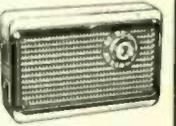**TRANSDNA FIVE. MED. AND LONG AND TRAWLER BAND WITH SPEAKER AND EARPIECE.** 5 transistors and 2 diodes. ferrite rod aerial, moving coil speaker. 6 1/2 x 4 1/2 x 1 1/2 in. Total Building Costs 47/6. P. & P. 3/6. Plans and Parts list 1/6 (free with parts).



**TRANSEIGHT 6 WAVEBANDS, MW, LW, 3 SHORT WAVES AND TRAWLER BAND.** 8 improved type transistors and 3 diodes. Ferrite rod and telescopic aerials. 3in speaker. Push pull output. Size 9 x 5 1/2 x 2 1/2 in. Total Building Costs 89/6. P & P. 5/6. Plans and Parts list 5/- (free with kit). Personal earpiece with switched socket for private listening 5/- extra.



**RADIO EXCHANGE CO. LTD.**  
Dept WW, 61 High Street, Bedford.  
'Phone 0234 52367

Open 10-1. 2.30-4.30. Sat. 9-12

## DIOTRAN SALES

P.O. BOX 5  
WARE, HERTS  
TEL. WARE 3442

S.C.R.'s 16AMP (unplated)  
100 PIV 1-24 25-99  
400 PIV 9/6 7/6  
All tested perfect functional guaranteed.

100 up 6/-  
We will also buy your surplus stock —Send us your lists.

OVER 3 MILLION SILICON ALLOY & GERM. TRANSISTORS AVAILABLE FOR IMMEDIATE DELIVERY.  
MANUFACTURERS END OF PRODUCTION SURPLUS.

TRANSISTORS	Qty. Price	Qty. Price	Qty. Price	Qty. Price	
A 1 Germ. A.F. PNP TO-1	=AC127, NKT773, AC157, ASY86	£3.10	£15	£25	£200
A 2 Germ. A.F. PNP TO-5	=AC17-21, NK237-245	£1	£3	£5	£40
A 3 Germ. A.F. PNP TO-1	=AC128, NKT271, 2G381	£1	£3	£5	£40
A 4 Germ. R.F. PNP TO-1	=OC44-45, BCY27-31, OC71-75	£1.10	£4.10	£7.10	£60
A 5 Germ. R.F. PNP TO-5	=2N1303, NKT164-7, 2G301-3	£1.10	£4.10	£7.10	£60
A 6 Germ. V.H.F. PNP TO-1	=AF116-7, KNT667, 2G417	£3.10	£15	£25	£200
A 7 Assorted Germ. A.F.-R.F. PNP mixed gains, general purpose		15s.	£2.10	£4	£32
A 8 Germ. A.F. SO-2 PNP	=2G371-89, ACY27-31, OC71-75	£2	£7.10	£12.10	£100
A 9 Sil. Alloy PNP TO-5	=2S301-5, BCY17-29, BCY30-34	£2	£7.10	£12.10	£100
A 10 Sil. Alloy PNP SO-2	=2S321-325, OC200-205	£2	£7.10	£12.10	£100

PLASTIC PNP SILICON TRANSISTORS. Manufacturers' seconds from 2N3702-3 family. Ideal cheap trans. for manufacturing etc. £8 500, £13.10 1,000 pieces.

PLASTIC NPN SILICON TRANSISTORS. Manufacturers' seconds from 2N3707-3711 family. Ideal cheap trans. for manufacturing etc. £7.10 500, £12.10 1,000 pieces.

TO-18 METAL CAN SILICON PLANAR TRANS. Very high quality 99% good. Type 2N706, BSY27. £8 per 500 pieces, £13 per 1,000 pieces.

TOP HAT SILICON RECTIFIERS. All good. No short or open circuit devices. Voltage range 25-400PIV, 750mA. £3 per 100, £12.10 per 500.

### 1/- TESTED TRANSISTORS 1/- each

ONE PRICE ONLY PNP, NPN, each	SILICON PLANAR 1/- EACH
BC108 2N696	2N1132 2N2220 2S733
BC109 2N697	2N1613 2N3707 2N3391
BFY50 2N706	2N1711 2N3711 71544
BFY51 2N708	2N2904 2S102 2N2906
BFX84 2N929	2N2905 2S103 2N2907
BFX86 2N930	2N2924 2S104 2N2906
BFX88 2N1131	2N2926 2S732

### TO-5 METAL CAN SILICON PLANAR TRANSISTORS. VERY HIGH QUALITY 99% good type.

2N697, BFY51, 2N1893. £8 per 500 pieces, £13/0/0 for 1,000 pieces.

### FULLY TESTED DEVICES AND QUALITY GUARANTEED—SURPLUS TO REQUIREMENTS

OA202 Silicon Diode. Fully Coded. 150 PIV 250mA Qty. Price £30 per 1,000 pieces.  
BY100 SIL. RECT'S 800 PIV 550 mA. 1-49 2/6 each; 50-99 2/3 each; 100-999 2/- each; 1,000 up 1/10 each. Fully Coded. 1st Qty.

TEXAS 2G371 A/B Eqt. OC71 Germ. Gen. Purpose Trans. Each  
1-99 .. .. 1/6  
100-499 .. .. 1/3  
500-999 .. .. 1/-  
1000 up .. .. 9d.  
All Brand New and Coded.

GERM. PNP AND NPN TRANSISTORS TESTED, UNMARKED SIM. TO 1/- 1/6 EACH  
AC125 ACY22 ACY36 NKT677 OC91  
AC126 ACY27 NKT141 NKT713 OC82  
AC127 ACY28 NKT142 NKT773 2G301  
AC128 ACY29 NKT212 OC44 2G302  
AC130 ACY30 NKT213 OC45 2G303  
ACY19 ACY31 NKT214 OC71 2G308  
ACY20 ACY34 NKT215 OC72 2G371  
ACY21 ACY35 NKT271 OC75 2G374


TRANSISTOR EQVT. BOOK  
2,500 cross references of transistors—British, European, American and Japanese. A must for every transistor user. Exclusively distributed by DIOTRAN SALES. 15/- EACH.

Vast mixed lot of subminiature glass diodes. Comprising of Silicon, Germ. Point Contact and Gold Bonded types plus some Zeners. 500,000 available at Lowest of Low Price. 1,000 pieces £3.0.0. 5,000 pieces £13.10.0. 10,000 pieces £23.

Post and Packing costs are continually rising. Please add 1/- towards same. CASH WITH ORDER PLEASE. QUANTITY QUOTATIONS FOR ANY DEVICE LISTED BY RETURN.

OVERSEAS QUOTATIONS BY RETURN SHIPMENTS TO ANYWHERE IN THE WORLD AT COST

# Quartz Crystal Units

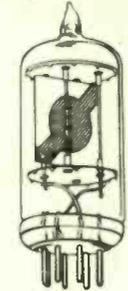

ECONOMICAL!  
ACCURATE!  
RELIABLE!



Private enquiries, please send two 5d. stamps for brochure.

THE QUARTZ CRYSTAL CO. LTD.  
Q.C.C. Works, Wellington Crescent.  
New Malden, Surrey (01-942 0334 & 2988)  
WW—097 FOR FURTHER DETAILS

## KJB PRINTED CIRCUITS

and ELECTRONIC EQUIPMENT MANUFACTURERS  
Large and small quantities. Full design and Prototype Service, Assemblies at Reasonable Prices. G.P.O. Approved  
Let us solve your problems  
**K. J. BENTLEY & PARTNERS**  
18 GREENACRES ROAD, OLDHAM  
Tel: 061-624 0939

# BI-PRE-PAK LIMITED

### FULLY TESTED AND MARKED

AC107	3/-	OC170	3/-
AC126	2/6	OC171	4/-
AC127	2/6	OC200	3/6
AC128	2/6	OC201	7/-
AC176	5/-	2G301	2/8
ACY17	3/-	2G303	2/6
AF114	4/-	2N711	10/-
AF115	3/6	2N1302-3	4/-
AF116	3/6	2N1304-5	5/-
AF117	3/6	2N1306-7	6/-
AF239	12/6	2N1308-9	8/-
AF186	10/-	2N3819 F.E.T.	9/-
AF139	10/-	Power Transistors	
BFY50	4/-	OC20	10/-
BSY25	7/6	OC23	10/-
BSY26	3/-	OC25	8/-
BSY27	3/-	OC26	5/-
BSY28	3/-	OC28	7/6
BSY29	3/-	OC35	5/-
BSY95A	3/-	OC36	7/6
OC41	2/6	AD149	10/-
OC44	2/6	2N2287	20/-
OC45	2/6	2N3055	15/-
OC71	2/6	Diodes	
OC72	2/6	AAY42	2/-
OC73	3/6	OA95	2/-
OC81	2/6	OA70	1/9
OC81D	2/6	OA79	1/9
OC83	4/-	OA81	1/9
OC139	2/6	IN914	1/6
OC140	3/6		

### TRY OUR X PACKS FOR UNEQUALLED VALUE

#### XA PAK

Germanium PNP type transistors, equivalents to a large part of the OC range, i.e. 44, 45, 71, 72, 81, etc.

PRICE £5 PER 1000

POST & PACKING 4/6 U.K.

#### XB PAK

Silicon TO-18 CAN type transistors NPN/PNP mixed lots, with equivalents to OC200-1, 2N706a, BSY27/29, BSY95A.

PRICE £4-5 PER 500

PRICE £8 PER 1000

POST & PACKING 2/6 U.K.

#### XC PAK

Silicon diodes miniature glass types, finished black with polarity marked, equivalents to OA200, OA202, BAY31-39 and DK10, etc.

PRICE £4-10 PER 1000

POST & PACKING 2/6 U.K.

ALL THE ABOVE UNTESTED PACKS HAVE AN AVERAGE OF 75% OR MORE GOOD SEMICONDUCTORS. FREE PACKS SUSPENDED WITH THESE ORDERS. ORDERS MUST NOT BE LESS THAN THE MINIMUM AMOUNTS QUOTED PER PAK.

### NEW TESTED & GUARANTEED PAKS

B2	4	PHOTO CELLS, SUN BATTERIES. INC. BOOK OF INSTRUCTIONS	10/-
B77	2	AD161—AD162 NPN/PNP TRANS. COMP. OUTPUT PAIR	10/-
B81	10	REED SWITCHES MIXED TYPES LARGE & SMALL	10/-
B89	2	5 SP5 LIGHT SENSITIVE CELLS LIGHT RES. 400 Ω DARK 1 M Ω	10/-
B91	8	NKT163/164 PNP GERM. TO -5 EQUIVALENT TO OC44. OC45	10/-
B92	4	NPN SIL TRANS. A06=BSX20. 2N2369. 500MHz. 360mW	10/-
B93	5	GET113 TRANS. EQUIV. TO ACY17-21 PNP GERM.	10/-
B96	5	2N3136 PNP SIL TRANS. TO-18 HPE100-300 IC. 600mA. 200MHz	10/-
B98	10	XB112 & XB102 EQUIV. TO AC126 AC156. OC81/2. OC71/2. NKT271. ETC.	10/-
B99	200	CAPACITORS, ELECTROLYTICS. PAPER, SILVER MICA. ETC. POSTAGE ON THIS PAK 2/6.	10/-
H4	250	MIXED RESISTORS POST & PACKING 2/-	10/-
H7	40	WIREWOUND RESISTORS MIXED TYPES & VALUES. POSTAGE 1/6	10/-

# FREE!

PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 10/- WITH ORDERS OVER £4

### LOOK! TRANSISTORS ONLY 1/- EACH

**TYPE A**  
PNP SILICON ALLOY  
TO-6 CAN

Spec:—  
ICER AT VCE = 20v  
1mA MAX.  
HFE. 15-100  
These are of the 2S300 type which is a direct equivalent to the OC200/205 range.

**TYPE B**  
PNP SILICON  
PLASTIC ENCAPSULATION

Spec:—  
ICER AT VCE = 10v  
1mA MAX.  
HFE. 10-200  
These are of the 2N3702/3 and 2N4059/62 range.

**TYPE C**  
NPN SILICON  
TO-18 CAN

Spec:—  
ICER AT VCE = 20v  
1mA MAX.  
HFE. 50-900  
These are similar to the BC108/109 types.

### Return of the unbeatable P.1 Pak. Now greater value than ever

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak **P.1**. Only **10/-**  
2/- P & P on this Pak.

Make a Rev. Counter for your Car. The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a perfectly linear and accurate rev. counter for any car. **20/- each**

### FREE CATALOGUE AND LISTS for:—

**ZENER DIODES  
TRANSISTORS, RECTIFIERS  
FULL PRE-PAK LISTS  
& SUBSTITUTION CHART**

MINIMUM ORDER 10/- CASH WITH ORDER PLEASE. Add 1/- post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

### MULLARD DATA BOOK

SEMICONDUCTOR & VALVE DATA & EQUIVALENTS **3/6**  
POSTAGE 6d EACH

### NEW UNMARKED UNTESTED PAKS

B78	12	INTEGRATED CIRCUITS, DATA & CIRCUITS OF TYPES, SUPPLIED WITH ORDERS	10/-
B80	8	DUAL TRANS. MATCHED O/P PAIRS NPL-SIL INTO-5 CAN	10/-
B82	10	OC45, OC81D & OC81 TRANS MULLARD GLASS TYPE	10/-
B83	200	200 TRANSISTORS. MAKERS REJECTS. NPN-PNP. SIL & GERM.	10/-
B84	100	SILICON DIODES DO-7 GLASS EQUIV. TO OA200, OA202	10/-
B86	150	HIGH QUALITY GERM. DIODES MIN. GLASS TYPE	10/-
B86	50	SIL. DIODES SUB. MIN. IN914 & IN916 TYPES	10/-
B87	100	GERM. PNP TRANS. EQUIV. TO OC44, OC45, OC81, ETC.	10/-
B88	50	SIL TRANS. NPN, PNP EQUIV. TO OC200/1, 2N706A, BSY95A, ETC.	10/-
B80	10	7 WATT ZENER DIODES. MIXED VOLTAGES	10/-
H5	16	1 AMP. PLASTIC DIODES 50-1000 VOLTS	10/-
H6	40	250mW. ZENER DIODES DO-7 MIN. GLASS TYPE	10/-



**SPECIAL OFFER**  
12 VOLT STABILISED  
POWER UNITS  
INPUT 110-250 V. AC.  
OUTPUT 11-13V Stabilised  
at 1 amp.  
Brand New makers surplus  
at the unrepeatabe  
Price of £5 each  
Post & Packing 7/6

**FREE!** A WRITTEN GUARANTEE WITH ALL OUR TESTED SEMICONDUCTORS

# BI-PRE-PAK LTD

DEPT. B, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX  
TELEPHONE: SOUTHEND (0702) 46344



# APPOINTMENTS VACANT

**DISPLAYED SITUATIONS VACANT AND WANTED:** £7 per single col. inch.  
**LINE advertisements (run-on):** 8/- per line (approx. 7 words), minimum two lines.  
Where an advertisement includes a box number (count as 2 words) there is an additional charge of 1/-.  
**SERIES DISCOUNT:** 15% is allowed on orders for twelve monthly insertions provided a contract is placed in advance.  
**BOX NUMBERS:** Replies should be addressed to the Box number in the advertisement, c/o Wireless World, Dorset House, Stamford Street, London, S.E.1.  
No responsibility accepted for errors.

Advertisements accepted up to  
**THURSDAY, 12 p.m., 8th JAN.**  
for the FEB. issue, subject to  
space being available.

## Senior Test Engineer

H.N.C. or equivalent knowledge of electronics. Responsibility will be to the Q.C. Manager for the supervision of the Test Room. Good knowledge of Transistor Pulse and Linear Circuitry Test procedures are essential. His main technical responsibility will be the commissioning of complete equipment and assisting in the assessment of new equipment.

### TEST ENGINEERS

Required for the above Test Room.  
Please apply:

**PANAX EQUIPMENT LIMITED**  
Holmethorpe Industrial Estate,  
Redhill, Surrey  
Tel: 63511

2765



## COMMUNICATIONS ENGINEER

British Petroleum has a vacancy for a Communications Engineer for Das Island in the Arabian Gulf. This is a bachelor posting only, but with generous home leave allowances. The successful candidate will be required to work on the installation, maintenance and supervision of an offshore oil producing, modern telecommunications, telemetry and control network.

Candidates should possess a minimum of HNC or equivalent and have several years experience in telecommunications/electronics.

Apply giving details and quoting reference R 11106/9WW to P. J. Montanjees, External Recruitment, The British Petroleum Company Limited, Britannic House, Moor Lane, London E.C.2.

UNIVERSITY OF CAMBRIDGE

## ELECTRONICS TECHNICIAN

required. Opportunity to gain experience of a wide range of instrumentation and to continue training on a day-release basis, if required. Candidates should have either ONC and be studying for HNC or have substantial servicing experience not necessarily in the field of chemical instrumentation.

Salary in the range of £924—£1,266.

Apply to the Superintendent, University Chemical Laboratory, Cambridge CB2 1EW.

2755

COUNTY BOROUGH OF LUTON

## Telecommunications Technician

For the Borough Architect's Department for servicing ground-to-air equipment at Luton Airport. The duties will involve the servicing of Decca 424 Radar, Marconi AD 210C Direction Finder, Mufax facsimile reproduction equipment and I.L.S. equipment.

Applicants should be in possession of City and Guilds Telecommunications Full Technological Certificate or Finals, but holders of Intermediate who are still studying will be considered.

Duties will involve shift working. Commencing salary within Technician Grades T.4/5/6 (£1,095-£1,775 per annum) according to qualifications and experience. Housing accommodation considered. Reasonable removal expenses paid.

Forms of application may be obtained from the Chief Executive Officer and Town Clerk, Town Hall, Luton, Beds., to whom completed applications should be returned as soon as possible.

2745

# Radio Operators

## Your chance of a shore job with good pay from the start!

If you hold a 1st Class Certificate of Competence in Radiotelegraphy issued by the Postmaster General or the Ministry of Posts and Telecommunications, or an equivalent certificate issued by a Commonwealth administration or the Irish Republic, the Post Office can now offer you a starting salary of £917-£1149 or, after 1st January, 1970, £965-£1215 (depending on your age). Annual rises will take you to £1650 and there are good prospects of promotion to more responsible and better paid posts.

If you are over 21, write for more details to:

**The Inspector of Wireless Telegraphy,  
External Telecommunications Services,  
Wireless Telegraphy Section, (ww)  
Union House, St. Martins-le-Grand,  
LONDON E.C.1.**

2682

# ELECTRONIC SYSTEMS SERVICE ENGINEERS

## THE JOB

Systems Service Engineering on Advanced Training Aids for Aircraft, Radar Networks, Nuclear Reactors and Submarines.

## THE MAN

Electronic Engineer preferably with O.N.C. or H.N.C. having had practical experience of electronic devices with a keen desire to learn new techniques and applications.

## THE AWARDS

Salary offered will be up to £1700. High job interest. Opportunity to work on complex systems incorporating digital and analogue computers, associated peripherals, colour television systems and servo systems, as a member of a team. Opportunity to fly and operate simulated aircraft and other equipments. High quality training will also be given.

## OTHER BENEFITS

Our terms and conditions of employment are good and include contributory pension scheme, free life assurance, etc. We are not merely offering posts which will afford candidates opportunities of attaining a good job. Selected candidates will be offered long-term careers. Opportunities for travel at home and overseas.

There are vacancies at both Aylesbury and Crawley locations. Applications should be made in the first place to

H. C. Hall, Personnel Manager  
REDIFON LIMITED  
Flight Simulator Division  
Gatwick Road, Crawley, Sussex  
Tel: Crawley 28811

**REDIFON** 

A Member Company of the Rediffusion Organisation

2694

**RACAL INSTRUMENTS LIMITED**  
**AIRMEC DIVISION**  
**SEATON, DEVON**

## REQUIRE TEST ENGINEERS

To work on a wide range of analogue and digital measuring instruments employing the latest techniques.

Entrants may be graded as Test Engineers Grade I, Grade II or Project Leaders according to qualifications and experience.

Salaries up to £1,600 per annum.

These positions offer permanent and progressive employment in a seaside area of great natural beauty. Both private and local authority housing will be available.

Apply:

**Personnel Department,**  
**Racal Instruments Limited,**  
**Airmec Division, Seaton, Devon.**  
Or telephone Mr. G. Hatt, Chief of Test.  
Seaton 1100/1.

2727

## SENIOR ELECTRONICS INSPECTOR

Due to expansion a vacancy for inspector has been created. Applicant will preferably have several years of inspection experience and be familiar with defence specifications and B.S. 9,000 procedure. A knowledge of high precision electrical and coaxial connectors would be advantageous, but a sound basic knowledge of electronic equipment may in itself be sufficient.

Attractive conditions of employment and commencing salary would be offered with good prospects of promotion for the right man.

Please apply in writing to:

**Technical Manager,**  
**PRECISION CONNECTORS LIMITED,**  
**56-58 GREEN STREET,**  
**FOREST GATE,**  
**LONDON, E.7. Tel.: 01-552 3405**

**A member of the Delta Metal Group  
of Companies.**

2736

# Government of UGANDA REQUIRES BROADCASTING ENGINEERS

To serve on contract for one tour of 21-27 months in the first instance. Salary according to experience in scale Uganda Shg. 21,120-27,780 (£Stg. 1,232-1,620) a year, plus an Inducement Allowance, normally tax free, of £Stg. 778-886 a year, paid direct into a Uganda bank account nominated by the officer. Gratuity 25% of total emoluments drawn. Liberal paid leave. Accommodation provided at reasonable rental. Outfit and education allowances. Free passages. Contributory pension scheme available in certain circumstances.

Candidates must possess the City and Guilds Final Certificate in Telecommunications (with Radio) or an equivalent qualification and have wide practical experi-

ence of technical broadcasting equipment including transmitting and studio control equipment.

The officer will be required to undertake senior operational duties including the maintenance of broadcasting equipment in transmitting stations and studios; outside broadcasts and recordings in remote districts; and to give assistance with the training of junior engineering staff.

Apply to CROWN AGENTS, 'M' Division, 4 Millbank, London, S.W.1., for application form and further particulars stating name, age, brief details of qualifications and experience and quoting reference M2K/690995/WF.

2691

## TECHNICIAN required for ELECTRONICS WORKSHOP

Applicants should have a minimum of two years' experience of construction and/or servicing of electronic equipment using transistors and integrated circuits, and some knowledge of digital and pulse techniques. Qualifications to ONC or Intermediate City and Guilds technicians level. Opportunities for day release. Salary according to age, qualifications and experience.

Apply to the Administrative Secretary, Medical Research Council's Laboratory of Molecular Biology, Hills Road, Cambridge.

2731

## NORTH-EAST ESSEX TECHNICAL COLLEGE

Sheepen Road, Colchester

DEPARTMENT OF ELECTRICAL ENGINEERING

## LECTURER GRADE II

is required to teach TELECOMMUNICATION SUBJECTS up to first degree standard. Applicants must have a University degree in Electrical Engineering or Physics with suitable teaching and/or industrial experience. Salary: Lecturer Grade II—£1,827-£2,417 p.a. Assistance with removal expenses may be considered.

Application forms are available from the Principal at the College, to whom they should be returned within fourteen days of the appearance of this advertisement. Please state ref. WW.

2730

Rank Strand Electric Limited, who are leaders in their field of theatre and television studio equipment, require two

## electronics commissioning engineers

around £1,500 p.a.

To test and commission sophisticated lighting control systems into theatres and television studios at home and abroad.

Based with the Research and Development Unit at Brentford, Middlesex, they will initially complete a three-month training course before commencing operations in the field.

Applicants must have sound knowledge and experience of electronics. Ability to communicate effectively with customers important. Knowledge of theatre and television an advantage.

Must be willing to travel extensively and work irregular hours.



Please apply for application form: The Personnel Officer,  
Rank Strand Electric Limited, 29 King Street, Covent Garden,  
London, W.C.2. 836 4444 ext. 147/148



**The Rank Organisation**  
The man with the gong — a man of many skills



2681



Become a  
**RADIO  
TECHNICIAN**

and work at  
the nerve centres  
of civil aviation

The National Air Traffic Control Service of the Board of Trade needs Radio Technicians to install and maintain the very latest electronic aids at Civil Airports, Air Traffic Control Centres, Radar Stations and specialist establishments. Vacancies exist in various parts of the United Kingdom.

This is responsible demanding work (for which you will get familiarisation training) involving communications, computers, radar and data extraction, automatic landing systems, and closed-circuit television. It offers excellent prospects with ample opportunities to study for higher qualifications in this fast-expanding field.

If you are 19 or over, with at least one year's practical experience in telecommunications, fill in the coupon now. Preference will be given to those having ONC or qualifications in Telecommunications.

Salary: £985 (at 19) to £1,295 (at 25 or over); scale maximum £1,500 (higher rates at Heathrow). Some posts attract shift-duty payments. The annual leave allowance is good and there is a non-contributory pension scheme for established staff.

Complete this coupon for full details and application form:  
To: A. J. Edwards, C. Eng., M.I.E.E., M.I.E.R.E., Room 705, The Adelphi,  
John Adam Street, London WC2, marking your envelope 'Recruitment'.

Name \_\_\_\_\_

Address \_\_\_\_\_

ww/B3

Not applicable to residents outside the United Kingdom.

**NATCS** National Air Traffic Control Service

2689

**INTERTEL  
COLOUR TELEVISION**

requires

**ENGINEERS**

in their Vision and Video Tape Departments to be based at their Dean Street, London, Studio. Applicants should have a good working knowledge of Colour Television Practice.

Applications to:

**CHIEF ENGINEER  
INTERTEL COLOUR TELEVISION  
WYCOMBE ROAD, WEMBLEY  
MIDDLESEX**

2726

**computer  
engineering**

NCR requires additional ELECTRONIC, ELECTRO MECHANICAL ENGINEERS and TECHNICIANS to maintain medium to large scale digital computing systems in London and provincial towns.

Training courses will be arranged for successful applicants, 21 years of age and over, who have a good technical background to ONC/HNC level, City and Guilds or radio/radar experience in the Forces.

Starting salary will be in the range of £900/£1,250 per annum, plus bonus. Shift allowances are payable, after training, where applicable. Opportunities also exist for Trainees, not less than 19 years of age, with a good standard of education, an aptitude towards and an interest in, mechanics, electronics and computers.

*Excellent holiday, pension and sick pay arrangements. Please write for Application Form to Assistant Personnel Officer NCR, 1,000 North Circular Road, London, NW2 quoting publication and month of issue.*

Plan your future with **NCR**

85

# Government of Zambia

## REQUIRES

# MAINTENANCE ENGINEER

for the Zambia Broadcasting Services, Ministry of Information, Broadcasting and Tourism, on contract for one tour of 36 months in the first instance. Commencing salary Kwacha 3,408 (£Stg. 1988) rising to Kwacha 3,516 (£Stg. 2051) a year, plus an Inducement allowance of Kwacha 1002-1034 (£Stg. 585-£Stg. 603). A Direct Payment of £291 is also payable direct to the officer's bank in the U.K. Salaries are subject to upward revision with effect from 1st January 1970. Gratuity 25% of total salary drawn. Both Gratuity and Direct Payment are normally TAX FREE. Free passages. Accommodation at moderate rental. Education allowances. Liberal leave on full salary or terminal payment in lieu. Contributory pension scheme available in certain circumstances. Candidates, between 25-55, must have passed City and

Guilds final certificate in Telecommunications or equivalent and should have had at least eight years experience with a broadcasting organisation, with particular experience in the installation of recording equipment and studio control equipment.

The officer will be required to maintain and service audio-visual aid equipment and install and operate public address/recording film projection equipment when and where required. He will be required to supervise workshops and staff in the absence of the Senior Maintenance Engineer.

**Apply to CROWN AGENTS, 'M, Division, 4 Millbank, London, S.W.1., for application form and further particulars stating name, age, brief details of qualifications and experience and quoting reference number MzZ/691029/WF.**

2692

### EXETER AND MID-DEVON HOSPITALS MANAGEMENT COMMITTEE GROUP WORKS DEPARTMENT

#### Technician—Medical Physics Grade II,

for maintenance of dialysis machines and electronic equipment.  
Salary £1,313 x (8) to £1,671.  
Qualifications required—H.N.C. or H.N.D. in Electrical Engineering or equivalent.

Applications together with names of three referees to reach the Group Engineer, 26 Queen Street, Exeter, Devon, within 10 days.

2769

## COMPUTER STAFF

Vacancies exist in our Computer Services Dept. for EQUIPMENT CONTROLLERS to be responsible for the installation and performance monitoring of three IBM360/50 Computers used for real-time data processing. Applicants should have some knowledge of digital computers and may at present be employed as commissioning engineers or in a similar post. Knowledge of teleprocessing, Datel services and computer terminal equipment would be an advantage though it is not essential as full training will be given.

Salary up to £2000 according to experience and ability. Assistance with house purchase is available.

Please apply in writing giving full particulars to: P. Jordan, Computer Services Manager, CENTRE-FILE LTD., Park House, 16 Finsbury Circus, London, E.C.2.

2763

## GEC-Marconi Electronics

### Technicians and Engineers for St. Albans and Luton

*qualified or not!*

#### Vacancies in all grades

- **VACANCIES** exist for work on testing and calibrating valve and solid-state electronic measuring equipments embracing all frequencies up to u.h.f. in Production, Service and Calibration departments.
- **APPLICATIONS** are invited from people of all ages with experience or formal training in electronics and from ex-Armed Services technicians.
- **SALARIES** up to £1,600 negotiable and backed by valuable fringe benefits.
- **RE-LOCATION EXPENSES** available in many instances.
- **CONDITIONS** excellent: free life assurance, pension schemes, canteen, social club.
- **37½-hour, 5-day, office-hours week.**
- **WRITE** or 'phone Personnel Department stating age, details of previous employment, training, qualifications, approximate salary required.



**Marconi  
Instruments  
Limited**



Longacres, St. Albans, Herts. Tel: St. Albans 59292  
Luton Airport, Luton, Beds. Tel: Luton 31441

A GEC-Marconi Electronics Company

2671

# Product Test Technicians

## Career Opportunities with IBM Manufacturing

We need high calibre men to fill vacancies created by promotion and programme expansion.

### The job

Is to commission the latest IBM products and systems in production at the Scottish plant, near Greenock, and requires an intimate knowledge of the equipment under test, which can include computers, punched card and tape peripherals, magnetic disk and tape storage, high and low speed printers, visual display units, multiplexors, Tele-processing and optical character recognition equipment. The products have to be tested thoroughly, and all faults traced and rectified. The work is interesting and absorbing, and the prospects for the right man are good.

### Training

Will be a mixture of formal and "on the job" instruction. We will teach you all you need to know about IBM equipment - providing your basic knowledge is to the required level.

### Pay and conditions

Starting salaries will be excellent.

Benefits include a non-contributory pension, immediate free life assurance and full sickness pay for up to 26 weeks in any 12 months. The 254,000 square feet plant is modern and situated in a pleasant rural valley. There is a subsidised restaurant.

Working conditions are excellent and there are good recreational facilities in the area. IBM will assist with removal expenses where applicable.

### The man

Will be at least 18 and probably less than 30 and have a strong electronic background, with experience in, for example, the testing of electronic products, maintenance of radio, radar or TV or similar work in the armed forces.

He will probably have, or be near to attaining, a qualification such as HNC, ONC, first class PMG, final RTEB, or final City and Guilds (Course Nos. 47, 48, 49, 57, 300). A knowledge of transistor circuitry and the use of oscilloscopes will be a distinct advantage.

If you have what we need, and are keen to join a vigorous, expanding and up-to-the-minute industry, please write, giving details of your age, experience and qualifications, and quoting ref. No. PT2/WW/169

to: Manager, Personnel Selection,  
IBM United Kingdom Limited,  
P.O. Box 30, Spango  
Valley, Greenock.

**IBM**



2690

# ASSISTANT ENGINEERS (INSTRUMENTS)



for  
**TRAWSFYNYDD NUCLEAR POWER STATION**  
Trawsfynydd, Merionethshire, North Wales.

The work involves the diagnosing of system faults, carrying out special investigations, originating, modifications and designing special test equipment. The successful applicant will also be expected to assist in the training of Maintenance Craftsmen. Some experience within this field would be an advantage.

Applicants must possess academic qualifications leading to Graduate Membership of the I.E.E. or I.E.R.E.

Salary is within the range £1,500 - £1,880 per annum. Superannuable.

Conditions of service are in accordance with the National Joint Board Agreement for the Electricity Supply Industry.

Applications in writing stating age, experience etc., to  
**Regional Personnel Manager, 825 Wilmslow Road, East Didsbury, Manchester M20 8RU** to arrive not later than 30th December 1969. Please quote Vacancy No. E.566/567/W.

2698

# University of London Audio-Visual Centre

requires

## TELEVISION ENGINEERS and JUNIOR TELEVISION ENGINEERS

to work on maintenance and operational duties with its studio and mobile equipment, under the supervision of the **Chief Engineer, R. H. Bradley, MBE.**

Applicants for the post of Television Engineer should have technical experience in broadcast or educational television. A broad knowledge of other audio-visual equipment would be an advantage.

Applicants for the Junior posts should be 18-20 years old, with a basic knowledge of electronic equipment and some experience in its use. Formal technical or educational qualifications would be an advantage.

Salaries:

TV Engineer. Starting at £1600-£2000 according to qualifications and experience. University Pension Scheme.  
Junior TV Engineer. Starting salary £800-£1000 according to qualifications.

**Applications to the Director:  
University of London Audio-Visual Centre  
11 Bedford Square, London, WC1**

2759

# EAST AFRICAN COMMUNITY

## Meteorological Department requires

### Sectional Engineer Grade II (Telecomms.)

To serve on contract for one tour of 21-27 months in the first instance. Salary in scale EA.Shg. 24300-27780 (approx. £S.1417-1620 p.a.) plus an Inducement Allowance normally tax free, of £S.822-886 p.a. paid direct into officer's bank in U.K. Gratuity 25% of total emoluments. Generous paid leave. Education Allowances. Furnished accommodation at reasonable rental. Free passages. Contributory pension scheme available in certain circumstances.

Candidates, up to age 45, must possess O.N.C. or City and Guilds Final Certificate (Telecomms) plus 7 years relevant experience in telecomms. engineering. Equivalent experience in one of the armed services is acceptable. Candidates must have a good theoretical and practical knowledge of FSK, ISB and SSB receivers and trans-

mitters and of Mufax and facsimile transmitters and recorders. A good working knowledge of radar systems is essential.

The officer will be responsible to the Chief Sectional Engineer for the operation and maintenance of the Department's radio telecommunications, radio-sounding and radar equipment. He will be liable for service anywhere in East Africa but will probably be stationed at Entebbe, Dar es Salaam or Nairobi.

Apply to CROWN AGENTS, 'M' Division, 4 Millbank, London, S.W.1., for application form and further particulars stating name, age, brief details of qualifications and experience and quoting reference number M2K/690413/WF

## TECHNICIAN

required for calibration and servicing of flow meter instruments. Electronic experience required in television servicing or pulse techniques. Transistor experience essential. Digital experience an advantage. Good commencing salary and prospects. Permanent pensionable position.

Apply: **B. RHODES & SON LTD.,**  
Danes Road, Off Crow Lane,  
Romford, Essex.  
Telephone Romford 62333/4/5.

2774

## ELECTRONICS TECHNICIANS

SENIOR TECHNICIAN prototype wireman required for research contract. TECHNICIAN for interesting project and development work in research and teaching laboratories. Day release available.

Incremental salary ranges £868-£1252, £1151-£1486 depending on age, experience and qualifications. 37½ hour week, good working conditions and holidays. Apply in writing to Mr. E. Thompson, Royal School of Mines, Mining & Mineral Technology Department, Prince Consort Road, London SW7

2764

# Electronics Engineer

Professional Audio, Video and  
Instrumentation Equipment.

3M Company, one of the world's foremost names in magnetic recording, is expanding distribution of its "Mincom" range of equipment in the audio, video and instrumentation fields in the United Kingdom.

An interesting opportunity is available for a young man aged 23-26 to join us as an Electronics Engineer. He must possess a good electronics background, possibly obtained in the radio communications field. Ideally he should be qualified to C & G or ONC/HNC standard but lesser qualifications may be acceptable in the case of an

applicant with exceptional practical experience.

The position will be London based but ultimately the successful applicant will be required to undertake some travelling working on his own initiative on field assignments.

*This is a progressive position in a fast growing field. The starting salary will be attractive and there are first class employee benefits. Please write in confidence with concise details, age, qualifications and experience to:*

**Mr. D. J. Stuckey (Ref. MT)**  
3M Company Ltd.,  
3M House,  
Wigmore Street,  
London W1A 1ET.



# TECHNICAL AUTHORS

We are one of the World's leading manufacturers of Flight Simulators which incorporate both analogue and digital computers. We require Technical Authors with a sound knowledge of electronics who preferably have some knowledge of basic digital computer operation. Authors will produce operating and maintenance manuals, and must be able to write literature in a clear and concise style. Formal qualifications are desirable, but not essential. There will be ample opportunity to employ a measure of creative expression. Simulation is based on novel applications of known techniques. This work is certainly not of a monotonous nature.

# INSTRUCTORS

are required to lecture to customers and engineers on digital and analogue computing techniques at basic, intermediate and advanced levels. Students are required to maintain and programme highly sophisticated flight simulators. Applicants should preferably be qualified to at least H.N.C. level or equivalent. Preference will be given to those with practical analogue or digital computing experience, but applications from men with several years' industrial experience and/or who have a flair for and a genuine interest in lecturing will certainly be welcome. Training in the Company's advanced computing techniques will be given.

This Company offers good working conditions, welfare benefits. There is a contributory pension scheme coupled with free life assurance.

Apply to: H. C. Hall, Personnel Manager,  
REDIFON LIMITED

**Flight Simulator Division,  
Gatwick Road, Crawley, Sussex  
Telephone: Crawley 28811**



A Member Company of the Rediffusion Organisation

## ST. JOHN'S COLLEGE OF EDUCATION • YORK

### Dept. of Closed Circuit Television

Applications are invited for the post of SENIOR TECHNICIAN, to join a team making television programmes for this and five associated colleges.

Duties will include the maintenance of cameras and videotape recording equipment. Opportunities for operational and production work will occur. A mobile recording van is in regular use and ability to drive would be an advantage.

Salary: Local Government Scales: Technical Grade 6 (at present £1,540-£1,775): the post is superannuated and good holidays are given.

**Applications (no special form), should be made in writing to the Principal, stating qualifications, experience and the names of two referees. Closing date 31st December, 1969.**

2762

## SOUTH AFRICA

### FULLY QUALIFIED RADIO & TELEVISION TECHNICIAN

Applicants should be capable of supervising a workshop from which the installation and repairs to all types of radios and television are undertaken.

Applications with full details of experience etc., should be sent in the first instance to Mr. E. B. UNWIN.

**NEL & UNWIN (PTY) LTD.  
P.O. BOX 199, KROONSTAD  
SOUTH AFRICA**

# CONTINUOUS EXPANSION

Standard Telephones & Cables, Microwave and Line Division based at Basildon are growing fast. In order to keep pace with this consistent growth rate we require the following


## Installation Engineers Technicians & Testers

Ref. 25720

To test and commission Multiplex, Co-axial Line and Microwave Radio Systems.

Ideal candidates will be less than 45 years of age with practical experience on some of the above equipment. These challenging posts call for drive, initiative and common sense. It is necessary for applicants to be prepared to work anywhere in the U.K.

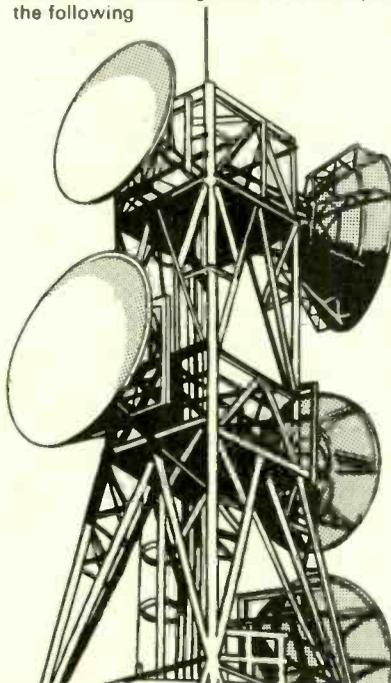Applications should be addressed to  
The Personnel Officer,  
STC Chester Hall Lane,  
Basildon, Essex.



## Test Technicians

Ref. 27221

The diversity of products manufactured at the Basildon Plant demands experienced testing staff for work on complex transmission systems.

Candidates should hold an ONC in electrical engineering and be able to offer considerable practical experience in the field of testing and fault clearing all types of land-unit, pcm and microwave equipment.

# STC

91

## TECHNICIAN

required in APPLIED ACOUSTICS RESEARCH LABORATORIES situated near Fulham Broadway, S.W.6. Varied work, but a knowledge of electronic construction and design an advantage. Day release facilities for further study.

Salary: £868—£1,252 p.a., depending upon age, experience and qualifications.

Application forms and further information from the Superintendent of Laboratories (T.A.), Department of Physics and Electronics, Chelsea College, Manresa Road, London, S.W.3. 2735

## EAST SUFFOLK COUNTY COUNCIL

Lowestoft College of Further Education  
Principal A. E. Boddy, B.Sc. (Econ.), F.R.G.S.

## LECTURER GRADE 1

required for City and Guilds Radio and Television Servicing Mechanics' and Technicians' Courses, including colour television.

Applicants should have appropriate technical qualifications, together with suitable Industrial and Teaching experience. Ability to offer teaching in similar courses would be an advantage.

The appointment is vacant as from the 1st April, 1970, but an earlier commencing date may be negotiated.

Salary in accordance with the Burnham Scale for Lecturers Grade 1, £1,110 to £1,955, plus increments for approved qualifications and training. Starting point within the scale determined by previous Industrial and Teaching experience.

Applications should be sent as soon as possible to The Principal of the College, on application forms available from the Secretary, Lowestoft College of Further Education, St. Peter's Street, Lowestoft, Suffolk. 2768



## SENIOR LABORATORY TECHNICIAN

**A SENIOR ASSISTANT** with a good understanding of electronics is needed to join a small team providing physics support to the Isotope Production Unit at Harwell. The team is mainly concerned with making accurate measurements of a wide variety of radiation sources and with the development and maintenance of the necessary measurement system. The post is tenable at Harwell.

### QUALIFICATIONS & EXPERIENCE:—

The minimum age for appointment is 27 and the minimum qualifications necessary are four 'O' levels including English Language and Mathematics or a Science subject. Electronics experience is essential and experience in the measurement of radiation sources would be advantageous.

**SALARY: £1,350 rising to £1,755**

**APPLY TO: The Personnel Officer**

**THE RADIOCHEMICAL CENTRE**  
Amersham Bucks

# SKILLED IN ELECTRONIC ENGINEERING?

## Help keep aircraft on the straight and narrow

Air traffic has become so congested that complex electronic techniques are used as an aid in controlling aircraft both on airways and on airport approaches. As a Telecommunications Technical Officer III in the National Air Traffic Control Service of the Board of Trade, your job would be to install and maintain various air navigational and landing aids at civil airports, and communications and computer systems at radar stations and signals centres.

Because you handle such advanced equipment, you will receive thorough training. Study for higher qualifications is encouraged, and this could range from short courses with financial assistance to full-time study at a university or technical college.

**Pay:** (London rates—a little less elsewhere) £1,350 starting salary at 23, £1,625 at age 28 or over on entry, rising to £1,810. Within 3 years you could be upgraded, and on a scale rising to £2,050. A few years after that, you could be in the salary bracket going up to £2,375, and there are several higher grades still.

**Qualifications:** O.N.C. in Engineering, including a Pass in Electrical Engineering; or equivalent standard of technical education.

Send for full details and an application form (which must be returned completed by January 2nd, 1970) to: Civil Service Commission, 23 Savile Row, London, W1X 2AA. Please quote S/207/-.

### HENRY'S RADIO LTD.

303 EDGWARE ROAD, LONDON, W.2  
HAVE THE FOLLOWING VACANCIES IN THEIR ORGANISATION

#### SALES ASSISTANTS

Young man with good general knowledge of electronic components required for our retail sales dept. Please telephone 723-1008/9 ext. 1.

#### SALES ASSISTANTS

Young man with a good general knowledge of HIGH FIDELITY EQUIPMENT required for our retail HI-FI SALES DEPT. Please contact MR. STEVENS, Telephone 723-6963. 2585

An immediate vacancy occurs at

### THE WIRELESS COLLEGE COLWYN BAY, NORTH WALES

for an additional instructor to assist in preparing students for P.M.G./M.P.T. examinations. The primary responsibility will be the practical instruction on modern marine radio equipment. Applicants must hold a P.M.G. Certificate and should have a sound technical knowledge. Recent marine operating and/or teaching experience is desirable but not essential. Write in the first instance to the Principal. 2776

### SPECIAL OPPORTUNITY

Small company in medical electronics development (Richmond, Surrey) offers starting salary £1300 to keen man suitable early directorship. Founder approaching retirement. Self-contained flat available. Phone 01-940 0865 evenings. 2766

### SITUATIONS VACANT

**A FULL-TIME** technical experienced salesman required for retail sales; write giving details of age, previous experience, salary required to—The Manager, Henry's Radio, Ltd., 303 Edgware Rd., London, W.2. [67]

**ARE YOU INTERESTED IN HI FI?** If so, and you have some experience of selling in the Retail Radio Trade, an excellent opportunity awaits you at Teleonic Ltd., 243 Euston Road, London, N.W.1. Tel. 01-387 7467. [21]

**CENTRAL AMERICA:** Radio Engineer required to install and manage broadcasting equipment at new Radio School to be established at Choluteca, Republic of Honduras. Challenging post for the adventurous, trying to get out of the rut! Volunteer terms: fares, board, lodging, pocket-money, allowances. — Write: CIIR/OV, 38 King Street, London, W.C.2. [2737]

**CHIEF ELECTRONICS TECHNICIAN** required to supervise Electronics Workshops developing and maintaining electronic equipment for use in the teaching and research laboratories of the Departments of Electronics and Physics. Salary £1,510—£1,703 p.a. according to age and experience. Further information and application form from the Laboratory Superintendent, Departments of Physics and Electronics, Chelsea College, Manresa Road, London, S.W.3. [2775]

**COLOUR TELEVISION.** Multi-National Advertising Agency require a Technical Assistant, or Assistant Engineer, to operate and maintain colour television film scanning equipment. Candidates should be between the ages of 22 and 30 and should have "C" and "O" Telecomms. or equivalent, and preferably with experience on this type of equipment. Salary is negotiable. Write to Mr. R. Martin, J. Walter Thompson Co. Ltd., 40 Berkeley Square, W1X 6AD. [2753]

**ELECTRONICS TECHNICIAN** required to assist in the development, construction and installation of electronics instruments used in biochemistry. Applicants should possess O.N.C. or equivalent and be able to construct and test equipment from circuit diagrams. Salary according to age and experience in the range of £1,025 to £1,295 per annum. Supplementary payments for certain qualifications. Superannuation scheme. Good conditions of service. Applications in writing to Departmental Superintendent, Department of Biochemistry, MRC Metabolic Reactions Unit, Imperial College, London, S.W.7. [2778]

**ELECTRONIC TEST ENGINEERS** required for work on a new range of Digital Measuring Equipment using Silicon Transistors and Microcircuits. Fully qualified applicants preferred, although proven experience in electronics would be considered. Prospects for advancement are good. Weekly staff status and salary commensurate with qualifications and experience. We would welcome applications from ex-service personnel or those about to leave the services. Please apply to: The Personnel Manager, Vener Limited, Kingston By-Pass, New Malden, Surrey. Telephone: 01-942 2442. [2760]

**I.P.C. research and development. ELECTRONIC ENGINEERS AND TECHNICIANS.** Advanced optical/electronic systems to process text and pictures for publication are being developed in the Information Science and Technology Unit's laboratory. There are several immediate opportunities for QUALIFIED ELECTRONIC ENGINEERS to join a team working on the design and development of systems using computer, CRT, TV, and optical techniques. Expert knowledge in at least one of these is essential. Salaries within the Development Officer scale, ranging from £1,500 to £3,500. LABORATORY TECHNICIANS for layout, construction and testing of prototype electronic apparatus. Salary scale up to £1,675. Write for application form to the Director of R & D, IPC Laboratories, Wood Lane, Hemel Hempstead, Herts. [2748]

**QUALIFIED ENGINEERS** considering emigration to Australia 1970 required to join new and vigorous firm of communications consultants. Interviews London and Birmingham. Brief resumé to Box W.W. 2627, Wireless World.

### SENIOR DEVELOPMENT ENGINEER.

WW.21.

£1900.

Our clients seek electronics engineer of at least H.N.C. standard with additional qualifications in control or digital techniques preferably around 30 years and living, or prepared to work, in the Hertfordshire area. The applicants should have shown some administrative ability in project coordination, possibly in avionics, military control systems, or high speed digital control circuits.

Please apply in writing and in strict confidence, quoting the above reference to:



### ELECTRONICS APPOINTMENTS LTD.

NORMAN HOUSE · 105/109 STRAND · LONDON · W.C.2  
TEL · 01-836 5557

2697

89

# ELECTRONICS TECHNICIANS



## this is the business machine explosion

Turnover doubled since 1962—now growing faster in the decimalization rush. Burroughs dominate the U.K. market in the new terminal computers and accounting machines. A wide variety of machines, an expanding market and a policy of promotion from within—all mean exciting opportunities, for trained electronics engineers, to develop their skills into the computer field or into the supervisory grades and beyond. Join the Burroughs boom—and grow with us.

If you are between 20 and 30, with an electronics qualification and want to train as a computer engineer—then there's a job for you with us. With Burroughs, you can find the free-



# Burroughs

dom to develop your talents, open fresh horizons, learn new skills—on the largest third-generation systems in the World—these are the exciting prospects at Burroughs. In return, we're offering you 3 weeks' paid holiday, free life assurance and a contributory pension scheme.

Take a big step now into one of today's development industries—fill in the coupon and send off for one of our application forms. The address is:

**Bob Timms, Personnel Officer,  
Burroughs Machines Limited (Z),  
Heathrow House, Cranford, Hounslow, Middlesex.**

NAME.....

ADDRESS.....

WW/d22/jan

2680

### Hampstead High Fidelity

require the services of a qualified

## SERVICE ENGINEER

He must be conversant with the repair and service of quality High Fidelity equipment, a useful asset would be experience with CCTV and Colour TV. The man we are seeking must be very conscientious, adaptable and prepared to undertake occasional field work. He will be expected to set up and organise a completely new service department and control a small staff.

Applications are invited in writing giving full details of qualifications, experience, etc., and marked for the attention of P. A. Rispoli, Esq., Hampstead High Fidelity, 91 Heath Street, London, N.W.3. 2746

### UNIVERSITY OF ESSEX

### DEPARTMENT OF PHYSICS

## SENIOR TECHNICIAN

required for maintenance of electronic equipment, supervision of equipment in a teaching laboratory and assistance to research groups. Candidates should preferably have H.N.C. or equivalent qualification in electronics and experience with modern electronic circuitry and equipment. Salary range £1,056-£1,311 with additional allowance for approved higher qualifications.

Applications to the Registrar, University of Essex, Wivenhoe Park, Colchester, Essex.

2732

# V.H.F. TELEVISION RELAY & COMMUNAL AERIAL SYSTEMS

We are planning a considerable expansion of our activities and have the following vacancies:

## I. A SENIOR ENGINEER

to have control of all aspects of systems design, planning, estimating, installation and commissioning.

## II. ENGINEERS

capable of undertaking either:

(a) System planning and estimating.

(b) control of installation work.

or (c) test and commissioning duties.

Candidates for these appointments must have a good background of practical experience in this field of work, and an up-to-date knowledge of techniques and equipment.

Applications, which will be treated in strict confidence, should be sent to:

## BRITISH RELAY

The General Manager,  
Special Services Division,  
British Relay House,  
41, Streatham High Road, S.W.16

2654

# REDIFFUSION

## Television Service Management

Applications are invited for vacancies in the North East Region from mature T.V. Service Managers who are experienced in the operation of a large scale rental service organisation.

Applicants must be technically competent and have a strong flair for the solution of organisational, administrative and personnel problems.

An attractive salary will be offered and a car provided.

Applications please to:

The Chief Engineer,  
Rediffusion (North East) Ltd.,  
Rediffusion House,  
Forth Banks,  
Newcastle upon Tyne,  
NE1 3RX.

2683

### BRISTOL POLYTECHNIC FACULTY OF APPLIED SCIENCE

Applications invited for the following post, duties to commence as soon as possible—

## SENIOR TECHNICIAN IN PHYSICS

(Grade T.3)—Ref. No. T698/66/2

to take charge of Nuclear Physics/Radiochemistry Laboratory.

Applicants should be over 21 and have qualifications to at least O.N.C. or C. & G. Ordinary Technician standard and previous laboratory experience. 38-hour, 5-day week with generous holiday and sick pay schemes. Opportunities for evening work with additional pay. Permanent posts with superannuation under Local Government conditions of service.

Salary Scale: £930—£1,095. Starting salary dependent upon age, qualifications and experience. An additional £50 or £30 per annum will be paid for appropriate National Certificate and C. & G. qualifications.

Further particulars and application forms (to be returned within fourteen days of this advertisement) from Chief Administrative Officer, Bristol Polytechnic, Ashley Down, Bristol B57 9BU.

Please quote Ref. No. T698/66/2 in all communications.

2767

**LTV**

**LING ALTEC**

Customer Services Department

## Service Engineers

These appointments will be of interest to electronic engineers who have attained High National Certificate standard.

The Department is responsible for the installation and maintenance of high-power electronic and mechanical equipment, mainly on customer premises, both in the U.K. and abroad.

These monthly staff appointments offer an attractive salary and, in addition, the full use of a Company car.

The Company operates a generous contributory pension scheme, with a holiday entitlement of three weeks per year.

Applications should be made by letter or telephone to the Customer Services Manager.

LTV Ling Altec Limited,  
Heath Works, Baldock Road, Royston, Herts.  
Tel: Royston 2424

2699

**RADIO SCHOOL IN PANAMA:** Radio Technician required to operate radio school in Santiago de Veraguas. The school provides an elementary adult education programme and is now unable to function for lack of a technician to take charge. Challenging opportunity to fill a vital need in the development of rural areas. Volunteer terms: board, lodging, pocket-money, fares, allowances. Write CHIR/OV 38 King Street, London, W.C.2. [2770]

**REDIFON LTD.** require fully experienced TELECOMMUNICATIONS TEST ENGINEERS and ELECTRONICS INSPECTORS. Good commencing salaries. We would particularly welcome enquiries from ex-Service personnel or personnel about to leave the Services. Please write giving full details to—The Personnel Manager, Redifon Ltd., Broomhill Road, Wandsworth, S.W.18. [26]

**SENIOR ELECTRONICS TECHNICIANS** are required by the Department of Applied Psychology to support the development of instrumentation for research work. Opportunities available for enterprising Technicians to gain experience in any of the following fields: Electro-physiological recording, magnetic tape systems, analogue computing, digital circuiting and building special peripherals for the departmental on-line PDP 9 computer. Experience and interest in building or maintaining equipment in at least one of the above fields essential. Salary on the scale £1,026 to £1,280 per annum, with supplementary payment up to £80 per annum if approved qualifications held. Five day week. Pension Scheme. Application Forms from the Staff Officer, The University of Aston in Birmingham, Gosta Green, Birmingham 4, quoting reference L/515/W.W. [2739]

**UNIVERSITY OF SHEFFIELD: CHIEF TECHNICIAN** required in Department of Chemistry to take charge of Electronics Workshop, concerned with development and construction of new electronic equipment for research and teaching, and maintenance and repair of wide range of electronic equipment. Experience necessary, qualifications preferable. Salary £1,385-£1,578 p.a. Write, stating age, qualifications and experience, to the Bursar (Ref. B.390), The University, Sheffield S10 2TN. [27411]

**WE HAVE VACANCIES** for Four Experienced Test Engineers in our Production Test Department. Applicants are preferred who have Experience of Fault Finding and Testing of Mobile VHF and UHF Mobile Equipment. Excellent Opportunities for promotion due to Expansion Programme. Please apply to Personnel Manager, Pye Telecommunications Ltd., Cambridge Works, Haig Road, Cambridge. Tel. Cambridge 51351, Extn. 327. [77]

### ARTICLES FOR SALE

**AR88** mains transformers, £2.10.0; 12/24V carbon pile voltage regulator units, 30/-; 40 amp. 4-way terminal blocks, 5/-; Rotax rotary Inverters, input 24V dc. output 115V. 3 phase, 400 Hz. 1.8 amps., £7.10.0; 200 amp. terminals, insulated heads, 8/6. Carriage and packing extra. Also, high voltage capacitors and insulators in stock. Westover Electronic Man. Co., Braidley House, St. Paul's Lane, Bournemouth. Tel. 23944. [2771]

**BRAND NEW ELECTROLYTICS**, 15/16 volt, 0.5, 1, 2, 5, 8, 10, 20, 30, 40, 50, 100, 200 mfd. 8d. Carbon Film Resistors 1 watt 5% E12 Series 10 ohms to 1 Megohm 1/6 dozen, minimum order 7/6, postage 1/-. The C. R. Supply Co., 127 Chesterfield Rd., Sheffield S8 7AT. [2747]

**BUILD IT** in a DEWBOX quality plastics cabinet. 2 in. X 2 1/2 in. X any length. D.E.W. Ltd. (W), Ringwood Rd., FERNDOWN, Dorset. S.A.E. for leaflet. Write now—Right now. [76]

**CLOSED CIRCUIT TV** Mobile Control Room for sale. Purchased January 1969 and built by Ampex. The unit includes 3 Vidicon Cameras by Marconi and full sound and communication facilities. There is also a helican scan V.T.R. unit and an audio tape recorder on board, both built by Ampex. Offers should be made to Television Facilities, Queens Hall, Leeds 1. Loan Finance available. [2738]

**COPIES** of "Wireless World" from 1954 to 1968; offers please.—Grant, The Bungalow, 93 London Road, Hurst Green, Sussex. [2743]

**DISC RECORDING UNIT** complete with Leak stereo amplifier, mod. meters, console, motorised swarf suction unit, spare blank, sapphires, etc., etc. Sudden cutter unit. Good condition. Best offer over £50.—John King (Films) Limited, Film House, 71 East Street, Brighton, BN1 1NZ. [2749]

**FERRANTI** AF3, AF5, B1, OP2, OPM1(2), OPM5, OPM6, OPM1c, X17, £5 o.n.o. CARRIAGE PAID.—Norwood, May Hill, Ramsey, I.o.M. [2757]

### FOR SALE BY TENDER 170,000 Valves

The Commissioners of CUSTOMS AND EXCISE are offering for sale by competitive tender approx. 170,000 valves in lots of approx. 1,000.

For further particulars, apply in writing to:

**The Officer, Customs and Excise,  
Queen's Warehouse, Custom House,  
Lower Thames St., London, E.C.3,  
before January 2nd, 1970.** 2751

**HOW** to Use Ex-Govt. Lenses and prisms. Booklets. Nos. 1 & 2, at 2/6 ea. List Free for S.A.E. H. W. ENGLISH, 469 RAYLEIGH RD., HUTTON, BRENTWOOD, ESSEX. [87]

# ELECTRONIC TECHNICIANS

Ampex Quality Control Department now has vacancies for technicians to be responsible for fault finding and testing a wide range of Professional Audio and C.C.T.V. Magnetic Recording Equipment.

Experience gained in the electronic industry, radio or television servicing would be an advantage or a qualification of O.N.C. standard.

Excellent salaries, three weeks annual holiday, canteen, life assurance, pension and sickness benefit schemes in operation.

Please write or telephone the **Personnel Officer,**  
**Ampex Electronics Limited, Acre Road, Reading,**  
**Berkshire. Telephone Reading 84411.**



2688

## PRODUCTION TEST ENGINEER

With experience of valve and transistor audio equipments, wanted to join our senior staff. 40 hour week. Salary £1,200 per annum.

**ASSOCIATED ELECTRONIC ENGINEERS LTD.,**  
**Dalston Gardens, Stanmore, Middlesex.**  
**Tel.: 01-204 2125 2729**



## RADIO & TELEVISION SERVICING RADAR THEORY & MAINTENANCE

This private College provides efficient theoretical and practical training in the above subjects. One-year day courses are available for beginners and shortened courses for men who have had previous training.

Write for details to: The Secretary, London Electronics College, 20 Penywern Road, Earls Court, London, S.W.5. Tel.: 01-373 8721.

84

## Bath University of Technology

### A TECHNICIAN

is required in the School of Mathematics to assist mainly in servicing and developing ANALOGUE AND DIGITAL COMPUTING devices.

Candidates should have experience in electronics, should possess a basic qualification and be competent in elementary workshop skills.

Salary in the range of £773—£1,077 per annum, according to age, experience and qualifications.

**Further details and application form from Registrar (S), The University, Bath, BA2 7AY, quoting ref. 69/83.**

2754

# RADIO OPERATORS

There will be a number of vacancies in the Composite Signals Organisation for experienced Radio Operators in 1970 and in subsequent years.

Specialist training courses lasting approximately nine months, according to the trainee's progress, are held at intervals. Applications are now invited for the course starting in September 1970.

During training a salary will be paid on the following scale:

Age 21	£800 per annum
" 22	£855 "
" 23	£890 "
" 24	£925 "
" 25 and over	£965 "

Free accommodation will be provided at the Training School.

After successful completion of the course, operators will be paid on the Grade 1 scale:

Age 21	£965 per annum
" 22	£1025 "
" 23	£1085 "
" 24	£1145 "
" 25 (highest age point)	£1215 "

then by six annual increases to a maximum of £1,650 per annum.

Excellent conditions and good prospects of promotion. Opportunities for service abroad.

Applicants must normally be under 30 years of age at start of training course and must have at least two years' operating experience. Preference given to those who also have GCE or PMG qualifications.

Interviews will be arranged throughout 1970.

Application forms and further particulars from:

**Recruitment Officer, Government Communications Headquarters, Oakley, Priors Road, CHELTENHAM, Glos., GL52 5AJ.**

Telephone No. Cheltenham 21491 Ext. 2270.

92

## TRANSFORMERS

### Working Foreman

for small shop producing transformers, 20vA-10KvA. Must be fully experienced, all stages of production. Commencing salary about £1,200.

**Also Young Assistant  
with testing experience**

**S.S. Electronics Limited,  
Severalls Avenue,  
Chesham, Bucks.  
Phone: Chesham 4774**

2761

# INTERNATIONAL AERADIO LTD TELECOMMUNICATIONS INSTRUCTOR

Applicants should possess a recognised qualification in telecommunications, e.g. City & Guilds, ONC, HNC with electronics. These are desirable qualifications but personnel with a sound basic and applied radio theory capability would be considered.

Ex-Services/Civilian personnel who have completed an instructional technique course and have had instructional experiences in the field of telecommunications would be preferred.

A liking and aptitude for this work is essential together with general experience of UHF, VHF and HF communications equipment providing fixed and mobile services. Applicants should also be familiar with Radio Navigational Aid equipment as installed at airports for use by aircraft and ATC personnel. It is inherent that applicants will have a knowledge of solid state techniques.

This is a permanent and pensionable position at our Radio Training School outside Southall which address is in easy access of surrounding areas. The post offers good career prospects. Starting salary will be in the region of £1500. Benefits also include membership of an excellent contributory pension and life assurance scheme and substantial rebates on holiday air fares, after a year's service.

To apply for this position write to



**Personnel Officer (Recruitment)**  
**INTERNATIONAL AERADIO LIMITED,**  
HAYES ROAD, SOUTHALL, MIDDLESEX. Tel: 574 2411

## THE HANNAH DAIRY RESEARCH INSTITUTE AYR ELECTRONICS TECHNICIAN

ASSISTANT EXPERIMENTAL/EXPERIMENTAL OFFICER required for duties in the Department of Physiology, including servicing of electronic and electrical equipment, construction of special instruments, devising and construction of electrophysiological apparatus. Previous experience in a physiological laboratory desirable, but not essential.

Qualifications: a degree, H.N.C., N.H.C., Grad. I.E.E.E. or equivalent in electronics engineering, applied science or applied physics.

Salary: A.E.O. up to £1,208 in a scale to £1,454;  
E.O. in a scale £1,190 to £2,006.

Further particulars may be obtained from the Secretary of the Institute, to whom applications, with the names of two referees, should be submitted by 17th January, 1970.

2734

## WE OFFER A YOUNG ENGINEER

the opportunity of working in an up-to-date tape recorder service department on Uher recording equipment.

The applicant should be familiar with the latest transistorised circuitry as well as being able to carry out mechanical work on such equipment.

We offer a good salary, non-contributory pension scheme, subsidised canteen facilities and some local transport.

If you are interested, please write giving brief details about your qualifications and experience to:

**The Personnel Manager,**  
**BOSCH LIMITED,**  
Rhodes Way, Watford, Herts.

2777

**NEW FULL SPECIFICATION DEVICES.** Integrated Circuits complete with data: GE PA230 Audio Pre-amplifier 18/6 each; GE PA234 1W Audio Amplifier 17/6 each; GE PA237 2W Audio Amplifier 32/6 each; MEL 11 Photo Darlington Amplifier 9/6 each; high quality low cost plastic transistors: GE 2N5172 NPN 200mW Transistor 1/9 each; ME 0412 PNP 200mW Transistor 3/9 each; Westinghouse guaranteed plastic rectifier: 1N4820 1.5A 400V Si Rectifier 2/6 each. GI W005 1A 50V Full Wave Bridge Si Rectifier 7/6 each. C.W.O. P. & P. 1/- per order. JEF ELECTRONICS, York House, 12 York Drive, Grappenhall, Warrington, Lancs. Mail Order Only. [2750]

### PYE VHF RADIO TELEPHONE

comprising one Base Station F27AM 25 watts output, and two 'CAMBRIDGE' mobile units type AM10D. Latest transistorised design—as new and in perfect order. Cost over £500.

Offered at £320 the lot.

H.P. terms available.

**For demonstration call Mr. K. M. V. Crump, Baldock, Herts. Tel. 3196.**

2752

**UHF KITS and T.V. SERVICE SPARES.** Suitable for Colour: Leading British Makers dual 405/625 six position push button transistorised tuners £5 5s. 0d., 405/625 transistorised sound & vision IP panels £2 15s. 0d. incl. circuits and data, P/P 4/6. Basic dual purpose 405/625 transistorised tuners incl. circuit £2 10s. 0d., P/P 4/6. UHF list available on request. UHF tuners, PLESSEY incl. valves 55/-, P/P 4/6. EKO/FERRANTI 4 position push button type, incl. valves, leads, knobs £5 10s. 0d., P/P 4/6. SOBELL/GEC UHF tuner kit incl. valves, right angle slow motion drive assy, leads, fittings, knobs, instructions £5 18s. 6d., P/P 4/6. SOBELL/GEC 405/625 IF & output chassis incl. circuit 32/6. P/P 4/6. Ultra 625 IF amplifier plus 405/625 switch assy incl. circuit 25/-, P/P 4/6. New VHF tuners, Cydon C 20/-, EKO 283/330 range 25/-, Pye CTM 13 ch. incremental 25/-, P/P 4/6. Many others available incl. large selection channel coils. Fireball tuners, used good cond. 30/-, Push button tuners RGD 612/619 type used good cond. 30/-, P/P 4/6. LOPTS, Scan coils, Frame output transformers, Mains droppers etc., available for most popular makes. TV signal boosters transistorised PYE/Labgear B1/B3 or UHF battery operated 75/- UHF mains operated 97/6. UHF masthead 85/-, post free. Enquiries invited, COD despatch available. MANOR SUPPLIES, 64 GOLDERS MANOR DRIVE, LONDON, N.W.11. CALLERS 589B, HIGH ROAD, N. FINCHLEY, N.12 (near GRANVILLE RD.). Tel. 01-445 9118. [60]

### BUSINESS OPPORTUNITIES

#### PROTOTYPE DEVELOPMENT

I seek a firm or individual of proven competence to design and produce prototype important invention (provisional pat.) involving op.-to-electronics, R.F., logic, control circuits and small high speed electro-magnetic mechanism (from specialists) Box No. 2635.

#### TEST EQUIPMENT — SURPLUS AND SECONDHAND

SIGNAL generators, oscilloscopes, output meters, wave voltmeters, frequency meters, multi-range meters, etc., etc., in stock.—R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [64]

STEREO GENERATORS: 1 Onmatsu LSG/230, £25; 1 Heathkit, £35; 14 volumes "Radio and TV Servicing" until 1962. Offers considered.—H. F. ENGINEERING, 3 Willowbank, Sunbury-on-Thames, Middlesex. Telephone 83232. [2756]

(1) Mullard Double Beam Oscilloscope, L.101. Excellent general condition but may possibly need recalibrating. £80. (2) Marconi BFO, type TF195L, £30. (3) Avo model 7, £15. (4) Evershed Bridge Megger 500 volt, £20.—Burgess Lane & Co. Ltd., Thornton Ave. Chiswick, London W.4. [2638]

#### RECEIVERS AND AMPLIFIERS — SURPLUS AND SECONDHAND

HERO Rx5s, etc., AR88, CR100, BRT400, G209, S640, etc., etc., in stock.—R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [63]

#### NEW GRAM AND SOUND EQUIPMENT

CONSULT first our 76-page illustrated equipment catalogue on HI-FI (6/6). Advisory service, generous terms to members. Membership 7/6 p.a.—Audio Supply Association, 18 Blenheim Road, London, W.4. 01-995 1661. [27]

GLASGOW.—Recorders bought, sold, exchanged; cameras, etc., exchanged for recorders or vice-versa.—Victor Morris, 343 Argyle St., Glasgow, C.2. [11]

#### TAPE RECORDING ETC.

IF quality, durability matter, consult Britain's oldest transfer service. Quality records from your suitable tapes. (Excellent tax-free fund raisers for schools, churches.) Modern studio facilities with Steinway Grand.—Sound News, 18 Blenheim Road, London, W.4. 01-995 1661. [28]

TAPE to disc transfer, using latest feedback disc cutters; EPs from 22/-; s.a.e. leaflet.—Deroy, High Bank, Hawk St., Carnforth, Lancs. [70]

**VALVES**

**VALVE** cartons by return at keen prices; send 1/- for all samples and list.—J. & A. Boxmakers, 75a Godwin St., Bradford. 1. [10]

**VALVES.** To clear Large quantity ex Admiralty. CV2127, CV455, CV4055, CV4024. 3/- each, 6 for 12/-. Post paid.—GREENE, Fieldings, Poulner, Ringwood, Hants. [2740]

**FOR HIRE**

**FOR** hire CCTV equipment including cameras, monitors, video tape recorders and tape—any period.—Details from Zoom Television, Amersham 5001. [75]

**ARTICLES WANTED**

**LEAK** Dynamic Moving Coil Pick-up for L.P. Records. Parts acceptable.—S.B., 167 South Avenue, Southend-on-Sea. [2744]

**WANTED,** all types of communications receivers and test equipment.—Details to R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4988. [63]

**WANTED:** Bruel & Kjaer automatic frequency response recorder type 3308 (2305/1022) 20 Hz-20 KHz (or earlier model). Details please to Mr. C. Heinlein, CTH ELECTRONICS, Hoddesdon, Herts. Phone Hoddesdon 64798. [2772]

**WANTED,** televisions, tape recorders, radiograms, new valves, transistors, etc.—Stan Willetts, 37 High St., West Bromwich, Staffs. Tel. Wes. 0186. [72]

**WANTED:** Wireless World 1938 Communication Receiver. Condition immaterial. Box WW 2773 Wireless World.

**VALVES WANTED**

**WE** buy new valves, transistors and clean new components, large or small quantities. All details, quotation by return.—Walton's Wireless Stores, 55 Worcester St., Wolverhampton. [62]

**SCRAP** R.F. Heating and Transmitting Valves wanted. TY5-500, TY6-800, TY7-600, ESA 1800, BR 1126. May be interested in other types. Good price paid for valves still under vacuum. Electronic Heat Co. 01-654 7172. [2606]

**CAPACITY AVAILABLE**

**AIRTRONICS, Ltd.,** for coil winding, assembly and wiring of electronic equipment, transistorised sub-unit sheet metal work.—3a Walerand Rd., London, S.E.13. Tel. 01-852 1706. [61]

**ELECTRONIC** and Electrical Manufacture and Assembly. Prototypes and short production runs. East Midlands Instrument Co. Ltd., Summergangs Lane, Gainsborough, Lincs. Tel. 3260. [88]

**METALWORK,** all types cabinets, chassis, racks, etc., to your own specification, capacity available for small milling and capstan work up to 1in bar.—PHILPOTT'S METALWORKS, Ltd., Chapman St., Loughborough. [17]

**SKILLED WIREMAN,** own workshop, seeks out-work. No estimating, your price accepted/refused. Box W.W. 2758 Wireless World.

**TECHNICAL TRAINING**

**BECOME** "Technically Qualified" in your spare time, guaranteed diploma and exam. home-study courses in radio, TV, servicing and maintenance. R.T.E.B. City & Guilds, etc., highly informative 120-page Guide—free.—Chambers College (Dept. 837K), College House, 29-31 Wrights Lane, Kensington, London. W.8. [16]

**CITY & GUILDS** (Electrical, etc.), on "Satisfaction or Refund of Fee" terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, T.V., automation, etc.; send for 132-page handbook—free.—B.I.E.T. (Dept. 152K), Aldermaston Court, Aldermaston, Berks. [13]

**RADIO** officers see the world. Sea-going and shore appointments. Trainee vacancies during 1970. Grants available. Day and boarding students. Stamp for prospectus. Wireless College, Colwyn Bay. [80]

**TECHNICAL TRAINING** IN Radio, TV and Electronics through world-famous ICS. For details of proven home-study courses write: ICS, Dept. 443, Intertext House, Stewarts Road, London, S.W.8. [24]

**TV** and radio A.M.I.E.R.E., City & Guilds, R.T.E.B.; certs., etc., on satisfaction or refund of fee terms; thousands of passes; for full details of exams and home training courses (including practical equipment) in all branches of radio, TV, electronics, etc., write for 132-page handbook—free; please state subject.—British Institute of Engineering Technology (Dept. 150K), Aldermaston Court, Aldermaston, Berks. [15]

**TUITION**

**ENGINEERS.**—A Technical Certificate or qualification will bring you security and much better pay. Elem. and adv. private postal courses for C.Eng., A.M.I.E.R.E., A.M.S.E. (Mech. & Elec.), City & Guilds, A.M.I.M.I., A.I.O.B., and G.C.E. Exams. Diploma courses in all branches of Engineering—Mech., Elec., Auto, Electronics, Radio, Computers, Drafts, Buildings, etc.—For full details write for FREE 132-page guide: British Institute of Engineering Technology (Dept. 151K), Aldermaston Court, Aldermaston, Berks. [14]

**KINGSTON-UPON-HULL** Education Committee. College of Technology. Principal: E. Jones, M.Sc. F.R.I.C.

**FULL-TIME** courses for P.M.G. certificates and the Radar Maintenance certificate.—Information from College of Technology, Queen's Gardens, Kingston-upon-Hull. [18]

**BOOKS, INSTRUCTIONS, ETC.**

**MANUALS,** circuits of all British ex-W.D. 1939-45 wireless equipment and instruments from original R.E.M.E. instructions; s.a.e. for list, over 70 types.—W. H. Bailey, 167a Moffat Road, Thornton Heath, Surrey, CR4-8PZ. [66]

**REQUIRED** 1937 Jones Radio Handbook. Litherland, G8CFB, 11 Birch Grove, Chippenham, Wiltshire. [2742]

**REDIFFUSION****COLOUR TELEVISION  
FAULTFINDERS & TESTERS**

We have a number of vacancies in our Production Test Departments for experienced faultfinders and testers.

Knowledge of transistor circuitry and experience with Colour Receivers together with R.T.E.B. Final Certificate or equivalent qualifications required.

These will be staff appointments with all the expected benefits.

Applications to:

Works Manager,  
Rediffusion Vision Service Ltd.,  
Fullers Way South,  
Chessington, Surrey (near Ace of Spades).  
Phone: 01-397 5411

83

**AIR FORCE DEPARTMENT  
RADIO TECHNICIANS**

Starting pay according to age, up to £1,189 p.a. (at age 25) rising to £1,500 p.a. with prospects of promotion.

Vacancies at RAF Sealand, Near Chester  
and RAF Henlow, Bedfordshire

Interesting and vital work on RAF radar and radio equipment.

Minimum qualification, 3 years' training and practical experience in electronics.

5-day week—good holidays—help with further studies—opportunities for pensionable employment.

Write for further details to:

Ministry of Defence, CE3h (Air),  
Sentinel House,  
Southampton Row,  
London, W.C.1.

Applicants must be UK residents.

2685

**FOR  
ANNECY (FRANCE)**

Winter sports town 50 Kms. from Geneve

International firm for Electronic Measurements  
is seeking

**Electrical Technical Editor**

Knowledge of French for use in measurement apparatus.

Monthly salary £135. Annual holidays, 4 weeks.  
Housing facilities.

Reply: METRIX B.P. N° 30 — ANNECY 74 — France

2733

**POWER TRANSISTORS** Ex. Eqpt. Sim. to OC28. 4 for 10/- p. & p. 1/-, 100 for £10. Post free

750µH Inductors 5/- doz. **THERMOSTATS.** 1" x 1/2" x 1 1/4". O.C. above 120°F. 1 1/4. 250v. 5/- ea.

**DESK TELEPHONES**



**REED SWITCHES**  
Glass encased, switches operated by external magnet—gold welded contacts.  
**Miniature.** 1in. long x approximately 1/8in. diameter. Will make and break up to 1A. up to 300 volts. Price 2/6 each. 24/- dozen.

**MINIATURE GLASS NEONS 12/6 doz.**

**TRIM POTS** on 2" x 4" bds. + Ta. caps. and other components. 100Ω, 500Ω, 15K, 20K. Please state requirements. 5 for 10/- + 2/- p. & p.

**THIS MONTH'S SNIP**  
9 OA5, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875. All long leaded on panels 1 3/4" x 4". 2 for 10/- p. & p. 1/6d. 4 for 20/- Post free.

**COMPUTER PANELS** 2in. x 4in. 10 for 10/- + 1/6 p. & p. Min. 35 transistors; 25 for £1 p. & p. 3/6. min. 85 transistors; 100 for 65/- p. & p. 6/6. min. 350 transistors; 1,000 for £30 + carr.

**GIANT PANELS** 5 1/2" x 4" min. 20 transistors 9 x 56 µH. Inductors, resistors, capacitors etc. 3 for £1 + 2/- p. & p.  
As above, only 21 transistors, 70 diodes, 62 min. 1/10th W resistors, 3 for 25/- p. & p. 2/-

**LARGE CAPACITY ELECTROLYTICS.** 4 1/2in. 2in. diam. Screw terminals. Top quality German manufacture. Will withstand short circuit discharge.  
4,000µF 72V d.c. wkg. 7/6  
6,300µF 72V d.c. wkg. 7/6  
16,000µF 12V d.c. wkg. 6/-

0.22 MFD 250V POLYESTERS 5/- doz.  
2.2 MFD 50V TANTALUM 10/- doz.

**NEW PLESSEY CAPS**  
1" x 3" 2000µF 25V d.c. 6/- each.  
2" x 4" 1,500µF 150V d.c. wkg. 8/- each.


250 Resistors 1/2 and 1/4 watt. 12/6  
150 Hi-Stab Resistors. 1/2 and 1 watt 12/6



**QUANTITIES AVAILABLE EXTRACTOR/FLOWER FANS (Papst)**  
100 c.f.m. 4 1/2" x 4 1/2" x 2in. 2800 r.p.m. 240v. A.C. Precision made in West Germany by Papst. These Fans are the best available. Genuine bargain at 50/- each. List price.

**DIODES EX EQPT SILICON**  
150 PIV 10Amp 4 for 10/-  
150 PIV 20Amp 4 for 20/-

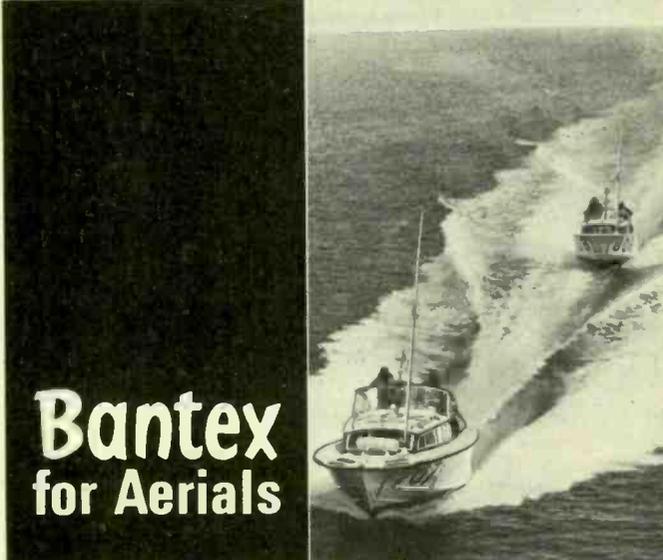**KEYTRONICS,**  
52 Earls Court Rd., London, W.8  
Tel. 01-478 8499  
**MAIL ORDER ONLY. Retail and Trade supplied. Export enquiries particularly welcome.**  
S.A.E. FOR LIST



**Bantex for Aerials**

All over the 5 continents and the 7 seas Bantex aerials are helping to maintain reliable communications. Day in and day out.

Bantex aerials are selected because of their established reputation for reliability. A reputation earned over many years.

Bantex manufacture all types of marine aerials and for land use they have a range of mobile and base station aerials which operate through all bands and are used by the armed forces, police, taxi networks and industry.

Although Bantex is best known for glass-fibre aerials with a unique process for high strength, designs for metallic aerials have also been developed.


The photograph shows two boats of the Ford team in the 1969 Round Britain Power Boat Race. Both used Bantex aerials.

**Bantex Ltd.** 186 WALMER ROAD, LONDON W.11  
Telephone 727 3432/3 Telex 82310

WW-099 FOR FURTHER DETAILS

**Kinver for Integrated Circuits**

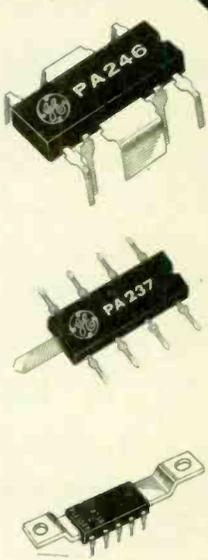**LINEAR INTEGRATED CIRCUITS FOR ALL YOUR REQUIREMENTS**



Plessey SL403A 3 Watt Audio Amplifier	49/6
G.E. type PA234 Low Level Amplifier	21/-
G.E. type PA234 1 Watt Audio Amplifier	23/-
G.E. type PA237 2 Watt Audio Amplifier	34/-
G.E. type PA246 5 Watt Audio Amplifier	57/-
RCA type CA3000 D.C. Amplifier	54/9
RCA type CA3011 Wide Band Amplifier	20/-
RCA type CA3020 1/2 Watt Wide Band Amplifier	32/-
RCA type CA3028A Differential/Cascode Amp (120 MHz)	20/-
RCA type CA3029 Operational Amplifier	55/2
RCA type CA3035 Ultra High Gain Amplifier	30/-
Mullard Type TAA263 A.F. Amplifier	15/9
Mullard Type TAA293 General Purpose Amplifier	21/8
Mullard Type TAA310 Record/Playback Pre-Amplifier	32/-
Mullard Type TAA320 MOS L.F. Amplifier	13/5
G.E. type 2N5306 Darlington Pair	11/8
G.E. type D13T1 Programmable Unijunction Transistor	10/8

ADD 1/- each to the above i.c.s. for data sheets if required. Data sheets may be purchased separately at 1/6d. each post free. Issued free with SL403A only.

**TRANSISTORS**

ACY17	8/8	BC212L	3/9	OC26	9/-	2N1308	9/6
ACY18	4/5	BC213L	3/9	OC28	9/-	2N1309	9/6
ACY19	5/3	BC214L	4/-	OC35	9/-	2N2906	13/-
ACY20	4/6	BCY70	5/4	OC36	9/-	2N2924	4/4
ACY21	4/11	BCY71	10/4	OC71	3/-	2N2925	5/3
ACY22	2/10	BCY72	4/6	OC72	3/9	2N2926	3/-
ACY39	18/-	BD121	18/-	OC75	3/9	2N3053	6/8
ACY40	3/5	BF184	7/6	OC81D	3/-	2N3055	19/6
ACY41	4/4	BF194	7/-	OC170	3/9	2N3702	3/6
ACY44	8/-	BFY50	5/-	OC171	3/9	2N3703	3/3
ASY26	6/2	BFY51	4/6	2N696	4/9	2N3704	3/9
ASY27	8/-	BFY52	5/-	2N697	5/-	2N3705	3/4
ASY28	6/2	BSY95A	3/11	2N706	3/3	2N3707	2/5
ASY29	8/-	MJ481	27/3	2N1132	10/9	2N3708	2/6
BC107	3/3	MJ491	32/11	2N1302	3/11	2N3819	9/-
BC108	3/-	TIP31A	17/-	2N1303	3/11	2N3820	18/9
BC109	3/3	TIP32A	23/-	2N1304	5/-	2N3826	5/11
BC182L	3/2	TIS44	1/9	2N1305	5/-	2N4058	4/6
BC183L	2/5	TIS49	2/6	2N1306	6/5	2N4059	3/5
BC184L	3/2	TIS50	3/9	2N1307	6/5	40408	14/11
2N2160	Unijunction		14/11				

**DIODES**

AA119	3/-	OA91	1/3	1N82A	9/6	1S134	5/3
AA111	2/6	OA202	2/-	1N87A	4/6	1S940	1/-
AA215	3/3	1N34A	4/-	1N914	2/-		
BA138	3/9	1N60	4/-	1S44	1/8		
OA47	2/-	1N64	4/-	1S131	3/-		

**VEROBOARD**

2 1/2" x 5"	0.1	0.15
2 1/2" x 3 1/2"	4/9	4/2
3 1/2" x 5"	4/2	3/5
3 1/2" x 3 1/2"	5/6	5/6
3 1/2" x 3 1/2"	4/9	3/11
17" x 2 1/2"		10/6
17" x 3 1/2"		14/8

Plain Veroboard (Uncoppered) (0.15" Matrix only)

2 1/2" x 5"	3/8
2 1/2" x 3 1/2"	3/-
17" x 2 1/2"	7/6
17" x 3 1/2"	9/8
17" x 5"	14/8

Cutter ..... 7/3  
Pin Insertion Tool (0.1) ..... 9/6  
Pin Insertion Tool (0.15) ..... 9/6  
Pkt. of 36 pins (0.1) ..... 3/11  
Pkt. of 36 pins (0.15) ..... 3/11

**INTERNATIONAL RECTIFIER HANDBOOKS**

HB10 Rectifier Engineering Handbook	16/9
HB20 Zener Diode Handbook	16/9
HB30 Solar Cell & Photocell Handbook	16/9
HB40 SCR Handbook	20/-

**PHOTOCELLS**

IR CS-120	19/8
Mullard Type ORP12	9/-

**ZENER DIODES**


1S2030 Series (400mW, 3.3v to 15v)	4/8
Z1100-C (1 Watt, 3.9v to 27v)	7/11

**COMPONENTS CATALOGUE—2/- Post Free (Inland)**  
P & P 1/6 inland, overseas at cost (min. 10/-)  
Cash with order please, discounts may be deducted as follows: order over £5—10%; order over £10—15%. Trade orders—net 30 days.  
Please send SAE with enquiries. CALLERS WELCOME  
Open 9.00 a.m.—12.50 p.m., 2.00 p.m. to 5.00 p.m. Weekdays and Saturday Mornings 9.00 a.m.—12.50 p.m.

**ELECTRONICS LTD**  
**Kinver**  
STONE LANE · KINVER  
STOURBRIDGE · WORCS  
Telephone: KINVER 2099

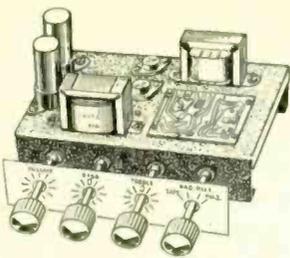**NEW! HSL 700 Mono Transistor Amplifier**

A really high fidelity monaural amplifier with performance characteristics to suit the most discriminating listener. 6 transistor circuit with integrated pre-amplifier assembled on special printed sub panel. AD-161-AD162 operating in symmetric complementary pair. Output transformer coupled to 3 ohm and 15 ohm speaker sockets. Standard phono input sockets. Full wave bridge rectifier power supply for A.C. mains 200-240 v. Controls: Bass, Treble, Volume/on/off. Function selector for PUI, PU2, Tape, Radio. The HSL 700 is strongly constructed on rigid steel chassis, bronze hammer enamel finish, size 9 1/2 in. x 5 in. x 4 1/2 in. high. Performance figures:



Sensitivity—PUI-50 mV, 50K input impedance. PU2-110 mV, 1 meg. input impedance. Tape—110 mV, 1 meg. input impedance. Radio—110 mV, 1 meg. input impedance. Output power measured at 1 Kc-6.2 watts RMS into 3 ohms, 5.8 watts RMS into 15 ohm. Overall frequency response 30 c/s-18 Kc/s; Continuously variable tone controls; Bass, + 8db to 12 db at 100 c/s. Treble, + 10 db to -10 db at 10 Kc/s. The HSL 700 has been designed for true high fidelity reproduction from Radio Tuner, Gramophone deck and Tape Recorder pre amp but is also capable of being used in conjunction with a guitar by connecting to PUI socket and the peak output power will then be in the region of 15 watts. Supplied ready built and tested, complete with knobs, attractive anodized aluminium front escutcheon panel, long spindles (can be cut to suit your housing requirements), full circuit diagram and operating instructions. OUR SPECIAL PRICE £7/19/6. P. & P. 7/6.

**BRAND NEW!**

**PARMEKO MAINS TRANSFORMERS**

Primary 110v-250v Secondary 330-0-330v. 100mA and 6.3v. at 2 amps. 6.3v. at 2 amps and 6.3v. at 1 amp. Conservatively rated. Fully impregnated. Electrostatic screen. Suitable for vertical or drop through mounting. Overall size 4 1/2 in. x 3 1/2 in. x 3 1/2 in. Weight 8lbs. Limited number only at 37/9 P. & P. 8/-.

**Transistor Stereo 8+8 Mk. II**

Now using Silicon Transistors in first five stages on each channel resulting in even lower noise level with improved sensitivity. A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors giving 8 watts push pull output per channel (16W, mono), integrated pre-amp. with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metal work. Cir-Kit board, attractive front panel knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief Specification: Freq. response ±3dB, 20-20,000 c/s. Bass boost approx. to +12dB. Treble cut approx. to -16dB. Negative feedback 18dB. over main amp. Power requirements 25V. at 6 amps. PRICES: Amplifier Kit £10/10/0; Power Pack Kit £3/0/0; Cabinet £3/0/0. ALL POST FREE. Circuit diagram, construction details and parts list (free with kit) 1/6 (S.A.E.).

**SPECIAL OFFER!**

**HI FI CELESTION SPEAKER UNIT.** Size 6in. x 4in. Powerful 11,000 line magnet with specially treated cone surround. 10-12 ohm impedance. Few only at 20/- P. & P. 3/6.

**QUALITY RECORD PLAYER AMPLIFIER MK. II**

A top-quality record player amplifier employing heavy duty double wound mains transformer. ECC83, EL84, EZ80 valves. Separate bass, treble and volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7 1/2 in. w. x 3 1/2 in. d. x 6 1/2 in. h. Ready built and tested. PRICE 75/- P. & P. 6/-. ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE 97/6. P. & P. 7/6.


**DE LUXE QUALITY PORTABLE R-PLAYER CABINET MK. 2** Uncut motor board size 14 1/2 x 12 1/2 in. clearance 2in. below, 2 1/2 in. above. Will take amplifier above and any B.S.R. or GARRARD Autochanger or single Player Unit (except AT60 or SP25). Size 18 x 15 x 8in. PRICE 79/6. Carr. 9/6.

**3-VALVE AUDIO AMPLIFIER MODEL HA34 MK. II**

Designed for Hi-Fi reproduction of records. A.C. mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 in. w. x 4 in. d. x 4 1/2 in. h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. The HA34 has been specially designed for us and our quality order enables us to offer them complete with knobs, valves, etc., wired and tested for only 24/15/- P. & P. 6/-.

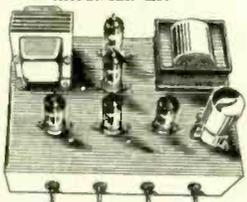**10/14 WATT HI-FI AMPLIFIER KIT**

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up: 2 EL84s, ECC83, EF86, and EZ80 rectifier. Simple instruction booklet 1/6 (Free with parts). All parts sold separately. ONLY 27/8/6. P. & P. 8/6. Also available ready built and tested complete with standard input sockets. 29/5/- P. & P. 8/6.



**HARVERSON SURPLUS CO. LTD.**

170 HIGH STREET, MERTON, LONDON, S.W.19  
Telephone: 01-540 3985

S.A.E. all enquiries.

Open all day Saturday (Wednesday 1 p.m.)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

**LONDON CENTRAL RADIO STORES**

**ELECTRICITY SLOT METER** (1/2 in slot) for A.C. mains. Fixed tariff to your requirements. Suitable for hotels, etc. 200/250 v. 10 A. 80/-; 15 A. 90/-; 20 A. 100/- P. P. 7/6. Other amperages available. Reconditioned as new, 2 years' guarantee.

**WIRELESS SET No. 38 A.F.V.** Freq. range 7.3 to 9.0 Mc/s. Working range 1 to 2 miles. Size 10 1/2 x 4 x 6 1/2 in. Weight 6 1/2 lb. Includes power supply 8lb.—and spare valves and vibrator also tank aerial with base. 28 per pair or 24 single. P.P. 25/-.

**MODERN DESK PHONES**, red, green, blue or topaz. 2 tone grey or black, with internal bell and handset with 0-1 dia. 24/10/- P.P. 7/6.

**10-WAY PRESS-BUTTON INTER-COM TELEPHONES** in Bakelite case with junction box handset. Thoroughly overhauled. Guaranteed. 28/10/- per unit.

**20-WAY PRESS-BUTTON INTER-COM TELEPHONES** in Bakelite case with junction box. Thoroughly overhauled. Guaranteed. 27/15/- per unit.

**TELEPHONE COILED HAND SET LEADS**, 3 core, 5/6. P.P. 1/-.

**QUARTERLY ELECTRIC CHECK METERS.** Reconditioned as new. 200/250 v. 10 A. 42/6; 15 A. 52/6; 20 A. 57/6. Other amperages available. 2 years' guarantee. P.P. 5/-.

**8-BANK UNISELECTOR SWITCHES.** 25 contacts, alternate wiping 22/15/-; 8 bank half wipe 22/15/-; 6 bank half wipe. 25 contacts 47/6. P.P. 3/6.

**FINAL END SELECTORS.** Relays, various callers, also 19 Receivers in stock. All for callers only.

**23 LISLE ST. (GER 2969) LONDON W.C.2**

Closed Thursday 1 p.m. Open all day Saturday

**FANTASTIC SPEAKER BARGAIN**

Famous English. 12" high flux, heavy cone, 10 watts speaker with built-in tweeter. 3 or 15 ohms. 12-month guarantee **39/6**  
2 for 70/- (P. & I. 6/9) (P. & I. 4/9)



**NEW RELEASE HI-FI COLUMN SPEAKER CABINET**

Beautifully made Suitable for 7-12" speakers. Rosewood finish. Screwed and glued. Attractive grey cloth front measures 24" x 13" x 10" with tweeter hole above. Mark II de luxe model (Carr. 10/-) With 12" speaker as advertised above **95/-**  
C6/5/0 (Carr. 10/-).



**LATEST RELEASE!**

**Nickel Cadmium**

**EVER READY RECHARGEABLE CELLS**

1.25v 1.6 A.H.	29/6
Size 2 1/2" high x 1 1/2" dia.	18/-
1.25v 0.45 A.H.	39/6
9v equiv PP3	

P & P 1/3 on each  
CHARGERS AVAILABLE—send S.A.E. for details

**4-TRANSISTOR AUDIO AMPLIFIER (1 watt) 27/6**

3 1/2" x 2 1/2" x 1 1/2"  
Output 8 or 16 ohms  
P & P 1/3 on each

**TAPE SPLICER/EDITOR 19/6**  
P&P 1/3 on each

**ELECTRAMA** Dept. WW22, 15 High St., Maitland, Sussex

**VACUUM**

OVENS, PUMPS, PLANT, GAUGES, FURNACES, ETC., GENERAL SCIENTIFIC EQUIPMENT EX-STOCK, RECORDERS, PYROMETERS, OVENS, R. F. HEATERS. FREE CATALOGUE.

**V. N. BARRETT & CO. LTD.**  
1 MAYO ROAD, CROYDON,  
CANTON 2QP. 01-684 9917-8-9

**WANTED—**

Redundant or Surplus stocks of Transformer materials (Laminations, C. cores, Copper wire, etc.), Electronic Components (Transistors, Diodes, etc.), P.V.C. Wires and Cables, Bakelite sheet, etc., etc.  
Good prices paid

**J. BLACK**  
44 Green Lane, Hendon, N.W.4  
Tel. 01-203 1855 and 3033

**EXCLUSIVE OFFER**

**AMPEX**

**MODEL FR-100 A**

**DATA TAPE**

**RECORDER-REPRODUCERS**

COMPLETELY FITTED IN 6 ft. TOTALLY ENCLOSED CABINETS with recording and reproducing Amplifiers, electronic frequency control and all Power Supplies.

- ★ SIX SPEEDS 1 1/2", 3", 7 1/2", 15", 30" and 60" per second.
- ★ INTERCHANGEABLE HEADS.
- ★ 1" TAPE, 5 TRACKS.
- ★ UP TO 14" REEL CAPACITY.
- ★ D.C. F.M. - P.C.M. - N.R.Z. SYSTEMS.
- ★ DC to 30,000 cycles.
- ★ UP TO 10,000 Pulse Rate.
- ★ DRIFT FREE WITHIN 1%.
- ★ SERVO CONTROL to 0.75 μs.
- ★ TRACK TIMING 5 μs.
- ★ ACCURACY 10<sup>3</sup> per week.
- ★ ELECTRONICS IN MODULES FRONT ACCESS TO ALL PARTS.
- ★ POWER INPUT 105/125v 48 to 500 A/c.



Made in U.S.A. these fine units cost the American Government 28,000 each before devaluation.  
Full details on application.

**FREE**

40-page list of over 1,000 different items in stock available—keep one by you.

★ Collins R-380 Communications Receivers 6.5/30.0 mcs	£365 0
★ Hoffman CV-157 15B SSB Converters	£230 0
★ Mackay 128 A.V.L.F. Receivers 15/600 Kcs.	£240 0
★ E.M.I. Tape Recorders BTR-1	£175 0
★ Weston 24-D.B. Meters -10/+6	£20 0
★ E.E.8 Telephones	£3 10
★ Wharfedale BFB-3 Loudspeakers walnut	£14 0
★ R.C.A. 6 ft. Enclosed 19" Cabinets open front with door	£14 0
★ Du Kane 6 ft. 8 in. Enclosed 19" Cabinets open front with door.	£15 0
★ Motorola 5 ft. ditto recessed 19" mounts and 2 doors.	£12 0
★ Candestik microphones with push to talk switch	£2 0
★ R.C.A. 5820 Image Orthicon	£55 0
★ Lattice lightweight steel triangular Aerial Masts 12 to 16 inch sides up to 200 ft. high	According to height

**WANTED VIDEO TAPE**  
Good price paid

★ Vitavox 20 watt 12" loudspeakers	£2 10
★ I.C. Testers with plug boards	£95 0
★ Williamson Amplifiers	£6 0
★ E.M.I. WM-3 Measuring Oscilloscopes	£32 10
★ Marconi TP-1055 Noise Measuring Sets	£150 0
★ 54 inch. dia. Meteorological Balloons	£1 10
★ Micrometer Wavemeters General Electric 900/1530 and 1530/4000 m/c.s.	each £22 0
★ 455 k/c.s Mechanical Band Pass Filters	£3 10
★ New Magnetic Recording Tape made by E.M.I. (USA) 3600 ft on N.A.B. Spools	£5 10
★ 1" Used ditto "Scotch" Brand 4800 ft.	£4 0
★ Siebert Measuring Microscopes .001 m/m	£5 5
★ Coliaro Transcription Turntables	£2 10
★ Collins 500 w. Radio Telephone Transmitters Autotune 2 to 18 m/c.s 230v. input new	P. U. R.
★ 8 Track Data High Speed Tape Readers	£40 0
★ Mason Illuminated Drawing Tables 50" x 36"	£17 10
★ Selma Telegraph Distortion Monitors	£25 0
★ Teletype Model 14 Tape Punches	£29 10
★ TS-487/URB Signal Generators 2/400 m/c.s	£25 0
★ Sarah Trans/Receivers and Aerials	£3 0
★ Freis Airport "Weather Man" Masts	£25 0
★ 75 foot high Lattice Triangular Wind up Masts	£285 0
★ Uniselectors 10 bank 25 way full wipe ex. new	£1 15
★ Precision Mains Filter Units new	£1 10
★ Marconi HR.29 SSB Receivers 2/32 m/c.s.	£75 0
★ Avo Gear Counter new	£7 10

Carriage extra at cost on all above.  
All goods are ex-Government stores.

We have a large quantity of "bits and pieces" we cannot list—please send us your requirements we can probably help—all enquiries answered.

**P. HARRIS**  
**ORGANFORD — DORSET**  
BH16 6ER  
WESTBOURNE 85051

# TECHNICAL TRAINING by ICS IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

First-class opportunities in Radio and Electronics await the ICS trained man. Let ICS train YOU for a well-paid post in this expanding field.

ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training, so essential to success. Diploma courses in Radio/TV Engineering and Servicing, Electronics, Computers, etc. Expert coaching for:

- ★ C. & G. TELECOMMUNICATION TECHNICIANS' CERTS.
- ★ C. & G. ELECTRONIC SERVICING.
- ★ R.T.E.B. RADIO AND TV SERVICING CERTIFICATE.
- ★ RADIO AMATEURS' EXAMINATION.
- ★ P.M.G. CERTIFICATES IN RADIOTELEGRAPHY.

Examination Students Coached until Successful.

### NEW SELF-BUILD RADIO AND ELECTRONIC COURSES

Build your own 5-valve receiver, transistor portable, signal generator, multi-meter and valve volt meter — all under expert guidance.

POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF THE ASSOCIATION OF BRITISH CORRESPONDENCE COLLEGES

**INTERNATIONAL  
CORRESPONDENCE  
SCHOOLS**

**A WHOLE WORLD  
OF KNOWLEDGE  
AWAITS YOU!**

International Correspondence Schools  
(Dept. 230), Intertext House, Stewarts Road,  
London, S.W.8.

NAME .....

Block Capitals Please

ADDRESS .....

1/70

## LAWSON BRAND NEW TELEVISION TUBES

- 12" Types £4.10.0
- 14" Types £4.19.0
- 17" Types £5.19.0
- 19" Types £6.19.0
- 21" Types £7.15.0
- 23" Types £9.10.0
- 19" Panorama £8.10.0
- 23" Panorama £11.10.0
- 19" Twin Panel £9.17.6
- 23" Twin Panel £12.10.0

Carrlage and insurance

- 12"-19"—12/6
- 21"-23"—15/0

The continually increasing demand for tubes of the very highest performance and reliability is now being met by the new Lawson "Century 99" range of C.R.T.s. "Century 99" are absolutely brand new tubes throughout manufactured by Britain's largest C.R.T. manufacturers. They are guaranteed to give absolutely superb performance with needle sharp definition screens of the very latest type giving maximum Contrast and Light output; together with high reliability and very long life.

"Century 99" are a complete range of tubes in all sizes for all British sets manufactured 1947-1968.

Complete fitting instructions are supplied with every tube.

**2 YEARS FULL REPLACEMENT GUARANTEE**

WW-100 FOR FURTHER DETAILS



### LAWSON TUBES

18 CHURCHDOWN ROAD  
MALVERN, WORCS.  
Tel. MAL 2100

### SURPLUS HANDBOOKS

19 set Circuit and Notes .. 8/6 p/p 6d.  
1155 set Circuit and Notes .. 8/6 p/p 6d.  
H.R.O. Technical Instructions .. 5/6 p/p 6d.  
39 set Technical Instructions .. 5/8 p/p 6d.  
48 set Working Instructions .. 5/6 p/p 6d.  
88 set Technical Instructions .. 7/- p/p 6d.  
BC.321 Circuit and Notes .. 5/6 p/p 6d.  
Wavemeter Class D Tech. Inst. .. 5/6 p/p 6d.  
18 set Circuit and Notes .. 5/6 p/p 6d.  
BC.1000 (31 set) Circuit and Notes .. 5/6 p/p 6d.  
CR.100/B.23 Circuit and Notes .. 7/- p/p 6d.  
R.107 Circuit and Notes .. 10/- p/p 6d.  
A.R.88D Instruction Manual .. 18/- p/p 6d.  
62 set Circuit and Notes .. 6/6 p/p 6d.  
Circuit Diagram 5/- each post free. R.1116/A, B.1224/A, B.1355, R.F. 24, 25 and 26, A.1134, T.1154, CR.300, BC.312, BC.342, BC.348J, BC.348 (E.M.P.), BC.824, 22 set.  
52 set Sender and Receiver circuits 7/6 post free.  
Colour Code Indicator 2/6, p/p 6d.  
S.A.E. with all enquiries please.  
Postage rates apply to U.K. only.  
Mail order only to:

**INSTRUCTIONAL HANDBOOK SUPPLIES**  
Dept. W.W. Talbot House, 28 Talbot Gardens, LEEDS 8

### WE PURCHASE

COMPUTERS, TAPE READERS AND ANY SCIENTIFIC TEST EQUIPMENT, PLUGS AND SOCKETS, MOTORS, TRANSISTORS, RESISTORS, CAPACITORS, POTENTIOMETERS, RELAYS TRANSFORMERS, ETC.

**ELECTRONIC BROKERS LTD.**  
49 Pancras Road, London, N.W.1. 01-837 7781

### GEARED MOTORS

Microswitches, Timers, Meters, Potentiometers, Capacitors, all new

6d. stamp for catalogue.

**F. HOLFORD & CO.**  
6 IMPERIAL SQUARE, CHELTENHAM

FOR YOUR ...

### SYNCHRO & SERVO REQUIREMENTS!

SERVO & ELECTRONIC SALES LTD.  
43 HIGH ST., ORPINGTON, KENT. Tel: 31066, 33976  
Also at CROYDON. Tel: 01-688 1512  
and LYDD, KENT. Tel: LYDD 252

### AMERICAN

TEST AND COMMUNICATIONS EQUIPMENT

★ GENERAL CATALOGUE AN/104 1/6 ★  
Manuals offered for most U.S. equipments

**SUTTON ELECTRONICS**  
Salthouse, Nr. Holt, Norfolk. Cley 289

# DRY JOINT LOCATOR

Techmation Limited  
58 Edgware Way Edgware  
Middx Tel 01-958 5636

### BAILEY 30 WATT AMPLIFIER

10 Tr's as spec'd and Fibreglass Pcb £6.7.6  
20 Tr's as spec'd and 2 Fibreglass Pcb's £12.10.0  
BC125/126/40361 11/6 40362 15/6  
MJ481 25/6 MPF103 8/6 MJ491 28/-  
R1-R27 (5% low noise) & P. 10/6 CI-C6 (Mullard) 7/6  
Mullard C431 2500mFd/64Vw with clip 15/-  
Ali H/Sink (Drilled 2 x TO3) 4 x 4 1/2 in. 10/-

### LINSLEY HOOD CLASS A AMP

Set 10 C.F. R's 5/- Set 5 Capacitors 22/6  
MJ480 (Matched for <0.1% T.H.D.) per pair 42/6  
MJ481 (Matched for <0.1% T.H.D.) per pair 52/6  
2N3906/2N4058/2N697/2N1613 6/6 BC109 3/6  
Pair of H/Sinks as spec'd for Mono 5 x 4 in. 21/-  
Lektrokite Pinboard 4 x 4 1/2 in. pins & Layout 5/6  
MJ480 16/6 Hunts KA112BT 2500mFd/50Vw 12/6  
1250mFd/40Vw 9/- 250mFd/50Vw 3/- 500mFd/50Vw 5/9

**A.I. FACTORS, 72 BLAKE ROAD, STAPLEFORD, NOTTS.**

### WE BUY

any type of radio, television, and electronic equipment, components, meters, plugs and sockets, valves and transistors, cables, electrical appliances, copper wire, screws, nuts, etc. The larger the quantity the better. We pay Prompt Cash.

**Broadfields & Mayco Disposals,**  
21 Lodge Lane, London, N.12

**RING 445 2713**

445 0749

958 7624

### R & R RADIO


51 Burnley Road, Rawtenstall  
Rossendale, Lancs  
Tel.: Rossendale 3152

**VALVES BOXED, TESTED & GUARANTEED**

EBF80 3/-	EBC41 4/6	PY81 3/6
EBF89 3/6	PCC84 3/-	PY800 3/6
ECC82 3/-	PCF80 3/-	PY82 3/-
ECL80 3/-	PCF82 3/6	U191 4/6
EF80 1/6	PCL82 4/-	6F23 5/-
EF85 3/-	PCL83 4/-	30F5 2/6
EF183 3/6	PCL84 5/-	30L15 5/-
EF184 3/6	PL36 5/-	30P12 4/6
EY86 4/-	PL81 4/-	30C15 5/-
EL41 5/-	PL83 4/-	30PL13 5/6
EZ40 4/6	PY33 5/-	30PL14 5/6

POST, ONE VALVE 9d. TWO TO SIX 6d.  
OVER SIX POST PAID.

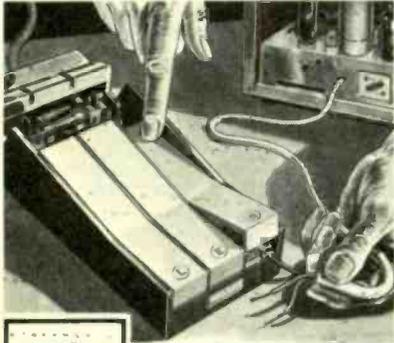**MAINS Keynector**  
*A REVOLUTIONARY NEW PRODUCT*  
**cuts out plugs**



**It's the Newest, Safest and Quickest way to connect Electrical Equipment to the mains**

No plugs—no sockets—no risk of bare wires. To connect anything electrical, from an oscilloscope to an electric drill, simply open the fuse housing, depress the keys, insert the wires and close the housing. A neon light on the front of the Keynector glows to indicate proper connection. Multi-parallel connections can be made up to 13 amps. Keys are colour coded and lettered LEN for quick identification. The Keynector casing is in two-tone plastic and measures 5in. x 3in. x 1½in. Please send for further information.

*issued by*  
**E.B. INSTRUMENTS**  
 DIVISION OF ELECTRONIC BROKERS LTD.  
 49-53 Pancras Road, London, N.W.1. Telephone: 01-837 7781

**BAKER MAJOR £8**



30-14,500 c.p.s., Hi-Fi double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 45 c.p.s. Rated 20 watts. Voice coils available 3 or 8 or 15 ohms. Price £8, or Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £10.19.6

LOUDSPEAKER CABINET WADDING  
 18 in. wide, 2/6 ft.


**ELECTRIC MOTORS**



(120v. or 240v. A.C.)  
 Clockwise 1,200 R.P.M. off load  
 Heavy duty 4 pole 50mA.  
 Spindle ¼ x 3/20 in. diameter.  
 Size 2½ x 2½ x 1½ in.  
**BARGAIN PRICE 17/6** Post 2/6

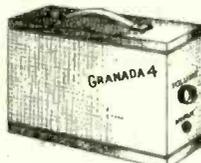**TRANSISTOR AMPLIFIER WITH LOUDSPEAKER**

A self-contained portable mini p.a. system. Many uses—Parties, Baby Alarm, Intercom, Telephone or Record Player Amplifier. Attractive roxine covered cabinet size 12x9x4 in., with powerful 7x4 in. speaker and four transistor one watt power amplifier. Uses PP9 battery. Brand new in Maker's carton with full maker's guarantee.



All for only **75/-** Post 4/6

**THE INSTANT BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER**



200/250 A.C. Leaflet S.A.E. **42/6** Post 2/6

**EXTENSION SPEAKER**

Smart plastic cabinet speaker with 20ft. lead for transistor radio, intercom, mains radio, tape recorder, etc. **30/-** Post 2/6  
 Size: 7½in. x 5½in. x 3in.



RETURN OF POST DESPATCH—CALLERS WELCOME  
 HI-FI STOCKISTS—SALES—SERVICE—SPARES  
**RADIO COMPONENT SPECIALISTS**  
 337 WHITEHORSE ROAD, CROYDON. Tel: 01-684 1665

*Thanks to a bulk purchase we can offer*

**BRAND NEW P.V.C. POLYESTER & MYLAR RECORDING TAPES**

Manufactured by the world-famous reputable British tape firm, our tapes are boxed in polythene and have fitted leaders, etc. Their quality is as good as any other on the market, in no way are the tapes faulty and are not to be confused with imported, used or sub-standard tapes. 24-hour despatch service.

Should goods not meet with full approval, purchase price and postage will be refunded.

S.P.	3in. 160ft.	2/-	5in. 600ft.	6/-
	5½in. 900ft.	8/-	7in. 1,200ft.	9/6
L.P.	3in. 225ft.	2/6	5in. 500ft.	8/6
	5½in. 1,200ft.	10/-	7in. 1,800ft.	13/-
D.P.	3in. 350ft.	4/6	5in. 1,200ft.	12/-
	5½in. 1,800ft.	16/-	7in. 2,400ft.	20/-

Postage on all orders 1/6

**COMPACT TAPE CASSETTES AT HALF PRICE**

60, 90, and 120 minutes playing time, in original plastic library boxes.  
 MC 60 9/- each. MC 90 12/6 each. MC 120 18/3 each.

**STARMAN TAPES**

**28 LINKSCROFT AVENUE ASHFORD, MIDDIX.**

Ashford 53020

WW-101 FOR FURTHER DETAILS

**Would IC's eat into YOUR pocket ?**



If you think that IC's are still too expensive for your equipment design - read on

**930 Series DTL:-**


ST 930	Dual 4-input gate	9/6
ST 962	Triple 3-input gate	9/6
ST 946	Quad 2-input gate	8/6
ST 936	Hex inverter	9/6
ST 951	Gated monostable	13/-
ST 945	Clocked R-S/J-K flip-flop	12/-

These IC's are completely compatible with other manufacturers DTL and TTL, and meet the full electronic spec for 930 series devices.

e.g.

- gates:- 25 ns propagation delay typ
- flip flops:- 4.5MHz toggle rate typ
- Power Dissipation:- 40mW per package typ
- Temperature Range:- 0 to +75°C
- Fan Out:- 8 min

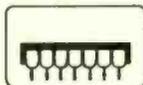- \* Dual in line Packages.
- \* Linear Devices also available.
- \* Data Sheets for S.A.E.
- \* Quotations for Quantities available on request.



Simpson Taylor and Company Limited  
 Brians, Newtongrange, Dalkeith, Scotland

include 1/6 postage & packing per order below £5

WW-098 FOR FURTHER DETAILS

**Grampian**  
for good  
**SOUND EQUIPMENT**  
GRAMPIAN REPRODUCERS LTD  
Hanworth Trading Estate, Feltham, Middlesex

**TRANSFORMER LAMINATIONS** enormous range in Radiometal, Mumetal and H.C.R., also "C" & "E" cores. Case and Frame assemblies.  
**CONNECTING WIRES** Large selection of stranded single p.v.c. covered Wire 7/0048, 7/0076, 14/0076 etc. P.T.F.E. covered Wire, and Silicon rubber covered wire, etc.  
**J. Black**  
OFFICE: 44 GREEN LANE, HENDON, N.W.4  
Tel: 01-203 1855. 01-203 3033  
STORES: 30 BARRETT'S GROVE, N.16  
Tel: 01-254 1991

**240 volt ELECTRICITY ANYWHERE**   
BEST EVER 200/240 VOLT "MAINS" SUPPLY FROM 12 VOLT CAR BATTERY. Exclusive World Scoop Purchase. The fabulous Mk.2D American Heavy Duty Dynamotor Unit with a massive 220 watt output and giving the most brilliant 200/240 volt performance of all time. Marvellous for Television, Drills, Power Tools, Mains Lighting, AC Fluorescent Lighting and all 200/240 volt Universal AC/DC mains equipment. Made at tremendous cost for U.S.A. Govt. by Delco-Remy. This magnificent machine is unobtainable elsewhere. Brand New and Fully Tested only £4.19.6 + 10/6 postage. C.O.D. with pleasure. Money back if not delighted. Please send s.a.e. for interesting illustrated details. Dept. W.W., STANFORD ELECTRONICS, Rear Derby Rd., North Promenade, Blackpool, Lancashire.

**INDEX TO ADVERTISERS**


Appointments Vacant Advertisements appear on pages 95-109

	PAGE		PAGE		PAGE
A1 Factors.....	112	Hall Electric Ltd.....	9	Radio & TV Components, Ltd.....	87
Acoustical Mfg. Co. Ltd.....	4	Harris Electronics (London), Ltd.....	46	Radio Components Specialists.....	113
Adcola Products Ltd.....	Cover iii	Harris, P.....	111	Radio Exchange Co.....	92
Adler, B. & Sons (Radio) Ltd.....	38	Hart Electronics.....	88	Radiospares, Ltd.....	42
AEI Semiconductors Ltd.....	39	Harversons Surplus Co., Ltd.....	111	Rank Wharfedale Ltd.....	36
Ahuja Radios.....	61	Hatfield Instruments, Ltd.....	60	Rendar Instruments.....	60
Amtronix.....	88	Hayden Laboratories.....	41	Reslo Mikes.....	44
Anders Electronics, Ltd.....	37, 44	Henry's Radio, Ltd.....	66, 67	Roband Electronics Ltd.....	34
A.P.A. Publishing (Catalogues) Ltd.....	23	Henson.....	112	R.R. Radio.....	112
Associated Electronic Eng. Ltd.....	42	Hi-Fi Year Book/Radio Year Book.....	Loose insert	R.S.C. Hi-Fi Centres, Ltd.....	79
Audix B. B., Ltd.....	24	Holford, F., Co., Ltd.....	112	R.S.T. Valves.....	86
Avo Ltd.....	1	Howells Radio, Ltd.....	58		
		I.C.S., Ltd.....	86, 112	Salford Electrical Inst. Ltd.....	47
Bantex Ltd.....	110	I.M.O. (Electronics), Ltd.....	35	Samsons (Electronics), Ltd.....	80
Barnet Factors, Ltd.....	22	Impectron Ltd.....	32	S.E. Laboratories (Eng.) Ltd.....	54
Barrett, V. N.....	111	Industrial Instruments, Ltd.....	58	Service Trading Co.....	72, 73
Batey, W., & Co.....	44	Instructional Handbook Supplies.....	112	Servo & Electronic Sales, Ltd.....	112
Bentley Acoustical Corporation, Ltd.....	68			Simpson Taylor & Co. Ltd.....	113
Bentley, K. J.....	92	Keyswitch Relays Ltd.....	Cover ii	Sinclair Radionics, Ltd.....	55, 56, 57
B.I.E.T.....	13	Keytronics.....	110	S.M.E. Ltd.....	10
Bi-Pak Semiconductors.....	72	Kinver Electronics, Ltd.....	110	Smith, G. W., (Radio), Ltd.....	76, 77
Bi-Pre-Pak, Ltd.....	93			Smith, H. L., Co. Ltd.....	28
Black, J.....	111, 114	Lasky's Radio, Ltd.....	75	Smith, J., Ltd.....	62
Bradley, G. & E., Monsanto.....	15	Lawson Tubes.....	112	Smiths Radio Services (W'ton) Ltd.....	90
Brenell Eng. Co., Ltd.....	40	Ledon Instruments, Ltd.....	46	S.N.S. Communications Ltd.....	14
Britec, Ltd.....	42	Levell Electronics, Ltd.....	18	Special Products Ltd.....	62
Bulgin, A. F., & Co., Ltd.....	Edit. 47	Light Soldering Developments, Ltd.....	28	Specialist Switches, Ltd.....	61
		Livingston Hire Ltd.....	70	Stanford Electronics.....	114
Calan Electronics Ltd.....	61	Lloyd, J. J., Instruments Ltd.....	17	Starman Tapes.....	113
Carston Electronics Ltd.....	40	London Central Radio Stores.....	111	S.T.C. Electroniques.....	8
Chiltmead Ltd.....	63	L.S.T. Components.....	74	Sugden, J. E.....	59
Computer Training Products.....	62			Sutton Electronics.....	112
Croydon Precision Instrument Co.....	47	Mainline Electronics, Ltd.....	82		
		Marshall, A., & Son (London), Ltd.....	91	Techmation Ltd.....	112
Danavox (Gt. Britain) Ltd.....	19	Mills, W.....	80, 81	Teclare Ltd.....	90
Daystrom, Ltd.....	7, 21	Milward G. F.....	83	Tektronix Ltd.....	12
Diotran, Ltd.....	92	M.R. Supplies, Ltd.....	38	Teleguipment Ltd.....	48
Drake Transformers Ltd.....	33	Mullard Ltd.....	11, 20	Telcon Metals Ltd.....	26
Duxford Electronics.....	70	Multicore Solders Ltd.....	Cover iv	Teonex, Ltd.....	29
Dynamco, Ltd.....	84	Myall, W. H.....	60	Thompson, A. J.....	90
		Newmarket Transistors Ltd.....	32	Thorn A.E.I. (Radio Valve & Tubes), Ltd.....	50
E.B. Instruments.....	113	Nombrex Ltd.....	42	Trio Corporation.....	2
Electrama.....	111	Omron Precision Controls.....	35	Trio Instruments Ltd.....	59
Electronic Brokers.....	64, 65, 112	Osmabet Ltd.....	88	T.R.S. Radio Components Specialists.....	84
Electronics (Croydon), Ltd.....	69	Oxley Developments Co., Ltd.....	60		
Electrovalue.....	78	Patrick & Kinnic.....	68	United-Carr Supplies, Ltd.....	36
Electro-Tech Sales.....	89	P.C. Radio, Ltd.....	85	Universal.....	92
Electro-Winds, Ltd.....	60	Peak Sound (Harrow) Ltd.....	30		
E.M.I. Electron Tube-Vidicons.....	45	Pinnacle Electronics Ltd.....	25	Valradio, Ltd.....	38, 59
E.M.I. Tape Ltd.....	52	Proops Bros. Ltd.....	71	Vitality Bulbs, Ltd.....	62
English Electric Valve Co., Ltd.....	3, 5	Pye Telecommunications, Ltd.....	27	Vortexion, Ltd.....	53
Erie Electronics, Ltd.....	16	Quality Electronics Ltd.....	59	Wayne Kerr, The, Co. Ltd.....	31
		Quarndon Electronics Ltd.....	43	Webber, R. A., Ltd.....	59
Farnell Instruments, Ltd.....	46	Quartz Crystal Co. Ltd.....	92	West Hyde Developments, Ltd.....	6
Ferroglyph, The, Co. Ltd.....	51			West London Direct Supplies.....	70
Futuristic Aids Ltd.....	47			Wilkinsons, L. (Croydon), Ltd.....	88
				Z. & I. Aero Services, Ltd.....	94
Garage Gifts Ltd.....	111				
General Eng. Co. Ltd.....	26				
Goldring Manufacturing Co. Ltd.....	24				
Grampian Reproducers, Ltd.....	114				
Greenwood, W. (London), Ltd.....	39				

Printed in Great Britain by Southwark Offset, 25 Lavington Street, London, S.E.1, and Published by the Proprietors, I.P.C. ELECTRICAL-ELECTRONIC PRESS, LTD., Dorset House, Stamford St., London, S.E.1, telephone 01-928 3333. *Wireless World* can be obtained abroad from the following: AUSTRALIA and NEW ZEALAND: Gordon & Gotch, Ltd, INDIA: A. H. Wheeler & Co. CANADA: The Wm. Dawson Subscription Service, Ltd.; Gordon & Gotch Ltd. SOUTH AFRICA: Central News Agency, Ltd.; William Dawson & Sons (S.A.) Ltd. UNITED STATES: Eastern News Co., 306 West 11th Street, New York 14. **CONDITIONS OF SALE AND SUPPLY:** This periodical is sold subject to the following conditions, namely that it shall not, without the written consent of the publishers first given, be lent, re-sold, hired out or otherwise disposed of by way of Trade at a price in excess of the recommended maximum price shown on the cover; and that it shall not be lent, re-sold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.


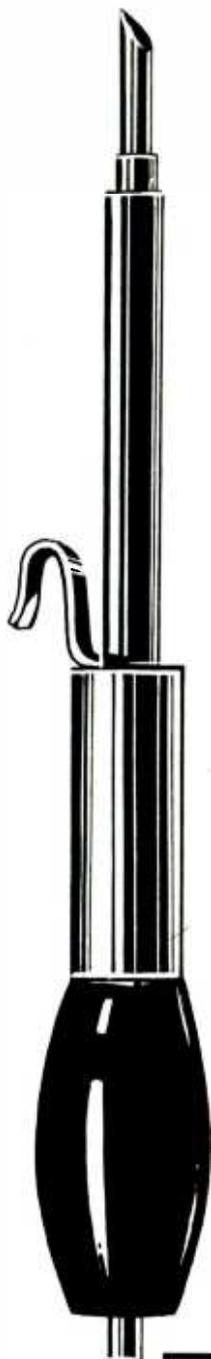
# CLEARWAY to lower production costs with ADCOLA Precision Tools



For increased efficiency find out more about our extensive range of ADCOLA Soldering Equipment—and we provide:

★ THREE DAY REPAIR SERVICE ★ INTER-CHANGEABLE BITS—STOCK ITEMS ★ SPECIAL TEMPERATURES AVAILABLE AT NO EXTRA COST.

ADCOLA TOOLS have been designed in co-operation with industry and developed to serve a wide range of applications. There is an ADCOLA Tool to meet your specific requirement. Find out more about our extensive range of efficient, robust soldering equipment.

◀ No. 107. GENERAL ASSEMBLY TYPE

*Fill in the coupon to get your copy of our latest brochure:*

**ADCOLA PRODUCTS LTD**

Adcola House · Gauden Road · London · SW4  
Tel. 01-622 0291/3 Grams: Soljoint, London SW4



*Please rush me a copy of your latest brochure:*

NAME .....  
COMPANY .....  
ADDRESS .....

WW



# The world's largest exporters of cored solder

## present a complete range of compatible Multicore products for mass soldering of printed circuit assemblies

- including
- NEW LIQUID FLUXES
  - NEW SOLDERING CHEMICALS
  - NEW PACKAGING providing indefinite storage life
  - EXTRUSOL high purity extruded solder



The main assembly function of most electronics companies is the manufacture of soldered joints. Mass-Soldering is not an art. When Multicore Soldering Chemicals, Liquid Fluxes and EXTRUSOL High Purity Solder alloy are used in combination, mass-soldering becomes a logical application of a Multicore technical process, achieving the highest standard of production.

### EXTRUSOL

#### High Purity Extruded Solder

provides the most economical soldering. Its high purity and freedom from oxides, sulphides and other undesirable elements result in the following advantages:—

- Less dross on initial melting.
- More soldered joints per pound of solder purchased.
- Less reject joints.
- Improved wetting of electronic components & printed circuit boards.
- More uniform results.

All Extrusol is completely protected by plastic film packaging from the moment of manufacture until it is used. Available in bars and pellets. Can be released under AID authority and supplied to USA QQ-S-571d.



#### PC.2 MULTICORE TARNISH REMOVER

removes tarnishes and inorganic residues as the second half of a pre-cleaning process before soldering. It leaves the copper unaffected.

#### PC.90 MULTICORE PEELOFF SOLDER RESIST

is a temporary solder resist which can be peeled off with tweezers after soldering, leaving the original clean surface. It can be used for masking gold plated edge connections and holes to which heat sensitive or other components must be added later.

#### PC.41 MULTICORE ANTI-OXIDANT SOLDER COVER

which forms a liquid cover on the solder bath either side of the solder wave, largely preventing the formation of dross.

#### PC.80 MULTICORE SOLVENT CLEANER

removes organic contaminants such as grease, perspiration and residues of organic solutions from prior processes, as a pre-cleaning process before soldering. It is also very efficient in removing rosin-based flux residues after soldering.

#### PC.10A MULTICORE ACTIVATED SURFACE PRESERVATIVE

is a pre-soldering coating for preserving the clean surfaces established by the PC.80 Multicore Solvent Cleaner and PC.2 Multicore Tarnish Remover. PC.10A does not need to be removed before soldering and in fact contributes to the efficiency of the soldering process. PC.10A should be used whenever there is a delay between cleaning and soldering.



**Gallon Containers**  
All liquid chemicals and fluxes supplied in 1 gallon polythene 'easy pouring' containers, with carrying handle.

**Aerosols**  
PC.21A, PC.25 and PC.52 available in 16 oz. aerosol sprays.


#### SEVEN STANDARD MULTICORE LIQUID FLUXES

are now available, five of which are new:— PC.21A Multicore Non-Corrosive Liquid Flux is normally recommended for wave, dip, brush, spray and roller flux application methods. PC.25 Multicore Rosin Foam Flux is designed for foam fluxing and exhibits an unusually stable foam with a fine bubble size.
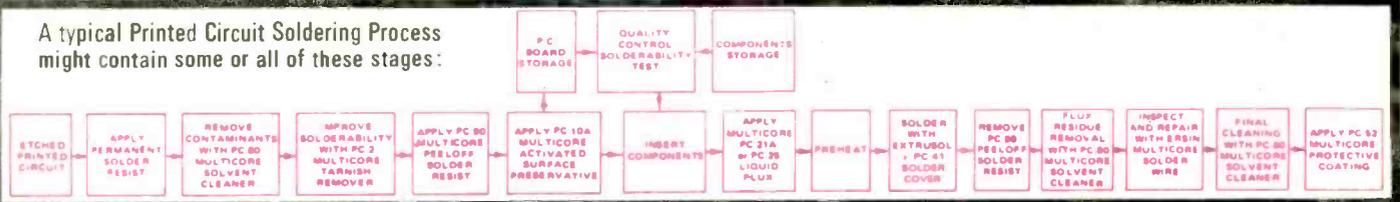
#### PC.52 MULTICORE PROTECTIVE COATING

is a lacquer which should be applied after soldering for protecting printed circuits from deterioration or failure in service. It can easily be soldered through if modifications or repairs are necessary at a later date.

A typical Printed Circuit Soldering Process might contain some or all of these stages:



Write for technical bulletins on your company's letter-head, for the products which interest you to:  
**Multicore Solders Ltd., Hemel Hempstead, Herts. Phone: Hemel Hempstead 3636. Telex: 82363.**