

# Wireless World


April 1970 3s 6d

Stabilized power supply unit  
Digital remote control





# A new STAR is born

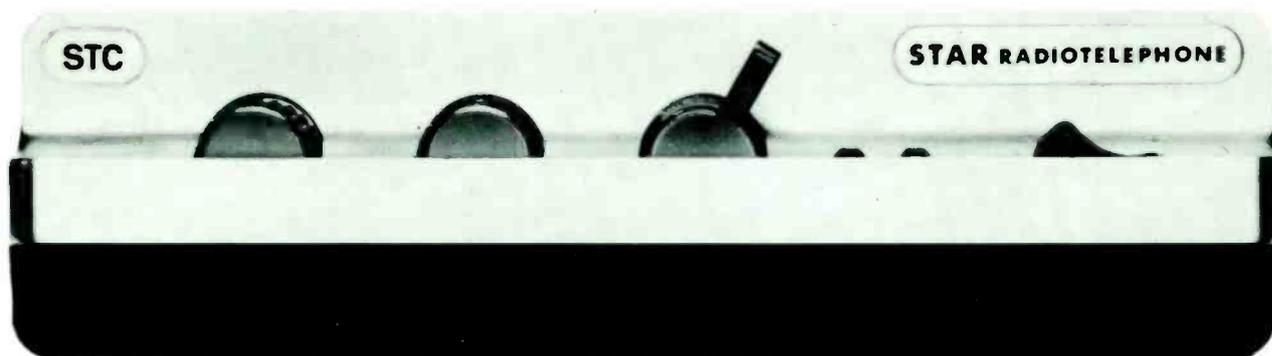

## STC announces a new AM VHF version of the STAR Mobile Radio Telephone series.

The new Star AM7 is designed expressly for British VHF bands. It is completely solid state and meets the latest Ministry of Posts and Telecommunications 12.5 kHz specifications. It incorporates the outstanding features that are making the Star UHF range so successful, combining excellent performance with elegant appearance and outstanding speech qualities. Star

mobile equipment has no relays or moving parts. For more information about the Star AM7 or Star UHF series, post the coupon today.


STC Mobile Radio Telephones Ltd.,  
New Southgate, London N.11.  
Tel: 01-368 1200, Telex: 261912.

an associate of  
**ITT**

Attach your letterheading to this panel.  
Please send me full details of your  
STAR MOBILE VHF RADIOTELEPHONE  
Name.....  
Position.....  
www.1

**STC**  
Mobile Radiotelephones
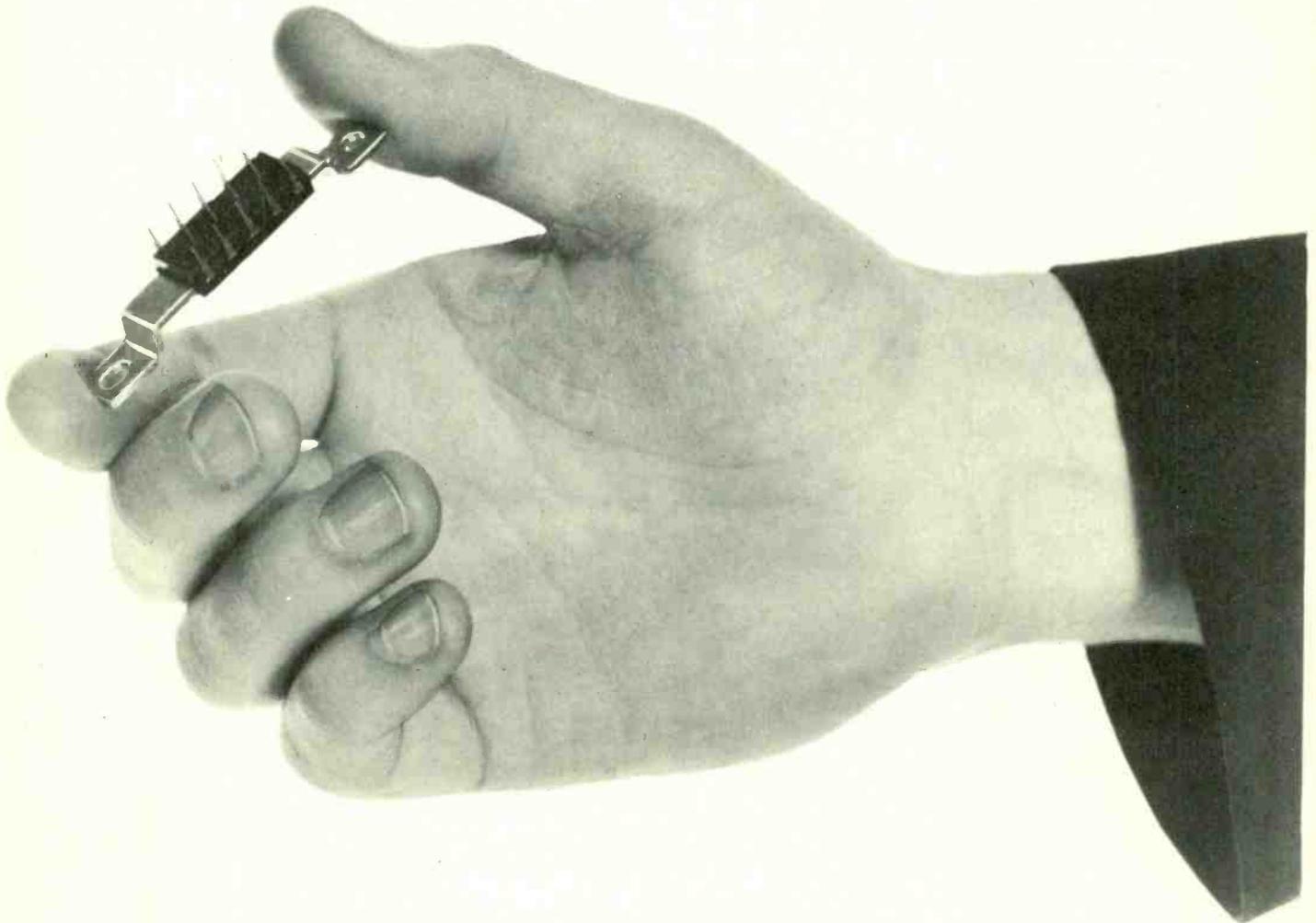
# 2 Watt and 3 Watt Professional IC Audio Amplifiers now available



These Plessey general purpose integrated circuit audio amplifiers are being used by a number of major equipment manufacturers throughout the country.

Through large scale production Plessey can now make these devices available to home constructors at reasonable prices.

Each circuit incorporates a preamplifier and a class A-B power amplifier stage and needs only a minimum of external components.

Take a look at these specifications opposite !  
These really outstanding Plessey IC audio amplifiers are immediately available off-the-shelf from our distributors listed below. Data application brochures (Price 1s. 9d. each) which include PC board layouts for mono and stereo amplifiers are obtainable from :

**Farnell Electronic Components Ltd**  
Canal Rd, Leeds LS 12 2TU  
Tel : Leeds 636311 Telex : 55147

**Characteristic**  
**Output power r.m.s.**  
**Input impedance**  
Preamplifier  
Main amplifier  
**Distortion**  
Preamplifier  
Main amplifier  
**Frequency response**  
Lower—3dB point  
Upper—3dB point  
**Operating voltage**  
**Min. operating load**

	<b>SL402A</b>	<b>SL403A</b>
<b>Output power r.m.s.</b>	2W	3W
<b>Input impedance</b>		
Preamplifier	20 M $\Omega$	20 M $\Omega$
Main amplifier	100 M $\Omega$	100 M $\Omega$
<b>Distortion</b>		
Preamplifier	0.1%	0.1%
Main amplifier	0.3%	0.3%
<b>Frequency response</b>		
Lower—3dB point	20 Hz	20 Hz
Upper—3dB point	30 kHz	30 kHz
<b>Operating voltage</b>	+14 V	+18 V
<b>Min. operating load</b>	7.5 $\Omega$	7.5 $\Omega$


**SDS (Portsmouth) Ltd**  
Hillsea Industrial Estate, Hillsea, Portsmouth, Hants.  
Tel : Portsmouth (0705) 62332 or 62180 Telex : 86114



## **PLESSEY** microelectronics

Cheney Manor Swindon Wiltshire England Telephone: Swindon (0793) 6251. Telex: 44375

WW—006 FOR FURTHER DETAILS

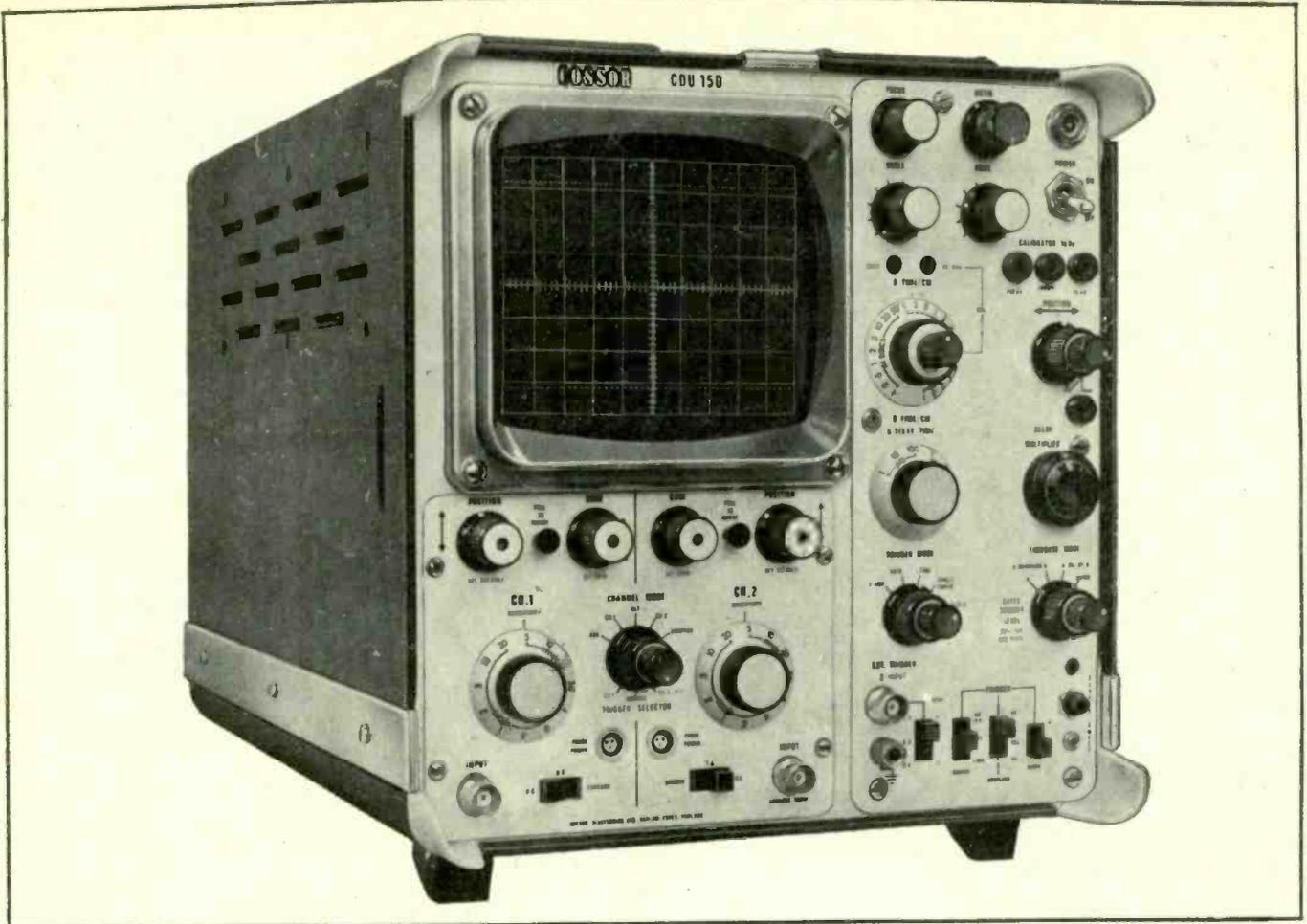

# Check this list— see how much scope you get from Cossor

- CDU 110** 20 MHz Dual Channel 5 mV/cm Sweep Speeds to 40 nS/cm Sweep Delay £360
- CDU 120** 50 MHz 5 mV/cm 25 MHz 1 mV/cm Dual Channel Sweep Delay £640
- CDU 130** 15 MHz 5 mV/div. Mains/Internal Batteries 16.5 lb. including battery £230
- CDU 150** 35 MHz Dual Channel 5 mV/cm Sweep Speeds to 20 nS/cm Sweep Delay £480

**COSSOR** — first in scopes

Please write or phone for further details:

COSSOR ELECTRONICS LIMITED, Instrument Division, The Pinnacles, Harlow, Essex. Telex: 81228 Telephone: Harlow 26862  
WW-007 FOR FURTHER DETAILS

# Experience:

Since the beginning of industrial r.f. heating, EEV have been the pace-setters. With this experience, backed by our equal know-how in the transmitter valve field, is it any wonder that we are so well known for power triodes?

EEV make power triodes for industrial heating applications from 1kW up to 250kW. They are all conservatively rated and realistically designed to give good length of life. Whatever your application —for drying paper, baking biscuits, welding plastic,

treating metal—r.f. heating the EEV way is economical and dependable.


Our sales engineers are at your service to discuss designs and to recommend the best tube or combination of tubes for your particular application.

For full details just post the coupon or telephone Mr. M. J. Pitt.

English Electric Valve Co Ltd. Chelmsford Essex, England. Telephone: 0245 61777. Telex 99103. Grams: Enelectico Chelmsford


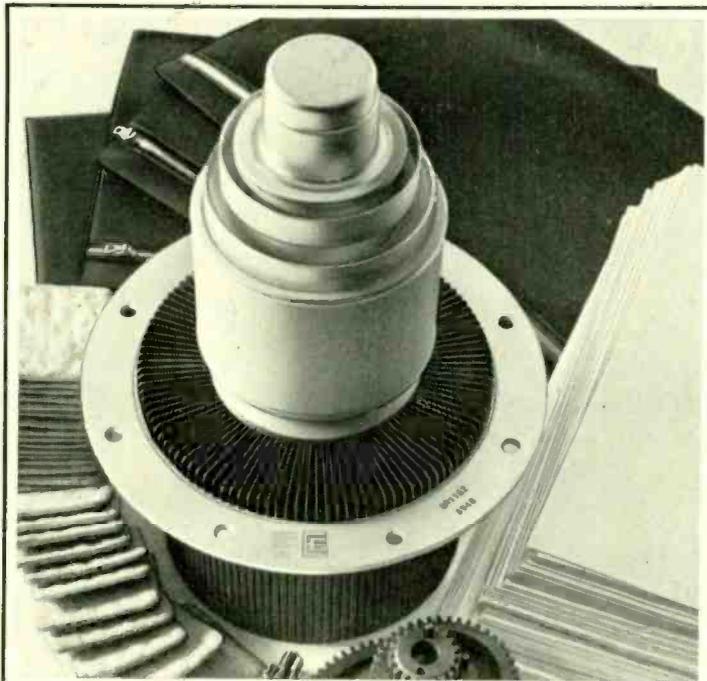
## the vital factor of EEV's industrial r.f. heating power triode range



To: English Electric Valve Co Ltd, Chelmsford, Essex, England.

Please send full data on power triodes for industrial heating.  
Please recommend triodes for an equipment with these ratings.

Output power (kW) \_\_\_\_\_ Anode voltage max. (kV) \_\_\_\_\_ Frequency (MHz) \_\_\_\_\_

Name & Position \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_  
\_\_\_\_\_

Telephone exchange or STD code \_\_\_\_\_

Number \_\_\_\_\_

Extension \_\_\_\_\_




WW-008 FOR FURTHER DETAILS

# The great EEV radar display

These radar components represent just part of our total radar capability, and they indicate the size of our investment in radar. We know radar from thyratrons to magnetrons, from duplexers to klystrons. And we have the resources to back this immense fund of knowledge. EEV's advanced tube technology is at your service. If a device to suit your equipment is not already in our catalogue, we would consider making one specially for you.

So that we can send you the latest, up-to-date information, please return the coupon opposite.

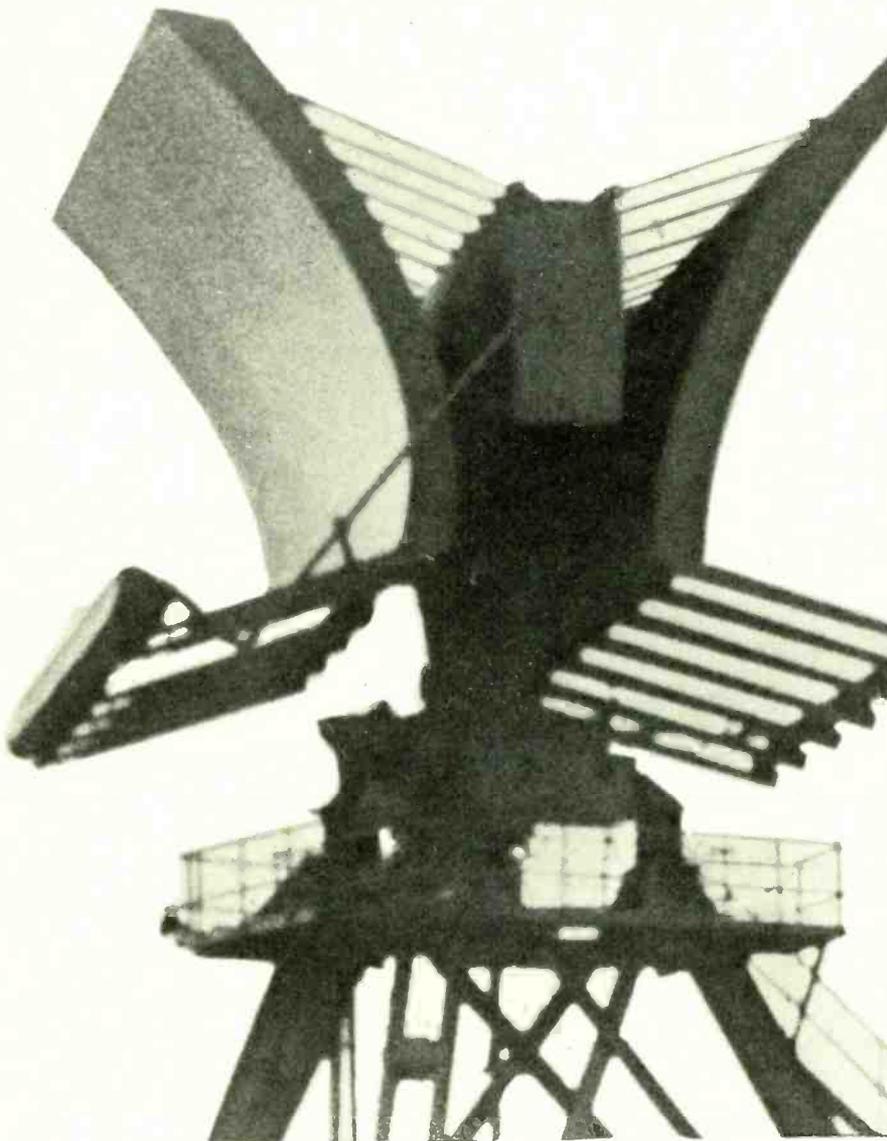
English Electric Valve Co. Ltd., Chelmsford, Essex, England.  
Telephone: 0245 61777. Telex: 99103. Grams: Enelectico, Chelmsford.




1. Magnetrons



2. High power klystrons

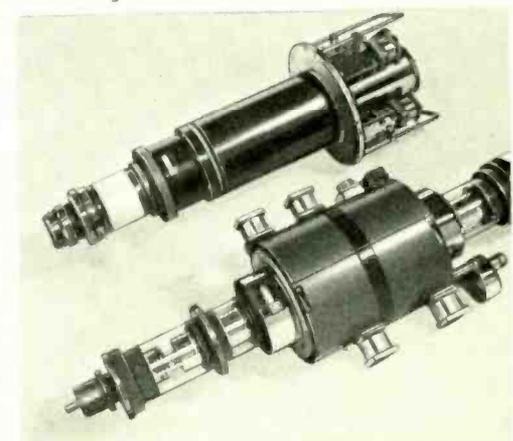


3. High-power travelling-wave tubes

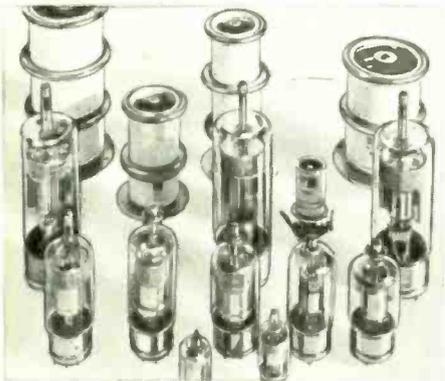


4. Hydrogen thyratrons




5. Pulse tetrodes

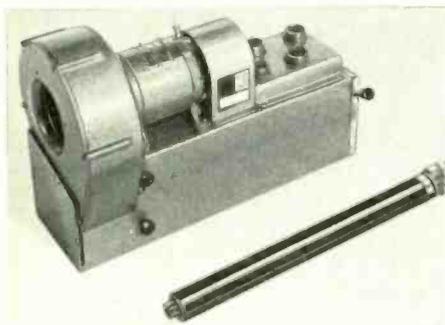

6. Low-power travelling-wave tubes

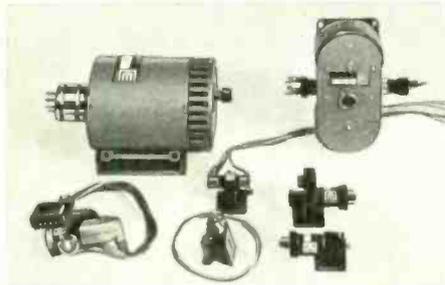

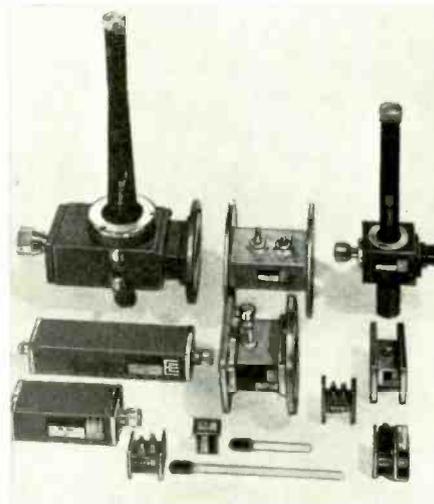7. Low power klystrons and backward wave oscillators



8. Duplexer devices



9. Voltage stabilisers



10. Storage tubes

1. Magnetrons  
 X-band  L-band  S-band  
 C-band  mm. band

2. High power klystrons

3. High-power travelling-wave tubes

4. Hydrogen thyratrons

5. Pulse tetrodes

6. Low-power travelling-wave tubes

7. Low power klystrons:  
 Receivers  Transmitters  
 Backward-wave oscillators

8. Duplexer devices:  
 X-band  L-band  
 S-band  C-band

9. Voltage stabilisers

10. Storage tubes

*Tick where appropriate and send this coupon for full data.*

To: English Electric Valve Co. Ltd.  
 Chelmsford, Essex, England

Name \_\_\_\_\_

Position \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_

Telephone exchange or STD code \_\_\_\_\_

Number \_\_\_\_\_ Extension \_\_\_\_\_

  
**ENGLISH  
 ELECTRIC  
 VALVE  
 CO LTD** 



## Post Haste

Drop us a line and you'll see. Morganite Filmet® resistors reach you faster. Because development batches of standard Filmet® are ready on the shelf right now. Waiting on your 'phone call. They come in three basic sizes, and they're not bound by the usual limitations of metal film resistors at all. Witness temperature coefficients like 15p.p.m./°C.

Selection tolerances as tight as  $\pm 0.1\%$ . What's more, we build the same kind of stability into special orders, too. We don't see why non-standard customers should get sub-standard service just because their supplier doesn't like putting his production line out of gear. In our books, made-to-measure resistors should be

made to *your* measure, not ours. With the performance *you* specify. And we don't make you pay through the nose when they arrive, either. You'll see what we mean when you ask for our price list covering the standard Filmet® range. Call us any time, and we'll send you a copy by return of post. First class, of course.



### MORGANITE RESISTORS LIMITED

Bede Industrial Estate, Jarrow, County Durham.  
Telephone: Jarrow 897771 Telex: 53353



® FILMET is a registered Trade Mark

WW—011 FOR FURTHER DETAILS

www.americanradiohistory.com

**QUAD 50** is a single channel 50 Watt amplifier designed for Broadcast, Recording and other applications in the Audio industry, completely proof against misuse and giving the highest quality of reproduction.



**INPUTS** - 0.5 Vrms unbalanced with provision for an optional plug-in transformer for bridging 600 ohms lines.

**OUTPUTS** - isolated providing 50 watts into almost any impedance from 4 to 200 ohms.

**DIMENSIONS** - 12 3/4" x 6 1/4" x 4 1/2"

*Complete the coupon and post today.*

**QUAD**  
for the  
closest approach  
to the  
original sound

Please send me full details of the QUAD 50 Amplifier

NAME .....

POSITION .....

COMPANY .....

ADDRESS .....

.....

(BLOCK CAPITALS)

**ACOUSTICAL MANUFACTURING CO. LTD.,**  
HUNTINGDON. Telephone: Huntingdon (0480) 2561/2

W W

# World Travellers pose for their passports

The Teonex family is big – 2,000 odd members, exclusive of semi-conductor relatives!

Like every family, they come in many shapes and sizes. Slim or fat, tall or squat, bigger or smaller, and in many ages: very young to very old.

But there are two common characteristics. They are very reliable and they all have to travel.


Nearly 60 countries now welcome Teonex, on Government and private contract. The family album is as comprehensive as you can get and most members are available from stock.

For technical specifications and price lists please write to Teonex Limited  
2a Westbourne Grove Mews · London W.11 · England  
Cables: Tosupply London W.11


## TEONEX



electronic  
valves &  
semi-conductors

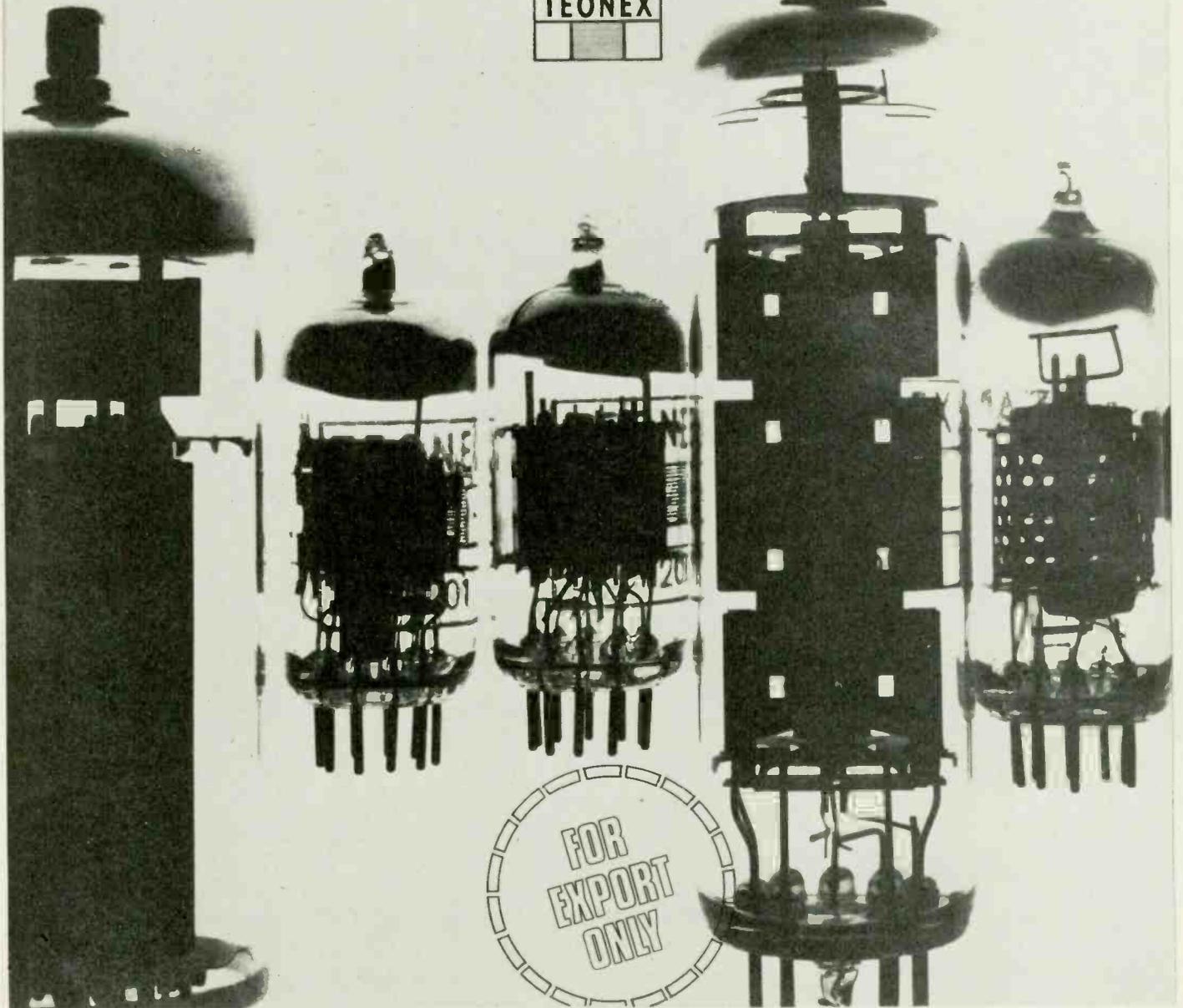

WW—013 FOR FURTHER DETAILS

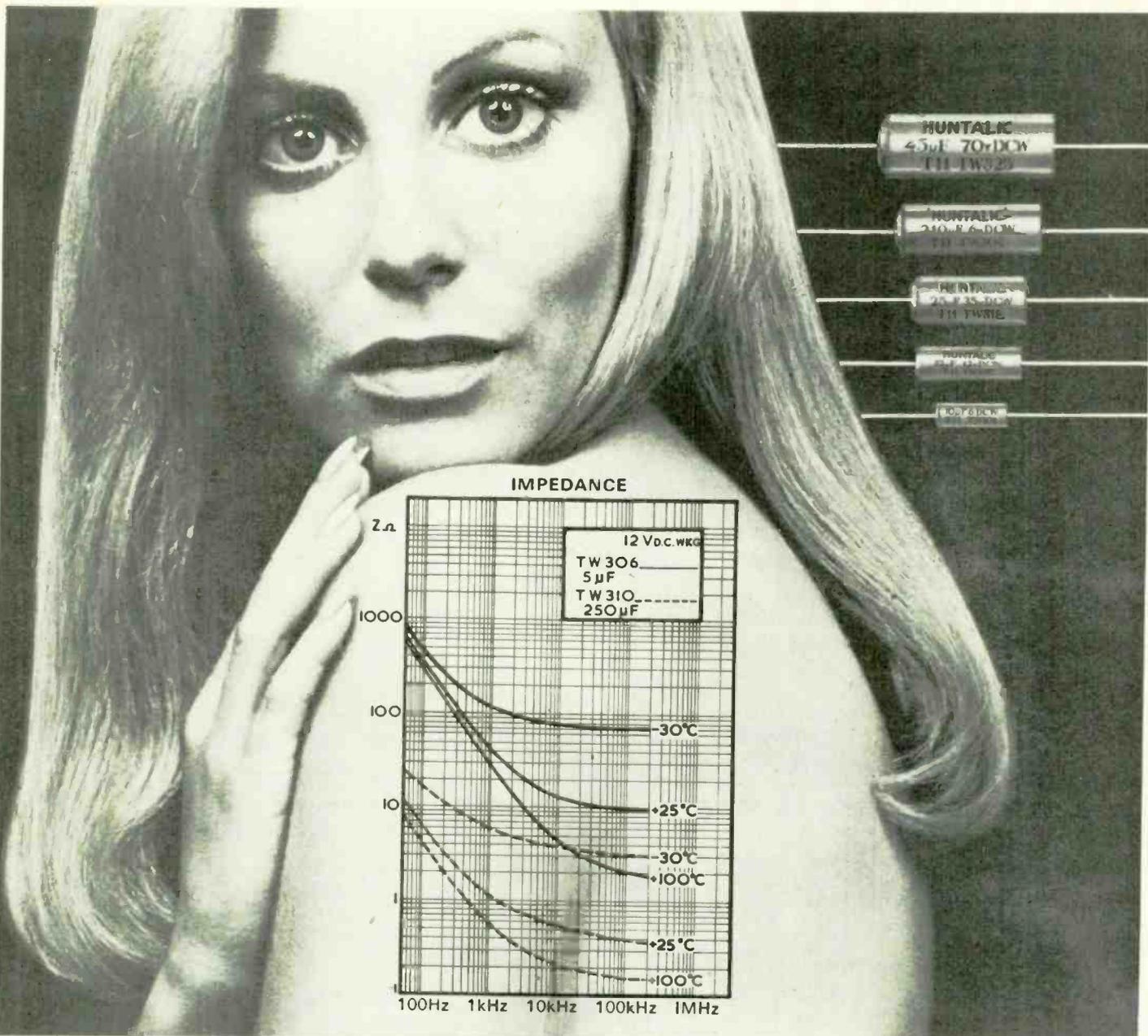

## We know a thing or two about Tantalum Capacitors — and here are the curves to prove it!

Erie T11 tantalums use every cubic millimetre, every gramme of weight, to give you more capacitance. Porous sintered slugs and high-conductivity electrolyte combine to give you high CV's per unit volume; in 5 case sizes; in values from 1 to 500  $\mu$ F; and in ratings from 6 to 70 Volts d.c.

Designed to operate at temperatures between  $-55$  and  $+100^{\circ}\text{C}$ , Teelevens eliminate corrosion risks by using completely neutral electrolyte ... and they are sealed in double cases. Leakage current characteristics are lower than accepted specifications. But see the curves yourself. They're



fascinating. Supply your name and address; we'll rush the leaflet to you.

**ERIE ELECTRONICS LTD.**  
Gt. Yarmouth, Norfolk.  
Telephone: 0493 4911  
Telex: 97421


# ERIE TANTALUM ELECTROLYTIC CAPACITORS

WW—014 FOR FURTHER DETAILS


# Vortexion

This is a high fidelity amplifier (0.3% intermodulation distortion) using the circuit of our 100% reliable—100 Watt Amplifier (no failures to date) with its elaborate protection against short and overload, etc. To this is allied our latest development of F.E.T. Mixer amplifier, again fully protected against overload and completely free from radio breakthrough. The mixer is arranged for 3-30/60Ω balanced line microphones, and a high impedance line or gram. input followed by bass and treble controls. 100 volt balanced line output.
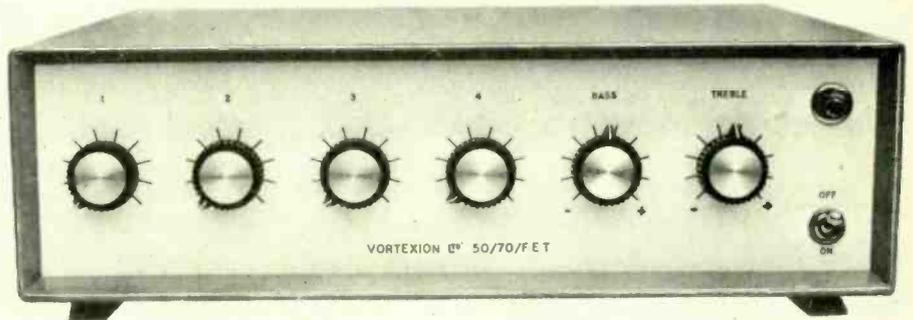
## THE VORTEXION 50/70 WATT ALL SILICON AMPLIFIER WITH BUILT-IN 4-WAY MIXER USING F.E.T.s.



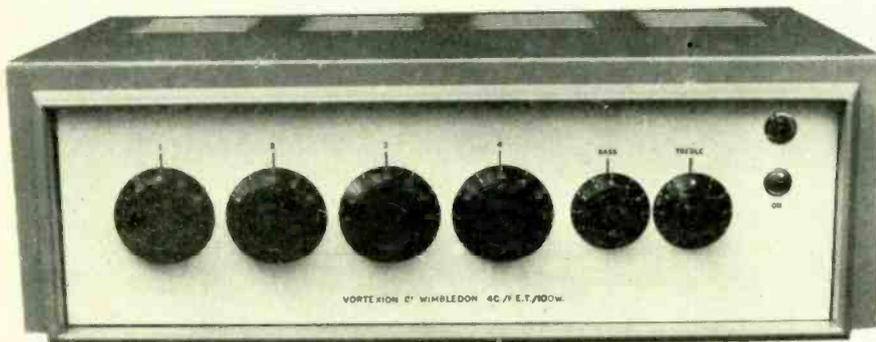**100 WATT ALL SILICON AMPLIFIER.** A high quality amplifier with 8 ohms—15 ohms or 100 volt line output for A.C. Mains. Protection is given for short and open circuit output over driving and over temperature. Input 0.4 V on 100K ohms.



**THE 100 WATT MIXER AMPLIFIER** with specification as above is here combined with a 4 channel F.E.T. mixer, 3 mic. 1 gram with tone controls and mounted in a standard robust stove enamelled steel case. A stabilised voltage supply feeds the tone controls and pre amps, compensating for a mains voltage drop of over 25% and the output transistor biasing compensates for a wide range of voltage and temperature. Also available in rack panel form.

**CP50 AMPLIFIER.** An all silicon transistor 50 watt amplifier for mains and 12 volt battery operation, charging its own battery and automatically going to battery if mains fail. Protected inputs, and overload and short circuit protected outputs for 8 ohms—15 ohms and 100 volt line. Bass and treble controls fitted.

Models available with 1 gram and 2 low mic. inputs. 1 gram and 3 low mic. inputs or 4 low mic. inputs.

**200 WATT AMPLIFIER.** Can deliver its full audio power at any frequency in the range of 30 c/s—20 Kc/s  $\pm$  1 dB. Less than 0.2% distortion at 1 Kc/s. Can be used to drive mechanical devices for which power is over 120 watt on continuous sine wave. Input 1 mW 600 ohms. Output 100—120 V or 200—240 V. Additional matching transformers for other impedances are available.

**ELECTRONIC MIXERS.** Various types of mixers available. 3-channel with accuracy within 1 dB Peak Programme Meter. 4-6-8-10 and 12-way mixers. Twin 2, 3, 4 and 5 channel stereo. Built-in screened supplies. Balanced line mic. input. Outputs: 0.5V at 20K or alternative 1mW at 600 ohms, balanced, unbalanced or floating.


see us at  
**SONEX'70**  
**Skyway Hotel**

Bath Rd, Hayes, Middx.  
April 24th — 26th 1970  
Fri & Sat: 11am — 9pm  
Sun: 11am — 6pm

**VORTEXION LIMITED,**  
Telephone: 01-542 2814 and 01-542 6242/3/4

**257-263 The Broadway, Wimbledon, S.W.19**  
Telegrams: "Vortexion, London S.W.19"

WW—015 FOR FURTHER DETAILS

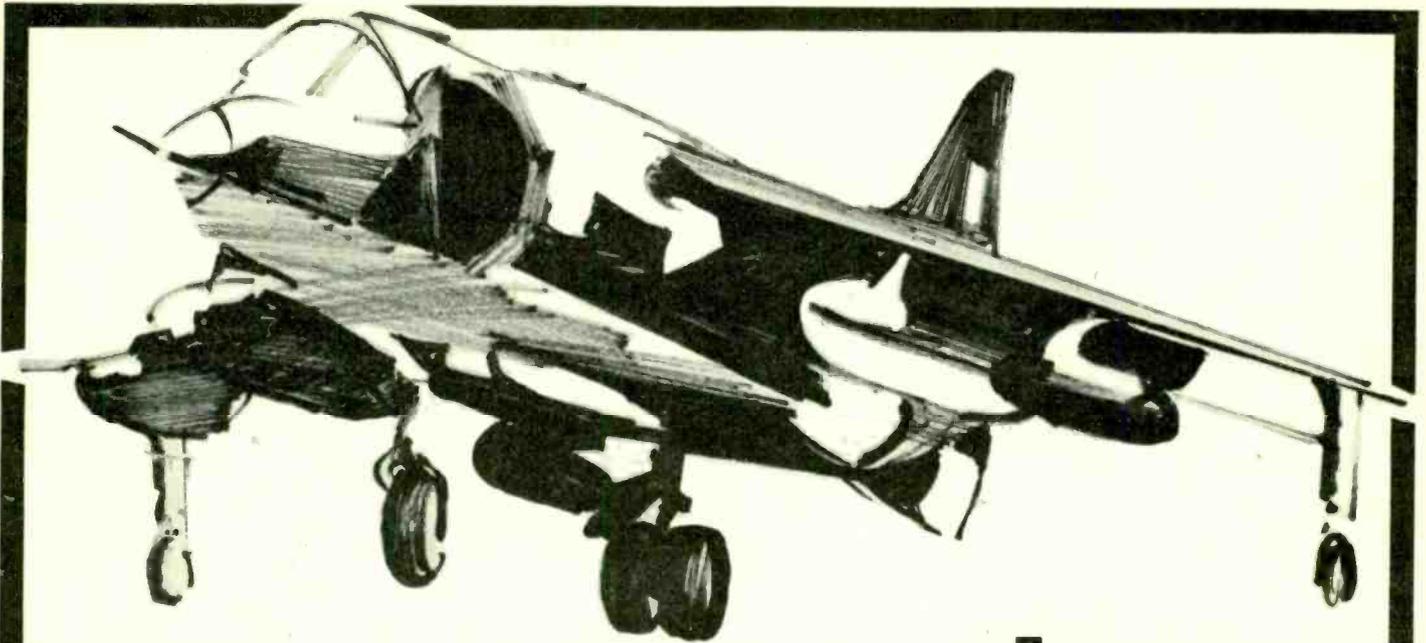

## What's so special about the **Jump Jet?**

The answer—*everything*.

It took years of intensive research and development to perfect every little part that goes to make the Hawker Harrier.

And these specially developed components include Gardners Transformers.

Many people seem to think that Gardners only provide 'off-the-shelf' equipment. It isn't true—80% of our production is for special components.

We design and develop highly specialised transformers for Defence projects, Radar, Sonar, electronics, control systems and similar sophisticated equipments.

Of course, we don't expect everyone to be making things like aircraft that don't need runways.

*They wouldn't be special anymore.*

---

Incidentally, Gardners manufacture the largest standard range of transformers in Europe. So even our un-specials are special!

Comprehensive publications available on request include.

*Microphone and Line Matching Transformers GT22.*

*Microminiature Transformers GT12.*

*Audio Transformers GT4.*

*Inverters GT21.*

*Saturable Reactors GT1.*

*Low Voltage, Isolating and Audio Transformers GT17.*

*Transformers for Tube Type Circuits GT24.*

**GARDNERS TRANSFORMERS LIMITED,**  
Christchurch, Hampshire BH23 3PN.

Tel: Christchurch 2284. (STD 0201 5 2284)  
Telex 41276 GARDNERS XCH.

the variable  
transformer  
range from  
the company  
with 35 years  
experience...

# Claude Lyons Regulac<sup>®</sup>



<sup>®</sup> Registered trade mark of Claude Lyons Limited

With every Claude Lyons Regulac comes the benefit of 35 years' experience in variable transformers. Regulacs come in hundreds of models from small single units for laboratory or instrument use to large ganged assemblies for high-power 3-phase operation at outputs from 210VA to 28.8 kVA and above.

The range includes portable, dual-output and oil-immersed models plus many high-frequency and special types—and is constantly being extended.

Regulacs provide smooth, continuous adjustment of voltage output from zero to line voltage and above, either hand-operated or motor-driven. No device is more useful, versatile and reliable for the control of AC voltage.



For full details write to Publicity Department, Hoddesdon  
**Claude Lyons Limited**  
Hoddesdon, Herts. Hoddesdon 67161 Telex 22724  
76 Old Hall St., Liverpool L3 9PX. 051-227 1761 Telex 62181

WW—017 FOR FURTHER DETAILS

[www.americanradiohistory.com](http://www.americanradiohistory.com)

CL71

# VALUABLE NEW HANDBOOK FREE TO AMBITIOUS ENGINEERS

Have you had *your* copy of "Engineering Opportunities"?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

### On 'SATISFACTION OR REFUND OF FEE' terms

This remarkable book gives details of examinations, and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

### WHICH OF THESE IS YOUR PET SUBJECT?

#### ELECTRONIC ENG.

Advanced Electronic Eng. — Gen. Electronic Eng. — Applied Electronics — Practical Electronics — Radar Tech. — Frequency Modulation — Transistors.

#### ELECTRICAL ENG.

Advanced Electrical Eng. — Gen. Electrical Eng. — Installations — Draughtsmanship — Illuminating Eng. — Refrigeration — Elem. Electrical Science — Electrical Science — Electrical Supply — Mining Electrical Eng.

#### CIVIL ENG.

Advanced Civil Eng. — Gen. Civil Eng. — Municipal Eng. — Structural Eng. — Sanitary Eng. — Road Eng. — Hydraulics — Mining — Water Supply — Petrol Tech.

#### RADIO ENG.

Advanced Radio — Gen. Radio Radio & TV Servicing — TV Eng. — Telecommunications — Sound Recording — Automation — Practical Radio — Radio Amateurs' Exam.

#### MECHANICAL ENG.

Advanced Mechanical Eng. — Gen. Mechanical Eng. — Maintenance Eng. — Diesel Eng. — Press Tool Design — Sheet Metal Work — Welding — Eng. Pattern Making — Inspection — Draughtsmanship — Metallurgy — Production Eng.

#### AUTOMOBILE ENG.

Advanced Automobile Eng. — Gen. Automobile Eng. — Automobile Maintenance — Repair — Automobile Diesel Maintenance — Automobile Electrical Equipment — Garage Management.

WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS INCLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRUMENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.

Which qualification would increase your earning power?  
 A.M.I.E.R.E., B.Sc. (Eng.), A.M.S.E., R.T.E.B., A.M.I.P.E.,  
 A.M.I.M.I., A.R.I.B.A., A.I.O.B., P.M.G., A.R.I.C.S.,  
 M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., C.ENG., CITY & GUILDS,  
 GEN. CERT. OF EDUCATION, ETC.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY  
 446A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

### THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointments Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

164 PAGES OF EXPERT CAREER-GUIDANCE

#### PRACTICAL EQUIPMENT

Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, etc. A.M.I.E.R.E. City & Guilds Radio Amateurs' Exam., R.T.E.B. Certificate, P.M.G. Certificate, Practical Radio, Radio & Television Servicing, Practical Electronics Engineering, Automation.

#### INCLUDING TOOLS

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.

## B.I.E.T.

You are bound to benefit from reading "ENGINEERING OPPORTUNITIES." Send for your copy now—FREE and without obligation.



## POST COUPON NOW!

TO B.I.E.T., 446A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE.

Please send me a FREE copy of "ENGINEERING OPPORTUNITIES." I am interested in (state subject, exam., or career).

.....

NAME .....

ADDRESS .....

.....

WRITE IF YOU PREFER NOT TO CUT THIS PAGE

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

WW-018 FOR FURTHER DETAILS

# Uncamouflaged stereo.

All too many stereo makers tend to gloss over their inadequacies with high-sounding rhetoric, hiding poor performance behind purple prose.

Sansui, Japan's foremost audio-only specialist, offers you stereo without camouflage. Complete, and all out in the open. We let features and figures do the talking for us, not empty phrases.

One of our most powerful and most popular systems, for example, offers:

The 180 watt 5000A receiver, with a 15 to 30,000Hz power bandwidth figure and distortion

of 0.8% or less. IC and FET circuitry, trouble-free output terminals, two AC outlets, MPX separation adjuster, and a ground terminal that permits a better than 65dB S/N ratio.

The 70 watt SP-2000 speaker system. You can hardly call those hand-carved "Kumiko" fretwork grilles "camouflage," when behind them are six perfectly positioned speakers, with a 12dB/oct. crossover network and 3-position level controls. Superb stereo reproduction throughout a wide 30

to 20,000Hz frequency response range.

Add the professional 2-speed manual turntable SR-3030BC, and 2-way 4-speaker SS-20 headphone set and you're ready for an eye-opening surprise in undisguised stereo.

If you've had enough of camouflage compromises and excess verbiage, we think you'll find us refreshingly frank. Because at Sansui, the only word that really counts is quality.

**Sansui**



England: BRUSH CLEVITE COMPANY LIMITED Thornhill, Southampton SO9 1QX Tel: Southampton 45166 / Ireland: RADIO CENTRE 122A, St. Stephen's Green, Dublin 2 / West Germany: COMPO HI-FI G.M.B.H. 6 Frankfurt am Main, Reuterweg 65 / Switzerland & Liechtenstein: EGLI, FISCHER & CO. LTD. ZURICH 8022 Zurich, Gotthardstr. 6, Claridenhof / France: HENRI COTTE & CIE 77, Rue J.-R. Thorelle, 77, 92-Bourg-la-Reine / Luxembourg: MICHAEL SHEN, EUROTEX 12, Route de Thionville / Austria: THE VIENNA HIGH FIDELITY & STEREO CO. 1070 Wien, Burggasse 114 / Belgium: MATELECTRIC S.P.R.L. Boulevard Léopold II, 1080 Brussels / Netherlands: TEMPOFOON BRITISH IMPORT COMPANY N.V. Tilburg, Kapitein Hatterasstraat 8, Postbus 540 / South Africa: GLENS (PTY) LTD. P.O. Box 6406 Johannesburg / Southern Yemen: BHICAJEE COWASJEE LTD. Steamer Point, Aden / SANSUI ELECTRIC CO., LTD. FRANKFURT OFFICE 6 Frankfurt am Main, Reuterweg 93, West Germany / SANSUI ELECTRIC CO., LTD. 14-1, 2-chome, Izumi, Sugiyama-ku, Tokyo, Japan

WW-019 FOR FURTHER DETAILS

# BROOKDEAL AMPLIFIERS: a limited guide to their unlimited uses.

Signal source	450	451	431	432
ac bridge (Hi-Z)	✓	✓		✓
ac bridge (Lo-Z)	✓		✓	
accelerometer (piezoelectric)	✓	✓		✓
accelerometer (moving coil)	✓		✓	
biological sensors				✓
CdS photocell	✓	✓		
condenser microphone	✓			✓
Cu dopad Ge photodetector	✓		✓	
electron multiplier	✓	✓		
Faraday cup	✓	✓		
Golay cell	✓	✓		
Hall-effect sample	✓	✓		
hydrophone	✓		✓	
hot carrier diode	✓		✓	
In Sb photocell (room temp)			✓	
In Sb photocell (cooled)	✓	✓		
inductive ratio divider	✓		✓	
ion detector	✓	✓		
magnetometer coils	✓		✓	
microwave point-contact diode	✓		✓	
moving coil microphone	✓		✓	
PbS photocell	✓	✓		
photodiode	✓	✓		
photomultiplier	✓	✓		
photovoltaic cell	✓	✓		
phototransistor	✓	✓		
plasma probes	✓	✓		
Pt wire detector			✓	
resistance thermometer	✓		✓	
scintillation detector	✓	✓		
thermistor	✓		✓	
thermocouple			✓	
thermopile			✓	
vibrating capacitor	✓	✓		

*This list includes present and envisaged applications of these amplifiers. For more information and specific applications assistance contact Geoffrey Gamble at 0344 23931/5.*



**Low-noise Amplifier Type 450**

Frequency Range 1Hz – 300kHz  
Gain 100dB – 18dB  
Noise Figure (1kΩ – 10MΩ) < 2dB above 0.5kHz  
Non Linearity < 0.05%  
Input Impedance 50MΩ, 20pF



**Systems Amplifier Type 451**

Frequency Range 1Hz – 1MHz  
Gain 80dB – 28dB  
Non Linearity (< 100kHz) < 0.05%  
Input Impedance 10MΩ, 25pF  
Output Impedance 600Ω



**Nanovolt Preamplifier Type 431**

Frequency Range 1Hz – 100kHz  
Gain 60dB  
Equivalent input noise voltage 400pV/√Hz  
Non Linearity < 0.1%  
Power Four PP7 batteries



**High IZI Amplifier Type 432**

Frequency Range 1Hz – 1MHz  
Gain 20, 40, 60dB  
Input Impedance 100MΩ, ~ 0.1pF  
Common Mode Rejection > 100dB below 1kHz  
Noise Figure (@ 1kHz) 0.5dB at 1MΩ

*If the signal source you are working with isn't listed above, this doesn't mean to say that we can't supply the amplifier you need. It's just that space is limited here. However, in the range 1Hz to 1MHz, we can noise-match most signal sources. Send for full information.*

# Brookdeal

Brookdeal Electronics Limited,  
Market Street, Bracknell, Berks. Tel: 0344 23931




**One  
of these  
ties will cut  
your wiring  
costs  
Which?**

Whatever cable tie you're using at the moment, Hellermann can almost certainly put a better one on your production line to cut your wiring costs. And with good reason.


Hellermann have the world's largest range of ties, clips, saddles, and binding systems. Each is purpose designed - one is certain to be exactly right for your purpose . . . whether for the semi-skilled operator, or the fully-trained engineer.

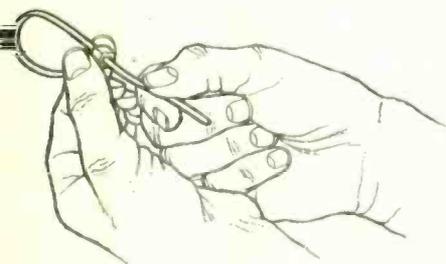And you'll find Hellermann ideas not only practical - but most often ingenious too.




For example, there's Insulok MS - one piece cable ties for quick, simple, hand

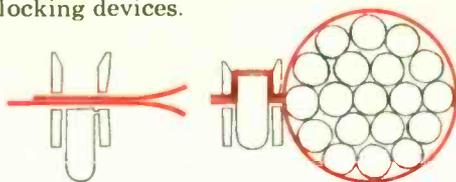or tool fixing without pins or metal locking devices.




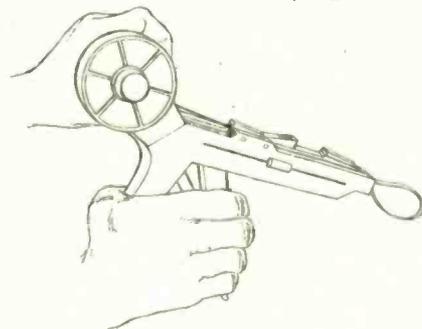More Hellermann ingenuity . . . an exclusive extrusion system that prevents strapping pulling out even under extreme vibration. The principle is utilised in two Hellermann tying systems.



The first is called Tyton - an 'off-the-reel' system that binds 50% faster than

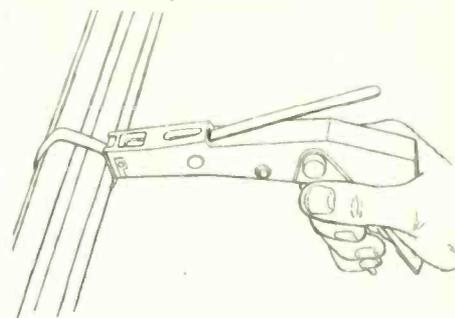any other comparable system. The second is Kabelrap - a heavy duty version using 'one-piece' ties.




These are just three of more than a dozen Hellermann systems.

So you can see, Hellermann are deeply involved in all aspects of cable tying.

Job for job - pound for pound - Hellermann will give you increased output, simplified production, minimised tie wastage, quick and easy wiring amendment and, as an added bonus, better looking cable bundles.

The only problem: which Hellermann tie suits you best.

# ask Hellermann

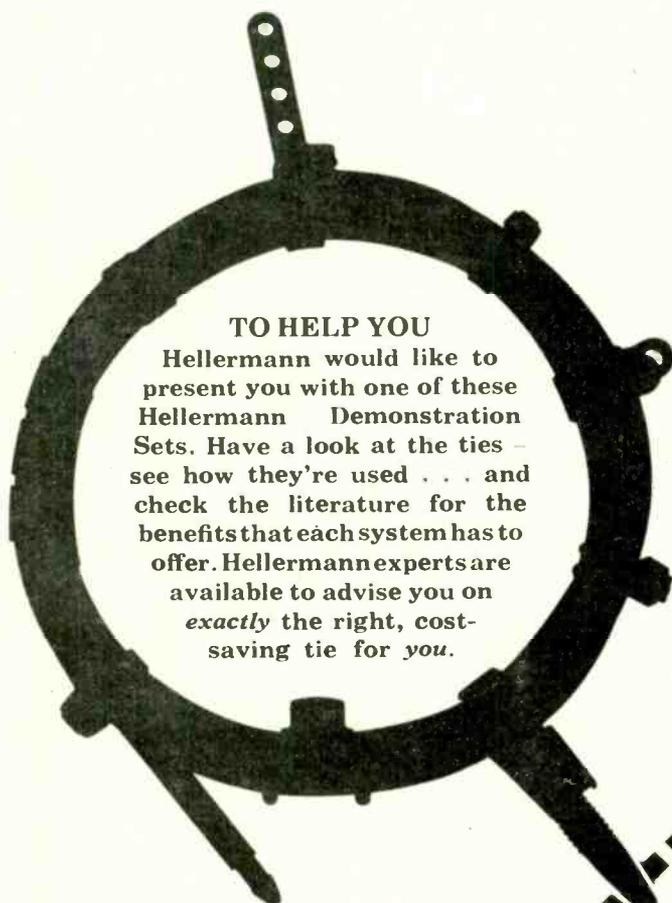

**TO HELP YOU**  
Hellermann would like to present you with one of these Hellermann Demonstration Sets. Have a look at the ties - see how they're used . . . and check the literature for the benefits that each system has to offer. Hellermann experts are available to advise you on *exactly* the right, cost-saving tie for you.

Please send me a Hellermann Demonstration Set and a copy of your Ties Selection Guide.

NAME \_\_\_\_\_

COMPANY \_\_\_\_\_

ADDRESS \_\_\_\_\_

WW4/70



WORLD LEADERS IN CABLE ACCESSORIES

**HELLERMANN ELECTRIC**

Division of Bowthorpe-Hellermann Ltd

Gatwick Road, Crawley, Sussex. Tel: Crawley 28888

A member of the Bowthorpe Holdings Group of Companies.

WW-021 FOR FURTHER DETAILS

# Radio Microphones mean an end to trailing cables!!

\*

See us at  
the Clubs'  
& Licensed  
Trade Exhibition  
Prince's Exhibition  
Hall, Birmingham  
11-15 May  
**STAND  
No. 42**  
  
**STAND  
No. 30**  
at Musical Ride  
New Century Hall  
Manchester  
28-30 May

## RESLO-AUDAC RADIO MICROPHONE GIVES REAL FREEDOM OF MOVEMENT

Here's the safe answer to the old problem of trailing cables. The Reslo-Audac Radio Microphone allows completely unhampered movement. Ideal for clubs, cabaret, theatres, bingo halls and many other applications. Illustration shows integrated microphone transmitter unit, no larger than a normal microphone.

**Star Names** using Reslo-Audac system include Des O'Connor, Ronnie Corbett, Mirelle Mathieu, Terri Stevens, Peter Gorden.


**Star Places** include the London Palladium, Victoria Palace, Churchills Club, Talk of the Town (London), The Carousel (London), Palace Theatre and many other places.

### Types Available


1. Integrated microphone transmitter
2. Separate transmitter packs
3. Choice of receiving units, including the new loudspeaker/amplifier unit

*Reslo-Audac radio microphone has to be heard to be believed. Ask for a demonstration!*

Full technical services available.

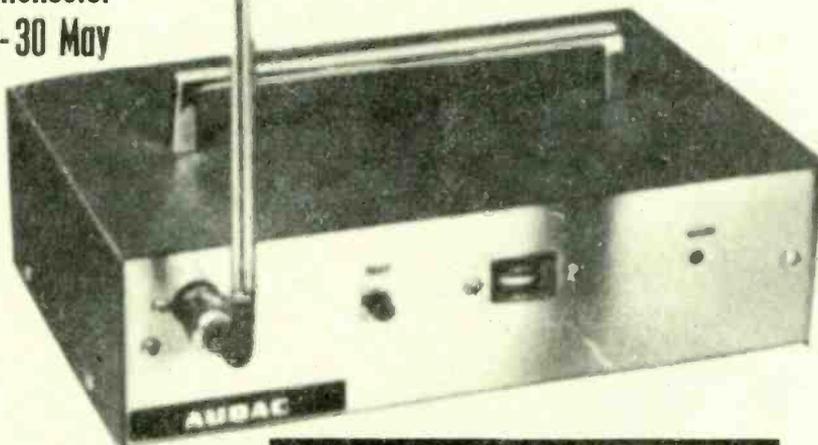

RESLO MIKES  
ROMFORD  
ESSEX

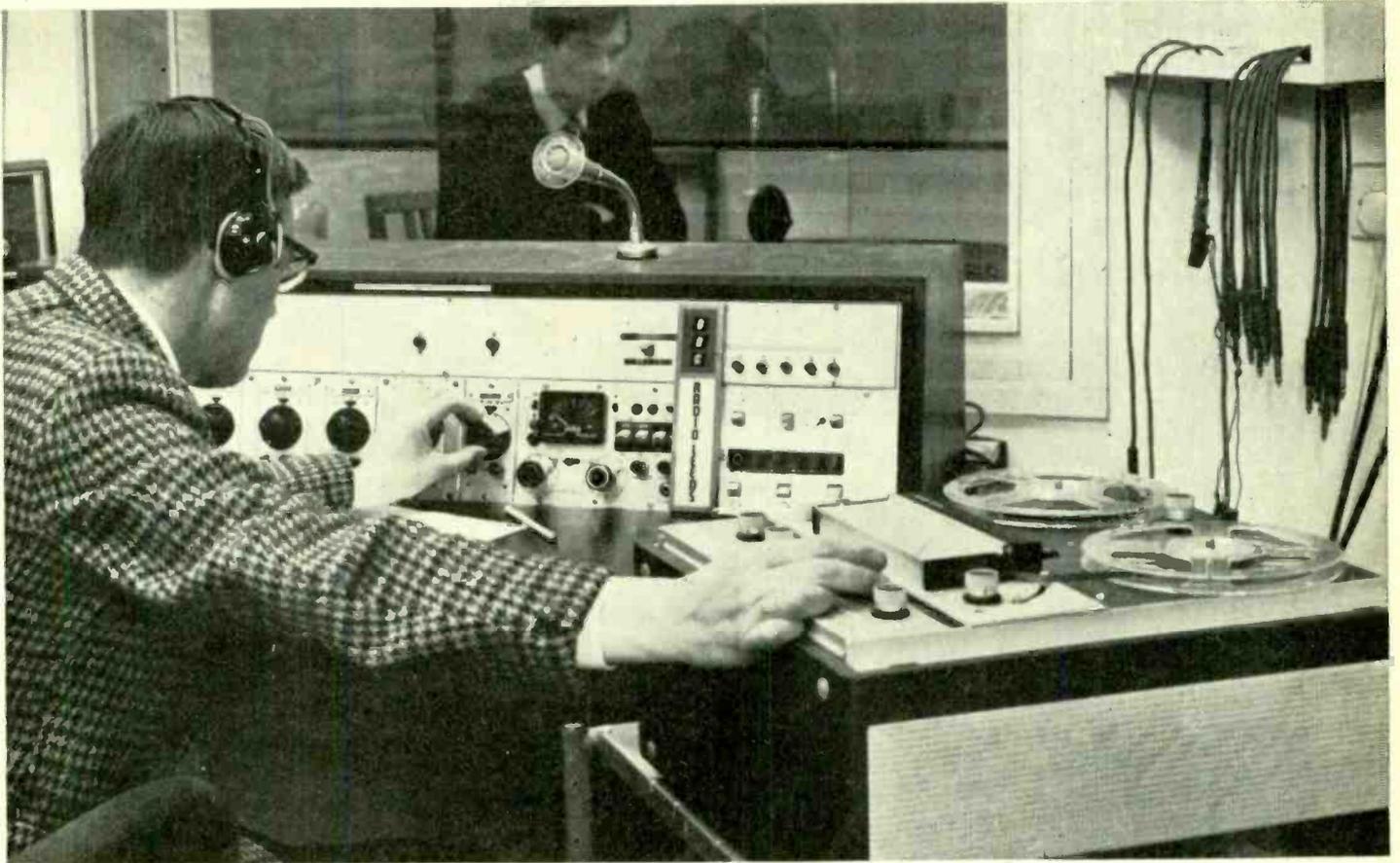

# Radio Leeds: Where a tape recorder must be good and reliable you'll find a Ferroglyph.

In a radio station, the tape recorder is in constant use. Technical performance is all-important; absolute dependability and split-second control are essential. So Radio Leeds uses the Ferroglyph Series 7 tape recorder.

Ferroglyph Series 7 recorders are British-made, available in Mono and Stereo, with and without end amplifiers, in two versions: in elegant hardwood case, or in grey vinyl case. All solid state, three speed, two inputs per channel with independent mixing, all incorporate a range of facilities

unparalleled in any other recorder. Retail prices are from £175 incl. P.T.

Follow the professionals; choose the recorder you know will serve you best at home or in your work: Ferroglyph—it makes sound sense. See your nearest stockist or send the coupon for details and address of nearest Ferroglyph specialist or ring 01-589 4485.

## Ferroglyph

*A member of the Wilnot Breeden Group*


To the Ferroglyph Co Ltd,  
Mercury House, 195 Knightsbridge,  
London, S.W.7.

Please send me a free brochure  
on the Ferroglyph Series 7   
or the Ferroglyph Manual   
for which I enclose £1.

Name \_\_\_\_\_

Address \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

ww

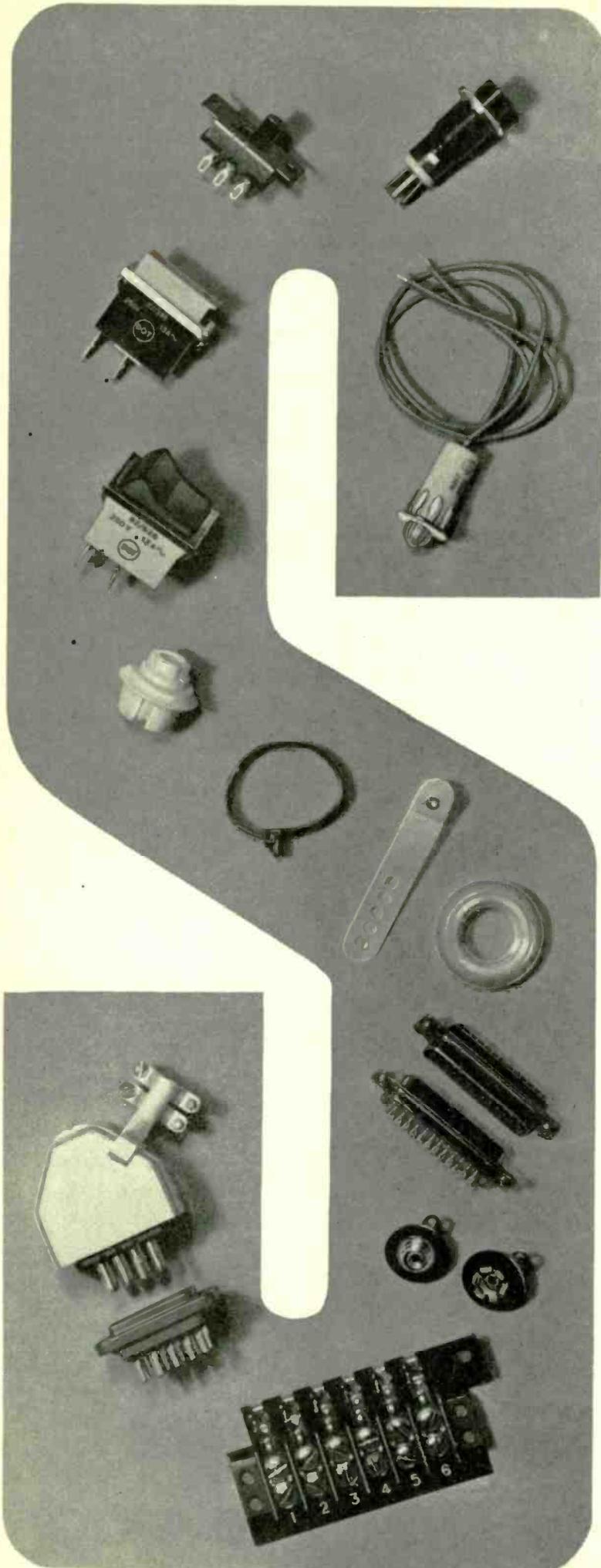

# SINGLE SOURCE SENSE

**OR**  
**How to get What you Want**  
**without Having to Try Very Hard**

If your parts requirements are small, and your call-off irregular, you have a problem. If, as often happens, you want parts quickly, you have another problem.

We are in business to help you solve both, quickly.

As stockholders of an enormous range of Radio, Electronic and Electrical Components, Metal Pressings, Clips, Fasteners and Assemblies by Cinch Dot and FT, we are the "single source" for pretty well everything of this kind you want in whatever quantity you want and at short notice.

**Two illustrated catalogues.** Thousands of stock items are detailed in our two fully illustrated catalogues—Fasteners and Electronics—either of which will be sent, post-free, to firms and organisations. Send for yours now, stating which catalogue you require.

**Make United-Carr Supplies**  
**your**

# SINGLE SOURCE

for Cinch Dot and FT Radio, Electronic and Electrical Components, Metal Pressings, Clips, Fasteners and Assemblies.

United-Carr Supplies Ltd.,  
 Frederick Road, Stapleford, Notts.  
 Sandiacre 2828 STD 060 239 2828




# Some notes on Bridge Measurement by WAYNE KERR

## Number 9 Four-Terminal Applications


In this issue we are illustrating the principal applications of four-terminal technique made available by the Transformer Ratio Arm Bridge.

The diagrams show six different measurement arrangements using four connection points to the bridge. The two upper terminals marked 'N' in the first diagram are the neutral connections, the two lower terminals representing connections to the bridge voltage and current transformers.

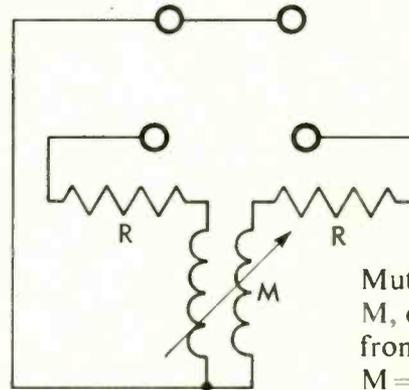
These diagrams are necessarily in summary form and, if further explanation is required, reference should be made to the first two issues of these notes.



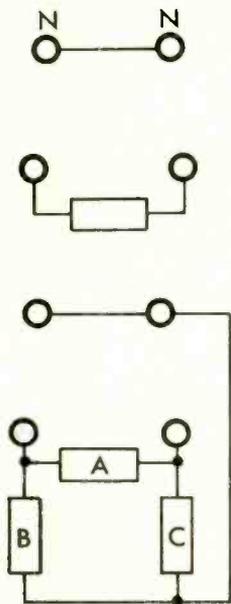
Mutual Inductance,  $M$ , can be derived from bridge C reading:  $M = R^2.C$ .



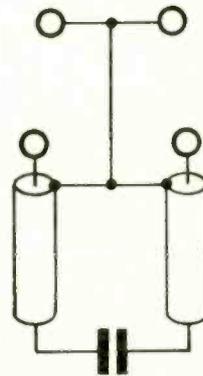
2-terminal connection for normal component measurements.



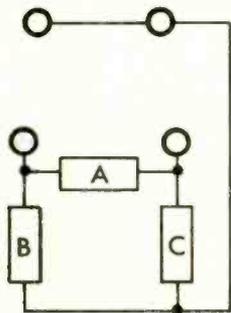
Small capacitors (and all other types of component) can be measured at the end of long test leads. The effect of the neutral connections is to prevent the cable capacitances appearing in shunt with the component under test.



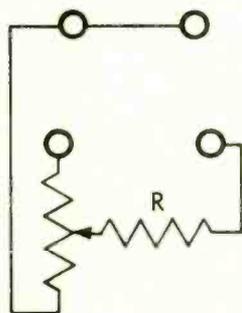3-terminal connection. Bridge reads A, ignores B & C. Ideal for in-situ checks.



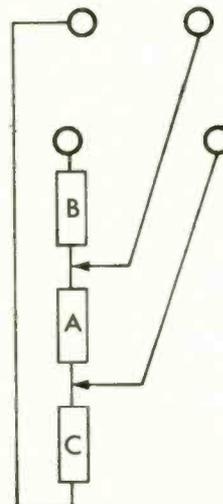Potentiometer ratios can be related to angular rotation. Bridge reads  $R \times (1/\text{ratio})$ .



4-terminal connections minimise lead and contact resistance errors. Bridge measures A, ignoring B & C.

THE WAYNE KERR COMPANY LIMITED  
NEW MALDEN · SURREY · ENGLAND

Telephone: 01-942 2202  
Cables: Waynkerr Malden  
Telex 262333

WW-025 FOR FURTHER DETAILS

# The cartridge recorder that gives you **all the professional features**

## CT80



### **concept**

Advanced — with outstanding professional technics in design and manufacture

### **design**

Solenoid operation — with motor size, number of amplifiers and facilities unequalled

### **componentry**

No compromise — with all devices to the highest telecommunication standards

### **construction**

Modular — with the latest technics and materials for heavy duty operation

### **facilities**

Complete — with every feature demanded by the industry, and more

### **finish**


Attractive, robust, up-to-the-minute — with extremely functional front panel

### **application**

For professional broadcasters — who appreciate the refinements and reliability of modern design and engineering

Ask for complete CT80 specifications and operating features!

**PLESSEY  
Electronics**

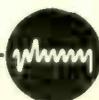

Sales and Service — Rola Recording Products Department —  
Garrard Engineering Limited Newcastle Street Swindon Wiltshire  
Telephone Swindon 5381 Telex 44271 or the manufacturer  
Plessey Electronics Pty Limited Equipment Unit 91 Murphy Street  
Richmond Australia 3121 Telex 30383 Cables ROLA Melbourne

WW—026 FOR FURTHER DETAILS


[www.americanradiohistory.com](http://www.americanradiohistory.com)

People  
keep  
talking  
about...

Solid State  
Microcircuits  
Integrated circuits  
Semiconductors  
? Integrated circuits  
Microcircuits  
State Solid Semiconductors  
etc Solid State etc etc



We  
talk  
valves!

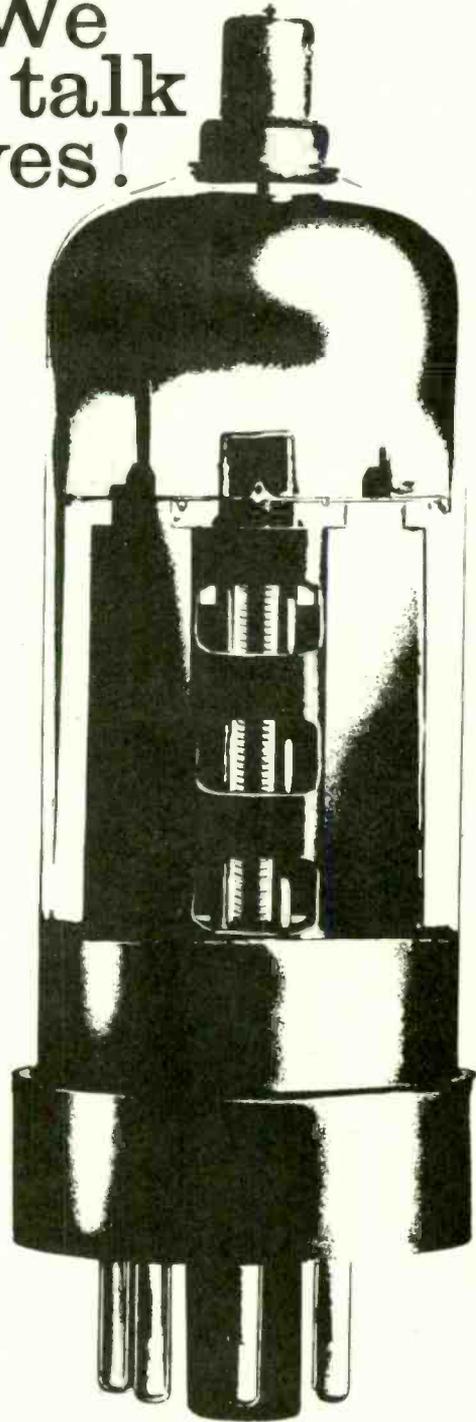

We can't, and don't,  
disregard current advancements  
in sophisticated electronics  
We can, and do,  
cater to an undiminishing requirement  
for replacement valves from all quarters of  
Industry, Education and Research.  
This requirement has been built up over  
many years past.  
So has Pinnacle

**Pinnacle**

**Pinnacle Electronics Limited**  
Achilles Street, New Cross, London, S.E.14.  
Phone: All departments 01-692 7285  
Direct orders: 01-692 7714

WW—029 FOR FURTHER DETAILS

# Make the most of sound - silently with the new Garrard SL95B

A Garrard gives you the perfect setting for music — silence.

With Garrard all you hear is the music.

The new Garrard SL95B is a superbly engineered transistor turntable with the added facility of automatic playing.

The SL95B features the constant-speed Garrard Synchro-LAB motor and incorporates:

- Cue and pause facility
- Low resonance wood and aluminium pick-up arm
- Gimbal-type pick-up arm pivots
- Slide-in cartridge carrier
- Calibrated pick-up arm bias compensation
- Calibrated fine stylus-force adjustment
- Automatic play of single records
- Styling of elegance and distinction

Hard-wood base and rigid clear plastic cover available as optional extras.



And this is what independent opinion said about the SL95, the immediate predecessor of the SL95B:

"I have tested it for wow, flutter and rumble and found them too low to be measured with any confidence. In every way I have tried to impede its working, I have failed!"

"I greatly admire the cueing device and I would not dream of setting my own manual clumsiness against the delicacy with which the automatic mechanism puts down the stylus in the groove. This is near perfection." Percy Wilson  
*Audio Record Review, August '68.*



**Garrard** a PLESSEY quality product



Garrard Engineering Limited, Newcastle Street, Swindon, Wiltshire, England. Telephone: Swindon 5381


WW-030 FOR FURTHER DETAILS

# Years of research...


... on accessories for dictating machines, tape recorders, tele-communications and electro acoustic equipment, etc.




STETOCLIP JUNIOR 60 HEADSET

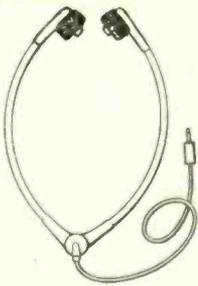

STETOCLIP LIGHTWEIGHT HEADSET

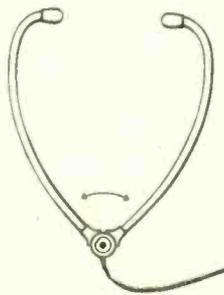


STETOCLIP SENIOR HEADSET

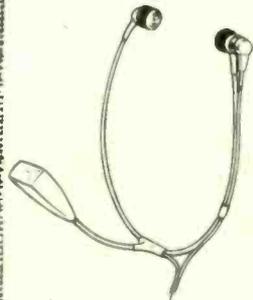

STETOMIKE BOOM MICROPHONE HEADSET




PLASTIC & NYLON EARHANGERS

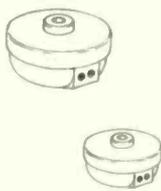


STANDARD & SUB-MINOR EARPHONES



STEREOCLIP HEADSET

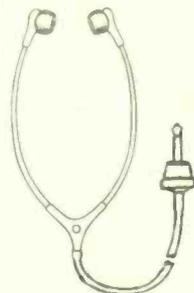

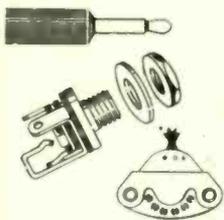
STETOTUBE HEADSET & SOUNDPLUG FOR HOSPITALS



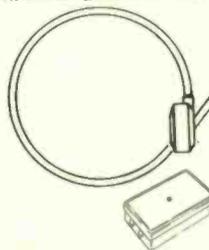
2.5 mm. and 3.5 mm. JACK PLUGS & SOCKETS & SUB-MINIATURE SWITCHES



DANASOUND HEADSET WITH OR WITHOUT BOOM MICROPHONE



THROAT MICROPHONE E.M. MICROPHONES

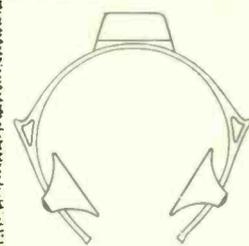

DANASONIC INDUCTION AUDIO LOOP RECEIVER

**Danavox**  
INTERNATIONAL

**DANAVOX (GT. BRITAIN) LTD.**

Electro-Acoustic Components and Hearing Aids  
"BROADLANDS" BAGSHOT ROAD,  
SUNNINGHILL, ASCOT, BERKS.

## No sulphur-sickness here

Factory chimneys turn out sulphur, and sulphur makes industrial receiving valves sick and unreliable. At Mullard we don't tolerate sick valves, so we set about eliminating the sulphur menace. Investigations – including putting a model of the factory in a wind tunnel – led finally to a new specification for fuel oil. Now before we use any fuel oil it's checked for sulphur content. We go to any lengths to ensure our special valves are healthy and reliable.


**The time we spend on environmental control cuts your equipment down-time...another reason it pays to ask your supplier for Mullard.**

# Mullard

Mullard Limited Industrial Electronics Division  
Mullard House Torrington Place London WC1 01-580 6633

### New Buyers Guide

There's a new wallchart on Mullard special quality receiving valves. It gives comprehensive equivalents information, and it's free from any Mullard Industrial Distributor – or use the reader enquiry service.

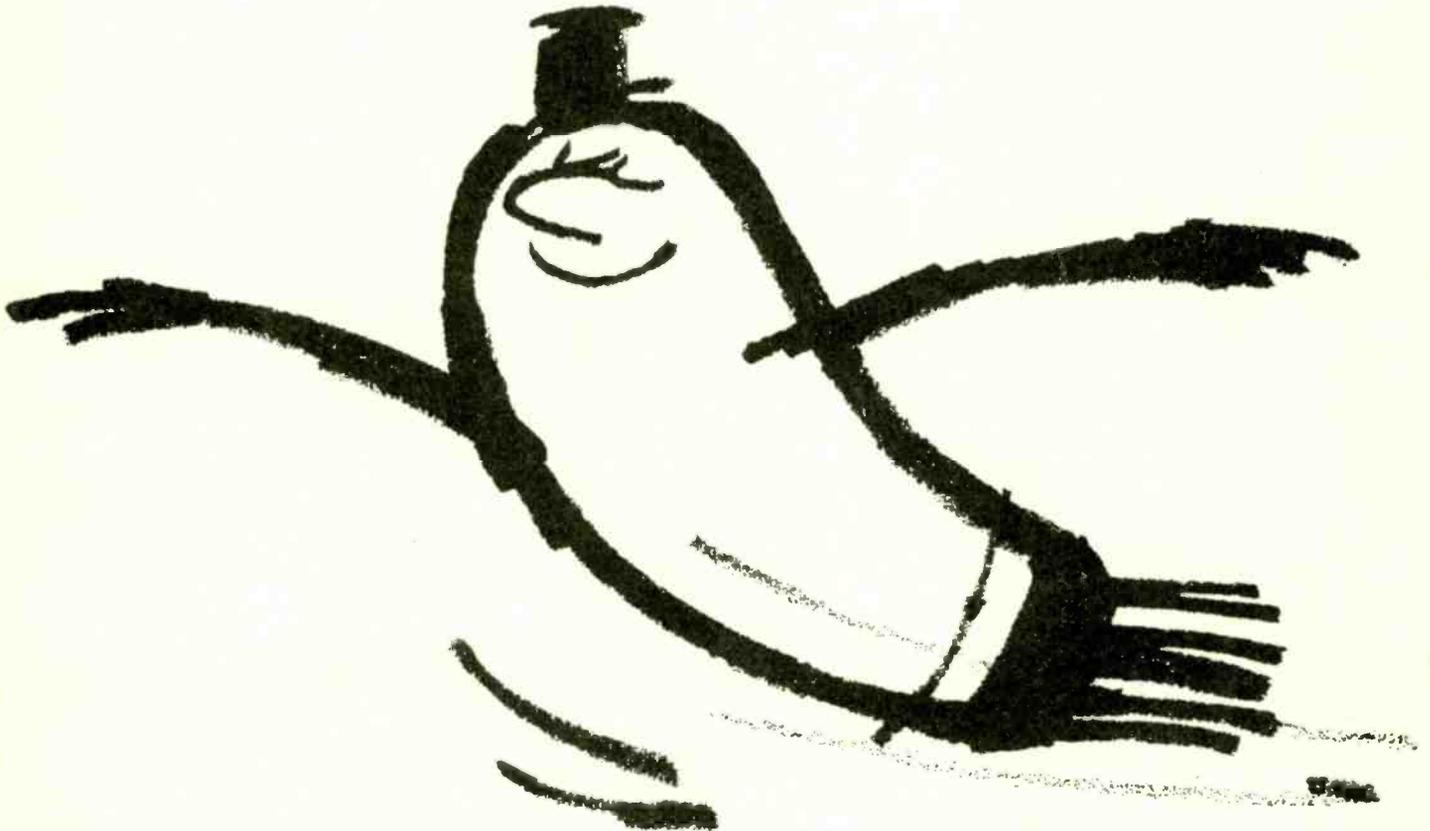

IED 268

WW—032 FOR FURTHER DETAILS

[www.americanradiohistory.com](http://www.americanradiohistory.com)

# Mullard industrial distributor service



**Birmingham: Central 5060**  
Gothic Electrical Supplies Ltd., Gothic House, Henrietta Street, Birmingham 19.

**Birmingham: Aston Cross 4301**  
Hawnt & Company Ltd., 112/114 Pritchett Street, Birmingham 6.

**Bristol 294313**  
Wireless Electric Ltd., 'Wirelect House', 122/123 St. Thomas Street, Bristol 1.

**Crawley 28700**  
SASCO, Gatwick Road, Crawley, Sussex.

**Glasgow: Govan 3347/3991**  
Harper Robertson Electronics Ltd., 82 Loanbank Quadrant, Glasgow SW1.

**Leeds 636311**  
Farnell Electronic Components Ltd., Canal Road, Leeds LS12 2TU.


**London: Elgar 7722**  
Cables & Components Ltd., Park Avenue, London N.W. 10.

**London: New Cross 9731**  
Edmundsons Electronics Ltd., 60-74 Market Parade, Rye Lane, London S.E. 15.

**Leicester: Leicester 768561**  
Townsend-Coates Ltd., Coleman Road, Leicester.


**Rochdale 47411**  
Swift-Hardmans, P.O. Box 23, Hardale House, Baillie Street, Rochdale.

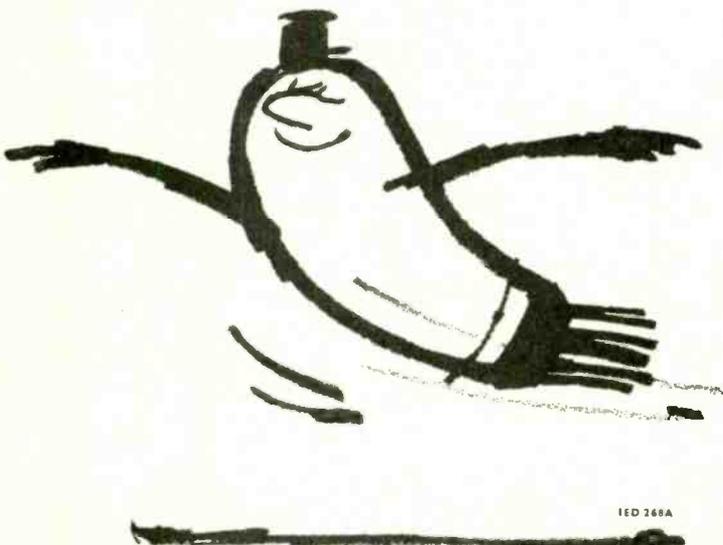**Sheffield 27161**  
Needham Engineering Co. Ltd., P.O. Box 23, Townhead Street, Sheffield 1.



1ED 268A

## TOWERS.. above all others

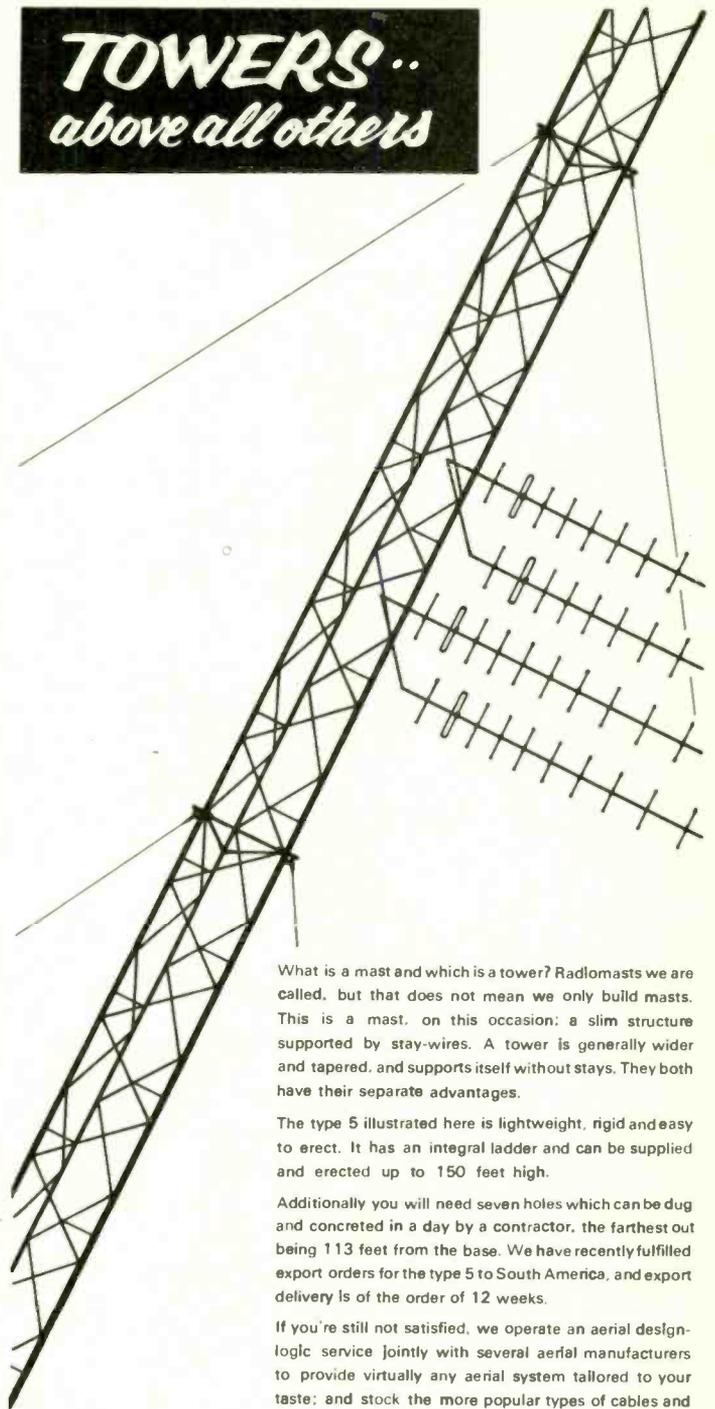

What is a mast and which is a tower? Radiomasts we are called, but that does not mean we only build masts. This is a mast, on this occasion: a slim structure supported by stay-wires. A tower is generally wider and tapered, and supports itself without stays. They both have their separate advantages.

The type 5 illustrated here is lightweight, rigid and easy to erect. It has an integral ladder and can be supplied and erected up to 150 feet high.

Additionally you will need seven holes which can be dug and concreted in a day by a contractor, the farthest out being 113 feet from the base. We have recently fulfilled export orders for the type 5 to South America, and export delivery is of the order of 12 weeks.

If you're still not satisfied, we operate an aerial design-logic service jointly with several aerial manufacturers to provide virtually any aerial system tailored to your taste; and stock the more popular types of cables and connectors, as well as the simpler aerial systems for all the commercial bands. If there's more you want—call us anytime.


**RM RADIOMASTS**   
19 CROSS STREET MOULTON  
NORTHAMPTON

☎ NN3 1RZ

☎ 0604 43728

WW—033 FOR FURTHER DETAILS

# MICROPHONES & ACCESSORIES

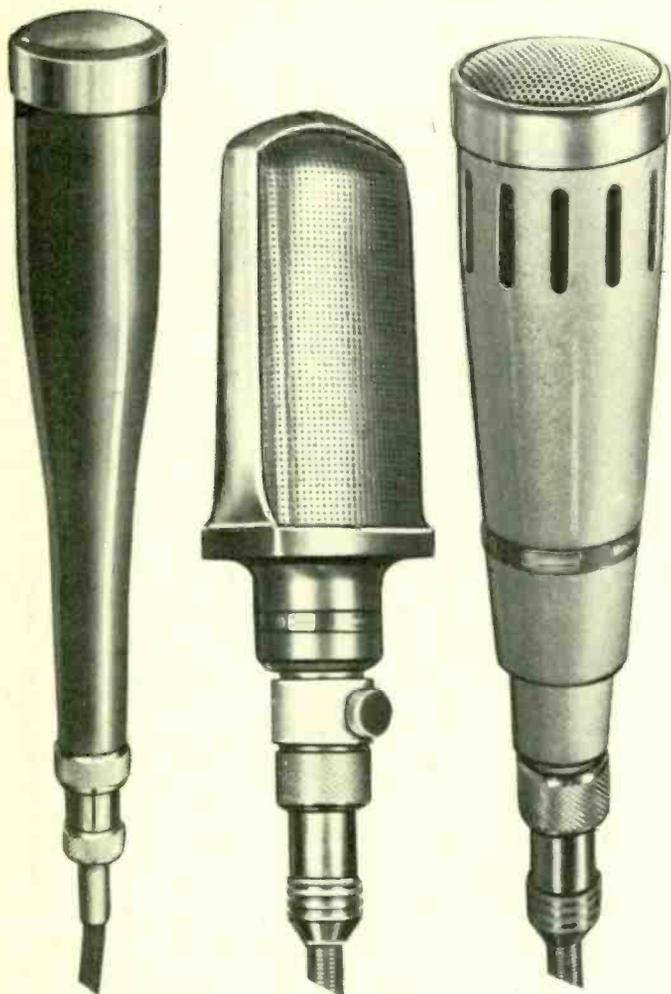

DP4

GR1

GC1

Our range of microphones includes various types, dynamic and ribbon, omnidirectional and cardioid patterns, with or without switches, for hand or stand use. All microphones are manufactured in a special section of our works, under strictly controlled conditions with stringent test and inspection at every stage. Each and every microphone is individually tested both aurally and on Bruel & Kjoer visual and graphic recording test equipment for conformity to a prescribed performance. Accessories such as desk or floor stands, wind shields and parabolic reflectors are available.

We also manufacture high grade amplifiers, mixers and ambiophonic units, loudspeakers and associated equipment for P.A. work, disc recorder amplifiers and cutter heads.

Please send for fully descriptive literature:

**Grampian**

SOUND EQUIPMENT

GRAMPIAN REPRODUCERS LTD

HANWORTH TRADING ESTATE,  
FELTHAM, MIDDLESEX.  
TELEPHONE: 01-894-9141

**Adamin**

## MODEL 15

### MICRO SOLDERING INSTRUMENT



- **EXTREME VERSATILITY**

Range of 8 interchangeable bits, from  $\frac{3}{64}$ in. (.047in.) to  $\frac{3}{16}$ in., including long-life PERMATIPS.

- **ULTRA-SMALL SIZE**

Length  $7\frac{1}{8}$ in. Weight  $\frac{1}{2}$  oz.  
Max. handle dia.  $\frac{7}{16}$ in.

- **EXTRA-HIGH PERFORMANCE**

Heating time 90 secs. Max.  
bit temp. 390°C. Loading 15  
watts—equal normal 30/40-  
watt iron.

- **ALL VOLTAGES**

The ADAMIN range includes five other models (5, 8, 12, 18 and 24 watts), Thermal Strippers (PVC and PTFE) and a De-Soldering Tool. Please ask for colour catalogue A/5.




### LIGHT SOLDERING DEVELOPMENTS LTD

28 Sydenham Road, Croydon, CR9 2LL

Tel: 01-688 8589 & 4559

WW-035 FOR FURTHER DETAILS

# Heathkit for Instrumentation

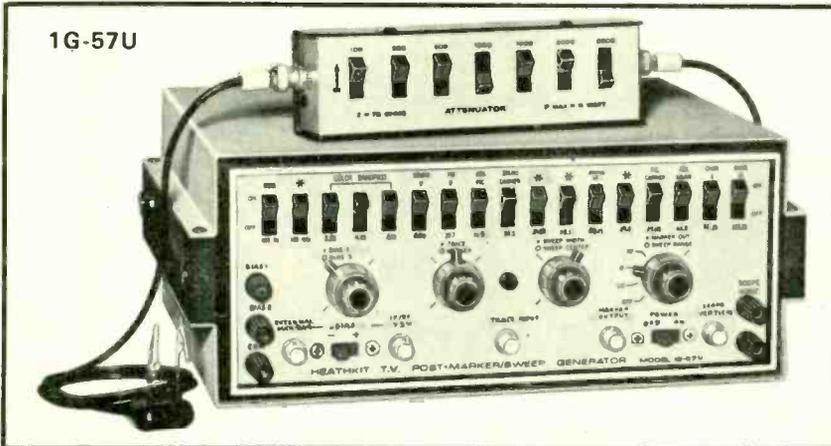

The Heathkit range of Electronic test instruments including the latest advances in Solid-State instrumentation has been especially prepared for the High Fidelity and Television Service Engineer as well as the Industrial and Laboratory Instrument User.

Whatever your requirements, be they Potentiometric Chart Recorders, Power Supplies or General Test Instruments, substantial savings against similar specifications of other Manufacturers can be made by using Heathkit Instrumentation.


## LATEST SOLID-STATE POST-MARKER/SWEEP GENERATOR, 1G-57U is typical of the Heathkit ultra-functional instrumentation styling

**1G-57U SPECIFICATION**—Marker frequencies: 100 kHz. Marker frequencies, crystal controlled: 3.83, 4.43, 5.03 and 6.0 MHz.  $\pm 0.01\%$ , 10.7, 31.5, 33.5, 34.65, 35.5, 38.15, 39.5, 39.65, 41.5, 58.25 and 196.25 MHz  $\pm 0.005\%$ . Modulation frequency: 400 Hz. Input impedance: External Marker, External sweep and Attenuator—75 ohms. Demod in—220 K ohms. Output impedance: Marker Output, Sweep Output and Attenuator—75 ohms. Scope Vert.—22 K ohms. Bias Voltage: Positive or negative 15 volts D.C. at 10 milliamperes. Type of marker: Birdie. Controls: Bias control with pull-on/push-off switch; Marker/Trace—dual concentric; Sweep Width/Sweep Centre—dual concentric; Marker out—concentric with Sweep Range switch; and Phase. Switches: Rocker type—Reverse; Modulation On/Off. Transistor—

diode complement: (19) 2N3692 transistors; (7) 2N3393 transistors; (1) 2N3416 transistor; (3) silicon diode rectifiers; (2) crystal diodes; (1) 13.6 volt zener diode; (1) 20 volt zener diode. Sweep frequency ranges and output voltage: LO Band—3.0 to 6.0. MHz  $\pm 1$  dB at 0.5 volts rms (min.) fundamentals, and 10.7 MHz on harmonics. IF Band—31 to 42 MHz  $\pm 1$  dB, at 0.5 volts/rms (min.) fundamentals, and 10.7 MHz on harmonics. RF Band—55 to 61 MHz  $\pm 1$  dB at 0.5 volts/rms (min.) fundamentals and 192 to 198 MHz on harmonics. Attenuator: Total of 70 dB or attenuation in seven steps—1 dB, 3 dB, 6 dB, 10 dB, 10 dB, 20 dB and 20 dB. Power requirements: 105-125 or 210-250 volts, 50 Hz A.C. at 20 watts.

Kit K/1G-57U, £75. Carr. 8/-.

Ready-to-Use A/1G-57U, £90. Carr. 8/-;

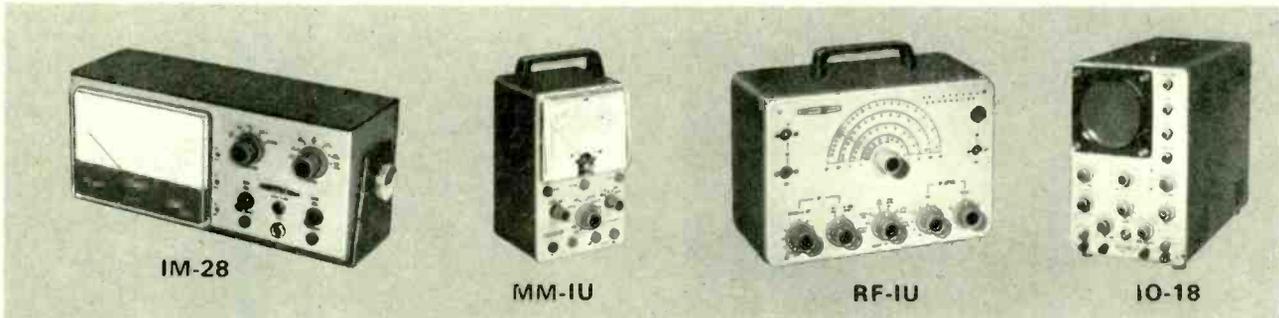

## RESTYLED TEST, SERVICE AND WORKSHOP INSTRUMENTS

The Heathkit range of instrumentation can adequately provide engineers with quality instruments at lowest cost, whatever your requirements, be they VVMs, Generators, Oscilloscopes, Transistor Testers or Power Supplies.

### FOR THE HOME WORKSHOP

The householder and hobbyist can, by purchasing easy-to-build Heathkits, obtain low cost models for testing household appliances, automobile circuitry, electrical/electronic models.



SEND FOR THE 1970 FREE HEATHKIT CATALOGUE and see for yourself the wide range of instruments, Hi-Fi, Amateur and Leisure products

Schlumberger Company


DAYSTROM LTD, Gloucester GL2 6EE, England. Tel: Glos 29451. Telex: 43216

To: DAYSTROM LTD, Gloucester, GL2 6EE, England  
 Please send me full details of Heathkit models  
 Send me FREE CATALOGUE  
 NAME .....  
 ADDRESS .....  
 POST CODE .....  
 Ref: 29/4




one man  
one hour  
one hundred feet

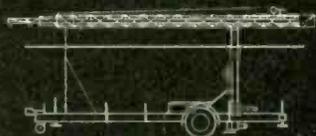The 100 ft free standing mobile is only one of our full range of telescopic, tilt-over towers from 25' to 120'. Road trailer conforms to the Road Traffic Act in all respects. Full specifications of our complete range: mobile, semi-portable and fixed, are in our brochure — send for it today!



**STRUMECH  
VERSATOWER  
SYSTEM**

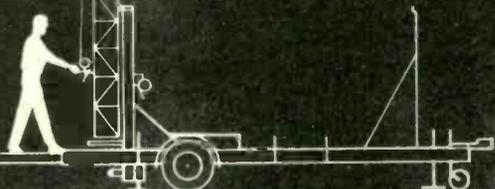Strumech Engineering Limited  
Portland House, Coppice Side,  
Brownhills, Walsall, Staffs, England.  
Telephone: Brownhills 3651




WW-037 FOR FURTHER DETAILS

This  
**new**  
range of  
**AIR SPACED  
VARIABLE  
CAPACITORS  
and TRIMMERS ...**
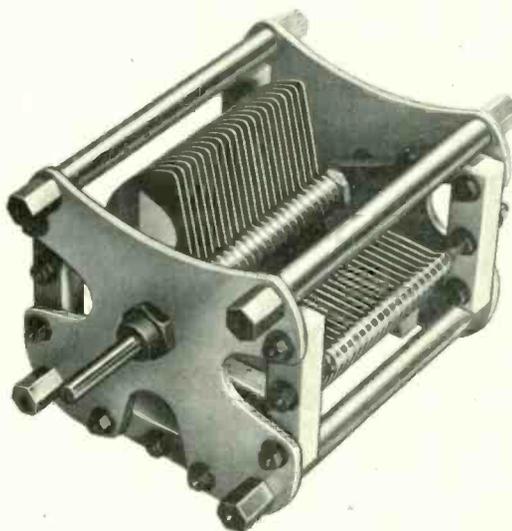
# TINSLEY

These Capacitors and Trimmers, previously made under the "Cydon" trademark are now being manufactured and marketed by us in London.




# TINSLEY

Write today for complete details  
H. TINSLEY & CO LTD · WERNDÉE HALL  
SOUTH NORWOOD · LONDON SE25 · 01-654 6046

WW-038 FOR FURTHER DETAILS


# OMRON PROCESS TIMERS

## SYS TIMER

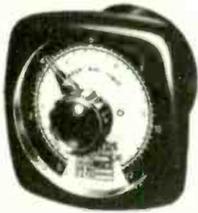

- ★ SYNCHRONOUS MOTOR & CLUTCH
- ★ 10 MILLION OPERATIONS
- ★ Instantaneous & Timed out 3 AMP contacts
- ★ Repeat Accuracy  $\pm \frac{1}{2}\%$
- ★ Dial ranges 0-10 secs up to 0-28 hrs. May also be used as impulse start

£11 dependent on quantity

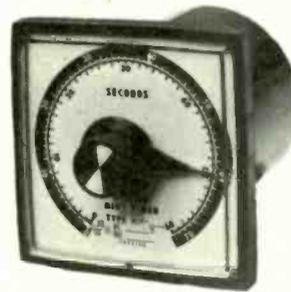

## NSY TIMER

- ★ 2 sets 5 amp changeover output contacts
  - ★ 5 Million operations
  - ★ Repeat accuracy  $\pm \frac{1}{2}\%$
  - ★ Set time can be altered whilst in operation
- Dial ranges from seconds to hours

Approx. 160/- each dependent on quantity.

## STP TIMER



- SYNCHRONOUS MOTOR & CLUTCH  
Matchbox size frontal area  
Automatic re-set
- ★ PLUG-IN OCTAL BASE
  - ★ INSTANTANEOUS AND TIMED OUT
  - ★ 2 AMP CONTACTS
- ★ RANGES: 0-10 SECS TO 0-36 MINS

£5 dependent on quantity



## TEMPERATURE CONTROLLER TYPE THP

- ★ THERMISTOR OPERATED
  - ★ OCTAL BASE PLUG IN
  - ★ COMPACT
- Temperature ranges up to 280°C  
Output contacts 4 amp  
Repeat Accuracy 3% full scale  
Complete with Thermistor

Approximately 121 dependent on quantity.

## OMRON PRECISION CONTROLS

OMRON APPROVALS: CSA. US Mil Spec. SEV.UL. IMMEDIATE DELIVERY OF LIMIT & MICRO SWITCHES, FLOATLESS LIQUID LEVEL CONTROLS, PROXIMITY SWITCHES

# WORLD FAMOUS I.M.O. (ELECTRONICS) LTD. VARIABLE VOLTAGE CONTROLS

## VARIABLE TRANSFORMERS



- ★ Output 0-260V
- ★ Input 230V 50/60CPS
- ★ Shrouded for Bench or Panel mounting

Inset shows latest pattern Brush gear ensuring smooth continuous adjustment.



£5.10.0 1 amp      2.5 amp £6.15.0      8 amp £14.10.0      12 amp £21.0.0  
 5 amp £9.15.0      10 amp £18.10.0      20 amp £37.0.0


## CONSTANT VOLTAGE TRANSFORMER.



Maintain spot-on test gear readings with Automatic Mains stabilizer.

- Specification:
- ★ Output 240V
  - ★ Accuracy  $\pm 1\%$
  - ★ Input 190-260V
  - ★ Capacity 250 watts
  - ★ Corrected wave
- £12.10.0 C & P 20/-


## 20 AMP LT SUPPLY UNIT

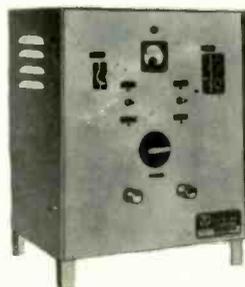

- ★ Input 240V
- ★ Output 20 amps at 24V and 12V fully adjustable
- ★ Size 18" x 12" x 20" high
- ★ Weight 50 lbs.

£35.0.0  
 40/- C & P (G.B.)

## SOLID STATE VARIABLE VOLTAGE CONTROL

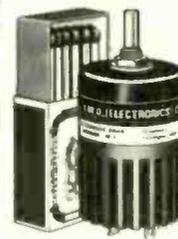

- ★ Output 25-240V
- ★ Input 240V 50 CPS
- ★ 5 amp & 10 amp models
- ★ Completely sealed

5 amp model £8.7.6  
 10 amp model £13.15.0

I.M.O. (PRECISION CONTROLS) LTD  
 (Dept WWX) 313 EDGWARE ROAD, LONDON, W.2. TEL. 01-723 2231

# EAGLE SERVICE & TEST EQUIPMENT



We understand what you need and we make sure that you get it — from the latest EP.100LN Band Suspension Multimeter/Transistor Tester, through Signal Generators, KV Probes and Circuit Tracers to the KEW.7 Pocket-Size Tester — Eagle have it. You can count on Eagle quality. What's more, you can count on Eagle prices. And above all — you can count on the

quickest possible delivery!

And another attractive thing about the range of Eagle Products is the rate at which fast-selling

new items are added! See our new catalogue, which proves the point!

Send the coupon to the Sole Distributors of Eagle Products — B. Adler and Sons (Radio)

Limited, Coptic Street,

London, W.C.1 or quicker still, dial 01-636 9606,

ask for Carol Hill, she'll send you one today!



CATALOGUE PLEASE - BY RETURN OF POST

NAME \_\_\_\_\_

COMPANY \_\_\_\_\_

ADDRESS \_\_\_\_\_

3D

WW-040 FOR FURTHER DETAILS

# No.1 in Solder

**ENTHOVEN** offers you Europe's Widest Range

One good reason for soldering with Enthoven — whatever your needs — is the Enthoven range. It gives you a wide choice of high quality products developed for use with modern techniques. It includes Flux Cored Solder Wires, Solder Pre-forms, Solid Solders, selective Fluxes, solder specialities, materials for printed Circuitry and for soldering Aluminium. For complete technical details of Europe's widest range, ask Enthoven Solders Limited, Dominion Buildings, South Place,

London EC2. Telephone 01-628 8030; telex 21457; cables: ENTHOVEN LONDONEC2

**FLUX CORED SOLDER WIRES**



- 'SUPERSPEED' — Activated resin
- 'SUPERSPEED XX' — Doubly activated
- 'SUPERSPEED RED FLASH' — Coloured flux residue
- 'ENTHOVEN PURE RESIN' — Non-activated
- 'L.S.', 'A' & 'B' — Lamp manufacture
- 'ENCORE' — Non-electrical work
- 'CAPACICOR' — Capacitor manufacture
- 'ALUMINIUM' — Non-corrosive

Available in a wide selection of alloys, core sizes and conforming to British & U.S. Government specifications.

WW-041 FOR FURTHER DETAILS



8th INTERNATIONAL  
**INSTRUMENTS  
 ELECTRONICS  
 AUTOMATION**  
 EXHIBITION

Olympia London  
 11-16 May  
 1970

**PROBING THE  
 WORLD'S FUTURE**

You can see the picture of world progress at the International IEA at Olympia, London.

Not only today's picture.

The men who are reshaping progress show glimpses of future techniques which will set the course of the new global industrial revolution.

There are 950 of the world's most progressive electronic and automation companies at the IEA. More than a fifth of them are from abroad.

They bring progress into focus.

IEA is again expanded in area—one of the world's greatest technological events. America, Canada, Japan, Germany, Poland, France, Belgium, Czechoslovakia are among the countries helping to make it a truly international occasion.

**IEA SHOWS THE WAY  
 THE WORLD IS GOING**



Visitors to the IEA who complete the reverse side of the trade ticket, or who register at the show, will receive on entry a free copy of the IEA New and Special Products Guide.

Admission: by ticket available only from exhibitors or by payment of 5/- at entrances. (Season: 10/-).

Times: 10.00—18.00 hrs. daily.

An **IEA** Exhibition

**INDUSTRIAL EXHIBITIONS LIMITED**

9 Argyll Street, London, W1V 2HA

WW—045 FOR FURTHER DETAILS

**ORYX**

are  
**trumps!**

**MODEL SR1**  
 Instant solder remover  
 Ideal for printed circuit work  
 and integrated circuits.  
 79/6  
**MODEL SR2**  
 with non recoil  
 action  
 82/6

**MINIATURE  
 SOLDER POT**  
 60/-  
 For rapid  
 tinning of  
 small tags  
 and com-  
 ponents.

**MODEL ST-60**  
 90/-  
 'Hot' wire  
 stripper for  
 P.T.F.E.  
 insulation.  
 24 v operation.

**MODEL 6A**  
 27/6  
 The smallest  
 low voltage  
 soldering iron,  
 ideal for Printed  
 Circuit work.  
 6v, 6 watts.

**MODEL WG50**  
 59/6  
 Thermostatically  
 controlled  
 miniature  
 soldering iron. 50 watts.  
 5 bit sizes  $\frac{1}{16}$ " —  $\frac{1}{4}$ "  
 Available for 12v,  
 24v, 110v and  
 210/250v. operation


**MODEL M1**  
 35/-  
 A miniature  
 mains voltage  
 soldering iron  
 10 watts, 5 bit  
 sizes  $\frac{1}{16}$ " —  $\frac{1}{4}$ "  
 210/250v  
 operation

Full details of  
 these and other  
 instruments  
 from the Sole  
 U.K. and Export  
 distributors.

**W. GREENWOOD ELECTRONIC LTD.**

21, GERMAIN STREET, CHESHAM, BUCKS  
 TELEPHONE: CHESHAM 4808/9.

WW—046 FOR FURTHER DETAILS

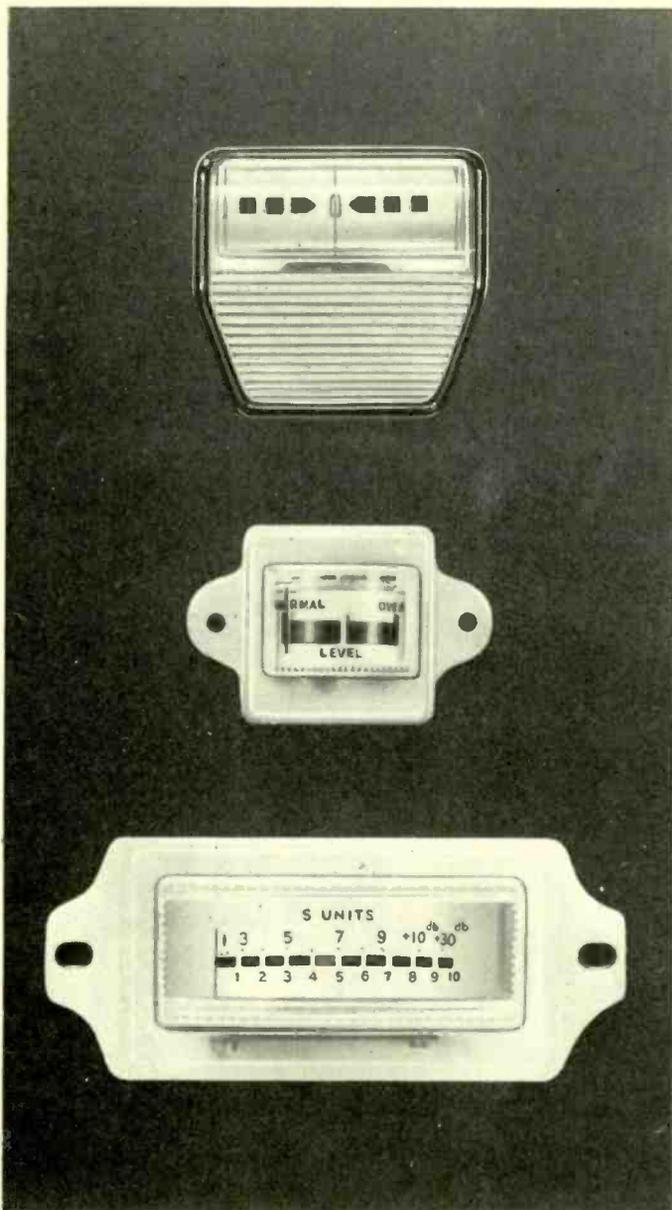

# LEVEL METERS...

For a wide range of applications in professional radio, recording, instrumentation, and domestic equipment. For further information contact, IMPECTRON LTD., 23-31, King Street, London, W.3, Telephone: 01-992 5388



WW-047 FOR FURTHER DETAILS



## DC TO AC TRANSVERTORS (transistorised Invertors/Convertors)



Type B12/250T  
PRICE £41-18-0


The "T" range of transvertors provide an AC output from static accumulators, mobile vehicles, boats, etc. These units are very economical for obtaining a stand-by AC supply or for operating equipment where no AC power supply is available. The 400/500 Hz output versions can and are frequently used as power tone generators for audio or visual fire alarms and other signalling systems in factories, ships, stores, schools, etc. A typical model B12/250T input 12V accumulator, output 115V and 230V 250W 50Hz. Other models for input voltages of 12 to 250V DC and outputs of square or sine wave. The standard range covers 50 or 60 Hz but frequencies of up to 10KHz are available to order. All units are fully transistorised. Send for full information and technical details.

### VALRADIO LTD.

Dept. WC6, BROWELLS LANE, FELTHAM, MIDDLESEX, ENGLAND  
Telephone: 01-890 4242 or 4837

WW-048 FOR FURTHER DETAILS

# FRAHM

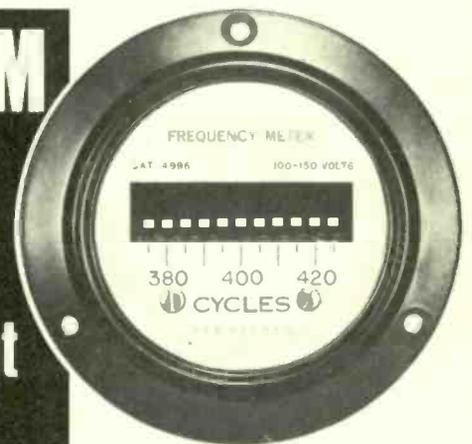

## resonant reed FREQUENCY METERS

used as standards in many industries

- Accurate to  $\pm 0.3\%$  or  $\pm 0.1\%$  as specified
- Not sensitive to voltage or temperature changes, within wide limits
- Unaffected by waveform errors, load, power factor or phase shift
- Operational on A.C., pulsating or interrupted D.C., and superimposed circuits
- Need only low input power
- Compact and self-contained
- Rugged and dependable

FRAHM Resonant Reed Frequency Meters are available in plastic and hermetically sealed cases to British and U.S. Government approved specification. Ranges 10-1700 Hz. Literature on these meters and Frahm Resonant Reed Tachometers available on request. Manufacture and Distribution of Electrical Measuring Instruments and Electronic Equipment. The largest stocks in the U.K. for off-the-shelf delivery.

### ANDERS ELECTRONICS LIMITED

Anders means meters

48/56 Bayham Place, Bayham Street, London NW1. Tel: 01-387 9092

WW-049 FOR FURTHER DETAILS



**Develop the art of good listening**


The best pick-up arm in the world. Write to SME Limited · Steyning · Sussex · England

**WW—050 FOR FURTHER DETAILS**

**SME**

# SSB
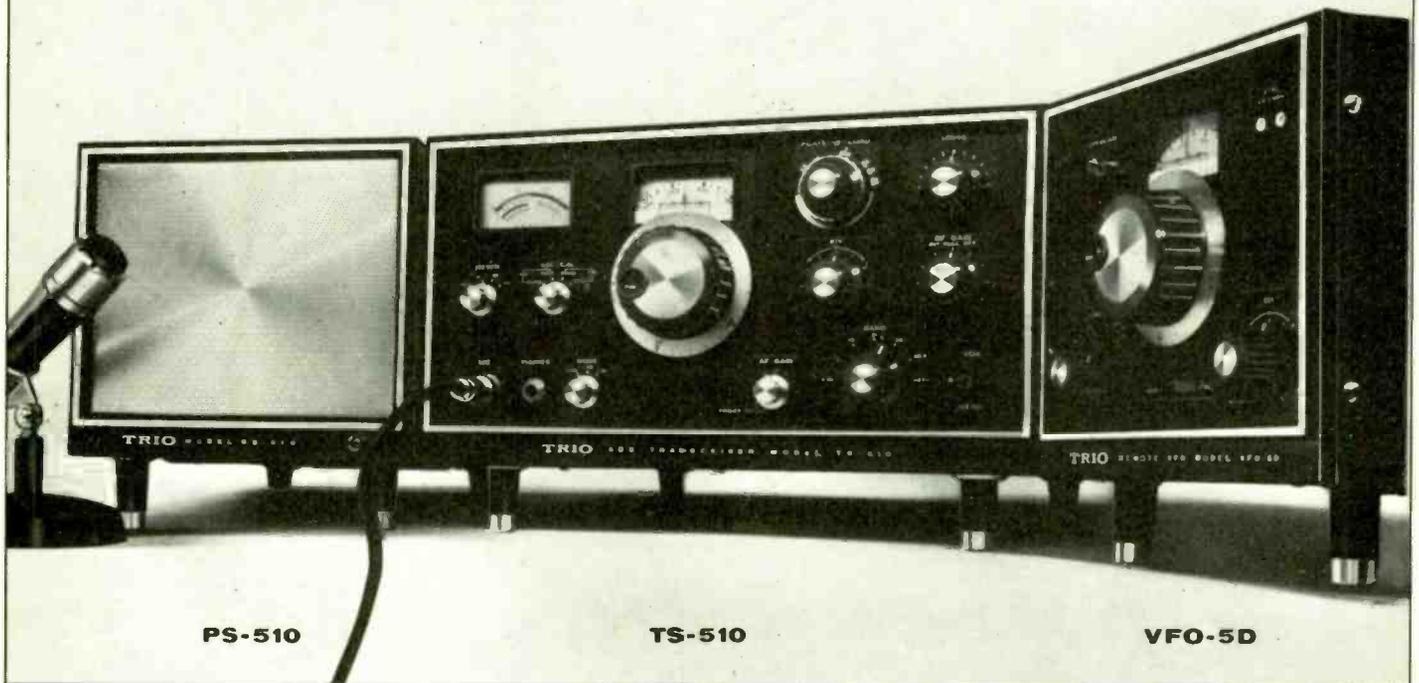
## FOR SUPERIOR SSB TRIO'S TS-510 TRANSCEIVER



**TRIO's TS-510** is the definitive instrument especially engineered for complete "SSB ERA" function. It's a high power, high stability product of imaginative design that fully lives up to the renowned "TRIO" name. Extremely stable VFO, a new development that is built around 2 FET's and 13 transistors, guarantees stable QSO's during entire use, an accurate double-gear tuning mechanism and a linear tuning capacitor produce a 1 kHz direct reading on all bands. There's easy tuning in of SSB signals because the TS-510's frequency coverage has been compressed to 25 kHz for one complete rotation of the dial. Sharp cutoff for both reception and transmission is achieved by a sharp factor frequency filter built just

for this 510 series model.

Combined with the TS-510's superb features are the distinctive, top quality **PS-510** (Power supply and speaker) and **VFO-5D** (Variable frequency oscillator). With an AC power supply that operates a built-in 16 cm speaker, the PS-510 has been created as an exclusive companion instrument for the TS-510. It can be installed at any location with the PS-510 because the power supply is regulated on or off at the TS-510.

The VFO-5D can match the TS-510 in performance and design. Its reading accuracy is unusually high since a double-gear dial covering 25 kHz per revolution is also used, as in the TS-510.



*the sound approach to quality*

**TRIO**

TRIO ELECTRONICS, INC.

TO: B.H. Morris & Co., (Radio) Ltd.

WW

Send me information on TRIO COMMUNICATION RECEIVERS & name of nearest TRIO retailer.

NAME:

AGE:

ADDRESS:

**TRIO-KENWOOD ELECTRONICS S.A.** 160 Ave., Brugmann, Bruxelles 6, Belgium


Sole Agent for the U.K. **B. H. MORRIS & CO., (RADIO) LTD.** 84/88, Nelson Street, Tower Hamlets, London E. 1. Phone: 01-790 4824

WW—051 FOR FURTHER DETAILS

www.americanradiohistory.com

# Before we sell you a Shure microphone we try to ruin it

## just to make sure that you never will

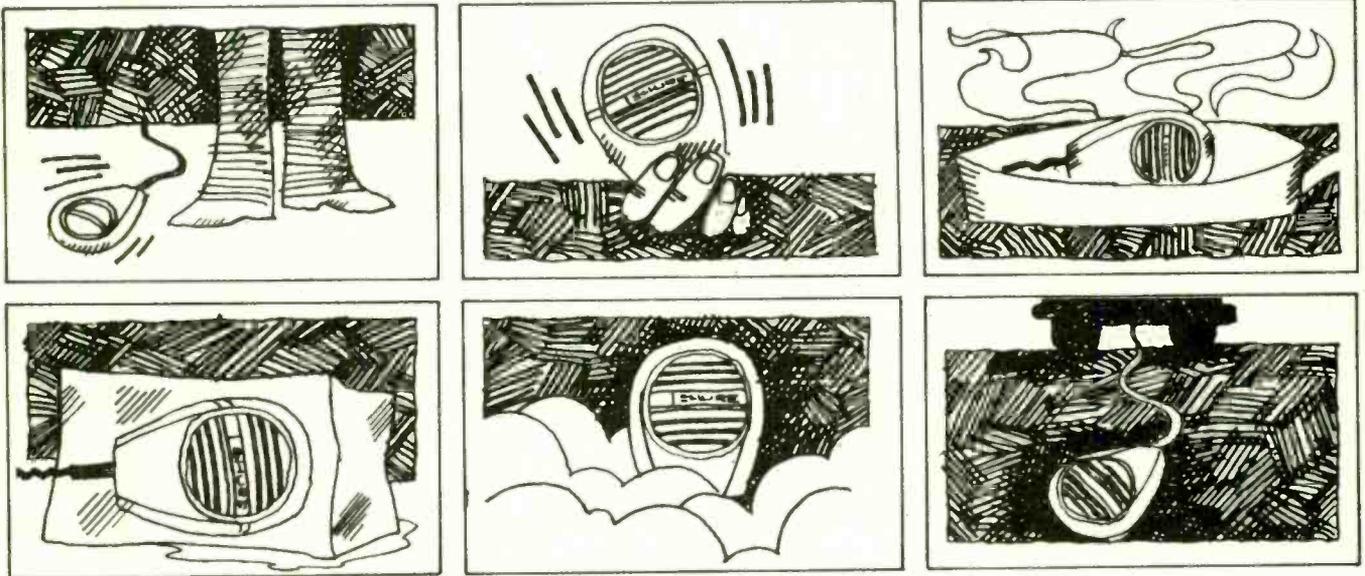

Microphones have to be rugged. Think of the punishment they take. That's why Shure Safety Communications Microphones get a tremendous going over before we dream of selling them.

**We drop them. We vibrate them.  
We fry them. We freeze them.  
We steam them in Turkish baths.  
We drag them behind fast moving cars.  
We subject them to all kinds of torture.  
Sand. Rain. Infra-red. Ultra-violet.  
Acids. Alcohol. Salt spray. Wind.  
Electrostatic fields. High altitude . . .  
and still they work**

This savage testing, backed by stringent quality control, ensures that every Shure communications microphone will give you reliable performance. And will go on doing so even under conditions where other microphones would pack up. Always use Shure, the microphones that never fail to get the message through.

### Communications

Controlled magnetic hand microphone providing a clear, crisp, highly intelligible voice response. Rugged and dependable, ideal for outdoor-indoor P.A., and communications. Frequency response 200 to 4,000 cps. High impedance. High output.

Model 414.



### Amateur Radio

Provides optimum radio communications performance from single sideband transmitters as well as AM and FM units. Response cuts off sharply below 300 cps and above 3,000 cps, ensuring maximum speech intelligibility and audio punch to cut through noise and interference.

Model 444.



For full details of Shure microphones, SEND IN THIS COUPON TODAY

To: Shure Electronics Ltd., 84 Blackfriars Road, London SE1. Tel: 01-928 3424

I'd like to know more about Shure Microphones for  
Communications  Professional Recording   
Amateur Radio  Professional Entertainers

Please send me the facts:

NAME .....

ADDRESS .....



setting the world's standard in sound

WW4

# You're on the right track- with Goldring 800 magnetic cartridges


**SONEX 70**  
SKYWAY HOTEL  
24th-26th APRIL

Goldring 800 magnetic cartridges track unerringly. Because that's the way we make them. They're designed to translate even the most delicate information stored in the groove back into an identical electrical signal. We call it the sound of true transduction.

Hear it for yourself. You'll know you're on the right track.

**Goldring 800/H**... the 800/H is designed for inexpensive changers to track between  $2\frac{1}{2}$ — $3\frac{1}{2}$  grams and has a high output of at least 8mV. £10.13.6 tax paid.

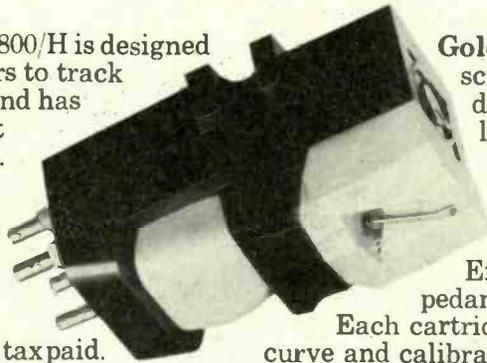**Goldring 800**  
... the 800 is designed for standard arms and changers where the requirements of high fidelity and robustness usually conflict. £13.0.0 tax paid.



**Goldring 800 E**... is designed for transcription arms and a micro-elliptical diamond is fitted to a finer cantilever, end damped against natural tube resonance £18.17.1 tax paid.

**Goldring 800 Super E**... the 800 Super E is for those to whom perfection is barely good enough. Extraordinarily low mechanical impedance for superb tracking capabilities. Each cartridge is supplied with its individual curve and calibration certificate. £26.0.0 tax paid.



Send for details and complete range of Goldring Hi-Fi equipment


**Goldring Manufacturing Co. (Great Britain) Ltd.**

486-488 High Road, Leytonstone, London, E.11. Tel: C1-539 8343.

WW—053 FOR FURTHER DETAILS

## LEKTROKIT

rack and  
chassis  
systems by

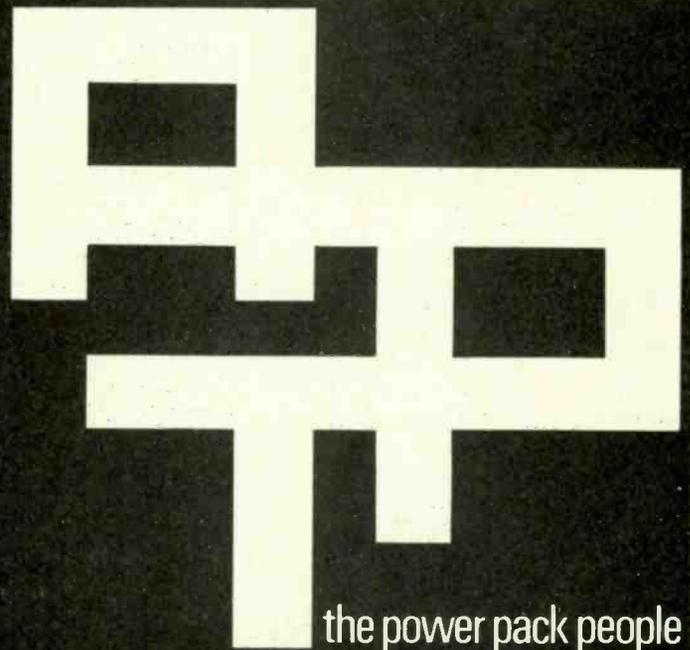

the power pack people

LEKTROKIT Rack and Chassis systems consist of a number of small, inexpensive, pre-fabricated components from which experimental racks, chassis, trolleys, etc., can be constructed and added to, instantly and cheaply. Designed to house standard commercial and inter-service electronic components, including I.C.'s, LEKTROKIT is ideal for pre-production models, factory test equipment and, with the addition of front panels and covers from the standard range, can be transformed to a permanent and elegant piece of equipment.


For further details of LEKTROKIT RACK AND CHASSIS systems send for fully descriptive literature and price list.

**A.P.T. ELECTRONIC INDUSTRIES LTD**

Chertsey Road, Byfleet, Surrey Tel: Byfleet 41131-2-3-4 Grams. APTRAN, BYFLEET

WW—054 FOR FURTHER DETAILS

www.americanradiohistory.com

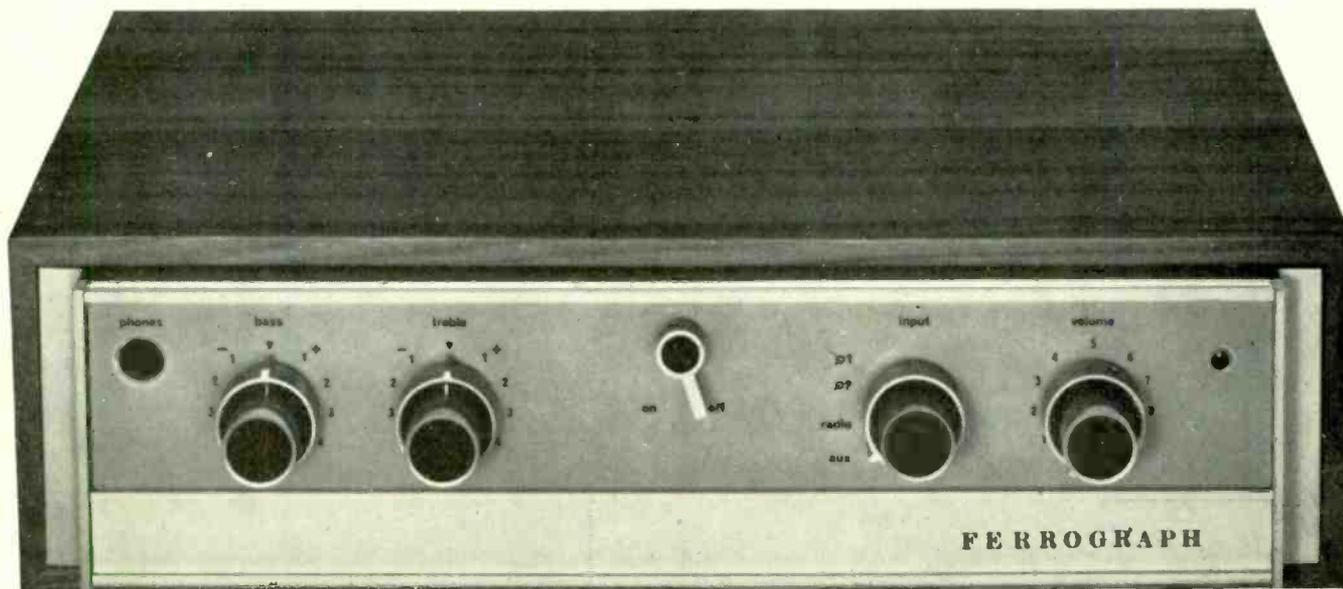

# Ferrograph F307 stereo amplifier— the heart of great Hi-Fi

F307 is an integrated Stereo Amplifier, built in a tradition of excellence and extremely versatile in its capabilities.

It presents a clean uncluttered appearance, conforming very closely with the Series Seven Recorder in this regard. Only its main controls appear on the panel—all subsidiary controls being housed beneath a hinged extruded aluminium flap.

F307 delivers power output of 20 watts RMS per channel into a load of 8 ohms and has a total harmonic distortion of less than 0.25% at 1kHz at all levels up to its rated output.

Your Ferrograph dealer will be pleased to demonstrate F307 to you. When planning your Hi-Fi system, this is an Amplifier to which the most serious consideration must be given and its Manual makes informative and compelling reading.

## FERROGRAPH

The Ferrograph Co. Ltd.  
Mercury House, 195 Knightsbridge, London, S.W.7.  
Telephone: 01-589 4485

To The Ferrograph Co. Ltd.  
Mercury House, 195 Knightsbridge, London, S.W.7.  
Please send me FREE details of the Ferrograph Stereo Amplifier F307   
OR send me the F307 Manual for which I enclose 5s 6d post paid

Name.....  
Address.....

ww

WW—C55 FOR FURTHER DETAILS

SOLE U.K. DISTRIBUTORS OF

# SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.

● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

## NEW "SEW" DESIGNS!

CLEAR PLASTIC METERS

BAKELITE PANEL METERS



**TYPE SW. 100**  
100 x 80 mm.

50µA	69/8
100µA	67/8
500µA	62/8
1mA	59/8
20V. D.C.	59/8

50V. D.C.	59/8
1 amp. D.C.	59/8
5 amp. D.C.	59/8
300V. A.C.	59/8



**TYPE S-80**  
80 mm. square fronts

50µA	62/8
100µA	59/8
500µA	52/8
1mA	49/8
20V. D.C.	49/8

50V. D.C.	49/8
1 amp. D.C.	49/8
5 amp. D.C.	49/8
300V. A.C.	52/8

### "SEW" CLEAR PLASTIC METERS

Type MR.85P. 4 1/2 in. x 4 1/2 in. fronts.



10mA	52/-
50mA	52/-
100mA	52/-
500µA	52/-
1 amp.	52/-
5 amp.	52/-
15 amp.	52/-
30 amp.	52/-
20V. D.C.	52/-
50V. D.C.	52/-
150V. D.C.	52/-
300V. D.C.	52/-
15V. A.C.	52/-
300V. A.C.	52/-
8 Meter 1mA	57/8
VU meter	72/-
1 amp. A.C.*	52/-
5 amp. A.C.*	52/-
10 amp. A.C.*	52/-
20 amp. A.C.*	52/-
5mA	52/-
50mA	52/-

Type MR.38P. 1 21/32 in. square fronts.



150mA	27/8
200mA	27/8
300mA	27/8
500µA	27/8
750µA	27/8
1 amp.	27/8
2 amp.	27/8
5 amp.	27/8
10 amp.	27/8
3V. D.C.	27/8
10V. D.C.	27/8
20V. D.C.	27/8
100V. D.C.	27/8
150V. D.C.	27/8
300V. D.C.	27/8
500V. D.C.	27/8
750V. D.C.	27/8
15V. A.C.	27/8
50V. A.C.	27/8
150V. A.C.	27/8
300V. A.C.	27/8
500V. D.C.	27/8
750V. D.C.	27/8
15V. A.C.	27/8
50V. A.C.	27/8
150V. A.C.	27/8
300V. A.C.	27/8
600V. A.C.	27/8
8 meter 1mA	32/-
VU meter	42/-

Type MR.52P. 2 1/2 in. square fronts.

50µA	62/-
50-0-50µA	52/-
100µA	52/-
100-0-100µA	47/8
500µA	45/-
1mA	40/-
5mA	40/-
10mA	40/-
50mA	40/-
100mA	40/-
500mA	40/-
1 amp.	40/-
5 amp.	40/-

10V. D.C.	40/-
20V. D.C.	40/-
50V. D.C.	40/-
300V. D.C.	40/-
15V. A.C.	40/-
300V. A.C.	40/-
8 Meter 1mA	42/-
VU meter	62/-
1 amp. A.C.*	40/-
5 amp. A.C.*	40/-
10 amp. A.C.*	40/-
20 amp. A.C.*	40/-
30 amp. A.C.*	40/-

Type MR.45P. 2 in. square fronts.

50µA	45/-
50-0-50µA	42/-
100µA	42/-
100-0-100µA	37/8
200µA	37/8
500µA	32/-
500-0-500µA	30/-
1mA	30/-
5mA	30/-
10mA	30/-
50mA	30/-
100mA	30/-
5 amp.	30/-
10V. D.C.	30/-
20V. D.C.	30/-
50V. D.C.	30/-
20V. D.C.	30/-
50V. D.C.	30/-
15V. A.C.	30/-
300V. A.C.	30/-
8 meter 1mA	37/8
VU meter	45/-
1 amp. A.C.*	30/-
5 amp. A.C.*	30/-
10 amp. A.C.*	30/-
20 amp. A.C.*	30/-
30 amp. A.C.*	30/-

Type MR.65P. 3 1/2 in. x 3 1/2 in. fronts.

50µA	67/8
50-0-50µA	55/-
100µA	55/-
100-0-100µA	52/-
500µA	47/8
500-0-500µA	42/-
1mA	42/-
5mA	42/-
10mA	42/-
50mA	42/-
100mA	42/-
500mA	42/-
1 amp.	42/-
5 amp.	42/-
10 amp.	42/-
15 amp.	42/-
20 amp.	42/-
30 amp.	42/-
50 amp.	47/8
10V. D.C.	42/-

20V. D.C.	42/-
50V. D.C.	42/-
300V. D.C.	42/-
15V. A.C.	42/-
50V. A.C.	42/-
150V. A.C.	42/-
300V. A.C.	42/-
500V. A.C.	42/-
8 meter 1mA	47/8
VU meter	67/8
50mA A.C.*	42/-
100mA A.C.*	42/-
200mA A.C.*	42/-
500mA A.C.*	42/-
1 amp. A.C.*	42/-
5 amp. A.C.*	42/-
10 amp. A.C.*	42/-
20 amp. A.C.*	42/-
30 amp. A.C.*	42/-

### "SEW" BAKELITE PANEL METERS

Type MR.65. 3 1/2 in. square fronts.



25µA	70/-
50µA	47/8
50-0-50µA	45/-
100µA	45/-
100-0-100µA	45/-
500µA	42/-
1mA	35/-
1-0-1mA	35/-
5mA	35/-
10mA	35/-
50mA	35/-
100mA	35/-
500mA	35/-
1 amp.	30/-
5 amp.	35/-
10 amp.	35/-
30 amp.	35/-
50 amp.	35/-
5V. D.C.	35/-
10V. D.C.	35/-
20V. D.C.	35/-
50V. D.C.	35/-
150V. D.C.	35/-
300V. D.C.	35/-
30V. A.C.	35/-
50V. A.C.	35/-
150V. A.C.	35/-
300V. A.C.	35/-
500mA A.C.*	35/-
1 amp. A.C.*	35/-
5 amp. A.C.*	35/-
10 amp. A.C.*	35/-
20 amp. A.C.*	35/-
30 amp. A.C.*	35/-
VU meter	62/-

\*MOVING IRON - ALL OTHERS MOVING COIL Please add postage



### EDGWISE METERS

Type PE.70. 3 17/32 in. x 1 15/32 in. x 2 1/2 in. deep.

50µA	80/-
50-0-50µA	57/8
100µA	57/8
100-0-100µA	55/-
200µA	55/-
500µA	52/-
1mA	47/8
300V. A.C.	47/8
VU meter	85/-


SEND FOR ILLUSTRATED BROCHURE ON SEW PANEL METERS—DISCOUNTS FOR QUANTITIES

U.K. DISTRIBUTORS OF

# TMK MULTIMETERS

This range of Multimeters, manufactured by Tachikawa Radio Instrument Co. of Japan, offers excellent value for money combined with quality and accuracy of measurement.

● IMMEDIATE DELIVERY ● DISCOUNTS FOR QUANTITIES ● TRADE ENQUIRIES INVITED

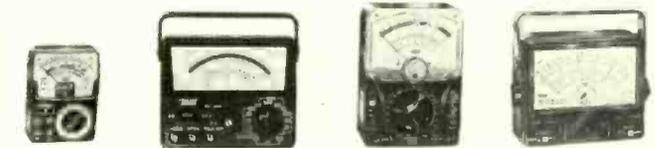

MD. 120

PL. 436

500

5025

★ All models fitted overload protection and supplied with batteries, prods and instructions.

LAB TESTER

TW. 50k

MODEL MD-120 Features Mirror Scale, Low Loss Switch and Robust Movement. Sensitivity: 20kΩ/Volt D.C. 10kΩ/Volt A.C. D.C. Volts: 30, 60, 300, 600, 3,000V. A.C. Volts: 6, 120, 1,200V. D.C. Current: 60µA, 12, 300mA. Resistance: 60k, 6 MEGΩ. Decibels: -20 to +63db. Rugged High Impact Plastic Case, size 3 1/2 in. x 4 1/2 in. x 1 in. **£4. 12. 6** p/p 2/6

MODEL PL 436 Features Mirror Scale and Wood Grain Finish Front Panel. Sensitivity: 20kΩ/Volt D.C. 8kΩ/Volt A.C. D.C. Volts: 6, 3, 12, 30, 120, 600V. A.C. Volts: 3, 30, 120, 600. D.C. Current: 50, 600µA, 60, 600mA. Resistance: 10k, 100k, 1MEGΩ, 10MEGΩ. Decibels: -20 to +45db. Rugged High Impact Plastic Case with Handle, size 6 1/2 in. x 4 1/2 in. x 2 1/2 in. **£6. 19. 6** p/p 2/6

MODEL TW-50K Features 48 ranges, mirror scale, Sensitivity 50kΩ/Volt D.C. 5kΩ/Volt A.C. D.C. Volts: 125, 25, 125, 2.5, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.C. Volts: 2.5, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.C. Current: 25, 50µA, 2.5, 5, 25, 50, 250, 500mA, 5, 10 amp. Resistance 10k, 100k, 1 MEGΩ, 10 MEGΩ. Decibels: -20 to +81.5dB. Plastic case with carrying handle. Size 4 1/2 in. x 2 1/2 in. x 6 in. **£8. 10. 0** p/p 3/6

MODEL 500 Features Mirror Scale and Buzzer Short Circuit Check. Sensitivity: 30kΩ/Volt D.C. 15kΩ/Volt A.C. D.C. Volts: 25, 1, 2.5, 10, 25, 100, 250, 500, 1,000V. A.C. Volts: 2.5, 5, 10, 25, 50, 100, 250, 500, 1,000V. D.C. Current: 5, 50, 500mA, 12 amp. Resistance: 60k, 6MEGΩ, 60MEGΩ. Decibels: -20 to +55db. Handsome Dustproof Black Plastic Case, size 3 5/16 in. x 6 1/16 in. x 2 1/4 in. **£8. 17. 6** p/p 2/6

MODEL 5025 Features 57 Ranges. Giant 5 1/2 in. Meter. Polarity Reverse Switch. Sensitivity: 60kΩ/Volt D.C. 5kΩ/Volt A.C. D.C. Volts: 125, 25, 1.25, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.C. Volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.C. Current: 25, 50µA, 2.5, 5, 25, 50, 250, 500mA, 5, 10amp. Resistance: 2k, 10k, 100k, 1MEGΩ, 10MEGΩ. Decibels: -20 to +85db. Plastic Case with Carrying Handle, size 6 1/2 in. x 2 1/2 in. x 5 1/2 in. **£12. 10. 0** p/p 3/6

MODEL 100,000 O.P.V. LAB TESTER Features Unique Range Selector, 5 1/2 in. Scale Buzzer Short Circuit Check. Sensitivity: 100,000 OPV D.C. 5kΩ/Volt A.C. D.C. Volts: 5, 2.5, 10, 50, 250, 1,000V. A.C. Volts: 3, 10, 50, 250, 500, 1,000V. D.C. Current: 10, 100µA, 10, 100, 500mA, 2.5, 10 amp. Resistance: 1k, 10k, 100k, 10MEGΩ, 100MEGΩ. Decibels: -10 to +49db. Plastic Case with Carrying Handle, size 7 1/2 in. x 6 1/2 in. x 3 1/2 in. **£18. 18. 0** p/p 5/-

SOLE U.K. AGENTS FOR JAPAN'S PREMIER MANUFACTURER

## "YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

● Excellent quality ● Low price ● Immediate delivery



ALL MODELS


INPUT 230 VOLTS, 50/60 CYCLES. OUTPUT VARIABLE 0-260 VOLTS

MODEL S-260

General Purpose

Bench Mounting

1 Amp	£5.10	MODEL S-260 B	
2.5 Amp	£6.15.0	Panel Mounting	
5 Amp	£9.15.0	1 Amp	£5.10.0
8 Amp	£14.10.0	2.5 Amp	£6.12.6
10 Amp	£18.10.0	Please add postage.	
12 Amp	£21.0.0	Special discounts for quality	
20 Amp	£37.0.0		

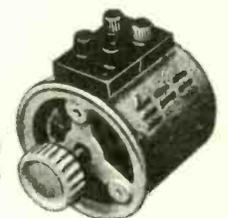

# BARNET FACTORS LTD

147 CHURCH STREET, LONDON, W.2

Telephone: 01-723 5328

# audix


## “Studio 80” amplifier



The “Studio 80” Power Amplifier has been produced to high performance standards for Studio and Laboratory applications.

Its proven characteristics puts it in a class beyond anything yet available in power, performance, and price, and is the ultimate in economic functional engineering design – Write for full details of guaranteed performance specification.

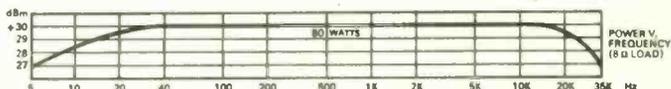- POWER OUTPUT:** Max 80W into 8 ohm.
- POWER BANDWIDTH:** 5 Hz to 35 KHz at 80 W.
- FREQUENCY RESPONSE:** + 0 dB 20 Hz to 20 KHz.  
- .5 dB
- TOTAL DISTORTION:** Less than 0.05 at 1 KHz.
- SIGNAL TO NOISE RATIO:** Better than -95 dB below maximum output.
- POWER SUPPLY:** 100/120-200/250 A/C 50-60 Hz.




# audix SOUND SYSTEMS

AUDIX B.B. LIMITED  
STANSTED · ESSEX  
Tel: STANSTED 3132/3437  
(STD 027-971)

WW-057 FOR FURTHER DETAILS

# Now you can get a fully equipped CCTV studio from GVS for as little as £3,000

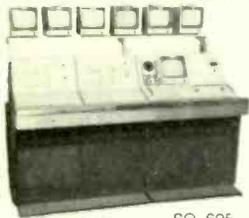

SO 605  
Studio Control Console



SV 800 EC 1" Video  
Taperecorder with  
built in 9" monitor



EA 101 Mixer and effects generator



FP100 Studio Camera  
with 5" viewfinder



SV 707 Battery powered  
portable 625-Line Camera and  
Video Taperecorder



HV 15.S Compact  
Camera

No matter what your CCTV requirements are, General Video Systems have the answer—with their wonderful range of SHIBADEN equipment. The result of extensive Research and Development, SHIBADEN equipment has been designed to a modular concept which means that you can fit and furnish your own CCTV studio for as little as £3,000.

The widespread need for this type of package deal within industry, commerce and education fields are numerous. And each individual requirement can be met from the simplest operation to a full broadcast studio.

If you are about to invest in CCTV equipment or would like to discuss your requirements, let GVS "put you in the picture"




Contact Norman Simpson today at:

**GENERAL VIDEO SYSTEMS LTD.**  
Main Distributors of SHIBADEN Equipment  
61-63 Watford Way, Hendon, London NW4,  
Telephone: 01-202 8056

WW—058 FOR FURTHER DETAILS
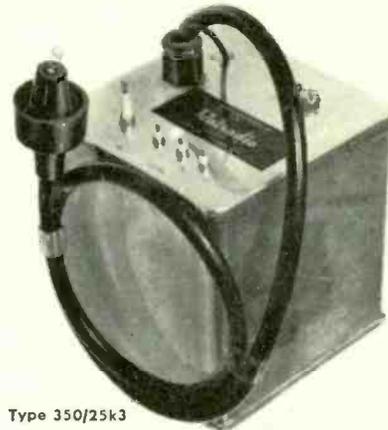
## Valradio 25kv Transformer/Rectifier Unit



Type 350/25k3

A compact oil filled ringing transformer/rectifier unit, supplying 25Kv. at up to 350 micro amps, suitable for dust extractors, air purifiers, paint spraying or any application requiring a smoothed well regulated 25Kv. supply.

The transformer needs an HT supply of 350v. and a drive of 1000 Hz. pulsed. This unit is an electrical equivalent to the Mullard type 10840 used in many projection T/V receivers.

We shall be happy to quote you for other output voltages.

Size 4 in. (102 m/m) x 4 in. (102 m/m) x 4 1/2 in. (114 m/m).

Send for details and circuits.

Recommended retail price £12 subject. Competitive price for quantities.

**VALRADIO LTD.**

Dept. WHT1, BROWELL'S LANE, FELTHAM, MIDDLESEX, ENGLAND

Telephone: 01-890 4242

WW—059 FOR FURTHER DETAILS

## Nombrex accuracy!



*in the palm of your hand*

TRANSISTORISED—COMPACT—MODERN STYLING

Standard Model 29-S

- 150KHz-220 MHz on fundamentals
- Eight clear scales. Total length 40"
- Smooth vernier tuning—ratio 7 1/2 : 1
- Magnifier cursor—precision tuning
- Overall accuracy, better than 1.5%
- Modulation, variable depth and frequency

Price £20-0-0

Xtal Check Model 29-X

- All the features of the Model 29-S AND
- Integral Crystal Oscillator providing calibration check points throughout all ranges. For adjustment of scale accuracy to ± 0.02%

Price £27-10-0

Illustrated: R. F. SIGNAL GENERATOR MODEL 29, Spin Wheel Tuning £1-0-0 extra



**NOMBREX (1969) LTD. EXMOUTH DEVON**  
Tel. 03-952 3515

Trade & Export enquiries welcome. Send for full technical leaflets. Post and Packing 6/6 extra

WW—060 FOR FURTHER DETAILS

# 'With a Weircliffe Bulk Eraser you can clean a tape whistle-clean without even taking it from the can'

## 'Now he tells me'

Let's come clean. Weircliffe Bulk Erasers are, quite simply, the best you can buy.


Magnetic tape/film - up to a maximum of 16" diameter x 35 mm width or 14 1/2" x 2" - can be instantaneously erased. Which means you can handle up to 250 tapes in an hour. And you can, we promise you, even clean a tape while it's still in its can.

What's more, nobody has yet produced a tape or recorded a signal - whether it's data, audio, pulsed or video - that can't be clearly erased to between 80dB and 90dB below saturation recording level. Weircliffe Bulk Erasers have a greater erase factor than any other known make.

Weircliffe Bulk Erasers have been tested and tested by tape manufacturers and technical institutes throughout the world. They're used by broadcasting authorities from Australia to Finland. They're approved and supplied by the major manufacturers of data recording equipment.

They're that good.

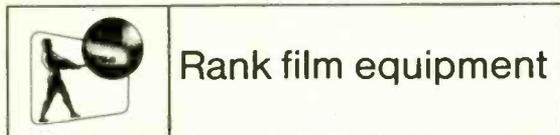For more information, fill in coupon or 'phone Ken Chapman 01-568 922 Ext. 366.



Rank film equipment

Rank Film Equipment, Rank Audio Visual,  
P.O. Box 70, Great West Road, Brentford, Middx.  
Phone 01-568 9222. Cables: Rankaudio London Telex: 24408

Please send me more information  Please arrange a demonstration

Name \_\_\_\_\_ Position \_\_\_\_\_

Company/Address \_\_\_\_\_

\_\_\_\_\_

Date \_\_\_\_\_ Telephone \_\_\_\_\_

WW-061 FOR FURTHER DETAILS

**Point to Point  
Broadcasting  
Radio Relay  
Ground to Air  
Navigational Aids  
Business Radio**

#### **Design**

Site layouts  
Aerial System Design

#### **Aerials**

LF 'T' and 'L' Aerials,  
Mast Radiators,  
HF Dipoles, Quadrants,  
Rhombics, Log Periodics,  
Vertical Incidence Arrays,  
Conicals, Biconicals  
VHF & UHF Yagis, Helices,  
Ground Planes, Colinears,  
Whips, Marine Aerials,  
Television Arrays to 100kW e.r.p  
**MICROWAVE** Passive Reflectors,  
Dishes 3" to 60 ft. dia.

#### **Supporting Structures**

Self-supporting Towers,  
Tubular and Lattice Masts,  
Telescopic Masts


#### **Accessories**

Coaxial and open wire Feeders,  
Filters, Aerial Switches,  
Lead-in panels, Earth Systems.  
Air-cooled Transmitter Loads.  
Termination Networks
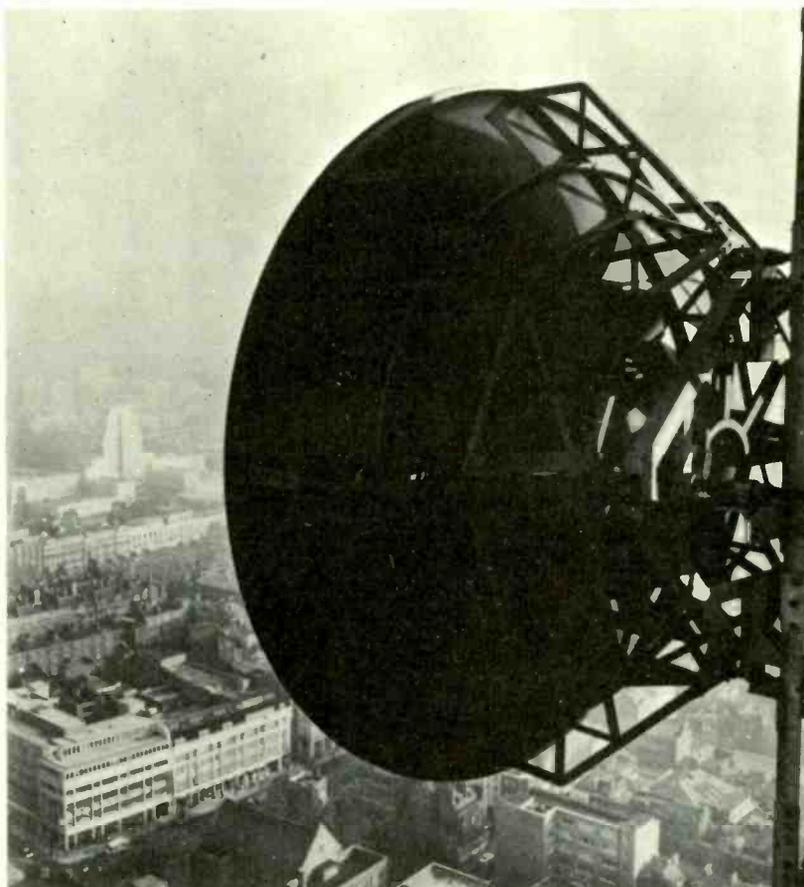
#### **Installation**

World Wide Service

**C&S Antennas**  
provide  
a complete  
aerial service  
**LF to Microwave**



**C&S Antennas Ltd**

Wentworth House, Eastern Avenue, Ilford, Essex, England.  
Telephone: 01-554-0102 Telex: 25850 Cables: Antennas Ilford (England)

WW—062 FOR FURTHER DETAILS

CS16A

# IF YOU HAVE A HOME RADIO CATALOGUE

Ordering components is easier and quicker with our new

## Credit Account Service




Just a phone call away

Our aim in life at Home Radio Components Ltd. is to make *your* life happier and less complicated! To this end we have recently introduced a **Credit Account Service**, one advantage of which is that you can order components by telephone *any time, any day*. If you phone out of shop hours a recording machine will take your message for us to deal with as soon as we open shop next day.

There are *other* advantages to the new Service—if you want to order by post we provide Order Forms and *Prepaid* Envelopes. You settle your account just once per month. We stipulate *no* minimum order value. Of course for ordering your components you first need our Catalogue, and after you have been in the Service 12 months we regularly send you an up-to-date catalogue—FREE!

For full details of our Credit Account Service just drop us a line or phone 01-648 8422.

# IF YOU HAVEN'T...

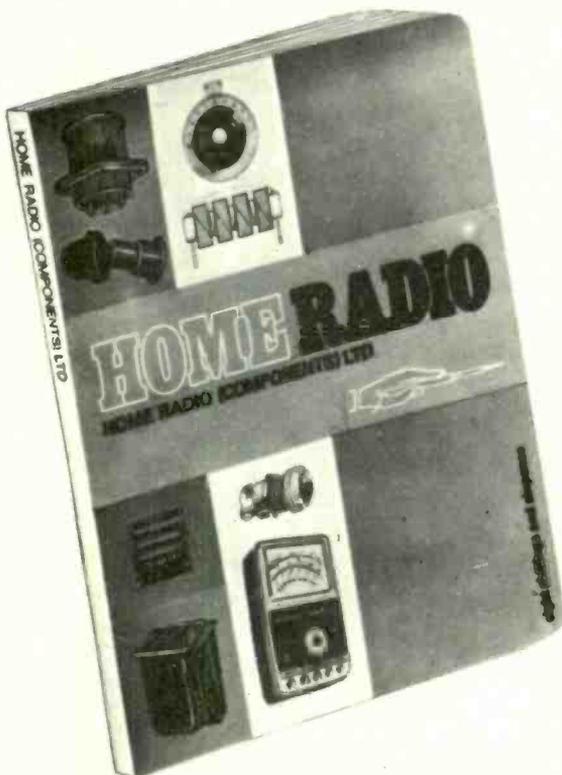

Whether or not you want to use the Credit Account Service described above, you certainly need the **Home Radio Components Catalogue** if you construct or repair radio and electronic gadgets. The catalogue has 350 pages, lists 8,000 components and has over 1,500 illustrations. It contains six vouchers, each worth 1/- when used as indicated. *Post the coupon with 12/- (8/6 plus 3/6 postage and packing)* and we will send a catalogue by return of post. By the way, we supply *free* a 30-page Price Supplement and a Bookmark giving electronic abbreviations.

Write Name and Address in block capitals

Name .....

Address .....

.....

.....

**HOME RADIO (Components) LTD.,** Dept WW,  
234-240 London Road, Mitcham, Surrey CR4 3HD

WW—063 FOR FURTHER DETAILS

# see you at SONEX '70

**Come and hear Hi-Fi of the Seventies.  
See what the new decade promises  
the Hi-Fi enthusiast and music lover**

SONEX is an important new series of annual Hi-Fi exhibitions. The best in Hi-Fi, the newest equipment, future trends in sound, sound demonstration, ideas for Hi-Fi in the home - a wealth of exhibits awaits the enthusiast.

Rooms with a view to listening. Special care has been taken in planning demonstration rooms. They help you evaluate equipment accurately. The hotel rooms are built much like your own at home and are a first class testing site for the equipment you will hear. Spatially and acoustically the setting is just right for the enthusiast and the music lover.

SONEX will be the highlight of your Hi-Fi year. Be sure to get your free ticket for the first of these great sound events from your Hi-Fi dealer.

**April 24th-26th, 1970**




Organised by British Audio Promotions Ltd.  
for the Federation of British Audio  
Fri & Sat: 11 am-9 pm.  
Sun: 11 am-6 pm.

**SKYWAY HOTEL**  
Bath Rd., Hayes, Middx.  
(free car park)


Luxury coaches from Hounslow West tube station. Skyway bus between airport and hotel.

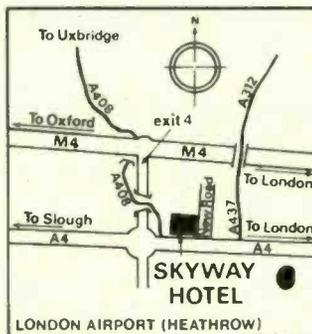**SONEX '70**  
Hear the Hi-Fi of the 70's



WW-064 FOR FURTHER DETAILS

## 'TRI-BOARD'

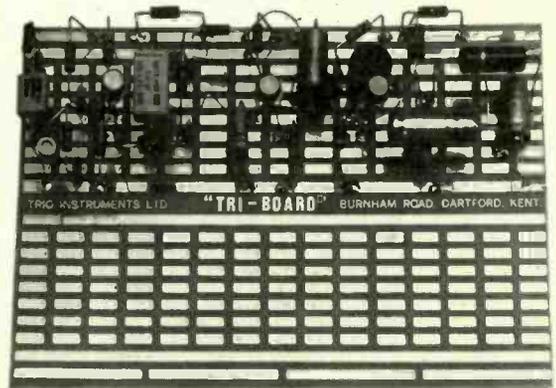

The ideal "Breadboard" material for rapid construction of electronic circuits at the design and prototype stages of development programmes.

TRI-BOARD is supplied in Fibreglass which is suitable for cold punching or cutting. Board size is  $7\frac{1}{2} \times 5\frac{3}{8} \times \frac{1}{16}$  thick with 1 oz. copper. A roller tinned finish is standard.

**PRICE** 15/- net per board.  
Quantity discounts apply:

TRIO INSTRUMENTS LTD.,  
BURNHAM ROAD,  
DARTFORD, KENT. Telephone: Farningham 2082

WW-065 FOR FURTHER DETAILS

## M. R. SUPPLIES (London) LTD., (Established 1935)

Universally recognised as suppliers of UP-TO-DATE MATERIAL, which does the job properly. Instant delivery. Satisfaction assured. Prices nett.

**ROOM THERMOSTATS.** Danfoss wall-mounted Thermostats. 40 d.g. F.-80 deg. F., 380 v. A.C., 4 amps.; 240 v. A.C., 6 amps. Our nett price **£1/12/6** (des. 2/-).

**MINIATURE RUNNING TIME METERS** (Sangamo). We have great demands for this remarkable unit and now can supply immediately from stock. 200/250 v. 50 c. synchronous. Counting up to 9,999 hours, with 1/10th indicator. Only  $1\frac{1}{2}$  ins. square, with cyclometer dial, depth 2 ins. Many industrial and domestic applications to indicate the running time of any electrical apparatus, easy to install, **63/-** (des. 1/6).

**SYNCHRONOUS TIME SWITCHES.** (Another one of our popular specialities) 200/240 v. 50 c., for accurate pre-set switching operations. Sangamo S.254, providing up to 3 on-off operations per 24 hours at any chosen times, with day-omitting device (use optional). Capacity 20-amps. Compactly housed 4 in. dia.,  $3\frac{1}{2}$  in. deep. **£8/4/6** (des. 4/6).

**ELECTRIC FANS** (Papst), for extracting or blowing. The most exceptional offer we have yet made. 200/250 v. A.C. Induction motor—silent running. 2,800 r.p.m. duty 100 C.F.M. Only 4 1/2 in. square and 2 in. deep. Ideal for domestic or industrial use. Easy mounting, **£3/5/-** (des. 3/6).

**SMALL GEARED MOTORS.** In addition to our well-known range (List G.M.169), we offer small open type S.P. Units 200/250 v. A.C., 1, 6, 12, 24, 60 r.p.m., approx. 5 in. long, with 1 in. shaft projection each side and enclosed gearbox. Suitable for display work and many industrial uses. Only **75/-** (des. 5/-).

**MINIATURE COOLING FANS.** 200/250 v. A.C. With open type induction motor (no interference). Overall 4 in. x 3 1/2 in. x 2 1/2 in. Fitted 6-bladed metal impeller. Ideal for projection lamp cooling, light duty extractors, etc., still only **£1/8** (des. 5/-).

**AIR BLOWERS.** Highly efficient units fitted induction totally enclosed motor 230/250 v. 50 c. 1 ph. Model SD.26, 60 CFM (free air) to 11.5 CFM (at 15 WG (size approx.)) 6 x 6 x 7 in. Outlet 2 1/2 in. square. **£8/10/-** (des. 5/-). Model SD27, 120 CFM (free air) to 40 CFM at 1.2 WG, 8 x 7 x 9 in. outlet 3 1/2 in. sq., **£11/15/6** (des. 5/-). Model SD28, 260 CFM (free air) to 127 CFM at 1.5 WG, 11 x 8 x 9 in., outlet 3 in. sq., **£13/17/6** (des. U.K. 7/6).

**SYNCHRONOUS ELECTRIC CLOCK MOVEMENTS** (as mentioned and recommended in many national journals). 200/250 v. 50 c. Self-starting. Fitted spindles for hours, minutes and central sweep second hands. Central one-hole fixing. Dia. 2 1/2 in. Depth behind dial only 1 in. With back dust cover, **39/6** (des. 2/-). Set of three brass hands in good plain style. For 5/7 in. dia. 2/6 For 5/10 dia. 3/6 set.

**SYNCHRONOUS TIMER MOTORS** (Sangamo). 200/250 v. 50 c/s. Self-starting 2 in. dia. x 1 1/2 in. deep. Choice of following speeds: 1 r.p.m., 12 r.p.m., 1 r.p.h., 1 rev. 12 hours, 1 rev. per day. Any one **42/-** (des. 2/-). Also high-torque model (G.R.C.). 2 1/2 in. x 2 in. x 1 1/2 in. 6 r.p.m., **57/6** (des. 2/-).

**SMITHS TIMER MOTORS.** Synchronous, self-starting 200/250 volts, 1 ph., 50 c. Clockwise. 4 r.p.m. only. Only **25/-** (des. 2/-).

**MINIATURE D.C. MOTORS.** 6/12 volts D.C. Ideal model makers. 4,000/9,000 r.p.m. no load. 1 1/2 in. x 1 1/2 in. diameter. Flange fixing. Only **5/-** (des. 1/6).

**EXTRACTOR FANS.** Ring mounted all metal construction. T/E induction motor, silent operation. 8 in. blade, 10 in. max. dia., 400 CFM. **£6/10/0** (des. 5/-) Same model 10 in. blade, 12 in. max. dia., 500 CFM. **£6/16/0** (des. 6/-).

**IMMEDIATE DELIVERY** of Stuart Centrifugal Pumps, including stainless steel (most models).


OFFICIAL STOCKIST: "PARVALUX" Electric Motors (List G.M. 169)

**M. R. SUPPLIES (LONDON) LTD., 68 New Oxford Street, London, W.C.1**  
(Telephone: 01-636 2958)

WW-066 FOR FURTHER DETAILS
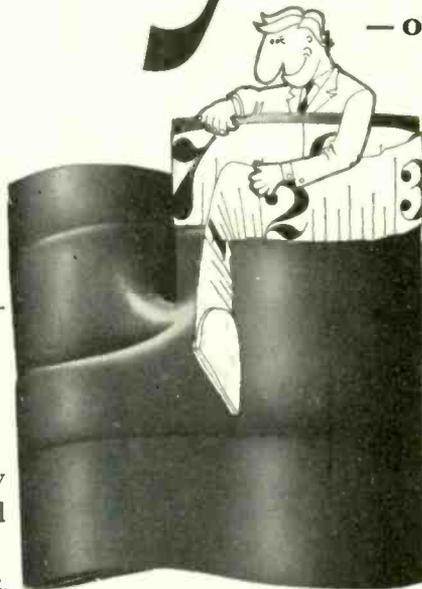
# Mnemo- polymers\*

— or 70 ways of shrinking your sealing, jointing and encapsulation costs!




\*Mnemopolymers—the science of heat-shrinkable polymers with a built-in memory—perfected after many years of research and development by Hellermann-Electric.

The Helashrink® range of Moldanized® Shapes gives you the fast, low-cost answer to encapsulation of electrical connectors; water sealing of cable glands; cable jointing; sealing crutches on power cables; covering spurs in wire harnesses and cable.

More than 70 standard shapes are available and specials can be supplied to meet your particular needs.


Shrinking is fast—by heat gun, gas flame or infra-red ovens.

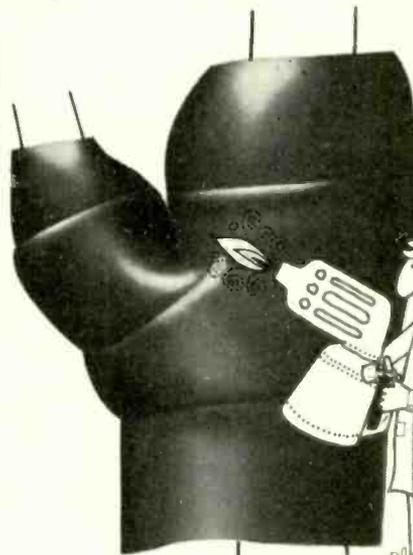*Moldanized Shapes come in shrink ratios up to 5:1, giving you room to work...*



Other Helashrink products: sleeves, cable markers, tubing and end caps. They shrink quickly, grip tightly, conform evenly—cut cable binding and sleeving costs!

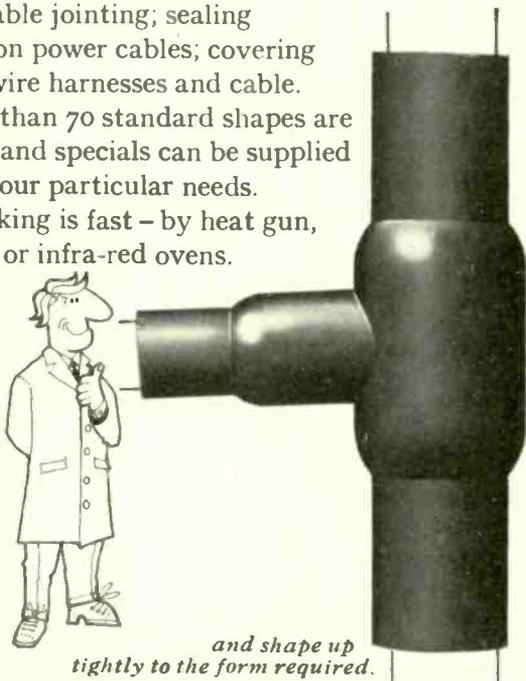*with heat applied, they shrink quickly and evenly...*



*and shape up tightly to the form required.*

**Shrink-it-yourself kit FREE**  
 (All you need is a match)

Please send me your free Mnemopolymers Demonstration Kit—plus full details of Helashrink Moldanized Shapes.

Name \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

WW 3


**WORLD LEADERS IN CABLE ACCESSORIES**  
**HELLERMANN ELECTRIC**  
 A division of Bowthorpe-Hellermann Ltd.  
 Gatwick Road, Crawley, Sussex. Tel: Crawley 28888  
 A member of the Bowthorpe Holdings Group of Companies

WW—067 FOR FURTHER DETAILS

**DC300****DUAL-CHANNEL POWER AMPLIFIER**

Frequency Response	± 0.1db Zero-20KHz at 1 watt into 8 ohms, ± 0.6db Zero-100KHz.
Phase Response	Less than 5°, 0-10KHz.
Power Response	± 1db Zero-20KHz at 150 watts RMS into 8 ohms.
Power at Clip Point	Typically 190 watts RMS into 8 ohms, 340 watts RMS into 4 ohms per channel.
Total Output (IHF)	Typically 420 watts RMS into 8 ohms, 800 watts RMS into 4 ohms
I.M. Distortion (60-7KHz 4:1)	Less than 0.1% from 0.01 watt to 150 watts RMS into 8 ohms, typically below 0.05%. (max 0.05%.
Damping Factor	Greater than 200 (Zero to 1KHz into 8 ohms at 150 watts RMS)
Hum and Noise (20-20KHz)	100db below 150 watts RMS output (unweighted, typical 110db).
Slewing Rate	8 volts per micro-second. S-R is the maximum value of the first derivative of the output signal.
Dimensions	19in. standard rack mount (W.E. hole spacing), 7in. height, 9½in. deep (from mounting surface).
Weight	40 pounds net weight.
Finish	Bright-anodized brushed-aluminium front-panel with black-anodized front extrusion, access door, and chassis.

★ DC-Coupled throughout!

★ Short Circuit proof!

★ 500 Watts RMS Mono.

★ 70 Volt Balanced line out!

★ Only £320 inc. duty!

**CARSTON ELECTRONICS LTD.**71 OAKLEY ROAD  
CHINNOR, OXON.

Telephone: Kingston Blount 8561.

WW—068 FOR FURTHER DETAILS

## TELEPRINTERS · PERFORATORS REPERFORATORS · TAPEREADERS DATA PROCESSING EQUIPMENT

Codes: Int. No. 2 Mercury/Pegasus, Elliot 803,  
Binary and special purpose Codes.**2-5-6-7-8- TRACK AND  
MULTIWIRE EQUIPMENT****TELEGRAPH AUTOMATION AND COMPUTER PERIPHERAL ACCESSORIES  
DATEL MODEM TERMINALS, TELEPRINTER SWITCHBOARDS**

Picture Telegraph, Desk-Fax, Morse Equipment; Pen Recorders; Switchboards; Converters and Stabilised Rectifiers; Tape Holders, Pullers and Fast winders; Governed, Synchronous and Phonic Motors; Teleprinter Tables and Cabinets; Silence Covers; Distortion and Relay Testers; Send/Receive Low and High Pass filters; Teleprinter, Morse, Teledeltos Paper, Tape and Ribbons; Polarised and specialised relays and Bases; Terminals V.P. and F.M. Equipment; Telephone Carriers and Repeaters; Diversity; Frequency Shift, Keying Equipment; Line Transformers and Noise Suppressors; Racks and Consoles; Plugs, Sockets, Key, Push,

Miniature and other Switches; Cords, Wires, Cables and Switchboard Accessories; Teleprinter Tools; Stroboscopes and Electronic Forks; Cold Cathode Matrices; Test Equipment; Miscellaneous Accessories, Teleprinter and Teletype Spares.

**W. BATEY & COMPANY**

Galeys Works, Akeman Street, Tring, Herts.

Tel.: Tring 3476 (3 lines)  
STD: 0442 82Cables: RAHNO TRING  
TELEX 82362

WW—069 FOR FURTHER DETAILS

## A SOLDIER'S BEST FRIEND IS HIS GUN

From the Burgess All-electric Workshop: a light, balanced solder gun with a range of screw-in tips. The tips—and only the tips—heat up in 7 short seconds, Anti-thermal casing keeps the rest of



the gun cool. Note the slim barrel—it reaches right down into confined spaces. There are spike-like extension barrels for real 'in-deep' work. A prefocused lamp pinpoints work detail. Fail-safe soldering even for delicate work! The price of this tough, modern instrument? Just £4 12 6 complete with two tips, a 6" extension barrel, a double-ended probe and solder. **FREE 24-PAGE CATALOGUE!** For details of the Burgess instant heat solder gun, plus other equipment in the Burgess All-Electric Workshop, write for a free copy of our information-packed catalogue.

# **BURGESS** take the work out of your workshop.

Burgess Products Company Limited, Electric Tools Division,  
Sapcote, Leicester LE9 6JW.

WW—070 FOR FURTHER DETAILS



*We are exhibiting at:—*  
**IEA EXHIBITION—OLYMPIA**  
 Stand No. G100      11th-16th May

# how to take levell- headed measurements...

**Measure  $\mu$ V's from 1Hz to 3MHz**



**VOLTMETER RANGES**  
 15 $\mu$ V, 50 $\mu$ V, 150 $\mu$ V ... 500V f.s.d.  
 Acc.  $\pm 1\% \pm 1\%$  f.s.d. = 1 $\mu$ V at 1kHz.

**db RANGES**  
 - 100dB, - 90dB, - 80dB ... + 50dB.  
 Scale - 20dB/+ 6dB rel. to 1mW/600 $\Omega$ .

**FREQUENCY RESPONSE**  
 Above 500 $\mu$ V:  $\pm 3$ dB from 1Hz to 3MHz,  
 $\pm 0.3$ dB from 4Hz to 1MHz.

Type TM3B can be set to a restricted B.W. of 10Hz to 10kHz or 100kHz.

**INPUT IMPEDANCE**  
 Above 50mV:  $> 4.3M\Omega < 20$ pf.  
 On 50 $\mu$ V to 50mV:  $> 5M\Omega < 50$ pf.

**AMPLIFIER OUTPUT**  
 150mV at f.s.d. on all ranges into 200k $\Omega$  and 50pF without loss.

**SIZES & WEIGHTS**  
 TM3A: 5" x 7" x 5". 5lb. 3 $\frac{1}{2}$ " scale.  
 TM3B: 7" x 10" x 6". 8lb. 5" mirror scale.

type **TM3A £49**      type **TM3B £63**

Long battery life and large overload ratings are leading features of these solid state instruments. Mains power supply units and leather carrying cases are optional extras.

**Measure  $\mu$ V's from 1Hz to 450MHz.**



**H.F. VOLTAGE RANGES**  
 1mV, 3mV, 10mV ... 3V f.s.d.  
 Square law scales. Acc.  $\pm 4\%$  of reading  $\pm 1\%$  of f.s.d. at 30MHz.

**H.F. db RANGES**  
 - 50dB, - 40dB, - 30dB ... + 20dB.  
 Scale - 10dB/+3dB rel. to 1mW/50 $\Omega$ .

**H.F. RESPONSE**  
 $\pm 0.7$ dB from 1MHz to 50MHz.  
 $\pm 3$ dB from 300kHz to 400MHz.  
 $\pm 6$ dB from 400MHz to 450MHz.

**L.F. RANGES**  
 As TM3 except for the omission of 15 $\mu$ V and 150 $\mu$ V ranges.

**AMPLIFIER OUTPUT**  
 As TM3 on L.F.  
 Square wave at 20Hz on H.F. with amplitude proportional to square of input.

**SIZES & WEIGHTS**  
 TM6A: 5" x 7" x 5". 6lb. 3 $\frac{1}{2}$ " scale.  
 TM6B: 7" x 10" x 6". 9lb. 5" mirror scale.

type **TM6A £85**      type **TM6B £99**

**Measure D.C.  $\mu$ V's, pA's &  $\Omega$ 's**



**VOLTAGE RANGES**  
 3 $\mu$ V, 10 $\mu$ V, 30 $\mu$ V ... 1kV. Acc.  $\pm 1\% \pm 1\%$  f.s.d.  $\pm 0.1\mu$ V. LZ & CZ scales.  
 Noise  $< 0.5\mu$ V p-p on 3 $\mu$ V range.  
 Drift  $< 0.7\mu$ V/ $^{\circ}$ C &  $< 0.7\mu$ V/day.  
 Input res.  $> 1M\Omega/\mu$ V up to 10mV,  $> 10kM\Omega$  on 30mV to 1V, 100M $\Omega$  above 1V.

**CURRENT RANGES**  
 3pA, 10pA, 30pA ... 1mA (1A for TM9BP)  
 Acc.  $\pm 2\% \pm 1\%$  f.s.d.  $\pm 0.3$ pA. LZ & CZ scales. Noise  $< 0.7$ pA p-p on 3pA. Drift  $< 1$ pA/ $^{\circ}$ C &  $< 1$ pA/day. Input res. 1M $\Omega$  up to 1nA, 100k $\Omega$  on 3nA to 1 $\mu$ A, 100 $\Omega$  on 3 $\mu$ A to 1mA, 0.12 $\Omega$  on 3mA to 1A.

**RESISTANCE RANGES**  
 3 $\Omega$ , 10 $\Omega$ , 30 $\Omega$  ... 1kM $\Omega$  linear. Acc.  $\pm 1\%$ ,  $\pm 1\%$  f.s.d. up to 100M $\Omega$ . Test voltage 3mV at f.s.d. on  $\Omega$  ranges. Test currents 1 $\mu$ A & 1nA on k $\Omega$  & M $\Omega$ .

**RECORDER OUTPUT**  
 1V at f.s.d. into  $> 1k\Omega$  on LZ ranges.

**SIZES & WEIGHTS**  
 TM9A as TM3A.      TM9B & BP as TM3B.

type **TM9A £75**      type **TM9B £89**      type **TM9BP £93**



*Hire terms and leaflets covering our full range of portable instruments are available from:*

**LEVELL ELECTRONICS LTD · PARK ROAD · HIGH BARNET · HERTS. · TEL: 01-449 5028**

W-071 FOR FURTHER DETAILS

**it's incredible!**

**it's new!**

**frequency sensitive switches in microcircuit form**

**breakthrough in size, cost, precision and versatility**




This FX-201 'Z TRIP' is unique—it is the only frequency sensitive switch in microcircuit form. It incorporates over 200 transistors on a single monolithic silicon chip, and is housed in a TO-5 style can.

This 'Z TRIP' consists of two independent 'band accept' frequency selective switches, incorporating an input amplifier, analogue/digital frequency discriminating circuits and buffered bistable output switches. It operates from a single d.c. supply and is rated for industrial environments.

The FX-201 accepts sinewave and pulse input signals: when the input signal frequency falls within either of the two predetermined acceptance bands the corresponding output is switched. Completely immune to random signal noise and harmonics.


- Adjustable band frequencies 10Hz to 30kHz
- Adjustable band separation 1% to 50%
- Adjustable bandwidths 1% to 50%
- Band edge 'slope' typically 0.1%
- Response time approx. 1.8 mSec @ 5kHz
- Signal amplitude range 20mV to 20V

**LOW COST IMMEDIATE DELIVERY**

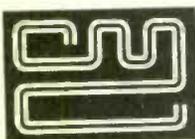


*Comprehensive data from*  
**CONSUMER MICROCIRCUITS LTD**  
 142/146 OLD STREET, LONDON, E.C.1  
 Telephone: 01-253 5838/9

WW—072 FOR FURTHER DETAILS

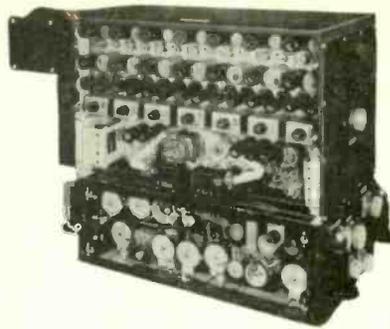

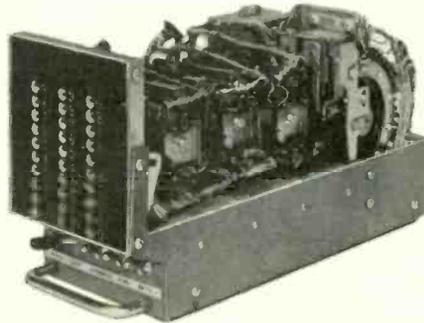**Ballistics Computers by Westinghouse.** Nine servo amplifiers with associated motors and Power Packs. Brand new in sealed containers. Price on application.



**Automatic Numbering Machine by Western Union.** Four Uniselectors and 30 neons. Ideal basis for amateur computer. Application leaflet. £12.10s. post free.

**PUNCHES, READERS, VERIFIERS AND TELEPRINTERS. NEW COMPUTER ENGINEERING SURPLUS MATERIALS, AT REALISTIC PRICES. MOBILE SHOWROOM. CALLS ON REQUEST TO SUITABLE LOCATIONS.**

Elliott 803B computers 4k store, 803C 8K store, film handlers, two tape readers, two tape punches. ICL 1901 Central Processors 8K store Lineprinter, 600 LPM. Elliott 903 8K store tape readers & punch. Prices on application.

**COMPUTER TRAINING PRODUCTS**

2 Lordship Lane, LETCHWORTH, HERTS. Tel: 4536 0462/6

WW—073 FOR FURTHER DETAILS

**WOW!**

**And how to stop it**

First, measure it — on the Rank Studio Flutter Meter. The Type 1740 measures accurately the degree of Wow and Flutter on sound recorders and reproducers.

For more information write to:

**RANK FILM EQUIPMENT**  
 Rank Audio Visual Limited  
 P.O. Box 70  
 Great West Road  
 Brentford, Middx.  
 Tel 01-568 9222


WW—074 FOR FURTHER DETAILS



# RADIO MASTS AND AERIAL ARRAYS
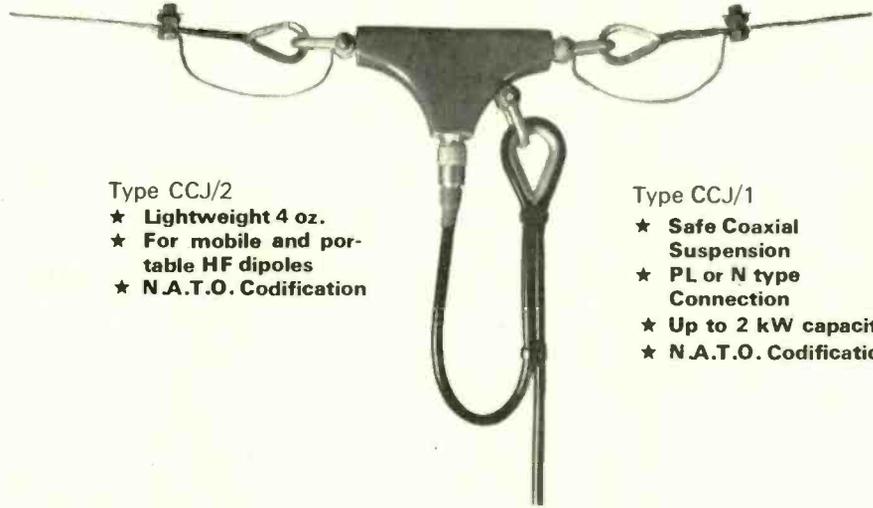
## COAXIAL CABLE TERMINATING UNITS

Designed for Centre Fed Tx and Rx Dipole Arrays.



MANUFACTURERS OF:  
**Aerial Systems for M.F. & H.F.**  
 range including:  
**Centre Fed Half Wave Dipoles.**  
**Delta Matched Dipoles.**  
**Folded Dipoles.**  
**Broad Band Cage Monopoles.**  
**Rhombic Systems.**  
**Quadrant Dipoles.**  
**Inverted "V" Arrays.**  
**Terminated Folded Dipoles.**  
**M.F. "T" & "L" Aerials.**  
**Radio Masts.**  
**Vertical Radiators.**  
**Transmission Line Equipment.**  
**Lead-in-Insulator Panels.**

Type CCJ/2  
 ★ **Lightweight 4 oz.**  
 ★ **For mobile and portable HF dipoles**  
 ★ **N.A.T.O. Codification**

Type CCJ/1  
 ★ **Safe Coaxial Suspension**  
 ★ **PL or N type Connection**  
 ★ **Up to 2 kW capacity**  
 ★ **N.A.T.O. Codification**

Also available: Portable half wave antennae designed for use with the modern HF transceiver. These antennae use the CCJ/2 centre connector with Terylene/Copper elements calibrated in  $\frac{1}{2}$  Mc/s. spacing to frequency nominated. Supplied with coaxial cable and fitted required type of plug.


SUPPLIERS TO:  
**Government Ministries, Crown Agents, principal manufacturers of Telecommunications equipment and overseas governments and administrations.**

**SOUTH MIDLANDS CONSTRUCTION LIMITED**  
**S. M. House, Osborne Road, Totton, Hants.**  
**Telephone: Totton 2785/4930**

WW—075 FOR FURTHER DETAILS

# 'Astronic' SERIES 1700

## A COMPLETE RANGE OF MODULES

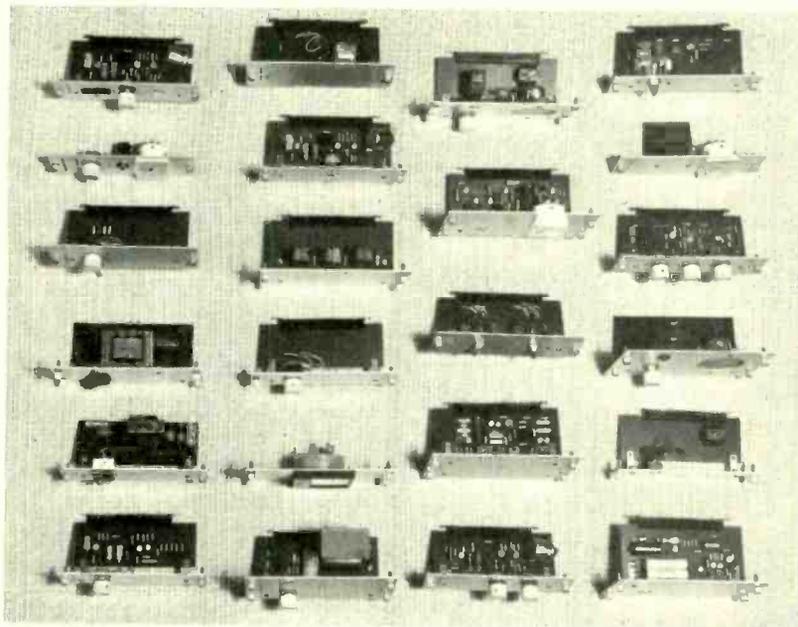

**ASSOCIATED ELECTRONIC ENGINEERS LTD.**  
**DALSTON GARDENS, STANMORE, MIDDLESEX. HA7-1BL**  
**TELEPHONE 01-204 2125**

WW—076 FOR FURTHER DETAILS

www.americanradiohistory.com

**T** made to  
**U**  
**R** **MEASURE**

made to

**MEASURE**

**R**

**N**

**INTER ALIA**

**E**

**M**

**E**

**T**

**E**

**R**

**exactly**

**to YOUR**

**requirements**

**ERNEST TURNER**  
ELECTRICAL INSTRUMENTS LTD.  
TOTTERIDGE AVENUE  
HIGH WYCOMBE  
BUCKS. ENGLAND.  
Telephone 30931/4

**LINEAR** RANGE OF

**SOLID STATE A.C. MAINS AMPLIFIERS**  
employing only high grade components and transistors

**LT55 6 WATT AMPLIFIER**  
A High Fidelity unit providing excellent results at modest output levels.



Output Rating I.H.F.M.  
Frequency Response 30-20,000 cps—2dB.  
Sensitivity 5 mv (max.)  
Harmonic Distortion 0.5% at 1,000 cps.  
Output for 3-8-15 ohm Loudspeakers.  
Input Sockets for 'Mike' Gram and Radio Tuner/Tape Recorder.  
Controls (5) Volume, Bass, Treble, Mains Switch, Input Selector Switch.

Recommended Retail price **£10**  
Size 9½ × 2½ × 5½ in.

If required an attractive wood cabinet with veneer finish can be supplied for any model. Prices from **£3-10-0**

**LT66 12 WATT STEREO AMPLIFIER**

A twin channel version of the LT55 providing up to 6 watts High Fidelity output on each channel.



Switched Input Facilities Socket (1) Tape or crystal PU (2) Radio Tuner (3) Ceramic PU Microphone.  
Controls (6) Volume, Bass, Treble, Balance, Mains Switch, Input Selector Switch, Stereo Mono Switch.

Recommended Retail price **18 GNS**  
Size 12 × 3½ × 6 in.

Available from your Local Hi-Fi Dealer

Facia Plate Rigid Perspex with black/silver background and matching black edged knobs with silver finish centres.

PLEASE SEND A STAMPED ADDRESSED ENVELOPE FOR FULL DESCRIPTIVE DETAILS OF ABOVE UNITS.

Wholesale and Retail enquiries to: **LINEAR PRODUCTS LTD**  
ELECTRON WORKS, ARMLEY, LEEDS

WW-077 FOR FURTHER DETAILS

**DIFFERENTIAL D.C. AMPLIFIERS**  
For use with d.c. energised Transducers



**150** series modular or cased versions

versatile, high performance instrumentation amplifiers for use with low or high level signals. Two outputs available to drive all U-V galvanometers, indicators, recorders and control devices.

FE-154-BD modular £69  
FE-154-BD/C cased mains powered £99

Complementary units:—

Bridge Supplies and Conditioning Units. Sample and Hold and Bridge Amplifiers.

**FYLDE**

Electronic Laboratories Limited.  
Oakham Court, Preston. PR1 3XP  
Telephone: Preston (0772) 57560

WW-078 FOR FURTHER DETAILS

# Introducing the tape decks that will probably start you thinking all over again about tape decks.



**A-6010**  
Our finest 4-track stereo tape deck. Everything about it is professional.

**A-1200**  
Medium priced tape deck with 3 heads, push-button operation, professional performance specifications. 2-track available as special order.



**A-1500W**  
Stereo tape deck with automatic reverse, 3 motors, 4 heads and push-button operation.



**A-4010S**  
4-head, 4-track stereo recorder with symmetrical control operation, 4 solid-state amplifiers, automatic reverse.



Have you watched a TEAC demonstration yet? Have you seen (and heard) what can happen when a company of unusual capability in the magnetic tape industry decides to create some exciting new standards for the knowledgeable music lover?

The TEAC decks shown here are now available exclusively in select hi-fidelity shops throughout Europe. We think they're pretty incomparable.

Example: Model A-6010 has exclusive features like Phase Sensing automatic reverse which gives you up to four hours of uninterrupted music on a single tape. It has symmetrical soft-touch control operation for fast-winding in both tape directions, playback and stop. And it has outer-rotor motors for reel drive, four TEAC Techno-built tape heads, four solid-state amplifiers with silicon transistors, and much, much more.

The other models cost much less, but still give you TEAC's flawless performance.

In this age of tape recording ingenuity, it still might surprise you to see what TEAC is doing.

## TEAC®

TEAC EUROPE N.V.

Amsterdam W2, Kabelweg 45-47,  
Postbus 8180, Netherlands

**TEAC DISTRIBUTORS:** U.K. B. H. Morris & Co., (Radio) Ltd., 84/88, Nelson St., London, E. 1 Ireland International Trading Group Ltd., 5 Cope St., Dame St., Dublin 2 West Germany TEAC European Service Center, Dotzheim Wiesbadenerstrasse 68, 6200 Wiesbaden HANIMEX (DEUTSCHLAND) GMBH, 3000 Hannover, Haltenhoffstr. 50 Belgium INELCO S.A., 20-24, Rue de l'Hospital, Brussel France Fabrications Electroacoustiques Frei 7, Rue Sainte-Isaure, Paris 18 Netherlands INELCO N.V., Arent Janszoon Ernststraat 801, Amsterdam Z. II Italy Audel s.a.s. 20124 Milano V. le Tunisia 45 Cyprus Electroacoustic Supply Co., Ltd., P.O. Box 625, Limassol Denmark Quali-Fi, Christiansholms Parkvej 26, Klampenborg Greece Elina Ltd., 59 & 59A Tritis Septemvriou Street, Athens 103 Portugal Jorge Goncalves, Avenida 5 de Outubro, 53, 1., Lisboa:1 Sweden Audio-Nike AB, Sunnavag 14E, Lund 7 Japan TEAC Corporation 2-8-8, Tsunohazu, Shinjuku-ku, Tokyo

WW-079 FOR FURTHER DETAILS

www.americanradiohistory.com

# 'WATTS' THE NAME FOR RECORD MAINTENANCE



## HI-FI PARASTAT (Reg'd.) Pat. App. 58216/67.



### Gramophone Record Maintenance and Stylus Cleaning Kit

Designed for use on NEW records or records in new condition which are to be played with pick-ups requiring very low tracking pressures. The 30,000 finely pointed tips of the Hi-Fi Parastat Brush positively explore every detail in the record groove to provide the high degree of record cleanliness necessary when

### STYLUS CLEANER

Available separately complete with instructions. Price 5/- Plus 1/3 P.T.

using ultra lightweight pick-ups tracking at 2 grammes or less. The cover pad in the lid of the case is provided for the purpose of cleaning and activating the brush which when enclosed within the case is kept at the correct level of humidity required to control all static at the working surface. Perfectly clean records must be played with a perfectly clean stylus and an integral part of the kit is the new Watts Stylus Cleaner which provides a safe and efficient method of cleaning the stylus. Supplied complete with instructions, 1 oz. New Formula dispenser, Distilled Water dispenser, spare pad cover and ribbons. Price 42/6 plus 1/3 P.T. Replacements: 1 oz. New Formula dispenser 4/6 Distilled Water Dispenser 4/- Pad Cover and Ribbons 1/9.

### 'PARASTAT' Reg'd. Manual Model with Humid Mop

A dual purpose record maintenance device. Keeps new records in perfect condition. Restores fidelity to older discs. The Humid Mop cleans and conditions the bristles and velvet pads. Ensures correct degree of humidity at the time of use. Complete with 1 oz. New Formula dispenser and instructions. Price: 52/6 Replacements: Pad Covers 2/- each, Brush 12/6, Sponge Cover Pad 1/-, 1 oz. New Formula dispenser 4/6, Humid Mop Sponge and 4 wicks 3/-, Manual Parastat available separately 47/6, Humid Mop available separately 5/-.

### The original DUST BUG Reg'd. (Patent No. 817598)

Automatic Record Cleaner. Easily fitted to any transcription type turntable. Provides a simple and effective method of removing static and dust while the record is being played. Surface noise and record and stylus wear is reduced, resulting in cleaner reproduction. Complete with 1/2 oz. New Formula Dispenser and instructions. Price 18/9 plus 4/5 P.T. Replacements: Nylon Bristle and Plush Pad 1/9, 1/2 oz. New Formula Dispenser 2/6.

### 'PARASTATIK' Reg'd. DISC PREENER (Patent No. 982599)

Keeps new records like new. Expressly designed for use with records which have not had previous antistatic treatment. Complete with instructions. Price 6/9. Replacements: Packet of 4 wicks 2/-.

### A GUIDE TO THE BETTER CARE OF L.P. AND STEREO RECORDS

Completely revised, 48 pages, fully illustrated, providing all necessary information on Record Care. 2/6 Post Free.

All obtainable from your local specialist or direct:

To CECIL E. WATTS LTD. DARBY HSE, SUNBURY ON THAMES, MIDDX.

Please send (Post Free U.K. and Commonwealth)

..... Disc Preeners @ 6/9 ..... Hi-Fi Parastats @ 42/6 plus 1/3 P.T.

..... Dust Bugs @ 18/9 plus 4/5 P.T. .... Manual Parastats @ 47/6

..... 48 page Booklets @ 2/6 ..... Stylus Cleaners @ 5/- plus 1/3 P.T.


..... Manual Parastat/Humid Mop @ 52/6

..... Spares as per attached list.

I enclose cheque/P.O. value £..... (Do not send postage stamps)

Name .....

Address .....

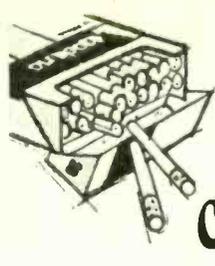

# We put 23,340 cigarettes



## in our Budget combination storage unit!

Think what you could put in it!

Storage. Lots of it. for a thousand things you stock: replacement parts: light bulbs: cameras: anything up to 7" x 8" x 10". Safety drawer-stops as 'standard'. Smooth guide runners thro'out. All in a compact 3ft 6in. high. 2ft 11in. wide. 1ft deep area. Ready assembled, in stove enamelled green or grey. With 18 handy. 6 large. 8 king-sized drawers. At £19.0s. worth every penny! See the rest of the N. C. Brown range!

**£19.0s.**  
carriage free on mainland

## N.C. BROWN LTD.

pacesetters in storage equipment

Send your FREE BROCHURE  or Send  (how many) Budget Storage Units @ £19.0s. in green or grey.

NAME .....

ADDRESS .....

Dept. WW Eagle Steelworks, Heywood, Lancs. Tel: 69018  
London: 25-27 Newton St., W.C.2. Tel: 01-405 7931

WW-080 FOR FURTHER DETAILS

## J E S AUDIO INSTRUMENTATION

Illustrated the Si 451 Millivoltmeter — pk-pk or RMS calibration with variable control for relative measurements. 40 calibrated ranges **£30.0.0**

Si 452 ..... **£25.0.0.** Si 453 ..... **£35.0.0.**

Distortion Measuring Unit. Low distortion Oscillator. 15 c/s — 20 Kc/s — .01% Sine — Square — RIAA


**J. E. SUGDEN & CO., LTD.** Tel. Cleckheaton (OWR62) 2501 BRADFORD ROAD, CLECKHEATON, YORKSHIRE

WW-081 FOR FURTHER DETAILS

## DIOTESTOR IN-CIRCUIT TRANSISTOR TESTER

**BRITEC LIMITED**, 17 Charing Cross Road, London, W.C.2  
Tel: 01-930-3070

WW-082 FOR FURTHER DETAILS

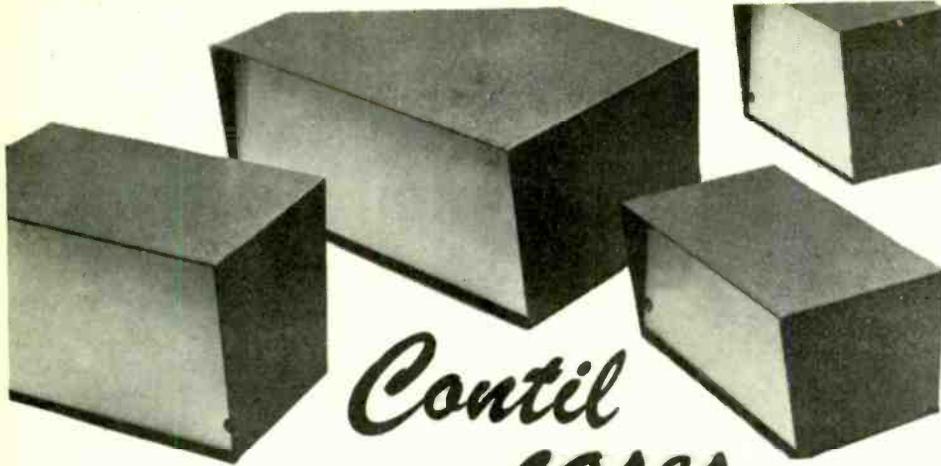

# Contil cases

Contil cases are mass-produced to give lowest prices yet. In 21-gauge steel. Finished hammer blue, with 18-gauge front panel supplied with easy-to-strip protective covering for easy marking out. For ease of ordering Contil cases are described by their dimensions, i.e. 755 is 7 x 5 x 5. Individually packed, including feet and screws.

Contil cases are also available with aluminium panels and Contilcote, which is applied after drilling and cutting.


**CASE PRICES** (All supplied with protective coated steel panels)

Nos. denote size in inches	1	5	10	25	50	100	P&P
755	48/-	46/-	45/-	44/-	43/-	41/-	6/-
867/975	50/-	49/-	48/-	46/-	45/-	43/-	6/-
1277 white or black panel	55/-	52/-	51/-	50/-	49/-	48/-	8/-
1277 unpainted	45/-	44/-	43/-	40/-	39/-	37/-	8/-
16127	106/-	104/-	102/-	101/-	99/-	97/-	9/6
191010	143/-	140/-	137/-	135/-	134/-	133/-	10/6
191010D	199/-	197/-	196/-	194/-	192/-	190/-	18/-
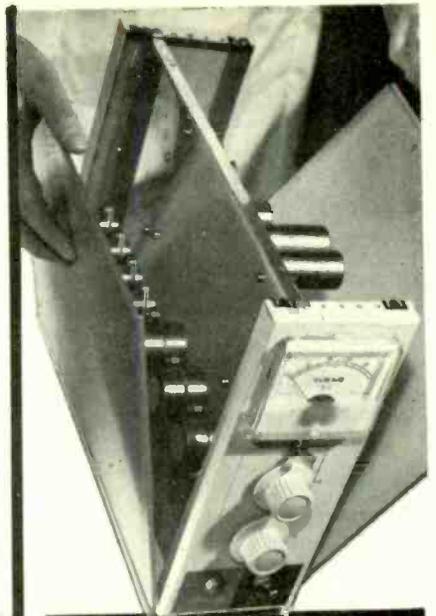
## Your third hand

The ONTOS UNIVERSAL VICE is a new type of multi-purpose, multi-position light engineering vice and stand, fully adjustable for any angle and location in any desired plane. Applications are virtually limitless within its size capacity; i.e. holding P.C. boards for assembly or testing, building up modules, as a micrometer or gauge stand, as a light general purpose vice, in the chemical laboratory, or in fact for all those occasions when you could use a third hand! The ONTOS TWIN TWO-IN-ONE UNIVERSAL VICE is a unique two-in-one version of the Ontos vice, with two sets of jaws, each capable of rotation through 360 deg. of every plane independently of each other. Positive locking enables any such setting to be maintained for repetition work. Ideal for copying P.C. boards, assembly, soldering, bonding, welding, laboratory testing, etc.

ONTOS: 68/- plus P&P 4/6.  
ONTOS TWIN: £5 18 0 plus P&P 6/-.




# CONTIL MOD-2

ideal for development  
cheaper for production

PVC COATED MATERIALS. No outside paint to be scratched. PVC easy to clean, surface is scuff resistant. PVC/ALUMINIUM FOR FRONT & BACK PANELS gives easy cutting with rigidity PVC/STEEL FOR SIDES. TOP & BOTTOM gives rigidity, low cost, ease of assembly. 3 HEIGHTS OF CASE. 4 WIDTHS. 2 DEPTHS. make 24 cases with screws on top and 24 cases with screws on side, that's 48 different cases. LOW COST. Prices include chassis. MODERN DESIGN. Metal work on front and back and chassis is made easier by aluminium with PVC cladding. PVC/steel on sides and bottom for strength. GOOD DELIVERY. Off the shelf range of all PVC coated cases.

NOTE THE LOW COST

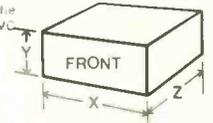


	X	Y	Z	1 off	P. & P.
A	4.5	3	6.5	34/-	3/-
B	4.5	7	6.5	40/-	4/6
C	4.5	10	6.5	50/-	4/6
D	9	3	6.5	50/-	4/6
E	9	7	6.5	55/-	4/6
F	9	10	6.5	65/-	4/6
G	13	3	6.5	55/-	4/6
H	13	7	6.5	65/-	4/6
I	13	10	6.5	73/-	6/-
J	18	3	6.5	65/-	4/6
K	18	7	6.5	89/-	6/-
L	18	10	6.5	107/-	6/-
M	4.5	3	13	40/-	4/6
N	4.5	7	13	55/-	4/6
O	4.5	10	13	73/-	6/-
P	9	3	13	55/-	4/6
Q	9	7	13	73/-	6/-
R	9	10	13	89/-	6/-
S	13	3	13	73/-	6/-
T	13	7	13	89/-	6/-
U	13	10	13	109/-	7/6
V	18	3	13	89/-	6/-
W	18	7	13	107/-	7/6
X	18	10	13	138/-	7/6

*Sizes in inches*

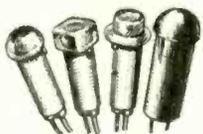
## 'Brightlife' NEONS

25,000 hour average life. PC type 1/8" diameter. 6" leads with resistor inside. Nine different caps available. 160-260V. 10 at 3/- each. 100 at 2/8 each. 1,000 at 2/4 each. 10,000 at 2/3 each. Also available with 30" leads: 110 volt resistor values. PP type 1/8" diameter also supplied with 30" leads and 110 volt variants. 10 at 3/- each. 100 at 2/8 each. 1,000 at 2/4 each. 10,000 at 2/3 each. Neon/resistor assemblies. 100 at 10d. each. 10,000 at 9d. each. Neons only. 100 at 9d. each. 10,000 at 6 1/2d. each. Neons driven by neon oscillator for 6 to 24 volt input down to 50 mW input. Neons driven by transistors with or without alphanumeric caps.


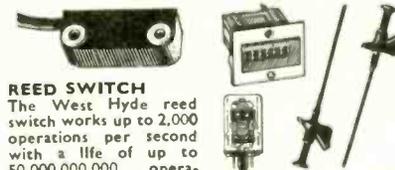
### SUB-MINIATURE NEONS

The smallest yet, type "Q". Overall diameter 1/16", body .7", resistor mounted externally, medium intensity. Minimum quantity 10 at 4/- each. 100 at 3/6 each. 500 at 3/4 each.



### REED SWITCH

The West Hyde reed switch works up to 2,000 operations per second with a life of up to 50,000,000,000 operations when used in the recommended circuit. The hermetically sealed switch is protected in a brass tube and moulded into a polypropylene block giving accurate placing of the contents in relation to the mounting screws. 30" nominal leads fitted. Used for Rev. Counters, flowmeters, burglar alarms, under and over speed monitors, etc. 1 at 15/-, 10 at 13/- each. 100 at 10/- each.

### ACCESSORIES

Flexible insulated test prods, colour red or black, at 13/- each with fine steel clips at the tip, opened by button on top. High speed resetting counter including bezel and socket with speed of over 40 operations per second 165/-, Plug in octal relay, 24 volts, with two changeovers 17/6.



WEST HYDE DEVELOPMENTS LTD.  
30 HIGH STREET NORTHWOOD MIDDXX.  
Telephone: Northwood 24941/26732

**PLEASE NOTE**  
All products ex-stock for normal quantities. Return of post service. Minimum order £1. Fully detailed leaflets available.

AN INTEGRATED CIRCUIT

# VOLTAGE REGULATOR



**BASIC LOW VOLTAGE REGULATOR**  
( $V_o = 2$  to  $6$  Volts)

**BASIC HIGH VOLTAGE REGULATOR**  
( $V_o = 8$  to  $37$  Volts)

**POSITIVE VOLTAGE REGULATOR**  
(External NPN Pass Transistor)

**NEGATIVE VOLTAGE REGULATOR**

**L123 Applications**


**TYPICAL PERFORMANCE**  
 Regulated Output Voltage:  $15$  V  
 Line Regulation ( $\Delta V_{in} = 8$  V):  $1.5$  mV  
 Load Regulation ( $\Delta I_L = 30$  mA):  $4.5$  mV

**TYPICAL PERFORMANCE**  
 Regulated Output Voltage:  $15$  V  
 Line Regulation ( $\Delta V_{in} = 3$  V):  $1.5$  mV  
 Load Regulation ( $\Delta I_L = 1$  A):  $15$  mV



## VOLTAGE REGULATOR L123T1

EQUIVALENT CIRCUIT

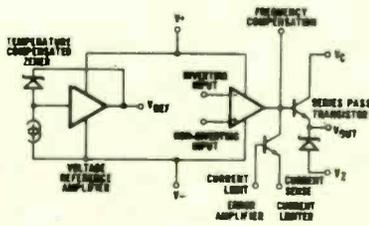

**VOLTAGE REGULATOR**  
 Series, shunt, switching or floating regulator for Positive or Negative Supplies



**ABSOLUTE MAXIMUM RATINGS**

Voltage from $V_+$ to $V_-$	40	V.
Input-Output Voltage Differential	40	V.
Maximum Output current	150	mA.
Current from $V_2$	25	mA.
Internal Power Dissipation	800	mW.
Operating Temperature Range	$0^\circ\text{C}$ to $70^\circ\text{C}$ .	


**CHARACTERISTICS.  $T_{amb} = 25^\circ\text{C}$ .**

	min.	typ.	max.	
Line Regulation $V_{in} = 12$ to $15$ V.	0.01	0.1	0.6	% $V_{OUT}$ .
$V_{in} = 12$ to $40$ V.	0.1	0.5	0.6	% $V_{OUT}$ .
Load Regulation $I_L = 1$ to $50$ mA.	0.6	—	—	% $V_{OUT}$ .
Ripple Rejection $C_{REF} = 5\mu\text{F}$ .	86	—	—	dB.
Short Circuit Current Limit	65	—	—	mA.
Reference Voltage	6.8	7.15	7.5	V.
Output Noise Voltage $C_{REF} = 5\mu\text{F}$ .	2.5	—	—	$\mu\text{VRMS}$ .
Load Term Stability	0.1	—	—	%/1000hrs
Standby Current Drain	2.3	4.0	—	mA.
Input Voltage Range	9.5	—	40	V.
Output Voltage Range	2.0	—	37	V.
Input-Output Voltage Differential	3.0	—	38	V.
Average Temp. Coeff. of Output Voltage $0^\circ\text{--}70^\circ\text{C}$ .	—	0.003	0.015	%/ $^\circ\text{C}$ .

PRICE 1—24 £3 3s. 9d.

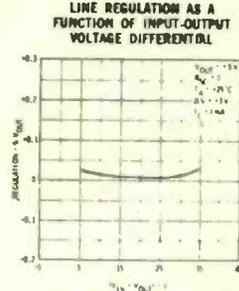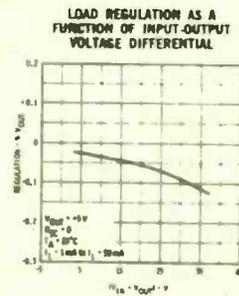

**CONNECTION DIAGRAMS TOP VIEWS**

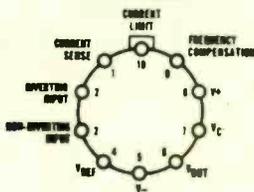

IS JUST ONE OF THE 1500 SEMICONDUCTORS DETAILED IN

# QUARNDON SEMICON'70

WHICH INCLUDES PRODUCTS STOCKED AND AVAILABLE

BY RETURN OF POST FROM

## QUARNDON ELECTRONICS

TELEPHONE  
(0332)  
32651


(SEMICONDUCTORS) LIMITED

SLACK LANE DERBY

TELEX  
37163

# NATO, NASA, Royal Navy, BBC use Uher. Now you can..

**..the Uher 714 for less than £60**

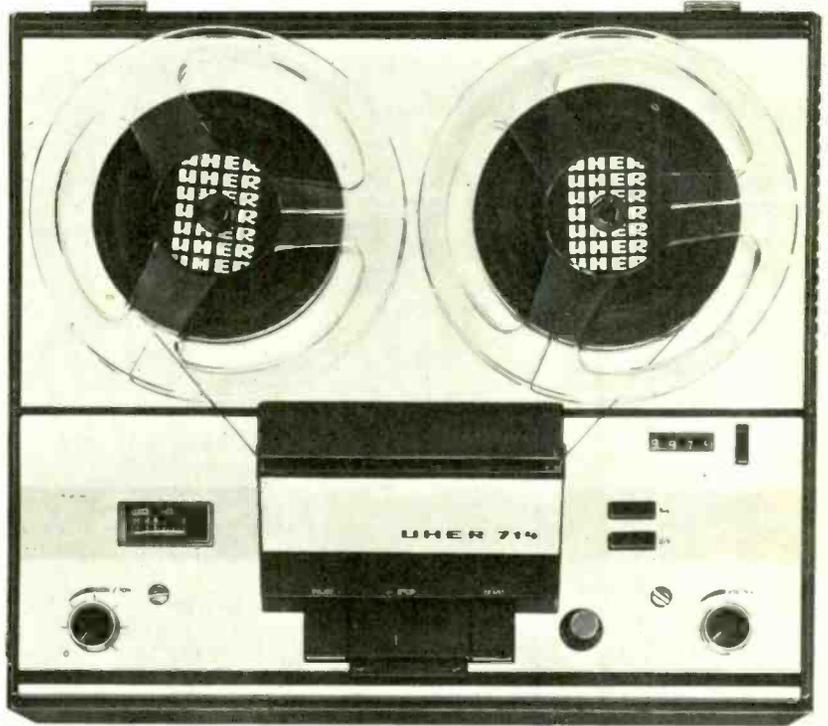

The same exacting standards of technical excellence demanded by these world pacesetters are applied to producing the Uher 714 which, for the first time, brings the superb quality of Uher below £60.


See and hear the Uher 714. It incorporates many features

associated with much more expensive instruments.


- All round tape speed of 3 3/4 ips
- Perfect four-track recording
- 7" reels
- Plays back stereo tapes
- Monitoring during recording
- Solid pressure-cast frame

- Silicon transistors
- Recording Level Instrument with dB scale
- Simple operation
- Light · Robust · Portable


The Uher 714 outclasses everything in its class.

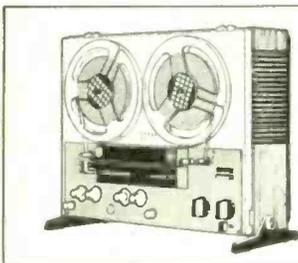


VARIOCORD 23

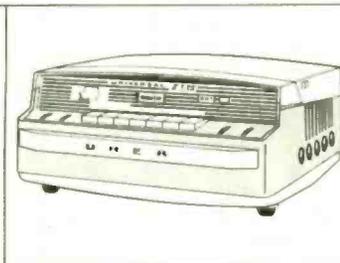

UNIVERSAL 5000

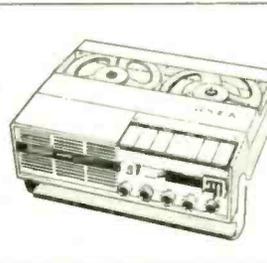

UHER 4000 REPORT L

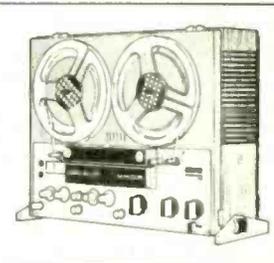

ROYAL DE LUXE

# UHER

DISTRIBUTED IN THE U.K. BY

# BOSCH

BOSCH LIMITED, WATFORD, WD2 4LB, HERTS. TELEPHONE: WATFORD 44233

WW—085 FOR FURTHER DETAILS


www.americanradiohistory.com

# ARE COSTS OUTWEIGHING YOUR PROFITS?

**Come and see what mechanisation can do.**

High productivity and full order books are fine. But if margins are down, you've got to look for new ways of improving efficiency. You'll find them—in plenty—at London's International Mechanical Handling Exhibition. It will be the biggest collection of time-saving ideas you've ever seen—the world's largest display of mechanized handling aids. New systems and equipment to cut costs and ensure maximum utilization of plant. The very latest in receiving techniques; storage inventory control; in-processing; packaging; transport; distribution; plus all that is new in ancillary services and equipment. Whether your business is large or small you can save money with modern handling methods.

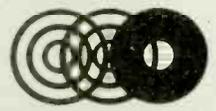**Don't miss this important event. Make a note of the date . . . and mail the enquiry now.**



**INTERNATIONAL  
MECHANICAL  
HANDLING  
EXHIBITION**  
5-15 MAY 1970  
EARLS COURT LONDON

MAIL NOW FOR FURTHER DETAILS AND FREE SEASON TICKET.  
 To: The Manager, Mechanical Handling Exhibition,  
 Dorset House, Stamford Street, London, S.E.1.

NAME.....  
 (please print)

COMPANY.....

ADDRESS.....

.....

.....

The Exhibition is sponsored by the journals  
 MECHANICAL HANDLING and MATERIALS HANDLING NEWS


WW2



## radio microphone systems



### system R.M.S.5

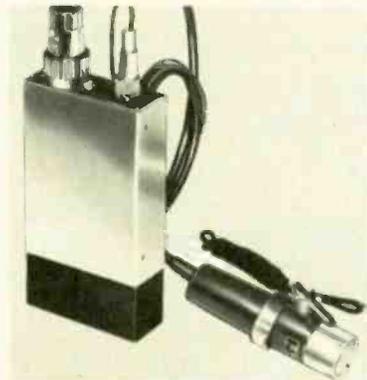



The **AUDIO** radio-microphone system R.M.S.5 meets the most stringent requirements for compactness, reliability and quality. It is extensively used in film, broadcast and television productions including those of the B.B.C and I.T.V companies. It is also the preferred choice in many fields of professional entertainment and has industrial and educational applications as well. As an alternative to the tiny transmitter, usually secreted about the person of the user, a complete hand-held microphone is now available with the transmitter contained within the tubular handle. Performance characteristics are the same for either version.

#### ABRIDGED SPECIFICATIONS

Frequency range from 50MHz to 175MHz, crystal controlled, with  $\pm 75$ KHz deviation. Power output from 1mW to 20mW. Stability  $\pm 10$ KHz at 175MHz from 0°C to 40°C, and correspondingly better at lower Hz. Hand-held model R.M.S.5H with microphone incorporates on/off switch and battery compartment.

**NARROW BAND VERSION**—The Post Office allows use of two wide band channels, or where speech quality is not important, five narrow band channels. A narrow band version of R.M.S.5 can be supplied accordingly.

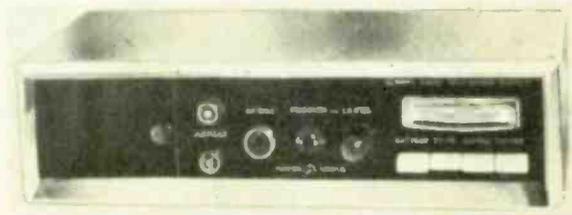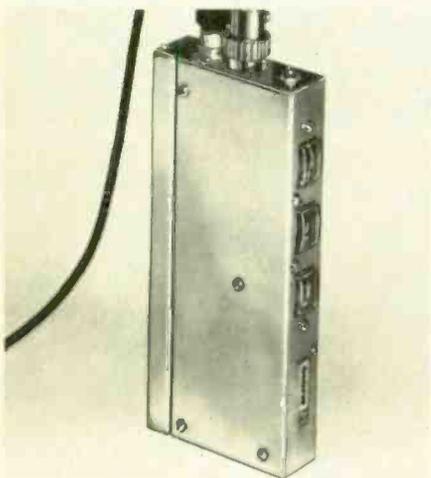**RECEIVER.** This is a crystal controlled superheterodyne with characteristics to suit the transmitter. A carrier/battery voltage indicator is incorporated.



### system R.M.S.7

A fully professional assembly in which exceptionally high standards of quality are maintained within unusually small units of equipment. The receiver is not very much larger than the transmitter. The receiver, shown to the left, is fitted with a flexible plug-in "whip" aerial and includes separate battery, signal level and tuning indicators. The transmitter is as that for R.M.S.5 except that effective audio compression is incorporated. Audio response is  $\pm 2$ dB from 30-15,000Hz over the entire system. System R.M.S.9 uses the same transmitter as R.M.S.7 but has a larger receiver with push button controls and monitoring facilities for headphones.

In addition to the programme detailed above, **AUDIO LIMITED** have under development a 470MHz radio-microphone for TV use overseas, a half-watt radio-microphone for outside broadcasts, a 4 watt transmitter for radio-microphone links, and studio talk-back systems. Enquiries invited.


# audio

**AUDIO LIMITED, 46 PENTONVILLE ROAD, LONDON, N.1**

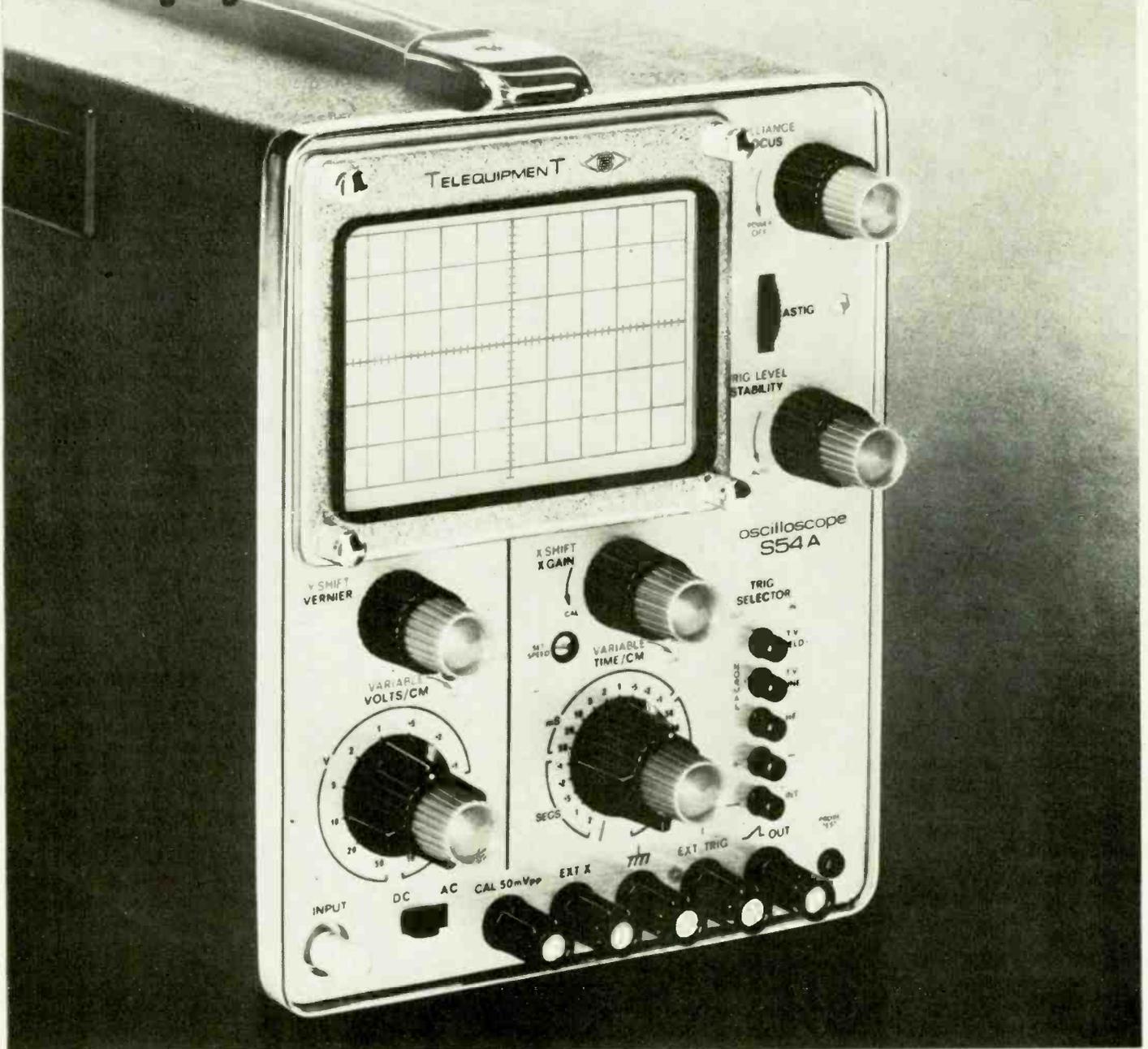**Telephone: 01-278 1020**

WW-094 FOR FURTHER DETAILS  
www.americanradiohistory.com

It's only a year since we launched the record selling S54



# Now we introduce the S54A...

... a single beam oscilloscope with a sensitivity of 10mV/cm at 10MHz bandwidth

The S54A is an all solid state oscilloscope developed from the S54. Smartly styled yet ruggedly built, the S54A has a wide application in field work, in the laboratory and in production line testing. Look at the features:

- \* 10MHz Bandwidth at 10mV/cm
- \* All Solid State Design
- \* Small Size — Light Weight
- \* FET Inputs
- \* Versatile Triggering including T.V. Line and Frame Sync.
- \* 6 x 10cm. Viewing Area
- \* Built-in Voltage Calibrator.

At £120 you will find no other oscilloscope of its type which offers such features at such low cost. Write or phone for full specification NOW!!!

**TELEQUIPMENT** 

Telequipment Limited, 313 Chase Road, Southgate, London, N.14. Telephone: 01-882 1166. Telex: 262004.  
A member of the Tektronix Group. For Overseas enquiries write to: Tektronix Ltd., P.O. Box 48, Guernsey, C.I.

# Wireless World

Electronics, Television, Radio, Audio

Sixtieth year of publication

April 1970

Volume 76 Number 1414



This month's cover illustration shows an unusual view of a watchmaker's wheel adopted by Pye to aid the handling of components in the production of small receivers (see p.158).

## Contents

- 149 Technology versus Education
- 150 Stabilized Power Supply by A. J. Ewins
- 154 H.F. Predictions
- 155 Low-angle Radiation by L. A. Moxon
- 158 Radio Fire Alarm
- 159 Class-B Audio Amplifier Circuits by K. C. Johnson
- 162 Speakers in Corners by H. D. Harwood
- 165 An Electronic Dice by Brian Crank
- 166 Announcements
- 167 News of the Month
- 170 Letter from America
- 171 Sonex '70
- 172 Letters to the Editor
- 175 Digital Remote Control Systems by H. N. Griffiths
- 178 Transients by Thomas Roddam
- 181 Conferences & Exhibitions
- 182 Circuit Ideas
- 183 Active Filters—9 by F. E. J. Girling & E. F. Good
- 189 Dynamic Range versus Ambient Noise by G. I. O'Veering
- 191 World of Amateur Radio
- 192 Personalities
- 193 New Products
- 198 Literature Received
- 200 April Meetings
- A117 SITUATIONS VACANT
- A142 INDEX TO ADVERTISERS

### IN OUR NEXT ISSUE

Simple high-quality pre-amplifier, having a high input impedance, suitable for radio and ceramic gramophone pickups.

Low-cost horn loudspeaker system



I.P.C. Electrical-Electronic Press Ltd  
Managing Director: Kenneth Tett  
Editorial Director: George H. Mansell  
Advertisement Director: George Fowkes  
Dorset House, Stamford Street, London, SE1  
© I.P.C. Business Press Ltd, 1970  
Brief extracts or comments are allowed provided acknowledgement to the journal is given.

PUBLISHED MONTHLY (3rd Monday of preceding month). Telephone: 01-928 3333 (70 lines). Telegrams/Telex: Wiworld Iiiffepres 25137 London. Cables: "Ethaworld, London, S.E.1." Annual Subscriptions: Home; £3 0s 0d. Overseas: 1 year £3 0s 0d. (Canada and U.S.A.; \$7.2). 3 years £7 13s 0d. (Canada and U.S.A.; \$18.50). Second-Class mail privileges authorised at New York N.Y. Subscribers are requested to notify a change of address four weeks in advance and to return wrapper bearing previous address. BRANCH OFFICES: BIRMINGHAM: 202, Lynton House, Walsall Road, 22b. Telephone: 021-356 4838. BRISTOL: 11, Elmdale Road, Clifton, 8. Telephone: OBR2 21204/5. GLASGOW: 2-3 Clairmont Gardens, C.3. Telephone: 041-332 3792. MANCHESTER: Statham House, Talbot Road, Stretford, M32 0EP. Telephone: 061-872 4211. NEW YORK OFFICE U.S.A.: 205 East 42nd Street, New York 10017. Telephone: (212) 689-3250.

## Why we are excited about the C333 range

In these fast-moving days you might wonder why we're excited about a new capacitor range. Well, sales figures tell us that a lot of circuit designers are also enthusiastic about this—the latest Mullard range of miniature plate ceramic capacitors. Setmakers have already ordered them by the million. And, as for us, we were excited about this new range long before we even sold the first one. In case you are not already using these plate ceramic miniature capacitors, let us tell you (enthusiastically) something about them.

**They're small.** Well, of course. This is the mini age. Naturally, we designed them to fit a 2.45 mm. grid printed circuit board. But we also made them rectangular and thin (2.1 mm. max.). In fact they are no bigger than the winder on your wrist-watch, so that they can pack very closely.

**Wide range.** This is something to be enthusiastic about. For the first time, circuit designers have available a wide

range of low-cost, high stability, close tolerance miniatures to choose from—at low prices. The full range (at present) has 28 values in five sizes from 1.8pF to 330pF (the E6 range). With temperature coefficients between NP0 and N750 the stability of tuned circuits can be maintained over a wide temperature range—this is the C333 series.

**High quality: low cost.** These two conflicting objectives provided their own solution. In the first place we chose the most suitable materials for the performance and stability we required. Then we developed special, highly-automated processes to produce these tiny components within the rigid specifications we had laid down. These very efficient processes gave us the desired results; closely-controlled quality and low production costs.

**Stability.** This is essential for the applications for which these capacitors are intended. We developed materials which would not oxidise or peel in arduous conditions. And a special lacquer coating to protect them in conditions of high humidity. In brief, we designed in high stability and long life.

**Tight tolerance.** Again, the use of very stable materials and highly automated manufacturing and quality control equipment ensures

that every capacitor is held within very close limits—essential for the components used in oscillator and filter stages. The tolerance on every capacitor is within 0.25pF or  $\pm 2\%$ —whichever is the greater.

**Worth it?** Our rising production figures indicate that a good many people think so.

Set designers appreciate that, at Mullard we continue to apply enthusiasm and care to the manufacture of all our devices—discrete components, valves and tubes, and semiconductors. And we continue to produce exciting results.

Materials research, applications research, automated quality production and control—all backed by experience in component manufacture stretching over the history of the electronics industry. All contributed to the quality and performance of this our latest range of capacitors.

## Mullard components for consumer electronics

Mullard Limited,  
Consumer Electronics Division,  
Mullard House, Torrington Place,  
London, WC1

CED98

# Wireless World

## Technology versus Education

**Editor-in-chief:**

W. T. COCKING, F.I.E.E.

**Editor:**

H. W. BARNARD

**Technical Editor:**

T. E. IVALL

**Assistant Editors:**

B. S. CRANK

J. H. WEADEN

**Editorial Assistant:**

J. GREENBANK, B.A.

**Drawing Office:**

H. J. COOKE

**Production:**

D. R. BRAY

**Advertisements:**

 G. BENTON ROWELL (*Manager*)

G. J. STICHBURY

 R. PARSONS (*Classified Advertisement Manager*)

Telephone: 01-928 3333 Ext. 538

Technology is a means towards a better material standard of living. Education is a means towards a better quality of life. The two activities have quite different purposes. Yet they do overlap slightly at the edges, particularly in the field of vocational training. Technology needs and draws upon the resources of educated people: education depends to some extent on technology to provide subjects and stimuli for stretching the human mind.

Perhaps because of this overlap we seem to be getting into a muddle, with passions raised on all sides, about the function of some of our newer universities. The rumpus at Warwick University a few weeks ago, when students uncovered documents revealing an intimate liaison between university authorities and big business, is a case in point. The basis of the trouble seems to be that some students feel the universities are being exploited as outside R & D establishments by "the industrial-military complex". They say that the university authorities have abandoned their independence in return for "industrial-military" gold (or even silver). The rejection of technology (more so than science) by boys at school may stem from some knowledge of this situation, coupled with an association of technology with destruction, and a consequent reluctance to be treated by "them" as "technology fodder".

In electronics, of course, we know that there has long been a close collaboration between industrial firms and certain university departments. At Warwick itself, for example, the School of Engineering Science does research in microwave integrated circuits partly supported by G.E.C.-A.E.I. and Racal (and employees of these firms work in the School). The Wayne Kerr Company has endowed a chair of measurement science at Surrey University. For some years the computer department of Ferranti was almost indistinguishable (in staff and activities) from a section of Manchester University's department of electrical engineering. Mullard Southampton run an M.Sc. "bridging" course in partnership with Southampton University. Brookdeal Electronics sponsor work in the physics department of Reading University and the company's research director is a senior lecturer at the university. . . . And so on. This is all quite openly done—in fact great pride is taken in it—and whether or not it is considered sinister depends on which side of the artificial Arts-Sciences barrier one has been forced to stand. (A barrier, incidentally, which the Open University has knocked down.)

There is perhaps one small thing we can do about the emotional muddle. We may not be able to get rid of hypocrisy, snobbery and prejudices about education but we *can* decide to be honest about the verbal descriptions applied to things. *If* some of the newer establishments are not real universities (note, we are not making assertions about this) then nobody is going to be hoodwinked by the mere fact that they have been called universities. If they are really institutes of higher technology with a few Arts courses tacked on to keep the critics quiet, let them be honest in the way they describe themselves. (The Massachusetts Institute of Technology and, more recently, the Cranfield Institute of Technology are, presumably, proud of their titles.)

Ultimately, education, including *all* universities, must get its money from industry. But, for the good of the spiritual side of us, it is questionable whether this money should be transferred so directly that the philistines—and there are plenty—can insist "he who pays the piper can call the tune". Lord Radcliffe, the chancellor of Warwick University, has said as much himself.

# Stabilized Power Supply

**A versatile unit which will provide a variable stabilized output voltage with adjustable current limiting or a variable constant current with adjustable voltage limiting**

by A. J. Ewins

The stabilized power supply to be described provides not only a fully variable, stable voltage output from 0 to 30 V at a continuous current rating of 1 A, but also a fully variable range of constant currents from 1 mA to 1 A at a maximum voltage of 45 V. In the voltage stabilized mode the constant current network provides current limiting over the same range of currents. In the constant current mode the stabilized voltage network provides voltage limiting from 0 to 30 V.

The power supply departs from convention in that the entire electronic circuitry, except the series regulator transistor, is powered by a separate voltage supply. As a result of this, no transistor, except the series regulator, need have a maximum  $V_{ce}$  rating greater than 20 V or a maximum power dissipation greater than 180 mW. This enables the constructor to select the transistors needed for the electronic stabilizing circuitry from the ever growing range of cheap, plastic encapsulated, silicon planar devices.

Although the maximum stabilized voltage provided by the power supply is only 30 V, it can easily be modified to provide an output voltage greater than this; the maximum value being dependant mainly on the  $V_{ce}$  rating of the series regulator transistor used. (The 2N3055 has a  $V_{ce}$  of 100 V max.) However, it is likely that the maximum current drawn from the supply would have to be reduced since a power dissipation of 100 watts (within the capabilities of the 2N3055) would call for an excessively large heat sink.

## Circuit Description

Before proceeding to a description of the circuit it will prove useful to show how the power supply departs from convention. Fig. 1 shows a fairly conventional stabilized power supply circuit. The output voltage,  $V_o$  is given by;  $V_o = (R_v/R_k) \cdot V_r$  and is directly proportional to  $R_v$  if  $V_r$  and  $R_k$  are kept constant. Keeping  $R_k$  constant has the advantage that the sensing current,  $I_v$ , drawn by the potential divider,  $R_v$  and  $R_k$ , remains constant for all output voltages, thus the current through the zener reference diode remains constant also, helping greatly towards the stability of the reference voltage. Looking now at Fig. 2 it will be seen that the circuit is similar to that of Fig. 1 in principle, however, the difference amplifier and the first two transistors of the series regulator triplet,  $Tr_2$  and  $Tr_3$ , are now powered by a separate voltage supply. The reference voltage is now a positive one since, due to the rearrangement of the circuit, a negative output voltage (with respect to the zero voltage line) is being regulated.


With this rearrangement of the circuit  $Tr_2$  and  $Tr_3$  do not have to withstand the full unregulated power supply voltage when supplying an output voltage of zero volts, with a consequent reduction in the maximum power dissipation required of  $Tr_2$ . If the series regulator,  $Tr_1$ , has a current gain of 30 at a collector current of 1 A, then  $Tr_2$  must be capable of supplying 33 mA for a maximum output current of 1 A. In Fig. 1,  $Tr_2$  would have had to have supplied this current at a maximum  $V_{ce}$  of about 35 V with a consequent maximum dissipation, when the output from the power supply is 0 V at 1 A, of  $35 \times 33 = 1.15$  W. In Fig. 2 the dissipation of  $Tr_2$  under similar conditions is:

$$33(V_s - V_{eb1} - 33 \cdot R_s).$$

With  $V_s = 13$  V (under load conditions),  $R_s = 270 \Omega$  and  $V_{eb1}$  of

the order of 0.6 V the dissipation in  $Tr_2$  is about 133 mW. However, in Fig. 2, the dissipation of  $Tr_2$  is a maximum when its collector current equals  $(V_s - V_{eb1})/2R_s$ , which, in the above example, equals 23 mA. Thus maximum dissipation in  $Tr_2$  is 142 mW.

The addition of a number of components in Fig. 3 limits the output current in the event of a short circuit or similar overload. When the output current is less than the value of the limiting current, the current flowing into the base of  $Tr_3$  is controlled by the "voltage" difference amplifier, thus maintaining a stable output voltage. When the current flowing through  $R_c$  (which is equal to the output current,  $I_L$ , plus  $I_{b1}$  and  $I_v$ ) is such that the voltage developed across  $R_c$  is equal to  $V_{r1} [R_2/(R_1 + R_2)]$  the "current" difference amplifier takes

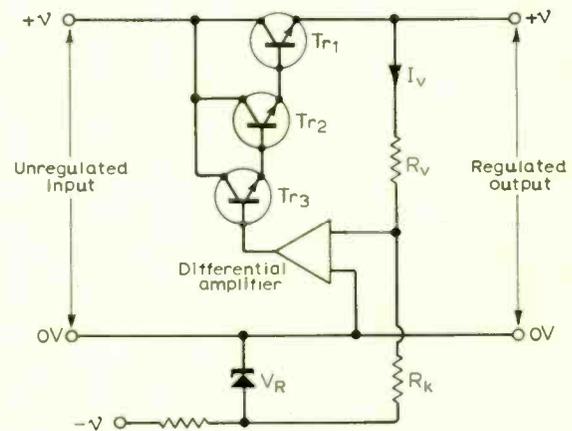

$$\text{Regulated output voltage } V_o = R_v \frac{V_R}{R_k} \quad V_o \propto R_v \text{ if } \frac{V_R}{R_k} \text{ is constant}$$

Fig. 1. A conventional stabilized power supply.

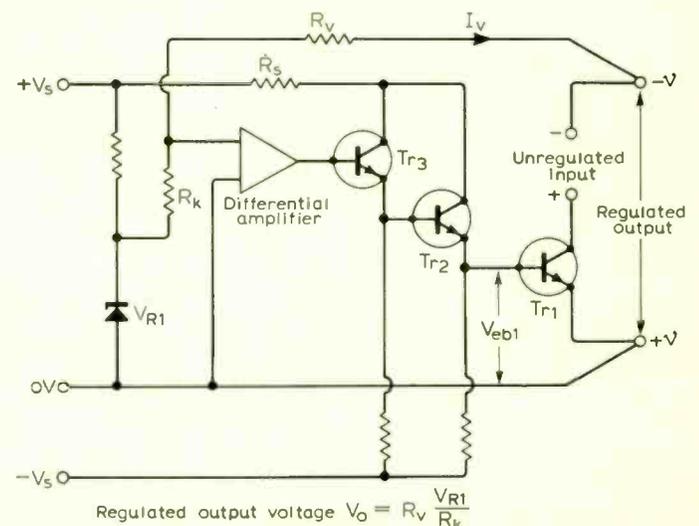


Fig. 2. Using a separate supply line for the stabilizer circuitry.

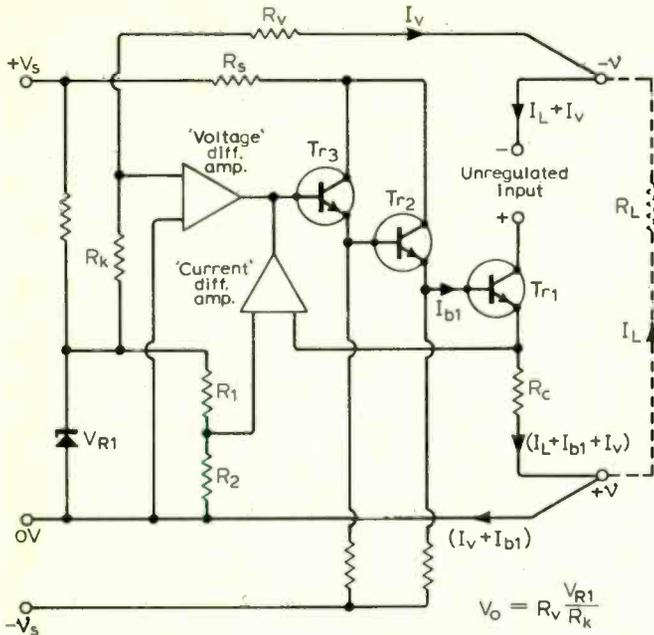


Fig. 3. Adding current limiting.

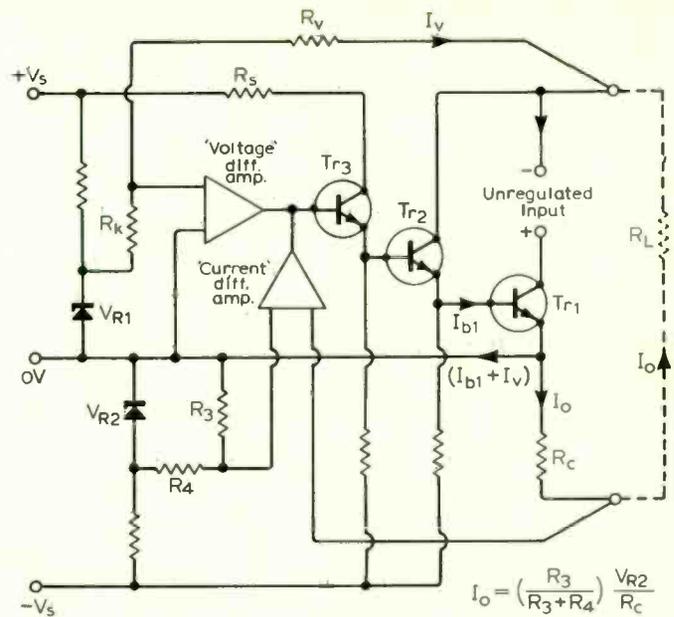


Fig. 4. Using the circuit to supply constant currents.

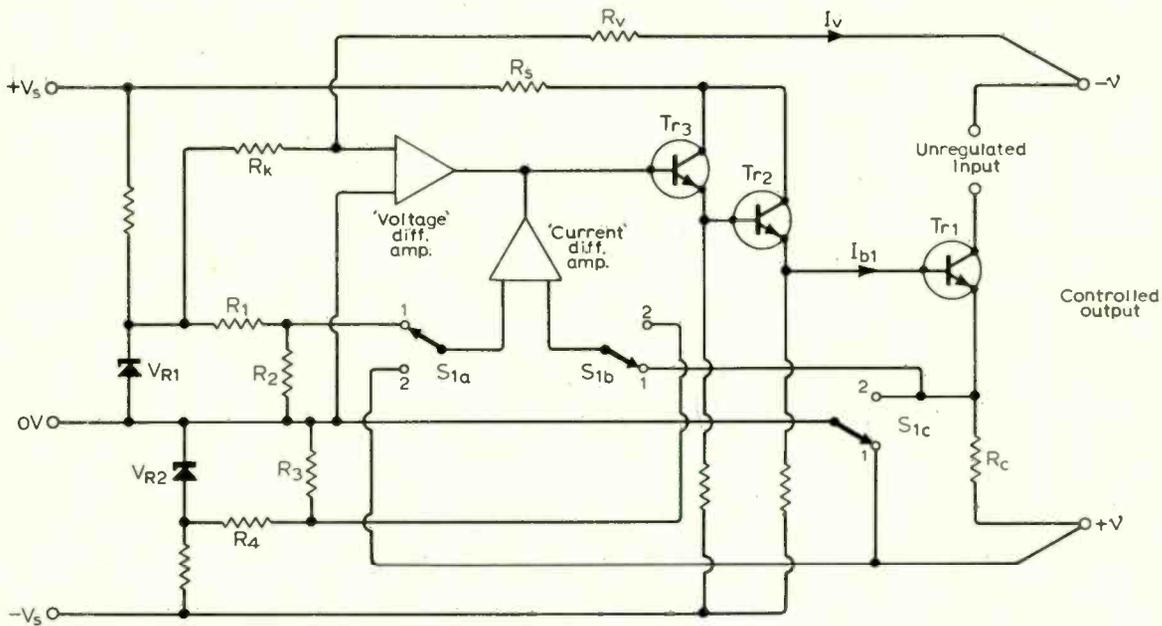


Fig. 5. Combining the circuits of Figs. 3 and 4 to provide a choice between a stabilized voltage output with current limiting or a constant current output with voltage limiting.

over control of the current flowing into the base of  $Tr_3$  with the result that the output voltage is adjusted to maintain a constant current through  $R_c$ .

The output current is thus limited to a value given by:

$$[R_2 / (R_1 + R_2)] V_{r1} / R_c - I_{b1} - I_v$$

now  $[R_2 / (R_1 + R_2)] V_{r1} / R_c$  is equal to the emitter current of  $Tr_1 (I_{e1})$  and

$$I_{e1} = (\beta_1 + 1) I_{b1}$$

where  $\beta_1$  is the current gain of  $Tr_1$ . Therefore:

$$I_{b1} = I_{e1} / (\beta_1 + 1) \quad \text{and}$$

$$I_L = [\beta_1 / (\beta_1 + 1)] [R_2 / (R_1 + R_2)] V_{r1} / R_c - I_v$$

Thus, provided that  $\beta_1$  is very much greater than 1 and does not vary greatly with the voltage drop across  $Tr_1$ , and  $I_v$  is very much less than  $I_L$ , then  $I_L$  is approximately limited to a value:

$$V_{r1} / R_c [R_2 / (R_1 + R_2)]$$

In order that a range of constant currents may be provided the

circuit of Fig. 3 must be rearranged in such a way that the voltage developed across  $R_c$  is directly proportional to  $I_L$ . Fig. 4 shows such a rearrangement. Whereas, in Fig. 3,  $R_c$  was effectively in the emitter line of  $Tr_1$ , it is now effectively in the collector line of  $Tr_1$ . The currents  $I_{b1}$  and  $I_v$  do not now flow through  $R_c$  and the constant output current,  $I_o$ , is given exactly by the expression:

$$I_o = (V_{r2} / R_c) [R_3 / (R_3 + R_4)].$$

In this circuit, should the constant current fall below the value:


$$(V_{r2} / R_c) [R_3 / (R_3 + R_4)]$$

the "current" difference amplifier will lose control of  $Tr_3$  base current to the "voltage" difference amplifier. In this event, the output voltage will be adjusted to a value equal to:

$$R_v \cdot (V_{r1} / R_k) - I_L R_c$$

and when the output is open circuited ( $I_L$  becoming zero) will be limited to a value  $R_v \cdot (V_{r1} / R_k)$ .

Fig. 5 is a combination of Figs 3 and 4 and includes the addition of switch  $S_1$  called the "mode" switch. With the mode switch in

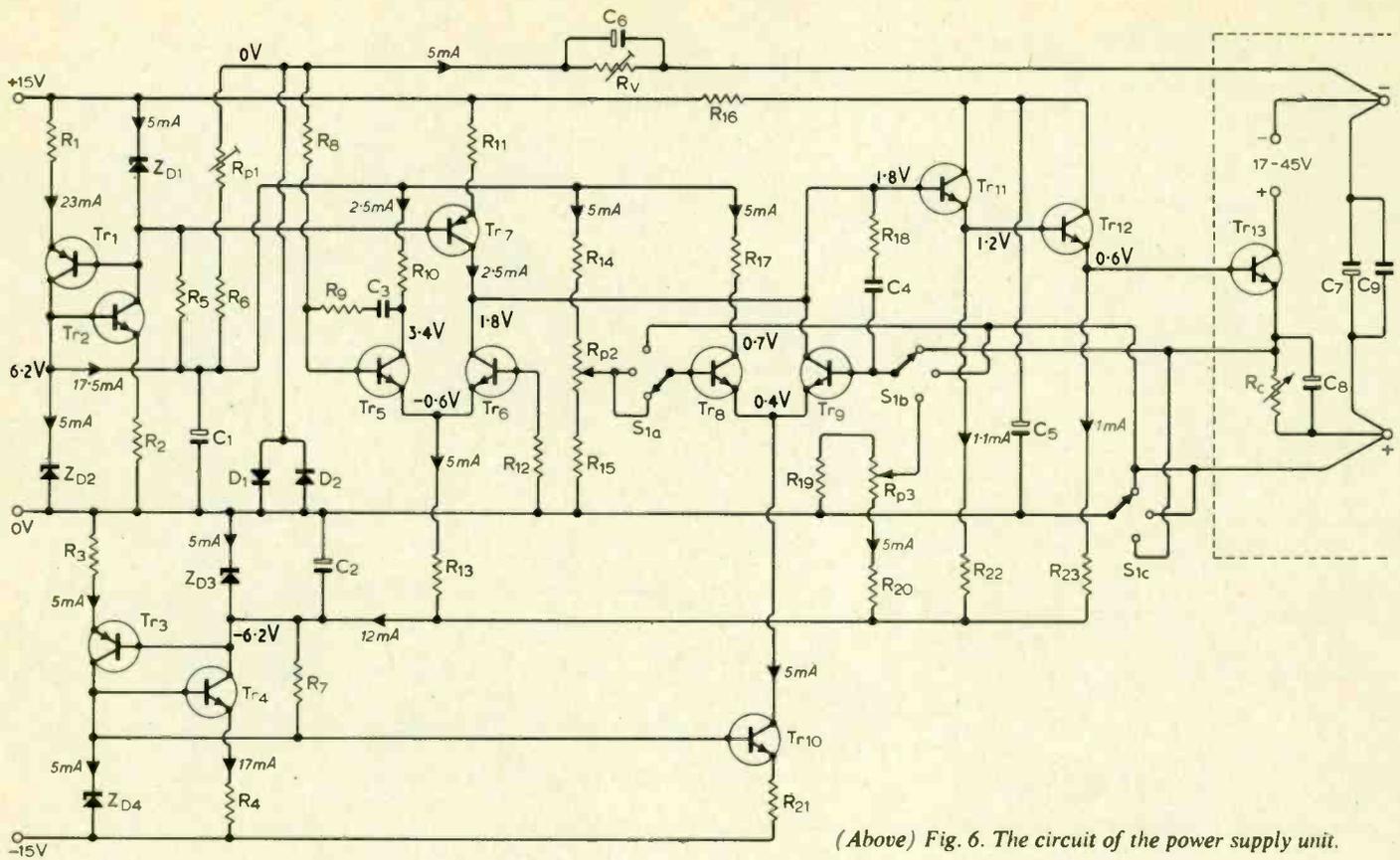

(Above) Fig. 6. The circuit of the power supply unit.

position 1 the output voltage is stabilized and the output current limited.

$$V_o = R_v \cdot (V_{r1}/R_k)$$

$$I_L = (V_{r1}/R_c)[R_2/(R_1 + R_2)] \cdot (\beta/\beta_1 + 1) - I_v$$

where  $I_v = (V_o + V_{r1})/(R_v + R_k)$

and  $V_o = R_v \cdot I_L$  is less than  $V_o$

With the mode switch in position 2 the output current is kept constant and the output voltage limited.

$$I_o = (V_{r2}/R_c)[R_4/(R_3 + R_4)]$$

$$V_L = R_v(V_{r1}/R_k) - I_o \cdot R_c$$

where  $I_o = V_L/R_L$ , is less than  $I_o$

Fig. 6 shows the electronic stabilizing circuitry of the power supply, as illustrated in simplified form in Fig. 5. The principle of operation is precisely as previously described, but with a considerable amount of circuit sophistication to improve the performance. The transistor pair,  $Tr_5$  and  $Tr_6$ , is the voltage difference amplifier and the transistor pair  $Tr_8$  and  $Tr_9$  is the current difference amplifier. The common collector load of  $Tr_6$  and  $Tr_9$  is made to appear very high by employing a constant current source, provided by  $Tr_7$ , instead of the usual resistor. Similarly, the emitter load of the current difference amplifier is replaced by a constant current source, provided by  $Tr_{10}$ . When switching from the voltage stabilizing mode to the constant current mode the emitter voltages of  $Tr_8$  and  $Tr_9$  vary from +0.4 V to -1.6 V, a change of 2 V. As it is desirable to keep the emitter current at the same value in either mode (for balanced operation of  $Tr_8$  and  $Tr_9$ ), this could have been achieved by switching in alternate values of emitter resistor. However, providing a constant current source was considered the better (if not cheaper) solution.

The two major reference voltages,  $V_{r1}$  and  $V_{r2}$ , are provided by the zener diodes,  $ZD_2$  and  $ZD_3$ . The currents through these two zener diodes are kept constant because the collector currents of  $Tr_1$  and  $Tr_4$  are constant by design as are the currents flowing away from the diodes. The additional zener diodes used in the reference voltage circuits,  $ZD_1$  and  $ZD_4$ , provide stable voltages to the bases of the transistors  $Tr_7$  and  $Tr_{10}$ , which, together with their respective emitter resistors,  $R_{11}$  and  $R_{17}$ , determine the values of the constant currents provided to the collectors of  $Tr_6$  and  $Tr_9$  and the emitters of  $Tr_8$  and  $Tr_9$ , as previously described.

The preset resistors,  $R_{p1}$ ,  $R_{p2}$  and  $R_{p3}$ , allow for accurate setting

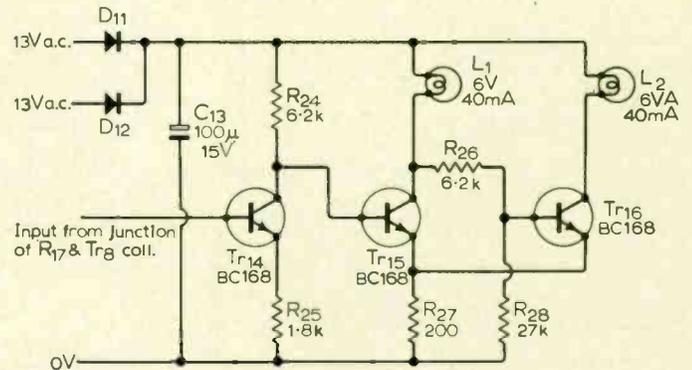


Fig. 7. Overload indicator circuit.

of the voltage, current limiting and constant current ranges.

The silicon diodes,  $D_1$  and  $D_2$ , prevent the voltage on the base of  $Tr_5$  from swinging beyond  $\pm 0.6$  V safeguarding the transistor from possible surges in the output voltage.  $C_6$  reduces the value of  $R_v$  to alternating signals increasing the loop gain of the amplifier and thus reducing the ripple content of the power supply. The capacitors,  $C_3$  and  $C_4$ , reduce the loop gain of the amplifier at high frequencies, preventing instability. As a result the output impedance of the power supply rises from about 0.01  $\Omega$  at 1 kHz to 0.03  $\Omega$  at 20 kHz.

It was found necessary to include the resistors  $R_5$  and  $R_7$  because it was discovered that the two reference voltage circuits were not self-starting. Should trouble of this nature still be encountered, a more positive solution is to connect a resistor between the zero voltage line and the negative end of  $ZD_1$  (or the zero voltage line and the positive end of  $ZD_4$ ) dispensing with  $R_5$  (or  $R_7$ ). The value of the resistor should be such that the current flowing through it is of the order of 1 mA. This will, naturally, degrade the performance of the reference voltage circuit, but not very seriously.

An additional feature of the power supply is the provision of a current or voltage overload indicator. The circuit of the indicator is shown in Fig. 7. In the voltage stabilized mode, with no current limiting, the collector voltage of  $Tr_8$  is a little above zero volts with the result that lamp  $L_1$  will be normally lit. When current limiting takes place the collector voltage of  $Tr_8$  rises to about 3 V, which is sufficient to turn lamp  $L_1$  off and lamp  $L_2$  on, indicating a current overload. In the constant current mode the operation of the indi-

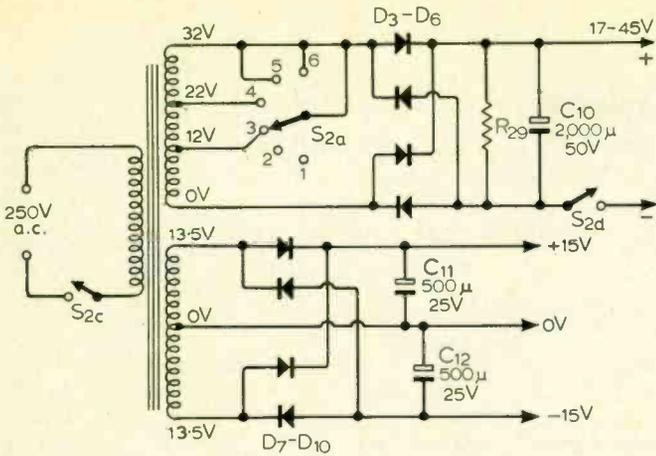


Fig. 8. The d.c. supply circuits.

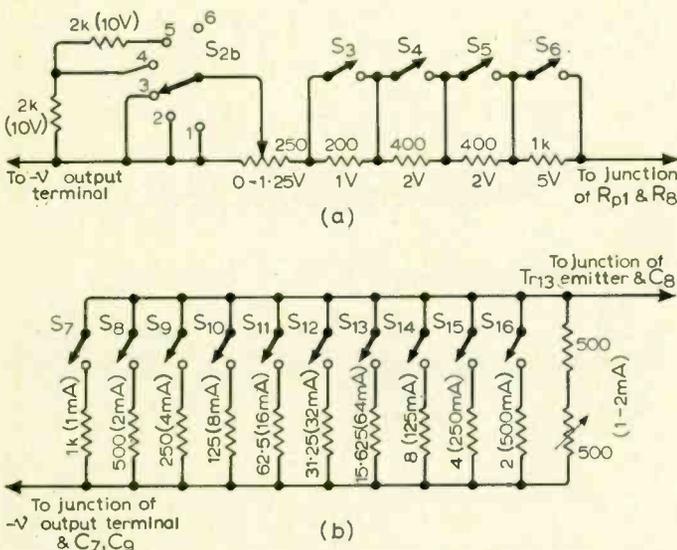



Fig. 9. (a) Construction of  $R_v$ ; (b) Construction of  $R_c$ .

cator circuit is reversed.  $L_2$  is normally on, indicating a constant current output, and goes off,  $L_1$  coming on, when the output current falls below the "constant" value, indicating voltage limiting. Thus, together with the position of the mode switch, the lamps  $L_1$  and  $L_2$  provide an indication of the operating conditions of the power supply. The voltage supply for the circuit of Fig. 7 is taken directly from the two 13.5 volt a.c. tappings on the mains transformer.

Fig. 8 shows the circuit diagram of the two voltage supplies. A word of explanation is necessary about the OFF/ON-Voltage Select switch,  $S_2$ . The two wafer banks,  $S_2(a)$  and  $S_2(b)$  (see Fig. 9(a) are self-explanatory, save the  $S_2(a)$  should be a break-before-make wafer and  $S_2(b)$  a make-before-break wafer.  $S_2(c)$  and  $S_2(d)$  are two halves of a mains ON/OFF switch operated by the 6-way rotary switch. The two halves are open in position 1 and closed in positions 2 to 6. The OFF/ON-Voltage Select switch provides the following functions:

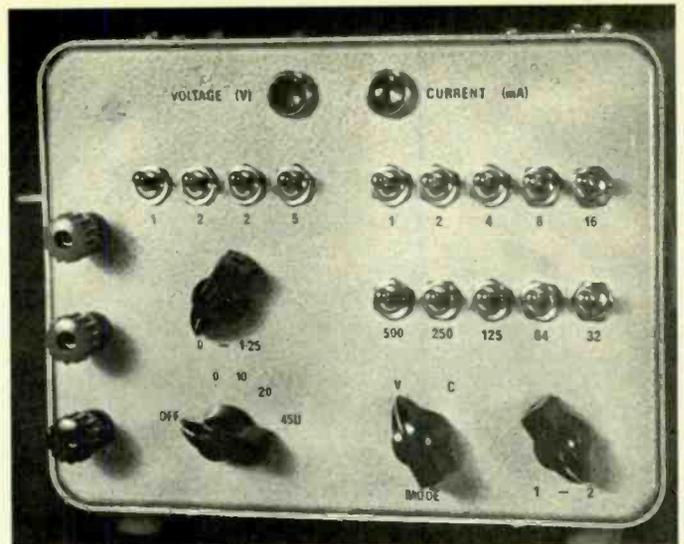- (1) All supplies off. (2) Stabilizer circuitry on—unregulated voltage supply off. (3) All supplies on—unregulated voltage output 17 V max. —0 to 11.25 V stabilized output available. (4) Ditto Position 3 except that unregulated voltage output 31 V max.—stabilized voltage output 10 to 21.05 V. (5) Ditto Position 3 except that unregulated voltage output 45 V max.—stabilized voltage output 20 to 31.25 V. (6) Unregulated output voltage of 45 V available at output terminals.

The inclusion of position 2 can be better understood by considering what happens when the power supply is switched off. If the



Front panel of the completed prototype.

### Specification

- Voltage ranges:** 0 to 30 V in switched steps of 1 V, plus 0 to 1.25 V fully variable.
- Current ranges:** 1 mA to 1 A in switched steps of 1 mA, plus 1 to 2 mA fully variable.
- Voltage limiting:** Operative on stabilized current output; limits voltage across the external load from 0 to 30 V.
- Current limiting:** Operative on stabilized voltage output; limits output current from 1 mA to 1 A.
- Setting accuracy:** 1% on all switched voltage and current ranges.
- Stability:** 10% mains variation—less than 0.1% on all voltage and current ranges.  
Voltage output—no load to full load—less than 0.1%.  
Current output—0 to 30 V across load—less than 0.1%.  
Temperature variation—dependent upon temperature coefficient of zener diodes.
- Output Impedance:** (Voltage stabilized mode—no current limiting) 0.01  $\Omega$  at 1 kHz to 0.03  $\Omega$  at 20 kHz.
- Voltage ripple:** (Voltage stabilized mode) 2 mV peak-to-peak on full load.

power supply is operating with the OFF/ON-Voltage Select switch in position 3, the output voltage will be determined by the position of the four toggle switches and the variable control. On switching to position 2, the unregulated voltage supply is switched off and—depending on the stabilized output voltage set, the size of the external load and the reservoir capacitor,  $C_{10}$ —the voltage provided by the unregulated supply will stay above the value of the stabilized output voltage for a short time. However, the stabilizing circuitry is still on so that the stable output voltage,  $V_o$ , will be maintained until the voltage across  $C_{10}$  falls below a value a few volts greater than  $V_o$ . If the stabilizing circuitry was switched off at the same time as the unregulated supply, it would be quite possible for the voltage at the output terminals to rise, for a short time, above the value  $V_o$ . As an extra precaution,  $S_2(d)$  is included in the negative line of the unregulated supply making it impossible for an output voltage to appear at the terminals when the OFF/ON-Voltage Select switch is finally turned to position 1. Including position 2 also ensures that the stabilizing circuitry is operating before the unregulated supply is switched on, again preventing a possible surge in the output voltage should the stabilizing circuitry fail to control the output level immediately.

Fig. 9(a) shows the construction of  $R_v$  as used in the prototype power supply. The sensing current,  $I_v$ , flowing in the voltage feedback line was designed to be 5 mA. Thus the resistance of  $R_v$  is 200  $\Omega$ /V.

Fig. 9(b) shows the construction of  $R_c$ . For current limiting and the constant current supply, the voltage across  $R_c$  is stabilized at 1 V

(it is, in fact, a little higher than this when current limiting because the current flowing through the external load is fractionally lower than that through  $R_c$ ). The limiting and constant current values are thus determined by dividing 1 V by  $R_c$ . Thus  $I_L$  and  $I_o$  equal  $1/R_c$ . Switching the ten individual values of  $R_c$  in and out provides a range of currents from 1 mA to 1 A. An additional fully variable range from 1 mA to 2 mA is provided by a wire-wound variable resistor connected in series with a fixed one of the same value.

The methods of constructing  $R_v$  and  $R_c$  have already been discussed but a word about the components may prove useful. 1%, high-stability, carbon resistors of 1 watt rating were used for all the standard values of resistance. The "odd" valued resistors were 1%, wire-wound, 1 watt types, available, to order, from the Planet Instrument Co., 25(E) Dominion Avenue, Leeds, 7.

The mains transformer used was a Douglas, type MT.3AT with rewound secondaries. The original secondary, 0-30 V, multi-tapped and rated at 2 A was removed, carefully noting the number of turns per volt. One secondary, providing 0-12-22-32 V at 1 A, was wound using 19 s.w.g. enamelled copper wire; the other secondary was wound using 33 s.w.g. enamelled copper wire to provide 13.5-0-13.5 V at 50 mA.

The two transistor pairs,  $Tr_5$  and  $Tr_6$ , and  $Tr_8$  and  $Tr_9$ , of the "voltage" and "current" difference amplifiers were mounted in individual heat-sinks, constructed from  $\frac{1}{2} \times \frac{1}{4}$ " brass bar, to improve the long-term stability of the power supply.

The series regulator transistor,  $Tr_{13}$ , was mounted on a large, finned heat-sink attached, on the inside, to the back of the power supply cabinet.

### Components List

#### Resistors

The prefix  $R$  and the suffix  $\Omega$  has been omitted from components in the list below for clarity.

1-160	2-1.1 k	3-1.1 k	4-240
5-560	6-1.1 k	7-560 k	8-680
9-1.1 k	10-1.1 k	11-1.5 k	12-680
13-1.1 k	14-1 k	15-180	16-270
17-1.1 k	18-1.1 k	19-180	20-1 k
21-820	22-6.8 k	23-6.8 k	24-6.8 k
25-1.8 k	26-6.2 k	27-200	28-27 k
29-2.2 k, 1 W, 10%			

all 0.25 W, 5%, carbon except where shown

p1-200	p2-50	p3-50
--------	-------	-------

wirewound preset potentiometers

#### Capacitors

The prefix  $C$  has been omitted in the list below

- 1-25  $\mu$ F, 12 V working electrolytic
- 2-25  $\mu$ F, 12 V working electrolytic
- 3-0.001  $\mu$ F disc ceramic
- 4-0.001  $\mu$ F disc ceramic
- 5-8  $\mu$ F, 25 V working electrolytic
- 6-8  $\mu$ F, 25 V working electrolytic
- 7-50  $\mu$ F, 50 V working electrolytic
- 8-25  $\mu$ F, 12 V working electrolytic
- 9-0.1  $\mu$ F, 250 V working polyester
- 10-2,000  $\mu$ F, 50 V working electrolytic
- 11-500  $\mu$ F, 25 V working electrolytic
- 12-500  $\mu$ F, 25 V working electrolytic
- 13-100  $\mu$ F, 25 V working electrolytic

#### Semiconductors

The prefix  $Tr$  has been omitted in the list below

1-2N4289	10-BC 168
2-BC 168	11-BC 168
3-2N4289	12-BC 168
4-BC 168	13-2N3055†
5, 6-BC 109*	14-BC 168
7-2N4289	15-BC 168
8, 9-BC 109*	16-BC 168

\* matched pairs

† must have a minimum gain of 30 at 1A

The prefix  $ZD$  has been omitted in the list below

1-4.3 V, ZB4.3	3-6.2 V, ZB6.2
2-6.2 V, ZB6.2	4-4.7 V, ZB4.7

all 250 mW. S.T.C. type numbers shown

The prefix  $D$  has been omitted in the list below

- 1, 2-any silicon diode
- 3 to 6 any diode rated at 1 A, 100 p.i.v.
- 7 to 12-any diode rated at 100 mA, 40 p.i.v.

Mains Transformer: secondaries

- 0-12-22-32 V at 1 A
- 13.5-0-13.5 V at 50 mA
- (see text)

6-pole, 6-way rotary switch plus mains ON/OFF switch (see text)

3-pole, 3-way rotary switch


Cabinet type-Y. G. W. Smith and Co. Ltd.

Resistors and toggle switches for constructing  $R_v$  and  $R_c$  (see text)

Two 6 V, 40 mA bulbs

Plugs, sockets, Veroboard, heatsink ( $4" \times 4\frac{5}{16}"$ ), etc.

## H.F. Predictions—April

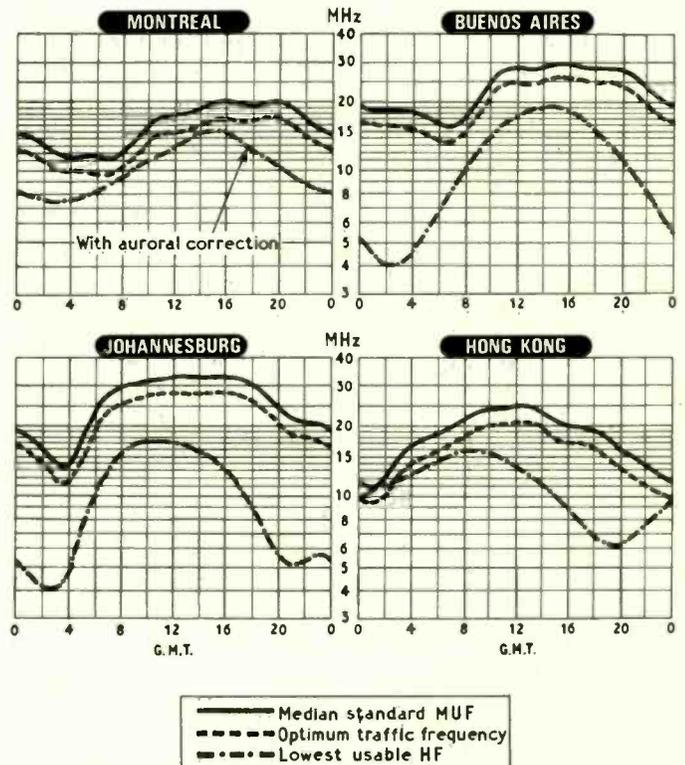

The predictions are based on an ionospheric index of 96, the corresponding sunspot number being 83. These are slightly lower than the observed values for 1968 and 1969.

The trans-equatorial paths have their highest MUFs during equinox months and conditions should be good above 20MHz. Evening fading is relatively independent of season and cycle on the South African route but is worse during this period on others. The Far East will have weak unstable signals from midnight to 09.00 G.M.T. and North America will be liable to several days of weak signals from 06.00 to 16.00 G.M.T. The MUFs shown apply to both directions of the route while LUFs are for reception in the U.K. only.

# Low-angle Radiation

## Describing how long-distance propagation can be improved by exploiting the natural terrain

By L. A. Moxon,\* B.Sc., M.I.E.E.

Since first hearing transatlantic morse signals in the early years of short-wave radio, the author has been fascinated by communication over long distances using low-power. This interest has been maintained by the frequent emergence of new and intriguing problems. In particular, by the discovery, when resuming amateur activities after the war from a new location, that communication was easy with Australia but almost impossible with anywhere else. Further, when Australian signals were at their best South Americans were usually weak or absent, clearly inconsistent with the usual theory of long-distance propagation by means of multiple earth-ionosphere reflections.

These mysteries were resolved by a process which stressed not only the importance of low-angle radiation, but also the need for more information on what constitutes a "low angle". A study of two medium-length east-west paths<sup>1</sup> has concluded that for these paths angles as low as 1 deg. are desirable, but for the most part quantitative data is in short supply.

Recent speculation<sup>2</sup> has suggested dramatic possibilities from the use of very low angles of radiation, perhaps even less than 1 deg., and it was with somewhat similar ideas in mind that a low-power (1W output), transistor s.s.b. transceiver was designed and built, light enough to be carried complete with aerial system up steep mountainsides.

\*Amateur station G6XN

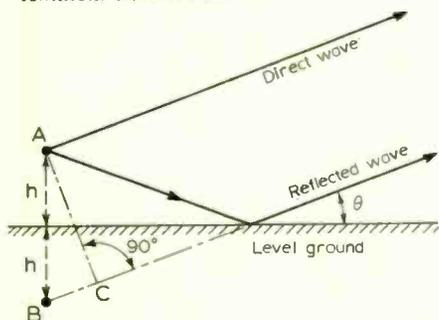


Fig. 1 When a horizontal aerial is erected at a height  $h$  over level ground, its image  $B$  is an antiphase. The direct and reflected waves are in phase at a distant point when  $BC = \lambda/2$ , i.e. when  $2h \sin \theta = \lambda/2$  where  $h$  is the angle of radiation.

It was hoped in this way to achieve efficient radiation at the desirable low angles whatever these might be, by exploiting natural ground features. An earlier exercise, complementary to this, was aimed at maximising the low angle radiation obtainable from a flat site with limited aerial heights, accepting the inevitable low efficiency and consequent need for relatively high power, to produce a given signal level.

On the basis of these experiments, and such information as can be found in the literature, solutions have been sought to the following problems:

(a) How to select the best site for an h.f. aerial, for communicating with low power over distances of 3,000 miles or more.

(b) How to make the best use of a given site.

The discussion which follows does not necessarily apply to commercial h.f. circuits for which 24-hour availability is likely to be more important than good results over shorter periods.

### Avoidance of cancellation

The difficulty of achieving low angles of radiation arises from cancellation of the direct signals by the ground-reflected wave as shown by Fig. 1. This can, in principle, be prevented by one or more of the following procedures:

(a) Using a high mast so that the path difference for the two rays is  $\lambda/2$ , which then add in phase giving 6dB gain relative to free-space propagation. For 14 MHz and a radiation angle of 1 deg. this requires a mast height of 1,000ft, which is unlikely to be popular with the neighbours.

(b) Using a steep ground slope, as in Fig. 2. If the slope is 45 deg. a height of only 25ft is required at 14MHz to bring the direct and reflected waves into phase. This height is not critical and only 3dB is lost by dropping the height to 12ft 6in. or raising it to 3ft 6in. Moreover, there is the advantage of a single broad lobe in the vertical plane, whereas a large height as in Fig. 1 produces an interference-pattern with lobes and nulls alternating at 1 deg. intervals. The best angle of radiation is not necessarily always the lowest, and the optimum may well coincide with a null. So far all this is well known, but most references overlook the fact that the slope has to end somewhere. As first pointed out by Norton and

Omberg<sup>3</sup> this has important consequences, of which more later.

(c) With vertical polarization and perfectly-conducting ground, the phase of the reflection coefficient is reversed and efficient low-angle propagation is achieved independently of aerial height. This can be approximated by laying down a conductive earth-mat of sufficient extent. A beam aerial designed on this principle<sup>4</sup> has been found to operate under radio conditions which render conventional equipment useless. The installation uses an earth mat 1,800ft long and 832ft wide, containing 25 miles of copper wire. Such a system is obviously beyond amateur resources, but sea-water is sometimes available and is a good-enough conductor to act as a useful (though not ideal) substitute.

(d) With vertical polarization and imperfect ground there is a "pseudo-Brewster angle", below which the phase of the reflection coefficient is reversed, so that for low angles and moderate or large aerial heights there is little to choose between vertical and horizontal polarization. In the vertical case, however, the reflection coefficient is less than unity so that cancellation is imperfect and some low angle radiation takes place, however, low the aerial. This principle has been exploited to produce a very effective, cheap and easily-erected beam for 7MHz, as described later.

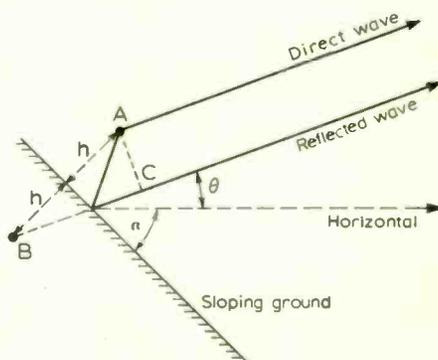


Fig. 2 With the aerial at a height  $h$  above ground sloping at an angle  $\alpha$ , the direct and reflected waves are in phase when  $2h \sin(\alpha + \theta) = \lambda/2$ . For small values of  $\theta$  this becomes  $2h \sin \alpha \approx \lambda/2$ . This diagram is identical with Fig. 1 except for rotation through the angle  $\alpha$ , and the increased ground angle.

**Fresnel zones**

Figs. 1 and 2 are oversimplified to the extent that reflection takes place not from a point but from a Fresnel zone which is defined by the fact that reflections from all parts of it tend to add in-phase.

Formulae for the sizes and required degrees of flatness of these zones are to be found in the literature<sup>3,5</sup>. The size of the zone for the previous example based on Fig. 1 is very large, the near edge being at 2½ miles range, and the far edge (ignoring earth curvature) at 85 miles. As the height is reduced and the angle of maximum radiation relative to the ground increases, the corresponding Fresnel zone contracts with the far edge moving in roughly as the inverse square of the angle.

For the example based on Fig. 2 the "near edge" is 25ft behind the aerial and the far edge only 175ft down the slope. The shape is elliptical, its effective width being roughly 5 times the aerial height, and the ground need not be particularly flat. Obstacles with dimensions up to about a quarter of the aerial height are acceptable. Very long distances to the far edge (as in the first example) are reduced somewhat when due allowance is made for earth curvature<sup>3</sup>.

**Double reflections**

Discussion so far has been concerned with situations which may seem ridiculous, since amateur resources have been implied and angles of 1 deg. assumed. Even if the angle is increased to 5 deg and a loss of 3dB accepted, the Fig. 1 situation would require a 100ft mast, and bottomless slopes exist only in mythology or mathematical fiction.

In practice, however, the steep slope is quite likely to sweep down like the Mountains of Mourne, or even Mull where the author conducted some experiments, to the sea, as illustrated by Fig. 3. A flat plain, however, is also a possibility and will serve equally well for the next part of this discussion.

It will be seen that there are now four waves to be considered, including two single and one double reflection, and if all these can be made to add in phase there is a possibility of obtaining not 6 but 12dB gain compared with free-space propagation. This may appear complicated, but resolves quite simply into a practicable combination of the two situations which have just been criticised as absurd; 6dB gain being obtained from each of them.

For numerical consistency with the previous examples there is required only a sloping patch of mountainside extending for at least 25ft above and 175ft below the aerial. It should be centred on 1,000ft altitude with an unobstructed view of the sea, of which the nearest visible point should be not more than 2½ miles away.

Since the mountain is, in effect, being used as a "tall mast", however, this entails the penalty of a multiple-lobe radiation pattern in the vertical plane (as in the case of Fig. 1 with a tall mast). So that if the appropriate angle of radiation happens

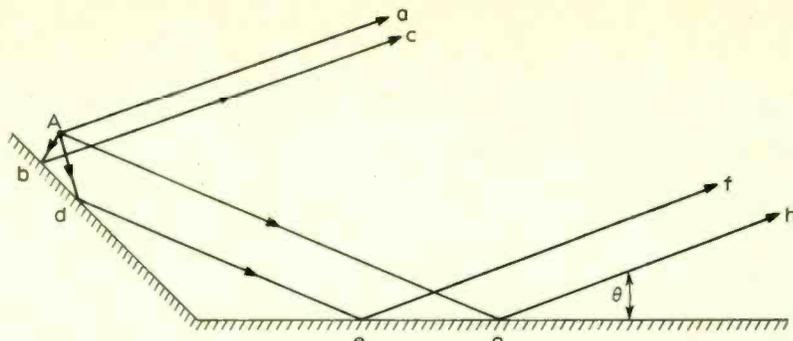


Fig. 3 Ground sloping down into the sea. The direct wave Aa, foreground reflection Abc, distant reflection Agh, and double reflection Adef add in phase if  $\theta$  is small,  $hg \approx \lambda / (4 \sin \theta)$ ,  $h_s \approx \lambda / (4 \sin \theta)$ , these being the heights of A above ground and sea respectively.

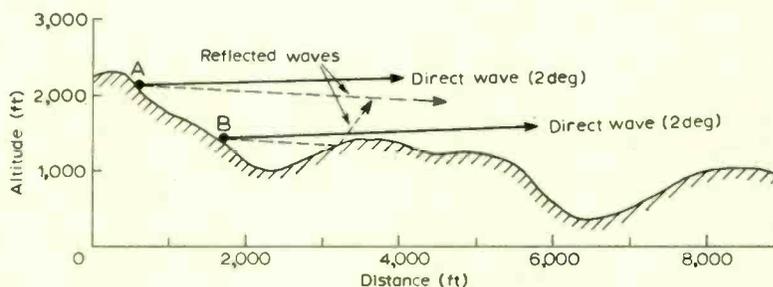


Fig. 4 Typical ground profile for mountainous country. Distant low-angle reflections are non-existent for transmitter at B, and probably unimportant (due to break up of Fresnel zones) for transmitter at A. In both cases low-angle reflections (not shown) are obtained from the foreground. (Isle of Mull, grid ref. NM 568332 bearing 104 deg.)

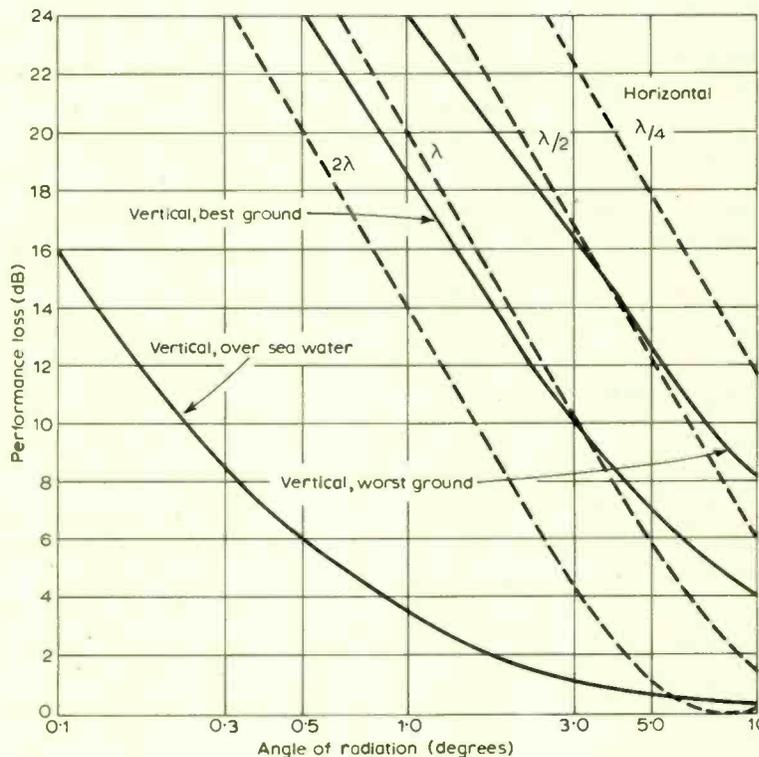


Fig. 5 Comparison of short horizontal and vertical radiators at h.f. assuming flat open country. "Zero loss" occurs with in-phase addition of the direct wave and a reflected wave of equal amplitude. Aerial heights are indicated in wavelengths for horizontal polarization (dotted curves). Vertical polarization curves are calculated for low height and a frequency of 7MHz; performance deteriorates slightly as frequency increases.

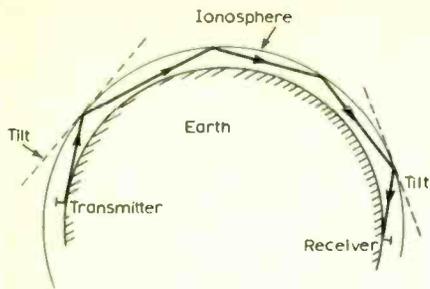


Fig. 6 Chordal hop. At the first and last reflection points, the ionosphere behaves as if tilted slightly towards the terminals. For tangential radiation (i.e. zero deg.), and tilt, however small, prevents a return to earth until a tilt of opposite sign occurs. (Ionosphere not to scale.)

to be not 1 deg. but 2 deg. signals will be almost completely cancelled and even if the operator were aware of this he would scarcely relish the idea of moving the aerial down 500ft to put the matter right. He might even prefer to sacrifice the 6dB gain obtainable from the sea reflection. But at this point it becomes appropriate to consider the situation sketched in Fig. 4.

Locations such as this are usually easier to find than those corresponding to Fig. 3 and it will be noticed that the distant reflecting areas are either blocked off by the foreground or badly broken up, thus failing to meet the required specification for the Fresnel zones. If the distant reflections are sufficiently reduced, Fig. 2 becomes after all a valid representation for the practical case and low-angle radiation should then be obtained with a gain of 6dB relative to free-space propagation.

Neglecting diffraction, this would be true for angles of elevation down to zero, assuming an aerial height of, say,  $0.7\lambda$  above any 45 deg slope 200ft in extent. For a 15 deg slope an aerial height of  $2\lambda$  and an extent of 1,800ft would be needed for the same result, but these dimensions are not critical and could probably be halved without serious loss of performance.

**Polarization**

With sloping ground horizontal polarization is preferable, because in the vertical case efficient use of the reflected wave is usually prevented by the Brewster-angle effect, tilting of the image, or both. In the case of flat ground, the best choice of polarization depends on the available aerial height, soil characteristics, and frequency.

Fig. 5 has been calculated from handbook data for vertical aerials above various types of ground<sup>9</sup> and on the basis of Fig. 1 for horizontal aerials at various heights. This provides a rough comparison between different aerials for given angles of radiation and soil conditions assuming, in the vertical case, heights low enough for the effect illustrated by Fig. 1 to be negligible.

In using these curves two points should be noted. Where horizontal polarization appears to be better, equally good results could usually be obtained with vertical aerials by raising them to the same height. The vertical aerial is then likely to be the more difficult of the two to support and

feed. On the other hand height is usually the main problem in aerial construction. Horizontal supporting wires for vertical elements can be used to provide end-loading which allows considerable reduction of vertical length and, therefore, height.

Although the useful energy radiated per element is rather small, it is often easier at the lower frequencies to construct, say, a 5- or 10-element vertical array in this manner than to put up a horizontal dipole at a height which would give comparable performance.

Fig. 5 shows the possibility of radiation at 0.5 deg. elevation with a loss of only 6dB by using vertical aerials surrounded by sea water, which may appeal to amateur enthusiasts with portable transceivers and a preference for paddling rather than mountain climbing.

**Experimental results**

The good results at 14MHz in the direction of the long path to Australia mentioned earlier, were attributable to a steep ground slope (22 deg.) in that direction. Aerial height was only 23ft which was adequate for the down-slope direction, but resulted in poor propagation in the opposite direction even for short ranges.

The use of a full-wave dipole, later backed by reflectors, produced a narrow azimuthal pattern, thus discriminating against directions other than towards Australia. Comparative tests were carried out over several years with the cooperation of numerous Australian stations plus a local amateur (G3DVM), whose location was more conventional, his aerial being located at a height of  $\lambda/2$  over flat ground.

Comparative reports, allowing for power differences and assuming 6dB per S-point, usually indicated an advantage of about 8dB in favour of the author's location and aerial system. Referring to Fig. 5, the loss for 6 deg. elevation at G3DVM would be 10dB, and a loss of 2dB would be applicable to G6XN for the same angle, which would, therefore, be the "most probable". It was noticed, however, that quite often the path remained open longer at G6XN with signal-strength differences reaching 20dB or more. This would be consistent with radiation angles in the region of 1-2 deg. On other occasions the advantage in favour of G6XN almost disappeared,

suggesting angles in excess of 10 deg.

It is interesting to note that good conditions on the long path to Australia occur when the path is mainly in darkness, and complementary ionospheric tilts might be expected at each end of the circuit due to the darkness-daylight transition. This leads to the chordal hop mode of propagation first described by Albrecht<sup>6,7</sup> depicted in Fig. 6, in which waves travel by successive F-layer reflections without intermediate ground reflection.

Note that the lower the angle at which the ray strikes the ionosphere, the less likely it is to be reflected back to earth. Similar modes of propagation occur frequently on other long-distance paths especially north-south paths<sup>8</sup>. Because of reduced D-layer absorption and ground-reflection losses, these modes tend to produce very high signal levels over very long paths.

Tests with the portable s.s.b. transceiver have been carried out from steep ground slopes, using an inverted-V dipole having its centre propped up to a height of 20-25ft and about 1W of peak r.f. power. Attempts to communicate with Australia over the long path were made from six different locations having features typified by Figs. 3 or 4, with success in every case. The inverted-V dipole when erected over ground sloping at angles of 30-40 deg. appeared roughly equivalent to a Quad aerial at the home location erected at a height of 50ft, although direct comparison was not possible.

This result is consistent with the previous estimate of a 6-deg. angle of radiation since, from Fig. 5, a loss of  $7\frac{1}{2}$ dB would be expected for the Quad despite its greater height, but this would be offset by an estimated 6dB or so of aerial gain. Insufficient results have so far been obtained to establish the practical advantage, if any, of using distant as well as foreground reflections on the lines of Fig. 3.

These tests were conducted in the 14MHz amateur band, but other contacts were made with Australia on 21MHz (short path), and with North America on 28, 21 and 14MHz. In these cases also, the combination of portable dipole plus steep ground slope appeared roughly comparable with the home "Quad". This was judged by the degree of difficulty in establishing contacts.

Fig. 7 shows one of the two "bays" of a

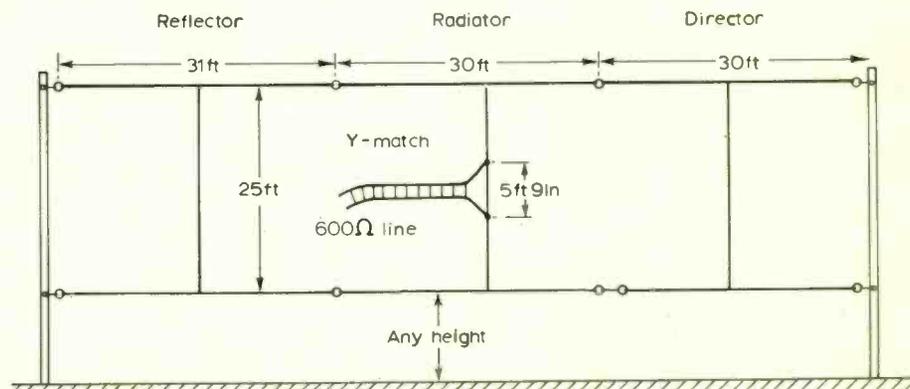


Fig. 7 Low-angle aerial for 7MHz. Height not critical. Reflector and director tunable, by adjusting length of verticals or of the lower horizontal wires. Dimensions approximate.

6-element 7MHz beam using short end-loaded vertical elements with the lower ends about 2ft from the ground. Results over the long path to Australia included good DX contest scores and, on one occasion resulting from failure of the main transmitter, two contacts with only 5 watts of peak r.f. power (s.s.b.). Fig. 5 suggests that for an angle of 6 deg., a vertical array having 6dB gain and located over average ground should be roughly equal in low-angle performance to a dipole at a height of  $1\frac{1}{2}\lambda$  or a Quad at  $\frac{3}{4}\lambda$ .

Relative to typical aerials at a height of 50ft the vertical array would, therefore, be expected to do much better at 7MHz and be roughly equal at 14MHz; the latter estimate has proved to be over-optimistic since results, though good on 7MHz, averaged about 6dB down relative to the Quad at 14MHz.

### Conclusion

From most locations it is difficult with simple aerials to achieve efficient radiation at angles below 5 or 10 deg. Attempts to reduce the angle lead to rapid escalation of cost and practical difficulties, and the difficulty of making cost-effective decisions is aggravated by lack of such information as how low an angle is desirable, and for what percentage of the time. On the other hand, given freedom in choice of location, a low angle of radiation is readily achievable by exploitation of natural ground features and is within the means of amateurs equipped with portable apparatus, and a set of Ordnance survey maps.

Much could also be learned from comparative tests from a number of fixed locations having different ground characteristics and various types of aerial.

### REFERENCES

1. N. F. Utlaut, "Effect of Antenna Radiation Angles upon H.F. Radio Signals Propagated over Long Distances." *Journal of Research of the National Bureau of Standards*, Vol. 65D No. 2, p. 167 March/April, 1961.
2. "Technical Topics," *Radio Communication*, p. 394, June, 1969.
3. K. A. Norton and A. C. Omberg, "The Maximum Range of a Radio Set," *Proc. I.R.E.*, Vol. 35, p. 17, 1947.
4. J. F. Ward, "A Low Delta, Surface Wave, Interferometer Array for High-Frequency Radio Communication," *Nature*, Vol. 205, p. 1062, March 13, 1965.
5. D. K. Bailey, R. Bateman and R. C. Kirby, "Radio Transmission at V.H.F. by Scatterers in the Lower Ionosphere," *Proc. I.R.E.*, Vol. 48, p. 1226, Oct. 1955.
6. H. J. Albrecht, "Further Studies on the Chordal-Hop Theory of Ionospheric Long-Range Propagation," *Archiv fur Meteorologie, Geophysik und Bioklimatologie*, Serie A, Vienna 1959 (Springer Verlag), p. 84.
7. H. J. Albrecht, "Investigations on Great-Circle Propagation between Eastern Australia and Western Europe," *Geophys. pura e applicata*, Vol. 38, pp. 169-180, 1957.
8. S. Stein, "The Role of Layer Tilts in Ionospheric Radio Propagation," *J. Geophys.*, Vol. 68, p. 217, 1958.
9. F. E. Terman, *Radio Engineers' Handbook*, pp. 700-709, McGraw Hill Book Company Inc., 1943.

## Radio Fire alarm


### Personal call-out system for firemen

Production techniques are not in general the concern of *Wireless World* but this month one is featured on our front cover. It shows, albeit in an artistic setting, a watchmaker's wheel which has been adopted by Pye Telecommunications Ltd to facilitate the production of the "microboards" used in the pocket receivers for a fireman's call-out system. The system, which is being adopted by the fire brigades in several areas, operates in the 142-174 MHz band. The transmitter carrier of the 25-W base station is frequency modulated by two signalling tones—one as a test call and the other for a fire call.

The pocket receiver, which measures  $12.7 \times 6.3 \times 2.5$  cm and clips in a breast pocket, has a built-in aerial and is powered by a rechargeable 9-V nickel-cadmium battery giving 30 hours operation. The receiver incorporates a battery economizer circuit which switches it on

for 0.5 sec and then off for 2.5 sec until the carrier is received and locks it on.

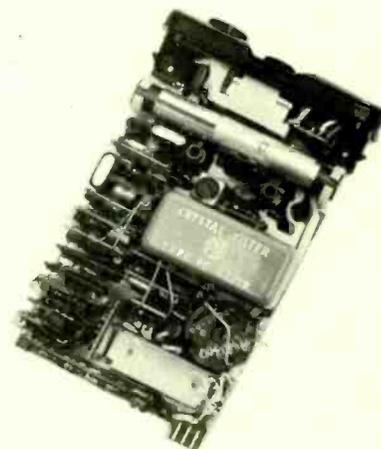Studs fitted to the receiver enable it to be inserted in a bedside battery charger. It remains fully operative while in the charger.



(Right) Chassis of the fireman's pocket receiver which has an operating range of between 5 and 8 km from the base station according to terrain.

(Below) The watchmaker's wheel in use at Pye's Cambridge works.



# Some improvements in the design of Class-B Audio Amplifier Circuits

by K. C. Johnson

A bewildering number of articles have appeared both in this journal and elsewhere describing class-B audio amplifiers using transistors. The reader might well think that all the possibilities had been thoroughly explored already. When, however, I started to build a new system recently I was surprised to discover just how many small improvements can be made even to a well-tried design. It is true that none of them is either overwhelmingly important or even really original, but taken together they make an appreciably better circuit and so seem to justify yet another article on this subject.

The amplifier from which I started was the Fairchild AF11, which was offered as a kit of semiconductor devices and a tested circuit, though it is no longer in production. The arrangement had been clearly derived from the pioneer circuit of Tobey and Dinsdale, but was brought up to date and much improved by the use of diffused silicon transistors throughout. The first stage was changed so as to use a complementary type of device, since these are now scarcely more expensive in the small sizes and allow some advantage to be gained in the feedback arrangements, but the final power stage still employed two identical devices.

My final circuit is shown opposite, and the various ways in which it differs from the more conventional arrangement will be described in turn.

## Earthing arrangements

Several writers have pointed out that it is an advantage to return the "dead" sides of the input, the feedback network, and the output all to the same power rail so as to avoid instability troubles. The first unusual feature of this circuit is that it is the *upper* rail which is chosen for this service rather than the lower one. One obvious advantage of this is that it allows the bootstrap line to be taken directly from the loudspeaker and so saves the need for a second electrolytic capacitor network. But there is a further advantage in that variations in the power supply voltage are much less important since there are no longer any large coupling capacitors bridging the supply rails. If the two rails are taken abruptly to the full working voltage, at switch-on for example, only the 40 $\mu$ F high-frequency bypass capacitor  $C_4$  carries any large current and

it is essentially just an extension of the power supply. The long time-constant at the base of  $Tr_1$  controls the charging rate of all the other capacitors and the maximum current in the loudspeaker is no more than 30mA.

In the same way this use of a common return rail and the absence of any signal capacitors bridging the power rails allows a considerable amount of ripple to be tolerated on the power-supply voltage so that power-pack requirements are eased. There are just four places in the circuit where signals change their reference from one power rail to the other, and in every case the collector junction of a transistor is used so that only the current flow is of importance and the voltage is relatively immaterial.

To keep the loudspeaker current surge within similar limits at switch-off it is only necessary to ensure that at least 1000 $\mu$ F of charged capacitor are left connected across the power rails. This enables the currents in  $Tr_1$  and  $Tr_2$  to be kept flowing so that the circuit is able to shut itself down at the rate determined again by the long time-constant at the base of  $Tr_1$ . This requirement will normally present no problem, but even if it is not met the surge generated will certainly be no worse than in most other circuits of this type.  $R_{16}$  serves to keep the circuit biased properly if the loudspeaker is disconnected whilst the power remains switched on.

The pre-amplifier for this circuit must also be arranged so that the positive rail is the earth and so that the output voltage measured this way changes smoothly when the power is switched.

## Middle rail voltage

In any circuit of this type the average voltage at the middle point between the output transistors must be set about half-way between the power rails so that equal output swings can be developed. The first-stage transistor is used at its full gain in this circuit for this purpose. The potentiometer formed by  $R_1$  and  $R_2$  sets a voltage on  $C_2$  which is applied through  $R_3$  to the base of  $Tr_1$ , while the actual average level is set on  $C_3$  by  $R_6$  and fed to the emitter. If these voltages do not correspond, the full power of the amplifier is available to correct the situation, with  $C_3$  ensuring that the action is stable.

Thus if slow variations of the supply voltage occur, or if the amplifier is used on different supplies, the middle voltage is always automatically adjusted so as to be close to the actual half-way value rather than remaining at some pre-set level. As a refinement the precise value of  $R_2$  can be set so that limiting of the output on overloading occurs symmetrically at the normal supply voltage, but if components of ordinary tolerance are used the loss of output swing if this is not done will be quite small.

## Transistor currents

In contrast to the above it is desirable that the levels of average current at which the various transistor stages work should remain comparatively constant when the power supply is altered. There is no reason to drive a stage with less current just because less voltage is applied, although it is true that a lower impedance loudspeaker system must be used if advantage is to be taken of the current available.

In the conventional form of circuit these standing currents are in fact stabilized in every stage except the second. The third improvement in this circuit is that the diodes  $D_3$  and  $D_4$  are added so as to control this stage also.

With the circuit shown the supply voltage can be reduced from 60V to as little as 18V and the full output current of 2A remains available at almost the full swing the voltage allows, without any adjustment. To match this the loudspeaker impedance required must be reduced from 15 $\Omega$  at the high voltage to about 4 $\Omega$  at the lowest. If the loudspeaker is not matched then some output is lost, since either the voltage or the current reaches its limit whilst the other one is less than maximum, but there is no other serious penalty if the mis-match is not worse than a factor of two or so.

## Cross-over current stabilization

Thermal runaway of the final transistors is not the problem with silicon devices that it was with germanium. Nevertheless the circuit has the resistor-diode networks  $R_{12} D_1$  and  $R_{13} D_2$  included between  $Tr_7$  and  $Tr_8$  to stabilize the cross-over current level more tightly. These resistors act to give a proportionate voltage for currents near the design value of 20mA, whilst the

diodes take over for currents greater than about 50mA so that the peak output capability is scarcely reduced at all.

Now it might be thought that non-linear networks of this kind would cause serious distortion—and arguments to this effect have indeed appeared in print—but consider what is actually happening. The signal being amplified leaves  $Tr_2$  as a collector current.  $Tr_4$  is arranged to supply a constant current and thus the signal is still in the form of a current when it arrives at  $Tr_5$  and  $Tr_6$ . It is amplified there and again at  $Tr_7$  and  $Tr_8$ , but at no point in these stages is there any sort of a load resistance. Thus the voltages are irrelevant, except in so far as small amounts of current can be lost since no system is ever perfect.

There is, however, an improvement of the thermal stability of the cross-over current by a factor of about five over the customary arrangement of linear resistors of about  $0.5\Omega$  at these positions, and less output swing is lost. Thus these networks are well worth having even though silicon devices have so much less leakage and much better stability anyway. The diodes used for  $D_1$  and  $D_2$  should be of germanium, so that they take over at about 250mV, and they must be capable of carrying the full output safely. Their reverse characteristics and switching speeds are clearly of little importance and Mullard type OA10 is suitable. The resistors can be of the ordinary small composition type, as they never have to carry more than perhaps 50mW of power at the most, and there is then no worry about their being inductive.

**Constant current transistor**

The transistor  $Tr_4$  has been added to serve as a constant current source, as has already been mentioned. It supplies the collector of  $Tr_2$  with about 2mA and draws this current from the loudspeaker side of  $C_8$  so as to

obtain the customary bootstrap action. The resistor  $R_7$  and capacitor  $C_6$  help to keep the current constant, whilst  $D_3$ ,  $D_4$  and  $R_{15}$  stabilize the value against variations of the supply voltage. The transistor for this position must be capable of withstanding half the maximum supply voltage but need have no other special features. The Fairchild type BC116, as used already in the first stage, meets the requirements.

In conventional circuits a simple feed resistor carries the current to  $Tr_2$  and the value used is usually no greater than  $5k\Omega$ . But the input impedance to  $Tr_5$  and  $Tr_6$  can easily rise to this same sort of value at the cross-over region, since the input impedances of the final transistors rise sharply at low currents and the value is directly multiplied by the current-gains of the driver stage devices. Away from cross-over these input impedances are very much lower, so that the effect is a fall in the value of the open-loop gain at cross-over. Put in figures we can say that the open-loop gain is multiplied by a factor of about 0.5 in this region.

Now the purpose of  $Tr_4$  is to force as much as possible of the signal current from  $Tr_2$  into the driver stage devices and so reduce this form of distortion. Since the effective resistance value obtained is in the region of  $100k\Omega$  the improvement is substantial despite the increase of the input impedance that results from the inclusion of  $R_{12}$  and  $R_{13}$ . The cost of the extra transistor required is comparatively small and in return we have obtained less distortion and better current stabilization in two stages of the amplifier.

**Voltage reference transistor**

The transistor  $Tr_3$  together with  $R_8$ ,  $R_9$  and  $C_5$ , determines the voltage used as a reference in the fixing of the value of the cross-over current. A transistor replaces the usual


chain of diodes as it can provide a more satisfactory form of adjustment and may perhaps now even actually be cheaper. Almost any type of transistor will do provided that there is a gain of at least ten at a current of 1.5mA. Clearly a silicon device can be expected to be more stable and to provide a better tracking when the stages being stabilized all use this same material.

Resistor  $R_8$  has to be reduced in value if the cross-over current is too large whilst  $R_9$  must be reduced if it is too small. Make any adjustment carefully as this setting is fairly critical. Capacitor  $C_5$  serves merely to provide an easy path for the signal current to reach  $Tr_6$ .

With silicon transistors of this kind the cross-over current is not at all critical. The value can rise to 50mA or more before the heating effect becomes significant whilst it can fall as low as 5mA before there is any appreciable increase in the distortion. The temperature differences would have to be in the region of  $100^\circ C$  before either of these limits could be approached, and temperatures of this order are certainly not developed in ordinary domestic usage even when no special heat-sink arrangements are made as is the case with my amplifiers.

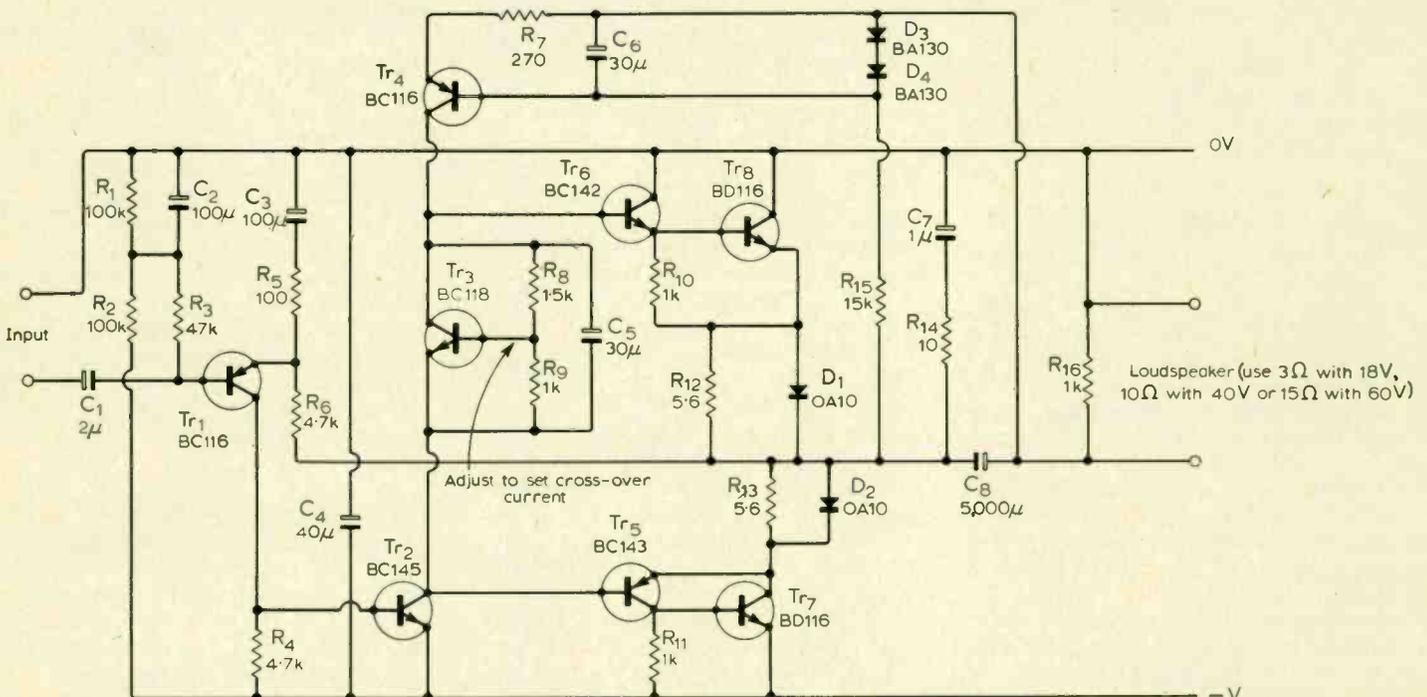**Matching the transistor gains**

The gain from the collector of  $Tr_2$  to the output in a circuit of this type is determined primarily by the products of the current-gains of the driver and final transistor on the two sides. Thus in this circuit it is the product for  $Tr_5$  and  $Tr_7$  for negative swings and  $Tr_6$  and  $Tr_8$  for positive ones. It is these products, rather than the gains of the corresponding devices, that ought to be matched to reduce distortion. There is no great difficulty in doing this and indeed it offers the big advantage that relatively poor specimens of one device can be sold paired with star performers of the other



Except for  $Tr_3$  and  $Tr_4$  the transistors are from the Fairchild AF11 kit, as are  $D_3$  and  $D_4$ . All the electrolytic capacitors must carry half the supply voltage except for  $C_4$ , which carries the full voltage, and  $C_5$  and  $C_6$  which carry a couple of volts at the most.

so as to give a standard product despite production spreads. So far as I know, though, no manufacturer has ever offered devices on this basis. When building an amplifier of this kind it is well worth taking the trouble to test the devices available and to select pairs for a constant value of this gain product.

An amplifier of this type has then, in principle, got a constant gain right through the cross-over region. The current from  $Tr_2$  is indeed split into two pieces in some ratio determined by the relative impedances at the inputs of  $Tr_5$  and  $Tr_6$ , and these are amplified separately. But they are simply added together again for the output, so that if the amplification factors are equal the exact manner of the splitting is of no importance. This situation is quite different from that in a valve class-B circuit where the signal is applied as a voltage to the two devices equally at all times, and their characteristics must be so shaped that the sum of their responses remains constant as the action transfers from one to the other. In this latter case a critical level of biasing, determined by the design of the valves, must be maintained so that the responses dove-tail together, but there is no corresponding requirement in the transistor circuit.

The only objection to an indefinite increase of the cross-over current here comes from excessive heating of the power stage and the need for a larger power-pack. There is no clear distinction with this type of circuit between class B with a large cross-over current and class A. The distortion decreases as the standing current is increased, and a compromise must be made between the distortion acceptable and the power level.

#### Choice of cross-over current

The value chosen for the cross-over current in my amplifiers is 20mA. This gives a standing power dissipation in the final transistors of 0.6W each at the full voltage. At this power level no heat-sinks are required in normal service, so that the devices can be mounted directly on the same small paxolin board as the other components. This in turn means that none of the wires concerned in the feedback loop need be more than 3in long and the stability problems are correspondingly reduced. There is no objection, however, to running at a higher level of standing current simply by reducing  $R_9$ , if a different compromise is required and heat-sinks and stabilization capacitors are provided.

But how serious is the distortion even at this level of 20mA? With modern diffused power devices, such as the Fairchild BD116, well over half the peak gain is still available at this sort of current. If we assume that the amount left is actually 75%, then this gain loss will cause a fall in the open-loop gain, due to the simple product of the betas, by a factor 0.75 at the cross-over point.

Further to this there is a loss of signal in the resistors  $R_{10}$  and  $R_{11}$  due to the rise of the input impedances of  $Tr_7$  and  $Tr_8$  at low currents. With typical silicon devices this is no worse than a factor of 0.95, and it is far less serious now than it was with

germanium where the leak resistors had to be made much lower in value. It is tempting to omit these resistors altogether with silicon but, in fact, this is foolish as they are required to help the power devices turn off after fast transients.

Lastly there is the fact that  $Tr_2$  is not really a perfect current source, but has a finite output impedance. Even if the standing current in this stage is cut to the bare amount required for driving the full output together with a minimum safety margin (2mA in this circuit) the collector impedance will still be no higher than about 50k $\Omega$ , as the base is current fed. The input impedance to  $Tr_5$  and  $Tr_6$  is, however, 45k $\Omega$  or more, since the 15 $\Omega$  of the loud-speaker is multiplied by at least 3000 due to the current-gains of the stages. Moreover, there is a further 10k $\Omega$  added to this, due again to the rise of transistor input impedances, at the cross-over point. Thus the loss of gain here is a factor 0.55 worsening to 0.45 at cross-over. The corresponding effect at  $Tr_4$  is rather less than this as it is voltage fed and returned to the bootstrap line. Its inclusion does not make any serious difference to the general picture.

The combined effect of all these causes is then a loss of perhaps a factor 0.6 in the open-loop gain in the region of the cross-over. If the cross-over current value were made greater than 20mA this loss would certainly be reduced, but what other changes occur in this open-loop gain that would remain unaltered despite such an increase of this current?

The most serious effect here comes again from the collector impedance of  $Tr_2$  and is due to the fact that this impedance is inversely proportional to the current in the device. Thus at the peak negative swing this impedance will fall as low as 30k $\Omega$ , while at the positive peak it will rise to perhaps 100k $\Omega$ . This causes a factor of loss of open-loop gain varying from 0.4 to 0.7. This effect is thus comparable with the factor 0.6 due to the effects at cross-over. The conclusion from this is that although a further increase of the cross-over current would indeed reduce the distortion the rate of reduction is becoming rapidly less so that, on balance, this value represents a reasonable compromise. If a more constant open-loop gain is required then something must be done to increase the effective output impedance of  $Tr_2$ .

#### Stability of the feedback loop

The full product of the current-gains of the second, third and fourth stages of this circuit is in the region of 350,000, but, as we have seen, this is reduced by various factors so as to be perhaps 140,000 at the least and 250,000 at the most with variations over the signal swing. Now roughly 1/600 of the output current is fed back through  $R_6$ ,  $R_5$  and  $Tr_1$ , so that the effective gain round the feedback loop in the passband varies over the range from 230 to 420. This very large amount of feedback serves to make the overall incremental gain fall short of the value determined by the potentiometer formed by  $R_6$  and  $R_5$  by no more than 0.43% at the worst and 0.24% at the best.

This variation is less than  $\pm 0.1\%$  from the mean and indicates that the performance of this type of amplifier is very good indeed. It is quite probable, in fact, that the linearity of the resistors used for  $R_6$  and  $R_5$  is not even as good as this and that they are, therefore, a major source of distortion. In any case there is little doubt that there are other components in any real audio system which are far worse than this circuit, so that there is little point in worrying about it overmuch.

However, this feedback will be quite useless unless the loop can be kept stable. The last feature in which my circuit is unconventional is in the fact that adequate stability is obtained without any extra capacitance having to be added between the collector and base of  $Tr_2$ . The network  $R_{14}$ ,  $C_7$  provides the usual dummy load to restrain the output voltage at the very high frequencies where the loudspeaker system is likely to be inductive and where oscillation is likely to occur, but the amplifier as built have a response time to a sharp step input of about 1 $\mu$ s rise-time with an overshoot of no more than perhaps 10%. Notice that the sort of wiring commonly used to feed loudspeakers has a characteristic impedance substantially higher than the load resistance, so that a long lead will make the inductive effect greater rather than less.

As already mentioned, the layout used is very compact with no signal lead more than 3in long, but the rather unexpected stability seems to come from the very high impedance at the collector of  $Tr_2$  due to the constant-current effect of  $Tr_4$ . This apparently makes the ordinary stray capacitances at this point have a time-constant which dominates the feedback action. At the same time the diffused power transistors used for  $Tr_7$  and  $Tr_8$  are so fast (they have  $f_T = 40\text{MHz}$ ), that they no longer make a serious second time-constant. With germanium the final devices used were more than a hundred times slower than this and their response was an important factor in the stability considerations.

It follows from this step-input behaviour that the high-frequency cut-off of this circuit is at over 100kHz. If this is thought to be excessive it can be reduced as required by adding collector-base capacitance at  $Tr_2$ , and this will still further ensure stability. The low-frequency cutting action of the circuit comes directly from the increase of the feedback factor due to the time-constant of  $R_5$  and  $C_3$ . The value of this is 10ms, so that the cut will come at about 16Hz. If this value is to be changed then  $C_1$ ,  $C_2$ ,  $C_3$  and  $C_8$  must all be multiplied by the required factor.

The result of all these modifications is an amplifier arrangement that works appreciably better than corresponding circuits of the same general type with only a marginal increase in the complexity. It is even possible that the total cost is no greater when the savings that can be made in the power pack are taken into account. Certainly there is no doubt that the component tolerances have been made substantially easier, and that these various features deserve consideration in the design of any future amplifier of this type.

# Speakers in Corners

**A disagreement with the widely held view that placing a loudspeaker in a corner of a room gives better sound quality**

by H. D. Harwood,\* B.Sc.

In his article "Loudspeaker Performance" in the February issue of *Wireless World*, P. W. Klipsch, states that "All speakers (I have found no exceptions) work better in a corner". This view, which seems to be very commonly held, does not agree with experience in the B.B.C.<sup>1</sup>. Historically it has been found that as the general sound quality of loudspeakers has improved, so the deleterious effects of mounting the loudspeaker in a corner have become more and more noticeable. The deterioration in quality has been found to be mainly in the middle and upper bass regions. It sounded as though the loudspeaker had a very irregular response/frequency characteristic and that the sound was apparently more reverberant and coloured. The effects in the lower frequency range were particularly noticeable on polyphonic organ music, the separate parts of which are changed in level according to their positions in the scale.

In the B.B.C. television sound control rooms have been chiefly affected, as the most convenient position for the monitoring loudspeaker has been above a group of picture monitors which are placed across a corner. This listening position is largely a forced choice because the listener's strong directional sense in the horizontal plane discourages the use of positions to one side of the monitors, while the space below is normally screened by the control desk and other obstacles. The monitoring loudspeaker is therefore normally placed near the ceiling in a corner, exactly the acoustic position favoured by Mr. Klipsch.

The hanging version of the LSU/10 studio monitoring loudspeaker (introduced in 1958) sounded satisfactory in such a position after a bass lift had been added. With the completion of Television Centre and the introduction in 1959 of the LS5/2A, it was found that these loudspeakers, which performed very well in most circumstances, gave inferior quality when hung in a corner, although it was often possible partially to overcome this by changes in the acoustics of the room. When the LS5/6<sup>2</sup> was introduced recently, the effect of mounting it in a corner was quite marked.

Three hypotheses have been suggested to explain the effects:

1. The release of load on the base of the cabinet when the loudspeaker is removed from its plinth allows the cabinet to vibrate more freely, thus colouring the sound at a series of resonance frequencies.
2. The quality change is entirely due to interference effects between the direct sound from the loudspeaker units and that reflected from the walls and ceiling in the neighbourhood of the loudspeaker.
3. The effects are psychological in origin and associated with the unnatural or unaccustomed direction of the sound reaching the listener. This is very difficult to check and therefore the first two suggestions were examined first.

To check the first suggestion, listening tests were carried out, using both speech

and music, when the loudspeaker was on its plinth near the middle of a wall and when it was raised just free of the plinth by means of a rope and pulley. No difference in sound quality could be detected at all and it was concluded that vibration of the base of the cabinet was not a cause.

If interference from reflections was the cause of the changes in quality, then past experience<sup>3</sup> would indicate that their amplitudes would be comparable with that of the direct sound, and the output of a microphone placed in the listening position would have a series of easily identified fluctuations.

Fig. 1 shows the arrangement used for experiments to test the hypothesis that the deterioration in quality was caused by reflections from the surfaces of the walls


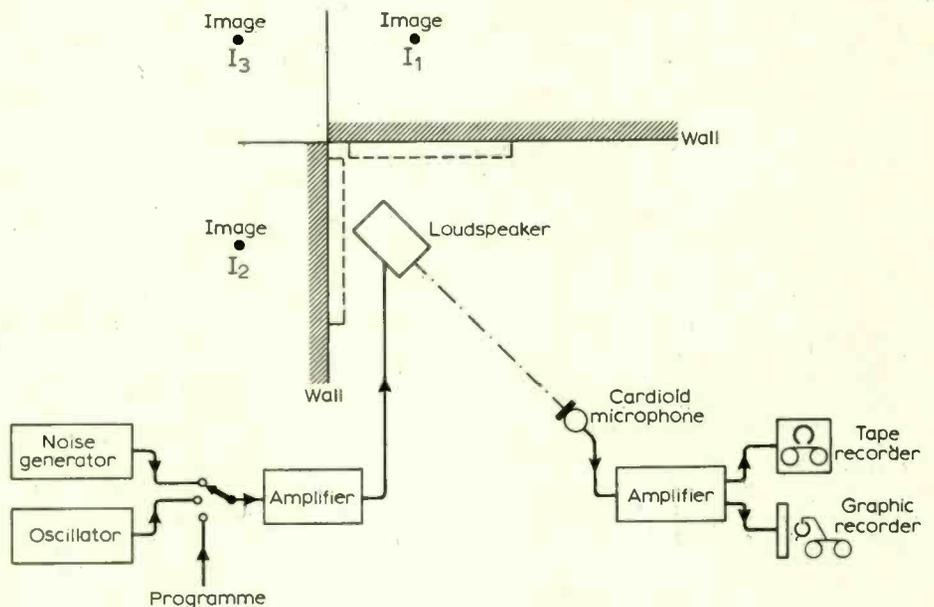


Fig. 1. Experimental set up used for investigating effects of corner placing.

Fig. 2. Response/frequency characteristic with loudspeaker symmetrically placed in upper corner of room. The signal source was a warble tone.

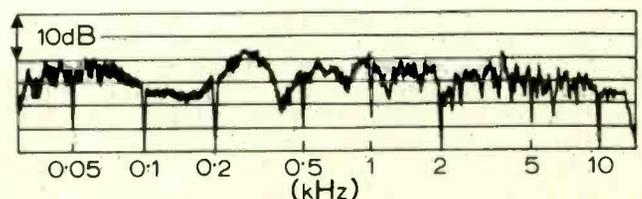

\*B.B.C. Research Department

and ceiling. For clarity it is shown in two dimensions only, but the extension to three dimensions is fairly obvious. For walls at right angles three images are formed,  $I_1$ ,  $I_2$ , and  $I_3$ . If the walls are not at right angles then  $I_3$  is split into two images, but for most rooms these two will coalesce at the wavelengths we are concerned with. Corresponding images will be formed in the ceiling.

In the tests the loudspeaker could be fed with pink noise, pure tone modulated over a range of  $\pm 63$  Hz at a rate of 10 times a second or with programme from recordings. A microphone with a cardioid directional pattern was used to reduce the effect of room reflections elsewhere and the output could be recorded on a graphic level recorder or on a magnetic tape recorder.

Fig. 2 shows the steady state characteristics with the loudspeaker in a symmetrical position in the corner of a room acoustically treated on surfaces other than that of the corner. The microphone was 1.3m above floor level on the loudspeaker axis. Fig. 3 shows the curve obtained in a listening room in an asymmetrical position with respect to the walls of the room. These curves of course represent the combined effect of room and loudspeaker and should in no way be confused with those of the loudspeaker alone.

Compared with Fig. 3, the curve in Fig. 2 shows a series of broad maxima and minima at low and middle frequencies, the maxima occurring at 50, 280, 630 and 950 Hz, the peak to trough variations reaching 11 dB; at high frequencies, too, there is a series of interferences. Listening tests on the loudspeaker using both pink noise and speech, in the condition corresponding to Fig. 2, showed a definite colouration just below 300 Hz, which agrees with the main peak in this region. There is a clear suggestion therefore that the colourations at low frequencies are associated with these peaks.

Fig. 4, curve A, shows the expected resultant of the sound pressure from the loudspeaker and its images calculated by ordinary vector summation from the following data:

1. Measured positions of loudspeaker and microphone.
2. Assumption of a value of 90% for the reflection coefficient at the walls with no significant phase change in reflection.
3. The assumption that the two images lying directly behind the loudspeaker could be neglected. One of these is formed by two successive reflections and the other by three, and both are formed by radiation inside a small solid angle at the back of the loudspeaker where the radiation is in any case low; otherwise the loudspeaker was assumed to be omnidirectional.

Curve B in Fig. 4 is a smoothed reproduction of a portion of Fig. 2 deliberately displaced from curve A. The similarity between the two curves is sufficiently close to confirm that interference by reflections from the surfaces surrounding the corner is an adequate explanation of the low frequency

Fig. 3. Characteristic with loudspeaker in an asymmetrical position in a quality listening room (warble tone).

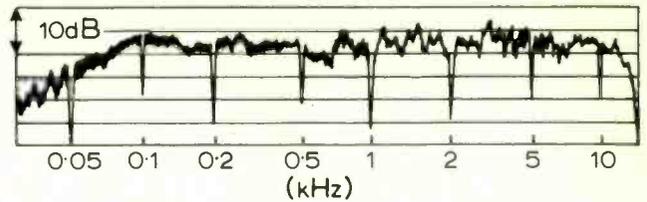


Fig. 4. Calculated response/frequency characteristics from loudspeaker in corner of room: curve A, calculated from direct and strongest three images; curve B, smoothed from measured characteristic in Fig. 2.


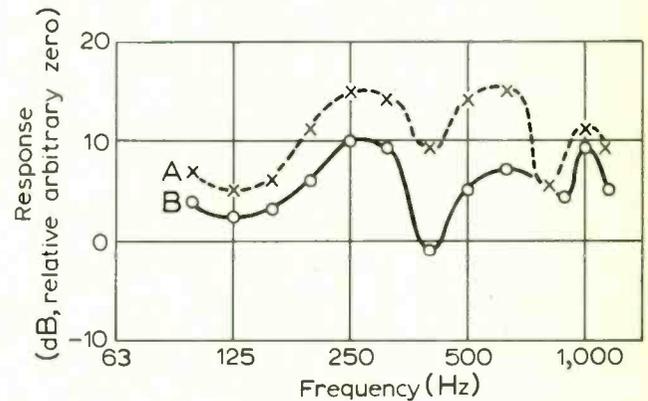


Fig. 5. Speaker moved to unsymmetrical position in room (warble tone).

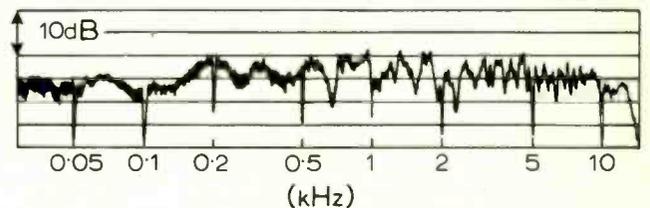

effects.

As the frequency is increased the fluctuations of Fig. 2 vary in depth owing to the varying directivity of the loudspeaker and the interaction of images at several different distances. From 3 kHz, however, the pattern becomes more regular, probably because the tweeter is in operation here and is more omnidirectional, giving stronger reflections from the nearby surfaces. The fluctuations still seem to be harmonically related to 270 Hz.

Fig. 5 is the steady state characteristic, for comparison with Fig. 2, obtained after moving the loudspeaker from its symmetrical position by 45 cm parallel to one wall. In this position the path lengths from two of the primary images are different and the fluctuations are therefore reduced at low frequencies.

A further response characteristic was taken at a symmetrical corner floor position, a carpet being on the floor. The low frequency fluctuations were similar to those in Fig. 2 but the high frequency ones were smaller, presumably due to the absorption of the carpet.

Fig. 6 shows the disastrous effect of placing the loudspeaker right in the corner so that it touches each of the walls.

The evidence given above shows that interference between reflections and the direct sound is sufficient to explain the measurable effects of the loudspeaker environment. It is also consistent with the subjective observations which were the starting point of the investigation. It may be a matter of some surprise that such large fluctuations as exist even in the best curves, i.e. Fig. 3, do not make the

loudspeakers completely unacceptable in any other situation than that of a free field room, but it is a common observation that one does not normally notice the even larger fluctuations due to room modes which must equally affect live speech in a room. The faculties of binaural hearing and central nervous analysis give considerable weight to the direct sound.

Assuming that the effects are entirely due to interference, there are thus three alternative methods for improving reproduction from a corner placed loudspeaker.

1. To absorb sound falling on the neighbouring surfaces. This will require a highly efficient absorber working over the entire audio bandwidth to be applied to a suitable area around the loudspeaker position. A suitable type is a partitioned air space 15 cm deep closed by 5 cm of dense rockwool and a fabric or highly perforated cover.
2. To use unsymmetrical loudspeaker positions, preferably chosen to eliminate the major fluctuations.
3. To avoid the corner as far as possible, will give the best results.

An opportunity to test out these conclusions arose in the sound-control cubicle of Studio 1 in Television Centre. A loudspeaker, type LS5/2, which it was agreed gave a high quality of reproduction when near the floor, gave an objectionable quality described as "tunnelly" when hung above the television monitors in a corner of the room. The position of the loudspeaker is such that very little can be done in the way of adding absorbent at the sides of the loudspeaker without covering large areas of viewing window in the

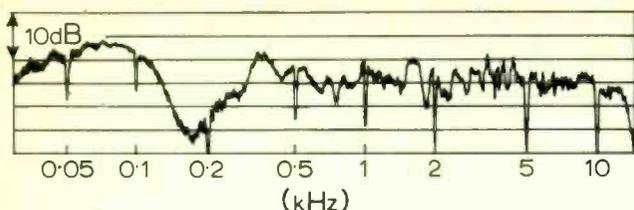


Fig. 6. Effect on characteristic of placing loudspeaker in corner touching walls and floor (warble tone).

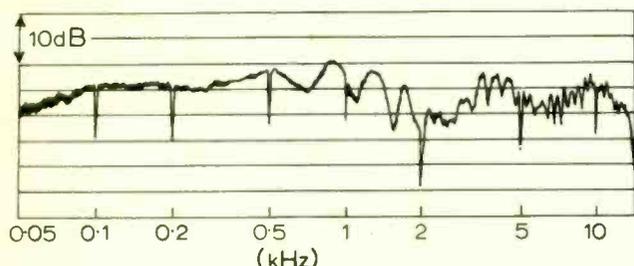


Fig. 7. High quality monitoring speaker placed in upper corner of television sound-control room (warble tone). The microphone had a cardioid characteristic.

control room. The wall area available behind the loudspeaker was treated as described above, but the quantity of absorbent involved was so small that it was not surprising that very little benefit resulted.

A response/frequency curve was taken with a cardioid-type microphone at the edge of the control desk facing the axis of the loudspeaker and with warbled tone applied as in the earlier curves. The result is shown in Fig. 7 and the expected irregularities are evident in the 500 Hz to 2 kHz region. To check that the irregularities were not due to interference from a reflection off the desk the measurement was repeated, the microphone having a figure-of-eight polar characteristic, the null being directed towards the desk. Results were substantially the same.

It was noted that the sound quality varied rapidly with distance from the desk and indeed throughout the whole room, although the impression of "tunnelliness" persisted everywhere.

Since the first suggestion of improving the sound quality was inapplicable, the second was tried. The loudspeaker was lowered about 35 cm from the ceiling until it touched the monitors and the angle adjusted until it again faced the sound supervisor.

It was immediately obvious on listening that the sound quality had greatly improved in the normal monitoring position and furthermore that it did not vary substantially with position and was acceptable throughout the whole room.

A further response/frequency curve was taken at the monitoring position with the microphone in the cardioid condition. It was observed that the irregularities in the 500 Hz to 2 kHz region had almost disappeared, and that even those at high frequencies had been somewhat reduced. As a matter of interest, it was not possible even on careful listening to attribute any effect to these latter irregularities and it appears, therefore, that the ear is more tolerant in this frequency range.

Enough has been said to show that, far from all loudspeakers working better in a corner, this position is to be avoided for direct radiator loudspeakers whenever

possible, if high quality sound is the criterion and not just a loud noise. If such a position is unavoidable, try first to make the distances to neighbouring surfaces appreciably different and if the floor is one surface use a thick carpet. If this measure is insufficient, acoustic absorbent material should be placed on the surfaces involved.

**Acknowledgement.** This article is published by permission of the Director of Engineering, B.B.C.

#### REFERENCES

1. B.B.C. Engineering Division Monograph No. 78, September 1969. Part II, by H. D. Harwood and C. L. S. Gilford.
2. "New B.B.C. Monitoring Loudspeaker", by H. D. Harwood. *Wireless World*, March, April, May 1968.
3. "Recent work on the effect of reflectors in concert halls and music studios", by T. Somerville, C. L. S. Gilford, N. F. Spring and R. D. M. Negus. *J. Sound Vib.*, 1966, 3 (2), pp. 127-134.

## Corrections & Amendments

We regret the need to draw readers' attention to the following amendments and corrections to recently published articles.

*L. Ibbotson writes:* My attention has been drawn to an error in question 15 of "Test Your Knowledge" No. 20 on Colour (January issue). The supposedly correct answer, (b), is wrong in the following particular. The three spectral wavelengths quoted were selected because the triangle on the chromaticity diagram with these as apices includes the largest pos-

sible range of real colours. It is clear from the chromaticity diagram that colour-mixing curves in terms of constant luminance would have maximum values around the three primary wavelengths quoted. However, to get the required filter (radiant flux) transmission characteristics, these curves require to be multiplied by the relative luminous efficiency curve: as a result the required radiant flux transmission peak for the red occurs at a wavelength of about  $600m\mu$ . The other two transmission curves still peak at round about the primary wavelengths.

"Ceramic Pickups and Transistor Pre-amplifiers" (Feb. p. 56): Referring to Fig. 8(b) mechanical compensation can be allowed for by adjusting  $R_4$ , not  $R_1$  as stated in the text. In the appendices (p.80) the diagram at the foot of the centre column should follow "... by thinking of the ceramic pickup capacitance as being a part of  $Z_1$ :", and the diagram in the right hand column should follow the text at the foot of the centre column.

"Digitally-controlled Tape-recorder Pre-amplifier" (March p.127): In Fig. 2  $Tr_9$  is n-p-n and should be drawn as is  $Tr_{11}$ . In Fig. 4(b)  $D_7$  should be inverted and  $C_{15}$ ,  $D_4$ ,  $D_5$  and  $D_6$  should share a common connection. In the caption to Fig. 4(a) and in Fig. 5 it is suggested that diode 1N914 is a germanium type when it is actually a silicon planar device. Four such silicon diodes should be employed ( $D_8 - D_{11}$ ) to give  $V_{ee}$ .

The following amendments should be made to the article "80-metre S. S. B. Receiver" by W. B. de Ruyter which appeared in the March issue:  $R_{12}$  should be connected to the a.g.c. line and not chassis as shown and the values of  $R_{28}$  and  $R_{21}$  should be interchanged.

Two corrections should be made to the article "Pulse Generator using Integrated Circuits" by C. Djokic (March p.130). The variable resistors in the output amplifiers (Fig.4) should be connected across the power supply as potential dividers with the wipers connected to the upper end of the  $470\Omega$  resistors, and gate C pin connections should be altered to 5 and 6 as per Fig. 6.

"Simple Linear A.C. Voltmeter": A printer's error in G. W. Short's letter (March, p.113) made nonsense of his correction. The oblique stroke was again omitted from the expression  $R_2 = (V_{CC} - V_{CE})/I_C$ .

"Pickup Characteristics" (December, p. 553): The stylus supplied with the Bang & Olufsen SP10 cartridge is spherical (0.6 thou) and not elliptical.

# An Electronic Dice

## Design for a digital novelty, the final details of which are left to the reader

by Brian Crank\*

A chance remark made at a game of snakes and ladders led to an interesting excursion into logic design. The dice had fallen off the table and as people searched the floor for it someone said "At least in this house you would think that there would be an electronic something to save all this trouble". Later the possibilities of making an electronic dice were investigated.

The circuit must have six stable conditions or states, each state corresponding to one of the sides of a dice as shown in Fig. 1 (a), and it must be capable of selecting anyone of these states at random. In practice the random element is provided by a high-speed multivibrator.

The groups of spots on the sides of the dice can be made up by using one, or by superimposing more than one, of the four patterns given in Fig. 1 (b). There are several ways in which these patterns can be displayed. One possibility is to use seven lamps, one lamp for each spot; in this case all the lamps to form a particular pattern in Fig. 1 (b) would be connected in parallel. Another solution would be to partially drill the spots in four sheets of Perspex, one sheet for each pattern, and to illuminate them using the edge lighting method employed in some numerical indicators. Finally, fibre optics could be tried. This would entail guiding the light from the lamps along fibre "light pipes" on to some form of translucent screen. (Fibre optic light guides which might be suitable can be obtained from Proops.)

The precise method of display is left to the ingenuity of the reader. However, it has been established that the logic circuit needed to drive the display must have four outputs, that is one output to illuminate each pattern.

\* Assistant editor *Wireless World*

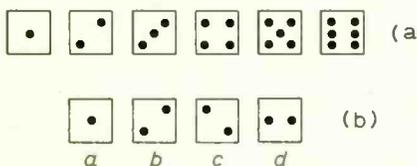


Fig. 1. (a) The arrangement of spots on a conventional dice; (b) the six scores of (a) can be formed with these four patterns

Several logic circuits were tried in the search for one using the minimum number of parts. The circuit finally chosen, although very simple, was arrived at after a good deal of effort had been expended.

The first stage in analysing the problem is to decide which of the four patterns are required to form the six sides of the dice and to present this information in a logical manner:

Dice score	Patterns required
1	= a
2	= b
3	= ab
4	= bc
5	= abc
6	= bcd

This states the facts but not in a way that is very meaningful. However, from these facts a table can be constructed. In this table a 1 is written when a particular pattern

is required and a 0 is written when it is not.

Dice score	Patterns
	a b c d
1	1 0 0 0
2	0 1 0 0
3	1 1 0 0
4	0 1 1 0
5	1 1 1 0
6	0 1 1 1

Do the first three columns of this table look familiar? If not some re-arrangement may help:

Dice score	Patterns
	a b c d
1	1 0 0 0
3	1 1 0 0
5	1 1 1 0
4	0 1 1 0
2	0 1 0 0
6	0 1 1 1

The first three columns closely resemble

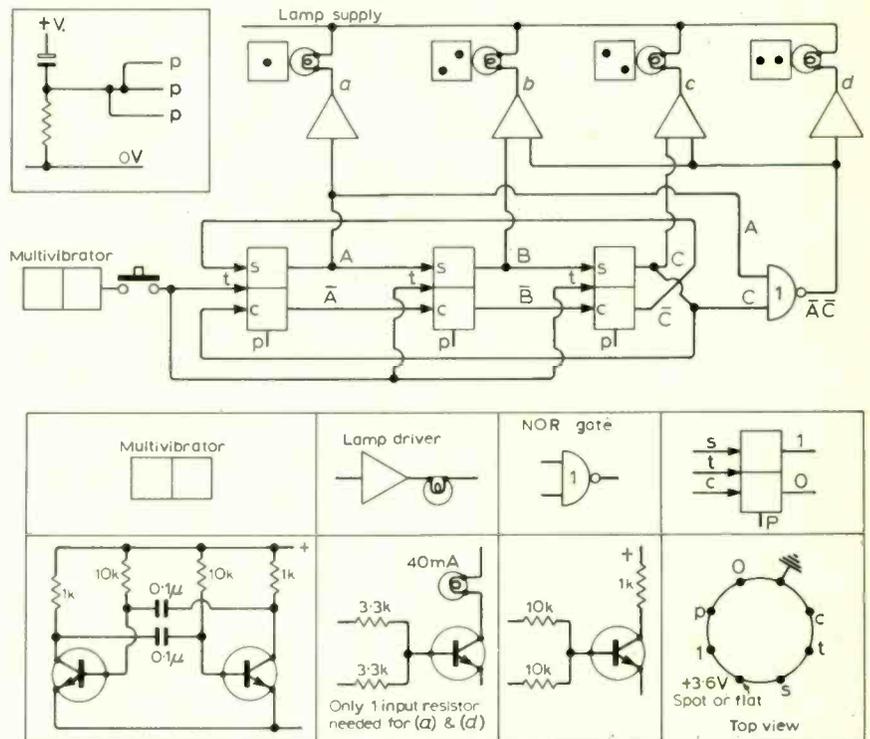


Fig. 2. The suggested circuit for a digital dice, the method of display is left to the reader, almost any general-purpose silicon transistors may be used.

the Johnson code. For readers who are not familiar with it the Johnson code is as follows:

```

0 0 0
1 0 0
1 1 0
1 1 1
0 1 1
0 0 1

```

This code is formed by a counter called a Johnson counter, sometimes known as a switch-tail ring counter. If the pattern requirements can be made to follow the Johnson code the lamps illuminating the patterns could be controlled directly by the counter and no gating at all would be required. Although we cannot reach this ideal solution we can come very close to it.

We will consider only the columns for patterns a, b and c at this stage; column d will be dealt with later.

The first line to depart from the Johnson code is the line for score two. This is 010 instead of the Johnson 001. This means that the Johnson code would have us illuminate pattern c instead of the required pattern b. Examining Fig. 1 (b) we find that patterns b and c both show a score of two so it does not matter which is used; 001 instead of 010 can be used, therefore, with no circuit changes.

The other line that needs modification is for score six. This should be 000 in Johnson code instead of 011. If the Johnson code is used no patterns would be shown at all for six, but we require patterns b, c and d to be illuminated. A gate must be employed to detect 000 and light the required patterns. A new table can now be drawn up:

Dice score	Patterns a b c
6	0 0 0 — light b, c and d
1	1 0 0
3	1 1 0
5	1 1 1
4	0 1 1
2	0 0 1

The gating requirements for the patterns can now be derived. It is assumed that a Johnson counter is employed in which the bistables are labelled A, B and C.

$$\begin{aligned}
 a &= A \\
 b &= B + \bar{A}\bar{C} \\
 c &= C + \bar{A}\bar{C} \\
 d &= \bar{A}\bar{C}
 \end{aligned}$$

The term  $\bar{A}\bar{C}$  detects line 000 for score six and illuminates the lamps b, c and d.

A circuit based on the foregoing is given in Fig. 2. The Johnson counter is a standard shift register with the output crossed and fed back to the input. The term  $\bar{A}\bar{C}$  is formed by a NOR gate fed with A and C. The  $+ \bar{A}\bar{C}$  function for lamps b and c is carried out using two resistors from the output of the NOR gate. Connection details for Fairchild  $\mu$ L 923 bistables are given although any similar device may be employed.

To "throw the dice" the push-button is pressed and released; during the time that the button is "made" the counter counts pulses from the multivibrator; the score is then displayed.

The Johnson counter has one serious

drawback. Three bistables have eight possible states, only six of these being used in the Johnson counter. If on switch-on the counter goes into one of the two unused states it will switch between these states on each input pulse and will never get into the proper counting sequence. This is eliminated by the resistor and electrolytic capacitor shown in the inset of Fig. 2. These cause the preset inputs of the bistables to go positive for a short period after switch-on ensuring that the counter starts at 000. The value of this capacitor can be found by experiment and is not critical.

An experimental lash-up of this circuit was found to perform well. If required more push buttons can be connected in parallel with the one shown in the circuit so that each player may have one.

The logic side of the circuit has been reduced to three bistables, one gate and two resistors. This is thought by the author to be the minimal form of the circuit, but perhaps this is a "dicey" statement as *Wireless World* readers are almost certain to find a better solution?

## Announcements

Revised dates have been announced for this year's **London Audio Festival and Fair** which will again be held at Olympia. The new dates are October 19th to 24th—the first day being reserved for the trade.

A **summer school in applied optics** for non-specialists is to be held from June 8th to 19th at Imperial College, London S.W.7. The course fee is £35 and further information and application forms may be obtained from the Registrar.

"**Hybrid Computer Techniques**" is the title of a course of six evening lectures to be held at Norwood Technical College, Knight's Hill, London S.E.27, commencing April 14th. Fee 15s.

Marconi Marine has received orders from three Japanese shipyards for the supply of **communications equipment, navigational aids** and dual radar installations for each of four new ore/oil carriers. The company is also supplying the communications and navigational equipment for *Esso Northumbria*, the largest ship ever to be built in the United Kingdom.

S.T.C. have been awarded a £350,000 contract by the Ministry of Technology for the development and construction of two functional models of a fully electronic access exchange for the Mallard project.

The Solartron Electronic Group Ltd, of Farnborough, Hants, has received an order from the Australian Government worth £2m to

design, manufacture and install a combined action information and **tactical trainer** for the Royal Australian Navy.

An agreement has been signed between **Siemens** of West Germany and **Ferranti Ltd**, Edinburgh, according to which these two companies will collaborate on the design, development and production of laser systems for the Multi-role Combat Aircraft (M.R.C.A.) project.

The Channel Electronic Division of LRW Electronics Ltd, Cheltenham, has been awarded a £60,000 contract for the supply of 'Safetylink' **marine radio telephones** by Channel Marine Commercial Ltd.

Link Electronics Ltd, has received a contract from the Post Office, valued at just under £20,000, for the supply of 40 **portable waveform generators** to be used in conjunction with differential gain and phase testing equipment.

The Aeronautical Division of Marconi has received an order worth nearly £100,000 from Air New Zealand for additional **Marconi Doppler equipment** to be fitted to their DC8 fleet.

GEC-AEI (Electronics), Leicester, have been awarded a share of a **£10m contract** for work on the Singapore Government's 'Bloodhound' missile defence system.

GEC-AEI Telecommunications Ltd has received orders worth £750,000 from the Post Office for **microwave radio equipment** to expand three routes in the P.O. network of high-capacity-radio trunk transmission routes.

Microwave Associates Ltd, of Cradock Road, Luton, Beds, have received an order, valued in the region of £40,000, from Sveriges Radio of Stockholm, for mobile all solid-state **television relay systems** for outside broadcast use.

H. Tinsley & Company Ltd, Werndee Hall, South Norwood, London S.E.25, will in future manufacture and market the range of air-spaced variable capacitors and trimmers previously made under the "**Cyldon**" name by Sydney S. Bird & Sons Ltd.

Highgate Acoustics, 184 Great Portland Street, London W.1, have been appointed distributors in the United Kingdom and Eire for the **Pickering** range of cartridges previously handled by Auriema.

A new division of Amphenol has been set up to manufacture components under licence from **Entrelec**, of Villeurbanne, France.

Electroustic Ltd, of 73b North Street, Guildford, Surrey, have been appointed the sole U.K. agent for the '**Silec**' range of **semiconductors**.

Tranchant Electronics (U.K.) Ltd, 17 Charing Cross Road, London W.C.2, have been appointed exclusive agents in Great Britain for the **Intersil** semiconductor range.

**Intertechnique Ltd**, Victoria Road, Portslade, Sussex BN4 1XQ, have been appointed sole representatives for the U.K. and other territories for the complete range of equipment manufactured by IGAB of Sweden.

Cole Electronics Ltd, Lansdowne Road, Croydon CR9 2HB, have been appointed sole U.K. agents for the range of **contactless solid-state switches** manufactured by Rafi Electronic, of Ravensburg, W. Germany.

# The professional one

Here it is, Solartron's outstanding 1240.

The multimeter that's not just a toy but a real step forward in instrument technology.

Now everyone can go digital!

You get Amps, Volts, Ohms - a.c. and d.c. - down to 100 micro-


volts and dual slope integration for noise rejection.

Technology apart, the 1240 has automatic polarity indication and a straightforward control layout including a single range selector and fingertip function switches. It's the easy-to-handle go-anywhere

portable multimeter.

Go digital with the new 1240. From Solartron, European leaders in digital instrumentation.

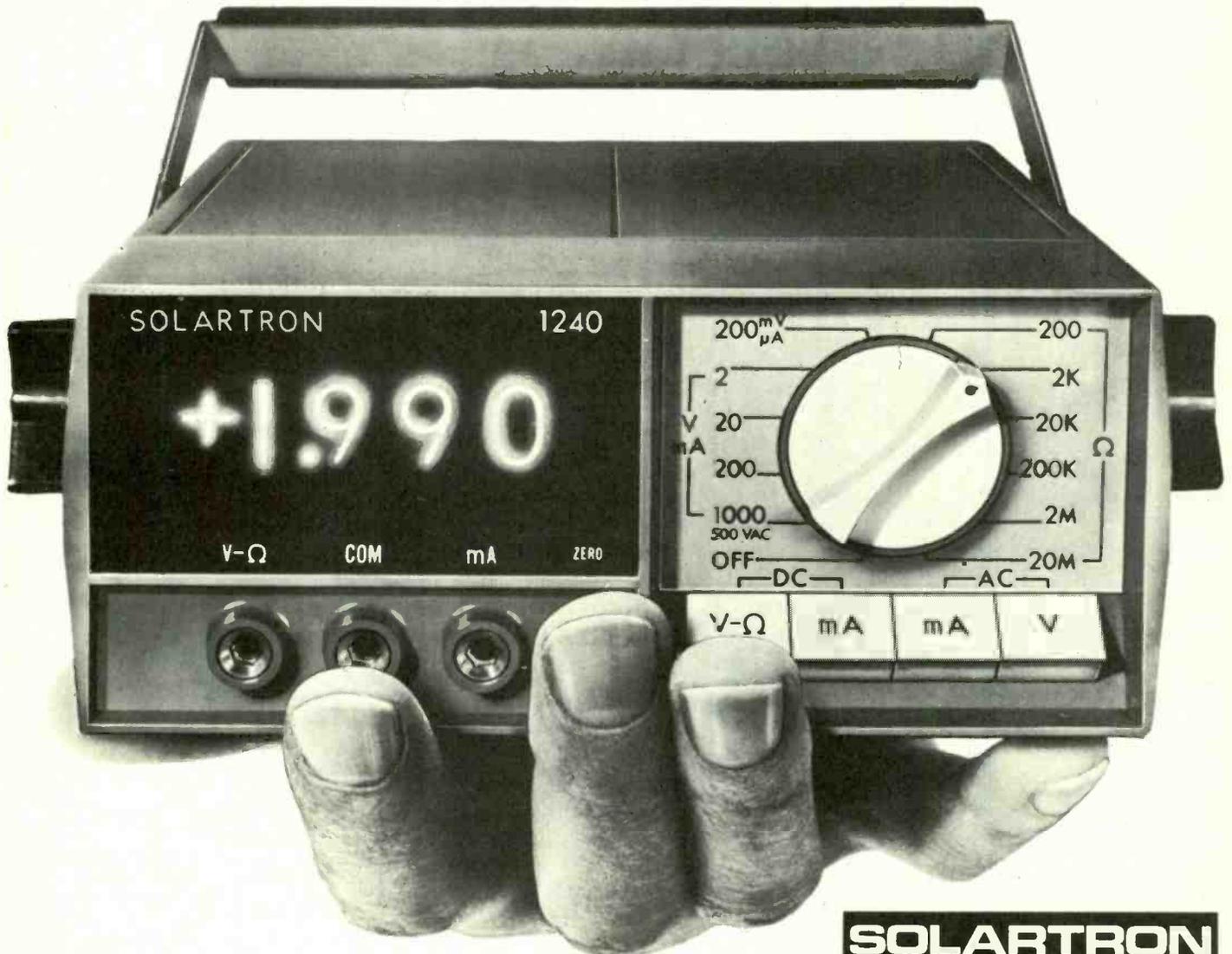Post the magazine's reply-paid card and we'll send you our data sheet of full details.




**SOLARTRON**  
**Schlumberger**

The Solartron Electronic Group Ltd Farnborough Hampshire England Telephone 44433

WW-096 FOR FURTHER DETAILS
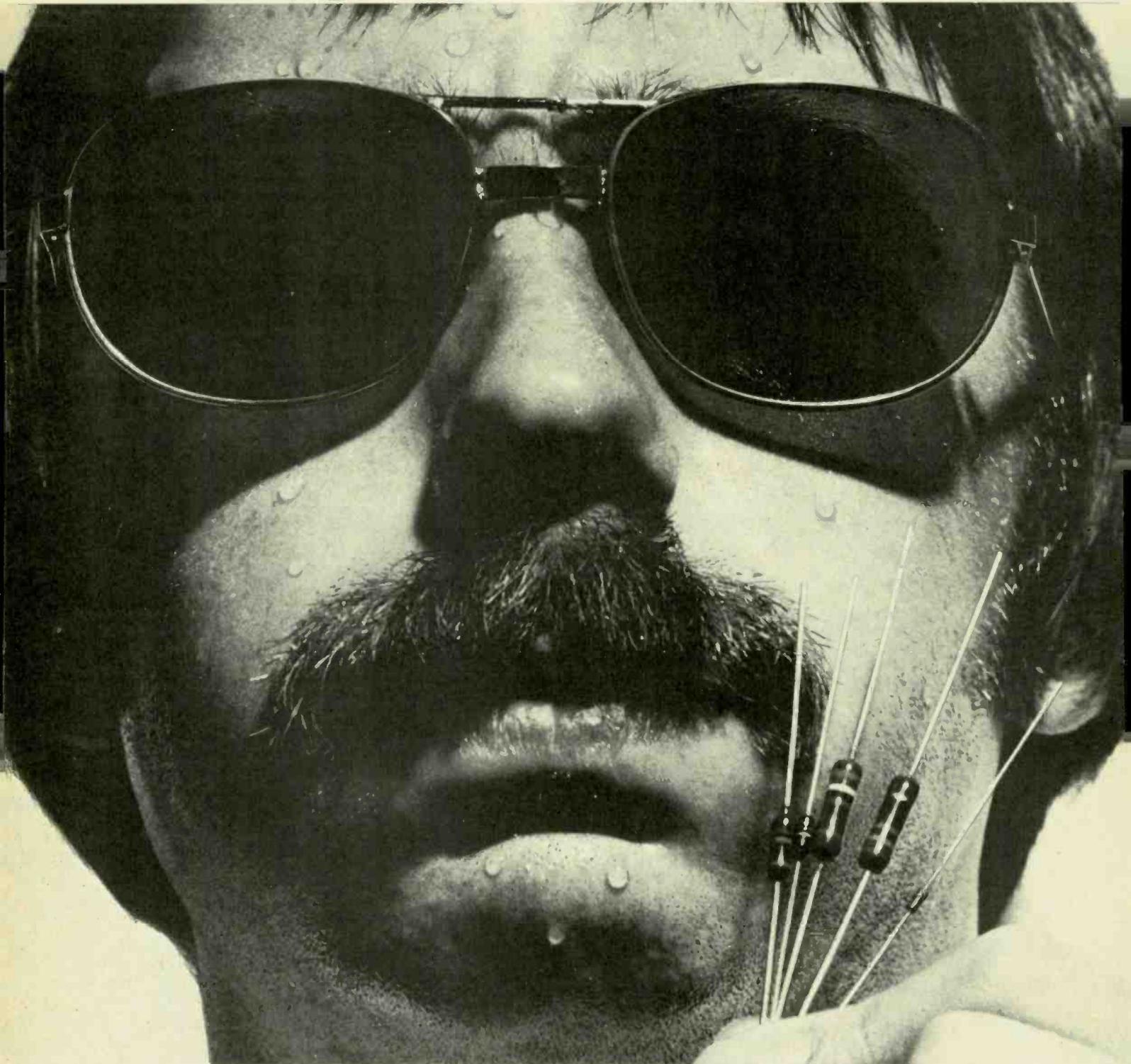
# We're the first ones to blow hot and cold about our resistors. So that you never will



Just be faithful to Electrosil resistors and they'll be constant, too! Because we demand consistent performance from them before we'll let you have them. Maybe they're in aircraft flying at 50,000 ft. which later land in equatorial heat. Maybe they're in Antarctic equipment. They're indifferent. They've already had,

from us, as savage thermal jolts as they're ever likely to get. They're glass-tin-oxide, of course, so you expect a much higher degree of stability and dependability.

ELECTROSIL LIMITED, P.O. Box 37,  
Pallion, Sunderland, Co. Durham.  
Telephone Sunderland 71481. Telex 53273.

If you're looking for this kind of performance in a small size, high stability resistor, have a look at the TR4.  $\frac{1}{4}$ W rating and only 0.281" long. Available in 1%, 2% or 5% tolerance. Remember—leave the hot and cold treatment to us—that's how we achieve unwavering reliability.

**Electrosil** LIMITED have the experience

# News of the Month

## Parliamentary affairs committee

The Council of Engineering Institutions has formed a committee which will keep chartered engineers in Parliament informed of developments and opinion within the engineering profession. The committee is made up of representatives from the fourteen member institutions of the Council and members from both Houses of Parliament.

The parliamentary members are: Mr. E. Lubbock, Sir Ian Orr-Ewing, and Mr. A. Palmer. The chairman of the committee will be the present chairman of C.E.I., Sir Eric Mensforth, and the electrical, electronics and radio representative will be Sir Harold Bishop.

## P.C.M. for B.B.C. stereo distribution?

It is now well known that the B.B.C. is experimenting with p.c.m. for distribution of high-quality sound—the advantages being, of course, the inherently stable characteristics of the system and immunity from noise and distortion in the sound transmission links. In fact, the Corporation has just finished a series of trials of the "sound-in-synchs" system using p.c.m. for television sound (*Wireless World* January 1969, page 38) between London and Kirk O'Shotts and this is expected to come into service within a year.

Writing in the first issue of *B.B.C. Engineering* (a journal replacing the *Engineering Monographs*), D.E.L. Shorter of the B.B.C. Research Department outlines what might be done in applying p.c.m. to monophonic and stereo sound signal distribution. If the stereo signal were applied to the p.c.m. system in the coded multiplex form in which it is required at the transmitter input, he says, it would be unnecessary to have a stereo coder at each transmitter. In the pilot-tone system used by the B.B.C., however, the spectrum of the multiplex stereophonic signals extends to 53 kHz and it would be a formidable task to design a system to accept the requirements for signal-to-noise ratio. Even if this were done such an

arrangement would not allow the information capacity of the channel to be fully utilised, if necessary, for other purposes. A more flexible arrangement could be achieved by transmitting the left- and right-hand signals over separate p.c.m. channels, each of which could then be used independently when required. This would also make more economical use of the capacity of the transmission circuit.

By using separate p.c.m. channels for the left- and right-hand signals, it would be possible to provide stereo coding in a rugged and simple way at the transmitter if the sampling frequency of the p.c.m. system were 38 kHz. The left-right switching, which is part of the stereo coding operation, could be done on the audio frequency signals appearing in sample-held form at the output of the digital-analogue converters. The signal resulting from this switching would then need only the addition of the 19-kHz pilot tone and filtration in a simple low-pass filter to remove components above 53 kHz in order to form the standard stereo signal.


This artifice would avoid the need for a conventional analogue stereo coder at each transmitter and would be more economical in circuit capacity than digital distribution of the fully coded stereo signal. However, the use of a 38 kHz sampling frequency would still need some 12% greater capacity in the distribution system than the otherwise satisfactory sampling rate of 33.5 kHz. The higher sampling rate and novel stereo coder are thus of doubtful value.

In the same article, Mr. Shorter discusses the general problem of maintaining the high quality of sound (stereo or mono) in the coding and decoding processes involved in digital distribution. The main problems, it seems, are quantizing noise and distortion from the low level signals. Investigations have shown, however, that the required performance on both counts can be obtained from a 13-bit p.c.m. code using a process of interpolation between quantizing levels. Thus a p.c.m. system is in principle capable of satisfying all the requirements of a high-quality sound signal distribution network which would be able to cope with monophonic and stereophonic signals.
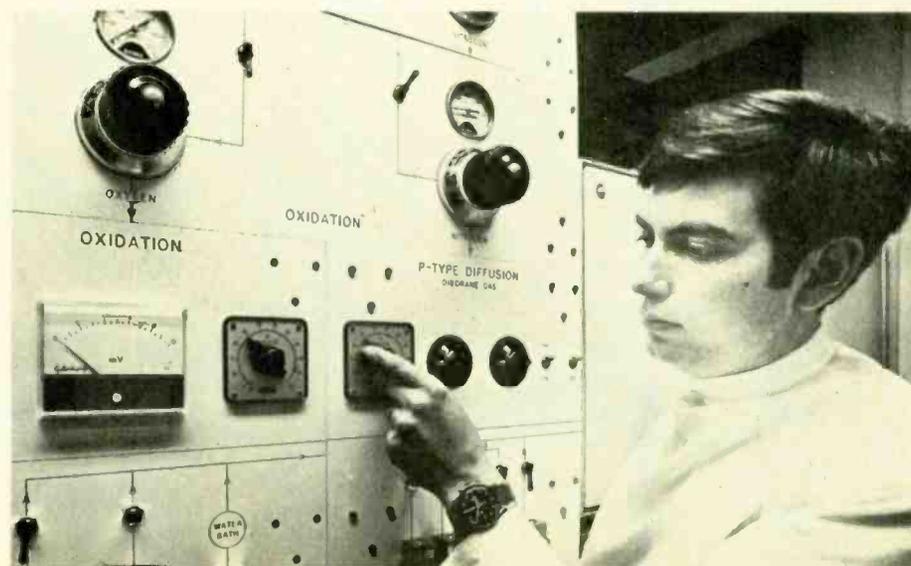
## What, not who, is calling

For many people the telephone is the only means of directly communicating with someone else. At the present time a subscriber to the telephone system has at his disposal a vast switching network and he can set selectors clicking in this country, in Europe or in America merely by dialling; a direct pair of wires can be established between one telephone and any other—it does not matter if this

*A fully equipped laboratory for the design and manufacture of bipolar micro-circuits has just been completed at Enfield College of Technology. The centre occupies only 750 square feet of floor space and cost about £40,000. The main idea seems to be to involve as many students as possible, in as many process steps as possible, and in projects of industrial value. Courses will be provided at all levels, from technician to post-graduate. Special courses can also be devised to meet particular needs, such as those of company managers and salesmen. Details of the three two-week practical courses to be held this year can be obtained from J. B. Butcher, Director, Microelectronics Centre, Enfield College of Technology, Queensway, Enfield, Middx.*



connection be over land-lines, submarine cable, satellite or microwave link.

Computers now chatter to one another over the telephone and many firms send picture facsimiles to and from equipment associated with a telephone. However, for the majority of users the telephone is only a means of voice communication; a fact which means that the telephone system is largely being wasted at the present time.

Perhaps the most important additional use of a telephone would be as a computer terminal. This opens up a vast number of possibilities, too many to go into here, that could place at the disposal of subscribers huge amounts of information. Such a system could hit the printing industry hard, and who knows, in years to come you may receive your *Wireless World* on a c.r.t. display associated with a telephone—with optional line printer of course!

You may wish to switch on your central heating or cooker when you are away from home, this could easily be done by dialling a code on your telephone after connection has been established; and so on and so forth.

The present method of dialling, the Strowger system, does not lend itself to being used in any of the above ways. Before additional services could be provided it would be necessary to go over to the push button method of dialling using tones instead of pulses. The main advantage of the touch-tone system is not a question of novelty or aesthetics it lies in the fact that the push-buttons can be used to send codes after the appropriate number has been dialled.

Unfortunately push-button telephones require special exchange equipment. The Post Office say that this equipment will be installed over the next few years, in fact the Post Office already use push-button

telephones in some of their buildings.

The telephone can be used as a means of sending huge amounts of information to a household, it can also be used as a means of extracting data from that household. In fact Bell Labs in America are running a pilot scheme at Holmdel, New Jersey, which reads domestic gas and electricity meters by computer over telephone lines. The computer "dials" the consumer's telephone number and is connected via special exchange equipment, which prevents the telephone bell from ringing, to transducers attached to the meters. The computer, on receiving the readings, carries out all the necessary accounting and recording. The process does not interfere with the normal operation of the telephone in any way.

Although all the above is technically feasible, and the main problem is one of economics, one is bound to ask if the meter reading system is socially acceptable. Apart from possible "big brother" implications many consumers rely on a chat with the "meter man" to gain some idea of what their bill is likely to be. In many areas, with modern high-speed computer processing, there is a gap of about a month between the meter being read and the bill arriving. This gives consumers time to prepare; with the proposed system there would be no early warning.

### Tracking vehicle movements

An experimental computer control system designed to simplify and improve the operation of large vehicle fleets has just been demonstrated by Marconi to senior representatives of the London Transport Executive. Centred on a Myriad

computer, the system is capable of continuously locating and identifying every vehicle throughout a network, presenting this information on a display screen, and immediately detecting any variations from schedule. This is done automatically without any involvement on the part of the vehicle driver. Additionally, it provides voice communication between the control centre and driver so that fresh instructions may be passed as and when necessary.

Each vehicle is fitted with a distance digitizer which counts the revolutions of its wheels, and therefore measures, digitally, the elapsed distance along a particular fixed route. Vehicles are also fitted with a radio telephone, adapted for two-channel operation, and a telemetry unit.

Digital information from each digitizer is passed into a register and is continuously updated at a prescribed rate—typically this might be every 25 feet of elapsed distance. The control room computer can interrogate any register, via the telemetry channel of the radio telephone, and the total elapsed distance count currently held in it will be passed over the link. This data is processed by the computer and displayed on the screen of a cathode-ray tube controlled by it. The display can take one of two basic forms. The route can be represented by a pair of straight lines, one for each direction, with prominent features such as fare stages identified. A vehicle is then continuously represented by a symbol at its current position on the route.

Alternatively, a second method of display allows all the vehicles in a particular area, a city centre for example, to be shown on a map electronically drawn on the screen.


The control room computer can be programmed to provide a number of other facilities. It can compare actual running times with those scheduled, and warn the operator if significant discrepancies are occurring. It can also generate a typewritten log of a day's operation, highlighting any 'out of schedule' running, and can provide this sort of 'history' for longer periods as well. Additional information such as crew meal break schedules may also be held on disc.

Finally, the radio telephone can easily be switched from the telemetry to a speech channel, to allow fresh instructions to be passed to drivers, or to allow emergency calls from them to base.
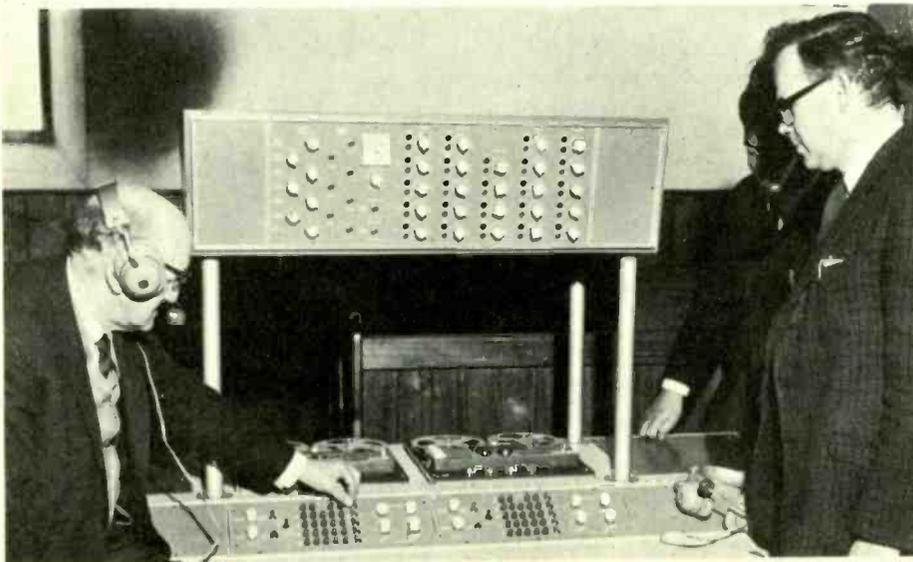
### University to industry, bridging the gap

A new four-phase sandwich course, lasting one year, is to be introduced by Birmingham University in October 1970. The first in a new series, this course has been developed on the principle that industrially related M.Sc. courses should be designed to bridge the gap between university and industry. It has been designed by several of the leading electronics companies in close collabora-

*Sykes-Robertson (Electronics) Ltd. came into being in February 1968, mainly as a result of proposals made to Mr. J. Sykes, an electronics engineering consultant, who went to Sanday (Orkney) to escape the hurly-burly of the South of England. The idea was to find interesting work, mainly for youths and girls who otherwise would have to leave their homes and families to seek employment in the South. The scheme has been a success and the firm, working in a former school and school-house, is currently manufacturing and exporting electronic equipment mainly in the civil and military fields. A recent despatch from Sanday is a high-quality language laboratory for Hong Kong which is shown in the photograph.*



tion with the University and is sponsored by the Conference of the Electronics Industry, with the support of the Ministry of Technology, the Engineering Industry Training Board, the Science Research Council and the Electronic Engineering Association.

The electronics industry has been concerned for some time over the difficulty of training high-grade systems engineers in the fields of radio communications and radar technology. Normally, each student will be sponsored by a firm in the electronics industry, which, with the assistance of the Science Research Council and the Engineering Industry Training Board will provide his salary and pay all his fees.

Features of the course are that a high proportion of the lectures will be given by people from industry and that the lecture periods have been designed in the form of "modules", each of about three to four weeks' duration which will be available to industry to use as short up-dating courses.

This presents a unique opportunity to graduates to enjoy an intensive course of study and training in industrial research and development while receiving the salary of a full-time staff member of the company by which they are sponsored. The two industry centres for the first year of the course are to be at the Marconi Company in Chelmsford and the Plessey Company at Ilford.

The normal entry qualifications are a first or second class honours degree in electronics, electrical engineering, physics or mathematics or an equivalent qualification "with experience". For further information contact the Post-Graduate Admission Tutor, Department of Electronic and Electrical Engineering, University of Birmingham, P.O. Box 363, Birmingham, 15.

## NEW COMPUTER TYPEFACE

A new computer typeface, shown above, has been chosen as the in-house style of Marconi-Elliott Computer Systems Ltd. The typeface, which is based on a square and has no curves or diagonals, makes the design of automatic readers a simpler task; it can also be easily read, even by the untrained eye, and it is not difficult to print by hand.

## Keeping passengers informed

Nelson Tansley, in co-operation with Southern Rail's signal and telecommunications engineers, have developed a public address system which has been installed along the fifty miles of line between Woking and Southampton airport. In this system there are three control points; taking the one at the signal box at Basingstoke as an example, the signalman can address any of the five Basingstoke

platforms and/or the "up" or "down" platforms at any of the four other stations under his control (Hook, Winchfield, Fleet and Farnborough).

The system employs two pairs of audio cable that already existed along the line. A signalman presses a button corresponding to the particular platform, at the required station, he wishes to address. All four wires are used to send a parallel digital address code which selects the p.a. equipment at the required platform. If the p.a. equipment is not already in use a cable pair is released from the addressing task and is used to inform the control point that this is so. The signalman can then make his announcement. The communication system employs a 20kHz f.m. carrier which is amplified at each remote point and then passed on to the next point.

The circuit is arranged to automatically provide a warning should any part of the transmission path be interrupted.

## Post-doctoral research fellowships

The Science Research Council has announced a new scheme of post-doctoral fellowships for outstanding young British research workers to enable them to devote the whole of their time to original and independent research. Under this scheme, starting in October, there will be about 25 awards of much higher value than the 40 awards made last year.

Selection will be based on ability and independent achievement. Graduates in the U.K. may, with the approval of their head of department, apply to S.R.C. for research grants. The new fellowships, which will normally be held for a period of two years and which will be worth between £1,450 and £1,800, will be tenable at institutions in the U.K. or abroad acceptable to the Council—these include universities, colleges and government or industrial laboratories—which can provide the facilities necessary for the proposed research.

## Component distributors association formed

With the primary objective of "defining clearly the role that the distributor plays in the chain of events from the creation and production of a product to bringing it to the market place", nineteen companies have formed the Association of Franchised Distributors of Electronic Components (AFDEC). Prime mover was Waldo Thorn, of Celdis Ltd, who called a meeting in February attended by 48 representatives of electronic component distributors. Following the election of a preliminary council with Mr. Thorn as chairman, objectives of AFDEC were discussed including its relationship with the Ministry of Technology and other associations such as the Radio and Electronic Manufacturers' Federation.

## Domestic receiver deliveries

The British Radio Equipment Manufacturers' Association has released details of the total disposals of receivers to the trade during 1969. In the list below the 1969 figure is followed by the 1968 figure in brackets and the percentage change. Totals given should be multiplied by 1,000.

Radio receivers 737 (1,025) - 28%; car radios 340 (388) - 12%; radiograms 201 (226) - 11%; monochrome television receivers 1,673 (1,753) - 5%; colour television receivers 154 (121) + 27%.

The highlight during 1969 was, without a doubt, the colour television disposals which showed a large increase, particularly in the last four months of the year.

The Electronic Industries Association of America has also produced results for 1969; these are presented as above, however a multiplication factor of one million should be applied.

Radio receivers 9.7 (11.8) - 17.7%; car radios 10.1 (10.7) - 5.4%; monochrome television receivers 5 (5.55) - 10.4%; colour television receivers 5.5 (5.8) - 7.7%.

It is interesting to note that of the 39.4M radio receivers sold in America in 1969 only 4.7M were home produced.

## Wildlife tape recording competition

The European Broadcasting Union felt that the European Conservation Year 1970 was an ideal time to recognize the importance of wildlife sound recording, so, at the suggestion of the B.B.C., it decided to sponsor a wildlife tape recording contest. The competition is open to all living in Europe and Iceland.

There will be four categories and the winner in each will receive a "silver nightingale trophy" and the runner up a "bronze nightingale trophy". An outright winner will be chosen from the category winners who will be presented with a "golden nightingale award". Enquiries for entry forms and rules should be addressed to the Wildlife Sound Librarian, B.B.C. Natural History Unit, Broadcasting House, Whiteladies Rd, Bristol BS8 2LR.

## Travelling award

The Royal Television Society invites applications for the 1970 John Logie Baird Travelling Award which has been increased this year to £500.

## What they say

"It wasn't until I joined the B.B.C. that I learned that the Heavyside layer was not the top brass at Broadcasting House!"—Lord Hill, chairman, B.B.C., speaking at the I.E.E. annual dinner.

# Letter from America

Sales of recorded stereo tapes accounted for approximately 26% of all recorded music sold in America during 1969 and should increase to 35% in 1970, according to Donald Hall, vice-president of Ampex. He went on to forecast that tape sales would equal sales of discs by 1972 or 1973.

At the moment, 8-track cartridges are still more than holding their own with 74% of the sales, followed by 15% for cassettes. There is no doubt that cassettes will gain in popularity and eventually overtake the 8-track cartridges which are mainly used in car-players. North American Philips confirm the rapid increase in popularity of cassettes and a spokesman said "Cassette equipment represents the fastest growing segment of the home entertainment industry—and it will gain a further impetus when cassette players are fitted to the new 1971 cars". Incidentally, nearly 10 million car radios are sold in the U.S.A. every year—more than the sales of domestic radios!

Before leaving the subject of sales—a few words about television. Last year colour sets sold just over 5 million—about 10% more than black-and-white. RCA have just announced plans to build a 20,000-ft plant in Mexico for the manufacture of colour tubes, and a larger one in Puerto Rico which will concentrate on shadow masks. One of the new RCA portables features a remote control unit which "gives instant shut off without need to turn down the volume control first". This is accomplished with a "computer-tested integrated circuit amplifier". The automatic fine tuning is also "computer designed"!

Meanwhile, that flat television screen is still just around the corner and the latest contender in the race is International Devices Ltd., of Fort Erie in Canada, who say they will have a flat-screen receiver in production by the end of the year. An electro-luminescent coated screen is used with vertical and horizontal potentials applied by an XY grid. It is claimed that picture brightness has been achieved up to 25% better than on standard colour TV sets now on the market. According to the company president they are only working with colour because "black and white is more difficult" and he is reported as saying that

screen sizes up to 36 by 50 inches would present no problems.

Much work is going on behind the scenes with video cassette recorders and Capitol announced recently that they had one on the drawing board awaiting the establishment of industry standards. They stated that "a cassette television programme of a half hour or full hour would probably sell for about \$30" (£12 10s.) and they also forecast a TV programme rental library system. The Capitol unit is simply wired to the aerial input of the home television set, and then all the user has to do is to insert a cassette and he can watch his favourite programme as many times as he likes.

Big news in the Hi-Fi world is the introduction of 4-channel stereo sound, or Quadrasonics. With present techniques this involves the use of two broadcasting stations but stations in Boston, New York and in other parts of the country have been pairing up to broadcast live concerts and tapes (made by Vanguard) and so have created considerable interest. True, there was some (predictable) criticism from a few sceptics who believe the whole idea is a gimmick thought up by speaker manufacturers or tape companies, but the majority of people who have heard 4-channel sound have been most impressed. How are the microphones placed? Well, for the initial Boston experiments (with the Boston Symphony Orchestra) two microphones were in the usual stereo positions and two more were placed at the rear. One station carried the signals from the left front and left rear and the other from the right front and right rear. This unusual arrangement was in the interests of compatibility but recently the organizers had second thoughts and now one station transmits the signals from the front pair and the other station from the rear two. Not compatible at all; but I wonder how many complaints were received?

It is claimed that 4-channel stereo is much more *immediate*, more exciting than 2-channel (you could not use it as background music) and some enthusiasts are even saying "the difference between 4-channel and conventional stereo sound is greater than between 2-channel stereo and monophonic reproduction". It is

certainly true that room acoustics become less important and there is a greater feeling of being at the actual performance. Some of the demonstrations feature large orchestral works where the rear channels supply most of the reverberation and this does help to give that 'you are there' feeling. However, I believe opera and drama will gain the most from the extra dimension. On the other hand, many contemporary composers are very enthusiastic about the possibilities and Henry Brant finds it ideal for his "space music". In a recent recording session at the large Eastman theatre, no less than five different groups of performers were used, on stage, in the balconies and in the aisles.

If Quadrasonics becomes popular, what are the record companies going to do about it? You may be sure they are not ignoring it and several companies are busily working on 4-channel discs using multiplex systems and it is rumoured that some will be demonstrated at a meeting of the Audio Engineering Society in New York very soon. It is obvious that it is not *really* feasible to use two separate broadcasting stations (except for experimental purposes) and so various schemes have been proposed that will allow 4-channel transmissions from one station. One of the most practical involves a multiplex arrangement and it is described by L. Feldman in *Audio* for January 1970. The only disadvantage is a slight loss in bandwidth of the rear channels but this may have to be accepted. Tapes, of course, present no problems and several recorders are now available with stacked heads. Scott brought out a Quadrasonic receiver in December but the majority of manufacturers are waiting to see what happens before they commit themselves. Among them curiously enough is Acoustic Research (AR) who have played a large part in organizing the Boston experiments. G. W. TILLET



*Our contributor George Tillett has been appointed editor of "Audio". Since going to the U.S.A. five years ago he has successively been director of engineering in the Pennsylvania plant of Fisher Radio Corp. and executive vice-president of Audio Dynamics Corp. Prior to leaving this country he had been with Daystrom, as chief engineer, and latterly with Wharfedale as technical director.*

# SONEX 70

## Exhibitors at the forthcoming London Hi-Fi Show


With the transfer of the annual London Audio Festival & Fair from a hotel setting to Olympia and from the spring to the autumn there has apparently been agitation by some manufacturers for a spring show similar to those run first at the Waldorf Hotel (under the auspices of the defunct British Sound Recording Association) and latterly at the Hotel Russell. As a result the Federation of British Audio formed a company—British Audio Promotions Ltd—to organize a specialist hi-fi exhibition. The first of what is planned as an annual event, is to be held for four days (April 23rd-26th) at the Skyway Hotel, near London Airport, Heathrow. Each of the 50 manufacturers taking space at 'Sonex 70', as the exhibition is called, will have an individual hotel room for demonstrations. One advantage of the Skyway Hotel is that, because of

its proximity to the airport, all the rooms are sound proof. The list of manufacturers exhibiting is given below.

It is encouraging to note that although the show is sponsored by the Federation of British Audio, there are a number of overseas names among the exhibitors.

The show will be open from 11.00 to 21.00 on each of the first three days. On the last day (Sunday) it will open at 11.00 but close at 18.00. Admission on the first day is restricted to the trade. Tickets for the other days are obtainable free from exhibitors, audio dealers or the exhibition organizers British Audio Promotions Ltd., 49 Russell Square, London W.C.1.

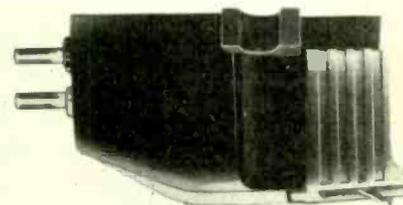In our June issue we plan to include a more detailed account of some of the new products, a few of which are illustrated here.




Goldring's G.850 stereo magnetic cartridge costs £6 10s and is designed to operate at a playing weight of between 2 and 3½ gm. The stylus has a 0.0007in diamond tip.

The XV-15 series of Pickering magnetic cartridges range in price from £15 15s (XV-15/100) to £39 (XV-15/750E). Some units have spherical and others elliptical styli. A groove-cleaning brush is fitted to each cartridge.

### Manufacturers at the Show

Acoustic Research	Metrosound
Akai	Modular Audio Components
Arena	Mullard
Armstrong	
Audiotechnica	Ortofon
	Peak Sound
BIB Multicore Solders	Pickering
Brenell	Pioneer
	Quad
Cambridge Audio	Radon
Cosmocord	Rank Wharfedale
	Revox
Daystrom	Richard Allan
Decca	Rogers
Dynatron	Rola-Celestion
	Rotel
Goldring	Sansui
Goodmans	Shure
Grampian	Sinclair Radionics
	Sugden, A. R.
I. M. F.	Sugden, J. E.
	Tape Recorder Spares
Jordan Watts	Teleton
	Thorens
KEF	Toshiba
	Vortexion
Leak	Williman Export
Lowther	
Lugton	
Lux	

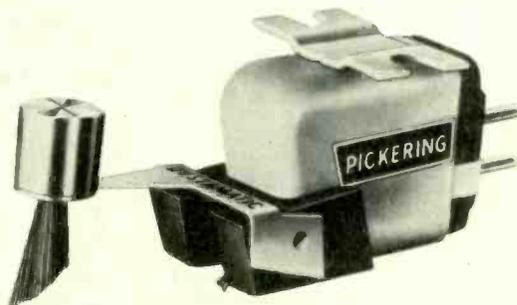

A reverberation amplifier, the SR202, from Pioneer enables controlled reverberation effects to be added to recordings that are judged to be too dry or dead. The system employs two time-delay circuits and the output is claimed to be free from peaks. The price is £45 9s 11d.

# Letters to the Editor

*The Editor does not necessarily endorse opinions expressed by his correspondents*

## Measuring crossover distortion

Even by allowing Mr. J. F. Golding his margin of decibels by calculating out the noise up to a level 3dB above that of the t.h.d. ("Letters" March 1970 issue), his 57dB s/n ratio amplifier turned down from maximum power to 10mW by means of the volume control would—based on 10W maximum power—permit easy measurement of little less than 0.5% t.h.d. Not easily down to 0.1% as stated by Mr. Golding in his letter. The reason for this, of course, is that the noise of the power amplifier although relatively small is significant. The full-power s/n ratio would not be retained at the low power, for this implies that the ratio of noise relative to full power is enhanced in exactly the same ratio as the power is diminished. In reality, while the output power is reduced from maximum by, say, 30dB by turning down the volume control, the noise yield at the output rarely falls by more than 10 to 15dB over the same volume control range. Obviously, the noise of the pre-amplifier section passed by the volume control adds to the noise of the power amplifier by a square law.

I initially test at maximum setting of the volume control because some pre-amplifiers tend to veer towards non-linearity more easily than may be appreciated. Moreover, the control might affect the frequency response either unintentionally or purposely (e.g., fixed 'loudness' action lifting treble and/or bass as the control is turned down), and the maximum setting ensures that an established test datum level can be quickly repeated, not always as simple as it may seem, by using the amplifier's volume control. Nevertheless, subsequent to exploratory tests there may be merit in rechecking at low volume-control settings and when so warranted I do this. It is also noteworthy that the noise decrease at the output, on turning the volume control right down to minimum from maximum, can be quite small, depending on the nature of the volume control circuit and the noise performance of the circuits either side.

Mr. Golding fails to specify the wave analyser which provides the 3,000:1 input noise bandwidth to filter bandwidth, but I am sure he will agree that the readout of such low-level distortion components as implied by his dB values relative to a low impedance output load is not exactly an

'easy' matter. I have found that an s/n ratio improvement of about 30dB based on a 10-W 8-ohm 80dB s/n ratio amplifier running at 0.1mW allows a threshold read-out little better than 0.1% selected harmonic. For ultimate measurements deep into noise one has to adopt phase detection and correlation techniques, the latter allowing useful signal indication up to 60dB deep in noise.

T.H.D. is a popular way of amplifier distortion appraisal in spite of all the other more sophisticated methods. It is less costly and less time consuming than analysis of individual waves. It is ideal for speedy distortion comparisons, and with a 'scope attached to the readout the knowledgeable operator can quickly glean useful information about the nature of the distortion and observe crossover artifacts if they exist. Treble-end performance can also be highlighted and the presence of odd-numbered high-order harmonics is revealed to the owners of both sensitive and cloth ears.

GORDON J. KING,  
Brixham,  
Devon.

## V.H.F. services

I was touched to notice in his March contribution that "Vector" has been studying the wisdom of the ages. Now that my friendly neighbourhood tower crane has moved away I think I was probably right in 1947 to urge a more detailed study of pulse modulation. But after all, was it in 1933 that the quite successful tests of single sideband and carrier were made from Daventry? And where did they lead us?

Two other articles of the period still have some interest. The f.m.-a.m. controversy was bedevilled by the statement in the House of Commons by the P.M.G. of the day that no discussion could fruitfully take place until he had considered an entirely new system of modulation. He did not tell the Post Office engineers what it was. He did not tell the BBC engineers what it was. But it was entirely new and there was a change of Government and when his party came back they didn't make him P.M.G. So we shall never know.

Another topical article followed, I think, my discovery that at Copenhagen

the British contingent regarded engineers and foreign office staff as Falstaff saw bread and wine.

Without going into details we can split music into three classes: pop, palm court and proper. Land-lines need not be rationed, so that by using synchronized carrier only a small number of m.f. channels need be locked up to provide three European music programmes. The remaining channels are available for speech programmes, which are essentially national or local. Any country getting two or three national channels then would offer a choice of five or six programmes, even though its share of the production costs of the three common programmes would be small. The only trouble is that this solution provides the most listening, not the most jobs.

A final memory is of a letter, circa 1946, urging that television services should not be resumed. As an engineering problem the transmission of moving pictures was worth doing, because it was there. But there would never be the talent to produce 30 or 40 hours of programmes a week. How right I was.

THOMAS RODDAM

## Theoretical and measured response

While musing on the operation of the tone circuitry in the pre-amplifier designed by Dr. Bailey, I did a few mental calculations, and was interested to note an apparently large discrepancy between the measured and theoretical treble response curve.

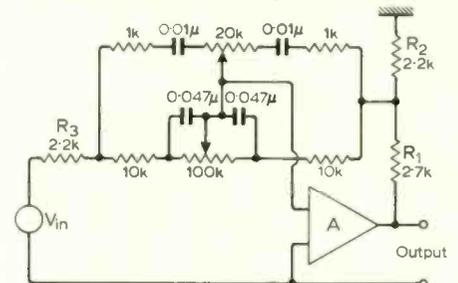


Fig. 1. Circuit of tone control.

Consider Fig. 1. At high frequencies all capacitors can be assumed low impedance, and in the limiting case, zero impedance. So for maximum treble setting the high-frequency gain asymptote can be calculated if it is assumed that the two arms of the network are acting operationally. The limiting high-frequency equivalent circuit of Fig. 1 is shown in Fig. 2.

So the high-frequency gain asymptote is given as below:

$$G = \frac{1.2 + \frac{21 \times 10}{21 + 10}}{2.2 + \frac{1 \times 10}{1 + 10}}$$

$$= \frac{8}{3.1}$$

So  $20 \log G = 8.2 \text{ dB}$ .

This value of  $G$  is about 10dB less than the apparent high-frequency asymptote given by Dr. Bailey. I would like, with

respect, to suggest that perhaps the frequency response curves given were measured before the output attenuator  $R_1$ ,  $R_2$  and the input resistor  $R_3$ , were added. These are respectively included to increase the overall gain of the circuit to about 2, and as load impedance to match the treble filter which feeds directly into this stage.

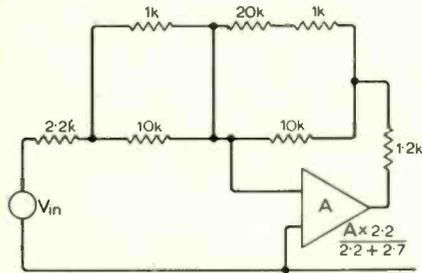


Fig. 2. High-frequency equivalent circuit.

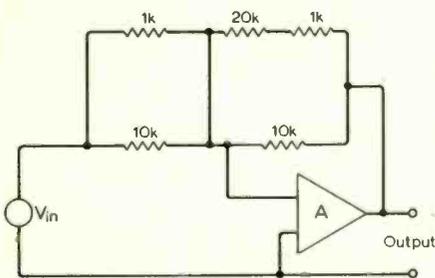


Fig. 3. Unity-gain version of Fig. 2 omitting  $R_1$ ,  $R_2$  and  $R_3$ .

The equivalent circuit at high frequencies for maximum treble lift can now be drawn as in Fig. 3 with  $R_1$ ,  $R_2$  and  $R_3$  removed.

Now

$$G = \frac{21 \times 10}{21 + 10} \bigg/ \frac{1 \times 10}{1 + 10}$$

$$= \frac{6.8}{0.91}$$

So  $20 \log G = 17.5 \text{ dB}$

This value agrees with Dr. Bailey's and is a reasonable figure.

It should be noted, therefore, that, so as not to restrict the range of the controls  $R_3$  should be as small as possible.

It is also apparent that  $R_3$  should equal the parallel combination of  $R_1$  and  $R_2$  otherwise the input and feedback portions of the network will not balance correctly with the controls centred.

P. M. QUILTER,  
University of Sussex,  
Brighton.

**The author replies:**

I was very interested in the letter from Mr. Quilter and his comments on the performance of the tone-control circuit. He is perfectly correct in his deductions and I must confess that the original curves were obtained with the treble filter circuit omitted. For this reason it is better to use the modified circuit where the filter components are bypassed with the filter out.

Personally, I have found that with speaker systems of low resonance (and similar performance pickups), treble filters are unnecessary unless a particularly dreadful recording is being played. 'Edginess' in reproduction is nearly always due to defects in speaker and/or

pickup transient response—assuming that there is no crossover distortion trouble in the amplifier in use.

Similarly my treble controls are nearly always 'flat' and I use only a small amount of bass boost to make up for dynamic levels in playback. For my part I cannot see the need for  $\pm 20\text{dB}$  variation in controls, but I must agree that it looks better on a specification than say  $\pm 12\text{dB}$ .

Perhaps this is the reason why only one or two people have queried the performance (and then only h.f. boost). However it becomes obvious from Mr. Quilter's deductions that the two end-stop resistors of  $1\text{k}\Omega$  on the treble control are redundant. Also the  $2.2\text{k}\Omega$  resistor  $R_3$  should be  $1.2\text{k}\Omega$  for accurately balanced controls.

All this goes to show how simple modifications for one purpose can seriously modify the performance of a circuit in other directions. Many thanks Mr. Quilter, for a very useful lesson in the value of fully analysing the effects of modifications.

ARTHUR R. BAILEY

**Capacitor-discharge ignition**


During the last five years I have been interested in electronic ignition systems and after seeing Mr. Marston's article in the January issue of *Wireless World* I am prompted to write offering several comments on my own experiences.

In winter sub-zero conditions, the battery may drop to as low as 7V with a big engine and can rise to 15.5V under alternator charging. These limits are very severe on any ignition circuit, and accordingly in this continent [America] nearly standard ignition systems consist of a  $1.5\Omega$  ignition coil and a  $1.5\Omega$  series ballast resistor. While starting the ballast resistor is shorted out and the system gives fantastically good cold-weather starting. I doubted whether Mr. Marston's self-regulating converter would regulate well over a 2 to 1 voltage range, so I set about constructing his converter with a 17V 2A transformer that I happened to have brought back to Canada from a recent two-year stay in Cambridge. It has 210-, 220- and 240-volt primary taps. After rewinding two times 65 turns (the original had 136 turns) the converter put out about 500V in an ignition circuit with identical high-voltage components to Mr. Marston's circuit! There were rather large

spikes at the transistor collectors and even at a very low sparking rate (induced manually) the voltage went down to 400V quickly. It seems the spikes do not have much energy to charge the  $1\mu\text{F}$  discharge capacitor. At 10V d.c. input, the output was still 400V unloaded but this dropped to 300V at a low sparking rate. At 7V d.c. input the spark was inadequate. Mr. Marston's circuit may have regulated better (no two transformers are alike) but I feel such circuit action is not desirable where reliability is necessary. My friends and I have solved low starting voltage problems in several ways. One friend designed his system for 500V with 15V d.c. input, and this suffices until the battery falls below about 8V. Another friend uses a relay to switch in extra secondary turns on the converter transformer only during starting. My own solution is to add across the s.c.r. a large electrolytic capacitor in series with a  $10\text{-}\Omega$  2-W resistor. The converter is a high-frequency unit ( $\sim 1\text{kHz}$ ) with no spikes, which supplies 400V with 15V input. When the ignition key is first turned on, the capacitor ( $\sim 40\mu\text{F}$ ) charges in a fraction of a second to  $\sim 400\text{V}$ , and the first 30 sparks are good and hot, no matter what the battery voltage.

Another serious problem is caused by the ballast resistor. After an ignition pulse, the converter again charges the discharge capacitor, causing typically several volts drop in the resistor. When charging ceases, the increasing voltage applied to the s.c.r. firing circuit could initiate a trigger. This has happened to some of my designs in the past and to combat any spurious triggering a 6-V 1-W zener diode was placed across the contact breaker. Any noise on the battery line produced by an erratic regulator will also be squelched by this zener. In Mr. Marston's circuit, transistor  $Tr_1$  has an emitter-base breakdown voltage of about 7V, and the zener will also prevent very large base reverse currents which must flow when the contact breaker closes in the circuit as drawn. I do admire the trigger circuit for its positive ability to remove harmful effects of point bounce, and have already adopted it in my own unit.

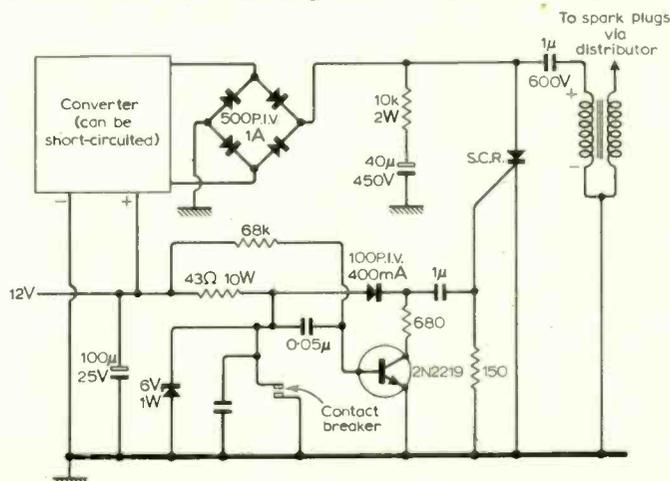The last point which I should mention as a purist is that a spark plug fires with lower voltage when the central electrode is negative, due to thermionic electron emission



Mr. Vanderkooy's circuit. The converter is an h.f. near-perfect square-wave unit using a nickel-tape-wound toroid.

from the hot electrode. All ignition systems, positive or negative earth, operate this way, and this feature should be preserved in an electronic system. A little analysis will show that in a standard ignition coil designed for a positive earth system (many British cars) the SW terminal should be grounded. (Fig. 6 in Mr. Marston's article.)

In conclusion perhaps readers would like to see my final circuit.

JOHN VANDERKOOY,  
University of Waterloo,  
Ontario.

*The author replies:*

From his letter, it seems that Mr. Vanderkooy has failed to grasp the operating principles of the converter circuitry, and does not appreciate the electrical requirements of an ignition system under cold start conditions.

I can assure Mr. Vanderkooy that the design of the converter section is such that it is virtually impossible for its output to exceed  $414V \pm 5\%$ . If higher voltages are obtained, it can only be because  $T_1$  has been given a turns ratio greater than 15:1, or because  $ZD_1$  and  $ZD_2$  are not  $27V \pm 5\%$  types. If output voltages rise appreciably above the designed value, the s.c.r. (a 400V type) may be destroyed.

The ignition system has been specifically designed to give good cold-start characteristics; overshoot regulation is utilized to this end. While it is true that the overshoot (what Mr. Vanderkooy calls 'rather large spikes') contains very little energy, this energy is sufficient to meet cold start needs. Typically, a starter motor will turn an engine over at a 'brisk' rate of about 300 r.p.m. under 10-V cold start conditions, and at a 'sluggish' rate of only 150 r.p.m. at 8V. The table below shows the measured performance of the circuit under these conditions, and also at 7V cold start; I consider the performance to be adequate under all conditions, and I feel sure that Mr. Vanderkooy will agree with me if he carries out a little practical research into the subject.


No. of cylinders	C <sub>1</sub> charge voltage		
	7V, 150 r.p.m.	8V, 150 r.p.m.	10V, 300 r.p.m.
4	260	290	325
6	250	280	322
8	240	270	310
12	237	265	300

Finally, I suggest that if Mr. Vanderkooy's battery potential does in fact fall as low as 7V under cold start conditions, there is something seriously wrong with either his battery, his starter motor, or his choice of lubricating oil; battery potential should in fact never fall below 8 volts, even under the most severe cold start conditions.

R. M. MARSTON

Having done some work on this system of ignition may I bring out a few points which may be of interest to readers? The converter transformer can conveniently be one of the centre tapped l.t. types which are on the market. Working backwards a 9-0-9 volt secondary is about right for square-wave working at 12V d.c. and gives a frequency

of a few hundred Hz. The capacitor  $C_1$  does need to be a low-loss type, a paper capacitor was found to become very warm at spark rates of 300 per second corresponding to 6000 revolutions per minute with a six-cylinder engine and 9000 with four cylinders. It is worthwhile to include a recovery diode across the s.c.r.: nearly 20% of the energy can be recovered from the leakage reactance on the backswing. Best results are usually obtained with a 6V 'sports' type coil which has a low primary inductance and resistance, the rated voltage of the coil does not matter much with this type of circuit. Putting a

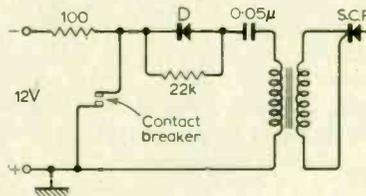

'crowbar' across the inverter output at each spark seems rather brutal and I have always used choke charging with an inductance of 3 to 5 henries between the inverter and  $C_1$ . The circuit can be simplified by using a small differentiating transformer to produce the s.c.r. firing pulse.

Diode  $D$  and the  $22k \Omega$  resistor give a delayed recovery to avoid misfiring as a result of contact bounce. The normal ignition capacitor is removed when using this circuit.

I have had an ignition system of this type in use now for some 6 years and 70,000 miles with complete success.

H. HARPER,  
Fleet,  
Hants.

*The author replies:*

When designing the original circuit I tried to find a standard l.t. transformer that could be used in the system; I considered the possibility of using a 9-0-9 volt one, but found that they were generally available in 2- and 4-amp ratings only. Unfortunately the 4-amp type (which is essential for operation up to c.b. frequencies of 660Hz) was found to be physically too large to fit inside the standard chassis in which I built the unit. The 2-amp type was found to give a reasonable performance when used on a four-cylinder engine at speeds up to 6000 r.p.m., but to be inadequate when used on engines with six or more cylinders (the reasons for this should be self evident).

Regarding the use of a diode to give energy recovery on the backswing;  $D_3$ - $D_6$  already perform this function in the original circuit!

Regarding the use of a 6V 'sports' coil and the removal of the normal c.b. capacitor; the original system was designed to use the existing coil and c.b. components, thus keeping building cost to a minimum and enabling the ignition to be changed from C-D to normal, and vice versa, with great ease. Mr. Harper's mods nullify these features!

R. M. MARSTON

I have been developing a capacitor-discharge ignition system for some time and I think you may be interested to know how I have attempted to overcome some of the problems mentioned by correspondents.

I have positively prevented s.c.r. latching by doing two things. I have arranged a feedback system to provide the gate drive. This consists of a monostable with a feedback connection from the s.c.r. anode which causes the drive pulse to be switched off as the s.c.r. switches on. This prevents gate drive from latching the s.c.r. I have also used a driver h.t. converter. In this the pulses from the driver circuit are fed through a gating circuit before being fed to the output transistors, driving the transformer. So by using the gating circuit to switch the converter on and off, very fast and reliable turn on, and turn off may be obtained. This facility may also be used to regulate the voltage to which the capacitor is charged by using a comparator to measure this voltage and switch the converter off when the capacitor is suitably charged.


Finally I would like to make a few comments about the e.h.t. coil and the contact breaker points. Standard coils are not the best for use with capacitor-discharge systems. A far better coil would be a low-inductance primary, closed-iron type. These offer higher efficiency, higher operating speeds and less need for energy retrieval to recharge the capacitor (that is using the coil's back e.m.f. to charge the capacitor).

Also I believe it would be worthwhile for the more ambitious constructor to try to replace the points with a photo-electric magnetic or reed switch pick-up as points can be quite troublesome when lightly loaded.

D. J. WHITE,  
Harborne,  
Birmingham.

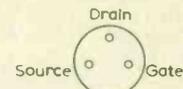**Modular pre-amplifier design**

Some users of this design (*W.W.* July 1969) have found a somewhat higher level of background 'hiss' than had been expected at very low settings of the volume control. Where this has occurred it is usually due to the f.e.t. used as  $Tr_5$  in the tone control circuit.



A much improved performance in this respect can be obtained by the use of an Amelco 2N4302 or 4303. In the former case it may be necessary to modify the biasing of the f.e.t. to ensure that the drain current is at a suitable level. (The voltage measured at the emitter of  $Tr_6$ , which is a convenient point, should be somewhere in the range 6-11 volts.)

The adjustment of the f.e.t. bias can be done either by alteration to the 33-k  $\Omega$  source resistor, or by connecting a resistor of about 3.3M  $\Omega$  between the emitter of  $Tr_6$  and the gate of the f.e.t.

J. L. LINSLEY HOOD,  
Taunton,  
Som.

# 17 ways to drive


## -all the signals needed for HF traffic

A new flexibility for your HF transmitters is yours immediately you install one of Redifon's three new HF drive units. Each generates up to 17 different modes of transmission covering telegraphy and telephony —CW, DSB, SSB and ISB —at the frequency of radiation. Each is a completely self-contained unit with its own


power supply and a 19-inch rack-mounting front panel to fit neatly into linear amplifier housings.

Units are available with spot tuning or full frequency synthesis, 1.5 to 30 MHz.


Automatic volume compression for extra talk power and voice-operated Transmit switching, both selectable.

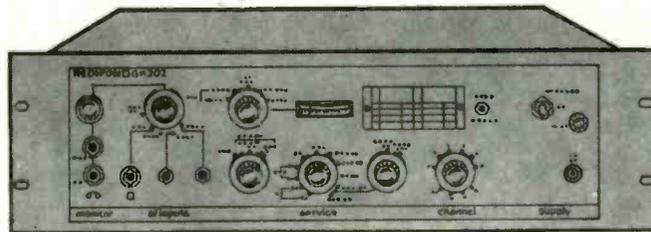

GK 202: 10 spot channels, set by a single switch

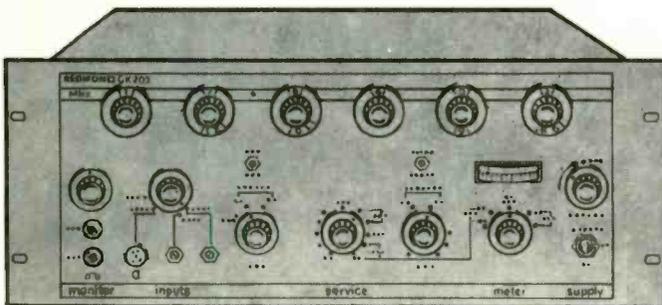

GK 203: Frequency synthesis in 100 Hz increments to provide maximum frequency flexibility

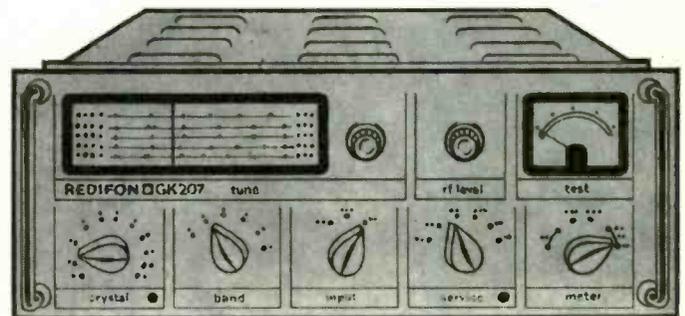

GK 207: 10 spot channels; manually tunable output circuits allow allocated channel frequencies to be changed rapidly by plugging in new crystals, without having to realign any pre-set circuits

Find out more about how flexible and economical your HF drive arrangements can be, by writing to:  
**The Sales Manager,**  
**Redifon Limited, Communications Division,**  
**Broomhill Road, Wandsworth, London, S.W.18.**


**REDIFON** 

A Member Company of the Redifusion Organisation

WW—098 FOR FURTHER DETAILS
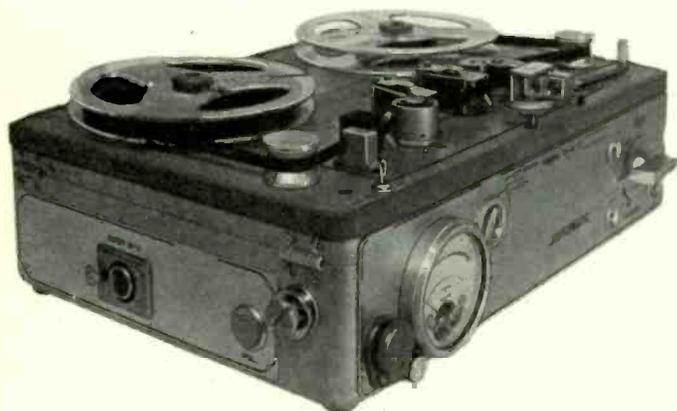
# NAGRA

The world's best portable  
professional audio tape recorder



MODEL IVA Automatic, single speed



MODEL IVB Manual, single speed



MODEL IVD Automatic/Manual, three speeds



MODEL IVL Neopilot, three speeds, Automatic/Manual

\* Lids of transparent, shock resistant plastic, have been removed for clarity of illustration.

These models plus eight variants give the professional user a choice of twelve basic Nagra IV tape recorders. Modular plug-in electronic circuit boards, available for each machine, allow unique flexibility in the choice of recording functions.

Study the Nagra IV brochure and see how you can select precisely the facilities you need, built in to one compact machine of outstanding performance and reliability.

Write or telephone for technical information.

**HAYDEN LABORATORIES LIMITED,**

East House, Chiltern Avenue, Amersham, Bucks., England  
Tel: 02403 5511    Telex: 83251    Cables: Haylab Amersham.

**HAYDEN**

WW—099 FOR FURTHER DETAILS

# Digital Remote Control System

Up to fifteen circuits may be controlled from a remote point with this system

by H. N. Griffiths\*

Up to fifteen circuits can be remotely controlled using this system, the block diagram of which is given in Fig. 1. As can be seen the system consists of two units, a coder and a decoder, connected by some form of data link; this could be a pair of wires or a radio transmitter and receiver.

The coder is a pulse generator which can generate a train of between one and fifteen pulses under the control of the switches  $S_1$  to  $S_{15}$ .

Initially the stop and set zero lines in the coder are UP (positive) so that the multivibrator is stopped and the counter is set to zero. Operation of any control switch ( $S_1$  to  $S_{15}$ ) earths the stop and set zero lines and the counter starts to count pulses from the multivibrator which will have started. When the counter reaches a preselected state, as determined by the logic network and the operated switch, the inhibit line goes UP and the multivibrator stops.

The decoder counter also counts the pulses from the multivibrator which are sent over the data link. When the multivibrator is inhibited the two counters will hold the same number. The logic network in the decoder now actuates the required control.

It is arranged that when the input to the decoder is UP (no signal) the decoder set zero line is also UP, resetting the counter. On receipt of the first negative edge the set zero line of the decoder goes down and is held down by capacitor  $C_5$  so that the counter can accept the incoming pulses.

On release of the control switch in the coder the stop and set zero lines in the coder go UP returning the coder to its initial state and the input to the decoder also goes UP (and stays there) so that the decoder counter also resets. The operated control is now released.

When fewer than fifteen controls are required, the decoder logic network can be simplified. Indeed, if relays are used to operate the controls it is possible to eliminate the logic network by using the relay contacts to perform the decoding logic functions. In such a system (Fig. 2) the relay coils are controlled directly by each stage of the binary counter via the transistor switches (see inset Fig. 3). Fewer relays are required to perform a given number of on-off control functions than is the case when a separate relay is used for each control. The overall reliability of the system is degraded, however, because each control is operated through a group of contacts in series and failure of any one of these will cause at least one control (and possibly half the total number of controls, depending on the position of the fault) to fail. However, the saving in circuitry and the increased simplicity of the system will, in many cases, offset the risk of simultaneous failure of more than one control.

**Communication Channel**  
The simplest form of data link is two wires between coder and decoder. In

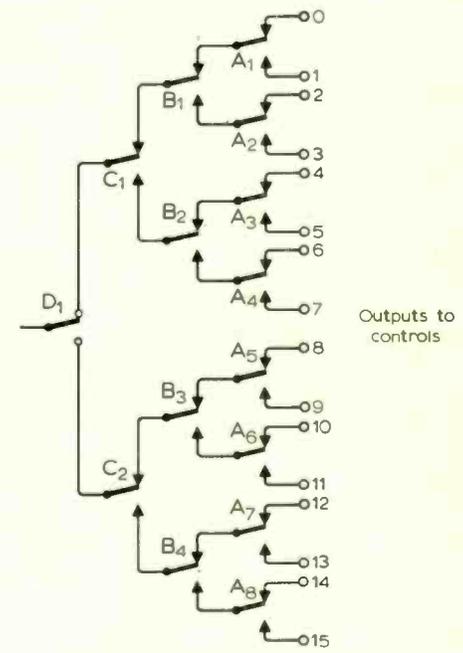
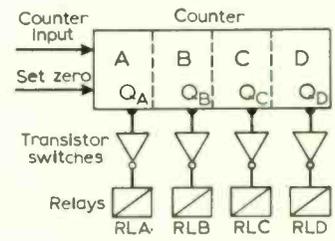


Fig. 2. (Above) Showing how the decoding can be performed with relays.

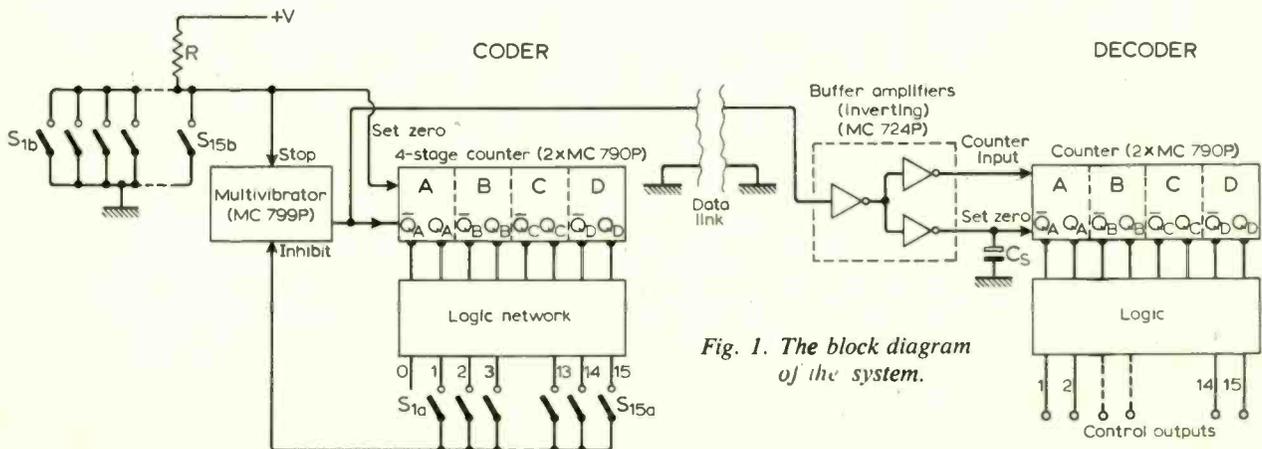


Fig. 1. The block diagram of the system.


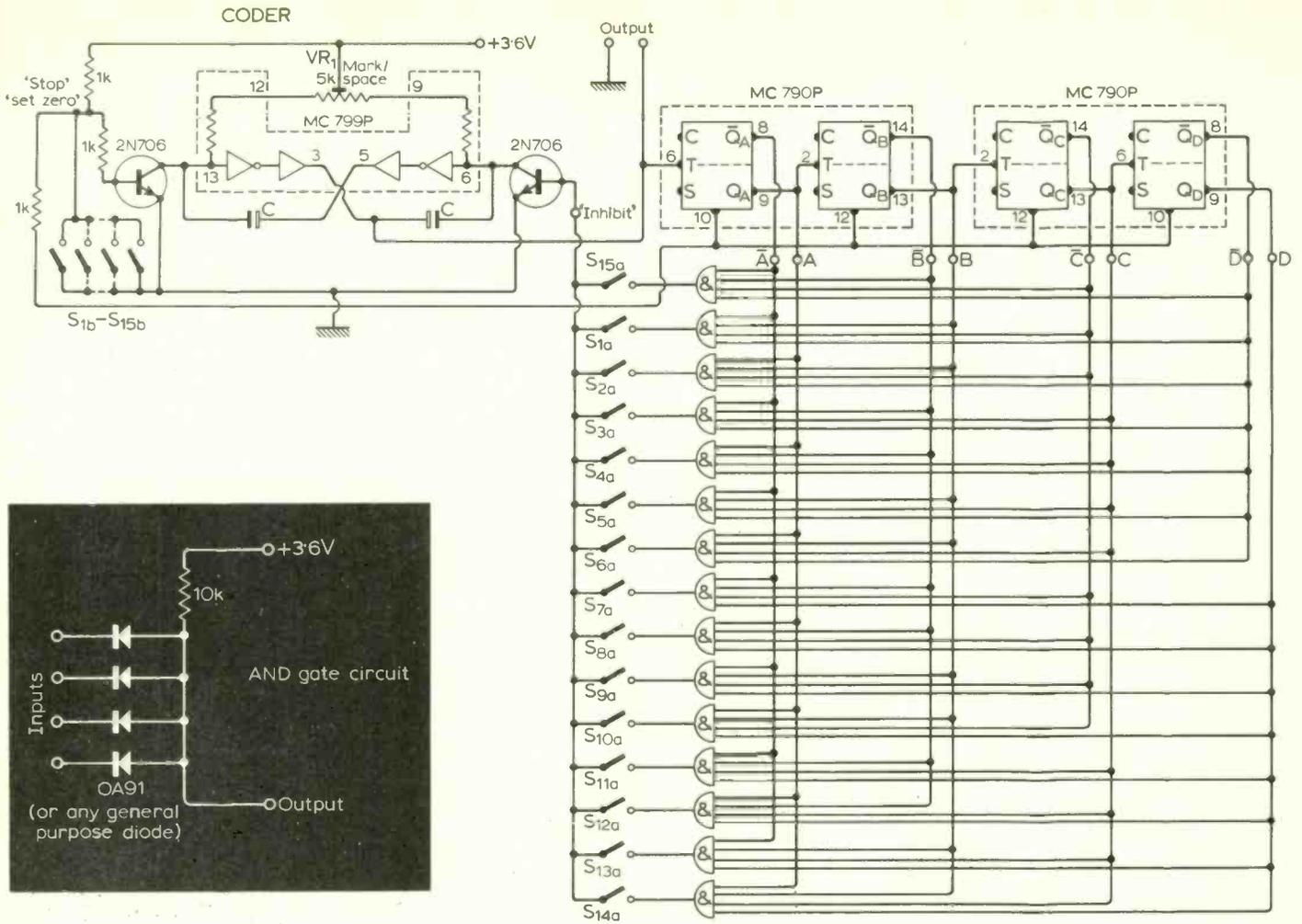
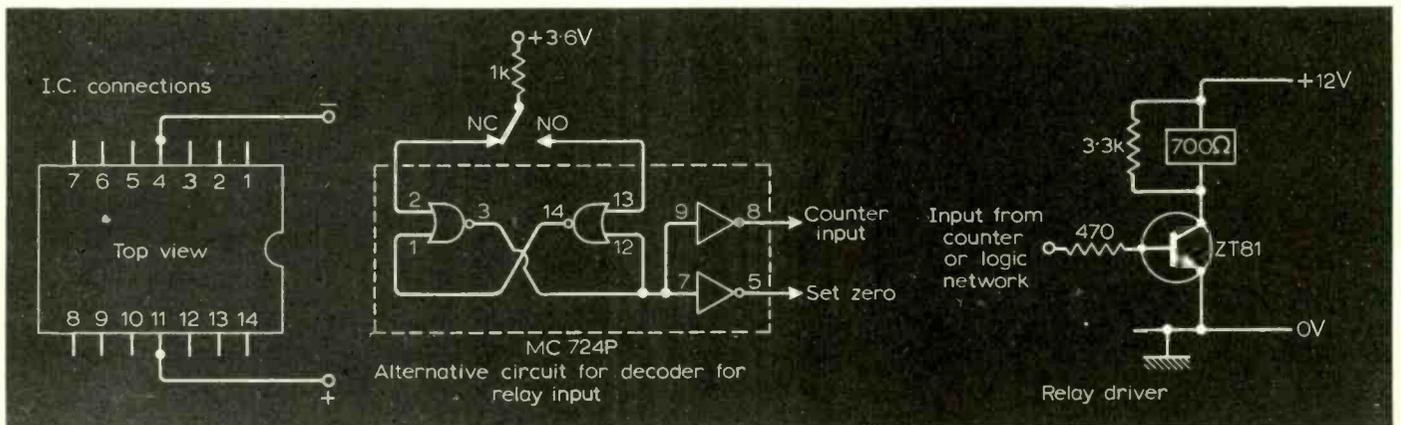


Fig. 3. The circuit of the coder (Above) and decoder (Below). If wished the decoder may be used with the relay decoding system of Fig. 2 or with the same AND gate networks as the coder. The inset above gives the circuit for the AND gates. A relay drive circuit for use with relay decoding and an alternative decoder input circuit for use with a relay input are given in the lower inset.

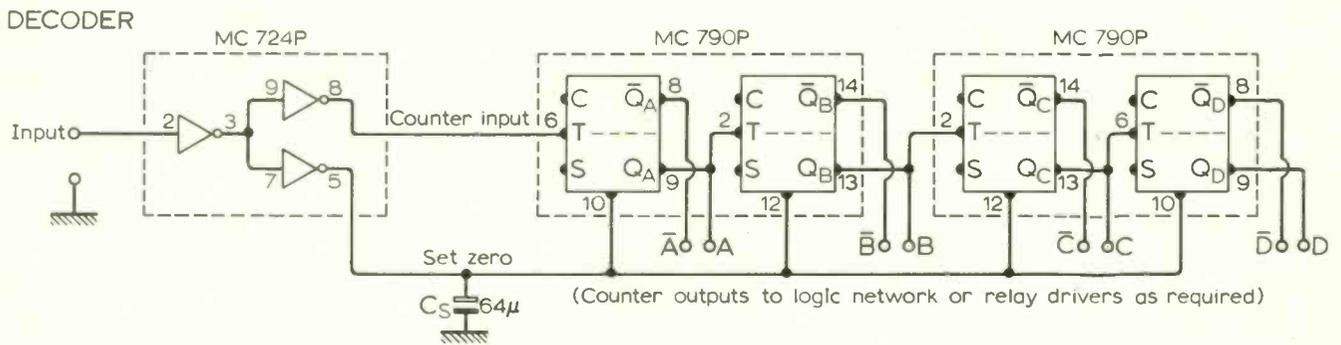

cases where complete freedom of movement of the remote unit is required a radio communication channel can be used to carry the control information. In fact, the original system was conceived as a means for the remote control of a model via a 27MHz radio link. Since amplitude modulation is used in the prototype, the system is susceptible to impulse interference which may be generated, for example, by the electric motors being controlled. It is therefore essential, in such a case, to incorporate a device which rejects impulsive spikes of short duration and allows the decoder to respond only to the relatively slow rate of the signal pulses.

Erratic operation may also occur if the supply voltages to the integrated circuits are allowed to drop too far below the nominal value of 3.6V. Since the decoder input is controlled by a relay in the radio control receiver, special precautions are taken to eliminate faulty triggering due to contact bounce. A 'set-reset' bistable is therefore interposed between the relay contacts and the counter input (see inset Fig. 3).

Transient operation of intermediate controls may occur when the counter in the decoder is stepping to its final state. One method of eliminating this is to connect a suitable capacitor in parallel with each relay.

The pulse rate in the prototype is chosen to be 20Hz. This is high enough to permit rapid selection of controls but sufficiently low to ensure reliable operation of the relay in the radio control receiver. This relay also provides a measure of impulse interference rejection since it responds to the signal pulses but rejects impulsive 'spikes' of short duration.

**Circuitry**

The circuit is given in Fig. 3. Simple diode AND gates are employed in the logic network. If used with a radio control receiver which employs a relay the alternative decoder input circuit should be used. The decoder may be built with the relay decoding circuit of Fig. 2 or with the same logic circuit as the coder, in this case the outputs of the AND gates are used to actuate the required controls.

Adjustment is confined to setting the pre-set potentiometer in the coder for satisfactory operation. It will be found that a mark-space ratio of 1:2 is about right.

In order to simplify the electronic

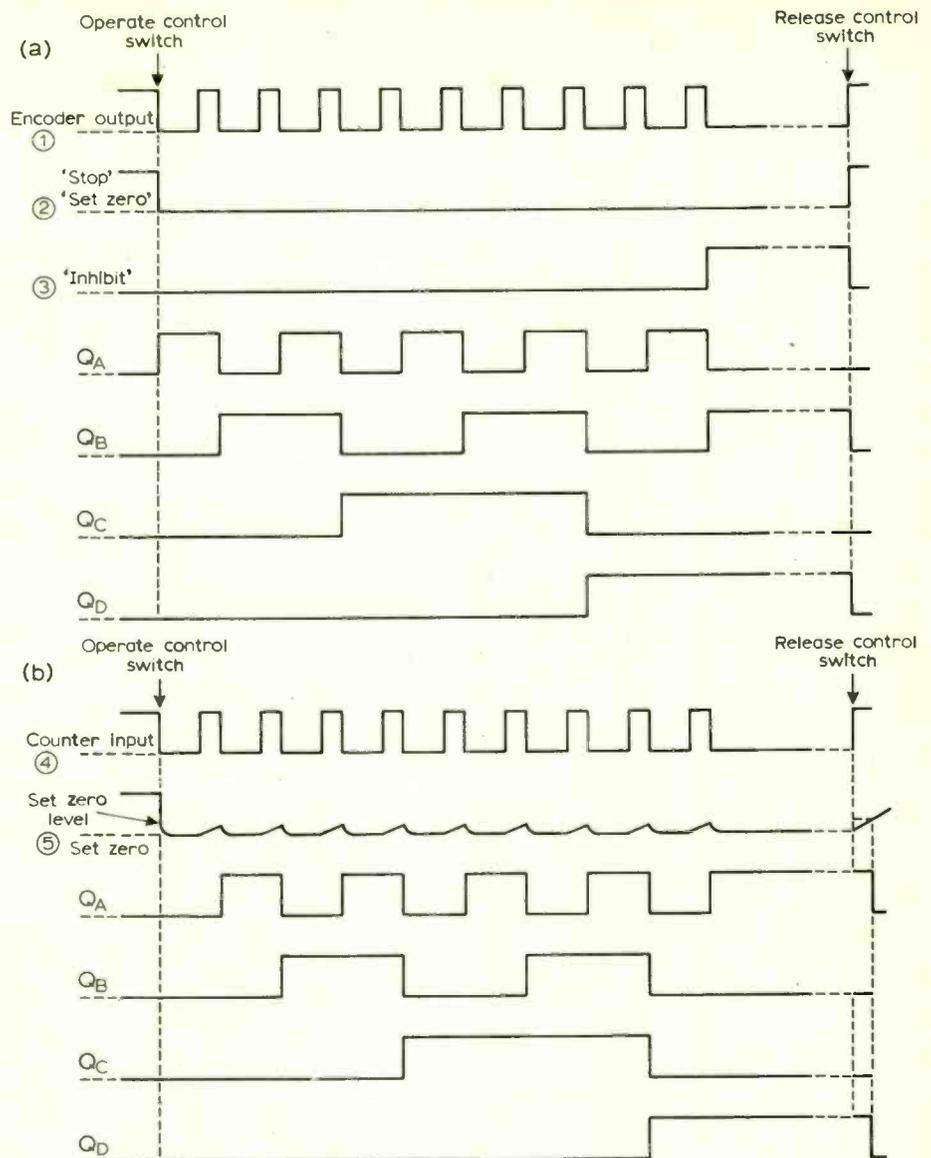


Fig. 4. (a) Coder and (b) decoder waveforms.

design and improve reliability integrated circuits have been employed in both the coder and decoder. The coder uses three dual-in-line packages: a dual buffer (multivibrator) and two dual J-K flip-flops (counter). The decoder also uses three dual-in-line packages: a quad two-input gate and two dual J-K flip-flops (counter). The dual buffer (MC799P), quad two-input gate (MC724P) and dual

J-K flip-flops (MC790P) are all from the Motorola range of r.t.l. circuits.

The prototype uses printed circuit construction but it is suggested that the first attempt at construction be made by mounting the packages on unclad 0.1-inch matrix Veroboard and interconnecting by direct wiring. Any mistakes are more easily rectified when the direct wiring technique is employed.

# Transients

## What happens to an LCR circuit when it's shocked

by Thomas Roddam

Two articles (*W.W.* February and March) have been devoted to considering the "natural" behaviour of simple circuits containing at most one inductance, one capacitance and one resistance. Even so, only one form of the LCR circuit has been considered, the form in which the same current appears at the terminals of each element. The same kind of result will be obtained for the other form, in which the same voltage appears at the terminals of each element. I do not propose to prove this: the actual solution can be obtained in an easier way and there is a limit to the amount of detailed examination which the editor, the reader and the author will stand.

Natural behaviour is the term used for the current which flows in a circuit when, having managed to get some energy in one of the energy stores, either as current in an inductance or charge in a capacitance, or both, the circuit is left isolated while the energy is being dissipated in the resistance element. We have seen that, as a general conclusion, we obtain a characteristic time for each storage type element in the circuit. If we have an LR or a CR circuit we get the current following the simple decay function

$$\exp(-t/\tau)$$

in which  $\tau = CR$  or  $L/R$ , which we call the time constant. For the LCR circuit the general form depends on

$$\exp(-t \cdot R/2L) \exp jt \left( \frac{1}{LC} - \left( \frac{R}{2L} \right)^2 \right)^{\frac{1}{2}}$$

in which we must take both positive and negative signs for the square root term. The interesting case at the moment is when  $L/C > R^2/4$ , which leads to the form

$$\exp(-tR/2L) \cos(\omega t)$$

It is usual to take, not  $\tau = 2L/R$ , but  $\alpha = R/2L$ , the damping constant. Then we have

$$\exp(-\alpha t) \cos(\omega t)$$

Fig. 1 shows the shape of this behaviour. As we increase  $R$ , keeping  $L$  and  $C$  constant, the decay envelope has a shorter time constant, a tighter time scale. In addition,  $\omega$ , the square root term, becomes smaller, thus increasing the time scale of the oscillatory wave. If the decay envelope is falling faster than the oscillatory wave it will dominate the situation. This is rather dull, in wave-form terms, and will not be discussed until

we get to the complex plane. I had, indeed, intended to devote this article to the idea of complex frequency, but when I came to sort out the basic facts I found that transients must come first.

The great problem with the study of the transient behaviour of circuits is that it is complicated and tedious, rather than difficult. There are basically two kinds of transient behaviour. In one, the circuit is given an instantaneous shock, by closing a switch or some other equivalent means, but essentially just hit with a package of energy. We have already the sort of solution we shall expect, although whether it is to be  $\cos \omega t$  or  $\sin \omega t$  or  $\cos(\omega t + \theta)$  depends on how the shock is delivered. The other kind of behaviour arises when we apply an energy source which can produce a continued action. The natural kind of source, which will go on indefinitely, is given by the function the circuit itself has defined, but with an infinite value for the decay time,  $1/\alpha$ . This means simply the common cosine wave,  $\cos \omega t$ . We set up the circuit of Fig. 2. After a good few times, the time  $1/\alpha$  (for the LCR circuit), any energy involved in the starting process will have been dissipated and the system will have settled to the steady state.

The voltage across the capacitor will be

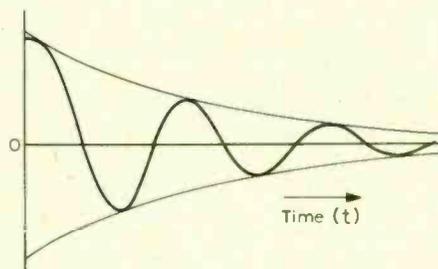


Fig. 1. The shape of  $\exp(-\alpha t) \cos(\omega t)$  enclosed in the decay curve  $\exp(-\alpha t)$ .

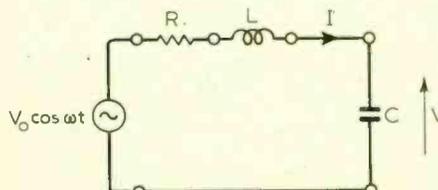


Fig. 2. The driven circuit.

given by the equation

$$V_C = \frac{1}{C} \int I dt = V_0 \exp(j\omega t) - L \frac{dI}{dt} - RI$$

The point of writing  $V_0 \exp(j\omega t)$ , with the implied operation of taking real parts later, is to make the mathematics have a simpler pattern. The equation is rearranged to the standard form

$$L \frac{dI}{dt} + RI + \frac{1}{C} \int I dt = V_0 \exp(j\omega t)$$

We are going on for ever, so the current will have the same shape as the voltage, or so we guess.

$$I = I_0 \exp(j\omega t)$$

If so:

$$(j\omega L + R + \frac{1}{j\omega C}) I_0 \exp(j\omega t) = V_0 \exp(j\omega t)$$

$$\text{or } I_0 = V_0 / \left( R + j\omega L + \frac{1}{j\omega C} \right)$$

$$\frac{V_0}{I_0} = R + j \left( \omega L - \frac{1}{\omega C} \right) = R + jX$$

This general form of Ohm's Law is one we use every day.  $X$  is the reactance and, if  $\omega L > 1/\omega C$ ,  $X$  is of an inductive kind: if  $\omega L < 1/\omega C$ ,  $X$  is of a capacitive kind.

Because  $I = I_0 \exp(j\omega t)$ , we can write

$$\begin{aligned} I &= V_0 \cdot \left( \frac{\cos \omega t + j \sin \omega t}{R + jX} \right) \\ &= \frac{V_0}{R^2 + X^2} (R - jX) (\cos \omega t + j \sin \omega t) \\ &= \frac{V_0}{R^2 + X^2} (R \cos \omega t + X \sin \omega t) + \text{terms in } j \end{aligned}$$

We take the real part of this, giving

$$I = \frac{V_0}{R^2 + X^2} (R \cos \omega t + X \sin \omega t)$$

If  $X/R = \tan \theta$

$$R/(R^2 + X^2)^{\frac{1}{2}} = \cos \theta$$

$$X/(R^2 + X^2)^{\frac{1}{2}} = \sin \theta$$

$$\text{and then } I = \left| \frac{V_0}{Z} \right| \cos(\omega t - \theta)$$

in which  $Z^2 = (R^2 + X^2)$

The voltage on the capacitance,  $V_C$ , is

$$V_C = \frac{1}{C} \int I dt = \left| \frac{V_0}{Z} \right| \cdot \frac{1}{\omega C} \sin(\omega t - \theta)$$

The voltage across the inductance is

$$V_L = L \frac{dI}{dt} = - \left| \frac{V_0}{Z} \right| \cdot \omega L \cdot \sin(\omega t - \theta)$$

Notice how, if  $\omega L = 1/\omega C$ ,  $V_C + V_L$  becomes zero. In a study of transient conditions we shall see that  $I_L$  and  $V_C$  are the terms we want.

The usual method of studying what happens when the oscillator signal is switched on is a straightforward affair of formal mathematics, followed by the consideration of a number of particular cases. The variety arises from the fact that we have the natural frequency of the circuit itself,  $\omega_0 = 1/(LC)^{1/2}$  (leaving out the damping correction), the damping correction, the frequency of the supply. The drive may be at,  $\omega = \omega_0$ , near, or well above or below the natural frequency. The actual switching instant may be when the generator voltage is a maximum, or zero, or somewhere in between. There may even be some current flowing in the inductor, some charge in the capacitor. So, find the general solution and put in the boundary conditions.

When I came to do this I found it was totally incomprehensible. At the end of the process one emerges with an answer, for the specific conditions, but on the way one had no contact with any sort of physical reality. In more advanced circuit work this is normal, and the more advanced the theory the more likely you are to have a large amount of "reality" wrapped up in a single symbol. With tears pouring down my cheeks I scrapped the elegant analysis and began to look for a more direct way of determining the transient behaviour of the circuit. The approach I chose is not in any of the books I looked at, although that is probably my bad luck.

The key to all transient behaviour is the way the free circuit settles down to the rest stage. When we looked at its behaviour before we found that the current was of the form

$$I = \exp(-\alpha t) \cos(\omega t)$$

This form does not contain any constants of integration. The voltage on the capacitance is best worked out from scratch. If we start with the capacitor charged, to correspond with the way we started with current flowing in the inductor, we get again

$$V = \exp(-\alpha t) \cos \omega t$$

By working through the analysis for the two cases in which we consider either fixed current starting and capacitor voltage or fixed voltage starting and inductor current we get expressions of the form

$$\exp(-\alpha t) \sin \omega t$$

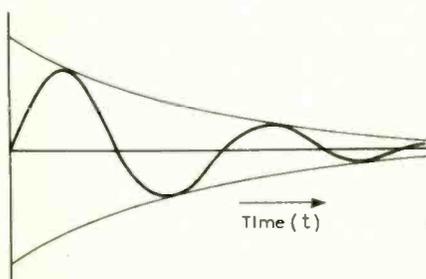


Fig. 3. The shape of  $\exp(-\alpha t) \sin \omega t$ .

In general, whatever the starting condition may be, we would expect the function to be of the form

$A \exp(-\alpha t) \cos(\omega t + \theta)$  [or  $\sin(\omega t + \theta)$ , whichever we choose, provided we adjust  $\theta$ ]. We have two constants of integration, which can be chosen to fit the initial current and voltage. Apart from the actual size of these functions, we can always write

So that any value of  $\theta$  can be realized if we take the right mix of the two curves, Fig. 1 and Fig. 3.

Let us adopt some low trickery. We set our circuit off with a current  $I_1$  and a voltage  $V_1$ .  $I_1$  is flowing into the capacitor, so that it will tend to increase  $V_1$ . Obviously  $V_1$  is opposing the flow of  $I_1$  and will tend to reduce it. We assume, since this is a fairly normal assumption among the more theoretical treatments, that  $\alpha$  is small compared with  $\omega$ . There is not much difference between successive cycles.

We began with a total energy of

$$\frac{1}{2} L I_1^2 + \frac{1}{2} C V_1^2$$

After a short time, all the energy will be in the capacitance and the current will have fallen to zero. The capacitance voltage will then be  $V_{max}$ , given by

$$\frac{1}{2} C V_{max}^2 = \frac{1}{2} C V_1^2 + \frac{1}{2} L I_1^2$$

Thus we can find  $V_{max}$ .

All this is on paper, so negative time is quite an acceptable thing. At a small value of  $t$ , with  $t$  negative, the curves show all the energy in the inductance, and  $V = 0$ . At this time

$$\frac{1}{2} L I_{max}^2 = \frac{1}{2} C V_1^2 + \frac{1}{2} L I_1^2$$

As we have decided that we will take the case of  $\alpha \ll \omega$ , then two quantities,  $V_{max}$  and  $I_{max}$ , are very close to the correct values for the envelopes  $(V, I)_{max} \exp(-\alpha t)$ .

At this point I begin drawing Fig. 4. I mark in  $V_{max}$  and  $-V_{max}$ ,  $I_{max}$  and  $-I_{max}$ , and then  $V_1$  and  $I_1$ . I also draw the exponential envelopes.

Now if  $V_1/V_{max} = \sin \omega t_0$ , the voltage wave must have crossed the zero axis at  $-t_0$ . We can measure along from here in angle units of  $\pi/2$ , or time units of  $\pi/2\omega (= 1/4f)$ . Now we sketch in the waveform. The error in this is always less than

$$\exp(-\alpha \pi/2\omega)$$

Because  $\alpha$  is small compared with  $\omega$  it is tempting to take  $\omega = \omega_0$ , that is to use the frequency fixed by  $LC$ . Guillemin seems to do this, but it would appear to me that it leaves a nasty ambiguity in one of the cases we are now going to study.

The really tricky problem is that of switching on a sine-wave generator in the circuit. We are allowed to simplify it by assuming that the circuit had not recently been disturbed, so that it contains no stored energy. As it happens, the method we are now going to use makes it relatively easy to take account of any stored energy. The applied waveform is shown in Fig. 5, where the switch has been closed at a quite arbitrary point in the cycle. "Typical cases" in the textbooks usually amount to the choice of either switching at cross-over or switching

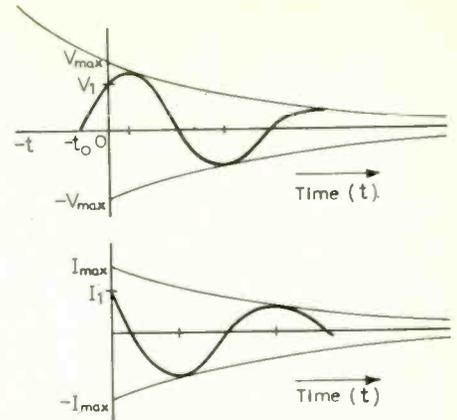


Fig. 4.

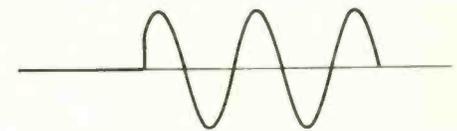


Fig. 5. Harmonic excitation applied at arbitrary phase.

at the peak. A typical case means one which is fairly easy to calculate, and I am not sure if these are, in fact, the easiest. Wait and see.

I am determined to do no more thinking than I need. I know that if I look for the steady state, the current in an  $RLC$  circuit from a voltage  $V_0 \sin \omega t$  will be given by

$$V_0 \sin \omega t = I(R + j\omega L + 1/j\omega C)$$

To make the expressions look simpler we write

$$R + j\omega L + 1/j\omega C = R + j(\omega L - 1/\omega C) = R + j\omega_0 L \left( \frac{\omega}{\omega_0} - \frac{1}{\omega \omega_0 LC} \right)$$

Now choose  $\omega_0^2 = 1/LC$ , giving

$$R + j\omega_0 L \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)$$

If we now write  $\omega_0 \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = \Omega$ , we have

$$I = V_0 \sin \omega t / (R + j\Omega L)$$

$$\text{or } I = \frac{V_0}{(R^2 + \Omega^2 L^2)^{1/2}} \sin(\omega t - \theta)$$

where  $\tan \theta = \Omega L/R$ . Although this looks like an  $LR$  circuit only, we can now have  $\Omega$  negative for positive values of  $\omega$ , whenever  $\omega < \omega_0$  in fact. So that this way of writing the result involves a range

$$\text{for } \omega = \begin{matrix} 0 \\ -\infty \end{matrix} \quad \begin{matrix} \omega_0 \\ -ve \end{matrix} \quad \begin{matrix} \infty \\ +ve \end{matrix}$$

The voltage across the capacitor is given by

$$\begin{aligned} V_C &= \frac{1}{C} \int I dt \\ &= \frac{V_0}{(R^2 + \Omega^2 L^2)^{1/2}} \cdot \frac{1}{C} \int \sin(\omega t - \theta) dt \\ &= - \frac{V_0}{(R^2 + \Omega^2 L^2)^{1/2}} \cdot \frac{1}{\omega C} \cos(\omega t - \theta) \end{aligned}$$

Now we know the two important terms in the steady state solution. Let us adopt a

simple trick. We use two voltage generators,

$$V_0 \sin \omega t \quad \text{and} \\ V_0 \sin (\omega t + \pi)$$

For one we get some current  $I_1$ , given by the equation above, and a capacitor voltage of  $V_{C1}$ . The other produces a current  $I_2 = -I_1$ , and a voltage  $V_{C2} = -V_{C1}$ . They might just as well not be there. Let us now, however, switch off the second generator. This is indicated in Fig. 6. The current produced by

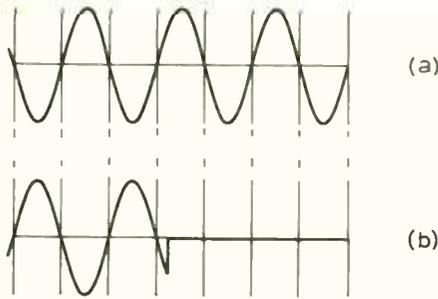


Fig. 6. Instead of switching on, as shown in Fig. 5, one signal is switched off.

the first generator continues to flow quite unperturbed. The stored energy associated with the second generator is the transient energy, and this sets up the decaying oscillation which we discussed earlier in the article. The formal justification for this method is that the equations are all linear.

If I were writing a rather grand textbook I should at this point begin to calculate a vast variety of examples. One simple way of doing this used to be to invite a selected group of students to lunch, flatter them by asking for unspecified help and then dole out the drudgery. Advances in modern technology make it possible to get one student to do it all on the department computer, and buy his own lunch into the bargain. But let us be realistic. In transient problems with a switched sine wave we normally have one of two situations. Either we don't know the switching phase, as in the ordinary switch-on situation, or the phase may vary systematically over a wide range, as in a phase-controlled rectifier circuit. We need a picture of the kind of behaviour we can expect. I am well aware that there are occasions when a detailed study of a special situation is required. Such problems can be solved by working out  $I_1$  and  $V_{C1}$ , using the equations just given, and then using these in determining the ring shown in Fig. 4. This is just added to the steady state solution. What sort of an answer do we expect.

First of all, notice that we are concerned with two frequencies, for which I shall use the letter  $f$ . We have the generator frequency,  $f_g$ , and the frequency of the transient ring,  $f_r$ . With  $f_r$  goes the damping coefficient, which is  $\alpha = R/2L$  and which modifies the undamped frequency slightly. For a lightly damped circuit we want  $\alpha \ll 2\pi f_r$ . This does not necessarily mean that  $\alpha \ll 2\pi f_g$ . A circuit with a very low  $Q$ , or very high damping, at the working frequency may ring vigorously at its natural frequency. Notice that this is likely when  $f_r \gg f_g$ .

Now we may proceed to pick out a few

special situations. Suppose that  $f_r$  is very much less than  $f_g$ . When the circuit is being driven by the two opposing generators, the quantity  $\Omega$  will be

$$2\pi f_r \left( \frac{f_g}{f_r} - \frac{f_r}{f_g} \right) = 2\pi \left( f_g - \frac{f_r^2}{f_g} \right)$$

This is very close to  $2\pi f_g$ , the value we should get if we made  $f_r = 0$ . The current is virtually that we should get in an  $RL$  circuit. It is quite easy to sketch out Fig. 7, which shows the current in the circuit. The switched-off generator leaves current flowing, and this decays exponentially. If we have a low value of  $\alpha$ , i.e.  $\alpha \ll 2\pi f_r$ , this exponential would be replaced by a long, slow, oscillation. The two generator sine waves shown represent the currents, not the voltages: we can job back to the voltage from the  $\tan \theta = \omega L/R$  equation. Obviously the most important case is when the current is a maximum. It should be noted that one very important feature of this circuit is that the current must follow a continuous curve. The inductance will always prevent a sharp step in current. Similarly the capacitance will always prevent a sharp step in voltage.

The second example is for the case when  $f_r$  and  $f_g$  are fairly close together. This is a rather tedious one to draw, because a good drawing needs about  $5f_r/(f_g - f_r)$  cycles to show the pattern. We set about it as before, though now for  $t > 0$  we have an exponentially decaying sine wave which does not necessarily have its peak at  $t = 0$ . To draw it properly we must work out the peak from the total stored energy equation and for this we need to draw the capacitance voltage curve too. Physically what happens is this. When the transient situation occurs, the stored energy appears as a damped sine wave of frequency  $f_r$ . The generator produces an undamped sine wave of frequency  $f_g$ . The two current waves beat together at  $|f_g - f_r|$  to produce the modulation effect shown more clearly in the sketch of Fig. 8(b). As the ring dies away the current settles to the steady state value. The detail at the beginning depends on the phase of the switch operation. It makes little difference to the kind of response whether  $f_g > f_r$ , or  $f_g < f_r$ . What is important is that the current may reach double its normal peak value. It is logical to guess that it is also possible for the capacitor voltage to reach double its normal peak value. Practical circuits in which this kind of transient condition can arise need tougher components than you thought.

At the desk one considers  $f_r = f_g$ . The analysis then finds that there are some small terms to throw away, and in the whole pro-

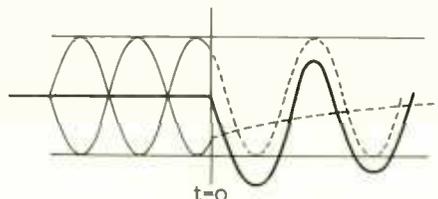


Fig. 7. Response of  $f_r \ll f_g$ . The decay curve at  $t > 0$  is the transient component, to which the steady state solution is added to give the overall behaviour.

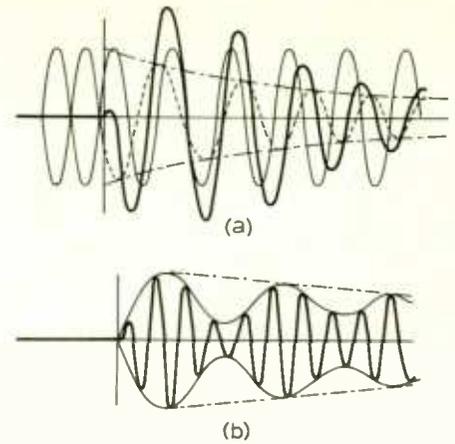


Fig. 8. Situation for  $f_r < f_g$  but  $f_g - f_r$  small.

cess I rather lose track of whether  $f_g$  is the damped or undamped frequency. Anyway, I do not believe in this sort of equality. If we go back to the nearly equal frequency problem, and then say that the beats are so slow that they have died away before the first maximum is reached, we get a normal "soft-keying" growth in a straightforward sine wave. Rather roughly, this means that we consider the case where

$$\alpha > (f_g - f_r), \text{ even though} \\ \alpha \ll f_g$$

Since  $\alpha$  will always exist, we never need to consider  $f_g = f_r$ : we just take them near enough together. In this way we avoid any awkward questions about roots of an equation coinciding.

Finally we come to the very interesting case when  $f_g \ll f_r$ : the ring frequency is high compared with the frequency of the drive. This is the kind of situation which is encountered when a mains transformer is switched on or off and the leakage inductance and stray capacitance form the ringing circuit. A feature of this situation is that if it is treated by purely analytical methods the result which emerges is totally unexpected in form. The conscientious student goes back over the analysis to find out just what went wrong. The method we adopt here gives us a direct feeling of the nature of the solution, with no surprises, or perhaps more appropriately, no unexpected shocks.

At the low drive frequency we can more or less ignore the circuit inductance. If the damping coefficient is low enough, we can even ignore the resistance. For this extreme case, the full generator voltage appears across the capacitance. If the resistance is not as low as all that, the voltage is split between capacitance and resistance and it is very easy to calculate the peak value of capacitance voltage. It is

$$V_C = V_0 / [1 + (\omega CR)^2]^{1/2}$$

Let us consider the extreme case. Let us also assume that the switching instant is when  $V_C$  is a maximum. The energy stored in the capacitance is  $\frac{1}{2}(CV_0^2)$ . For the transient waveform we have an exchange of energy between capacitance and inductance, and, as we have assumed that  $\alpha$  is very small, the

first current maximum,  $I_L$ , must satisfy the equation:

$$\frac{1}{2}I_L^2L = \frac{1}{2}CV_c^2$$

$$\text{Thus } I_L = V_c(C/L)^{\frac{1}{2}}$$

But if  $\omega_r = 2\pi f_r$ , we know that  $\omega_r^2LC = 1$

Then  $C/L = \omega_r^2C^2$  and so

$$I_L = V_c \cdot \omega_r C$$

The steady state current through the inductance is limited by the capacitance, and is  $I_{L,s} = V_0 \cdot \omega_0 C$ . Taking  $V_c = V_0$

$$I_{L,t} = \frac{f_r}{f_0} \cdot I_{L,s}$$

It will be seen that the transient current is very large indeed compared with the normal current (Fig. 9). We could have chosen a dif-

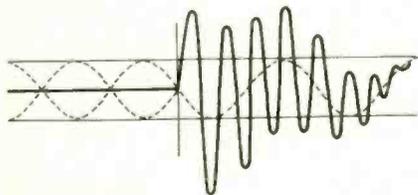


Fig. 9. For  $f_r \gg f_0$  the current ring is very much larger than the steady state current.

ferent switching phase. Had we done so we should have found a smaller value of transient current, which we can work out for any phase by the energy equations. Worst case solutions are, however, the ones which normally interest us.

Very much the same pattern of results is obtained when we study the way a parallel tuned circuit behaves with the switching of a current source. The commonest form here, numerically, is the line transformer of a television set. Here, as indeed in all the variations, we would study the voltage across the capacitance and we know, in the similar but more general form of a transistor with an inductive load, it is energy associated with volts which we must watch. Energy associated with volts, because second breakdown is not a linear phenomenon.

More complex circuits can be handled on a piece by piece basis, but the labour involved is often prohibitive. Transients are not normally central to the main problem, and the main problem takes most of our effort. A knowledge of the sort of transient behaviour to expect, together with a quick calculation of the stored energy which has easy access to the danger points, will normally be sufficient. Then, if the situation is potentially dangerous, wheel out the oscilloscope.

Nowhere in this article is there any mention of musical transients in amplifiers. This is, of course, a topic of great importance. There are two aspects which make it unsuitable for treatment here and now. Musical transients are not produced by a click-on mechanism, but have finite rise and fall times; they pass through circuits, feedback amplifiers, with a much sharper phase shift characteristic than our single tuned circuit. Anyway, this article is quite long enough.

## Conferences and Exhibitions

Further details are obtainable from the addresses in parentheses

### LONDON

Apr. 8-15 Earls Court  
**Electrex '70**  
(Electrical Engineers A.S.E.E. Exhibition, Museum St., London W.C.1)

Apr. 13-16 University College  
**Atomic and Molecular Physics**  
(I.P.P.S., 47 Belgrave Sq., London S.W.1)

Apr. 23-26 Skyway Hotel  
**Sonex '70 HiFi Exhibition**  
(Federation of British Audio, 49 Russell Sq., London W.C.1)

Apr. 28 & 29 Royal Garden Hotel  
**Microelectronics Conference**  
(Business Conferences & Exhibitions, Mercury House, Waterloo Rd., London S.E.1)

### BIRMINGHAM

Apr. 14-17 The University  
**Automatic Test Systems**  
(I.E.R.E., 8-9 Bedford Sq., London W.C.1)

### HARWELL

Apr. 2-3 A.E.R.E.  
**High Voltage Electron Microscopy**  
(I.P.P.S., 47 Belgrave Sq., London S.W.1)

### OXFORD

Apr. 6-11 The University  
**Biological Engineering Conference**  
(J. Gasking, Dept. of Pharmacology, St. Bartholomew's Hospital Medical School, Charterhouse Sq., London E.C.1.)

### READING

Apr. 6-8 The University  
**Thin Films Conference**  
(I.P.P.S., 47 Belgrave Sq., London S.W.1)

Apr. 15-17 The University  
**Defects in Semiconductors**  
(I.P.P.S., 47 Belgrave Sq., London S.W.1)

### UXBRIDGE

Apr. 14-16 Brunel University  
**Computer Graphics International Symposium**  
(R. Elliot Green, Brunel University, Uxbridge, Middx.)

### OVERSEAS

Mar. 31-Apr. 2 New York  
**Submillimetre Waves**  
(Polytechnic Inst. of Brooklyn, 333 Jay St., Brooklyn, New York 11201)

Mar. 31-Apr. 3 Paris  
**Electrical-Electronic Engineering Seminar**  
(E.E.E. Seminar, 80 rue Jouffroy 75-Paris 17e)

Apr. 3-8 Paris  
**Electronic Components Show**  
(Fed. Nat. des Ind. Electroniques, 16 rue de Presles, Paris 15e)

Apr. 5-9 Berlin  
**Cybernetics Congress**  
(Deutsche Gesellschaft für Kybernetik, 21 Stresemann Allee, 6 Frankfurt/Main 70)

Apr. 6-10 Paris  
**Advanced Microelectronics Conference**  
(Fed. Nat. des Ind. Electroniques, 16 rue de Presles, Paris 15e)

Apr. 7-9 Las Vegas  
**Reliability Physics Symposium**  
(K. H. Zaininger, RCA Labs, Princeton, N.J. 08540)

Apr. 10-20 Tokyo  
**Japan Electronics Show**  
(Japan Elec. Show Assoc., Tokyo Chamber of Commerce Bldg., 2-2 Marunouchi 3-chome, Chiyoda-ku, Tokyo)

Apr. 14-17 Washington  
**Geoscience Electronics Symposium**  
(I.E.E.E., 345 East 47th St., New York, N.Y. 10017)

Apr. 14-19 Frankfurt  
**Hi-Fi Show**  
(U.S. Trade Centre, Frankfurt/Main)

Apr. 21-24 Washington  
**International Magnetics Conference (INTERMAG)**  
(D. S. Shull, Bell Telephone Labs, 3300 Lexington Ave, Winston-Salem, N.C. 27102)

Apr. 21-24 Budapest  
**Microwave Communication Colloquium**  
(Microcoll—Technica Háza Budapest, V. Szabadsag tér 17, Hungary)

Apr. 22-24 Dallas  
**Southwestern I.E.E.E. Conference**  
(A. P. Sage, Inst. of Tech., S.M.U., Dallas, Texas 75222)

Apr. 27-29 Atlantic City  
**Frequency Control Symposium**  
(Electronic Components Lab., U.S. Army Electronics Command, Fort Monmouth, New Jersey 07703)

Apr. 27-30 Los Angeles  
**National Telemetering Conference**  
(A. V. Balakrishnan, UCLA, Rm. 3531, 405 Hilgard Ave, Los Angeles, Calif. 90024)

# Circuit Ideas

## H. F. Predictions—April

### High-gain f.e.t. tuned amplifier

The reverse transfer capacitance of a field-effect transistor can be employed as a very stable  $Q$  multiplier with inherent automatic bandwidth control. Essentials are (Fig. 1) resistive drain and source loads and selection of  $C$ , which is smaller in value than a bypass capacitor.  $C$  determines the no-signal  $Q$ : decreasing the value moves the stage towards oscillation; increasing it has the reverse effect. This circuit, with no additional components, will replace two double-tuned 470-kHz i.f. stages. With a constant current supply it is reproducible using wide-tolerance f.e.t.s. The response of Fig. 2, after optimum adjustment of  $C$ , is a shallow curve, peaking reasonably close to oscillation over the middle third of each

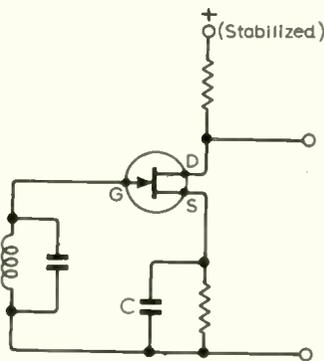


Fig. 1. F.E.T. as  $Q$  multiplier.

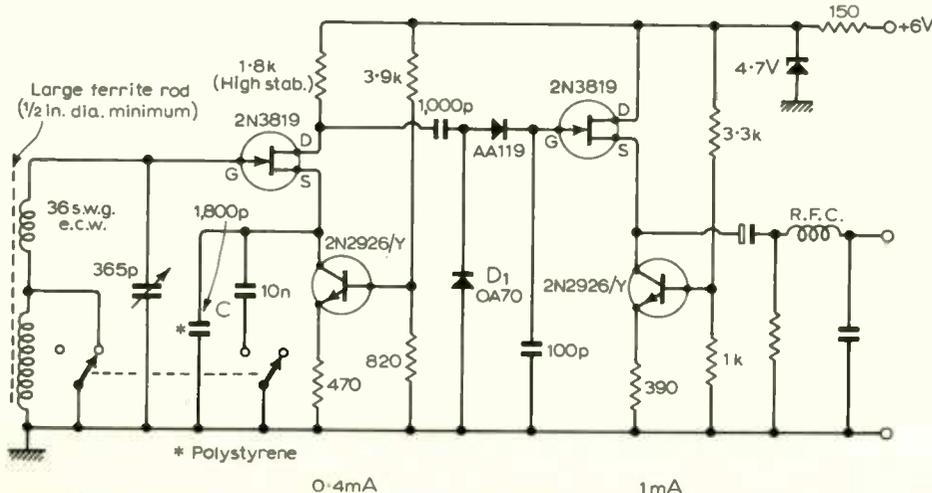



Fig. 2. M.W./L.W. tuner employing  $Q$  multiplier.

band. The detector stage assists in bandwidth control (varying the impedance of  $D_1$ ), and even on weak signals accurate tuning is indicated by wideband quality. For operation at frequencies higher than 2MHz the drain load must be progressively reduced.

K. W. MAWSON,  
Bradford,  
Yorks.
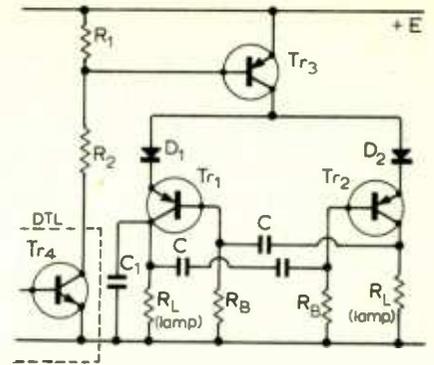
### Logic circuit gates astable multibrator

When  $Tr_4$ —the output transistor of a d.t.l. logic stage—is switched off, the current in  $R_1$  is very slight and  $Tr_3$  is effectively off:  $R_2$  is chosen so that when  $Tr_4$  saturates,  $Tr_3$  saturates thus permitting the multi to function.  $D_1$  and  $D_2$  are included to prevent base-emitter breakdown in  $Tr_1$  and  $Tr_2$  for a large voltage at the collector of  $Tr_3$ .  $C_1$  is a small capacitor (100pF) included to make the collector circuits of  $Tr_1$  and  $Tr_2$  dissimilar: this ensures that the multi will not block. Conventional design theory governs the choice of  $C$ ,  $R_L$ ,  $R_B$ . The circuit functions just as well if  $R_2$  is omitted and the base of  $Tr_3$  is driven from a high impedance source, e.g. the collector of a current-mode switch. For a 5V rail suitable values of  $R_1$  and  $R_2$  are  $R_1 = 1k\Omega$  and  $R_2 = 2.2k\Omega$ , for current in  $R_L$  up to 16mA. Typical low-cost devices which are



suitable are: diode IN4148 (G.E.); transistors (Ferranti plastic 'E' line) ZTX 500. B. L. HART,  
West Ham College of Technology,  
London E.15.

### F.E.T. push-pull oscillator

Wide frequency range  $LC$  oscillators are usually Colpitts or Hartley configurations. Higher output can be obtained using a push-pull arrangement. Many thermionic valve circuits have been evolved and n-channel field-effect devices can be substituted without significant modifications. The use of p-channel enhancement devices can however simplify the bias arrangement using no

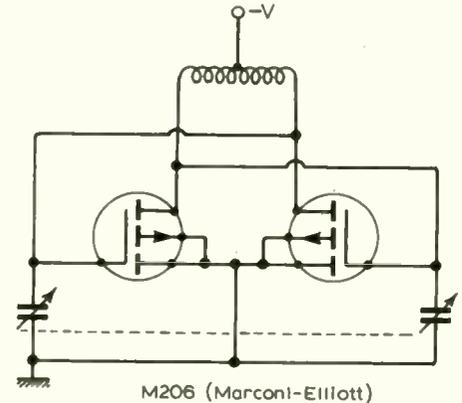


Fig. 1. Oscillator operating up to 300MHz.

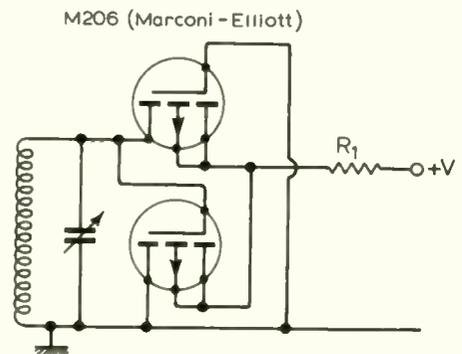



Fig. 2. Arrangement for operation between 50 kHz and 350MHz.

components other than the active devices and the tuning components is shown in Fig. 1. The tap on the coil can be omitted if a pair of chokes or resistors are used to feed f.e.t. drain connections.

The unusual re-arrangement shown in Fig. 2 allows the tuning components to be at ground potential. The circuit is no longer balanced and a resistor ( $R_1$ ) or choke is required.

J. A. ROBERTS,  
University College of Swansea.

# the Pacemaker

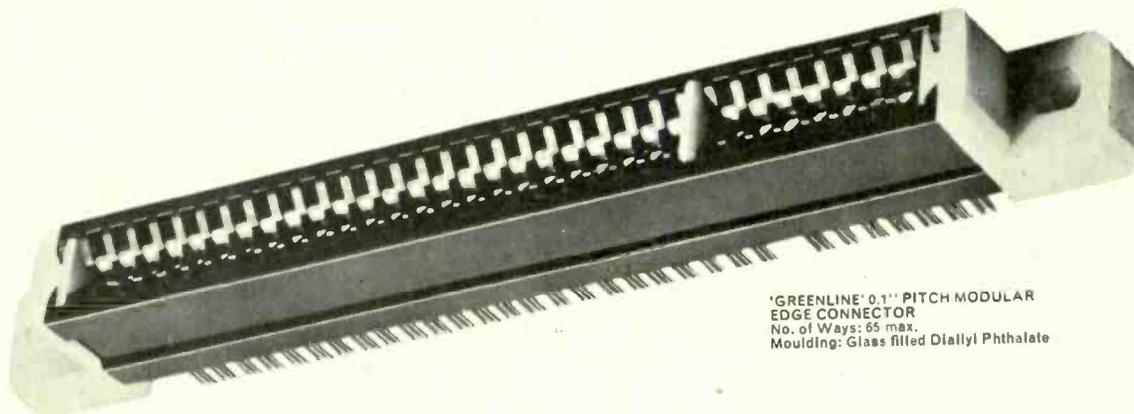


'GREENLINE' 0.1" PITCH MODULAR  
EDGE CONNECTOR  
No. of Ways: 65 max.  
Moulding: Glass filled Diallyl Phthalate
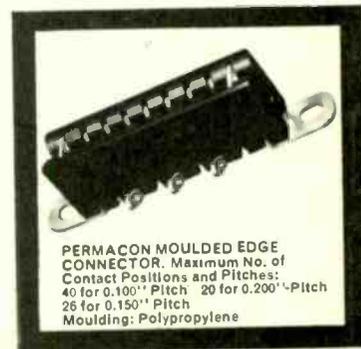
## in optimum-reliability electronic components



'GREENLINE' 0.150" PITCH MOULDED  
EDGE CONNECTOR  
No. of Ways: 4, 8, 12, 16, 24, 32 and 40.  
Moulding: Glass filled Diallyl Phthalate



PERMACON MOULDED EDGE  
CONNECTOR. Maximum No. of  
Contact Positions and Pitches:  
40 for 0.100" Pitch 20 for 0.200" Pitch  
26 for 0.150" Pitch  
Moulding: Polypropylene



REED ELECTRONIC EXCHANGE  
CONNECTOR Mk. 10 0.2" PITCH  
No. of Ways: 12+12 and 18+18  
Moulding: Glass filled Polycarbonate



SUB-MINIATURE CONNECTORS  
No. of Ways: 9, 15, 25, 37 and 50  
Light alloy shell and base

In the continually-evolving technology of the electronics industry, Carr design and research keep pace with, and often ahead of, the ever-changing demands for increasingly sophisticated components. But whilst designs may change from week to week, Carr quality and reliability remain constant, ensuring that complex high-precision specifications are met with absolute and consistent accuracy.

The connectors illustrated here are typical examples from our ranges. We have, of course, many other components of special interest to the computer and communications industries, with rapid, reliable deliveries in bulk quantities assured. Ask for data, or for a visit from one of our Technical Sales Staff. The application of his wide experience to your problems can help you towards easier, more advanced assembly techniques, with the collateral benefits of worthwhile savings on time and costs.

# CINCH


RADIO AND ELECTRONIC CONNECTORS

OPTIMUM-RELIABILITY COMPONENTS FOR HIGH-PRECISION ELECTRONIC APPLICATIONS

**CARR FASTENER** CARR FASTENER CO. LTD. STAPLEFORD NOTTINGHAM Telephone 0602-39-2661 Telex 37637

the firm with the best connections

WW-100 FOR FURTHER DETAILS

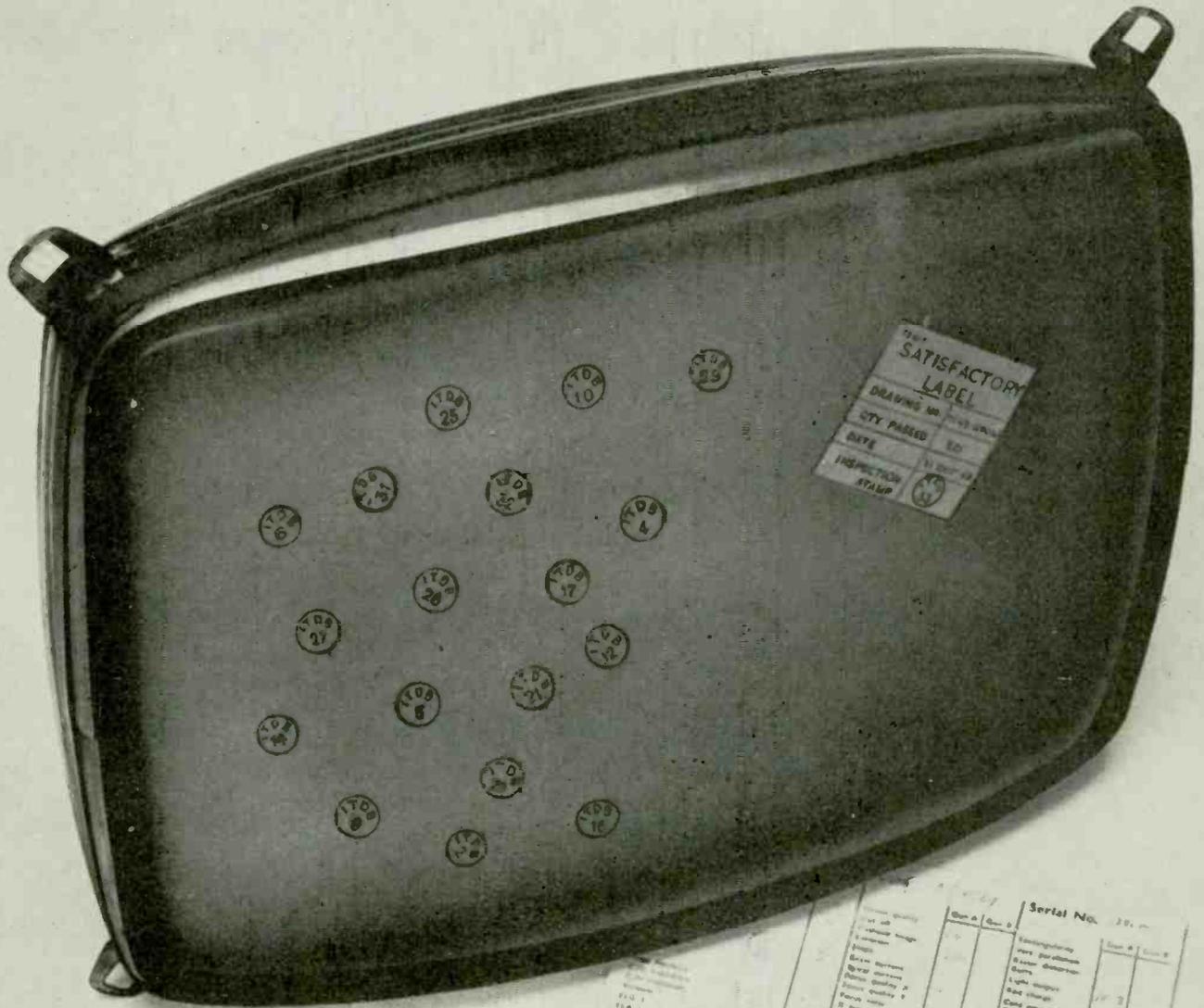

# spot check or 100% inspection?

There is nothing random about quality control with BRIMAR data display tubes. Every single tube is subjected to an exacting test at every stage of production, from the raw materials used, through the various complex stages of manufacture, to the finished product.

A typical example of BRIMAR'S advanced inspection methods is the use of Spatial Frequency measuring equipment, built to their own uncompromising standards, and used for the measurement of final spot size and focus uniformity in such tubes.

And in addition to this, an unparalleled capability in chemistry, electron optics and vacuum physics enables Brimar to offer the widest design diversity backed by a *personalised customer service*. This

service, provided by engineers with extensive experience of the electronics industry, covers advice on tube characteristics, operating conditions and associated components.

Tailored packaging, and reliable delivery to meet production schedules are also part of the BRIMAR Service.

Want to know more about BRIMAR Industrial Cathode Ray Tubes? - ask to see our latest catalogue.



**Thorn Radio Valves  
and Tubes Limited**

7 Soho Square, London, W1V 6DN.  
Telephone: 01-437 5233



WW-101 FOR FURTHER DETAILS

www.americanradiohistory.com

# Active Filters

## 9. Synthesis by factors

by F. E. J. Girling\* and E. F. Good\*

**It is shown how a filter may be synthesized as a product of factors, and a number of numerical examples are given.**

So far in this series we have dealt mainly with principles. In this article, although some important methods of realization still remain to be described, it is shown how some of the circuits already described can be put to use. The method is that of synthesizing the complete filter as a cascade of 1st- and 2nd-order sections, each with output impedance low enough for its response to be unaffected by the connection to it of the following section. Thus the response of the whole filter is the product of the responses of the individual sections. It is a practical method of design for specifications of moderate stringency, and also throws light on the nature of filters of higher order and their transfer functions.

It is not possible in this series to say very much about the design of filters as such, but an attempt is made in this Part to help the non-specialist reader—partly by calculation, and partly by the use of reference works—to make a start on the design of filters to a variety of specifications.

### 5th-order low-pass filter with Darlington response

In a conventional wave filter the important characteristic is the steady-state amplitude (or gain-versus-frequency) response. This can be specified, Fig. 1, by three parameters:  $A_p$  the maximum deviation from level response in the pass band;  $A_s$  the minimum attenuation in the stop band;  $(\Omega_s - 1)$  the relative width of the transition band,  $\Omega_s$  being the start of the stop band in the normalized characteristic ( $\omega_p = 1$ ). And if any two are specified, the work of Darlington shows how to proportion the elements of a given structure to give the best value of the third. The nature of the relationship between the three is that, if for constant  $A_s$  a smaller value of  $\Omega_s$  is required, then either a greater ripple in the pass band ( $A_p$ ) must be accepted or a structure of greater complexity must be adopted. The steady-state amplitude response of a filter of Darlington design (sometimes called an elliptic-function filter) is of equal-ripple type in pass band and stop band, as indicated in Fig. 1.

Thus we may quote from Reference 1 as a representative optimum set of values for the structure shown in Fig. 2:  $A_p = 0.1$  dB,  $A_s = 40$  dB,  $\Omega_s = 1.44$ ; and the "ladder coefficients", i.e. the element values for the normalized filter, are given in Table 1,  $\omega_p$  being used as the reference frequency, not  $\omega_B$  as in the paper referred to

TABLE 1

Normalized component values for 5th-order Darlington filter, Fig. 2.

$A_p = 0.1$ dB, $A_s = 40$ dB, $\Omega_s = 1.44$ $\omega_p = 1$ radian/second, $R_s = R_L = 1$ ohm			
$C_1$	1.016	$C_2$	0.175
$L_2$	1.197	$C_4$	0.521
$C_3$	1.596	$T_2$	0.4576
$L_4$	0.882	$T_4$	0.6780
$C_5$	0.773		

Although of symmetrical topology the filter is not symmetrical, since  $C_1 \neq C_5$ ,  $L_2 \neq L_4$ , etc. This is always the case in an efficient filter of order higher than three; one reason is that the rejector circuits ( $L_2C_2$  and  $L_4C_4$ ) are tuned to different frequencies.

The five elements in the left-hand column of the table, by themselves, form a 5th-order simple ladder filter and give the transfer function a 5th-order denominator. The addition of the capacitances  $C_2$  and  $C_4$  does

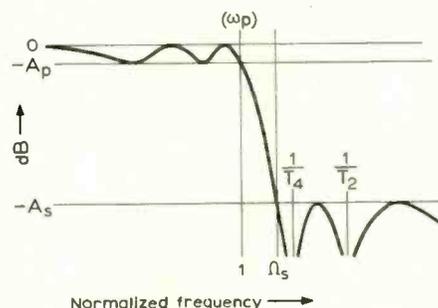


Fig. 1. Diagrammatic representation of 5th-order Darlington response.

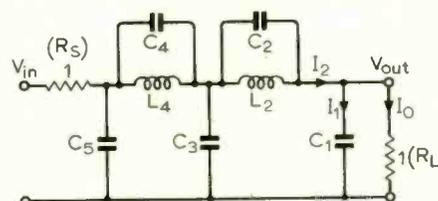


Fig. 2. Standard passive realization of 5th-order Darlington low-pass filter.

not change this order (although it does change the coefficients of the terms), but the numerator becomes 4th-order. Because  $R_L = R_s$  and the reactances are assumed to be without loss, the voltage ratio at zero frequency is one half. Consequently the transfer function may be written

$$G(p) = \frac{V_{out}}{V_{in}} = \frac{1}{2} \frac{N(p)}{D(p)} = \frac{1 + ap + bp^2 + cp^3 + dp^4}{2(1 + Ap + Bp^2 + Cp^3 + Dp^4 + Ep^5)} \quad (1)$$

The industrious may find the coefficients by analyzing the network:

$$\begin{aligned} I_0 &= V_{out}/R_L \\ I_1 &= V_{out} p C_1 \\ I_2 &= I_0 + I_1 \\ V_2 &= I_2 Z_2 = \frac{(I_0 + I_1) p L_2}{1 + p^2 L_2 C_2} \\ V_3 &= V_2 + V_0 \\ I_3 &= V_3 p C_3 \end{aligned}$$

and so on. It is only fair to give warning, however, that over forty products have to be formed in working out the denominator. The numerator, however, is easily obtained. It is

$$1 + p^2(L_2C_2 + L_4C_4) + p^4L_2C_2L_4C_4$$

and so depends only on the components of the two infinite-rejection circuits. For the chosen example the numerical values of the denominator coefficients are:  $A = 2.73$ ,  $B = 4.19$ ,  $C = 4.68$ ,  $D = 2.85$ ,  $E = 1.38$ .

For our present purpose the transfer function is required factorised. This may be regarded as the mathematical exercise of finding the roots of the equations  $N(p) = 0$  and  $D(p) = 0$ . These roots are the  $z_1, z_2$ , etc., and  $p_1, p_2$ , etc. of the identities

$$N(p) \equiv d(p-z_1)(p-z_2)(p-z_3)(p-z_4) \quad (2)$$

$$D(p) \equiv E(p-p_1)(p-p_2)(p-p_3)(p-p_4)(p-p_5) \quad (3)$$

and are referred to as the zeroes and poles of  $G(p)$ , since if  $p = \text{any of } z_1, \text{ etc. } G(p) = 0$ , while if  $p = \text{any of } p_1, \text{ etc. } G(p) = \infty$ . The numerator of the chosen example can be treated generally as it factorizes into

$$N(p) = (1 + p^2L_2C_2)(1 + p^2L_4C_4); \quad (4)$$

but  $p_1, p_2$ , etc. can be expressed only as particular numerical values:

$$\begin{aligned} p_1, p_2 &= -0.1080 \pm j1.065 \\ p_3, p_4 &= -0.413 \pm j0.784 \\ p_5 &= -0.667. \end{aligned}$$

By multiplying together the denominator factors containing the complex conjugates  $p_1$  and  $p_2$  a 2nd-order factor with real coefficients is formed,

$$(p^2 + \alpha_1 \omega_1 p + \omega_1^2);$$

and by writing  $p_1, p_2 = -a \pm jb$ , it is seen that

$$\omega_1^2 = a^2 + b^2, \quad (5)$$

$$\alpha_1 \omega_1 = 2a, \quad (6)$$

i.e.  $\alpha_1 = 2a/(a^2 + b^2)^{1/2} \quad (7)$

\* Royal Radar Establishment.

If the factor is now divided by  $\omega_1^2$ , which gives

$$\frac{p^2 + \frac{\alpha_1 p}{\omega_1} + 1}{\omega_1^2}$$

it is easily compared with the preferred form

$$1 + pT/q + p^2T^2,$$

whence  $T = 1/\omega_1 = (a^2 + b^2)^{-1/2}$  (8)

and  $q = 1/\alpha_1 = (a^2 + b^2)^{1/2}/2a$

$$= \left(1 + \frac{b^2}{a^2}\right)^{1/2} / 2. \quad (9)$$

Or, by reference to Fig. 3,

$$T = \frac{1}{OP}, \quad q = \frac{OP}{2OA}. \quad (10), (11)$$

For the example then

$$T_1 = 0.9357, \quad q_1 = 4.94$$

$$T_3 = 1.129, \quad q_3 = 1.073$$

and for the real 1st-order factor

$$T_5 = -1/p_5 = 1.499.$$

Thus the transfer function has been obtained in the form  $N(p)/D(p)$

$$= \frac{(1 + p^2T_2^2)}{(1 + pT_1/q_1 + p^2T_1^2)} \times \frac{(1 + p^2T_4^2)}{(1 + pT_3/q_3 + p^2T_3^2)(1 + pT_5)} \quad (12)$$

with parameters as given above, and  $T_2 = \sqrt{L_2C_2} = 0.4576, T_4 = \sqrt{L_4C_4} = 0.6780$ .

The 2nd-order numerator and denominator factors may now be paired arbitrarily to give sections with unsymmetrical notch response, Part 2, Fig. 19. As the highest  $Q$  factor is not very high, both sections may conveniently be realized by the Sallen-and-Key type of circuit with added parallel path, Part 6, Fig. 11(b).

Consider the transfer function

$$G(p) = \frac{1 + p^2T_4^2}{1 + (1/q)pT_1 + p^2T_1^2} \quad (13)$$

and let it be identically equal to the standard form

$$\frac{1 + ap^2T_1^2}{1 + (1/q)pT_1 + p^2T_1^2} \quad (14)$$

Then  $a_1 = T_4^2/T_1^2 = 0.523$ . Similarly for the other 2nd-order section,  $a_3 = T_2^2/T_3^2 = 0.164$ . Hence the schematic for the whole filter may be as in Fig. 4. This gives the relative component values for the case of ideal amplifiers,  $K = 1, A = \infty$ .

Equation (8) of Part 6, which becomes when  $b = \frac{1}{2}$

$$\frac{1}{q} = \frac{1}{q_i} + \frac{2q_i}{A+1}, \quad (15)$$

shows that for  $q_i = 5$  and  $A = 1000$  the

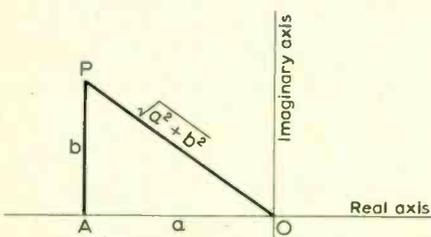


Fig. 3. P is the position of a pole,  $p = -a + jb$ .

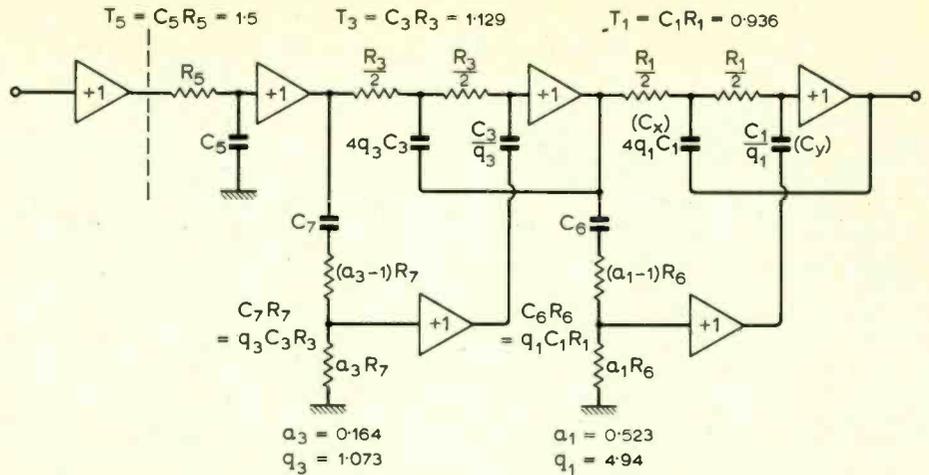


Fig. 4. Schematic for realization by factors of 5th-order Darlington response with 0.1 dB ripple in the pass band, 40 dB minimum attenuation in the stop band, and cut off at 1 radian/second.

ideal component values would give an actual  $q$  approximately 5% low, and that if compensation is made by increasing the ratio  $C_x/C_y$ , the appropriate value of  $q_i$  is 5.28. If this method is used it should be remembered that for a good zero the equality

$$C_6R_6 = C_xR_1/4 \quad (16)$$

must be maintained. Hence  $C_6$  may have to be changed. A more convenient method of compensation would perhaps be to increase  $K$  slightly by using less than 100% feedback as shown in Fig. 5 of Part 6. The calculation really shows, however, that for accurate design  $A$  should be high, say 10,000 minimum, for  $q$  of this value. Alternatively a two-integrator loop may be used (Part 7), or a parallel-T system (to be described in a following Part). For the other 2nd-order section,  $q = 1.073$ , a moderate value of  $A$  is sufficient, although for practical convenience the same type of amplifier is likely to be used.

Moving the cut-off frequency to the required value is a simple matter of scaling. So, to set the -3 dB frequency at 1000 radians/second (= 159 Hz)  $\omega_p$  must be 923 radians/second and all time constants of the normalized filter must be divided by this figure. This gives (including small adjustments based on an accurate computation of the overall response) the values shown in Table 2 below.

TABLE 2

Component values for 5th-order Darlington filter, Fig. 4, scaled for -3 dB at 159 Hz.

Stage 1	Stage 2	Stage 3
$T_5 = 1.623\text{ms}$	$q_3 = 1.073$	$q_1 = 5$
$R_5 = 16.2\text{k}\Omega$	$T_3 = 1.222\text{ms}$	$T_1 = 1.018\text{ms}$
$C_5 = 0.1\ \mu\text{F}$	$T_7 = 1.313\text{ms}$	$T_6 = 5.09\text{ms}$
	$R_3/2 = 26.3\text{k}\Omega$	$R_1/2 = 20.4\text{k}\Omega$
	$4q_3C_3 = 0.1\ \mu\text{F}$	$4q_1C_1 = 0.5\ \mu\text{F}$
	$C_3/q_3 = 21.700\text{pF}$	$C_1/q_1 = 5000\text{pF}$
	$C_7 = 0.01\text{pF}$	$C_6 = 0.05\ \mu\text{F}$
	$(a_3-1)R_7 = 110\text{k}\Omega$	$(a_1-1)R_6 = 48.6\text{k}\Omega$
	$a_3R_7 = 21.5\text{k}\Omega$	$a_1R_6 = 53.3\text{k}\Omega$

TABLE 3

Parameters for 5th-order Darlington response, normalized to cut-off frequency  $\omega_p = 1\ \text{rad/s}$ .

$$G(p) = \frac{(1 + p^2T_2^2)(1 + p^2T_4^2)}{(1 + pT_1/q_1 + p^2T_1^2)(1 + pT_3/q_3 + p^2T_3^2)(1 + pT_5)}$$

$A_s$ (dB)	$1/\Omega_s$	$A_p$ (dB)	$q_1$	$T_1$	$q_3$	$T_3$	$T_5$	$T_2$	$T_4$
20	0.9	0.077	9.73	0.955	1.469	0.975	1.029	0.662	0.881
	0.95	0.38	17.38	0.988	2.017	1.065	1.380	0.746	0.937
30	0.7	0.009	4.262	0.850	0.962	0.871	0.900	0.456	0.676
	0.75	0.025	4.96	0.895	1.042	0.951	1.044	0.499	0.726
	0.8	0.071	5.724	0.935	1.167	1.033	1.238	0.546	0.776
	0.85	0.21	8.071	0.969	1.387	1.115	1.522	0.598	0.828
	0.9	0.72	12.60	0.994	1.857	1.187	2.02	0.663	0.881
	0.95	2.8							
40	0.6	0.012	3.554	0.842	0.885	0.927	1.043	0.378	0.576
	0.65	0.033	4.096	0.889	0.959	1.018	1.225	0.416	0.625
	0.70	0.09	4.902	0.932	1.070	1.108	1.460	0.456	0.675
	0.75	0.24	6.19	0.966	1.247	1.196	1.791	0.499	0.726
	0.80	0.66	8.489	0.992	1.560	1.270	2.295	0.546	0.777
	0.85	1.8	13.31	1.010	2.193	1.318	3.175	0.598	0.827
50	0.55	0.04	3.655	0.889	0.9188	1.073	1.364	0.342	0.527
	0.6	0.12	4.382	0.934	1.033	1.178	1.661	0.378	0.576
	0.65	0.32	5.405	0.971	1.213	1.274	2.078	0.416	0.626
	0.7	0.82	7.410	0.997	1.518	1.354	2.701	0.456	0.675
	0.75	2.0	10.886	1.015	2.076	1.407	3.710	0.499	0.726
	0.8	4.24							
60	0.45	0.039	3.331	0.881	0.884	1.096	1.424	0.274	0.430
	0.5	0.13	4.052	0.934	1.006	1.221	1.790	0.308	0.479
	0.55	0.38	5.162	0.975	1.203	1.334	2.311	0.342	0.527
	0.6	1.0	7.033	1.004	1.335	1.424	3.107	0.378	0.576
	0.65	2.4	10.367	1.022	2.145	1.479	4.397	0.416	0.626
	0.7	4.9							

In the pass band distortion from the theoretical curve is most likely to be caused by misalignment of the high-*q* section with respect to the other two. The greatest slope of the response of this section in the pass band is 1/4 dB for a 1% change of frequency. For not more than 1/10th dB error in the passband, therefore, an accuracy in the component values of ±0.4% is indicated.

Points in favour of realization by factors are that requirements for amplifier gain and the effect of errors in component values are easily calculated, and hence amplifier gains and component tolerances are easily specified. A further convenience is that errors can be localized by measuring the responses of the individual section. These responses for the given example are shown in Fig. 5. The overall response was given in Part 1, Fig. 1.

An experimental filter of this design was shown by the Royal Radar Establishment on the Ministry of Aviation stand at the I.E.A. Exhibition, London, in 1964; and at the Physics Exhibition, London, in 1969 G.E.C., Ltd., (Hirst Research Centre, Wembley) showed some interesting developments of the same type of circuit.

The derivation of the factors of the transfer function from the element values of the passive filter serves to show the relationship between the several ways of specifying the filter and its responses. For accuracy, however, the *qs* and *Ts* of the factors are better computed directly from the Darlington theory as given in Ref. 1, Ref. 2, and elsewhere; and some sets of values so obtained are given in Table 3. The *k* of Ref. 1 = 1/Ω<sub>c</sub>. Tables of poles and zeroes for Darlington and some other types of filter are given in Ref. 3 and may be converted into real factors as shown above, Fig. 3 and equations (10) and (11).

**3rd-order Darlington response**

3rd-order Darlington is specified as in Fig. 1, though there is only one trough in

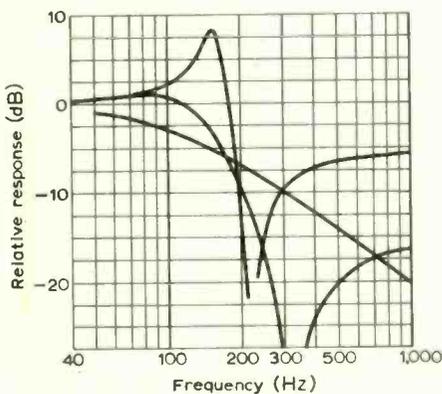


Fig. 5. Measured responses of the individual stages of a filter as Fig. 4, scaled to give -3 dB at 159 Hz.

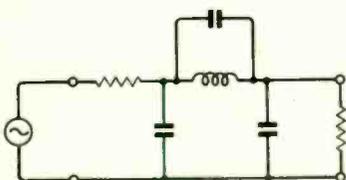


Fig. 6. Schematic for passive realization of 3rd-order Darlington response.

the pass band, and one zero in the stop band. Such a specification is met by a structure as shown in Fig. 6. There is no longer any necessity to use an unsymmetrical structure, and in practice a symmetrical structure is used. This can be bisected into two equal halves, and hence a general expression for the transfer function found in factorized form,

$$G(p) = \frac{1 + p^2 T_2^2}{2(1 + (1/q_1)pT_1 + p^2 T_1^2)(1 + pT_3)} \quad (17)$$

The response may then be analyzed by simple algebraic methods. However, some ready-computed results are given here:

TABLE 4

Parameters for 3rd-order Darlington response, normalized to cut-off frequency ω<sub>c</sub> = 1 rad/s.

$G(p) = \frac{1 + p^2 T_2^2}{(1 + pT_1/q_1 + p^2 T_1^2)(1 + pT_3)}$						
<i>A<sub>s</sub></i> (db)	1/Ω <sub>c</sub>	<i>A<sub>p</sub></i>	<i>q</i> <sub>1</sub>	<i>T</i> <sub>1</sub>	<i>T</i> <sub>3</sub>	<i>T</i> <sub>2</sub>
20	0.5	0.05	1.635	0.704	0.699	0.441
	0.6	0.15	1.929	0.826	0.928	0.533
	0.7	0.5	2.480	0.931	1.252	0.630
	0.8	1.5	3.731	1.007	1.778	0.731
30	0.4	0.1	1.515	0.766	0.919	0.351
	0.5	0.4	1.909	0.909	1.328	0.441
	0.6	1.3	2.685	1.010	1.959	0.533
	0.65	2.2	3.354	1.030	2.418	0.581
40	0.3	0.15	1.486	0.807	1.074	0.261
	0.4	0.8	2.080	0.978	1.778	0.350
	0.45	1.6	2.604	1.036	2.305	0.395
	0.5	2.9	3.373	1.074	3.012	0.441

**Butterworth response**

The occasional designer may like to have at command without resort to reference books a few design formulae suitable for meeting specifications of only moderate stringency such as might occur in the experimental laboratory in acoustical and vibrational work. In such applications the steep cut off given by a zero in the stop band may not be required, and the easily defined Butterworth (or maximally flat) response is often used:

$$|G(\omega)| = \frac{V_{out}}{V_{in}} = \frac{1}{(1 + x^{2n})^{1/2}} \quad (18)$$

where *x* = ω/ω<sub>c</sub>, ω<sub>c</sub> is the -3 dB (or corner) frequency, *n* is the order of the response. The nature of this family of responses is shown in Fig. 7. Each for its own value of *n* is the best monotonic approximation to the two asymptotes, i.e. the closest-fitting curve with a slope continuously increasing in one direction, and all pass through -3 dB at ω = ω<sub>c</sub>, i.e. at *x* = 1.

The first three we already know in factorized transfer-function form, Table 5.

TABLE 5

Amplitude and transfer functions for low-pass Butterworth filters, *n* = 1 to *n* = 3.

$ G(\omega) $	<i>G</i> ( <i>p</i> )
$\frac{1}{(1 + x^2)^{1/2}}$	$\frac{1}{1 + pT}$
$\frac{1}{(1 + x^4)^{1/2}}$	$\frac{1}{1 + \sqrt{2}pT + p^2 T^2}$
$\frac{1}{(1 + x^6)^{1/2}}$	$\frac{1}{(1 + pT)(1 + pT + p^2 T^2)}$

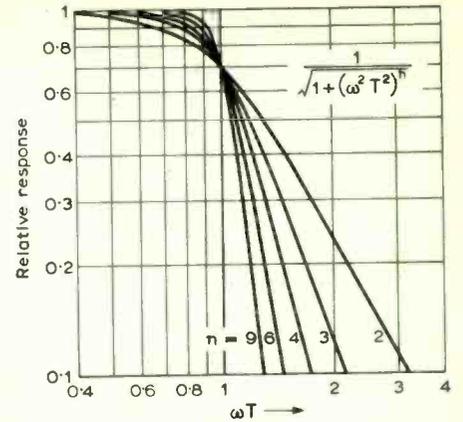


Fig. 7. Butterworth response, low-pass.

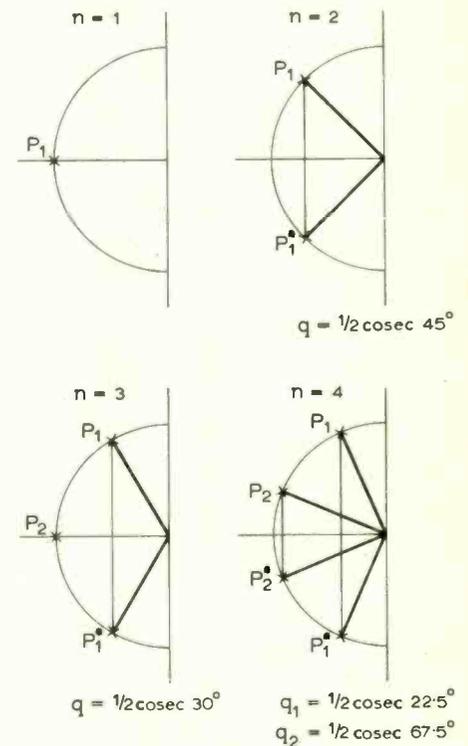


Fig. 8. Location of Butterworth poles.

To find the remainder the amplitude function |*G*(ω)| must be factorized. This involves finding the roots of the equation

$$x^{2n} + 1 = 0 \quad (19)$$

i.e.  $x^{2n} = -1, \quad (20)$

and is, therefore, an exercise in complex algebra using the concept of the *n*th roots of -1. (See, for example, Loney: Plane Trigonometry, Pt. 2, p. 141.) The complex conjugate factors so obtained are multiplied together, giving real 2nd-order factors in ω<sup>2</sup>, with one real 1st-order factor when *n* is odd, and compared with the 2nd-order amplitude factor, equation (21) of Part 2, corresponding to the standard transfer-function factor

$$\frac{1}{1 + (1/q)pT + p^2 T^2}$$

The result is that the *r*th factor has

$$\frac{1}{q} = 2 \sin \frac{(2r-1)\pi}{2n}, \quad (21)$$

and numerical results up to *n* = 10 are

given in Table 6. For all odd values of  $n$  there is also a 1st-order (simple-lag) factor; hence for odd orders the products of the  $q_s$  is 1, and for even orders  $1/\sqrt{2}$ .

TABLE 6

$n$	$q_1$	$q_2$	$q_3$	$q_4$	$q_5$
2	0.707				
3	1.000				
4	1.306	0.541			
5	1.618	0.618			
6	1.932	0.707	0.518		
7	2.247	0.802	0.565		
8	2.563	0.900	0.601	0.510	
9	2.880	1.000	0.653	0.532	
10	3.196	1.101	0.707	0.561	0.506

The results of the analysis can also be given in memorable form as the positions of the poles of  $G(p)$  in the complex plane. As all  $T_s$  are equal the poles lie on a circle, and they are evenly spaced as shown in Fig. 8. It is clear that the highest  $Q$  factor increases with increasing  $n$ , and the curves, Fig. 9, give an idea of how the opposing curvatures of the high- $Q$  and low- $Q$  factors go towards giving an approximation to a level response in the pass band and to a constant rate of fall above cutoff.

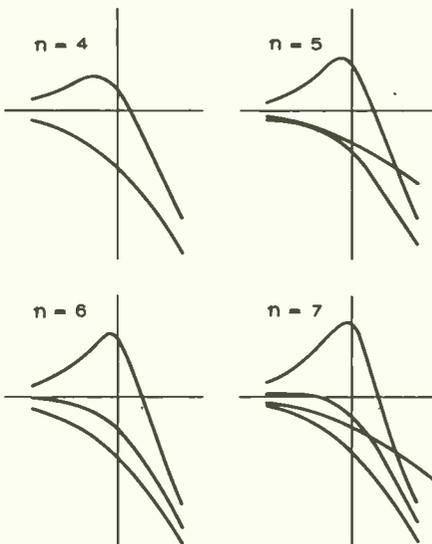


Fig. 9. Response of individual factors of Butterworth responses,  $n = 4$  to  $n = 7$ .

It can also be seen that for  $n$  even and  $\geq 4$  the lowest  $Q$  factor is little greater than  $\frac{1}{2}$ . If it is divided by a factor  $x$  so that it is made equal to  $\frac{1}{2}$ , the gain at  $\omega_c$  can be returned to  $-3$  dB by multiplying the highest  $Q$  factor by  $x$ . The overall response is hardly altered by the change, Fig. 10; and the  $Q$  factors for these approximate Butterworth filters are given in Table 7. The importance

TABLE 7

$n$	$q_1$	$q_2$	$q_3$
4	1.414	0.5	
6	2.0	0.707	0.5

of the modification is that the low- $Q$  factor is now two buffered lags, and it may be

possible to save an amplifier by incorporating them in some existing part of a system.

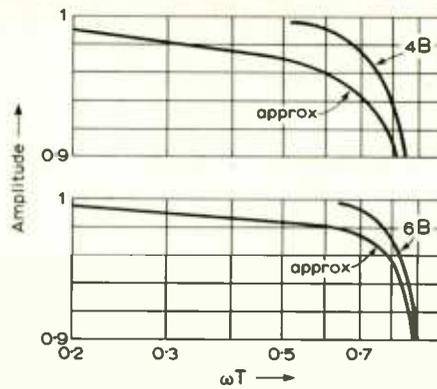


Fig. 10. Approximate Butterworth responses compared with exact responses.

### 3rd-order Chebyshev response

If some ripple is allowed in the pass band the corner can be sharper and the fall just beyond steeper. Consider the simple 3rd-order filter shown in Fig. 11. If it is equally terminated,  $R_L = R_S = R$  (say), the network can be bisected into two halves, and the voltage transfer ratio easily found as

$$\frac{V_{out}}{V_{in}} = \frac{1}{2(1+pCR)(1+pL/R+p^2LC)} \quad (22)$$

$$= \frac{1}{2(1+qpT)(1+(1/q)pT+p^2T^2)} \quad (23)$$

where  $T = 1/\omega_c = \sqrt{LC}$ , (24)

$$q = \frac{R}{\omega_c L} = \omega_c CR \quad (25)$$

$$= R \sqrt{\frac{C}{L}} \quad (26)$$

This confirms that high  $R$  gives light damping (high  $q$ ), and also shows that as  $q$  increases the corner frequency of the 1st-order factor,  $1/qT$ , moves down the frequency scale, giving increased attenuation at high frequency. This "corrects" the increased gain in the vicinity of  $\omega_c$  contributed by the 2nd-order factor, and so is consistent with the fact that when  $R_L = R_S$  no peak in the response can rise higher than the zero-frequency level ( $-6$  dB), since this is the optimum match between equal resistances. Ignoring the factor  $\frac{1}{2}$ , the normalized

( $T = 1$ ) amplitude response is given by  $|G(j\omega)|$

$$= [(1+q^2\omega^2)\{(1-\omega^2)^2+\omega^2/q^2\}]^{-1/2} \quad (27)$$

$$= [1+\omega^2\{(q-1/q)-q\omega^2\}^2]^{-1/2} \quad (28)$$

Consider

$$y = \omega\{(q-1/q)-q\omega^2\}. \quad (29)$$

If  $q < 1$ ,  $(q-1/q)$  is negative and the slope  $dy/d\omega$  is continuously negative; but if  $q > 1$ ,  $(q-1/q)$  is positive and  $y$  is zero at a finite positive value of  $\omega$  as well as at the origin, Fig. 12. Consequently when  $q > 1$ , the normalized amplitude response, which is given by  $(1+y^2)^{-1/2}$ , has a trough and then returns to unity before descending towards zero. (See Fig. 13.) As  $Q$  increases the sharpness of the corner and the rate of attenuation just beyond the corner increase: so does the amplitude of ripple in the pass-band. This is a simple example of the general

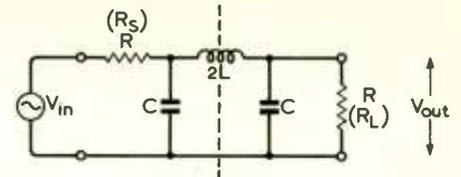


Fig. 11. Structure of simple (all-pole) passive 3rd-order low-pass filter.

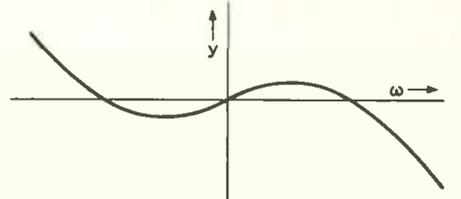


Fig. 12. Illustrating the mathematics of the production of a ripple.



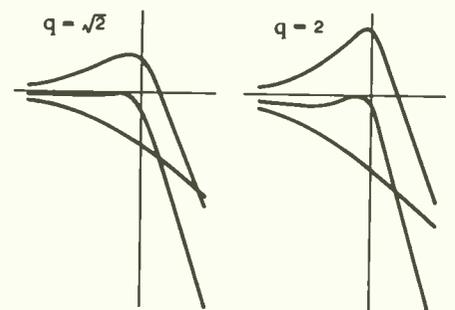


Fig. 13. Chebyshev responses, 3rd-order, and the responses of their factors.

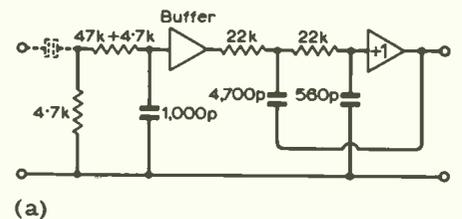

(a)

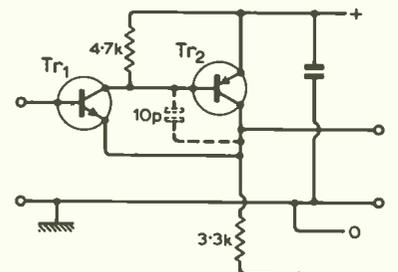

(b)

Fig. 14. (a) 3rd-order low-pass filter,  $-3$  dB at  $4.75$  kHz. (b) Suggested amplifier.  $Tr_1$ : 2N3707, 2N3904, BC109C etc.  $Tr_2$ : 2N4058, 2N3906 etc.

nature of Chebyshev or equal-ripple response. The peak occurs where

$$\omega^2 = 1 - \frac{1}{q^2}, \quad (30)$$

So as  $q \rightarrow \infty$  the peak approaches  $\omega_c$ , while for  $q = 1$  it is at  $\omega = 0$  (i.e. the ripple disappears). As shown in Part 1 this is maximally-flat-amplitude (Butterworth) response, and here the corner frequency of the 1st-order factor is equal to that of the 2nd-order factor. For  $q < 1$  the corner frequency of the 1st-order factor is at a higher frequency than that of the 2nd-order factor, and this adds to the greater roundness of the corner compared with the Butterworth.

The trough occurs at

$$\omega^2 = \frac{1}{3} \left( 1 - \frac{1}{q^2} \right), \quad (31)$$

and the depth of the trough may be derived from the relationship

$$y_t^2 = \frac{4q^2}{27} \left( 1 - \frac{1}{q^2} \right)^3 \quad (32)$$

For 1 dB depth, maximum,  $q$  must be  $\approx 2$  approx., Fig. 13.

As a compromise between low ripple and a sharper corner  $q$  may be chosen in the region 1.4 (0.15 dB ripple) to 1.5 (0.25 dB ripple); and Fig. 14(a) shows a schematic for an audio-frequency low-pass filter with  $q = 1.43$  approx. The  $\omega_c$  of the 2nd-order factor is  $10^6/36$  radians/second (= 4.4 kHz), and the -3 dB point for the whole filter is at 4.75 kHz approximately.

The amplifiers may be of a variety of types, and will probably be chosen for convenience and ready availability. The circuit shown in Fig. 14(b) is suitable, and although of only moderate internal gain (c. 500), gives enough loop gain to reduce distortion at (say) 1 V r.m.s. output to a very low level. An input buffer amplifier should be used if the output impedance of the previous stage is not negligible or cannot be incorporated into the first resistance of the filter. Provided  $Tr_1$  maintains a high current gain at low  $I_c$  all impedances, and the two resistances in the amplifier, may be increased several times, giving economy in h.t. current and in the size of capacitors.

For higher-order Chebyshev filters the parameters must form a proper set, and the ripples will not be equal. Table 8 gives the  $Q$  factors and the relative magnitudes of the  $T$ s for five 5th-order curves with depth of ripple from 0.02 dB to 0.8 dB. All these may be considered a better approximation to constant gain in the pass band, and the table shows that all but the first give more attenuation than 5th-order Butterworth, both at twice the cut-off frequency and at higher frequencies (Fig. 15).

**Filters for pulse transmission**

The high  $Q$  factor of at least one factor of a

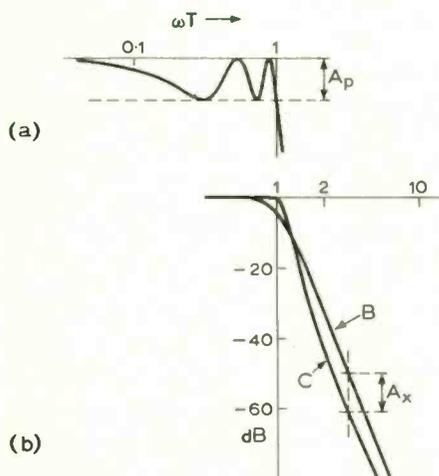


Fig. 15. Illustrating 5th-order Chebyshev response: (a) pass-band ripple, (b) increased attenuation compared with Butterworth 5th-order response, B.

$$\tau_g = \frac{d\phi}{d\omega} \quad (34)$$

TABLE 8

Parameters for 5th-order Chebyshev response					$\frac{1}{(1 + \rho T_0)(1 + \rho T_1/q_1 + \rho^2 T_1^2)(1 + \rho T_2/q_2 + \rho^2 T_2^2)}$		
$\frac{T_0}{T}$	$\frac{T_1}{T}$	$q_1$	$\frac{T_2}{T}$	$q_2$	$A_p$	$A_s$ $\omega T = 2$	$A_s$ $\omega T = \infty$
1.337	1.051	0.786	0.827	2.618	0.02	-3	0
1.642	1.181	0.859	0.885	3.000	0.06	2	5
2.164	1.337	1.000	0.946	3.702	0.2	7	10
2.377	1.383	1.062	0.962	4.000	0.3	9	12
3.236	1.506	1.328	1.000	5.236	0.8	14	17

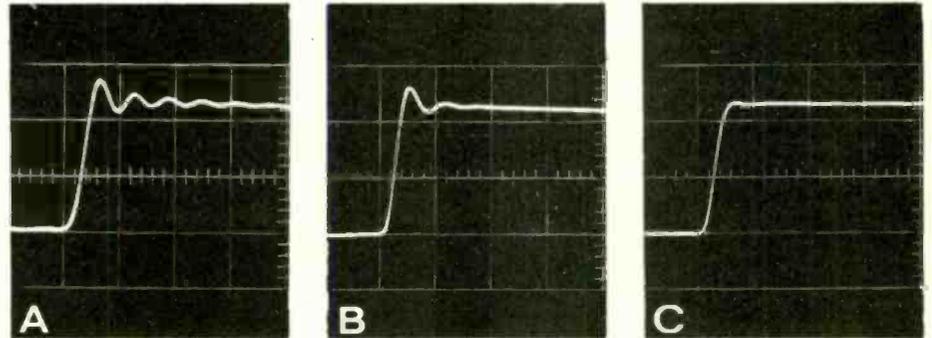


Fig. 16. Step responses of three filters: (a) a 5th-order Darlington, (b) a 5th-order Butterworth, (c) an approximate linear-phase filter.

filter with a sharp corner and rapid fall at the end of the pass band gives an oscillatory transient response. Thus for the Darlington filter described in the previous section the response to a step function, Fig. 16(a), shows an overshoot of about 15% and several subsequent oscillations of appreciable amplitude. To avoid such ringing it is not necessary for all factors to have  $q \leq \frac{1}{2}$  ( $q = \frac{1}{2}$  is critical damping), but it is necessary that all factors with corner frequencies falling within the passband should have low values of  $q$ . Thus the simple 5th-order filter with transfer function

$$G(p) = \frac{1}{(1 + \rho T)^3 (1 + \rho T + \rho^2 T^2)} \quad (33)$$

has a step response, Fig. 16(c), quite suitable for pulse work; though the frequency response, Fig. 17(a), falls away considerably in the pass band and has a very rounded corner.

It is generally agreed that for good pulse response the phase lag should increase linearly with frequency through as much of the pass band as possible. If a high  $Q$  factor is present the slope of the phase curve is less near zero frequency but increases as the resonant frequency of the factor is approached. If the corner of the amplitude response curve is unnecessarily rounded, meaning that only very low  $Q$  factors are present, the slope of the phase curve is greater near zero frequency, but slowly decreases. The transient response then is not ringing, but the rise time is unnecessarily long. Note: a linear frequency scale is assumed.

The slope of the phase curve is associated with the idea of a group delay used in the wave theory of optics,

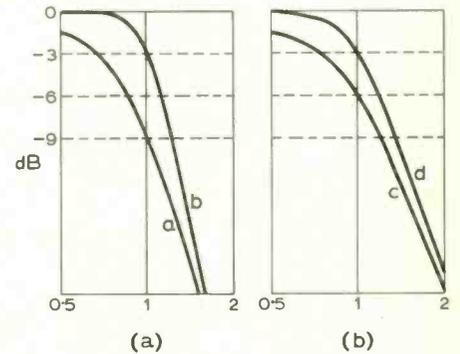


Fig. 17. Amplitude responses of Butterworth and approximately linear-phase filters.

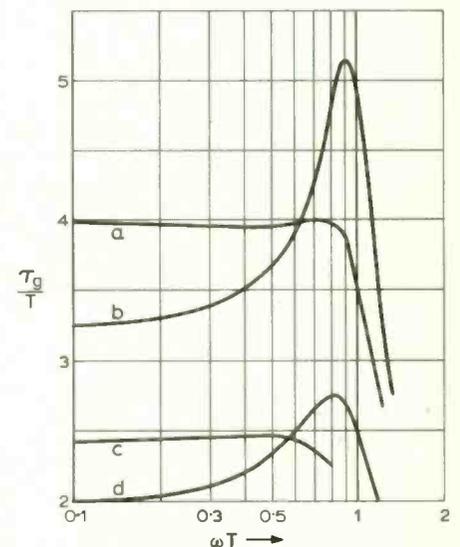


Fig. 18. Normalized group delay of Butterworth and approximately linear-phase filters.



# Dynamic Range versus Ambient Noise

## A practical solution involving metal-cone loudspeakers and high-power amplifiers

by George Izzard O'Veering

The essential requirements for a high quality sound reproduction system are adequate power and adequate bandwidth. Since loudspeakers are inefficient, and the attainment of wide bandwidth systems is generally incompatible with high efficiency, the achievement of the desired acoustic spectrum from the subsonic to the ultrasonic makes heavy demands on amplifier output.

Moreover, it will be apparent on reflection that many of the musical and other instruments, the acoustic output of which it is desired to reproduce, are themselves both powerful and developed to a high degree of acoustic efficiency. It is clearly laughable to suppose that the majestic splendour of a full orchestral fortissimo or the lung power of a Wagnerian tenor in full cry can be represented adequately on an acoustic budget of a few hundred milliwatts. Inconvenient though it may be, there can be no doubt that to recreate the true dynamic range of much recorded sound over the required sonic spectrum makes demands on the output power of the audio amplifier/reproducer system which are well beyond the capabilities of most, if not all, of the equipment at present on the market.

### Calculation of required power

The quietest sound which can be heard in a given environment depends entirely upon the background noise level of that environment. Unfortunately, most people live in close proximity to traffic, neighbours with television sets, dogs, and noisy children, and these things, together with the normal background sounds of the home, combine to give an ambient noise level of about 50dB. The minimum sound level which can be distinguished clearly above this background level is therefore 53dB. The dynamic range of orchestral music can be as much as 70dB, therefore in order to be able to hear the pianissimo as well as the fortissimo passages, a peak level of 123dB is required.

The acoustic power in watts required to produce a sound intensity level of 53dB is about  $6\mu\text{W}$  for an average-size living room. Since a 10-dB increase in power output requires a tenfold increase in power, the 123-dB peak-power level will therefore require a maximum acoustic output of some

50W. If the loudspeaker efficiency is 5% (and this is significantly better than is obtained from most commercially available loudspeaker systems) a peak-power output of 1000W per stereo channel is obviously required if the total dynamic range of a symphony orchestra is to be heard in comfort.

It was clear from discussions both with manufacturers and distributors that no serious attempt had been made to meet the requirement for drive units capable of handling as little as 250W. Initial trials made with some of the more likely units, were generally unsatisfactory. In particular there was a tendency for the cone and speech coil to become detached, and for fraying of the surround. In addition, the failure was often made more serious by partial combustion of the inflammable materials within or in proximity to the speech-coil assembly.

When more substantial reproducer units had been evolved, this only brought to light the flimsy nature of the housings which had been supplied, and considerable annoyance was caused by a minor injury sustained when one of the cabinets burst during an orchestral transient and the room was filled with flying splinters. At this stage it was accepted that the cabinets used would require to be of comparable strength to the reproducers, and the assistance of the specialist who constructed the metal cone loudspeaker assemblies was sought to manufacture four sheet-steel column-loaded units, of a suitable type to take the 23in  $\times$  14in elliptical wide-band speakers. These are

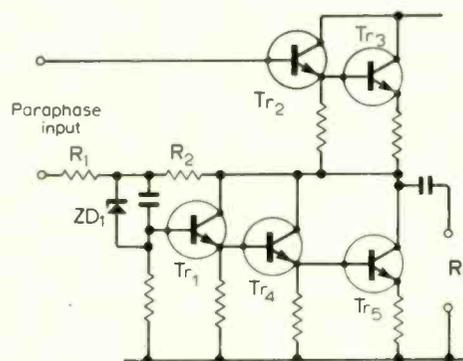


Fig. 1. Symmetrical output stage using only n-p-n transistors.

situated at the four corners of the listening room and the opposite units are connected in parallel but in antiphase. This has the effect of increasing the apparent dimensions of the listening room, in addition to reducing the  $P/R$  losses in the speaker wires.

Each unit is rated at 500W, with a nominal  $20\Omega$  impedance. The required output from the amplifier is therefore 10A at 100V r.m.s. (282 volts pk-pk) per channel.

### Power amplifier design

The use of a solid-state, transformerless amplifier to provide an output of 1kW into a  $10\Omega$  load imposes certain limitations on the designer. In particular, the normal complementary or quasi-complementary output stage configurations are no longer practicable since the only useful and relatively cheap high-voltage transistors which are available are all of the n-p-n construction.

The basic output stage configuration employed, to provide a fully symmetrical push-pull class B output stage using only n-p-n transistors, is shown in Fig. 1. As shown, this would be satisfactory for power outputs up to about 50W.

In this circuit arrangement,  $Tr_2/Tr_3$  and  $Tr_4/Tr_5$  are Darlington pairs with  $Tr_2$  and  $Tr_4$  being normal small-power driver transistors.  $Tr_1$ , in combination with  $R_1$  and  $R_2$ , provides the necessary signal level and amplitude transformation for the lower half of the output stage, and  $ZD_1$  effectively stabilizes the voltage level at the power output point. This is chosen so that the largest symmetrical voltage swing is obtainable. The symmetry of this stage is maintained up to a frequency determined by the resistance of  $R_1$  and  $R_2$  and the input shunt capacitance of  $Tr_1$ . This will normally be well above the audible spectrum.

The final circuit employed is shown in Fig. 2. Although for simplicity only four parallel-connected output transistors are shown in each half of the output stage, this is only adequate for intermittent use at 1kW output. In practice six parallel connected transistors are required in each half of the output stage.

The paraphase input is obtained from two medium-power high-voltage transistors,  $Tr_3$  and  $Tr_4$ , the h.t. supply for which is obtained from a separately smoothed 400-V line, because bootstrapping is not practicable with this type of driver stage.

The input is derived from a long-tailed pair of p-n-p transistors, of a type chosen for high voltage linearity, and freedom from avalanche or collector leakage (Early effect) distortion. Although 150V is applied to the end of the 'tail', the maximum collector-emitter voltage is limited to about 52V, because the base of  $Tr_2$  is returned to the 50V tap on the zener diode chain. A variable resistor is included in the 'tail' to set the current through  $Tr_1$  and  $Tr_2$ . This controls the current through  $Tr_3$  and  $Tr_4$ , and, since the output d.c. level is determined by  $ZD_1$ , thereby controls the

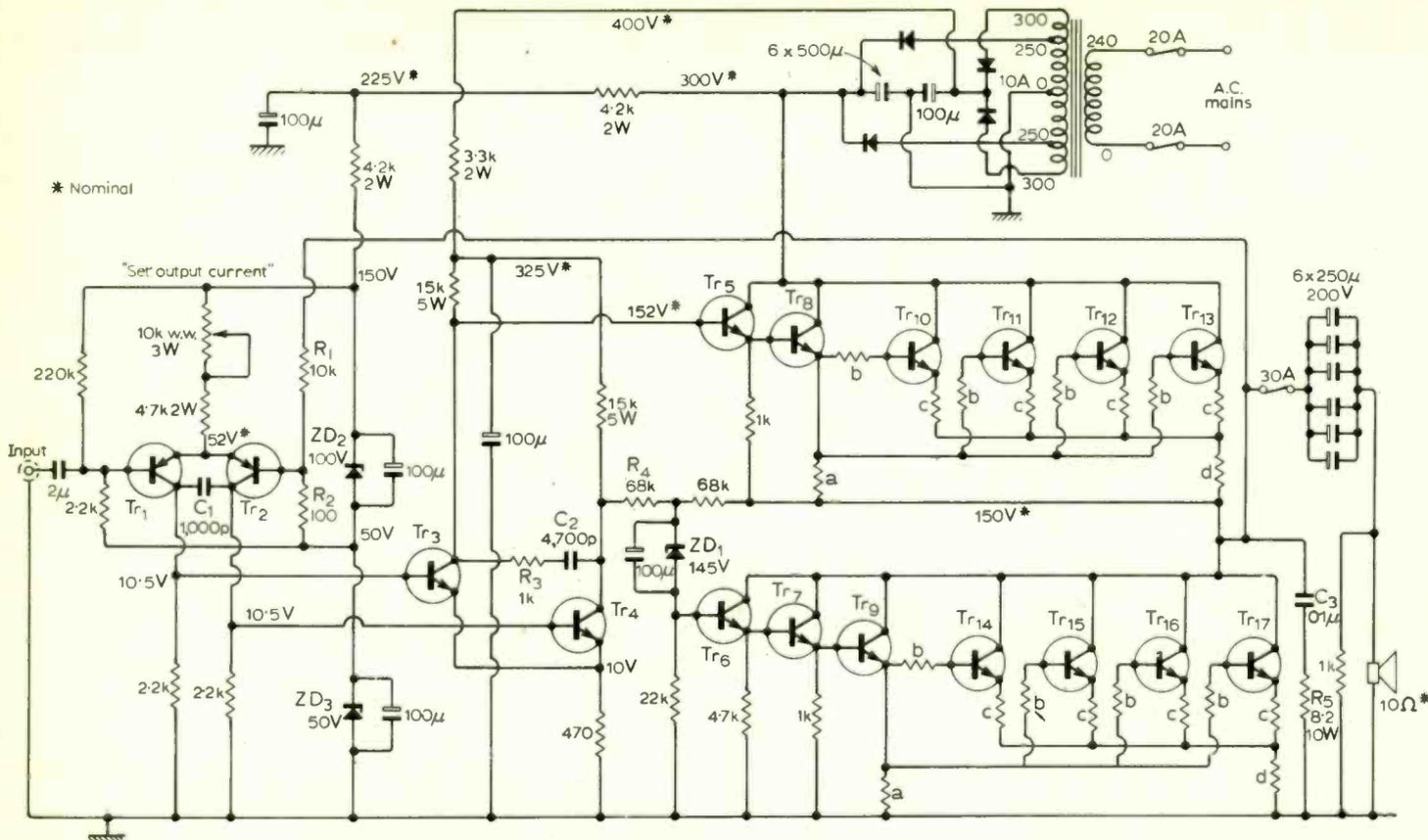


Fig. 2. Expanded version of Fig. 1 employing a Darlington triple as the output device.  $Tr_1, Tr_2$ —R.C.A. 38496;  $Tr_3$  to  $Tr_7$ —MJE340;  $Tr_8$  to  $Tr_{17}$ —MJ413. Lettered resistor values: a = 22Ω, 2W; b = 10Ω, 2W; c = 0.5Ω, 5W; and d = 0.1Ω, 5W.

quiescent current of the output stage. This should be set to about 200mA. Because of the absence of coupling or bootstrapping capacitors the gain of the circuit from the base of  $Tr_1$  to the output of the power transistors is constant from the h.f. roll-off point down to d.c. The l.f. roll-off point is therefore determined solely by the 2-μF input capacitor and the output time constant.

The input impedance is 2kΩ in series with 2μF. The h.f. roll-off point and the phase stability margin is determined by  $C_1$ , (the input-lag capacitor)  $C_2$  and  $R_3$ , and  $C_3$  and  $R_5$ . The loop gain is determined by resistors  $R_1$  and  $R_2$  and is approximately 100. The full output is given by an input of 1V r.m.s., which can be obtained from any suitable high-quality pre-amplifier capable of operating into a 2-kΩ load.

**Constructional details**

The construction of the power amplifier unit follows conventional lines, and no unusual precautions are required apart from the need for generous heat sinks. Very satisfactory results were given in the prototype by the use of a pair of old cast-iron radiators, such as can be found second-hand for a few pounds in a builder's yard, to which the transistors can be individually attached by small bridges made from a suitably substantial gauge of copper sheet. The bottom and sides of an old copper preserving pan would be ideal. Care should, of course, be taken in drilling the attachment holes to make sure that the radiator shell is still capable of retaining water without leakage.

If such radiators cannot be found, a

copper hot-water storage cylinder would serve admirably, but it would probably be more difficult to introduce such an item inconspicuously into the listening room. The siting of the output transistors should combine shortness of signal leads with the required thermal separation of the power transistors one from another. It should also be borne in mind that the circulating currents at full power are of the order of 30A. The leads to the loudspeaker terminal bosses—for which old car battery connectors are suggested—to the collector and emitter rails of the output transistors, and to the h.t. and earthy ends of the h.t. decoupling capacitor block must be substantial. A 3/8in × 1/4in bore copper pipe is preferable, but as an alternative, lengths of 12 s.w.g. copper wire may be plaited together.

After assembly, it is recommended that the amplifier units be bench-tested on a dummy load before attachment to the speaker units, since quite trifling faults can lead to a surprising amount of energy being released. For example, in preliminary listening trials with the prototype, an intermittent o/c in the earth braiding on an input to the pre-amp, led to the necessity for the listening room ceiling to be substantially restored and replastered.


**Listening arrangements**

Although the results obtained with good quality gramophone recordings have been most astonishing, and have brought home to the author in the most vivid way the qualities of stamina and emotional detachment required of an instrumental player situated, as the fortunate listener, in the midst of a large orchestra, it is clear that

there are a large number of residual problems in the life-like reproduction of disc recordings, of which the major one is the avoidance of acoustic feedback. As with many other of these problems, it is suspected that the manufacturers of the equipment have not really got down to serious thought on this matter, and the solution which the author feels most people must adopt, that of housing the record player unit in some detached building, such as a small garden shed, is inconvenient and prevents the listener from hearing the beginning of the recorded piece. Moreover, if in one's hurry to return to the audition room, the pickup cartridge is let fall too rapidly upon the record, extensive damage can be caused to windows and other glazing.

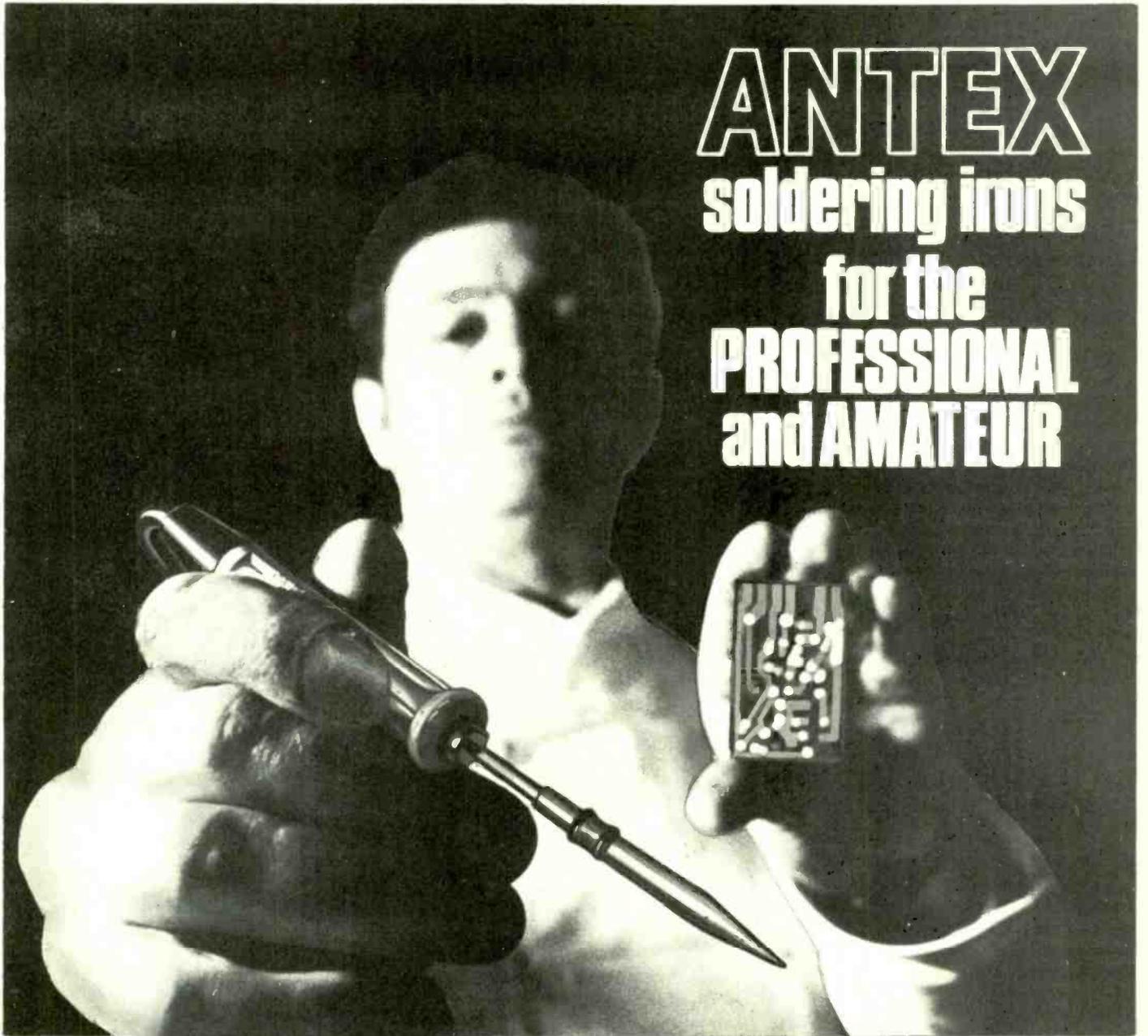**Summing up**

The performance of the equipment as installed is entirely satisfactory, and a wide variety of sound sources have been explored during the assessment of the scope of this system, and many sounds have been recaptured with a degree of realism not previously encountered. However, the development of this apparatus has not been without difficulty, scepticism and expense, and it has been suspected at times that unnecessary difficulties have been placed in the author's way. For these reasons, it is thought unlikely to appeal to those for whom high-fidelity reproduction is merely a passing interest. On the other hand, it has proved possible to purchase several of the adjoining properties at a very advantageous price, and this has undoubtedly offset a large part of the constructional costs.



# ANTEX

## soldering irons

### for the

# PROFESSIONAL

## and AMATEUR



G 18 watts. Fitted 3/32" bit for miniature work on production lines. Interchangeable spare bits, 1/8", 3/16" and 1/4" available. For 240, 220 or 110 volts. 32/6.



E 20 watts. Fitted with 1/4" bit. Interchangeable spare bits 3/32", 1/8", 3/16" available. For 240, 220, 110 volts. From 35/-




ES 25 watts. Fitted with 1/8" bit. Interchangeable bits 3/32", 3/16" and 1/4" available. Ideal for high speed production lines. For 240, 220, 110, 24 or 12 volts. From 35/-



F 40 watts. Fitted 5/16" bit. Interchangeable bits 1/4", 3/16", 1/8", 3/32" available. Very high temperature iron. For 240, 220, 110, 24 or 20 volts. From 42/6 Spare bits and elements for all models and voltages immediately available from stock.

### Complete precision soldering kit

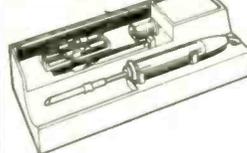

PLUS 36-page booklet on "How-to-Solder"—a mine of information for amateur and professional.

This kit—in a rigid plastic "tool-box" — contains

- Model CN 15 watts miniature iron, fitted 3/32" bit. Interchangeable spare bits 1/8", 3/16"
- Reel of resin-cored solder
- Felt cleaning pad
- Stand for soldering iron

From Electrical and Radio Shops or send cash to Antex. **49/6**



Model CN 240/2  
15 watts - 240 volts  
Fitted with nickel plated bit (3/32") and in handy transparent pack. From Electrical and Radio Shops or send cash to Antex. **31/**



### PRECISION MINIATURE SOLDERING IRONS

Antex, Mayflower House, Plymouth, Devon.  
Telephone: Plymouth 67377/8.  
Telex: 45296. Giro No. 2581000.

- Please send me the Antex colour catalogue
- Please send me the following irons
- | Quantity | Model | Bit Size | Volts | Price |
|----------|-------|----------|-------|-------|
| .....    | ..... | .....    | ..... | ..... |
| .....    | ..... | .....    | ..... | ..... |

I enclose cheque/P.O./cash value


NAME .....

ADDRESS .....

..... WW4

# Know the latest from C.I.

No. 2

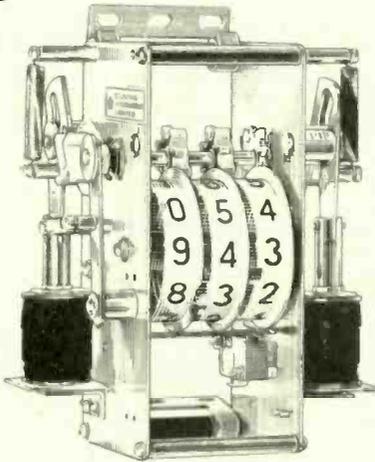

## Count up, count down counter SERIES 943

Now in quantity production, this new C.I. counter has been produced with the needs of the Gaming and Amusement Machine manufacturers in mind. Nevertheless, it will have many other outlets where a robust unit of uncomplicated design is needed.

The three drum wheel bank can be indexed by solenoid actuators in either direction. The wheel bank registers from 000 to 999 where a stop prevents an additional pulse zeroing the wheels. Similarly the counter cannot subtract from 000 to 999. When readout is 001, a subtract pulse will find 000 and a change-over micro-switch will operate. Approximately 6½" high, 4½" wide, 3½" deep. 230 volts. AC 50 cycle supply. Other operating voltages available.

### ELAPSED TIME METER SERIES 36

Records time in hours and tenths of hours an electric circuit or machine has been in use; provides data on servicing and plant maintenance.



**COUNTING INSTRUMENTS LIMITED**  
Elstree Way, Boreham Wood, Herts. Tel: 01-953 4151

A MEMBER OF THE G.H.P. GROUP LIMITED

Please send details of Series 943 Counter  
Series 36 Elapsed Time Meter

Name \_\_\_\_\_ Position \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

ww

WW-103 FOR FURTHER DETAILS

# Buying a scope



## First ask DYNAMCO

Save yourself time by talking about your applications (PCM, TV, pulse, HF, etc) to our specialist engineers. If we can't meet your requirements from our own extensive range, then we'll tell you who can. Call Chertsey 2636 — and ask for Barrie Newman.

# The scope specialists

Dynamco  
Hanworth Lane  
Chertsey Surrey England

World Wide Sales & Service



DYNAMCO

WW-104 FOR FURTHER DETAILS

# World of Amateur Radio

## Amateurs urged to tackle TV interference

As a result of renewed efforts by many British amateurs to overcome the problem of causing interference to local television receivers, the number of stations to be heard operating during television programme hours has risen appreciably during the past year. However, there are signs that the Ministry of Posts & Telecommunications is concerned at the number of requests being made to the Post Office by both amateurs and viewers for assistance in overcoming television interference (TVI). While the Ministry is responsible for all technical matters relating to the orderly use of the r.f. spectrum, interference investigation field work is now carried out by Post Office engineers under contract to the Ministry. Interference investigation costs the Ministry about £2 per hour.

Amateurs are being urged to acquaint themselves with the basic causes of TVI and to tackle interference problems without calling in the Post Office teams. Amateurs are also being encouraged to persuade manufacturers of commercially built amateur transmitters to pay more attention to design features likely to reduce the problem, including the choice of oscillator frequencies. It is being suggested that only when cases of TVI prove intractable or where the viewers concerned adopt an unco-operative attitude should the Post Office investigation officers be called in.

## Australis Oscar 5 satellite

The Australian-built Oscar 5 satellite carrying 28- and 144-MHz beacon transmitters (see the March issue), launched on January 23rd, continued to function as planned until February 14th when, during the 273rd orbit, a commanding "on" of the h.f. beacon brought the battery voltage below that needed to operate the v.h.f. beacon. At the time of writing, the h.f. beacon continues in operation but is expected to have ceased by the time these notes appear.

Bill Browning, G2AOX, the European co-ordinator, has already received over 100 reports on the Oscar 5 telemetry signals, including many from Germany,

Sweden and the U.K. The reports cover reception of the 144-MHz beacon since telemetry signals were not satisfactory on 28MHz, due to a modulator malfunction, although the carrier and "HI" identification signals were radiated. The simple stabilizing system also proved rather less satisfactory than had been expected resulting in deep fading of signals when the satellite was overhead. Many novel techniques were used by amateurs to read out the telemetry, including matching of incoming tones with a local generator by means of stereo headphones (giving accurate results at low signal/noise ratios). Almost all the reports showed close agreement in results.

Another highly satisfactory feature was the effective amateur communications links which brought masses of orbital predictions and other information to the London co-ordinator. These included radio-teleprinter links with Australia and the United States operated by Reg Wigg, G6JF in Devon and fed to London on 3.5MHz a.m. Direct London to U.S. links on s.s.b. were also used.

Many amateurs are hoping that the next Oscar will include (as in 1965) an active transposer, possibly 144MHz down and 432MHz up, to allow long-distance contacts to be made via the satellite. It is not known yet when the next amateur satellite is likely to be launched.

## New group for the north east

A new North East England amateur radio group has been formed from within local clubs and societies to organize major amateur radio events, mainly evening "technical conventions". It is hoped that some five or six large meetings can be arranged each year to attract speakers from all over the country. Members of the group cover the whole of County Durham, Tyneside and Teesside as well as parts of Northumberland and the North Riding of Yorkshire. Members will be free from the commitments normally associated with regional and local radio clubs.

The first event takes place in Durham City on Friday, March 20th when F. J. U. Ritson, G5RI, of the University of Newcastle-upon-Tyne, is to give a lecture demonstration on aerials.

The secretary, J. Melvin, G3LIV, 5 Lancashire Drive, Belmont, Durham, will provide further details and a sample Newsletter to those interested. Peter Martin, G3PDM, is the interim chairman of what promises to be something new in the dissemination of technical information among amateurs.

## Amateur microwave record?

An excellent contact was established during February between A. Wakeman, G3EEZ, operating portable on Clee Hill in the Midlands, and L. W. G. Sharrock, G3BNL, on Cleeve Common in the Cotswolds, on the 10-GHz (3-cm) band.

This is believed to be a new British record for amateur two-way operation on this band. A pulsed klystron transmitter was used at G3EEZ/P while frequency modulation was used at G3BNL/P.

A large number of v.h.f. and u.h.f. enthusiasts are expected to attend the 16th annual R.S.G.B. v.h.f./u.h.f. convention at the Winning Post hotel at Whitton on Saturday, April 25th. Technical lectures and an exhibition of equipment during the afternoon will be followed by a dinner. Tickets can be obtained from Frank Green, G3GMY, 48 Borough Way, Potters Bar, Hertfordshire.

**In Brief:** A change of address for the general secretary of the British Amateur Television Club: Ian Lever, G8CPI, 65 Dynes Road, Kemsing, Sevenoaks, Kent, replaces the former Swanley address. . . . The first totally blind Irish amateur, Cathal O'Reilly, has recently been licensed as EI9CA. . . . Amateur licences in force at the end of October 1969 included 13,413 class A, 1,897 class B and 179 amateur television—class B licences are increasing much faster than class A. . . .

The 28.185 MHz beacon station, GB3SX at Crowborough operates on a 24-hour basis with an output power of 20 watts to a three-element Yagi aerial usually, but not always, pointing East, or alternatively with an omni-directional aerial. . . . A German beacon station, DL0IGI operates on 28.20 MHz with a power of 200 watts to a vertical dipole. . . . The next U.K. Radio Amateurs Examination is being held on Monday, May 11th at 18.30 at many local venues. . . . A low-power 3.5-MHz contest is being held on April 5th. . . . W. E. Gardner, G3FYR, recently reported longish delay echoes during a contact with W2ELW on 28 MHz and received a letter from Professor O. G. Villard, Jr., W6QYT, acknowledging the usefulness of all such reports even though the present investigation (see December, 1969) is basically concerned with echoes of over one or two seconds and particularly those of five to ten seconds. These appear to be heard usually on only one station, and for time intervals of only a few minutes. . . . A printing error appeared in last month's note "50 years of call signs"—line eight should refer to G4-three-letter call signs.

PAT HAWKER, G3VA

# Personalities

Several senior appointments in the Engineering Training Department have been announced by the B.B.C. **H. V. Sims**, M.I.E.E., F.I.E.R.E., previously head of training section (engineering) has been appointed to the new post of head of technical projects and services. He will be concerned with investigating new methods of presenting maintenance information and with the maintenance and installation of all the broadcasting training equipment at the Training Centre. **J. H. Brooks**, B.Sc.(Eng.), M.I.E.E., previously a senior lecturer, has become head of training section (engineering). He is responsible for the training of engineering and technical assistants in the Operating and Maintenance Departments of the Corporation. **D. G. Enoch**, M.I.E.R.E., previously a senior lecturer, has been appointed head of training section (technical operations) in succession to **G. W. MacKenzie** who was recently appointed head of engineering, Northern Ireland. Mr. Enoch is responsible for the technical training of the B.B.C.'s technical operators. **A. W. Harris**, B.Sc., A.C.G.I., M.I.E.E., is appointed assistant, overseas trainees, and is concerned with training courses and attachments for non-B.B.C. staff.

Among the 1970 recipients of awards by the Institute of Physics & Physical Society are: **Professor A. B. Pippard**, of Cambridge University, who receives the Guthrie Medal "for his contributions to low-temperature and solid-state physics"; **Dr. E. Eastwood**, director of research of the English Electric Company, who receives the Glazebrook Medal "for his work on radar and the application of physics in the electrical and electronics industry"; and **Dr. A. Hewish**, of Cambridge University, who receives the Charles Vernon Boys Prize "for his work in radio astronomy and particularly his discovery of the pulsar".

**A. H. Ellson**, M.B.E., B.Sc.(Eng.), M.I.E.E., has been appointed manager of the optical character reading group of the M.E.L.

Equipment Company and **Th. P. Reede** will lead the company's technical marketing group, responsible for market research, business and product planning. Mr. Ellson was, until his new appointment, technical manager of the Microwave Division of M.E.L. and Mr. Reede joins M.E.L. from Philips Electrológica at Rijswijk in the Netherlands.

**Norman Doyle**, formerly marketing manager of Cossor Electronics' Communications Division, has been promoted divisional manager with overall responsibility for all aspects of the sales and marketing of Cossor's "Commando" range of radiotelephones and other u.h.f. and v.h.f. communications equipment. He is succeeded as marketing manager by **John Bonner** who recently joined the company. Mr. Bonner was previously sales promotion manager of Ultra Electronics for seven years.

Rank Precision Industries has announced the appointment of **James Warden** as chief engineer of the telecommunications product group of its Broadcast Division. Mr. Warden was formerly technical manager of the industrial products group of Cossor Electronics Ltd. He will be responsible for controlling the group's research and development programmes and will be based at Welwyn Garden City until June, when he will move to the new Rank Precision Industries factory at Ware.

**Robert R. Heikes**, B.Sc., Ph.D., director of engineering at Motorola's Semiconductor Products Division headquarters in Phoenix, Arizona, has been appointed as the company's managing director in Europe. Dr. Heikes will now be responsible for all Motorola activities in Europe. He will be based at the company's European Service Centre in Geneva and his responsibilities will cover the European sales offices and distributors and the manufacturing facilities in Toulouse, France, and

East Kilbride, Scotland. Dr. Heikes received his degree in 1948 from the Massachusetts Institute of Technology and his doctorate in 1951 from the University of Chicago. Before joining Motorola he was associated with Westinghouse for 18 years.

**Derek Ashby** has joined Venner Electronics as their sales manager. Prior to joining Venner, Mr. Ashby, who is 34, was with Marconi Instruments for five years. He joined M.I. as a technical representative and was appointed manager of factored products in 1967. After National Service with the R.A.F. he joined Furzehill Laboratories as a development engineer.

Ferranti Ltd announces the appointment of **John Begbie** as general service manager with responsibility for all service policy in the Scottish Group and for co-ordinating activities with other departments in the Company. In addition, Mr. Begbie, who is 47, is appointed acting manager of the Ferranti factory at Dalkeith, Midlothian. Mr. Begbie studied at Edinburgh University, and after war-time radar experience joined Ferranti in Edinburgh in 1950 as a trials engineer. Following a spell in Australia as chief project engineer with a Vickers guided weapon team, he returned to Ferranti in 1957 to start the service department in Edinburgh. He is succeeded as service manager by **Eric Henney** who is 40. Mr. Henney was educated at the Royal College of Science and Technology, Glasgow, and after experience with I.B.M. and Barr & Stroud joined Ferranti in 1954.

Marconi-Elliott Computer Systems Ltd, Borehamwood, Herts, announces the appointment of **Iorwerth Evans**, B.Sc., as marketing director. He joins the company from Marconi Radar Systems Ltd in which he was general manager (Borehamwood) and a director. Born in 1932 Mr. Evans took a degree in mathematics at Imperial College, London. He joined the Guided Weapons Division of English Electric in 1953 where he stayed until 1959. After two years with Decca Radar Systems he joined Elliott Automation as chief systems analyst (defence systems), ultimately becoming general manager of Elliott Space and Weapons Automation Ltd. The 1968 merger between G.E.C. and English Electric resulted in the formation of Marconi-Elliott Computer Systems Ltd.

**D. G. Smee**, who joined Marconi in 1933, has been appointed an assistant managing director of both G.E.C.-Marconi Electronics and of the Marconi Company. He has held various senior manage-

ment positions for the past 20 years (including manager of the Broadcasting Division) and has been Marconi's deputy managing director since 1968.

MCP Electronics Ltd (a subsidiary of Mining and Chemical Products Ltd) which acts both as a manufacturer and as a distributor for such companies as TRW Semiconductors Inc., will now operate with two principal divisions: intermetallics division, offering mainly semiconductor metals, under the management of **B. J. Wray**, a director of the company, and semiconductor division, with **David Cunningham** (newly appointed to the board) as general manager. Before joining MCP Electronics as sales manager, Mr. Cunningham was sales manager at SGS-Fairchild. Marketing in the semiconductor division has been divided into four groups, each with a product manager. **Terry Roeves** has been appointed product manager of the r.f. power devices group; **J. C. A. Chaimowicz**, of the optoelectronics group; and **W. E. B. Baldwin**, of the thick film integrated circuit group. A product manager for the industrial devices group has yet to be appointed.

## OBITUARY

**Lord Jackson of Burnley**, F.R.S., D.Sc., F.I.E.E., professor of electrical engineering at Imperial College, London, from 1946-53 and 1961-67 died on February 17th aged 65. Willis Jackson graduated from the University of Manchester in 1925 and started on his academic career as a lecturer in electrical engineering at Bradford Technical College. In 1938 he became professor of electrotechnics at his old university, a post he held until his appointment to the chair at Imperial College. For the eight years between his incumbencies he was director of research and education with Associated Electrical Industries in Manchester. He was knighted in 1958 and created a life peer in 1967 for his services to education, science & technology. Lord Jackson served on many Government and scientific committees including the Television Advisory Committee of which he was appointed chairman in 1963.

**Kenneth E. Harris**, B.Sc., F.I.E.E., F.I.E.R.E., who died on January 27th aged 52, was in Sir Robert Watson-Watt's radar research team throughout the war and then for 14 years (1949-63) with Cossor latterly as technical director. His particular interest was secondary radar. In 1963 he joined Redifon as manager of the communications division and was appointed to the board in 1964. A year ago Mr. Harris left Redifon and has been associated with several other companies.

# New Products

## Two-hour Tape Cassette

The range of Scotch magnetic tape cassettes has been expanded to include a two-hour version. The new Philips-compatible cassette—the Scotch C-120—has an improved shim material which is reliable and eliminates tape binding and jamming. The shim material effectively reduces frictional drag and increases recorder battery life. The cassette uses Scotch Dynarange low-noise tape, giving good high-frequency response at slow ( $1\frac{1}{4}$  i.p.s.) recording speed. The cassette is supplied in a durable hinged plastic case. Price 33s 6d. 3M Company, 3M House, Wigmore Street, London W.1.

WW 306 for further details

## Coherent Filter

An active filter claimed to be capable of recovering signals which are more than 100dB below noise level has been introduced by Brookdeal Electronics (who tend to specialize in signal recovery instruments). Called the Type 467, it is a narrow-band coherent filter using a multi-path filter technique\*, and is designed particularly for use in the signal channel of "lock-in amplifiers" (perhaps better



known to some readers as synchronous detectors). Its centre frequency is established by an external reference waveform, giving it the ability to follow a varying wanted signal, and normally it will use the same reference waveform as the synchronous detector. The bandwidth of the filter is 3Hz and the frequency range of operation is 10Hz to 100kHz. The output of the device is a square wave at the reference frequency with an amplitude 40dB greater than the in-phase component of that frequency at the input (max.


\*See, for example, *W. W.* March 1966, p.130.

output 3V pk-pk. from 600Ω). Input impedance of the filter to the signal is 100kΩ, 50pF, while the input impedance to the reference waveform is 10kΩ, 80pF. The design is such that the instrument requires no setting up or adjustment by the user. Brookdeal Electronics Ltd., 1 Market Street, Bracknell, Berks.

WW 301 for further details
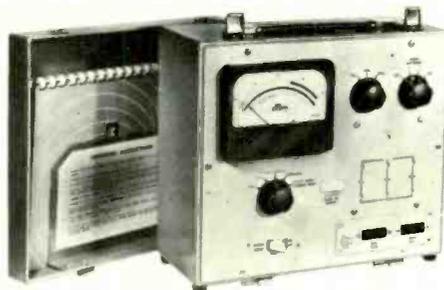
## Milliwatt Test Set

Hatfield Instruments, Type 747 universal milliwatt test set is a precision thermocouple meter for checking the standard 0dBm send level in 75Ω unbalanced, 140Ω balanced, and 600Ω balanced circuits. The 75Ω input covers frequencies up to 20MHz, whilst the 140 and 600Ω balanced inputs cover frequencies up to



1MHz. The instrument is protected against overloads of up to +25dBm on all inputs and the measurement range of -1 to +1dBm is displayed over the full 4-in scale of the meter. The accuracy of the standard version is ±0.05dB on all inputs. However, it is now available as option 1 with special calibration charts guaranteeing an accuracy of 0.02dB on all three inputs. Hatfield Instruments Ltd, Burrington Way, Plymouth PL5 3LZ, Devon.

WW 307 for further details

## Memory Voltmeter with Chart Recorder

A dual-readout memory voltmeter with a built-in strip chart recorder, for use where a permanent record of transient or spike occurrences is desired, is available from Sintrom Electronics. This portable instrument, the 5201CR, has applications in

monitoring power stations, power supplies, computer equipment and other similar installations. It employs amplitude memory to measure and hold 50 nanosecond or longer one-shot voltage peaks of single, transient, random or repetitive pulses permanently or until reset. A dual-shielded cabinet precludes common mode errors. The cabinet is isolated to 1000V. An optional gate circuit permits use as a sample-and-hold voltmeter. The recorder is a dry process, pressure-sensitive 63ft chart with a front access window. It will deliver 25 hours of continuous recording from a 30in/hr standard chart speed. A five position high response selector control is provided permitting the instrument bandwidth to be reduced in specific applications where the waveform to be measured is of




low frequency and where unwanted high-frequency noise is present. Voltage ranges are 0.3, 30, 100, 1000V to 30kV with optional probes. Input impedance is 10MΩ to 30kΩ depending on the range and accuracy ±3% of full scale. Sintrom Electronics Ltd, 2 Castle Hill Terrace, Maidenhead, Berks.

WW 316 for further details
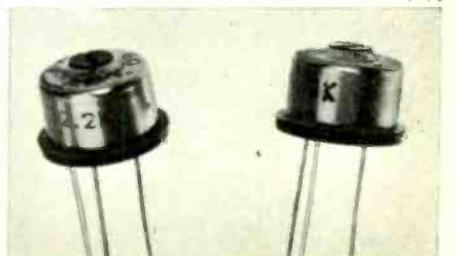
## Miniature Wire-wound Potentiometer

A miniature wire-wound trimmer potentiometer, the ADT05, available from Guest International Ltd, is housed in a TO-5 type nickel-alloy case and may be mounted on a printed circuit board in exactly the same manner as a transistor. The terminal centres are spaced so as to enable flush fitting to a standard 2.54mm (0.1in) hole-pitch printed-circuit board. Rotation extends over 320° and mechanical overload protection is provided in the form of a slipping-clutch mechanism. Moulded-in terminations and a silicon rubber sealing ring help the device to withstand extremes of environmental conditions. The terminations are 0.28 to 0.36mm square copper/nickel alloy. The resistance range available covers from 15Ω to 15kΩ in preferred values. The power rating is 0.5W at 40°C and the temperature range is -55° to +150°C. The temperature



coefficient is not greater than 50 parts/10<sup>6</sup> per °C for the 15Ω to 47Ω values, 20 parts/10<sup>6</sup> per °C for the 100Ω to 200Ω values, and 120 parts/10<sup>6</sup> per °C for the 470Ω to 15kΩ values. Guest International Ltd, Nicholas House, Brigstock Road, Thornton Heath, Surrey.

WW 302 for further details

## Laboratory Power Supplies

Guest Electronics have modified their recently announced type 606 laboratory bench power supplies. These all-transistor units feature continuously variable ranges of 0-7.5, 15, 30 and 60V. Voltage output is controlled by a precision 10-turn helical potentiometer fitted with a vernier scale allowing the voltage to be set to a pre-determined value with guaranteed repeat-



ability. A built-in meter enables the output voltage or current to be monitored. Ripple noise is less than 0.5mV pk-pk and overload protection limits the output current to 110% of maximum. Reset is automatic. The model 606 is available in current ranges from 0-500mA up to 0-2.5A. Dimensions are 156 × 152 × 102mm and prices from £34 15s to £42 15s. Guest International Ltd, Nicholas House, Brigstock Road, Thornton Heath, Surrey.

WW318 for further details.

## Linear Power Controllers

A range of solid-state linear power controllers has been introduced by Eurotherm to provide efficient control of a.c. loads from 10 to 300A. Units supplying d.c. and three-phase loads are also available. Power is controlled by an inverse pair of thyristors in series with the load. R.F. suppression and protection against supply-voltage transients can be incorporated. An additional feature is a 'soft start' characteristic—the firing angle is gradually increased over the first few



cycles after switching on, thus preventing the sudden application of full power which may be harmful to certain loads. In addition, facilities exist for an override control via external contacts. The control module is calibrated 0-100% power, with a linear scale owing to the "square law" feedback employed, and is fully compensated against supply voltage variations from +10% to -15% at 240V a.c. Units can also be supplied for operation from 415V a.c. Eurotherm Ltd, Broadwater Trading Estate, Worthing, Sussex.

WW 305 for further details

## D.V.M. Multi-range Adaptor

Electrotech Instruments (of Coutant Electronics) have developed an adaptor unit that will convert any 1V full-scale digital voltmeter (input resistance  $\geq 10M\Omega$ ) to a multi-range digital meter for the measurement of a.c. and d.c. voltages, currents, and resistance. Known as the MMA 100 the adaptor is available either as a free-standing unit or built in to Electrotech's modular system cabinet which includes their new CDM 100 digital panel meter. The MMA 100 is built with push-button range selection and, when used in conjunction with a 1V full-scale digital meter, provides five voltage ranges and five current ranges for a.c. and d.c., and five resistance ranges. These are 0.1, 1, 10, 100 and 660V a.c.; 0.16, 1.6, 16, 160 and 1000V d.c.; 100μA, 1mA, 10mA, 100mA and 1A a.c.; 160μA, 1.6mA, 16mA, 160mA and 1A d.c.; and 160Ω,




1.6kΩ, 16kΩ, 160kΩ, and 1MΩ. According to the measurement function and range selected, the full-scale accuracy is between 0.1% and 0.5% and the sampling rate is between 2 and 3 per sec. Overvoltage protection is provided on a.c. and d.c. ranges—1000V on the three highest d.c. ranges and 250V on the two lowest; and 700V for the three highest a.c. ranges and 180V for the two lowest. On a.c. it will operate at frequencies from 40Hz to 10kHz. In the free-standing form the multimeter adaptor unit measures 147 × 60 × 180mm. The price is £70. Electrotech Instruments, Coutant Electronics Ltd, Instrument Division, 5 Loverock Road, Reading, Berks.

WW323 for further details.
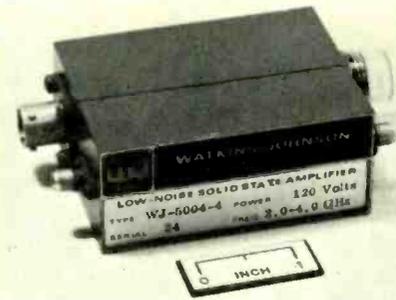
## S-band Low-noise Transistor Amplifier

Watkins-Johnson Co. has placed on the market a low-noise microwave transistor amplifier for operation in the S-band (2 to 4GHz). Designated the WJ-5004-4, this amplifier, with integral power supply has



a guaranteed noise figure of 8.5dB maximum and power output of +7dBm (for 1dB gain compression). Overall design is consistent with the respective environmental requirements of MIL-E-16400F. Watkins-Johnson International, Shirley Avenue, Windsor, Berks.

WW 308 for further details


## Oscilloscope for TV Servicing

Fully automatic television line and field triggering is featured in a new Philips oscilloscope, model PM3200X, specially designed for TV service and maintenance work. This ensures a completely stable display of all line- and field-signal waveforms. Other features are a 10MHz bandwidth, 2mV input sensitivity and the elimination of d.c. balance-correction by automatic drift compensation circuits in the vertical deflection pre-amplifier. The timebase circuit is triggered automatically but in the absence of a trigger it starts "free running". Sweep speeds cover the range 0.1μs/div to 0.5s/div. A separate triggering facility is provided for line/field triggering giving a stable display of both line and field information. The unit measures 175 × 210 × 330mm and weighs 5.3kg. Pye Unicam Ltd, York Street, Cambridge.

WW321 for further details.
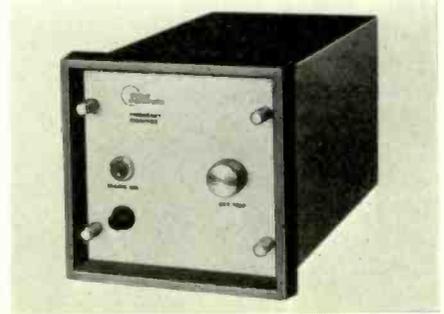
## Frequency monitor

Designed to provide an alarm or control signal when the input frequency deviates from a pre-determined figure, a new range of frequency monitors has been added to the Orbit 70 series of industrial control instruments. The principle of operation is based on the digital measurement of the period of the incoming signal giving a rapid single cycle response when the input frequency goes out of limits. Three versions, zero speed, underspeed and overspeed are available and combinations of under-



speed and overspeed modules can be housed in a single instrument to provide bandpass or high- and low-limit facilities. Thirteen overlapping ranges cover the frequency spectrum 1Hz to 30kHz. Alarm operation is within 0.1% of the set point and reset is automatically carried out without hunting. Output can be in the form of a relay changeover or of a logic level change. Construction is of i.c.s mounted on plug-in p.c. modules. Orbit Controls Ltd, Alstone Lane Industrial Estate, Cheltenham, Glos.

**WW 310 for further details**

## Field Intensity Receiver

A field intensity measuring receiver, designation number VSME1510, from Microwave International, covers the frequency band 30–300MHz in six ranges. The voltage measuring range covers 0–120dB (1 $\mu$ V to 1V). The unit employs transistors throughout and has an accuracy on its frequency calibration of 0.5% without a warm-up period. The frequency response is  $\pm 2.5$ dB on all ranges. The scale arrangement consists of a 340mm long cylindrical linear scale with continuously progressive frequency calibration. Total scale length is approximately 2 metres. The measuring accuracy when used on an accurate calibration source is better than  $\pm 1$ dB. By narrowing the bandwidth it is possible to measure sinusoidal voltages down to 0.1 $\mu$ V. The standard input impedance is 60 $\Omega$ , and a 50- $\Omega$  unit is available on request. The bandwidth is 120–130kHz with 6dB drop. Microwave International (U.K.) Ltd, 33-37 Cowleaze Road, Kingston Upon Thames, Surrey.

**WW 303 for further details**

## H.F. Receiver

Astro Communications have announced a new h.f. communications receiver, model S.R.502. This is a compact all-transistor modular unit suitable for table top or standard 19-in rack mounting. Only 3½ in high, the main frame contains fully protected power supplies, audio, demodulator and i.f. circuits. Two cavities are provided which will accept a variety of plug-in modules. The right-hand cavity will accept either an h.f. tuning unit (0.5–30MHz in one band) or a v.l.f. tuning unit (10–500kHz in one band). The left-hand

cavity can accept a battery pack which contains its own automatic charging circuit, a panoramic display, a digital frequency read-out unit with digital a.f.c. facilities or a digital frequency synthesizer with 100-Hz resolution. The receiver has been designed for a.m., s.s.b, c.w. and f.m. operation. The use of separate upper and lower sideband filters enables independent sideband operation with a simple adaptor. A high m.t.b.f. of 10,000 hours is claimed. Astro Communications Laboratory (U.K.), Coventry.

**WW317 for further details.**

## Colour TV Pattern Generator

The Philips PM 5508 pattern generator, available from Pye Unicam, takes full advantage of the "self checking" properties of the PAL system which enables a receiver to be adjusted using the picture tube as the only indicator. This virtually eliminates the need for an oscilloscope, but, if one is used it can be synchronized by line and field sync pulses from the generator. The generator delivers ten signals which are selected by the push-buttons arranged across the front panel: (1) Black and white checkerboard of 6 squares by 8 squares for checking tuning, scanning, amplitude and linearity, (2) Blank raster with constant white content for purity check, (3) Blank raster with constant red content for purity check, (4) Eight-step staircase for grey scale tracking, (5) 11 dots by 15 dots for adjustment of static and dynamic convergence, on 625 lines only, (6) Cross hatch, 11 lines by 15 lines, for adjustment of static and dynamic convergence, on 625 lines only, (7) Four colour bars for delay line phase and amplitude adjustment, using tube as indicator, (8) Four colour bars for demodulator phase adjustment, using tube as indicator, (9) Four colour bars for matrix check, using an oscilloscope, (10) Eight colour bars similar to B.B.C. signal for general check. The lower half of the picture is white to serve as reference to enable the adjustment of the amplitude ratio of the colour-difference signals to the picture tube. Alternatively a simple modification enables colour bars to be produced over the whole screen if this is preferred. The



ranges covered are bands I, III, IV and V, which are selected by push-buttons and continuous tuning is provided. Outputs are 15–20mV at r.f. (continuously variable) and 1V at video, both into 75 $\Omega$ . Burst amplitude is variable for checking colour killer and a.g.c. The sound carrier can be modulated internally, unmodulated or switched off. The generator measures approximately 270 × 290 × 190mm and weighs approx. 5.6kg. Pye Unicam Ltd, York Street, Cambridge.

**WW331 for further details**

## Transistors for switching 150W Pulses

Three new silicon planar transistors announced by Mullard have high switching rates and very low saturation voltages of not greater than 0.9V. Consequently, although the transistors, types BDY60, BDY61 and BDY62, have a continuous power rating of only 15W they can switch 150W pulses that have a duration not exceeding 50 $\mu$ s and a duty factor of 0.1. Earlier devices that switched 150W pulses had to have a higher continuous rating because they could not switch so rapidly. Although particularly suitable for use in high-frequency, silent, inverters and converters where efficiency is required, these types can also be used with advantage as pulse modulators in communications and radar systems. Typical transition frequency,  $f_T$  ( $I_C = 0.5A$ ,  $V_{CE} = 5V$ ) is 100MHz, and minimum  $h_{FE}$  ( $I_C = 0.5A$ ,  $V_{CE} = 10V$ ) is 45. Mullard Ltd, Torrington Place, London W.C.1.

**WW 313 for further details**

## Sine/Cosine Module

Burr-Brown have announced a sine/cosine function generator, model 4118/25, that may be used to produce various trigonometric gain responses. The module provides non-linear gain-shaping such that the output is  $-10 \sin \theta$ , where  $\pm 10V$  of input voltage represents a  $\pm 90^\circ$  of angle  $\theta$ . In addition, the unit may be connected to form cosine functions. By adding one or more external operational amplifiers, operation may be extended to include four-quadrant sine and cosine functions. Arc cosine and arc sine response functions may also be obtained. Accuracy is  $\pm 1\%$  of full-scale for  $\pm 10V$  input and




improves for small signals. Frequency response for accuracy of  $\pm 1\%$  is d.c. to 1kHz—this accuracy includes both amplitude and phase shift errors. Temperature range is  $-25^\circ$  to  $+85^\circ$  C. The module is self contained and requires no external components. Operation is from  $\pm 15$ V supply. Fluke International Corporation, Garnett Close, Watford WD2 4TT.

**WW330 for further details**
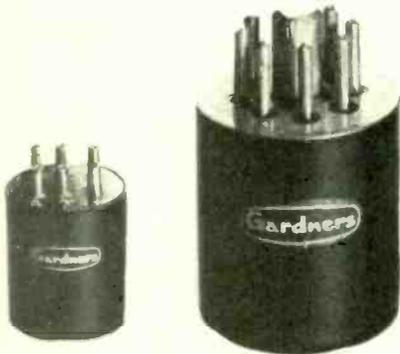
## New Audio Transformers

A new range of line-matching and microphone transformers for audio equipment is announced by Gardners Transformers. These complement the existing range introduced in 1961 and they come in two basic sizes using international octal, British 7-pin or flying screen lead connections. They are suitable for general purpose applications at high and low signal levels. Some of the new transformers, although similar in size and performance



to the existing types, now have a 20,000V capability to meet the Post Office requirement. They are protected mechanically by a new filling of closed-cell epoxide resin foam compound (the smaller types are vacuum-impregnated with a micro-crystalline wax). Advanced technical data sheets AT15, AT16 and AT17 are available from the makers. Gardners Transformers Ltd, Christchurch, Hants., BH23 3PN.

**WW 304 for further details**

## Precision R.F. Power Leveller

Weinschel Engineering introduces its model 1805 precision r.f. power leveller. This instrument is specifically designed to ensure precision and simplicity in systems used for transferring calibration factors of primary standards to bolometer mounts or secondary power standards (terminating or feed-through type) and power meters. Model 1805 in conjunction with a d.c.-to-r.f. continuously variable attenuator, such as a p.i.n. modulator, establishes and maintains constant, precisely known reference values of r.f. power incident upon a terminating mount or emerging from a feedthrough mount into a  $Z_0$  load. Minimum power level control range of 20dB is employed and only d.c.-substituted and bias power is used to maintain precise power levels, thus eliminating the a.c./d.c. error which is commonly found in some r.f. power bridge circuits. Selectable d.c.-



substituted power levels are 0.5, 1.0, 5.0 and 10mW; an external input capability is provided for establishing power levels between the fixed values. A selected level is maintained to within  $\pm 0.1\% + 1\mu$ W and is held constant for long periods of time over an ambient temperature range of  $20^\circ$  C and r.f. source level variations of  $\pm 3$ dB. Once the desired power is selected with the range selector, the setting of a single toggle switch results in automatic control to maintain the selected value. If a deviation occurs, it is indicated on a meter having a  $0.2\mu$ W resolution. Price \$2,950. Weinschel Engineering Co, Inc., Gaithersburg, Maryland 20760, U.S.A.

**WW324 for further details.**

## General Coverage Receiver Kit

The GR-78 general coverage receiver recently announced by Heath Company provides a.m., c.w. and s.s.b. coverage from 190 kHz to 30 MHz in six switch-selected bands. Solid-state circuit employs field-effect transistors in the r.f. section and four ceramic i.f. filters for improved sensitivity and selectivity and eliminating the need for alignment. Built-in bandspread tuning can be calibrated for either the shortwave broadcast or amateur bands, and a switchable 500-kHz crystal calibrator insures accurate dial calibration. This receiver comes complete with a rechargeable nickel-cadmium battery pack with a built-in charging circuit. Wiring options permit operation from either 120 or 240V a.c. and 12V d.c. Other features include switched a.g.c., an automatic noise limiter, receiver muting for use with a transmitter and a front panel relative signal strength meter. Price £68 18s. Daystrom Ltd, Heathkit Division, Gloucester.

**WW 311 for further details**

## Time-interval Module

Time-interval measurements between pulses derived from two different lines can now be made with the addition of a time-interval unit, the PM6631, to the Philips PM6630 counter available from Pye Unicam. The unit can measure time



intervals between pulses with the same or opposite polarity, and also with amplitude differences as great as 20:1. With the addition of the PM6631, the counter can measure time intervals in the range 50ns to  $10^6$  seconds on pulses with widths down to 5ns. The triggering level for both pulses is individually adjustable in the range  $\pm 1.5$ V (no attenuation) to  $\pm 30$ V (20:1 attenuation), and trigger sensitivity is 150mV (pk-pk) for all pulses with widths greater than 5ns. Also provided is a separate d.c. output which indicates the trigger level used on the stop pulse and an oscilloscope output which can be used to display the exact position of the stop pulse in relation to the start one. Apart from this new measuring facility, the PM6630 combines a 160MHz frequency range with a 50mV r.m.s. input-signal sensitivity and an input impedance of either  $1M\Omega/15pF$  or  $50\Omega$ . A 100 MHz internal clock makes the instrument useful for signal-generator and communications equipment calibration, oscillator drift measurements and computer-clock frequency checks. Pulse width and delay measurement can also be obtained. Pye Unicam Ltd, York Street, Cambridge.

**WW326 for further details**

## Rotary Stud Switch

The Elma sub-miniature rotary stud switch now features an improved case in glass-filled polycarbonate. This material is unaffected by most common solvents and is easily marked to aid wiring. Switches are available with tags for direct wiring to p.c. boards and may be supplied with screwdriver slots instead of shafts. Different torque settings are available. The



standard torque setting is 200 gm/cm; 400 and 600 gm/cm can be supplied to order. A ceramic wafer and gold-plated stud contacts are used. Contact resistance is better than  $5m\Omega$  and wafer insulation better than  $10^{13}\Omega$ . Switching capacity is up to 1A. Radiation Components Ltd, 76 Crown Road, Twickenham, Middlesex.

**WW 309 for further details**

## Rotary Switch Kit

Switch kit series 44K30 by Highland Electronics enables designers to assemble their own prototype rotary switches. Over 400 switch combinations can be constructed with up to 12 poles and 12 switch positions. Assembled switches have an adjustable stop which can be changed without break-

*continued on page 197*

# There is an M in Ferguson

It stands for Motorola and you'll see it in the Ferguson single standard 3000 colour TV chassis. It's the mark of Motorola quality and reliability that got radio on the road and helped to put men on the moon.

**A few facts:**

Motorola is one of the largest semiconductor manufacturers in the world. Principal manufacturing facility and development labs in Phoenix, Arizona; European HQ in Geneva; European factories in France and Scotland.

Motorola understands quality and reliability - it was their equipment that provided the essential communication links (radio and TV) between the moon's surface and earth.


That's why there is an M in Ferguson. — it stands for reliability

Motorola Semiconductors Limited  
York House, Empire Way, Wembley, Middx.  
Tel: 01-903 0944. Telex: 21740  
Motsem Wembley.

Motorola makes  
a world of  
semiconductors



**MOTOROLA  
Semiconductors**

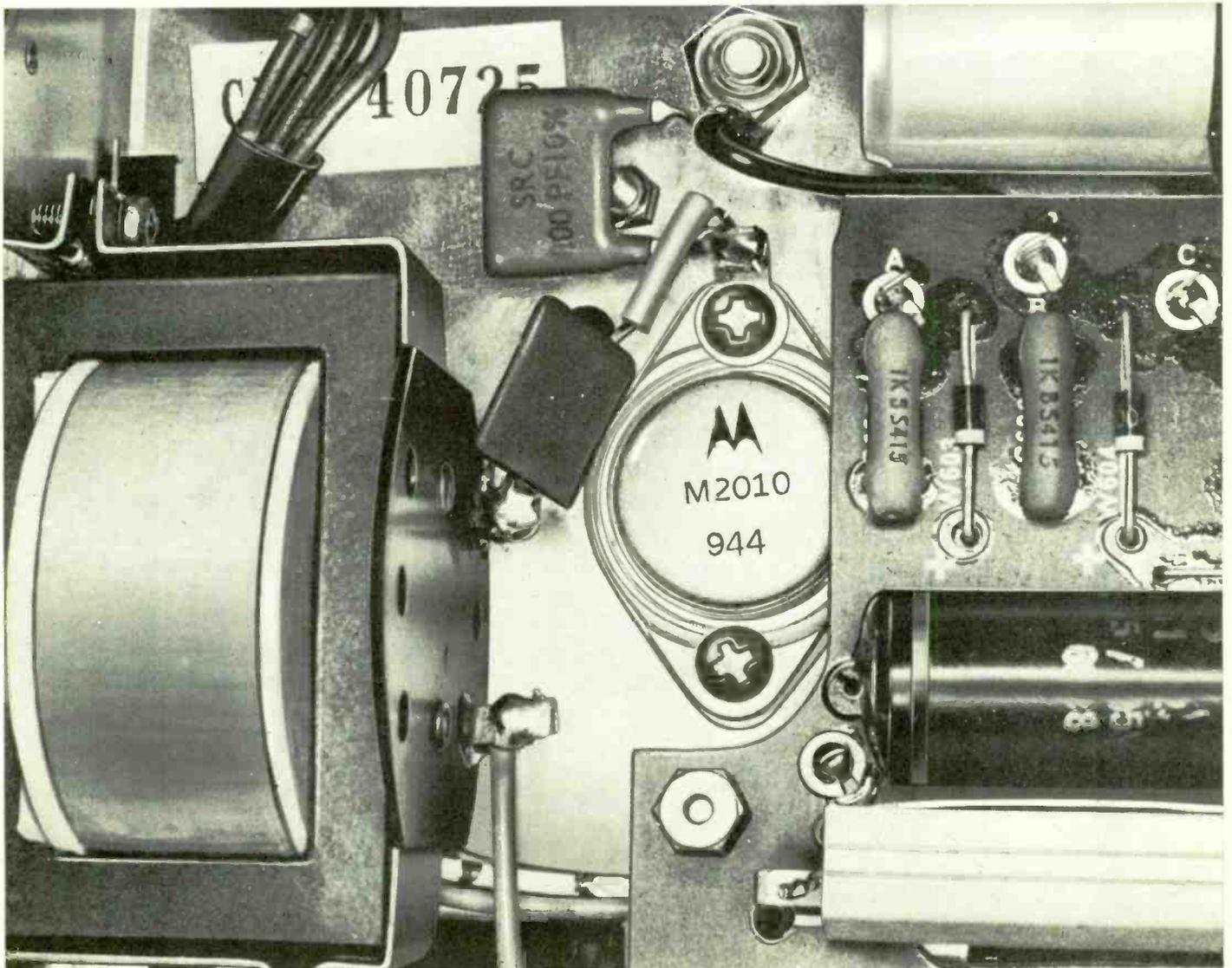

WW-105 FOR FURTHER DETAILS

# Europe's biggest sellers are still going strong



You're in excellent company with these general purpose instruments, they've just passed their 20,000th sale.

Understandable when you consider their price performance.

## The 1420 D.V.M.

2.5 $\mu$ V-1000V  
120 dB noise rejection  
0.05% accuracy  
33 conversions per sec  
5000 M $\Omega$  input resistance

## The 1400 Scope

Large, bright display  
9 modules to choose from  
for your 'tailor-made' spec.  
Choice of 3 amplifiers,  
including differential.  
3 time bases, including  
sweep delay.  
An X-Y plotter and custom  
blanks.



Post the magazine's reply-paid card and we'll send you our data sheet of full details.

**SOLARTRON**  
**Schlumberger**

The Solartron Electronic Group Ltd Farnborough Hampshire England Telephone 44433


WW-106 FOR FURTHER DETAILS

[www.americanradiohistory.com](http://www.americanradiohistory.com)

ing-down the switch. Components are re-usable and can be returned to the kit when the prototype is dismantled. Typical contact resistance is  $10\text{m}\Omega$  and contact rating is 0.5A at 230V a.c. resistive; 1A at 28V D.C. resistive. Highland Electronics Ltd, 33-41 Dallington Street, London E.C.1. **WW322 for further details.**
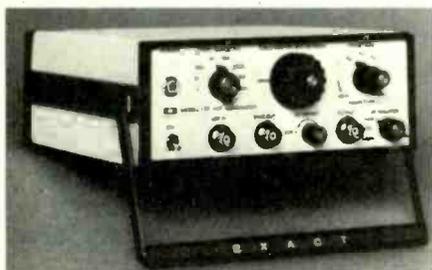
## Voltage-coupled Waveform Generator

A waveform generator with voltage-controlled frequency over a 1000:1 ratio, and a bandwidth from 0.1Hz to 3MHz, is being marketed by Environmental Equipments. The instrument, model 123, produces sine, square and triangular waveforms, as well as a sync pulse. Frequency is controlled to  $\pm 2\%$  accuracy by a Kelvin-Varley divider in the form of a multiplier with both digital and vernier adjustments. External voltage control can



either be d.c. programming or a.c. frequency modulation. The output for all waveforms is at least 20V pk-pk into an open circuit, or 10V pk-pk into a  $50\Omega$  load. Attenuation of 60dB in steps of 20dB is provided, as well as variable  $\pm 5\text{V}$  d.c. offset and floating output. A search mode is provided so the operator can use the vernier in the multiplier to sweep over a 1000:1 (three-decade) range within the frequency range selected. Both top and bottom panels of the instrument case are easily removable for calibration and maintenance. Environmental Equipments Ltd, Denton Rd., Wokingham, Berks.

**WW328 for further details**

## 50-MHz Counter/Timer

Latest addition to the Marconi Instruments counter/timer range, TF2411, features a choice of plug-in frequency standards permitting the user to order an instrument with a performance and accuracy best suited to his applications. The TF2411 performs a wide range of functions including period and multi-period measurements, time interval, ratio and frequency measurements up to 50MHz. Using mainly integrated circuits and based on a system of plug-in printed circuit boards, the counter/timer has an f.e.t. input giving 10mV sensitivity and  $1\text{M}\Omega$  input impedance. Seven-digit readout is provided with a binary memory, and there is an optional b.c.d. printer-output. The cabinet measures  $89 \times 280 \times 254$  mm. The three plug-in




frequency standards at present available for TF2411 are: TM9933—a high-performance crystal and oven with an age rate of  $1 \times 10^{-7}$  per month and a warm-up time of 10 minutes to reach  $1 \times 10^{-7}$  operation; TM9888H—simple crystal oscillator which includes a 10-MHz external standard panel; and TM9890 which accepts external standard frequency signals between 1 and 10MHz. The choice of standard is made at the time of ordering. Marconi Instruments Ltd, Longacres, St. Albans, Herts.

**WW 312 for further details**
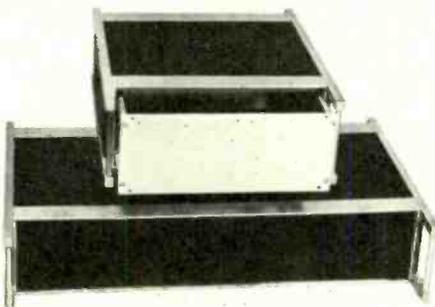
## Equipment Cases

A range of modular instrument cases from Case Systems has been designed to give a flexible and compact method of housing electronic equipment. The cases are constructed from aluminium extrusions and plastic mouldings. Each case is mechanically stable when placed on any of its six sides, and the handles protect panel components, such as meters and switches, when the case is placed face



downwards or accidentally dropped. The protrusions at the rear which allow the case to stand face upwards, also protect rear connectors and components. The standard case, CS1 which is bench mounting can be converted to 19-in rack mounting simply by fitting brackets to each side. The CS1 will accept one module M1 or two modules M2. The CS2 or "half rack" case accepts one module M2 only. Case Systems, 20 Hunt Lane, Chadderton, Lancs.

**WW329 for further details**

## High-Q Varactor Diodes for X-Band


Four gallium arsenide, Schottky barrier diodes announced by Mullard are intended for use as tuning elements in microwave circuits. Because the four devices, which form the 821CXY family, have resistances of not more than  $3\Omega$ , high Q-factors can be achieved. The diodes have zero-bias junction capacitances of 0.8 to  $2.5\text{pF}$ , depending on the type. Breakdown voltage

is not less than 12V, and the minimum ratio of junction capacitance at zero bias to capacitance at 12V reverse bias is 3. Mullard Ltd, Mullard House, Torrington Place, London W.C.1.

**WW327 for further details**
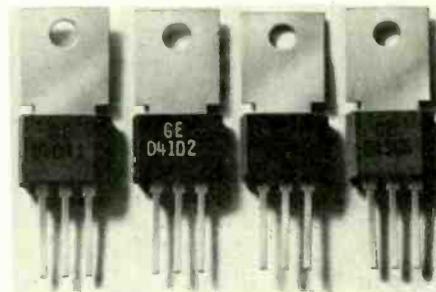
## Colour-coded Audio Output Transistors

The full range of G.E. (U.S.A.) Power-Tab a.f. output transistors is now available from Jermyn Industries. Four main types, colour-coded for easy identification, make up two sets of complementary stereo



pairs: D40 brown, 1A 6W, n-p-n; D41 black, 1A 6W, p-n-p; D42 red, 3A 12W, n-p-n; D43 green, 3A 12W, p-n-p. Each type is available with 30, 45 or 60V continuous rating, with a wide range of gains up to 30. The flat pins are easily formed to TO5 or TO66 configurations. 100 up prices range from 7s 8d to 21s. Jermyn Industries, Vestry Estate, Sevenoaks, Kent.

**WW325 for further details**

## Low-drift Op. Amps.

Advance Electronics announce three low-drift versions of their ZEL 1 series operational amplifiers. They are designated ZEL 1/02, /03 and /04 and have drift characteristics of 2.5, 5 and  $10\mu\text{V}/^\circ\text{C}$  respectively. Other main features of the ZEL 1 range are: d.c. gain  $5 \times 10^5$  min; offset current 5nA max; slew rate  $6\text{V}/\mu\text{s}$  min; c.m.r.r. 20,000 and input noise  $2\mu\text{V}$  r.m.s. Prices £18 10s (/02), £11 (/03) and £8 10s (/04). Advance Industrial Electronics, Raynham Road, Bishops Stortford, Herts.

**WW 314 for further details**

## Subminiature Relays

Two miniature relays measuring only 20.3mm long by 14.2mm wide by 6.35mm high have been introduced by Bourns. These are models 3120 s.p.d.t. and 3121 d.p.d.t. Both have a 1A rating at 26V d.c. and an operating temperature range of  $-65$  to  $+125^\circ\text{C}$ . Coil resistance and sensitivity ranges for the 3120 and 3121 respectively are  $50-2,000\Omega$ , 100mW nominal, and  $65-2,000\Omega$ , 160mW nominal. Contact material is gold-plated semi-precious metal and a life of 100,000 cycles is claimed. Bourns (Trimpot) Ltd, Hodford House, 17/27 High Street, Hounslow, Middx.

**WW319 for further details.**

# Literature Received

*For further information on any item include the WW number on the reader reply card*

## ACTIVE DEVICES

We have received the following literature from Marconi-Elliott Microelectronics Ltd, Witham, Essex.

- t.t.l. 9000 series applications handbook .. price 30s
- medium scale integrated circuits and memory elements product guide ..... WW401
- emitter coupled current steering logic data sheets: MB501 dual four-input gate with bias driver ..... WW402
- MB502 dual four-input gate with bias driver and phantom NOR output ..... WW403
- MB503 eight-input logic gate with bias driver ..... WW404

Microwave Associates, Ltd, Luton, Beds., have sent us a folder containing the following:

- Micronotes ..... WW405
- high-power varactors (two) data sheet .. WW406
- bulletin 4058 p.i.n. switching diodes (low-medium power) ..... WW407
- bulletin 4059 p.i.n. switching diodes (high-power) ..... WW408
- bulletin 4060 35V tuning varactors ..... WW409
- bulletin 4061A avalanche oscillator diodes WW410
- bulletin 4063 varactors, high-power ..... WW411
- bulletin 4065A snap varactors ..... WW412
- bulletin 4067A varactors, high-power ... WW413
- bulletin 4073 X-band Schottky diodes ... WW414
- bulletin 4074/5/6/7/8/9, snap varactor diodes ..... WW415
- bulletin 4081 90V tuning varactors ..... WW416

A number of additions for the Microspot cathode-ray tube manual and display equipment manual may be obtained from Ferranti Ltd, Gem Mill, Chadderton, Oldham, Lancs ..... WW417

"What is Thick Film?", is the title of a leaflet which may be obtained from Reliance Controls Ltd, Drakes Way, Swindon, Wilts ..... WW418

National Semiconductor Corporation, 2975 Ysidro Way, Santa Clara, California 95051, have published a data sheet on the LH101 operational amplifier, which is a variant of the LM101, and is now being manufactured in monolithic form ..... WW419

Silicon General Inc., 7382 Bolsa Ave., Westminster, California 92683, U.S.A., have sent us data on the following products:

- SG-1402, -2402, -3402 variable gain wideband amplifier/multiplier ..... WW420
- SG-710A, -710 differential voltage comparator ..... WW421
- SG-710B, -710C differential voltage comparator ..... WW422
- SG-711A, -711 voltage comparator ..... WW423
- SG-711B, -711C voltage comparator ... WW424
- SG-105, -205, -305 voltage regulators .. WW425

Two more data sheets on d.t.l./t.t.l. compatible m.t.n.s. circuits from General Instrument Microelectronics, Stonefield Way, Ruislip, Middx, HA4 0JT, are available.

- SS-6-2004 dual 4-bit parallel access, reversible static shift register ..... WW426
- SL-6-4025/32, quad 28/32-bit static shift register ..... WW427

Leaflet No. 1, volume 1, of the Hivac Application Bulletin describes the use of glow diodes (cold-cathode glow-discharge tubes), in a number of circuits. Hivac Ltd, Stonefield Way, Ruislip, Middlesex ..... WW428

A loose-leaf catalogue produced by Rastra Electronics Ltd, 275 King St, Hammersmith, London W.6, lists integrated circuits, transistors, diodes and many other items ..... WW429

Quarndon Electronics (Semiconductors) Ltd, Slack Lane, Derby, DE3 3ED., who are distributors for Texas Instruments, S.G.S., Raytheon, Emihus and Sprague, have produced a comprehensive semiconductor catalogue, "Semicon 70", which is now available ..... WW 462

The E.E.V. equivalents for nearly 2000 valves are listed in the "Equivalents Index—1970" which is published by the English Electric Valve Co. Ltd., Chelmsford, Essex ..... WW 463

We have received a short-form catalogue from the Signetics Corporation, Trident House, Hayes, Middlesex, which lists linear and digital integrated circuits ..... WW 464

## PASSIVE COMPONENTS

The 5th edition of "Components Applications Data", may be obtained from Radiospares, P.O. Box 427, 13-17 Epworth St, London E.C.2 ..... WW430

A leaflet, "Electrolube Contact Lubricant", is available from Electrolube Ltd, Oxford Avenue, Slough, Bucks ..... WW431

Microwave waveguide filters manufactured by Ferranti Ltd, Components Division, Dunsinane Avenue, Dundee DD2 3PN, Scotland, are described in a leaflet ..... WW432

"Military Specification Connector Manual", lists the products of Elco Pacific, 2200 Park Place, El Segundo, California 90245 ..... WW433

Two additions have been received for the Eric Catalogue dealing with r.f.i. filter devices. Eric Electronics Ltd, South Denes, Great Yarmouth, Norfolk ..... WW434

"Product Selector Guide", from the Dialight Corporation, 60 Stewart Avenue, Brooklyn, N.Y.11237 lists indicator lamps, digital readouts and illuminated push-button switches ..... WW435

The new range of "Control-Line" Modules, which operate high-current loads from low-level control systems without mechanical contacts, are described in a catalogue from FR Electronics, Flight Refuelling Ltd, Wimborne, Dorset ..... WW436

"Component Socket Guide", from the Elco Corporation, Willow Grove, Pennsylvania 19090, U.S.A., lists valve, crystal, relay, transistor and d.i.l. sockets ..... WW437

Reed relays are the subject of a new catalogue from:

Kempston Electrical Co. Ltd, Shirley Rd., Rushden, Northants ..... WW438

A catalogue listing the products distributed by the D-T-V Group, 126 Hamilton Rd, London S.E.27, is available ..... WW439

A range of contactless switches is described in a catalogue from Cole Electronics Ltd, Lansdowne Rd, Croydon CR9 2HB ..... WW440

Miniature switches, microphones, headsets, leads, plugs and sockets are the subject of a catalogue from Danavox (Great Britain) Ltd, "Broadlands", Bagshot Rd, Sunninghill, Berks. .... WW 465

Two engineering bulletins received from Sprague (U.K.) Ltd., Sprague House, 159 High St., Yiewsley, West Drayton, Middlesex, describe capacitors.

2705A Metalized polycarbonate-film capacitors ..... WW466

3456A Aluminium capacitors, non-aqueous electrolyte ..... WW467

An eight-page potentiometer selection guide is available from Reliance Controls Ltd, Drakes Way, Swindon, Wilts. .... WW 468

Details of a seven-day prototype illuminated pushbutton switch service are given in literature from Forder Graham Ltd., Pinnacle Hill, Keslo, Roxburghshire. The service is based on a 4-pole change-over switch which can be supplied in banks with a variety of mechanical actions and contact configurations ..... WW 469

## HARDWARE, ETC.

A data sheet from Firth Cleveland Fastenings Ltd, Treforest, Pontypridd, Glamorgan, pictorially shows the uses of a range of Spire fasteners ..... WW441

A copy of a paper "New Cleaning and Drying Techniques for Critical Electronic Assemblies", is available from: I.C.I. Ltd, Thames House North, Millbank, London S.W.1 ..... WW442

A modular connecting system called Hypertac is described in a leaflet S/294C from Smiths Industries, Industrial Instrument Division, Kelvin House, Wembley Park, Middx ..... WW443

Applications data and technical information on Loctite products for thread locking, retaining and sealing is given in a brochure from: Douglas Kane Group Ltd, Swallowfields, Welwyn Garden City, Herts. WW444

## EQUIPMENT

Over 200 power supply modules and about 50 measuring instruments are the subject of a leaflet from Lambda Electronics, 21 Aston Rd, Waterlooville, Portsmouth, Hants ..... WW445

Performance details of the type TSA 6636/3 counter timer are in a data sheet. Venner Electronics Ltd, Kingston By-Pass, New Malden, Surrey. ... WW446

Helium-neon lasers are described in a leaflet from Ferranti Ltd, Dunsinane Avenue, Dundee DD2 3PN, Scotland ..... WW447

A leaflet describing the digital voltmeter type LM 1867 may be obtained from the Solartron Electronic Group Ltd, Farnborough, Hants ..... WW448

Lyons Instruments Ltd, Hoddesdon, Herts, have produced a leaflet which describes six pulse generators ..... WW449

A Gunn-oscillator, type PM7015X is described in a leaflet from Sivers Lab, U.K. Office, Old Haverhill Rd, Little Wratting, Suffolk ..... WW450

The following literature is available from Dana Electronics Ltd, Bilton Way, Dallow Rd, Luton, Beds:

- Series 5740 digital voltmeters ..... WW451
- Series 5700 digital voltmeters ..... WW452

We have received the following literature from

Marconi Instruments Ltd, Longacres, St. Albans, Herts.

Automatic testing—the way ahead ..... WW453  
TF 2210, 100MHz oscilloscope ..... WW454

Lyons Instruments (Hoddesdon, Herts), newsletter for January 1970 discusses a programmed pulse system for dynamic testing ..... WW455

Thyristor controllers for use between 100 and 300A are the subject of a data sheet published by AEI Semiconductors Ltd, Carholme Rd, Lincoln. WW456

“Servoscribe” flat-bed chart recorders are described in a leaflet from the Industrial Instrument Division, Smiths Industries Ltd, Wembley, Middx ..... WW457

The diverse products of Hewlett Packard Ltd, 224 Bath Rd, Slough, Bucks, for measurement, analysis and computation are described in a handsome 647-page hard-bound volume ..... WW458

The following two brochures are obtainable from Racial Group Services Ltd., 26 Broad St., Wokingham, Berks.

Solid state h.f. communications receivers .. WW 470  
Radio telecommunications equipment and systems ..... WW 471

V. N. Barrett & Co. Ltd., 1 Mayo Rd., Croydon, CRO 2QP. Surrey, have produced a new catalogue of used scientific and industrial equipment .. WW 472

**GENERAL INFORMATION**

“Product Guide—1970”, published by the Electronic Engineering Association, Berkeley Square House, Berkeley Square, London W.1, lists manufacturers of electronic capital equipment ..... WW459

The Mullard Educational Service, Mullard House, Torrington Place, London W.C.1, have produced a leaflet listing all the publications available from them ..... WW460

“Measuretest” instrument application notes (numbers 001 and 002), for colour television are available from Marconi Instruments Ltd, Longacres, St. Albans, Herts ..... WW461

Tektronix U.K. Ltd, Beaverton House, P.O. Box 69, Harpenden, Herts, have three more books in their “Concept” series available; the price is 10s each including packing and postage. They are:

- Horizontal Amplifier Circuits
- Oscilloscope Probe Circuits
- Probe Measurements

R.C.A. Great Britain Ltd, Lincoln Way, Windmill Rd, Sunbury-on-Thames, Middx, have available application note ICAN-4158 “Application of the CA 3059 zero-voltage switch in thyristor circuits”..... WW 462

The Scientific Instrument Manufacturers’ Association of Great Britain, SIMA House, 20 Peel St, London W.8, have produced a booklet called “Metrication Guide” which is available from them price 50s.

Two new publications are available from the Mullard Educational Service, Mullard House, Torrington Place, London W.C.1

“A simple f.e.t. voltmeter” ..... WW 473  
“Introducing thyristors” ..... WW 474


We have received two publications from the British Calibration Service, Millbank Tower, London S.W.1, which are listed below. The first of these explains what the British Calibration Service is and how a laboratory may apply for approval. The second publication lists all the laboratories that have obtained approval so far together with the type of measurements they can carry out and the degree of accuracy guaranteed.

About the British Calibration Service ... WW475  
Directory of Approved Laboratories ... WW476



# BULGIN PRECISION ELECTRONIC COMPONENTS
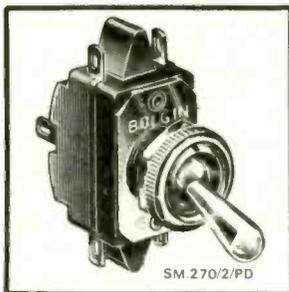
## COMPREHENSIVE RANGE OF MOULDED SWITCHES





**DOUBLE POLE RANGE**

Illustrated left is the SM.270/2/PD, one of a new range of 14 Double Pole Moulded Insulation Switches, universally D.P. Change-Over, which can switch On-Off or Off-On as desired, by not connecting two tags. The body moulding is Grey, internal contacts and solder tags are silver plated and metal front of panel parts are chromed. Operation can be Toggle, Biased Toggle, Biased Push, Push-Push (successional) Action, Push-Pull Action, Semi-Rotary Shaft or Key and the connection tags accept solder or 110 series push on tabs. Various modifications can be supplied, to agreed quantity orders. Send for the Moulded Switch Wall chart listed for the full list of modifications available.

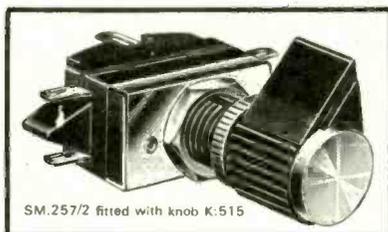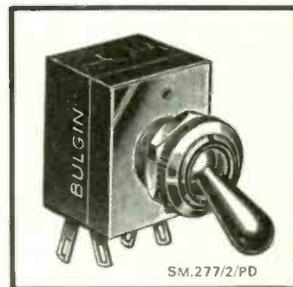**NEW 4 CONTACT & 8 CONTACT MODELS**

Illustrated right is one of a range of two NEW further types of Double Pole Moulded Insulation Switch with a higher rating than the Double Pole range above.

Two versions are available, both Toggle operated SM.277/2/PD is a D.P. Make-Break (4 contact) Switch (illustrated), rated at 4A at 250V A.C. and SM.301/2/PD is a D.P. Change-Over 8 contact model, rated 3A at 250V A.C. for double pole alternative circuit switching. In both cases the body is a polished Grey moulding, the internal contacts and solder tags are silver plated and the front of panel parts are chromed. Only one modification is available for this range as tabulated.





**DOUBLE POLE ROTARY MODEL**

Illustrated left is a semi-rotary shaft version of one of the above mentioned Double Pole Moulded Switches. The model is rated at 2A 250V A.C. N.1. with 1/4" Ø shaft and head guide Make and Break action fine silver cleaning contacts and solder tag connections.

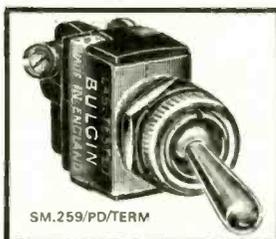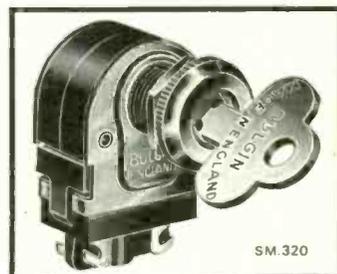**SINGLE POLE RANGE**

Illustrated right is one of the complete range of Single Pole Moulded Insulation Switches manufactured by the latest automatic methods, with constant testing ensuring that the highest standard of finish is always maintained. All front of panel parts are plated in brilliant chrome, except where moulded operators are used, which are black. Internal contacts and solder tags are heavily silver plated for the best possible connection whilst all other metal parts are suitably protected against corrosion, the polished Black moulded body gives excellent insulation.



A wide range of different models are available. Operation can be Toggle (illustrated left), Biased Toggle, Biased Push, Push-Push (successional) Action, Push-Pull, Slider, Key, and Semi-rotary Shaft (illustrated above right). Connection in all cases is to Solder Tags, with Screw Terminals available to order as an alternative on some models. A wide range of modifications can be supplied to agreed quantity orders, see the moulded switch wall chart.  
Proof Test=2K.V. at 50 c/S. I.R. <  
100MΩ dry or recovered at 500V.

**SEND FOR COMPREHENSIVE MOULDED SWITCH/LAMINATED SWITCH EQUIVALENT LIST REF 1536/C**

**A. F. BULGIN & CO. LTD.,**  
Bye Pass Rd., Barking, Essex.  
Tel: 01-594 5588 (12 lines)

MANUFACTURERS AND SUPPLIERS OF RADIO AND ELECTRONIC COMPONENTS TO

ADMIRALTY	MINISTRY OF WORKS	B.B.C.
WAR OFFICE	MINISTRY OF AVIATION	G.P.O.
AIR MINISTRY	MINISTRY OF TECHNOLOGY	I.T.A.
HOME OFFICE	RESEARCH ESTABLISHMENTS	N.P.L.
CROWN AGENTS	U.K.A.E.A.	D.S.I.R.

WW-107 FOR FURTHER DETAILS

# April Meetings

*Tickets are required for some meetings: readers are advised, therefore, to communicate with the society concerned*

## LONDON

1st. I.E.E.—Discussion on "Electrical measurement on acoustic surface wave devices" at 17.30 Savoy Pl, W.C.2.

1st. I.E.E.—Discussion on "Direct digital measurement of physical quantities" at 18.00 at 9 Bedford Sq., W.C.1.

3rd. I.E.E.—"Implementation of digital filters" by Prof. R. Boite at 17.30 at Savoy Pl., W.C.2.

3rd. I.E.E.—Discussion on "Aeronautical communication by satellite" at 17.30 at Savoy Pl., W.C.2.

6th. I.E.E.—Discussion on "Multi-element phased arrays" at 17.30 at Savoy Pl., W.C.2.

7th. I.E.E./R.Ac.S.—"Satellite communication" by J. K. S. Jowett at 18.00 at Savoy Pl., W.C.2.

8th. I.E.E.—Colloquium on "High resolution systems" at 14.30 at 9 Bedford Sq., W.C.1.

9th. R.T.S.—"Creating colour television titles" by M. H. Cox and R. Knight at 19.00 at I.T.A., 70 Brompton Road, S.W.3.

15th. I.E.E.—Discussion on "Photolithographic techniques in microelectronics" at 17.30 at Savoy Pl., W.C.2.

15th. B.K.S.T.S.—"The Minicam: the Pye/CBS miniature colour television camera" by Len Cosgrove at 19.30 at I.T.A., 70 Brompton Road, S.W.3.

20th. I.E.E./I.E.R.E.—Colloquium on "Skynet" at 10.00 at the I.E.E., Savoy Pl., W.C.2.

22nd. I.E.E.—"Telecommunications support for the Apollo programme" by Lorne M. Robinson (N.A.S.A.) at 17.30 at Savoy Pl., W.C.2.

22nd. I.E.R.E.—"Real-time computer model (business games)" by D. Simpson at 18.00 at 9 Bedford Sq., W.C.1.

23rd. I.E.E.—"Quasars and radiogalaxies" by Professor F. Hoyle at 17.30 at Savoy Pl., W.C.2.

23rd. Inst. Electronics—"Modern aspects of electronic instrument design" by G. F. Penner at 18.30 at West Ham College of Technology, Stratford, E.15.

23rd. R.T.S.—Fleming Memorial Lecture "The impact of automation on television transmission" by F. H. Steele, G. A. McKenzie and R. H. Vivian at 19.00 at the Royal Institution, Albermarle St., W.1.

28th. I.E.R.E.—Symposium on "Capacitors" at 10.00 at 9 Bedford Sq., W.C.1.

29th. I.E.E.—"Ionospheric research by means of oblique incidence sounders" by P. Bradley at 17.30 at Savoy Pl., W.C.2.

29th. I.E.R.E.—"Scanning circuits for 110° colour tubes" by K. E. Martin at 18.00 at 9 Bedford Sq., W.C.1.

30th. I.E.E./I.E.R.E.—"Microprogramming and processor design" by Prof. M. V. Wilkes at 17.30 at Savoy Pl., W.C.2.

30th. R.T.S.—"An image analyser for medicine using colour television techniques" by M. B. Coyne, F. Paice & Prof. E. D. Williams at 19.00 at the Wolfson Institute, Royal Postgraduate Medical School, Hammersmith Hospital, Ducane Road, W.12.

## BARROW-IN-FURNESS

15th. I.E.E.—"Application of lasers" by Prof. E.D.R. Shearman at 19.30 at the Hotel Imperial, Cornwallis St.

## BELFAST

10th. I.E.R.E.—"Aerials" by H. V. Sims at 18.30 at the Ashby Inst., the Queen's University, Stranmillis Road.

14th. I.E.E.T.E.—"Concorde—flight/auto controls and navigation" by H. Hill at 19.30 at the Ashby Institute, the University, Stranmillis Road.

17th. I.E.E.—Faraday Lecture—"People, communications & engineering" by J. H. H. Merriman at 20.00 at Sir Wm. Whitla Hall, Queen's University.

21st. I.E.E. Grads.—"Metal oxide silicon transistors" at 18.30 at the Main Lecture Theatre, Ashby Institute, Stranmillis Road.

## BIRMINGHAM

8th. I.E.E. Grads.—"Thyristor drives" by M. F. Arnold at 19.00 at the Sumpner Bldg, the University of Aston, Gosta Green.

9th. I.E.R.E.—"Gramophone records—past and present" by G. M. Nathan at 19.30 at the University's Dept. of Electronic & Electrical Eng'g.

15th. R.T.S.—"University of Birmingham television service" by Dr. Peter Whitaker at 19.00 at the University.

## BLETCHLEY

21st. I.E.E.—"Lasers and their applications" at 19.15 at Harwood House College.

## BRIGHTON

14th. I.E.E.—"On the future of world communication" by Prof. E. C. Cherry at 18.30 at the College of Technology, Lewes Rd, Moulsecoumb.

## CARDIFF

6th. I.E.E.—"Digital filters" by Dr. R.C.V. Macario at 18.00 at U.W.I.S.T.

23rd. R.T.S.—"The E.V.R. system" by Sir Francis McLean at 19.00 at the B.B.C. Llandaff.

## CARLISLE

8th. I.E.E.T.E.—"Application of thyristors to industrial control systems" by S. Denyer at 19.30 at the Technical College, Victoria Place.

## CHATHAM

23rd. I.E.R.E.—"Automatic trains on the Victoria Line" by R. I. M. Arthurton at 19.00 at the Medway College of Technology.

## CHELMSFORD

15th. I.E.E.—"Radio-astronomy, thirty-five years progress" by F. W. Hyde at 18.30 at the King Edward Grammar School.

28th. I.E.R.E./I.E.E.—"24-channel p.c.m." by A. Stevens at 18.30 at the Civic Centre, Duke Street.

## DUBLIN

15th. I.E.E.—Faraday Lecture—"People, communications & engineering" by J. H. H. Merriman at 20.00 at R.D.S. Hall.

## DURHAM

22nd. I.E.E.T.E.—"Application of thyristors to industrial control systems" by S. Denyer at 19.30 at the University's Science Laboratories, South Road.

## EVESHAM

20th. I.E.E./I.E.R.E.—"Large scale integration in microelectronics" by D. D. Jones at 19.30 at the B.B.C. Engineering Training Centre, Woodnorton.

## LEEDS

16th. I.E.R.E.—"Thyristors into the home and industry" by R. Willis at 19.30 at the University's Dept. of Electronic and Electrical Eng'g.

28th. I.E.E.—"Electronic measurement as a guide to archeological research" by E. T. Hall at 18.30 at the University.

## LIVERPOOL

1st. I.E.E. Grads.—"Laser holography" by Dr. J. M. Burch at 18.30 at the University.

6th. I.E.E.—"The pulsars" by Prof. F. Graham Smith at 18.30 at the University.

22nd. I.E.R.E.—"Schools project technology" at 19.30 at the University's Dept. of Electrical Eng'g.

## MANCHESTER

8th. I.E.E. Grads.—"Communications bit by bit" by H. B. Law at 18.45 at U.M.I.S.T.

14th. I.E.E.—"History and development of time & frequency measurement" by C. R. Cordwell at 18.15 at U.M.I.S.T.

22nd. I.E.E.—"Radar data processing techniques with application to air traffic control" by Dr. P. J. C. Child at 18.15 at Renold Bldg, U.M.I.S.T.

## NEWCASTLE-UPON-TYNE

8th. I.E.R.E.—"The symbolic integrated maintenance systems" by J. Hambleton at 18.00 at the Polytechnic (Rutherford College), Ellison Pl.

## NORWICH

14th. I.E.E.—"Electronic performance testing of motor vehicles" by E. Gamble at 19.30 at the Assembly Hall.

## NOTTINGHAM

16th. R.T.S.—"Duplication of BBC-1 on u.h.f. & introduction of 3-channel colour" at 19.30 at the B.B.C. Studios, Wilson House, Derby Road.

## PLYMOUTH

14th. I.E.E.T.E.—"Oceanographic instrumentation" by Lt. Cdr. T. J. Woodfin and Eng. Sub. Lt. M. Rushton at 19.30 at the Lecture Theatre, the College of Technology.

## PORTSMOUTH

21st. I.E.E.—"Aids to all-weather landing of aircraft" by M. Catton at 18.30 at the Polytechnic, Anglesea Rd.

## READING

16th. I.E.R.E.—"The design of solid-state audio amplifiers" by P. J. Baxandall at 19.30 at the J. J. Thomson Lab., the University, Whiteknights Pk.

## RUGELEY

2nd. I.E.R.E.—"Engineer to manager—effecting the transition" by M. W. Lauerman at 19.00 at the Shrewsbury Arms Hotel, Market St.

## SALFORD

13th. I.E.E.—"Electronics, man & aerospace" by R. E. Young at 19.30 at the University.

14th. I.E.E.—"Electronics, man & aerospace" by R. E. Young at 14.30 (students) and 19.30 at the University.

## SALISBURY

13th. I.E.E.—"Colour television" by L. G. Dive at 19.00 at the Salisbury & Wilts College of Further Education, the Friary.

## STOKE-ON-TRENT

9th. I.E.E. Grads.—"Voltage and its measurement from 'A' to about 'Q'" by F. W. Senior at 19.15 at the North Staffs College of Technology.

## SWANSEA

9th. I.E.E.—"M.O.S. integrated logic" by J. A. Roberts at 18.15 at University College, Singleton Pk.



## Go digital-with SE

See voltage, frequency, period, time, count, ratio — clearly, accurately.

With many variables, the instrument of the future is digital. As you would expect, S.E. Laboratories is in the forefront of this development, already offers you a huge range of accurate, versatile instruments at a rational price.

S.E. Digital Voltmeters are so cleverly designed that you can virtually have your D.V.M.s made to measure, from basic laboratory instruments to sophisticated data logging versions. The choice includes 3 models and 8 variations, with a maximum range up to 1kV, maximum resolution 10 $\mu$ V, accuracy 0.01%, and many different options including floating input, stored display, printer output, etc.

S.E. Timer Counters give you digital display at its most attractive and dependable: Five large, vividly illuminated figures. Simple and handy controls. Five modes — frequency, period, time, count and ratio — you see all these, accurate to one part in a million  $\pm 1$  count! With the Counters, too, S.E. offers you many features, including indefinitely held display, manual reset, remote start/stop, and others.

All S.E. digital instruments give you top value for your money. *See for yourself:* Write for details or for immediate demonstration.




**SE Laboratories (Engineering) Limited.** North Feltham Trading Estate, Feltham, Middlesex.  
Telephone: 01-890-1166 & 5246 (sales); 01-890-5876 (works). Telegrams: Selab, Feltham. Telex: 23995.  
Northern Sales Office, Bessell Lane, Stapleford, Nottingham. Telephone: Sandiacre 3255.

WW-108 FOR FURTHER DETAILS

[www.americanradiohistory.com](http://www.americanradiohistory.com)
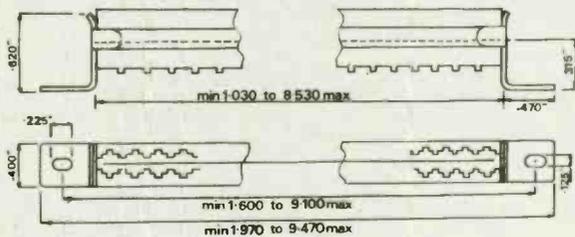
# McMurdo's new 0.10" Pitch Connector - "RL" Series




5 to 85 way single sided with solder and printed wiring tails.  
 10 to 170 way double sided with solder and printed wiring tails.  
 Wire Wrap and Crimp tails will shortly be available.

Working Voltage	(To be advised)
Proof Voltage	(To be advised)
Insulation resistance (dry)	10 <sup>9</sup> Megohms min.
Contact resistance to test gauge	10 Milli-ohms max.
Insertion and withdrawal forces	6 oz. per contact max.
Contact finish	Flow tin or hard gold (specify when ordering)

Another new product from:  
 McMurdo Instrument Co. Ltd., Rodney Road, Portsmouth,  
 Hampshire. Telephone: Portsmouth 35361. Telex: 86112.

**mcMurdo**  
 great facility for service

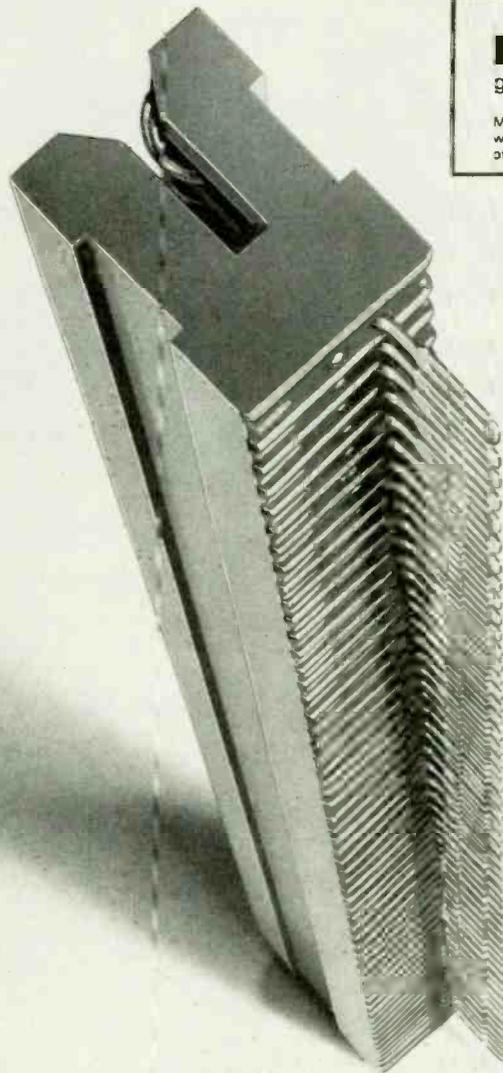
Member of the Louis Newmark Group,  
 with access to the combined facilities  
 of all other member companies.




Authorised Stockists:—Lugton & Co. Ltd., 209/210 Tottenham  
 Court Road, London W.1. Tel: 3261  
 I.T.T.—electronic services, Standard Telephones & Cables Ltd.,  
 Edinburgh Way, Harlow, Essex. Tel: Harlow 26777.  
 and agents in principal overseas countries.

WW—109 FOR FURTHER DETAILS

# SINCLAIR IC-10

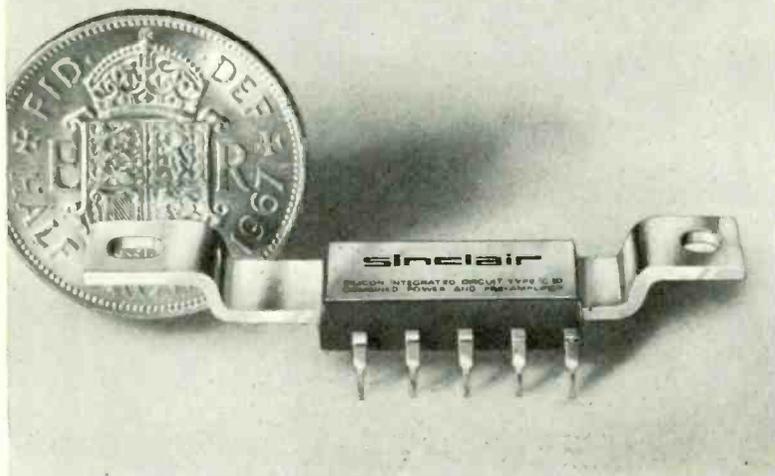
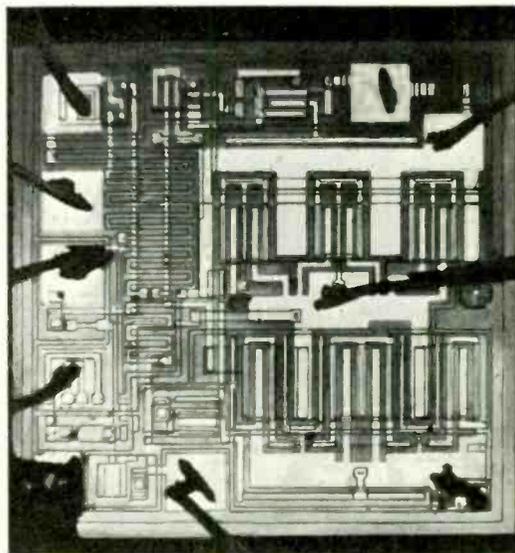
## MONOLITHIC INTEGRATED CIRCUIT AMPLIFIER AND PRE-AMP



*A 13 transistor circuit measuring only one twentieth of an inch square by one hundredth of an inch thick!*

## the world's most advanced high fidelity amplifier

The Sinclair IC-10 is the world's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself, a chip of silicon only a twentieth of an inch square by one hundredth of an inch thick, has 5 watts R.M.S. output (10w. peak). It contains 13 transistors (including two power types), 2 diodes, 1 zener diode and 18 resistors, formed simultaneously in the silicon by a series of diffusions. The chip is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins. This exciting device is not only more rugged and reliable than any previous amplifier, it also has considerable performance advantages. The most important are complete freedom from thermal runaway due to the close thermal coupling between the output transistors and the bias diodes and very low level of distortion.

The IC-10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of such components as tone and volume controls and a battery or mains power supply. However, it is so designed that it may be used simply in many other applications including car radios, electronic organs, servo amplifiers (it is d.c. coupled through-out), etc. Once proven, the circuits can be produced with complete uniformity which enables us to give a full guarantee on every IC-10, knowing that every unit will work as perfectly as the original and do so for a lifetime.

MORE SINCLAIR DESIGNS ON PAGES FOLLOWING

# sinclair

SINCLAIR RADIONICS LTD. 22 NEWMARKET ROAD, CAMBRIDGE  
Telephone: 0223 52731

WW-110 FOR FURTHER DETAILS

www.americanradiohistory.com

### ■ SPECIFICATIONS

Output:	10 Watts peak. 5 Watts R.M.S. continuous
Frequency response:	5 Hz to 100 KHz $\pm 1$ dB
Total harmonic distortion:	Less than 1% at full output.
Load impedance:	3 to 15 ohms.
Power gain:	110dB (100,000,000,000 times) total.
Supply voltage:	8 to 18 volts.
Size:	1 x 0.4 x 0.2 inches.
Sensitivity:	5mV.
Input impedance:	Adjustable externally up to 2.5 M ohms.

### ■ CIRCUIT DESCRIPTION

The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. Class AB output is used with closely controlled quiescent current which is independent of temperature. Generous negative feedback is used round both sections and the amplifier is completely free from cross-over distortion at all supply voltages, making battery operation eminently satisfactory.

### ■ APPLICATIONS


Each IC-10 is sold with a very comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include stabilised power supplies, oscillators, etc. The pre-amp section can be used as an R.F. or I.F. amplifier without any additional transistors.

SINCLAIR

# IC-10

with IC-10 manual  
Post free.

# 59' 6

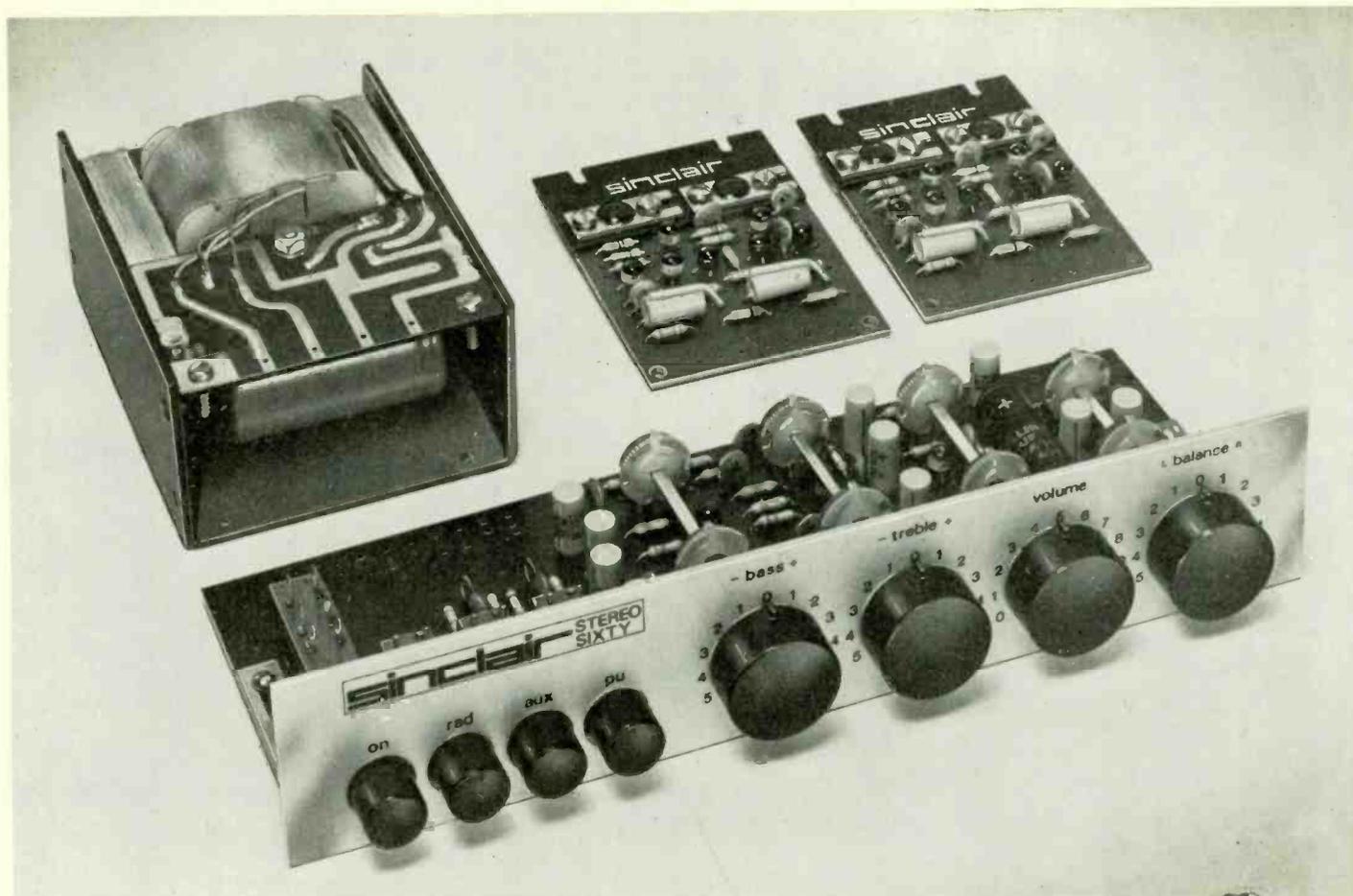

## Project 60 an exciting alternative

The buyer of an amplifier today has a remarkably wide variety to choose from. It is unlikely that a purchaser would have real difficulty in finding a unit that met all his requirements, although the price might not be as low as could be wished. The only snags are that one's needs can change and that the technically correct amplifier may be physically inconvenient. If you are confident that there is an amplifier available, of the right size and price, which will meet all your needs for the foreseeable future, then that is your best buy. If not, however, we can offer you another possibility which we believe to be an exciting alternative approach. That alternative is **Project 60**.

Project 60 is a range of modules which connect together simply to form a complete stereo amplifier with really excellent performance. So good, in fact, that only 2 or 3 amplifiers in the world can compare with it in overall performance.

The modules are: 1. The Z-30 high gain power amplifier, which is an immensely flexible unit in its own right. 2. The Stereo 60 preamplifier and control unit. 3. The PZ.5 and PZ.6 power supplies. A complete system comprises two Z-30's, one Stereo-60 and a PZ-5 or PZ-6. The power supplies differ in that the PZ-6 is stabilised whilst the PZ-5 is not. This means that the former should be used where the highest possible

continuous sine wave rating is required. In a normal domestic application there will not be a significant difference between using either power unit unless loudspeakers of very low efficiency are being used.

All you need to assemble your system is a screwdriver and a soldering iron. No technical skill or knowledge whatsoever is required and, in the unlikely event of you hitting a problem, our customer service and advice department will put the matter right promptly and willingly.

Perhaps the greatest beauty of the system is that it is not only flexible now but will remain so in the future. We shall shortly be introducing additional modules which will include a comprehensive filter unit, a stereo F.M. tuner and an even more powerful amplifier for very large systems. These and all other modules we introduce will be compatible with those shown here and may be added to your system at any time.

Project 60 modules have been carefully designed to fit into virtually every known type of plinth or cabinet. Only holes have to be drilled into the wood of the plinth or cabinet to mount the Stereo 60 and any slight slips here will be covered completely by the aluminium front panel of the control unit. The Project 60 manual gives all the instructions you can possibly want clearly and concisely.

# sinclair

SINCLAIR RADIONICS LTD · 22 NEWMARKET ROAD · CAMBRIDGE  
Telephone: 0223 52731

WW—111 FOR FURTHER DETAILS

# Z-30 TWENTY WATT R.M.S. (40 WATT PEAK) POWER AMPLIFIER

The Z-30 is a complete power amplifier of very advanced design employing 9 silicon epitaxial planar transistors. Total harmonic distortion is incredibly low being only 0.02% at full output and all lower outputs. As far as we know, no other high fidelity amplifier made can match this specification, no matter what the price. Thus you can be utterly certain that your Project 60 system will do full justice to your other equipment however good it may be. The Z-30 is unique in that it will operate perfectly, without adjustment, from any power supply from 8 to 35 volts. It also has sufficient gain to operate directly from a crystal pickup. So in addition to its use in a high fidelity system you can use a Z-30 to advantage in your car or a battery operated gramophone for your children, for example. These, and many other applications of the Z-30, are covered in the Project 60 manual.

## SPECIFICATIONS

Power output—15 watts R.M.S. (30 watts peak) into 8 ohms using a 35 volt supply; 20 watts R.M.S. (40 watts peak) into 3 ohms using a 30 volt supply.

Output—Class AB.

- Frequency response: 30 to 300,000 Hz  $\pm$  1dB.
- Signal to noise ratio: better than 70dB unweighted.
- Distortion: 0.02% total harmonic distortion at full output into 8 ohms and at all lower output levels.
- Size:  $3\frac{1}{2} \times 2\frac{1}{2} \times \frac{1}{2}$  inches.
- Input sensitivity: 250mV into 100 Kohms.
- Damping Factor: >500.
- Loudspeaker impedances 3 to 15 ohms.
- Power requirements: 8 to 35 V.d.c.


# STEREO SIXTY PREAMPLIFIER AND CONTROL UNIT

The Stereo 60 is a stereo preamplifier and control unit designed for the Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout and great attention has been paid to achieving a really high signal-to-noise ratio and excellent tracking between the two channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs. The tone controls are also very carefully designed and tested.

## SPECIFICATIONS

- Input sensitivities—Radio—up to 3mV; Magnetic Pickup—3mV Correct within  $\pm$  1dB on R.I.A.A. curve. Ceramic Pickup—up to 3mV; Auxiliary—up to 3mV.
- Output—250mV.
- Signal-to-noise ratio—better than 70dB.
- Channel matching—within 1dB.
- Tone Controls—TREBLE +15 to -15dB at 10 KHz; BASS +15 to -15dB at 100Hz.
- Power consumption 5mA.
- Power requirement—PZ.5 or PZ.6.
- Finish—brushed aluminium front panel with black knobs.
- Mounting—on cabinet front by spindle bushes and adjustable brackets.

# SINCLAIR POWER SUPPLY UNITS

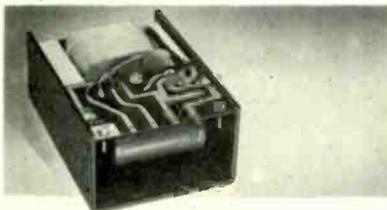

**PZ-5** 30 volts un stabilised—sufficient to drive two Z-30's and a Stereo 60 for the majority of domestic applications.

Price: £4. 19s. 6d.


**PZ-6** 35 volts stabilised—ideal for driving two Z-30's and a Stereo 60 when very low efficiency speakers are employed.

Price: £7. 19s. 6d.


**SINCLAIR RADIONICS LIMITED**  
22 NEWMARKET ROAD, CAMBRIDGE  
Telephone 0223 52731
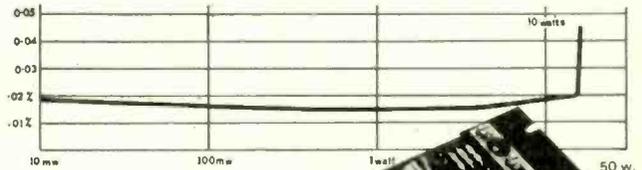
## APPLICATIONS

High fidelity amplifier; car radio amplifier; record player fed direct from pick-up; intercom; electronic music and instruments; P.A., laboratory work, etc. Full details of these and many other applications are given in the manual supplied with your Z.30.



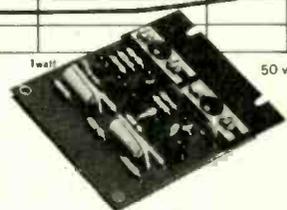
Power versus distortion curve of Sinclair Z.30.



**Z.30**

Ready built, tested and guaranteed, with Z.30 manual.

**89/6**

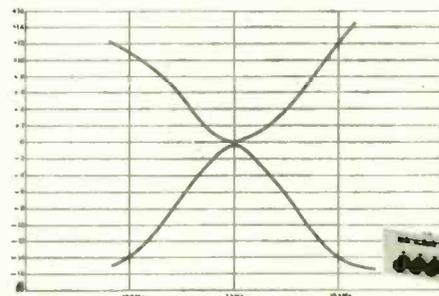

Treble and bass control curves



**STEREO SIXTY**

Ready built, tested and guaranteed **£9. 19s. 6d.**

## GUARANTEE

If at any time within 3 months of purchasing Project 60 modules from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter.

To: SINCLAIR RADIONICS LTD., 22 NEWMARKET RD., CAMBRIDGE

Please send

NAME

ADDRESS

for which I enclose cash/cheque money order

WW370

WW—112 FOR FURTHER DETAILS

## Low cost regulated DC power supplies

Compact modular design providing optimum performance at low cost. Fully stabilised supplies from 0 - 60V up to 3A per module. Modules can be arranged for series or parallel operation.

the new  
M.V. range



**KSM** KSM Electronics Ltd., Bradmore Green  
Brookmans Pk., Herts. Tel Potters Bar 59707

WW-113 FOR FURTHER DETAILS

# CHILTON

## 2 CHANNEL AUDIO RECORDER

- ★ 10 watts continuous per channel
- ★ Fully transistorised on 10 printed circuit boards
- ★ 3 head system and 3 speeds 19-9.5-4.75 cms
- ★ Mechanism operated by 4 DC solenoids
- ★ Provision for full remote control


Robust construction and attention to detail make this an outstanding British tape recorder for industrial or domestic use. 38 cms version to special order.

Portable 4 speaker version

Oiled Teak surround version

RELIABLE

SHORT CIRCUIT  
PROOF

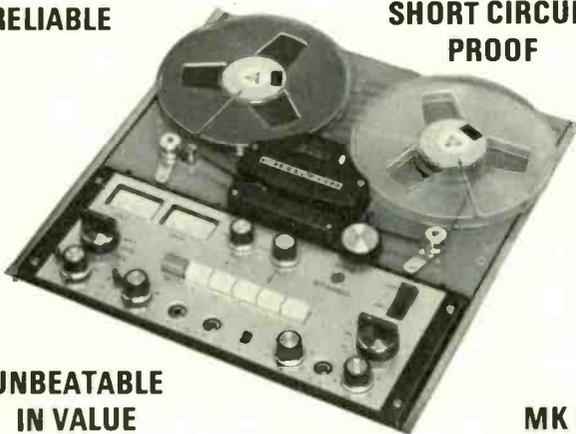

UNBEATABLE  
IN VALUE

MK II



Send for informative brochure fully explaining:

1. Why a single motor. 2. Electrical performance. 3. Wow and flutter.

**MAGNETIC TAPES LTD.**  
CHILTON WORKS, GARDEN ROAD, RICHMOND, SURREY  
Tel: 01-876 7957

WW-115 FOR FURTHER DETAILS

# WELWYN TOOLS

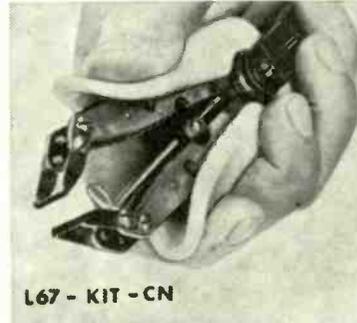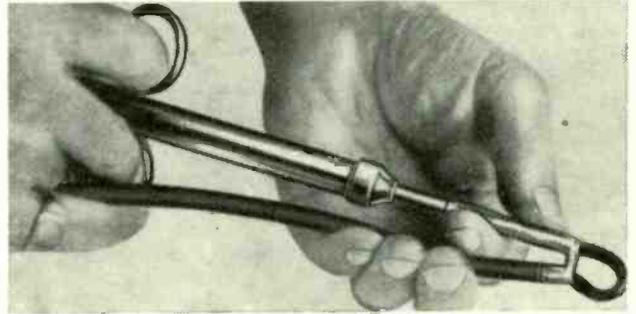

L67 - KIT - CN

For Inner Core  
Ejection and Heated  
Wirestripping  
Miniature Soldering  
and Electronic  
Instrument Work

USE W.T.C. Wire Ejectors, LUCO Electrically Heated Wire Strippers (see illustration), Finest Soldering Needles, Box Joint Miniature Cutters and Pliers including Tip Cutting Pliers, Printed Circuit Crimping and Cutting Pliers, Torque Wrenches and Piercing Punches. If you require quality tools ask for Catalogue WW/70



Welwyn Tool Co. Ltd.

STONEHILLS HOUSE WELWYN GARDEN CITY  
WELWYN GARDEN 25403

WW-114 FOR FURTHER DETAILS

## Cut costs with Sprague

### 36D SERIES CAPACITORS



# WEL

High surge current capacity for discharge use. High ripple current rating for power supply use.

	Price	Price
11,000 μF 100V	1-49	50 up
14,000 μF 75V	62/-	59/-
42,000 μF 30V	34/-	31/6
36,000 μF 30V	47/6	45/-
24,000 μF 30V	40/-	38/-
	31/-	29/-

Microfarads come cheaper from WEL

**WEL COMPONENTS LTD.**  
5 Loverock Road, READING. Tel. 580616/9  
MINISTRY OF TECHNOLOGY APPROVED DISTRIBUTOR

WW-116 FOR FURTHER DETAILS

# TEST GEAR

**CONVERTOR/BATTERY CHARGER.** Input 240v 50 c/s, output 12v 5 amp DC. Input 12v DC, output 240v AC. 170 watt max. With fuse and indicator lamps. Size 9 1/2 x 10 x 4 1/2 in. Weight 19lb. An extremely compact unit that will give many years' reliable service. Supplied with plug and lead. Only £4/10/-. P. & P. 15/- extra. As above—fully serviceable—perfect interior but soiled exterior cases. £3. P. & P. 15/-.

**G.M. TUBES.** Brand new. G24/G38/G80 at 27/6 ea. G53/1, brass cases. £6 ea.

**PHOTOMULTIPLIERS.** EMI 6097X at £8/10/- ea. **TRANSISTOR OSCILLATOR.** Variable frequency 40 c/s to 5 kc/s. 5 volt square wave o/p. for 6 to 12v DC input. Size 1 1/4 x 1 1/4 x 1 1/4 in. Not encapsulated. Brand new. Boxed. 11/6 ea.

**COUNTENAY TIMER** sub-chassis with 2-12AU7, transistor, relay etc. Requiring 12V. A.C. or D.C. to operate 22/6.

As above but 1, 5, 10 or 15 minutes. State which. 25/- ea. **RECEIVER UNIT TYPE 114.** Freq. coverage 124-156 mc/s I.F. out 9.72 mc/s. Size 7 x 1 1/4 x 5 1/4 in. In original service carton, complete with valves, connections, etc. 32/6 ea. P. & P. 5/- ea.

### RELAYS

Omron/Schrack octal based plug-in relays. 2 pole c/o 5A, 6v only. Brand new. Boxed. 12/6 ea.

G.E.C. 4 pole c/o 6/12v operation 180 ohms. Platinum contacts. Brand new. Boxed 12/6 ea.

Min. VARLEY type VP4. 4 pole c/o 15 K/ohm. Brand new 4/6 ea.

Min. S.T.C. 4-pole c/o 7.5-18V. 185 ohms. Brand new boxed. 8/- ea. 6/- ea. per 100.

S.T.C. sealed 2 pole c/o 48V. 2,500 ohm 48v. 3/6 ea. 12v 7/- ea.

**CARPENTERS** polarised single pole c/o 20 and 65 ohm coil as new, complete with base 7/6 ea. Single pole c/o 680, 1,110 and 1,570 ohm coil. As new 6/6 ea. Brand New. Single Pole c/o (type 5A2), 2 x 1200 ohms. 8/6 ea.

### POTENTIOMETERS

**COLVERN** Brand new. 5; 10; 50; 100; 250; 500 ohms; 1; 2.5; 5; 10; 25; 50k all at 2/6 ea. Special Brand new **MORGANITE** 250K 1 in. sealed. Normal price 9/-, our price 3/6 ea.

**INSTRUMENT** 3" Colvern. 5; 25; 100 ohms; 2.5. All at 7/- ea.

**TRIM POTS:** Paignton-solder lugs 5, 10 & 25K at 5/- each; Pins 10; 20; 50; 100; 200; 250; 500 ohms; 2.5; 25 and 50K at 10/- each.

**DARSTAN** preset-sealed 1/2" dia. 1 high. 1; 2 and 5K 1/4 ea.

**HIGH RESOLUTION** 25K 80 turns. Complete with knob 6/6

**GENERAL CONTROLS.** 100K Ten turn. Brand new. Boxed 25/- ea.

**ALMA** precision resistors 100K; 400K; and 998K—0.1% 5/6 ea; 3.25K—0.1% 4/- ea.

**DALE** heat sink resistors. non-inductive 50 watt. Brand new. 15 ohms—6/6 ea.; 8.2K 4/6 ea. Excellent dummy load.

### CAPACITORS

**ERIE** feed through ceramic 1000 pf—9d. ea. Sub-min. **TRIMMER** 1 square. 8, 5pf. Brand new 2/6 ea. Concentric **TRIMMER** 3/30 pf. Brand new 1/6 ea.

**DUBILIER** Electrolytic. 32+32+16mfd. 350V. D.C. Brand new. 4/6 ea.; 3/9 per doz.

**EHT** 1000pf 20KV working. Ideal transmitter blocking capacitors 6/6 ea.

**VISCONOL EHT.** Brand new 0.0005 25 kV. 16/- ea. E.H.T. 0.02mfd 8KV. 6/- ea.; 0.1mfd 2.5 KV-nitrogel—4/6 ea.; 0.5mfd 5KV—11/- ea.; 0.05mfd 10KV—7/6 ea.; 0.5mfd 2.5KV 7/- ea.

**GEARED MOTORS** 240v 50 c/s synchronous. Geared down to 80 rpm. Brand new 30/- ea. P. & P. 7/6.

**DIODES** 1N914. Brand new 1/3 ea.; 12/- doz.; £4—100; £25—1,000.

**PHOTOCELL** equivalent OCP 71 2/6 ea.

**BURGESS** Micro Switches VS 5930. Brand new 2/6 ea.

**BULGIN** panel mounting Lamp holders. Red. Brand new 2/3 ea.

**MINIATURE SPEAKERS** 15 ohm 2in. diameter. Brand new. 7/- ea. P. & P. 2/6 ea.

**CANNON XLR 11C** Plug. Brand new 10/- ea.

**TRANSISTORS** BC 114—NPN Low noise high gain audio. etc.; BC 116—PNP General purpose 200 mc/s. Ex brand new equipment. Guaranteed perfect. Good lead length. 2/- ea.

### NUCLEONIC INSTRUMENTS

**SCALER** type 1009 by Dynatron. Suitable Beta/gamma counts. Built in test signal. Calibrated adjustable discriminator. Read out 2 decade neon and 4 digit counter. Supplied in as new condition at £5 ea. Carr. 30/-.

Few only **RATEMETER** type 1181B Complete with built in EHT supply. Separate metering EHT and Count. EHT available for external equipment 0 to 8 kv. As new £35. Carr. 30/-.

E.H.T. Power unit 0 to 5 kv. Stabilized by General Radiological. As new £20. Carr. 30/-.

**100 CHANNEL PULSE HEIGHT** analyser type 1863B. As new £75. As above but type 1863C. £120.

**ECKO PULSE HEIGHT ANALYSER** type N101 £25. Carr. 30/-.

**DEKATRON** Display unit type NIS 223. £20. Carr. 30/-.

**CINTEL** Transistorised Nucleonic Scaler with adjustable discriminator. 6 meter display 0-9 giving count of 10 to the 5. New Condition. Now ONLY £20. Carr. 15/-.

**PULSE** Generator type 1147A. £10. Carr. 30/-.

### OSCILLOSCOPES

**E.M.I.** WM 2 DC—13 mc/s £35

**SOLARTRON** 7118.2 D.B. DC—9 mc/s £60

**SOLARTRON** 643 DC—15 mc/s NOW only £65.

**SOLARTRON** 513/528 DC—10 mc/s £35

**SOLARTRON** 568 DC—6 mc/s £18

**COSSOR** 1035 DB. £20

**COSSOR** 1049; 1049 Mk. 3. DB. £22/10 and £30

**HARTLEY** 13A DB. £18/10/-

All carefully checked and tested. Carriage 30/- extra.

### MARCONI

TF 956 (CT44) Audio Freq. Wattmeter £15. Carr. 10/.

TF 886 Magnification Meter £45 Carr. £1

TF 782C UHF Generator £40 Carr. £1

TF 369 N. 5 Impedance Bridge £55 Carr. 30/-

TF 144G Signal Generator, Serviceable, Clean £15

In exceptional condition £25. Carr. 30/-

TF 885 Video Oscillator Sine/Square £35 Carr. 30/-

TF 899 Millivolt meter £8 Carr. 10/-

TF 195M Sine wave oscillator 0/40kc/s £12 Carr. £1

TF 1343/2 'X' Band gen. £35 Carr. 30/-

TF 428B/1 Valve voltmeter £4 Carr. 10/-

TF 428B/2 Valve voltmeter £8 Carr. 10/-

Type 801 Sig. Gen. £45. Carr. 30/-

TF 934/2 FM Deviation Meter £30. Carr. 30/-

TF 791B Carrier Deviation Meter £40 Carr. 30/-

### SOLARTRON

Pulse generator POS 100C 50 c/s—1 mc/s £18 Carr. £1

Laboratory amplifier AWS51A. 15c/s—350kc/s £35 Carr. £1

Stabilised P.U. SRS 151A £20 Carr. 30/-

Stabilised P.U. SRS 152 £15 Carr. 30/-

Stabilised P.U. AS 516 & AS 517 £3, and £6 Carr. 10/-

### AVO

**AVO VALVE CHARACTERISTIC** Meter. Excellent condition. £30 Carr. 30/-

Generator 50kc/s—80 mc/s £16 Carr. 15/-

Testmeter No. 1 £14 Carr. 15/-

Electronic Testmeter CT 38. Complete £18 Carr. £1

**SPECIAL** by G. & E. BRADLEY. Multimeter type CT471B. Battery operated, fully transistorised, sensitivity 100 M ohm/V, measures a.c./d.c. voltage (12mV-200V scales) +/— 3% /+ /— 2% (s.d.) a.c./d.c. current (12 microA-1.2A scales, +/— 3% /+ /— 2% (s.d.) resistance (12 ohm-120M ohm scales, +/— 3% m.s.d.), h.f./v/hf. voltage with multiplier (4V-400V scales up to 50 MHz; 40 mV-4V up to 1000 MHz). Brand new. Few only. £60 Carr. 30/-

### CINTEL

Wide Range Capacitor Bridge £25 Carr. 15/-

Sine and Pulse Generator type 1873 £25 Carr. 15/-

### AIRMEC

Valve Millivoltmeter type 264. 3MV-1V £20 Carr. £1

Counter type 865. 6 decades. Bright Vertical display gate facilities. Very good condition £30 Carr. 30/-

Klystron Power Supply 698B £25 Carr. £1

Signal Generator type 701. £35. Carr. 30/-

**OSCILLOSCOPE CAMERA** Cossor type 1428. Brand new with standard 4in. fitting and spare cassettes. £45

Also Shackman 26ft. Exp 270 frames. Times from 1/250 to 1 sec, auto. Dabene Fl. 9 Focal 1 1/2 in. with standard 4in. to 5in. fitting. £30.

**SOLARTRON CALIBRATION UNIT** type AT203. £25 Carr. 30/-

**SOLARTRON.** Process Response Analyser. Fine condition. £350.

E.H.T. Base B9A in Polystyrene holder with cover. Brand new. 2/6 ea.

**ZENITH E.H.T.** Tester, with Probes. Metered 0-3.5 kv. £25 Carr. 30/-

**DENCO** Travelling Wave Amplifier £40. Carr. 30/-

**HEINZ GUNTHER** AM/FM Generator 9—200 mc/s. £30 Carr. £1

**SIGNAL** Generator CT 63. Complete with leads. Good condition. £10 Carr. 15/-.

With copy of charts.

**FREQUENCY** Meter LM 14. Modulated version of BC 221 with charts and covers. Brand new £30. Carr. 30/-

**SPECIAL. FURZEHILL** V200 Valve millivolt meter. 10 mv to 1 kv. £25 Carr. £1

**MIC-O-VAC** type 22 (CT54) Volts; Current; Ohms. D C to 200 mc/s with probe, leads etc. As new £8/10/0 P. & P. 10/-

**VIBRATING REED ELECTROMETER** type N 572 by ECKO. Range 10 to the -14. Max sensitivity FSD for 1 of 0.03 Micro-microamps. £20 ea. Carr. £1

**SHORTS ANALOGUE COMPUTER.** Complete. Fine condition. £180 ea.

As above, complete, not serviced. £75 ea.

Also large quantity spares available. Carriage at cost.

**DISTRIBUTED AMPLIFIER** type 2C/3 50 c/s 100 mc/s Gain 300. £30 each

Type 2C 50 c/s to 100 mc/s £16 each.

**DAWE** Wide Range oscillator type 400A. 20 cs to 20 kc/s Sine wave. 500, 600 and 2000 ohm. Fine condition. £25. Carr. 30/-

**MUIRHEAD** type D729 AM. Phase meter. As new condition. In transit cases. £160

**PAIGNTON ATTENUATORS** 0.1 db. to 100 db. In 3 decades, 600 ohm. 19" rack mounting. £20 ea. Carr. 15/-

**PISTON ATTENUATOR** in carrying case. 30-140 mc/s calibrated 0/70 db. £10 ea. Carr. £1

**Precision THERMOSTOR** by YSI. 100 k. at 25°C. Range: 40°C. to 150°C. Supplied with charts giving ohms for each degree over entire range. Brand new. £2 ea.

**ADVANCE** Signal Generator type D1. 2 mc/s to 190 mc/s. Sine and square mod. With original charts. Excellent condition £12/10/0 P. & P. £1

**SERVOMEX.** Stabilized D.C. Power unit. Type 38. Bench mounting. 0-15 volts. 0-2.5 amps. Separate voltage and current meters £25.

**TRANSISTOR** Stabilised Power Unit. 48v. 4 amp. Manufactured by E.M.I. Open chassis. Brand new. Highest quality. Size 10 1/2 x 5 1/2 x 6 1/2 in. high. £6 ea.

**HOLGATE** 6 channel Event recorder. 1in. or 10in. inches per second. Size 4 1/2 x 5 x 8in. Excellent condition. £20.

**HEWLETT PACKARD** Recorder and Decoder type 20610. As new. Write or phone for further details. 19in. Rack Mounting CABINETS 6ft. high 2ft. deep. Side and rear doors. Fully tapped, complete with base and wheels. £12/10/0 Carriage at cost.

**MULLARD** Transistorised Analogue to Digital Converter Model L 281. As new. £20 Carr. 15/-

**SUNVIC DC** chopper Amplifier type DCA 1. Superb condition. £22/10/0 ea. Carr. 20/-

**PROCESS TIMERS** 8 individual timer circuits, each with 0-100 sec calibrated dials. Ideal displays, processes, etc. Standard mains input £20 Carr. 25/-

**ISOLATING TRANSFORMERS** 240V in 240V 7 KVA out. As new. £25 ea. Carr. £2/10/-

**DESK** Telephones. Current type. Standard dial. 3 wire red, green, white. Ideal extensions etc. As new £3 each. Same but older type 17/6 each. P. & P. 5/-

**DIECAST ALLOY** boxes. Size 4 x 2 1/2 x 1 1/2 in. Drilled ends for Belling Coax socket. 3 compartments link holes between. 6/6 each. P. & P. 2/-

**CONVERTOR** 50 c/s single ph. to 400 c/s 3 ph. 250w. in 8ft. enclosed 19" rack cabinet. £45 ea. Carr. at cost.

### METERS

**EHT ELECTROSTATIC** Ernest Turner, etc. 0-1.5kV. £2 ea.; 0-3.5 KV £2/15/0 ea.; 0-5 KV £3/10/0 ea.; 0-7.5 KV £4/5/0 ea.

**TAYLOR** 100-0-100 Micro amp scaled size 4 x 2" with internal lamp scaled 6-0-6 1/10/0 ea.

**GRIFFIN & GEORGE** 3" round in sloped open ended case with terminals 2 types 0/20; 2. £4/10/0. All 50 c/s. £1 ea.

### 4 DIGIT RESETTABLE COUNTERS, 1000 ohm.

coll. Size 1 1/2 x 1 x 4 1/2 in. As new, by Sedoco of Geneva. £2/10/0 each.

As above but 350 ohm. £3/10/0 ea.

### TRANSFORMERS. All standard inputs.

**STEP DOWN ISOLATING** trans. Standard 240v AC to 120v tapped 00-0-80 700w. Brand new. £6 ea. As above but 500w. £4 ea.

**75 WATT** Constant voltage transformer. 195 to 255 volts—240v out. 30/- each. P. & P. 5/-

**MODULATION** trans. PP—6 BW6. 30/- each. P. & P. 5/-

Transformer 0-215-250 120 MA; 6.3V 4A CT x 2; 2 x 6.3v 0.5A and separate 90v 100 MA 25/- each P. & P. 4/-

Matching contact cooled bridge rectifier 7/6 each. 3kv 4.5mA, 4v 0.5 amp x 2, 4v 1.1 amp. £3/10/- ea.

350-0-350 75mA, 5v 2 amps x 2, 21/- ea. Gardners 6.3v 2A; 6.3v 1.5A; 6.3v 0.1A. Size 3 x 1 1/2 x 4 1/2 in. As new. 9/6 ea. P. & P. 3/- ea.

Parmeko/Gardners. Potted. 475-60-0-60-475 at 160 mA; separate winding 215-0215 at 45mA; 6.3v 5A; 6.3v 0.75A; 5v 3A. As new. £3 ea.

Gardners 400-350-0-350-400 at 250MA; 0/4/6.3v 4 amp x 2; 0/4/6.3 2 amp; 0/4/5 3.5A. In original boxes. £4/10/- inc. post. Gardners 2kv 10MA. As new, £3 incl. postage.

Gardners 2kv 10MA and 4 volts x 2. £4/10/0 ea. incl. postage.

Parmeko 65v 1 amp. Separate 0-18-24v at 0.5 amp. 30/- ea. Gard/Par/Part. 450-400-0-400-450. 180 MA. 2 x 6.3v. £3 ea.

**ADVANCE** Constant Voltage Trans. 6 volts 50 watt. As new £3 P. & P. 10/-

Gardners 5v 30amp. Brand new £1/10 each incl. postage.

**CHOKES.** 5H; 10H; 15H; up to 120mA, 8/6 ea. Up to 250mA 12/6 ea.

Large quantity LT, HT, EHT transformers. Your requirements, please.

Panel switches DPDT ex eq. 2/6 ea.; DPST Brand new 3/6 ea.; DPDT twice, brand new 6/-; heavy duty DPST brand new 6/- ea.

**SPECIAL.** 813 valves. Brand new, boxed £2/10/0.

**PRECISION** continually rotatable stud switches. Single pole. 80 way can be stacked if required. £3 ea.

**PRECISION** rotary stud switches 2 pole 12W size 2" sq., 1" shaft. £2/10/0 ea.

Min. SEALED 4 pole 3 way and 3 pole 4 way rotary switches. 1" shaft 1" dia. x 1" 10/- ea. Solartron Storage. Oscilloscope type QD 910. MUST GO. Now only £100 each.

## CASH WITH ORDER

FOR CALLERS. Always a large quantity of components, transformers, chokes, valves, capacitors, odd units, etc., at 'Chiltmead' prices. Callers welcome 9 a.m. to 10 p.m. any day.

# CHILTM EAD LTD.

22 Sun Street · Reading · Berks · Tel. No. 65916

moving to 7-9-11 ARTHUR ROAD, 300 yds. east (rear Tech. College) Tel. No. 582605



**FREE NOW!**

16-PAGE TEST EQUIPMENT CATALOGUE. ALL ASPECTS OF LOW COST INSTRUMENTS FOR AMATEUR, PROFESSIONAL AND EDUCATIONAL USE. OVER 50 UNITS DETAILED.

**FREE!** ORDER AS PUBLICATION 'T.'

- ★MULTIMETERS
- ★VALVE VOLTMETERS
- ★AF, RF MILLIVOLTMETERS
- ★PANEL, FS METERS
- ★VARIABLE TRANSFORMERS
- ★SCOPE, DECADES
- ★POWER SUPPLIES
- ★AUDIO, RF GENERATORS
- ★TESTERS, CHECKERS

**\* SINE/SQUARE WAVE AUDIO GENERATOR**



Provides audio output on 4 bands. Sine wave 20c/s to 200 kc/s, output up to 7V. Square wave 60c/s to 30kc/s, 7V p-p. Distortion under 2%. Output impedance 1kΩ. Variable output amplitude control. Supplied with leads and instructions. A.C. mains operated.

TE22 Price £16.10.0  
Also TE22D (Size as TE20D) £16. 0.0

**\* GRID DIP METER**

All transistor grid dip meter, absorption wavemeter and osc. detector. Frequency range 440kc/s to 280Mc/s in 6 coils. Uses 3 transistors plus diode with 500μA meter. Internal battery.



TE15 £11.10.0 p.p. 3/6

**\* TRANSISTOR CHECKER**

Complete capacity for checking all transistors npn and pnp for alpha, beta and leakage. Also diodes. Complete with leads and instructions.



ZQM2 £5.19.6 p.p. 3/6

**\* VACUUM TUBE VOLTMETER**


Features low price for such an instrument. Large 6in. full view scaled meter. 28 ranges. D.C. volts: 0.1/1/5/15/50/150/500. A.C. volts: 0.1/1/5/15/50/150/500/1500 r.m.s.: 0.1/1/4/14/40/140/400/1400/4000 p-p. Resistance: R x 10-100k-10k-100k-1m-10m. Range 0.2 ohm to 1000MΩ. dB scales: -10 to +65dB. Complete with instructions and leads.



TE65 £17.10.0 p.p. 7/6

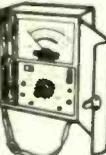**\* 50,000 OHMS PER VOLT MULTIMETER**

Recommended quality instrument with mirror scale and overload protection. 0/0.3/12/60/120/300/600/1200V d.c. (50KΩ/V); 0/16/30/120/300/600/1200V a.c. (10KΩ/V); 0/30/150/60/300mA, 0/12/24 resistance 0/10kΩ/1/10/100MΩ. Meter movement 20μA. Polarity reversing switch. Complete with batteries, leads and instructions.



AF105 £8.10.0 p.p. 2/6  
Leather case 28/6

**\* TRANSISTORISED RF MILLIVOLTMETER**

Mains or battery operated. 0/3mV up to 300V A.C. Input 1Meg. Response ±0.2dB 20c/s to 1Mc/s and ±1dB at higher and lower frequencies. Fully stabilised. Size: 150 x 240 x 114mm. Complete with handbook. 11 scales 0.003 FSD to 300V FSD. Also dBm and dBV scales.



YM51 Price £32 p.p. 8/6

**\* PORTABLE OSCILLOSCOPE**

Features 3in. clear view tube, easy to use controls and good stability. Y amp. Sensitivity. 1V p-p/CM. Bandwidth 1.5cps-1.5MHz. Input imp. 2 meg Ω. 25 PF. X amp sensitivity. 9V p-p/CM. Bandwidth 1.5 cps-800 KHz. Input imp. 2 meg Ω. 20 PF. Time base. 5 ranges 10 cps-300 KHz. Synchronization. Internal/external. Illuminated scale.



TO3 Price £37.10.0 p.p. 10/-

**\* 20,000 OHMS PER VOLT MULTIMETER**

Popular model but with extra scale range. 20,000 ohms per volt. 0/5/25/50/250/500/2500 V d.c., 0/10/50/100/500/1000V a.c., 0/150μA, 0/2/1/250mA. Resistance 0-6kΩ and 6MΩ. Also dB scales or capacitance. Model 200H Price 77/6 (Leather case, Price 15/- p.p. 2/-)



**\* RF SIGNAL GENERATOR**

Accurate wide range signal generator covering 120Kc/s-500Mc/s on 6 bands. Directly calibrated. Variable RF. attenuator, audio output. Xcal socket for calibration. 220/240V. A.C. Brand new with instructions. Size 140 x 215 x 170mm.



TE20D Price £15 p.p. 7/6

**NOMBREX TRANSISTORISED Test Equipment**

MODEL	PRICE £ s. d.
25x RF. Generator ..	21 10 0
29x Xtal RF Gen. ..	29 10 0
30 Audio Generator ..	19 10 0
31 R.F. Generator ..	12 10 0
32 C.R. Bridge ..	10 10 0
33 Inductance Bridge ..	20 0 0

**\* DC STABILISED POWER SUPPLY**



Switched DC Stabilised Outputs UP TO 1 AMP. 3-6-9 & 12 VOLTS. Indicator lamp for each voltage. Fully fused. Mains operated. Negligible ripple. Regulation 1% SE101A £8.15.0

**QUALITY PANEL METERS**



38 SERIES  
Face Size 42 x 42mm. DC types.

50 μA	37/6
100 "	35/-
200 "	32/6
500 "	27/6
50-0-50 "	35/-
100-0-100 "	32/6
500-0-500 "	25/-
1 mA	25/-
5 "	23/-
10 "	23/-
50 "	23/-
100 "	23/-
500 "	25/-
1 Amp	25/-
5 "	25/-
10 Volts	25/-
20 "	25/-
50 "	25/-
300 "	25/-
500 "	25/-
'S' Meter 1mA	29/6
VU Meter	37/6

65 SERIES  
Face Size 86 x 78mm. DC types.

50 μA	62/6
100 "	52/6
200 "	47/6
500 "	45/-
50-0-50 "	52/6
100-0-100 "	49/6
500-0-500 "	37/6
1 mA	37/6
5 "	37/6
10 "	37/6
100 "	37/6
500 "	37/6
10 Volts	37/6
20 "	37/6
50 "	37/6
100 "	37/6
300 "	37/6
500 "	37/6
'S' Meter 1mA	42/6

85 SERIES  
Face Size 120 x 110mm. DC types.

50 μA	69/6
100 "	59/6
500 "	52/6
100-0-100 "	59/6
1 mA	49/6
100 "	49/6

Trade list on request.

**PUBLIC ADDRESS SYSTEM**



Complete system comprising Control Unit 4 Tannoy loud hailer, microphone and headphones, etc. 12V D.C. operation. Low battery drain. 8 watts power output. The ideal system for mobile use, outdoor meetings, sports days, factories, garden fetes, etc. Speakers can be spaced effectively over hundreds of yards. Also has talk back facility. Guaranteed BrandNew in sealed cartons. Original cost over £60.

**GRAVINER FIRE DETECTOR UNIT**

Fire Detector Unit containing G31A photo multiplier and cold cathode tube. Shock and fire proof. Originally made for £74. Price complete with data sheet £6 Brand new.



**STC CRYSTAL FILTER ±7.5 K/c/s BAND WIDTH**

25Kc/s Spacing. New purchase, brand new type 445 LQU 923E. 10.7 Mc/s. 6dB ± 7½Kc/s. Insertion Loss 3.5dB. Terminations 820 Ohms. Usually £12. Price £6 with Data Sheet.



**PORTABLE GEIGER COUNTERS**

FOR MEASUREMENT OF RADIO ACTIVITY Supplied complete with instructions, haversack, cables and probe. List price £70. Our price, new, tested, complete with batteries, £7.10.0 Post 10/- Plug in mains units 75/- 4 cell battery H.T. eliminator 55/- Dosimeters 0-50r 12/6. 0-150r 10/-



**HIGH CAPACITY ELECTROLYTICS**

40,000 mfd 10 volt .. 10/0  
35,000 mfd 15 volt .. 12/6  
25,000 mfd 25 volt .. 15/-  
45,000 mfd 25 volt .. 19/6  
Discounts for quantities. At a fraction of normal price. MADE BY MALLORY, USA.




**E.A.C. DIGIVISOR mk. II**

At a fraction of normal price. Moving Coil 0 to 9 Display. One inch character size. Light beam lens operated meter. Movement 500μA. Character lamp 6.3 volts. Also lamp for decimal point. Overall size: 4 1/2 x 1 1/2 x 2 1/2. Brand new. Price 79/6.



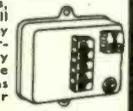**STC TIME DELAY MOOULE**

Ideal for experimenters, educational projects as well as for practical uses. Delay adjustable 3-15 sec. Operates 9-12 volts. Heavy Duty Relay Contacts. Complete with suggested applications sheet. Price 35/-, or 3 for 90/-



**ELECTRONIC COMPONENTS**

★Vast range of transistors, diodes, valves, tubes, IC's in stock. Free list No. 36, or see Catalogue A.

★Complete range of components in stock, including special and hard to get components.

If you are at all interested in Electronics then you are missing out without a copy of 'Henry's' 320-page Catalogue 'A.' Price 7/6 p.p. 2/- with 10/- value discount vouchers.

FREE To all schools, colleges etc. and all companies interested.

UK's largest stockists of Electronics for every use. Over 6500 lines in stock.

**ELECTRONIC ORGANS**

★MODERN ALL BRITISH TRANSISTORISED DESIGNS AVAILABLE AS KITS OR READY BUILT

★VENEERED CABINETS FOR ALL MODELS


★49 NOTE, 61 NOTE SINGLE MANUAL DESIGNS ALSO TWO MANUAL 49 NOTE

★KITS AVAILABLE IN SECTIONS AS REQUIRED

★H.P. AND CREDIT SALE FACILITIES

When in London call in and try for yourself.

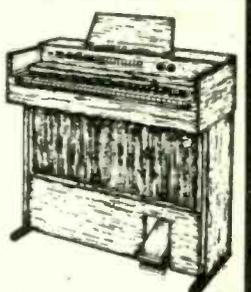FREE! 16 PAGE ORGAN BROCHURE COVERING ORGANS IN KIT FORM AND READY BUILT—WRITE OR PHONE TO ORGAN DEPT. ASK FOR PETER ELVINS.



**HI-FI equipment to suit EVERY POCKET**

Complete range always in stock with special low prices for complete systems and individual units. Two Demonstration Rooms, HP and Credit Sale facilities and plenty of free advice. New 120 page Catalogue covers every aspect, costs 5/-, p.p. 1/-, but contains 12/6 single extra discount voucher Order as catalogue 'B'—SEND TODAY.



**\* DISCOTHEQUE AND PUBLIC ADDRESS—A SPECIALITY**


**HENRY'S RADIO LTD.**

Mail Order Dept, Electronic Components and Equipment, and Electronic Organ Dept, 303 EDGWARE ROAD, LONDON W2. Telephone: 01-723 1008/9 Open Mon-Sat, 9am-6pm. Thurs, 9am-1pm

High Fidelity and Audio Centre 309 EDGWARE ROAD, LONDON W2. Telephone: 01-723 6963 Open all day Saturday.

# HENRY'S RADIO LTD. ENGLAND'S LEADING COMPONENT AND EQUIPMENT CENTRES

## NEW FOR 1970

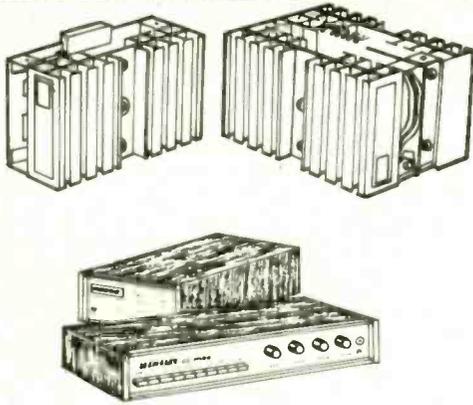

### ON DEMONSTRATION

#### \* HENELEC 'IC STEREO'

Three dual-channel integrated circuits are used in this new design by Henry's Radio, which has the unusual facility of doubling as a high quality headphone amplifier. Inputs are provided for magnetic, crystal and ceramic pickups and microphones, radio tuners, equalised tape signals, etc. Wide range tone controls and switched high and low pass filters are incorporated, and the unit has its own power supply. The silver and gold front panel, and almine teak cabinet, give an impressive appearance to this fine amplifier. **PRICE £25.0.0**

#### \* HENELEC STEREO 25-25

Comprises two PA25 amplifiers and MU442 in matching teak cabinet for direct use with above IC Stereo. **PRICE £23.0.0**

#### \* HENELEC 'PA25' POWER AMPLIFIER

This silicon design uses complementary transistors in the symmetrical output stage, direct coupled to a loudspeaker of 8 ohms impedance or higher. Power output is 25 watts RMS with an 8 ohm load or 12 watts into 15 ohms, over a frequency range of 15Hz-25Hz 3db. Cool running is assured by the use of generously dimensioned black anodised heatsinks. Input 700mV 15Kcm. **PRICE £7.10.0**

#### \* HENELEC 'PA50' POWER AMPLIFIER

Basically similar to the 'PA25', the 'PA50' will deliver 50 watts RMS to a 3-4 ohm load. Extra power is handled by complementary triplet circuits using the latest PNP and NPN silicon power transistors. As a result of extra heatsinking, the 'PA50' runs as cool as the 'PA25'. **PRICE £9.10.0**

#### \* HENELEC MU442 POWER SUPPLY

Designed to run one or two 'PA25's' or one 'PA50' the MU442 connects to the amplifiers by means of plug-on harnesses. No soldering is required to connect up the item. Audio input plug and speaker plug go to the panel of the MU442. **PRICE £6.0.0**

#### \* Mk.I 100 watts RMS with stabilised power supply overcurrent trip 100mV input sensitivity. Ideal for public address and discotheque equipment. **PRICE £49.10.0**

### THE FINEST SOLID STATE UNITS ALL SILICON BRITISH EQUIPMENT

\* SEND FOR FREE BROCHURES \*

### TRANSISTORS

FROM STOCK THE LARGEST RANGE AVAILABLE. COVERING ALL TYPES OF TRANSISTOR, INTEGRATED CIRCUITS, DIODES, RECTIFIERS, ZENERS, LIGHT DEVICES. FREE LIST No. 36 OF OVER 1,000 TYPES ON REQUEST.

### TRADE AND INDUSTRIAL ENQUIRIES INVITED

ALSO IN STOCK. TRANSDUCERS £5.18.0 PAIR WITH CIRCUITS. LARGE RANGE OF NUMICATOR TUBES AND INDICATORS. RELAYS AND COUNTERS, SOLENOIDS AND ACTUATORS—SEE CATALOGUE "A".



### GARRARD TURNTABLES

\*GOLDRING\*BSR\*THORENS


- 2025GRS25 £5.19.6
- 2025TC 9TAHC £7.19.6
- 3000LM DIAM £8.19.6
- 3500 CERAMIC £12.19.6

Cartridge Model	Less Cartridge			9TAHC Diam.			AT21 or M3DM			G850 AT21X*			AT33 Deram*			G800			J2203 800SE*			CS91E Ceramic		
	£	s	d	£	s	d	£	s	d	£	s	d	£	s	d	£	s	d	£	s	d	£	s	d
SP25 Mk II	11	9	6	13	12	6	19	0	0	16	15	0	16	10	0	21	0	0	15	10	0	19	0	0
AP75	17	15	0	19	15	0	25	10	0	23	0	0	27	0	0	27	0	0	21	17	6	25	10	0
GL75P	46	0	0	—	—	—	53	10	0	60	0	0	55	10	0	53	0	0	70	0	0	53	10	0
GL69P	35	0	0	37	0	0	42	10	0	40	0	0	44	10	0	42	0	0	39	0	0	42	0	0
MA70	12	10	0	14	10	0	20	0	0	17	12	6	—	—	—	16	10	0	20	0	0	—	—	—
AT60 Mk II	13	10	0	15	15	0	21	7	6	19	0	0	18	0	0	—	—	—	17	12	6	21	10	0
GL75	33	0	0	35	0	0	40	10	0	47	0	0	42	10	0	40	0	0	57	0	0	40	10	0
SL72B	25	0	0	27	0	0	32	10	0	30	10	0	34	10	0	34	0	0	29	0	0	32	10	0
SL75B	31	0	0	33	0	0	33	10	0	36	10	0	40	10	0	40	0	0	35	0	0	38	10	0
SL95B	39	0	0	41	0	0	46	10	0	53	10	0	48	10	0	48	0	0	43	0	0	46	10	0
SL65B	15	19	6	18	0	0	23	10	0	21	10	0	20	10	0	25	0	0	19	15	0	23	10	0
GL69	23	0	0	25	0	0	30	10	0	28	0	0	32	10	0	30	0	0	47	0	0	30	10	0


PLINTHS/COVERS DE LUXE TYPE FOR GARRARD DECKS £8.10.0 (STATE MODEL) P.P. 6/-  
\* STOCK LIST REF 16/17 FREE. 10 PAGES ALL HI-FI SPECIAL PRICES
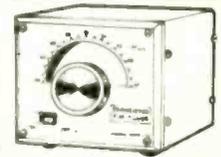
### BUILD THIS VHF FM TUNER

5 MULLARD TRANSISTORS. 300 kc/s BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. ALL PARTS SOLD SEPARATELY. **TOTAL COST £6.19.6** **DECODER £5.19.6 (FOR STEFEO)**  
ASK FOR BROCHURE No. 3


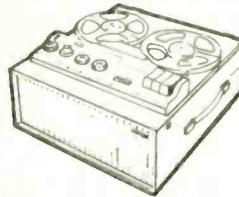
### BUILD A QUALITY 4 TRACK TAPE RECORDER



To get the best out of your MAGNAVOX DECK, you need a MARTIN RECORDAKIT. This comprises a special high quality 6 valve amplifier and pre-amplifier which comes to you assembled on its printed circuit board—in fact everything for making a superb Tape Recorder. You need no experience or technical skill to bring this about. THE INSTRUCTONS MANUAL MAKES BUILDING EASY, AND SUCCESS IS ASSURED. Kit comprises Deck, Amplifier Cabinet and speaker, with microphone, 7" 1,200 ft. tape, and spare spool. **ASK FOR BROCHURE 6 TODAY'S VALUE £60**  
**PRICE 39 gns. p. & p. 22/6 NOTHING ELSE TO BUY**

### HENELEC 5-5 STEREO AMPLIFIER

Excellent low-priced British designed Stereo Amplifier for use with Record Decks, Tuners. 16 transistor mains operated. Output 5-5 watts for 8-15 ohm speakers. Black, silver and wood finish, size 13in. X 3in. X 6in. **PRICE £13.10.0, p.p. 7.6.** (Leaflet on request.)



Complete Stereo System 5-5. Garrard 2025TC stereo, 5-5 Amplifier, Plinth/Cover. Two 10 watt speakers with tweeters in polished cabinets, size 18in. x 11in. x 7in. Usual price £49.10.0. **OUR PRICE £39.10.0, p.p. 20/- ASK FOR BROCHURE 13.**  
**OTHER SYSTEMS—ASK FOR BROCHURE 16/17.** Over 40 specially designed systems, covering all price ranges.

### AUDIO EQUIPMENT

Mono or Stereo Audio equipment developed from Dinsdale Mk. II—each unit or system will compare favourably with other professional equipment selling at much higher prices. COMPLETE SYSTEMS AND MIXERS from £11.12.6 to £38.17.6 (all units available separately).



CHOOSE FROM 25 SYSTEMS THE FINEST VALUE IN LOW-COST HIGH FIDELITY—CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE YOURSELF POUNDS. Amplifiers 7, 12 and 25 watts, two types of Stereo Preamplifier, Mono Preamps and Mixer Modules. \*SEND FOR BROCHURES No. 12/14 and 21

### INTEGRATED MICRO CIRCUITS



BP1010	3 watt Amp.	25/-
MC1304	Stereo Decoder	55/-
TAD100	AM Radio	47/6
PA237	2 watt Amp.	37/6
PA234	1 watt Amp.	20/-
PA230	Preamp.	22/6
MC1303	Stereo Preamp.	52/6

LA709C	Amp.	22/6
SL403	3 watt Amp.	49/6
TAA253	Amp.	15/-
SL702	Amplifier	29/6
µL90C	Buffer	10/-
TAD110	AM/FM Radio	59/6
CA302B	Osc/Mixer	24/6
CA302C	Dual Dar	18/6
CA302D	Amplifier	27/6
CA302E	Array	22/6
CA302F	FM	29/6

TRANSDUCERS. Type 1404 for LF communication with circuit £5.18.0 pair. Complete list and details of all integrated circuits No. 35A free on request.

### 9 AND 12 VOLT STABILISED SUPPLIES

Size approx. 3in. X 2in. X 1 1/2in. Output 100mA. Transistorised and Zener stabilised. Also unstab. output. UK made on PC with metal chassis. **PS 900 9 volt. 45/- p.p. 2/-**  
**PS1200 12 volt. 47/6 p.p. 2/-**

### HENRY'S RADIO COMPONENT/EQUIPMENT ILLUSTRATED CATALOGUE



Continually revised and enlarged. Now 350 pages of all types of components and equipment for every use. Complete with 5 2/- Discount Vouchers for purchases. \*Order as Catalogue 'A' Price 7/6, p.p. 2/-.

Why not send today! 9th edition, 6th impres.

# HENRY'S RADIO LTD.

Mail Order Dept. Electronic Components and Equipment, and Electronic Organ Dept.  
**303 EDGWARE ROAD, LONDON W2.**  
Telephone: 01-723 1008/9  
Open Mon-Sat. 9am-6pm. Thurs. 9am-1pm

High Fidelity and Audio Centre  
**309 EDGWARE ROAD, LONDON W2.**  
Telephone: 01-723 6963  
Open all day Saturday.



# R.S.C. SENSATIONAL HIGH FIDELITY STEREO 'PACKAGE' OFFERS

Matching as recommended for optimum performance. Compare prices with equipment and cabinets purchased individually.

- ★ Super 30 Amplifier (30 Watt) in veneered housing.
- ★ Goldring Transcription Turntable on Plinth.
- ★ Shure or Goldring Magnetic Pick-up Cartridge.
- ★ Pair of Stanway II Loudspeaker Units.

Special total price. Four fully wired units ready to "plug-in". Really superb performance. Send S.A.E. for leaflet. Carr. 30/-



- ★ Super 30 Amplifier (30 Watt) in veneered housing.
- ★ Garrard SP25 Mk. II Turntable on Plinth.
- ★ Goldring CS90 Ceramic diamond tipped Cartridge.
- ★ Pair of Stanway II Loudspeaker Units.

Extremely Attractive Plinths finished in Teak or Afrormosia veneer. Tinted Transparent Plastic cover.

Special total price. Four fully wired units ready to "plug-in".

**76 Gns.**  
Carr. 30/-

- ★ TA12 13W Amplifier in veneered housing.
- ★ Pair of Dorchester Loudspeaker Units.
- ★ Garrard SP25 Mk II 4-speed Player on Plinth.
- ★ Goldring CS90 Ceramic P.U. Cartridge with diamond Stylus. Special total price. **53 Gns.**

Transparent Plastic cover 3 gns. extra inc. carr. Terms Dep. £10.0.3 and 9 monthly payments £5.15.5 (Total 59 Gns.). Carr. 25/-

As above but with Garrard 3000 and Sonotone 9TA cartridge in lieu of SP25 and CS90. Special total price **47 1/2 Gns.** Carr. 25/-

## AUDIOTRINE HIGH FIDELITY LOUSPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Treated Cone surround or "D" indicates Roll Rubber surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Exceptional performance at low cost. Impedance 3 or 15 ohms.

Prices include carriage. PLEASE STATE IMPEDANCE

HF 510L 5" 10W	49/9	HF 105DL 10" 10W	£8/8/0
HF 801D 8" 8W	59/9	HF 120 12" 15W	79/9
HF 511D 8" 10W	£4/4	HF 120D 12" 15W	89/9
HF 102D 10" 10W	65/-	HF 12D 12" 15W	£5/5/-
HF 100D 10" 15W	£4/19/9	HF 12SD 12" 15W	£5/5/-

## HIGH FIDELITY LOUSPEAKER UNITS

Cabinets of latest styling Satin Teak or Afrormosia veneer. Acoustically lined or filled with acoustic damping material. Ported where appropriate. Credit terms available.

**DORCHESTER** Size 16 x 11 x 9in. Appr. Range 45-15,000 c.p.s. Rating 8-10 watts. Pitted High flux 13 x 8in. Dual cone speaker. Impedance 3 or 15 ohms. Carr. 7/6

**STANWAY II** Size 20x10x9in. approx. Rating 10 watts. Inc. Pane 13x8in. speaker with highly flexible cone surround, low throw voice coil and 11,000 line magnet. High flux tweeter. Handsome Scandinavian design cabinets. Range 35-20,000 c.p.s. Impedance 15 Ω. 16Gns. F.V.S. smooth realistic sound output. Inc. carr.

**F.A.L. "PHASE 100" AMPLIFIER** Fully Transistorised (Silicon) 100 watt Music Bating, 4 individually controlled Jack Inputs. For 3-30 ohm Speakers. S.A.E. for leaflet. **59 Gns.**

## R.S.C. TA6 6 Watt HIGH FIDELITY SOLID STATE AMPLIFIER

200-250v. A.C. mains operated Frequency Response 30-20,000 c.p.s. -2dB. Harmonic Distortion 0.3%. At 1,000 c.p.s. Separate Bass and Treble controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output rated 3-15 ohm speakers. Max. sensitivity 5mV. Output rating I.H.F.M. In fully enclosed enamelled case. approx. 9 1/2 x 2 1/2 x 9 1/2 in. Attractive brushed silver finish face plate with matching knobs. Complete kit of parts with full wiring diagrams and instructions. Or factory built with 12 months guarantee. £8.19.9.

**R.S.C. COLUMN SPEAKERS** Covered in two-tone Rexine/Vynal, ideal for vocalists and Public Address. 15 ohm matching.

**TYPE C57** 16 watt inc. five 7 x 4in. spkrs. £7/19/11.  
**TYPE C46S**, 30 watts. Fitted four 8in. high flux 8 watt speakers. Overall size approx. 42x10x5in. 18 Gns. Or deposit 87/- and 9 mthly pmt. 34/9 (Total £18/19/9). Carr. 10/-

**TYPE C412S**, 50 watts. Fitted four 12in. 11,000 lines 15 watt speakers. Overall size 36 x 14 x 9in. approx. £6 Gns. Or deposit £5/17/8 and 9 monthly payments Carr. 15/- of 54/6 (Total £20/7/-).

**High Quality LOUSPEAKERS** In Teak or Afrormosia veneered cabinets. L13 13" x 8" 10 Watt 10,000 lines, 3 or 15 ohms. Carr. 7/6. £4/19/9

L12 12" 20 Watt Model. 15 ohm. Size 18 x 16 x 10in. approx. Gauss 10,000 lines. Rexine covered 10/- £8/19/9

**FANE ULTRA HIGH POWER L'SPEAKERS** High flux ceramic magnets. Imp. 8-15 Ω. 2 yrs. guarantee.

12" 50w 10Gns.  
15" 60w 12Gns.  
18" 100w 21Gns.

All carr. price

## AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. **£5.15.0**

OR SENIOR 15 watt inc. HF 126 15,000 line Speaker £6/15. Carr. 6/6.

**HI-FI LOUSPEAKER ENCLOSURES** Teak or Afrormosia veneer finish. Modern design. Acoustically lined. All sizes approx. Prices inc. carr. JES Size 16x11x9in. Pressurised. Gives pleasing results with any 8in. Hi-Fi speaker. **£4.14.6**

SEB For optimum performance with any 8in. Hi-Fi speaker. **£5.15.0**  
SE10 For outstanding results with Hi-Fi 10in. speaker. 24 x 15 x 10in. Ported. **£5.19.9**  
SE12 For high performance with 12in. Hi-Fi speaker and Tweeter. Size 25 x 18 x 10in. Pressurised. **£6.19.9**

## THE 'YORK' HIGH FIDELITY 3'SPEAKER SYSTEM

Moderate size approx. 25 x 14 x 10 in. Range 30-20,000 Complete kit, c.p.s. Impedance 15 ohms. Performance comparable with units costing considerably more. Consists of (1) 12 in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system. (3) 8 x 5in. high flux middle range speaker (4) High efficiency tweeter. (5) Appropriate quality acoustic damping material. (6) Teak veneered cabinet. (7) Circuit and full instructions. REMARKABLE VALUE **20 Gns.**

etc. Gram, Radio or Tape. Reserve 1000 c.p.s. Separate Bass and Treble controls so that two separate inputs such as Gram and "Mike" can be mixed. 200-250 v. 50 c/s. A.C. mains. For 3 and 15 ohm speakers. Complete Kit parts wiring diag., instructions. Twin-handled perforated cover £7/8. Or factory built with EL34 output valves and 15 Gns. 12 months guarantee for 18 Gns. Tech. figs. apply to factory built units. Carr. 12/6. TERMS: Deposit £8.3.0 and 9 monthly payments of 34/- (Total £21/9/0) Send S.A.E. for leaflet.

## R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output. Pre-amp. Tone Control. Hum level -70dB. Frequency response ±3dB 30-20,000 c/s. Sectionally wound output transformer. All high grade components. Valves EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls. Sensitivity 36 millivolts. Suitable for High Impedance mic. or pick-ups. Designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions. For use with Electronic Organ, Guitar, String Bass, Piano, etc. and Hi-Fi Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram and "Mike" can be mixed. 200-250 v. 50 c/s. A.C. mains. For 3 and 15 ohm speakers. Complete Kit parts wiring diag., instructions. **15 Gns.** 12 months guarantee for 18 Gns. Tech. figs. apply to factory built units. Carr. 12/6. TERMS: Deposit £8.3.0 and 9 monthly payments of 34/- (Total £21/9/0) Send S.A.E. for leaflet.

INTEREST CHARGES REFUNDED On Credit Sales settled in 3 months.

## R.S.C. A11 HIGH FIDELITY 12-14 WATT AMPLIFIER

Push-pull ultra linear output "built-in" tone control pre-amp. Two input sockets with associated controls allowing mixing of "mik" and gram, etc. etc. High sensitivity. 5 valves - ECC83 (2), EL84 (2), EZ81. High quality sectionally wound output transformer. IND. BASS AND TREBLE CONTROLS. Frequency response ±3dB 30-20,000 c/s. Hum level -60dB. SENSITIVITY 40 millivolts. For Crystal or Ceramic P.U.s. High Impedance "mikes". For Musical Instruments such as String Bass, Electronic Guitars, etc. Complete kit **9 1/2 Gns.**

Size approx. 12 x 9 x 7in. For AC mains 200-250v. 50 c/s. Output 12-14 watts. S.A.E. for leaflet. Full instructions and point-to-point wiring diagrams. Carr. 11/6 (or factory built with 12 months guarantee for 18 Gns. Tech. figs. apply to factory built units. Deposit 9/9/6 and 9 monthly payments of 26/- (Total £16/13/6). RSC A11 transistorised version of above complete kit 9 Gns. (Assembled 13 gns.)

## W.B. 'STENTORIAN' HI-FI 10" SPEAKERS HF1012 £4.19.9

10w 3 or 15 ohms. Cambrie Cone. Cast chassis. Mail Order only

## R.S.C. TFM1 SOLID STATE VHF/FM RADIO TUNER

★ High-sensitivity. ★ 200-250v. A.C. Mains operation. ★ Sharp A.M. Selection. ★ Drift-free reception. ★ Output ample for any amplifier (approx. 600 m.v.). ★ Output for feeding Stereo Multiplexer. ★ Tuner head using silicon Planar Transistors. ★ Designed for standard 80 ohm co-axial input. Visually matching our Super 15 and 30 amplifiers. Printed circuit. A quality product at considerably less than the cost of comparable units. Factory built 18 Gns. Or in Teak finished cabinet as illustrated 21 Gns. Terms: Deposit 26/1/- and 9 monthly payments £2/2/- Total £24/19/-

STEREO VERSION 23 1/2 gns. or in Cabinet 26 1/2 gns. All prices include carriage.

# R.S.C. SUPER 30 MK II HIGH FIDELITY STEREO AMPLIFIER

HIGH GRADE COMPONENTS. SPECIFICATIONS COMPARABLE WITH UNITS COSTING CONSIDERABLY MORE

Employing Twin Printed Circuits 200/250v. A.C. mains operation. TRANSISTORS: 9 high-quality types per channel. OUTPUT: 10 Watts R.M.S. continuous into 15 Ω (Per channel) 15 Watts R.M.S. continuous into 3 Ω

INPUT SENSITIVITIES: Mag. P.U. 4 m.v. Ceramic P.U. 50 m.v. Tape Amp. 400 m.v. Aux. 100 m.v. Mic. 5 m.v. Tape Head 2.5 m.v. FREQUENCY RESPONSE: ±2dB. 10-20,000 c.p.s. TREBLE CONTROL: +17dB to -14dB at 10 Kc/s. BASS CONTROL: +17 dB to -15 dB at 50 c/s. HUM LEVEL: -80 dB. HARMONIC DISTORTION: 0.1% at 10 Watts 1,000 c.p.s. CROSS TALK: 52 dB at 1,000 c.p.s.

CONTROLS: 5-position Input Selector, Bass, Treble, Vol., Bal., Stereo/Mono Sw., Tape Monitor Sw., Mains Sw. INPUT SOCKETS: (1) P.U. (2) Tape Amp. (3) Radio (4) Mic. or Tape Head. (Operation of Input Selector assures appropriate equalisation.) CHASSIS: Strong Steel construction. Approx. 12 x 3 x 8 in. FACIA PLATE: Attractive design in rigid Perspex. Spun silver matching control knobs as available.

EMINENTLY SUITABLE FOR USE WITH ANY MAKE OF PICK-UP OR MIC. (Ceramic or Magnetic Moving Coil, Ribbon or Crystal). CURRENTLY AVAILABLE. SUPERB SOUND OUTPUT QUALITY CAN BE OBTAINED BY USE WITH FIRST-RATE ANCILLARY EQUIPMENT. COMPLETE KIT OF PARTS, point to point wiring diagrams, 22 Gns. Carr. & detailed instructions. 22 Gns. 15/-

UNIT FACTORY BUILT 29 Gns. or Deposit 27/5/- and 9 mthly. payments 58/9 (Total £33/13/9) or in Teak or Afrormosia veneer housing 32 gns. Carr. 15/- Terms: Deposit 27/3/6 and 9 mthly. payments 66/6 (Total £37/2/-) Send S.A.E. for leaflet.

32 High Street (Half-day Thurs.). Tel. 56420 LEICESTER  
5-7 County Arcade, Briggate LEEDS  
(Half-day Wed.) Tel. 28252  
73 Dale St. (Half-day Wed.). Tel. CENTRAL 3573 LIVERPOOL  
238 Edgware Road, W.2 (Half-day Thurs.). Tel. PAD 1629 LONDON  
60A Oldham Street (Half-day Wed.) Tel. CENTRAL 2778 MANCHESTER  
106 Newport Rd. (Half-day Wed.). Tel. 47096 MIDDLESBROUGH  
41 Blakett Street (opp. Fenwicks Store) (Half-day Wed.). Tel. 21469 NEWCASTLE UPON TYNE  
13 Exchange Street (Castle Market Bldgs.) SHEFFIELD (Half-day Thurs.). Tel. 20716

BRADFORD 10 North Parade (Half-day Wed.). Tel. 25349  
BLACKPOOL (Agent) O & C Electronics 227 Church St.  
BIRMINGHAM 30/31 Gt. Western Arcade. Tel. 021-236 1279. Half-day Wed. Tel. 41361  
DERBY 26 Osmaston Rd. The Spot (Half-day Wed.). Tel. 68043  
DARLINGTON 18 Priestgate (Half-day Wed.). Tel. 68043  
EDINBURGH 133 Leith St. (Half-day Wed.). Tel. Waverley 5766  
GLASGOW 326 Argyle St. (Half-day Tues.). Tel. CITY 4158  
HULL 91 Paragon Street (Half-day Thurs.). Tel. 20505

MAIL ORDERS to: 102-106 Henconner Lane, Leeds 13. No C.O.D. under £1. Terms C.W.O. or C.O.D. Postage 4/6 extra under £2. 5/9 extra under £5. Trade supplied S.A.E. with enquiries Branches open all day Sats. MAIL ORDERS MUST NOT BE SENT TO SHOPS.

## RSC TA12 MK II 13 WATT STEREO AMPLIFIER

FULLY TRANSISTORISED. SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL

Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge. Radio tuner. 3 separate switched input sockets on each channel. Separate Bass and Treble controls. Slide Switch for mono use. Speaker Output 3-15 ohms. For 200-250 v. A.C. mains. Frequency Response: 30-20,000 c.p.s. -2dB. Harmonic Distortion 0.3% at 1000 e.p.s. Hum and Noise 30,000 c.p.s. Sensitivities (1) 300 mV (2) 80 mV (3) 100 mV (4) 2 mV. Handsome brushed silver finish Facia and Knobs. Output rating I.H.F.M. Complete kit of parts with full wiring diagrams and instructions. 13 1/2 GNS. Carr. 7/9. Factory built with 12 mth. gntee. 17 GNS. Or Dep. £52/8 and 9 mthly. pymts. 34/-. (Total £20/8/6). Or in Teak or Afrormosia veneer housing 20 GNS. or Dep. £5/10/6 and 9 mthly. pymts. £2/1/7 (Total £24/4/9).

R.S.C. BATTERY/MAINS CONVERSION UNITS Type B31. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 in. approx. Completely replaces batteries supplying 1.5 v. and 90 v. where A.C. mains 200/250 v. 50 c/s. is available. Complete kit with diagram 52/8 or Ready for use 3 GNS.

R.S.C. SEMIUM RECIPIERS F.W. Bridge 6/15v. D.C. Output Input Max. 18v. A.C. 1a. 4/3; 2a. 6/11; 3a. 9/9; 4a. 12/9; 6a. 15/9.

R.S.C. MAINS TRANSFORMERS FULLY GUARANTEED. Interleaved and Impregnated. Primaries 200-250v. 50c/s. Screened MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 in. 250 v. 60 mA. 6.3 v. 2 a. 17/11 250-0-250v. 60mA. 6.3v. 2a. 18/11

FULLY SHEROUED UPRIGHT MOUNTING 350-0-350v. 60mA. 6.3v. 2a. 0-6-6.3v. 3a. 24/9 250-0-250v. 100mA. 6.3v. 4a. 0-6-6.3v. 3a. 39/9 300-0-300v. 100mA. 6.3v. 4a. 0-6-6.3v. 3a. 39/9 300-0-300v. 130mA. 6.3v. 4a. c.t. 6.3v. 1a. 47/11 For Mullard 510 Amplifier 350-0-350v. 100mA. 6.3v. 4a. 0-6-6.3v. 3a. 39/9 350-0-350v. 150mA. 6.3v. 2a. 0-6-6.3v. 3a. 47/9 425-0-425v. 200mA. 6.3v. 4a. c.t. 5v. 3a. 89/9 425-0-425v. 200mA. 6.3v. 4a. c.t. 6.3v. 3a. 93/9 450-0-450v. 250mA. 6.3v. 4a. c.t. 5v. 3a. 99/9

TOP SHEROUED DROP-THROUGH TYPE 250-0-250v. 70mA. 6.3v. 2a. 0-6-6.3v. 2a. 23/9 250-0-250v. 100mA. 6.3v. 3.5a. 27/9 250-0-250v. 100mA. 6.3v. 2a. 0-6-6.3v. 2a. 28/9 250-0-250v. 80mA. 6.3v. 2a. 0-6-6.3v. 2a. 29/11 250-0-250v. 100mA. 6.3v. 4a. 0-6-6.3v. 3a. 39/9 300-0-300v. 100mA. 6.3v. 4a. 0-6-6.3v. 3a. 39/9 300-0-300v. 130mA. 6.3v. 4a. 0-6-6.3v. 1a. 47/11 Suitable for Mullard 510 Amplifier 350-0-350v. 100mA. 6.3v. 4a. 0-6-6.3v. 3a. 39/9 350-0-350v. 150mA. 6.3v. 4a. 0-6-6.3v. 3a. 48/11 FILAMENT or TRANSISTOR POWER PACK Types 6.3 v. 1.5a. 8/9; 6.3v. 2a. 9/9; 6.3v. 3a. 13/9; 6.3v. 6a. 22/9; 12v. 1a. 9/11; 12v. 3a. or 24v. 1.5a. 23/9; 0-18-18v. 1 1/2a. (or 12v. 1 1/2a.) 0-12-25-42v. 2a. 31/9

CHARGER TRANSFORMERS 0-15v. 1.5a. 19/9; 0-15v. 2.1A. 21/11; 0-25v. 1.5a. 29/9; AUTO STEP UP STEP DOWN TRANSFORMERS 0-110/120v. 200-230-250v. 60-80 watts 19/9 180 watts 33/6; 250 watts 49/9; 600 watts 105/-

OUTPUT TRANSFORMERS Standard Pentode 5,000 Ω or 7,000 Ω to 3 Ω 8/9 Push-Pull 7 watts EL84 to 3 Ω or 15 Ω 14/9 Push-Pull 10 watts 6V6 ECL86 to 3, 5, 8 or 15 Ω 24/9 Push-Pull EL84 to 3 or 15 Ω 10-12 watts 23/9 Push-Pull Ultra Linear for Mullard 510, etc. 39/9 Push-Pull 15-18 watts sectionally wound 6L6 35/9

K766, etc. for 3 or 15 Ω. Push-Pull 20 watt high quality sectionally wound EL34, 6L6, K766, etc. to 3 or 15 Ω 59/9

SMOOTHING CHOKES 150mA. 7-10 Ω. 250 Ω 12/9; 100mA. 10 Ω. 200 Ω 10/9; 80mA. 10 Ω. 350 Ω. 8/9; 60mA. 10 Ω. 400 Ω 4/11.

R.S.C. PLINTHS for Record Playing units. Cut for Garrard 1025 2025 3000 AT60 SP25 etc. etc. Available with Transparent plastic cover. Price inc. carr. **6 Gns.**

Record Playing Units MONEY SAVING UNITS Ready to plug into Amplifier. RP2C Consisting of Garrard SP25 Mk. II (with heavy turntable fitted Goldring CS90 high compliance ceramic Stereo/Mono cartridge with diamond stylus. Mounted on plinth. Transparent plastic cover included. 23 Gns. Inc. carr.

RP5C Garrard 2025 Auto Unit fitted with GC923 Stereo Cartridge with diamond tip. Plinth and cover as RP2C. Inc. Carr. **15 Gns.**

Various other types with Magnetic P.U. Cartridges and "Lift off" or "Roll over" transparent covers at lowest prices.

FANE 'POP' 30C LOUSPEAKER 12" 25 w 15 Ω Dual cone Post Free **£5.19.9**



# BETTER BARGAINS SERVICE FROM T.R.S.

## Amplifier Kits

Styled and kitted by T.R.S., using quality components, including valves or transistors and excellent instructions. Backed by T.R.S. service.

**MULLARD 5-10.** Mono. Basic kit (requires pre-amp as below or passive controls £2 extra.) Input Sensitivity—40 mV; Resoonse 20Hz-15KHz + 1dB; Output 10 watts R.M.S. at 3 or 15 ohms. **KIT** £10.10.0; **BUILT** £13.0.0 (Carr. either, 7/6).

**MULLARD 2-VALVE PRE-AMP** with switching for 5 inputs; bass/treble/volume controls, etc. Sensitivity at Input—4mV max. to 330 mV into 80K-1 Megohm; Response 20-25,000 Hz + 1dB. **KIT** £6.19.6; **BUILT** £9.10.0 (Carr. either, 5/6).

**MULLARD 10-10 STEREO AMPLIFIER.** Input sensitivity—210 mV per ch.; Response 12 Hz—35KHz + 3dB; 10 watts R.M.S. output per channel into 3 or 15 ohms. **KIT** £18.10.0; **BUILT** £22.10.0 (Carr. either, 12/6).


As above, less controls and panel. **Kit** £17.0.0; **Built** £21.0.0 (2+2 pre-amp. essential). **2+2 STEREO PRE-AMP** similar to Mullard 2-valve pre-amp, but doubled with gang controls and balance. **BUILT** £13.19.6 (Carr. 7/6).

**T.R.S. 4+4 STEREO AMP**  
Low cost transistor amplifier based on Mullard modules. 4+4 watts output. For 8-15 ohms speakers. Input switching, etc. Bass and treble controls. Simple module assembly. Amp and pre-amp with front panel and knobs. **Kit** £7.19.6 (Carr. 3/6); **Teak sided cabinet** £11.7.6 (Carr. 2/6); **24V. Power pack** £2.5.0 (Carr. 2/6); **Complete kit inc. DIN plugs and sockets** £12.10.0 (Carr. 7/6).
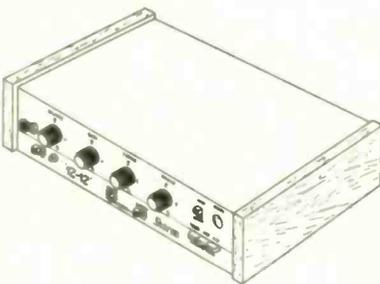
## THE NEW T.R.S. P.W. 12-12

T.R.S. have produced their own kit version of this outstandingly good combined stereo amp and pre-amp. It conforms closely to Practical Wireless's excellent circuit but is styled for a flatter, more conventional cabinet which will be shortly available. Kit includes two-tone front panel and control knobs.

Inputs—Mag. P.U. (R.I.A.A.) 2.5mV Into 68 Kohms; Ceramic—Radio: Response—20Hz to 30KHz + 1dB. Output—12 watts per ch. R.M.S. Into 15 ohms.



Complete Kit of parts less cabinet (carr. 7/6) **£24.10**

Power/Amp/Pre-amp Kits available separately.

**VINAIR**—Latest I.C.I. Cabinet and Speaker covering. Mottled Light-Grey, Off-White, Fawn, Black, etc., 2/6 per sq. ft. Multiples of 6 in. cut. 27/6 per yd. Maximum width 48 in.

Send 1/- for Samples—Refundable. **BONDACOUST**—Speaker Cabinet Acoustic Wadding (as used by leading Hi-Fi Speaker mfrs.), 18 ins. wide. Any length cut 2/6 per ft.; 7/- per yard

**ENAMELLED COPPER WIRE**

New 2 oz. reel prices  
14g—20g, 3/1; 22g—28g, 3/6; 30g—34g, 4/3; 36g—38g, 4/9; 39g—40g, 5/-

Other gauges quoted for.

**TINNED COPPER WIRE**

16g—22g 4/6 per 2 oz.  
**EXCLUSIVE T.R. TAPE BARGAIN**

Professional quality full frequency Mylar Tape by famous mfr. Attractively presented in coloured simulated leather wallets with space for spare reel.

5 in. 900 ft. 12/6 5 1/2 in. 1200 ft. 17/6  
7 in. 1200 ft. 17/6 7 in. 1800 ft. 22/6  
Post and packing 1/6 per reel, plus 6d. each for extra reels.

**VEROBOARD**—All standard sizes stocked.

2 1/2 x 3 1/2, 3/-; 2 1/2 x 5, 3/8; 3 1/2 x 3 1/2, 3/9; 3 1/2 x 5, 5/2; 1 7/8 x 2 1/2, 12/6; 1 7/8 x 3 1/2, 15/-

Accessories—Term Pins, 1/- doz., 3/- pkt. Face Cutter, 7/3. Pin inserting tool 9/6  
"CIR-KIT"—Adhesive copper strip 5 ft. by 1/16 in. spool 2/-

## PLUGS AND SOCKETS

Phono plugs, 1/-; sockets, 1/-, twin, 1/6  
DIN 5-pin plugs, 3/-; 5-pin sockets, 1/6;  
3-pin plugs, 3/3; 3-pin sockets, 1/6.

## VOLUME CONTROLS

1 1/2 in. dia. Long Spindles. Famous make. All values 5000 ohms-2 Megohms. Guaranteed 12 months.

Log or Linear tracks.  
Less Sw. 3/6; DP Sw. 5/-  
1 Megohm With DP Sw. Each 10/6

**STEREO BALANCE CONTROLS**  
Log/Anti-Log 5K, 10K, 1 Meg, 1 Meg, 2 Meg. Each 9/6

**RESISTORS**  
Full Range 10 ohms-10 Megohms. (Midget type, modern ratings.)

10% 1w, 1w, 4d.; 1w, 6d.  
20% 1w, 8d.; 2w, 1/-  
5% Hi Stab (Cracked Carbon) all pref. values.

10 ohms-1 Meg. 1w, 6d.; 1w, 6d.  
ditto 1 1/2 Meg-10 Meg.  
10% 1w, 8d.; 1w, 6d.

1% Hi Stab 1w, 2/- (10 ohms-100 ohms, 2/3).

**SKELETON PRE-SETS** for P/circuit use. 100 ohms-2.5 Meg., 2/-.

## GRAMO UNITS, PLINTHS, ETC.

**GARRARD SP.25 Mk. II**  
10 1/2 in. die-cast t/table, cueing device and counterbalance. Less cartridge. In maker's carton £12.7.6 (Carr. 7/6)

**GARRARD LM.2025**  
With latest stereo cartridge and lift control £10.19.6 (Carr. 7/6)

**PLINTHS**  
Garrard WB.1 £3.15.0 (Carr. 5/-)

**SINCLAIR PRODUCTS AS ADVERTISED**

Also T.R.S. 6-valve AM/FM Tuner Kit, £12.10.0 (Carr. 7/6); T.R.S. FM Transistor Tuner, parts £15.15.0 (Carr. 7/6).

Garrard Clearview Cover SCP.1 £3.10.0 (Carr. 4/6)  
Garrard Scandinavian type plinth and cover £5.5.0 (Carr. 5/-)

**CARTRIDGES**  
When bought together with playing units: Decca Deram, £5.5.0; BSR TCB/H (Stereo compatible), 25/-; BSR Stereo TC.85, 28/6; Sonotone 9TA/H/C, with diamond 60/-; Acos GP.93-1, 30/-.

**T.R.S. FOR TRANSFORMERS.** Mains and output supplied to spec, for single or short production runs. Also comprehensive service in replacement line O/P transformers. Enquiries Invited. S.A.E. from private individuals please.

# T.R.S. RADIO COMPONENT SPECIALISTS

70 BRIGSTOCK RD., THORNTON HEATH, SURREY

Open Saturday all day. Wednesday 1 p.m.

Next to Thornton Heath Station (S.R.)

Phone: 01-684 2188

## A NEW ADDITION TO THE RANGE



## Miniature P.T.F.E. Tubular Capacitors

Oxley Developments Company Limited have introduced a new and improved range of miniature P.T.F.E. Tubular Trimmer Capacitors with capacitance swings from 5 to 30pF; TU/30/PC1, for horizontal mounting on printed circuit boards, as illustrated.

This range of components uses P.T.F.E. as the dielectric medium, resulting in a power factor of less than 5.10<sup>-4</sup> at 10kHz, and the patented concentric design ensures uniformly smooth adjustment with linear, reversal-free tuning and temperature coefficient of 50 ppm/°C.

Please contact our Sales Department for the technical data sheet.

OXLEY DEVELOPMENTS COMPANY LIMITED  
Priory Park, ULVERSTON, North Lancs.  
Telephone ULVERSTON 2621. Telex 6541



WW—117 FOR FURTHER DETAILS

# Kinver for Components

## LINEAR INTEGRATED CIRCUITS

High Performance operational Amplifiers  
Texas Type SN72709N 21/-each  
This device is electrically similar to MIC709, MC709C, UA709C, N5709A, etc., supplied complete with specification sheet.

Also in stock:	CA3012	26/3	TAA293	21/8	
PA234	23/-	CA3020	27/6	TAA310	32/-
PA237	34/-	CA3028A	20/-	TAA320	13/5
CA3000	54/9	CA3028B	37/6	SL403A	49/6 net
CA3001	79/6	CA3029	26/3	IC-10	59/6 net
CA3011	20/-	CA3035	30/-	O13T1	10/8
		TAA231	56/8	2N5306	11/6

Add 1/- to the above i.c.s. for data sheets if required (1/9 with SL403A, free with IC-10). Other data sheets (apart from IC-10) may be purchased separately at 1/6 per sheet, post free.

## 1 WATT AMPLIFIER MODULE TYPE PCM1

This amplifier unit is a printed circuit module incorporating the popular and well tried PA234 i.c. amplifier. The unit is a complete AUOIO AMPLIFIER and requires no external components, you simply connect an 18 volt power supply and a 15 or 16 ohm speaker or head phone, even the supply smoothing capacitor and the output capacitor are included! The overall dimensions, including capacitors, are 2 1/2" x 3" x 1 1/2". The input for 1 watt output at 1 kHz is typically 300mV into 100 kohms. This unit is available at only 36/- net, complete with descriptive leaflet or 70/- net per pair. Send for free leaflet.

## SILICON TRANSISTORS FOR HIGH QUALITY EQUIPMENT

BC107	3/3	BD125	24/3	TIP32A	23/-	2N3055	15/9
BC108	3/3	BDY20	24/3	TIS44	1/9	2N3702	3/6
BC109	3/3	BF184	7/6	TIS49	2/6	2N3703	3/3
BC158	7/6	BF194	7/-	TIS50	2/6	2N3704	3/9
BC182L	2/2	BFX29	10/4	2N696	4/9	2N3705	3/4
BC183L	2/5	BFXB4	6/8	2N697	5/-	2N3707	4/-
BC184L	3/2	BFX85	8/8	2N706	3/3	2N3708	2/5
BC121L	3/9	BFY50	5/-	2N1132	10/9	2N3819	9/-
BC213L	3/9	BFY51	4/6	2N2908	13/-	2N3820	18/9
BC214L	4/-	BFY52	5/-	2N2924	4/4	2N3826	5/11
BCY70	5/4	BSY95A	3/11	2N2925	5/3	2N4058	4/6
BCY71	10/4	MJ481	27/3	2N2926	3/-	2N4059	3/5
BCY72	4/6	MJ491	32/11	2N3053	6/8	2N5457	9/9
BD121	17/3	TIP31A	17/-				

## COMPONENTS CATALOGUE—2/- post free (inland)

P & P 1/6 inland, overseas at cost (min. 10/-)

Cash with order please. discounts may be deducted as follows: order over £5—10%; order over £10—15%. Trade orders—net 30 days.

Please send SAE with enquiries. CALLERS WELCOME  
Open 9.00 a.m.—12.50 p.m. 2.00 p.m.—5.00 p.m. Weekdays  
Saturday Mornings 9.00 a.m.—12.50 p.m.



STONE LANE KINVER  
STOURBRIDGE WORCS  
Telephone: KINVER 2099

WW—118 FOR FURTHER DETAILS

# New 1970 prices L.S.T. Electronic Components Ltd.

AC107	14/6	BD119	15/-	NKT123	6/-	OC72	4/6	2G306	8/6	2N3133	6/-	2S003	12/6
AC126	5/6	BD121	18/-	NKT125	5/6	OC75	4/6	2G319A	5/-	2N3135	6/-	2S004	15/-
AC127	5/6	BD124	21/6	NKT127	5/6	OC76	2/6	2G371	3/-	2N3136	6/-	2S005	15/-
AC128	4/-	BF115	5/-	NKT128	5/6	OC77	5/6	2G371B	3/-	2N3235	28/6	2S006	15/-
AC176	5/-	BF152	13/6	NKT129	6/-	OC81	4/6	2G374	5/-	2N3234	27/6	2S012	25/-
AC187	12/-	BF154	9/-	NKT141	7/-	OC81D	3/-	2G378	7/-	2N3391A	6/-	2S012A	22/6
AC188	12/-	BF159	9/-	NKT142	6/-	OC82	5/-	2G381	5/-	2N3392	5/-	2S017	15/-
AC177	5/-	BF163	15/-	NKT144	8/-	OC82D	11/6	2N109	3/-	2N3393	5/-	2S018	17/6
AC18	3/6	BF167	5/-	NKT152	3/6	OC83	3/6	2N174	16/-	2N3394	4/9	2S019	19/6
AC19	4/6	BF173	6/-	NKT161	6/-	OC84	5/-	2N217	7/6	2N3402	5/6	2S104	12/6
AC20	3/7	BF178	10/6	NKT162	6/-	OC123	7/-	2N370	15/-	2N3403	5/6	2S201	8/6
AC21	4/-	BF179	12/6	NKT163	5/6	OC139	5/-	2N384	17/-	2N3404	7/6	2S202	7/6
AC22	2/9	BF180	6/-	NKT164	5/6	OC140	7/-	2N386	12/-	2N3414	5/6	2S203	10/6
AC24	3/6	BF181	6/-	NKT165	6/-	OC170	5/-	2N385A	12/-	2N3415	6/-	2S204	12/6
AC41	4/4	BF184	7/-	NKT211	6/-	OC171	6/-	2N388A	15/-	2N3416	7/6	2S206	15/-
AC44	8/-	BF185	8/-	NKT212	6/-	OC200	6/3	2N404	4/6	2N3436	15/3	2S209	9/-
AD140	11/6	BF194	3/6	NKT213	4/4	OC201	9/6	2N410	8/-	2N3525	21/9	2S231	6/-
AD149	11/6	BF200	10/6	NKT214	4/4	OC202	18/-	2N458A	25/-	2N3528	19/-	2S232	10/6
AD161	6/-	BFX13	5/-	NKT215	4/4	OC203	7/6	2N511A	49/6	2N3606	5/6	2S271	8/6
AD162	6/-	BFX29	8/-	NKT216	10/6	OC204	8/-	2N513A	122/6	2N3607	4/6	2S273	12/6
ADT140	12/6	BFX44	8/-	NKT217	13/6	OC205	9/-	2N599	10/6	2N3702	3/3	2S270	25/-
AF102	12/6	BFX84	7/6	NKT218	5/3	OC206	10/6	2N601	25/6	2N3703	3/3	2S272	8/6
AF106	7/6	BFX85	6/-	NKT219	6/-	OC207	7/6	2N657	20/6	2N3704	3/3	2S1002	10/-
AF114	5/-	BFX86	6/-	NKT221	5/6	OC309	12/-	2N696	4/-	2N3705	3/3		
AF116	5/-	BFX90	6/-	NKT222	5/6	OC371	19/6	2N697	4/-	2N3707	3/3		
AF117	5/-	BFY50	6/-	NKT223	3/6	ORP12	9/6	2N698	6/-	2N3708	2/-		
AF118	12/6	BFY52	4/6	NKT224	4/6	ORP60	8/-	2N706	2/6	2N3709	2/-	AA119	2/-
AF121	6/-	BFY53	3/2	NKT225	3/6	ORP61	8/-	2N706A	2/6	2N3710	3/-	AA119	2/-
AF124	4/6	BFW57	5/6	NKT226	10/6	ORP63	9/-	2N708	4/-	2N3711	3/-	AA112	2/6
AF125	3/6	BFW70	5/6	NKT227	5/6	P346A	5/-	2N711	7/6	2N3711	3/-	AA112	2/6
AF127	3/6	BFW59	5/6	NKT228	6/-	RAS310AF	6/-	2N711A	7/6	2N3820	18/9	BA110	6/-
AF139	7/6	BFX10	4/6	NKT261	4/3	RAS50BAF	6/-	2N715	7/6	2N3826	6/6	BA111	6/-
AF178	9/6	BSW19	3/6	NKT262	4/3	S1M	15/-	2N743	4/6	2N3854	5/6	BA112	18/-
AF179	11/6	BSX20	3/4	NKT264	4/3	S4M	33/6	2N744	6/-	2N3854A	5/6	BA115	1/6
AF180	12/6	BSX21	7/6	NKT271	4/4	ST140	3/-	2N753	5/6	2N3855	5/6	BA130	3/-
AF186V	9/-	BSX78	6/6	NKT272	4/4	ST141	5/-	2N914	4/6	2N3856	6/-	BA131	2/6
AF186G	9/-	BSX78	6/6	NKT273	4/4	ST2	9/9	2N929	5/6	2N3856A	6/-	BY100	5/-
AF239	7/6	BSY27	4/6	NKT274	4/4	ST2	9/9	2N930	7/6	2N3858	5/-	BY125	3/6
AFY19	22/6	BSY29	5/-	NKT275	5/-	T1407	9/8	2N930	7/6	2N3858A	6/-	BY127	3/6
AFZ11	8/6	BSY32	5/-	NKT276	3/6	T1534	17/6	2N1090	6/6	2N3858A	6/-	BY142	5/9
ASV26	5/-	BSY36	5/-	NKT277A	2/6	T1543	6/6	2N1091	6/6	2N3859	5/6	BY110	3/3
ASV27	6/-	BSY37	5/-	NKT278	4/4	T1544	1/8	2N1131	6/6	2N3859A	6/3	BYX10	3/3
ASV28	5/-	BSY38	5/-	NKT301	16/-	T1545	3/3	2N1132	8/-	2N3860	6/-	BYX36	2/6
ASV29	6/-	BSY38	5/-	NKT302	11/-	T1546	3/3	2N1302	4/-	2N3866	25/-	150	2/6
ASZ21	7/6	BSW41	8/6	NKT303	10/6	T1547	3/3	2N1303	4/-	2N3877	9/6	BYX36	2/10
AT110	40/-	BSW42	8/6	NKT304	9/6	T1548	3/3	2N1304	5/-	2N3877A	9/6	300	3/9
AUY10	30/-	BTX39	8/6	NKT351	8/6	T1549	3/6	2N1305	5/-	2N3900	10/6	BYX36	3/9
B2M	12/6	600	120/-	NKT352	7/6	T1550	3/6	2N1305A	5/-	2N3900A	11/6	600	3/9
B3M	15/-	BTX40	120/-	NKT401	17/6	T1551	4/-	2N1307	5/-	2N3903	7/-	BY21	25/-
BC107	2/9	600	120/-	NKT402	24/-	T1552	4/-	2N1308	7/-	2N3904	7/-	BY22	26/3
BC108	2/9	BTY87	31/-	NKT403	15/-	T1553	6/6	2N1309	7/-	2N3905	7/6	BY225	31/9
BC109	3/6	BS98	15/-	NKT404	12/6	T1560	6/6	2N1496	3/4	2N3906	7/6	BY210	9/-
BC113	5/-	C106F1	9/-	NKT405	15/-	T1561	7/-	2N1507	28/-	2N3907	4/6	BY212	6/-
BC115	6/6	C111	18/-	NKT451	12/6	TIP31A	22/6	2N1613	3/6	2N4058	4/6	BY213	5/-
BC116	8/-	C111E	12/-	NKT452	12/6	TIP32A	22/6	2N1711A	29/6	2N4059	5/-	CG6	4/-
BC118	5/-	C400	12/-	NKT453	10/-	U23AAA	5/-	2N1711	6/6	2N4061	4/-	CG61	2/-
BC125	11/6	C426	8/3	NKT674F	5/-	V205	20/-	2N2147	17/-	2N4062	4/6	CG13	3/6
BC134	5/-	D13T1	10/-	NKT675	5/-	V405A	9/2	2N2152	27/6	2N4284	3/-	EC402	4/6
BC135	6/-	GET102	6/-	NKT676	5/-	XA102	6/-	2N2148	12/6	2N4286	3/-	EB383	3/6
BC136	8/-	GET113	6/-	NKT677	5/-	XA702	15/-	2N2160	14/9	2N4287	3/-	GEX45/1	4/6
BC137	8/6	GET114	4/-	NKT703	8/-	ZE12V7	3/6	2N2243	26/-	2N4288	3/-	G33M	4/-
BC138	12/-	GET120	5/6	NKT713	7/6	ZT22	19/-	2N2368	5/-	2N4289	3/-	OAS	3/8
BC140	3/3	GET880	9/-	NKT773	5/-	ZT220	19/8	2N2369	5/-	2N4290	3/-	OA10	6/-
BC147	2/9	GET887	4/-	NKT10339	40250	12/6	2N2369A	5/6	2N4291	3/-	OA47	1/6	
BC148	3/3	GET889	6/-	40309	9/6	2N2432	6/7	2N4292	3/-	OA70	1/6		
BC149	3/3	GET890	6/6	40310	13/-	2N2484	8/6	2N4293	6/9	OA73	1/6		
BC154	12/-	GET896	4/6	40311	10/6	2N2613	7/6	2N5027	10/6	OA79	1/6		
BC167	3/6	GET898	4/6	40312	13/6	2N2644	10/-	2N5029	11/6	OA81	1/6		
BC168	3/9	GET898	6/-	40314	10/6	2N2646	10/-	2N5029	9/6	OA85	1/6		
BC169	3/9	GEX45/1	3/-	40315	10/6	2N2711	6/-	2N5030	8/6	OA90	1/6		
BC182L	3/6	MAT100	5/-	40316	13/-	2N2712	6/-	2N5172	3/-	OA91	1/6		
BC183L	2/6	MAT101	3/6	40317	11/-	2N2713	5/6	2N5174	10/6	OA95	1/6		
BC184L	3/6	MAT120	5/-	40319	15/-	2N2904	8/6	2N5175	10/6	OA200	2/-		
BC212L	3/9	MAT121	5/6	40320	10/6	2N2904A	8/-	2N5176	9/-	OA202	2/-		
BCY10	10/6	MJ400	21/6	40323	10/6	2N2905	10/-	2N5232	5/6	SD19	-7		
BCY12	12/6	MJ420	22/6	40324	12/6	2N2905A	8/-	2N5249	13/6	TD716	12/-		
BCY30	5/6	MJ421	22/6	40326	10/6	40326	10/6	2N5249A	13/6	IN34A	4/-		
BCY31	5/6	MJ430	20/6	40329	7/6	40329	7/6	2N5305	7/6	IN64	4/-		
BCY32	10/6	MJ440	19/6	40344	8/-	40344	8/-	2N5306	8/-	IN64	4/-		
BCY33	4/-	MJ480	20/6	40347	9/6	2N2926	2/-	2N5309	12/6	IN82A	9/6		
BCY34	5/-	MJ481	27/6	40348	6/6	Green	2/-	2N5354	3/6	IN87A	9/6		
BCY38	6/-	MJ490	22/6	40360	11/6	2N2926	2/-	2N5355	3/6	IN191	5/-		
BCY40	10/6	MJ491	29/6	40361	12/-	Yellow	2/-	2N5356	10/6	IN194	1/9		
BCY42	4/-	MPF102	8/6	40362	14/-	2N2926	2/-	3N84	29/6	IN4001	2/-		
BCY54	7/6	MPF103	7/6	40370	8/6	Orange	2/-	3N128	18/6	IN4005	4/-		
BCY57	4/-	MPF105	8/-	40406	4/6	40406	4/6	3N140	19/6	IN4007	5/-		
BCY71	8/-	MPS3638	6/6	40408	4/6	40408	4/6	3N141	21/6	IN4148	1/9		
BCY72	4/-	NKT0013	9/6	40467	16/6	2N3011	12/6	3N142	16/6	IS44	1/9		
BCZ11	86/9	NKT121	8/-	40468A	16/6	2N3036	39/-	3N143	19/6	IS130	2/-		
		NKT122	8/-	40602	9/-	2G303	3/9	3N152	24/-	IS131	2/6		
				40603	9/-	2G304	3/9	2N3054	12/6	IS132	3/6		
				40604	9/-	2G305	3/9	2N3055	15/-	IS133	3/6		
				40605	9/-	2G302	3/9	2N3055	15/-	IS133	3/6		

## LOWEST I.C. PRICES YET!

IC10	59/6	Sinclair IC amp.
PA230	20/-	IC Preamplifier
PA234	20/-	1 watt audio amp.
PA237	32/6	2 watt audio amp.
PA246	52/6	5 watt audio amp.
PA424	43/-	Zero voltage switch
SL403A	49/6	3 watt Plessey amp.
TAA263	15/-	Mullard linear amp.
TAD100	45/-	IC receiver
TAA293	20/-	Mullard gen. purp. amp.
TAA310	30/-	Record/Playback preamp.
TAA320	13/-	MOS LF amplifier
UL702C	29/6	Plessey linear amplifier

Data sheets available on request 1/- per copy.

**PLEASE NOTE:** Only new—full specification integrated circuits, no below-specification types.

### FAIRCHILD MICRO-LOGIC

ul 900	1-6	7-11	12+
ul 914	9/9	9/-	8/-
ul 923	12/6	11/9	11/-

Prices for 100+ and 1,000+ on application. 5 page data and circuits article—2/6. Plastic spreaders—1/6 each.



### ULTRASONIC TRANSDUCERS

Operate at 40

# ELECTRONIC BROKERS

## MEASURING INSTRUMENTS AND RECORDERS

### NEW

**6 Pen Event Recorder,**  
6 in. Chart width. Available in wide range of chart speeds. Rack mounted £79/10/0. Case to suit extra.

### VOLTMETER—Solartron VM 1484

Very suitable for the measurement of distorted or complex signals, noise or pulse voltages, employs thermocouples in a self-compensating bridge circuit. Reads true RMS values. Highest factors. Output up to 1 volt in available as a drive source for a DV3. Frequency range 10 Hz - 10 MHz. Accuracy 1% of F.S.D. Sensitivity 1 millivolt - 300 volts. Dimensions H. 8 1/2 in., W. 5 1/2 in., L. 13 in. £150. Carr. extra.



### PORTABLE AC/DC PEN RECORDER

A most versatile pen recorder. Produces a trace on a curvilinear 3 1/2 in. strip chart. Two speeds 1 in. and 6 in./hr. Limiting contacts to give alarm, and limits the current when it exceeds the high and/or low preset values. Range: 0 - 1MA D.C. Meter Resistance 400 ohms; 0 - 1MA A.C. Meter Resistance 1800 at 50 Hz; -10 to +5 dB into 600 Ω Impedance Source. Power supply: 230/250 Hz. driving Synchronous Motor.

Price: £52.10.0. Postage and packing £1 5s. 0d.

### STRIP-CHART INDICATING RECORDER

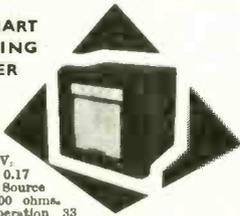



Chart width 9 1/2 in. 10 mV. Sensitivity ± 0.17 of full scale. Source impedance 100 ohms. Speed of operation 33 sec. for full-scale travel. Chart speed 1/2 in. 3 in. 6 in. per hour. Single point. £49.10.0. P. & P. 30/-.

### NEW PORTABLE RECORDING AMMETER




Specification. Type: Moving Coil. D.C. Range: 0-5 amp. D.C. Chart Width: 100 mm. Scale Length: 127 mm. Chart Speeds: 20, 60, 180, 600, 1800 and 5400 mm/hr. Dimensions: 180h x 163 w x 245mm. Weight: 5.5kg. List price £65. Our price £35.

### PEN RECORDER

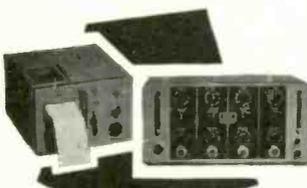

Portable 1, 2 and 4 channel pen recorders by Kelvin Hughes. General purpose recorders providing clear instantaneous and permanent records of phenomena with comparatively high rates of change. The torsion-strip suspension of the moving-coil renders the instrument immune to the effects of vibration and acceleration. Six possible chart speeds, chart width 55 mm. length 150 ft. linearity 8 v. at 3 mA. response D.C. to 100 c/s. Single pen with amplifier £99; 2 pen recorder £85, 4 pen with amplifier £149. Also 5 pen recorder complete with amplifiers, specification as above but housed in cabinet £225. P. & P. extra.

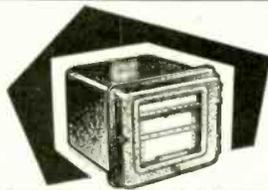


### POTENTIOMETRIC 6 POINT STRIP CHART RECORDER BRAND NEW

For use with thermocouples, pyrometers and other e.m.f. sources. 6 point. Range (-100) - 0 - (+100) mV; 0 - 1600 deg. C. 6 1/2 in. chart width; pen speed 8 secs. Accuracy ± 0.5%; 10 chart speeds 20-720mm/hr. Tropicalised. Including tools and spares. Listed at over £200. Our price £79.10.0. Also available 0-100mV F.S.D. £88.10.0.

## POWER SUPPLIES
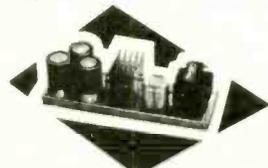
### UNUSED MINIATURE MILLION MAGNETIC STORAGE DRUM

Type N.S. 1389 16 write and 16 read heads 256 tracks magnetic storage drum. Each track at 600 r.p.m. Holds 1024 bits (32 words of 32 bits). Total storage 250,000 bits. Suitable for many data storage problems. 8" high, 10" dia., 2 1/2" base. £280. carr. extra.



### ADVANCE TRANSISTORISED DC POWER UNITS

	Input Volts	Output Volts	Amps	Price
DC 4	200-245 ± 15%	12	4	£14.10.0
DC 6	230-245 ± 15%	24	5	£17.10.0
DC 8	230-245 ± 15%	48	4	£19.10.0

## METERS



### DIGITAL VOLTMETERS

DM2023 digital voltmeter and ratiometer, accurate to 0.0025% offering exceptional linearity. Reading rate of 50 per second. Outputs: Parallel B.C.D. scale 39999. Inputs: 25000MΩ CMR 160dB on d.c. Range 10<sup>-4</sup>V to 2KV. This is a rare opportunity to obtain such an instrument at such a low price of £350. Carriage free. DM2006. An all solid state D.V.M. having a wide application. Scale 9999. D.C. accuracy 0.017%.s.d. with a D.C. range of 10<sup>-4</sup>V to 1KV. Input impedance 10000MΩ. C.M.R. 154dB. Outputs parallel B.C.D. £245. Carriage free. DM2023. This D.V.M. is suitable for data-logging due to the high C.M.R. 170dB. It has six operating modes. Accurate to 0.001% and complete with plug in units to give either manual or automatic ranging from 10<sup>-4</sup>V to 1KV with a 10MΩ input impedance. £480. Carriage free. All the above units have been calibrated. Digital Voltmeters 2003 A.C./D.C. D.C. range 1mV - 1KV. 4 Digits. £135. Type 2025. Scale 19,999. Accuracy 0.05%. Range 10 micro volts - 2 Kilo Volts. Input Z greater than 25,000 megohms. CMR 160 d.B. Price new £660. Our price £285. Carr. extra.

2 in. dia. mounting A.C. voltmeter 0-300 V. A.C. £1.15.0. Carriage 6/-.  
3 1/2 in. dia. Electrostatic Kilo Voltmeter in wooden case. £2.15.0. Carriage 10/-.  
Precision A.C. & D.C. Wattmeter. Model 8.67 certificated. Accuracy to 1% up to 133 c/s. Range 250/450 V. and 0.5 to 1 A. £29.10.0. Carriage 30/-.

### INDICATING MEASURING AMPLIFIER PR 7410

Suitable for vibration and frequency analysis. Frequency response 10-1,000 Hz. £45. Carr. 40/-.

**BRAND NEW S.E. LABORATORIES TRANSDUCER** 8.E. complete with encapsulated Amplifier/demodulator 8.E. 441/2  
Frequency D.C.—60 c.p.s.  
Available in the following ranges:  
SE150, SE250 or SE180A.  
0 - 50 p.s.i. 0 - 600 p.s.i. 0 - 3000 p.s.i.  
0 - 200 p.s.i. 0 - 750 p.s.i. 0 - 4000 p.s.i.  
0 - 350 p.s.i. 0 - 2000 p.s.i.  
Also available differential types ± 10 p.s.i.  
Also available differential types, + 10 p.s.i.  
List price £70+.

## COMPUTER AND PERIPHERAL EQUIPMENT



### 7 TRACK DIGITAL MAGNETIC TAPE STORAGE DECK

These machines originally ex-computer, are multi-track recording units, ideal for data storage. Record and Replay heads encased in one common unit. Low resistance heads. Frequency response approximately 0 Kc/s. to 50 Kc/s. Bit density 557 b.p.l. 1/2 in., 10 1/2 in. spools 230 V. to 380 V. A.C. Capstan Motor speed 1,500 r.p.m. 48 V. D.C. Rewind motors complete with vacuum Assembly. Finished in brush aluminium and matt-black. Size 27 in. x 26 in. x 8 in. Weight 90 lb. Price £72.10.0. Carriage extra.

**1/2" 7 TRACK**  
Ex-computer record/replay head complete with guides. Little used. Price £12.10.0 Carriage 15/-.

**BRAND NEW**  
Gresham Lion 1 in. 1 + 7 track record/replay heads. Of the highest professional quality. Cost £100 plus price £12.10.0. Carr. 15/-.

**9 TRACK 1 in.** Record/replay heads with sprocket drive, driven by synchronous motor. Mounted with integrated head assembly eliminating alignment problems. This can be fitted to any suitable type of transport system. Price £8.10.0. Carriage 15/-.

### MODEL 72 MAGNETIC TAPE DATA STORAGE UNIT

This unit consists of 1/2 in. 8 channel read-write heads. Can be used to record any 6 bit code. Data can be read in either a forward or backward direction plus giving search facilities. The unit consists circuits for receiving and storing instruction signals. Recording density 250 characters per inch. Tape speed 100 in. per second, price £190. Excellent condition.

### CANCELLED EXPORT ORDER

90 Column card sorter and punch type 425/0. Price on application.

### BRAND NEW COMPUTER TAPES AND EMPTY SPOOLS



Made by well known manufacturers  
1 in. certified 2,400 ft. 800 b.p.l. £28.10.0  
1/2 in. 2,400 ft. £28.10.0  
1/2 in. Highest grade 2,400 ft. £3. 0.0  
1/2 in. 10 1/2 in. dia. spool and cassette £21.10.0  
1/2 in. 8 1/2 in. dia. spool and cassette £21.10.0  
1 in. metal 10 1/2 in. dia. spool and cassette £22.10.0  
1/2 in. N.A.B. centres 10 1/2 in. spool only £21. 0.0

### TAPE PUNCH MODEL 25 7 HOLE

A multiwire tape punch designed for general application involving the conversion of parallel wire electrical impulses into punched paper-tape at 33 characters per second. Unit completely self-contained requiring only motor power and signal supplies.

### 7 HOLE NON PARITY TAPE PUNCH

New condition.

### LOW SPEED 7 HOLE TAPE PUNCH

60 characters per second by well-known manufacturer.

### TELETYPE 8 HOLE PAPER PUNCH BRPEII

Also available 5 hole punch BRPE2 as above. This model has interchangeable heads. Complete with spooler. Price £35.

### HIGH SPEED 5/7 HOLE OPTICAL READER

20 characters per second.

### CARD READERS

80 column 1500/80 model, punch } £325 Excellent  
80 column 1400/80 model verifier. } condition.

### HOLLERITH 80 COLUMN CARD PUNCH TYPE HO29 & VERIFIER AVAILABLE

### MULTI-RANGE TRANSISTORISED VOLT-METER 1063

Employing silicon planar F.E.T., this instrument gives long-term stability and negligible drift over a wide temperature range. Wide frequency band 0-500 MHz, using HFV 1063. Voltage range 0-30KV. Centre zero on DC ranges for differential circuit application. Input resistance 1 M.ohm/Volt on all DC ranges. Accuracy ± 3% F.S.D. Meter scale 5in. with 1M different colour for different scales. Special price £42/10/0 each. Carriage £1/10/0.

## PROGRAMME BOARDS BY SEALECTRO

These boards are basically a multi pole multi throw switch device consisting of a X-Y Matrix with two contact decks in the Z Plane running at 90 degrees to each other. Contact is made by either, aborting or plugging in pins. Ideal for prototype work, etc. Boards available in 24 x 60 Z plane £12.10.0. Pins available 1/3 each.



## MEMORY PLANES

Ferrite core memory planes with wired Ferrite cores. Used for building your own computer or as an interesting exhibit in the demonstration of a computer. Mounted on plastic material, frame 5 x 8 in. Consisting of matrices 40 x 25 x 4 cores each one individually addressable and divided into 2 halves with independent sense and inhibit wires. £8.10.0. P. & P. 3/-.

## MULLARD MATRIX CORE STORE STACKS

A.W. 510 5 planes 8 x 16 cores/per plane £12/10  
A.W. 511 5 planes 18 x 32 cores/per plane £25  
A.W. 534 20 planes 64 x 64 cores/per plane £89/10  
A.W. 537 8 planes 32 x 32 cores/per plane £55  
Single plane 40 x 25 x 4 £8/10  
Flexi-writer 7 hole punch and key-board £199/10

## MEMORY STORE

M. M. 1044 complete with logic circuits mounted in Imhof cabinet

## COMPUTERS Burroughs E 201

225 words store. £450

## LINEAR THYRISTOR CONTROLLED LIGHT DIMMER

600w. module. Ideally suitable for photoflood or speed controller, etc. Will mount into standard socket boxes. Our price 49/6 + p. & p. 3/-.

## DATA DISC HANDLER MK. IV

Self contained magnetic disc memory unit. Designed for integration with small computers and other digital systems. Suitable for Random Access. High density contact, recording, etc.

## TRANSFER CASE



For sending data by personal carrier, GPO post, passenger train, etc. Ideal. Suitable for despatching tape 20/- P. & P. 5/-.

## EICHNER 8 Hole Punch OR READERS

No motor drive required. Solenoid operated equipment using 48v. Reader £29.10 Punch £42.10 Carriage 25/-.

## FLEXIWRITERS FPC8

Both Punch and Read Type Available. Any code can be made to suit customers requirements. Price on application.

# LOW COST ELECTRONIC AND SCIENTIFIC EQUIPMENT AND COMPONENTS

## SOLARTRON MILLIVOLTMETER Type F252

1% accuracy on all ranges. 1.5 millivolts - 150 volts. F8D. Input resistance 30 Megohms. £35. Carr. extra.

## 5 DIGIT COUNTER

A very sturdy counter. Coil resistance 100 ohms. Minimum operational voltage 5v. Counting speed 13 counts per sec. Suitable for continuous counting with sine wave drive. Coincidence, recording and frequency meter 35/- p. & p. 6/-.

## VEEDER ROOT 6 DIGIT COUNTER



Suitable for counting all kinds of production runs, business machine operation. Mechanically driven Type KA1357. Reset manual knob. Ex-equipment but new condition. Special price 25/- plus 5/- p. & p.



### MINIATURE SQUARE COUNTER 6 DIGIT

by Veeder Root. Rotary ratchet type, adds 1 count for each 36° movement of shaft 9/8 + 2/6 p. & p.

## 6 DIGIT ELECTRICAL IMPULSE COUNTER

With electrical and mechanical reset. Counter driven by a 110V D.C. 4,400 ohms coil. Reset 110V D.C. 800 ohm coil. Housed in plastic-alloy case. The units can be interlocked with each other to give vertical or horizontal displays. Price 79/6 p. & p. 6/-.



## HAND TACHOMETERS

By SMITHS within 2 p.c. accuracy. 4 ranges, 500, 1,000, 5,000 and 50,000 Price

**£19.10.0**  
carr. extra

## BERKELEY DECIMAL COUNTING UNIT 0-9

4 valves double triode type 6865 special quality Unit plugs into standard octal base. Modular construction with 10 miniature neon lamps on display panel. Power supplies 6.3v A.V. 150V D.C. Cut-on or Cut-off—15v. Size 5 1/2 x 5 1/2 in. xl. 1/2 in. Price 65/- p. & p. 5/-.

## UNISELECTOR

8 and 4 Banks, 25 contact per bank, 2 sets of wipers 2 in. radius. Complete with surge capacitor. 25/- and 45/- respectively.

## MINIATURE DIGITAL DISPLAY

Operates on a rear projection 6.3 pilot lamp. The lamp projects the corresponding digit on the condensing lens through a projector lens, on to the viewing screen at the front of the unit. 1 in. width. 3 1/2 in. deep. 1 1/2 in. high. Weight 3 1/2 oz. Character size 1/2 in. high. 0.9 with 8 right hand decimal point and degree. Available to special order, words and other characters or colour, at cost of artwork or plates. List price 6 gns. Our price 49/6.

## LOW OHM SAFETY METER

12 mill-amps 5 ohms, suitable for testing circuits where currents must be limited £12/10/- p. p. 17/8.

ALL ORDERS ACCEPTED SUBJECT TO OUR TRADING CONDITIONS A COPY OF WHICH MAY BE INSPECTED AT OUR PREMISES DURING TRADING HOURS OR WILL BE SENT ON APPLICATION THROUGH THE POST.

## MOTORS

### HYSTERESIS REVERSIBLE MOTOR

Incorporating two coils. Each coil when energised will produce opposite rotation of output shaft. 240V 50 Hz. 1/2 r.p.m., 1 r.p.m., 120V 60 Hz, 1/10 r.p.m., 30/- each. P. & P. 3/-.

### HIGH TORQUE INDUCTION MOTOR.

3-30 oz/inch. Available in the following speeds only 240V 50 Hz 1/2 r.p.m., 1 r.p.m., 2 r.p.m. 120 V 60 Hz 20 r.p.m. 30/- each. P. & P. 3/-.

### LOW TORQUE HYSTERESIS MOTOR MA23

Ideal for instrument chart drives. Extremely quiet, useful in areas where ambient noise levels are low. High starting torque enable relative high inertia loads to be driven up to 6-oz/in. Available in the following speeds and ranges: 240V 50 Hz 4 r.p.m., 2 r.p.m., 1 1/2 r.p.m., 1 r.p.m., 1/2 r.p.m., 1/3 r.p.m., 1/6 r.p.m., 1/10 r.p.m., 1/12 r.p.m., 1/20 r.p.m., 1/40 r.p.m., 1/60 r.p.m., 1/75 r.p.m., 1/120 r.p.m., 1/360 r.p.m., 1/720 r.p.m., 1/20, 1/45 r.p.m.; 190V 50 Hz 1/2 r.p.m., 1/15 r.p.m., 1/16 r.p.m., 1/20 r.p.m., 1/24 r.p.m., 1/30 r.p.m., 1/60 r.p.m., 1/120 r.p.m., 1/240 r.p.m., 1/300 r.p.m., 1/720 r.p.m., 1440 r.p.m. 25/- each. P. & P. 3/-.

### HYSTERESIS CLUTCH MOTOR

With integral clutch allowing the motor to drop out of engagement with the gear train, thereby facilitating easy resetting when used in timers or in conjunction with a light spring. 6 oz. torque at 1 r.p.m., 240 v., 50 c/s. L—left, R—right, 15 r.p.m. L, 4 r.p.m., 1/2 r.p.m., 1/6 r.p.m., 1/8 r.p.m., B & L, 1/10 r.p.m., 1/12, 1/15 r.p.m. L. Also 120 v. 50 c/s 2, 1/6, 1/12, 5/12, 4/11, 1/10 r.p.m. 25/- P. & P. 3/-.

### HIGH PRECISION MAINS MOTOR

230V 50 Hz 1/8 h.p. continuously rated. 3000 r.p.m. Made by Croxford Engineering Model KA 80 JFB. Suitable for capstan motor. Size 8 in. long, 4 1/2 in. diameter with 8 in. diameter flange and 4 fixing holes. £4.10.0 each. £1.5.0 postage and packing.

### SYNCHRONOUS MOTORS

Model 8 71 r.p.h. and 1/60 r.p.h. Self starting complete with gearing shaft 1/2" dia. 1/2" long. 200/250 V 50 Hz. New Condition Ex. Equipment. 30/- p. & p. 3/-.

## OSCILLOSCOPES

Solartron AD 513 £49/10

Solartron CD 513/2 £48/10

Solartron AD 557 £55

Solartron CD 711 £85

Solartron CD 718-2 £80

Solartron QD 910 £275

Solartron 5238-2 £52.10

Furzehill 0.100 £25

Airmec 249 £25

Airmec 723 £19/10

Phillips 3230 £85

Mullard L101 Double Beam £96/10

Cossor 1035 £25

Cossor 1049 MkIII £40

Cossor 1049 £35

## DOUBLE FADERS 3W

1000 & 500 dimmer, ideal for light and heat control. Each resistive dimmer is adjustable and independent of each other. Ex. equipment but in an almost new condition. Price £3.19.6. Postage & packing 7/6.

## PRECISION POTENTIOMETERS

### TEN TURN 360° ROTATION BRAND NEW

Res. Ohms	Linearity Percent	Manufacturer	Model	Price
5	0.2	Colvern	2506	80/-
100/100/100		Beckman	A	150/-
100	0.5	Beckman	A.8	80/-
200	0.5	Beckman	A	80/-
500	0.1	Beckman	8	70/-
500		Colvern	2501	45/-
500		Foxes	FX4	40/-
500		Colvern	2610	50/-
2K	0.5	Beckman	8A1101	80/-
2K		Beckman	7216	60/-
2K		Reliance	GFML6	40/-
10K	0.5	Beckman	A	80/-
10K	0.1	Beckman X	A	70/-
15K		Foxes	GFMB	50/-
18K		Beckman	A	60/-
20K	0.5	Beckman	A	60/-
30K		Colvern	2402	30/-
30K		Beckman	8A95C	80/-
30K	0.1	Beckman	A.88	70/-
30K		Beckman	8A 1892	60/-
30K	0.25	Beckman	8A 1892	65/-
50K		Reliance	07.10	45/-
50K		Colvern	07.5	45/-
50K		Colvern	2503	45/-
50K		Foxes	FX4	45/-
50K		Beckman	A	60/-
50K	0.1	Beckman	A	70/-
100K/100K		Ford	A	100/-
100K	0.1	Beckman	A	70/-
100K	0.5	Beckman	A	60/-
100K		Colvern	2501	45/-
100K		Colvern	2610	50/-
298K	0.1	Beckman	8A3902	70/-
300K	0.1	Beckman	A	70/-

### THREE TURN 780° ROTATION

100/100	0.5	Beckman	A	60/-
300		Beckman	9303	45/-
10K	0.5	Beckman	C.8	45/-
20K/20K	0.1	Beckman	C.8	60/-
10K/10K	0.1	Beckman	C	60/-
50K	0.5	Beckman	C.8	35/-

### FIFTEEN TURN 5400° ROTATION

25K/25K		Beckman B	10 watts	28.10s
46K/46K		Beckman B	10 watts	28.10s

### TWENTY TURN 7200° ROTATION

250 ohms	General Controls	PXM130	80/-
1 Meg.	General Controls	PXM130	80/-
50K Reliance			40/-

### 156 TURN 56, 160° ROTATION

460 ohms	Kelvin Hughes	KTP0701	£9.10s
----------	---------------	---------	--------

### FIVE TURN 1800° ROTATION

500 ohms	Colvern	CLB 2505	40/-
U1.5K	Colvern	CLB 2605	40/-

### SINE COSINE

Kelvin & Hughes SCP9	14.4K	£17.10.0
Colvern 8601	30K	£17.10.0
CLB 9602—Cam Corrected	25K	£17.10.0
SCP4	32K	£17.10.0
SCP1	35K	£17.10.0

### PRECISION BECKMAN 40 TURN 14,400° ROTATION

Wirewound Precision Potentiometer. BE 107A 20 watts at 40°C. 3 1/2" Diameter. Servo Mounting. 200 K. Brand New £12.10s. List Price £20.

## GENERATORS

### SIGNAL GENERATOR

T.F. 801A Sine Wave, Square Wave Generator. Frequency Range: 10-310 M.c/s. Output Voltage (maximum) 200 milli-volts ± 5db. Output impedance 75 ohms. Mark/Space Ratio 90/50 on square wave. Price £20. Packing and carriage £2.

### SIGNAL GENERATOR

T.F. 817F1 Sine Wave, Square Wave Generator. Frequency Range: 120-300 M. C/s. Auxiliary 18-58 Meg. c/s. Output Voltage 0.2 Volts. Output impedance 75 ohms. £85.

### MARCONI T.F. 144G

Frequency Range 85 k.c/s. 25Mc/s. Output voltage 1 micro-volt to 1 volt. Output impedance 1 micro-volt, 100 milli-volt, 10 ohms. 100 milli-volt to 1 volt. 52.5 ohms. £25 + £2 carriage.

### PULSE GENERATORS

Model 101 Repetition rate 10 Hz-10MHz. Delay 30 n-10 m. sec. Output 10V. into 50 ohms. £95.

### SQUARE WAVE GENERATOR

Frequencies: 1M, 100Kc/s, 10Kc/s, 500/s. Load impedance 75 ohms. Output Voltage 10V. 75 ohms. 0-15 volts into 2000 ohms.

Rise time from 30-50 Mill micro seconds at 1 meg. Cycle. £85.


### MARCONI VALVE VOLT METER TF 428B/1

Frequency response on probe 10Kc/s/8-100Mc/s. Five separate Voltage Ranges. Overload Protection 100-250 A.C.P.F. Input 1MΩ Acc. ±2% or 0.02V. Size: 10 x 16 1/2 x 9 1/2. £518/6.

## VOLSTAT

Advance CV500/27. Input 95-130V. 50 Hz. Output 85v. R.M.S. Load 4 1/2 A/10 CV25E. Input 190-260v. 50 Hz. Output 6v. 25 watts £9/10/0 CV50J. Input 190-260V. 50 Hz. Output 230V. 50 watts £12/10/0 Carriage extra 15/-.

## RIGHT ANGLED GEAR BOXES

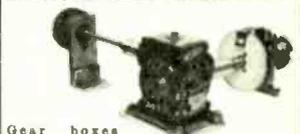

Gear boxes give a drive ratio of 2.5 : 1 at right angles to the input. Driveable through the 1/2 shaft only. Dimensions 4in. wide x 3 1/2 in. deep x 4 1/2 in. high. Robust construction in cast iron. Price 74/- With pulley and ball race shaft mountings. Price 99/6. Carriage 15/-


## OSCILLATORS

### DAWE 443 B AUDIO SWEEP OSCILLATOR AND CONTROLLER

Brand new. 2C C/8—20 Kilocycles per sec. Accuracy. P 1%. FM and adjustable frequency sweeps from 0 - 250 c/s. Sweep repetition rates 1 - 25 sweeps/sec. Price £89.10.0 Carr. extra.

## BRAND NEW LABORATORY TEST EQUIPMENT AT LESS THAN HALF PRICE
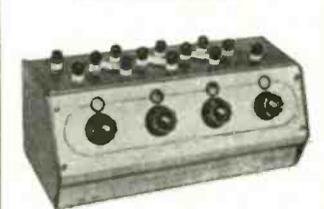
### HIGH VALUE RESISTANCE BOX TYPE R.7003



Specification. Range: 0.01-111 Meg. in 0.01 Megohm divisions. Accuracy: 0.05%. Maximum power rating: 0.1W per step. Case: Hammer finished stove enamel. List price £60. Our price £22/10/-.

### PORTABLE WHEATSTONE BRIDGE



Specification. Type: Moving Coil Galvanometer. Ranges: 1. 0.05 to 5 ohms. 2. 0.5 to 50 ohms. 3. 5 to 500 ohms. 4. 50 to 5,000 ohms. 5. 500 to 50,000 ohms. Scales: Switched. Slidewire: 0.5 to 50. Galvanometer Scale: 10-0-10. Case: Moulded plastic. Internal Source: 4V. Dry battery. Dimensions: 200 x 110 x 65mm. Weight: 0.9 kg. List price £25. Our price £29/19/6.

### MUTUAL INDUCTANCE BOX TYPE R.7005

Specification. Range: 0 - 11,100 mH in 0.002 mH divisions. Accuracy: ±(0.3 x 0.012)% where M = value of mutual inductance in mH set on the box. Frequency range: 0 - 2.5 K/c/s for all decades except X1=0.15 K/c/s. Maximum current: 0.5A for decades 1A for variometer (both primary and secondary windings). Case: Polished teak. List price £65. Our price £26.10.

### MUTUAL INDUCTANCE COIL TYPE R.7006

Specification. Value: 0.001 H. Accuracy: ±0.3%. Operating Frequency: 5 Kc/s, 10 Kc/s. Maximum current: 1A. 3A. Resistance of coils: 4 ohm, 1 ohm. Case: Moulded plastic. List price 8 gns. Our price 50/-

CARRIAGE EXTRA

ELECTRONIC BROKERS LTD., 49-53 PANCRAS ROAD, LONDON, N.W.1. Tel: 01-837 7781/2 Cables: SELELECTRO

# TECHNICAL TRAINING

## in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- P.M.G. Certs. in Radiotelegraphy
- General Certificate of Education, etc.

Examination Students coached until successful

## NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, incl. professional-type valve volt meter—all under expert tuition. Transistor Portable available as separate course.

### POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.



**INTERNATIONAL CORRESPONDENCE SCHOOLS**

EST. 1891

Dept. 222, Intertext House, Stewarts Road, London, S.W.8

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.)

NAME

ADDRESS

4/70

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

## R.S.T. VALVE MAIL ORDER CO.

BLACKWOOD HALL, 16A WELLFIELD ROAD  
STREATHAM, S.W.16

A61 9/8	EULL900	PL509 29/-	XR13/200	12AC6 10/-	2G414 6/-
ACT9 500/-	EP9 30/-	PL802 18/6	Z66 120/-	12AD6 11/-	2G415 8/-
ARF38 16/-	EP9 20/-	PT15 15/-	Z66 15/-	12A26 9/8	2G416 6/8
AZ31 10/-	EP37 A 7/-	PX4 24/-	Z319 25/-	12A76 4/9	2G417 6/-
BT19 60/-	EP39 8/-	PX25 27/8	Z739 30/-	12AT7 7/-	2P347 9/8
BT79 57/-	EF41 10/-	PY32 10/9	Z800 20/-	12AU7 5/9	2N555 12/6
BT89 67/-	EF60 5/-	PY33 10/9	Z801 30/-	12AX7 6/3	AC107 5/8
C1C 20/-	EF80 4/6	PY81 5/9	Z803U 15/-	12BA6 6/-	AC127 5/8
CB131 16/-	EF86 8/6	PY82 5/3	OA2 6/3	12BE6 6/3	AC128 4/6
COH35 15/-	EF89 5/6	PY83 7/-	OB2 8/-	12E1 20/-	AC129 5/-
CV5 95/-	EF91 3/6	PY900 18/6	OZ4 4/6	12K7GT 7/-	AC130 5/-
CV14 80/-	EF92 2/6	PY900 9/8	1H3GT 7/3	12K8GT 6/-	AC131 4/6
CV42 50/-	EF98 15/0	PY801 9/6	1Z2 25/-	12Q7GT 6/-	AD140 3/-
CV315 80/-	EF183 6/6	PZ30 10/-	2C39A 140/-	13E1 190/-	AF114 5/-
CV354 110/-	EF184 7/-	QF41 400/-	2C43 70/-	20P4 20/-	AF115 5/-
CV370 300/-	EF804 21/-	QQV02/6	2D21 8/6	24B1 110/-	AF116 4/6
CV372 57/-	EF804 10/-	QQV03/10	2E26 20/-	25Z4 6/3	AF117 7/-
CV408 50/-	EH90 7/6	QQV03/20	2K25 160/-	25Z6GT 8/-	BT100 4/6
CV428 45/-	EL33 12/6	QQV03/20	3A/167M	25Z6GT 8/6	GET871 5/-
CV429 350/-	EL34 10/8	QQV03/20	105/-	27M1 72/8	GET875 6/-
CV450 25/-	EL38 9/3	QQV04/15	105/-	30C15 15/-	NKT211 6/6
CV1144 60/-	EL41 11/-	3B24 20/-	105/-	30C17 16/-	NKT214 4/4
CV1385 140/-	EL42 11/8	3B240M	105/-	30F5 17/-	NKT216 8/4
	EL41 9/-	3B241M	105/-	30FL1 15/-	NKT217 8/4
	EL41 9/-	3B241M	105/-	30L15 110/-	NKT218
	EL41 9/-	3B241M	105/-	30L17 17/-	NKT228 6/-
	EL41 9/-	3B241M	105/-	30P4 15/-	NKT404
	EL41 9/-	3B241M	105/-	30P19 16/-	
	EL41 9/-	3B241M	105/-	30PL1 16/-	
	EL41 9/-	3B241M	105/-	30PL13 18/6	NKT475 6/-
	EL41 9/-	3B241M	105/-	30PL14 18/-	NKT757 5/-
	EL41 9/-	3B241M	105/-	35L6 9/-	NKT713 7/8
	EL41 9/-	3B241M	105/-	35LAGT 9/-	OC16 15/-
	EL41 9/-	3B241M	105/-	35W4 4/8	OC19 8/6
	EL41 9/-	3B241M	105/-	35Z4GT 8/8	OC20 20/-
	EL41 9/-	3B241M	105/-	50C8 6/3	OC24 9/-
	EL41 9/-	3B241M	105/-	50CDB6	OC25 7/8
	EL41 9/-	3B241M	105/-	80 7/6	OC28 6/-
	EL41 9/-	3B241M	105/-	85A1 25/-	OC29 14/6
	EL41 9/-	3B241M	105/-	85A2 7/3	OC35 6/8
	EL41 9/-	3B241M	105/-	88L 160/-	OC44 4/-
	EL41 9/-	3B241M	105/-	90A4 45/-	OC45 3/8
	EL41 9/-	3B241M	105/-	90C1 12/-	OC71 3/8
	EL41 9/-	3B241M	105/-	90C2 25/-	OC72 4/6
	EL41 9/-	3B241M	105/-	90C9 25/-	OC73 4/6
	EL41 9/-	3B241M	105/-	150B2 11/8	OC76 3/8
	EL41 9/-	3B241M	105/-	150B3 8/8	OC77 8/-
	EL41 9/-	3B241M	105/-	725A 10/-	OC81 4/-
	EL41 9/-	3B241M	105/-	725A 120/-	OC81D 3/-
	EL41 9/-	3B241M	105/-	725A 240/-	OC81M 5/-
	EL41 9/-	3B241M	105/-	801 9/6	OC81DM 3/-
	EL41 9/-	3B241M	105/-	803 9/6	OC82 3/-
	EL41 9/-	3B241M	105/-	807 9/-	OC82D 3/-
	EL41 9/-	3B241M	105/-	811 85/-	OC83 4/6
	EL41 9/-	3B241M	105/-	813 75/-	OC169 6/-
	EL41 9/-	3B241M	105/-	813USA	OC170 5/8
	EL41 9/-	3B241M	105/-	829B 80/-	OC171 6/-
	EL41 9/-	3B241M	105/-	833A 380/-	OC200 5/6
	EL41 9/-	3B241M	105/-	837 17/8	X5642 3/8
	EL41 9/-	3B241M	105/-	866A 15/-	XA111 3/8
	EL41 9/-	3B241M	105/-	872A 57/8	XA112 4/6
	EL41 9/-	3B241M	105/-	831A 72/8	XA125 5/6
	EL41 9/-	3B241M	105/-	954 3/8	XA141 7/-
	EL41 9/-	3B241M	105/-	955 3/-	XA142 5/-
	EL41 9/-	3B241M	105/-	2050 15/-	XA143 5/-
	EL41 9/-	3B241M	105/-	5644 40/-	
	EL41 9/-	3B241M	105/-	5651 7/3	<b>TUBES</b>
	EL41 9/-	3B241M	105/-	5654 8/-	2AP1 80/-
	EL41 9/-	3B241M	105/-	5672 7/-	3BP1 50/-
	EL41 9/-	3B241M	105/-	5687 10/-	3D1 40/-
	EL41 9/-	3B241M	105/-	5691 25/-	3FG 65/-
	EL41 9/-	3B241M	105/-	5694 30/-	3FP7 29/-
	EL41 9/-	3B241M	105/-	5702 15/-	30P1 40/-
	EL41 9/-	3B241M	105/-	5749 10/-	5BP1 50/-
	EL41 9/-	3B241M	105/-	5763 12/-	5CP1 55/-
	EL41 9/-	3B241M	105/-	5784 35/-	5FP7 35/-
	EL41 9/-	3B241M	105/-	5842 65/-	85L 80/-
	EL41 9/-	3B241M	105/-	5876 60/-	88D 200/-
	EL41 9/-	3B241M	105/-	5879 22/6	ACR22 80/-
	EL41 9/-	3B241M	105/-	5893 150/-	C27A 160/-
	EL41 9/-	3B241M	105/-	5899 10/-	CV960 76/-
	EL41 9/-	3B241M	105/-	5992 15/-	CV968 35/-
	EL41 9/-	3B241M	105/-	5963 10/-	CV1328 85/-
	EL41 9/-	3B241M	105/-	6037 10/-	CV1587 80/-
	EL41 9/-	3B241M	105/-	6058 10/-	CV1588 35/-
	EL41 9/-	3B241M	105/-	6059 18/-	E4504/B16
	EL41 9/-	3B241M	105/-	6060 8/-	76/-
	EL41 9/-	3B241M	105/-	6061 12/-	ECR30 35/-
	EL41 9/-	3B241M	105/-	6062 12/-	ECR35 50/-
	EL41 9/-	3B241M	105/-	6063 7/-	EW-2 100/-
	EL41 9/-	3B241M	105/-	6064 7/-	MW-2
	EL41 9/-	3B241M	105/-	6065 9/-	100/-
	EL41 9/-	3B241M	105/-	6067 10/-	06D 80/-
	EL41 9/-	3B241M	105/-	6072 12/-	09G 80/-
	EL41 9/-	3B241M	105/-	6080 25/-	09L 80/-
	EL41 9/-	3B241M	105/-	6111 12/6	VCR97 45/-
	EL41 9/-	3B241M	105/-	6148 27/8	VCR1386/9
	EL41 9/-	3B241M	105/-	7475 14/-	VCR138A
	EL41 9/-	3B241M	105/-	9003 9/-	60/-
	EL41 9/-	3B241M	105/-	9004 2/6	VCR139A
	EL41 9/-	3B241M	105/-		45/-
	EL41 9/-	3B241M	105/-		VCR516
	EL41 9/-	3B241M	105/-		80/-
	EL41 9/-	3B241M	105/-		VCR517A
	EL41 9/-	3B241M	105/-		46/-
	EL41 9/-	3B241M	105/-		VCR517B
	EL41 9/-	3B241M	105/-		46/-
	EL41 9/-	3B241M	105/-		VCR517C
	EL41 9/-	3B241M	105/-		46/-

Valves tested and released to A.R.B. specification if required.

Express postage 9d. per valve.  
Ordinary postage 6d. per valve.  
Over £5 postage free.  
Tel. 01-769 0199/1649

Monday to Saturday  
9 a.m.—5.30 p.m.  
Closed Sat 1-30—2-30 p.m.  
Complete range of TV Tubes  
available from £45.0.

**SEND S.A.E. FOR LIST OF 6,000 TYPES  
VALVES, TUBES AND TRANSISTORS**

BRAND NEW SEMICONDUCTORS & COMPONENTS GUARANTEED

TRANSISTORS Brand new and fully guaranteed. PLEASE NOTE!—A large number of our transistors have now been reduced in price. Many more semi-conductors in stock. Please enquire for types not listed.

Table listing various semiconductor components including transistors (e.g., 2G301, 2G302, 2G303), diodes, and other parts with their respective part numbers and specifications.

SILICON RECTIFIERS table listing PIV ratings (1A, 3A, 6A, 10A, 15A) and current ratings (100, 200, 400, 600, 800, 1000, 1200).

DIODES & RECTIFIERS table listing various diode models like 1N461, 1N914, 1N916, 1N4007, etc.

MAINS TRANSFORMERS table listing transformer types and their specifications (e.g., 1 amp. Sec. tappings from 6 to 50v).

PLESSEY table listing components like SL402A, SL403A, and their applications.

FAIRCHILD and MOTOROLA table listing integrated circuits like L900 Buffer, L914 Dual Gate, etc.

MULLARD I.C.'s table listing data sheets and components like FCH 211, FCH 221, etc.

GENERAL ELECTRIC table listing audio amplifiers like PA230, PA234, etc.

THYRISTORS table listing PIV ratings and current ratings for various thyristor models.

VEROBOARD table listing board sizes and matrix configurations (e.g., 24 x 32, 24 x 52).

RESISTORS table listing carbon film and wire wound resistors with various wattage and resistance values.

CAPACITORS table listing polyester, ceramic, polystyrene, silver mica, tantalum, trimmers, etc.

THERMISTORS (MULLARD) table listing R53 (5TC) and K151 (5ic-mens) models with various specifications.

PANEL METERS table listing various meter types like 38 Series—FACE SIZE 42 x 42 mm, Microamp, 200, 500, etc.

SPEAKERS (3ohm) table listing speaker models like 10" x 6", 8" x 5", etc.

CARBON POTENTIOMETERS table listing potentiometer types like Log. and Lin. Less switch, Log. and Lin. With switch.

WIRE-WOUND POTS (3 watts) table listing potentiometer models like 4.8" x 4" x 1" Finned, etc.

HEAT SINKS table listing heat sink models like 4.8" x 4" x 1" Finned, etc.

ZENER DIODES table listing zener diode models like 400 m W (from 3.3v to 33v), etc.

CIR-KIT table listing kit components like 5 ft. x 1/16 in. and in. D.G. 30 W. Soldering Irons.

SPECIAL OFFERS table listing offers like Bag of transistors (new) approx. 100 pieces @ 10/-, Bag of 1W mixed resistors approx. (120 pieces) @ 5/-, etc.

SPECIAL OFFER table listing offers like To encourage personnel callers we are happy to offer a discount of 5% to all our customers on Saturdays only.


Telex 21-492 A. MARSHALL & SONS LTD CALLERS WELCOME Hours 9-5.30 Mon.-Sat. 28 CRICKLEWOOD BROADWAY, LONDON, N.W.2

**ADMIRALTY B.40 RECEIVERS**




High quality 10 valve receiver manufactured by Murphy. Coverage in 5 bands 650 Kc/s-30 Mc/s. I.F. 800 Kc/s. Incorporates 2 R.F. and 3 I.F. stages, bandpass filter, noise limiter, crystal controlled B.F.O. calibrator I.F. output, etc. Built-in speaker, output for phones. Operation 150/230 volt A.C. Size 19 1/2 x 13 1/2 x 10 1/2 in. Offered in good working condition. £22/10/0, carr. 30/-, With circuit diagrams. Also available B41 L.F. version of above. 15 Kc/s-700 Kc/s. £17/10/-, Carr. 30/-.

**R209 Mk. II COMMUNICATION RECEIVER**

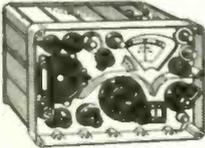

11 valve high grade communication receiver suitable for tropical use. 120 Mc/s. on 4 bands. AM/CW/PM operation. Incorporates precision variable drive. B.F.O. Aerial trimmer, internal speaker and 12v. D.C. internal power supply. Supplied in excellent condition. fully £15.00 Carr. tested and checked. 20/-.

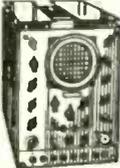**TYPE 13A DOUBLE BEAM OSCILLOSCOPES BARGAIN**



An excellent general purpose D/B oscilloscope. T.B. 2 cps-750 Kc/s. Bandwidth 6.5 Mc/s. Sensitivity 33 Mv/cm. Operating voltage 0/110/200/250 v. A.C. Supplied in excellent working condition, £22/10/-. Or complete with all accessories, probe, leads, lid, etc. £25. Carriage 30/-.

**MARCONI CT44 TF956 AF ABSORPTION WATTMETER**



1 μwatt to 6 watts. £20. Carr. 20/-.

**CLASS D. WAVEMETERS**




A crystal controlled heterodyne frequency meter covering 1.7-8 Mc/s. Operation on 6 v. D.C. Ideal for amateur use. Available in good used condition £5.19.8 Carr. 7/6. Or brand new with accessories £7.19.8 Carr. 7/6.

**CLASS D WAVEMETERS No. 2**




Crystal controlled, 1.2-19 Mc/s. Mains or 12v. D.C. operation. Complete with calibration charts. Excellent condition £12/10/0. Carr. 30/-.

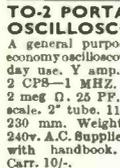**LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS**



0-20 Kc/s. Output 5K or 500 ohms. 200/250 v. A.C. Offered in excellent condition, £12/10/-. Carriage 10/-.

**VOLTAGE STABILISER TRANSFORMERS.**

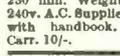

180-260v. input. Output 230v. Available 150w or 225w. £12.10.0. Carr. 5/-.

**TO-2 PORTABLE OSCILLOSCOPE**



A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth 2 CPB-1 MHz. Input imp. 2 meg Ω. 25 PF. Illuminated scale. 2" tube. 115 x 180 x 230 mm. Weight 8lbs. 220/240v. A.C. Supplied brand new with handbook. £22/10/-, Carr. 10/-.

**TO-3 PORTABLE OSCILLOSCOPE. 3" TUBE**



Y amp. Sensitivity. 1v p-p/CM. Bandwidth 1.5 cps-1.5 MHz. Input imp. 2 meg Ω. 25 PF. X amp sensitivity. 9v p-p/CM. Bandwidth 1.5 cps-800 KHZ. Input imp. 2 meg Ω. 20 PF. Time base. 5 ranges 10 cps-300 KHZ. Synchronisation. Internal/external. Illuminated scale. 140 x 215 x 330 mm. Weight 15 1/2 lbs. 220/240 v. A.C. Supplied brand new with handbook. £27.10.0 Carr. 10/-.

**CRYSTAL CALIBRATORS NO. 10**



Small portable crystal controlled transmitter. Size 7 1/2 x 7 1/2 x 4 1/2 in. Frequency range 500 Kc/s-10 Mc/s (up to 30 Mc/s on harmonics). Calibrated dial. Power requirements 300 V. D.C. 10mA and 12 V. D.C. 0.3A. Excellent condition. 89/8. Carr. 7/6.

**MARCONI TF885 VIDEO OSCILLATORS**

0-5 mc/s sine square wave £45. Carr. 20/-.

**MARCONI TF155M BEAT FREQUENCY OSCILLATORS**

0-40 kc/s. £20. Carr. 30/-.

**WS62 TRANCEIVERS**  
Large quantity available for EXPORT! Excellent condition. Enquiries invited.

**UNR-30 4 BAND COMMUNICATION RECEIVER**  
Covering 550 Kc/s-30 Mc/s. Incorporates BFO. Built-in speaker and phone jack. Metal cabinet. Operation 220/240 v. A.C. Supplied brand new, guaranteed with Instructions. 13gns. Carr. 7/6.



**EDDYSTONE V.H.F. RECEIVERS**  
770R. 19-165 Mc/s. £150.  
Both types in excellent condition.




**LAFAYETTE SOLID STATE HA600 RECEIVER**  
5 BAND AM/CW/SSB AMATEUR AND SHORT WAVE. 150 kc/s-400 Kc/s AND 550 Kc/s-30 Mc/s. F.E.T. front end ● 2 mechanical filters ● Hure dial ● Product detector ● Variable BFO ● Noise limiter ● 8 Meter ● 24in. Bandspread ● 230 v. A.C./12 v. D.C. neg earth operation ● RF gain control. Size 18 1/2 x 9 1/2 x 8 1/2 in. Wt. 18 lbs. EXCEPTIONAL VALUE £45. CARR. 10/-, S.A.E. FOR FULL DETAILS.

**UR-1A SOLID STATE COMMUNICATION RECEIVER**

4 bands covering 550 Kc/s-30 mc/s continuous. Special features are use of P.E.T transistors, 8 meter, built-in speaker and telescopic aerial, variable BFO for SSB reception, noise limiter, bandspread control, sensitivity control. Output for low impedance headphones. Operation 220/240 volt A.C. or 12 volt D.C. Size 12 1/2" x 4 1/2" x 7". Excellent value. Only £24. carr. 7/6.



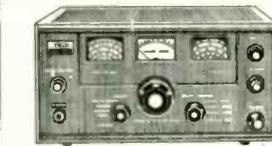**TRIO COMMUNICATION RECEIVER MODEL 9R-59DE**



4 band receiver covering 500 Kc/s to 30 Mc/s, continuous and electrical bandspread on 10-15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. 88B-CW ● Variable BFO ● 8 meter. ● Bandspread dial ● IF 455 Kc/s ● audio output 1.5 w. ● Variable RF and AF gain controls. 115/250 v. A.C. mains. Beautifully designed. Size 7 x 15 x 10in. With instruction manual and service data. £42. Carriage paid Trio Communication Type Headphones. Normally £5.19.8. Our price £3.15.0 if purchased with above receiver.

**TRIO TS 510 Amateur Transceiver with speaker and mains P.S.U. £112**  
**TRIO JR 500SE 10-80 Metre Amateur Receiver £65**

**LAFAYETTE HA.800 SOLID STATE AMATEUR COMMUNICATION RECEIVER SIX BANDS 3.5-4, 7-7.3, 14-14.35, 21-45, 28-29.7, 50-54 Mc/s.**

Dual conversion on all bands. 2 x 455 Kc/s mechanical filters. Product detector. Variable B.F.O. 100 Kc/s crystal calibrator. 8" meter. Huge slide rule dial. Operation 230v AC or 12v DC. Size 10" x 9" x 6". Complete with instruction manual. £57.10.0. Carr. Paid. (100 Kc/s Crystal 39/8 extra.)




**TRIO JR-310 NEW AMATEUR BAND 10-80 METER RECEIVER IN STOCK £77.10.0**




**RCA COMMUNICATIONS RECEIVERS AR88D**  
Latest release by ministry BRAND NEW in original cases. 110-250v. A.C. operation. Frequency in 6 Bands, 535 Kc/s-32 Mc/s continuous. Output impedance 2.5-600 ohms. Incorporating crystal filter, noise limiter, variable BFO, variable selectivity, etc. Price £87.10.0. Carr. £2.

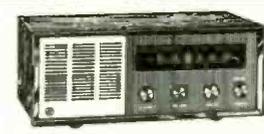**LAFAYETTE PF-60 SOLID STATE VHF FM RECEIVER**

A completely new transistorised receiver covering 152-174 Mc/s. Fully tuneable or crystal controlled (not supplied) for fixed frequency operation. Incorporates 4 INTEGRATED CIRCUITS. Built-in speaker and illuminated dial. Squelch and volume controls. Tape recorder output. 75 Ω aerial input. Headphone jack. Operation 230 v. A.C./12 v. D.C. Neg. earth. £37/10/-, Carr. 10/-.



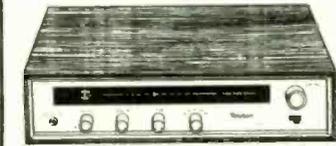**TELETON MODEL CR-10T AM/FM STEREO TUNER AMPLIFIER**



A new model from Teleton. 31 solid state devices. 4+4 watt output. Inputs for ceramic/crystal cartridge. Frequency range AM 540-1600 KHz, FM 88-108 MHz. Automatic FM Stereo reception. Stereo Indicator. Controls: Tuning, function selector, Tone and B & L volume controls. AFC switch. Stereo headphone socket. Size 13 1/2 x 9 1/2 x 9 1/2 in. approx. Price £34.0/0. Carr. 7/6.

**SEW PANEL METERS**


Type MR.38P. 1 21/32in. square fronts.			
50μA	40/-	50mA	27/6
50-0-50μA	37/6	100mA	27/6
100μA	37/6	150mA	27/6
100-0-100μA	35/-	200mA	27/6
200μA	35/-	300mA	27/6
500μA	30/-	500mA	27/6
500-0-500μA	27/6	750mA	27/6
1mA	27/6	1 amp	27/6
1-0-1mA	27/6	2 amp	27/6
2mA	27/6	5 amp	27/6
5mA	27/6	3V. D.C.	27/6
10mA	27/6	10V. D.C.	27/6
20mA	27/6	20V. D.C.	27/6
		100V. D.O.	27/6
		150V. D.C.	27/6
		300V. D.O.	27/6
		500V. D.O.	27/6
		750V. D.C.	27/6
		18V. A.C.	27/6
		50V. A.C.	27/6
		150V. A.C.	27/6
		300V. A.C.	27/6
		500V. A.C.	27/6
		8 meter 1mA	32/-
		VU Meter	42/-

FULL RANGE OF OTHER SIZES IN STOCK—SEND SAE FOR LEAFLET

**POWER RHEOSTATS**

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fixing, 1/2 in. dia. shafts. Bulk quantities available. 14/6. P. & P. 1/6. 25 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. 21/-, P. & P. 1/6. 50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. 21/-, P. & P. 1/6. 100 WATT. 15/10/25/50/100/250/500/1000 or 2500 ohms. 27/6. P. & P. 1/6.

**AVOMETER MOVEMENTS**

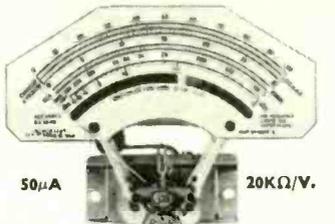

Spare movements for Model 8 or 9. (Fitted with Model 9 scale) or basis for any multimeter. Brand New and Boxed 89/8 P. & P. 3/6

**MARCONI TF.142E DISTORTION FACTOR METERS**

Excellent condition. Fully tested £20. Carr. 15/-.

**T.E.40 HIGH SENSITIVITY A.C. VOLTMETER**

10 meg. input 10 ranges: .01/.03/.1/.3/1/3/10/30/100/300 v. R.M.S. 4 cps-1.2 Mc/s. Decibels -40 to +50 dB. Supplied brand new complete with leads and Instructions. Operation 230 v. A.C. £17/10/-, Carr. 5/-.

**PLESSEY SL 403A**

3-watt. Integrated amplifier circuit. 49/6 post paid.

**TE-45 VALVE VOLTMETER**



High quality instrument with 28 ranges. D.C. volts 1.5-1,500 v. A.C. volts 1.5-1,500 v. Resistance up to 1,000 megohms. 220/240v. A.C. operation. Complete with probe and Instructions £17/10/0. P. & P. 6/-.

**COSSOR 1049 DOUBLE BEAM OSCILLOSCOPES**

D.C. coupled. Band width 1 Kc/s. Perfect order. £25. Carr. 30/-.

**AM/FM SIGNAL GENERATORS**




Oscillator Test No. 2. A high quality precision instrument made for the Ministry by Airtec. Frequency coverage 20-80 Mc/s. AM/CW/PM. Incorporates precision dial, level meter, precision attenuator 1μV-100Mv. Operation from 12 volt D.C. or 0/110/200/250 v. A.C. Size 12 x 8 1/2 x 8 1/2 in. Supplied in brand new condition complete with all connectors, fully tested. £45. Carr. 20/-.

**GEARED MAINS MOTOR**




Parlux type 8D19 230/250 v. A.C. Reversible. 30 r.p.m. 40 lb. lbs. Complete with capacitor. Excellent condition. 89/8. Carr. 10/-.

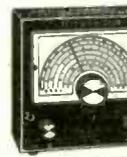**TE-16A TRANSISTORISED SIGNAL GENERATOR**



5 Ranges 400 KHZ-30 MHZ. An inexpensive instrument for the handyman. Operates on 9v. battery. Wide easy to read scale. 800 KHZ modulation. 5 1/2" x 5 1/2" x 3 1/2". Complete with instructions and leads. £7/19.8. P.P. 4/-.

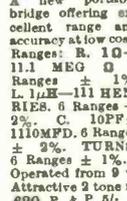**TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE**



A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 10-11.1 MEG Ω 6 Ranges ± 1%. L. 1 1/2 H-111 HENRIES. 6 Ranges -10%. C. 10PF ± 110MFD. 6 Ranges ± 2%. TURNS RATIO 1:1/1000-1:11000. 6 Ranges ± 1%. Bridge voltage at 1,000 CPS. Operated from 9v. battery. Meter indication. Attractive 2 tone metal case. Size 7 1/2" x 5" x 2". £20. P. & P. 6/-.

**AUTO TRANSFORMERS**

0/115/230v. Step up or step down. Fully shrouded 150 W. 42/8. P. & P. 3/6  
300 W. 55/6. P. & P. 4/6  
500 W. 24/10/0. P. & P. 6/6  
1,000 W. 28/10/0. P. & P. 7/6  
1,500 W. 27/19/6. P. & P. 8/6  
7,500 W. 215/10/0. P. & P. 20/-.

**G. W. SMITH & Co. (Radio) Ltd.**  
ALSO SEE OPPOSITE PAGE

**ARF-100 COMBINED AF-RF SIGNAL GENERATOR**



**AF. SINE WAVE**  
20-200,000 cps. Square wave 20-30,000 cps. O/P HIGH IMP. 21 v. P/P 600 Ω 3.8 v. P/P.  
E.F.P. 100 kc/s-500 Mc/s. Variable R.F. attenuation. Int./Ext. Modulation. Incorporates dual purpose meter to monitor AF output and % mod. on R.F. 220/240 v. A.C. £32.10.0 Carr. 7/6.

**TE-20RF SIGNAL GENERATOR**



Accurate wide range signal generator covering 120 kc/s-260 Mc/s. on 6 bands. Directly calibrated. Variable R.F. attenuator. Operation 200/240 v. A.C. Brand new with instructions. £15.

P. & P. 7/6. S.A.E. for details.

**PEAK SOUND PRODUCTS**

Full range of Amplifiers, kits, Speakers in stock.

**TE22 SINE SQUARE WAVE AUDIO GENERATORS**

Sine: 20 cps to 200 kc/s. on 4 bands. 20 cps to 30 kc/s. Output impedance 5,000 ohms, 200/250 v. A.C. operation. Supplied brand new and guaranteed with instruction manual and leads. £18.10.0. Carr. 7/6.



**LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER**



2 pf-2,000 mfd. 2 ohms-200 meg. ohms. Also checks impedance turns ratio insulation. 200/250 v. A.C. Brand New, £17.10 Carr. 7/6.

**TY75 AUDIO SIGNAL GENERATOR**

Sine Wave 20 CPB-200 Kc/s. Square Wave 20 CPB-30 Kc/s. High and low impedance output. Output variable up to 6 volts. 220/240 volts A.C. Brand new with instructions. £16. Carr. 7/6. Size 210 x 160 x 120 mm.



**TE-20D RF SIGNAL GENERATOR**



Accurate wide range signal generator covering 120 Kc/s-500 Mc/s on 6 bands. Directly calibrated. Variable R.F. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions. £15. Carr. 7/6. Size 140 x 216 x 170 mm.

**ADVANCE TEST EQUIPMENT**

**J1B. AUDIO SIGNAL GENERATOR**

15 cps to 50 Kc/s. Sine wave. Output 600 ohms or 5 ohms. £30.0.0.

**VM79. UHF MILLIVOLT METER**

100 Kc/s to 1,000 Mc/s. A.C. 10 mV to 3v. D.C. 10 mV. to 3v. Current 0.01 uA to 0.3 mA. Resistance 1 ohm to 10 megohm. £125.0.0.

**TT15. TRANSISTOR TESTER**

Full range of facilities for testing PNP or NPN transistors in or out of circuit. £37.10.0. Carriage 10/- per item.


**MODEL ZQM TRANSISTOR CHECKER**

It has the fullest capacity for checking on A, B and Ico. Equally adaptable for checking diodes, etc. Spec.: A: 0.7-0.9967. B: 0-200. Ico: 0/50 micro-amps. 0.6 mA. Resistance for diode 200 Ω +1 MEG. Supplied complete with instructions, battery and leads. £5.19/6. P. & P. 2/6.

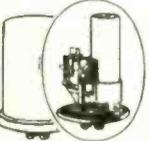**CAR LIGHT FLASHERS**

Heavy duty light flasher employs a condenser discharge principle operating on electro-mechanical relay. (As inset)

Housed in strong plastic case. Flashing rate between 60-120 per minute. 12 volt D.C. operation. Maximum load 6 amps. Size 2 1/2 in. dia. by 4 in. Supplied brand new at a fraction of original cost. 6/6 each, P. & P. 2/6. (3 for 17/6. P. & P. 4/6.)



**Latest Catalogue**

The latest edition giving full details of a comprehensive range of HI FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. . . . Nearly 200 pages, fully illustrated and detailing thousands of items—many at bargain prices. FREE DISCOUNT COUPONS VALUE 10/-.



SEND NOW—ONLY 7/6 P & P 1/-


**GARRARD**

Full current range offered brand new and guaranteed at fantastic savings

1026 Stereo	£7.19.6	AP75	£18.19.6
2026 T/C		BL75	£25.19.6
Stereo	£8.17.6	SL75B	£28. 0.0
3000 Stereo	£8.19.6	SL95B	£35. 0.0
8P25 Mk II	£11. 9.6	A70/11	£11.19.6
8L55	£11.12.6	401	£25. 0.0
8L65B	£14.19.6	8L55 with Sonotone	
8L72B	£25. 0.0	WAHCD	£12.10.0

Carriage 7/6 extra each item.

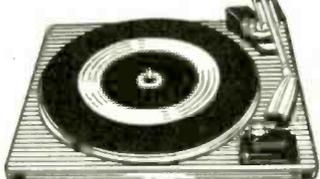**TEAK BASES AND PERSPEX COVERS**  
1. For 8P25, 8L65, 8L55, 3000, 2026T/C, 2026, 1000, £4.10.0.  
2. For AP75, BL75, 8L95, £5.19.6.  
3. For 8P25 etc. to operate with lid in place £5.19.6. Carriage 7/6 extra each type.



**LAFAYETTE LA-224T TRANSISTOR STEREO AMPLIFIER**



19 transistors, 8 diodes, IHF music power 30 watts at 8 ohms. Res. 30-50,000 ± 2 dB at 1 w. Distortion 1% or less. Inputs 3 mV and 250 mV. Output 3-18 ohms. Separate L and R volume controls. Treble and bass controls. Stereo phone jack. Brushed aluminum, gold anodised extruded front panel with metal case. Size 10 1/2 in. x 3 1/2 in. x 7 1/2 in. Operation 115/230 volt A.C. £24. Carr. 7/6.

**Variable Voltage TRANSFORMERS**

Brand new, guaranteed and carriage paid. High quality construction. Input 230 v. 50-60 cycles. Output full variable from 0-280 volts. Bulk quantities available. 1 amp.—£5/10/-; 2.5 amp.—£6/15/-; 5 amp.—£9/15/-; 8 amp.—£14/10/-; 10 amp.—£18/10/-; 12 amp.—£21; 20 amp.—£37



**MULTIMETERS for EVERY purpose!**



**TE-800 20,000 Ω/VOLT GIANT MULTIMETER**  
Mirror scale and overload protection. dim. full view meter. 2 colour scale. 0/2.5/10/250/1,000/5,000 v. A.C. 0/25/12.5/10/50/250/1,000/5,000 v. D.C. 0/50 μA/110/300/600 mA. D.C. 10 amp. D.C. 02K/200K/20 MEG. OHM. £15/- P. & P. 5/-.

**MODEL AS-100D. 100 Ω/Volt. Sin. mirror scale. Built-in meter protection 0/3/12/60/120/300/600/1,200 v. D.C. 0/6/30/120/300/600 v. A.C. 0/10 μA/60/300/600 mA/12 Amp. 0/2K/200K/2M/200M Ω. —20 to +17dB. £12/10/- P. & P. 3/6.**



**MODEL TE-90 50,000 O.P.V. Mirror scale overload protection. 0/3/12/60/300/600/1,200 v. D.C. 0/6/30/120/300/600 mA. D.C. 0/50 μA/110/300/600 mA. D.C. 10 amp. D.C. 02K/200K/20 MEG. OHM. £17/6. P. & P. 3/6.**

**MODEL TE-70. 30,000 O.P.V. 0/3/15/60/300/600/1,200 v. D.C. 0/6/30/120/300/600/1,200 v. A.C. 0/30 μA/30/300 mA. 0/16K/160K/1.6M/16 MEG Ω. £5/10/- P. & P. 3/6.**



**MODEL TE-30. 20,000 O.P.V. 0/10/50/100/500/1,000 v. A.C. 0/5/25/50/250/500/1,000 v. D.C. 0-50 μA. 5/50/500 mA. 0/6K/60K/600K/6 meg. £4/17/6. P. & P. 3/6.**

**MODEL TE-12. 20,000 O.P.V. 0/0.01/30/120/300/1,200/3,000/6,000 v. D.C. 0/6/30/120/600/1,200 v. A.C. 0/50 μA/60/600 mA. 0/6K/600K/6 MEG Ω. 60 Meg Ω. 50 PF. 2 MFD £5/19/6. P. & P. 3/6.**



**TE-51 NEW 20,000 Ω/VOLT MULTIMETER with overload protection and mirror scale. 0/6/60/120, 1,200 v. A.C. 0/3/30/60/300/600/3,000v. D.C. 0/60 μA/12/300mA A.D.C. 0/60K/6 meg. ohm. 92/6. P. & P. 2/6.**



**MODEL PT-34. 1,000 O.P.V. 0/10/50/100/500/1,000V. a.c. and d.c. 0/1/100/500 mA. d.c. 0/100 K Ω 30/6. P. & P. 1/6.**




**MODEL TE-10A. 20k Ω/Volt 5/25/50/250/500/2,500 v. D.C. 10/50/100/500/1,000 v. A.C. 0/60 μA/2.5 mA/250 mA D.C. 0/6K/6 meg. ohm. —20 to +22 dB. 10-0, 100 mfd. 0.100-0.1 mfd. 60/6. P. & P. 2/6.**

**LAFAYETTE 57 Easne Super 50K Ω/V. Multimeter. D.C. volts 125mv-300v. A.C. volts 1.5v-1000v. D.C. Current 25 μA-10 Amp. Ohms 0-10 Meg Ω. D.B.—20 to +81 db. Overload protection. £12/10/- P. & P. 3/6.**



**TRANSISTOR FM TUNER**

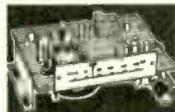

6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6in. x 4in. x 0 1/2in. 3 I.F. stages. Double tuned discriminator, ample output to feed most amplifiers. Operates on 9 volt battery. Coverage 88-108 Mc/s. Ready built ready for use. Fantastic value for money. £6/7/6. P. & P. 2/6. STEREO MULTIFLEX ADAPTORS, 99/6.

**SINCLAIR EQUIPMENT**

Project 60 range of new models now in stock  
Z30 Amplifier. Stereo 90 and P25 Power Supply (Carr. 7/6). £24/9/6  
Stereo 60 Control Unit. £28/19/6  
P25 Power Supply. £24/19/6  
P26 Power Supply. £27/19/6  
Q16 Speakers. £28/19/6

**SPECIAL PACKAGE OFFER!**

2 x Z30 Amplifier, Stereo 90 and P25 Power Supply (Carr. 7/6). £19  
or with 2 x Q16 Speakers (Carr. 7/6). £35  
Micromatic Radio Kit. £49/6  
Micromatic Radio Built. £59/6  
Sinclair IC10 in stock. £59/6  
9000 Amplifier £29/10/0. Carr. 7/6.  
Neoteric Amplifier £42/10/0. Carr. 7/6.

**ECHO HS-606 STEREO HEADPHONES**



Wonderfully comfortable. Lightweight adjustable vinyl headband, 6ft. cable and stereo jack plug, 25-17,000 cps., 8 Ω imp. 67/6. P. & P. 2/6.

**HOSIDEN DH04S 2-WAY STEREO HEADPHONES**



Each headphone contains a 2 1/2 in. woofer and a 1 in. tweeter. Built in individual level controls. 25-18,000 cps. 8 Ω imp. with cable and stereo plug. £5/19/6. P. & P. 2/6.

**HOSIDEN DH-02S STEREO HEADPHONES**



Wonderful value and excellent performance combined. Adjustable headband, 8 ohm impedance. 20-12,000 cps. Complete with lead and stereo jack plug. ONLY 47/6 P. & P. 2/6.

**TRANSISTORISED TWO-WAY TELEPHONE INTERCOM**



Operative over amazingly long distances. Separate call and press to talk buttons. 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £6/19/6 pair. P. & P. 3/6.

**TE111 DECADE RESISTANCE ATTENUATOR**

Variable range 0-111 db. Connections. Unbalanced T and Bridge T impedance 600 ohms. Range (0.1 db x 10) + (1 db x 10) + 10 + 20 + 30 + 40 db. Frequency: DC to 200 KHZ (—3db). Accuracy: 0.05 db. + indication db x 0.01. Maximum input less than 4 watts (50 volts). Built in 600 Ω load resistance with internal/external switch. Brand new £27/10/- P. & P. 5/6.

**RECORDING HEADS**

Cosmoord 1/2 track heads: Post extra. 85/-  
Record/Play. High imp. 20/-  
Eraser. Low imp. 20/-  
Marriott 1/2 track heads: Post extra.  
Record/Play track, high imp. 65/-  
Eraser. low imp. 20/-

**AMERICAN RECORDING TAPES**

3in. 225ft. L.P. Acetate 3/6  
First grade 3 1/2in. 600ft. T.P. Mylar 10/-  
quality 5in. 600ft. Std. plastic. 8/6  
American 6in. 900ft. L.P. acetate 10/-  
tapes. 6in. 1,200ft. D.P. Mylar 15/-  
Brand new 6in. 1,200ft. L.P. acetate 12/6  
and 6in. 1,200ft. L.P. Mylar 16/-  
guaranteed. 6in. 1,800ft. D.P. Mylar 22/6  
Discounts for quantities. 7in. 1,200ft. Std. acetate 12/6  
7in. 1,800ft. L.P. acetate 15/-  
7in. 1,800ft. L.P. Mylar 20/-  
Over £3 post paid. 7in. 2,400ft. D.P. Mylar 25/-  
7in. 3,600 ft. T.P. Mylar 45/-

**TAPE CASSETTES**

Top quality in plastic library boxes.  
C80—60 min. 8/6; 3 for 24/6.  
C90—90 min. 12/6; 3 for 36/-.  
C120—120 min. 15/-; 3 for 43/6.  
Cassette Head Cleaner 11/3 All Post Extra.

**G.W.S. SMITH & CO. (RADIO) LTD**

All Mail Orders to—  
147, Church Street, London, W.2  
Tel: 01-262 6562  
(Trade supplied)

3, LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204  
34, LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155  
311, EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387  
OPEN 9-6 MONDAY TO SATURDAY (EDGWARE ROAD 1/2 DAY THURSDAY)

# SUPER-BARGAIN STOCKTAKING SALE!!

Use form below for your order. **CONDENSERS MUST BE ORDERED BY STOCK NUMBER ONLY.**  
If any sale item is 'sold-out' when order received we shall substitute items of equal value.

## ELECTROLYTIC CAPACITORS

Stock No.	Capacity	Voltage	Price s. d.	No. Required	£ s. d.	Stock No.	Capacity	Voltage	Price s. d.	No. Required	£ s. d.
1	1 uf	6	4			45	350	12	9		
2	4 uf	25	4			46	20/4	275	1 0		
3	4 uf	4	4			47	250	50	2 0		
4	6 uf	6	4			48	500	25	1 6		
6	64 uf	9	4			49	400	15	1 0		
7	20 uf	6	4			50	400	2.5	3		
11	8 uf	6	4			51	64	275	1 9		
16	32	150	9			52	32/32	350	2 6		
17	64	2.5	3			53	8/8/8	275	1 9		
18	100/200/200/50	275	7 6			54	500	6	6		
19	50/80	300	3 0			55	64	275	1 3		
21	24	275	1 0			56	25	6	3		
22	10	25	3			57	100	9	6		
23	125	2.5	3			58	400	50	2 0		
25	16/32	350	2 6			59	400	30	1 6		
26	32	275	1 6			60	500	4	3		
28	75/75/75/75	150	2 6			61	150	30	1 6		
30	12.5	40	9			62	64/32/8	275	2 6		
32	3,000	35	7 6			64	40	6.4	3		
33	3,000	15	3 0			67	30	6	3		
34	3,000	30	7 0			68	100/100/50	275	5 0		
35	250	70	2 0			69	50/50/50	350	4 0		
36	2,500	9	2 0			70	40/40/20	275	2 0		
38	750	12	1 9			71	400	6.4	3		
39	100 uf	275	2 6			72	320	10	3		
40	30 uf	10	3			73	32/32	275	2 6		
42	16 uf	50 REV	2 0				+ 25	25			
43	16/16	275	2 0								
44	16	275	1 0								

Total:

## RESISTORS. EXCELLENT QUALITY. MAINLY 5%. 7/6d. per 100 of any one value.

2/- per dozen of any one value. Smaller quantities 3d. each.

Tick the values required:

13 ohms	560 ohms	3.3 k ohm	10 k ohm	39 k ohm	91 k ohm	1.2 meg ohm	8.2 meg ohm
22 ohms	750 ohms	3.6 k ohm	16 k ohm	43 k ohm	130 k ohm	1.5 meg ohm	9.1 meg ohm
36 ohms	1 k ohm	4.3 k ohm	18 k ohm	47 k ohm	360 k ohm	1.8 meg ohm	10 meg ohm
47 ohms	1.5 k ohm	4.7 k ohm	22 k ohm	51 k ohm	430 k ohm	3.6 meg ohm	
91 ohms	1.8 k ohm	5.6 k ohm	24 k ohm	62 k ohm	470 k ohm	5.1 meg ohm	
220 ohms	2.2 k ohm	6.8 k ohm	27 k ohm	75 k ohm	560 k ohm	6.2 meg ohm	
470 ohms	2.4 k ohm	7.5 k ohm	30 k ohm	82 k ohm	620 k ohm	7.5 meg ohm	

or our selection (mixed) 6/6d. per 100.

Total:

## SILVER MICA/CERAMIC/POLYSTYRENE CONDENSERS. 10/- per 100 of any one value. 3/- per dozen of any one value. Smaller quantities 6d. each. As available. In following values. Tick those required.

2 pf	5 pf	12 pf	25 pf	50 pf	80 pf	135 pf	180 pf	250 pf	680 pf	1,000 pf	2,500 pf
3.9 pf	6 pf	15 pf	27 pf	58 pf	82 pf	140 pf	190 pf	330 pf	800 pf	1,100 pf	2,700 pf
4 pf	8 pf	18 pf	30 pf	62 pf	100 pf	158 pf	200 pf	450 pf	820 pf	1,500 pf	3,000 pf
4.7 pf	10 pf	22 pf	39 pf	72 pf	125 pf	170 pf	240 pf	600 pf	900 pf	2,200 pf	6,200 pf

Total:

# COMPARE THESE PRICES!!

## MULLARD POLYESTER CONDENSERS

No.	Price
1,000 pf	3d. each
1,500 pf	3d. each
1,800 pf	3d. each
2,200 pf	3d. each
.15 uf	6d. each
.22 uf	6d. each
.27 uf	6d. each
1 uf	1/- each

Total:

25% discount lots of 100 per type.

50% discount lots of 1,000 per type.

**TRANSISTOR BARGAIN! THEY CAN'T GET ANY CHEAPER! ! ! !**

P.N.P. Audio. Untested, unmarked. MAINLY O.K. 10/- per 100

N.P.N. Silicon. R.F. types unmarked ALL USEABLE 10/- per 50

POWER OUTPUT (Similar OC35) ALL TESTED 4/- each £2 dozen

SILICON PLANAR TRANSISTORS. ALL TESTED. NO LEAKS OR

SHORTS. Gain of 20/50 6d. each, 50/100 9d. each, 100/200 1/- each.

**LIGHT SENSITIVE TRANSISTORS, 2/- each.**

**LIGHT SENSITIVE DIODES**

Can be used to control any transistorised device, 1/- each.

75/- per 100. £25 per 1,000.

**THYRISTORS.** 400 volt BTY 79 7/6d. each. SCR 51 (10 amp) £1 each.

**RECTIFIERS.** Latest type. All marked. 800 volt peak, 1 amp mean current

type 1N4006. 2/6 each, 24/- dozen, £7/10/- 100. S.T.C. 3/4 (400 volt)

2/6 each, 24/- dozen, £7/10/- 100. BYZ 13 or 19 (6 amp) 2/6 each, 24/- dozen,

£7/10/- 100.

BY 127 2/6d. each. 24/- dozen. £7/10/- per 100. £50 per 1,000.

**RECORDING TAPE GIVE-AWAY! ALL BRITISH MADE, BEST**

**QUALITY!**

5" Standard .. .. . 7/6d.

5 1/2" Standard .. .. . 9/-

7" Standard .. .. . 12/-

3" "Oddends" Minimum 150 2/3d.

**MAINS DROPPER TYPE RESISTORS.** Hundreds of types from .7 ohm

upwards. 1 watt to 50 watts. A large percentage of these are Multi-tapped

droppers for radio/television. Owing to the huge variety these can only be

offered "assorted". 10/- per dozen.

**GIANT SELENIUM SOLAR CELLS.** Last few to clear at half price!

Circular, 67 mm. diameter 5/- each. 50 mm. x 37 mm. 3 for 10/-.

## SKELETON PRESETS. Mixed. 6/- dozen.

**VOLUME CONTROLS.** 1/2 meg. 1 meg. with D.P. switch 5k. (No switch) all 2/-

**RECORD PLAYER AMPLIFIERS.** All transistor. Complete with screened

input lead, volume control and speaker leads. This excellent unit also has built-in

rectifier and smoothing components enabling same to be used direct on 6 to

9 volt A.C. supply. Small number only! Cannot be repeated at this price! 30/- ea.

**TRANSISTOR RADIOS.** Fantastic bargain! Tremendous value! Superb

quality sound from large speaker! Excellent sensitivity! Complete with earpiece,

battery and plastic carrying case, all packed in a colourful presentation box.

You would expect to pay £5—but our price due to huge purchase is only 37/6d.!

**CO-AXIAL CABLE.** Semi-air spaced. 8d. yard. 60 yd. rolls 30/- Postage 4/6d.

**CRYSTAL TAPE-RECORDER MIKES, 12/- each. CRYSTAL EAR-**

**PIECES WITH PLUG, 5/- each. Magnetic earpieces. No plug. 1/6d. each.**

**THIN CONNECTING WIRE.** 10 yds 1/-, 100 yds 7/6d., 1,000 yds. 50/-.

**RECORD PLAYER CARTRIDGES**

ACOS GP67/2 15/- (Mono) GP94/1 30/- (Stereo, ceramic)

ACOS GP91/3 20/- (Compatible) ACOS GP93/1 with diamond needle 32/6d.

ACOS GP93/1 25/- (Stereo) ACOS GP94/1 with diamond needle 37/6d.

**TRANSISTORISED FLUORESCENT LIGHTS. 12 VOLT**

8 watt 12" tube, Reflector type 59/6 15 watt 18" tube, Batten type 79/6

Complete with tube. Postage 3/-

**TRANSISTORISED SIGNAL INJECTOR KIT .. .. . 10/-**

**TRANSISTORISED SIGNAL TRACER KIT .. .. . 10/-**

**TRANSISTORISED REV. COUNTER KIT (CAR) .. .. . 10/-**

**VERO-BOARD**

2 1/2" x 1" x .15 .. .. . 1/3

3" x 2 1/2" x .15 .. .. . 3/3

3 1/2" x 3" x .15 .. .. . 3/11

5" x 2 1/2" x .15 .. .. . 3/11

5" x 3" x .15 .. .. . 5/6


17" x 2 1/2" x .15 .. .. . 11/-

Spot Face Cutter 7/6d. Pin Insert Tool 9/6d. Terminal Pins 3/6d. for 36.

Spot Face Cutter and 5 2 1/2" x 1" boards 9/9d.

These prices cannot be repeated. Order now. Don't forget to add your name and address!  
Please include suitable amount to cover post and packing. Minimum 2/-.

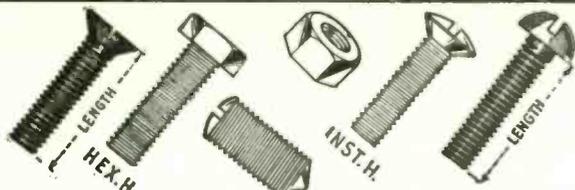**G. F. MILWARD, DRAYTON BASSETT, near TAMWORTH, STAFFS. Phone: TAMWORTH 2321**



We supply B.A. Screws, etc. in brass, steel, stainless, phosphor bronze and nylon to laboratories throughout the Commonwealth.

We can also offer early delivery for many sizes of screws, etc. with Metric Threads

Please send for List W2/69 (WW)

**WALKER-SPENCER COMPONENTS LTD.**  
 5, High Street, Kings Heath, Birmingham, 14.  
 Telephone: 021-444 3155 (Sales) and 5278

WW-124 FOR FURTHER DETAILS



**SANWA MULTI TESTERS**

USED THROUGHOUT THE WORLD. SANWA'S EXPERIENCE OF 30 YEARS ENSURES ACCURACY, RELIABILITY, VERSATILITY, UNSURPASSED TESTER PERFORMANCE COMES WITH EVERY SANWA.

6 Months Guarantee. Excellent Repair Service

Model P-1B	£3 7 6	Model K-30THD	£12 0 0
Model J-50	£5 10 0	Model F-80TRD	£15 15 0
Model U-50DN	£7 10 0	Model 380-CE	£15 2 6
Model 360-YTR	£7 17 6	Model 430-ES	£19 0 0
Model A-303TRD	£10 10 0	Model EM-700	£51 0 0
Model AT-J	£11 7 6		

Cases available with most meters

MODEL 360-YTR PLEASE WRITE FOR ILLUSTRATED LEAFLETS OF THESE SANWA METERS

**SOLE IMPORTERS IN U.K.;**  
**QUALITY ELECTRONICS LTD.**  
 47-49 HIGH STREET, KINGSTON-UPON-THAMES, SURREY. Tel: 01-546 4585

WW-125 FOR FURTHER DETAILS

**4-STATION INTERCOM**



Our Price Only **£7/15/0**

Solve your communication problems with this new 4-Station Transistor Intercom system (1 master and 3 subs), in de luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Operates on one 9 v. battery. On/off switch. Volume control. Ideally suitable to modernise Office, Factory, Workshop, Warehouse, Hospital, Shop, etc., for instant inter-departmental contacts. Complete with 3 connecting wires, each 66ft. and other accessories. Nothing else to buy. P. & P. 7/6 in U.K.

**INTERCOM/BABY ALARM**



OUR PRICE ONLY **3gns.**

Same as 4-Station Intercom for two-way instant conversation from MASTER to SUB and SUB to MASTER. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 2/6. P. & P. 4/6.

**MAINS INTERCOM**

No wires—no batteries. Just plug in and it is ready to use. Room to room or house to house. Both units must be on the same side of power line distribution. Lock button. Uselul as baby alarm. Price per pair £11.19.6. P. & P. 8/6.

**Transistor TELEPHONE AMPLIFIER**



**59/6**

Why not increase efficiency of Office, Shop and Warehouse with this incredible De-Luxe Portable Transistor **TELEPHONE AMPLIFIER** which enables you to take down long telephone messages or converse without holding the handset. A useful office aid. A must for every telephone user. Useful for hard of hearing persons. On/off switch. Volume Control. Operates on one 9 v. battery which lasts for months. Ready to operate. P. & P. 3/6 in U.K. Add 2/6 for Battery.

Full price refunded if returned in 7 days.

**WEST LONDON DIRECT SUPPLIES (W.W.),**  
 169 Kensington High Street, London, W.8

**ATES**  
 PRONOUNCED R-TEZ

**SEMICONDUCTORS**

Write now for catalogue

**ATES ELECTRONICS LTD., MERCURY HOUSE,**  
 PARK ROYAL, LONDON W5  
 TEL: 01-998 6171 TELEX: ATES LONDON 262401

WW-119 FOR FURTHER DETAILS

**MINIFLUX** audio magnetic recording  
 MANUAL VOL. 1.

A complete set of Laboratory Application Reports on the replay of audio magnetic recordings.

Packed with hitherto unpublished information. Full constructional details are included for several high quality pre-amplifiers of advanced design as well as multi-channel integrated circuit modules. Each design step is thoroughly discussed and supported by detailed test measurements and calculations.

Size A4. 131 Pages. Price 31s. 6d. inc. UK postage.

Direct from the Publishers:

**MINIFLUX ELECTRONICS LIMITED,**  
 8 Hale Lane, London, N.W.7, ENGLAND.



WW-120 FOR FURTHER DETAILS

**Lasky's**  
**AUDIO TRONICS**  
**1970**

The 1970 edition of Lasky's famous Audio Tronics catalogue is now available—FREE on request. The 28 tabloid pages—equal to over 100 pages of our normal "WW" advertising—are packed with 1,000's of items from the largest stocks in Great Britain of everything for the Radio and Hi-Fi enthusiast. Elec-tronics Hobbyist, Servicemen and Communications Ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals), tape recording and Audio accessories **PLUS** Lasky's amazing money saving vouchers worth over £25. All the goods shown are available from any of our branches or by Mail Order—bringing the benefits of shopping at Lasky's to you in the comfort of your home. Over 150,000 customers have already received their copy of the 'Audio Tronics' catalogue—don't delay.

Send: Your name, address and 2/- to cover post only and the inclusion of your name on our regular mailing list.

**Lasky's Radio Limited**  
 3-15 Cavell Street, London, E.1.

**36 YEARS**  
 LASKY'S RADIO ESTABLISHED OVER



KING OF THE PAKS Unequaled Value and Quality SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Table listing various semiconductor components like diodes, transistors, and rectifiers with their respective part numbers and prices.

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

BI-PAK SEMICONDUCTORS (DEPT. W.W.)

NEW LOW PRICE TESTED S.C.R.'S

Table showing specifications for Silicon Controlled Rectifiers (SCRs) with 1 Amp, 3 Amp, 7 Amp, 16 Amp, and 30 Amp ratings.

UNIUNION

UT46 Eqt. 2N2848, Eqt. T1843 BEN3000 5/8 25-99 5/-, 100 up 4/- each

F.E.T.'s To-18 case. FE18. Eqt. 2N3819, MPF105, etc. 7/8 each. Data supplied.

FULL RANGE OF ZENER DIODES

VOLTAGE RANGE 2-18V. 400mV (D0-7 Case) 2/8 ea. 1-5W (Pop-Hat) 3/8 ea. 10W (80-10 Stud.) 5/- ea. All fully tested 5% tol. and marked. State voltage required.

BRAND NEW TEXAS GERM. TRANSISTORS

Table listing Germanium transistors with part numbers like T1, T2, T3, T4, T5, T6, T7, T8, T9, T10 and their prices.

ALL 10/- EACH PAK

2N3055 115W SIL. POWER NPN ORT. PRICE 12/6 each

120 VCB NIXIE DRIVER TRANSISTOR

2N1693 FULLY TESTED AND CODED WARE. HERTS. Postage and packing still 1/- per order. Minimum order 10/-

FREE Pack of your own choice free with orders valued £4 or over.

I.C. AMPLIFIER



Identical encapsulation and pin configuration to the following: SL402-3, IC10 and IC408. Each circuit incorporates a pre-amp and class A.B. Power amp stage capable of delivering up to 3 watts RMS. Fully tested and guaranteed. Supplied complete with circuit details and data. CODED BP1010. OUR LOWEST PRICE 30/- each. 10 up 25/- each

OTHER MONOLITHIC DEVICES

BP424, Zero voltage switch. 8/8 each. This device is a monolithic I.C. that acts as a combined threshold detector and trigger circuit for controlling a triac. It is designed to pulse the gate of a thyristor at the point of zero supply voltage, and therefore eliminate radio frequency interference when used with resistive loads. D1SD1 Silicon Unilateral switch 10/- each

MULLARD I.C. AMPLIFIERS

TAA245, Operational amplifier, 70/- each. TAA263, Linear AF amplifier, 18/6 each. TAA293, General purpose amplifier, 21/- each.

QUALITY-TESTED PAKS

Large table listing various semiconductor components like diodes, transistors, and rectifiers with their respective part numbers and prices.

BI-PAK GUARANTEE SATISFACTION OR MONEY BACK

Wilkinsons FOR RELAYS

P.O. TYPE 3000 AND 600 BUILT TO YOUR REQUIREMENTS - QUICK DELIVERY COMPETITIVE PRICES - VARIOUS CONTACTS DUST COVERS - QUOTATIONS BY RETURN LARGE STOCKS HELD OF G.E.C. MINIATURE SEALED RELAYS

EQUIPMENT WIRE P.V.C. covered 80/- per 1000 yds. 71.0076, 1/1.024, 141.0046 type 1 and 2, all colours. 141.0076 type 11 Red and Natural £14 per 1,000 yds.

MINIATURE SILVER ZINC ACCUMULATOR. 1.5 volt, 1.5 ampere. Size 2x1.13x0.63in. Weight 1 1/2 oz. Ideal for model work, 12/6 each. 120/- doz. post 1/6.

SUB-MINIATURE LAMPS. Flying leads, 0.75 v. 50/- 100. LEDEX ROTARY SOLENOIDS AND CIRCUIT SELECTORS. SIZE 5s. 4 pole, 11 way and off 110/-, 4 pole, 12 way 110/-, 24 pole, 11 way and off 210/-, 54 pole On/Off 150/-.

SOLENOIDS type 3E in stock at 17/6 each. CERAMIC AND PAXOLIN WAFER SWITCHES available from stock at keener prices. send for list. 24 way Double Pole Pax Wafer Switches 12/6 each, post 2/6. P.O. STANDARD EQUIPMENT RACKS 6ft. U channel sides drilled for 19in. panels heavy angle base. 150/-, cge 20/-.

ONE HOLE FIXING SWITCHES DOUBLE POLE ON/OFF 3 amp 250 volt A.C. 1 1/2 in. x 3/4 in. x 1 in. 30/- per dozen, 200/- per 100. Post 3/- per dozen, 6/- per 100.

AIR BLOWERS. 200/250v. A.C. cylindrical 7in.-7 1/2in. suitable for intake or extraction. 1/50th h.p. £10. 1/15th h.p. £11. 1/10th h.p. £14. Stockists of Stuart Turner Centrifugal Pumps. Nos. 9, 10 and 12, Details available.

GEARED MOTORS. 1 r.p.m. or 3 r.p.m. 4 watts very powerful, reversible 24v. A.C. 35/-, post 2/6. can be operated from 230v. with our A.C. Transformer. Post 5/-.

STANDARD LEVER KEYS, 3 POSITION 4C lock/4C lock 17/6 each. Stop/6C 13/6 each. 2C 2M non-lock/2C 2M non-lock 14/6 each. 4C non-lock/6C lock 20/- each.

ONE HOLE FIXING. Step/4 C.O. non-locking 2 position 10/6. 6 C.O. lock/2 C.O. lock 3 position 17/6.

VACUUM GAUGES. 2in. scaled. 0/30 inches of mercury, 20/- each, post 2/6.


PRESSURE GAUGES. 2 1/2in., 60, 250, 400 or 600 p.s.i., 25/- each. 4in. flange 30, 60, 300 p.s.i., 37/6, 100 p.s.i. with 0/30ins. vac. 37/6, 200 p.s.i.

BATTERY CHARGERS at special price made by Westinghouse, worth £35. Input 200/250v. A.C. output 6v. 15 amps D.C. with ammeter, fuses; regulated by a 4-position switch and sliding resistance. OUR PRICE 170/-, Csa. 20/-.

MINIATURE 1/2in. IN LINE DIGITAL DISPLAY UNIT, an assembly of five units each displaying 0 through 9 with right and left hand decimal points, words and other characters also available; quick disconnect at the rear for lamp replacement, it's lightweight only 1 1/2 oz., send for full details.

HIGH SPEED COUNTERS

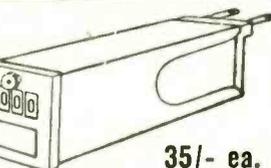3 1/2 x 1 1/2in. 10 counts per second with 4 figures. The following D.C. voltages are available, 6v., 12v., 24v., 50v. or 100v.



35/- ea.

SUB-MINIATURE Microswitch Honeywell S.P.D.T. type 11 SM1 TN 13 size 1/2 in. x 3/4 in. x 3/8 in. 6/6 each, or mounted in frames for 22/6 post free.

JACK PLUGS. 2 Point with screw-on cover, 2/6, post 9d. PO 201 on telephone cord 3/-, post 1/6.

PLUG-IN RELAYS. Londex 4 change-over HD contacts 28v. D.C. with base and cover, 35/- each.

UNISELECTORS. New 8 bank, 25 way, non-bridging full wipers, £7.10 each.

VARLEY Miniature Relays. 700 ohms 4 CO, 15/6 ea.

MINIATURE BUZZERS. 12 volts with tone adjuster, 7/6 each as illustrated. Special rates for quantities.

FOR MANUFACTURERS, LOW PRICE SEMICONDUCTORS: TEXAS INSTS 2N1305, 3,000 available 3/- ea. MULLARD AS220, 3,000 available 6/6 ea. MULLARD GET 875, 1,000 available 6/- ea. Send for Complete Stock List.

MAGNETIC COUNTERS. Veed - Root with zero reset. 800 counts per minute, counting to 999,999. 110 or 120 volts A.C. 110 volts D.C. 65/- each, post 3/-.

PRECISION GERMAN MADE MAGNETIC COUNTERS. 2 1/2in. x 1 1/2in. x 1in. with push button zero reset. 3 digits, 12 volts D.C., 25 imp/sec., 50/- ea.

METERS GUARANTEED. Complete list available. Microamps 0/500 2in. MC. ... 25/- Microamps 0/500 2 1/2in. MC. ... 37/6 Milliamps 0/50 2 1/2in. MC. ... 35/- Milliamps 0/50 3 1/2in. MC. ... 54/- Amps 50-0-50 2in. MC. ... 17/6 Amps 0/5 2in. MC. ... 42/6 Volts 5/0/5 2 1/2in. MC. ... 25/- Volts 0/20 2in. MC. ... 42/6 Volts 0-40 2in. MC. ... 42/6 Volts 0/10 A.C. 3 1/2in. MCR. ... 70/-

"VISCON-CATHODRAY" CONDENSERS. 002 mfd. 15 kV, 9/-; 02 mfd. 10 kV, 10/-; 025 mfd. 2.5 kV, 8/-; 05 mfd. 5 kV, 9/-; 0.1 mfd 4 kV, 9/-; 6 kV, 17/6; 0.5 mfd. 2.5 kV, 17/6; 1 mfd. 2kV, 17/6.

PORTABLE VOLTMETERS 30v moving coil DC precision sub standard grade 5in. mirror scale, in polished wood case £8.17.6, post 8/6; 150v moving iron AC/DC 8in. mirror scale in p. wood case £4.19.6, post 7/6; 250v moving iron AC/DC 6in. scale in p. wood case £8.10.0, post 7/6.

CELL TESTING VOLTMETERS 3-0-3 v moving coil DC with leads and prods. in leather case 3in. scale 35/- ea., post 4/6

CAMBRIDGE PORTABLE MILLIAMMETER precision 7in. scale ranges-50, 100, 200, 500 and 1,000 mA. enclosed case £25, post 10/6.

PORTABLE AMMETERS 0-3 A. moving iron AC/DC 3in. scale in case, 35/- ea., post 4/-

MEGGERs, SERIES 2. 500 volts, range 0/100 Meg ohms-infinity. Metal case. Complete with test leads in leather case with strap £37.10, cge 2/6.

ELLIOTT CENTURY TEST SETS. First-grade, reading Absolute. D.C. volts .075, 3, 30, 150, 300 and 750 (FSD 20mA) and Absolute D.C. amps 1.5, 15, 150 and 600 (75 mV) on 5in. Mirror scale. Wood case, with shunts in fitted compartment. £25, cge 15/-.

L. WILKINSON (CROYDON) LTD. LONGLEY HOUSE LONGLEY RD. CROYDON SURREY

Phone: 01-684-0236 Grams: WILCO CROYDON

**FLUORESCENT CONTROL KITS**

Each kit comprises seven items—Choke, 2 tube ends, starter, starter holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Girolux" tubes for fish tanks and indoor plants. Chokes are super-silent, mostly resin filled. Kit A—15-20 w. 19/8. Kit B—30-40 w. 19/8. Kit C—80 w. 23/6. Kit E—65 w. 19/8. Kit MF1 for 6in., 9in. and 12in. miniature tubes, 19/8. Postage on Kits A and B 4/6 for one or two kits then 4/6 for each two kits ordered. Kits C, D and E 4/6 on first kit then 3/6 for each kit ordered. Kit MF1 3/6 on first kit then 3/6 on each two kits ordered.

**REED SWITCHES**

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types: **Miniature.** 1in. long x approximately 1/4in. diameter. Will make and break up to 1A up to 350 volts. Price 2/6 each, 24/- dozen. **Standard.** 2in. long x 3/16in. diameter. This will break currents of up to 1A, voltages up to 250 volts. Price 2/- each, 18/- per dozen. **Flat.** Flat type, 2in. long, just over 1/16in. thick, approximately 1/4in. wide. The Standard Type flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1 amp 200 volts. Price 6/- each, 23/- per dozen. Small ceramic magnets to operate these reed switches 1/8 each, 18/- dozen.

**TELESCOPIC AERIAL**

For portable, car radio or transmitter. Chrome-plated—six sections extends from 7 1/4 to 47in. Hole in bottom for 6BA screw, 7/8.

**TOGGLE SWITCH**

3 amp 250v. with fixing ring, 1/6 each 15/- doz.

**MINIATURE EAR PIECE**

As used with imported pocket radios, 1/6 each 15/- doz.

**ISOLATION SWITCH**

20 Amp D.P. 250 Volts. Ideal to control Water Heater or any other appliance. Neon indicator shows when current is on. 4/6 48/- per dozen.

**15/20 AMP CONNECTORS**

Polythene insulated 12-way strip, 2/6 each 24/- doz.

**13 AMP FUSED SWITCH**

Made by G.E.C. For connecting water heater etc., into 13 amp ring main. Flush type 3/6 each 30/- doz. Metal boxes for surface mounting 1/6 each 15/- doz.

**MICRO SWITCH**

5 amp. changeover contacts, 1/9 each 18/- doz. 15 amp model 2/- ea. or 21/- doz.

**SUPPRESSOR CONDENSER TCC**

1 mfd. 250v. A.C. working metal cased with fixing lug, 1/9 each 18/- doz.

**REED RELAY**

Glass encapsulated reed switch in 24-volt solenoid, neatly enclosed in neat metal case, size 2 1/4in. x 1 1/4in. x 1 1/4in. 3/6 each. Operates from 24 volts D.C. or from A.C. mains using rectifier, resistor and condenser (3/6 extra).

**SHEET PAXOLON**

Ideal for transistor projects, panels 12in. x 6in., 1/9 each, 15/- per dozen.

**G.E.C. MULTIPLE SWITCHES**

Metal boxes (with cable knockouts) sprayed silver with cover and switch mounting grid. For 12 switches 6/-, 6 switches 5/-, 4 switches 4/-, 2 switches 3/6.

**G.E.C. Clipper Switches**

For the above boxes, 5 amp A.C. rating, one-way 1/8, 2-way 2/-. Bell push 2/-. Intermediate 2/6, secret 2/6, 15 amp one-way 2/6.

**THERMOSTAT**

Continuously variable 30°-90°C. Has sensor bulb connected by 33in. of flexible tubing. On operation a 15 amp 250 volt switch is opened and in addition a plunger moves through approx. 1/4in. This could be used to open valve on ventilator etc. 29/6 plus 4/6 p. & ins.

**HI FI BARGAIN**


**FULL F1 12-INCH LOUDSPEAKER.** This is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi load and Rhythm Guitar and public address. Flux Density 11,000 Gauss—Total Flux 44,000 Max. Power Handling 15 watts R.M.S.—Cone moulded fibre—Freq. response 30-10,000 c.p.s.—specify 3 or 15 ohms—Main resonance 60 c.p.s.—Chassis Diam. 12in.—12" over mounting lugs—Baffle hole 11in. Diam.—Mounting holes 4, holes 1in. diam. on pitch circle, 11in. diam.—Overall height 4in. A 29 speaker offered for only 23.19.6 plus 7/6 p. & p. Don't miss this offer. 15in. 25 watt 27.19.6. 18in. 100 watt 27.19.10.

**RING MAIN JUNCTION BOXES**

Made by Rock. This won Design Award for making quick and neat junctions in 9,029 twin and earth cable as used for ring main circuits. Our price 1/6 each, 15/- per dozen.

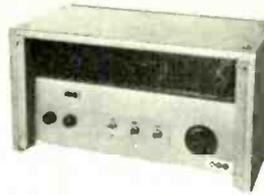**ERGOTROL UNITS**

These units made by the Mullard Group are for operating and controlling d.c. Motors and equipment from A.C. mains. Thyristors are used and these supply a variable d.c. resulting in motor speed control and operating efficiency far superior to most other methods. The units are contained in wall mounting cabinets with front control panel on which are fuses—push buttons for on/off and the variable thyristor firing control. 4 models are available—all are brand new in makers cases: Model 2410 for up to 5 amps £17.10.0 Model 2411 for up to 10 amps £27.10.0 Model 2413 for up to 45 amps £47.10.0 Model 2415 for up to 80 amps £95. 0.0 Note: 2415 is a floor mounting unit.



**MINIATURE EXTRACTOR FAN**

Beautifully made by famous German Company, PAPST System, 230/240 A.C. Mains operated, size 3 1/4in. x 3 1/4in. x 2in. Made for instrument cooling but ideal to incorporate in a cooker hood, etc. 65/- P. & p. 2/9.



**DISTRIBUTION PANELS**

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work 39/6 less plug, 45/- with fitted 13 amp plug, 47/6 with fitted 16 amp plug, plus 4/6 P. & I.



**STANDARD WAFER SWITCHES**

Standard size 1 1/2 wafer—silver-plated 5-amp contact, standard 1/2" spindle 2" long—with locking washer and nut.

No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	10 way	12 way
1 pole	6/8	6/8	6/8	6/8	6/8	6/8	6/8	6/8
2 poles	6/8	6/8	6/8	6/8	6/8	6/8	10/8	10/8
3 poles	6/8	6/8	6/8	6/8	10/8	10/8	14/8	14/8
4 poles	6/8	6/8	6/8	10/8	10/8	10/8	18/8	18/8
5 poles	6/8	6/8	10/8	10/8	14/8	14/8	22/8	22/8
6 poles	6/8	10/8	10/8	10/8	14/8	14/8	26/8	26/8
8 poles	6/8	10/8	10/8	14/8	18/8	18/8	30/8	30/8
9 poles	10/8	10/8	14/8	14/8	18/8	18/8	34/8	34/8
10 poles	10/8	10/8	14/8	18/8	22/8	22/8	38/8	38/8
11 poles	10/8	14/8	14/8	18/8	26/8	26/8	42/8	42/8
12 poles	10/8	14/8	14/8	18/8	26/8	26/8	50/8	50/8

**24 HOUR TIME SWITCH**

Mains operated. Adjustable Contacts give on/off per 24 hours. Contacts rated 15 amps, repeating mechanism so ideal for shop window control, or to switch hall lights (anti-burglar precaution) while you are on holiday. Made by the famous Smiths Company. This month only 39/6 complete with perspex cover, new and unused, plus 3/6 postage and insurance, a real snip which should not be missed.



**THIS MONTHS SNIP**

**1 HOUR MINUTE TIMER**

Made by famous Smiths company, these have a large clear dial, size 4 1/4in. x 3 1/4in., which can be set in minutes up to 1 hour. After pre-set period the bell rings. Ideal for processing, a memory logger or, by adding simple lever, would operate micro-switch. 22/6.



**1 WATT AMPLIFIER & PRE-AMP**

5 transistors—highly efficient made for use with tape-head G4 but equally suitable for microphone or pick up. Limited quantity 29/6. Full circuit diag. also shows tape controls 5/-.



**VARIAC CONTROLLERS**

With these you can vary the voltage applied to your circuit from zero to full mains without generating undue heat. One obvious application therefore is to dim lighting. We offer a range of these, ex-equipment but little used and in every way as good as new. Any not so, will be exchanged or cash refunded. 2 amp 24.19.6. 5 amp 27.19.6. 8 amp 27.19.6. 10 amp 27.19.6.



**HOUR COUNTERS**

If you wish to know how long your equipment has been switched on then this is what you need. Counts running time up to 999 hours, 50 c/s mains operation. 49/6 plus 3/6 post and insurance. Resettable type 69/6 plus 3/6 post and insurance.

**THE PECTRON HEATING/VENTILATING CONTROL**

This neat unit contains all the controls needed for a gas-fired central heating system as follows:—

- (a) A clock switch giving 2 on/off periods per 24 hours.
  - (b) A thermal delay switch to prevent cold air being blown while fire warms up.
  - (c) Auto transformer to vary voltage and thus control fan speed.
  - (d) A 24-volt transformer to provide the low voltage necessary to operate solenoid of gas valve.
  - (e) A changeover switch to bypass the clock.
  - (f) Changeover switch to cut off heat so allowing cold air to be blown for Summer ventilation.
  - (g) Neon indicator and fuses.
- The unit has a circuit diagram and five leads labelled "Mains," "Fan," "Thermostat 1," "Thermostat 2," "Gas valve." 25.19.6 plus 4/6 postage and insurance.



**INFRA RED MONSCOPE**

This equipment is complete and portable. Basically it consists of an infra red image converter tube with optical lenses for focusing the image and a Zamboni pile to provide the necessary E.H.T. The monoscope is housed in a hide case size 9 x 6 x 4in. approx. Made originally for the army for night observations, sniping etc., this equipment has many scientific and practical applications; a limited quantity only is available in original sealed carton. Price 28.19.6. **NOTE.** Although unused in fact still in original sealed cartons. The equipment is approx. 25 years old and consequently the Zamboni pile may not now be operative. Drying out might help but a better idea might be to replace it with a battery operated power unit; there is plenty of room.



Where postage is not stated then orders over £3 are post free. Below £3 add 2/9. Semi-conductors add 1/- post. Over £1 post free. S.A.E. with enquiries please.

**MINIATURE WAFER SWITCHES**

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 6 way—1 pole, 12 way. All at 3/6 each, 36/- dozen. Your assortment.



**WATERPROOF HEATING ELEMENT**

26 yards length 70W. Self-regulating temperature control. 10/- post free.

**DRILL CONTROLLER**

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions 19/8, plus 2/6 post and insurance. Made up model also available 37/8 plus 2/6 p. & p.



**MAINS MOTOR**

Precision made—as used in record decks and tape recorders—ideal also for extractor fans, blower, heater, etc. New and perfect. Snip at 9/6. Postage 3/- for first one then 1/- for each one ordered. 12 and over post free.




**ELECTRIC CLOCK WITH 25 AMP SWITCH**

Made by Smith's, these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only 39/6, less than the value of the clock alone—post and insurance 2/9.



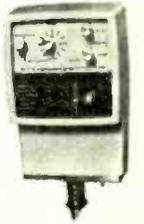**COOKER CLOCK with temperature controller**

Cooker clock with temperature controller. This is as the clockswitch described above but with additional panel which incorporates oven thermometer and thermostatic switch. The thermostat switch may be set anywhere between 50°C. and 90°C. Made for high-class continental cooker, this is a very fine instrument. 24.19.6, plus £1.10.0 for oven sensor unit.



**THERMAL CUTOUT**

A miniature device (1/2in. dia.) on one screw fixing mount—can be used for motor overload protection—fire alarm—soldering iron switch off, etc.—16 amp contacts open with flame radiant or conducted heat. 1/6 each, 15/- doz. 25 10/0.

**COPPER CLAD ELEMENT**

1250 watts—4ft. long but bent to U shape, ideal for overhead heater—just mount reflector above. 12/6 each, plus 4/6 post. 26 doz. post paid.

**0-0005mFd TUNING CONDENSER**

Proved design, ideal for straight or reflex circuits 2/6 each, 24/- doz.



**SUB-MINIATURE MOVING COIL MICROPHONE**

As used in behind the ear deaf aids Acts also as earphone size only (1/2in. x 1/4in. x 1/4in. Regular price probably £3 or more. Our price 19/6. Note these are ex-equipment but if not in perfect working order they will be exchanged.

**MAINS TRANSISTOR POWER PACK**

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 16/6, plus 3/6 postage.

**PP3 BATTERY ELIMINATOR**

Run your small transistor radio from the mains—full wave circuit. Made up ready to wire into your set and adjustable high or low current. 8/6 each.



85 Watt Tubular Element. Very well made unit. The element is wound on a porcelain former then encased in a brass tube terminated with better leads 12in. long. Normal mains voltage. Price 5/- each or 54/- per doz.

250V AC working condensers for power factor correction, motor starting etc. 3.3 mfd. 6/6 ea., 6.5 mfd. 8/6 ea., 8 mfd. 9/6 ea.

3 amp battery charger kit comprises copper backed circuit board, 3 amp mains transformer, regulator resistors and smoothing condenser 29/6 inc. wiring diagram, post & ins, 4/6.

**BALANCED ARMATURE**

500 ohm, operates speaker or microphone, so useful in intercom or similar circuits. 6/6 ea., 23.10.0 doz.



Acos crystal microphone. Adjustable stand converts this from hand mic. to desk mic. 19/6 ea.

**HEAVY DUTY POWER PACK** 40V 6 amps DC output—comprises 1st class mains transformer with normal primary, screen 20-0-20 6-amp output. Fully smoothed. Completely wired ready to work 23.19.6 + 8/6 p. & i.

**ELECTRONICS (CROYDON) LTD**  
Dept. WW, 266 London Road, Croydon CRO-2TH  
Also 102/3 Tamworth Road, Croydon

**ISOLATING/STEP DOWN TRANSFORMER**


Primary 0, 240v., Sec. 0, 115, 240v. 10a. Ideal for workshop supply, only 6in. x 7in. x 7in. £8, carr. 20/-.

**STEP DOWN TRANSFORMER**

Primary 0, 240v., Secondary 0, 115v. 300 watts (conservatively rated). 4½in. x 4in. x 4in. 45/-, p. & p. 8/-.

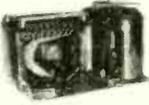**12v. 4a. POWER SUPPLY**

Brand new, weighs 11 lb. Constant voltage transformer, input 0 - 112.5 - 123.5 - 195 - 220 - 235v., produces 12v. 4a. capacitor smoothed output. £9.10.0 plus 10/- carr.



**EX-COMPUTER POWER SUPPLIES**

Reconditioned, fully tested and guaranteed. These very compact units are fully smoothed with a ripple better than 10mv. and regulation better than 1%. Over voltage protection on all except 24v. units. 120v. - 130v. a.c. 50c/s input. Mains transformer to suit £3 extra if required.

We offer the following types:

6v. 8a. £10	20v. 15a. £15
6v. 15a. £14	30v. 7a. £12
12v. 20a. £16	24v. 4a. £14

Carriage 15/- per unit

**DIODES EX EQUIP, SILICON**

150 PIV 10 amp. . . . .	4 for 10/-
150 PIV 20 amp. . . . .	4 for 20/-
400 PIV 35 amp. . . . .	4 for 45/-

p. & p. 1/-

**LARGE CAPACITY ELECTROLYTICS**


4½in., 2in. diam. Screw terminals. Top quality German manufacture. Will withstand short circuit discharge.

4,000µF 72v. d.c. wkg.
16,000µF 12v. d.c. wkg.

7/6 each, p. & p. 1/-  
£3.10.0 doz., p. & p. 10/-.

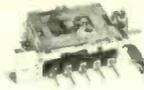**PYE CAR RADIO Push Button Tuning Heart**

This PRESTOLOCK 5 station Push-Button Tuner Heart with Manual Over-ride is an ideal basis for a quality AM car radio. Size 6½in. x 4in. x 2in. 25/- plus 3/- p. & p.



**RELAY OFFER**

Single pole changeover. 2in. x 0.6in. x 0.75in. 50v. 2.5KΩ coil, operates on 24v. 8 for 10/-, 5,000 available, p. & p. 1/6.

**MEMORY CORE STORE PLANES**

160 BITS £1.	P. & P. 2/-
4,000 BITS £4.	P. & P. 4/-
1,000 BITS £8.	P. & P. 8/-

**EXTENSION TELEPHONES**

Why get out of the bath when the phone rings. Install one in the bathroom. 19/6 each, p. & p. 5/-, 35/- for 2, p. & p. 8/-, These are extension phones and do not have bells.



**1,750 COMPONENTS FOR 65/- ??**

YES, QUITE TRUE, READ ON

**BUMPER BARGAIN PARCEL**

We guarantee that this parcel contains at least 1,750 components. Short-leaded on panels, including a minimum of 350 transistors (mainly NPN and PNP germanium, audio and switching types—data supplied). The rest of the parcel is made up with: Resistors 5% or better (including some 1%) mainly metal oxide, carbon film, and composition types. Mainly ¼ and ½ watt . . . diodes, miniature silicon types OA90, OA91, OA95, IS130, etc. . . . capacitors, including tantalum, electrolytics, ceramics and polyesters . . . inductors, a selection of valves . . . also the odd transformer, trimpot, etc., etc. . . . These are all miniature, up to date, professional, top quality components. Don't miss this, one of our best offers yet!! Price 65/-, post and packing 6/6 U.K., New Zealand 20/-, Limited stocks only.

9 OA5, 3OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875. All long leaded on panels 13in. x 4in. 2 for 10/-, p. & p. 3/6d. 4 for 20/-, post free.

**EX COMPUTER PRINTED CIRCUIT PANELS**

2in. x 4in., packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price, 10 boards 10/-, p. & p. 2/-, With a guaranteed minimum of 35 transistors. 25 boards for £1, p. & p. 3/6. With a guaranteed minimum of 85 transistors. Transistor data included.

**COMPONENT PACKS**

200 capacitors, electrolytics, paper, silver mica, etc. 10/-, Postage on this pak 2/6.  
250 mixed resistors 10/-, post & packing 2/-  
40 wirewound resistors, mixed types and values. 10/-, postage 1/6.



**QUANTITIES AVAILABLE**


**EXTRACTOR/BLOWER FANS (Papst)**

100 c.f.m. 4½ x 4½ x 2in. 2,800 r.p.m., 240v. A.C. Precision made in West Germany by Papst. These Fans are the best available. Genuine bargain at 50/- each.

**KEYTRONICS**

52 Earls Court Road, London, W.8  
Tel. 01-478 8499  
MAIL ORDER ONLY. Retail and Trade supplied. Export enquiries particularly welcome. S.A.E. FOR LIST

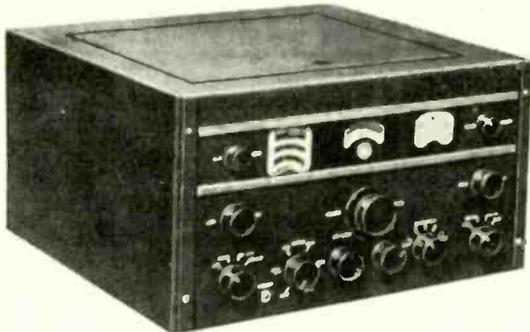**LATEST RELEASE OF RCA COMMUNICATION RECEIVERS AR88**



**BRAND NEW** and in original cases—A.C. mains input. 110V or 250V. Freq. in 6 bands 535 Kc/s-32 Mc/s. Output impedance 2.5-600 ohms. Complete with crystal filter, noise limiter, B.F.O., H.F. tone control, R.F. & A.F. variable controls. Price £87/10/- each, carr. £2.


Same model as above in secondhand cond. (guaranteed working order), from £45 to £60, carr. £2.

\*SET OF VALVES: new, £3/10/- a set, post 7/6; SPEAKERS: new, £3 each, post 10/-; \*HEADPHONES: new, £1/5/- a pair, 600 ohms impedance. Post 5/-.

**AR88 SPARES.** Antenna Coils L5 and 6 and L7 and 8. Oscillator coil L55. Price 10/- each, post 2/6. RF Coils 13 & 14; 17 & 18; 23 & 24; and 27 and 28. Price 12/6 each. 2/6 post. By-pass Capacitor K.98034-1, 3 x 0.05 mfd. and M.980344, 3 x 0.01 mfd., 3 for 10/-, post 2/6. Trimmers 95534-502, 2-20 p.f. Box of 3, 10/-, post 2/6. Block Condenser, 3 x 4 mfd., 600 v., £2 each, 4/- post. Output transformers 901666-501 27/6 each, 4/- post.

\* Available with Receiver only.

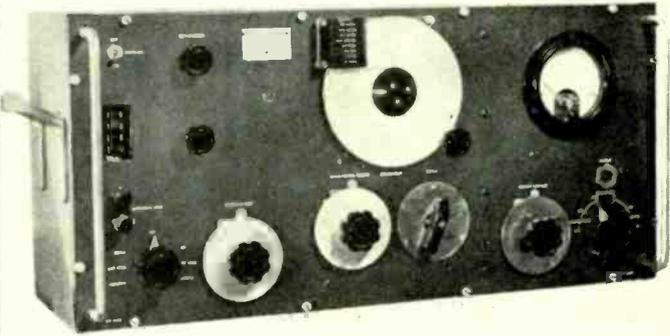S.A.E. for all enquiries. If wishing to call at Stores, please telephone for appointment.



**MARCONI SIGNAL GENERATORS TYPE TF-144G**

Freq. 85Kc/s-25Mc/s in 8 ranges. Incremental: +/— 1% at 1Mc/s. Output: continuously variable 1 microvolt to 1 volt. Output Impedance: 1 microvolt to 100 millivolts, 10 ohms 100mV-1 volt-52.5 ohms. Internal Modulation: 400 c/s sinewave 75% depth. External Modulation: Direct or via internal amplifier. A.C. mains 200/250V, 40-100 c/s. Consumption approx. 40 watts. Measurements: 19¼ x 12¼ x 10 in. The above come complete with Mains Leads, Dummy Aerial with screened lead, and plugs. As New, in Manufacturer's cases, £40 each. Carr. 30/-, DISCOUNT OF 10% FOR SCHOOLS, TECHNICAL COLLEGES, etc.

**W. MILLS** 3-B TRULOCK ROAD, TOTTENHAM, N.17  
Phone: 01-808-9213



**HRO RECEIVER.** Model 5T. This is a famous American High Frequency superhet, suitable for CW, and MCW, reception crystal filter, with phasing control. AVC and signal strength meter. Complete HRO 5T SET (Receiver, Set of 5 Coils & Power Unit) for £27/10/-, carr. 30/-.

**COMMAND RECEIVERS;** Model 6-9 Mc/s., as new, price £5/10/- each, post 5/-.

**COMMAND TRANSMITTERS,** BC-458: 5.3-7 Mc/s., approx. 25W output, directly calibrated. Valves 2 x 1625 PA; 1 x 1626 osc.; 1 x 1629 Tuning Indicator; Crystal 6,200 Kc/s. New condition—£3/10/- each, 10/- post.

(Conversion as per "Surplus Radio Conversion Manual, Vol. No. 2," by R. C. Evenson and O. R. Beach.)

**AIRCRAFT RECEIVER ARR. 2:** Valve line-up 7 x 9001; 3 x 6AK5; and 1 x 12A6. Switch tuned 234-258 Mc/s. Rec. only £3 each, 7/6 post; or Rec. with 24 v. power unit and mounting tray £3/10/- each, 10/- post.

**RECEIVERS:** Type BC-348, operates from 24 v D.C., freq. range 200-500 Kc/s, 1.5-18 Mc/s. (New) £35.0.0 each; (second hand) £20.0.0 each, good condition, carr. 15/- both types.

**MARCONI RECEIVER 1475 type 88:** 1.5-20 Mc/s, second-hand condition £10.0.0 each. New condition £25.0.0 each, carr. 15/-.

**RACAL EQUIPMENT:** Frequency Meter type SA20: £35 each, carr. £1. Frequency Counter type SA21: £65 each, carr. 30/-.

Converter Frequency Electronic VHF Type S.A.80 (for use with the SA.20): 25 Mc/s-160 Mc/s, £40 each, carr. £1.

**ROTARY CONVERTERS:** Type 8a, 24 v D.C., 115 v A.C. @ 1.8 amps, 400 c/s 3 phase, £8/10/- each, 8/- post. 24 v D.C. input, 175 v D.C. @ 40mA output, 25/- each, post 2/-.

**CONDENSERS:** 150 mfd, 300 v A.C., £7/10/- each, carr. 15/-.

40 mfd, 440 v A.C. wkg., £5 each, 10/- post. 30 mfd, 600 v wkg. D.C., £3/10/- each, post 10/-.

15 mfd, 330 v A.C. wkg., 15/- each, post 5/-.

10 mfd, 1000 v, 12/6 each, post 2/6.

10 mfd, 600 v, 8/6 each, post 5/-.

8 mfd, 1200 v, 12/6 each, post 3/-.

8 mfd, 600 v, 8/6 each, post 2/6.

4 mfd, 3000 v wkg., £3 each, post 7/6.

2 mfd, 3000 v wkg., £2 each, post 7/6.

0.25 mfd, 2Kv, 4/- each, 1/6 post. 0.01 mfd. MICA 2.5 Kv. Price £1 for 5. Post 2/6. Capacitor: 0.125 mfd, 27,000v wkg. £3.15.0 each, 10/- post.

**OSCILLOSCOPE Type 13A,** 100/250 v. A.C. Time base 2 c/s.-750 Kc/s. Bandwidth up to 5 Mc/s. Calibration markers 100 Kc/s. and 1 Mc/s. Double Beam tube. Reliable general purpose scope, £22/10/- each, 30/- carr.

**COSSOR 1035 OSCILLOSCOPE,** £30 each, 30/- carr.

**COSSOR 1049 Mk. 111,** £45 each, 30/- carr.

**RELAYS:** GPO Type 600, 10 relays @ 300 ohms with 2M and 10 relays @ 50 ohms with 1M., £2 each, 6/- post.

12 Small American Relays, mixed types £2, post 4/-.

Many types of American Relays available, i.e., Sigma; Allied Controls; Leach; etc. Prices and further details on request 6d.

**GEARED MOTORS:** 24 v. D.C., current 150 mA, output 1 r.p.m., 30/- each, 4/- post. Assembly unit with Letcherbar Tuning Mechanism and potentiometer, 3 r.p.m., £2 each, 5/- post.

**SYNCHROS:** and other special purpose motors available. British and American ex stock. List available 6d.

**TCS MODULATION TRANSFORMERS,** 20 watts, pr. 6,000 C.T., sec. 6,000 ohms. Price 25/-, post 5/-.

**SOLENOID UNIT:** 230 v. A.C. input, 2 pole, 15 amp contacts, £2/10/- each post 6/-.

**CONTROL PANEL:** 230 v. A.C., 24 v. D.C. @ 2 amps., £2/10/- each, carr. 12/6.

**OHMITE VARIABLE RESISTOR:** 5 ohms, 5 1/2 amps; or 2.6 ohms at 4 amps. Price (either type) £2 each, 4/6 post each.

**TX DRIVER UNIT:** Freq. 100-156 Mc/s. Valves 3 x 3C24's; complete with filament transformer 230 v. A.C. Mounted in 19in. panel, £4/10/- each, 15/- carr.

**POWER SUPPLY UNIT PN-12A:** 230V a.c. input 50-60 c/s. 513V and 1025V @ 420 mA output. With 2 smoothing chokes 9H, 2 Capacitors, 10Mfd 1500V and 10Mfd 600V. Filament Transformer 230V a.c. input. 4 Rectifying Valves type 5Z3. 2 x 5V windings @ 3 Amps each, and 5V @ 6 Amp and 4V @ 0.25 Amp. Mounted on steel base 19" W x 11" H x 14" D. (All connections at the rear). Excellent condition £8.10.0. each, Carr. £1.

**AUTO TRANSFORMER:** 230-115V, 50-60c/s, 1000 watts. mounted in a strong steel case 5" x 6 1/2" x 7". Bitumin impregnated. £5 each, Carr. 12/6. 230-115V, 50-60c/s, 500 watts. 7" x 5" x 5". Mounted in steel ventilated case. £3 each, Carr. 10/-.

**POWER UNIT:** 110 v. or 230 v. input switched; 28 v. @ 45 amps. D.C. output. Wt. approx. 100 lbs., £17/10/- each, 30/- carr. SMOOTHING UNITS suitable for above £7/10/- each, 15/- carr.

**DE-ICER CONTROLLER MK. III:** Contains 10 relays D.P. changeover heavy duty contacts, 1 relay 4P, C/O. (235 ohms coil). Stud switch 30-way relay operated, one five-way ditto, D.C. timing motor with Chronometric governor 20-30 v., 12 r.p.m.; geared to two 30-way stud switches and two Lexed solenoids, 1 delay relay etc., sealed in steel case (4 x 5 x 7 ins.) £3 each, post 7/6.

**MODULATOR UNIT:** 50 watt, part of BC-640, complete with 2 x 811 valves, microphone and modulator transformers etc. £7/10/- each, 15/- carr.

ALL GOODS OFFERED WHILST STOCKS LAST IN "AS IS" CONDITION UNLESS OTHERWISE STATED

CALLERS BY TELEPHONE  
APPOINTMENT ONLY

**W. MILLS**

3-B TRULOCK ROAD, TOTTENHAM, N.17

Phone: 01-808 9213

**NIFE BATTERIES:** 4 v. 160 amps, new, in cases, £20 each, £1 10/- carr.

**FUEL INDICATOR Type 113R:** 24 v. complete with 2 magnetic counters 0-9999, with locking and reset controls mounted in a 3in. diameter case. Price 30/- each, postage 5/-.

**FREQUENCY METERS:** BC-221, meter only £30 each, BC-221 complete with stabilised power supply £35 each, carr. 15/-.

LM13, 125-20,000 Kc/s., £25 each, carr. 15/-.

TS.175/U, £75 each, carr. £1.

FR-67/U: This instrument is direct reading and the results are presented directly in digital form. Counting rate: 20-100,000 events per sec. Time Base Crystal Freq.: 100 Kc/s. per sec. Power supply: 115 v., 50/60 c/s., £100 each, carr. £1.

**AUDIO OSCILLATOR 382/F:** Input 115 v. A.C., 50 c/s, 20-200,000 c/s per sec. in 4 ranges. Cont. wave. Output 0-10 v. in 7 ranges. Power output 100 mW. Output impedance 1,000Ω. £27/10/- each, £1 carr.

**RACK CABINETS** (totally enclosed) for std. 19in. panels. Size: 6ft. high x 21in. wide x 16in. deep. With rear door. £12 each, £2/10/- carr. OR 4ft. high x 23in. wide x 19in. deep. With rear door. £8/10/- each, £2 carr.

**CATHODE RAY TUBE UNIT:** With 3in. tube, Type 3EG1 (CV1526) colour green, medium persistence complete with nu-metal screen, £3/10/- each, post 7/6.

**APNI ALTIMETER TRANS./REC.,** suitable for conversion 420 Mc/s., complete with all valves 28 v. D.C. 3 relays, 11 valves, price £3 each, carr. 10/-.

**TEST EQUIPMENT**

<b>MARCONI</b>	TF-1274	VHF Bridge Oscillator	£75 each
	TF-1275	VHF Bridge Detector	£75 each
	TF-1067/1	Heterodyne Frequency Meter	£85 each
	TF-899	Valve Millivoltmeter	£35 each
	TF-978	VHF Admittance Bridge	£85 each
	TF-894A	Audio Tester	£55 each
	TF-329G	Circuit Magnification Meter	£45 each
	TF-428/2	Valve Voltmeter	£12/10/- each
	TF-428/1	Valve Voltmeter	£8/10/- each
	TF-726C	UHF Signal Generator	£65 each
	TF-934	Deviation Test Meter	£35 each
6075A	Deviation Test Meter	£65 each	
TF-987/1	Noise Generator	£20 each	
TF-956	(CT.44) A.F. Absorption Wattmeter	£20 each	
<b>FIRZ HILL</b>	V.200	Sensitive Valve Voltmeter	£35 each
	B.810	Incremental Inductance Bridge	£75 each
<b>SOLATRON</b>	CD-513	Oscilloscope	£45 each
	CD-513-2	Oscilloscope	£47/10/- each
	AW-553	Power Amplifier	£30 each
<b>AIRMEC</b>	Type 701	Signal Generator	£50 each
<b>PHILLIPS</b>	Type GM-6008	Valve Voltmeter	£35 each
<b>DAWE</b>	Type 402C	Megohm Meter	£12 each

**CANADIAN C52 TRANS/REC.:** Freq. 1.75-16 Mc/s on 3 bands. R.T., M.C.W. and C.W. Crystal calibrator etc., power input 12V. D.C., new cond., complete set £50. Carr. £2/10/-.

Power Unit for Rec., new £3/5/-, Carr. 10/-.

**DECADE RESISTOR SWITCH:** 0.1 ohm per step. 10 positions. 3 Gang, each 0.9 ohms. Tolerance ±1% £3 each, 5/- post. 90 ohms per step. 10 positions, total value 900 ohms. 3 Gang. Tolerance ±1% £3/10/- each, 5/- post.

**TELESCOPIC ANTENNA:** In 4 sections, adjustable to any height up to 20 ft. Closed measures 6 ft. Diameter 2 in. tapering to 1 in. £5 each + 10/- carr. Or £9 for two + £1 carr. (brand new condition).

**COAXIAL TEST EQUIPMENT: COAXSWITCH—Mnfrs.** Bird Electronic Corp. Model 72RS; two-circuit reversing switch, 75 ohms, type "N" female connectors fitted to receive UG-21/U series plugs. New in ctns., £6/10/- each, post 7/6.

**CO-AXIAL SWITCH—Mnfrs.** Transco Products Inc., Type M1460-22, 2 pole, 2 throw. (New) £6/10/- each, 4/6 post. 1 pole, 4 throw, Type M1460-4. (New) £6/10/- each, 4/6 post.

**PRD Electronic Inc. Equipment: FREQUENCY METER:** Type 587-A, 0.250-1.0 KMC/SEC. (New) £75 each, post 12/6.


**FIXED ATTENUATOR:** Type 130c, 2.0-10.0 KMC/SEC. (New) £5 each, post 4/-.

**FIXED ATTENUATOR:** Type 1157S-1, (new) £6 each, post 5/-.

**FOR EXPORT ONLY  
BRITISH & AMERICAN  
COMMUNICATION EQUIPMENT**

Type B.44 Tx/Rx, Crystal controlled, 60-95 Mc/s, 12V. d.c. operation. W.S. Type 88, Crystal controlled, 40-48 Mc/s. W.S. Type HF-156, Mk. II, Crystal controlled, 2.5-7.5 Mc/s. W.S. Type 62, tunable, 1.5-12 Mc/s. C.44, Mk. II, Radio Telephone, Single Channel, 70-85 Mc/s, 50 watts, output, 230V. a.c. input. G.E.C. Progress Line Tx Type DO36, 144-174 Mc/s, 50 watt, narrow band width. A.C. input 115V. BC-640 Tx, 100-156 Mc/s, 50 watt output, 110V or 230V input. STC Tx/Rx Type 9X, TR1985; RT1986; TR1987 and TR1998, 100-156 Mc/s. TRC-1 Tx/Rx, Types T.14 and R.19, FM 60-90 Mc/s. With associated equipment available. Redifon GR410 Tx/Rx, SSB, 1.5-20 Mc/s. Sun-Air Tx/Rx Type T-10-R. Collins Tx/Rx/Type 18S4A. Collins Tx/Rx Type ARC-27, 200-400 Mc/s, 28V d.c. With associated equipment available. ARC-5; ARC-3; and ARC-2 Tx/Rx. BC-375; 433G; 348; 718; 458; 455 Tx/Rx. Directional Finding Equipment CRD.6 and FRD.2 complete Sets available and spares. Telephone Installation type XY, (U.S.A.), 600 Line Automatic Telephone Exchange. Complete system with full set of Manuals. Mobile Communications Installation mounted in a trailer with 4 x pneumatic tyres. Consisting of 3xARC-27 Tx/Rx with all associated equipment (as new).

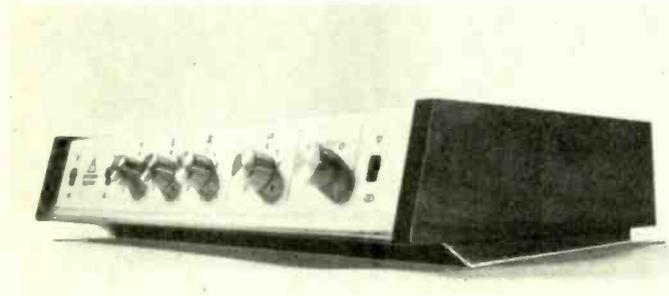proved performance  
high fidelity with  
specification  
guarantee



## THE ENGLEFIELD SYSTEM

The Peak Sound Englefield system assembles from laboratory designed modules to provide a cost-performance ratio which has never been bettered in high fidelity. Here is top-flight circuitry housed in a cabinet of elegantly original design which is both beautiful and completely practical back and front. By assembling these Peak Sound units, you can own one of the best high fidelity instruments you have ever heard or seen and all for a cost of about £38 (about £33 if assembled from kit of parts). The assembly is supplied complete down to the necessary connecting wires supplied colour coded, cut to length and stripped at the ends for soldering. You can use the Englefield Cabinet design to house either the 12 + 12 system as published in *Practical-Wireless*, or the 25 + 25 watt system as approved for the *Hi-Fi News* Twin Twenty by Reg Williamson. The modules are all obtainable separately and are recommended for highest quality work. Go to your stockist and ask to see and hear Peak Sound equipment now. Leaflets on request.

Matching F.M. Tuners will be available very shortly.

### THE SPECIFICATION

Using two Peak Sound PA. 12-15's. driven simultaneously at 1 KHz from 240 V. mains supply.  
Output per channel: 11 watts into 15Ω; 14 watts into 8Ω. (see spec. guarantee).  
Frequency bandwidth: 10Hz to 45 KHz for 1dB at 1 watt.  
Total Harmonic Distortion at 1 KHz at 10 watt into 15Ω—0.1%.  
Input sensitivities: Mag. PU. 3.5 mV imp. R.I.A.A. equalized into 68 KΩ; Tape, 100mV linear into 100 KΩ; Radio, 100 mV linear into 100 KΩ.  
Overload factor: 29 dB on all input channels.  
Signal/noise ratio: —65 dB on all inputs. Vol. control max.  
Controls: Volume, Treble, Bass, Low-pass Filter, Mono/Stereo, On/off; Balance.  
Power bandwidth for —1 dB at 20 watts R.M.S. into 15Ω at less than 0.25% distortion is 20 Hz to 20 KHz.

### PEAK SOUND BAXENDALL SPEAKER

Peak Sound can supply the parts necessary to build the famous Baxendall Speaker described originally in *Wireless World*. All to designer-approved spec. Details on request. Also available built in teak finished cabinet 18" x 12" x 10"—18½ gns.

### PEAK SOUND SPECIFICATION GUARANTEE

Peak Sound guarantee that their equipment meets all specifications as published by them and that these are written in the same terms as are used in equipment reviews appearing in this and other leading high fidelity journals. Audio output powers are quoted at continuous sine wave power in terms of Root Mean Square values (R.M.S.) into stated loads at stated frequencies.

**peak sound**

AT SONEX 70  
ROOMS 231  
AND 236

PEAK SOUND (HARROW) LTD., 32 St. Jude's Road, Englefield Green, Egham, Surrey Telephone: EGHAM 5316

To Peak Sound, 32 St. Jude's Rd., Englefield Green, Egham, Surrey.

Details of Englefield systems etc., please and .....

Name .....

Address .....

WW4

Write your stockists name and address in margin below and cut out with coupon if necessary

# Money-making repair data for over 1250 POPULAR MODELS RADIO & TV SERVICING

The most comprehensive library of Servicing data available.

TELEVISIONS,  
STEREOGRAMS,  
RADIOS,  
TAPE RECORDERS,  
CAR RADIOS,  
RECORD PLAYERS  
PLUS  
286 pages of data on  
COLOUR  
TELEVISION

In 5 handy sized volumes you have all the vital data required for servicing the popular models produced over the last 5 years. Information on earlier models that still come in for repair is now unavailable through any other channel. Here in 2860 pages you have all the circuits, data and repair information for servicing over 1250 of the popular 1965-70 Televisions (including Colour TV), Radios, Stereograms, Car Radios, Record Players, and Tape Recorders. Radio & TV Servicing is the only work of its kind and is much sought after in the trade—a guaranteed money-spinner for years to come.



2860 PAGES, 3321 CIRCUITS, PRINTED PANEL DIAGRAMS, COMPONENT LAYOUT DIAGRAMS & WAVEFORM GRAPHS

See Radio & TV Servicing and assess its value for yourself, on 10 days Free Trial—all you have to do is complete the coupon below and post today.

## FREE 10-day Trial

Buckingham Press Ltd., P.O. Box 14, Gatehouse Rd., Aylesbury, Bucks. Please send RADIO & TV SERVICING—5 VOLS, without obligation to buy. I will return the books in 11 days or post—

Tick   Full cash price of £20. or

here  25/- dep. & 20 monthly payments of 20/-, paying £21.5s.

If you are under 18 your father must fill up coupon

Full Name .....  
(Block letters)  
Address .....  
County .....

Occupation .....

Signature .....  
RV4/5114

Please tick (✓) here  
Address on left is  
My/our property   
Rented unfurn.   
Rented furn.   
Parent's home   
Temp. address

Mr.   
Mrs.   
Miss

# ELECTROVALUE

EVERYTHING BRAND NEW AND TO SPECIFICATION • LARGE STOCKS

## BARGAINS IN NEW TRANSISTORS

ALL POWER TYPES SUPPLIED WITH FREE INSULATING SETS

2N696	5/6	2N3707	4/-	AF127	7/-
2N697	5/6	2N3708	3/-	BA102	9/-
2N706	2/9	2N3709	3/-	BC107	2/9
2N1132	9/9	2N3710	3/6	BC108	2/6
2N1302	4/-	2N3711	3/11	BC109	2/9
2N1303	4/-	2N3904	7/6	BC147	3/6
2N1304	4/6	2N3906	7/6	BC148	3/3
2N1305	4/6	2N3731	24/-	BC149	3/6
2N1306	6/9	2N4058	5/3	BC153	10/-
2N1307	6/9	2N3325	10/9	BC154	11/-
2N1308	8/9	2N3794	3/3	BC157	3/9
2N1309	8/9	2N4284	3/3	BC158	3/6
2N1613	6/-	2N4286	3/3	BC159	3/9
2N1711	7/-	2N4289	3/3	BC167	2/6
2N2218	9/3	2N4291	3/3	BC168	2/3
2N2147	18/9	2N4292	3/3	BC169	2/6
2N2369A	5/3	2N4410	4/9	BC177	6/3
2N2646	10/9	2N5192	25/-	BC178	5/8
2N2924	4/-	2N5195	28/3	BC179	6/-
2N2925	4/6	40361	12/6	BD121	18/-
2N2926R	2/3	40362	16/-	BD123	24/3
2N2926O	2/3	AC126	6/6	BF178	10/6
2N2926Y	2/3	AC127	6/-	BFX29	10/9
2N2926G	2/3	AC128	6/-	BFX85	8/3
2N3053	5/6	AC176	11/-	BFX88	6/9
2N3054	14/3	ACY22	3/9	BFY50	4/6
2N3055	16/-	ACY40	4/-	BFY51	4/3
2N3391A	6/3	AD140	19/-	BSX20	3/9
2N3702	3/6	AD149	17/6	MJ480	21/-
2N3703	3/3	AD161	16/-	MJ481	27/-
2N3704	3/9	AD162	16/-	MJ491	30/-
2N3705	3/5	AF118	16/6	NKT403	15/6
2N3706	3/3	AF124	7/6	NKT405	15/-

## PEAK SOUND ENGLEFIELD KITS



Build it  
12+12  
or  
25+25

Brilliant new styling and available in two forms:  
**STEREO 15 WATTS PER CHANNEL**  
Supplied in kit form with complete amplifier and pre-amplifier modules and power supply components. Output per channel into 15Ω —13 watts R.M.S. Price £38.9.0 Nett

**STEREO 25 WATTS PER CHANNEL**  
Supplied in kit form with complete amplifier, pre-amplifier and regulated power supply modules. Output per channel into 15Ω —28 watts R.M.S. Price £58.15.0 Nett

Specifications on these amplifiers in accordance with the Specifications in Guarantee published in Peak Sound advertisements.

**Inputs:**  
Magnetic, RIAA 3.5mV Tape 100mV  
Ceramic 35mV Radlo 100mV

Signal to noise ratios: Better than 60dB all inputs.

**ENGLEFIELD CABINET** to house either above assemblies (as illustrated) £6.0.0. Nett  
Other Peak Sound Products as advertised.

## RESISTORS

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	82Ω-220K Ω	E12	18	16	15
C	1/8W	5%	4.7Ω-330K	E24	2.5	2	1.75
C	1/4W	10%	4.7Ω-10M Ω	E12	2.5	2	1.75
C	1/2W	5%	4.7Ω-10M Ω	E24	3	2.5	2.25
MO	1/2W	2%	10Ω-1M Ω	E24	9	8	7
C	1W	10%	4.7Ω-10M Ω	E12	6	5	4.5
WW	1W	10% ±1/20Ω	0.22Ω-3.3Ω	E12		15d. all quantities	
WW	3W	5%	12Ω-10K Ω	E12		15d. all quantities	
WW	7W	5%	12Ω-10K Ω	E12		18d. all quantities	

Codes: C = carbon film, high stability, low noise.  
MO = metal oxide, Electrosl TR5, ultra low noise.  
WW = wire wound, Plessey.

**Values:**  
E12 denotes series: 1, 1.2, 1.5, 1.8, 2.2, 2.7, 3.3, 3.9, 4.7, 5.6, 6.8, 8.2 and their decades.  
E24 denotes series: as E12 plus 1.1, 1.3, 1.6, 2, 2.4, 3, 3.6, 4.3, 5.1, 6.2, 7.5, 9.1 and their decades.

**NEW PLESSEY INTEGRATED CIRCUIT POWER AMPLIFIER TYPE SL403A.** Only 48/6 nett. Operates with 18V power supply. Sensitivity 20mV into 20MΩ, 3 watts into 7.5Ω.

Supplied complete with application Data on orders for 2 or more.

**PE NOV. 69 STEREO AMPLIFIER KIT** less metalwork £11/18/- NET complete

**CARBON SKELETON PRE-SETS**  
Small high quality, type PR: Linear only: 100Ω, 220Ω, 470Ω, 1KΩ, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1MΩ, 2M2, 5M, 10MΩ vertical or horizontal mounting 1/- each

**S-DeCs PUT AN END TO "BIRDS-NESTING".** Components just plug in. Saves valuable time. Use components again and again.  
S-DeC ... Only 30/6 post free  
Compact T-DeC, increased capacity, may be temperature-cycled.  
T-DeC ... only 50/- post free

**WAVECHANGE SWITCHES**  
IP 12W; 2P 6W; 3P 4W; 4P 3W—long spindles ... 4/9 each  
**SLIDER SWITCHES**  
Double pole, double throw ... 3/- each

Prices are in pence each for same ohmic value and power rating, NOT mixed values. (Ignore fractions of one penny on total resistor order.)

**MULLARD SUB-MIN ELECTROLYTICS C426 RANGE** Price 1/3 each  
Axial leads. Values (μF/V): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5/64; 6.4/6.4; 6.4/25; 8/4; 8/40; 10/2.5; 10/16; 10/64; 12.5/25; 16/40; 20/16; 20/64; 25/6.4; 25/25; 32/4; 32/10; 32/40; 32/64; 40/16; 40/2.5; 50/6.4; 50/25; 50/40; 64/4; 64/10; 80/2.5; 80/16; 80/25; 100/6.4; 125/4; 125/10; 125/16; 160/2.5; 200/6.4; 200/10; 250/4; 320/2.5; 320/6.4; 400/4; 500/2.5.

**LARGE CAPACITORS. ALL NEW STOCK**  
High ripple current types: 2000μF 25V 7/4; 2000μF 50V 11/4; 5000μF 25V 12/6; 5000μF 50V 21/11; 1000μF 100V 16/3; 2000μF 100V 28/9; 5000μF 70V 36/-; 5000μF 100V 58/3; 1000μF 50V 8/2; 2500μF 64V 15/5; 2500μF 70V 19/6.

**MEDIUM RANGE ELECTROLYTICS**  
Axial leads. Values (μF/V): 50/50 2/-; 100/25 2/-; 100/50 2/6; 250/25 2/6; 250/50 3/9; 500/25 3/9; 1000/10 3/3; 500/50 4/6; 1000/25 4/-; 1000/50 6/-; 2000/25 6/-; 330/25 2/6.

**SMALL ELECTROLYTICS**  
Axial leads: 5/10, 10/10, 25/10, 50/10 1/- each  
25/25, 47/25, 100/10, 220/10 ... 1/3 each

**COMPONENT DISCOUNTS**  
10% on orders for components for £5 or more.  
15% on orders for components for £15 or more.  
(No discount on nett items)

**POSTAGE AND PACKING**  
Free on orders over £2.  
Please add 1/6 if order is under £2.  
Overseas orders welcome: carriage charged at cost.

**ZENER DIODES:** Full range of 5% 400 mV available in E24 series, 2.7 V to 30 V ... 4/6 each

**COLVERN 3 WATT WIRE-WOUND POTENTIOMETERS:** 10Ω, 15Ω, 25Ω, 50Ω, 100Ω, 150Ω, 250Ω, 500Ω, 1KΩ, 1.5KΩ, 2.5KΩ, 5KΩ, 10KΩ, 15KΩ, 25KΩ, 50KΩ.  
Price ... only 5/6 each

**CARBON TRACK POTENTIOMETERS**  
Double wiper ensures minimum noise level. Long plastic spindles.  
Single gang linear ... 220Ω, 470Ω, 1K, etc. to 2M2Ω 2/6  
Single gang log. ... 4K7, 10K, 22K, etc. to 2M2Ω ... 2/6  
Dual gang linear ... 4K7, 10K, 22K, etc. to 2M2Ω ... 8/6  
Dual gang log. ... 4K7, 10K, 22K, etc. to 2M2Ω ... 8/6  
Log/Anti-log. ... 10K, 47K, 1MΩ only ... 8/6  
Dual anti-log ... 10K only ... 8/6  
Any type with 1/2 amp double pole mains switch ... extra 2/3  
Please Note—only decades of 10, 22 and 47 are available with range quoted.

**FETS n-channel**  
Low cost general purpose 2N5163, 25 volt ... only 5/- each  
Audio/r.f. Texas 2N3819 ... 8/6 each  
Motorola 2N5457 (MPF103) ... 9/9 each  
Motorola 2N5459 (MPF105) ... 9/9 each

**30 WATT BAILEY AMPLIFIER COMPONENTS:**  
Transistors for one channel £7/5/6 list, with 10% discount ... only £6/11/-  
Transistors for two channels £14/11/- list, with 15% discount ... only £12/7/5  
Capacitors and resistors for one channel, Nov. '68 circuit list £2.  
Printed circuit board free with each transistor set.  
Complete unregulated power supply kit £4/17/6 mono or stereo, subject to discount.  
Complete regulated power supply kit Nov. '68 circuit £9/5/- subject to discount.  
Further details on application.

**MAIN LINE AMPLIFIER KITS AS ADVERTISED. PRICES NET AUTHORISED DEALER**

**SINCLAIR IC.10 INTEGRATED CIRCUIT AMPLIFIER AND PRE-AMPLIFIER**  
This remarkable monolithic integrated circuit amplifier and pre-amplifier is now available for despatch from stock. It is the equivalent of 13 transistor/18 resistor circuit plus 3 diodes and the first of its kind ever. It is d.c. coupled and applicable to an unusually wide range of uses all of which are detailed in the manual provided with it.  
Sinclair products as advertised 59/6 NETT post free

# ELECTROVALUE

DEPT. WW.704, 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY,  
Hours: 9-5.30 daily; 1.0 p.m. Saturdays. Telephone: Egham 5533 (STD 0784-3)

# BI-PRE-PAK LIMITED

### FULLY TESTED AND MARKED

AC107	3/-	OC170	3/-
AC126	2/6	OC171	4/-
AC127	2/6	OC200	3/6
AC128	2/6	OC201	7/-
AC176	5/-	2G301	2/6
AC177	3/-	2G303	2/6
AF114	4/-	2N711	10/-
AF115	3/6	2N1302-3	4/-
AF116	3/6	2N1304-5	5/-
AF117	3/6	2N1306-7	6/-
AF239	12/6	2N1308-9	8/-
AF186	10/-	2N3819 F.E.T.	9/-
AF139	10/-	Power	
BFY50	4/-	Transistors	
BSY25	7/6	OC20	10/-
BSY26	3/-	OC23	10/-
BSY27	3/-	OC25	8/-
BSY28	3/-	OC26	5/-
BSY29	3/-	OC28	7/6
BSY95A	3/-	OC35	5/-
OC41	2/6	OC36	7/6
OC44	2/6	AD149	10/-
OC45	2/6	2S034	10/-
OC71	2/6	2N2287	20/-
OC72	2/6	2N3055	15/-
OC73	3/6	Diodes	
OC81	2/6	AAY42	2/-
OC81D	2/6	OA95	2/-
OC83	4/-	OA79	1/9
OC139	2/6	OA81	1/9
OC140	3/6	IN914	1/6

### TRY OUR X PACKS FOR UNEQUALLED VALUE

#### XA PAK

Germanium PNP type transistors, equivalents to a large part of the OC range, i.e. 44, 45, 71, 72, 81, etc.

PRICE £5 PER 1000

POST & PACKING 4/6 U.K.

#### XB PAK

Silicon TO-18 CAN type transistors NPN/PNP mixed lots, with equivalents to OC200-1, 2N706, BSY27/29, BSY95A.

PRICE £4.5 PER 500

PRICE £8 PER 1000

POST & PACKING 2/6 U.K.

#### XC PAK

Silicon diodes miniature glass types, finished black with polarity marked, equivalents to OA200, OA202, BAY31-39 and DK10, etc.

PRICE £4.10 PER 1000

POST & PACKING 2/6 U.K.

ALL THE ABOVE UNTESTED PACKS HAVE AN AVERAGE OF 75% OR MORE GOOD SEMICONDUCTORS. FREE PACKS SUSPENDED WITH THESE ORDERS. ORDERS MUST NOT BE LESS THAN THE MINIMUM AMOUNTS QUOTED PER PAK.

### NEW TESTED & GUARANTEED PAKS

B2	4	PHOTO CELLS, SUN BATTERIES. .3 to .5 volts .5 to 2mA	10/-
B77	2	AD161—AD162 NPN/PNP TRANS. COMP. OUTPUT PAIR	10/-
BB1	10	REED SWITCHES MIXED TYPES LARGE & SMALL	10/-
BB9	2	5 SP5 LIGHT SENSITIVE CELLS LIGHT RES. 400 Ω DARK 1 M Ω	10/-
B91	8	NKT163/164 PNP GERM. TO -5 EQUIVALENT TO OC44, OC45	10/-
B92	4	NPN SIL TRANS. AO6=BSX20. 2N2369. 500MHz. 360mW	10/-
B93	5	GET113 TRANS. EQUIV. TO ACY17-21 PNP GERM.	10/-
B96	5	2N3136 PNP SIL TRANS. TO-18 HPE100-300 IC. 600mA. 200MHz	10/-
B98	10	XB112 & XB102 EQUIV. TO AC126 AC156, OC81/2, OC71/2, NKT271, ETC.	10/-
B99	200	CAPACITORS, ELECTROLYTICS, PAPER, SILVER MICA, ETC. POSTAGE ON THIS PAK 2/6.	10/-
H4	250	MIXED RESISTORS POST & PACKING 2/6.	10/-
H7	40	WIREFOUND RESISTORS MIXED TYPES & VALUES. POSTAGE 1/6	10/-

# FREE!

PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 10/- WITH ORDERS OVER £4

### LOOK! TRANSISTORS ONLY 6d EACH

#### TYPE A PNP SILICON ALLOY TO-5 CAN

Spec:—  
ICER AT VCE = 20v  
1mA MAX.  
HFE, 15-100  
These are of the 2S300 type which is a direct equivalent to the OC200/205 range.

#### TYPE B PNP SILICON PLASTIC ENCAPSULATION

Spec:—  
ICER AT VCE = 10v  
1mA MAX.  
HFE, 10-200  
These are of the 2N3702/3 and 2N4059/62 range.

#### TYPE E PNP GERMANIUM FULLY MARKED & TESTED

### NEW UNMARKED UNTESTED PAKS

B78	12	INTEGRATED CIRCUITS, DATA & CIRCUITS OF TYPES, SUPPLIED WITH ORDERS	10/-
B80	8	DUAL TRANS. MATCHED O/P PAIRS NPL-SIL INTO-5 CAN	10/-
B82	10	OC45, OC81D & OC81 TRANS. MULLARD GLASS TYPE	10/-
B83	200	200 TRANSISTORS, MAKERS REJECTS, NPN-PNP, SIL. & GERM.	10/-
B84	100	SILICON DIODES DO-7 GLASS EQUIV. TO OA200, OA202	10/-
B66	150	HIGH QUALITY GERM. DIODES MIN. GLASS TYPE	10/-
B86	50	SIL. DIODES SUB. MIN. IN914 & IN916 TYPES	10/-
B87	100	GERM. PNP TRANS. EQUIV. TO OC44, OC45, OC81, ETC.	10/-
B88	50	SIL TRANS, NPN, PNP, EQUIV. TO OC200/1, 2N706A, BSY95A, ETC.	10/-
B60	10	7 WATT ZENER DIODES, MIXED VOLTAGES	10/-
H5	16	1 AMP. PLASTIC DIODES 50-1000 VOLTS	10/-
H6	40	250mW, ZENER DIODES DO-7 MIN. GLASS TYPE	10/-

### Return of the unbeatable P.1 Pak. Now greater value than ever

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak **P.1**. Only **10/-** 2/- P & P on this Pak.

Make a Rev. Counter for your Car. The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a perfectly linear and accurate rev. counter for any car. **20/- each**

### FREE CATALOGUE AND LISTS for:—

**ZENER DIODES  
TRANSISTORS, RECTIFIERS  
FULL PRE-PAK LISTS  
& SUBSTITUTION CHART**

MINIMUM ORDER 10/- CASH WITH ORDER PLEASE. Add 1/- post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

**P.O. RELAYS** 8 for  
VARIOUS CONTACTS AND COIL RESISTANCES. NO INDIVIDUAL SELECTION. POST & PACKING 5/- **20/-**

**SPECIAL OFFER**  
12 VOLT STABILISED  
POWER UNITS  
INPUT 110-250 V. AC.  
OUTPUT 11-13V Stabilised  
at 1 amp.  
Brand New makers surplus  
at the unrepeatable  
Price of £5 each  
Post & Packing 7/6.


**FREE! A WRITTEN GUARANTEE WITH ALL OUR TESTED SEMICONDUCTORS**

# BI-PRE-PAK LTD

DEPT. B, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX  
TELEPHONE: SOUTHEND (0702) 46344
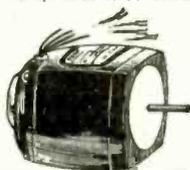
# Electro-Tech Sales

**NEW HYSTERESIS MOTORS BY WALTER JONES.** Type 14050/12, 240v. 50 c/s 1500 RPM cont. rating, output 2.0 oz./in. Size: Length (less spindle) 3 3/4". Width 2 1/4" x 2 1/4". Spindle 1" x 3/16". Weight 3 lb. Maker's price in region of £22.10.0. Our price £6.10.0. each.




**K.L.G. Sealed Terminals.** Type TLS1 AA, overall length 1 1/16", box of 100, 25s. Type TLS1 BB, overall length 1", box, of 100, 35s.



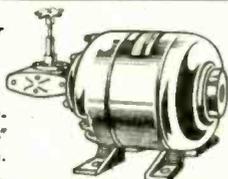
**"Parvalux" Reversible 100 RPM Geared Motor**

Type S.D.14, 230/250v. A.C. 22 lb./in. Standard foot mounted, variable angle final drive. Removable 9-tooth chain spigot on 3/16" spindle. 1st class condition. £7.10.0 each. P. & P. 10/-.



**PARVALUX TYPE S/D23 GEARED MOTORS.** 240v. A.C. 1 RPM. 14lbs./in. Also 240v. A.C. 2 RPM. 11 lbs./in. Continuous rating. Standard foot mounting. £4.15.0 each. P. & P. 10/-.

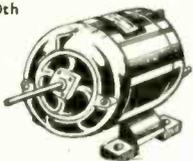**NEW "CROYDON" 240v. A.C. reversible motors.** Choice of 1/50th HP, 1,500 RPM, or 1/100th HP, 750 RPM (identical in appearance). Size 3 1/2" high x 5" long plus spindle 1 1/8" x 1/8" dia. A beautiful motor at less than half maker's original price. £6.10.0 each.




**English Electric 1/2 h.p. Motors.** 240v. single-phase, standard foot mounted, 1,425 r.p.m., continuous rating. £4.15.0. Carriage 20/-.

**Isolation Transformers.** 1 to 1 ratio. 240v. input, 240v. centre tapped out, at 2 K.V.A., mounted in metal case measuring 8 1/2" x 8 1/2" x 11" high. Weight 65lb. £16.10.0. Plus £1 carriage.

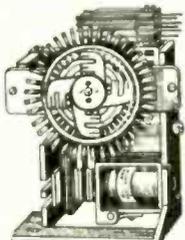**SCHRACK ROTARY STEPPING RELAY RT304**

48v. coil (28 ohm). The relay has 48 basic segments shorted in step by the 4 sweep contacts to 4 pole-plates (banks of 12). There are 2 secondary switches: (1) one c/o H/Duty contact set which changes over and back with each step; (2) two H/Duty changeovers which changeover on each 12th step and return on the following pulse. Size: Base 3 1/2" x 1 1/2" x 4 1/2" high. New in maker's packing, also, as above, but 110v. (1,290 ohm coil), £4.15.0 each.



**Welwyn high value Resistors Type GA 36501.** Values between 9.4 and 10.9 kilo-meg ± 1%, glass encapsulated 15/-.

**Victoreen "Hi-Meg" Resistors.** One value only 50,000 meg ± 2%, glass encapsulated 15/-.


**THORN DIGITAL INDICATOR** designed as a modular unit for easy mounting where 1st class numerical readout is required. Easily read through a wide angle of view and under bright ambient lighting. 12 characters, 0 to 9, decimal point and minus sign. Characters 13/16" high engraved on acrylic slides and individually edge-lit by 1 watt midjet-panel lamps. Overall size of front panel 4 1/2" high x 1 1/2" overall depth 1" finished in matt black supplied with 12 lamps, choice of following ratings—6v. .1A. or 12-14 v. .08A. £4.0.0 each, spare lamps 24/- per dozen.




**ATLAS SUB-MINIATURE LAMPS** type L1122 and L1123—high efficient light-source with excellent light-output and low power demand. Ratings 5v. 60 ma. .35 ± 25% lumens. Life expectancy 60,000 hours or at 6 v. 70 ma. .75 ± 25% lumens 5,000 hours. Dimensions: Uncapped 6.3 x 3.1 mm, leads 12.7 mm. capped 9.1 x 3.1 mm. Ideal for instrument lighting normally sold in excess of 12/- each, our price 30/- per dozen or boxes of 50 at £5 per box.



**ATLAS MIDGET PANEL LAMPS** unrivalled for indication purposes requiring a brilliant but tiny light source. Available with flange cap or wire ended in the following ratings: Capped: 6v. .1A and 12-14v. .08A. Uncapped: 4v. .25A., 6v. .1A., 6v. .2A. 24/- per dozen or boxes of 50 at £4 per box. **INDICATOR LAMP HOLDERS AND CAPS** for MIDGET PANEL LAMPS (as above) available red, green, blue. 2/6 each (complete) minimum order 4 units.

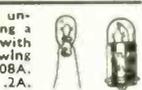

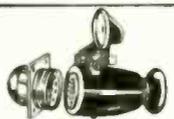**THORN TRAILER CONNECTORS**—These special 12 way connectors are for heavy vehicle applications and allow uncoupling by strain on the cable. Spring loaded protection caps give a full weather insulation sealing immediately on uncoupling. Heavy rubber sleeve on plug ensures maximum safety £3.0.0 per pair (plug and socket).



**THORN ILLUMINATED PRESS SWITCH** for 250v. operation. M.E.S. Pressure on cap completes a second circuit. Very robust. Length 44.5 mm. dia. 30.5 mm. in amber, green or red. 10/6 each.



**"Tansitor" (U.S.A.) Tantalum, Wet Sintered Anode Polarized Capacitors.** 1200 UF. 6v. D.C. size: 1 1/2" long x 1" dia. 200 UF. 25v. D.C. size: 1" long x 1/2" dia. 180 UF. 25v. D.C. size: 1" long x 1/2" dia. 150 UF. 30v. D.C. size: 1" long x 1/2" dia. 33UF. 75v. D.C. size: 1" long x 9/32" dia. One wire each end. All types 5/- each. Also few only, Tansistor "MICRO-MODULE" capacitors 0.2 Mfd. 15v. wire-ended, size: 3/32" dia. (disc) 5/- each.

**American "Powerstat" Variable Voltage Transformer** by Superior Electric Co. Input 120v. 50/60 c.p.s. Output 0-120v. at 2-25 amps. 1/2" spindle with alternative pre-set locking device. Size (approx.) 3" dia. x 2" long. First class condition. £2.15.0. P. & P. 5/-.

**Berco Rotary "Regavolt" variable voltage transformers** input 240v. 50/60 c.p.s., output 0-240v. C.T. at 6 amps. Not new, but in 1st class condition. Few only, £8.10.0. P. & C. 10/-.

**Gardner Transformer Type I.T.N. 876 (new).** Enclosed in ventilated metal case. Prim 200/250, sec. 2 x 12v. windings rated 4 amps each (96 v.a. in series/parallel). £3.2.6.

**WE WELCOME OFFICIAL ORDERS FROM ESTABLISHED COMPANIES, EDUCATIONAL DEPTS., ETC.**

**SYLVANIA MAGNETIC SWITCH**—a magnetically activated switch operating in a vacuum. Switch speed—4ms. temperature —54 to +200° C. Silver contacts normally closed rated 3 amps. at 120v. 1.5 amp. at 240v. 10/- each. £4.10.0 per dozen. Special quotations for 100 or over. Reference Magnets available 1/6 each.




**SYLVANIA CIRCUIT BREAKERS** gas filled providing a fast thermal response between 80° and 180°C. Will withstand pressures up to 2,000 lb. sq./in. rated 10 amp. at 240v. continuous. Fault currents of 28 amps. at 120v. or 13 amp. at 240v. silver contacts. Supplied in any of the following opening temperatures (degs. cent.) 80, 85, 95, 100, 105, 110, 120, 125, 130, 135, 140, 145, 150, 155, 160, 170, 175, 180. 10/- each or £4.10.0 per dozen.

**MINIATURE "LATCH-MASTER" RELAY** 6, 12, or 24v. D.C. operation. One make one break, contacts rated 5 amps. at 30v. Once current is applied, relay remains latched until input polarity is reversed. Manufactured for high acceleration requirements by Sperry Gyroscope Co. Size: Length 1 1/2", dia. 9/16" (including mount). Please state vertical or horizontal mount and voltage. £2.5.0 each.



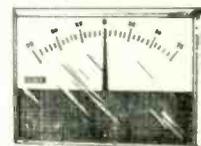**New 75-0-75 Micro-ammeter by Sifam.**

750 ohm movement, clear reading, 5µa divisions x 1/2"; plastic front, projection 1/8" (tapering forward). Size: 4 1/2" x 3 1/2", 57/6 each.



**Ernest Turner 5" x 4" 0-1 Ma. calibrated 0-10 in 50 divisions mirrored scale, handsome chrome escutcheon for flush mounting. A quality instrument. £6.10.0.**

**MINIATURE B.P.L. 500-0/500 Micro-Ammeter.** 13/16" Diam. scale. Through-Panel mounting, 45/-.

**"AUTOMATIC ELECTRIC" ENCLOSED RELAYS**  
6v. 50Ω 2 c/o, 12/6  
24v. 470Ω 4 c/o, 13/6  
48v. 2,780Ω 4 c/o, 13/6  
48v. 1,260Ω 6 c/o, 15/-



**New "Magnetic Devices" solenoid 240v. A.C. Type 42117, 1 to 3 lb. pull, frame size 1 1/2" x 1 1/2" x 1". 20/- each.**



**Motor Driven Variable Voltage Transformers by Ohmite (U.S.A.).** Input 120/240v., 50/60. c.p.s. Output 0-240v. at 480 v.a. A reversible 115v. a.c. geared motor drives the contact sweep arm in the direction required. There is a micro switch mounted at each end of the track which is cam-operated and intended to be connected as a safety-stop. First class condition. £8.15.0. P. & P. 10/-.



We have a considerable range of glassware, many grades of filter paper, balances, centrifuges, ovens, pumps, etc., etc., for personal callers.

**WHERE NO CARRIAGE CHARGE IS INDICATED PRICE IS INCLUSIVE. PERSONAL CALLERS WELCOME.**

## ELECTRO-TECH SALES

**BUSINESS HOURS: 264 PENTONVILLE ROAD, LONDON, N.1**  
9.30-6 (1 p.m. Sats.) (ONE MIN. FROM KINGS X STATION) Tel. 01-837 7401

### TRANSFORMERS

### COILS

LARGE OR SMALL QUANTITIES

### CHOKES

TRADE ENQUIRIES WELCOMED

SPECIALISTS IN

### FINE WIRE WINDINGS

MINIATURE TRANSFORMERS  
RELAY AND INSTRUMENT COILS, ETC.  
VACUUM IMPREGNATION TO APPROVED STANDARDS

### ELECTRO-WINDS LTD.

CONTRACTORS TO G.P.O., A.W.R.E., L.E.B., B.B.C., ETC.

123 PARCHMORE ROAD, THORNTON HEATH, SURREY  
01-653 2261 CR4.8LZ EST. 1933

WW-121 FOR FURTHER DETAILS



**For electronic components fast...**

### Radiospares

13-17 Epworth St., London E.C.2.  
Tel: 01-253 9561. Telex: 262341.

WW-122 FOR FURTHER DETAILS

**CURRENT RANGE OF BRAND NEW LT. TRANSFORMERS, FULLY SHROUDED (\*excepted) TERMINAL BLOCK CONNECTIONS. ALL PRIMARIES 220/240v**

No.	Sec. Taps	Amps	Price	Carr.
1A	25-33-40-50	15	£10 0 0	12/6
1B	25-33-40-50	10	£7 12 6	9/6
1C	25-33-40-50	6	£6 15 0	9/6
1D	25-33-40-50	3	£7 0 0	7/6
2A	4-16-24-32	12	£7 2 6	8/6
2B	4-16-24-32	8	£5 7 6	8/6
2C	4-16-24-32	4	£3 12 6	7/6
2D	4-16-24-32	2	£2 7 6	5/-
3A*	25-30-35	40	£16 10 0	12/6
3B*	25-30-35	20	£10 3 0	10/6
3C	25-30-35	10	£7 5 0	8/6
3D	25-30-35	5	£4 2 6	7/6
3E	25-30-35	2	£3 2 6	7/6
4A*	12-20-24	30	£13 0 0	12/6
4B	12-20-24	20	£8 5 0	9/6
4C	12-20-24	10	£4 5 0	8/6
4D	12-20-24	5	£3 12 6	7/6
5A	3-12-18	30	£9 12 6	9/6
5B	3-12-18	20	£7 2 6	8/6
5C	3-12-18	10	£4 5 0	7/6
5D	3-12-18	5	£2 17 6	7/6
6A	48-56-60	2	£3 12 6	6/6
6B	48-56-60	1	£2 12 6	6/6
7A*	6-12	50	£10 7 6	10/6
7B	6-12	20	£6 2 6	8/6
7C	6-12	10	£3 17 6	7/6
7D	6-12	5	£2 15 0	6/6
8A	12-24	8	£1 12 6	6/6
9A	17-32	8	£6 3 0	8/6
10A*	9-15	2	£1 9 6	6/6
11A	6-3	15	£2 10 0	7/6
12A	30-25-0-25-30	2	£3 12 6	6/6

Note: By using the intermediate taps many other voltages can be obtained.

Example: No. 1 ... 7-8-10-15-17-25-33-40-50v.  
 No. 2 ... 4-8-12-16-20-24-32v.  
 No. 5 ... 3-6-9-12-15-18v.

**AUTO TRANSFORMERS**

240v.-110v. or 100v. Completely shrouded fitted with two-pin American sockets or terminal blocks. Please state which type required.

Type	Watts	Approx. Weight	Price	Carr.
1	80	2½ lb	£1 19 6	5/6
2	150	4 lb	£2 12 6	6/6
3	300	6½ lb	£3 12 6	6/6
4	500	8½ lb	£5 2 6	8/6
5	1000	15 lb	£7 2 6	9/6
6*	1500	25 lb	£9 15 0	10/6
7*	1750	28 lb	£14 15 0	12/6
8*	2250	30 lb	£17 17 6	15/-

\* Completely enclosed in beautifully finished metal case fitted with two 2-pin American sockets, neon indicator, on/off switch, and carrying handle.

TRANSFORMERS, VARIABLE TRANSFORMERS, CHOKES, CAPACITORS, L.T. SUPPLY UNITS. Send 6d. stamp for latest 12-page Price List.

**SPECIAL OFFER LT. TRANSFORMERS**

PRI 220-240v. sec tapped 6-12 volts 2 amps fully shrouded terminal block connections. Tropicalised screen between PRI and sec. By famous manufacturers. Size H 3ins., D4 ins., inc. T.B.W. 2½ins. 15/- P. & P. 3/6.

**PARMEKO NEPTUNE SERIES TRANSFORMERS**  
 PRI tapped 200-220-240v. Sec. 250-0-250v. 50M/A. 6.3v. 1A. Size H 4 x 3 x 2½ins. with fixing bolts brand new in makers' carton. 22/6. P. & P. 4/6. PRI 230v. Sec. 4.2v. 1A. Size H 3½ x 2½ x 2½ins. with fixing bolts. 10/6. P. & P. 4/6. PRI 230v. Sec. tapped 1.8v. 2A. 3.6v. 3A. 4.1v. 3.2A. 4.9v. 3.6A. 17/6. P. & P. 3/6.

**Samson's**  
 (ELECTRONICS) LTD.  
 9 & 10 CHAPEL ST., LONDON, N.W.1  
 01-723-7851 01-262-5125

**PARMEKO CHOKES—NEPTUNE SERIES**  
 10H. 180M/A., 25/- P. & P. 5/-. 10H. 120M/A., 12/6. P. & P. 4/-. 10H. 75M/A., 15H. 75M/A., 15H. 50M/A., 5H. 120M/A., 5H. 60M/A., 50H. 25M/A. all types. 8/6 each. P. & P. 3/6. 0.7H. 450M/A. 12/6. P. & P. 4/6. 1H. 300M/A. 10/6 P. & P. 4/6. 5H. 150M/A. 17/6.  
**JUPITER SERIES SWINGING CHOKE**  
 34H. 60M/A.-70H. 35M/A., 2.8kv., D.C. Wkg. 25/- P. & P. 6/-.  
**PARTRIDGE TOTALLY ENCLOSED CHOKES**  
 5H. 250M/A. 19/6. P. & P. 6/-. GRESHAM SEALED OIL-FILLED CHOKES: 12H. 200M/A. 29/6. P. & P. 7/6. HADDONS: 12H. 60M/A. 10/6. P. & P. 5/-. L.T. SMOOTH SWINGING CHOKE: 16M/H. 8 amps. 35/- P. & P. 5/-. GRESHAM SWINGING CHOKE: 20H. 100M/A. 10H. 450M/A. 49/6. P. & P. 7/6.

**GARDNERS H.T. TRANSFORMERS**  
 C core Pri 200-240v. Sec 300-0-300v. 60M/A., 6.3v. 4 amps. Size 3½ x 3 x 3ins. 25/- P. & P. 4/6.  
**LOW VOLTAGE ISOLATION TRANSFORMERS**  
 Sec. 6.3v. Sec. 2.0-2v. 4A 5kv. Wkg. "C" core potted type. 17/6. P. & P. 3/6.

**SPECIAL OFFER OF SLIDING RESISTORS**  
 Single tube sliders. 14Ω 1-4A. 15/- P. & P. 3/6. 1Ω 12A. 15/- P. & P. 3/6. 1000Ω 1A. 47/6. P. & P. 8/6. R/angle geared drive 30Ω 1.5A. 19/6. P. & P. 4/6. Normal geared drive. 782Ω 1A. 52/6. Carr. 8/6. Single tube fixed 45-4-12Ω 6.5A/4A. 27/6. P. & P. 6/6. Single tube adjustable 57.2Ω 2.8A. 27/6. P. & P. 5/6. Single tube fixed 71.5Ω 2.8A. 25/- P. & P. 5/6. Single tube adjustable 0.6Ω 16A. 15/- P. & P. 3/6. vitreous fixed 1KΩ 70 watts. 5/- P. & P. 1/6.

**COLVERN INST POTS**  
 20KΩ 2½ins. dia. 10/- P. & P. 2/-. 1500Ω 1½in. dia. ceramic. 8/6 P. & P. 2/-. 220Ω 3in. dia. 10/- P. & P. 2/-. Curtis 1250Ω 0.3A 2ins. dia.

**2-INCH ROUND PANEL METERS**  
 0-20 D.C. amps. M.C. 12/6. P. & P. 2/-. 0-40 D.C. amps M.C. 12/6. P. & P. 2/-. 0-50 D.C. volts M.C. 12/6. P. & P. 2/-. 3-inch sq. flush. 0-80v. D.C. M.C. 1000Ω per volt. 17/6. P. & P. 2/-.  
**AIR MINISTRY HEAVY DUTY CUT-OUTS**  
 Type 6. ZA2413. Enclosed in bakelite case, 3½ x 3½ x 2½ins. 12/6. P. & P. 3/6.

**24v. D.C. MINIATURE GEAR MOTORS**  
 600 r.p.m. Overall size 2 x 1½ x 1½ins. spindle length 1in. jin. dia. 10/6. P. & P. 2/6.

**PLESSEY A.C. 220-240v. SOLENOIDS**  
 Very powerful. Overall size 2½ x 2 x 2ins. Pull 1½ins. 19/6. P. & P. 3/6.

**DIGITAL HOUR METERS**  
 6 figs inc. 1/10ths, 1/100ths 40v. A.C. but complete with transformer for 240v. A.C. operation. All in plastic case. Size 6½ x 6½ x 3in. Condition as new 45/- P. & P. 5/-.  


**NEWMARK SYNCHRONOUS MOTORS**

220-240v. 50 cycles, 3 watts 8 r.p.m. Overall size 2 x 2 x 2ins. 10/6. P. & P. 1/6.



**LONDEX 220-240v. A.C. RELAYS**  
 Open frame type 12 heavy make contacts. 27/6. P. & P. 5/-.

**VENNER SYNCHRONOUS BIO-DIRECTIONAL MOTORS**


220-240v. 50 cycles 40 r.p.m. automatically reverses wherever spindle stop is placed overall size 2½ x 2 x 2ins. Spindle length ½in. dia. 1/16th. An ideal motor for display, giving a forward and reverse motion. 12/6. P. & P. 2/6.

**CROUZET SHADED POLE MOTORS**  
 A.C. 115/230v. 10 watts. 1 r.p.m. Overall size 2½in. dia. depth 2ins. Spindle ½in. dia. ½in.

**INGRAM SYNCHRONOUS GEARED MOTORS**  
 220-240v. 50 cycles, 3 watts, 6 rev. per hour. Overall size 2½ x 2 x 2ins. Cog spindle length ½in. 8/6. P. & P. 2/-.  
**ISOLATION TRANSFORMERS**  
 Built into metal case, size 8 x 7 x 7ins., with on/off switch, neon indicator. 13A 3-pin socket outlet. Pri. 220-240v. Sec. 220-240v. 1000 watts. £16.10.0. Carr. 15/- 750 watts. £14.10.0. Carr. 12/6. Sec. Open frame type. Terminal block connections. Pri. 240v. Sec. tapped 110-240v. 2½kva. cont. rating. Size 9 x 8 x 8ins. Weight 65 lbs. £29.10.0. ex warehouse.


**VARIABLE D.C. SUPPLY UNITS TYPE S.E.4**

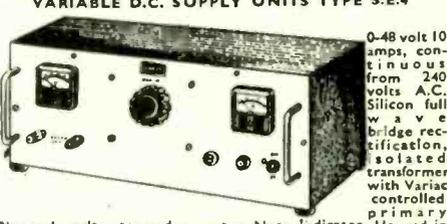0-48 volt 10 amps, continuous from 240 volts A.C. Silicon full wave bridge rectification, isolated transformer with Variac controlled primary  
 3in. scale voltmeter and ammeter. Neon indicator. Housed in strong metal case. Size 17 x 7 x 6½in. £32.10.0. Carr. 15/-



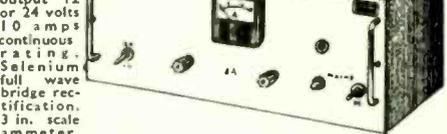**L.T. SUPPLY UNITS TYPE S.E.3**

A.C. input 220-240 volts. D.C. output 12 or 24 volts 10 amps continuous rating. Selenium full wave bridge rectification. 3 in. scale ammeter, neon indicator. Housed in strong metal case. £17.10.0. Carr. 15/-



**HEINEMANN MAGNETIC CIRCUIT BREAKERS**  
 3 ph 440v. 3 pole 7.5 amps panel mounting. 25/- P. & P. 5/-. Chilton circuit breakers 440v.-240v. 2 pole with solid neutral. 15 amps. 25/- P. & P. 5/-. Single pole with solid neutral 20 amps. 15/- P. & P. 3/6.

**WEYRAD**

**COILS AND I.F. TRANSFORMERS IN LARGE-SCALE PRODUCTION FOR RECEIVER MANUFACTURERS**

- P.11 SERIES** 10 mm. x 10 mm. x 14 mm. Ferrite cores 3 mm. 472 kc/s operation. Single-tuned I.F.s and Oscillator Coils.
- P.55 SERIES** 12 mm. x 12 mm. x 20 mm. Ferrite cores 4 mm. 472 kc/s operation. Single-tuned I.F.s and Oscillator Coils.
- T.41 SERIES** 25 mm. x 12 mm. x 20 mm. Ferrite cores 4 mm. 472 kc/s operation. Double-tuned 1st and 2nd I.F.s and Single-tuned 3rd I.F. complete with diode and by-pass capacitor.

These ranges are available to manufacturers in versions suitable for most of the popular types of Transistors. The Oscillator coils can be modified to enable specific tuning capacitors to be used provided that bulk quantities are required.

**OUR WINDING CAPACITY NOW EXCEEDS 50,000 ITEMS PER WEEK**

On the most up-to-date and efficient machines backed by a skilled assembly labour force for all types of coils and assemblies.

**WEYRAD (ELECTRONICS) LIMITED, SCHOOL ST., WEYMOUTH, DORSET**

# R+TV

**RADIO & TV COMPONENTS (Acton) LTD**  
 21a High Street, Acton, London, W.3.  
 also 323 Edgware Road, London, W.2.  
 Goods not dispatched outside U.K. Terms C.W.O. All enquiries S.A.E.

## Complete stereo system—£29 10s.

The new Duo general-purpose 2-way speaker system is beautifully finished in polished teak veneer, with matching vinylair grille. It is ideal for wall or shelf mounting either upright or horizontally.

**Type 1 SPECIFICATION:**

Impedance 3, 8, or 10 ohms (please state impedance required). It incorporates high flux 6" x 4" speaker and 2 1/2" tweeter. Teak finish 12" x 6 1/2" x 5 1/2". 4 guineas each, 7/6 p. & p.

**Type 2** as type 1. Size 17 1/2" x 10 1/2" x 6 1/2". Incorporating 10 1/2" x 6 1/2" bass unit and 2 1/2" tweeter. 3 ohms impedance. 6 guineas plus 15/- p. & p.

Garrard Changers from £7.19.6d. p. & p. 7/6d.

Cover and Teak finish Plinth £4.15.0d. 7/6d. p. & p.

*Duetto* Integrated Transistor Stereo Amplifier **£9 10s.**  
 plus 7/6d. p. & p.

The Duetto is a good quality amplifier, attractively styled and finished. It gives superb reproduction previously associated with amplifiers costing far more.

**SPECIFICATION:**

R.M.S. power output: 3 watts per channel into 10 ohms speakers

**INPUT SENSITIVITY:** Suitable for medium or high output crystal cartridges and tuners. Cross-talk better than 30dB at 1 Kc/s.

**CONTROLS:** 4-position selector switch (2 pos. mono and 2 pos. stereo) dual ganged volume control.

**tone CONTROL:** Treble lift and cut. Separate on off switch. A preset balance control.



These 5 items can be purchased together for £29 10s+£1 10s p. & p.



*The Classic*  
 TEAK FINISHED CASE  
**£9**  
 plus 7/6 p. & p.  
 Built and tested.

**SPECIFICATION**

Sensitivities for 10 watt output at 1 KHz into 3 ohms. Tape Head: 3mV (at 3 1/2 l.p.s.). Mag. P.U.: 2 mV. Cer. P.U.: 80 mV. Tuner: 100 mV. Aux. 100 mV. Tape/Rec. Output: Equalisation for each input is correct to within ±2dB (R.I.A.A.) from 20 Hz to 20KHz. Tone Control Range: Bass ±13 dB at 60 Hz. Treble ±14 dB at 15 KHz. Total Distortion: (for 10 watt output) <1.5%. Signal Noise: <-60dB. AC Mains 200-250v. Size 12 1/2" long, 4 1/2" deep, 2 1/2" high.



*The Viscount*  
 INTEGRATED HIGH FIDELITY TRANSISTOR STEREO AMPLIFIER  
**£14 5s.** + 7/6 p. & p.  
 Built and tested.

**SPECIFICATION**

OUTPUT: 10 watts per channel into 3 to 4 ohms speakers (20 watts) monoral.  
 INPUT: 6-position rotary selector switch (3 pos. mono and 3 pos. stereo). P.U. Tuner. Tape and Tape Rec. out Sensitivities: All Inputs 100 mV into 1.8M ohm.  
 FREQUENCY RESPONSE: 40Hz-20KHz±2DB.  
 TONE CONTROLS: Separate bass and treble controls. TREBLE 13dB lift and cut (at 15KHz) BASS: 15dB lift and 25dB cut (at 50Hz).  
 VOLUME CONTROLS: Separate for each channel. AC MAINS INPUT: 200-240v. 50-60Hz.  
 Viscount Mark II for use with magnetic pick ups specification as above. Fully etalised for magnetic pick ups. Suitable for cartridges with minimum output of 4mV/cm/sec at 1kc. Input Impedance 47k. **£15 15s.** plus 7/6 p. & p.



**THE RELIANT MK.II**  
 Solid State  
 General Purpose Amplifier  
 In teak-finished case  
**£6 16s.**  
 +7/6 p. & p.

**SPECIFICATION**

OUTPUT: 10 watts into a 3 ohms speaker.  
 INPUTS: (1) for mike (10 m.v.). Input (2) for gram. radio (250 m.v.) individual bass and treble control.  
 TRANSISTORS: 4 silicane and three germanium.

MAINS INPUT: 220/250 volts.  
 SIZE: 10 1/2" x 4 1/2" x 2 1/2".

Mk. 1 **£5 15s.** + 7/6d. p. & p. less Teak-finished case

**X101 10w. SOLID-STATE HI-FI AMP**  
 With Integral Pre-amp.



Specifications: Power Output (into 3 ohms speaker) 10 watts. Sensitivity (for rated output): 1mV into 3K ohms (0.33 microamp) Total Distortion (at 1 KHz): At 5 watts 0.35%. At rated output 1.5%. Frequency Response: Minus 3 dB points 20 Hz and 40 KHz. Speaker: 3-4 ohms (3-15 ohms may be used). Supply voltage: 24v D.C. at 800 mA (6-24v may be used).


**69/6** plus 2/6 p. & p.

**CONTROL ASSEMBLY:** (including resistors and capacitors). 1. Volume: Price 5/-. 2. Treble: Price 5/-. 3. Comprehensive bass and treble: Price 10/-. The above 3 items can be purchased for use with the X101. **POWER SUPPLIES FOR X101:** P101 M (mono) 35/- p. & p. 4/6; P101 Stereo) 42/6 p. & p. 4/6.



**THE DORSET**  
 (600mW Output)  
**£5.5.0**  
 plus 7/6 p. & p.  
 Circuit 2/6. FREE WITH PARTS  
**MAINS POWER PACK KIT:**  
 9/6 extra.

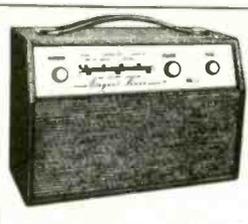7-transistor fully tunable M.W.-L.W. superhet portable—with baby alarm facility. Set of parts. The latest modulized and pre-alignment techniques makes this simple to build. Sizes: 12" x 8" x 3".



**ELEGANT SEVEN MK. III**  
 (350mW Output)  
**£5.5.0**  
 plus 7/6 p. & p.  
 Circuit 2/6. FREE WITH PARTS  
**MAINS POWER PACK KIT:**  
 9/6 extra.

7-transistor fully tunable M.W.-L.W. superhet portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.



**50 WATT AMPLIFIER**  
 AC MAINS 200-250V  
**£28 10s.**  
 plus 20/- p. & p.

An extremely reliable general purpose valve amplifier. Its rugged construction yet space age styling and design makes it by far the best value for money.

**TECHNICAL SPECIFICATIONS**  
 3 electronically mixed channels, with 2 inputs per channel, enables the use of 6 separate instruments at the same time. The volume controls for each channel are located directly above the corresponding input sockets. **SENSITIVITIES AND INPUT IMPEDANCES.** Channels 1 & 2 4mV at 470K. These 2 channels (4 inputs) are suitable for microphone or guitars. Channels 3 & 4 300mV at 1M. Suitable for most high output instruments (gram, tuner, organ, etc.). Input sensitivity relative to 10w output. **tone CONTROLS ARE COMMON TO ALL INPUTS.** Bass Boost +12dB at 60 Hz. Bass Cut -13dB at 60 Hz. Treble Boost +11dB at 15 KHz. Treble Cut -12dB at 15 KHz. With bass and treble controls central -3dB points are 30 Hz and 20 KHz. **POWER OUTPUT:** For speech and music 50 watts rms. 100 watts peak. For sustained music 45 watts rms. 90 watts peak. For sine wave 38.5 watts rms. Nearly 80 watts peak. Total distortion at rated output 3.2% at 1KHz. Total distortion at 20 watts 0.15% at 1KHz. Output in match into 8 or 15 ohms speaker system. **NEGATIVE FEEDBACK** 20dB at 1 KHz. **SIGNAL TO NOISE RATIO** 60dB. **MAINS VOLTAGES** adjustable from 200-250V. AC 50-60 Hz. A protective fuse is located at the rear of unit. Output impedance 3, 8 and 15 ohms.

**NEW COMPLETE HI-FI STEREO SYSTEM £41**  
 comprising SP25 Garrard Mk II with diamond stereo cartridge or 2025TC. Viscount amplifier Mk I. Two type 2 speakers, plinth and cover.  
**£41** plus £2.10s. p. & p.

**SPECIAL OFFER**  
 Complete stereo systems comprising BALFOUR 4 speed auto player with stereo head 2 DUO speaker systems size 12 x 6 1/2 x 5 1/2. Plinth (less cover) and the DUETTO stereo amplifier. All above items  
**£25** plus £2 p. & p.

**A WIDE SELECTION OF SERVOMOTORS NOW AVAILABLE INCLUDES THE FOLLOWING TYPES:**

Mil size 11-400 Hz versions for 26 and 115v. operation with 10/20, 13/26 and 57.5/115v. control phase windings.  
 Mil size 08, 10, 11, 15 and 18 motor generators for 400 Hz operation with 26 and 115v. energised tachogenerators.  
 Mil size 08, 10, 15 and 18 two phase servomotors also available with 400 Hz windings and a limited range in 50 Hz types.  
 Mil Permanent Magnet Field Servomotors Size 08, 11, 15 and 18 with supply voltages from 6 to 50v. D.C.  
 Mil Tachogenerators Size 08 and 10 for 400 Hz supply.  
 Mil Size 11 Servomotor gearheads available in various ratios from 10:1 to 1000:1.  
 All items available ex stock and at extremely competitive prices.  
**Evershed and Vignoles' Servomotors and Servomotor-generators**—we hold stocks of this well known manufacturer's items amounting to about 100 different types—an enquiry stating your broad design considerations will bring a reply by return indicating ex stock availability of the motor most nearly meeting your requirements.  
 Write for our Data Sheets A 131 onwards for details of available Servomotors.  
**MIL SYNCHROS** available ex stock in sizes 08, 11, 15, 16, 18 and 23 for 50, 60 and 400 Hz operation.  
**Synchro Control Transformers**  
 Synchro Control Transmitters  
 Synchro Torque Differential Transmitters  
 Synchro Torque Transmitters and Receivers  
 Synchro Resolvers  
**Equivalent MAGSLIP ELEMENTS** more suitable for educational use also in stock.  
 Write for our Data Sheets A 001 onwards for Synchro and Magstrip information.  
**400 Hz. MOTOR ALTERNATOR SETS** Input 400/440v. 50 Hz 3 ph. output 115v. 400 Hz 150VA. (coml. rating) for external excitation £15.

**PRECISION POTENTIOMETERS**

Numerous instrument types, continuous rotation potentiometers for control application and HELIPOTS in stock. List on application.

**Gertsch COMPLEX RATIO BRIDGE Model CRB28.** Six digits in phase, four digits in quadrature. Our Price £200. Carriage extra at cost on all items.



**DRY REED INSERTS** Overall length 1.85" (Body length 1.17" Diameter 0.14" to switch 500mA at up to 250v. D.C. Heavily gold clad contacts. 12/6d. per doz., 75/- per 100, £27.10.0 per 1000 for quantities over 1000, £25.0.0 per 1000 for quantities over 10,000. All carriage paid.

**REED RELAYS** Low voltage 200 ohm coil, 4 make contacts 7/6d. each (P. & P. 1/-). Send for our list of several other reed relays available.

**I.S.E.P. CONNECTORS** Quantities of 11-wire male P.C. version in stock.  
**TRANSISTORS** Manufacturers' quantities of the following available: BSX76 (CV8615) fast switching silicon n-p-n. For quantities 100-999 2/- ea., 1000-4999 1/9d., over 5000 1/7d. ea. ACY20 medium power a.s. germanium. For quantities 100-999 1/10d. ea., 1000-4999 1/8d. ea., over 5000 1/6d. ea. Both items in makers' packs.

**CAMBRIDGE DYNAMOMETER VOLTMETERS** in as new condition. 10 range up to 150v. In as new condition £45.0.0 ea. plus carriage.

**NOISE GENERATORS** CT82 15KHz-160MHz into 43, 75 or 400 ohms £22.10.0.

**OSCILLOSCOPES** Solartron Type CD568 £27.10.0. Fully serviced.

**EVERSHED** 500v. WEE MEGGER in leather case. Fully checked £14.0.0 (Carr. Pd.).

**PLUGS, SOCKETS AND CONNECTORS**

Large stocks of PLESSEY Mk. IV or VI, 104; PAINTON ELECTROMETHODS; CANNON; BELLING LEE; AMPHENOL; TRANSRADIO items.

Enquiries to Orpington or Lydd.

**TANTALUM CAPACITORS**

We hold large stocks by S.T.C., DUBILIER, T.C.C. Immediate delivery!  
 KEMET PLESSEY GENERAL ELECTRIC

**G.E.C. SEALED RELAYS**

A very wide range of these difficult-to-obtain items in stock. List available.

**PRESENTING THE AUDIO Executive SIXTY**


A high output all-silicon AMPLIFIER of advanced design. We have incorporated into an amplifier all the desirable features that we would always have liked to offer during our several years experience of selling amplifiers—we now have a design incorporating the latest solid state all-silicon circuitry and the result is—

**THE AUDIO EXECUTIVE SIXTY!**

This creation, while being reasonably priced, provides the following desirable features:—

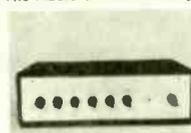1. A true 60 Watt R.M.S. continuous rating into 8 ohms.
2. True High Fidelity Performance.
3. Built-in filters to protect speakers.
4. Three independently mixed inputs which can be high or low impedance microphone, crystal ceramic or magnetic cartridge from disc, or from tape, tuner or other auxiliary equipment.

The amplifier is built into a luxurious, supple black semi-quilted plastic covered timber cabinet; the chassis, backed by a massive heat sink carrying the output transistors, input jacks, output sockets, mains voltage adjuster, mains and output fuses, carries the driver transistors mounted on their own substantial heat sink, the input and output controls and the on/off switch. The power supply components are mounted direct on the sturdy chromatised cadmium plated chassis. The Audio Executive Sixty fully meets the requirements for



Discotheques  
 General Sound Reinforcement Systems.  
 High Power HiFi Systems.  
 Vocal and Guitar Amplification.

Price **£58.15.0**

Guaranteed for six months. Individually packed in cartons. Trade Supplied

**SPECIFICATION**

Power Output: 60 watts continuous sine wave into 8 ohms (resistive), 40 watts continuous sine wave into 15 ohms (resistive). 5A fuse incorporated in output circuit.  
 Damping Factor: 30 (source impedance 0.5 ohm approx.).  
 Distortion: Total Harmonic Distortion at 1KHz at 60 watts into 8 ohms less than 1%, at 40 watts into 15 ohms less than 0.3%.  
 Frequency Response: ± 1db 40 Hz to 15 KHz.  
 Hum and Noise: -70 db.  
 Sensitivity: Input 1a 15mV Z=50K ohms flat.  
 1b 1.5mV Z=5K ohms flat.  
 Input 2a 4.5mV Z=50K ohms RIAA compensated.  
 2b 200mV Z=100K ohm. flat.  
 Input 3 200mV Z=100K ohm. flat.  
 Inputs 1 and 2 and 3 operate simultaneously offering full mixing facilities: choice of either a or b inputs, automatically disconnects the other. Alteration in level from any two inputs on altering the third from zero to maximum is typically -1 db.  
 Overload Capacity: Input 1 26 db. Input 2 26 db. Input 3 Infinity.  
 Power Bandwidth: -3 db. (8 ohms) 50Hz-18KHz.  
 Tone Control: Bass + 13 db to -16 db at 50 Hz.  
 Treble + 16 db to -13 db at 10 KHz.  
 Filters: -1 db points at 40 HZ and 15 KHz.  
 Mains Supply: 110, 120, 220, 240v 40-50 Hz.  
 Input fused at 2A.

*Servo and Electronic Sales Ltd.*

Electrical and Servo Control Engineers - Electrical Suppliers - Engineering Stockists - Aeronautical Suppliers  
 43 HIGH STREET, ORPINGTON, KENT. Phone: Orpington 31066/33976/33221  
 19 MILL ROAD, LYDD, KENT (Works). Phone: Lydd 252  
 67 LONDON ROAD, CROYDON, SURREY (Retail Branch and Instrument Repairs).  
 Phone: 01-688-1512 (Croydon)

**NO EXCUSES! NO DELAYS! FROM STOCK! VARIABLE VOLTAGE TRANSFORMERS**

**INPUT 230 v. A.C. 50/60**  
**OUTPUT VARIABLE 0/260 v. A.C.**  
**BRAND NEW.** Keenest prices in the country. All Types (and spares) from 1/2 to 50 amp. available from stock.

0-260 v. at 1 amp. ....	£5 10 0
0-260 v. at 2.5 amps. ...	£6 15 0
0-260 v. at 5 amps. ....	£9 15 0
0-260 v. at 8 amps. ....	£14 10 0
0-260 v. at 10 amps. ...	£18 10 0
0-260 v. at 12 amps. ...	£21 0 0
0-260 v. at 15 amps. ...	£25 0 0
0-260 v. at 20 amps. ...	£37 0 0
0-260 v. at 37.5 amps. ...	£72 0 0
0-260 v. at 50 amps. ...	£92 0 0

**20 DIFFERENT TYPES AVAILABLE FOR IMMEDIATE DELIVERY.**

**Double Wound Variable Transformers**  
 Fully isolated, low tension Secondary winding. Input 230 v. A.C. OUTPUT CONTINUOUSLY VARIABLE 0-36 v. A.C.

0-36 v. at 5 amp. £9.12.6—	p. & p. 8/6
0-36 v. at 20 amp. £21.0.0—	15/- p. & c.

These fully shrouded Transformers, designed to our specifications, are ideally suited for Educational, Industrial and Laboratory use.

**INSULATION TESTERS (NEW)**

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L. 8in. W. 4in. H. 6in. Weight 6lb.

**500 VOLTS, 500 megohms. Price £28 carriage paid.**  
**1,000 VOLTS, 1,000 megohms, £34 carriage paid.**

**5Amp. AC/DC VARIABLE VOLTAGE OUTPUT UNIT**

Input 230 v. A.C. Output 0-260 v. A.C. Output 0-240 v. D.C. Fitted large scale ammeter and voltmeter. Neon indicator, fully fused. Strong attractive metal case 15in. X 8in. X 6in. Weight 24 lb. Infinitely variable, smooth stepless voltage variation over range. Price £38 plus 30/- p. & c. Similar in appearance to illustration below.

**OPEN TYPES**  
 Designed for Panel Mounting.  
 Input 230 v. A.C. 50/60 Output variable.

0-260 v. ....	£3 10 0
1 amp. ....	£5 10 0
2 amp. ....	£6 12 6

P. & P. 7/6

1 AMP. 1 AMP.

**VAN DE GRAAF ELECTROSTATIC GENERATOR**

1 fitted with motor drive for 230 v. A.C. giving a potential of approx. 50,000 volts. Supplied absolutely complete including accessories for carrying out a number of interesting experiments, and full instructions. This instrument is completely safe, and ideally suited for School demonstrations. Price £7/7/- plus 4/- P. & P. L.T. on req.

**CONSTANT VOLTAGE TRANSFORMER**

Input 185-250 v. A.C. Output constant at 230 v. A.C. Capacity 250 watt. Attractive metal case. Fitted red signal lamp. Rubber feet. Weight 17lbs. Price £11/10/-, P. & P. 10/-.

**LATEST TYPE SOLID STATE VARIABLE CONTROLLER**  
 Ideal for lighting and heating circuits, compact panel mounting. Built in fuse protection. CONTINUOUSLY VARIABLE.  
 Input 230v AC output 25-230v AC  
 5 amp model £8. 7. 6  
 10 amp model £13. 5. 0

**SPEEDIVAC HIGH VOLTAGE HIGH FREQUENCY GENERATOR**  
 Input 100/110 volts or 200/250 volts AC/DC Output 19KV variable. Ideal for testing insulation, vacuum, leakage path, gas discharge lamps, neon etc. A useful ozone and HF supply. Manufactured by Edwards High Vacuum Ltd. Brand new in maker's polished wooden carrying case. Offered at fraction of maker's price. £10.0.0 plus 7/6 p. & p.

**36 volt 30 amp. A.C. or D.C. Variable L.T. Supply Unit**

INPUT 220/240 v. A.C. OUTPUT CONTINUOUSLY VARIABLE 0-36 v.

Fully isolated. Fitted in robust metal case with Voltmeter, Ammeter, Panel Indicator and chrome handles. Input and Output fully fused. Ideally suited for Lab. or Industrial use. £55 plus 40/- p. & c.

**SERVICE TRADING COMPANY**

# SERVICE TRADING CO

Postage and Carriage shown below are inland only. For Overseas please ask for quotation. We do not issue a catalogue or list.

## LARGE DIGIT 12-18 v. D.C. MAGNETIC COUNTER

4in. drum, calibrated 0-9. Figures 1 1/2in. high 3/16in. wide. Set of 1m, 1b, 1c/o contacts operated by drum cam. The units which can be used in multiples are ideally suited for batch or lap recording or for the many purposes where large easily read numerals are required. Price 18/6, P. & P. 2/6.



## VEEDER ROOT COUNTER

230 v. A.C. 50 cycle 5 figure counter (non resettable). 18/6, P. & P. 1/6.



## RING TRANSFORMER


Functional Versatile Educational

This multi-purpose Auto Transformer, with large centre aperture, can be used as a Double wound current Transformer, Auto Transformer, H.T. or L.T. Transformer, by simply hand winding the required number of turns through the centre opening. E.g. Using the RT.100 V.A. Model the output could be wound to give 8V. @ 12 1/2Amp., 4V. @ 25Amp. or 2V. @ 50Amp., etc. Price: RT.100VA 3.18 turns per volt, £2 5 0+3/6 p. and p. RT.300VA 2.27 turns per volt, £4 4 0+5/6 p. and p. RT.1KVA 1.82 turns per volt, £6 10 0+6/6 p. and p.


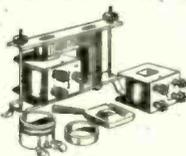
## DEMONSTRATION TRANSFORMER (STENZYL TYPE)

Two removable coils are tapped at 0, 110, 220 volts, and 6, 12, 36 volts respectively. A composite apparatus designed for class demonstration. Electro magnetic induction, jumping ring, induction lamp, relationship between field intensity and ampere turns. Induction melting, are just a few of the possible experiments. New modified model. £14/10/-, P. & P. 10/-.



## L.T. TRANSFORMERS

All primaries 220-240 volts.	Type No.	Sec. Taps	Price	Carr.
1	12 v. at 5A		£1 17	6 5/6
2	30, 32, 34, 36 v. at 5 amps.		£4 13	6 6/6
3	30, 40, 50 v. at 5 amps.		£6 17	6 6/6
4	10, 17, 18 v. at 10 amps.		£4 19	0 4/6
5	6, 12 v. at 20 amps.		£6 8	6 6/6
6	17, 18, 20 v. at 20 amps.		£7 5	6 6/6
7	6, 12, 20 v. at 20 amps.		£6 17	6 7/6
8	24 v. at 10 amps.		£5 4	6 5/6
9	4, 6, 24, 32 v. at 12 amps.		£7 3	0 6/6

**AUTO TRANSFORMERS.** Step up, step down. 110-200-220-240 v. Fully shrouded. New. 300 watt type £3/10/- each, P. & P. 4/6. 500 watt type £4/12/6 each, P. & P. 6/6. 1,000 watt type £5/15/- each, P. & P. 7/6.

**LATEST TYPE SOLID STATE DEVICES**  
**R.C.A.** plastic Triac 400 PIV 8 amp. Price 25/6.  
**R.C.A.** Diac for above, price 6/- . Price includes data sheet and circuit.

**R.C.A.** 40432 Triac and Diac in TO5 can 6 amp. 35/-.

**G.E. P.U.T.,** D13, T1, 12/- . Texas F.E.T. 2N3819, 7/6.

All above prices plus 1/6 P. & P.

**INSULATED TERMINALS**  
 Available in black, red, white, yellow, blue and green. New 2/- each.

**A.C. CONTACTOR**  
 2 make and 2 break (or 2 c/o) 15 amp. contacts. 230/240 v. A.C. operation. Brand new. 22/6 plus 1/- P. & P.



**LIGHT SENSITIVE SWITCHES**  
 Kit of parts including ORP.12 Cadmium Sulphide PhotoCell. Relay Transistor and Circuit. Now supplied with new Siemens High Speed Relay for 6 or 12 volt operations. Price 25/-, plus 2/6 P. & P. ORP. 12 and Circuit 12/6 post paid.



**220/240 A.C. MAINS MODEL**  
 Incorporates mains transformer rectifier and special relay with 2 x 5 amp. mains c/o contacts. Price inc. circuit 47/6, plus 2/6 P. & P.

**LIGHT SOURCE AND PHOTO CELL MOUNTING**  
 Precision engineered light source with adjustable lens assembly and ventilated lamp housing to take MBC bulb. Separate photo cell mounting assembly for ORP.12 or similar cell with optic window. Both units are single hole fixing. Price per pair £2/15/0 plus 3/6 P. & P.



**CONDENSERS**  
 New at a fraction of maker's price.  
 2,500 mfd. 100 v... 12/6      4,000 mfd. 25 v... 10/-  
 10,000 mfd. 35 v... 15/-      4,000 mfd. 50 v... 15/-

## BELLIN MULTI WAY PLUGS AND SOCKETS

10 way plug and socket. (Socket chassis mounted.)  
 7 way reversed plug and socket. (Plug chassis mounted.)  
 Price: either type 3/6 pair. 9d. P. & P.



## BURGESS MICRO SWITCH

Lever operated c/o contacts. Price 4/- plus 9d. P. & P. 10 in maker's carton. 35/- post paid.



## MOTORIZED SWITCHING UNIT (Ex-W.D.)

Powerful, precision-made, ex-W.D., 12 v. D.C., reversible motor, drives multiple gear train with outputs approx. 4 r.p.m. and 5 r.p.m. Price 25/- P. & P. 4/6.



## Ex. W.D. MINIATURE BLOWER UNIT

18-24 v. D.C. operation, overall length 3 1/2 in. Blower 2 1/2 x 2 1/2 in., 20/- P. & P. 2/6.

## POWER RHEOSTATS


(NEW) Ceramic construction, winding embedded in Vitreous

Enamel, heavy duty brush assembly designed for continuous duty. AVAILABLE FROM STOCK IN THE FOLLOWING II VALUES: 100 WATT 1 ohm 10a., 5 ohm 4.7a., 10 ohm 3a., 25 ohm 2a., 50 ohm 1.4a., 100 ohm 1a., 250 ohm 7a., 500 ohm 45a., 1k ohm 280mA., 1.5k ohm 230mA., 2.5k ohm 2a., 5k ohm 140mA., 15k ohm 3in. Shaft length 3in. dia. 1 1/2in., 27/6. P. & P. 1/6.  
 50 WATT 1/5/10/25/50/100/250/500/1K/1.5K/2.5K/5K ohm. All at 21/-, P. & P. 1/6.  
 25 WATT 10/25/50/100/250/500/1K/1.5K/2.5K ohm. All at 14/6, P. & P. 1/6.  
 Black Silver Skirted knob calibrated in Nos. 1-9. 1 1/2 in. dia. brass bush. Ideal for above Rheostats, 3/6 each.
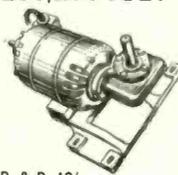
## STROBE! STROBE! STROBE!

\* THREE EASY TO BUILD KITS USING XENON WHITE LIGHT FLASH TUBES. SOLID STATE TIMING + TRIGGERING CIRCUITS. PROVISION FOR EXTERNAL TRIGGERING. 230-250v. A.C. OPERATION. The Strobe is one of the most useful and interesting instruments in the laboratory or workshop. It is invaluable for the study of movement and checking of speeds. Many uses can be found in the psychiatric and photographic fields, also in the entertainment business. It is used a great deal in the motor industry and is a real tool as well as an interesting scientific device.  
 \* EXPERIMENTERS "ECONOMY" KIT  
 1 to 36 Flash per sec. All electronic components including Veroboard 5.C.R. Unijunction Xenon Tube + instructions £8.50 plus 5/- P. & P.  
 \* NEW INDUSTRIAL KIT  
 Ideally suitable for schools, laboratories etc. Roller tin printed circuit. New trigger coil, plastic thyristor 1-80 (6.s.). Price 9 gns. 7/6 P. & P.  
 \* HY-LIGHT STROBE  
 This strobe has been designed for use in large rooms, halls and the photographic field. It has 4 times the light output at 30 f.p.s. and utilizes a silica tube for longer life expectancy, printed circuit for easy assembly, also a special trigger coil and output capacitor. Light output approx 4 joules. Price £10.17.6. P. & P. 7/6.  
 \* 7-INCH POLISHED REFLECTOR. Ideally suited for above Strobe Kits. Price 10/6 & 2/6 p. & p. or post paid with kits.

\*\*\*\*\*  
**PARVALUX TYPE SDI9 230/250 VOLT AC REVERSIBLE GEARED MOTORS**  
 30 r.p.m. 40 lb. ins. Position of drive spindle adjustable to 3 different angles. Mounted on substantial cast aluminium base. Ex-equipment. Tested and in first-class running order. A really powerful motor offered at a fraction of maker's price. 6 gns. P. & P. 10/-.



## DRY REED SWITCHES

2 x 1 amp Dry Reeds (make contacts) mounted in 870 ohm 9-18v coil. Size 3in. x 3 1/2in. x 1in. New. Price 8/6 per pair. Post Paid.  
 6 of the above mentioned units (12 Reeds, 6 coils) fitted in metal box. Size 4in. x 3 1/2in. x 1 1/2in. Mfg. by Elliott Bros. New 45/- each. Post Paid.



**MINIATURE UNISELECTOR**  
 3 banks of 11 positions, plus homing bank. 40 ohm coil. 24-36 v. D.C. operation. Carefully removed from equipment and tested. 22/6, plus 2/6 P. & P.

## UNISELECTOR SWITCHES NEW

### 4 BANK 25 WAY FULL WIPER


25 ohm coil, 24 v. D.C. operation. £5.17.6, plus 2/6 P. & P.

### 6 BANK 25 WAY FULL WIPER

25 ohm coil, 24 v. D.C. operation. £6.10.0, plus 2/6 P. & P.
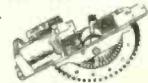
### 8-BANK 25-WAY FULL WIPER

24 v. D.C. operation, £7/12/6, plus 4/- P. & P.



## RELAYS

NEW SIEMENS PLESSEY, etc. MINIATURE RELAYS AT A HIGHLY COMPETITIVE PRICE.



COIL	WORKING D.C. VOLT	CONTACTS	PRICE
170	9-12	4 c/o H.D.	14/6
170	9-12	3 c/o + 1 H.D. c/o	12/6
230	6-12	2 c/o	12/6
280	6-12	2 c/o incl. base	14/6
700	12-24	2 c/o incl. base	12/6
700	16-24	4 c/o incl. base	15/6
700	16-24	4M 2B incl. base	12/6
2500	30-50	2 c/o H.D. incl. base	12/6
9000	40-70	2 c/o incl. base	10/-

H.D. = Heavy Duty POST PAID

## MINIATURE RELAYS

9-12 volt D.C. operation. 2 c/o 500 M.A. contacts. Size only 1in. x 1 1/2in. Price 11/6 Post paid.  
 30-36 v. D.C. operation. 2 c/o 500 M.A. contacts. 3,200 ohm coil. Size only 1 x 1 1/2 x 1 1/2 in. 8/6 post paid.

**230 VOLT AC RELAY LONDEX** four c/o 3 amp contacts. 18/6, incl. base. Post Paid.

## SANWA MULTI RANGE TESTERS

NEW MODEL U-50D MULTI TESTER, 20,000 O.P.V. MIRROR SCALED WITH OVERLOAD PROTECTION. Ranges: D.C. volts: 100mV., 0.5 v., 5 v., 250 v., 1,000 v. A.C. volts: 2.5 v., 10 v., 50 v., 250 v., 1,000 v. D.C. current: 5mA., 0.5 mA., 5 mA., 50 mA., 250 mA. Size: 5 1/2 x 3 1/2 x 1 1/2 in. Complete with batteries £7.50 and test prods. Post paid



## PANEL METERS AT BARGAIN PRICES

A.C. AMMETERS 0-1, 0-5, 0-10, 0-15, 0-20 amp. F.R. 2 1/2in. dia. ALL AT 21/- EACH.  
 A.C. VOLTMETERS 0-25 v., 0-50 v., 0-150 v. M.1 2 1/2in. Flush round ALL AT 21/- EACH. P. & P. extra.  
 0-300 v. A.C. Rect. M-Coil 2 1/2in. .... 29/-  
 0-300 v. A.C. Rect. M-Coil 3 1/2in. Type W23 ..... 45/-

## FOOT SWITCH

Suitable for Motors, Drills, Sewing Machines, etc. 5 amp. 250 volts. Price 17/6 plus 2/- P. & P.



230 v. A.C. SOLENOID. Heavy duty type. Approx. 31b. pull. 17/6 plus 2/6 P. & P. 12 v. D.C. SOLENOID. Approx. 11b. pull. 10/6, P. & P. 1/6.  
 50 v. D.C. SOLENOID. Approx. 11b. pull. 10/6, P. & P. 1/6.  
 50 v. D.C. SOLENOID. Approx. 21b. pull. 12/6, P. & P. 1/6.



## NEW MODEL HIGH FREQUENCY TRANSISTORISED MORSE OSCILLATOR

Adjustable tone control. Fitted with moving coil speaker, also earpiece for personal monitoring. Complete with morse key. 45/- plus 3/6d. p. & p.

## SEMI-AUTOMATIC "BUG" SUPER SPEED MORSE KEY

7 adjustments, precision tooled, speed adjustable 10 w.p.m. to as high as desired. Weight 2 1/2lb. £4/12/6 post paid.




## NICKEL CADMIUM BATTERY

1.2 v. 35 AH. Size 8 1/2 high x 3 x 1 1/2. 30/- each, plus 4/- P. & P.  
 Sintered Cadmium Type 1.2 v. 7AH. Size: height 3 1/2 in., width 2 1/2 in. x 1 1/2 in. Weight: approx. 13 ozs. Ex-R.A.F. Tested 12/6. P. & P. 2/6.
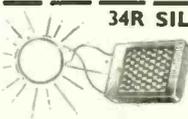
## 34R SILICON SOLAR CELL

4 x .5 volt unit series connected, output up to 2 v. at 20 mA. in sunlight, 30 times the efficiency of selenium. 45/- P. & P. 1/6d.



ALL MAIL ORDERS. ALSO CALLERS AT:

57 BRIDGMAN ROAD, LONDON, W.4. Phone: 995 1560  
 Closed Saturdays.

# SERVICE TRADING CO.

SHOWROOMS NOW OPEN  
 AMPLE PARKING

PERSONAL CALLERS ONLY

9 LITTLE NEWPORT STREET, LONDON, W.C.2.  
 Tel.: GER 0576

# HI-FI, AUDIO AND TAPE RECORDER DEALERS AROUND THE BRITISH ISLES

CHESHIRE Stockport

## AUDIO CENTRE

We stock the full range of Hi-Fi Tape Recorders and special Transistor Radios

Fairbotham and Co. Ltd.  
58/62 Lr. Hillgate, Stockport  
Tel: 480-4872

FULL SERVICE FACILITIES

Southport

## Hi-Fi in West Lancashire WAYFARERS RADIO LTD

18-20/29 BURTON ARCADE,  
LORD ST., SOUTHPORT • Tel. 4070

OXFORDSHIRE Oxford

HIGH FIDELITY IN OXFORD

HORNS

SIX SOUTH PARADE OXFORD  
Telephone: Oxford 55360  
Information • Demonstration • Installation

ESSEX Ilford

## UNIQUE RADIO LTD.

HI-FI & PUBLIC ADDRESS  
6 THE FACADE, HIGH ROAD  
GOODMAYES, ESSEX  
SEVEN KINGS 590 8277

St. Helens

## HAROLD STOTT LTD.

18 Westfield Street, St. Helens

Hi-Fi Consultant

Agents for leading makes of Tape Recorder, etc.  
Equipment Planned and Supplied.

Telephone - ST. HELENS 26791 or 23105

SURREY Guildford

## MERROW SOUND LTD.

Specialists in Hi-Fi & Tape Recording

Fully equipped for comparative demonstrations.  
Leading Agents for: B & O and TANDBERG.  
Open 9.30 a.m. to 5.30 p.m. daily incl. Sats.  
Early closing Wed. 1 p.m. EASY PARKING  
229 Epsom Road, Merrow, Guildford.  
Tel: Guildford 64171

GUILDFORD

Loughton

## SOUND SUPPLIES (Loughton) CO. LTD.

TEL: 01-508-2715

HI-Fi Showroom  
BROOKLANDS PARADE,  
309 HIGH ROAD, LOUGHTON  
Spares and Repairs  
12 SMART'S LANE, LOUGHTON, ESSEX.

LONDON South East

## G.A. ELECTRIC

81 Portland Road  
South Norwood  
01-654 3200

Hi-Fi and Public Address Equipment  
Rogers and other leading makes

SUSSEX Brighton

## LANES (RADIO) LTD.

LARGEST STOCKIST OF ALL HI-FI  
EQUIPMENT IN THIS AREA

94 CHURCH ROAD, HOVE  
TEL. Brighton 738517

Romford

We Give the Finest Hi-Fi Service in the Area  
Romford Sound & Vision Service Ltd.

7Ba BRENTWOOD ROAD  
ROMFORD

TEL. ROMFORD 41644 OR COME AND SEE

South West

## In South London it's FRANCIS OF STREATHAM

169-173 STREATHAM HIGH ROAD, S.W.16  
Phone: 01-769 0192 • 01-769 0466

Leading stockists for Tandberg, Akai, Ferrograph, Quad,  
Rogers, Leak, Shure, Garrard, etc., etc.

WARWICKSHIRE Birmingham

## GRIFFIN RADIO LTD.

021-692 1359 021-643 0867

94 Bristol Street • Birmingham 5

★ Complete advisory facilities for all makes of  
equipment.

★ Full range of Classical and Light Music LPs.

GLAMORGANSHIRE Cardiff

## J. GOUGH & CO. LTD.

DESIGNERS OF THE FAMOUS GOUGH  
LOUDSPEAKERS

THE LARGEST STOCKIST OF HI-FI  
EQUIPMENT AND FOR DEMON-  
STRATION IN SOUTH WALES

148-154 NORTH ROAD, CARDIFF  
Telephone: 28473

South West

## TAPE RECORDER HI-FI CENTRE (SHEEN) LTD

SPECIALISTS IN TAPE RECORDERS, ACCESSORIES,  
HI-FI EQUIPMENT  
YOUR CENTRE FOR FRIENDLY HELP, SALES AND  
SERVICE

3 & 4 STATION PARADE, Tel. 876 0985  
SHEEN LANE, SHEEN, Opposite Mortlake Station, S.R.  
LONDON, S.W.14 Closed Wednesdays

Coventry

## ELECTRONIC SERVICES

HI-FI SPECIALISTS

33 CITY ARCADE  
COVENTRY

TEL: 24632

HAMPSHIRE Southampton

High Fidelity  
Specialists



Hamilton Electronics (Southampton) Ltd  
39 London Road Southampton Phone 28622 3 Lines

West

## Lasky's Radio

Stockist for all the leading makes of Hi-Fi  
Audio Equipment

33 TOTTENHAM CT. RD., W.1 01-636 2605  
207 EDWARE ROAD, W.2 01-723 3271  
152/3 FLEET STREET, E.C.4 01-353 2833  
109 FLEET STREET, E.C.4 01-353 5812

Hi-Fi Centres

42-45 TOTTENHAM CT. RD., W.1 01-580 2573  
118 EDWARE ROAD, W.2 01-723 9789

WORCESTERSHIRE Worcester

HIGH-FIDELITY SPECIALISTS

## JOHNSONS SOUND SERVICE

43 Friar Street, Worcester

Worcester 25740

LANCASHIRE Bury

## J. SMITH & SON

HI-FI EQUIPMENT • STEREOGRAMS  
TAPE RECORDERS • 2 SHOWROOMS

B. & O. Dynatron, Hacker, Quad, Leak, B. & W., Tandberg,  
Sony, Rogers, Stax, Armstrong, Ferrograph, Garrard,  
Thorens, Goodmans, etc. Comparator Demos.  
Closed all Tuesday

Specialists in 'SOUND' for 36 years  
184 THE ROCK, BURY. Tel: 1242

West Central

The best in  
**Tape** & TAPE RECORDERS  
At lowest prices  
RE-RECORDING AUDIO VISUALS  
Interest FREE offers!

Call write or Phone  
146 CHARING CROSS RD LONDON WC2 Tel 01 836 3365

SCOTLAND Glasgow

G. H. STEEL LTD.

Scotland's leading Tape Recorder, Video and Hi-Fi  
Specialists. Agents for: B & O, Armstrong, Leak, Fisher,  
Arens, Dynatron, Rogers, Quad, Truvox, Philips, Sony,  
Akai, Sanyo, Revox, Tandberg, Brenell, Ferrograph, Uher,  
Grundig, Goldring, Garrard, Thorens, Connoisseur,  
Goodmans, Wharfedale, KEF, Celestion, Decca, Scott.  
Equipment Cabinets, Earphones, Tapes, Accessories,  
Repairs and Servicing. Credit Terms, Part Exchanges,

141 St. George's Road, Glasgow C.3. Tel. Douglas 7124

# VALVES

CY31	7/-	PL94	6/8
DAP96	7/10	PL500	14/9
DF96	7/8	PL504	19/-
DK96	7/10	PL600	30/-
DL92	6/8	PX1	14/-
DL94	6/8	PX25	12/6
DM70	6/-	PY33	12/-
DM71	7/6	PY80	6/6
DY86	6/8	PY81	5/6
DY87	6/8	PY82	6/8
DY89	6/8	PY83	7/6
EABC80	6/8	PY88	7/6
EAF42	10/-	PY800	9/6
EB91	2/-	PY801	9/6
EBC33	8/-	PY802	13/6
EBC41	10/8	QV03-10	8/6
EBC81	6/8	QV06	8/5
EBF80	7/8	QV06-40A	10/10
EBF83	8/6	R10	17/8
EBF89	6/-	R17	8/-
ECC81	6/-	R19	7/8
ECC82	6/8	8TV280/80	80/-
ECC83	6/8	U25	14/8
ECC86	7/6	U26	14/8
ECC88	7/-	U27	8/-
ECC89	8/9	U191	14/-
ECP80	6/8	U301	11/6
ECP82	8/6	U801	20/-
ECP83	15/6	UABC80	6/8
ECP801	12/6	UAF42	10/8
ECP802	12/6	UBC41	9/6
ECH32	13/-	UBP80	7/-
ECH81	5/9	UBP89	7/-
ECH83	8/8	UCP80	10/-
ECH84	7/8	UCH42	12/6
ECH200	12/6	UCH81	7/-
ECL80	9/-	UCL82	7/6
ECL82	6/6	UCL83	12/-
ECL83	10/6	UF41	9/6
ECL86	8/6	UF80	7/3
EP36	3/6	UF89	6/9
EP37A	7/-	UL41	11/8
EP38	6/6	UL84	6/6
EP40	10/-	U05	7/-
EP41	12/6	UY41	8/6
EP80	5/-	UY85	5/9
EP83	9/7	VR105/30	6/-
EP85	6/6	VR150/30	6/-
EP86	6/3	Z800U	29/-
EP89	6/3	Z801U	25/-
EP91	3/-	Z900T	12/-
EP92	2/6	11A	2/6
EP95	5/-	11B	6/6
EP183	6/8	184	6/6
EP184	7/-	185	4/4
EP186	20/6	186	4/4
EP812	15/8	174	3/6
EPL200	15/8	1X2A	7/8
EL34	10/6	1X2B	7/8
EL41	11/6	3A4	4/-
EL42	10/6	3D6	3/-
EL84	4/8	3Q4	7/8
EL85	8/-	384	6/6
EL86	8/-	3V4	8/-
EL90	8/-	5B254M36	80
EL91	8/-	5B255M	80
EL95	7/-	5B25	85/-
EL900	12/-	5R4Y	10/8
EL8035	17/-	5U4G	5/8
EM31	5/-	5V4G	7/8
EM80	7/8	544G	7/-
EM84	7/-	5Y3GT	6/-
EM87	11/-	6Z4	14/-
EY61	8/-	6Z4G	7/8
EY71	7/-	6AB7	4/-
EY86	7/-	6AC7	3/-
EY88	8/6	6AH6	11/6
EZ41	8/6	6AK5	5/-
EZ80	5/-	6AL5	5/-
EZ81	5/-	6AL5W	7/-
GZ34	10/8	6AM5	5/-
KT66	27/6	6AM6	3/-
KT88	32/-	6AN5	20/-
N78	25/-	6AN8	10/-
OA2	6/-	6AQ6	6/6
OB2	6/-	6AQ8W	9/-
PAC80	7/6	6AS6	6/-
PC97	9/-	6A87G	16/-
PC900	9/6	6AT6	4/6
PC84	6/6	6AU6	6/6
PC89	9/6	6AX4	8/-
PC189	11/6	6AX5GT	13/-
PC8500	15/-	6B7	5/6
PCF80	6/6	6BK7	8/-
PCF82	9/6	6BA6	4/6
PCF84	9/3	6BE5	5/-
PCF86	10/-	6BGG	11/-
PCF200	15/6	6BJ6	8/6
PCP201	15/6	6BQ7A	6/9
PCP801	15/6	6BR7	18/-
PCP802	9/6	6BW7	13/-
PCP805	14/6	6C4	4/9
PCP806	13/6	6C6	4/9
PCP808	14/6	6CH6	7/9
PCF200	12/8	6CL6	9/-
PCF801	9/6	6D6	3/-
PCF802	9/6	6EA8	9/-
PCF805	14/6	6EUT	7/6
PCF808	14/6	6F23	15/-
PCF200	12/8	6F33	20/-
PCF801	9/6	6H6M	3/-
PCF802	9/6	6J4WA	12/-
PCF805	14/6	6J5	7/-
PCF808	14/6	6J5GT	8/-
PCF200	12/8	6J6	3/6
PCF801	9/6	6J7G	8/-
PCF802	9/6	6J7M	8/-
PCF805	14/6	6K6GT	8/-
PCF808	14/6	6K7	6/8
PCF200	12/8	6K7G	2/-
PCF801	9/6	6K8G	4/-

## MARCONI TEST EQUIPMENT

**SIGNAL GENERATOR TF 801/A.** 10-300 Mc/s. in 4 bands. Internal at 400 c/s. 1 kc/s. External 50 c/s to 10 kc/s. Output 0-100 db below 200 mV from 75 ohms source. £85. DITTO but 801/A/1 with additional high level output. £89. Both P. & P. 20/-, including necessary connectors, plugs, and instruction manual.

## HEWLETT-PACKARD TEST EQUIPMENT

**MODEL 524B ELECTRONIC COUNTER WITH MODEL 525B PLUG IN UNIT.** Basic counter measures frequencies from 10Hz to 10MHz and time from 0 to 10 kHz. Automatic positioning of decimal point, eight place registration. Full self check facility from built in frequency standards. Plug In unit extends frequency range of basic counter to 100 to 220MHz. Full specification and price on request.

## AVO VALVE CHARACTERISTIC METER



complete with manual, £45 Carriage 30/-.

## SPECIAL OFFER OJ2 TUBE 35/-

**PHASE MONITOR ME-63/U.** Manufactured recently by Control Electronics Inc. Measures directly and displays on a panel meter the phase angle between two applied audio frequency signals within the range from 20-20,000 c.p.s. to an accuracy of ± 1.0°. Input signals can be sinusoidal or non-sinusoidal between 2 and 30 v. peak. In excellent condition. £75. Carriage 30/-.

**AIRMEC INSULATION TESTER O-5KV** built-in ionisation amplifier, £28.

**BOONTON SIGNAL GENERATOR TS 497/B/URR, 2-400MHz.** £95.

**TS 418 B/U SIGNAL GENERATOR, 400-1000MHz.** £105. Carr. 30/-.

**AVO SIGNAL GENERATOR CT 378, 2-225MHz.** £38.10.0. Carr. 18/-.

## TELEPHONE ENQUIRIES

relating to TEST EQUIPMENT should be made to 01-748 8006 Extension 23. To view TEST EQUIPMENT please phone for appointment

## INTEGRATED CIRCUITS MANUFACTURERS IN STOCK

RCA CA 3005 wide band RF Ampl 300mW diss...	27/-
CA 3012 wide band ampl 150mW diss...	22/-
CA 3020 Audio power ampl...	30/-
CA 3036 Audio pre-amp...	19/-
STC MIC 9301B Digital dual 4 input gates...	86/-
MIC 709-1C Linear operational ampl...	190/-
MIC 9005D Highspeed flip-flop...	54/-
Plessey A.F. Amps with PRE-AMP 2.5W. £2.2.6. 3.5W. £2.12.6. Mono with tone controls £6.2.6. Stereo with tone controls £12.19.6.	

## TRANSISTORS, ZENER DIODES

OA5	2/6	OC35	8/8	OC201	7/6	3FR5	8/6	AF178	12/6
OA10	6/-	OC38	8/8	OC206	10/-	3N128	17/8	AFV19	22/8
OA70	2/-	OC44	4/-	IN21	3/6	3N139	35/-	ASV26	5/8
OA71	2/-	OC45	2/6	IN21B	5/6	3N140	19/6	ASV28	5/8
OA79	1/8	OC70	3/-	IN25	12/-	3N154	19/-	BAW19	5/8
OA81	1/8	OC71	2/6	IN43	4/-	3N159	29/-	HC107	3/8
OA890	1/8	OC72	4/-	IN70	4/-	6FR5	7/8	BC108	4/-
OA292	2/-	OC73	11/-	IN702-725		12FR60	14/9	BCV10	9/-
OA210	7/6	OC75	4/6	IN702-725	7/3	10D1	3/4	BCV72	7/9
OA211	9/6	OC76	5/-	IN746A		40594	27/8	BFV51	4/6
OA220011/-		OC81	4/-	series 5/3		40595	27/8	BFV52	4/6
OA220110/-		OC81D	3/-	IN821A	21/-	40638	29/-	R805	7/8
OA220210		OC81DM	3/-	IN822A	26/-	40668	27/-	B8	9/1
OA2206	8/8	OC82	5/-	IZMT5	7/-	40669	29/-	B82	9/3
OA2207	9/6	OC82DM	3/-	IZMT10	6/9	AC128	4/6	BU100	36/-
OA2208	10/-	OC83	4/8	IZT5	13/6	AC127	4/6	BY213	5/6
OA2213	8/6	OC83B	3/-	IZT10	12/8	AC128	4/6	BY215	15/-
OA2223	10/-	OC84	5/-	2N1306	6/6	AC176	7/8	CR81	10/5
OA222510		OC122	10/-	2N1307	6/6	ACV28	4/-	CR8120	9/8
OC16	15/-	OC139	8/8	2N303	10/-	AD148	11/-	CR1130	
OC22	8/8	OC140	8/-	2N3053	6/6	AD161	7/-	Z Range	
OC25	7/6	OC170	5/-	2N3054	12/6	AD162	7/-	Zener diodes	
OC26	5/-	OC171	6/-	2N3055	15/-	AF117	4/9	3/8 ea.	
OC29	8/-	OC172	7/8	2N5109	12/6	AF118	10/-	7/8 ea.	
OC29	16/-	OC200	6/-	3P100	12/8	AF139	10/-	5/1 ea.	

MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. U.K. P. & P. up to 10/- 1/-; to £1 2/-; over £1 2/- in £, over £3 post free. C.O.D. 4/- extra.  
Open 9-12.30, 1.30-5.30 p.m. except Thursday 9-1 p.m.



**VALVE VOLT METER TYPE TF 958.** Measures AC 100mV; 20 c/s to 100 mc/s; DC 50mV to 100V, multiplier extends ac range to 1.5kV. Balanced input and centre-zero scale for 100MHz. £32.10.0.

**DISTORTION FACTOR METER TYPE TF 142E.** Frequency range: 100-8,000Hz in four ranges. Distortion range: 0.05 to 50%. Input impedance 600Ω, attenuation 0-60db continuously variable. Sensitivity 1mV. £42.10.0. Carriage 20/-.

**TF 899 VALVE VOLT METER, 10mV to 2V, £17.10.0. Carriage 30/-.**  
**F.M. DEVIATION METER TF 934, £57.10.0. Carriage 30/-.**  
**VISCO OSCILLATOR TF 885A & 885A/I, £55 and £85 resp. Carr. 30/-.**

**FM DEVIATION METER TYPE TF 791B.** Frequency range: 4-250MHz, deviation 1-75kHz. Specification and price on application.

**FOR EXPORT ONLY 53 TRANSMITTERS.** All spares available. COLLINS TCS. Complete installations and spare parts. 62 WIRELESS SETS. Complete installations and spare parts. P.S.U. for C42 & C45 12v and 24v R.C.A. TRANSMITTERS ET 4336. Complete installations and all spares. BC 610E & I TRANSMITTERS. Complete installations and all spares. No. 19 WIRELESS SETS. H.P. SETS and all spares R.210 RECEIVERS with all necessary accessories.  
**PYE CTC 2002N A.M. Ranger** Mobile Radio Telephone, brand new and complete, £45.

4, 5 and 8 bank 25 way uniselectors, 24V, guaranteed perfect, £3.15.6; £4.10.0; £6.17.6 respectively.

**DAWE STORAGE OSCILLOSCOPE** complete with trace shifter, complete as new, specification and price on request.

**SPARES FOR AR.88D. RECEIVERS.** Ask for your needs from our huge selection.

**HARNESS "A" & "B"** control units, junction boxes, headphones, microphones, etc.

**PULSE GENERATOR TYPE TF 675F.** Repetition frequency: 50Hz to 50kHz. Pulse duration: 0.15 to 1000 sec; built in 0.1 and 0.5µ sec delay lines. £40.10.0. Carriage 20/-.

**CIRCUIT MAGNIFICATION METER TYPE TF 329F.** Frequency range: 50kHz to 50MHz. Magnification 10 to 500 Q. Tuning Capacitor: 40 to 450pF with ±3pF vernier. Fully overhauled and calibrated, £70. Carriage 30/-.

**LIMITED QUANTITY ONLY SIGNAL GENERATOR TYPE TF 937 (CT 218).** Frequency range: 35 kHz-30MHz. 50 ft. Frequency scale. 200 kHz to 2MHz. Built-in Crystal calibrator Sinewave A.M. V.F.M. Output: D.19V-1V. Price on application.

**AVO'S METERS**  
Model 85X with leads, £18.  
Model 7X with leads £15.10.0.  
Model 7 with leads, £14.10.0.  
Model 47A complete with multiplier shunts, etc., in special fitted wooden case, £12.  
Model 48A equipped as 47A, £14.10.0. Carriage for each of above 7/6.  
**WEE MEGGER 500v., £14.10.0.**  
**TF 144G SIGNAL GENERATOR** offered unchecked but in very good condition, rack model, mounted complete with cables, etc., £20. Carriage 20/-.

## SOLARTRON EQUIPMENT

**LAB. AMP AWS 151A.** Frequency: 15Hz to 350kHz. Metered output, scope viewing, etc. £29.10.0. Carriage 20/-.

Regulated and stabilised P.S.U. **SRS 151A**, 20 to 500V positive at 300mA in two ranges. Variable and fixed 170V negative output, £35. Carriage 20/-.  
**CD 7115.2.** Double beam, DC to 7MHz 'scope, £85. Carriage 30/-.  
**CD 643.2.** Single beam Laboratory Model, DC to 14MHz price upon application.  
**QD 910.** Storage Oscilloscope, as new. Price on request.

**29/41FT. AERIALS** each consisting of ten 3ft., 3/16 in. dia. tubular screw-in sections. 11ft. (6-section) whip aerial with adaptor to fit the 7in. rod, insulated base, stay plate and stay assemblies, pegs, reamer, hammer, etc. Absolutely brand new and complete ready to erect, in canvas bag, £39/6. P. & P. 10/6.

**FIELD TELEPHONE TYPE "F".** Housed in portable wooden cases. Excellent for communication in and outdoors for up to 10 miles. Pair including batteries, fully tested. £6.10.0, or with 220 yds field cable in drum £7.10.0.

**END OF RANGE ITEMS** in 'as seen' condition: H.R.O.—£10; Coils at 15/-; Furzhill VTVM 10mV to 100V—£15.

## PANEL METERS

Just a few from our huge stock:

25µA round p.j. M.C. 2 1/2"	27/6
50µA round M.C. 2 1/2"	32/6
100µA round M.I. 2 1/2"	32/6
100µA round M.C. 3 1/2"	35/-
200µA round M.C. 2 1/2"	27/6
500-0-500µA round M.C. 2 1/2"	22/6
500µA round M.C. 1" (calibrated 1mA)	22/6
1mA round M.C. 2 1/2"	25/-
5mA round M.C. 2" clip fit.	22/-
10mA round M.C. 2 1/2"	22/6
10-0-10mA round M.C. 2 1/2"	20/-
20mA round M.C. 2 1/2"	20/-
25mA round M.C. 2 1/2"	22/6
25-0-25mA round M.C. 2 1/2"	22/6
30mA round M.C. 2 1/2"	22/-
30-0-30mA round M.C. 2 1/2"	19/6
50mA round p.j. M.C. 2 1/2"	19/-
100mA square M.C. 2"	22/6
200mA square M.C. 2"	20/-
10-0-100mA round M.C. 2 1/2"	20/-
100-0-100mA round M.C. 2 1/2"	22/6
400mA round M.C. 2 1/2"	18/-
3 amp round R.F. 2 1/2"	27/6
6 amp round M.C. 2 1/2"	18/-
9 amp round R.F. 2 1/2"	32/-
25 amp round M.C. p.j. 3 1/2"	27/6
25amp round M.C. 3 1/2"	19/-
8V square M.C. 3"	27/6
15V round M.I. 2 1/2"	30/-
20V square M.C. 2" clock scale.	17/6
50V round M.C. 2 1/2" black face.	20/-
100V round M.C. 4"	25/-
300V round M.I. 2 1/2"	19/-
1500V round electrostatic, plug-in 2 1/2"	32/6
7KV round electrostatic 3 1/2"	27/6
59-63 cycles 2 1/2" freq. meter.	32/6
and very many others, full list of meters upon request.	

All overseas enquiries & orders please address to:  
**COLOMOR (ELECTRONICS) LTD.**  
170 Goldhawk Rd., London, W.12  
Tel. 01-743 0899

# Z AND AERO SERVICES LTD



## INTEGRATED CIRCUIT AMPLIFIERS

- CA3005 RF Amplifier with 100mc/s bandwidth. Max. dissipation 26mW. For use as RF amplifier, balanced mixer, product detector or self-oscillating mixer. 27/-
- CA3012 Wide Band Amplifier (up to 20mc/s), suitable as IF Amplifier for VLF/FM receivers. 22/-
- CA3020 General Purpose Audio Amplifier of 550mW output. 30/-
- CA3036 Buffer Amplifier consisting of two "super-alpha" pair of transistors suitable for stereo pick-up systems. 19/-
- The above four I.C.s are in TO8 encapsulation.
- PA222 Audio Amplifier providing a max. output of 1.2 watts. 65/-
- PA234 Audio Amplifier providing a max. output of 1 watt. 27/8
- PA237 2 watts Audio Amplifier. 40/-
- The above three I.C.s are in epoxy moulded double four-in-line package.
- MC1709CG General Purpose operational amplifier in TO-99 case. 40/-
- TAA263 3-stage direct coupled amplifier for use from DC to 600kc/s; 70mW dissipation. Output 10mW into 150Ω load. 15/-
- TAA283 2-stage amplifier with connection brought out to the individual leads. Bandwidth 600kc/s. 160mW dissipation. Output 10mW into 150Ω load. 20/-
- TAA320 MOST input stage followed by a bi-polar transistor stage. 200mW dissipation. 13/-
- TAD100 All active components required for an A.M. Receiver comprising mixer, oscillator, i.f. amplifier, a.g.c. and pre-amplifier stages. To build complete receiver only coils, capacitors and resistors are required and output stage for which one of the above described I.C.s can be used. Dual seven-in-line package. 45/-
- Data sheet available for all the above I.C.s.—free with I.C.s or 1/- per data sheet if ordered separately.

## TRANSISTORS

2N404 3/6	2N2923 3/-	AC128 5/-	AY77 7/-	BY95A 3/9
2N410 3/6	2N2924 3/-	AC127 5/6	AY82 4/-	D29A4 3/6
2N412 3/6	2N2925 3/-	AC128 4/6	AY86 4/6	D29A4 3/6
2N444 4/6	2N2926 3/-	AC153 5/-	BC107 3/-	OC16 15/-
2N696 5/6	2N2926 3/-	AC154 3/-	BC108 3/-	OC22 13/-
2N697 4/6	2N2926 3/-	AC176 6/6	BC109 4/-	OC23 12/6
2N698 8/6	2N2926 3/-	AC177 6/6	BC118 8/6	OC24 15/-
2N705 15/-	2N2926 3/-	AC178 4/6	BC147 4/6	OC25 7/6
2N706 3/-	2N2926 3/-	AC199 4/6	BC148 3/6	OC26 8/-
2N708 3/6	2N2926 3/-	AC199 4/6	BC149 3/6	OC28 14/8
2N753 4/6	2N2926 3/-	AC199 4/6	BC152 3/6	OC29 14/9
2N929 6/6	2N2926 3/-	AC199 4/6	BC175 5/6	OC30 15/-
2N930 6/6	2N3053 6/3	AD140 16/-	BCY30 7/-	OC35 11/3
2N987 6/6	2N3055 15/-	AD149 12/6	BCY31 5/-	OC36 12/6
2N1131 2/6	2N3133 7/6	AD162 9/-	BCY33 5/-	OC42 6/6
2N1132 6/6	2N3134 8/6	AD162 9/-	BCY34 5/-	OC44 4/-
2N1184 25/-	2N3134 8/6	AD162 9/-	BCY39 5/-	OC45 3/6
2N1301 7/-	2N3391 4/-	AF114 6/-	BCY72 0/0	OC71 3/6
2N1302 7/-	2N3392 3/6	AF115 6/-	BCZ11 7/8	OC73 7/8
2N1304 4/6	2N3394 2/6	AF117 5/8	BD121 18/-	OC75 5/-
2N1305 4/6	2N3395 3/6	AF118 10/-	BF123 25/-	OC76 5/-
2N1306 5/-	2N3402 5/-	AF125 9/3	BF167 5/-	OC78 5/-
2N1307 6/-	2N3403 5/-	AF126 5/3	BF173 6/-	OC78 5/-
2N1308 7/6	2N3404 6/6	AF127 5/3	BF174 3/6	OC78D 3/3
2N1309 9/6	2N3414 4/-	AF178 12/6	BF194 3/6	OC81 4/6
2N1756 15/-	2N3415 4/6	AF186 11/-	BF195 3/6	OC83 4/6
2N2147 14/6	2N3416 4/6	AF239 10/-	BF198 5/4	OC84 5/6
2N2160 23/-	2N3417 5/2	AFY19 22/6	BFY17 8/6	OC139 7/6
2N2217 6/6	2N3702 4/6	AFZ11 9/-	BFY18 5/-	OC140 9/6
2N2218 7/9	2N3703 3/10	AFZ26 6/6	BFY19 5/6	OC140 9/6
2N2219 6/6	2N3704 5/6	AFZ26 6/6	BFY50 5/-	OC171 5/6
2N2269A 4/6	2N3707 4/6	AFZ28 6/6	BFY51 4/6	OC200 4/4
2N2277 12/6	2N3709 3/5	AFZ29 6/6	BFY52 4/10	OC201 10/-
2N2640 12/6	2N3710 3/-	AFY54 6/-	BFY52 4/10	OC202 13/-
2N2905 10/-	2N3908 12/-	AFY73 10/-	BFY52 4/10	OC203 16/3
	2N3909 8/-	AFY74 10/-	BFY52 4/10	OC203 16/3
	2N3910 8/-	AFY74 10/-	BFY52 4/10	OC203 16/3
	2N3911 8/-	AFY74 10/-	BFY52 4/10	OC203 16/3
	2N4000 8/-	AFY74 10/-	BFY52 4/10	OC203 16/3

## PLESSEY SL403A INTEGRATED CIRCUIT AUDIO AMPLIFIER

Dual-in-line 10-lead flat package with heat sink strip. Maximum audio output 3 watts into 7.5Ω loudspeaker. Circuit consists of a pre-amplifier followed by a main amplifier. Distortion 0.3% at 1 watt increasing to 0.5% at full output. Frequency response 20 c/s to 20 mc/s. Operating voltage 18v. Built-in overvoltage cut-out. Price, complete with sheet set 49/6

## SILICON MATCHED DIODE PAIRS

1N4551 Two diodes in common TO92 epoxy case. Separate anode leads and joint cathode. Diodes are statically and dynamically balanced. Max. reverse voltage 20V. Max. dissipation 200mW. Suitable for TV horizontal phase discriminators and similar applications. Price 3/- each. Considerable discount for quantities.

## ZENER DIODES

BZY88 series, from 3.3V to 9.1V ± 5% 400mW .. 3/6 each  
 BZY94 series, from 10.0V to 12.0V ± 5% 400mW .. 3/6 each  
 DB14 series, from 7.5V to 13.0V ± 10% 340mW .. 3/- each  
 DB15 series, from 4.7V to 18.0V ± 10% 8 Watts .. 7/6 each  
 DB16 series, from 2.7V to 4.7V ± 10% 5 Watts .. 7/6 each  
 DB17 series, from 5.6V to 10.0V ± 10% 5 Watts .. 7/6 each  
 Outlines: BZY series—miniature—wire ended  
 DB14—Top Hat type  
 DB15-DB17—stud mounted, supplied complete with hardware

Please state voltage required—nearest standard voltage will be supplied.

WHEN ORDERING BY POST PLEASE ADD 2/6 IN £ FOR HANDLING AND POSTAGE.  
 NO C.O.D. ORDERS ACCEPTED  
 ALL MAIL ORDERS MUST BE SENT TO HEAD OFFICE AND NOT TO RETAIL SHOP.

## FULLY GUARANTEED FIRST QUALITY VALVES



OA2 6/6	5B/254M	6BN6 8/-	6Q7 7/8	12AQ5 8/-	30C15 15/-	150C4 11/-	CIA 90/-	EAP42 10/-	EF80 5/-	EY4 10/-	ME91 8/-	PD500 30/-	QY4-250A	UF9 11/-
OA3 9/-	45/-	6BQ5 5/-	6B7G 7/-	12AT7 6/8	30C17 16/-	305 12/6	CLK 90/-	EAF901 9/6	EF86 5/-	EY86 7/-	ME4 8/-	PE06-40N	230/-	UF11 10/-
OA4G 22/-	5B/255M	6BQ6GTB	6B7G 7/-	12AT7 6/8	30C18 15/-	311A 27/6	CLB11 17/-	EAF91 9/6	EF86 5/-	EY86 8/6	MH4 9/-	PE06-80N	230/-	UF11 10/-
OB2 6/6	5D21 45/-	6BQ7A 7/8	6B7G 7/-	12AT7 6/8	30C19 15/-	328A 40/-	CL4 12/-	EBC33 6/6	EF86 5/-	EY86 8/6	MH4 9/-	PEN4DD	300/-	UF42 12/-
OB3 10/-	5J6 8/-	6B7 17/-	6B7G 7/-	12AT7 6/8	30C20 15/-	328A 40/-	CL4 12/-	EBC33 6/6	EF86 5/-	EY86 8/6	MH4 9/-	8/-	R10 20/-	UF42 12/-
OC2 17/-	5R4GY 11/-	6BR8 13/-	6B7G 7/-	12AT7 6/8	30C21 15/-	328A 40/-	CL4 12/-	EBC33 6/6	EF86 5/-	EY86 8/6	MH4 9/-	PEN45 7/8	R10 20/-	UF42 12/-
OD3 6/6	5U4G 6/-	6B87 26/-	6B7G 7/-	12AT7 6/8	30C22 15/-	328A 40/-	CL4 12/-	EBC33 6/6	EF86 5/-	EY86 8/6	MH4 9/-	PEN45 7/8	R10 20/-	UF42 12/-
LA3 5/-	5U4GB 7/8	6B87 26/-	6B7G 7/-	12AT7 6/8	30C23 15/-	328A 40/-	CL4 12/-	EBC33 6/6	EF86 5/-	EY86 8/6	MH4 9/-	PEN45 7/8	R10 20/-	UF42 12/-
1A9GT 5/8	5V4G 8/-	6B87 26/-	6B7G 7/-	12AT7 6/8	30C24 15/-	328A 40/-	CL4 12/-	EBC33 6/6	EF86 5/-	EY86 8/6	MH4 9/-	PEN45 7/8	R10 20/-	UF42 12/-
1A7GT 7/8	5W4GT 7/8	6B87 26/-	6B7G 7/-	12AT7 6/8	30C25 15/-	328A 40/-	CL4 12/-	EBC33 6/6	EF86 5/-	EY86 8/6	MH4 9/-	PEN45 7/8	R10 20/-	UF42 12/-
1C9G 6/-	5Z3 10/-	6B87 26/-	6B7G 7/-	12AT7 6/8	30C26 15/-	328A 40/-	CL4 12/-	EBC33 6/6	EF86 5/-	EY86 8/6	MH4 9/-	PEN45 7/8	R10 20/-	UF42 12/-
1G4GT 8/8	5Z4G 7/8	6B87 26/-	6B7G 7/-	12AT7 6/8	30C27 15/-	328A 40/-	CL4 12/-	EBC33 6/6						

# APPOINTMENTS VACANT

DISPLAYED SITUATIONS VACANT AND WANTED: £7 per single col. inch.

LINE advertisements (run-on): 8/- per line (approx. 7 words), minimum two lines.

Where an advertisement includes a box number (count as 2 words) there is an additional charge of 1/-.  
SERIES DISCOUNT: 15% is allowed on orders for twelve monthly insertions provided a contract is placed in advance.

BOX NUMBERS: Replies should be addressed to the Box number in the advertisement, c/o Wireless World, Dorset House, Stamford Street, London, S.E.1.  
No responsibility accepted for errors.

Advertisements accepted up to THURS., 12 p.m., 5th MARCH for the APRIL issue, subject to space being available.

## SALES ENGINEERS

### ETHER ENGINEERING

are expanding in the  
TRANSDUCER MARKET  
and require additional sales effort.

If you are successfully selling quality transducers or associated equipment to professional users, you may wish to consider this excellent opportunity to join a rapidly expanding member of the Pye Group.

also have an interesting new development line in  
AUTOMATIC TEST EQUIPMENT  
Sales Engineers at present qualified in this field are invited to join an expanding division of this company.

Modern marketing methods are employed and the company offers excellent working conditions, including:

- ★ Company Car
- ★ Pye Group pension and life assurance scheme
- ★ Superior dining facilities
- ★ Active Sports and Social Club

Applicants will receive immediate response and a quick decision.

Apply in writing, giving brief details of career to date, to:

**Personnel Manager**  
**Ether Engineering Ltd.**  
Park Avenue, Bushey, Herts.



Ether Engineering Ltd

A Member of the



Group of Companies

409

A Special Project R & D team is being set up by Control Systems Ltd. at Uxbridge to provide group facilities for subsidiary companies manufacturing and marketing internationally-known electronic equipment of advanced concept. New staff are required as follows:-

### ELECTRONIC ENGINEERS

at graduate and qualified level with an interest in the application or design of M.O.S. integrated circuits in Mini Computer equipment with an emphasis on office mechanisation.

**GRADUATES** in computer science or mathematics seeking a first appointment in industry who will carry out original work on the development and programming side of the new equipment.

Members of the Research and Development team enjoy first-class conditions of employment including the opportunity of four weeks holiday and a very good Life Assurance and Pension Scheme. The modern R & D building is in pleasant surroundings overlooking the Buckinghamshire countryside. Apply, with relevant particulars of experience to:

**Group Personnel Manager,**  
**Control Systems Ltd.**  
The Island,  
Uxbridge, Middx.

Lamson Industries Group



# There is scope, variety and responsibility as a **RADIO TECHNICIAN** in Air Traffic Control

Join the National Air Traffic Control Service of the Board of Trade as a Radio Technician and you have the prospect of a steadily developing career in a demanding and ever-expanding field.

**Entrance qualifications:** you should be 19 or over, with at least one year's practical experience in telecommunications. Preference will be given to those having ONC or qualifications in Telecommunications.

Once appointed and given familiarisation training, you will be doing varied and vital work on some of the world's most advanced equipment including computers, radar and data extraction, automatic landing systems, communications and closed-circuit television. Work is based on Civil Airports, Air Traffic Control Centres, Radar Stations and specialist establishments. Vacancies exist in various parts of the United Kingdom.

Salary: £985 (at 19) to £1,295 (at 25 or over); scale maximum £1,500 (higher rates at Heathrow). Some posts attract shift-duty payments. Promotion prospects are excellent and ample opportunity and assistance is given to study for higher qualifications. The annual leave allowance is good and there is a non-contributory pension scheme for established staff.

Send this coupon for full details and application form:-  
**To: A. J. Edwards, C.Eng., M.I.E.E., M.I.E.R.E.,**  
**Room 705, The Adelphi, John Adam Street, London WC2**  
 marking your envelope 'Recruitment'.

Name.....

Address.....

WW/A4

Not applicable to residents outside the United Kingdom.

**NATCS** National Air Traffic Control Service

# computer engineering

NCR requires additional **ELECTRONIC, ELECTRO MECHANICAL ENGINEERS** and **TECHNICIANS** to maintain medium to large scale digital computing systems in London and provincial towns.

Training courses will be arranged for successful applicants, 21 years of age and over, who have a good technical background to ONC/HNC level, City and Guilds or radio/radar experience in the Forces.

Starting salary will be in the range of £900/£1,250 per annum, plus bonus. Shift allowances are payable, after training, where applicable. Opportunities also exist for Trainees, not less than 19 years of age, with a good standard of education, an aptitude towards and an interest in, mechanics, electronics and computers.

*Excellent holiday, pension and sick pay arrangements. Please write for Application Form to Assistant Personnel Officer NCR, 1,000 North Circular Road, London, NW2 quoting publication and month of issue.*

Plan your future with



# SERVICE ENGINEERS

Our Instruments Company is currently expanding its activities and range of products.

Senior and Intermediate vacancies exist at the Service Department situated in Reading Berks.

The Department is furnished with modern test and fault finding equipment and the work is varied and interesting. Equipments are modern analogue and digital devices incorporating the latest techniques in instrumentation.

Previous servicing experience is desirable but our main requirement calls for an enthusiastic sound approach to the servicing of our wide range of products.

Applications in writing please to:

Mr. L. A. Jemmett,  
 Racal Instruments Ltd.,  
 Bennet Road,  
 Reading,  
 Berks.



# EAST AFRICAN COMMUNITY

## Meteorological Department

requires

# Sectional Engineer Grade II (Telecomms.)

to serve on contract for one tour of 21-27 months in the first instance. Salary in scale EA. Shg. 24300-27780 (approx. £S. 1417-1620 p.a.) plus an Inducement Allowance normally tax free, of £S. 822-886 p.a. paid direct into officer's bank in U.K. Gratuity 25% of total emoluments. Generous paid leave. Education Allowances. Furnished accommodation at reasonable rental. Free passages. Contributory pension scheme available in certain circumstances.

Candidates, up to age 45, must possess O.N.C. or City and Guilds Final Certificate (Telecomms.) plus 7 years relevant experience in telecomms. engineering. Equivalent experience in one of the armed services is acceptable. Candidates must have a good theoretical and practical knowledge of FSK, ISB and SSB receivers and transmitters and of Mufax and facsimile


transmitters and recorders. A good working knowledge of radar systems is essential.

The officer will be responsible to the Chief Sectional Engineer for the installation, operation and maintenance of the Department's radio telecommunications, radio sounding and radar equipment. He will be liable for service anywhere in East Africa but will probably be stationed at Entebbe, Dar es Salaam or Nairobi.

Apply to **CROWN AGENTS, 'M' Division, 4 Millbank, London, S.W.1., for application form and further particulars stating name, age, brief details of qualifications and experience and quoting reference number M2K/690413/WF**

379

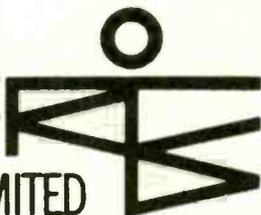RACECOURSE  
TECHNICAL  
SERVICES LIMITED



OPERATE A

**TELEVISION UNIT FOR HORSERACING**

and require a

**TELEVISION ENGINEER**

for operation and maintenance of the MCR

#### QUALIFICATIONS

- ★HNC, City & Guilds or equivalent.
- ★Experience in operation and maintenance of high grade television equipment.
- ★Willing to travel.

#### OPPORTUNITIES

- ★The Company is planning further expansion in the fields of television and electronics.
- ★Good salary and prospects.
- ★Expenses paid on location.

Applications stating age and experience should be sent to:

**RACECOURSE TECHNICAL SERVICES LTD.,  
88 Bushey Road, Raynes Park, London, S.W.20.**

400

## Opportunities with Redifon in Radio Communications

Experienced Test Engineers are invited to write to Redifon with regard to vacancies in our Test Department at Wandsworth.

The Company is engaged in the design and manufacture of a wide range of radio communications and allied equipment from military pack-set to broadcast transmitter, including communications receivers, M.F. beacons, teleprinter terminals, complete radio office installations for the Merchant Marine and mobile H.F. S.S.B. Stations. Our Test Engineers have sound technical knowledge coupled with good practical experience in the alignment and test of H.F. and V.H.F. Communications equipment. The work is varied and interesting and offers excellent opportunity to broaden experience in semiconductor, S.S.B. and Frequency synthesis.

Limited vacancies also exist for engineers experienced in Test gear maintenance.

Please write in the first instance to: The Personnel Officer

REDIFON LTD.,

Broomhill Road, Wandsworth, SW18.

**REDIFON**

A Member Company of the Rediffusion Organisation.

Suppliers of Radio Communications equipment to Home, Commonwealth, and foreign governments. Contractors to B.B.C., G.P.O., Crown Agents, Cable and Wireless, leading shipping companies of the world, etc.

403

**INTERTEL  
COLOUR  
TELEVISION**

have vacancies for

**VTR ENGINEERS**

at their studio at  
**66 DEAN STREET  
LONDON, W.1**

Applicants should have a good working knowledge of colour video tape recording. Applications giving full details of previous experience should be forwarded to

*Chief Engineer*

**INTERTEL COLOUR TELEVISION**  
WYCOMBE ROAD  
WEMBLEY, MIDDLESEX

410

**Work as a  
RADIO  
TECHNICIAN  
attached to  
Scotland Yard**

You'd be based at one of the Metropolitan Police Wireless Stations. Your job would be to maintain the portable VHF 2-way radios, tape recorders, radio transmitters and other electronic equipment, which the Metropolitan Police must use to do their work efficiently.

We require a technical qualification such as the City & Guilds Intermediate (telecommunications) or equivalent.

Salary scale: £1,095 (age 21), rising by increases to £1,500 plus a London Weighting Allowance. Promotion to Telecommunication Technical Officer will bring you more.

For full details of this worthwhile and unusual job, write to: Metropolitan Police, Room 733 (RT), New Scotland Yard, Broadway, London, S.W.1.

319

**V.H.F. TELEVISION RELAY &  
COMMUNAL AERIAL SYSTEMS**

We are planning a considerable expansion of our activities and have the following vacancies:

**I. A SENIOR ENGINEER**

to have control of all aspects of systems design, planning, estimating, installation and commissioning.

**II. ENGINEERS**

- capable of undertaking either:
- (a) System planning and estimating.
  - (b) control of installation work.
- or (c) test and commissioning duties.

Candidates for these appointments must have a good background of practical experience in this field of work, and an up-to-date knowledge of techniques and equipment.

Applications, which will be treated in strict confidence, should be sent to:



The General Manager,  
Special Services Division,  
British Relay House,  
41, Streatham High Road, S.W.16

343

**ELECTRONIC ENGINEER**

PRECISION TAPES LIMITED offer an excellent career to a man preferably between the ages of 25-40 years.

He would take full responsibility for the Electrical Servicing and maintenance of high speed tape duplicating systems and associated audio equipment operating under production conditions. Applicants must have experience in the Audio field and should have a thorough knowledge of Solid State Circuitry and hold H.N.C. Telecommunications or equivalent, but we would consider O.N.C. combined with a thorough practical experience of electronics. Salary to be negotiated. Location Chadwell Heath, Dagenham.

**Apply Mr. R. W. Holme,  
PRECISION TAPES LTD.,  
A.T.V. House,  
17 Great Cumberland Place,  
London, W.1**

391

**LEEVERS-RICH**

**EQUIPMENT LIMITED**

319 TRINITY ROAD, S.W.18 01-874-9054  
Manufacturers of Professional Tape  
Recorders and Allied Equipment. require

**SENIOR ELECTRONICS ENGINEERS**

for the DEVELOPMENT and TEST  
Departments. Staff position with top  
salaries

Apply in writing stating age and experience

# Government of ZAMBIA

## Police Department

requires

# RADIO SPECIALIST

on contract for one tour of 36 months in the first instance. Salary according to experience in the Scale Kwacha 2460 to 3000 (Approx. £.Stg.1435–Stg.1750) plus an Inducement Allowance of £.Stg.684 a year which is payable direct to the Officer's bank in the U.K. Gratuity of 25% of total salary drawn. Both gratuity and Inducement Allowance are normally TAX FREE. Liberal leave on full salary or terminal payment in lieu. Free passage. Accommodation at moderate rental. Education Allowances. Outfit and plain clothes allowances. Contributory pension scheme available in certain circumstances.

Candidates, who will serve in the rank of Inspector of Police, must have completed a five year apprenticeship or hold a Service Trade Certificate or equivalent qualification and have had at

least six years post-qualification experience in the Installation and maintenance of modern low and medium power H.F. equipment, S.S.B. and I.S.B. equipment, and of V.H.F. equipment including multiplex links. Knowledge of maintenance of teleprinters, diesel and petrol generators preferred.

The Officer will be required to maintain and install police radio equipment throughout Zambia, travelling by road and air, and to train Zambian Officers for City and Guilds examinations.

Apply to **CROWN AGENTS, 'M' Division, 4 Millbank, London, S.W.1, for application form and further particulars stating name, age, brief details of qualifications and experience and quoting reference number M2Z/61274/WF.**

404

### Borough of Lowestoft Committee for Education

LOWESTOFT COLLEGE OF  
FURTHER EDUCATION

Engineering and Science Department

Principal: A. E. Boddy, B.Sc.(Econ.), F.R.G.S.

## LECTURER

LECTURER GRADE I required for teaching radio, electronics and other subjects associated with the General Certificate for the Radio Officer (Merchant Navy) Course.

Salary in accordance with the Burnham Scale, at present £1,110 to £1,850, plus allowances for approved qualifications. Starting point within the scale determined by past teaching and/or appropriate industrial experience.

The post is vacant as from the 1st of May, 1970. Applicants preferably with teaching experience, suitable qualifications and industrial experience should apply to the Secretary, The Lowestoft College of Further Education, St. Peter's Street, Lowestoft, Suffolk, for further particulars and application form.

393

## Blind landings depend on AVIONICS

SKILLED MEN are required for the repair and overhaul of aircraft instruments and flight control units at BEA's Workshops at Heathrow Airport – London.

Applicants should preferably be apprentice trained in one of the following trades—

Electrical  
Instruments (Fine mechanical)  
Radio  
Electronics

and can expect a certain amount of 'on-the-job' training.

Commencing rate £27.4.6. rising within 6 months to £28.16.0. and ultimately to £32.16.6. according to qualifications and responsibility. Avionics supplement of £2.10.0. pw may later be earned by

qualified staff.

- \* Good promotion prospects
- \* Generous shift payments when applicable
- \* Opportunities for holiday air travel.

Write or phone for an application form to  
Personnel Officer Engineering  
(Employment) (W/W)  
BEA, Engineering Base,  
Heathrow Airport – London,  
Hounslow, Middlesex.  
SKYport 3131 Exts. 4302, 4185 or 4692

# BEA

# Electronics Maintenance Engineers

There are excellent opportunities in the Installation and Maintenance Division of U.K. Electronics and Industrial Operations of E.M.I. Ltd., at Hayes, Middlesex, for engineers to carry out maintenance work on a wide variety of electronic equipments including laboratory test gear and trans-ceivers.

Candidates should be between 21 and 45 years of age and have some experience in this type of work. Consideration will be given to experienced Radio and Television servicing technicians and to ex service personnel.

Commencing salaries of up to £1,500 per annum will be paid and staff conditions include contributory pension scheme and free life assurance.

*Please apply in writing giving brief personal and career details to:*

G. W. Fox, Personnel Department,  
U.K. Electronics & Industrial Operations,  
E.M.I. Ltd., Blyth Road,  
Hayes, Middlesex.  
Tel: 01-573 3888, Ext. 411.



309

## GEC-Marconi Electronics

# ELECTRONIC TECHNICIANS

**Marconi can offer you**

- Attractive salary. Annual salary reviews**
- Good working conditions. 37-hour working week**
- Non-tied housing in a new town in certain circumstances**

At Basildon we have a number of vacancies for technical staff to work on the design and manufacture of specialised electronic test equipment and also on the repair and maintenance of general electronic test apparatus. Applicants should have a good basic knowledge of electronics and have some previous industrial or retail trade experience.

## Marconi



Please telephone or write for an application form to: Mr. R. McLachlan, Personnel Officer, The Personnel Dept, The Marconi Company Limited, Christopher Martin Road, Basildon, Essex. Phone: Basildon 22822.

A GEC-Marconi Electronics Company

2814

## SENIOR TELEVISION TECHNICIAN

is required to be responsible for facilities in a small wired TV Systems Laboratory. He should be conversant with Colour Television Receivers and will be responsible for the maintenance of specialised test equipment. Other duties will include maintenance of records and equipment movement control.

Qualifications in R.T.E.B. and Colour Endorsement or H.N.C. desirable.

Good prospects of promotion for a keen young man with initiative. Salary negotiable up to £1,500 p.a. depending on qualifications. Training can be given. Subsidised canteen.

Write, giving details of past experience to:

**Head of Operational Services Dept.  
Rediffusion Engineering Ltd.  
187 Coombe Lane West  
Kingston-upon-Thames, Surrey**  
Tel: 01-942 6641

390

## COUNTY MEDICAL PHYSICS DEPARTMENT

### ST. GEORGE'S HOSPITAL, LINCOLN ELECTRONICS TECHNICIAN

(Medical Physics Technician Grade III)

Salary scale: £1,180—£1,500 p.a.

required to assist in the development and construction of electronics instruments used in Medical Physics. Applicants should possess O.N.C. or equivalent electro-technical qualifications and should be able to construct and test equipment from circuit diagrams. Applications, including age, details of qualifications and experience with the names of two referees to be sent to **The Hospital Secretary, St. George's Hospital, Lincoln.**

356

# Government of UGANDA REQUIRES BROADCASTING ENGINEERS

To serve on contract for one tour of 21-27 months in the first instance. Salary according to experience in scale Uganda Shg. 21,120-27,780 (£Stg. 1,232-1,620) a year, plus an Inducement Allowance, normally tax free, of £Stg. 778-886 a year, paid direct into a Uganda bank account nominated by the officer. Gratuity 25% of total emoluments drawn. Liberal paid leave. Accommodation provided at reasonable rental. Outfit and education allowances. Free passages. Contributory pension scheme available in certain circumstances.

Candidates must possess the City and Guilds Final Certificate in Telecommunications (with Radio) or an equivalent qualification and have wide practical experi-

ence of technical broadcasting equipment including high power M.F. transmitting and studio control equipment. The officer will be required to undertake senior operational duties including the maintenance of broadcasting equipment in transmitting stations and studios; outside broadcasts and recordings in remote districts; and to give assistance with the training of junior engineering staff.

Apply to CROWN AGENTS, 'M' Division, 4 Millbank, London, S.W.1., for application form and further particulars stating name, age, brief details of qualifications and experience and quoting reference M2K/690995/WF.

405

## METROSOUND GROUP OF COMPANIES

### ELECTRO-MECHANICAL ENGINEER

A vacancy exists for a skilled Electro-mechanical Engineer who will be required to service and maintain a production unit of high speed tape duplicating equipments.

The applicants must be thoroughly conversant with the latest transistorised circuitry as applied to professional tape recorders and ideally should have had some experience with studio equipments.

The successful applicant who will be laboratory based will be paid a minimum salary of £1,600 p.a. which could be considerably increased in the case of an exceptionally experienced or qualified applicant.

Please write or telephone in the first instance to:

Mr. R. Bishop,  
Audio Works, Cartersfield Road,  
Waltham Abbey, Essex.  
Waltham Cross 31933.

402

## OMRON PRECISION CONTROLS

SUPPLIERS OF

### PROCESS TIMERS MICRO & LIMIT SWITCHES

are still expanding  
and require experienced  
FIELD SALES ENGINEERS

also

### SALES OFFICE MANAGER

to co-ordinate operations

Apply: P. A. LEIGH.  
Tel. 01-723 2231

349

## RADIOLOGICAL PROTECTION SERVICE

(Department of Health and Social Security and Medical Research Council)

Clifton Avenue, Belmont, Sutton, Surrey

requires

### Junior Technician and Technician

- POST 1. JUNIOR TECHNICIAN required for duties in the Department of Electronics to assist in the construction of nucleonic instruments. Preference will be given to those candidates with aptitude and interest in electronic and mechanical practice. Salary according to experience at a point on the scale £467 (-922) plus London Weighting. M.R.C. conditions of employment. Applications with the names and addresses of two referees to the Administrative Officer at the above address, quoting reference 70/3/4/17.
- POST 2. TECHNICIAN required for duties in the Department of Electronics to maintain nucleonic instruments and systems. Previous experience of testing and 'fault-finding' on Electronic equipment is essential. Two 'A' level G.C.E.'s desirable but not essential. Salary according to qualifications and experience at a point on the scale £982 (-1255) plus London Weighting. M.R.C. conditions of employment. Applications with the names and addresses of two referees to the Administrative Officer at the above address, quoting reference 70/3/4/9.

Closing Date: 19.3.70

386

# COMPUTER ENGINEERS



## the big Burroughs challenge!

Burroughs large on-line systems dominate the U.K. market. A wide variety of concepts, a rapidly expanding market and a policy of promotion from within - all mean exciting opportunities for trained computer engineers to develop their skills in the large, on-line systems field or into the supervisory grades and beyond. Join the Burroughs boom - and grow with us.

We want experienced computer engineers to work on our B5500 and B6500 installations in the Greater London area. With Burroughs, you can find the freedom to enlarge your talents, open fresh horizons, learn new skills -



# Burroughs

on the largest third generation systems in the world - these are the exciting prospects at Burroughs. In return we are offering you three weeks' paid holiday, free life assurance and a contributory pension scheme.

If you have an electronics qualification and experience with computer systems, then take a big step now into one of today's development industries - fill in the coupon and send off for one of our application forms. The address is:

The address is: **Geoff Lewis, Burroughs Machines Ltd. (Z), Heathrow House, Bath Road, Cranford, Hounslow, Middlesex.**

NAME .....

ADDRESS .....

ww/a

Vacancies exist in our **AYLESBURY** and **CRAWLEY** factories for:

# SERVICE ENGINEERS

**Our Product.**

Flight Simulators

**Requirements.**

A complete theoretical knowledge coupled with at least 2 years practical experience in one or more of the following:—  
Digital computing techniques, hardware, software & computer peripherals.  
We are prepared to train suitable applicants who have considerable experience in transistorised and integrated circuits.  
A knowledge of analogue computing techniques and principles of hydraulics systems would be advantageous. **ONC** or **City & Guilds Electronics.**

**Travel.**

Must be prepared to travel anywhere in the U.K. and Overseas.

**Salary.**

Negotiable but we are prepared to go as high as £1,800. for the right persons.

**Applications to:**

**Personnel Manager, Redifon Air Trainers Limited, Bicester Road, Aylesbury, Bucks.**      **Personnel Manager, Redifon Limited, Flight Simulation Division, Gatwick Road, Crawley, Sussex.**

413

# BP

requires an

## ASSISTANT TECHNICIAN

to undertake maintenance and development work in the Communications Division of their **LONDON OFFICE**. The maintenance element involves a sound knowledge of Teleprinters and associated telegraph equipment, and the development work requires a good working knowledge of Electronics and/or Audio systems.

Candidates, aged 25 to 30 years, should possess a minimum qualification of **ONC** and have at least 2 years' relevant practical experience. Preference will be given to applicants continuing their studies to **HNC**.

We offer three weeks' holiday, subsidised lunches, non-contributory pension and other benefits.

Please write giving brief details to **Mrs. M. G. Park, External Recruitment, The British Petroleum Company Limited, Britannic House, Moor Lane, London, E.C.2**, quoting reference **R.11193/ZH**.

407

## ANTARCTIC EXPEDITION

require

### Wireless Operator/Mechanics

With current morse speed of 20 w.p.m. **PMG Certificate**, teleprinter experience essential. Salary from £1,003 according to qualifications and experience with all living and messing free.

For further details apply to:

**BRITISH ANTARCTIC SURVEY**

30 Gillingham Street, London, S.W.1

406

# CONTINUOUS EXPANSION

Standard Telephones & Cables, Microwave and Line Division based at Basildon are growing fast. In order to keep pace with this consistent growth rate we require the following


## Installation Engineers Technicians & Testers

Ref. 25720

To test and commission Multiplex, Co-axial Line and Microwave Radio Systems.

Ideal candidates will be less than 45 years of age with practical experience on some of the above equipment. These challenging posts call for drive, initiative and common sense. It is necessary for applicants to be prepared to work anywhere in the U.K.

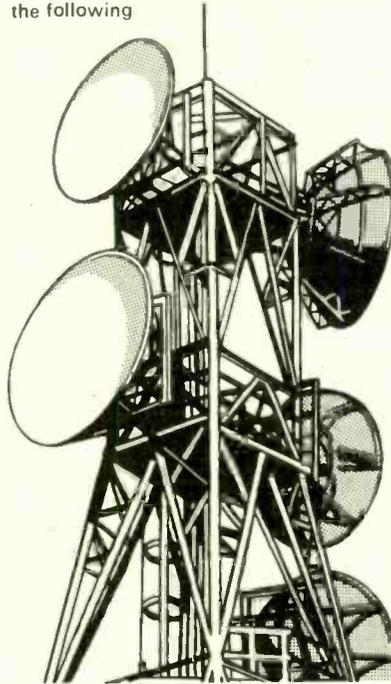*Applications should be addressed to*  
The Personnel Officer,  
STC Chester Hall Lane,  
Basildon, Essex.



## Test Technicians

Ref. 27221

The diversity of products manufactured at the Basildon Plant demands experienced testing staff for work on complex transmission systems.

Candidates should hold an ONC in electrical engineering and be able to offer considerable practical experience in the field of testing and fault clearing all types of land-unit, pcm and microwave equipment.

# STC

91

## UNIVERSITY OF LIVERPOOL Institute of Child Health Alder Hey Children's Hospital

Applications are invited for the post of  
**ELECTRONICS TECHNICIAN**

to assist with research. Applicants should be suitably qualified and have experience in general instrumentation and pulse techniques. The successful applicant will be expected to be able to assist in the design and development of medical electronic instruments. Initial salary, according to age, qualifications and experience. Application forms may be obtained from the Registrar, The University, P.O. Box 147, Liverpool L69 3BX. Quote ref. RV/5643/W.W.

384

## JUNIOR ELECTRONICS TECHNICIAN

required for construction and repair of electronic instruments and maintenance of a Linear Accelerator. G.C.E. "O" level in Physics and Maths required; "A" levels or O.N.C. an advantage. Day release for further study is possible. Salary according to age and experience.

Apply with full details to The Director,  
Medical Research Council Cyclotron  
Unit, Hammersmith Hospital, London,  
W.12.

360

## MALE TECHNICIAN

**BRISTOL POLICE** require a Technician to service and maintain facsimile and dictation equipment.

38 hour week. Salary £965-£1,130 according to qualifications. The post is superannuable. Applications to:

The Chief Constable  
Bristol Police Headquarters, Bristol 1 389

## CRAFTSMEN and SEMI-SKILLED MEN

are required for interesting work in the  
Signal Engineering Department of  
London Transport at FULHAM



The workshop in which these vacancies exist undertakes a considerable variety of work which includes the manufacture of prototype mechanical and electronic equipment for Signalling, Automatic Trains and Automatic Fare Collection projects together with the overhaul of electro-pneumatic equipment, ticket machines, clocks, telephones and allied apparatus and fault finding on electronic components.

- GOOD RATES OF PAY AND PROSPECTS OF PROMOTION
- ADDITIONAL PAYMENT FOR OVERTIME
- EXCELLENT WORKING CONDITIONS
- FREE TRAVEL ON AND OFF DUTY
- PENSION AND SICK SCHEMES

This is an opportunity for a secure, absorbing and worthwhile occupation. Please apply to a London Transport Recruitment Centre:—

Griffith House,  
280 Old Marylebone Road,  
London, N.W.1

Chiswick Works,  
566 High Road,  
Chiswick,  
London, W.4 359



## RADIO & TELEVISION SERVICING RADAR THEORY & MAINTENANCE

This private College provides efficient theoretical and practical training in the above subjects. One-year day courses are available for beginners and shortened courses for men who have had previous training.

Write for details to: The Secretary, London Electronics College, 20 Penywern Road, Earls Court, London, S.W.5. Tel.: 01-373 8721.

84

# Electronic Test Engineers

Pye Telecommunications of Cambridge has immediate vacancies for Production Test Engineers, The work entails checking to an exacting specification VHF/UHF and SSB radio telephone equipment before customer delivery; applicants must therefore have experience of fault finding and testing electronic equipment, preferably communications equipment. Formal qualifications, while desirable, are not as important as practical proficiency. Armed Service experience of such work would be perfectly acceptable.

Pye Telecom is the world's largest exporter of radio telephone equipment and is engaged in a major expansion programme designed to double present turnover during the next 5 years. There are therefore excellent opportunities for promotion within the Company. Pye also encourages its staff to take higher technical and professional qualifications. These are genuine career opportunities in an expansionist company so write, or telephone, for an application form without delay. Interviews can be arranged anywhere in the country at locations to suit the majority of applicants.

Mrs A. E. Darkin, Pye Telecommunications Ltd.,  
Cambridge Works, Haig Road, Cambridge.  
Telephone: Cambridge 51351.



387

## MOBILE COMMUNICATION ENGINEERS SOUTHERN GERMANY

Design engineers are required for interesting projects in an attractive area of Southern Germany. Engineers are required for a contract of two years' duration and should be qualified to a minimum standard of H.N.C. and some years' experience in either of the following fields:

- (a) Mobile V.H.F. or U.H.F. solid state transmitter output stage design. Preferably at outputs of 20W or more.
- (b) Vehicle aeriels and matching network design for wideband V.H.F.

The remuneration will be in the range of £3,000-£4,000 p.a., depending upon qualifications and experience. Write in confidence to:

**INTERNATIONAL SCIENTIFIC CONSULTANTS LTD.**  
P.O. BOX 75, NORMANDY HOUSE, ST. HELIER, JERSEY, C.I. Quote Ref: EG.14

385

## LARGS of Holborn for High Fidelity

the leading retailers of Radio and Hi-Fi equipment require top-class **RADIO AND HI-FI SERVICE ENGINEERS** First-class working conditions and top rates of pay (according to experience) for the right men.

Apply in confidence to:

A. BARROWS, LARGS OF HOLBORN,  
76/77 HIGH HOLBORN, LONDON, W.C.1.  
Phone: 01-242 2626 365

### GUY'S HOSPITAL MEDICAL SCHOOL Department of Physics

#### ELECTRONICS ENGINEER

or TECHNICIAN required to join Blood Flow Research Group for three-year project. Applicants should possess specialist experience/interest in construction/development of analogue solid state circuitry, and Grad.I.E.E.E., H.N.D., H.N.C., O.N.C., or equivalent qualifications. Salary according to qualifications and experience, with superannuation.

For further details of work telephone Dr. Gosling or Mr. King, 01-407 7600 Ext. 546. Applications giving full particulars and quoting ref. PH.2, to The Secretary, Guy's Hospital Medical School, London Bridge, S.E.1. 372

We are reorganising our service department and require three

#### TOP GRADE SERVICE ENGINEERS/ TECHNICIANS

to work exclusively on Quad amplifiers and tuners returned for factory overhaul or repair.

Apply, in confidence, giving full details of training and experience to

Mr. J. H. Walker

**ACOUSTICAL MANUFACTURING CO. LTD**  
St. Peter's Road, Huntingdon 375

### LANCASHIRE CONSTABULARY HUTTON

wanted

#### RADIO TECHNICIANS

Must have experience in Radio/Television servicing and have obtained CGLI/TREB in Television Final Servicing Certificate or equivalent.

Pay £985 to £1,500.

Starting point according to age and experience.

Apply to: The Chief Constable,

P.O. Box 77, Lancashire Constabulary,  
Hutton, Preston, PR4 5SB 380

### An immediate vacancy occurs at THE WIRELESS COLLEGE, COLWYN BAY, NORTH WALES

for a SENIOR INSTRUCTOR to take overall charge of the preparation of students for P.M.G./M.P.T. examinations, and to be directly responsible for telegraphy instruction. Applicants must hold a P.M.G. First Class Certificate. Recent marine operating and/or teaching experience is desirable but not essential. Write in the first instance to the Principal. 355

## ENGINEERS

Have you considered a career in Technical Authorship? If you have sound experience in electronics and ability to write clear concise English we can offer positions as Technical Authors. The salary range is £1500-£2000 plus with excellent prospects and rewards. Box No. W.W.364, Wireless World.

# RADIO OPERATORS

There will be a number of vacancies in the Composite Signals Organisation for experienced Radio Operators in 1970 and in subsequent years.

Specialist training courses lasting approximately nine months, according to the trainee's progress, are held at intervals. Applications are now invited for the course starting in September, 1970.

During training a salary will be paid on the following scale:

Age 21	£800 per annum
" 22	£855 "
" 23	£890 "
" 24	£925 "
" 25 and over	£965 "

Free accommodation will be provided at the Training School.

After successful completion of the course, operators will be paid on the Grade 1 scale:

Age 21	£965 per annum
" 22	£1025 "
" 23	£1085 "
" 24	£1145 "
" 25 (highest age point)	£1215 "

then by six annual increases to a maximum of £1650 per annum.

Excellent conditions and good prospects of promotion. Opportunities for service abroad.

Applicants must normally be under 35 years of age at start of training course and must have at least two years' operating experience. Preference given to those who also have GCE or PMG qualifications.

Interviews will be arranged throughout 1970.

Application forms and further particulars from:

**Recruitment Officer, (R.O.3) Government Communications Headquarters, Oakley, Priors Road, CHELTENHAM, Glos., GL52 5AJ**

Telephone No. Cheltenham 21491, Ext. 2270

92

## THE UNIVERSITY OF MANCHESTER

### TELEVISION SERVICE

Applications are invited for the post of **ASSISTANT STUDIO ENGINEER**, to assist with the maintenance and operation of television equipment used in the University studios and Mobile Unit.

Applicants should possess a Higher National Certificate or equivalent and have a good knowledge of basic electronics with particular emphasis on transistor circuitry. They should have experience in maintenance of electronic equipment, radar, television or similar field.

Initial salary range £1050-£1300 per annum.

Applications, giving full details of age, qualifications and previous experience and giving the names of two persons to whom reference may be made, should be sent as soon as possible to The Director of Television Services, The University, Manchester M13 9PL.

368

# SKILLED IN ELECTRONIC ENGINEERING?

## Help keep aircraft on the straight and narrow

Air traffic has become so congested that complex electronic techniques are used as an aid in controlling aircraft both on airways and on airport approaches. As a Telecommunications Technical Officer III in the **National Air Traffic Control Service** of the Board of Trade, your job would be to install and maintain various air navigational and landing aids at civil airports, and communications and computer systems at radar stations and signal centres.

Because you handle such advanced equipment, you will receive thorough training. Study for higher qualifications is encouraged, and this could range from short courses with financial assistance to full-time study at a university or technical college.

**Pay:** (London rates—a little less elsewhere) £1,350 starting salary at 23, £1,625 at age 28 or over on entry, rising to £1,810. Within 3 years you could be upgraded, and on a scale rising to £2,050. A few years after that, you could be in the salary bracket going up to £2,375, and there are several higher grades still.

**Qualifications:** O.N.C. in Engineering, including a Pass in Electrical Engineering; or equivalent standard of technical education.

Send for full details and an application form (which must be returned completed by April 3rd, 1970) to Civil Service Commission, 23 Savile Row, London, W1X 2AA. Please quote S/207/13

397

## NORFOLK EDUCATION COMMITTEE

The County Technical College, King's Lynn

### LECTURER GRADE I

in **RADIO and TELEVISION SERVICING** to teach electronics, radio and TV Servicing (including Colour) to C & G Final.

Applicants should have considerable relevant practical experience and hold a C & G Final Certificate.

Salary £1100-£1900 p.a. point of entry depending upon qualifications and experience. Details and forms from the Registrar at the College.

County Hall,  
Martineau Lane,  
Norwich,  
NOR 49A

F. LINCOLN RALPHS,  
Chief Education Officer

388

## TV MECHANICS FOR NEW ZEALAND

**RADIO and TV MECHANICS**—are you dissatisfied with your present working conditions, high taxation and lack of progress? Why not shift to the sunny South Pacific and join the friendly team at TISCO, New Zealand's largest Service Company! Being purely in Television Service, our mechanics are important people, not just numbers on a time sheet.

All 30 of our Branch Managers are mechanics. You can be with us in 3 months if you write now. Requirements: 5 years' experience and £20 towards the family's fare, remainder of which will be paid.

**Mr. B. I. Wells, Tech. Supervisor,  
TISCO Ltd.,  
Private Bag, Royal Oak, Auckland,  
NEW ZEALAND.**

351

# CAREERS IN RECORDING

**PHILIPS PHONOGRAPHIC INDUSTRIES** in Baarn, Holland, offer excellent career possibilities to young men between 22 and 30 years of age to join the Classical Recording Department as technicians.

Duties will include the installation and maintenance of equipment on major recording sessions in various parts of Europe.

Candidates must be prepared to reside in Holland and should have a thorough knowledge of at least one European language, ideally German or French.

Essential requirements are a good knowledge of music and the ability to follow a musical score; practical knowledge of basic electronics with experience in transistor circuitry and techniques; a general knowledge of recording and test equipment. ONC in telecommunications and audio experience would be an advantage.

Please apply in writing, giving details of age, education and experience, to:

**The Personnel Officer,  
Philips Records Limited,  
Stanhope House,  
Stanhope Place,  
London, W.2.**

*Initial interviews will be held in London.*

345

**Experienced Mfr./Working Jewellers** have spare capacity to diversify with **Electronics manufacturer. Five/soft soldering-Rhodium Plating of small component parts.**

**Strictest confidence. Box No. WW392**  
392

## NOTTINGHAMSHIRE

### BEESTON COLLEGE OF FURTHER EDUCATION

#### Radio, TV and Electronics Technicians, Part I Course No. C & G 434

A one-year, full-time and/or block release course will commence in September, 1970. The course will be open to students already engaged in the industry and to students leaving school this year who possess a good standard in mathematics and science. Minimum age of entry is 16 years.

#### Radio, TV and Electronics Mechanics, Part I & II Course No. C & G 433

A two-year block release course will be offered in September, 1970. Part I of 13 weeks and Part II of 22 weeks. Minimum age of entry is 15 years.

#### Radio and Television Servicing, Part I Course No. C & G 48

This one-year, full-time course will be offered next session for the last time after which it will be replaced by the Technicians and Mechanics courses. Students already in industry and those leaving school this year who possess a good standard in mathematics and science will be accepted on this course.

**For further particulars and entry forms for the above courses write to: The Principal, Beeston College of Further Education, High Road, Beeston, Nottingham, NG9 4AH.**

## SITUATIONS VACANT

**A FULL-TIME** technical experienced salesman required for retail sales; write giving details of age, previous experience, salary required to—The Manager, Henry's Radio, Ltd., 303 Edgware Rd., London, W.2. [57]

**ARE YOU INTERESTED IN HI FI?** If so, and you have some experience of selling in the Retail Radio Trade, an excellent opportunity awaits you at Telesonic Ltd., 243 Euston Road, London, N.W.1. Tel. 01-387 7467. [21]

**DEPARTMENT** of Nuclear Physics, University of Oxford, has a vacancy in the experimental electronics group for a technician to work on the development, building and maintenance of modern nuclear electronic equipment. Salary within the range of £659-£1,316 depending on age, qualifications and experience. Five-day week working and good paid leave. Write to T. L. Green, Nuclear Physics Laboratory, Keble Road, Oxford, mentioning reference A123. [408]

**ELECTRONICS OFFICER** required to run C.C.T.V. and Audio Section of the Department of Audio-Visual Communication, British Medical Association. He will be required to give information and advise on equipment to medical teachers. His responsibilities will include establishing contact with manufacturers, ordering equipment and materials, maintaining, modifying and operating equipment for demonstration and experimental purposes. Applicants should be able to present evidence of formal training and practical experience will be essential. The starting salary will be up to £1,550 p.a. according to qualifications and experience. Write briefly, in the first instance, stating age, education, qualifications and experience to the Director, Department of Audio Visual Communication, The British Medical Association, B.M.A. House, Tavistock Square, London, W.C.1. [347]

**RADIO TEST ENGINEERS.** Production testing and fault finding on transistorised Audio Amplifiers & FM Receivers. 5-day week. Apply, Chief Engineer, Rogers Developments (Electronics) Ltd., 4-14 Barneston Road (off Bromley Road), Catford, S.E.6. Tel: 01-698 7424/4340. [22]

**REDIFON LTD.** require fully experienced TELECOMMUNICATIONS TEST ENGINEERS and ELECTRONICS INSPECTORS. Good commencing salaries. We would particularly welcome enquiries from ex-Service personnel or personnel about to leave the Services. Please write giving full details to—The Personnel Manager, Redifon Ltd., Broomhill Road, Wandsworth, S.W.18. [26]

**SERVICE ENGINEER** for repairing Audio Equipment required by Dixons Photographic Ltd., to be employed at North Acton. If interested, please contact P. Rowles for more details, either by telephone (01-965 0411) or by letter to Camera House, 95 Victoria Road, London, N.W.10. [362]

**WE HAVE VACANCIES** for Four Experienced Test Engineers in our Production Test Department. Applicants are preferred who have Experience of Fault Finding and Testing of Mobile VHF and UHF Mobile Equipment. Excellent Opportunities for promotion due to Expansion Programme. Please apply to Personnel Manager, Pye Telecommunications Ltd., Cambridge Works, Haig Road, Cambridge. Tel. Cambridge 51351, Extn. 327. [77]

# ELECTRONICS TECHNICIANS

As part of our rapid expansion in production requirements, we need a number of experienced men to trace and rectify faults in the complex equipment we use in the assembly and testing of semi-conductors. A sound knowledge of basic electronics is essential, and experience of working with advance equipment is highly desirable.

Good pay and conditions. Overtime work readily available.

Please write brief details or telephone for application form to:

**ITT**

**Personnel Manager  
STC Semiconductors Limited  
Footscray, Sidcup, Kent  
01-300-3333 Ext. 397**

**STC  
SEMICONDUCTORS**

369

## £2,200 — £2,600 ELECTRONIC ENGINEERS

are required for interesting contracts in the SOUTHERN HOME COUNTIES. Min. qualification H.N.C. and design experience in one of the following fields—wide band solid state feedback amplifiers, filters and networks or communication repeater amplifiers. Write to:

### STRAND TECHNICAL CONTRACTORS LTD.

Norman House, 105-109 Strand, London, W.C.2; or Tel.: 01-836 6443

Quote Ref. B.37

346

## TECHNICIAN

Applications are invited for the post of technician to maintain computer systems, to construct computer hardware, and to assist in the general running of a small electronics laboratory.

Suitable qualifications are experience in electronic equipment construction and maintenance of electro-mechanical devices and an interest in the subject generally.

Salary range £868—£1,486.

Pension plan.

Apply in first instance by letter stating briefly personal details and relevant experience to:

**Mr. P. FENWICK, C.C.A.**

**R.S.M. Building, Imperial College,  
Prince Consort Road, London, SW7**

383

## CRANFIELD INSTITUTE OF TECHNOLOGY

### DEPARTMENT OF ELECTRICAL AND CONTROL ENGINEERING

Applications are invited for appointment as

### TECHNICAL OFFICER

in the High Frequency and Radar laboratories which are concerned with postgraduate teaching and research.

The duties, which are interesting and varied include the supervision of the day-to-day activities in the laboratories and responsibility for the development of specialised experimental equipment. Candidates should have appropriate experience and possess an H.N.C. or Graduateship of a professional institution as a minimum qualification. Salary within scale rising to £1,623 p.a. (under review). 37-hour week of five days, staff superannuation and sick pay schemes, generous holidays. Subsidised transport over a wide area.

Application form from Staff Records Officer, Cranfield Institute of Technology, Cranfield, Bedford.

373

## RADIO TECHNICIAN

with initiative, responsibility, and ability to work unsupervised, is required by company operating construction barges and rigs in the North Sea.

The applicant should be capable of carrying out all repairs to VHF, SSB, Marine I.F. R-T, Radar, Sonar, and C.C.T.V.

Offshore and away from base duties may be frequent.

Salary will be negotiable.

Applicants should write giving brief details of experience and stating qualifications to:

**Mr. Paul Nagelsmit  
Brown & Root (U.K.) Limited  
Casing Yard, Suffolk Road,  
Great Yarmouth, Norfolk**

Tel: Great Yarmouth 53371

352

### SITUATIONS WANTED

**E**LECTRONIC ENGINEER, 22 years experience D.C., L.F., Audio, etc. Products and test gear. Presently £2,000 p.a., London. seeks responsible position West of line Salisbury/Worcester. Alternatively seeks others to start small Design/Manufacture Business same area. Box No. W.W. 396 Wireless World.

# Radio Operators

## Your chance of a shore job with good pay from the start!

If you hold a 1st Class Certificate of Competence in Radiotelegraphy issued by the Postmaster General or the Minister of Posts and Telecommunications, or an equivalent certificate issued by a Commonwealth administration or the Irish Republic, the Post Office can offer you employment at a United Kingdom Coast Station, with a starting salary of £965—£1,215 (depending on age). Annual rises will take you to £1,650 and there are good prospects of promotion to more responsible and better paid posts.

If you are 21 or over, please write for more details to:

**The Inspector of Wireless Telegraphy,  
External Telecommunications Services,  
Wireless Telegraph Section (WW),  
Union House, St. Martins-le-Grand,  
LONDON E.C.1.**

# REDIFFUSION

## COLOUR TELEVISION FAULTFINDERS & TESTERS

We have a number of vacancies in our Production Test Departments for experienced faultfinders and testers.

Knowledge of transistor circuitry and experience with Colour Receivers together with R.T.E.B. Final Certificate or equivalent qualifications required.

These will be staff appointments with all the expected benefits.

Applications to:

**Works Manager,  
Rediffusion Vision Service Ltd.,  
Fullers Way South,**

**Chessington, Surrey (near Ace of Spades).**

**Phone: 01-397 5411**

93

# Test Technicians

Our test department is expanding. It is responsible for the testing of magnetic storage devices, high-speed printers, punched-card and paper-tape equipment.

For people with experience in electronics, opportunities exist immediately. Further vacancies will arise over the next few months. Training will be given to those who do not have previous computer experience.

Applicants must have worked on the testing, maintenance or repair of electronic equipment, and preference will be given to those qualified to ONC (Elect.) or C&G Final.

Locations: Kidsgrove and Winsford. Both are situated in rural surroundings bordering on the Cheshire Plain. Housing is available at attractive prices, and assistance with mortgage can be arranged.

Write giving details of age, qualifications, and experience, to:

Brian Buckley, Personnel Services Manager,  
International Computers Ltd., Kidsgrove,  
Stoke-on-Trent, quoting reference WW239M.

**International Computers**

**ICL**



## ELECTRONICS CIRCUIT DESIGN ENGINEER

for varied and interesting work on the application of I.C.'s and discrete component circuits to the control and regulation of electric power.

Minimum qualifications: O.N.C. (Electronics). Experience in closed loop system design would be valuable.

Housing and removal assistance available in some circumstances.

Write with full details to:

**The Technical Director,  
BRENTFORD ELECTRIC LIMITED,  
Manor Royal, Crawley,  
Sussex**

358

**LEEDS POLYTECHNIC**  
Calverley St., Leeds LS1 3HE

Full-time three-week courses:

### The Principles of COLOUR TELEVISION

4th-22nd May and 8th-26th June

For details, write to:  
Department of Electrical Engineering  
370

## PERKIN-ELMER LIMITED OF BEACONSFIELD

is actively engaged in the development and manufacture of automatic analytical equipments using infra-red, ultra-violet, nuclear magnetic resonance and other techniques.

The Company is in the process of considerable expansion and requires:

### ELECTRONIC TEST ENGINEERS

The job descriptions for these appointments call for a sound knowledge of modern electronic circuits and the ability to diagnose faults logically and systematically using standard test methods. O.N.C. (Elec); City and Guilds Technicians Certificate or equivalent is desirable, but applications will be considered from those who have good practical test experience.

Apply to:

**P. L. Nielsen  
Personnel Officer  
PERKIN-ELMER LIMITED  
Post Office Lane  
Beaconsfield, Bucks.**

#### ARTICLES FOR SALE

AMAZING VALUE	
Plessey SL402A Preamp and 2W Amp	42/-
GE PA234 1W Audio Amplifier	17/6
RCA 40669 BA 400V Triac	24/-
Notes supplied FREE with each order.	
New Full Specification Devices, by Return.	
P & P 1/-	Cash With Order. Mail Order Only.
Unbeatable rates for medium quantities.	
<b>JEF ELECTRONICS (W.W.),</b>	
York House, 12 York Drive, Grappenhall, Warrington, Lancs. 394	

#### CAPACITOR DISCHARGE IGNITION SYSTEM (W.W. JANUARY 1970)

Inverter transformer 30VA Ratio 15 : 1  
CWO 32/- + 5/- p. & p.  
**MAGTOR LTD., 68 Dale St., Manchester M1 2HS**  
361

**A** CY22, BC108, BFY52, OC45, OC71, OC202, ZTX300, 2N2926, 2N3708. All at 1/9 each or 16 for £1. Money back guarantee. P. & P. 1/-.—J. M. King, 17 Buckridge, Portpool Lane, London, E.C.1. [382]

**BRAND NEW ELECTROLYTICS** 15/16V. 0.5, 1, 2, 5, 8, 10, 20, 30, 40, 50, 100 mfd. 8s. 5d. 200 mfd. 10d. 1 watt 5% carbon film resistors E.12 series 10 ohms to 1 Megohm 1/5. Wirewound 5W 5% E.12 series 15 ohms to 15,000 ohms 10d.; postage 1/- per order.—The C.R. Supply Co., 127 Chesterfield Road, Sheffield, S.8. [381]

**BUILD IT** in a DEWBOX quality plastics cabinet. 2 in. X 2 1/2 in. X any length. D.E.W. Ltd. (W), Ringwood Rd., FERNDOWN, Dorset. S.A.E. for leaflet. Write now—Right now. [76]

**HOW to Use Ex-Govt. Lenses and prisms.** Booklets. Nos. 1 & 2, at 2/6 ea. List Free for S.A.E. H. W. ENGLISH, 469 RAYLEIGH RD., HUTTON, BRENTWOOD, ESSEX. [87]

**MUSICAL MIRACLES.** Send S.A.E. for details of Cymbals and Drum Modules, versatile independent bass pedal unit for organs, pianos or solo, musical novelties, waa-waa kits (49/-). Also bargain components list reed switches etc. D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset. [95]

**NEW CATALOGUE** No. 18, containing credit vouchers value 10/-, now available. Manufacturers' new and surplus electric and mechanical components, price 4/6, post free. Arthur Sallis Radio Control Ltd., 28 Gardner Street, Brighton, Sussex. [94]

**SHIP'S R/T and Alarm** for sale. Siemen F.20. Best offer secures. Box W.W. 363, Wireless World.

**SOLARTRON QD 910** storage Oscilloscope perfect £250. Frequency decade Schomandl 20 CS to 31-111 MCS new. Offers, Burgess, East Lake, London Road, Bognor Regis. [357]

**UHF, COLOUR and TV SERVICE SPARES.** Leading British makers' surplus Colour Frame and Line time base units incl. EHT transformer, £5, carriage 10/-. Integrated UHF/VHF 6 position push button tuner, 4 transistors, knobs, circuit data. Easily adjusted for use as 6 position UHF tuner. £4/10/-, P/P 4/6. UHF 3 transistor tuner incl. circuit. £2/10/-, P/P 4/6. UHF/VHF transistorised IF panel. £3/10/-, P/P 4/6. MURPHY 600/700 series complete UHF conversion kits incl. tuner, drive assy. 625 IF amplifier, 7 valves, accessories, housed in special cabinet plinth assembly, £8/10/- or less tuner. £2/18/6, P/P 10/. SOBELL/GEC 405/625 switchable IF amplifier and output chassis, 32/6, P/P 4/6. UHF tuners incl. valves, slow motion drive assy, knobs, aerial panel, £5/10/-, P/P 4/6. UHF list available on request. New or manufacturer tested VHF tuners, AT7650 Philips 19TG170. Sobell 1010. KB Featherlight 35/-. AT7639 Peto Scott, Decca. Ekco, Ferranti, Cossor 50/-. Cydon C 20/-. AB miniature with UHF injection incl. valves 78/6, Ekco 283/330, Ferranti 1001/6 25/-. New fireball tuners, Ferguson, HMV, Marconi type 37/6, Plessey 4 position push button tuners with UHF injection, incl. valves, 58/6. Many others available. P/P all tuners 4/6. Large selection channel coils. Surplus Eye, Ultra, Murphy, 110" scan coils 30/-. Sobell 110" Franke C/P transformers 17/6, P/P 4/6. Perdio "Portoram" LOFT assy incl. DY86, suitable for transistorised TV, 40/-. P/P 4/6. LOFTs, Scan Coils, FOFTs available for most popular makes. PYE/LABGEAR transistorised booster units B1/B3 or UHF, battery operated 75/-. UHF mains operated 97/6, post free. COD despatch available. **MANOR SUPPLIES**, 64 GOLDERS MANOR DRIVE, LONDON, N.W.11. CALLERS 589B HIGH ROAD, N FINCHLEY, N.12 (near GRANVILLE ROAD). Tel. 01-445 9118. [60]

**TEST EQUIPMENT — SURPLUS AND SECONDHAND**

**SIGNAL** generators, oscilloscopes, output meters, wave m. voltmeters, frequency meters, multi-range meters, etc., etc., in stock.—R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [64]

**RECEIVERS AND AMPLIFIERS—SURPLUS AND SECONDHAND**

**HERO** Rx5s, etc., AR88, CR100, BRT400, G209, S640, etc., etc., in stock.—R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [65]

**NEW GRAM AND SOUND EQUIPMENT**

**CONSULT** first our 76-page illustrated equipment catalogue on HI-FI (6/6). Advisory service, generous terms to members. Membership 7/6 p.a.—Audio Supply Association, 18 Blenheim Road, London, W.4. 01-995 1661. [27]

**GLASGOW**—Recorders bought, sold, exchanged; cameras, etc., exchanged for recorders or vice-versa.—Victor Morris, 343 Argyle St., Glasgow, C.2. [11]

**TAPE RECORDING ETC.**

**IF** quality, durability matter, consult Britain's oldest transfer service. Quality records from your suitable tapes. (Excellent tax-free fund raisers for schools, churches.) Modern studio facilities with Steinway Grand.—Sound News, 18 Blenheim Road, London, W.4. 01-995 1661. [28]

**YOUR TAPES TO DISC**—£6,000 Lathe. From 25/- Studio/Location Unit. S.A.E. Leaflet. Deroy Studios, High Bank, Hawk St., Carnforth, Lancs. [70]

**VALVES**

**VALVE** cartons by return at keen prices; send 1/- for all samples and list.—J. & A. Boxmakers, 75a Godwin St., Bradford, 1. [10]

**ARTICLES WANTED**

**VOLUNTARY** Rescue Services seek 2 VHF hand-portables, 1 mobile, 1 base station (minimum); GPO approved; limited budget. Write W. H. Jarvis, Rannoch School, via Rannoch Station, Perthshire. [371]

## DESIGN AND DEVELOPMENT ENGINEER

A progressive and interesting position is available at our factory in London, W.11, for an experienced circuit development engineer, with first class knowledge of Transistor Radio, both A.M. and F.M., duplex, transistor tape recorders.

Top salary according to experience and ability.

Please apply to: **Mr. J. Dickman, Managing Director, Fidelity Radio Ltd.**  
Olaf Street, London, W.11  
Telephone: 727 0131

374

## SENIOR ENGINEER

(Colour Television)

The Road Transport Industry Training Board operates at its Wembley Park headquarters one of the most modern closed circuit colour television studios in the country from which teaching and training programmes are produced on both film and video-tape.

An opportunity exists for an experienced engineer to join our small, enthusiastic team. He will be responsible to the Chief Engineer primarily for the operation and maintenance of the video-tape recording and telecine systems.

Applicants must be experienced in the latest systems of broadcast quality colour television. Knowledge of PAL Encoding systems and TR50 videotape equipment would be a distinct advantage. It is unlikely anyone under 24 years old will have sufficiently varied experience.

A salary will be negotiated in the region of £2250 depending on experience. Conditions of service include three weeks holiday, life assurance and a contributory pension scheme.

Please send relevant personal history, stating how the above requirements are met and quoting reference ZH.150, to:



**J. R. Barber,**  
Personnel Manager,  
RTITB, Capitol House,  
Empire Way, Wembley,  
Middlesex.

395

# ELECTRONICS EXPORT SALES ENGINEER Based on PARIS

**RAPIDLY EXPANDING FRENCH** electronics firm specialising in TV and F.M. translators and transmitters seeks mature export sales engineer

## CANDIDATES MUST

- speak and write absolutely perfect English
- like travelling. The work entails about 4 months a year away from Paris (throughout the world)
- be at least 28 years old
- have at least 3 years technical/commercial experience in our field
- be technically and intellectually sound
- be commercially dynamic

*Candidates are preferred who speak a little French and Spanish*

## THIS IS A RESPONSIBLE POSITION

Exactly the right man will be offered a salary of at least 30 000 Frs. (£2 500) per year

*Curriculum vitae in English, in writing, with photograph (which will be returned)*

**L.G.T., 4, rue de Garches 92 St-CLOUD • France • as soon as possible**

376

# ELECTRONIC ENGINEERS

Service Engineers required for Offices, throughout the United Kingdom, of well-known Company manufacturing Electronic Desk Calculating Machines. Applicants should possess a sound knowledge of basic Electronics with experience in Electronics, Radar, Radio and T.V. or similar field. Position is permanent and pensionable. Comprehensive training on full pay will be given to successful applicants. Please send full details of experience to the Service Manager, Sumlock Comptometer Ltd., 102/108 Clerkenwell Road, London, E.C.1.

82



## Norwich City College

Department of Electrical Engineering

### H.N.D. Course in Electrical and Electronic Engineering

The Department of Electrical Engineering of the Norwich City College offers students who have studied Physics and Mathematics at Advanced level in the GCE and passed in one subject (or have obtained a good ONC or OND in Engineering) a modern sandwich course for the Higher National Diploma in Electrical and Electronic Engineering. Subjects studied include Computation, Statistics, Economics and Law, Electronics, Control, Telecommunications, Power and Machines. Well balanced and interesting industrial training with pay will be arranged as required. The course is approved for major grant awards by Local Authorities.

Accommodation will be arranged by the College if desired.

*Enquiries about the course starting in September 1970 should be made to:*

**E. Jones, B.Sc., Ph.D., C.Eng., M.I.E.E.,**  
Head of Department of Electrical Engineering,  
Norwich City College,  
Ipswich Road, Norwich, Norfolk, NOR 67 D.

**WANTED**, all types of communications receivers and test equipment.—Details to R. T. & I. Electronics, Ltd. Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [63]

**WANTED**, televisions, tape recorders, radiograms, new valves, transistors, etc.—Stan Willetts, 37 High St., West Bromwich, Staffs. Tel. Wes. 0186. [72]

**WANTED**, PYE Link TX 450L, Eddystone EA12, EC10, Heathkit HW17, Beam Rotators, Prompt Cash, ALLSETS & Co. Ltd., 15 Burscough Street, Ormskirk. Tel.: 73005. [273]

### VALVES, WANTED

**WE** buy new valves, transistors and clean new components, large or small quantities, all details, quotation by return.—Walton's Wireless Stores, 55 Worcester St., Wolverhampton. [62]

### CAPACITY AVAILABLE

**AIRTRONICS, Ltd.**, for coil winding, assembly and wiring of electronic equipment; transistorised sub-unit sheet metal work.—3a Walerand Rd., London, S.E.13. Tel. 01-852 1706. [61]

**ELECTRONIC and Electrical Manufacture and Assembly**, Prototypes and short production runs. East Midlands Instrument Co. Ltd., Summergangs Lane, Gainsborough, Lincs. Tel. 3260. [88]

**METALWORK**, all types cabinets, chassis, racks, etc., to your own specification, capacity available for small milling and capstan work up to 1 1/2 bar.—PHILPOTT'S METALWORKS, Ltd., Chapman St., Loughborough. [17]

### TECHNICAL TRAINING

**BECOME "Technically Qualified"** in your spare time, guaranteed diploma and exam, home-study courses in radio, TV, servicing and maintenance. R.T.E.B., City & Guilds, etc., highly informative 120-page Guide—free.—Chambers College (Dept. 837K), College House, 29-31 Wrights Lane, Kensington, London, W.8. [16]

**CITY & GUILDS** (Electrical, etc.), on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, T.V., automation, etc.; send for 132-page handbook—free.—B.I.E.T. (Dept. 152K), Aldermaston Court, Aldermaston, Berks. [13]

**RADIO officers** see the world. Sea-going and shore appointments. Trainee vacancies during 1970. Grants available. Day and boarding students. Stamp for prospectus. Wireless College, Colwyn Bay. [80]

**TECHNICAL TRAINING IN Radio, TV and Electronics** through world-famous ICS. For details of proven home-study courses write: ICS, Dept. 443, Intertext House, London, S.W.8. [24]

**TV and radio A.M.I.E.R.E., City & Guilds, R.T.E.B.;** certs., etc., on satisfaction or refund of fee terms; thousands of passes; for full details of exams and home training courses (including practical equipment) in all branches of radio, TV, electronics, etc., write for 132-page handbook—free, please state subject.—British Institute of Engineering Technology (Dept. 150K), Aldermaston Court, Aldermaston, Berks. [15]

### TUITION

**ENGINEERS**—A Technical Certificate or qualification will bring you security and much better pay. Elem. and adv. private postal courses for C.Eng., A.M.I.E.R.E., A.M.S.E. (Mech. & Elec.), City & Guilds, A.M.I.M.I., A.I.O.B., and G.C.E. Exams. Diploma courses in all branches of Engineering—Mech., Elec., Auto, Electronics, Radio, Computers, Draughts, Building, etc.—For full details write for FREE 132-page guide: British Institute of Engineering Technology (Dept. 151K), Aldermaston Court, Aldermaston, Berks. [14]

**KINGSTON-UPON-HULL Education Committee**, College of Technology. Principal: E. Jones, M.Sc. F.R.I.C. **FULL-TIME** courses for P.M.G. certificates and the Radar Maintenance certificate.—Information from College of Technology, Queen's Gardens, Kingston-upon-Hull. [18]

**MERCHANT NAVY: Residential Radio Officer** Training.—R.M.S. Wray Castle, Ambleside, Westmorland. [311]

### BOOKS, INSTRUCTIONS, ETC.

**FOR SALE**—Wireless Journals, 1911-1940. Lambert, 60 Salhouse Road, Rackheath, Norwich. [366]

**MANUALS**, circuits of all British ex-W.D. 1939-45 wireless equipment and instruments from original R.E.M.E. instructions; s.a.e. for list, over 70 types.—W. H. Bailey, 167a Moffat Road, Thornton Heath, Surrey, CR4-8PZ. [66]

### BUSINESS OPPORTUNITIES

**GROUP OF YOUNG** qualified electronic engineers with development laboratory in London wish to undertake development projects of low to medium complexity. Box W.W. 348, Wireless World.

### FOR HIRE

**FOR HIRE** CCTV equipment, including cameras, monitors, video tape recorders and tape—any period.—Details from Zoom Television, Amersham 5001. [75]

# development engineer

For the programming, development and modification of automatic and airborne test equipment. Applicants should have knowledge and experience of electrical and electronic measurement, servomechanism tests, Manometric measurements and Gyroscopic equipment tests. In addition, familiarity with computer fundamentals and programming is required, and at least HNC or equivalent in a relevant subject.

Apply, giving brief details of education and experience to:

**Personnel Officer Engineering  
(General) (\*)  
BEA Engineering Base,  
Heathrow Airport—London,  
Hounslow, Middlesex**

414

## A NEW HI FI pulse rate F.M. TUNER M-70

- 14 SI TRANSISTORS, 4 SI DIODES
- TUNING METER
- DISTORTION—LESS THAN 0.5%
- SUITABLE FOR STEREO
- SIGNAL/NOISE—60db
- NOMINAL TUNING 88-108Mc/s
- NO COILS! NO ALIGNMENT!
- AUDIO O/P—300mV
- FREQUENCY RESPONSE 25c/s-15kc/s
- 3 STAGES OF LIMITING
- ULTRA HIGH SENSITIVITY
- POWER REQUIREMENTS 12V AT 25mA

11" by 5" printed circuit board for above tuner with fitted tuning tank, together with complete shopping list and assembly details for all components required:

**75/-** (approx. cost of remaining components—£6)

### \*A HIGH FIDELITY TUNER FOR ABOUT £10!

Printed circuit accommodates all components, you just insert each one—if you can read and use a soldering iron—45 mins.

The shopping list consists of two prepared orders which are sufficient for you to obtain all the components required.

If you are building a HI FI set up, an excellent tuner is a must; a tuner that will impress you as well as your friends. p. & p. 5/-

Mail Orders to: **DEPT. WW, MULTEL  
30 BAKER STREET • LONDON • W.1**

WW-126 FOR FURTHER DETAILS

## Electronics and Instrumentation

Robert L. Ramey.


The purpose of this book is to provide a sound groundwork for understanding the basis of existing instruments and their applications. It will prove a useful introduction to instrumentation for students of electronics and a single course in electronics and instrumentation for students in other branches of science and engineering.

**55s net** by post 57s 321 pp. 207 illustrations

obtainable from your bookseller or:
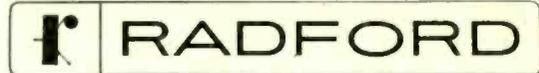
### THE BUTTERWORTH GROUP

Butterworths-Hiffes-Newnes  
**88 KINGSWAY LONDON W.C.2 01-405 6900**



## NEW POWER AMPLIFIERS

**MONO POWER AMPLIFIER PA50  
STEREO POWER AMPLIFIER SPA50**

The PA 50 is a transistor power amplifier having a power output in excess of 50 watts. The SPA 50 is a dual channel power amplifier having identical characteristics. The amplifier was designed basically for sound reproduction for professional use, but its exceptional characteristics in respect of distortion, transient response and power bandwidth make it also suitable for commercial and industrial uses.

The presentation is a low format of a depth suitable for shelf mounting. The amplifier is supplied in a metal housing suitable for fitting into a cabinet if required. The front facia is of extruded aluminium section with end pieces to form a complete frame. It is fitted with an anodised aluminium panel, screen printed.

The amplifier uses a true complementary symmetry output circuit with matched NPN and PNP transistors to obtain a virtually zero 'crossover' distortion. Improved circuitry has been developed to provide high gain in the output stages and drive circuits with wide bandwidth permitting a large amount of feedback to ensure an extremely low overall distortion. The success of the circuitry and the devices used is exhibited by the power bandwidth characteristic of 0.5 MHz at the -3 dB point.

The amplifier is unconditionally and absolutely stable with any form of output load of any impedance characteristic, from short-circuit to open-circuit. The amplifier itself is fully protected by current and voltage limiting and in addition is protected against the failure of a device in the power amplifier itself by a high speed current protection circuit in the power supply.

A new low distortion level of 0.01% has been reached for the amplifier at the -3 dB reference to the rated output, with the distortion proportionally decreasing with output power. Approximately 60 watts (continuous tone rating) is available at clipping level at 0.025% distortion both channels driven simultaneously.

Considerable attention has been given to reliability and ease of service. All components are to Mil specifications where possible. The amplifier is constructed in modules and all active circuits are on plug in type circuit boards. The contacts in the sockets and circuit boards are hard electro gold plated and the circuit boards themselves are immersion gold plated. Circuit board sockets are fitted to a printed circuit mother board thus eliminating wiring with its variations in performance and stability.

### SPECIFICATION

<b>Mains Input</b>	110 volts, 120 V, 130 V, 220 V, 230 V, 240 V, 50-60 Hz.
<b>Output Matching Impedance</b>	4-16 ohms (100 V line extra).
<b>Output Power</b>	50 Volt-amperes nominal. (Watts into an 8 ohm resistive load).
<b>Distortion</b>	0.025% at clipping onset. 0.01% at -3 dB ref: clip level.
<b>Input Facilities</b>	High impedance 22K ohms. Low impedance, optional 200/600 ohms balanced/unbalanced.
<b>Input Sensitivity</b>	High impedance, 1 Volt r.m.s. Low impedance, 0.5 Volt r.m.s.
<b>Functions</b>	Switched on front panel Mains on/off. Loudspeaker 1. Loudspeaker 2. Hi/Low Impedance input.

**Price: PA 50—£55 SPA 50—£85**

A complementary matching stereo pre-amplifier control unit SC 24 is also available price **£75**. Further details available upon request.

## Radford Audio Limited

Bristol BS3 2HZ, England

WW-126 FOR FURTHER DETAILS

# NEW FROM ILIFFE

## Colour Receiver Techniques

**T. D. TOWERS, M.B.E., M.A.(Camb.), M.A.(Glasgow),  
B.Sc., C.Eng., M.I.E.E., A.M.I.E.R.E., F.C.P.S.**

This book is based on 12 articles printed in 1967 in the "Wireless World" and is one of the first publications to give an account of current U.K. practice in the design of colour television receivers.

The style of this book is simple and clear, with a minimal use of mathematics, presenting a logical, easily assimilated guide to the complexities of colour television receivers, starting with a clear exposition of the characteristics of the U.K. PAL "swinging burst" signal.

The general plan of a colour receiver is discussed thoroughly before dealing with the designers of individual sections (including the aerial—treated as part of the receiver). After a chapter reviewing the sections in relation to a complete receiver, the book concludes with two essentially practical chapters on colour test equipment and servicing procedures.

### CONTENTS

The Colour Television signal	Elements of the Colour Television Receiver
The Colour Tube	Using a Three-coloured Pencil of Light
Colour Decoding "Matrix" Circuits	Replacing the Missing Colour Subcarrier
Sorting out the Colour Signals	D.C. Power Supplies
Aerials for Colour Television	Circuit Round-Up
Colour TV Test Equipment	"Setting-Up" a Colour TV Set

88 pp. 79 illustrations. **35s. net**, 36s. by post


obtainable from your bookseller:

**THE BUTTERWORTH GROUP**

Butterworths—Iliffes—Newnes

88 KINGSWAY LONDON WC2 01-405 6900

## SURPLUS BARGAINS (EX GOVT)

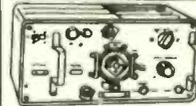

**AMPLIFIER RF No. 2 MK III.** Increases output of 19 set to 25 watts. Brand New. 12v operation. 75/-. Carr. 15/-. No. 19 Sets. £4.5.0. Carr. 17/6. All Ancillary Equipment Available. 12v D.C. Power Units 50/-. Carr. 10/-. 12/24v D.C. Power

Units with Vibrator Mk. II No. 2 70/- Carr. 10/-. **E.MIC SETS** Used 15/-. New 22/6. P & P 5/-. R.F. Antenna Tuner (ATU) 25/-. P & P 5/-.  
**FEW ONLY!**  
**No. 19 MK. III CANADIAN TRANSCEIVERS** Rebuilt as new. Complete station with all connectors, headset, variometer, control box and aerials. £22.10.0. Carr. 50/-.  
**B.41 RECEIVER LP** Version of B.40. Coverage 15 Kc/s-700Kc/s. Mains Operation. As received from Ministry. £8.10.0. Carr. 30/-. Tested working £15. Carr. 30/-.  
**R.209 MK II COMMUNICATION RECEIVERS.** 11 valve. Covers 1-20 Mc/s. 4 bands. AM/FM. CW. BFO. 12v D.C. Internal Power Supply. Tested. £13.10.0. Carr. 10/-.  
**TELESCOPIC MASTS.** 20ft. Closes to 5ft. 9in. 70/-. Carr. 15/-. 34ft. Ditto 80/-. Carr. 15/-.  
**35ft. AERIAL MASTS.** Seven 2in. dia. sections. Interlock 8in. Complete with Base, Nylon Guys. £12.10.0. Carr. 50/-.  
**TELEPHONE FIELD TELEPHONES.** Communication up to 10 miles. Tested with batteries. £5.15.0. pair. Carr. 20/-.  
**LIVINGSTONE LAB TRANSISTOR AMPLIFIER.** 50 watts R.M.S. Size 14in. x 9in. x 4in. With mains p.s.u. size 16in. x 9in. x 6in. 22 Gns. Carr. 20/-.  
**A.J. THOMPSON (Dept. W)**  
"Eiling Lodge," Codicote, Hitchin, Herts. Phone: Codicote 242  
C.W.O. Carriage charges apply to mainland only.

Units with Vibrator Mk. II No. 2 70/- Carr. 10/-. **E.MIC SETS** Used 15/-. New 22/6. P & P 5/-. R.F. Antenna Tuner (ATU) 25/-. P & P 5/-.  
**FEW ONLY!**  
**No. 19 MK. III CANADIAN TRANSCEIVERS** Rebuilt as new. Complete station with all connectors, headset, variometer, control box and aerials. £22.10.0. Carr. 50/-.  
**B.41 RECEIVER LP** Version of B.40. Coverage 15 Kc/s-700Kc/s. Mains Operation. As received from Ministry. £8.10.0. Carr. 30/-. Tested working £15. Carr. 30/-.  
**R.209 MK II COMMUNICATION RECEIVERS.** 11 valve. Covers 1-20 Mc/s. 4 bands. AM/FM. CW. BFO. 12v D.C. Internal Power Supply. Tested. £13.10.0. Carr. 10/-.  
**TELESCOPIC MASTS.** 20ft. Closes to 5ft. 9in. 70/-. Carr. 15/-. 34ft. Ditto 80/-. Carr. 15/-.  
**35ft. AERIAL MASTS.** Seven 2in. dia. sections. Interlock 8in. Complete with Base, Nylon Guys. £12.10.0. Carr. 50/-.  
**TELEPHONE FIELD TELEPHONES.** Communication up to 10 miles. Tested with batteries. £5.15.0. pair. Carr. 20/-.  
**LIVINGSTONE LAB TRANSISTOR AMPLIFIER.** 50 watts R.M.S. Size 14in. x 9in. x 4in. With mains p.s.u. size 16in. x 9in. x 6in. 22 Gns. Carr. 20/-.  
**A.J. THOMPSON (Dept. W)**  
"Eiling Lodge," Codicote, Hitchin, Herts. Phone: Codicote 242  
C.W.O. Carriage charges apply to mainland only.

Units with Vibrator Mk. II No. 2 70/- Carr. 10/-. **E.MIC SETS** Used 15/-. New 22/6. P & P 5/-. R.F. Antenna Tuner (ATU) 25/-. P & P 5/-.  
**FEW ONLY!**  
**No. 19 MK. III CANADIAN TRANSCEIVERS** Rebuilt as new. Complete station with all connectors, headset, variometer, control box and aerials. £22.10.0. Carr. 50/-.  
**B.41 RECEIVER LP** Version of B.40. Coverage 15 Kc/s-700Kc/s. Mains Operation. As received from Ministry. £8.10.0. Carr. 30/-. Tested working £15. Carr. 30/-.  
**R.209 MK II COMMUNICATION RECEIVERS.** 11 valve. Covers 1-20 Mc/s. 4 bands. AM/FM. CW. BFO. 12v D.C. Internal Power Supply. Tested. £13.10.0. Carr. 10/-.  
**TELESCOPIC MASTS.** 20ft. Closes to 5ft. 9in. 70/-. Carr. 15/-. 34ft. Ditto 80/-. Carr. 15/-.  
**35ft. AERIAL MASTS.** Seven 2in. dia. sections. Interlock 8in. Complete with Base, Nylon Guys. £12.10.0. Carr. 50/-.  
**TELEPHONE FIELD TELEPHONES.** Communication up to 10 miles. Tested with batteries. £5.15.0. pair. Carr. 20/-.  
**LIVINGSTONE LAB TRANSISTOR AMPLIFIER.** 50 watts R.M.S. Size 14in. x 9in. x 4in. With mains p.s.u. size 16in. x 9in. x 6in. 22 Gns. Carr. 20/-.  
**A.J. THOMPSON (Dept. W)**  
"Eiling Lodge," Codicote, Hitchin, Herts. Phone: Codicote 242  
C.W.O. Carriage charges apply to mainland only.

Units with Vibrator Mk. II No. 2 70/- Carr. 10/-. **E.MIC SETS** Used 15/-. New 22/6. P & P 5/-. R.F. Antenna Tuner (ATU) 25/-. P & P 5/-.  
**FEW ONLY!**  
**No. 19 MK. III CANADIAN TRANSCEIVERS** Rebuilt as new. Complete station with all connectors, headset, variometer, control box and aerials. £22.10.0. Carr. 50/-.  
**B.41 RECEIVER LP** Version of B.40. Coverage 15 Kc/s-700Kc/s. Mains Operation. As received from Ministry. £8.10.0. Carr. 30/-. Tested working £15. Carr. 30/-.  
**R.209 MK II COMMUNICATION RECEIVERS.** 11 valve. Covers 1-20 Mc/s. 4 bands. AM/FM. CW. BFO. 12v D.C. Internal Power Supply. Tested. £13.10.0. Carr. 10/-.  
**TELESCOPIC MASTS.** 20ft. Closes to 5ft. 9in. 70/-. Carr. 15/-. 34ft. Ditto 80/-. Carr. 15/-.  
**35ft. AERIAL MASTS.** Seven 2in. dia. sections. Interlock 8in. Complete with Base, Nylon Guys. £12.10.0. Carr. 50/-.  
**TELEPHONE FIELD TELEPHONES.** Communication up to 10 miles. Tested with batteries. £5.15.0. pair. Carr. 20/-.  
**LIVINGSTONE LAB TRANSISTOR AMPLIFIER.** 50 watts R.M.S. Size 14in. x 9in. x 4in. With mains p.s.u. size 16in. x 9in. x 6in. 22 Gns. Carr. 20/-.  
**A.J. THOMPSON (Dept. W)**  
"Eiling Lodge," Codicote, Hitchin, Herts. Phone: Codicote 242  
C.W.O. Carriage charges apply to mainland only.

## RCA Electronic Components

RCA Semiconductors from stock

Cat. & Price List by return  
Hams-free QSL cards &  
"Ham Tips" with every order.



**Hi-Fi 45w Amplifier Set**  
(Data Sheet 204 by Request)

2N2147 (2)	16/3 each	2N3241	6/9 each
40329	4/9	40248 (2)	3/-

**Miscellaneous Small Sig. AF. Transistors**

2N406	5/3	2N408	5/6
2N2813	5/6	2N2814	5/-
2N2953	5/-	2N217	6/3

**Miscellaneous Power AF. Transistors**


2N2869/		2N2870/	
2N301	15/9	2N301A	32/3
40022	8/3	40254	8/-
2N2147	16/3	2N2148	11/3
40612	6/6	40421	11/9

Many other types in stock. Make sure of your copy of "Ham Tips" & QSL card by ordering NOW!

**REL EQUIPMENT AND COMPONENTS LTD.**  
17 Hermitage Road, Hitchin, Herts.
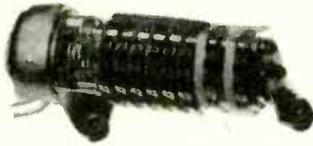
# P. F. RALFE

10 Chapel St London N.W.1  
Phone 01-723-8753



**LEDEX ROTARY SOLENOID SWITCHES** suitable for all types of remote circuit selection and a variety of switching operations—brand new stocks—no waiting—off the shelf deliveries of the following types.

- (1) Miniature type—1 pole 12 positions 3 banks wafer dia. 1 1/2 in., 3 position foot mounting. Operating voltage. 24 Volts D.C. .... 50/-
- (2) Miniature type—1 pole 7 position 5 banks 1 1/2 in. dia. wafers for flange mounting. Operating voltage. 12 Volts D.C. 37/6
- (3) Standard type—2 pole 6 way 13 bank. 48 Volts D.C. Operating voltage ..... 55/-
- (4) Standard type with 1 1/2 in. wafers, 2 pole 12 position 6 banks plus 2 pole 12 position 2 bank in ceramic insulation. 50/-
- (5) Standard type—1 pole 2 positions with long shaft to enable user to build up wafers to suit requirements. Voltage 48 Volts D.C. .... 40/-
- (6) Standard type wafers—1 pole 12 position 3 banks for 24 Volts flange mounting. .... 45/-

**TUBE BASES EIMAC SK 200A** for 4X250 transmitting valves. New. Boxed. With fixing clips. Price 42/6 ea.

**AMPHENOL AERIAL C/O RELAYS.** High quality type terminated to N Type connectors 75 ohms 48V DC coil. Brand new 50/- each.

**GEC QUARTZ CRYSTALS.** Type QA/328 600 KHz of recent manufacture. Brand new. Only 12/6 each.

**MINIATURE SEALED RELAYS STC TYPES**  
**4184GE.** 2 change over. Medium duty. 48 v. 2500Ω.  
**4184GD.** 2 change over. Medium duty. 24 v. 700Ω.  
**4184GB.** 2 change over. Medium duty. 6 v. 45Ω. All at 8/6 each. P. & P. 6d.

**MAGNETIC DEVICES LTD.** Mini relay 12 v. 590Ω. 2 pole change overs plus 2 makes and 2 breaks. Medium duty contacts. New. Boxed. Above relays 8/6 each. Post/packing 6d.

**LARGE QUANTITY OF 600 TYPE RELAYS** removed from equipment. Coil resistance 50Ω. 2 break contacts. 30/- per doz. Special price to clear the lot.

**HIGH SPEED RELAYS.** "Suitable for transistor circuits."  
 Plessey. Type mini sealed. 1 C/O contacts. 12 v. 3100Ω. Brand new. 15/- ea.  
 Siemens High Speed. Type H96E. Twin 1700Ω coils. 48 v. 15/-  
 Siemens High Speed. Type H96D. Twin 500Ω coils. 12 v. 15/-.

**PAXOLIN PC BOARD** contains 63 Lucas DD006 diodes. Rates at 400 P.I.V. 500 mA. New and unused. With long leads. Board size 8x4 ins. 30/- ea.

**LUCAS CAR RELAYS.** 12 v. Heavy duty make. Suitable for spotlights, horns, overdrives, etc. Brand new. Only 7/6. Special price for quantities.

**NICKEL-CADMIUM BATTERIES** D.E.A.C. manufacture RS 3-5 rating 3-5 Ah 1-24 v. Size as British U2, fully rechargeable. Offered BRAND NEW 19/6 each. P. & P. 1/6.

**"PERISTALTIC PUMPS" HR FLOW INDUCER TYPE MHRE 72 L WATSON MARLOW LTD.**  
 These very versatile pumps have facilities for two feed lines. The pumps are standard type but less variable speed control. Ideally suitable for highly corrosive liquids. Offered as new for A.C. mains operation, at the greatly reduced price of £24.10. Post/packing 10/-.

**R.F. ATTENUATORS TYPE A38**  
 These attenuators are contained in a screened cast case and are suitable for the audio to VHF range up to 300 Mc/s. Input level 0-5 watts max. Impedance 75 ohms. Attenuation 80 dB in steps of 20 dB. Weight: 9 oz. Panel mounting. List price £10. Special offer price 85/- post paid.

**VARIABLE R.F. ATTENUATORS.** By famous manufacturer 0-12 dB. In one OHM steps. 50 ohm impedance terminated to BNC connectors, also 0-120 dB in ten ohm steps, 50 ohm and 75 ohm types.

**LANGBOURNE DYNAMICS TYPE 4B**  
 Low Voltage/Highly Stabilised POWER SUPPLY UNIT  
 Variable between 3-30 v. D.C. at 1 A. Fully transistorised and current limiting offered. BRAND NEW at only £13.10 inclusive of P. & P.

**BURNDEPT RF PLUGS**  
 These difficult to obtain plugs suitable for the Londex aerial c/o relay and many other types of equipment are offered. New, ex. equipment at 4/6 each. P.P. 6d.

**DIRECT CURRENT AMPLIFIER**  
 Contains "Browh Converter", for continuous balance system and associated circuit. Complete less valves (5) Brand new ..... 50/- P.P. 4/6

**ALWAYS IN STOCK AT REASONABLE PRICES**  
 Communications Receivers. Audio Oscillators. AC and DC Calibration Equipment. Schomandle Frequency Meters. Counter Timers to 220 MHz. Oscilloscopes/Pulse generators. RF and AF generators. Digital Volt Meters AC and DC. DC Potentiometers/Thermo Couple Pots. Storage Oscilloscopes and many other items of test equipment. We may be able to help so phone 01-723-8753.



## SPECIAL OFFER

**"INSULATION TESTERS" TYPE No. II METROHM** by famous British manufacturer. All solid state. No handles to crank. Runs off 9 volt transistor battery. Simply press button for function. Range 0-1 to 25M ohms for insulation testing. Also 0-1 to 100 ohms for resistance and continuity checking. Clear, concise scale. Small size modern instrument, complete with carrying strap and protecting cover. Offered in good used condition with battery ready to work. For 250 volt pressure only. List Price £19.10.0. Our price £5.19.6 plus 4/6 post/packing.

**DIRECTIONAL COUPLERS FOR REFLECTOR POWER MEASUREMENT**  
 One of the major uses of a directional coupler is to obtain a sample of the R.F. Power in a transmission line and apply it to an indicator. We can supply couplers with a power handling capacity of up to 300 Watts, the response is flat over the 66-88 Mc/s, 156-184 Mc/s and 200-450 Mc/s bands. Two pick-up probes are mounted on the coupler, one giving incidence the other reflective power, the voltage developed is rectified and may be fed to a calibrated meter, C/W 50 ohm plugs. Price 60/- P. and P. 3/6.

**MINIATURE SIGNAL GENERATORS—A.T.E. MANUFACTURE**  
 \* Contains RF Attenuator Gold Plated Components  
 Specially designed for operators of VHF mobile equipment, these units are of very small size and are completely portable, the interior circuit and associated parts are gold plated and built to a very high standard. There are two models with attenuated output, CW and Modulation. Type MIP Range 215-270 Mc/s; Type MIG Range 45-92 Mc/s; both models are powered by U2 dry cell, directly calibrated and built into grey hammer tone alloy case, brand new. Our price is only £9.19.6, plus 5/6 post/packing for both models.

**HIGH VOLTAGE EHT INSULATION TESTERS. TELEX TYPE 115.**  
 Variable EHT output from 1 to 15 Kv. Leakage current 0 to 100 microamps. For A.C. operation. 110 to 250 volts. Cost over £70. Our price, in good used condition, £35.

**ADVANCE VOLT STAT CV500/31**  
 Input 162-276 v. A.C., 50—1 phase output 115 v. constant at 410 watt. Offered BRAND NEW at only £8. P. & P. 15/-.


**KLAXON HOOTER ALARMS**  
 240 v. A.C. These alarms produce an ear splitting noise which can be up to 250 yards. Good used condition. Only 75/- P.P. 4/6.

**ADVANCE D.C. SERIES**  
 Output 24 v. D.C. at 5 amps. Input 200-245 v. A.C. ± 15%. Fully smoothed and protected. BRAND NEW units at only £10 each

**SPECIAL OFFER AVO LTD. TRANSISTOR ANALYSER MODEL TA**  
 These extremely versatile instruments are offered in first-class and serviceable condition. Incorporates all facilities for transistor testing. List price £115. Only £40.

**A.E.I. MINIATURE UNISELECTOR SWITCHES**  
 No waiting, straight off the shelf and into your equipment the Catalogue Nos. are 2202A, 4/33A63/1; coil resistance is 250 ohms. Complete with base, and the price is £4.19.6. Limited quantity only available.

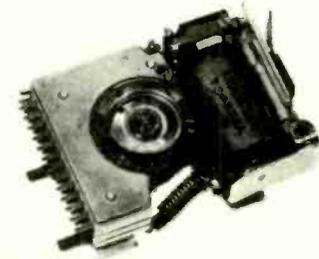**EDDYSTONE DIE-CAST BOXES**  
 Contains sensitive amplifier originally intended for amplification of P.E. cells. C/W input socket, fuse, signal lamp. P.S.U. (mains) amplifier, fully transistorised. Brand new 32/6. P. and P. 2/6.



**MARCONI STANDARD SIGNAL GENERATOR T.F.867**  
 Frequency range 15 kHz-30 MHz. output variable from 4 micro volts to 4 volts at 75 ohms. Built in crystal calibrator. Calibration accuracy 1%. Supplied like NEW GUARANTEED.

"One Micovac Valve Voltmeter for one-eighth of original price." Will measure 0-480 Volt A.C. at frequencies up to 200 Mc/s. 0-480 Volt D.C. with centre zero facilities 0-10 Megohms resistance in 5 ranges. This extremely accurate meter was made to Services specification and comes complete with R.F. Probe, full instructions in guaranteed working order. Battery powered (not supplied). Price is only £9.19.6, plus 10/6 P.P. Excellent condition. Completely portable.

**MARCONI AUDIO TESTER TYPE TF894**  
 This directly calibrated AF oscillator from 50c/s to 12kc/s has a maximum output of 300mW. into 600 ohm and is fitted with an output level meter and 600 ohm ladder attenuator of 0-50dB. An alternative 5,000 ohm outlet is provided and the level in each case is continuously variable. AF measurements: the voltmeter may be used for AF inputs (external) over the ranges of 0 to 80 v. in 4 ranges, providing a very useful facility. Supplied in excellent condition and working order for only £18.10. Power supply 240 v. A.C. (internal).

- HIGH QUALITY SIGNAL GENERATORS**
- \* Marconi TF867 Standard generator frequency range 15 kHz. to 30 MHz.
  - \* Marconi TF 144H/4 range 10 kHz to 72 MHz.
  - \* Marconi TF144g range 85 kHz to 25 MHz.
  - \* Marconi TF762C range 300 MHz to 600 MHz.
  - \* General Radio range 8 MHz to 330 MHz.
  - \* Hewlett Packard 616A 1-8 GHz to 4 GHz.
  - \* Rhode & Schwarz BN41022 300 MHz to 1 GHz.
  - \* Rhode & Schwarz BN41026 1 GHz to 1.9 GHz.
  - \* Rhode & Schwarz BN41042 1.7 GHz to 5 GHz.
- USA Pattern Modulated grid dip Meter built to rigid military specifications frequency range 2.5 MHz to 400 MHz. The Accurate calibration of this meter makes it ideal for use as signal generator and wave meter C/W. Small transit case all coils and leads for 115 v. A.C. operation. Price £18. P. & P. 10/6.

## LONDON CENTRAL RADIO STORES

**ELECTRICITY SLOT METER** (1/- in slot) for A.C. mains. Fixed tariff to your requirements. Suitable for hotels, etc. 200/250 v. 10 A. 80/-, 15 A. 90/-, 20 A. 100/-, P.P. 7/6. Other amperages available. Reconditioned as new, 2 years' guarantee.

**WIRELESS SET No. 38 A.F.V.** Freq. range 7.3 to 9.0 Mc/s. Working range 1/2 to 2 miles. Size 10 1/2 x 4 x 6 1/2 in. Weight 6 1/2 lb. Includes power supply 8 lb.—and spare valves and vibrator also tank aerial with base 28/- per pair or 24 single, P.P. 25/-.

**MODERN DESK PHONES**, red, green, blue or topaz, 2 tone grey or black, with internal bell and handset with 0-1 dia. 24/10/-, P.P. 7/6.

**10-WAY PRESS-BUTTON INTER-COM TELEPHONES** in Bakelite case with junction box handset. Thoroughly overhauled. Guaranteed. 28/10/- per unit.

**20-WAY PRESS-BUTTON INTER-COM TELEPHONES** in Bakelite case with junction box. Thoroughly overhauled. Guaranteed. 27/15/- per unit.

**TELEPHONE COILED HAND SET LEADS**, 3 core, 5/8. P.P. 1/-.

**QUARTERLY ELECTRIC CHECK METERS**. Reconditioned as new. 200/250 v. 10 A. 42/6; 15 A. 52/6; 20 A. 57/6. Other amperages available. 2 years' guarantee. P.P. 5/-.

**8-BANK UNISELECTOR SWITCHES**, 25 contacts, alternate wiping 22/15/-; 8 bank half wipe 22/15/-; 6 bank half wipe, 25 contacts 47/6. P.P. 3/6.

**FINAL END SELECTORS**. Relays, various callers, also 19 Receivers in stock. All for callers only.

23 LISLE ST. (GER 2969) LONDON W.C.2

Closed Thursday 1 p.m. Open all day Saturday

### BAILEY 30 WATT AMPLIFIER

10 Tr's as spec'd and Fibreglass Pcb	£6.7.6
20 Tr's as spec'd and 2 Fibreglass Pcb's	£12.10.0
BC125/126/40361 11/4	40362 15/6
MJ481 25/6	MJ491 28/-
RI-R27 (5% low noise) & P. 10/4 C1-C6 (Mullard) 7/6	
Mullard C431 2500mFd/64vw with clip	15/-
Ali H/Sink (Drilled 2 x TO3) 4 x 4 1/2 in	10/-

### LINSLEY HOOD CLASS A AMP

Set 10 C.F. R's 5/- Set 5 Capacitors 22/6  
 MJ480 (Matched for <0.1% T.H.D.) per pair 42/6  
 MJ481 (Matched for <0.1% T.H.D.) per pair 52/6  
 2N3906/2N4058/2N697/2N1613 4/6 BC109 3/6  
 Pair of H/Sinks as spec'd for Mono 5 x 4 in.  
 Lektrokrit Pinboard 4 x 4 1/2 in., pins & Layout 5/6  
 MJ480 16/6 Hunts KA112BT 2500mFd/50vw 12/6  
 1250mFd/40vw 9/- 250mFd/50vw 3/- 500mFd/50vw 5/9  
**A.I FACTORS, 72 BLAKE ROAD, STAPLEFORD, NQJTS.**

**TRANSFORMER LAMINATIONS** enormous range in Radiometal, Mumetal and H.C.R., also "C" & "E" cores. Case and Frame assemblies.

### MULTICORE CABLE IN STOCK CONNECTING WIRES

Large selection of stranded single p.v.c. covered Wire 7/0048, 7/0076, 14/0076 etc. P.T.F.E. covered Wire, and Silicon rubber covered wire, etc.

### J. Black

OFFICE: 44 GREEN LANE, HENDON, N.W.4  
 Tel: 01-203 1855. 01-203 3033  
 STORES: 30 BARRETT'S GROVE, N.16  
 Tel: 01-254 1981

## LAWSON BRAND NEW TELEVISION TUBES

- 12" Types £4.10.0
- 14" Types £4.19.0
- 17" Types £5.19.0
- 19" Types £6.19.0
- 21" Types £7.15.0
- 23" Types £9.10.0
- 19" Panorama £8.10.0
- 23" Panorama £11.10.0
- 19" Twin Panel £9.17.6
- 23" Twin Panel £12.10.0

Carriage and insurance  
 12"-19"—12/6  
 21"-23"—15/0

The continually increasing demand for tubes of the very highest performance and reliability is now being met by the new Lawson "Century 99" range of C.R.T.s. "Century 99" are absolutely brand new tubes throughout manufactured by Britain's largest C.R.T. manufacturers. They are guaranteed to give absolutely superb performance with needle sharp definition. Screens of the very latest type giving maximum Contrast and Light output; together with high reliability and very long life.

"Century 99" are a complete range of tubes in all sizes for all British sets manufactured 1947-1969. Complete fitting instructions are supplied with every tube.

2 YEARS FULL REPLACEMENT GUARANTEE  
 WW—130 FOR FURTHER DETAILS



### LAWSON TUBES

18 CHURCHDOWN ROAD  
 MALVERN, WORCS.  
 Tel. MAL 2100

## AKC

# K60

The new K60 Mono/  
Stereo Headset, retail  
price £13 10s

Good bass response,  
balanced middle  
response, brilliant high  
response.  
Frequency range  
16/20,000 Hz  
Utmost comfort with  
foam rubber ear pads  
Double Headbands  
Firm and solid  
construction

FOR FURTHER INFORMATION PLEASE WRITE TO AKG  
EQUIPMENT LTD., 182/184 CAMDEN HILL ROAD,  
LONDON, W.8 Telephone: 01-273 3695/6

**YUKAN SELF-SPRAY** SO PROFESSIONAL THE YUKAN AEROSOL WAY—

*Get these NOW!* air drying **GREY HAMMER** OR **BLACK WRINKLE (CRACKLE)** finishes

Yukan Aerosol spraykit contains 16 ozs. fine quality durable easy instant spray. No stove baking required. Hammers available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 15/6 at our counter or 16/6 carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Matt finish (12 ozs. self-spray cans only) 13/6 carriage paid.  
**SPECIAL OFFER:** 1 can plus optional transferable snap-on trigger handle (value 5/-) for 18/6 carriage paid. Choice of 13 self-spray plain colours and primer (floor car quality) also available. Please enclose cheque or crossed P.O. for total amount direct to:  
 Dept: YUKAN, 307A, EDGWARE ROAD, LONDON, W.2.  
 We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations—we can supply you too.  
 Closed ALL DECEMBER for annual holiday

## Quartz Crystal Units

**ECONOMICAL  
ACCURATE  
RELIABLE**

Private enquiries, send two 5d stamps for brochure  
**THE QUARTZ CRYSTAL CO. LTD**  
 Q.C.C. Works, Wellington Crescent,  
 New Malden, Surrey (01-942 0334 & 2988)  
**WW—132 FOR FURTHER DETAILS**

## BUILD YOURSELF A TRANSISTOR RADIO

**ROAMER EIGHT Mk 1 WITH TONE CONTROL SEVEN WAVEBANDS—MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND.** 8 transistors and 3 diodes. Ferrite rod aerial and telescopic aerial. Socket for car aerial. 7 x 4 in. Speaker. Airspaced ganged tuning condenser. Earpiece socket and earpiece. Selectivity switch. Size 9 x 7 x 4 in. Total Building Costs £6.18.6. P & P 7/6. Plans and Parts list 5/- (free with parts).

**POCKET FIVE, MED. AND LONG WAVES & TRAWLER BAND WITH SPEAKER AND EARPIECE.** 5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, moving coil speaker, etc. 5 1/2 x 1 1/2 x 3 1/2 in. Total Building Costs 44/8. P & P 3/8. Plans and Parts list 1/8 (free with parts).

**ROAMER SEVEN Mk 4, 7 WAVE-BANDS MW1, MW2, LW, SW1, SW2, SW3, AND TRAWLER BAND.** 7 transistors and 2 diodes. Ferrite rod aerial and telescopic aerial. Socket for car aerial. 7 x 4 in. speaker. Airspaced ganged tuning condenser etc. Size 9 x 7 x 4 in. Total Building Costs £5/19/6. P & P 7/6. Personal earpiece with switched socket for private listening 5/- extra. Plans and Parts list 3/- (free with parts).

**TRANSONA FIVE, MEDIUM, LONG AND TRAWLER BAND WITH SPEAKER AND EARPIECE.** 5 transistors and 2 diodes, ferrite rod aerial, moving coil speaker, 6 1/2 x 4 1/2 x 1 1/2 in. Total Building Costs 47/6. P & P 3/8. Plans and Parts list 1/8 (free with parts).

**TRANSEIGHT 6 WAVEBANDS, MW, LW, 3 SHORT WAVES AND TRAWLER BAND.** 8 Improved type transistors and 3 diodes. Ferrite rod and telescopic aerials. 3in speaker. Push pull output. Size 9 x 5 1/2 x 2 1/2 in. Total Building Costs 89/6. P & P 5/6. Plans and Parts list 5/- (free with kit). Personal earpiece with switched socket for private listening 5/- extra.

**RADIO EXCHANGE CO. LTD.**  
 Dept WW, 61 High Street, Bedford.  
 Phone 0234 52367  
 ● Open 10-1, 2.30-4.30, Sat. 9-12

# SPECIAL MONEY SAVING DISCOUNTS

on the Best Hi-Fidelity Equipment on the Market Today

AMPLIFIERS	Rec. Retail Price	Discount Price		Rec. Retail Price	Discount Price
ARENA F210 2x10 watts Stereo Amplifier teak case	£34 13 0	£29 10 0	KEF Concerto	£53 10 0	£45 0 0
ARMSTRONG 521 teak case	£52 0 0	£44 0 0	QUAD Electrostatic	£66 0 0	£59 10 0
PHILIPS RH580 stereo amplifier magnetic input	£26 0 0	£21 5 0	WHARFEDALE Denton per pair	£33 12 0	£29 10 0
DULCI 207 amplifier	£25 0 0	£17 0 0	WHARFEDALE Super Linton per pair	£42 0 0	£37 10 0
DULCI 207M as above but accepts magnetic cartridge	£30 0 0	£21 15 0	WHARFEDALE Dovedale III	£39 10 0	£32 19 6
GOODMANS Max amp teak or walnut	£54 0 0	£42 15 0	WHARFEDALE UNIT 3 Speaker Kit	£10 17 6	£9 5 0
LEAK Stereo 30 plus chassis model	£53 0 0	£43 10 0	<b>PLAYING DECKS</b>		
LEAK Stereo 30 plus teak case	£59 10 0	£48 12 6	GARRARD 401	£31 14 2	£27 0 0
LEAK Stereo 70 chassis model	£63 0 0	£50 15 0	GARRARD AP75	£23 16 7	£17 15 0
LEAK Stereo 70 plus teak case	£69 10 0	£55 15 0	GARRARD 8P25 Mark II	£15 11 11	£11 12 6
NIKKO TRM 40B	£46 10 0	£39 10 0	GARRARD SRP22	£6 12 10	£5 10 0
NIKKO TRM 120	£95 0 0	£84 10 0	GARRARD SL85B	£45 9 1	£37 10 0
ROGERS RAVENS-BOURNE teak case	£64 0 0	£54 10 0	GARRARD SL75	£35 12 5	£30 10 0
ROGERS RAVENS-BROOK chassis model	£44 0 0	£35 0 0	GARRARD SL85B	£19 0 5	£15 15 0
ROGERS RAVENS-BROOK in teak case	£46 10 0	£39 10 0	GARRARD SL55	£13 17 9	£11 12 6
SANSUI AU 222	£62 17 7	£56 10 0	GARRARD 60 Mark II	£17 5 10	£14 19 6
SANSUI AU 555	£80 9 7	£69 10 0	GARRARD 3500	£12 4 10	£10 19 6
TRUVOX TSA200 teak case	£54 12 0	£45 5 0	GARRARD 2025 T/C	£11 3 11	£10 10 0
METRO SOUND ST20 teak case 10 x 10 watts output	£32 0 0	£27 10 0	GARRARD 1025	£10 6 2	£9 10 0
QUAD 33 Control Unit and 303 Power Amplifier	£98 0 0	£82 10 0	GOLDRING L69	£25 1 6	£20 19 6
TELETON 203E	£28 7 6	£22 10 0	GOLDRING GL69P	£33 11 9	£28 10 0
<b>FM TUNERS</b>			GOLDRING GL75	£35 15 5	£28 15 0
ARENA F211 with Decoder	£39 18 0	£34 15 0	GOLDRING GL75P	£46 18 8	£37 10 8
DULCI FMT7 Mono tuner	£22 1 0	£18 10 0	THORENS TD150	£29 8 1	£26 10 0
DULCI FMT7S Stereo tuner	£29 8 0	£23 10 0	THORENS TD150A Mk II	£41 14 9	£35 0 0
GOODMANS Stereo max teak stereo tuner	£82 10 5	£70 10 0	THORENS TD150AB Mk II	£45 10 7	£39 10 0
LEAK Stereofetic chassis model	£56 11 0	£46 10 0	THORENS TD125	£63 4 9	£54 5 0
LEAK Stereofetic teak case	£64 14 0	£52 47 0	Plinth, tape and accessories of above available at 10% discount on retail price.		
QUAD Stereo Tuner	£51 0 0	£45 15 0	<b>STEREO CARTRIDGES</b>		
TRUVOX FM200 less Decoder	£37 12 11	£32 10 0	AUDIO TECHNICA AT66	£8 0 0	£5 10 0
ARMSTRONG 523 AM/FM teak case	£52 9 0	£44 17 6	SHURE M3DM	£7 8 3	£6 2 6
ARMSTRONG 524 FM teak case	£40 4 6	£34 17 6	SHURE 31E	£12 19 5	£11 10 0
<b>TUNER AMPLIFIERS</b>			SHURE 32E	£12 0 11	£10 15 0
ARENA T1500 teak only	£64 1 0	£57 10 0 (add 7 gns. for decoder)	SHURE 55E	£16 13 6	£13 19 0
ARMSTRONG 525	£87 16 9	£74 15 0	SHURE 44E	£14 16 6	£12 19 6
ARMSTRONG 526	£98 15 6	£85 10 0	SHURE M75E	£25 18 10	£23 5 0
GOODMANS 3000	£79 14 9	£67 10 0 (with decoder)	SHURE V13 Mk II	£40 15 3	£35 0 0
B & O Beomaster 1400 with decoder	£110 0 0	£97 10 0	GOLDRING C890	£5 4 0	£4 2 6
NIKKO FAM 12F	£68 8 3	£59 10 0	GOLDRING 800	£13 0 0	£8 10 0
NIKKO ST 701	£136 3 11	£120 0 0	GOLDRING 800E	£18 17 1	£15 10 0
SANSUI 350	£129 1 10	£114 10 0	<b>STEREO TAPE DECKS AND RECORDERS</b>		
SANSUI 2000	£162 3 0	£147 10 0	AKAI Model 4000D 3-head stereo tape deck		
SANYO DC60 2x30 watts rms	£99 0 0	£89 10 0 (with decoder)	AKAI X150E Stereo tape deck, crossfeed head	£130 0 0	£104 10 0
TELETON F2000 2x5 watts rms	£51 19 0	£43 10 0 (with decoder)	AIWA TP 1011 professional stereo 3 head tape deck	£184 6 0	£139 10 0
TELETON CR10T Tuner Amplifier AM/FM with decoder	£39 10 0	£34 10 0	SANYO MR910 4 track stereo tape recorder	£87 10 0	£74 10 0
TELETON MX990 Tuner Amplifier AM/FM with decoder, two speakers, 8" bass and 2" tweeter speakers in matching cabinets	£64 12 0	£49 10 0	SANYO MR929 4 track stereo tape recorder, 2 detachable speakers	£100 16 0	£89 10 0
<b>SPEAKERS</b> (Prices quoted for single speaker unless otherwise specified)			SANYO MR801 stereo tape deck	£70 0 0	£67 10 0
ARENA HT7	£19 19 0	£17 0 0	REVOX model 1104 4-track tape deck	£187 19 0	£169 10 0
ARENA HT10 teak or rosewood	£19 19 0	£17 10 0	AKAI 1710W 4-track stereo recorder	£100 0 0	£89 10 0
CELESTION Ditton 10	£21 13 1	£17 15 0	<b>MONAURAL MAINS TAPE RECORDERS</b>		
CELESTION Ditton 15	£31 3 7	£26 5 0	GRUNDIG TK120 continental twin-track tape recorder	£39 5 0	£29 10 0
GOODMANS Maxin	£20 15 6	£16 15 0	GRUNDIG TK144 4-track tape recorder	£47 13 1	£41 10 0
GOODMANS Marimba	£24 0 5	£19 15 0	GRUNDIG TK149 Automatic 4-track tape recorder	£55 18 10	£49 10 0
GOODMANS Mezzo II	£30 18 0	£25 10 0	PHILIPS 4307 4-track tape recorder	£48 11 0	£41 10 0
GOODMANS Maxium K	£40 2 0	£29 15 0	PHILIPS 4308 2-speed 4-track tape recorder	£60 0 10	£51 10 0
LEAK Sandwich	£43 10 0	£37 10 0	<b>COMPLETE HI-FI SYSTEMS</b>		
LEAK Mini Sandwich	£29 15 0	£25 5 0	RADON 404 SYSTEM Garrard 8P25, separate 2x8 watt amplifier, 2 bookshelf type speakers teak or blond oak	£57 4 0	£49 10 0
LOWTHER Accousta PM6	£45 10 0	£40 10 0	TOSHIBA SOPHIA Transcription turntable, magnetic cartridge, integrated tuner/amplifier, 2x12 watts rms, decoder, fitted hinged perspex top	£82 10 0	£75 0 0
LOWTHER Accousta PM7	£55 10 0	£50 10 0	SANYO DC584E Transcription turntable, magnetic cartridge, integrated tuner/amplifier, 2x12 watts rms, decoder, fitted hinged perspex top	£132 10 0	£119 10 0
KEF Cresta	£22 3 7	£18 10 0	Matching SANYO SX/X speakers per pair	£37 16 0	£32 10 0
KEF Celeste	£29 0 0	£25 0 0	<b>TRANSCRIPTION ARMS</b>		
KEF Concord	£43 10 0	£37 10 0	SME 3009 with shell	£31 6 3	£25 0 0
			SME 3012 with shell	£33 5 3	£27 0 0
			GOLDRING L75	£12 10 10	£10 0 0
			GOLDRING L69 arm	£9 5 9	£8 5 0

All goods are in manufacturer's sealed cartons and are insured against loss or damage in transit. Guaranteed "by return" service. Add 7/6 to all orders for p. & p. Send cash/cheque with order. Personal Callers Welcome—Business Hours.

**SMITH'S RADIO SERVICE (Wolverhampton) LTD.**  
Dept. W.W.1, 26 Victoria Street, Wolverhampton, Staffs. Tel: Wolv. 29246

## POWER ENGINEERING USING THYRISTORS

VOLUME 1

Techniques of Thyristor Power Control

30/- Mullard Postage 1/-  
**PRINCIPLES OF PULSE CODE MODULATION** by K. W. Cattermole. 95/- Postage 2/-.

**SIGNAL PROCESSING, MODULATION AND NOISE** by J. A. Betts. 42/- Postage 1/6.

**CLOSED CIRCUIT TV FOR ENGINEERS & TECHNICIANS** by Leonard C. Showalter. 50/- Postage 1/6.

**THE HI-FI AND TAPE RECORDER HANDBOOK** by Gordon J. King. 40/- Postage 2/6.

**UNDERSTANDING AND USING UNIUNCTION TRANSISTORS** by S. Hoberman. 24/- Postage 1/-.

**20 SOLID STATE PROJECTS FOR THE HOME** by R. M. Marston. 18/- Postage 1/-.

**MINIFLUX MANUAL** by Miniflux Electronics Ltd. 30/- Postage 1/6.

**THE SEMICONDUCTOR DATA BOOK** by Motorola. 60/- Postage 4/6.

**TRANSISTOR SWITCHING AND SEQUENTIAL CIRCUITS** by John J. Sparkes. 25/- Postage 1/-.

## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET, LONDON, W.2

Phone PADdington 4185

Closed Sat. 1 p.m.

WW-132 FOR FURTHER DETAILS

## Radar Scanner & Ind Units

Comprise Elliptical scanner with twin horn feed and tuning unit 8.2 to 12.4 K Mc/s. Rotation mount with bearing indicator, slip ring unit, azimuth control and levelling adjustments. Mounting frame with feet. Indicator unit with cables. These are for use on 12 v. D.C. The Ind uses transistors and sub. min. valves. Size of scanner 29" x 14" x 15" deep, overall size of unit on stand 5' high 3' 6" x 2' 6". The exact purpose of these units is not known, appear to be a 2 channel Rx with visual and aural indication. These would lend themselves to conversion to small radar set, supplied in good condition, made in France.

Price £45 plus £3 carr.

## Radio Telephone Units

Boot mounting type for remote control 80 to 100 Mc/s single channel, double conversion Rx with crystal filter, use 16 valves and 14 transistors as 2 Invertors size 11" x 6" x 18" for use on 12v. +Ea, made by Hudson. Supplied in good internal condition slightly soiled outer cases, less xtals.

Price £15 plus 10/- carr.

S.A.E. for lists.

## A. H. SUPPLIES

57 Main Road, Sheffield, S9 5HL

## "SPECIAL OFFER"

Ex LCC Ultra radios requiring attention to clear from £4-0-0, each, callers only. 10 watts output, provision for microphones. Suit small factory, hall, public address. Standard play Professional Scotch Boy 1 1/2 Polyester and Acetate recording tape. (Low noise). Used once only. Approx., 2,500 ft. 19/6. List Price £4-0-0.

**HARRINGAY PHOTOGRAPHIC LTD.**  
435 Green Lanes, London, N.4 • 01-340 5241

# TRAIN TODAY FOR TOMORROW

Start training TODAY for one of the many first-class posts open to technically qualified men in the Radio and Electronics industry. ICS provide specialized training courses in all branches of Radio, Television and Electronics—one of these courses will help YOU to get a higher paid job. Why not fill in the coupon below and find out how?

Courses include:

- RADIO/TV ENG. & SERVICING
- AUDIO FREQUENCY
- CLOSED CIRCUIT TV
- ELECTRONICS—
- ELECTRONIC MAINTENANCE
- INSTRUMENTATION AND CONTROL SYSTEMS
- NUMERICAL CONTROL ELECTRONICS
- COMPUTERS
- PRACTICAL RADIO (with kits)

Guaranteed Coaching for:

- C. & G. Telecom. Techns' Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/TV Servicing Cert.
- Radio Amateur's Examination
- P.M.G. Certs. in Radiotelegraphy
- General Certificate of Education



Start today the ICS way  
**INTERNATIONAL CORRESPONDENCE SCHOOLS**  
EST. 1891  
Dept. 230, Intertext House, Stewarts Rd., London, S.W.8.  
Please send FREE book on

Name .....

Address .....

470

**PRINTED CIRCUITS**  
PROTOTYPE AND BATCH PRODUCTIONS

Instrument panels and dials  
In Metal and Perspex

★ SCREEN PROCESS PRINTERS ★

**Brooklands Plating Co. Ltd.**  
Splice's Yard, South End, Croydon CR0 1BF 01-688-2128

**MARCONI RADAR TEST SET**  
8500-9680 Mc/s Type TF890A/4

Incorporating: KLYSTRON SIGNAL GENERATOR,  
THERMISTOR POWER MONITOR, SPECTRUM  
ANALYSER AND DIRECTIVE FEED ASSEMBLY.

Brand new, maker's guarantee.


**Offers: Tel. 021-454 8305**

**VACUUM**

OVENS, PUMPS, PLANT, GAUGES, FURNACES,  
ETC., GENERAL SCIENTIFIC EQUIPMENT  
EX-STOCK, RECORDERS, PYROMETERS, OVENS,  
R. F. HEATERS. FREE CATALOGUE.

**V. N. BARRETT & CO. LTD.**  
1 MAYO ROAD, CROYDON,  
CRO 2QP. 01-684 9917-8-9

## CAPACITOR DISCHARGE IGNITION SYSTEM

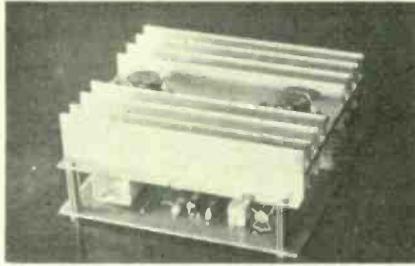

Using the article as published in the January 1970 issue of Wireless World, a universal printed-circuit board has been designed suitable for both positive and negative earth ignition systems. This also enables simple conversion to opposite polarity if the vehicle is subsequently changed. The printed-circuit board incorporates Cinch printed-circuit mounted screw terminal blocks for the input and output connections, together with a printed-circuit mounted fuse carrier with fuse. A complete complement of components and semiconductors are supplied together with a ready drilled and fluxed printed-circuit board, drilled heatsink, hardware and suitable transformer. Although wiring details are supplied for both positive and negative earth versions, customers must state which version they require so that the correct semiconductors can be supplied.

**Price £9-5-0 plus 10/- carriage.**  
**Trade Enquiries Invited.**  
**Mail Order Only.**

**DABAR ELECTRONIC PRODUCTS**  
98a, Lichfield Street,  
Walsall, Staffs.

**WW 133 FOR FURTHER DETAILS**



NITE-LITE Dimmerswitch will dim, up to 400 watts of incandescent lighting between zero and full brilliance. This unit simply replaces the normal light switch. It is supplied with MK mounting frame for use where more depth is required. 63/-

12v Fluorescent lights, attractive styling	69/11d
P.U. Cartridges GP91/3	18/-d
P.U. Cartridges GP93/1 stereo	25/-d
Potentiometers: 100ohms-5Mohms plain	1/9d
switched	2/8d
ganged	5/-d
Quadrac (insulated case Triac) 400v 4A	29/6d
SCRs untested 300v 1A T05 case	2/-d

**MU 914 INTEGRATED CIRCUITS PRICE 8/-**

Send S.A.E. for full lists of transistors and integrated circuits to:

**DIATHANE LTD.**  
111 Sheffield Road, Wymondham, Norfolk

## GEARED MOTORS

Microswitches, Timers, Meters,  
Potentiometers, Capacitors, all new

6d. stamp for catalogue.

**F. HOLFORD & CO.**  
6 IMPERIAL SQUARE, CHELTENHAM

## AMERICAN

TEST AND COMMUNICATIONS EQUIPMENT

★ GENERAL CATALOGUE AN/104 1/6 ★

Manuals offered for most U.S. equipments

**SUTTON ELECTRONICS**  
Salthouse, Nr. Holt, Norfolk. Cley 289



## ELECTRIC TIME SWITCH

MADE BY SIEMENS

Reconditioned, but perfect, 200/250 volts A.C. 10 amp. contacts. Once on/off every 24 hours. 45 min. minimum time lapse. In iron clad case with lid. Size 5" x 4 1/2" x 4 1/2". Weight 6 lb. Can also be supplied with solar dial if required. ON dusk, OFF at any manually pre-set time. 37/6 Post  
Extra trips 6/- per pair. 5/-

**HORSTMANN Clockwork TIME SWITCHES**  
15-day Jewelled Movement. Once ON/OFF every 24 hours at any manually pre-set times. One hour min. time lapse. Key and mounting bracket. Used but perfect, 39/6 Post  
guaranteed. 5 amp. 4/6

**VENNER TIME SWITCHES**  
200/250v. Reconditioned. Geared motor. I R.P.M. Removable cam. ON 15 secs. OFF 15 secs. 39/6 Post  
10 amp. contacts. In metal case. 4/6

**Box 365 KINGSWOOD SUPPLIES (W.W.23)**  
4 Sale Place, London, W.2. Tel.: 01-723 8189

**COMPONENT PARTS EX STOCK FOR FOLLOWING HI FI DESIGNS**


**BAILEY, LINSLEY-HOOD, TEXAS INSTRUMENTS**

For list of parts and other information send S.A.E. to:


**TELERADIO ELECTRONICS**  
325 FORE STREET, N.9 807 3719

THERE ARE GEMS IN IRELAND

This is one

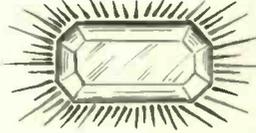

THIS is another

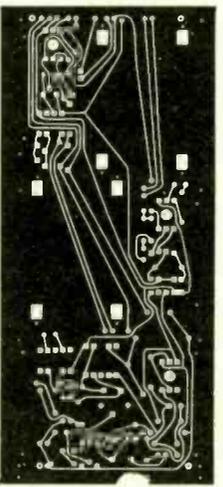

IF YOU WANT A REAL GEM CONTACT




**T ECLARE LTD**  
ENNIS, CO. CLARE. Phone: 21559

AFTER ALL, WE'RE IN THE EMERALD ISLE

WW-129 FOR FURTHER DETAILS

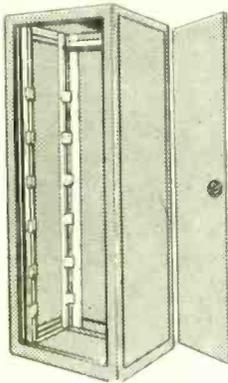**EXCLUSIVE OFFERS**  
**LATEST TYPE HIGHEST QUALITY**  
**CABINETS**  
**FOR STANDARD 19" RACK PANELS**  
**TOTALLY ENCLOSED**



**TYPE A:** 64" high x 24" deep x 24" wide.  
**TYPE B:** 78" high x 30" deep x 24" wide.  
**DOUBLE SIDED.** These cabinets will take rack panels both sides, that is back and front and are drilled and tapped all the way down every 1/2" for this purpose. They are fitted with "Instantit" patent fully adjustable rack mounts which are vertically and horizontally adjustable—these allow the panels to be recessed when they are fitted with projecting components and it is desired to enclose them by doors.

\*Other features include—all corners and edges rounded. Interior fittings tropicalised. Removable built in cable ducts. Removable built in blower ducts. Ventilated and insect proofed tops. Detachable side panels. Full length instantly detachable doors fitted expanding bolts if ordered with cabinets. Made in U.S.A.—cost the American Government £107 before devaluation. Finished in grey primer and in new condition.

**PRICE £26.10.0 each (Carriage extra)**  
 Full length door £5 each extra

Doors are not needed if panels are mounted back and front and they are not required to be enclosed.  
**TYPE C:** 60" high x 27" deep x 22" wide. American Standard First Grade totally enclosed ventilated 18" rack panel mounting cabinets, made by Dukane, U.S.A. Open front fitted rack mounts drilled and tapped all the way down every 1/2". Full length rear door with latch. Finished in grey these cabinets have been used but are in good condition but if decoration is of importance it is recommended they are re-sprayed before use.

**PRICE £15.0.0 each (Carriage extra)**

**TYPE D:** 76" high x 18" deep x 22" wide. These are slightly smaller and finished in black otherwise they are similar in construction and condition to Type C above. Made by B.C.A. of U.S.A.

**PRICE £12.10.0 each (Carriage extra)**

**TYPE E:** 68" high x 16" deep x 22" wide, totally enclosed ventilated rack mounting cabinets made by Motorola, U.S.A. These units have front and rear doors and rack mounts internally recessed within the cabinet. The rack mounts are standard 19" wide. The actual front panel height is 4" 10", the remaining 9" being fitted with removable glazed panel.

**PRICE £9.10.0 each (Carriage extra)**

**TRANSPORT:** We have made special economical transport arrangements for these cabinets to ensure they arrive undamaged and to avoid expensive crating.

**FREE**

40-page list of over 1,000 different items in stock available—keep one by you.

- ★ Ampex FR-100A Tape Recorder-Reproducers, six speeds 1 1/2"/16" to 60" per sec. on request
- ★ Ampex FR-1100 Tape Recorder-Reproducers, four speeds 3 1/2" to 60" per sec. on request
- ★ E.M.I. (U.S.A.) 1/4" Finest Quality Computer tapes suitable video work, 2400 ft. spooled and in transparent outer plastic case £4 0
- ★ 1" Tape Spools and Plastic Locking Cases 8 1/2" £1 0
- ★ 10 foot long 6" sides Triangular Lattice Steel Mast Sections with mating lugs for joining up to 200 feet. New condition. £27 0
- ★ Collins R-390 Communications Receivers 0.5/30.0 m/c £345 0
- ★ Hoffman CV-167 ISB/SSB Converters £225 0
- ★ E.M.I. Tape Recorders BTR-1 £175 0
- ★ Weston 24-D.B. Meter -10" x 6" £2 0
- ★ Redifon RA-10 ISB Adaptors £40 0
- ★ TT-4 Lightweight Teletypewriters £45 0
- ★ TT-63 Telegraph Repeaters £35 0
- ★ Candlestick microphones with push to talk switch £2 0
- ★ R.C.A. 5820 Imaer Orthicons £35 0
- ★ Lattice lightweight steel triangular Aerial Masts 12 to 16 inch sides up to 200 ft. high According to height

**WANTED 1/2" VIDEO TAPE**  
 Good price paid

- ★ I.C. Testers with pin boards £95 0
- ★ E.M.I. WM-3 Measuring Oculoscopes £32 10
- ★ 64 inch dia. Meteorological Balloons £1 10
- ★ 1" New Magnetic Recording Tape made by E.M.I. (USA) 3600 ft on N.A.B. Spools £5 10
- ★ 1" Used ditto "Scotch" Brand 4800 ft £4 0

**BARGAIN FOR THIS MONTHLY ONLY**

- E.E.8 Telephones, operate up to 17 miles on 2-UE batteries. Carriage paid £2 10 0 each
- ★ 8 Track Data High Speed Tape Readers £40 0
- ★ Mason Illuminated Drawing Tables 50" x 36" £17 10
- ★ Sielma Telegraph Distortion Monitors £25 0
- ★ Teletype Model 14 Tape Panchos £25 10
- ★ TS-497/URR Signal Generators 2/400 m/c £25 0
- ★ Sarah Trans/Receivers and Aerials £3 0
- ★ Preis Airport "Weather Man" Masts £25 0
- ★ Uniselectors 10 bank 25 way full wipe ex. new £21 15
- ★ Precision Main Filter Units new £1 10
- ★ Avo Gekler Counters new £7 10

We have a large quantity of "bits and pieces" we cannot list—please send us your requirements we can probably help—all enquiries answered.

**P. HARRIS**  
**ORGANFORD — DORSET**  
 BH16 6ER  
 WESTBOURNE 65051

**TAPE RECORDING YEAR BOOK**  
 COMPLETELY NEW NINTH EDITION  
 WITH COMPREHENSIVE CATALOGUE  
 SECTION AND ARTICLES BY EXPERTS  
**PRICE 10/6d. from**  
**7 ALVERSTONE AVENUE,**  
**EAST BARNET, HERTS.**

**DEIMOS LTD**  
**TAPE RECORDERS FOR**  
**RESEARCH, INDUSTRY AND**  
**PROFESSIONAL AUDIO**  
*single and multichannel*  
**8 CORWELL LANE, HILLINGDON, MDX.**  
 HAYes 3561

**SURPLUS HANDBOOKS**

- 19 set Circuit and Notes £7/- p/p 9d.
- 1155 set Circuit and Notes £7/- p/p 9d.
- H. R. O. Technical Instructions £6/- p/p 9d.
- 35 set Technical Instructions £6/- p/p 9d.
- 46 set Working Instructions £6/- p/p 9d.
- 88 set Technical Instructions £7/6 p/p 9d.
- BC.221 Circuit and Notes £6/- p/p 9d.
- Wavemeter Class D Tech. Inst. £6/- p/p 9d.
- 18 set Circuit and Notes £6/- p/p 9d.
- BC.1000 (31 set) Circuit and Notes £6/- p/p 9d.
- Clit. 100/B.28 Circuit and Notes £10/6 p/p 9d.
- R.107 Circuit and Notes £7/6 p/p 9d.
- A.R.88D Instruction Manual £18/6 p/p 10d.
- 62 set Circuit and Notes £7/- p/p 9d.
- Circuit Diagram 5/8 each post free. R.1116/A. R.1224/A. R.1355, R.P. 24, 26 and 28, A.1134, T.1154. CR.300, BC.312, BC.342, BC.343, BC.348 (E.M.P.), BC.624, 22 set.
- 52 set Sender and Receiver circuits 8/- post free.
- Colour Code Indicator 2/6, pp 6d.

S.A.E. with all enquiries please.  
 Postage rates apply to U.K. only.  
 Mail order only for

**INSTRUCTIONAL HANDBOOK SUPPLIES**  
 Dept. W.W. Talbot House, 28 Talbot Gardens, LEEDS 8

**OSMABET LTD.**

WE MAKE TRANSFORMERS AMONGST OTHER THINGS  
**AUTO TRANSFORMERS:** 0-110-200-220-240 v a.c. up or down, fully shrouded fitted terminal blocks. 30 w 26/6; 50 w 34/-; 75 w 41/6; 100 w 49/-; 150 w 60/-; 200 w 75/-; 300 w 97/6; 400 w 120/-; 600 w 142/6; 800 w 165/-; 1000 w 195/-; 1500 w 240/-; 2000 w 345/-; 3000 w 480/-; 7500 w 600/- and up to 8000 watt to order.

**MAINS TRANSFORMERS:** Prim 200/240 v a.c. TX1. 425-0-425 v 250 Ma. 6.3 v 4 a, CT. 6.3 v 4 a, CT. 0-5-6.3 v 3 a. 135/-; TX2. 250-0-250 v 150 Ma. 6.3 v 4 a, CT. 0-5-6.3 v 3 a. 78/6; TX3. 250-0-250 v 100 Ma. 6.3 v CT. 2 a, 6.3 v 1 a. 80/-; TX4 300-0-300 v 50 Ma. 6.3 v 2 a, CT. 6.3 v 1 a. 60/-; TX5 300-0-300 v 120 Ma. 6.3 v 2 a, CT. 6.3 v 1 a. 78/6; TX6 250-0-250 v 63 Ma. 6.3 v 1.5 a. 42/-; MT1 200 v 30 Ma. 6.3 v 1 a. 24/-; MT2 230 v 45 Ma. 6.3 v 1.5 a. 29/6.

**MULTIVOLT TRANSFORMERS:** Prim 200/240 v a.c. OMT/4/1 One tapped sec. 5-20-30-40-60 v giving 5-10-15-20-25-30-35-40-55-60, 10-0-10, 20-0-20, 30-0-30 v a.c. 1 amp. 45/-; ditto tran 2 amp OMT/4/2. 67/6; OMT5/1 One tapped sec. 40-50-60-80-90-100-110 v, giving 10-20-30-40-50-60-70-80-90-100-110, 10-0-10, 20-0-20, 30-0-30, 40-0-40, 50-0-50 v a.c. 1 amp. 67/6; OMT/4/3 one sec 40 v CT 3 amp. 67/6.

**DUOVOLT TRANSFORMERS:** Prim 200/240 v a.c. "D12V" Sec 1, 12 v 4 a. Sec 2, 12 v 4 a. 71/6; "D25V" Sec 1, 10-20-25 v 2 a, Sec 2, 10-20-25 v 2 a. 71/6.

**LT AUTO TRANSFORMERS:** Prim 200/240 v a.c. output 24 v a.c. 150 watt 90/-; 250 watt 135/-; for quartz iodine lamps.

**HEATER TRANSFORMERS:** Prim 200/240 v a.c. 6.3 v 1.5 a 16/6; 3 a 20/-; 6 a CT 34/-; 12 v 1.5 a 21/-; 3 a CT 34/-; 6 a CT 45/-; 18 v 1.5 a CT 26/6; 24 v 1.5 a CT 34/-; 3 a CT 58/6; 6 a 75/-; 8 a 112/6; 12 a 165/-.

**MIDGET RECTIFIER TRANSFORMERS:** For FW rectification, size 1 1/2 x 2 1/4 ins. Prim 200/240 v a.c. output PPT1 9-0-9 v 0.3 a; PPT2 12-0-12 v 0.25 a; PPT3 20-0-20 v 0.15 a, 21/- each. Size 2 x 2 1/4 ins. MT12V 12-0-12 v 1 a, MT20V 20-0-20 v 0.75 a, 22/6 each.

**OUTPUT TRANSFORMERS:** Mullard 5/10 UL 67/6; 7 watt stereo UL 60/-; 3 watt PPS 30/-; PP 11K/ 3-8-15 ohm 21/-; Multi ratio 17/10 watt 33/-; 30 watt (KT66 etc.) 3-15 ohm 78/6; 50 watt (KT88 etc.) 135/-; 100 watt 225/-; auto matching tran. 10 watt 3-8-15 ohm up or down 15/-.

**W.W. IGNITION CIRCUIT** tran to spec 150/- plus 4/6 p.p.  
**W.W. COLOUR TELE.** Choke L1, 60/-; Tran T1 57/6; Field O/P 60/-.  
**BULK TAPE ERASERS:** 200/250 v a.c. immediate erasure of any size spool of magnetic tape, new boxed 42/6 pp 3/.

**FLUORESCENT LOW VOLTAGE LIGHTING**

12 v d.c. fittings and transistor inverters.  
 Fitted perspex diffusers, 12 ins. 8 watt, 70/-; 21 ins. 13 watt, 95/-; lens diffuser, 18 ins. 15 watt, 70/-.  
 Transistor inverters for 40 watt or twin 20 watt tubes at 150/-, for single 20 watt tube 100/- plus postage. New and guaranteed.

**CONDENSERS:** Electrolytic, 1000 mfd 25 v, 4/6; 2500 mfd 50 v, 10/8; 6000 mfd 15 v, 5/-; 1500 mfd 150 v, 12/8; 80 mfd 450 v, 5/-; 100 x 200 mfd 350 v, 7/6; 60 x 100 mfd 450 v, 7/6.  
**LOUDSPEAKERS:** New boxed, famous makes, 25 watt 107/-; 35 watt 130/-; 60 watt 180/-; 60 watt 215/-; 100 watt 350/-; 13 x 8 ins. 40/-; 13 x 8 ins. fitted 2 tweeters and crossover 70/-.  
**LOUDSPEAKER.** Ex-equip. perfect Elac etc., 6 ins. 3 ohms, 10/- plus 3/- min. carriage.  
 Carriage extra on all orders.

S.A.E. ALL ENQUIRIES PLEASE. MAIL ORDER ONLY  
 46 KENILWORTH ROAD, EDGWARE, MIDDX.  
 HA8 8YG. Tel: 01-958 9314

**MACLEANS 6" FAN**  
 230 v AC 3 Amp. 2,800 rpm.  
 55/- pp 6/-.

**IMLOCK COLLAPSIBLE ALUMINIUM CHASSIS FRAMES**  
 Size 10 1/2" x 8 1/2" x 6 1/2".  
 20/- pp 3/-.

**AIR CONTROL INST. BLOWER MOTORS**  
 Single phase 200-250v AC 2,800 rpm.  
 Outlet size 2 1/2" x 1 1/2".  
 £3 15s. 0d. pp 7/6

**20-WAY 2-POLE P.O. TYPE JACK STRIPS**  
 10 1/2" x 3 1/2". 19'6 pp 3/6. Ex-equip.

**CLAUDE LYONS VOLTAGE STABILIZER**  
 Type TS-2—5440 Input 198-258v 47-65  
 Output 240± 0.25%v 12 Amp. 2.88KVA  
 Ex-equipment. Brand new condition.  
 £35 0s. 0d. plus £2 carriage.

**ANALEX POWER SUPPLIES**  
 Size 7" x 19" x 13". 230v AC Input.  
 Output 6v 5Amp x 2; 18v 7.5 Amp. DC  
 Fully Transistorised  
 Marginal adjustment on output  
 £35 0s. 0d plus £3 carriage.

**ANALEX POWER SUPPLY**  
 Size 13" x 19" x 5 1/2". 230 v AC Input.  
 36v 14A Output. Stabilized.  
 Ex. Equip. Fully Tested. New condition.  
 £27 0s. 0d. plus £2 10s. carriage.

**AUTOTRANSFORMER: MAJESTIC WINDINGS—3 ONLY**  
 Input 240v 50 cycle. Output 115v 4.2 KVA  
 In metal case size 10" x 8 1/2" x 11"  
 £17 10s. 0d. plus £2 carriage.

**TRANSFORMERS**  
 Input 230v  
 Output: 6.3v 8 Amp x 2; 6.3v 4Amp x 3.  
 Size 4 1/2" x 4 1/2" x 6" approx.  
 New condition tested.  
 £2 5s. 0d. pp 12/6d.  
 Input 230v. Output: 6.6v 122Amp  
 Size 6 1/2" x 7 1/2" x 9" including terminals  
 Brand new. £15 0s. 0d plus £2 carriage.

**DAVIS DIMMER TRANSFORMERS**  
 Manufactured by Ariel Davis Mfg., U.S.A.  
 Input: 230v AC 60 cycle  
 Maximum overall rating amps—26.  
 Variable outputs Type 1  
 6.5v x 3; 13v x 1; 26v x 2.  
 Type 2 as above but outputs  
 19.5v x 3; 13v x 1. Only 2 of each type  
 All outputs and inputs have resettable  
 circuit breakers. Ex-equipment but fully tested.  
 £17 10s. 0d. each £2 10s.0d. carriage  
 mainland only.  
 Size 21" x 10 1/2" x 8".

**GARRARD 2 TRACK TAPE DECKS**  
**MAG TYPE**  
 Solenoid operated 230v 50v Solenoid  
 Ideal for contin. tape players etc.  
 £7 10s. 0d. each. Brand new in manufacturers  
 cartons. pp 22/6d.

**STC SEALED RELAYS**  
 Double pole change over  
 48v 2500Ω ex-equipment  
 2/6d. each pp 1/6d.

**OMRON MIDGET POWER RELAY**  
 Type MK1 230v AC New 10/6d. each pp 1/6d.

**TELESCOPIC AERIALS CHROMED**  
 7" closed 28" extended. 6 section  
 Ball jointed base 4/6d. each pp 1/6d. New

**4 MULLARD DM160 INDICATORS**  
 Size approx. 1 1/2" x 1 1/2" x 1 1/2" in plastic holder;  
 green plastic cover ex-equipment  
 7/6d. complete pp 1/6d.

**VIBRASHOCK EQUIPMENT MOUNTS**  
 Made by delaney galley  
 Type 7002—R2 45—75lbs.  
 Size 2 1/8" x 2 1/8" x 2". 5/- each pp 1/-.

**POWER SUPPLIES MANUFACTURED BY POWER ELECTRONICS LTD**  
 20v 4.5 amp  
 10v 3A; 10v 300ma.  
 £15 0. 0. pp 30/-.

**AC INPUT 200-250v AC In;**  
 20v 4.5 Amp; 10v 3 Amp; 10v 300 MAMP.  
 £15 0. 0. pp 30/-.

**FIELD ELECTRIC LTD.**  
 3 SHENLEY ROAD, BOREHAMWOOD, HERTS.  
 Telephone Elstree 6009  
 ADJACENT ELSTREE MAINLINE STATION  
 CALLERS WELCOMED

High grade of stability of electric parameters  
Resistance and durability  
Long operational life

# Polish

electronic tubes for radio receiver sets  
electronic tubes for TV receiver sets  
and  
electronic components  
are offered by



## UNIVERSAL

Foreign Trade Enterprise  
Warszawa, Al. Jerozolimskie 44, Poland  
P.O. Box Warszawa 1 No. 370.  
Telex No. 81437

To persons interested we forward detailed information,  
catalogues and tenders.

### DIOTRAN SALES

P.O. BOX 5  
WARE, HERTS  
TEL. WARE 3442

S.C.R.'s 16AMP (unplated)  
100 PIV 1.24 25-99  
400 PIV 9/6 7/6  
14/- 12/-  
All tested perfect functional  
guaranteed.

100 up 6/-  
10/-  
We will also buy  
your surplus stock  
—Send us your  
lists.

OVER 2 MILLION SILICON ALLOY & GERM. TRANSISTORS AVAILABLE FOR IMMEDIATE DELIVERY.  
MANUFACTURERS END OF PRODUCTION SURPLUS.

TRANSISTORS Type and Construction	QTY. Price	QTY. Price	QTY. Price	QTY. Price
	100	500	1,000	10,000
A 1 Germ. A.F. PNP T0-1 = AC127, NKT773, AC157, ASY86	£3.10	£15	£25	£200
A 2 Germ. A.F. PNP T0-5 = ACY17-21, NK237-245	£1	£3	£5	£40
A 3 Germ. A.F. PNP T0-1 = AC128, NKT271, 2G381	£1.10	£4.10	£7.10	£60
A 4 Germ. R.F. PNP T0-1 = OC44-45, NKT72125, ASY54	£1.10	£4.10	£7.10	£60
A 5 Germ. R.F. PNP T0-5 = 2N1303, NKT164-7, 2G301-3	£3.10	£15	£25	£200
A 6 Germ. V.H.F. PNP T0-1 = AF116-7, KNT667, 2G417	15s.	£2.10	£4	£32
A 7 Assorted Germ. A.F.-R.F. PNP mixed cans, general purpose	£2	£7.10	£12.10	£100
A 8 Germ. A.F. 50-2 PNP = 2G371-89, ACY27-31, OC71-75	£2	£7.10	£12.10	£100
A 9 Sil. Alloy PNP T0-5 = 2S301-5, BCY17-29, BCY30-34	£2	£7.10	£12.10	£100
A10 Sil. Alloy PNP 50-2 = 2S321-325, OC200-205	£2	£7.10	£12.10	£100

A1 to A7 Guaranteed 80% Good usable Transistors ideal for low cost production work and experimental use.  
A8 to A10 are all perfect devices, factory tested, no open or short circuit Transistors in these lots.

1/- TESTED TRANSISTORS 1/- each  
ONE PRICE ONLY PNP, NPN, SILICON PLANAR 1/- EACH

BC108	2N696	2N1132	2N2220	2S733
BC109	2N697	2N1613	2N3707	2N3391
BFY50	2N706	2N1711	2N3711	T1544
BFY51	2N708	2N2904	2S102	2N2906
BFX84	2N929	2N2905	2S103	2N2907
BFX86	2N930	2N2924	2S104	2N2696
BFX88	2N1131	2N2926	2S732	

From Manufacturers' Over-runs—Unmarked

GERM. PNP AND NPN TRANSISTORS TESTED, UNMARKED SIM. TO—1/- EACH

AC125	ACY22	ACY36	NKT677	OC81
AC126	ACY27	NKT141	NKT713	OC82
AC127	ACY28	NKT142	NKT773	2G301
AC128	ACY29	NKT212	OC44	2G302
AC130	ACY30	NKT213	OC45	2G303
ACY19	ACY31	NKT214	OC71	2G308
ACY20	ACY34	NKT215	OC72	2G371
ACY21	ACY35	NKT271	OC75	2G374

TRANSISTOR EQVT. BOOK  
2,500 cross references of transistors—British, European, American and Japanese. A must for every transistor user. Exclusively distributed by DIOTRAN SALES. 15/- EACH.

Post and Packing costs are continually rising. Please add 1/- towards same. CASH WITH ORDER PLEASE.  
QUANTITY QUOTATIONS FOR ANY DEVICE LISTED BY RETURN.

TO-5 METAL CAN SILICON PLANAR TRANSISTORS. VERY HIGH QUALITY 99% good type. 2N697, BFY51, 2N1893, £8 per 500 pieces. £13/0/0 for 1,000 pieces.

HIGH QUALITY SILICON PLANAR DIODES. 5UB-MINIA-TURE DO-7 Glass Type, suitable replacements for OA200, OA202, BAY38, IS130, IS940, 200,000 to clear at £4 per 1,000 pieces. GUARANTEED 80% GOOD.

FULLY TESTED DEVICES AND QUALITY GUARANTEED—SURPLUS TO REQUIREMENTS

OA202 Silicon Diode. Fully Coded. 150 PIV 250mA Qty. Price £30 per 1,000 pieces. BY100 SIL. RECT'S 800 PIV 550 mA. 1-49 2/6 each; 50-99 2/3 each; 100-999 2/- each; 1,000 up 1/10 each. Fully Coded. 1st Qty.

Vast mixed lot of subminiature glass diodes. Comprising of Silicon, Germ. Point Contact and Gold Bonded types plus some Zeners. 500,000 available at Lowest of Low Price. 1,000 pieces £3.0.0. 5,000 pieces £13.10.0. 10,000 pieces £23.

OVERSEAS QUOTATIONS BY RETURN SHIPMENTS TO ANYWHERE IN THE WORLD AT COST

SEMICONDUCTORS FOR W.W. CAP.-DIS. IGNITION SYSTEM. Each

2N3525	..	..	15/-
2N3055	..	..	12/-
2N3702	..	..	3/-
2N3704	..	..	3/-
IN4001	..	..	1/6
IN4005	..	..	4/-

New and fully guaranteed. PLASTIC PNP SILICON TRANSISTORS. Manufacturer's seconds from 2N3702-3 family. Ideal cheap trans. for manufacturing etc. £8 500, £13.10 1,000 pieces.

PLASTIC NPN SILICON TRANSISTORS. Manufacturer's seconds from 2N3707-3711 family. Ideal cheap trans. for manufacturing etc. £7.10 500, £12.10 1,000 pieces.

TO-18 METAL CAN SILICON PLANAR TRANS. Very high quality 99% good. Type 2N706, BSY27. £8 per 500 pieces, £13 per 1,000 pieces.

TOP HAT SILICON RECTIFIERS. All good. No short or open circuit devices. Voltage range 25-400PIV, 750mA. £3 per 100, £12.10 per 500.

TEXAS 2G371 A/B Evt. OC71 Germ. Gen. Purpose Trans. Each

1-99	..	..	1/6
100-499	..	..	1/3
500-999	..	..	1/-
1000 up	..	..	9d.

All Brand New and Coded.

### Thanks to a bulk purchase we can offer BRAND NEW P.V.C. POLYESTER AND MYLAR RECORDING TAPES

Manufactured by the world-famous reputable British tape firm, our tapes are boxed in polythene and have fitted leaders, etc. Their quality is as good as any other on the market, in no way are the tapes faulty and are not to be confused with imported, used or sub-standard tapes. 24-hour despatch service. Should goods not meet with full approval, purchase price and postage will be refunded.

S.P.	3in.	160ft.	2/-	5in.	600ft.	6/-
	5 1/2in.	900ft.	8/-	7in.	1,200ft.	9/-
L.P.	3in.	225ft.	2/6	5in.	500ft.	8/6
	5 1/2in.	1,200ft.	10/-	7in.	1,800ft.	13/-
D.P.	3in.	350ft.	4/6	5in.	1,200ft.	12/-
	5 1/2in.	1,800ft.	16/-	7in.	2,400ft.	20/-

Postage on all orders 1/6

COMPACT TAPE CASSETTES AT HALF PRICE

60, 90, and 120 minutes playing time, in original plastic library boxes. MC 60 9/- each. MC 90 12/6 each. MC 120 18/3 each.

### STARMAN TAPES

28 LINKSCROFT AVENUE, ASHFORD, MIDDX. Ashford 53020

WW-136 FOR FURTHER DETAILS

### WANTED—

Redundant or Surplus stocks of Transformer materials (Laminations, C. cores, Copper wire, etc.), Electronic Components (Transistors, Diodes, etc.), P.V.C. Wires and Cables, Bakelite sheet, etc., etc.

Good prices paid

J. BLACK

44 Green Lane, Hendon, N.W.4  
Tel. 01-203 1855 and 3033

### WE BUY

any type of radio, television, and electronic equipment, components, meters, plugs and sockets, valves and transistors, cables, electrical appliances, copper wire, screws, nuts, etc. The larger the quantity the better. We pay Prompt Cash.

Broadfields & Mayco Disposals,  
21 Lodge Lane, London, N.12

RING 445 2713

445 0749

958 7624

### WE PURCHASE

COMPUTERS, TAPE READERS AND ANY SCIENTIFIC TEST EQUIPMENT. PLUGS AND SOCKETS, MOTORS, TRANSISTORS, RESISTORS, CAPACITORS, POTENTIAL Meters, RELAYS TRANSFORMERS, ETC.

ELECTRONIC BROKERS LTD.  
49 Pancras Road, London, N.W.1. 01-837 7781

### ENTHUSIASTS



for tape recording subscribe to the only Magazine devoted exclusively to the subject. 25/- (U.S.A.) \$3.75 yrly. incl. postage.


FREE SPECIMEN COPY ON REQUEST

7 ALVERSTONE AVENUE, EAST BARNET, HERTS.

### WANTED RELAYS

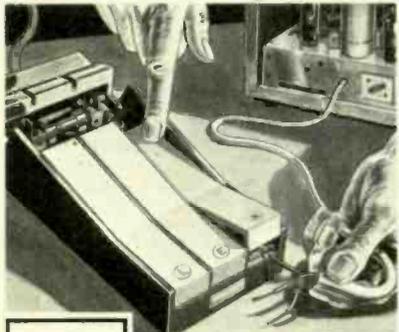1. GEC Sealed Type M1574, 12v, 180 ohms; 2. Ericsson or Plessey Tubular types: a. 48v, 1650 ohms, Ref. 12-0306; b. 48v, 1650 ohms, Ref. 12-0307; c. 24v, 440 ohms, Ref. 11-9145. 3. Plessey or Ericsson Plug-in type 24v, 670 ohms with transparent cover, exactly same size as GEC sealed type. 4. STC Type 4189GD 28v, 700 ohms.  
PHONE ANY TIME: 021-454 8305

**MAINS Keynector**  
 A REVOLUTIONARY NEW PRODUCT  
**cuts out plugs**




**It's the Newest, Safest and Quickest way to connect Electrical Equipment to the mains**

No plugs—no sockets—no risk of bare wires. To connect anything electrical, from an oscilloscope to an electric drill, simply open the fuse housing, depress the keys, insert the wires and close the housing. A neon light on the front of the Keynector glows to indicate proper connection. Multi-parallel connections can be made up to 13 amps. Keys are colour coded and lettered LEN for quick identification. Please send for further information.

issued by  
**E.B. INSTRUMENTS**  
 DIVISION OF ELECTRONIC BROKERS LTD  
 49-53 Pancras Road, London, N.W.1.  
 Telephone: 01-837 7781

the DESIGN CENTRE LONDON

**BAKER 12 in. MAJOR £8**




30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 14,500 Maxwells. Bass resonance 45 c.p.s. Rated 20 watts. Voice coils available 3 or 8 or 15 ohms. Price £8, Module kit, 30-17,000 c.p.s. Size 19x12 1/2 in. with tweeter, crossover, baffle and Instructions. Ideal for Hi Fi or P.A. Post Free **£10.19.6**

**LOUDSPEAKER CABINET WADDING**  
 18 in. wide, 2/6 per ft. run. Post 2/6 per order.

**ELECTRIC MOTORS**  
 (120v. or 240v. A.C.)  
 Clockwise 1,200 R.P.M. off load  
 Heavy duty 4 pole 50mA.  
 Spindle 1/2 x 3/20 in. diameter.  
 Size 2 1/2 x 2 1/2 x 1 1/2 in.  
**BARGAIN PRICE 17/6** Post 2/6

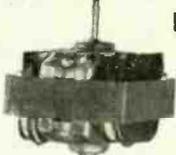**TRANSISTOR AMPLIFIER WITH LOUDSPEAKER**  
 A self-contained portable mini p.a. system. Many uses—Parties, Baby Alarm, Intercom, Telephone or Record Player Amplifier. Attractive resin covered cabinet size 12x9x4 in., with powerful 7 x 4 in. speaker and four transistor one watt power amplifier. Uses PP9 battery. Brand new in Maker's carton with full maker's guarantee.




All for only **75/-** Post 4/6

**THE INSTANT BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER**  
 200/250 A.C. Leaflet S.A.E. **42/6** Post 2/6



**EXTENSION SPEAKER**  
 Smart plastic cabinet speaker with 20ft. lead for transistor radio, Intercom, mains radio, tape recorder, etc. **30/-** Post 2/6  
 Size: 7 1/2 in. x 5 1/2 in. x 3 in.



**RETURN OF POST DESPATCH—CALLERS WELCOME HI-FI STOCKS—SALES—SERVICE—SPARES**  
**RADIO COMPONENT SPECIALISTS**  
 337 WHITEHORSE ROAD, CROYDON. Tel: 01-684-1665

**BAILEY PRE-AMPLIFIER**  
 High quality pre-amplifier circuit described by Dr. A. R. Bailey in the December, 1966, "Wireless World". This is a low distortion circuit of great versatility with a maximum output of 2 volts making it suitable for driving Bailey 20W and 30W Amplifiers, Linsley Hood Class A Amplifier and many others. All normal pre-amplifier facilities and controls are incorporated. A new Printed Circuit Board containing latest modifications 7in. by 3 1/2in. features edge connector mounting, roller tinned finish and silk screened component locations. This board is available in S.R.B.P. material or fibreglass and the complete Kit for the unit contains gain graded BC.109 transistors, polyester capacitors and metal oxide resistors where specified.

**BAILEY 30W AMPLIFIER**  
 All parts are now available for the 60-volt single supply rail version of this unit. We have also designed a new Printed Circuit intended for edge connector mounting. This has the component locations marked and is roller tinned for ease of assembly. Size is also smaller at 4 1/2 in. by 2 1/2 in. in SRBP material 11/6d. in Fibreglass 14/6d.


**BAILEY 20W AMPLIFIER**  
 All parts in stock for this Amplifier including specially designed Printed Circuit Boards for pre-amp and power amp. Mains Transformer for mono or stereo with bifilar wound secondary and special 218V primary for use with CZ6 Thermistor, 35/6d., post 5/-.  
 Trifilar wound Driver Transformer, 22/6d., post 1/-.  
 Power Amp. PC Board, 12/6d., post 9d.  
 Reprint of "Wireless World" articles, 5/6d. post free.

**DINSDALE 10W AMPLIFIER**  
 All parts still available for this design.  
 Reprint of articles 5/6d., post free.

**LINSLEY HOOD CLASS A AMPLIFIER**  
 Parts now available for this unit including special matt black anodised Metalwork and all power supply components.  
 PLEASE SEND S.A.E. FOR ALL LISTS.

**HART ELECTRONICS,**  
 321 Great Western St., Manchester 14  
 The firm for quality.  
 Personal callers welcome, but please note we are closed all day Saturday.

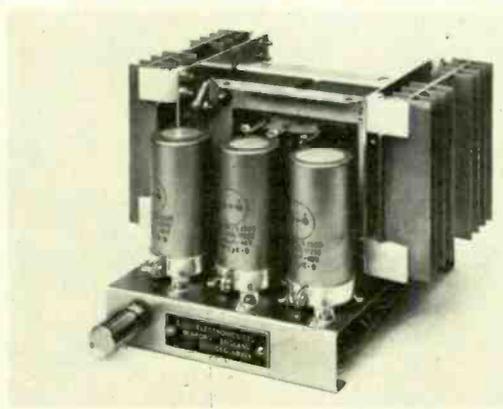**G & M POWER SUPPLIES FOR YOUR POWER NEEDS**



**THIS MODEL IS:**  
**CONVECTION COOLED 2 TO 15 VOLTS ADJUSTABLE**  
**3 AMPERES LIMIT LOAD REGULATION BETTER THAN 0.01%**  
**PRICE: £22**

**OTHER MODELS IN THIS RANGE:**

VOLTS	CURRENT	CHASSIS MODEL	ENCASED MODEL
0-15	3A	£25	£33
0-30	1.5A	£25	£33
2-15	3A	£22	£30
2-30	1.5A	£22	£30
8-15	3A	£20	—

**G & M ELECTRONICS LIMITED** . 46 Castle Road . Bedford . England  
 Telephone: Bedford 68219

# We can't wait to expand your laboratory

in 24 hours you can hire some of the World's top instruments at competitive prices

ring **LABHIRE** South: 06-285 23106 North: 061-928 0800

Southern Office: Station Approach, Bourne End, Bucks. Northern Office: Shearer House, Dunham Road, Altrincham, Cheshire.

## INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 117-132

A1 Factors.....	PAGE 136	Harnsworth Townley & Co.....	PAGE 37	Radford Audio Ltd.....	PAGE 133
A.H. Supplies.....	137	Harringay Photographic Ltd.....	137	Radio Masts Ltd.....	29
A.K.G. Equipment Ltd.....	136	Harris Electronics (London) Ltd.....	65	Radio & TV Components Ltd.....	111
A.N.T.E.X. Ltd.....	77	Harris, P.....	139	Radio Components Specialists.....	141
A.P.T. Electronics.....	44	Hart Electronics.....	141	Radio Exchange Co.....	136
Acoustical Mfg. Co., Ltd.....	7	Hatfield Instruments Ltd.....	65	Radiospares Ltd.....	109
Adcola Products, Ltd.....	Cover iii	Hayden Laboratories.....	74	Ralfie, P. F.....	135
Adler, B. & Sons (Radio) Ltd.....	36	Henry's Radio Ltd.....	88, 89	Rank Audio Visual Ltd.....	49, 56
Anders Electronics, Ltd.....	34, 40	Henson, R., Ltd.....	140	R.E.L. Equipment & Components Ltd.....	134
Associated Electronic Engineers, Ltd.....	57	Hi-Fi Dealers.....	138	R.S.C. Hi-Fi Centres Ltd.....	91
Ates Electronics Ltd.....	101	Holford, F., & Co.....	51	R.S.T. Valves.....	96
Audio Ltd.....	67	Home Radio (Components) Ltd.....	96, 138	Redifon Ltd.....	73
Audix, B. B., Ltd.....	47	I.C.S. Ltd.....	35	Reslo Mikes.....	18
Barnet Factors, Ltd.....	46	I.M.O. (Electronics) Ltd.....	40	Rola Celestion Ltd.....	65
Barrett, V. N.....	138	Impectron Ltd.....	39		
Batey, W., & Co.....	54	Industrial Exhibitions Ltd.....	139	Samsons (Electronics) Ltd.....	110
Bentley Acoustical Corporation Ltd.....	90	Instructional Handbook Supplies.....	33	Sansui Electric Co. Ltd.....	14
B.I.E.T.....	13	Jackson Bros. (London) Ltd.....	86	Service Trading Co.....	112, 113
Bi-Pak Semiconductors.....	102	K.S.M. Electronics.....	104	Servo & Electronic Sales Ltd.....	112
Bi-Pre-Pak, Ltd.....	108	Keytronics.....	138	Shure Electronics Ltd.....	43
Black, J.....	136, 140	Kingswood Supplies.....	92	Sinclair Radionics Ltd.....	83, 84, 85
Bosch Ltd.....	63	Kinver Electronics, Ltd.....	142	S.E. Laboratories (Eng.) Ltd.....	81
Bowthorpe Hellerman Ltd.....	16, 17, 53	Labhire Ltd.....	101	S.M.E. Ltd.....	41
Britec Ltd.....	60	Lasky's Radio Ltd.....	136	S.T.C. Mobile Radio Telephone.....	Cover ii
British Audio Promotions Ltd.....	52	Lawson Tubes.....	66	Smith, G. W. (Radio) Ltd.....	98, 99
Brookdeal Electronics Ltd.....	15	Ledon Instruments Ltd.....	55	Smith's Radio Service (W'ton).....	137
Brooklands Plating Co. Ltd.....	138	Level Electronics Ltd.....	66	Solartron Electronic Group Ltd.....	71, 80
Brown, N. C., Ltd.....	60	Light Soldering Developments Ltd.....	30	South Midlands Construction Ltd.....	57
Buckingham Press Ltd.....	106	Linear Products Ltd.....	58	Starman Tapes.....	140
Bulgin, A. F., & Co., Ltd.....	Edit. 199	Lodge Trading Co.....	66	Strumech Eng. Ltd.....	32
Burgess Products Co., Ltd.....	54	London Central Radio Stores.....	136	Sugden, J. E.....	60
Butterworth, & Co. (Pub.) Ltd.....	133, 134	L.S.T. Components.....	93	Sutton Electronics Ltd.....	138
		Lyons, Claude, Ltd.....	12		
C. & S. Antennas Ltd.....	50	Magnetic Tapes Ltd.....	86	Tape Recording Magazine.....	140
Carr Fastener Co. Ltd.....	75	Marshall, A., & Son (London) Ltd.....	97	Tape Recording Year Book.....	139
Carston Electronics Ltd.....	54	Mechanical Handling.....	64	TEAC Corp.....	59
Cesar Products Ltd. (Yukan).....	136	Millbank Electronics.....	38	Teclare Ltd.....	138
Chiltmead, Ltd.....	87	Mills, W.....	104, 105	Tektronix Ltd.....	23
Clubmans Club, The.....	Loose insert	Milward, G. F.....	100	Telequipment Ltd.....	68
Computer Training Products.....	56	Miniflux Electronics Ltd.....	101	Teleradio, The, (Edmonton) Ltd.....	138
Consumer Microcircuits Ltd.....	56	Modern Book Co.....	137	Teonex Ltd.....	8
Cossor Electronics Ltd.....	2	Morganite Resistors Ltd.....	6	Thompson, A. J.....	134
Counting Instruments Ltd.....	78	M.R. Supplies Ltd.....	52	Thorn Radio Valves & Tubes Ltd.....	76
		Motorola Semiconductors Ltd.....	79	Tinsley, H., & Co. Ltd.....	32
Dabar Electronic Prods.....	138	Mullard Ltd.....	28, 29, 70	Trio Corporation.....	42
Danavox (G.B.) Ltd.....	27	Messrs. Multel.....	133	Trio Instruments Ltd.....	52
Daystrom, Ltd.....	31	Multicore Solders Ltd.....	Cover iv	T.R.S. Radio Component Specialists.....	92
Deimos Ltd.....	139	McMurdo Instrument Co. Ltd.....	82	Turner, E., Electrical Insts.....	58
Diathane Ltd.....	138				
Diofran, Ltd.....	140	Nombrex Ltd.....	48	United-Carr Supplies Ltd.....	20
Dyhamco Ltd.....	78	O. & R. Electronics Ltd.....	66	Universal.....	140
		Omron Precision Controls.....	35	Valradio Ltd.....	40, 48
E.B. Instruments.....	141	Osmabet Ltd.....	139	Vortexion Ltd.....	10
Electrical Remote Control Co. Ltd.....	24	Oxley Developments, Ltd.....	92		
Electro-Tech Sales.....	109			Walker-Spencer Components.....	101
Electronic Brokers.....	94, 95, 140	Parker, A. B.....	66	Watts, Cecil E., Ltd.....	60
Electronics (Croydon) Ltd.....	103	Patrick & Kinnie.....	90	Wayne Kerr, The Co. Ltd.....	21
Electrosil Ltd.....	72	P.C. Radio Ltd.....	115	Webber, R. A., Ltd.....	66
Electrovalve.....	107	Peak Sound (Harrow) Ltd.....	106	Wel Components Ltd.....	86
Electro-Winds, Ltd.....	109	Pinnacle Electronics Ltd.....	25	Welwyn Tool Co.....	86
English Electric Valve Co. Ltd.....	3, 4, 5	Plessey Electronics Ltd.....	22	West Hyde Developments Ltd.....	62
Enthoven Solders Ltd.....	36	Plessey Microelectronics.....	1	West London Direct Supplies.....	101
Erie Electronics Ltd.....	9			Weyrad (Electronics) Ltd.....	110
		Quality Electronics Ltd.....	101	Wilkinsons, I. (Croydon) Ltd.....	102
Farnell Instruments Ltd.....	38	Quarndon Electronics Ltd.....	61		
Ferroglyph, The, Co. Ltd.....	19, 45	Quartz Crystal Co. Ltd.....	136	Z. & I. Aero Services Ltd.....	116
Field Electric Ltd.....	139				
Fylde Electronic Laboratories.....	58				
G. & M. Electronics Ltd.....	141				
Gardners Transformers Ltd.....	11				
Garrard Engineering Ltd.....	26				
General Video Systems Ltd.....	48				
Goldring Manufacturing Co. Ltd.....	44				
Gramplan Reproducers Ltd.....	30				
Greenwood, W. (London) Ltd.....	39				

# CLEARWAY to lower production costs with ADCOLA Precision Tools

For increased efficiency find out more about our extensive range of ADCOLA Soldering Equipment—and we provide:

★ THREE DAY REPAIR SERVICE ★ INTER-CHANGEABLE BITS—STOCK ITEMS ★ SPECIAL TEMPERATURES AVAILABLE • AT NO EXTRA COST.

ADCOLA TOOLS have been designed in co-operation with industry and developed to serve a wide range of applications. There is an ADCOLA Tool to meet your specific requirement. Find out more about our extensive range of efficient, robust soldering equipment.

◀ No. 107. GENERAL ASSEMBLY TYPE

*Fill in the coupon to get your copy of our latest brochure:*

**ADCOLA PRODUCTS LTD**

Adcola House · Gauden Road · London · SW4  
Tel. 01-622 0291/3 Grams: Soljoint, London SW4



*Please rush me a copy of your latest brochure:*

NAME .....


COMPANY .....

ADDRESS .....

WW

WW-002 FOR FURTHER DETAILS

# HIGH

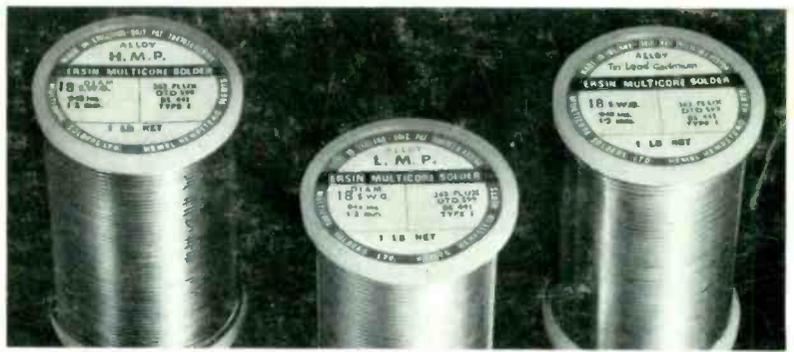

# & LOW

MELTING POINT SOLDERS FOR SOLDERING

- Gold plated surfaces
- Flexible printed circuits
- Silver plated surfaces
- High working temperature components

## H.M.P.

### HIGH MELTING POINT

For service at high temperature, or service at very low temperatures. Outstanding creep strength. Melting range 296°C - 301°C (565°F - 574°F).

#### Applications

A useful application of H.M.P. is the soldering of joints close to each other in such a way that the connections made first are not re-melted while later joints are made, with for example, a standard 60/40 alloy, melting point 188°C. Essential for use where high operating temperatures are experienced, for instance, electrical motors, car radiators, high temperature lamps. H.M.P. is also ideal for equipment, which is being operated in low temperatures, as it reduces the chance of the joint becoming brittle.

#### Specification

Multicore H.M.P. alloy complies with BS.219 Grade 5S. Supplied in a form of Ersin Multicore 5 core solder wire on 11b. or 71b. reels, incorporating Ersin 362 rosin based flux. This non-corrosive flux-cored solder wire complies with BS.441 and is available from 10 to 26 s.w.g., and in Multicore Solder Preforms. Ask for Technical Bulletin No. 1369.

## L.M.P.

### LOW MELTING POINT

A low melting point solder for soldering silver plated and gold plated surfaces. Melting point 179°C (354°F).

#### Applications

L.M.P. reduces the absorption of silver or gold into the solder alloy whilst soldering, and therefore, preserving the silver or gold plated surfaces. Also reduces the chance of a brittle joint being made.

#### NOTE

- a) The solution of gold into tin rises rapidly with temperature and so the use of L.M.P. Low Melting Point Solder is preferable.
- b) The solution rate of gold into tin is also reduced because L.M.P. is a ternary alloy comprising tin, lead and silver.

#### Specifications

L.M.P. is normally supplied in the form of Ersin Multicore 5 core solder wire, incorporating Ersin 362 rosin based flux, which complies with Min. Tech. specification D.T.D. 599A. It is available from 10 to 34 s.w.g. in 11b. or 71b. reels and Multicore Solder Preforms. Ask for Technical Bulletin 1469.

## T.L.C.

### EXTRA LOW MELTING POINT

Extra low melting point solder. Melting point 145°C (293°F).

#### Applications

T.L.C. alloy can be used whenever a soldered joint should be made with the minimum heat input. This would include heat sensitive transistors, flexible printed circuits and gold plated surfaces. The melting point of T.L.C. alloy is 38°C lower than any tin/lead alloy. Because of its low temperature application it is considered completely non-toxic in use unlike the high temperature cadmium-bearing brazing alloys.

#### Specification

T.L.C. alloy is normally supplied in the form of Ersin Multicore 5 core solder wire, incorporating Ersin 362 rosin based flux, which complies with Min. Tech. Specification D.T.D. 599A. T.L.C. alloy can also be supplied in the form of Multicore precision made solid solder wire, Extrusol extruded solid solder bars for solderbaths and Multicore Solder Preforms. Available from 10 to 34 s.w.g. on 11b. or 71b. reels. Ask for Technical Bulletin No. 1569.



See us on Stand 37  
at the International  
Electronic Components  
Exhibition Paris 3-8 April.

MULTICORE SOLDERS LTD.  
HEMEL HEMPSTEAD, HERTS.

PHONE:  
HEMEL HEMPSTEAD 3636  
TELEX: 82363



1914

1915

1916

1917

1918

1919

1920

1921

1922

1923

1924

1925

1926

1927

