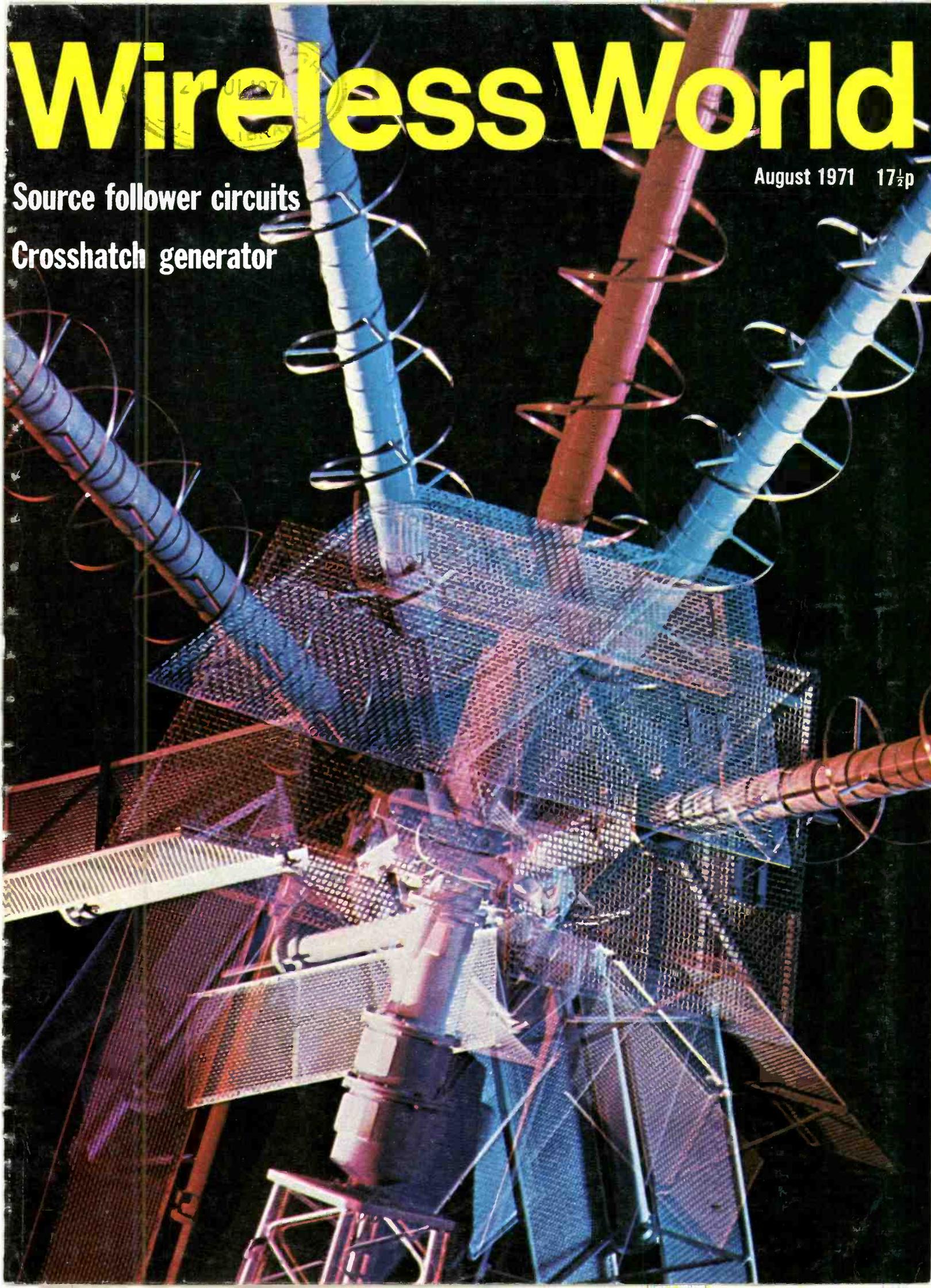


# Wireless World

August 1971 17½p

Source follower circuits

Crosshatch generator



# To keep them in touch.

**Chauffeurs. Drivers of taxis, ambulances, lorries and tankers. Firemen and policemen. Builders. Dockers. Doctors and nurses.**

ITT's Star range of vehicle and pocket radiotelephones. For people on the move who need to communicate.


Star mobile radiotelephone. For faultless, fade-free communication in vehicles. Wherever you are, however fast you're travelling. It has excellent range and signal

penetration in built-up areas. Its noise cancelling microphone gives crystal clear speech reception whatever background noise there might be.

Then there's Starphone, ITT's truly pocket-sized radiotelephone, with no external aerial rod or wires. Yet despite its diminutive size Starphone gives amazingly clear communication over a wide area. There's a version approved by the Ministry of Technology for safe use wherever a fire hazard exists.


There's also the Briefcase Portable, a complete communication system in a briefcase. Installed and operational in seconds.

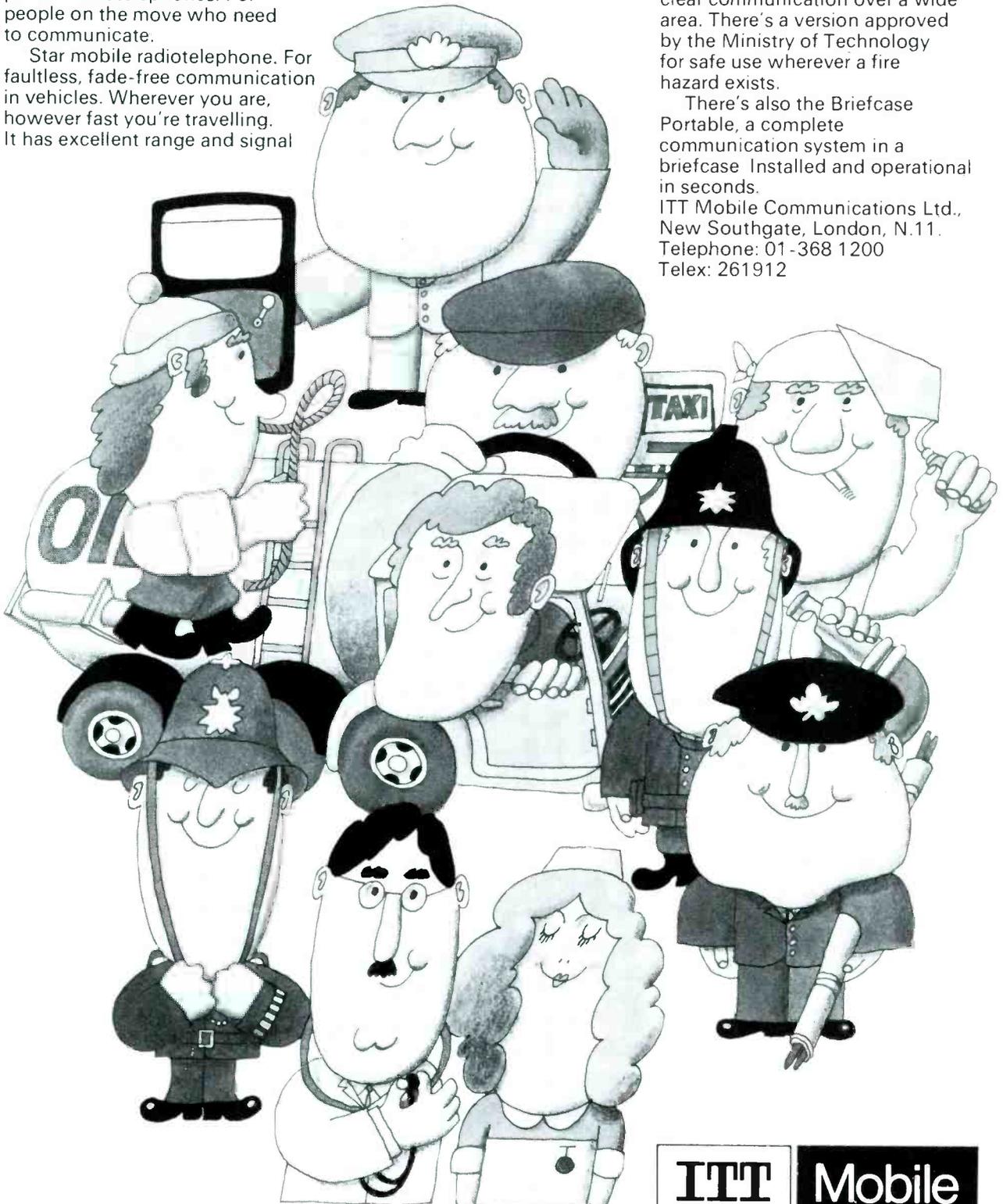ITT Mobile Communications Ltd.,  
New Southgate, London, N.11.  
Telephone: 01-368 1200  
Telex: 261912



**ITT**

**Mobile**

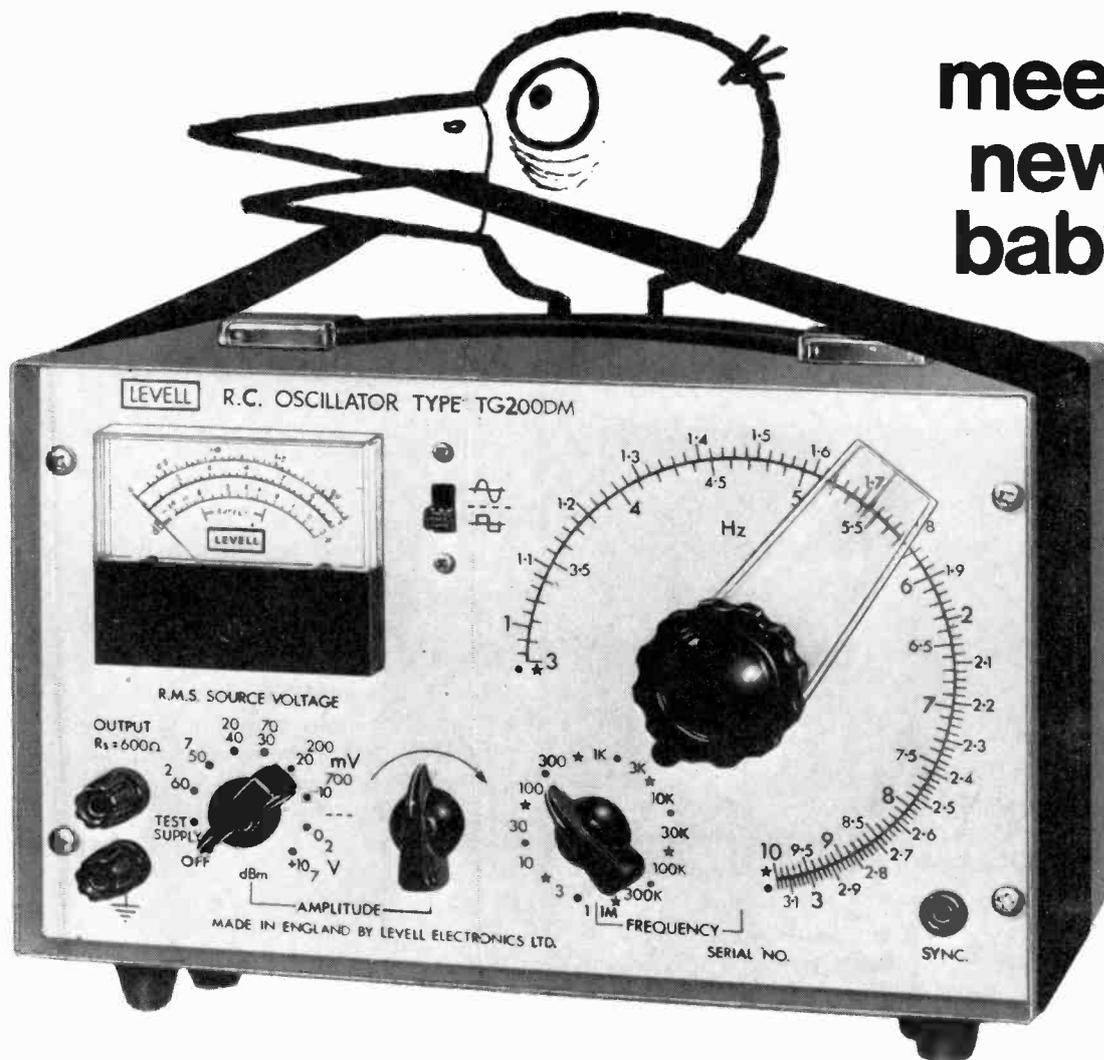

meet our  
new  
baby

## 7V r.m.s. Sine or Square from 1Hz to 1MHz

<b>FREQUENCY:</b>	1 Hz to 1MHz in 12 ranges. Accuracy $\pm 2\% \pm 0.03$ Hz.
<b>SINE WAVE OUTPUT:</b>	7V r.m.s. reducible to $< 200\mu\text{V}$ with $R_s = 600\Omega$ at all levels.
<b>DISTORTION:</b>	$< 0.1\%$ up to 5V output, $< 0.2\%$ at 7V from 10Hz to 100kHz.
<b>AMPLITUDE STABILITY:</b>	$< \pm 1\%$ variation with frequency up to 300kHz.
<b>SQUARE WAVE OUTPUT:</b>	7V peak reducible to $< 200\mu\text{V}$ . Rise time $< 150\text{nS}$ .
<b>SYNC. OUTPUT:</b>	$> 1\text{V}$ r.m.s. sine wave in phase with the main output.
<b>SYNC. INPUT:</b>	$\pm 1\%$ frequency lock range per volt r.m.s. input.
<b>SIZE &amp; WEIGHT:</b>	7" high $\times 10\frac{1}{4}$ " wide $\times 5\frac{1}{2}$ " deep. 10 lbs.

Types TG200 and TG200M generate only sine waves. Types TG200M and TG200DM have a meter calibrated 0/2V, 0/7V and  $-14/+6\text{dBm}$ . Types TG200 and TG200D have a calibrated control instead of a meter.

type **£42** type **£45** type **£52** type **£55**  
TG200 TG200D TG200M TG200DM

Prices include batteries with 400 hour life. Mains power units are £10 extra.



# LEVELL

PORTABLE INSTRUMENTS

# R.C. OSCILLATORS

LEVELL Electronics Ltd · Park Road · High Barnet · Herts. · Tel: 01-449 5028

Send for literature covering our full range of portable instruments.


WW-006 FOR FURTHER DETAILS

# Vortexion
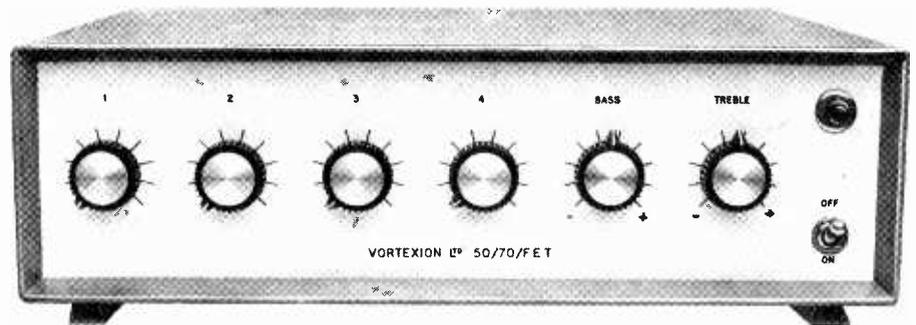
## 50/70 WATT ALL SILICON AMPLIFIER WITH BUILT-IN 4-WAY MIXER USING F.E.T.s.

This is a high fidelity amplifier (0.3% intermodulation distortion) using the circuit of our 100% reliable 100 Watt Amplifier with its elaborate protection against short and overload, etc. To this is allied our latest development of F.E.T. Mixer Amplifier, again fully protected against overload and completely free from radio breakthrough.

The mixer is arranged for 2-30/60 $\Omega$  balanced line microphones, 1-HiZ gram input and 1-auxiliary input followed by bass and treble controls. 100 volt balanced line output or 5/15 $\Omega$  and 100 volt line.



## 50/70 WATT ALL SILICON AMPLIFIER WITH BUILT-IN 5-WAY MIXER USING F.E.T.s

This is similar to the 4-way version but with 5 inputs and bass cut controls on each of the three low impedance balanced line microphone stages, and a high impedance (10 meg) gram stage with bass and treble controls plus the usual line or tape input. All the input stages are protected against overload by back to back low noise, low intermodulation distortion and freedom from radio breakthrough. A voltage stabilised supply is used for the pre-amplifiers making it independent of mains supply fluctuations and another stabilised supply for the driver stages is arranged to cut off when the output is overloaded or over temperature. The output is 75% efficient and 100V balanced line or 8-16 $\Omega$  output are selected by means of a rear panel switch which has a locking plate indicating the output impedance selected.

**100 WATT ALL SILICON AMPLIFIER.** A high quality amplifier with 8 ohms-15 ohms or 100 volt line output for A.C. Mains. Protection is given for short and open circuit output over driving and over temperature. Input 0.4 V on 100K ohms.

**THE 100 WATT MIXER AMPLIFIER** with specification as above is here combined with a 4 channel F.E.T. mixer, 2-30/60 $\Omega$  balanced microphone inputs, 1-HiZ gram input and 1-auxiliary input with tone controls and mounted in a standard robust stove enamelled steel case. A stabilised voltage supply feeds the tone controls and pre amps, compensating for a mains voltage drop of over 25% and the output transistor biasing compensates for a wide range of voltage and temperature. Also available in rack panel form.

**CP50 AMPLIFIER.** An all silicon transistor 50 watt amplifier for mains and 12 volt battery operation, charging its own battery and automatically going to battery if mains fail. Protected inputs, and overload and short circuit protected outputs for 8 ohms-15 ohms and 100 volt line. Bass and treble controls fitted. Models available with 1 gram and 2 low mic. inputs, 1 gram and 3 low mic. inputs or 4 low mic. inputs.

**200 WATT AMPLIFIER.** Can deliver its full audio power at any frequency in the range of 30 c/s-20 Kc/s  $\pm$  1 dB. Less than 0.2% distortion at 1 Kc/s. Can be used to drive mechanical devices for which power is over 120 watt on continuous sine wave. Input 1 mW 600 ohms. Output 100-120 V or 200-240 V. Additional matching transformers for other impedances are available.


**20/30 WATT MIXER AMPLIFIER.** High fidelity all silicon model with F.E.T. input stages to reduce intermodulation distortion to a fraction of normal transistor input circuits. The response is level 20 to 20,000 cps within 2 dB and over 30 times damping factor. At 20 watts output there is less than 0.2% intermodulation even over the microphone stage at full gain with the treble and bass controls set level. Standard model 1-low mic. balanced and 1 auxiliary input.

**VORTEXION LIMITED, 257-263 The Broadway, Wimbledon, S.W.19**

Telephone: 01-542 2814 and 01-542 6242/3/4

Telegrams: "Vortexion, London S.W.19"

WW-007 FOR FURTHER DETAILS

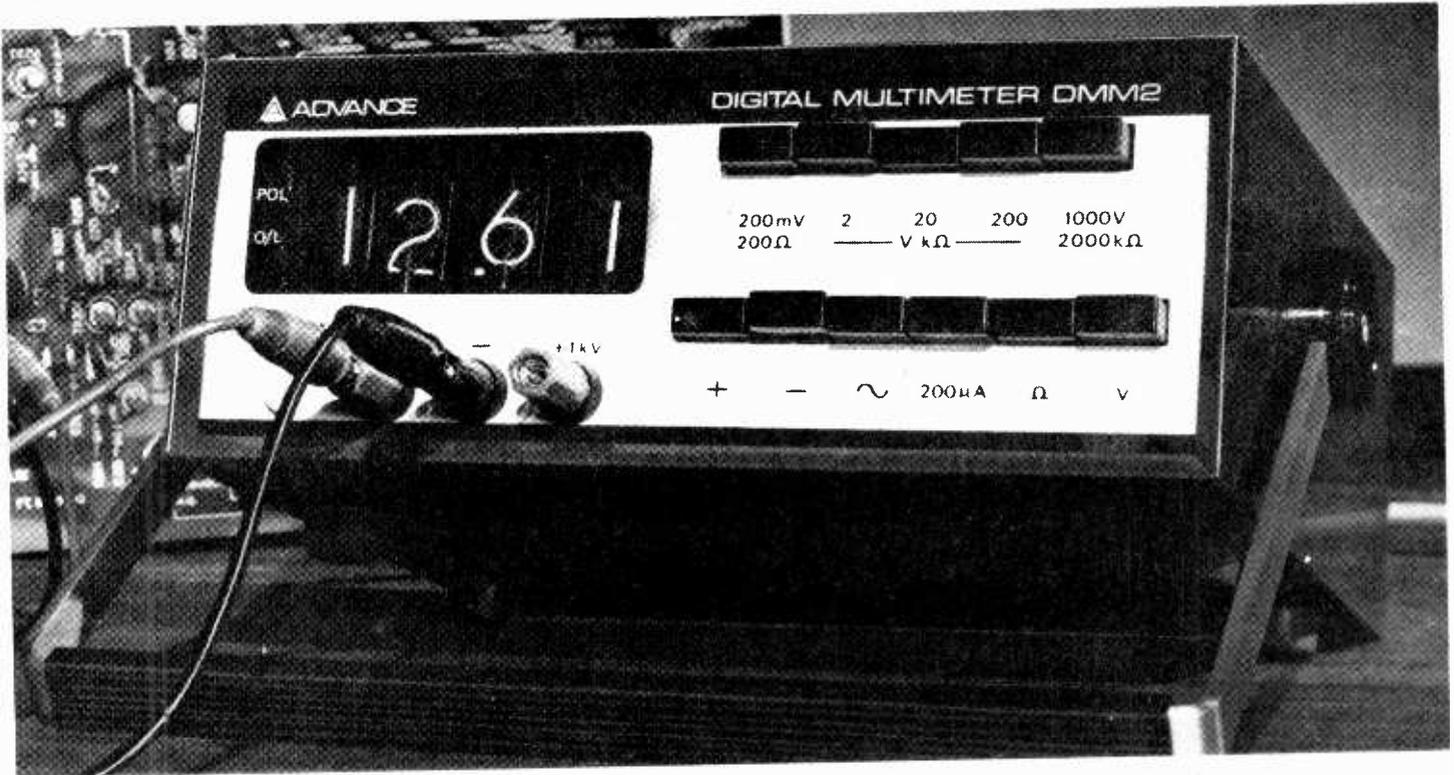

# Multimeter motivation!

There are seven good reasons for choosing an Advance DMM2 Multimeter—

- 1 Price—only £99 for one off—less for bulk orders.
- 2 Clear non-ambiguous digital reading of AC and DC voltage (100 $\mu$ V resolution), resistance and current—with optional shunts, type SP2.
- 3 L.S.I. reliability from a purpose designed package which performs the counting and storage functions.
- 4 Push button range selection. Maximum reading 1999 with decimal point.
- 5 Overrange and reverse polarity indication.
- 6 Lightweight (3½ lbs.) portability in an attractive ergonomically designed high impact plastic case.
- 7 Operation from AC supply, external 12V DC or optional rechargeable battery pack, BP2.

Write for data—or call Bishop's Stortford (0279) 55155 for up to date delivery information—availability may be an eighth reason for choosing the DMM2!

## DMM2 DIGITAL MULTIMETER

from **ADVANCE**



**ADVANCE  
ELECTRONICS  
LIMITED**

**INSTRUMENT DIVISION SALES OFFICE**

**WW—008 FOR FURTHER DETAILS**

Raynham Road  
Bishop's Stortford, Herts.

Telephone:  
Bishop's Stortford (0279) 55155  
Telex: 81510




# SME

The best pick-up arm in the world

SME precision pick-up arms offer a standard of design and engineering which has earned them many distinctions. Throughout the world thousands are used daily by enthusiasts, professionals, and broadcasting and recording companies, who appreciate a specification that is eminently suited to the needs of modern high-quality sound reproduction.

Write to SME Limited · Steyning · Sussex · England

# TRANSISTOR POWER

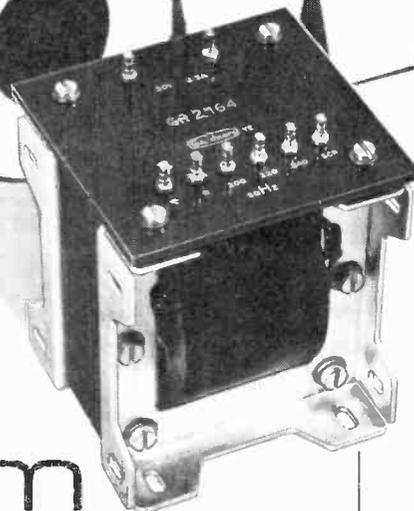

Another range of standard transformers from Gardners – acknowledged leaders in electronic transformers – TRANSISTOR POWER SUPPLY TRANSFORMERS.

You can select from more than fifty standard types and be sure of finding something suitable for any contemporary transistor power requirement – and most probably from stock! Write for GT.25.

from **GARDNERS**

There are nine other GT Brochures and we'll be pleased to mail any in which you are interested if you will post us this coupon.

- GT.1 POWER CONTROLLING SATURABLE RECTORS 50W to 1kW with application notes.
- GT.5 AUDIO TRANSFORMERS including Microphone and line matching, Driver, output and impedance matching transformers.
- GT.12 LILLIPUT SERIES OF MICROMINIATURE TRANSFORMERS including Inverter, A.F. and wide-band carrier matching A.F. Driver and pulse types, miniature smoothing and A.F. inductors.
- GT.16 ALPHA SERIES OF ASSEMBLIES for filters, delay lines, modulators, etc.
- GT.17 LOW VOLTAGE, ISOLATING AND AUTO TRANSFORMERS in nearly two hundred ratings, 6v. to 440v. and 5vA to 2kVA in six assembly styles.
- GT.21 MANUAL OF INVERTER TRANSFORMERS AND MODULES.
- GT.23 INDUCTORS, including heavy current and commutation types.
- GT.24 POWER TRANSFORMERS for use with tube type circuits (including obsolescent types) and E.H.T. and Magnetron Supply Transformers.
- GT.25 TRANSISTOR POWER SUPPLY TRANSFORMERS.
- GT.100 GENERAL REFERENCE CATALOGUE with data sheets of assemblies available for specially designed transformers.



**GARDNERS TRANSFORMERS LIMITED**

Christchurch, Hampshire, BH23 3PN, England

Tel: Christchurch 2284 (STD 0201 5 2284) Telex: 41276 GARDNERS XCH

Please indicate your requirement by circling the number/s below

1 5 12 16 17 21 23 24 25 100

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

WW 8

# TRIO's CS-1554 Passes The Most Rigid Testing Requirements



**CS-1554**  
130mm Dual  
Trace Oscilloscope

Waveform analysis and other electrical equipment and electronic installation testing is performed at the highest possible peak of efficiency with TRIO's CS-1554. This wide-band dual trace triggering oscilloscope operates at ultra-high sensitivity while also offering an over-all expansive range of test capabilities. Lightweight because of its all-solid state construction, this completely dependable instrument is remarkably versatile. For example, dual trace waveform analysis with very wide synchronization capabilities is possible from DC-10 MHz. It has no equal for speedy analysis efficiency.

 <p><b>CS-1553</b> 130mm Oscilloscope An essential device for signal waveform analysis and TV alignment and servicing. Complete solid state circuitry. Trigger sweep and automatic sweep potential. Very high sensitivity with wide frequency response from DC to 10 MHz extremely versatile.</p>	 <p><b>VT-106</b> High sensitivity Electronic Voltmeter This is a solid state electronic voltmeter employing IC and FET for high sensitivity and stability, capable of measuring voltages from 0.02mV to 300V.</p>	 <p><b>AG-201</b> ALL SOLID STATE CR type low-frequency Oscillator An all-transistor, compact CR type wide-band low-frequency oscillator, the AG-201 produces sine waves with a minimum of distortion and rectangular waves with a quick rise time at a low output impedance.</p>
--	---	---



TRIO KENWOOD ELECTRONICS S.A. 482 Chaussee de Haren 1800 Vilvoorde Belgium Tel: (02) 51.41.10  
Sole Agent for the U.K. B.H. MORRIS & CO., (RADIO) LTD. 84/88, Nelson Street, Tower Hamlets, London E.1. Phone: 01-790 4824

WW—011 FOR FURTHER DETAILS

# Let's cut the crackle! Telefunken 204 TS.

You don't want a load of waffle about the brilliance of the Telefunken 204TS all-stereo tape recorder.

It speaks for itself!

Whatever you put in, comes out unmolested. No irritating hums, buzzes or crackles find their way on to the track.

But what you want is facts not words.

It complies with the very, very stringent German tape recorder standards.

Separate controls for recording and playback, including sound level meters.

Single selector switch for all operating functions.

Three speeds.


Signal to noise ratio  $\geq 50\text{db}$  at  $7\frac{1}{2}\text{ips}$ .

And it can be used as a straight-through stereo amplifier as well!


Another fine example of the Telefunken philosophy: dedication to faithful reproduction.

Get the full story from your dealer or write direct.

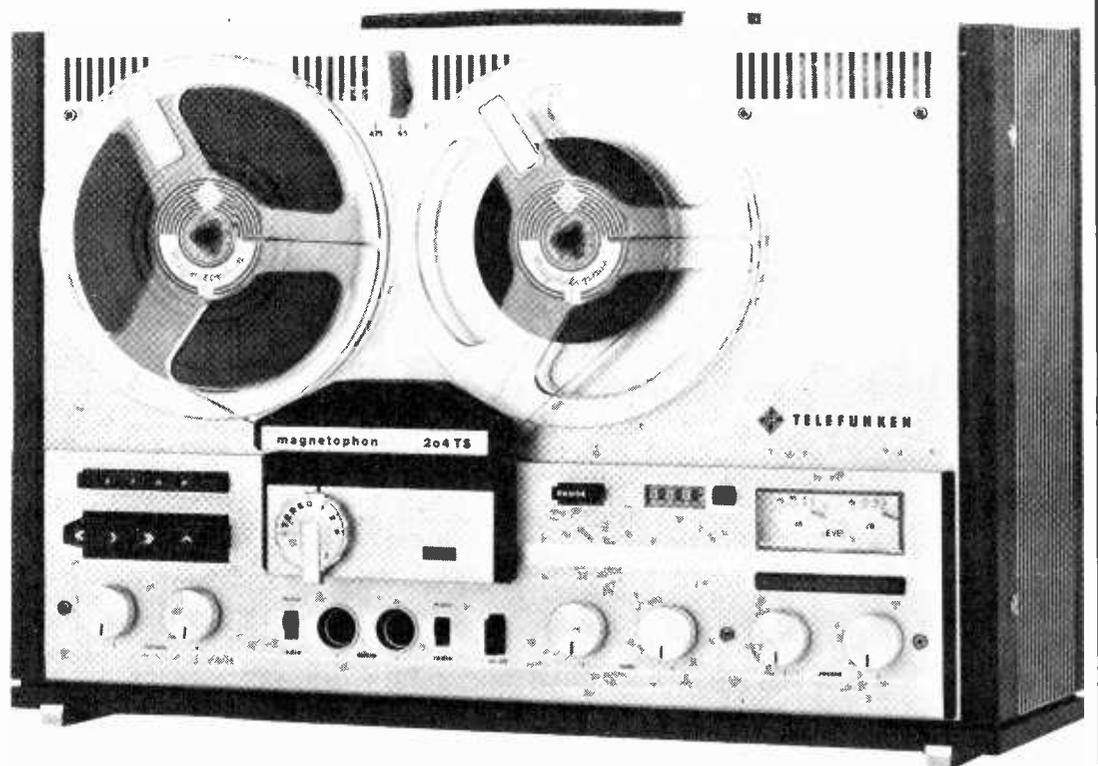AEG/Telefunken  
AEG House  
Chichester Rents  
Chancery Lane  
London WC2 A1NH  
01-242 9944



WW-012 FOR FURTHER DETAILS

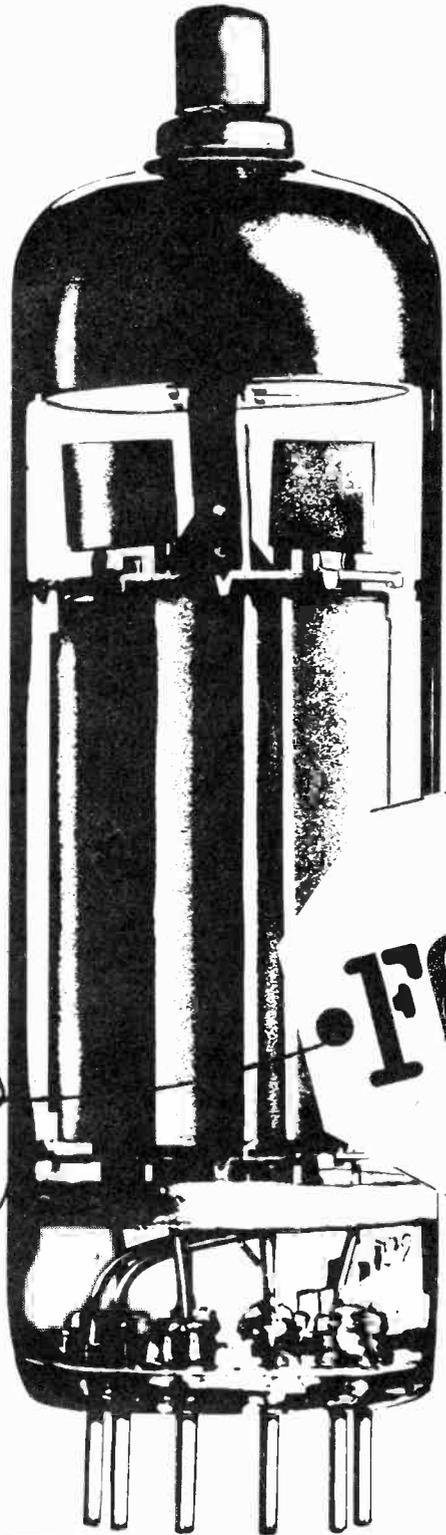

**Over 3,500  
specific  
types**


**• FOR EXPORT**

For quality, reliability  
and world-wide  
availability you can  
rely on Haltron valves . . .  
and on Hall Electric's speed,  
intelligence and reputation.  
*Ministry of Technology EID approval*  
*Air Registration Board approval.*

**HALTRON**  
Radio Valves and Tubes

Hall Electric Limited  
Haltron House, Anglers Lane  
London, N.W.5.  
Telephone: 01-485 8531 (10 lines) Telex: 2-2573  
Cables: Hallelectric, London, N.W.5.

**CUTTING OF THE MONTH**  
**MOLDANIZED® HEAT SHRINKABLE SHAPES.**  
 To **insulate** — **strengthen** — **protect**.  
 Hellermann Moldanized® Heat Shrinkable shapes are specially processed products with a built-in thermal memory which are available in a wide variety of forms and different materials.  
 Review your present methods — Hellermann Moldanized® Shapes could prune your installation costs!  
 For further information, please return the coupon.

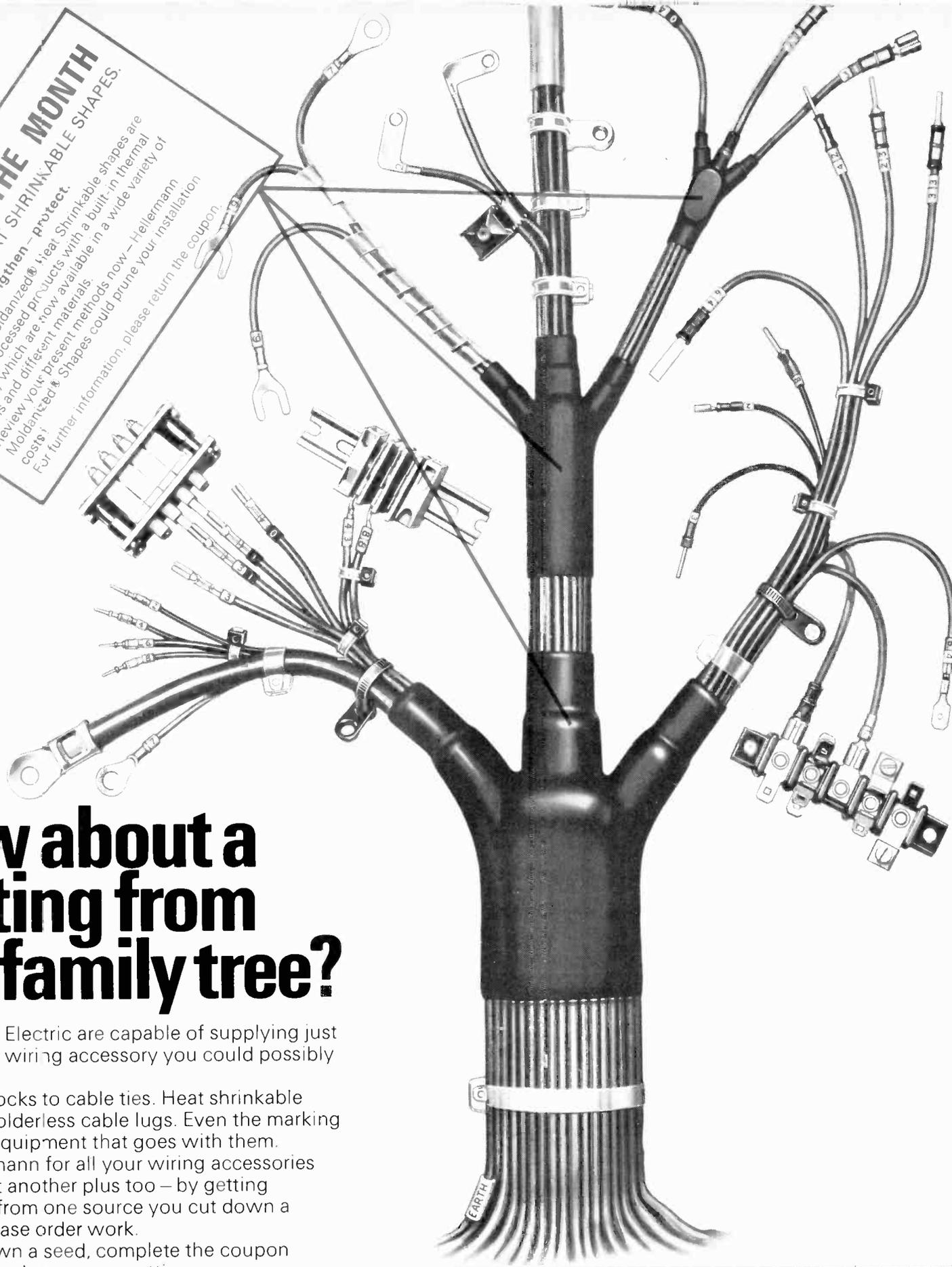

# How about a cutting from our family tree?

Hellermann Electric are capable of supplying just about every wiring accessory you could possibly need. Terminal blocks to cable ties. Heat shrinkable shapes to solderless cable lugs. Even the marking and fixing equipment that goes with them. Use Hellermann for all your wiring accessories and you get another plus too — by getting everything from one source you cut down a lot of purchase order work. If we've sown a seed, complete the coupon and we'll send you some cuttings.

Please let me have samples and literature on the following systems:—

<input type="checkbox"/> Heat shrinkable sleeves and shapes.	<input type="checkbox"/> Identifying/insulating sleeves.	<input type="checkbox"/>
<input type="checkbox"/> Terminal blocks.	<input type="checkbox"/> Cable binding and fixing systems.	<input type="checkbox"/>
<input type="checkbox"/> Solderless cable terminals.	<input type="checkbox"/> Cable stripping tools.	<input type="checkbox"/>

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

TEL. NO. \_\_\_\_\_



WORLD LEADERS IN CABLE ACCESSORIES  
**HELLERMANN ELECTRIC**  
 Division of Bowthorpe-Hellermann Ltd.,  
 Gatwick Road, Crawley, Sussex. Tel: Crawley 28888  
 A member of the Bowthorpe Holdings Group of Companies  
**WW—014 FOR FURTHER DETAILS**



**Slide-rule L C R Bridge** has ten overlapping ranges for rapid 1% measurements of any component, also tolerance and phase angle. Switch selects 1kHz or 100/120Hz operation. 2, 3 and 4-terminal connections. Adjustable overall sensitivity, special 'search' facility, and automatic increase of detector gain as balance is approached.

B 500



**Universal Bridge** for 0.1% measurements of any LCR combination from 2 micro-ohms to 500 gigohms. Source/detector (1592Hz) operate from a.c. or internal rechargeable battery. Sockets for external 200Hz - 20kHz. Display gives units, zeroes and decimal point. Four-terminal connections for accurate low impedance measurements.

B 224




**Autobalance Component Bridge** for immediate readout of resistance, capacitance and shunt loss, inductance and series loss. C and R comparisons from -25% to +25%. Electrolytics tested with d.c. Accuracy 0.25% (R & C), 2% (L). Internal 1kHz source/detector.

B 421




**Autobalance Universal Bridge** for continuous 0.1% readout of in-phase and quadrature terms, with analog outputs of both. Backing-off facilities. DVM connections, optional BCD outputs. Push-buttons for optimum discrimination up to five figures. Illuminated readout.

B 641

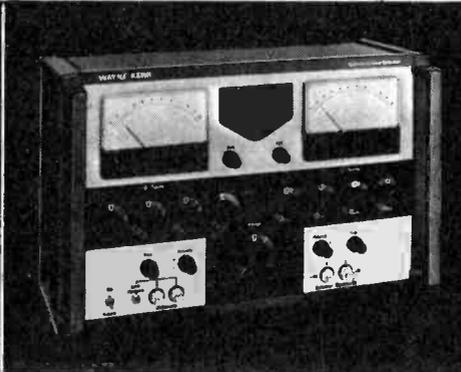

**Autobalance Universal Bridge** gives four-figure readout on all ten ranges covering every practical value of L, C, R & G. Sensitivity increases automatically when decade back-off controls are used but can be selected manually. External Standards sockets permit comparative measurements and increase discrimination to 5 or 6 figures. Accuracy 0.1%.

B 642

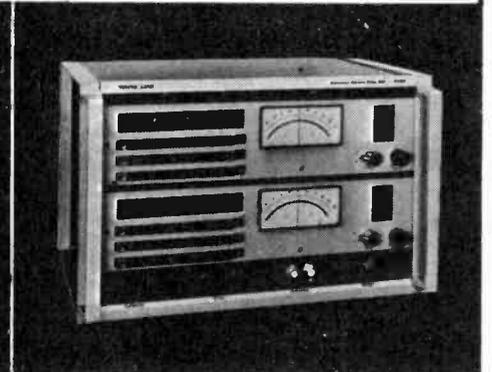

**Autobalance Precision Bridge** accurate of 0.01% though simple to operate. It measures virtually any meaningful impedance in any quadrant. Automatic compensation for measurement lead impedance. Six-figures discrimination. Analog outputs.

B 331 MkII

## Wide range A.F. Bridges

Wayne Kerr Bridges provide accurate measurement of L, C and R values over an unusually wide range. They employ a minimum number of fixed stable Standards in association with precision tapped transformers giving voltage and current ratios. Speed and ease of operation are assured by functional styling.

# WAYNE KERR


THE WAYNE KERR COMPANY LIMITED.

Roebuck Road, Chessington, Surrey. Tel: 01-397 1131. Cables: Waynkerr, Chessington. Telex 262333

WW-015 FOR FURTHER DETAILS
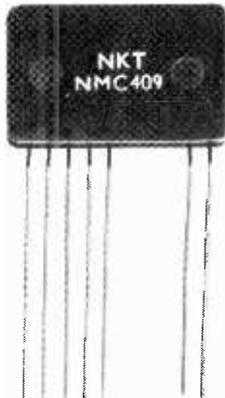
# “good gear in sma’ buik” from NKT

With a range of thick film hybrid microcircuits off the shelf, Newmarket brings alive for you the old Scottish Proverb quoted above—“Good things come in small packages”.



## NMC 409

### Slow Speed Eccles-Jordan “Divide-by-two”

This RST flip-flop is designed specifically for slow speed switching in industrial controls where standard monolithic TTL/DTL finds it difficult to cope with the large voltage transients arising and where the precise stabilised 5.1Vd.c. supply needed for TTL/DTL is difficult to provide (and costly). The NMC 409 can work on any unregulated supply of 6–24V, and is immune to fast voltage spikes because it is designed not to switch faster than 10 kHz.

Size: 1.1" x 0.7" x 0.23". One-off price £2.50.

## NMC 396

### Precision 6V Regulator D.C. Supply

This self-contained d.c. voltage regulator provides a precise 6V, 150mA d.c. output from a 7–15V d.c. input. The hybrid assembly

technique allows the output voltage to be set during manufacture typically to within 25mV of 6V (in contrast to the wider absolute tolerances unavoidable in monolithics). The NMC 396 has all the electrical robustness and stability of a discrete-component assembly and incorporates overload protection. Ideal for deriving a precise 6V from a 9 or 12V battery, it can also be fed from a standard d.c. power pack such as the NKT PC 101.

Size: 0.60" x 0.60" x 0.25". One-off price £2.50.




## NMC 426

### Optoelectronic Solid State Logic Indicator

This microcircuit is designed primarily to indicate visually the state of a binary logic circuit but can be used in any circuit calling for a visual indication of the existence or absence of a d.c. voltage at a test point. Completely self contained it only requires three connections to a nominal 5V d.c. supply, to earth and to the test point. The light display is a gallium arsenide phosphide solid state diode lamp with virtually unlimited life. The NMC 426 incorporates an internal d.c. amplifier enabling the light to

switch on with an input drive of only 1 $\mu$ A or 2V, and it takes a current of only a few  $\mu$ A from standard TTL/DTL logic gates.

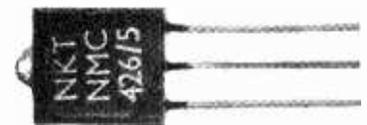Size: 0.42" x 0.31" x 0.13". One-off price £2.83.



## NMC 809A

### Wide Band Amplifier

This wide band amplifier is a self contained d.c. feedback pair (with output buffer stage) with access to the internal feedback loop for response tailoring. The hybrid assembly technique enables the low frequency gain to be set in manufacture to precisely 22dB and gives a narrow gain spread difficult to achieve by monolithic techniques. Usable for bandwidths up to 50MHz, the NMC 809A employs the easily handleable standard dual-in-line package. Its thick film hybrid assembly eliminates the parasitic stray capacitances to earth unavoidable with monolithics and gives it the electrical stability and robustness of discrete component designs.

Size: 0.71" x 0.28" x 0.15". One-off price £3.34.



For further details contact one of the distributors listed below. (In the case of large scale requirements you can save time by referring direct to Newmarket.

## distributors

Coventry Factors Ltd.,  
Coronet House,  
Upper Well Street,  
Coventry CV1 4AF, Warwickshire.  
Tel: 0203-21051/5  
Telex: 311243

Eastern Aero Electrical Services Ltd.,  
Building 202,  
Enfield Road,  
Hounslow, Middlesex.  
Tel: 01-759 1314

G.S.P.K. (Sales) Ltd.,  
Hookstone Park,  
Harrogate,  
Yorkshire.  
Tel: Harrogate 86258  
Telex: 57962

Hird-Brown Electronics Ltd.,  
Lever Street,  
Bolton BL3 6BJ,  
Lancashire.  
Tel: Bolton 27311  
Telex: 63478

I.T.T. Electronic Services Ltd.,  
Edinburgh Way,  
Hailow Essex.  
Tel: 02796/26777  
Telex: 81146

L.S.T. Electronic Components Ltd.,  
7 Coptfold Road,  
Brentwood,  
Essex.  
Tel: Brentwood 226470  
Telex: 99443


S.D.S. (Portsmouth) Ltd.,  
Hilsea Industrial Estate,  
Portsmouth PO3 5JW  
Tel: 0715/65311  
Telex: 86114

NKT—Newmarket Transistors Ltd.,  
Exning Road,  
Newmarket, Suffolk.  
Tel: Newmarket (0638) 3381  
Telex: 81358

# NKT

Newmarket Transistors Ltd., Exning Road, Newmarket. Tel: 0638 3381.

WW—016 FOR FURTHER DETAILS

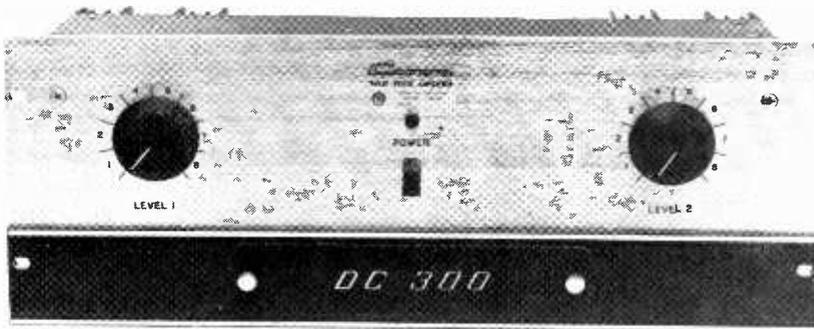**DC300****DUAL-CHANNEL POWER AMPLIFIER**

<b>Frequency Response</b>	$\pm 0.1\text{db}$ Zero-20KHz at 1 watt into 8 ohms. $\pm 0.6\text{db}$ Zero-100KHz.
<b>Phase Response</b>	Less than $5^\circ$ 0-10KHz.
<b>Power Response</b>	$\pm 1\text{db}$ Zero-20KHz at 150 watts RMS into 8 ohms.
<b>Power at Clip Point</b>	Typically 190 watts RMS into 8 ohms, 340 watts RMS into 4 ohms per channel.
<b>Total Output (IHF)</b>	Typically 420 watts RMS into 8 ohms, 800 watts RMS into 4 ohms.
<b>T.H.D.</b>	Better than 0.03% at 1KHz at 190 watts level.
<b>I.M. Distortion (60-7KHz 4:1)</b>	Less than 0.1% from 0.01 watt to 150 watts RMS into 8 ohms, typically below 0.05% (max 0.05%.
<b>Damping Factor</b>	Greater than 200 (Zero to 1KHz into 8 ohms at 150 watts RMS).
<b>Hum and Noise (20-20KHz)</b>	100db below 150 watts RMS output (unweighted, typical 110db).
<b>Slewing Rate</b>	8 volts per micro-second. S-R is the maximum value of the first derivative of the output signal.
<b>Dimensions</b>	19in. standard rack mount (W.E. hole spacing), 7in. height, $9\frac{1}{2}$ in. deep (from mounting surface).
<b>Weight</b>	40 pounds net weight.
<b>Finish</b>	Bright-anodized brushed-aluminium front-panel with black-anodized front extrusion, access door, and chassis.

- ★ DC-Coupled throughout!
- ★ Short Circuit proof!
- ★ 500 Watts RMS Mono.
- ★ 70 Volt Balanced line out!
- ★ UNEQUALLED QUALITY!
- ★ 3 YEAR PARTS WARRANTY!
- ★ ONLY **£320** inc. DUTY!

**CARSTON ELECTRONICS LTD.**  
**SHIRLEY HOUSE**  
**27 CAMDEN ROAD**  
**LONDON, N.W.1 9LN**  
**01-267 2748**

WW—017 FOR FURTHER DETAILS

**SPEEDY DELIVERY IS OUR AIM****CLOSED CIRCUIT TELEVISION****SYSTEMS ENGINEERING AND INSPECTION SERVICE**

We manufacture a range of industrial and educational television equipment and undertake the construction of complete systems for special purposes. We also inspect pipework, industrial plant etc. by television and fibre optics, and are able to retrieve lost objects from difficult locations

**J. D. Jackson Electronics**



**EGGLESTON WORKS, LOMBARD STREET, NEWARK, NOTTS.**  
**TELEPHONE: NEWARK 5718**

WW—018 FOR FURTHER DETAILS

# In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering...

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn on 'SATISFACTION - OR REFUND OF FEE' terms. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

## WHICH SUBJECT WOULD INTEREST YOU?

### Mechanical

A.M.S.E. (Mech.)  
Inst. of Engineers  
Mechanical Eng.  
Maintenance Eng.  
Welding  
General Diesel Eng.  
Sheet Metal Work  
Eng. Inspection  
Eng. Metallurgy  
C. & G. Eng. Crafts  
C. & G. Fabrication

### Draughtsmanship

A.M.I.E.D.  
Gen. Draughtsmanship  
Die & Press Tools  
Elec. Draughtsmanship  
Jig & Tool Design  
Design of Elec. Machines  
Technical Drawing  
Building

### Electrical & Electronic

A.M.S.E. (Elec.)  
C. & G. Elec. Eng.  
General Elec. Eng.  
Installations & Wiring  
Electrical Maths.  
Electrical Science  
Computer Electronics  
Electronic Eng.

### Radio & Telecomms.

C. & G. Telecomms.  
C. & G. Radio Servicing  
Radio Amateurs' Exam.  
Radio Operators' Cert.  
Radio & TV Engineering  
Radio Servicing  
Practical Television  
TV Servicing  
Colour TV  
Practical Radio & Electronics (with kit)

### Auto & Aero

A.M.I.M.I.  
MAA/IMI Diploma  
C. & G. Auto Eng.  
General Auto Eng.  
Motor Mechanics  
A.R.B. Certs.  
Gen. Aero Eng.

### Management & Production

Computer Programming  
Inst. of Marketing  
A.C.W.A.  
Works Management  
Work Study  
Production Eng.  
Storekeeping  
Estimating  
Personnel Management  
Quality Control  
Electronic Data Processing  
Numerical Control  
Planning Engineering  
Materials Handling  
Operational Research  
Metrication

### Constructional

A.M.S.E. (Civ.)  
C. & G. Structural  
Road Engineering  
Civil Engineering  
Building  
Air Conditioning  
Heating & Ventilating  
Carpentry & Joinery  
Clerk of Works  
Building Drawing  
Surveying  
Painting and Decorating.  
Architecture  
Builders' Quantities

### General

C.E.I.  
Petroleum Tech.  
Practical Maths.  
Refrigerator Servicing.  
Rubber Technology  
Sales Engineer  
Timber Trade  
Farm Science  
Agricultural Eng.  
General Plastics

### General Certificate of Education

Choose from 42 'O' and 'A' Level subjects including:  
*English*  
*Chemistry*  
*General Science*  
*Geology*  
*Physics*  
*Mathematics*  
*Technical Drawing*  
*French*  
*German*  
*Russian*  
*Spanish*  
*Biology*  
*B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.*

**WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.**

*Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.*

## THEY DID IT— SO COULD YOU

"My income has almost trebled . . . my life is fuller and happier." - Case History G/321.

"In addition to having my salary doubled, my future is assured."—Case History H/493.

"Completing your Course meant going from a job I detested to a job I love." - Case History B/461.

## FIND OUT FOR YOURSELF

These letters—and there are many more on file at Aldermaston Court—speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help *you*.

# Free!

Why not do the thing that really interests you? Without losing a day's pay, *you* could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you . . . but it could be the best thing you ever did.

## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept B7, Aldermaston Court, Reading RG7 4PF.

## POST THIS COUPON TODAY

(Write if you prefer not to cut this page)



To: B.I.E.T., Dept B7, Aldermaston Court, Reading RG7 4PF  
Please send me book and details of your Courses in

Name..... Age.....


Address.....

Occupation.....

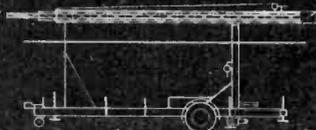**B.I.E.T.—IN ASSOCIATION WITH THE SCHOOL OF CAREERS—ALDERMASTON COURT, BERKSHIRE**

one man  
one hour  
one hundred feet

The 100 ft free standing mobile is only one of our full range of telescopic, tilt-over towers from 25' to 120'. Road trailer conforms to the Road Traffic Act in all respects. Full specifications of our complete range; mobile, semi-portable and fixed, are in our brochure — send for it today!



**STRUMECH  
VERSATOWER  
SYSTEM**

Strumech Engineering Limited  
Portland House, Coppice Side,  
Brownhills, Walsall, Staffs, England.  
Telephone: Brownhills 3651



WW—020 FOR FURTHER DETAILS

# TELEPRINTERS · PERFORATORS REPERFORATORS · TAPEREADERS DATA PROCESSING EQUIPMENT

SALE OR HIRE



**2-5-6-7-8 TRACK AND  
MULTIWIRE EQUIPMENT**

Special Codes Prepared

**TELEGRAPH AUTOMATION AND COMPUTER PERIPHERAL ACCESSORIES  
DATEL MODEM TERMINALS, TELEPRINTER SWITCHBOARDS**

Picture Telegraph, Desk-Fax, Morse Equipment: Converters and Stabilised Rectifiers; Line Transformers and Noise Suppressors; Tape Holders, Pullers and Fast Winders; Governed, Synchronous and Phonic Motors; Teleprinter Tables and Cabinets; Silence Covers; Distortion and Relay Testers; Send/Receive Low and High Pass Filters; Teleprinter, Morse,



Teledeltos Paper, Tape and Ribbons; Polarised and specialised Relays and Bases; Terminals V.F. and F.M. Equipment; Telephone Carriers and Repeaters; Diversity; Frequency Shift, Keying Equipment;

Racks and Consoles; Plugs, Sockets, Key, Push, Miniature and other Switches; Cords, Connectors, Wires, Cables, Jack and Lamp strips, and Switchboard Accessories; Teleprinter Tools; Stroboscopes and Electronic Forks; Cold Cathode Matrices; Test Equipment; Miscellaneous Accessories, Teleprinter and Teletype Spares.



**W. BATEY & COMPANY**

Ggioty Works, Akeman Street, Tring, Herts  
Tel: Tring 3476 (STD 0442 82) Cables: RAHNO TRING  
Telex: 82362, A/B BATEY TRING

WW—021 FOR FURTHER DETAILS

## POWER UNITS

**Valradio**

Now available with 3 OUTPUTS making these units more versatile for:

**DEVELOPMENT    PRODUCTION TESTING    SERVICING**



Type VRU/30/20\* — £144.35

\*OUTPUT 1, 0-30V 20A DC.

Will provide accumulator performance from AC mains for production testing and servicing of battery operated equipment. Output continuously variable 0-30V at up to 20A.

\*OUTPUT 2, 0-80V 10A AC.

For the testing and development of low voltage AC equipment.

\*OUTPUT 3, 0-260V 4A.

Continuously variable AC mains supply voltage for testing equipment at various voltages.

Send for publication WPU9

**VALRADIO LTD.**

Dept. WPU9, BROWELL'S LANE, FELTHAM, MIDDLESEX, ENGLAND  
Telephone: 01-890 4242


WW—022 FOR FURTHER DETAILS

# NEW temperature controlled soldering iron.



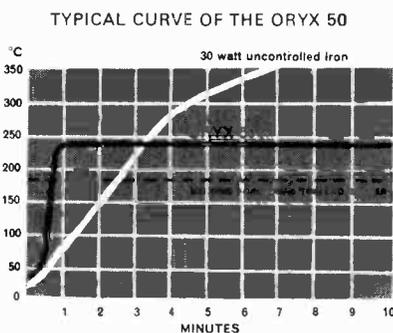
## THE ORYX 50

- \*Screw adjustment range 200°C to 400°C.
- \*Heat settings accurate to  $\pm 2\%$ .
- \*One tip for all temperatures.
- \*Temperature adjustable whilst iron is on.
- \*Cool, comfortable handle.
- \*Standard tip — long life iron coated.
- \*Choice of 11 tip sizes.
- \*Built-in indicator lamp — thermostat controlled.
- \*Rated at 50 watts.
- \*12, 24, 50, 115 or 210/250v. a.c. models.



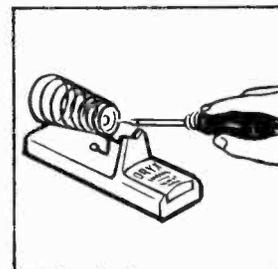
**Price**  
with long life tip.  
**£3.75**  
STAND:  
**£1.25**



Send for Technical Literature to

**W. GREENWOOD ELECTRONIC LIMITED**  
21 Germain St, Chesham, Bucks, England. Tel: Chesham 4808/9. Telex 83647. Cables: Greenelec, Chesham.

WW—023 FOR FURTHER DETAILS

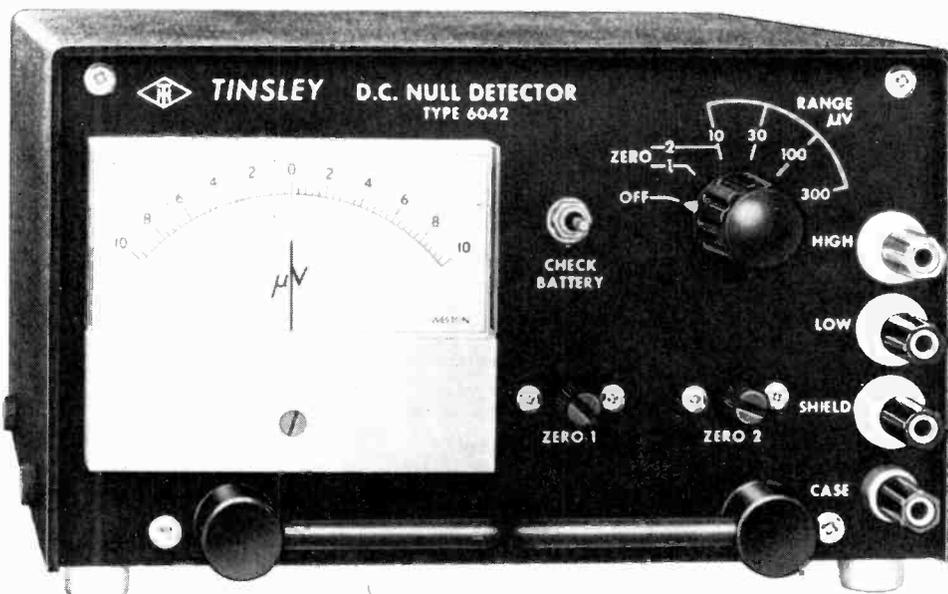

### D.C. NULL DETECTOR, TYPE 6042 \*

Portable detector for use with d.c. bridges and potentiometers. Sensitivity 10  $\mu$ V full scale. Input impedance 14,000  $\Omega$ . Fully transistorised. 4 ranges. Resolution 1  $\mu$ V in 10,000  $\Omega$  source resistance. Noise less than 0.15  $\mu$ V peak to peak.

### NULL DETECTOR AMPLIFIER, TYPE 6040\*

Similar to above but with increased sensitivity — 1  $\mu$ V full scale. Resolution 0.1  $\mu$ V. 7 ranges.

\* SEND FOR LEAFLETS 175/2049 and 175/2047

# TINSLEY

H. TINSLEY & CO LTD · WERNDÉE HALL  
SOUTH NORWOOD · LONDON SE25 · 01-654 6046

WW—024 FOR FURTHER DETAILS



## RESISTANCE BRIDGE TYPE P.W.3/E

**RANGE**  
0.001 ohm to 10 Megohms

**ACCURACY** ± 0.1%

**HIGH RESOLUTION WITH ELECTRONIC NULL DETECTOR**

**PRICE** £78.50  
**DELIVERY** EX-STOCK

A robust general purpose bridge for D.C. resistance measurements with a practical measuring range of from 1 ohm to 10 Megohms when used with its own built in supply and null detector. It has been designed to work under adverse factory or field conditions and the control functions are logically arranged and will be quickly understood by personnel not familiar with this type of measurement.

Request full details from:

### CROYDON PRECISION INSTRUMENT COMPANY

Hampton Road, CROYDON (Postal Code: CR9 2RU)  
Telephone 01-684 4025 and 4094

WW—025 FOR FURTHER DETAILS

# RESLO

## Just walk and talk!

No messy leads to hamper or hinder. Complete freedom of movement with studio quality reproduction. The Reslo Radio Microphone provides the perfect answer to a wide range of situations where the traditional type microphone is a handicap.

*For further details contact:*

### RESLOSOUND LIMITED

115 SALUSBURY ROAD, LONDON, N.W.6. TEL: 01-328 3262

WW—026 FOR FURTHER DETAILS

## A true bargain by Post:

**The famous PA 263**  
plus heatsink/pc board for **£1.75!**

The PA263 monolithic audio power amp. provides 3.5W rms, 10W peak, to a 16 ohm load. Ideal for mono or stereo players, tape, disc or intercom amplifiers, FM or AM receivers, Op. Amp. boosters etc.

Now we supply it complete with a specially designed heavy duty pc board ready drilled for PA263 and up to 12 other components all ready for soldering. No other heatsink is necessary. ONLY £1.75 COMPLETE, +p & p £0.15. Or stereo £3.50 plus £0.15 p & p. Delivery by return. FREE 4-PAGE PA263 DATA SHEET PLUS DESIGN INFORMATION WITH ALL ORDERS.

Jermyn Industries,  
Vestry Estate, Sevenoaks, Kent.

## JERMYN

WW—027 FOR FURTHER DETAILS

## J E S AUDIO INSTRUMENTATION

Illustrated the Si 451 Millivoltmeter — pk-pk or RMS calibration with variable control for relative measurements. 40 calibrated ranges **£35.00**

Si 452 ..... **£30.00**  
Distortion Measuring Unit.  
15 c/s — 20 Kc/s — .01%

Si 453 ..... **£40.00**  
Low distortion Oscillator.  
Sine — Square — RIAA

**J. E. SUGDEN & CO., LTD.** Tel. Cleckheaton (OWR62) 2501 BRADFORD ROAD, CLECKHEATON, YORKSHIRE

WW—028 FOR FURTHER DETAILS

## SANWA MULTI TESTERS

USED THROUGHOUT THE WORLD, SANWA'S EXPERIENCE OF 30 YEARS ENSURES ACCURACY, RELIABILITY, VERSATILITY, UNSURPASSED TESTER PERFORMANCE COMES WITH EVERY SANWA.

6 Months' Guarantee, Excellent Repair Service

Model P-28	£4.87	Model F-80TRD	£13.75
Model JP-50	£5.87	Model 380-CE	£16.00
Model U-50DN	£8.00	Model N-101	£18.50
Model 360-YTR	£8.25	Model 460-EO	£21.75
Model A-303TRD	£11.00	Model EM-700	£45.00
Model AT-1	£11.37	Model R-1000CB	£60.00
Model K-30THD	£12.50		



Cases available with most meters

PLEASE WRITE FOR ILLUSTRATED LEAFLETS OF THESE SANWA METERS

**SOLE IMPORTERS IN U.K.;**  
**QUALITY ELECTRONICS LTD.**  
47-49 HIGH STREET, KINGSTON-UPON-THAMES, SURREY, Tel: 01-546 4585

WW—029 FOR FURTHER DETAILS

# SNS SYSTEMS SHAPE NEW SOUNDS

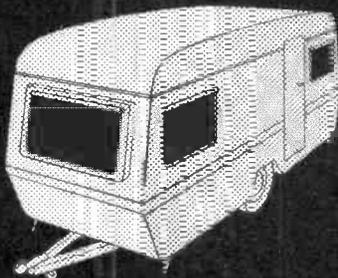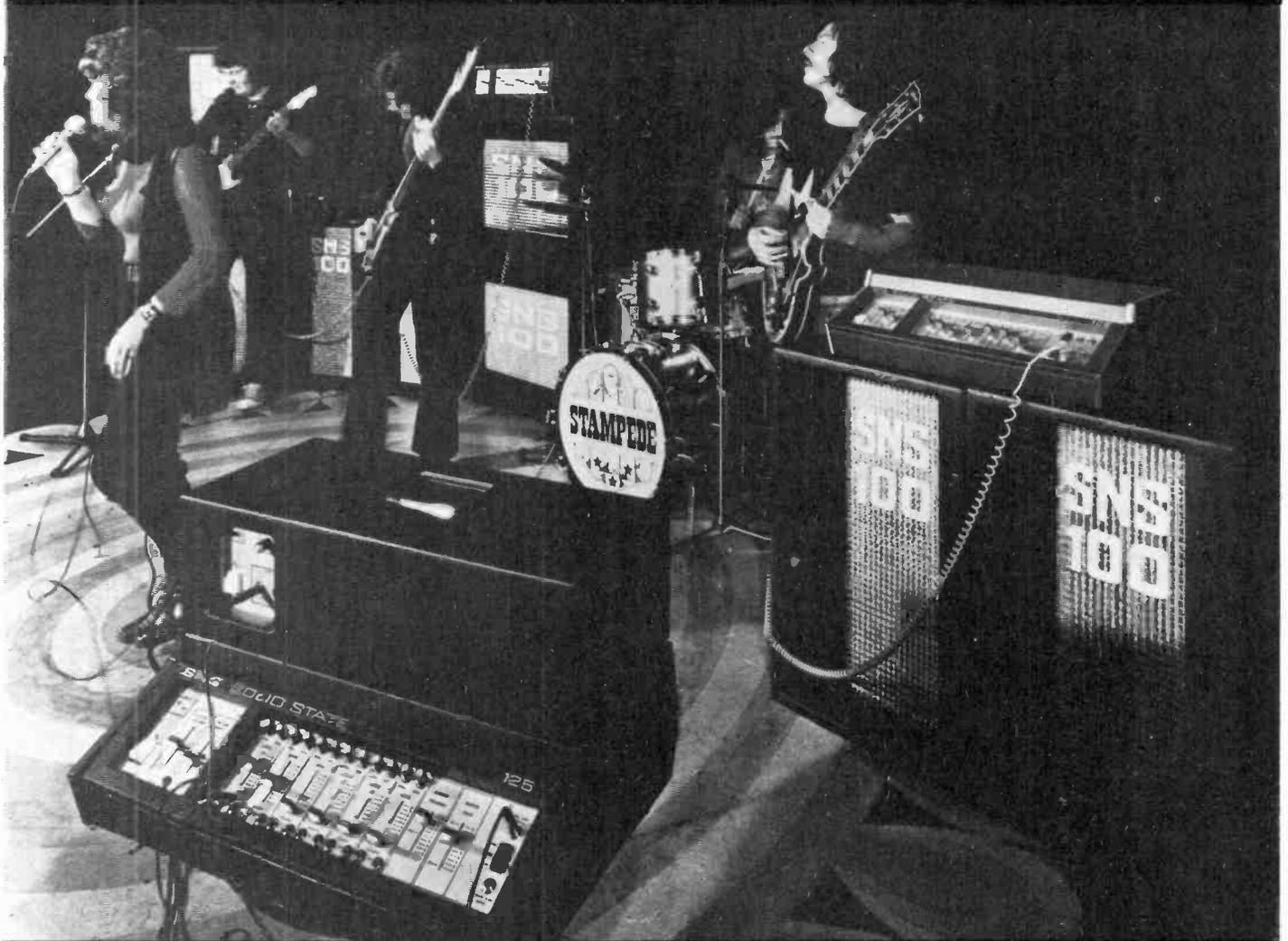

**ANOTHER FIRST FOR SNS—**  
*Our mobile demonstration unit is now touring the country—make sure it visits your area—send the coupon to John Banfield—he'll bring the New Big Sounds to you.*

SNS Instrument and P.A. amps, a powerful range of slave amps and a variety of speaker and horn enclosures in modular form—these add up to the biggest Pop News in years. Sounds come alive with SNS equipment—new big sounds you can shape yourself.

There's only one way to judge and that's hear it for yourself. We've carried out field trials in theatres, studios, discos, halls, pubs and clubs and we're now ready to play to you.

Send us the coupon—we'll come to you.

# SNS

COMMUNICATIONS LIMITED

## Shaping new sounds

851 Ringwood Road, Bournemouth, BH11 3LN  
Tel: Northbourne (0202 E) 5331


To: John Banfield, S.N.S. Communications Ltd.,  
851 Ringwood Road, Bournemouth BH11 3LN.  
Yes, I want to hear the New Big Sounds—please  
let me know when this can be arranged.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
Tel. No. \_\_\_\_\_

W1

# Farnell LFM Mk2 Sine/Square Oscillator

Frequency range of 1Hz to 1MHz

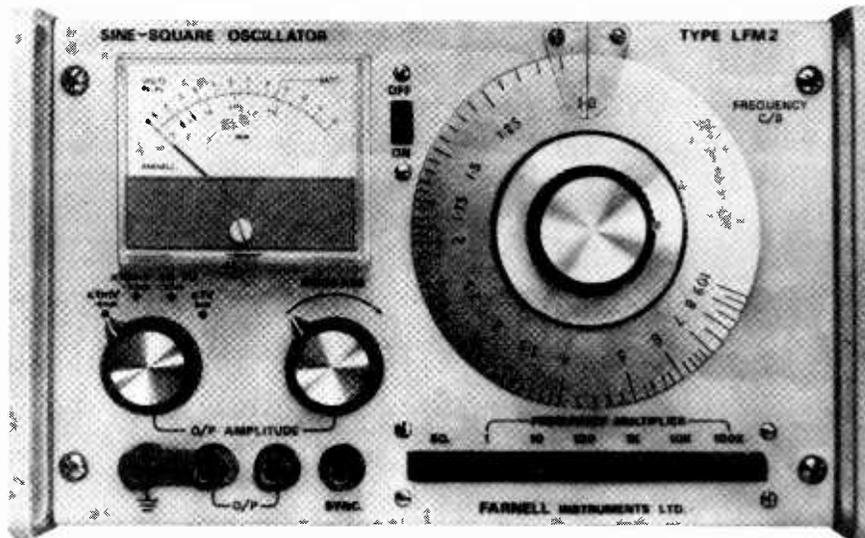

- \* SINE OR SQUARE WAVE OUTPUT FULLY VARIABLE 1mV to 12V peak to peak, thermistor stabilised.
- \* SQUARE WAVE RISE TIME BETTER THAN 0.15 MICROSECONDS throughout frequency range.
- \* SEPARATE 5V TRIGGER OUTPUT.
- \* MAINS OR BATTERY OPERATED.



For full details on the LFM MK2 please contact us at the address below. (Please state if you require details on the full range of Farnell Instruments).

**FARNELL INSTRUMENTS LIMITED**  
Sandbeck Way, Wetherby LS22 4DH, Yorks.

Telephone: 0937-3541/6

**LONDON OFFICE**

Telephone No. 01-802-5359

WW-031 FOR FURTHER DETAILS

# No.1 in Solder

**ENTHOVEN** offers you Europe's Widest Range

One good reason for soldering with Enthoven – whatever your needs – is the Enthoven range. It gives you a wide choice of high quality products developed for use with modern techniques. It includes Flux Cored Solder Wires, Solder Pre-forms, Solid Solders, selective Fluxes, solder specialities, materials for printed Circuitry and for soldering Aluminium. For complete technical details of Europe's widest range, ask Enthoven Solders Limited, Dominion Buildings, South Place,

London EC2M 2RE. Telephone 01-628 8030; telex 21457; cables:

ENTHOVEN LONDON EC2

## SOLID SOLDERS

PLUMBERS BARS—CAR BODY FILLERS  
TINSMITHS

STICKS —BLOW PIPE STICKS

INGOTS IN A VARIETY OF WEIGHTS

WIRE IN ALL GAUGES

—1 lb. & 7 lb. REELS

FASHION JEWELLERY CASTING

ALLOYS

SHEET—RIBBON

Available in a wide range of alloys—standard or custom-made. Certificates of analysis provided.

WW-032 FOR FURTHER DETAILS



## COMPAK 8 can be tuned in seconds —by anyone!

### Labgear **COMPAK 8** **HF SSB PACKSET**


**10W p.e.p. speech over entire range  
2-9 MHz. Unprecedented serviceability**

- \* Light, sturdy, inexpensive
- \* Externally-loaded Aerial for higher efficiency (Prov. Pat.)
- \* Plug-in Tx and Rx modules for instant replacement
- \* 8 crystal controlled channels
- \* Fully submersible

The forward looking COMPAK 8 Transceiver gives outstanding performance over the frequency range 2-9 MHz by making use of the very latest in integrated circuits, F.E.T. and wide band techniques.

Operating directly from a rechargeable battery it gives a power output of 10 watts p.e.p. on any of 8 channels in this H.F. band. The use of wide-band circuits eliminates the complexity of individual tuning and band switching with its time consuming channel alignment. The result is a completely self-contained back-pack

SSB transceiver with a minimum of controls – lower in weight, smaller in size, and with greater flexibility of performance than any comparable equipment. Labgear COMPAK 8 is designed for single side-band suppressed-carrier voice or key operation in A3J or A2J modes under the most severe environmental conditions. It meets the needs of military, security forces, police, emergency, surveying etc. and is designed for use by non-technical operators.

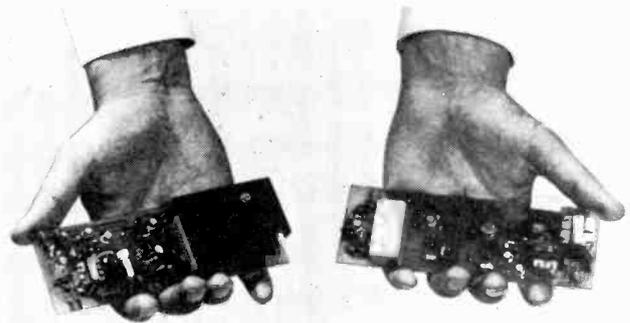

*Transmitter and receiver use plug-in modules for ease of servicing. Low-noise high-gain receiver employs dual gate MOSFET RF devices in conjunction with fast attack, slow release AGC, to give exceptional immunity to blocking and cross modulation and performance approaching base station standards.*




*For full specification etc, please contact*

CROMWELL ROAD, CAMBRIDGE CB1 3EL, ENGLAND

Telephone: 0223 47301. Telex: 81105 LAB. Telegrams: Labgear, Cambridge

**WW—033 FOR FURTHER DETAILS**
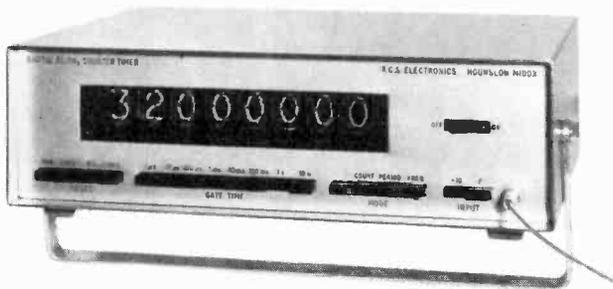
## THIS HIGH PERFORMANCE 32MHz TIMER/COUNTER



is only **£160**

MADE BY R.C.S. ELECTRONICS WHO PRODUCED THEIR FIRST ECONOMY INSTRUMENT NEARLY 10 YEARS AGO.


IF YOU CANNOT BELIEVE THAT AN **EIGHT** FIGURE COUNTER WITH AN ELECTRONICALLY CONTROLLED CRYSTAL OVEN AND AN INPUT SENSITIVITY OF 10mV (WHICH WOULD NORMALLY COST YOU AT LEAST £300) CAN BE BOUGHT FOR THIS FIGURE WRITE FOR FULL SPECIFICATION SHEET OR PHONE ROY GRIFFIN ON EXT. 4 FOR THE FULL GRIFF.



R.C.S. ELECTRONICS, NATIONAL WORKS,  
BATH ROAD, HOUNSLOW, MIDDX.  
TELEPHONE 01-572 0933/4/5

WW-034 FOR FURTHER DETAILS

## Oxley Snales

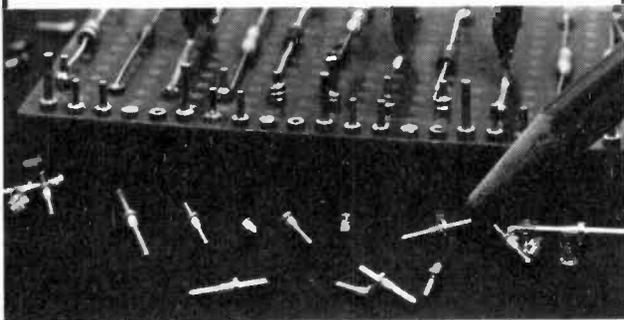

The extensive range of Oxley Snales now include an Eyelet version (which is ideally suited for mounting I.C. Packs and other components for experimental work). They augment the well known standard range of Oxley "Snales" suitable for mounting in 0.040 inches, 0.050 inches diameter holes.

Send for technical details and samples.

**OXLEY DEVELOPMENTS CO. LTD.**  
Priory Park, Ulveston, North Lancs. England  
Tel: Ulveston 2621 Telex: 6541 Cables:  
Oxley Ulveston



WW-036 FOR FURTHER DETAILS

# How to install a CCTV system for only **£700**



For only £700 you can buy a complete closed circuit television system from Dixons.

Camera, monitor and video recorder.

And if you need a more sophisticated system, you'll find it less expensive at Dixons than anywhere else.

Send us this coupon and we'll arrange a demonstration. Or phone us at 01-437 8811.

To Dixons CCTV Ltd., 3 Soho Square, London, W.1.

I am interested in CCTV equipment.

Please get in touch with me

Please send me your literature  (Tick box required)

NAME .....

ADDRESS .....

**Dixons  
CCTV**

W W I

WW-035 FOR FURTHER DETAILS

# Foundations of Wireless and Electronics

8th Edition

M. G. SCROGGIE, B.Sc., C.Eng., F.I.E.E.


The present edition, like the previous ones, covers the whole basic theory, starting with a sound exposition of the elementary principles needed in all branches of electronics. No previous technical knowledge is assumed and mathematics are used only where essential. While the foundational chapters are basically as before, those that follow, on application, have been almost completely rewritten. This was made necessary by the 'semiconductor explosion.' Much more is now included on transistors, integrated circuits, frequency modulation, vhf and uhf, radio senders and television (including colour).

0 592 05961 8 522 pages illustrated 1971

**£3.00**

00592 00041 9

**£1.80**

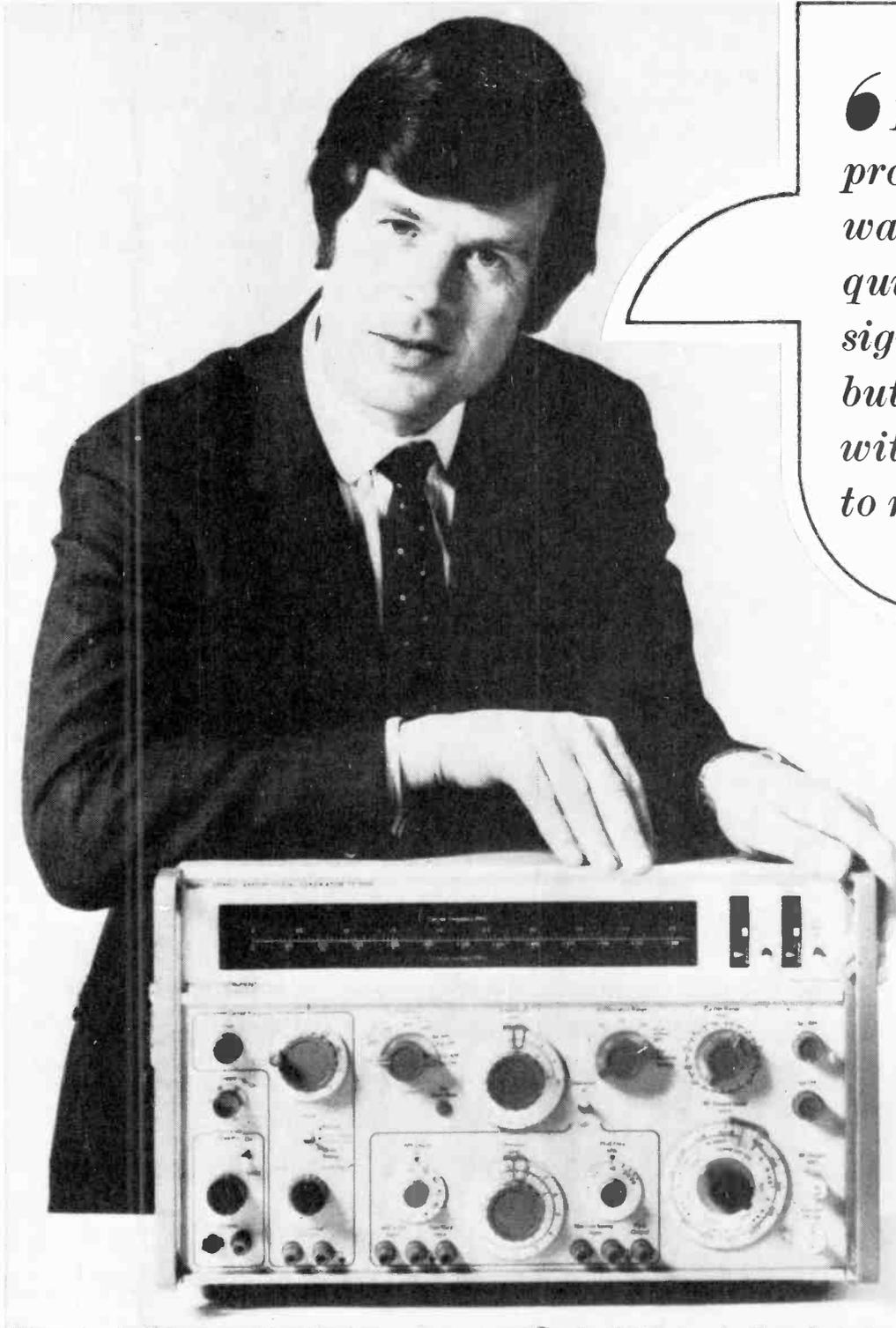

*“I really had two problems. I not only wanted something quite exceptional in signal generators— but also a sweeper with performance to match.”*

## Marconi Instruments came up with both—*in a single unit!*

The M.I. TF2008 brings together two first-class analytical tools. By providing an exceptional signal generator with the facility to sweep its output signal at any frequency setting, in one integrated unit, M.I. have produced an instrument which is unrivalled by any competitor.

The instrument — which is fully solid state — covers the incredibly wide frequency range of 10kHz to 510MHz and, in addition to all usual signal generator functions, it can be operated in a frequency swept mode with a sweep width adjustable up to the entire cover of each frequency band. Frequency stability is of a very high order and spurious signal and microphony are kept to a very low level.

*Other salient features are:*

R.F. output: 0.2 $\mu$ V to 200mV e.m.f.

Incremental tuning: directly calibrated panel controls

Swept frequency markers: derived from the crystal calibrator  
Internal mod. frequency: 300Hz to 3kHz  
Frequency Modulation: up to 300kHz deviation  
Amplitude Modulation: 0 to 80%

M.I. — Europe's largest single source of signal generators. TV, Narrow Band, FM, PCM — whatever the purpose or the frequency to be covered, Marconi is the company most likely to have the precise instrument you need. Behind it: brainpower and experience unique in the business.



**MARCONI INSTRUMENTS LIMITED**

*A GEC-Marconi Electronics Company*

Longacres, St. Albans, Hertfordshire, England.  
Tel: St. Albans 59292 Telex: 23350



## Wonders of the modern world

Teonex products, of course! Over 3,000 of them, electronic valves, semi-conductors, and now - neons and indicators too... all performing superbly in many climates... all at prices that are very competitive.

How do Teonex do it? Specialisation in one field. Concentration on export only. Very strict quality control.

Sold in sixty countries, on Government or private contract, Teonex offers you a comprehensive range, with most items immediately available.

For technical specifications and prices, please write to Teonex Limited, 2a Westbourne Grove Mews, London W.11, England. Cables: Tosuply London W.11.

# TEONEX

electronic valves  
semi-conductors  
neons & indicators for export



WW-038 FOR FURTHER DETAILS

We are a Polish company exporting high stability electronic components which have good mechanical characteristics and long life expectancy.

Valves

TV Picture Tubes

Tape Recorder Heads

Electron Guns

Sub-assemblies

We can offer production capacity and the ability to produce tape recorder heads to meet our customers' own specifications.

EXPORTER:

# Elektrim




Polish Foreign Trade Company for  
Electrical Equipment Ltd.  
Warszawa 1, Czackiego 15/17, Poland.  
Telegrams: ELEKTRIM-WARSZAWA,  
Phone: 26-62-71, Telex: 814351  
P.O. Box: 638

*If you are interested, please send for catalogues and quotations.*

WW-039 FOR FURTHER DETAILS
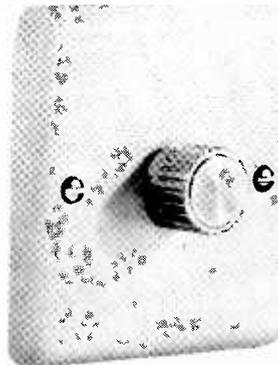
## Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The ivory mounting plate of the DIMMASWITCH matches modern electric fittings. The bright chrome control knob activates an on-off switch and controls 40-600 watts of all lights except fluorescents at mains voltages from 200-250 V, 50 Hz. The DIMMASWITCH has built-in radio interference suppression. Price: £3.20 plus 10p post and packing Kit Form: £2.70 plus 10p post and packing Please send C.W.O. to:-

**DEXTER & COMPANY**  
4 ULVER HOUSE, 19 KING STREET,  
CHESTER CH1 2AH. Tel: 0244-25883.  
As supplied to H.M. Government Departments,  
Hospitals, Local Authorities, etc.

WW-040 FOR FURTHER DETAILS

## COLOUR TELEVISION PICTURE FAULTS

K. J. Bohlman £2.50 Postage 6p  
There are over 120 illustrations, including 88 colour photographs.

**TELEVISION SERVICING HANDBOOK** by Gordon J. King. £3.80. Postage 12p.

**RCA SOLID STATE HOBBY CIRCUITS MANUAL** by R.C.A. £1.05. Postage 10p.

**THE RADIO AMATEUR'S HANDBOOK** by A.R.R.L. £2.60. Postage 20p.

**TRANSISTOR AUDIO & RADIO CIRCUITS** by Mullard. £1.50. Postage 60p.

**TRANSISTOR CIRCUITS IN ELECTRONICS** by S. S. Haykin & R. Barrett. £2.50. Postage 15p.

**COLOUR TELEVISION WITH PARTICULAR REFERENCE TO THE PAL SYSTEM** by G. N. Patchett. £2.50. Postage 6p.

**RADIO VALVE & TRANSISTOR DATA** by A. M. Ball. 75p. Postage 10p.


## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST  
of British and American Technical Books


19-21 PRAED STREET,  
LONDON, W.2 1NP

Phone 723 4185  
Closed Sat. 1 p.m.
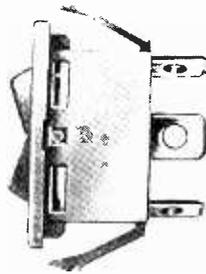
# MY VITAL STATISTICS ARE 30mm.X14mm.X33mm. 250V 10AMP A.C. SINGLE POLE SNAP-IN FIXING




## now meet the family

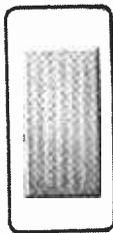


1109




1100

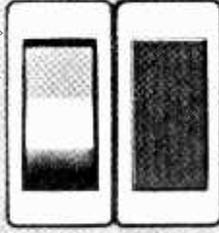

1100/1109

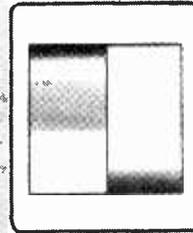

1100 twins

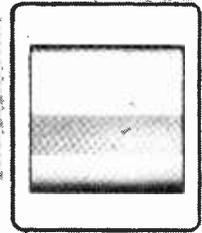

1110

Being a snappy little 1100 rocker who is getting around fast, I am often asked about my family. Now, having managed to persuade them to have their photograph taken with me, I have much pleasure in introducing them.

1109—often seen around with me, is a most illuminating little pilot light with a variety of colour lenses. At times we are very close and can often be seen working together very harmoniously on a wide range of appliances and equipment.

The 1100 twins are going to be very popular and you can expect to see them on many companies' panels soon.

1110, the fat one, is double pole and the clever member of the family, he can operate two circuits at a time.

Like to know more about us? Give us a ring at 01-574 2442, we would certainly like to meet *YOU* some time. P.S. I have just been awarded my BS.3955 approval certificate.

# ARROW

## ARROW ELECTRIC SWITCHES LTD.

BRENT ROAD • SOUTHALL, MIDDLESEX, ENGLAND • PHONE: 01-574 2442

subsidiary of

Telex: 23332 Cables: ARROWHART LONDON

Scottish office: 13 Murray Place, Stirling Phone: 0786 3823

Distributors: Comway Electronics Ltd., Downshire Way, Bracknell, Berks. RG12 1ND. Phone: Bracknell 24765


ITT Electronic Services Ltd., Industrial Estate, Edinburgh Way, Harlow, Essex. Phone: 0279-6 26777


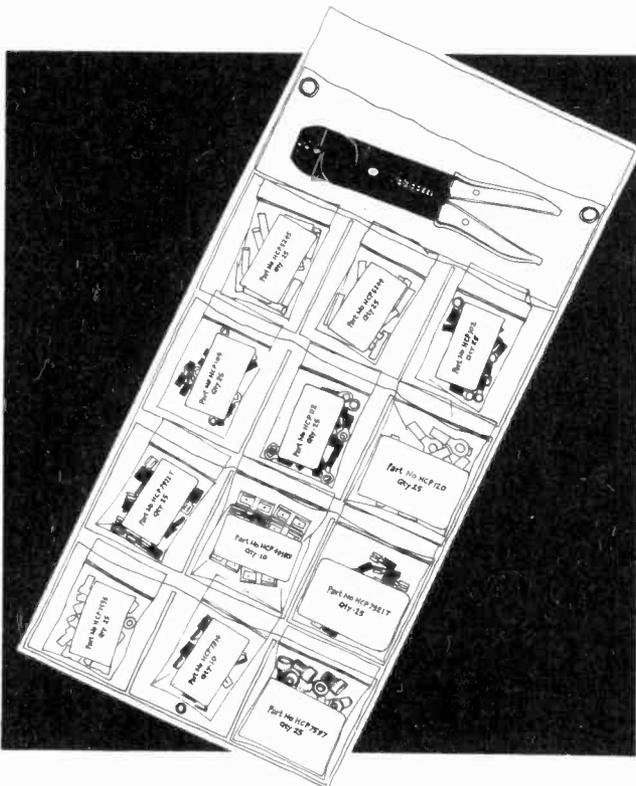
# Terminate your wiring problems

Use Hellermann-GKN Compression Terminal Kits. They're ideal for general maintenance work on electrical and electronic equipment — domestic or industrial — and one of the Kits is specially made for automobile electronics.

Take your pick from three different Kits, each one containing 12 of the most popular compression terminals. With or without a hand crimping tool. The terminal packets are re-sealable, and fit into the pockets of the plastic wallet that can either be hung on a wall or folded neatly into a tool bag.



**UNIVERSAL** with pre-insulated terminals for general electrical maintenance and domestic appliances.

Kit No. 1 — without tool: £6.15 Kit No. 1-CT — including tool: £8.30

**MAINTENANCE** with pre-insulated terminals for factory and general maintenance.

Kit No. 2 — without tool: £6.15 Kit No. 2-CT — including tool: £8.30

**GARAGE** with non-insulated terminals and covers used on most automobiles.

Kit. No. 3 — without tool: £3.25 Kit No. 3-CT — including tool: £5.40

All prices are subject to quantity terms. Each of these Kits can be made up to customers' requirements, subject to quantity.

Write for descriptive leaflet to:


## NETTLEFOLD & MOSER LTD

170-194, Borough High Street, London, SE1 1LA.  
Tel: 01-407 7111.



WW—081 FOR FURTHER DETAILS

## METER PROBLEMS?

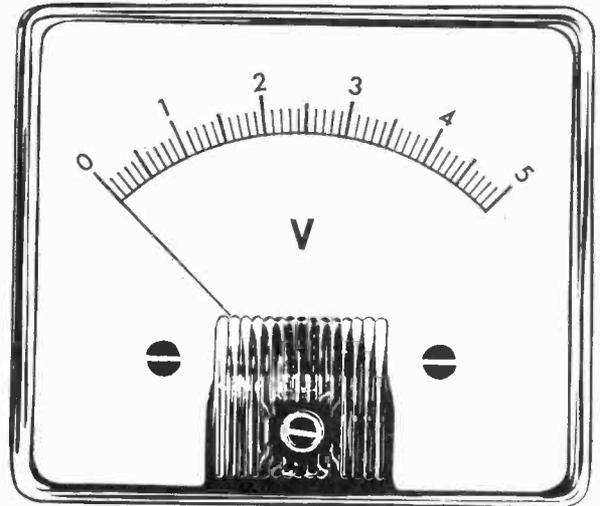

A very wide range of modern design instruments is available for 10/14 days' delivery.


Full Information from:

**HARRIS ELECTRONICS (London)**

138 GRAYS INN ROAD, W.C.1 Phone: 01/837/7937

WW—042 FOR FURTHER DETAILS

## XENON STROBOSCOPE

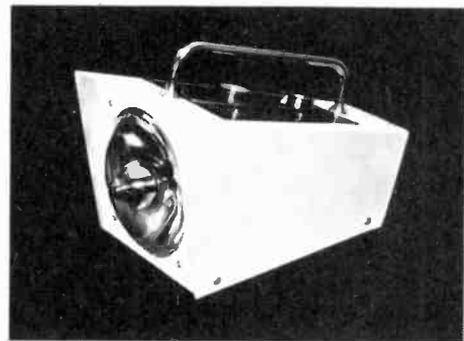

A Stroboscope designed primarily for laboratory, industrial and educational applications where the elaboration and expense of more complex equipment may not be required. Features include simplicity of operation, robust construction, exceptionally low price and built in reliability.

The instrument is of modern appearance, small, light in weight, convenient to use and portable. A wide range of flashing rates is covered by the large accurately calibrated dial, allowing operation at low frequencies for strobo photographic experiments and at high speeds for observation of rapidly rotating or reciprocating phenomena.

The external triggering facility permits single shot operation by an external closing contact and also provides a synchronising input for high and low speed repetitive phenomena which might otherwise be difficult to maintain in exact phase.

Light source.

High intensity Xenon tube mounted in a parabolic reflector.

Flashing rate.

1-250 flashes/second in 3 ranges.

Frequency accuracy.

Typically  $\pm 2\%$  of each full scale.


Triggering.

(a) by internal oscillator  
(b) by external closing contacts.

Price: £38.50

**Edwards Scientific International Ltd.**  
Knowle Road, Mirfield, Yorkshire. Tel: 092484 4242

WW—043 FOR FURTHER DETAILS

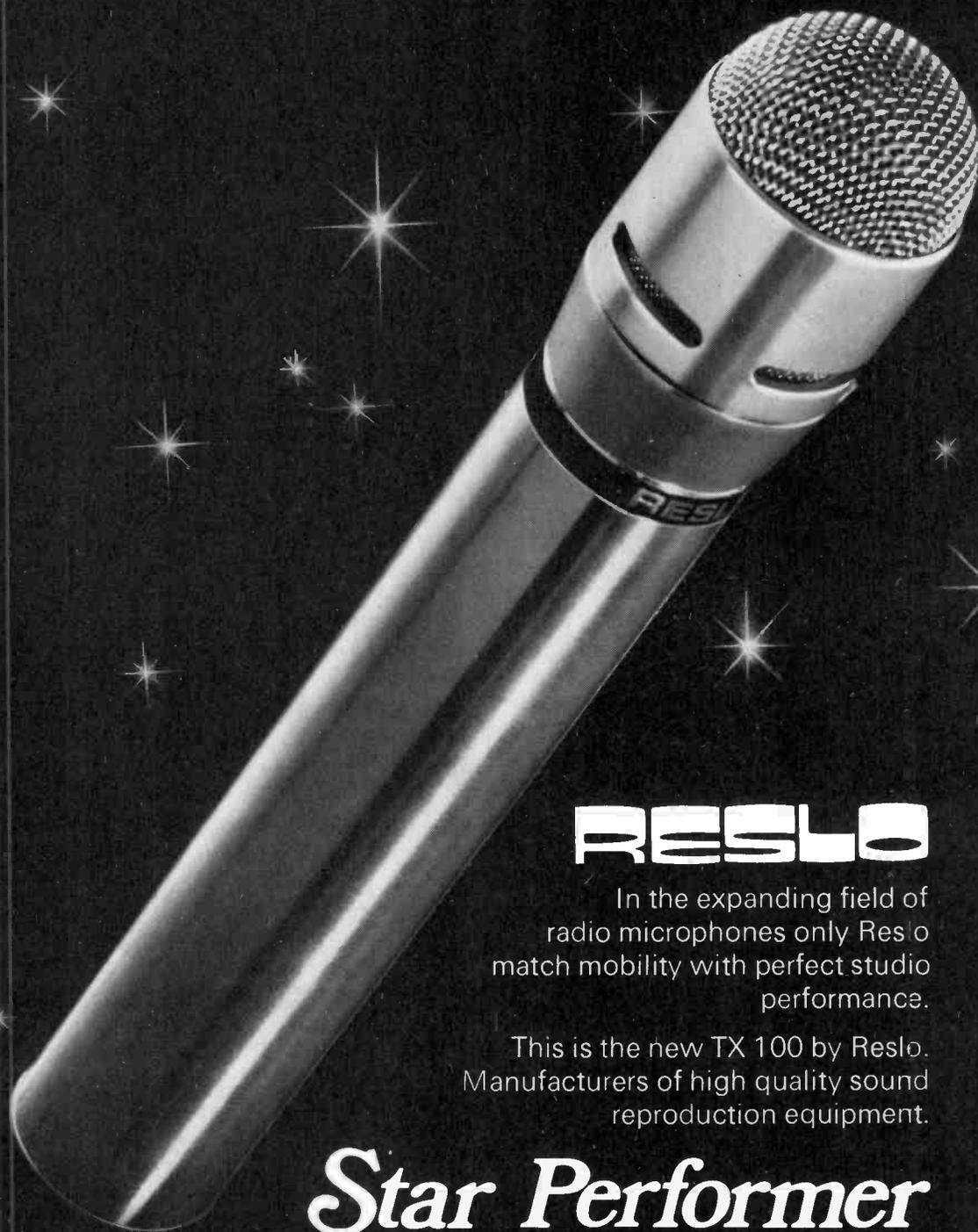

**RESLO**

In the expanding field of radio microphones only Reslo match mobility with perfect studio performance.

This is the new TX 100 by Reslo. Manufacturers of high quality sound reproduction equipment.

# *Star Performer*

RESLOSOUND LTD, SPRING GARDENS, LONDON ROAD,  
ROMFORD, ESSEX, TEL: ROMFORD 61926.

# Litestat

## TEMPERATURE CONTROLLED SOLDERING INSTRUMENTS



- 2 Models, 55 and 70 watts
- Control within  $\pm 2\frac{1}{2}^{\circ}\text{C}$
- Temperature infinitely adjustable 200/400°C
- Available for all voltages
- Built-in indicator lamp
- Cool, comfortable unbreakable Nylon handle
- Range of bit sizes, Copper or Philips iron-coated.
- Prices from **£3.84**

*Please ask for New Leaflets 5/1009/11*

## LIGHT SOLDERING DEVELOPMENTS LTD

28 Sydenham Road, Croydon, CR9 2LL  
Tel: 01-688 8589 and 4559



WW-045 FOR FURTHER DETAILS

## T. B. TECHNICAL LTD. CONSULTANCY • INSTALLATION MAINTENANCE

*Our service covers:*

Broadcast, Recording, Film, Audio and Video Electronics, also Electro-Acoustic Design.

Experienced Technicians available for installation, wiring, routine and emergency maintenance.

Test equipment hire and contract service.


## T. B. TECHNICAL LTD.

38 HEREFORD ROAD, LONDON, W.2

Telephone: 01-229 8054

1076

WW-046 FOR FURTHER DETAILS

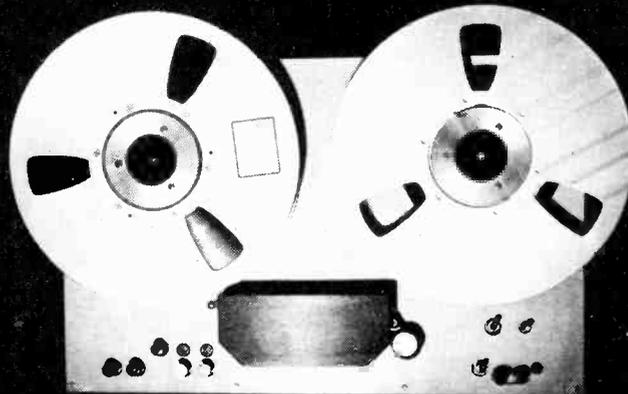

We proudly present the production version of our professional custom tape transport, featuring full studio standards of performance, ruggedness and dependability.

$\frac{1}{4}$ " and  $\frac{1}{2}$ " tape interchangeably, reel diameters from 7" to 11 $\frac{1}{2}$ ".  
2-speed hysteresis direct capstan drive at high torque. .05% wow and flutter or better, choice of 3 $\frac{1}{2}$ /7 $\frac{1}{2}$ " or 7 $\frac{1}{2}$ /15" second speeds.

Extremely quiet solenoid operation, relay and solid state controlled, electrically latched by gentle push-button switches. All push-button functions can be removed, and include MAINS ON/OFF, PLAY, RECORD, STOP, FAST FORWARD and REWIND. Other functions by toggle switching include MASTER MAINS ON/OFF, SPEED and REEL DIAMETER selection.

Solid state control of the two reel-drive motors permits rapid start, but minimum running tape tension for lowest wow and flutter with no loop throwing, hence no dancing idlers, and simplest tape path for rapid threading of tape. Tension levels are changed by REEL DIAMETER switch.

Tape lift system causes tape to contact all three heads in RECORD, but only play head in PLAY for maximum tape and head-life. Plug-in interchangeable head systems.

Motors, relays and solid state circuits are plug-in. Deck is cool-running and suitable for tropical operation. Available with a variety of plug-in electronic configurations of finest quality, including 4 channels on both tape widths.


*Full details and prices from*

**JOHN STEED RESEARCH LTD,**  
220 EDGWARE RD, LONDON W2, Phone 01-723 5066

WW-047 FOR FURTHER DETAILS
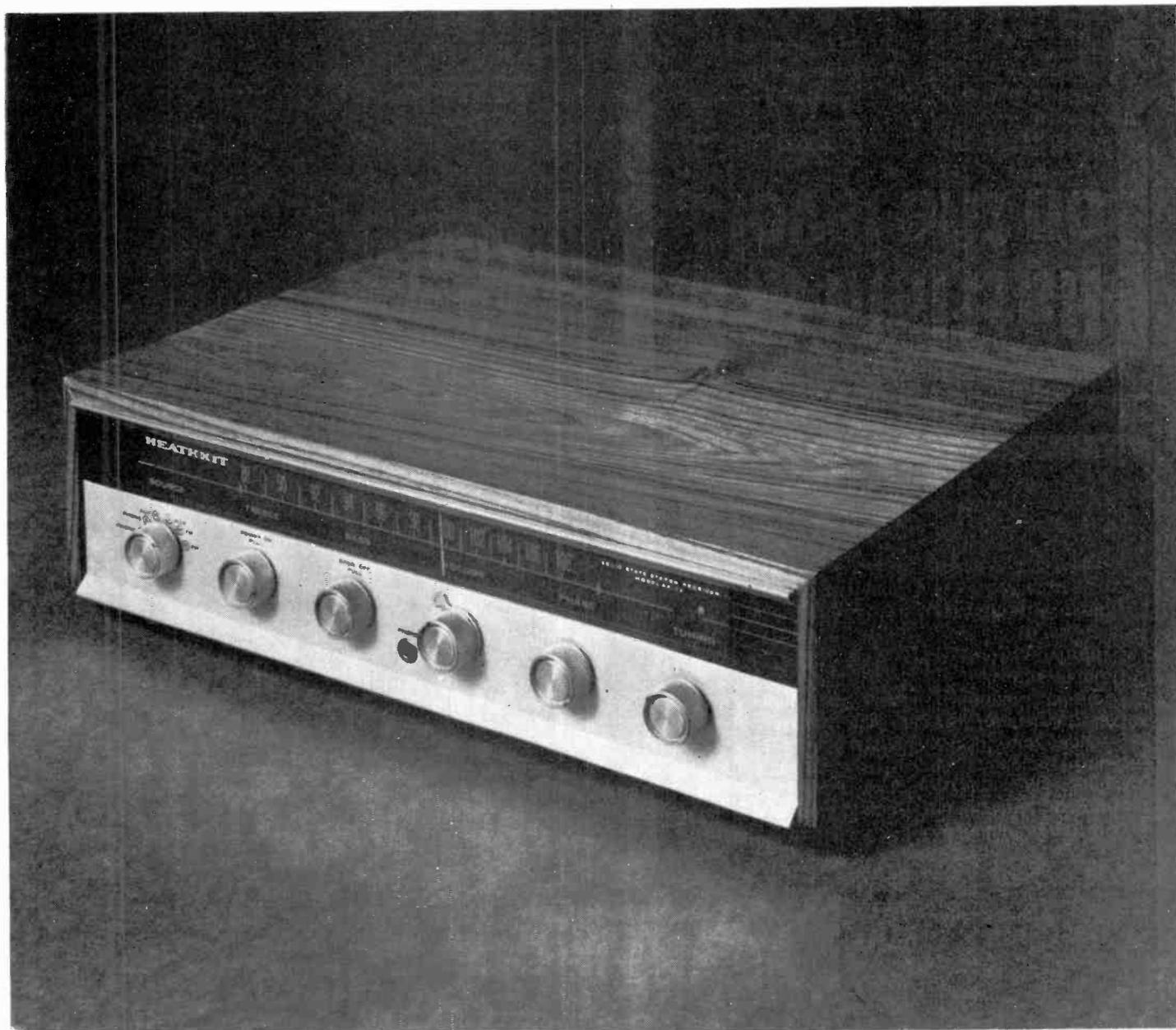
# Send for Heathkit – and send for the best

The best in hi-fi; the best in short-wave;  
the best in domestic, marine and auto equipment;  
the best in everything electronic.



Heathkit comes direct from the world's leading suppliers of top-quality electronic equipment. You assemble your components using the unique Heathkit 'step-and-check' method and there's a team of experts ready to help and advise you on any problem. But you won't need them. Hardly anyone does!

Send for your FREE catalogue – NOW.


**Please send me details of your complete range of kits.**  
Name \_\_\_\_\_  
Address \_\_\_\_\_

Heath (Gloucester) Limited,  
Gloucester, GL2 6EE  
**HEATHKIT**  
a Schlumberger Company  
WW 08

WW-048 FOR FURTHER DETAILS

# audix

## AUDIO MIXER TYPE MXT/800

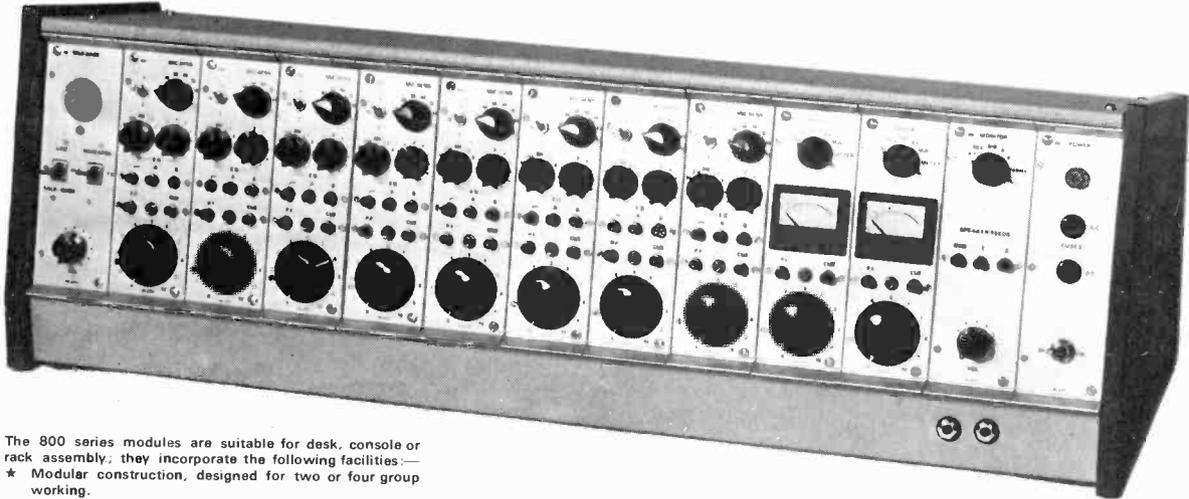

The 800 series modules are suitable for desk, console or rack assembly; they incorporate the following facilities:—

- ★ Modular construction, designed for two or four group working.
- ★ Fully professional in performance and in facilities.
- ★ Overload margins, noise levels, distortion figures and frequency response, are equal to those of large studio desks.
- ★ A single plug in board per module includes all active components.

Modules available include:—


Microphone channels (2 & 4 group working): Line Channels: Group modules (including V.U. & P.P.M. metering): Monitor module: Talkback module: Power supply module: Echo channel: Tone generator module: Limiter compressor module: Line equaliser module.

# audix SOUND SYSTEMS

AUDIX B.B. LIMITED  
STANSTED ESSEX  
Tel: STANSTED 3132/3437  
(STD 027-971)

WW—049 FOR FURTHER DETAILS

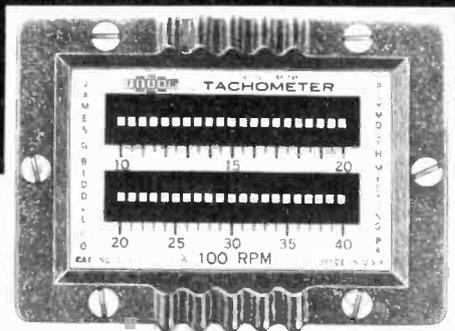**Accurate and direct  
measurement of speed without  
coupling to moving parts**



# FRAHM

## resonant reed TACHOMETERS

for hand use or permanent mounting

Ranges and combinations of ranges from 900 to 100,000 r.p.m.

Descriptive Literature on Frahm Resonant Reed Tachometers and Frequency Meters available from the sole U.K. Distributors. Manufacture and Distribution of Electrical Measuring Instruments and Electronic Equipment. The largest stocks in the U.K. for off-the-shelf delivery.

Anders means meters

**ANDERS ELECTRONICS LIMITED**

48/56 Bayham Place, Bayham Street,  
London NW1. Tel: 01-387 9092

WW—050 FOR FURTHER DETAILS

**Nombrex accuracy!**



*in the palm of your hand*

TRANSISTORISED—COMPACT—MODERN STYLING

Standard Model 29-S

- 150KHz-220 MHz on fundamentals
- Eight clear scales. Total length 40"
- Smooth vernier tuning—ratio  $7\frac{1}{2} : 1$
- Magnifier cursor—precision tuning
- Overall accuracy, better than 1.5%
- Modulation, variable depth and frequency

Price £20.00

Xtal Check Model 29-X

- All the features of the Model 29-S AND
- Integral Crystal Oscillator providing calibration check points throughout all ranges. For adjustment of scale accuracy to  $\pm 0.02\%$

Price £27.50

Illustrated: R. F. SIGNAL GENERATOR MODEL 29, Spin Wheel Tuning £1.00 extra

Trade & Export enquiries welcome. Send for full technical leaflets. Post and Packing 32½p extra



**NOMBREX (1969) LTD. EXMOUTH DEVON**

Tel. 03-9523515

WW—051 FOR FURTHER DETAILS


wireless



It has been suggested that a perfect amplifier would be equivalent to a piece of wire with gain.

A piece of wire? First of all it would hum, so we'd have to screen it. This would increase the input capacity so we'd have to make the screening large or the conductor small. Then we would have output resistance and, if of appreciable length, we'd have inductance and termination problems as well. All in all a 303 power amplifier would be much easier.

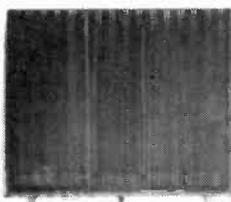The funny thing is; even if we had our perfect piece of wire with gain and compared it with a 303, the two would sound *exactly* the same no matter how carefully we listened.



# QUAD

for the closest approach to the original sound



Send postcard for illustrated leaflet to Dept. WW Acoustical Manufacturing Co. Ltd., Huntingdon, Tel: (0480) 2561. QUAD is a Registered Trade Mark.

**Catering to your particular  
service and production requirements**

# Speciproduct

**Our range includes:**

**Aerosol Aids:** From Kontakt, Antistatik spray—cold spray—Fluid spray—Graphit spray—Oil spray—Plastik spray—Soldering Lacquer—Switch and contact cleaners—Video spray for cleaning tape heads.

**Allen & Bristol Keys:** L Type. Standard and Long Arm.

**Contact Cleaners:** Diacrom Diamonded Spatulas and Kontakt aerosols.

**Nutdrivers:** Hex—A.F.—Metric. Solid and hollow shaft and Palnut.

**Pliers Seizers & Nippers:** Quality Precision made hand tools from Xcelite, and other leading producers of special tools.

**Screwdrivers:** Allen—Ball head—Bristol—Clutch head—Hold-e-Zee-Phillips and slotted.

**Soldering Equipment:** Resistance and heat controlled units. Also thermal wire stripping equipment from American Beauty and Waseco.

**Tweezers:** Quality Swiss made electronic tweezers.

**Ultrasonic Cleaners:** Bench models and accessories from American Beauty.

**Work Positioners:** The versatile Panavise 300 series for modern precision and allied industries.

**Work Viewers:** Distortion free Ednalite viewers and optical glass lenses for single and group viewing.


For catalogues and other information on the above write.

Special Products Distributors Ltd  
81 Piccadilly, London W1V 0HL  
Tel: 01-629 9556 Cables: Speciproduct London W1

WW—053 FOR FURTHER DETAILS
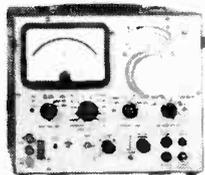
## Hatfield are on the level...

with the new Hatfield Selective Level Measuring Set comprising Level Meter 1001 and Level Oscillator 1003 you can measure cross talk attenuation to 115dBm.



Two light weight units provide level measurements at any audio frequency in 140 and 600 systems, even in the presence of other signals.

Measurements range: +25 dBm to -115 dBm  
Frequency range: 30 MHz. to 30 KHz.  
Oscillator output range: +21 dBm to -105 dBm

Send for full details of Hatfield Selective Level Measuring Set and a copy of our Short Form Catalogue.

**HATFIELD**  
forward thinking  
in electronics

**HATFIELD INSTRUMENTS LIMITED**  
Burrington Way, Plymouth PL5 3LZ, Oevon.  
Tel. Plymouth (0752) 72773/4 Grams: Sigjen, Plymouth. Telex: 45592  
South-East Asia: for prompt service and deliveries, contact:  
Hatfield Instruments (NZ) Ltd., P.O. Box 561, Napier, New Zealand.

WW—054 FOR FURTHER DETAILS



STOCKISTS



MULTIMINOR MK. IV

**REPAIR SERVICE  
7-14 DAYS**

We specialise in repair, calibration and conversion of all types of instruments, industrial and precision grade to BSS.89.

Release notes and certificates of accuracy on request.



MODEL 8 MK. III

Suppliers of Elliott, Cambridge and Pye instruments

**LEDON INSTRUMENTS LTD**

76-78 DEPTFORD HIGH STREET, LONDON, S.E.8

Tel.: 01-692 2689

G.P.O. APPROVED

CONTRACTOR TO H.M. GOVT.

WW—055 FOR FURTHER DETAILS

# Plessey CT80 at the BBC

and I.T.A., A.T.V.  
Radio Luxembourg  
Scottish Television  
Ulster Television  
and  
Nederlandse Omroep Stichting

The Plessey CT80 Cartridge Recorders shown here are installed in the World Service Continuity Studio of the B.B.C. External Services Studio Centre at Bush House, London. From this centre broadcasts originate to all English speaking regions of the world including South-East Asia and Australia. The studios are in operation twenty-four hours a day and the CT80 units are used for both programme material and standby announcements. Having met the specification requirements of the B.B.C. the CT80 Recorder is now demonstrating its reliability in operational service.



**PLESSEY**  
**Electronics**



Sales and Service — Hayden Laboratories Limited East House  
Chiltern Avenue Amersham Bucks Service Department 12 Poland Street  
London W1Y3DE Telephone 01.734 3748-9 — or the manufacturer  
Plessey Electronics Pty Limited Equipment Unit The Boulevard  
Richmond Australia 3121 Telex 30383 Cables ROLA Melbourne


# JACKSONS

Radio and Electronic Components  
(Made in England)
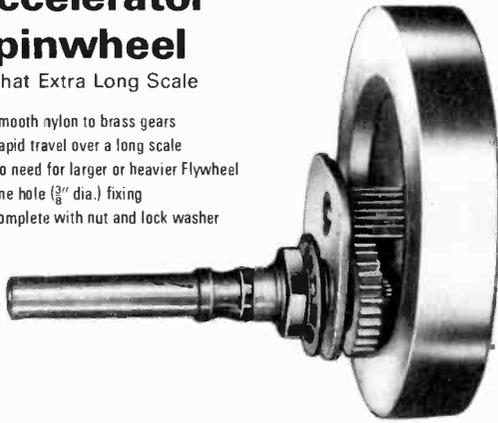
## Accelerator Spinwheel

for that Extra Long Scale

- ★ Smooth nylon to brass gears
- ★ Rapid travel over a long scale
- ★ No need for larger or heavier Flywheel
- ★ One hole ( $\frac{3}{8}$ " dia.) fixing
- ★ Complete with nut and lock washer



The latest addition to the JACKSON range of

## P.T.F.E. Dielectric Tubular Trimmers

- ★ Several models available
- ★ UHF Tuning
- ★ Panel mounting, Vertical P.C. Board Mounting or Horizontal P.C. Board Mounting
- ★ Varic's capacities: from 1/4 pF—8pF to 2pF—30pF
- ★ Power factor less than .0005 at 1MHz
- ★ High Test Voltage




Style 330 H.P.C.  
P.T.F.E. Trimmer 30pF  
Cat. No. 4252/HPC
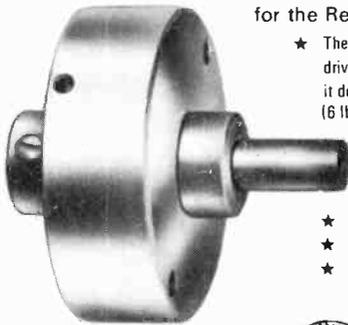
## Heavy Duty Epicyclic Drive

for the Really Heavy Job

- ★ The main housing of this powerful friction drive is only  $1\frac{1}{2}$ " diameter and  $\frac{1}{2}$ " deep yet it delivers an output torque of 100 oz. ins. (6 lb. ins.).



- ★ The reduction ratio is 6:1
- ★ The complete assembly weighs only 3 oz.
- ★ Essential parts are hardened and ground to provide long life.



It's reliable if it's **made by Jackson!**

Write for literature  
**JACKSON BROTHERS (London) LTD.**

DEPT. W. W. KINGSWAY, WADDON  
CROYDON, CR9 4DG

Phone: 01-688 2754-5 Grams: Walfilco, Croydon

U.S. office: M. Swedgal, 258 Broadway, N. York, N.Y. 10007

WW—057 FOR FURTHER DETAILS

# BOOKS BY G.A. BRIGGS

OVER A QUARTER OF A MILLION COPIES SOLD SINCE 1948

## LOUDSPEAKERS

Fifth edition—336 pages, 230 illustrations.  
Cloth bound.

PRICE **£1.50 (£1.63 post free)**.

A standard work on the subject of loudspeakers, now in its 24th impression.



## CABINET HANDBOOK

112 pages, 90 illustrations. PRICE **38p**  
(**46p post free**). Semi-stiff cover.

Cloth bound **75p (85p post free)**.

Practical information about woodworking, veneering, polishing, etc., plus 22 pages on loudspeaker cabinet design.



## AERIAL HANDBOOK (Second Edition)

176 pages, 144 illustrations.

PRICE (Semi-stiff cover) **75p (83p post free)**.

Cloth bound **£1.13 (£1.23 post free)**.

This revised edition includes explanations and requirements relating to colour TV and Multiplex stereo.



## MUSICAL INSTRUMENTS AND AUDIO

240 pages, 212 illustrations. Cloth bound.

PRICE **£1.63 (£1.76 post free)**.

Intended to appeal to both the concert-goer and the audiophile.



## ABOUT YOUR HEARING

132 pages, 112 illustrations.

PRICE (semi-stiff cover) **78p (86p post free)**

Cloth bound **£1.13 (£1.23 post free)**.

Many aspects of audiology, age and noise effects are expertly covered, with guidance for the hard of hearing.



## AUDIO BIOGRAPHIES

344 pages, 64 contributions from pioneers and leaders in Audio. 112 illustrations. Cloth bound.

PRICE **£1.25 (£1.38 post free)**.

Vital information on the development of radio, audio, hi fi, etc., from the early days up to 1961.



## A TO Z IN AUDIO

224 pages, 160 illustrations. Cloth bound.

PRICE **78p (88p post free)**.



## PIANOS, PIANISTS AND SONICS

190 pages, 102 illustrations. Cloth bound.

PRICE **92p (£1 post free)**.



All the above books contain the usual touches of humour associated with this writer.

Please send orders and enquiries to:

**RANK WHARFEDALE BOOK DEPT. B.W.S.**

**13 WELLS ROAD ILKLEY YORKS LS29 9AZ**

Telephone: ILKLEY 4246

Published by:

**RANK WHARFEDALE LTD., IDLE, BRADFORD, YORKS.**

WW—058 FOR FURTHER DETAILS

# VARIABLE TRANSFORMERS ARE ALWAYS AVAILABLE FROM STOCK AT THE LOWEST PRICES



Fully shrouded variable transformers—input 250VAC output 0-260VAC

- |               |               |
|---------------|---------------|
| 1 amp £6.50   | 10 amp £21.35 |
| 2.5 amp £7.80 | 12 amp £24.25 |
| 5 amp £11.30  | 20 amp £45.00 |
| 8 amp £16.75  |               |



Constant voltage transformer stabilises mains voltage to  $\pm 1\%$  output 240VAC  $\pm 1\%$  input 240VAC  $\pm 20\%$  capacity 250 Watts price £12.50 with quantity discounts



New solid state variable voltage control input 240VAC output 25-240VAC

- |               |
|---------------|
| 5 amp £9.50   |
| 10 amp £15.15 |




U.K. SPECIALISTS IN AUTOMATIC CONTROLS & SWITCHING

313 Edgware Rd., London W.2  
Telephone 01-723 2231

WW—059 FOR FURTHER DETAILS

## We're sensitive to everyone's needs.

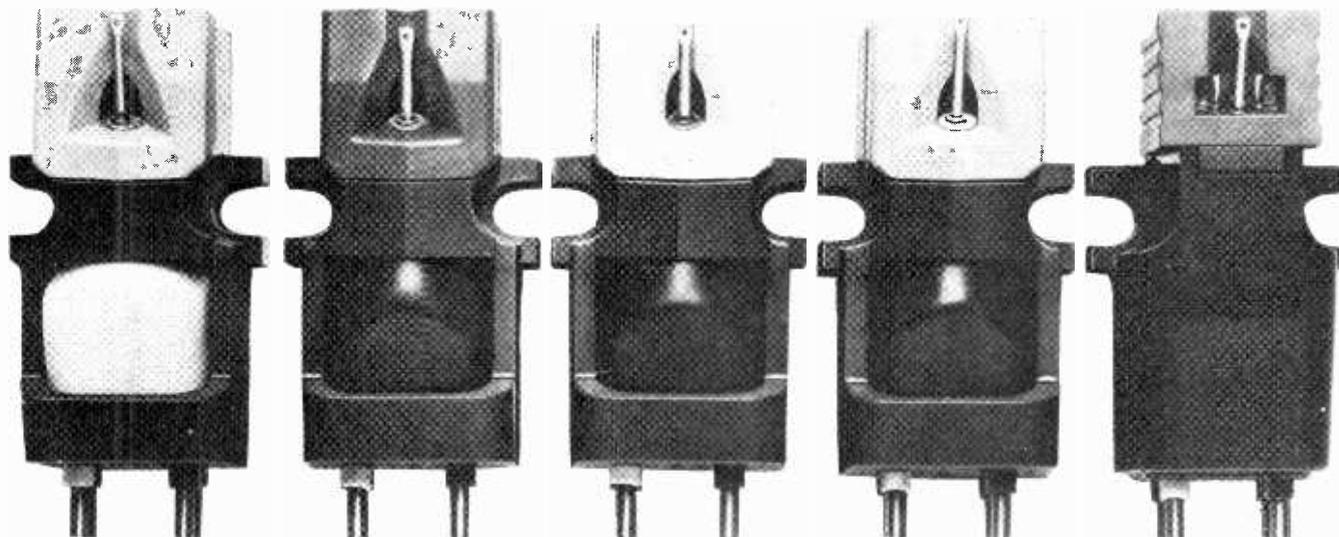

Different people have very different requirements in Hi-Fi, so Goldring developed a comprehensive range of stereo magnetic cartridges that are superb in performance and realistic in price.

From the G800 Super E for those who seek perfection down to the G850 for systems on a budget, the Goldring range offers unsurpassed quality and value.

Your request will bring full details of these and other Goldring products.

Goldring Manufacturing Company (GB) Limited,  
10 Bayford Street, Hackney, London E8 3SE.  
Tel; 01-985 1152.

# Goldring Series 800


Stereo Magnetic Cartridges.

WW—060 FOR FURTHER DETAILS
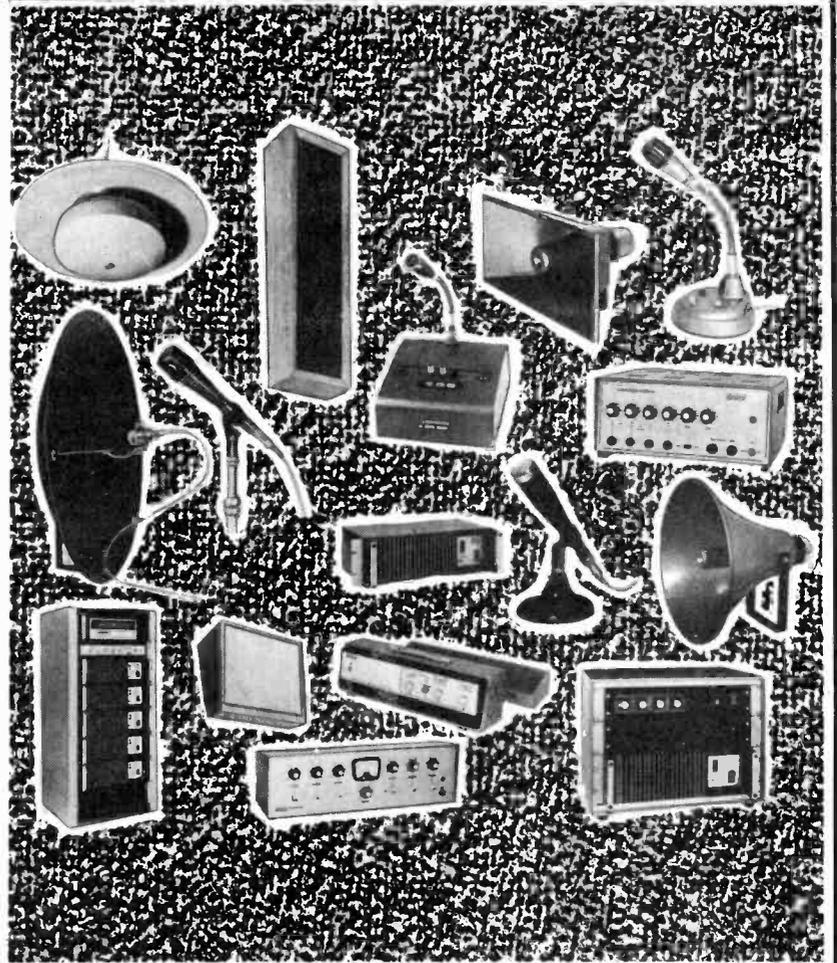
# Grampian

All these current items  
and many more!  
Design and quality from  
forty years of experience  
in equipment for  
sound systems.

**Grampian**  
SOUND EQUIPMENT  
GRAMPIAN REPRODUCERS LTD  
Hanworth Trading Estate  
Feltham, Middlesex  
Telephone: 01 894 9111



JACW/S/125

WW-062 FOR FURTHER DETAILS

MON.1.

## AUDIO SUPPLIES

**SLASH PRICES up to 60%**

### SUPERB PLINTHS AND COVERS

£3.25 p. & p. 50p

Suitable for Garrard AT60, SP25, 2000, 2500, 3000, 3500, 5100, 2025, 1025, SL65B and B.S.R. McDonald range. Superbly finished plinth, ready cut for use (fully assembled). Complete with tinted perspex cover. This unit is finished in Teak polish and will blend in any home. Please state deck when ordering.

**SUPERIOR PLINTHS AND COVERS**  
For Garrard AP75, AP76, SL72B, SL75B and SL95B (Recommended list price £10.00). Our price £4.50 + 60p p. & p.

### TURNTABLES p. & p. 75p

GARRARD 2025TC with Sonatone 9TAHC cartridge ..... £8.75  
GARRARD 40B with Sonatone 9TAHC cartridge ..... £11.00  
GARRARD A70 Mk. II ..... £10.50  
GARRARD SP25 Mk. II ..... £11.00  
GARRARD SL65B ..... £13.50  
GARRARD AP76 ..... £19.00  
GARRARD SL75B ..... £25.50  
GARRARD SL95B ..... £34.00  
GARRARD 401 ..... £27.50  
B.S.R. MP60 ..... £11.75  
Thorens TD150AB Mk. II ..... £42.50

### CARTRIDGES p. & p. Free

GOLDRING G850 ..... £4.50  
GOLDRING G800 ..... £7.00  
GOLDRING G800/E ..... £11.00  
SHURE M3D ..... £4.75  
SHURE M75E ..... £14.50  
SHURE M55E ..... £9.00  
AUDIO TECHNICA AT66 ..... £4.75  
SONATONE 9TAHCD ..... £1.75

### SPECIAL OFFERS

A VICEROY VA4 COMPLETE STEREO SYSTEM For ONLY £38.00 p. & p. £1.25

GARRARD SP25 Mk. II GOLDRING G800 H Plinth and cover complete OUR PRICE £19.00 p. & p. £1.00

ARMSTRONG 526 GARRARD AP 76 SHURE M55E Plinth and cover complete STE-MA 400 speakers OUR PRICE £148.00 p. & p. £1.25

### AMPLIFIERS p. & p. £1

ARMSTRONG 521 ..... £43.00  
AMSTRAD 8000 ..... £17.75  
H.L. SA707 ..... £18.95  
TELETON SAQ206 ..... £19.00  
VICEROY AS70 ..... £42.00  
VICEROY 55 ..... £18.00  
SANSUI in stock ..... £22.50  
METROSOUND ST20 ..... £25.00  
SINCLAIR 2000 ..... £33.50  
SINCLAIR 3000 ..... £43.50  
SINCLAIR NEOTERIC ..... £46.00  
SINCLAIR A.F.U. ..... £4.50  
SINCLAIR STEREO 60 x 2230/PZ5 ..... £18.50

### SPEAKER KITS p. & p. £1

WHARFEDALE UNIT 3 ..... per Dr. £28.00  
WHARFEDALE UNIT 4 ..... £39.00  
RICHARD ALLAN TWIN ASSY. .... £16.00  
RICHARD ALLAN TRIPLE ASSY. .... £28.00  
RICHARD ALLAN SUPER TRIPLE ..... £33.00

**EASY TO FIND.** 50 yards from (B.R.) Stoke Newington Station. 67, 149, 247, 76, 243 Buses pass our door.

**OPEN.** Monday-Wednesday 9.30 a.m. to 7 p.m. Half day Thursday until 1 p.m. Late night Friday until 8 p.m. SATURDAY 9.30 a.m. to 6 p.m.

All prices subject to change without notice.

Many more items in stock. For full list send s.a.e.

**AUDIO SUPPLIES LTD.** Dept. WW8, 50 STAMFORD HILL, LONDON N16. 01-806 3611/7311.

Personal callers please note that cheques are only accepted if accompanied by a bank cheque card. (NOT BARCLAYCARDS)

WW-061 FOR FURTHER DETAILS

## PARKER SHEET METAL FOLDING MACHINES



Forms channels and angles down to 45 degrees which can be flattened to give safe edge. Depth of fold according to height of bench.

One year's guarantee. Money back if not satisfied.

Send for details:

**A. B. PARKER**

FOLDING MACHINE WORKS, UPPER GEORGE STREET, HECKMONDWIKE, YORKS.

Telephone 3997


36" x 18 gauge capacity ..... £30.00  
24" x 16 gauge capacity ..... £29.00  
Carriage Free

Also the well-known vice models of  
36" x 18 gauge capacity ..... £15.00  
24" x 18 gauge capacity ..... £10.00  
18" x 16 gauge capacity ..... £10.00  
Carriage Free

WW-063 FOR FURTHER DETAILS
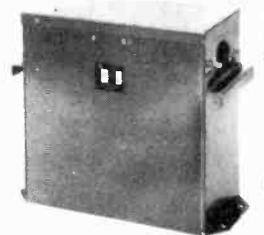
## ENCAPSULATION

low tool cost method of cylindrical coils and potting. Enquiries also for:—




**REED RELAYS**  
**SOLENOIDS**  
**COIL WINDING**  
**TRANSFORMERS**  
to 10 K.V.A.

3 phase 'Polyweb' encapsulated transformer. As low as £9.30 per RVA.

**R. A. WEBBER LTD.**


9 Knapps Lane, Bristol 5. 0272 657228

WW-064 FOR FURTHER DETAILS

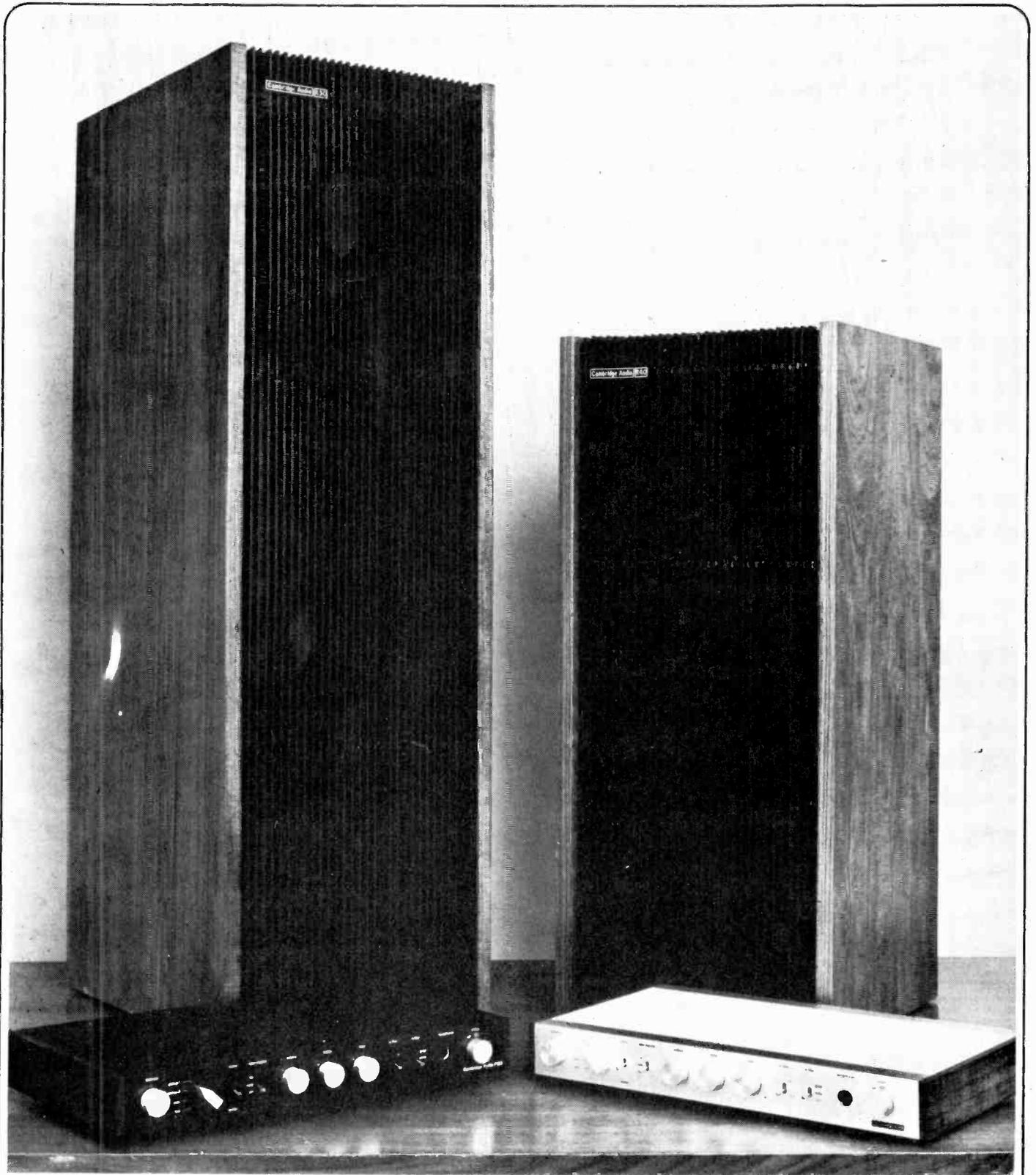

Recommended retail prices: R50 Loudspeaker £98, R40 Loudspeaker £65, P100 Amplifier £145, P50 Amplifier £38

# Cambridge Audio

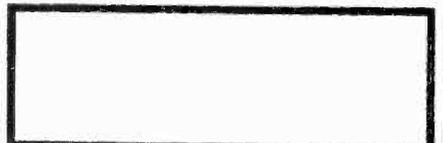

Cambridge Audio Laboratories Limited, The River Mill, St. Ives, Huntingdon PE17 4EP

telephone St. Ives (04306) 2901

WW—065 FOR FURTHER DETAILS

# Enhancing our image

In 1969 Telequipment introduced the D53S which was universally acclaimed as the world's first realistically-priced true dual-beam storage oscilloscope. Now Telequipment announce the DM53A - with all the features of the D53S and the added advantages of variable enhancement and the remote control of Erase and single shot time base Reset.

The tube circuitry provides five alternative conditions of operation:

- (a) Normal: P31 characteristics as in a conventional non-storage oscilloscope.
- (b) Variable Persistence: Provides continuous control from 0.2 second to more than 1 minute.
- (c) Storage (without enhancement): As a storage oscilloscope, it is capable of storing traces for periods of up to 10 minutes.
- (d) Store (with variable enhancement): The writing speed may be increased up to about ten times.
- (e) Hold: Retention time of image written in the store condition is prolonged up to one hour.

A choice of differential, ultra high gain, or wide band with Signal Delay plug-in Y amplifiers, makes the DM53A capable of meeting almost any measurement requirement.


Send for full details now and see just how great is the value offered in the Telequipment DM53A. U.K. Prices: £490-£556, depending on choice of amplifiers.



**TELEQUIPMENT** 

Telequipment, 313 Chase Road, Southgate, London, N.14 6JJ. Telephone: 01-882 1166  
A division of Tektronix U.K. Ltd.

WW-066 FOR FURTHER DETAILS

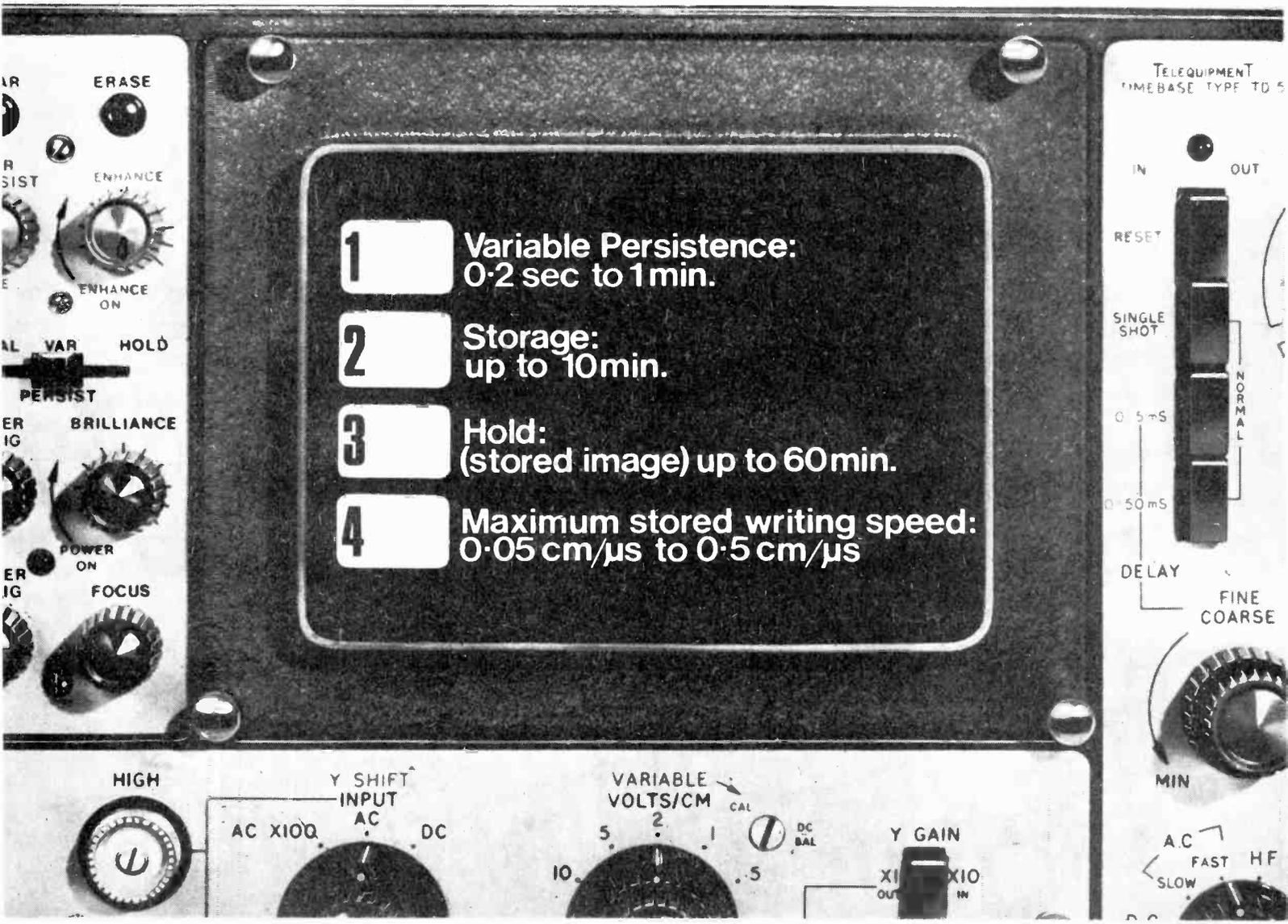

# Wireless World

Electronics, Television, Radio, Audio

Sixty-first year of publication

August 1971

Volume 77 Number 1430



The rotating 11-dB helical aerial, shown on the front cover, forms a major part of receiving equipment for picture transmission from weather satellites. It was designed and manufactured by Rohde & Schwarz, of Munich, whose U.K. agents are Aveley Electric.

## IN OUR NEXT ISSUE

Constructional details of a helical aerial of unusual design covering the 88-170 MHz band.

Swept-frequency audio oscillator in which two decades are covered in one band using a beat-frequency technique.



I.P.C. Electrical-Electronic Press Ltd

Managing Director: George Fowkes

Publishing & Development Director:  
George H. Mansell

Advertisement Director: Roy N. Gibb  
Dorset House, Stamford Street, London, SE1

© I.P.C. Business Press Ltd, 1971

Brief extracts or comments are allowed provided acknowledgement to the journal is given.

## Contents


- 361 Wasted R&D?
- 362 Double-trace Oscilloscope Unit—1 by *W. T. Cocking*
- 365 Announcements
- 366 Ten Practical Source-follower Circuits by *J. O. M. Jenkins*
- 368 Simple Crosshatch and Dot Generator by *A. W. Critchley*
- 371 Square-root Circuit by *B. L. Hart & A. Cheetham*
- 372 News of the Month
- 374 Letters to the Editor
- 377 Phase-locked-loop Stereo Decoder I.C.
- 379 Ceramic Pickup Equalization—2 by *B. J. C. Burrows*
- 383 The Diagnosis of Logical Faults (concluded) by *R. G. Bennetts*
- 386 Circuit Ideas
- 387 Electro-optical Gearbox by *Jack Dinsdale*
- 388 H.F. Predictions
- 389 Touch-switch Controller by *R. Kreuzer*
- 390 Electronic Building Bricks—14 by *James Franklin*
- 391 Charging by *'Cathode Ray'*
- 393 Single-sideband Experimental Broadcasts
- 394 Telephone Exchanges of the Future
- 395 Elements of Linear Microcircuits—10 by *T. D. Towers*
- 398 Conferences and Exhibitions
- 399 Complementary Darlington Output Transistors in Audio Amplifiers
- 400 Automatic Titration Potentiometer by *D. R. Bowman*
- 401 Sixty Years Ago
- 402 World of Amateur Radio
- 403 Personalities
- 404 Literature Received
- 405 New Products
- 410 Real & Imaginary by *'Vector'*
- A85 APPOINTMENTS VACANT
- A98 INDEX TO ADVERTISERS

Published monthly on 3rd Monday of preceding month, 17½p (3s 6d).

Editorial & Advertising offices: Dorset House, Stamford Street, London S.E.1. Telephone 01-928 3333. Telegrams/Telex, Wiworld Bispres 25137 London. Cables, "Ethaworld, London S.E.1."

Subscription & Distribution offices: 40 Bowling Green Lane, London E.C.1. Telephone 01-837 3636. Subscribers are requested to notify a change of address four weeks in advance and to return envelope bearing previous address.

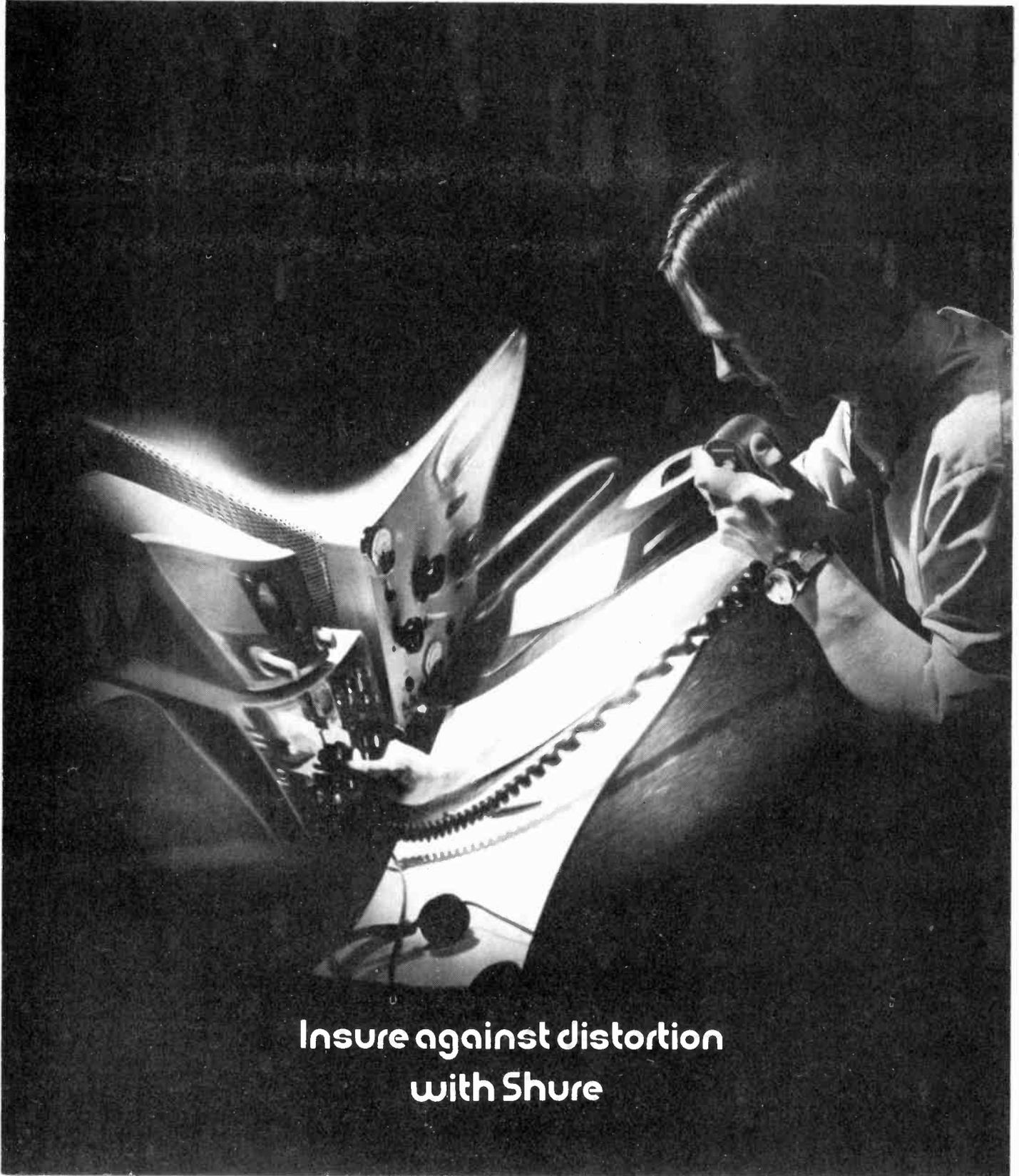Subscription rates: *Home*, £4.00 a year. *Overseas*, 1 year £4.00; 3 years £10.20 (U.S.A. & Canada 1 year \$10, 3 years \$25.50).



**Insure against distortion  
with Shure**

**Shure Model 444—**  
Controlled magnetic  
microphone. Specially  
designed for radio  
communications applications.  
Special response  
characteristic gives optimum  
speech intelligibility.



ww6

Please send me full information on  
Shure Communications Microphones.

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_



**SHURE**

Shure Electronics Ltd.  
84 Blackfriars Rd., London SE1. Tel: 01-928 3424

# Wireless World

**Editor-in-chief:**

W. T. COCKING, F.I.E.E.

**Editor:**

H. W. BARNARD

**Technical Editor:**

T. E. IVALL, M.I.E.R.E.

**Deputy Editor:**

B. S. CRANK

**Assistant Editors:**

J. GREENBANK, B.A.

G. B. SHORTER, B.Sc.

**Drawing Office:**

L. DARRAH

**Production:**

D. R. BRAY

**Advertisements:**

 G. BENTON ROWELL (*Manager*)

G. J. STICHBURY

 B. STOREY (*Classified Advertisement Supervisor*)

Telephone: 01-928 3333 Ext. 533 &amp; 246.

 G. DONOVAN (*Classified Advertisements*)

## Wasted R & D

One aspect of research and development costs which we did not consider in our discussion on value for money in R & D in the June issue is highlighted in a report just issued by the Centre for the Study of Industrial Innovation\*. It is called 'On the Shelf' and surveys industrial R & D abandoned for non-technical reasons. The main conclusion of the survey, which analyses 53 shelved projects belonging to 20 companies in the UK, is that the failure to make an adequate market assessment before research and development is the most common reason for firms having to abandon technically viable projects. Eight of the companies or divisions (mostly unnamed) are classified as 'electrical and electronics' and, in fact, a third of the 53 abandoned projects were electronic. Incidentally, the nationality of five of the eight companies is given as U.S., one European and two U.K. Together they employ about 1,500 graduate R & D staff and about the same number of technicians and support staff. Details are given of case studies (some under disguised names) and together they raise important questions central to the management of R & D. With hindsight, some projects should never have been started; in others development resources were exhausted beyond the point of economic justification.

There are apparently three main points of project rejection, which can occur for technical or non-technical reasons. Projects can fail first to measure up to initial selection criteria for development expenditure; secondly, to measure up to criteria of satisfactory development at a periodic progress review; and thirdly, a fully developed prototype can fail to measure up to the conditions required for marketing. Probably most of the projects described in the report were rightly shelved, although we question the attitude of one research director interviewed who stated that the onus is on the individual at the bench to force his own project through; 'He must know how to sell, what to sell, when to sell and who to sell to'. This attitude which, according to the survey is not untypical of research directors and other senior personnel interviewed, lays a tremendous burden on the initiators of a project and may well inhibit progressive thinking.

One of the aims of the study was to assess what steps firms took after the 'shelving' decision to gain some commercial return from the accumulated, but abandoned, know-how. It is this aspect of shelving which we consider is of paramount importance, for it can turn to good effect what would otherwise be wasted R & D. Of the 53 shelved projects reviewed only six were subsequently economically exploited by three of the 20 companies. Sometimes the resurrection occurred as a result of changed circumstances but only one firm, incidentally Rolls-Royce, had a regular system of project reappraisal. While this aspect of research should not be overlooked by individual companies, it is of paramount importance to organizations undertaking research on behalf of others. In this regard we were particularly interested to learn during a recent visit to the Cranfield Unit for Precision Engineering (see 'Electro-optical Gearbox' in this issue) that written into all its research contracts is a clause permitting the use in any field not competing with the originating company's activities of know-how resulting from research projects.

While it can be said that all R & D efforts contained an element of fruitless endeavour, there must come a point when this proportion is no longer acceptable as inevitable and it is seen that *avoidable* wastage has begun to occur.

\*The Centre for the Study of Industrial Innovation, of 162 Regent St, London W1R 6DD, was set up last year, with industrial backing, to study the economics of innovation and R & D in industry. 'On the Shelf' is its first report.

# Dual-trace Oscilloscope Unit—1

by *W. T. Cocking\**, F.I.E.E.

In this series of articles the development of a unit which enables two signals to be observed simultaneously on almost any cathode-ray oscilloscope will be described and the series will conclude with full details of the final design. In all design work there is compromise and it is necessary to obtain a good balance between conflicting requirements. Sometimes there are several different ways of obtaining a required performance and a designer naturally starts by considering the one which he thinks most likely to be satisfactory. Sometimes, his first choice is a good one; at others, he ends up with something entirely different.

Usually, he says little or nothing about his unsuccessful attempts and only his successful design is presented for all to see. It occurred to the writer that a detailed account of the development, including the unsuccessful arrangements, would be of general interest and might be of some educational value. It is usually true that one learns more from one's mistakes than from one's successes. It might be true that one could learn more from other people's mistakes than from their successes, if one knew about them!

If the course of the development, a great variety of problems was met and some were a little unusual. For example, a continuous control of gain was considered desirable and provided by far the most difficult of all problems. In fact, the final choice of circuit was made almost entirely to suit the requirements of gain control.

## Requirements

The first step in design is always to formulate the requirements clearly. The designer does this in the light of his experience of what is practicable. He knows, for instance, that it will probably be difficult to obtain a voltage amplification of 100 times with a bandwidth of 25 MHz from two transistors. He knows, too, that it will probably be easy to obtain a gain of 4 times with a bandwidth of 10 MHz from only one transistor and that it might not be too hard to get a gain of 10 times. The designer has this sort of information available from his past experience but there are always gaps in his knowledge, and then he has to carry out some experiments to see what can be done,

or else a theoretical analysis. This usually takes longer, but is generally more valuable.

Coming now to the particular (that is, to the dual-trace unit), the first thing is to decide what it must do. Its purpose is to enable two different signals to be displayed so that they can be viewed simultaneously on the screen of the c.r.o. They cannot, of course, be actually present simultaneously, for the tube has only one electron beam. There must be two separate signal channels and an electronic switch to switch the input of the c.r.o. from one to the other and back again repeatedly at an adequately high speed. Persistence of vision coupled with the persistence of the c.r.t. screen makes the traces appear to be present simultaneously.

Both traces are, of course, displayed by the same horizontal deflection of the beam, and so the two signals must be of the same frequency or harmonically related. Also, if the two traces are separated to appear one above the other, the maximum input to the oscilloscope for each signal can only be one half of the normal. The screen cannot be stretched to accommodate two normal size traces!

## Experiment

It is not necessary for the switching frequency to be synchronized to either the signals or to the oscilloscope timebase. Here, for brevity, we are anticipating a little. In reality, at this stage we did not know what would happen, so we rigged up an electronic switch and fed the same sinewave signal to both sides to find out what did happen. This is what we did find. For signals from about 200 Hz to perhaps 1 MHz the best results are obtained and the operation is easiest when the electronic switch is triggered by the oscilloscope timebase. No spurious effects are then observable, the two signals are displayed alternately on successive sweeps and the switching occurs during flyback. It was found, however, that for the display of higher frequencies, the timebase frequency became too high for the electronic switch to operate properly. It was found, too, that at lower frequencies flicker quickly became intolerable. The cure for both is the same, to use an unsynchronized switch. At low frequencies, the switching frequency is made much higher than the signal frequency. Switching occurs 100

times or more during each signal cycle. If, by accident, the frequencies are integrally related, or there is some unintentional synchronizing action by stray coupling, the traces appear dotted. Flicker is not now any worse than in a normal oscilloscope display. At high frequencies, the switching frequency is made much lower than the signal frequency. One signal is then displayed for ten or more sweeps before the other is switched on, but as long as the switching frequency is above a few hundred Hz one does not notice this.

Unsynchronized operation can be used for all signal frequencies, but peculiar effects occur at certain relations between the signal and switching frequencies. They are in the nature of stroboscopic effects and can be most disturbing. To minimize them the ratio of the frequencies must be very large or small and a fine control of switching frequency is necessary.

In the light of these early experiments it was decided that synchronized operation would be used for most signals, but that an alternative pulse generator would be provided for low- and high-frequency signals. It should be noted also that synchronized operation demands that the oscilloscope has a pulse or sawtooth output available from its timebase.

It was noticed, too, in the experiments that it is impossible to use the internal synchronization of the oscilloscope. With unsynchronized operation of the switch, the timebase invariably locks to the switch frequency and not to the signal.

On its most sensitive range the average oscilloscope needs no more than 1 V peak-to-peak of signal for full screen deflection. Many oscilloscopes need less. It was decided that the dual-trace unit should have an overall gain of unity, with a maximum signal output of 1 V. The oscilloscope used in the development was the Marconi Instruments TF 1330. This is now an oldish model but its performance is quite adequate for most general purposes. It has a 3-dB bandwidth up to 15 MHz and an input impedance of 1 M $\Omega$  shunted by 30 pF.

When using the dual-trace unit, the input attenuator of the oscilloscope cannot be employed unless the unit is made capable of handling large signal amplitudes. In any case, the two signals to be observed may have very different amplitudes. It follows that each channel must have its own input

\*Editor in Chief, *Wireless World*

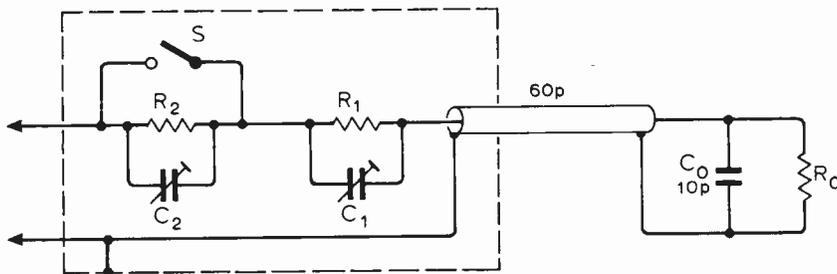


Fig. 1. A passive probe designed to give attenuations of 3.33:1 and 10:1 according to the position of the switch and to reduce the capacitance of the cable and oscilloscope in the same ratios.

attenuator. If it were not for one thing, amplification of the signals would be unnecessary. This thing is cable capacitance. A minimum of 3 ft of coaxial cable is needed for the input. If this is ordinary 75-Ω cable its capacitance will be about 60 pF. Special low-capacitance cable can be used, but is less readily available, and even then its capacitance is unlikely to be under 30 pF. The usual practice is to use a passive probe which attenuates the signal to  $\frac{1}{10}$  of the input and at the same time reduces the capacitance by the same amount. This is eminently practical, but necessitates an amplifier with a gain of 10 times to make up for the loss.

At this stage we did not know what gain and bandwidth would be practicable. We felt that the minimum requirement was a 3-dB bandwidth of 5 MHz and that it should be as much greater as proved reasonably practicable. We felt it might be hard to get a gain of 10 times with a bandwidth of more than this, and decided that a compromise was desirable. What we initially decided was this. There would be an input probe with an attenuation of 1/3.33. With a total cable plus unit input capacitance of 70 pF, this would give a probe input capacitance of  $70/3.33 = 21$  pF about. For the next range, a resistance would be switched in series to give an attenuation of 1/10, making the capacitance 7 pF.

The arrangement is sketched in Fig. 1, where  $R_0$  and  $C_0$  are the input resistance and capacitance of the dual-trace unit. The attenuation is

$$\frac{1}{\alpha} = \frac{R_0}{R_0 + R_1}$$

when the switch is closed and

$$\frac{1}{\alpha} = \frac{R_0}{R_0 + R_1 + R_2}$$

when it is open. If  $\alpha = 3.33$  and  $R_0 = 100$  kΩ,  $R_1 = 233$  kΩ and if  $\alpha = 10$ ,  $R_1 + R_2 = 900$  kΩ, whence  $R_2 = 667$  kΩ. These are non-standard values, but can be obtained from the combination of two or three preferred values. With an amplifier gain of 3.33 times, a 1-V input with S closed will give 1-V output. A 3-V input with the switch open will give  $(3/10) \times 3.33 = 0.99$  V = 1 V output.

The combination of this with one 10:1 attenuator in the unit would provide ranges of 1 V, 3 V, 10 V and 30 V, which would suffice for many, if not most requirements. The input resistance would be 333 kΩ on

the 1 V and 10 V ranges and 1 MΩ on the 3 V and 30 V ranges.

Frequency compensation of the potential divider requires that all time constants be alike. If the cable capacitance is  $C_c$ , this means

$$(C_0 + C_c)R_0 = C_1R_1 = C_2R_2$$

and there must be trimmers  $C_1$  and  $C_2$  in the probe to enable these capacitances to be adjusted precisely. Easy adjustment requires a square-wave signal of suitable repetition frequency. Adjustment is carried out for a square corner to the signal. If  $C_1$  or  $C_2$  in Fig. 1 is too small the square-wave has rounded corners as shown at (a) in Fig. 2, whereas if it is too large there is overshoot as at (c). The correct adjustment gives the square corners (b). If the input signal is a good one, the adjustment is remarkably easy to carry out.

A square-wave generator is not always available, of course, but the switching circuits of the dual-trace unit will, in fact, be operated by a square-wave generator and it was felt that this could be arranged to provide the signal for adjusting the attenuator. At this stage, this was merely noted as a possibility.

At this point it may be advisable to say why 100 kΩ was selected for  $R_0$ . It is usual for an oscilloscope to have an input resistance of 1 MΩ. This arose originally because this was about the highest stable value which could readily be provided with valve circuits. It is actually on the low side when the c.r.o. is used to investigate valve circuits, and a 10:1 probe is often used to

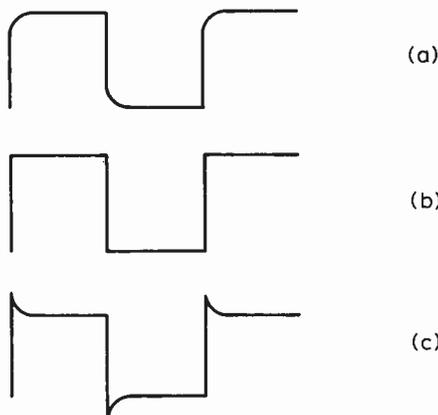


Fig. 2. With the capacitors  $C_1$  and  $C_2$  properly adjusted a square wave is correctly reproduced (b). Too small capacitance gives rounded corners (a) while too much capacitance gives overshoot (c).

bring it up to 10 MΩ when the signal is large enough.

Most transistor circuits are of a good deal lower impedance and 1 MΩ is ample for them. It is more important to reduce capacitance than to increase resistance. The use of high value resistors is to be avoided as far as possible because they are more likely to be unstable than lower values and are certainly more affected by surface leakage in damp weather.

It is important that the input resistance  $R_0$  be substantially defined by a resistor and not by a semiconductor. If  $R_0$  is 100 kΩ, this means that the input resistance of the first stage should not be less than 5 MΩ if its effect is to be small. This input resistance is usually highly variable. Of course, if a field-effect transistor is used a much higher input resistance is obtainable, but at this stage we had not decided which would be used and we initially chose values which would suit a bipolar transistor.

### Signal Control

It will be noted at this point that we had tentatively decided on an amplifier gain of 3.33 times because we thought that this should be easy to obtain. We note that the scheme worked out has two disadvantages. One is that, as already mentioned, the input impedance varies with the range. The other is the practical difficulty of including a switch, two resistors and two trimmers in a probe head without making it unwieldy. Further, with one range control on the probe and the other in the instrument, one must remember to note the setting of both to determine the actual range employed.

It would clearly be more convenient for the probe to give constant attenuation for then it need contain only one resistor and capacitor and the input impedance would be the same on all ranges viz. 1 MΩ and 7 pF. Two attenuators in the instrument would singly and in combination provide ranges of 1, 3, 10, 30 V; the attenuators having ratios of 3.33:1 and 10:1, under the control of a range switch. The possibility of this depends on being able to obtain a stable gain of 10 times from the amplifier with an adequate bandwidth, and at the start we did not know whether this was reasonably practicable. The gain control range required is, of course, unaltered and remains at about 3.5:1, for it has only to fill in the gaps in the attenuator steps.

Whatever the input stage, protection against overloading is required. Few transistors are rated for more than 6 V reverse base bias and there is always the possibility that the probe will be connected inadvertently to the 240 V supply mains of 340 V peak value or 360 V if 6% high. Protection is obtained by connecting two diodes back to back across  $R_0$ , as shown in Fig. 3. On the lowest range  $R_1$  is always in circuit and limits the current to  $360/233 = 1.54$  mA. This is the maximum diode current and few diodes will drop more than 1 V at this current.

The signal amplitude is 0.3 V p-p and we hope that, even without bias, silicon diodes will not conduct on it. The circuit

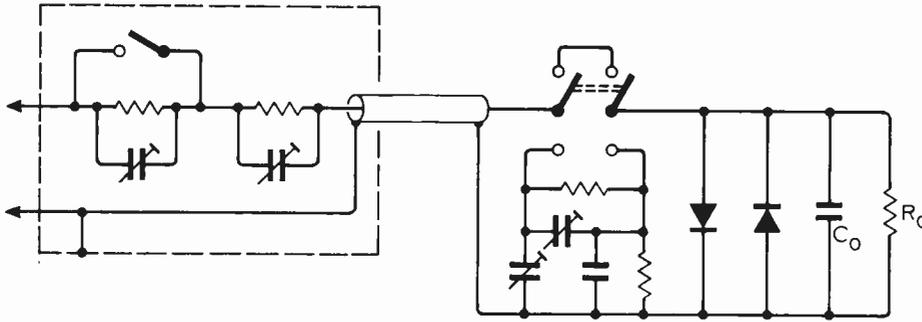


Fig. 3. This diagram shows the probe of Fig. 1 connected via the cable to a further attenuator of 10:1 ratio and diodes arranged to protect the amplifier against overloads.

has now grown to the form of Fig. 3.

One other decision had to be made. This was whether to make provision for a d.c. input. In any case, a series capacitor would be provided for a.c. only. The writer's experience is that a d.c. input is used only rarely and that when it is wanted it often cannot be used, because the same input range cannot be used for d.c. and a.c. together unless the two are comparable in magnitude. The input circuits become complicated if a bipolar transistor is used because of the base supply voltage. It was decided, therefore, to make provision for a.c. inputs only.

The capacitor can be inserted in series with the cable at the output end and the effective resistance is 333 k $\Omega$  on the 1 V and 10 V ranges and 1 M $\Omega$  on the 3 V and 30 V ranges. The drop in response (i.e., the sag) at a time  $t$  after the application of a unit step is simply  $t/CR$ . For a 50-Hz square wave,  $t = 10$  msec. If  $C = 0.5 \mu\text{F}$  and  $R = 333 \text{ k}\Omega$ , the sag is  $10^{-2}/(5 \times 10^{-7} \times 3.33 \times 10^5) = 1/16.65 = 0.06 = 6\%$ . This is as much as should be tolerated and 0.5  $\mu\text{F}$  is the minimum capacitance to be used. For a 1 M $\Omega$  input resistance, a 0.22  $\mu\text{F}$  capacitor can be used to give a sag of 4.5%.

For the initial experiments we did not build the full arrangement of Fig. 3 but used only the simplified system of Fig. 4. The probe must always be screened, of course, and for bench work it proved essential to screen the capacitor to prevent hum pick-up.

At this stage of the proceedings we had solved in principle the input circuit problems and could define the amplifier requirements more closely, which were:

1. To operate into an output load of 1 M $\Omega$  shunted by 55 pF (30 pF oscilloscope input capacitance plus 20 pF for 1 ft cable plus 5 pF strays)
2. To provide an output of at least 1 V p-p
3. To give a voltage amplification of 3.33 times (N.B. It was noted that if it should prove possible to obtain an amplification of 10 times this might be adopted and the attenuator system altered).

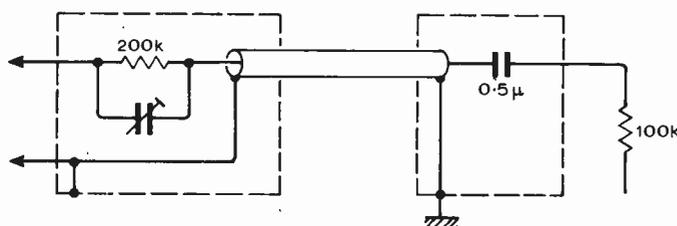


Fig. 4. Simplified probe used in experimental work, and input coupling capacitor to remove d.c.

4. To have a continuous gain control of at least 3.33:1.
5. To be able to handle an input of up to 1 V p-p (so that full output could be obtained with the gain control at minimum).
6. To include a shift control so that the traces could be moved vertically and independently on the screen. A range of  $\pm 0.5$  V at the output would be sufficient.
7. The gain and shift controls to have no interaction.
8. The whole amplifier to be stable and easy to set up.

With regard to the last item, it was considered that as this is a piece of test equipment, which will normally be used under laboratory conditions, it would suffice to take the temperature range as  $\pm 12.5^\circ\text{C} = \pm 22.5^\circ\text{F}$  about a mean of  $65^\circ\text{F}$ . This covers room temperatures of  $42.5 - 87.5^\circ\text{F}$ .

The mean room temperature is thus  $18.3^\circ\text{C}$ . The internal case temperature, which is the ambient of the transistors, is higher than this by what is at present a completely unknown amount, but it will vary with the room temperature and by the same amount. Transistor junctions will be higher than the ambient by an amount depending on their dissipation. Most small transistors have a thermal resistance between junction and case of about  $0.5^\circ\text{C}/\text{mW}$ . Anticipating a little, few, if any, transistors will dissipate more than 20 mW and so their junctions will not be more than  $10^\circ\text{C}$  above the ambient. No great attention need thus be paid to temperature.

In what follows, we shall assume at first that all junctions are at  $25^\circ\text{C}$  because this is the figure for which transistor characteristics are usually quoted. Corrections can be applied later. Because of the low power needed in this case, no dangerously high dissipation will occur, and the only important thing to watch is that the case is adequately ventilated. Apart from this the only effect of choosing the wrong design temperature is to change slightly the required bias voltages and as they may in any case have to be adjustable to allow for other

variations, the result is likely to be trivial.

Before concluding this part, it will be well to say something about the output stage which is controlled by the electronic switch. The arrangement referred to earlier, which was used for some experimental tests, is shown in Fig. 5. The transistors  $Tr_1$  are the output transistors of the two signal channels, and they are switched by  $Tr_2$  which have square waves applied in opposite phase to their bases; when  $Tr_{2a}$  conducts  $Tr_{2b}$  is cut off and vice versa.

When a  $Tr_2$  is cut off the  $Tr_1$  to which it is connected operates as a normal amplifier with collector load  $R_c$  and emitter resistor  $R_E$ . When a  $Tr_2$  is conductive it drains sufficient current through  $R_E$  to cut off the  $Tr_1$  to which it is connected.  $Tr_{1a}$  and  $Tr_{1b}$  have a common load resistor  $R_c$  and in this way the signals from the two channels are alternatively routed to the oscilloscope.

The oscilloscope input capacitance is about 30 pF and 1 ft of coaxial cable adds 20 pF. With 5 pF for strays, the total capacitance is 55 pF. If  $R_c$  is 330  $\Omega$ , then at 5 MHz, the response is

$$-20 \log [1 + \omega^2 C^2 R^2]$$

$$= -10 \log [1 + 0.57^2] = -1.22 \text{ dB.}$$

At 10 MHz, it is  $-3.61 \text{ dB}$ . This is very reasonable as a starting point.

If  $R_E = R_C$  the gain will be unity, or nearly so.

With a minimum supply of 10.5 V, maximum output demands that  $V_{CE}$  be one-half of the supply voltage and so  $I_C = 5.25/0.66 = 7.95 \text{ mA}$ . The emitter is then 2.625 V above earth and the base about 0.65 V higher, or about 3.3 V. The maximum signal output will then approach 5.2 V p-p. The collector dissipation will be  $5.25 \times 7.95 = 41.8 \text{ mW}$ . Each transistor  $Tr_1$  operates for only 50% of the time, however, so each has a mean current of 4 mA and a mean dissipation of 21 mW in round figures.

Experimentally, it was found unnecessary to operate at quite such a high current and the decision was made to set  $V_B$  at 2.7 V,

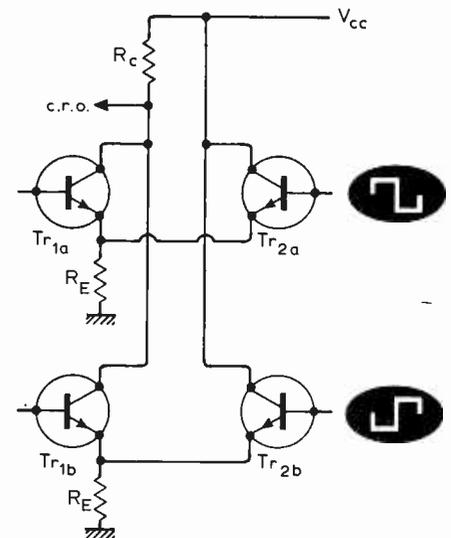


Fig. 5. This diagram shows the two output stages  $Tr_1$  of the two signal channels. These are turned on and off alternately by transistors  $Tr_2$  which are in turn driven on and off by push-pull square waves on their bases.

making  $V_E = 2.05$  V, and  $I_C = 6.21$  mA. Consequently,  $V_{CE} = 10.5 - 4.1 = 6.4$  V and the dissipation is 39.9 mW. With  $V_{cc} = 13.5$  V, if  $V_E$  is unaltered the current is unchanged and so  $V_{CE}$  rises by 3 V to 9.4 V and the dissipation to 58.4 mW. The maximum mean dissipation is thus 29.2 mW.

Typically, the thermal resistance is  $0.5^\circ\text{C}/\text{mW}$ , and  $V_{BE}$  changes by  $2\text{mV}/^\circ\text{C}$ . Thus  $V_{BE}$  falls by  $1\text{mV}/\text{mW}$  for a constant ambient temperature. The change of mean dissipation with  $V_{cc}$  is  $29.2 - 21 = 8.2$  mW and so  $V_{BE}$  decreases by 8.2 mV when  $V_{cc}$  is at its maximum, and  $V_E$  rises by the same amount and  $V_{CE}$  drops by twice this, or 16.4 mV. The current rise is  $0.0082/0.33 = 0.0249$  mA. At  $V_{cc} = 13.5$  V, therefore,  $I_C = 6.235$  mA and  $V_{CE} = 9.4 - 0.0164 = 9.384$  V, making  $P_c = 58.5$  mW. The change is quite negligible.

The normal output is 1 V p-p maximum. It is desirable to design for twice this to ensure a factor of safety; this is  $1V_p$ . The base of  $Tr_1$  swings from 1.7 V to 3.7 V with respect to earth, since the bias is set at 2.7 V. To cut-off  $Tr_1$ , therefore,  $Tr_2$  must draw sufficient current through  $R_E$  to bring the emitter of  $Tr_1$  at least 3.7 V above earth. The current must thus be at least  $3.7/0.33 = 11.2$  mA. The BC107 transistor has a  $V_{EB}$  rating of 6 V maximum. Thus,  $V_E$  must not exceed  $6 + 1.7 = 7.7$  V and so  $I_{c2}$  must be under  $7.7/0.33 = 23.3$  mA.

If  $Tr_2$  is saturated with a high supply voltage (13.5 V),  $V_{CE2} \approx 0.2$  V, and the total resistance must be greater than  $13.3/23.3 = 0.57$  k $\Omega$ . A resistance of more than  $570 - 330 = 240$   $\Omega$  must be included in the collector circuit to limit the current. If the current is to exceed 11.2 mA on low supply voltage (10.5 V), the resistance must not be greater than  $10.3/11.2 = 916$   $\Omega$ , so the collector resistance must be under  $916 - 330 = 586$   $\Omega$ . This assumes that the base current is negligible, which may not be true under saturated conditions. We thus see that the collector resistance of  $Tr_2$  must lie between 240  $\Omega$  and 586  $\Omega$ , and 470  $\Omega$  would seem a suitable choice.

With a conventional bistable driving  $Tr_2$  at its base, the bistable output will vary from

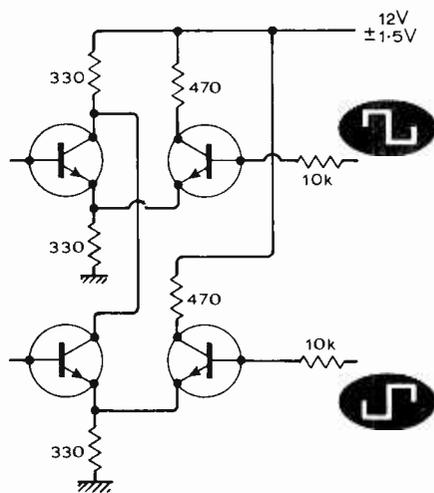


Fig. 6. The circuit of Fig. 5 redrawn with component values and protective resistors in the base and collector circuits of the switching transistors.

about 0.2 V to perhaps 2 V below  $V_{cc}$ . It may be less than this, but taking this figure, the maximum will be 11.5 V. The emitter voltage of  $Tr_2$  will be at least 3.7 V, so the effective base-emitter drive will be  $11.5 - 3.7 = 4.8$  V. If we arbitrarily limit the base current to 0.5 mA, a series resistor of  $9.6$  k $\Omega \approx 10$  k $\Omega$  must be placed in series with the base of  $Tr_2$ . The resistor can, in fact, be a little less than this because the above figure includes the output resistance of the bistable which is likely to be 1.5–2.5 k $\Omega$ .

The output stages and their switching transistors are shown in Fig. 6 with the above calculated circuit values. A final decision, of course, depends on a trial. We might find, for example, that 10 k $\Omega$  base resistors make the switching speed too low and we may have to think again.

So far the supply voltage has been considered but little. It is, however, obvious that with the low signal voltage no high voltage supply is needed. The output stage could, in fact, be designed for a 6-V supply. As will appear later, the amplifier really demands more and the decision was made quite early to adopt a nominal 12 V supply. It was desired to avoid a stabilized supply and so a tolerance of  $\pm 1.5$  V on the supply was allowed. It was thought that this would be sufficient to cover a  $\pm 6\%$  mains voltage and component tolerances.

## High-speed cassette duplicator

A tape speed of 1.9m/s (75 i.p.s.) is used in a new cassette duplicating system, intended for schools, libraries and the like which is being produced by Ampex. The equipment consists of a master unit which plays back the master tape to five slave duplicating units. Each duplicating unit will handle 45, sixty-minute playing time cassettes, in one hour; all tracks are duplicated at the same time. The sequence of events goes something like this: With a cassette in position a slave unit will carry out the recording in 45 seconds; it then takes 17 seconds to rewind the tape which is done at 3.8m/s (150 i.p.s.); finally the cassette is ejected and a new one is automatically loaded, accounting for a further five seconds. The system, which has five slave units, will therefore produce five duplicated cassettes every 67 seconds.

The tape transports employ vacuum servo columns. The tape is pulled out of the cassette into vacuum chambers and against the heads. The result is close tape-to-head contact and precise and gentle tape handling despite the very high tape speed. The bandwidth of the electronics is 320kHz.

## Announcements

An S-band air surveillance radar, the AR-15, has been introduced by Plessey which replaces the AR-1 introduced in 1965, of which over 100 (valued at approximately £10M) are now in service throughout the world. The AR-15 is available in both static and air transportable versions. It uses fully variable polarization, low noise parametric amplifiers, tunable magnetrons, digital moving target indication, background averaging techniques for clutter suppression, and multi p.r.f. integration for best target response.

Ericsson Marine, the newly formed marine communications department of the Ericsson Group, has set up a marine training school for ships' radio officers at the Norway Trade Centre in Pall Mall London. The first three-week course, for Cunard officers, began on 5th July. Initially, courses will be confined to experienced ships' radio officers and electronic technicians to familiarize them with the company's equipment.

A new collective call sign, GZ XV, has been allocated to Ericsson Marine. It will be principally used to facilitate 'all ships' calls in the operation of the Ericsson Marine service to shipowners.

A course of eight evening lectures on video recording systems starts at Norwood Technical College, Knight's Hill, London, SE27. OTX. On 19th October. Fee £2.

The Service Division of Marconi Instruments Ltd has been appointed as an approved repair and calibration centre for the Salford Electrical Instruments range of multirange test instruments. Both companies are in the GEC Group.

Eight of Canada's major civil airports are to have Marconi 'bright' radar displays, type S3006, incorporated into their air traffic control systems. The value of the order is in excess of £100,000.

The Carrier Corporation, of California, has announced an agreement in principle for the acquisition of Reliance Controls Ltd, of Swindon, Wiltshire, formed in the 1930s. Bowmar Instrument Corp., of Fort Wayne, Indiana, at present own 55% of the Reliance share capital and Booker McConnell Ltd of London, 45%. The transaction will involve approximately £0.25M.

Hamlin Electronics Inc., reed switch manufacturers of Wisconsin, U.S.A., have acquired Inter-Market Services Ltd, and re-formed it as Hamlin Electronics Ltd. The new company will market the complete range of Hamlin reed switches and power packs in the U.K. and Scandinavia, as did Inter-Market Services.

Servicing of test gear of all types is offered by a new service introduced by S. C. Murison, 9 Leas Road, Warringham, Surrey CR3 9LN. (Tel.: 01-820 3830.)

Pye Telecommunications Ltd has appointed the Hallicrafters Company, of Illinois, exclusive U.S.A. distributor of its land mobile radio equipment.

UK Solenoid Ltd, rotary switch and contractor manufacturers, are moving from Hungerford, Berkshire, to 115 London Road, Newbury, Berkshire. (Tel: Newbury 5991.)

T.E.M. Sales Ltd, of Crawley, Sussex, have been appointed distributors for R.E.M. Inc., of California.

# Ten Practical F.E.T. Source-follower Circuits

by J. O. M. Jenkins\*, M.Sc.

Virtually every source-follower configuration can be covered from ten basic circuits, and by considering the related parameters a designer can obtain consistent performance despite inherent device variations. It is true to say that insufficient knowledge and a paucity of written matter has rather inhibited the use of f.e.t.s in circuit design. This is regrettable, as the high input impedance and low output impedance of the field-effect device suits it to impedance transformations with bipolars.

There are two basic connections for source followers—with gate feedback and without gate feedback, and for simplicity these are taken separately.

## Biasing without feedback


1. A self-bias arrangement in which the voltage drop across  $R_S$  biases the gate through  $R_G$ . Since no gate-to-source voltage ( $V_{GS}$ ) can be developed when  $I_D=0$ , the self-bias load line will pass through the origin. Using the 2N4339 as a standard for this and the other configurations, the quiescent drain current lies between 0.25 and 0.55mA when  $R_S=1k\Omega$ . Hence the quiescent output voltage lies between 0.25 and 0.55V.
2. A similar arrangement to the above with a negative supply ( $-V_{SS}$ ) added. This provides an advantage over the first arrangement: namely that the signal voltage can now swing negatively to approximately  $-V_{SS}$ . The two bias lines shown are for  $V_{SS}=-15V$  and  $V_{SS}=-1.6V$ . In the first case the quiescent output voltage lies between +0.18 and +0.74V; in the second between +0.3V and +0.82V.
3. Here a current source improves drain-current ( $I_D$ ) stability, hence the bias load line will be horizontal when  $I_D=\text{constant current}$ . For  $I_D=0.3mA$  the quiescent output voltage is between +0.15 and 0.7V.
4. This is similar to 3, except that the current source is now f.e.t. A which allows constant current, the value of which corresponds to a  $V_{GS}=0$  volts. It will be seen that f.e.t. A loses current linearity as its  $V_{DS}$  approaches zero, so that this technique can only be used to bias f.e.t.s which have a significantly higher pinch-off voltage than the f.e.t. forming the current source.
5. By using a pair of matched f.e.t.s, one as a source follower and the other as a current source, the operating drain current ( $I_{DQ}$ ) is set by  $R_{S2}$ . In this case (1.5k $\Omega$ ) the drain current can be in the range 0.2 to 0.42mA (as shown by the intercepts). However, as the f.e.t.s are matched  $V_{GS1}=V_{GS2}$  and since  $I_{D1}=I_{D2}$ , by making  $R_{S1}=R_{S2}$  the voltage across A-B will equal the voltage across C-D, which in this case is zero. This arrangement exhibits zero or near-zero offset, and if the f.e.t.s are temperature matched at the operating  $I_D$ , the arrangement will provide zero or near-zero temperature drift.

## Biasing with feedback

The following circuits appear in the same sequence as before for comparative purposes. In each case  $R_G$  is returned to a point such that almost unity feedback is provided to the lower end of  $R_G$ . If the value of  $R_S$  is selected so that  $R_G$  is returned to zero d.c. volts (except for 6), then the input/output offset is zero.  $R_I$  is usually much larger than  $R_S$ .

6. This arrangement is suitable for a.c.-coupled circuits, and with  $R_S \ll R_I$  provides near unity feedback. The bias load line is set by the value of  $R_S$ . The output load line, however, is the sum of  $R_S+R_I$ . The feedback voltage ( $V_{FB}$ ) at the junction of  $R_S/R_I$  is determined by the intercept of this  $R_S+R_I$  load line with the  $V_{GS}$  axis. Quiescent output voltage is  $V_{FB}-V_{GS}$ .
7. Here  $R_S$  can be trimmed to provide zero offset. Reference to the graph shows that  $R_S$  will be between 670 $\Omega$  and 2.5k $\Omega$  (and very much less than  $R_I$ ). The source load line intercepts the  $V_{GS}$  axis at  $V_{SS}=-V_{GG}=-15V$ . Note that this load line is not perfectly flat; it has a slope of  $-1/50k$  because the current source is not perfect, having a finite impedance however high.
8. Here  $R_I$  is replaced by the ideal current source, and as this has theoretical infinite impedance, the load line is now perfectly flat.
9. By taking the output from the top of  $R_S$ , output impedance is reduced, and  $R_S$  must be trimmed if the circuit is to operate effectively. The constant-current load line ( $I_S=0.3mA$ ) and the effect of a 1k $\Omega$  source resistor is shown to provide an offset voltage between 0.2 and 0.75V. The intercept of the  $R_S$  load line and the  $V_{GS}$  axis sets the voltage ( $V_{FB}$ ) at the junction of  $R_S$  and the current source. For  $R_S=1k\Omega$ ,  $V_{FB}$  will lie between  $-0.1V$  and  $-0.45V$ . Since  $V_{FB}$  appears at the gate, it must be zero if the d.c. input impedance of the circuit is to be preserved. This can be done by trimming  $R_S$  (dotted line) the biasing, then reverting to that of circuit 8.
10. This is identical to circuit 5 except that feedback is added to raise the input impedance.

\* Siliconix Ltd.

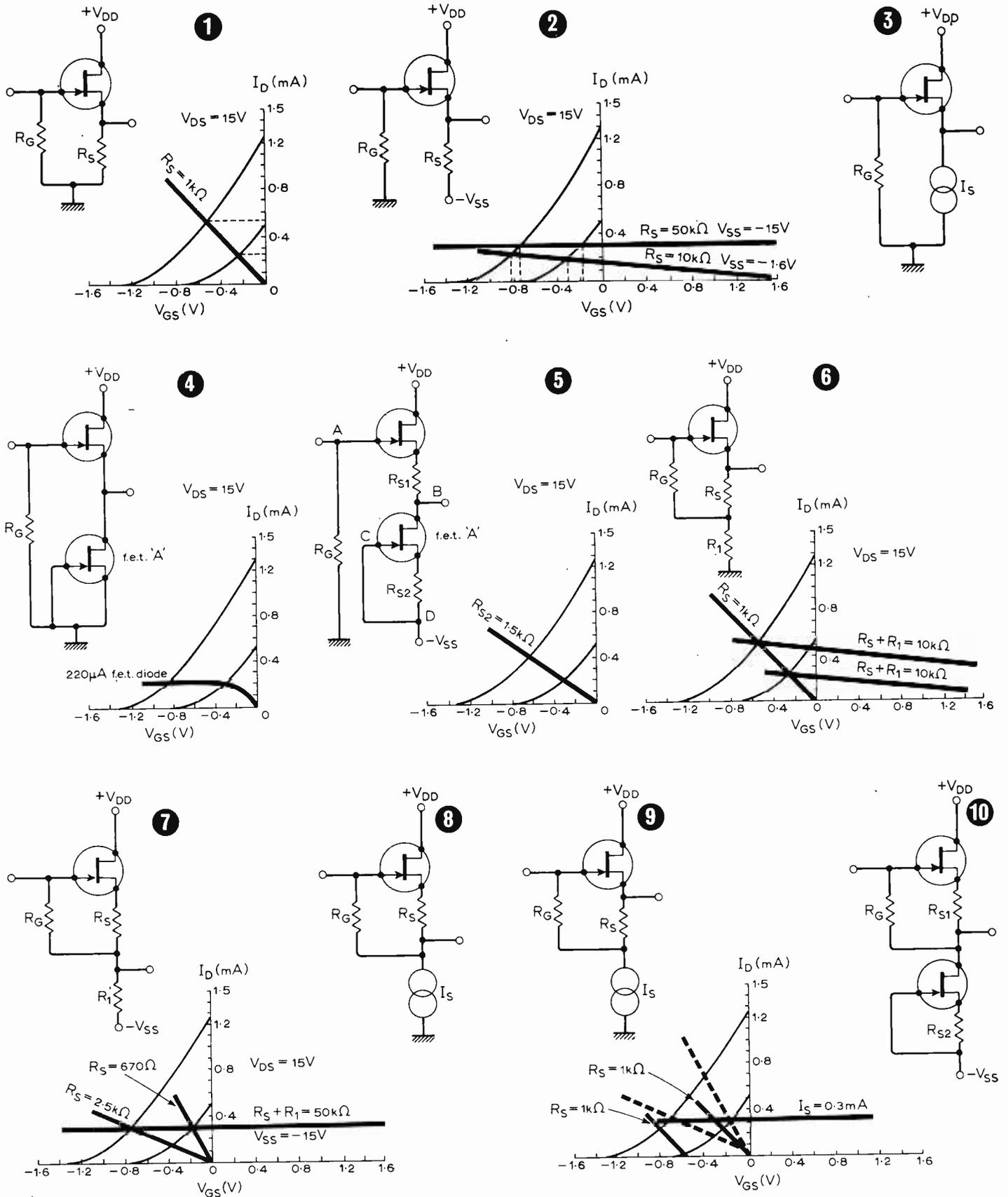

**Summary**

Circuits 1, 4 and 6 can accept only positive and small negative signals, as the source resistors are to ground. All other circuits can handle large positive and negative signals inhibited only by the available supply voltages and device breakdown voltage. Circuits 3, 4, 5, 8, 9 and 10 employ current sources to improve  $I_D$  stability and improve gain. Of these 4, 5 and 10 employ f.e.t.s as current sources. Circuits 5, 7 and 10 employ a source resistor,  $R_S$ , which may be selected to provide a quiescent output voltage equal to zero. Circuits 5 and 10 use matched f.e.t.s.  $R_S$  is selected to set  $I_D$  near the specified low-drift operating current. The input-output offset voltage is zero.

# Simple Crosshatch and Dot Generator

A generator developed from the circuit published in the September 1968 issue which is cheap enough to install permanently in a colour television receiver

by A. W. Critchley\*

The crosshatch pattern of white lines has proved to be the best type of pattern to carry out the convergence adjustments on a television receiver, although white dots are sometimes used. Either pattern is possible with the circuit described by means of a changeover switch or link.

The generator has four disadvantages as can be expected with such a simple device: the receiver has to be synchronized by a transmitted programme; the pattern position on the screen depends on the type of pulses feeding the generator; the pattern can occur during some of the

flyback time causing a foldover; and the horizontal lines may not be evenly spaced. The latter three disadvantages are not very serious provided that the pattern is stationary and the lines are fewer in number than the normal crosshatch pattern of some twenty-six in each direction.

### Waveforms

The waveform required from the generator consists of two independent sets of pulses representing the vertical and horizontal lines of the crosshatch. Vertical lines are some 200ns wide with a repetition every 5µs or so, but occurring only during the active, or scanning, line time of the pic-

ture which is approximately 52µs for 625 line systems). Horizontal line pulses last for one such active line and recur once every thirty-two lines or so, also only during the active line-times of the picture. The repetition rates of these horizontal pattern lines are not important provided that they occur only during the picture time and they are steady. The actual number of crosshatch lines is continuously variable in both directions over a three to one range.

**Vertical lines:** These are generated by a multivibrator which is permitted to run only during the active lines of the picture

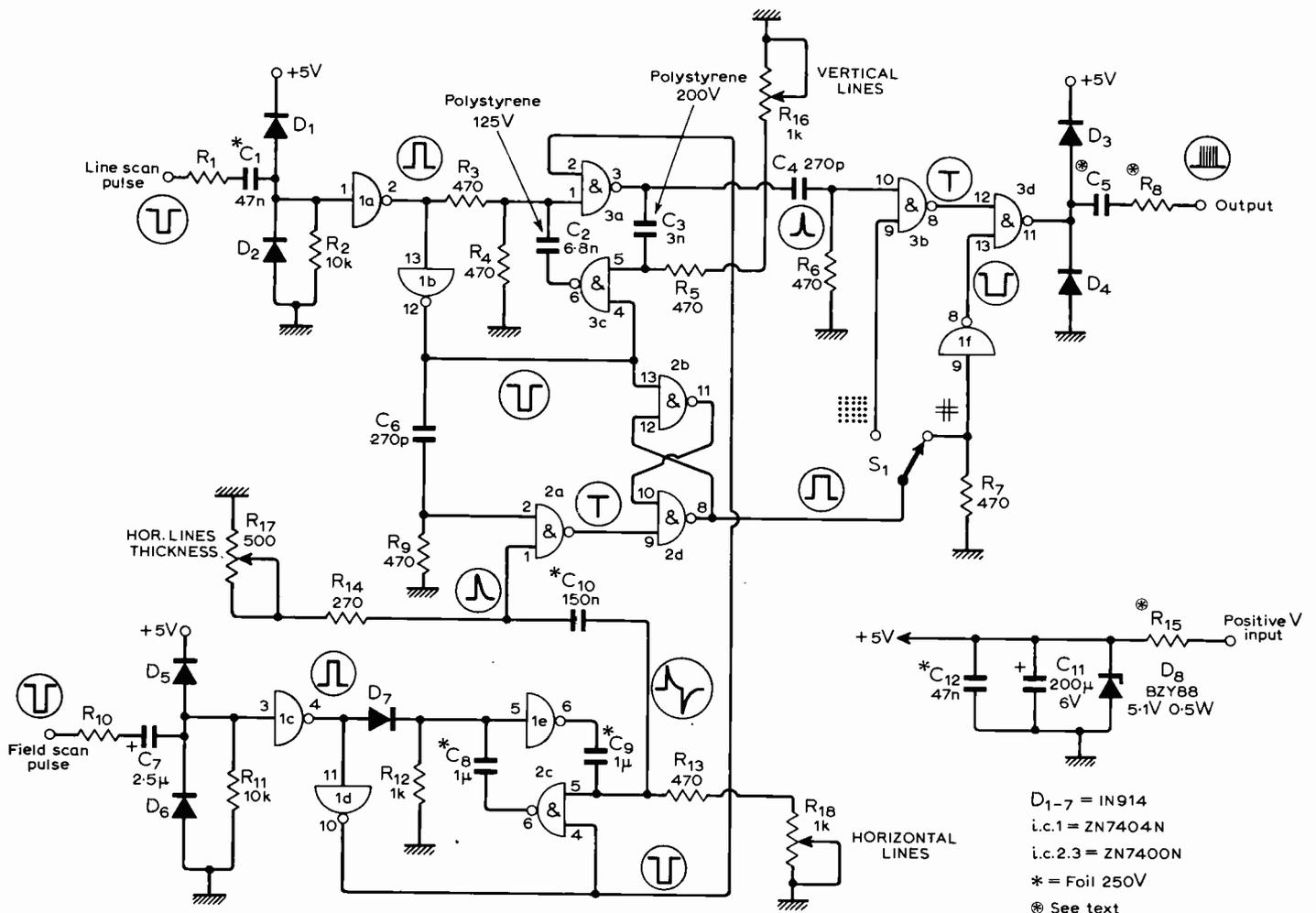


Fig. 1. Block diagram of the crosshatch generator.

- D1-7 = IN914
- i.c.1 = ZN7404N
- i.c.2,3 = ZN7400N
- \* = Foil 250V
- ⊗ See text

as both line and field blanking are applied to prevent any pattern during flyback time. This blanking depends on the widths of the timebase pulses used and varies from receiver to receiver. It is likely that the blanking will not be perfect and some foldover of the pattern is to be expected depending on the receiver.

**Horizontal lines:** The basic oscillator is a multivibrator which is driven by field flyback pulses. The output square wave is differentiated to form a pulse of about 64µs duration and is used to open a gate which is also fed with narrow line-frequency pulses. The output of this gate will consist of one narrow line pulse for every period of oscillation which is given the timing of the trailing-edge of the line-flyback driving pulse by differentiation before the gate. This timing is also the start of the active-line—as near as can be obtained by simple means. An R-S bistable is triggered by this single pulse and is thereby turned 'on' at the start of the active line. The 'off' input of the bistable is fed with continuous line driving pulses which start at the end of the active line and finish before the 'on' pulse. The net result is an output from the bistable of one active line once per period of oscillation of the multivibrator.

The effect of varying the oscillator frequency is to cause a 'shuffling' of the horizontal lines as the optimum frequencies are passed through with a relatively

smooth variation in the number of horizontal lines obtained. These lines are always of the correct length.

**Circuit description (Fig. 1)**

C<sub>1</sub>, D<sub>1</sub>, D<sub>2</sub> and R<sub>1</sub> form an excess-voltage protection circuit for the negative-going line-scan input pulses. Integrated circuit 1a amplifies and clips this signal to give clean rectangular positive-going pulses into i.c. 1b. This pulse is also fed to an attenuating network consisting of R<sub>3</sub> and R<sub>4</sub> which together form one timing resistor for the vertical line multivibrator i.c. 3a and 3c.

R<sub>3</sub> and R<sub>4</sub> are virtually in parallel when the input to the network is low during the picture time and the multivibrator then oscillates normally. When the input from i.c. 1a is high the multivibrator is prevented from oscillating because the potential at the input of i.c. 3a is such as to turn it off. R<sub>3</sub> is really an isolating resistor to remove the shunting effect of the low-impedance output of i.c. 1a from the timing resistor R<sub>4</sub>, but since the parallel combination of R<sub>3</sub> and R<sub>4</sub> is low, then the value of C<sub>2</sub> is correspondingly higher than C<sub>3</sub>. By this means the oscillator always has the same conditions at the start of every picture line. C<sub>2</sub> and C<sub>3</sub>, with R<sub>3</sub> and R<sub>16</sub> form the rest of the multivibrator.

The output from i.c. 1b is also used to help to control the starting and stopping of the multivibrator and in fact improves the

linearity of the first space in the cross-hatch pattern. There is a feed of field scan pulses to i.c. 3a to inhibit the multivibrator during the field flyback time.

The field-scan negative-going pulse is used to drive the horizontal line multivibrator i.c. 1e and 2c in the same manner as for the vertical oscillator except that the value of C<sub>8</sub> has to be kept low because of its physical size. Therefore the input resistor is replaced by a diode to provide automatic isolation of the timing resistor from the gate output.

Both the multivibrators generate approximately square waves and both of them feed differentiating networks. The vertical line network of C<sub>4</sub> and R<sub>6</sub> provides a positive-going pulse of some 200ns width at the input to i.c. 3b—the negative-going pulses being ignored by this gate because they merely turn the gate 'on' harder than it already is whereas the positive-edges turn it 'off' as required.

A similar network of C<sub>10</sub> and R<sub>14</sub> with R<sub>17</sub> generates the positive-going 64µs pulse at the input to i.c. 2a. The other input to i.c. 2a is the positive-going pulse with the timing of the line-scan drive pulse trailing-edge, which is obtained by yet another differentiating network C<sub>6</sub> and R<sub>9</sub>.

The negative-going output of i.c. 2a, which is one narrow line pulse for every cycle of oscillation of the multivibrator, feeds the bistable input of i.c. 2d. The other side of the bistable is fed from i.c. 1b with cleaned-up negative-going line-scan flyback pulses. Integrated circuit 2d provides the output of positive-going single active lines, or horizontal lines of the pattern, and these are combined with the vertical lines in i.c. 3d, via i.c. 1f, to form a crosshatch of 4V peak-to-peak positive-going pulses at i.c. 3d. output. To enable a single-pole switch to be used—or a simple link—for switching to dots—the inverter 1f has to be used in the feed to i.c. 3d and its input has a low value resistor R<sub>7</sub> to earth so that when dots are selected the input of i.c. 1f is virtually earthed and so its output is 'high' and permits i.c. 3d to act as an inverter for the dot signal from i.c. 3b.

The simple multivibrators used in this generator have the very poor stability factor of some 30% change in the period of oscillation per volt of supply.

**Construction and testing**

Construction should present little difficulty if the printed circuit board illustrated in Fig. 2, is employed. Normally the amount of testing required for such a unit is very small especially with integrated circuit construction since the unit either works or it doesn't. However in the case of this crosshatch generator the supply arrangement and the various connections need to be optimized.

The value of R<sub>15</sub>, the zener series resistance should be chosen to allow some 20mA through the zener diode whilst the complete generator takes 40mA making a total of 60mA at 5.1 V.

Next the line pulse resistor R<sub>1</sub> should be chosen to give between 2.5 and 4 V

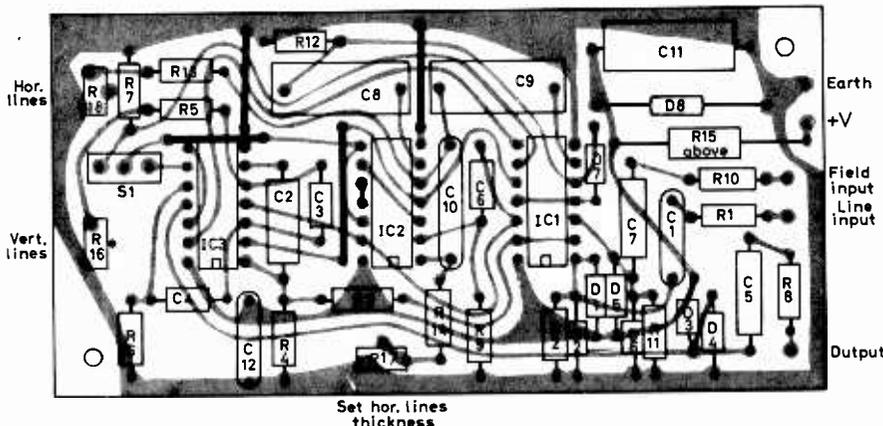
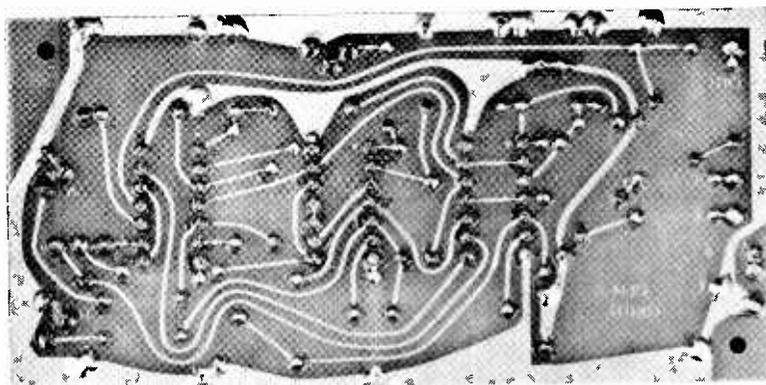


Fig. 2 (Upper) Photograph of the printed circuit board shown actual size (101 mm in length). (Below) Drawing of the component side of the board.

peak-to-peak at  $C_1$ . When this is so there should be an output from the generator, with the switch set to crosshatch, which can be fed into the luminance amplifier.  $R_{16}$  can then be adjusted to give a suitable number of vertical lines.

For optimum results on the receiver, the colour should be turned off, the brightness increased and the contrast decreased, so that the receiver remains synchronized and the crosshatch appears on top of the picture.

For the best results the output signal should be fed into the luminance amplifier after the detector output amplifier stage, where the video is positive-going for white.  $R_8$  determines the crosshatch amplitude. Feeding into the amplifier before the sync. separator does cause a slight problem with vertical sync, if the horizontal lines occur just before the field sync. pulse. However adjustment of the number of horizontal lines should prevent trouble in which the receiver 'chases its own tail'.

The field input resistor  $R_{10}$  is chosen to give a peak-to-peak reading of 2.5 to 4 V at  $C_7$ . The polarity of  $C_7$  depends on the input source. If the line & field pulse sources do not exceed the i.c. supply voltages—at any time—then the protection diodes are not necessary and should be omitted. This should be observed by means of an oscilloscope.

When the field input pulses are correct the output should contain horizontal lines as well as vertical lines, but they will probably be jittering about and  $R_{18}$  should therefore be adjusted. On turning this control clockwise the lines will be observed to get wider apart, and fewer in number, in reasonably smooth steps with certain positions of vertical jitter. It should be a simple matter to find several positions where the pattern is stationary.

$R_{17}$  can now be set so that the horizontal lines are not of double thickness, but at the same time none are omitted. The optimum setting may vary slightly with different settings of  $R_{18}$ . The setting of  $R_{16}$  may also slightly affect the jitter.

If the generator output resistor  $R_8$  is sufficiently high then the removal of the generator's supply should cause no noticeable effects on the normal picture in which case this is a simple means of switching the crosshatch pattern off. Otherwise the output feed will have to be removed instead of switching off the supply.

The input and output connections may be made with ordinary insulated wire as all feeds are of relatively low impedance, but care should be taken with the run of the output lead due to stray capacitance reducing the amplitude of the vertical

lines. If this happens then  $C^4$  should be increased in value slightly.

## Appendix

### Operation of crosshatch generator with B.R.C. 3000 series colour receivers

$R_1$  should be 3.3k $\Omega$ ,  $R_{10}$  should be 8.2k $\Omega$ ,  $R_8$  should be 12k $\Omega$ ,  $R_{15}$  the zener resistor, is 470 $\Omega$ , 3W—stood away from the board and  $C_5$  should be 150nF.

**Line pulse:** Chrominance board, Junction of  $C_{337}$ ,  $R_{359}$  and  $R_{362}$ . Solder the lead to the end of  $R_{362}$  nearest the back of the receiver.

**Field pulse:** Field Scan board. Solder the wire to the top pin of the  $R_{427}$  (field hold potentiometer).

**Output:** I.F. Board.  $L_{117}/R_{127}$ . Solder the wire to the end of this combination nearest to the front of the receiver (above  $VT_{105}$ )—keep the length fairly short.

**Earth:** Convenient point on the i.f. board. +30V. P.U. board. Solder the lead to the 5 $\Omega$  resistor on the top of the lower board—the end which goes to the positive end, of  $W_{620}$ . This lead should be taken via a suitably placed on/off switch to the generator.

### Method of operation

Turn off the colour, turn down the contrast, and turn up the brightness a little. The potentiometers should be adjusted for optimum results. Note that the horizontal lines upset the field timebase at certain settings because the crosshatch signal is put into the video chain before the sync. separator and the field timebase tends to chase 'its own tail'.

The Line and Field pulses should be 2.5 to 3.5 V p.p. at the inputs to the i.c.'s when the generator is switched on and about 2 V when off.

Both these waveforms are fairly wide and thus there is no visible fold-over or flyback.

The pattern is still visible under no-transmission conditions but the video noise masks the crosshatch and renders it unusable.

A worthwhile modification to the receiver would be to replace  $R_{423}$  on the field scan board by a 470 $\Omega$  potentiometer (from earth) with a 1.8k $\Omega$  resistor in series. The potentiometer slider is then the field output point. The voltage at this point should be set to be less than 5 V p.p. The input capacitor and diodes on the generator field input can be deleted if this is done. The series resistor should be retained but changed in value to 220 $\Omega$  or so, to protect the i.c.—otherwise  $D_5$  could be retained instead.

A further improvement would be a series-regulator in the supply to the generator instead of the zener arrangement in order to reduce the supply impedance and thereby eliminate the slight tilting of the vertical lines at the right-hand-side of the picture which occurs when the zener supply is used. Each vertical section between horizontal lines is tilted by about a line thickness and whilst the effect does not affect the observation of convergence errors, the pattern does not look good.

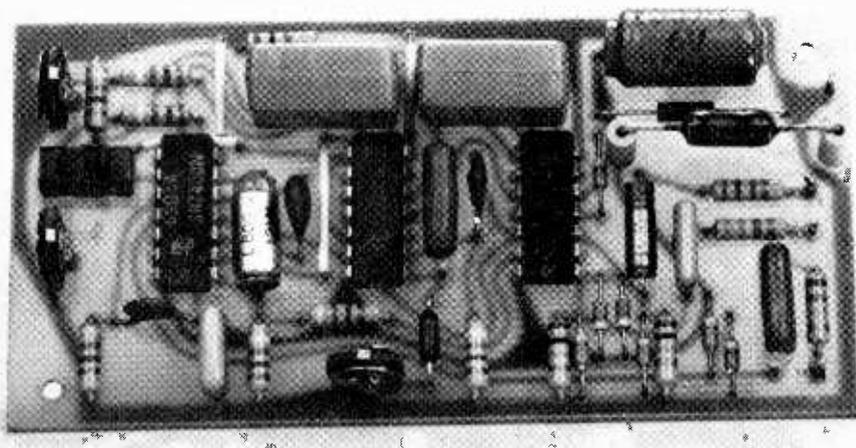
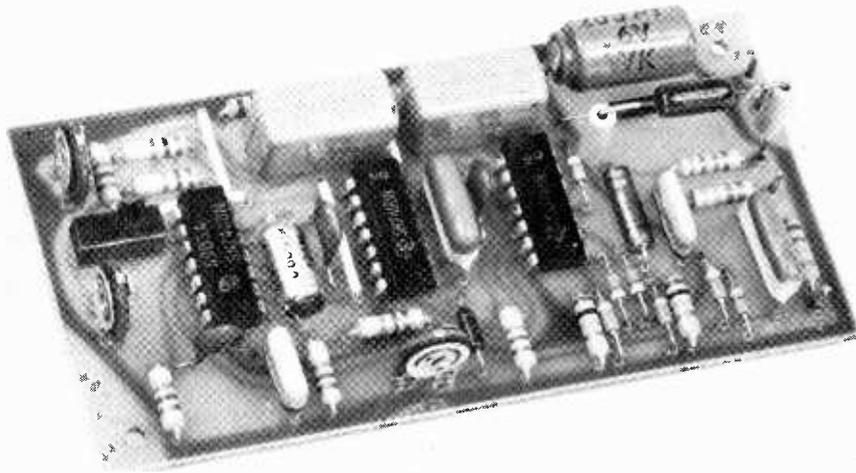


Fig. 3. The prototype.

# Square-root Circuit

Using dual silicon-gate m.o.s.f.e.t. to give 1% accuracy

B. L. Hart\*, B.Sc., M.I.E.R.E., M.I.E.E.E., and A. Cheetham\*, M.Sc., M.I.E.R.E.

There are various ways of achieving the square-root operation—for instance the biased diode and multiplier techniques.† However, a simple low-cost approach is made possible by the capability to make an f.e.t. with an accurate square-law transfer characteristic, and of making pairs with their electrical parameters almost identical.

Consider the circuit arrangement shown below, in which the direct-coupled differential amplifier has a d.c. and low-frequency small-signal voltage gain  $A_v$ , and  $Tr_1$  constitutes two matched p-channel enhancement-mode devices of a dual m.o.s.f.e.t. unit. One of the devices— $Tr_{1a}$ —is in the feedback network of the amplifier and passes the input current  $I$ ; the other— $Tr_{1b}$ —is connected in series with the output of the amplifier and passes a small constant current derived from the interconnection of the integrated bipolar transistor pair  $Tr_2$ . Transistor  $Tr_{1b}$  cancels out part of the amplifier output voltage.

As  $Tr_1$  operate with drain-gate straps, each has a voltage-current relationship of the form

$$I_{SD} = \Psi(V_{SG} - V_T)^2$$

where  $I_{SD}$  is the source-drain current,  $V_{SG}$  is the source-gate voltage,  $V_T$  is the threshold voltage, and  $\Psi$  is the device constant (a function of material type, doping, geometry). (The order of the subscripts for  $I$ ,  $V$  corresponds to positive values of these quantities for a p-channel enhancement device.)

For simplicity in a first-order approximation assume that  $Tr_1$  have identical  $V_T$ 's and identical values of  $\Psi$ . Assuming  $A_v \gg 1$  and ignoring the input current, feedback action ensures that

$$I_{SD1} = I = V_I/R = \Psi(V_{SG1} - V_T)^2 \quad (1)$$

$$\text{If } \sqrt{I_{SD2}/\Psi} \ll V_T \text{ then } V_{SG2} \approx V_T \quad (2)$$

But,

$$V_O = (V_{SG1} - V_{SG2}) \quad (3)$$

Using equations (1) and (2) in (3)

$$V_O = \sqrt{V_I/\Psi R} \quad (4)$$

For the special case  $\Psi R = 1$  volt,

$$V_O = \sqrt{V_I} \quad (5)$$

The successful practical realization of equation (4) depends on the choice of  $Tr_1$ .

Now for  $V_I \approx 0$ , the amplifier output voltage is approximately  $V_T$ ; thus for maximum range in  $V_O$  m.o.s.f.e.t.s with a low  $V_T$  are required. This suggests the use of devices made by the silicon gate process. Preliminary measurements indicated a  $V_T < 1.5$  V and a  $V_T$  matching of a few millivolts for the two devices of the recent silicon-gate dual m.o.s.f.e.t. type ME1202 (Marconi-Elliott Microelectronics) so this was used. The amplifier can be any good quality operational amplifier: a Burr-Brown type 3057/01 was used. Values for  $V_{EE}$  and  $R_b$  were chosen so that  $Tr_2$  (SL301-A, Plessey) in the "current mirror" configuration supply a current  $I_{SD2} \approx V_E/R_E \approx 5 \mu A$ .

A convenient way of operating the circuit, and the one used for the tests reported here, is to set  $V_I$  at a point  $V_I^*$  in the middle of the desired input operating range, then adjust  $R$  so that a precision digital voltmeter indicates  $V_O = V_O^* = \sqrt{V_I^*}$ . This ensures  $\Psi R = 1$  in equation (4) and hence the validity of equation (5) at the "set" point

A selection of the results obtained with one of the units is given in the table, in which the fourth column records the error  $\epsilon$  calculated from

$$\epsilon = |(V_O - \sqrt{V_I})/\sqrt{V_I}| \times 100\%$$

To obtain the readings shown the circuit was set up at  $-V_I = -4.000$  V. For a 20-V input range the maximum departure from

square-root law behaviour is less than 1%. Other readings (not given) show this to be true also when the circuit is set up at  $-V_I = -9.000$  V.

Test results showing accuracy of square-root circuit

$-V_I$	$\sqrt{V_I}$	$V_O$	$\epsilon$
-0.5000	0.7071	0.6960	1.6%
-0.7500	0.8660	0.8692	↑
-1.000	1.000	1.009	
-2.000	1.414	1.424	< 1%
-4.000	2.000	2.000	
-9.000	3.000	2.998	↓
-16.00	4.000	4.009	
-20.00	4.472	4.492	
-25.00	5.000	5.073	1.4%


\* Set-up point

Throughout  $V_I$  has been taken as a positive quantity—the circuit extracts the square root of the magnitude of an applied negative signal. To find the root of the magnitude of a positive voltage the circuit must be preceded with a unity-gain inverting amplifier.

## Correction

### Audio sweep generator

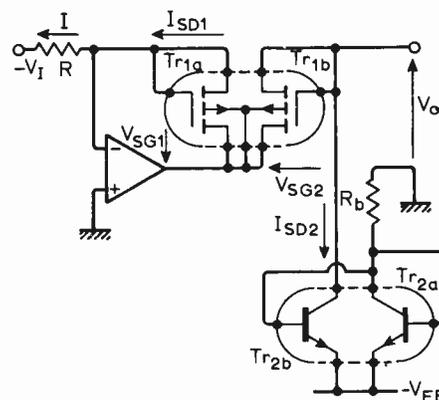F. H. Trist has asked us to make some additions to the circuit of his suggested sweep generator (page 337, July issue). In the v.c.o., a 10-k $\Omega$  resistor should be connected at the junction of the 10- $\mu$ F coupling capacitor with the following resistor and to earth. In the output level amplifier, a 470- $\Omega$  resistor should be connected between the negative input of the i.c. and earth. The three level-control resistors in the feedback loop should be reduced by three orders of magnitude. In the frequency-to-voltage converter, a 10-k $\Omega$  resistor should be connected between the negative input of the second i.c. and earth. In this circuit, we apologise for showing the X-output incorrectly connected. It should be taken from the wiper of switch  $S_e$ , and the common connection of the capacitors earthed.



Using a m.o.s.f.e.t. with an accurate square-law characteristic in a feedback loop is the basis of this simple square-root circuit.

\*North East London Polytechnic

†C. A. A. Wass. "An introduction to electronic analogue computers". Pergamon: 1956

# News of the Month

## Scientific fellowship for authors

A scientific fellowship, worth over £750, is to be awarded by the Butterworth Group to commemorate 25 years of scientific publishing. The Fellowship, to be presented annually from October, 1972, is designed to allow would-be authors to take time off from their work to write a book. By this means, each year, Butterworths hope to encourage a work on some aspect of a physical or biological science, or its application. Proposals will be judged both on academic merit and relevance to current research.

Candidates should work in a British university or institute or in an industrial laboratory of similar standing. Depending on the amount of work involved, the fellowship will be tenable for a period of three to twelve months, and during this time advances against royalties will be made to cover the loss of normal income. In addition an award of £750 will be made on acceptance of the manuscript.

The fellowship will be awarded by Butterworth's Scientific Advisory Board whose members are: Professor Sir Harold Thompson, C.B.E., F.R.S., (Department of Physical Chemistry, University of Oxford); Professor D. H. R. Barton, F.R.S., (Department of Chemistry, Imperial College, London); J. A. Charles

(Department of Physics, University of Bristol) and Professor J. L. Harley, F.R.S., (Department of Forestry Science, University of Oxford).

Applications must be submitted by 1st October, 1971 and must be backed by a head of department. It is expected that the fellow will be selected in the same month. Applicants should write for more information and entry forms to The Scientific Publisher, Butterworth Group, 88 Kingsway, London WC2B 6AB.

## Atlantic air traffic control by satellite

Further steps towards using satellite communication links for air traffic control are being taken with the award of a study contract to the Marconi Company by the Department of Trade and Industry. Under the contract Marconi's Radio and Space Communications Division will prepare a detailed analysis of the ground-based parts of a possible aeronautical satellite system for the North Atlantic. This will entail a detailed study of the ground equipment

necessary to relay several different types of information between aircraft and ground via satellite and to determine the best way of putting the study into practice.

Aircraft over the North Atlantic are under the control of oceanic air traffic control centres and the present system is under the jurisdiction of several centres including Gander in Newfoundland, Prestwick in Scotland, New York and Santa Maria (Azores). Aircraft report to these stations using normal h.f. radio, to give position information derived from their own on-board navigational instruments.

Improvements to the system are made continuously to cope with the demand of increasing transatlantic air traffic and it is in anticipation of the time when current methods are no longer effective, that consideration of satellite systems is being undertaken on both sides of the Atlantic.

## Computer telegram system

The Post Office has placed a £3.25M order with Pye/T.M.C. for a computer-controlled telegram routing system which will replace electro-mechanical systems in 1973 at Cardinal House, Farringdon St, London. It will be the largest system of its type in the world and will be controlling the receipt and dispatch of the 21 million international telegrams handled in Britain every year.

Initially the equipment will receive telegrams for transmission abroad from international area offices throughout the country and will perform all the necessary switching and routing automatically. The same process will apply to telegrams received from abroad which will be automatically routed to the appropriate area office. Eventually the system will convert addresses on incoming telegrams to the telex address (if there is one) so that the message can be immediately sent over the telex network.

## Radar at Heathrow

Marconi Radar Systems has received an order from the Ministry of Defence (Aviation Supply), on behalf of the Department of Trade and Industry, to supply a high-power, 50cm transmitter/receiver to replace radar equipment at Heathrow Airport which has been in service for twelve years. The new transmitter/receiver (type S2020) is a self-contained 500kW 50cm equipment designed for use in coherent moving target indication systems and will be installed towards the end of the year. The power amplifier stage is a three-cavity klystron valve, with a typical life of 30,000 hours.



(left) S2020 radar for Heathrow

## Surveillance system for Southampton docks

An extensive surveillance system is to be installed to provide increased safety to shipping using the port of Southampton. The scheme is being carried out by the British Transport Docks Board. Decca Radar and Marconi Communications Systems have been awarded contracts totalling over £0.25M.

Decca Radar are to equip two unmanned radar stations, at Hythe and Calshot, from which data will be transmitted by microwave link to six 400mm displays in the operations room at the port communications centre. At Calshot and Hythe the radar stations will consist of 7.6m scanners mounted at a height of 33m. Remote control of both stations will be effected by microwave link to the port communications centre. The six displays to be installed by Decca in the operations room will be able to receive data from either unmanned station (two normally being fed from Hythe and four from Calshot). The Decca computer-assisted measurement system will be provided for all six displays, and a Deccaspot system will be available on all pictures received from Calshot. The former system uses a small Honeywell computer to enable rapid and accurate measurements to be made of any point, such as a ship's position, relative to any other point on the display. Deccaspot, a method employing a series of bright spots on the display to depict with great accuracy any permanent feature required, will be used to delineate the centre of the navigation channel from Southampton Docks.


## Desk-top optical mark reader

Interscan Data Systems (U.K.) Ltd, normally associated with complex and expensive, optical character recognition machines, have announced a new low-cost relatively simple document reader. The new reader—there are two versions—can be operated by a company for as little as £2,000 per year. Once loaded the reader will continue to operate all day without attention.

The machine, called o.m.r. (optical mark reader) reads characters on special forms and gives an output in computer compatible code. As long as the characters are put in the correct position on the form they can be machine or hand printed.

The reading head, which is made to mechanically scan the rows of characters, consists of two photodiodes which simultaneously read the upper and lower halves of the characters. Only vertical sections of the characters are sensed, horizontal marks being redundant. The reading head also contains two magnetic proximity sensors which provide clock

*Submarine cable repeaters being manufactured in an S.T.C. plant under clinical conditions. Repeaters of this sort will be used on a new £22M transatlantic cable (CANTAT-2) which will run from Wide-mouth Bay in Cornwall to Halifax in Nova Scotia. The 14MHz coaxial cable will carry 1840 simultaneous telephone conversations: Repeaters will be fitted at intervals of about six nautical miles. S.T.C. have been awarded the contract by the Post Office and it is calculated that the cost is about £6 per circuit per mile.*

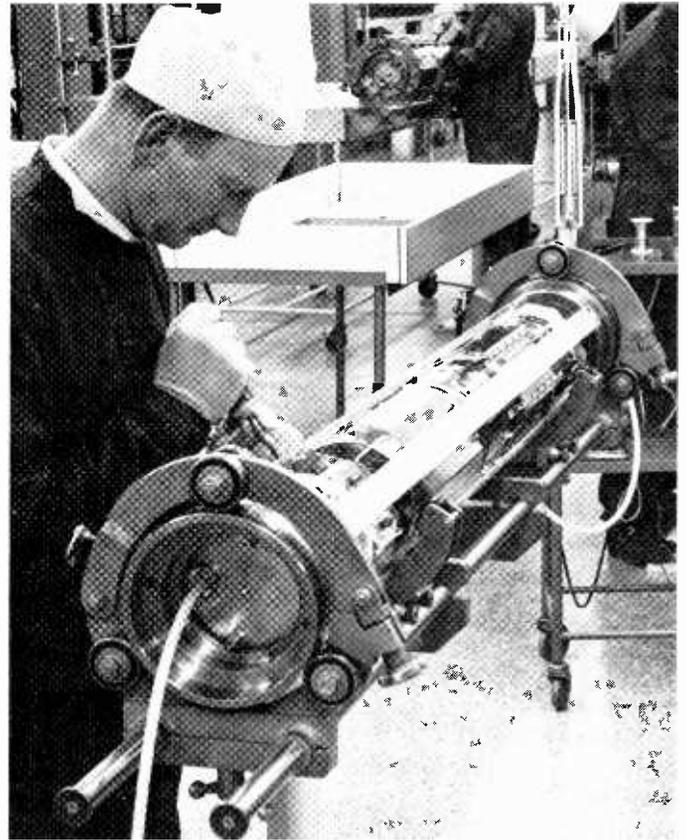

pulses, when a character is under the reading head, from castellations machined into a piece of metal mounted parallel to the moving reading head.

Document size can vary from 50 × 100mm to 216 × 280mm and the reading speed is up to 20 characters per second. The makers say that the equipment costs less than a paper tape station to hire and has ten times the throughput. To another piece of equipment the machines electronically look like a Teletype machine and therefore can be easily interfaced with other data processing equipment or the output can be recorded on a cassette tape recorder.

## Motorists' laser warning system

Scientifica and Cook Electronics are working hard to find new applications for the laser. Recently they described a system, which could be used on small airfields, employing a laser to provide a visible glide path to assist landing aircraft.

Another idea, and apparently a good one, entailed fitting photocell detectors on the nose of aircraft and connecting them to the aircraft's intercom system. The idea being that the control tower staff could contact an aircraft on the airfield very quickly in an emergency using a modulated laser beam regardless of the channel selected on the aircraft's radio.

An extension of this idea has resulted in photocells being fitted to a motor car, the

cells being connected directly to the a.f. stage of the car's radio so that it is possible to transmit warning messages to motorists by using a diffused laser beam directed down the centre of the carrieway. Trials have shown that this idea works well in practice.

## One-plus-one equals party line privacy

One-plus-one is the name given to a new piece of equipment which is to be installed on an experimental basis at 10,000 locations up and down the country by the Post Office. It enables two subscribers to share a line to a telephone exchange with complete privacy and if desired both subscribers can use their telephones at the same time.

A filter is fitted at the point where the line from the exchange divides to go to the individual telephones. One of the telephones operates in the normal manner at audio frequencies and does not require any additional equipment. Two carrier frequencies are used for the second telephone, 40kHz for send and 64kHz for receive. Equipment at the exchange and at the subscriber's premises carries out the necessary modulation and demodulation functions. Electronic equipment at the subscriber's end is powered by a small nickel-cadmium battery which is trickle charged over the line from the exchange. The system was designed by G.E.C.'s Telephone division laboratories at Aycliffe.

# Letters to the Editor

*The Editor does not necessarily endorse opinions expressed by his correspondents*

## Ceramic pickup equalization

Without reflecting on other parts of Mr. Burrows' article in the July issue I am appalled at his ability to read out of context.

His quotation from my book 'Pick-ups: Key to Hi-Fi' is given as a *myth* about 'electrical loading affecting the mechanical operation' of a pickup.

But the quotation clearly mentions correction by electrical means (via element *capacity*), of a mechanically accomplished equalization. It has nothing to do with damping mechanical resonances at all. It seems this myth belongs to Mr. Burrows.

JOHN WALTON,  
Windsor,  
Berks.

I was interested in the excellent article by Mr. Burrows (July issue) basing the mechanical/electro independence of pick-ups on low energy conversion. This is the first time that I have seen this direction of approach.

However, it is only fair to point out that hosts of manufacturers other than Leak imply by instruction booklet or text or input circuit design that an approximation to velocity characteristics is achieved by connecting a piezo pickup across the relatively low value load of an R.I.A.A.-equalized input.

Surely the point of the exercise is that all quality amplifiers are deliberately equipped with R.I.A.A. low-level inputs so that the advantage can be taken of the optimum performance at the present state of the art provided by the magnetic cartridge?

The lack of simple solid-state, high resistance inputs prior to the f.e.t. obviously made it necessary for manufacturers to suggest a simple artifice to accommodate the minority of 'lower-fi' piezo users. Since the f.e.t. has become more commonplace and less costly, manufacturers who consider that the piezo cartridge is being treated unfairly are yielding designs with an f.e.t. input solely for piezo cartridges or in addition to the usual R.I.A.A.-equalized input. The piezo input is typically  $2M\Omega$ , and with this kind of cartridge mild bass roll-off is not always amiss.

In my judgment it is debatable whether manufacturers would have very much

call for an amplifier with a specifically engineered piezo input possibly requiring adjustment to suit the cartridge used. The hi-fi enthusiast is a magnetic man for various reasons, and now that magnetic species of surprisingly high quality (in terms of the three main parameters of tracking performance, frequency response and crosstalk) are available for a few pounds the man hitherto piezo prone is turning towards electromagnetic energy for this programme source.

Apart from the obvious lack of true velocity coincidence by running a typical piezo across  $47k\Omega$  into an R.I.A.A.-equalized circuit, the major offence is pre-amplifier overload, since this partnership is not uncommonly practised without input attenuation. Bearing in mind the poor overload margin of such pre-amplifiers it is possible that this rates higher in the poor-piezo-quality stakes than lack of absolute equalizing.


GORDON J. KING,  
Brixham,  
Devon.

## Transformer phase reversal

I am most grateful to your eminent contributor 'Cathode Ray' for throwing his very considerable professional weight behind the campaign for the truth about the transformer (June p.285). Although, as he explained, he had to argue the matter on paper without practical demonstration, I take it that your readers can and will check the experimental fact as to the phase relations between terminal voltages and currents in primary and secondary for themselves (see circuit); or perhaps not, since during the past seven years of teaching the experimental fact (preceded by two years of teaching orthodox phase reversal!) I have invariably found that learners will argue heatedly for an hour among themselves but when invited to make a five-minute measurement say they haven't got the time.

Electronics is above all (apart from instrument transformers, where only the direction of a wattmeter deflection is at stake) the field where phase cannot be fumbled. A power engineer, paralleling two 10 MVA transformers and assuming a

phase reversal in *both*, will come to no harm, being protected no doubt by the same Divinity which looks after children and drunks. But an audio amplifier designer getting his transformer polarities wrong in a feedback amplifier is going to produce fierce oscillations and a damaged loud-speaker. It would be helpful therefore, if manufacturers of interstage transformers who do mark winding starts and finishes,

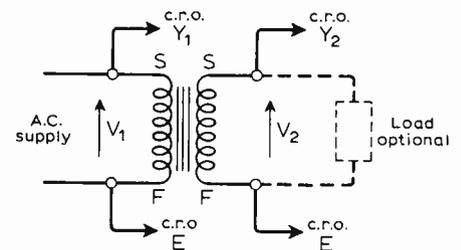

*If the starts and finishes of the windings are not marked they can be quickly established by measuring the inductance of the two windings in series. The connection giving the larger inductance is that in which the finish of one winding is connected to the start of the other winding.*

and some others who don't, would tell us what the phase relations in their transformers are, and if manufacturers of feedback amplifiers using interstage transformers and output transformers would say what phase relations they assumed in designing their amplifiers and getting them to work so very satisfactorily.

VICTOR MAYES,  
Gloucester Technical College,  
Gloucester.

## Audio sweep generators

While Mr. F. H. Trist is to be congratulated for answering the long-felt need for an audio sweep generator, we feel that his design (July issue) falls short of engineering requirements on several counts.

1. Sweep frequency range. The 10:1 frequency change satisfies only a small proportion of the possible uses; in fact only those for investigating narrow-band filters. A 1,000:1 change, from 20Hz to 20kHz seems a minimum specification for ampli-

fiers, tone controls and filters, and this sort of range is normally offered by commercial designs.

2. An amplitude accuracy of 1dB is marginally adequate for transducer measurements, and not good enough for amplifier and filter work.

3. A sweep time of four seconds is only suitable for oscilloscopes with c.r.t. phosphors which most users are unlikely to have.

4. Logarithmic scaling of both frequency and amplitude axes in all graphical representation in audio engineering is normal and necessary. To give one example, it is not possible to differentiate between a 26dB and a 40dB notch filter on an oscilloscope, if the system responds linearly to amplitude. (A fast enough sweep time to make the use of a normal oscilloscope possible can be achieved only if the sweep is logarithmic.)

It seems to us that most of the drawbacks in Trist's design result from the wrong choice of oscillator. Any bridge-type oscillator is far too "sensitive" (in the sense that Bode gives the term<sup>1</sup>) to achieve a wide frequency change without unreasonably close matching of components. The design considered demands 5% matching of f.e.t. drain-source resistances for only a 10:1 frequency range, and even then an a.g.c. network is needed to compensate for the varying losses in the bridge. Furthermore this a.g.c. system introduces another time constant into the oscillator, which is too long to allow for amplitude correction during the sweep.

Two alternatives to the bridge oscillator suggest themselves, if only to eliminate component selection and complex setting-up procedures (Trist's calibrator alone contains fifteen pre-sets); these are the non sinusoidal oscillator<sup>2</sup> and the two-integrator loop<sup>3</sup>. A switched Miller integrator, of which Trist's ramp generator is an example, can itself be frequency controlled by another ramp generator, producing a swept triangular wave with its amplitude independent of component matching and fixed only by the reference level of the comparator. Provided this triangular waveform is equilateral, a pure sinusoid can be obtained with a simple function generator. A diode network will produce better than 3% harmonic distortion<sup>2</sup> and other methods easily better this<sup>4</sup>. Alternatively the two-integrator loop generates sine waves with amplitude fixed by a limiter and tracking errors between the two frequency varying elements produce proportionate errors in frequency only, none in amplitude. Frequency ratios of 1,000:1 are easily obtainable, in practice with both the above oscillator types.

We are working on a sweep generator using a two-integrator loop, which we hope to submit for publication shortly. Although our design requires a greater number of i.c. operational amplifiers, it does satisfy requirements 1-4 above namely a 1,000:1 sweep range, good amplitude accuracy, fast sweep rate and logarithmic frequency and amplitude axes. We feel therefore that alternative oscillators to the Wien bridge should be considered by those interested in sweep oscillator design.

A. FALLA, R. S. SNELL,  
University of Sussex,  
Brighton.

1. H. W. Bode: Network analysis and feedback amplifier design (p52), D. Van Nostrand, N.J. 1945.
2. P. J. Kindlman: 'Sound synthesis: a flexible modular approach with i.cs', *I.E.E.E. Transactions on Audio*, Vol. AU-16 no. 4, Dec. 1968.
3. E. F. Good: 'A two-phase low-frequency oscillator', *Electronic Engineering*, Apr. 19, '57.
4. 'Triangular-to-sine convertor', *Electronics*, Vol. 38, no. 5, p96.

*The author replies:*

It was with considerable interest that I read Messrs Falla and Snell's comments on my sweep generator. Before answering each point in turn, may I say that all of them occurred to me (unceasingly!) during design stages.

(1). Perhaps I did not state sufficiently clearly that there are four frequency ranges available at the flick of a switch, thus enabling 10-10<sup>5</sup>Hz to be covered. This seems to me to be of greater use than squeezing the entire spectrum into some 4 in of c.r.o. display. I do not consider the range quoted by Falla and Snell as adequate; my system allows break points to be studied in detail—you don't gaze at the stars whilst tying your shoelace!

(2). It is doubtful whether a linearity of better than 1dB is necessary in any audio system. In any case, displaying the input to the network under study will reveal where and by how much the amplitude varies during a sweep.

(3). I should point out that:  
(a) Only the lowest range is limited to a 4 second sweep.

(b) Ideally, for normal c.r.o. work, a sweep rate in excess of 25/sec. is required, in order to fool the eye. My system would generate garbage at this speed, even if the a.g.c. could respond fast enough, as there is no control over the starting phase of the oscillator. I assume that the two-lag system proposed will control this function, but sweeping at any rate faster than 0.1 of the minimum oscillator frequency will give little indication of response as frequency will change faster than phase.

(4). The prototype contained a logarithmic operator to provide the display time-base; this was of little practical use, due to the non-linearity of the voltage-resistance characteristic of the tuning devices. At the price—£20 including case—I don't apologize. As my unit does not attempt to process the signal from the observed network, how could it possibly be expected to provide a logarithmic amplitude display? Perhaps the writers would have me compress the signal to the network!

I do not follow the last sentence of (4). Only an antilogarithmic timebase function could permit faster sweep rates at low frequencies; this would diminish the phase problems detailed above; a logarithmic function must accentuate them.

I do not feel that 5% matching of two devices is too much to ask for. Falla and Snell mentioned diode shaping an equilateral triangular waveform to produce a low—3% is low?—distortion sinusoid. If they were to use the switched Miller

integrator proposed, they would require to match a pair of current defining resistors to better than 5%.

It is simply not true that amplitude correction is not applied during a sweep. The sweep frequency is much lower than the minimum oscillator frequency on each range; while the smoothing time-constant all but eliminates ripple from the oscillator, it is small enough to respond to the ramp-generator frequency—the fundamental frequency at which the amplitude attempts to change. I could scarcely claim a maximum deviation of ±0.5dB unless this were so.

Non-linear shaping of a triangular waveform can, by definition, never achieve the low-distortion of the Wien bridge. My instrument produced less than 1% distortion at 10Hz; on the upper three ranges no reliable reading could be made using a Marconi distortion factor meter.

F. H. TRIST,  
Stoke-on-Trent,  
Staffs.

**Karnaugh map display**

Fig. 5 in the article (published in April) showing the 'equivalent' circuit for the ladder network on Fig. 4 demands some clarification. It may have been tempting to suggest that for a 00-input (Fig. 5(a)) the value of the equivalent series resistor does not matter very much (its value is not mentioned) as the operational amplifier, with this network connected to its inverting input and with the non-inverting input at ground, will have an 0V-output whatever the input resistance. However, this resistance together with the feedback resistance determines the amplification of the signal applied to the non-inverting input. The right value is 10/3 kΩ. In the same way Fig. 5(d) for an 11-input is in error: the fact that no current flows through the two paralleled 10kΩ resistors with unloaded ladder doesn't imply that the left hand resistors can be neglected when determining the equivalent circuit; the two remaining 10kΩ resistors would give an equivalent resistance of 5kΩ whereas in reality it should again become 10/3kΩ.

A first inspection of the ladder network shows that if the terminating resistor had not been returned to ground but instead used to feed the operational amplifier, where it sees a virtual earth, then the two voltage sources feeding the ladder would have seen exactly the same load (15kΩ) but this doesn't seem to be a necessary requirement. A second inspection shows

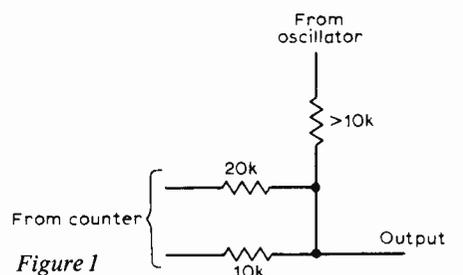


Figure 1

that the terminating resistor could have been dispensed with, even when the ladder output had not been connected to a virtual earth, without upsetting the digital-to-analogue conversion: for an unloaded ladder this would have given a 50% increase in voltage output. The third inspection reveals that two (or three) resistors instead of five (or six) would have done an even better job (Fig. 1).

The clamping circuit shown gives considerable voltage loss; if necessary this can be improved upon by replacing the two silicon diodes by one low-voltage zener diode (about 3.3V). With a 4V swing even an oscilloscope having an X-sensitivity as low as 1 cm/volt would still give a readable image. What happens exactly when one doesn't use a clamping network? From Mr. Crank's observations we may infer that only the clock pulse can be responsible for a double image but this is easier to remedy by using an asymmetric clock signal (small ON/OFF ratio); all other waveform distortions of the type shown will cause some of the 16 centre positions of the Karnaugh map to be shifted only slightly from an 'ideal' orthogonal raster in a reproducible way without provoking a double image. As these shifts are very small their effect will hardly be noticeable. A clamping network is therefore unnecessary!

The output swing being much larger now than in the original version the two operational amplifiers are redundant and the output to drive the 'scope can be taken direct from the digital-to-analogue converter. This results in considerable savings as the major part of the power supply can be dispensed with as well.

Having now only 5 or 6V available for driving the phase-shift oscillator, its output amplitude is reduced. The two output resistances may thus have to be reduced as well. The larger resistance is required at the collector output and it is therefore this output upon which the 1/0 switch should act in order to minimize the effect of the switching action upon the X-amplitude. It is also preferable to connect the switching transistor in the "inverted mode" in series with a capacitor.

The total savings are impressive: no operational amplifiers instead of two; one battery supply instead of three; a one-pole switch instead of a three-pole one; one electrolytic instead of three; no need for diode/resistor clamping; two transistors instead of four.

The final conclusion is that, without doing any difficult exercise and while retaining some of Mr. Crank's ideas and statements, his simplified logic display aid could have been further simplified.

G. J. NAAIJER,  
Limeil-Brevannes,  
France.

#### The author replies:

Perhaps Mr. Naaijer misunderstood the purpose of my equivalent circuits for the ladder networks. The object was to provide a simple explanation of how the square wave outputs of the counter became a stair-

case and to have considered the operational amplifier as well would have only confused the issue. If in my quest for simplicity I have offended the purists I apologize. Perhaps if the offending diagram had been labelled 'simplified circuit' instead of equivalent circuit (with all that this implies), the confusion would not have arisen. I would recommend that readers adopt Mr. Naaijer's digital-to-analogue converter circuit because of the component saving it affords.

I can assure Mr. Naaijer that some form of counter output waveform correction is essential to achieve a 'respectable' display. The zener diode idea was considered during the design but rejected on the grounds that two general-purpose silicon diodes can be purchased at a lower cost than one low-voltage zener diode. By far the best solution was that proposed by A. W. Critchley in the May issue (p. 257). He suggested using four 'pull-up' resistors connected to the counter outputs.

The question of dispensing with the two operational amplifiers is debatable and depends on the use to which the unit is to be put. The original intention was that the device should be used in schools, I could not see many private constructors building it. In this application the device would very often be required to operate with long leads to the oscilloscope, or perhaps several oscilloscopes might be used, situated at strategic points around the classroom. In these circumstances the low output impedance afforded by the operational amplifier is essential as the visual effects of hum pick-up are particularly unpleasant with this type of display.

No trouble was experienced in the prototype with the 1/0 switch loading the phase-shift oscillator and I can therefore see no point in altering the 1/0 switch if the rest of the circuit is built as published (with the recommended alterations). If Mr. Naaijer's suggestion is adopted it would probably be necessary to redesign the phase-shift oscillator to run on 6V.

Most of the component savings claimed mean putting up with a high output impedance with the attendant hazard of hum pick-up. Mr. Naaijer's reference to two, instead of four, transistors refers to using the unused exclusive-OR gates as a multivibrator. (This was described in A. W. Critchley's letter already published and, therefore, the print was removed from Mr. Naaijer's letter to avoid duplication.)  
BRIAN CRANK

### Stereo mixer

For readers who wish to build the designs published in the May and June issues, here are some details of suitable components. Capacitors used in equalization, tone-control and filter networks should be 5% components, polystyrene types for values less than 0.01 $\mu$ F, and polycarbonate (e.g. Siemens B32540) above 0.01 $\mu$ F. The 4.7pF high-frequency compensation capacitors, connected from collector to base of the second transistor in Figs. 3, 8(a) and (b) are not critical and could be

increased to 10pF so that polystyrene types can be used. Electrolytic capacitors are from the Mullard C426 and C437 ranges, and non-polarized coupling capacitors are from the Mullard C280 range. Fixed resistors are 5%  $\frac{1}{4}$ W carbon film, unless stated otherwise.

The apparently blank statements concerning residual noise and mixing level made in part 1 (May issue) require explanation as this point was given theoretical treatment in an unpublished part of the manuscript. A noise analysis of the virtual-earth mixer Fig. 10, shows the signal to residual noise to be  $v_i \sqrt{4.k.T. \Delta f.R.n}$  where  $v_i$  is the maximum nominal signal at the slider of the channel fader,  $R$  is the resistance level of the mixer (i.e. the value of the channel fader or summing resistor) and  $n$  is the number of channels. As the maximum output of the pre-mixing circuits is between 8 and 9V r.m.s. an overload margin of 30dB requires  $v_i$  to be around 120mV after allowing for a 6dB loss in the channel balance control. If  $R$  is 20k $\Omega$  and  $n$  is 5, then the residual noise level is -84.5dB on a 30kHz noise bandwidth. The expression indicates that the residual noise level deteriorates as the number of channels is increased but is improved by a reduction in the resistance level  $R$ , and by an increase in the signal level at mixing. Both the latter effects also reduce the overload margin, so a compromise has to be found. Alternatively the preset sensitivity control can be moved, for example to the feedback loop, though this presents its own problems of stability.

HUGH WALKER,  
South Queensferry,  
Scotland.

### F.M. stereo tuner

I have found that there have been a small number of tuners produced to my design\* which have given signs of instability, and I have been able to reproduce this effect in my own tuners. The trouble is not instability in the normal sense, but gives the impression that it is. The trouble is 'squegging' of the local oscillator, and the cure is the standard one—reduce the base time-constant. I have found that the base capacitor, now 47pF, is best reduced to 15 or 22pF, which cures the problem; the only side effect being due to the slight lessening of oscillator amplitude, with a slight reduction in sensitivity. This is of little consequence because of the very high sensitivity and is largely offset by a slight reduction in background noise. After changing the base capacitor to 15pF in two tuners both of which exhibited the apparent instability, there was no trace of any effects nor could they be provoked by any setting of the tuning or trimming controls. In both tuners the background between stations was very quiet despite a sensitivity for 3dB limiting below 1 $\mu$ V.

L. NELSON-JONES,  
Bournemouth,  
Hants.

\*W.W., April & May 1971.

# Phase-locked-loop Stereo Decoder I.C.

## Build a high-performance decoder with the minimum number of components

It is possible to make a high-performance phase-locked-loop stereo decoder with just sixteen components and a printed circuit board. Only one coil is required and only one adjustment is necessary. The major component in the decoder is an integrated circuit (CA3090Q), containing 126 transistors, which has just been introduced by R.C.A.

A block diagram of the i.c. is given in Fig. 1. The composite output signal from the discriminator of an f.m. receiver is applied to pin 1 of the i.c. where it is amplified for distribution to other parts of the chip. The phase-locked-loop consists of a voltage controlled oscillator (v.c.o.), two divide-by-two stages and a phase comparator (phase-lock detector). An inductor and a capacitor connected to pins 15 and 16 give the v.c.o. a natural centre frequency of 76kHz. This 76kHz signal is divided by four in two cascaded divide-by-two stages to provide a 19kHz

reference for the phase-lock detector. The phase-lock detector compares the locally generated 19kHz signal with the incoming 19kHz pilot tone and provides an output to alter the operating frequency of the v.c.o. if there is any difference. The bandwidth of this loop—which may be likened to a servo system—is determined by an RC network connected to pin 14.

The whole purpose of the loop is to regenerate the 38kHz sub-carrier which is suppressed at the transmitter before the signal is transmitted. The 38kHz sub-carrier is necessary to demodulate the composite stereo signal and the action of the loop ensures that the regenerated sub-carrier is very closely related in phase to the transmitted 19kHz pilot tone.

When the v.c.o. is running at exactly the right frequency the output from the phase-lock detector is zero so it is necessary to provide a second detector, to sense the presence of the pilot tone, in order

that the chip can distinguish between a stereo and a mono signal—the pilot tone is not present on a mono signal.

This detector is called the pilot presence detector and it is driven by a second divide-by-two stage operating from the chip's 38kHz line. The resulting 19kHz signal is compared with the composite input signal and if a pilot tone is present the pilot presence detector trips a Schmitt trigger. The sensitivity of the pilot presence detector is set by a resistor connected between pins 7 and 8. With the value shown in Fig. 2, a 4mV input signal (pin 1) will be sufficient to operate the Schmitt trigger. If greater sensitivity is required the resistor can be replaced with a 4.7mH coil in series with 15nF capacitor across pins 7 and 8. The Schmitt trigger will then operate at 3.3mV (off at 2mV) and an improved overload characteristic is obtained as a by-product. An RC combination connected to pin 6 is a filter for the pilot presence detector.

When the Schmitt trigger operates it lights the stereo indicator lamp via an integral driver amplifier and informs the left/right channel detector that a stereo signal is being received and switches the whole chip to stereo operation.

The left/right channel detector uses the 38kHz sub-carrier (stereo gating signal), generated by the phase-locked-loop, and the composite input signal to produce a stereo difference signal which drives the matrixing circuits. The matrix extracts the left and right channel outputs from the composite input signal in the normal way and after amplification the left and right channel outputs appear at pins 9 and 10.

### Practical notes

The complete circuit diagram is given in Fig. 2 and little need be said about it as the purposes of most of the components have already been described. The capacitors  $C_1$  and  $C_2$  provide the necessary de-emphasis and the two 10k $\Omega$  resistors are the collector loads of the 'open ended' channel amplifier output transistors.

The stereo indicator lamp can be a light-emitting diode as shown or a normal filament lamp which may be connected in place of the light emitting diode and 680 $\Omega$  series resistor provided that the lamp does

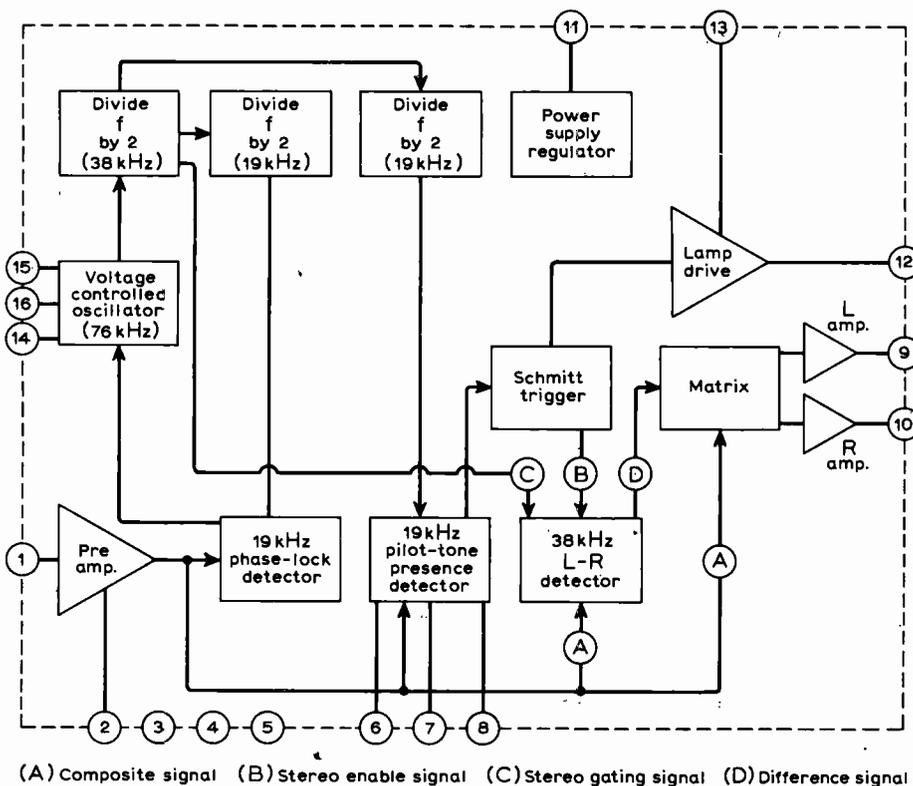


Fig. 1. Block diagram of the CA3090 integrated circuit which forms the major part of a phase-locked-loop stereo decoder.

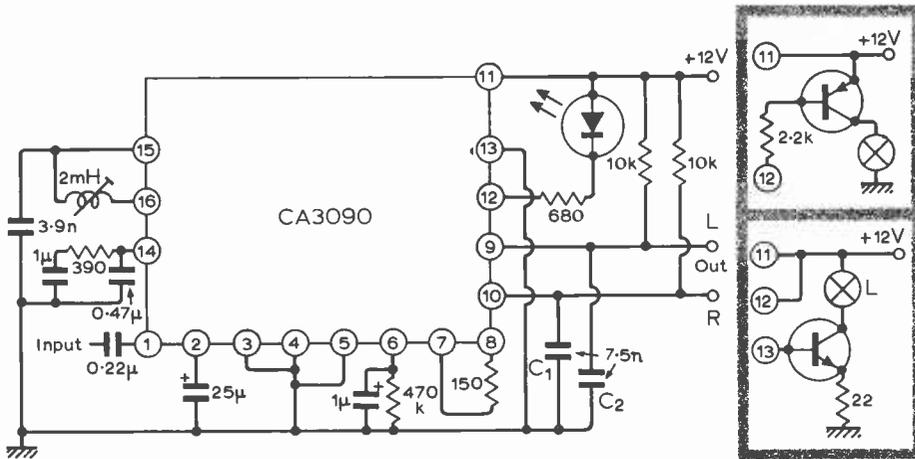


Fig. 2. Additional components required to complete the decoder. For operation in the UK ( $50\mu\text{s}$  de-emphasis) change the value of the  $7.5\text{nS}$  capacitors to  $5\text{nS}$ .

not consume more than  $14\text{mA}$  at  $12\text{V}$ . If a higher current lamp is used an out-board driver transistor must be added. The inset shows circuits using either a p-n-p or an n-p-n transistor. The transistor type is not critical provided that it can handle the lamp current. For instance, a  $40\text{mA}$ ,  $12\text{V}$ , lamp could be used if it were driven by a BC108 (use the n-p-n circuit in this case). However, the maximum lamp current—whatever the transistor used—should not exceed  $100\text{mA}$  because the drive is limited to  $14\text{mA}$ . Anyway who wants to use a searchlight to indicate that a stereo signal is being received!

The decoder can be built on the printed circuit board shown in Fig. 3 full size, or 'pin-board' construction can be employed. The  $2\text{mH}$  coil can be obtained from Harrogate Radio Ltd., 2/3 Sykes Grove, Harrogate, Yorks., price  $15\text{p}$  including postage, etc. Ask for type 87BN135BX2. The prototype used a coil of American origin. The type we have specified in fact contains two coils so for this application use coil pins 3 and 4 only. A slight alteration to the printed circuit board may be necessary. Alternatively use any  $2\text{mH}$  coil which allows a  $\pm 25\%$  adjustment.

When connecting the decoder to the discriminator output of a receiver care should be taken to ensure that the receiver's de-emphasis network is disconnected. The decoder will accept inputs between  $40$  and  $400\text{mV}$ . If the discriminator

of your receiver provides an output higher than this use a potentiometer of about  $100\text{k}\Omega$  to reduce the signal. Make sure your receiver has enough bandwidth for stereo operation.

Two methods may be employed to set-up the decoder both of which are extremely simple. If you have access to a digital frequency meter connect it to pin 15 of the i.c. and adjust the core of the  $2\text{mH}$  coil to give  $76\text{kHz}$ . This adjustment is done when there is no input to pin 1.

The second method of adjustment does not require the use of any test equipment. Connect the decoder to a receiver via a  $100\text{k}\Omega$  potentiometer and tune in a stereo broadcast. Start with the core of the  $2\text{mH}$  coil fully out and the potentiometer set to give maximum input to the decoder. Screw in the core of the  $2\text{mH}$  coil until the stereo indicator lamp lights; continue turning the core in the same direction,

counting the turns, until the stereo indicator lamp goes out. Set the core at a point midway between the points where the lamp came on and went off.

Alter the potentiometer setting so as to reduce the input to the decoder and extinguish the stereo indicator lamp. Rock the core of the  $2\text{mH}$  coil about its centre position to see if the indicator lamp lights. If not, slightly increase the potentiometer setting and rock the core again. The correct position for the coil's core is the one that lights the lamp with the minimum input signal.

R.C.A. manufacture two versions of the decoder i.c. One is in a staggered 16-pin dual-in-line package which is used in the illustrated printed circuit board and is called type CA3090Q, the second—type CA3090E—is electrically identical and is housed in a conventional 16-pin dual-in-line package. The i.c. is available from R.C.A. distributors, price  $\pounds 3.46$ .

#### Typical Decoder Specification

Input impedance	$50\text{k}\Omega$
Channel separation	$40\text{dB}$
Channel balance (mono)	$0.3\text{dB}$
Mono gain	$6\text{dB}$
Stereo/mono gain	$0.3\text{dB}$
Indicator lamp turn-on voltage*	$4\text{mV}$
Capture range (deviation from $76\text{kHz}$ centre frequency)	$\pm 10\%$
Distortion	
2nd harmonic	$0.35\%$
3rd, 4th and 5th harmonic	$0.1\%$
19kHz rejection	$35\text{dB}$
38kHz rejection	$25\text{dB}$
Input voltage range	$40$ to $400\text{mV}$
Supply voltage	$12\text{V}$
Supply current (lamp off)	$22\text{mA}$
Operating temperature range	$-40$ to $+85^\circ\text{C}$
* For improved pilot sensitivity and overload characteristics replace the $150\Omega$ resistor between pins 7 and 8 with a coil of $4.7\text{mH}$ in series with a capacitor of $0.015\mu\text{F}$ .	

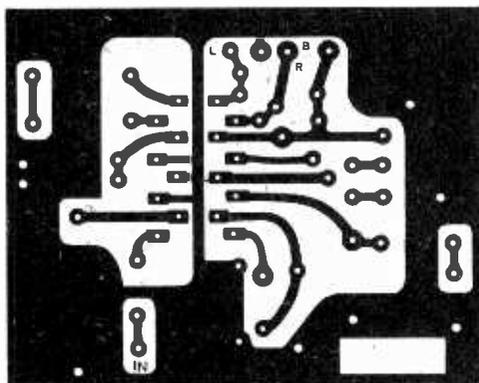


Fig. 3. Prototype printed circuit board layout shown actual size.

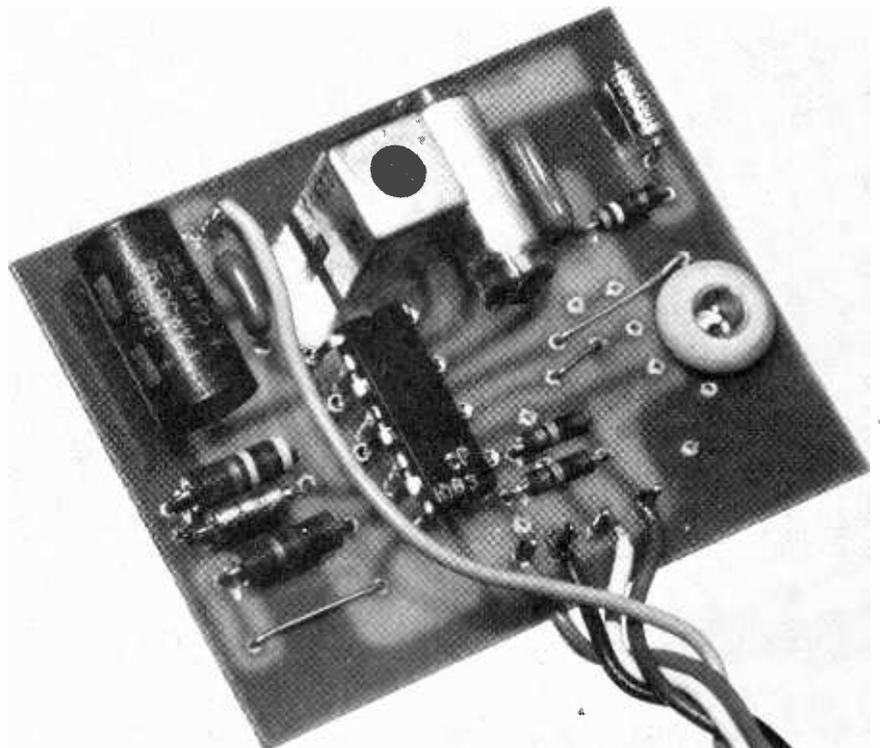


Fig. 4. Photograph of the prototype. Because this is a demonstration model built by R.C.A. some of the components shown in Fig. 2 are not included.

# Ceramic Pickup Equalization

## 2—Practical low-impedance circuits

by B. J. C. Burrows, B.Sc.

This article gives full circuit details of an economy and a high-performance pre-amplifier which use a new design principle to provide optimum performance from stereo and mono ceramic cartridges.

Many ceramic cartridges are capable of a very high standard of performance—but this is seldom realized in practice. This is because conventional pre-amplifiers cannot cope satisfactorily with the wide range of electrical parameters encountered in different makes of ceramic cartridge.

The two factors that cause the problems in pre-amplifiers for piezo-electric cartridges are (i), self capacitance, and (ii), the degree of built-in mechanical equalization. In conventionally designed circuits using high-value load resistances (1–2M $\Omega$ ), the pickup self-capacitance has a profound effect on low-frequency performance and hence on the rumble performance. Fig. 1 shows curves of output voltage against frequency for two well known pickups when operated into a conventional pre-amplifier with 2M $\Omega$  input impedance. These show that the overall frequency response is far from flat.

Typical pickups vary in capacitance from 200pF to greater than 1500pF, and with manufacturing tolerances plus the uncertain nature of the lead capacitance an overall variation of 180pF to >2000pF is possible. To obtain good l.f. performance with 180pF needs a loading resistance of 18M $\Omega$  (not 1–M $\Omega$  as commonly provided). If 18M $\Omega$  were used with a pickup of 2000pF the bass turnover frequency would be 4.5Hz! This of course would result in very objectionable rumble and l.f.

arm resonance† problems.

Conventional pre-amplifier designs do not allow for built-in mechanical equalization which varies from one pickup to another, and unfortunately the usual type of tone controls are not suitable for providing the necessary correction.

We can draw up a list of performance characteristics which an ideal pre-amplifier should possess:

- (1) l.f. performance independent of cartridge capacitance;
- (2) accurate rumble filtering independent of cartridge capacitance;
- (3) means of correcting for variability in mechanical equalization (i.e. some form of 'tone balance' control).
- (4) ability to cope with pickups of widely differing output voltages.

To these may be added: low noise, low distortion, good overload capability, built-in tone controls, etc.

### Economy pre-amplifier

The complete circuit of the economy design is given in Fig. 2 for a positive h.t.


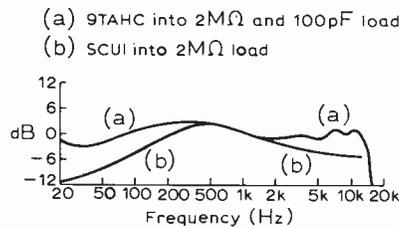


Fig. 1. Voltage/frequency curves of two well-known ceramic cartridges when used with a conventionally-designed pre-amp with  $R_{in}=2M\Omega$ , and a flat frequency response.

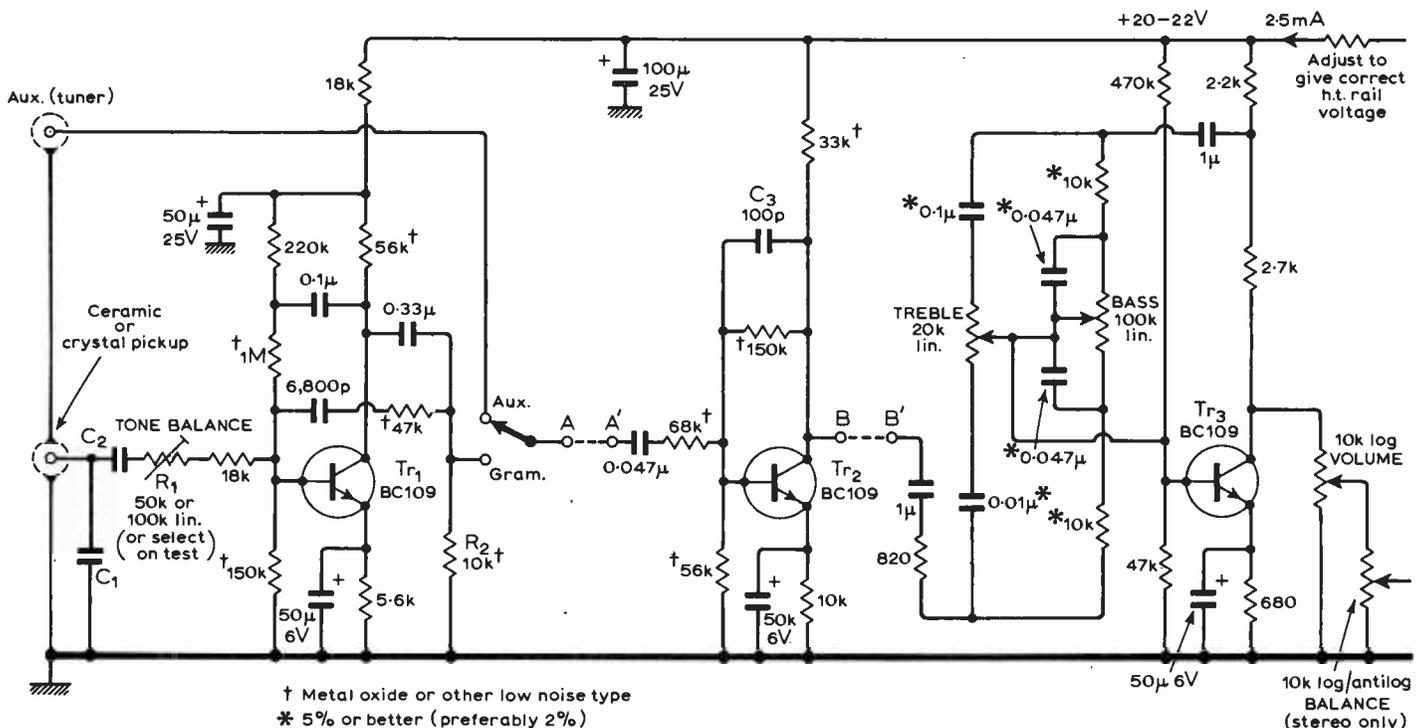


† Metal oxide or other low noise type  
\* 5% or better (preferably 2%)

†See Appendix II.

Table of values for  $C_1$ ,  $C_2$  &  $R_1$  in economy circuit.

Cartridge type	$C_1$	$C_2$	$R_1$ (optimum value)	Comment
Decca Deram } Goldring CS91E }	3.3nF	0.1 $\mu$ F	18-27k $\Omega$	low output
Goldring CS90 } Sonotone 9TAHC }			56k $\Omega$	medium output
Connoisseur SCU1 } B.S.R. SC5M }	3.3nF	0.1 $\mu$ F	22k $\Omega$	medium output
Acos GP94/1 } Garrard KS40A }			0	high output
	10nF	6.8nF	22-56k $\Omega$	

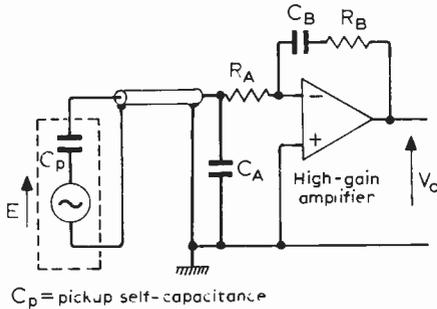

$C_p = \text{pickup self-capacitance}$   
 $\pi R_B \times C_B = 318 \mu\text{sec}$  then for a flat overall frequency response  
 $R_A(C_A + C_p) = 318 \mu\text{sec}$

Fig. 3. First-stage design of equalization circuit.


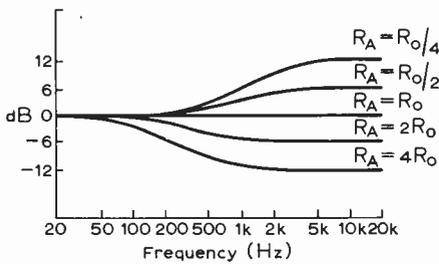


Fig. 4. Operation of tone-balance control,  $R_A$  in Fig. 3.

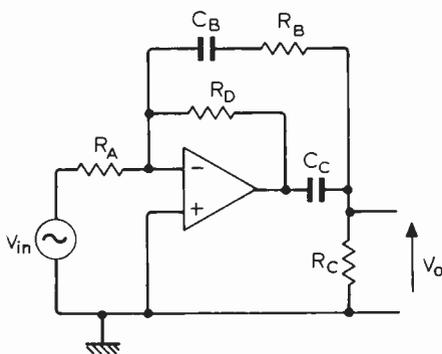

- Design formulae for  $Q=1$
- Choose  $R_C$
  - Make  $R_B$  several times  $R_C$
  - $C_B = \frac{1}{2\pi f_1 R_B}$
  - $C_C = \frac{1}{2\pi R_C} \left( \frac{1}{f_0} - \frac{1}{f_1} \right)$
  - $R_D = R_B \left( \frac{(C_C R_C + C_B R_B)^2}{C_C R_C C_B R_B} - 1 \right)$

Fig. 5. Baxandall bass lift-and-cut circuit.

rail system. A negative h.t. rail version is given in Appendix I. For normal use connect  $A$  to  $A'$  and  $B$  to  $B'$  and use full circuit. For ultra-economy operation with any of the pickups except the Deram or CS91E, the second stage may be omitted by connecting  $A$  direct to  $B'$  and omitting the intervening circuitry associated with  $Tr_2$ . Thus a very good, yet simple, gramophone amplifier may be built by using only  $Tr_1$  and  $Tr_3$  directly connected into an amplifier with 100mV sensitivity for full output.

**Design principles of equalization stage**

Last month the merits of the shunt feedback (or virtual earth) amplifier were mentioned as being very suitable for ceramic pickup equalization. Further, it was shown that loading the pickup with a low impedance had no effect on its internal e.m.f. In the present design, then, the effects of the variability in capacitance have been eliminated by swamping the pickup in every case with a shunting capacitor of 3.3nF or more. An input resistor of 75k $\Omega$  then gives an input time constant of 318 $\mu$ s (equivalent to 500Hz); to match this, the feedback circuit has a time constant of 318 $\mu$ s also (see Fig. 3); the complete circuit has a flat frequency response:

$$\frac{V_O}{E} = \text{constant} = \frac{R_B}{R_A} = \frac{C_p + C_A}{C_B}$$

If any one of the components suffixed  $A$  or  $B$  is made variable, a 'tone balance' type of control is achieved in a much simpler manner than circuits described previously<sup>1</sup>.  $R_A$  is the best one to vary and provides

performance variation as in Fig. 4. The value of  $R_A$  to give an overall flat frequency response is termed  $R_0$ . In practice only values of  $R_A$  between  $R_0$  and  $R_0/4$  are needed to fully correct all ceramic pickups for their lack of complete mechanical equalization, e.g. the Sonotone 9TAHC pickup needs  $R_A = R_0/1.8$  and the Connoisseur SCU1 needs  $R_A = R_0/4$ .

With an infinite gain amplifier in Fig. 3, overall gain is flat down to d.c. theoretically. This is no use in audio work because of rumble and the Lf. arm resonance. Some form of rumble filtering is essential and may be built into the equalization stage by using the circuit due to P. J. Baxandall<sup>2</sup>. The essence of this circuit is in Fig. 5, and its performance in Fig. 6.

**Economy pre-amplifier specification**

rated output	500mV r.m.s.
distortion (1KHz)	0.1% at maximum recorded level
noise	below audibility at normal listening level
hum	depends on layout and h.t. decoupling
overload capacity	> 6dB above maximum recorded level
sensitivity	full output for pickup with 50mVcm/sec
sensitivity is reduced by	raising $C_1$ and lowering $C_2$ to keep $C_1 C_2 / (C_1 + C_2) \approx 4000\text{pF}$
input impedance	not applicable (68k $\Omega$ for aux input connected as shown)
disc equalization	in conjunction with the better ceramic pickups can be adjusted to flat $\pm 1.5\text{dB}$ 30Hz-10KHz. Low-frequency performance independent of pick-up capacitance.
rumble filter	18dB/oct, $f_0 = 50\text{Hz}$ independent of pick-up capacitance
low-pass filter	fixed, $C_3 = 100\text{pF}$ gives $f_{-3\text{dB}} = 12\text{KHz}$ Scale $C_3$ up in proportion for low $f_{-3\text{dB}}$
tone controls	h.f. about $\pm 14\text{dB}$ l.f. about $\pm 14\text{dB}$
current consumption	$\approx 2.5\text{mA}$

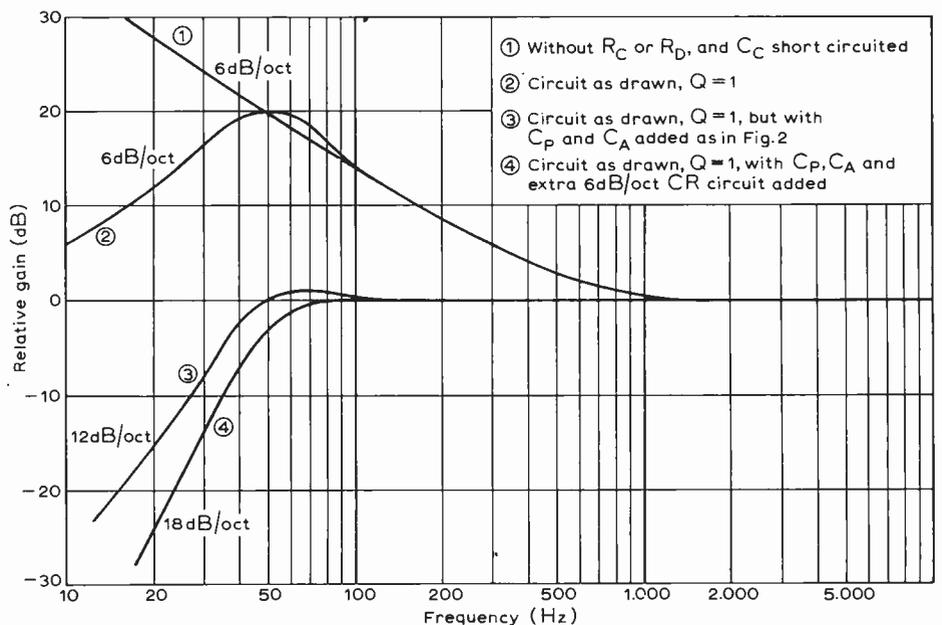


Fig. 6. Performance of circuit of Fig. 5 with  $f_0 = 50\text{Hz}$  and  $f_1 = 500\text{Hz}$ .



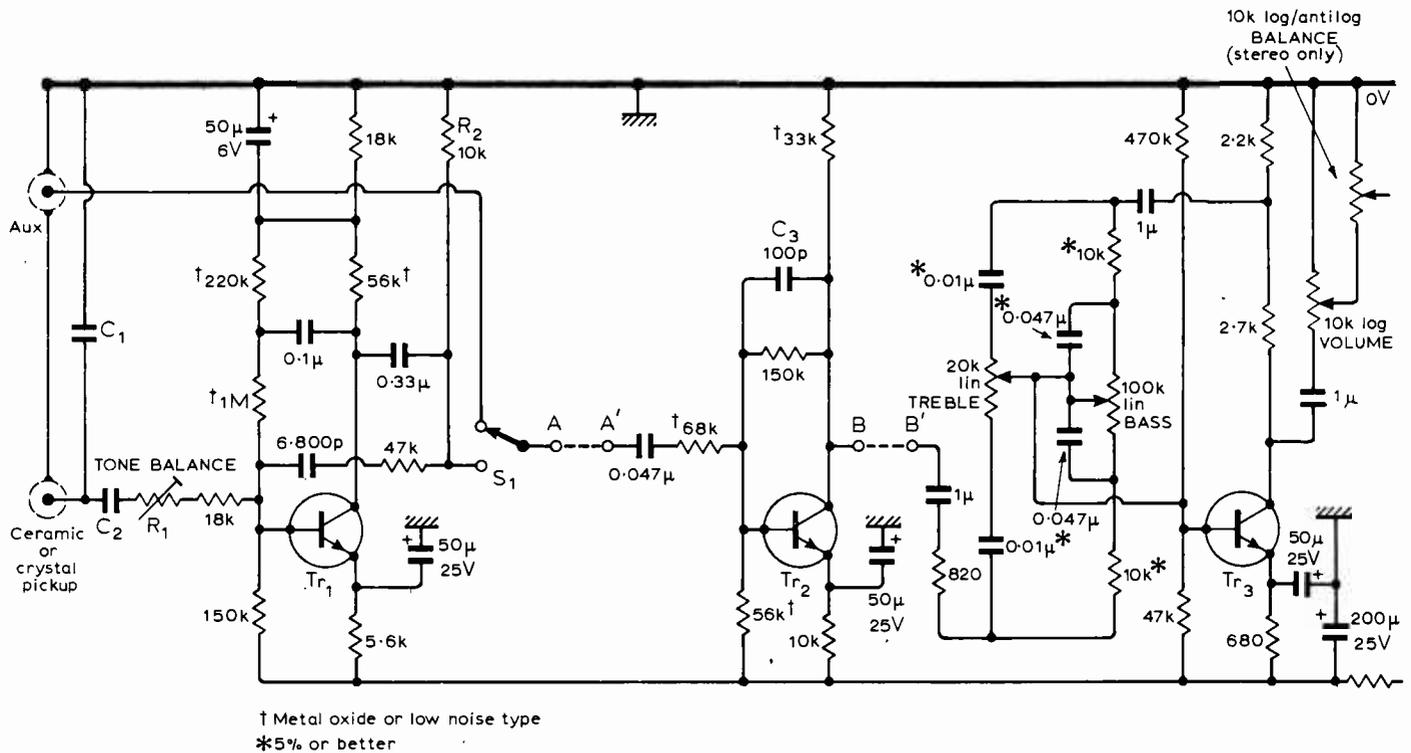


Fig. 9. Economy circuit arranged for negative h.t. rail. For values of  $C_1$ ,  $C_2$ , and  $R_1$ , see table earlier.

cartridge to give comfortable listening level with the main volume control at about half of its maximum rotation. This control need be only a preset with screwdriver slot adjustable from the back of the pre-amplifier. The tone balance could be the same, or it could be brought out as a front panel control, or as a skeleton pot mounted internally or even a 'select-on-test' fixed resistor.

On paper, the specification of the high performance pre-amplifier looks most impressive, but subjectively the economy version is very good indeed, and both represent a considerable improvement on conventional designs in that reproducible low-frequency performance, effective rumble filtering independent of pickup capacitance, and a simple means of correcting for partial mechanical equalization have been incorporated. Fig. 8 in conjunction with Fig. 1 gives a comparison of the performance of the Sonotone 9TAHC and Connoisseur SCU1 using conventional loading ( $2M\Omega$  plus flat amplifier), compared with the measured results on the author's 9TAHC using the economy circuit.

The calculated performance of the Connoisseur SCU1 with  $R_d = R_0/4$  is a straight line coincident with the 0dB line on Fig. 8, although in practice there would be a variation of up to  $\pm 1$  dB about the 0dB line.

Modifications to provide a similar standard of performance with the Dinsdale Mark I and Mark II pre-amplifier circuits were incorporated in a previous article<sup>6</sup>.

#### Appendix I

Alteration of economy circuit for negative h.t. rail operation, e.g. from a germanium-transistor amplifier like the Dinsdale Mark I or II, is basically to return all elec-

trolytic capacitors to the positive potential rail, viz. the earth line (see Fig. 9). There are no modifications to circuit values apart from the voltage rating of the electrolytics.

#### Appendix II

Arm resonance (l.f.) is the tendency toward damped oscillation at a low frequency and is exhibited by most pickup arms. It has the effect of greatly increasing the cartridge output voltage at or near the resonant frequency. The frequency,  $f_{lr}$ , is normally in the range 10-25Hz, so its effect is to greatly increase rumble. The frequency of the oscillation is:

$$f_{lr} = \frac{1}{2\pi\sqrt{MC}} \text{ Hz}$$

$M$  is the mass of cartridge plus effective mass of arm measured at cartridge.

$C$  is the compliance of stylus cantilever suspension. With  $M$  in grams,  $C$  is in cm/dyne.

With modern high compliance cartridges it is desirable to keep  $M$  very low—hence lightweight headshells—to make  $f_{lr}$  as high as possible. Generally speaking the lower the frequency of resonance the higher the  $Q$ , and vice versa. But a higher resonant frequency is more trouble electrically. A low-frequency high- $Q$  resonance causes mechanical difficulties—the pickup tends to leave the record surface when excited. A resonance at 25Hz is acceptable mechanically if the  $Q$  is low enough and its electrical effects can be removed with a steep slope filter. Below this resonant frequency the cartridge output voltage falls off very sharply indeed (24dB/octave) thus providing the required severe attenuation of sub-audio frequencies.

With regard to pre-amplifier design, the point to note is that the highest amplitude rumble components will be at, or near, the

l.f. arm resonance. A filter in the pre-amplifier should ideally provide 12dB or more of attenuation at 25Hz, yet not interfere with l.f. audio response. A cut off frequency of 50Hz with slope approaching 18dB/octave is a very good compromise since it causes very little error in the R.I.A.A. equalization, yet gives  $-15$ dB at 25Hz and  $-25$ dB at 15Hz.

#### References

1. Ambler R., 'Tone Balance Control', *Wireless World*, March 1970, pp. 124-6.
2. Hutchinson P.B., 'Tone Control Circuit', *Wireless World*, November 1970, pp. 538-40.
3. Baxandall P.J., 'Gramophone and Microphone Pre-amplifier', *Wireless World* January 1955, pp. 8-14.
4. Bailey A.R., 'High Performance Transistor Amplifier', *Wireless World*, December 1966, pp. 598-602.
5. Bailey A.R., 'Modified Treble Filter for Bailey Pre-amplifier', *Wireless World*, June 1969, p. 275.
6. Quilter P.M., Letter to the editor, *Wireless World*, April 1970, pp. 172/3.
6. Burrows B.J.C., 'Ceramic Pickups and Transistor Pre-amplifiers', *Wireless World*, February 1970, pp. 56-60.

# The Diagnosis of Logical Faults

## Conclusion

by R. G. Bennetts\*, B.Sc., M.Sc.

One of the problems that the designer and user of logical systems is confronted with is that of testing the logical functioning of the circuits within the system. The procedure is usually split into two main processes—namely a simple go/no go test followed by, in the event of a no go decision, a more thorough analysis to determine the location of the fault. The former is known as fault detection whereas the full detection and location process is termed diagnosis. It is the purpose of this series of two articles to illustrate, through the use of examples, some of the techniques that have been developed to assist in determining the necessary tests and to comment on their advantages and disadvantages. The first part of this article appeared last month and concludes this month with a discussion of Boolean difference and partitioning techniques.

### 3: Boolean difference

Before describing how the Boolean difference can be used to determine a detection test set, it is instructive to define the term "Boolean difference" and show how it may be derived.

Consider a Boolean function  $z$  given by:

$$z = f(x_1 x_2 \dots x_i \dots x_n),$$

$x_1 \rightarrow x_n =$  primary inputs

If  $x_i$  is in error, then a new function  $z_{x_i}$  is defined by:

$$z_{x_i} = g(x_1 x_2 \dots \bar{x}_i \dots x_n)$$

i.e.,  $z_{x_i}$  is formed by replacing  $x_i$  ( $\bar{x}_i$ ) in  $z$  with  $\bar{x}_i$  ( $x_i$ ). The Boolean difference,

$$\frac{dz}{dx_i}$$

is defined:

$$\begin{aligned} \frac{dz}{dx_i} &= Z \oplus Z_{x_i} \\ &= h(x_1 x_2 \dots x_n) \end{aligned}$$

\*Department of Electronics, University of Southampton

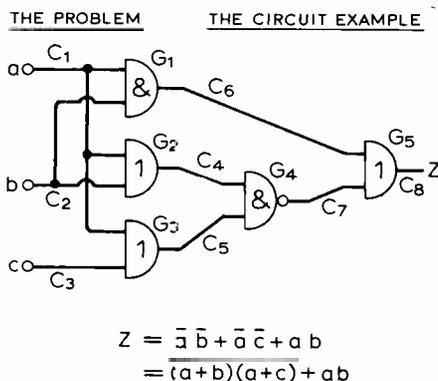


Fig. 4. The circuit example; reproduced from last month's issue.

where  $\oplus$  denotes the Boolean exclusive-OR operator.

As an example, we will derive the Boolean difference expression for the example circuit with primary input " $C_3$ " as " $x_i$ ". (This was given in Fig. 4 last month and is repeated here.)

From Fig. 4,

$$\begin{aligned} z &= \bar{a}\bar{b} + \bar{a}c + ab \\ &= \bar{C}_1 \bar{C}_2 + \bar{C}_1 C_3 + C_1 C_2 \end{aligned}$$

$$Z_{C_3} = \bar{C}_1 \bar{C}_2 + \bar{C}_1 C_3 + C_1 C_2$$

$$\frac{dz}{dC_3} = (\bar{C}_1 \bar{C}_2 + \bar{C}_1 C_3 + C_1 C_2) \oplus$$

$$\bar{C}_1 \bar{C}_2 + \bar{C}_1 C_3 + C_1 C_2$$

There are mathematical rules for manipulating such expressions but for a small number of input variables, the Karnaugh map (K-map) can be used quite easily and also serves to illustrate very clearly the actual exclusive-OR operation. The procedure is to map  $Z$  into one K-map,  $Z_{C_3}$  into another and by comparing similar locations to

derive the mapping of  $\frac{dz}{dC_3}$  by inserting a 1

if there is a difference in the values at the two locations, otherwise blank. The method is illustrated in Fig. 8.

Returning to the theory, let us examine the significance of the Boolean difference expression. If there is a fault in the value of

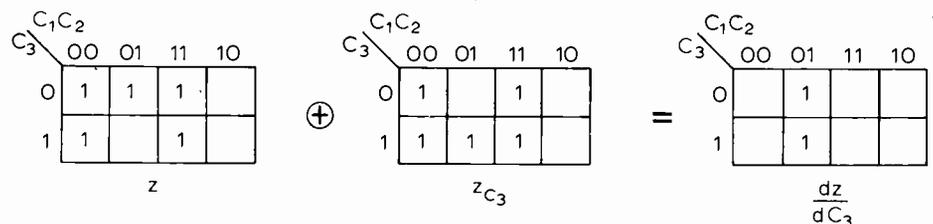


Fig. 8. Karnaugh maps for deriving  $dz/dC_3$ .

$x_i$ , then the function that the faulty network will realize will be that defined by  $Z_{x_i}$ . Under these conditions, the faulty output will differ from the true output only for

those terms that make  $\frac{dz}{dx_i} = 1$ , i.e.  $\frac{dz}{dx_i}$  de-

fines the full set of inputs (tests) that will cause an incorrect and hence observable output if there is a fault in the logical value of  $x_i$ . Note that so far we have not defined whether  $x_i$  is s-a-1 or s-a-0—only that it is logically incorrect. It therefore remains to

partition the set of tests defined by  $\frac{dz}{dx_i}$

into those pertaining to  $x_i$  s-a-1 and  $x_i$  s-a-0. This is achieved by splitting the list of all tests into those containing  $x_i$  and those containing  $\bar{x}_i$ . The former will demand a 1 on  $x_i$  and therefore test for  $x_i$  s-a-0 and the latter conversely will test for  $x_i$  s-a-1.

Thus, for  $\frac{dz}{dC_3}$  in Fig. 8:

$$\frac{dz}{dC_3} = \bar{C}_1 \bar{C}_2 C_3 + \bar{C}_1 C_2 \bar{C}_3$$

and the  $\bar{C}_1 C_2 C_3$  ( $t_3$ ) term defines the test for  $C_3/0$  ( $f_3$ ) and  $\bar{C}_1 C_2 \bar{C}_3$  ( $t_2$ ) defines the test  $C_3/1$  ( $f_6$ ). These can be confirmed from the detection matrix  $G_D$  of Fig. 6 (last month). Note that for each fault, there is only one test and hence  $t_2$  and  $t_3$  are both essential.

As another example, we will consider how the Boolean difference can be used to determine the tests for a fault on one of the lines that is not a primary input,  $C_4$  say.

As above, we have:

$$Z = \bar{C}_1 \bar{C}_2 + \bar{C}_1 C_3 + C_1 C_2$$

and  $C_4 = C_1 + C_2$

$$= \bar{C}_1 \bar{C}_2 \text{ (by De Morgan's theorem)}$$

by substitution  $Z = \bar{C}_4 + \bar{C}_1 C_3 + C_1 C_2$

$$\text{and } Z_{C_4} = C_4 + \overline{C_1}\overline{C_3} + C_1C_2$$

By using four variable K-maps, the Boo-

lean difference  $\frac{dz}{dC_4}$  is found to be given by:

$$\frac{dz}{dC_4} = C_1\overline{C_2}C_3 + C_1\overline{C_2}\overline{C_3} + \overline{C_1}C_2C_3 + \overline{C_1}\overline{C_2}C_3$$

Now, since  $C_4 = C_1 + C_2$ , the only time it will be 0 will be when both  $C_1$  and  $C_2$  are 0. Thus in order to detect for  $C_4/1$ , the input must contain the terms  $\overline{C_1}\overline{C_2}$ . All other combinations of  $C_1C_2$  will detect  $C_4/0$ . From this we see that only  $\overline{C_1}\overline{C_2}C_3(t_1)$  will detect  $C_4/1$  whereas  $C_1\overline{C_2}C_3(t_5)$ ,  $C_1\overline{C_2}\overline{C_3}(t_4)$  or  $\overline{C_1}C_2C_3(t_3)$  will serve for  $C_4/0$ , and again the fault matrix  $G_D$  confirms this.

The Boolean difference tends to be limited to circuits having a relatively small number of input variables, but it can be expressed as a fairly rigid algorithm and would seem quite suitable for implementation in a computer program. Its main advantage is in spotting essential tests and once these are known, the path sensitizing procedure (discussed last month) for evaluating all other faults detected by that test can be used. Using these two techniques together can result in an efficient procedure for deriving an optimal test sequence.

At present, the technique is restricted to combinational networks, but successful excursions into the area of sequential networks have been reported though this aspect is still very much in its infancy.

**4: Partitioning**

As has been indicated previously, the partitioning technique is more applicable to multi-flow testing procedures and this calls for certain criteria to be used. Before considering these criteria in detail, let us consider the basic technique itself.

The circuit under test is usually simulated in order to arrive at the test set for detection and/or location and the simulated model can be converted from its no-fault version  $f_0$  to any of  $n$  previously defined faulty versions  $f_1 \rightarrow f_n$ . (In the case of our example,  $f_1 \rightarrow f_{16}$ ). A test is then applied to all versions of the circuit and this will effect a partition based on the value at the output. The members of each equivalence class, as it is called, indicate that the output is the same and further tests are required to increase the degree of resolution until either  $f_0$  is identified alone (fault detection) or all versions are isolated (fault location).

The value of this procedure lies in its ability to try different tests and ascertain which one is best for the job in hand. This implies the use of criteria and we will consider initially the use of the *checkout criterion* for fault detection only. Again, we will illustrate this through use of the circuit example.

**Fault detection using the checkout criterion:** The initial equivalence class for the example circuit is  $f_0 \rightarrow f_{16}$  inclusive and we require to isolate  $f_0$  as quickly as possible by means of a set of test inputs. This amounts to determining which test separates the largest

Test	No. of faulty circuits detected			
	$N_1$	$N_2$	$N_3$	$N_4$
$t_0$	3	2	0	—
$t_1$	5	④	—	—
$t_2$	4	4	②	—
$t_3$	⑧	—	—	—
$t_4$	7	2	1	1
$t_5$	7	2	1	1
$t_6$	3	2	1	1
$t_7$	4	3	2	②

Fig. 9. Assignment of checkout weighting and selection of best tests.

number of faulty circuits from the good circuit—this being the checkout criterion. If we look at the detection matrix  $G_D$  of Fig. 6 (last month) we can list the number of detectable circuits for each test and this is shown in column  $N_1$  of Fig. 9.

Obviously,  $t_3$  is first choice and this will create a partition  $P_1$  defined by the two equivalence classes  $P_1^1$  and  $P_1^2$  where:

$$P_1^1 = \{f_0f_1f_4f_6f_8f_{10}f_{11}f_{13}f_{15}\}$$

$$P_1^2 = \{f_2f_3f_5f_7f_9f_{12}f_{14}f_{16}\}$$

The exercise must now be repeated on the equivalence class containing  $f_0$  and the test weightings are shown in column  $N_2$  of Fig. 9. This can be derived from the detection matrix  $G_D$  by removing all those columns in  $P_1^2$  and then counting the number of detectable faults on the remaining columns. When this is completed, there is a choice between  $t_1$  and  $t_2$  and we shall arbitrarily choose  $t_1$ . This creates the partition  $P_2$  given by:

$$P_2^1 = \{f_0f_1f_6f_{10}f_{11}\}$$

$$P_2^2 = \{f_4f_8f_{13}f_{15}\}$$

The procedure is again repeated until eventually at partition  $P_i$  (in this case  $i = 4$ ),  $f_0$  is isolated from all other versions and the full detection set can be defined. The remainder of the calculation are shown in columns  $N_3$  and  $N_4$  and the partition sequence is shown pictorially in Fig. 10.

**Fault location using the information gain or distinguishability criteria:** The prime object for fault location is to continue partitioning of every equivalence class until each version  $f_0 \rightarrow f_{16}$  has been completely isolated as

far as possible (obviously indistinguishable fault-sets are not subject to any further partitioning). To assist this process, two criteria have been proposed—information gain and distinguishability.

The *information gain criterion* is similar in concept to the entropy function used in information theory. Initially there is uncertainty as to which of the  $f_0 \rightarrow f_{16}$  versions of the circuit exists and the application of a particular test will remove some of this uncertainty, i.e. will result in a gain in information. This can be expressed mathematically as a function of the particular test and again a table similar to that of Fig. 9 would be created enabling the correct test selection to be made.

The alternative criterion is the *distinguishability criterion*. This is derived in the following manner: for a particular equivalence class, one wishes to select the test that distinguishes between the greatest number of circuits. This amounts to determining how many pairs of circuits within the same class are distinguishable using test  $t_i$ ,  $0 \leq i \leq n$  for  $n$  tests. This criterion is more applicable to multi-output circuits in which the partitioning is to some other radix rather than two (binary) and it too can be expressed mathematically. Since the example circuit has only one output, the partition is simple binary as shown in Fig. 10.

Both criteria are somewhat complex in their evaluation and the usual process is to derive the full detection partition using the relatively simple checkout criterion; determine the degree of diagnostic resolution that is already available and then use the more complex criteria to increase the resolution to its maximum. If this is applied to the partition of Fig. 10, it is found that only one further test need be specified in order to achieve maximum diagnostic resolution. The full partition is shown in Fig. 11 and the addition of  $t_4$  enables partitioning of  $\{f_1, f_{11}\}$ ,  $\{f_4f_8\}$  and  $\{f_5f_7f_9f_{12}f_{14}f_{16}\}$ . The remaining classes of  $\{f_7f_9f_{12}f_{14}f_{16}\}$  and  $\{f_6f_{10}\}$  are indistinguishable fault sets and consequently cannot be further partitioned without the use of extra access such as test points.

The sequence of test dictated by the partition is  $t_3t_1t_2t_7t_4$  and one aspect of this approach is that not only can the fault be located by analysis of the output sequence corresponding to the test set, but that it is now possible to specify a test for a particular fault. This is a common requirement when trouble-shooting new designs.

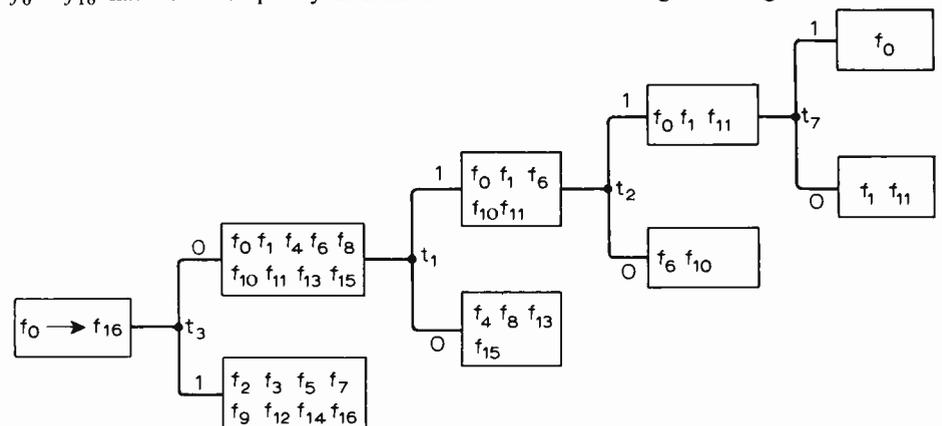


Fig. 10. Partition showing detection test set.

**Concluding remarks**

I have introduced the general problems associated with the diagnosis of faults in logical systems and described four of the techniques that have been developed to assist in determining a satisfactory diagnostic test sequence. The techniques themselves tend to be restrictive but it has been indicated how they may be combined in an attempt to broaden their overall coverage. The real problem however has been shown to be in diagnosing faults occurring in sequential circuits, and although some of the techniques can be applied, they are not really satisfactory. Other approaches are currently being studied, the most important of which is based on an analysis of the state table for a sequential circuit. (The state table is used to formally describe the behaviour of a sequential circuit—much in the same way as a truth table does for a combinational circuit. Every configuration of the sequential circuit is defined by a *state variable* and there are procedural techniques for deriving the actual circuit, in terms of its connections and gates, from the initial state table description).

One major advantage with state table analysis is that a check can be made on the table at the initial design phase to ascertain the diagnosability of the sequential circuit it describes and if necessary, apply modifications to make it fully diagnosable. This is a departure from previous diagnostic philosophy in that it is now possible to make the diagnosis requirement an initial design restraint and not something that is determined after the circuit has been designed. State table analysis does rely however on being able to formulate the state table for the sequential circuit and in the case of the intuitive design, this represents quite a problem. If however a switching theory approach has been adopted in designing the circuit, then the state table is already known and this in itself is sufficient justification for using switching theory in logical design.

In this paper, we have confined ourselves only to considering faults that can occur in logical circuits. The successful diagnosis of faults at full system level, a digital computer say, is a much greater problem and the "diagnosis is a design restraint" requirement becomes even more important. The current approach is to devise a hierarchical set of tests such that if an overall system fault is detected, a more detailed set of tests can be applied that will theoretically converge onto the fault. This can sometimes be somewhat haphazard and really what is required is a fundamentally new approach to the system design process such that diagnostic capability is a design parameter not only at circuit level, but also at full system level.

One final comment. The advent of m.s.i. and l.s.i. has caused a shift in emphasis in diagnosis requirements in that in general one only requires fault location to the smallest replaceable unit and if this is a full circuit or a sub-system itself, i.e. an l.s.i. chip, this tends to ease the locational extensions of detection techniques, such as the fault matrix, since the faults on the same chip can be grouped together and treated

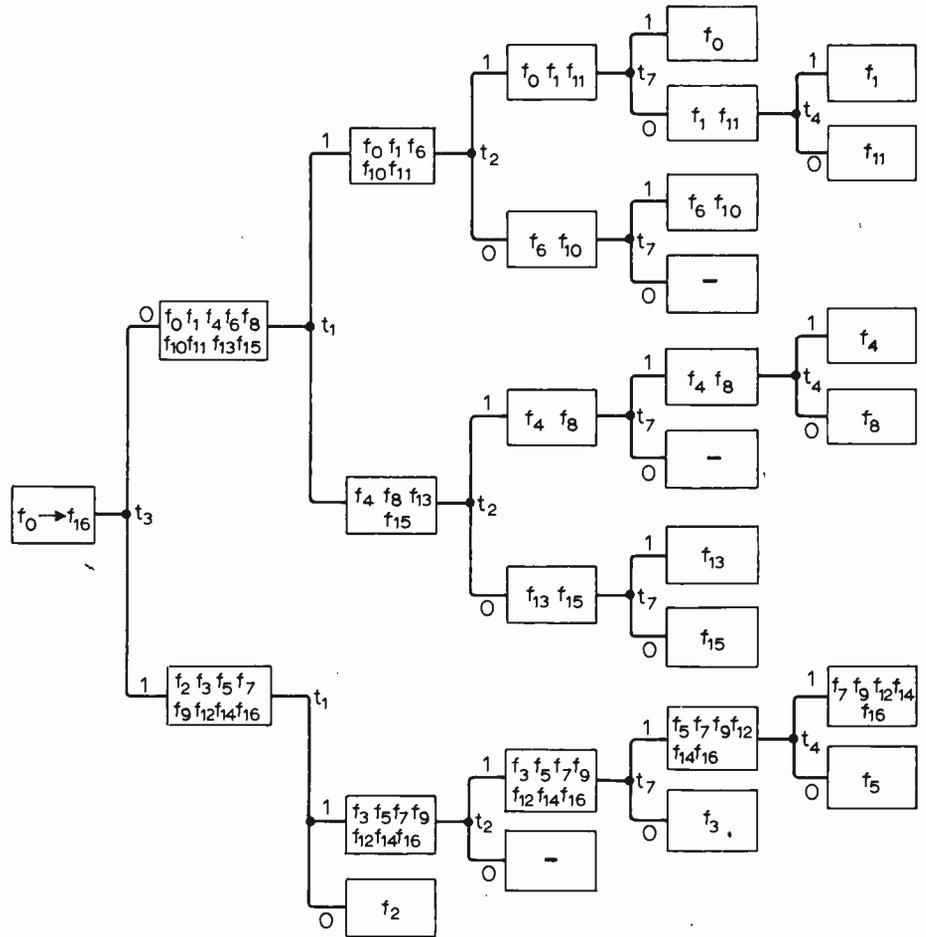


Fig. 11. Partition showing detection and location test set.

"en bloc". It does however bring us back to the overall system test problems and serves to reinforce the comments about system check-out techniques.

**References**

Since 1960, there has been a profusion of papers dealing with fault detection and location and the most recent bibliography (86 referenced papers) is including in the review<sup>1</sup> written by myself and D. W. Lewin. This paper also summarizes the main techniques and has pertinent comments on the effect of diagnosis requirements on computer system engineering, the requirements of digital systems in terms of diagnosis and functional testing and diagnosis of l.s.i.

We have recently seen the publication of the first book<sup>2</sup> to be entirely devoted to this problem and this in itself is indicative of the importance that is now attached to fault diagnosis.

In terms of the actual techniques, the paper by Kautz<sup>3</sup> is a well written and lucid account of the fault matrix approach and similar comments may be made about the paper by Sellers *et al*<sup>4</sup> dealing with the Boolean difference.

The most famous implementations of path sensitization is the D-algorithm of Roth<sup>5</sup> and its subsequent modification<sup>6</sup>. Both papers are somewhat heavy going due to the "calculus of D-cubes" that he defines and uses to implement the concept and the contents of the first paper is well covered in<sup>2</sup>. The basic D-algorithm and its extensions have been employed by IBM to prepare diagnostic routines for their System/360

range of computers.

The technique of partitioning has been programmed by Seshu<sup>7,8</sup> and the suite of programs, known as the *Sequential Analyser*, has been in use for many years now.


1. Bennetts, R. G. and Lewin, D. W. "Fault Diagnosis of digital systems—a review". To be published in *The Computer Journal*.
2. Chang, H. Y., Manning, E. G. and Metzger, G. "Fault diagnosis of digital systems". Wiley Interscience 1970.
3. Kautz, W. H. "Fault testing and diagnosis in combinational digital circuits". *I.E.E.E. Trans. on Computers*, Vol. C-17, 1968, pp. 352-366
4. Sellers, F. F. Jr., Hsiao, M. Y. and Bearson, L. W. "Analysing errors with the Boolean difference". *I.E.E.E. Trans. on Computers*, Vol. C-17, 1968, pp. 676-683.
5. Roth, J. P. "Diagnosis of automata failure: a calculus and a method". *IBM Journal R & D*, Vol. 10, 1966, pp. 278-291.
6. Roth, J. P., Bouricius, W. G. and Schneider, P. R. "Programmed algorithms to compute tests to detect and distinguish between failures in logic circuits". *I.E.E.E. Trans. on Electronic Computers*, Vol. EC-16, 1967, pp. 567-580.
7. Seshu, S. and Freeman, D. N. "The diagnosis of asynchronous sequential switching systems". *I.R.E. Trans. on Electronic Computers*, Vol. EC-11, 1962, pp. 459-465.
8. Seshu, S. "On an improved diagnosis program". *I.E.E.E. Trans. on Electronic Computers*, Vol. EC-14, 1965, p. 69-76.
9. Hennie, F. C. "Fault detecting experiments for sequential circuits". 1964, *Proc. of the 5th Annual Switching Theory and Logical Design Symposium*, S-164, pp. 95-110.

# Circuit Ideas

## F.E.T. voltage regulator

The regulator described here provides fairly good performance with a minimum number of components. The basic circuit is shown below (top). Any change in output voltage caused by a change in load resistance alters the gate-source voltage of the f.e.t. via  $R_1$  and  $R_2$ . This causes a compensating change in drain current. The stabilization ratio is excellent ( $\approx 1000$ ) but the output resistance is very high  $R_O > 1/Y_{FS} > 500\Omega$  and the output current is low. To overcome these defects, the lower circuit can be used. The output resistance is greatly reduced and the stabilization ratio is still high. The maximum output current is limited by the allowable dissipation in the final transistor. Resistor  $R_3$  is chosen to produce a quiescent current of a few mA in  $Tr_3$ . An experimental set-up using the values shown produced a change of less than 0.1V when the load current was altered from 0 to 60mA at 5V output. The effect of temperature on the output voltage has not been investigated but it could probably be minimized by appropriate choice of the drain current of the f.e.t.

C. R. MASSON,  
Edinburgh.

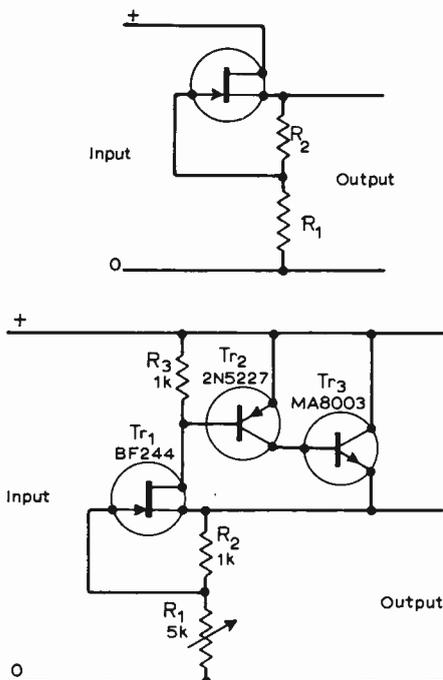


transistor to detector. The effective loading imposed by the detector on the resonator (which should be six times the impedance at the 'ring') can be taken as one quarter of the net d.c. load resistance.

G. W. SHORT,  
South Croydon.
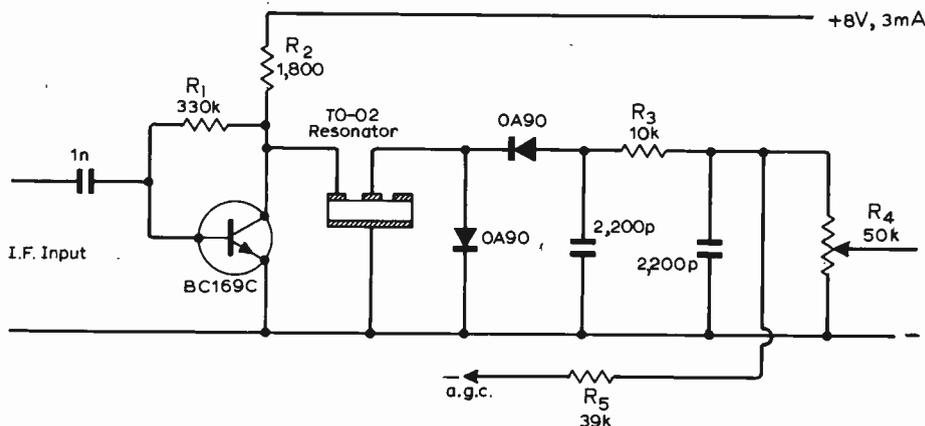
## D.C. motor controller

Fine control of a d.c. motor can be obtained using an op-amp and a tachogenerator. The op-amp is used as a voltage sensitive switch. In the circuit shown, when the output of the generator is less than the preset reference voltage the switching transistor will bottom and full power will be delivered to the motor. Switching will take place within one or two millivolts




## Reversed operation of 'Transfilter'

Piezo-electric overtone resonators (e.g. Brush Clevite "Transfilters") are normally used as interstage couplings in i.f. amplifiers, where the requirement is to match the relatively high output impedance at the collector of one stage to the relatively low base input impedance of the next. This is accomplished by connecting the 'dot' of the resonator to the collector and the 'ring' to the base. In the final i.f. stage shown above the impedances run the other way, and the resonator is used 'backwards' to couple the transistor to a high-impedance detector. This arrangement gives a useful voltage step-up (about 2.5 times) from

of the reference voltage. A dual power supply is required, but need only be zener stabilized. This system allows for infinitely variable drive without mechanical complication. For a record deck, for example, the speeds can be set by the simple switching of a voltage divider. The op-amp switches to within a volt or two of the supply rails, and by using a double emitter follower large motors can be controlled. The reference voltage may be set by thermistors, light-dependent resistors etc. The experimental arrangement shown used an RCA 3047A op-amp, and a 0.25W 6V motor as generator giving about 4V at 13000 r.p.m.

N. G. A. BOREHAM,  
Newton Abbot, Devon.

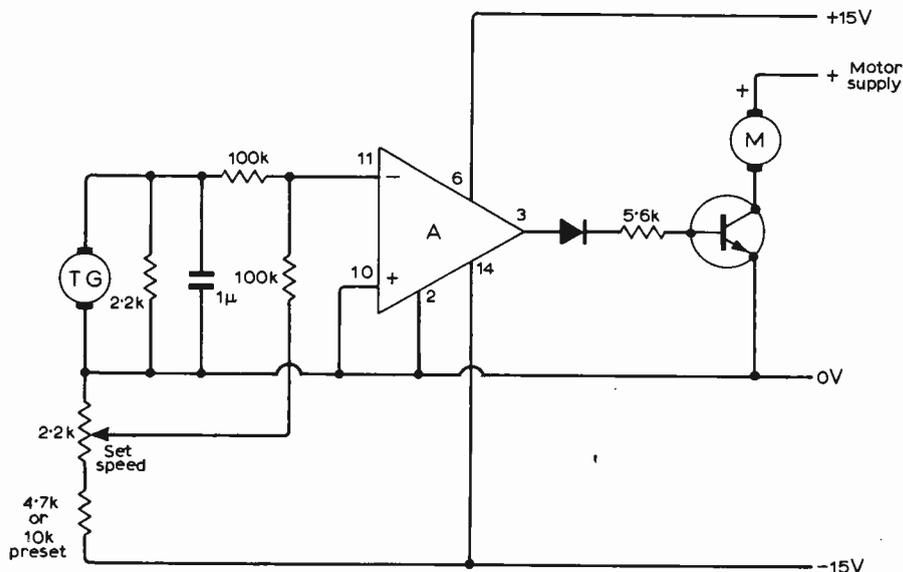

# Electro-optical Gearbox

## using moire fringe technique

by J. Dinsdale\*, M.A.

Mechanical gearboxes are generally used either for transmitting rotary power from one shaft to another, where the emphasis is on the torque ratio, or for controlling the angular velocity of one shaft with respect to another, where the emphasis is on the velocity ratio. In both cases the performance of practical gearboxes falls short of the ideal due to variable friction losses, backlash, and non-uniform velocity transmission caused by errors in the form and pitch of individual gears.

Backlash and friction effects are to some extent interdependent; in general, attempts to reduce backlash generally lead to significant increases in friction losses and the degree of backlash may be critically dependent on the working temperature of the gearbox, itself a function of friction losses.

The accuracy with which motion may be transmitted clearly depends on the precision of the form of each tooth of the gears within the gearbox. A continuous linear transmission is desirable first to maintain linearity of motion of the member being controlled by the gearbox, and second, to minimize vibrations which can be set up by a non-linear transmission. The high-frequency vibrations caused by a typical geartrain can lead to rapid deterioration of bearings and, more seriously, to the early onset of fatigue failure. This latter effect is of particular significance in aero engines, and much work has been devoted in recent years to improving the accuracy of gears used in aero engines and machine tools.

In the light of these deficiencies, the design of a "gearless" transmission system for controlling the angular velocity of a shaft with respect to another was investigated, the system to possess the following properties

- variable speed ratio from 1:999 to 999:1, numerator and denominator to be integral
- minimum backlash—less than 20 arc seconds over full working range
- input shaft speed range from zero to 2000 rev/min (nominal)
- output shaft speed range from zero to 200 rev/min (nominal)
- bi-directional motion
- output shaft power to be  $\frac{1}{4}$  h.p.

\* Principal Research Engineer, Cranfield Unit for Precision Engineering

- (nominal) approx. 200 watts
- transmission errors not to exceed 20 arc seconds at any speed or load up to the specified maxima.

The system† developed consists essentially of two shafts: an input or driven shaft, and an output or driver shaft on which is mounted an electric motor (Fig. 1). Both of the shafts are fitted with incremental shaft encoders of very high resolution. Each encoder consists of a glass disc on which has been photographed or etched a uniform pattern or grating of alternate opaque and transparent radial lines. It would not be possible to detect individual lines at this spacing by normal electro-optical means, but if such a grating is mounted in close proximity to a further small piece of similar grating (the reference grating) and the pair illuminated by white light, moiré fringes appear as a series of broad light and dark bands normal to the grating lines.

The breadth and pitch of the fringes depend on the angle between the lines on the main grating and the reference. Because each moire fringe is formed over

a relatively large area (say one sq. cm) by the integration of a large number of lines on the grating, any small pitch errors or blemishes on the grating tend to average out to give an extremely accurate fringe spacing. In fact, a grating will still give observable fringes even when 95% of its lines have been mutilated or even obliterated.

When the main grating is moved with respect to the reference, the fringes move at an equivalent rate; i.e. if the movement of the main grating with respect to the reference is at a rate of 1000 lines per second, then the fringes will move at 1000 fringes per second. The fringes are of such a size that they can easily be detected by a suitable photo-detector arrangement to give a sinusoidal signal whose frequency is proportional to the rate of angular rotation of the grating, and the number of lines on the grating. Typical gratings may have from 10,800 lines to 72,000 lines, giving angular resolutions of 2 arc minutes and 18 arc seconds respectively.

The reading head for moiré fringes normally consists of a number of photo-sensitive devices and a light source

† Patents applied for

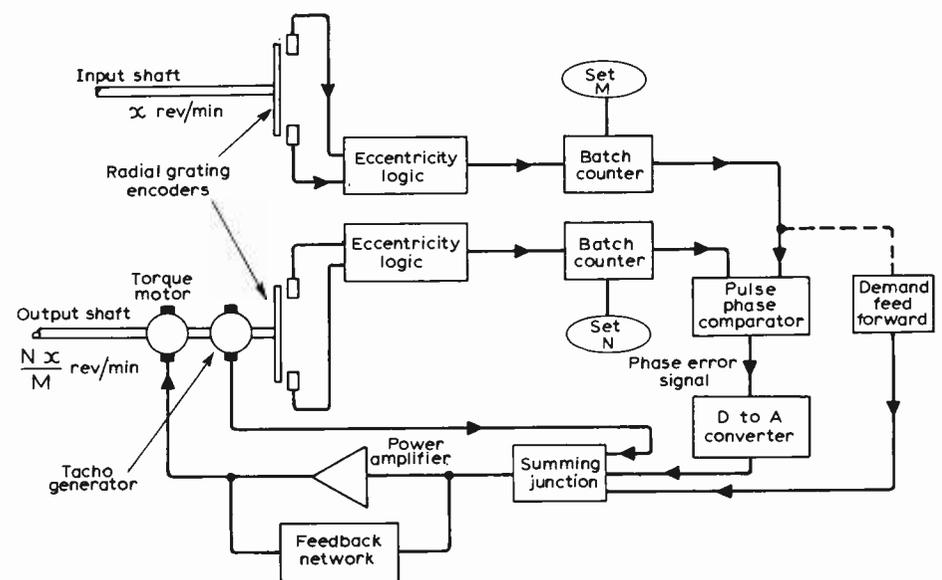


Fig. 1. In the electro-optical gearbox sinusoidal signals whose frequency is proportional to the rate of angular rotation of input and output shafts are fed to separate batch counters to set the gearbox ratio. A phase comparator provides an error signal proportional to their phase difference which controls the torque-motor driving the output shaft.

placed on either side of the small reference grating (Fig. 2). By incorporating multiple photo-sensitive devices, two signals at phase quadrature can be produced, and subsequent circuitry can determine the direction of movement of the grating.

Two diametrically opposed reading heads are normally used at each grating, and the reference and quadrature signals fed to "eccentricity logic" circuits which combine the signals in such a way as to reduce the effects of any eccentricity in mounting of the grating. In addition the signals may be interpolated electronically by a factor of up to 20 times, to increase the resolution of the system. By this means, a 72,000-line grating can give an effective resolution of 0.9 arc second.

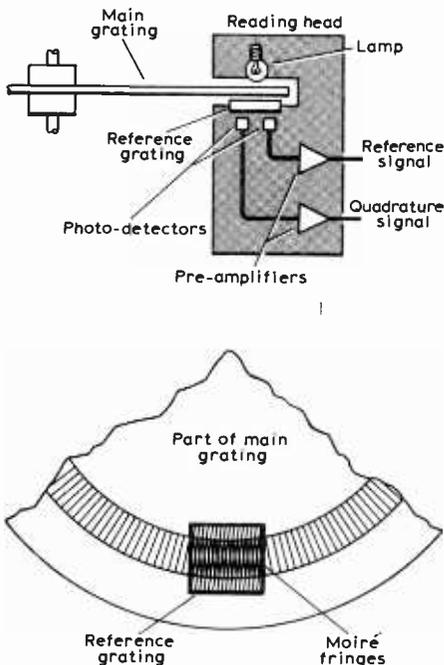


Fig. 2. In practice the encoder gratings are too fine to read directly, and a stationary reference grating is used to produce moiré fringes which move at the same rate as the shaft but are formed over a larger area. In practice two signals—in quadrature—are needed to establish direction of rotation and to reduce the effects of any eccentricity in the mounting.

The signals from each eccentricity logic or pulse multiplier circuit are squared to give a train of pulses whose frequency is exactly proportional to the speed of rotation of the shaft, with every small fluctuation shown immediately as a corresponding variation in pulse frequency.

These pulse trains are now fed to manually set batch counting circuits, which may be arranged to give an integral batch size from 1 to 999 (or higher if need be). It is by means of these batch counters that the gearbox ratio is set, a ratio which may be altered manually at any time, even while the shafts are rotating. The outputs from the batch counters are input to a pulse-phase comparator, which

produces an error signal proportional to the instantaneous phase difference between the two pulse trains, and the phase error signal is converted to analogue form, amplified and used to feed the torque-motor driving the output shaft, thus closing the negative feedback loop.

The system is so arranged that the output shaft tries to rotate at a speed which gives pulse trains of equal frequency at the comparator. In this condition the output of the comparator appears as a square wave of unity mark/space ratio, which when integrated gives zero error. Any deviation from the correct shaft speed is detected initially as a small change in the mark/space ratio at the comparator output, equivalent to a fraction of a fringe spacing. This means that the maximum error in the transmission can be reduced to a fraction of a fringe over a speed range from zero to several hundred revolutions per minute. It must be emphasized that this is a "phase servo"—not a velocity servo.

In addition to the basic system as described some additional features ensure that the specification is maintained. Local tachogenerator feed-back around the torque motor ensures system stability at very low speeds. "Direction logic" ensures that the direction of rotation of the output shaft is always the same as that of the input shaft. (Of course, a switch can be used to reverse this direction if desired.) A counting system built into the comparator ensures that any gross errors built up during vicious acceleration and deceleration will ultimately be corrected by the system and not lost.

Velocity lag error, an inherent characteristic of position servos, is eliminated. It is explained simply by saying that if the output shaft were running at, say, 100 rev/min and providing, say, 100 watts to an external load, there will be zero signal output from the comparator when the system operates with zero error, zero current either into or out of the power amplifier and hence no power to drive the load. In other words, some inherent error must exist to drive the system. Velocity lag error is reduced by feeding forward part of the demand signal directly to the power amplifier via a frequency-to-voltage conversion circuit.


The principal motor-driving signal is always supplied by the input demand, and the error circuit is used solely to correct any deviations from the ideal performance.

The electronic gearbox has many obvious applications, wherever a precise drive between two shafts is required with the absolute minimum of backlash and transmission errors. The technique is already being applied in the machine tool industry, and it is expected that many more situations will arise where the extreme precision and smooth transmission properties of this system, and especially its potentially high reliability and freedom from wear, will make it more attractive than its mechanical counterpart.
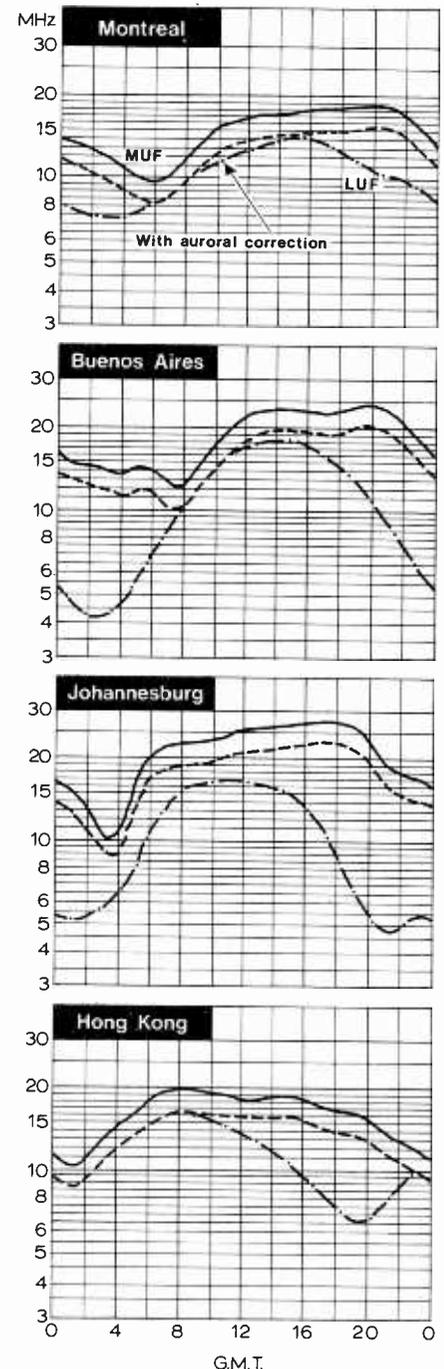
## H.F. Predictions —August

The charts show median standard MUF, optimum traffic frequency (FOT) and lowest usable frequency for reception in the UK.

LUFs are calculated by Cable and Wireless Ltd. for point-to-point telegraph circuits. Curves for domestic broadcast reception would be almost identical but for the amateur service would be typically 5MHz higher at mid-day. The variable effectiveness of low-power services is caused by day-to-day changes in the ionosphere which are on the increase at this time of the year.



# Touch-switch Controller

by R. Kreuzer

This article describes the operation and construction of three units, a touch switch, a variable d.c. memory and a thyristor power control unit. These units can be used separately in other equipment or together as described here for controlling a.c. power. If used as a lamp dimmer the longer one keeps a finger on the touch switch the brighter the lamps will become.

## Touch switch

The touch switch is a simple high-gain, high input impedance non-linear amplifier. The f.e.t.,  $Tr_1$ , provides a high input impedance and some voltage gain. The potentiometer  $R_2$  in the f.e.t.'s source is the sensitivity control which sets the bias for  $Tr_2$ . It should be adjusted so that  $Tr_2$  is just turned on with no input signal to  $Tr_1$ . When a finger is placed on the touch plate a minute a.c. voltage appears across  $R_1$  via  $C_1$  because of the capacitive coupling between the mains cable and the operator. This voltage is amplified by  $Tr_1$  and  $Tr_2$  and a 50 Hz square wave appears across  $R_4$ .

## Memory unit

The square waves across  $R_4$  charge the capacitor  $C_3$  via  $R_5$  and  $Tr_3$  so that  $Tr_5$  (connected as a source follower) provides an output voltage across  $R_8$ . A transistor,  $Tr_3$ , is used instead of a diode to prevent  $C_3$  discharging because its base-to-collector reverse resistance is much higher than that of an ordinary silicon diode. However, if the 'diode' is too perfect  $C_3$  may charge up slowly due to leakage current from  $Tr_5$  &  $Tr_6$ . This is unlikely to occur in practice but if it

does a 'less perfect diode' must be used since it is essential that  $C_3$  should be able to discharge very slowly. The unijunction transistor  $Tr_4$  discharges  $C_3$  when the voltage across  $C_3$  reaches the emitter trigger voltage of  $Tr_4$ ; thus enabling the switch to be turned off. The zener diode  $D_1$  is used to bias  $Tr_5$  so that with approximately 0.5V on its gate the voltage across the resistor  $R_8$  is approximately 2V ( $R_8 = 2.5k\Omega$ ). This voltage can be varied by adjusting  $R_8$ . It is essential that when  $C_3$  has been discharged by  $Tr_4$  the voltage across  $R_8$  should not be more than 2V. If this can be achieved only by using very low values of  $R_8$  then a different voltage zener diode should be used.

## Thyristor power controller

The voltage across  $R_8$  charges  $C_4$  via  $R_9$ . At 10ms intervals  $C_4$  is discharged by  $Tr_6$  because this transistor is operated directly from the rectified mains and, therefore, its emitter junction becomes forward biased when the mains voltage falls to zero. When an input signal is applied the voltage across  $R_8$  increases,  $C_4$  charges to the emitter trigger voltage of  $Tr_6$  and  $Tr_6$  produces an output pulse; the thyristor is triggered on. With a high voltage across  $R_8$ , say 4V, the thyristor is triggered on early in the mains cycle and maximum power is supplied to the load.

The power taken by the touch switch and

the memory is supplied by  $R_{12}$ ,  $D_3$  and  $C_5$  running from the rectified mains. The maximum current taken by the two units is 5.5mA at 10V. Diodes  $D_4$  to  $D_7$  ensure that control is provided over both positive and negative half cycles of the mains supply. High-frequency noise generated by the thyristor is suppressed by  $C_6$ .

## Construction

The method of construction used is up to the individual since it is not particularly critical. The prototype switch was assembled on two 50 x 50mm printed circuit boards one being mounted on top of the other behind the faceplate. The touch plate was a piece of copper foil 25 x 12mm glued to the front of the faceplate and covered by a thin sheet of plastic. The following points should be noted:


The wiring from the touch plate to the gate of  $Tr_1$  should not be longer than 50mm otherwise feedback from the power supply and cabling to the switch may occur.

All wiring to  $C_3$  and  $R_5$  should be as short as possible and must be self-supporting to minimize leakage current.

Resistor  $R_{12}$  should be adequately ventilated as it runs hot.

The mains on/off switch should not be omitted. The circuits can then be isolated from the mains for safety reasons.

To test the unit connect a 200Ω resistor across  $R_{12}$ , a 4.7kΩ resistor across  $R_{11}$ , connect a 12V a.c. supply to the input of the diode bridge  $D_4$  to  $D_7$  and use a 12V lamp as a load. The unit can then be set up without the danger of getting an electric shock. Remember to remove these additional components before connecting the unit directly to the mains supply. Apart from the diodes  $D_1$  and  $D_2$  and  $Tr_3$  the other component values are not critical. Although the prototype employed a 1.5A thyristor higher current devices may be used. The complete device can be used for dimming lights, controlling heaters or other electrically operated equipment.

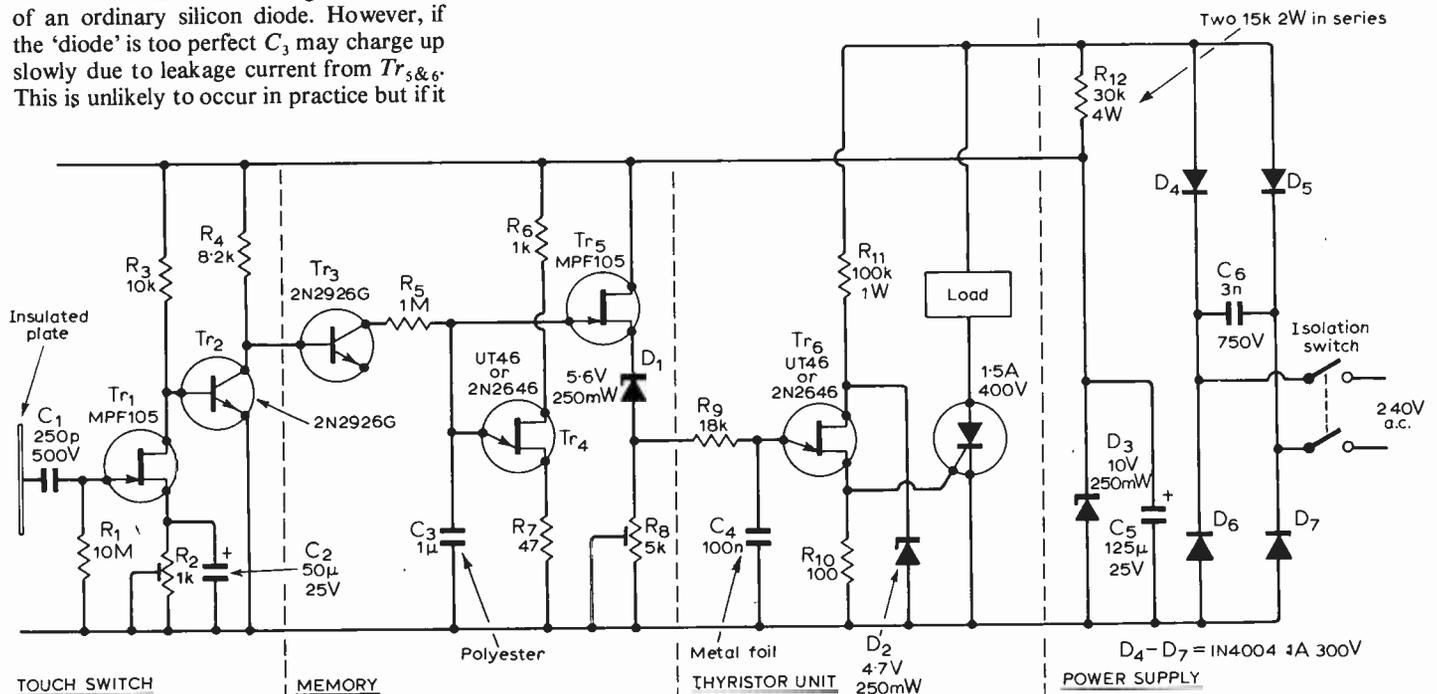

# Electronic Building Bricks

## 14. The comparator and subtractor

by James Franklin

In processing information in electronic systems we sometimes wish to compare the value of one electrical quantity with another, decide which is the bigger and which is the smaller, and perhaps measure the difference between the two. This may be needed, for example, in self-adjusting systems—say a power supply stabilizer or an electronic temperature controller—or for the control of switching operations.

Measuring the difference between two quantities is another way of saying subtraction. As such it is an arithmetical process which can be performed electronically by analogue or digital computing methods.

A familiar mechanical analogue of the comparator is the kitchen scales or the laboratory balance. One weight is compared with another and if there is any difference between them the balance arm

swings one way or the other (though there is no measurement of the actual difference). The essential principle of the balance, that one weight offsets the effect of the other, can be applied to electrical quantities. We utilize the adding methods shown in Figs 1 and 3 of Part 12\*, but reverse one of the e.m.f. or signal sources so that it opposes, instead of assists, the other. This gives the effect of adding a minus quantity—which of course is the same as subtraction.

For example if we use the method of adding voltages by series connection (shown in Part 12 as Fig. 1 (a)), to adapt this for subtraction we reverse the connections of one of the batteries—say the 6-volt one, as at Fig. 1. The 6-volt battery now opposes the effect of the 9-volt source because, as an e.m.f. source, it is acting to move electrons in the opposite direction to that in which the 9-volt e.m.f. source is moving them. The e.m.f. of the 9-volt battery is offset to the extent of 6 volts and so the net e.m.f. is 3 volts. Thus the subtraction  $9 - 6 = 3$  has been performed.

This principle can be applied to the subtraction of one continuously varying e.m.f.—a signal—from another. The connections of one of the signal sources are reversed—shown symbolically in Fig. 2 by “Signal source B” being printed upside-down—and then the varying e.m.f. of source B, instead of assisting that of source A opposes it. At each instant the effect of the e.m.f. of source B on electron movement is subtracted from the effect of the e.m.f. of source A. This is illustrated graphically in Fig. 3, where the voltage scale for  $v_A$  is drawn upwards from zero (as in Fig. 2 of Part 12) but the scale for  $v_B$  is drawn downwards from zero, by convention, so that graph  $v_B$  becomes a “mirror image” of what it was in Part 12. Values of  $v_B$  are subtracted from corresponding values of  $v_A$ , giving a set of difference values which are plotted as the graph  $v_A - v_B$ . So  $v_A - v_B$  is the varying voltage, or signal, formed by continuously subtracting  $v_B$  from  $v_A$ .

For subtraction of signals represented by varying currents, again the principle is to use the adding circuit of Part 12 (Fig. 3) but reverse the connections of one of the signal sources so that its e.m.f. acts to move electrons in the opposite direction.

Fig. 4 illustrates this for subtracting  $i_C$  from  $i_A$  and  $i_B$  instead of adding it to them. Electron flow in the common path is the result of the combined e.m.fs of the three sources. In this path there is an aggregate movement of free electrons in one direction resulting from sources A and B assisting each other, but also an aggregate free-electron movement in the opposite direction resulting from the oppositely acting source C. Since number of electrons moved in a given time is electron flow rate, which is current, the net current in the common path is  $i_A$  plus  $i_B$  diminished by  $i_C$  or  $i_A + i_B - i_C$ . Thus the signal  $i_C$  is subtracted from the signals  $i_A$  and  $i_B$ .

Digital subtraction can be performed by for example, a binary computing method or by an incremental system such as a reversible counter. In the last-mentioned, one sequence of events (e.g. electrical pulses) accumulates a total count in the normal way, while another sequence of events causes the counter to work backwards and so diminish (subtract from) this total count.

\*Correction. The Electronic Building Bricks article in the May issue, “Adding quantities and numbers”, should have been shown as Part 12.

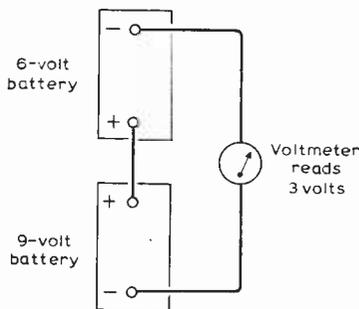


Fig. 1. Two batteries connected in series opposition give an overall voltage that is the difference between the individual battery voltages.

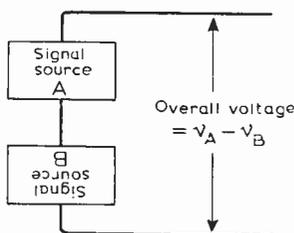


Fig. 2. The subtraction principle of Fig. 1 applied to two voltages which are varying with time.

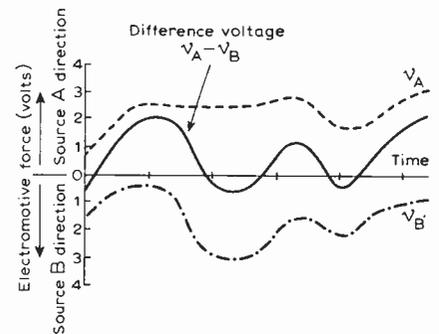


Fig. 3. Graphical illustration of what happens in Fig. 2 over a period of time. At any instant the voltage in the solid-line graph is the result of subtracting  $v_B$  from  $v_A$ .

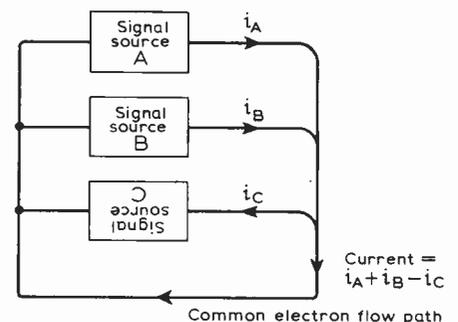


Fig. 4. Principle of subtraction with currents. Current in the common flow path due to source C is flowing in the opposite direction from that due to sources A and B.

# Charging

## A further look at the CR coupling

by Cathode Ray

In reviewing basic theory since 1911 for the 60th birthday issue of *Wireless World* I mentioned that during the second World War I was shocked to find radar instructors teaching that when (say) a positive-going input signal was applied to a CR coupling the output also went positive because of the charging of C. In actual fact (as I went on to say) any charging or discharging of C appears only as distortion of the signal at the output. I included also the words 'of course', by way of apology to readers for wasting their time by explaining where the quoted teaching was wrong. Wasn't it too obvious in these enlightened days?

Apparently not, for I soon got a letter to say that it was I, not the instructors, who was wrong. Touched though I was by this loyalty to a fine body of men, I felt that this evidence that my own experience of them was not unique called for some more detailed exposition of the point in question, in case the fallacy lingered on in a bigger way than I had suspected. I admit that some trainees might have misunderstood what their instructors taught about this. I will go farther and declare that many trainees did misunderstand what their instructors taught about this and about many other things. So not all that they taught in 1941 should be judged by what their trainees thought they said. And even if some of them were wrong on this point of circuit theory, we won the war so what the hell?

No one is likely to argue that uncertainty on the part of some radar mechs about the precise mode of functioning of inter-stage couplings in pulse amplifiers was responsible for a major loss of effectiveness in Britain's wartime radar defences, but I will and do hold that anybody who wants to be clever with electronic circuits ought not to have a fundamental misconception about how capacitors function in such circuits. So let's make sure.

The vital fact to be remembered is that the potential difference between the plates of a capacitor cannot change instantaneously, but only as a gradual process due to current flowing in or out.

This follows from the basic equation for capacitance, as important for it as 'Ohm's law' for resistance:

$$V = \frac{Q}{C} \quad (1)$$

in which C is any capacitance (in farads), Q the electric charge stored in it (in coulombs) and V the p.d. between its plates (in volts). We usually think in terms of current (amps) rather than coulombs, so we also have to remember that

$$Q = It \quad (2)$$

which means that the charge Q in equation (1) is equal to the amount of current I (in amps) that has been flowing into C, and t is the time in seconds during which it has been flowing. (To make things simple we are assuming I is constant.) Putting (1) and (2) together, therefore, we see that the voltage across a capacitor cannot change unless the capacitor receives a proportionate charge, and that takes time. If time were not allowed, t would be zero, so for any charge at all I would have to be infinitely large, which is impossible.

Fig. 1 shows the classic capacitor-charging experiment. Before the switch is closed the capacitor C is uncharged, so in the basic equation (1)  $Q=0$ , so  $V=0$ . The moment the switch is closed the voltage E is applied across C and R in series. No time has elapsed since it was closed, so  $t=0$ , so  $Q=0$ , so  $V=0$  still. So the whole of E appears across R. That

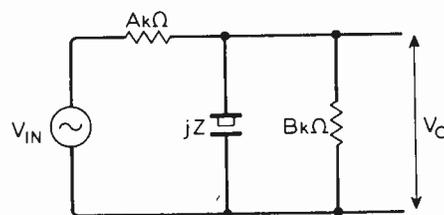


Fig. 1 The familiar circuit used to study the charging of a capacitor.

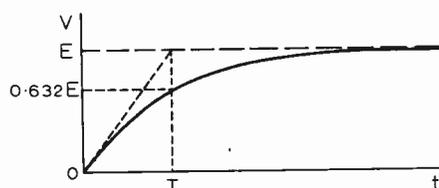


Fig. 2 The familiar (exponential) charging curve; a graph of voltage against time.

means that a current (call it I) is flowing through R, and 'Ohm's law' tells us it is equal to  $E/R$ . That same current is flowing into C, charging it. After one second,  $t=1$ , so equation (2) tells us that  $Q=I$ . And we already know that  $I=E/R$ , so  $Q=E/R$ , so  $V=E/CR$ . The capacitor voltage is rising at the rate of  $E/CR$  volts per second.

But not quite. By the end of the first second the voltage across R is no longer E; it is  $E-V$ . So the charging current is less than it was, so the rate of charging is less. The nearer the capacitor voltage gets to E, the less voltage is left to drive current through R and the slower the charging continues. This is shown by the familiar rate-of-charging curve, Fig. 2. Theoretically the capacitor never quite gets charged to the full voltage applied, E, but the deficiency soon becomes negligible.

To continue this lesson in elementary theory we draw the dotted line sloping upwards in Fig. 2 to show how the capacitor would charge if the starting rate could somehow be maintained. The instant at which C would be charged to the applied voltage E is indicated by the point at which the sloping line reaches the E level. Dropping a vertical dotted line from there to the time scale shows (or would do if the scale were graduated in seconds) how long this would take. As our scale is not graduated we will call the answer T.

From what we already know we can find a general formula for T. Combining equations (1) and (2) by substituting It for Q in (1) we get

$$V = \frac{It}{C}$$

At the end of our imaginary uniform-rate charge,  $V=E$ ,  $t=T$ , and  $I=E/R$ . So

$$E = \frac{ET}{CR}$$

and for that to be true

$$T = CR$$

I'm quite sure that all the radar instructors included this result in their repertoire, whether or not they proved it in the above or any other way. T, the time a capacitance C would take to charge to the applied voltage through a resistance R if the starting rate could be maintained, is called the time constant of the series combination of C and R. If they are in farads and ohms (or more conveniently in microfarads and megohms) T will be in seconds.

Because it refers to a mode of charging that doesn't exist in normal practice you might consider all this a waste of time. But as we noted earlier one cannot say how long a capacitor takes to charge in the real practical Fig. 1 way, because theoretically it always takes an infinitely long time, and that is not a very helpful piece of information. The only thing left, then, is to decide on how charged is 'charged'; 99%, say?

The mere suggestion may bring before you a vision of endless committee meetings all over the world trying to agree on a percentage to use as an international standard. Happily, there is no need for this. It turns out that the actual charging curve in Fig. 2 has a fixed shape, so that the time taken to charge to any given percentage of

'full' is an easily calculated factor of  $T$ , which is so simply equal to  $CR$ . The simplest possible factor is of course 1, and it happens that  $CR$  is the time taken to charge to 63.2% of 'full', as shown in Fig. 2. That looks like rather short measure. 99% requires an odd factor, so I suggest a choice of either  $4CR$  (for 98.17%) or  $5CR$  (for 99.33%).

The radar instructors probably mentioned the name of the curve of this particular shape (the exponential curve) but they may well have decided it was unnecessary (for the purpose of fitting people to keep radar equipment working) to go into the mathematics of the thing. I too am saying it is unnecessary for our present purpose, and anyone who really wants to know can find it in almost any of the textbooks on electricity (with or without magnetism). The only vital point to carry away just now is that some idea of how long in seconds  $C\mu F$  takes to charge through  $R M\Omega$  is given by multiplying  $C$  by  $R$ , and that charging is practically complete in 4 or 5 times  $CR$ .

Now we have got the basic principles straight we can apply them to a circuit of the type which might have given rise to the lecture on  $CR$  time constants. It is a circuit in which a square wave developed in the output of one stage has to be passed on to the input of another stage for amplifying, blanking, gating or whatever. Fig. 3(a) shows the relevant part of such a system. Valves are shown, because they were used in wartime radar and because in many cases the input of the second stage had such a high resistance that  $R$  was not appreciably shunted by it. Fig. 3(b) is a transistor equivalent for the benefit of those to whom valves are devices that used to be used, too long ago to be worth trying to understand. But an allowance will have to be made for the shunting of  $R$ .

The square input waveform is shown in Fig. 3(a), and the object is to reproduce it, with as little distortion as possible, at the

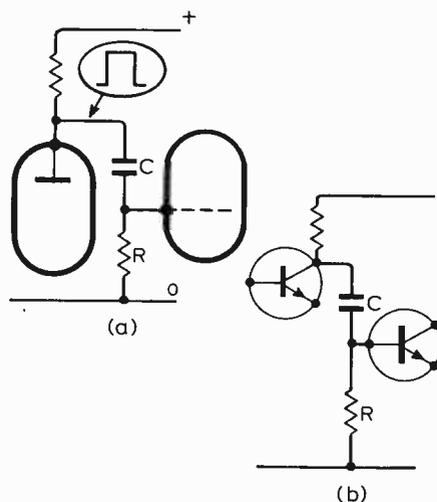


Fig. 3 The part of a circuit in which the theory developed in Figs. 1 and 2 is useful: (a) the valve version considered, and (b) its transistor equivalent.

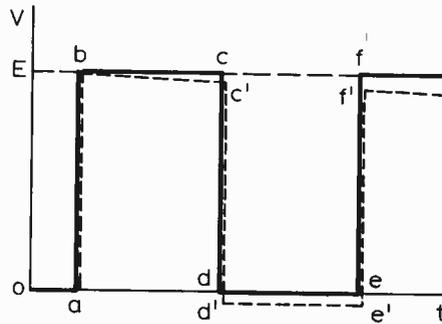


Fig. 4 The solid-line square wave is the input to  $CR$  (shown in Fig. 3), less any continuous voltage bias, and the dotted line is the output at the junction of  $C$  and  $R$ .

input to the next stage—i.e., the junction of  $C$  and  $R$ . Of course if direct coupling is used  $C$  and  $R$  are not needed and distortion does not arise, but with valve circuits especially it is usually necessary to maintain a fixed p.d. between the two stages by means of  $C$ , to keep the electrode working voltages right. When considering signal voltages this fixed p.d. can be ignored. So in the signal-voltage/time graph (Fig. 4) we can assume both the input voltage (applied across  $C$  and  $R$ ) and the resulting output voltage (across  $R$ ) start from zero level.

Up to the point on the time scale marked  $a$  the input signal voltage remains at zero, and so does the output, so there is no voltage across the capacitor, so (as equation (1) tells us) it must be totally uncharged. But at  $a$  the input suddenly goes  $E$  volts positive. (Of course it can't do this absolutely instantaneously, but let us suppose that compared with the time  $ad$  the rise time is negligible.) This is the point at which I have heard instructors go on to say 'so  $C$  charges, making the output (which is the input to the next stage) positive'. But I have, I hope, by now convinced even the most instructor-loving reader that it just isn't possible for  $C$  to charge appreciably during the rise time, and the fact that the output follows the input and goes positive to the same extent is actually evidence of it. In other words,  $C$  does this part of its job by *not* charging. For as long as it stays uncharged, both sides of it are at the same potential and the output is an exact undistorted copy of the input waveform. The ideal, then, is for  $C$  never to be charged, at all.

Let us now consider the state of affairs from  $b$  to  $c$ . Because the input,  $E$  volts, is applied across  $C$  and  $R$ , and the voltage across  $C$  alone (at  $b$ ) is zero, the whole  $E$  comes across  $R$ , causing a current to flow through it. Assuming (as we did) that the second valve takes no grid current, all the current has to go into  $C$ , beginning to charge it at a rate of  $E/CR$  volts per second. The voltage now rising across  $C$  is no longer available for  $R$  as output voltage. So the output voltage falls. How much it falls in the period  $bc$  depends on the time constant,  $CR$ . If the output is to be undistorted, it mustn't fall at all; which means that  $CR$  must be infinite. It can be made very nearly

so by removing  $R$  altogether, leaving a gap. But then the grid potential would be at the mercy of stray circuit leakages. To ensure that it starts definitely from zero (or any other designed voltage)  $R$  must be used, but its resistance should be made not lower than is needed to anchor the grid to zero volts. Provided that  $C$  also is made large enough, the drop in output signal voltage, represented in Fig. 4 by  $cc'$ , can be kept small, as shown. Incidentally, because the voltage across  $R$  is nearly constant, the rate of charge is nearly constant and  $bc'$  is nearly a straight line.

At  $c$  the input returns abruptly to zero volts ( $d$ ), and as the p.d. across  $C$  cannot change so quickly the grid side of  $C$  drops by the same voltage ( $E$ ). As it started from  $c'$ , less than  $+E$  volts, it now goes slightly negative,  $d'$ . This negative voltage,  $dd'$ , to which  $C$  became charged during the period  $bc'$ , is now applied to  $R$ , through which the charge leaks away during the period  $d'e'$ . Because the voltage is so small the rate of discharge is very small and  $d'e'$  is practically horizontal. So when the input goes positive again, from  $e$  to  $f$ , the output at  $f'$  is practically the same as at  $c'$ . It therefore starts its decline during the next positive half-cycle from a lower voltage than it did in the first.

### Effect of d.c. barrier

So long then as the output half-cycles continue to be more positive than negative, the different rates of charge and discharge bring them gradually more nearly equal, as shown by the dotted waveform in Fig. 5. In the end, whatever the input waveform, the output will arrange itself so that the time  $\times$  voltage area below the line is equal to that above the line. The line, of course, represents the level to which the output is anchored by  $R$ ; in this case zero volts. This phenomenon, which we have been examining in detail, results inevitably from the fact that a capacitor is a barrier to d.c. So a signal that starts (as in Fig. 4) all above the line, or more one side of the line than the other, inevitably adjusts itself so that this d.c. component disappears and the output is wholly alternating. The less the time constant  $CR$  the faster it adjusts—and the more distortion it introduces.

If the signal frequency is very low, so that  $C$  has a long time in which to discharge during each half-cycle, a very long time constant is needed to avoid appreciably distorting a square wave. And the system takes a very long time to readjust to a change of input amplitude. This problem arises in oscilloscopes where capacitance couplings are used in the deflection ampli-

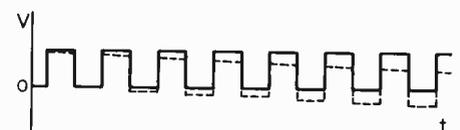


Fig. 5 How the voltage/time graph started in Fig. 4 continues.

# Single-sideband Experimental Broadcasts

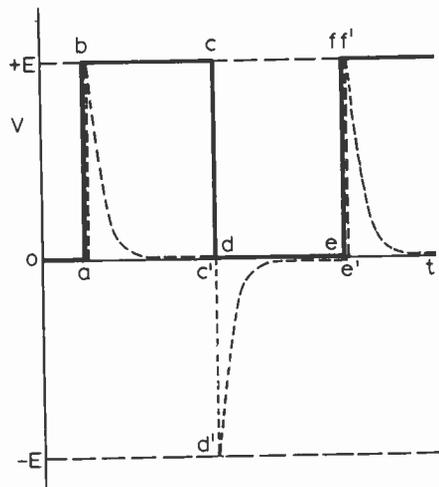


Fig. 6 Here for comparison with Fig. 4 is what happens when the time constant is only a fraction of one half cycle.

fiers. It is so tedious waiting for them to settle down that nowadays designers almost always provide direct-coupled amplifiers.

The d.c.-losing effect can be prevented by suitably connecting a rectifier in the circuit, creating a 'd.c. restorer'—but that is another story.

The only other thing I think I need mention—and it will be familiar to radar trainees past and present—is that a CR coupling is often used not to pass on the original undistorted form but to introduce deliberate distortion. The commonest application is for changing square waves into brief pulses. For this purpose the time constant is made much less, so that instead of a gradual charge such as *bc'* in Fig. 4 the capacitor charges practically completely within the half-cycle, as in Fig. 6. When the end of the square-wave half-cycle comes (*cd*) the output going negativewards by the same amount (*c'd'*) yields equal negative and positive half-cycles from the start. The negative ones can then be removed by a rectifier and the positive ones clipped by another, to give a train of pulses.

Note that (whatever the instructor said) C charges from *b* to *c'* and discharges from *d'* to *e'*, in Fig. 4 and in Fig. 6.

I used to find that even fellows who could state Kirchhoff's voltage law quite correctly when asked for it seemed to forget all about it when considering the CR type of circuit. One form of the law says that the sum of the voltages across the components in a series circuit is equal to the voltage applied. Now in Figs. 4 and 6 the voltage applied is represented by the height above zero of the 'input' waveform: alternately *E* and *O*. The Voltage across R ('output') is represented by the height of the dotted line, so the voltage across C (due to its charge) must, by Kirchhoff's law, be the vertical difference between the two. Looking at the matter this way, one can be in no doubt about when and how much the capacitor is charging and discharging.

The essential thing is to grasp the message of Figs. 1 and 2. Then a correct view of the action of any CR circuit is (to coin a phrase) a piece of cake.


For some years there have been discussions on the possibility of utilizing the medium-wave sound broadcasting band more effectively by means of single-sideband transmissions. At first sight it seems attractive in view of the fact that s.s.b. is now so well established in h.f. communications. But there are complications in reception, the main one being that the simple envelope detector found in conventional sound receivers inevitably leads to excessive distortion and must be replaced by a product detector, in which case, for tuning, a local oscillator of high stability, among other things, is required. In Britain the broadcasting authorities don't seem very enthusiastic about s.s.b. but in Germany there is considerable interest—measured by the fact that the Deutschlandfunk broadcasting organization has been putting out experimental s.s.b. transmissions from its station at Mainflingen, near Frankfurt.

The broadcasts took place in the early hours of the morning, after close-down of normal broadcasting, on 1475 kHz. At least one group of British radio research people was willing to stay up in order to study and listen to the transmissions. This was a radio section of the Department of Electrical and Electronic Engineering at University College Swansea, headed by Dr. R. C. V. Macario (author of an article on an s.s.b. receiver module in the July


issue). Some results of their monitoring are shown in the accompanying frequency spectra. Fig. 1 is a 200 kHz wide part of the m.f. spectrum showing the s.s.b. transmission at 1475 kHz, in relation to the permanent a.m. transmission from the Mainflingen broadcasting station on 1538 kHz and to Radio Luxembourg on 1439 kHz. More detail can be seen in Fig. 3, which is 50 kHz wide. The upper sideband of the s.s.b. transmission can be seen as an asymmetrical distribution of energy in contrast to the symmetrical distributions, like church spires, of the a.m. stations on each side of it. In Fig. 4 the frequency scale is 20 kHz wide and shows the upper sideband in even greater detail.

The carrier alone of the s.s.b. transmission was suppressed 20dB below the peak sideband levels, and is shown in Fig. 2, on a frequency scale 20 kHz wide.

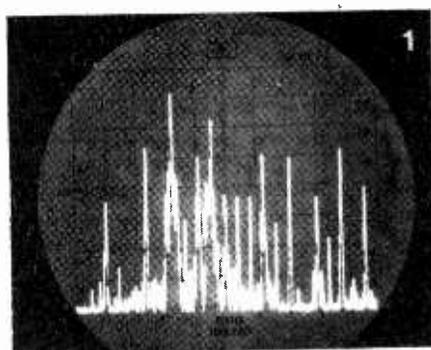
The spectra were displayed on a Hewlett-Packard spectrum analyser, model 8552A/8553L, with a stored display. A simple roof wire aerial was used. Recordings of the transmissions were made via various receiving systems, but it is interesting to note that direct conversion was possible since the lower sideband of the transmission was relatively free of interference.




Luxembourg    s.s.b.    Mainflingen

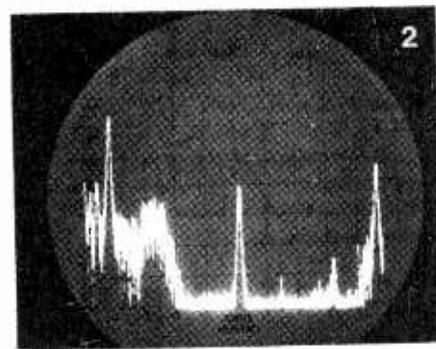

s.s.b. carrier only

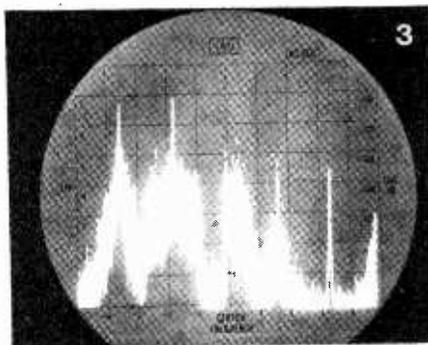

u.s.b. 1475 kHz

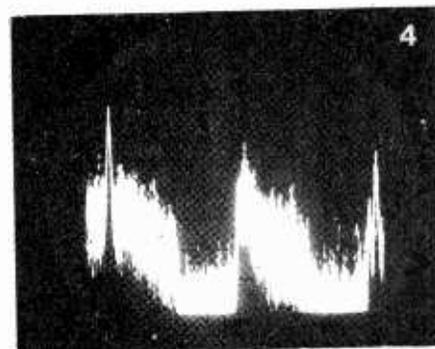

u.s.b. 1475 kHz

# Telephone Exchanges of the Future

**A new type of telephone exchange is in operation at a GEC-Marconi establishment (at Writtle in Essex) which does not use any electromechanical switches or in fact any moving parts. The system is called Martex and is typical of the sort of exchange which is to be built in the future.**

The system is a modular range of equipment which covers all aspects of switching and transmitting telephone traffic, and some types of data communications. The complete system is based on the use of digital switching and computer techniques to switch information in digital form.

Equipment employing pulse code modulation, a particular form of digital speech transmission, is now being used increasingly by the Post Office, to increase the capacity of existing telephone lines. Each telephone channel is converted into a stream of digital pulses which provide a complete representation of the original voice signals. These signals can be reconstituted into normal speech with rather less loss of quality and fidelity than would be experienced by a conventional telephone transmission line.

The great advantage of the digital network of transmission is that the spaces between consecutive pulse groups from a single voice input are arranged to be sufficiently large for a number of other pulse streams, from other telephone circuits, to be fitted into these spaces. If this is done in an ordered fashion, then a number of separate telephone inputs can be fed simultaneously along the same transmission line, and separated at the far end into the original voice signals.

This method of combining channels is known as time division multiplexing, t.d.m. It has the advantage that signals in this form make better use of the digital switching equipment.

At the start of a call, the first event in the complete sequence will be the lifting of the receiver, which will initiate a demand for a signal path into the exchange system. This will be established through a local concentrator system, which will allocate a particular time slot in one of the digital input circuits of the exchange. In the exchange system, a register will be connected to the appropriate line, through the digital switch returning 'dial tone' to the calling subscriber. The subscriber will

then dial a code, using either a conventional rotary dial, or push-buttons. When the register has accepted the complete information, the control computer in the exchange will examine the contents of this register. Using information from a magnetic drum store, it will generate control signals to produce the appropriate switching functions in the exchange, together with additional switching instruction codes for onward transmission to a subsequent exchange, depending on the routing of the call. These latter will be assembled in the memory of the 'sender', and transmitted through the system when the switching operation is complete.

On arrival at the exchange, each speech channel will have been converted into digital form by its relevant p.c.m. terminal, allocated on a demand basis in a local exchange system. The digital signals are multiplexed into groups of 30 speech channels to form a single time division multiplex signal. Two additional channels (or time slots) provide control and supervisory information. This format uses a total of 32 time slots in each signal 'frame', with a frame repetition rate of 8kHz. Each slot contains eight digital bits which define the polarity and amplitude of the speech sample being transmitted. Each incoming speech channel is thus sampled at a rate of eight thousand per second. These groups of channels enter the exchange switching system over digital transmission paths linked directly with the digital switch and its associated control system.

Concentrators will be employed which will enable large numbers of subscribers economically to be connected to a central digital exchange. The concentrators will replace small local exchanges, and will normally be connected to the main exchange through three digital links, providing for up to 90 subscribers to be connected simultaneously to the main exchange. With normal circuit usage, this would cater for 1,000 subscribers per

concentrator. Twenty five or more concentrators may be connected to the Martex switch to deal with up to 25,000 subscribers.

Each digital input circuit consists of thirty speech channels with an additional two supervisory and control signal circuits. This produces a stream of digital pulses in which every 32nd group of pulses, or time slots, relates to a particular speech channel.

Switching will require connection of input and output circuits in either the same time slot or in a different time slot. In the first case connection is by a relatively simple switching action, but in the second, time delays have to be introduced into both directions of transmission to match up the input and output circuits. This process is in addition to the normal switching process, and is also carried out under the direction of the central computer.

In both cases, any incoming signal, on a given digital input circuit, will need to be connected with another digital output. This part of the switching is carried out by providing physical connections between the appropriate wires on a matrix of crossed wires. The connection is made through solid-state digital switches which are pulsed at the 8kHz repetition frequency of the appropriate pulse group in one of the 32 time slots in each multiplexed input.

However, in general, a second type of switching, incorporating a time delay, will have to be introduced to each switched circuit, in order that it will match up with the appropriate time slot in the output circuit.

If, for example, in order to establish a particular connection, it is necessary to connect the third time slot in one multiplexed input signal to the twelfth time slot of another multiplexed output channel (i.e. nine time slots later), it is necessary to delay the input signals by the equivalent of nine time slots in the forward direction of 35.2 $\mu$ s, and 23 time slots or 89.9 $\mu$ s in the reverse direction. This is achieved by the use of 'juncter' units, which use shift registers, controlled by the central control computer, to provide the appropriate time delay.

The program control unit contains a number of processors in a fully triplicated system. Fixed program, read-only stores, provide the basic programming for the computer control system, while drum stores are used for channel routing instructions and other semi-permanent control data. Magnetic tape units are used to record call charge data and accounting information.

All critical parts of the system are fully triplicated, with a constant comparison of the data passing any point in the system. A majority voting technique is employed to ensure that a fault in one of the three systems will not introduce errors. In the event of two failures at parallel points in the system, the third channel can be switched to provide a continuous service. All three systems work in synchronism under the control of the exchange clock, to ensure that comparable data arrive at the voting point simultaneously.

# Elements of Linear Microcircuits

## 10: Amplitude modulated radio receivers

by T. D. Towers\*, M.B.E.

Despite the increasing number of f.m. sets in use, most domestic and car radio receivers are still a.m. only, usually covering the m.w. band, 540 to 1640 kHz, and sometimes also the l.w. band, 155 to 280 kHz. In this article, we will take a look at the application of linear microcircuits in this field.

When off-the-shelf linears first began to come into the hands of set designers in the mid 1960s, they offered a possible alternative to the use of six to ten separate transistors in a conventional superhet circuit, which had by then become almost a way of living. This market presented a tempting large-scale outlet to semiconductor manufacturers, and as a result a lot of effort has gone into trying to develop microcircuits for a.m. receivers.

The ideal microcircuit design for this purpose would be a device with all active and passive circuit components incorporated with the exception of the aerial, tuning control and indicator, volume control, loudspeaker and power supply. This may come some day, but for the present we must be satisfied with microcircuits which do not go as far as this.

Most approaches to the problem started from the conventional superhet circuit arrangement and were aimed at producing monolithic silicon chips containing as many of the transistors, resistors and capacitors of the discrete designs as possible. However, one school of design (using phase-locked-loop techniques to be described later) has abandoned the conventional superhet.

### Partitioning superhets

If you cannot reach the ideal solution of the single chip, then you are faced with the problem of how to break the superhet down into sections. Receiver designs using i.c.s have followed three main paths:

**Discrete approach**, in which only the active components are integrated. This fails to make use of the full potential of the monolithic circuit art because separate passive component counts are not reduced.

**Functional approach**, in which single functions of the receiver are fabricated in separate monolithic circuits and are

assembled with additional discrete components to form a complete radio.

**System approach**, in which multiple receiver functions (e.g. the mixer, oscillator and i.f. amplifier) are fabricated on the monolithic circuit chip.

The discrete approach soon proved to have no advantages over discrete assembly, and is of historical interest only. The functional approach, too, proved uncompetitive with discrete assembly but, although it has now been abandoned, we

will take a look at one example of it as a significant step towards current practice.

### Single i.f. stage

Fig. 1 (a) shows the internal circuitry of the Motorola MC1550G, a versatile common-emitter, common-base cascode-circuit high-frequency amplifier capable of 30dB gain at 60MHz but which can be used for a 470kHz i.f. amplifier in the circuit of Fig. 1 (b).

It will be seen that all the resistors and

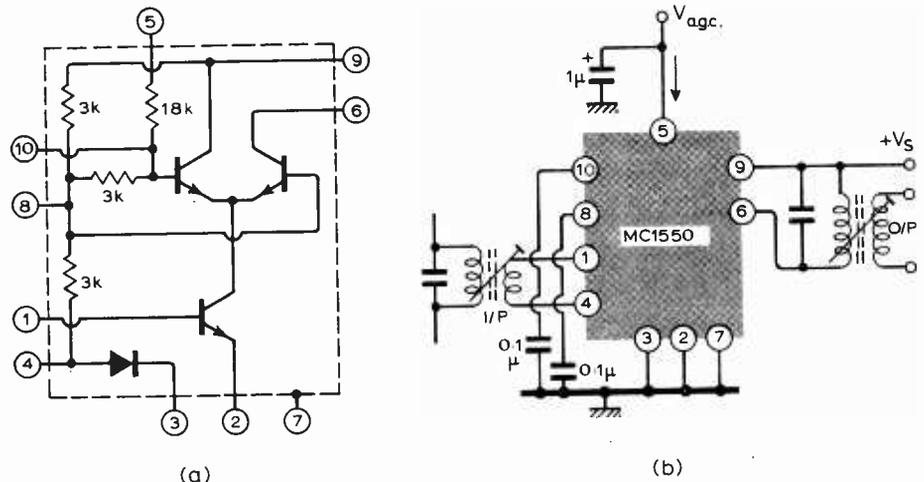


Fig. 1. Example of single-stage integration; (a) internal circuit of Motorola MC1550G r.f./i.f. amplifier; (b) MC1550G in single i.f. stage.

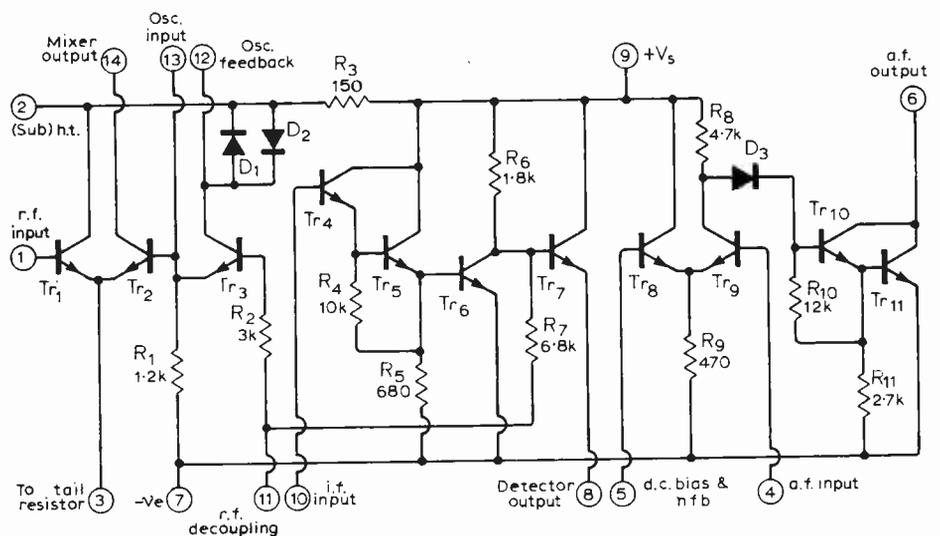


Fig. 2. Internal circuitry of Mullard TAD100 a.m. radio receiver microcircuit handling signal from local oscillator via mixer up to audio driver stage.

\*Newmarket Transistors Ltd.



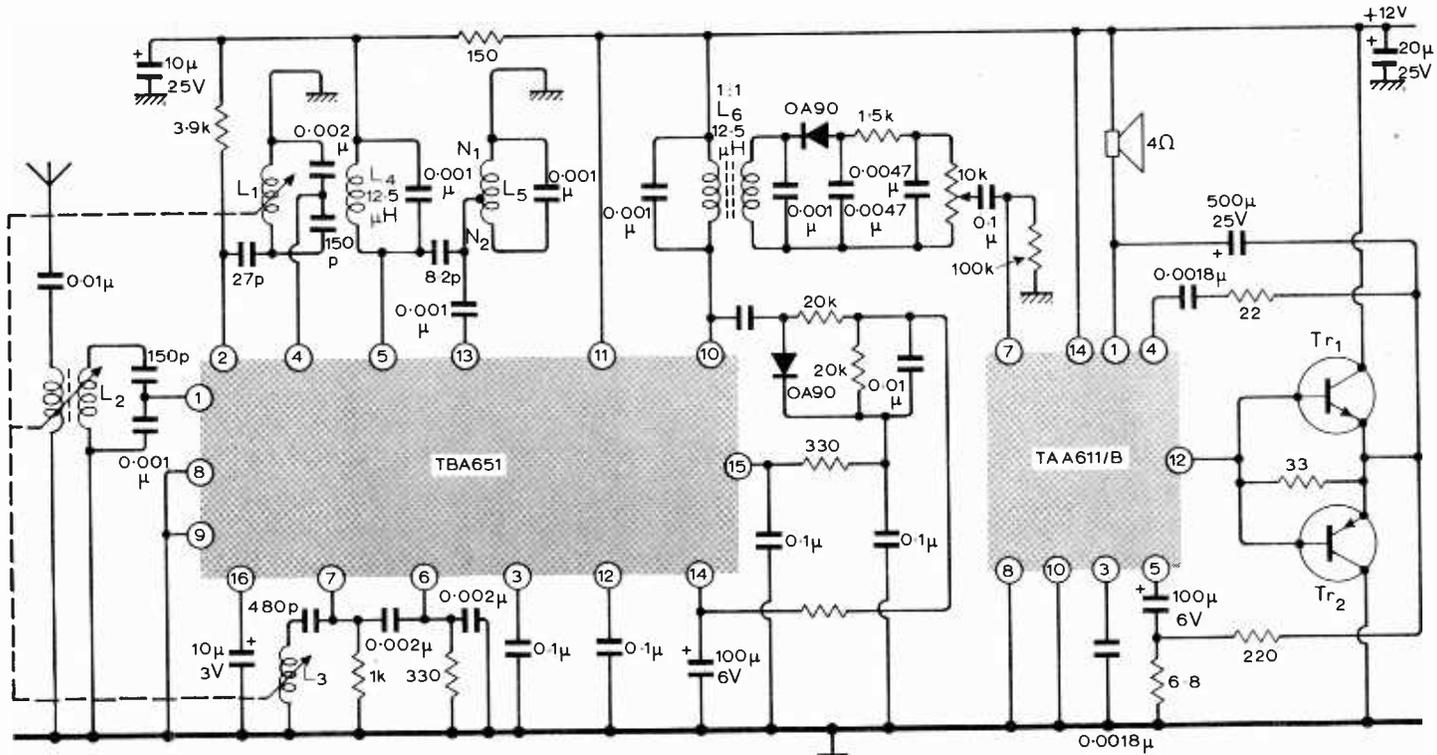


Fig. 5. 12v broadcast-band a.m. car radio receiver utilizing TBA651 microcircuit.

fed back to (1). From the volume control slider the audio is fed into (4) and reappears amplified at (6) to drive the output stage. In this design the output transistors are a discrete n-p-n/p-n-p pair in single-ended push-pull, capacitor-coupled to a 4Ω loudspeaker to give over 1W output.

At first sight there seems still to be a very large number of components outside the microcircuit, but it should be noted that most of them are passive and of wide tolerance, and unlikely to give trouble in assembly. Also the use of a block i.f. filter requiring no 'adjustment' simplifies set assembly.

**One chip, r.f. in to i.f. out**

The TAD100 was designed to integrate as much of the a.m. receiver as practicable. The a.f. output stage was left out because of dissipation limitations in the package used. A different partitioning was adopted by S. G. S. in their TBA651 linear integrated circuit that processes the whole high-frequency signal in a.m. receivers. It consists of five stages: r.f. amplifier, mixer, oscillator, i.f. amplifier, and a.g.c. control and voltage regulator and was designed primarily for high quality domestic and car radios. This explains the inclusion of a separate r.f. amplifier stage, and also the ability to work from voltage rails of 4.5 to 18V. The circuit is packaged on a 'split' (staggered pins) 16-lead dual-in-line.

In Fig. 4 you will find details of the internal circuitry of the TBA651. Tr<sub>1</sub> is an r.f. amplifier; Tr<sub>6</sub> and Tr<sub>7</sub>, the mixer; Tr<sub>5</sub> (with Tr<sub>4</sub>) the local oscillator; Tr<sub>2</sub> and Tr<sub>3</sub> the a.g.c. control on the r.f. amplifier; Tr<sub>8</sub> and Tr<sub>9</sub> (with Tr<sub>10</sub> tail current source), Tr<sub>11</sub>, Tr<sub>12</sub>, Tr<sub>13</sub> the i.f. amplifier; and Tr<sub>14</sub>, Tr<sub>15</sub>, Tr<sub>16</sub>, Tr<sub>17</sub> a voltage regulator circuit providing three output voltages to set the d.c. bias conditions of the various transistors.

An a.m. car radio circuit using the TBA651 is given in Fig. 5. A three-ganged permeability unit tunes the aerial input, r.f. amplifier and local oscillator circuits. A double-tuned i.f. bandpass circuit L<sub>4</sub> and L<sub>5</sub>, connected between (5) and (13) in series with the input to the i.f. amplifier section provides part of the required i.f. selectivity and the balance is provided by the single-tuned circuit L<sub>6</sub> at the i.f. output (10). The input LC filter can be replaced by a ceramic-plus-LC filter similar to the LP1175 for greater skirt selectivity.

In Fig. 5 it will be seen that a conventional a.m. diode detector is used externally to the TBA651; unlike the TAD100 where a transistor detector is included in the microcircuit. After the volume control, a number of arrangements are possible. In Fig. 5 the monolithic TAA611/B is used to drive a pair of output transistors (medium power, with a current gain at 3A of greater than 20) to give 5W output. A number of completely integrated 5W, 12V audio amplifiers are coming on the market with sufficient gain to be driven direct from the volume control in applications such as these, and ultimately we should see two-chip complete radio receivers.

**Phase-locked-loop alternative to the superhet**

The difficulty of microminiaturizing frequency selective circuits has shown the lack of adaptability of the conventional superheterodyne system to an integrated radio receiver, particularly in the lower frequency bands. Because of this, designers are exploring systems that do not call for such fixed-tuned frequency selective circuits.

One area where there is much activity is the p.l.l. (phase locked loop) receiver. This has been around as an idea since the early

1930s, when H. de Bellescize published an article on 'La Reception Synchrone' in *e'Onde Electrique*, Vol. 11, pp. 230-240, June, 1932. Nothing came of this, but in *Electronic Engineering*, pp. 75-76, March, 1947, D. G. Tucker raised the matter again in 'The Synchrodyne'. The p.l.l. receiver also goes variously under the names of 'Homodyne', 'Synchronous Detector', 'PL' (phase locked) and 'PC' (phase coherent).

Fig. 6 (a) shows the principle of the phase locked loop. A carrier of amplitude A<sub>c</sub> frequency f<sub>c</sub>, and phase φ<sub>c</sub>, with modulation S is applied to a phase detector which compares this input with the unmodulated output from a local oscillator of amplitude A<sub>o</sub>, frequency f<sub>o</sub>, phase φ<sub>o</sub>. If the local oscillator frequency is adjusted to equal the carrier frequency, the phase detector gives an output proportional to the phase difference θ = φ<sub>c</sub> - φ<sub>o</sub> between the input and oscillator phases. This output is then passed through a low-pass filter and an amplifier and fed back to vary the control voltage on the local oscillator in such a way as to reduce the phase difference between the two signals. The end result is that the local oscillator phase advances or retards until it is in phase with the carrier phase. The local oscillator need not be tuned exactly to the carrier frequency for the phase locked loop to operate. There is a capture effect, in that the local oscillator need be brought only roughly to the carrier frequency and the system then pulls into frequency and phase synchronism with the carrier.

The most elementary p.l.l. receiver can consist of a voltage-controlled local oscillator, a mixer (phase detector) and an audio amplifier with the audio signal fed back to control the local oscillator. In the mixer the signal carrier is converted to a

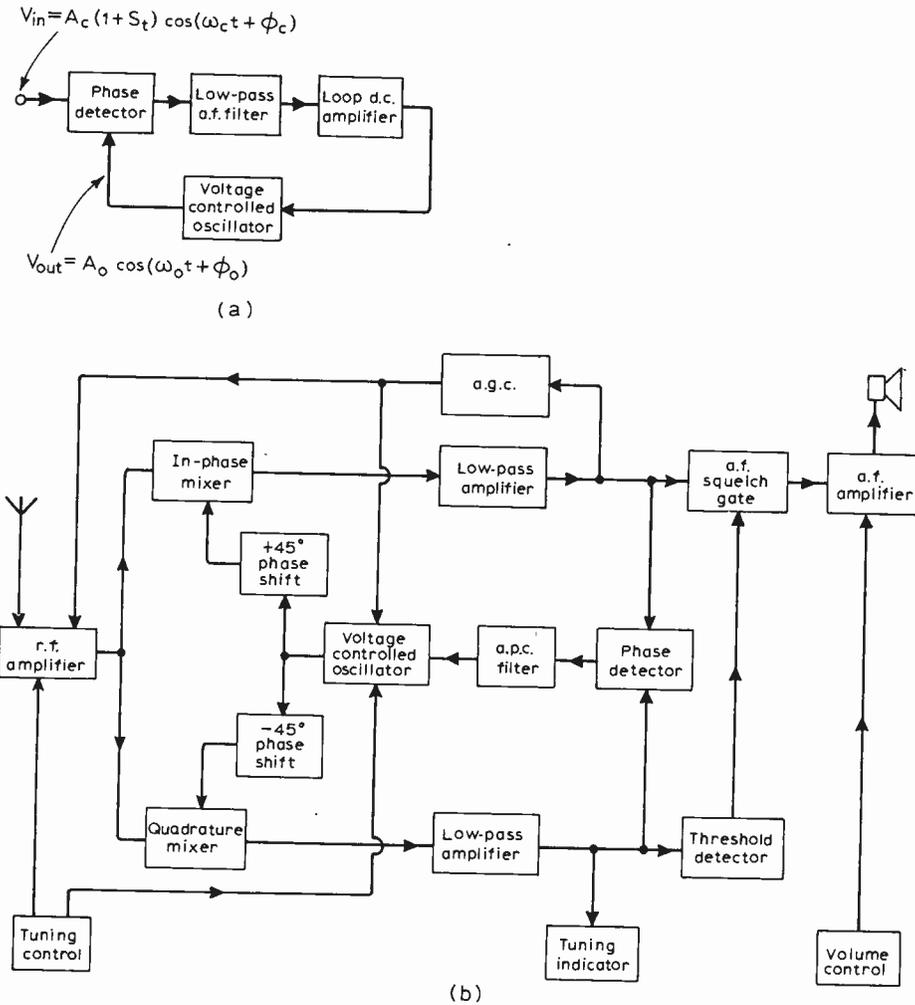


Fig. 6. The phase-locked-loop receiver alternative to the superhet; (a) basic phase-locked-loop; (b) system layout for phase-locked-loop a.m. receiver capable of implementation in microcircuit form.

zero-frequency intermediate frequency, the output from the mixer containing only demodulated information from the sidebands.

There are now indications from theoretical and experimental investigations that p.l.l. receivers are performance and cost-wise competitive with (even perhaps better than) conventional superhets. And the important thing is that the fixed-tuned LC bandpass circuits of the superhet are avoided.

The p.l.l. receiver has some distinctive advantages over the superhet, apart from the lack of i.f. coils. Any interference will not be synchronous with the local oscillator, so that the mixer output resulting from an interference signal will be a beat note suppressed by the audio filtering. Also there is no image response in the system because the intermediate frequency is zero. These nearly ideal selectivity characteristics and the lower possible thresholds of reception have led to the wide use of p.l.l. receivers in difficult signal environments such as reception from artificial satellites where low signal level, doppler shift and oscillator drift present problems. In the more mundane field of a.m. receivers, p.l.l. techniques have hitherto been prohibitively expensive, but now monolithics are appearing which would seem to make the p.l.l. domestic receiver a strong contender.

The National Semiconductor LM565

phase-locked-loop (although essentially a high quality professional microcircuit) is indicative of the sort of circuit that will soon become available to set designers. It contains a stable, highly linear voltage controlled oscillator and a double balanced phase detector. The v.c.o. (voltage controlled oscillator) frequency is set with an external resistor and capacitor, and a tuning range of 10:1 can be obtained with the one capacitor.

Fig. 6 (b) shows the outline of an a.m. p.l.l. receiver system that could be put together with currently available monolithic microcircuits. The r.f. input from the aerial is passed through a tunable r.f. amplifier. Unfortunately this still involves some form of inductance. The main purpose of the r.f. amplifier is to reject harmonics of the signal frequency to which the mixer might respond. The bulk of the receiver gain will still be at audio frequencies.

From the r.f. amplifier the input signal passes to the in-phase mixer (which can be a simple diode bridge) where it is mixed with the output from the v.c.o.—not directly but with a +45° phase-shift. The frequency of the v.c.o. will have been adjusted to approximately the right value from the tuning control. The in-phase mixer acts as a phase (and frequency) detector. The output then passes through the low pass amplifier and back via the

second phase detector, the a.p.c. (automatic phase control) filter to lock the v.c.o. to the frequency and phase of the r.f. input.

The output from the r.f. amplifier is also fed into the quadrature mixer where it is mixed with a -45° phase shifted output from the v.c.o. Through the second loop amplifier and the path phase detector-a.p.c. filter it also helps to lock the v.c.o. on signal. The quadrature signal channel can be used to drive a visual tuning indicator.

A difficulty with p.l.l. receivers is that an annoying beat note 'heterodyne whistle' is heard as the receiver is tuned between stations. This can be eliminated by a threshold detector and a.f. squelch gate. When the receiver is off-tune, there is a significant output from the quadrature channel which activates the threshold detector and holds the squelch gate closed thus suppressing audio output. On tune, the quadrature channel output falls to virtually zero, the squelch gate is opened and audio output passes to the a.f. amp and the loudspeaker.

Finally, an a.g.c. signal is taken from the in-phase channel via the a.g.c. amplifier to control the gain levels of both the r.f. amplifier and the local oscillator.

You can find a fuller discussion of the p.l.l. receiver described above in L.P. Chu 'A phase-locked a.m. radio receiver' in *Trans. I.E.E.E.* Vol. BTR 15, No. 3, pp 300-308, Oct. 1969. For the whole subject of phase-locked-loops an excellent standard reference is 'Phaselock Techniques' by F.M. Gardner, John Wiley and Sons, 1966.

(to be continued)

## Conferences and Exhibitions



Further details are obtainable from the addresses in parentheses

- OVERSEAS
- Aug. 11-13 St. Louis  
Automatic Control  
(I.E.E.E., 345 E. 47th St., New York, N.Y. 10017)
- Aug. 16-20 Jerusalem  
Impact of Computers on Developing Nations  
(Jerusalem Conf. on Information Technology, 75 Grosvenor St., London W1X 0DT)
- Aug. 17-19 Ithaca  
H.F. Generation and Amplification  
(Prof. L. Eastman, Cornell School of E. Eng., Phillips Hall, Ithaca, N.Y. 14850)
- Aug. 18-26 Budapest  
Acoustics Congress
- Aug. 23-28 Stockholm  
Microwave Conference  
(Dr. H. Steyskal, Fack 23, 104 50, Stockholm 80)
- Aug. 24-27 San Francisco  
Western Electronic Show & Convention  
(WESCON, 3600 Wilshire Blvd, Los Angeles, Calif. 90005)
- Aug. 25-27 Washington  
Geoscience Electronics  
(I.E.E.E., 345 E. 47th St., New York, N.Y. 10017)
- Aug. 27-Sept. 5 Berlin  
International Radio & TV Show  
(A.M.K., Messedamm 22, 1 Berlin 19)

# Complementary Darlington Output Transistors in Audio Amplifiers
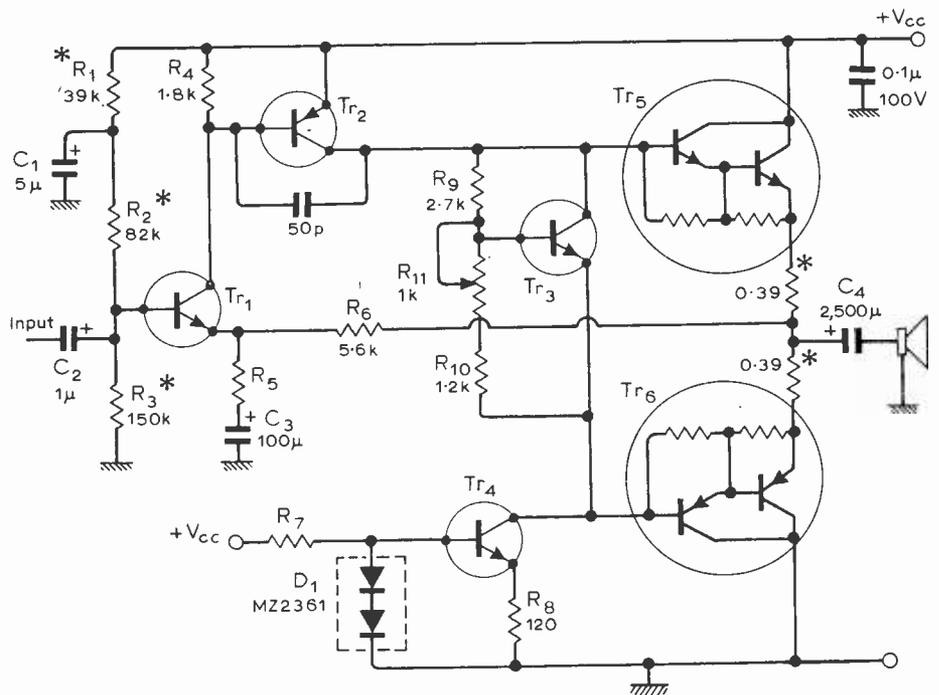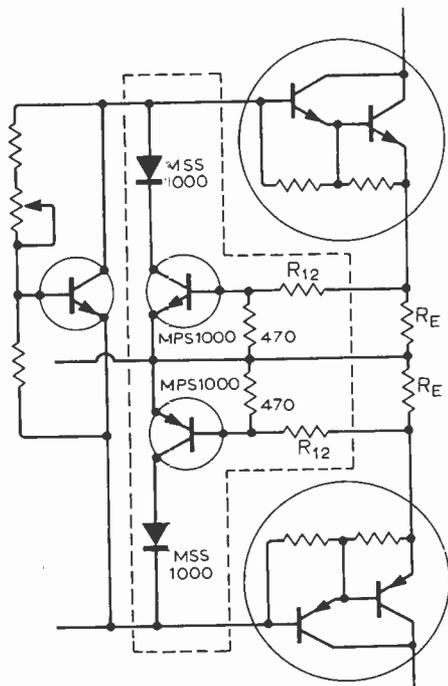
## Product application note

Circuit shown right is designed around integrated Darlington power transistors, made by Motorola. With these, external bias components are not needed and their high gains limit the gain and power dissipation requirements of driver transistors, thus simplifying amplifier designs. Design is suitable for power outputs from 15 to 60W working into a loudspeaker of 4 or 8Ω—see table. This and a direct-coupled version are contained in Motorola application note AN-483A.



Circuit gives harmonic distortion of less than 0.2% at rated output from 50Hz to 20kHz and 0.1% at 100mW output from 200Hz to 20kHz, rising to 0.25% at 20Hz for both power levels. Intermodulation distortion is 0.2% at half power with 1kHz and 10kHz signals in 4:1 ratio. Resistor  $R_{11}$  sets bias current—20mA—to minimize cross-over distortion. As an alternative to bootstrapping,  $Tr_5$  base is connected to a constant-current source— $Tr_4$  and diodes  $D_1$ . (Resistors marked with an asterisk should be 5% tolerance, others 10%.)

Several short-circuit protection techniques can be used. The short-term one shown (left) allows a short-circuit to be driven for a few minutes—average power dissipation increasing by four times—using heat dissipators with thermal resistance specified in the table and at 25°C ambient temperature.

Components for 15 to 60 watt amplifier not specified in circuit

Rated power W	load Z Ω	$R_{12}$ Ω	$V_{cc}$ V	$R_5$ Ω	$R_7$ kΩ	$Tr_{1,4}$	$Tr_2$	$Tr_3$	$Tr_5$	$Tr_6$	$C_1$ rating V	$C_{2,3}$ rating V	$C_4$ rating V	heat sink†
15	4	330	32	620	33	MPSA05	MPSA55	MPSU01	MJE1100	MJE1090	35	20	40	9.5
	8	150	38	510	39	MPSA05	MPSA55	MPSU01	MJE1100	MJE1090	40	25	45	9.5
20	4	470	36	560	39	MPSA05	MPSA55	MPSU01	MJE1100	MJE1090	40	25	45	7.0
	8	180	46	470	47	MPSA05	MPSA55	MPSU01	MJE1100	MJE1090	50	30	55	7.0
25	4	510	38	560	39	MPSA05	MPSA55	MPSU01	MJE1102	MJE1092	40	25	45	5.0
	8	220	48	390	47	MPSA05	MPSA55	MPSU01	MJE1100	MJE1090	50	30	55	5.0
35	4	750	44	470	47	MPSA05	MPSA55	MJE520	MJ3000	MJ2500	45	25	50	6.0
	8	390	56	330	56	MPSA06	MPSA56	MPSU01	MJ1001	MJ901	60	35	65	5.5
50	4	910	50	390	47	MPSA05	MPSA55	MJE520	MJ3000	MJ2500	50	30	60	4.0
	8	560	65	270	68	MPSA06	MPSA56	MJE520	MJ3001	MJ2501	65	35	75	4.0
60	4	1k	56	330	56	MPSA06	MPSA56	MJE520	MJ3001	MJ2501	60	35	65	3.0
	8	620	72	220	68	MPSA06	MPSA56	MJE520	MJ3001	MJ2501	75	40	80	3.0

†Maximum thermal resistance in deg.C/watt at 55°C ambient temperature and 10% high supply voltage. Heat sink area can be found from J. Johnstone's nomograph on p.22 of January 1971 issue (instruction 5).

# Automatic Titration Potentiometer

by D. R. Bowman, M.I.E.R.E.

The instrument described employs dual-gate m.o.s.f.e.t.s and was originally intended to monitor a chemical process known as titration. However the measuring circuit can be used for other applications in which an electrometer is required.

A measuring circuit was required that would link the output of a very high internal impedance probe with an indicating apparatus such as a chart recorder. The probe in question had an internal impedance in the kilo-megohm region and an output of between 100 and 400mV. One of the various thermionic electrometer valves available would have performed well but with the disadvantage of requiring h.t. and l.t. power supplies. Investigation of the various semiconductor amplifying devices available revealed that only the m.o.s.f.e.t. approached the input resistance requirement. Previous experience with these transistors has taught the author to be wary, for although the gate-to-source breakdown rating may be 20 or 30V the high inherent resistance inevitably means that even the smallest charge cannot leak away and is liable to accumulate until the gate insulation is destroyed.

A number of transistor manufacturers

being alive to this problem have introduced devices with zener diodes internally connected across the gate electrode. The diodes exhibit a very high shunt resistance until the potential across them exceeds about  $\pm 6V$ . At this potential their resistance drops to a low value and so protects the transistor's gate insulation.

The basic circuit, which is shown in Fig. 1, is a differential amplifier. The d.c. level drift with temperature, an always present problem in electrometer amplifiers, is not so serious here because the drifts in the two transistors are in opposition and therefore tend to cancel each other.

To maintain the maximum input resistance a gate leak resistor has not been included, however, the probe's series resistance provides an earth return for the gate electrode. The first device operates as a source follower, the inherent negative feedback tending to maintain the high input resistance. The second stage is connected as a common gate amplifier.

The overall power gain provided by the amplifier is of the order of 70dB.

The second gate electrodes of the cascade devices are connected together and biased to about 0.6 of the drain potential. The two source electrodes are taken via a potentiometer to earth. This couple is adjusted for minimum thermal drift. The output potentiometer alters the gain slightly, but is primarily intended for setting the output to zero when there is no input signal. The exact amplitude of the output signal is unimportant when the instrument is used in titration so this deficiency has not proved to be a great disadvantage. No attempt has been made to match the m.o.s.t.s and yet the temperature stability has proved to be adequate.


Two transistor types are suitable, the 40673 and the 3N187. Of these the 40673 seems to be the best choice; it is identical in performance with the 3N187, but is considerably cheaper.

## Power supply

The circuit shown in Fig. 2 exhibits a very low output ripple together with automatic overload protection. As the series regulating transistor is capable of supplying at least 200mA other auxiliary equipment can be connected to the supply if required. In the diagram an unearthed 9V unit is shown whose polarity can be altered by earthing either the positive lead for +9V. This instrument requires two such supplies, one of each polarity. The mains transformer used is a Radiospares miniature type with two 12V secondaries, but any other transformer with two independent secondaries will do as the current requirement is only 10mA. The two power supply circuits should be adjusted to provide about 9V.

The setting up of the amplifier is extremely simple; the only point needing description being the minimum thermal drift adjustment. The dual gate m.o.s.t.s are mounted in an electrically insulated dual heat sink. A hot soldering iron should be brought into thermal contact with this heat sink and the potentiometer adjusted

Fig. 1. Circuit of the amplifier unit. The switched capacitors are used to filter out interference from the magnetic stirrer which is employed during titration.

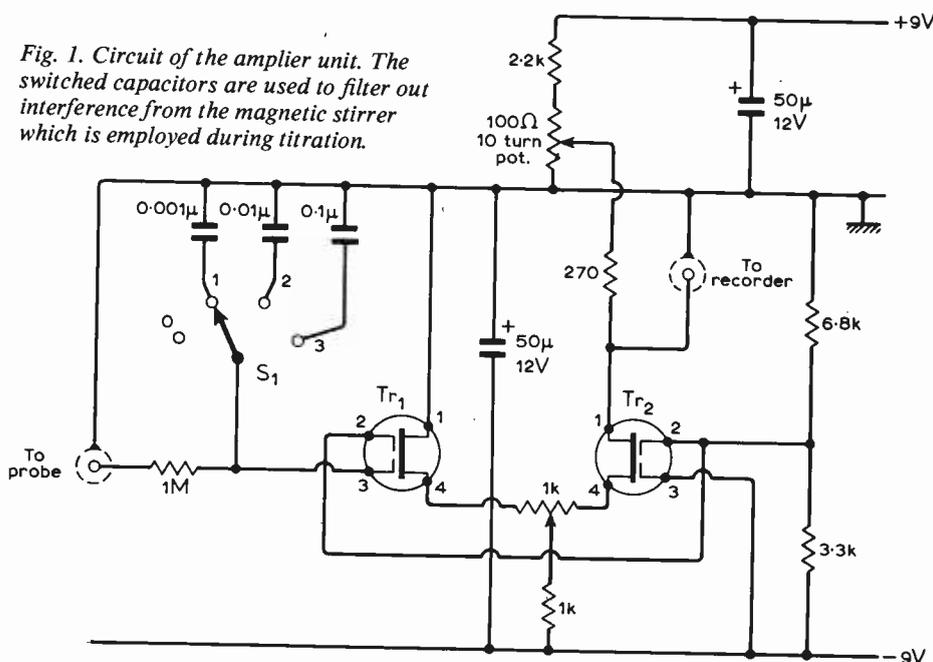

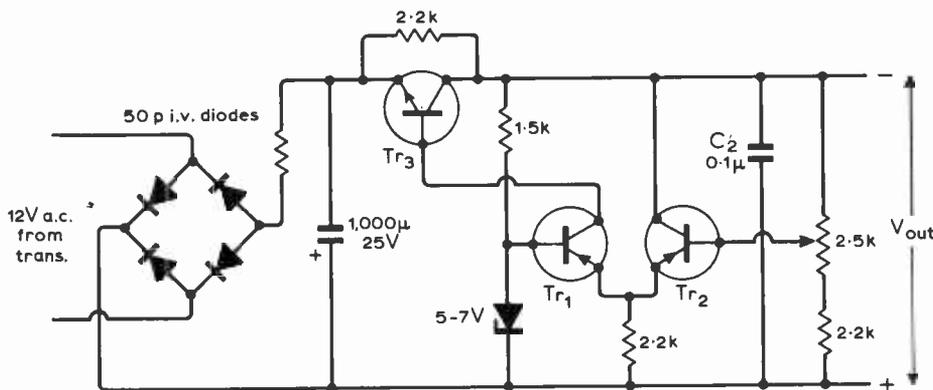


Fig. 2. Power supply circuit. Two of these are required.

for minimum drift as shown by the recorder. The gain potentiometer should be used to set the amplifier for zero signal out with the input short circuited.

**Titration**

Many quantitative chemical analyses are made by adding measured amounts of acid to the unknown alkali solution until the two cancel one another out to leave a neutral solution. The stage at which balance occurs, the end-point, has to be determined very accurately and is normally done using one of the coloured chemical indicators of which Litmus is an example.

If two electrodes are dipped into the solution during the titration process the voltage across these electrodes will change as the solution goes through the neutral point. It was to detect this change that this instrument was designed.

The probe employed was a 'Silver billet combination electrode' (Cat. No. 39187). During the titration process the mixture was stirred using a magnetic stirrer and a piston burette was used to add one liquid to the other. The piston burette is driven by a motor and adds liquid at an accurately known rate. As this motor is synchronous the chart recorder and the piston burettes will automatically keep in step.

The titration probe and amplifier tend to be sensitive to noise generated by the

magnetic stirring system and for this reason a switched filter has been included in the input circuit of the amplifier. This filter should be used with care, only enough smoothing being used to reduce the noise or the response of the whole system may become excessively damped. Fig. 3 shows a basic differentiating circuit which if applied to the output of the amplifier and used in turn to drive the recorder makes the titration end point on the graph more easy to discern. With this simple circuit it will be necessary to increase the sensitivity of the chart recorder.

biplane in this country. In the latter case no loose wires were used, and thus he had been limited to the amount of aerial that could be attached to the machine itself—about 50 ft. Instead, however, of using balanced aeriels, he coupled them to each end of an inductance coil, and increased their effective length to the greatest extent possible without sacrificing efficiency. In the latest form of the apparatus he was using a 6-in. induction coil with a 1/8-in. spark gap, fixed at a considerable distance from the apparatus, so as to be away from the petrol tank. Two light brass rods extended from the coil well into the space between the two main planes of the machine, and to one side of the tank, and two 1/8-in. brass rods sliding over these and 1/8-in. apart formed the spark gap terminals. Shunted across the spark gap was a condenser of the Leyden jar type, and an inductance coil consisting of seven turns of No. 14 copper wire wound on a light ebonite drum. This inductance had sliding contacts so that the number of turns used could be varied in the usual manner, in order to tune the two circuits. The two aerial wires were connected to the two ends of the inductance in use, and the aerial circuit was brought into tune with the shunt circuit. A secondary battery of eight or ten volts supplied the primary energy, about 50 or 60 watts being required.

"Two new arrangements have since been adopted, which should greatly enhance the efficiency of the plant. The chief of these is a long light brass tube attached to, but insulated from, one side of the tail of the aeroplane. This acts as a counter capacity, or 'earth', to a long aerial wire on the other side. This aerial starts from the nose of the machine, is carried thence to the extreme outer edge of the main plane, thence back to the tail, and thence to a loose extension, a length of 60 ft. of copper wire trailing behind."

Coming down to earth, another article, 'At the Royal Investiture', described how two Marconi portable wireless telegraph sets were used at the Investiture at Carnarvon of the Prince of Wales. These particular sets were normally employed by the Cumberland Yeomanry and as can be seen from the photograph, consisted of a motor generator and the wireless set itself. It is pictures like this which emphasize the tremendous advances that have taken place in just sixty years.

**Sixty Years Ago**

August 1911. Two reports in this issue were concerned with mobile communications. An article 'Wireless Telegraphy and Aeroplanes' described an experimental installation as follows:

"In a lecture before the Royal Institution, Mr. T. Thorne Baker passed in review some of the work already accomplished in the application of wireless telegraphy to aerial navigation and referred to some satisfactory results obtained by Mr. Farman by using two trailing aeriels, each consisting of rather thin wire about one hundred metres in length. Those experiments were carried out some time after Mr. Baker had adapted a similar arrangement to a Bristol


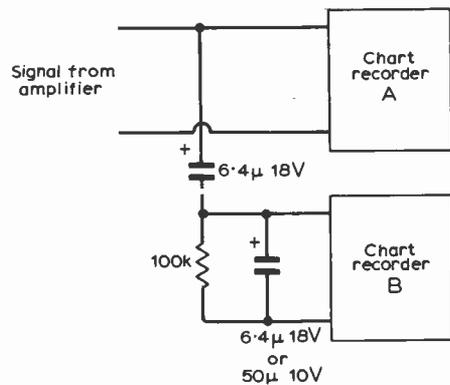


Fig. 3. Chart recorder A is set for 50mV f.s.d. and is the potentiometric titration recorder. Chart recorder B is set for 5mV f.s.d. and is the differential potentiometric titration recorder.

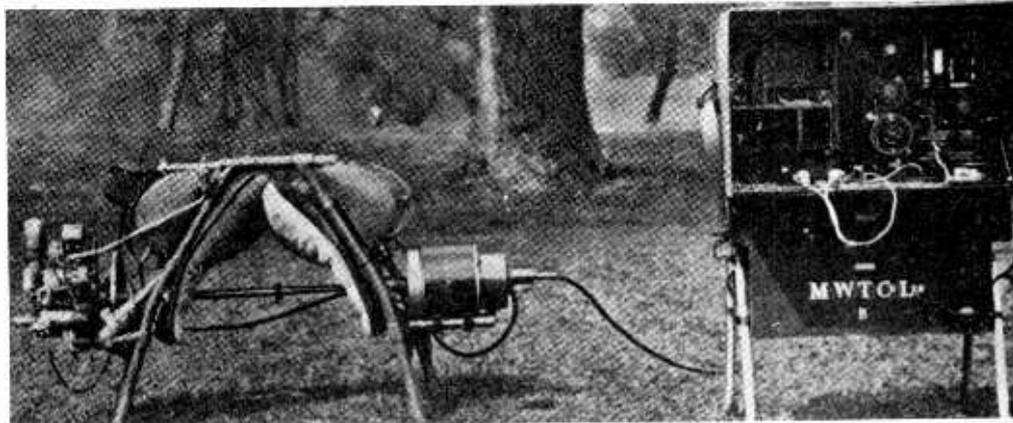

# World of Amateur Radio

## Morse outmoded?

Since the earliest days of amateur radio, the imminent demise of c.w. operation has been regularly forecast—yet dits and dahs still retain the interest of many amateur operators and account for a significant proportion of all activity. But c.w. has its critics. The notes in this column in May on the possible effects of the proposed F.C.C. changes to U.S. phone allocations brought a strongly contrary opinion from Dr John Irwin, (K6SE/5), of Louisiana State University. He feels that my notes showed a "negative attitude" towards "the switch from c.w. to s.s.b." This, he suggests, is happening all over the world and should be encouraged. "Phone is so much more efficient and interesting and satisfying than code that I have not used c.w. at all for the past two years", he writes. In that time he has worked over 900 different Japanese amateurs on s.s.b., many of them using less than 20 watts. "These Japanese are forced to use and speak English and I think this is a great thing for international fellowship and understanding, and they deserve to be commended for overcoming the severe language barrier. I only wish more Russians used s.s.b. . . . It is a complete misconception to believe that non-U.S.A. amateurs cannot work, do not want to work and do not work in the U.S. phone bands. . . . Widening U.S. phone bands will thin out the interference, benefiting all amateurs, the world over. . . . Single-sideband equipment is now so satisfactory, so potent and so cheap that the present trend from code to voice cannot help but continue; and I'm all for it", he stresses.

Those of us who continue to believe there should be a future for c.w. will disagree with several of Dr Irwin's arguments, but must respect his right to express them—the more so since it now seems pretty certain that there *will* be an extension of the U.S. phone allocations. But two amateurs chatting on s.s.b. occupy as much frequency space as perhaps 30 or 40 would need for c.w. Where frequencies are under extreme pressure (e.g. 7 and 14 MHz), surely narrow-band c.w. should be given reasonable priority? On other bands, the decision to opt for c.w. or phone is rightly one for individual amateurs to make.

It is worth noting that c.w. users retain an above average interest in the hobby. A breakdown of 100 British stations worked from G3VA on c.w. (3.5, 7 and 14 MHz) in recent months showed that about 25% had been licensed during the past 5 years; about 13% from 5 to 10 years; 16% from 10 to 20 years; 18% from 20 to 25 years; and 28% over 30 years!

Beyond question s.s.b. is effective—but, because of the peaky nature and wide bandwidth of voice waveforms, c.w. of equivalent power is still a far more effective means of communication, provided that appropriate narrow-band filters are used in the receiver. Essential information can be passed as quickly, and more accurately. So most of us want to see both modes continuing in general use.

## Amateur finds radio "bug"

The recent disclosure, as the result of an Old Bailey trial, that W. H. Borland (G3EFS) of Bromley, Kent, had been responsible for first discovering and then tracking down illegal "bugging" equipment installed about half-a-mile from his home, highlights the continued interest in amateur direction-finding. For almost 20 years, each summer, a series of D/F hunts is organized, culminating in the annual R.S.G.B. National Final. The contests usually take the form of hunting down, over distances up to ten miles, in the course of a single afternoon, two concealed 1.8 MHz transmitters.

## Space communications and amateurs

Amateurs who have been following the progress of the I.T.U. World Administrative Radio Conference on Space Matters in Geneva are concerned at the long-term implications of the extremely strong pressure for microwave frequencies for all forms of space communications. No longer are there any "unwanted" frequencies in this part of the radio spectrum. Amateurs have been disappointed at the apparent lack of liaison between the national amateur radio societies of a number of European countries and their official delegations, who often appear to be virtually unaware

of the amateur service. While it is still expected that some extensions will be granted to amateur space facilities (at present confined to 144 MHz), a number of proposals, supported by the official U.K. delegation, are unlikely to be approved. The position taken up by the delegations from such countries as France, Norway, Sweden and the U.S.S.R. is contrasted with that of the U.K. where Minpostel invited the R.S.G.B. to nominate a member of its Council (Roy Stevens, G2BVN) to attend the meetings as an official adviser to the U.K. delegation.

## V.H.F. activities

Several notable tropospheric and sporadic E "openings" were noted during June. TF3VHF, the 70 MHz beacon station in Iceland, was heard in the U.K. on several days. In just over two hours on June 13th, 9H1BL (Malta) worked 13 British stations cross-band 70/28 MHz (70 MHz is not available in Malta). In a long series of observations on the London 70 cm beacon GB3GEC, two Dutch amateurs, PA0VZL and PA0GDV, have been hearing the station consistently, almost regardless of band conditions. A recent 144 MHz portable contest was won by G. W. Tibbetts, GW3NUE/P, who made 331 contacts. Peter Blair, G3LTF, has resumed 1296 MHz "moonbounce" contacts with W2NFA.

## In brief

The R.S.G.B. National Mobile Rally is at Woburn Abbey on Sunday, August 8th with talk-in stations GB2VHF, G3VHF and GB3RS on 14, 70 and 144 MHz. Events will include a trade exhibition, demonstrations of amateur TV, bring-and-buy sale, etc. . . . A special station, GB3ESP, will be operated by members of the International League of Esperantist Radio Amateurs during the 56th Universal Esperanto Congress in London from July 31st to August 7th. . . . F.C.C. regional offices in America have been asking a number of "Technician" licensees to submit to re-examination; about half turn in their licences without trying. . . . F.C.C. have issued a Notice of Inquiry seeking to determine what improvement (*including TV receiver design*) could be made to achieve interference-free TV reception; the American Consumers Union intends to report more fully on the susceptibility of TV and hi-fi gear to interference from h.f. transmitters. . . . An American amateur, W0WYX, has his home station located at a height of 11,500 ft on Squaw Mountain, Colorado. . . . Increased subscriptions and the aftermath of the postal strike appear to have hit severely recruitment of new R.S.G.B. members; in the three months March to May only 165 new members were elected compared with 545 in the same period in 1970.

PAT HAWKER, G3VA

# Personalities

**T. A. Duerden**, B.Sc., Ph.D., who joined Plessey as manufacturing facilities planning executive just over a year ago, has been appointed general manager (Pentex). Dr. Duerden, who will be primarily responsible for the Pentex electronic telephone exchange business, will be based at the Group's Beeston, Nottingham, factory. A graduate of Manchester University, where he read physics and later received his doctorate, he was head of management services at the Preston Division of British Aircraft Corporation prior to joining Plessey.

**G. C. F. Whitaker**, F.I.E.E., F.I.E.R.E., who was for two years on the staff of Yorkshire Television as senior planning engineer followed by a further two years as engineering consultant, has retired. Mr. Whitaker, who is 66, was educated at the Royal Naval Colleges Osborne and Dartmouth. He retired from the Navy in 1928. Re-joining the Navy at the outbreak of war, he was, initially engaged on global, long-range h.f. direction finding, followed by a period in the Radio Physics Laboratory of the University of Sydney, where he studied radio location. At the close of hostilities he was re-instated on the Active List and after appointments in the Department of Naval Ordnance and, on two occasions as deputy superintendent of the Admiralty Signals and Radar Establishment, he was promoted to the rank of Captain. His final Naval appointment was on loan to the Australian Commonwealth Government as director of electrical engineering in the Department of The Navy, Melbourne, Victoria. Retiring in 1959, he was employed by Central Rediffusion Services Ltd. and from 1960 to 1967 was chief engineer of Rediffusion television operating the London weekday contract of the I.T.A.

**Derek Stanners** is appointed U.K. sales manager of Racal Instruments Ltd. of Windsor. Previously on the board of the B & K Group, with overall marketing control of their instrumentation products

company. Mr. Stanners has also worked for the Plessey Group, at Northampton. He is an enthusiastic radio amateur. His call sign is G3HEJ.

**John R. Brinkley**, F.I.E.R.E., A.M.I.E.E., international manager of mobile radio for the I. T. & T. Corporation since 1969, has joined Redifon Ltd as an executive director of the company. The Communications and Marine Division of Redifon is to be formed into a subsidiary company and it is intended that Mr. Brinkley should



**John R. Brinkley**

be its managing director. Mr. Brinkley received his early training with the Post Office. He transferred to the Home Office Communications Directorate in 1942 and six years later joined Pye. He was managing director of Pye Telecommunications Ltd from 1956 until 1966 when he joined Standard Telephones and Cables where he was executive director until his transfer to I.T.T., the parent company.

**Air Chief Marshal Sir Donald Evans**, K.B.E., C.B., D.F.C., R.A.F. (Ret'd), has joined Ferranti Ltd in Edinburgh, as a consultant on military aviation matters but will be based at Ferranti's London Office, Millbank Tower, S.W.1. Air Chief Marshal Evans, who is 59, commanded a night fighter trials unit during the war and later the Royal Radar Establishment's Flying Unit. His Air Force service included his appointment as Air Officer Commanding-in-Chief, Technical Training Command (1964-66); as Air Secretary

(1966-67); and as Commandant of the Imperial Defence College (1968-69).

**C. J. Kent** has joined A.P.T. Electronic Industries Ltd. of Byfleet, Surrey, as sales manager. Mr. Kent joins the company from Advance Electronics Ltd where he was employed for four years as senior sales engineer. He served his apprenticeship with A.E.I. at Trafford Park, Manchester.

**J. E. Everitt**, M.A., M.I.E.E., joins the board of Rank Bush Murphy Ltd in the newly created post of director of overseas operations. Mr. Everitt, who is 35 and took his degree in mechanical sciences at Cambridge, joins Rank Bush Murphy from Ultra Electronic Holdings Ltd. of which he was marketing director.

**G. Boris Townsend**, B.Sc., Ph.D., F.I.E.E., F.Inst.P., for the past six years head of engineering research at Thames Television, has joined the I.T.A. as deputy head of the Engineering Information Service. Dr. Townsend, a graduate of King's College, London, began his career at the General Electric Company where he worked on the development of colour television receivers. He is co-author with P. S. Carnt of the two volumes on colour television published by Butterworth and received his doctorate from London University for a thesis on colour television. In 1963 he joined Rank Cintel as technical manager of the Professional Television Equipment Division. Dr. Townsend was president of the British Amateur Television Club from 1960 to 1965.

**A. R. Wilkinson**, M.A., M.I.E.E., has been appointed technical director of Radiatron Ltd and Radiatron Components Ltd. of Twickenham, Middx. He will be chiefly engaged on development work and market research. Mr. Wilkinson was formerly principal test equipment engineer with G.E.C. at Aycliffe, Co. Durham.

Ates Electronics Ltd have announced the appointment of **Howard Prescott**, who will have responsibilities for product marketing and technical liaison on the company's application circuits. Mr. Prescott, started his career with Ultra Electronics Ltd as a student apprentice, and moved to R & D before joining Air-Tech Ltd as projects engineer. Immediately prior to joining Ates, he was applications engineer with S.G.S. Ltd. where he specialized in linear i.c.s.

**C. Rhodes Oliver**, B.Sc., M.I.E.R.E., has joined Semiconductor Production Equipment Co. Ltd. of West Byfleet, Surrey, as technical director. He will be responsible for all technical aspects

and development of the Centronic product range which includes diffusion furnaces, laminar flow cabinets, profilers, semiconductor ovens and lighting intensity controllers. After the Second World War, which was spent in the New Zealand Air Force working on radar and navigational aids, Mr. Oliver was with Pye Radio and Newmarket Transistors for several years before joining Standard Telephones & Cables in 1958. This was followed by a period with A.E.I., Brimsdown, as development manager and with R.C.A. at Catania, Sicily.

## BIRTHDAY HONOURS

Few men in the world of electronics were included in the Queen's Birthday Honours List. Among those receiving honours are:

### Knights Bachelor

**John Allen Clark**, Companion I.E.E., chairman & chief executive, Plessey.

**John Henry Davis**, chairman & chief executive, Rank Organisation.

### C.B.E.

**H. Barker**, director, network planning, Post Office Telecommunications.

**Rear Admiral B. J. Castles**, F.I.E.R.E., R. Australian Navy.

**H. W. French**, chief inspector, Dept. of Education & Science.

**L. S. Yoxall**, chairman, Foxboro-Yoxall Co.

### O.B.E.

**R. E. Burnett**, M.A., F.I.E.E., managing director, Marconi Instruments.

**R. W. P. Cockburn**, controller (admin.) external broadcasting, B.B.C.

**W. Nethercot**, chairman, Min. Posts & Telecoms advisory technical sub-committee on wireless interference from industrial apparatus.

**L. A. Samson**, sales & service director, Guided Weapons Div., Brit. Aircrafts Corp.

**Wing Commander W. E. Satterthwaite**, M.I.E.R.E., R.A.F.

### M.B.E.

**H. Ledger**, senior engineer, Plessey Telecommunications Ltd. Beeston.

**M. R. Neville** for services to the Electrical & Electronics Industries Benevolent Assoc.

**H. J. Plater**, asst. manager, studio operations, B.B.C. Television.

## OBITUARY

**Lord Reith**, under whose guidance broadcasting was started in this country in 1922 by the British Broadcasting Company, of which he was general manager, died in Edinburgh on June 16th. He was 81. John Charles Walsham Reith, a mechanical engineer by profession, became the first director-general of the B.B.C. when in 1927 it became a public corporation. Although he resigned from the B.B.C. in 1938 he has left his mark indelibly on British broadcasting.

# EEV know how many nano-



**1971**

	January	February	March	April
Sunday	31 3 10 17 24	7 14 21 28	7 14 21 28	
Monday	6 11 18 25	1 8 15 22	1 8 15 22 29	4 11 18
Tuesday	8 12 19 26	2 9 16 23	2 9 16 23 30	5 12 19
Wednesday	9 13 20 27	3 10 17 24	3 10 17 24 31	6 13 20
Thursday	1 8 15 22 29	4 11 18 25	4 11 18 25	7 14 21
Friday	2 9 16 23 30	5 12 19 26	5 12 19 26	8 15 22 29
Saturday	10 15 22 29	6 13 20 27	6 13 20 27	9 16 23 30
				10 17 24
	May	June	July	August
Sunday	30 2 9 16 23	6 13 20 27	4 11 18 25	1 8 15 22 29
Monday	31 3 10 17 24	7 14 21 28	5 12 19 26	2 9 16 23 30
Tuesday	4 11 18 25	1 8 15 22 29	6 13 20 27	3 10 17 24 31
Wednesday	5 12 19 26	2 9 16 23 30	7 14 21 28	4 11 18 25
Thursday	6 13 20 27	3 10 17 24	8 15 22 29	5 12 19 26
Friday	7 14 21 28	4 11 18 25	9 16 23 30	6 13 20 27
Saturday	8 15 22 29	5 12 19 26	10 17 24 31	7 14 21 28
	September	October	November	December
Sunday	5 12 19 26	31 3 10 17 24	7 14 21 28	5 12 19 26
Monday	6 13 20 27	4 11 18 25	1 8 15 22 29	6 13 20 27
Tuesday	7 14 21 28	5 12 19 26	2 9 16 23 30	7 14 21 28
Wednesday	1 8 15 22 29	6 13 20 27	3 10 17 24	1 8 15 22 29
Thursday	2 9 16 23 30	7 14 21 28	4 11 18 25	2 9 16 23 30
Friday	3 10 17 24	1 8 15 22 29	5 12 19 26	3 10 17 24 31
Saturday	4 11 18 25	2 9 16 23 30	6 13 20 27	4 11 18 25

# seconds make 10,000 hours.

In nuclear physics you need absolute accuracy and long-term reliability from your electronic tubes. Especially thyratrons. EEV thyratrons can be fired with nano-second precision, with repetition rates of up to 50 kHz due to very rapid deionisation characteristics. Long life - 10,000 hours can be achieved - enables EEV ceramic thyratrons to be bolted into the circuit as with passive components.

EEV thyratrons meet the demands of major nuclear physics applications :

In linear accelerators they can withstand peak inverse voltages up to 20 kV following a pulse, and they give trouble-free operation in oil-filled equipment.

In particle accelerator work missed pulses are rare. Annular current-flow means rapid peak-current switching, too, without risk of arc extinction.


In spark chambers EEV thyratrons will eliminate spurious firing, and jitter can be kept as low as 1 ns. The CX1154 for example operates over a wide range of H.T. voltages at currents up to 10 kA without significant change in characteristics, so drive units can be used with different chambers - and the low trigger voltage means that simple firing circuits are possible.

So, whether you're concerned about nano-seconds or thousands of hours, specify EEV thyratrons. And remember that EEV also make ignitrons, photo tubes, storage tubes, image intensifiers, vacuum capacitors, spark gaps, RF tubes (like tetrodes for driving RF separators) and magnetrons especially for linear accelerators. Send for details. ❀

## EEV know how.


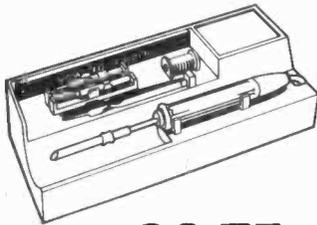
# cut out the coupon and answer your soldering problems



**£2-75**

### SK1 SOLDERING KIT

In rigid plastic "tool box" containing Model CN - 15 watts - 240 volts miniature iron fitted  $\frac{3}{16}$ " bit. Spare bits  $\frac{5}{32}$ " and  $\frac{3}{32}$ ". Reel of resin-cored solder, heat sink, cleaning pad, stand and booklet "How to Solder".



### SK2 Soldering Kit

In polystyrene pack, containing 15 watt miniature soldering iron, 240 volts fitted with  $\frac{3}{16}$ " bit, 2 spare bits  $\frac{5}{32}$ " and  $\frac{3}{32}$ ". Coil of resin-cored solder, heat sink, 1A fuse and booklet "How to Solder".

**£2-40**



Model CN 240/2  
15 watts - 240 volts

**£1-70**

Fitted with nickel plated  $\frac{3}{32}$ " bit and packed in handy transparent box.



ES240 D 25 watt  
soldering iron

In transparent display pack, fitted with long life iron-coated bit  $\frac{1}{8}$ " diam.

**£1-83**

Interchangeable spare bits  $\frac{3}{32}$ ",  $\frac{3}{16}$ ",  $\frac{1}{4}$ " (extra) available. Improved design to ensure strong and reliable high speed iron. Heats up in 2 minutes.

### GSS Desoldering Tool

Model GSS with  $\frac{3}{32}$ " tip diameter

**£4-67**

De-soldering tool working on compressed air for industrial use with an air line or occasional use with foot pump. Efficient, self-cleaning operation on Venturi principle. Split-second action. Press valve control.




### ESS Desoldering Tool

Model ESS with  $\frac{5}{32}$ " tip diameter

**£4-67**

Model ESS or GSS complete with foot pump

**£5-65**

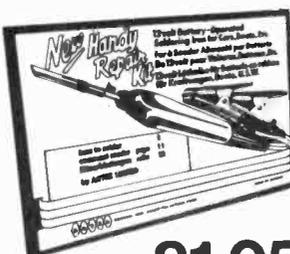

**£1-95**

### M.E.S. Battery-operated 12 volt soldering iron

Complete with 15 ft (4.50m) lead, 2 heavy gauge clips for instant connection to car battery and a guide 'How to Solder'. Packed in strong plastic wallet.



- Please send the ANTEX colour catalogue.
- Please send the following:

\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

from electrical and radio shops or by Free Post (No stamp required) from ANTEX Ltd., FREE POST, PLYMOUTH, PL1 1BR. Tel (0752) 67377/8.

I enclose cheque/P.O./Cash (Giro No. 2581000)

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_

WW8

# New Products

## Rugged disc store

A disc store for computer application which is extremely rugged has been developed by a 16-month old company Process Peripherals Ltd, with N.R.D.C. backing. As the disc rotational speed reaches the crystal-controlled 3000 rev/min, specially profiled heads are lowered very close to the disc. A special head suspension keeps the heads at a constant 'flying' height and attitude even under severe vibration. The ferro-magnetic disc has a capacity of 256,000 words of 16 bits each—4.2M bits—which can be arranged in various ways including four separate stores of 1M bits each. Mean access time is 10ms, which can be halved by simple rearrangement of the heads. An error rate of 1 in  $10^{10}$  has been achieved with this store and operational life is quoted as 100,000h. Process Peripherals Ltd, The Broadway, Thatcham, Berks.

**WW 305 for further details**

## Automatic record cleaner


An automatic record cleaner, with the brand name Bib Groov-Kleen model 40, resembles a miniature cartridge arm, being finished mainly in anodized aluminium. The base is supplied with a self-adhesive disc to fix it to the player deck. The base has a chromium-plated pivot pillar which can be raised or lowered so that the arm can be adjusted to be parallel with the turntable. The arm, which is cranked to provide better tracking, has a brush at one end and a counterweight at the other. A small roller mounted behind the brush automatically sets its own level. A swivelling arm-rest is provided to hold the arm when a record is being placed on the turntable. The device has been designed so

that it is suitable for mounting on any make of turntable deck, including the Garrard SP.25 Mk.III where very little space is available when the plastic cover is *in situ* on the plinth. When a record is being played, dust which is loosened by the brush is collected on the roller (which does not revolve) and can be removed with a separate brush included in the outfit. From time to time a fresh face of the roller can be presented to the record. A replacement kit of roller and brush is available. Price is £2.59. Bib Division, Multicore Solders Ltd, Hemel Hempstead, Herts.

**WW315 for further details**
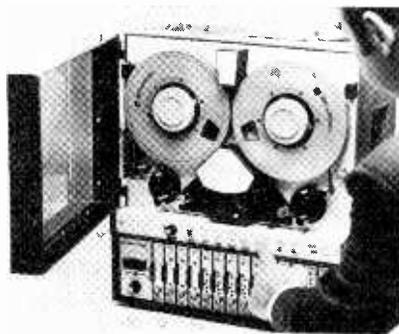
## Portable instrumentation recorder

The CPR-4000 portable instrumentation tape recorder from Bell & Howell records up to seven channels on  $\frac{1}{2}$ in tape, will accept N.A.B. reels up to 230mm in



diameter, and has seven electrically switchable speeds from  $\frac{15}{16}$  to 60 i.p.s. Tape speed accuracy when used with the servo loop closed is  $\pm 0.05\%$ . Frequency range is 300kHz direct at 60 i.p.s. The f.m. system offers both I.R.I.G. wideband

group I of 40kHz and an intermediate band of 20kHz at 60 i.p.s. The record and reproduce heads, made of a wear-resistant material, have an edge voice channel for use with the optional voice logging accessory. An optional automatic tape-threading device is also available. Power requirements are 115/230 V a.c. ( $\pm 10\%$ ), 48 to 420 Hz single phase. Maximum consumption is approximately 200VA. Bell & Howell Ltd, Electronics & Instruments Group, Lennox Road, Basingstoke, Hants.

**WW322 for further details**

## 50MHz counter

Model FC50 from Wayne Kerr is a six-digit readout instrument with automatic location of the decimal point. The effective resolution can be increased, in some instances up to eleven digits, by under-ranging. The ranges are 0.1Hz to 50MHz and  $1 \mu s$  to  $10^5$  seconds, with a count facility to 999,999. Start and stop can be manual or electrical (or a mixture of the two) and facilities are provided for inhibit, gating, storage and varying the up-dating rate. Clock signals are available for external use and there is an option of



b.c.d. outputs from the six number tubes. The display can be switched to show a 'non-blink' series of completed counts of the run as it proceeds. Acceptable input levels range from 20mV (r.m.s.) to 100V, and provision is made for correctly terminating 50  $\Omega$  or 75 lines. The Wayne Kerr Co. Ltd, Roebuck Rd, Chessington, Surrey.

**WW328 for further details**


## Battery-operated soldering iron

The Antex MES 12 soldering iron operates from a 12 volt d.c. supply. Two large crocodile clips on 4.50m of 2-core cable provide connection to the battery terminals. The recommended U.K. price is £1.95. Anglo-Netherlands Technical Exchange Ltd, Mayflower House, Plymouth, Devon.

**WW 308 for further details**
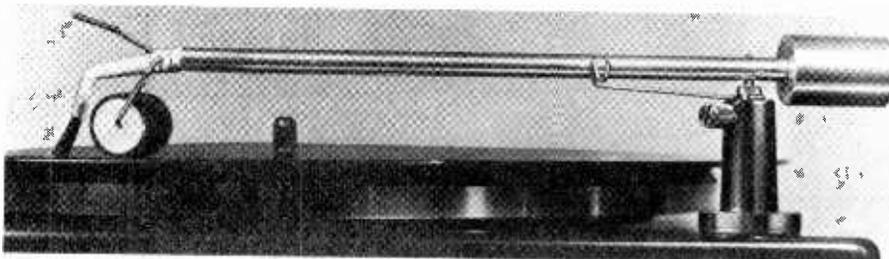
## Gunn oscillator

A Gunn oscillator made by Mullard gives an output of 35mW at 10.525GHz  $\pm 20$ MHz. Type CL8631, it operates at a



fixed frequency over the temperature range  $-20$  to  $+50^{\circ}\text{C}$  and can be used satisfactorily with any phase or load mismatch up to a v.s.w.r. of 1.3. It requires a power supply of 8V, total consumption being less than 2W. A square flange output mates directly with waveguide size RG-52 (WR90/WG16). The device can replace a klystron oscillator in many applications. Mullard Ltd, Mullard House, Torrington Place, London W.C.1.

**WW323 for further details**

### Shift registers

The MA86S/87S silicon gate 100/128-bit dual independent shift registers, from GEC Semiconductors, operate from a single t.t.l. level clock and the t.t.l. system noise immunity specification is preserved. The registers can be clocked from zero frequency to more than 3MHz. All inputs and outputs (including the clock input) are t.t.l. compatible and the device operates from standard voltage levels. Since the registers are completely independent they may be clocked separately. The device is available in a TO-5 style package. GEC Semiconductors Ltd, Freebourne Rd, Witham, Essex.

**WW 304 for further details**

### Intensifier vidicon

A vidicon camera tube with more than 250 times the sensitivity of a conventional 26 mm vidicon is being produced by the Electron Tube Division of EMI-Electronics. The tube, which employs an intensifier and is designated the Ebitron type 9777 vidicon, is claimed to produce television pictures when illumination is equivalent to half moonlight. The vidicon employs electron-bombardment induced conductivity in the zinc sulphide target with a high sensitivity photocathode. The image section is all electrostatic and the scanning portion similar to a conventional 13mm magnetic vidicon. The Ebitron can replace existing 26mm vidicons in c.c.t.v. cameras, the 9777 tube and its coils being no bigger. The 18.2mm photocathode makes it suitable for use with standard 26mm vidicon lenses. The weight is 230g potted,

100g unpotted.

Typical operating conditions:

<b>image section</b>	
overall e.h.t.	14,000 V
<b>scanning section</b>	
cathode	0 V
$g_1$ modulator	$-30$ V
$g_2$ limiter	300 V
$g_3$ beam focus	290 to 330 V
$g_4$ vidicon mesh	500 V
axial magnetic focus field	550 V
output signal	0.15 $\mu\text{A}$ peak white
overall sensitivity	50 mA/1m

The heater requires 90mA at 6.3V. EMI Electronics Ltd, Hayes, Middlesex.

**WW 310 for further details**

### Thermally controlled soldering iron

A range of lightweight, thermally controlled, soldering instruments has been introduced by Adcola. Known as the Invader, the new models incorporate a proven element combined with a new 'pencil-slim' handle. The rectangular centre heat-shield allows the instruments to be placed on any surface without rolling, and the tool is balanced to keep the working bit clear of the surface. A hanging hook is moulded into the handle. Noryl plastic, used for the handle, does




not readily transmit heat—the company claim the 25W and 27W tools are the slimmest available in these powers. The plug-in element can be replaced in 90 seconds. The collet can also accommodate

the complete range of 70 standard and special-purpose bits. Standard Invader models are available for seven voltages—6, 12, 24, 50/55, 110, 220 and 230/250V. Three collet sizes— $\frac{1}{16}$ in,  $\frac{1}{8}$ in and  $\frac{1}{4}$ in—are available, and the recommended price for the largest tool is £1.95. Elements with bit temperatures between 250 and  $410^{\circ}\text{C}$  can be supplied at no extra charge. The temperature of the standard-bit face is  $360^{\circ}\text{C}$  controlled to  $\pm 10^{\circ}\text{C}$ . Adcola Products Ltd, Adcola House, Gauden Rd, London S.W.4.

**WW 307 for further details**
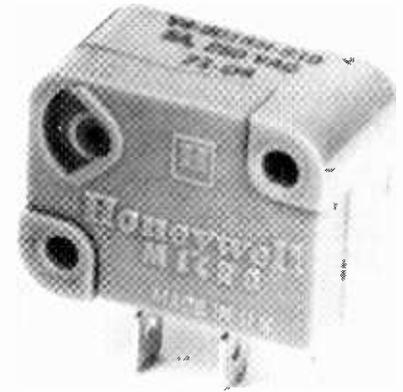
### Rotary-action switches

A range of low-torque, rotary-action, miniature switches, with a mechanical life in excess of ten million operations, has been introduced by Honeywell. The 900 Series 'V4' switches can operate in clockwise or anti-clockwise direction with no change in operating characteristics, and alternative shaft positions are possible.




Both s.p.c.o. and s.p.d.t. versions are available with 0.187in quick-connect or solder termination. They are rated at 5A and 125 or 250V a.c. Inrush current values should not exceed 10A. Operating temperature range extends from  $-40$  to  $+100^{\circ}\text{C}$ . Honeywell Ltd, Charles Square, Bracknell, Berkshire.


**WW327 for further details**
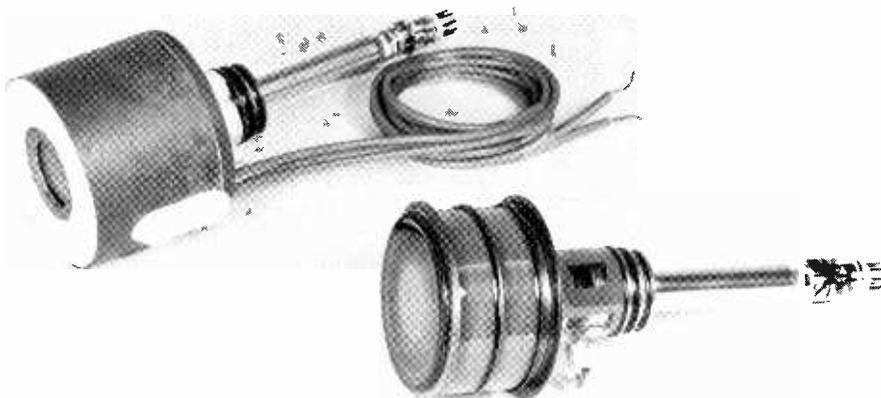
### Inexpensive XY plotter

The XY plotter type PL100 from J. J. Lloyd Instruments, is suitable for applications where extreme accuracy and high speed are not essential. It is sold as a basic potentiometric assembly with a sensitivity which may be adjusted from 150 to 300mm/V. The response speed is approximately 200 mm/s and adjustable damping is provided for the servos on both X and Y axes. The amplifiers for both axes are independent, with floating inputs, and a suppressed-zero facility is incorporated which enables the instrument to plot small changes in voltage or current about a given reference level. Calibrated plug-in amplifiers are available to extend the range and enable the instrument to



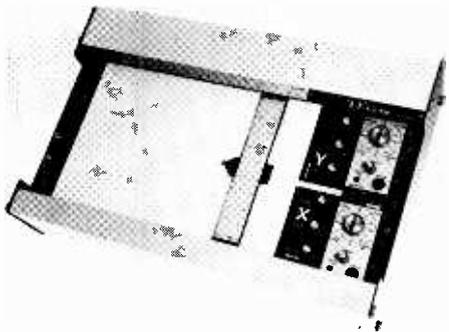plot either voltage or current. Each amplifier has a calibrated reference, stepped attenuator and vernier sensitivity control, allowing the gain to be adjusted between 0.5mV/cm and 40V/cm or 0.5µ A/cm and 40 mA/cm. The accuracy




and repeatability is  $\pm 1\% \pm 1$  mm and the maximum paper size is 254 × 330mm. Price of plotter only is £124. The plug in amplifier costs £30. J. J. Lloyd Instruments Ltd, Brook Avenue, Warsash, Southampton SO3 6HP.

**WW314 for further details**
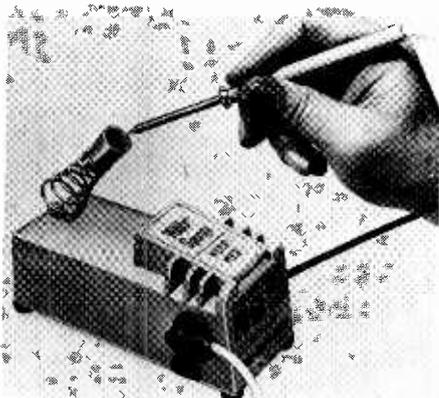
### Soldering pencil

A soldering pencil, the MCP from Weller Electric, can be fitted with any of seven iron-plated tips ranging from 0.01in 'micropoint' to 0.125in double flat. Overall




reach is 2½in. The element operates at 24V supplied from its own power pack operating from the 240V mains. The power unit carries a spring pencil holder, and a cleaning sponge. Price £14.95; tips 45p each. Weller Electric Ltd, Redkirk Way, Horsham, Sussex.

**WW326 for further details**
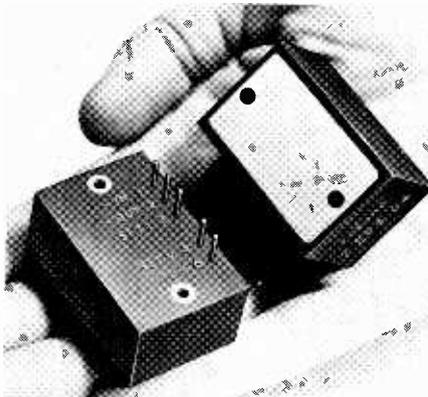
### Encapsulated regulators

The Roband Limpet range of encapsulated series regulators for stabilized power supply systems achieves high dissipation by providing an isolated metal heat transfer surface in one face of each module. The modules, which operate from a single unstabilized d.c. rail or from a battery, give well stabilized outputs up to 55V or 20A and have full over-current protection. The output voltage and protection levels

are each preset externally by a fixed resistor, or they can be remotely programmed. The modules fit a standard heat sink extrusion, but can be mounted on any conventional metal surface. A typical 2A unit which measures 47 × 30 × 22mm can give a stabilized rail set anywhere between 6V and 24V with a maximum internal dissipation of 25W. The cost of



such a unit is £15.50. Roband Electronics Ltd, Charlwood Works, Charlwood, Horley, Surrey.

**WW 306 for further details**


### Coaxial connectors

Sealectro have introduced a new range of r.f. coaxial front panel connectors. The 'Kwick Connect' range provides locking and exhibits a v.s.w.r. of better than 1.30:1 at frequencies up to 18GHz. Assembly to cables is by crimp or clamp of the outer conductor, and by crimp or solder to the inner conductor. Once mated, it is virtually impossible to break the connection by pulling on the connecting cable. To disconnect a knurled ring is pulled back and the connectors disengage. Sealectro Ltd, Walton Road, Farlington, Portsmouth, Hants.

**WW 309 for further details**
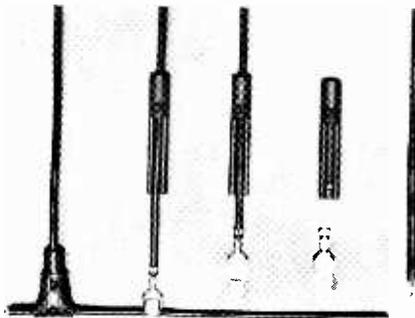
### T line connectors

Pressac have developed a new system of T line connectors. They are designed to allow electrical accessories to be connected into main wiring harnesses without cutting



the conductors. They can be applied directly to insulated wire without stripping. Each connector has an insulating sleeve which is threaded over the accessory lead

and a brass contact is crimped to the conductor. The brass connector cuts through the insulation to make an electrical connection. The insulation sleeve is then wrapped around the contact and fixed by an integral latch. The connectors can be supplied either on reels, for machine assembly or loose. Pressac Ltd, Leopold Street, Long Eaton, Nottingham.

**WW 311 for further details**


### Power transistors

A range of homotaxial silicon power transistors from Ates, suitable for high-power amplifier circuits, employs a structure in which the base region exhibits homogeneous resistivity in the axial direction—i.e. emitter-to-collector—eliminating secondary voltage breakdown within the maximum ratings of the device. The 2N3771 of this TO-3 range provides 150W output, with 30A ( $I_C$ ) at 50V ( $V_{CBO}$ ). For 100V operation, the 2N3772 gives 20A, and the 2N3773 16A at 160V. Ates Electronics Ltd, Mercury House, Park Royal, London W.5.

**WW 303 for further details**
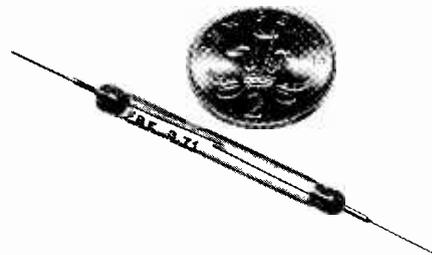
### Reed switch

Reed switch type DRA-291 from F.R. Electronics is capable of switching up to 5A at 50VA and up to 1A at 100VA. It is



standard size, and has rhodium contacts with low contact resistance. F. R. Electronics Ltd, Wimborne, Dorset, BH21 2BJ.

**WW 312 for further details**

### Logic level pulse generator

From Grange Electronics (Production) we have received details of a wide-range pulse generator which covers repetition frequencies from 1 Hz to 5 MHz in seven overlapping ranges. Delay and output pulse widths are variable between 100ns and 100ms in six overlapping ranges. Additional features include manual and external triggering, a pre-pulse output and simultaneous complementary outputs at t.t.l. levels. The price is £66. Grange Electronics (Production) Ltd, Stone Lane, Wimborne, Dorset, BH21 1HD.

**WW318 for further details**

## Oven for TO-5 devices

Jermyn's 4ST2 self-regulating oven is designed for devices in TO-5 size packages when lead lengths are restricted to 12.5mm. Devices having up to eight leads may be accommodated and can be installed without the use of special tools. Ovens having control temperatures of 65, 80 and 115°C are available and will operate in ambient temperatures from -50 up to 50, 60 and 100°C respectively.



The ovens have no moving parts or electronic circuitry but incorporate a semiconductor heater to provide a self-regulating proportional temperature control. Power requirements are 24V ( $\pm 4V$ ) a.c./d.c. 0.6W (at 25°C ambient). Maximum warm-up time from -55°C is 3 minutes. Jermyn Industries, Manufacturing Division, Vestry Estate, Sevenoaks, Kent.

**WW319 for further details**

## Transient voltmeter

Model 3206 voltmeter from Sintrom Electronics will measure and hold the peak value of a single pulse which has a 10ms duration or longer. The instrument has a



four-figure digital readout and an accuracy of 1% of full scale. There are four switched ranges with full-scale values ranging from 10mV to 19V. The input impedance is 1 M $\Omega$ . The peak value is held in store until reset. Automatic reset for driving a printer or recorder is provided. The input is floating and is double screened to reject radiated transients. Other models in this range include instruments capable of measuring

pulses up to 30kV and as short as 50 nanoseconds. Analogue and digital read-outs are available. Prices range from £580. Sintrom Electronics Ltd, 2 Castle Hill Terrace, Maidenhead, Berks.  
**WW 302 for further details**


## Sub-miniature chokes

Cambion's 550-339 sub-miniature radio frequency choke is available in a wide range of inductance values—0.1 through to 1,000  $\mu$  H in 49 steps. Each choke has a small moulded body 6 mm long and 24 mm in diameter. Cambion Electronic Products Ltd, Castleton, near Sheffield, S30 3WR.

**WW313 for further details**
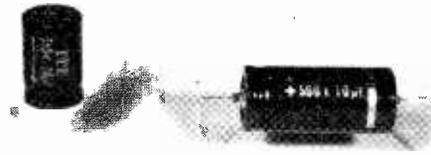
## Axial-lead electrolytic capacitors

A series of axial-lead miniature aluminium electrolytic capacitors, type EN12.12, has been added to the range of ITT single ended miniature capacitors type EN12.35.



The axial-lead versions are available from 1  $\mu$  F to 4,700  $\mu$  F rated up to 500V (dependent on capacitance value). These capacitors have an operating temperature range of -25 to +70°C. Plastic sleeves are employed for case insulation. ITT Components Group Europe, Standard Telephones and Cables Ltd, Edinburgh Way, Harlow, Essex.

**WW316 for further details**

## High-frequency counters

Series 7900 counters from Dana Electronics are seven-digit units with an optional eighth digit, and all have optional systems interface units. Sensitivity is 1mV up to 500 MHz. Three counters typical of the range are the 7910 (to 150MHz) at

£595 (illustrated), the 7920 (to 550 MHz) at £750, and the 7960 (to 3 GHz) at £1395. Dana Electronics Ltd, Bilton Way, Dallow Road, Luton, Beds.  
**WW324 for further details**

## Panel drilling bit

A Bradrad (Type A), from West Hyde Developments, provides panel holes of different sizes, drilling and deburring in a single operation. Two versions are available providing holes of 1½ to 2½ inches in ⅛in steps, or 36mm to 60mm in 3mm steps.



The bit is made of cobalt 'high speed' steel and has a 12.5mm diameter shank. Price £23 plus 35p postage and packing. West Hyde Developments Ltd, Ryefield Crescent, Northwood Hills, Northwood, Mddx.


**WW321 for further details**
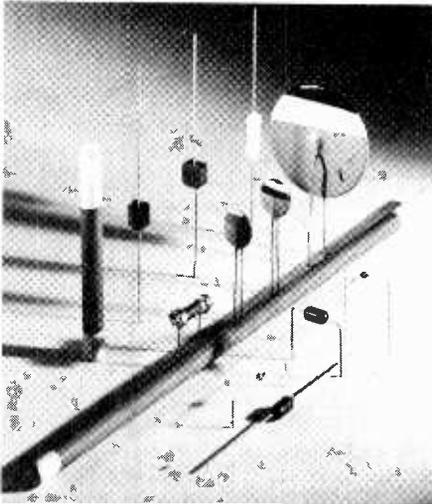
## Voltage-dependent resistors

A new range of silicon carbide and diffused junction silicon voltage-dependent resistors (varistors) is available from ITT. Silicon carbide voltage-dependent resistors are available in rod or disc form, and can be supplied with leads for direct wiring into position or without leads for direct mounting. These devices have a wide range of applications for voltage control and component protection. Silicon diffused junction varistors are particularly suitable for a very wide range of currents at low



voltage levels. A particular application of this type is for temperature compensation




in semiconductor circuits. ITT Components Group Europe, Resistor Products Sales, Edinburgh Way, Harlow, Essex.  
**WW 301 for further details**

### Variable transformers

Variable transformers from the Zenith Electric Company, in the Variac-Setavolt range, are fully encapsulated for 200-250 volt operation, covering the current ranges 0.75 to 4A in 5 sizes. The frequency range is 50-400Hz. Motorized two-gang and three-gang units are also available. The Zenith Electric Co. Ltd, Wavendon, Bletchley, Bucks.  
**WW317 for further details**
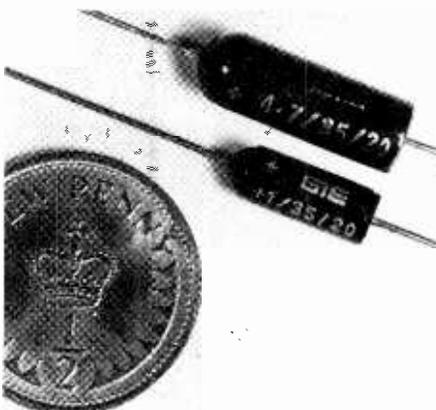
### Tantalum capacitors

The MT series of moulded tantalum capacitors, available from General Instrument (UK) Ltd, are dry sintered anode units, moulded in epoxy resin and not subject to gassing or electrolyte



leakage. Capacitance range is from 0.068 to 47 $\mu$ F rated up to 50V. The working temperature can be as high as 85°C. General Instrument Ltd, Stonefield Way, Ruislip, Middx  
**WW325 for further details**

### Improved recording tape

A new family of recording tapes which exhibit increased output and a 4dB improvement in signal-to-noise ratio with no modification to existing equipment has been developed by the 3M Company. Known as High Energy tapes, they are based on a cobalt-modified ferric oxide formulation. Unlike chromium-dioxide tape, which requires separate circuitry to be switched in, High Energy tape can be used on existing cassette machines without any modification to the standard low-noise bias and equalization levels to give greater undistorted output and an increase in dynamic range from 2dB at low frequencies to 6dB at the upper end of the scale. Circuitry designed around the potential performance characteristics of the new tapes could improve reproduction still further. It is expected that the new tapes will be marketed in the U.K. later this year in helical-scan video form, and that broadcast video and audio cassettes will follow. 3M Company, 3M House, Wigmore Street, London W1A 1ET.

plastic case. Price is 79p for 1-24 and 59p for 100 up. RCA Ltd, Solid State Division, Sunbury-on-Thames, Middx.  
**WW 320 for further details**

### Stylus balance


The BIB stylus balance model 32 is produced specifically for determining the 'pressure' of modern cartridges and is calibrated in 0.25g



divisions. It has a non-magnetic base mounted on foam plastic. The cross-bar of the beam has recesses which are mounted on a pair of low-friction pivot points. Price £1.80. BIB Division, Multicore Solders Ltd, Hemel Hempstead, Herts.  
**WW 330 for further details**
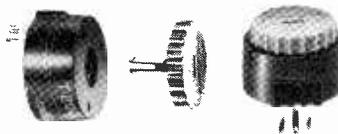
### Miniature trimmer pot


The T-200-K single-turn wirewound potentiometer in the Contelec range of trimmers has a knurled plastic-moulded knob, with bifurcated



shaft that pushes into the pot and interlocks with the keyway. It can equally easily be turned by a screwdriver. Power rating is 2W at 40°C. Resistance range is 10 $\Omega$  to 50k $\Omega$ . Size is 20 x 10mm. Operating temperature is -25 to 125°C. The T-200 series is available in eight standard versions, in either bush mounting or printed circuit types. Kynmore Engineering Co. Ltd, 19 Buckingham Street, London WC2.  
**WW 331 for further details**
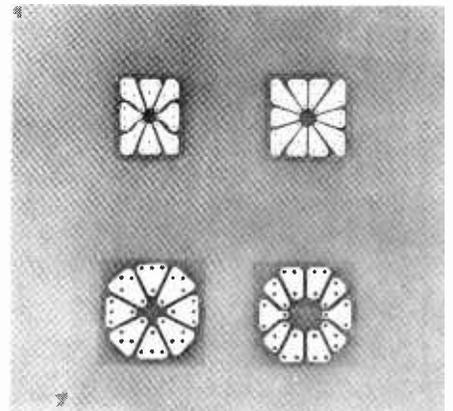
### Printed circuit elements

Conducting elements for wiring semiconductor devices to printed circuits are made by Circuit-Stik Inc. of California. With an adhesive backing, the 1000 and 2000 series of



elements are designed to suit most types of TO-5 and TO-18 packages. The former are drilled to match a 0.1 in grid and the latter undrilled to save space. Available in the U.K. from Bourns (Trimpot) Ltd, 17 High Street, Hounslow, Middx.  
**WW 329 for further details**

### Zero-voltage switch for thyristors

A low-cost version of the RCA zero-voltage switch for thyristor gate triggering is the CA3079. It has the same temperature range as the earlier CA3059 (-40 to 85°C) but the fail-safe, inhibit and over-ride functions are not included. The economy type includes a power supply, allowing operation from an a.c. line of 24 to 277V at 50 to 400Hz, a differential sensing amplifier; a zero-crossing detector and a triac gating circuit. The zero-crossing detector, of course, allows thyristor switching at the voltage zeros of the a.c. line, eliminating r.f. interference when used with resistive loads. The circuit is packaged in a 14-lead dual in-line

### Press-button switches

The Arrow Adapt-a-Switch range of illuminated and non-illuminated press-button switches is based on a small number of components that fit together simply. The actuator can be chosen for momentary or alternate action. Press-in lenses give a range of three shapes—round, square and oblong—in six colours. The standard duty ratings are 5A at 125V a.c., 2A at 250V a.c., and 5A at 28V d.c. Electrical and mechanical life is 100,000 cycles minimum at full rating. Arrow Electric Switches Ltd, Brent Road, Southall, Middlesex.  
**WW 332 for further details**

# Real & Imaginary

by "Vector"

## On Stopping the Home Fires Burning

I wonder whether you've ever thought of the domestic 'telly' as a lethal instrument? I must confess I hadn't until I read a study of statistics relating to fires in television sets. This paper was written by a member of the Joint Fire Research Organization and the figures quoted give food for thought.

For in 1968 (the last year for which figures were presumably available) 1244 fires occurred in Britain which were directly attributable to the magic box. In 1960, the figure stood at 528 and rose significantly in every subsequent year.

You may well say 'Ah yes, but the number of sets in use increases every year'. True. But other figures given show that the number of fires increased at a considerably higher rate than licences did. In 1965 the incidence of fires to licences was 61.8 per million; three years later it was up to 82.4 per million and after another three years I wouldn't be surprised to find that it had taken another comparable jump. The older the set, the greater the risk, is a logical conclusion and possibly, with the cost of living steadily rising, people are hanging on to their sets longer.

One rather less sombre side is that (taking the 1968 statistics) about 83% of these fires occurred between 3 p.m. and midnight when someone is likely to be able to initiate prompt action. Only 5% of the total—roughly 4.5 per million licences—occurred between 1 and 2 a.m. Compared with the annual incidence of fires from all causes between these hours, which amounted to some 500 per million dwellings, the number of television fires are chickfeed; but they are nonetheless dangerous, since at that time most people are asleep in bed and totally unprepared for disaster. You may remember that recent fire in a hotel, in which eleven people died. That was attributed to a television receiver. What effect has the advent of colour, with its higher operating voltages, had on the figures? No significant alteration up to 1968, but that doesn't mean much because colour hadn't got going, and even today colour sets are not in wide enough use to make much difference.

How were these fires caused? It was no part of the report's aim to specify and so we don't know. Component breakdown must have played a part but, to be fair on the manufacturers, by no means all TV receiver fires are started in this way. All

dealers know the old lady who drapes a blanket over the top of the set to let her cat sleep on, and how, by drooping over the back, this (the blanket I mean, not the cat!) can block all ventilation. Tatty do-it-yourself flex wiring (often using bare staples) with the lead to the set permanently 'live' is another well-known phenomenon. And again, smoke pouring from the cabinet may panic the householder into calling the fire brigade when in fact no fire, as such, exists. The statistics given seem to indicate the presence of this last factor, for of the 1244 fires quoted for 1968, 612 were 'confined to the set' and might therefore have been smoke only—or does a fire brigade have to see flames to record the incident as a fire? As to the remainder, a further 560 were 'confined to the room', while 72 spread to other areas. These 632 were, without doubt, genuine no-nonsense fires, but it would be instructive to know whether outbreaks originating in the mains lead to the set or in its feed wire along the skirting (where this exists) are classified as television fires, or whether the outbreak must originate in the set in order to qualify.

In the U.S.A. the incidence of fires in TV sets is causing considerable concern. In August 1969 the Federal Government's National Commission began to put the whole question under the microscope and in due course came up with the pronouncement that more than 10,000 such fires occurred annually. Predictably, this was hotly denied (no pun intended!) by the Electronic Industries' Association, which put up a rival figure of 2600 over a five-year period. Subsequently, other reports were produced from various sources with figures that fell somewhere between the two extremes.

One such (the 'Jitco') was especially enlightening. This was in essence a tabulation of data supplied by set manufacturers concerning fires reported for each of their models. It did far more than tabulate, however; it also pinpointed the components that were responsible. One startling fact that emerged was that colour sets were *forty times more likely to cause fires than black-and-white models*. Forty times. That's a fantastic jump.

In the list of delinquent components the line output transformer emerges as the worst offender by a considerable margin (29.26% of the total fire/smoke cases, rising

to 40% in colour sets). Then come high-voltage components (18.1%), the receiver on-off switch (12.7%), the yoke (7.4%), controls (5.9%) and so on through seven more groupings, ending with fuses at 0.4%. Nothing much to surprise the British service engineer here, I fancy. Understandably, fires occurred in chassis runs—that is, if a given component was fitted which subsequently proved to be unequal to its job, an epidemic of fires would be experienced with the particular model that embodied the component.

Now, to judge from a comprehensive report on the subject in *Electronics*, the United States can scarcely be set up as a pattern upon which to model future British procedure. The bible in the matter of standards seems to be the Underwriters' Laboratories UL492, which runs to 402 paragraphs and which is continuously being updated. But apparently there is no legal obligation to conform to it and it is left to individual cities to decide whether sets used within their boundaries should carry the U.L. stamp. Only three cities insisted on this at the time of the survey (August 1970) and so many manufacturers just don't bother with it. The U.L. standards, it is stated, are not so much those which ensure public safety as ones which the manufacturers can conveniently work to. One example cited is the permissible leakage between case and earth which is 5mA—sufficient to pack a nasty wallop; efforts are now being made to reduce this to 0.5mA. Again, the permitted level of X-ray radiation from TV sets has been set at 0.5 milliröntgen/hour at 5cm, but not because this gives a good margin of safety; it is merely a level that manufacturers can conveniently meet. Recently, however, some improvement has been effected; from January 1st, 1971, all sets have had to conform to this level even if all controls are maladjusted to 'worst case' and component failure increases emission.


Signs are not wanting, in fact, to indicate that American television manufacturers are at last treating the fire hazard much more seriously than formerly. This may reflect an improved sense of social conscience. On the other hand the more cynical might think that it stems from a test case in the U.S. Courts concerning a man who died in a TV-originating fire. The receiver manufacturers were ordered to pay \$212,000 dollars compensation to the man's family. If this establishes a precedent as to where responsibility lies, it could make for an expensive future for television manufacturers.

Returning now to the British scene, one benefit from our delayed entry into colour is that we have a breathing space before colour receivers become the rule rather than the exception. This gives us opportunity to benefit from American mistakes.

For the information contained in the above I am indebted to: 'Fires in television sets', S. E. Chandler, *Fire*, Sept. 1970. 'Customer hazards: why they happen', and 'Customer hazards: how they can be fixed', *Electronics*, Aug. 3, 1970.

# new

## Super IC-12

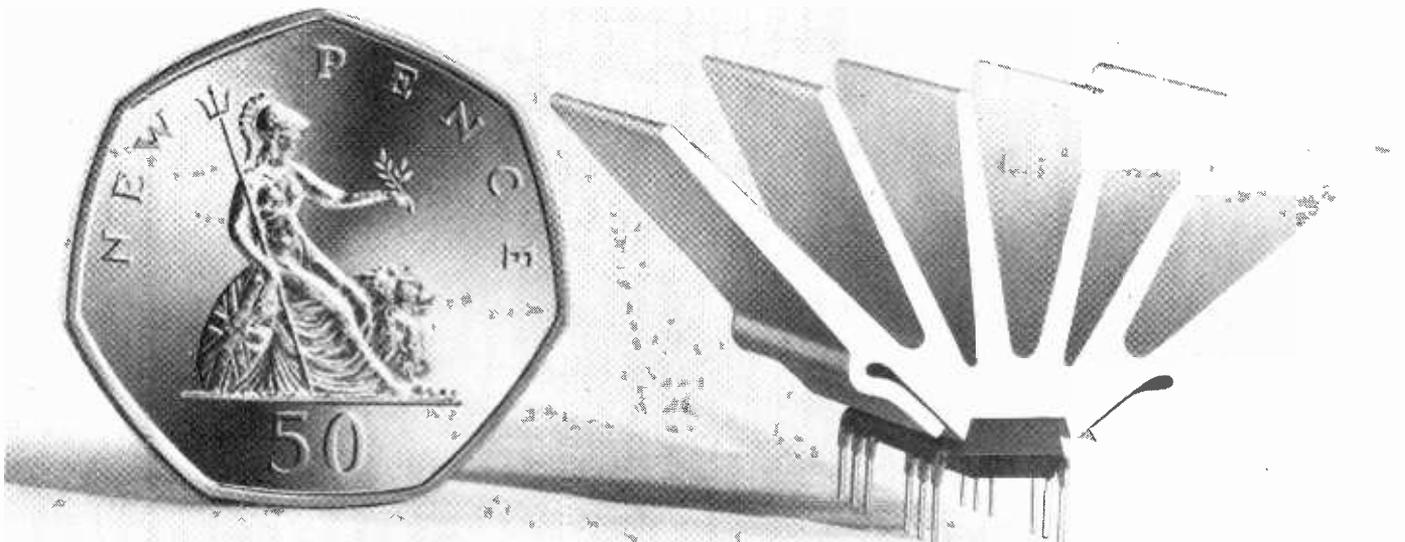

### High fidelity Monolithic Integrated Circuit Amplifier

Two years ago Sinclair Radionics announced the World's first monolithic integrated circuit Hi-Fi amplifier, the IC.10. Now we are delighted to be able to introduce its successor, the Super IC.12. This 22 transistor unit has all the virtues of the original IC.10 plus the following advantages:

1. Higher power.
2. Fewer external components.
3. Lower quiescent consumption.
4. Compatible with Project 60 modules.
5. Specially designed built-in heat sink. No other heat sink needed.
6. Full output into 3, 4, 5 or 8 ohms.
7. Works on any voltage from 6 to 28 volts without adjustment.
8. NEW 22 transistor circuit.

**Output power** 6 watts RMS continuous (12 watts peak).

**Frequency Response** 5 Hz to 100KHz  $\pm$  1 dB.

**Total Harmonic Distortion** Less than 1%. (Typical 0.1%) at all output powers and all frequencies in the audio band.

**Load Impedance** 3 to 15 ohms.

**Power Gain** 90dB (1,000,000,000 times) after feedback.

**Supply Voltage** 6 to 28 volts (Sinclair PZ-5 or PZ-6 power supplies ideal).

**Size** 22 x 45 x 28 mm including pins and heat sink.

**Input Impedance** 250 Kohms nominal.

**Quiescent current** 8mA at 28 volts.

With the addition of only a very few external resistors and capacitors the Super IC.12 makes a complete high fidelity audio amplifier suitable for use with pick-up, F.M. tuner etc. Alternatively, for more elaborate systems, modules in the Project-60 range such as the Stereo 60 and A.F.U. may be added. The comprehensive manual supplied with each unit gives full circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include car radios, oscillators etc. The very low quiescent consumption makes the Super IC.12 ideal for battery operation.



Price, inc. FREE printed circuit board for mounting.

**£2.98** Post free

Sinclair Radionics Ltd, London Rd, St. Ives  
Huntingdonshire PE17 4HJ  
Telephone St Ives (048 06) 4311




**sinclair**

**SINCLAIR GENERAL GUARANTEE**  
Should you not be completely satisfied with your purchase when you receive it from us, return the goods without delay and your money will be refunded in full, including cost of return postage, at once and without question. Full service facilities are available to all Sinclair customers.

WW—071 FOR FURTHER DETAILS
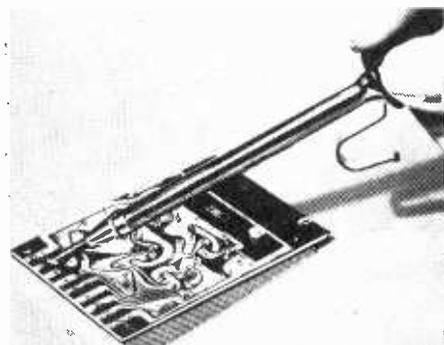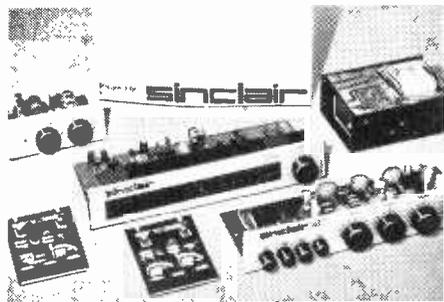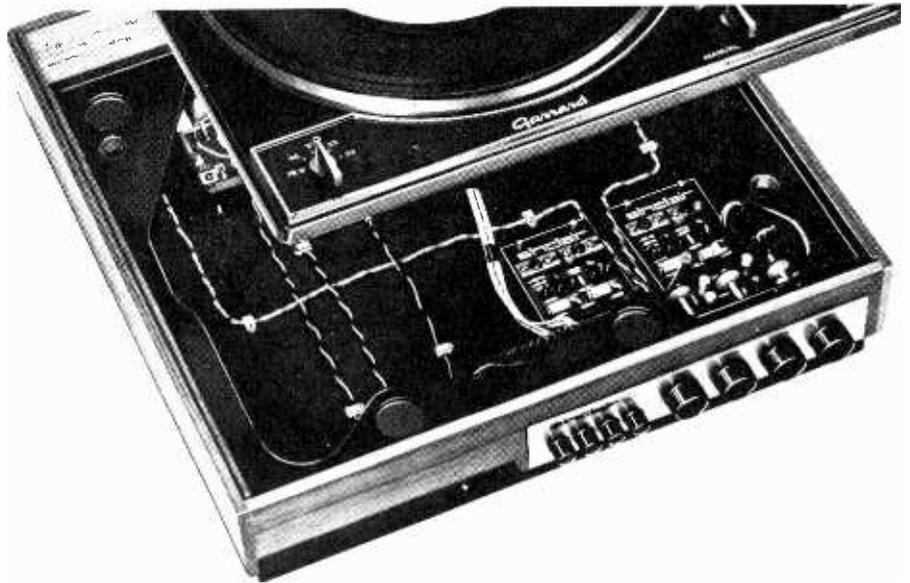
# Sinclair Project 60

The World's leading range of high fidelity modules



Project 60 offers more advantage to the constructor and user of high fidelity equipment than any other system in the world.

Performance characteristics are so good they hold their own with any other available system irrespective of price or size.

Project 60 modules are more versatile – using them you can have anything from a simple record player or car radio amplifier to a sophisticated and powerful stereo tuner-amplifier. Either power amplifier can be used in a wide variety of applications as well as high fidelity. The Stereo 60 pre-amplifier control unit may also be used with any other power amplifier system, as can the AFU filter unit. The stereo FM tuner operates on the unique phase lock loop principle to provide the best ever standards of sensitivity and audio quality. Project 60 modules are very easily connected together by following the 48 page manual supplied free with all Project 60 equipment. The modules are great space savers too and are sold individually boxed in distinctive white and black cartons. With all these wonderful advantages, there remains the most attractive of all – price. When you choose Project 60 you know you are going to get the best high fidelity in the world, yet thanks to Sinclair's vast manufacturing resources (the largest in Europe) prices are fantastically low and everything you buy is covered by the famous Sinclair guarantee of reliability and satisfaction.

#### Typical Project 60 applications

System	The Units to use	together with	Cost of Units
Simple battery record player	Z.30	Crystal P.U., 12V battery volume control	£4.48
Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control etc.	£9.45
20 + 20 W. stereo amplifier for most needs	2 x Z.30s, Stereo 60, PZ.5	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	£23.90
20 + 20 W. stereo amplifier with high performance spkrs.	2 x Z.30s, Stereo 60, PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.90
40 + 40 W. R.M.S. de-luxe stereo amplifier	2 x Z.50s, Stereo 60 PZ.8, mains trsfmr	As above	£34.88
Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£19.43


F.M. Stereo Tuner (£25) & A.F.U. Filter Unit (£5.98) may be added as required.

Sinclair Radionics Limited, London Road,  
St. Ives, Huntingdonshire PE17 4HJ.  
Tel: St. Ives (048 06) 4311

**sinclair**

# from a simple amplifier to a complete stereo tuner amplifier with Project 60 modules

## Z.30 & Z.50 power amplifiers

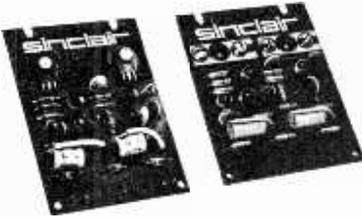

The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and may be used with other units in the Project 60 range equally well.

**SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).**

**Power Outputs**

**Z.30** 15 watts R.M.S. into 8 ohms using 35 volts; 20 watts R.M.S. into 3 ohms using 30 volts.

**Z.50** 40 watts R.M.S. into 3 ohms using 40 volts; 30 watts R.M.S. into 8 ohms using 50 volts.

**Frequency response:** 30 to 300,000Hz  $\pm 1$  dB.

**Distortion:** 0.02% into 8 ohms.

**Signal to noise ratio:** better than 70dB unweighted.

**Input sensitivity:** 250mV into 100 Kohms.

For speakers from 3 to 15 ohms impedance.

**Size:** 14 x 80 x 57 mm.

**Z.30**

Built, tested and guaranteed with circuits and instructions manual. **£4.48**

**Z.50**

Built, tested and guaranteed with circuits and instructions manual. **£5.48**

## Project 60 Stereo F.M. Tuner



*First in the world to use the phase lock loop principle*

The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other original features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and squelch circuit for silent tuning between stations. Good reception is possible in difficult areas, and often a few inches of wire are enough for an aerial. In terms of a high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with any other high fidelity system.

**SPECIFICATIONS—Number of transistors:** 16 plus 20 in I.C. **Tuning range:** 87.5 to 108 MHz. **Capture ratio:** 1.5dB. **Sensitivity:** 2  $\mu$ V for 30dB quieting; 7  $\mu$ V for full limiting. **Squelch level:** 20  $\mu$ V. **A.F.C. range:**  $\pm 200$  KHz. **Signal to noise ratio:** > 65dB. **Audio frequency response:** 10 Hz – 15 KHz ( $\pm 1$  dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2  $\mu$ V. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. **Operating voltage:** 25-30 VDC. **Indicators:** Mains on; Stereo on; tuning. **Size:** 93 x 40 x 207 mm.

Built and tested. Post free.

**£25**

## Stereo 60 Pre-amp/control unit



Designed for Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.

**SPECIFICATIONS—Input sensitivities:** Radio – up to 3mV. Mag. p.u. 3mV; correct to R.I.A.A curve  $\pm 1$ dB; 20 to 25,000 Hz. Ceramic p.u. – up to 3mV; Aux – up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE + 15 to -15dB at 10 KHz; BASS + 15 to -15dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207 mm. **£9.98**  
Built tested and guaranteed.

## Power Supply Units


Designed special for use with the Project 60 system of your choice. Use PZ.5 for normal Z.30 assemblies and PZ.6 where a stabilised supply is essential.

**PZ.5** 30 volts unstabilised **£4.98**


**PZ.6** 35 volts stabilised **£7.98**

**PZ.8** 45 volts stabilised (less mains transformer) **£7.98**

**PZ.8** mains transformer **£5.98**

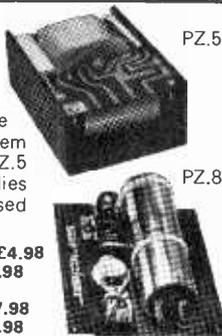

## A.F.U. High & Low Pass Filter Unit

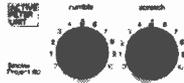

For use between Stereo 60 unit and two Z.30s or Z.50s, and is easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less

loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. Two filter stages – rumble (high pass) and scratch (low pass). Supply voltage – 15 to 35V. Current – 3mA. H.F. cut-off (-3dB) variable from 28KHz to 5KHz. L.F. cut-off (-3dB) variable from 25Hz to 100Hz. Distortion at 1KHz (35V. supply) (0.02% at rated output. **£5.98**  
Built tested and guaranteed.

## The Sinclair Guarantee

If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send

Name

Address

I enclose cash/cheque/money order.

WW8



# Contil INSTRUMENT CASES

The ideal 'off the shelf' low cost instrument housing. 2.1-gauge steel. Finished hammer blue, with 18-gauge panel supplied with easy-to-strip protective covering for easy marking out. Individually packed, including feet and screws.

Case No.	W	X	Y	Z
755	5	7	5	4
975	7	9	5	6
867	6	8	7	5
1277	7	12	7	6
18127	12	16	7	11
191010	10	19	10	9
191010	10	19	10	9

(Panel size—10" x 19" x 4 1/2" with 6" vertical)

## CHASSIS AND SPARE PANELS

Contil cases are also available with aluminium panels and Contilcoat, applied after drilling and cutting. There is also a chassis to fit each size of Contil case. Three smaller sizes in 18 gauge aluminium and three larger sizes in 16 gauge. Prices from 15p to 75p.

BRONZE	BLANKING PLUGS
100 off	500 off
500 off	1000 off

INCHES

25p	3/16	35p	30p
20p	5/16		
	3/8		
35p	7/16		
30p	1		
55p	1 1/8	55p	45p
50p	1 1/4	80p	70p

Assorted £1.40 lots  
1000 3/16" 50 ea. of others 1000 off 3/16", 50 ea. of others  
Postage & Packing 15p

## HANDLES

West Hyde carry stacks of four types of handles. The two Delrin types are 5.5/8" and 8 1/2" long with prices from 8p to 20p each. The two chrome panel handles are also in two sizes 3" and 5" with prices from 20p to 37p each. Both types of handles are ideal for our cases as the illustration shows.

## FEET

You could tramp the World and not find better feet!  
The West Hyde foot is moulded from a resilient, high hysteris material, giving a high friction coefficient. Self-adhesive or screw fixing or both (6BA countersunk). Size 5/8" dia. 3/8" high. Grey. Price from 0.010 to 0.017 each.



# WEST HYDE WH

WEST HYDE DEVELOPMENTS LTD. RYEFIELD CRESCENT, NORTHWOOD HILLS, MIDDX. HA6 1NN  
Telephone: Northwood 24941/26732 Telex: 923231 Code: West Hyde Nthwd.  
WW—074 FOR FURTHER DETAILS



'Brightlife' neons give greater brightness and 25,000 hours average life. The 1/2" diameter neons are moulded in polypropylene which diffuses the light and the 3/4" diameter neons are moulded in polycarbonate which gives higher light transmission. Both types give a glow behind the panel to warn maintenance staff. Units are one hole fixing 1/2" and 3/4" diameter clearance.

The very low cost of these neon/resistor assemblies makes them ideal for safety uses, particularly in transistorised equipment where most voltages are safe to be handled. Usually the mains transformer has the only dangerous terminals and for a few pence these indicators can be soldered on directly as a warning light. Unlike incandescent indicators these can be fitted and forgotten.

10 off	100 off	1000 off
0.15	0.14	0.12
0.17	0.16	0.14
0.20	0.18	0.16
0.05	0.04	0.04
0.05	0.04	0.03
0.03	0.02	0.01

6" PC, 6" PP, 110PC, 110PP, T, K  
30" PC, 30" PP, R  
PP/G, PP/H, Q, Alpha numeric.  
M or M110  
N  
PP/I, PP/J, L, Spare caps & bodies

Post and Packing—15p any quantity

# WEST HYDE WH

WEST HYDE DEVELOPMENTS LIMITED, RYEFIELD CRESCENT, NORTHWOOD HILLS, NORTHWOOD, MIDDX., HA6 1NN.  
Telephone: Northwood 24941/26732 Telex: 923231  
WW—075 FOR FURTHER DETAILS

# ONTOS UNIVERSAL VICE

For use wherever a third hand is needed. Fully adjustable for any angle in any plane. £3.60. P & P 28p

Another PAIR of hands. £5.95. P & P 35p

A unique two-in-one version with 2 sets of jaws, each rotatable through 360° in any plane.

# TEST ADAPTOR

The Ontos is a multi-purpose, multi-position vice, ideal for holding P.C. boards for assembly, soldering or testing. The jaws will hold flat, round, square, or hexagonal parts. It is quickly reset to any new angle, in any plane, making it ideal for building up modules, as a micrometer or gauge stand, as a light general purpose vice, in the laboratory, or whenever you need an extra pair of hands!

Always ready for the out of reach socket. Easy-to-carry lightweight reel with neon indicator, moulded in rewind handle and easy wind non-twist cable, 13 amp fused plug and socket. Either 50 ft of 5 amp or 30 ft of 13 amp cable, 30 ft 13 amp or 50 ft 5 amp. 1 at £4.98. P & P 35p.

DISCOUNTS FOR QUANTITY. POSTAGE & PACKING EXTRA

# WEST HYDE WH

Typically used in quantities by washing machine manufacturers and suitable for lab use etc. Fitted with non-wire-cutting contacts and fuse. Suitable for up to 13 amps. A neon indicator lights when mains is on the outer sockets. 1 at £1.35. P&P 15p

SEND FOR FREE LEAFLETS & PRICE LIST  
WEST HYDE DEVELOPMENTS LTD., RYEFIELD CRESCENT, NORTHWOOD HILLS, MIDDX., HA6 1NN  
Telephone: Northwood 24941/26732 Telex: 923231 WEST HYDE NTHWD  
WW—076 FOR FURTHER DETAILS

# CONTIL MOD-2

This illustration shows Sinclair Project 60 made-up using Mod-2 Greedy punched case

Contil Mod-2 instrument cases are ideal for development and cheaper for production. Made with PVC coated materials there is no paint to scratch, the surface is scuff resistant and easy to clean. Coated aluminium front and back panels gives easy cutting with rigidity and coated steel top, bottom and sides gives strength and ease of assembly. Three heights of cases, four widths and two depths give 48 different cases. Mod-2 means modern design, low cost, off the shelf delivery.

	X	Y	Z	1 off	P & P		X	Y	Z	1 off	P & P
A	4.5	3	6.5	1.90	15p	N	4.5	7	13	3.05	28p
B	4.5	7	6.5	2.20	28p	O	4.5	10	13	4.00	35p
C	4.5	10	6.5	2.75	28p	P	9	3	13	3.05	28p
D	9	3	6.5	2.75	28p	Q	9	7	13	4.00	35p
E	9	7	6.5	3.05	28p	R	9	10	13	4.90	35p
F	9	10	6.5	3.60	28p	S	13	3	13	4.00	35p
G	13	3	6.5	3.05	28p	T	13	7	13	4.90	35p
H	13	7	6.5	3.60	28p	U	13	10	13	6.00	45p
I	13	10	6.5	4.00	35p	V	18	3	13	4.90	35p
J	18	3	6.5	3.60	28p	W	18	7	13	8.00	45p
K	18	7	6.5	4.90	35p	X	18	10	13	7.60	45p
L	18	10	6.5	6.00	45p	G	Woodgrain			4.00	28p
M	4.5	3	13	2.20	28p						

Sizes in inches

Kit of Sinclair hardware inc. capacitors, plugs, sockets, screws, wire heat sink, fuse, fuse holder, etc. £3.40 P & P 22p  
Sinclair punched case and chassis. Mod 2 type G in wood grain. £4.25 P & P 28p

Type G is now available in simulated teak in wood grain finish and ideally suited for domestic equipment. Also available ready punched for Sinclair Project 60, with or without A.F.U. It is available with a set of fitting plugs, sockets, fuses, etc.

# WEST HYDE WH

WEST HYDE DEVELOPMENTS LIMITED, RYEFIELD CRESCENT, NORTHWOOD HILLS, NORTHWOOD, MIDDX., HA6 1NN.  
Telephone: Northwood 24941/26732 Telex: 923231  
WW—077 FOR FURTHER DETAILS

# EXCLUSIVE OFFER of COMMUNICATION RECEIVERS RC410/R and RC411/R and H.F. SYNTHESIZERS RC460/S

- MANUFACTURED BY WORLD RENOWNED BRITISH COMPANY
- ALL TRANSISTOR/I.C. CIRCUITRY
- COVERAGE RC410/R 2-31MHz in 29 BANDS  
RC411/R 15KHz-31MHz in 31 BANDS
- DIGITAL DISPLAY INDICATING TUNED FREQUENCY GENERATED BY INTEGRAL SYNTHESIZER
- LOCAL OSCILLATOR DRIFT LESS THAN 1 PART IN  $10^8$  PER DAY
- OVERALL FREQUENCY STABILITY BETTER THAN 5 PARTS IN  $10^7$

OTHER CHARACTERISTICS INCLUDE:—

Aerial input impedance 50 ohms unbalanced  
Maximum Sensitivity:—  $0.5\mu\text{V}$  for 12dB  $\frac{S+N}{N}$

at standard output (Odbm into 600 ohm balanced load)  
Intermediate Frequencies 1.6MHz and 100KHz  
I.F. Selectivities:— 3dB Bandwidths of  $\pm 3.5\text{KHz}$ ,  $\pm 1.5\text{KHz}$ ,  
 $\pm 0.6\text{KHz}$ ,  $\pm 0.15\text{KHz}$ .


Notch Filter  $\pm 4\text{KHz}$  about a centre frequency of 100KHz.  
A.G.C. 3 switched attack/decay times of 10/600, 20/800 and  
30/2000 mS.

Audio Output 1 watt into 3 ohms or 10mW into 600 ohms.  
Noise Limiter

'S' Meter.

Mains Input 100/125 or 200/250v. 50/60Hz 70W.

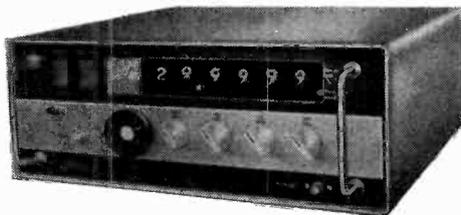Dimensions 9" high, 19.2" wide, 18.75" deep, suitable for  
19" rack mounting.



**THE SYNTHESIZERS TYPE RC460/S have the following main characteristics:—**

- FREQUENCY COVERAGE 1MHz to 29.9999 MHz in 100Hz steps
- FACILITY FOR USING EXTERNAL FREQUENCY STANDARDS OF 5MHz, 1MHz, 200KHz or 100KHz AS WELL AS THE INTERNAL STANDARD OF 5MHz
- FREQUENCY STABILITY OF BETTER THAN 1 PART IN  $10^6$  PER 100 DAYS, 3 PARTS IN  $10^8$  PER DAY
- OUTPUT 0.3-1v r.m.s. INTO 50 OHMS (metered)

The Mains supply to the unit is 100/125 or 200/250v. 50/60Hz 60W.

The dimensions 7" high, 19.2" wide, 18" deep, suitable for rack mounting.

**PRICES OF THE ABOVE INSTRUMENTS ARE:—**

**RC410/R £300, RC411/R £350 (List £1,500 approx.)  
RC460/S (Bench or Rack Mounting version) £150**

All instruments supplied complete with handbooks.

Carriage extra at cost but we would recommend customers to arrange to collect from any of the addresses below by appointment at all of which the equipments can be demonstrated. Alternatively, delivery to U.K. Mainland can be arranged by special carrier at a cost of £5 per item (England) or £10 per item (Scotland). (Plus insurance £1.) TERMS: Strictly C.W.O. or supply against official order from approved customers.

**THESE RECEIVERS AND SYNTHESIZERS HAVE BECOME AVAILABLE OWING TO RATIONALISATION OF RANGE FOLLOWING AN AMALGAMATION OF COMMERCIAL INTERESTS  
DON'T DELAY OUR STOCKS ARE STRICTLY LIMITED!**

Demonstration equipments are held at the following points:—

**S. and S.W. London:** Servo and Electronic Sales Ltd., 67 London Road, Croydon, Surrey. Tel. 01-688-1512. **S.E. London and N.W. Kent:** Servo and Electronic Sales Ltd., 43 High Street, Orpington, Kent. Tel. 31066. **Sussex and Southern England:** G.W.M. Radio Ltd., Portland Road, Worthing, Sussex. Tel. 34897. **E. Kent:** Servo and Electronic Sales Ltd., Mill Road, Lydd (STD 06792), Kent. Tel. Lydd 252. Overseas enquiries and home orders to our Lydd address please.

**SERVO AND ELECTRONIC SALES LTD.**  
ELECTRONIC SUPPLIES FOR INDUSTRY AND EDUCATION THROUGHOUT THE WORLD

# BI-PRE-PAK LIMITED

### FULLY TESTED AND MARKED

AC107	15p	OC170	23p
AC126	13p	OC171	23p
AC127	17p	OC200	25p
AC128	13p	OC201	25p
AC176	25p	2G301	13p
ACY17	15p	2G303	13p
AF239	37p	2N1302.3	40p
AF186	50p	2N1304.5	25p
AF139	37p	2N1306.7	30p
BC154	25p	2N1308.9	35p
BC171 = BC107	13p	BC113	10p
BC172 = BC108	13p		
BF194	15p	<b>Power Transistors</b>	
BF274	15p		
BFY50	20p		50p
BSY25	37p	OC23	30p
BSY26	13p	OC25	25p
BSY27	13p	OC26	25p
BSY28	13p	OC28	30p
BSY29	13p	OC35	25p
BSA95A	13p	OC36	37p
OC41	13p	AD149	30p
OC44	13p	2N3055	63p
OC45	13p	2S034	25p
OC71	13p	<b>Diodes</b>	
OC72	13p	AA442 = OA5	10p
OC81	13p	OA91	9p
OC81D	13p	OA79	9p
OC139	13p	OA81	9p
OC140	17p	IN914	7p

**FREE!**  
PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 50p WITH ORDERS OVER £4

### CLEARANCE LINES

	1-10	10-50	50+
SL 403D Audio Amp.	2.00	1.95	1.80
IC. 709C Linear Opp. Amp.	50p	40p	35p
A.E.I. Fully marked & tested Gates	25p	22p	20p
A.E.I. Fully marked & tested Flipflops	50p	40p	30p
OC71/72. Fully tested, unmarked	5p	5p	4p
Matched Sets. 1-OC44, 2-OC45 Per set	25p	20p	15p
Matched Sets. OC45, 1st & 2nd I.F. Per set	15p	12p	10p
TIC45 Thyristors. -6A, 60V, Texas	15p	15p	12p
OA47 Gold bonded Diodes, marked & tested	3p	3p	2p
1W Zener Diodes:			
6.8V, 7.5V, 24V, 27V, 30V & 43V	5p	4p	3p
10W Zener Diodes:			
7.5V, 11V, 13V, 20V & 100V	20p	17p	15p
Micro Switches, S/P, C/O. Popular size	25p	20p	15p
1 Amp. Bridge Rectifiers, 25V, RMS	25p	22p	20p

1 Amp Plastic Rectifiers: These are voltage, reverse Polarity and other rejects from the BY127 range. Ideal for low voltage Power Units etc. Price: £1 per 100.

### COLOUR T.V. LINE OUTPUT TRANSFORMERS.

Designed to give 25 K.V. when used with PL509 and PY500 valves. As removed from colour receivers at the factory.  
**ONLY £1 each**  
Post and packing 23p

### BUMPER BUNDLES

These parcels contain all types of surplus electronic components, printed panels, switches, potentiometers, transistors and diodes, etc.

**2 LBS IN WEIGHT FOR £1**  
Post and packing 25p

### NEW TESTED & GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries .3 to .5 volt, .5 to 2 ma.	50p
H8	4	BY127 Silicon Recs. 1000 P.I.V. 1 amp. Plastic. Replaces the BY100.	50p
B79	4	1N4007 Sil. Rec. Diodes, 1,000 P.I.V. 1 amp. Plastic.	50p
B81	10	Reed Switches, mixed types, large and small.	50p
B99	200	Mixed Capacitors, Post and packing 13p Approx. Quantity counted by weight.	50p
H4	250	Mixed Resistors, Post and packing 10p. Approx. Quantity counted by weight.	50p
H7	40	Wirewound Resistors, Mixed Values, Postage 7p.	50p
H9	2	OC71 Light Sensitive Photo Transistors.	50p
H12	20	NKT155/259 Germ diodes, brand new stock clearance.	50p
H18	10	OC71/75 uncoded black glass type PNP Germ.	50p
H19	10	OC81/81D uncoded white glass type PNP Germ.	50p
H28	20	OC200/1/2/3 PNP silicon uncoded TO-5 Can	50p
H29	20	OA47 gold bonded diodes coded MCS2.	50p

### F.E.T. PRICE BREAKTHROUGH

This field effect transistor is the 2N3823 in a plastic encapsulation; coded 3823E. It is an ideal replacement for the 2N3819. Data Sheet supplied with device.  
1-10 = 30p each, 10-50 = 25p each, 50+ = 20p each.

**Make a Rev. Counter for your Car.** The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a perfectly linear and accurate rev. counter for any car. **£1 each**

### OUR VERY POPULAR 3p TRANSISTORS FULLY TESTED & GUARANTEED

TYPE "A"	TYPE "B"	TYPE "F"	TYPE "E"
<b>PNP Silicon</b> alloy, metal TO-5 can. 2S300 type, direct replacement for the OC200/203 range	<b>PNP Silicon</b> PLASTIC ENCAPSULATION, low voltage but good gain, these are of the 2N3702/3 and 2N4059/62 range.	<b>NPN Silicon</b> PLASTIC ENCAPSULATION Low Noise Amplifier of the 2N3707/8/9/10/11 Series.	<b>PNP Germanium</b> AF OR RF please state on order. Fully marked and tested.

### BULK BUYING CORNER

NPN/PNP Silicon Planar Transistors, mixed untested, similar to 2N706/6A/8, BSY26-29, BSY95A, BCY70 etc. £4.25 per 500. £8.00 per 1,000.

Silicon Planar NPN Plastic Transistors, untested, similar to 2N3707-11 etc. £4.25 per 500. £8.00 per 1,000.

Silicon Planar Diodes, DO-7 Glass, similar to OA200/202, 8AY31-36. £4.50 per 1,000.

NPN/PNP Silicon Planar Transistors, Plastic TO-18, similar to BC113/4, BC153/4, BF153/160 etc. £4.25 per 500. £8.00 per 1,000.

OC44, OC45 Transistors, fully marked and tested. 500 plus @ 8p each, 1,000 plus @ 6p each.

OC71 Transistors, fully marked and tested. 500 plus @ 6p each, 1,000 plus @ 5p each.

3823E Field effect Transistors. This is the 2N3823 in plastic case. 500 plus @ 13p each, 1,000 plus @ 10p each.

1 Amp Miniature Plastic Diodes:  
1N4001 500 plus @ 3p each, 1,000 plus @ 3p each.  
1N4004 500 plus @ 5p each, 1,000 plus @ 4p each.  
1N4006 500 plus @ 6p each, 1,000 plus @ 5p each.  
1N4007 500 plus @ 8p each, 1,000 plus @ 7p each.

### NEW UNMARKED UNTESTED PAKS

B80	8	Dual Trans. Matched O/P pairs NPN, Sil. in TO-5 can	50p
B83	200	Trans. manufacturer's rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP, equiv. to OC200/1, 2N706A, 8SY95A, etc.	50p
B60	10	7 watt Zener Diodes Mixed Voltages	50p
H6	40	250mW Zener Diodes DO-7 Min. Glass Type	50p
H10	25	Mixed volts, 1 1/2 watt Zeners. Top hat type	50p
B66	150	High quality Germ. Diodes. Min. glass type	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers, 1 amp plastic. Mixed volts	50p

### FREE CATALOGUE AND LISTS for: -

**ZENER DIODES  
TRANSISTORS, RECTIFIERS  
FULL PRE-PAK LISTS  
& SUBSTITUTION CHART**

MINIMUM ORDER 50p CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE

**P.O. RELAYS** 8 for  
VARIOUS CONTACTS AND COIL RESISTANCES.  
NO INDIVIDUAL SELECTION.  
POST & PACKING 25p **£1**

**FREE! A WRITTEN GUARANTEE WITH ALL OUR TESTED SEMICONDUCTORS**


**BI-PRE-PAK LTD**

DEPT. B, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX  
TELEPHONE: SOUTHEND (0702) 46344

# Laskys

**EXCLUSIVE**

## DIGITAL CLOCK MECHANISM

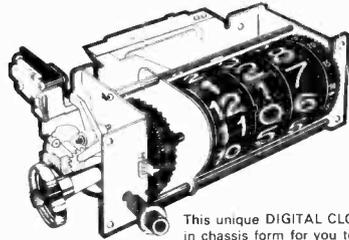

- Made especially for Lasky's by famous maker
- Mains operation
- 12 hour alarm
- Auto "SLEEP" switch
- Hours, minutes and seconds read-off
- Forward and backward time adjustment
- Silent operation synchronous motor
- Shock and vibration proof
- Built in alarm buzzer

This unique DIGITAL CLOCK is now available EXCLUSIVELY FROM LASKY'S in chassis form for you to mount in any housing that you choose. All settings are achieved by two dual-concentric controls at the front including: ON-OFF-

AUTO and AUTO ALARM, "sleep" switch, 10 minute division "click" set alarm (up to 12 hour delay), time adjustment. Ultra simple mechanism and high quality manufacture guarantee reliable operation and long life.

The sleep switch will automatically turn off any appliance—radio, TV, light, etc., at any pre-set time up to 60 min. and in conjunction with the AUTO setting will switch on the appliance again next morning.

The clock measures 4 1/2" x 1 1/2" x 3 1/2" (overall from front of drum to back of switch). SPEC: 210/240V AC. 50Hz operation—switch rating 250V 3A. Complete with instructions. HUNDREDS OF APPLICATIONS.

COMPLETE WITH SET OF CONTROL KNOBS

SPECIAL QUOTATIONS FOR QUANTITIES

**LASKY'S PRICE £6.95** P & P 18p.

## BSR McDonald MP60

High precision, low-mass, counterbalanced pick-up arm, heavy balanced turntable, viscous cueing device, slide in cartridge, 4 pole motor.




**LASKY'S PRICE £12.50** POST 35p  
With plinth and cover £15.75 POST 40p.

### BSR McDonald units and packages

A. Chassis only. B. Complete with Lasky's plinth and cover. C. Complete with Lasky's plinth, cover and AD76K cart. D. comp. wired on BSR plinth with cover. E. As D plus AD76K cartridge.

Model	A	B	C	D	E
610	£15.45	£18.75	£22.50	£24.50	£28.50
510	£13.45	£16.95	£20.75	£22.00	£26.00
310	£9.95	£13.45	£17.25	£21.00	£23.50
MP60	£12.50	£15.75	£19.50	£21.50	£25.50

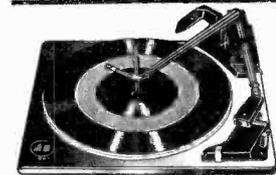

## GARRARD SL55B

Four speed autochanger that accepts up to 8 LP's. Has all the refinements that Garrard SL turntables are famous for. With lifting device that allows 'spot-on' track selection on all discs and perfect cueing facilities for singles. Wired for mono and stereo. Size 14in (W) x 11 1/2in (D) 4 1/2in above and 3in below unit plate.

**LASKY'S PRICE £10.50** POST 35p.

### GARRARD DECKS

Garrard SP 25 Mk.II	£11.50	Garrard SP 25 Mk.III with 9TA	£10.50
Garrard SP 25 Mk.III	£13.95	Garrard 2025TC with 9TA	£9.85
wired	£12.00	Garrard AP 76	£20.95

### GARRARD PACKAGES

Package	Price
Garrard AP 76 with AD76K cart. and Lasky's plinth and cover	£35.00
Garrard AP 76 with Shure M44E cart. and Lasky's plinth and cover	£40.00
Garrard SP 25 Mk.III, AD76K cart. and Lasky's plinth and cover	£20.00
Garrard SP 25 Mk.III, Micro M2100/e cart. and Lasky's plinth and cover	£25.00

## DENSHI BOARD KITS

The Denshi Board system enables the young experimenter and electronics hobbyist to produce a wide range of transistor circuits of increasing sophistication—without soldering or the use of any tools at all. Each kit utilizes plug-in encapsulated components.

### DENSHI KIT SR-1A


Kit comprises: Base board; tuner block, 4 resistors; choke coil; transformer; 2BA transistor for RF; 2 diodes; 3 capacitors; battery block; morse key; antenna lead; crystal earphones; various bridge and connecting pieces. This kit permits the building of 16 basic circuits.

### DENSHI KIT SR-3A

Kit comprises of: 2 base boards, 50 component and accessory parts inc. 3 transistors and 2 diodes, vol. control, 2 1/2in speaker in extension baffle housing, cadmium sulphide photo cell, crystal mic., earpiece, test probes, morse key, extension leads etc. Build at least 100 projects Comp. with batt.
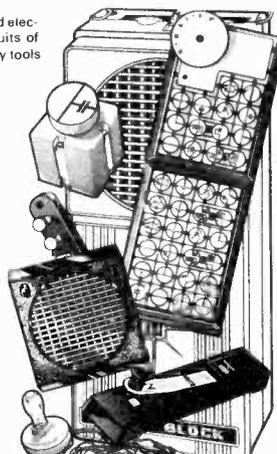
### DENSHI DR-7 (illustrated)

With this kit you can build various types of IF amplifiers and both audio and power amplifiers which can be used with external auxiliary equipment. Comprises 3in loudspeaker, personal earpiece, 7 transistors, diode, thermistor, volume control, capacitors, resistors, tuning capacitor, battery connectors, external project terminal blocks, shoulder carrying strap, battery, etc. PLUS 35 page manual of theory and schematics. High impact resistant case. Will house any of the radio receiver circuits thus making an excellent portable radio.



SR-1A £3.35 SR-3A £11.00 DR-7 £9.75

POST ON ALL KITS 15p

207 EDGWARE ROAD, LONDON, W.2  
33 TOTTENHAM CT. RD, LONDON, W1P 9RB.  
109 FLEET STREET, LONDON, E.C.4.  
152/3 FLEET STREET, LONDON, E.C.4.  
**HIGH FIDELITY AUDIO CENTRE**  
42-45 TOTTENHAM CT. RD, LONDON, W1P 9RD.  
**MAIL ORDERS AND CORRESPONDENCE TO**  
3-15 CAVELL STREET, LONDON, E1 2BN

# TRANSFORMERS

**MAINS ISOLATING SERIES**  
Primary 200-250 Volts Secondary 240 Volts Centre Tapped (120V) and Earth Shielded  
ALSO AVAILABLE WITH 115/120V SECONDARY WINDINGS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Qty. 1-24	Qty. 25-99	P.P. each Np
61	100	5 12	10.2 x 8.9 x 8.3	2.28	2.13	52
62	250	12 4	9.5 x 12.7 x 11.4	5.05	4.66	67
63	500	27 0	17.1 x 11.4 x 15.9	9.74	9.01	..
92	1000	40 0	17.8 x 17.1 x 21.6	17.94	16.59	..
128	2000	63 0	24.1 x 21.6 x 15.2	29.66	27.43	..
129	3000	84 0	21.6 x 21.6 x 20.3	46.38	42.90	..
190	6000	178 0	31.1 x 35.6 x 17.1	76.11	70.48	..



### AUTO SERIES (NOT ISOLATED)

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	Qty. 1-24	Qty. 25-99	P.P. each Np
113	20	1 1	7.3 x 4.3 x 4.4	0-115-210-240	0.74	0.69	20
64	75	1 4	7.0 x 4.4 x 7.6	0-115-210-240	1.44	1.33	30
4	150	3 0	8.9 x 6.4 x 7.6	0-115-200-220-240	1.74	1.61	36
66	300	6 0	10.2 x 10.2 x 9.5	..	3.38	3.13	52
67	500	12 8	14.0 x 10.2 x 11.4	..	5.03	4.65	67
84	1000	16 0	11.4 x 14.0 x 14.0	..	9.12	8.84	82
93	1500	28 9	13.5 x 14.9 x 16.5	..	13.22	12.23	..
95	2000	40 0	17.8 x 16.5 x 21.6	..	19.26	15.95	..
75	3000	45 8	17.4 x 18.1 x 21.6	..	23.47	21.73	..

### LOW VOLTAGE SERIES (ISOLATED) PRIMARY 200-250 VOLTS 12 AND/OR 24 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Windings	Qty. 1-24	Qty. 25-99	P.P. each Np
111	0.5	2 5	7.6 x 5.7 x 4.4	0-12V at 0.25A x 2	0.74	0.69	22
213	1.0	5 1	8.3 x 5.1 x 5.1	0-12V at 0.5A x 2	0.88	0.81	22
71	2	1 0	7.0 x 6.4 x 5.7	0-12V at 1A x 2	1.16	1.07	22
18	4	2 4	8.3 x 7.0 x 7.0	0-12V at 2A x 2	1.62	1.50	36
70	6	3 12	10.2 x 7.6 x 8.6	0-12V at 3A x 2	1.95	1.81	42
72	10	5 6	7.9 x 10.8 x 10.2	0-12V at 5A x 2	2.56	2.37	52
17	16	7 8	12.1 x 9.5 x 10.2	0-12V at 8A x 2	3.95	3.16	52
115	20	10 13	12.1 x 11.4 x 10.2	0-12V at 10A x 2	5.03	4.70	67
187	30	15 12	13.3 x 12.1 x 12.1	0-12V at 15A x 2	9.28	8.58	82

### 30 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Taps	Qty. 1-24	Qty. 25-99	P.P. each Np
112	0.5	1 4	8.3 x 3.7 x 4.9	0-12-15-24-30V	0.88	0.81	22
79	1.0	2 0	7.0 x 6.4 x 6.0	..	1.16	1.10	36
3	2.0	3 2	8.9 x 7.0 x 7.6	..	1.75	1.63	36
20	3.0	4 6	10.2 x 8.9 x 8.6	..	2.16	1.95	42
21	4.0	6 0	10.2 x 9.5 x 8.6	..	2.56	2.37	52
117	6.0	7 8	12.1 x 9.5 x 10.2	..	3.79	3.51	52
89	10.0	12 2	14.0 x 10.2 x 11.4	..	6.21	5.74	67

### 50 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Windings	Qty. 1-24	Qty. 25-99	P.P. each Np
102	0.5	1 11	7.0 x 7.0 x 5.7	0-19-25-33-40-50V	1.16	1.07	30
103	1.0	2 10	8.3 x 7.3 x 7.0	..	1.69	1.57	36
104	2.0	5 0	10.2 x 8.9 x 8.6	..	2.34	2.16	42
105	3.0	6 0	10.2 x 10.2 x 9.3	..	3.18	2.95	52
106	4.0	9 4	12.1 x 11.4 x 10.2	..	4.20	3.89	52
107	6.0	12 4	12.1 x 11.1 x 13.3	..	6.21	5.74	67
118	8.0	18 9	13.3 x 13.3 x 12.1	..	8.10	7.49	97
119	10.0	19 12	16.5 x 11.4 x 15.9	..	10.15	9.39	97

### 60 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Windings	Qty. 1-24	Qty. 25-99	P.P. each Np
124	0.5	2 4	8.3 x 9.5 x 6.7	0-24-30-40-48-60V	1.18	1.09	36
126	1.0	3 0	8.9 x 7.6 x 7.6	..	1.64	1.52	36
127	2.0	5 6	10.2 x 8.9 x 8.6	..	2.56	2.37	42
123	3.0	10 6	11.4 x 9.5 x 11.4	..	5.03	4.65	67
120	6.0	16 12	13.3 x 12.1 x 12.1	..	7.28	6.73	82
122	10.0	23 2	16.5 x 12.7 x 16.5	..	12.05	11.15	..

### LEAD ACID BATTERY CHARGER TYPES PRIMARY 200-250 VOLT FOR CHARGING 6 OR 12 VOLT BATTERIES

Ref. No.	Amps	Weight lb oz	Size cm.	Qty. 1-24	Qty. 25-99	P.P. each Np
45	1.5	1 9	7.0 x 6.0 x 6.0	1.17	1.08	30
5	4.0	3 11	10.2 x 7.0 x 8.3	1.77	1.64	42
86	6.0	5 12	10.2 x 8.9 x 8.3	2.67	2.47	52
146	8.0	6 4	8.9 x 10.2 x 10.2	3.04	2.82	52
50	12.5	11 14	13.3 x 10.8 x 12.1	4.52	4.18	67

★ CARRIAGE VIA B.R.S.

All ratings are continuous. Standard construction: open with solder tags and wax impregnation. Enclosed styles to order.

### VARIABLE VOLTAGE TRANSFORMERS (ENCLOSED)

Input	Output	Price
2.5 Amp.	5-50	18.50
1 Amp.	6-75	21.00
5 Amp.	9-75	37.00
8 Amp.	14-50	..

Higher current types available on application.  
ALSO AVAILABLE: Open construction variable voltage transformers, suitable for panel mounting.  
0.5 Amp. £3.93 | 1 Amp. £5.50 | 2.5 Amp. £6.63

★ Custom production winding service.  
★ Ex stock items same day service.  
Also stocked: SEMICONDUCTORS · VALVES  
MULTIMETERS · MAINS KEYNECTOR  
SEE PAGE 93

**BARRIE ELECTRONICS**  
11 MOSCOW ROAD · QUEENSWAY  
LONDON, W.2  
Telephone: 01-229 6681/2 or 550 1128  
Nearest Tube Stations: Bayswater, Queensway

VALVES		EAB80		EP91 0-83		GY501 0-80		PCF201		QV03/10		QV06-20		UABC80		2D21 0-85		6AQ4 0-50		68G7 0-30		30C17 0-85		886A 0-75		
CV4031 0-60	CV4033 0-60	CV4044 0-60	CV4045 0-75	CV4048 0-90	CV4062 1-50	CV4064 2-75	CV4068 0-60	CV4072 0-60	CV4074 0-60	CV4076 0-60	CV4078 0-60	CV4080 0-60	CV4082 0-60	CV4084 0-60	CV4086 0-60	CV4088 0-60	CV4090 0-60	CV4092 0-60	CV4094 0-60	CV4096 0-60	CV4098 0-60	CV4100 0-60	CV4102 0-60	CV4104 0-60	CV4106 0-60	
AS1 0-48	ACT9 25-90	ARF38 1-25	AZ31 0-55	BT19 4-60	BT79 3-60	BT99 4-10	CIC 1-90	CBL31 0-90	OCH35 0-75	CV5 7-90	CV74 6-60	CV82 4-25	CV815 4-25	CV854 5-50	CV872 17-90											
CV4031 0-60	CV4033 0-60	CV4044 0-60	CV4045 0-75	CV4048 0-90	CV4062 1-50	CV4064 2-75	CV4068 0-60	CV4072 0-60	CV4074 0-60	CV4076 0-60	CV4078 0-60	CV4080 0-60	CV4082 0-60	CV4084 0-60	CV4086 0-60	CV4088 0-60	CV4090 0-60	CV4092 0-60	CV4094 0-60	CV4096 0-60	CV4098 0-60	CV4100 0-60	CV4102 0-60	CV4104 0-60	CV4106 0-60	

Transistors		2G416 0-33		2N4289 0-18		AD161 0-85		BCV72 0-90		GET875		NKT217		NKT718		OC24 0-80		OC45 0-15		OC78 0-20		OC82D 0-15		OCPT1 0-88	
18111 0-13	2G210 0-88	2N3055 0-75	2N3707 0-15	2N3710 0-13	2N4068 0-18	2N4286 0-15	AD140 0-50	BC109 0-13	BCV750 0-83	NKT211	NKT218	OAS5 0-13	OC26 0-25	OC72 0-25	OC74 0-30	OC75 0-25	OC76 0-25	OC77 0-40	OC82 0-25	OC83 0-25	OC84 0-25	OC81M 0-20	OC169 0-20	OC170 0-25	OC171 0-30
18111 0-13	2G210 0-88	2N3055 0-75	2N3707 0-15	2N3710 0-13	2N4068 0-18	2N4286 0-15	AD140 0-50	BC109 0-13	BCV750 0-83	NKT211	NKT218	OAS5 0-13	OC26 0-25	OC72 0-25	OC74 0-30	OC75 0-25	OC76 0-25	OC77 0-40	OC82 0-25	OC83 0-25	OC84 0-25	OC81M 0-20	OC169 0-20	OC170 0-25	OC171 0-30

Valves tested and released to A.R.B. specification if required.

Express postage 5p for one valve, 1p each additional valve. Over £3 postage free. Open to callers Mon. to Sat., 9 a.m.—5 p.m. Closed Sat., 1—2.30 p.m. Complete range of TV Tubes available from £4.25. Postage 1p for each transistor, over 10 post free.

# R.S.T.

## VALVE MAIL ORDER CO.

BLACKWOOD HALL, 16A WELLFIELD ROAD, LONDON, SW16 2BS  
Telephone: 01-769 0199/1649

SEND FOR LIST OF 6,000 TYPES VALVES, TUBES & TRANSISTORS  
Manufacturers and Export enquiries welcomed

# WEYRAD

## COILS AND I.F. TRANSFORMERS IN LARGE-SCALE PRODUCTION FOR RECEIVER MANUFACTURERS

**P.11 SERIES** 10 mm. x 10 mm. x 14 mm. Ferrite cores 3 mm. 472 kc/s operation. Single-tuned I.F.s and Oscillator Coils.

**P.55 SERIES** 12 mm. x 12 mm. x 20 mm. Ferrite cores 4 mm. 472 kc/s operation. Single-tuned I.F.s and Oscillator Coils.

**T.41 SERIES** 25 mm. x 12 mm. x 20 mm. Ferrite cores 4 mm. 472 kc/s operation. Double-tuned 1st and 2nd I.F.s and Single-tuned 3rd I.F. complete with diode and by-pass capacitor.

These ranges are available to manufacturers in versions suitable for most of the popular types of Transistors. The Oscillator coils can be modified to enable specific tuning capacitors to be used provided that bulk quantities are required.

**OUR WINDING CAPACITY NOW EXCEEDS  
50,000 ITEMS PER WEEK**

On the most up-to-date and efficient machines backed by a skilled assembly labour force for all types of coils and assemblies.

**WEYRAD (ELECTRONICS) LIMITED, SCHOOL ST., WEYMOUTH, DORSET**

# 28watts, r.m.s. 40Hz to 40kHz ±3dB



## Viscount III Audio Suite complete £49

### PRICES SYSTEM 1

Viscount III RT101 amplifier £22.00 + 90p p&p  
 2 x Duo Type II speakers, £14.00 + £2 p&p  
 Garrard SP25 Mk. III with  
 MAG. cartridge, plinth  
 and cover

£23.00 + £1 p&p  
**Total £59.00**

Available complete for only **£52.00 + £2.50 p&p.**

### SYSTEM 2

As System 1, but with 2 x Duo Type III  
 speakers at pair £32.00 + £3 p&p  
**Available complete for £69 + £4 p&p**

### SYSTEM 3

Viscount III Amplifier RT100 £17.00 + 90p p&p  
 2 x Duo Type II speakers, pair £14.00 + £2 p&p  
 Garrard SP25 Mk. III with CER. diamond  
 cartridge, plinth and cover £21.00 + £1 p&p

**Total £52.00**

Available complete for only **£49.00 + £2.50 p&p**

### SPECIFICATION


14 watts per channel into 3 to 4 ohms. Total distortion @ 10W @ 1kHz 0.1%. P.U.1 150mV into 3 Meg. P.U.2 4mV @ 1kHz into 47K, equalised within ±1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power.) Tape out facilities; headphone socket, power out 250 mW per channel. *Tone controls and filter characteristics.* Bass: + 12 dB to - 17 dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control; treble + 12 dB to - 12 dB @ 15 kHz. Treble filter: 12 dB per octave. *Signal to noise ratio:* (all controls at max) RT101 - P.U.1. & radio - 65dB, P.U.2 - 58 dB. RT100 same as RT101 but P.U.2. 450 mV into 3 Meg. *Cross talk* better than -35dB on all inputs. *Overload characteristics* 26dB on all inputs.

Size 13 3/4" x 9" x 3 3/4".

### SPEAKERS Duo Type II

Size 17" x 10 1/2" x 6 1/2". Drive unit 13" x 8" with parasitic tweeter. Max. power 10 watts, 3 ohms. Teak veneer cabinet. **£14 pair + £2 p&p.**  
 Duo Type III Size 23 1/2" x 11 1/2" x 9 1/2". Drive unit 13 1/2" x 8 1/2" with H.F. speaker. Max. power 20 watts at 3 ohms. Freq range 20Hz to 20kHz. Teak veneer cabinet. **£32 pair + £3 p&p.**
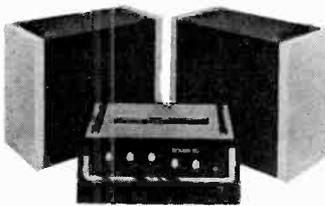
## SOUND 50 50 WATT AMPLIFIER & SPEAKER SYSTEM



*Output Power* 45 watts R.M.S. (Sine wave drive). *Frequency response:* -3 db points 30 Hz at 18 KHz. *Total distortion:* less than 2% at rated output. *Signal to noise ratio:* better than 60 db. *Speaker Impedance:* 3, 8 or 15 ohms. *Bass Control Range:* ±13 db at 60 Hz. *Treble Control Range:* ±12 db at 10 KHz. *Inputs:* 4 inputs at 5 mV into 470 K. Each pair of

inputs controlled by separate volume control. 2 inputs at 200 mV into 470K. To protect the output valves, the incorporated fail safe circuit will enable the amplifier to be used at half power. *SPEAKERS:* Size 20" x 20" x 10" incorporating 12" heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two tone colour scheme—Black and grey.

**COMPLETE SYSTEM £50**  
 Sound 50 amp and 2 speakers

Plus E4 P. & P.  
 or available separately  
 Amplifier: £28.50 plus £1.50 P. & P.  
 Speaker: £12.50 each plus £1.75 P. & P.



### ELEGANT SEVEN Mk 3 (350mW)

7 transistor fully-tunable M.W.-L.W. superbet portable Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.

MAINS POWER PACK KIT 75p extra  
 Price **£5.25** plus 50p P. & P.  
 Circuit 13p FREE WITH PARTS



### The DORSET (600 mW)

7 transistor fully-tunable M.W.-L.W. superbet portable —with baby alarm facility. Set of parts. The latest modulsised and pre-alignment techniques makes this simple to build. Sizes 12" x 8" x 3".

Price **£5.25** plus 50p P. & P.  
 Circuit 13p FREE WITH PARTS



## TOURIST MARK 3 ALL TRANSISTOR CAR RADIO

Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensures excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1 MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts. Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7" x 2" x 4 1/2" deep.

SET OF PARTS

Circuit diagram 13p Free with parts.  
 Speaker, baffle and fixing kit £1.25  
 extra plus 20p P. & P.  
 Speaker postage free when ordered with parts

**£6.30**

Plus 50p P. & P.

# TRANSISTORS

BRAND FULLY  
NEW GUARANTEED  
NEW LIST - NEW PRICES

Send today for your FREE copy  
of our new 1971 list

2N404	20p	BC109	12p	BYZ11	35p
2N696	15p	BC113	15p	BYZ12	30p
2N697	15p	BC114	25p	BYZ13	25p
2N706	10p	BC115	20p	BYZ15	£1.00
2N708A	12p	BC116	25p	GET880	37p
2N990	25p	BC116A	30p	MAT100	25p
2N1131	25p	BC118	25p	MAT101	30p
2N1132	25p	BC119	35p	MAT120	25p
2N1302	20p	BC137	25p	MAT121	30p
2N1303	20p	BC135	20p	MJ2801	£1.37
2N1304	25p	BC136	22p	MJ2901	
2N1305	25p	BC137	25p		£2.25
2N1306	25p	BC138	25p	MJE370	97p
2N1307	25p	BC147	17p	MJE520	87p
2N1308	25p	BC148	12p	MJE2655	
2N1309	25p	BC149	20p		£1.37
2N1613	22p	BC154	37p	MJE3055	
2N1711	25p	BC157	20p		87p
2N2147	75p	BC158	17p	MPF102	42p
2N2190	65p	BC159	20p	MPF103	35p
2N2218	20p	BC160C	30p	MPF104	37p
2N2219	20p	BC177	25p	MPF105	40p
2N2222	20p	BC178	25p	NKT217	40p
2N2222A	25p	BC179	27p	NKT277	20p
2N2369	20p	BC182L	12p	NKT403	75p
2N2484	35p	BC183L	12p	NKT404	62p
2N2486	50p	BC184L	15p	OA5	20p
2N2904	20p	BC212	12p	OA9	10p
2N2904A	25p	BCY30	25p	OA10	25p
2N2905	25p	BCY31	30p	OA47	10p
2N2906	20p	BCY32	50p	OA70	10p
2N2906A	25p	BCY39	25p	OA79	10p
2N2907	23p	BCY34	30p	OA81	10p
2N2926	10p	BCY38	40p	OA85	12p
2N3011	25p	BCY39	85p	OA90	10p
2N3053	20p	BCY40	50p	OA91	7p
2N3054	50p	BCY58	25p	OA95	7p
2N3055	75p	BCY59	25p	OA200	7p
2N3525	£1.10	BCY70	15p	OA202	10p
2N3702	10p	BCY72	15p	OC16	50p
2N3703	10p	BCY78	30p	OC20	97p
2N3704	15p	BCY79	30p	OC22	50p
2N3705	15p	BCZ10	35p	OC23	60p
2N3707	15p	BCZ11	45p	OC24	60p
2N3709	10p	BD112	50p	OC25	37p
2N3710	10p	BD121	65p	OC26	25p
2N3819	35p	BD123	80p	OC28	60p
2N3820	60p	BD124	75p	OC29	60p
2N4058	15p	BD125	50p	OC35	50p
2N4061	15p	BD131	75p	OC36	60p
2N5457	35p	BD132	85p	OC41	25p
2N5458	37p	BD153	62p	OC42	30p
2N5459	50p	BD156	57p	OC43	40p
28301	20p	BDY10	15p	OC44	40p
28302	50p	BDY10E1	25p	OC45	15p
28303	60p	BDY11	£1.62	OC70	12p
28304	75p	BDY17		OC71	15p
40250	50p		£1.50	OC72	25p
40361	50p	BDY18		OC73	30p
40362	55p		£1.75	OC74	30p
4AAY30	10p	BDY19		OC75	25p
4AAY42	15p		£1.97	OC76	25p
4AAZ13	12p	BDY61		OC77	40p
4AAZ17	10p		£1.25	OC81	25p
AC126	37p	BDY62		OC82	25p
AC126	25p	BF115	25p	OC83	25p
AC127	25p	BF115	25p	OC84	25p
AC128	25p	BF152	30p	OC139	25p
AC176	25p	BF154	40p	OC140	37p
AC187	30p	BF158	30p	OC141	62p
AC188	30p	BF159	60p	OC170	25p
AC197	30p	BF167	25p	OC171	30p
AC198	25p	BF170	35p	OC200	40p
AC199	25p	BF173	30p	OC201	70p
AC200	20p	BF177	40p	OC202	85p
AC201	20p	BF178	25p	OC203	40p
AC202	10p	BF179	40p	OC204	40p
AC203	10p	BF180	35p	OC205	75p
AC204	15p	BF181	35p	OC206	90p
AD140	50p	BF182	30p	OC207	90p
AD149	50p	BF184	20p	OC271	97p
AD161	37p	BF185	20p	ORP12	50p
AD162	37p	BF194	17p	ORP60	40p
AF114	25p	BF195	15p	ORP61	42p
AF115	25p	BF196	15p	TIP29A	50p
AF116	25p	BF197	15p	TIP29A	60p
AF117	25p	BF200	37p	TIP31A	60p
AF118	62p	BF274	35p	TIP32A	75p
AF124	25p	BFX13	25p	TIP33A	£1.00
AF125	20p	BFX29	25p	TIP34A	
AF126	17p	BFX30	25p		£2.00
AF127	17p	BFX37	32p	TIS43	40p
AF139	30p	BFX84	25p	TIS60	22p
AF178	47p	BFX85	35p	TIS61	25p
AF179	65p	BFX86	25p	TIS62	27p
AF180	52p	BFX87	25p	ZTX107	15p
AF181	42p	BFX88	20p	ZTX108	15p
AF186	40p	BFY18	30p	ZTX109	15p
AF239	40p	BFY50	22p	ZTX301	15p
ASV26	25p	BFY51	20p	ZTX302	20p
ASV27	32p	BFY52	22p	ZTX303	20p
ASV28	25p	BFY53	17p	ZTX304	25p
ASV29	30p	BFY90	65p	ZTX500	20p
ASV67	47p	BSX20	17p	ZTX501	25p
ASZ21	42p	BSX21	20p	ZTX502	25p
BA115	7p	BSX76	15p	ZTX603	20p
BA164	10p	BSY95	15p	ZTX504	40p
BAX13	6p	BSY95A	15p	ZTX531	30p
BAX16	7p	BSY100	15p	Discounts	
BAX31	10p	BY126	10p	10% 2+	
BAX38	17p	BY127	20p	15% 25+	
BC107	12p	BY182	85p	20% 100+	
BC108	12p	BYZ10	40p	Any one type	

# HENRY'S LOW COST INTEGRATED CIRCUITS

WE OFFER FROM STOCK AN EXCLUSIVE RANGE OF  
BRAND NEW CERAMIC FULL SPECIFICATION  
LOW COST TTL 7400 INTEGRATED CIRCUITS

Part	Description	Price and Qty. Prices
		1-24 25-99 100 250+ 500+ 1000
7400	Quadruple 2-input NAND Gate	23p 20p 15p 13p
7401	Quadruple 2-input Positive Nand Gate (with open collector output)	23p 20p 15p 13p
7402	Quadruple 2-input Positive Nor Gates	23p 20p 15p 13p
7403	Quadruple 2-input Positive Nand Gates (with open collector output)	23p 20p 15p 13p
7404	Hex Inverter	23p 20p 15p 13p
7405	Hex Inverter with open collector	23p 20p 15p 13p
7410	Triple 3-input Positive Nand Gates	23p 20p 15p 13p
7413	Dual 4-input Schmitt Trigger	35p 32p 29p 25p
7420	Dual 4-input Positive Nand Gates	23p 20p 15p 13p
7430	8-input Positive Nand Gates	23p 20p 15p 13p
7440	Dual 4-input Positive Nand Buffers	23p 20p 15p 13p
7441	BCD to decimal mixer driver	87p 77p 67p 60p
7442	BCD to decimal decoder (4-10 lines, 1 of 10)	87p 77p 67p 60p
7447	BCD-Seven-Segment Decoder/Drivers (15-V outputs)	£1.40 £1.30 £1.20 £1.05
7450	Expandable dual 2-input And-Or-Invert	23p 20p 15p 13p
7451	Dual 2-wide 2-input And-Or-Invert Gates	23p 20p 15p 13p
7453	Quad 2-input Expandable And-Or-Invert	23p 20p 15p 13p
7475	4-wide 2-input And-Or-Invert Gates	23p 20p 15p 13p
7460	Dual 4-input Expander	23p 20p 15p 13p
7470	Single-phase J-K Flip-Flop	35p 32p 29p 25p
7472	Master-slave J-K Flip-Flop	35p 32p 29p 25p
7473	Dual Master-slave J-K Flip-Flop	43p 40p 37p 33p
7474	Dual O type Flip-Flop	43p 40p 37p 33p
7475	Quad latch	47p 45p 43p 40p
7476	Dual J-K with pre-set and clear	47p 45p 43p 40p
7480	Gated Full Adders	87p 77p 67p 60p
7481	16-bit read/write memory	£1.35 £1.25 £1.15 £1.00
7482	2-bit Binary Full Adders	£1.30 £1.20 £1.00 85p
7483	Quad Full Adder	87p 77p 67p 60p
7486	Quad 2-input Exclusive Or Gates	87p 77p 67p 60p
7490	BCD decade counter	87p 77p 67p 60p
7491	8-bit Shift Registers	£1.21 £1.00 87p 60p
7492	Divide-by-Twelve Counters	87p 77p 67p 60p
7493	4-bit Binary Counters	87p 77p 67p 60p
7494	Dual entry 4-bit shift register	87p 77p 67p 60p
7495	4-bit up-down Shift Register	87p 77p 67p 60p
7496	5-bit Parallel in Parallel out Shift Register	87p 77p 67p 60p
74100	8-bit Bistable Latches	£1.75 £1.65 £1.55 £1.35
74118	Hex Set-Reset Latches	£1.30 £1.20 £1.00 85p
74121	Monostable Multivibrators	87p 77p 67p 60p
74141	BCD-to-Decimal Decoder/Driver	87p 77p 67p 60p
74145	BCD-to-Decimal Decoder/Drivers	£1.80 £1.70 £1.60 £1.50
74151	8-bit Data Selectors (with Strobe)	£1.40 £1.30 £1.20 £1.05
74153	Dual 4-Line-to-1-Line Data Selectors/Multiplexers	£1.40 £1.30 £1.20 £1.05
74191	Binary Counter reversible	£3.50 £3.25 £3.00 £2.50

Devices may be mixed to qualify for quantity price.  
Data available for above series in booklet form, price 10p. (Ref. No. 30).  
Larger quantity prices Extn. 4. Dual In-line 14 Pin Sockets 30p each; 16 Pin 35p each.

# TRIACS

P.I. Cur.				P.I. Cur.			
Type	Volts	rent	1-49	50+	100+	500+	1000+
SC35A	100	3A	90p	75p	65p	60p	50p
SC35B	200	3A	95p	80p	70p	65p	55p
SC35D	400	3A	£1.00	85p	75p	70p	60p
SC40A	100	6A	£1.00	85p	75p	70p	60p
SC40B	200	6A	£1.20	£1.00	85p	80p	70p
SC40D	400	6A	£1.25	£1.10	£1.00	90p	80p
SC45A	100	10A	£1.25	£1.10	£1.00	90p	80p
SC45B	200	10A	£1.35	£1.20	£1.10	£1.00	90p

# SILICON RECTIFIERS

1 AMP MINIATURE WIRE ENDED PLASTIC							
Type	P.I.V.	1-49	50+	100+	500+	1000+	
IN4001	50	8p	7p	6p	5p	4p	
IN4002	100	9p	8p	7p	5p	4p	
IN4003	200	10p	9p	7p	6p	5p	
IN4004	400	10p	9p	8p	7p	6p	
IN4005	600	12p	10p	9p	7p	6p	
IN4006	800	15p	14p	12p	11p	9p	
IN4007	1000	20p	16p	13p	12p	10p	

# MINIATURE POTTED BRIDGE RECTIFIERS

(Silicon) Size 1 in. x 1 in. x 1 in.							
Type	P.I.V.	rent	1-49	50+	100+	500+	
1002	100	2 amps	60p	55p	50p	45p	
2002	200	2 amps	70p	65p	60p	55p	
4002	400	2 amps	80p	75p	70p	65p	
6002	600	2 amps	90p	80p	75p	70p	
1004	100	4 amps	70p	60p	55p	50p	
2004	200	4 amps	75p	70p	65p	60p	
4004	400	4 amps	80p	75p	70p	65p	
6004	600	4 amps	85p	75p	70p	65p	
1008	100	8 amps	75p	70p	65p	60p	
2006	200	6 amps	80p	75p	70p	65p	
4006	400	6 amps	£1.10	£1.00	90p	80p	
6006	600	6 amps	£1.25	£1.10	£1.00	90p	

# INTEGRATED CIRCUITS

MFC4000P		MC1304	
£1.12	£2.75	£2.75	£2.75
IC.12	MC74P	741C (T05)	85p
PA246	741C (DIL)	85p	85p
TA246	709C (T05)	65p	65p
TAD110	709C (DIL)	65p	65p
MC1303	Toshiba	£2.60	
UL900	20w Amp	£4.47	
UL914	Toshiba		
UL923	Pre Amp	£1.50	
LA709C		65p	

# POWER RECTIFIERS

Stud Mounting 6 amp Range			
Type	P.I.V.	1-49	50+
BYZ10	800	40p	35p
BYZ11	600	35p	30p
BYZ12	400	30p	25p
BYZ13	200	25p	20p

# SEMI-CONDUCTORS

LOOK AT THESE PRICES

# Stock clearance

- STC GH.206**  
Data console complete with tally reader BRP Punch **£500**
- Creed**  
75 Page Printer 5H..... **£25**  
25 Punch. 5.7.8H..... **£60**  
Transmitter. 5H..... **£20**  
3000 Punch..... **£49-50**  
Punch Verify Set. 8H..... **£100**  
80 by 80 Power Supplies..... **£9-50**  
25 by 75 Spares @ 50% off list.
- Welmec**  
Punches & Readers 7 & 8 Hole..... From **£55**
- Bima**  
Paper Tape Prep Machine 5H with hard copy..... **£120**
- Westrex**  
BRPE 11. 5 & 8 Hole..... **£175**
- Elliott**  
Paper Tape Readers Optical. 5.7.8H..... **£195**  
803B Computers Complete..... From **£900**  
B41. Card read Station..... From **£295**  
B46. Card Reader & Amps..... From **£149-50**  
Data Discs Plus 1 Disc..... **£49-50**  
B46-B41. Reader Spares. 60% off list.
- ICE**  
5-8 Hole Tape Parity & Block length checking device complete with optic Read..... **£45**
- Core Stores**  
Mullard, Plessey, ICL 1300 Complete..... From **£60**
- Ampex Tape Transports With Control**  
FR.300 1"..... From **£75** each  
FR.30C 1/2"..... Spares available at  
TM2 1"..... 60% off list  
TM4 1/2".....  
Potter Tape Transports 906/11/2 1"..... **£49-50**  
Spares at 50% off list.  
RCA. 1/2" Transport Only..... **£25**  
DR7C0 1004 MTV Complete..... **£750**  
1004 MTV Complete..... **£1,250**
- Analex**  
Line Printers. Printer Only..... From **£550**  
Line Printers. With EMI Buffered Control..... **£500**  
Spares Available at 60% off list.
- Fridon**  
Paper Tape To Card Converter Only..... **£50**  
Model SPD Writers BCD Coded..... **£480**  
Rack Mounted Punch Verifier Sets With Fast Entry, Keyboard ISO Coded..... **£220**  
Fridon Punches & Readers..... From **£49-50**  
Flexowriters 8 Hole..... From **£75**
- NCR**  
400/208 Machine..... From **£3,500**
- ICT/ICL**  
29 80 col card Punch..... From **£149**  
129 Verifier..... From **£149**  
103 Verifier..... **£89-50**  
Keyboards Alpha & Numeric..... From **£25**  
665 Line Printers..... **£550**  
34 Punch Verifiers..... **£175**  
Hand Punches..... **£95**
- IBM**  
029 Card Punches..... **£980**  
026..... **£1,095**  
024..... **£650**  
7330 Mag Transports (Read Only)..... **£600**  
151 Card Verifiers..... **£49-50**  
1401/C3 Central Processor..... **£2,200**
- English Electric. KDF8**  
1040 Line Printer..... **£300**  
Card Reader..... **£200**

**RING 01-278 5571 NOW!**

Computer Sales & Services (Equipment) Ltd  
49-53 Pancras Road London NW1  
Telephone 01-278 5571  
Telex 267307

WW-079 FOR FURTHER DETAILS

# HENRY'S RADIO LTD.



**COMPLETELY NEW  
10TH EDITION  
CATALOGUE!**

**350** PAGES

Fully detailed and illustrated covering every aspect of Electronics plus data and information.

**10,000  
STOCK LINES**

New stock lines—all at special prices plus full guarantees.

**PLUS**

FIVE 10p VOUCHERS for use with retail and mail order purchases.

**FREE**

Catalogue given FREE to industry or any Organisation, including Schools, Colleges etc.  
Apply on official heading to Henry's Radio Ltd., 303 Edgware Road, London, W.2.

**CATALOGUE PRICE**

**55p** Post Paid (or 40p for callers)

Callers welcome at 303, 309, 354 and 356 Edgware Road, London, W.2. Tel. 01-723 1008/9.

**MORE OF EVERYTHING AT LOW PRICES—ALWAYS AT HENRY'S**

To Henry's Radio Ltd., (Dept W.W.)  
3 Albemarle Way,  
London, E.C.1.

USE BLOCK CAPITALS. CUT OUT AND SEND WITH CHEQUE or P.O. (No cash please)

Please send ..... copies of your 10th Edition Catalogue at 55p each. Post Paid. I enclose Cheque/P.O. for .....

Name .....

Address .....

WW

Allow 7-10 days from date of ordering



**RHODE & SCHWARZ POWER SIGNAL GENERATOR Type SMLR (BN41001)**

100 KHz-30 MHz in 5 ranges.  $\pm 1\%$ . O/P 1.7 w. MAX O/P volts 0-10 into 60 ohms and 1 micro-volt-3 v. A.M. Modulation to 90%. This is a high quality laboratory instrument currently priced at £583. ELECTRONIC BROKERS PRICE £300. O/W Calibration certificate.




**DYNAMCO 2010 DIGITAL VOLTMETER (EI MODULE)**

Fully overhauled, Calibrated (Certified) and Guaranteed.

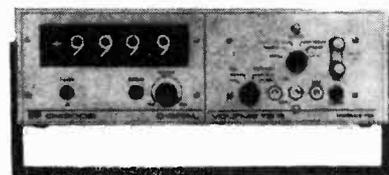**Specification:**

Scale: 109999. D.C. Accuracy: 0.001%  
F.S.D. Range: 10 micro V-1 kV; I/P Z greater than 25,000 Mohm; C.M.R. D.C. 160 dB. 50 Hz 130 dB O/P. Parallel B.C.D. Inductive potentiometric system for excellent stability. Price: £850 (new price over £1,600).



**DIGITAL VOLTMETER DYNAMCO 2006**

Scale 9999. D.C. range. 10 micro-volt-1 kV. I/P. Z. greater than 10,000 Mohms. B.C.D. Parallel O/P (isolated). Supplied with D.2 Module. Overhauled Calibration certificate. To maker's specification. New price £765. Our price £400. Carriage extra.


**7-TRACK DIGITAL MAGNETIC TAPE STORAGE DECK (Ref. 13)**

These machines, originally ex-computer, are multi-track recording units, ideal for data storage. Record and Replay heads encased in one common unit. Low resistance heads. Frequency response approximately 0 Kc/s. to 50 Kc/s. Bit density 557 b.p.i.  $\frac{1}{2}$  in. 101 in. spools 230 v. to 380 v. A.C. Capstan Motor speed 1,500 r.p.m. 48 v. D.C. Rewind motors. Finished in brush aluminium and matt-black. Size 27 in.  $\times$  26 in.  $\times$  8 in. Weight 90 lb. Price £65. Carriage extra.



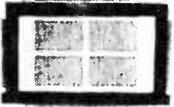**MEMORY PLANES (Ref. C4)**

Ferrite core memory planes with wired Ferrite cores. Used for building your own computer or as an interesting exhibit in the demonstration of a computer. Mounted on plastic material, frame 8  $\times$  8 in. Consisting of matrices 40  $\times$  25  $\times$  4 cores each one individually addressable and divided into 2 halves with independent sense and inhibit wires. £8.65. P. & P. inclusive.




**BRAND NEW COMPUTER TAPES AND EMPTY SPOOLS**

Made by well known manufacturers  
 $\frac{1}{2}$  in. certified 2,400 ft. 800 h.p. .... £8 50  
 $\frac{1}{2}$  in. 2,400 ft. .... £8 50  
 $\frac{1}{2}$  in. Highest grade 2,400 ft. .... £3 00  
 $\frac{1}{2}$  in. 10  $\frac{1}{2}$  in. dia. spool and cassette ..... £1 50  
 $\frac{1}{2}$  in. 8  $\frac{1}{2}$  in. dia. spool and cassette ..... £1 50  
 $\frac{1}{2}$  in. metal 10  $\frac{1}{2}$  in. dia. spool and cassette ..... £2 50  
 $\frac{1}{2}$  in. N.A.B. centres 10  $\frac{1}{2}$  in. spool only ..... £1 00

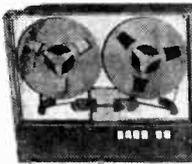**HONEYWELL MODEL 6200 INCREMENTAL DIGITAL RECORDER**

Records digital (binary) data on 7 track  $\frac{1}{2}$  in. tape in steps of 0.005 in. with a packing density of 200 bits/inch. Almost new and in excellent condition. This recorder offers excellent value for many applications involving data logging. One only available. Price: £750.



TEXAS BALL BONDER. Overhauled. £250.

**50 MHz. 8 DIGIT FREQUENCY COUNTER SYSTRON-DONNER Model 1037**


D.C. I/P 0-50 MHz. A.C. I/P 10-50 MHz. Gate time 1 micro-second -10 seconds in Decade steps. Accuracy  $\pm 1$  count  $\pm$  time base accuracy. Reads in KHz or MHz with positioned decimal point. Sensitivity 100 Mc. r.m.s. B.C.D. O/P. PRINT COMMAND. OVER-LOAD PROTECTION. DIMENSIONS: H. 5  $\frac{1}{2}$  in., W. 17  $\frac{1}{2}$  in., D. 17  $\frac{1}{2}$  in. Wt. 42 lbs. Mains I/P. This instrument has been overhauled and calibrated and is offered in excellent condition. £350. Carriage extra.

**EYELET BONDER PLANNER B801**

V.G. condition. O/W stand. Overhauled. £750.

**5 KV IONISATION TESTER AIRMEC 732**

Non-destructive insulation testing. Audible indication of ionisation currents. Variable voltage from 250-5 kV. High impedance source. Mains I/P. £35.

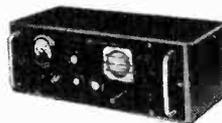


**WELMEC 5-8 CHANNEL TAPE PUNCHES AND READERS**

Magnetically driven up to speed of 17 codes/second. Ideally suitable for data logging applications. NO continuously running motor. NO power consumption unless actually punching. Ideal producing tape from keyboards or office machines. Free standing units in attractive cases.

PUNCH contains transport and power solenoids 240V AC (pulsed operation required). Punch magnets. Reverse transport magnet and Tape marker Magnet 110V DC. PARITY unit for checking parity or coincidence. Large checking BOX to prevent jamming. High Chad Bridge to eliminate punch blocking. OUR PRICE £75 each. Carriage extra.

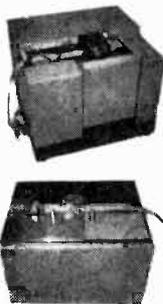READER. Transport and Power solenoids 240V DC (pulsed operation). All units completely refurbished and available EX-STOCK. Supplied with circuit diagrams and 3 months warranty. OUR PRICE £75 each. Carriage extra.



**FACSIMILE RECORDERS**

D49 K 18 in. Chart Recorder. Helix speed: 60, 90, 120 rev./min. Transmission speed:  $\frac{1}{2}$  in.; 15/16 in.;  $\frac{1}{4}$  in. per min. Scanning rate 96 lines/in. Ref. C3..... Price £350. Completely overhauled plus carriage.

**X Y PLOTTERS**

We are now able to offer the following Recorders in an overhauled and tested condition:

**1. MOSELEY AUTOGRAF MODEL 2A**

Table size: 11 in.  $\times$  17 in. Dimensions: W. 24 in., H. 9 in., D. 16 in. Wt. 55 lbs. Power I/P: 115 v. 1 phase 100 w. Signal I/P: X Axis 0-7  $\frac{1}{2}$ , 15, 75, 150, 750 mV; 0-1  $\frac{1}{2}$ , 7  $\frac{1}{2}$ , 15, 75, 150 v. Y Axis 0-5, 10, 50, 100, 500 mV; 0-1, 5, 10, 50, 100 v. Sensitivity not less than 200 k ohms/V. Accuracy: 0.25%. FS on all ranges. Response speeds: 1 sec. for full scale. Supplied complete with copy of handbook. £310 Carriage extra.

**2. HOUSTON INSTRUMENTS MODEL HR 934**

Table size: 8  $\frac{1}{2}$  in.  $\times$  10  $\frac{1}{2}$  in. Dimensions: W. 14 in., H. 8 in., D. 16 in., Wt. 30 lb. Power I/P: 115 v. 1 phase. Signal I/P: "X" and "Y" Axes. 0-7, 7-8, 10, 19, 68 mV and 0-5 v. Switched Attenuators on both Axes. Response speeds: 2 sec. for full scale. £195. Carriage extra.

**DIGITAL INDICATORS KGM Type M3**

A neat compact indicator providing selective display 0-9. Fig. height 18 mm. panel mounting. 6 mm. tubular nidget flange lamps. Supplied with 28 v. bulbs. Finished matt black anodized. W. 1 in., H. 2 in. Wt. 4 ozs. Price £3.25. P. & p. Free.



**TRANSISTORISED TIMER Ekco M5220**

An extremely versatile timer for use with high stability pulse counting systems. Less power supply. £45. Carriage extra.

**TRANSISTORISED SCALER M5200**

£45. Carriage extra. This unit can be used to power the Timer M5220.



**SOLAROSC OSCILLATOR CO546**

25Hz-500K Hz. Attenuator and O/P meter. Very good condition. £55 (carriage extra).

# ELECTRONIC

**SIGNAL GENERATOR "X" BAND**

SANDERS MODEL CT 460 (SG 480) and CT 478 (SG 478). Specifications: CT 480 8-11.5 KMHz; CT 478 1.3-4.2 KMHz. O/P of 1mW from 8-0-11.0 KMHz (CT 480) and 1.5-4.0 KMHz (CT 478). These high grade generators comprise a klystron oscillator in a co-axial cavity fed from a stable power source. Provision for application of square wave or pulse modulation internal or external sources. Attenuator calibrated from 0-100 db below 1 mW. I/P 110-250 v. 50-500 Hz. 200 w. Rack mounting. W. 19 in., H. 14 in., D. 15 in. Wt. 74 lb. Supplied complete with copy of handbook. Tested before despatch. £275. Carriage extra.



**DEVIATION METER Marconi TF 928**

20-100 MHz. Can be used to 500 MHz. Measurement of deviation up to 400 KHz. Crystal Standard. Used in setting up deviation in VHF Wide Band Multi Channel FM Systems and Radar. I/P 100-150 v. and 200-250 v. 40-100 Hz 120 w. H. 14". W. 20  $\frac{1}{2}$ ". D. 17" Wt. 70 lb. £95.00. Carriage extra.



**NUMICATORS**

End Reading 0-9 Display (16 mm Fig. Ht.)	Quantity	Price Each (less Base)	Bases
GR10M (Clear)	1-3	£1.40	Each
GR10M (Amber filter)	4-10	£1.35	Each
	11-25	£1.30	Each
	26-100	£1.20	Each
Side Reading (14 mm Fig. Ht.) 0-9 display			Less Bases
XN3/FA 38 m/m lead (Amber filter)			£1.15
XN3/F 38 m/m lead (Red ..)	1-3		£1.10
XN3A/F 6 m/m lead (Red ..)	4-10		£1.05
XN3A 6 m/m lead (Clear ..)	11-25		£1.05
XN11/F 38 m/m lead (Red ..)	26-100		£0.95
XN23/FA 38 m/m lead (Amber ..)			Post Free.

**SPECIAL DISPLAYS**

XN9 38 m/m leads (Clear filter)	Displays Fig. "1"
NX10/C 6 m/m leads (Clear filter)	Displays "+, - and 0"
NX22 38 m/m leads (Clear filter)	Displays "Vx, A, Q VmV"

**RCA U.H.F. SIGNAL GENERATOR Type 710A**

Frequency range 370-560 MHz. Modulation facility. I/P 117 v. 50/60 Hz 50w. Overhauled and supplied complete with auto transformer for 230/250 v. I/P. £85 (carriage extra).

**VIBRON ELECTROMETER MODEL 33B**

An exceptionally stable laboratory instrument for the measurement of very small d.c. voltages and currents derived from a high impedance source. The Vibron Electrometer has input ranges of 10 mV, 30 mV, 100 mV, 300 mV and 1 V and the output is 1 mA full scale on all ranges. £75 (carriage extra).



**CURRENT & RESISTANCE MEASURING UNIT A33B**

To extend the range of the ELECTROMETER to measure very small currents and high insulation resistances. £15.

**WIDE BAND DIFFERENTIAL DC AMPLIFIER**

Astrolata Model 885-235. High performance, solid state, fast settling time, low drift and noise. Wide bandwidth and high reliability uses F.E.T.'s. Spec.: Grain 3 to 3000. Grain accuracy  $\pm 0.1\%$ . Stability  $\pm 0.01\%$  for 40 hours  $\pm 0.05\%$  for 1000 hours. Linearity  $\pm 0.02\%$  of FS O/P from DC to 1 KHz I/P Z greater than 100 Mohms. I/P capacitance less than 500 picofarads. Full spec. on request. These amplifiers are BRAND NEW. Offered at fraction of new price. £595.

IF YOU CANNOT FIND THE INSTRUMENT YOU WANT IN



### KENT CHROMALOG I DIGITAL INTEGRATOR

For use with gas chromatography apparatus or anything with an output expressed as a varying direct voltage. Automatic print out and 0-10mA O/P to drive recorder. Offered in excellent condition. 3 months warranty and copy of handbook. **£325.** Carriage extra.

### DECADE VOLTAGE AND CURRENT GENERATOR

Ekco Type 1482A. Provides accurate test voltages and currents which can be varied by small increments 0.1 v. in steps of 0.0001 v. 0-10 v. in steps of 0.001 v. Current O/P 1 v. range, 10<sup>-5</sup> to 10<sup>-13</sup> amps on 10 v. Range 10<sup>-4</sup>-10<sup>-12</sup> amps. Mains I/P. 19 in. Rack Mounting C/W Manual. **£45.**

### GRESHAM INSULATION FLASH-TESTER Mk 6

0.5-2.5 kV. Mains I/P. Overhauled **£35.** Carriage extra.

### R.C. POWER OSCILLATOR (Associated Electronic Eng. A1302)

Frequency range: 20 Hz to 200 KHz, in 4 ranges. Output power: 0-250v., 4.5 watts r.m.s. Output impedances: 15 ohms, 1,000 ohms, 4,000 ohms; 600 ohms attenuator adjustable. Loaded 600 ohms, 0-5 ohms. Output termination: High impedance, earthed; low impedance, isolated. Output level: Output level control 0-10 div. Meter ranges: Switched 10 v., 50 v., 250 v. Input voltage: 200-250 v. A.C. 50 Hz. Output terminal switch: Switchable to High or Low impedance output. O/H. Very good condition. **£95.** Carriage extra.

### NUCLEONIC INSTRUMENTS

High Accuracy Metal Wall Gauge Ekco Type N563B. Portable, transistorised gamma back scatter gauge up to 18 mm. in 2 ranges. Indicator only. NO probe. **£15.** Carriage extra. Field Rate Meter Ekco Type N045A. 0-1,000 counts/sec. in 5 ranges. Portable transistorised. C/W Dipping Probe N675A for Beta counting in liquids. C/W Manual. **£105.** Batemeter ONLY **£35.** Amplifier Logarithmic D.C. Part of Monitor Gamma Reactor. Type N638A. **£25.** Carriage extra.

### BRAND NEW CAPACITOR REVERSIBLE SINGLE PHASE PARVALUX MOTORS

230/250 v. 50 Hz 2,800 r.p.m. 1/30 h.p. Cont. rated.  $\frac{1}{8}$  in. shaft dia. x 34 in. long. Foot mounting. Weight 6 lb. **£3.50** post free.

**BRAND NEW NIMTEC AMPLIFIER 151** ..... **£30**  
Timing Unit 219. .... **£25**  
**DISCRIMINATOR 95/2127-1/6** ..... **£10**

TEKTRONIX 517A. Single Beam. C/W Power Supply Unit and type B170-A170 ohm. attenuator. Rise Time 7nsec. Sensitivity Y Amp 0.05 v./cm. Rime Base 10-500 micro-sec./cm. and 1-20 micro-sec./cm. in 11 ranges. C/W copy of handbook. **£295.** Carriage extra.

## POWER SUPPLIES



### DUAL STABILISED VARIABLE DC POWER SUPPLY ADVANCE PP3

0-30 v. in 3 ranges at 1 amp. Voltmeter and ammeter. Overload protection. Mains I/P. Overhauled V.G. condition. **£55.** Carriage extra.

We specialise in all kinds of POWER SUPPLIES. Current stock includes the following Modular units. All have mains I/P.

Volts	Current	Make	Type	Price
6	1A	Roband	T.98	£10 00
6	2	Roband	T.98	£12 00
12	6			£15 00
15	6	Advance	P.M7	£15 00
17	6	Farnell	88U 17/6	£18 00
28	1	Roband	T109	£25 00
32	2	APT	10459/14	£25 00
150	200mA	Farnell	8PU 150	£14 00
50/80	1A	Roband		£22 00
74-9U	10A	I.E.		£19 50
74-9U	10A	Farnell		£25 00

### MULTI OUTPUT UNITS AND SPECIALS



O/P V	A	I/P V	Make	Price
335	unstablised			
0-3 A.C.	2A (400Hz)	115 v. 400Hz	Farnell (PU.335)	£10 00
-12-0+12 +24		240	Livingstone (LM050)	£9 50
0-10 v. Unstablised Variable	2A	240		£18 00
160-300 6-3 v. A.C. Variable (Voltmeter and Ammeter)	150mA 3A	240	I.E.	£35 00
30 A.C. 400 Hz adjustable	300mA	240		£36 00
175-260 Adjustable (Metered)	80mA	240	Smiths	£30 00
3-15-0-3-15 A.C. 3A				
Universal Labpack HT & LT Supply Unstablised adjustable			Radford	£20 00

### EX-COMPUTER HIGHLY STABILISED TRANSISTORISED LOW VOLTAGE POWER SUPPLIES

These modular units incorporate overload protection on both INPUT and OUTPUT. LOAD regulation of 1% or better. Low Ripple and a fast response time. All units checked and O/H before despatch. 1/P VOLTAGE 120-130 v. 50Hz available in the following types:

6 volt.....	8 amp.....	£12 00
6 volt.....	12 amp.....	£17 00
6 volt.....	16 amp.....	£20 00
12 volt.....	4 amp.....	£20 00
12 volt.....	12 amp.....	£22 00
12 volt.....	20 amp.....	£24 00
12 volt.....	28 amp.....	£25 00
20 volt.....	6 amp.....	£18 00
20 volt.....	15 amp.....	£24 00
30 volt.....	7 amp.....	£19 00
48 volt.....	6 amp.....	£20 00

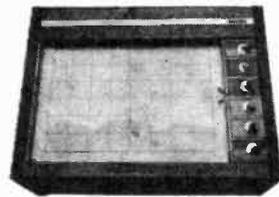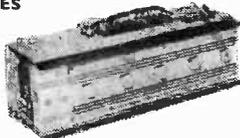These units are in great demand. ORDER NOW while stocks last.




### ELECTRONIC ASSOCIATES VARIPLOTTER 1100E

X-Y plotter, suitable for recording analogue information. Table size 15 in. x 10 in.; slow speed 20 in./sec.; I/P sensitivity for F.S.D. 0.05-30 v. in 9 ranges. Basic I/P sensitivity. Arm 10 m.v./in. Pen 1 v./in. Fully overhauled, tested, guaranteed and in new condition. Price: **£350.**

## VIBRATION EQUIPMENT
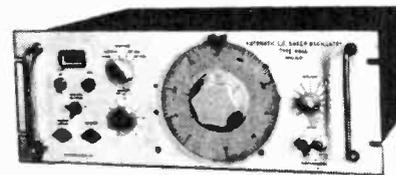
### 1. AUTOMATIC L.F. SWEEP OSCILLATOR PYE-LING ACO 1 (DAWES 44D)

An automatic unit providing motorised sweep facilities and automatic changeover from displacement to acceleration characteristic. Applications Resonance Search and Endurance testing.



5 Hz-5 KHz 21 sweep speeds from 0.1-10 octaves/minute. Variable O/P up to 10 v. r.m.s. Mains I/P. Excellent condition. **£95.** Carriage extra.

### 2. POWER OSCILLATOR 5VA by PYE-LING

5 Hz-30 KHz. Overhauled. **£49.** Carriage extra.

### 3. CATHODE FOLLOWER. GOODMAN'S E504

7 channel. Very good condition. **£45.** Carriage extra.

### 4. PHASE SHIFTER MODEL E556 (GOODMANS)

19 in. Rack Mtg. Mains I/P. Very good condition. **£56.** Carriage extra.

### AVO TRANSISTOR ANALYSER CT 446

A portable direct-reading instrument capable of giving accurate transistor measurements in the grounded emitter configuration. Battery power unit 1.5V to 10.5V in 5 steps. Base current 0.1 mA. 1.40 mA. Collector current 250 mA. Size: 151 x 94 x 5 ins. Weight with batteries: 13 lbs. Price **£42.50.** Carriage extra.



### KLYSTRON POWER SUPPLY AIRMEC 698B


Reflector voltages 1450-1650 adjustable. Grid 1430-1530v. Heater 1420-1436 v. Metered. Rebuilt. 3-month warranty. **£65.** Carriage extra.

# BROKERS

49-53 PANCRAS ROAD, LONDON, N.W.1.  
Tel: 01-837 7781/2. Cables: SELELECTRO  
Telex: 267307 (Open Mon-Fri. 9 a.m.-6 p.m.)

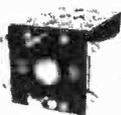
### FINE COSINE POTENTIOMETER 47K

precision component by Pye. Model 2002. manufactured to rigid Ministry specification. The assembly consists of three units mounted on one frame. Each unit contains two sine wave cosine potentiometer sections, the dials being ganged together. Electrical connections, 2 end taps, slider and centre p. Mechanical I/P: 30 r.p.m. Max torque: 0.2 in. lb. Dimensions: W. 6 1/2 in. H. 5 in. 7 1/2 in. Wt. 7 1/2 lb. Ex equipment. Good condition. **£10 00** each. Carriage extra.



### LF SPECTRUM ANALYSER FENLOW S.A.2.

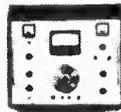0-3 Hz-1 KHz in 5 ranges. Bandwidth 0.06-37.5 MHz in 5 steps. **£350.**



### L.F. OSCILLATOR EDISWAX R666.

0-5 Hz-5 KHz in 4 ranges. O/H bargain at **£30.** Carriage extra.

### PORTABLE FREQUENCY METERS

TF1026/1. A direct reading absorption meter, employing a concentric line closed at one end and turned by variable capacitor at the other end of the line, giving a frequency range: 250 MHz-500 MHz, on an almost linear scale approx. 9 in. in length. Complete in polished wooden case. Price **£17.50.** Carriage extra.

### E.M.I. INSTRUMENT L.F. TAPE RECORDER

Portable equipment consisting of 3 units (Deck, Amplifier and P.S.U.) in transit cases. Four speeds using standard 1/2 in. tape. Exceptional value, two only available. Price **£75.**

### OSCILLOSCOPES

SOLARTRON STORAGE OSCILLOSCOPE QD 910 Double Beam. DC-1 MHz "Y" Sensitivity 10 mv./cm. to 30 v./cm. in 8 ranges. 5 in. dia. Memotron CRT. Time Base 1 micro-sec./cm. to 10 sec./cm. in 10 ranges. Overhauled in V.G. condition. C/W trolley and copy of handbook. **£180.**

CAWELL REMSCOPE 801 STORAGE OSCILLOSCOPE. Single Beam. Time Base 0.3 micro-sec. to 10 sec. in 16 ranges. Y Amp. Frequency Response. Low Gain 4 MHz. Med. Gain 2 MHz. High Gain 0.5 MHz. Sensitivity 5 mv./cm. at 0.3 MHz band width. Adjustable Display Time 15-120 mins. in 4 steps. Variable persistence 1 sec.-2 mins.

TRACE SHIFTER TS1 for use with above. Enables display of 3 or 10 steps at 30 micro-sec. min. intervals. Inclusive price **£225.**

SOLARTRON CD1400. Double Beam. DC-15 MHz. CX 1441 and 1443 plug-in units. Rise Time 2nsec. Sensitivity 100 mv./cm.-50 v./cm. 9 ranges. Time base 0.5 micro-sec.-200 micro-sec./cm. in 18 ranges. 19 in. Rack Mounting. Overhauled, V.G. condition. Handbook. **£165.**

### MARCONI SIGNAL GENERATOR 144HS.

10 KHz-72 MHz Crystal calibrator. V.G. condition. **£165.** Carriage extra.



### WELDING POWER SUPPLY—Hughes Model

FD 550. Constant voltage. Weld voltage and duration controls. 100 v. input. Price **£125.**

### OSCILLOSCOPE CAMERAS

#### Ilford Polaroid Type A

Illustrated.

ice..... **£99.50** plus carriage

swing head to suit Type 'A' camera.

ice..... **£25.50** plus carriage



**Opportunities Unlimited in RADIO, TELEVISION, ELECTRONICS**

**C & G Telecommunication Techns' Certificate**  
**C & G Electronic Servicing Certificate**  
**R.T.E.B. Radio/T.V. Servicing Certificate**  
**Radio Amateurs' Examination**  
**General Certificate of Education, etc.**

*Which one would qualify you for higher pay?*

International Correspondence Schools provide specialized training courses for all these certificates, and with the help of the Schools' experienced tutors you can be sure of early success. You will have the advantage of building on your practical experience and ensuring that you have the technical knowledge so essential for success in electronics.

**And the result?** You'll soon be qualified in your field of electronics, and in a position to choose your opportunity.

Find out how ICS can help you. Send for our *free* prospectus right away.

**ALL EXAMINATION STUDENTS ARE COACHED UNTIL SUCCESSFUL**

**NOW—COLOUR TV SERVICING COURSES**

As the demand for colour TV increases, so does today's demand for trained servicing engineers. You can learn the techniques of servicing colour and monochrome TV sets through new home study courses specially prepared for the practical TV engineer.

**SELF-BUILD RADIO COURSES**

We'll teach you both the theory and practice of valve and transistor circuits, as well as how to service them, while you build your own 5 valve receiver, transistor portable and high grade test instruments. You build equipment of real practical use!

**POST TODAY FOR FULL DETAILS OF ICS COURSES IN RADIO, TV AND ELECTRONICS**

International Correspondence Schools, Dept. 221, Intertext House, Stewarts Road, London, SW8 4UJ

Please send me *free* and *without any obligation* the ICS Prospectus

(State subject or Exam) .....

Name ..... Age .....

(BLOCK CAPITALS PLEASE)  
 Address .....



**INTERNATIONAL CORRESPONDENCE SCHOOLS**

**W.W. AMPLIFIER KITS**

**100 W AMPLIFIER (OVERLOAD PROTECTION INCLUDED)**  
 Designer, Texas Instruments Approved.

Matched Set 22 guaranteed Texas transistors, diode, 13 caps, 32 resistors, 3 pots, choke, 2 h/sinks 4 in. x 4.6 in. x 1.3 in., drilled 2 x TO3, fibreglass P.C.B., construction notes .. 18-00  
 2 sets .. 35-00  
 F/glass P.C.B. .. 0-95 Mains transformer .. 6-00  
 4700 mfd. 63v. .. 1-70 1000 mfd. 64v. .. 0-70  
 Power supply; 42v. + 50v. transformer, all cpts., h/sink .. 15-00  
 2 power supply kits .. 28-50

**30W BLOMLEY (New approach to class B)**  
 Semiconductor set .. 6-00 Resistors, caps, pots .. 1-95  
**30W BAILEY (SINGLE POWER RAIL)**  
 10 transistors .. 5-30 Resistors, caps, pot .. 1-30  
**LINSLEY HOOD CLASS AB**  
 MJ481, MJ491, MJE521, BC182L, BC212L, Zener .. 3-35  
 16 resistors, 10 capacitors, 2 pots .. 2-20  
**LINSLEY HOOD CLASS A (DEC., 1970, CIRCUIT)**  
 4 transistors .. 1-55 Resistors, caps, pot .. 1-80

**REGULATED 60v. POWER SUPPLY**  
 A design, suitable for a pair of Bailey or Blomley amplifiers, featuring very effective S/C protection. All components, including mech. parts, heat sink, fuses, etc. .. 7-85

Please state 8Ω or 15Ω for L.H. amps.  
 Transistor matching and mica washers at no charge.  
 Resistors, except power types, 1/2W 5%. Low noise carbon film.

**SEMICONDUCTORS MANY PRICES DOWN**

2N1613	0-20	2N3904	0-27	BFY50	0-20	1B40K20	1-40
2N1711	0-25	2N3906	0-27	40361	0-50	1N916	0-07
2N3053	0-20	2N4058	0-13	40362	0-60	1S44	0-05
2N3055	0-60	2N4062	0-12	MJ481	1-20	1S920	0-10
2N3707	0-11	BC107	0-10	MJ491	1-30	1S3062	0-25
2N3708	0-07	BC109	0-10	MJE521	0-72	TIP29A	0-50
2N3709	0-09	BC125	0-15	MPSA05	0-30	TIP30A	0-60
2N3710	0-09	BC126	0-22	MPSA55	0-35	TIP31A	0-60
2N3711	0-09	BC182L	0-10	MPSU05	0-60	TIP32A	0-74
2N3716	2-85	BC184L	0-11	MPSU55	0-70	TIP33A	1-05
2N3819	0-23	BC212L	0-12	MPSH05	0-20	TIP34A	2-00
2N3820	0-55	BFX84	0-25	1B08T20	0-50	TIP3055	0-60

BRAND NEW TOP QUALITY COMPONENTS. FAST SERVICE  
 MAIL ORDER ONLY  
 POST FREE

**POWERTRAN ELECTRONICS**  
 2 KENDALL PLACE · LONDON · W1

WW-080 FOR FURTHER DETAILS

**FM TUNER**

**NELSON-JONES**

Approved parts for this outstanding design (W.W. April 1971).

Featuring 0.75 μV sensitivity. Mosfet front end. Ceramic I.F. strip. Triple gang tuning. 1/2V r.m.s. output level, suitable for phase locked decoder, as below. Designer's own P.C.B.

All parts including P.C.B. S.A.E. please lists.

**PHASE LOCKED STEREO DECODER**

**PORTUS AND HAYWOOD**

Approved kit for this superb decoder (W.W. Sept. 1970).

Featuring 40dB separation up to 10 kHz. Low distortion. Negligible spurious tones (birdies). Simple setting up. Suitable for wide variety of tuners including the **NELSON-JONES TUNER** as above.

Complete kit **£8-97**, p.p. & ins. 15p  
 plus stabilised P.S.U. kit for decoder  
 plus tuner. **£3-55**, p.p. & ins. 18p

**INTEGRIX LIMITED**  
 P.O. BOX 45 DERBY DE1 1TW

# SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.  
 ● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

## NEW "SEW" DESIGNS! CLEAR PLASTIC METERS BAKELITE PANEL METERS



**TYPE SW. 100**  
 100 x 80 mm.

50μA	£3.471	20V. D.C.	£2.971
50-0-50μA	£3.371	50V. D.C.	£2.971
100μA	£3.371	300V. D.C.	£2.971
100-0-100μA	£3.371	1 amp. D.C.	£2.971
	£3.25	5 amp. D.C.	£2.971
500μA	£3.121	300V. A.C.	£2.971
1mA	£2.971	VU Meter	£3.75

**TYPE S-80**  
 80 mm. square fronts

50μA	£3.121	50V. D.C.	£2.471
50-0-50μA	£2.971	300V. D.C.	£2.471
100μA	£2.971	1 amp. D.C.	£2.471
100-0-100μA	£2.871	5 amp. D.C.	£2.471
500μA	£2.821	300V. A.C.	£2.821
1mA	£2.471	VU Meter	£3.71
20V. D.C.	£2.471		

### "SEW" CLEAR PLASTIC METERS

Type MR.85P. 4 1/2 in. x 4 1/2 in. fronts.



50μA	£3.60	10mA	£2.60
50-0-50μA	£3.10	50mA	£2.60
100μA	£3.10	100mA	£2.60
100-0-100μA	£3.10	500mA	£2.60
200μA	£2.971	1 amp.	£2.60
500μA	£2.971	5 amp.	£2.60
500-0-500μA	£2.60	15 amp.	£2.60
1mA	£2.60	30 amp.	£2.60
1-0-1mA	£2.60	20V. D.C.	£2.60
5mA	£2.60	50V. D.C.	£2.60

Type MR.82P. 2 1/2 in. square fronts.

50μA	£3.10	10V. D.C.	£2.00
50-0-50μA	£2.60	20V. D.C.	£2.00
100μA	£2.60	50V. D.C.	£2.00
100-0-100μA	£2.371	300V. D.C.	£2.00
500μA	£2.25	15V. A.C.	£2.00
1mA	£2.00	300V. A.C.	£2.00
5mA	£2.00	8 Meter 1mA	£2.10
10mA	£2.00	VU Meter	£3.10
50mA	£2.00	1 amp. A.C.*	£2.00
100mA	£2.00	5 amp. A.C.*	£2.00
300mA	£2.00	10 amp. A.C.*	£2.00
1 amp.	£2.00	20 amp. A.C.*	£2.00
5 amp.	£2.00	30 amp. A.C.*	£2.00

Type MR.85P. 3 1/2 in. x 3 1/2 in. fronts.

50μA	£3.371	10V. D.C.	£2.10
50-0-50μA	£2.75	20V. D.C.	£2.10
100μA	£2.75	50V. D.C.	£2.10
100-0-100μA	£2.60	150V. D.C.	£2.10
200μA	£2.60	100V. D.C.	£2.10
500μA	£2.371	15V. A.C.	£2.10
500-0-500μA	£2.10	50V. A.C.	£2.10
1mA	£2.10	150V. A.C.	£2.10
5mA	£2.10	300V. A.C.	£2.10
10mA	£2.10	500V. A.C.	£2.10
50mA	£2.10	8 Meter 1mA	£2.371
100mA	£2.10	VU Meter	£3.371
500mA	£2.10	50mA A.C.*	£2.10
1 amp.	£2.10	100mA A.C.*	£2.10
5 amp.	£2.10	200mA A.C.*	£2.10
10 amp.	£2.10	500mA A.C.*	£2.10
15 amp.	£2.10	1 amp. A.C.*	£2.10
20 amp.	£2.10	5 amp. A.C.*	£2.10
30 amp.	£2.10	10 amp. A.C.*	£2.10
50 amp.	£2.371	20 amp. A.C.*	£2.10
5V. D.C.	£2.10	30 amp. A.C.*	£2.10

\* MOVING IRON—  
 ALL OTHERS MOVING COIL  
 Please add postage

### SEW EDUCATIONAL METERS



**Type ED 107**  
 Size overall 100mm x 90mm x 108mm

A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3in. mirror scale. The meter movement is easily accessible to demonstrate internal working.

Available in the following ranges—

50μA	£4.50	10V d.c.	£3.97
100μA	£4.25	20V d.c.	£3.97
1mA	£3.97	50V d.c.	£3.97
50-0-50μA	£4.25	300V d.c.	£3.97
1-0-1mA	£3.97	Dual range	
1A d.c.	£3.97	500mA/5V d.c.	£4.25
5A d.c.	£3.97	5V/50V d.c.	£4.25

### "SEW" BAKELITE PANEL METERS

Type MR.65. 3 1/2 in. square fronts.



25μA	£3.50	500mA	£1.75
50μA	£3.371	1 amp.	£1.75
50-0-50μA	£2.25	5 amp.	£1.75
100μA	£2.25	15 amp.	£1.75
100-0-100μA	£2.25	30 amp.	£1.75
500μA	£2.10	50 amp.	£1.75
1mA	£1.75	5V. D.C.	£1.75
1-0-1mA	£1.75	10V. D.C.	£1.75
5mA	£1.75	20V. D.C.	£1.75
10mA	£1.75	50V. D.C.	£1.75
50mA	£1.75	150V. D.C.	£1.75
100mA	£1.75	30V. A.C.*	£1.75
		60V. A.C.*	£1.75
		300V. A.C.*	£1.75
		500mA A.C.*	£1.75
		1 amp. A.C.*	£1.75
		5 amp. A.C.*	£1.75
		15 amp. A.C.*	£1.75
		20 amp. A.C.*	£1.75
		50 amp. A.C.*	£1.75
		VU Meter	£3.10

### EDGWISE METERS



Type P.E.70. 3 1/2 in. x 1 1/2 in. x 2 1/2 in. deep.

50μA	£3.00	500μA	£2.60
50-0-50μA	£2.871	1mA	£2.371
100μA	£2.871	300V. A.C.	£2.371
100-0-100μA	£2.75	VU Meter	£3.25
200μA	£2.75		

Send for illustrated brochure and further details on all Sew Panel Meters—Discounts for quantities

## MULTIMETERS FOR EVERY purpose!

**TECH PT.34.** 1,000 O.P.V. 0/10/50/250/500/1,000 v. a.c. and d.c. 0/1/100/500 mA. d.c. 0/100 K. £1974 P. & P. 121p.

**MODEL TE-200** 20,000 O.P.V. Mirror scale, overload protection. 0/5/25/125/1,000 V. D.C. 0/10/50/250/1,000 V. A.C. 0/50 μA/250 MA. 0/60K/6 meg. + 20 to + 62 db. £375 P. & P. 15p

**MODEL TE-70.** 30,000 O.P.V. 0/3/15/60/300/600/1,200 v. D.C. 0/6/30/120/600/1,200 v. A.C. 0/30μA/3/300mA. 0/16K/160K/1.6M/16 Meg. £550 P. & P. 15p

**MODEL TE-12.** 20,000 O.P.V. 0/0.6/6/30/120/600/1,200/3,000/6,000 v. D.C. 0/6/30/120/600/1,200 v. A.C. 0/60μA/6/60/600 mA. 0/6K/60K/6Meg./60 Meg. Ω. 50 PF. 2 MFΩ. £5971 P. & P. 171p.


**MODEL PL438.** 20k Ω/Volt D.C. 8k Ω/Volt A.C. Mirror scale. 0/3/12/30/120/600V D.C. 3/30/120/300V A.C. 50/600μA/60/600 mA. 10/100K/1 Meg/10 meg Ω. —20 to —46db. £6971 P & P. 121p.

**MODEL 500** 30,000 O.P.V. with overload protection, mirror scale. 0/5/2.5/10/25/100/250/500/1,000 v. D.C. 0/2.5/10/25/100/250/500/1,000 v. A.C. 0/50μA/5/50/500 mA. 12 amp. D.C. 0/60K/8 meg. 60 meg Ω. £8871. Post paid.

**TMK MODEL TW-20CB** FEATURES RESETTABLE OVERLOAD BUTTON. Sensitivity: 20K Ω/Volt D.C. 5K Ω/Volt A.C. D.C. Volts: 0-0.5, 2.5, 10, 50, 250, 1,000V. A.C. Volts: 0-2.5, 10, 50, 250, 1,000V. D.C. Currents: 0-0.05, 0.5, 5, 50, 500mA. -10 amp. Resistance: 0-5K, 50K, 0-500K. 5 MEG. Decibels: -20 to +32db. £1150. P. & P. 171p.

**TMK LAB TESTER** 100,000 O.P.V. 6 1/2 in. Scale Buzzer Short Circuit Check. Sensitivity: 100,000 OPV D.C. 5K/Volt A.C. D.C. Volts: 5, 2.5, 10, 50, 250, 1,000V. A.C. Volts: 3, 10, 50, 250, 500, 1,000V. D.C. Current: 10, 100mA, 10, 100, 500mA, 2.5, 10 amp. Resistance: 1K, 10K, 100K, 10MEG, 100MEG. Decibels: -10 to +49 db. Plastic Case with carrying handle. Size 7 1/2 x 6 1/2 x 3 1/2. £1890. P. & P. 25p.

### HONEYWELL DIGITAL VOLTMETER VT.100

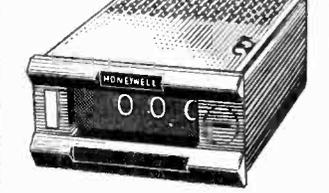

Can be panel or bench mounted. Basic meter measures 1 volt D.C. but can be used to measure a wide range of AC and DC volt, current and ohms with optional plug in cards.

Specification:  
 Accuracy: ± 0.2, ± 1 digit.  
 Resolution: 1mV.  
 Number of digits: 3 plus fourth overrange digit.  
 Overrange: 100% (up to 1.999)  
 Input impedance: 1000 Meg ohm.  
 Measuring cycle: 1 per second.  
 Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage.  
 Overload: to 100V. D.C.  
 Input: Fully floating (3 poles).  
 Input power: 110-250V. A.C. 50/60 cycles.  
 Overall size: 5 1/2 in. x 2 1/2 in. x 8 3/16 in.  
 AVAILABLE BRAND NEW AND FULLY GUARANTEED AT APPROX. HALF PRICE  
**£49.97 1/2 Carr. 50p**

**HONOR TE.10A.** 20 kΩ/Volt 5/25/50/250/500/2,500 v. D.C. 10/50/100/500/1,000 v. A.C. 0/50μA/2.5 mA/250 mA. D.C. 0/5K/6 meg. ohm. —20 to +22 dB. 10-0, 100 mfd. 0.100-0.1 mfd. £3-471. P. & P. 15p.

**MODEL TE-300** 30,000 O.P.V. Mirror scale, overload protection 0/6/3/15/60/300/1,200 V.D.C. 0/6/30/120/600/1,200 V.A.C. 0/30μA/300MA/600MA. 0/8K/80K/800K/8 meg. —20 to +63 db. £5-971. P. & P. 15p.

**TMK MODEL MD.120** Mirror scale. 20K/Volt D.C. 10K Ω/Volt A.C. 30/60/300/600/3,000 Volt D.C. 6/120/1,200 Volt A.C. Current 0-60 μA/10-120/300mA. 0-60K/0-6 Mohms —20 to +63 db. £4 621 P. & P. 15p.

**MODEL TE-90** 50,000 O.P.V. Mirror scale, overload protection. 0/3/12/60/300/600/1,200 v. D.C. 0/6/30/120/300/1,200 v. D.C. 0/5/50/500 mA. D.C. 16K/160K/1.6/16 MEG. —20 to +63 db. £7.50. P. & P. 15p.

**SKYWOOD SW-500** 50 K Ω/Volt. Mirror scale. D.C. volts: 0.6/3/12/30/300/600. A.C. volts: 3/30/300/600. D.C. current: 20μA/6/60/600mA. Resistance: 10K/100K/1 Meg. Decibels: —20 to +57 db. £7.50. P. & P. 15p.

**MODEL AS-100D.** 100K Ω/Volt 5 in. mirror scale. Built-in meter protection 0/3/12/60/120/300/600/1,200 v. D.C. 0/6/30/120/300/600 v. A.C. 0/6/30/120/300/600/1,200 v. D.C. 0/2K/200K/2M/200M. —20 to +17 db. £12.50. P. & P. 171p.

**TE-300** 20,000 Ω/VOLT GIANT MULTIMETER. Mirror scale and overload protection. 6 in. full view meter. 2 colour scale. 0/2.5/10/25/100/500/1,000 v. A.C. 0/25/12.5/10/50/250/1,000/5,000 v. D.C. 0/50μA/0/10/100/500mA/10 amp. D.C. 0/2K/200K/2M MEG. OHM. £15 P. & P. 25p

**FTC-401 TRANSISTOR TESTER** Full capabilities for measuring A, B and ICs. Buzzer Short Circuit Check. Sensitivity: 100,000 OPV D.C. 5K/Volt A.C. D.C. Volts: 5, 2.5, 10, 50, 250, 1,000V. A.C. Volts: 3, 10, 50, 250, 500, 1,000V. D.C. Current: 10, 100mA, 10, 100, 500mA, 2.5, 10 amp. Resistance: 1K, 10K, 100K, 10MEG, 100MEG. Decibels: -10 to +49 db. Plastic Case with carrying handle. Size 7 1/2 x 6 1/2 x 3 1/2. £1890. P. & P. 25p.

**T.E.40 HIGH SENSITIVITY A.C. VOLTMETER** 10 meg. input 10 ranges: 0/1/0.3/1/3/10/30/100/300 v. R.M.S. 4 cps. 1.2 Mc/s. Decibels —40 to +50 db. Supplied brand new complete with leads and instructions. Operation 230 v. A.C. £17.50 Carr. 25p.

**TE-65 VALVE VOLTMETER** High quality instrument with 28 ranges. D.C. volts 1.5-1,500 v. A.C. volts 1.5-1,500 v. Resistance up to 1,000 megohms. 220/240v. A.C. operation. Complete with probe and instructions £17.50. P. & P. 30p. Additional Probes available: R.F. £2-121 H.V. £2-50.

**270° WIDE ANGLE 1mA METERS** MW1-6 60mm. square £3-971 MW1-8 80mm. square £4-971 P. & P. extra

**G. W. SMITH & Co. (Radio) Ltd.**  
 ALSO SEE NEXT TWO PAGES

# SEMI-CONDUCTOR VALVES

## ALL DEVICES BRAND NEW AND FULLY GUARANTEED

### TRANSISTORS

2C301	20p	2N3606	27p	40310	45p	BC175	22p	B8X20	17p	NKT278	25p
2C302	19p	2N3607	27p	40311	35p	BC177	22p	B8X21	37p	NKT281	27p
2C303	20p	2N3608	15p	40312	47p	BC178	22p	B8X22	45p	NKT401	87p
2C304	30p	2N3609	27p	40313	47p	BC179	22p	B8X27	47p	NKT402	90p
2C306	30p	2N3641	15p	40315	37p	BC182L	10p	B8X60	82p	NKT403	75p
2C309	10p	2N3642	15p	40316	47p	BC183	10p	B8X61	82p	NKT404	82p
2C371	15p	2N3643	20p	40317	37p	BC183L	10p	B8X76	15p	NKT405	75p
2C374	20p	2N3644	25p	40319	55p	BC184	10p	B8X77	20p	NKT406	82p
2C381	25p	2N3645	25p	40320	47p	BC184L	10p	B8X78	20p	NKT451	82p
2C388A	49p	2N3691	15p	40323	32p	BC186	25p	B8Y24	15p	NKT452	82p
2N404	21p	2N3692	15p	40324	47p	BC187	27p	B8Y25	15p	NKT453	47p
2N496	15p	2N3693	15p	40326	37p	BC212L	12p	B8Y26	17p	NKT713	20p
2N497	15p	2N3694	15p	40329	30p	BC213L	12p	B8Y27	17p	NKT717	42p
2N498	25p	2N3702	12p	40344	27p	BC214L	15p	B8Y28	17p	NKT734	27p
2N499	42p	2N3703	10p	40347	57p	BCY10	27p	B8Y32	25p	NKT736	25p
2N705	75p	2N3704	10p	40348	55p	BCY31	30p	B8Y36	25p	NKT773	35p
2N706A	11p	2N3705	10p	40360	42p	BCY32	50p	B8Y37	25p	NKT776	35p
2N708	15p	2N3706	10p	40361	47p	BCY33	20p	B8Y38	20p	NKT781	30p
2N709	45p	2N3707	12p	40362	57p	BCY34	25p	OC16	50p	OC19	37p
2N718	25p	2N3708	8p	40370	32p	BCY38	30p	OC21	30p	OC22	50p
2N718A	30p	2N3709	10p	40406	57p	BCY39	60p	OC29	62p	OC23	60p
2N726	25p	2N3714	10p	40407	40p	BCY40	50p	OC35	50p	OC36	62p
2N727	25p	2N3711	10p	40408	52p	BCY41	15p	OC37	60p	OC42	25p
2N914	17p	2N3713	11.87	40409	55p	BCY42	15p	OC43	60p	OC44	12p
2N916	17p	2N3714	22.00	40410	62p	BCY43	15p	OC45	12p	OC46	15p
2N918	30p	2N3715	22.22	40412	50p	BCY44	15p	OC46	15p	OC47	12p
2N929	22p	2N3716	22.90	40467A	57p	BCY45	15p	OC48	20p	OC48	20p
2N930	24p	2N3773	22.45	40468A	35p	BCY46	15p	OC49	20p	OC49	20p
2N937	25p	2N3704	10p	40528	22.75	BCY58	22p	OC50	37p	OC50	37p
2N1090	22p	2N3819	34p	40600	57p	BCY59	22p	OC51	37p	OC51	37p
2N1091	22p	2N3820	57p	40603	50p	BCY60	97p	OC52	25p	OC52	25p
2N1131	25p	2N3823	75p	AC107	30p	BCY70	20p	OC53	50p	OC53	50p
2N1132	25p	2N3854	27p	AC126	20p	BCY71	30p	OC54	60p	OC54	60p
2N1302	17p	2N3854A	27p	AC127	25p	BCY72	15p	OC55	60p	OC55	60p
2N1303	17p	2N3855	27p	AC128	20p	BCY73	30p	OC56	62p	OC56	62p
2N1304	22p	2N3855A	30p	AC151	18p	BCY78	30p	OC57	22p	OC57	22p
2N1305	22p	2N3856	30p	AC152	22p	BCY79	30p	OC58	22p	OC58	22p
2N1306	24p	2N3856A	35p	AC154	22p	BCZ10	27p	OC59	22p	OC59	22p
2N1307	24p	2N3858	25p	AC176	22p	BCZ11	40p	OC60	22p	OC60	22p
2N1308	25p	2N3858A	25p	AC187	25p	BD112	57p	OC61	22p	OC61	22p
2N1309	24p	2N3859	27p	AC188	27p	BD116	11.12	OC62	22p	OC62	22p
2N1507	17p	2N3859A	32p	AC197	27p	BD121	85p	OC63	22p	OC63	22p
2N1613	21p	2N3860	30p	AC198	24p	BD123	80p	OC64	12p	OC64	12p
2N1631	35p	2N3866	11.50	AC199	24p	BD124	80p	OC65	12p	OC65	12p
2N1632	30p	2N3877	40p	AC200	24p	BD131	75p	OC66	12p	OC66	12p
2N1637	30p	2N3877A	40p	AC21	20p	BD132	85p	OC67	12p	OC67	12p
2N1638	27p	2N3902	40p	AC212	20p	BD110	11.07	OC68	12p	OC68	12p
2N1639	27p	2N3900A	40p	AC218	17p	BDY20	11.06	OC69	12p	OC69	12p
2N1701	11.10	2N3901	97p	AC219	47p	BDY61	11.25	OC70	12p	OC70	12p
2N1711	24p	2N3903	26p	AC240	14p	BDY62	11.00	OC71	12p	OC71	12p
2N1889	32p	2N3904	25p	AC241	25p	BP117	47p	OC72	12p	OC72	12p
2N1893	37p	2N3905	25p	AC242	25p	BP122	28p	OC73	12p	OC73	12p
2N2147	75p	2N3906	27p	AC243	25p	BP123	28p	OC74	12p	OC74	12p
2N2160	57p	2N4058	16p	AD149	47p	BP158	28p	OC75	22p	OC75	22p
2N2193	40p	2N4059	10p	AD150	62p	BP159	57p	OC76	22p	OC76	22p
2N2193A	42p	2N4060	12p	AD161	35p	BP163	35p	OC77	22p	OC77	22p
2N2194	27p	2N4061	12p	AD162	35p	BP167	25p	OC78	22p	OC78	22p
2N2194A	30p	2N4062	12p	AF109	45p	BP170	35p	OC79	22p	OC79	22p
2N2217	27p	2N4244	15p	AF114	27p	BP173	30p	OC80	22p	OC80	22p
2N2218	27p	2N4248	15p	AF115	25p	BP177	30p	OC81	22p	OC81	22p
2N2219	81p	2N4249	15p	AF116	25p	BP178	25p	OC82	22p	OC82	22p
2N2220	25p	2N4250	18p	AF117	25p	BP179	30p	OC83	22p	OC83	22p
2N2221	25p	2N4254	42p	AF118	44p	BP180	35p	OC84	22p	OC84	22p
2N2222	25p	2N4255	42p	AF121	45p	BP181	35p	OC85	22p	OC85	22p
2N2225A	25p	2N4256	42p	AF124	45p	BP182	30p	OC86	22p	OC86	22p
2N2227	80p	2N4285	17p	AF125	19p	BP184	25p	OC87	22p	OC87	22p
2N2368	15p	2N4286	17p	AF126	16p	BP185	25p	OC88	22p	OC88	22p
2N2369	17p	2N4287	17p	AF127	16p	BP194	17p	OC89	22p	OC89	22p
2N2369A	17p	2N4288	15p	AF129	28p	BP195	15p	OC90	22p	OC90	22p
2N2410	42p	2N4289	15p	AF178	45p	BP196	15p	OC91	22p	OC91	22p
2N2483	27p	2N4290	15p	AF179	45p	BP197	15p	OC92	22p	OC92	22p
2N2484	32p	2N4291	15p	AF180	50p	BP198	42p	OC93	22p	OC93	22p
2N2539	22p	2N4292	16p	AF181	40p	BP200	35p	OC94	22p	OC94	22p
2N2540	22p	2N4294	17p	AF186	39p	BP224	20p	OC95	22p	OC95	22p
2N2613	27p	2N4303	47p	AF239	37p	BP225	20p	OC96	22p	OC96	22p
2N2614	30p	2N4864	15p	AF271	35p	BP228	20p	OC97	22p	OC97	22p
2N2644	47p	2N4965	67p	AF280	47p	BP237	25p	OC98	22p	OC98	22p
2N2711	25p	2N5027	52p	AF211	32p	BP244	42p	OC99	22p	OC99	22p
2N2712	25p	2N5028	57p	ASy28	25p	BPW61	17p	OC100	22p	OC100	22p
2N2713	27p	2N5029	57p	ASy27	31p	BPW87	25p	OC101	22p	OC101	22p
2N2714	30p	2N5030	42p	ASy28	24p	BPW88	25p	OC102	22p	OC102	22p
2N2901	22p	2N5172	29p	ASy29	37p	BPW89	30p	OC103	22p	OC103	22p
2N2904A	32p	2N5173	29p	ASy30	37p	BPW90	22p	OC104	22p	OC104	22p
2N2905	37p	2N5175	52p	ASy31	32p	BPW91	20p	OC105	22p	OC105	22p
2N2905A	40p	2N5176	45p	ASy32	25p	BPX12	22p	OC106	22p	OC106	22p
2N2906	25p	2N5232A	30p	ASy37	45p	BPX13	22p	OC107	22p	OC107	22p
2N2906A	27p	2N5245	45p	ASy38	32p	BPX14	22p	OC108	22p	OC108	22p
2N2907	20p	2N5246	45p	ASy39	32p	BPX20	30p	OC109	22p	OC109	22p
2N2923	15p	2N5249	47p	AUY10	11.50	BPX37	30p	OC110	22p	OC110	22p
2N2924	15p	2N5265	33.25	BC107	10p	BPX44	37p	OC111	22p	OC111	22p
2N2925	15p	2N5305	37p	BC108	10p	BPX68	67p	OC112	22p	OC112	22p
2N2926B	12p	2N5306	40p	BC109	10p	BPX84	25p	OC113	22p	OC113	22p
2N2926S	12p	2N5307	37p	BC113	15p	BPX85	25p	OC114	22p	OC114	22p
2N2927	12p	2N5308	47p	BC114	15p	BPX86	25p	OC115	22p	OC115	22p
2N3011	24p	2N5309	62p	BC115	15p	BPX87	27p	OC116	22p	OC116	22p
2N3014	25p	2N5310	42p	BC116	15p	BPX88	25p	OC117	22p	OC117	22p
2N3053	24p	2N5354	27p	BC118	15p	BPX89	25p	OC118	22p	OC118	22p
2N3054	49p	2N5355	27p	BC119	15p	BPX93A	70p	OC119	22p	OC119	22p
2N3065	72p	2N5356	32p	BC121	20p	BPY11	45p	OC120	22p	OC120	22p
2N3133	25p	2N5365	47p	BC122	20p	BPY18	25p	OC121	22p	OC121	22p
2N3134	30p	2N5366	37p	BC125	15p	BPY19	25p	OC122	22p	OC122	22p
2N3135	25p	2N5367	57p	BC126	25p	BPY21	42p	OC123	22p	OC123	22p
2N3136	25p	2N5457	34p	BC134	15p	BPY24	45p	OC124	22p	OC124	22p
2N3390	25p	2N5458	35p	BC135	15p	BPY29	40p	OC125	22p	OC125	22p
2N3391	20p	2N5459	45p	BC136	15p	BPY30	40p	OC126	22p	OC126	22p
2N3392	17p	2N5460	37p	BC137	15p	BPY41	50p	OC127	22p	OC127	22p
2N3393	15p	2N5461	25p	BC138	37p	BPY43	62p	OC128	22p	OC128	22p
2N3394	15p	2N5462	25p	BC140	35p	BPY50	25p	OC129	22p	OC129	22p
2N3395	15p	2N5463	47p	BC141	35p	BPY51	20p	OC130	22p	OC130	22p
2N3402	22p	2N5464	37p	BC142	35p	BPY52	20p	OC131	22p	OC131	22p
2N3403	22										

# HI-FI EQUIPMENT

## SAVE UP TO 33 1/3% OR MORE

### SEND S.A.E. FOR DISCOUNT PRICE LISTS AND PACKAGE OFFERS!



### RECORD DECKS

<b>B.S.R.</b>	
Mini Mono	£4.97
CI29	£8.87
MP60	£11.95
610	£15.90
510	£12.95
310	£10.95
MP60 T.P.D.1	£19.50
MTP60 T.P.D.	£19.50
610 T.P.D.1	£22.97
510 T.P.D.1	£20.97
210 Package*	£11.75
H.T.70	£17.25
H.T.70 Package	£24.97
<b>THORENS</b>	
TD125	£24.95
TD125AB	£29.97
TX25	£8.95
TD150A II	£29.50
TD150AB II	£42.95
TX11	£3.92

1 Mono Stereo Cartridge  
All other models less Cartridge  
Carriage 50p extra any model.

### RECORD DECK PACKAGES

Decks supplied ready wired in plinth and cover fitted with cartridge.  
Garrard 2025 T/C with Sonotone 9TAHCD £15.00  
Garrard SP25 III with Goldring G800 £20.95  
Garrard AP76 with Goldring G800... £30.95  
BRR MP60 with Audio Technica AT.35 £21.00  
Goldring GL69/2 with Goldring G800 £39.00  
Goldring GL75 with Goldring G800... £47.50  
Goldring GL75 with Goldring G800E £52.50  
Carriage 50p extra any model.

### SINCLAIR EQUIPMENT Project 60. Package Offers



2 x Z30 amplifier, stereo 60 pre-amp, P25 power supply. £18.75. Carr. 37p. Or with P26 power supply. £18.85. Carr. 37p. 2 x Z50 amplifier stereo 60 pre-amp, F28 power supply. £20.25. Carr. 37p. Transformer 4 P28. £2.97 extra. Add to any of the above £4.37 for active filter unit and £18 for a pair of Q18 speakers. PROJECT 60 FM TUNER £20.97. Carr. 37p. All other Sinclair products in stock. IC12 £22.50. 2,000 amplifier £25.00. Carr. 37p. Nesteric amplifier £45.97. Carr. 37p.

## Latest Catalogue


New 6th edition giving full details of a comprehensive range of HI-FI EQUIPMENT COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 50p. 272 pages, fully illustrated and detailing thousands of items at bargain prices.

**SEND NOW! STILL ONLY 37 1/2p P & P 10p**

Hi-Fidelity Electronic Components & Equipment Catalogue

NOTE! All shops and offices closed for annual holidays August 2nd to 14th. No goods will be despatched during this period—please order early.

### TELETON SAQ-206 STEREO AMPLIFIER

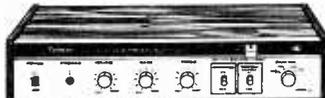

Latest exciting release. Brand new model, beautifully styled with walnut case, 6 + 6 watts r.m.s. Switched inputs for mag. xtal. aux. tape. Incorporates volume, bass, treble and sliding balance control, scratch filter and loudness control. Rec. List £32.50. Our Price £19.97. Carr. 37p. Suggested system: SAQ 206 amplifier, SP25 III, plinth and cover, G800 cartridge, pair DI 3 way speakers. Total Rec. List £81. Our Price £59.50. Carr. £1.50.

### TELETON F.2000 AM/FM STEREO TUNER/AMPLIFIER




Probably the most popular budget Tuner/ Amp. and now offered at a ridiculous low price. 5 watts r.m.s. per channel. Tape/Cer. phono inputs. APC/Built-in MPX. List £51. Our Price £32.50. Carr. 50p.

#### SUGGESTED SYSTEM

F.2000, Garrard 2025 T/C Changer fitted stereo cartridge, with plinth and cover and pair of GWS 3-way speakers. Total Rec. Price £97.73. Our Price £59.45. Carr. £1.

### TRANSISTOR FM TUNER

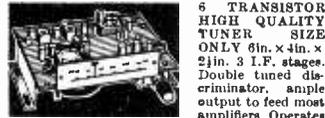

6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6in. x 4in. x 2 1/2in. 3 I.F. stages. Double tuned discriminator, simple output to feed most amplifiers. Operates on 9 volt battery. Coverage 88-108 Mc/s. Ready built ready for use. Fantastic value for money. £28.37. P. & P. 12p.

STEREO MULTIPLEX ADAPTORS, £4.97.

### MARCONI CT44 TF95 AF ABSORPTION WATTMETER

1 μwatt to 6 watts £20. Carr. £1.

### BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR



New high-quality portable instrument. Sine 1 Hz to 100 KHz. Square 20 Hz to 20 KHz. Output max. +10 db (10 K ohms). Operation 220/240 v. A.C. Size 215 mm x 150 mm x 120 mm. Price £27.50 Carr. 25p.

### MARCONI TF.142E DISTORTION FACTOR METERS


Excellent condition. Fully tested £20. Carr. 75p.

### TE-20RF SIGNAL GENERATOR



Accurate wide range signal generator covering 120 kc/s-260 Mc/s. on 6 bands. Directly calibrated. Variable R.F. attenuator. Operation 200/240 v. A.C. Brand new with instructions. £15. P. & P. 37p. S.A.E. for details

### BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

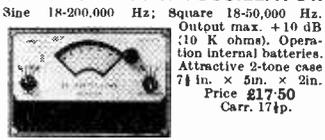

Sine 18-200,000 Hz; Square 18-50,000 Hz. Output max. +10 db (10 K ohms). Operation internal batteries. Attractive 2-tone case 7 1/2 in. x 5 in. x 2 in. Price £17.50 Carr. 17p.

### TRANSISTORISED L.C.R. A.C MEASURING BRIDGE.


A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1 Ω - 11.1 MEG Ω 6 Ranges ± 1%. L. 1 μH - 111 HEN. RIBS. 6 Ranges ± 2%. C. 10PF ± 1110MPD. 6 Ranges ± 2%. TURNS RATIO 1:1/1000 - 1:11100. 6 Ranges ± 1%. Bridge voltage at 1,000 CPS. Operated from 9 volts. 100 μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2" x 5" x 2" £20. P. & P. 25p.

### TE-16A TRANSISTORISED SIGNAL GENERATOR




5 Ranges 400 kHz-30 MHz. An inexpensive instrument for the handyman. Operates on 9 v. battery. Wide easy to read scale. 800 kHz modulation. 5 1/2 in. x 5 1/2 in. x 3 1/2 in. Complete with instructions and leads. £7.97 P. & P. 20p.
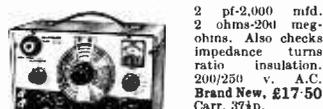
### LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER




2 pf-2,000 mid. 2 ohms-200 meg-ohms. Also checks impedance turns ratio insulation. 200/250 v. A.C. Brand New. £17.50 Carr. 37p.

### TO-3 PORTABLE OSCILLOSCOPE. 3" TUBE

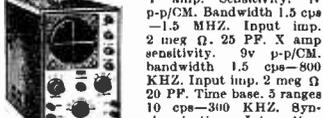

Y amp. Sensitivity. 1v p-p/CM. Bandwidth 1.5 cps - 15 MHz. Input imp. 2 meg Ω. 25 PF X amp sensitivity. 9v p-p/CM. bandwidth 1.5 cps-800 KHZ. Input imp. 2 meg Ω 20 PF. Time base. 5 ranges 10 cps-300 KHZ. Synchronisation. Internal/external. Illuminated scale. 140 x 215 x 330 mm. Weight 15 1/2 lbs. 220/240 V. A.C. Suggested brand new with handbook £37.50. Carr. 50p.
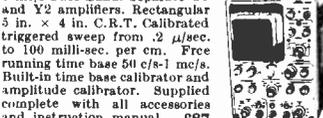
### RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPE



5 inch Pass Band. Separate Y1 and Y2 amplifiers. Rectangular 3 in. x 4 in. C.R.T. Calibrated triggered sweep from 2 μsec. to 100 mill-sec. per cm. Free running time base 50 c/s-1 mc/s. Built-in time base calibrator and amplitude calibrator. Supplied complete with all accessories and instruction manual. £37 Carr. paid.

### TE111 DECADE RESISTANCE ATTENUATOR



Variable range 0-111 db. Connections. Unbalanced T and Bridge T. Impedance 600 ohms. Range (0.1 db x 10) + 10 + 20 + 30 + 40 db. Frequency: DC to 200 KHZ (-3db) Accuracy: 0.05 db. + indication db x 0.01 Maximum input less than 4 watts (50 volts). Built in 600 Ω load resistance with internal/external switch. Brand new £27.50 P. & P. 25p.

### AM/FM SIGNAL GENERATORS




Oscillator Test No. 2. A high quality precision instrument made for the Ministry by Alrmec. Frequency coverage 20-80 Mc/s. AM/CW/FM. Incorporates precision dial, level meter, precision attenuator 1 μV-100 μV. Operation from 12 volt D.C. or 0/110/200/250 v. A.C. Size 12 x 8 1/2 x 9 in. Supplied in brand new condition complete with all connectors, fully tested, £45. Carr. £1.


## POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. 1/2 inch hole fixing. 1/2 in. dia. shafts. Bulk quantities available. 25 WATT. 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms. 72 1/2p. P. & P. 7p. 50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. £1.05. P. & P. 7p. 100 WATT. 1/5/10/25/50/100/250/500/1000 or 2500 ohms. £1.37 1/2p. P. & P. 7p.
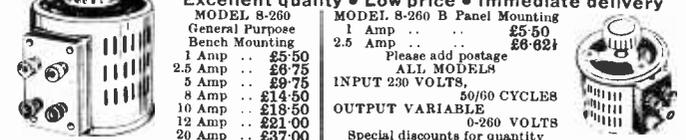
### "YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS



Excellent quality • Low price • Immediate delivery  
MODEL 8-260 General Purpose Bench Mounting  
1 Amp .. £5.50  
2.5 Amp .. £6.75  
5 Amp .. £9.75  
8 Amp .. £14.50  
10 Amp .. £18.50  
12 Amp .. £21.00  
20 Amp .. £37.00  
MODEL 8-260 B Panel Mounting  
1 Amp .. £5.50  
2.5 Amp .. £6.82  
Please add postage  
ALL MODELS INPUT 230 VOLTS, 50/60 CYCLES  
OUTPUT VARIABLE 0-260 VOLTS  
Special discounts for quantity

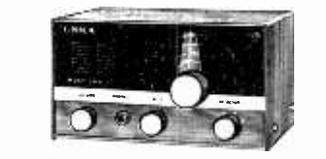

**UNR 30 RECEIVER**  
4 Bands covering 550kc/s - 30mc/s. B.P.O. Built in Speaker 220/240v A.C. Brand new with instructions. £15.75. Carr. 37p.

### WS42 TRANSCEIVERS

Large quantity available for EXPORT! Excellent condition. Enquiries invited

### LAFAYETTE HA-600 RECEIVER



General coverage 150-400 kc/s, 550kc/s-30 mc/s. FET front end, 2 mech. filters, product detector, variable B.F.O., noise limiter, 3 Meter Band-pass. RF Gain. 15" x 9 1/2" x 8 1/2". 18 lb. 220/240v AC or 12V DC. Brand new with instructions. £45 Carriage 50p.

### FULL RANGE TRIOEQUIPMENT

### CRYSTAL CALIBRATORS NO. 10



Small portable crystal controlled wavemeter. Size 7in. x 7 1/2in. x 4in. Frequency range 500 Kc/s-10 Mc/s (up to 80 Mc/s on harmonics). Calibrated dial. Power requirements 500 V.D.C. 15mA and 12 V.D.C. 0.3A. Excellent condition. £4.47. Carr. 37p.

### B.C. 221 FREQUENCY METERS

Latest release 125 KHz-20 MHz. Excellent condition. Fully tested and checked and complete with calibrator charts. £27.50 each. Carr. 50p.

### SOLID STATE VARIABLE A.C. VOLTAGE REGULATORS



Compact and panel mounting. Ideal for control of lamps, drills, electrical appliances etc. Input 230/240 v. A.C. Output continuously variable from 20 v.-240 v. Model MR 2305 5 amp 68 x 46 x 43 mm. £3.37. Model MR 2310 10 amp 90 x 68 x 60 mm. £11.97. Postage 12p.

### AUTO TRANSFORMERS

0/115/230v. Step up or step down. Fully shrouded. 150 W. £2.37. P. & P. 17p. 300 W. £3.25. P. & P. 22p. 500 W. £4.97. P. & P. 32p. 1,000 W. £7.25. P. & P. 37p. 1,500 W. £9.71. P. & P. 42p. 5,000 W. £38.00. P. & P. 21.

### VOLTAGE STABILISER TRANSFORMERS.

180-260v. Input. Output 230v. Available 150w or 225w. £12.50. Carr. 25p.

### 230 VOLT A.C. 50 CYCLES

Brand new. 3 sets of changeover contacts at 5 amp rating. 50p each P. & P. 10p (100 lots £40) Quantities available.

### LARGE STOCKS OF TEST EQUIPMENT AND RECEIVERS—MARCONI, ETC., FOR CALLERS

# G.W.SMITH & CO. (RADIO) LTD

27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715  
3 LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204  
34 LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155  
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387

OPEN 9-6 MONDAY TO SATURDAY

All Mail Orders to -  
11-12, Paddington Green,  
London W.2  
Tel: 01-262 6562  
(Trade supplied)

# QUALITY PARTS FOR THE DISCERNING BUILDER

**BAILEY PRE-AMPLIFIER** still offers lowest distortion level and best overload capability. Edge Connector Mounted Printed Circuit in Fibreglass or Paxolin material to choice. Highest quality parts including gain graded transistors.

**BAILEY 30w POWER AMPLIFIER.** Edge Connector Mounted Printed Circuit in Fibreglass or Paxolin material, size 4 1/2" x 2 1/2". This unit and the above Pre-amplifier can both be used in our new Metalwork Assembly.

**BAILEY 30w POWER SUPPLY.** We have now designed a Printed Circuit Board for the power supply, again intended to be used with our Metalwork, which also has edge connector mounting. Available in Fibreglass material only.

**BAILEY 20w AMPLIFIER.** Special driver transformer and bifilar wound mains transformer. Printed circuits and all parts available for this design.

**LINSLEY HOOD CLASS A.** Full sets of parts now available to the new specification given in the December, 1970, Wireless World.

**FULL KITS OF PARTS** including Edge Connector Mounting Printed Circuit now available for Linsley Hood AB Design. This unit is fully compatible with our Metalwork Assembly.

**SUGDEN CLASS A AMPLIFIER.** A Hi-Fi News design. All parts are in stock except the Metalwork.

**WADDINGTON STEREO DECODER.** Printed circuits now available in fibreglass and paxolin material.

**J. R. STUART TAPE CIRCUITS.** We will be designing Printed Circuit Boards and supplying parts for this interesting design.

Full details are given in our Free lists. Please send foolscap s.a.e.

## HART ELECTRONICS

PENYLAN MILL, MORDA, OSWESTRY, SY10 9AF SALOP  
Tel: Oswestry 2894

Personal callers are always welcome at our retail shop, but please note we are closed on Saturdays.

**EX COMPUTER PRINTED CIRCUIT PANELS** 2" x 4" packed with smi-conductors and top quality resistors, capacitors, diodes, etc. Our price, 10 boards, 50p. P. & P. 7p. With a guaranteed minimum of 35 transistors. Transistor Data included.

**SPECIAL BARGAIN PACK.** 25 boards for £1. P. & P. 18p. With a guaranteed minimum of 85 transistors. Transistor Data included.

**PANELS** with 2 power transistors sim. to OC28 on each board plus components. 2 boards (4 x OC28) 50p. P. & P. 5p.

9 OAS, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET872, 3 GET872B, 1 GET875. All long leaded on panels 13" x 4 1/4" for £1. P. & P. 25p.

### 12V 4A POWER SUPPLY

Extremely well made by FRAKO GmbH in W. Germany, with constant voltage mains transformer, tapped input from 115V to 240V. Full wave rectification and capacitor smoothing. Size 9" x 6" x 5", weight 11 lb. These units are brand new, unused and fully guaranteed. Maker's price believed to be around £80. Our Price £9.50. Carr. 50p

### 250 MIXED RESISTORS

1/2 and 1/4 Watt 62p

### DIODES EX EQPT. SILICON

1 Amp 1,000 PIV 4 for 50p  
20 Amp 150 PIV 4 for £1.00  
P. & P. 5p

### QUARTZ HALOGEN BULBS

with long leads 12V 55W for car spotlights and projectors etc. 50p

### RELAY OFFER

Single Pole Changeover Silver Contacts 25 x 6 x 7 1/2 5K Ohm Operates on 25 to 50V. 8 for 50p. P. & P. 8p.

## KEYTRONICS

### BUMPER BARGAIN PARCEL

We guarantee that this parcel contains at least 1,750 components. Short-leaded on panels, including a minimum of 35 transistors (mainly NPN) and PNP germanium, audio and switching types—data supplied). The rest of the parcel is made up with: Resistors 5% or better (including some 1% mainly metal oxide, carbon film, and composition types. Mainly 1/2 and 1 watt diodes, miniature silicon types OA90, OA91, OA95, IS130, etc.). capacitors including tantalum, electrolytics, ceramics and polyester... inductors, a selection of values... also the odd transformer, trim-pot, etc., etc... These are all miniature, up to date, professional, top quality components. Don't miss this, one of our best offers yet! Price £3.25. P. & P. 33p—U.K. New Zealand £1 P. & P. Limited stocks only.

### EX-COMPUTER POWER SUPPLIES

Reconditioned, fully tested and guaranteed. These very compact units are fully smoothed with a ripple better than 10mv. and regulation better than 1%. Over voltage protection on all except 24v. units. 120v. 130v. a.c. 50c/s input. Mains transformer to suit £3 extra if required.

We offer the following types:  
6v. 8a. £10 20v. 15a. £15  
6v. 15a. £14 30v. 7a. £12  
12v. 20a. £16 24v. 4a. £14  
Carriage 75p per unit.

### 150 High Stabs 1/2 and 1 Watt, 5% and Better 62p

### LARGE CAPACITY ELECTROLYTICS

4 1/2" x 2" dia. 10,000 mfd 30V 40p each  
5,000 mfd 55V 30p  
16,000 mfd 12V P. & P. 6p  
4 1/2" x 3" dia. 8,000 mfd 55V each  
50p each P. & P. 12p each

### EXTENSION TELEPHONES

99p ea. P. & P. 25p  
£1.75 for 2 P. & P. 50p  
These phones are extensions and do not contain bells.



MAILING ADDRESS  
44 EARLS COURT ROAD, LONDON W.8  
WAREHOUSE AND DISPATCH  
01-478 8499

# MARSHALL'S INTEGRATED CIRCUITS

NEW LOW PRICES • LARGEST RANGE • BRAND NEW • FULLY GUARANTEED

SPECIAL OFFER: 5% DISCOUNT TO ALL SATURDAY CALLERS (JULY AND AUGUST ONLY)

ROCA LINEAR ICs				MOTOROLA				MULLARD TTL				MULLARD DTL				GENERAL ELECTRIC					
Type	1-24	25-99	Type	1-24	25-99	Type	1-24	25-99	100-499	Type	1-24	25-99	Type	1-24	25-99	Type	1-24	25-99	Type	1-24	25-99
CA3000	1.80	1.60	CA3049	1.80	1.43	CA3059	1.85	1.48	SN7411	0.25	0.20	0.18	FJH101	0.87		TAAB41	1.82				
CA3001	2.08	2.40	CA3050	1.84	1.44	CA3060	4.81	4.37	SN7413	0.50	0.45	0.40	FJH121	0.87		TAAB42	2.42				
CA3002	1.80	1.80	CA3051	1.34	1.20	CA3062	2.55	2.27	SN7420	0.25	0.20	0.18	FJH141	0.87		TAAB43	2.43				
CA3004	1.80	1.80	CA3052	1.65	1.47	CA3064	1.20	1.07	SN7430	0.25	0.20	0.18	FJH161	0.87		TAAB44	2.63				
CA3005	1.17	1.05	CA3053	0.46	0.41	CA3065	1.20	1.07	SN7440	0.25	0.20	0.18	FJH171	0.87		TAAB45	2.93				
CA3006	2.80	2.50	CA3054	1.09	0.97	CA3075	1.13	1.00	SN7441	1.00	0.80	0.80	FJH221	0.87		TAAB46	3.00				
CA3007	2.63	2.34	CA3055	2.40	2.13	CA3076	1.30	1.16	SN7442	1.00	0.80	0.80	FJH101	1.37		TAAB47	3.10				
CA3008	1.80	1.60							SN7443	1.25	1.10	1.00	FJH121	1.87		TAAB48	3.20				
CA3008A	2.80	2.84							SN7444	1.25	1.10	1.00	FJH141	3.12		TAAB49	3.50				
CA3010	1.37	1.23							SN7447	1.10	1.00	0.90	FJH191	1.87		TAAB50	3.62				
CA3010A	2.53	2.25							SN7448	1.00	0.90	0.80	FJH211	1.87		TAAB51	3.80				
CA3011	0.74	0.65							SN7450	0.25	0.20	0.18	FJH261	3.12		TAAB52	4.30				
CA3012	0.89	0.78							SN7451	0.25	0.20	0.18	FJY101	0.80		TAAB53	4.45				
CA3013	1.05	0.94							SN7453	0.25	0.20	0.18				TAAB54	4.81				
CA3014	1.24	1.10							SN7454	0.25	0.20	0.18				TAAB55	5.70				
CA3015	2.09	1.86							SN7460	0.25	0.20	0.18				TAAB56	6.70				
CA3015A	3.40	3.03							SN7470	0.50	0.45	0.35				TAAB57	7.20				
CA3016	2.46	2.19							SN7472	0.40	0.35	0.30				TAAB58	7.20				
CA3016A	3.73	3.33							SN7473	0.45	0.40	0.35				TAAB59	7.20				
CA3018	0.84	0.75							SN7474	0.45	0.40	0.35				TAAB60	7.20				
CA3018A	1.10	0.99							SN7475	1.00	0.90	0.80				TAAB61	7.20				
CA3019	0.84	0.75							SN7476	0.45	0.40	0.35				TAAB62	7.20				
CA3020	1.26	1.13							SN7483	1.00	0.90	0.80				TAAB63	7.20				
CA3020A	1.80	1.43							SN7486	0.50	0.45	0.40				TAAB64	7.20				
CA3021	1.58	1.39							SN7487	1.00	0.90	0.80				TAAB65	7.20				
CA3022	1.30	1.18							SN7488	0.50	0.45	0.40				TAAB66	7.20				
CA3023	1.26	1.13							SN7490	1.00	0.90	0.80				TAAB67	7.20				
CA3026	1.00	0.90							SN7492	1.00	0.90	0.80				TAAB68	7.20				
CA3028A	0.74	0.65							SN7493	1.00	0.90	0.80				TAAB69	7.20				
CA3028B	1.05	0.94							SN7495	1.00	0.90	0.80				TAAB70	7.20				
CA3029	0.87	0.77							SN7496	1.00	0.90	0.80				TAAB71	7.20				
CA3029A	1.65	1.47							SN74107	0.45	0.40	0.35				TAAB72	7.20				
CA3030	1.37	1.23							SN74121	0.90	0.85	0.80				TAAB73	7.20				
CA3030A	2.53	2.25							SN74151	1.10	1.00	0.90				TAAB74	7.20				
CA3033	2.53	2.25							SN74153	1.90	1.70	1.50				TAAB75	7.20				
CA3033A	4.26	3.80							SN74154	2.20	1.45	1.80				TAAB76	7.20				
CA3035	1.23	1.10							SN74160/T157D1	1.80	1.70	1.60				TAAB77	7.20				
CA3038	0.73	0.65							SN74161	2.80	2.50	2.40				TAAB78	7.20				
CA3037	1.65	1.47							SN74164	2.20	1.95	1.80				TAAB79	7.20				
CA3037A	2.53	2.25							SN74165	2.20	1.95	1.80				TAAB80	7.20				
CA3038	2.53	2.25							SN74192	2.25	1.95	1.80				TAAB81	7.20				
CA3038A	3.40	3.03							SN74193	2.25	1.95	1.80				TAAB82	7.20				
CA3039	0.84	0.75														TAAB83	7.20				
CA3040	2.40	2.14														TAAB84	7.20				
CA3041	1.09	0.97														TAAB85	7.20				
CA3042	1.09	0.97														TAAB86	7.20				
CA3043	1.37	1.23														TAAB87	7.20				
CA3044	1.20	1.07														TAAB88	7.20				
CA3045	1.23	1.10														TAAB89	7.20				
CA3046	0.69	0.60														TAAB90	7.20				
CA3047	1.37	1.23														TAAB91	7.20				
CA3047A	2.53	2.25														TAAB92	7.20				
CA3048	2.04	1.81														TAAB93	7.20				

**A. MARSHALL & SON LTD.** See our Ad. on opposite page for Transistors, Diodes, Passive Components and P. & P. charges. Many more types in stock and arriving daily. PLEASE ENQUIRE.

LARGEST STOCK

WIDEST SELECTION

LOW PRICES AND RETURN OF POST SERVICE

TRANSISTORS Brand new and fully guaranteed. PLEASE NOTE:—Matching charge (Audio Transistors only) 12p extra per pair. Many more semi-conductors in stock. Please enquire for types not listed.

SILICON RECTIFIERS PIV 50 100 200 400 600 800 1000 1200 1400

DIODES AND RECTIFIERS IN914 0.07, IN916 0.07, IN4007 0.22, IS113 0.15, IS120 0.15, IS121 0.17, IS130 0.12, IS131 0.12, IS132 0.15, IS940 0.07, AA119 0.10, AA129 0.10, AA213 0.10, AA215 0.12

MAINS TRANSFORMERS 1 amp Charger, Sec. 0-3.5-9-18v Post and packing 0.22, 1 amp Charger, Sec. 0-3.5-9-18v Post and packing 0.22, 2 amp (Douglas) MT103 Sec. tappings from 6v to 50v, 2 amp (Douglas) MT104 Sec. tappings from 6v to 50v

TRIACS SC36D 1.00, SC36E 1.25, SC40D 1.20, SC41D 1.50, SC45D 1.20, SC46D 1.42, SC50D 2.00

Economy Range Triacs TC410 (Pressfit) 4 amp 100 PIV, TC420 (Pressfit) 4 amp 200 PIV, TC440 (Pressfit) 4 amp 400 PIV

THYRISTORS PIV 50 100 200 300 400 1A 0.25, 5A 0.47, 7A 0.55, TIC47 0.6 amp, 200 PIV 0.55, TIC44 0.6 amp 50 PIV 0.47

VEROBOARD 2 1/2" x 3 1/2" .15 Matrix .1 Matrix, 2 1/2" x 5" .01, 3 1/2" x 3 1/2" .01, 3 1/2" x 17" .01, 5" x 17" .01, 5 1/2" x 17" (Plain) .01, 5 1/2" x 17" (Bag) .01

RESISTORS 1/2 W & 1/2 W E24 Series. Carbon Film 1/2 W., 1/2 W. E12 Series. 1/2 watt 5% .01, 1/2 watt 10% .01, 1 watt 5% .01, 1 watt 10% .01

Wire Wound 2 1/2 watt 5% (up to 270 ohms only), 5 watt 5% (up to 8.2k ohms only), 10 watt 5% (up to 25k ohms only)

CAPACITORS. Polyester, ceramics, Polystyrene, silver mica, tantalum, trimmers etc. in stock, please enquire.

Electrolytics MFD. V. £ MFD. V. £ MFD. V. £ 1 18 0.07, 1 25 0.07, 1 32 0.07, 2 350 0.10, 2 5 16 0.07, 4 40 0.07, 4 350 0.11, 5 18 0.07, 5 50 0.07, 6 4 6 0.07, 8 450 0.15, 10 12 0.07, 10 25 0.07, 12.5 25 0.07, 16 15 0.07, 16 450 0.16, 25 6 0.07, 25 10 0.07, 25 25 0.07

THERMISTORS (MULLARD) R53 (STC) VA1010 0.12, VA1039 0.13, VA1077 0.20, K151 (Sic) VA1015 0.19, VA1040 0.12, VA1091 0.22, mens) IK VA1034 0.12, VA1066 0.12, VA1096 0.20, VA1005 0.15, VA1038 0.12, VA1074 0.12, VA1075 0.22, VA1097 0.20, VA1075 0.22, VA1097 0.20, VA1075 0.22, VA1097 0.20

PANEL METERS 38 SERIES—FACE SIZE 42 x 50 mm. All prices for 1-9 pieces. All meters D.C. 100 Microamp 2.00, 100 1.87, 100 1.75, 500 1.50, 500-50 1.87, 1000-100 1.87, 500-0-500 1.37

SPEAKERS (3 ohm) 10" x 6" 2.37, 9" x 4" 1.27, 8" x 5" 1.27, 7" x 4" 1.27, 5" x 3" 0.75

Log. and Lin. With switch .25, Wire-wound Pots (3 watts) .37, Twin-Ganged Stereo Pots. (Log. and Lin.) Less Switch 0.40

HEAT SINKS 4 1/2" x 4" x 1/2" Finned for Two TO-3 Trans. .47, 4 1/2" x 2" x 1/2" Finned for One TO-3 Trans. .47, For SO-1 0.025 For TO-18 0.025 Fined For TO-18 0.025 Fined For TO-18 0.025 Fined

ZENER DIODES 400 mV (from 3.3v to 33v) .05, 1 Watt (from 2.7v to 20v) .37, 10 Watt (from 3.5v to 100v) .52, 20 Watt BZ193 Series (from 7.5v to 75v) .52

Antex 15W. Soldering Iron .62, D.G. 30 W. Soldering Irons .10

POSTAGE AND PACKING CHARGES U.K. .12, EUROPE .25 (minimum), COMMONWEALTH (AIR) .65 (minimum)

ALL PRICES SUBJECT TO ALTERATION WITHOUT PRIOR NOTICE

Telex 21492 A. MARSHALL & SON LTD Tel: 01-452 0161/2/3 28 CRICKLEWOOD BROADWAY, LONDON, N.W.2

SEND 1/- (15 np) FOR NEW COMPREHENSIVE SEMI CONDUCTOR PRICE LIST. (24 pages) CALLERS WELCOME Hours: 9-5.30 pm Mon-Fri 9-1 pm Thurs 9-5 pm Sat

# BEST BUY IN TTL!!

SIEMENS QUALITY PLUS BARGAIN PRICES PLUS LST SERVICE - A full design range of high quality TTL available from LST your Officially Appointed Siemens Distributors

Part No.	Description	Equal to	1-24	25-99	100 up	Part No.	Description	Equal to	1-24	25-99	100 up	Part No.	Description	Equal to	1-24	25-99	100 up
FLH101	Quadruple 2-input NAND gate	7400	20p	16p	14p	271	Hex inverter with open collector output	7405	25p	21p	18p	141	Dual D-type edge triggered flip-flop	7474	46p	38p	33p
111	Triple 3-input NAND gate	7410	20p	16p	14p	281	BCD to decimal decoder TTL output	7442	£1-16	94p	81p	151	Quad bistable latch	7475	45p	40p	37p
121	Dual 4-input NAND gate	7420	20p	16p	14p	291	Quadruple 2-input NAND gate with open collector output	7403	20p	16p	14p	161	Decade counter	7490	80p	67p	57p
131	8-input NAND gate	7430	20p	16p	14p	341	Quadruple 2-input exclusive-OR element	7486	33p	27p	23p	171	Divide-by-12 counter	7492	85p	71p	61p
141	Dual 4-input NAND buffer	7440	24p	20p	17p	351	Schmitt Trigger	7413	35p	29p	25p	181	4-bit binary counter	7493	80p	67p	57p
151	Expandable dual 2-wide 2-input AND-OR-INVERT gate	7450	20p	16p	14p	361	Excess 3 to decimal decoder	7443	£1-45	£1-20	£1-08	191	4-bit shift register	7495	87p	72p	62p
161	Dual 2-wide 2-input AND-OR-INVERT gate	7451	20p	16p	14p	371	Excess 3 gray to decimal decoder	7444	£1-45	£1-20	£1-08	201	Synchronous up down 4-bit decade counter with one line mode control	74190	£1-80	£1-48	£1-27
171	Expandable 4-wide 2-input AND-OR-INVERT gate	7453	20p	16p	14p	381	Quad 2-input positive AND gate Totem pole output	7408	25p	21p	18p	211	Synchronous up down 4-bit binary counter with one line mode control	74191	£1-80	£1-48	£1-27
181	4-wide 2-input AND-OR-INVERT gate	7454	20p	16p	14p	391	Quad 2-input positive AND gate open collector	7409	25p	21p	18p	221	8-bit shift register	7491A	£1-28	£1-07	92p
191	Quadruple 2-input NOR gate	7402	20p	16p	14p	FLY101	Dual 4-input expander	7460	20p	16p	14p	231	4-bit shift register	7494	£1-13	94p	81p
201	Quadruple 2-input NAND gate with collector output	7401	20p	16p	14p	111	J-K master-slave flip-flop	7470	45p	37p	32p	241	Synchronous up down 4-bit decade counter	74192	£1-74	£1-45	£1-25
211	Hex inverter	7404	25p	21p	18p	121	Dual J-K master-slave flip-flop	7473	45p	40p	35p	251	(As above)—binary counter	74193	£1-74	£1-45	£1-25
221	Gated full adder	7480	67p	56p	48p	131	Dual J-K master-slave flip-flop with preset and clear	7476	45p	40p	36p	261	5-bit shift register	7496	£1-48	£1-22	£1-05
231	2-bit binary full-adder	7482	87p	73p	62p							271	Dual J-K master-slave flip-flop with preset and clear	74107	52p	43p	36p
241	Four-bit binary full adder	7483	£1-32	£1-16	£1-00							301	Dual quadruple bistable latch	74100	£1-64	£1-37	£1-17

Types may be mixed to qualify for price breaks

## CONTRACT ORDER PRICES AND BULK QUANTITY PRICES QUOTED ON REQUEST

AC107	37p	BYZ13	20p	NKT10439	27p	IN4007	20p
AC126	25p	BZ188	15p	NKT10519	22p	2G302	19p
AC127	25p	C18	15p	NKT20329	15p	2G301	19p
AC128	20p	C3V6	15p	0013	31p	2G371	15p
AC176	25p	C3V9	15p	NKT80111	67p	2G374	25p
AC187	30p	C4V3	15p	NKT80112	83p	2N174	80p
AC188	30p	C4V7	15p	NKT80113	83p	2N385A	75p
ACY17	29p	CSV1	15p	NKT80211	75p	2N388A	23p
ACY18	20p	CSV4	15p	NKT80212	75p	2N404	15p
ACY19	20p	CV2	15p	NKT80214	75p	2N696	15p
ACY20	19p	C6V8	15p	NKT80216	75p	2N697	17p
ACY21	19p	C7V5	15p	OA5	20p	2N698	30p
ACY22	19p	C8V2	15p	OA10	25p	2N706	10p
ACY40	15p	CV91	15p	OA47	8p	2N706A	12p
ACY41	15p	C10	15p	OA91	8p	2N708	16p
AD140	15p	C18	15p	OA73	8p	2N711	37p
AD149	57p	C12	15p	OA79	8p	2N711A	37p
AD161	37p	C13	15p	OA81	8p	2N911	50p
AD162	37p	C15	15p	OA85	8p	2N914	20p
AF114	25p	C16	15p	OA90	8p	2N918	42p
AF115	25p	C18	15p	OA91	8p	2N1090	30p
AF116	25p	C20	15p	OA95	8p	2N1091	33p
AF117	25p	C22	15p	OA200	10p	2N1131	30p
AF118	44p	C24	15p	OA202	10p	2N1132	30p
AF124	25p	C27	15p	OC19	37p	2N1302	20p
AF126	25p	C30	15p	OC20	37p	2N1303	20p
AF139	37p	DI171	15p	OC22	47p	2N1304	20p
AF186	37p	MJ520	75p	OC23	60p	2N1305	25p
AF239	37p	MJ480	97p	OC24	60p	2N1306	30p
ASY26	25p	MJ481	£1-25	OC25	37p	2N1307	30p
ASY27	30p	MJ490	£1-00	OC26	33p	2N1308	34p
ASY28	22p	MJ491	£1-35	OC28	60p	2N1309	31p
ASY29	30p	MPF102	43p	OC29	75p	2N1507	23p
ASY31	37p	MPF103	37p	OC35	50p	2N1613	22p
AU110	£1-50	MPF104	37p	OC36	63p	2N1711	25p
BA115	8p	MPF105	40p	OC41	25p	2N2147	82p
BC107	12p	NKT1124	30p	OC42	30p	2N2148	63p
BC108	12p	NKT1125	40p	OC44	15p	2N2160	17p
BC109	12p	NKT1126	31p	OC45	15p	2N2368	17p
BC147	15p	NKT1128	25p	OC71	15p	2N2369	17p
BC148	15p	NKT1135	26p	OC72	23p	2N2369A	20p
BC149	15p	NKT1137	32p	OC75	25p	2N2646	50p
BC158	17p	NKT1210	25p	OC76	23p	2N2904	44p
BC169C	19p	NKT211	25p	OC77	40p	2N2904A	44p
BC182	30p	NKT212	25p	OC81	23p	2N2905	65p
BC182L	10p	NKT213	25p	OC81D	20p	2N2905A	75p
BC183	9p	NKT214	23p	OC81Z	55p	2N2906	44p
BC183L	9p	NKT215	21p	OC82	25p	2N2906A	54p
BC184	15p	NKT216	46p	OC82D	15p	2N2926	all colours
BC184L	15p	NKT217	30p	OC83	43p	2N3051	10p
BC212	12p	NKT218	25p	OC84	25p	2N3052	10p
BC212L	12p	NKT219	25p	OC139	35p	2N3054	63p
BCY30	25p	NKT223	25p	OC140	35p	2N3055	75p
BCY31	48p	NKT224	25p	OC170	25p	2N3702	11p
BCY32	30p	NKT225	21p	OC171	30p	2N3703	10p
BCY33	20p	NKT229	29p	OC200	37p	2N3705	11p
BCY34	20p	NKT237	31p	OC201	47p	2N3705	10p
BCY38	30p	NKT238	19p	OC202	63p	2N3706	9p
BCY70	19p	NKT239	23p	OC203	37p	2N3707	11p
BCY71	37p	NKT240	20p	OC204	40p	2N3708	7p
BCY72	16p	NKT241	21p	OC205	65p	2N3709	9p
BD121	£1-10	NKT242	15p	OC206	65p	2N3710	9p
BD123	£1-10	NKT243	56p	OC207	75p	2N3711	9p
BD124	£1-03	NKT244	17p	OC207	75p	2N3819	35p
BDY20	£1-05	NKT245	17p	ORP12	50p	2N3820	60p
BF115	25p	NKT261	21p	ORP60	60p	2N3826	30p
BF163	40p	NKT262	19p	ORP61	60p	2N4058	19p
BF167	25p	NKT264	15p	P346A	19p	2N4060	20p
BF173	30p	NKT271	18p	ST140	15p	2N4061	20p
BF178	52p	NKT272	17p	ST141	20p	2N4062	20p
BF180	37p	NKT274	18p	TD716	60p	2N4284	15p
BF181	37p	NKT275	23p	TIP31A	62p	2N4287	15p
BF184	25p	NKT279A	12p	TIP32A	74p	2N4289	15p
BF185	25p	NKT281	65p	TIP8A	45p	2N4871	40p
BF194	17p	NKT302	87p	Y05A	46p	2N5245	45p
BF195	15p	NKT304	79p	ZTX108	11p	3N84	£1-30
BF196	15p	NKT351	75p	ZTX300	13p	3N128	69p
BF200	35p	NKT401	71p	ZTX302	18p	3N140	76p
BFX13	25p	NKT402	77p	ZTX303	18p	3N141	73p
BFX29	31p	NKT403	65p	ZTX304	27p	3N152	86p
BFX04	25p	NKT404	69p	ZTX314	11p	40250	55p
BFX85	34p	NKT405	79p	ZTX320	30p	40309	39p
BFX86	25p	NKT406	62p	ZTX330	18p	40310	45p
BFX87	30p	NKT420	£1-83	ZTX500	16p	40312	48p
BFX88	25p	NKT451	58p	ZTX501	16p	40320	35p
BFY50	23p	NKT452	58p	ZTX502	16p	40340	43p
BFY51	19p	NKT453	56p	ZTX503	17p	40361	48p
BFY52	20p	NKT603F	30p	ZTX504	40p	40362	58p
BFY53	16p	NKT613F	30p	IN34A	20p	40406	56p
BFY90	67p	NKT674F	30p	IN60	20p	40407	39p
BSX19	16p	NKT676F	30p	IN64	20p	40408	51p
BSX20	16p	NKT677F	28p	IN82A	47p	40409	54p
BSX21	35p	NKT713	25p	IN77A	23p	40477	35p
BSY27	20p	NKT717	44p	IN914	7p	40468A	35p
BSY29	25p	NKT734	26p	IN4001	7p	40600	58p
BSY95A	15p	NKT736	32p	IN4002	7p	40601	55p
BY100	20p	NKT773	25p	IN4003	10p	40602	40p
BYX10	15p	NKT778	29p	IN4004	10p	40603	49p
BYZ10	40p	NKT10339	25p	IN4005	12p	40603	49p
BYZ12	40p	NKT10419	19p	IN4006	15p	40673	90p

### ALL STOCKS ADVERTISED LAST MONTH STILL AVAILABLE

F NO GIMMICKS !! F  
 R Our catalogue is Free R  
 E postage appreciated (5p) E

### NEW PRODUCT !!

(Siemens Tantalum Bead Capacitors)

Mfd. Voltage	Mfd. Voltage
1 35	2 2
22 35	4 7
47 35	10 16
1 35	15 16
2 2	35 22
4 7	33 10
6 8	25 10
10 25	22 6.3
15 20	47 6.3
	100 3

Epoxy encapsulated miniature sinter Tantalum Electrolytics—polarized  
 Size example: 10mfd 16v 4.5 x 7.5 mm  
 All one price: 12p each; 25 pieces 1 type 10p each.

### BOOKS

- G.E. Transistor Manual £1-47
- R.C.A. Transistor Manual £1-40
- Designers' Guide to British Transistors (data book) £1-25
- R.C.A. Hobby Circuits Manual £1-40
- New edition now available. Many new circuits. Substitution chart supplied.
- 110 Semiconductor Projects £1-25
- Photo Diode Handbook 84p
- Zener & Solarcell Handbook 84p

### BZY88 SERIES ZENERS 400mw

5% tolerance  
 All voltages available 3.3 to 33 Volt  
 25 + 12p 100 + 10p  
 500 + 9p 1000 + 8p

### SPECIAL OFFER IN4000 SERIES 1 AMP RECTIFIERS

Part No.	p.i.v.	1-49	50 + 100 +
IN4001	50	070	060 050
IN4002	100	070	065 060
IN4003	200	090	085 070
IN4004	400	100	090 080
IN4005	600	120	100 090
IN4006	800	140	130 110
IN4007	1000	190	150 120

Should any item be out of stock we reserve the right to supply at higher voltage rated item at no extra charge.

TERMS: Cash with order please. Postage: 10p inland, 25p Europe, 60p elsewhere.  
 All goods carry manufacturers warranty. Counter Sales—Same Address.

# NOW ONE OF THE LEADING FRANCHISED SEMICONDUCTOR DISTRIBUTORS OFFERS NEW BRANDED DEVICES AT INDUSTRIAL TRADE PRICES

**MULLARD, INTERNATIONAL RECTIFIER, SENSITRON, S.G.S., NATIONAL SEMICONDUCTOR**

THIS IS THE FIRST TIME D.T.V. GROUP LTD. HAVE EXTENDED SALES OF THIS RANGE TO PRIVATE READERS OF WIRELESS WORLD

**BULK QUANTITY PRICES ON REQUEST**

WE HOLD ONE OF THE LARGEST SEMICONDUCTOR STOCKS IN THE U.K.



## LOW COST DIGITAL TTL 7400 RANGE FROM FRANCHISED DISTRIBUTOR STOCK

		(0°C to +70°C) Silicone Moulded Package		
Compare these prices!		1-24 £p	25-99 £p	100+ £p
DM7400N (SN7400N)	Quad Two-Input Gate ..	0.250	0.200	0.167
DM7401N (SN7401N)	Quad Two-Input Gate (Open Collector) ..	0.250	0.200	0.167
DM7402N (SN7402N)	Quad Two-Input NOR Gate ..	0.250	0.200	0.167
DM7403N (SN7403N)	Quad Two-Input Gate (Open Collector) ..	0.250	0.200	0.167
DM7404N (SN7404N)	Hex Inverter ..	0.275	0.225	0.188
DM7405N (SN7405N)	Hex Inverter (Open Collector) ..	0.275	0.225	0.188
DM7410N (SN7410N)	Triple Three-Input Gate ..	0.250	0.200	0.167
DM7420N (SN7420N)	Dual Four-Input Gate ..	0.250	0.200	0.167
DM7430N (SN7430N)	Eight-Input Gate ..	0.250	0.200	0.167
DM7440N (SN7440N)	Dual Four-Input Buffer ..	0.250	0.200	0.167
DM7450N (SN7450N)	Expandable Dual AND-OR-INVERT Gate ..	0.250	0.200	0.167
DM7451N (SN7451N)	Dual AND-OR-INVERT Gate ..	0.250	0.200	0.167
DM7453N (SN7453N)	Expandable AND-OR-INVERT Gate ..	0.250	0.200	0.167
DM7454N (SN7454N)	AND-OR-INVERT Gate ..	0.250	0.200	0.167
DM7460N (SN7460N)	Dual Four-Input Expander ..	0.250	0.200	0.167
DM7472N (SN7472N)	J-K Master Slave Flip Flop ..	0.325	0.263	0.221
DM7473N (SN7473N)	Dual J-K Flip Flop ..	0.525	0.417	0.350
DM7474N (SN7474N)	Dual D Flip Flop ..	0.450	0.363	0.300
DM7476N (SN7476N)	Dual J-K Flip Flop with Preset and Clear Inputs ..	0.563	0.450	0.375
DM7486N (SN7486N)	Quad Exclusive-OR Gate ..	0.575	0.488	0.425
DM74107N (SN74107N)	Dual J-K Flip Flop with Vcc and GND on Corners ..	0.525	0.417	0.350

## TRANSISTORS

### LARGE QUANTITY-PRICES ON APPLICATION

	1-24	25+		1-24	25+
BC 107	10p	8p	2N1132	25p	21p
BC 108	10p	8p	2N1303	16p	13p
BC 109	10p	8p	2N1304	22p	18p
BC 113	15p	13p	2N1305	22p	18p
BC 114	14p	12p	2N1613	20p	16p
BC 115	16p	14p	2N2193	27p	20p
BC 116	15p	13p	2N2218	23p	17p
BC 116A	19p	16p	2N2219	23p	17p
BC 118	10p	8p	2N2221	23p	17p
BC 125	20p	17p	2N2222	23p	17p
BC 126	20p	18p	2N2369	15p	12p
BC 147	10p	9p	2N2369A	18p	13p
BC 148	9p	8p	2N2484	27p	20p
BC 149	13p	12p	2N2904	31p	23p
BC 153	18p	16p	2N2907	30p	22p
BC 154	20p	17p	2N2924	13p	9p
BC 178	26p	23p	2N2925	14p	9p
BC 182	10p	9p	2N2926	8p	7p
BC 183	9p	8p	2N3011	15p	12p
BC 184	11p	9p	2N3053	18p	12p
BCY 58	25p	20p	2N3055	78p	62p
BCY 59	27p	22p	2N3133	22p	17p
BCY 70	17p	12p	2N3134	23p	18p
BCY 71	22p	15p	2N3135	23p	16p
BCY 72	12p	10p	2N3136	27p	22p
BF 115	18p	15p	2N3390	30p	25p
BF 167	21p	17p	2N3391	20p	17p
BF 173	24p	20p	2N3391A	22p	19p
BF 180	35p	28p	2N3392	13p	11p
2N697	15p	12p	2N3393	14p	12p
2N699	29p	22p	2N3414	14p	12p
2N706	11p	9p	2N3415	16p	15p
2N708	16p	14p	2N3643	27p	22p
2N722	79p	67p	2N3646	26p	21p
2N918	42p	36p	2N4392	£1.40	£1.20
2N929	17p	12p	2N4393	£1.42	£1.20
2N930	17p	12p			

## POWER DEVICES, SENSITRON GUARANTEED. INDUSTRIAL STOCK ITEMS

	1-99	100-999		1-99	100-999
2N3054	467	362	IN5171	171	121
2N3055	629	525	IN5172	183	129
2N3232	417	375	IN5173	237	167
2N3235	667	467	IN5174	300	212
2N3441	925	800	IN5400	162	112
2N3442	£1.700	£1.375	IN5401	183	129
2N3715	£1.467	£1.300	IN5402	204	146
2N3716	£1.637	£1.375	IN5403	221	154
2N3771	£1.700	£1.400	IN5404	267	187
2N3772	£1.800	£1.500	IN1199	392	308
2N3773	£2.875	£2.475	IN1202	775	633
2N4347	£1.050	875	IN1183	667	533
2N4348	£1.625	£1.375	IN1186	£1.108	887
STS1134	£2.950	£2.525			
IN5170	133	096			

Quantity Prices are Available on Request


## YOUR SMALL AUDIO AMPLIFIER PROBLEMS SOLVED WITH S.G.S. INTEGRATED CIRCUITS

### Audio Amplifier TAA 621

Designed for use in mains operated T.V. sets and record players as an audio amplifier. The supply voltage range is from 6 to 24V and the device can deliver up to 4W output power.
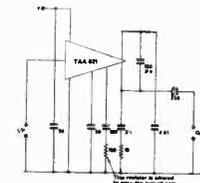
### Absolute Maximum Rating

Max. Supply Voltage (no signal): 27V; Power dissipation (TA=60°C) 1.06W; Input Voltage: -0.5 to 1.5Vp; Peak Output Current: 0.8A; Storage Temperature: -25 to 100°C; Junction Temperature: 125°C. 1-24 £2.025; 25-99 £1.755.



## EA 1000

### NEW COMPLETE MODULE

3 Watts min. output power; 50Hz-25Hz bandwidth. Signal to noise ratio-86dB. Complete with Capacitors and Resistors on 76 x 65 mm printed board; 1-24 £2.625; 24-99 £2.275. Supplied with data sheet and application report.

## ZENER DIODES

	1-19	20-99	100+
<b>BZY95 Series</b> 40p 32p 28p			
1.5 Watt			
±5%			
10 Volt			
75 Volt			
<b>BZX70 Series</b> 24½p 20p 17½p			
2.5 Watt			
±5%			
7.5 Volt			
75 Volt			
<b>IZMT10</b>	1-24	25+	
3.3 Volt-8.2 Volt	23p	19½p	
1 Watt ±10%			
<b>IZMT5</b>		25p	21p
3.3 Volt-8.2 Volt			
1 Watt ±5%			
<b>IZMT10</b>		15p	13p
9.1 Volt-33 Volt			
<b>IZMT5</b>		17½p	14½p
9.1 Volt-33 Volt			

## TRIACS

### SENSITRON AT NEW LOW PRICES

		Current Amps	P.I. Volts	1-99 £	100-999 £
SSC41B	6	200	0.865	0.693	
*SSC40B	6	200	1.016	0.814	
SSC41D	6	400	1.146	0.915	
*SSC40D	6	400	1.302	1.050	
SSC46B	10	200	1.167	0.932	
*SSC45B	10	200	1.318	1.050	
SSC46D	10	400	1.520	1.218	
*SSC45D	10	400	1.675	1.398	
SSC51B	15	200	1.201	0.966	
*SSC50B	15	200	1.352	1.075	
SSC51D5	15	400	1.806	0.882	
*SSC50D	15	400	1.953	1.562	
SSC61B	25	200	2.108	1.701	
*SSC60B	25	200	2.297	1.822	
SSC61D	25	400	3.008	2.402	
*SSC60D	25	400	3.192	2.541	

All ½ in. Press Fit. \* ½ in. Press Fit Stud

## SILICON RECTIFIERS, 1 AMP WIRE-ENDED PLASTIC

Type	P.I.V.	1-100	100+	1000+
IN4001	50	7p	6p	4p
IN4002	100	8p	7p	4p
IN4003	200	10p	9p	5p
IN4004	400	10p	9p	5p
IN4005	600	12p	10p	7p
IN4006	800	14p	12p	9p
IN4007	1000	16p	13p	10p

FOR INDUSTRIAL TRADE "SWIFT SERVICE" 60 PAGE CATALOGUE. SEND 35p. TERMS C.W.O. OR C.O.D. EXCEPT FOR EST. ACCOUNTS, GOVERNMENT DEPTS., ETC. PLEASE ADD 10p P.&P. (U.K.), 50p OVERSEAS

As these are trade prices it is regretted that we have to impose a minimum order value of £2.50 U.K., £5 overseas. Orders to:

**D.T.V. GROUP LTD** (Dept. M/OI), 126 HAMILTON ROAD, LONDON SE27 9 SG

Tel: 01-670 6166  
Telex 262145

# BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1  
THE VALVE SPECIALISTS Telephone 01-722-9090  
GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX. Littlehampton 6743

Please forward all mail orders to Littlehampton

0A2 0-80	6B87 1-25	6H87 0-53	128K7 0-24	50L6GT 4-5	DF96 0-35	BC386 0-40	EM81 0-40	PC88 0-49	PY83 0-27	UY85 0-27	1N4952 0-50	AF178 0-68	FSY28A 2-3	OC22 0-38
0B2 0-30	6B87 0-72	6H7GT 3-5	128Q7GT 7-2	0-33	DF97 0-43	EC388 0-35	EM83 0-75	PC95 0-53	PY88 0-33	U10 0-45	2N404 0-18	AF180 0-48	GD4 0-33	OC23 0-38
OZ4 0-23	6B87 0-57	6H7GT 3-5	128Q7GT 7-2	0-33	DF97 0-43	EC388 0-35	EM84 0-82	PC97 0-38	PY301 0-60	U12/14 0-38	2N966 0-53	AF181 0-70	GD5 0-28	OC24 0-38
1A3 0-23	6C4 0-25	6B87 0-38	14H7 0-48	85A2 0-43	DH76 0-28	ECC804 0-57	EM87 0-36	PC900 0-35	PY500 0-95	U16 0-75	2N1756 0-50	AF186 0-55	GD6 0-28	OC25 0-38
1A7GT 0-33	6C8 0-19	6U4GT 0-20	18A 0-63	85A3 0-40	DH77 0-20	ECC807 1-70	YV1 0-35	PC884 0-31	PY800 0-35	U17 0-35	2N2147 0-55	AF239 0-38	GD 0-20	OC26 0-38
1B3GT 0-37	6C9 0-73	6U7G 0-53	19A05 0-24	90AG 3-38	DH81 0-58	ECF80 0-28	YV1 0-35	PC885 0-29	PY801 0-34	U18/20 0-75	2N2297 0-23	ASV27 0-43	GD9 0-20	OC28 0-60
1D5 0-38	6CB6A 0-28	6V6G 0-17	1966 1-45	90AV 3-38	DH101 1-25	ECF82 0-23	YV1 0-35	PC888 0-44	PZ30 0-48	U19 1-73	2N2369A	ASV28 0-53	GD11 0-20	OC29 0-63
1D6 0-48	6C12 0-23	6V6GT 0-31	19H1 2-00	90C3 1-70	DK32 0-33	ECB86 0-45	YV1 0-35	PC890 0-46	QV03/10	U22 1-35	2N3866 1-00	ASV13 0-50	GD12 0-20	OC32 0-32
1FD1 0-35	6C17 0-43	6X4 0-22	20D1 0-66	90CV 1-83	DK40 0-55	ECF804	YV1 0-35	PC8189 0-49	1-20	U25 0-45	2N3013 0-39	BA102 0-45	GD14 0-50	OC36 0-43
1FD9 0-20	6C6DG 1-00	6X5GT 0-25	20D4 1-05	90C1 0-59	DK92 0-41	ECH21 0-63	YV1 0-35	PCF80 0-29	Q875/20	U26 0-59	2N3653 0-38	BA115 0-14	GD15 0-40	OC38 0-43
1G6 0-30	6C68A 0-50	6Y6G 0-55	20F2 0-66	150B2 0-58	DK92 0-41	ECH21 0-63	YV1 0-35	PCF82 0-31	0-63	U31 0-30	2N3121 2-50	BA116 0-25	GD16 0-20	OC41 0-50
1H5GT 0-33	6C86 0-38	6Y7G 0-63	20L1 0-88	150C2 0-30	DK96 0-36	ECH42 0-62	YV1 0-35	PCF84 0-40	Q885/10 49	U33 1-50	2N3708 0-20	BA129 0-13	GET111 7-8	OC42 0-63
1L4 0-13	6CL6 0-43	7A7 0-88	20P1 0-88	301 1-00	DL33 0-35	ECH81 0-28	YV1 0-35	PCF86 0-45	Q8150/15	U35 0-63	2N3709 0-20	BA130 0-10	GET113 2-0	OC43 1-18
1LD5 0-30	6CU5 0-50	7B9 0-58	20P3 0-84	302 0-93	DL92 0-27	ECH83 0-40	YV1 0-35	PCF88 0-23	FW4/80	U37 1-75	2N3866 1-00	BA133 0-15	GET116 0-40	OC44 0-10
1LNS 0-40	6CW4 0-63	7B7 0-35	20P4 0-91	303 0-75	DL94 0-32	ECH84 0-38	YV1 0-35	PCF90 0-27	FW4/500	U49 0-65	2N3985 0-50	BCY10 0-45	GET118 2-0	OC45 0-11
1NGT 0-37	6D3 0-38	7C6 0-30	20P5 1-00	305 0-63	DL96 0-36	ECH80 0-36	YV1 0-35	PCF820 0-40	R11 0-88	U49 0-65	2N3985 0-50	BCY12 0-50	GET119 2-0	OC46 0-15
1R5 0-27	6D6 0-15	7F8 0-88	25A6G 0-29	306 0-66	DM70 0-30	ECL82 0-31	YV1 0-35	PCF8020 0-40	R11 0-88	U49 0-65	2N3985 0-50	BCY33 0-20	GET153 3-8	OC45 1-18
184 0-24	6DE7 0-50	7H7 0-28	25L6G 0-22	807 0-59	DM71 0-38	ECL83 0-52	YV1 0-35	PCF805 0-63	R16 1-75	U50 0-28	AA129 0-15	BCY34 0-23	GET157 4-3	OC70 0-13
185 0-20	6D76 0-50	7R7 0-65	25Y5 0-38	956 0-10	DW4/350	ECL84 0-40	YV1 0-35	PCF806 0-58	R17 0-88	U76 0-24	AA129 0-15	BCY38 0-23	GET157 4-3	OC70 0-13
1U4 0-29	6F1 0-59	7T7 0-25	25Y6 0-43	1821 0-53	DY867 0-38	ECL85 0-55	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
1U5 0-43	6F6 0-33	7Z4 0-35	25Z4G 0-39	5702 0-22	DY867 0-38	ECL85 0-55	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
2D21 0-35	6F6G 0-25	8BW6 0-50	25Z5 0-40	5763 0-50	DY802 0-48	EE80 0-70	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
3A4 0-20	6F12 0-17	9D7 0-78	25Z6G 0-43	6060 0-30	E80F 1-20	EF22 0-83	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
3B7 0-25	6F13 0-33	10C1 1-25	30C1 0-29	7193 0-53	E83F 1-20	EF36 0-33	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
3D6 0-19	6F14 0-44	10C2 0-50	30C15 0-62	7475 0-70	E88CC 0-60	EF37A 0-45	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
3Q4 0-38	6F15 0-45	10C14 0-31	30C17 0-79	1A1834 1-00	E92CC 0-40	EF39 0-40	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
3Q5GT 0-35	6F18 0-45	10D1 0-50	30C18 0-83	A2134 0-98	E180F 0-95	EF40 0-50	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
384 0-27	6F23 0-70	10DET 0-60	30F5 0-70	A3042 0-75	E182CC	EF41 0-50	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
3V4 0-32	6F24 0-68	10F9 0-45	30FL1 0-62	AC044 1-16	E1148 0-53	EF42 0-33	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
5R4GY 0-36	6P25 0-80	10F18 0-35	30FL2 0-75	AC2PEN	E1148 0-53	EF42 0-33	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
5V4G 0-36	6P26 0-28	10D11 0-53	30FL12 0-71	0-98	E1148 0-53	EF42 0-33	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
5Y3GT 0-28	6P28 0-70	10P13 0-54	30FL14 0-70	AC2PEN/D	E1148 0-53	EF42 0-33	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
5Z3 0-45	6P32 0-13	10P14 1-10	30L1 0-31	EAB'90	E1148 0-53	EF42 0-33	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
5Z4G 0-35	6G6G 0-75	10P18 0-32	30L15 0-60	AC6/PEN	E1148 0-53	EF42 0-33	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
630L2 0-57	6H6GT 0-15	12A6 0-63	30L17 0-71	0-38	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6A80 0-33	6J5G 0-19	12AC6 0-40	30P4MR	AC/PEN(7)	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6A87 0-15	6J5GT 0-28	12AD6 0-40	0-88	0-88	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6A88 0-25	6J6 0-18	12AE6 0-48	30P12 0-89	AC/TH1	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6AK5 0-25	6J7G 0-24	12AT7 0-23	30P16 0-31	0-31	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6AK6 0-30	6J7GT 0-38	12AT7 0-17	30P18 0-31	AC/TP 0-98	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6AL5 0-11	6K7G 0-12	12AU6 0-22	30P19	AL60 0-78	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6AM4 0-88	6K7GT 0-20	12AU7 0-20	30P4 0-60	ARP 0-35	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6AM6 0-17	6K8G 0-16	12AV6 0-28	30P11 0-61	ATP4 0-12	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6AN8 0-49	6L1 0-98	12AX7 0-23	30P12 0-33	AZ1 0-40	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6AQ8 0-24	6L6GT 0-39	12AY7 0-38	30P13 0-78	AZ31 0-46	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6AR6 1-00	6L7GT 0-83	12BA6 0-30	30P14 0-67	AZ41 0-43	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6AT8 0-20	6L18 0-45	12BE6 0-30	30P15 0-89	B319 0-31	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6AU6 0-21	6L19 1-38	12BH7 0-27	35A3 0-50	CL33 0-91	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6AV6 0-30	6LD20 0-48	12E1 0-85	35A5 0-75	CV6 0-53	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6B8G 0-13	6N7GT 0-40	12J7GT 0-33	35D5 0-70	CV988 0-10	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6BA6 0-21	6P15 0-23	12K5 0-50	35L6GT 4-2	CY1C 0-53	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6BC8 0-50	6P28 0-59	12K7GT 0-34	35W4 0-22	CX31 0-82	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6BE6 0-22	6Q7G 0-30	12Q7GT 0-28	35Z3 0-50	D63 0-25	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6BH6 0-43	6Q7GT 0-43	12AT7GT	35Z4GT 2-4	DAC32 0-33	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6BJ6 0-40	6R7 0-35	0-40	35Z5GT 0-30	DAF91 0-20	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6BQ5 0-23	6R7 0-35	128C7 0-23	50B5 0-35	DAF96 0-35	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6BQT 0-38	6R7GT 0-35	128GT 0-23	50C5 0-32	D14 0-53	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6BR7 0-79	6R7GT 0-33	128H7 0-15	50C16G	DF33 0-37	EAC91 0-38	EF86 0-31	YV1 0-35	PCF808 0-27	R18 5-0	U78 0-22	AA213 0-18	BCY39 0-25	GET159 2-0	OC72 0-11
6BR8														

**SOLARTRON PULSE GENERATOR GP1101.2:** Period—2 microseconds to 100 msec; Pulse Duration—1 microsec to 100 msec; Delay time—1 microsec to 10 msec. All continuously variable in 5 ranges with fine control. Accuracy  $\pm 10\%$ . Pulse Amplitude—0.5V-100V. Accuracy  $\pm 10\%$  continuously variable in 4 ranges with fine control. Double Pulses; Pre-Pulse; Triggering; Square Wave O/put; Squaring Amplifier. Input—100-250V, 50-60 c/s. New condition with Manual. Price: £85 each + £1.25 carr.

**USM-24C OSCILLOSCOPE:** 3 in. oscilloscope with 2c/s to 10Mc/s vertical response, and 8c/s to 800Kc/s horizontal response. Sensitivity 50 mv. rms/inch. Triggered sweep, built-in trigger pulses and markers. Mains input 115V, 50c/s. Complete with all leads, probes and circuit diagram. £42.50 each, carr. £2.

**OS-46/U OSCILLOSCOPE:** A general purpose oscilloscope suitable for measuring signals from 0-1000V d.c. to over 50,000 c.p.s. (Further details on request, S.A.E.) £35 each, carr. £1.50.

**SIGNAL GENERATOR TS-403B/U (or URM-61A):** (Hewlett Packard). A portable, self-contained, general-purpose test equipment designed for use with radio and radar receivers and for other applications requiring small amounts of RF power such as measuring standing-wave ratios, antenna and transmission line characteristics, conversion gain, etc. Both the output freq. and power are indicated on direct-reading dials. 115V, AC, 50 c/s. Freq.—1800-4000 Mc/s. CW, FM, Modulated Pulse—40-4000 pulses per sec. Pulse Width—0.5-10 microseconds. Timing—Undelayed or delayed from 3-300 microseconds from external or internal pulse. O/put—1 milliwatt max., 0 to -127 db variable. O/put Impedance—50  $\Omega$ . Price: £120 each + £2 carr.

**SIGNAL GENERATOR TYPE 902:** (P.R.D.). A portable, general-purpose, broadband, microwave signal generator designed for testing and maintenance of aircraft radio and radar receivers in the SHF band. The RF output level is regulated by a variable attenuator calibrated in dbm. The frequency dial is calibrated in Mc/s. Provision is made for external modulation. Power Supply—115V,  $\pm 10\%$  A.C., 50  $\pm$  s. Freq.—3650-7300 Mc/s. Internal Transmission—CW, Pulse, FM. External Transmission—Square Wave, Pulse. Power O/put—0.2 milliwatts. O/put Attenuator: -7 to -127 dbm. Load—50  $\Omega$ . Price: £135 each + £2 carr.

**TEST SET TS-147C:** Combined signal generator, frequency meter and power meter for 8500-9600 Mc/s. CW or FM signals of known freq. and power or measurement of same. Signal Generator: O/put -7 to -85 dbm. Transmission—FM, PM, CW. Sweep Rate—0-6 Mc/s per microsec. Deviation—0-40 Mc/s per sec. Phase Range—3-50 microsec. Pulse Repetition Rate—to 4000 pulses per sec. RF Trigger for Sawtooth Sweep—5-500 watts peak. 0.2-6 microsec. duration, 0.5 microsec pulse rise time. Video Trigger for Sawtooth Sweep—Positive polarity, 10-50V peak. 0.5-20 microsec duration at 10% max. amplitude, less than 0.5 microsec rise time between 90% and 10% max. amplitude points. Frequency Meter: Freq. 8470-9360 Mc/s. Accuracy— $\pm 2.5$  Mc/s per sec. absolute,  $\pm 1.0$  Mc/s per sec. for freq. increments of less than 60 Mc/s relative,  $\pm 1.0$  Mc/s per sec. at 9310 Mc/s per sec. calibration point. Accuracy measured at 25° C and 60 humidity. Power Meter: Input: +7 to +30 dbm. Output -7 to -85 dbm. Price: £75 each + £1 carr.

**SIGNAL GENERATOR TS-418/URM49:** Covers 400-1000 Mc/s range. CW, Pulse or AM emission. Power Range—0-120 dbm. Price: £105 each + £1.25 carr.

**SIGNAL GENERATOR TS-497B/URR:** (Boonton). Freq. 2-400 Mc/s in 6 bands. Internal Mod. 400 or 1000 c/s per sec. External Mod. 50 to 10,000 c/s per sec. External PM. Percent Mod. 0-30 for sine wave. Am or Pulse Carrier. O/put Voltage 0.1-100,000 microvolts cont. variable. Impedance 50  $\Omega$ . Price: £85 each + £1.50 carr.

**FREQUENCY METER TS-74 (same TS-174):** Heterodyne crystal controlled. Freq. 20-280 Mc/s. Accuracy .05%. Sensitivity 20 mV. Internal Mod. at 1000 c/s. Power Supply—batteries 6V and 135V. Complete with calibration book. (Manufactured for M.O.D. by Telemax. "As new" in cartons.) £75 each. Fully stabilised Power Supply available at extra cost £7.50 each. Carr £1.50.

**CT.54 VALVE VOLTMETER:** Portable battery operated. In strong metal case with full operating instructions. 2.4V-480V. A.C. or D.C. in 6 Ranges, 10 to 10Meg $\Omega$  in 5 Ranges. Indicated on 4in. scale meter. Complete with probe, excellent condition. £12.50, carr. 75p.

**CT.381 FREQUENCY SWEEP SIGNAL GENERATOR:** 85Kc/s-30Mc/s and response curve indicator with 6in. CRT tube and separate power supply. Fully stabilised. Price and further details on request.

**CANADIAN HEADSET ASSEMBLY:** Moving coil headphones 100 $\Omega$  with chamois leather earmuffs. Small hand microphone complete with switch and moving coil insert. New Condition. £1.75 each, post 25p.

**HEADSET ASSEMBLY TYPE No. 10:** Moving coil headphones and microphone. (Similar to above) new cond. £1.75, post 25p; or second-hand cond. £1.25, post 25p.

**HEADSET ASSEMBLY:** with lightweight boom microphone. Good second-hand condition. £2.50, post 75p.

**DLR HEADPHONES:** 2  $\times$  balanced armature earpieces. Low resistance. £1.25 a pair, 25p post.

**POWER UNITS AVAILABLE FOR FOLLOWING SETS:** 52 set—mains input, 150V @ 60mA and 12V @ 3 amps, new cond. £3.50. Receiver type 88 (1475)—mains input, 250V @ 80mA and 6.3V @ 4 amps, new cond. £3.50. No. 19 set £2.50. C12 set £4.00. 88 set £2.50. Carriage all types £1 extra.

**STABILISED BENCH POWER SUPPLY:** fully smooth, dual output, positive or negative, 2-6V; 6-9V; 9-12V and 12-16V all at 2 amps d.c. from mains input. £25 + £2 carr.

**DIGITAL VOLTMETER & RATIO METER Model BIE. 2116,** £65, carr. £2. **DIGITAL VOLTMETER Model BIE. 2114,** £55, carr. £2. (Mnfrs. Blackburn Instruments).

**MARKA SWEEP GENERATOR MODEL VIDEO (Kay Electric, USA)** £65, carr. £2.

**ROTARY CONVERTERS:** Type 8a, 24 v D.C., 115 v A.C. @ 1.8 amps, 400 c/s 3 phase, £6.50 each, post 50p. 24 v D.C. input, 175 v D.C. @ 40mA output, £1.25 each, post 20p.

**CONDENSERS:** 40 mfd, 440 v A.C. wkg. £5 each, 50p post. 30 mfd 600 v wkg. d.c., £3.50 each, post 50p. 15 mfd 330 v a.c., wkg., 75p each, post 25p. 10 mfd 1000 v. 63p each, post 13p. 10 mfd 600 v. 43p each, 25p post. 8 mfd 2500 v. £5 each, carr. 63p. 8 mfd 600 v. 43p each, post 15p, 8 mfd. 1% 300 v. D.C. £1.25, post 25p, 4 mfd. 3000 v. wkg. £3 each, post 37p. 4 mfd 2000 v. £2 each, post 25p. 4 mfd 600 v., 2 for £1. 0.25 mfd, 2Kv, 20p each, post 10p. 0.01 mfd MICA 2.5Kv. £1 for 5, post 10p. Capacitor 0.125 mfd, 27,000 v. wkg. £3.75 each, 50p post.

**TCS MODULATION TRANSFORMERS,** 20 watts, pr. 6,000 C.T., sec. 6,000 ohms. Price £1.25, post 25p.

**SOLENOID UNIT:** 230 v. A.C. input, 2 pole, 15 amp contacts, £2.50 each, post 30p.

**CONTROL PANEL:** 230 v. A.C., 24 v. D.C. @ 2 amps, £2.50 each, carr. 75p. **OHMITE VARIABLE RESISTOR:** 5 ohms, 5 $\frac{1}{2}$  amps; or 40 ohms at 2.6 amps. Price (either type) £2 each, 25p post each.

**TX DRIVER UNIT:** Freq. 100-156 Mc/s. Valves 3  $\times$  3C24's; complete with filament transformer 230 v. A.C. Mounted in 19in. panel, £4.50 each, carr. 75p.

**POWER SUPPLY UNIT PN-12A:** 230V a.c. input 50-60 c/s, 513V and 1025V @ 420 mA output. With 2 smoothing chokes 9H, 2 Capacitors, 10Mfd 1500V and 10Mfd 600V. Filament Transformer 230V a.c. input. 4 Rectifying Valves type 5Z3. 2  $\times$  5V windings @ 3 Amps each, and 5V @ 6 Amp and 4V @ 0.25 Amp. Mounted on steel base 19"wx11"Hx14"D. (All connections at the rear.) Excellent condition £6.50 each, carr. £1.

**AUTO TRANSFORMER:** 230-115V, 50-60c/s, 1000 watts. mounted in a strong steel case 5"  $\times$  6 $\frac{1}{2}$ "  $\times$  7". Bitumen impregnated. £6 each, Carr. 63p. 230-115V, 50-60c/s, 500 watts. 7"  $\times$  5"  $\times$  5". Mounted in steel ventilated case. £3.50 each, Carr. 50p.

**LT TRANSFORMER:** PRI 230V. Output 4  $\times$  6.3 at 3 amps each winding, 3 $\frac{1}{2}$ "  $\times$  4"  $\times$  5". Fully shrouded £1.50 post 50p.

**MODULATOR UNIT:** 50 watt, part of BC-640, complete with 2  $\times$  811 valves, microphone and modulator transformers etc. £7.50 each, 75p carr.

**CATHODE RAY TUBE UNIT:** With 3in. tube, Type 3EG1 (CV1526) colour green, medium persistence complete with nu-metal screen, £3.50 each, post 37p.

**APN1 ALTIMETER TRANS./REC.,** suitable for conversion 420 Mc/s., complete with all valves 28 v. D.C. 3 relays, 11 valves, price £3 each, carr. 50p.

**ANTENNA WIRE:** 100 ft. long. 75p + 25p post.

**APN-1 INDICATOR METER,** 270° Movement. Ideal for making rev. counter. £1.25, post 25p.

**VARIABLE POWER UNIT:** Complete with Zenith variac 0-230V., 9 amps.; 2 $\frac{1}{2}$  in. scale meter reading 0-250V. Unit is mounted in 19 in. rack. £15 each, £1.50p carr.

**AIRCRAFT SOLENOID UNIT D.P.S.T.:** 24V, 200 Amps, £2 each, 25p post.

**RADAR SCANNER ASSEMBLY TYPE 122A:** Complete with parabolic reflector (24 in. diameter), motors, suppressors, etc. £35 each, £2 carr.

**DECADE RESISTOR SWITCH:** 0.1 ohm per step. 10 positions. 3 Gang, each 0.9 ohms. Tolerance  $\pm 1\%$  £3 each, 25p post. 90 ohms per step. 10 positions, total value 900 ohms. 3 Gang. Tolerance  $\pm 1\%$  £3.50 each, post 25p.

**MARCONI DEVIATION TEST SET TF-934:** 2.5-100Mc/s (can be extended up to 500Mc/s on Harmonics). Dev. Range 0-75Kc/s in modulation range 50c/s-15Kc/s. 100/250V. a.c. £45 each, £1.50 carr.

**CRYSTAL TEST SET TYPE 193:** Used for checking crystals in freq. range 3000-10,000Kc/s. Mains 230V, 50c/s. Measures crystal current under oscillatory conditions and the equivalent parallel resistance. Crystal freq. can be tested in conjunction with a freq. meter. £12.50 each, £1 carr.

**LEDEX SWITCHING UNIT:** 2 ledex switches, 6 Bank and 3 Bank respectively, 6 Pos.; 1 Manual switch, 16 Bank 2 Pos. £4 each, 50p post.

**GEARED MOTOR:** 24c. D.C., current 150mA, output 1 rpm, £1.50 each, 25p post. **ASSEMBLY UNIT** with Letcherbar Tuning Mechanism and potentiometer, 3 rpm, £2 each 25p post. **SYNCHROS:** and other special purpose motors available. List 3p.

**DALMOTORS:** 24-28V d.c. at 45 Amps, 750 watts (approx. 1hp) 12,000rpm. £5 each, 50p post.

**GEARED MOTOR:** 28V d.c. 150 rpm (suitable for opening garage doors). £4 each, 50p post.

**SMALL GEARED MOTOR:** 24V d.c., output 200 rpm. Meas'm'ts 1 $\frac{1}{2}$ in. dia.  $\times$  3 $\frac{1}{2}$ in. long. £2 each, 25p post.

**FUEL INDICATOR Type 113R:** 24V complete with 2 magnetic counters 0-9999, with locking and reset controls mounted in 3in. diameter case. Price £2 each, 25p post.

**COAXIAL TEST EQUIPMENT:** COAXSWITCH—Mnfrs. Bird Electronic Corp. Model 72RS; two-circuit reversing switch, 75 ohms, type "N" female connectors fitted to receive UG-21/U series plugs. New in ctns., £6.50 each, post 37p. CO-AXIAL SWITCH—Mnfrs. Transco Products Inc., Type M1460-2, 2 pole, 2 throw. (New) £6.50 each, post 25p. 1 pole, 4 throw, Type M1460-4. (New) £6.50 each, post 25p.

**PRD Electronic Inc. Equipment:** FIXED ATTENUATOR; Type 130c, 2.0-10.0 KMC/SEC. (New) £5 each, post 25p. FIXED ATTENUATOR; Type 1157S-1 (New) £6 each, post 25p.

**MOVING COIL INSERT:** Ideal for small speakers or microphones. Box of 3 £1, post 23p.

**HAND MICROPHONE:** (recent design) with protective rubber mouthpiece. £2, post 23p.

**MICROLINE IMPEDANCE METER MODEL 201:** 5300-8100Mc/s. £75 each, £1 carr.

**MICROLINE DIRECTIONAL COUPLER MODEL 209:** 5260-8100Mc/s. 24DB. £12.50 each, post 35p.

CALLERS BY TELEPHONE  
APPOINTMENT ONLY

W. MILLS

3-B TRULOCK ROAD, LONDON, N17 0PG

Phone: 01-808 9213

# Wilkinsons

EST. 1921

for RELAYS P.O. TYPE 3000 AND 600  
BUILT TO YOUR SPECIFICATION

Contacts up to 8 changeover

- ★ QUICK DELIVERY
- ★ KEEN PRICES
- ★ DUST COVERS—QUOTATIONS BY RETURN

UNISELECTORS AVAILABLE FROM STOCK: 3 LEVEL, 4 LEVEL, 5 LEVEL, 8 LEVEL, 11 LEVEL. WRITE OR PHONE FOR DETAILS.

METERS, DC Moving coil type, 2 in. flush round, complete with fixing clip, 3 types, 0-5 amp, 0-20 volts or 0-40 volts £2.75 each. New six-page instrument list now available. P.O. STANDARD EQUIPMENT RACKS. 6 ft. U channel sides, drilled for 19 in. panels. Heavy Angle Base £9.50 each. Cge. £1.50.

GEARED MOTORS. 1 r.p.m. or 3 r.p.m. 4 watts very powerful, reversible 24v. A.C. £1.75. post 20p. can be operated from A.C. mains with our £1 Transformer. Post 30p.

GEARED CAPACITOR MOTORS, 220/240v, 50cy., 30 watts, 300 r.p.m., also spindle for 1,425 r.p.m. Very powerful. £5 each. Post 50p.

MINIATURE DIGITAL INDICATOR, size of digit 1/4 in., 28 v. lamps, 0 through 9 with right and left hand decimal points, quick disconnect at rear for easy lamp replacement, when one of the twelve lamps at the rear of the unit is lighted, the lamp projects the corresponding digit on the condensing lens through a projection lens on to the viewing screen at the front of the unit. Brand new £2.50 each.

EQUIPMENT WIRE P.V.C. covered £4 per 1,000 yds. 7/0076, 14/0048 type I and 2, all colours. 14/0076 type II, Red and Natural only £10 per 1,000 yds.

MINIATURE BUZZERS, 12 volts, with tone adjuster 40p each as illustrated.

LEDEX ROTARY SOLENOIDS AND CIRCUIT SELECTORS, size 5S, 4 pole 11 way and off £5.50, 24 pole 11 way and off £10.50, 54 pole On/Off £7.50.


SINGLE FUSE HOLDERS. Belling Lee L356 one hole fixing. 10p each.

VEEDER-ROOT MAGNETIC COUNTERS WITH ZERO RESET 800 COUNTS PER MINUTE. 6 Figures. General Purpose Type. 110v. A.C. £5 post 20p.

Send for new potentiometer list, Wire Wound and Carbon types available from stock.
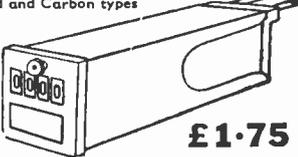
## HIGH SPEED COUNTERS

3 1/2 in. x 1 in. 10 counts per second, with 4 figures. The following D.C. voltages are available, 6 v., 12 v., 24 v., 50 v., or 100 v. Also supplied with auxiliary contacts, normally open 40p extra.



£1.75

**L. WILKINSON (CROYDON) LTD.**  
LONGLEY HOUSE LONGLEY RD. CROYDON SURREY

Phone: 01-684 0236 Grams: WILCO CROYDON

# BATTERY PORTABLE RECEIVER

SUPERHETERODYNE

## 8 WAVEBANDS. The most exciting radio ever!

Picks up ALL THE USUAL BBC Programmes. ★ All the new local radio stations. ★ Continental ★ World-wide transmissions. ★ Pop Pirates ★ Radio Hams. ★ Aircraft ★ Shipping. ★ Police. ★ Taxis. ★ R.A.C. ★ A.A. ★ Fire Brigades. ★ T.V. Sound. ★ Ambulances and 1000s more. THE BEST PORTABLE RADIO EVER MADE! We think so. What radio priced at under £120 gives you such a varied choice of transmissions? As well as the standard long and medium wavebands it has three shortwave bands (including the Marine and Trawler Band) AND NO LESS THAN THREE V.H.F. BANDS truly a complete WORLD-WIDE communications Receiver. Hours and hours of enjoyable listening. JUST THINK! one minute you can be listening to your favourite B.B.C. programme and then—at the flick of a switch—you can tune into the control tower and hear a crippled airliner being talked down to safety. Or listen to the trawlers and Ocean-going liners! Eavesdrop on the taxi-cabs, fire brigades, ambulances, A.A. R.A.C. and 100s of other R.T. mobiles—even your local police! Extensive shortwave coverage can give you Australia, Pakistan, Luxembourg, North America, Far East, etc., you name it—it gets it! Manufactured by one of the world's leading specialists in communications and T.V. equipment, each set carries a FULL 3-YEAR WRITTEN GUARANTEE. Beautifully finished in black leather and stainless steel—will add distinction to any living room. Completely portable. 12in. x 9in. x 4in. using standard batteries—or can be plugged directly into mains. 17 transistors, 8 diodes, 1 thermistor, internal ferrite rod aerial PLUS two external telescopic antennae—with sockets for additional aerials or car aerials. Complete with Beat Frequency Oscillator for the real enthusiast! Automatic Frequency Control—locks onto a station and ensures Drift-Free reception, Tone control. Fine squelch control. Hi-Fidelity earphone which automatically cuts out the main speaker when in use. local DX switch. FREQUENCIES: Long W 150-350 Kcs. Medium W 540-1650 Kcs. Marine 1.8-4 Mcs. Short W

1.3-7 Mcs. Short Wave 2 9-22 Mcs. F.M. (V.H.F.) 8-108 Mcs Aircraft (V.H.F.) 108-136 Mcs Public Service (V.H.F.) 148-174 Mcs

THE ULTIMATE in communications receivers—used by professionals and Amateur enthusiasts all over the world INSTANT CASH REFUND if not overwhelmed by the superb tone clarity and performance range

## CASH PRICE £47.50

Plus 50p post & packing or sent for £12.50 deposit and 6 monthly payments of £7. (Total Credit Price £54.40 + 50p p&p). Refund g'tee



ST SCIENTIFIC & TECHNICAL  
W W 1 507-511 LONDON ROAD, WESTCLIFF, ESSEX

WW—081 FOR FURTHER DETAILS

## 4-STATION INTERCOM



Our Price Only £6.75

Solve your communication problems with this new 4-Station Transistor Intercom system (1 master and 3 subs), in de luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Operates on one 9 v. battery. On/off switch. Volume control. Ideally suitable to modernise Office, Factory, Workshop, Warehouse, Hospital, Shop, etc., for instant inter-departmental contacts. Complete with 3 connecting wires, each 66 ft. and other accessories. Nothing else to buy. P. & P. £0.40 in U.K.

## INTERCOM/BABY ALARM



OUR PRICE ONLY £3.15

A top quality DE-LUXE transistorised intercom consists of MASTER and SUB for desk/wall mounting. Call, talk or listen from either unit. On/Off switch, volume control. Ideally suitable as "BABY SITTER" or Door Phone. A boon for spastics and invalids. Useful in the home, surgery or business for instant 2-way conversations, effective range 300ft. Unsurpassed in QUALITY AND PERFORMANCE. Complete with 66ft. connecting lead. Battery £0.12 extra. P. & P. £0.25. Price Refund if not satisfied in 7 days.

## TELEPHONE AMPLIFIER



£2.98

Why not increase efficiency of Office, Shop and Warehouse with this incredible De-Luxe Portable Transistor TELEPHONE AMPLIFIER which enables you to take down long telephone messages or converse without holding the handset. A useful office aid. A must for every telephone user. Useful for hard of hearing persons. On/off switch. Volume Control. Operates on one 9 v. battery which lasts for months. Ready to operate. P. & P. £0.18 in U.K. Add £0.12 for Battery. Full price refunded if returned in 7 days.

WEST LONDON DIRECT SUPPLIES (W.W.) 169 KENSINGTON HIGH STREET, LONDON, W.8

## IN 15 MINUTES YOU COULD HAVE CAPACITIVE DISCHARGE ELECTRONIC IGNITION FITTED TO YOUR CAR.

Capacitive Discharge Ignition is recognised as being the most efficient ignition system and will give you:—

- CONTINUAL PEAK PERFORMANCE
- UP TO 20% REDUCED FUEL CONSUMPTION
- EASIER ALL-WEATHER STARTING
- INCREASED ACCELERATION & TOP SPEED
- LONGER SPARK PLUG LIFE
- INCREASED BATTERY LIFE
- CONTACT BURN ELIMINATED
- PURER EXHAUST GAS EMISSION
- RADIO INTERFERENCE SUPPRESSED



For all petrol engines—cars boats etc. Guaranteed for 5yrs.

Complete Installation Kit for 12 volt vehicles £12.95 + 35p P&P. State earth polarity of vehicle—POSITIVE or NEGATIVE earth. Unit Construction Kit also available for the radio/electronics constructor £9.95 + 35p P&P. The construction kit includes instructions and all components for wiring as positive or negative earth, and is complete with the stove enamelled steel case and aluminium base. All components are available separately.

## ELECTRONICS DESIGN ASSOCIATES

82 BATH ST., WALSALL WS1 3DE.

WW—082 FOR FURTHER DETAILS

# VITAVOX

FOR HIGH QUALITY

## MICROPHONES

## LOUDSPEAKERS

and ancillary equipment

Further information from:

**VITAVOX LTD., Westmoreland Rd., London, NW9 5YB**  
(Tel: 01-204 4234)

WW083 FOR FURTHER DETAILS

# AUDIOTRINE A55 HIGH QUALITY STEREO SYSTEM

**5 + 5 WATT OUTPUT**  
Garrard 5200  
Changer with low  
mass pick-up arm  
and Stereo  
Cartridge.

Luxurious Teak Veneer Finished Cabinets. Trans-  
parent plastic (tinted) cover included for main unit.  
Silver finished fascia plate and  
matching control knobs.



**PAIR OF  
LOUDSPEAKER  
UNITS**

Incorporating high flux  
8 in. x 5 in. speaker.  
Size approx. 13 x 7 1/2 x 8 1/2 ins.

**PRICE COMPLETE  
ONLY**

**£42**

Carr. £1-25  
Terms: Deposit £5.50  
and 9 monthly payments  
£4.50 (Total £46).

Operation on 200-250 v. A.C.  
mains. Output rating I.H.F.M.

**A REALLY SURPRISING STANDARD OF QUALITY IS OBTAINED FROM THIS COMPACT LOW PRICED SYSTEM**

# FANE 807 HIGH FIDELITY LOUDSPEAKER

A full range  
8 in. 10 watt  
Unit for excellent sound quality in suitable  
enclosure. Roll P.V.C. cone surround and  
long throw voice coil to achieve very low  
fundamental resonance at 30 c.p.s. Tweeter  
cone is fitted to extend high note response.  
Frequency range 25 Hz to 15 KHz.  
Impedance 3Ω or 8-15Ω. Cast Chassis.  
**REMARKABLE VALUE AT ONLY £3-50**



**AUDIOTRINE HIGH FIDELITY  
LOUDSPEAKERS** Heavy  
construction. Latest high efficiency ceramic  
magnets. Treated Cone surround or "L"  
indicates Roll Rubber surround. "D"  
indicates Tweeter Cone providing  
extended frequency range up to 15,000  
c.p.s. Exceptional performance at low  
cost. Impedance 3 or 8-15 ohms.

**WHEN ORDERING PLEASE STATE IMPEDANCE**  
HF 801D 8" 8W £2-71 HF 120D 12" 15W £2-75  
HF 102D 10" 10W £3-40 HF 128 12" 15W £2-50  
HF 120 12" 15W £2-25 HF 128D 12" 15W £2-50

# FANE ULTRA HIGH POWER

**LOUDSPEAKERS** All power ratings are  
continuous.  
2 years' guarantee. High flux ceramic magnets.  
Heavy cast chassis. ALL CARRIAGE FREE.

- 'POP' 100 18in. 100 watt 14,000 gauss 8/15 ohms **£22-05**
  - 'POP' 60 15in. 60 watt 14,000 gauss 8/15 ohms **£12-90**
  - 'POP' 50 12in. 50 watt 13,000 gauss 15 ohms **£10-50**
- Dep.: £6 and 9 monthly payments £2-10 (Total £24-90)  
Dep.: £3-30 and 9 monthly payments £1-30 (Total £15)  
Dep.: £2 and 9 monthly payments £1-15 (Total £12-35)  
**PAIR SUITABLE ALL PURPOSES.**
- FOR BASS GUITAR OR ELECTRONIC ORGAN, ETC.

# FANE LOUDSPEAKERS 'POP' 25/2

Dual cone 15Ω (for users other than Bass Guitar or Electronic Organ. Carr. free.)  
Or dep.: £1 and 9 monthly payments 75p (Total £7-75)

# R.S.C. TA6 6 Watt High Fidelity Solid State Amplifier

200-250v. A.C. mains operated Frequency Response 30-20,000 c.p.s. —2dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 8-15 ohm speakers. Max. sensitivity 5mV. Output rating I.H.F.M. In fully enclosed enamelled case, approx. 9 1/2 x 2 1/2 x 4 1/2 in. Attractive brushed silver finish fascia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. Carr. 40p.  
**OR FACTORY BUILT WITH 12 months' g'tee. £9-75**

# R.S.C. BATTERY/MAINS CONVERSION UNITS

Type BML. An all-dry battery eliminator. Size 5 1/4 x 4 1/2 x 2 in. approx. Completely replaces batteries supplying 1.5 v. and 90 v. where A.C. mains 200/250 v. 50 c/s. is available.  
**COMPLETE KIT WITH DIAGRAM £3 OR READY FOR USE £3-00**

# HIGH QUALITY LOUDSPEAKERS

- In teak or afrormosia veneered cabinets.
- EL3 3 or 15 ohms. 13 x 8 in. 8-10 Watt Models
- Gauss 10,000 lines. Carr. 40p **£5-25**
- L12 12in. 20 Watt Model. Gauss 11,000 lines. Size 18 x 18 x 10 in. approx. 15Ω. Carr. 45p. **£10-50**
- Or dep. £3 and 9 monthly pmts £1. (Total £12)

# R.S.C. COLUMN SPEAKERS

Covered in Rexine and Vynair, ideal for vocalists and Public Address. Type C688, 30 watts. Fitted four 8 in. high flux 8w. speakers. Or dep. £3 **£17-75**

and 9 monthly pmts £2 (Total £21). Carr. 50p.

TYPE C1258, 50 watts. Fitted four 12 in. 11,000 lines 15 watt speakers. Or dep. £4 and 9 monthly pmts. **£27-50**

£3 (Total £31). Carr. 75p

# AUDIOTRINE HI-FI SPEAKER SYSTEMS


Consisting of matched 12in. 11,000 line 15 watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. Carr. 30p.

- OR SENIOR 15 WATT inc. HF126 15,000 lins Speaker **£6-75**
- HI-FI LOUDSPEAKER ENCLOSURES Teak or Afrormosia veneer finish. Modern design. Acoustically lined. All sizes approx. Carr. 25p extra.
- J28 Size 16 x 11 x 9 in. Pressurised. Gives pleasing results with any 8 in. HI-FI speaker. **£5-35**
- J29 For optimum performance with any 8 in. HI-FI speaker. **£6-47**
- SE10 For outstanding results with HI-FI 10 in. speaker. 24 x 15 x 10 in. Forged. **£6-74**
- SE12 For high performance with 12 in. HI-FI speaker and Tweeter. Size 22 x 15 x 10 in. Pressurised. **£7-87**
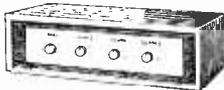
# R.S.C. G66 6+6 WATT HIGH QUALITY STEREO AMPLIFIER

Individual Ganged controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 transistors plus Diodes. Output rating I.H.F.M. Suitable for Crystal Pick-ups etc., and for loudspeaker output impedances of 3 to 15 ohms. For standard 200-250 v. A.C. mains operation. Attractive silver finished metal fascia plate and matching control knobs. Complete KIT of PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT, and comprehensive wiring diagram and instructions. Carr. 40p.  
**OR FACTORY BUILT IN Teak veneered cabinet as illustrated £12-99**

WHARFEDALE PAL PACKAGE OFFER 1 pair of Wharfedale Super Linton Speakers. Rec. Retail £49-90. 1 PAL Phase 32 HI-FI 15 + 15 watt stereo Amplifier Rec. Retail £37-80. Total **£87-70**. Package price **£66-50**. M.O. only.



# R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Full high output, with Pre-amp/Tone Control Stages. Hum level —70dB. Frequency response ±3dB 30-20,000 c/s. All high grade components. Valves EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls. Sensitivity 36 millivolts. Suitable for High Impedance mic. or pick-ups. Designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions, etc. For use with Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape, Receiver, L.T. and H.T. for Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram and "Mike" can be mixed. 200-250 v., A.C. For 3 & 15 Ω. **COMPLETE KIT PARTS, WIRING DIAGRAMS, INSTRUCTIONS. Twin-handled speakers. perforated cover £1-75.** Or factory built with EL34 output valves and 12 months' guarantee for **£19-75**. Tech. figs. apply to factory built units. Carr. 65p.  
**TERMS: Deposit £4 and 9 monthly payments of £2-10 (Total £22-90). Send S.A.E. for leaflet.**



# RSC BASS-REGENT 50 WATT AMPLIFIER


A powerful high quality, all purpose unit. For lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak output rating. Employing current valves and reliable components. FOUR JACK INPUTS and TWO VOLUME CONTROLS for simultaneous use of up to 4 pick-ups or 'mikes'. SEPARATE BASS and TREBLE CONTROLS. **OR SUPPLIED COMPLETE with matched twin loudspeaker unit as illustrated for £60.** Carr. £1-50. Terms: Dep. £18 and 9 monthly payments £5-75 (Total £67-75). **£30-50** Carr. 90p

# THE 'YORK' HIGH FIDELITY 3'SPEAKER SYSTEM

Moderate size (approx. 25 x 14 x 10 in.). Range 30-20,000 c.p.s. KIT COMPLETE Impedance 15 ohms. Performance comparable with units costing **£22** Carr. 63p considerably more. Consists of (1) 12 in. 15 watt Bass unit with cast chassis. Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system. (3) 8 x 5 in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Teak veneered cabinet. (7) Circuit and full instructions.  
**REMARKABLE VALUE HEAR IT AT ANY BRANCH**
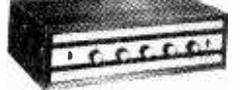
# TA12 MK III 6+5 + 6+5 WATT STEREO AMPLIFIER

FULLY TRANSISTORISED, SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL. Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge, Radio tuner, Tape recorder, 'P.U.' etc. 3 separate switched input sockets on each channel. \* Separate Bass and Treble controls. \* Slide switch for mono use. \* 8 speaker Output 3-15 ohms. \* For 200-250 v. A.C. mains. \* Frequency Response 20-20,000 c.p.s. —2dB. \* Harmonic Distortion 0.3% at 1000c.p.s. Hum and noise —70dB. \* Sensitivities (1) 50 mV (2) 400 mV (3) 100 mV \* Handsome finish. \* Facia Plate and Knobs. Output rating I.H.F.M. Complete kit of parts with full wiring diagrams and instructions. Carr. 40p.  
**FACTORY BUILT WITH 12 MONTHS' G'TEE. £19-50.** Or dep. £3 and 9 monthly pmts. **£2-15 (Total £22-35).** Or in Teak veneer housing. **£23.** Or Dep. £3 and 9 mthly. pmts **£2-55 (Total £25-95)**



SELENIUM RECTIFIERS F.W. Bridged 6/12v. D.C. Output Input Max. 18v. A.C. 1a., 25p; 2a., 35p; 3a., 50p; 4a., 65p; 6a., 80p.

# INTEREST CHARGES REFUNDED


On Credit Sales settled in 3 months

# R.S.C. MAINS TRANSFORMERS

- FULLY GUARANTEED.** Interleaved and Impregnated. Primaries 200-250v. 50c/s. Screened MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 in.
- 250-0-250v., 60mA, 6.3v. 2a. .... 90p
  - 250-0-250v., 60mA, 6.3v. 2a. .... 95p
  - FULLY SROUDED UPRIGHT MOUNTING**
  - 250-0-250v., 60mA, 6.3v. 2a., 0-5-6.3v. 2a. .... **£1-25**
  - 250-0-250v., 100mA, 6.3v. 4a., 0-5-6.3v. 3a. .... **£1-98**
  - 300-0-300v., 100mA, 6.3v. 4a., 0-5-6.3v. 3a. .... **£1-99**
  - 450-0-450v., 130mA, 6.3v. 4a., c.t., 5v. 3a. .... **£2-40**
  - For Mullard 510 Amplifier. .... **£2-40**
  - 350-0-350v., 100mA, 6.3v. 2a., 0-5-6.3v. 3a. .... **£1-99**
  - 350-0-350v., 150mA, 6.3v. 4a., 0-5-6.3v. 3a. .... **£2-40**
  - 425-0-425v., 200mA, 6.3v. 4a., c.t., 5v. 3a. .... **£2-49**
  - 425-0-425v., 200mA, 6.3v. 4a., 6.3v. 3a., 5v. 3a. .... **£2-69**
  - 450-0-450v., 250mA, 6.3v. 4a., c.t., 5v. 3a. .... **£2-69**
  - TOP SROUDED DROP-THROUGH TYPE**
  - 250-0-250v., 70mA, 6.3v. 2a., 0-5-6.3v. 2a. .... **£1-20**
  - 250-0-250v., 100mA, 6.3v. 3.5a. .... **£1-40**
  - 250-0-250v., 100mA, 6.3v. 2a., 6.3v. 1a. .... **£1-45**
  - 350-0-350v., 80mA, 6.3v. 2a., 0-5-6.3v. 2a. .... **£1-50**
  - 450-0-450v., 100mA, 6.3v. 4a., 0-5-6.3v. 3a. .... **£1-99**
  - 300-0-300v., 100mA, 6.3v. 4a., 0-5-6.3v. 3a. .... **£1-99**
  - 300-0-300v., 130mA, 6.3v. 4a., 0-5-6.3v. 1a. .... **£2-35**
  - Suitable for Mullard 510 Amplifier. .... **£2-35**
  - 350-0-350v., 100mA., 6.3v. 4a., 0-5-6.3v. 3a. .... **£1-99**
  - 350-0-350v., 150mA., 6.3v. 4a., 0-5-6.3v. 3a. .... **£2-35**
  - FILAMENT OR TRANSISTOR POWER PACK TYPES**
  - 300-0-300v., 100mA, 6.3v. 4a., 6.3v. 3a. .... **£1-99**
  - 6.3v. 6a. £1-15; 12v. 1a. 50p; 0.9-14v. 1.1a. 90p; 0.12-25-42v. 2a. £1-60; 12v. 3a. or 24v. 1.5a. £1-20;
  - CHARGER TRANSFORMERS 0.9-15v. 1.1a. 95p;**
  - 2.4a. 99p; 3a. £1-10; 5a. £1-30; 6a. £1-49;
  - 8a. £1-85
  - AUTO Step UP/STEP DOWN Transformers**
  - 0-110/120v. 200-230-250v. 50-80 watts. .... 99p
  - 150 watts, £1-70; 250 watts £2-49; 500 watts £5-25.
  - OUTPUT TRANSFORMERS**
  - Standard Pentode 5000 Ω to 7,000 Ω to 3 Ω 45p
  - Push-Pull 8 watts EL84 to 3 Ω or 15 Ω .... 75p
  - Push-Pull 10 watts 6V6 ECL86 to 3, 5, 8 or 15 Ω .... **£1-25**
  - Push-Pull EL84 to 3 or 15 Ω 10-12 watts. .... **£1-20**
  - Push-Pull Ultra Linear for Mullard 510, etc. **£1-99**
  - Push-Pull 15-18 watts, sectionally wound 6L6 K766, etc. for 3 or 15 Ω .... **£1-80**
  - Push-Pull 20 watt high quality sectionally wound EL34, 6L6, K766, etc. to 3 or 15 Ω .... **£2-99**
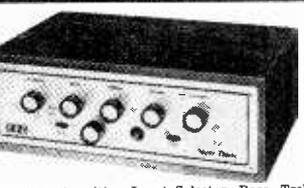
# R.S.C. SUPER 30 Mk II HIGH FIDELITY STEREO AMPLIFIER

**HIGH GRADE COMPONENTS. SPECIFICATIONS COMPARABLE WITH UNITS COSTING CONSIDERABLY MORE**  
Employing Twin Printed Circuits.  
200/250v. A.C. mains operation.  
**TRANSISTORS:** 9 high-quality types per channel.  
**OUTPUT (Per channel):** 10 Watts R.M.S. continuous into 15 Ω; 15 Watts R.M.S. continuous into 3 Ω.  
**INPUT SENSITIVITIES:** Mag. P.U. 4 m.v. Ceramic P.U. 35 m.v. Tape Amp. 400 m.v. Aux. 100 m.v. Mic. 5 m.v. Tape Head 2.5 m.v.  
**FREQUENCY RESPONSE:** ±2dB. 10-20,000 c.p.s.  
**TREBLE CONTROL:** +17 dB to —14 dB at 10 Kc/s.  
**BASS CONTROL:** +17 dB to —15 dB at 50 c/s.  
**HUM LEVEL:** —80 dB.  
**HARMONIC DISTORTION:** 0.1% at 10 Watts 1,000 c.p.s.  
**CROSS TALK:** 52 dB at 1,000 c.p.s.



**EMINENTLY SUITABLE FOR USE WITH ANY MAKE OF PICK-UP OR MIC.** (Ceramic or Magnetic, Moving Coil, Ribbon or Crystal) **CURRENTLY AVAILABLE. SUPERB SOUND OUTPUT QUALITY CAN BE OBTAINED BY USE WITH FIRST-RATE ANCILLARY EQUIPMENT. COMPLETE KIT OF PARTS, point to point wiring diagrams & detailed instructions £23-25** Carr. 75p  
**UNIT FACTORY BUILT £30-50**

**CONTROLS:** 5-position Input Selector, Bass, Treble, Vol., Bal., Stereo/Mono Sw., Tone Monitor Sw., Mains Sw.  
**INPUT SOCKETS:** (1) P.U. (2) Tape Amp. (3) Radio. (4) Mic. or Tape Head. (Operation of Input Selector assures appropriate equalisation).  
**CHASSIS:** Strong Steel construction. Approx. 12 x 3 x 8 in.  
**FACIA PLATE:** Attractive design in rigid "Perapex" with silver background. Spun silver matching control knobs as available.

- BRADFORD** 10 North Parade (Half-day Wed.). Tel. 25349
- BLACKPOOL** (Agent) O & C Electronics 227 Church St.
- BIRMINGHAM** 30/31 Gt. Western Arcade. Tel. 41361
- DERBY** 26 Osmaston Rd. The Spot (Half-day Wed.). Tel. 41361
- DARLINGTON** 18 Priestgate (Half-day Wed.). Tel. 68043
- EDINBURGH** 133 Leith St. (Half-day Wed.). Tel. 556 5766
- GLASGOW** 326 Argyle St. (Half-day Tues.). Tel. CITY 4158
- HULL** 91 Paragon Street (Half-day Thurs.). Tel. 20505

# R.S.C. HI-FI CENTRES LTD.

**MAIL ORDERS TO:** 106, Hencomer Lane, Leeds 13 Terms C.W.O. or C.O.D. Postage 25p extra under £2. 30p extra over £2, or as stated. Trade supplies S.A.E. with enquiries. EXPORT ENQUIRIES welcomed. Branches open ALL DAY SATS **MAIL ORDERS MUST NOT BE SENT TO SHOPS.**

- LEICESTER** 32 High Street (Half-day Thurs.). Tel. 56420
- LEEDS** 5-7 County (Mecca) Arcade, Briggate (Half-day Wed.) Tel. 28252
- LIVERPOOL** 73 Dale St. (Half-day Wed.). Tel. CENTRAL 3573
- LONDON** 238 Edgware Road, W.2 (Half-day Thurs.). Tel. PAD 1629
- MANCHESTER** 60A Oldham Street (Half-day Wed.). Tel. CENTRAL 2778
- MIDDLESBROUGH** 106 Newport Rd. (Half-day Wed.). Tel. 47096
- NEWCASTLE** UPON 41 Blackett Street (opp. Fenwicks TYNE Store) (Half-day Wed.). Tel. 21469
- SHEFFIELD** 13 Exchange Street (Castle Market Bldg.) (Half-day Thurs.). Tel. 20716

# R.S.C. PLINTHS

Superior Solid Natural Wood Construction for Record Playing units. Cut for Garrard 1025 2025, 3000, 8P25 etc. **£3-15** Available with Trans-parent plastic cover. **£6-30**

# RECORD PLAYING UNITS

- MONEY SAVING UNITS** Ready to plug into Amplifier.
- RP23C** Consisting of Garrard 8P25 Mk. III fitted Goldring C590 high compliance ceramic Stereo/Mono cartridge with diatremite stylus. Mounted on plinth. Transparent plastic cover included **£26-09** Carr. 50p
- RP6C** Garrard 5200 Auto Unit fitted Stereo Cartridge. Plinth and Cover as RP23C. Carr. 50p **£15**
- OTHER TYPES** with Magneto F.U. Cartridges and "Lift off" or "Roll over" transparent covers at lower prices.

**THIS MONTH'S NEW BARGAINS**

**TO 3 Heat Sink.** Suitable for most power transistors OC26, etc. This is aluminium, anodized black for maximum heat dissipation. Supplied complete with mica disc and insulation bushes. Price 10p each or 10 for 90p. Size approx. 2 1/2 x 3 1/2 ins.

**12 Volt 500 M.A. Mains Transformers.** Miniature type now available, price 55p each or 10 for 45p.

**Core Plate, New Colours.** 18" x 18" for live, blue for neutral, yellow/green for earth. This is completely P.V.C. covered and ribbed, virtually non-kinkable. Suitable for washing machines (without heaters) and all portable tools, lawn mowers, etc. Conductor size 23/36. 11 per dozen yards or 110 per 100-yard coil.

**Valve Holders** at remarkably low prices—moulded construction—made by most famous company. Price each:

- 1-9 10-99 100-999 1,000 up
- B7G Flanged .. 2p 1-5p 1-25p 1p
- B7G Skirted .. 3p 2p 1-75p 1-5p
- B7G Printed Circuit .. 2p 1-8p 1-2p 1-2p
- B9A Flanged .. 2p 1-6p 1-5p 1-1p
- B9A Skirted .. 2-5p 2-25p 2p
- B9A Printed Circuit .. 2p 1-8p 1-6p 1-3p

**MOTOR by A.E.I.** 1/20 hp, 1,275 rpm. Self-starting for normal A.C. Mains. A well-made enclosed motor with standard 1/2 in. dia. shaft 1 in. long. Suitable for light power operation. Continuous rating. £1.50 plus 20p post.

**Instrument Motor by Eveready—Hysteresis motor—maker's type No. FEK25—CG38—this is a capacitor start motor for 110V A.C. working, double-ended shaft. £3.50 plus 20p post and insurance.**

**Cut and Prepared 3 Core Leads.** 2 yards long, P.V.C. covered and ribbed virtually non-kinkable 23/36 conductors. Old colour scheme. 9p each, 10 for 70p. New colour scheme 15p each or 10 for £1.35.

**Hearing Aid Amplifiers.** (Ex behind ear deaf aids.) 3 transistors on tiny P.C. board with volume control—whole thing only about half as big as Oxo cube. £1.75 or with sub-miniature microphone and L.S. attached £3.50.

**Totally Enclosed Mains Transformer.** With primary for normal 230/240 50Hz mains and secondary rated at 4 amp 80V tapped at 75V and 70V. This is a very well-made transformer, totally enclosed in metal case. Size 4 1/2 in. x 5 1/2 in. x 6 1/2 in. high. Made to be mounted above chassis with terminations all on bottom. £3.50 each plus 65p post.

**8 Amp Variacs.** 0-250V—panel mounting type—excellent equipment, fully guaranteed £0 each. Carriage: England, £1; Wales and Scotland, £1.50.

**Water Switches.** Standard Size (1 1/2" high) built to Post Office spec., good contacts and generally very reliable. 9 pole, 3 way on 3 wafers, 45p; 10 for £4. Ditto 2 pole, 3 way 20p—10 for £1.80.

**P.O. Edge Connector.** 18 contact switch with 2 mounting/carrying lugs—30p each; 10 for £2.70.

**Pointer Knobs.** Bulgin brass insert type Ref. No. K.357. Black with white line down pointer. Grub screw fixing. 5p each—10 for 45p.

**Jack-socket.** Bulgin. Catalogue No. J14. This is a standard size panel mounting jack, with 20 leaf contact circuit switches incorporated. Maker's recommended price 41p. Our price 30p or 10 for £2.70.

**Miniature Water Switch.** 1 pole, 8 way. This has a short spindle and is therefore suitable only for mounting through a metal panel. Price 12p or 10 for £1.05.

**24 way Rotary Switch.** Single pole, £1.25; double pole, £1.95.

**Double-pole, Double-throw Toggle Switch.** Suitable for mains voltage and up to 10 amps, 15p or 10 for £1.35.

**Musio on Tapes.** Very Special Offer. Regular speed (3 1/2 i.p.s.). Mono tape recordings of popular long playing records. Each tape plays for approximately 15 minutes per track. These are on 5 in. spools but can easily be joined together to make a long tape for background music. We are offering these at less than one-third of the regular price.

**Classical Recordings Offer.** 32 recordings of all popular pieces, "Pomp and Circumstance Marche", "Nutcracker Suite" and others, all by famous composers. Total of 32 different recordings (giving a playing time of approx. 16 hours). Price £20.

**Popular Recordings Offer.** 36 recordings of popular music by Frank Sinatra, Dean Martin, Cliff Richards, Nat King Cole, etc. (giving a total time of approx. 18 hours). Price £22.

**Battery Model, Balfour Auto-charger.** As mains model but for 24V operation, also these are new ex-factory stock not returned export. Less cartridge £8 each plus 50p post and insurance.

**BREAK GLASS FIRE ALARM PUSH**

Made by AFA and used all over the country. Made from heavy cast steel. Drop front opened with Allen key for test. Switch normally closed, opens when glass is broken. Diameter approx. 5 ins. £1.25 or with cast steel mounting box £1.75. Post and ins. 20p.

**CAR ELECTRIC PLUG**

Fits in place of cigarette lighter. Useful method for making a quick connection into the car electrical system. 35p each or 10 for £3.42.

**ROCKER SWITCH**

13 amp self-fixing into an oblong hole. Size approximately 1 x 1 1/2 ins. 6p each, 10 for 54p.

**MAINS RELAY BARGAIN**

Special this month are some single, double and treble pole changeover relays. Contacts rated at 15 amps. Operating coil wound for 240V. A.C. Good British Make. Unused. Size approx. 1 1/2 x 1 ins. Open construction. Single pole 25p each 10 for £2.25. Double pole 32p each 10 for £2.90. Treble pole 40p each 10 for £3.60.

**PUSH BUTTON CHANGE OVER SWITCHES**

This is a Honeywell micro switch mounted on a metal frame with spring-loaded plunger to operate. Panel fixing by single 1/4 in. hole. Single Changeover switch 25p each or ten for £2.25. 2 changeover switch operated by single plunger 35p each or ten for £3.15.

**DRILL CONTROLLER**

New 1kW model. Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions £1.50, plus 13p post and insurance. Made up model also available £2.25 plus 13p p. & p.

**MAINS TRANSISTOR POWER PACK**

Designed to operate transistor sets and amplifiers. Adjustable output 6v, 9v, 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: P11, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 83p, plus 18p postage.

**HORSTMANN "TIME & SET" SWITCH**

(A 30 Amp Switch). Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fire, etc., up to 14 hours from setting time or you can use the switch to give a boost on period of up to 3 hours. Equally suitable to control processing. Regular price probably around £5. Special snip price £1.50 Post and ins. 25p.

**ERGOTROL UNITS**

These units made by the Mullard Group are for operating and controlling d.c. Motors and equipment from A.C. mains. Thyristors are used and these supply a variable d.c. resulting in motor speed control and operating efficiency far superior to most other methods.

The units are contained in wall mounting cabinets with front control panel on which are fuses—push buttons for on/off and the variable thyristor firing control.

4 models are available—all are brand new in makers cases:

- Model 2410 for up to 5 amps £17.50
- Model 2411 for up to 10 amps £27.50
- Model 2413 for up to 45 amps £47.50
- Model 2415 for up to 80 amps £95.00

Note: 2415 is a floor mounting unit.

**OUT OF SEASON BARGAIN**

**TANGENTIAL HEATERS**

Once again we are able to make a special bargain offer of these very popular heating units. Tangential heaters although brought out a few years ago are still the latest and best type as nothing has yet been made which could be called an improvement on them. The Tangential unit is still the only one used in good quality heaters made by Hoover, G.B.C. and all the famous names. The unit comprises quiet running AC induction motor with special bearings, the tangential impeller and a 2 section heater element which allows switching half and full heat in the case of the 2kw and one-third-two-thirds and full heat in the case of the 3kw. These heaters are also fitted with a safety cut-out to cut the heaters should the impeller stop or the air flow be impeded. They are free standing and need only the simplest of cases, even a wooden cabinet is suitable (or the plinth of the kitchen cabinet). Lots of customers missed our special summer offer of these heaters last year so order early. 200/240 2kw model £25.00. 200/240 3kw model £35.00. Control switch heaters only 25p or two-heat, cold-blow and off 35p. Postage and insurance 33p on heaters.

**AMPLIFIER MAINS TRANSFORMER**

50V 1 1/2 amp. Upright mounting with fixing brackets and metal shrouds to contain magnetic field. 50 c/s primary, tapped 110V, 117V, 210V, 230V and 250V 2 secondaries, one 50V 1 1/2 amp, other 6V 1 amp for pilot light, etc. £1.95, postage 30p.

**THIS MONTH'S SNIP**

**LIGHT DIMMER**

For any lamp up to 200 watt. Mounted on switch plate to fit in place of standard switch. Virtually no radio interference. Price £1.99 plus 20p post and ins.

**CAPACITOR DISCHARGE CAR IGNITION**

This system which has proved to be amazingly efficient and reliable was first described in the *Wireless World* about a year ago. We can supply kit of parts for improved and even more efficient version. Price £4.95 plus 30p post. When ordering please state whether for positive or negative systems.

**STANDARD WAFER SWITCHES**

Standard size 1/2 wafer—silver-plated 5-amp contact, standard 1/2" spindle 2" long—with locking washer and nut.

No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way
1 pole	40p	40p							
2 poles	40p	40p							
3 poles	40p	40p							
4 poles	40p	40p	40p	70p	70p	70p	70p	21.20	21.20
5 poles	40p	40p	70p	70p	95p	95p	95p	21.45	21.45
6 poles	40p	70p	70p	70p	95p	95p	95p	21.70	21.70
7 poles	70p	70p	70p	95p	21.20	21.20	21.20	21.65	21.65
8 poles	70p	70p	70p	95p	21.20	21.20	21.20	22.90	22.90
9 poles	70p	70p	95p	95p	21.45	21.45	21.45	22.45	22.45
10 poles	70p	70p	95p	21.20	21.45	21.45	21.45	22.70	22.70
11 poles	70p	95p	35p	21.20	21.70	21.70	21.70	22.95	22.95
12 poles	70p	95p	95p	21.20	21.70	21.70	21.70	23.20	23.20

**INSTRUMENT SWITCHES**

Precision made with diecast indexing mechanism. Full length 1/2 in. spindle, 5 amp and silver-plated contacts. Range except for 9-way, read 60p; for 70p, read £1; for 95p, read £1.40; for £1.20, read £1.80; for £1.45, read £2.20. Note also 2-way types available up to 36 poles; 3-way, 30 poles; 4-way, 24 poles; 5-way, 10 poles; but 10- and 12-way only available up to 6 poles.

**3 STAGE PERMEABILITY TUNER**

This Tuner is a precision instrument made for the famous Radiomobile Car Radio. It is a medium wave tuner (but set of long wave coils available as an extra if required) with a frequency coverage 1020 Kc/s-925 Kc/s and intended to operate with an I.F. value of 470 Kc/s. Extremely compact (size only 2 1/2 x 2 1/2 in. thick) with reduction gear for fine tuning. 65p, with circuit of front end suitable for car radio or as a general purpose tuner for use with Amplifier.

**ELECTRIC CLOCK WITH 20 AMP. SWITCH**

Made by Smith's these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set—also on the left is another time or alarm—this may be set in minutes up to 1 hour. At the end of the period a bell will sound. Offered at only a fraction of the regular price—£2.50, less than the value of the clock alone—post and ins. 15p.

**DISTRIBUTION PANELS**

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work £2.25 plus 13p; £2.50 with fitted 13 amp plug; £2.65 with fitted 15 amp plug, plus 23p P. & P.

Where postage is not stated then orders over £5 are post free. Below £5 add 20p. S.A.E. with enquiries please.

**MAINS OPERATED SOLENOIDS**

Model 772—small but powerful 1 1/2" pull—approx. size 1 1/2 x 1 1/2 x 1 1/2" 80p.  
Model 400/1 1/2" pull. Size 2 1/2 x 2 x 1 1/2" 75p.  
Model TT10 1 1/2" pull. Size 3 x 2 1/2 x 2 1/2" £1.80 plus 20p post and ins.

**DOOR INTERCOM**

Know who is calling and speak to them without leaving bed, or chair. Unit comprises microphone with call push button, connectors and main intercom. Simply plugs together. Originally sold at £10. Special snip price £2.50 plus 20p postage.

**MAINS CONNECTOR**

A quick way to connect equipment to the mains safely and firmly—disconnection by plugs prevents accidental switching on; has sockets which allow insertion of meter without disconnection; cable inlets firmly hold one hair wire on up to four 7,029 cables. 85p each.

**MINIATURE WAFER SWITCHES**

2 pole, 2 way—4 pole, 2 way—2 pole, 3 way—4 pole, 3 way—2 pole, 4 way—2 pole, 6 way 1 pole, 12 way. All at 18p each, £1.80 dozen, your assortment.

**WATERPROOF HEATING ELEMENT**

26 yards length 70W. Self-regulating temperature control. 50p post free.

**INVERTER UNITS**

Transistorised for working fluorescent lighting from 12V or 24V car batteries. For caravan lighting, mobile displays, etc. we have 7 types all made by the famous Philips Company all available at about half list price.

Type No. 126123. This is for working 3 miniature 6 watt 8" tubes from 12V battery. In sheet steel case. Size: 10" x 2 1/2" x 2" with connection diagram. Price £4.25.

Type No. 126328 for working one 2" 20 watt tube from 12V battery. This is on a metal plate which can also be used to hold the tube (using Terry clips). Price £3.50.

Type No. 126451 same as 126328 except that it works off 24V battery. Price £4.50.

Type No. 126345 same as 126328 except that it is for 21" tube of 24V. Price £3.75.

Type No. 59814 for working up to 6 9" miniature 6W tubes from 24V in pressed steel case. Size: 10" x 2 1/2" x 2" with connection diagram. Price £4.50.

Type No. 59801 for working one 2" 20W tube off 24V battery. This is in a pressed steel case. Size: 10 1/2" x 2 1/2" x 1 1/2" Price £3.50.

Type No. YB. This is a very big 24V unit. We have few details at present, but it weighs about 60lb and measures 24" x 8" x 7" approx. Generally it looks big enough to light a bus. It uses Mullard OC20 power transistors, in fact twenty-two of them. The input voltage is 24V d.c. and the output 220/240V a.c. Price £30 each, carriage at cost.

**COMPUTER TAPES**

2,400 ft. of the Best Magnetic Tape money can buy—users claim good results with Video and sound. 1 in. wide with cassette £1.45 plus 35p post and insurance. 1/2 in. wide with cassette £1.25 plus 30p post and insurance; 1/4 in. wide with cassette £1 plus 25p post and insurance. Spare spools and cassettes—1 in. £1. 1/2 in. 85p; 1/4 in. 75p each plus 20p post and insurance.

**BALANCED ARMATURE UNITS**

These Capsules are 1 in. diameter and 1/4 in. thick. They will operate as a microphone or loud speaker so can be used in intercom and similar circuits. 33p. Ten for £3.

**MULTI-SPEED MOTOR**

Replacement in many well-known food mixers. Six speeds are available 500, 850 and 1,100 r.p.m. from either or both of the nylon sockets (where the beaters of the food mixers normally go) and 8,000, 12,000 & 15,500 r.p.m. (ideal polishing speeds) from the main drive shaft. This drive shaft is 1/2 in. diameter and approximately 1 in. long. A further point about this motor is that being 230/240V. A.C.-D.C. series wound its speed may be further controlled with the use of our Thyristor controller. This is a very powerful and useful motor size approx. 2 in. dia. x 5 in. long, mains 230/240V. Price 85p plus 23p postage and insurance. 12 or more post free.

**MAINS OPERATED CONTACTOR**

220/240V. 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10 amps. Extremely well made by a German Electrical Company. Overall size 2 1/2 x 2 x 2 in. £1 each.

**QUICK CUPPA**

Mini Immersion Heater. 350W. 200/240V. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. £1.25, post and insurance 14p. 12V car model also available. Same price. Jug model also available £1.50 plus P. & P. 14p.

A New Service to Readers. A bulletin bringing news of new lines, special snips and "too few to advertise" lines will be posted to subscribers during first week of each month. The bulletin will be called "Advance Advert News" and the Subscription is 60p per year. Subscribers will also receive our completed 1971 catalogue when this is published.

Modern **TELEPHONES** type 706. Two-tone grey and two-tone green. £3.50 ea. P. & P. 25p ea. Brand new £6 ea. P. & P. 25p ea.

**STANDARD GPO DIAL TELEPHONES** (black) with internal bell. 87p. P. & P. 25p. Two for £1.50. P. & P. 37p.

**SURVEY METER RADIAC** No. 3. Hand portable size 94x5x5 1/2 ins. 3 ranges (scale changes) 0.03; 0.3; 3 R/H. Internal Ion Chamber. Nice condition £3 ea. P. & P. 50p.

**PHOTOMULTIPLIERS.** EMI 6097X at £8.50 ea. 6097B—£5 ea. Type 931A—£2.25 ea.

**SPECIAL OFFER**

5 in. Photomultiplier type, PDP84G by 20th Century. £3 ea. P. & P. 30p.

**TRANSISTOR OSCILLATOR.** Variable frequency 40 c/s to 5 kc/s. 5 volt square wave o/p. for 6 to 12v DC input. Size 1 1/2 x 1 1/2 x 1 1/2 in. Not encased. Brand new. Boxed. 57p ea.

**CRAMER TIMER** 28V DC Sweep 1/100th sec & sweep 60 secs. 4" dial. Remote control stop/start reset £5.00.

**RELAYS**

G.E.C. Sealed Relays High Speed 24V. 2m 2b—23p ea. S.T.C. sealed 2 pole c/o. 2,500 ohms. (okay 24v) 13p ea; 12v 35p ea.

**CARPENTERS** polarised Single pole c/o 20 and 65 ohm coil as new, complete with base 37p ea. Single pole c/o 14 ohm coil 33p ea; Single pole c/o 45 ohm coil 33p ea. Single pole c/o 4,000 ohm coil 33p ea. Varley VP4 Plastic covers 4 pole c/o 5K—30p ea. 15K—30p ea.

**POTENTIOMETERS**

**COLVERN** 3 watt. Brand new. 5; 10; 25; 50; 100; 250; 500 ohms; 1; 2.5; 5; 10; 25; 50k all at 13p ea. **MORGANITE** Special Brand new. 2.5; 10; 100; 250; 500K; 2.5 meg. 1 in. sealed. 17p ea.

**BERCO SQ.** Brand new. 5; 10; 50; 250; 500 ohms; 1; 2.5; 5; 10; 25; 50K at 25p ea.

**STANDARD** 2 meg. log pots. (Current type 15p ea. INSTRUMENT 3 in. Colvern 5 ohm 35p ea; 50k and 100K 50p ea.

**BOURNE TRIM POTS.** 10; 20; 50; 100; 200; 250; 500 ohms; 1; 2.5; 5; 25K at 35p ea.

**ALMA** precision resistors 100K; 400K; 497K; 998K; 1 meg—0.1%; 27p ea.; 3.25k 13K—0.1% 20p ea.

**DALE** heat sink resistors, non-inductive 50 watt. Brand new 8.2K at 13p ea.

**SILVER ZINC** Non-spill. Brand new. Single cell 1.5V 4AH size 1 1/2 x 1 x 3/4. 4oz. weight £1 ea.

**MALLORY CELLS.** 25p per set of 5.

**CAPACITORS**

**ERIE** feed through ceramic 2200 pf—4p ea. Sub-min. TRIMMER 1/2 square. 8, 5pf. Brand new 13p ea. Concentric TRIMMER 3/30 pf. Brand new 7p ea.

**ELECTROLYTICS.** Brand new. 250 mfd. 70V 23p ea. E.H.T. 2 mfd 5 KV. Brand new £1.50 ea.

**MULLARD ELECTROLYTICS.** Brand new. 2200 mfd 100VDCW. Size 1 1/2" dia x 4 1/2". Price 75p ea. Reduction for quantity.

**VISCONOL EHT Capacitors.** Brand New.

**VISCONOL EHT CAPACITORS**

Size 1 x 2 1/2 ins.		Size 1 1/2 x 5 1/2 ins.	
0.05mfd 2.5kV	50p ea.	0.01mfd 10kV	50p ea.
0.001mfd 5kV	40p ea.	0.002mfd 18kV	65p ea.
0.001mfd 10kV	50p ea.	0.05mfd 15kV	80p ea.
		0.01mfd 15kV	80p ea.
		0.0005mfd 20kV	80p ea.
		0.1mfd 7kV	40p ea.
		0.1mfd 5kV	35p ea.

Size 2 1/2 x 6 1/2 ins.  
0.05mfd 8kV 50p ea.  
Brand new 0.25mfd 5 KV. Dubilier 50p ea. P. & P. 15p.  
Rapid discharge 1mfd 5.6KV £1 ea. P. & P. 15p.

**DUBILIER.** Brand new. 1 mfd 15 KV 30KVt. £7 ea. Carr. £1.

**DECADE DIAL UP SWITCH.** Finger-tip. Engraved 0/9. Gold plated contacts. Size 2 1/2" high. 2 1/2" deep 1" wide. 75p ea. Bank of 4 with euscechon plates, etc. 2 1/2" high, 2 1/2" deep, 2 1/2" wide £2.50.

**PHOTOCELL** equivalent OCP 71 13p ea. Photo-resist type Clare 703. (T05 Case). Two for 50p.

**BURGESS** Micro Switches V3 5930. Brand new 13p ea. **HONEYWELL.** Sub-min. Microswitches type 11SM3-T. Brand new. 17p ea.

**PANEL** mounting lamp holders. Red or green. 9p ea.

**BRAND NEW PLUGS AND SOCKETS**

**CANNON.** 50 way DDM50P 75p ea.; DDM50S 50p ea. £1 per pair.

As above but 25 way 50p ea. plug; 35p ea. socket; 75p per pair; 9 way 33p ea. plug and socket, 50p per pair.

U.H.F. Plugs fit UR57, 59, 65 etc., 40p ea.  
B.N.C. to U.H.F. Adaptor £1.25 ea.; Min. B.N.C. to U.H.F. £1.50 ea.; 7" Junction B.N.C. £1 ea.; B.N.C. plug to B.N.C. plug £1 ea.; B.N.C. right angle £1 ea.; Min. B.N.C. right angle £1.25 ea.; Min. socket round 50p ea. Standard B.N.C. round 35p ea. Many others too numerous to list. All prices quoted for 'one off'.

**TRANSFORMERS.** All standard inputs.

**STEP DOWN ISOLATING** trans. Standard 240v AC to 120V tapped 60-0-60 700W. Brand new. £5 ea. As above 55-0-55V 300W. £3 ea. P. & P. 35p.

Neptune series 460-435-0 etc. 230 MA and 600-570-540-0 etc. 250 MA. £3.50 incl. post.

Multi 6.3Volts to give 48V 3.5Amps etc. £3.50 incl. post. Transformer 0-215-250 120 MA; 6.3V 4A CT x 2; 2 x 6.3V 0.5A and separate 90V 100 MA £1.25 ea. P. & P. 20p.

Matching contact cooled bridge rectifier 3p ea. 4.5V 40 amp (180Va) £1.75 ea. incl. postage or 3p for £4.50 incl. postage. Designed to be Series paralleled.

Parneko 6.3v 2 amp x 4—£1.13 ea.  
Gard/Parma/Part. 450-400-0-400-450. 180 MA. 2 x 6.3v. £3 ea.

**Transformer** 250-80MA; 13V-1.2A and 6.3V 5A. £1.50. P. & P. 25p.

**MARCONI** Wide Range Oscillator TF1370's and TF1370A's. 10c/s—10mc/s from £140.

**TEST GEAR**

**E.M.I. SOLARTRON** WM 2 DC—13 mc/s £25. CD1014 D.B. DC—6 megs. £55. 7118.2 D.B. DC—9 mc/s. In fine condition £50.

**SOLARTRON** 643 DC—15 mc/s Brand new £85. Good condition £50.

**SOLARTRON** DC—10 mc/s. CD513—£40. CD513-2—£42.50. CD523S—£45.

**SOLARTRON** CT916 (D300 range) DC—6 megs. £17.50.

**SOLARTRON** Storage scope QD910 £150. 1049 Mk. 3. DB. £25

**COSSOR** 13A DB. £25.

**HARTLEY** All carefully checked and tested. Carriage £1.50 extra.

**MARCONI**

Noise gen. TF1301. £40. Carr. £1.50. Vacuum tube Voltmeter TF1041A. £35; 1041B. £45.

Deviation Meter TF934/2. £50 ea. Carr. £1.50. Deviation type 719. £30 ea. Carr. 75p.

TF888 AM Portable Test Set 70 kc/s-70 m/c/s. Brand new crated. £40 ea. Carr. £1.25.

TF 1026 Frequency Meter £12.50. Carr. 75p. TF 329 Magnification Meter. As new condition £60.

TF 195 Audio Generator £10. Carr. £1.50. TF 801A Signal generator £35. Carr. £1.50.

Better grade £55 ea. Carr. £1.50. TF801B Sig Gen 10-500 mc/s from £150.

TF 886 Magnification Meter £45. Carr. £1. TF 369 N. 5 Impedance Bridge from £50 ea. Carr. £1.50.

TF 144G Signal Generator. Serviceable. Clean £15. In exceptional condition £25. Carr. £1.50.

Valve voltmeter type (T208. £17.50 ea. Carr. 75p. TF 885 Video Oscillator Sine/Square £35 Carr. £1.50.

TF885/1 £55. Carr. £1.54. TF 1343/2 'X' Band gen. £35. Carr. £1.50.

**SOLARTRON**

Laboratory amplifier AWW51A. 15c/s—350kc/s £35 Carr. £1

Stabilised P.U. SRS 151A £20. Carr. £1.50. Stabilised P.U. SRS 152 £15. Carr. £1.50.

Precision Millivoltmeter VP252. £25. Carr. £1. Process Response Analyser. Fine Condition £250

Oscillator type OS 101. £30. Carr. £1.50. D.C. Amplifier type AA900. £30. Carr. £1.

**AVO**

Testmeter No. 1 £12 ea. Carr. 75p. Electronic Testmeter CT 38. Complete £20 Carr. £1

**CINTEL**

Square and Pulse gen. PW 0/05 to 0.3 micro secs. 15mV to 50V; rep rate 5 hz to 250 kc £20. Carr. £1.

**AIRMEC**

Signal Generator type 701. £25. Carr. £1.50. AIRMEC Generator type 210 £120. Carr. £1.50.

**MARCONI TF 1277.** Colour studio scope, will line select. In superb condition. £120.

**E.M.I. Oscilloscope** type WM16. Main frame £125. Choice of Plug in 7/2 DC—24 mc/s x 2 £35; 7/1 DC—40 megs £25. Differential unit available from £40.

**E.M.I. WM8.** DC to 15 mc/s. Complete with plug in pre-amp. from £40.

**BRADLEY ATTENUATORS** 0/500 meg cycles. 0/12 db and 0/120 db—£20 per pair.

**BECKMAN MODEL A.** Ten turn pot complete with dial. 100k 3% Tol 0.25%—only £2.13 ea.

**E.H.T. Base** B9A in Polystyrene holder with cover. Brand new. 13p ea.

**DVM's** BIE 2114 £50 ea.; BIE 2116 £50 ea. Carr. £1.50.

**BC221**—Brand new £35 ea. Carr. £1. **NAGARD** Double pulse gen type 5002 £50. Carr. £1.50.

**MARCONI SPECTRUM ANALYSERS** type OA 1094, from £325.

**FIBRE GLASS PRINTED CIRCUIT BOARD.** Brand new. Single side 1p per sq. in. Double sided 1p per sq. in. Cut to size (Max. 2 1/2" x 15"). Postage 5p per order.

**BERCO** miniature variac type 31C. 0-250V 1 amp. 2 1/8" high, 3" diameter. Complete with dial and pointer. As new £3. P. & P. 37p.

**SEQUENTIAL TIMERS** 240V synchronous motor 1/2 rpm. 12 cam operated 2 pole micro switches. Individually adjustable from 0° to 180°. £6 ea.

Standard 240V MOTORS by CITENCO reduction gearbox to 19 r.p.m. reversible. £5 ea.

Single pole 3-way 250 V AC 15 amp switch. 8p ea. P. & P. 5p. Large discount for quantity.

Modern replacement for VCR 138 tube. Flat face 3 in. £1.63. P. & P. 25p. Bases 17p.

**FERRITE** rods complete with L.W. MW and coupling coils. Brand new. 25p ea. P. & P. 7p.

Squirrel cage **BLOWER ASSEMBLY** complete with standard mains input motor. Size 7" x 2 1/2" dia. only 80p ea. P. & P. 25p ea.

**DUNFOSS**—solenoid valves. 240V 50 c/s. Type EVJ 2. Brand new boxed £5; Second hand £3. P. & P. 30p.

**CLAUDE LYONS** Main Stabilizer. Type TS-1L-580. Input 119-135 volts 47/65 cs. Output 127+/-0.25% 16 amps. £35. Carr. £2.

**SERVOMEX.** Stab. Transistor P.U. 0-15V 2.5 amps. Volt and Current meters, overload trip. £15 ea. Carr. £1.50.

**E.H.T. Unit** by Brandenburg model S.0530/10. £55.

**MAGNETRONS TYPE CV370.** Brand new Boxed. £8 ea.

**KELVIN & HUGHES** 4-channel multi-speed recorders complete with amplifiers. £60 ea.

**EVERSHED & VIGNOLES** Recording paper. Brand new boxed. L618H4 7" wide, 1 1/2" dia. 17p roll; 8" dia. £1 roll. JL900H4 7" wide, 1 1/2" dia. 25p roll.

19in. Rack Mounting CABINETS 6ft. high 19in. deep. Side and rear doors. Fully tapped, £12.50. Carriage at cost.

Double Bay complete with doors. Fine condition. £25. Carriage at cost.

**ADVANCE** Sig. gen type D1. £15 ea. Carr. £1.50. Calibration unit type CT155. £6 ea. Carr. 50p.

Signal Generator CT53. Complete with charts £15. Carr. £1.50.

**TIME CALIBRATOR** unit by Cawell any or all time intervals from 0.5 microsecond to 1,000 microsecond. Internal calibration; gate generation £40. Carr. £1.50.

**WAYNE** Kerr Universal Bridge type CT375 £45 ea. Carr. £1.50.

**MUIRHEAD** Swept Audio Oscillator £50 ea. Carr. £1.50. EMI Swept Audio Oscillator type SRO2 £40 ea. Carr. £1.50.

Travelling **WAVE** oscilloscopes—Sweep speed from 10 micr secs to 10 nano secs. £150 ea.

**4 DIGIT RESETTABLE COUNTERS.** 1000 ohm. coil. Size 1 1/2" x 1" x 4 1/2 in. As new, by Sodeco of Geneva. £2.50 ea.

As above but 350 ohm. £3.50 ea.

**METERS**—Model 3705. 25-0-25 micro amp. Scaled. -100-0-+100. 5 1/2" x 4". £3 ea.

**SANGO** 50 micro amp 4" round. Brand new boxed. £1.38. P. & P. 38p.

**SANGO** 50 micro amp rectangular meter. Size 2 1/2" x 3" with 4 separate scales, lever operated, 0/6 white, 0/60 blue, 0/600 red and set zero. £1.75. P. & P. 17p.

**SANGO** 50 micro amp 3" round meters. Ex brand new radiation equip. £1 ea. P. & P. 17p.

**SEEING IS BELIEVING!**

**STILL AVAILABLE.** BC221 complete with correct charts, circuit diagrams, in fine condition for ONLY £13.34. Carr. £1.

**C.R.T.'s** 5" type CV1385/ACR13. Brand new with spec. sheet. 63p ea. P. & P. 35p.

**MARCONI** Valve Voltmeter 428B/1 £5 ea. Carr. £1.

**RESISTORS** by PIHER. Carbon Film. 1 and 2 watt. All 5%. Brand new Perfect. Mixed values. Only 50p per 1-lb. weight. P. & P. 12p.

**COSSOR D.B.** Scopes—some models from £15.

**MARCONI** Absorption Wattmeter 1 micro watt to 6 watts. Type TF956. FANTASTIC at £7 ea.

**SOLARTRON** Stab. PU AS516 & AS517. Circuits supplied. Fantastic value at £2 and £4 each.

**SUPERB BUYS.** Furzehill V200A Valve millivolt meter 10mv to 1 kv. £10 ea.

Genuine **MULLARD** Transistors/Diodes. Tested and guaranteed. OC41, 42, 76, 77, 83; OA5, 10. All at 3p ea. OC23—10p ea.

**MAINS MOTORS** Standard voltage. Size up on R/P tape recorders. Extremely quiet. Snp at 40p ea. P. & P. 15p ea.

**COMPONENT PACK** consisting of 2-2 pole 2 amp push on/off switches; 4 pots 1 double; 1-small double pole vol control; 250 resistors 1 and 1/2 watt many high stabs. Fine value at 50p per pack. P. & P. 17p.

3000 Series relays—15 mixed values (new and as new, no rubbish) £1.50. P. & P. 37p.

**STUART TURNER** No. 12 Water pump GPH720/10FT.HI) or GPH150/45FT.HI). Complete with standard mains input isolating transformer. Ideal fountains, waterfalls, etc. ONLY £5 ea. P. & P. £1.25.

Carriage extra.

**TRANSISTOR EHT INVERTORS.** 12 volt in, o/p (+ or -) 1.5 KV 2 MA and 3 KV +100 micro amp. Ideal CRT supply, photomultipliers etc. Full information supplied. Brand new at £6.50 ea. P. & P. 25p.

Also, as above but 1.5KV AC 20 kc/s. £3.50. P. & P. 25p.

Panel switches DPDT ex eq. 13p ea.; DPST Brand new, 17p ea.; DPST twice, brand new 25p ea.

**WAFER** Switches. 4 pole, 2 way. 13p ea. Brand new heads for TR50 and TR51 Tape Recorders £1.60.

**GYROS** Large clear plastic topped. Type A £5 ea. P. & P. 75p.

**ALBRIGHT** Heavy Duty Contactors. Single make. 200 amp. 24V coil. Brand new, boxed. £1 ea. incl. P. & P.

Official Orders Welcomed, Gov./Educational Depts., Authorities, etc., otherwise Cash with Order

FOR CALLERS. Always a large quantity of components, transformers, chokes, valves, capacitors, odd units, etc., at 'Chiltmead' prices. Callers welcome 9 a.m. to 10 p.m. any day.

**CHILTMEAD LTD**

7/9 ARTHUR ROAD, READING, BERKS. (rear Tech. College) Tel.: Reading 582605/65916

# STEPHENS ELECTRONICS, P.O. BOX 26, AYLESBURY, BUCKS.

SEND S.A.E. FOR LISTS GUARANTEE Satisfaction or money refunded

## GUARANTEED VALVES BY THE LEADING MANUFACTURERS BY RETURN SERVICE 1 YEAR'S GUARANTEE ON OWN BRAND, 3 MONTHS' ON OTHERS

AZ31	50p	E88CC	62p	EL803	85p	PC088	42p	PY83	50p	UL41	57p	6AR6	32p	6EW6	60p	68L7GT	32p	12K7GT	35p	35A5	55p
AZ50	60p	ECF90/2	47p	EL821	55p	PC088	70p	PY88	41p	UL84	50p	6AR6	32p	6EW6	60p	68L7GT	32p	12K7GT	35p	35B5	65p
CB11	80p	ECF86	55p	EL830	75p	PC089	61p	PY800	£1.00	UM90/4	45p	6AT6	45p	6FR6	45p	68G7	40p	128G7	25p	35C5	35p
CB131	80p	ECH35	67p	ELM34	80p	PC189	61p	PZ30	80p	UY41	40p	6AU6	30p	6F11	32p	6T8	32p	128H7	25p	35D5	65p
DAF91	31p	ECH42	66p	EM71	62p	PCF80	51p	QQU02-6	£2.10	UY85	34p	6AU6	30p	6F12	32p	6UAGT	62p	128J7	25p	35L6GT	47p
DAF96	41p	ECH81	51p	EM80	40p	PCF82	52p	QQU03-12	65p	W729	55p	6BE6	60p	6F13	35p	6U8	35p	128K7	40p	35W4	25p
DF91	45p	ECH83	40p	EM81	42p	PCF84	61p	R19	65p	Z759	£1.22	6BH6	42p	6F14	55p	6X4	25p	128L7GT	40p	35Z4	25p
DF96	45p	ECH84	47p	EM84	37p	PCF86	61p	R20	75p	OA2	32p	6B7	42p	6F15	45p	6X5GT	27p	128Q7	40p	35Z5GT	37p
DK91	57p	ECL50	40p	EM87	55p	PCP200/1	81p	R20	75p	OA3	45p	6BK7A	50p	6F18	40p	6F22	32p	128R7	32p	50A5	35p
DK96	57p	ECL83	57p	EY51	40p	PCF801	61p	SU2150A	75p	OAB	45p	6BN5	42p	6F22	32p	6X8	55p	128S7	32p	50B5	35p
DL92	37p	ECL86	49p	EY80	45p	PCF805	65p	TT22	£2.50	OB3	50p	6BN6	42p	6F23	77p	6Y6G	60p	1487	80p	50A5	65p
DL94	37p	ECL800	£1.50	EY81	40p	PCF806	61p	U18/20	67p	OC3	35p	6BN6	40p	6F26	35p	7Y4	60p	20D1	45p	50B5	35p
DL96	45p	EF39	52p	EY83	55p	PCF806	67p	U20	67p	OD3	32p	6BQ5	25p	6F26	35p	9BW6	42p	20L1	£1.00	50C5	35p
DM70	32p	EF80	40p	EY86	40p	PCF800	70p	U25	75p	OF2	30p	6BR7	75p	6F28	70p	10D1	40p	20P3	60p	50L6GT	40p
DM66/7	40p	EF83	50p	EY87	42p	PCL82	51p	U26	75p	384	35p	6BR8	95p	6F29	32p	10D2	40p	20P4	£1.00	83A1	30p
DY802	42p	EF85	41p	EY88	27p	PCL83	61p	U31	45p	3V4	40p	6BW6	82p	6F29	32p	10P1	30p	20P5	£1.00	85A2	37p
E551	£2.75	EF86	68p	EZ35	27p	PCL84	51p	U37	£1.50	5E4GY	55p	6BW7	69p	6F30	30p	10P9	50p	25C5	45p	90AU5	£2.40
E580C	40p	EF89	40p	EZ88	27p	PCL85	52p	U50	30p	5U4G	30p	6BX6	25p	6J4	47p	10P8	40p	25L6GT	37p	90C1	£2.40
E130L	£4.50	EF91	42p	EZ40	45p	PCL86	51p	U52	30p	5U4GB	37p	6BZ6	32p	6J7	42p	10L11	55p	25Z6GT	50p	90C2	£1.25
E180F	80p	EF92	50p	EZ41	45p	PD500	£1.82	U78	74p	U78	25p	5V3GT	30p	6CGT	30p	6K7	32p	10P13	45p	30A5	40p
EAB080	52p	EF93	47p	EZ80	27p	PLF200	74p	U78	25p	5V3GT	30p	6CGT	30p	6CA4	27p	6K8G	30p	10P14	£1.00	30A6	40p
EAF42	50p	EF94	77p	EZ81	27p	PL36	64p	U191	75p	5Z3	45p	6CD6G	£1.40	6CA7	27p	6K23	50p	12AB5	50p	30C15	75p
EBC33	55p	EF95	62p	EZ90	25p	PL38	90p	U193	41p	5Z4GT	40p	6CA4	27p	6CB2	27p	6K23	50p	12AC6	37p	30C17	80p
EBC41	47p	EF183	56p	G810C	£5.00	PL81	61p	U201	35p	6/30L2	75p	6CA7	27p	6CB2	27p	6K23	50p	12AD6	37p	30C18	80p
EBC81	32p	EF184	35p	GY501	30p	PL81A	62p	U202	40p	6AB4	32p	6CB2	27p	6CD6GA	£1.15	6L7	35p	12A15	40p	30C15	75p
EBC90	47p	E280F	£2.10	GZ30	37p	PL82	36p	U282	40p	6AFA	47p	6CG7	45p	6CH6	55p	6L8	30p	12AQ5	40p	30FL1	75p
EBF80	40p	EF900	£1.00	GZ31	30p	PL83	51p	U403	50p	6AFA	47p	6CG7	45p	6CH6	55p	6L8	30p	12AQ5	40p	30FL2	92p
EBF83	40p	EF904	£1.00	GZ32	47p	PL84	41p	U404	37p	6AG7	37p	6CH6	55p	6LD20	32p	12AT6	25p	30FL2	92p	6080	£1.37
EBF89	40p	EF811	75p	GZ33	37p	PL500	82p	U801	£1.00	6AH6	50p	6CL6	50p	6LN7GT	62p	12AV6	30p	30FL13	50p	6146	£1.50
EB91	20p	EL34	52p	GZ34	55p	PLB04	85p	UABC80	52p	6AJ8	29p	6CY6	40p	6P1	60p	12AV7	45p	30L1	45p	6267	32p
EC33	50p	EL36	47p	HL90	32p	PL505	61p	UAB79	40p	6AK5	30p	6CY7	60p	6P25	61p	12AX7	30p	30L15	85p	6360	32p
EC86	60p	EL41	57p	HL92	30p	PL508	£1.00	UBC41	45p	6AK6	57p	6D3	40p	6P28	67p	12AY7	67p	30L17	85p	6360	32p
EC88	60p	EL42	57p	HL94	40p	PL509	£1.54	UCC85	48p	6AL3	42p	6D6C	67p	6Q7	37p	12B4A	50p	30P12	80p	6939	£2.10
EC90	30p	EL41	50p	KT66	£1.37	PL802	86p	UCH42	69p	6AL5	15p	6DQ6B	60p	6R2	40p	12BA6	32p	30P18	35p	7199	75p
EC92	32p	EL83	41p	KB88	£1.66	PL805	86p	UCH81	54p	6AM5	20p	6DQ6B	60p	6R4	50p	12BA7	32p	30P19	75p	7360	£1.80
EC93	47p	EL85	42p	N78	£1.05	PY33	62p	UCL82	51p	6AM6	22p	6D84	75p	6R4	50p	12BE6	32p	30P11	77p	7586	£1.25
EC98	40p	EL86	42p	PA36	40p	PY60	35p	UCL83	61p	6AM6	22p	6E8A	55p	6R7	60p	12C7	32p	30P13	80p	9002	32p
ECC82/3	42p	EL90	33p	PC86/8	51p	PY81	61p	UP4/2	55p	6AM6	22p	6E8A	55p	6S7	37p	12D7	32p	30P14	85p	9003	50p
ECC82/3	42p	EL91	25p	PC85	36p	PY800	41p	UP80/5	37p	6AM6	22p	6E8A	55p	6S7	37p	12D7	32p	30P14	85p	9003	50p
ECC84/5	42p	EL95	35p	PC87	41p	PY801	41p	UP80/5	37p	6AM6	22p	6E8A	55p	6S7	37p	12D7	32p	30P14	85p	9003	50p
ECC88	55p	EL360	£1.15	PC84	46p	PY82	35p	UP89	41p	6AR5	32p	6EJ7	35p	6S7	37p	12K5	32p	30P14	85p	9003	50p

### CATHODE RAY TUBES

New and Budget tubes made by the leading manufacturers. Guaranteed for 2 years. In the event of failure under guarantee, replacement is made without the usual time wasting forms.

Type	New	Budget	Type	New	Budget
MW36-20	£4.50	£4.50	A50-120W/R	CME2013	£10.85
MW36-21	£4.50	£4.50	AW53-80		£28.93
MW43-69Z	CRMI171	£26.80	AW53-88	CME2101	£28.93
	CRMI172	£26.80	AW59-80		£29.58
MW43-80Z	CRMI173	£26.80	AW59-90	CME2303	£27.20
AW43-80Z	CME1702	£26.80	AW59-15W	CME2301	
	CME1703	£26.80		CME2303	£20.58
	CME1706	£26.80	A59-11W	CME2305	
	C17AA	£26.80	A59-13W	CME2306	£13.05
	C17AF	£26.80	A59-16W	CME2307	£10.97
AW43-88	CME1705	£26.80	A59-23W	CME2305	£12.60
AW47-90			A59-23W/R	CME2413	£12.60
AW47-91	A47 14W	£25.95	A65-11W	CME2501	£16.50
A47 14W	CME1901	£25.95			
	CME1902	£25.95			
	CME1903	£25.95			
A47-11W	C19AH	£25.95			
A47-13W	CME1905	£28.86			
A47-26W	CME1906	£10.27			
A47-26W/R	CME1905	£28.86			
	CME1913R	£20.33			

### COLOUR TUBES

A49-191X	19 inch	£52.50
A56-120X	22 inch	£57.50
A56-111X	25 inch	£62.50

### PORTABLE SET TUBES

TSD217	£11.50
TSD282	£11.50
A28-14W	£20.16

Not supplied  
£7.75  
£8.00

### TRANSISTORISED UHF TUNER UNITS NEW AND GUARANTEED FOR 3 MONTHS

Complete with Aerial Socket and wires for Radio and Allied TV sets but can be used for most makes. Continuous Tuning, £4.50; Push Button, £5.00.

### SERVICE AIDS

Switch Cleaner, 55p; Switch Cleaner with Lubricant, 55p; Freeza 62p. P. & P. 7p per item.

### PLUGS

Jack Plugs and Sockets			Co-Axial Plugs		
Standard Plugs	19p		Belling Lee (or similar type)	61p	
Standard Sockets	12p		Add 2p per doz. p. & p.		

### LINE OUTPUT TRANSFORMERS

G.E.C. BT454	£4.75	G.E.C. 2028	£4.75
G.E.C. BT456	£4.75	G.E.C. 2041	£4.75
G.E.C. 2010	£4.75	G.E.C. 2000 Series	
G.E.C. 2013	£4.75	Phillips 19TG	£4.75
G.E.C. 2014	£4.75	Fye Mod. 36	£4.75
G.E.C. 2018	£4.75	Fye Mod. 40	£4.75
G.E.C. 2043	£4.75	Fye Mod. 45	£4.75
G.E.C. 2048	£4.75	Thorn 800-850	£4.75

### STYLII—BRITISH MANUFACTURED

All types in stock		Double Tip "S"	33p
Single Tip "C"	13p	Double Tip "D"	47p
Single Tip "D"	37p		

A discount of 10% is also given for the purchase of 3 or more tubes at any one time. All types of tubes in stock. Carriage and insurance 75p anywhere in Britain.

### SEMICONDUCTORS BRAND NEW MANUFACTURERS MARKINGS NO

2N368A	62p	R.C.A.	AF106	42p	BC142	30p	BF224	30p
2N614	20p	40253	P.A. AF114	35p	BC143	30p	P.A. BF225	30p
2N697	20p	40398	P.A. AF116	30p	BC147	17p	BF257	47p
2N698	25p	40458	P.A. AF116	25p	BC148	15p	BF254	30p
2N706	12p	2N4061	AF117	25p	BC149	17p	BFY19	33p
2N706A	12p	2N4062	AF118	25p	BC152	17p	BFY50	22p
2N890	27p	2N4286	AF119	20p	BC157	20p	BFY51	22p
2N1132	32p	2N4291	AF124	22p	BC158	17p	BFY52	22p
2N1303	17p	AC107	AF125	30p	BC169B	14p	BCX21	37p
2N1305	22p	AC117	AF126	20p	BC169C	15p	OC25	50p
2N1306	25p	AC126	AF127	17p	BC171	17p	OC26	32p
2N1307	25p	AC127	AF129	37p	BC175	27p	OC28</	

# SERVICE TRADING CO

Postage and Carriage shown below are inland only. For Overseas please ask for quotation. We do not issue a catalogue or list.

## VARIABLE VOLTAGE TRANSFORMERS

INPUT 230 v. A.C. 50/60

OUTPUT VARIABLE 0/260 v. A.C.

BRAND NEW. Keenest prices in the country. All types (and spares) from 1/2 to 50 amp. available from stock.

- 0-260 v. at 1 amp. . . . . £5-50
- 0-260 v. at 2.5 amps. . . . . £6-75
- 0-260 v. at 5 amps. . . . . £9-75
- 0-260 v. at 10 amps. . . . . £18-50
- 0-260 v. at 15 amps. . . . . £25-00
- 0-260 v. at 20 amps. . . . . £37-00
- 0-260 v. at 25 amps. . . . . £49-00
- 0-260 v. at 37.5 amps. . . . . £72-00
- 0-260 v. at 50 amps. . . . . £92-00



OPEN TYPE (Panel mounting). 1/2 amp. £3-93  
1 amp £5-50, 2 1/2 amp. £6-63. P. & P. 40p.

## RING TRANSFORMERS

Functional Versatile Educational

These multi-purpose Auto Transformers, with large centre aperture, can be used as a Double wound current Transformer, Auto Transformer, H.T. or L.T. Transformer, by simply hand winding the required number of turns through the centre opening. E.g. Using the RT.100 V.A. Model the output could be wound to give 8V @ 12Amp., 4V @ 25Amp. or 2V @ 50Amp., etc. Price: RT.100VA 3.18 turns per volt, £2-25+28p p. and p. RT.300VA 2.27 turns per volt, £4-20+38p p. and p. RT.1KV 1.82 turns per volt, £6-50+58p p. and p. RT.2KVA 1.5 turns per volt, £10-50+80p p. and p. RT.3KVA 1.5 turns per volt, £14-00+80p p. and p.



## L.T. TRANSFORMERS

Type No.	Sec. Taps	Price	Carr.
1	12 v. at 5A	£1-88	28p
2	30, 32, 34, 36 v. at 5 amps.	£4-68	45p
3	30, 40, 50 v. at 5 amps.	£6-88	45p
4	10, 17, 18 v. at 10 amps.	£4-95	45p
5	6, 12 v. at 20 amps.	£6-43	45p
6	17, 18, 20 v. at 20 amps.	£7-28	55p
7	6, 12, 20 v. at 20 amps.	£6-88	55p
8	24 v. at 10 amps.	£5-23	35p
9	4, 6, 24, 32 v. at 12 amps.	£7-15	45p

## ALARM BELL

Manufactured by GENTS. 6 inch bell, 3/6 volt D.C. operation. As NEW. Only £1.50 plus 45p P. & P.

## LIGHT SOURCE AND PHOTO CELL MOUNTING

Precision engineered light source with adjustable lens assembly and ventilated lamp housing to take MBC bulb. Separate photo cell mounting assembly for ORP.12 or similar cell with optic window. Both units are single hole fixing. Price per pair £2-75 p & p 18p.



## LIGHT SENSITIVE SWITCHES

Kit of parts including ORP.12 Cadmium Sulphide Photocell. Relay Transistor and Circuit. Now supplied with new Siemens High Speed Relay for 6 or 12 volt operations. Price £1-25, plus 12p P. & P. ORP. 12 and Circuit 63p post paid.



## 220/240 A.C. MAINS MODEL

incorporates mains transformer rectifier and special relay with 1 make, 1 break, H.D. contacts. Price inc. circuit £2-38, plus 20p P. & P.

## 200-250 v. A.C. NEON INDICATOR

Available in RED or AMBER at 30p each, or in GREEN at 32p. Min. order 3 units. P. & P. 5p.

## MOTOROLA MAC11/6 PLASTIC TRIAC 400 PIV 8 AMP

Now available EX STOCK supplied complete with full data and applications sheet. Price £1-05 plus 7p P. & P. Suitable diac 30p (RCA40583)

## ELECTRONIC ORGAN KIT



Easy to build, solid state. Two full octaves (less sharps and flats). Fitted hardwood case, powered by two penlite 1 1/2 batteries.

Complete set of parts including speaker, etc., together with full instructions and 10 tunes. £3-00. P. & P. 25p.

## 50 in 1 ELECTRONIC PROJECT KIT

50 easy to build Projects. No soldering, no special tools required. The Kit includes Speaker, meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound level Meter, 2 Transistor Radio, Amplifier etc., etc. Price £7-75. P. & P. 30p.

## CRYSTAL RADIO KIT

Complete set of parts including: crystal diode, ferrite aerial, drilled chassis and personal ear-piece. No soldering, easy to build, full step-by-step instructions. £1-75 inc. post.

## POWER RHEOSTATS

(NEW) Ceramic construction, winding embedded in Vitreous Enamel, heavy duty brush assembly designed for continuous duty. AVAILABLE FROM STOCK IN THE FOLLOWING II VALUES:

100 WATT I ohm 10a., 5 ohm 4.7a., 10 ohm 3a., 25 ohm 2a., 50 ohm 1.4a., 100 ohm 1a., 250 ohm .7a., 500 ohm .45a., 1k ohm 280mA., 1.5k ohm 230mA., 2.5k ohm .2a., 5k ohm 140mA., Diameter 3 1/2 in. Shaft length 3/4 in. dia. 3/8 in., £1-50. P. & P. 15p. 50 WATT I.12/10/25/50/100/250/500/1K/1.5K/2.5K/5K ohm. All at £1-12. P. & P. 11p. 25 WATT 10/25/50/100/250/500/1K/1.5K/2.5K ohm. All at 78p. P. & P. 5p.

Black Silver Skirted knob calibrated in Nos. 1-9. 1 1/2 in. dia. brass bush. Ideal for above Rheostats, 18p ea.

## UNISELECTOR SWITCHES-NEW 4 BANK 25 WAY FULL WIPER

25 ohm coil, 24 v. D.C. operation £5-88. plus 22p P. & P.

## 6 BANK 25 WAY FULL WIPER

25 ohm coil, 24 v. D.C. operation. £6-50, plus 22p P. & P.

## 8 BANK 25 WAY FULL WIPER

24 v. D.C. operation. £7-63, plus 22p P. & P.

## 12-28 VOLT D.C. BLOWER UNIT

Powerful, smooth running, precision made Blower Unit. 5,000 RPM, .54 amps. Size 3" diameter x 3 3/8" long over all. Price £2-00 post paid.



## VERY SPECIAL OFFER

Cannot be repeated. 500 v. 50 Meg Record insulation testers. Excellent condition, fully tested. Complete with leather carrying case. £12. P. & P. 50p.

## STROBE! STROBE! STROBE!

THREE EASY TO BUILD KITS USING XENON WHITE LIGHT FLASH TUBES. SOLID STATE TRIGGERING CIRCUITS. PROVISION FOR EXTERNAL TRIGGERING. 230-250v. A.C. OPERATION. The Strobe is one of the most useful and interesting instruments in the laboratory or workshop. It is invaluable for the study of movement and checking of speeds. Many uses can be found in the psychiatric and photographic fields, also in the entertainment business. It is used a great deal in the motor industry and is a real tool as well as an interesting scientific device. EXPERIMENTERS "ECONOMY" KIT Adjustable 1 to 36 Flash per sec. All electronic components including Veroboard S.C.R. Unijunction Xenon Tube+instructions £6-30 plus 25p P. & P. NEW INDUSTRIAL KIT Ideally suitable for schools, laboratories etc. Roller tin printed circuit. New trigger coil, plastic thyristor Adjustable 1-80 f.p.s. Price £10-50. 50p P. & P. HY-LIGHT STROBE This strobe has been designed for use in large rooms, halls and the photographic field, and utilizes a silica tube for longer life expectancy, printed circuit for easy assembly, also a special trigger coil and output capacitor. Speed adjustable 1-30 f.p.s. Light output approx. 4 ioules. Price £12-00. P. & P. 50p.

## AND NOW!

### THE 'SUPER' HY-LIGHT KIT

Approx. 4 times the light output of our well proven Hy Light strobe. Incorporating, Heavy duty power supply. Variable speed from 1-23 flash per sec. Fantastic Octal based tube with massive electrodes. Reactor control circuit producing an intense white light. The brilliant light output of the 'SUPER' HY-LIGHT gives fabulous effects with colour filters. Never before a Strobe Kit with so HIGH an output at so LOW a price. ONLY £20-00 plus 75p P. & P. 7-INCH POLISHED REFLECTOR. Ideally suited for above Strobe Kits. Price 53p and 13p P. & P. or post paid with kits.



RUNNING HOUR METER. 240 volt, 50 cycle, 2-2 watt. Calibrated in minutes. Six figure. PRICE: £3-00 including Post & Packing.

## VENNER ELECTRIC TIME SWITCH

200/250 volt. Ex-GPO. Tested, perfect condition. Two ON, two OFF, every 24 hrs. at any manually pre-set time. Price: 10amp. £2-75. (5amp. £3-25. 20amp. £3-75. P. & P. 20p. Also available with Solar Dial ON at dusk, OFF at dawn. Prices as above.



INSULATED TERMINALS Available in black, red, white, yellow, blue and green. New 10p each. Post paid.

## RELAYS NEW SIEMENS PLESSEY, etc.

MINIATURE RELAYS AT COMPETITIVE PRICES.

1	2	3	4	1	2	3	4
45	6-9	2HD M	50p	700	12-24	2 c/o	63p*
185	6-12	2 c/o	63p*	700	15-35	2 c/o HD	73p*
185	6-12	4 c/o	73p*	700	16-24	6 M	63p*
230	9-18	2 c/o HD	63p*	1250	24-36	4 c/o	63p*
230	9-12	4 c/o	78p*	2500	36-45	6 M	63p*
280	9-12	2 c/o	73p*	2400	30-48	4 c/o	50p
600	18-32	4 c/o	78p*	5800	40-70	4 c/o	63p*
700	16-24	4 M 2 B	63p*	9000	40-70	2 c/o	50p*
700	16-24	4 c/o	78p*	15k	85-110	6 M	50p*

(1) Coil ohms: (2) Working d.c. volts; (3) Contacts: (4) Price HD = Heavy Duty. All Post Paid. \*including Base.

## MAINS RELAY

230 v. A.C. coil 3 c/o, 10 amp. A.C. contacts. 50p + 8p p. & p. Similar to above illustration.

## RECHARGEABLE NICKEL CAD. BUTTON CELLS.

2 x 1.2 v. 250 MA/HR Nickel Cad. Cells, connected to give 2.4 v., at 25 milliamp/10 hour rate, complete with 200/250 v. A.C. charger, unused. Price 48p each plus 8p p. & p. or 2 units for £1-00 post paid.




## NICKEL CADMIUM BATTERY

1.2 v. 35 AH. Size 80 high x 3 x 10. £1-50 each, plus 20p P. & P. Sintered Cadmium Type 1.2 v. 7AH. Size: height 3 1/2 in., width 2 1/2 in. x 1 1/2 in. Weight: approx. 13 ozs. Ex-R.A.F. Tested 63p. P. & P. 15p.
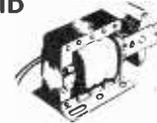
## 230 VOLT AC SOLENOID

EXTREMELY POWERFUL SOLENOID with approximately 14lb. pull, 1 inch travel. Fitted with mounting feet. Size 4 inches long, 2 1/2 inches wide and 3 inches high. Price £2-00 including post & pkg.



## 230-250 VOLT A.C. SOLENOID

(Similar in appearance to above illustration.) Approx. 1 1/2 lb. pull. Size of feet 1 1/2 x 1 1/2. Price 85p incl. post. Manufactured by Westool Ltd.

## 36 volt 30 amp. A.C. or D.C. Variable L.T. Supply Unit

Input 220/240 v. A.C. Output Continuously variable 0-36 v. A.C./D.C. Fully isolated. Fitted in robust metal case with Voltmeter, Ammeter, Panel Indicator and chrome handles. Input and Output fully fused. Ideally suited for Lab. or Industrial use. £58 plus £2 p. & c.



## 230V/240V COMPACT SYNCHRONOUS GEARED MOTORS

Manufactured by either Sangamo, Haydon or Smith. Built-in gearbox. 1 rev. per hour. Clockwise rotation. 1 rev. per hour. Anti-clockwise rotation. 2 revs. per hour. Clockwise rotation. 3 revs. per hour. Anti-clockwise rotation. 5 revs. per hour. Anti-clockwise rotation. 15 revs. per hour. Anti-clockwise rotation. 60 revs. per hour. Clockwise rotation.



## 12 VOLT DC MOTOR

Powerful 12 volt 1 amp REVERSIBLE motor. Speed 3,750 rpm. Complete with external gear train (removable) giving final speed of 125 RPM. Size 4 1/2 in. x 2 1/2 in. dia. Price inc. post 95p.



## PARVALUX TYPES DI9 230/250 VOLT AC REVERSIBLE GEARED MOTORS

30 r.p.m. 40 lb. ins. Position of drive spindle adjustable to 3 different angles. Mounted on substantial cast aluminium base. Ex-equipment. Tested and in first-class running order. A really powerful motor offered at a fraction of maker's price. £6-30, P. & P. 50p.



## BODINE TYPE N.C.1 GEARED MOTOR

(Type 1) 71 r.p.m. torque 10 lb. in. Reversible 1/70th h.p. 50 cycle .38 amp. (Type 2) 28 r.p.m. torque 20 lb. in. Reversible 1/80th h.p. 50 cycle .28 amp. The above two precision made U.S.A. motors are offered in 'as new' condition. Input voltage of motor 115v. A.C. Supplied complete with transformer for 230/240v. A.C. input. Price, either type £3-15 plus 35p P. & P. or less transformer £2-13 plus 27p P. & P. These motors are ideal for rotating aerials, drawing curtains, display stands, vending machines etc. etc.



ALL MAIL ORDERS, ALSO CALLERS AT:

57 BRIDGMAN ROAD, LONDON, W4 5BB. Phone: 01-995 1560 Closed Saturdays.

# SERVICE TRADING CO.

SHOWROOMS NOW OPEN AMPLE PARKING

PERSONAL CALLERS ONLY

9 LITTLE NEWPORT STREET, LONDON, WC2H 7JJ. Tel.: 01-437 0576

**Special offer of AMPEX professional tape heads, mu-metal shrouded.** (Designed for model AG20). Full track record, or playback, £3.00. Erase head £2.00. Set of 3 with mounting bracket and cover £7.50. Half track record only, £3.00 each. Carriage paid.



**OXLEY P.T.F.E. BARB TERMINALS.** Stand off  $\frac{1}{8}$ " or  $\frac{1}{4}$ ". £2.75 box of 100.

**HARWIN.** Tapped (6 Ba) high voltage "stand off" insulators, length  $\frac{1}{2}$ ", tapped (8 Ba)  $\frac{1}{4}$ " long. £2.00 per 100. Carriage Paid.

**"BENSON BROS."** 12v. D.C. HEAVY DUTY SOLENOID. Size: 3" overall x  $1\frac{1}{2}$ " x 1". Very powerful. Cont. rated. £1.00 each. P. & P. 15p.

**"DECCO" MAINS SOLENOID.** Compact and very powerful. 16 lb. pull.  $\frac{3}{8}$ " travel which can be increased to 1" by removing captive-end-plate. Overall size 2" x 2 $\frac{1}{2}$ " x 2 $\frac{3}{8}$ " high. £1.50. P. & P. 25p.

**WEBBER MAINS SOLENOID.** Robust and strong. On this item the plunger travel is 1". Performance: 6 lb. pull at 1 $\frac{1}{2}$ "; 8 lb. at 1"; 10 lb. at  $\frac{1}{2}$ ". The non-captive plunger has a fixing eye to take up to  $\frac{1}{8}$ " bolt. Size: 2 $\frac{1}{2}$ " high x 2" x 2". £1.25 plus 25p P. & P.

**SPECIAL OFFER MAINS SOLENOID BY MAGNETIC DEVICES LTD.** A beautifully constructed solenoid at half normal price. A two-sided bracket is incorporated for vertical or horizontal mounting. Size: 2" x 1 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ ". Pull is approx. 2 lb., plunger travel 1 $\frac{1}{2}$ ". Fixing eye takes up to  $\frac{1}{8}$ " bolt. Plunger non-captive. New in original makers boxes. 75p each, plus 25p P. & P. Large number available, special price for quantity.

**RELAYS**  
Perspex enclosed, plug in, with base. Size 1 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ " x 3"  
MQ 308 600Ω 24v. 4 c/o. 60p ea., £5.00 per doz.  
MQ 508 10,000Ω 100v. 4 c/o. 50p ea., £4.50 per doz.  
S.T.C. Midget Field Relay type 4109EC. 12v. 40 mA  
170Ω, single H.D. make. 53p each.

**"B. & R."** 3 c/o. 10 amp. contacts (silver) operates on 2 volts D.C. Draws approx. 1 amp. Size: 2" x 1 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ ". £1.00.

**"OMRON" OCTAL BASE.** A.C. mains. 2 x 5 amp. C/O contacts. Perspex enclosed. 88p.

**A.E.** Perspex enclosed, plug in, 50Ω 6v. 2 c/o. 63p ea. 470Ω 12v. 4 c/o. 73p ea. 2,780Ω 48v. 4 c/o. 73p ea. 1,260Ω 48v. 6 c/o. 83p ea.

**MAGNET DEVICES.** 12v. 3xH.D. c/o Contacts size 1 $\frac{1}{2}$ " x 1" x 1 $\frac{1}{2}$ ". 63p each.  
**E.R.G.** 1,000Ω 6v. D.C. 1 make encapsulated reed type. Size:  $\frac{3}{8}$ " x  $\frac{1}{8}$ " x 1 $\frac{1}{8}$ ". 4 for £1.00.

**NEW "F.I.R.E." PLUG-IN RELAY.**—115v. Coil 50/60 c.p.s. 3 heavy duty silver change-over contacts. Very robust. 63p.




**NEW "ISKRA" 240v. A.C. RELAY.**—3 x 6 amp Changeover contacts. 63p.



**SIEMENS HIGH SPEED RELAY.** Type 89L. 1,700Ω + 1,700Ω coil. New 63p each.



**MINIATURE "LATCH-MASTER" RELAY 6, 12, or 24v. D.C. operation.** One make one break, contacts rated 5 amps. at 30v. Once current is applied, relay remains latched until input polarity is reversed. Manufactured for high acceleration requirements by Sperry Gyroscope Co. Size: Length  $\frac{1}{2}$ " dia.  $\frac{3}{8}$ " (including mount). Please state vertical or horizontal mount and voltage. £1.63 each.

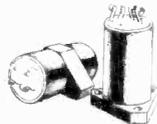


**ELECTROLYTIC CAPACITORS MULLARD.** 900μF 100v. heavy ripple screw terminals 1 $\frac{1}{2}$ " dia. x 3 $\frac{1}{2}$ " 70p ea., £6.00 per doz. 1,600μF 64v. 1 $\frac{1}{2}$ " dia. x 3" 38p ea., £3.50 per doz. 10,000μF 10v. 1 $\frac{1}{2}$ " dia. x 3" 38p ea., £3.50 per doz. 1,250μF 25v. 1" dia. x 2". 50p ea., £4.50 per doz.

**HUNTS 1,000μF 50v. 1 $\frac{1}{2}$ " dia. x 2", 25p ea., 10,000μF 6v. 1 $\frac{1}{2}$ " dia. x 2", 30p ea., £3.00 per doz. 16μF 350v.  $\frac{3}{8}$ " x 1 $\frac{1}{2}$ " wire ends, £2.00 per doz. 1,000μF 50v. 1" dia. x 3", 30p ea., £3.00 per doz. 32-32μF 275v. 1" dia. x 2", 38p ea. 100μF 100v. 1" dia. x 2", 25p ea.**


**ERIE.** Ceramicon capacitor. Type CHV411P. 500 P.F. 30KV Size 1-5" dia. x 1-44" long. 50p ea. Carriage paid.  
**HIGH CAPACITY ELECTROLYTICS.** Cylinder type with screw terminals on top. Average size 3" dia. x 4 $\frac{1}{2}$ " high. "Mallory" 20,000μF 30v. D.C. 45v. D.C. surge. "Mallory 25,000μF 25v. D.C., 40v. D.C. surge. Mallory 35,000μF 15v. D.C., 20v. D.C. surge. "Mallory" 40,000μF 10v. D.C., 12v. D.C. surge. "Sprague" 40,000μF 10v. D.C., 12v. D.C. surge. "General Electric" 46,500μF 25v. D.C., 30v. D.C. surge. "General Electric" 55,000μF 15v. D.C., 20v. D.C. surge. 50p each. Minimum order £1.00 on these items. P. & P. 10p each.

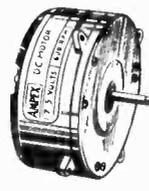**WHERE NO CARRIAGE CHARGE IS INDICATED PRICE IS INCLUSIVE. PERSONAL CALLERS WELCOME.**


**MOTORS**  
**AMPEX 7.5v. D.C. MOTOR.** This is an ultra-precision tape motor designed for use in the AMPEX model AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 60ma on run. 600 rpm ± 5% speed adjustment, internal AF/RF suppression.  $\frac{1}{2}$ " dia. x 1" spindle, motor 3" dia. x 1 $\frac{1}{2}$ ". Original cost £16.50. Our price £4.25. P. & P. 25p. Large quantity available (special quotations). Mu-metal enclosure available 75p each.



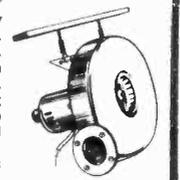**Brand New "DISCUS" Centrifugal Blower by Watkins & Watson.** 240v. 50 Hz. Powered by A.E.I. continuous rating 2850 rpm motor. Cowl diameter 10". Outlet flange 2" I.D. Coupling flange supplied. These superb precision units are ideally suited for Organ construction. Offered at approx. half makes price £12.50. Carriage £1.50.



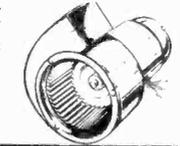
**POWERFUL DUAL VOLTAGE.** 110/240v. 50Hz. Blower by Fanmenco Ltd. A compact powerful unit with 3" dia. x 1 $\frac{1}{2}$ " wide impeller giving powerful thrust. 2" x 1 $\frac{1}{2}$ " outlet. Weight 3 $\frac{1}{2}$ lb. These units are unused and offered at only £3.50. P. & P. 30p.



**SPECIAL SUMMER OFFER**  
**LIMITED PERIOD ONLY FROM NOW UNTIL 31st AUG. 1971 A DISCOUNT OF 20% WILL BE DEDUCTED ON ALL ORDERS OF £7.50 AND OVER**

We welcome orders from established companies, educational depts., etc. (To cover invoicing costs minimum £2.50, please.)


**PROGRAMME TIMER BY HONEYWELL**  
A bank of 15 micro-switches are each independently operated by 15 pairs of cams which in turn are individually adjustable to give switching periods of zero to 12 seconds with infinitely variable combinations. A mains synchronous motor drives the cam shaft at 1 rev. per 12 seconds (5 R.P.M.). Designed originally for vending machines at a cost of £15.00 plus. Many applications where continuous sequence programmes are required, such as lighting effects etc. New in original makers cartons. First class value at £5.75 plus 25p P. & P.

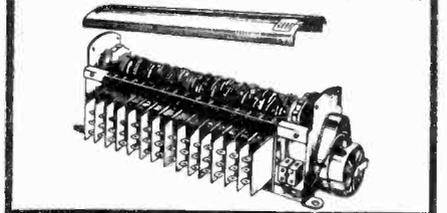


**DEAC. RECHARGEABLE PERMA-SEAL Nickel-Cadmium Batteries** Type 900D. 1.2v. at 900 mA (10-hr. rate). Size 90 mm. x 13.5 mm. Weight 40 gr. Unused 63p ea. P. & P. 12p. Stock now running low.



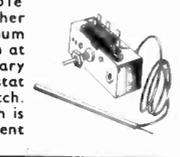**"TEDDINGTON" CONTROLS THERMOSTAT.**—Adjustable between 75° and 100°C. A further internal adjuster takes the maximum up to 120°C. Circuit cuts in again at 3° below cut-out setting. 42" capillary and sensor probe. The thermostat actuates a 15 amp. 250v. c/o switch. A second single pole on/off switch is incorporated in the adjustment mechanism. 88p.



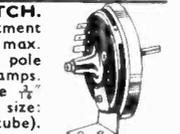**"GOYEN" PRESSURE SWITCH.**—Incorporating differential adjustment between 2" and 12" water gauge (a max. of approx.  $\frac{1}{2}$ " p.s.i.). A single pole change-over switch rated 15 amps. 250v. is actuated. Air inlet tube  $\frac{3}{8}$ " dia. Projection  $\frac{1}{2}$ ". Overall size: dia. 3 $\frac{1}{4}$ ", depth 2" plus  $\frac{1}{4}$ " (air tube). £1.25.



**VINKOR POT CORE ASS. TYPE LA.2103** (core LA.2100). Normal price £1.48. Our price 75p each. Special quote for quantity.

**UNISELECTORS.** 8 Bank 25-way 24v. Double sweep. Brand new in maker's boxes. £5.25. P. & P. 25p.

**HEAVY DUTY PORTABLE BATTERIES.** New ex WD. 12v. 75 AH. Built in stout metal cases with carrying handles and nifam socket outlet. Size 15 $\frac{1}{2}$ " x 7 $\frac{1}{2}$ " x 10 $\frac{1}{2}$ " high, weight 73lb. £8.75. Carriage £2.


**L.T. TRANSFORMER.** Prim. 0-110-240v. Sec. 4.5v.-0-4.5v. at 2A. Size 1 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ " x 1 $\frac{1}{8}$ " 60p. P. & P. 15p.

**GEARED MOTORS**  
**"Parvalux" Reversible 100 RPM Geared Motor.** Type S.D.14. 230/250v. A.C. 22 lb./in.  $\frac{3}{8}$ " spindle. 1st class condition. £7.50 each. P. & P. 50p. Also limited number only as above. Brand New. £12.50 each P. & P. 50p.



**ELECTRO CONTROL (CHICAGO).** Shaded pole 240v. 50 Hz. 200 rpm 10 lb./in. £2.50. P. & P. 25p.  
**MYCALEX.** Open frame, shaded pole motors. 240v. 50 Hz. 7 rpm. 28 lb./in. 80 rpm. 12 lb./in. £2.25 each. P. & P. 25p.

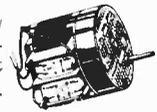**"CROUZET" TYPE 965.** 115/240v. 50 Hz. 47/68 watts. 50 rpm. Stoutly constructed. Size: 2 $\frac{1}{2}$ " dia. x 3 $\frac{1}{2}$ " long, plus spindle 1" x  $\frac{1}{4}$ " dia. Anti-clock. £2.75. P. & P. 25p.



**MYCALEX MAINS.** Shaded pole, 1425 rpm.  $\frac{3}{8}$ " spindle. 2 for £1.25. Carriage Paid.

**MAINS INDUCTION MOTOR.** Open frame,  $\frac{3}{8}$ " spindle, weight  $\frac{1}{2}$  lb. Powerful. 88p each. P. & P. 12p  
**E.M.I. PROFESSIONAL TAPE MOTOR.** 110/240 v. 50 Hz. 1500 rpm, reversible, silent running. 4 $\frac{1}{2}$ " dia. x 4 $\frac{1}{2}$ " long. Spindle  $\frac{3}{8}$ " x 2". Weight 6 lbs. £3.50 each or £6.00 per pair. P. & P. 50p each.


**"FIBRE GLASS" COPPER CLAD.** Top grade. One size only. 7 $\frac{1}{2}$ " x 4 $\frac{1}{2}$ " x  $\frac{1}{8}$ ". 3 panels £1.00. 12 panels £3.50. P. & P. 15p.

**"SRBP" COPPER CLAD.** Sizes: 7 $\frac{1}{2}$ " x 4 $\frac{1}{2}$ " x  $\frac{1}{8}$ ", 16 for £1.00. 13 $\frac{1}{2}$ " x 5 $\frac{1}{2}$ " x  $\frac{1}{8}$ ", 8 for £1.00. 14 $\frac{1}{2}$ " x 5 $\frac{1}{2}$ " x  $\frac{1}{8}$ ", 8 for £1.00. 19 $\frac{1}{2}$ " x 7 $\frac{1}{2}$ " x  $\frac{1}{8}$ ", 4 for £1.00.

**SYLVANIA MAGNETIC SWITCH**—a magnetically activated switch operating in a vacuum. Switch speed—4ms. temperature —54 to +200°C. Silver contacts normally closed rated 3 amps. at 120v. 1.5 amp. at 240v. Price 4 for £1. £2.50 per doz. P. & P. 10p. Special quotations for 100 or over. Reference magnets available 8p each.



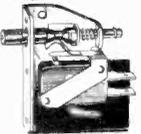**"HONEYWELL" TYPE 23AC-NE.**—15 amp. change-over micro switch is fitted on angled metal mount with spring-loaded plastic rod operating cam. 50p each.




**PLUNGER SWITCHES.** Spring return. 3 P.D.T. 1 amp. Single action. Size:  $\frac{1}{2}$ " x  $\frac{1}{2}$ " plus plunger. £1.50 per doz. Carr. Paid.



**SLIDER SWITCHES.** 3 amp. type D.P.D.T. 1" x  $\frac{3}{8}$ " x  $\frac{1}{2}$ " deep. 1 amp. type 3 P.D.T.  $\frac{1}{2}$ " x  $\frac{3}{8}$ " x  $\frac{1}{2}$ " deep. £1.25 per doz. Either type or mixed as required. Carr. Paid.



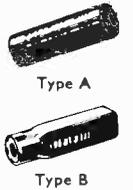**"MALLORY" LONG LIFE BATTERIES.** Type A. RM12 cell 1.35v. 3,600 ma/H. CAP. 250/300 ma cont. current. Size: 2" x  $\frac{1}{2}$ ". 5 for £1.00 or £2.00 per doz. Carr. Paid. Type B. Comprises 8 x RM 625 cells. Nom. volts. 1.35 each 10.5v. Overall. 350 ma/H. CAP. 20/25 ma cont. current. Size: 2 $\frac{1}{8}$ " x  $\frac{1}{2}$ " x  $\frac{1}{2}$ ". 3 for £1.00 or £3.00 per doz. Carr. Paid.



**A.C./D.C. M/IRON AMMETERS.** 0-5 amps or 0-8 amps (suitable battery chargers etc.). Perspex front. Size: 1 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ ". Any 2 for £1.10. Carr. Paid.



**CURRENT FLOW INDICATOR.** Ideal for all types of battery operated equipment (portable machines, tape recorders etc.). Four white segments appear when current flows. Coil is 600Ω 6/12v. Drawing only 8 ma on function. Neat in appearance. Size: dia.  $\frac{1}{2}$ " x  $\frac{1}{2}$ " deep. Fixing centres  $\frac{1}{4}$ ". £1.25 each. Carr. Paid.



**BIO-CHEMISTRY AND CHEMISTRY LABORATORIES PLEASE NOTE WE HAVE PURCHASED A NUMBER OF THE GRIFFIN AND GEORGE BIOANALYST CHEMISTRY MODULE G. & G. CAT. NO. S54-320. COMPLETE AUTOMATED SYSTEM. BRAND NEW IN ORIGINAL MAKER'S PACKING. CURRENTLY LISTED AT £925. WE OFFER THESE AT £425 NETT. CARRIAGE EXTRA.**

**G. F. MILWARD**

Mail Orders: DRAYTON BASSETT, TAMWORTH, STAFFS

# ELECTRONIC COMPONENTS

Wholesale/Retail:

**369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339**

TRANSISTOR EQUIVALENT BOOK. LATEST EDITION ..	40p
Mikes, Low impedance, dynamic stick type with on/off switch ..	£1-00
.. Crystal, hand ..	50p
.. Crystal, Inserts with bracket ..	20p
Lockable car aerials ..	£1-25
Dee-Gee 25 watt pencil bit soldering irons ..	98p
Speakers, 2½in, 8 ohms ..	50p
Insulating Tape, ¼in wide, 10 yard rolls ..	5p
Miniature Output Transformers ..	12p
Rotary Switches, 4 pole 3 way or 2 pole 6 way ..	15p
Switch cleaner, aerosol cans ..	50p

Transistorised Modules,		Electrolytic Capacitors	
BM 1 Phono pre-amp	£1-25	2,000 µf 25 volt Rev.	25p
BM 2 Tape pre-amp	£1-25	1,000 µf 70 volt	35p
BM 3 Mike pre-amp	£1-25	10,000 µf 35 volt	50p
BM21 F.M. Transmitter	£1-25	10,000 µf 25 volt	35p
BM22 F.M. Wireless Guitar	£1-25	2,000 µf 18 volt	20p
BM31 Electric Organ	£1-25	60µf + 200µf 300 volt	30p
BM41 Code Oscillator	£1-25	400 µf 275 volt	25p
BM42 Wireless Oscillator	£1-25	10 µf 6 volt	2p
		10 µf 25 volt	4p
		16 µf 250 volt	8p
		32 µf 275 volt	8p

**TRANSISTORS AND I.C.s**

**ALL BRAND-NEW WITH MANUFACTURERS MARKINGS**

ASY22	10p	OC45	10p	2N709	50p	2N3703	13p
ASY29	25p	OC46	15p	2N1302	15p	2N3704	18p
ASZ17		OC141	22p	2N1309	23p	2N3707	15p
(OC35)	25p	OC139	22p	2N1613	25p	2N3877A	40p
BC167	15p	OC74	20p	2N1711	25p	7401	40p
BCY70	18p	OC204	25p	2N2646	58p	7410	40p
BFX12	20p	2G345	10p	2N2926	15p	7430	40p
OC41	20p	2G371	10p	2N3053	25p	7472	55p
OC42	23p	2G378	10p	2N3055	75p	7473	90p
OC43	20p			2N3702	18p	7475	£1-15
OC44	15p						

**VEROBOARD**

2½in x 1in x 0.15in 6p 5in x 3½in x 0.15in 28p 3½in x 3½in x 0.1in 24p  
 3½in x 2½in x 0.15in 16p 17in x 2½in x 0.15in 55p 5in x 2½in x 0.1in 23p  
 3½in x 3½in x 0.15in 20p 17in x 3½in x 0.15in 74p 5in x 3½in x 0.1in 28p  
 5in x 2½in x 0.15in 20p 3½in x 2½in x 0.1in 21p  
 Spot Face Cutter 38p. Pin Insert Tool 48p. Terminal Pins (0-1 or 0-15) 36 for 18p. Special Offer Pack consisting of 5 2½in x 1in boards and a Spot Face Cutter—50p.

**RECORD PLAYER CARTRIDGES.** Well below normal prices!  
 G90 Magnetic Stereo Cartridges, Diamond Needle, 6mV output, £4. ACOS GP 67/2 (Mono, Crystal) 75p. ACOS GP 91/3 (Compatible, Crystal) £1. ACOS GP 93/1 (Stereo, Crystal, Sapphire) £1-25. ACOS GP 93/1D (Stereo, Crystal, Diamond) £1-63. ACOS GP 94/1 (Stereo, Ceramic, Sapphire) £1-50. ACOS GP 94/1D (Stereo, Ceramic, Diamond) £1-88. ACOS GP 95/1 (Stereo, Crystal with two L.P./Stereo needles) £1-25.

**TRANSISTORISED FLUORESCENT LIGHTS,** 12 volt. All with reverse polarity protection. 8 watt type with reflector, suitable for tents, etc., £3. Postage/Packing 25p. 15 watt type, batten fitting for caravans £4. Postage/Packing 25p. 13 watt type, batten with switch. 22in x 2in x 1in £5. Postage/Packing 25p. THESE CAN BE SENT ON APPROVAL AGAINST FULL PAYMENT.

**MULLARD POLYESTER CONDENSERS**  
 1,000pf, 1,200pf, 1,500pf, 1,800pf, 2,200pf, 15p per dozen (all 400V working). 0-15µf, 0-22µf, 0-27µf, 30p per dozen (all 160V working). 25% discount for lots of 100 of any one type.

**RESISTORS**  
 ½ and ¾ watt. Most values in stock. 50p per 100, 10p per dozen of any one value. WIRE WOUND MAINS DROPPERS. Hundreds of values from 0-7 ohm upwards. 1 watt to 50 watts. A large percentage of these are multi-tapped droppers for radio/television. Owing to the huge variety these can only be offered "assorted" at 50p per dozen.

**SILVER MICA/CERAMIC/POLYSTYRENE CONDENSERS**  
 Large range in stock, 75p per 100 of any one value. 15p per dozen.

**RECORDING TAPE BARGAIN!** The very best British Made low-noise high-quality Tape! 5in Standard 38p. Long-play 45p. 5½in Standard 45p. Long-play 60p. 7in Standard 60p. Long-play 82p. We are getting a fantastic number of repeat orders for this tape. Might we suggest that you order now whilst we still have a good stock at these low prices?

**STOCKTAKING CLEARANCE! IMPOSSIBLE TO REPEAT!**

We have huge numbers of components in quantities too small to advertise individually. In order to "clear the decks" we have made up parcels containing a mixture of carbon and wire-wound resistors, electrolytic and paper condensers, controls, transistors, diodes etc., for a tiny fraction of normal price. It is emphasised that these are mixed parcels only—contents cannot be stipulated! Sold only by weight.

Gross weight 2 lb. .. .. .	£1 (postage 20p)
Gross weight 5 lb. .. .. .	£2 (postage 30p)

## 4,000,000 DIODES

SILICON, GERMANIUM OR ZENER (STATE CHOICE)

LOTS OF 100,000—£150

10,000—£20

1,000—£3

500—£2

100—50p

## 1,000,000 GERMANIUM TRANSISTORS

(OC71/OC75)

LOTS OF 100,000—£250

10,000—£30

1,000—£3-50

500—£2

100—50p

**NEW! NEW! NEW! NEW!**

An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.

Method: Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner. Light sensitive aerosol spray .. .. . £1-00  
 Developer spray .. .. . 50p

**SPECIAL 50p PACKS. ORDER 10 PACKS AND WE WILL INCLUDE AN EXTRA ONE FREE!!!!**

<b>RESISTORS, ½/¾ watt</b>			
assorted	100	50p	
Wire-wound 1 to 3 watt	20	50p	
5 to 7 watt	15	50p	
10 watts	10	50p	
Multi-tapped	12	50p	
<b>PAPER CONDENSERS</b>			
Tv types	50	50p	
Miniature	100	50p	
<b>ELECTROLYTIC CONDENSERS</b>			
Suitable for Mains			
Radio/Tv	10	50p	
Transistor types	20	50p	
Mixed (both types)	15	50p	
<b>POLYSTYRENE CONDENSERS</b>	100	50p	
<b>MULLARD POLYESTER COND.</b>	50	50p	
<b>SILVER MICA WIRE-WOUND 3-Watt SLIDERS</b>	100	50p	
	15	50p	
<b>VOLUME CONTROLS</b>	5	50p	
Assorted			
<b>NUTS AND BOLTS. Mixed length/type</b>			
8 B.A.	100	50p	
6 B.A.	100	50p	
4 B.A.	100	50p	
2 B.A.	100	50p	
<b>METAL SPEAKER GRILLES</b>			
7½in. x 3½in.	6	50p	
<b>EARPIECES, MAGNETIC</b>			
No Plug	6	50p	
2-5mm Plug	4	50p	
3-5mm Plug	4	50p	
<b>500 MICRO-AMP LEVEL METERS</b>	1	50p	
<b>VEROBOARD, TRIAL PACK</b>			
5 BOARDS + CUTTER		50p	
<b>TRANSISTORS</b>			
P.N.P. Untested but mainly O.K.	50	50p	
N.P.N. Untested but mainly O.K.	50	50p	
OC71 equivalent	5	50p	
Light-sensitive Diodes	10	50p	
(These produce up to 1ma from light)			
OC44 Mullard 1st grade	4	50p	
OC45 Mullard Boxed	5	50p	
2G378 Output, Marked	5	50p	
2G371 Driver, Marked	5	50p	
ASY 22, Marked	5	50p	
BY 127 Rectifiers	4	50p	
IN4007 Rectifiers (1200V peak)	4	50p	
STC 3/4 Rectifiers	6	50p	
DIODES (0A 81 & OA 91)	40	50p	
<b>WIRE</b>			
Solid Core. Insulated	100yds.	50p	
Stranded ditto	50yds.	50p	
<b>SOLAR CELLS</b>			
Large Selenium	2	50p	
Small	3	50p	
(6 cells will power a Micromatic radio)			
<b>CO-AXIAL CABLE</b>			
Semi Air-spaced	15yds.	50p	
<b>CRYSTAL TAPE RECORDER</b>			
MIKES	1	50p	
<b>CRYSTAL EARPIECES</b>			
3-5mm Plug	2	50p	
<b>TRANSISTORISED Signal Injector Kit</b>	1	50p	
<b>TRANSISTORISED Signal Tracer Kit</b>	1	50p	
<b>TRANSISTORISED CAR REV. COUNTER KIT (Needs 1 ma. meter as indicator)</b>	1	50p	

**OSCILLOSCOPE PROBE TM8119**  
High impedance 100/1 resistive attenuated probe for accurate display of HF waveforms or short rise time pulse signals, offered brand new with all accessories and instruction manual. List price £17. Our price £7.50 including earth bayonet TM8194. **A MARCONI PRODUCT**

**WAVE ANALYSER MARCONI TF455E**  
20Hz to 16KHz or modulated RF up to 500MHz.

**MARCONI RF WATTMETERS TYPE TF912/A1**, Input impedance 50 ohms dual scale 0.5 and 0-25 watts. In good used condition. Price... £17.50  
Also **MARCONI TF1020A RF POWER METER**, Range 0-100 watts 75 ohms. £50 P. & P. 75p.

We have in stock wattmeters and RF loads up to 1,000 watts.

**BARGAIN OFFER 6V DC TAP RECORDER MOTORS Type DM148-I**. Fully screened \* reversible \* constant speed \* specially designed for Portable Recorders \* Price only £1 P.P. 10p

**20Kv ELECTROSTATIC VOLTMETER UNIT**  
5 in. scale Ernest Turner Model 32 contained in polished wood case with HV input sockets. Only £10 Carr. 15p

**MARCONI 12 KHz QUARTZ CRYSTAL** contained in 87G envelope with flying lead connections. Brand new only £2.2p each.

**TEKTRONIX TYPE 310. PORTABLE OSCILLOSCOPE. PERFECT CONDITION. PRICE £150.**

**MARCONI TF930**  
H.F. field strength measuring equipment. 18-125 mHz. £65.

**SPECIAL OFFER AC VOLT-METER TYPE TM2A**  
These small portable instruments measure AC RMS volts from 500V to 100 microvolts. The meter is also scaled in dB. In perfect condition. Price only... £18.50

**MARCONI DUAL TRACE OSCILLOSCOPE TYPE TF 1331**. Offered in little used condition with probe/handbook/guarantee.

**IMPEDANCE BRIDGES**  
AVO Type 1 with slide rule scale as new £35  
Bradley Type 131 LC/R bridge... £30  
Cossor Model 1446 with C.R.T. phase balance... £35  
Wayne Kerr Model B221 0-1% accuracy... £85  
Wayne Kerr Model B521 LC/R Bridge... £40  
Solartor Model MM906 -1 to 300pf & -1 to 300uH... £33  
Marconi Model TF936 Measures L&C at 80Hz I & 10kHz... £55

**RECEIVERS COMMUNICATIONS**  
Eddystone 770U range 150 to 500MHz £145  
Marconi CR150/2 Range 2 to 60 mHz double conversion... £60  
HRO. MX Model range .5 to 30 mHz full set coils... £27  
R155 Trawler band model with super slow motion drive... £17  
APR/4 Search Receiver range 38 to 1,000 mHz... £95

**4-INCH G.E.C. DOUBLE GUN**  
C.R. Tubes Spiral P.D.A. type 1046F. Brand new. Boxed. Price £10.50.

**MARCONI TF1041B ELECTRONIC VOLTMETER**. Frequency response 20Hz to 1,500 Hz. AC volts 25mV to 300 volts; DC volts 10mV to 1,000 volts. Resistance 0.02 ohm to 500M ohms. Offered in good calibrated condition. Price only £50 P. & P. 50p.

**PHILLIPS MODEL GM 6010**. DC low level electronic voltmeter measurements from 1mV for full scale deflection to 300Vdc in twelve ranges. Indication on 5 inch mirror scale. A first-class instrument at an economical price. Only £40 plus battery. P. & P. 75p.

**B. & K. Type 2409 ELECTRONIC VOLTMETER**. AC measurements can be made at Average, Peak or RMS from 0.01 for FSD to 1,000V frequency response 2Hz to 200KHz in eleven ranges. Mirror scale indication is also scaled in dB from -60 to +40 dB. Function can be either VU damping or slow response. As new condition £75 P. & P. 50p.

**ADVANCE TYPE 78A ELECTRONIC VOLTMETER**. Range 1mV for FSD to 1,000 volts. RMS frequency response 1Hz to 1MHz. Also scaled in dBm -60 to +50. As new. Price £50

**WE HAVE IN STOCK MANY OTHER TYPES, LET US KNOW YOUR REQUIREMENTS**

**EVERSHED & VIGNOLES CIRCUIT TESTING OHMMETER**. Dual scale from 0-1 to 1,000 and 100 to 200K ohms in good serviceable condition... £3.25 P. & P. 25p

**Crompton Parkinson direct reading Kilowatt Meters**. Range 0 to 4 Kilowatts, 4 inch flush panel mounting for 250v single phase operation 50Hz with external resistance... £15

**PYE Electrostatic Voltmeter model 11310** scalamp type Voltage range 18KV mains operated in good used condition... £22



**SPECIAL OFFER**

**"INSULATION TESTERS" TYPE No. 11 METROHM** by famous British manufacturer. All solid state. No handles to crank. Runs off 9 volt transistor battery. Simply press button for function. Range 0-1 to 25M ohms for insulation testing. Also 0-1 to 100 ohms for resistance and continuity checking. Clear, concise scale. Small size modern instrument, complete with carrying strap and protecting cover. Offered in good used condition ready to work. For 250 volt pressure only. List Price £19.50. Our Price £6.00 plus 22p post/packing.

**EVERSHED QUICK RESPONSE RECORDER (DUPLEX) Type QU/CRD 10** with amplifier unit type PA. 10.M/G/2 with cables handbook. In as new condition, these small portable recorders are very popular and are of current manufacture offered at less than half price.

**MUIRHEAD PHASE METER Type 729-AM** with associated power supply in perfect order... £275

**CROSSHATCH & DOT GENERATOR OL21** for 625 or 405 lines. Brand new... £40 P. & P. 50p

Honeywell Brown Electronic Recorder. Potentiometric type, single pole, 7 pos., 3 wafers. Primarily used for channel switching in Radio-Telephones. Wafers may be substituted offered as new perfect order £225

Miniature solenoid driven wafer switches, type-Ledex Recorder. Potentiometric type, single pole, 7 pos., 3 wafers. Primarily used for channel switching in Radio-Telephones. Wafers may be substituted offered as new perfect order £225

**AIRMEC PORTABLE RF SIGNAL GENERATOR. AM/FM. Type CT212**. Specially designed for field use for mains or 12v operation. Frequency range 85kHz to 30MHz. Accurate scale calibration. \*Variable output from 1 micro V 100mV 0 to 80db. Offered in excellent condition. Only £45

**TEKTRONIX 551 WITH TWO PLUG INS PERFECT CONDITION**

**MARCONI 801D A.M. SIGNAL GENERATOR 10-470 MHz OUTPUT 0.1 µV to 1V**

**MARCONI TF867** Standard RF Signal Generator, range 16kHz to 30MHz. Variable output from 4 micro V to 4 Volts. Extremely accurate attenuator, high output stability and discrimination make the generator very suitable for precision measurements on networks and filters. Modulation up to 100% may be applied at 400 or 1000 Hz. Built in crystal calibrator. Offered in first class condition. Price £175.

**MAGNIFICATION METERS**

Marconi Q Meter Model TF329G perfect condition £50  
Marconi HF Q Meter TF886A perfect condition... £40  
Advance Q Meter Model T.2 perfect condition... £40  
Dawe Production Q Meter Model 620C brand new £55

**TEKTRONIX 515A and TEKTRONIX 524AD AVAILABLE NOW**

**GOOD QUALITY TEST EQUIPMENT ALWAYS REQUIRED, QUOTATION BY RETURN.**

**LF OSCILLATORS & GENERATORS**

Solartor constant output generator model DO905 range 50kHz-50MHz OP between 10mV & 10 volts as new... £85  
Donner sinewave oscillator 1Hz-100kHz... £35  
AIRMEC Model 257 LF signal generator. Range 0-003-30Hz... £85  
AIRMEC Model-858 range 30-1,000kHz & 1-30MHz in 7 ranges... £37  
Wayne Kerr Video Osc' model 0-228 10Hz to 10MHz... £75  
Marconi oscillator TF885A 25Hz-5MHz sine & 50Hz-150kHz square wave, variable O.p. 316uV to 31.6 volts... £30  
TS-47APR range 40-500MHz. function modulated/pulse/CW. mains or battery operated small portable unit... £30  
The above instruments are in excellent operational order & condition, for mains voltage operation unless stated.

**CANNON XLR AUDIO SERIES PLUGS & SOCKETS**

XL 3-31 3-Pole Socket } 150p  
XL 3-12 3-Pole Plug } The pair  
XL 3-11 3-Pole Plug } 125p  
XL 3-32 3-Pole Socket } The pair  
XL 6-11 6-Pole Plug } 150p  
XL 6-32 6-Pole Socket } The pair  
Offered Brand New. Sealed Packs at a little over 1/2 List Price.

**MARCONI 1094 A/S HF SPECTRUM ANALYSER 3-30MHz LATE MODEL FOR SALE OR HIRE**

**MULLARD HIGH SPEED VALVE TESTERS**. We have a small quantity of these very popular testers available late model. Complete with cards and in good working order. Price £45

**LUCAS CAR RELAYS**. 12 v. Heavy duty make. Suitable for spotlights, horns, overdrives, etc. Brand new. Only 37p. Special price for quantities.

**BARGAIN OFFER**  
200-yard reels equipment wire, size 1/024, STC quality, various colours. Brand new reels only 75p. P. & P. 12p.

**LOW VOLTAGE POWER SUPPLY UNITS**

To supply 12-15-20-24 and 30 volts at continuous 5 amps with current control and ammeter employs silicon heavy duty rectification and high quality components very suitable for light duty plating and charging duties. 240 v. AC supply, fully fused. Small size only 10x7x6 in. Offered brand new units. Price £12.50.

**HUNTER MAGSLIPS 3 inch Series, Type E-18-V/2**. Very suitable for servo operation of hydraulic valves radar aerials and other applications for 50 volt 50 cycle operation. Offered brand new in transit boxes, at only £3.25 each.

**Rhode & Schwarz UHF 1000 Load Resistor**. An oil immersed load 0-600 MHz 60 ohms 1000 watts. Type RD 1/60-FNr H3086/14. Price £85 carriage extra.

**LEEDS & NORTHRUP Integra**. Slow speed chart recorder and Temperature controller for use with chrome AL couples/temperature range 0-1000°C incorporates POTENTIOMETRIC RECORDER & Sensitive Controller Series 60. Offered in good used condition... £105

**Noise Generator Model CT-82** Range 15kHz to 160MHz very useful noise for factor measurements of receivers/wide band I.F. amplifiers etc., the instrument is directly calibrated in noise factor and displayed on panel meter, also output meter calibrated in db, for 115-250 vac operation offered in good used condition, small size low price only £8 Carr. 50p.

**Cossor Electronic Invertors type CRA 200**. A high quality device for producing a 115v 400Hz single phase output. Incorporating the following features: Input 23-28V D.C.  
\* Full overload protection.  
\* Sine wave output.  
\* Remote control facilities.  
\* Completely Solid State (Silicon transistors).  
\* Built to Aircraft specifications.  
\* 180VA of output continuous.  
May be run in series operation for 3 phase requirements. Offered brand new boxed units. Price £17.50 Carriage 50p

**Constant Voltage DC Power Supplies Model DC8**

A stabilised unit supplying 48vdc at 4 amps input 200-245vac stabilised to within +1% at full load. Supplied new... £22

**VARIAC TRANSFORMERS**

8 amp type fully shrouded with scale plate & control knob. Good used condition. Price £10 Carriage 75p.  
Also 3 amp type as above £4.50p Carr.50p

**KIENZLE ELECTRONIC PRINTER model D11-E** as new condition... £150  
\*Videoon Tubes Cathodeon type C9138A brand new at surplus price... £15  
Cambridge model D.E. Potentiometric Recorder. Single point type. Range 0-10 mVs. Chart speed 30in./Hr. Slide wire accuracy 0.3% offered brand new with manual and components, charts etc.

**A.E.I. MINIATURE UNISELECTOR SWITCHES**

No waiting, straight off the shelf and into your equipment, the Catalogue Nos. are 2202A, 4/33A63/1; coil resistance is 250 ohms. Complete with base, and the price is £5. Limited quantity only available.  
Also: 2203A, 2200A, 2202A.

**SEARCH RECEIVERS AN/APR/4** Range 38-1000 mHz with 3 RF tuning heads, circuit diagrams, etc. £95.

**AERIAL CHANGE/OVER RELAYS**

of current manufacture designed especially for mobile equipments, coil voltage 12 v., frequency up to 250 MHz at 50 watts. Small size only, 2 in. x 1/2 in. Offered brand new, boxed. Price £1.50, inc. P.&P.

**COAXIAL SWITCHES American Manufacture**

Suitable for aerial changeover and high frequency switching up to 1,000 MHz miniature Vacuum drawn type 110 v dc operation connections BNC and N types. Offered brand new, boxed. Price £3.25.

**LEAD-ACID EQUIPMENT BATTERIES 10v 5AH.**

Transparent casing. Size 2 1/2 x 5 x 7 in. Offered brand new and boxed, 2 batteries per box, complete with links and full instructions. Can supply voltages in the range from 2-20V. Price £2.25, inc. P.&P.

**BURNDIPT RF PLUGS** still available.

These hard to find plugs are used on a multitude of equipment, especially Lendex aerial c/o relays. Offered new ex. equipment. 2 for 50p, inc. p.p.

**NIFE traction Batteries Nickel Iron.**

1-2V per cell rated at 180 A.H. Sold in crates of three cells or crates of five cells. £4 per cell. Guaranteed best buy.

**BT91-500R THYRISTORS**

500 PIV Max rect. Current 16 amps. Guaranteed perfect. Price £1.25 each.

**COLVERN HELICAL POTS**

1K ohms }  
5K ohms } ALL TEN TURN  
10K ohms }  
20K ohms }  
30K ohms } PRICE £1.75

**ELECTRONICS VOLTMETERS** for low level signal sources.

**PYE High Impedance DC Amplifier** for measurements better than 20 uV to 10 volts centre zero. Price £56.

**PHILLIPS GM 6010** 1 mV FSD to 300 V in 12 ranges. Price £45

**PHILLIPS PM 2530** 1 mV FSD to 300 V in 12 ranges RMS voltmeter 10 Hz to 1 MHz. Price £45

**SOLARTRON VF-252**. AC millivoltmeter 1-5 mV for FSD to 15 V 30 M ohms impedance. Price £65

**H. W. SULLIVAN STANDARD AIR SPACED CONDENSERS**

Capacitance range 0 to 100 pf fully screened with engraved vernier subdivided into 100 equal divisions complete with vernier index and original manufacturers seal offered brand new, at only £25 each.

**P.F. RALFE** 10 CHAPEL ST. LONDON N.W.1 Phone 01-723 8753

# NEW 1971 CATALOGUE NOW READY—10p post free

64 pages—thousands of items plus pages of valuable technical information. OUR BEST YET.

# ELECTROVALUE Electronic Component Specialists

**EVERYTHING BRAND NEW TO SPEC • LARGE STOCKS • NO SURPLUS**

## ★ SIEMENS

### TTL INTEGRATED CIRCUITS

FLH101 (7400) Quad 2-input NAND	20p
FLH201 (7401) Quad 2-input NAND (open collector)	20p
FLH191 (7402) Quad 2-input NOR	20p
FLH211 (7404) Hex inverter	25p
FLH271 (7405) Hex inverter (open collector)	25p
FLH111 (7410) Triple 3-input NAND	20p
FLH351 (7413) Dual 4-input Schmitt trigger	35p
FLH121 (7420) Dual 4-input NAND	20p
FLH141 (7440) Dual 4-input NAND power	24p
FLH281 (7442) BCD to decimal converter	£1.16
FLH151 (7450) Expandable dual 2 wide 2 input	20p
FLH171 (7453) Expandable 4 wide 2 input	20p
FLY101 (7460) Dual 4-input expander	20p
FLJ101 (7470) J-K flip flop	45p
FLJ111 (7472) J-K master slave flip flop	32p
FLJ141 (7474) Dual D-type edge triggered flip flop	45p
FLJ151 (7475) Quad bi-stable latch	45p
FLJ131 (7476) Dual J-K master slave flip flop	45p
FLH341 (7486) Half adder	33p

## ★ SIEMENS 5% TOLERANCE POLYCARBONATE CAPACITORS

250V up to 0.1mF: 100V 0.1mF and above

0-01, 0-012, 0-015, 0-018, 0-022, 0-027	5p
0-033, 0-039, 0-047, 0-056, 0-068, 0-082, 0-1, 0-12, 0-15, 0-18	6p
0-22	7p
0-27	8p
0-33	8p

## NEW PEAK SOUND SPECIAL OFFER

Fantastic new Englefield 840 amplifier with add-in facilities for stereo tuner, advertised at £45. Special Electrovalue offer, plus choice of case finish in black, red, blue or green simulated leather. In makers sealed carton and guaranteed. **NETT £38.75**

## MISCELLANEOUS ITEMS

**PLESSEY INTEGRATED CIRCUIT**  
SL403D ... £2.10 nett  
Application data ... 10p

**30W BAILEY AMP. PARTS**  
Transistors R5 and PCB for one channel ... £6.46  
R5 and C5, and PCB for one channel ... £8.41

**MAIN LINE AMPLIFIERS**  
70 watt kit ... £12.60 nett

**INDICATOR LAMPS**  
NEON chrome bezel, round red NR/R, 24p; chrome bezel, round amber NR/A, 24p; chrome bezel, round clear NR/3, 24p. Neon, square red type LS5C/R, 18p; amber type LS5C/A, 18p; clear type LS5C/C, 18p. All above are for 240v. mains operation.  
Filament: 6v, 0-04A square red type LS5C/R-6v, 30p; 6v, 0-04A amber type LS5C/A-6v, 30p; 6v, 0-04A clear type LS5C/C-6v, 30p; 6v, 0-04A green type LS5C/G-6v, 30p; 12v, 0-04A LS5C/R-12v, 34p; 28v, 0-04A LS5C/R-28v, 45p. Other colours available in 12 and 28 volts.

**DIN CONNECTORS**

Pole	Plug	Socket
2 (Spkr)	12p	10p
3	13p	10p
4	14p	12p
5 180°	15p	12p
5 240°	15p	12p
6	15p	13p

**ENAMELLED COPPER WIRE**  
Even No. SWG only: 2 oz. reels: 16-22 SWG 25p; 24-30 SWG 30p; 32, 34 SWG 33p; 36-40 SWG 35p. 4 oz. reels: 16-22 SWG only 41p.

**S-DECS**  
Components just plug in—saves time—allows reuse of components. S-Dec (70 points), £1.00 T-Dec, may be temperature-cycled (208 points), £2.50. Also µ-Decs and IC carriers.

**TYGAN SPEAKER MATERIAL**  
7 designs, 36 x 27 in. sheets, £1.58 sheet.

**THERMISTORS**  
VA1039, VA1040, VA1055, VA1066, VA1077, CZ-6, K151-1K, 15p, £2.4, R53, £1.35.

**LIGHT DEPENDENT RESISTORS**  
Cadmium Sulphide type TPMD (equiv. ORP.12), 40p.

**BRIDGE RECTIFIERS**

Silicon	rms	Imax	
1B40K10	70	4A	£1.75
W02	140	1A	£0.40
WPO2	140	2A	£0.95
BY164	42	1.4A	£0.45
B1912	80	*1.5A	£0.66
C1412	80	*3.2A	£1.02
E2512	80	*1.5A	£1.64

\*Reduce rating by 30% if nos contact cooled.

## BARGAINS IN NEW SEMI-CONDUCTORS

MANY AT NEW REDUCED PRICES • ALL POWER TYPES WITH FREE INSULATING SETS

40361	55p	2N2905	44p	2N4291	15p	BC148	9p	BFX88	29p
40362	65p	2N2905A	47p	2N4292	15p	BC149	10p	BFX87	26p
2N696	17p	2N2924	20p	AC107	46p	BC153	19p	BFY50	23p
2N697	18p	2N2925	22p	AC126	20p	BC154	20p	BFY51	20p
2N706	12p	2N2926	11p	AC127	20p	BC157	12p	BFY52	23p
2N930	29p	2N3053	27p	AC128	20p	BC158	11p	BSX20	16p
2N1131	29p	2N3055	60p	AC153K	22p	BC159	12p	C407	17p
2N1132	29p	2N3702	13p	AC176	16p	BC167	11p	MCI40	25p
2N1302	19p	2N3703	13p	ACY20	20p	BC168	10p	MPS6531	35p
2N1303	19p	2N3704	13p	ACY22	16p	BC169	11p	MPS6534	30p
2N1304	26p	2N3705	13p	AD140	43p	BC177	14p	NKT211	25p
2N1306	26p	2N3706	13p	AD142	50p	BC178	13p	NKT212	25p
2N1307	33p	2N3707	13p	AD149	58p	BC179	14p	NKT214	23p
2N1308	36p	2N3708	10p	AD161	33p	BC182L	11p	NKT274	18p
2N1309	36p	2N3709	11p	AD162	36p	BC183L	10p	NKT403	65p
2N1613	23p	2N3710	13p	AF114	24p	BC184L	11p	NKT405	79p
2N1711	26p	2N3711	13p	AF115	24p	BC212L	16p	OC71	38p
2N1893	54p	2N3819	23p	AF117	22p	BC213L	16p	OC81	25p
2N2147	95p	2N3904	35p	AF124	33p	BC214L	16p	OC83	20p
2N2218	34p	2N3906	35p	AF127	22p	BCY70	19p	ZTX300	14p
2N2218A	44p	2N4058	13p	AF139	33p	BCY71	33p	ZTX301	16p
2N2219	38p	2N4059	10p	AF239	36p	BCY72	15p	ZTX302	22p
2N2219A	53p	2N4060	11p	ASY26	27p	BF115	23p	ZTX303	22p
2N2270	62p	2N4061	11p	ASY28	27p	BF167	18p	ZTX304	27p
2N2369A	19p	2N4062	12p	BC107	12p	BF173	19p	ZTX500	18p
2N2483	35p	2N4124	18p	BC108	11p	BF194	14p	ZTX501	21p
2N2484	42p	2N4126	27p	BC109	12p	BF195	15p	ZTX502	25p
2N2646	47p	2N4284	15p	BC125	15p	BFX29	31p	ZTX503	22p
2N2904A	42p	2N4286	15p	BC126	22p	BFX84	25p	ZTX504	52p
		2N4289	15p	BC147	10p	BEX85	34p		

## RESISTORS—10%, 5%, 2%

Code	Power	Tolerance	Range	Values available	to 9 (see note below)	10 to 99	100 up
C	1/20W	5%	82Ω-220KΩ	E12	9	8	7
C	1/8W	5%	4.7Ω-470KΩ	E24	1	0.8	0.7
C	1/4W	10%	4.7Ω-10MΩ	E12	1	0.8	0.7
C	1/2W	5%	4.7Ω-10MΩ	E24	1.2	1	0.9
C	1W	10%	4.7Ω-10MΩ	E12	2.5	2	1.8
MO	1/2W	2%	10Ω-1MΩ	E24	4	3.5	3
WW	1W	10% ± 1/20Ω	0.22Ω-3.9Ω	E12	7	7	6
WW	3W	5%	12Ω-10KΩ	E12	7	7	6
WW	7W	5%	12Ω-10KΩ	E12	9	9	8

Codes: C = carbon film, high stability, low noise.  
MO = metal oxide, Electrocoil TR5, ultra low noise.  
WW = wire wound, Plessey.

Values:  
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.  
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

**CARBON TRACK POTENTIOMETERS**, long spindles. Double wiper ensures minimum noise level.  
Single gang linear 100Ω to 2.2MΩ, 12p; Single gang log, 4.7KΩ to 2.2MΩ, 12p; Dual gang linear 4.7KΩ to 2.2MΩ, 42p; Dual gang log, 4.7KΩ to 2.2MΩ, 42p; Log/antilog, 10K, 47K, 1MΩ only 42p; Dual antilog, 10K only, 42p. Any type with 1/2 A D.P. mains switch, 12p extra.  
Only decades of 10, 22 & 47 available in ranges quoted.

**CARBON SKELETON PRE-SETS**  
Small high quality, type PR, linear only: 100Ω, 220Ω, 470Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10MΩ. Vertical or horizontal mounting, 5p each.

**COLVERN 3 watt Wire-wound Potentiometers**, 10Ω, 15Ω, 25Ω, 50Ω, 100Ω, 150Ω, 250Ω, 500Ω, 1K, 1.5K, 2.5K, 5K, 10K, 15K, 25K, 50K, 32p each

**ZENER DIODES 5% full range E24 values**: 400mW: 2.7V to 30V, 15p each; 1W: 6.8V to 82V, 27p each; 1.5W: 4.7V to 75V, 60p each.  
Clip to increase 1.5W rating to 3 watts (type 266F), 4p.

Appointed Distributors for SIEMENS (UK) LTD.  
Appointed Stockists for NEWMARKET TRANSISTORS RADIOHM POTENTIOMETERS

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions on total value of resistor order.)

## CAPACITORS

**MULLARD polyester C280 series**  
250V 20%: 0-01, 0-022, 0-033, 0-047 3p each; 0-068, 0-1, 4p each; 0-15, 4p; 0-22, 5p. 10%: 0-33, 7p; 0-47, 8p; 0-68, 11p; 1μF, 14p; 1.5μF, 21p; 2.2μF, 24p.

**MULLARD SUB-MIN ELECTROLYTIC C426 range, axial lead** 6p each  
Values (μF/V): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5/64; 6.4/6.4; 6.4/25; 8/4; 8/40; 10/2.5; 10/16; 10/64; 12.5/25; 16/10; 16/40; 20/16; 20/64; 25/6.4; 25/25; 32/4; 32/10; 32/40; 32/64; 40/16; 40/2.5; 50/6.4; 50/25; 50/40; 64/4; 64/10; 80/2.5; 80/16; 80/25; 100/6.4; 125/4; 125/10; 125/16; 160/2.5; 200/6.4; 200/10; 250/4; 320/2.5; 320/6.4; 400/4; 500/2.5.

**LARGE CAPACITORS**  
High ripple current types: 1000/25, 28p; 1000/50, 41p; 1000/100, 82p; 2000/25, 37p; 2000/50, 57p; 2000/100, £1.44; 2500/64, 77p; 2500/70, 98p; 5000/25, 62p; 5000/50, £1.10; 5000/100, £2.91; 10000/50, £2.40.

**HANDBOOK OF TRANSISTOR EQUIVALENTS & SUBSTITUTES** 40p (Post 3p if ordered alone.)

## COMPONENT DISCOUNTS

Not allowed on nett price items  
**10%** on orders for components for £5 or more.  
**15%** on orders for components for £15 or more.  
Prices subject to alteration without prior notice.

**POSTAGE & PACKING**  
FREE on orders over £2. Please add 10p if orders under £2. Overseas orders welcome: carriage and insurance charged at cost.

# ELECTROVALUE

DEPT. WW.871, 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY,  
Hours: 9-5.30, 1.0 p.m. Saturdays. Phone: Egham 5533 and 4757 (STD 0784-3) Telex 264475

# BI-PAK=LOW COST I.C.'s VALUE ALL THE WAY

BI-PAK Semiconductors now offer you the largest and most popular range of I.C.'s available at these EXCLUSIVE LOW PRICES. T.T.L. Digital SN 74N Series fully coded, brand new to Manufacturers' Specifications. Dual In-Line plastic 14 & 16 pin packages.

BI-PAK Order No.	Description	Price and Qty.	Prices 1-24	Prices 25-99	Prices 100 up
BP 00 = 7400	Quadruple 2-input NAND Gate	23p	20p	15p	
BP 01 = 7401	Quadruple 2-input Positive NAND Gate (with open collector output)	23p	20p	15p	
BP 02 = 7402	Quadruple 2-input Positive NOR Gates	23p	20p	15p	
BP 03 = 7403	Quadruple 2-input Positive NAND Gates (with Open-Collector Output)	23p	20p	15p	
BP 04 = 7404	Hex Inverters	23p	20p	15p	
BP 10 = 7410	Triple 3-input Positive NAND Gates	23p	20p	15p	
BP 13 = 7413	Dual 4-input Schmitt Trigger	35p	32p	29p	
BP 20 = 7420	Dual 4-input Positive NAND Gates	23p	20p	15p	
BP 30 = 7430	8-input Positive NAND Gates	23p	20p	15p	
BP 40 = 7440	Dual 4-input Positive NAND Buffers	23p	20p	15p	
BP 41 = 7441	BCD to decimal niche driver	87p	77p	67p	
BP 42 = 7442	BCD to decimal decoder (4-10 lines, 1 of 10)	87p	77p	67p	
BP 47 = 7447	BCD-Seven-Segment Decoder/Drivers (15-V Outputs)	£1.40	£1.30	£1.20	
BP 50 = 7450	Expandable dual 2-input AND-OR-INVERT	23p	20p	15p	
BP 51 = 7451	Dual 2-wide 2-input AND-OR-INVERT GATES	23p	20p	15p	
BP 53 = 7453	Quad 2-input Expandable AND-OR-INVERT	23p	20p	15p	
BP 54 = 7454	4-wide 2-input AND-OR-INVERT Gates	23p	20p	15p	
BP 60 = 7460	Dual 4-input Expander	23p	20p	15p	
BP 70 = 7470	Single-phase J-K Flip-Flop	35p	32p	29p	
BP 72 = 7472	Master-slave J-K Flip-Flop	35p	32p	29p	
BP 73 = 7473	Dual Master-slave J-K Flip-Flop	43p	40p	37p	
BP 74 = 7474	Dual 0 type Flip-Flop	43p	40p	37p	
BP 75 = 7475	Quad latch	47p	45p	43p	
BP 76 = 7476	Dual J-K with pre-set and clear	47p	45p	43p	
BP 80 = 7480	Gated Full Adders	77p	77p	67p	
BP 81 = 7481	16-bit read/write memory	£1.25	£1.25	£1.15	
BP 82 = 7482	2-bit Binary Full Adder	£1.30	£1.20	£1.00	
BP 83 = 7483	Quad Full Adder	87p	77p	67p	
BP 86 = 7486	Quad 2 input Exclusive OR Gates	80p	70p	60p	
BP 90 = 7490	BCD decade counter	87p	77p	67p	
BP 91 = 7491	8-bit Shift Registers	£1.21	£1.00	87p	
BP 92 = 7492	Divide-by-Two Counters	87p	77p	67p	
BP 93 = 7493	4-bit Binary Counters	87p	77p	67p	
BP 94 = 7494	Dual entry 4-bit shift register	87p	77p	67p	
BP 95 = 7495	4-bit up-down shift register	87p	77p	67p	
BP 96 = 7496	5-bit Parallel in parallel out Shift-Register	£1.10	£1.00	90p	
BP 99 = 7499	5-bit Bistable Latches	£1.75	£1.65	£1.55	
BP118 = 74118	Hex Set-Reset Latches	£1.30	£1.20	£1.00	
BP121 = 74121	Monostable Multivibrators	87p	77p	67p	
BP141 = 74141	BCD-to-Decimal Decoder/Driver	87p	77p	67p	
BP145 = 74145	BCD-to-Decimal Decoder/Drivers	£1.80	£1.70	£1.60	
BP151 = 74151	8-bit Data Selectors (with Strobes)	£1.40	£1.30	£1.20	
BP153 = 74153	Dual 2-Line-to-1-Line Data Selectors/Multiplexers	£1.50	£1.40	£1.30	
BP191 = 74191	Binary Counter reversible	£3.50	£3.25	£3.00	

Devices may be mixed to quantity for quantity price. Larger quantities—prices on application. (TTL 74 Series only).

Data is available for the above series of I.C.'s in booklet form. PRICE 13p.

## TTL INTEGRATED CIRCUITS

Manufacturers' "Full out"—out of spec. devices including functional units and part function but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C.'s and experimental work.

PAK No.	PAK No.	PAK No.
UIC00 = 12 x 7400N 50p	UIC42 = 5 x 7450N 50p	UIC80 = 5 x 7480N 50p
UIC01 = 12 x 7401N 50p	UIC50 = 12 x 7450N 50p	UIC82 = 5 x 7482N 50p
UIC02 = 12 x 7402N 50p	UIC51 = 12 x 7451N 50p	UIC83 = 5 x 7483N 50p
UIC03 = 12 x 7403N 50p	UIC60 = 12 x 7460N 50p	UIC86 = 5 x 7486N 50p
UIC04 = 12 x 7404N 50p	UIC70 = 8 x 7470N 50p	UIC90 = 5 x 7490N 50p
UIC05 = 12 x 7405N 50p	UIC72 = 8 x 7472N 50p	UIC92 = 5 x 7492N 50p
UIC10 = 12 x 7410N 50p	UIC73 = 8 x 7473N 50p	UIC93 = 5 x 7493N 50p
UIC20 = 12 x 7420N 50p	UIC74 = 8 x 7474N 50p	UIC94 = 5 x 7494N 50p
UIC40 = 12 x 7440N 50p	UIC75 = 8 x 7475N 50p	UIC95 = 5 x 7495N 50p
UIC41 = 5 x 7441AN 50p	UIC76 = 8 x 7476N 50p	UIC96 = 5 x 7496N 50p

Packs cannot be split but 20 assorted pieces (our mix) is available as PAK UICX1. Every PAK carries our BI-PAK Satisfaction or money back GUARANTEE.

## DTL 930 SERIES

Type No.	Function	Price
BP930	Expandable dual 4-input NAND	23p
BP932	Expandable dual 4-input NAND buffer	23p
BP933	Dual 4-input expander	25p
BP935	Expandable Hex Inverter	25p
BP936	Hex Inverter	25p
BP944	Dual 4-input NAND expandable buffer without pull-up	25p
BP945	Master-slave JK or RS	35p
BP946	Quad, 2-input NAND	23p
BP948	Master-slave JK or RS	35p
BP951	Monostable	80p
BP962	Triple 3-input NAND	23p
BP9093	Dual Master-slave JK with separate clock	80p
BP9094	Dual Master-slave JK with separate clock	80p
BP9097	Dual Master-slave JK with Common Clock	80p
BP9099	Dual Master-slave JK Common Clock	80p

Devices may be mixed to quantity for quantity price. Larger quantity prices on application. (DTL 930 Series only).

DTL (Diode Transistor Logic) INTEGRATED CIRCUITS manufacturers' "Full out"—out of spec. devices including functional units and part functional but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C.'s and experimental work.

PAK No.	PAK No.	PAK No.
UIC930 = 12 x $\mu$ A 930 50p	UIC948 = 8 x $\mu$ A 948 50p	UIC985 = 12 x $\mu$ A 985 50p
UIC932 = 12 x $\mu$ A 932 50p	UIC951 = 12 x $\mu$ A 951 50p	UIC986 = 12 x $\mu$ A 986 50p
UIC933 = 12 x $\mu$ A 933 50p	UIC952 = 12 x $\mu$ A 952 50p	UIC987 = 12 x $\mu$ A 987 50p
UIC935 = 12 x $\mu$ A 935 50p	UIC9093 = 5 x $\mu$ A 9093 50p	UIC988 = 12 x $\mu$ A 988 50p
UIC936 = 12 x $\mu$ A 936 50p	UIC9094 = 5 x $\mu$ A 9094 50p	UIC989 = 12 x $\mu$ A 989 50p
UIC944 = 12 x $\mu$ A 944 50p	UIC9097 = 5 x $\mu$ A 9097 50p	UIC990 = 12 x $\mu$ A 990 50p
UIC945 = 8 x $\mu$ A 945 50p	UIC9099 = 5 x $\mu$ A 9099 50p	UIC991 = 12 x $\mu$ A 991 50p
UIC946 = 12 x $\mu$ A 946 50p	UIC 9 25 Assorted 930 Series 51.50	UIC992 = 12 x $\mu$ A 992 50p

Packs cannot be split but 25 assorted Pieces (our mix) is available as Pack UICX9. Every PAK carries our BI-PAK Satisfaction or money back guarantee. Data Booklet available for the BP930 Series. PRICE 13p

## LINEAR I.C.'s

Type No.	Case	Leads	Description	Price
BP201C-8L201C	To-5	8	G.P. Amp	43p
BP701C-8L701C	To-5	8	OP Amp.	63p
BP702C-8L702C	To-5	8	OP Amp Direct O/P.	63p
BP709-72709	D.I.L.	14	G.P. O.P. Amp (Wide Band)	53p
BP709-72709	D.I.L.	14	High Gain OP Amp.	53p
BP709P-8L709C	To-8	8	High Gain OP Amp.	53p
BP741-72741	D.I.L.	14	High Gain OP. Amp (Protected)	73p
8L709C-8L709C	TP-5	6	R.F.-IF Amp	43p
TAA263	To-72	4	A.F. Amp	70p
TAA263	To-74	10	G.P. Amp	90p

## "Q" PAKS QUALITY TESTED SEMICONDUCTORS

PAK No.	Description	Price
Q 1	20 Red spot trans. P.N.P.	50p
Q 2	16 White spot R.F. trans. P.N.P.	60p
Q 3	4 OC 77 type trans.	50p
Q 4	6 Matched trans. OC44/45/81/81D	50p
Q 5	4 OC 75 transistors	50p
Q 6	4 OC 72 transistors	50p
Q 7	4 AC 128 trans. P.N.P. high gain	50p
Q 8	4 AC 126 trans. P.N.P.	50p
Q 9	7 OC 81 type trans.	50p
Q 10	7 OC 71 type trans.	50p
Q 11	2 AC 127/128 Comp. pairs PNP/ NPN	50p
Q 12	3 AF 115 type trans.	50p
Q 13	3 AF 117 type trans.	50p
Q 14	3 OC 171 H.F. type trans.	50p
Q 15	5 2N2950 811. Epoxy trans.	50p
Q 16	2 GET860 low noise Germ. trans.	50p
Q 17	3 NPN 1 BT141 & 2 BT140	50p
Q 18	4 Mad's 2 MAT 100 & 2 MAT 120	50p
Q 19	3 Mad's 2 MAT 101 & 1 MAT 121	50p
Q 20	4 OC 44 Germ. trans. A.F.	50p
Q 21	3 AC 127 NPN Germ. trans.	50p
Q 22	20 NKT trans. A.F. R.F. coded	50p
Q 23	10 OA920 811 diodes sub-min.	50p
Q 24	8 OA 81 diodes	50p
Q 25	6 IN914 811. diodes 75PIV 75mA	50p
Q 26	8 OA95 811. diodes sub-min. IN69	50p
Q 27	2 10A 600PIV Sil. Rects. 18425R	50p
Q 28	2 Sil. power trans. BYZ13	50p
Q 29	4 Sil. trans. 2 x 2N696, 1 x 2N697, 1 x 2N698	50p
Q 30	7 Sil. switch trans. 2N706 NPN	50p
Q 31	6 Sil. switch trans. 2N708 NPN	50p
Q 32	3 PNP Sil. trans. 2 x 2N1131, 1 x 2N1132	50p
Q 33	3 Sil. NPN trans. 2N1711	50p
Q 34	7 Sil. NPN trans. 2N2369, 500MHZ	50p
Q 35	3 Sil. NPN TO-5 2 x 2N2904 & 1 x 2N2950	50p
Q 36	7 2N346 TO-18 plastic 300MHZ NPN	50p
Q 37	3 2N3063 NPN Sil. trans.	50p
Q 38	7 PNP trans. 4 x 2N3703, 3 x 2N3702	50p
Q 39	7 NPN trans. 4 x 2N3704, 3 x 2N3705	50p
Q 40	7 NPN trans. 4 x 2N3707, 3 x 2N3708	50p
Q 41	3 Plastic NPN TO-18 2N3904	50p
Q 42	6 NPN trans. 2N5172	50p
Q 43	7 BC 107 NPN trans.	50p
Q 44	7 NPN trans. 4 x BC108, 3 x BC109	50p
Q 45	3 BC 113 NPN TO-18 trans.	50p
Q 46	3 BC 115 NPN TO-5 trans.	50p
Q 47	6 NPN high gain 3 x BC167, 3 x BC168	50p
Q 48	4 BCY70 NPN trans. TO-18	50p
Q 49	4 NPN trans. 2 x BPY31, 2 x BPY52	50p
Q 50	7 B8Y 28 NPN switch TO-18	50p
Q 51	7 B8Y 95A NPN trans. 300MHZ	50p
Q 52	8 BY100 type sil. rect.	2p
Q 53	25 Sil. & 2 diodes trans. mixed all marked new	£1.50

TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalent book for European, American and Japanese Transistors. Exclusive to BI-PAK. 75p each.

## NEW LOW PRICE TESTED S.C.R.'s

PIV 1A	3A	7A	10A	16A	30A
50	206	206	206	206	206
100	25p	47p	50p	53p	£1.15
200	35p	53p	58p	63p	£1.40
400	35p	47p	57p	61p	£1.60
600	43p	47p	57p	59p	£1.75
800	53p	57p	77p	79p	£1.25
1000	63p	70p	80p	£1.20	£1.50

## EA POTTED BRIDGE RECTIFIERS

300mW	SIL. G.P. DIODES
200V. 50p	TO48 TO48
	50p
	Sub-Min. 500
	Full Tested 1000
	Ideal for Organ Builders.

## PRINTED CIRCUITS EX-COMPUTER

Packed with semiconductor components. 10 boards give a guaranteed 30 trans. and 30 diodes. Our price 10 boards 50p + 10p p. & p. 100 boards £3+30p p. & p.

## DUAL-IN-LINE LOW PROFILE SOCKETS

Order No.	Price each
T801 14 pin type	33p
T801 616 pin type	27p
	37p

## CADMIUM CELLS

ORP12	FET's
43p	2N3819 40p
40p	2N3820 21
40p	2N3821 43p

## PHOTO TRANS

OCPT1 Type	Price
43p	BY130 20p
	10-44p 3-KV. 3000 P.I.V.) Stud Type with Flying Leads, 80p each.


Please send all orders direct to our warehouse and despatch department. Postage and packing add 7p. Overseas add extra for Airmail. Minimum order 50p. Cash with order please.

## BI-PAK SEMICONDUCTORS P.O. BOX 6, WARE, HERTS.

## ANOTHER BI-PAK FIRST!

### THE NEW S.G.S. EA1000 AUDIO AMPLIFIER MODULE

\*GUARANTEED NOT LESS THAN 3 WATTS RMS

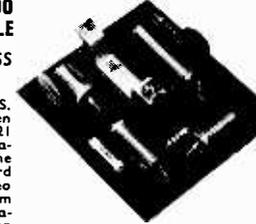

Especially designed by S.G.S. incorporating their proven Linear I.C. Audio Amp. TA621 providing unlimited applications for the enthusiast in the construction of radios, record players, Audio and Stereo units, also ideal for intercom systems, monitoring applications and phone answering machines. OTHER USES:— portable applications where supply rails as low as 9v are of prime importance.

- Overall Size 2x3x1/2".
- Typical Total Harmonic distortion at 1 Watt less than 1%.
- Supply Voltage (Vs) = 24V 15 ohm load.

- Sensitivity 40mV for 1 watt VOLTAGE GAIN 40dB but can be varied up to 73dB for some applications.
- Signal to Noise Ratio 66dB.
- Frequency response better than 50 Hz to 25 KHz for —3dB.
- Normal supply Voltage 9-25V.
- Suitable for 8-16 Ohm Loads.

Module Tested and Guaranteed. Qty. 1-9 10-25 Price each £2.63 £2.28 Larger quantities quoted on request.

Full hook-up diagrams and complete technical data supplied free with each module or available separately at 10p each.

## SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Unequaled Value and Quality Satisfaction GUARANTEED in Every Pak, or money back.

PAK No.	Description	Price
U1	120 Glass SUB-MIN. General Purpose Germanium Diodes	50p
U2	60 Mixed Germanium Transistors AF/RF	50p
U3	75 Germanium Gold Bonded Diodes sim. OA5, OA47	50p
U4	40 Germanium Transistors like OC81, AC128	50p
U5	60 200mA Sub-min. Sil. Diodes	50p
U6	30 Silicon Planar Transistors NPN sim. B8Y95A, 2N706	50p
U7	16 Silicon Rectifiers Top-Hat 750mA up to 1,000V	50p
U8	50 Sil. Planar Diodes 250mA OA/200/202	50p
U9	20 Mixed Volts 1 watt Zener Diodes	50p
U11	30 PNP Silicon Planar Transistors TO-5 sim. 2N1132	50p
U13	30 PNP-NPN Sil. Transistors OC290 & 28104	50p
U14	150 Mixed Silicon and Germanium Diodes	50p
U15	25 NPN Silicon Planar Transistors TO-5 sim. 2N697	50p
U16	10 3-amp Silicon Rectifiers stud Type up to 1,000 PIV	50p
U17	30 Germanium PNP AF Transistors TO-5 like ACY17-22	50p
U18	8 6-amp Silicon Rectifiers BYZ13 Type up to 600 PIV	50p
U19	25 Silicon NPN Transistors like BC108	50p
U20	12 1-5 amp Silicon Rectifiers Top-Hat up to 1,000 PIV	50p

**T.E.C. 240-110v. ISOLATION TRANSFORMERS**

Pri Tapped 10, 0, 200, 220, 240v. sec. Tapped 110-112.5-115v. Conservatively rated at 9 amps. Tropicalised open frame type. Terminal Board connections. Size 9 x 9 x 7 ins. Weight 60 lbs. £15-00. Carr. 90p.

**GARDNERS HEAVY V DUTY HT TRANSFORMERS**  
Pri. 110-220-240v. Sec. 255-0-6a. Conservatively rated. 'C' core Table top connections. Size 10 x 8 x 7 in. £12-75. Carr. £1-50.

**PARMEKO TRANSFORMERS**

Jupiter Series. Pri. 110v., 200-220-240v. Sec. 24-0-24v., 470 m/a. and 150v. 15 m/a. Hermetically sealed. £1-75. P. & P. 25p. Neptune Series. Pri. 110-200-220-240v. Sec. 250-0-250v. 70 m/a., 6-3v. 2a., 6-3v. 1a. £1-75. P. & P. 45p.  
Pri. T. 110-200-220-240v. Sec. 500-0-500v. 250 m/a., 6-3v. 4a., 6-3v. 4a., 6-3v. 3-5a., 5v. 3-5a. £6-75. Carr. 50p.  
Pri. T. 115-230v. Sec. 400-0-400v. 150 m/a. £2-50. P.P. 40p.  
Pri. T. 200-240v. Sec. 500-0-500v. 120 m/a., 6-3v. 3-5a., 6-3v. 3a., 5v. 3a. £2-50. P.P. 45p.

**GARDNERS EHT TRANSFORMERS**

Pri. 205-225-240v. E.S. Sec. 3200 2 m/a., 2v. 1.5a., 4v. 0-2a. £2-50. P.P. 35p. Pri. 200-220-240v. E.S. Sec. 3000v. 5 m/a., 4-6-3v. 2a., 4Kv. D.C. wkg. £3. P.P. 35p. Pri. 200-220-240v. E.S. Sec. 3500v. 25 m/a. £3-50. P.P. 40p. Parmeko. Pri. 230v. E.S. Sec. 2000v. 5 m/a., 4v. 1a., 4v. 0-5a. £2-50. P.P. 35p.

**ENGLISH ELECTRIC TRANSFORMERS**

Pri. 220-240v. Sec. tapped 30-57.5-115v. 0-5a. and 3v. 4a. 'C' core. £1-75. P.P. 30p. Pri. 230-250v. Sec. tapped 6-3-6-4-6-5-6-6v. 27a. 'C' core. £2-50. P.P. 30p.

**GARDNERS LT TRANSFORMERS**

Pri. 200-220-240v. Sec. 2-0-2v. 11a. Twice 8Kv. D.C. wkg. £3. P.P. 50p. Pri. 200-220-240v. Sec. 6-6v. 7a. Four time 4Kv. D.C. wkg. £3-50. P.P. 50p. Pri. 230-250v. Sec. 2-0-2v. 11a. 25Kv. D.C. wkg. £5-50. Carr. 75p.

**LT TRANSFORMERS**

**BY FAMOUS MANUFACTURERS**

Pri. 240v. Sec. 10-3v. 5a. Twice Conservatively rated. Table top connections. £3-75. Carr. 50p. Pri. 200-220-240v. Sec. 15v. 2-5a. and 13v. 6a. T.T. Connections conservatively rated £2-50. P.P. 50p. Pri. 100-110-220-240v. Sec. 24-5-0-24-5v. 0-75a. Conservatively rated 'C' core T.T. connections. £1-50. P.P. 35p. Pri. 200-220-240v. Sec. 15v. 1a. Twice. £1. P.P. 35p.

**REDCLIFFE 'C' CORE TRANSFORMERS**

All Primaries tapped 200-220-240v. Table top connections. Sec. 130v., 450 m/a. Three times. £4-25. P. & P. 40p. 11-0-11v., 176 m/a. 75p. P. & P. 20p. 22v., 0-9a. and 21v., 60 m/a. 75p. P. & P. 25p. 370-390-410v., 6 m/a. 50p. P. & P. 20p. 28-8-0-28-8v., 150 m/a. 90p. P. & P. 25p. 128-0-128v., 20 m/a. 90p. P. & P. 25p. 45v., 25 m/a. and 1v., 0-5a. 50p. P. & P. 20p. 23-5v., 0-1a. twice. 75p. P. & P. 20p. 6-3v., 10-6a. Conservatively rated. £1-75. P. & P. 25p. 20-24-28-32-36-40v., 250 m/a. Twice. £1-50. P. & P. 30p. 90-0-90v., 100 m/a. 75p. P. & P. 20p.

**LOW TENSION SMOOTHING CHOKES**

By Redcliffe. 100MH. 2 amps. £2-50 P. & P. 45p. Swinging Types. 10MH. 6-5 amp-5CMH. 2 amps. £2-25 P. & P. 45p. Both types less than 1 ohm res. Hermetically sealed. Oil filled. Brand new. In makers cartons.

# Samson's

(ELECTRONICS) LTD.

9 & 10 CHAPEL ST., LONDON, N.W.1

01-723-7851

01-262-5125

**CURRENT RANGE OF BRAND NEW L.T. TRANSFORMERS. FULLY SHROUDED (excepted) TERMINAL BLOCK CONNECTIONS. ALL PRIMARIES 220/240v**

No.	Sec. Taps	Amps	Price	Carr.
1A	25-33-40-50	15	£10-50	65p
1B	25-33-40-50	10	£7-75	50p
1C	25-33-40-50	6	£6-75	50p
1D	25-33-40-50	3	£4-00	40p
2A	4-16-24-32	12	£7-25	45p
2B	4-16-24-32	8	£5-50	45p
2C	4-16-24-32	4	£3-75	40p
2D	4-16-24-32	2	£2-50	30p
3A*	25-30-35	20	£10-25	75p
3B*	25-30-35	10	£7-25	60p
3C	25-30-35	6	£4-25	45p
3D	25-30-35	5	£3-25	45p
3E	25-30-35	2	£13-00	75p
4A*	12-20-24	30	£3-00	40p
4B	12-20-24	20	£3-75	50p
4C	12-20-24	10	£4-50	50p
4D	12-20-24	5	£3-75	45p
5A	3-12-18	30	£9-75	45p
5B	3-12-18	20	£7-25	50p
5C	3-12-18	10	£4-50	45p
5D	3-12-18	5	£3-00	40p
6A	48-56-60	2	£3-75	50p
6B	48-56-60	1	£2-75	35p
7A*	6-12	50	£10-50	55p
7B	6-12	20	£6-25	45p
7C	6-12	10	£3-75	35p
7D	6-12	5	£2-75	35p
8A	12-24	10	£3-75	35p
9A	17-32	1	£1-75	35p
10A*	9-15	2	£1-50	35p
11A	6-3	15	£2-50	35p
12A	30-25-0-25-30	2	£3-75	35p
13A	36	45	£16-50	75p

Note: By using the intermediate taps many other voltages can be obtained.  
Example: No. 1 ... 7-8-10-15-17-25-33-40-50v.  
No. 2 ... 4-8-12-16-20-24-32v.  
No. 5 ... 3-6-9-12-15-18v.

**AUTO TRANSFORMERS**

240v., 110v., or 100v. Completely Shrouded fitted with Two-pin American Sockets or terminal blocks. Please state which type required.

Type	Watts	Approx. Weight	Price	Carr.
1	80	2 1/2 lb.	£2-00	30p
2	150	4 lb.	£2-75	35p
3	300	6 1/2 lb.	£3-75	35p
4	500	8 1/2 lb.	£5-25	45p
5	1000	15 lb.	£7-25	50p
6	1500	25 lb.	£9-75	55p
7*	1750	28 lb.	£14-75	75p
8*	2250	30 lb.	£17-85	75p

\* Completely enclosed in beautifully finished metal case fitted with two 2-pin American sockets, neon indicator, on/off switch, and carrying handle.

**HIGH CAPACITY ELECTROLYTICS**

20,000 mfd. 35v. wkg. 10,000 mfd. 70v. wkg. Size 4 1/2 in. x 2 1/2 in. dia. 74p each. P.P. 10p. 25,000 mfd. 12v. wkg. 16,000 mfd. 25v. wkg. 1,250 mfd., 180v. wkg. 60p. P.P. 10p. T.C.C. Block type CE40M. 200 mfd. 380v. wkg. Size 9 x 3 x 2 in. 75p. P.P. 15p. Type CE44H. 250 mfd. 250v. wkg. Size 5 x 4 x 3 in. 50p. P.P. 15p.

**G.P.O. 4-WAY TELEPHONE CORDS**

Non kink coil type. Length closed 10 in. Fully expanded, 4 ft. Red only. 40p. inc. post.

**DIAMOND H RELAYS**

Type BR 115 BIT-9C 4 CO Contacts, 150 ohms. 26v., 250v. 15a. Enclosed in metal case. Size 1 1/2 x 1 in. dia. 75p. inc. post.

**OMRON SUB MINIATURE RELAYS**

Type 105IN. 12v. D.C. 1 C.O. 5 amp contact overall. Size 1 x 1 x 1 in. New and boxed with mounting screws. 45p. P.P. 5p.

**MAGNETIC DEVICES SEALED RELAYS**

5,000Ω, 3 C.O. contacts. Overall size 2 x 2 x 1 1/2 in. New boxed. 37 1/2p. P.P. 7 1/2p.

**ELECTRO METHODS 2.3v. A.C. CONTACTORS**

1 Heavy Duty Change-over Contact. Size 2 1/2 x 1 1/2 x 1 in. 50p. P.P. 10p.

**LONDEX PLUG-IN RELAYS**

Sealed type, 28v. D.C. Three heavy duty silver contacts. Size 2 x 2 x 1 in. Complete with base. 50p. P.P. 10p.

**MAGNETIC DEVICES 6v. D.C. CONTACTORS**

3 Heavy Makes contacts. Size 2 x 1 1/2 x 1 in. 50p. P.P. 10p.



**G.P.O. RELAYS 3000 TYPE**

75Ω 3M. 1B. 1 C.O. contacts. 30p. 200Ω 6M. 35p. 200Ω 2 heavy duty M. 2M. 35p. 500Ω 1 C.O. 1M. 30p. 250Ω 1 heavy make. 3B. 1M. 35p. P.P. all types 5p.

**G.P.O. MAGNETIC COUNTERS**

Type 100D. 4 digits. Operating voltage 3-6v. D.C. Size 3 1/2 x 1 x 1 in. 50p. P.P. 5p.

**HONEYWELL MICRO SWITCHES**

Type YZ RVW 84-N88. Lever operated. Make or break (3 tags). Three for 70p. inc. post.

**BURGESS MICRO SWITCHES**

Type MK 3BR/74. Norm closed or Norm open. 1/2 in. raised. Press Button, three for 60p. P.P. 5p.

**ADVANCE C/V TRANSFORMERS**

Type CV 15/95. Input 95-130v., 190-260v. Output 4v. rms + or -1%. 3 watts. Open frame type. £1-25. P.P. 75p.

**RANCO REFRIGERATION THERMOSTATS**

Type A.10. 100-250v. A.C. 1/2 h.p. 75p. P.P. 10p. Teddington type QJ. 100-150v. A.C. 1/2 h.p. 75p. P.P. 20p.

**NEWMARK SYNCHRONOUS MOTORS**

220-240v. 50 cycles, 3 watts 8 r.p.m. Overall size 2 x 2 x 2 in. 50p. P.P. 10p.



**VENNER SYNCHRONOUS BIO-DIRECTIONAL MOTORS**

220-240v. 50 cycles 40 r.p.m. automatically reverses wherever spindle stop is placed. Overall size 2 1/2 x 2 x 1 in. Spindle length 1/2 in. dia. 1/16th. An ideal motor for display, giving a forward and reverse motion. 60p. P.P. 15p.

# Would You Believe

that an aircraft can cut costs and improve your company's EFFICIENCY?

Come and find out—at  
**CRANFIELD**  
Bedfordshire, England

SPONSORED BY



September 1-5 1971

**TICKET DISCOUNT COUPON**

Worth £1 on a single-day ticket (normal price £2)

Please send the following tickets to the address below:  
Single-day ticket at £1 each. Number required .....  
Remittance enclosed £.....  
Please write (block capitals) in the space below the name and address to which the tickets should be sent:  
NAME .....  
ADDRESS .....

Completed coupons and remittances (cheques or postal orders) should be addressed with this coupon to ITF-Iliffe Exhibitions Ltd, Commonwealth House, New Oxford Street, London WC1A 1PB. Individual members of the BLAC, the BAUA, the Guild of Air Pilots and Air Navigators, GASCO and SLAET can obtain discount tickets direct from these organisations.  
Details of the Show: "Flight" for June 24, 1971, page 942.

# Great new OFFER from DIOTRAN

## TRANSISTORS

AC107	15p	AD149	43p	BC108	10p	BC177	17p	BF119	70p	BFX84	20p	EC401	15p	OC201	27p	2N524	55p	2N294	27p	2N3403	22p	2S323	60p
AC113	20p	AD161	35p	BC109	10p	BC178	17p	BF152	35p	BFX85	27p	EC403	15p	OC202	27p	2N527	60p	2N297	20p	2N3404	32p	2S324	CL20
AC115	23p	AD162	35p	BC113	25p	BC179	17p	BF153	35p	BFX86	27p	GEI880	27p	OC203	25p	2N596	12p	2N298	25p	2N3405	45p	2S325	CL20
AC125	17p	AD16U		BC174	30p	BC180	20p	BF154	35p	BFX87	25p	MAT100	15p	OC204	25p	2N597	15p	2N299	27p	2N3414	20p	2S326	CL20
AC126	17p	AD16V	63p	BC175	30p	BC181	22p	BF157	45p	BFX88	27p	MAT101	17p	OC205	35p	2N598	24p	2N220	22p	2N3415	20p	2S327	CL20
AC127	17p	AD17	50p	BC176	35p	BC182	20p	BF158	25p	BFY50	20p	MAT120	15p	OC309	35p	2N599	55p	2N221	22p	2N3417	37p		
AC128	17p	AD17	£2.00	BC177	35p	BC182L	10p	BF159	30p	BFY51	20p	MAT121	17p	P.346A	17p	2N706	7p	2N222	22p	2N3418	37p		
AC14K	17p	AD17	£2.10	BC178	25p	BC183	10p	BF160	30p	BFY52	20p	MAT122	17p	P.397	45p	2N706A	8p	2N238	17p	2N3419	37p		
AC142K	17p	AF14	17p	BC179	45p	BC183L	10p	BF162	30p	BFY53	17p	MAT123	17p	P.397	45p	2N708	12p	2N239	15p	2N3420	37p		
AC151	15p	AF15	17p	BC125	35p	BC184	13p	BF163	35p	BSY19	15p	OC19	30p	ORP12	43p	1N709	45p	2N269A	15p	2N3704	15p		
AC154	15p	AF16	17p	BC126	35p	BC184L	13p	BF164	35p	BSY20	15p	OC20	50p	ORP60	40p	2N711	40p	2N270	25p	2N3705	12p		
AC155	17p	AF17	17p	BC132	25p	BC186	27p	BF165	35p	BSY25	15p	OC22	30p	ORP61	40p	2N717	42p	2N242	50p	2N3706	12p		
AC156	17p	AF18	30p	BC134	30p	BC187	27p	BF167	22p	BSY28	15p	OC23	33p	ST140	12p	2N718	24p	2N246	55p	2N3707	13p		
AC157	17p	AF124	21p	BC135	30p	BC207	11p	BF173	22p	BSY27	15p	OC24	45p	ST141	17p	2N718A	50p	2N271	22p	2N3708	8p		
AC165	17p	AF125	20p	BC136	30p	BC208	11p	BF176	35p	BSY28	15p	OC25	25p	1T543	40p	2N726	27p	2N272	22p	2N3709	8p		
AC166	17p	AF126	20p	BC137	35p	BC209	11p	BF177	35p	BSY29	15p	OC26	25p	UT46	27p	2N727	27p	2N274	25p	2N3710	10p		
AC167	20p	AF127	20p	BC139	45p	BC212L	11p	BF178	45p	BSY38	15p	OC28	40p	V405A	25p	2N743	17p	2N294	25p	2N3711	10p		
AC168	20p	AF139	33p	BC140	35p	BC212L	11p	BF179	50p	BSY39	15p	OC29	40p	V405A	25p	2N744	17p	2N294A	30p	2N3819	40p		
AC169	14p	AF178	50p	BC141	35p	BC214L	12p	BF180	50p	BSY40	31p	OC35	33p	2G301	19p	2N914	17p	2N295	25p	2N3820	CL10		
AC176	23p	AF179	50p	BC142	45p	BC225	25p	BF181	30p	BSY41	35p	OC36	40p	2G302	19p	2N918	30p	2N295A	30p	2N3803	25p		
AC177	20p	AF180	50p	BC143	45p	BC226	35p	BF182	30p	BSY92	12p	OC41	20p	2G303	19p	2N929	22p	2N296	25p	2N3904	27p		
AC178	30p	AF181	50p	BC145	45p	BC218	12p	BF183	30p	BSY93A	12p	OC42	22p	2G304	20p	2N930	25p	2N296A	27p	2N3905	25p		
AC180	30p	AF186	45p	BC147	45p	BC219	12p	BF184	30p	BSY94	12p	OC44	15p	2G306	35p	2N131	20p	2N297	25p	2N3906	27p		
AC187	30p	AF239	37p	BC148	12p	BC319	12p	BF185	30p	C11E	60p	OC45	12p	2G308	35p	2N132	22p	2N297A	30p	2N4058	15p		
AC188	30p	AF239	37p	BC149	12p	BC319	12p	BF186	30p	C400	30p	OC70	15p	2G309	35p	2N130T	27p	2N297A	30p	2N4059	10p		
AC19	27p	AF212	45p	BC150	17p	BC321	22p	BF187	24p	C407	25p	OC71	9p	2G319	17p	2N130T	27p	2N292	13p	2N4060	12p		
AC20	20p	AL102	85p	BC151	20p	BCY32	25p	BF195	24p	C424	17p	OC72	12p	2G339A	15p	2N130A	20p	2N2925	13p	2N4061	12p		
AC21	20p	AL103	85p	BC152	17p	BCY33	17p	BF196	30p	C425	40p	OC74	12p	2G334	15p	2N1305	20p	2N2926G	12p	2N4062	12p		
AC22	19p	AF176	25p	BC153	27p	BCY34	20p	BF197	35p	C426	30p	OC75	15p	2G345	15p	2N1306	22p	2N2926Y	11p	2N4062	12p		
AC27	27p	AF177	30p	BC154	30p	BCY10	17p	BF200	45p	C428	20p	OC76	15p	2G313	10p	2N1307	27p	2N2928	10p	2N4063	43p		
AC28	19p	AF178	25p	BC157	20p	BCY11	30p	BF201	30p	C441	27p	OC77	25p	2G318	10p	2N1308	27p	2N2929	10p	2N4064	35p		
AC29	30p	AF179	25p	BC158	20p	BCY12	15p	BF202	35p	C442	35p	OC81	15p	2G317	17p	2N1309	27p	2N301	20p	2N4065	50p		
AC30	25p	AF180	25p	BC159	20p	BCZ11	20p	BF203	30p	C444	27p	OC80	15p	2G317	17p	2N1309	27p	2N301	20p	2N4066	50p		
AC31	25p	AF181	25p	BC167	13p	BD121	85p	BF204	30p	C450	17p	OC82	15p	2G318	15p	2N1311	20p	2N304	50p	2N4067	45p		
AC34	34p	AF182	25p	BC168	13p	BD123	85p	BF205	30p	C451	17p	OC80	15p	2G318	15p	2N1311	20p	2N304	50p	2N4068	45p		
AC35	30p	AF183	25p	BC169	13p	BD124	75p	BF206	30p	C452	17p	OC83	20p	2G410	30p	2N1310	45p	2N309	17p	2N4069	45p		
AC36	30p	AF184	25p	BC170	12p	BD131	85p	BF207	30p	C453	17p	OC84	20p	2G411	30p	2N1310	45p	2N309A	20p	2N4070	45p		
AC40	15p	AF185	25p	BC171	13p	BD132	85p	BF208	30p	C454	17p	OC139	15p	2G412	25p	2N1310	45p	2N309B	20p	2N4071	45p		
AC41	18p	AF187	25p	BC172	13p	BDY20	£1.00	BF209	37p	C444	17p	OC140	17p	2N368	30p	2N1312	25p	2N3393	15p	2N4072	45p		
AC44	35p	AF188	25p	BC173	13p	BF15	75p	BF210	35p	C455	17p	OC170	15p	2N389A	50p	2N1313	25p	2N3394	15p	2N4073	45p		
AD140	40p	AS52	40p	BC174	13p	BF17	45p	BF211	45p	C456	17p	OC171	15p	2N394	22p	2N1312	25p	2N3395	20p	2N4074	45p		
AD142	40p	BC107	10p	BC175	22p	BF18	60p	BFX29	27p	C164		OC200	25p	2N404A	30p	2N1313	25p	2N3402	22p	2S322A	45p		

**10 MILLION DIODES SILICON OR GERMANIUM**  
—state which when ordering

200	50p.	10,000	£10.00
1000	£2.00	50,000	£30.00
5000	£7.00	100,000	£50.00

**2,000,000 SILICON PLANAR TRANSISTORS**  
**TO18 P.N.P. & N.P.N TYPES**  
state which when ordering

100	£1.50	10,000	£90.00
500	£6.00	50,000	£400.00
1,000	£10.00	100,000	£625.00

**LINEAR INTEGRATED CIRCUIT 709/PC S.G.S.**  
TO-5 can 8 lead. Full specification high gain Operational Amplifier data supplied. Lowest ever price.

QUANTITY	1-9	10-24	25-99	100-999
PRICE EACH	37p.	34p.	30p.	25p.

**BRAND NEW UNIJUNCTION TRANSISTORS**  
BRAND NEW FULLY TESTED EPOXY CASE UNIJUNCTION TRANSISTORS. Type 1S43 and BEN 3000 and replacement for 2N2646. Full data available. LOWEST PRICE AVAILABLE ANYWHERE. 100 off 20p each = £20; 500 off 17p each = £87.50; 1,000 off 15p each = £150. Sample devices 35p each on request.

**SILICON PLANAR DIODES**  
HIGH QUALITY SILICON PLANAR DIODES, SUB-MINIATURE DO-7 Glass Type, suitable replacements for OA200, OA202, BAY38, IS130, IS940, 200,000 to clear at £4 per 1,000 pieces. GUARANTEED 80% GOOD. OA90 GERM. DIODES 30Pw 45MA 00-7 GLASS, 30,000 Available New and Coded. Price £3 per 100, £11 per 500, £17 per 1,000 pieces. Once sold cannot be repeated.

**DIOTRAN SALES**  
P.O. BOX 5, WARE, HERTS.  
Full money-back guarantee  
POSTAGE & PACKING 7p

**ELECTRONIC ORGAN DIVIDER BOARDS** built to high industrial/computer spec. 5 octave set £15. Complete with connection data and oscillator details.

**COPPER LAMINATE P.C. BOARD**  
8½ x 5½ x 1/16 in. 12½p sheet, 5 for 50p  
11 x 6½ x 1/16 in. 15p sheet, 4 for 50p  
11 x 9 x 1/16 in. 20p sheet, 3 for 50p  
Offset pack (smallest 4 x 2 in.) 50p 300 sq. in.  
P&P single sheet 4p. Bargain packs 10p

**SPEAKERS AND CABINETS**

**E.M.I.** 19 x 14 in. 50 watts (14A/600A). Four tweeters mounted across main axis. Separate "X-over" unit balances both bass and h.f. sections. 20Hz to 20,000Hz. Bass unit flux 16,500Gss. A truly magnificent system. £25. Carr. £1-50.

**E.M.I.** 13 x 8 in. (10 watt) with two tweeters and cross-over 3/8/15 ohm models. £3-75. P.P. 25p.

**E.M.I.** 13 x 8 in. base units (10 watt) 3/8/15 ohm models £2-25. P.P. 25p.

**E.M.I.** 6½ in. rnd. 10 watt Woofers. 8 ohm. 13,000 gss £2-25. P.P. 15p.

**E.M.I.** 20 watt (13 x 8 in.) with single tweeter and "X-over" 20 Hz to 20,000 Hz. Ceramic magnet 11,000Gss. £8. P.P. 40p. 20 watt base unit only. £6. P.P. 40p.

**CABINETS** for 13 x 8 in. Speakers made from ½ in. teak finish blockboard. 20 watt cabinet (21 x 15 x 8½ in.) £6. P.P. 50p. 10 watt cabinet (16 x 11 x 8 in.) £4-80. P.P. 40p.

**"AIRMAX" 7½ in. FANS.** Aluminium diecast housing (9 in.) 240v. a.c. New. £5. P.P. 50p.

**"KLAXON" GEARED MOTORS** (8 lb-in.) 112 r.p.m. 240v. £2-25.

**BRIDGE MEGGERS** (500v. series 2) £18 ea. in good working order.

**BRIDGE RECTIFIERS** (Mullard GEX 54INBIPIF) Output 74volt. at 18 amps. £2 ea. (brand new).

**BULK COMPONENT OFFER.** Resistors/Capacitors. All types and values. All new modern components. Over 500 pieces £2. (Trial order 100cps. 50p.) We are confident you will re-order.

**BERCO WIRE-WOUND POTS.** New individually boxed. 200 ohm 25 watt 50p; 725 ohm 50 watt 75p; 300 ohm 100 watt £1 ea.

**HIGH SPEED MAGNETIC COUNTERS** (4 x 1 x 1 in.) 4 digit. 24/48v. (state which), 32½p ea. P.P. 5p.  
3 Digit (Re-settable) 12v. working £1-75.



**LEVEL METERS** (1½ x ½ in.) 200 micro amp. Made in Germany 75p ea. 2 x 1½ in. (Japan) £1 ea.

**MICROAMMETERS** (4 in. sq. Weston) 25-0-25 micro-amps. New/boxed. £2-25 ea. P.P. 25p.

**PRECISION CAPACITANCE JIGS.** Beautifully made with Moore & Wright Micrometer Gauge. Type 1, 18.5p to 1220pF. £10 ea. Type 2, 9.5p to 11.5pF. £6 ea.

**POT CORES LA1/LA2/LA3.** 50p ea.

**LIGHT DIMMERS** (2000 watt) Triac Controlled. 3½ x 2 x 1½ in. £5-75 ea. P.P. 25p.

**TRANSFORMERS**

**L.T. TRANSFORMER.** (Shrouded) Prim. 200/250v. Sec. 20/40/60v. 2 amp. £2 ea. P.P. 40p.

**L.T. TRANSFORMER.** (Shrouded) Prim. 200/250v. Sec. 20/40v. 1.5 amp. £1-50 P.P. 30p.

**L.T. TRANSFORMER.** Prim. 240v. Sec. 8/12/20/25v. 3.5 amp. £1 ea. P.P. 40p.

**L.T. TRANSFORMERS.** Prim. 2

# VALVES

KT88	1-15	KT88	1-15	KT88	1-15
N78	1-25	N78	1-25	N78	1-25
OA2	0-35	OA2	0-35	OA2	0-35
OB2	0-35	OB2	0-35	OB2	0-35
PABCS90	0-37	PABCS90	0-37	PABCS90	0-37
PC97	0-40	PC97	0-40	PC97	0-40
PC900	0-47	PC900	0-47	PC900	0-47
PC84	0-37	PC84	0-37	PC84	0-37
PC89	0-45	PC89	0-45	PC89	0-45
PCF189	0-55	PCF189	0-55	PCF189	0-55
PCF200	0-77	PCF200	0-77	PCF200	0-77
PCF60	0-30	PCF60	0-30	PCF60	0-30
PCF82	0-33	PCF82	0-33	PCF82	0-33
PCF84	0-48	PCF84	0-48	PCF84	0-48
PCF86	0-57	PCF86	0-57	PCF86	0-57
PCF200	0-77	PCF200	0-77	PCF200	0-77
PCF801	0-48	PCF801	0-48	PCF801	0-48
PCF802	0-48	PCF802	0-48	PCF802	0-48
PCF805	0-72	PCF805	0-72	PCF805	0-72
PCF806	0-65	PCF806	0-65	PCF806	0-65
PCF808	0-72	PCF808	0-72	PCF808	0-72
PCH200	0-70	PCH200	0-70	PCH200	0-70
PCL81	0-47	PCL81	0-47	PCL81	0-47
PCL82	0-37	PCL82	0-37	PCL82	0-37
PCL83	0-65	PCL83	0-65	PCL83	0-65
PCL84	0-42	PCL84	0-42	PCL84	0-42
PCL85	0-42	PCL85	0-42	PCL85	0-42
PCL86	0-42	PCL86	0-42	PCL86	0-42
PPL200	0-57	PPL200	0-57	PPL200	0-57
PL36	0-53	PL36	0-53	PL36	0-53
PL81	0-50	PL81	0-50	PL81	0-50
PL82	0-40	PL82	0-40	PL82	0-40
PL83	0-42	PL83	0-42	PL83	0-42
PL84	0-35	PL84	0-35	PL84	0-35
PL500	0-73	PL500	0-73	PL500	0-73
PL504	0-75	PL504	0-75	PL504	0-75
PL508	0-60	PL508	0-60	PL508	0-60
PL580	0-35	PL580	0-35	PL580	0-35
PL581	0-27	PL581	0-27	PL581	0-27
PL582	0-27	PL582	0-27	PL582	0-27
PL583	0-35	PL583	0-35	PL583	0-35
PL584	0-37	PL584	0-37	PL584	0-37
PL585	0-40	PL585	0-40	PL585	0-40
PL586	0-42	PL586	0-42	PL586	0-42
PL587	0-45	PL587	0-45	PL587	0-45
PL588	0-45	PL588	0-45	PL588	0-45
PL589	0-45	PL589	0-45	PL589	0-45
PL700	0-45	PL700	0-45	PL700	0-45

QVVO	£	UBC41	£ 0.47	VR150/30	£ 0.35	5B254M	£ 2.20	6AQ5	£ 0.35	6C4	£ 0.30	6K7G	£ 0.20
6-40A	5-25	UBF80	0.35	Z759	1-85	5B/255M	1.75	6AQ5W	0.50	6C6	0.25	6K8GT	0.45
R17	0-45	UBF89	0-35	Z801U	1-50	5R4GY	0-60	6A86	0-37	6CH6	0-85	6K9	0-70
R19	0-37	UC35	0-40	Z803A	1-25	5U4G	0-32	6A87G	0-80	6CL6	0-49	6SA7	0-40
STV		UCF90	0-55	Z900T	0-75	5V4G	0-40	6AT6	0-30	6D6	0-20	6SA7GT	0-32
280/40	3-00	UCH42	0-70	1L4	0-15	5Y4G	0-40	6AU6	0-25	6EA8	0-55	68C7GT	0-25
STV		UCH81	0-35	1R5	0-35	5Y3GT	0-35	6AX4GT	0-40	6F23	0-75	68G7	0-35
280/80	0-00	UCL82	0-35	1R4	0-25	5Z4	0-75	6AX5GT	0-65	6F33	1-50	68H7	0-37
TT21	2-75	UC183	0-80	185	0-24	5Z4GT	0-40	6B7	0-40	6H6M	0-20	68I7GT	0-32
U25	0-75	U41	0-45	1A4	0-22	6A7	0-30	6B7K	0-40	6J4WA	0-75	68K7	0-35
U26	0-75	UF80	0-35	1T4	0-22	6AC7	0-15	6BA6	0-25	6J5	0-40	68L7GT	0-32
U27	0-50	UF89	0-35	1X2A	0-40	6AH6	0-50	6BE6	0-30	6J5	0-40	68N7GT	0-35
U191	0-70	UL41	0-80	1X2B	0-40	6AK5	0-30	6BG6G	0-55	6J5GT	0-25	68Q7	0-39
U801	1-00	UL84	0-30	3A4	0-30	6AK8	0-32	6BJ6	0-45	6J6	0-20	68Q7GT	0-35
UABC80	0-35	U5	0-55	3D6	0-15	6AL5	0-15	6BQ7A	0-35	6J7G	0-35	68VGT	0-35
UAF42	0-50	U81	0-45	3Q4	0-37	6AL5W	0-40	6B7R	0-80	6J7M	0-40	6X4	0-27
		U85	0-30	3R4	0-35	6AM6	0-30	6BW6	0-80	6K6GT	0-56	6X5G	0-25
		VR105/30	0-35	3Y4	0-45	6AN8	0-50	6BW7	0-70	6K7	0-32	6X5GT	0-32

## SPECIAL OFFER TRANSISTORS, ZENER DIODES

OA5	0-25	OC29	0-62	IN21	0-17	2N5109	£ 0.05	AF127	£ 0-17	CR81/30	£ 0-40	7C5	0-85	30P19	0-80
OA10	0-25	OC35	0-50	IN21B	0-25	40362	0-62	AF139	0-30	CR81/35	0-43	7C6	0-40	30PL1	0-70
OA70	0-10	OC38	0-4												



# AERO SERVICES LTD



### TWO NEW A.C./D.C. MULTIMETERS FROM RUSSIA

**TYPE 4312**—low sensitivity (667 o.p.v.) extremely sturdy instrument for general electrical use. D.C. ranges: 0.3-1.5-7.5-30-60-150-300-600-900V and 75mV; 300µA-1.5-6-15-60-150-600mA 1.5-6A. A.C. ranges: 0.3-1.5-7.5-30-60-150-300-600-900V, 1.5-6-15-60-150-600mA, 1.5-6A. Resistance: 0.2-3-30k Ω. Accuracy: D.C. 1%; A.C. 1.5%. PRICE, with carrying case and leads **£9.75**



**TYPE 4313**—high sensitivity for general electronic and TV-radio repair applications. Sensitivity: 20,000 o.p.v. DC and 2,000 o.p.v. AC. D.C. ranges: 75mV-1.5-3-7.5-15-30-60-150-300-600V. 60-120-600µA-3-15-60-300mA-1.5Amp. A.C. ranges: 1.5-3-7.5-15-30-60-150-300-600V. 600µA-3-15-60-300mA-1.5A. Resistance: 0.5-5-50-500k Ω.

Capacity and Transmission level scales. Accuracy: 1.5% D.C.; 2% A.C. PRICE, with carrying case and leads **£10.50**. Both instruments have knife edge pointers and mirror scales.

WHEN ORDERING BY POST PLEASE ADD £0.12½ (2/6) IN £ FOR HANDLING AND POSTAGE. NO C.O.D. ORDERS ACCEPTED ALL MAIL ORDERS MUST BE SENT TO HEAD OFFICE AND NOT TO RETAIL SHOP.

### NEW TRANSISTORS ADDED SILICON PNP PLANAR EPITAXIAL LOCK-FIT

BFW87	60V	hfe min. 80	0.30
BFW88	60V	hfe min. 40	0.25
BFW89	40V	hfe min. 80	0.23
BFW91	20V	hfe min. 40	0.20

### MINIATURE WIRE ENDED SILICON RECTIFIERS

1N4002	100 p.i.v.	1A	0.10
1N4004	400 p.i.v.	1A	0.12
1N4006	800 p.i.v.	1A	0.15

### MV10B LIGHT EMITTING DIODE

To 18 outline. Brightness 500 Ft.L at 50 mA. Forward voltage 1.65 to 2V. Spectral length 6300 to 7000Å (red light). Lens diameter 0.170in. PRICE **£1.05** plus 0-10 P. P.

### INTEGRATED MONOLITHIC DUAL OPERATIONAL AMPLIFIER MC1435P

Two identical amplifiers in 14-pin dual-in-line epoxy package. 400mW dissipation. Typical open loop voltage gain 7000. Max. differential input ± 5V. Power supplies 6 to 9V. Max. frequency 1 mc/s. **£2.00**.

### MINIATURE CERAMIC CAPACITORS 25V D.C. WORKING

5% tolerance: 22-27-33-39-47-56-68-100-120-150-180-220-270-330-390-470-560	20p per 20
680-820-1000pF	22p per 20
20% + 50% tolerance: 1500-2200pF	22p per 20
3300-4700-6800-10,000pF	25p per 20
20% + 80% tolerance: 0.015µF	25p per 20
0.022µF	26p per 20
0.033µF	28p per 20
0.047µF	30p per 20

Note: Minimum orders accepted 20 per type.

### TWO NEW OSCILLOSCOPES FROM RUSSIA



### CI-5 SINGLE BEAM OSCILLOSCOPE

10 mc/s passband, triggered sweep from 1 µ sec. to 3 milli-sec. Free running time base from 20 c/s to 200 kc/s. Built-in time marker and amplitude calibrator, 3-in. cathode ray tube with telescopic viewing hood. **£39.00**

### CI-16 DOUBLE BEAM OSCILLOSCOPE

5 mc/s passband. Separate Y1 and Y2 amplifiers, rectangular 5 in. x 4 in. cathode ray tube. Calibrated triggered sweep from 0.2 µ sec. to 100 milli-sec. per cm. Free running time base 50 c/s to 1 mc/s. Built-in time base calibration and amplitude calibrator. Full servicing facilities and spares available. **£87.50**



OUR 1970/1971 CATALOGUE IS AVAILABLE. PLEASE SEND S.A.E. FOR YOUR FREE COPY.

FULLY GUARANTEED



FIRST QUALITY VALVES

0A2	0-38	5R4GY	0-60	6BQ7A	0-40	684A	0-60	12A7T	0-33	30C15	0-80	329	1-15	AC/TH2	E186F	1-25	E180F	0-95	EL95	0-35	HF93	0-35	PCF806	0-70	QV06-40A	0-75	UCH45	0-75	
0A3	0-45	5U4G	0-33	6BR7	0-35	68A7	0-40	12AU6	0-30	30C17	0-85	329A	1-90	AX50	0-45	E188CC	0-90	ECL81	0-45	EL360	1-15	HF94	0-30	PCF808	0-75	QV08-40A	0-50	UCH81	0-35
0A4C	1-15	6A4G	0-40	6B8	0-65	68C7	0-70	12A7U	0-30	30C18	0-75	715A	2-50	AX50	0-25	E280F	2-10	ECL82	0-35	EL360	1-15	HK90	0-35	PCF808	0-75	QV08-40A	0-50	UCH81	0-35
0B2	0-35	5W4GT	0-40	6B8T	1-30	68G7	0-35	12AV6	0-33	30P5	0-55	715C	5-00	AZ31	0-55	E280F	2-10	ECL83	0-65	EL821	0-55	HL23	0-40	PCF805	0-50	RG3-250A	0-40	UCL81	0-60
0B3	0-60	5X8	0-50	6BW6	0-85	68H7	0-35	12AV7	0-50	30FL1	0-70	723A	7-00	CI166	25-00	EA50	2-00	ECL84	0-55	EL822	0-90	HL23D	0-40	PCF805	0-50	UCL81	0-60	UCL82	0-35
0C2	1-00	5Y3GT	0-32	6BX6	0-70	68J7	0-40	12AX7	0-50	30FL2	0-93	725A	16-00	CIK	4-50	EA52	4-50	ECL85	0-55	ELL80	0-75	HL23D	0-40	PCF805	0-50	UCL81	0-60	UCL83	0-60
0C3	0-38	5Z3	0-32	6BX6	0-70	68K7	0-40	12AX7GT	0-50	30FL3	0-93	725B	16-00	CIK	4-50	EA52	4-50	ECL85	0-55	ELL80	0-75	HL23D	0-40	PCF805	0-50	UCL81	0-60	UCL83	0-60
0D3	0-35	5Z4G	0-40	6BX7GT	0-75	68L7	0-35	12AX7GT	0-50	30FL4	0-75	807	0-50	CBL1	0-90	EA50	2-00	ECL85	0-55	ELL80	0-75	HL23D	0-40	PCF805	0-50	UCL81	0-60	UCL83	0-60
1A3	0-90	6A0L2	0-20	6BZ6	0-35	68M7	0-35	12AX7GT	0-50	30FL5	0-93	811A	1-60	CBL1	0-90	EA50	2-00	ECL85	0-55	ELL80	0-75	HL23D	0-40	PCF805	0-50	UCL81	0-60	UCL83	0-60
1A5GT	0-32	6A0L3	0-35	6BZ6	0-35	68N7GT	0-35	12AX7GT	0-50	30FL6	0-93	811B	1-60	CBL1	0-90	EA50	2-00	ECL85	0-55	ELL80	0-75	HL23D	0-40	PCF805	0-50	UCL81	0-60	UCL83	0-60
1B3GT	0-38	6A3A	0-35	6C4	0-33	68P7GT	0-35	12AX7GT	0-50	30FL7	0-93	811C	1-60	CBL1	0-90	EA50	2-00	ECL85	0-55	ELL80	0-75	HL23D	0-40	PCF805	0-50	UCL81	0-60	UCL83	0-60
1B24	4-00	6AC7	0-25	6CB6	0-30	68Q7	0-40	12AX7GT	0-50	30FL8	0-93	811D	1-60	CBL1	0-90	EA50	2-00	ECL85	0-55	ELL80	0-75	HL23D	0-40	PCF805	0-50	UCL81	0-60	UCL83	0-60
1C3GT	0-35	6AF4A	0-50	6CD6GA	0-40	68R7	0-40	12AX7GT	0-50	30FL9	0-93	811E	1-60	CBL1	0-90	EA50	2-00	ECL85	0-55	ELL80	0-75	HL23D	0-40	PCF805	0-50	UCL81	0-60	UCL83	0-60
1C9T	0-60	6AG5	0-22	6CD6GA	0-40	68S7	0-40	12AX7GT	0-50	30FL10	0-93	811F	1-60	CBL1	0-90	EA50	2-00	ECL85	0-55	ELL80	0-75	HL23D	0-40	PCF805	0-50	UCL81	0-60	UCL83	0-60
1G4GT	0-45	6A4G	0-40	6CG7	0-75	68T7	0-35	12AX7GT	0-50	30FL11	0-93	811G	1-60	CBL1	0-90	EA50	2-00	ECL85	0-55	ELL80	0-75	HL23D	0-40	PCF805	0-50	UCL81	0-60	UCL83	0-60
1G6GT	0-40	6AH6	0-50	6CH6	0-55	68U7	0-35	12AX7GT	0-50	30FL12	0-93	811H	1-60	CBL1	0-90	EA50	2-00	ECL85	0-55	ELL80	0-75	HL23D	0-40	PCF805	0-50	UCL81	0-60	UCL83	0-60
1H6GT	0-42	6AJ8	0-30	6CL6	0-50	68V7	0-40	12AX7GT	0-50	30FL13	0-93	811I	1-60	CBL1	0-90	EA50	2-00	ECL85	0-55	ELL80	0-75	HL23D	0-40	PCF805	0-50	UCL81	0-60	UCL83	0-60
1L4	0-20	6AK5	0-30	6CU6	0-65	68W7	0-35	12AX7GT	0-50	30FL14	0-93	811J	1-60	CBL1	0-90	EA50	2-00	ECL85	0-55	ELL80	0-75	HL23D	0-40	PCF805	0-50	UCL81	0-60	UCL83	0-60
1N6GT	0-42	6AK5W	0-30	6CW4	0-65	68X7GT	0-35	12AX7GT	0-50	30FL15	0-93	811K	1-60	CBL1	0-90	EA50	2-00	ECL85	0-55	ELL80	0-75	HL23D	0-40	PCF805	0-50	UCL81	0-60	UCL83	0-60
1Q5GT	0-50	6C25	0-45	6CY5	0-45	68Y7GT	0-35	12AX7GT	0-50	30FL16	0-93	811L	1-60	CBL1	0-90	EA50	2-00	ECL85	0-55	ELL80	0-75	HL23D	0-40	PCF805	0-50	UCL81	0-60	UCL83	0-60
1R4	0-35	6AK6	0-57	6CY7	0-65	68Z7GT	0-35	12AX7GT	0-50	30FL17	0-93	811M	1-60	CBL1	0-90	EA50	2-00	ECL85	0-55	ELL80	0-75	HL23D	0-40	PCF805	0-50	UCL81	0-60	UCL83	0-60
1R5	0-35	6AL3	0-43	6D3	0-45	68Z7GT	0-35	12AX7GT	0-50	30FL18	0-93	811N	1-60	CBL1	0-90	EA50	2-00	ECL85	0-55	ELL80	0-75	HL23D	0-40	PCF805	0-50	UCL81	0-60	UCL83	0-60
1S4	0-27	6AL5	0-20	6DC6	0-75	68Q7	0-40	12BA7	0-35	30P19	0-80	837	0-85	DAF41	0-50	EB34	0-20	EF39	0-40	EM87	0-55	KT36	1-00	PEN46	0-40	SP61	0-55	UY85	0-30
1S5	0-25	6AM5	0-32	6DK6	0-48	68R7	0-40	12BE6	0-35	30PL1	0-70	866A	0-75	DAF91	0-25	EB91	0-20	EF40	0-50	EN10	4-00	KT44	0-50	PEN383	0-75	TP22	0-60	VP1831	0-90
1T4	0-25	6AM6	0-33	6DQ6B	0-63	68S7	0-40	12BH7	0-40	30PL13	0-93	872A	3-00	DAF92	0-50	EB33	0-50	EF41	0-55	EN11	3-50	KT45	0-50	PEN384	0-60	TP25	0-40	VP173	1-00
1T5GT	0-45	6AN8	0-50	6DS4	0-75	68T8	0-35	12BV7	0-55	30PL14	0-90	884	0-80	DAF96	0-42	EB41	0-55	EF42	0-50	EN12	1-50	KT46	0-50	PEN384	0-60	TP25	0-40	VP173	1-00
1U4	0-27	6AQ5	0-35	6E5	0-55	6L4GT	0-60	12C8	0-35	35B5	0-65	889A	0-80	DAF96	0-42	EB41	0-55	EF42	0-50	EN12	1-50	KT46	0-50	PEN384	0-60	TP25	0-40	VP173	1-00
1U6	0-50	6AQ6	0-55	6E8A	0-58	6U8A	0-40	12E1	1-35	35C5	0-40	899A	0-80	DAF96	0-42	EB41	0-55	EF42	0-50	EN12	1-50	KT46	0-50	PEN384	0-60	TP25	0-40	VP173	1-00
1V2	0-45	6AR5	0-35	6EH7	0-50	6V6GT	0-38	12E14	3-57	35D5	0-70	927	3-00	DF92	0-20	EB20	0-30	EF85	0-35	EY80	0-45	KT88	2-00	PEN43D	0-60	U17	0-75	VR105/30	0-45
1X2B	0-40	6AR6	0-40	6EJ7	0-35	6X4	0-30	12H6	0-30	35L6GT	0-50	931A	3-50	DF96	0-42	EBF80	0-40	EF86	0-30	EY81	0-40	KTW630	0-50	PF86	0-60	U18/20	0-75	VR150/30	0-38
2A3	0-40	6AR11	1-25	6F5	0-50	6X5GT	0-35	12J5GT	0-25	35W4	0-30	931A	3-50	DF96	0-42	EBF80	0-40	EF89	0-28	EY83	0-55	ME91	0-45	PF818	0-85	U19	2-90	VR150/30	0-38
2AP1	2-25	6AN5	0-35	6P0A	0-30	6X8	0-55	12J7GT	0-45	35Z3	0-60	955	2-25	DR81	0-60	EBF89	0-30	EF91	0-33	EY84	0-55	MH4	0-50	PF2000	0-70	U20	0-75	VR150/30	0-38
2C26A	0-50	6AN6	0-37	6P11	0-38	6Y6G	0-65	12K5	0-55	35Z4G	0-40	4378	1-40	DH101	0-55	EBL1	1-75	EF92	0-40	EY86	0-40	ML4	0-45	PF2000	0-70	U22	0-75	VR150/30	0-38
2C39A	7-00	6AN7A	0-80	6P13	0-38	6Z4	0-35	12K7GT	0-35	35Z5GT	0-40	4687	1-75	DK40	0-55	FBL31	1-50	EF93	0-25	EY87	0-43	ML6	0-40	PF2000	0-70	U23	0-75	VR150/30	0-38
2C40	3-50	6AT6	0-30	6P14	0-65	7B5	0-75	12K7GT	0-35	42	0-50	5544	0-60	DK91	0-35	EC53	0-50	EF94	0-25	EY88	0-43								

# APPOINTMENTS VACANT

**DISPLAYED SITUATIONS VACANT AND WANTED:** £8 per single col. inch.

**LINE advertisements (run-on):** 45p per line (approx. 7 words), minimum two lines.

Where an advertisement includes a box number (count as 2 words) there is an additional charge of 25p.

**SERIES DISCOUNT:** 15% is allowed on orders for twelve monthly insertions provided a contract is placed in advance.

**BOX NUMBERS:** Replies should be addressed to the Box number in the advertisement, c/o Wireless World, Dorset House, Stamford Street, London, S.E.1.  
No responsibility accepted for errors.

Advertisements accepted up to  
THURSDAY, 12 p.m., 5th AUG.,  
for the SEPTEMBER issue,  
subject to space being available.

## Imperial College of Science & Technology DEPARTMENT OF AERONAUTICS

There is a vacancy in this Department for an  
**ELECTRONICS TECHNICIAN**  
or  
**SENIOR TECHNICIAN**

to work primarily on a general purpose instrumentation project. **Salary ranges are £1,136-£1,535 p.a. and £1,493-£1,832 p.a. respectively.** Superannuation scheme, four weeks holiday and canteen facilities.

Apply in writing giving details of experience and qualifications to the Assistant Director, Department of Aeronautics, Imperial College, Prince Consort Road, London, S.W.7.

1264

## UNIVERSITY OF SHEFFIELD

### SENIOR TECHNICIAN AND TECHNICIAN

required for University Television Service  
from September 1971

One post requires appropriate qualifications and experience in field of electronics, particularly T.V.; for the other, training in electrical and/or laboratory techniques. Familiarity with wood and metal work an advantage.

Training given in T.V. operations to enable appointees to become members of a team working on educational T.V. productions.

Applicants for Senior Technician should be at least 25 years old and have C. & G. Final Certificate or equivalent; Technician, minimum age 20, with C. & G. Intermediate Certificate in a suitable subject.

**Salary: Senior Technician £1,398-£1,707 p.a. Technician £1,041-£1,410 p.a. each with basic qualification. Supplement for approved higher qualification. Superannuation Scheme.**

Write immediately to the Bursar (Ref. B.854), The University, Sheffield S10 2TN.

1265

## EXPANDING COMPANY IN SAUDI ARABIA REQUIRES EXPERIENCED CERTIFICATED ENGINEERS

FOR THE FOLLOWING POSTS

### CHIEF ENGINEER

B.Sc. or equivalent with 10 or more years experience in Operation and Maintenance of Transmission and Broadcasting Equipment.

### ENGINEERS TECHNICIANS

Experience in Operation and Maintenance of Broadcasting Equipment, Studio Equipment and Teleprinters.

Please submit a complete resume and state availability and salary required. Box WW 1270

## Service Technicians

Move to Harlow and enjoy the benefits of a good job with a successful company in the pleasant surroundings of our New Town.

Your job will be to service and repair products from our wide range of Airborne Instruments, Scopes and Test Gear. You will be working in our Harlow base workshop with the opportunity for occasional field trips. We will give you product training but we'll expect a good basic knowledge of Electronics preferably backed up with fault finding experience on transistorised and solid state devices.

Your starting salary would be from £1,310 per annum with excellent opportunities of promotion to Section Leader grades. In many cases we can assist with local New Town housing and help with your removal costs.

If you want to find out how to secure your position then 'phone or write now to:



**R. T. Reid,**  
**COSSOR ELECTRONICS LIMITED,**  
**The Pinnacles, Harlow, Essex.**  
**Tel: Harlow 26862**

LONDON BOROUGH OF HILLINGDON

## EDUCATION DEPARTMENT

Two suitably qualified and experienced technicians are required to undertake the maintenance and repair of visual and aural aids equipment in all parts of the Borough schools and other educational establishments. These are new posts.

### POST ONE

£1,605-£1,866 incl. LW. Additional responsibility for planning and operating the maintenance and repair programme.

### POST TWO

£1,179-£1,362 incl. LW.

8 cwt. van and tools provided for each post. Work base in Uxbridge. Current clean driving licence essential.

Application form and further particulars from the Establishment Officer, Ref. E/186/30, Manor House, Church Road, Hayes, Mx. Closing date August 2.

1292

# Opportunities with Redifon in Radio Communications

Experienced Test Engineers are invited to write to Redifon with regard to vacancies in our Test Department at Wandsworth.

The salary range for these positions is £1,248-£1,749 plus. The Company is engaged in the design and manufacture of a wide range of radio communications and allied equipment from military pack-set to broadcast transmitter, including communications receivers, M.F. beacons, teleprinter terminals, complete radio office installations for the Merchant Marine and mobile H.F. S.S.B. stations. Our Test Engineers have sound technical knowledge coupled with good practical experience in the alignment and test of H.F. and V.H.F. Communications equipment.

The work is varied and interesting and offers excellent opportunity to broaden experience in semiconductors S.S.B. and Frequency Synthesis.

Please write in the first instance to  
**Norman Manion,**  
The Recruitment Officer, Redifon Limited  
Broomhill Road, Wandsworth, S.W.18

**REDIFON** 

A Member Company of the Rediffusion Organisation



1174



## Telecommunications Engineers

required for the installation, maintenance and supervision of modern electronic systems used in our offshore oilfield complex at Das Island in the Arabian Gulf. These are bachelor postings but carry generous home leave and allowances.

Candidates, aged 23 to 40, should possess a minimum of HNC or equivalent, and have several years' practical experience with radio systems ranging from MF to Microwave multi-channel, with a good working knowledge of digital telemetry and automatic telephone systems.

● Please write, quoting reference R.943/ZH and giving relevant information about yourself to: G. I. Andrews, External Recruitment, The British Petroleum Company Limited, Britannic House, Moor Lane, London, EC2Y 9BU, or ring 01-920 6522 for an application form.

### POOLE GENERAL HOSPITAL, POOLE, DORSET

Applications are invited from qualified candidates for the following post in the Electronics Department at Poole General Hospital:

#### ELECTRONICS TECHNICIAN III

Qualifications: ONC, HNC, City & Guilds or equivalent.

Salary: £1,356 x 8 increments to £1,764 p.a.

The Department will be primarily concerned with the installation, testing and maintenance of an extensive range of diagnostic/therapeutic and allied electronic equipment, and ultimately with research and development of bio-medical equipment in consultation with medical staff.

The position offers adequate scope for initiative and career progression, including the possibility of assistance with further training.

Applications, giving full details, including qualifications, experience and the names and addresses of two referees, to the **Hospital Secretary, Poole General Hospital, Poole, Dorset.**

1266

### EDINBURGH CITY POLICE REQUIRE A WIRELESS TECHNICIAN

for Servicing and Maintenance of fixed and mobile broadcasting receiving system.

Salary scale £1,413 rising by annual increments to £1,611.

Applicants will be required to have a knowledge of UHF and VHF apparatus used on fixed and mobile stations, and be able to diagnose and repair faults.

They would be expected to have attained the City and Guilds Telecommunications Technicians Certificate or an equivalent qualification. A Current Driving Licence is essential.

Applications to:  
EDINBURGH CITY POLICE  
RECRUITING DEPARTMENT,  
7 CHAMBERS ST., EDINBURGH, EH1 1HR [1269]

### THE UNIVERSITY OF SUSSEX ELECTRONICS TECHNICIAN

An interesting post is available in a small growing department for a technician with experience of transistor circuits. Formal qualifications are not essential but applicants should be capable of designing and constructing simple apparatus for a variety of experiments.

Salary scale: (a) £1,011-£1,380 or (b) £1,041-£1,410. Salary scale (a) is applicable to those not holding an approved basic qualification.

Further particulars and forms of application can be obtained from the Secretary (Establishment), Office of Arts and Social Studies, Arts Building, University of Sussex, Falmer, Brighton, BN1 9QN to whom applications should be sent not later than 31st July or by telephoning Mr. Crook, Brighton, 66755, ext. 339.  
1276

### ST. BARTHOLOMEW'S HOSPITAL LONDON, E.C. 1

Applications are invited for two TECHNICIAN posts in the DEPARTMENT OF MEDICAL ELECTRONICS. The work involves routine servicing of electronic apparatus and the construction of new equipment for special purposes.

Applicants must have an O.N.C. or the final City and Guilds certificate, or two 'A' level passes in science subjects and at least four years' relevant technical experience. Experience of hospital work is not essential.

Salary will be on the Technician III and IV scales. £1,446 rising to £1,854 and £1,296 rising to £1,590 respectively. Applications in writing with the names of two referees should be sent to the Clerk to the Governors.

1278

# SECTIONAL ENGINEER GRADE II

## EAST AFRICAN COMMUNITY

- ★ Up to £2,718
- ★ 25% gratuity
- ★ Low taxation
- ★ Contract 21-27 months
- ★ Subsidised accommodation
- ★ Education allowances
- ★ Appointments Grant payable in certain circumstances

Required by the Meteorological Department for the installation, operation and maintenance of their radio telecommunications, radio sounding and radar equipment.

Candidates, up to age 45, must possess O.N.C. or the City and Guilds Final Certificate (Telecommunications) plus 7 years relevant experience or have equivalent experience in one of the armed services. They should have a good theoretical and practical knowledge of FSK, ISB and SSB receivers and transmitters, Mufax and facsimile transmitters and recorders. A good working knowledge of radar systems is essential.

Apply to **CROWN AGENTS, 'M' Division, 4 Millbank, London, S.W.1**, for application form and further particulars, stating name, age, brief details of qualifications and experience and quoting reference number **M2K/690413/WF**.

1304

# up to £1741 p.a. and all the variety you want as a Radio Technician

Variety is the keyword. As a Radio Technician with the National Air Traffic Services, you would be installing and maintaining a wide range of sophisticated electronic systems and highly specialised equipment. You would be involved with RT, radar, data transmission links, navigation aids, landing systems, closed circuit T.V. and computer installations. All custom-built to meet the stringent operational requirements of air traffic control throughout the U.K.

If you're aged 19 or over and have at

least one year's electronics experience, preferably with O.N.C. or C. & G. (Telecoms.), you could qualify for entry to our training course. Your starting salary would be £1,143 (at 19) to £1,503 (at 25 and over), scale max. £1,741 - shift duty allowances. Good career prospects.

Write NOW for full details to:  
A. J. Edwards, C.Eng., MIEE,  
Room 705, The Adelphi, John Adam  
Street, London WC2N 6BQ,  
marking your envelope  
'Recruitment — B/WW/27'.

Not applicable to residents outside the United Kingdom.

## NATS

National Air Traffic Services

## Senior Engineer (Aerials)

£2799 - £3258

The INDEPENDENT TELEVISION AUTHORITY is seeking to fill a new post of Aerial Engineer in its Station Operations and Maintenance Department. Although this post will be based in Leeds, the person selected will be required to travel extensively throughout the United Kingdom.

The work will involve the execution and direction of maintenance projects on aerial and combining systems in liaison with the Senior Engineer—Aerial Maintenance. It is essential that applicants have had thorough experience of the techniques used in assessing the performance of aerial and combining systems and they must be prepared to climb and work on tall structures. A recognised qualification at graduate level in the field of R.F. Engineering would be an advantage.

Salary according to qualifications and experience will be in the range quoted above. Those interested should write or telephone for an application form quoting

Ref. WW 1685 to:



The Personnel Officer,  
INDEPENDENT  
TELEVISION AUTHORITY,  
70 Brompton Road,  
London, S.W.3.  
Tel: 01-584 7011 Ext. 482

Completed application forms to be returned by:  
2nd August 1971.  
1303

## ELECTRONIC ENGINEERS

required

for new Technical Service Centre to be established at Hemel Hempstead by British Manufacturers and Servicing Group of a wide range of Business Equipment Products. Ideally suited for engineers experienced in Radio/T.V. H.M. Forces, Industrial electronics.

Please write to: **Mr. D. D. Davies, Technical Services Manager, Control Systems Ltd., Technical Services Centre, 1 Frogmore Road, Apsley, Hemel Hempstead, Herts.**

1284

## Closed Circuit Television Engineer

This interesting and responsible position involves all aspects of the installation and service of a wide range of monochrome C.C.T.V. for use with medical X-ray apparatus. The equipment would include vidocon, orthicon, plumbicon and isacon tubes, light intensifying systems and 35 mm. video tape recording apparatus.

The position would ideally suit an engineer experienced in C.C.T.V. systems preferably with ONC/HNC, looking for a responsible position and a secure future in a progressive firm.

A good salary and several fringe benefits including a Company car will be offered to the successful applicant.

Please apply for an application form to:

**The Personnel Officer, G.E.C. Medical Equipment Ltd., East Lane, Wembley, Middx. Tel. 904 1288**

1277

### WESSEX REGIONAL HOSPITAL BOARD and WESSEX HOSPITAL MANAGEMENT COMMITTEES REGIONAL ELECTRONICS SERVICE

Suitably qualified Engineers and Technicians are required for the Board's new Regional Department of Electronics and Bio Medical Engineering and in similar departments in Hospitals located in Hampshire and Dorset.

#### 1. ELECTRONICS ENGINEER

Qualifications: Chartered Member I.E.E., I.E.R.E.

#### 2. ELECTRONICS TECHNICIAN I

Qualifications: H.N.C.—H.N.D. Full Technological Certificate C. & G.

#### 3. ELECTRONICS TECHNICIAN III

Qualifications: O.N.C.—H.N.C.—C. & G.

#### 4. ELECTRONICS TECHNICIANS V

Qualifications: O.N.C. or A.2.

#### Salary Scales:

1. £2,088, rising by nine annual increments to £2,868 per annum.
2. £1,877 rising by five annual increments to £2,346 per annum.
3. £1,800 rising by eight annual increments to £2,500 per annum.
4. £900, rising by seven annual increments to £1,160 per annum.

Point of entry to the scale dependent on qualifications and/or experience.

Posts (1) and (2) will be based at the Board's Headquarters in Winchester; Posts (3) and (4) in various centres in the Region.

Departments will be concerned with all aspects of design—installation—testing and commissioning of a wide range of diagnostic/therapeutic and allied electronic equipment and data transmission systems.

Research and Development in conjunction with Medical Staff will be undertaken in the short term future.

Application forms available from the Personnel Department, Highcroft, Romsey Road, Winchester, to which they should be returned by 2nd August, 1971.

1281

### UNIQUE OPPORTUNITY

Electronic engineer to join the management team of a small but fast expanding company supplying a wide range of advanced projection, sound and lighting control systems.

We want an experienced inventive engineer fully capable of designing and developing, relay and solid state sequence control equipment sound amplifiers, lighting control equipment, etc.

Salary by negotiation.

Apply: **Technical Director, Audio Visual Equipment Ltd., 73 Surbiton Road, Kingston, Surrey**  
01-546-4565 1285

### TECHNICIAN REQUIRED

September for electronics workshop. Salary according to qualifications,

Senior technician H.N.C. £1,305-£1,712

Technician O.N.C. £902-£1,415

Junior technician 'O' level maths & science  
£525-£803

Day release possible for technicians and juniors. Written applications stating age, qualifications and experience, and names of two referees to **Administrator, University Laboratory of Physiology, Parks Road, Oxford.**

1271

## Sea-going Radio Officers can now make sure of a shore job and good pay.

If you'd like a job ashore, at a United Kingdom Coast Station, the Post Office will start you off on £1,080—£1,360, depending on age, with annual rises up to £1,850. There are good prospects of promotion to higher posts, opportunities exist for overtime and you would receive additional remuneration for attendance during the late evenings, at night and on Saturday afternoons and Sundays.

You will need to be 21 or over, with a 1st Class Certificate of Competence in Radiotelegraphy issued by the Postmaster General or the Ministry of Posts and

Telecommunications, or a Radiocommunication Operator's General Certificate issued by the Ministry of Posts and Telecommunications, or an equivalent certificate issued by a Commonwealth administration or the Irish Republic.

Find out more by writing to:  
The Inspector of Wireless  
Telegraphy,  
I.M.T.R.

Wireless Telegraph Section ( L.5 . )  
Union House,  
St. Martins-le-Grand,  
London,  
EC1A 1AR.

Post Office  
Telecommunications

93

# SENIOR TELECOMMUNICATIONS TECHNICIAN

GILBERT & ELLICE ISLANDS

- ★ Up to £2942
- ★ 25% gratuity
- ★ Low taxation
- ★ Appointments Grant payable in certain circumstances.
- ★ Contract 24 months
- ★ Education and outfit allowances
- ★ Subsidised accommodation

Required by the Posts and Telecommunications Department to be responsible for the implementation of the planning, the installation and maintenance of all telecommunications facilities, the control of stores and the technical training of local staff.

Candidates should possess the City and Guilds Full Technological Certificate (Telecomms.) or H.N.C. They should have at least 10 years relevant experience in the provisioning, installation and maintenance of HF, MF, and VHF communications installations in the AM, CW and SSB modes; both valve type and transistorised solid state radio beacons; radio teleprinter using both tone on/off and two tone keying; multi channel VHF equipment and manual CB telephone exchanges.

Apply to CROWN AGENTS, 'M' Division, 4 Millbank, London, S.W.1, for application form and further particulars, stating name, age, brief details of qualifications and experience and quoting reference number M2K/7008100/WFI305.

1305

## RADIO OPERATORS

DO YOU HOLD

**PMG II OR PMG I OR NEW GENERAL CERTIFICATE  
OR HAD TWO YEARS' RADIO OPERATING EXPERIENCE?  
LOOKING FOR A SECURE JOB WITH GOOD PAY AND CONDITIONS?**

Then apply for a post with the Composite Signals Organisation—these are Civil Service posts, with opportunities for service abroad, and of becoming established, i.e. non-contributory pension scheme.

Specialist training courses (free accommodation) starting January, April and September, 1972.

If you are British born and resident in the United Kingdom write NOW for full details and application form from

**Recruitment Officer, Government Communications Headquarters,  
Oakley, Priors Road, CHELTENHAM, Glos. GL52 5AJ.**  
(Telephone: Cheltenham 21491, Ext. 2270)

92

## EXPERIMENTAL OFFICER IN MECHANICAL ENGINEERING

Required to assist in development and research activities and provide technical support for maintaining laboratory equipment. Experience in designing experimental engineering equipment and in using electronic instrumentation are considered essential and some practical knowledge of pneumatic and/or hydraulic control systems would be desirable.

Candidates should hold a B.Sc. degree, H.N.D. or an H.N.C. with considerable industrial experience, and would be expected to organise the work of a small technical force as necessary. It is unlikely that candidates under 25 years of age would be considered.

Salary Scale £1,902 to £2,592 per annum.

Applications should be sent to the Staff Officer, University of Surrey, Guildford, Surrey.

1296

## SITUATIONS VACANT

### O.E.M.

require

### ELECTRONIC ENGINEERS

to service a range of desk calculators and/or visible record computers. If you have experience in this field or in servicing digital equipment employing bipolar or M.O.S. semiconductors and are looking for a change, why not ring 01-407 3191 or write to:

**E. J. LANDON, OFFICE AND ELECTRONIC MACHINES LTD.,**

140/148 Borough High Street, London S.E.1,  
for an interview. 1309

## LABORATORY TECHNICIANS ELECTRONICS

(£1,056—£1,881 p.a. inc.)

The Central Electricity Research Laboratories, Kelvin Avenue, Leatherhead, Surrey, wish to recruit Laboratory Technicians for the construction and testing of a varied range of electronic and electro-mechanical apparatus and equipment, mostly prototypes, including chassis construction and layout, working from circuit diagrams, sketches and verbal instructions.

Applicants must be at least 25, have served a craft apprenticeship or recognised period of training with several years' practical experience and possess ONC or equivalent. A radio and television engineer with suitable practical experience in this field would also be considered.

Write or phone for application form to the Personnel Officer at above address (L'head 4488, ext. 363) as soon as possible. Full details of the work and conditions of employment will be discussed with short-listed applicants during interview. Ref. WW/193.

1308

**ROYAL HOLLOWAY COLLEGE  
(UNIVERSITY OF LONDON)  
Englefield Green, Surrey**

requires an

### AUDIO-VISUAL AIDS TECHNICIAN

Based in new Chemistry Department, the successful applicant will be required to operate a system of audio-visual aids including television and photography. Good wages and conditions of service. Applications, together with the names and addresses of two referees should be sent to the Personnel Officer not later than 31st August 1971. 1299

## THE UNIVERSITY OF SUSSEX SCHOOL OF MOLECULAR SCIENCES ENGINEER

required to work on Electronics and Instrumentation in the Chemical Laboratory. Candidates should be skilled in fault clearing in modern electronic equipment.

Salary scale: £1398-£1707. Three weeks paid holiday. Protective clothing provided. Superannuation and sickness benefit schemes.

Applications and/or enquiries for further information should be addressed to: the Laboratory Superintendent, School of Molecular Sciences, University of Sussex, Brighton, BN1 9QJ.

1286

**UNIVERSITY OF ESSEX  
DEPARTMENT OF ELECTRICAL ENGINEERING**

### TECHNICIAN

A Technician vacancy exists in the  
**VISUAL SYSTEMS RESEARCH LABORATORY**

Applicants should have an interest and preferably some experience in television. The position offers interesting work on cameras and CRT displays, both colour and monochrome, for use in video telephone experiments being carried out under a research contact with the British Post Office.

Salary scale (with approved basic qualifications) £1,041-£1,410 plus £51 higher qualification allowance where appropriate.

Applications, giving age, technical qualifications and details of experience to the Registrar, University of Essex, Wivenhoe Park, Colchester, Essex.

1294

**BRUNEL TECHNICAL COLLEGE, BRISTOL**  
Department of  
**MARINE AND AERO-ELECTRONICS**

Applications invited for following post,  
Duties to commence 1st September, or as soon as possible thereafter.

### LECTURER GRADE II in AERO-ELECTRONICS

Applicants must hold current Aircraft Radio Maintenance Engineers Licences, with Radar Ratings. Additional qualifications such as 'X' Electrics, 'X' Instruments, etc., an advantage.

Further particulars and application form from: Registrar(S) Brunel Technical College, Ashley Down, BRISTOL BS7 9BU. Please quote reference number 71/33. Closing date 30th July.

1290

## BUSINESS OPPORTUNITY

Earn a substantial extra income through a fascinating part-time business of your own that you could share with your wife and operate from your own home. This is an outstanding business opportunity with rewards exceeding £5000 per annum at the higher levels. We are looking for organisational and managerial ability. Telephone for an appointment.

**VISTA MARKETING MAIDENHEAD 28754  
1313**

**A FULL-TIME** technical experienced salesman required for retail sales; write giving details of age, previous experience, salary required to—The Manager, Henry's Radio, Ltd., 303 Edgware Rd., London, W.2. 167

**DRAUGHTSMEN.** Mechanical and Electrical required by expanding electronics company specialising in lighting control and audio visual products. This position is salaried and gives ample opportunity for advancement. Please apply Electronics Ltd., 47 Old Woolwich Road, Greenwich, London, S.E.10. Tel. 858 4784. 122

**INSTALLATION ENGINEER** required for the servicing, testing and installation of audio projection and lighting control equipment. An excellent opportunity for applicant with initiative and a sound knowledge of basic electronics. Starting salary £1,250. The post offers opportunities for travel in England and overseas. Apply to The Personnel Director, Electrosonic Ltd., 47 Old Woolwich Road, Greenwich, S.E.10. 1298

**TRANSMITTER Technician (34)** seeks new position giving test and maintenance experience on (a) VHF Transmitters, or (b) professional quality Audio equipment for Broadcasting, Sound Recording, or Public Addresses, etc., anywhere in U.K. Box W.W. 1311 Wireless World.

**WANTED:** Ambitious young man with good electronics knowledge for small workshop in Caterham, Surrey. Ring Caterham 42515. 1273

## ARTICLES FOR SALE

**AMERICAN 2N3055** transistors new, boxed, at 55p each. Forgestone Components, Ketteringham, Wymondham, Norfolk. 1255

**AERIAL BOOSTERS,** we make three types, L45 U.H.F. T.V., L12 V.H.F. T.V., L11 Radio. Price £2.95. S.A.E. for details. Velco Electronics, 62b Bridge Street, Ramsbottom, Bury, Lancs. 1297

**BUILD IT** in a DEWBOX quality plastics cabinet 2 in. X 2 1/2 in. X any length. D.E.W. Ltd. (W), Ringwood Rd., FERNDOWN, Dorset. S.A.E. for leaflet. Write now—Right now. 126

**BARGAINS P.S.U.'s,** test gear, etc. Lists S.A.E. Don Smith, 12 Channel Heights, Weston-Super-Mare, phone Bleadon 672. 1283

**COLOUR TV CAMERAS** complete with lenses, tubes and cables. Can be seen working. 01-229-0898 day or 01-907-0548 evening. 1279

**CREED 75,** reader and fitted punch £40. IMB model 'B' I/O typewriter £30. 01-262 6058 after 10 p.m. 1312

**17" BBC/ITV TELEVISIONS £5**

Working perfectly PLUS P. & P. £1.00 C.W.O. SUITABLE FOR ANY AREA  
3 Channel 19" D/S TVs. ITV, BBC 1, BBC 2, £25 inc. carriage. 17" 13 Channel, complete but untested, £1.50 each, plus £1 P. & P., C.W.O.

**SPEAKERS**

6" x 4", 7" x 4" 30HM, 20p plus Ep P. & P. each, C.W.O.  
REGULAR DELIVERIES THROUGHOUT ENGLAND AND NORTHERN IRELAND

**TRADE TV's**

407 Thornton Road, Gillingham, Bradford 8, Yorks. 77

**TV's TV's TV's**

SPECIAL OFFER—LIMITED PERIOD ONLY

Thorn 800 (chassis 13 Channel slim TVs. Good working order. Polished cabinets. Only £9.50 PLUS £1.50 carr.

**EX-RENTAL TV's**

Complete with 13 channel tuners. (Good cabinets. Carriage £1.50 extra.  
17" (Semi-Slim (90" tube) £2.50; 17" 21" Slim (110" tube) £4.50; 19" Slimline £6.50; 23" Slimline £8.50; 19" BBC2 Sets £14.50.

**PERFECT SPEAKERS EX TV**

Pm 3 ohm (minimum order two) 5 in. round, 8 in. by 2 in. rectangular, 12 1/2 p each. Add 7 1/2 p per speaker p. and p.

**VALVES EX EQUIPMENT**

EB91	5p	30P4	12 1/2p	PL36	22 1/2p
EBF89	12 1/2p	PC97	17 1/2p	PL81	17 1/2p
EC'82	12 1/2p	PCF86	17 1/2p	PY81	15p
EC180	7 1/2p	PC84	7 1/2p	PY800	15p
EF80	12 1/2p	PCF80	7 1/2p	PY82	7 1/2p
EF85	12 1/2p	PC'80	12 1/2p	PY83	22 1/2p
EF183	12 1/2p	PCL85	22 1/2p	UI91	17 1/2p
EF184	12 1/2p	PCL85	17 1/2p	6P23	17 1/2p
EY86	17 1/2p	PCL82	17 1/2p	30PL1	22 1/2p
30PL13	20p	PCL82	17 1/2p	30PL2	20p
630LZ	12 1/2p	PCL86	17 1/2p	30F5	10p
30L15	12 1/2p	PCL83	12 1/2p		

Add 2 1/2p per valve p. and p. Orders over £1 p. and p. free

**UHF TUNERS**

To suit Ferguson 850, 900 chassis £2.50. p. & p. 50p.

**SLOT METERS—SPECIAL OFFER**

Smiths Mk. 11 6d. Convertible to 5p (Smiths Kit costs 35p) £1 each incl. post and packing or 10 for £5 incl. post and packing.

Please write with SAE for quotations on any spares.

**TRADE DISPOSALS (Dept. T.S.), Thornbury Roundabout, Leeds Road, Bradford, Yorks.** (Tel. 665670)

**NOW UNDER NEW MANAGEMENT**

**FERRIC CHLORIDE**

Anhydrous, Technical Quality Packed in steel drums containing 100 x 11lb. bags Guaranteed High Quality—Low Price

S. J. BRANSON

111 Park Road, Peterborough PE1 2TR 1287

Marconi T.F. 144 G. £10

Wavemonitor G. 302 £6

Signal Injector A/S 85 £2

C.T. 54 V.V.M. with P.S.U. £10

8 M.F.D., 2,500 volt capacitors £3

50 yard Interpolation Oscillator £15

**GREENWELD ELECTRONICS**

24 Goodhart Way, West Wickham, Kent

Phone: 01-777 2001 1288

**COMPUTER PERIPHERALS**

Closure of computer site makes available the following tape editing equipment:

CRED Model 75 Teleprinter with soundproof cover, desk and auto transmitter, choice of two at £300 each.

CRED Verifier with Model 92 reader and Model 25 punch at £150.

CRED Teleprinter, type 54 also keyboard perforators (in Ferranti Pegasus Code) at £25.

Teletype punches BRPE 11, 8 hole with soundproof box at £155 also BRPE 1, 5 hole converted to phonic wheel sync, choice of two at £40 each.

ELLIOTT T.2/94. 250. c.p.s. 8 hole Optical Tape readers, choice of four at £150 each.

For further details contact

**Business Engineering Services, Gt. Bentley, Colchester, Essex.**

Telephone: 0473 (Ipswich)/77197 or 0206 (Gt. Bentley)/25/550. 1293

**MARTIN ASSOCIATES**

TELEPHONE: ARBORFIELD CROSS 610

Oscilloscope H.P. 175A 0-50MHz c/w 1781B and 1755A Plug-ins £350

Oscilloscope Tektronix 545A 0-33MHz £275

Oscilloscope Tektronix Plug-in Type CA £20

Freq/Timer Counter HP 5233L 0-2MHz 6 digit £160

Freq/Timer Counter HP 3734A 0-5MHz 5 digit £210

Freq/Timer Counter Venner TSA 53/HP 0-10KHz 6 digit £50

PSU Solartron AS 1410 0-30V 1A £35

PSU Advance PP6 Twin 0-30V 3A £75

Recorder Record 3" Graphic 0-1mA 1" and 6"/Hr £42-50

Recorder HP 7035B X-Y Plotter. Almost new £235

Recorder Cambridge Type L Potentiometric 4 point—100-0+100°C 0-100mV and 0-200mV FSD. Chart width 8". Chart speed 1", 2" and 4"/hr £95

Wave Analyser Airmec 853 HF Analyser 30 KHz-30MHz £40

Signal Generator Airmec 210 HF Generator 30KHz-30MHz. Stability .005% £75

Signal Generator Marconi TF1446 £10

Millivoltmeter Advance VM 78 £22-50

Digital Voltmeter Dymaco DM 2006 £325

Digital Voltmeter Dymaco DM 2020 £250

1000lb Thrust Vibration Systems Consisting of Shaker and Amplifier. Also available 250lb Thrust. Please ring for fuller details. We are always in need of Good Test Equipment. Contact us if you are considering disposal. 1306

**COLOUR, UHF and TV SERVICE SPARES. SPECIAL OFFER.** leading Brit. maker's Colour Monitor Panels designed to BBC standards. Pal filter and delay £6, chrominance £6, luminance £4-50, encoded video input £2-20 P/P 25p (or set of 4 £17-50 P/P 35p). Also quantity Colour TV Camera Panels. Plessey colour scan coils £5-75 P/P 35p, convergence coils £3-80 P/P 25p. Blue lateral £1-25 P/P 10p (or complete set £10 P/P 50p). Latest type colour scan and convergence coils, with electrical control of static convergence £6-25 P/P 35p. Colour LOPT assembly incl. EHT output and focus control £4-50 P/P 35p, luminance/chrominance panels £1 P/P 25p. Integrated transist. decoder incl. circuits £1-25 P/P 10p. **SPECIAL OFFER,** leading Brit. maker's surplus 625 single standard TV chassis, latest design, almost complete, includes transist IF stages, frame and line time bases, transformers, etc., incl. circuit, £8-65 P/P 50p. B9D valve bases for colour valves and PL500 series 12 1/2p P/P 5p. UHF tuners transistorised, rotary slow motion drive or push button £5-25 P/P 25p. Integrated UHF/VHF 6 position push button transistorised tuner easily adjusted as 6 position UHF tuner, incl. circuit £4-50 P/P 50p. Transist. UHF/VHF IF panels £4-75 (or salvaged £2-50) P/P 25p. MURPHY 600/700 series complete UHF conversion kits incl. tuner, drive assy., 625 IF amplifier, 7 valves, accessories, housed in special cabinet plinth assembly, £7-50 or less tuner £3 P/P 50p. SOBELL/GEC 405/625 switchable IF amplifier and output chassis, £1-50 P/P 30p. Ultra 625 IF AMP chassis and circuit £1-50 P/P 30p. Philips 625 IF AMP panel and circuit, £1 P/P 30p. SOBELL/GEC 2015 series 405/625 printed circuit IF panel incl. circuit £1-95 P/P 30p. UHF list available on request. VHF tuners AB miniature with UHF injection suitable K.B., Baird, Ferguson 75p P/P 30p. Cylcon C £1 P/P 30p, Pye 13 ch. incremental £1-25 P/P 30p. Ekco, Ferranti, Plessey push button tuner with UHF injection £1-50 P/P 30p. New fireball tuners Ferguson, HMV, Marconi type £1-90 P/P 30p. Philips export continental turret tuners 75p P/P 30p. Many others available. Large selection channel coils, LOPTs, Scan Coils. FOPTs available for most popular makes. Surplus Ultra, Murphy 110° Scan coils 75p P/P 30p. Sobell frame o/p transformers 90p P/P 30p. Transistorised time base panel for Ferguson portable £2-50 P/P 30p. Pye/Labgear transist. masthead UHF booster £4-25, UHF/VHF/FM set back booster, mains operated £5-90 Vols/F masthead amplifier power unit £2-50 P/P 25p. Surplus BBC2 Belling Lee "Skyline" distribution amplifiers £3 (Callers only)—MANOR SUPPLIES, 172 WEST END LANE, LONDON, N.W.6 (No. 28 Bus or W. Hampstead Tube Station). MAIL ORDER: 64 GOLDERS MANOR DRIVE, LONDON, N.W.11. Tel. 01-794 8751. [60

**COLOUR TELEVISION** components for the home constructor, all parts listed in new specialist catalogue, including delay lines, scan parts L.O.P.T.'s, Xtals, etc. S.A.E. to Forgestone components, Ketteringham, Wymondham, Norfolk. [1254

**FOR** sale over 450 Diodes, transistors and thyristors including high power types. All items are new and unused. Write for lists to Box W.W. 1272.

**LOWREY** Model K Electronic Organ complete working less Keyboards, contains 13 rhythm generator Leslie unit, Power Amplifier, Reverb, 12 note generators 4 dividers on each, etc. £75. Carriage arranged. PB Electronics, 47 Cowleigh Road, Malvern, Worcs. [1302

**MINI MAINS** Transformer for 9V dc power packs. Robust, yoked, flying leads, 30 x 30 x 37mm, 0-230-250V to 7-0-7V, 120mA. Only £0-70, UK post 5p. Amatronic Ltd., 396 Selsdon Road, S. Croydon, Surrey CR2 0DE. [1161

**NEW CATALOGUE** No. 18, containing credit vouchers value 50p, now available. Manufacturers' new and surplus electric and mechanical components, price 22 1/2p, post free. Arthur Sallis Radio Control Ltd., 28 Gardner Street, Brighton, Sussex. [94

**ONE** Slee R.K. Welding Machine complete with Thyatron Synchronous Timer, suitable for welding miniature assemblies, e.g. Radio Valves. Please telephone: The Administrative Officer, Brooke Bond Liebig Research Centre. 073-525 2411 [1295

**ONE** Collins type 30J Radio Transmitter. Frequencies 40, 20, 10 Metres. Circa 1939. Offers to Yates, Vandervell Products Ltd., Maidenhead, Berks. [1307

**SERVICE** Sheets (1925-1971) for TV's, Radios, Transistors, Tape Recorders, Record Players, etc.; over 8,000 models available. S.A.E. enquiries. Hamilton Radio, 54 London Road, Bexhill. Tel. Bexhill 7097. [1281

**VACUUM** pumps, coating plant, pyrometers, recorders spectrophotometers/ovens, etc. Free catalogue. Barrett, 1 Mayo Road, Croydon, CRO 2QP, Surrey. Phone 01-684-9917. 1056

**VHF.** 80-180 mHz Receiver, Tuner, Converter Kit, remarkable results from single transistor. £4-13 complete or S.A.E. for free literature. Johnsons (Radio), Worcester WR1 2DT. [WW99

**WIRELESS** WORLD Jan. 1913-Dec. 1950 (1920-1942 bound). Offers Tel. Huddersfield 52453. [1262

**6MM** Tubular Flanged Bulbs, 6V 0-2A, 5p each in lots of 50. Quantity available. Box No. W.W. 1301.

**TEST EQUIPMENT — SURPLUS AND SECONDHAND**

**SIGNAL** generators, oscilloscopes, output meters, wave voltmeters, frequency meters, multi-range meters, etc., etc., in stock.—R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [64

**RECEIVERS AND AMPLIFIERS — SURPLUS AND SECONDHAND**

**HERO** Rx5s, etc., AR88, CR100, BRT400, G209, S640, etc., etc., in stock.—R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [65

**NEW GRAM AND SOUND EQUIPMENT**

**GLASGOW.**—Recorders bought, sold, exchanged; cameras, etc., exchanged for recorders or vice-versa.—Victor Morris, 343 Argyle St., Glasgow, C.2. [11

**TAPE RECORDING ETC.**

**YOUR** TAPES TO DISC.—£6,000 Lathe. From £1-50. Studio/Location Unit. S.A.E. Leaflet. Deroy Studios, High Bank, Hawk St., Carnforth, Lancs. [70

**FOR HIRE**

**FOR** HIRE CCTV equipment, including cameras, monitors, video tape recorders and tape—any period. —Details from Zoom Television, Chesham 6777 [75

**ARTICLES WANTED**

**HIGHEST** CASH PRICES for Revox, Ferrograph, Brenell, Vortexion, Tanberg. 9.30-5.00. 01-837 8200. [102

**SPEAKERSET** STENTORIAN WHITELEY HF1012, T816, CX1500. Box No. W.W. 1268

**SERVICEABLE** CRT for Tektronix 555 double beam oscilloscope also plug-in amplifier units working or not and circuit manual. Ring Oxshot (Surrey) 3311. [1310

**WANTED,** all types of communications receivers and test equipment.—Details to R. T. & I. Electronics, Ltd. Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [63

**WANTED,** televisions, tape recorders, radiograms, new valves, transistors, etc.—Stan Willets, 37 High St., West Bromwich, Staffs. Tel. Sec. 0186. [72

**VALVES WANTED**

**WE** buy new valves, transistors and clean new components, large or small quantities, all details, quotation by return.—Walton's Wireless Stores, 55 Worcester St., Wolverhampton. [62

**CAPACITY AVAILABLE**

**AIRTRONICS** LTD., for Coil Winding—large or small production runs. Also PC Boards Assemblies. Suppliers to P.O., M.O.D., etc. Export enquiries welcomed. 3a Walerand Road, London, S.E.13. Tel. 01-852 1706 [61

**COIL** winding capacity. Transformers, chokes R.F. coils, etc., to your specification. Sweetnam & Bradley Ltd., Bristol Road, Malmesbury, Wilts., or Tel. Malmesbury 3491. [905

**DESIGN,** development, repair, test, and small production of electronic equipment, low rates. YOUNG ELECTRONICS, 54 Lawford Rd., London, N.W.5. 01-267 0201. [1057

**METALWORK,** all types cabinets, chassis, racks, etc., to your own specification, capacity available for small milling and capstan work up to 1 in. bar.—PHILPOTT'S METALWORKS, Ltd., Chapman St., Loughborough. [17

**WE** undertake the manufacture of transformers singly or in quantities to any specification. All work guaranteed for 12 months.—Ladbroke Transformer Co. Ltd., 820a Harrow Road, Kensal Rise, N.W.10. Tel. 01-969 0914. [100

**WE** can assist you by manufacturing p.c.b.s, control panels, sub-assemblies, short and long runs. Electronic Allied Components Ltd., BCA Estate, Measham, Staffs. Telephone: Measham 8225. [19

**TECHNICAL TRAINING**

**A.M.S.E. (ELEC.),** City & Guilds, R.T.E.B. Cert., Radio Amateurs' Cert., etc., on "Satisfaction or Refund" terms. Wide range of Courses in Elec. Engineering, Design, Installation, Repairs, Refrigeration, Electronics, Radio & TV, etc. Send for full details and illustrated book—FREE—BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY, Dept. 152K, Aldermaston Court, Reading RG7 4PF. [13

**BECOME "Technically Qualified"** in your spare time, guaranteed diploma and exam. homestudy courses in radio, TV servicing and maintenance. R.T.E.B., City & Guilds, etc., highly informative 120-page Guide—free.—Chambers College (Dept. 837K), Aldermaston Court, Reading RG7 4PF. [16]

**TECHNICAL TRAINING** in Radio, TV and Electronics through world-famous ICS. For details of proven home-study courses write: ICS, Dept. 443, Intertext House, London, S.W.8. 4UJ. [24]

**TUITION**

**COLOUR TV SERVICING.** Be ready for the coming Colour TV boom. Learn the techniques of servicing colour TV sets through new home-study courses specially prepared for the practical TV technician, and approved by leading manufacturer. Full details from ICS, (D 558), Intertext House, London, S.W.8 4UJ. [1263]

**HUNDREDS** of top paid jobs in Engineering await qualified men. Get a certificate through B.I.E.T. Home Study—Mech., Elec., Auto, Radio, TV, Draughts., Electronics, Computers, Building, etc. Send for helpful **FREE** book.—B.I.E.T., Dept. 151K, Aldermaston Court, Reading RG7 4PF. [14]

**MEN!** You can earn £50 p.w. Learn Computer Operating. Send for **FREE** brochure—London Computer Operations Training Centre, C.96, Oxford House, 9-15 Oxford Street, London, W.1. [1070]

**RADIO** and Radar M.P.T. and C.G.L.I. Courses. Write: Principal, Nautical College, Fleetwood, NY7 8JZ. [71]

**SERVICE & REPAIRS**

**INSTRUMENT SERVICING** AVO, Taylor, etc., multi-meters, meggers, signal generators, etc. Quick and competitive estimates free, guaranteed repairs, calibrated, collection locally. V. W. & E. Smith, 69 Chestnut Drive, Leigh 6674, Lancs. [1282]

**Thermistors**  
**F. J. Hyde, DSc, MSc, BSc.**

The aim of this book is to give for the first time a comprehensive account of the properties and applications of both positive and negative temperature coefficient (NTC and PTC) types of thermistors, in order that their potential usefulness in a wide range of instrumentation and measurement may be made evident. It will prove to be an indispensable reference book for all those interested in the application of this extremely useful circuit component.

0 592 02607 0 208 pages illustrated 1971 **£3.20**

Available from leading booksellers or:  
**The Butterworth Group**  
 88 Kingsway London WC2B 6AB  
 Showrooms and Trade Counter  
 4-5 Bell Yard London WC2

**COURSES**

**The POLYTECHNIC of NORTH LONDON**

**3-year full-time course for students with 2 'A' levels to become—**

**CHARTERED PROFESSIONAL ELECTRONIC AND RADIO ENGINEERS**

This modern course in solid-state electronics, starting in Sept. 1971, prepares students for entry into the Institution of Electronic and Radio Engineers and the Institution of Electrical Engineers.

*For further information return the slip below.*

Department of Electronic and Communications Engineering, The Polytechnic of North London, Holloway Road, London N.7. 8DB

Please send further details of your electronic engineering courses to:

NAME .....

ADDRESS .....

..... 1300

**Electronics at The Open University**

**Catch up in your spare time** by studying at home a new, introductory university course in Electromagnetics and Electronics which the Open University is offering in 1972.

Accepted students each receive an oscilloscope, and other equipment, to augment tuition by text, tutor, TV and radio. Whilst applicants are expected to have a scientific or technical background, no formal qualifications are needed. Further information can be obtained by writing to

G. A. H. Kiloh,



**The Open University**

Walton Hall, Bletchley, Bucks.



**TELEVISION AND RADIO TRAINING (DAY ATTENDANCE COURSES)**

This private College provides theoretical and practical training in Radio and TV Servicing. Courses of one year's duration, with daily attendance, are available for beginners and shorter courses for men with previous training in Electronics and Radio. Training courses in Radar and Radio Transmission are also available following the TV course. Write for prospectus to: **London Electronics College, Dept. B/5, 20 Penywern Road, Earls Court, London, S.W.5. Tel. 01-373 8721.**

## LAWSON NEW TUBES

Lawson "Century 99" are brand new tubes. Using silver activated screens, micro fine aluminizing, high definition electron guns. resulting in superb performance and very long life.



## TELEVISION TUBES REBUILT TUBES

Lawson "Red Label" rebuilt crts are particularly useful where cost is a vital factor such as in older sets or rental use. Red Label are completely rebuilt from selected glass and are exact replacements.

NEW TUBES		REBUILT TUBES	
CME 1602	£8.50	17"	£6.25
19"		14"	£4.25
21"	£7.25	17"	£4.87
23"	£8.50	19"	£5.25
19" TWIN PANEL	£10.25	21"	£6.87
23" TWIN PANEL	£15.50	23"	£7.25
19" PANORAMA	£9.38		
20" PANORAMA	£9.50		
23" PANORAMA	£11.95		

**2 years Guarantee both new and rebuilt**

**FULL TUBE FITTINGS**

**INSTRUCTIONS SUPPLIED**

CARR. INS. BY EXPRESS PASSENGER

14-19" 62p    21-23" 75p

WW-084 FOR FURTHER DETAILS

## EXCLUSIVE OFFERS

### AMPEX

#### Precision Instrumentation and Data TAPE RECORDER-REPRODUCERS



**TYPE FR 100A:** Six speeds, 15/16", 3/4", 15", 15" and 30" per second, 5 tracks, 1/2" tape (easily changed to 1/4" or 1" by changing rollers and heads), 10 1/2" reel capacity. Push button control. Precision servo control to 0.75 μ sec. track timing 5 μ sec. Drift free within 1 per cent. Accuracy 10<sup>6</sup> per week. Power input 105/125v 48 to 400 cycles.

**TYPE FR 1100,** as above but 4 speeds, 3/4", 7/8", 15" and 30" per second, and 4 track, easily changed to 1/4" or 1" and of lighter and more modern construction than Type FR 100A. **PRICE £380** for either type.

The above comprise complete units with electronics in 6 ft. cabinets

### HIGHEST QUALITY 19" RACK MOUNTING CABINETS

**Totally Enclosed**

**TYPE A:** 84" high x 24" deep x 24" wide.  
**TYPE B:** 78" high x 30" deep x 24" wide.

**DOUBLE SIDED.** These cabinets will take rack panels both sides, that is back and front and are drilled and tapped all the way down every 1/4" for this purpose. They are fitted with "Instant" patent fully adjustable rack mounts which are vertically and horizontally adjustable—these allow the panels to be recessed when they are fitted with projecting components and it is desired to enclose them by doors.

★ Other features include—all corners and edges rounded. Interior fittings tropicalised. Removable built in cable ducts. Removable built in blower ducts. Ventilated and insect proofed tops. Detachable side panels. Full length instantly detachable doors fitted expanding bolts if ordered with cabinets. Made in U.S.A.—cost the American Government £107 before devaluation. Finished in grey primer and in new condition.

**PRICE £26.50 each (Carriage extra)**

Full length door £5 each extra  
 Doors are not needed if panels are mounted back and front and they are not required to be enclosed.

**TYPE C:** 80" high x 27" deep x 22" wide. American Standard First Grade totally enclosed ventilated 19" rack panel mounting cabinets, made by Dukane, U.S.A. Open front fitted rack mounts drilled and tapped all the way down every 1/4". Full length rear door with latch. Finished in grey these cabinets have been used but are in good condition but if decoration is of importance it is recommended they are re-sprayed before use.

**PRICE £15 each (Carriage extra)**

**TYPE D:** 76" high x 18" deep x 22" wide. These are slightly smaller and finished in black otherwise they are similar in construction and condition to Type C above. Made by R.C.A. of U.S.A.

**PRICE £12.50 each (Carriage extra)**

ALSO OTHER TYPES 80" TO 88" HIGH AVAILABLE

Full details of all above available on request.  
**TRANSPORT:** We have made special economical transport arrangement for these cabinets to ensure they arrive undamaged and to avoid expensive crating. Full details on request.

**FREE**

40-page list of over 1,000 different items in stock available—keep one by you.

- ★ Sorensen 3KVA Stabilised Power Supplies 150/250 v ..... **245**
- ★ Avco Electronic Multimeters CT-4711 ..... **250**
- ★ Avco 180 Valve Testers ..... **245**
- ★ Ferranti High Speed Tape Readers S/7 Track ..... **235**
- ★ Marconi TF-887 Standard Signal Generators 15 K/cs/30 m/cs ..... **2155**
- ★ Airmec 701 Signal Generators 20 to 250 m/cs ..... **230**
- ★ Rhode and Schwarz E.S.M. 85/300 m/cs V.E.F. Receivers ..... **2280**
- ★ Video Tape Recorder 1/4" Shibaden, excellent working order, one only ..... **2140**
- ★ Laggear Stabilised Power Units D.4140, 2300 v 7 m/a ..... **235**
- ★ All Power Regulated Power Supplies 500 v 500 m/a ..... **240**
- ★ Marconi 825 lines BD-971 C.C.T.V. Camera, Control Unit, 14 in. Monitor with cables complete channel working order ..... **2195**
- ★ Flann Microwave Attenuators 4/12 G/mc ..... **250**
- ★ Portable Tape Deck Tester ..... **29**
- ★ CR-150/2 Marconi Communications Receivers, 1.5 to 22.0 m/cs ..... **224**
- ★ E.H.T. 40KV Transformers and associated Equipment up to 6KW available ..... **P.U.R.**
- ★ 10 foot long 8" sides Triangular Lattice Steel Mast Sections with mating lugs for joining up to 200 feet. New condition ..... **29**
- ★ Collins R-390 Communications Receivers 0.5/30.0 m/cs ..... **2275**
- ★ E.M.I. Tape Recorders BTR ..... **2125**
- ★ Weston 21-D.B. Meters -10/+6 ..... **22**
- ★ Commercial & Broadcasting type Lattice lightweight steel triangular Aerial Masts According to height 12 to 30 inch sides up to 200 ft. high to height

**WANTED C.C.T.V. EQUIPMENT**  
 Good price paid


- ★ 54 inch. dia. Meteorological Balloons ..... **21.50**
  - ★ 1" New Magnetic Recording Tape made by E.M.I. (USA) 3600 ft on N.A.B. Spools ..... **25.50**
  - ★ 1" Used ditto "Seetoh" Epan 4800 ft ..... **23**
  - ★ Beckman 5 decade Eput Meters ..... **240**
  - ★ Uniselectors 10 bank 25 way full wipe ex. new ..... **23**
  - ★ Precision Mains Filter Units new ..... **21.50**
  - ★ Avco Geiger Counters new ..... **27.50**
- Carriage extra at cost on all above  
 All goods are ex-Government stores.

We have a large quantity of "bits and pieces" we cannot list—please send us your requirements we can probably help—all enquiries answered.

**P. HARRIS**  
**ORGANFORD - DORSET**  
 BH16 6ER  
 BOURNEMOUTH 65051

# "Stella 99"

## INSTRUMENT CASES

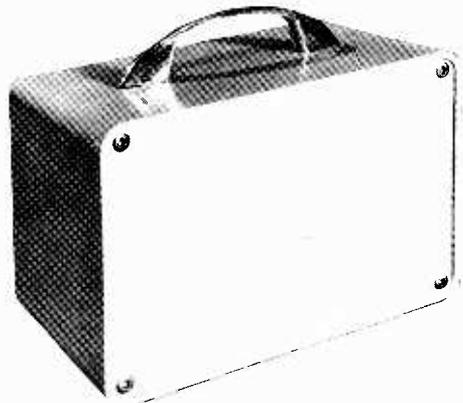

**PRICE**  
**£1.25p**  
 + 25p p.p.

**SIZE**  
 6"W x 4" H x 4"D

**WE BELIEVE THE FINEST INSTRUMENT CASE IN THE COUNTRY.  
 BEATS ALL COMPETITORS FOR PRICE AND STRENGTH.**

FIBREGLASS PRESS MOULDED IN GREY, AND BLUE. SUPPLIED WITH 4 RUBBER FEET, 18 SWG ALLOY CHASSIS, 16 SWG ALLOY FRONT PANEL. FRONT PANEL HAS PROTECTIVE FILM FOR MARKING OUT AND PROTECTION. CHROMED DIE CAST HANDLE. THE CASE HAS TWO SETS OF RUNNERS MOULDED IN WHICH WILL TAKE ALLOY OR P.C. BOARD CHASSIS. SAME DAY OFF-THE-SHELF DELIVERY. THIS SIZE OF CASE CAN BE TURNED ON END TO MAKE 4"W x 6"H x 4"D. PLEASE ADVISE IF HANDLE & FEET TO BE SUPPLIED LOOSE. PANEL PUNCHING AVAILABLE ON 100 UP. TRADE AND QUANTITY DISCOUNTS ON REQUEST.

FULL LIST OF ACCESSORIES AVAILABLE, SENT WITH EACH ORDER, i.e. SWITCHES, PANEL LAMPS, AMPLIFIERS, FUSES, ETC. NEXT SIZE OF CASE READY END OF JULY. 9"W x 4"H x 3"D. Ref. WW

## E. R. NICHOLLS,

46 Lowfield Road, Stockport, Cheshire. Tel: 061-480 2179

## ANDOR ELECTRONICS LTD.

for new  
 Mullard, Ferranti, R.C.A. Motorola  
 semiconductors

**Mullard—resistors—capacitors**

ZTX108 12p	MPF102 42 1/2p	AF117 25p
ZTX300 15p	MPF105 40p	BC107 19p
ZTX500 15p	2N3053 27p	BC109 19p

P. & P. 10p

Visit our new retail shop  
 45 LOWER HILLGATE  
 STOCKPORT  
 061-480-9791

## MAINS KEYNECTOR FAST & SAFE

For fast mains input to one or more electrical appliances up to 13 amps without plugs.

SEE PAGE 53



**£2.75**  
 p&p 0.25

Send for leaflet

## BARRIE ELECTRONICS

11 MOSCOW ROAD · QUEENSWAY  
 LONDON, W.2 Tel: 01-229 6681/2

WW-085 FOR FURTHER DETAILS

## WANTED C.C.T.V. EQUIPMENT

Good price paid

- ★ 54 inch. dia. Meteorological Balloons ..... **21.50**
- ★ 1" New Magnetic Recording Tape made by E.M.I. (USA) 3600 ft on N.A.B. Spools ..... **25.50**
- ★ 1" Used ditto "Seetoh" Epan 4800 ft ..... **23**
- ★ Beckman 5 decade Eput Meters ..... **240**
- ★ Uniselectors 10 bank 25 way full wipe ex. new ..... **23**
- ★ Precision Mains Filter Units new ..... **21.50**
- ★ Avco Geiger Counters new ..... **27.50**

Carriage extra at cost on all above  
 All goods are ex-Government stores.

We have a large quantity of "bits and pieces" we cannot list—please send us your requirements we can probably help—all enquiries answered.

## P. HARRIS

### ORGANFORD - DORSET

BH16 6ER  
 BOURNEMOUTH 65051

## DESIGNER-APPROVED "W.W." HI-FI KITS

### ★ LINSLEY HOOD MODULAR PRE-AMP

July 1969 no-compromise design for the purist. Compactly built on Lektrokit. Layout details. Kit price from £7.40 (mono, mag.p.u.+2 I/P.s). Dec 1970 mods. for pre-amp & low amp available.

### ★ LINSLEY HOOD SIMPLE PRE-AMP

Designer-approved PCB (marked component locations) gives excellent results with ceramic pick-up. Kit includes all parts as in May 1970 article plus front panel. Mono £6.35. Stereo £11.50 inc. p.p.

### ★ BAILEY 30W AMPLIFIER (Nov. '68)

Mk. IV PCB has extra pre-set for quiescent current. Output capacitor and PCB mount directly and compactly on specially designed generous heat-sink.

### ★ LINSLEY HOOD 15-20W AMPLIFIER

July 1970 latest and ultimate design. O/P capacitor, PCB, Tr3, 4 & 5 mount compactly onto heat-sink. Our kit personally tested and approved by the designer. Gain of O/P TR's > 100.

POWER SUPPLIES (simple and stab'd) available.

HIGH QUALITY components inc'g Mullard, Hunts, TCC capacitors, Plessey moulded pre-sets. O/P Tr's matched ±10% @ Ic=1 amp.

AFTER-SALES SERVICE at reasonable cost.

REPRINTS of any one article at 30p

DETAILED PRICE LISTS at 5p inc. p.p.

PERSONAL CALLERS WELCOME—BY APPOINTMENT. DESPATCH BY RETURN


## A.1 FACTORS

72 Blake Road, Stapleford,  
Nottingham

Tel. Nottingham 46051 Giro No. 487 6008

(8 a.m.—10 p.m. 7 days/week)

## BETTER GET 'SET'

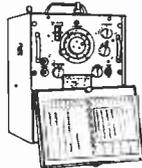

**BEST OFFER YET! Famous BC.221 Frequency Meter 125 KHz-20 MHz.** Complete with valves, crystal and charts. **Only £13.50.** Carr. £1.50. **Limited number. Order Now!**

**Marconi 801A Signal Generator.** 10-310 MHz. In original transit case. £45. Carr. £2.50.

**Crystal Calibrator No. 10.** Crystal controlled heterodyne wavemeter covering 500 KHz-10 MHz (Harmonics up to 30 MHz). Power required 300V. D.C. 15mA. 12V. 0.3A D.C. Test equipment for 62TM/RC. **Only £4.25.** P. & P. 50p. **Few only—No. 62 TM/RC 1-5-10 MHz. £17.50.** Carr. £2.



### AERIAL MAST EQUIPMENT

**20' Telescopic Masts.** £3.75. Carr. £1.  
**5' 2" extension sections** to fit bottom of above mast to increase height. £1.25 each (any number supplied)

**35' Mast.** (7-5' 2" interlocking sections) with base plate and 12 nylon guys with semi-auto tensioner. £22.50. Carr. £2.50.  
**70' Mast.** Ditto. 16 guys, block and tackle. £45. Carr. £2.75.

**R.F. ANTENNA TUNER (A.T.U.)** Cylinder design 10" x 4". Precision calibrated scale. Suitable for tuning most aerials for increased signal strength. A must for serious operators for RC or TM. Full instructions. **Only £1.75.** P. & P. 25p.

### R.F. ANTENNA TUNER (A.T.U.) OPEN TYPE

Mounted on ceramic former and feet. "Roller Coaster" design 16G silver or silver plated wheel traversing on wire on ceramic former. Will handle considerable R.F. In original packing. As used with No. 53 Transmitter. **Only £2.50.** P. & P. 50p.

**VHF Communication Receiver 1392.** Frequency range 95-150 MHz. Normally crystal controlled. (Mods. supplied for tuneable operation). Power requirements 240v A.C. 80mA 6.3v-4A. **Only £8.50.** Carr. £1.



**No. 19 TM/RC Rebuilt.** Complete station with PSU, Cables, Mic, Aerial etc. £22.50. Carr. £3.  
**No. 19 SET 500uA Meters.** Scaled 0-600 and 0-15v. Brand 'New, Boxed. £1.25. Post paid. (Quantity prices on request.)

**All No. 19 spares in stock.** Complete instruction book with circuits for No. 19 equipment. 37½p. Post paid.  
**R.F. Amplifier.** To increase output of No. 19 set. **Only £3.75.** Carr. £1.25. Instruction book for RF Amp. 37½p. Post paid.



**Heavy Duty Batteries.** New in metal cases with carrying handles.  
6v. 40AH. 10½" x 9½" x 5" £2.25. Carr. £1.  
6v. 85AH. 13" x 9½" x 7" £3.25. Carr. £1.25.

**Famous Tele 'F' Field Telephones.** Suitable for Farms, Building Sites, etc. Communication up to 5 miles or more. Rugged construction, will last a lifetime. **Only £5.75 pair.** Carr. £1. (Twin telephone wire for above available—ask for price.)



**Ex RAF Periscopes.** Made by Kelvin Hughes containing a precision made optics system providing crystal clear wide range vision (2 prisms and 8 lenses). Built in 24v heating circuit to prevent misting and freezing. Approx. 24" long with folding handles and rubber eyepiece. Complete, as new, in instrument case. **Only £5.** Carr. 75p. (Less case—store soiled £3.75. Carr. 75p.)

Many other Ex-Govt. Surplus Equipment items in stock. Receivers etc. in small quantities too numerous to mention. Enquiries invited. List 25p. Post paid. (Refundable against purchases over £3.)



## Surplus Electronic Trading

Drivers End Lane, Codicote, Hitchin, Herts, SG4 8TP

## INTERCONTINENTAL COMPONENTS

for:

## Electrolytic Capacitors

from 6V to 500V DC wkg

5 mfd to 10,000 mfd

Available from  
stock

## INTERCONTINENTAL COMPONENTS

Electric House,  
18 King St., Maidenhead,  
Berks. 5L6 IEG

Tel: MAIDENHEAD 32466

**YUKAN**  
**SELF-SPRAY**

Get these *all drying* **GREY HAMMER**  
**NOW!** OR **BLACK WRINKLE**  
(CRACKLE) finishes

Yukan Aerosol spraykit contains 453g fine quality, durable easy-mist spray. No stove baking required. Hammers available in grey and blue, 90p can pd. Modern Eggshell Black Wrinkle (Crackle) producing 3D textured finish. 90p can pd. all at 85p per push-button self-spray can at our counter. Also: Durable heat and water resistant Black Matt finish (330g self-spray can only) 75p can pd. SPECIAL OFFER One can plus optional transferable snap-on trigger handle (value 25p) for 96p can pd. Choice of 13 self-spray plain colours and primer (motor car quality) also available.

Other Yukan Air Drying Aerosols 453g at 90p can pd include: Zinc Chromate Clear Lacquer Metallic Grey Blue New British—even better

Please enclose cheque or crossed P.O. for total amount direct to Dept: O8 YUKAN, 307a EDGWARE ROAD, LONDON, W2 1BN


We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations. We can supply you too

Open all day Saturday. Closed Thursday afternoons

**CASH IMMEDIATELY AVAILABLE** for redundant and surplus stocks of radio, television, telephone and electronic equipment, or in component form such as meters, plugs and sockets, valves, transistors, semi conductors, capacitors, resistors, cables, copper wire, screws and nuts, speakers, etc. The larger the quantity the better we like it.
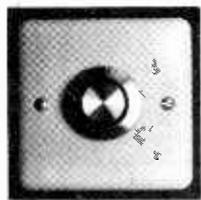
### BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, London, N12.  
Telephone: 01 445 2713 01 445 0749  
Evenings: 01 958 7624



## Dimmerswitch

Will dim up to 400 watts of incandescent lighting from zero to full brilliance. This unit simply replaces the normal light switch, and is fitted in a matter of minutes. An MK mounting frame is supplied, for use when more depth is required.

Complete Kit £2.80  
PRICE— Built and tested £3.20  
as supplied to Industry, Schools, Hospitals,  
Government Depts., etc.

## Diathane Ltd.

111, Sheffield Road, Wymondham, NORFOLK  
Please add £0.10 postage and packing

## AMERICAN

TEST AND COMMUNICATIONS EQUIPMENT

★ GENERAL CATALOGUE AN/104 1/6 ★

Manuals offered for most U.S. equipments

## SUTTON ELECTRONICS

Salthouse, Nr. Holt, Norfolk. Cley 289

**TRANSFORMER LAMINATIONS** enormous range in Radiometal, Mumetal and H.C.R., also "C" & "E" cores. Case and Frame assemblies.

**MULTICORE CABLE IN STOCK CONNECTING WIRES**

Large quantities of miniature potentiometers (trim pots) 20 ohm to 25K. Various makes. Wholesale and Export only.

**J. Black**

OFFICE: 44 GREEN LANE, HENDON, N.W.4. 2AH

Tel: 01-203 1855. 01-203 3033

STORE: LESWIN ROAD, N.16

Tel: 01-249 2260



**THE ONLY COMPREHENSIVE RANGE OF RECORD MAINTENANCE EQUIPMENT IN THE WORLD!**



Send P.O. 15p for 48 page booklet providing all necessary information on Record Care.

**CECIL E. WATTS LIMITED**

Derby House

Sunbury-on-Thames, Middx.

**OSMABET LTD.**

We make transformers amongst other things.

**AUTO TRANSFORMERS.** 0-110-200-220-240v a.c. up or down, fully shrouded fitted insulated terminal blocks, 30 watt **£1.35**; 50w **£1.80**; 75w **£2.10**; 100w **£2.55**; 150w **£3.15**; 200w **£3.90**; 300w **£5.25**; 400w **£6.30**; 500w **£7.50**; 600w **£8.25**; 750w **£9.75**; 1000w **£12.75**; 1500w **£18**; 3000w **£24.75**; 3000w **£33**; 4000w **£45**; etc.

**MAINS TRANSFORMERS.** Prim 200/240v a.c. TX2 250-0-250v 150 Ma, 6-3v 4A CT, 0-5-6-3v 3A, **£4.05**; TX5 300-0-300v 120 Ma, 6-3v 2A CT, 6-3v 2A, 6-3v 1A, **£4.05**; TX8 250-0-250v 65 Ma, 6-3v 1-5A, **£2.10**; MT1 200v 30 Ma, 6-3v 1A, **£1.20**; MT2 230v 45 Ma, 6-3v 1-5A, **£1.50**; MT2A 250v 60 Ma, 6-3v 2A, **£1.95**; MT3 Prim 110/240v, Sec 250v 100 Ma, 6-3v 2A, **£2.25**.

**MULTIVOLT TRANSFORMERS.** Prim 200/240v a.c. OMT4/1 one tapped sec, 5-20-30-40-60v giving 5-10-15-20-25-30-35-40-55-60, 10-0-10, 20-0-20, 30-0-30v a.c. 1 A **£2.25**; OMT4/2 2A **£3.45**; OMT5/1 One tapped sec 40-60-80-80-100-110v giving 10-20-30-40-50-60-70-80-90-100-110, 10-0-10, 20-0-20, 30-0-30, 40-0-40, 50-0-50v a.c. 1A **£3.45**; Duo 12v 4A-12v 4A **£3.60**; Duo 0-10-20-25v 2A **£3.60**.

**24v AUTO TRANSFORMERS.** Input 200/240v a.c., output 24v 150w **£4.50**; 250w **£6.75**; for quartz iodine lamps.

**LOW VOLTAGE TRANSFORMERS.** Prim 200/240v a.c. 6-3v 1-5A **83p**; 3A **£1.13**; 6A CT **£1.80**; 12v 1-5A **£1.13**; 3A CT **£1.80**; 6A CT **£2.70**; 18v 1-5A CT **£1.80**; 24v 1-5A CT **£1.80**; 3A CT **£2.70**; 5A **£3.75**; 8A **£6**; 12A **£8**; 40v 3A CT **£3.45**; 50v 6A CT **£9.75**.

**MIDGET RECTIFIER TRANSFORMERS.** Prim 300/240v a.c. size 1 1/2 x 2 1/4 in. PPT1 9-0-9v 0.3A; PPT2 12-0-12v 0-25A; PPT3 20-0-20v 0.15A **£1.20** each; size 2 x 1 1/4 in. MT9v 9-0-9v 1A **95p**; MT12v 12-0-12v 1A; MT20 20-0-20v 0-75 **£1.13** each.

**W.W. CAPACITOR DISCHARGE IGNITION TRANSFORMER** to specification, **£2.50** plus 25p p. & p.

**O/P TRANSFORMERS FOR POWER AMPLIFIERS.** 30 watt, A-A load 6-6K, sec 3-7-5-15 ohms, **£4.05**; 50 watt, A-A load 3K, **£6.75**; 100 watt A-A load 3K, **£11.40**; up to 400 watt to order.

**MAINS TRANSFORMERS FOR POWER AMPLIFIERS.** TX 6 Prim 200/240v a.c. Sec, 425-0-425v 500 Ma, 6-3v 6A CT, 6-3v 6A CT; 0-5-6-3v 3A, **£18.75**; TX1 Sec 425-0-425v 250 Ma, 6-3v 4A CT, 6-3v 4A CT, 0-5-6-3v 3A **£7.50**.

**LOUDSPEAKERS FOR POWER AMPLIFIERS.** New boxed, famous makes for public address systems, bass guitars, electronic organs, Hi-Fi, etc. 12in. 15W W/Tweeter **£4.05**; 12in. 25W **£5.60**; 12in. 35W **£7.20**; 12in. 50W **£9.45**; 15in. 60W **£11.30**; 18in. 100W **£19.90**; E.M.I. 13 1/2 x 8in. 10W 3, 8 and 15 ohms **£2.25** each; 13 1/2 x 8in. Hi-Fi 10W fitted twin tweeters with crossover network, 3, 8 and 15 ohms, **£4** each. Horn tweeters 2-16 KHz 8, 16 ohms, **£1.50** each.

**LOUDSPEAKERS** 5in. **90p**; 6in. **£1.10**; 8in. **£1.75**; 10in. **£1.95**; 7 x 4in. **£1.25**; 8 x 5in. **£1.35**; 10 x 6in. **£1.90**, 8 or 15 ohms.

**BULK TAPE ERASER.** Instant erasure of any size spool magnetic tape. Cassettes, demagnetizing of tape heads, 200/240v a.c. **£2.40**. P. & P. 20p. Leadet S.A.E.

**12v LT FLUORESCENT LIGHTING.** Complete 8 watt 12 in. fitting with tube **£3.75**; 12v inverter for 20 watt tube **£5.75**.

**PRINTED CIRCUIT ETCHING KITS.** Comprehensive factory pack, with all solutions, and equipment to make your own P.C. boards, instructions, **£1.25**.

**S.A.E. ENQUIRIES—LISTS. MAIL ORDER ONLY**  
46 KENILWORTH ROAD, EDGWARE, MIDDX, HA8 8YQ  
Carriage extra on all orders. Tel: 01-958 9314

**CUT THE COST OF SERVICING WITH LONG LIFE**

**Toshiba VALVES**

LOOK AT THESE PRICES AND MAKE YOURSELF POUNDS MORE PROFIT

Type	Goods	P.Tax	Total
EB.91	13 1/2p	5 1/2p	19p
ECC.82	21p	9p	30p
EF.80	19p	8p	27p
EF.183	26p	11p	37p
EF.184	26p	11p	37p
PCC.189	29p	12p	41p
PCF.80	24p	10p	34p
PCF.86	28p	11 1/2p	39 1/2p
PCF.801	30p	12 1/2p	42 1/2p
PCF.802	29p	12p	41p
PCL.82	24p	10p	34p
PCL.84	24p	10p	34p
PCL.85	26p	11p	37p
PCL.86	27p	11p	38p
PFL.200	37p	16p	53p
PL.36	38p	16p	54p
PL.84	19 1/2p	8p	27 1/2p
PL.504	39p	16p	55p
PL.508	44p	18p	62p
PL.509	67p	28p	95p
PY.500A	44p	18p	62p
PY.800	20 1/2p	8 1/2p	29p

Subject to settlement discount 5% of Goods content 7 days and 2 1/2% monthly.

Toshiba valves are being used extensively by major national companies. Here is your opportunity to take advantage of the savings to be made.



Write or Phone

**COMBINED PRECISION COMPONENTS, (PRESTON) LTD.**

3, Moor Park Avenue, Preston, PR1 6AS, Lancashire  
Tel. Home Sales Division. Preston 0772 56347  
Export Division. Preston 0772 54157

**JOHN SAYS...**

**RING MODULATOR** by Dewtron is professional, transformerless, 5-transistor, has adjustable F1/F2 rejection. Module **£7**. Unit **£8.90**. WAA-WAA Pedal kit of all parts, incl. all mechanics & instr. **ONLY £2.45**  
**AUTO RHYTHM** from Dewtron modules. Simple unit for waltz, foxtrot etc., costs **£16.55** in modules  
**ORGAN PERCUSSION** and other fascinating effects. Send 15p for illust. list. D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

**Quartz Crystal Units**  
**ECONOMICAL ACCURATE RELIABLE**

Private enquiries, send 5p in stamps for brochure

**THE QUARTZ CRYSTAL CO. LTD**

Q.C.C. Works, Wellington Crescent, New Malden, Surrey (01-942 0334 & 2988)

**LOWE ELECTRONICS**

119 Cavendish Road, Matlock, Derbyshire  
Tel: Matlock 2817

**SSB Communications Equipment, Test Gear, etc. Importers of Yaesu Musen, F E & Inoue Equipment.**

In addition to our wide range of new equipment, we offer the following second-hand receivers and test gear.

**Receivers:**

- R.C.A. 8516L, £150.
- Collins URR 391, £250.
- Collins 51J3, £150.
- Collins 51J4, £275.
- Collins URR 390A, £350.
- Collins URR 388, £225.

**Test Gear:**

- Valve tester TV-2C/U, £35.
- Frequency shift converters CV-116/URR, £75; CV-89A/URA-8A, £60.
- Signal generators CT212 (85 kHz to 32 MHz AM/FM), £29-50.
- BC221's, £15-£25, according to condition and linearity.

Mikes, keys, keyers, monitors, mobile antennas (Tavasut), headsets, intercomms., VTVM's, low voltage regulated p.s.u.'s, SWR bridges, components, etc., etc.

Have you equipment to sell? May pay you to get our quote.

Send a large s.a.e. and we will fill it with lists of equipment, components, sundries, etc., etc.

**Thanks to a bulk purchase we can offer BRAND NEW P.V.C. POLYESTER AND MYLAR RECORDING TAPES**

Manufactured by the world-famous reputable British tape firm, our tapes are boxed in polythene and have fitted leaders, etc. Their quality is as good as any other on the market, in no way are the tapes faulty and are not to be confused with imported, used or sub-standard tapes. 24-hour despatch service. Should goods not meet with full approval, purchase price and postage will be refunded.

S.P.	3in.	160ft.	10p	5in.	600ft.	30p
	5 1/2in.	900ft.	40p	7in.	1,200ft.	45p
L.P.	3in.	225ft.	12 1/2p	5in.	500ft.	42 1/2p
	5 1/2in.	1,200ft.	50p	7in.	1,800ft.	65p
D.P.	3in.	350ft.	22 1/2p	5in.	1,200ft.	60p
	5 1/2in.	1,800ft.	80p	7in.	2,400ft.	£1.00

Postage on all orders 7 1/2p

**COMPACT TAPE CASSETTES AT HALF PRICE**

60, 90, and 120 minutes playing time, in original plastic library boxes.  
MC 60 45p each. MC90 62 1/2p each. MC 120 92p each

**STARMAN TAPES**

28 LINKSCROFT AVENUE, ASHFORD, MIDDX. Ashford 53020

WW-086 FOR FURTHER DETAILS

**UP TO 40% OFF**  
**SCOTCH BASF PHILIPS**  
**TAPES & CASSETTES**  
 Incredible but true! We offer these famous brands at prices at least 5p per reel lower than any other cut-price advertiser. SEND for details now.

**Leda tapes**  
 Dept. WW 8  
 17 Leigh Park Road,  
 Leigh-on-Sea, Essex.  
 London Office: 01-226 7004


7400	21p	7410	21p	7474	40p
7486	43p	709	40p	741	73p
DALO PC MARKER			80p	2N3055	60p
ME0402	21p	ME0412	20p	ME0413	17p
ME1002	12p	ME4101	11p	ME4102	12p
ME6001	15p	ME6101	15p	MEL11	35p
MEF104	51p	MP8111	35p	1N4001	7p

**JEF ELECTRONICS (WW7)**  
 York House, 12 York Drive, Grappenhall, Warrington, Lancs.  
 Mail Order Only. C.W.O. P. & P. 5p per order. Overseas 37p  
 Money back if not satisfied.

**PRINTED CIRCUITS & ELECTRONIC EQUIPMENT**  
 ■ LARGE & SMALL QUANTITIES  
 ■ FULL DESIGN & P.T.H. PROTOTYPE SERVICE  
 ■ ASSEMBLIES AT REASONABLE PRICES

for full details contact  
**K.J. BENTLEY & PARTNERS**  
 18 GREENACRES ROAD, OLDHAM  
 P.O. APPROVED Tel 061 624 0939

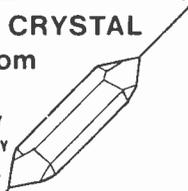**QUARTZ CRYSTAL UNITS from**  
 • 1.4 - 20 MHz  
 • FAST DELIVERY  
 • HIGH STABILITY  
 • TO DEF 5271-A



WRITE FOR LEAFLET AT-1  
**McKNIGHT CRYSTAL Co.**  
 SHIPYARD ESTATE HYTHE, SOUTHAMPTON  
 TEL. HYTHE 8961

**WE PURCHASE ALL FORMS OF ELECTRONIC EQUIPMENT AND COMPONENTS, ETC.**  
**CHILTMEAD LTD.**  
 7, 9, 11 Arthur Road, Reading, Berks.  
 Tel: 582 605

**WANTED**  
 surplus transistors, semiconductors, capacitors, cable, electrical goods, radio television and electrical equipment, wire, aluminium, motors, recording accessories and all surplus equipment for SPOT CASH.  
 Buyer will call to inspect anywhere.  
**Concorde Instrument Co.**  
 28 Cricklewood Broadway London, N.W.2  
 Telephone: 01-452 0161/2/3  
 Telex: 21492  
 Cables: CONIST LONDON

**KEYNECTOR**  
 The safe quick way to connect electrical equipment to the mains



Connects anything electrical in seconds. No plugs, sockets or bare wires! Takes multi-parallel connections up to 13 amps. Send for leaflet.

**EB INSTRUMENTS**  
 49-53 PANCRAS ROAD LONDON N.W.1 Tel: 01-837 7781

WW-087 FOR FURTHER DETAILS

**Thermistors**  
 F. J. Hyde DSc, MSc, BSc.

The aim of this book is to give for the first time a comprehensive account of the properties and applications of both positive and negative temperature coefficient (NTC and PTC) types of thermistors, in order that their potential usefulness in a wide range of instrumentation and measurement may be made evident. It will prove to be an indispensable reference book for all those interested in the application of this extremely useful circuit component.

0 592 02807 0 208 pages illustrated 1971 £3.20

Available from leading booksellers or:

**The Butterworth Group**  
 88 Kingsway London WC2B 6AB

Showrooms and Trade Counter  
 4-5 Bell Yard London WC2


**SURPLUS HANDBOOKS**

19 set Circuit and Notes	35p p/p 4p
1155 set Circuit and Notes	35p p/p 4p
H.R.O. Technical Instructions	30p p/p 4p
38 set Technical Instructions	30p p/p 4p
46 set Working Instructions	30p p/p 4p
88 set Technical Instructions	371p p/p 4p
BC.221 Circuit and Notes	30p p/p 4p
Wavemeter Class D Tech. Inst.	30p p/p 4p
18 set Circuit and Notes	30p p/p 4p
BC.1000 (31 set) Circuit and Notes	30p p/p 4p
CR.100/B.28 Circuit and Notes	521p p/p 4p
R.107 Circuit and Notes	371p p/p 4p
AR.88D Instruction Manual	821p p/p 5p
62 set Circuit and Notes	35p p/p 4p

Circuit Diagram 271p each post free. R.1116/A, R.1224/A, R.1365, R.F. 24, 26 and 26, A.1134, T.1154, CR.300, BC.312, BC.342, BC.348J, BC.348 (E.M.P.), BC.624, 22 1475(88), 1302. 52 set Sender and Receiver circuits 40p post free.  
 Colour Code Indicator 121p p/p 24p.  
 S.A.E. with all enquiries, please. Postage rates apply to U.K. only.  
 Mail order only to:  
**INSTRUCTIONAL HANDBOOK SUPPLIES**  
 Dept. W.W. Talbot House, 28 Talbot Gardens, LEEDS 8

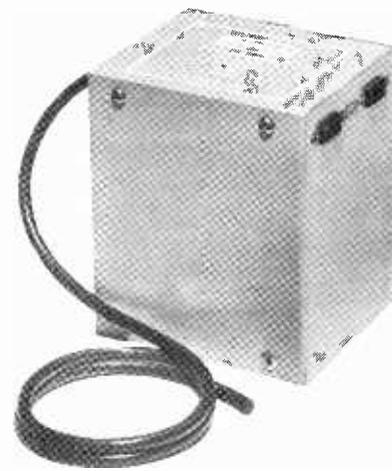**DOUGLAS AUTO-TRANSFORMERS**

Steel Case with Flexible Input Lead & American 15 Amp. Two-Pole Outlet Socket(s): 1 Socket up to 400 VA., 2 Sockets above 400 VA.



All sizes tapped:— 115-220-240 Volts. 50-100 HZ.  
 20 VA. Code XMT 1131 G. Price £1.87. P. & P. 24p.  
 500 VA. Code XMT 671 G. Price £6.75 P. & P. 50p.

TRANSFORMERS for all purposes available. Over 200 types IN STOCK; and from agents.  
 Please send for lists.  
**DOUGLAS ELECTRONIC INDUSTRIES LTD.,**  
 Dept. MO.12, Thames St., LOUTH, Lincs.

**★ DUMET—FULL SPEC. COMPONENTS ★**

74N TTL Gates: 7400, 10, 20, 30 etc.	20p	18p	1-24	25-99	100+
--------------------------------------	-----	-----	------	-------	------

See special Offer

Dec./Drivers: 74141, 42	85p	75p	65p
Ctrs: 7490, 92, 93	85p	75p	65p
Quad Latch: 7475	45p	43p	41p
F/F's: 7470, 72	34p	30p	28p
Dual F/F's: 7473, 74, 76	42p	39p	35p
Dual Schmitt: 7413	34p	30p	28p
Mon: 74121 (one shot) 122 (Retrig)	84p	74p	64p
Memories: 7481	£1-32	£1-22	£1-12
Ex. Or. Gate: 7486	78p	70p	59p
Op. Amps: 709N (Dij), 709P (8 Pin), 709C (Tos)	50p	43p	39p
741N, 741P, 741C	73p	58p	48p
Duals: 709DN, 741DN, 747N	£1-30	£1-20	99p
Diodes: 1N4148/914/916	4p	3p	2p

\*SPECIAL OFFER: 100 TTL Gates Any mix for £10. PLUS Beautiful TTL wall chart free with every I/C order.  
 Terms: Cash with order. Min. order 50p. P. & P. 10p. U.K.: 25p Europe; 60p Overseas.  
 Indicator Tubes—End View  
 High Rel. ... £2.90 £2.85 £2.80  
 Adders: 7480, 83 ... 85p 75p 65p  
 Dual Retrig: Mono: 74123 ... £1.90 £1.80 £1.60  
 80Ma Dec./Driv. 7445 (30v), (15v) ... £1.75 £1.65 £1.55  
 Up/Dwn Ctrs: 74190 (Dec.), 191 (4 Bit) ... £3.30 £3.00 £2.80

**DUMET PRODUCTS MAIL ORDER DEPT.**  
 P.O. BOX 19,  
 102, SOUTH STREET, BISHOPS STORTFORD, HERTS

**TELERADIO ELECTRONICS SPECIAL SERVICES**


Hi Fi Amplifier Kits by Linsley Hood Bailey, Texas & Nelson Jones with P.C. Board Layouts. Digital Clock Readout Kits. Radio Control Kit Systems.  
 Details gladly sent on request.  
**TELERADIO**  
 325/7, Fore St., Edmonton, N.9. 01.807.3719

**WW DESIGNS BUILT & TESTED**  
 example:  
 Nelson Jones FM Tuner £16  
 Phased locked stereo decoder £13  
 S.A.E. details:  
**YOUNG ELECTRONICS**  
 54 Lawford Road, London NW5 2LN. 01-267 0201

**INTER-LOCKING PLASTIC STORAGE DRAWERS**

NEAT! HANDY! TIDY!

**DISCOUNT PRICES**

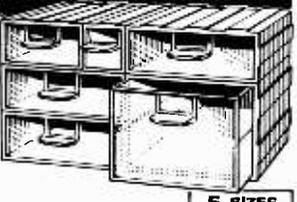

**5 SIZES ALL INTERLOCK**

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/handles on front. Build up any size cabinet for wall, bench or table top.

**BUY AT TRADE PRICES!**

Single units (1D) £1.35 per dozen size approx (2 1/4" high 2 1/4" wide 5" deep)  
 2D £2.25 per dozen. 3D £2.35 for 8 units.  
 6D2 £3.65 for 8 units (2 3D's in 1 outer)  
 6D1 £3.30 for 8 units. Postage/Carriage 35p for orders under £5. Carriage paid for orders over £5.

**PLUS QUANTITY DISCOUNTS!**

Orders £5 and over DEDUCT 5% in the £  
 Orders £10 and over DEDUCT 7 1/2% in the £  
 Orders £20 and over DEDUCT 10% in the £

QUOTATIONS FOR LARGER QUANTITIES

**IVORYET LIMITED** (Dept. WW8), 124 CRICKLEWOOD BROADWAY, LONDON, N.W.2 TEL. 01-450 4844

★ ALL PURPOSE TRANSISTOR PRE-AMPLIFIER ★  
 FOR MIKE, TAPE, P.U., GUITAR  
 Battery 9-12v. or 200-300v. H.T. Line. Size 1 1/2 x 1 1/2 x 1 in.  
 Response 25 c.p.s. to 25 Kc/s, 26 db gain. For use with valve or transistor equipment. Full instructions. 90p Post Free  
 Brand new. British made. Details S.A.E.

**BAKER 12 in. MAJOR £9**




30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. Rated 20 watts. Voice coils available 3 or 8 or 15 ohms. Post Free.

Module kit, 30-17,000 c.p.s. Size 19 x 12 1/2 in. with tweeter, crossover, baffle, instructions. **£11.50**  
 Ideal for Hi Fi or P.A.

**LOUDSPEAKER CABINET WADDING**  
 18 in. wide, 15p per ft. run.  
 Post extra 10p per order.

**E.M.I. QUALITY TAPE MOTORS** Post 15p  
 120/240v. A.C. 1,200 r.p.m., Heavy Duty 4 pole 135 mA.  
 Spindle 0.187 x 0.75in.  
 Size 3 1/2 x 2 1/2 x 2 1/2 in. **£1.25**

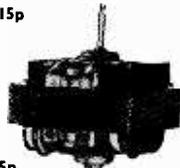**BALFOUR GRAM MOTORS**  
 120/240v. A.C. 1,200 r.p.m. Heavy duty 4 pole 50mA.  
 Spindle 0.15 x 0.75 in.  
 Size 2 1/2 x 2 1/2 x 1 1/2 in. **85p** Post 15p




**THIS ELAC CONE TWEETER IS OF THE VERY LATEST DESIGN AND GIVES A HIGHER STANDARD OF PERFORMANCE THAN MORE EXPENSIVE UNITS.**  
 The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3 1/2 x 3 1/2 x 2in. deep. Rating 10 watts. 3 ohm or 15 ohm **£1.90** Post 10p models.

**THE INSTANT BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER**



200/250 A.C. **£2.35** Post 15p  
 Leaflet S.A.E.

RETURN OF POST DESPATCH - CALLERS WELCOME  
 HI-FI STOCKISTS - SALES - SERVICE - SPARES  
**RADIO COMPONENT SPECIALISTS**  
 337 WHITEHORSE ROAD, CROYDON. Tel: 01-684-1665

**STOP PRESS**

**KIENZLE ELECTRONIC PRINTERS**  
 Type D1 14 print positions **£160.**  
 Type D1 13 print positions **£150.**  
 Type D1-SW 14 print positions, programmable carriage **£200.**  
 Type D11-E 14 print positions **£150.**  
 Stands for above **£10.**  
 These printers are fully refurbished and are sold with a 3 months warranty.

**TEKTRONIX OSCILLOSCOPE TYPE 517A**  
 This is a wide band high voltage single beam oscilloscope designed for observing waveforms having extremely short rise times. Transient response—rise time 7 nanoseconds. Sensitivity—0.05 v/cm; with probe 0.1 v/cm. Price **£295** with 3 months warranty.

**HILGER & WATTS ULTRASCAN TYPE H999 Mk. II**  
 A simple to operate recording spectrophotometer for rapid routine analysis in the range 200-750 millimicron to an accuracy of ±1% or better. This instrument is ideal for laboratories where a great deal of spectrophotometric work is done.  
 This instrument is in excellent condition and is offered at £500 complete with accessories and instruction manual.

**ELECTRONIC BROKERS LIMITED**  
 49-53 Pancras Road, London, N.W.1  
 Telephone 01-837 7781

**CLASSIFIED ADVERTISEMENTS**

**Use this Form for your Sales and Wants**

To "Wireless World" Classified Advertisement Dept., Dorset House, Stamford Street, London, S.E.1

PLEASE INSERT THE ADVERTISEMENT INDICATED ON FORM BELOW

- Rate: 45p (9/-) PER LINE. Average seven words per line. Minimum two lines.
  - Name and address to be included in charge if used in advertisement.
  - Box No. Allow two words plus 25p (5/-).
  - Cheques etc., payable to "Wireless World" and crossed "& Co."
  - Press Day 12th August for September 1971 issue.
- NAME.....
- ADDRESS .....

			REMITTANCE VALUE..... ENCLOSED

Please write in block letters with ball pen or pencil. NUMBER OF INSERTIONS.....

# We can't wait to expand your laboratory

in 24 hours you can hire some of the World's top instruments  
at competitive prices

ring **LABHIRE** South: **06-285 23106**  
North: **061-928 0800**

Southern Office: Cores End Road, Bourne End, Bucks. SL8 5AS. Northern Office: Shearer House, Dunham Road, Altrincham, Cheshire.

## INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 85-92

	PAGE		PAGE		PAGE
Al Factors.....	94	Hall Electric Ltd.....	8	Quality Electronics Ltd.....	16
Acoustical Mfg. Co., Ltd.....	29	Harris Electronics (London) Ltd.....	24	Quartz Crystal Co., Ltd.....	95
Adcola Products Ltd.....	Cover iii	Harris, P.....	93		
Advance Electronics Ltd.....	3	Hart Electronics.....	64		
A.E.G. (G.B.) Ltd.....	7	Hatfield Instruments Ltd.....	30	Radio & TV Components Ltd.....	54
Anders Electronics Ltd.....	28, 34	Heath (Gloucester) Ltd.....	27	Radio Components Specialists Ltd.....	97
Andor Electronics Ltd.....	93	Henry's Radio Ltd.....	56, 57	Ralfe, P. F.....	78
A.N.T.E.X. Ltd.....	44	Henson, R., Ltd.....	94	Rank Wharfedale Ltd.....	32
Arrow Electric Switches Ltd.....	23			R.C.S. Electronics.....	20
Audio Supplies.....	36			Resound Ltd.....	16, 25
Audix, B. B. Ltd.....	28			R.S.C. Hi-Fi Centres Ltd.....	71
				R.S.T. Valves Ltd.....	54
		I.C.S. Ltd.....	60		
Barrie Electronics.....	53, 93	I.M.O. Precision Controls Ltd.....	35		
Batey, W., & Co.....	14	Instructional Handbook Supplies.....	96		
Bentley, K. J., & Partners.....	96	Integrex Ltd.....	60		
Bentley Acoustical Corporation Ltd.....	68	Intercontinental Components.....	94		
B.I.E.T.....	13	I.T.T. Mobile Communications.....	Cover ii		
Bi-Pak Semiconductors.....	80	Ivoryet Ltd.....	97		
Bi-Pre-Pak Ltd.....	52			Samson (Electronics) Ltd.....	81
Black, J.....	95	J.E.F. Electronics.....	96	Scientific & Technical Services.....	70
Bowthorpe Helleman Ltd.....	9	Jackson Bros. (London) Ltd.....	32	Service Trading Co.....	75
Bull, J. (Electrical) Ltd.....	72	Jackson, J. D., Electronics.....	12	Servo & Electronic Sales Ltd.....	51
		Jermyn Industries.....	16	Shure Electronics Ltd.....	40
				Sinclair Radionics Ltd.....	47, 48, 49
Cambridge Audio Laboratories Ltd.....	37			S.M.E. Ltd.....	4
Carston Electronics Ltd.....	12	Keytronics.....	64	Smith, G. W. (Radio), Ltd.....	61, 62, 63
Cesar Products Ltd. (Yukan).....	94			S.N.S. Communications Ltd.....	17
Chiltmead Ltd.....	73, 96	Labgear Ltd.....	19	Special Product Distributors Ltd.....	30
Colomor (Electronics) Ltd.....	83	Labhire Ltd.....	98	Starman Tapes.....	95
Combined Precision Components.....	95	Lasky's Radio Ltd.....	53	Steed, John, Research Ltd.....	26
Computer Sales and Service Ltd.....	57	Lawson Tubes.....	93	Stephens Electronics.....	74
Concorde Instrument Co.....	96	Leda Tapes.....	96	Strumech Eng. Ltd.....	14
Croydon Precision Inst. Co.....	16	Ledon Instruments Ltd.....	30	Sugden, J. E., Ltd.....	16
		Levell Electronics Ltd.....	1	Surplus Electronic Trading.....	94
Dewtron.....	95	Light Soldering Developments Ltd.....	26	Sutton Electronics Ltd.....	94
Dexter & Co.....	22	Lowe Electronics.....	95		
Diathane Ltd.....	94	L.S.T. Components Ltd.....	66		
Diotran Ltd.....	82			T.B. Technical Ltd.....	26
Dixons Technical (CCTV) Ltd.....	20	Marconi Instruments.....	21	Telequipment Ltd.....	38
Douglas Electronic Industries Ltd.....	96	Marshall, A., & Sons (London), Ltd.....	64, 65	Teleradio, The (Edmonton), Ltd.....	96
D.T.V. Group Ltd.....	67	McKnight Crystal Co.....	96	Teonex Ltd.....	22
Dumet Products.....	96	Mills, W.....	68, 69	Tinsley, H., & Co., Ltd.....	15
		Milward, G. F.....	77	Trio Corporation Ltd.....	6
		Modern Book Co.....	22		
E.B. Instruments.....	96	Multicore Solders Ltd.....	Cover iv	Valradio Ltd.....	14
Edwards Scientific Int. Ltd.....	24			Vitavox Ltd.....	70
Electronic Brokers.....	58, 59, 97	Newmarket Transistors Ltd.....	11	Vortexion Ltd.....	2
Electronics Design Associates.....	70	Nettlefold & Moser Ltd. (GKN).....	24		
Electro-Tech Sales.....	76	Nicholls, E. R.....	93	Watts, Cecil E., Ltd.....	95
Electrovalue.....	79	Nombrex Ltd.....	28	Wayne Kerr, The, Co., Ltd.....	10
Elektrim.....	22	Osmabet Ltd.....	95	Webber, R. A., Ltd.....	36
English Electric Valve Co., Ltd.....	42, 43	Oxley Developments Co., Ltd.....	20	West Hyde Developments Ltd.....	50
Enthoven Solders Ltd.....	18			West London Direct Supplies.....	70
		Parker, A. B.....	36	Weyrad (Electronics) Ltd.....	54
Farnell Instruments Ltd.....	18	Patrick & Kinnie.....	82	Wilkinson, L. (Croydon), Ltd.....	70
Ferroglyph, The, Co., Ltd.....	41	P.C. Radio Ltd.....	83		
		Plessey Electronics Ltd.....	31	Young Electronics.....	96
Gardners Transformers Ltd.....	5	Powertran Electronics.....	60		
Goldring Mfg. Co., Ltd.....	33, 35			Z. & I. Aero Services Ltd.....	84
Grampian Reproducers Ltd.....	36				
Greenwood, W., Electronic Ltd.....	15				

with

# ADCOLA you're on the right wave-length



FEATURING THE NEW INVADER MODEL (L 646)



## ADCOLA PRECISION SOLDERING EQUIPMENT

offers you the right quality at the right cost for every requirement from home output to full scale industry.

- Extensive range to choose from.
- Precision quality for increased efficiency.
- Speedy after-sales service.
- Interchangeable bits—ex stock.
- Special temperatures available at no extra cost.
- Designed and developed to lower your production costs.

*Always choose ADCOLA for sound soldering!*

# ADCOLA

Regd Trade Mark

**ADCOLA PRODUCTS LTD.**

Adcola House, Gauden Rd. London S.W.4

Tel: 01-622 0291/3

Grams: Soljoint, London

Telex: Adcola London 21851

**POST COUPON NOW FOR DETAILS OF OUR EXTENSIVE RANGE**

To ADCOLA PRODUCTS LTD. (Dept. H), Adcola House, Gauden Road, London, S.W.4.

*Please send me a copy of your latest catalogue by return.*

NAME.....

ADDRESS .....

W.W.I

# Don't risk it-use SAVBIT

**THE EXCLUSIVE MULTICORE ALLOY WHICH IS SATURATED WITH COPPER TO PREVENT ABSORPTION OF COPPER FROM COPPER WIRES, CIRCUIT BOARDS AND SOLDERING IRON BITS**



When soldering fine copper wire, ordinary tin/lead solder alloys will absorb some of the copper, so that the diameter of the wire will be reduced.

Ersin Multicore Savbit Type 1 solder contains a small percentage of copper so that the solder is already 'saturated' with copper and will not absorb it from copper wire or copper laminate.

Savbit will also prolong the life of copper soldering iron bits by 10 times, thus eliminating the need for frequent resurfacing of copper bits and by keeping

the copper bits in good condition, the soldering speed and efficiency are increased.

Savbit Type 1 alloy contains 5 cores of non-corrosive extra fast rosin based Ersin Flux. Melting point is 215°C. Recommended bit temperature is 275°C.

Savbit Type 1 alloy with Type 362 Ersin Flux has received Ministry approval under number DTD.900/4535. It may be used for soldering processes on equipment for Services use in lieu of solder to BS.219.

**FOR  
FACTORY  
USE**

**7 lb. REELS**

Available in standard wire gauges from 10-22 swg., on strong plastic reels.



**1 lb. REELS**

Available in all standard wire gauges from 10-34 swg., on unbreakable plastic reels. (From 24-34 swg. only 1/2 lb. is wound on one reel.)



**FOR  
MAINTENANCE  
AND SERVICE  
ENGINEERS**

**SIZE 1 CARTONS**

In 14, 16 and 18 swg. Packed in a coil, so it can be drawn out through the top of the carton.



**SIZE 5**

A Coil of 18 swg., packed in a unique handy dispenser.



**SIZE 12**

75 ft. approx. of 18 swg. on a plastic reel packed individually in a carton.



**USED  
THROUGHOUT  
THE WORLD**




**HOLLAND**

Ersin Multicore Savbit Alloy is used by Bull Nederland of Amsterdam, Holland for the assembly of administration and statistics machines.

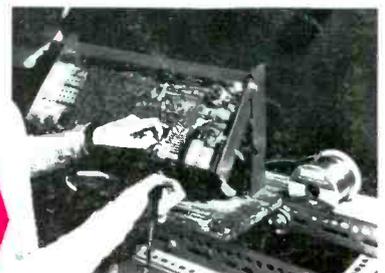**NEW ZEALAND**

Ersin Multicore Savbit Alloy is seen being used at the factory of Bell Radio Television Corpn. Ltd., Auckland, New Zealand.



For further details, please apply on your Company's notepaper to:  
**MULTICORE SOLDERS LTD., HEMEL HEMPSTEAD, HERTS. Telephone: HEMEL HEMPSTEAD 3636**  
 Telex: 82363