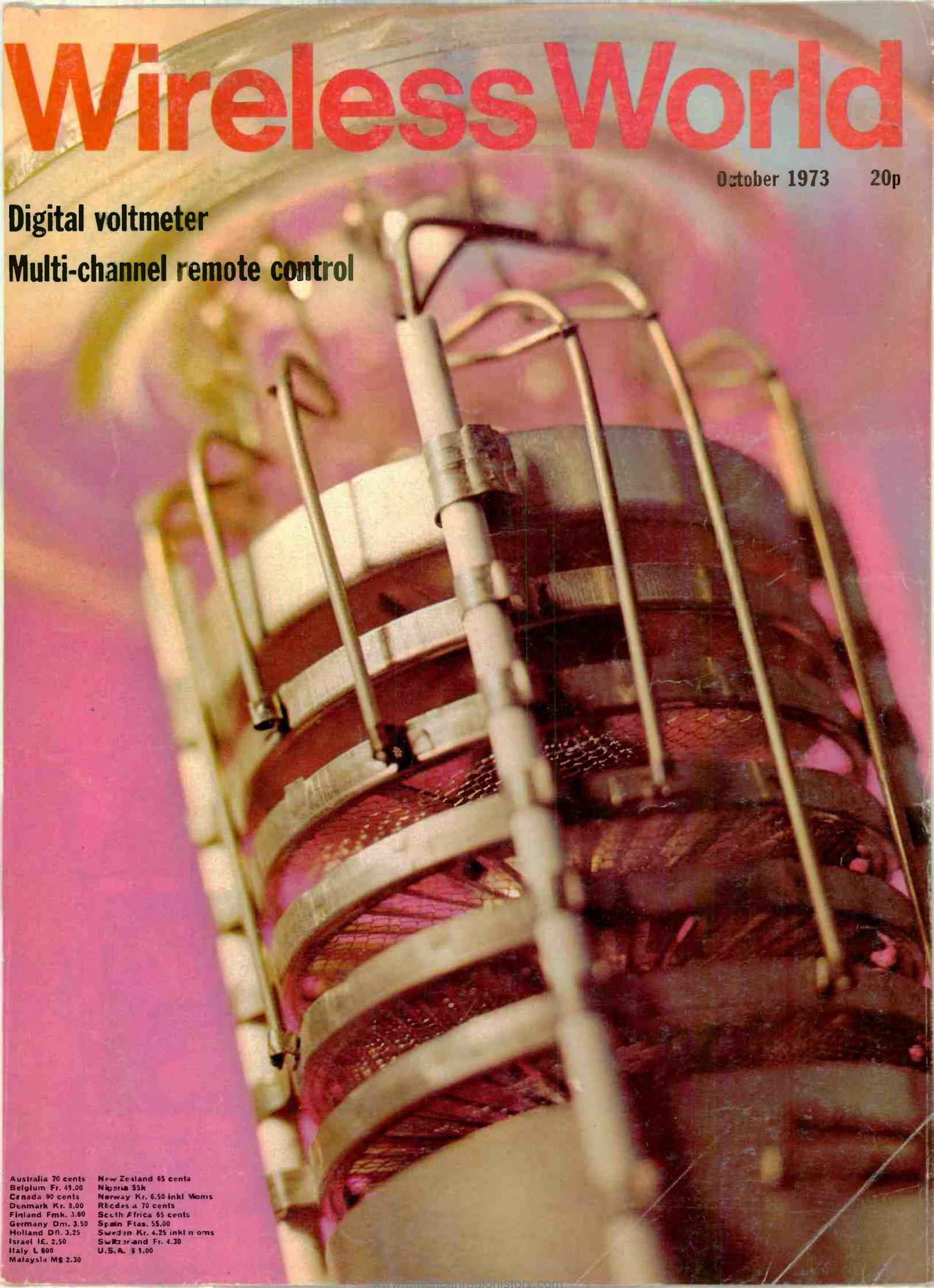


Wireless World

October 1973 20p

Digital voltmeter

Multi-channel remote control



Australia 70 cents
Belgium Fr. 41.00
Canada 90 cents
Denmark Kr. 3.00
Finland Fmk. 3.60
Germany Dm. 3.50
Holland Dfl. 3.25
Israel L. 2.50
Italy L. 600
Malaysia M\$ 2.30
New Zealand 65 cents
Nigeria 55k
Norway Kr. 6.50 inkl. Moms
Rwanda a 70 cents
South Africa 65 cents
Spain Ptas. 55.00
Sweden Kr. 4.25 inkl. moms
Switzerland Fr. 4.30
U.S.A. \$ 1.00

**CALIBRATION SOURCE
AC VOLTS + AMPS**

There's a whole catalogue of excellent reasons why you should choose the new Bradley 232 for your critical AC calibration source requirements.

To begin with it's exceptionally versatile, suitable for a wide range of applications. First-class short-term stability (typically 20 ppm over 5 minutes) make it ideal for calibrating digital and differential AC voltmeters or for checking frequency response of multimeters and amplifiers.

It offers a first-class performance over a wide dynamic range. There are five voltage ranges from 0.1 to 1000V and four current ranges from 0.1 to 1.0A. Frequency is continuously variable from 30Hz to 100kHz internally, or can be controlled from an external oscillator.

You can take it to your production line to set up AC attenuators quickly and easily – or use it in your development lab to probe breakdown factors in components and systems. Couple two in tandem and you can check power meters as well.


The Bradley 232 is a compact, highly-stable instrument that can replace a whole rack of conventional gear, yet it carries the eminently reasonable price of just £540 in the UK.

To find out more about the Bradley 232 AC Calibration Source, please telephone Ashley Stokes on 01-450 7811, extension 113. Or write to him at the address below.

Price quoted does not include VAT

Our own BCS Certificate is available.

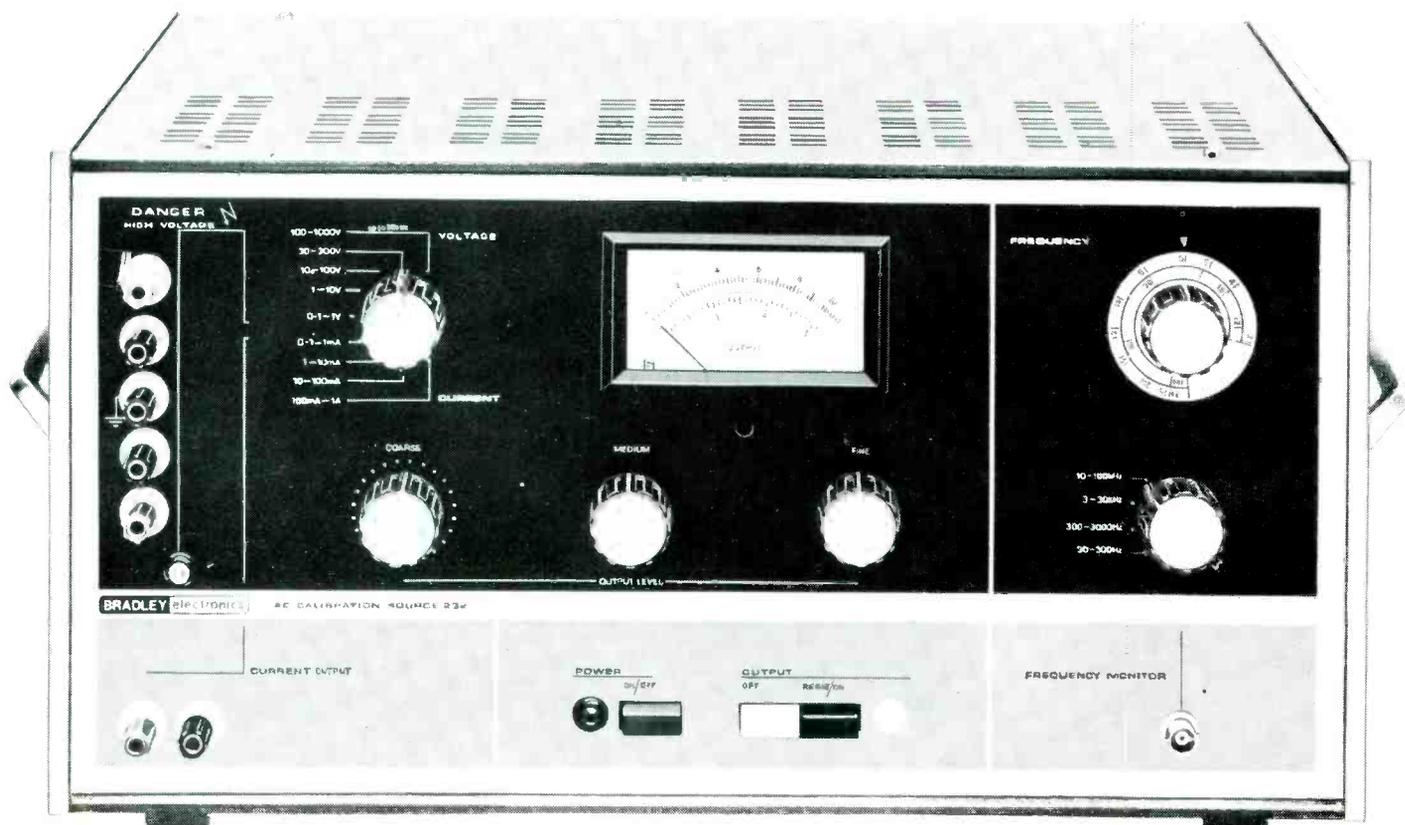G & E BRADLEY LIMITED,
Electral House, Neasden Lane,
London, NW10 1RR
Telephone : 01-450 7811
Telex : 25583
A Lucas Company



WW-001 FOR FURTHER DETAILS

LOW COST RC OSCILLATORS 1Hz TO 1MHz



LEVELL
PORTABLE INSTRUMENTS




ANALOGUE

FREQUENCY 1Hz to 1MHz in 12 ranges. Acc. $\pm 2\%$
 $\pm 0.03\text{Hz}$.
SINE OUTPUT 7V r.m.s. down to $<200\mu\text{V}$ with $R_s = 600\Omega$
DISTORTION $<0.1\%$ to 5V, $<0.2\%$ at 7V from 10Hz to 100kHz.
SQUARE OUTPUT 7V peak down to $<200\mu\text{V}$. Rise time $<150\text{nS}$.
SYNC. OUTPUT $>1\text{V}$ r.m.s. sine in phase with output.
SYNC. INPUT $\pm 1\%$ freq. lock range per volt r.m.s. input.
METER SCALES 0/2V, 0/7V & $-14/+6\text{dBm}$. on TG200M & DM only.
SIZE & WEIGHT 7" high x $10\frac{1}{2}$ " x $5\frac{1}{2}$ " deep. 10 lbs.

TG200	TG200D	TG200M	TG200DM
£42	£45	£52	£55
Sine O/P	Sine & Sq. O/P.	Sine O/P + meter.	Sine & Sq. O/P + meter.

NOTE: All prices subject to V.A.T.

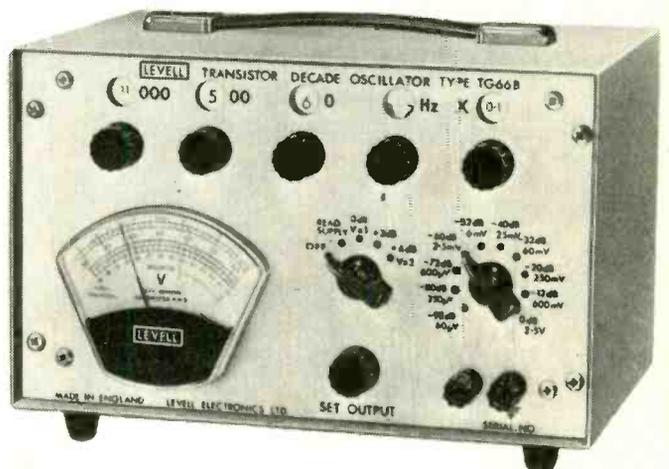

DIGITAL

FREQUENCY 0.2Hz to 1.22MHz on four decade controls.
ACCURACY $\pm 0.02\text{Hz}$ below 6Hz
 $\pm 0.3\%$ from 6Hz to 100kHz
 $\pm 1\%$ from 100kHz to 300kHz
 $\pm 3\%$ above 300kHz.
SINE OUTPUT 5V r.m.s. down to $30\mu\text{V}$ with $R_s = 600\Omega$
DISTORTION $<0.15\%$ from 15Hz to 15kHz.
 $<0.5\%$ at 1.5Hz and 150kHz.
METER SCALES 2 Expanded voltage & $-2/+4\text{dBm}$.
SIZE & WEIGHT 7" high x $10\frac{1}{2}$ " wide x 7" deep. 12 lbs.

TG66B
£120
Batteries only.

TG66A
£150
Mains unit & batteries incl.

Prices include batteries with 400 hour life. Mains power units £10 extra. Leather cases £6 extra.

Send for literature covering our full range of portable instruments.

LEVELL ELECTRONICS LTD. Moxon Street, High Barnet, Herts. EN5 5SD
Tel: 01-449 5028/440 8686



ARROW

miniature rockers and pilot lights snap-in to action!

A good-looking lineup—the Arrow miniature rocker brigade! They're reporting for 10A 250V ac duty, and just as soon as you call them up, they start saving you assembly time—and panel space. They parade shoulder, to shoulder with their unique snap-in facility securing them tightly in an instant. Eight single and eight double pole versions, 2 and 3 position switching with biased action, pilot lights, illuminated rockers—there's a really wide matching choice. Many to BS3955 and CEE24 standards, and ready to face 100,000 ops and still come out switching! Ask for the full data on Arrow 1100 series rockers.

16 AMP VERSIONS


The single pole on/off and some changeover versions are now available with a 16 amp rating. Send for further details.



ARROW-HART (EUROPE) LTD.
PLYMOUTH ROAD, ESTOVER,
PLYMOUTH PL6 7PN, ENGLAND.

TEL: 0752 701155 Telex: 45340 Cables: ARROWHART PLYMOUTH
Scottish Office: 13 Murray Place, Stirling Telephone: 0786 3823

Arrow switches *right* across the panel

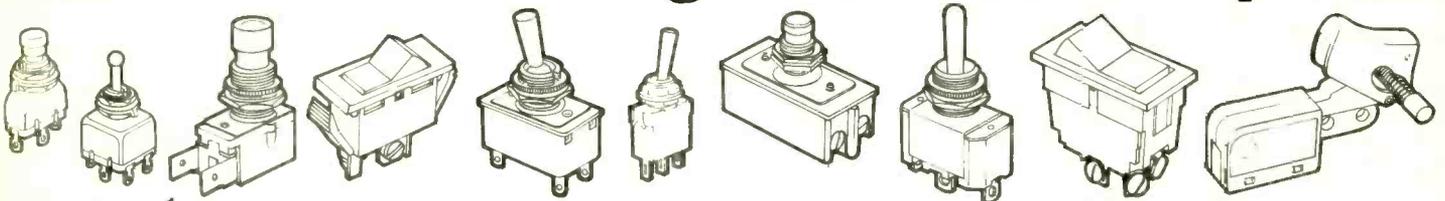

U.K. Distributors

COMWAY ELECTRONICS LTD.
BRACKNELL—Bracknell 24765

ITT ELECTRONIC SERVICES
HARLOW—Harlow 26777
SUTTON COLDFIELD—021-355 4511

LEIGH—Leigh 5211/2/3
JOHNSTONE, Renfrewshire—
Johnstone 23457

COMBINED ELECTRONIC SERVICES LTD.
CROYDON—01-686 0505

Overseas Agents in Arabian Gulf, Belgium, Ceylon, Denmark, East Africa, Eire, Finland, France, Greece, Holland, Hong Kong, India, Israel, Italy, Kuwait, Federation of Malaysia, Norway, Philippines, Portugal, Singapore, South Africa, Spain, Sweden, Switzerland, Trinidad and Western Germany.

WW—005 FOR FURTHER DETAILS

Here it is!

Our two new ranges of 75 ohm TV distribution cables are now made on an extrusion line unique in Western Europe.

We're one of the most technologically advanced cable manufacturers, using new techniques to produce TV distribution cables at a consistently high standard to tolerances much closer than previously possible. At very competitive prices.

The two ranges:

Aeraxial Semi Air Spaced Polyethylene dielectric copper taped braided and polythene sheathed television distribution cables. Five cables in the range, with inner conductor sizes from 1.27 mm to 3.05 mm.

Solid Polyethylene dielectric copper taped and polyethylene sheathed television distribution cables. Five cables in the range, with inner conductor sizes from 0.73 mm to 3.65 mm.



Aerialite will specially manufacture TV distribution cables for any special TV application—also, you can make use of the Aerialite free technical advisory service to help you in the selection and application of distribution cables.

For further information, send for Aerialite's new publication giving full technical specifications of the latest range of TV Distribution Cables.

Aerialite

Aerialite Cables Limited,
Castle Works,
Stalybridge, Cheshire SK15 2BS.
Telephone: 061-338 2223
Cables: Aercables, Stalybridge.
Telex: 669902

To Aerialite Cables Limited:
Please send me your brochure
entitled Aerialite Television Distribution Cables.

NAME _____

POSITION _____

COMPANY _____

ADDRESS _____

WW-006 FOR FURTHER DETAILS

SE Universal



- (A) SM 202** From £395.00
150 MHz Ultra High Performance Universal Counter Timer
 Perhaps the most sophisticated counter timer available under £1000 - and it costs much less than half that! Full eight decade, 150 MHz, three channel spec. with almost every possible plus feature.

- (B) SM 190** From £195.00
Variable Time Base (Computing) Counter Timer.
 For the industrial user. Five or optionally six decade display, two channels. Total variable time base range $1\mu\text{s}$ to 10 secs. Frequency, count (totalize) time interval & ratio modes. Stored or non-stored display. Ultra low cost.



- (D) SM 201** From £265.00
100 MHz Universal Counter Timer
 Best value general purpose unit of 6 decade 100MHz, capability. Three channel input with seven operational modes. Standard or high stability versions.



- (C) SM 200** From £175.00
25 MHz Counter Timer
 Six decade, frequency, count, Period, time and ratio meter having 25 MHz bandwidth and two-line stop start at very low cost.

- (E) SM 209** From £495.00
500 MHz DIRECT Frequency Meter.
 Nine full decade display. Input circuit giving 1 Hz resolution right up to 500 MHz. Optional I.F. subtraction circuit. Ultra fast warm up very high stability oscillator. 10mV sensitivity. All at a fraction of the price you would expect.

Counter Timers



(D)



(F)



(E)

(F) SM 205 From £295.00
Automatic Universal Counter
Timer (70 MHz)

The Automatic one. Completely auto-ranging in all frequency & time modes. 7 decade display with two channel input and 100 nano-second resolution. Remote programming and BCD output as standard. High stability reference.

HIRE OR BUY For a small charge you can hire any of the instruments shown here, singly or as part of a system which we can design for you.
If you decide later to purchase the equipment, we can refund part of the hire fee to you.
You save your capital and space. You beat obsolescence.
Why not ring our Hire Department for details?
Included in the range are Transducers, Recorders, Oscilloscopes, Digital Voltmeters, Dynamic Analyses, Data Systems, Magnetic Recorders.

EMI Labs (EMI) Ltd.,

North Feltham Trading Estate, Feltham, Middlesex. Telephone: 01-890-1166 Telex: 23995
Northern Sales Office, Bessell Lane, Stapleford, Nottingham. Telephone: Sandiacre 3255



EMI A member of the EMI Group of Companies
International leaders in Electronics, Records and Entertainment

WW-007 FOR FURTHER DETAILS


BIG NEWS FROM BARR & STROUD

Modular Filtering


ONE MAIN FRAME—MANY OPTIONS

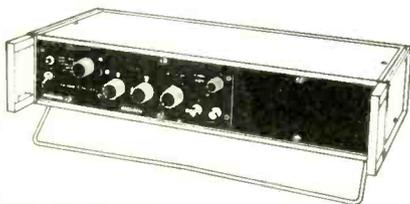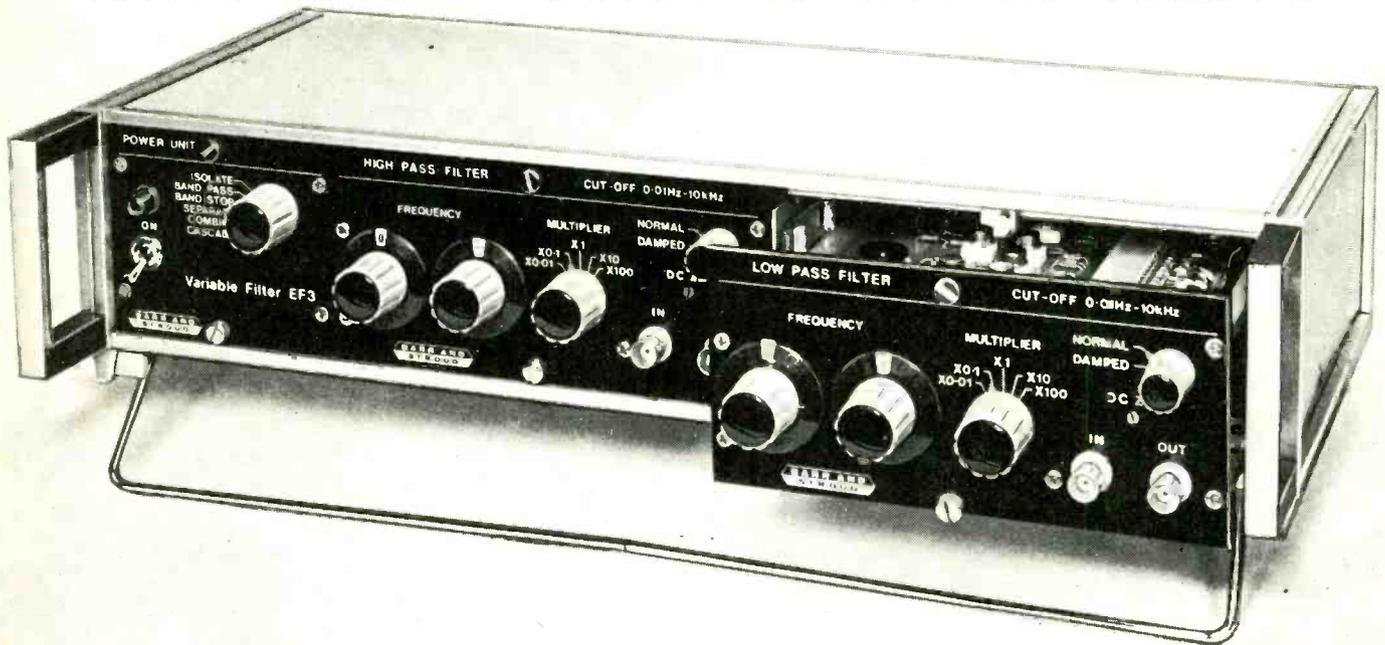


High Pass

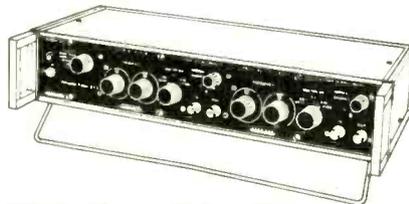


High Pass/Low Pass

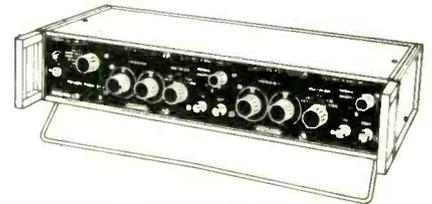

High Pass/High Pass

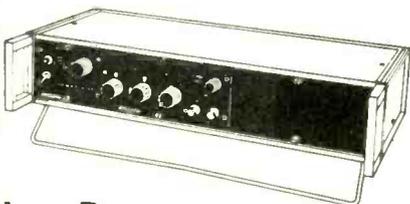

Low Pass

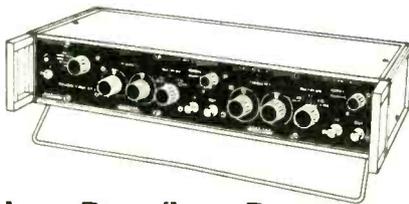

Low Pass/Low Pass

and that's only the start!

Barr & Stroud's new EF3 Electronic Filter System means no more compromises when you buy variable filters. Now you can get the filter you need today, and additional plug-in units tomorrow. Today — the basic main frame and your choice of two modules to operate in low-pass, high-pass, band-pass, band-stop, band-separate, band-combine or cascade modes. Tomorrow — other interchangeable modules to meet your newest requirements. The first two modules,

already available, provide filtering with variable cut-offs between 0.01Hz and 10.0kHz, stop-band attenuation of 48dB/oct. (96dB/oct. in cascade), and pass-band response from dc to 500kHz. Get full details of EF3, the big breakthrough in electronic filtering by using the reply card.

BARR & STROUD LIMITED
 London Office: 1 Pall Mall East, London SW1Y 5AU
 Telephone: 01-930 1541 Telex: 261877




Glasgow and London

WW—008 FOR FURTHER DETAILS

ANDERS MEANS METERS...


OXFORD LONG SCALE 250°

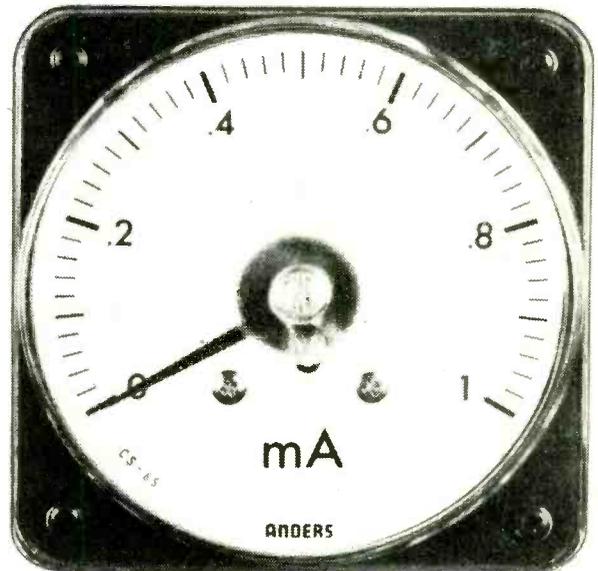- Now available, long scale meter to satisfy budgetary requirements for low cost equipment.
- Models CS65 and CS85 with scale lengths of 6" and 7.75"
- OEM quantity prices extremely competitive
- 500µA upwards, DC or AC rectified
- Shadow-free dial—easy to read scale



Anders provide what is probably the largest range of meters available from a single source in Europe: MC/MI, dynamometer, vibrating reed, electrostatic, etc. in over 100 case styles and sizes, a few of which are shown below.

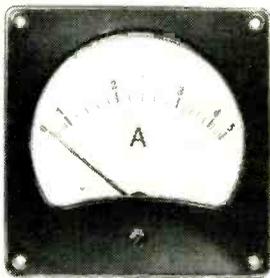Popular models and ranges are stocked in depth while a specially equipped instrument department enables swift production of non-standard ranges and scales, to suit individual customer requirements, in large or small quantities.




Vulcan Moving Iron. 4 models, 1.5", 1.8", 2.7", 3.7" scales. Voltmeters, ammeters and motor starting meters.




Profile 350 edgewise 4.3" scale. DC moving coil and AC moving coil rectified. Horizontal or vertical mounting.



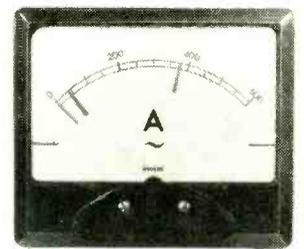
Crescent Long Scale 180°. 3 models, 4", 5", 6.25" scales. DC moving coil and AC moving coil rectified. Clear plastic.



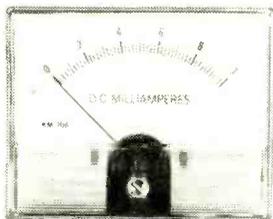Soliconcontroller Moving Coil Relay. DC moving coil and AC moving coil rectified. 1 or 2 adjustable alarm controls.



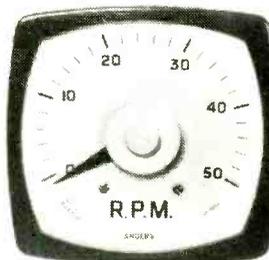Kestrel Clear Front. 7 models, 1.3"—5.25" scales. DC moving coil, AC moving coil rectified, AC moving iron.



Stafford Long Scale 240° 6 models, 3.5"—11.5" scales. DC moving coil, AC moving coil rectified, AC moving iron. Also 98° scale.




Lancaster Long Scale 240°. 2 models, 4", 5.5" scales. DC moving coil and AC moving coil rectified.

ANDERS ELECTRONICS LIMITED 48/56 Bayham Place, Bayham Street, London, N.W.1. Telephone 01-387 9092.

Manufacturers and distributors of Electrical Measuring Instruments. Sole U.K. distributors of FRAHM Resonant Reed Frequency Meters and Tachometers. Manufacturers of purpose built electrical and electronic equipment to customers' requirements.

WW—009 FOR FURTHER DETAILS

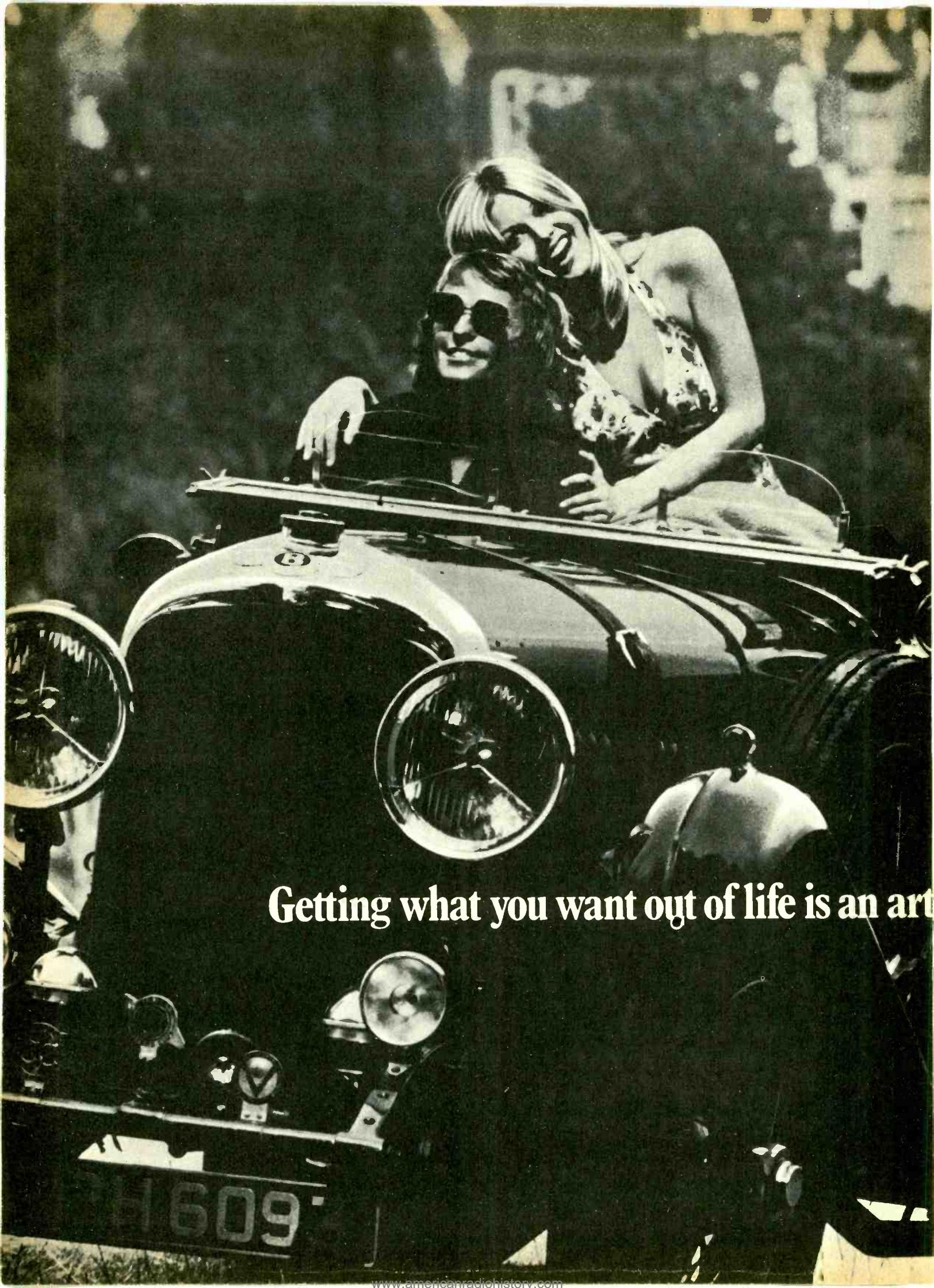


Getting what you want out of life is an art

Strictly for the enthusiast.
Something to get really enthusiastic about.
Garrard have some really good things to
show you here.

And, as you might expect, something
designed to help you get more lifelike sound
reproduction – to make life richer for you.

It's time to take a fresh look at Garrard's
hi-fi deck range. You'll discover these two
superb units offering highly refined
engineering, excellent value, plus important
features including new belt drive.

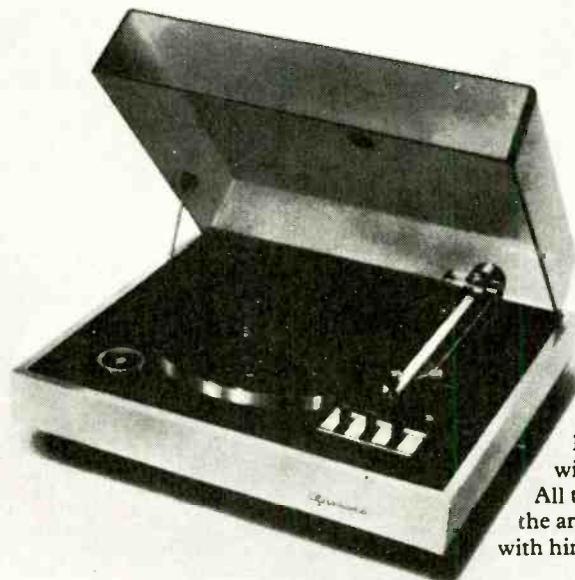Go to your hi-fi dealer and discover
how you can get more out of life.



Zero 100 SB Module

Automatic single player. One of the
world's most sophisticated transcription
turntables, with unique tangential
tracking arm; pivoting head reduces
tracking error and consequent harmonic
distortion. New belt drive system. Record
counter monitors stylus wear. Magnetic
bias compensation. Fingerlight tab controls.
12in, 10in and 7in discs can all be played
with automatic set down of pick-up arm.
All the best features in the present state of
the art. Low resonance aluminium-clad base
with hinged/lift off cover.

and Garrard know a great deal about it.



AP 86 SB Module


Automatic single player. Performance
sets a new standard in medium-priced
hi-fi, a heavy, machined diecast platter,
screened 4-pole synchronous motor,
and new belt drive, together give
highest standards in maintaining
constant speed. Wow and flutter
typically 0.12% peak, rumble typically
– 63 dB (DIN). Bias compensator
adjustable to match stylus force –
separate scales for elliptical and conical
styli. Fingerlight tab controls. Low
resonance wood grain finish base with
hinged/lift off cover.

Garrard

A PLESSEY QUALITY PRODUCT

Garrard, Newcastle Street, Swindon, Wiltshire England SW1 1DA.

WW-010 FOR FURTHER DETAILS

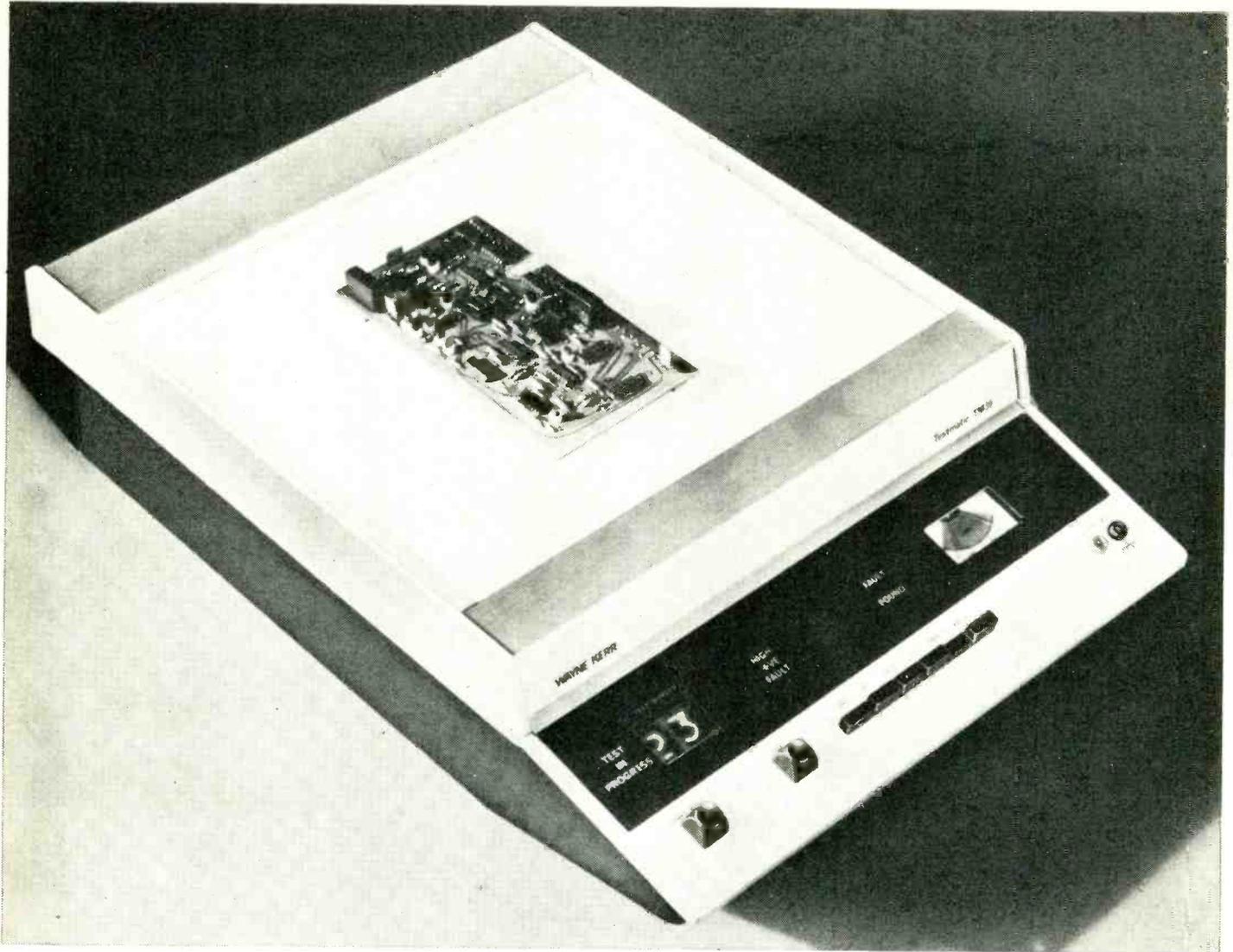

Wayne Kerr TM30:

the high-speed circuit tester that saves you high-cost time

The Testmatic TM 30 is, above all things, simple. It has been developed for efficient circuit-board testing, in the light of operational experience with the TM 60. It is designed to be worked by people who—whatever other talents they may have—need not be qualified electronics engineers. In saving time it thereby saves you money.

It will tell the operator where there is a defective circuit point, as well as indicating whether the value is high or low. And it can handle 30 tests—in seconds.

WAYNE KERR
a member of the Wilmot Breedon group

For more information phone Bognor Regis (02433) 25811, or fill in the coupon.

Please send details of the TM 30.

For the attention of Mr. _____

Company name _____

and address _____

Post to Wayne Kerr, Durban Road,
Bognor Regis, Sussex PO22 9RL.

WW-OCT



WW—011 FOR FURTHER DETAILS

FREE

HEATHKIT Catalogue



Ask
about our
low-deposit
terms

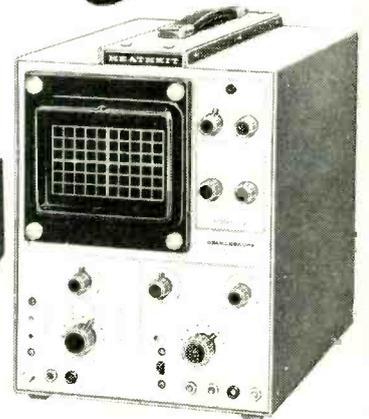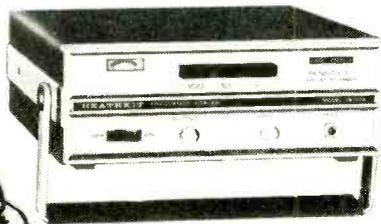

The FREE Heathkit Instrumentation Catalogue describes the latest Heathkit solid-state oscilloscopes, 120 MHz frequency counter with 8 digit readout, 3½ digit multimeter for measuring AC and DC voltage, current and resistance with automatic switching for DC polarity, Portable FET VOM with 53 ranges on 4 scales, FET/transistor tester, plus many, many more Heathkit test instruments — all designed for easy assembly and kit-form savings. Send today for your FREE Heathkit catalogue, the world's largest selection of electronic kits — test, marine, amateur radio, b/w television, stereo hi-fi, automotive, home appliances, educational and more.

sistor tester, plus many, many more Heathkit test instruments — all designed for easy assembly and kit-form savings. Send today for your FREE Heathkit catalogue, the world's largest selection of electronic kits — test, marine, amateur radio, b/w television, stereo hi-fi, automotive, home appliances, educational and more.

FREE Heathkit Catalogue

offers something for everyone.
Send for your copy today.

VISIT THE HEATHKIT CENTRES

LONDON

233 Tottenham Court Road.

GLOUCESTER (Factory & Showroom)
Bristol Road, Gloucester.



Please send me the FREE Heathkit catalogue


Name _____

Address _____

Heath (Gloucester) Limited
Department WW/10/73
Gloucester GL2 6EE
Telephone 0452 29451

HEATH
Schlumberger

WW—012 FOR FURTHER DETAILS

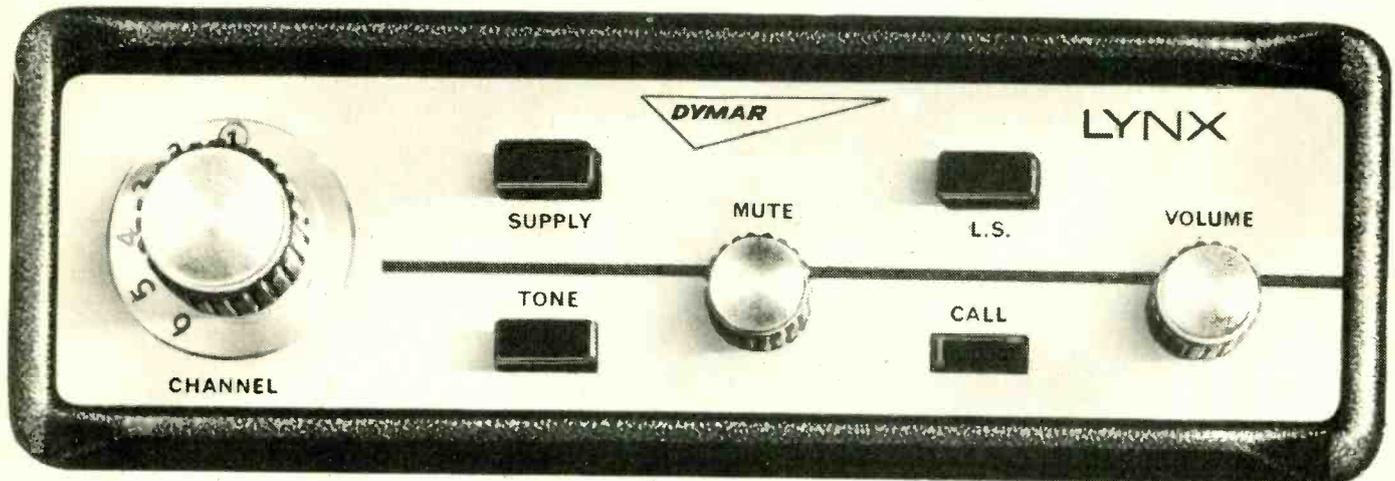

ACTUAL SIZE

The Dymar Lynx. A mobile radiotelephone system so special we put our own name on it.

This Lynx has a pedigree. Since 1964 Dymar has designed and built VHF radiotelephones which have borne some of the most famous names in the industry.

Now we have something special. A complete VHF AM and FM mobile radiotelephone system. It cost £100,000 to develop. It's different. It's our own. The name is Dymar. The brand is Lynx.

Lynx mobiles come as local control units. The entire circuitry, space for options and a 5in elliptical speaker in a single 26.4in³ package. Or as extended control types, when the panel unit demands only 6.75 x 3.5 x 2.3in of dash space and the transmitter/receiver vanishes into the boot or under a seat.

Selective calling, if specified, is one of the options that gets built-in.

AM sets - 15/20W RF output standard - are Low, Home Office, Air, Mid or High band. FM cover Low, Home Office or High at a standard 20/25W. One, six or 10 channel versions are available, with 12.5 kHz or 25kHz channel spacing.

Before specifying a VHF mobile, check on the rest of the spec. The tough diecast aluminium construction; the clever use of ICs and FETs; the modular approach to sub-assemblies and the accessibility of components; the safety padding; the lot.

It's all in the leaflet Lynx Mobile Communication, and in a series of Data Sheets. Use the Reader Enquiry Service today, or write direct to Dymar.



DYMAR

the name in radiotelephones

DYMAR ELECTRONICS LIMITED,
Colonial Way, Radlett Road, Watford,
Herts. WD2 4LA. Tel: Watford 37321
Telex: 923035. Cables: Dymar Watford.



Minimod

Made in Britain by Gardners...

First of a new range of all-British miniature encapsulated power supplies, the Minimod series is designed and manufactured by Gardners to provide reliable, regulated power supplies in a neat pack designed to plug into your P.C. board. Minimod simplifies development or production of equipment by providing power where you need it.

Minimod provides a choice of a standard 5 volt output (available up to 1 Amp) for digital circuits or 12-0-12 or 15-0-15 volts for linear circuits, using a 230 volt input. Each unit is fully stabilised with fold back current limiting, and in the case of 5 volt units, over voltage crowbar is provided . . .

Ask Gardners to tell you more about Minimod.
Standard or special models can be supplied.

Gardners

Specialists in Electronic Transformers and Power Supplies

GARDNERS

TRANSFORMERS LIMITED

Gardners Transformers Limited, Christchurch, Hampshire BH23 3PN
Telephone 02-015 2284 Telex 41276 Gardners XCH

WW-614 FOR FURTHER DETAILS

audix

SOUND SYSTEMS AND ELECTRONICS


TALK *of* THE TOWN

insists on quality from stars and equipment

Audix know-how and wide range of standard equipment, including consoles, modules, amplifiers and loudspeaker systems combine to create a highly-commerced sound reinforcement system for London's famous theatre-restaurant.

Why not contact Audix before ordering your new sound system.

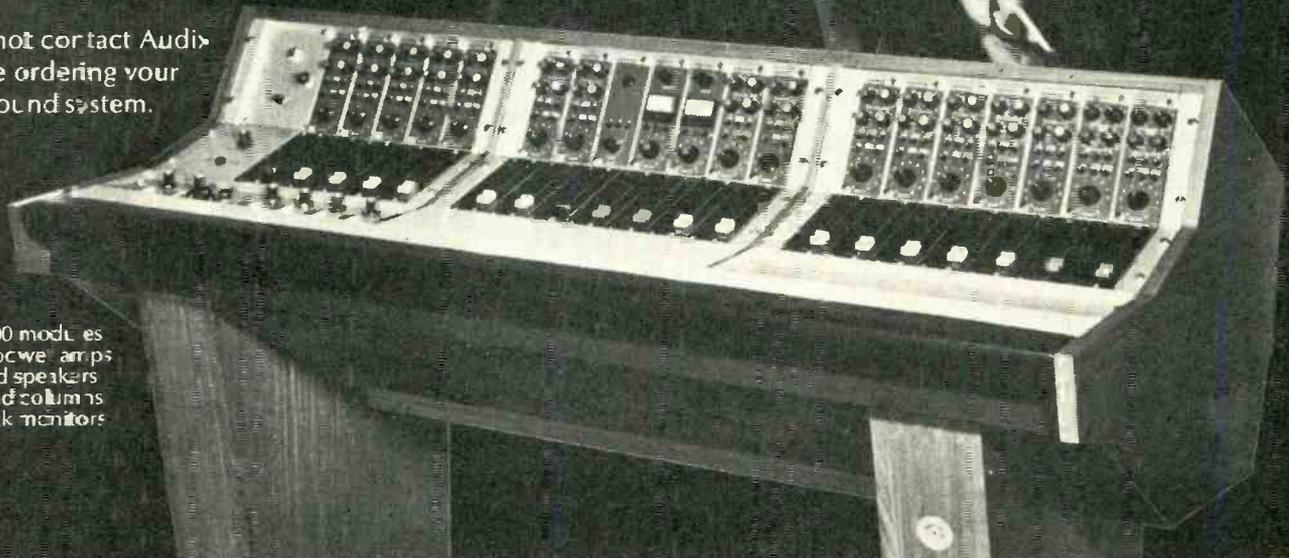MXT-800 modules
PA200 power amps
cardioid speakers
16' sound columns
foldback monitors





audix

MANUFACTURERS OF
SOUND SYSTEMS AND
ELECTRONICS

AUDIX LIMITED · STANSTED · ESSEX CM24 8HS
TELEPHONE: BISHOP'S STORTFORD 813132
(4 Lines) (STD 0279)

WW-015 FOR FURTHER DETAILS

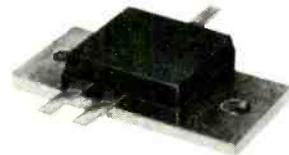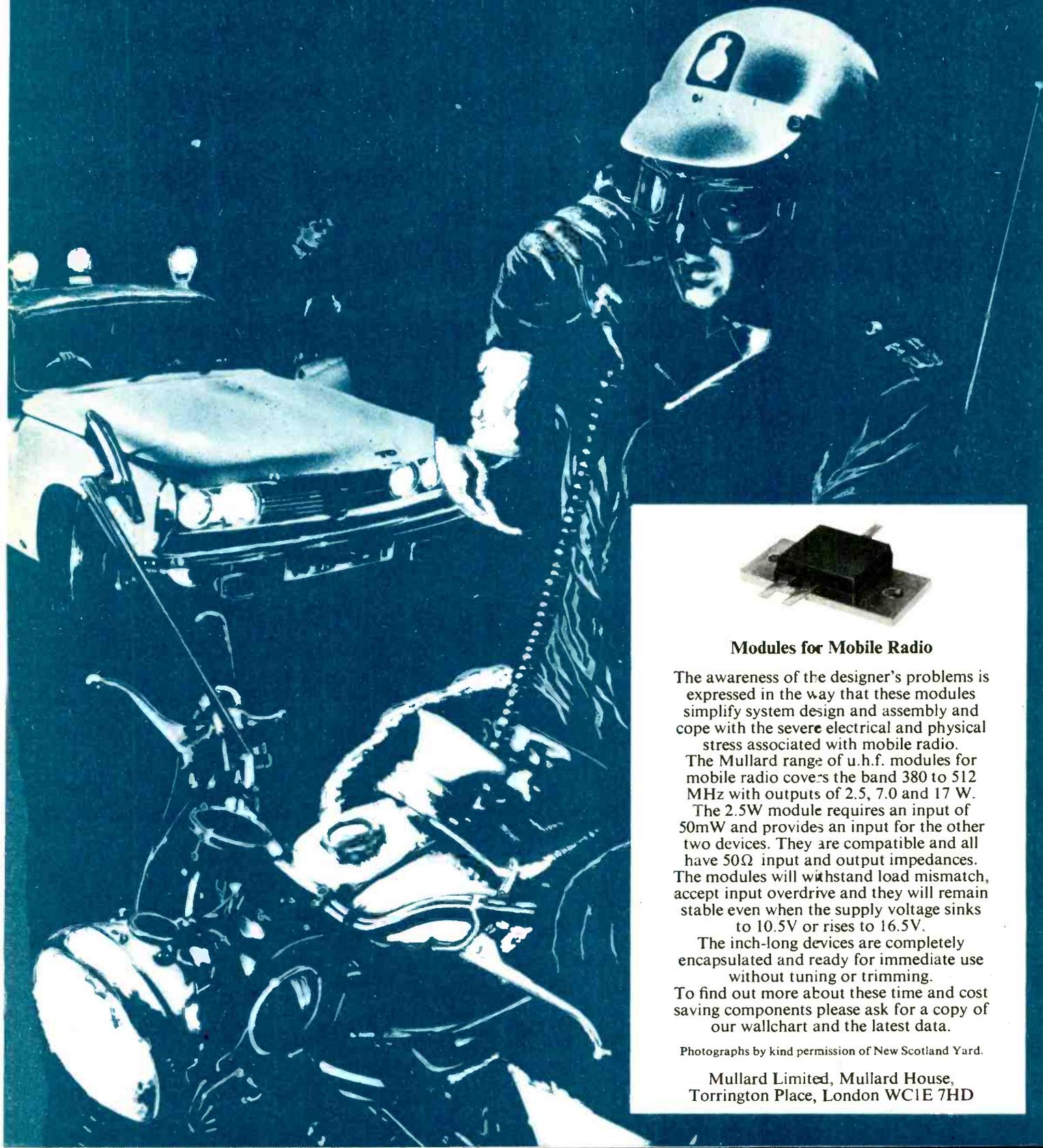Mullard r.f. power modules are the products of a real awareness of the designer's problems and a leading position as manufacturers of semiconductors and hybrid circuits. We have been working with the major manufacturers of mobile radio since its infancy.



Modules for Mobile Radio

The awareness of the designer's problems is expressed in the way that these modules simplify system design and assembly and cope with the severe electrical and physical stress associated with mobile radio.

The Mullard range of u.h.f. modules for mobile radio covers the band 380 to 512 MHz with outputs of 2.5, 7.0 and 17 W.

The 2.5W module requires an input of 50mW and provides an input for the other two devices. They are compatible and all have 50 Ω input and output impedances. The modules will withstand load mismatch, accept input overdrive and they will remain stable even when the supply voltage sinks to 10.5V or rises to 16.5V.

The inch-long devices are completely encapsulated and ready for immediate use without tuning or trimming.

To find out more about these time and cost saving components please ask for a copy of our wallchart and the latest data.

Photographs by kind permission of New Scotland Yard.


Mullard Limited, Mullard House,
Torrington Place, London WC1E 7HD

Mullard components for communications



BROADCASTING · TELECOMMUNICATIONS · RADAR · NAVAIDS · MILITARY

Audio Test Set RTS 2

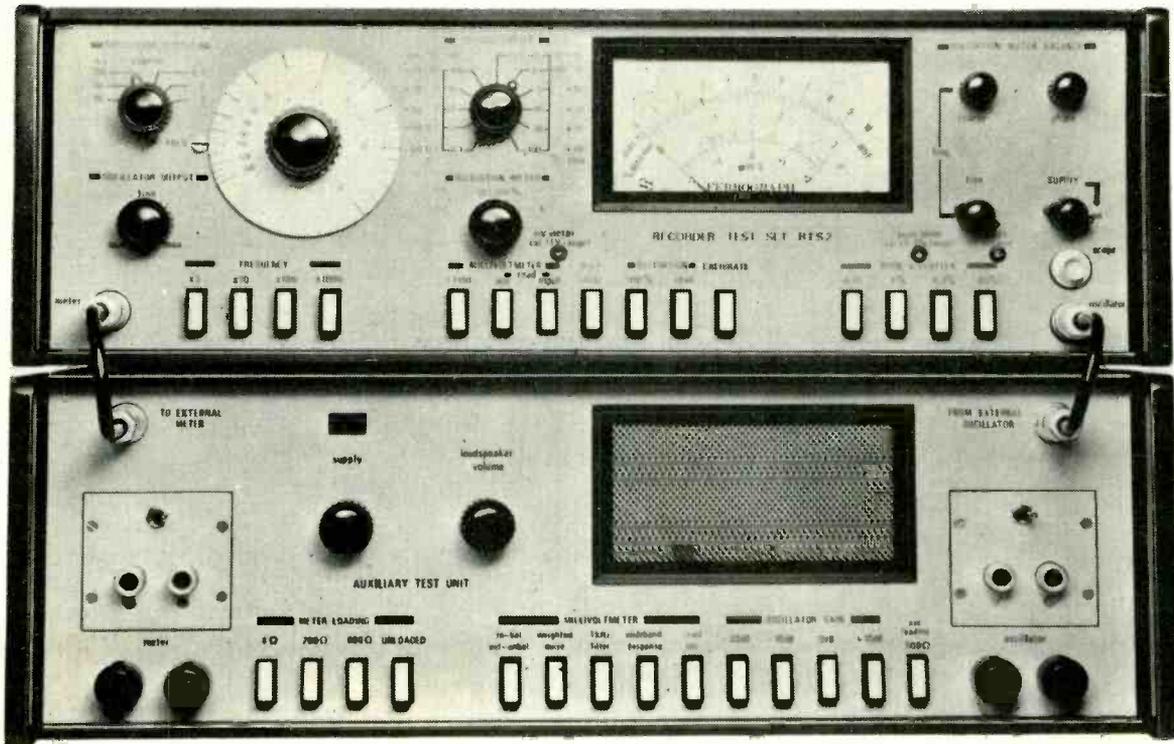

and Auxiliary Test Unit ATU1 for professional users

RTS2 Checks Amplifiers,
mixers, tape-recorders

For Frequency Response ·
Signal/noise ratio ·
Distortion · Cross-talk ·
Wow & flutter · Drift ·
Erasure · Sensitivity ·
Output power · Gain

ATU1 Extends output level and
measurement sensitivity.
Provides balanced
input/output facilities.
Incorporates weighting
filters, loading circuits.
Has built-in speaker
for monitoring purposes.

Send for leaflets RTS2 & ATU1

FERROGRAPH


A member of the Wilmot Breeden group

Ferrograph Company Limited Auriema House 442 Bath Road Cippenham Slough Buckinghamshire SL1 6BB Tel: Burnham (062 86) 62511 Telex: 847297

WW—017 FOR FURTHER DETAILS

TONE Operated SWITCHING


in Monolithic Form

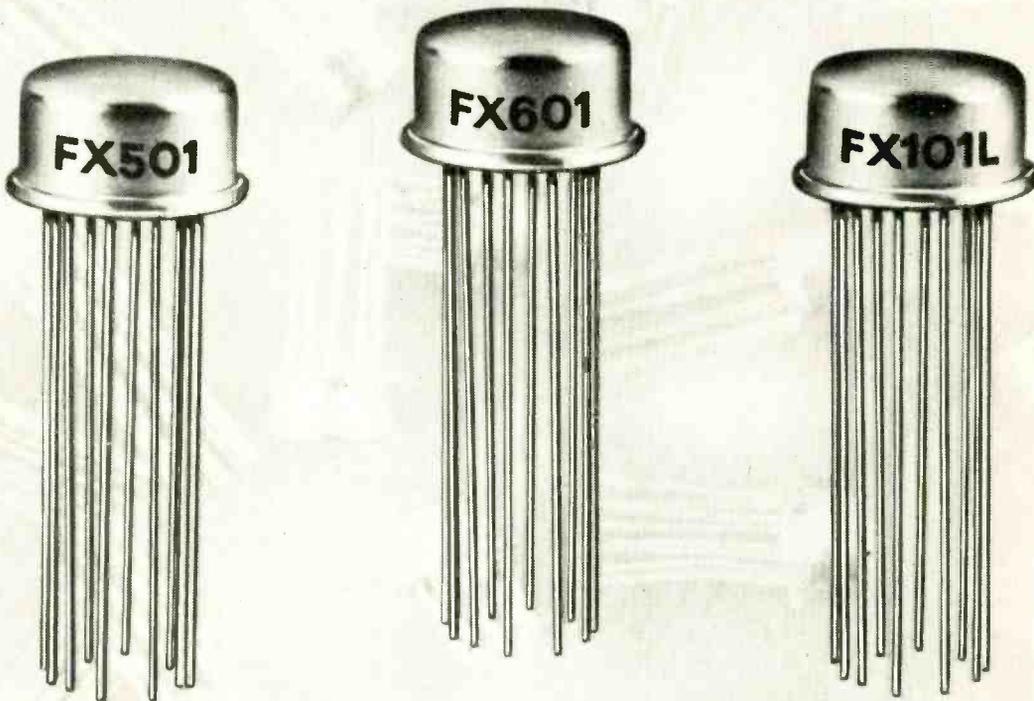


The FX-101L, FX-501 and FX-601 series of tone operated switches are designed for use as tone receivers in Remote Control, Alarm, Automation, Communications and Telemetry systems. Each device incorporates a semiconductor switch which operates when a specific input tone frequency is received. A choice of Direct Acting, Bistable or Monostable switching functions are available according to the device type. All frequency discrimination and timing

circuits are included on-chip and require only the addition of simple external RC networks. Tone operating frequencies are adjustable between 10Hz and 20kHz and the devices incorporate input signal amplifiers for operation with low-level sine/square wave input signals. Rated for operation over the temperature range -30°C to $+85^{\circ}\text{C}$, the devices require only a single low current 8V/15V d.c. supply.

All three devices available from stock.

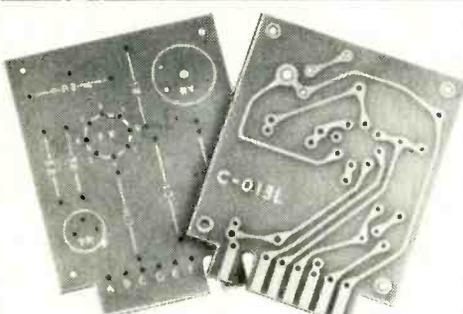

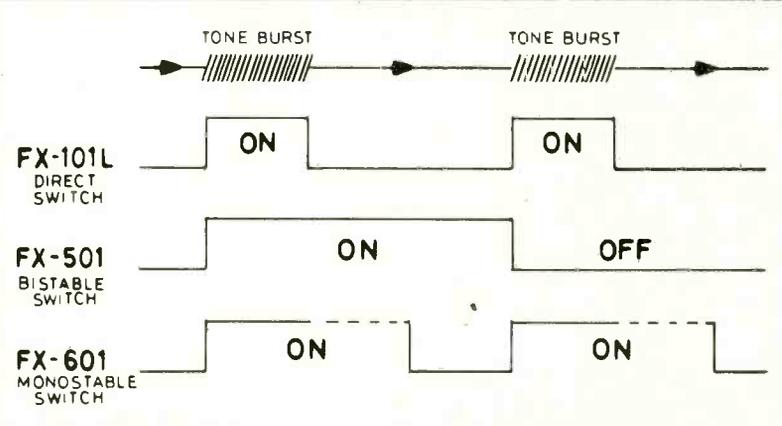
To make your experimental breadboarding easy, two P.C.B.'s are available - C-013L (for FX-101L) and C-015 (for FX-501 and FX-601). They are supplied ready drilled and with the positions of all external components screen printed. Components not included.



The diagram shows two 'TONE BURST' signals at the top. Below them are three waveforms:

- FX-101L DIRECT SWITCH:** The output is 'ON' during each tone burst and returns to 'OFF' immediately after the burst ends.
- FX-501 BISTABLE SWITCH:** The output is 'ON' during the first tone burst and remains 'ON' until the second tone burst occurs, at which point it switches to 'OFF'.
- FX-601 MONOSTABLE SWITCH:** The output is 'ON' during the first tone burst and remains 'ON' for a fixed duration (indicated by a dashed line) after the burst ends, before returning to 'OFF'.

Frequency is our business

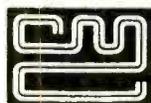

CONSUMER MICROCIRCUITS LTD.

Rickstones Road, Witham, Essex
Telephone Witham 3833 Telex 99382 (Reaction)

Send for fully detailed Data Sheets and information by circling the reader reply card number.

WW-018 FOR FURTHER DETAILS

KEF UNITS


 KEF ELECTRONICS LIMITED
 TOVIL MAIDSTONE ME15 6QP
 Tel 0622 57258
 Reg in England No 702392

Research based on the premise that loudspeakers could be made to reproduce sound more accurately by the efficient utilisation of plastics and metal alloys has enabled KEF engineers to evolve the current range of chassis speakers.

Results of research on these materials plus spin-off from other technologies has enabled KEF to achieve precise quality control in production, reliability and accurate sound reproduction under wide extremes of operating conditions.

Many of the world's leading manufacturers recognise these salient points and insist on using KEF drive units in their equipment.

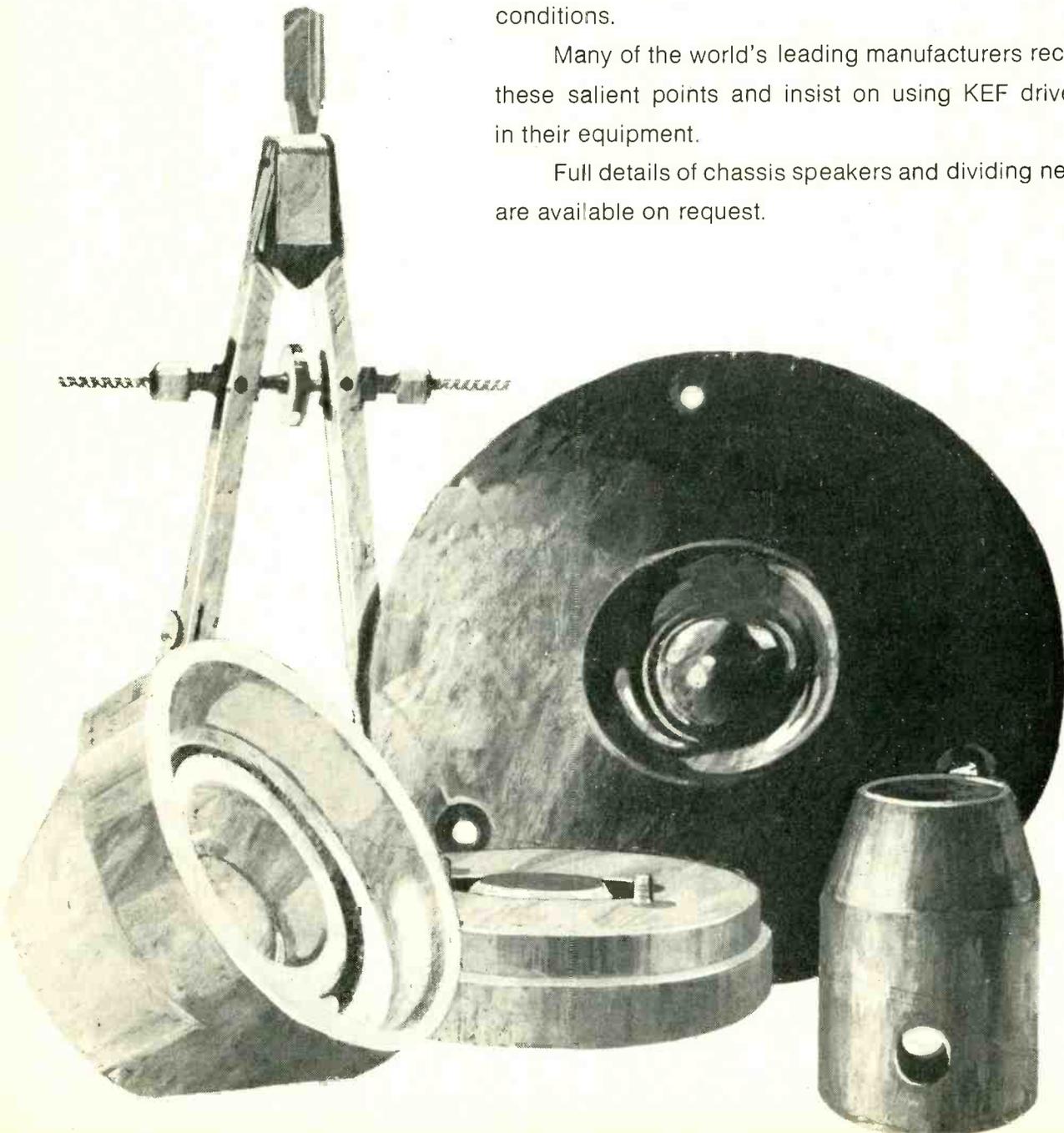Full details of chassis speakers and dividing networks are available on request.



WW—019 FOR FURTHER DETAILS

Westinghouse TV colour tubes guarantee purity in both colour and black & white

Today's Westinghouse Electric colour tubes, in addition to offering recognised excellence of colour definition, have white field purity...vitaly important to reception of black and white transmission.

Two 67 cm diagonal versions

These improved Westinghouse tubes are made available in two configurations – the standard 90° and the 10 cm shorter profile wide-neck 110° version... permitting their compatibility to the needs of the larger portion of European TV set manufacturers.

Expanded European facilities

Pacing the growing demand in Europe for Westinghouse tubes, we have made a permanent commitment to fully support our customer. ■ With trained technical sales personnel in major European cities. ■ With

warehousing and testing facilities in Kassel, W. Germany and Le Mans, France. ■ With a sustaining European oriented R&D programme.

Customer oriented

In these ways-compatible product availability-outstanding development facilities-local technical assistance...Westinghouse Electric respond to dynamic customer requirements – here in Europe and throughout the world.

Westinghouse Electric S.A.
1 Curfew Yard, Thames Street
Windsor Berks. Phone Windsor
63392. Telex 847069.

GENEVA FRANKFURT LONDON
MILAN PARIS STOCKHOLM



The 110°  A67-140X TV colour tube is 10 cm shorter in profile than the 90°  A67-120X... both offer superb colour definition as well as white field purity for black & white.



Westinghouse Electric

WW—020 FOR FURTHER DETAILS

SME

The best pick-up arm in the world


Whichever way you look at it

Write to SME Limited · Steyning · Sussex · England
Telephone: Steyning (0903) 814321

LTD/520

WW—021 FOR FURTHER DETAILS

www.americanradiohistory.com

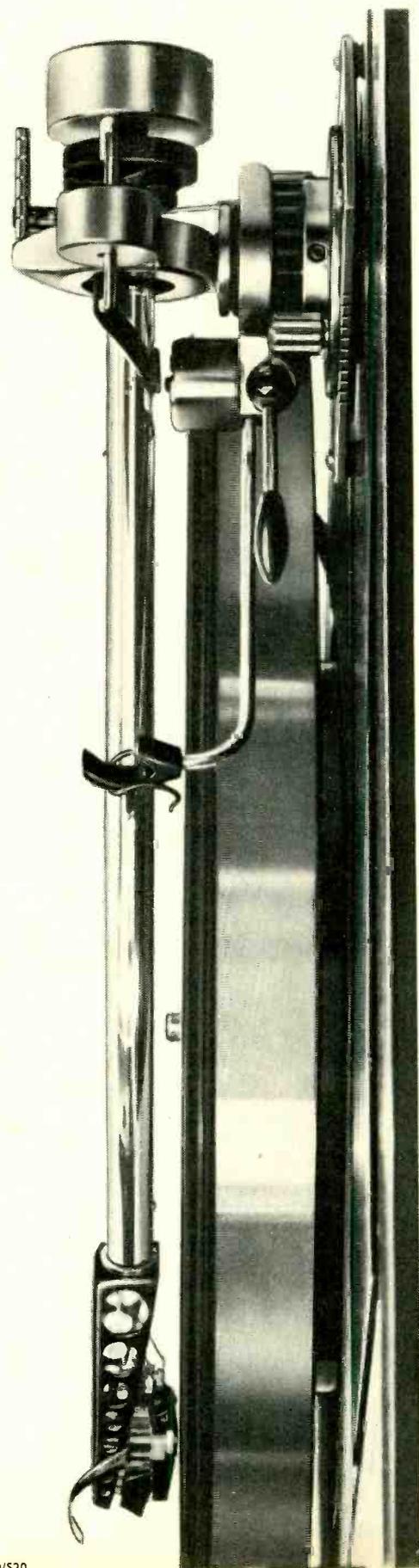

new! **ADCOLA R500**


ELECTRIC DE-SOLDERING INSTRUMENT



Removes unwanted solder!

- R500** is PURPOSE DESIGNED NOT AN ADAPTION TO A SOLDERING IRON
- NO AIR OR VACUUM LINES
- ONE HAND OPERATION
- ROBUST CONSTRUCTION
- EASY TO USE
- OVERALL DESIGN GIVES CLEAR VISION OF WORK PIECE
- WELL BALANCED
- TROUBLE FREE
- ALL VOLTAGES AVAILABLE

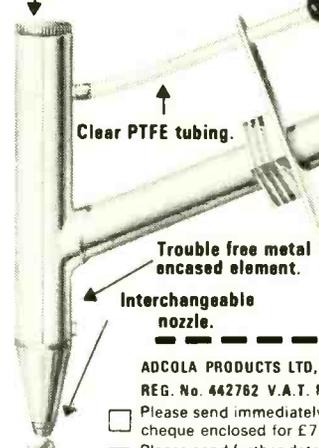Removable plug for holder cleaning (when cold).



Cool strong handle glass filled nylon.

"A" frame support for idling position.

Trouble free metal encased element.

Interchangeable nozzle.

ADCOLA PRODUCTS LTD, ADCOLA HDUSE, DEPT. WW7, GAUDEN RD, CLAPHAM SW4 6LH. REG. No. 442762 V.A.T. No. 235-6153-72

- Please send immediately an R500 De Soldering Instrument cheque enclosed for £7.35 plus 10% V.A.T. (postage paid U.K. only)
- Please send further details. (Tick appropriate box)

NAME

ADDRESS



Post now to **ADCOLA**

WW-022 FOR FURTHER DETAILS

Telford Oscilloscope cameras

Type A modular system with widest range of film backs, lenses, viewing systems and adaptors to meet virtually all requirements.

Plus inexpensive Type P (prices from £50) utilising coaterless Polaroid® film and Type C with economical 35mm film for continuous feed.



® Reg. Trade Mark.


More complete details available on request from:

Telford PRODUCTS LTD.

WADSWORTH ROAD PERIVALE GREENFORD MIDDX. ENGLAND. Telephone: 01-998 1011 Telex: 935524 **DAVALL** A MEMBER COMPANY OF BENTIMA INDUSTRIES LIMITED

WW-023 FOR FURTHER DETAILS


Linstead Laboratory Instruments

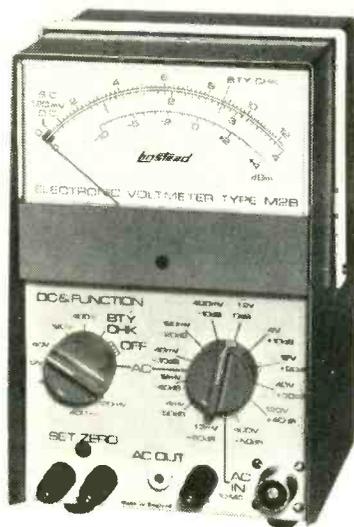

M2B

WIDE RANGE MILLIVOLTMETER
High impedance millivoltmeter with 20 scales total measurement range 60 micro-amp a.c. to 400 volts d.c. 10 megohm input with overload protection and frequency range of 500 kHz.

£35.00

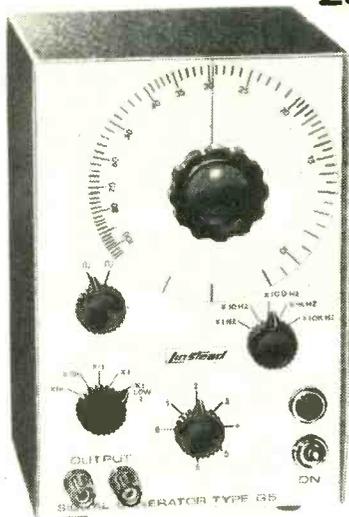

G5

WIDE BAND SIGNAL GENERATOR
Sine-square wave wide band high power signal generator. 10 Hz—1 MHz. 0—6 volts r.m.s., 2 watts into 5 ohms incorporating short circuit protection.

£32.00


Linstead
means a good deal
in electronics

Linstead Electronics, Roslyn Works, Roslyn Road,
London N15 5JB. Telephone: 01-802 5144

WW—024 FOR FURTHER DETAILS


AMTRON kits for the Audio Enthusiast

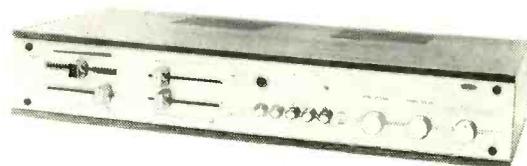These kits have been selected from AMTRON's vast range of electronic kits. Each unit comes with all components, instructions, and solder.



UK187 HI-FI QUADRIC STEREO AMPLIFIER 20+20W.

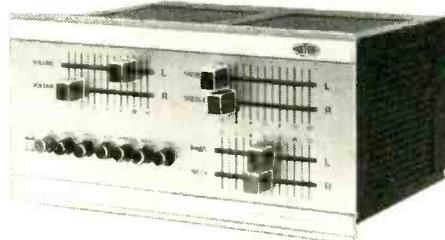The UK187 Hi-Fi Amplifier has an output of 20W per channel plus a 'quadric' section feeding two groups of speakers, front and rear.



UK175 STEREO PREAMPLIFIER WITH TONE CONTROLS

The UK175 has been specially developed to be used with UK192 50W per channel stereo amplifier.




THREE-WAY CROSS OVER FILTER 12db/OCTAVE

The UK800 three-way cross-over filter with a 12db/Octave roll off is a true separation for bass speaker, mid range and tweeter units

THE BIG NAME IN ELECTRONIC KITS



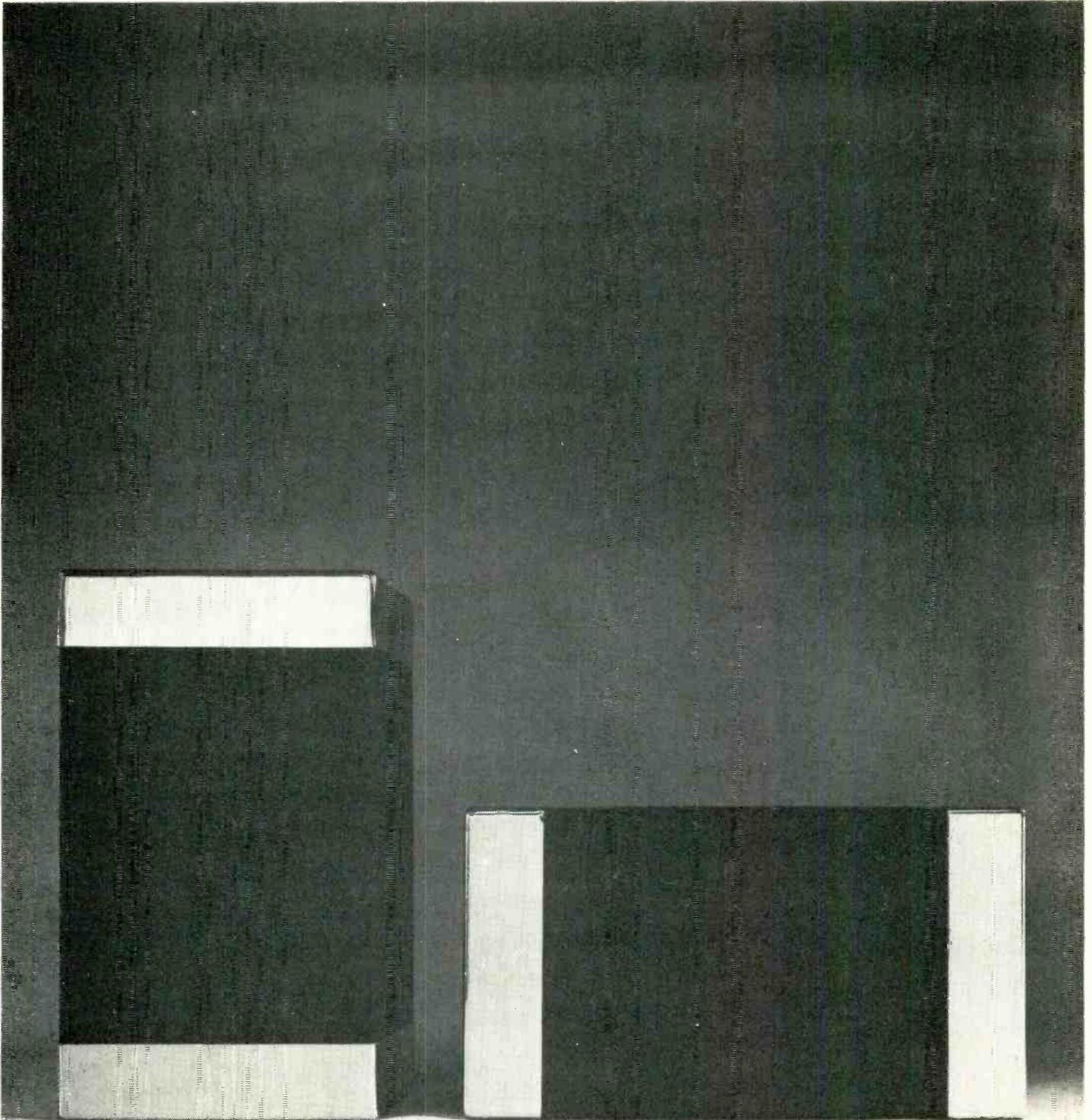4 & 7 CASTLE STREET, HASTINGS, SUSSEX TN34 3DY
TEL: HASTINGS 2875



The Ultimate Draws a Little Closer

How can the qualities of the new Gale GS401A be conveyed? Not in words, certainly. To assess this new speaker, there's nothing for it but to go along to a dealer. He will tell you first that the GS401A carries a seven year guarantee. Then, when you've admired the handsome exterior created by Jon Bannenberg in matt black and chrome, we suggest you use some test equipment. All you have to do is take a good pair of ears. This delicate apparatus will tell you that, for a speaker only 23¼ x 13 x 10½ inches, the GS401A combines an unusually high power handling with breathtaking clarity.

You will also need a favourite record. Preferably the one you use to impress your friends with the quality of your existing equipment. The one with prominent percussion and a wide dynamic range. We have only one serious anxiety. With the GS401A being the breakthrough it is, we worry that you simply won't believe the evidence of your ears. At the time of going to press, the Gale GS401A can be seen at the following franchised dealers only.

Audio T 190 West End Lane London NW6
 Design Audio 36 Marylebone High Street London W1
 Grahams 86-88 Pentonville Road London N1
 Hampstead High Fidelity 91 Heath Street London NW3
 Thomas Heinitz 35 Moscow Road London W2
 Henry's Radio 354-356 Edgware Road London W2
 R.E.W. Audio Visual Co 146 Charing Cross Road London WC2
 R.E.W. Audio Visual Co 266-268 Upper Tooting Road SW17
 Studio 99 81 Fairfax Road London NW6
 Audio T - Cambridge 172-174 Mill Road Cambridge

If the nearest of these is out of reach, write for literature to:
 Gale Electronics & Design Limited
 39 Upper Brook Street London W1Y 1PE

At Blackburn



Components for
the finest colour
tv sets in the
world.



We grew up with the TV industry. So we're pretty good at meeting its requirements.

Mullard Blackburn have been anticipating and meeting the demand for TV components for many years. Their capacity has grown with the industry. Valves, capacitors, delay lines; by the million. Each and every one to the stringent specifications laid down for Mullard quality components. Even today TV first equipment, uses some 9 million valves a year and Mullard Blackburn produce 7 million of

them. Famous valves like the PL504 output pentode and the PCL84 triode-pentode.


And millions of capacitors. Like the flat metallised-film C280; still increasing in popularity because of its excellent CV/volume ratio. (The hundred-millionth metallised film capacitor came off the line last year.) And, at the rate of a million per week, Mullard's efficient small and miniature electrolytic ranges with their many applications.

Blackburn make thousands of delay lines every week (including

the latest and smallest DL50). Increasing automation means that this output is being stepped up considerably . . .

Blackburn's job is to carry on in top gear. Helping the British TV industry to produce the best sets in the world, and to increase the already imposing export performance of Mullard Limited.

Mullard

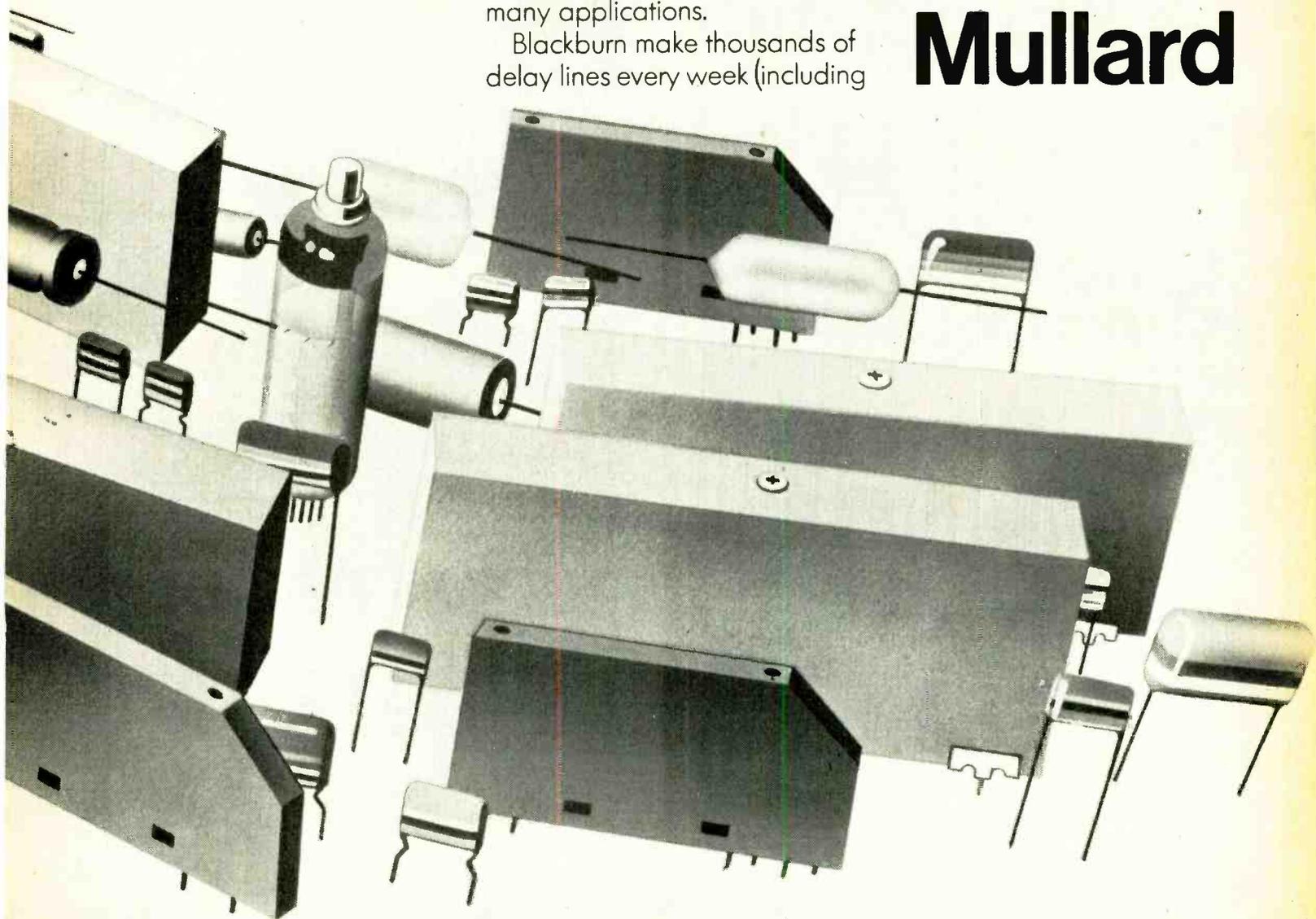


Two big advances in quality COMMERCIAL SOUND SYSTEMS

Welcome the new range of SNS PA Mixer-Amplifiers. New? They're all of that. A new flexibility, new features which incorporate 12W. or 40W. RMS output and the latest integrated circuits used throughout the pre-amplifier stage – in fact a new kind of finesse in medium power Commercial Sound Systems.

Link them to another big new range – SNS column and cabinet speakers. That's a seven league step forward! Put each range together or use them apart. Quality marks them both. Performance singles them out. Where else could they come from but SNS?

Of course, you need a trial to feel as confident about them as we do. Call your SNS representative soon.

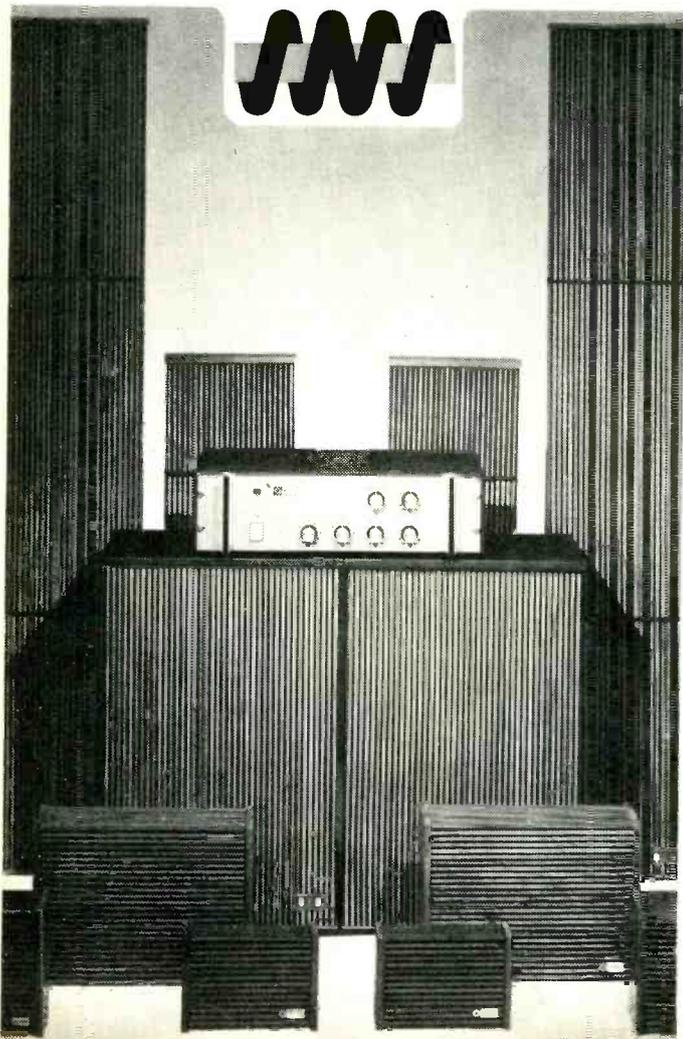SNS Communications Ltd., 851 Ringwood Road,
Bournemouth BH11 8LN. Tel: Northbourne (02016) 5331



WW—027 FOR FURTHER DETAILS



Magnetic shielding

TELCON offers these simple answers

Standard shields


Telcon Metals offer an extensive standard range of high efficiency Mumetal shields, which fit most cathode ray, photo multiplier and radar tubes, together with a selection of boxes and cans for microphones pick-ups, transistors and transformers. These are normally supplied stove enamelled in hammer grey externally and matt black internally. Other finishes can be supplied by arrangement.

Fabricated shields

Telcon Metals offer complete facilities for fabricating special shields in Mumetal and composite shields in Mumetal/Radiometal to customers' individual requirements. All Telcon shields are made to close tolerances and have excellent finish and appearance. For the highest efficiency and extra close fitting tolerances, the 'Telform' technique is recommended. These shields can be produced in complex shapes with a minimum of welded seams and very close uniformity throughout batches. A comprehensive design/advice service is available to assist all customers.

'Telshield' wrap around foil

'Telshield' is an easy to use, ferromagnetic shielding foil, which can be cut with scissors, wound into cylinders, cones, etc., and fixed with adhesive tape, clips or spot welds, to provide a permanent efficient shield. It is economical to use, especially for research, development and short-run applications which do not merit the tooling involved in the production of fully fabricated shields. 'Telshield' is supplied in a standard thickness of 0.05 mm. in widths of 150, 50 and 25 mm in convenient packs costing approximately £5. Other thicknesses and widths are available by arrangement.

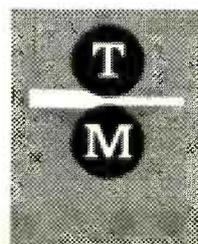


TELCON

Telcon Metals Ltd
Manor Royal, Crawley, Sussex
Crawley: 28800

WW—028 FOR FURTHER DETAILS

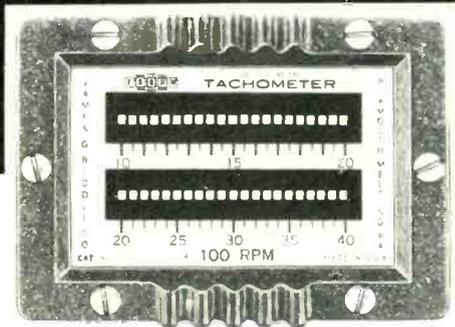**Accurate and direct
measurement of speed without
coupling to moving parts**



FRAHM resonant reed TACHOMETERS

for hand use or permanent mounting
Ranges and combinations of ranges from 900 to 100,000 r.p.m.
Descriptive Literature on Frahm Resonant Reed Tachometers and
Frequency Meters available from the sole U.K. Distributors. Manufacture
and Distribution of Electrical Measuring Instruments and Electronic
Equipment. The largest stocks in the U.K. for off-the-shelf delivery.


ANDERS ELECTRONICS LIMITED
Anders means meters 48/56 Bayham Place, Bayham Street,
London NW1. Tel: 01-387 9092

WW—029 FOR FURTHER DETAILS

PRODUCTION TESTING
DEVELOPMENT
SERVICING
EDUCATION

POWER UNITS

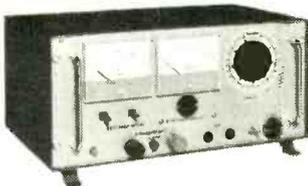NOW AVAILABLE WITH **3**
VARIABLE OUTPUTS



Type VRU/30/25 — £158.80

Input 200-250V. 50Hz
or 100-120V. 60Hz to order
Output 1:0-30V. 25A. D.C.
Output 2:0-70V. 10a. A.C.
Output 3:0-250V. 4A. A.C.

Other units are also available
with outputs of:
0-60V 12A.
0-120V 6A.
0-240V 3A.

ALL CONTINUOUSLY
VARIABLE

SEND FOR FURTHER DETAILS
OF THESE VERSATILE UNITS TO

Valradio LIMITED, BROWELLS LANE,
FELTHAM, TW13 7EN, MIDDLESEX.
TELEPHONE 01-890 4242

WW—030 FOR FURTHER DETAILS

ENGINEERS!

**WRITE FOR THE BOOK
THAT CAN CHANGE
YOUR WHOLE FUTURE**

The B.I.E.T. guide to success should be read by every ambitious engineer. Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost B.I.E.T. home study course. There are no books to buy and you can pay-as-you-learn. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

CUT OUT THIS COUPON CHOOSE A NEW FUTURE NOW!

Tick or state subject of interest. Post to address below.

- | | | |
|---|--|---|
| <input type="checkbox"/> MECHANICAL | <input type="checkbox"/> Work Study | <input type="checkbox"/> CONSTRUCTIONAL |
| <input type="checkbox"/> A.M.S.E. (Mech) | <input type="checkbox"/> Works | <input type="checkbox"/> A.M.S.E. (Civil) |
| <input type="checkbox"/> C & G Eng. Crafts | <input type="checkbox"/> Management | <input type="checkbox"/> Architecture |
| <input type="checkbox"/> C & G Fabrication | <input type="checkbox"/> DRAUGHTSMAN- | <input type="checkbox"/> Building |
| <input type="checkbox"/> Diesel Eng. | <input type="checkbox"/> SHIP | <input type="checkbox"/> Carpentry & Joinery |
| <input type="checkbox"/> Inst. Eng. & Tech. | <input type="checkbox"/> A.M.I.E.D. | <input type="checkbox"/> Civil & Municipal Eng. |
| <input type="checkbox"/> Inst. Motor Ind. | <input type="checkbox"/> Electrical | <input type="checkbox"/> Constructional Eng. |
| <input type="checkbox"/> Maintenance Eng. | <input type="checkbox"/> Draughtsmanship | <input type="checkbox"/> Construction |
| <input type="checkbox"/> Mechanical Eng. | <input type="checkbox"/> Gen. | <input type="checkbox"/> Surveyors Institute |
| <input type="checkbox"/> Sheet Metal Work | <input type="checkbox"/> Draughtsmanship | <input type="checkbox"/> Council Eng. |
| <input type="checkbox"/> Welding | <input type="checkbox"/> Jig & Tool Design | <input type="checkbox"/> Health Eng. |
| <input type="checkbox"/> ELECTRICAL & | <input type="checkbox"/> Technical Drawing | <input type="checkbox"/> Hydraulics |
| <input type="checkbox"/> ELECTRONIC | <input type="checkbox"/> RADIO & TELE- | <input type="checkbox"/> Inst. of Builders |
| <input type="checkbox"/> A.M.S.E. (Elec.) | <input type="checkbox"/> COMMUNICATIONS | <input type="checkbox"/> Inst. Clerk of Works |
| <input type="checkbox"/> C & G Elec. Eng. | <input type="checkbox"/> C & G Radio/TV/ | <input type="checkbox"/> Inst. Works & |
| <input type="checkbox"/> C & G Elec. Inst. | <input type="checkbox"/> Electronics | <input type="checkbox"/> Highway Supers. |
| <input type="checkbox"/> C & G Elec. Tech. | <input type="checkbox"/> C & G Telecomm. | <input type="checkbox"/> Painting & |
| <input type="checkbox"/> Computer Elec. | <input type="checkbox"/> Technicians | <input type="checkbox"/> Decorating |
| <input type="checkbox"/> Electronic Eng. | <input type="checkbox"/> Prac. Radio & Elec. | <input type="checkbox"/> Structural Eng. |
| <input type="checkbox"/> Electrical Eng. | <input type="checkbox"/> (with kit) | <input type="checkbox"/> Surveying |
| <input type="checkbox"/> Install. & Wiring | <input type="checkbox"/> Radio Amateurs | <input type="checkbox"/> GENERAL |
| <input type="checkbox"/> MANAGEMENT & | <input type="checkbox"/> Exam. | <input type="checkbox"/> Agricultural Eng. |
| <input type="checkbox"/> PRODUCTION | <input type="checkbox"/> Radio Servicing & | <input type="checkbox"/> Council of Eng. Inst. |
| <input type="checkbox"/> Computer Prog. | <input type="checkbox"/> Repairs | <input type="checkbox"/> General Education |
| <input type="checkbox"/> Electronic Data | <input type="checkbox"/> Transistor Course | <input type="checkbox"/> Pract. Slide Rule |
| <input type="checkbox"/> Processing | <input type="checkbox"/> TV Main & Serv. | <input type="checkbox"/> Pure & Applied |
| <input type="checkbox"/> Estimating | <input type="checkbox"/> AUTO & AERO | <input type="checkbox"/> Maths. |
| <input type="checkbox"/> Foremanship | <input type="checkbox"/> Aero Eng. | <input type="checkbox"/> Refrigeration |
| <input type="checkbox"/> Inst. Cost & Man. | <input type="checkbox"/> A.M.I.M.I. | <input type="checkbox"/> Rubber Technology |
| <input type="checkbox"/> Accountants | <input type="checkbox"/> A.E.C. Cert. | <input type="checkbox"/> Sales Engineers |
| <input type="checkbox"/> Inst. Marketing | <input type="checkbox"/> Auto Engineering | <input type="checkbox"/> University Ent. |
| <input type="checkbox"/> Management | <input type="checkbox"/> Auto Repair | |
| <input type="checkbox"/> Motor Trade Man. | <input type="checkbox"/> C & G Auto Eng. | |
| <input type="checkbox"/> Network Planning | <input type="checkbox"/> Garage | |
| <input type="checkbox"/> Personnel Man. | <input type="checkbox"/> Management | |
| <input type="checkbox"/> Production Eng. | <input type="checkbox"/> MAA/IMI Diploma | |
| <input type="checkbox"/> Quality Control | <input type="checkbox"/> Motor Vehicle | |
| <input type="checkbox"/> Salesmanship | <input type="checkbox"/> Mechanics | |
| <input type="checkbox"/> Storekeeping | | |

G.C.E. 58 'O' & 'A'
LEVEL SUBJECTS
Over 10,000
Group Passes

Coaching for many major exams, including C & G and also assistance in ONC/HNC

**SEND FOR
YOUR FREE
BOOK NOW!**



**BRITISH INSTITUTE
OF ENGINEERING
TECHNOLOGY**




DEPT. BWW09 ALDERMASTON COURT, READING RG7 4PF

QL BWW09

NAME _____
BLOCK CAPITALS PLEASE
ADDRESS _____

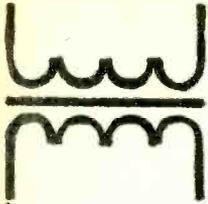OTHER SUBJECTS _____ AGE _____
Accredited by the Council for the Accreditation of Correspondence Colleges.



transformers

mains, audio, microphone, ferrite core and other wound components

A wide range of transformers manufactured to customers individual requirements.


Prompt Prototype Service available



MICROPHONE TRANSFORMER IN MUMETAL CAN



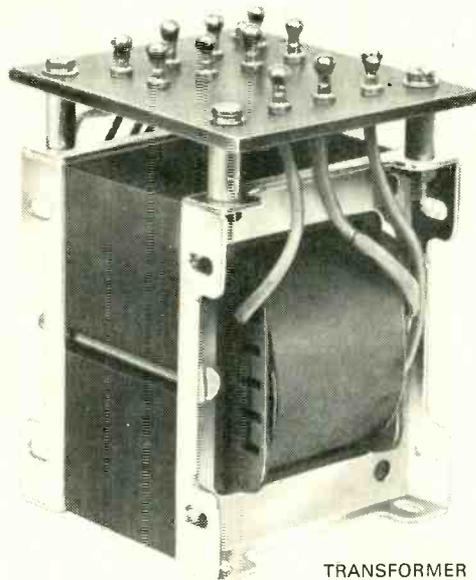TRANSFORMER WITH TWO HOLE CLAMP AND SOLDER TAG CONNECTIONS



TRANSFORMER WITH UNIVERSAL END FRAMES AND TURRET LUG CONNECTIONS

Drake Transformers Limited


Telephone: Billericay 51155

Kennel Lane, Billericay, Essex.

WW—031 FOR FURTHER DETAILS

Everything you asked for in a VOM — for only £26.00

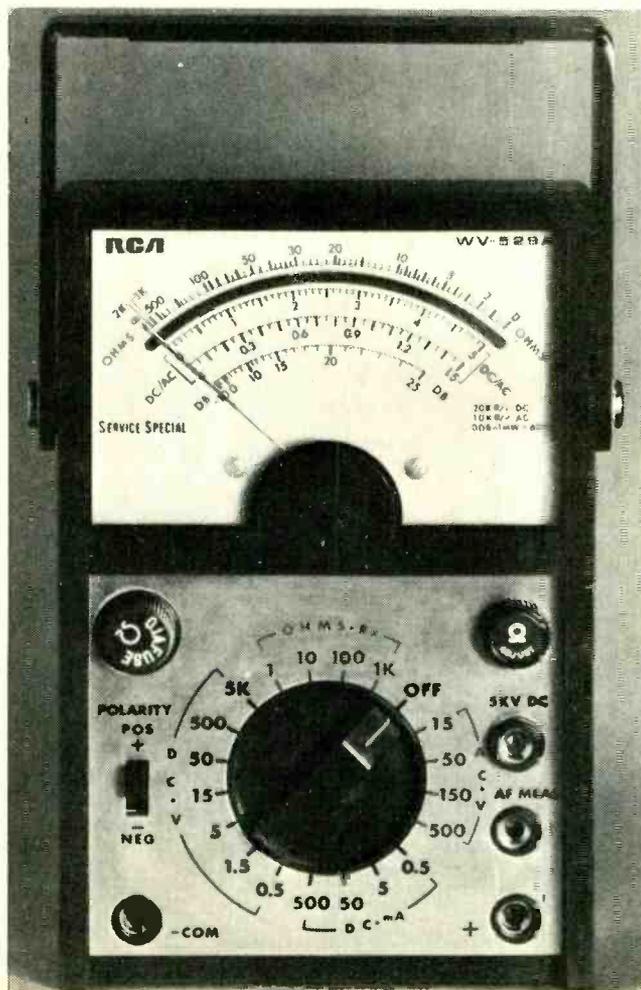complete with test leads, batteries and spare fuse.



The new RCA WV 529A "Service Special" VOM features:

- Taut-band meter movement with mirror scale for accuracy. Diode protected against burnout.
- High-impact plastic case with recessed panel for rugged handling.
- Measures up to 5,000 volts DC without add-on accessories to meet a broader range of servicing needs.
- Input polarity reversal switch for DC voltage and current measurements. Also reverses battery polarity in ohms function — aids in solid-state servicing.
- Fuse-mounted on front panel for easy access — protects ohms circuits.
- 3-colour coded panel and meter face for faster identification.
- Convenient 3-to-1-step ranges (VTVM-type).
- One year guarantee.

Try the new RCA WV-529A today and see for yourself why we believe it offers the best price/performance combination on the market. For more information on this and other electronic instruments in the range contact

RCA Limited
Sunbury-on-Thames, Middlesex, England.
Tel: Sunbury-on-Thames 85511

RCA
Electronic Components

WW—032 FOR FURTHER DETAILS

Reach for the facts

The facts are never very far away when you've got the latest Hi-Fi Year Book. Because it tells you everything you need to know about the Hi-Fi equipment on the market - what it does, what it costs, who makes it and where to buy it. It's packed with all the information you need to arrive at wise buying decisions - and it will save you money and time. The 1974 edition is completely updated, with extra pages and hundreds of new illustrations and specifications. And there is a host of absorbing articles on the latest Hi-Fi developments. Order your copy right away.

SPECIAL PRE-PUBLICATION PRICE
(effective until November 1)
£1.50 inclusive

Hi-Fi Year Book 1974



ORDER FORM

To: Room 15, Dorset House, Stamford Street, London SE1 9LU

Please send me.....copy(ies) of Hi-Fi Year Book 1974 at £1.50 per copy inclusive.

I enclose cheque/p.o. value £.....payable to IPC Business Press Ltd.

Signature Date.....

Name
(please print)
Address

Company registered in England No. 677128
Regd. Office: Dorset House, Stamford Street, London SE1 9LU **WW**

LITTLE WONDER



THE MINITEST IS PREFERRED

The SE1 MINITEST has made a remarkable impact in the pocket-sized multi-range meter market, by making itself a firm favourite with discerning people in the industry. Let's look into the reasons why.

First, the appearance. Diminutive, neat, wipe-clean plastic cover with pressed steel case. Controls are simple and easy to use.

Second, the range. The Minitest measures a.c. and d.c. voltages d.c. current and resistance over 20 ranges to a sensitivity of 20,000 and 2,000 ohms per volt d.c. and a.c. respectively.

Third, high voltage probes. These extend the range to 25 or 30kV d.c.

Little wonder the Minitest is preferred!

SALFORD ELECTRICAL INSTRUMENTS LTD

Peel Works, Barton Lane, Eccles, Manchester M30 0HL.
Telephone: 061-789 5081. Telex: 667711
A member company of GEC Electrical Components Ltd.



WW-033 FOR FURTHER DETAILS

M-OV TETRODES

TT 21, THE TUBE THAT GOES ON.

You could design yourself a reputation around this M-OV tube.

- It's the best beam tetrode you can buy.
- Offers lowest possible cost per watt.
- Communications transmitters all over the world depend – and go on depending – on the famous M-OV TT21.

For more details, just ask us.




EEV AND M-OV KNOW HOW.

THE M-O VALVE CO LTD, Hammersmith, London, England W6 7PE.
Tel: 01-603 3431. Telex: 23435. Grams: Thermionic London. **S&C**

WW-034 FOR FURTHER DETAILS



Series 7 Modular Sound Systems

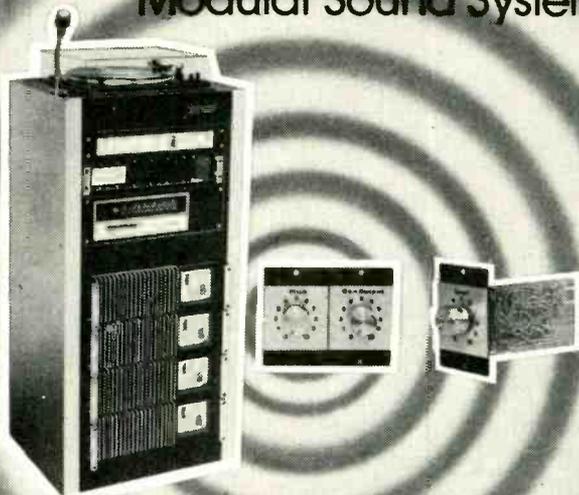


GRAMPIAN REPRODUCERS LTD
HANWORTH TRADING ESTATE,
FELTHAM, MIDDLESEX.
TELEPHONE: 01-894 9141.
GRAMS: REAMP FELTHAM

JACW/X170

WW-035 FOR FURTHER DETAILS

METER PROBLEMS?

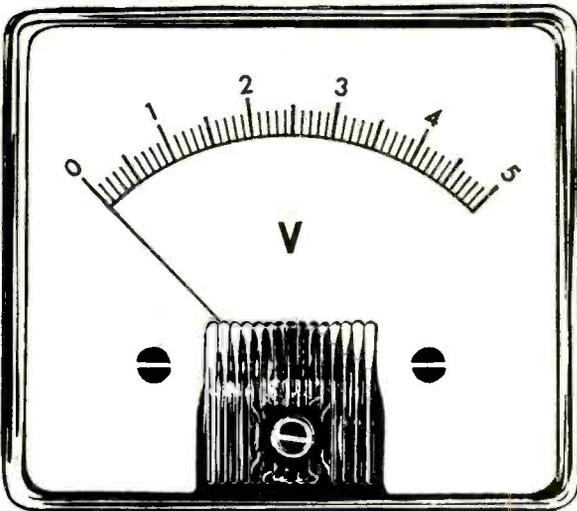

A very wide range of modern design instruments is available for 10/14 days' delivery.

Full Information from:

HARRIS ELECTRONICS (London)
138 GRAYS INN ROAD, W.C.1 Phone: 01/837/7937

WW—036 FOR FURTHER DETAILS

Transducer and Recorder amplifiers and systems



reliable high performance & practical controls
individually powered modules—mains or dc
option single cases and up to 17 modules
in standard 19" crates small size—low weight
—realistic prices.


FYLDE ELECTRONIC LABORATORIES LIMITED
16 Oakham Court Preston PR1 3XP
Telephone 0772 57560

WW—037 FOR FURTHER DETAILS



Eddystone

DIECAST BOXES

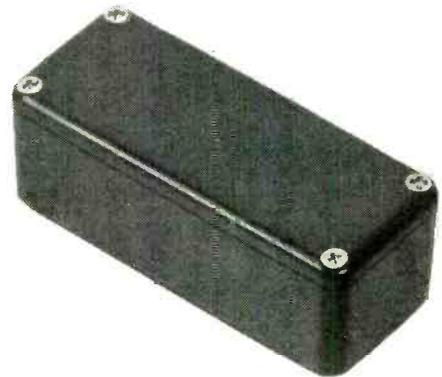

WORLD-WIDE AVAILABILITY

Diecast in aluminium alloy, BS 1490 LM2

SIX SIZES

- Cat. No. 7969P— $3\frac{5}{8} \times 1\frac{1}{2} \times 1\frac{17}{32}$ in
(Illustrated) 92.1 x 38.1 x 31 mm
- Cat. No. 7134P— $4\frac{3}{8} \times 2\frac{3}{8} \times 1\frac{17}{32}$ in
111.1 x 60.3 x 31 mm
- Cat. No. 6908P— $4\frac{11}{16} \times 3\frac{11}{16} \times 2\frac{27}{32}$ in
119.1 x 93.6 x 56.4 mm
- Cat. No. 6827P— $7\frac{25}{64} \times 4\frac{45}{64} \times 2\frac{27}{32}$ in
187.3 x 119.1 x 56.4 mm
- Cat. No. 6357P— $7\frac{25}{64} \times 4\frac{45}{64} \times 3\frac{7}{32}$ in
187.3 x 119.1 x 81.8 mm
- Cat. No. 7970P— $7\frac{3}{8} \times 7\frac{3}{8} \times 2\frac{21}{32}$ in
187.3 x 187.3 x 67.5 mm

(Nominal outside dimensions)

Rugged. Corrosion resistant.

Self adhesive plastic strip available for mounting PCB's internally.

Easily Machined. Good Surface Finish.

Illustrated brochure and information on your local Distributor from:


Eddystone Radio Limited

Alvechurch Road, Birmingham B31 3PP, England
Telephone: 021-475 2231. Telex: 337081

A Member of Marconi Communication Systems Limited

LTD/ED103

WW—038 FOR FURTHER DETAILS

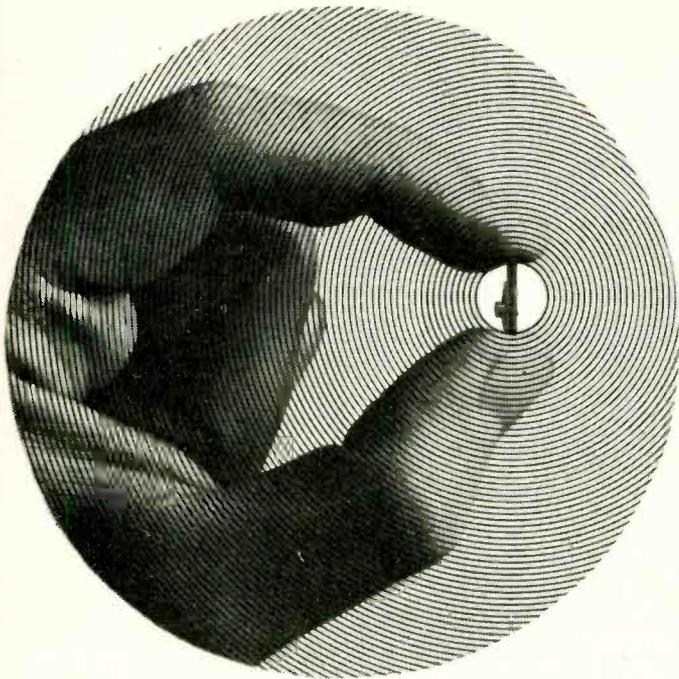


Discon gives you the slimmest possible chance of failure.


When you use Jackson 'Discon' Trimmers you're using the slimmest trimmers on the market. With a maximum thickness of only 2.8mm, capacitance ranges up to 40pF, a Discon miniature ceramic dielectric trimmer capacitor is space saving, with a high capacitance per unit of volume.

With Jackson you know you're using tried and tested components that will give perfect reliability over a long life. And you can have components custom made to suit your individual requirements.

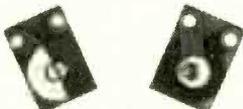With skilled personnel and modern equipment backed by 45 years of technical know-how, we are your guarantee of a reliable product.



Catalogue No. 10,000

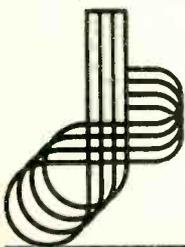

Write for fully illustrated catalogue:

**JACKSON BROTHERS
(LONDON) LIMITED**


KINGSWAY, WADDON, CROYDON CR9 4DG.
TEL: 01-681 2754/7. TELEX: 946849.
U.S. OFFICE: M. SWEDGAL
258 BROADWAY, NEW YORK, N.Y. 10007.

JB7

WW-039 FOR FURTHER DETAILS

Celestion Loudspeaker Engineering
advances the state of the art to a
new plateau.

Ditton 66 Studio Monitor

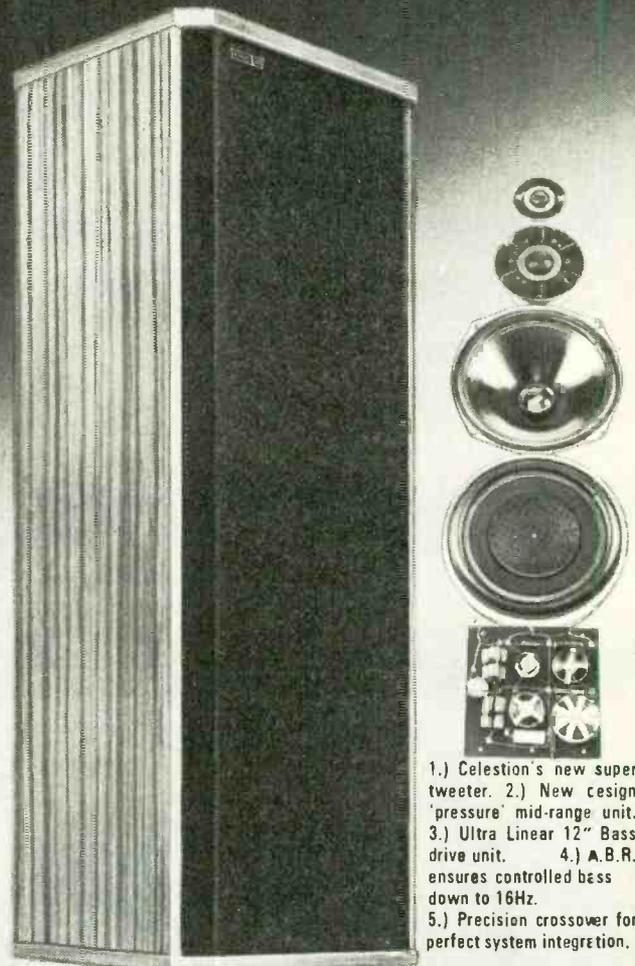

1.) Celestion's new super tweeter. 2.) New design 'pressure' mid-range unit. 3.) Ultra Linear 12" bass drive unit. 4.) A.B.R. ensures controlled bass down to 16Hz. 5.) Precision crossover for perfect system integration.

A new Loudspeaker of advanced design suitable for studio use and for home installations of the highest quality.
UNITS: HF 2000 (dome 'pressure' type) MF 500 (Mid-range Dome 'pressure' type) Ultra linear 12" bass driver and 12" ABR. The crossover has resulted from considerable research and crossover points are at 500 Hz and 5000 Hz 80 Watts Maximum, 4-8 ohm. This monitor loudspeaker system has an exceptionally wide and flat frequency response. Very low order harmonic and inter-modulation distortion. Precise response to transients. Beautifully maintained polar response ensures absence of unwanted directional effects and provides a highly satisfactory stereo image throughout the listening area. Matched pairs.
SIZE 40 x 15 x 11 1/2 Natural Teak or Walnut Cabinet

Celestion



Loudspeakers for the Perfectionist

ROLA CELESTION LTD.
DITTON WORKS, FOXHALL ROAD, IPSWICH, SUFFOLK IP3 8JP


WW-040 FOR FURTHER DETAILS

Litesold

Total capability in soldering



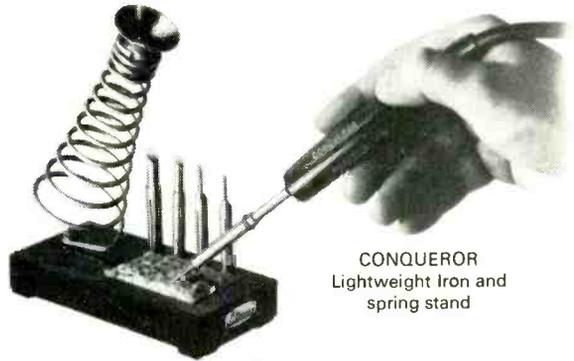ETC/I Electronically Temperature Controlled System



CONQUEROR Lightweight Iron and spring stand




LITESOLD High Quality Soldering Irons. 10w to 60w



ADAMIN Ultra Miniature Irons 15w and 18w



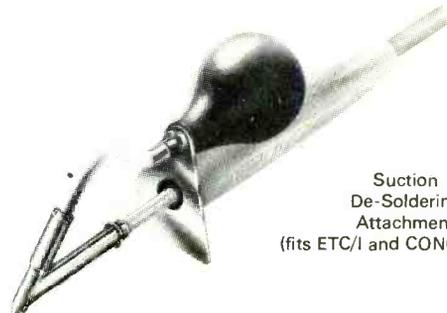D.I.L. I.C. De-Soldering Head (fits ETC/I and CONQUEROR)



Suction De-Soldering Attachment (fits ETC/I and CONQUEROR)



Pliers



De-Soldering Aids



De-Soldering Braid



Tweezers



Cutters

Send TODAY for FREE CATALOGUE with full details of this and other equipment

LIGHT SOLDERING DEVELOPMENTS LTD

28 SYDENHAM ROAD, CROYDON CR9 2LL

Tel: 01-688 8589 & 4559

WW-041 FOR FURTHER DETAILS

for you, the reward




D5



DM4




DM2

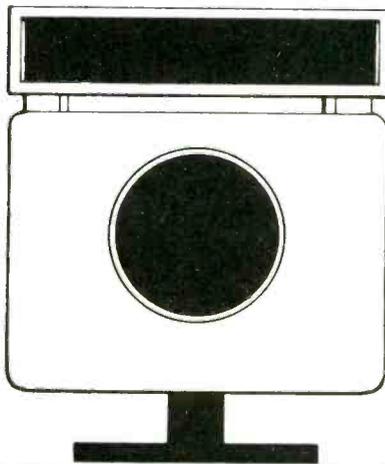

DM70

for us, the award

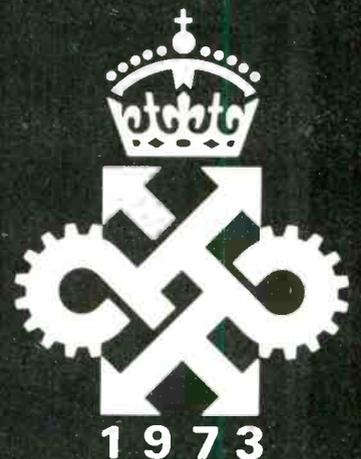To B & W Electronics
the Queen's Award to Industry
for outstanding export achievement



B&W electronics

Meadow Road Worthing BN11 2RX Telephone (0903) 205611

WW-042 FOR FURTHER DETAILS

Rohde & Schwarz offer

A fully transistorized **SIGNAL GENERATOR**



of high output power, with facilities for

swept-frequency and programmed operation

The newest signal generator from the Rohde & Schwarz range, the SMLU uses the latest solid state techniques to give finest performance combined with ruggedness and ease of use. Frequency coverage **25 MHz to 1000 MHz**, output powers up to 2 watts with ALC and calibrated attenuation. Sweepable or fully programmable using a **single 15 bit DTL/TTL Compatible BCD word**.


This generator is especially suitable for measurements:

- on power stages, frequency multipliers and power transistors**
- of antenna directional patterns and impedances without stray field effects**
- of receiver overload capacity**
- of electromagnetic compatibility (RFI, EMC)**
- of intermodulation and crossmodulation at high levels**
- on attenuators and filters with high stop-band attenuation**
- of the attenuation, reflection coefficient and transfer impedance of cables for feeding impedance meters**

and for direct operation as well as in conjunction with Automatic Test Systems



Please request our Technical Publication R26753 for a description of intermodulation and crossmodulation measurements with this unit.

25 to 1000 MHz

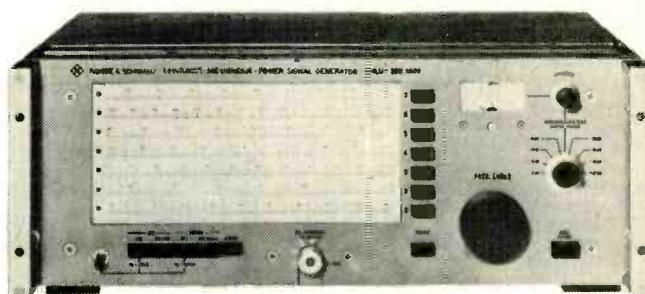

Impedance and Transmission Measurements on Active Four-terminal Networks

The following diagram shows the SMLU used as a high-power signal generator in a test setup for determining the impedance and transmission characteristic of power semiconductors such as transistors and varactors with a high driving level. A standing-wave detector in conjunction with Selective Microvoltmeter USU 1 is used for measuring the input impedance. Power matching of the output is carried out with two adjustable shorts. After removing the test item, the same setup can be employed for measuring the terminating impedance as a conjugate complex value of the transistor output impedance.

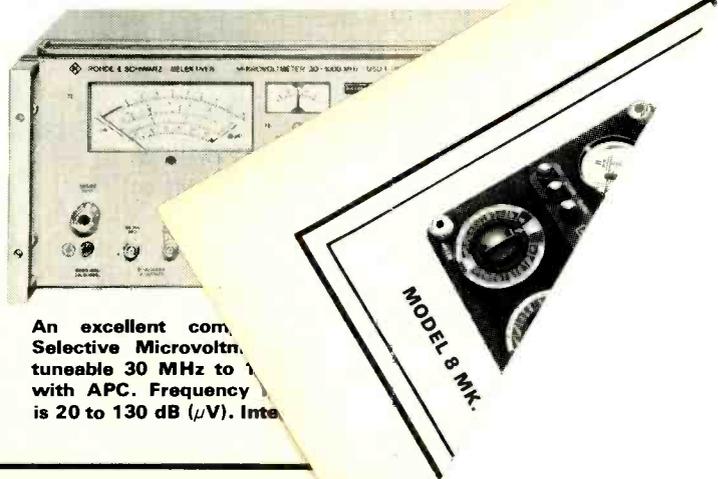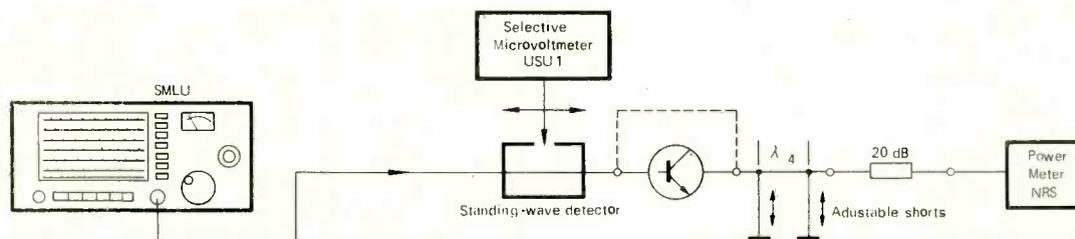

For full details and specifications apply to:

AVELEY ELECTRIC LTD.

Roebuck Road,
Chessington, Surrey

Tel: 01-397 8771
Telex: Avel London 928479

An excellent com
Selective Microvoltr
tunable 30 MHz to
with APC. Frequency
is 20 to 130 dB (μ V). Inte

WW-043 FOR FURTHER DETAILS

JAMES SCOTT

CUT ALIGNMENT TIME & COST

F.M. ELECTRONICS ALIGNMENT UNITS

This is a companion unit to the DR Alignment Unit and is used to align the record and reproduce electronics of F.M. recording channels of multi-channel instrumentation tape recorders conforming to the I.R.I.G. Intermediate and low band requirements.

The two main functions in an F.M. recording system which require periodical checking are:

- (a) The accuracy and linearity of the Record Modulator.
- (b) The accuracy and linearity of the Reproduce Demodulator.

The F.M. Alignment unit checks both these functions by the use of a standard voltage and a range of standard frequencies corresponding to the tape speed carrier centre frequencies and the $\pm 40\%$ deviation frequencies for each recording speed.



JAMES SCOTT (ELECTRONIC ENGINEERING) LTD. Carntyne Industrial Estate Glasgow E2 Tel. 041-778 4206

WW-044 FOR FURTHER DETAILS

PARKER SHEET METAL FOLDING MACHINES



Forms channels and angles down to 45 degrees which can be flattened to give safe edge. Depth of fold according to height of bench.

One year's guarantee. Money back if not satisfied.

Send for details: **A. B. PARKER**

FOLDING MACHINE WORKS, UPPER GEORGE STREET, HECKMONDWIKE, YORKS.

Telephone 3997

BENCH MODEL

36" x 18 gauge capacity £35.00 carr. 75p

24" x 16 gauge capacity £32.00 carr. 75p

Also the well-known vice model of

36" x 18 gauge capacity £17.00 carr. 50p

24" x 18 gauge capacity £12.00 carr. 38p

18" x 16 gauge capacity £12.00 carr. 38p

Add 10% VAT to total price of machine and carriage

WW-045 FOR FURTHER DETAILS



MODEL U-50DX

SANWA MULTI TESTERS

USED THROUGHOUT THE WORLD. SANWA'S EXPERIENCE OF 30 YEARS ENSURES ACCURACY, RELIABILITY, VERSATILITY. UNSURPASSED TESTER PERFORMANCE COMES WITH EVERY SANWA 6 Months' Guarantee Excellent Repair Service

MODEL P2B	£6.67	MODEL AT45	£21.52
MODEL JP5D	£8.00	MODEL 380CE	£21.85
MODEL 360YTR	£11.30	MODEL N101	£25.41
MODEL U50DX	£11.43	MODEL 460ED	£29.72
MODEL A303TRD	£15.04	MODEL EM800	£72.79
MODEL K30 THD	£17.21	MODEL R1000CB	£75.27
MODEL F80TRD	£18.73		

TO AN ADDITIONAL CHARGE OF 10% FOR V.A.T.

Cases extra, available for most meters, but not sold separately.

Please write for illustrated leaflet of these and other specialised Sanwa meters

SOLE IMPORTERS IN U.K.

QUALITY ELECTRONICS LTD.

47-49 HIGH STREET, KINGSTON-UPON-THAMES, SURREY. KT1 1LP

Tel: 01-546 4585

WW-046 FOR FURTHER DETAILS



v

CONTRACTORS TO H.M. GOVT. P.O. APPROVED

REPAIRS

7-14 DAYS SERVICE

TO SOLVE YOUR INSTRUMENT PROBLEMS CONTACT

LEDON INSTRUMENTS LTD.

76-78 DEPTFORD HIGH STREET, LONDON, SE8. TEL: 01-692 2689


GLADSTONE WORKS, GLADSTONE ROAD, FOLKESTONE, KENT. TEL: (STD) 0303 57555

OF ELECTRICAL MEASURING INSTRUMENTS Industrial and Precision Grade



STOCKISTS ALSO SUPPLIERS OF GEC RISSO AND OTHER MULTI-RANGE TEST SETS

WW-047 FOR FURTHER DETAILS

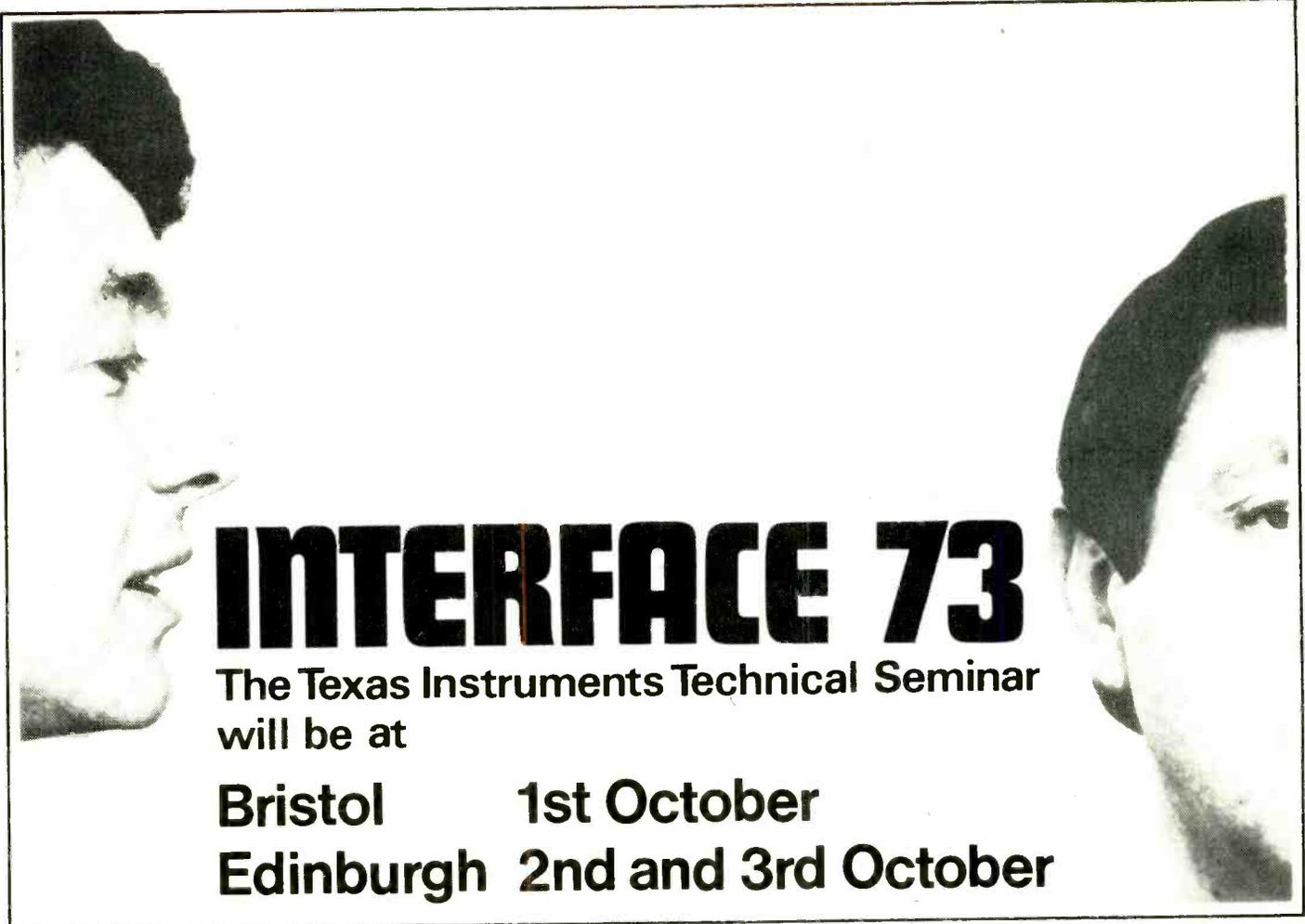

INTERFACE 73

The Texas Instruments Technical Seminar
will be at

Bristol 1st October
Edinburgh 2nd and 3rd October

In direct response to last years highly successful Seminar, Texas Instruments take pleasure in announcing INTERFACE 73. And what an "Even-better-than-last-time" show it will be. This year we offer an even more sophisticated visual presentation and a totally new broader based programme, as presented earlier this year at London's Talk of the Town.

Texas Instruments are continually reviewing their Seminars. All material is updated month-by-month to keep pace with advances in the rapidly developing semiconductor technologies. Their acknowledged expertise in this field ensures a sophisticated presentation and the calibre of speakers guarantees the depth and authority of lectures.

Every Interface 73 Delegate will receive: Semiconductor Circuit Design Vol. 2 (value £5), The new TTL Data Book (value £2); a comprehensive Data Package containing information on the subjects discussed. PLUS OF COURSE A SUPERB 3 COURSE LUNCH.

Please return the order form below to
Mrs Gina Penman Texas Instruments Limited
Seminar Centre MS21 Manton Lane
Bedford MK41 7PA

Telephone: Bedford 67466



Surname	Initials	NO	
Company			
Address			
Town/County		Office Use	Office Use

ORDER FORM

Please complete using block capitals only and one letter to each box

Bristol	1st October	
Edinburgh	2nd October	
	3rd October	

Indicate number of tickets required in appropriate box

TICKET PRICE £10
including 91p VAT

I enclose Cheque/M.O./P.O. to the value _____ or Please invoice my Company – the order number is _____

WW-048 FOR FURTHER DETAILS

MODEL: TTR-21

*Easy-handling,
superb performance!!*

PORTABLE VHF TRANSCIVER



(150MHz, 1W)

FEATURES:

- Three operating frequencies in any 2MHz segment of the 42-172MHz range may be selected
- A monolithic HCM filter produced by our own crystal division is used in the IF amplifier. Performance and selectivity in this single superheterodyne set are excellent.
- A light emitting diode is used to indicate the transmit output level and condition of the battery. This approach improves reliability and allows checks under poor lighting conditions.
- Use of a resistor eliminates the troublesome fuse and alleviates maintenance requirements

TOYOCOM
TOYO COMMUNICATIONS
EQUIPMENT CO., LTD.

EXPORT DEPARTMENT
TOYO BUILDING, 6C 6 12 20 JINGUMAE
SHIBUYA-KU, TOKYO, JAPAN
CABLE: EXPORT TOYO COM TOKYO
TEL (03) 406-3332
TELEX 0242300

WW-049 FOR FURTHER DETAILS

**THE HIGHEST PERFORMANCE DIGITAL FREQUENCY COUNTERS
AT THE PRICE IN THE WORLD EVERYBODY BUYS THEM**

	301 5 DIGIT, 32 MHz STABILITY 3 parts in 10 ⁸ SENSITIVITY 50mV	£75
	401 6 DIGIT, 32 MHz. STABILITY 1 part in 10 ⁸ SENSITIVITY 10mV	£110
	501 8 DIGIT, 32 MHz. STABILITY 3 parts in 10 ⁸ (crystal oven) SENSITIVITY 10mV	£160
	701 8 DIGIT, 50 MHz. STABILITY 3 parts in 10 ⁸ SENSITIVITY 10mV	£170
	801A 8 DIGIT, 300 MHz. STABILITY 3 parts in 10 ⁸ SENSITIVITY 10mV	£260

PRICES EXCLUSIVE OF VAT
ELECTRONIC START/STOP version PLUS £10
MEMORY version PLUS £25
DIRECTLY COUPLED INPUT AND SPECIALS TO ORDER
Write for illustrated leaflet.

*Supplied to and acclaimed by professional engineers everywhere
who have purchased our electronic instruments for the past 10 years.*
Norwegian Agent: **ELECTRO-TRADE, TRONDHEIM, NORWAY.**
Australian Agent: **ANELCO ELECTRONICS SOUTH AUSTRALIA 5049**

**RCS ELECTRONICS, NATIONAL WORKS,
BATH ROAD, HOUNSLOW, MIDDX. TW4 7EE**
Telephone: 01-572 0933/4

WW-050 FOR FURTHER DETAILS

CONVERTERS

British Made



VOLTAGE to FREQUENCY CONVERTERS

- 15VF-1 Wide frequency range, floating output, input neg.
- 15VF-2 pos. input accuracy 0.01% to 0.05%.
- 15VF-5 Audio range 0.01%, general purpose.
- 15VF-6 Low cost, general purpose.
- 15VF-8 High speed.

FREQUENCY to VOLTAGE CONVERTERS

- 15FV-3 Wide frequency range 0.02% to 0.05%.
- 15FV-4 Audio range, general purpose.
- 15FV-4a 0-500 Hz .2% accuracy.
- 15FV-7 .1% to 10 Hz.

TIME to VOLTAGE CONVERTER

- 15TV-7 Measures voltage free contact closure.

PERIOD to VOLTAGE CONVERTER


- 15PV-7 Measures interpulse periods.

AUXILIARY MODULES

- TELEMETRY AMPLIFIERS Line transmission.
- CLOCK MODULES Accurate pulses.

ancom limited devonshire street cheltenham 53861

WW-051 FOR FURTHER DETAILS

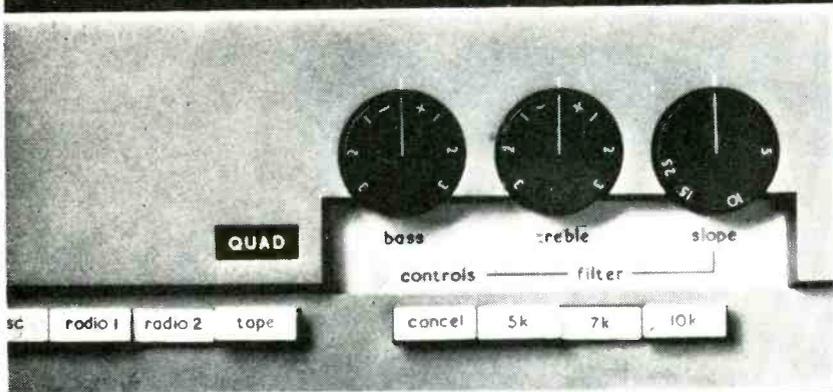

Even with a perfect pickup, the distortion from a gramophone record for sounds of equal level increases very rapidly at high frequencies, eventually doubling for every major third increase in pitch.

There comes a point when, to musical ears, the distortion is increasing faster than the musical quality. The QUAD filter system is designed to enable those with ears to hear to obtain more of the music and less of the distortion.



QUAD

for the closest approach to the original sound

Send postcard for illustrated leaflet to Dept. WW
Acoustical Manufacturing Co. Ltd., Huntingdon, Tel: (0480) 52561. QUAD is a Registered Trade Mark.

WW—052 FOR FURTHER DETAILS

Naval Supremacy

Redifon's new Naval Radiotelephone equipment is now in Senior Service. Selected by the Royal Navy, the 643 transmitter is the product of private initiative and development. With its companion CJP general-purpose receiver, this new radiotelephone has the vital responsibility of updating medium and long distance communications between British warships of all classes and shore bases.

Despite its big task, the 643 can be operated easily with minimum training. Operators can set rapidly to pre-determined frequencies, search

crowded bands or hunt for those elusive coast stations.

Throughout the 1970's the Redifon 643 will play a key naval role; not only for the Royal Navy but also for all the most modern navies throughout the world.

**Redifon Telecommunications Ltd,
Marine Division,
Broomhill Road, London, SW18 4JQ
Telephone: 01-874 7281 Telex: 264029**

☀ A member of the Rediffusion organisation




Redifon Telecommunications Limited



WW-053 FOR FURTHER DETAILS

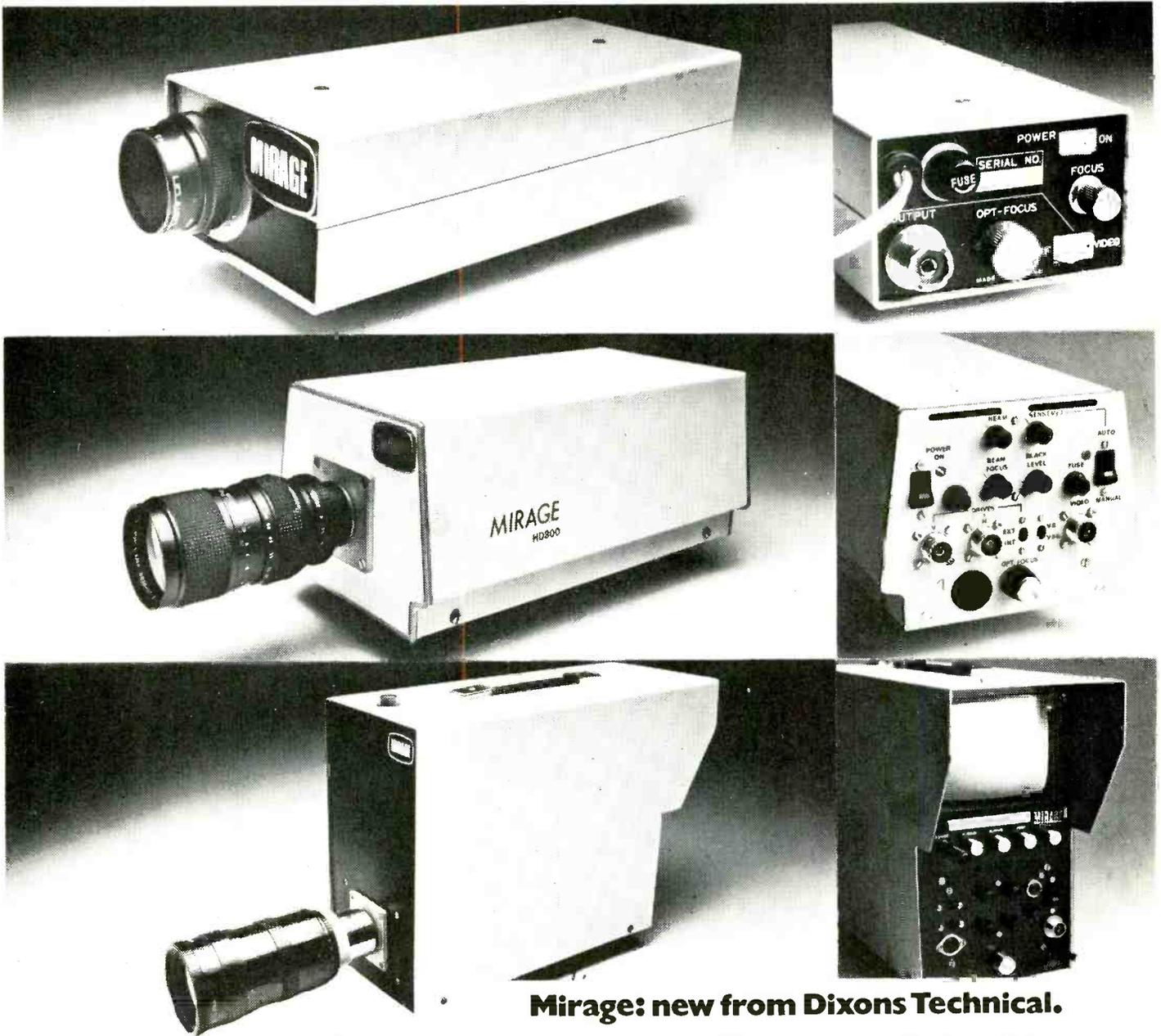Dixons Technical have something in black and white to make CCTV importers green with envy.



Mirage: new from Dixons Technical.

Dixons Technical have the largest range of CCTV equipment in the country. And now they've added Mirage: their very own CCTV system.

Mirage is the all-purpose CCTV system comprising the finest components available. It can be used by schools, by industry, as an audio-visual aid, or with Mirage automatic video, switchers and monitors, it's perfect for surveillance purposes.

The Mini 500 is a small, discreet camera specially designed for surveillance. It comes complete with an f1.8 lens.

The HD800 gives a high definition picture. Incorporates a Mullard separate mesh tube. And accepts external drives.

The HD800 VF boasts the same high standard of specifications as the HD800, but

also has a 5" monitor screen. It's the perfect semi-professional studio camera.

With both HD800 models, Plumbicon (R,* and Silicon tubes can be fitted without modification to the circuitry.

Every piece of equipment is backed by Dixons Technical superb after-sales service.

If you don't wish to spend cash, no problem. The entire Mirage range is available for hire, lease or rent.

To: Dixons Technical Ltd., 3 Soho Square, London, W.1.
Tel: 01-437 8811. www//DID

Please send me lots of information on the entire Mirage range.

Name: _____
Address: _____

Dixons
Technical Ltd
OF SOHO SQUARE

*Plumbicon is the registered trade mark of Mullard.

WW-054 FOR FURTHER DETAILS

Listen



to the irresistible sound.
of Martin Speakers

The sound of Martin Speakers can be as quiet and irresistible as the gentle meeting of sand and surf. Or vibrant and depthroated as the roar of thunder in the summer sky. Martin Speakers, for people who are attuned to the irresistible sounds of the audible universe.



Acos for sound enjoyment.

COSMOCORD

Cosmocord Ltd., Eleanor Cross Road, Waltham Cross, Hertfordshire.
Telephone: Waltham Cross 27331

Martin speakers are distributed exclusively in the U.K. by Cosmocord.



WW—055 FOR FURTHER DETAILS

BIAS ELECTRONICS

B
E
I
O
O

S
T
U
D
I
O

R
E
C
O
R
D
E
R


Excellent Performance
High Reliability
Mono or Stereo 1/4"
4 track 1/2" versions
in console, rack mounting
or transportable form.
At very reasonable prices.



Phone or write to
BIAS ELECTRONICS LTD. 01-947 3121
UNIT 8 COOMBE TRADING ESTATE
112-120 COOMBE LANE, LONDON SW20 0BA.

WW—114 FOR FURTHER DETAILS

FOUR INSTRUMENTS FOR THE PRICE OF ONE

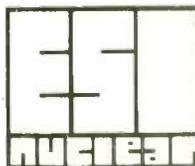

The new 237 offers
★ Nuclear autoscaling
★ Timing
★ Rate and frequency measurements
For only £157


For full information:
ESI NUCLEAR LIMITED
2 CHURCH ROAD, REDHILL,
SURREY RH1 6QA
Tel: Redhill 64993

An associate company of Edwards Scientific International, Mirfield, Yorkshire

WW—056 FOR FURTHER DETAILS

NEW STANDARD CASES from OLSON

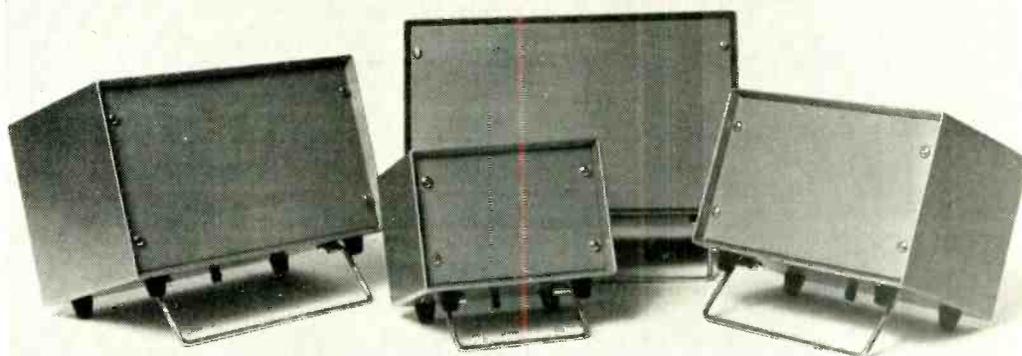NEW SERVICE FROM STOCK — DESPATCHED BY RETURN OF POST



TYPE	WIDTH	HEIGHT	DEPTH	FRONT PAN DIM.	PRICE	LEG EXTRA
21	6 1/2"	4 1/2"	4 1/2"	6" x 4"	£2.65	60p
22	8 1/2"	5 1/2"	5 1/2"	8" x 5"	£3.00	60p
23	10 1/2"	6 1/2"	6 1/2"	10" x 6"	£3.60	65p
24	12 1/2"	7 1/2"	7 1/2"	12" x 7"	£3.90	65p

Cases made from 20swg. zinc coated m/s. Front & rear panels 16swg. aluminium. Cases finished in Olive green hamertone with front panels in light straw shade 384. All cases fitted with ventilated rear panels and a very attractive chrome plated retractable leg can be fitted as an optional extra.


Our Trade Counter is open for personal callers from 9 a.m. to 5.30 p.m. Monday-Friday

OLSON ELECTRONICS LTD., FACTORY NO. 8, 5-7 LONG ST., LONDON E2 8HJ.

POSTAGE EXTRA + 10% V.A.T.

TEL: 01-739 2343

WW—057 FOR FURTHER DETAILS

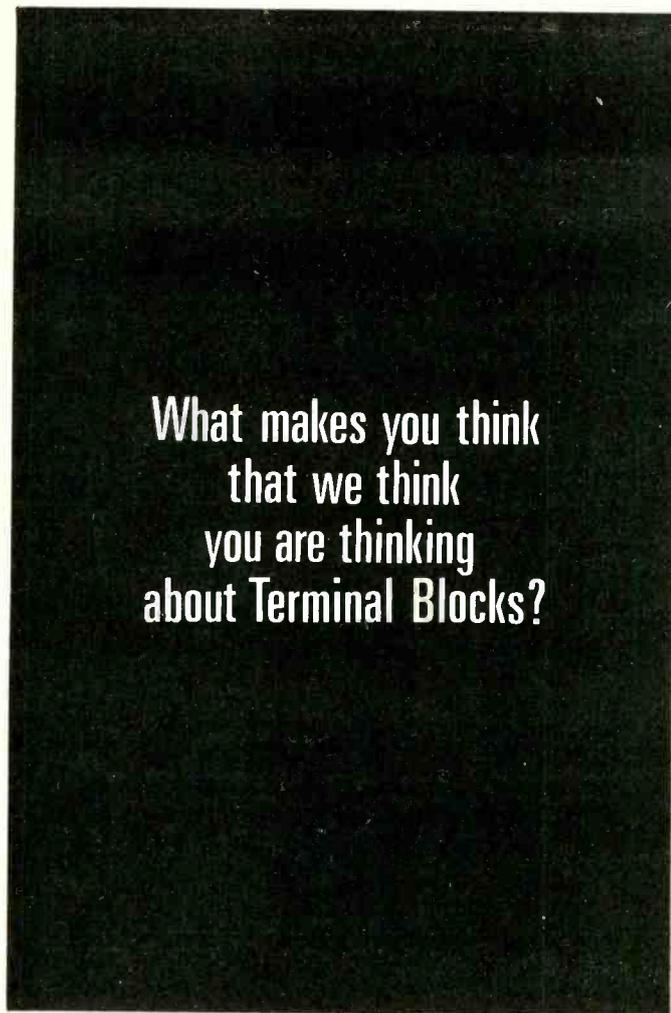

What makes you think
that we think
you are thinking
about Terminal Blocks?

**WE AREN'T
YOU KNOW!**

Actually, we *were* thinking that *you* might be thinking of Indicator Lights, Voltage Selectors, Connectors, or perhaps Metal Pressings or Plastic Components. And we were thinking that, even if you only wanted a few of any or each of these, it would be a pleasure to do business with you.

And *you* might find it a pleasure to do business with *us*, especially as we can solve so many of your supply problems.

For instance, suppose you *did* want just a few of these or any other Cinch, Dot or FT components very quickly, we could, as stock holders, have them on the way to you the day we got your order.

Perhaps you'd like to put this promise to the test.

UNITED-CARR SUPPLIES
*The single source
that simplifies.*

Let us have your next inquiry — it will be dealt with immediately



United-Carr Supplies Ltd.
Clifton Works, Frederick Road,
Stapleford, Nottingham.
Sandiacre 6003 STD 0602 39 6003 Telex No. 377117



A2

WW—058 FOR FURTHER DETAILS

P.C. BORED?

— not with the


DECON- DALO 33PC



A unique drafting aid for the electronics engineer enabling him to prepare in minutes a perfect PCB.

A fine-tipped marker charged with a free-flowing etch-resist ink. Simply draw the desired circuit onto copper laminated board—etch—clean.

The circuit is ready to use.

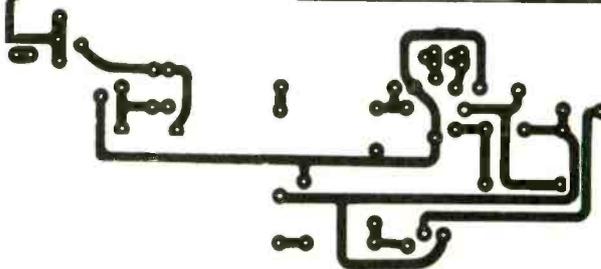

NO MESS — NO MASKING
A perfect circuit every time !

The Decon-Dalo 33 PC marker is now available in France, Germany, Italy, Switzerland, Austria and all Scandinavian countries. Send for details of local supplier.

Please send me further details on the 33PC:

Name


Address

..... W.W. 10.

Post to: **DECON LABORATORIES LTD.**
FREEPOST
PORTSLADE, BRIGHTON, ENGLAND
(No Stamp Needed) Phone 0273 414371

WW—059 FOR FURTHER DETAILS

BARGAIN COUNTER

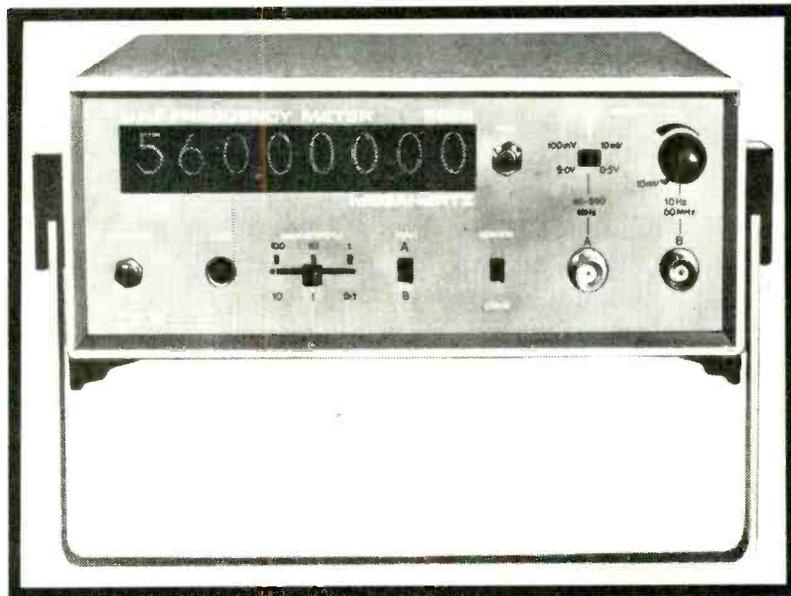

A new high precision low cost 560 MHz frequency meter from Racal Instruments

Racal believes that high standards don't necessarily mean high prices. So they're introducing a new 560 MHz Frequency Meter that embodies Racal's high standards of workmanship and quality—at a very low price.

The 9839 is a high precision instrument with an unrivalled price performance ratio and offers these outstanding features—

- direct reading to 560 MHz
- 10 mV sensitivity
- eight digit memory display
- fast warm-up standard
1 part in 10^7 in 4 minutes
- Ageing 5 parts in 10^9 per day
- up to 10 sec. count time
- portable and compact

Use the coupon to bring you more details of how you can count on the 9839 to save you money without sacrificing quality.

To: Racal Instruments Limited, Duke Street, Windsor, Berks. SL4 1SB.
Tel: Windsor 69811. Please send me details of your high quality, low price 9839 frequency meter.

Name _____

Position _____

Company _____

Address _____

RACAL
The Electronics Group

WW—060 FOR FURTHER DETAILS

www.americanradiohistory.com

QUALIFY TO EARN MORE MONEY In a better job

Exciting new career opportunities! They're just waiting to be grasped — in the ever-growing industries of electronics, radio and television. And with ICS behind you, you can soon win the qualifications you need to assure your career success. Win them in your own time, in your own home, by starting an ICS learn-as-you-earn correspondence course now. You get personal, individual attention from really expert and experienced tutors. We teach you the theory, we teach you the practice. Books and components are provided. So is all the assistance, all the backing you need.

We also have a complete range of courses at the ready for people keen to score success in other fields. Whatever qualification you're after, we can help you get it, whether you're pushing ahead where you are or switching to something completely new.

Take your first step *now* towards a better paid, more assured future. Send for your FREE Careers Guide today.

Take one of these courses

Society of Engineers Graduateship (Electrical Engineering)
 C & G Telecommunications Technicians Certificates
 C & G Electrical Installation Work
 C & G Certificate in Technical Communication Techniques
 C & G Radio Amateurs
 MPT General Certificate in Radio Telegraphy
 Audio, Radio and TV Engineering & Servicing
 Electronic Engineering Maintenance, Engineering systems
 Instrumentation & Control systems
 Computer Engineering & Technology
 Electrical Engineering, Installations, Contracting, Appliances
 Self-build radio courses

... or take one of these if your future lies in other fields

GCEO and A Level

Basic foundation for success is a thousand and one careers — recognised by everybody. All Boards — 64 subjects

Building

Tuition for recognised technical qualifications in all fields.

Architecture
 Builders Quantities
 Carpentry, Joinery
 Draughtsmanship
 * Quantity Surveyors
 Clerk of Works
 Heating, Ventilating

Engineering

Theoretical and practical tuition geared either to professional and technical examinations or to vocational (non-exam) courses.

Mechanical, Motor, Diesel, Chemical
 Welding
 Refrigeration
 Draughtsmanship
 Garage Management

Management, Marketing and Business

Instruction in the latest proved principles and techniques used in each highly specialised area.

* Personnel
 * Administrative
 * Works
 * Transport
 Business
 Industrial
 Sales

Marketing

* Advertising
 * Marketing
 * Public Relations
 Sales

Business

* Computers
 * Purchasing
 * Book-keeping
 * Work Study
 Storekeeping
 Small Business Owners

Fire Service

* Promotion and Institute of Fire Engineers
 Police
 * Entrance and Promotion

* Courses for appropriate professional exams available in addition to ICS Diploma courses.

POST TODAY FOR FREE DETAILS

ICS your key to a brighter better future

To: International Correspondence Schools, Dept. 234U, Intertext House, Stewarts Road, London, SW8 4UJ.

Name

Address

Age Occupation

234U

Accredited by the Council for the Accreditation of Correspondence Colleges.

nombrex



**MODEL 42
R.F. SIGNAL GENERATOR
Price £17.50 + V.A.T.**

- Wide Range 150 KHz-300 MHz.
- Accuracy 2%
- R.F. Output 50 millivolts minimum
- A.F. Output approximately 1 volt at 800 Hz
- Fully transistorised circuitry
- Powered by 9V battery
- Provision for external supply

Trade and Export enquiries welcome

Send for full technical leaflets

Post and Packing 35p extra per unit

**NOMBREX (1969) LTD., EXMOUTH, DEVON.
Tel: 03-952 3515**

WW—061 FOR FURTHER DETAILS

INSIST ON VERSATOWER

Acclaimed as the World's leading telescopic tiltover tower in the field of radio communication
 Models from 25' to 120'

Look for the name
STRUMECH

Strumech Engineering Co Ltd
 Coppice Side, Brownhills, Walsall, Staffs

WW—062 FOR FURTHER DETAILS


WHO, WHAT HOW and WHERE?

The busy retailer needs quick answers. This is the book that's got them. In a moment you can put your finger on a manufacturer, wholesaler or service depot; check a specification or a telephone number. The 1973 edition of the Electrical and Electronic Trader Year Book has been thoroughly updated to provide the most comprehensive reference to the trade available. At £2.25 inclusive you can't afford to be without it.

Contents include:

- Legal guide
- Rates of pay
- P.O., government and other licences
- Station guide and contour maps
- Directory of trade organizations
- Specifications (TV, radio, tape recorders, etc.)
- Battery equivalents
- Valves and transistors
- Technical literature
- Wholesalers
- Service depots
- Proprietary names directory
- Buyers' guide
- Trade addresses

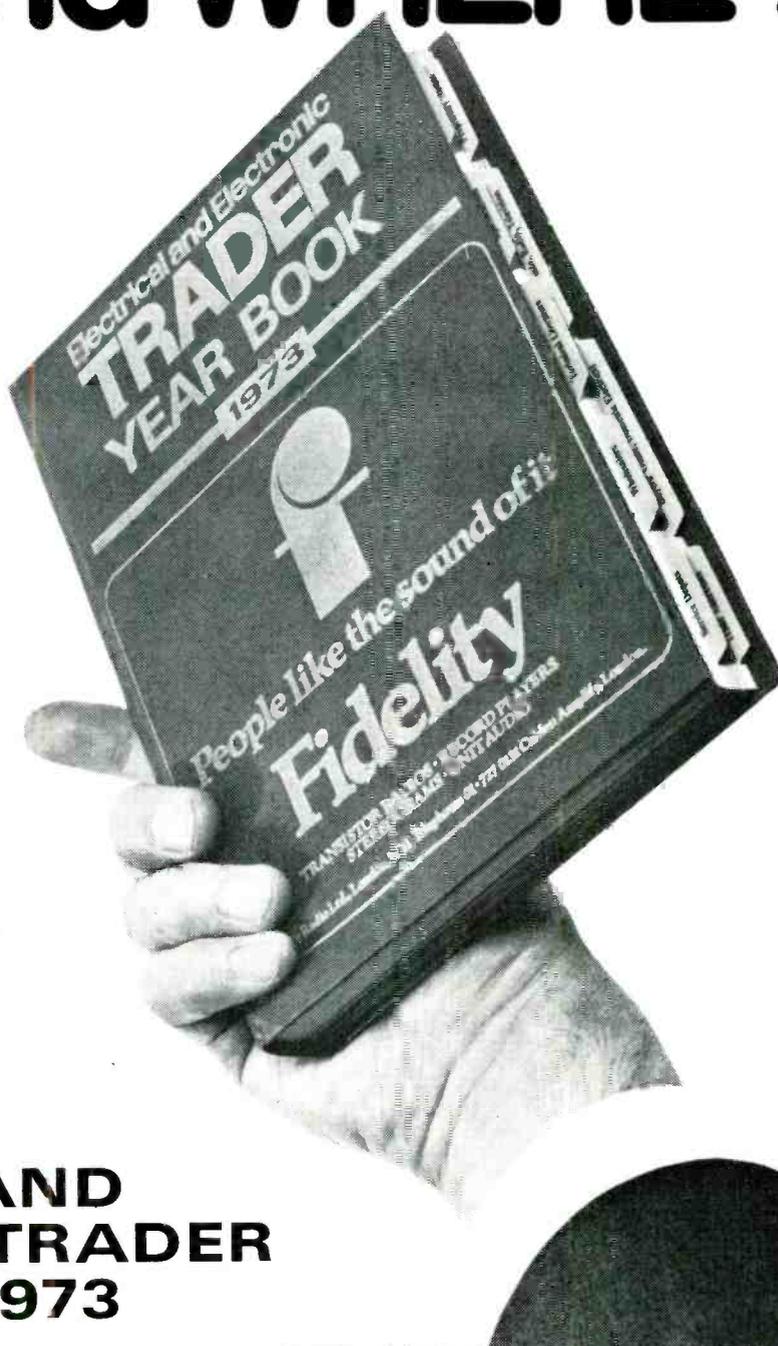ELECTRICAL AND ELECTRONIC TRADER YEAR BOOK 1973



MAIL THIS COUPON NOW

IPC Electrical-Electronic Press Ltd., General Sales Dept., Room 11, Dorset House, Stamford Street, SE1 9LU

Please send me _____ copies of the Electrical and Electronic Trader Year Book 1973. I enclose cheque/p.o. number to the value of _____ (£2.25 per copy inclusive). Cheques made payable to IPC Business Press Ltd.

Name _____

Address _____

Company registered in England. Registered address: Dorset House, Stamford Street, SE1 9LU. Registered number: 522305



Now a very sophisticated Hi-Fi stereo tape recording deck and pre-amp unit from Philips.

3 heads. 3 DC motors. Tip-touch Solenoid operation.
Remote controllable. Every facility.

This is the N4510 – the tape deck from the Philips range of advanced Hi-Fi stereo tape recorders.

It easily surpasses the DIN Hi-Fi standard, and in every detail of styling and construction will satisfy the most critical user. It is ruggedly built, gives you every facility and precision control of sound, and is of such sophisticated design that operation is simple. Here are the most important features:

4 tracks. 3 speeds – $7\frac{1}{2}$, $3\frac{3}{4}$, $1\frac{7}{8}$ ips.

Suitable for stereo and mono recording and playback, multiplay, echo during recording, A-B monitoring.

Three motors – two DC motors for reel drive, one DC capstan motor electronically governed to keep tape speed constant.

Tape tension comparators for constant winding torque.

Three magnetic heads – one each for recording, playback and erase.

Detachable lower head cover for easy editing and cleaning.

For control of transport functions and recording mode, illuminated tip-touch controls are linked to solenoids – giving easier, quieter and more reliable operation.

Remote control unit (extra) with same tip-touch buttons as recorder.

Sliding switches for function selection – selected function illuminated.

Precise sliding faders for two microphones and another signal source.

Separate volume control for each headphone channel.

Recording stand-by (level adjustable with tape stationary).

Two illuminated calibrated VU type meters for recording/playback.

4-digit counter, zero reset, and on/off Autostop to halt tape at pre-determined position.

Reels lockable by means of metal hub locks.

Sockets for headphones and microphones easily accessible at front, concealed under sliding lid.

Removable transparent lid.

Frequency response:

40–20,000 Hz at $7\frac{1}{2}$ ips	} DIN 45 500
40–15,000 Hz at $3\frac{3}{4}$ ips	
60– 8,000 Hz at $1\frac{7}{8}$ ips	

Wow and Flutter less than 0.15% at $7\frac{1}{2}$ ips.

See your Philips dealer for a demonstration. And for a free book on all Philips Hi-Fi stereo tape recorders, write to Philips Electrical Limited, Dept SP, Century House, Shaftesbury Avenue, London WC2H 8AS.

PHILIPS
Simply years ahead.



Surely the best value in variable filters!



Look, for instance, at these three features of the Barr & Stroud solid state EF2.

- Two independent lowpass/highpass filter channels
 - Attenuation slope 36 or 72 dB/octave
 - 6th order response through computer-aided design
- Then add all these other features and we think you will agree the EF2 is worth a closer look.
- Frequency range from 0.1 Hz to 100 kHz in five decades
 - Frequency tolerance $\pm 5\%$ except at range limits
 - Maximum attenuation greater than 75 dB
 - Combined channels provide band pass, band stop or band separation modes

- Mode switching without use of external links
- Digital selection of cut-off frequency giving accurate repeatability
- Response switchable to 'normal', 'narrow', or 'damped' condition
- Up to 20 dB gain available in 'narrow' condition
- Operation from internal power supply or external batteries
- Output protected against short circuit

Price: £450 + VAT

Further details in pamphlet 1652/ available on request.

Barr and Stroud also design and build special filters to individual customer requirements. Extensive use of computer facilities ensures economical and accurate realisation of the desired characteristics.



BARR & STROUD LIMITED

Anniesland, Glasgow, G13 1HZ. Telephone: 041-954 9601 Telex: 778114

Kinnaird House, 1 Pall Mall East, London, SW1P 1RT. Tel: 01-930 1541 Telex: 261877

WW-064 FOR FURTHER DETAILS

£150


DIOTESTOR IN-CIRCUIT TRANSISTOR TESTER



BRITEC LIMITED, 17 Devonshire Road, London SE23 3EN
Tel: 01-699 8844 Telex: 896161

WW-065 FOR FURTHER DETAILS

J E S AUDIO INSTRUMENTATION

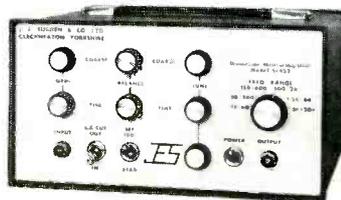

Illustrated the Si452 Distortion Measuring Unit—low cost distortion measurement down to .01% **£30.00**

Si451 **£35.00**
Comprehensive Millivoltmeter
350µ Volts 20 ranges

Si453 **£40.00**
Low distortion Oscillator
sine square RIAA

prices plus VAT

J. E. SUGDEN & CO., LTD. Tel. Cleckheaton (09762) 2501
CARR STREET, CLECKHEATON, YORKSHIRE.

WW-066 FOR FURTHER DETAILS



for the professional

contact **Derek Owen** at 01-874 9054 or Telex 923455

LEEVERS-RICH

EQUIPMENT LIMITED

Agents in Scandinavia, Eastern and Western Europe, Middle East, Africa, Australasia and the Far East.

LEEVERS-RICH EQUIPMENT LIMITED
319 TRINITY ROAD · LONDON SW18 3SL
Telephone 01 874 9054 · Telex 923455
Cables LEEMAG LONDON



WW-067 FOR FURTHER DETAILS

COMPREHENSIVE HOME CONSTRUCTOR KITS
AS SPECIFIED IN THE P.E. RONDO
COMPLETE QUADRAPHONIC HI-FI SYSTEM

CBS SQ* MATRIX DECODER

*REGD. CBS INC

COMPLETE KIT **£8-00** POST FREE INCLUDING CBS LICENCE FEE+80p V.A.T.

PREAMPLIFIER BOARD

COMPLETE KIT **£3-00** POST FREE+30p V.A.T.

**MASTER/VOLUME TONE CONTROLS/4 CHANNEL
BALANCE CONTROL BOARD**

COMPLETE KIT **£8-50** POST FREE+85p V.A.T.

POWER AMPLIFIER BOARDS AND HEATSINKS
 (EACH BOARD CONTAINS A STEREO PAIR OF AMPLIFIERS)

COMPLETE KIT PER BOARD **£7-50** POST FREE+75p V.A.T.

ALL OTHER KITS AND COMPONENTS USED IN THE P.E. RONDO WILL BE AVAILABLE AS THEY APPEAR IN THE SERIES IN "PRACTICAL ELECTRONICS".
 KITS ARE COMPLETE IN EVERY DETAIL (RIGHT DOWN TO THE SOLDER) AND USE ONLY TOP QUALITY COMPONENTS AND FIBREGLASS P.C.Bs.

TRADE ENQUIRIES WELCOME

SONAX ELECTRONICS

SPENCER HOUSE, BRETENHAM ROAD, EDMONTON
 LONDON, N.18 TEL. 01-807 5544


Please send me:

- | | | |
|---------------------------------|--------------------------|-----------------------|
| GBS SQ DECODER | <input type="checkbox"/> | CHEQUE |
| PREAMPLIFIER BOARD | <input type="checkbox"/> | P.O. |
| MASTER VOL/TONE/4/CHANNEL BOARD | <input type="checkbox"/> | MONEY ORDER |
| POWER AMPLIFIER BOARD(S) | <input type="checkbox"/> | MONEY ENCLOSED £..... |

Name

Address

BLOCK CAPITALS PLEASE
 WW10

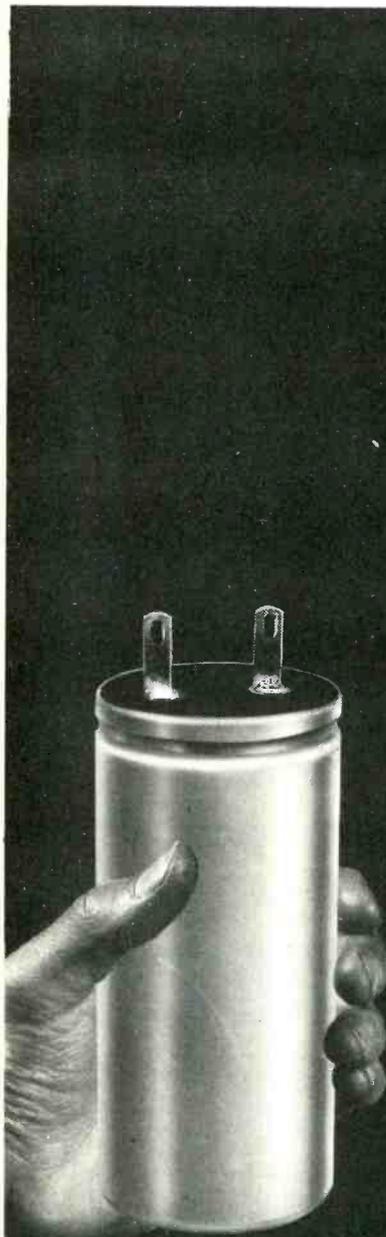

Get to grips
with your problem
by using WCL
electrolytic
capacitors
NOW!

BLORE-BARTON LTD
Reedham House
Burnham Bucks
telephone Burnham 5524
telex 847322



THERMOCOUPLE POTENTIOMETER

TYPE P4/E

FOR

**TEMPERATURE MEASUREMENT
RECORDER CALIBRATION**



WITH
**ELECTRONIC
NULL
DETECTOR**

EX-STOCK

This is a robust portable instrument suitable for temperature measurement with all thermocouples and for calibrating the indicating instruments that are used with thermocouples.

Two ranges are provided: 0-105mV for use with base metal couples, and 0-21 mV for precious metal couples.

An auxiliary potential divider included provides an adjustable potential which can be injected into external instruments for calibration purposes.

**CROYDON PRECISION
INSTRUMENT CO.
HAMPTON ROAD, CROYDON
CR9 2RU**

Telephone: 01-684 4025 and 4094

Convert your stereo HI-FI to a Quadraphonic Sound System!

FREE 2 Datacards

first pair of a set of three pairs

Free in the next three issues of PRACTICAL WIRELESS will be a set of invaluable Datacards giving you at-a-glance, technical information that is a must to all radio and electronics enthusiasts. This month's free cards are - 1. Standard Resistor Values and Colour Code
2. Common Capacitor Values and Colour Code
The second pair will be given away in November issue and the third pair in the December issue.

NEW SERIES! EXPERIMENTAL WORKSHOP

First of a new series offering a new approach to learning how circuits operate by making up simple working projects and experimenting with the component values to alter their function.



Build the PW PROJECT Q4

Now, at very low cost, you can convert your stereo system to reproduce quadraphonic sound! Starting in this month's PRACTICAL WIRELESS is a great new series which will show you how to build an exclusively designed decoder.

- CD-4 Victor-RCA discrete system
- RM Regular Matrix surround sound
- QS Sansui system
- SQ CBS system

Q4 is a first time exclusive to PRACTICAL WIRELESS that enables you to play any current stereo or quadraphonic recording through your hi-fi system.

OCTOBER ISSUE OUT NOW - 20p.

STEREO IC DECODER

HIGH PERFORMANCE PHASE LOCKED LOOP
(as in 'W.W.' July '72)

MOTOROLA MC1310P EX STOCK DELIVERY
SPECIFICATION

Separation: 40dB 50Hz-15kHz. Distortion: 0.3%
I/P level: 560mV rms O/P level: 485mV rms per channel.
Input Impedance: 50kΩ. Power requirements: 8-16V at 16mA

Will drive up to 75mA stereo 'on' lamp or LED.

KIT COMPRISES FIBREGLASS PCB
(Roller tinned), Resistors, I.C., Capacitors,
Preset Potm. & Comprehensive Instructions

LIGHT EMITTING DIODE (Red)
Suitable as stereo 'on' Indicator. For above
with panel mounting clip and Instructions

MC1310P only £2.77 plus p.p. 6p

ONLY WHY PAY MORE?
£3.40 post free.

ONLY 29p plus p.p.

NOTE
As the supplier of the first MC1310P decoder kit, of which we have sold literally thousands, our customers can benefit from our wide experience.

V.A.T.
From April 1st add V.A.T. at the standard rate to all prices

FI-COMP ELECTRONICS
BURTON ROAD, EGGINGTON, DERBY, DE6 6QY

WW-071 FOR FURTHER DETAILS

HYBRID AUDIO CONTROL MODULE MODEL HM80



- ★ 24 Pin D.I.L. Package.
- ★ Built-in coupling and decoupling capacitors.
- ★ Zero to 40 db GAIN.
- ★ Zero to 40 db ATTENUATION.
- ★ 2 Hz to 200 KHz BANDWIDTH
- ★ 50 K input and 600 Ohms output impedance.
- ★ 4.5 to 24 Volts neg. ground supply.
- ★ Excellent quality and reliability.
- ★ Extensive application report.
- ★ Free of charge design for your particular application.

THE IDEAL WAY FOR BUILDING SUBSONIC, AUDIO & SUPERSONIC PROFESSIONAL EQUIPMENT INVOLVING THE LEAST POSSIBLE EXTERNAL COMPONENTS, SUPERIOR QUALITY, RELIABILITY, AND EASY MAINTENANCE.

APOLLO ELECTRONICS
96 MILL LANE, LONDON N.W.6 1NQ
Tel: 01-794 8326

WW-072 FOR FURTHER DETAILS



The New Loudspeaker Range...

The sound of music, from the lowest frequency to the highest is now brought to the connoisseur of quality in sound reproduction with the new, Vitavox Power Loudspeaker Range.

The Range blends four superb units into one matchless composite, or each element as a separate unit available for use with other systems. The range gives exceptional quality of sound reproduction and handles up to 100 watts of musical power. The four units are: a High Power, High Frequency Pressure Unit and a High Power Bass Loudspeaker, each designed to give increased power handling capacity without sacrificing either efficiency or frequency response; a High Frequency Dispersive Horn, designed for use with the Pressure Unit - matching accurately the Unit's output characteristics and giving superb sound dispersion; a High Power Dividing Network for use in both high and low power systems and which ensures correct allocation of the frequency spectrum between high and low frequency units.

Carrying the Vitavox stamp of quality, this is the Range which brings you...

Please send me further information on your product range V3
Name _____
Company _____
Address _____

The Great Sound of Vitavox



Westmoreland Road, London NW9 9RJ Telephone: 01-204 4234

WW-073 FOR FURTHER DETAILS



If you're thinking of looking for trouble do it with this Special Extra 4-page Pull-out Supplement

Presented as a special extra to all its readers, TELEVISION has produced this basic colour TV faults guide – the first of its kind ever devised for a British magazine.

An outstanding feature of the supplement is the reproduction of full-colour photographs taken direct from the television screen, showing basic colour television fault conditions.

Faults are explained and guidance is given on where to look for the trouble in the receiver.

Other special features include "110°" COLOUR TV CHASSIS – a look at the new techniques involved in receivers for 110° colour tubes ... PLUS up-to-the-minute coverage of television technology in depth.


Special emphasis on colour and servicing techniques together with the latest advances and developments ... equipment, components, and instruments.

TELEVISION

MAGAZINE

OCTOBER ISSUE ON SALE – NOW! 20p
ORDER FROM YOUR NEWSAGENT TODAY

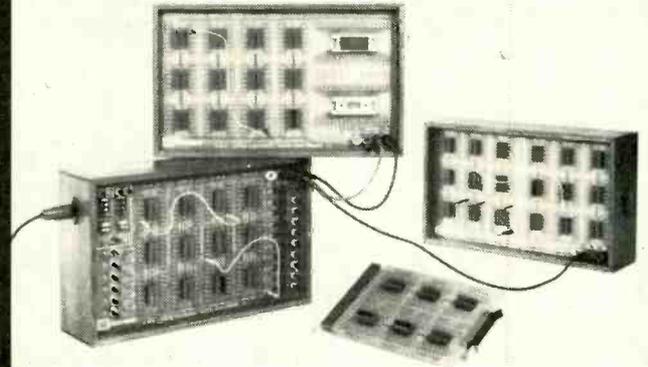IC PATCHBOARDS and plug-in cards low cost, high performance units



Limrose's new family of low-cost universal mounting boards, plug-in cards and breadboarding systems is useful for development work, device testing and circuit evaluation.

Delivery is usually ex-stock. For prices and other information please contact



LIMROSE ELECTRONICS LIMITED
8-10 Kingsway, Altrincham,
Cheshire WA14 1PJ.

limrose Tel. 061 928 8063

WW—074 FOR FURTHER DETAILS

TWO NEW SOLDER SIPPERS MAKE DESOLDERING QUICK & EASY



Maxi-Super HT 1810 and Maxi-Mini HT 1800 Solder Sippers

Designed for use when working or re-working P.C. Boards. Permits removal of molten solder from Multi-leg components, enabling easy extraction. The solder is 'sipped' through the nozzle, and automatically ejected when the instrument is next used. A Swiss precision instrument manufactured to a high degree of accuracy.

The anti-corrosive outside casing has a knurled finish for more positive grip, and encases plated internal parts.

The Maxi-Super has been designed with a 3.5 kg. spring action recoilless plunger, whilst the Maxi-Mini with its conveniently shaped operating button, has a 2.5 kg. spring action plunger, protected by a channel guard. Both models have been designed with an easy-to-replace 'dupont' teflon screw-in nozzle.



Longs Ltd.
Hanworth Lane
Trading Estate
Chertsey Surrey
KT16 9LZ.

PLEASE FORWARD without obligation further details. PLEASE SUPPLY Maxi-Super HT 1810 at £6.60 PLEASE SUPPLY Maxi-Mini HT 1800 at £4.95

I enclose cheque value £ _____

NAME _____ POSITION _____


COMPANY _____

ADDRESS _____

SIGNED _____

Prices include VAT Reg. England 68496

WW—076 FOR FURTHER DETAILS

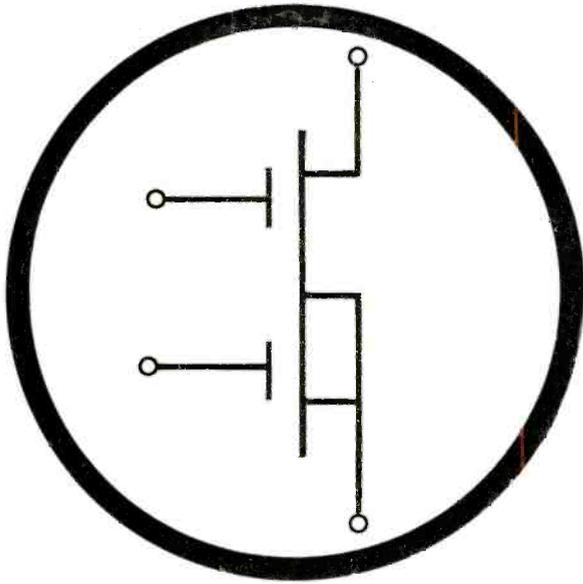

N-CHANNEL DUAL-GATE MOSFETS FROM STOCK.

MEM 616 series; MEM 630 series dual gate MOSFETS with gate protection diodes available now. 20p to 29p (100 up).

Another 122 MOSFETS available. Will second source RCA, Motorola, Siliconix, and Texas types at competitive prices.

General Instrument Microelectronics Limited,
57-61 Mortimer Street, London W1N 7TD.
Telephone: 01-636 2022




Distributors:

Semicomps Ltd. 01-903 3161, Semicomps (Northern) Ltd. Kelso 2366
SDS Components Ltd. Portsmouth 65311, Semiconductor Specialists W. Drayton 46415

Agents in France, Germany, Italy, Belgium, Holland, Denmark, Sweden, Norway, Finland, Spain, Austria, Israel.

WW—077 FOR FURTHER DETAILS

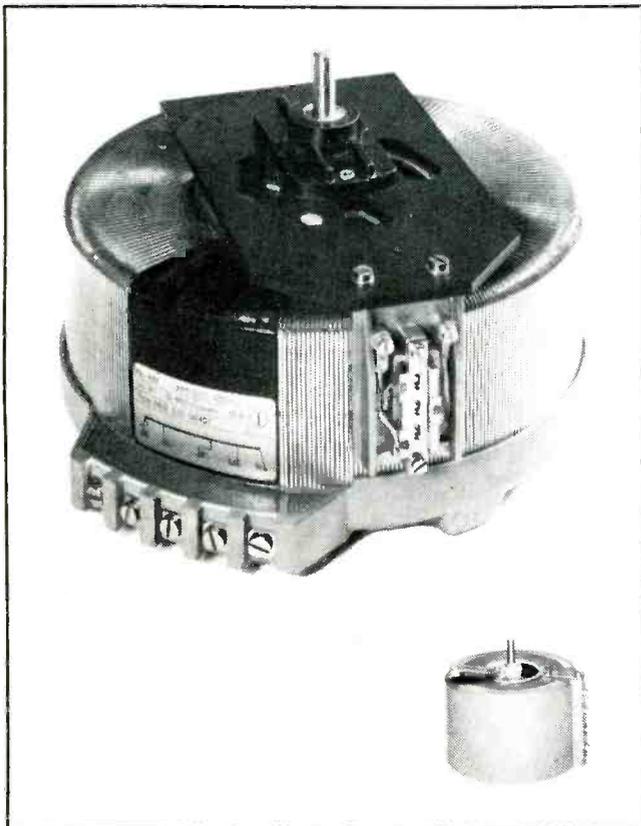Philips Variable Transformers and Stabilisers



**If You Use Variable Transformers Contact Us For Low Prices
And Ex Stock Delivery.**

PHILIPS VARIABLE TRANSFORMERS

- A choice of 280 models with ratings from 0.5 to 132 amps (0.16 to 31.8 KVA) 50—400Hz.
- Skeleton, encapsulated open and enclosed models.
- Single and three phase manual or motorised with traverse times from 6 secs to 5 days.
- Silver alloy plated track with long life floating brushes.
- Laboratory models with meters, fuses and carrying handles.

PHILIPS STABILISERS

- A choice of over 80 models with ratings from 0.29 to 81.0 KVA.
- Open or enclosed models.
- Adjustable output.
- Stability ± 1 volt.
- Single or three phase with single or three phase sensing.
- No wave form distortion.
- Unaffected by load variations.

RILTON ELECTRONICS LIMITED
13 Harecombe Rise, Crowborough, Sussex.



WW—078 FOR FURTHER DETAILS

From Goldring. New support for the belief that what goes into a record ought to come out of it.

The Theory is perfectly simple.

A good cartridge should take from a record all the subtle shades of original sound that are stored there, and re-create them for your enjoyment.

The Practice is a little more difficult.

Now Goldring bring the ideal closer with the new 820 series.

A brand new family of cartridges that builds on the advances already achieved by the Goldring 800 series. Providing cartridges that are not only capable of making the most of all that good recording can offer now, but have the capacity to keep pace with new developments in the art of quality recordings.

The 820 series retains the true transparency of sound and the true transduction techniques of earlier designs.

It brings advances in every aspect of design.

The small low-mass diamond point which is mounted on a new type of specially polished lightweight aluminium tube, combined with the new visco-elastic material used for the pivot pad, makes for greater tracking ability.

A special 'tie wire' minimises fore and aft stylus movement, reducing non-linear distortion to a minimum.

The total effect is a cartridge that, other equipment being equal, can narrow almost to vanishing point the difference between the original recording and the sound that comes out of your speakers.

There are three models in the range. The 820 with spherical stylus. The 820E and 820 Super E, both with spheri-radial styli. Write for details and full specifications.

And satisfy yourself that 'what goes in comes out'.

The 820 - one of the models in the new range.
Performance characteristics:
Sensitivity @ 5 cm/sec - 1 KHz: 5mV.
Separation @ 1 KHz: 20dB.
Recommended playing wt. 2 grammes.
Stylus point radius: .0006" 15µ.
Frequency range: 20Hz - 20KHz.



The new 820 series

The expert's cartridge by **Goldring** ©

Goldring Limited, 10 Bayford Street, Hackney, London E8 3SE. Tel: 01-985 1152

WW-079 FOR FURTHER DETAILS

TEST PROBE

for logic circuits



Each **£9.00**
including P.P.+VAT
Discounts for quantity

- ★ High-Low Level Probe (2-colour indication)
- ★ Uses L.E.D.
- ★ Reverse Pole Protected
- ★ Very fast response
- ★ 50 nano seconds
- ★ Up to 12 MHz

Still available at **£5.50** each
incl. P.P.+VAT
Quantity discount!

Prober Size LED Applied
LOGIC TESTER
For use with DTL, TTL and other pulse circuits
Response frequency DC to 12 MHz

JH Associates Ltd.
Cricketfield Lane,
Bishop's Stortford, Herts.

Telephone: 0279-56347 Telex: 81675 JAYLAMPS STORT

WW-081 FOR FURTHER DETAILS

VARI-STAT

THERMOSTATIC SOLDERING IRON

HIGH PRODUCTION MINIATURE
MODEL D. 50 WATT

Weight 2 oz.
Heating time 50 secs.
Bit Sizes $\frac{1}{16}$, $\frac{3}{32}$, $\frac{1}{8}$, $\frac{3}{16}$, $\frac{1}{4}$ "
Nickel or Iron Plated Voltage 250 to 12 volts
Price **£4**

HIGH PRODUCTION INSTRUMENT
MODEL H. 150 WATT

Weight 6 oz.
Heating time 1 min. 45 secs.
Bit Sizes $\frac{3}{16}$, $\frac{1}{4}$, $\frac{3}{8}$, $\frac{7}{16}$ "
Nickel or Iron Plated, Voltage 250 to 12 volts
Price **£5.75**

OTHER VARI-STAT IRONS:—

Miniature Model M 50 watt Push-in Bits $\frac{1}{32}$, $\frac{1}{16}$, $\frac{3}{32}$ "
Instrument Model B 70 watt Bit Size $\frac{11}{64}$ "
Industrial Model I 500 watt Bit Size $\frac{5}{8}$ "

Model D and H now incorporate a modified bit which can be split open in the event of seizure and allows the bit to be removed without damage to the element block.

CARDROSS ENGINEERING CO., LTD.
Woodyard Road, Dumbarton

Phone: Dumbarton 62655



MINIATURE IRON (Half Size)

WW-082 FOR FURTHER DETAILS

Vortexion

50/70 WATT ALL SILICON AMPLIFIER
WITH BUILT-IN 4-WAY MIXER USING F.E.T.s.

This is a high fidelity amplifier (0.3% intermodulation distortion) using the circuit of our 100% reliable 100 Watt Amplifier with its elaborate protection against short and overload, etc. To this is allied our latest development of F.E.T. Mixer Amplifier, again fully protected against overload and completely free from radio breakthrough.

The mixer is arranged for 2-30/60Ω balanced line microphones, 1-HiZ gram input and 1-auxiliary input followed by bass and treble controls. 100 volt balanced line output or 5/15 Ω and 100 volt line.

50/70 WATT ALL SILICON AMPLIFIER WITH BUILT-IN 5-WAY MIXER USING F.E.T.s.

This is similar to the 4-way version but with 5 inputs and bass cut controls on each of the three low impedance balanced line microphone stages, and a high impedance (10 meg) gram stage with bass and treble controls plus the usual line or tape input. All the input stages are protected against overload by back to back low self capacity diodes and all use F.E.T.'s for low noise, low intermodulation distortion and freedom from radio breakthrough. A voltage stabilised supply is used for the pre-amplifiers making it independent of mains supply fluctuations and other stabilised supply for the driver stages is arranged to cut off when the output is overloaded or over temperature. The output is 75% efficient and 100V balanced line or 8/16Ω output are selected by means of a rear panel switch which has a locking plate indicating the output impedance selected. The mixer section has an additional emitter follower output for driving a slave amplifier, phones or tape recorder, output .3V out on 600 ohms upwards.


100 WATT ALL SILICON AMPLIFIER. A high quality amplifier with 8 ohms-15 ohms or 100 volt line output for A.C. Mains. Protection is given for short and open circuit output over driving and over temperature. Input 0.4 V on 100K ohms.

THE 100 WATT MIXER AMPLIFIER with specification as above is here combined with a 4 channel F.E.T. mixer, 2-30/60Ω balanced microphone inputs, 1-HiZ gram input and 1-auxiliary input with tone controls and mounted in a standard robust stove enamelled steel case. A stabilised voltage supply feeds the tone controls and pre amps, compensating for a mains voltage drop of over 25% and the output transistor biasing compensates for a wide range of voltage and temperature. Also available in rack panel form.


CP50 AMPLIFIER. An all silicon transistor 50 watt amplifier for mains and 12 volt battery operation, charging its own battery and automatically going to battery if mains fail. Protected inputs, and overload and short circuit protected outputs for 8 ohms-15 ohms and 100 volt line. Bass and treble controls fitted.

Models available with 1 gram and 2 low mic. inputs, 1 gram and 3 low mic. inputs or 4 low mic. inputs.

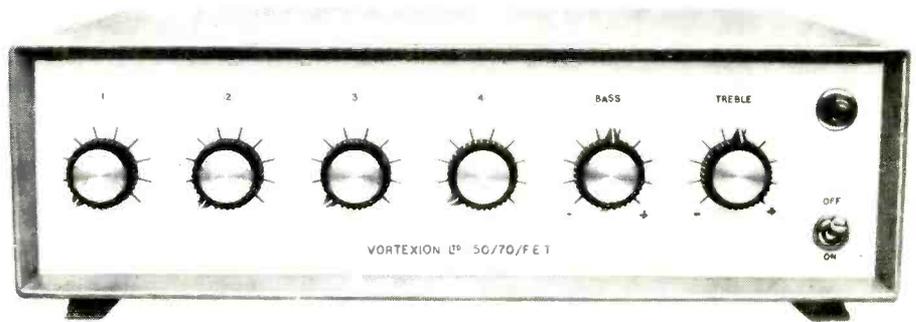200 WATT AMPLIFIER. Can deliver its full audio power at any frequency in the range of 30 c/s-20 Kc/s ± 1 dB. Less than 0.2% distortion at 1 Kc/s. Can be used to drive mechanical devices for which power is over 120 watt on continuous sine wave. Input 1 mW 600 ohms. Output 100-120 V or 200-240 V. Additional matching transformers for other impedances are available.



F.E.T. MIXERS and PPMs.

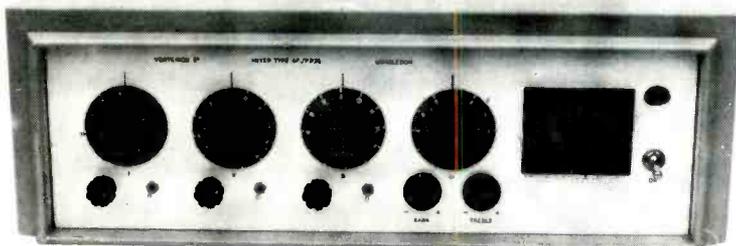

Since we have been supplying professional mixers for 25 years we have delayed the introduction of solid state units until they were at least as good as their valve counterparts. (Which will continue where required.)

The various sections of the FET mixers and BBC type PPM's have been performing successfully for several years in other equipments with complete reliability. The PPM also uses an FET in its time constant circuit so that polyester capacitors can be used. The response from the 600Ω output (25Ω source impedance) is level 20 Hz to over 30 kHz with very low intermodulation distortion to zero level + 12dB. The input signal voltage range is over twice that of the valve unit and the noise at least halved.

VORTEXION LIMITED,
Telephone: 01-542 2814 and 01-542 6242/3/4

257-263 The Broadway, Wimbledon, S.W.19
Telegrams: "Vortexion, London S.W.19"

WW-095 FOR FURTHER DETAILS

www.americanradiohistory.com

Radio and Line Transmission, Vol. 2—2nd Edition

George L. Danielson MScTech, BSc, CEng, MIEE and Ronald S. Walker CEng, MIERE

The second in a series of three books written to meet the needs of the technician specialising in Radiocommunication in the City and Guilds Telecommunication Technicians' Course. The volume covers the revised syllabus of *Radio and Line Transmission B*, and is suitable for third-year students on a part-time course or for second-year full-time students. Though written primarily for students on technician courses, the work will provide a background for those engaged in more advanced studies.

304pp illustrated 0 592 00067 2 1972 (2nd Impression 1972) £1-60

Radio and Electronic Laboratory Handbook—8th Edition

M. G. Scroggie BSc, CEng, FIEE

This completely revised edition of a book which has been a standard work of reference within its field for over thirty years contains much useful new information. There are new or extended sections on microelectronics, integrated circuits and operational amplifiers and a fuller treatment of the use of transistors in instrumentation. SI units are now used throughout the book.

628pp illustrated 0 592 05950 2 1971 (2nd Impression 1972) £5-25

Operational Amplifiers

G. B. Clayton BSc, FInstP

This text is designed to provide an insight into the capabilities and applications of the modern operational amplifier. As it is simpler and potentially more reliable to work with operational amplifiers than using only the traditional discrete components, the non-specialist should find it easier to design his own measurement systems if he makes use of them, either in modular or in integrated circuit form. Practising instrumentation engineers and research workers using electronic instrumentation techniques will all find the insights afforded by the text of great practical help in their respective programmes.

244pp illustrated 0 408 70202 8 1971 £3-50

110 Integrated Circuit Projects for the Home Constructor

R. M. Marston

Integrated circuits are the most important new semiconductor devices to have been developed within the last decade. They are compact, easy to use and less expensive than their discrete transistor-resistor equivalents. This work gives an entirely practical introduction to these devices by describing one hundred and ten constructional projects in which they can be used. The book will be of great value to and a fruitful source of ideas for the professional engineer, the student and the amateur constructor. Like the author's other books, such as the successful *20 Solid State Projects for the Home* and *20 Solid State Projects for the Car and Garage*, this volume is written in a clear and straightforward manner which makes this important subject accessible even to those with little technical knowledge.

138pp illustrated 0 592 00063 X cased 1971 £1-80 0 592 00058 3 limp £1-20

Available from leading booksellers or **The Butterworth Group**

88 Kingsway, London WC2B 6AB. Showrooms and Trade Counter, 4-5 Bell Yard, London WC2



Purpose-built servo and actuator systems using standard components




Low Inertia DC motor

Typical precision gears


McLennan have considerable experience in the solution of actuator and servo problems using synchronous, stepping and D.C. motor techniques as well as solenoid-powered types. An important facet of our skill lies in purpose-designing around standard components for speed and economy of building.



Control Amplifier

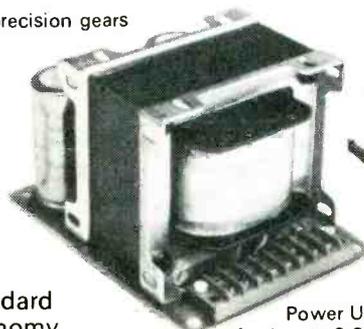

Power Unit to feed up to 3 Servos

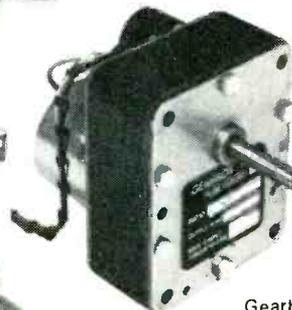

Gearhead with integral feed-back Potentiometer

The illustration shows a selection of modules from the McLennan standard range which are available as individual items or can be supplied engineered to custom-built systems.

Such a system could be complete in itself or form part of your own design.

Typical examples include:

Camera positioning: Plotting Devices:
Self-steering Systems: Signal-seeking Aerial Drives:
Professional Tape Drives:
Automated Production Lines.

Stimulation of output position or velocity may be by optical, radio, electrical, mechanical, pneumatic or hydraulic signals.




McLennan Engineering Ltd

Control Systems and Components

Kings Road, Crowthorne, Berkshire. Tel: Crowthorne 5757/8.

THE NEW NELSON-JONES FM TUNER

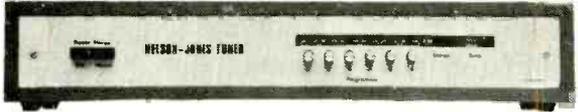

**PUSH-BUTTON VARICAP DIODE TUNING
(6 Position)**

Exclusive Designer Approved Kits

The Nelson-Jones Turner is now available as a **complete kit** with all Metalwork, Printed and anodised Front Panel and Teak veneered cabinet. A Six Position push-button unit is used with each pre-selector button fully tuneable with its own scale and pointer and incorporating AFC disable for fine tuning.


Provision is also made for a Stereo LED, (RED or GREEN). Stereo Decoder, Internal PSU and Fine Tuning indication (Meter or LED type). Push-button switches are also used for Stereo Mute and Mains On/Off. All sockets, board standoffs and panel mounting fuse are supplied. The tuner is available in two gain versions, and our **alignment service** is available to customers without access to a signal generator.

Prices for **complete kits** start at **£23.75** (mono) plus p.p. 45p., and of course all components are available separately.

Please send large SAE for our latest price lists which detail all of the many options and special low prices for complete kits. All our other products remain available e.g. The Portus and Haywood Phase Locked Stereo Decoder Kit.

PLEASE NOTE. Existing tuners are readily convertible and kits /parts are available for this purpose.

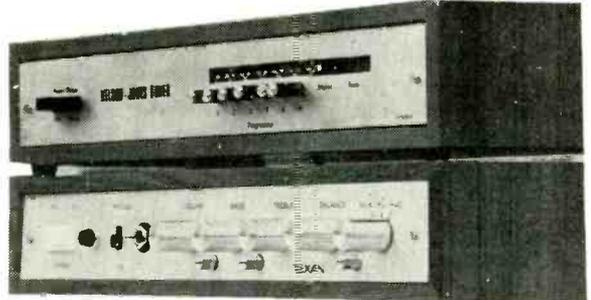TEXAN AMPLIFIER. We have designed the tuner case and metalwork to match the Texan amplifier (see photograph). Complete designer approved Texan kits are available at **£28.50** plus p.p. 45p including a Teak Sleeve.



You can order these goods by Telephone on Access. Simply quote your Access Number

OPTO-DEVICES

Panel mounting LED's.

RED	1-9	29p	10-24	23p
GREEN	1-9	69p	10-24	59p

7 Sec. LED's

0.325" RH Dec Point.
Common Anode 1-4 £2.46; 5-24 £2.10.
Common Cathode 1-4 £2.33; 5-24 £1.93.
7447 Dec Driver £1.30 (C.A.).

V.A.T. Please add V.A.T. at 10% to all prices for U.K. orders.

INTEGREX LIMITED, P.O. Box 45, Derby, DE1 1TW

Phone Repton (028389) 3580

cavern electronics

We have moved to:

**94 STRATFORD ROAD, WOLVERTON,
MILTON KEYNES, BUCKS. MK12 5LU**

★ ★ ★
RETAIL COUNTER NOW OPEN

Mail Order Service for those who cannot visit us

Please send stamp for our Component Lists

WW-085 FOR FURTHER DETAILS

Audio Connectors



Broadcast pattern jackfields, jackcords, plugs and jacks


Quick disconnect microphone connectors
Amphenol (Tuchel) miniature connectors with coupling nut

Hirschmann Banana plugs and test probes
XLR compatible in-line attenuators and reversers

Low cost slider faders by Ruf

Future Film Developments Ltd.
90 Wardour Street,
London W1V 3LE
01- 437 1892/3

WW-086 FOR FURTHER DETAILS

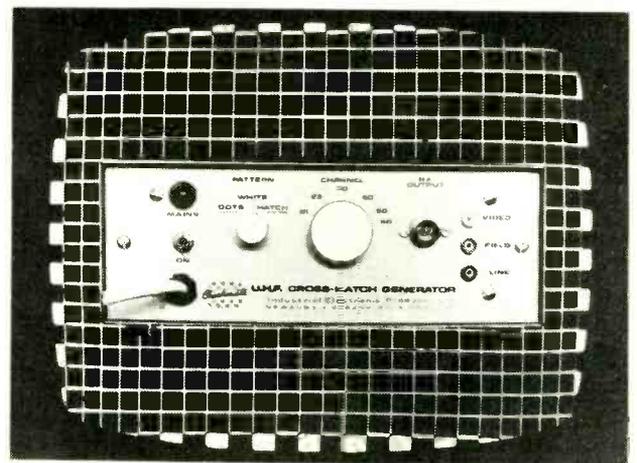

CHECKMATE PROFESSIONAL CROSSHATCH GENERATOR

The unique test card edge enables the completely accurate alignment of colour and monochrome receivers without the need of a broadcast test pattern. The crystal derived patterns and waveforms make extensive use of digital i.c. logic. The stable and reliable 625 line high resolution patterns are crosshatch dot and white field, full 2:1 interlace with complete synchronising and blanking waveforms. Continuous tuning over all channels in each band B.N.C. video outputs into 75 ohms available for CCTV use on all models.

Model CCH-1 UHF Bands IV & V	£69.00
Model CCH-V VHF Band 1	£70.00
Model CCH-V2 VHF Band 11	£70.00
Model CCH-V3 VHF Band 111	£70.00

U.K. Customers add VAT. Overseas Customers CIF at cost.

Send for further information from the sole agents:

MANOR ENGINEERING,
The School House, Crookham Common,
Newbury, RG15 8EJ, England.
Telephone: Headley 487.
Telegrams: MANORENG, NEWBURY.

WW-087 FOR FURTHER DETAILS



This is the D75

- Lightweight
- 50MHz bandwidth at 5mV/div
- 1mV/div at 15MHz
- 3% accuracy
- Mixed sweep
- Calibrated sweep delay
- Gated trigger
- Bright 8x10cm display

A new Dual Trace, 50MHz Portable Oscilloscope for £420

(Exclusive of V.A.T.)

Yes indeed! A 50MHz dual-trace instrument costing you only £420. And it's portable too – the lightweight, comfortable-to-carry, take-it-anywhere kind of portable. Developed by engineers for engineers this newcomer from Telequipment offers unprecedented

value when compared with similar 50MHz instruments.

The outstanding specification of the D75 includes a wide-range dual timebase incorporating sweep intensifying, delaying, mixed sweep and single-shot facilities, an 8 x 10 cm CRT operating at

15kV, and dual-trace operation in alternate and chopped modes with 5 mV/div all the way up to 50MHz.

Write or telephone now for the specification and a demonstration, and prove for yourself that the D75 is the oscilloscope for you.

Tektronix U.K. Ltd.
Beaverton House, P.O. Box 69,
Harpenden, Herts.
Telephone: Harpenden 61251
Telex: 25559

TELEQUIPMENT 

WW-100 FOR FURTHER DETAILS


Wireless World

Electronics, Television, Radio, Audio

Sixty-third year of publication

October 1973

Volume 79 Number 1456

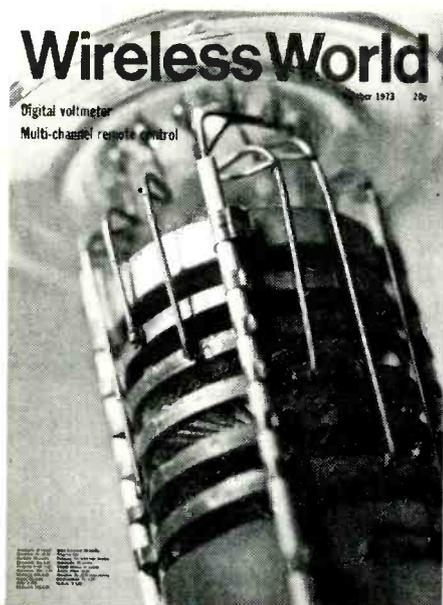

This month's cover picture shows part of the internal structure of an image intensifier made by Cathodeon. (Photographer Paul Brierley)

Contents

- 469 **The Educated Ear**
- 470 **Dual-polarity Digital Voltmeter** by *A. J. Ewins*
- 476 **H. F. Predictions**
- 477 **News of the Month**
 - Miniature TV camera
 - New laser-induced effect
 - Berlin radio and TV shows
- 479 **Multi-channel Proportional Remote Control** by *M. F. Bessant*
- 482 **Books Received**
- 483 **Independent Local Radio**
- 485 **Electronic Sound Synthesizer — 3** by *T. Orr and D. W. Thomas*
- 491 **An Approach to Amplifier Design — 3** by *J. R. Stuart*
- 494 **Sixty Years Ago**
- 495 **Circards — 10: Micropower circuits** by *J. Carruthers, J. H. Evans, J. Kinsler & P. Williams*
- 497 **Letters to the Editor**
 - Tuner front-end devices
 - Record equalization
 - Breakdown of c.m.o.s. devices
- 499 **Communications 74**
- 500 **October Meetings**
- 501 **The Realm of Microwaves — 6** by *M. W. Hosking*
- 505 **Literature Received**
- 506 **Total Communications — 2** by *E. J. Gargini*
- 510 **Presenting Maintenance Information** by *S. W. Amos*
- 514 **Books Received**
- 515 **Circuit Ideas**
- 516 **World of Amateur Radio**
- 517 **New Products**
- 522 **Real and Imaginary** by *"Vector"*
- A110 **APPOINTMENTS VACANT**
- A138 **INDEX TO ADVERTISERS**

In our next issue

(publication date October 15)

Model railway control system, using different d.c. levels, provides control of speed, locomotive whistle and coach interior illumination.

Multi-flash trigger unit initiates flashes at equal intervals from milliseconds to seconds for sequence photography.

ibpa

International Business
Press Associates

I.P.C. Electrical-Electronic Press Ltd

Managing Director: George Fowkes

Administration Director: George H. Mansell

Publisher: Gordon Henderson

© I.P.C. Business Press Ltd, 1973

Brief extracts or comments are allowed provided acknowledgement to the journal is given.

Price 20p. (Back numbers 40p.)

Editorial & Advertising offices: Dorset House, Stamford Street, London SE1 9LU.


Telephones: Editorial 01-261 8620; Advertising 01-261 8339.

Telegrams/Telex, Wiworld Bisnespres 25137 London. Cables, "Ethaworld, London S.E.1."

Subscription rates: *Home*, £4.35 a year. *Overseas*, 1 year £5; 3 years £12.50 (U.S.A. & Canada 1 year \$13, 3 years \$32.50) Student rates: Home 1 year £2.18, 3 years £5.55. Overseas, 1 year £2.50; 3 years £6.25 (U.S.A. & Canada 1 year \$6.50, 3 years \$16.25).

Distribution: 40 Bowling Green Lane, London EC1R 0NE. Telephone 01-837 3636.

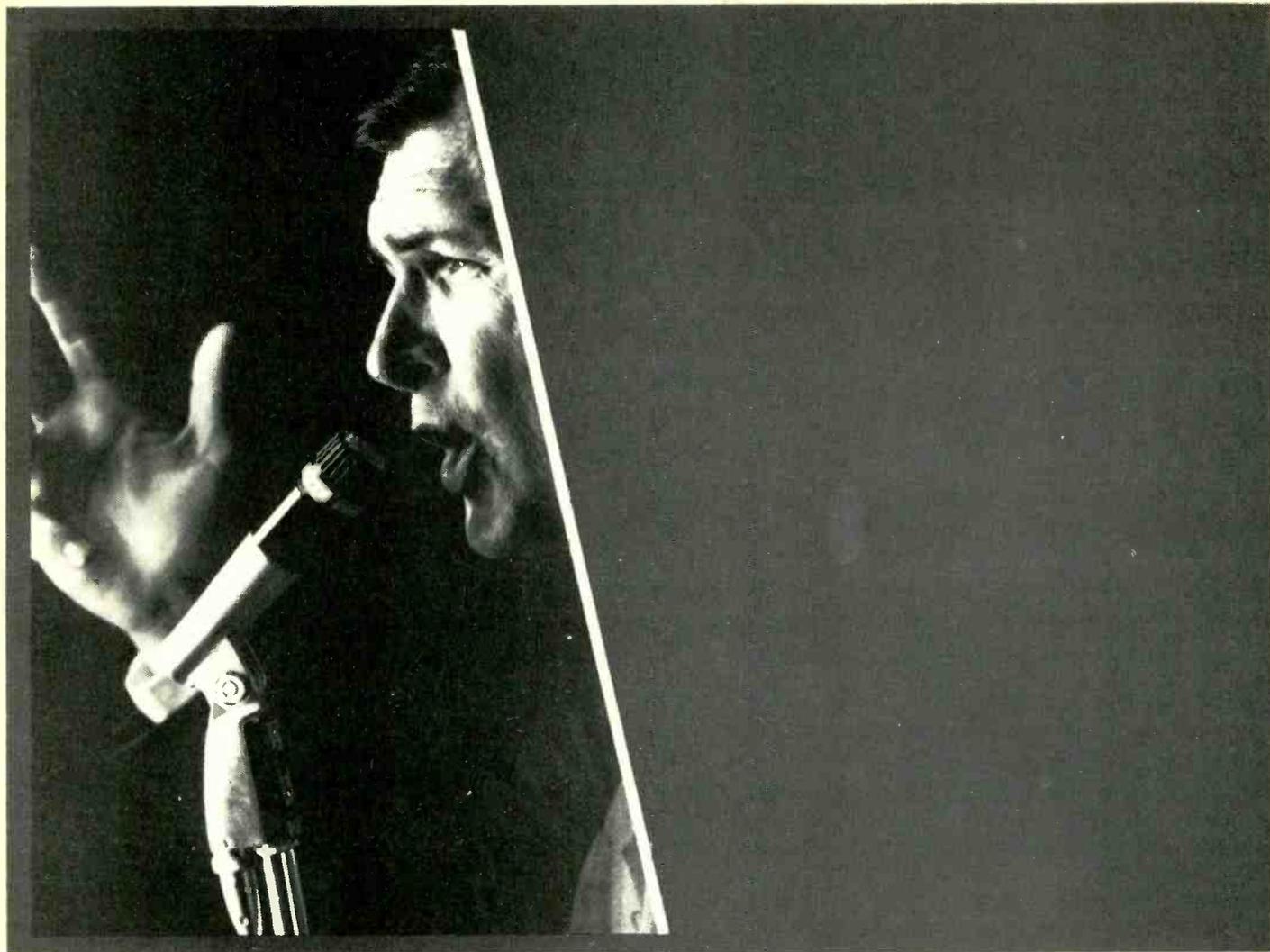Subscriptions: Oakfield House, Perrymount Rd, Haywards Heath, Sussex RH16 3DH. Telephone 0444 53281. Subscribers are requested to notify a change of address four weeks in advance and to return envelope bearing previous address.



Microphones matter most.



Never have so few words said so much about sound system installations. The truth is that a carefully chosen, top-quality microphone makes a measurable difference in sound system quality—regardless of the other components in the system. It is false economy at it worst to be a microphone miser. Install *Shure Unidyne* or *Unisphere* microphones—for installations with a marked superiority in voice intelligibility (and fewer service calls due to microphone problems).

Shure Electronics Limited
Eccleston Road, Maidstone ME15 6AU



WW—088 FOR FURTHER DETAILS

Wireless World

The Educated Ear

Editor:
TOM IVALL, M.I.E.R.E.

Deputy Editor:
PHILIP DARRINGTON

Technical Editor:
GEOFFREY SHORTER, B.Sc.

Assistant Editors:
BILL ANDERTON, B.Sc.
BASIL LANE

Drawing Office:
LEONARD H. DARRAH

Production:
D. R. BRAY

Advertisements:
G. BENTON ROWELL (*Manager*)
Phone 01-261 8339
KEITH NEWTON
Phone 01-261 8515
A. PETERS (*Classified Advertisements*)
Phone 01-261 8508 or 01-928 4597

In our July issue we published a letter bemoaning the lack of a "figure of goodness" for f.m. tuners. In the August issue J. R. Stuart's article on amplifier design told of the attempt to find a co-relation between objection measurements and subjective tests of harmonic distortion. These passages, and no doubt the unexpressed thoughts of many audiophiles, indicate a yearning for that mysterious formula, an objective standard of quality in reproduced sound. In its absence we must make do with subjective assessments. Fortunately, for those in mental distress, there are plenty of people around who will give you a subjective assessment at the drop of a hat. There are those who can tell the difference between "transistor sound" and "valve sound", those who can distinguish between a high quality Class B amplifier and a high quality Class A one, and above all there are the reviewers of equipment in the audio magazines.

One presumes that these people (especially the reviewers, who publish their conclusions) have a highly discriminating sense of hearing. Perhaps they were born with it, but at any rate we are told that whatever the initial state of the faculty it can be developed by training — the ear can be educated. But what exactly is the nature of the training, what are the criteria for an educated ear, what levels of aural education are attainable, how do we know what level a particular assessor has reached, and to what extent can we rely on the judgments resulting from the training? In fact we know very little about these qualifications. It appears that the training is self-administered and consists largely of constant listening, straining to distinguish minute differences of sound quality, development of a good aural memory, and familiarization with the aural correlates of engineering measurements such as distortion. From advertisements in which items of audio equipment are endorsed by famous musicians we are led to believe that these powers of assessment are normal attributes of musically trained people — and, perhaps conversely, that equipment reviewers and other assessors have musical ability of the kind possessed by professional musicians. But this is dangerous territory — a quagmire of subjectivism.

For those who feel lost in such considerations it is comforting to know that there is, at least, an objective standard of audio equipment performance. This is the group of specifications, DIN 45 500, issued by the German standards institution Deutscher (Industrie) Normenausschuss, which lays down in quantitative engineering terms the minimum performance requirements for domestic equipment that will permit it to be described as "high fidelity". Regrettably the British Standards Institution does nothing equivalent (only recommended methods of measurement), so those British audio manufacturers that are interested are making use of DIN 45 500. For the customer who does not have an educated ear but does have a highly developed sense of value for money it must be some satisfaction to know that what he has bought is, in a sense, sound of guaranteed minimum quality. The conformity to DIN 45 500 and the figures contained in the specifications do not tell him the *nature* of this sound quality he has bought but, whatever it is, he does know that he has got it.

Dual-polarity Digital Voltmeter

1 — Circuit operation

a 3½-digit instrument for alternating and direct voltages

by A. J. Ewins

This article describes the design and construction of the electronics of a 3½-digit, dual-polarity digital voltmeter for measuring alternating and direct voltages in the range 200mV to 400V full-scale. It is capable of an accuracy of $\pm 0.05\%$ of full-scale which in practice is limited by the precision of the input attenuator resistors and the accuracy of the a.c. rectifier circuit. A relatively inexpensive attenuator system is described which is capable of being adjusted to an accuracy of $\pm 0.1\%$ giving an overall accuracy to the d.c. ranges of $\pm 0.1\%$ of reading, $\pm 0.05\%$ of full-scale. For the a.c. ranges the accuracy is further limited by the rectifying circuit but nevertheless an accuracy of $\pm 0.5\%$ of reading, $\pm 0.05\%$ of full-scale is achieved over a frequency range of 30Hz to 100kHz. The full-scale reading of the d.v.m. is 1999 (with suitable positioning of the decimal point) and an overload indication is given for readings in excess of this value. In spite of the overload indication it is possible to interpret readings up to an indication equivalent to 2500.

An additional feature of the d.v.m. is its ability to operate in either an automatic or a manual mode. In the auto. mode the d.v.m. continually samples the input voltage but can be made to "hold" and display the latest reading by depressing a sample/hold switch. In the manual mode the d.v.m. holds and displays the latest reading of the input voltage but can be made to further sample it by depressing the sample/hold switch, after which it again holds.

Details of the construction of the electronics on suitable circuit boards only is

given, it being left to the reader to devise a suitable cabinet construction.

Design principles

The d.v.m. operates on the by now well-known dual-slope integration method. Two previous designs presented in this journal^{1,2} operate on this principle and a detailed account of the theory was given in Waddington's article, "Digital Multimeter"¹. However, for those readers who missed both previous articles and are unfamiliar with the technique a brief description of the principle will be given.

Single polarity. With reference to the block circuit diagram of Fig. 1, a capacitor C , is charged (negatively) by connecting the positive input voltage, V_{in} , (via the electronic switch) to the resistor R for a known time. The resistor R , capacitor C and the high-gain operational amplifier form an integrating circuit with highly linear characteristics. At the end of this time the voltage on the capacitor will be V_c , given by the expression:

$$V_c = (1/RC) \int_0^{t_1} V_{in} \cdot dt = V_{in} \cdot t_1 / RC.$$

The electronic switch now connects the resistor R to the accurately known negative reference voltage and the capacitor is discharged (positively) until V_c reaches the value it was before it was charged (usually zero volts). Thus,

$$0 = V_c - (1/RC) \int_0^{t_2} V_{ref} \cdot dt = V_c - V_{ref} \cdot t_2 / RC.$$

Hence, $V_{in} \cdot t_1 / RC = V_{ref} \cdot t_2 / RC$ and $V_{in} = V_{ref} \cdot t_2 / t_1$.

The value of t_1 is determined by the frequency of the clock oscillator and the divide-by-10 and 2000 counters. (The divide-by-ten counter has been introduced to ensure that the control logic operates at a speed at least ten times faster than the time represented by the least significant digit of the main, divide-by-2000 counter.) At the beginning of the charging process these two counters are set to zero. The logic is so arranged that when the divide-by-2000 counter reaches a total count of 2000 (after 20,000 clock pulses, and hence after a time $2 \times 10^{-5} \times 10^4 = 100\text{ms}$) the charging process is stopped and the discharging process begun (by disconnecting R from V_{in} and connecting it to $-V_{ref}$). The divide-by-2000 counter now counts the number of clock pulses (divided by ten) received in the time it takes to discharge the capacitor to zero volts. The comparator, of Fig. 1, detects the zero voltage level and transmits a pulse to the control logic, commanding the transfer of the time indicated by the main counter to the display. Immediately after the transfer, the divide-by-10 and 2000 counters are reset to zero and the resistor R reconnected to $+V_{in}$. A new measurement cycle then begins. (N.b., there is no need to reset the divide-by-10 and 2000 counters to zero at the end of the charging process because they automatically recycle at the end of this period.) Because the full-scale of the main counter is effectively a display of 2000, the value of V_{in} may be read directly in terms of t_2 if $-V_{ref}$ is given a value of -2 volts, i.e. $V_{in} = t_2 \cdot 2V / 2000$. This is the case of the d.v.m. described in this article and the basic range is thus 2 volts.

The beauty of the dual-slope integration method lies in the fact that the long-term stability of the clock oscillator and the precise values of R and C are unimportant. Providing they are stable over the short-term (not more than 200ms for a full-scale reading) which may more than reasonably be expected, the accuracy of the system is theoretically only dependant upon the accuracy of the reference voltage.

As has already been mentioned, the divide-by-10 and 2000 counters are reset to zero immediately after the time t_2 has been transferred to the display. This is unlike the

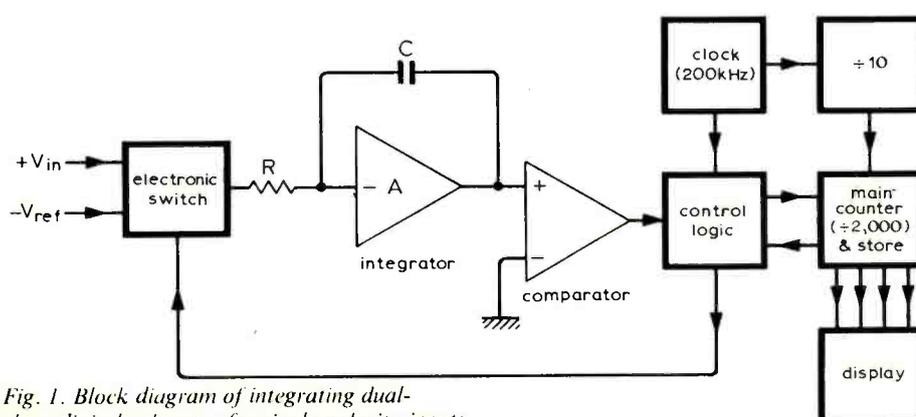


Fig. 1. Block diagram of integrating dual-slope digital voltmeter for single-polarity inputs.

previous designs described in this magazine, which had a "dead period" at the end of the discharging process, whilst the main counter continued towards a total count of 2000, before reconnecting the input to the integrator to V_{in} . The modification to this design allows readings in excess of full-scale (up to a limiting value discussed later) to be accurately interpreted and is one of the reasons why existing large-scale integrated circuits were not considered for the control and display logic. The main reason, at the time of construction, was one of cost and availability. The article, "Digital Panel Meter"², published in this journal, amply illustrates the advantages to be obtained from using l.s.i.c.s. However, while the use of individual logic circuits may be cheaper than the large-scale ones (if considerably more bulky) the author has taken advantage of the opportunity to "stamp" his own originality upon the design of d.v.m. circuits. Eventually, when the cost of l.s.i.c.s become really low, the designer will no longer be free to indulge his own whims and fancies upon the basic designs, but will have to be content to accept the designs of others.

The lack of a "dead period" in the operation of the d.v.m. measurement cycle does have one other advantage in the simplification of the switching circuitry when only one resistor is used in the integrator. If more than one resistor is used, say, one for $+V_{in}$ and one for $-V_{ref}$, a possible source of error is introduced due to the differing ageing characteristics between resistors.

Dual polarity. The principle of operation of a dual-slope integrating digital voltmeter so far described has only been for a single polarity type. For a dual-polarity type, some modification to the basic block diagram of Fig. 1 is necessary. Fig. 2 is a block diagram of the dual-polarity principle adopted by the author. The method of conversion of voltage into time is exactly as described before. However, the capacitor C will be charged negatively or positively as determined by the polarity of the input voltage. Thus two reference voltages, of equal magnitude but opposite sign, are needed to discharge the capacitor, positively or negatively as appropriate. Two comparators are also required to detect the direction of the

charge on the capacitor and hence select the appropriate reference voltage for discharging. Except for the addition of polarity detecting logic, the operation of the control and display logic remains unaltered.

Initially the capacitor C is discharged and the output from the integrator, V_c , will satisfy the following condition; $-2mV < V_c < +2mV$. The output from comparator 1 will therefore be logical "1" and that of comparator 2, logical zero. Due to the inversion of the logical level at the output of comparator 2 by inverter 1, the input to the control logic and from the AND gate will be logical "1", which is the same as for the single-polarity d.v.m. of Fig. 1. This is thus the beginning of the measurement cycle and the control logic connects the resistor, R , via the electronic switch, to V_{in} . Providing that the magnitude of V_{in} is greater than zero, the capacitor C will be charged. If V_{in} is positive, C will be charged negatively and the output of comparator 1 will become logical zero. Comparator 2 remains unaltered at the logical zero level.


The output from the AND gate thus changes to logical zero. Similarly, if V_{in} is negative, C will be charged positively and the output of comparator 2 will become logical "1", comparator 1 remaining at the logical "1" level. Once again, the output from the AND gate becomes logical zero. At the end of the timing period, the control logic commands the connection of one of the reference voltages to the input of the integrator. The reference voltage selected is dependant upon the logical states of the two comparators fed-back to the electronic switch. If the output from both comparators is logical zero, $-V_{ref}$ will be selected and if they are both logical "1", $+V_{ref}$ will be selected. The logic of the electronic switching circuit is so arranged that a logical zero at the output of either comparator inhibits the selection of $+V_{ref}$ and a logical "1" at the output of either comparator inhibits the selection of $-V_{ref}$. Because of this it is impossible for both reference voltages to be selected simultaneously. Having connected the appropriate reference voltage to the integrator the capacitor is discharged until the voltage across it again satisfies the condition, $-2mV < V_c < +2mV$. When this occurs, the output from the AND gate

again becomes logical "1", commanding the control logic to transfer the time t_2 from the main counter to the display, reset the divide-by-10 and main counters to zero and reconnect the input of the integrator to V_{in} .

Polarity indication is achieved by detecting the logical states of the two comparators at the end of the initial timing period. If at the end of this time the outputs of both comparators are logical zeros (when V_{in} is positive) the J input to the $J-K$ flip flop will be logical "1" (due to the inverting action of inverter 2) and the K input will be logical zero. A pulse from the control logic, transmitted at the end of the timing period, transfers the logical "1" at the J input to the Q output, which in turn operates drivers in the display unit to indicate the positive sign. Similarly, if at the end of the timing period the outputs of both comparators are logical "1", then the J and K inputs will be logical zero and "1", respectively, and a logical "1" will be transferred to the \bar{Q} output. Thus the negative sign will be displayed. When the input voltage is zero, the outputs of both comparators remain unaltered, from their original conditions, at the end of the initial timing period. Both J and K inputs are thus logical zeros and the polarity sign indicated is that of the last input voltage greater than zero. In this manner, the sign indicated by the display remains illuminated until an input voltage of opposite polarity is applied. By shorting the V_{in} input to earth, the polarity indication may be used to accurately set the zero reading of the d.v.m.

The $-2mV$ and $+2mV$ reference voltages applied to the negative inputs of comparators 1 and 2, respectively, are necessary in order to define clearly the discharged state of the integrating capacitor. It would not be possible to do this if both reference inputs were connected to earth. In practice it is sufficient to separate the reference levels of the comparators by such an amount as to guarantee the discharged state to be clearly defined, allowing for temperature drift of the differential offset voltages of the comparators. The fact that the two comparator reference levels are at different voltages in no way impairs the accuracy of the system. However, the closer the two reference levels, the easier it is to assess a true zero condition in the absence

Fig. 2. The system of Fig. 1 adapted to accept dual-polarity inputs.

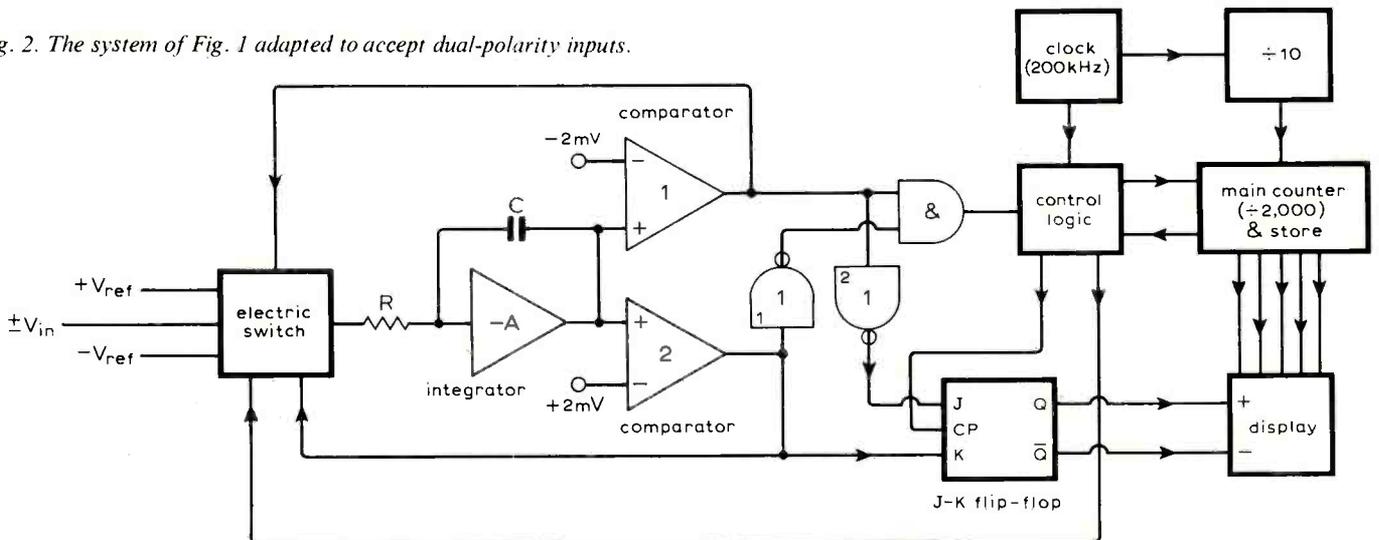

of an input voltage, and 2mV represents a resolution of less than the least significant digit displayed.

Basic d.v.m. circuit

For convenience the basic circuitry of the d.v.m. has been split up into two. Fig. 3 is a detailed circuit diagram of all the analogue circuitry of the d.v.m. plus the electronic switching circuitry and the polarity logic. Fig. 4 is a detailed block circuit diagram of the control and display logic. It will be seen that the total circuitry uses only well known and easily obtainable, inexpensive, operational amplifiers, transistors and t.t.l. digital circuits.

Analogue circuit. Examining first of all the circuit of Fig. 3 it will be seen that Z_2 , which is fed with a constant current of about 5mA by Tr_5 and its associated circuitry, provides a reference voltage of +5.6 volts. This large positive reference voltage is converted into a smaller positive one of 2 volts, with low output impedance, by IC_1 and its associated circuitry. It is similarly converted into a -2 volt reference level, with low output impedance, by the inverting action of IC_5 and its circuit. Variable resistors, R_1 and R_2 , allow for a precise setting of these two reference levels. IC_3 provides a buffer input for V_{in} , has unity gain and a low output impedance. The output from IC_3 is voltage limited by zener diodes Z_3 and Z_4 for the protection of

the transistors used in the electronic switch. R_3 allows the output from IC_3 to be adjusted precisely to zero when the input voltage is zero. IC_6 is the integrating operational amplifier and IC_8 and IC_9 are the comparators, 1 and 2, respectively. Tr_1 is the transistor switch for $+V_{ref}$, Tr_4 the switch for $-V_{ref}$ and transistors Tr_2 and Tr_3 , in parallel, the switch for V_{in} . The operation of these transistor switches is controlled by IC_2 and IC_4 and the outputs from the two comparators via the diodes D_1 to D_8 . The operation of these transistors as switches may be unfamiliar to some readers and will therefore be explained. Figs. 5(a) and 5(b) illustrate, respectively, the conventional use of a transistor as a switch and the more unconventional mode as used in this d.v.m. In Fig. 5(a), when a sufficiently large current is applied to the base of the transistor, it saturates with a collector-emitter voltage of typically 200mV, which varies little with varying supply volts, V_s , providing the collector resistor is of a reasonably high value. This offset voltage is very high when compared with a resolution for the d.v.m. of 1mV and makes the use of a transistor as a switch, in this mode, quite unsuitable. It is a curious fact, however, that when the same transistor is turned upside down, see Fig. 5(b), (V_s must not now exceed the V_{be} breakdown voltage of the transistor) and a sufficiently large current is applied to the base of the transistor, it saturates, this time with an

emitter-collector voltage of only a few millivolts. Experiments with n-p-n and p-n-p transistors, types BC182 and BC212 respectively, in the test circuits of Figs. 5(c) and 5(d) (which are effectively rearrangements of the circuit of Fig. 5(b), allowing for transistor types), yielded the results in Table 1.

Table 1

V_{in} (volts)	V_{ce} (mV)	
	BC182	BC212
+2	+3.3	+2.1
+1	+1.5	+1.3
0	-0.3	+0.3
-1	-1.7	-1.0
-2	-2.8	-2.5

The above two transistors were selected randomly and others of the same two types produced only slightly different results. From the above results it was thought quite satisfactory to use a BC182, in this switching mode, for switching $+V_{ref}$ and a BC212 for switching $-V_{ref}$. The very small voltages dropped across the collector and emitter of the transistors are easily allowed for in the adjustment of the two reference levels.

Neither of the two transistors was thought ideal for switching the input voltage because, although the small voltages dropped across the transistors at V_{in} equals zero could be allowed for in the zero adjustment

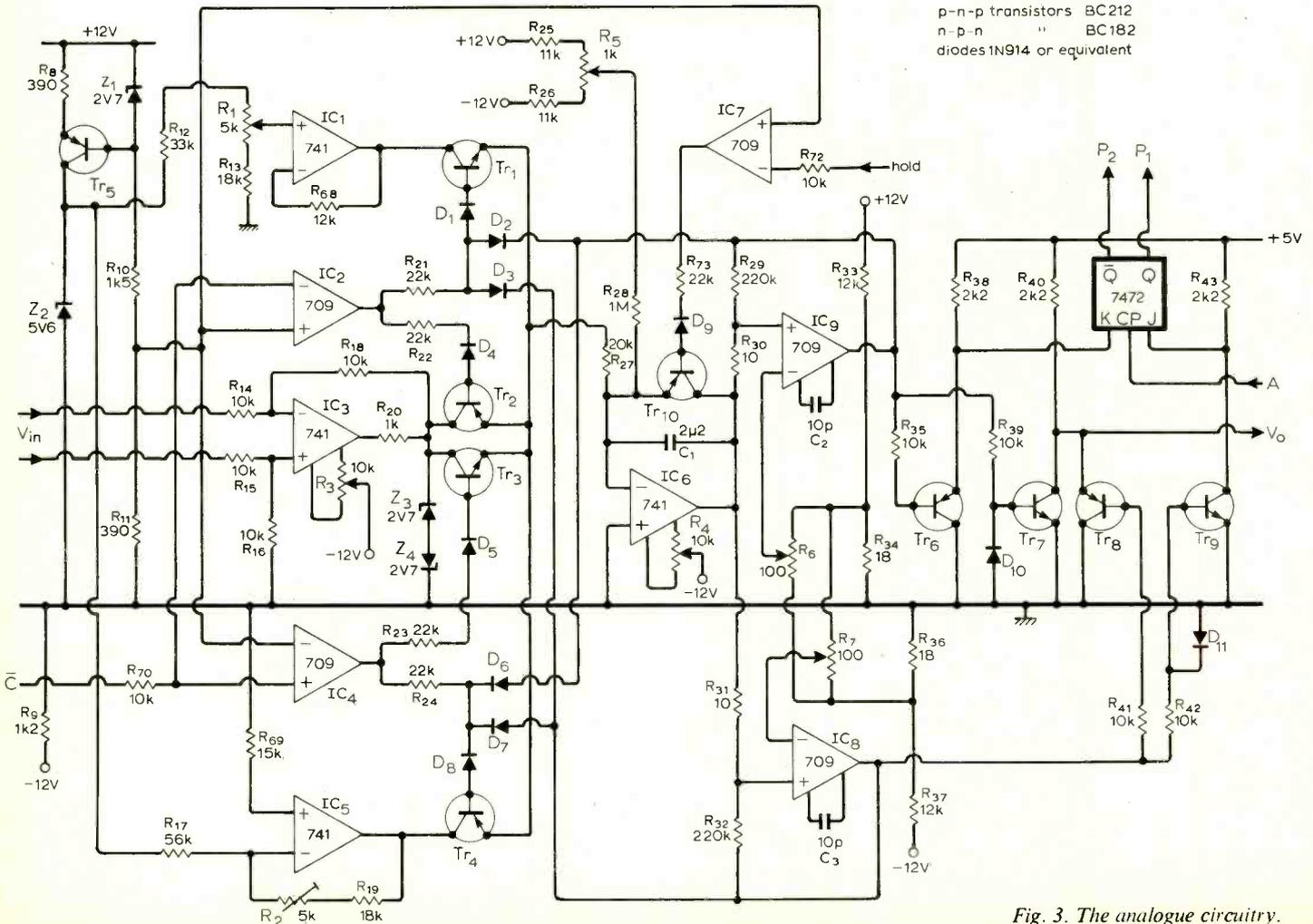


Fig. 3. The analogue circuitry.

of the input op-amp, the relationship between V_{ce} and V_{in} were not exactly linear. However, the author discovered that if both types of transistor were used (by connecting them back-to-back as in Fig. 5(e)) and were switched on simultaneously, a nearly ideal switch was produced. Using the same two transistors, as tested above, in the experimental circuit of Fig. 5(e) produced the results in Table 2.

Table 2

V_{in} (volts)	V_{ce} (mV)
+2	+2.7
+1	+1.4
0	~0
-1	-1.3
-2	-2.7

The two transistors were thus acting together to produce a switch with very nearly zero offset voltage and an effective "on" resistance of $(2.7\text{mV} \times 20\text{k}\Omega) / 2\text{V} = 27\Omega$. A parallel combination of a BC182 and a BC212 is thus used as the switch for V_{in} . The above table of results is interesting in view of the fact that the two transistors used were not precisely matched, except for their values of V_{ce} at zero input voltage. The author, therefore, feels fairly confident that any pair of transistors, types BC182 and BC212, should function satisfactorily in this manner without the need for special matching.

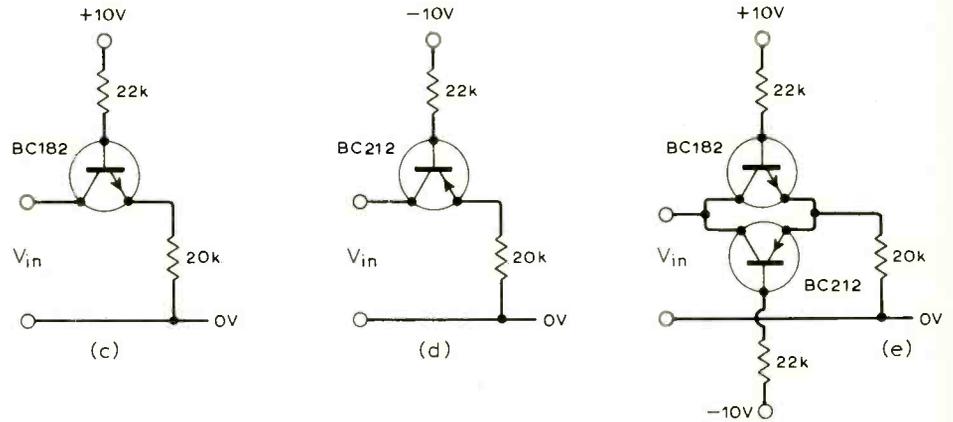
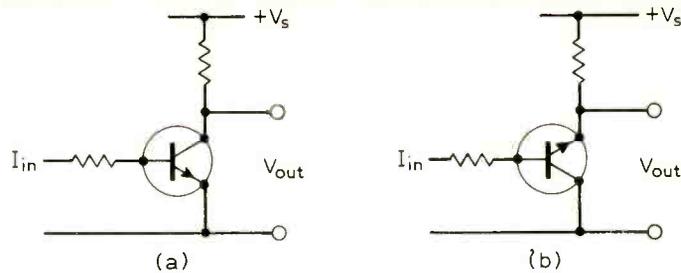


Fig. 5. (a) Conventional and (b) inverted transistor switches. Test circuits, using n-p-n and p-n-p devices are shown in (c) and (d) and (e) in the final form using both types.

Fig. 4. Control and logic circuitry.

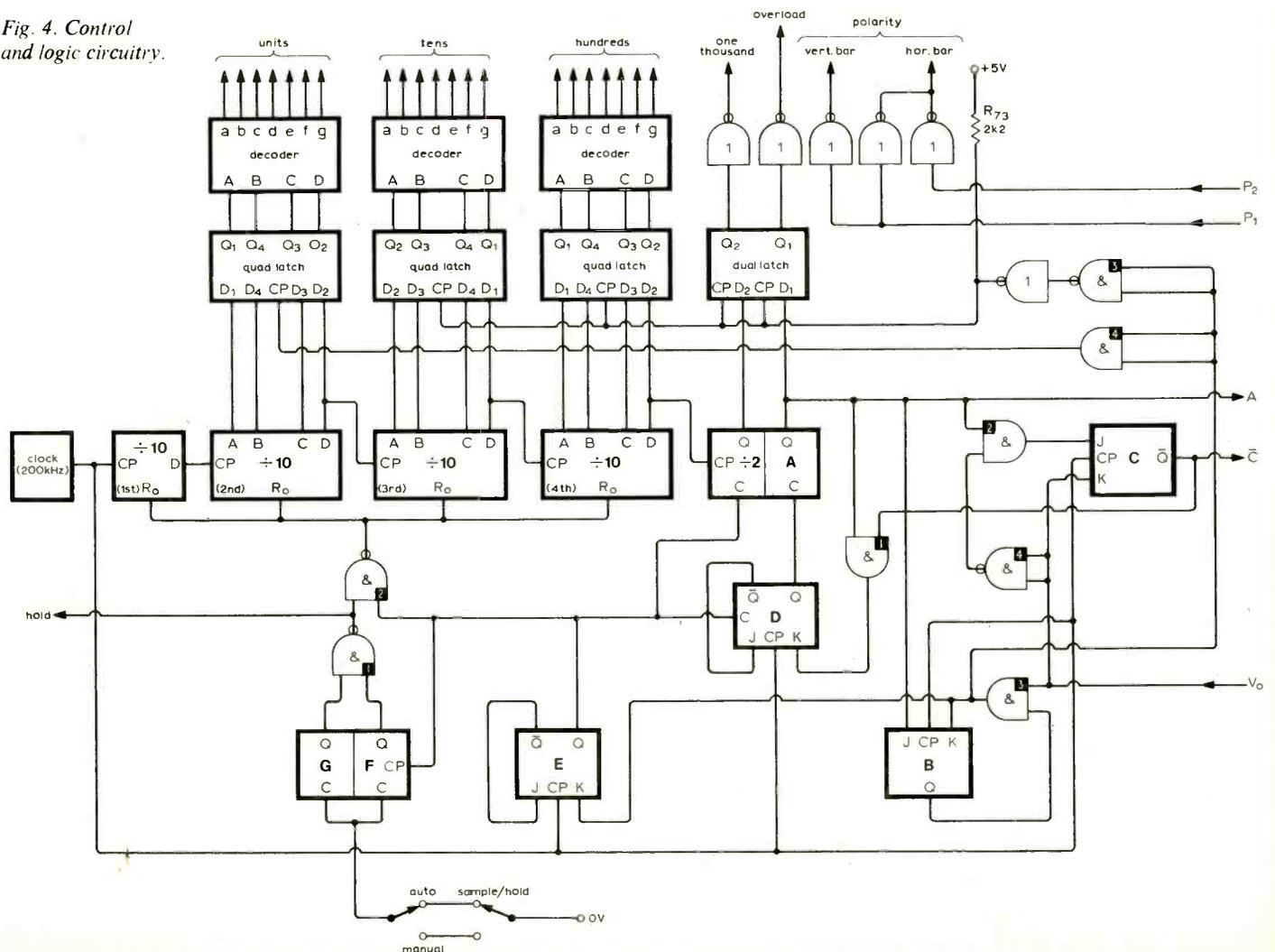


Fig. 6 illustrates the complete switching circuitry of the d.v.m. and, remembering that the outputs from the two comparators (IC_8 and IC_9) and IC_2 and IC_4 are either + or - 10 volts (approx.), operates as follows: At the onset of the measurement cycle (i.e. V_{in} connected to the input of the integrator) the voltage at the output of IC_8 is +10V; that of IC_9 , -10V; that of IC_2 , -10V and IC_4 , +10V. The voltage at the junction of the diodes, D_1 , D_2 and D_3 , is thus approx. -10V and Tr_1 is OFF, the voltage at the junction of the diodes, D_6 , D_7 and D_8 , is approx. +10V and Tr_4 is OFF; the voltage at the base of Tr_2 is negative of its collector and therefore it is ON, and the voltage at the base of Tr_3 is positive of its collector and therefore it is also ON. At the end of the timing period the voltages at the outputs of IC_2 and IC_4 reverse, to become +10V and -10V respectively, turning transistors Tr_2 and Tr_3 OFF. In the absence of any feedback from the outputs of the two comparators, transistors Tr_1 and Tr_4 would simultaneously be turned ON, shorting $+V_{ref}$ and $-V_{ref}$ together. However, with the connections as shown and assuming a positive input voltage, the output of comparator one (IC_8) will have become -10V by the end of the timing period, the output of comparator two remaining -10V. The junction of diodes D_6 , D_7 and D_8 is thus free to swing in a negative direction at the command of IC_4 and Tr_4 is turned ON connecting $-V_{ref}$ to the input of the integrator. -10V at the outputs of both comparators prevent Tr_1 from being turned ON. If the input voltage had been negative, the output of comparator two (IC_9) would have become +10V by the end of the timing period, the output of comparator one remaining +10V; the junction of diodes D_1 , D_2 and D_3 would then have been free to swing in a positive direction at the command of IC_2 and Tr_1 would have been turned ON, connecting $+V_{ref}$ to the input of the integrator. +10V at the output of both comparators prevent Tr_4 from being turned ON. The diodes D_1 , D_4 , D_5 and D_8 prevent breakdown of the emitter-base junctions of the transistors Tr_1 to Tr_4 , respectively, when they are held in their OFF states.

The switching currents feeding into the bases of the transistors Tr_1 to Tr_4 to turn them ON are of the order of 300 μ A to 500 μ A, and it is because of this relatively heavy current that the output impedances of the sources of $+V_{ref}$, $-V_{ref}$ and V_{in} must be low. A higher output impedance would result in these voltage levels being altered in the presence of the switching currents, impairing the accuracy of the d.v.m.

Returning now to Fig. 3, it will be appreciated that the outputs from the two comparators (either + or - 10 volts) are not compatible with t.t.l. digital circuit logic levels. (For the t.t.l. circuits, logical 0 \equiv 0.2V and logical 1 \equiv 2.5 to 5.0V.)

Transistors Tr_6 to Tr_9 are included to achieve this conversion in voltage levels and to provide the inversion function of the inverters 1 and 2 of Fig. 2 and also to provide the function of the AND gate. Thus, when the output from IC_8 is +10 volts, the collector of Tr_9 is about 0.2 volts and hence the

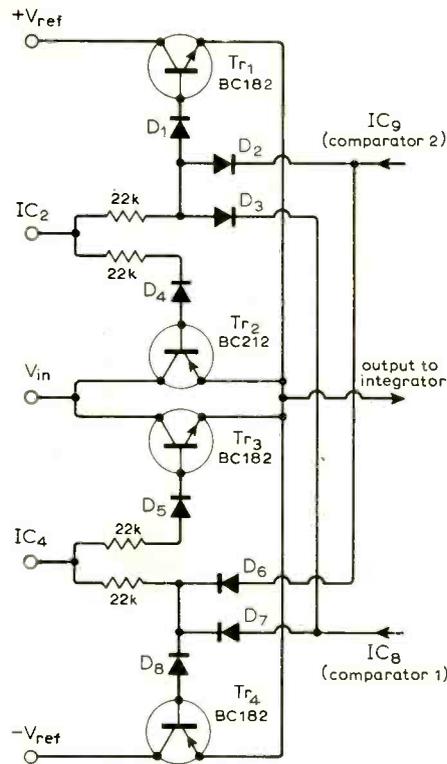


Fig. 6. The complete analogue switching circuit.

J input of the J - K flip-flop is logical "0"; when it is -10 volts, the collector of Tr_9 and the J input are at about 5 volts, i.e. logical "1". Similarly, when the output from IC_9 is -10 volts, the collector of Tr_6 is about zero volts and hence the K input to the J - K flip-flop is logical "0"; when it is +10 volts, the collector of Tr_6 and the K input are at the logical "1" level. When the outputs from IC_8 and IC_9 are +10 volts and -10 volts respectively, the output to the control logic, V_o (the junction of the collector of Tr_7 and the emitter of Tr_8), is at the logical "1" level. If either IC_8 is -10 volts or IC_9 is +10 volts, the output, V_o , becomes logical zero.

IC_2 and IC_4 are included for similar reasons to the transistors Tr_6 to Tr_9 ; they convert the t.t.l. logic level from C to the necessary plus and minus 10 volt levels for the operation of the electronic switch circuitry. The positive input of IC_2 and the negative input of IC_4 are held at a voltage level of about +2 volts. A logical "0" at the C output from the control logic thus produces voltage levels at the outputs of IC_2 and IC_4 of +10V and -10V, respectively. Logical "1" at the C output produces voltage levels of -10V and +10V at the outputs of IC_2 and IC_4 , respectively.

It has already been stated that the inclusion of zener diodes Z_3 and Z_4 is to limit the output from IC_3 for the protection of the switching transistors. The necessity for this protection can best be understood by assuming that a voltage much greater in magnitude than 2V, say +4V, were applied to the input of IC_3 . Since it has unity gain, the voltage on the collectors of Tr_2 and Tr_3 would also be +4V. Now, if the input of the integrator were connected to $-V_{ref}$ then the voltage on the emitters of Tr_2 and Tr_3 would be -2V and the emitter-base junc-

tion of Tr_2 would be in danger of breaking down, since V_{be} for all four transistors is only rated at 5 volts. (N.b., a transistor with a reverse voltage connected across its emitter and collector can only withstand a voltage equivalent to its V_{be} breakdown voltage plus the voltage across the forward biased collector-base diode.) Similar danger would be experienced if V_{in} were -4V and the input to the integrator connected to $+V_{ref}$ (+2V); the emitter-collector junction of Tr_3 would then be threatened. The emitter-collector junctions of Tr_1 and Tr_4 could also be threatened if the input to the integrator were connected to V_{in} when it was at a level of +4V or -4V, respectively. Z_3 and Z_4 limit the voltage on the collectors of Tr_2 and Tr_3 to approx. ± 3.3 volts so that the magnitude of the maximum possible voltage across the collector-emitter junctions of all four switching transistors is 5.3 volts.

The variable resistors R_4 and R_5 , of Fig. 3, allow the short circuit and open circuit input offsets of the integrating op-amp IC_6 , to be set to zero.

The action of IC_7 , together with Tr_{10} and its associated circuitry, allows the output of the integrator to be held at the zero volt level by shorting the integrating capacitor. This circuitry is used in conjunction with the auto/manual facility of the d.v.m.

Control logic. The inter-connections between the various t.t.l. digital circuits of the control and display logic are shown in the block diagram of Fig. 4. The second, third and fourth decade counters and the divide-by-two flip-flop form the basic divide-by-2000 counter. A , B , C , D , E , F and G are all J - K flip-flops and are contained in four t.t.l. circuits, type SN7473. Not shown are the connections between the outputs of the divide-by-two flip-flop and the clock pulse, C_p , input of flip-flop A , and the output of the F flip-flop and the C_p input of flip-flop G . The six inverters, which are buffer/drivers with open collector outputs capable of sinking 40mA, are all contained in the t.t.l. circuit, type SN7416. The four dual-input NAND gates are all contained in the t.t.l. circuit, type SN7400, and the four dual-input AND gates in the t.t.l. circuit, type SN7408. The clock circuit is made from a t.t.l. dual-Schmitt trigger circuit, type SN7413, together with a resistor and a capacitor. The circuit is shown in Fig. 7.

The binary outputs from the three decade counters of the main counter are transferred to suitable decoders via three quadruple latches, t.t.l. circuits type SN7475. In a similar manner, the outputs from the divide-by-two flip-flop and the A flip-flop are transferred to the inputs of two inverter buffer/drivers via a dual-latch, t.t.l. circuit type SN7474. Three other inverter buffer/drivers accept the outputs of the polarity flip-flop (see Fig. 3) and drive the horizontal and vertical bars of the polarity display. The sixth inverter buffer/driver is used to provide increased power for driving some of the C_p inputs of the latches.

In order to understand the operation of the control logic, and hence the operation of the d.v.m., Table 3 has been drawn up. It shows the logical states of the outputs of

the relevant elements of the control logic for various steps in the operation of the d.v.m. For the moment the functions of flip-flops *F* and *G* have been ignored and the logical state of the output of NAND 1 is assumed to be a permanent logical "1". For the initial conditions it will be assumed that all the logical elements are in such states as at the beginning of a measurement cycle. This is as in step 0 of the above table. No clock pulses have as yet been generated, the first decade counter and the main counter are all set to zero and the output \bar{C} is a logical "1". The output V_o is also a logical one. The input of the integrator is thus connected to V_{in} , which is assumed to have a magnitude greater than zero but less than 2 volts. The clock is running and the first decade counter and the main counter start to count up to a total of 20,000 clock pulses (a period of 100ms). At some time during this period the output V_o will become logical "0" and the outputs of the various logic elements become as in step 1 of Table 3.

At the end of this period the state of the main counter is again 0000 (2000 \equiv 0000) but the output of *A* will be logical "1", see step 2. On receipt of another clock pulse, step 3, several things happen. Output *B* changes from "0" to "1"; *D* from "1" to "0", resetting output *A* to "0"; and \bar{C} becomes 0 connecting the input of the integrator to the appropriate reference voltage. The resetting of *A* to "0" transmits a pulse to the polarity flip-flop of Fig. 3, transferring appropriate logic levels to the outputs *P*₁ and *P*₂. A further clock pulse, step 4, resets *D* to logical "1". The main counter now continues counting and nothing further happens to the logic until V_o again becomes logical "1", indicating the end of the measurement cycle and the fact that the integrating capacitor has been discharged, see step 5. Immediately V_o becomes logical "1", the *k* input to flip-flop *B* becomes logical "1". *B*_k is the latch pulse and a logical "1" is immediately transmitted to the latches via AND gate 4, NAND gate 3 and inverter 3. The logical states of the outputs of the main counter and flip-flop *A* are thus transferred to the three decoders and inverter buffer/drivers 1 and 2, indicating the count reached by the main counter and whether there is an overload or not. Since the magnitude of V_{in} was assumed to be less than 2 volts the counter will not have reached 2000 and the output of *A* will be logical "0", indicating no overload. On receipt of the first clock pulse after V_o has become logical 1, step 6, again a number of things happen. Output *B*, and thus its input *B*_k (the latch pulse), changes from logical "1" to "0"; output *E* changes from "1" to "0", setting output *D* and the output from the divide-by-two flip-flop to "0" and also, via NAND gate 2, resetting all four decade counters to zero; and output \bar{C} changes from logical "0" to "1", reconnecting the input of the integrator to V_{in} . Since output *D* has become "0" output *A* will also be set to "0" if it were a logical "1" before. A second clock pulse, step 7, resets *E* from "0" to "1", releasing the first decade counter and the main counter (allowing it to begin counting again) and flip-flop *D*. A third clock pulse, step 8, resets *D* from "0" to "1",

Table 3. Sequence of logical states of control logic elements

Step	CP	Count.	A	V _o	B _j	B _k	B	C _j	C _k	\bar{C}	D _j	D _k	D	E _j	E _k	E
0	0	0000	0	1	0	0	0	0	1	1	0	0	1	0	0	1
1	?	??	0	0	0	0	0	0	0	1	0	0	1	0	0	1
2	0	2000	1	0	1	0	0	1	0	1	0	1	1	0	0	1
3	1	0000	0	0	0	0	1	0	0	0	1	0	0	0	0	1
4	2	0000	0	0	0	0	1	0	0	0	0	0	1	0	0	1
5	0	??	0	1	0	1	1	0	1	0	0	0	1	0	1	1
6	1	0000	0	1	0	0	0	0	1	1	1	0	0	1	0	0
7	2	0000	0	1	0	0	0	0	1	1	1	0	0	0	0	1
8	3	0000	0	1	0	0	0	0	1	1	0	0	1	0	0	1
9	0	2000	1	1	1	0	0	0	1	1	0	1	1	0	0	1
10	1	0000	0	1	0	1	1	0	1	1	1	0	0	0	1	1
11	2	0000	0	1	0	0	0	0	1	1	1	0	0	1	0	0
12	3	0000	0	1	0	0	0	0	1	1	1	0	0	0	0	1
13	4	0000	0	1	0	0	0	0	1	1	0	0	1	0	0	1
14	0	2000	1	0	1	0	1	1	0	0	0	0	1	0	0	1
15	0	2000+	1	1	1	1	1	1	1	0	0	0	1	0	1	1
16	1	0000	0	1	0	0	0	0	1	1	1	0	0	1	0	0
17	2	0000	0	1	0	0	0	0	1	1	1	0	0	0	0	1
18	3	0000	0	1	0	0	0	0	1	1	0	0	1	0	0	1

In terms of logical levels: $B_j = A$; $B_k = B.V_o$; $C_j = A.V_o$; $C_k = V_o$; $\bar{D}_j = D$; $D_k = A.\bar{C}$; $E_j = E$; $E_k = B.V_o$.

leaving the outputs of the various logical elements exactly as at the beginning of the measurement cycle. A new measurement cycle was, in fact, begun at step 7, the moment the main counter was released after being reset.

When the input voltage is zero or its magnitude is greater than 2 volts, the operation of the control logic is slightly modified. When V_{in} is zero volts, V_o does not become logical "0" so that when the main counter reaches 2000 the conditions of the various logic elements become as in step 9. After a further clock pulse the output of *B* becomes logical "1", so that *B*_k also immediately becomes logical "1" and a zero count is transferred (remembering, 2000 \equiv 0000) to the decoders. Simultaneously, the output of *D* becomes "0" and *A* is reset to zero, preventing an overload indication being given. At the end of three more clock pulses, steps 11, 12 and 13, the initial conditions, at the beginning of a measurement cycle, are arrived at once more.

When the magnitude of V_{in} is greater than 2 volts, the counter will become 2000 for a second time before V_o has become logical "1". The conditions of the outputs of the logic elements when this state is reached are as shown in step 14. Having passed 2000 the

counter effectively starts counting again from 0000. Nothing further happens to the logic until eventually V_o does become logical 1, step 15. Immediately, *B*_k becomes logical "1" and the state of the main counter is transferred to the decoders, etc., together with the overload information on flip-flop *A*. Three more clock pulses, steps 16, 17 and 18, reset all the logic elements to their initial conditions. Since the overload indication represents a count of 2000, it may be added to that shown by the display to indicate a reading in excess of 2000.

The upper limits for reliable readings in excess of 2000 are determined by the precise breakdown voltages of zener diodes *Z*₃ and *Z*₄, and the reverse breakdown voltage of the holding transistor *Tr*₁₀ across the integrating capacitor. When V_{in} is negative, the integrating capacitor charges positively so that *Tr*₁₀ will breakdown if the voltage across the capacitor exceeds about 5.7 volts ($V_{be} = 5V$). The integrating capacitor charges up to a voltage level, V_c , equivalent to

$$(1/RC) \int_0^{100ms} V_{in} \cdot dt.$$

i.e. $V_c = V_{in} \cdot 100ms/RC$, and since $RC = 20k\Omega \times 2.2\mu F = 44ms$, $V_c = 2.27V_{in}$. Theoretically then, the upper limit for reliable readings in excess of 2000, when V_{in} is negative, is, $5.7V/2.27 = 2.500$. When V_{in} is positive, the upper limit for a reliable reading in excess of 2000 is the breakdown voltage of *Z*₃ plus the forward diode voltage drop across *Z*₄ which in total, is about 3.300.

Having discussed the operation of the control logic of the d.v.m. in its Auto mode (by neglecting the operation of flip-flops *F* and *G*) it is now time to consider the function of the Auto/Manual and Sample/Hold switches and flip-flops *F* and *G* in conjunction with the hold circuitry, *IC*₇ and etc., of Fig. 3. As shown in Fig. 4, with the Auto/Manual switch in the Auto position and the Sample/Hold switch as indicated, the output of flip-flops *F* and *G* are held at logical zero and hence the output of NAND gate 1

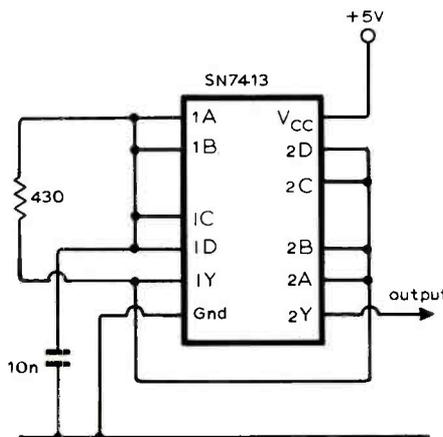


Fig. 7. Clock pulse generator, using a dual 4-input Schmitt NAND.

is a logical "1". The operation of the control logic and the d.v.m. is therefore as described above, providing a continuous sampling of the input voltage. If now the Auto/Manual switch is switched to the Manual position, flip-flops *F* and *G* begin to count the main counter's resetting pulses transmitted by flip-flop *E*. After three such pulses the outputs of both *F* and *G* become logical "1" and hence the output of NAND gate 1 becomes logical "0" and that of NAND gate 2, logical "1". The main counter is thus held permanently reset and no further pulses are transmitted by flip-flop *E*. Simultaneously, the logical "0" level at the output of NAND gate 1 switches the output of *IC*₇ to -10V, switching *Tr*₁₀ ON and holding the voltage across the integrating capacitor to zero volts. The d.v.m. remains in this state, holding the last reading of *V*_{in} on the display, until either the Auto/Manual switch is switched back to Auto, or the Sample/Hold switch (which is a simple, returning, push-button changeover switch) is depressed. If the Sample/Hold switch is depressed and released, the outputs of *F* and *G* are cleared to zero and the d.v.m. operates for a further three cycles until *F* and *G* are once more logical ones, when it again holds, displaying the latest reading of *V*_{in}. If, when the Auto/Manual switch is in the Auto position, the Sample/Hold switch is depressed and held down, the d.v.m. will hold its reading, after three further cycles, until the Sample/Hold switch is released. In this manner the d.v.m. can be made to continuously sample *V*_{in} and hold the information for as long as is desired by depressing the Sample/Hold switch, or sample *V*_{in} only on demand when the Sample/Hold switch is momentarily depressed.

Having described the operation of the d.v.m., there are now but a few points to clear up concerning the analogue circuit of Fig. 3. As mentioned earlier, the two comparators, 1 and 2, are *IC*₈ and *IC*₉ respectively. The two reference voltages, -2mV and +2mV, applied to the two comparators are provided by the two 100-ohm preset potentiometers and their associated circuitry. Each 100-ohm pot. provides an output voltage in the range of +12mV to -12mV, approximately. This allows for the offset tolerance of the 709 op-amps, used for the two comparators, of about ±8mV. The output of the integrating op-amp connects to the non-inverting (positive) input of each comparator via a 10-ohm resistor. A very small amount of positive feedback is applied to each comparator by feeding their outputs back to their respective positive inputs via a 220kΩ resistor. In practice this results in about 2mV of hysteresis in the switching action of the two comparators. The output of comparator 2 changes from +10V to -10V when the output from the integrator exceeds about +3mV, and changes back again to +10V when the integrator output falls to about +1mV. Comparator 1 (*IC*₉) operates in a similar manner about levels of -1mV and -3mV. This small amount of positive feedback results in a more positive switching action of the comparators without impairing their resolution. The output from the integrator is about 2.27*V*_{in}, thus 2mV

hysteresis represents a resolution of about 0.88mV, which is less than the resolution of the display (1mV).

This concludes the description of the circuitry and operation of the basic d.v.m. The rest of the article deals with the description of the a.c. rectifier circuit, a suitable input attenuator and buffer stage, power supplies and, finally, circuit board layouts and a discussion on some of the components.

References

1. Digital Multimeter, by D. E. O'N. Waddington. *Wireless World*, March 1973.
2. Digital Panel Meter, by P. Bartlam. *Wireless World*, April 1973.

Correction

In the article "Frequency Shifter for 'Howl' Suppression" by M. Hartley Jones (July issue, pp. 317-322) the following corrections should be made.

Appendix (p. 321)

In Fig. 8, the point where the ϕ_1 curve crosses the frequency axis should be labelled f_{01} instead of f_{02} .

The line immediately after equation (2), should read

$$\left| \frac{v_o}{v_i} \right| = \sqrt{\frac{\alpha^2 + \beta^2}{\alpha^2 + \beta^2}}$$

Components list (p. 322)

Unfortunately there was a duplication of resistor numbers in Fig. 4 and Fig. 6. The values given in the list refer only to Fig. 4. The following additions are necessary:

Components in Fig. 4

*R*₄₅ 6.8kΩ

*IC*₅, *IC*₆ Motorola MC1495L or Silicon General SG1495D.

Components in Fig. 6

*R*₄₄, *R*₄₅ 12kΩ


*R*₄₆ 560Ω

*C*₂₂ 470nF

In the article "F.M. Tuner Design—Two Years Later" by L. Nelson-Jones (June issue, pp. 271-275), the 68pF capacitor shown connected to the tap of *L*₃ in Fig. 2 should be connected to the emitter of *Tr*₃—as in the original article.

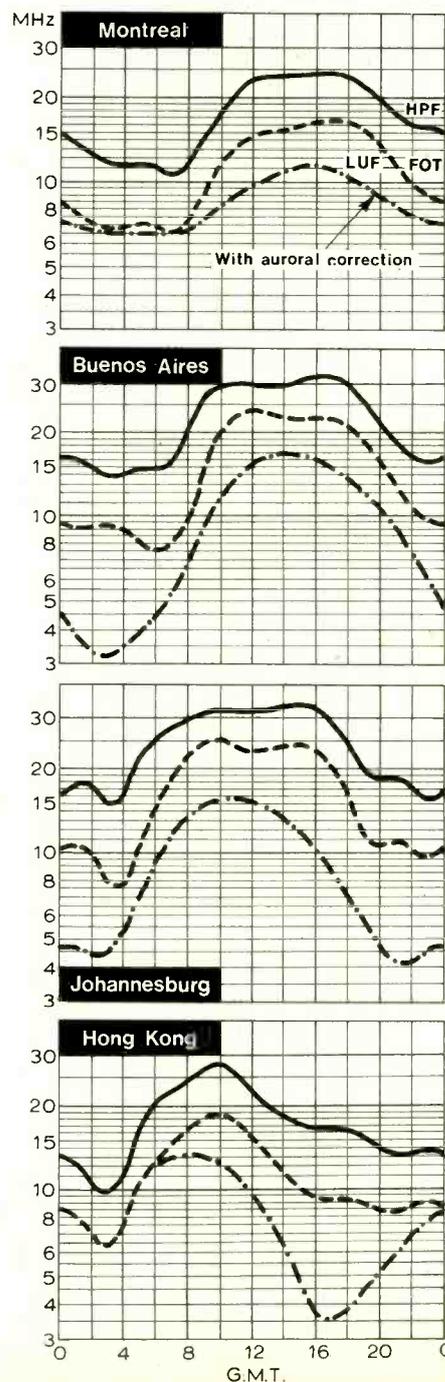H. F. Predictions for October

Magnetic disturbances at 27-day intervals (one solar rotation) have been clearly evident since January of this year. Comparison with the previous sunspot cycle minimum period (as was done for the solar index in last month's notes) shows that the current disturbances are several days longer lasting than in the corresponding year of 1962. The intensity of current disturbances has dropped over the past two months, a feature also found in 1962 when, after two or three quiet rotations, the disturbances appeared consistently with each rotation for the following two years. The next most likely period of magnetic disturbance is September 23rd to October 7th.



News of the Month

Fifth Intelsat IV satellite

The latest Intelsat IV communications satellite to be launched has undergone two weeks of testing before being placed in commercial service. The fifth to be put in orbit, it is positioned over the Atlantic Ocean and has a capacity to provide an average of 5,000 two-way telephone calls or 12 simultaneous colour television programmes. By the end of this year 91 aeriats at 73 earth stations in 55 countries are expected to be operating with the five Intelsats.

The first two Intelsat IVs were launched in January and December 1971 over the Atlantic to provide commercial services between the U.S.A. and Europe. The third was launched over the Pacific in January 1972. The fourth was launched last June over the Indian Ocean. Each satellite is designed to have a life of seven years.

New laser-induced electrical effect discovered

An unusual and totally unexpected electrical effect has been discovered by Robert J. von Gutfeld and Eugene E. Tynan at I.B.M.'s Thomas J. Watson Research Centre at Yorktown, New York.

Von Gutfeld and Tynan have found that when the surface of a thin film of a metal such as molybdenum or tungsten is irradiated with brief pulses of laser light, voltage pulses of up to 50mV are generated in the plane of the film, for 1kW of incident power. Such pulses can readily be detected without special amplification, and the planar direction of the voltage makes for simple attachment of electrical connections on the film surface.

Exploitation of the new effect could result in inexpensive arrays of fast photo-detectors responsive over a broad optical spectrum and operable over a wide temperature range. Moreover, detectors based on the new effect would be resistant to the heat-degradation characteristic of such now-common photodetectors as silicon-based devices. Some experimental detectors based on the effect in fact show an actual increase in sensitivity with rise in temperature.

The new phenomenon was discovered during studies of heat conductivity in which a pulsed laser was used to "inject"

bursts of thermal energy into small samples of various materials under controlled and monitored conditions. A temperature gradient through the depth of the irradiated films does appear to play a central role in giving rise to the voltage, at right angles to the gradient.

At least as surprising as the voltage direction is the fact that the voltage polarity remains the same, for fixed contacts, no matter how one rotates the film in its own plane around the axis of the laser beam. The only way to reverse polarity for a sample to which measurement contacts are fixed is to shine the laser beam on the other side of the film.

In a paper in the August 15 issue of *Applied Physics Letters*, Dr. von Gutfeld suggests that underlying the newly found effect is an asymmetry within the films themselves — microscopic distortion caused by such factors as stress arising while the film is being deposited and/or misplacement of atoms as they stack up while the film is being formed. This type of asymmetry would be independent of rotations around the laser-beam axis and could result in the "crosswise" voltage observed, as von Gutfeld shows by an analysis of the so-called Boltzmann transport equations, which relate symmetry structure to electrical and thermal parameters. The voltage would, in fact, be a photo-induced transient thermoelectric effect.

Alphanumerics on a TV picture

A new modular Series 204 "Display controller" from Ann Arbor Terminals, Inc., Ann Arbor, Michigan has been developed specifically for superimposing alphanumeric data on an ordinary TV picture in cable TV, closed-circuit TV, video tape recording, and annunciator applications.

The 204 has an alphanumeric display repertoire of 64 alphanumeric characters. Up to 16 lines with 32 characters per line may be displayed, and all 512 characters are stored in an internal m.o.s. dynamic shift register memory. Character size is proportional to screen size, and is typically 0.22in on an 11in screen. The controller accepts either picture video or composite sync from the video source. A choice of

three output signals is provided: alphanumerics added to the picture; alphanumerics added to the composite sync; or synchronized non-composite alphanumerics that can be mixed externally with other video signals.

A switch is provided which allows the full screen of alphanumeric data to be added to the video for data display and annunciator applications, or 1, 2, or 3 lines near the bottom of the picture for titling applications.

Congress on Acoustics — 1974

Environmental acoustics will be the theme of the Eighth International Congress on Acoustics, to be held at Imperial College, London, on 23-31 July 1974. The main address at the opening plenary session, to be held in the Royal Albert Hall, will be given by R. H. Bolt (U.S.A.). This address will be on the general subject of acoustics and the environment. Other invited speakers will be continuing this theme in a series of lectures designed to review particular aspects of the subject. Offers of papers for the sessions of contributed papers are now invited, and full details on the submission of these are contained in the Second Circular, which is available from The Administrative Secretary, 8 ICA 1974, 47 Belgrave Square, London SW1X 8QX.

Spacelab — new agreement

Six member states of the European Space Research Organization (ESRO) have recently signed the "Arrangement between certain member states of ESRO and ESRO" for the development of the Spacelab that forms the European contribution to the American space shuttle programme. The financial contributions of the six member states concerned represent 76% of the overall sum that Europe will devote to the Spacelab programme.

Berlin highlights

The Berlin radio and television exhibition is without doubt the largest and most influential entertainment electronics show in Europe. Its strength lies not only in its size — 600,000 visitors, 88,000 sq.m area and 253 exhibitors — but also in its multi-level scope. It attracts top management, marketing executives, broadcasters, designers, dealers, enthusiasts and the public from all over Europe; indeed many came from Japan and the U.S.A. But despite its huge size it is relatively easy to find ones way about because of the superb organisation; moreover most of the 1973 exhibitors occupied the same places as they did in 1971.

There was much talk about a new magnetic video disc. Thought up by a private inventor earlier this year, it is presently being developed by Bogen in Berlin. Basic idea is to produce a disc that will record and playback pictures on a conventional turntable. In this idea, scanning is achieved by a record/playback head

attached to an arm that is guided by the conventional stylus-in-groove technique. Roughly half the disc has a spiral groove to guide the arm, the remaining area being treated with chromium dioxide and scanned with 0.1 μ m-gap head attached to the arm.

So far, with a rotational speed of 156 rev/min (chosen so that 78 rev/min stroboscopic markings could be used) a playing time of 5 min and a bandwidth of about 2.5MHz has been achieved (this is about four months) and work is now directed at achieving a 12-min playing time with a speed of 78 rev/min and a bandwidth of 3MHz.

Not a challenge to the Teldec video disc yet because the TED system, as it is now called, is well advanced and will be sold in Germany this coming January, the greater challenge coming from the Philips long-playing disc (see page 474, 1972), about which more next issue.

RCA's SelectaVision MagTape system was given its European première. In this $\frac{3}{4}$ -in system, tape is retained in the cassette (called a cartridge by RCA) which means that the elaborate and no doubt expensive tape extraction mechanism of other systems is avoided.

In surround-sound systems it seems any question of standardization is being left to the market place to decide; but unfortunately not all systems are built into the hardware available. One system is not yet launched, though it was given its first public demonstration in Berlin. This is the "New Discrete" or QMX system, devised by Duane Cooper and developed by Nippon Columbia. It has the feature that software for it can be played in two quadraphonic modes, one using an inexpensive decoder and relying on the two audio channels on discs to give a very satisfactory performance. For better image definition a demodulator for two carrier channels can be added, the two additional audio channels having the feature that they are narrow bandwidth and as a consequence the highest frequency on this disc is around 36kHz rather than the 45kHz of the CD-4 system. Both mono and stereo compatibility sound excellent.


Meanwhile, more makers on the Continent are fitting the Motorola i.c. SQ decoder in their equipment.

Further details of these developments together with a brief look at some other areas of activity will be published in the next issue.

Toshiba subsidiary in U.K.

It's not well known that Toshiba first produced surround-sound equipment in 1964 — called "dynamic stereo". Lack of public interest meant shelving the development, but Toshiba haven't been slow in introducing other innovations, like a photoelectric cartridge, an i.c. cartridge and an electret capacitor cartridge. When the Japan market was ready for surround sound, Toshiba introduced their own matrix known as

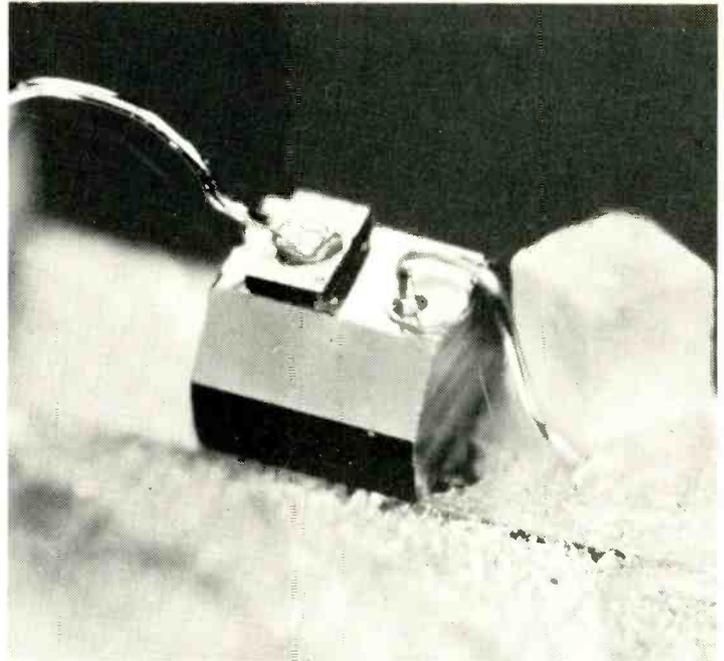Much smaller than the grain of salt to its right, this solid-state laser (small rectangle on top of block) may hasten the day when the laser proves to be sufficiently reliable, efficient and economical for a future optical communications system. Bell Laboratories' scientists have developed a system which has operated a battery-powered semiconductor laser continuously for over three months.



QM and, more recently, they have developed a new stylus shape that gives similar advantages to the JVC Shibata stylus.

Now, of course, QM has given way to RM and the current Toshiba equipment is fitted with RM and SQ decoding functions.

The range of equipment now available through 600 U.K. dealers (50 being "hi-fi" specialists) comprises 34 products. It includes two and four-channel amplifiers and tuner-amplifiers, a matrix decoder with rear amplifiers, a stereo tuner, two open-reel tape decks (one four-channel), four cassette decks (one with Philips and two with Dolby noise limiters), headphones (one with a crosstalk switch), loudspeakers and "unit audio" systems. As well, there is an 18-in solid-state colour television receiver (Toshiba have a PAL licence) at £295, three u.h.f. black and white receivers — one 14-in model using a 110-degree tube — in-car equipment, and a few other items. An unusual feature on the amplifiers is a choice of turnover frequencies for bass and treble controls of 400Hz and 1kHz.


There is only one sad point about Toshiba's entry to the U.K. market. Data sheets we have that were printed in Japan show performance curves of equipment, but the U.K. printed ones don't.

Toshiba (UK) Ltd are at Toshiba House, Great South West Road, Feltham, Middx, telephone 01-751 1281.

Miniature Solid-state TV Camera

An all solid-state television camera using an array of 10,000 photosensors with charge coupling, assembled on a 24-pin dual-in-line package, has been demonstrated in the United States. Developed by the Fairchild Camera and Instrument Corporation, it measures 3 $\frac{1}{2}$ -in \times 1 $\frac{1}{2}$ -in \times 2 $\frac{1}{4}$ -in, weighs six ounces and has

a power consumption of about one watt. The camera will work in conditions ranging from bright sunshine to subdued room lighting. Accessories include an optical viewfinder, tripod, monitor, pistol grip, a range of lenses and a separate unit providing battery power and radio transmission up to 100 feet. The camera is a commercial product and Fairchild say the price and availability will be announced later this year.

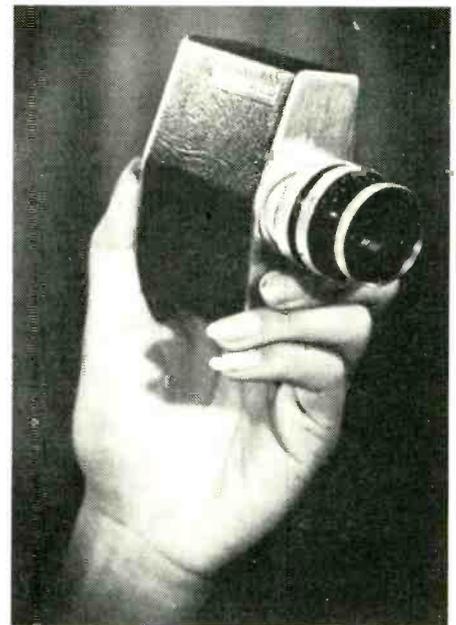

Solid-state miniature television camera made by Fairchild.

Briefly

Enter the consumer. "Consumerism is not a fad," says Nathan W. Aram, a Zenith Radio Corporation vice president. "Ignoring it will not make it go away. In fact we shouldn't want it to go away, rather let's accept consumerism. Serving today's consumer is an opportunity for all of us."

Multi-channel Proportional Remote Control

Use of t.t.l. in low cost system giving nine channels

by M. F. Bessant*

The introduction of inexpensive servo torque units and integrated-circuit pulse-width servo amplifiers has opened up new possibilities in the field of low-cost proportional remote control for general laboratory or industrial use. Unfortunately the associated drive circuitry available commercially is intended for model radio control, and is often built on the same printed-circuit cards as a 27MHz transmitter and receiver. The cost-effective application of torque units and amplifiers to a system not requiring a radio link therefore depends upon the user's ability to construct suitable drive circuitry. This article outlines a remote control system offering a maximum of nine fully proportional channels, using medium scale integration t.t.l. to obtain a low component count and level of wiring complexity, at a lower cost than currently available construction kits.

Coder

The purpose of the coder is to scan sequentially nine parallel input commands (from potentiometers for fully proportional information and switched resistors for "go/no-go" or multi-step information) and present them to the single-line data link as a series of nine varying width pulses followed by a fixed width synchronisation pulse.

To understand the operation of the coder shown in Fig. 1, it is advisable to start on familiar ground with the collector-coupled astable multivibrator formed by transistors Tr_1 , Tr_2 , and Tr_3 , then assume that on the initial application of power the decode counter holds a number between 0000 and 1001 (i.e. a b.c.d. number), say 0001. This will result in charging current being "pulled down" through channel 1 command resistor R_3 via pin 2 of the open-collector b.c.d.-to-decimal converter, thereby allowing astable action to commence. The coder's first output pulse (taken from the collector of Tr_3) will be in the 1-2ms range with an exact duration determined by the setting of R_3 . The positive transition produced at the collectors of Tr_1 and Tr_2 by the termination of this pulse clocks the counter into the next state (0010) and after a 0.25ms delay fixed by the CR time constant at the base of Tr_3 , the second coder output pulse is generated (the duration of which will this time depend upon the setting of R_4). All the command resistors will be sampled

sequentially in this manner until a count of 0000 is reached, when a 0.5ms sync pulse is generated, thus "labelling" the next output pulse as a command function corresponding to channel 1 (or 0001 again).

When displayed on an oscilloscope the repeating train of nine 1-2ms varying-width pulses, with equal 0.25ms spacing, has a distinctive "concertina" appearance (see Fig. 2(a)), with each command function being sampled approximately every 20ms. (This coding is compatible with commercial radio-control equipment should interfacing become necessary.) In the event of a non-b.c.d. number being held in the counter at

"switch on", resistor R_1 will enable the astable to free run at a low clock rate until one of the b.c.d.-to-decimal converter outputs goes low, preventing the system from locking up.

Fig. 1 shows channels 1-6 as fully proportional and channels 7-9 as "go/no-go" functions. This is only to illustrate the idea; in practice any mix of commands can be used, depending on the application.

Decoder

The decoder accepts the serial information from the coder (via some form of data link) and by detecting the sync. pulse, passes the

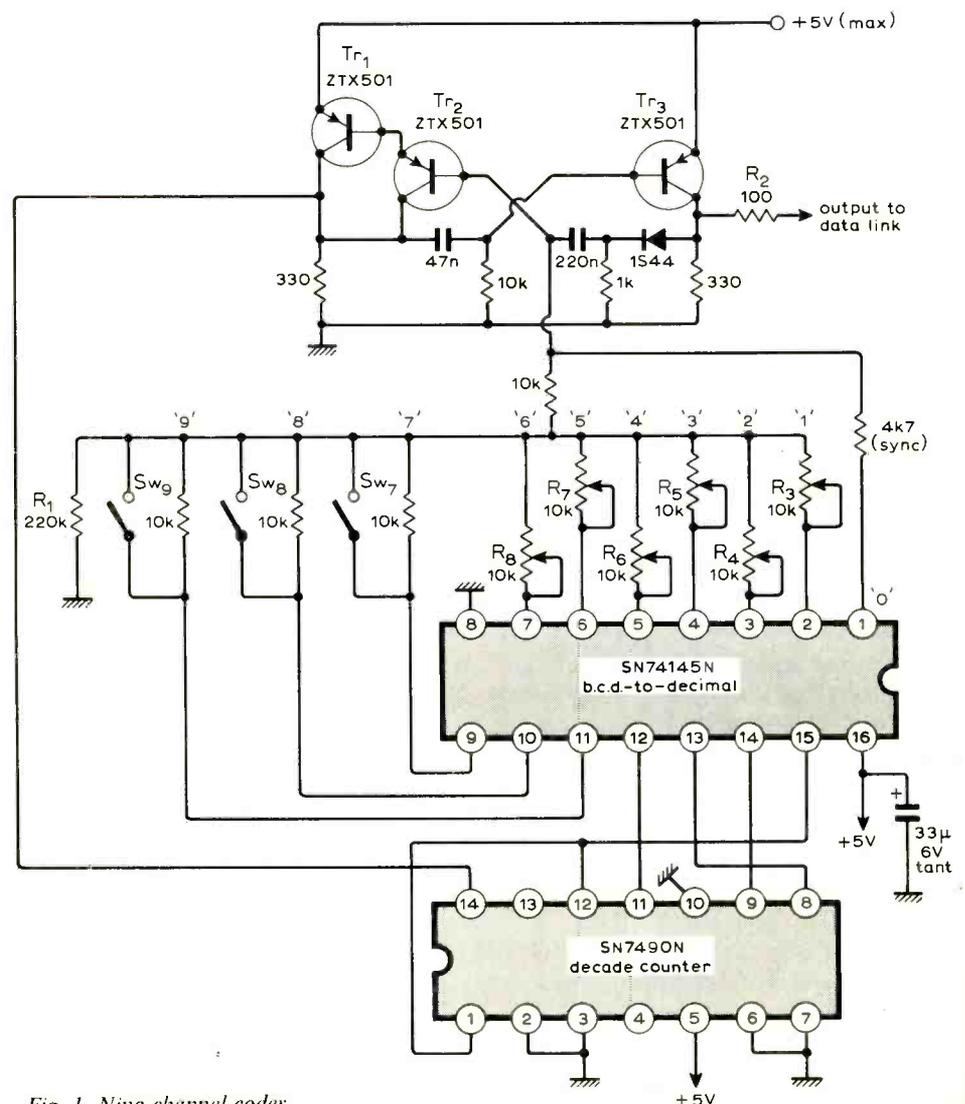


Fig. 1. Nine-channel coder.

*University of Bristol.

nine individual commands to their respective servo amplifiers. It can be seen from Figs. 2(b) and 3 that the operation of the coder and decoder is in many ways similar due to their both being effectively clocked by opposite collectors of the same astable. Both b.c.d.-to-decimal converter outputs will therefore be almost identical (the decoder output has a 0.25ms "offset") providing the counters are locked in step by the sync. detector clearing them both simultaneously. A change in the value of VR_3 for example will result in a corresponding change in the duration of the negative going pulse fed to channel 3 servo amplifier via pin 4 of the decoder's b.c.d.-to-decimal converter.

Detection of the synchronization pulse is achieved by comparing the length of inverted input pulses with the output of a 0.6ms monostable reference. Fig. 4 shows that as the minimum length of all command pulses exceeds 0.6ms only the 0.5ms sync. pulse presents the counter's internal "clear" NAND gate with two high inputs simultaneously, thus clearing the counter to 0000 before the arrival of the next channel 1 command pulse. A similar combination of reference monostable and gating could be used after the decoder to detect the "go/no-go" information pulses.

Data Link

If the data link between the output short-circuit protection resistor R_2 (Fig. 1) and the decoder's input consists of more than a simple cable link (optical coupling etc.) then care must be taken not to subject the decoder t.t.l. inputs to voltages outside the decoder's supply rail limits. Transistor Tr_4 (Fig. 3) has therefore to serve the dual purpose of logical inverter and voltage clamp.

Data link bandwidth limitations present no critical problems to decoder operation for the following reasons:

- (a) command pulse width information is carried on positive transitions only;
- (b) these transitions are reshaped before clocking the counter by the sync. detector's Schmitt/monostable. Deterioration of the incoming pulses will not, therefore, result in reduced counter noise immunity, although excessive "pulse rounding" will eventually lead to reduced servo resolution.

Compared with the widely used technique of cascading discrete-component monostables to produce "concertina" pulse trains which are then decoded by some form of shift register (s.c.r. etc.), the approach described in this article offers many advantages. One advantage not already stated is the ability to reduce the size or power consumption of the decoder simply by substituting the standard t.t.l. shown in Fig. 3 with low power or flat pack versions where appropriate.

Servo amplifier in t.t.l.

The system for driving six servo torque units from the m.s.i. decoder is based on torque units originally designed to provide radio control models with a reliable method of converting electrical commands into proportional mechanical movement.

A typical unit costing five pounds would

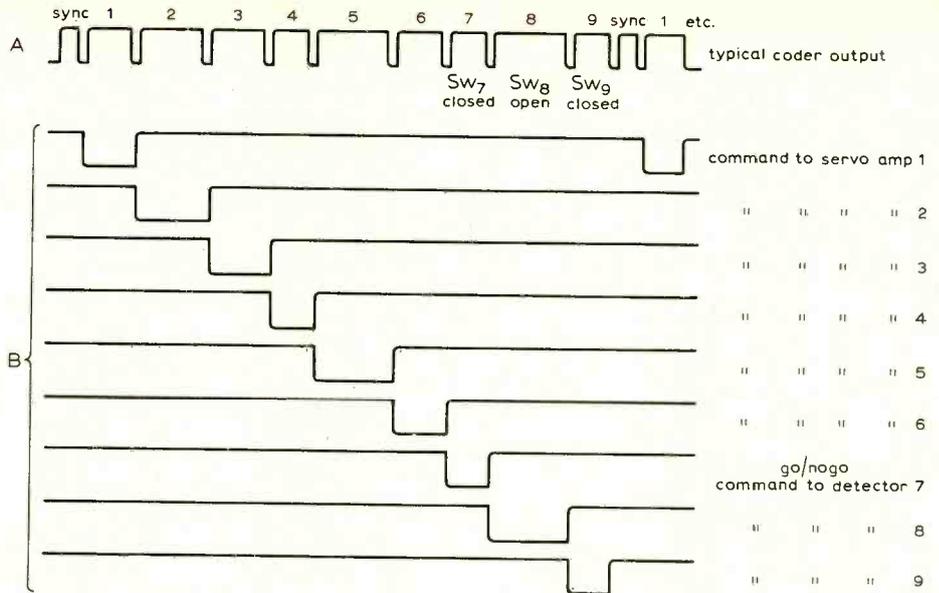


Fig. 2. Timing diagrams for (a) coder output, top, and (b) decoder output, bottom.

Fig. 3. Nine-channel decoder.


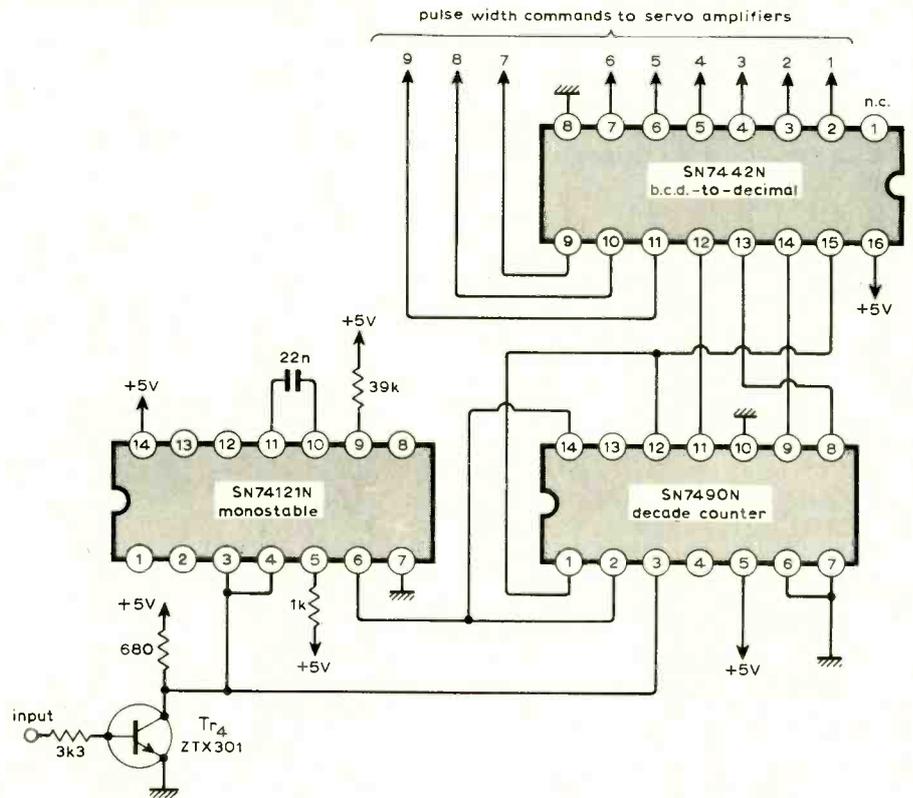


Fig. 4. Sync detector operation.

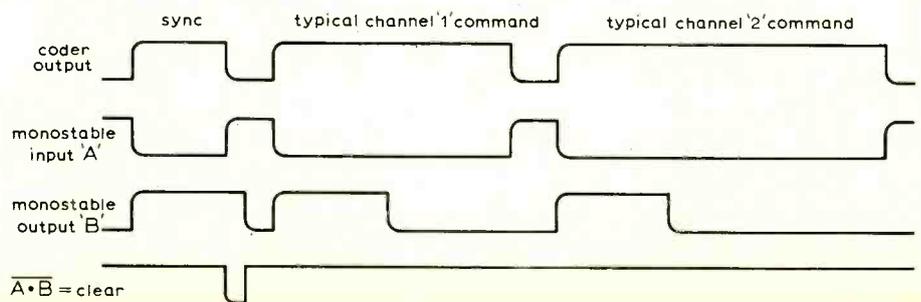

contain within its matchbox-size case a low voltage d.c. motor driving a reduction gear train, the final shaft of which connects at one end to a positional feedback potentiometer and at the other to mechanical output coupling. Backlash on this shaft would be less than 1° and stall torque approximately 15oz/in. Unloaded full drive transit time for 300° travel would be in the order of a second. These basic characteristics are compatible with low-cost, light laboratory/industrial servo applications.

The principle of pulse proportional servo control is now well established, with the most popular types of commercially available "amplifier" (for driving the motor in the required direction to cancel errors between command and feedback pulse length) falling into the following two categories:

(a) Discrete amplifiers using push-pull motor drive that require a centre-tapped supply. Apart from the high component count (typically ten semiconductor devices plus associated passive components) these amplifiers can, in the event of power supply voltage differences, have the added disadvantage of lopsided response.

(b) Integrated circuits, custom built for radio control servo manufacturers (i.e. not available directly from semiconductor manufacturers) have the obvious size and reliability advantage over discrete counterparts, plus in some cases a bridge motor drive. They are, however, rather specialized and not easily adapted to different motor voltage, gear ratio and potentiometer resistance combinations. Both fully assembled amplifiers cost between five and six pounds.

The amplifier shown in Fig. 5 is based on a t.t.l. pulse width comparator feeding a discrete bridge motor drive circuit. This combination offers a reduced component count compared with totally discrete amplifiers and improved flexibility (with comparable complexity) compared with custom i.c. amplifiers. A considerable cost saving can also be achieved if the components for all six channels are mounted on the same card (see Fig. 6). Under these conditions each t.t.l. servo amplifier will cost approximately £1.

Circuit operation

The position of the torque units output shaft determines the value of R_T which together with C_T and a 2kΩ resistor, form the feedback monostable's timing elements. Decoded command pulses trigger the monostable via an inverter and are compared with the resultant Q and \bar{Q} outputs. If the position requested by the command pulse differs from the output shaft's present position an error signal proportional to the difference in pulse lengths will appear at the output of either G_1 or G_2 open collector NAND gate depending on whether the feedback is longer or shorter in duration than the command (see Fig. 7). Provided that this error exceeds the drive amplifier's "turn-on pedestal", one side of the bridge will be turned on and the motor driven in the required direction (assuming the "sense" of the feedback is correct) to reduce the error below the turn-on level. When this is accomplished neither side of the bridge

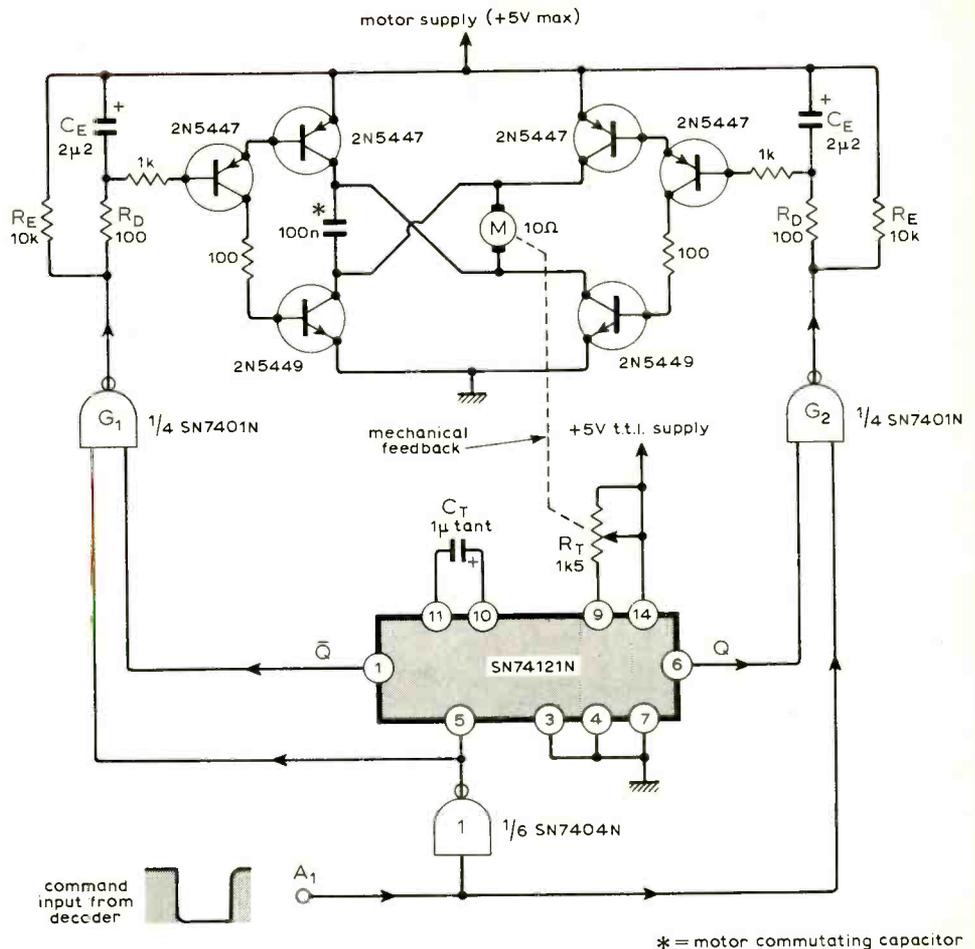


Fig. 5. Servo amplifier using t.t.l.

conducts and negligible current is drawn from the motor supply.

Expansion and deadband considerations

After being time-division multiplexed by the coder and decoder, an individual 1.25ms–2.25ms command will only appear at the input of its allotted servo amplifier approximately once every 20ms. In order to sustain motor current between commands it is therefore necessary to expand the pulse length of any error produced by the comparator. As the value of the expansion components R_E , C_D and R_D must be equal for symmetrical servo operation only one side of the bridge will be referred to below.

The pulse expansion ratio N depends on the charge and discharge time of C_E , together with the turn-on pedestal and is

$$N \approx \frac{R_E Z_{in}}{Z_{in} + R_E} \cdot \frac{1}{R_D}$$

where Z_{in} is the drive amplifier input impedance above the pedestal. In practice N must be a compromise between servo response time and "pile up" at the higher command repetition rates (i.e. all commands set to minimum width).

Resistor R_D defines the minimum error pulse capable of charging C_E to the drive amplifier's turn on pedestal and thus cause motor current to flow. An error below this level is usually referred to as being within the "deadband". In the circuit of Fig. 5 the

width of the deadband t_d is

$$t_d \approx \frac{C_E R_D}{4}$$

The minimum usable deadband width is limited by the motor and gear box inertia, which may be sufficient to cause "hunting" (oscillation about the requested position). The deadband is often expressed as a percentage of command pulse modulation. For the values given we have t_d approximately equal to 50μs with 1ms modulation; the servo is therefore said to have a 5% deadband.

Although the expansion and deadband component values shown are not critical and can be used with most commercial units in a multi-channel system, some trade off between response time and deadband may be necessary to optimize the servo for a particular application.

Complementary bridge

By using the complementary bridge configuration shown in Fig. 5 a wide range of motors can be driven (in either direction) from a single supply, and as any variation in this supply can only result in symmetrical changes in servo response time, the two main disadvantages associated with push-pull centre-tapped amplifiers has been eliminated. With the values shown the bridge is capable of saturation with motor stall current of up to 300mA (typical "motor run" current is approximately

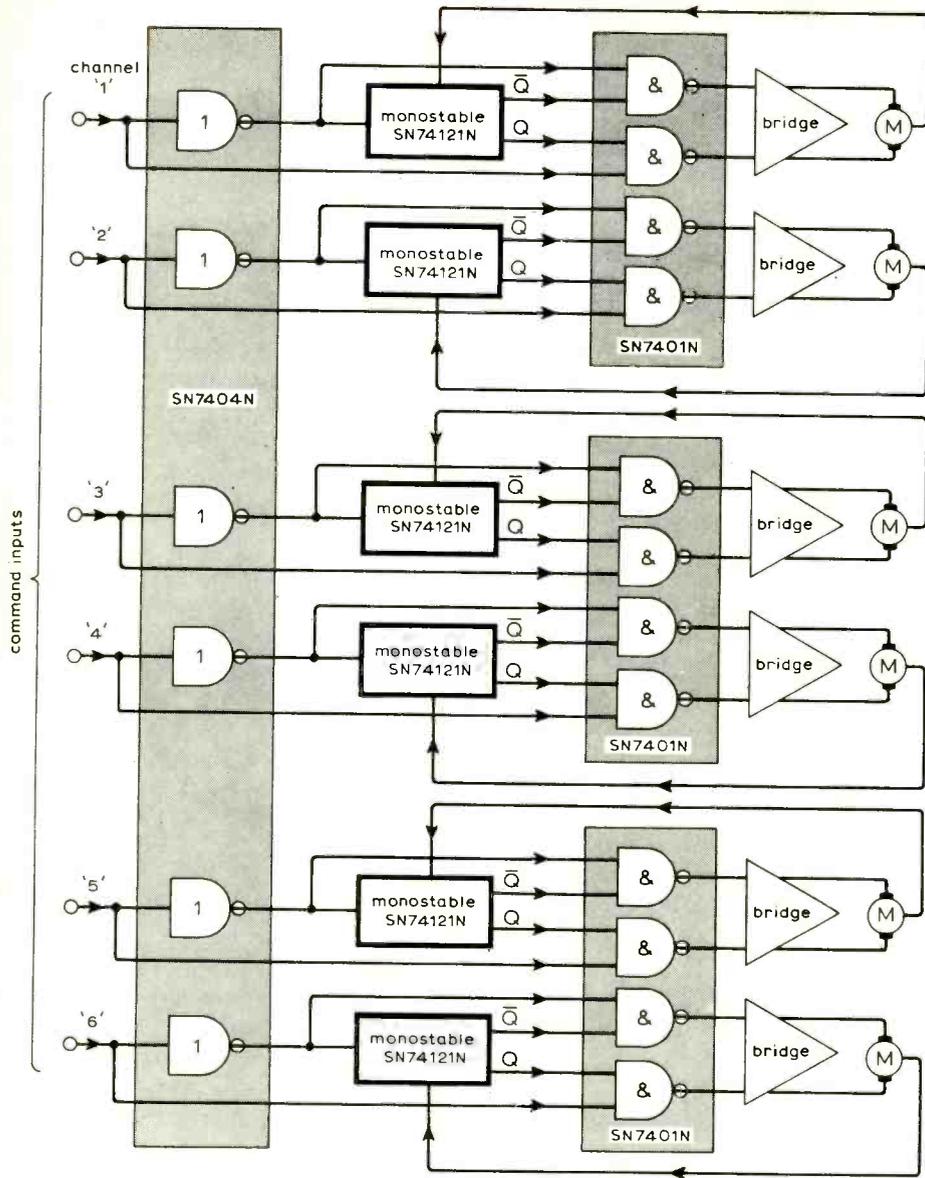


Fig. 6. Layout of components for least cost.

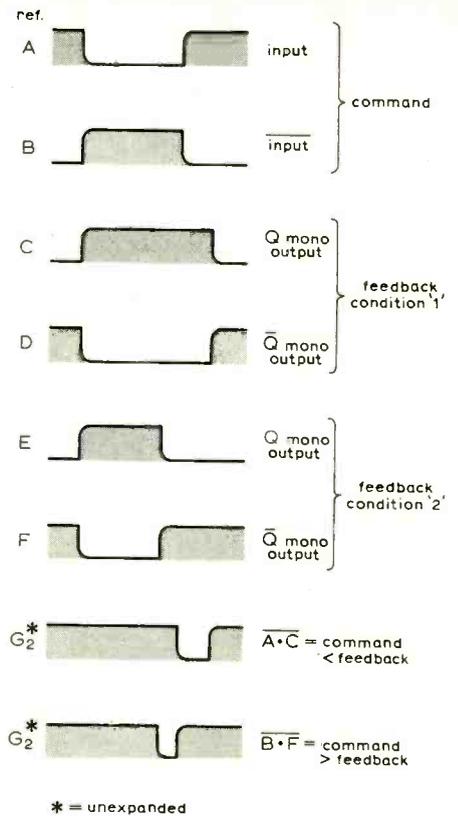


Fig. 7. Pulse-width comparator logic.

15mA). Small plastic-cased transistors are quite adequate even at higher stall currents due to the very efficient saturating nature of the bridge. In order to accommodate motor voltages in excess of the SN7410N 5-volt limit, as SN7401AN must be used, which has an open-collector rating of 15 volts. If the torque unit is capable of operating from the t.t.l. supply, decoupling between the motor and logic must be included to avoid instability.

Books Received

Transistor — TV Servicing Guide by Robert G. Middleton. The first chapter covers the overall subject of transistor servicing, test procedures, test equipment and basic circuit functions. Succeeding chapters describe the various picture and/or sound symptoms that may be encountered. A list of various circuit defects that could produce a particular symptom is presented, with procedures for analysing and isolating each effect. Price £2.25. Pp.128. W. Foulsham & Co. Ltd, Yeovil Road, Slough, SL1 4JH.

Understanding Electronic Circuits by Ian R. Sinclair explains amplifying, oscillating, switching and logic circuits, and deals extensively with the subject of integrated circuits, their merits and limitations in different applications. The level has been set for those who have some circuit wiring experience but may be uncertain of how the circuits function. Although this book is designed as a self contained work on modern circuitry, it has been written partly as a companion volume to "Understanding Elec-

tronic Components" by the same author. The two books between them offer a compact treatment covering the field of electronic components and the circuits built around them, from a practical and a theoretical point of view. Price £3.50. Pp.205. Fountain Press, Model & Allied Publications Ltd, Book Division, Station Road, Kings Langley, Hertfordshire.

Electrical Engineering Principles and testing methods by Rhys Lewis covers fundamentals of a.c. and d.c. circuits, including network theorems, three-phase a.c. systems, transformers, d.c. machines, amplifiers, instruments and principles of testing and testing methods, the latter including the basic essentials of quality control techniques. The book is for people undertaking courses leading to technician and technologist status in electrical and electronic engineering. The latter part of the book covers the common testing methods syllabus of the City and Guilds of London Institute. Much thought has also been given to the presentation

of transformer theory. Price £4.00. Pp.289. Applied Science Publishers Ltd, Ripple Road, Barking, Essex.

Lightning Protection by J. L. Marshall is an examination of the phenomenon which maintains a balance in the global electrical system. It is a collation and consolidation of available information on the nature, effects and principles of protection against lightning. Its nine chapters discuss: losses resulting from lightning; the nature of lightning; magnitude of the lightning discharge; the earth as a discharge terminal for the dissipation of energy; types of protective grounding systems and methods for measuring their effectiveness; specific measures for the protection of human life; grounding communication towers and systems; protection systems for buildings and finally protection of power-transmission systems. Bibliographies are provided at the end of each chapter. Price £7.50. Pp. 190. John Wiley & Sons Ltd, Baffins Lane, Chichester, Sussex.

Independent Local Radio

Preparations for sound broadcasting service opening in October

Commercial "Independent Local Radio" services will open in London in October with a general programme provided by Capital Radio and a special news service by the London Broadcasting Company. These will be the first two of what may eventually be as many as 60 different I.L.R. programmes in the U.K., each transmitted on both v.h.f. (Band II) and m.f. By about next spring, the London services will be joined by those for Birmingham, Manchester and Glasgow, with two more — one for Swansea, the other for Tyneside and Wearside — opening in the summer of next year. Then over the next two years stations are likely to be opened in Bradford, Edinburgh, Ipswich, Liverpool, Nottingham, Plymouth, Portsmouth, Reading, Sheffield, Teesside and Wolverhampton, though not in that order. Stations are also being planned for Belfast, Blackburn, Bournemouth, Brighton, Bristol, Cardiff, Coventry, Huddersfield and Leeds. These 27 stations should provide services for just over half of the population of the U.K.

For all these services the controlling body is the I.B.A., which will build and operate all the transmitters and, in conjunction with the Post Office, provide the distribution links. The studios and studio equipment will be the concern of the programme companies, although these are required to operate within the technical characteristics set out in a detailed I.B.A. code of practice.

The planning and engineering of an entirely new series of broadcasting services is not something that happens every day — and sound radio has a life style very different from television. The problems include:

1. The search for suitable frequency allocations with the need to achieve close co-operation with the existing users of the crowded frequency spectrum.

2. The search for suitable transmitter sites (with relatively large areas needed for m.f. aerial systems) close to major cities.

3. The provision of balanced coverage on both m.f./a.m. and v.h.f./f.m.

All these problems need to be solved without making the whole operation so costly that it would be no longer viable.

Before the Sound Broadcasting Act 1972 (now consolidated into the Indepen-

dent Broadcasting Act 1973) reached the statute book in July 1972, preliminary planning was undertaken by the Ministry of Posts and Telecommunications, and two I.B.A. engineers — J. B. Sewter and F. Wise — were temporarily seconded to M.P.T. to help in this work.

The problems of planning frequencies and coverage areas were formidable. For many years the medium-wave band in Europe has appeared to be grossly overcrowded — and this is certainly the case after dark. Yet in daytime listeners have not been well served in programme choice compared with what is theoretically feasible. So what chance was there of setting up a whole new network — each carrying a different programme — without finally breaking the camel's back?

Then again many of the views on what constitutes an adequate m.f. signal in urban centres dates back to the days before the widespread use of steel-framed buildings and car radios. And although superficially Band II might appear less crowded large sections were then occupied by police, ambulance and similar two-way mobile communications services. Further, there were some anomalies in the B.B.C. network — for example the use of Wenvoe to carry both Welsh and West regional programmes — that proved to have serious repercussions on the planning of I.L.R. stations. Again, the widening use of stereo, with its added susceptibility to adjacent channel interference, tends to emphasize the complexity of the problem. Yet another restriction arises



I.B.A. transmitter for v.h.f. coverage in London.

from the need to avoid harmonics of the 10.7MHz i.f. channel used in v.h.f. broadcast receivers.

For m.f. only one main "U.K.-assigned" channel (261m, 1151kHz) is being made available exclusively for I.L.R. stations; 1546kHz (194m) will be shared with B.B.C. stations; other frequencies will be those internationally agreed under Article 8 of the 1948 Copenhagen Convention and Article 9 of the Radio Regulations.


Despite these various limitations, the I.B.A. engineers felt that the setting up of a new system provided an unusual opportunity to look afresh at the technical side of sound broadcasting. Much of the standard work in this field dates back to the 'thirties before the "distraction" of television.

A small team from what was then still the I.T.A. visited North America to investigate recent experience in designing and operating local radio stations in the United States and Canada. What they found made a profound impression. For example advantage was being taken by many v.h.f. stations of mixed polarization — circular or slant polarized signals — to provide a better and more homogeneous coverage for car radios and portables using telescopic v.h.f. whip aerials; again, on m.f., there was growing use of complex directional transmitting aerials using quite large numbers of mast radiators and capable of producing deep nulls in the radiation pattern to limit interference with co-channel stations. It was also noted that American practice aimed at providing relatively strong signals in the centres of towns to overcome local screening. It is not unusual to find American planning based on providing m.f. field strengths of 50 or even 100 mV/m in city centres. One result has been that after many discussions, the contour of 3 mV/m has now been adopted for the planning of m.f. stations for the I.L.R. system: it is no secret that higher figures were proposed.

The combination of strong signals and multiple use of the same channel may seem mutually contradictory — and this would certainly be the case were the network to depend on omni-directional transmitting aerials. By opting for three- and four-mast radiators, the I.B.A. are planning to use 1151kHz in London, Birmingham, Manchester and Glasgow.

This again imposes important restrictions on the choice of m.f. sites. In the London area no less than 200 different sites were investigated. The need to reduce radiation towards Birmingham points to a site to the north-west of London from which signals can be directed over the main London area while minimized in the Birmingham direction.

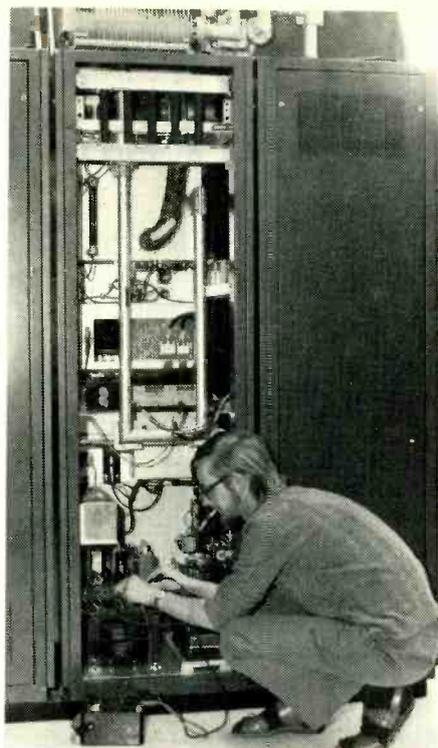Such sites are difficult to find — an even greater difficulty is that of obtaining planning permission for their use. Local authorities and local opinion are acutely conscious of questions of "environment" and they approach any suggestion of a site requiring the erection of a number of moderately high aerials with more than a little misgiving. It soon became



Working on the London v.h.f. transmitter.

clear to the I.B.A. that permission to use any of the possible sites in north-west London would take time, and might delay the start of the service. For that reason the decision was taken to find a temporary site where an omni-directional aerial would prove reasonably effective. This has resulted in the m.f. station at the London Transport Executive's power station at Lots Road, Chelsea, where the tall chimneys provide supports for a simple wire T aerial. The aerial has a 212ft twin-wire top loading section with a 275ft vertical radiating section in conjunction with a very effective earthing system which benefits from the presence of the Thames. The same aerial is used simultaneously for transmissions on 557kHz and 719kHz to be used by Capital Radio and London Broadcasting Company respectively. Despite the low power — less than 500 watts e.r.p. — the coverage achieved by this station is extremely good.

Clearance for the use of 557kHz was sought in the summer of 1972 when the interference levels in the London area were shown to be low; subsequently the unauthorized ship station "Radio Veronica" off the Dutch coast moved on to this channel. Veronica causes some interference in the eastern part of the London area and more especially in areas beyond the intended coverage. I.B.A. hope to transfer these services to the permanent site at Saffron Green, near Barnet, towards the end of 1974.

For v.h.f. coverage in London a suitable site exists at the I.B.A. 405-line television station at Croydon. This introduces to the London area the problem of v.h.f. broadcasting from different sites (the B.B.C. station is at Wrotham, Kent) but it was felt that the more central site offered significant advantages. To overcome the problem of "swamping" local

listeners a special transmitting aerial with a narrow beam in the vertical plane has been adopted (see April 1973 issue, p.175). The aerial — the first broadcast aerial in the U.K. designed for circular polarization — is of six tiers, with the result that all homes less than about a mile away "see" less than 100 watts e.r.p. compared with the 2kW in the main lobe.

Surveys made since the start of some preliminary tests in July-August 1973 suggest that generally there is less than 6dB difference between horizontal and vertical components of the signal, with a tendency for the vertical component to be slightly stronger towards the north. American experience suggests that although polarization is relatively unimportant in cluttered surroundings, the use of circular polarization can in clear sites give an advantage of between 6 and 12dB where reception is on portable or car receivers. The I.B.A. intend to use circular or slant polarization at all stations where new v.h.f. aerials are installed; generally circular polarization will be used.

The v.h.f. stations are designed for pilot-tone stereo and a stereo link is being provided between the local studios and the v.h.f. transmitters — because of the local nature of this operation the problems associated with nation-wide stereo distribution do not arise. It is expected that the programme companies (other than the special news station) will make considerable use of locally originated stereo. In addition, the studios will be linked by a monophonic "music" line to the local m.f. station. There will also be a monophonic distribution link between the London news station and all stations requiring a news feed.

The engineering of I.L.R. has meant the setting up of a new local radio planning group within the I.B.A. Engineering Division and a local radio section within the existing station design and construction department; most of the other work has been achieved within the structure established for television.

What is regarded as a most important engineering pre-requisite has been the drawing up and issue of a detailed Code of Practice for the technical performance of studios and the specification of audio distortion measurements. This has provided the various programme companies with a clear idea of the technical standards expected from them. It includes, for example, sections on studio acoustics, in terms of reverberation time and ambient noise levels. It is part of the determination that I.L.R. broadcasting will be based on up-to-date engineering techniques and equipment.

Clearly companies will need some time to gain experience of their facilities — time scales are such that some equipment for the London operations is likely to arrive only hours away from the start of service. But once the settling down period is over it will be fascinating to see what new head of steam is given to sound broadcasting in the United Kingdom.

Electronic Sound Synthesizer: Part 3

Final circuit details, interconnection of functions by patch-panel, keyboard and joystick control

by T. Orr† *B.Sc. and D. W. Thomas† Ph.D., M.I.E.R.E.

The final part of this series describing the construction and operation of a sound synthesizer completes the circuit functions provided with sample and hold, noise sources and the waveform generator circuitry.

Sample and hold

It is very useful to have an analogue memory function, for use in such cases as a long fadeout where a constant control signal may be required throughout. One method of implementing this requirement is to use a sample and hold device with the following characteristics. The output should have a very small offset voltage coupled with a low output impedance; also a long storage time, so that the output voltage will only drift by a few per cent per minute; and a high accuracy over the specified input range. The sampling period is relatively short, being initiated by a positive-going pulse. Also, there is no input buffer because the output impedance of all the units of the synthesizer is low. The input voltage range is approximately $-0.5V$ to $+6.5V$, being deliberately limited by D_1 (Fig. 28).

The signal is stored on C_3 , a low leakage capacitor, which is connected to the input voltage by an f.e.t. (Tr_1). This transistor is used as an analogue gate and is controlled by a monostable ($Tr_{5,6,7}$). During the monostable period, the gate is opened and the signal is sampled. The voltage stored on C_3 is monitored by Tr_3 , a current-driven source follower which can be preset to give a zero input/output offset voltage. Using a 500Ω source resistor, the spread in V_{GS} may range from about $-0.5V$ to $-5.0V$, for drain current drives from about $0.5mA$ to $10mA$, respectively. The constant current source may be pre-set to lie anywhere in this range. Thus by keeping Tr_3 operating in its saturation region, and maintaining I_D virtually constant, variations in V_{GS} can be kept very low for considerable changes in V_{DS} .

Setting up procedure: set R_4 to about 500Ω (this is the "fine adjust" and it is preferable that R_4 is a trimmer) and, with the input short-circuited, initiate the sampling with a positive pulse (this clears any charge on C_3). Adjust R_8 until the output voltage is as near to zero as possible and then use R_4 to finely "zero" the output.

Storage time with input short-circuited is 30 minutes for 5% droop and sampling time 14ms.

Noise sources

The noise sources fill two functions, firstly, a source of noise that can be filtered and modulated, and secondly, a low frequency source that can be used as a randomly fluctuating control voltage. This was achieved by constructing a white noise source and injecting the output into a spectrum shaping network and a low pass filter.

White noise source

The major difficulty in producing a simple, reliable white noise source is the very nature of noise itself; it is non-deterministic. Several methods were available, but the simplest and cheapest seemed to be the use of the leakage current I_{CBO} of a faulty (high leakage) germanium transistor. However, this approach requires that the leaky transistor is specially selected, or even manufactured by gentle frying! A suitable device (Tr_1) Fig. 29, should produce an average noise level of approximately $40mV$ pk-pk, when used in the configuration shown. The white noise generator consists of three parts; the noise source Tr_1 , an equalized high gain amplifier, and an output buffer. A high gain amplifier is used because the signal level from Tr_1 is relatively low, thus particular care must be taken to

isolate Tr_1 and the input of the amplifier from any power supply fluctuations. Preset R_3 is adjusted to give a suitable output level of between 2 to $3V$ pk-pk average.

Coloured noise source

Coloured noise is produced by driving a spectrum shaping network with white noise, this network being a Baxandall tone control. Preset R_{17} is adjusted so that with both tone control pots at maximum the output shows no signs of clipping.

V.L.F. noise


Very low frequency noise is extracted from the white noise source by two low pass filters, only one of which is available at one time, the selection being made by operating switch S_1 , Fig. 29. One of the drawbacks of this method of producing v.l.f. noise, is that very little signal remains after filtering, the amplitude rapidly diminishing with decreasing cut-off frequency.

Preset R_{42} is adjusted so that the two v.l.f. outputs have the same amplitude, of approximately $3V$ pk-pk average.

Waveform generator

The waveform generator produces a control voltage that may be used to either frequency or amplitude modulate other units. The

Fig. 28. Circuit providing the sample and hold functions. Resistors are 5%, 1/4W, capacitor C_3 should be a polyester low-leakage type.

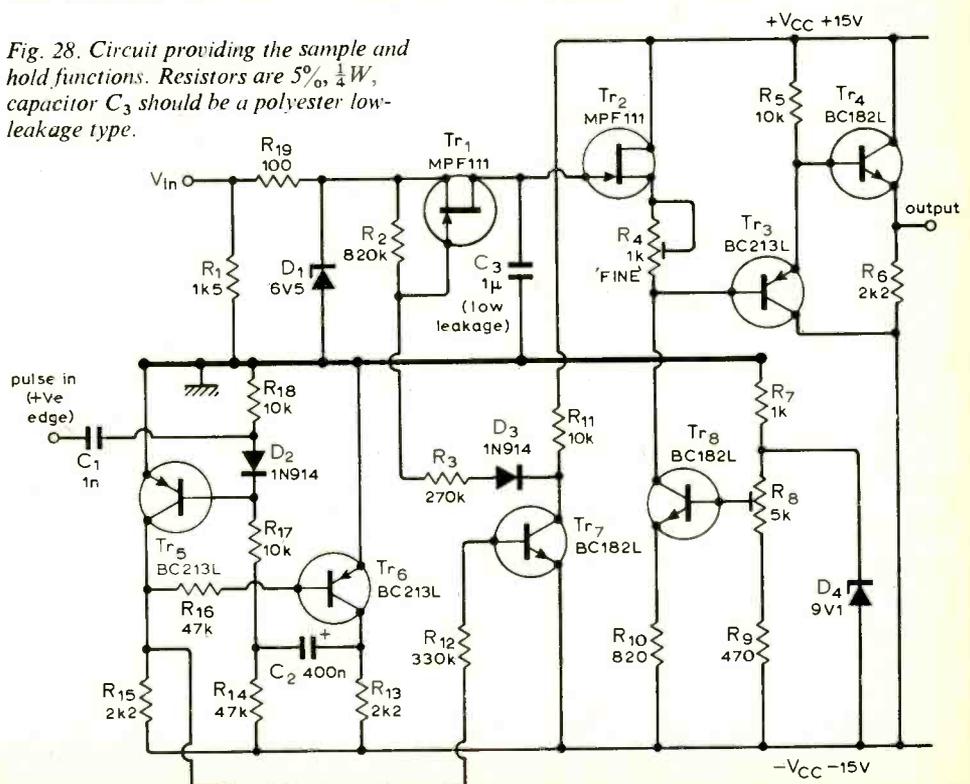

†University of Southampton
*Now with Electronic Music Studios Ltd

start of the waveform is initiated by a pulse input, the output rises "exponentially" and, after a predetermined period, falls "exponentially" (Fig. 30). Three controls are provided, attack, duration and decay and the pulse may be introduced electronically or from a manual pulse source.

The circuit operation is as follows (see Fig. 31). The first section is a current driven monostable, the monostable period or duration being controlled by the current drive which is proportional to the wiper setting of R_6 . The monostable is triggered by either a positive going input pulse or from a manual pulse upon release. The square wave produced is then fed into the attack/decay section where a capacitor is charged via the attack control R_{14} and diode D_3 . When the monostable period is over, the capacitor discharges via R_{12} , the decay control, and D_2 . The potential across the

capacitor is monitored, and an attenuated and buffered output signal is produced. A choice of duration times is available (C_3 or $C_3 + C_4$ with S_1 closed) and also a choice of time constants (C_6 or $C_6 + C_7$ with S_2 closed).

Joystick control



The joystick is a mechanically controlled voltage source having two degrees of freedom, and thus generating two independent control voltages, which are proportional to the stick's position. The device is essentially a position transducer (Fig. 32) with two sense pots (R_4 and R_8 , Fig. 33) mounted orthogonally. The range of the joystick is limited by the rectangular opening in the front panel giving approximately 90° of freedom in both the x and y directions. An extra pot can also be seen (Fig. 32) but this is used only as a spindle. The connecting

cable should be thin and flexible so as to present as little restriction as possible to the stick's movement. Also, this cable should be firmly held by two 'P' clips, one on the joystick assembly and one on the front panel so as to stop continual wear on the soldered connections.

The circuit function is illustrated in Fig. 34. A constant potential is maintained across the control pots $R_{4,8}$, in Fig. 33 and by the zener diodes $D_{2,3}$. Also, the potential of these pots relative to 0V may be shifted by presets $R_{2,6}$. Wiper crackle is attenuated by capacitors $C_{3,5}$ and the wiper is buffered to the output by $Tr_{2,3}$ and $Tr_{5,6}$. With the joystick in the bottom left hand corner of its range, the two outputs x and y are zeroed by adjusting $R_{2,6}$; movement of the joystick in the x and y directions will then produce corresponding positive increases in the potential of the respective outputs.

Keyboard

The keyboard generates a control voltage that is linearly proportional to the status of the key that is pressed. This voltage is produced for the duration of the key's depression, returning to 0V when the key is released. If two or more keys are pressed, the highest frequency key is selected automatically. Also, when a key is pressed, a pulse is generated, this being intended to trigger the waveform generator or the sample and hold unit. However, if the

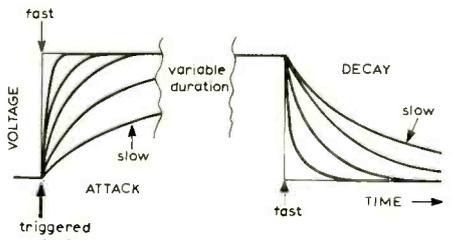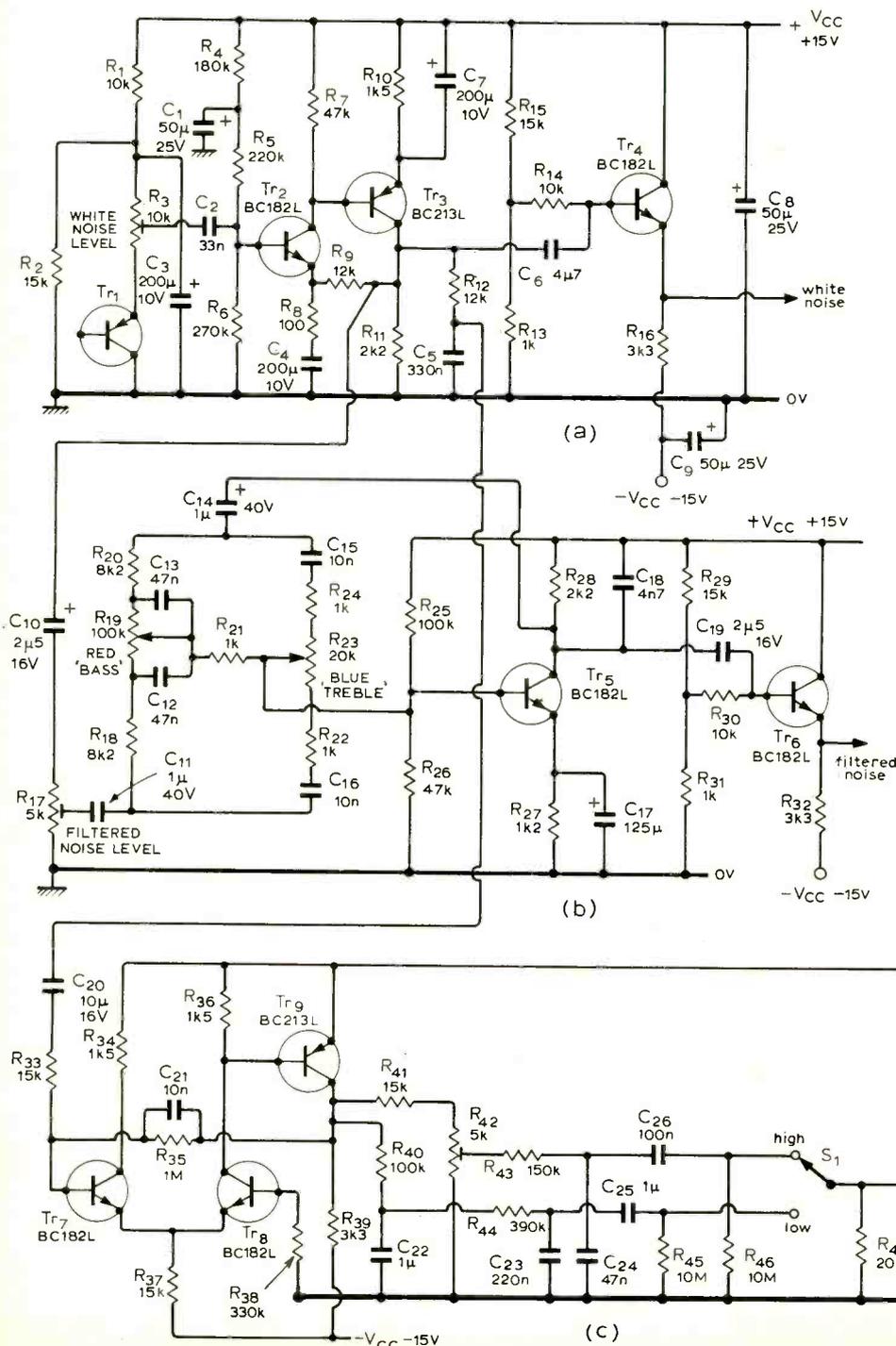

	ATTACK	DECAY	DURATION
	fast	slow	short
	slow	slow	long
	fast	v. fast	short
	slow	fast	long

Fig. 30. Outputs available from the waveform generator.

Fig. 29. Noise source circuitry which provides white, filtered or v.l.f. noise. Resistors are 5%, 1/4W, capacitors $C_{22} - C_{26}$ are polyester low-leakage types.

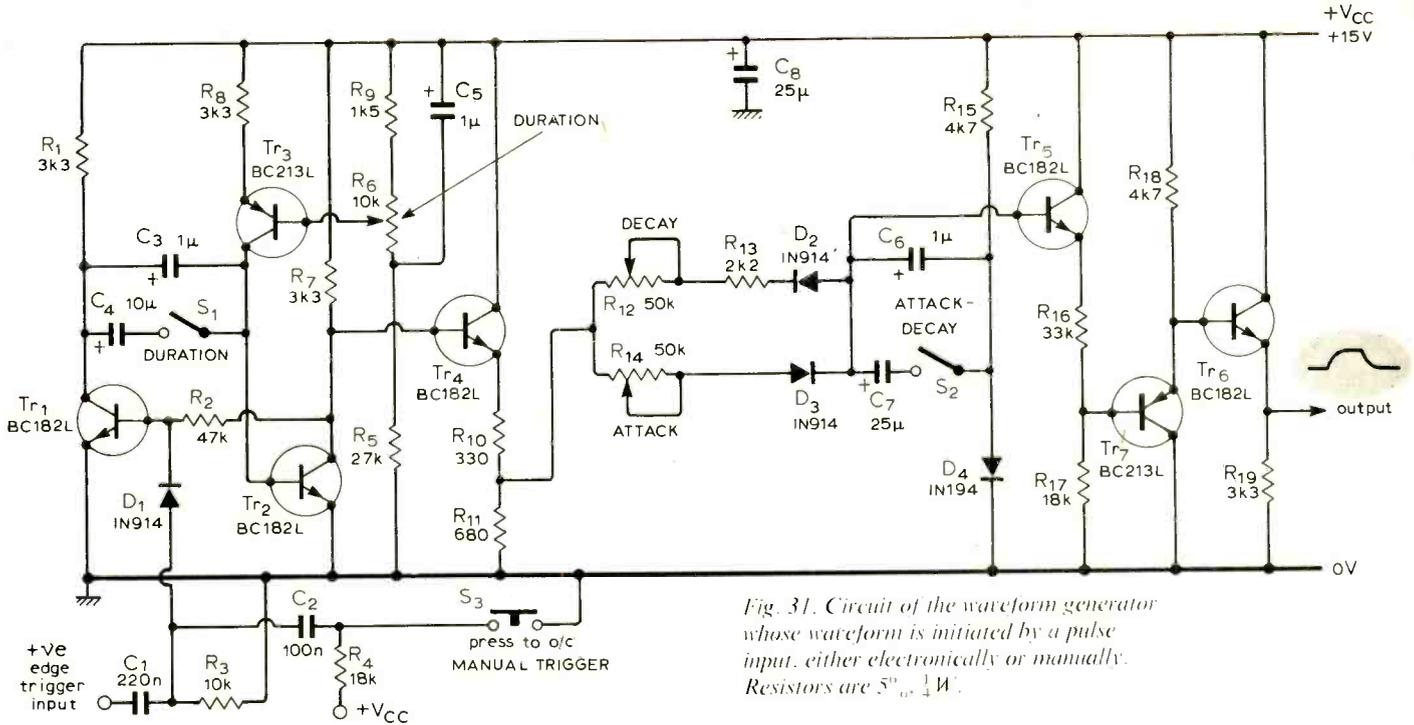


Fig. 31. Circuit of the waveform generator whose waveform is initiated by a pulse input, either electronically or manually. Resistors are 5%, 1/4 W.

production of this trigger pulse is required, then care must be taken when playing the keyboard to ensure that each key is released before the next key is pressed. If this procedure is not observed, then, even though the control voltage does change correctly, no pulse will be generated. The result is the production of a signal somewhat different to that intended.

The keyboard control circuit is shown in Fig. 35. A constant potential is maintained across resistors R₁ to R₄₈, and as all these resistors are the same, they form a potential divider composed of equally spaced steps. The switches S₁ to S₄₉ are operated by the keyboard and form, with diodes D₁ to D₄₉ and resistor R₅₁, a "Minof" analogue gate. Thus, whatever combination of switches are pressed, the most negative voltage is selected, this voltage appearing at the emitter of Tr₃. Note that when no switches are pressed, the emitter of Tr₃ rises to nearly +V_{cc}. This voltage must be modified so that it is in a suitable form to act as a control

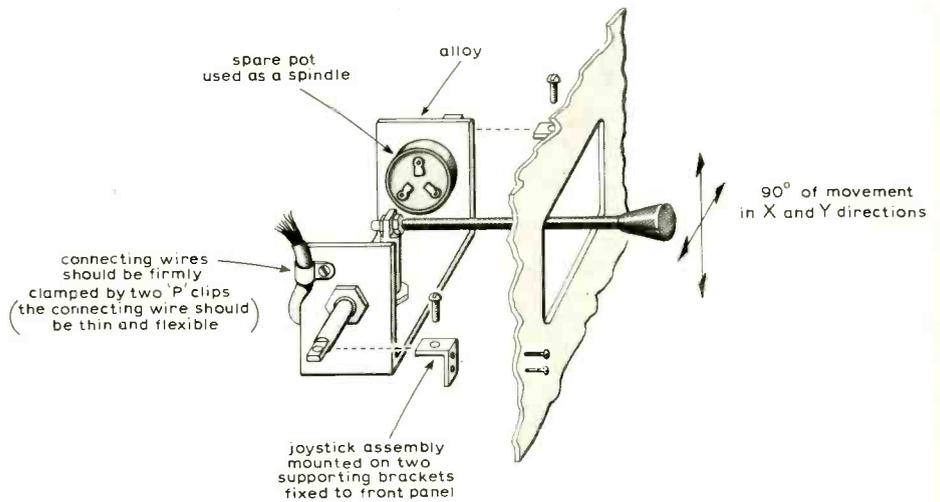


Fig. 32. Mechanical assembly of the joystick control.

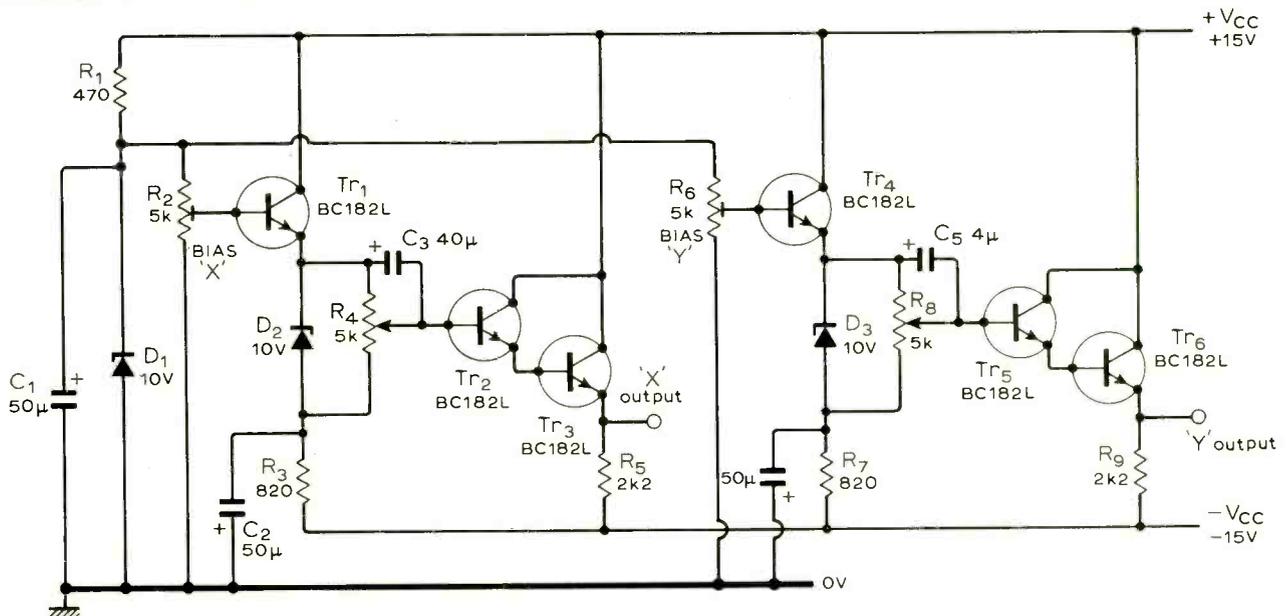


Fig. 33. Circuitry associated with the joystick control. Resistors are 5%, 1/4 W.

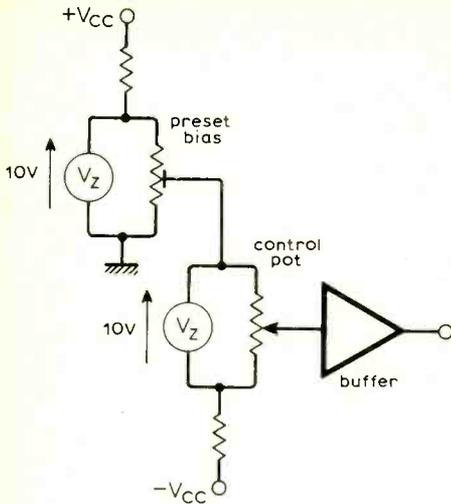


Fig. 34. Illustration of the joystick control circuit function.

Fig. 35. Keyboard control circuit. Switches S_1 to S_{49} are operated by the keyboard and form with diodes D_1 to D_{49} and resistor R_{51} , a "Minof" analogue gate. Resistors are 5%, $\frac{1}{4}W$.

signal. It is attenuated (R_{55}), inverted and its d.c. level is shifted (R_{59}) so that the range of outputs is from 0V to +3V. Also, the feedback around IC_1 is such that when no keys are pressed, and the emitter of Tr_3 rises to nearly + V_{CC} , the output (V_C) is prevented from going negative, and stays at 0V.

It is required that a pulse is generated at the moment when a key is pressed, but not when it is released. This would be a simple response to achieve (by detecting the transition direction of the "Minof" voltage) if it were not for the phenomenon of contact bounce. The spikes produced by the bounce can be largely suppressed (C_3) but there is still a possibility of generating a pulse by mistake. One method of overcoming this dilemma is to use a Schmitt trigger with a sizeable hysteresis loop, so that, as the "Minof" signal plus spikes rises or falls, it causes the Schmitt to change state only once. The direction of this change is determined by whether the input is rising or falling (i.e. whether the key is being released or pressed) and can thus be made to produce a pulse only on the falling transient.

Some applications of the keyboard are given in Fig. 36. Fig. 36(a) shows a patch

diagram of simulated piano sound. A sinusoidal signal is given a fast attack and a slow decay. Note that the control output (V_C) from the keyboard is modified by the exponential converter, so that an equally tempered scale is produced. However, if the key is prematurely released, the output promptly changes frequency. Fig. 36(b) overcomes this difficulty, by using the sample and hold circuit to store the control signal. Also, reverberation with a slow sinusoidal modulation has been added producing a pleasant effect similar to a xylophone. Fig. 36(c) shows a network for producing bell-like "clanging" noises.

Patch panel


To provide a flexible means of programming the synthesizer, a patch panel similar to the type used in analogue computers has been included. As the input and output impedance of all the units is low, it was possible to use an unscreened system. In fact, ordinary 4mm banana plugs and sockets were eventually chosen, this decision being greatly influenced by cost factors. This choice, however, presents a danger of damage due to misuse. If two outputs are connected together, then it is possible that some damage will eventually occur, although how long it takes is difficult to predict. Certainly, from previous experience of a similar synthesizer, no lasting damage was seen to occur when an error of this sort was made. To minimize this danger the sockets are coloured, all the inputs being yellow, the outputs being any other colour.

The synthesizers on the market appear to have overcome this difficulty, but at some cost. One method is to employ a series of horizontal and parallel conductors, one set being the inputs, the other set the outputs. Pins are then plugged in to make a connection between an input and an output, thus the danger of an "output to output" never arises. Other methods are to use switches or jack plugs instead of pins. These systems are all pre-wired and so another problem, that of the "birds' nest" of patch cords (an all too familiar sight to those who have ever used an analogue computer) has also been eliminated. However, this advantage has been gained at some expense.

The layout of the patch panel was determined on a logical basis; that is, all the oscillators on one section, the v.c.as and v.c.f. in another, the noise sources in one block etc. Also, to make connections with an external amplifier, a coax. socket was included as well as two sockets which were connected to "ground" potential, these being used as a 0V reference point for external equipment such as voltmeters or oscilloscopes.

Power supply

Many units of the synthesizer are sensitive to power supply fluctuations and so a stabilized supply is desirable. The circuit diagram of the supply used is given in Fig. 37. Without this suppression it is possible to trigger a response by switching on and off unconnected (except via the mains) equipment. Care should be taken in constructing the power supply to avoid introducing any high current paths that might adversely affect the circuit operation.

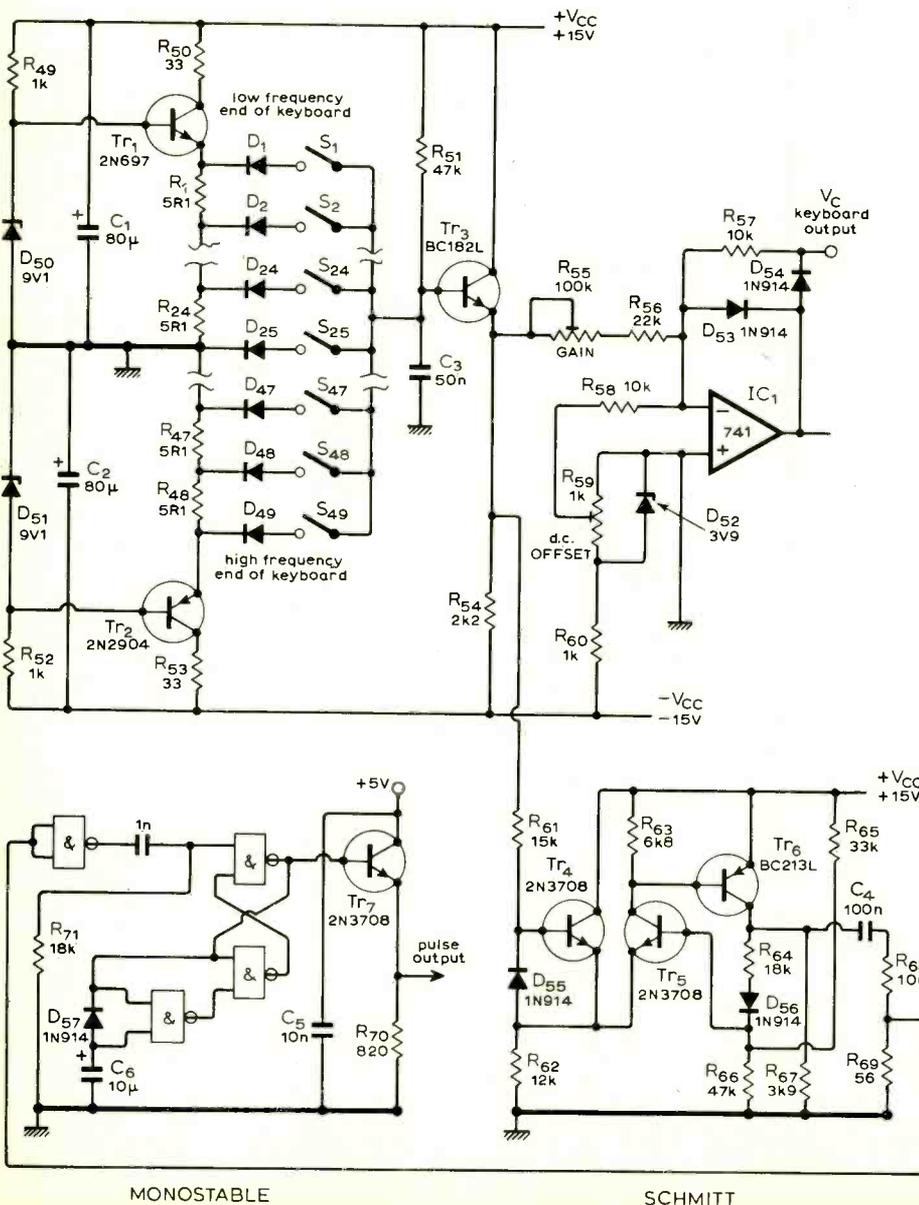

Appendix
Voltage controlled filter

Consider a bandpass filter consisting of a series LCR network. The behaviour of this system is characterized by a linear second order differential equation with constant coefficients. Using analogue techniques, it is possible to model this system, but more important it is possible to make the coefficients variable, in fact, voltage controlled.

The general equation of a linear second order system is

$$F(t) = \ddot{x} + 2k\omega_n\dot{x} + \omega_n^2x$$

Where ω_n is the undamped natural frequency, k is the damping factor (note, the quality factor $Q = 1/2k$), and $F(t)$ is a generalized forcing function. The solution of this equation consists of two parts; the particular integral that depends on $F(t)$, and the complementary function that depends on the solution of the right hand side only. Using the network shown in Fig. 38(a) it is possible to implement the complete solution. Different forms of $F(t)$ can be inserted, and by varying pots 4 and 5, the values of ω_n^2 and $2k\omega_n$ can be modified. By monitoring the voltage at the output of integrator 1 ($-\dot{x}$), the response of a bandpass filter, with the same coefficients, under the influence of the same forcing function $F(t)$, is observed. (The coefficients for a series LCR circuit would be $\omega_n = 1/LC$ and $k = R/2C/L$). By monitoring x , a low pass response would be seen, and \ddot{x} a high pass response. If pot 4 were an electronic

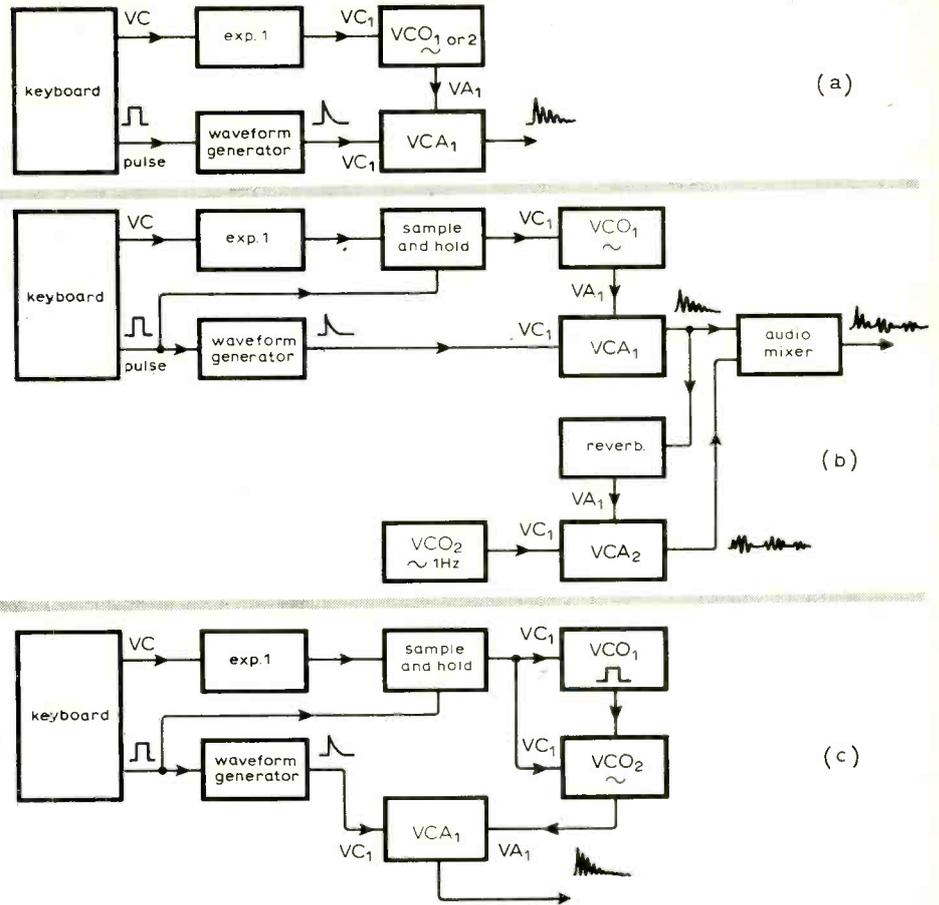


Fig. 36. Three examples of how the patch-board can be programmed for a particular sound synthesis. See text for explanation.


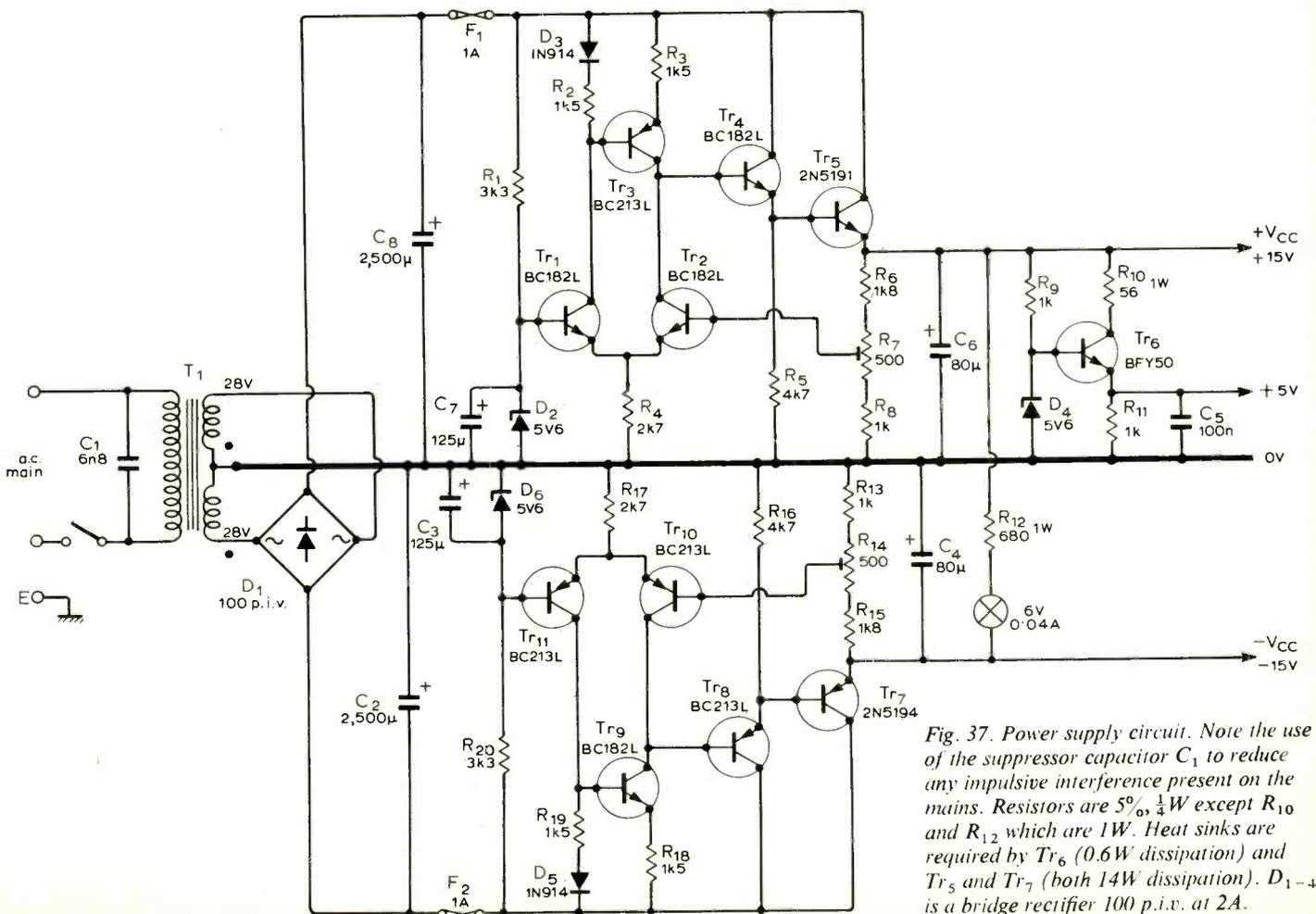


Fig. 37. Power supply circuit. Note the use of the suppressor capacitor C_1 to reduce any impulsive interference present on the mains. Resistors are 5%, 1/4W except R_{10} and R_{12} which are 1W. Heat sinks are required by Tr_6 (0.6W dissipation) and Tr_5 and Tr_7 (both 14W dissipation). D_{1-4} is a bridge rectifier 100 p.i.v. at 2A.

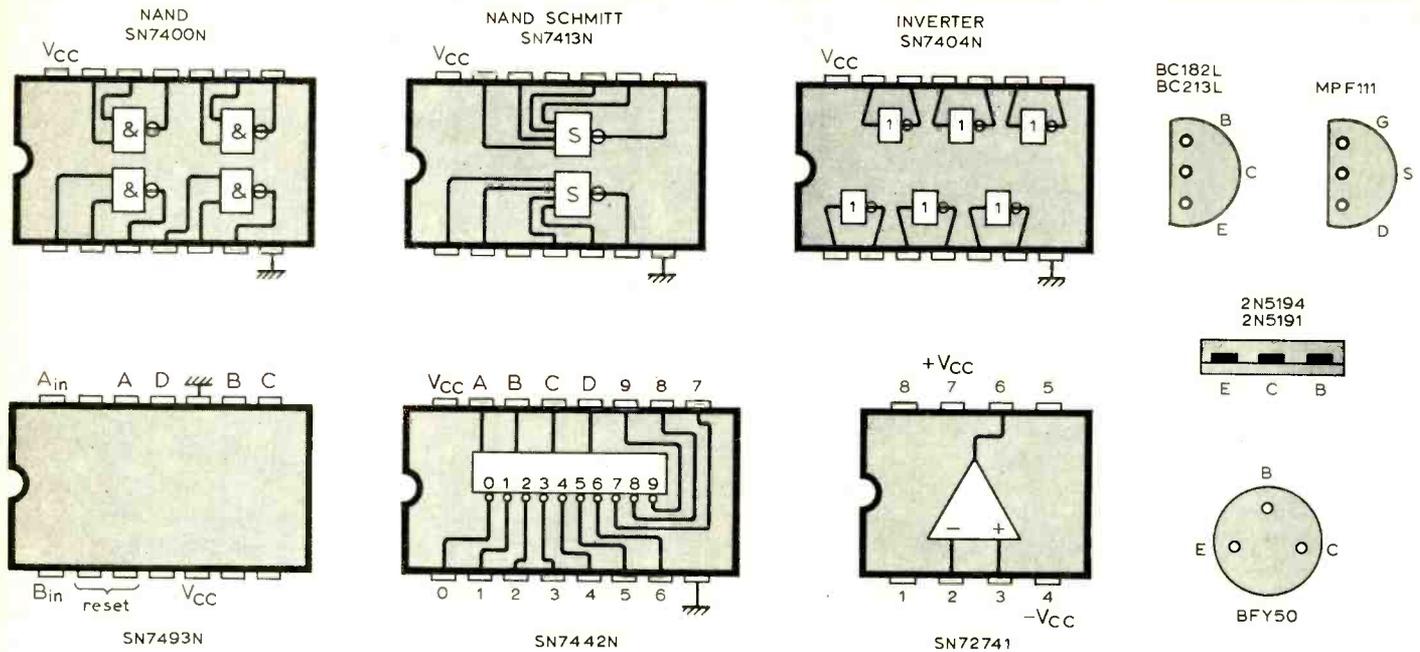

Pin connections for the transistors and integrated circuits used in the synthesizer's circuitry.

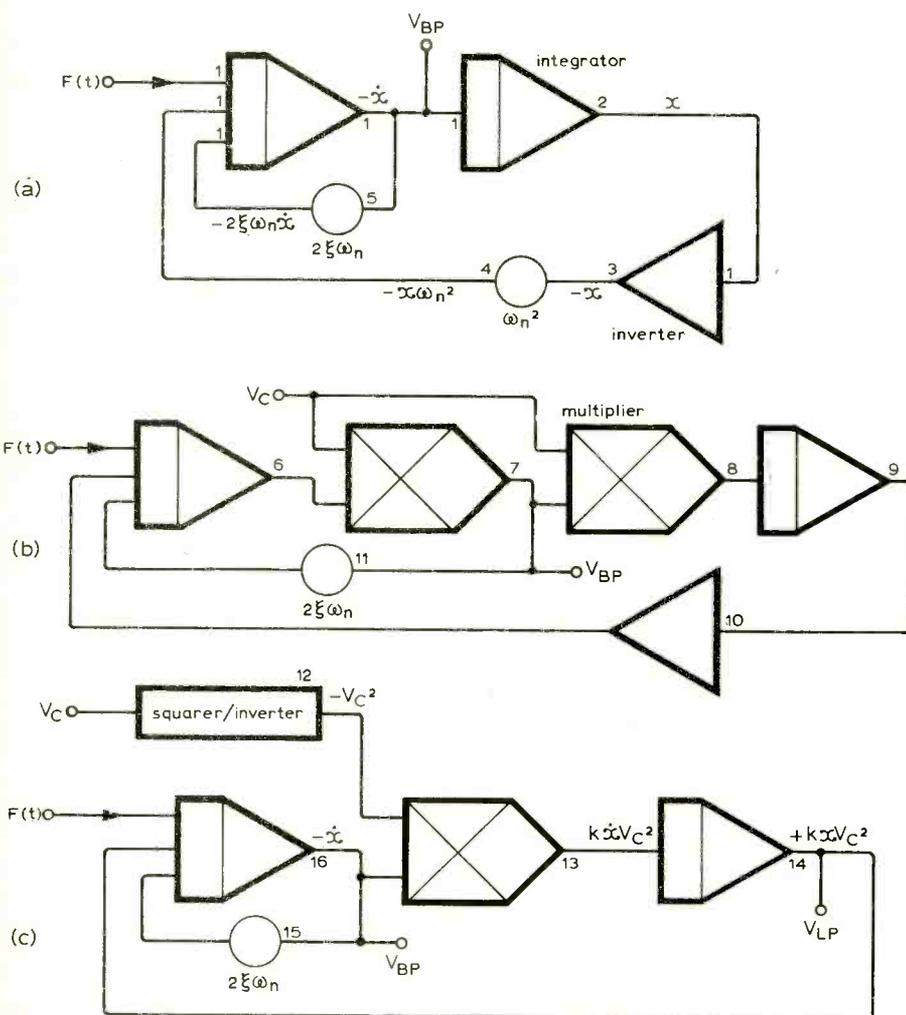


Fig. 38. Programmes for solving the second order differential equations of the form $F(t) = \ddot{x} + 2\zeta\omega_n\dot{x} + \omega_n^2x$ where $Q = 1/2\zeta$ (see appendix).

multiplier, then ω_n (and hence k) could be voltage controlled. Now $1/2k = Q$, so it is thus possible to control both the resonant frequency and thus the quality factor. Two points are immediately noticeable; one, the Q factor increases with frequency. This is because if pot 5 remains constant, we have

$$2k\omega_n = \text{constant}$$

$$\text{but } k = \frac{1}{2Q}, \therefore \frac{\omega_n}{Q} = \text{constant.}$$

Fractional changes in pot 4 i.e. ω_n^2 , result in the square root of that change in ω_n .

One method of curing both of these effects is to use two multipliers Fig. 38(b). It is easily shown that there is a linear relationship between the control voltage V_c and ω_n . Also the Q factor is invariant with resonant frequency changes (assuming multipliers 7 and 8 are matched), and the dynamic range of the filter is equal to that of one of the multipliers. It would also be possible to control the Q factor with yet another multiplier, but the use of multipliers is both expensive and introduces complications. It was for these reasons that the configuration shown in Fig. 38(c) was finally chosen. Hence, the relationship between V_c and ω_n is "linear", the dynamic range is nearly 10 to 1 and the Q factor increases with frequency. The variation of the Q factor is not as disturbing an effect as it may appear to be, especially when it is considered qualitatively.

Acknowledgements

We wish to acknowledge the help received from Henry's Radio in the supply of certain parts, especially for the donation of the keyboard.

Capacitor ratings

Voltage ratings of electrolytic capacitors shown in Figs. 28-38 are as follows:

- Fig. 28— $C_2/35V$.
- Fig. 29— $C_1/25V, C_3/10V, C_4/10V, C_7/10V, C_8/25V, C_9/25V, C_{10}/16V, C_{11}/40V, C_{14}/40V, C_{17}/16V, C_{19}/16V, C_{20}/16V, C_{27}/10V$.
- Fig. 31— $C_3/40V, C_4/16V, C_5/40V, C_6/40V, C_7/25V, C_8/25V$.
- Fig. 33— $C_1/25V, C_2/25V, C_3/10V, C_4/25V, C_5/10V$.
- Fig. 35— $C_1/25V, C_2/25V, C_6/16V$.
- Fig. 37— $C_2/40V, C_3/16V, C_4/25V, C_6/25V, C_7/16V, C_8/40V$.

An approach to audio amplifier design

3 System design, applying the figure of merit.

by J. R. Stuart, B.Sc. (Eng.), M.Sc., DIC, M.I.E.E.E.

In the second part of this series, the discussion of an approach to the design of an amplifier as part of a system led to a detailed analysis of the application of negative feedback loops. Highlighted in this analysis was the way in which the open loop characteristics of an amplifier need to be related to the closed loop operating conditions in order to achieve the correct compromise of phase, transient and steady-state distortions.

Steady-state distortions

The transistor parameters which contribute to non-linearity have been listed in part 1, as follows.

- The exponential form of the relationship between i_b and V_{be} and of V_{be} with temperature.
- Variations of h_{fe} and h_{FE} with collector current i_c , with collector-emitter voltage V_{ce} (Early effect), and with temperature.

At high frequencies other effects are in variations of C_{be} , C_{cb} and C_{ce} with chip temperature, V_{ce} and i_c . Apart from controlling quiescent conditions, the major freedom available to the designer in defining the forward or open-loop characteristics of

an amplifier is the choice of source and load impedance for each stage and of the amount of local feedback to be applied.

The two most useful techniques for reducing distortion introduced by device non-linearities are local emitter feedback (in a common emitter amplifier) and the cascode configuration. Fig. 32 shows a simple common emitter amplifier with and without local feedback supplied by R_e , and the small signal equivalent circuit for each.

We have for the case with local feedback, the trans-impedance

$$R_b = \frac{V_o}{i_s} = \frac{h_{fe} R_L R_S}{h_{11} + R_S + R_e(h_{fe} + 1)}$$

Setting $R_e \rightarrow 0$ gives the case of no feedback Fig. 32(a)

$$R_a = \frac{V_o}{i_s} = \frac{h_{fe} R_L R_S}{R_S + h_{11}}$$

By partial differentiation the sensitivity of R_a and R_b to device parameters can be shown, e.g. for change of h_{fe} for whatever reasons we have:

Case (a) no feedback

$$\frac{\delta R_a}{\delta h_{fe}} = \frac{R_L R_S}{h_{11} + R_S}$$

Case (b) with feedback

$$\frac{\delta R_b}{\delta h_{fe}} = \frac{R_L R_S}{h_{11} + (h_{fe} + 1)R_e + R_S} \left[1 - \frac{h_{fe} R_e}{h_{11} + (h_{fe} + 1)R_e + R_S} \right]$$

This represents an improvement in gain stability of:

$$\frac{[h_{11} + (h_{fe} + 1)R_e + R_S]^2}{(h_{11} + R_S)(h_{11} + R_e + R_S)}$$

Analysis will show the same improvement for many device parameters and a similar form of improvement in high frequency effects.

The cascode arrangement shown in Fig. 33 allows the common-emitter stage to be virtually freed from the Early effect and modulation of C_{ce} , as the device is allowed to operate at constant V_{ce} ; this clearly also allows a higher bandwidth to be achieved by the stage for given source and load impedances as the Miller effect is considerably reduced.

Design of a system

The preceding arguments in parts 1 and 2 indicate that an amplifier designed to sound very good cannot necessarily be synthesized from the basic specification:

1. Output power in excess of 40W.
2. Power bandwidth 20Hz – 30kHz \pm 1dB.
3. Very low noise and hum, say – 80dB.
4. t.h.d. less than 0.1% at all frequencies and power levels in the bandwidth.
5. i.m.d., however measured, less than 0.1%.
6. Low output impedance, say 400m Ω .

However it seems reasonable in the light of the preceding discussions to propose a starting point specification for very good quality as below.

1. Output power in excess of 40W.
2. Power bandwidth 10Hz – 30kHz \pm 1dB.
3. Very low noise and hum, say – 80dB flat, – 80dB C.C.I.R. weighted.
4. Weighted total harmonic distortion less than 0.1% at all frequencies and power levels; i.e. 10Hz – 20kHz, 0–40 watts.
5. i.m.d., however measured, less than 0.1%.
6. Low output resistance, say 400m Ω ; 10Hz – 20kHz.

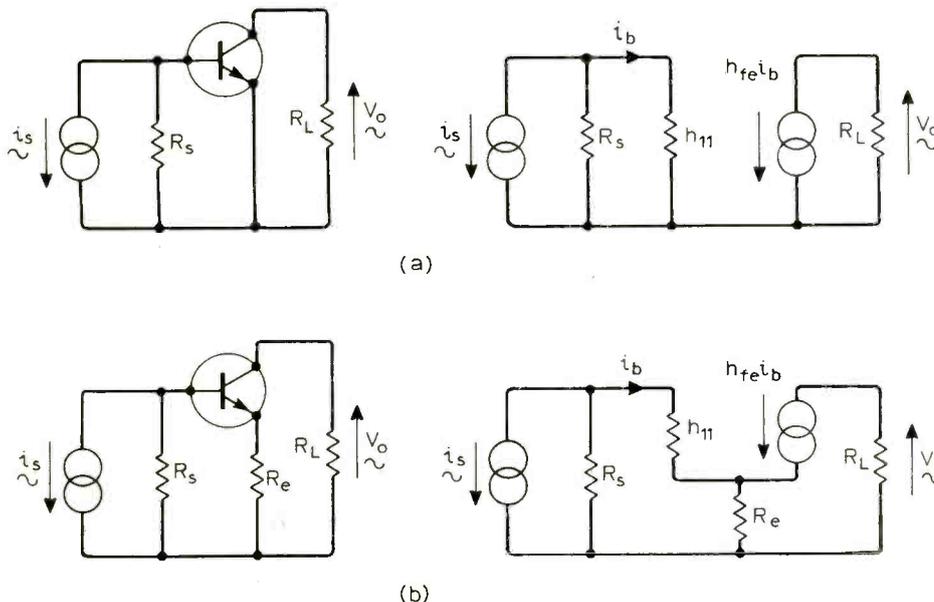


Fig. 32. Common emitter amplifier drawn (a) without feedback and (b) with feedback together with their small signal equivalents.

7. Open loop frequency response—any loop -3dB at 20kHz min.
8. Feedback factor -40dB any loop.
9. Phase accuracy $\pm 10^\circ$ 20Hz-20kHz.
10. Accurate overload characteristic inside the loops.

A typical audio amplifier system will be as shown in Fig. 34; here three major negative feedback loops are isolated. These are around the low noise input amplifier, in which equalization may be applied, the tone control stage and the power amplifier. In addition there is the volume control and a stage of filtering which need not be achieved by feedback loops.

It has been shown earlier that for any single stage to have a phase shift of 2° at 20kHz then the minimum -3dB closed loop bandwidth for that stage is 570kHz; three such stages cascaded would have a total lag of 6° . It has also been demonstrated that it is not desirable to drive any audio feedback amplifier significantly above its open-loop bandwidth; therefore if the signal can be restrained to say 45kHz in the filter stage, then the open-loop response of the two stages following the filter should be as similar as possible, thus giving a guide to the feedback factor that can be applied for a given overload margin.

The choice of 45kHz for a passive roll-off is a compromise between the phase distortion introduced by such a filter and t.i.d. in the power amplifier. It is not in any way a magic number and may be different in every design.

At this stage the designer runs seriously short of information, in particular the extent to which phase shift can be traded off for incipient t.i.d., and this is discussed later. However, it seems reasonable to me that in view of the poor phase performance of parts of the audio chain outside direct control, e.g. the recording studio, and in view of the high apparent sensitivity of the ear to t.i.d., that it would always be preferable to err on the side of a lower passive roll-off and higher phase shift—but as a compromise—not a rule.

A recent design. A commercially available amplifying system* designed by myself is shown in block diagram form in Fig. 35.

A low-noise high overload input stage is followed by an active volume control, filters and tone control; in each case the open-loop bandwidth and feedback factor, F dB, is shown. Care has been taken to ensure that no transient distortion effects can arise with an audio signal, and the signal bandwidth of the system is constrained to 45kHz with

a third-order Bessel roll-off which introduces a lag of 12° at 20kHz.

It is clear from the arguments presented that, for an unconditionally stable characteristic in an amplifier which exhibits no transient distortion effects in the signal bandwidth, a low feedback factor is necessary. This is because any increase of feedback factor must be accompanied (in the general and practical situation†) by a reduction of open-loop bandwidth, ω_{OL} . The consequences of this are a rise of steady-state distortion starting below ω_{OL} and an increased possibility of t.i.d. Therefore, in order that the amplifier should also have a weighted t.h.d. of less than 0.1% at any frequency or power level, it was essential to achieve a low open loop distortion figure.

The final power amplifier design, which is shown in block diagram form in Fig. 36, uses a new configuration which is the subject of a British patent application.

Use of local stage feedback combined with a complementary form and output triples operating in class AB gives an open-loop bandwidth of 17.5kHz and distortion of 0.2%. The application of 32dB of feedback reduces the weighted t.h.d. well below 0.1% and gives an unweighted t.h.d. of 0.005% between 100Hz and 3kHz.

A figure of merit

Earlier I put forward the idea of a figure of merit which describes the quality of an audio chain or a link of that chain. This is a number derived from a weighted sum of undesirable characteristics, measured in terms of the critical parameters. This figure of merit (f.o.m.) may be time variant; that is, an amplifier may have for example a rating of 0.8 (1971) and 0.7 (1973).

It was further proposed that by using collective subjective results, any parameter could be assigned a measure of significance, and further that the starting points for each parameter would be the thresholds of perception and objection—the latter Mantel³ calls “the threshold of non-neglectability”.

Successive experiments may then show improved accuracy in the choice of parameters, defining thresholds and curve fitting between the thresholds.

In this article I propose to outline a workable f.o.m. which is based on current knowledge as outlined, in the hope that its defects can be improved upon by large-scale experimental work.

The working of an f.o.m. Let us consider that the figure of merit for a chain or item in the chain be M , where M is the probability that a person will not be able to detect a shortcoming in the sound. This could be restated as M = probability of non-detection of a shortcoming by a member of the population chosen at random. Therefore an ideal audio system would have an $M = 1$ and a poor system $M = 0$.

For each stage in the chain of n elements we propose m_i ($i = 1, 2 \dots n$) such that the total figure of merit for the n cascaded stages is $M_T = \prod_{i=1}^n M_i \alpha_i$, where α_i is a weighting factor.

Each partial f.o.m. M_i is composed of a weighted product of factors believed to influence the quality of the sound, such that M_i shows the joint probability that any one factor may be detected as a shortcoming. Therefore in a simple example, if M_i considers only the terms

- $p(d)$ the probability of detection of $d\%$ weighted t.h.d., and
- $p(n)$ the probability of detection of ndB s/n ratio

then we may write

$$M_i = q(d) \cdot q(n)$$

where $q(d) = 1 - p(d)$
 $q(n) = 1 - p(n)$

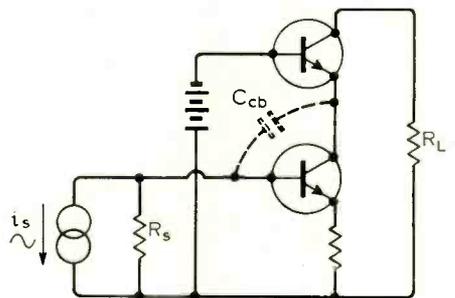


Fig. 33. The cascode circuit.

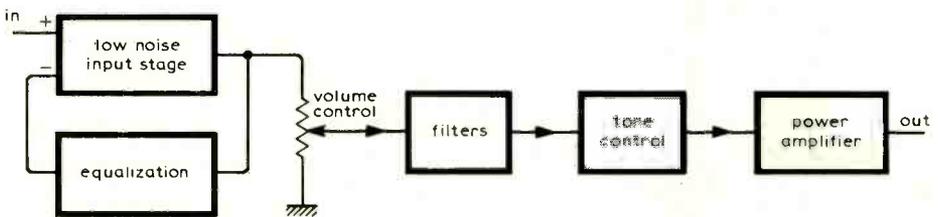


Fig. 34. Block diagram of a typical audio amplifier.

*The Lecson AC1 + AP1 given output transistors e.g.

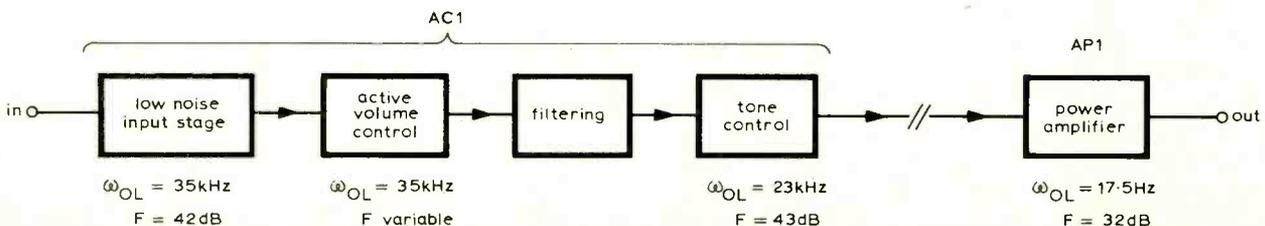


Fig. 35. Block diagram of the Lecson system showing the bandwidth and feedback factors for each section.

Now this is clearly a simple example and does not take account of perception thresholds or interactions of parameters and masking effects. It will not be sufficient to write, for example, $p(n)$ as the probability of detection of n dB signal to noise ratio, but possibly as a conditional probability of detection of weighted noise—say C.C.I.R. weighting—given a specific bandwidth.

So an f.o.m. which would be useful in the predictive design of audio components could be made up from tables of conditional probabilities and give a performance measure of universal use.

In this analysis I propose to use the thresholds of perception and non-neglectability ($p(x) = 0$ or 1) for all the parameters discussed so far and to discuss interpolation between these points.

In Table 1 a list is given of these parameters, and of thresholds which seem to be reasonable in the light of current knowledge.

Frequency response is treated by considering the two roll-off points—items 1 and 2—and determining a rough measure of $q(\omega_L)$ and $q(\omega_H)$ from Fig. 6 which are from results produced by Snow. Thus a response 20Hz–20kHz has a partial M of 1 while 100Hz–10kHz has a partial M of $0.9 \times 0.95 \approx 0.86$. Phase and amplitude linearity have been considered as being logarithmically interpolated in the absence of any other information—the same method has also been used by Mantel³.

Steady state distortions are again interpolated logarithmically; this being chosen as a reasonable assumption in the absence of further knowledge. The whole basis of this experiment is to test the values and curves I have offered as a starting point.

I would suggest that at this starting point in the derivation of an f.o.m. the *a priori* measure of the likelihood of t.i.d.—the transient intermodulation index—be used, and the interpolation is as shown in the Table.

Signal to noise ratio is shown weighted according to the C.C.I.R. standard, and it is intended that this should include only hum and noise and not measures of crosstalk or other interfering signals.

Other parameters which have not been listed but are clearly essential when discussing elements of the chain other than amplifiers include a frequency modulation measurement to include wow, flutter and Doppler effects.

A review of the f.o.m. In the form proposed here it is possible to produce a single number which is intended to describe the subjective sound quality of a piece of equipment derived from objective measurements based on the following suppositions:

- (i) it is possible to tabulate a conditional probability for the detection of any single shortcoming in terms of population.
- (ii) that this probability will move in some way from 0 to 1 between the levels of perception and objection.

In order that a number may be derived, and that the behaviour of the f.o.m. may be investigated, I have used the thresholds discussed in this article, and tentatively pro-

Table 1

Measurement	$p(x) = 0$ $q(x) = 1$	$p(x) = 1$ $q(x) = 0$	Interpolation
1. Amplitude-frequency response lower -3dB point ω_L	20Hz	1kHz	See Fig. 6 rating /10
2. Upper -3dB point ω_H	20kHz	1kHz	
3. Amplitude linearity $\pm L$ dB*	0.25	30dB	$p(L) = 0.48 \log_{10} (4L)$
4. Phase linearity $\pm \theta^\circ$	5°	100°	$p(\theta) = 0.77 \log_{10} (0.2\theta)$
5. Maximum weighted t.h.d. or i.m.d.* $d\%$	0.1%	50%	$p(d) = 0.37 \log_{10} (10d)$
6. Transient intermodulation index (t.i.i.) t_i	0.1	100	$p(d) = 0.33 \log_{10} (10t_i)$
7. Rise-time $\tau_{\mu s}$	5 μs	1ms	$p(\tau) = 0.44 \log_{10} (0.2\tau)$
8. C.C.I.R. weighted $s/n^* n$	70dB	30dB	$p(n) = (1 - (n-30)/40)$
9. Cross-talk c	60dB	0dB	$p(c) = (1 - n/60)$

*In the band 20Hz–20kHz or $\omega - \omega$ whichever is the smaller. Note $0 \leq p(x) \leq 1$ only.

Fig. 36. Simple block diagram of the Lecson power amplifier.


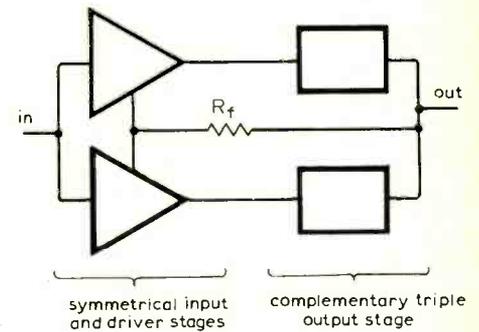


Fig. 37. Circuit switching arrangements for listening tests.

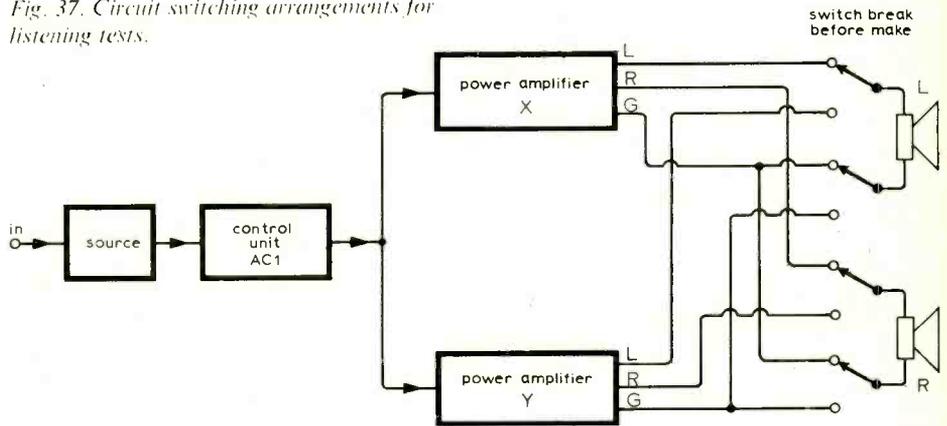

posed others with an interpolation. Clearly if such an f.o.m. is shown to give accurate results then it would be of great use to designers and users of audio equipment. However, in order that a f.o.m. of this kind can evolve, very extensive listening tests should be carried out. These are probably best controlled by and published through a respected journal such as *Wireless World*. [We are considering this.—Ed.]

The figures tabulated in Table 1 indicate that an amplifier which equals or betters the perception threshold for every parameter would have an $M_i = 1$. This rating would reduce to 0.9 with a low frequency cut off of 100Hz, or an amplitude deviation of 0.4dB or a phase deviation of 8° etc.

Some experiments

The author has recently carried out some listening experiments in an attempt to measure the significance of t.i.d. in high quality power amplifiers and, while the

tests are not completed, some preliminary results have been obtained which are of interest.

The approach has been to use the basic Lecson AP1 power amplifier design and to vary only the open-loop bandwidth and feedback factor.

Three amplifiers were used:

- 1. The standard amplifier with an open loop bandwidth of 17.5kHz and feedback factor of 32dB as summarised earlier.
- 2. A modified version with an open-loop bandwidth of 4kHz and feedback factor of 40dB. This amplifier exhibited amplitude and phase responses identical to the first example, within the accuracy of the measurements (0.25dB, 2°), and showed t.h.d. results within 10% weighted of the first example.
- 3. A modified version with an open-loop bandwidth of 17.5kHz and a feedback factor of 6dB. This amplifier exhibited t.h.d. of 0.11% 50Hz–3kHz, rising to 0.18% at

Appendix

The three amplifiers used in these listening experiments were all of very high quality showing an f.o.m. based on the routine of Table 1, of 0.9, 0.82 and 0.83, for the amplifiers A, B and C respectively.

Test 1. The test routine was performed using a panel of 8 listeners. Programme was derived from a very high quality disc player and monitor-standard loudspeakers employed (Spendor BC3).

Comparison A and B. On all programme material chosen, amplifier A was preferred by 87% of the listeners. The reaction of all listeners subjectively defined a clear difference, A being preferred for greater clarity at high frequencies. On switching to B the impression was obtained of a veil being drawn over the sound, particularly with strings or percussive material.

Comparison A and C. All listeners observed audible differences; C was preferred by 62% on all programme material and by 75% on folk music or percussive music. The overall impression was that C handled transient material very well but showed slight high frequency colouration, possible due to the weighted distortion.

Comparison B and C. Of the total audience, 75% preferred C on all material. Of particular interest in this test was that the two amplifiers showed subjectively different balance, C sounding to have less high frequency content than B. Also it was noted that B showed up background noise on the disc—hiss, clicks and pops—much more than C.

20kHz, 35W r.m.s. The distortion was such that the second harmonic was 40dB above any other so the weighted t.h.d. was below 0.2% at all times.

In each case the output impedance at the terminals of the amplifier was less than 250mΩ 20Hz–20kHz, so any effect that a change of feedback factor may have had on this, was swamped by the 3m long loud-speaker leads used.

Three experiments were conducted, two formal, one informal. In each case the amplifying equipment was arranged as Fig. 37; only two amplifiers are used in any one test and both are driven continually by the pre-amplifier. Instantaneous comparison on programme is made by switching the loudspeakers between the two power amplifiers.

In accordance with the testing procedures laid down by Percy Wilson the participants had no knowledge, until the end of the experiments, of the nature of the differences between the amplifiers (if any) nor of the kind of subjective difference (if any) to expect. At no time was it asked which of the amplifiers sounded most natural, but simply "which of two, X or Y, do you prefer?"

The results of the tests are summarized in the Appendix. It is clear that, between amplifiers which are otherwise extremely good,

Test 2. A panel of 4 listeners using a high quality disc source and monitor-standard loudspeakers (Lecson HL1).

Comparison A and B. All preferred A for reasons of high frequency clarity.

Comparison B and C. This test produced confusion, no direct results were applicable as preference depended upon the material used. The faults of amplifier B on transient sounds seemed to be contrasted with a slight lack of clarity on high notes with amplifier C.

Tests 3 and 4. Devised as a control test for the comparison B and C. Two panels took part, consisting of three and seven listeners respectively. Again a disc source was employed and small loudspeakers used (Spendor BC1). In the first test C was unanimously preferred, to the second—as before, preference depended to an extent on the source material.

A working hypothesis to explain reactions to amplifiers B and C could be, that subjectively the amount of t.i.d. produced by B was as significant as any high frequency t.h.d. or i.m.d. produced by C. However these listening tests are only the beginning of a serious programme of tests which will aim to establish significance over a much wider range, and so these results can only be considered to be provisional. For example no attempt has been made to establish an f.o.m. for the loudspeakers used in these tests or to calculate or measure any interactions in the reproducing systems.

despite relatively small changes to the t.i.i. performance, differences can definitely be detected by the ear as changes in the clarity and tonal balance of sound.

In a future article the author intends to describe further listening and objective tests and procedures in an attempt to quantify t.i.d. in absolute terms within the f.o.m. and with respect to t.h.d.

Conclusions

In these articles the author has attempted to study the relationships between objective tests made on amplifiers and the subjective results. Many aspects of amplifier performance have not been covered, the discussion concentrating more on distortions.

While it has been possible to outline in detail the rigorous compromises that face the designer of negative feedback amplifiers, the way in which each of the subjective effects trade-off is still not precisely known. A figure of merit calculation is given which makes an inquiring step in this direction, but it is clearly necessary that a programmed and controlled series of tests be carried out on a large scale.

Sixty Years Ago

From time to time over the years, successive editors of *Wireless World* have taken issue with the Post Office on the subject of licensing, especially when it has been considered that the Postmaster-General has tried to overstep the bounds of reason by claiming a proprietorial interest in the forces of nature. A correspondent in 1913 obviously felt very much the same way. . . . "We have heard lately of bedsteads and gas pipes being successfully used as substitutes for receiving aerials. Suppose I go a little further and discover that I get Paris, using only domestic appliances (such as a bedstead on an upper floor as an aerial, the wires of a piano suitably connected as a tuning coil, a nest of cake tins with buttered paper between them as a condenser, a piece of washing soda and a darning needle as a detector, and my tongue in place of the 'phones), must I obtain a licence from the Postmaster-General before I dare use such apparatus to get the time from E.L.? A few more discoveries(!) in "wireless" and we shall require to get a licence from the Postmaster-General before we furnish a house, and we shall have inspectors inspecting our pots and pans to see that they conform to the wireless regulations!"

Darts Game Calculator

Apprentices at the Guided Weapons Division of the British Aircraft Corporation, Bristol, have built an experimental automatic darts game calculating system which registers and keeps scores. It comprises a special dartboard with sensing devices, and a computer-controlled display unit which acts as the scoreboard. This unit, using 120 integrated circuits, shows the running totals for the competing teams and adds up each individual score.

The dartboard is designed with each segment internally divided and connected to the display unit. Impact of a dart on each segment causes an electrical signal to be sent to the computer in the display unit. The conclusion of an individual three-dart score is signalled by the removal of the darts from the board. The system is then re-activated by the next player standing on the throwing mat, under which is concealed a proximity detector. This causes a bulb on the display unit to be lit, showing that the system is ready to accept the next score.

Any variation of the game can be fed into the display unit before the game starts, so that the starting total could be set at, say, 1001 or 301 depending on the type of game to be played. If a double is required to start the game, then a "double" light is switched on and the system ensures that electrical signals from the dartboard will not alter the setting until the first double is obtained.

The apprentices were given just 13 weeks to design, build and test the project and were allowed to spend no more than £100 on materials.

Circards — 10

Micropower circuits

by J. Carruthers, J. H. Evans, J. Kinsler and P. Williams*

Think small! In tune with the broadening of the frequency spectrum, so has the range of powers grown at which electronic circuits may be coerced into functioning. Within modern integrated circuits it is common to find individual transistors operating at microampere currents, with device p.d.s of a volt or so. Discrete transistors can retain useful gain at currents several orders of magnitude less at room temperatures (even with silicon transistors leakage current imposes constraints on the usable current/temperature combinations). Since the leakage currents may be markedly reduced by controlling the doping levels and depth of penetration, by attention to surface impurities and by reduction of device area, it is difficult to define this lower limit. Collector currents of 1nA at 20°C and 1μA at 100°C are possible, though it would be foolhardy in the extreme to suggest that these could not be improved on — undoubtedly before publication some brilliant new process will appear capable of improving on these figures by a factor of ten or more!

The position is quite different in respect of minimum operating voltages. Fig. 1 shows the variation of I_c and I_b against V_{be} for a low-leakage planar silicon transistor operated at constant V_{ce} . No matter how low the current is reduced the fundamental relationship $I_c \propto \exp V_{be}$ ensures that the value of V_{be} changes at a much slower rate. For example, a ten-fold reduction in I_c corresponds to a reduction of approximately 60mV in V_{be} at room temperatures. Since the minimum value of I_c is likely to be fixed by load requirements etc. no amount of juggling can reduce the minimum supply voltage below that of the corresponding V_{be} , and in most circuits the supply voltage will have to be significantly higher. Excepting special cases such as certain complementary oscillators where only one of a complementary pair needs to conduct at a time, the minimum supply voltage will be greater than 1V and may have to be greater than 1.5V for op-amp type circuits.

In the above discussion no mention has been made of constraints imposed by transistor V_{ce} . At low currents the value of $V_{ce(sat)}$ is very much less than the V_{be} values above, though it must be observed

that $V_{ce(sat)}$ often rises with temperature while V_{be} always falls (typically the temperature coefficient of V_{be} is $-2mVK^{-1}$). At high current densities the bulk resistance of the semiconductor comes to dominate the junction characteristics and the minimum p.d.s may well exceed a volt for both base and collector-emitter paths. Self-heating will cause the value of V_{be} to fall somewhat but the effect should be negligible for circuits coming under the micropower heading.

The use of germanium transistors to minimize voltage requirements is well known, but the leakage currents are such that high temperatures are inconsistent with micropower operation. When using diodes, an intermediate region is provided by Schottky-barrier devices. As shown in Fig. 2, these have a p.d. appreciably less than that for a silicon diode, and can be used as bias elements as well as for rectification.

The interpretation of this term "micropower" has been made a generous one in this series because the techniques used in micropower circuits can be usefully applied in many other fields. For a given specification of load resistance and the required voltage or current swing, the minimum theoretical voltage can be determined assuming a voltage supply (if the circuit is to be supplied from a constant current then it is the minimum value of current that is defined). If this voltage is significantly greater than the minimum operating p.d.s of semiconductor devices as discussed above, then standard circuit configurations may well give satisfactory results. At lower load p.d.s new circuits are necessary to allow operation from correspondingly low supply voltages. As a rough guide, it is now possible to produce a.c. amplifiers, oscillators both RC and LC, voltage regulators, and astable and monostable circuits that will operate from supply voltages in the region of 1V, though with obvious limitations on output voltage swing and with reduced stability against supply/temperature variations. Other circuits such as power amplifiers and operational amplifiers may require somewhat higher voltages but nearly all functions can be provided while operating from a single dry cell. In designing these circuits a critical parameter is the minimization of wasted voltage, and this is equally applicable to conventional

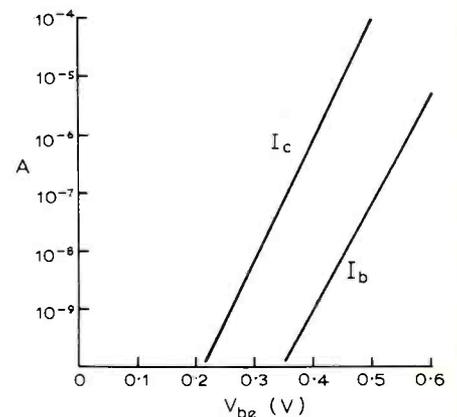


Fig. 1. Variation of I_c and I_b against V_{be} for a low leakage planar silicon transistor operated at constant V_{ce} .

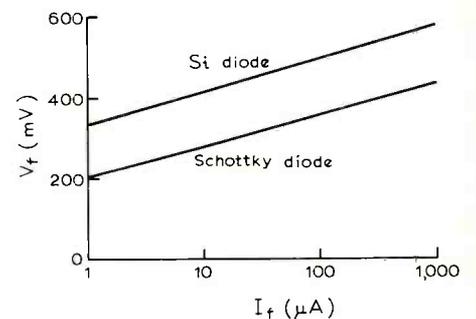


Fig. 2. The Schottky-barrier diode has a p.d. appreciably lower than that of a silicon diode.

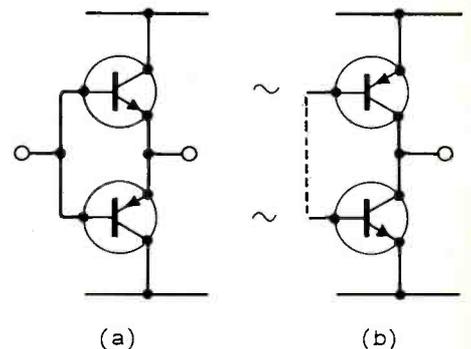


Fig. 3. Replacement of a complementary pair of emitter followers (a) by common emitter stages with emitters taken to opposite sides of the supply (b).

*All with Paisley College of Technology.

circuits where the load-swing is to approach the available supply voltage. A good example is the replacement of a complementary pair of emitter followers Fig. 3(a) by common emitter stages with emitters taken to opposite sides of the supply Fig. 3 (b). In the former case, since the bases can only be driven with difficulty to within hundreds of millivolts of the supply, then the output suffering an additional V_{be} loss may be up to 1V less than the supply at both extremes, i.e. the output has a peak-peak value up to 2V less than the supply voltage even at relatively low currents. In the circuit of Fig. 3 (b), though the drive conditions may be more difficult to meet, only the transistor $V_{ce(sat)}$ appears in series with the load, and outputs to within a couple of hundred millivolts of the supply are feasible. It is for the same reason that the series-pass transistor is in the common-emitter mode in voltage regulators where minimum input-output differential is important.

Two other related parameters that may be important in micropower circuits are maximum efficiency and the minimum quiescent power. As discussed in the article Power Amplifiers (June issue), these two conditions are often associated, as, for example, in class B power amplifiers. For minimum distortion it may be necessary to increase the quiescent power. Where the amplifier normally operates close to maximum output then this contribution to the power consumption is negligible. Conversely if the amplifier operates at full output only for short periods, then the mean power is strongly dependent on the quiescent power. In summary, for continuous operation at maximum outputs, saturation voltages will be the limiting factor, while the quiescent power needs most design ingenuity for large peak/mean ratios in output.

A different problem arises when efficiency at maximum output is really critical. Then the need to saturate the output transistor(s) to minimize lost voltage would bring the corresponding disadvantage that the base current becomes a large fraction of the load current. The combination of high current gain together with low saturation voltage is not an easy one, though at least high breakdown voltages are not required of the device. Special transistors called "super- β " devices are now used as the input stages for high input impedance operational amplifiers. These have a very thin base region, achieve gains in excess of 1,000 but have very low breakdown voltages. They are the extreme examples of another source of the trend towards low-power operation — in this case for the higher input impedance that it brings rather than for the low power itself.

The definition and control of operating current becomes difficult at low currents because of the high-value resistors needed, which are not compatible with monolithic processing in its most economic form. Circuit techniques based on the current-mirror have mitigated this problem, so

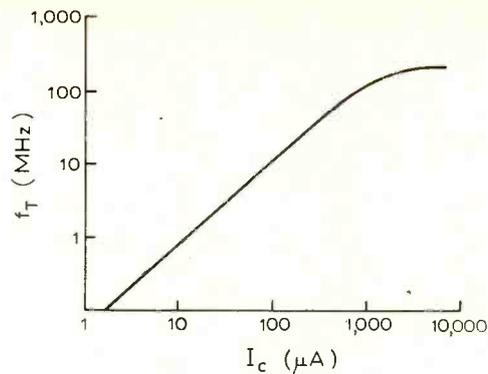


Fig. 4. At high frequencies the gain-bandwidth product of a transistor is an almost linear function of quiescent current.

that all the currents in an amplifier are controlled by a single low-current source. Recent micropower op-amps leave this to the choice of the user, with a single external resistor programming the operating currents of all the transistors in the i.c. At low supply voltages the p.d. across any such resistor, whether internal or external, becomes temperature-dependent and the design problems multiply.

Temperature problems are even more severe in low-voltage/low-current voltage regulators since conventional voltage reference elements cannot be used — the lowest zener diode has a breakdown voltage of approximately 2.7V. Combinations of dissimilar diodes (e.g. Si and Ge) can be produced that have a voltage difference which is almost temperature compensated, while i.c. designs have exploited the properties of forward-biased silicon p-n junctions to achieve the same effect.

The one area of operation where the inherent limitations of micropower operation have not been overcome is the high-frequency region. As the quiescent current in a transistor is reduced, so the rate at which it can charge its own internal and/or external stray capacitances falls. The gain-bandwidth product is an almost linear function of quiescent current (as shown in Fig. 4) with an upper limit to this parameter short of its maximum operating current for most devices. Thus a device normally thought of as a "100MHz transistor", when operated at collector currents below $1\mu A$ may have a cut-off frequency of less than 10kHz. Clearly it becomes of critical importance to minimize the stray and load capacitances in such applications. For micropower operations at high frequencies, transistors with the very highest quoted gain-bandwidth products should be selected — even 1GHz devices are not out of place provided they can sustain current gain at these low currents. Low-voltage operation brings increased problems since, for example, the collector-base diode has increasing (non-linear) capacitance as the p.d. approaches zero and eventually becomes slightly forward biased.

A major area of concern is in the digital field, where ever larger numbers of gates and other functions are being concentrated into single monolithic i.c.s. These l.s.i.

(large scale integration) circuits are limited in complexity by two mechanisms — the number of external connections, and the total dissipation. Complementary m.o.s. with its extremely low standby power is the ideal logic family from this latter standpoint and is likely to dominate the market. The dissipation is significant only where high-speed operation is demanded, since then the charge/discharge of internal capacitances dissipates power. Since the choice of circuits available in this family is growing so rapidly, the user is best advised to refer to the manufacturers' data sheets, while the properties of the basic gates will be discussed in the following article.

How to get Circards

Order a subscription by sending £9 (U.K. price; £10.50 elsewhere) for a series of ten sets to:

Circards
I.P.C. Electrical-Electronic Press Ltd
General Sales Dept.
Room 11
Dorset House
Stamford Street
London SE1 9LU

Specify which set your order should start with if not the current one. One set (normally 12 cards) costs £1 U.K. and £1.15 elsewhere, postage included.

Cheques should be made payable to I.P.C. Business Press Ltd.

Topics covered in Circards are

- 1 active filters
- 2 switching circuits (comparators & Schmitts)
- 3 waveform generators
- 4 a.c. measurement
- 5 audio circuits (equalizers, tone control, filters)
- 6 constant-current circuits
- 7 power amplifiers (classes A, B, C, D)
- 8 astable circuits
- 9 optoelectronics: devices and applications
- 10 micropower circuits

Subsequent issues will cover logic gate circuits, wideband amplifiers, alarm circuits, digital counters, pulse modulators. Introductory articles in *Wireless World* indicate availability of Circards, which are normally ready for despatch on the 1st of the month, and the Circard concept was outlined in the October issue, pages 469/70.

Letters to the Editor

The Editor does not necessarily endorse opinions expressed by his correspondents

Breakdown of c.m.o.s. devices

I was very interested to read the article "Complementary m.o.s. Integrated Circuits" in the August issue. However, on page 396 there was the statement "To avoid failures due to destructive breakdown of the gate insulation, possible with such high impedances . . . etc".

Motorola in a recent leaflet entitled CMOS state that stress voltages can be caused by improper testing and even more likely causes are random electrostatic charges. They suggest that all leads are shorted together, antistatic clothing should be worn, personnel handling c.m.o.s. should be electrically grounded, equipment which comes in contact with finished pieces of equipment should be properly grounded — and yet they fit input protection diodes.

RCA claim to have fitted protection devices to the inputs of their devices which will have a controlled breakdown of something of the order of 30V-100V in the reverse direction, and have given figures for the maximum voltages which can appear between pins on the i.c.

SGS also fit input protection diodes but, so far as I can ascertain, make no claims one way or the other.

This problem of breakdown due to static build-up appears to be a serious drawback to the large-scale use of c.m.o.s., or maybe I am looking at the wrong manufacturers' data sheets!

Can any of your readers enlighten me as to whether I can safely wear my nylon coat when using c.m.o.s. or do I have to chain myself and all my test gear solidly to earth?

Peter Seddon,
Rugby,
Warwickshire.

Tuner front-end devices

I have recently read in *Wireless World* two articles which have raised some rather large doubts in my mind as to the best device available for the reduction of cross- and inter-modulation.

In June there was Mr Nelson-Jones employing dual gate m.o.s. f.e.t.s in his v.h.f. tuner which, with a sensitivity of the order of 1 microvolt, one hopes

will pick out a weak v.h.f. signal in the presence of strong local nearby frequencies.

In August P. Antoniazzi and A. Mauceri were saying the dual gate m.o.s. f.e.t. is not the answer and the bipolar transistor has a better performance, achieving a 40dB suppression of signals with a 4MHz separation at 500MHz. When used as the v.h.f. part of their tuner I deduce they will claim a similar performance.

I do not have available the data sheets for the BF479; however, those for the 40673 show that careful selection of bias and a.g.c. is needed to get the best out of the m.o.s. f.e.t.

The problem I wish to pose is essentially how does one receive a 1 microvolt signal, which obviously cannot produce much a.g.c., in the presence of strong nearby v.h.f. f.m. transmissions which can easily be of the order of hundreds of millivolts.

Could these respected authors clarify this point, which is becoming a real problem with the almost saturation of v.h.f. frequency spectrum? The published literature is full of wavetraps and heli-coidal filters which unfortunately are to some extent attenuators for weak signals.

Even better still would be an article from some brave soul on the relative merits of bipolars and m.o.s. f.e.t.s in weak signal conditions. I am sure such an article would fill a gap in a little discussed but very real problem.

F. F. Maher,
Madrid,
Spain.

Record equalization

In response to Mr Ewer's letter on record equalization (August issue) I would like to point out some factors which he has overlooked or perhaps does not know about.

First of all I must hold up the record companies' flag by saying that discs are recorded to the BS 1928 equalization standard and that there is no equipment "penny-pinching" when Neumann or Scully cutting lathes are in use.

The reason behind the apparent lack of extreme bass on some records is *not* due to the use of a modified equalization

characteristic. Despite what J. L. Linsley Hood and others say, it is due to the fact that extreme bass signals, of even moderate amplitude, can (a) damage, very easily, delicate stereo cutter heads (especially if present as a difference signal) and (b) result in groove wall breakdown, i.e. "groove-jumping". To prevent cutter head damage, fast, accurate stereo limiters are employed, but to avoid the triggering of these too often a careful watch must be kept on peak levels and difference channel levels at all frequencies, with the result that occasionally a modicum of "cut" must be applied at selected places within the audio spectrum.

There are several ways to prevent (b): (i) a deeper cut — impractical because many cheaper arms and cartridges would fail to track it; (ii) wider minimum groove spacing (before use of variable groove spacing unit) — a possible solution but it conflicts heavily with the amount of time needed per disc side for a given piece of music (Varigroove is not always the answer!); and (iii) a "roll-off" of extreme bass to allow a more normal groove spacing.

So, Mr Ewer, don't blame the cutting engineers or their equipment: blame the totally conflicting elements of time and fidelity required from a poor little piece of black plastic and just turn up the bass!

Robert L. Artherton,
London, N.16.

VAT and prices

Like your correspondent W. B. Henniker in September's letters, I have fallen foul of the "VAT addition" thing in your advertisements, in one case with further complications since by the time the VAT had been received the goods had become exhausted. At least I *think* they were, because I have heard nothing since the fourth of July.

Your advertisers in general were very slow to respond to VAT, and in some cases were showing advertisements in the May issue which were not clear about the tax addition.

If *Wireless World* depends on advertisements for a living, or if the advertisers depend on advertisements for a living, then someone will have to brighten their ideas — and their conceptions of service.

J. R. Dykes,
Winsford,
Cheshire.

Inverter for fluorescent tubes

I was very sorry to read in the September issue of the trouble that Mr Chappell has had with the heaters of his fluorescent tube in my circuit (August issue).

I can only plead that I tested the circuit with at least three different tubes and that none of them showed any sign of the discharging from which he has suffered.

This type of tube was, of course,

designed originally for operation from the a.c. mains, and the circuits in which they are normally used arrange for the feed to the heaters for starting up to be essentially the same defined current as is used in normal running. In such a circuit discharging across the heaters is no disadvantage as the power dissipated is reduced rather than increased. Furthermore there is no reason why the heater resistance, and hence its working voltage, should be tightly controlled for such service. The value may, in fact, vary appreciably from one manufacturer to another.

Mr Chappell's suggestion of the insertion of a ten ohm resistor in series with each heater looks like a very satisfactory solution to the problem.

I am sorry that I missed this point and I hope that no other readers have suffered similar trouble.

I must apologize also for the fact that Figs 3 and 4 of my article as published had the positive power supply point omitted. This should, of course, have been at the centre-tap of the transformer just as it was in Fig. 1 (b).

K. C. Johnson,
Chedale,
Cheshire.

Printed circuits the easy way

My own resists are invariably photographically produced, so I cannot speak to the drawing technique which is described by J. Ferguson on page 332 of the August issue. But it ought to go on record that the only reason commercial etching of copper is done with ferric chloride (the commercial grade of which usually contains a variable proportion of free hydrochloric acid) is that this chemical is relatively inexpensive. In amateur printed circuit work there may well be other solutions which have advantages over it.

I pass over nitric acid, since it emits brown choking fumes when attacking copper. But its action is very swift, and those whose resist can stand up to its onslaught might feel it worth trying, in 10% concentration in the open air.

My own choice would be 10% ammonium persulphate in water. This dissolves copper very well, though perhaps a little slowly, but the solution stays fairly clear and the submerged board can be seen pretty clearly. If about 5% by volume of strong ammonia solution is added to the persulphate, action is accelerated considerably, but the solution turns deep blue very quickly as copper is dissolved, and the effect on submerged pieces cannot be so easily seen.

Though I have not personally tried it, there would seem to be something in the electrolytic method of etching. Assuming that the unwanted copper areas of the board can be commoned, they can become an anode of the electrolytic cell, while any odd piece of scrap brass of roughly the same area can be used

as cathode. All that is now needed is a source of 6 volts 4 amps d.c. which nearly everyone must have at hand these days.

Quite a number of possible electrolytes suggest themselves, but for first trials I would suggest 10% common salt in water. If too little current passed — a board 4 × 4 inches would probably need some 4 amps of current to dissolve the copper reasonably fast — the addition of a little vinegar (i.e. dilute acetic acid) should increase the conductivity to some extent. But it will not have anything like the effect that a few ml of a strong acid, such as hydrochloric acid, will produce.

P. C. Smethurst,
Bolton,
Lancs.

Electronic music

Having been interested in the use of electronics for musical experiments, I would like to hear from any readers who have had experience in this field. I am particularly referring to the music synthesizer using voltage controlled oscillators as well as other voltage controlled functions.

The purpose of this is to collect any ideas for the design of a small synthesizer capable of fairly advanced work while still retaining its low cost.

G. Wade,
Knowle Orchard,
Churchill,
Nr. Bristol.

Projection television

I was most interested to find reference to my old company, in conjunction with the other old stalwarts of projection television, in G. W. Tillet's Letter from America in the September issue.

It may be interesting to mention that much of the original work, culminating in the formation of White-Ibbotson Ltd, took place while I was with E.M.I. and was based on 3in. c.r.t.s designed by Drs Broadway and Cairns, and using all-glass Schmidt lenses designed and made by Optical Works Ltd of Ealing. When E.M.I. decided not to proceed with the venture, I left and formed W.I. Ltd — the directors of E.M.I. giving every assistance and helpful co-operation.

Thus, we were not altogether tied to the disadvantages that Mr Tillet states applied to the Philips unit. However, I must hasten to add that *neither* system suffered from the dust occlusion problem mentioned if the systems were put together with proper precautions to exclude dust. In fact, the most serious problem with either the E.M.I. or the Philips c.r.t. was, in my experience, that of X-ray staining of the face glass. This could cause a 50% light loss in a few hundred hours running.

So far as viewing "under cinema conditions" is concerned, again I must cross

swords with Mr Tillet. It is a matter of history that we had a 4ft × 3ft back projection picture running under 2.5kW of exhibition lighting at Earls Court with a very good viewability for the passing public — and this was with a standard Philips unit. Obviously we used our lenticular screen but this provided a good horizontal angle of view and, by limiting the vertical angle to about 15° (ample for normal viewing with this size of picture), we had a minimum of projection light waste and a maximum rejection of overhead lighting interference.

It may also be interesting to record that we found a French optical company who made ordinary convex lens systems for the Philips tube with similar efficiency to the Schmidt, and at very little extra cost, which clearly avoided many of the dust exclusion/cleaning problems inherent in a basic Schmidt.

At that particular time Mullard's proved a point of view that I had always held, namely that projection would come into its own with the advent of colour. They used three primary-coloured monochrome tubes and three Philips' Schmidts. Such tubes are much less expensive to produce than the traditional panchromatic black and white tubes. The results were startlingly good but orientation of the Schmidts with dichroic mirrors etc. was far from practical. Had there been colour transmission at that time, we would have used the French lenses and I think a commercially viable result would have been obtained.

It's a great pity that we have had to leave it to the Japanese, yet again, to appreciate the advantages and go-ahead. However, I think that Sony have gone to a great deal of trouble in the wrong direction — if, of course, ours and Mullard's experiments meant anything.

H. Ibbotson,
Penryn,
Cornwall.

Reflex Circuits

I was delighted to read John Scott-Taggart's letter in your September issue. First, to discover that he had not departed, nor lost interest. Second, to acknowledge his very generous final paragraph. It was all the more generous in view of the fact that I have been known to indulge in a little thinly disguised leg-pulling about such things as the celebrated ST 100 (younger readers will have to ask their elders to explain). And still more generous after I had forgotten his pioneer work on the reflex circuit. For this I must plead age, not ignorance, as I will now make clear. And I hope it will also go some way towards atoning for my sins of commission and omission as I reveal for the first time that the very book from which he quoted (*Thermionic Tubes in Radio Telegraphy and Telephony*) provided the foundation for my knowledge of the subject, since the degree course in electrical engineering at Edinburgh in 1921 was all "heavy". During one par-

ticular course of lectures by a notoriously ineffective expositor, while most of the inflated intake of students after the War were amusing themselves at his expense I sat in the back row, where the signal/noise ratio was fractional so did not break through my concentration, and read S-T's book from cover to cover.

As it was one of the very few "historical" books that survived my drastic pruning on moving recently to smaller premises, I really have no excuse for not refreshing my memory from it.

So far as I was concerned the Scott-Taggart ubiquity to which I referred in August was mainly in print. I can recall only two sightings: one was when he came to Edinburgh about 1923 to explain and demonstrate his "Negatron"; the other was 22 years later in the Air Ministry. I am glad to acknowledge my debt to his books in the days when reliable sources of information were scarce.

M. G. Scroggie,
Bexhill,
Sussex.

"Empty" cassettes wanted

The remedial reading department at this school uses a number of devices to encourage pupils who find difficulty in learning to read.

Our most recent innovation is a tape-loop which runs for about 18 seconds and on which are recorded about half-a-dozen words containing the same sounds.

The tape-loop is housed in an ordinary cassette by fitting additional rollers. Our difficulty is obtaining cassette cases. We cannot afford to purchase cassettes at normal price and then to modify them. Would any reader having empty or broken cassettes please send them to me at the school? Postage would gladly be refunded.

C. S. Smith,
The Walmer Secondary School,
Salisbury Road,
Deal,
Kent.

New names for old devices

The headline in *Electronics Weekly* of August 8th reads, "Amorphous Devices Seeking a Role". Forgetting the updated terminology, these devices seem to be little more than the original coherer used in the early days of wireless to "detect" a signal. The r.f. signal fused iron filings in a tube, causing the passage of d.c. to indicate that a signal had been detected.

Newly fledged engineers should perhaps be reminded that we might never have developed an electronics industry but for Amorphous Devices.

Some readers may be interested to know that they can construct an amorphous memory device with a piece of wood, two pins and a blob of aluminium paint. The pins should be hammered into the wood about $\frac{1}{8}$ in apart. A thin layer of paint is applied between the pins and allowed

to dry. Apply about 20 volts via a few kilohms to limit the current and the aluminium particles in the paint will link together and close a "switch" capable of carrying perhaps $\frac{1}{2}$ amp. Apply about 6 volts without a current limiting resistor and the switch opens. It is rather like blowing a fuse. There is one difference — it can be mended again by applying the 30 volts activation supply for a moment.

I once caused great mystification amongst colleagues at the Emley Moor transmitting station with a little device able to switch a torch bulb on or off without using a switch or other familiar device. Readers wishing to repeat the experiment should beware of vibration; it will disturb the coherer link. In the event of failure please consult the paint manufacturer rather than myself.

P. J. Unwin,
Rochdale,
Lancs.

equipment; components and ancillaries.

Data networks; message switching; modems; data terminals; telemetry systems.

Mobile radio equipment and systems for land, sea and air; selective calling; radio paging; frequency allocation and channel spacing; traffic control and vehicle location systems; radio navigation receivers and systems.

Radio communications equipment and systems for fixed applications; point-to-point links; remote control systems; digital encoding systems; tropospheric scatter.

Special techniques associated with military systems; electromagnetic compatibility; routing problems; equipment parameters for future requirements; underwater communications.

Microwave communication systems; microwave antennas, ground stations and receiving systems; waveguide communication systems.

Original papers are invited from industry, government departments, the armed services, universities, etc. In the first instance, authors should submit summaries of 200-300 words (in English), describing the subject and scope of the paper, to: The Editor, *Electronics Weekly*, Dorset House, Stamford Street, London SE1 9LU.

Deadline for the receipt of summaries is October 26, 1973. Speakers will be notified of acceptance by December 31, 1973. Final drafts will be due by March 11, 1974.

John Gilbert retires

After being associated with the Northern Polytechnic (now The Polytechnic of North London) for 39 years, 22 of them as head of the Department of Electronic and Communications Engineering, J. C. G. Gilbert, F.I.E.R.E., F.R.S.A. has retired. Perhaps best known to the public for his part in the television programme "Inventor's Club", his major contributions have been in the world of audio.

He was educated at Westminster City School and went on to part-time courses while, at the same time, studying music at Trinity College of Music, London, giving broadcast piano recitals between 1924 and 1928. He became interested in radio while still at school and, in 1934 joined Partridge & Mee of Leicester on the strength of two articles on disc recording published in *Wireless World*, and that summer was in control of the installation of the public address system at the Regent's Park Open Air Theatre. In September of that year, Mr. Gilbert joined the "Northern Poly" as part-time lecturer on radio servicing and in 1935 became the first full-time lecturer in radio and kindred subjects. He also took up the position of technical editor of *Music Trades Review*. During the war years he worked under Sir Robert Renwick in the Directorate of Communications Development at M.A.P. and, on return to the Polytechnic, became senior lecturer and, in 1951, head of department — a position he held until August this year. He has been chairman of several societies, among them the British section of the Audio Engineering Society, was chairman of several B.S.I. committees and is technical consultant to the journal *The Gramophone*, where he continues his work. He has written several articles for *Wireless World*. We wish him a long and happy retirement.

Synthesizer Keyboards

The following company has informed us that they can supply keyboards for the *Wireless World* sound synthesizer (see pp.485-490 this issue): Elvins Electronic Musical Instruments, 12 Brett Road, London E.8. Tel. 01-986 8455.

"Communications 74" — call for papers

An international conference, Communications 74, is being organized by *Electronics Weekly* and *Wireless World*, and will be held at the Metropole Convention Centre, Brighton, 4-7 June 1974, in conjunction with a Communications 74 exhibition. Suggestions for papers are now invited.

The conference will be divided into two parallel sessions on each of the four days, one session being on user topics and the other on technical topics. Afternoon sessions, for the presentation of short papers, and evening meetings are also being planned.

The four main subjects of the conference will be: data communications; mobile radio communications; fixed radio communications; and defence communications. Suggested topics for papers include the following:

Transmitter and receiver circuit techniques; propagation; error correction; facsimile; antennas; cables; recording systems; test

October Meetings

Tickets are required for some meetings: readers are advised therefore to communicate with the society concerned

LONDON

9th. AES — "The integrated circuit in audio systems" by Jonathan A. Dell at 19.15 at the IEE, Savoy Pl., WC2.

10th. IERE — Colloquium on "Electromagnetic compatibility or confusion on land, in ships and in aircraft" at 14.30 at 9 Bedford Sq., WC1.

10th. IEE — "Computers and communication — convergence or conflict?" by J. R. Pollard at 17.30 at Savoy Pl., WC2.

17th. IERE — "The feedback classroom" by K. Holling at 18.00 at 9 Bedford Sq., WC1.

18th. IEE Grads. — "The computer-oriented research laboratory by G. M. Rhodes at 18.30 at Savoy Pl., WC2.

22nd. IEE/I.Mech.E. — "Sequence control of analogue computers" by Dr. G. C. Barney and Dr. D. Miller at 17.30 at Savoy Pl., WC2.

23rd. IEE — "TV supply by a combination of omnidirectional 12GHz transmission and cable distribution networks" by Dr. J. Feldmann at 17.30 at Savoy Pl., WC2.

23rd. IEE Grads. — "Frequency synthesizers" by Dr. P. N. Nield at 18.30 at the Polytechnic of the South Bank, Borough Rd., SE1.

25th. IERE — AGM at 18.00 followed by presidential address by Dr. I. Maddock at 18.45 at London School of Hygiene and Tropical Medicine, Keppel St., WC1.

26th. IEE — Discussion on "Stripline and microstrip techniques for antennas" at 17.30 at Savoy Pl., WC2.

30th. IEE/I.Mech.E. — Discussion on "Remote measurement and control using Post Office data transmission facilities" at 17.30 at Savoy Pl., WC2.

30th. IEE — Discussion on "Making the most of airborne frequency allocation" at 17.30 at the Royal Aeronautical Society, 4 Hamilton Pl., W1.

31st. IERE — Colloquium on "Remote control system organization" at 10.15 at Middlesex Hospital Medical School, Mortimer St., W1.

ABINGDON

10th. IEE — "Electricity in medicine" by Dr. D. W. Hill at 19.00 at Culham Laboratory.

AYLESBURY

16th. IEE — "Recording and reproducing quadrasonic sound" by J. C. G. Gilbert at 19.30 at Aylesbury College, Oxford Rd.

BATH

18th. IERE/IEE — "Optical fibre communications" by F. F. Roberts at 18.00 at Lecture Room 4E3, 10, the University.

BELFAST

10th. IERE — Northern Ireland section AGM followed by "T.Eng. and all that" by J. T. Attridge at 18.30 at the Board Room, Ashby Institute, Queens University.

BIRMINGHAM

3rd. IEETE — "Technician engineers and technicians — in the EEC, and elsewhere in the

world" by E. A. Bromfield at 19.00 at Midlands Electricity Board, Summer Lane.

29th. IEE/I.Mech.E. — Discussion on "Applications of multivariable control theory" at 18.00 at the Midlands Electricity Board, Summer Lane.

BOURNEMOUTH

17th. IEETE — "Stereo broadcasting" by J. H. Brooks at 19.30 at The Tralee Hotel, West Hill Road, West Cliff.

BRADFORD

18th. IEETE — "The present state of colour television" by Prof. G. N. Patchett at 19.00 at the University.

20th. Sept. IERE — "Modern developments in hi-fi reproduction" by Dr. A. R. Bailey at 19.00 at the University.

CAMBRIDGE

17th. IEETE — "Technician engineers and technicians — in the EEC, and elsewhere in the world" by E. A. Bromfield at 19.00 at the University Centre, Mill Lane.

25th. IERE/IEE — "Situation display — a new and unique approach to radar presentation" by F. K. H. Birnbaum at 18.30 at the University Engineering Laboratories, Trumpington St.

CARDIFF

10th. IERE — "New integrated circuits for television receivers" by G. Baskerville at 18.30 at Dept. of Applied Physics, UWIST.

CHATHAM

3rd. IERE — "Recent advances in radio navigation" by J. E. Viles at 19.00 at Medway and Maidstone College of Technology.

CHELMSFORD

25th. Sept. IERE/IEE — "An anti-collision radar employing storage of radar pictures on tape" by J. Watt at 18.30 at the Civic Centre.

CRANWELL

24th. IERE — "Space instrumentation" by R. Young and B. R. Kendall at 19.30 at the RAF College.

DURHAM

17th. IEETE — "TV and stage lighting" by E. Birch at 19.30 at the Lecture Theatre, Science Site, Durham University, South Road.

EVESHAM

20th. Sept. IERE — "Colour television displays — the next stage" by W. W. Wright at 19.30 at the BBC Evesham Club.

FARNBOROUGH, Hants

24th. IERE — "Multiphonic organs" by J. H. Asbery at 19.00 at Queen's Hotel.

GLOUCESTER

18th. IERE — "Provision of communications for remote clustered visual display units" by F. B. Sanders at 19.30 at the College of Technology.

IPSWICH

17th. IERE/IEE — "Radio astronomy" by Dr. R. S. Booth at 18.30 at The Civic College.

LEICESTER

10th. IERE — "Delta modulation systems" by R. Steele at 19.30 at the Lecture Theatre 'A', Physics Block, the University.

LIVERPOOL

17th. IERE — "The semiconductor story" by Dr. K. J. Dean at 19.00 at the Dept. of Electrical Engineering and Electronics, the University.

MANCHESTER

15th. IEETE — "An engineer behind the Iron Curtain" by Prof. M. G. Say at 19.30 at Reynold Building, UMIST.

NORWICH

24th. IERE/IEE — "Sonar and underwater communications" by Dr. V. G. Welsby at 19.00 at Assembly House.

PORTSMOUTH

24th. IEETE/IEE — "The engineer in Europe" at 14.00 at the Polytechnic, Anglesea Road.

31st. IERE — "Exploring the deep oceans" by K. Haigh at 18.30 at the Polytechnic.

READING

10th. IERE — "Digital phase lock loops" by K. Thrower and P. Atkinson at 19.30 at J. J. Thomson, Physical Laboratory, University of Reading, Whiteknights Park.

REDHILL

24th. IEE — "Solid state radars by K. L. Fuller at 19.30 at the Mullard Research Laboratories, Cross Oak Lane, Salfords.

SOUTHAMPTON

17th. IERE — "Charge couple devices" by J. D. E. Benyon at 18.30 at the Lanchester Theatre, University of Southampton.

SWANSEA




24th. IERE/IEE — "Recent developments in the design of transfer function analysers" by W. A. Evans at 18.15 at University College.

WOLVERHAMPTON

16th. IERE — "The electronic control and communication network employed on the Midland links motorways" by W. A. Hambrey at 19.00 at RAF Cosford, Albrighton.

EEV
CAMERA
TUBES

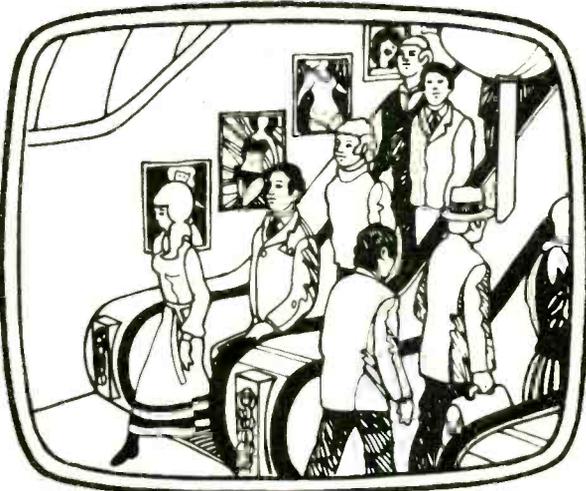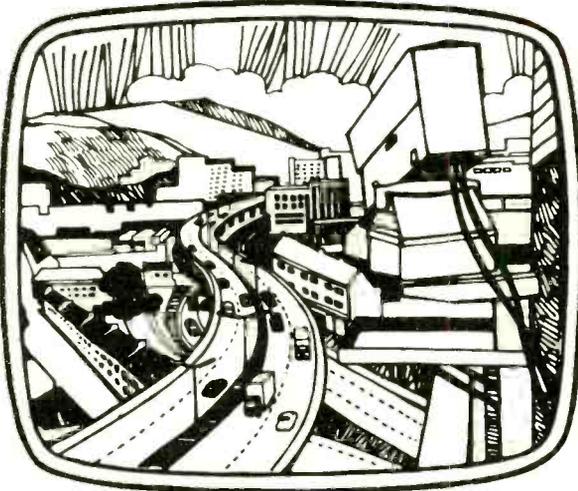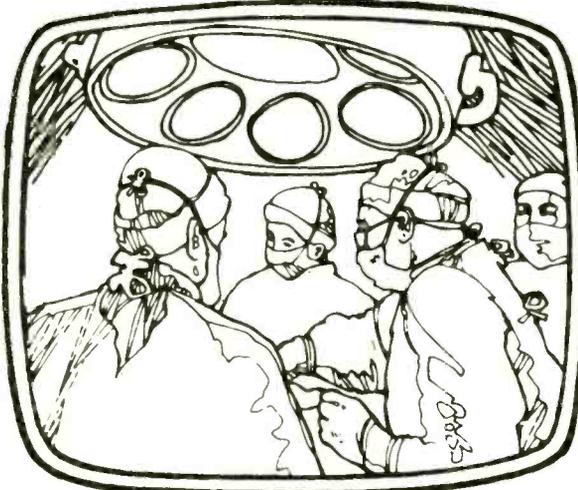
SECURITY DEPENDS ON CCTV- AND ON EEV VIDICONS.



Surveillance equipment must be reliable. EEV vidicons give you tube reliability you can depend on.

Reliable operation – hour after hour, year after year – is essential for closed circuit cameras. You're more likely to get this kind of consistent reliability with tubes from the vidicon experts: EEV.

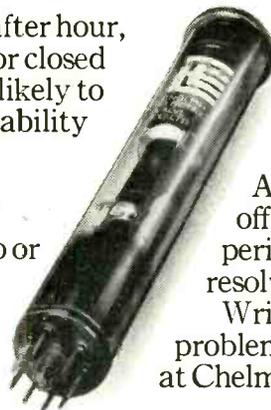EEV vidicons cover all TV pick-up applications, in mono or colour, for most cameras – in electrostatically focused and magnetically focused types (separate or integral mesh)



with a range of photo-surfaces. Special rugged types are available to withstand shock or vibration.

The EEV vidicon range is wide.

And it grows. And every tube offers you the benefits of EEV experience: good picture geometry and resolution and a long life expectation.

Write for type lists: or if you have a problem, call our camera tube engineers at Chelmsford.


EEV AND M-OV KNOW HOW.

LAP 50

ENGLISH ELECTRIC VALVE CO LTD, Chelmsford, Essex, England CM1 2QU. Tel: 0245 61777. Telex: 99103. Grams: Enelectico Chelmsford. **S.E.C.** 

WW—089 FOR FURTHER DETAILS

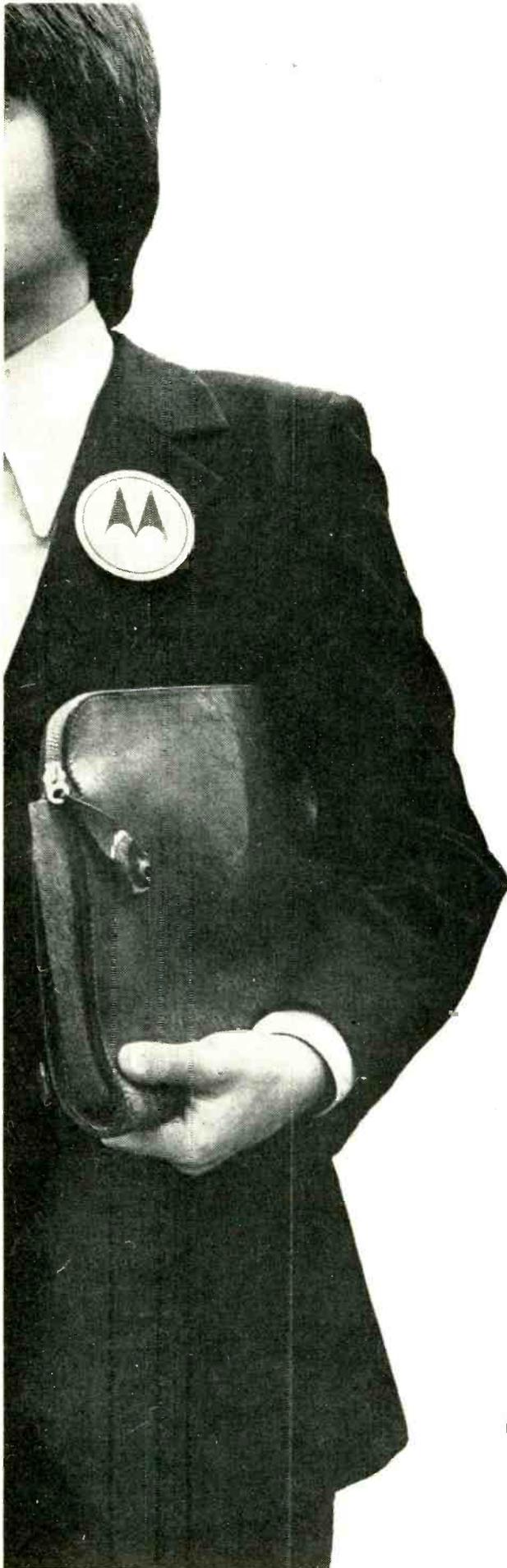In the power business, others follow our lead.



When it comes to the power devices, Motorola has every application buttoned up.

Automotive. Motorola transistors for high voltage ignition and seat belt interlock systems lead the way to safety and pollution control, while transistorised voltage regulators help to improve reliability.

Computers. Motorola's low cost Darlington's permit CMOS and MOS to interface with large current/voltage devices - from milliamps to Amps easily.

Consumer. Motorola leads again with plastic and metal transistors for T.V. convergence, deflection and power supply stages. Our NPN and PNP Darlington's are suited to the fully complementary designs of today's audio amplifiers.

Industrial. Motorola high voltage power transistors make for smaller more efficient switching power supplies. And we are still very much committed to Germanium - the most economic solution for low voltage/high current applications.

Silicon or Germanium (6 types of device construction available in plastic or metal packages) and monolithic Darlington's mean that there's a reliable Motorola power device for every application.

So you see in the power business we lead and others follow.

For full further details press the Motorola power button - write or phone your nearest Motorola distributor or get in touch direct.

 **MOTOROLA Semiconductors**

Motorola Semiconductors Ltd., York House, Empire Way, Wembley, Middlesex. Telephone: 01-903 0944.
European manufacturing facilities at Toulouse and East Kilbride.
Distributors: Celdis Ltd., Reading, East Kilbride; GDS (Sales) Ltd., Slough, Dublin; Jermyn, Sevenoaks; Lock Distribution, Oldham; Semicomps Ltd., Wembley.

WW-090 FOR FURTHER DETAILS

Realm of Microwaves

6. Microwave antennae

by M. W. Hosking,* M.Sc.

Microwave antennae, although no different in principle to other types, are much smaller in size for a given gain. This is because of the relatively small wavelengths involved, making it possible to use aerial dimensions tens or hundreds of times the wavelength. It thus becomes more convenient and realistic to talk about an aerial aperture for transmitting or receiving power rather than an effective height for coupling to the electric field. Before discussing individual aerials it will be as well to start off with some basic definitions.

An isotropic source is an origin of energy which radiates uniformly in all directions. Placed at the centre of a sphere, the power density anywhere on the surface of the sphere would be constant. Needless to say, such a radiator is not realisable in practice, but the concept is used as a point of reference for comparing the performance of an aerial.

Gain and directivity

There are two measures of aerial gain related by the efficiency of the aerial. The power gain G is defined by

$$G = \frac{\text{radiated power density}}{\text{power density from isotropic source}}$$

This is the figure usually quoted as it includes all the losses and imperfections associated with the antenna. Usually, gain is expressed in dB and often quoted without reference to direction, when it is then taken as applying to the peak of the main beam.

The second type of gain is the directivity D and can either be calculated or measured from the polar diagram. It is defined as

$$D = \frac{\text{maximum power density}}{\text{average power density}}$$

and as this does not take into account the effect of any losses it represents the ideal case. From the polar diagram of Fig. 1, the maximum of the pattern is readily seen and the average value is obtained by integrating the power density over the full 360° to give the directivity in that particular plane.

Further, as the directivity is a ratio, it is not necessary to know any absolute values; when working out the directivity from a polar plot, one reads off the peak value as a

unit of length and divides it by the mean value obtained with the aid of a planimeter. Directivity and gain are related by $G = \eta D$, where η is the efficiency of the antenna. Depending on type and quality of manufacture, the efficiency of most microwave antennae lies between 50 and 75%.

From the definition of directivity, it is possible to obtain a "rule of thumb" estimate of the gain of an antenna from its 3-dB beamwidth. It is necessary to assume an equivalent polar diagram in which the radiated power is confined to within the solid angle formed by the product of the beamwidths in two orthogonal planes. One plane is usually taken as that parallel to the radiated electric field vector—the E-plane—and the other as parallel to the magnetic field vector—the H-plane. So if this pattern has an amplitude of unity, the maximum power density is $1/\theta_E\theta_H$, θ_E and θ_H being the half-power beamwidth in radians. The

average power density is simply $1/4\pi$ and so the directivity is $4\pi/\theta_E\theta_H$, or $41,253/\theta_E\theta_H$ with the beamwidths in degrees. To obtain the gain an estimate must be made of the efficiency.

Sidelobes

The great majority of polar patterns consist of a single main beam and a series of minor beams which occur at certain angular positions and the amplitudes of which decrease as the angular distance from the main beam increases. The presence of radiated power in these sidelobes is wasteful and gives a reduction in efficiency, so effort is made to reduce them. In addition, many radar systems these days have to operate in environments where they may be electrically "jammed" and the presence of high sidelobes would make them that much more susceptible. For use in low-angle tracking, high sidelobes could give rise to spurious and misleading echoes from the ground.

Antenna aperture

It is convenient to consider microwave antennae as having an effective area which collects the incident power. Such a concept is reasonable in the case of dish types, but not so obvious for, say, a dipole. Where there is a physical aperture to measure, the effective area is less than the geometrical one by a factor which takes into account the efficiency of the aperture as a radiator. The effective area A_e is related to antenna gain by $G = 4\pi A_e/\lambda^2$. The isotropic radiator, having a gain of unity, has an effective area of $\lambda^2/4\pi$.

Impedance is important from the point of view of maximum power transfer, either transmitting or receiving, and of therefore obtaining a good match. It happens that this parameter is exceedingly complex to determine and, apart from a few very simple antennae, it has not been possible or worthwhile to compute the impedance of all types. Instead, the quite-satisfactory process of empirical matching is carried out when needed.

Having thus established some of the main parameters used to describe the performance of an antenna, this article concentrates on a widely-used type in the microwave region which radiates from an area aperture. An interesting fact about the polar pattern produced from such a radiator is that besides the gain being governed by the

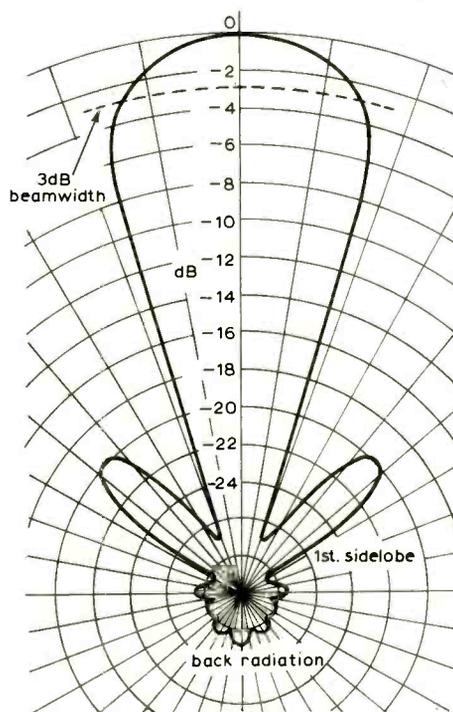
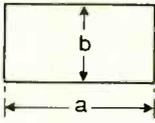
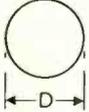


Fig. 1. General polar diagram showing the directive type of main beam that can be obtained in the microwave region. Parameters such as gain, beamwidth and side-lobe level are within the control of the designer.

*British Aircraft Corporation

Beam dimensions from open-ended rectangular and circular waveguides

	Directivity	3-dB beamwidth		Width to first null		
		E-plane	H-plane	E-plane	H-plane	
Rectangular	$\frac{10.2 ab}{\lambda^2}$	$\frac{\lambda}{b} \cdot 50^\circ$	$\frac{\lambda}{a} \cdot 65^\circ$	$2 \sin^{-1}(\lambda/b)$	$2 \sin^{-1}(3\lambda/2a)$	
Circular	$\frac{2.87D^2}{\lambda}$	$\frac{\lambda}{D} \cdot 29.4^\circ$	$\frac{\lambda}{D} \cdot 50^\circ$	$2 \sin^{-1}(1.22\lambda/D)$	$2 \sin^{-1}(1.7\lambda/D)$	

physical size, both the gain and the sidelobe level are functions of the electric and magnetic field amplitudes across the aperture. One can consider the whole area to be made up of a large number of small, individual radiators, each of which is supplied with its own electromagnetic fields. By varying the field strength by different amounts at different points, it is thus possible to taper the overall aperture field in any desired way. When all radiating points have the same amplitude, the aperture is called uniformly illuminated and has its maximum gain.

However, this distribution also gives the highest sidelobe level. By illuminating the aperture in various non-uniform ways and accepting a slight decrease in gain, together with widening of the main beam, the sidelobes may be reduced. A widely-used distribution, for instance, follows a cosine law, the electric field being zero at the edges of the aperture and rising to a maximum at the centre. In this case, a reduction in sidelobes of about 10dB together with a decrease in gain of 1dB would be obtained compared with a uniform illumination on a rectangular aperture.

A practical form of antenna, often used as the feed for a larger reflector-type, is simply open-ended rectangular or circular waveguide. In this case, the aperture distribution is governed by the field pattern within the waveguide, which in turn depends on the particular mode it is supporting. Usually the dominant mode is the one of interest and the Table (p. 502) lists the main beam dimensions for rectangular and circular guide when just the dominant mode is present. Both gain and beamwidth of the waveguide radiator are proportional to the area of the aperture, so that to obtain a narrow beam or high gain, a large waveguide would be needed.

As shown in part 2 of this series (March) once a certain, fairly limited, range of waveguide dimensions had been exceeded, then higher-order modes can propagate. So that using oversized waveguide to obtain a larger effective area is not recommended; any higher modes appearing would serve only to waste power and to distort the radiated pattern. Instead, the technique used is to flare out the waveguide dimensions in a controlled way to form a waveguide horn. If only two sides of a rectangular guide are flared, this is called either an E or H-plane sectoral horn as in Fig. 2; while flaring in other directions as well produces pyramidal and conical horns.

Higher-order modes can be generated at a discontinuity in a transmission line, although in the case of a guide below cut-off, they are rapidly attenuated. The horn flare angle must be chosen so that any higher-modes generated at the throat of the horn are suppressed by the time they reach horn dimensions wherein they can propagate. Within this constraint, the gain of a sectoral horn increases with increasing aperture area.

If the axial length L of the horn is kept constant, together with the height b (in the case of the E-plane horn), and the aperture then widened, the gain steadily increases, passes through a maximum and then decreases. Horns with dimensions corresponding to this maximum are called optimum horns and Fig. 3(a) shows the variation in directivity of the E-plane sectoral horn for various axial lengths. Similar results obtain for the H-plane horn with constant L and a , and are shown in Fig. 3(b).

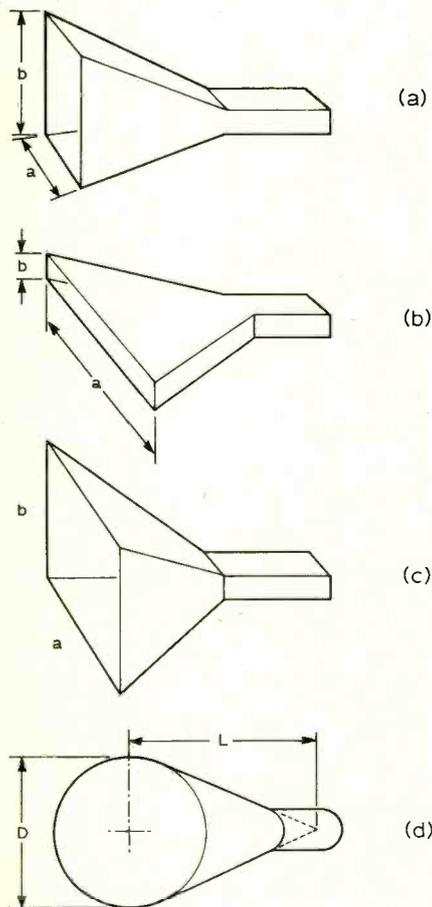


Fig. 2. Main types of waveguide horn formed by flaring the waveguide walls in a controlled fashion (a) E-plane sectoral horn, (b) H-plane sectoral horn, (c) pyramidal horn, (d) conical horn.

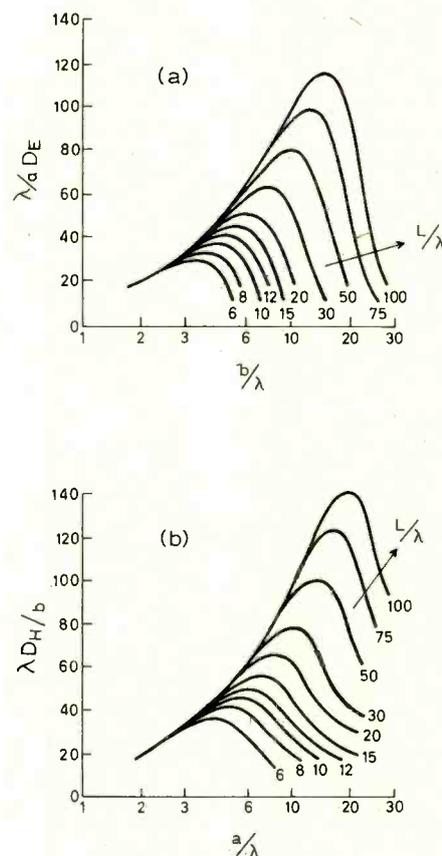


Fig. 3. For a fixed length of horn, directivity increases as the aperture widens and passes through a maximum value. Composite plots are shown here of the directivities of (a) E-plane and (b) H-plane sectoral horns having various lengths. Dimensions for an optimum horn can easily be seen.

By combining the E and H-plane flares, the pyramidal horn is produced and, because the radiating mechanism is well-understood, enabling the gain to be accurately calculated, this type of horn is often used as a gain standard. Theoretically, the directivity of the pyramidal horn can be obtained from the sectoral horn directivities, D_E and D_H and is $D_E D_H \pi \lambda^2 / 32ab$. Optimum dimensions for this type of horn are summarized in Fig. 4(a). For example, a horn with a 25-dB directivity and of optimum proportions would have a length of 20 wavelengths and an aperture of 8.3 by 6.7 wavelengths.

Finally, circular waveguide can be used to produce the conical horn, the optimum dimensions versus directivity of which are plotted in Fig. 4(b). The dimensions of pyramidal and conical horns are very similar for a particular gain so, in that respect, there is no advantage of one over the other. The conical shape is more suited to a circularly-polarized antenna, but the useful waveguide bandwidth is lower in circular than in rectangular guide.

Reflector antenna

A widely-used class of antenna fully exploits the advantages of the small microwave wavelengths to produce a highly-directive narrow beam from a conveniently-sized aperture. This is the reflector antenna and consists of a small radiator called the primary source or feed, which is used to illuminate a large reflecting dish which reflects radiation into space in the form of a concentrated beam. The feed can be of any convenient design, but the pyramidal or conical horn is widely used. For the main dish a paraboloidal contour finds most application, the geometry of the system being shown in Fig. 5 together with some important relationships.

The parabola has two important properties which account for its wide usage. Firstly, with the feed placed at the focus of the parabola, reflected rays are concentrated within a beam parallel to the axis. Conversely, when used as a receiver, the incident radiation on the main dish will be focused to the one point on the axis. Secondly, the path lengths of rays from the focus to the reflector and out into the distance are the same. This means that, for a small feed and large dish, the feed appears as a point source with a spherical wavefront which is converted by a parabola into a plane wavefront having a uniform phase. Because the reflecting dish is usually several tens of wavelengths in diameter high gains can be achieved, 30 to 45dB being typical, resulting in beamwidths of less than 2° and making the system eminently suitable for target-tracking radar or as part of a low signal-strength receiver.

When designing a parabolic reflector, one of the first parameters to settle is the ratio of focal length to dish diameter (F/D). This is determined by both mechanical and electrical considerations, a small ratio meaning a deep dish and a large ratio meaning a very shallow one, both have their problems when it comes to mounting both dish and feed. In addition, the small diameter, large focal length dish requires a larger feed to produce the narrower illu-

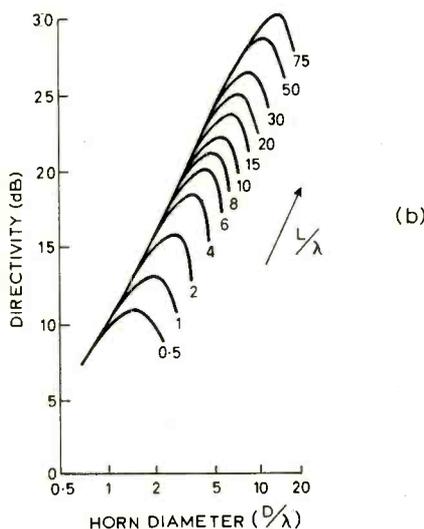
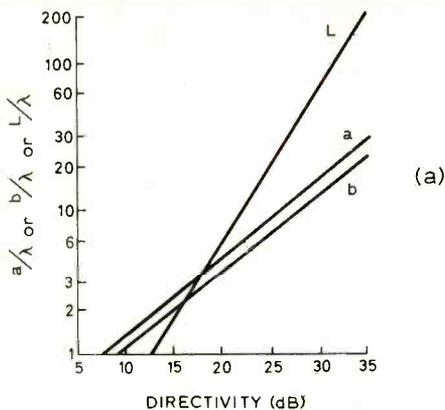


Fig. 4. In similar fashion to the sectoral horns, the pyramidal and conical versions also have optimum aperture dimensions for a fixed length. Directivities are plotted for (a) pyramidal horn and (b) conical horn.

Fig. 6. For a quick estimate of feed-horn performance, this graph presents the half-angle ψ as a function of F/D ratio.


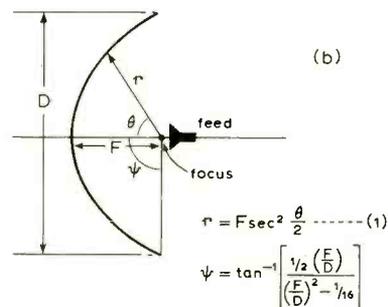
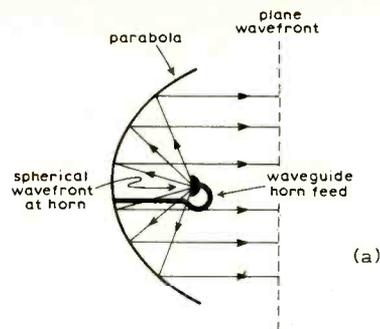


Fig. 5. Paraboloid reflector can produce high directivity and a narrow, pencil beam and allows side-lobe level control by proper design of the feed. Because all path-lengths from the feed to the far field are equal, the paraboloid converts the initially spherical wavefront into a plane-wavefront, collimated beam.

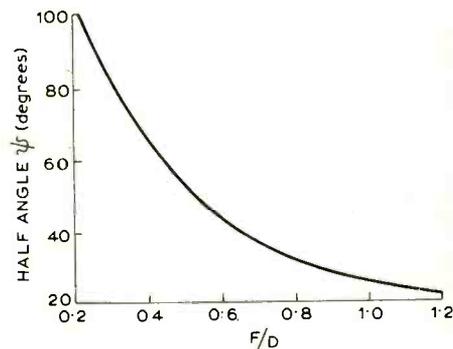

minating beam, thereby introducing more aperture blocking, while the large dish makes feed design difficult in obtaining a uniform phase. Generally, parabolas have an F/D ratio of between 0.3 and 0.5.

Another important factor in this type of antenna and one which affects the overall efficiency is the variation in field amplitude across the aperture of the reflector. For maximum gain, a uniformly illuminated aperture is required, and to obtain that with this system, a paraboloid with large F/D ratio and a very wide-beam feed would be needed. With such a feed, a lot of the radiated power would spill over the edge of the reflector and be lost, defeating the object. On the other hand, the dish diameter could be increased, giving a small F/D ratio and intercepting more of the feed radiation. Efficiency would then fall because of the departure from a non-uniform field distribution. There would thus seem to be a compromise situation between these two effects

and it is found in practice that optimum efficiency occurs for a reflector illumination such that the power level at the edge is 10 to 12 dB below that of the centre. In this case, the level of the first side-lobes below the main beam is about 23 dB.

Often, maximum gain is not all-important and a lower side-lobe level is desired, so for a sacrifice of 1 to 2 dB of gain, decreasing the edge illumination to 20 dB gives a side lobe level of about -26 dB. Clearly then, the radiation pattern of the feed is of utmost importance in controlling the efficiency of the system.

When assessing the design of a paraboloidal reflector, some useful relationships can be presented in graphical form. Equation 2 of Fig. 5, for instance, is plotted in Fig. 6 to give the subtended half-angle of the feed on the dish. Having chosen F/D , the half-angle can be used to determine the radiation pattern of the feed required to produce a particular illumination taper.

First, a correction factor must be applied. Referring to Fig. 5, the path length of a ray, r , increases as its axial angle θ increases. So as the power level of a spherical wavefront varies as the inverse square of path length, there is already some aperture taper across the paraboloid. The amount of attenuation is $20 \log_{10} (r/F)$ which from equation 1 can be written as $20 \log_{10} \sec^2 (\theta/2)$ and is plotted in Fig. 7.

Suppose we had a paraboloid with an F/D of 0.35 and we require an edge taper level of -15 dB. Fig. 6 shows that the subtended half-angle is about 71° , resulting in an inverse-square attenuation of 3.6 dB. This means that 3.6 dB of the required 15 dB is inherent in the system and, therefore, the feed has to have a radiation pattern which is only 11.4 dB down on its peak at an angle of 71° .

By taking into account the E and H-plane radiation characteristics of the feed, together with the dish illumination required, it is possible to define an overall directivity for the reflector system. The useful expression emerging is $D = D_E + D_H + 10 \log_{10} A/\lambda^2$ (dB) where A is the area of the reflector, and equals $\pi D^2/4$ for a circular parabola. Directivity factors D_E and D_H take into account the illumination taper and the type of feed. A popular feed is the pyramidal horn and for this case the directivity factors are plotted in Fig. 8. Thus, if the reflector of the previous example was required to have a directivity of 40 dB at a frequency of 20,000 MHz, $D_E = 4.8$ dB and $D_H = 4.5$ dB. So, $10 \log_{10} \pi D^2/4\lambda^2 = 30.7$ dB and the reflector diameter would need to be 58 cm. In practice, there are more losses associated with the system and typical efficiencies lie between 55 and 65%.

Finally, from the relationship given earlier between beamwidth and directivity, a rough estimate of the 3-dB beamwidth is $70\lambda/D$ degrees. In the above example, the beamwidth will be just under 2° . This serves to demonstrate the highly directive type of beam which can be produced by this type of moderately-sized antenna at microwave frequencies.

One problem that exists with this type of antenna arises from the physical presence of the feed in the aperture of the main reflector. Firstly, the feed and its support introduce aperture blocking or shadowing which has the effect of reducing the gain and degrading the sidelobe level. As the transverse feed dimensions do not change markedly with dish diameter, this effect obviously gets worse for smaller reflectors. Secondly, there is interaction between feed and dish, in that energy reflected from near the axis of the paraboloid enters the feed aperture and interacts with the primary radiation. The effect is similar to a condition of mismatch and impairs the radiation efficiency of the feed. To counteract this, various matching devices can be incorporated in the feed, or, as shown in Fig. 9(a) a plate can be placed at the apex of the paraboloid and its size and position adjusted until the reflected signal is equal in amplitude but opposite in phase to signals arriving from other parts around the apex. Under these conditions, cancellation of the mismatch occurs.

Fig. 9(b) illustrates another technique: that of offsetting the feed. The feed is still placed at the focus of the paraboloid, but is inclined to illuminate an off-centre section and the remainder of the reflector can be removed. There is no longer any aperture

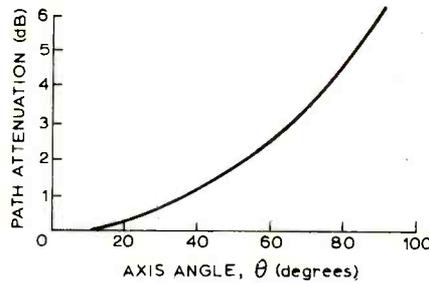


Fig. 7. Natural $1/r^2$ variation in radiated energy contributes towards the aperture taper and must be taken into account when designing the feed.

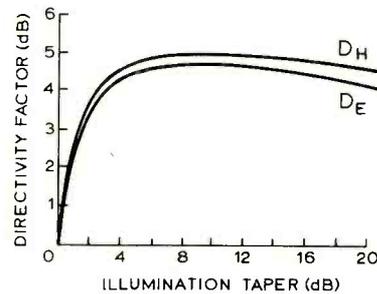


Fig. 8. Directivity of the complete parabolic aerial can be estimated with relation to the feed parameters. Plotted here are E- and H-plane directivity factors for a pyramidal horn.

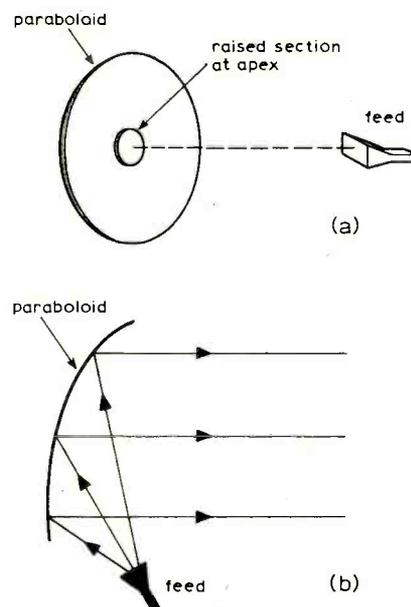


Fig. 9. Aperture blocking by the feed reduces the gain and degrades the side-lobe level of the paraboloid antenna and several methods exist for reducing the effect. Two are shown (a) raising the apex of the dish and (b) offsetting the feed.

blocking, nor any feed/reflector mismatch effects. The main advantage of the offset feed is that it gives several dB improvement in sidelobe level. The aperture field distribution is no longer symmetrical and at offset angles greater than about 15° , transversely-polarized field components and an effective broadening of the radiation pattern start to significantly reduce the gain.

Cassegrain antenna

A widely-used variation of the simple paraboloid reflector is the Cassegrain system, which operates on the same principles as the optical versions in telescopes. Fig. 10 shows the general layout, together with some important geometrical relationships. An extra element has been added in the form of a hyperboloid sub-reflector and the position of the primary feed has been changed. The hyperboloid has two focal points, one real and one virtual, which are made to coincide with the feed position in one case and the focus of the paraboloidal main reflector in the other. The effect of this arrangement can be seen from the ray-tracing of Fig. 10(a) where an image of the real feed is produced at the virtual focus. Thus, as far as the paraboloid is concerned, it is being illuminated from this point and we have the system already described. Because of the magnifying properties of an hyperbola the image feed has a smaller effective area than the real one, but a correspondingly broader beamwidth and this can be used to advantage in cases where the feed is bulky.

One of the *raison d'etre* of the Cassegrain system is that it has an effective focal length which is larger than the focal length of the paraboloid by a factor equal to the magnification. A paraboloid with a particular F/D ratio can be made to have the same effect as one with a larger ratio by using the Cassegrain system. As regards tapering the aperture illumination of the main dish, this is done in similar fashion to that already described. The difference in the Cassegrain system is that the focal length of the paraboloid is now the effective focal length. For simplicity, only the true Cassegrain parabola/hyperbola system has been mentioned, but to obtain various combinations of beam shape and aperture-blocking, the sub-reflector can be varied from convex to flat to concave and can also be elliptical. Similarly with the main reflector.

Aperture blocking itself is more serious with the Cassegrain type of antenna because the sub-reflector tends to be larger than a simple feed. Several methods exist for minimizing this, one of which depends on an optimum choice of dimensions for both feed and sub-reflector. Fig. 10(a) shows that the sub-reflector diameter may be reduced either by bringing it closer to the feed, or by making the feed itself more directive. After a certain point the stage is reached where the shadowing caused by the feed on the paraboloid is greater than the blocking due to the sub-reflector. There thus exists an optimum when the shadows projected by the sub-reflector and feed are equal in area.

A second technique, the principles of which will be covered in a later article, makes use of the fact that it is not necessary

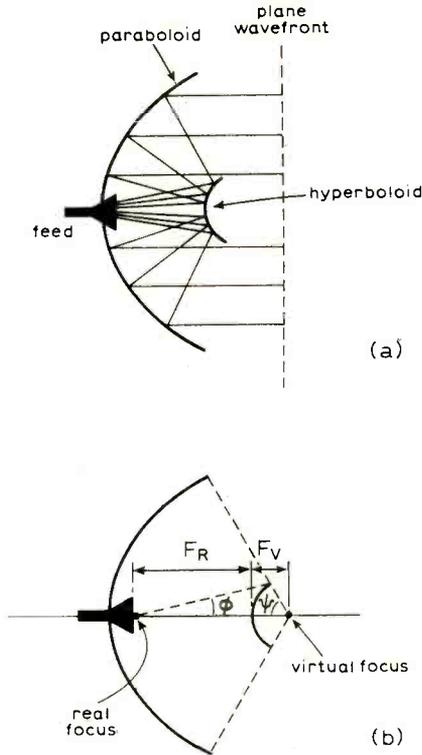


Fig. 10. Cassegrain antenna uses an additional element in the form of an hyperbolic sub-reflector and has an effective focal length which is longer than the focal length of the parabola. An image of the feed is formed at the virtual focus and illuminating radiation appears as coming from this point.

to have a solid metal dish to reflect energy. A properly designed grating of wires will do the job just as well, reflecting radiation whose electric field vector is parallel to the wires. For an E-vector perpendicular to the wires, the grating appears transparent and the radiation can pass through undisturbed. Also, by using a wire grating, it is possible to construct a reflector which will rotate the polarization of the incident radiation. So the sub-reflector could be made of a grid of horizontal wires and the main parabolic dish could incorporate a polarization-twisting arrangement. Horizontally-polarized radiation from the feed would be reflected from the sub-reflector as onto the main dish and would emerge as a vertically-polarized field, to which the sub-reflector is transparent. Thus—no aperture blockage by the sub-reflector. It is evident that this system can only be used with singly-polarized antennae.

Besides the ability to tolerate a large feed, the Cassegrain antenna has several other advantages over the simple parabolic reflector. Having the feed tucked away at the rear of the dish eliminates the relatively long waveguide run and the associated losses. Although perhaps only a fraction of a dB, this is important to low-noise receivers such as might be used in radio-telescope and communication systems. Because of the positioning of the feed, there is also less noise introduced into the Cassegrain system by spill-over radiation being reflected from the ground.

Literature Received

For further information on any item include the WW number on the reader reply card

ACTIVE DEVICES

"Laser trimming techniques for thick film resistors" is a 6-page publication describing the advantages and use of laser trimming techniques. DuPont de Nemours International S.A., Post Office Box CH-1211, Geneva 24, Switzerland WW 401

PASSIVE DEVICES

"Precision Self-latching Electrical Connectors" is a wall chart containing details of the sizes, make-up, and electrical characteristics of standard Lemo connectors from size 00 to 06. Lemo (U.K.) Ltd, Worthing House, 6 South Street, Worthing, Sussex, BN11 3AE WW 402

EQUIPMENT

We have received a data sheet describing the series RO200C Parallel Display Controllers which provide alphanumeric data display from a computer data bus. Output is composite video, compatible with E.I.A. standard 525-line video monitors. Ann Arbor Terminals Inc., 6107 Jackson Road, Ann Arbor, Michigan 48103, U.S.A. WW 403

A leaflet describing a series of on-line and off-line electrostatic proofers designed for use with phototypesetting systems explains the "Matrix Electrostatic Writing Technique" and illustrates how Versatec Matrix Proofer fit into the proofing cycle of a phototypeset publication. Versatec Inc., 10100 Bubb Road, Cupertino, California 95014, U.S.A. WW 404

The HP-45 and HP-46 are pocket and desk top calculators respectively which are described in a leaflet sent to us by Hewlett-Packard Ltd, 224 Bath Road, Slough, Bucks. SL1 4DS.

Electrical and pneumatic input strip indicators are the subject of a brochure we have received. These instruments are designed in two ranges for use in control room and on-plant environments. Andrew Salanson, Penny & Giles Ltd, Mudeford, Christchurch, Hampshire BH23 4AT WW 405

A six-page leaflet illustrating a comprehensive selection from their current range of electrical indicating instruments provides a selection guide for all standard ranges of Crompton instruments for applications ranging from educational and medical to industrial and military use. Crompton Parkinson Ltd, 50/52 Marefair, Northampton NN1 1NY WW 406

Bahco Tools Ltd, 266B St. Ann's Road, Tottenham, London N.15, has published a leaflet containing illustrations, dimensions and cutting capacities of the range of sixteen types of pliers and nippers developed by Bahco of Sweden WW 407

We have received four brochures on new products which B. Hepworth are to handle for the Hickok company of America. B. Hepworth & Co., P.O. Box 10, Chemical Works, Kidderminster, Worcestershire.

- Basic electronic systems technology WW 408
- Fluid power teaching systems WW 409
- Numerical control WW 410
- Electronics equipment for vocational/technical programs WW 411

GENERAL INFORMATION

The British Overseas Trade Board has published a 1973 edition of its Export Handbook for British firms trading abroad. The book is an up to date description of all the Government services available for exporters, together with mention of private agencies, addresses and a bibliography. British Overseas Trade Board, 1 Victoria Street, London S.W.1 WW 412

The Middlesex Polytechnic Prospectus for 1973-74 describes the available degree, postgraduate, diploma, certificate and short courses. Entry requirements are also listed. Middlesex Polytechnic, P.O. Box 40, Enfield, Middlesex EN3 4SF WW 413

"Training for Company Secretaryship" is one of a series of booklets published by the Department of Employment dealing with commercial and administrative occupations prepared in accordance with the procedure laid down in the Central Training Council's Memorandum No.7 for "training standards for occupations common to a number of industries". Her Majesty's Stationery Office, 49 High Holborn, London WC1V 6HB Price 25p.

Announcements

The product range of Integrated Photomatrix Ltd, Dorchester, Dorset, is now handled in the United States by a subsidiary company, Integrated Photomatrix Inc. The new company is based at 1101 Bristol Road, Mountainside, New Jersey 07092.

"Stereo and Public Address Systems" and "Video Recording" are two courses to be presented (one lecture per week commencing in October) at Norwood Technical College, Main Building, Knight's Hill, London SE27 OTX. Applications to the Senior Administrative Officer.

Rendar Instruments Ltd have appointed Edmundson Electronic Components as their franchised distributors covering the South-East of England and the Midlands. This appointment completes a country-wide distribution network for Rendar. Customers in the South-East should place their orders for Rendar products through Edmundson Electronic Components, 30/50 Ossory Road, London SE1 5AN. Customers in the Midlands should use the Birmingham office at 40/45 Lower Tower Street, Birmingham 19. Products include control knobs, jack plugs and sockets, switches and DIN plugs.

A five day course on "Image Processing" will be held from 12th - 16th November at the Campus Inn, 1920 Northwestern Avenue, West Lafayette, Indiana. The course is intended to familiarize engineers and scientists with the state of the art of optical and digital image processing. For additional information contact Paul A. Wintz, Course Chairman, 605 Lingle Avenue, Lafayette, Indiana 47901, U.S.A.

Total Communications

Switching-centre applications: concluding part of an article on two-way information systems

by E. J. Gargini, * M.I.E.E., M.I.E.R.E.

The first part of this article (September issue) concluded with a discussion of central switching systems for use in two-way information services. In this second part I shall briefly review the progress of the Rediffusion Dial-a-Program (DAP) central switching system, using it as an indication of possible future developments.¹⁰

The basic DAP exchange frame comprises a 12096 cross-point system, using magnet-operated reed switches, for connecting any one of 36 input lines to any one (or more than one) of 336 output lines. After the introduction of a small-scale DAP installation at Thames Television, Teddington, a prototype exchange — capable of operating on 36 channels, but with active equipment for 12 off-air channels and a few locally originated or two-way transmissions — was installed at Dennisport in Cape Cod, U.S.A., together with a network to reach 250 dwellings in an area of about one-third

* Rediffusion Engineering Ltd.

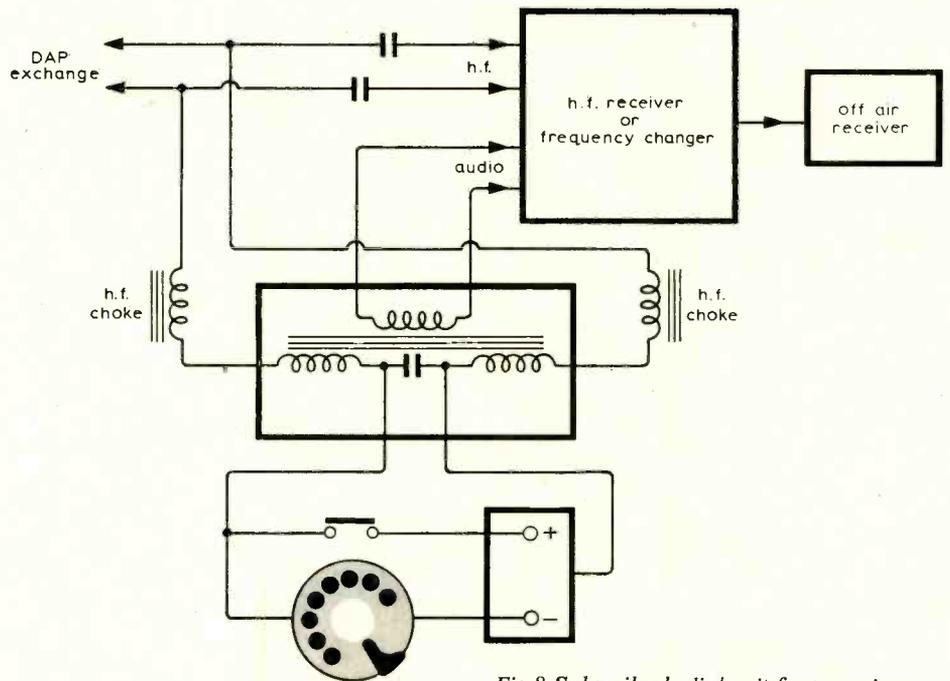


Fig. 8 Subscriber's dial unit for two-wire Dial-a-Program system.

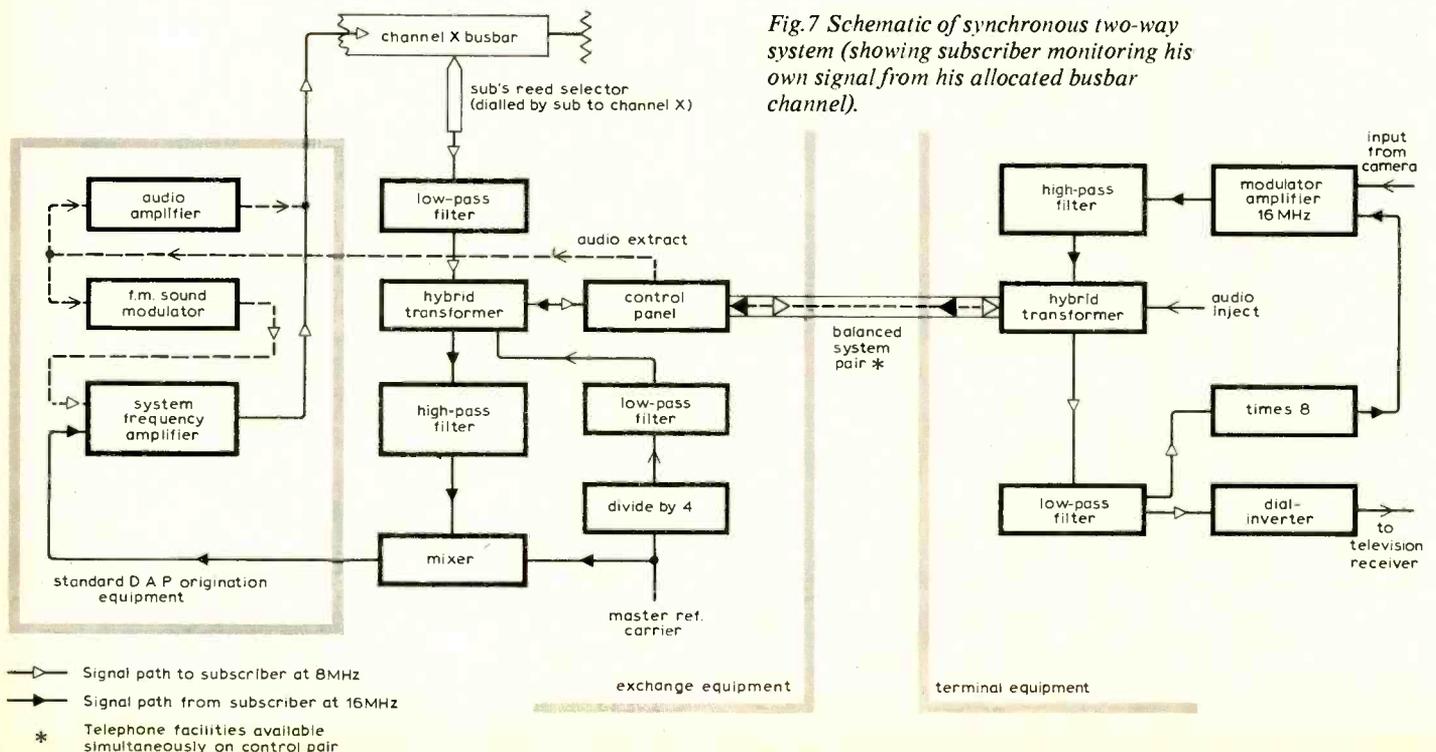


Fig. 7 Schematic of synchronous two-way system (showing subscriber monitoring his own signal from his allocated busbar channel).

of a square mile. Extra lines were made available to feed extra points in half these homes. Some 160 homes are at present using this service, which became operational in August 1970. This prototype installation was undertaken as an engineering field test of the system. The results have been entirely satisfactory, both in quality of television transmission and in reliability. There has been no reported reed switch fault or failure of the distribution network, despite quite wide variation of temperature.

The Cape Cod installation includes two experimental additions which have to do with the communication concept: (1) Television cameras have been operated at two distribution points on the network, i.e. with two-way television signals passing in opposite directions on the same cable circuit; one provides local shoppers with current prices in a small supermarket, the second was used for demonstration purposes. (2) The control pair of the DAP system has been used for telephone purposes on a dedicated basis in conjunction with a two-wire version of DAP, i.e. a DAP system in which dialling and resetting signals are carried on the pair which carries the selected television signals.

Fig. 7 indicates the operation of the two-way television system in which the subscriber originated signal is sent to the exchange on a carrier frequency of twice that of output signals from the exchange. Fig. 8 shows the arrangement of the subscriber's dial unit for the two-wire DAP system.

Fig. 9 shows an application of DAP central switching now installed and working at the Case Western Reserve University at Cleveland, Ohio, U.S.A. In this system the control pair is used on a shared basis — for DAP signalling and for two-way telephonic communication between students and the video tape machine operator. The dial units can be adapted later to include a touch tone signalling system which will permit the student to control video tape machines directly.

The two-way television filtering and frequency changing equipment permits vision signal origination from a number of lecture halls which also serve as viewing centres. This equipment is of course portable and the two-way capability of the DAP system permits the use of cameras from any outlet point; thus separate feed lines for remote programme origination are not required.

Fig. 10 is an outline of a DAP installation at the Nova Park Hotel, Zurich, Switzerland, which has just become operational. This installation is a joint undertaking by Rediffusion International, Rediffusion AG, which is an independent company, and Philips. The system, when completed, will deal with a number of off-air channels and 54 locally originated channels. Eighteen of the locally originated channels and initially six channels from off-air sources will be applied to the DAP exchanges for direct selection by dialling. The remaining 36 locally originated channels will be routed to indi-

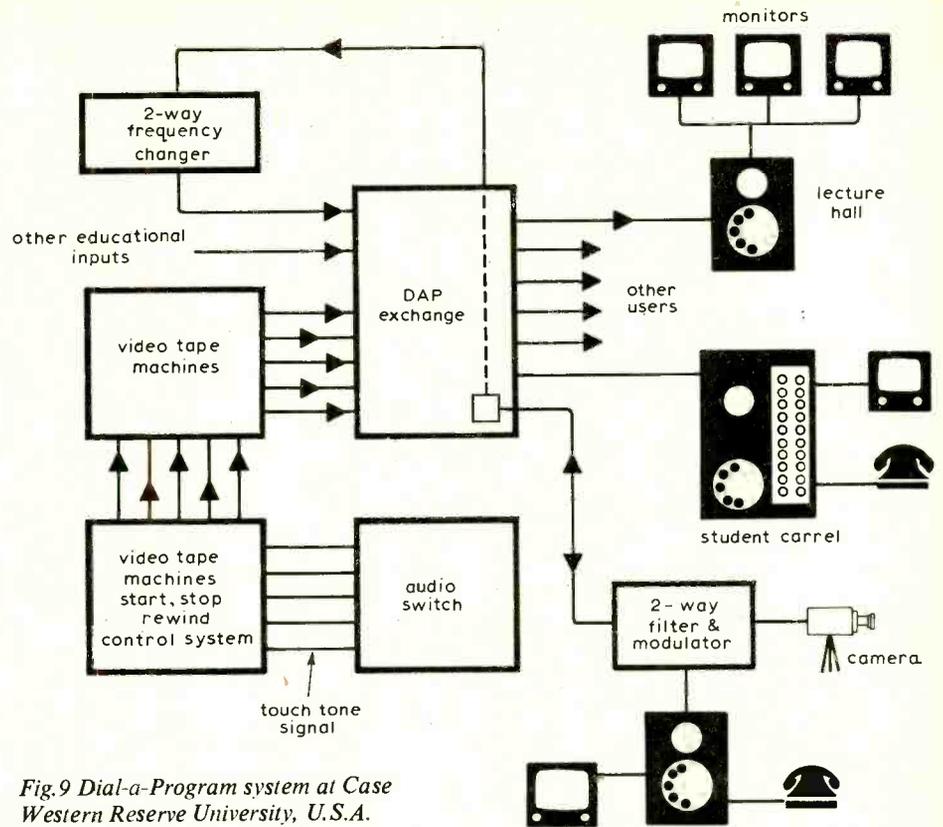


Fig.9 Dial-a-Program system at Case Western Reserve University, U.S.A.

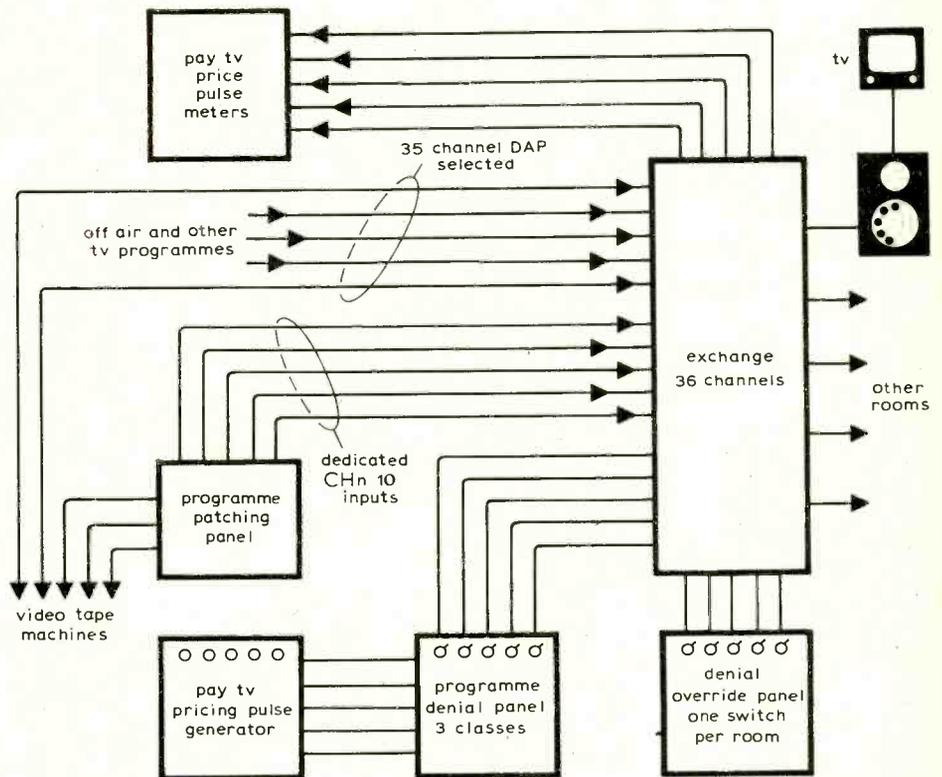


Fig.10 Dial-a-Program conference hotel system in Zurich.

vidual subscribers or groups of up to ten subscribers manually on the programme patching panel indicated. All subscribers have provision on the channel 10 position to receive a dedicated input from the patching panel, and to obtain this service the subscriber will dial a zero and use his telephone. The Nova Park Hotel is to be used as a conference centre and

conference television will be available only to delegates. A "denial" panel equipped with switches for each of 560 rooms will enable hotel staff to permit conference viewing only in rooms assigned to delegates. The switches are three-position types and control the viewing of two or three classes of programme. A programme "denial" panel is provided for placing any


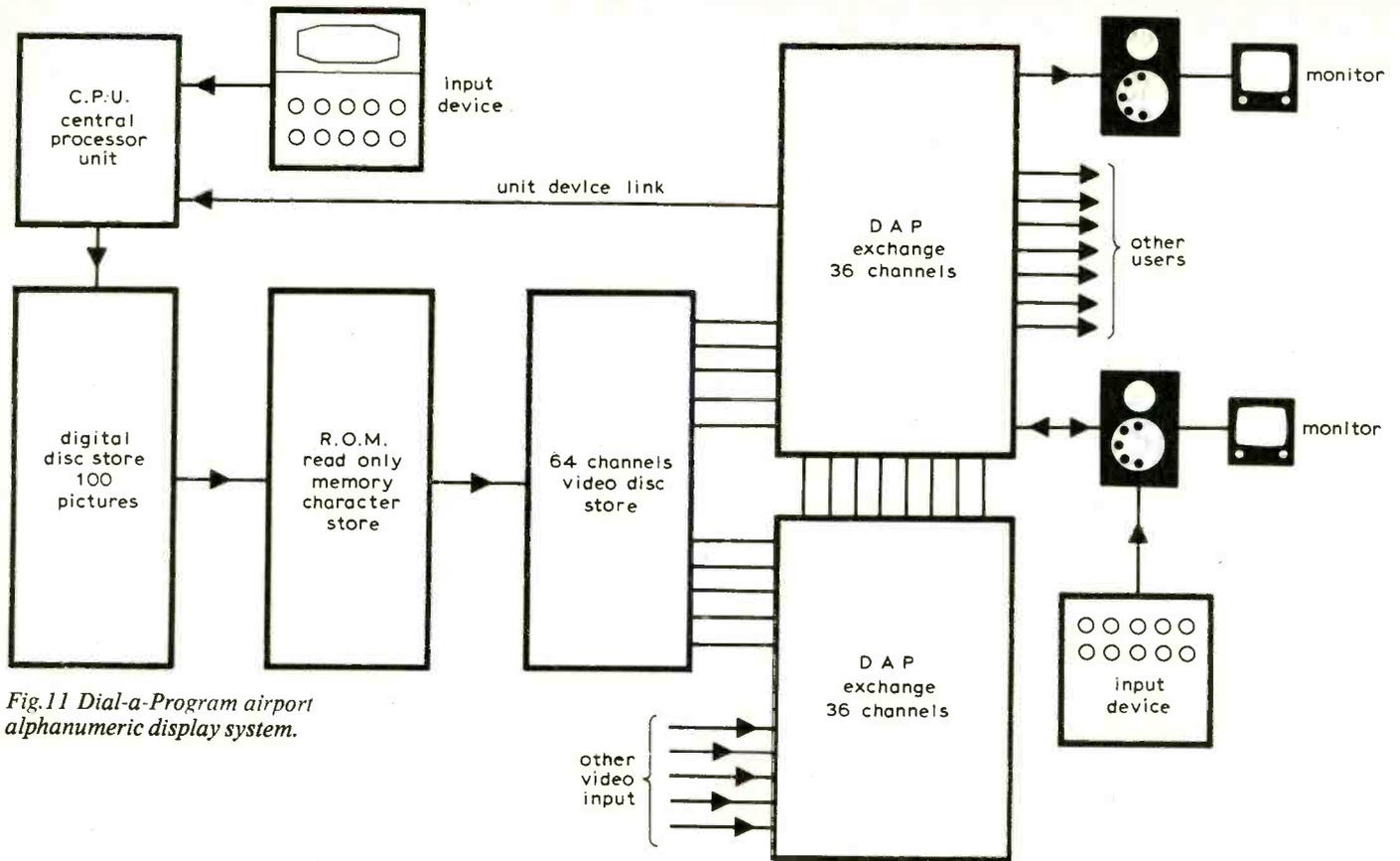


Fig.11 Dial-a-Program airport alphanumeric display system.

Fig.12 Total central-switching system.

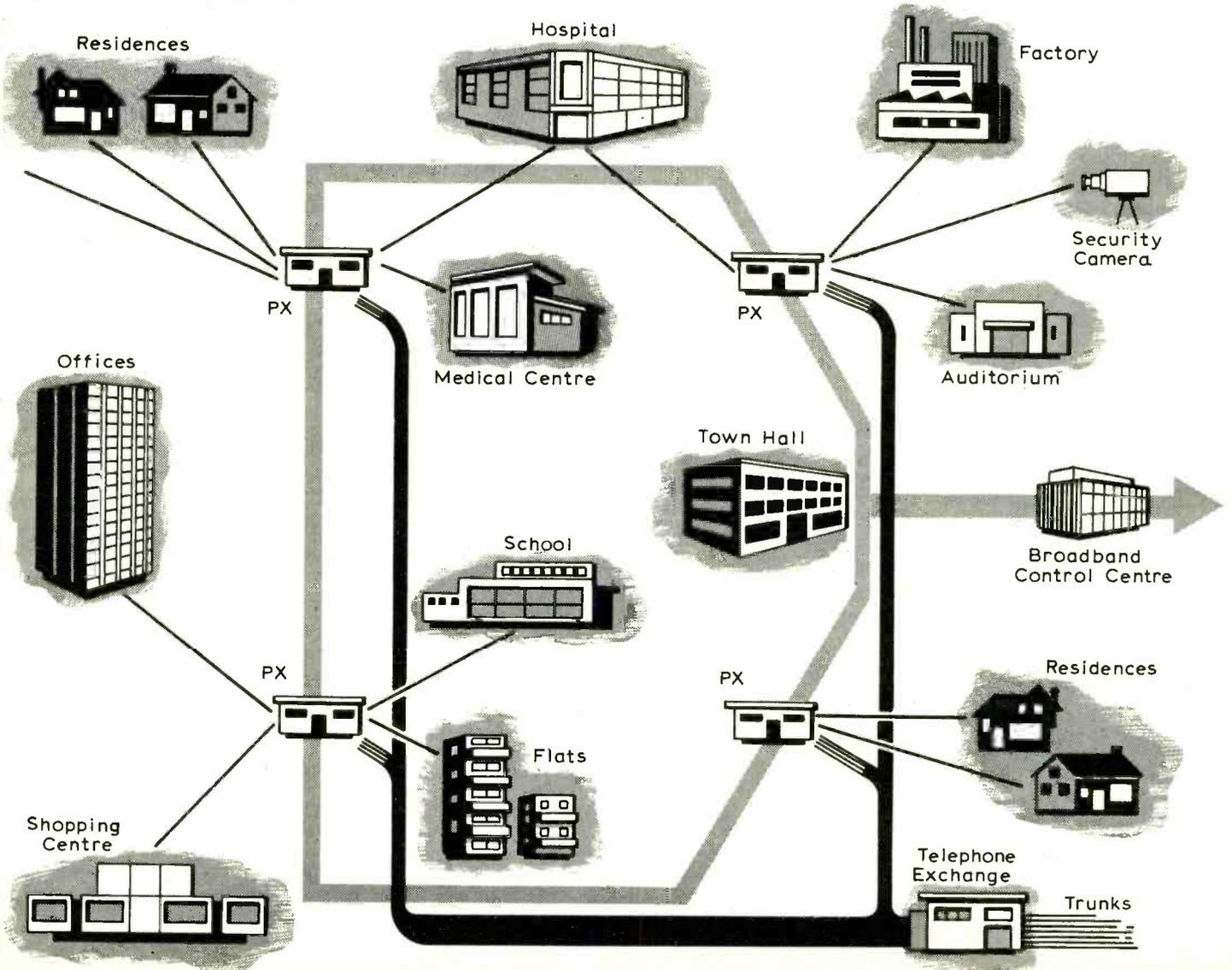

one or more of the 36 DAP busbar channels into the three classes, i.e. two "denial" and one "non-denial".

A feature of the system is that any one or more channels can be pay-television channels, and a pricing panel is included for generating pay-TV pulses on selected channels at a rate determined by the value of the programme. Pay-TV meters, one per room, record the charge to be made to each guest.

Fig. 11 outlines a proposal for an alphanumeric system for airports and demonstrates the versatility of a central switching system. New alphanumeric information, i.e. flight arrival schedules, can be entered by keyboard into the central processor unit either directly or from any of the DAP outlet points using the two-way capability of the system to handle digital data.

Conclusions

I believe the future of telecommunication lies in a total communication system of the central switching type. Fig. 12 summarizes this concept as a marriage between the telephone system of a central exchange embracing a large area and a greater number of integrated television programme and telephone concentrators or local communication exchanges.

Some 85-90% of the wired network route in a town would be a network dedicated to individual subscribers; the remaining 10-15% would be network dedicated to bringing information into and out of communication exchanges. The subscriber network would deal with any amount of visual data and would not need replacement with development of the visual art.

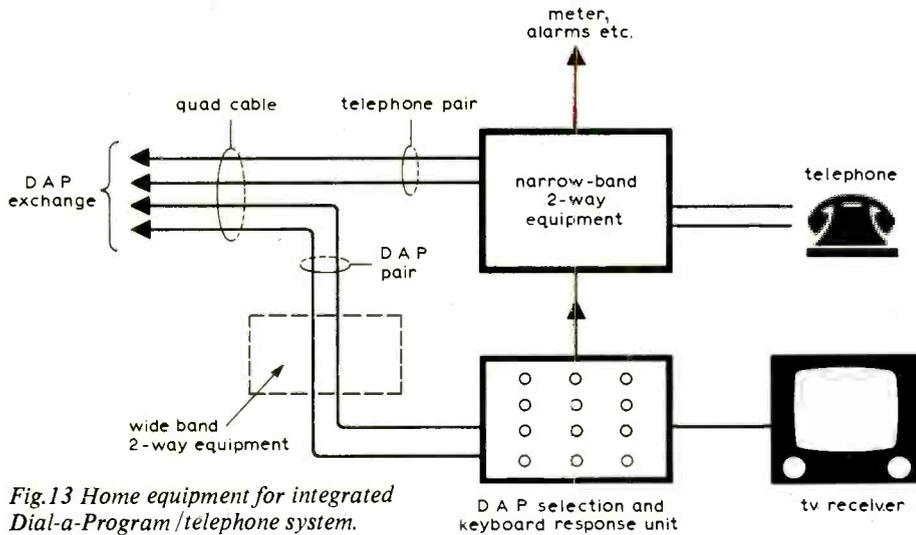


Fig.13 Home equipment for integrated Dial-a-Program/telephone system.

Fig. 13 indicates the simplicity of equipment in the home for an integrated system which is capable of dealing with all the features discussed in this article. Fig. 14 outlines the main components of the integrated switching centre or communication exchange.

At an I. E. E. meeting early in 1972 it was suggested that telephone micro-processors could be used to organize and link up small exchanges or concentrators to large exchanges and that this possibility becomes more attractive as the cost of integrated circuits drops.

Perhaps an organization such as the Independent Communication Authority suggested by Professor H. M. Barlow¹¹ will be formed to consider these matters and to develop a total communication concept for the future.

Acknowledgements. I wish to acknowledge the work done by Rediffusion Engineering Ltd. and its engineers, particularly J. F. Pacey who was responsible for the installation and commissioning of the pilot Dial-a-Program projects in the U.S.A. I thank the directors of Rediffusion Engineering Ltd for permission to publish this article, although I would emphasize that the views expressed are personal and not necessarily the views of the company.

References

10. R. P. Gabriel. "Cable TV and the Wired City". Paper presented to I.E.E., 10th Nov.1971 (*Electronics & Power*, April 1972), also R. P. Gabriel. "Experience with the Dial-a-Program System". Paper presented to I.E.E.E. North East Regional Electronics Meeting (NEREM), Boston, Mass., 2nd-5th Nov.1971.
11. Prof. H. M. Barlow. "Telecommunications services in the U.K. Future development and overall policy", *National Electronics Review*, Vol.7, No.2, March/April 1971.

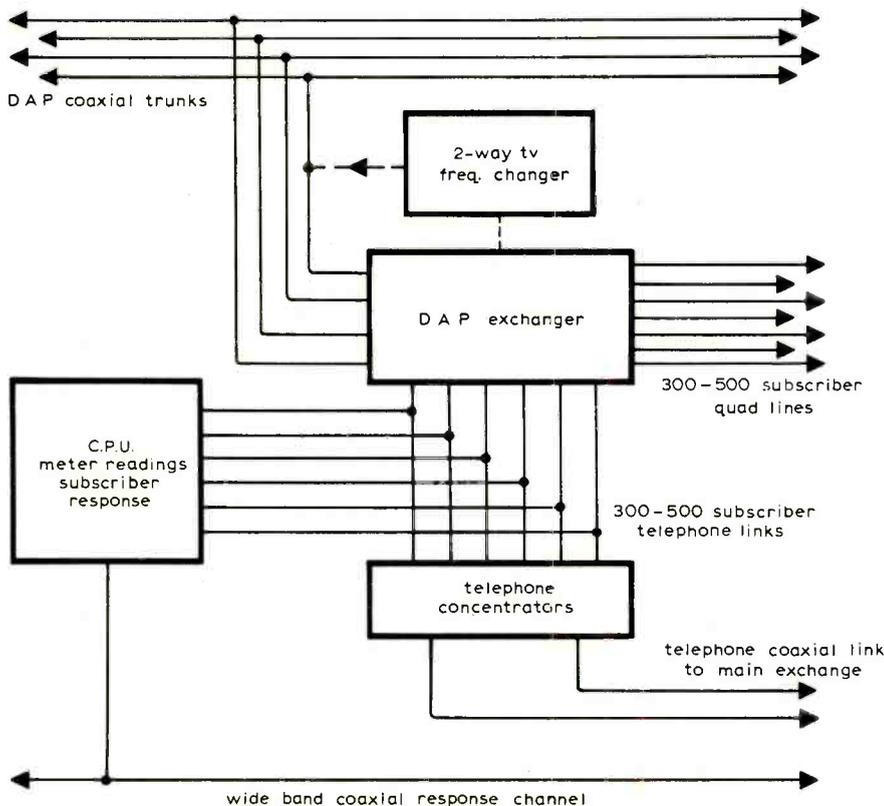


Fig.14 Local communication centre.

Presenting Maintenance Information

Techniques developed by B.B.C. use functional diagrams and minimum of text

by S.W. Amos*, B.Sc., M.I.E.E.

The introduction of the transistor and more particularly the integrated circuit have made possible the construction of extremely compact equipments. The extent of the miniaturization possible with modern solid-state devices is well illustrated by a typical integrated circuit which contains nearly one hundred transistors and as many resistors — all in a package measuring 1in by $\frac{1}{4}$ in by $\frac{1}{8}$ in! An equipment with fifty such i.c.s would contain nearly 5,000 transistors: to use such a wealth of active devices would have been unthinkable in the days of valves. It is practical to employ active devices in such prodigious numbers and thus to construct equipments of very great complexity because solid-state devices are inherently reliable. Nevertheless modern equipments do develop faults which must be found and corrected and this article is concerned generally with the maintenance of modern solid-state equipment and in particular with the form in which maintenance information is presented in the B.B.C.

Factors influencing the form of maintenance literature

The following three features of modern equipment have a direct influence on the form of maintenance literature:

1. The complexity of modern equipment can be such that only the designer understands it thoroughly, and he is unlikely to be enthusiastic about calls on his time to maintain one of his earlier designs. It follows that the equipment must be maintained by staff who do not understand its method of working in detail: they must, of course, understand or be capable of learning its operation in principle, otherwise they would be incapable of locating a fault.

2. Integrated circuits and other packaged components such as thick- and thin-film circuits cannot be repaired if they fail: they are replaced if faulty. Thus maintenance staff do not need a detailed knowledge of the internal circuitry of such devices. They must, however, know sufficient about the function of the device, its input and output voltage levels, terminating resistances etc., to be able to test it. Again, therefore, the main-

tenance man needs a general rather than a detailed knowledge of the active device.

3. Because breakdowns are rare in modern equipment, maintenance staff have little experience of tracing faults in it. When a fault does occur the maintenance man has the problem of locating the fault in an unfamiliar equipment. Thus the maintenance information must be designed to assist the rapid location of faulty areas.

Such observations prompted the B.B.C. Technical Publications Section to devote some time to experiments on the form in which maintenance information for modern equipment should be presented.

It had been known for some years that maintenance men tended to rely on-circuit diagrams and did not normally read associated text unless the diagram failed to give the required information. It was decided therefore to concentrate on diagrammatic forms of presentation

and to reduce text to a minimum. In early experimental forms of literature care was taken to ensure that the diagram and associated text could always be seen at the same time and the normal arrangement was for text and diagram to be on facing pages. This was an improvement on earlier layouts but still required readers to switch their attention from one page to the other in following the operation of a complex circuit. Each time the reader returned to the text or to the diagram he had to find his place and this was felt to be an undesirable interruption to the continuity of the story.

Use of functional diagrams

There is no need to give details of the circuitry of packaged components such as i.c.s but the function of such components must be indicated, otherwise it is impossible to follow the diagram.

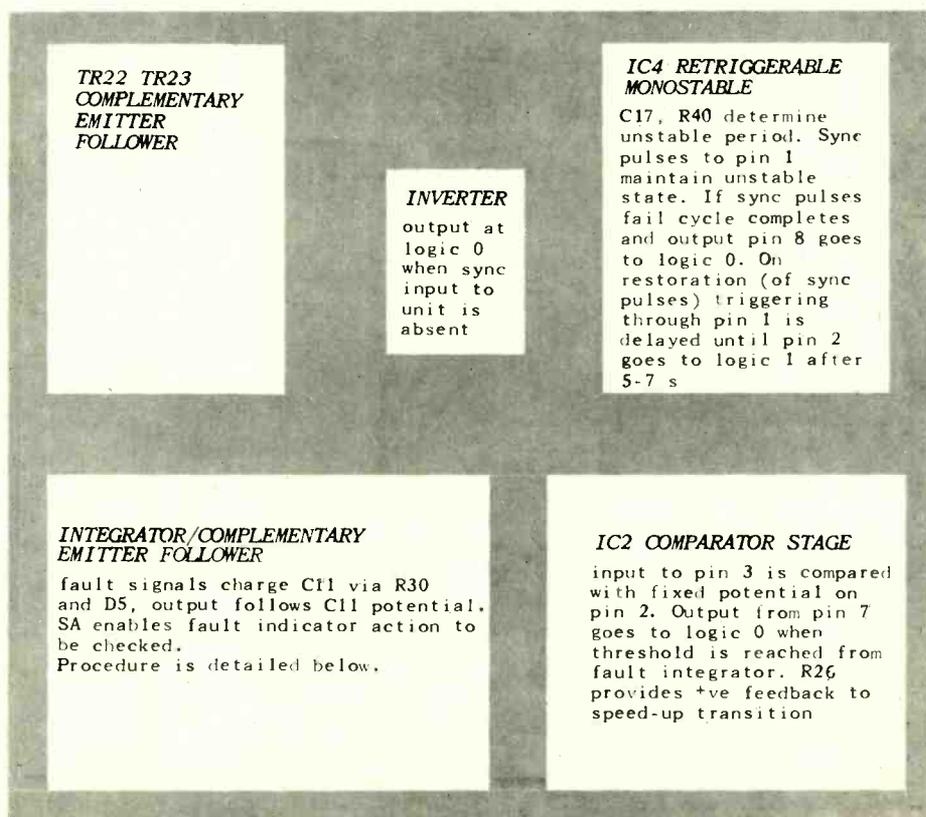


Fig. 1 Block text diagram facing circuit diagram, both divided into functional areas.

* B.B.C. Engineering Training Centre.

If the maintenance man is to be able to locate faults rapidly the diagram must show clearly the interrelationships between the stages which enable the equipment to achieve its purpose. Thus the diagram must show not only the function of i.c.s but also those of other stages using for example discrete components. The functions of many basic circuits are obvious to experienced maintenance men because the circuits are (or should be) drawn with a standard layout which helps rapid recognition. Typical of such well-known circuits (which can be regarded as electronic building bricks) are common-emitter amplifiers, emitter followers, long-tailed pairs; a number of others are given in BS 3939. Although such circuits may be familiar they must be recognized before their function can be appreciated and this takes a finite time; recognition of an unfamiliar layout takes an even longer time. Thus it was decided that all stages should be labelled with their function.

Great care is taken in arranging the functional blocks on the diagram to obtain a clear signal flow and whenever possible this is from left to right and from top to bottom of the diagram: main signal paths can be printed in heavy lines to distinguish them from subsidiary signal paths.

To define the boundaries of the functional stages these are printed on blue backgrounds (shown as white boxes in Figs. 1 and 2) so that the blue areas with the associated signal paths form a block diagram in which each block represents a mathematical or logical operation upon a signal. A light blue was chosen for the background colour

The illustrations in this article are taken from original drawings intended for reproduction on A3 size paper (approximately 16½in by 11½in) in BBC Technical Instructions. To obtain illustrations of a size suitable for publication in *Wireless World* only part of each diagram is reproduced — sufficient to show the type of presentation described in the article. The backgrounds of the functional areas in Figs. 1 and 2 are printed in blue in BBC Technical Instructions but are shown as white boxes in the article. The circuit diagram of Fig. 4 is intended for reproduction in black and the explanatory notes in red but in this article the circuit is shown in white and the notes in black.

because it does not impede reading of the circuit if this is printed on it in black. An important point about this kind of diagram is that each block represents a circuit function and not an item of hardware. It could happen, for a particular equipment, that functional and hardware boundaries coincide but in general they do not. Functional diagrams aid fault location because they illustrate the division of the equipment into functions and thus give directly the information required to test any individual stage: to permit this the diagram must include terminal numbers, pin and socket connections etc., so that the input and output connections of each stage can be found on the equipment itself.

It can be assumed that a number


of basic circuits such as common-emitter amplifiers and emitter followers are so familiar to the maintenance staff that no text is necessary to explain their behaviour. Other circuits require text and this was located, in earlier maintenance instructions, on the page facing the functional diagram. To minimize the difficulty of locating the text for a particular functional block the text was also printed on blue backgrounds of the same size as those of the functional diagram and arranged in the same layout. An example of such a pair of facing pages is given in Fig. 1. It is certainly easy to find a wanted text of a functional circuit stage but this form of presentation is still open to the objection that the maintenance man must consult two pages and must switch his attention from one to the other in following explanations of circuit behaviour. This form of presentation can also be criticized on the grounds of duplication: the breakdown of the equipment into functional areas is shown twice, one on each page. Both difficulties can be overcome by dispensing with the block text diagram and including the text within the blue areas of each functional circuit. An example of this form of presentation is given in Fig. 2: this gives the maintenance man on one side of a piece of paper most of the information he is likely to require on the particular part of the circuit featured.

Levels of treatment

For ease in handling, diagrams are limited in size to A3 and these are folded to A4 format for inclusion in standard folders which can be accommodated in normal-sized filing cabinets. The information which can be contained on an A3 page is limited, particularly when it is combined with text, waveforms, tables and other items of information. Thus a number of diagrams, possibly as many as 20, are required to describe a complete equipment such as one capable of generating all the standard waveforms required to line up a picture monitor.

To break-down the circuitry into 20 diagrams without destroying the continuity of the treatment requires some thought, and the technique adopted is to present the information at a number of levels. The first diagram in the service manual (level 1) is a diagram of the complete equipment divided into its major functions which are limited to about 20 which is the maximum which can be accommodated on an A3 page with ancillary text while maintaining adequate clarity of presentation. To limit the number of functions may require some of the functions in the level-1 diagram to be complex, and at this stage it may be sufficient to label a function for example as a waveform processor (without indicating how many stages it contains). Clearly a diagram as general as this cannot contain details such as i.c.s, transistors, resistors, etc.

In subsequent (level-2) diagrams these complex functions are split into simpler

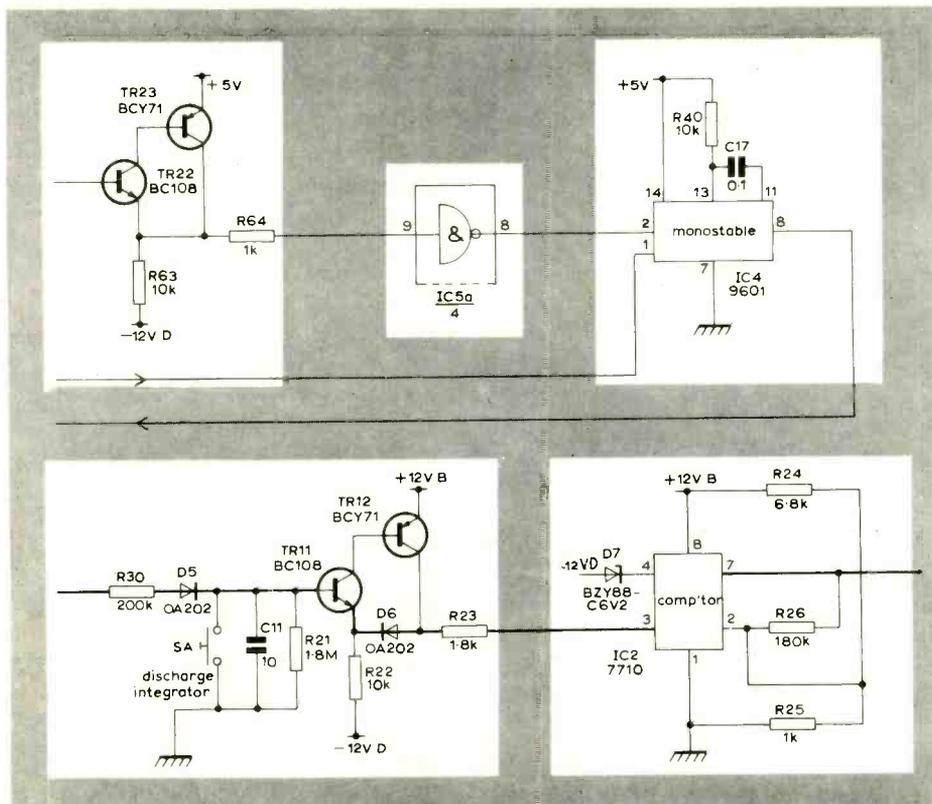

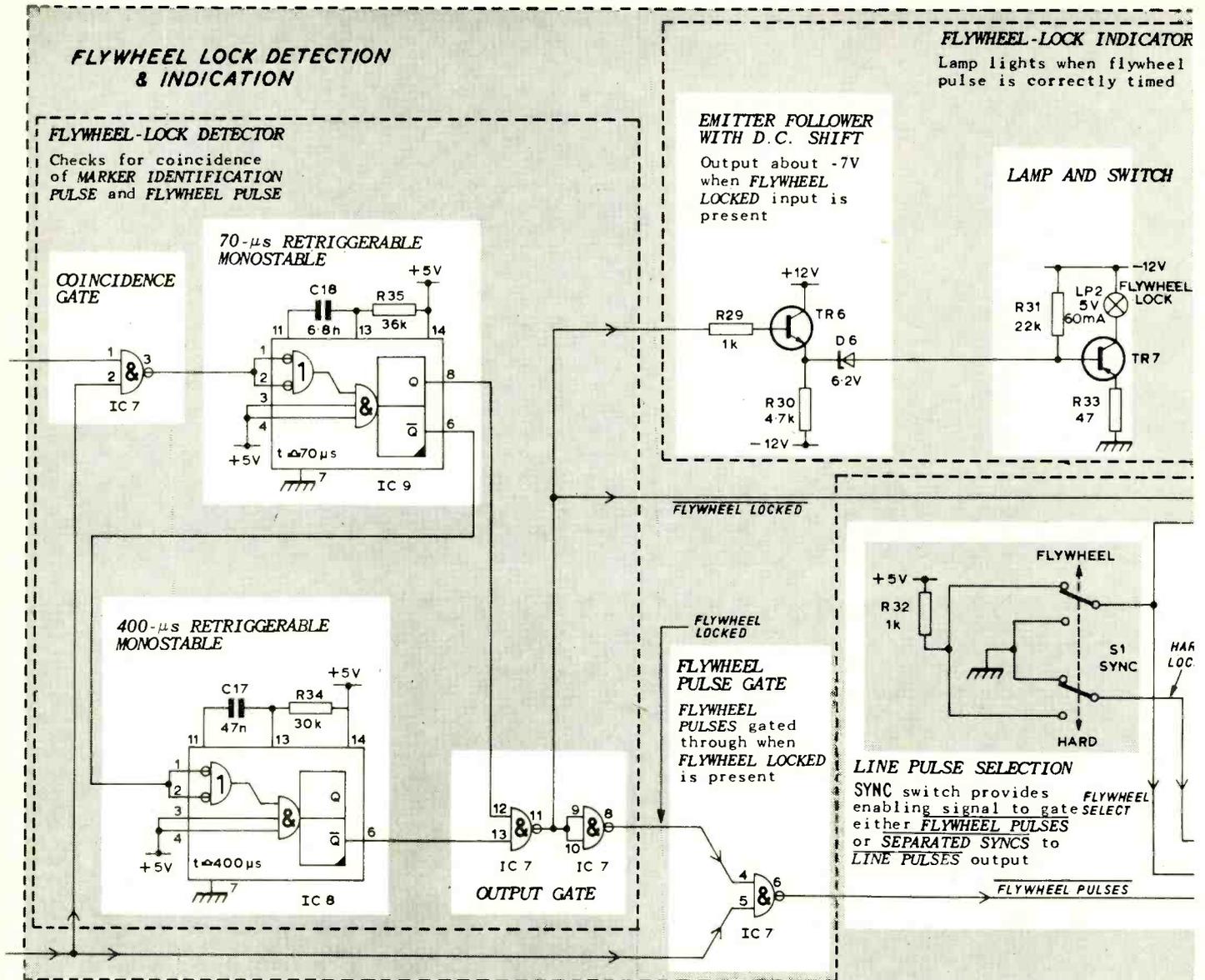


Fig. 2 Text combined with circuit diagram. Fig. 3 A waveform-text diagram.

functions, these being again chosen to keep the total number of blue blocks per page to below 20. It may be that the functions in the level-2 diagram are so simple that the circuitry can be included within the blocks without overcrowding the diagram: if not then the functions can be subdivided further to a third level at which circuit details can be included.

In all diagrams it is essential, of course, that the functional blocks should be laid out so as to emphasize the paths of signal flow.


Waveform diagrams

For certain types of equipment the circuit behaviour is best explained with the aid of waveform diagrams. If the account is given in conventional text with reference to separate waveform diagrams the explanations can become tedious. The usual method is to allocate letters to the edges and other significant features of the waveforms and to use these letters in referring to these features in the text. Such a technique has the disadvan-

tages already mentioned that the reader has to switch his attention between text and drawing. The repeated need of the reader to find his place in text and drawing is frustrating and wastes time: it can be avoided by using the technique employed in the functional circuit diagram, i.e. by condensing the text to a minimum, breaking it into sections and by inserting these sections at appropriate points in the waveform diagram (Fig. 3). There is then no need to label the waveform features because they can be identified by arrows. To distinguish it from the waveform the text is printed in a different colour.

Relay circuits

Few examples of technical writing can be so boring and repetitious as detailed descriptions of the operation of a circuit including a large number of relays. It is better to provide the information in the form of a table designed to illustrate the sequence of operations. If it is possible perhaps the best method of explaining the operation of the circuit is on the circuit

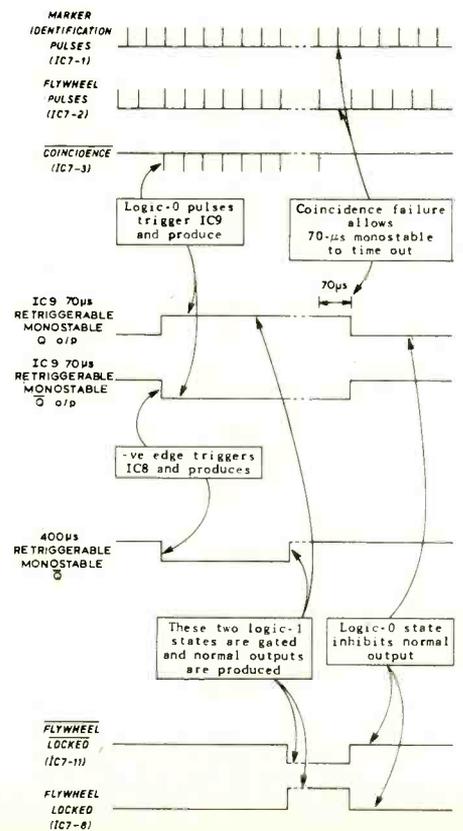

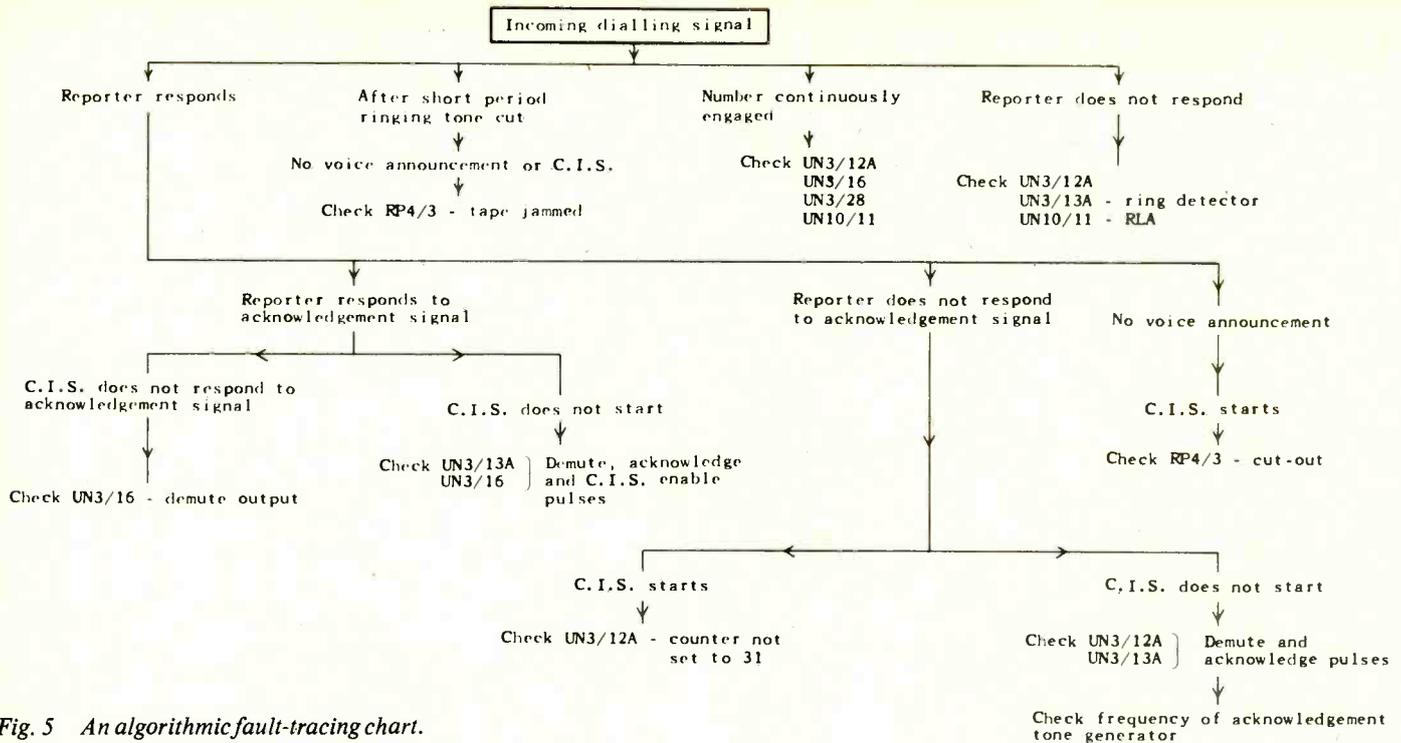


Fig. 5 An algorithmic fault-tracing chart.

provide some locational information if the terminals of transistors and the pin numbers of i.cs and of plugs and sockets are numbered. However, further information is required to enable, for example, the junction of a particular resistor and capacitor to be found physically. To this end diagrams showing the layouts of components on the printed cards are also provided and particular care is taken to identify test points on the cards.

Wiring diagrams

For equipment which consists of a number of inter-connected units it is essential, of course, to give complete information on the inter-unit wiring. This can be in the form of a diagram or a list of connections. Probably the diagram is better, particularly if it shows the units in their correct relative positions: this simplifies transfer of attention from the printed page to the equipment itself.

Parts lists

If a component is faulty it may still be recognizable and the type number may still be legible: all the information is then available to enable a replacement component to be obtained. Often, however, the faulty component has been destroyed (e.g. a resistor has burned out) or any markings on it have become illegible. The component cannot now be replaced until sufficient information on it has been obtained. The circuit diagram can supply some details, e.g. the resistance of resistors and the capacitance of capacitors, but this is often insufficient to enable a suitable replacement component to be obtained. Complete information on all components should therefore be included in the maintenance information. Equivalent components are sometimes satisfactory as replacements but there are some components for which replacements must be precisely the same type as those used originally.

Conclusion

The methods outlined in this article have been introduced into B.B.C. Technical Instructions over the last three years and are regarded by the maintenance staff as a considerable improvement over earlier methods of presenting maintenance

information. In particular the reduction in the volume of conventional text and the introduction of the functional diagrams have been welcomed. Experiments in presentation will continue but it is anticipated that changes will be confined to details in the immediate future.

Books Received

Electronic Maintenance Management contains the contributions made to the 1973 Symposium of the Society of Electronic and Radio Technicians held at the University of Nottingham earlier this year. Subjects covered range through maintenance philosophies, technical documentation and design requirements to personnel organizations and careers. Speakers at the symposium represented all sectors of the industry from large to small specialized companies. Titles of the 21 papers contained in the proceedings include — Education and Training for Maintenance Management, The Economics of Servicing, Training in Fault Diagnostic Techniques, The Effect of Service on Design, The Use of Algorithmic Fault Finding Guides, The Maintenance Task on Commercial Computers — A Different Approach, and The Need for a Standard Format of Maintenance Data for Electronic Equipment. Price £5 (incl. p & p). Pp. 189 plus unpaginated papers (3). Society of Electronic and Radio Technicians, Faraday House, 8-10 Charing Cross Road, London WC2H 0HP.

Search the Solar System by James Strong discusses the future role of unmanned inter-planetary probes. Emphasis has now been placed on the continued exploration of the Solar System by probes similar to the "Mariner" reconnaissance of Mars and Venus and the "Pioneer" probe now on its way to Jupiter. Because every planet presents a fresh set of problems, various types of space probe will be necessary. Some will be purely reconnaissance orbiters while others will soft-land sophisticated

capsules that will search for evidence of life on the surface by remote control. The author discusses ways of exploring hot planets, like Venus and Mercury, and how fast- or slow-moving comets can be intercepted. He also describes how to control a television-guided mobile probe, special balloon probes and radar satellites, how to explore the rings of Saturn, and describes a new way of maintaining continuous radio communication between Earth and a planetary surface anywhere in the Solar System. The book also describes the latest techniques for sending fast probes to the Outer Planets and a "kamikaze" probe to take close-up pictures of the Sun. Price £3.25. Pp. 160. David & Charles (Holdings) Ltd, South Devon House, Newton Abbot, Devon.

Included in recent additions to the list of books in the Foulsham-Tab series and published by W. Foulsham & Co. Ltd, Yeovil Road, Slough, SL1 4JH are:

- Radio Control Manual — Systems Circuits and Construction** by Edward L. Safford. Price £1.25. Pp.190.
- Audio Systems Handbook** by Norman H. Crowhurst. Price £1.25. Pp.189.
- New IC FET Principles & Projects** by K.W. Sessions and D. Tuite. Price £1.10. Pp.160.
- Simple Transistor Projects for Hobbyists and Students** by Larry Steckler. Price £1.25. Pp.192.
- Video Tape Production & Communication Techniques** by Joel L. Efrein. Price £1.30. Pp.252.


Circuit Ideas

Avoiding power supply hum

Units such as a radio tuner or tape recorder feeding into an amplifier normally require their own separate power supplies, though it is often more convenient if such feeders, with their relatively small requirements, could take their supplies from the amplifier itself. This cannot be achieved without the earth line between feeder and amplifier being shared by both the power supply and the signal. The result of this arrangement is considerable hum due to positive feedback.


This can be relatively easily overcome. The power supply used by the amplifier will almost certainly be of higher voltage than that needed by the feeder, and thus a "potentiometer" can be used to reduce the voltage. If this consists of a constant-current source in series with a constant-voltage sink, and is close up against the feeder, then feedback is eliminated as there will be no current fluctuations in the power supply line.

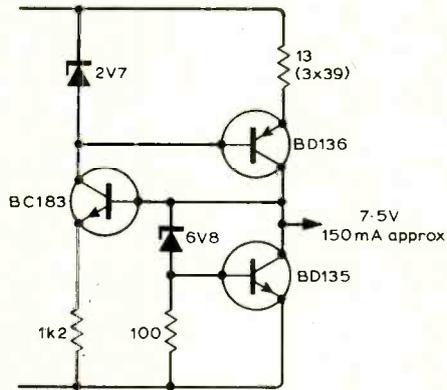The first circuit (left) provides power for a small cassette recorder. It supplies up to 150mA at 7.5 volts from supplies varying from 12 to 24 volts, and gives completely hum-free service.



In the more difficult case of a high-quality tuner (e.g. Nelson-Jones), together with stereo decoder, the second circuit has been used with similar success, even at the end of eight feet of cable.

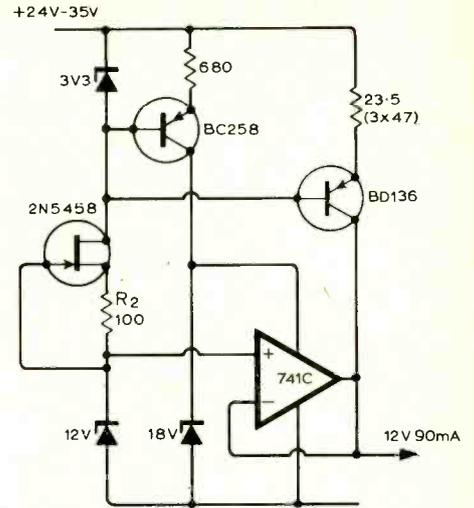With its exceedingly low output impedance, this circuit not only eliminates all likely sources of feedback, but also provides the high degree of smoothing required by this tuner.




With the values shown the constant-current supplied is about 100mA of which 10 to 15mA are "sunk" by the 741. The circuit requires careful setting up as the current that can be sunk is severely limited. Coarse adjustment of the current source is achieved by altering R_1 , the BD136 emitter resistor, fine adjustment by R_2 .

Giles Hibbert,
Blackfriars,
Oxford.

Resistance-to-voltage converter has low output impedance

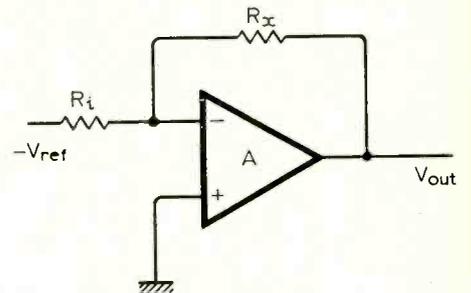Driving a constant current through an unknown resistance R_x yields a voltage across it proportional to the unknown's value. This commonly used method provides a linear conversion function, but the



signal source has an output resistance equal to R_x . Better drive capability is available by using an operational amplifier in the inverting configuration, resulting in closed loop gains of $-R_x/R_i$ when the unknown value functions as the feedback resistor. Constant input V_{ref} then results in output voltage directly proportional to the resistance value and a power of ten scaling factor selected by proper choice of R_i and V_{ref} . Output voltage from the amplifier has a very low source resistance, which approaches zero as R_i is set at higher values and loop gain decreases.

David R. Schaller,
Milwaukee,
Wisconsin.

Symmetrical power supply


Shown is a simple power supply having symmetrical outputs and overload protection such that if a heavy load or short circuit is applied to either output both switch off rapidly. Each transistor derives its forward bias from the opposite supply rail and while the transistors are in saturation an increasing load will cause the output to fall under the regulation of the transformer. With a further increase in load the transistors come out of saturation and eventually remove each other's forward bias. If the trip circuit

is used with an active power supply having negligible output resistance then switch off occurs solely to the transistors coming out of saturation. The zener voltage must be between V_o and $2V_o$ and the value of R

$$\leq \frac{h_{FE}(2V_o - V_Z - 0.7)}{I_L}$$

where I_L is the maximum load current required.

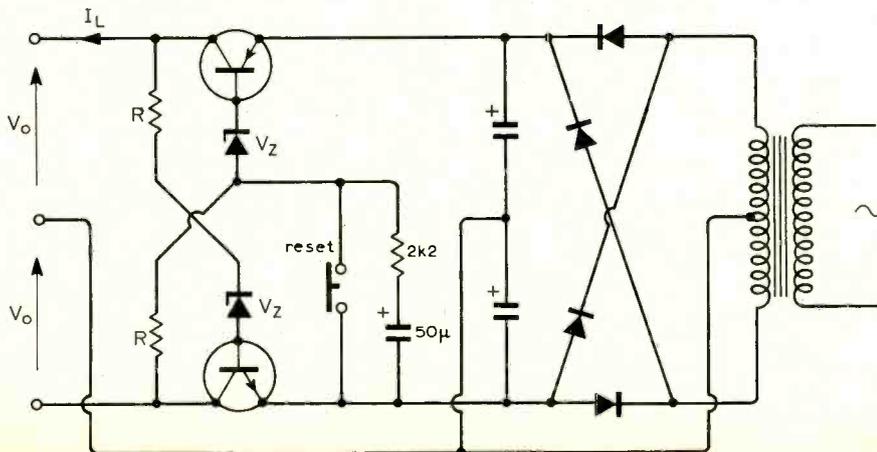L. D. Thomas,
Post Office Research Department.



World of Amateur Radio

Should there be a U.K. novice licence?

The U.K. is one of the very few countries with a large amateur population (total of Class A and B licences has just passed the 18,000 mark) that eschews "incentive licensing" and any form of novice or beginner's licence. Once anyone has qualified for a Class A or B licence no restrictions are placed on their activities or whether this includes any element of "self-training". As an individualist such freedom from official pressures seems wholly admirable — but as one concerned with the future development of the hobby this absence of incentives seems puzzling. A British "beginner's licence" was announced in March 1968 but did not appear to be part of any fully thought-out scheme and was never implemented.

One of the latest countries to introduce such a system is Norway where a new novice-type Class B licence is now being issued. This is valid for two years only and is not renewable, is for c.w. operation with a maximum input of 15 watts and has the prefix LB to distinguish these stations from the Norwegian Class A stations which use the LA prefix. Such facilities encourage newcomers to become proficient in Morse operation by learning while using. Should the U.K. look again at this now well tried system of encouraging newcomers to become experienced in h.f. Morse operation? Or is it accepted that the day of the Morse key is now almost done?

Communications receivers now 40 years old

Although it could be argued that "communications receivers" are as old as radio, the type of receiver which this term usually defines really emerged in the early thirties with the coming of low-noise single-signal-superhets. A major step forward came in 1931 when James Lamb of A.R.R.L. showed how the crystal i.f. filter — developed in the U.K. by Dr J. Robinson in 1929 for his broadcast "stenode" receiver — could be put to extremely good use for amateur operation. One of the first receivers using such a filter and intended for amateurs was the National FBXA of 1934 — and

this was a later version of the FB7 receiver of 1933, regarded by some amateur historians as perhaps the first true "communications receiver". During the next five years a whole string of such receivers appeared and pushed aside the "straight" regenerative receivers: the HRO Senior in 1936; the Hammarlund Comet Pro and Super Pro; the RME69; the Tobe Deutschmann kit; the wide range of Hallicrafters from the £7 Sky Buddy to more advanced sets with crystal filters. At about the time when such receivers began appearing on the British market in 1936-37, the only home product was possibly the £20 Evrizon single-signal-superhet. A sign of the change was the use by the leading British station of the 1936 BERU contest of a Comet Pro — but the Australian winner still used a straight 0-v-2 receiver. Because of their widespread wartime use, the HRO and the slightly later RCA AR88 (first marketed in 1940-41) remain as outstanding examples of the early days of communications receivers: in how many other branches of electronics can equipment built over 30 years ago still prove capable of performing well even in comparison with modern equipment?

Coming Soon

The second Midland National Amateur Radio & Electronics Exhibition at Granby Halls, Leicester on October 25-27 will feature a fully equipped amateur station, GB3ARE, plus a reproduction of the 1913 club station of the Derby and District society. A film theatre will show films of interest to amateurs and a Tombola stand is being run on behalf of the Radio Amateur's Invalid & Bedfast Club. Trade stands look like being fully booked.

One of the very popular Racal Amateur Radio Club Junk Sales — at which an unusually wide range of ex-professional equipment usually changes hands — is being held at St Sebastian's Hall, Nine Mile Ride, Crowthorne, Berkshire on Saturday, October 27 at 2 p.m.

The South East Counties H.F. Convention on Sunday, November 18 from 11 a.m. until 7 p.m. at the Airport Hotel, Crawley, Sussex, will include trade stands, club stands, informal lectures and an operational station.

A dinner for direction-finding enthusiasts which it is hoped will be the first of an annual event is to be held at "The Chicken in the Basket", Benson, between Oxford and Wallingford on Friday, November 16.

More courses for would-be amateurs

Additions to last month's list of places where evening courses are being run for would-be amateurs — based on information supplied by the R.S.G.B. — include:

London and the Home Counties: Acton, Bedford, Borehamwood, Brentwood, Chingford, Croydon, Harlow, Harrow, Highgate, Ilford, Islington, Princes Risborough.

Provinces: Aldridge, Staffs, Bangor, Co. Down, Birkenhead, Bridgend, Glam. Brighton, Bury, Chesterfield, Glasgow, Grantham, Grimsby, Loughborough, Newport, Mon., Oldham, Perth, Plymouth, Portsmouth, Stoke-on-Trent, Wolverton and Wombourne (near Wolverhampton).

In Brief

A recent BBC Radio 4 programme ("In Touch") for visually handicapped listeners included an explanation and taped demonstrations of amateur radio operation by Philip Storey, G3ZGG. He said there are now about 50 blind amateurs in the U.K. and advised those interested to gain experience by listening on a communications receiver; where necessary assistance may be obtained from the Radio Amateur Invalid & Bedfast Club (Hon. Secretary Mrs Frances Woolley, G3LWY, Woodclose, Penselwood, Wincanton, Somerset) . . . What is thought to be the longest-distance contact ever made on "Top Band" (1.8MHz) was made last July between Tokuro Matsumoto, JA7AO and VP8KF on the Falkland Islands. The Japanese amateur has also contacted Fred Laun, LU5HFI (formerly HS5ABD) in Cordoba, Argentina . . . The Harlow and District Mobile Rally is to be held at Netteswell Comprehensive School, Harlow, on Sunday, September 23 (talk-in stations on 144, 3.5 and 1.8MHz) . . . The prefix DT is being used by some DM stations until the end of the year to mark the 20th anniversary of amateur licensing in the German Democratic Republic . . . Walter Turner, GW3YPH, of Pontypridd was electrocuted while putting up an aerial in his back garden not far from an overhead electric cable . . . By the end of August, Oscar 6 has completed 4000 orbits. British and French amateurs have made contact through Oscar 6 with KL7MF at Anchorage, Alaska, at distances of over 7000 km. F9FT in Reims has made more than 2500 contacts through the amateur satellite.

PAT HAWKER, G3VA

Some TV tubes take a terrible bashing.



... but this one* beats the lot. Because even when a young child took a hammer to it it didn't implode. It didn't even crack.

There you have remarkable proof of the exceptional safety of Mazda tubes, safety based on the exclusive Rimguard construction technique. And there is further proof in the fact that seven different sizes of Mazda monochrome tubes have now received BSI approval for implosion protection to BS415 (1972) Clause 18. You'll see special labels indicating BSI certification on the back of the tubes. No tube could have a better backing.

For Mazda give top priority to the safety of your customers. And that could have a very important effect on your business.

So the question is:

Are your replacement tubes as safe as Mazda?

** Tube returned by Midland Rentals, Sheffield.*

Thorn Radio Valves and Tubes Limited
Mollison Avenue, Brimsdown, Enfield,
Middlesex EN3 7NS. Tel: 01-804 1201.



WW-091 FOR FURTHER DETAILS

The Sinclair Cambridge... no other calculator is so powerful and so compact.

Complete kit- £24.95!

(PLUS VAT)

The Cambridge – new from Sinclair

The Cambridge is a new electronic calculator from Sinclair, Europe's largest calculator manufacturer. It offers the power to handle the most complex calculations, in a compact, reliable package. No other calculator can approach the specification below at anything like the price – and by building it yourself you can save a further £5.50!

Truly pocket-sized


With all its calculating capability, the Cambridge still measures just $4\frac{1}{2}'' \times 2'' \times \frac{11}{16}''$. That means you can carry the Cambridge wherever you go without inconvenience – it fits in your pocket with barely a bulge. It runs on U16-type batteries which gives weeks of life before replacement.

Easy to assemble

All parts are supplied – all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our service department will back you throughout if you've any queries or problems.

The cost? Just £27.45!

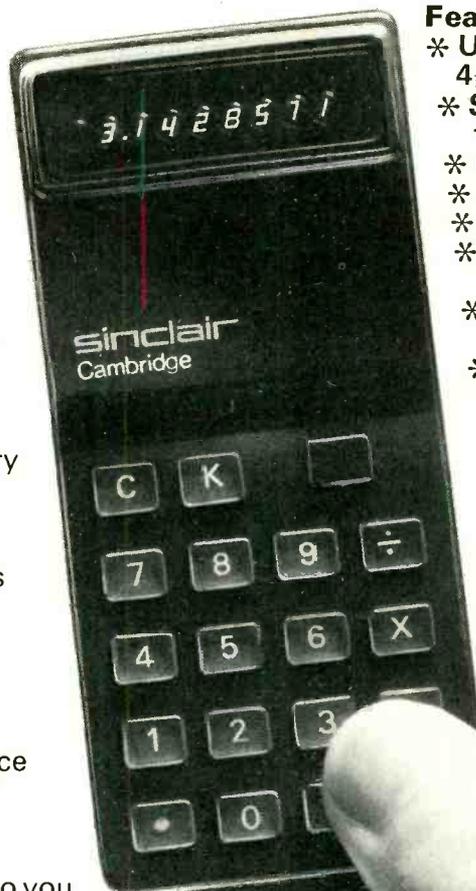The Sinclair Cambridge kit is supplied to you direct from the manufacturer. Ready assembled, it costs £32.95 – so you're saving £5.50! Of course we'll be happy to supply you with one ready-assembled if you prefer – it's still far and away the best calculator value on the market.



Features of the Sinclair Cambridge

- * Uniquely handy package. $4\frac{1}{2}'' \times 2'' \times \frac{11}{16}''$, weight $3\frac{1}{2}$ oz.
- * Standard keyboard. All you need for complex calculations.
- * Clear-last-entry feature.
- * Fully-floating decimal point.
- * Algebraic logic.
- * Four operators (+, -, x, ÷), with constant on all four.
- * Constant acts as last entry in a calculation.
- * Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £30.
- * Calculates to 8 significant digits, with exponent range from 10^{-20} to 10^{79} .
- * Clear, bright 8-digit display.
- * Operates for weeks on four U16-type batteries. (MN 2400 recommended).

A complete kit!

The kit comes to you packaged in a heavy-duty polystyrene container. It contains all you need to assemble your Sinclair Cambridge. Assembly time is about 3 hours.

Contents :

1. Coil.
2. Large-scale integrated circuit.
3. Interface chip.
4. Thick-film resistor pack.
5. Case mouldings, with buttons, window and light-up display in position.
6. Printed circuit board.
7. Keyboard panel.
8. Electronic components pack (diodes, resistors, capacitors, transistor).
9. Battery clips and on/off switch.
10. Soft wallet.



Actual size!




4½in long x 2in wide x 1¼in deep

This valuable book – free!

If you just use your Sinclair Cambridge for routine arithmetic – for shopping, conversions, percentages, accounting, tallying, and so on – then you'll get more than your money's worth.

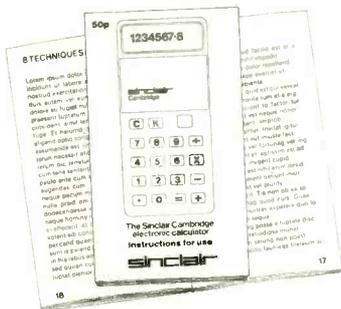But if you want to get even more out of it, you can go one step further and learn how to unlock the full potential of this piece of electronic technology.



How? It's all explained in this unique booklet, written by a leading calculator design consultant. In its fact-packed 32 pages it explains, step by step, how you can use the Sinclair Cambridge to carry out complex calculations like:

- Logs Tangents Currency conversion
- Sines Reciprocals Compound interest
- Cosines nth roots and many others...

sinclair

Sinclair Radionics Ltd, London Road, St Ives, Hunts.
Reg. no: 699483 England VAT Reg. no: 213 8170 88

Why only Sinclair can make you this offer

The reason's simple: only Sinclair – Europe's largest electronic calculator manufacturer – have the necessary combination of skills and scale.

Sinclair Radionics are the makers of the Executive – the smallest electronic calculator in the world. In spite of being one of the more expensive of the small calculators, it was a runaway best-seller. The experience gained on the Executive has enabled us to design and produce the Cambridge at this remarkably low price.

But that in itself wouldn't be enough. Sinclair also have a very long experience of producing and marketing electronic kits. You may have used one, and you've almost certainly heard of them – the Sinclair Project 60 stereo modules.

It seemed only logical to combine the knowledge of do-it-yourself kits with the knowledge of small calculator technology.

And you benefit!

Take advantage of this money-back, no-risks offer today

The Sinclair Cambridge is fully guaranteed. Return your kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee a correctly-assembled calculator for one year.

Simply fill in the preferential order form below and slip it in the post today.

Price in kit form: £24.95 + £2.50 VAT. (Total: £27.45)

Price fully built: £29.95 + £3.00 VAT. (Total: £32.95)

To: Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire, PE17 4HJ

Please send me

a Sinclair Cambridge calculator kit at
£24.95 + £2.50 VAT (Total: £27.45)

a Sinclair Cambridge calculator ready built
at £29.95 + £3.00 VAT (Total: £32.95)

*I enclose cheque for £ _____, made
out to Sinclair Radionics Ltd, and crossed.

*Please debit my *Barclaycard/Access
account. Account number _____

*Delete as required.

Name _____

Address _____

PLEASE PRINT

FWW-092 FOR FURTHER DETAILS

Co-axial Cable Problems? RG/U UNI RADIO WALMORE have the answer




Walmore Electronics Ltd.,
11-15, Betterton Street, Drury Lane, London WC2H 9BS Telephone 01-836 0201 Telex London 28752



WW—093 FOR FURTHER DETAILS

We're sensitive to everyone's needs.

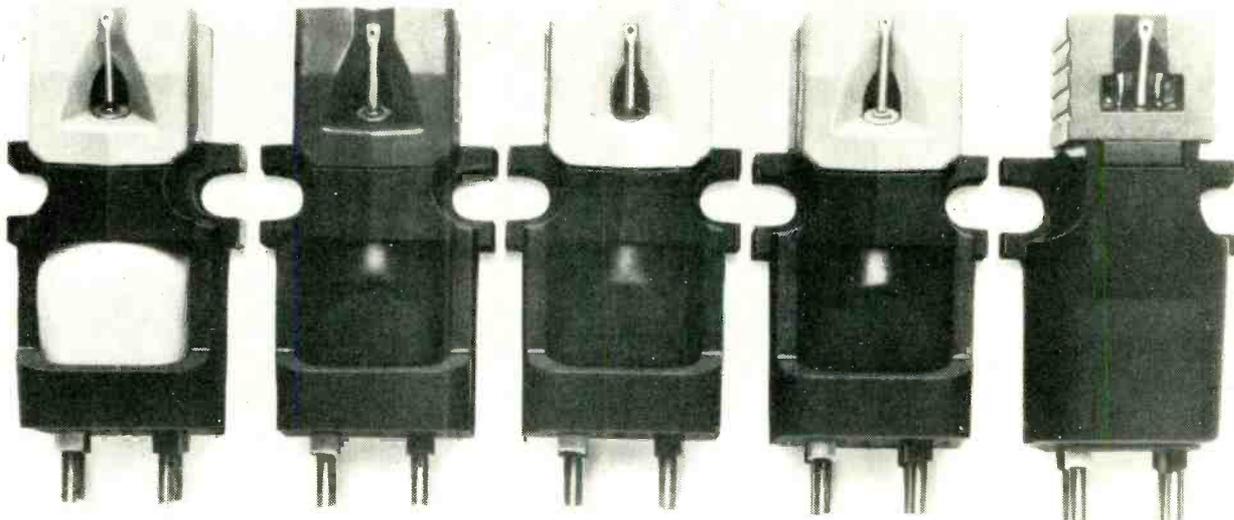

Different people have very different requirements in Hi-Fi, so Goldring developed a comprehensive range of stereo magnetic cartridges that are superb in performance and realistic in price.

From the G800 Super E for those who seek perfection down to the G850 for systems on a budget, the Goldring range offers unsurpassed quality and value.

Your request will bring full details of these and other Goldring products.

Goldring Limited,
10 Bayford Street, Hackney, London E8 3SE.
Tel: 01-985 1152.

Goldring Series 800

Stereo Magnetic Cartridges.

WW—094 FOR FURTHER DETAILS

New Products

Two-tone generator

Racal Instruments have introduced a two-tone generator, Model 9063, which complements the r.f. synthesized signal generator system introduced earlier this year. Designed primarily as a modulation source, the 9063 provides an aid to s.s.b. servicing and alignment.

An entirely self-contained instrument covering the 10Hz to 100kHz frequency range, the 9063 provides a stable synthesized tone referenced to an internal crystal standard and a second tone derived from a tuneable oscillator. The two tones may be used independently or combined, the intermodulation distortion being less than -70dB . Fully remotely programmable using t.t.l. logic, the instrument provides outputs from $100\mu\text{V}$ to 10V with low hum and spurious content. The 9063 is 88mm (3.5in) high, 483mm (19in) wide and 406mm (16in) deep and weighs 13.7kg (30lbs). Racal Instruments Ltd, Duke Street, Windsor, Berks SL4 1SB.

WW 316 for further details

50MHz portable oscilloscope

The dual-trace oscilloscope, model D75 from Telequipment is a light-weight portable oscilloscope with a vertical sensitivity of 5mV/div. on both channels over the full 50MHz bandwidth. The sensitivity can be increased to 1mV/div. at all frequencies up to 15MHz by the operation of the $\times 5$ gain switch. Both vertical channels can be used independently or in alternate, chopped, added or differential modes, and the vertical signal delay which

is incorporated allows the leading edges of signals to be observed.


The horizontal deflection system consists of a dual timebase which provides normal sweep, mixed sweep, sweep intensifying, sweep delaying and single shot facilities. The fastest normal sweep speed of 100ns/div. can be increased to 10ns/div. by switching on the $\times 10$ sweep magnifier. Time measuring accuracy is $\pm 3\%$ with the magnifier off, $\pm 6\%$ with the magnifier on. A useful extra feature is the "trace locate" button which reduces vertical and horizontal deflection so as to present an on-screen display and free runs the main timebase.

A built-in calibrator provides square wave test outputs on the front panel of 30mV, 300mV and 3mA peak-to-peak with an accuracy of $\pm 1\%$ at a nominal frequency of 1kHz. The c.r.t. is a single-gun mesh tube, operating at a potential of 15kV. The U.K. list price of the D75 is £420 excluding v.a.t. The weight is 25.5lb and the dimensions are $5\frac{3}{8}\text{in}$ high, 15in wide, and $18\frac{3}{4}\text{in}$ deep. Tektronix U.K. Ltd, Beaverton House, P.O. Box 69, Harpenden, Herts.

WW307 for further details

Metal detector

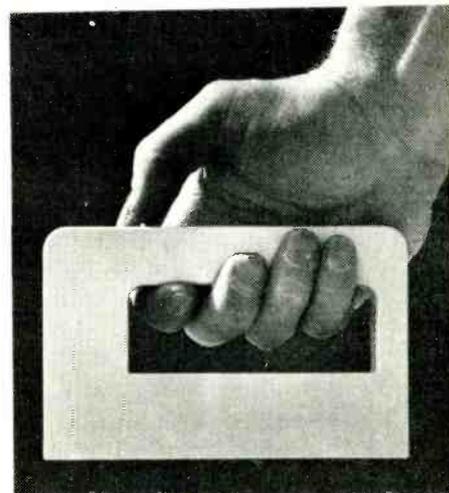The Contil-Voll metal detective, marketed by West Hyde Developments, is pocket size, hand held, very light (under $\frac{1}{2}\text{lb}$) and so easy to operate that a child can use it. It is held in either hand and a small knurled knob is turned by the thumb until a red indicator light



goes out. It is then ready for use: any nearby metal turns the light on again. The Contil-Voll metal detective reacts to all metals and finds them through any other substance. To quote West Hyde, "just think of the possibilities; this means the metal clip on your pen through your jacket; the money in your pocket; a gun in your belt! It will find a paper staple at $\frac{1}{2}\text{in}$ and a paper clip buried under a pile of papers 2in thick. But think of the practical possibilities in a factory or at home!" Made in tough impact-proof plastic and using a single 9V battery as the power source, it is priced at £22.85 plus v.a.t. West Hyde Developments Ltd., Ryefield Crescent, Northwood Hills, Northwood, Middx HA6 1NN.


WW308 for further details

Electronic watches

Solidev Ltd announce a range of solid quartz controlled electronic watches. They have no hands and no dials. Instead, a simple black face registers time and date by l.e.d. display. Control is by push button.

There are several models available in both men's and ladies' styles. All feature gold bracelets. All are accurate to within 1 digit over the course of a year, and cost £180 r.r.p. Solidev Ltd, Edison Road, Elms Industrial Estate, Bedford MK41 0HG.


WW 319 for further details

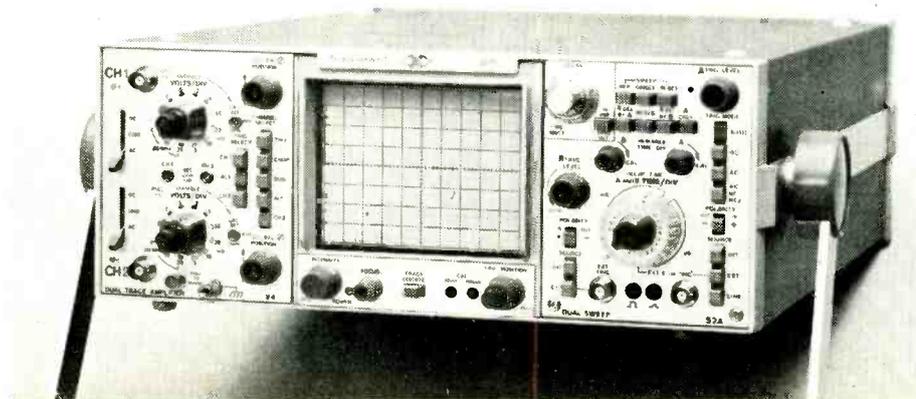

Trip amplifiers

Rotraco Systems Ltd have developed a range of trip amplifiers which are compatible with their Model 4 and 4R monitoring and alarm systems. The trip amplifiers are intended for operation from signal sources providing 0-2.5V, 4-20mA, or direct from thermocouples, resistance thermometers, thermistors, strain gauge pressure transducers, tachometers etc. They can be combined with alarms to provide alarm and trip systems for plant and process control applications. Facilities are also provided for an indication of temperature, pressure etc. either on a common indicator or individual indicators. The indicator unit can also be used to inject a signal to check the trip setting.

The basic trip amplifiers carry two trip channels with controls for set point and differential but other versions are available e.g. one channel with two trip settings, switch selection of trip high or low, fixed differential etc. A light emitting diode indicates whether or not a channel has tripped. The setting and differential potentiometers of temperature trip amplifiers are calibrated directly in degrees centigrade and for other parameters they

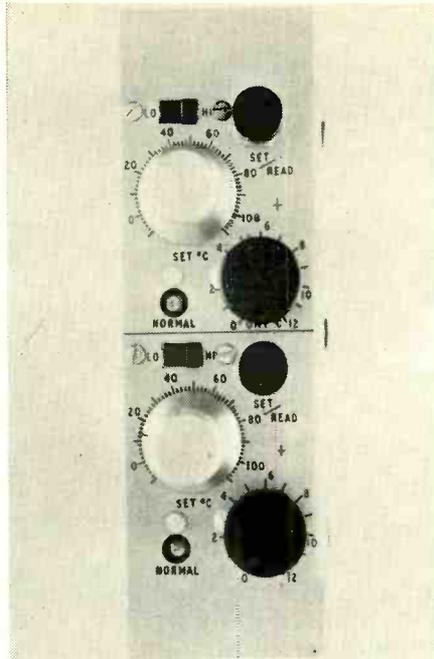

are calibrated in percentage. Rotraco Systems Ltd, Garden Street, Darlington, Co. Durham DL1 1QR.
WW 314 for further details

Liquid level control units

The ELC2 electronic level control produced by Gearing & Watson (Electronics), is used to control the level of liquids where the conductivity varies with level, such as water, milk, sewage etc. Two level probes may be used, so that the level is controlled between the two probes; for example a container may be filled to the upper level probe but the level may fall to the lower probe before the control operates to restore the level to the upper probe again. The ELC2 is designed for "fill" applications, the ELC24 is available with a reverse action.

The ELC2 uses modern semiconductor technology, the level comparator being an integrated circuit, while the load switch is a triac; thus no contact maintenance is required. The probe circuit is insulated by a double wound mains transformer from the supply for complete safety. The unit is encapsulated for protection and can operate in high ambient temperatures. Electrical connections are by "Faston" connectors. Dimensions 63.5 × 51 × 108mm. Gearing & Watson (Electronics) Ltd, Birch Close, Eastbourne, Sussex BN23 6PE.


WW306 for further details

Logic analyzer

Logic circuit analysis by the "freezing" and display of the states of any 32 bits in a stream is the function of a new instrument by Hewlett-Packard, the Model 5000A. A light-emitting diode array indicates the "up" or "down" states of the 32 selected bits, which are selectable by thumbwheel switches from a stream of information in relation to a trigger signal (before it as well as after). A fault con-

dition can be made to trigger the display. The instrument will cope with clock frequencies up to 10MHz and is compatible with all logic families. L.e.d.s display the state of the input signal, and if the probe is not making contact, the fact is again indicated by l.e.d. Hewlett-Packard Ltd, 224 Bath Road, Slough, Bucks SL1 4DS.

WW305 for further details

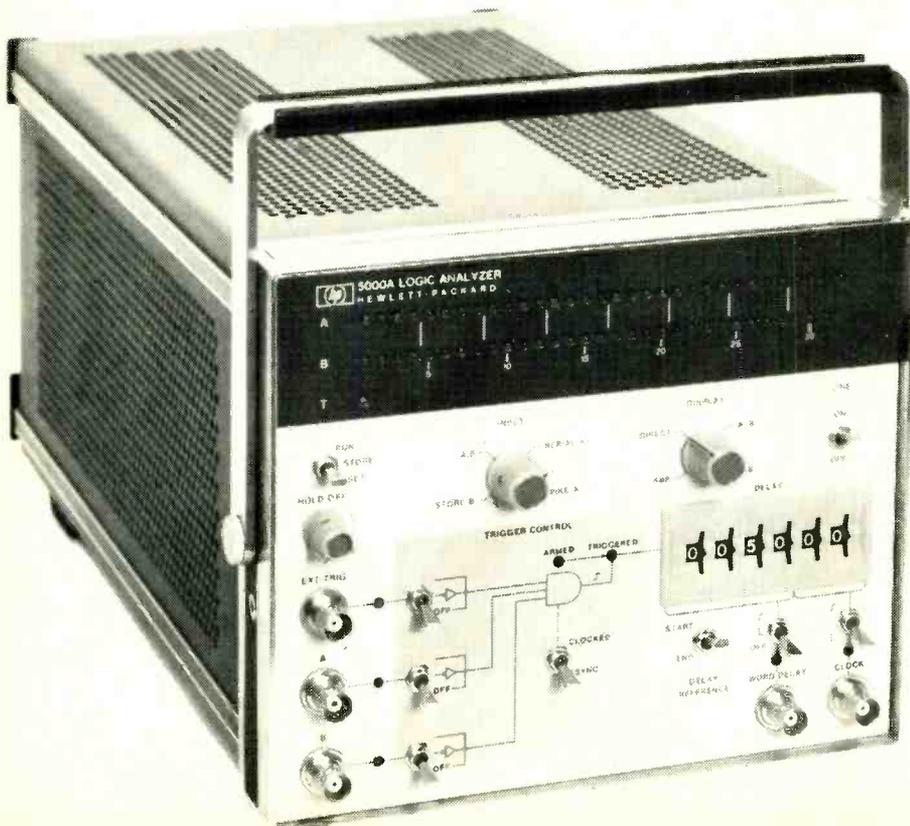

Glass miniature trimmers

Voltronics are now manufacturing a range of glass dielectric trimmers up to 40pF capacitance, but 40 per cent shorter in length than the standard MIL-C 14409C capacitor. Two mounting styles, for vertical or horizontal mounting, are available. Both are sealed, providing protection against pressures up to 40 p.s.i. to keep out dust, moisture and encapsulents. The non-rotating piston construction permits more linear tuning, no capacitance reversals, high Q, longer life, low constant inductance and a high self-resonant frequency. Suvicon Ltd, Hagley House, Hagley Road, Birmingham B16 8QW.

WW304 for further details

Hall effect d.c. motors

Communication Technology have announced a range of constant speed brushless d.c. motors for instrumentation and recorder applications. Incorporating Hall effect elements to control the coil current by sensing the rotor position, the PHM series can be programmed to operate at selected motor speeds or for reverse rotation. By the addition of an external switching circuit, multi-speed operation and forward or reverse rotation can be arranged without the need to use a separate gear box for this purpose.

The rotator is external to the fixed coils and as there are no brushes or a commutator, as in a conventional d.c. motor, friction is greatly reduced and

no electrical noise is generated. The use of special copper sleeve bearings is said to ensure a minimum of motor noise and long life. Communication Technology Ltd, 279 Addiscombe Road, Croydon, CRO 7HY.

WW303 for further details

Audio mixers

Neltronic (UK) Ltd is to enter the audio market with a range of audio mixers, with full mixing input channels and frequency response 20Hz to 20kHz. In size and sophistication the range covers many requirements but units can be designed specially to fulfil customers' needs. The equipment is made in the UK, to a design which employs up-to-date technology and components to bring the price of the standard unit, model 6/2, to under £900. For the standard unit, the mixer features switching for one microphone and one line input, a sensitivity -80 to ± 10 dB in 10dB steps, filters covering low, mid and high frequencies and horizontal faders. Cueing to internal speaker from all channels and all outputs is available with independent reverberation, selectable mix, 2 reverberation units for stereo operation, switchable to main output, a fold-back output for mixed signals and a p.u. unit with R.I.A.A. equalization. Two v.u. meters switchable to every channel and all outputs; pan between 1 and 2 on every channel. Outputs 2 group, 2 fold-back, 2 reverberation and one monitor. Neltronic (UK) Ltd, 442 Bath Road, Slough SL1 6BB, Bucks.

WW302 for further details

Noise generator cards

Manufactured by Elenco, Inc., U.S.A., specialists in noise generators, the Series 3600 noise generator cards cover the range of 10Hz to 5MHz with an output level of 3V r.m.s. open circuit. A dynamic range of 3.5:1 peak to r.m.s. is provided. Output impedance is 600Ω or 200Ω depending on the upper frequency specification, with other output impedances optionally available. The amplitude probability distribution is Gaussian.

Cards are available with specified uniformities of ± 0.5 dB, ± 1 dB, ± 2 dB and ± 3 dB for many frequency ranges between lower frequencies of 10Hz, 20Hz, 50Hz, 200Hz and 5kHz and upper frequencies of 20kHz, 50kHz, 100kHz, 200kHz, 500kHz, 1MHz, 2MHz and 5MHz. Size is $4\frac{1}{2} \times 6\frac{1}{2} \times \frac{7}{8}$ in and weight approximately 7oz. Single unit prices range from £87 to £285 (excluding duty and v.a.t.), lower prices in quantity. Lyons Instruments Ltd, Hoddesdon, Herts.

WW313 for further details


Three-pen recorder

The Model 303 "Dial-a-Span" three-pen recorder by Chessell Ltd is designed to provide good flexibility. The ranging facility is controlled by front panel thumbwheel selectors to give 450 spans per channel from 1mV to 99V plus 1999 datum shift settings permitting at least 10 times span suppression or elevation on all ranges, with a constant input impedance of $10M\Omega$.

The calibrated datum shift facility

allows 1 metre chart width resolution on a 100mm chart. Other features include high speed pen servos and 10-speed electronic chart drive. The Model 303 recorder is available in two forms: a free-standing model with integral carrying handle/tilt stand and a 19in rack mounting version. Chessell Ltd, Broadwater Trading Estate, Southdownview Road, Worthing, Sussex BN14 8NL.

WW 311 for further details

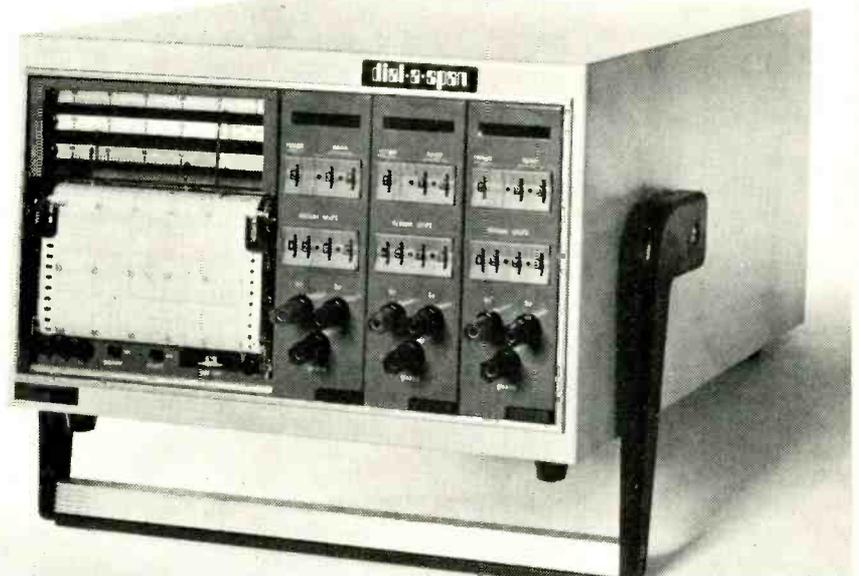

Low-cost TV system

Pye Business Communications has introduced a low-cost television system — the Philips' "Mini-Studio". Designed for educational and industrial training purposes, the equipment, constituting a basic studio, costs £1,450. The system includes two cameras with various lenses (zoom, standard microscopy), tripods, camera fixings, headsets, telecine,

mounting rack with three 10cm monitors and control unit, microphone and audio mixer with all necessary cables, stands and connections. The TV equipment can be used with either a video tape recorder (from £150) or video cassette recorder with professional facilities (from £750). Pye Business Communications Ltd, Cromwell Road, Cambridge.

WW 310 for further details



D.I.P. heat pipes

Small flat pipes for cooling flat packs and d.i.p. devices are the latest designs from Jermyn Manufacturing. Each pipe is 0.1in thick and 0.25in wide and will easily fit under d.i.p. packs. The flat surface of a d.i.p. heat pipe makes it easy to add or remove heat and due to the isothermal characteristics of heat pipes all devices will be maintained at the same temperature.

The d.i.p. heat pipes can be fabricated in matrix configurations with the heat

pipe tails terminating in a cold wall and on a 4 × 7in matrix up to 80 d.i.p. packs can be maintained within 1°C of each other.

The normal temperature of operation is 20°C to 150°C and a 6in long d.i.p. heat pipe will handle 18 watts at 100°C and with a weight of only 10g these components are suitable for airborne applications. Jermyn Manufacturing, Sevenoaks, Kent.

WW 312 for further details

Modular bench supply

Gardners Transformers have introduced a power supply system for industrial and educational laboratory applications where either a.c. or d.c. may be required at power levels up to several hundred watts. The complete power supply system comprises a basic a.c. module, ACO1, and four d.c. modules. The a.c. modules provide a continuously variable a.c. output, fully isolated, with coarse and fine controls, together with meter monitoring. There are three output ranges: up to 70V at 12A; up to 140V at 6A; and up to 280V at 3A.

The incorporated isolation transformer ensures that the user and valuable test equipment are protected against the risks associated with testing circuits connected

to mains earth. This feature, coupled with the usual flexibility of the system as a whole, should be valuable where students or inexperienced personnel are involved.


Three of the d.c. modules are rectifier-capacitor units matching the three output ranges of the a.c. module. The fourth d.c. module, which can be used in conjunction with any of the other d.c. modules, is a filter and protection unit offering very low output ripple levels in addition to full short-circuit and over-voltage protection. The complete system is housed in two instrument cases which may be used on the bench or mounted in standard 19in racks. Gardners Transformers Ltd, Christchurch, Hants.

WW309 for further details



Time delay modules

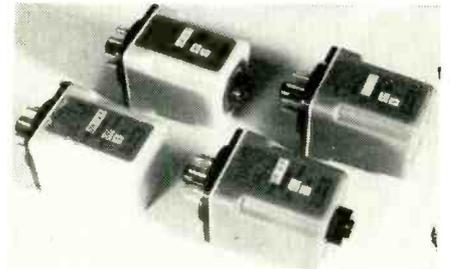The time delay modules TM and TD by Keyswitch can be supplied for a.c. or d.c. applications where timed delay periods of 2.5 to 300s are required. The units are



“non-blip”, and the delay period is set by potentiometer adjustment. This potentiometer can be included on the discrete unit, or wired from a remote situation. At the end of the set delay period (which is initiated by connection of the supply) the timer will deliver an output.


The TM timer incorporates a Keyswitch MS relay with changeover contacts rated at 2A. The TD version is designed for use with an external relay, and at the end of the timed interval the TD timer output is supplied via an integral s.c.r. circuit. The solid state switch rating is 300V, 10-800mA.

Both timers have 120ms reset time, and are supplied in polypropylene casings 1.3in (33mm) wide × 1.2in (33mm) deep, overall height above socket 2.025in (51mm). Gothic Electronic Components, Beacon House, Hampton Street, Birmingham 19.

WW 315 for further details

Ceramic filters

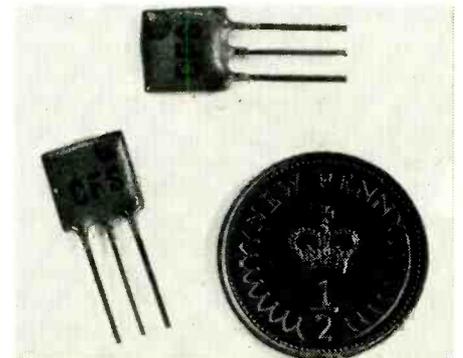10.7MHz centre frequency ceramic filters, type CFS 107M, are offered by Toko (UK) Ltd. The five ranges available have centre frequencies between 10.64 and 10.76MHz, each with an accuracy of ±300kHz at 3dB and ±600kHz at 20dB. Insertion loss is not more than 6dB, and impedance 330Ω ±15%.



The performance parameters are closely specified, and include a centre frequency shift within ±150 p.p.m. per °C in the temperature range -10 to +60°C.

Delivery times are short and prices competitive for these type CFS 107M ceramic filters claim the suppliers, Toko (UK) Ltd, Shirley Lodge, 470 London Road, Slough, Bucks SL3 8QY.

WW301 for further details

Solid State Devices

Each section under the title of Solid State, is devoted to the new semiconductor products offered by one manufacturer or distributor. The type number and device title is given in bold type, followed by a brief description of features or application. The section is terminated with the address of the company together with reader reply card numbers associated with the device numbers or types.

Announced from Guest International Ltd:

SH730. Sample and hold amplifier manufactured by Hybrid Systems Corporation. This is characterized by a linearity of 0.01% and the capability of acquiring a $\pm 10V$ to this accuracy in less than $1\mu s$. The mode control is t.t.l./d.t.l. compatible and the droop rate of $5mV/ms$ can be improved by the addition of an external capacitor which, however, lengthens the acquisition time.

4403 and 4440 Red-Lit high brightness l.e.ds are Gallium Arsenide devices having a luminous intensity of 1.2mcd at 20mA and a power dissipation of 200mW. The 4440 is a lower cost version with a luminous intensity of 0.8mcd at 20mA. Both can be soldered directly to a p.c.b. or mounted in a panel with a snap-in mounting clip.

DAC328-4-BCD 4 decade b.c.d. current output digital-to-analogue converter, packaged in a $2 \times 2 \times 0.4in$ module. It is t.t.l./d.t.l. compatible and operates from a standard $\pm 15V$ power supply.

Industrial Electronic Components Division, Guest International Ltd, Redlands, Coulsdon, Surrey CR3 2HT.

WW350 sample/hold amplifier
WW351 high brightness l.e.ds
WW352 4 decade b.c.d.

Announced from Mullard:

TAA320A voltage level detector is an i.c. for use in flame control systems, radiation detectors, timers, thermostats and liquid level detectors. It is a development of the audio amplifier TAA320. Operating with an input current of only $1pA$, it will produce an output of 60mA at 20V when a predetermined input threshold voltage is exceeded.

SAJ110 frequency divider i.c. is suitable for electronic organ applications and will produce seven different notes. Thus, twelve i.cs with oscillators to generate the fundamentals will provide all the notes required in an electronic organ. Combining outputs via resistor networks produces an increased range of harmonics and facilitates the synthesis of a wider number of tones.

TCA420 i.f. amplifier for use with f.m. receivers, contains a four-stage i.f. amplifier/limiter and a symmetrical quadrature detector providing a high degree of a.m. rejection. It will also supply an output for a tuning meter, and an automatic stereo inhibit switch when the signal drops below a predetermined value. The switch hysteresis can be adjusted to prevent its continual operation by small signal changes. Inter-station muting is provided and to assist tuning the TCA420A also has "side response" damping.

Mullard Ltd, Mullard House, Torrington Place, London WC1E 7HD.

WW353 voltage level detector
WW354 frequency divider
WW355 i.f. amplifier

Announced from Burr-Brown International Ltd:

SHC23 hybrid sample/hold amplifier has a guaranteed dynamic non-linearity of less than $\pm 0.01\%$. The addition of an external capacitor enables optimization of acquisition time and hold time. The device is packaged in a TO-8 can and is available with an operating temperature range of $0^{\circ}C$ to $+70^{\circ}C$.

3506J and 3508J high-gain wideband operational amplifiers. The model 3506J has a small signal bandwidth of 12MHz and a slew rate of $7V/\mu s$ and is internally compensated for stability at all gains, including the unity gain voltage follower configuration. Model 3508J has a gain-bandwidth product of 100MHz, a slew rate of $35V/\mu s$ and is internally compensated for all gains greater than five. Both units have an open loop gain of 103dB into $2k\Omega$, a common mode rejection of 100dB, bias current of 25nA and a differential input impedance of $300M\Omega$.

3507J high-slew operational amplifier has a slew rate of $120V/\mu s$, a settling time to 0.1% of 200ns and a gain-bandwidth product of 20MHz. For gains greater than 3 the roll-off is 6dB/octave and by adding a single external 20pF capacitor the 3507J can be stabilized at unity gain.

3505J fast settling operational amplifier will settle to 0.1% in 300ns, gives a slew rate $30V/\mu s$ and a gain-bandwidth product of 12MHz. The amplifier is stable at all gains down to unity, without the need for external compensation.

4310 true r.m.s.-to-d.c. converter uses the thermal conversion technique. The heart of the device is a pair of monolithic chips, each containing a resistor-transistor element. The function of the converter is first input voltage to heat, followed by conversion of the heat into a current change and finally from the current change to a d.c. voltage equivalent to the true r.m.s. value of the input voltage. Two versions are available, the 4130K characterized by midrange accuracies of 0.05% and non-linearity of 0.4mV, and the 4130J providing an accuracy of 0.1% and non-linearity of 1.0mV. Minimum bandwidth of both units is 40Hz to 100kHz and a 10MHz minimum upper frequency limit for 2% accuracy. Crest factors from 5:1 up to 100:1 maximum and the ability to accept from 100mV r.m.s. to 2V r.m.s. with peaks up to $\pm 10V$ are also typical. Fully protected from over-voltage, the 4130 also features an input impedance of $10k\Omega$, a settling time of 4s or less, external adjustments for gain, offset voltage and i.f. cut-off.

UAF11/15 series and UAF21/25 series hybrid active filters. Both of these are produced in d.i.l. packages and can be externally tuned for gain, frequency and Q over their specified ranges by adding four resistors. The basic filter utilizes the state variable principle in which low-pass, bandpass and high-pass responses are simultaneously available as outputs from a single 2-pole filter element. Complex responses can be realized for almost any filter function by cascading units. Full power bandwidth for the UAF11/15 series low pass output is 10kHz for $\pm 10V$ signal ranges and is useable at frequencies up to 100kHz for $\pm 1V$ signal ranges. The UAF21/25 series have a full power bandwidth of 100kHz at the low-pass output for $\pm 10V$ signal ranges and is useable up to 1MHz for $\pm 1V$ signal ranges.

Burr-Brown International Ltd, 25A King Street, Watford WD1 8BT.

WW356 hybrid sample/hold amplifier
WW357 wideband operational amplifiers
WW358 high-slew operational amplifier
WW359 fast settling operational amplifier
WW360 true r.m.s.-to-d.c. converter
WW361 hybrid active filters

Real and Imaginary

by "Vector"

Odd Ode (with apologies to Cyril Fletcher et al)

This is the tale of Phil A Ment
Whose pa, a scientific gent,
Subjected himself religiously
To r.f. in large quantity
"For", quoth he, "This dosage will
Prove as effective as the Pill."
— Alas for Family Planning, when
His spouse conceived a sudden yen
— Quite devoid of rhyme or reason —
For strawberries right out of season
Which forced papa in chagrined terror
To admit experimental error
With his "Letter to Nature" finishing in
A convenient waste-paper bin.
But the r.f. currents by some means
Had gingered the paternal genes
For baby Phil 'twas plain to see
Was born an infant prodigy
At six months old the little tot
Instead of lying in his cot
And practising his coo and drool
Was learning Fleming's Left-hand Rule
And by the tender age of three
Had mastered trigonometry,
Sine waves and alternating forces
And eddy currents and their losses
Capping this tour de force sans fuss
With differential calculus —
By five he'd found a grievous flaw
In Einstein's monumental Law.
His school career through "prep" and
"high"
And likewise university
Was lustrous with "distincts" and "hons"
(He frequently advised the dons.)
Thus at the age of twenty he
Acquired a king-sized Ph.D.
Young Phil, his banner thus unfurled
Emerged into the outside world
Turning his back on cloisters he
Elected to join our industry
And soon the rash youth deftly nabs
A job at the Gargantuan Labs.
His team-mate here was Humphrey Naild
A redbrick Bachelor of Science (failed)
Who thought that Ohm was where the
'eart is
And only shone at office parties.
Phil, being an ambitious lad
And anxious to acquire a wad
Of doubloons, burnt the midnight tapers
And churned out reams of Learned Papers

Which brought him references in flocks
But nothing else, for Learned Socs.
Adopt the parsimonious stance
That honour is adequate advance —
A commodity which honest toilers
Find incombustible in boilers
Or for settling bills or monies due
To H.M. Inland Revenue.
His colleague Humphrey, sad to say,
Did nothing to enhance his pay
Or prestige, filling in his tome
With noughts-and-crosses, ribald rhyme,
Electronic timing for his Mini
Or amplifiers for home cine,
With evenings spent in loosening hip-joints
In Soho's less salubrious clip-joints.
But Phil, who scorned such carnal larks
As making love to birds in parks,
Reorientated his intention
And sought his fortune by invention.
He patented in quick succession
Brain-children in a long procession
Including a unique device
For electronically catching mice.
His grateful Company, while pocketing
Royalties which sent the shares a-rocketing,
Displayed their human circumspection
By raising Phil to Chief of Section
And — mark the carrot, gentle reader —
Hinted a future as Group Leader;
A circumstance which came to pass
Helped by a calculating lass
Named Alpha Kerve, a lab assistant
With ash-blond hair and aim persistent
Towards a matrimonial life
As a Lab. Manager's gracious wife —
A laudable ambition quite
For which she laboured day and night.
But colleague Humphrey stayed immune
From Cupid's dart and, like a loon,
Withdrew his hem from toil and strife
In his laboratory life —
Conduct which labelled him "also ran"
With his employers, Gargantuan,
Who showed their grievous discontent
By freezing Humph's emolument.
Thus, on the ladder's lowest rung
Humphrey precariously hung
While Phil continued still to thrive —
The busiest bee in all the hive
(not a foot wrong and ne'er a cropper
A perfect ant to Humph's grasshopper

In you'll forgive this rhymster for
The mixing of a metaphor.)
And so the youthful years flew by
With Phil advancing annually
While Humphrey, wallowing in sloth,
Sowed oats sufficient for them both —
An object-lesson and reminder
To keep our hooters to the grinder
If in life's rat-race we'd succeed
And thus aspire the field to lead.

EPILOGUE

A figure in moth-eaten rags
Squats miserably upon the flags
Outside the tube at Baron's Court
"WIFE AND TV TO SUPPORT"
Proclaims the placard on his chest
And, touched by this oblique request,
The passer-by donates his mite
Despite the cost of living's bite;
Pfennig and centimes tinkle in
The thoughtfully provided tin.
But stay! A sleek Rolls-Royce approaches
And o'er the double line encroaches
While from the car steps a retainer
Depositing tuppence in the container
And then his Christian duty done,
Lord Humphrey Naild is driven on
While Phil the coinage quickly clutches
And gratefully his forelock touches. . . .

Patience, reader, I'll explain
'Til truth's as clear as windowpane
Our Phil's inventive wells ran dry
And brought him to redundancy,
While Humphrey, tired of bread and water
Craftily wed the Chairman's daughter
Becoming, through this master-plan,
The whizz-kid of Gargantuan.

MORAL:

There isn't one.

MAVIS

ELECTRONIC CROSS-OVER

PORTABLE MIXER



The Mavis 3 way electronic cross-over is intended for use primarily with music and speech amplifying systems. It enables the bass range, mid-range and treble range to be separately controlled. The cross-over frequency for each range can be specified if required but will be, in the standard unit, as follows:

Bass roll-off 45 c.p.s.

Bass to mid-crossing point 800 c.p.s.

Mid to treble crossing point 5000 c.p.s.


The unit's output is balanced 600 ohm Line for each channel capable of driving six 600 ohm balance sources. The input to the cross-over is also 600 ohm balance.

GENERAL SPECIFICATION

Size	19" x 12" deep x 7" high (standard 19" racking)
Weight	35lb.
Input	0 dbm 600 ohm balance
Output	+10 dbm 600 ohm balance
Power Requirements	110/230 volts 50/60 c.p.s. at 80 watts approx.
Optional extra	Sub plate

PRICE — £500

WW—111 FOR FURTHER DETAILS

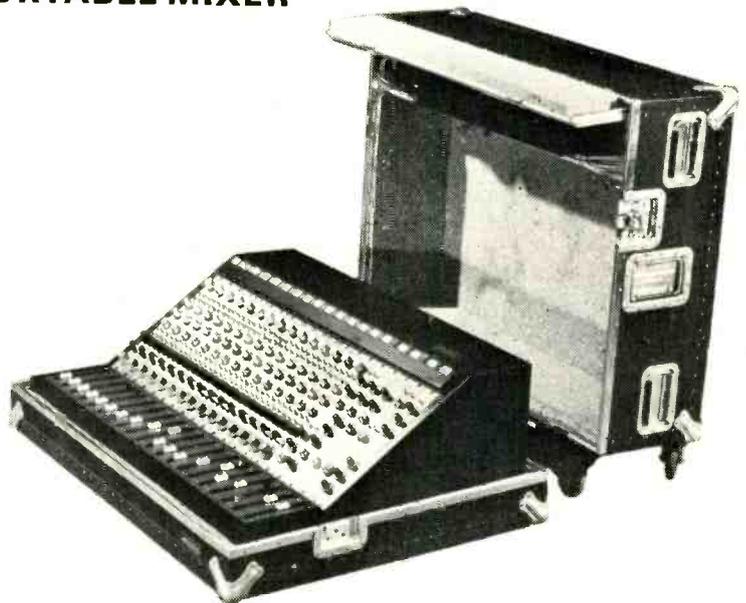

This mixer has been designed for mobile use in conjunction with high quality audio systems. It has basically 15 fully equalized input channels, plus 2 high level auxiliary input channels. The mixer can be used in two configurations, either 4 track full range output or 2 track output split into 3 channels each track, each channel controlled by an electronic cross-over. The remaining 2 tracks can be used either as full range tracks or re-mixed into tracks 1 & 2 as sub-mixers. The mixer also has 2 fully equalized independent monitor outputs and drive facilities for an external echo system. There is also an output for use with headphones to listen through for cueing each channel.


GENERAL SPECIFICATION

Size	38" x 27" x 12"
Weight	190lb approximately
Power Consumption	80 watts approximately
Input Impedance	600 ohm balanced
Output Impedance	600 ohm balanced
Input level 15 modules	-60 dbm
Input level auxiliary 2 inputs	-0 dbm
Output level	+10 dbm all channels
Cue output level	-300 milliwatts
Equalisation range	±14 db treble
	±20 db mid
	±14 db bass
	±20 db bass peak
Overall noise	better than -60 db below full output
Channel separation	better than -80 dbm

PRICE — £6,000 INCLUDING FREIGHT CASE

WW—112 FOR FURTHER DETAILS

INTRODUCING THE P.A.S. 30/30

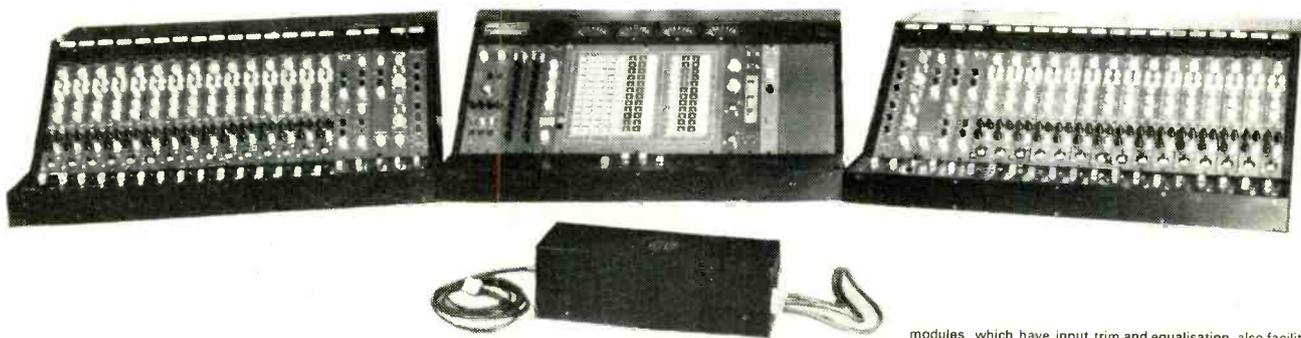

P.A.S. 30/30

This 30 Channel Desk is a development of the Mavis Four Group 15 Channel Mixer to meet the growing demands of modern P.A. and Studio work. It is designed such that every channel may be operated with total flexibility in a four channel quadrasonic setup, and for purposes of live recording it is unique in the fact that a multi-track tape machine of up to 30 tracks may be directly coupled to the channels and a 4 track Tape Machine to the main groups. The Mixer can then at a later stage be used for mixing down to a stereo or quad-master using the main group outputs.

As a compromise between a P.A. Mixer and a conventional Studio Desk, it differs from the latter in the fact that apart from the usual foldback, echo send, cueing facilities etc., only eight sub-groups and four main groups are employed when the desk is used in total; the line drives for recording are derived directly from each channel, and are fully equipped for patching in auxiliary equipment, and may be switched before or after the channels' "EQ" section.

The desk is built in three sections. Two wings (which may be used independently in stereo for P.A.) are equipped with fifteen channels each and a complete output arrangement including four groups and a stereo cross-over. The third section — the routing for the two wings and all the extra equipment needed for master quad control and mix-down into four or two track. This is dealt with in Section B of the Instruction Manual.

Using an extra stereo cross-over each wing can drive a quadrasonic P.A. system.

GENERAL SPECIFICATION

The 30/30 Mixer is divided into four parts. A Centre Desk containing Routing, Foldback, Monitor, Talkback, Echo & Cueing Combiner, Oscillator and Master Quad and Pan facilities with 4 Master Faders. There also can be built-in remote control facilities for Dolby's Machine Control and Auto Tape Locators. The Centre Desk has 4 group outputs, 4 machine inputs, two foldback outputs and 4 monitor outputs also group break "in and out" facilities. There are also sockets to connect this desk to the two wings and a plug for the power supply. Two input wings which are mirror images, and contain 15 input

modules, which have input trim and equalisation, also facilities which enable the module to supply a line level drive for a tape machine with or without equalisation also 4 group outputs which may be combined by switches to be used as quadrasonic output or a pan output. There are facilities for 2 monitor or effects outputs and one echo output. The module has a switch which controls the output to group, off or cue.

There is also a switch which enables a break socket on the rear panel for effects drive and inputs to be switched in and out.

The fourth unit is the power supply which powers the Centre Desk and two wings and provides a 48 volts Phantom Microphone supply to the thirty microphone inputs.

Wing and Centre Desk Size	101 x 82 x 41 cm. approx.
Weight Wing	120 Kg. approx.
Centre	100 Kg. approx.
Power Consumption	500 watts.
Input Impedance	600 or 1200 ohms. Balanced
Output Impedance	600 ohms. Balanced
Maximum Input Sensitivity	
Microphone Input	-60 dbm
Machine Input	0 dbm
Nominal Output	+10 dbm PA
Nominal Output	0 dbm Machine
Cue Output	300 milliwatts
Monitor Output	+10 dbm
Foldback Output	+10 dbm
Echo Output	+10 dbm

**11a SHARPLESHALL ST.,
LONDON, N.W.1**

Tel. 01-722 7161/2/3/4

Telex: London 27655

WW—113 FOR FURTHER DETAILS

Sinclair Project 60

New performance standards ... new safety margins



**Z.50
Mk 2**

Such are the results of using a PZ8 Mk.3 to drive two Z.50 Mk.2 power amplifiers. Developed from the original Z.50, the Mk.2 has improved thermal stability, better regulated D.C. limiting to ensure more symmetrical output voltage swing with still less distortion at lower outputs and automatic transient overload protection. The PZ.8 Mk.3 is the most advanced power supply unit ever to be made at a reasonable price. It cannot be damaged by direct shorting, nor will it fail through overloading, because of an ingenious re-entrant current limiting principle used usually only in expensive laboratory equipment. Because output voltage is variable, the PZ8 Mk.3 makes a worthwhile alternative where PZ.5 and PZ.6 are recommended for Project 60 applications, particularly since this most powerful of all Sinclair supply units can be operated from a smaller mains transformer. Together, the Z.50 Mk.2 and PZ8 Mk.3 provide new standards of performance and reliability and these modules are compatible with earlier types in the Project 60 range.

Z.50 Mk.2 SPECIFICATIONS

Input impedance 100 K Ω
Input (for 30w into 8 Ω) 400mV
Signal to noise ratio, referred to full o/p at 30v HT 80dB or better
Distortion 0.02% up to 20W at 8 Ω .
See published curve
Frequency response 10Hz to more than 200 KHz \pm 1dB
Max. supply voltage 45v (4 Ω to 8 Ω speakers) (50v 15 Ω speakers only)

Min. supply voltage 9v
Load impedance - minimum: 4 Ω at 45v HT
Load impedance - maximum: safe on open circuit


£5.48 + V.A.T.
54p

PZ.8 Mk.3 SPECIFICATIONS

Nominal working output 45V.
Adjustable between 20 & 50V.

£7.98 + V.A.T.
79p

Mains Transformer £5.98 + V.A.T. 59p

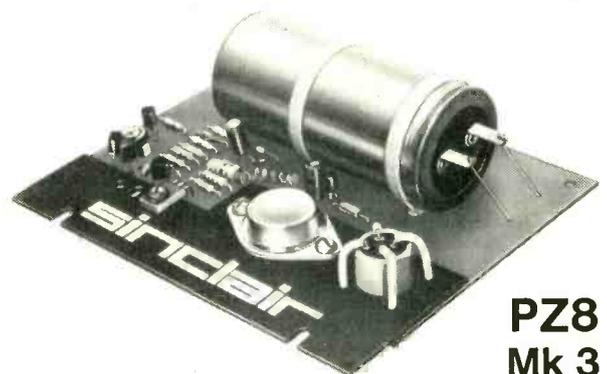

**PZ8
Mk 3**

Other power supplies

In addition to the remarkable Sinclair PZ.8 Mk.III as described, there are two other power units available, which should be chosen according to their types in order to buy to best advantage. All are for operation from A.C. mains 240V.

PZ.5 30 volt, unstabilised **£4.98**
+ V.A.T. 49p

PZ.6 35 volt, stabilised (Not suitable for Super IC.12). **£7.98**
+ V.A.T. 79p

Guarantee

If, within 3 months of purchasing any product direct from Sinclair Radionics Ltd., you are dissatisfied with it, your money will be refunded at once. Many Sinclair appointed Stockists also offer this same guarantee in co-operation with Sinclair Radionics Ltd.

Each Project 60 module is tested before leaving our factory and guaranteed to work perfectly. Should any defect arise in normal use, we will service it at once and without any charge to you. A small charge may be made in those cases where damage arises through miss-use. No charge is made for postage by surface mail. Air Mail charged at cost.

Typical Project 60 applications

System	The Units to use	together with	Units cost
Simple battery record player	Z.50	Crystal P.U., 12V battery volume control, etc.	£5.48 + V.A.T. 54p
Mains powered record player	Z.50, PZ.5	Crystal or ceramic P.U. volume control, etc.	£10.46 + V.A.T. £1.04
12W. RMS continuous sine wave stereo amp. for average needs	2 x Z.50, Stereo 60; PZ.5	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	£25.92 + V.A.T. £2.59
25W. RMS continuous sine wave stereo amp. using low efficiency (high performance) speakers	2 x Z.50, Stereo 60; PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£28.92 + V.A.T. £2.89
80W. (3 ohms) RMS continuous sine wave de luxe stereo amplifier. (60W. RMS into 8 ohms)	2 x Z.50 Mk.2, Stereo 60; PZ.8 Mk.3 transformer	As above	£34.90 + V.A.T. £3.49
Indoor P.A.	Z.50 Mk.2, PZ.8 Mk.3 transformer	Mic., guitar, speakers, etc., controls	£19.44 + V.A.T. £1.94

A.F.U. (£5.98 + V.A.T. 59p) may be added as required.

sinclair

SINCLAIR RADIONICS LTD., LONDON RD., ST. IVES, HUNTINGDONSHIRE PE17 4HJ Telephone: St. Ives (0480) 64311 Telex: 32250 Reg No. 699483 England

WW—096 FOR FURTHER DETAILS

www.americanradiohistory.com

Henry's Palace

the world's most advanced high fidelity modules

Q.16 high fidelity loudspeaker

The Q 16 employs original and by now well proven acoustic principles in which a special driver assembly is meticulously matched to a uniquely designed cabinet. In performance it comfortably stands comparison with very much more expensive loudspeakers. A solid teak surround is used with a special all-over cellular black foam front chosen both for its appearance and ability to pass all audio frequencies without masking.


Specifications

Construction: A sealed seamless sound or pressure chamber is used with internal baffle, and special high flux driver

Loading: Up to 14 watts RMS, into 8 ohms

Frequency response: From 60 to 16,000 Hz

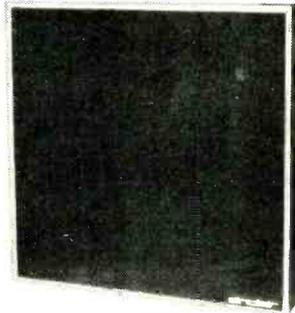Size and styling: 248 mm square x 120 mm deep (9 3/4" x 4 1/4") with neat pedestal base.



£7.70 + V.A.T. 77p

Project 605



the simple way to build a Project 60 system without soldering

For the many audio enthusiasts anxious to build to high standards without too many involvements, there could be nothing better or simpler than Project 605. It offers the advantages of Project 60 and is absolutely complete down to the last piece of wire cut to length. Whilst not as powerful as assemblies using Z.50 power amplifiers, we know from experience that there are many for whom the specifications of Project 605 are ideal, particularly in relation to the environment in which it is required to be used. In Project 605 you have everything necessary to build a versatile Project 60 thirty watt high fidelity amplifier system suitable for all domestic requirements. The convenient pack includes two Z.30 power amplifiers, a Stereo 60 pre-amp control unit and the special Masterlink unit to and from which all input and output connections are made. For power a PZ.5 is provided. Building is particularly easy since all necessary leads are supplied colour coded, cut to length and terminated by contact clips which connect firmly to the modules. There is absolutely no soldering to be done. Complete with comprehensive, easy to follow instructions manual.

£29.95 + V.A.T. £2.99 Post free

Send coupon for leaflet

Please send leaflet and name and address of my nearest Sinclair stockist

Name _____

Address _____

SINCLAIR RADIONICS LTD., LONDON ROAD, ST. IVES, HUNTINGDON PE17 4HJ


ww 2

sinclair

Stereo 60 pre-amp/control unit

Designed specifically for Project 60 systems, the Stereo 60 is equally suitable with any high quality power amplifier. Silicon epitaxial planar transistors used throughout ensure high signal-to-noise ratio and excellent tracking between channels. Input selection is by press buttons, with accurate equalisation on all input channels. The unit is easy to mount.

SPECIFICATIONS—Input sensitivities: Radio – up to 3mV. Mag. p.u. 3mV; correct to R.I.A.A. curve ± 1dB; 20 to 25,000Hz. Ceramic p.u. – up to 3mV; Aux – up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE+12 to –12dB at 10KHz; BASS+12 to –12dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.

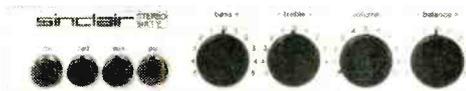

Built, tested and guaranteed.

£9.98 + V.A.T. 99p

AFU filter unit

For use between Stereo 60 and two Z.30's or Z.50's in stereo formation. Cut off frequencies are continuously variable, with 12dB/octave cut in the rejection band. Two stages of filtering – rumble (high pass) and scratch (low pass). Amplitude and phase distortion are negligible. Supply voltage needed – 15–35V. H.F. cut-off (–3dB) 28KHz to 55KHz; L.F. (–3dB) 25Hz to 100Hz. For Project 60 or any good stereo system.


Built, tested and guaranteed

£5.98

+ V.A.T. 59p



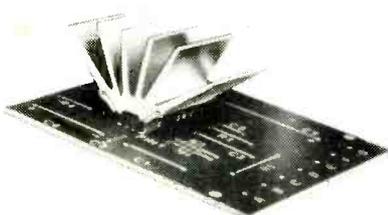Super IC.12 Integrated circuit high fidelity amplifier



Having introduced Integrated Circuits to hi-fi constructors with the IC.10, which was the first time an IC had ever been made available for such purposes, we followed it with an even more efficient version, the Super IC.12. This needs very few external resistors and capacitors to make an exceedingly efficient high fidelity amplifier for pick-up, F.M. radio or small P.A. set up etc. The free 40 page manual supplied details many other applications which this remarkable IC make possible. The Super IC.12 is the equivalent of a 22 transistor circuit

contained within a 16 lead DIL package, and the finned heat sink is sufficient for all likely requirements. The Super IC.12 is also compatible with those Project 60 modules which would be used with the Z.50 and Z.30 amplifiers. Complete with free manual and printed circuit board.

SPECIFICATIONS

Output power: 6 watts RMS continuous (12 watts peak) into 6–8 Ω. **Frequency Response:** 5Hz to 100KHz ±1dB. **Total Harmonic Distortion:** Less than 1%. (Typical 0.1%) at all output powers and frequencies in the audio band (28V). **Load Impedance:** 3 to 15 ohms. **Input Impedance:** 250 Kohms nominal. **Power Gain:** 90dB (1,000,000,000 times) after feedback. **Supply Voltage:** 6 to 28V. **Quiescent current:** 8mA at 28V. **Size:** 22 x 45 x 28mm including pins and heat sink.

Manual available separately 15p post free

With FREE printed circuit board and 40 page manual.

£2.98 + V.A.T. 29p Post free

ALL PRICES QUOTED IN THIS ADVERTISEMENT ARE THE RECOMMENDED RETAIL PRICES.

WW—097 FOR FURTHER DETAILS

www.americanradiohistory.com

Henry's

U.K.'s LARGEST RANGE OF BRANDED AND GUARANTEED DEVICES. (Quantity Discounts 10% 12+, 15% 25+, 20% 100+)

(Any one type except where quantity discounts show) Min. Order £1.00 please, Post 10p.

INTEGRATED CIRCUITS

VERY IMPORTANT. ONLY branded I.C.'s are the FULL manufacturers specifications. ALL others are not. Henry's sell only branded Integrated Circuits. From TEXAS ... I.T.T. ... FAIRCHILD ... SIGNETICS. So why buy alternatives or unbranded devices when you can purchase the genuine article from us—ex stock... need we say more!

Type	1/11	12/29	30/99	Type	1/11	12/29	30/99	Type	1/11	12/29	30/99
	£p	£p	£p		£p	£p	£p		£p	£p	£p
SN7400N	0.20	0.18	0.16	SN7448N	1.50	1.27	1.13	SN74141N	1.00	0.90	0.80
SN7401N	0.20	0.18	0.16	SN7450N	0.20	0.18	0.16	SN74142N	2.88	2.88	2.52
SN7401AN	0.38	0.38	0.33	SN7451N	0.20	0.18	0.16	SN74145N	1.44	1.44	1.26
SN7402N	0.20	0.18	0.16	SN7453N	0.20	0.18	0.16	SN74147N	2.30	2.30	1.83
SN7403N	0.20	0.18	0.16	SN7454N	0.20	0.18	0.16	SN74148N	2.01	2.01	1.63
SN7403AN	0.38	0.38	0.33	SN7460N	0.20	0.18	0.16	SN74150N	2.30	2.30	2.01
SN7404N	0.24	0.21	0.18	SN7470N	0.33	0.30	0.27	SN74151N	1.15	1.15	1.00
SN7405N	0.20	0.18	0.16	SN7472N	0.38	0.38	0.34	SN74153N	1.09	1.09	0.95
SN7405AN	0.44	0.44	0.38	SN7473N	0.44	0.41	0.37	SN74154N	2.30	2.30	2.01
SN7406N	0.40	0.38	0.35	SN7474N	0.48	0.45	0.42	SN74155N	1.15	1.15	1.00
SN7407N	0.20	0.18	0.16	SN7475N	0.50	0.50	0.51	SN74156N	1.09	1.09	1.00
SN7408N	0.25	0.22	0.19	SN7476N	0.45	0.36	0.32	SN74157N	1.09	1.09	0.95
SN7409N	0.33	0.33	0.28	SN7480N	0.80	0.70	0.50	SN74159N	2.44	2.44	2.14
SN7409AN	0.44	0.44	0.38	SN7481N	1.25	1.10	0.95	SN74160N	1.58	1.58	1.38
SN7410N	0.20	0.18	0.16	SN7482N	0.87	0.80	0.72	SN74161N	1.58	1.58	1.38
SN7411N	0.25	0.23	0.21	SN7483N	1.20	1.10	1.00	SN74162N	1.58	1.58	1.38
SN7412N	0.28	0.28	0.25	SN7485N	1.87	1.87	1.63	SN74163N	1.58	1.58	1.38
SN7412AN	0.38	0.38	0.33	SN7486N	0.50	0.50	0.44	SN74164N	2.01	2.01	1.76
SN7413N	0.30	0.27	0.25	SN7489N	4.32	4.32	3.78	SN74165N	2.01	2.01	1.76
SN7416N	0.30	0.27	0.25	SN7490N	0.75	0.70	0.63	SN74166N	2.16	2.16	1.89
SN7417N	0.30	0.27	0.25	SN7491N	1.10	1.00	0.90	SN74167N	4.10	4.10	3.59
SN7420N	0.20	0.18	0.16	SN7492N	0.75	0.70	0.63	SN74170N	2.88	2.88	2.01
SN7422N	0.28	0.28	0.25	SN7493N	0.75	0.70	0.63	SN74172N	5.76	5.76	5.04
SN7422AN	0.38	0.38	0.33	SN7494N	0.85	0.80	0.75	SN74173N	1.66	1.66	1.45
SN7423N	0.37	0.34	0.32	SN7495N	0.85	0.80	0.75	SN74174N	1.80	1.80	1.57
SN7425N	0.37	0.37	0.32	SN7496N	1.00	0.90	0.83	SN74175N	1.29	1.29	1.13
SN7427N	0.37	0.37	0.32	SN7497N	2.16	1.89	1.89	SN74176N	1.44	1.44	1.26
SN7428N	0.43	0.43	0.37	SN74104N	0.60	0.53	0.45	SN74177N	1.44	1.44	1.26
SN7430N	0.20	0.18	0.16	SN74105N	0.60	0.53	0.45	SN74178N	1.44	1.44	1.26
SN7432N	0.37	0.37	0.32	SN74107N	0.51	0.51	0.45	SN74181N	5.18	5.18	4.53
SN7433N	0.43	0.43	0.38	SN74110N	0.57	0.57	0.50	SN74182N	1.44	1.44	1.26
SN7433AN	0.57	0.57	0.50	SN74111N	2.16	2.16	1.89	SN74184N	2.16	2.16	1.89
SN7437N	0.43	0.43	0.37	SN74168N	1.00	0.90	0.83	SN74185AN	2.16	2.16	1.89
SN7438N	0.43	0.43	0.37	SN74119N	1.92	1.92	1.68	SN74188N	6.48	6.48	5.67
SN7440N	0.20	0.18	0.16	SN74120N	1.05	1.05	0.92	SN74190N	3.30	3.30	2.01
SN7441AN	0.85	0.79	0.73	SN74121N	0.57	0.57	0.50	SN74191N	2.30	2.30	2.01
SN7442N	0.85	0.79	0.73	SN74122N	0.80	0.80	0.70	SN74192N	2.30	2.30	2.01
SN7443N	1.50	1.27	1.13	SN74123N	1.44	1.44	1.26	SN74193N	2.30	2.30	2.01
SN7444N	1.50	1.27	1.13	SN74125N	0.69	0.69	0.60	SN74194N	1.72	1.72	1.51
SN7445N	2.16	2.16	1.89	SN74126N	0.69	0.69	0.60	SN74195N	1.44	1.44	1.26
SN7446N	2.16	2.16	1.89	SN74132N	0.72	0.72	0.63	SN74196N	1.58	1.58	1.38
SN7447AN	1.80	1.80	1.57	SN74136N	0.63	0.63	0.55	SN74198N	3.16	3.16	2.77
				SN74199N	2.88	2.88	2.52				

LARGER QUANTITY AND O.E.M. PRICES PHONE (01) 723 3646. PRICING OF SN7400 SERIES IS CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX. SN74... HIGH POWER... LOW POWER SERIES IN STOCK... SEND FOR LIST 36, FREE ON REQUEST. LOW PROFILE SOCKETS 14 PIN... 15p. 16 PIN... 17p. 8 PIN... 14p.

TRANSISTORS

AAZ13	10p	BC182	12p	BYZ13	35p	OC36	65p	ZTX108	10p	2N3711	1.60
AC107	35p	BCY32	85p	OC41	55p	ZTX300	14p	2N3774	1.75		
AC128	20p	BCY39	45p	GET111	55p	OC45	18p	ZTX302	18p	2N3773	2.25
AC187	20p	BCY55	2.50	GET115	75p	OC71	15p	ZTX500	15p	2N3790	2.25
ACV17	35p	BCY70	15p	LET880	55p	OC72	25p	2G301	40p	2N3919	35p
ACV39	65p	BCY71	20p	LM309K	1.87	OC77	55p	2N697	15p	2N3866	75p
AD149	50p	BCY72	13p	MAT121	1.87	OC81	28p	2N706	10p	2N3903	15p
AD161	39p	BD124	80p	MJE340	50p	OC83	25p	2N930	20p	2N4002	14p
AD192	39p	BD131	85p	MJE520	65p	OC140	65p	2N987	45p	2N4126	14p
AF117	20p	BF115	22p	MJE3055	75p	OC170	25p	2N132	25p	2N4871	35p
AF118	50p	BF180	33p	MPF105	45p	OC200	55p	2N1304	22p	2N5457	36p
AF139	33p	BF194	13p	NKT217	45p	OC202	90p	2N1613	20p	2S001	3.40
AF186	40p	BFX13	25p	NKT404	60p	ORP12	1.00	2N1871	1.00	2S206	8.90
AF239	44p	BFX34	55p	OAS	60p	TIL209	25p	2N2147	75p	2S303	7.00
ASV27	30p	BFY39	45p	OA81	10p	TP29A	49p	2N3054	45p	40361	45p
BA115	10p	BFY50	20p	OAC200	8p	TP30A	58p	2N3055	45p	40408	50p
BA137	10p	BFY51	20p	OAB202	10p	TP31A	61p	2N3440	50p	40636	1.00
BC108	12p	BFY90	75p	OC18	85p	TP41A	74p	2N3442	1.00	40430	85p
BC109	12p	BLV36	6.25	OC20	1.25	TP42A	90p	2N3525	80p		
BC119C	14p	BSX20	15p	OC28	65p	TIS43	26p	2N3614	59p		
BC113	16p	BU105	2.20	OC35	55p	V405A	25p	2N3702	11p		
BC147	12p	BY100	15p								
BC169C	14p	BY127	15p								

TRIACS

3 AMP RANGE	Price	1-11	Price
SC45B	200v	£1.15	
SC45D	400v	£1.45	
SC45E	500v	£1.85	
15 AMP RANGE	Price	1-11	Price
SC50A	100v	£1.45	
SC50B	200v	£1.65	
SC50C	400v	£1.95	
SC50E	500v	£2.25	

SILICON CONTROLLED RECTIFIERS

Type	1-11
ONE AMP (T05) P.I.V.	
CRS 1/05AF	50v
CRS 1/10AF	100v
CRS 1/20AF	200v
CRS 1/40AF	400v
CRS 1/60AF	600v
THREE AMP (T048)	
CRS 3/05AF	50v
CRS 3/10AF	100v
CRS 3/20AF	200v
CRS 3/40AF	400v
CRS 3/60AF	600v
FIVE AMP	
CRS 5/400	400v
SEVEN AMP (T048)	
CRS 7/100	100v
CRS 7/200	200v
CRS 7/400	400v
CRS 7/600	600v
SIXTEEN AMP (T043)	
CRS 16/100	100v
CRS 16/200	200v
CRS 16/400	400v
CRS 16/600	600v

KITS BY



UK LTD

EASY TO BUILD—EVERYTHING SUPPLIED

Model No.	1-11	12/29	30/99
310 Radio control receiver	3.00		
300 4-channel R/C transmitter	5.75		
345 Superhet R/C receiver	5.08		
450 TV sweep generator	10.24		
455 AM signal generator	9.25		
460 FM signal generator	9.91		
65 Simple transistor tester	1.18		
115 8 watt Amplifier	2.87		
120 12 watt amplifier	3.88		
125 Stereo control unit	4.20		
130 Mono control unit	3.52		
605 Power supply for 115	4.08		
610 Power supply for 120	4.85		
615 LF generator 10Hz-1mHz	2.79		
230 AM/FM aerial amplifier	5.18		
240 Auto packing light	5.83		
275 Mic. preamplifier	17.51		
480 Electronic voltmeter	9.68		
485 0-12v 300mA STAB. supply	12.60		
570 LF generator 10Hz-1mHz	12.87		
575 Sq. wave generator 20Hz-20kHz	10.24		
900 SWR meter	7.47		
620 Ni-CAD Charger 1.2-12v	7.65		
630 STAB Power supply 6-12v 0.25-0.1A	2.63		
690 DC motor speed Gov.	5.96		
700 Electronic Chaffinch	5.56		
705 Windscreen wiper timer	8.87		
760 Acoustic switch	7.27		
780 Metal Detector (electronics only)	6.16		
790 Capacitive Burglar alarm	6.75		
810 Dynamic Compressor	3.75		
835 Guitar preamp	5.20		
845 Delay car alarm	10.68		
875 CAP. Discharge ignition for car engine (-Ve Earth)	1.90		
80 Scope Calibrator	5.50		

Henry's

U.K.'s LARGEST RANGE OF ELECTRONIC COMPONENTS AND EQUIPMENT AT BARGAIN PRICES

Latest Catalogue price 55p post paid. Complete with Discount Vouchers



Now built and used by thousands of satisfied customers. Features slim design overall size in cabinet 15 1/2 x 2 1/2 x 6 1/2 6-IC's, 10 transistors, stabilisers Gardners low field transformer. Fibre Glass PC Panel, complete chassis work. Now available built and tested as well as in kit form. **HIGH QUALITY AND STABILITY ARE PRE-DOMINATE FEATURES - DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION. FACILITIES.**

On/off switch indicator, headphones socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector, Mag. P.U. Radio Tuner, Aux. Can be altered for Mic., Tape, Tape-head, etc. Constructional details Ref. No. 21 30p. Distributed by Henry's throughout UK.

FREE—Teak cabinet with complete kit. Kit price £28.50 (+VAT+50p carr/packing) or built and tested £35.00 (+VAT+50p carr/packing) as illustrated.


BUILD THE TEXAN

20 + 20 WATT IC STEREO AMPLIFIER

As featured by Practical Wireless 1972



BUILD THE NEW HENELEC STEREO FM TUNER

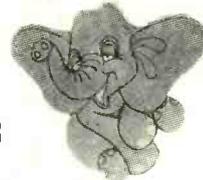



You pay less VAT with Henry's Low Prices

A completely new high stability stereo FM tuner. Features variable capacity diode tuning, stabiliser power supply, IC Decoder, high gain low noise, IF stages, LED indicators, Tuning meter, AFC, easy to construct and use. Mains operated. Slim modern design with fibre glass PC, teak cabinet etc. Available as a kit to build or ready built. Overall size 8" x 2 1/2" x 6 1/2". Produced to give high performance with a realistic price. (Parts list and constructional details Ref. No. 5 30p). Henry's are sole distributors UK and Europe. Kit price £21.00 (+ VAT) or built and tested £24.95 (+ VAT).



EARN YOURSELF EASY MONEY, WITH PORTABLE DISCO EQUIPMENT

- DISCO MINI A complete portable disco, fitted mixer/preamp, 2 decks all facilities £98.50
- 100 watt amplifier for above £38.75
- SL100 100 watt mixer/amplifier with slider controls £69.00
- R50 50 watt mixer/amplifier £49.50
- DISCO AMP 100 watt mixer/amplifier chassis unit £65.85
- DISCO MIXER/PREAMPLIFIERS (OP for up to 6-100 watt amplifiers)
- SDL1 (rotary controls) £49.50
- SDLII (slider controls) £58.50
- DISCO VOX (slider controls) the complete disco unit £69.50
- DJ100 100 watt power amplifier for above £38.75
- DJ30L 3 channel 3kw sound to light £29.50
- DJ40L as 30L plus built in microphone £38.75
- DIMANATIC 1 kW adjustable speed auto dimmer £25.00
- SCENE STROBE £19.00. ROAD STROBE £25.00
- Disco anti-feedback microphone £11.95
- CoIt 150 watt liquid wheel projector £22.50
- 150 watt QI liquid wheel projector £50.00

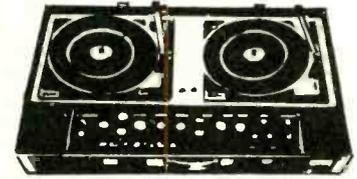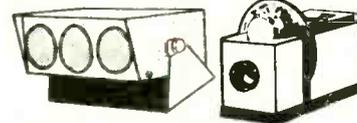

- 150 watt QI cassette wheel projector £50.00
- Spare Effects cassettes large range of patterns £8.00
- Mini spot bank fitted 3 lamps £11.00
- Auto Trillite (mini with flashers) £17.00
- Mixer/Misc/Speakers/Lighting UK's largest range. FREE stock list ref. No. 18 on request.

TEXAN STEREO SYSTEM PLUS PRICE SAVINGS

The Texan Stereo Systems include the high quality Texan Stereo amplifier assembled and ready to use. A pair of Type 200 20 watt Speaker-Tweeter systems size 21" x 12" x 10" and a choice of Garrard players built into a plinth with cover with Goldring G800 magnetic cartridge. Systems 25 uses Garrard SP25 Mk III and system 76 the Garrard AP76 de luxe turntable. All necessary leads are supplied. System 25 (list approx. £109) £79.50 System 76 (list approx. £117) £89.50 (plus 10% VAT and plus £1.45 carr/packing)



SINCLAIR AND MINIATURE AMPLIFIERS

- AMPLIFIERS (carr. etc. 20p).
- 4-300, 0.3 watt 9 volt £1.75
- 104, 1 watt 9 volt £2.20
- 304, 3 watt 9 volt £2.50
- 555, 3 watt 12 volt £2.85
- E1208, 5 watt 12 volt £4.50
- 608, 10 watt 24 volt £4.10
- 410, 10 watt 28 volt £4.95
- Z30, 15 watt 30 volt £3.57
- E1206, 30 watt 45 volt £9.75
- Z50, 30 watt 50 volt £4.37
- E1210, 2 1/2 + 2 1/2 watts 12 volt £5.25
- RE500, 5 watt IC mains operated Amplifier with controls £6.30
- SAC14, 7 + 7 watt Stereo with controls £8.00
- SAC13, 15 + 15 watt Stereo with controls £11.00
- SINCLAIR UNITS (carr. 20p)
- Z30 3-57 250 £4.37
- Stereo 60 Preamplifier £7.97
- PZ5 £3.97, PZ6 £6.37, PZ8 (for Z50) £4.77
- (TRANS £2.95)
- AFU £4.45
- SINCLAIR PACKAGE DEALS (Post 25p)
- 2 x Z30, Stereo 60, PZ5 £15.95
- 2 x Z30, Stereo 60, PZ6 £18.00
- 2 x Z50, Stereo 60, PZ8 £20.25
- Transformer for PZ8 £2.95
- PROJECT 605 KIT £19.95




GARRARD BATTERY TAPE DECK

GARRARD 2 speed 9 volt tape decks. Fitted recorder/play and oscillator/erase heads. Wind and rewind controls. Takes up to 4" spools. Brand new complete with head circuits. £9.50 carr. 30p.



POWER SUPPLIES FOR EVERY PURPOSE

- (All cases unless stated chassis)
- 470C 6/7 1/2 volt 300 MA (Includes Multi-Adaptor for Tape Recorders, etc.) £1.95 post 20p
- Car Lighter Voltage Adaptors 300mA (State voltage 6v, 7.5v, 9v) £1.95 ea. post 25p
- SC202 3/6 7/8 volt 400mA £3.25 carr. 30p
- HC244R Stabilised version £4.25 carr. 30p
- P500 9 volt 500mA £2.80 post 20p
- P11 24 volt 500mA (chassis) £2.80 post 20p
- P15 26/28 volt 1 amp (chassis) £2.70 post 20p
- P1080 12v 1 amp (chassis) £3.25 post 20p
- P1081 45v 0.9 amp (chassis) £4.40 post 20p
- P12 4 1/2-12 volt 0.4-1 amp £6.75 post 30p
- SE101A 3/6 9/12 volt 1 amp (Stab.) £9.15 post 25p
- RP164 6/7 1/2 9/12 1 amp (Stab.) £9.95 post 30p

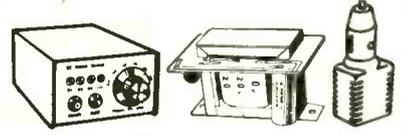


All types offered subject to availability. Prices correct at time of press E.&O.E. 10% VAT to be added to all orders. U.K. post, etc., 15p per order.

HI-FI AND TAPE EQUIPMENT Big Discounts—Demonstrations
Phone 01-402 5854 for quotes on stocklist.
You can order by phone with Barclaycard or Access.
EASY TERMS FOR CALLERS

LOW COST HI-FI SPEAKERS

- SPECIAL OFFER**
- EMI 13" x 8"—full range speakers (post 20p each or 30p pair)
- *150TC—8 ohms Twin Cone 10 watt £2.20 each or £4.00 pair.
- *450 10 watt C/o Twin Tweeters 3, 8 or 15 ohms £3.50 each or £6.90 pair.
- EW 15 watt 8 ohms C/o Tweeter £4.30 each or £7.90 pair.
- 350 20 watt C/o Tweeters 8 or 15 ohms £7.50 each or £14.20 pair.
- * Polished wood cabinet £4.60 post 35p.
- 8 ohms full range (post 20p)**
- FR4 4" 5 watt £4.00
- FR65 6 1/2" 10 watt £5.50
- FR8 8" 15 watt £7.60
- FR23 9 x 6" 15 watt £6.00
- BASS & MID RANGE—8 ohms (post 20p)**
- AA12 5 1/2" 15 watt £3.20
- B110 5 1/2" 15 watt £5.60
- B200 8" 15 watt £6.45
- B139/2 13" x 8" 30 watt LF £10.25
- TWEETERS AND CROSSOVERS (post 20p)**
- K2006 10 watt 8 or 15 ohms £1.90
- FHT6 15 watt 8 ohms £3.20
- K2011 30 watt 8 ohms £3.75
- T27 8 ohms £4.25
- Accent 100 KEF 30 watt 8 ohms £4.90
- K4009 30 watt 1kHz/5kHz C/o £2.00
- SN75 3kHz var. C/o £1.75
- SPEAKER KITS (carr. etc. 35p)**
- 20-2 8" 30 watt £10.00 each
- 20-3 8" 40 watt £15.00 each
- LINTON 2 20 watt £15.95 pair
- GLEND ALE 3 30 watt £28.95 pair
- DOVED ALE 3 50 watt £42.00 pair
- KEF KK2 £20.40 each
- KEF KK3 £32.00 each

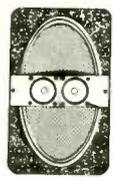

TEST EQUIPMENT MULTIMETERS

- (carr. etc. 30p)
- 200H 20K/Volt Siimline with case £4.95
- TLH33D 2K/Volt Robust with case £4.95
- U437 10K/Volt Steel case. AC up to 40kHz £4.95
- U4324 20K/Volt with AC current ranges £3.00
- AF105 50K/Volt with Leather case £9.50
- U4313 20K/Volt AC current. Steel case £10.50
- U4341 Plus Built in transistor tester £10.50
- Model 500 30K/Volt £9.95



Henry's RADIO LIMITED

EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
354-356 High Fidelity and Tape Equipment 01-402 5854/4736
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Hi-Fi and Tape Equipment **BIG DISCOUNTS. DEMONSTRATIONS**
Phone 01-402 5854 For quotes or stock list. You can order by phone with Barclay or Access Card.
EASY TERMS FOR CALLERS.

Open: 9 am-6 pm 6 days a week

All stores open all day Saturday

COMPONENTS FOR W.W. AMPLIFIER DESIGNS

100W AMPLIFIER (FEB. 1972)	
Designer approved kit.	15-60
Semiconductor set	2-50
Resistors, capacitors, pots	1-30
F/Glass PCB	
POWER SUPPLY (For 100W Amp.)	
Designer approved kit.	14-70
Semiconductors, Resistors, capacitors, pots, trans-formers, F/Glass PCB	
30W BLOMLEY (New approach to class B)	
Semiconductor set	5-60
Resistors, capacitors, pots	1-85
F/Glass PCB	0-70
30W BAILEY (Single power rail)	
Transistor set	4-60
Resistors, capacitors, pots	1-45
F/Glass PCB	0-65
LINSLEY-HOOD CLASS A (Dec., 1970, circuit)	
Designer approved kit.	1-20
2N3055 pair, BC212L, 2N1711	1-80
Resistors, capacitors, pot	0-60
F/Glass PCB	
LINSLEY-HOOD 20W CLASS AB	
Designer approved kit.	3-35
MJ481/491, MJE521, BC182L, BC212L, zener	2-20
Resistors, capacitors, pots	0-70
F/Glass PCB	
Please state 8Ω or 15Ω	
REGULATED 60V POWER SUPPLY	
A 5 regulator series stabiliser, suitable for a pair of Bailey or Blomley amplifiers, featuring very effective S/C protection. All Semi/C's, R's, C's, F/Glass PCB	4-85
Power supplies for other amplifiers also available	
BAILEY/BURROWS PRE-AMP (Aug., 1971)	
Component Set: Mono	2-75
Component set: Stereo	6-35
Each component set comprises of all specified resistors, capacitors, transistors pots, including special balance control for stereo sets.	
Stereo F/Glass PCB	1-60
STUART TAPE RECORDER	
Set of stereo f/glass PCBs	2-70
Components sets on price list.	

'TEXAN' TEXAS INSTRUMENTS DESIGNED & APPROVED FULL KIT



£28.50 INCLUDES TEAK CASE

20 Watt per channel stereo amplifier designed by Richard Mann of Texas Instruments and published in Practical Wireless May-July 1972.

This low distortion (0.09% at 20W into 8 ohm), wide bandwidth (-3dB 5Hz-35KHz) design is offered as a Texas Instruments approved full kit (including all metalwork and Teak case for a total of £28.50 post paid. Full details in price list.

METALWORK SYSTEM

Designed to house Bailey, Blomley or Linsley Hood Class AB amplifiers with simple or regulated power supplies and Bailey Burrows pre-amp. Options of standard or hum reducing toroidal mains transformer.

TOROIDAL TRANSFORMER 60 volt 2 amp.

Max. height 2in. Suitable for our regulated power supply	£7.40
Simple clamp	£0.20
Magnetically screening clamp	£0.75


SEMICONDUCTORS

2N699	0-25	BC184L	0-11
2N1613	0-20	BC212L	0-12
2N1711	0-25	BC214L	0-14
2N2926G	0-10	BCY72	0-13
2N3053	0-15	BF257	0-40
2N3055	0-45	BF259	0-47
2N3442	1-20	BFR39	0-25
2N3702	0-11	BFR79	0-25
2N3703	0-10	BFY50	0-20
2N3704	0-10	BFY51	0-20
2N3705	0-10	BFY52	0-20
2N3706	0-09	MJ481	1-20
2N3707	0-10	MJ491	1-30
2N3708	0-07	MJE521	0-60
2N3709	0-09	MPSA05	0-30
2N3710	0-09	MPSA12	0-55
2N3711	0-09	MPSA14	0-35
2N3819	0-23	MPSA55	0-35
2N3904	0-17	MPSA65	0-40
2N3906	0-20	MPSA66	0-40
2N4058	0-12	MPSU05	0-70
2N4062	0-11	MPSU55	0-70
2N4302	0-60	SN72741P	0-58
2N5087	0-42	SN72748P	0-58
2N5210	0-54	THB11	1-10
2N5457	0-30	TIP29A	0-50
2N5830	0-30	TIP30A	0-60
40361	0-40	TIP31A	0-60
40362	0-45	TIP32A	0-70
BC107	0-08	TIP33A	1-00
BC108	0-08	TIP34A	1-50
BC109	0-08	TIP41A	0-74
BC125	0-15	TIP42A	0-90
BC126	0-15	TIP3055	0-60
BC182K	0-10	TIP42A	0-90
BC212K	0-12	1B08T20	0-50
BC182L	0-10	1B40K20	1-40
		1N914	0-07
		1N916	0-07
		1S44	0-05
		1S920	0-10
		1S3062	0-25
		5B05	1-20

HI-FI NEWS 75 WATT AMPLIFIER BY J. L. LINSLEY-HOOD

Published Nov. 1972 to Feb. 1973

DESIGNER APPROVED KIT

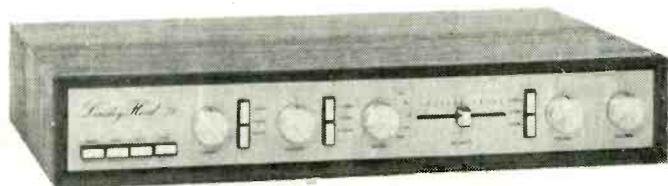

SLIMLINE STYLE CHASSIS DIMENSIONS: 17.0in. x 2.0in. x 12.0in. This slimline unit has been made practical by the use of a specially designed TOROIDAL TRANSFORMER and highly compact printed circuit boards which have been fully tested and approved by Mr. Linsley-Hood.

FREE TEAK CASE

Total cost of individually purchased packs: **£63.95**

WITH 75 WATT PER CHANNEL COMPLETE AMPLIFIER KITS

Cost of complete kit: **£56.60**

TRADE ENQUIRIES WELCOME

P.S. Full circuit description in handbook 30p

FOR FURTHER DETAILS PLEASE WRITE TO:

POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE, ANDOVER : HANTS

MAIL ORDER ONLY POST FREE TO U.K. OVERSEAS AT COST
U.K. Orders Subject to 10% V.A.T. Surcharge

- ★ 75 WATTS PER CHANNEL
- ★ BANDWIDTH (3dB) 3HZ-40KHZ
- ★ DISTORTION LESS THAN 0.01%
- ★ UNCONDITIONAL STABILITY

COMPONENT PACKS


Pack	
1	Fibre glass printed circuit board for power amp. £0.75
2	Set of resistors, capacitors, pre-sets for power amp. ... £1.50
3	Set of semi-conductors for power amp. (highest voltage version) £5.50
4	Pair of 2 drilled, finned heat sinks £0.80
5	Fibre glass printed circuit board for pre-amp..... £1.10
6	Set of low noise resistors, capacitors, pre-sets for pre-amp £2.70
7	Set of low noise, high gain semi-conductors for pre-amp £2.10
8	Set of potentiometers (including mains switch) £1.55
9	Set of 4 push button switches, rotary mode switch ... £3.10
10	Toroidal transformer complete with magnetic screen/housing primary: 0-117-234 V. secondaries: 33-0-33 V. 24-0-24 V., electrostatic screen £9.15
11	Fibre glass printed circuit board for power supply ... £0.55
12	Set of resistors, capacitors, secondary fuses, semi-conductors for power supply £3.50
13	Set of miscellaneous parts including DIN skts., mains input skt. fuse holder, interconnecting cable, control knobs £3.25
14	Set of metal workparts including silk screen printed fascia panel and all brackets, fixing parts, etc. £6.30
15	Handbook, based on Hi-Fi News articles £0.30
16	Teak cabinet £7.35
	2 each of packs 1-7 inclusive are required for complete stereo system.

Basic Component Set

Set of semi-conductors, resistors, capacitors, printed circuit boards for stereo power amp, pre-amp. and power supply.

£31.35

Handbook Included

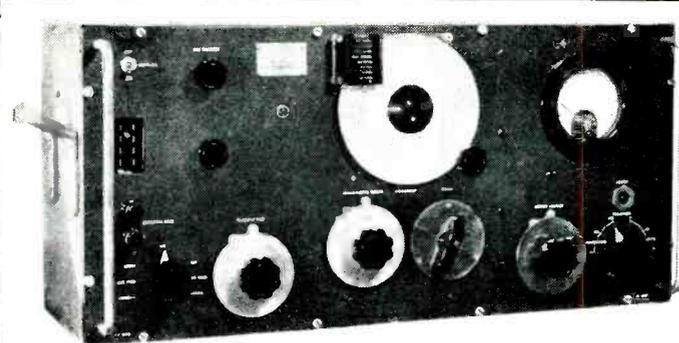

MARCONI SIGNAL GENERATOR TYPE TF-144G: Freq. 85 Kc/s-25 Mc/s in 8 ranges. Incremental: $\pm 1\%$ at 1 Mc/s. Output: continuously variable 1 microvolt to 1 volt. Output Impedance: 1 microvolt to 100 millivolts, 10 ohms 100mV - 1 volt - 52.5 ohms. Internal Modulation: 400 c/s sine wave 75% depth. External Modulation: Direct or via internal amplifier. A.C. mains 200/250V, 40-100 c/s. Consumption approx. 40 watts. Measurements 29 x 12 1/2 x 10 in. Secondhand condition. £27.50 each, Carr. £1.50.

T.1509 TRANSMITTERS (FOR EXPORT ONLY): General-purpose HF communications transmitter for use in fixed or mobile ground stations. Hand or high-speed keying. Crystal or MO control, with temperature compensated MO circuit. CW, MCW and R/T. Frequency: 1.5 to 20 Mc/s. Modulation: 100% O/p ut impedance: 50 ohms. Audio input: 600 ohms. Valves: Power Amplifier 2 x 813 and Modulator 2 x 813. Power requirements 200-250 volts a.c., 50 cycles. Power out put 300 watts. Dimensions 2ft. 6in. W. x 2ft. D. x 5ft. H. Weight: 800 lbs. Excellent condition, price £225.00 each.

AN/ARC-27 TRANSMITTER/RECEIVER (FOR EXPORT ONLY): Frequency 225-400 mc. 1750 channels 100 Kc apart with 18 preset channels. Modulation: am. Power output 9 watts. Receiver is superheterodyne. Max. output 2 watts. Antenna: 50 ohm impedance. Power requirements 24v d.c. Complete transmitter with operating cables, control box, headphones, microphone. Price £250.00 each secondhand, excellent condition.

POWER SUPPLY suitable for AN/ARC-27: 100 volts to 250 volts a.c. input. 24v d.c. output @ 41 amps fully smoothed. £45.00 each.

FREQUENCY METER BC-221: 125-20,000 Kc/s, complete with original calibration charts. Checked out, working order. £18.50 + £1.00 carr. BC-221 Unused as new condition complete with headset, spare valves, charts. £35.00 + £2.00 carr.

CT.52 MINIATURE OSCILLOSCOPE: Portable. Operates from 115V or 250V 50-60c/s; or 180V 500c/s. A small compact tropicalised instrument designed to meet requirements of radar and communication engineers and general electronic service. Measures 9 in. x 8 in. x 6 1/2 in. Time base 10c/s-40Kc/s. Y plate sensitivity 40V per cm. Tube 2 1/2 in. Frequency compensated amplifier up to 38dB gain. Bandwidth up to 1 Mc/s. Single sweep facilities. Complete with test leads, metal transit case. As new £27.50 each. Carr. £1.

TUNING UNIT: 24V geared motor driving double 25pf double spaced variable capacitor. One m/c relay and 2 other relays. £2.50 each 30p post, good condition.

UHF ASSEMBLY: (suitable for 1,000MHz conversion) including UHF valves: 2C42, 2C46, 1B40 (complete with associated capacitors and screening), 3 manual control 0-999. Valves 6AL5 and 8x6AK5. £10.00 plus 60p post, good condition.

MODULATOR UNIT: complete with transformer and 2x807 valves mounted in 19 in. chassis x 8 in. high x 8 in. deep. £4.50 secondhand cond., or £6.50 new cond. Carriage £1.

RF UNIT: suitable for use with the above unit. Complete with 2x3E29 valves. Ideal for conversion to 4 metres. £5 secondhand cond., or £7.50 new cond. Carriage £1.

POWER SUPPLY UNIT PN-12A: 230V a.c. input 50-60 c/s. 513V and 1025V @ 420 mA output. With 2 smoothing chokes 9H, 2 Capacitors, 10Mfd 1500V and 10Mfd 600V. Filament Transformer 230V a.c. input. 4 Rectifying Valves type 5Z3. 2 x 5V windings @ 3 Amps each, and 5V @ 6 Amp and 4V @ 0.25 Amp. Mounted on steel base 19"Wx11"Hx14"D. (All connections at the rear.) Excellent condition £6.50 each, carr. £1.

AUTO TRANSFORMER: 230-115V, 50-60c/s, 1000 watts, mounted in a strong steel case 5" x 6 1/2" x 7". Bitumen impregnated. £7 each, Carr. 75p. 230-115V, 50-60c/s, 500 watts. 7" x 5" x 5". Mounted in steel ventilated case. £4.00 each, Carr. 75p.

MODULATOR UNIT: 50 watt, part of BC-640, complete with 2 x 811 valves, microphone and modulator transformers etc. £7.50 each, 75p carr.

CATHODE RAY TUBE UNIT: With 3in. tube, Type 3EG1 (CV1526) colour green, medium persistence complete with nu-metal screen. £3.50 each, post 50p.

APN-1 INDICATOR METER, 270° Movement. Ideal for making rev. counter. £1.25, post 30p.

AIRCRAFT SOLENOID UNIT S.P.S.T.: 24V, 200 Amps, £2 each, 30p post.

DECADE RESISTOR SWITCH: 0.1 ohm per step. 10 positions. 3 Gang, each, 0-9 ohms. Tolerance $\pm 1\%$ £3 each, 25p post. 90 ohms per step. 10 positions, total value 900 ohms. 3 Gang. Tolerance $\pm 1\%$ £3.50 each, post 30p.

TF-1041B VALVE VOLTMETER: Measures 25mV to 300V, 20 c/s to 1500 Mc/s a.c. Also 10mV to 1000V d.c. Resistance 0.02 ohms to 500 Meg. ohms. Power requirements 200-250 volts a.c. Secondhand, excellent con. £35.00. Carr. £1.

VARIAC TRANSFORMERS: Input 115V, output 0-135V at 2 Amps. £3 each 75p post.

RACK CABINETS: (totally enclosed) for Std. 19 in. Panels. Size 6 ft. high x 21 in. wide x 16 in. deep, with rear door. £12 each, £2.50 Carr. OR 4 ft. high x 23 in. wide x 19 in. deep, with rear door. £8.50, each, £2 Carr.

INSTRUMENT CABINETS: 19"W. x 16"H. x 16"D. £5.00 + £1.25 carr. 19"W. x 10"D. x 5"H. £2.50 + £1.00 carr.

FUEL INDICATOR Type 113R: 24V complete with 2 magnetic counters 0-9999, with locking and reset controls mounted in 3in. diameter case. Price £2 each, 30p post.

TS-418/URM49 SIGNAL GENERATOR: Covers 400-1000MHz range. CW Pulse or AM emission. Power Range 0-120 dbm. £125 each. Carr. £1.50.

TN/130/APR.9 UHF TUNING UNIT: Freq. 4300-7350MHz. IF Output 160MHz with bandwidth of 20MHz and is electrically tuned by a d.c. reversible motor. £27.50 each. Carr. £1.

APR-4 AM RADIO RECEIVER: 90-1000MHz. This receiver is suitable for monitoring and measuring frequencies as well as relative signal strength. Power Supply 115V 50c/s. £100 each. Carr. £2.

SIGNAL GENERATOR TS-497B/URR: (Boonton). Freq. 2-400 Mc/s in 6 bands. Internal Mod. 400 or 1000 c/s per sec. External Mod. 50 to 10,000 c/s per sec. External PM. Percent Mod. 0-30 for sine wave. Am or Pulse Carrier. O/p ut Voltage 0.1-100,000 microvolts cont. variable. Impedance 50Ω. Price: £85 each + £1.50 carr.

CLASS "D" WAVEMETER NO. 1 MK. II: Crystal controlled heterodyne frequency meter covering 2-8MHz. Power supply 6V d.c. Good secondhand cond. £7.50 each. Post 60p.

RCA TE-149 HETERODYNE WAVEMETER: V-cut, 1MHz crystal (0-005%). Accuracy better than 0.02%. Dial directly calibrated every 1KHz from 2.5-5MHz. Useful harmonics up to 20MHz. Provision for fitting internal dry batteries. "As new" complete with Manual and Spares. £14 each. Carr. 75p.

POWER UNIT TYPE 24: (for R.216 Receiver) A.C. operated 100-125V or 200-250V, 50c/s. "As new" £10 each. Carr. 75p.

ROTARY INVERTERS: TYPE PE.218E—input 24-28V d.c., 80 Amps, 4,800 rpm. Output 115V a.c. 13 Amp 400 c/s. 1 Ph. P.F.9. £17.50 each. Carr. £1.50.

POWER SUPPLY: 230V a.c. input; 3000V @ 2.5mA; 4v @ 1 Amp, 300-0-300 200mA; 6V @ 7 Amp; 6V @ 3 Amp. With smoothing capacitors etc. £10.00 each. £1.50 carr.

ACTUATOR UNIT: With 115V d.c. geared motor; o/p ut 12.5 rpm; torque 16 ins. oz; reversible; microswitches and potentiometer. £3.50 ea. + 40p post.

DALMOTORS: 24-28V d.c. at 45 Amps, 750 watts (approx. 1hp) 12,000rpm. £5 each, 60p post.

MOTOR: 240V single phase, 2,400 rpm. 1/40 H.P. approx. Price £1.75 each, 30p post.

CONDENSERS: 30 mfd 600V wkg. d.c., £3.50 each, post 50p. 10 mfd 1000v wkg. 80p, post 30p. 8 mfd 2500v £5, carr. 80p. 8 mfd 600v 45p, post 15p. 8 mfd 1° 300v d.c., £1.25, post 25p. 4 mfd 3000v wkg. £3, post 50p. 4 mfd 2000v £2, post 40p. 4 mfd 600v, 2 for £1.00, post 30p. Capacitor 0.125 mfd 27,000v wkg. £3.75, post 50p. 2.25 mfd 25Kv wkg. £20, carr. £3. 2 mfd 12.5Kv wkg. TCC RL 7002-97, £8.50, carr. £1. 10 mfd 3Kv wkg. 55°C. TCC oil filled, £7.50, carr. £1. 5 x 1 mfd 3Kv wkg. 55°C. £6.50, carr. £1. 12 mfd 1500v d.c. wkg. £3.50, post 50p.

CONTROL PANEL: 230 v. A.C., 24 v. D.C. @ 2 amps, £2.50 each, carr. 75p.

OHMITE VARIABLE RESISTOR: 5 ohms, 5 1/2 amps; or 40 ohms at 2.6 amps; 500 ohms, 0.55 amps. Price (either type) £2 each, 30p post each.

TX DRIVER UNIT: Freq. 100-156 Mc/s. Valves 3 x 3C24's; complete with filament transformer 230 v. A.C. Mounted in 19in. panel, £4.50 each, carr. 75p.

AR88 RECEIVER: List of spares, 5p.

TELEPRINTER EQUIPMENT, REPERFORATORS, READERS, and AUTO TRANSMITTERS ETC. Send for list, 5p.

REDIFON TELEPRINTER RELAY UNIT NO. 12: ZA-41196 and power supply 200-250V a.c. Polarised relay type 3SEITR. 80-0-80V 25mA. Two stabilised valves CV 286. Centre Zero Meter 10-0-10. Size 8in. x 8in. X 8in. New condition £7.50, Carr. 75p.

WESTON INDUSTRIAL THERMOMETER MODEL 221: 0-100°C. 3in. dia. scale. Accuracy 1%. Precision made coil within-coil structure. Changes in temperature cause a rotary action of the Helix turning the shaft to which the pointer is mounted. £2.80 each 30p post. Unused condition.

TRANSMITTER UNITS: Complete with 12V vibrator unit QQVO3-20A and 5 other valves with modulation transformer, etc. Two crystal controlled channels. Suitable for conversion to 2 metres. £5 + £1 carr.

THERMOCOUPLE METER: Scale 3-5 AE 2in. square flush mounting. £2.50 + 25p post.

TS 15C/AP FLUXMETER: Used to provide qualitative measurements of flux densities between pole faces of magnets. Range 1200-9600 gauss. $\pm 2\%$. S/hand good cond. £25 + 60p post.

SYNCHRO DISTORTION AND MARGIN TEST SET: (Onwood Type 4A2) S/hand excellent cond. £85 each. Carr. £2.

MASTER SYNCHRO TEST SET T.101031 (U.S.A.): 115 volts 400 c/s. S/hand cond. £15 each + £1 carr.

MAGSLIP TESTER NO. 2 MK. I: S/hand cond. £25 each + £1 carr.

SYNCHROS: and other special purpose motors available. Send for list. S.A.E.

PANORAMIC ADAPTOR TYPE ALA2: Suitable for use with APR-1, APR-4, and other Receivers having an I.F. frequency of 30 MHz. Will display signals up to 5 MHz either side of the received frequency. Power Supply 115V a.c. 400 c/s. Tube 3PB1 with nu-metal screen. £8.50 each. £1 carr. S/hand cond.

MUIRHEAD PAMETRADA WAVE ANALYSER D-489-D: Primarily used for the analysis of complex vibration waveforms, but will measure audio and power frequency waveforms from 19 c/s to 21 kc/s. Complete with power supply unit 230 volts 50 c/s. S/hand good cond. £82.50 + £2 carr.

D-652 L.F. MODULATOR: Suitable for use with the above Wave Analyser D-489-D enabling the analysis of low frequencies between 2 and 20 c/s. S/hand good cond. £25 each + £1 carr.

AUTOMATIC VIBRATION EXCITER CONTROL UNIT TYPE 1016 Manufactured by Bruel & Kjoer. 5-5000 c/s. per second. S/hand very good cond. £90 + £2 carr.

INSULATION TEST SETS: A.C. or D.C. 0-5 kV. £22.50. S/hand cond. AND 0-3 kV. Positive and negative outputs, fine and course control. £17.50. S/hand cond. Carr. both types £2.

INSULATION TEST SET: 0-10 kV negative, earth with amplifier provision for checking ionisation. 110/230V a.c. input. S/hand good cond. £30 + £1 carr.

BOONTON SIGNAL GENERATOR TYPE 202B A.M./F.M.: 54-216 MHz in three bands. Deviation 24, 80 and 240 kc/s. Attenuator is adjustable 0.1 Uv to 0.2V. As new condition. £175 + £2 carr.

AVO FIXED ATTENUATORS: 75 ohms. £2.50 + 20p post. New cond.

R.F. POWER METER: 0-30 watts s/hand good cond. £27.50 + £1 carr.

AVO VALVE TESTER AND CHARACTERISTIC METER: S/hand good condition. £35 each + £2 carr.

AVO VALVE TESTER MK. III: £30 + £2 carr.

ALL U.K. ORDERS SUBJECT TO 10% VALUE ADDED TAX. THIS MUST BE ADDED TO THE TOTAL PRICE (including post or carriage).

If wishing to call at stores, please telephone for appointment.

W. MILLS

3-B TRULOCK ROAD, LONDON, N17 0PG
Phone: 01-808 9213 and Bedford 740605 (STD 0234).

New Branches BOLTON COVENTRY SUNDERLAND STOCKPORT
opening Sept. at **DONCASTER**

- BIRMINGHAM** 30-31 Gt. Western Arcade (Closed Wed.) Tel.: 236 1279
BOLTON 23 Deansgate (Closed Wed.) Tel: 33512
BRADFORD 10 North Parade (Closed Wed.)
COVENTRY 17 Shelton Square (Closed Thurs.) Tel: 25983
DARLINGTON 19 Northgate (Closed Wed.)
DERBY The Spot, 26 Osmaston Rd. (Closed Wed.) Tel.: 41361
DONCASTER 3 Queensgate, Waterdale Centre.
EDINBURGH 101 Lothian Road (Closed Wed.)
GLASGOW 326 Argyll St (Closed Tues.)
HULL 1 Whitefriargate (Closed Thurs.)
LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.) Tel. 28252
LEICESTER 32 High St. (Closed Thurs.)
LIVERPOOL 73 Dale St. (Closed Wed.)
LONDON 238 Edgware Rd. (Closed Thurs.)
MANCHESTER 60a Oldham St. (Closed Wed.)



HI-FI CENTRES LTD

- MAIL ORDERS to:**
 106 HENCONNER LANE, LEEDS 13.
 Terms C.W.O. or C.O.D. Postage 28p extra under £2. 33p extra over £2, or as stated. Trade supplied. S.A.E. with enquiries.
EXPORT ENQUIRIES WELCOMED
BRANCHES OPEN ALL DAY SATURDAYS AND OPERATE A 5-DAY WEEK
MAIL ORDERS NOT TO BE SENT TO SHOPS.
MIDDLEBRO 106 Newport Rd (Closed Wed.)
NEWCASTLE-ON-TYNE 24 Newgate Shopping Centre (Closed Wed.) Tel. 21469
NOTTINGHAM 19 Market St. (Closed Thurs.)
SHEFFIELD 13 Exchange St. (Closed Thurs.) Tel.: 20716
STOCKPORT 8 Little Underbank Tel. 490 0777 (Closed Thurs.)
SUNDERLAND 5 Market Square (Closed Wed.)

ALL PRICES INCLUDE VAT AND FULL LABOUR AND MATERIAL GUARANTEES.

HUGE DISCOUNTS ON LEADING BRAND TAPE AND TURNTABLE UNITS

- AKAI GXC 40D Tape Unit** £62.95 (Rec Price £89.74). Carr. £1.
AKAI 4000DS Tape Unit £68.95 (Rec Price £93.50). Carr. £1.
AKAI 1721L Tape Unit £66.95 (Rec Price £93.87). Carr. £1.
AKAI CR81D Tape Unit £58.95 (Rec Price £84.10). Carr. £1.
GOLDRING GL72 T/Table & P.U. £27.70 (Rec Price £37.29). Carr. 75p.
Also FREE with above GL72 Goldring G800 cartridge worth over £10
B.S.R. MACDONALD MP60 T/Table & P.U. £9.95 (Recom. Price £14.95). Carr. 40p.
CREDIT TERMS AVAILABLE. MINIMUM DEPOSIT 10%.
Above is only a selection of Discount Lines, also Leak, Wharfedale etc.
 Above discount prices correct at time of going to press.



R.S.C. G66 MkII 6+6 WATT STEREO AMPLIFIER
 High Quality Output. Rating I.H.F.M. Ind. Ganged Controls Bass Treble, Vol. and Balance. Solid state constr. employing 10 Trans plus diodes. Range 20-20,000Hz. Bass control ± 12 dB Treble ± 18 dB. Selector switch P.U. or Tape/Radio. Output for 3-15 ohm Standard 200-250v. 50 Hz mains operation. Attractive Black/Silver metal face plate and matching knobs.

COMPLETE KIT OF PARTS INC. FULLY WIRED PRINTED CIRCUIT £12.65 OR **FACTORY BUILT IN TEAK VENEERED CABINET £16.50**
 Dep. £2.50 & 9 mthly pymts £1.83 (Total £18.97)

FANE ULTRA HIGH POWER LOUDSPEAKERS

- Power Rating R.M.S. continuous. 2 years guarantee. Carr. free
- | | | |
|--------------------|--------------------|---------------------|
| 12" 'POP' 50 Watts | 15" 'POP' 60 Watts | 18" 'POP' 100 Watts |
| £11.99 | £14.75 | £25.95 |
| 15Ω | 8/15Ω | 8/15Ω |
| 13,000 Gauss | 14,000 Gauss | 14,000 Gauss |
- Or Dep. £2.99 and 9 monthly payments £1.28 (Total £14.51) Pair suitable for all purposes
 Or Dep. £3.75 and 9 monthly payments £1.50 (Total £17.25) **SUITABLE FOR BASS GUITAR, ELECTRONIC ORGAN, etc.**
 Or Dep. £5.95 and 9 monthly payments £2.56 (Total £28.99)

FANE MODE ONE HI-FI SPEAKER KIT
 Inc. 803 8" unit, 303 Pressure Tweeter, Printed circuit, inductive capacitive cross-over, acoustic filling, panels, screws, etc. **£9.96**
 Response **ONLY** £9.96
 30-20,000 Hz Post free

FANE SPEAKERS 'POP' 25/2
 12" 25 WATT Dual Cone. 15 ohms NOT for Bass Guitar.
£7.95 Or Dep. £1.25 and 9 monthly payments 29p (Total £9.25)

HI-FI SPEAKER ENCLOSURES
 Teak veneer finish. Pleasing design. Acoustically lined. All sizes approx.
 12B 16 x 11 x 9 in. Pressur. **£5.50**
 with 8 in. HI-FI Speaker. **£6.50**
 19 x 10 1/2 x 9 in. **£6.75**
 SE10 outstanding performance with HI-FI 10-in. speaker. 25 1/2 x 16 x 9 in. Ported. **£7.95**
 SE12 for high grade results with 12 in. HI-FI speaker and Tweeter. 25 1/2 x 16 x 9 in. Pressurised.

R.S.C. MAINS TRANSFORMERS

- FULLY GUARANTEED.** Interleaved and impregnated where necessary. Primaries 200-250v. 50 Hz. Screened MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 in.
- | | |
|---|-------|
| 250v., 60mA, 6.3v. 2a. | £1.10 |
| 250-0-250v., 80mA, 6.3v. 2a. | £1.16 |
| FULLY SHROUDED UPRIGHT MOUNTING | |
| 200-0-200v. 60mA, 6.3v. 2a., 0-5-6.3v. 2a. | £1.55 |
| 250-0-250v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. | £2.45 |
| 300-0-300v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. | £2.45 |
| 300-0-300v. 130mA, 6.3v. 4a., c.t., 6.3v. 1a. | £2.85 |
| For Mullard 510 Amplifier. | |
| 350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. | £2.45 |
| 350-0-350v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a. | £2.95 |
| 425-0-425v. 200mA, 6.3v. 4a. c.t., 6v. 3a. | £5.45 |
| 425-0-425v. 200mA, 6.3v. 4a., 0-5-6.3v. 3a., 5v. 3a. | £5.60 |
| 450-0-450v. 250mA, 6.3v. 4a., c.t., 6v. 3a. | £6.00 |
| TOP SHROUDED DROP-THROUGH TYPE | |
| 350-0-350v. 70mA, 6.3v. 2a., 0-5-6.3v. 2a. | £1.49 |
| 250-0-250v. 100mA, 6.3v. 3a. | £1.75 |
| 250-0-250v. 100mA, 6.3v. 2a., 6.3v. 1a. | £1.75 |
| 350-0-350v. 80mA, 6.3v. 2a., 0-5-6.3v. 2a. | £1.81 |
| 250-0-250v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. | £2.45 |
| 300-0-300v. 100mA, 6.3v. 4a., c.t., 6.3v. 1a. | £2.85 |
| Suitable for Mullard 510 Amplifier | |
| 350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. | £2.45 |
| 350-0-350v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a. | £2.85 |
| FILAMENT or TRANSISTOR POWER PACK Types | |
| 6.3v. 1.5a. 55p; 6.3v. 2a. 60p; 6.3v. 3a. 85p; | |
| 6.3v. 6a. £1.45; 12v. 1a. 61p; 0-9-18v. 1 1/2a. £1.25; | |
| 0-12-25-42v. 2a. £1.95; 12v. 3a. or 24v. 1.5a. £1.50; | |
| CHARGE TRANSFORMERS 0-9-18v. 1 1/2a. £1.10; | |
| 3a., £1.25; 3a., £1.40; 5a., £1.60; 6a., £1.85; | |
| 8a., £2.20. | |
| AUTO (Step UP/Step DOWN) Transformers | |
| 0-110/120v., 200-230-250v. 50-80 watts £1.25; | |
| 150w., £2.10; 250w., £3.00; 500w., £6.40 | |
| OUTPUT TRANSFORMERS | |
| Standard Pentode 5,000 Ω to 7,000 Ω 55p | |
| Push-Pull 8 watts EL84 to 3 Ω or 15 Ω 95p | |
| Push-Pull 10 watts 6V6 ECL86 to 3 or 5, 8 or 15 Ω £1.55 | |
| Push-Pull EL84 to 3 or 15 Ω 10-15 watts £1.50 | |
| Push-Pull Ultra Linear for Mullard 510, etc. £2.45 | |
| Push-Pull 15-18 watts, sectionally wound 6L6 KT66, etc., for 3 or 15 Ω £2.20 | |
| Push-Pull 20 watt high quality sectionally wound EL34, 6L6, KT66, etc. to 3 or 15 Ω £3.65 | |

BATTERY/MAINS CONVERSION UNITS
 R.S.C. BM1 battery eliminator completely replaces 1.5v. and 90v. Radio batteries where normal 200-250v. AC mains is available. **£4.15**
 Ready for use

LASKYS 1974 CATALOGUE

FREE Send this coupon with 15p for post and inclusion on our regular mailing list.

NAME

ADDRESS

AUDIOTRONIC HOUSE, THE HYDE, LONDON, NW9 6JJ

Contil INSTRUMENT CASES

New Textured Finish.

Type	1 off
755	£5 12
867/975	£5 56
1277 wh. or bl. etc.	£6 11
1277 unp.	£5 06
16127	£8 69
191010	£11 99
191010D	£15 35

Type No. indicates size XYZ in inches. Prices include VAT & p&p

Available in a range of seven sizes in 21 gauge Zinc: steel with new textured finish. Front panels are 18 gauge Zinc in white or PVC coated aluminium. Cases supplied with non-slip feet, ex stock by return of post. Please consult catalogue or ask for quote for larger quantities.

WEST HYDE

WEST HYDE DEVELOPMENTS LIMITED, RYEFIELD CRESCENT, NORTHWOOD HILLS, NORTHWOOD, MIDDX., HA6 1NN.
 Telephone: Northwood 24941/26732. Telex: 923231

WW-104 FOR FURTHER DETAILS

NEW GOOD LOOKS 'Brightcase'

Constructed in attractive anodised aluminium with black PVC coated steel panels, these cases are available in two heights and two widths. They can be used as free-standing instrument cases or by attaching the bolt on brackets as 19 inch rack mounting cases. Units come complete with front and rear panels and are delivered ex stock fully assembled.

BC21 (31" Whole Rack)	1 off incl. VAT and P & P	£9.74
BC22 (31" Half Rack)		£7.98
BC31 (51" Whole Rack)		£11.72
BC32 (51" Half Rack)		£9.74

Quantity Discounts

Rack Brackets 3 1/2" 66p per pair incl. VAT
 Rack Brackets 5 1/2" 94p per pair incl. VAT
 Add "L" for louvers 0.55p incl. VAT

WEST HYDE

WEST HYDE DEVELOPMENTS LIMITED, RYEFIELD CRESCENT, NORTHWOOD HILLS, NORTHWOOD, MIDDX., HA6 1NN.
 Telephone: Northwood 24941/26732. Telex: 923231

C. T. ELECTRONICS 267 ACTON LANE, LONDON W4 5DG 01-994 6275

MAIL ORDER DEPT./REGISTERED OFFICE/COMPONENT COUNTER

ANNUAL WAREHOUSE CLEARANCE SALE SAT. OCT. 8 - NOV. 3 TUES. - SAT. 10 a.m. - 5 p.m.

THOUSANDS OF BARGAINS

Test Equipment ★ Oscilloscopes ★ Signal Generators ★ Counters ★ Cabinets ★ Bridges
Meters ★ Transmitters ★ Receivers ★ Power Supplies ★ Laboratory Equipment ★ Galvanometers
Audio Equipment ★ Video Equipment ★ Meters ★ Battery Chargers ★ Motors ★ Etc. ★ Etc.

20 TONS OF ELECTRONIC COMPONENTS

Resistors ★ Relays ★ Capacitors ★ Switches ★ Transformers ★ Meters ★ Potentiometers
Component Panels ★ Semiconductor ★ Cable ★ Values ★ Etc. ★ Etc. ★ Etc.

Regret no lists available. Personal callers only. Cash and Carry only.

TEST EQUIPMENT

Manufacturer	Type	Price (ex V.A.T.)
EMI 9524H	Photomultiplier	£8
Teletrex 551	Oscilloscope and B+G Plug-in	£300
Teletrex 53/54B	Plug-in	£20
Teletrex 53/54E	Plug-in	£20
Croydon Precision Instruments KBI	Kelvin Bridge Ohmeter	£60
Vibro-Meter Corp. PBA-1/A	Bridge Supply and Indicator	£120
Muirhead 21-A	Varley/Wheatstone/Murray Bridge	£40
Emouzy E.I.L. 22B	Electronic Multimeter	£15
Marconi Mod. 12	Micouac Electronic Testmeter	£18
Cawkeil S.O.1.	AM/FM Signal Generator 35kHz-18.3MHz	£65
Teletrex 551	Storage Oscilloscope	from £75
Teletrex D. G	Oscilloscope and 2 x G Plug-in	£300
Teletrex 536	Plug-in units	ea. £25
Teletrex 661	X-Y Oscilloscope and 2 x B Plug-in	£300
Eddystone	Sampling scope and 5TA1 + 4S1 Plug-in	£450
Marconi TF 1100	Receiver 500-1000MHz	£275
Marconi TF428C	Sensitive Valve Voltmeter	£28
Marconi TF899	Valve Voltmeter	£18
Marconi TF887A	Valve Millivoltmeter	£12
Marconi	Valve Voltmeter	£12
Marconi TF1374	H.F. Absorption Wattmeter 52 ohm 1W/70 ohm 25W	£30
Pye	Precision Crystal Calibrator	£20
Advance MG5-40	Scalamp Galvo	£70
Marconi TF894	5V 40A Stabilized Power Pack	£50
Cossor R109AD5	Audio Tester	£60
Teletrex c 545	25W Transmitter	£225
H.P. 614A	Oscilloscope and G Plug-in	£85
Cohn	UHF Sig. Generator 750-2100MHz	£525
Marconi TF1272	D.C. Voltage Standard 10µV-1000V 6 decade	£24
Solartron JM1067	Transistor Test Set	£52
Solartron LM903	Precision RMS Millivoltmeter 3mV-300V	£50
Cossor R109 AB5 Mk. 3	AC Converter-Voltmeter	£50
Marconi TF144G	Receiver	£35
Cambridge	Standard Sig. Gen. 85kHz-25MHz	£18
Teletrex B. G. D. H	Spot Galvo 430 ohm	ea. £27
Advance PM48	Plug-ins	ea. £23
E.M.I. WM16	Stabilised Power Pack 15-30V 3A	£140
Baird & Tatlock	Oscilloscope and 7/6 Diff. Amp.	£50
Sullivan	0.1% Wheatstone Bridge	£75
Cambridge L358113	Standard Mica Capacitor 1mf. 4 decade	£58
Teletrex 107	Decade Bridge	£18
Marconi TF1041	Square Wave Generator	£30
Sony PV-120VE	Valve Voltmeter	£30
Marconi TF928	Broadcast Standard Videotape Recorder, 2in. tape; 625 line CCIR, 2 Audio Channels	£650
Solartron OS103	FM Deviation Meter 20-100MHz	£28
Ediswan R666	LF Decade Oscillator .01-11kHz 0.009-10V 4 phase and square wave outputs	£85
Marconi TF1165	L.F. Oscillator .15Hz-5kHz	£20
Sanders L026	Electronic Counter 7 digit 1MHz	£35
B.P.L. LC100-C	Lab. Magnetic Amplifier	£40
Roband V50/50	Coil Comparator, 1µH-100mH	£55
A.P.T. 2445	Stabilised Power Supply 0-500V 500mA	£50
Muirhead D-729	Twin Stabilised Power Supply 0-100V 250mA	£38
Farnell TSV12/2	Phasemeter and P.S.U.	£80
Airmec 252	Transistor P.S.U. 0-12V 2A Metered	£10
Marconi TF1300	A.F. Signal Generator 30-300kHz bal./unbal.	£28
E.M.I.	Vacuum Tube Voltmeter	£30
Wayne Kerr M121	14in. TV Monitor	p.o.A.
E.M.I.	AF Voltmeter	p.o.A.
	Magnetic Drum Delay Units (Studio Echo Units)	p.o.A.

This is just a sample list of Test Equipment available. We have hundreds of other items available. Enquiries welcome. Please telephone 01-994 6275.

LOW COST OSCILLOSCOPES

Cossor 1035, D.B.	Solartron CD643.2.
1049 Mk. 3A, D.B.	CD711S.2.
1049 Mk. 4, D.B.	EMI. WM2.
Solartron AD557.	WM3B.
CD513.2.	WM7.
CD523 S.2.	WN8.
CD643.	WM16.
	WM18.
	WM26.

All prices and details on application phone 01-994 6275. Inspection welcome—call at warehouse.

STABILISED D.C. POWER PACKS (Brand New)

Farnell IR 24/10 24V. 10 Amp.	£40
Farnell STE 234 30V. 1A. +10V. 2A.	£38
Coutant ED 200/12/12 5-30V. 2A. Dual supply	£45
Coutant ES 500/26 6-30V. 5A	£35
Coutant HTD 60/150/150 Dual supply	£35
A.P.T. SCV 32 FI 150V. 1/4A.	£20

COMMUNICATIONS EQUIPMENT

POCKET V.H.F. F.M. RADIOTELEPHONE

Cossor Type CC2/8 Mk. 2.
Fully transistorised transmitter/receiver available in two versions:—
Low band; Freq. range 71.5-104MHz, R.F. Output 500mW.
Complete with 1/2 wave whip aerial, combined microphone/loudspeaker and 13.3V. rechargeable nickel-cadmium DEAC battery.
Price £75 + v.a.t.

U.H.F. 2 watt FIXED RADIO LINK. 24V. dc./240V. ac. F.M. TRANSMITTER/Type CC RTX 4A Mk. 1
R.F. Output 2W at 450-470MHz.
RECEIVER/Type CCRR4A Mk. 1
Price £80.00 per unit

Full Technical and operating data available. Prices and details on request.
Mains Power Pack for the above £12.00 each

1 + 1 CARRIER EQUIPMENTS. Cossor Type CC M2A.
Solid state multiplex installations designed for U.H.F. radio systems enabling 2 speech channels each with out of band signalling, if required or the equivalent in telemetry information, to be transmitted simultaneously over a radio system. Prices and details on request.

V.H.F. RADIOTELEPHONE BASE STATION. Cossor Type CC 603 Transmitter. Simplex or duplex operation, local or remote control with talk through facilities, using double sideband a.m. modulation.

Low-band 71.5-104MHz. or High-band 156-174MHz. versions available.
RF. Output power 25W. into 50 Ohms.
24V. dc. operation.

Prices and details on request
OPTIONAL POWER SUPPLY Type CC 101 for type CC603 base station P.O.A.

SELECTIVE CALL SYSTEM. Coder Type CC 505/50 (50 way) or CC 505/100 (100 way). The Cossor selective call system may be used with any communication system where a base station is required to call any one or all of a number of sub-stations. Both versions available, all new and in original packing.
Price: 50 way £65 + v.a.t. 100 way £80 + v.a.t.

DECODERS £15 ea.
DEAC RECHARGEABLE BATTERY CASSETTES 13.4V (nom.) type B/SA 80351/108. Heavy duty encapsulated DEAC supply. Size 3 1/2 x 2 1/4 x 1 1/4 in. Price £5 + v.a.t.

8-WAY BATTERY CHARGER Type CC 999. Charges up to 8 of the above battery cassettes. Price £25 + v.a.t.

12-WAY BATTERY CHARGER Type CC 999. Charges up to 12 of 13.4V. DEAC batteries. Metered battery condition check. Price £35 + v.a.t.

MICROPHONES

S. G. Brown Stick Microphone and Stand. Push-to-talk button. 300Ω. £5 complete.

S. G. Brown Hand-held with push-to-talk button. £8 each.

SPECIAL OFFERS

BRIDGE RECTIFIER. 6A. 100V. Motorola MDA952-2 65p.

POWER SUPPLY. 12V. 6.5A. Stabilised Power Supply. Contains 18.5V. 8.5A. sec. Transformer, 4 x 4000µF 25V. Mullard capacitors, 2 x 2N3055 on 2 Redpoint heatsinks, 12A., 120V. Bridge rectifier, stabilised p.c.b. + circuit diagram. The parts alone are worth the asking price of £13 each inc. carriage.

SHACKMAN . . . AUTO CAMERA Mk. 3. Complete with long focus lens assembly. 4 Film Carriers. Boxed in as new condition. £75 each.

OC71 Transistors, unmarked. £15 per 1,000. HG5008 80mA 40V p.i.v. equiv. OA47. £20 per 1,000. S2B25 25A 200V Rectifier Diode. £2.50 per 4. S6 A20 20A 600V Rectifier Stack. £3 each. Transistor Mounting Pads. £2.50 per 500. Diode & Triac Mica Washer. £1 per 100. T.O.3 Transistor Socket. £1 per 50.

Send s.a.e. for free circuit diagram.

ELECTRONIC COMPONENTS BARGAIN COMPONENT PACKS

- Pack No.
- 500 Carbon resistors, 1/4, 1/2, 1, 2 watt.
 - 100 Electrolytic Condensers.
 - 250 Ceramic, Polystyrene, Silver Mica, etc., Condensers.
 - 250 Polyester, Polycarbonate, Paper, etc., Condensers.
 - 25 Potentiometers, assorted.
 - 250 High-stab. 1%, 2%, 5% resistors.
 - 50 Assorted Tagstrips.
 - 11b Assorted nuts, bolts, washers, spacers, etc.
 - 25 Assorted switches, rotary, lever, micro, toggle, etc.
 - 50 Preset Potentiometers.
 - 11 Trial mixed component pack £1.
 - 12 Jumbo mixed pack £5.

ALL COMPONENTS NEW AND UNUSED
£1 + 25p p.p. per pack, £5 for 5 packs p/free.

NOW OPEN:

AUDIO ACCESSORY SHOP

17 TURNHAM GREEN TERRACE, W.4.

HEADPHONES, MICROPHONES, SPEAKERS, etc., etc.

WAREHOUSE

20-24 BEAUMONT ROAD, W.4.

SURPLUS COMPONENTS, TEST EQUIPMENT, etc., etc.

BI-PRE-PAK

SUPPLIERS OF SEMICONDUCTORS TO THE WORLD



COMPLETE TELEPHONES
NORMAL HOUSEHOLD TYPE
AS SUPPLIED TO THE POST OFFICE
EX. G.P.O.

ONLY £1.05p
P & P 45p EACH



TELEPHONE DIALS

Standard Post Office type
Guaranteed in working order

ONLY 27 1/2p
P & P 16 1/2p EACH

TESTED AND GUARANTEED PAKS

- B79 **4** IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic **55p**
- B81 **10** Reed Switches 1" long 3/4" dia. High speed P.O. type **55p**
- B99 **200** Mixed Capacitors. Approx. quantity, counted by weight. P & P 15p. **55p**
- H4 **250** Mixed Resistors. Approx. quantity, counted by weight. P & P 15p. **55p**
- H7 **40** Wirewound Resistors. Mixed types and values **55p**
- H9 **2** OCP71 Light Sensitive Photo Transistor **55p**
- H28 **20** OC200/1/2/3 PNP Silicon uncodded TO 5 can **55p**
- H30 **20** 1 Watt Zener Diodes. Mixed Voltages 6.8-43V. **55p**
- H35 **100** Mixed Diodes. Germ. Gold bonded etc. Marked and Unmarked. **55p**
- H38 **30** Short lead Transistors. NPN Silicon Planar types **55p**
- H39 **6** Integrated circuits. 4 Gates BMC 962. 2 Flip Flops BMC 945 **55p**
- H40 **20** BFY50/2, 2N696, 2N1613 NPN Silicon uncodded TO-5 **55p**
- H41 **2** Power Transistors Comp. Pair BD 131/132 **55p**

UNMARKED UNTESTED PAKS

- B1 **50** Germanium Transistors PNP, AF and RF. **55p**
- B66 **150** Germanium Diodes Min. glass type **55p**
- B83 **200** Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ. **55p**
- B84 **100** Silicon Diodes DO-7 glass equiv. to OA200, OA202 **55p**
- B86 **100** Sil. Diodes sub. min. IN914 and IN916 types **55p**
- H6 **40** 250mW Zener Diodes DO-7 Min. Glass Type **55p**
- H15 **30** Top Hat Silicon Rectifiers. 750mA Mixed volts **55p**
- H16 **15** Experimenters Pak of Integrated Circuits. Data supplied **55p**
- H17 **20** 3 Amp. Silicon Stud Rectifiers. Mixed volts **55p**
- H26 **40** NPN Silicon Trans. 2N3707-11 range, low noise amp. **55p**
- H34 **15** Power Transistors. PNP, Germ. NPN Silicon TO-3 Can. P & P 5p extra. **55p**

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK' This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1.10 each



OVER 1,000,000 TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed Transistors. Power Transistors, Diodes and Rectifiers at very competitive prices. Please send for Free Catalogue.

Silicon Planar Plastic Transistors.

Unmarked, untested — factory clearance Audio PNP, similar to ZTX500, 2N3702/3, BCY70 etc. Audio NPN, similar to ZTX300, 2N3708/9, BC107/8/9, BC168/9 etc. R.F. NPN and Switching NPN.
Please state type of transistor required when ordering.

ALL AT 500 for £3.30. 1,000 for £5.50. 10,000 for £44.00.

OUR VERY POPULAR 4p TRANSISTORS

FULLY TESTED & GUARANTEED

- TYPE "A" PNP Silicon alloy, TO-5 can.
- TYPE "B" PNP Silicon, plastic encapsulation.
- TYPE "E" PNP Germanium AF or RF.
- TYPE "F" NPN Silicon plastic encapsulation.
- TYPE "G" NPN Silicon, similar ZTX300 range.
- TYPE "H" PNP Silicon, similar ZTX500 range.

Various Types
8 RELAYS FOR £1.10
Post & Packing 27 1/2p

Our famous P1 Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.1. Only **55p**
11p P & P on this Pak.



A CROSS HATCH GENERATOR FOR £3.85

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This was a project in the September 1972 edition of Practical Television.

This complete kit of parts costs £3.85, post paid.

A MUST for Colour T.V. Alignment.

ELECTRONIC TRANSISTOR IGNITION

Now in kit form, we offer this "up to the minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features: Transistor and conventional switchability, burglar proof lock up and automatic alarm, negative and positive compatibility. This project is a "star" feature in the September edition of "Electronics Today International" magazine. Our kit is recommended by the E.T.I. magazine.

Complete kit including P & P **£7.92.**
Ready built and tested unit **£3.02 EXTRA.**

FREE CATALOGUE

for TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS AND FULL PRE-PAK LISTS



Plastic Power Transistors



NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

RANGE 1 VCE. Min. 15	1-12	13-25	26-50
HFE. Min. 15			

40 Watt	22p	20p	18p
90 Watt	26 1/2p	24 1/2p	22p

RANGE 2VCE. Min. 40			
HFE. Min. 40			

40 Watt	33p	31p	29p
90 Watt	38 1/2p	36 1/2p	33p

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

INTEGRATED CIRCUITS

We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available.

This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc.
Pocket size **15p.** Wall Chart **18p.**

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at **16 1/2p** each } low new low profile type.
16 pin type at **18p** each

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:

B.P.1. Transistors Equivalents and Substitutes 40p. This includes many thousands of British, U.S.A., European and C.V. equivalents.

The Iltife Radio Valve and Transistor Data Book, 9th Edition 75p. Post & Packing 23 1/2p extra. Characteristics of 3,000 valves and tubes. 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits. Send for lists of these English publications. N.B. No V.A.T. to pay on books.

BUMPER BUNDLES

These parcels contain all types of surplus electronic components, printed panels, switches, potentiometers, transistors and diodes, etc.

2 LBS IN WEIGHT FOR £1.10

Post and packing 27 1/2p.

Please send me the FREE Bi-Pre-Pak Catalogue.

ALL PRICES INCLUDE 10% VAT

NAME

ADDRESS

MINIMUM ORDER 50p CASH WITH ORDER PLEASE.
Add 11p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE.

Buy these goods with Access.

BI-PRE-PAK LTD

DEPT. B, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

BEDFORD ELECTRONICS TEL.

7, PRIORY STREET, BEDFORD 51961

OSCILLOSCOPES

TEKTRONIX		
545 with 'L' P.I.U.	£200	
545 with 'C' P.I.U.	£220	
536 with 2 'K' & 'T' P.I.U.	£300	
551 with 2 'L' P.I.U.	£280	
Type 'Q' P.I.U. Brand New	£150	
HEWLETT PACKARD		
185B with 187B P.I.U.	£320	
188A P.I.U. & 1100A Delay line also available.		
TELEQUIPMENT		
S54U Mains/Battery	£150	
S31	£20	
D31	£35	

CARD READER

Data Products SPEEDREADER 300 Mechanism and Electronics P.O.A.

POWER SUPPLIES

MILES HIVOLT TH25 Regulated EHT supply 100V. to 25kV. @ 1mA., voltage and current meter, overload protection. AS NEW £160.
MILES HIVOLT TH20 Similar to above but 100V. to 20kV. @ 500µA., no meter. BRAND NEW £150.
A.E.I. R2325 2.5 to 30V. @ 10A. Regulated, fully adjustable supply, voltage and current meters £11. Callers only.
A.E.I. R2240. As above but 2A. £7. Callers only.

OTHER TEST EQUIPMENT AVAILABLE THIS MONTH

F. W. BELL 620 Gauss Meter.
B.P.L. FM405/C Frequency meter.
E.M.I. Type 6 Stroboscope.
DAWE 1202C Stroboscope and torch.
DAWE 1200S Stroboscope neon.
DAWE 1200D Stroboscope neon.
DAWE 412B Pulse Generator.
DAWE 1460B sound level meter.
DAWE 1401D A.F. analyser.
HEWLETT PACKARD 428A Clip on Ammeter.
HEWLETT PACKARD 456A Current probe.
MARCONI TF1400 Double pulse gen. with TM6600 Secondary pulse unit.

MARCONI TF1073 Attenuator.
MARCONI TF1041B Valve volt meter.
NAGARD 5002 Pulse Generator.
SOLARTRON S46 Oscillator.
VENNER TSA3336 Timer counter.
TELEQUIPMENT S42 Oscilloscope.
7J.0076 P.T.F.E. Equipment wire to EL1930 Type A £2 per 100 yds. Please check availability before ordering.

Colvern TEN TURN POTS. 500R. 5% Lin. 0.1%. £1.25 each.

Veeder Root 6 digit counters. Type LR1643. Mech. reset, 24V. Recent manufacture. As new £3 each.

Pressure transducers KDG, Type TD216. 0-1200 P.S.I. Complete with calibration chart. £5 each.

CARPENTERS polarised relay SPCO 2 x 1000R, complete with base and retainer as new. 45p each.

POT CORES LA3. 40p each.

METERS, 3/16in. diameter, sealed, 50-0-50 µA/1300R, £2.25 each. 1 mA/130R, £1.75 each.

BALL RACES Type RCL 1/4. Flanged 3/16in. bore 5/16in. dia. Sealed packs, 25p each.

PANEL FUSE HOLDERS with indicator lamp. The cap of these 1/2in. fuse holders is provided with an amber lens and min. flanged lampholder to allow a fuse failure neon to be fitted. Bulb not included. 20p each.

MINIATURE THUMB WHEEL SWITCHES, matt black, BCD and complement, as new. 70p each.

FLUID LOGIC teaching sets. These well made teaching aids contain the following components mounted on an engraved panel within a polished wooden box, 2 bistable, 1 and 3 or more logic elements, 2 press transmitters, 2 press receivers, 2 pressure regs. and gauges, 2 actuating cylinders and press. amplifiers, 4 position sensors. Supplied complete with all accessories £37.50.

V.A.T. PLEASE ADD 10% V.A.T. TO ALL PRICES.

MARCONI TF 807 SIGNAL GENERATOR
 Range: 15KHz to 30MHz. Output 0.4µV to 4V at 13 or 75 ohms. Impedance with termination (supplied). Built in crystal check facility with handbook. £138 including carr.

MARCONI CA 1094A/S H.F. SPECTRUM ANALYSER
 Carrier range: 3 to 30 Mc/s. Sweep width: up to 30 Kc/s. 60 dB amplitude differences measurable. P.O.A.

THERMOCOUPLES. Mineral Insulated Metal Sheathed. Conductors: Positive Nickel-Chromium. Negative Nickel-Aluminium. Conductor Diameter: .011 inch nominal. Tolerance: ± 3°C. up to 400°C. ± 2% between 400°C. and 1000°C. Length 3ft. 2in. (96 cm. approx.). £2.25 post paid.

NEUTRON COUNTING ASSEMBLY Mk. NNHA.
AMPLIFIER ASSEMBLY Mk. 112AA for Monitoring Equipment Type IN.C.A.
ALPHA COUNTER Mk. 11NH.
 More information and Price on request.

L.F. SOLARTRON DECADE OSCILLATOR TYPE OS103.2. Frequency range: 0.01 c.p.s.—111 c.p.s. In steps of 0.01 c.p.s. with multipliers of 10, 100 and 1000 giving a maximum frequency of 11.1 Kc/s. Frequency accuracy ± 1.5%. £90.

"WESTON" clear plastic meters 50-0-500µA type S.221-3.150 size 120 x 120 mm. £2.50 postage included.
 Also as above 20 V. M.C. size 60 x 60 mm. type S.2193.254. £1.95 post paid.

TEKTRONIX OSCILLOSCOPES TYPES:
 515A, 524AD, 543, 545, 545A, 545B. Plug-In Units: CA, G, 1A1, 10A1. P.O.A.

QUANTIZATION DISTORTION TESTER. Checks a.f. to a.f. distortion of p.c.m. systems. Utilises system power supply. Output level: Variable in 1 dB steps, from -20 to +2 dBm. Accuracy: ± 0.2 dB at +2 dBm. ± 0.5 dB incremental. Quantization distortion: 0 to -40 dB in 0.5 dB steps. Meter Indication: True r.m.s. Input impedance: 600Ω ± 10% balanced.

AVO MODEL 3 VALVE TESTER
 Enables comprehensive characteristics to be plotted, or measures valves on a simple good/bad basis. £55 incl. carr.

AVO CT 160 VALVE TESTER
 As above but in portable valise form as illustrated. Price £65 incl. carr.

AVO TRANSISTOR ANALYSER CT 406. £70 incl. carr.

GALVANOMETER by "Weston" scale 0-100 M.C. F.S.D. 200 µA., round 2 1/2in. £1.50 post paid.

Carriage extra for overseas orders. Inland V.A.T. add 10%. Please phone 01-540 9534

TRANSFORMERS

MAINS ISOLATING SERIES
 Primary 200-250 Volts Secondary 240 Volts Centre Tapped (120V) and Earth Shielded
 ALSO AVAILABLE WITH 115/120V SECONDARY WINDING

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P
07	20	1 11	7.0 x 6.0 x 6.5	1.94 30
100	60	3 8	8.9 x 8.0 x 7.7	2.88 36
61	100	5 12	10.2 x 8.9 x 8.3	3.16 52
30	200	9 8	12.0 x 10.3 x 10.0	5.31 52
62	250	12 4	9.5 x 12.7 x 11.4	7.61 67
52	350	15 0	14.0 x 10.8 x 12.4	9.40 82
63	500	27 0	17.1 x 15.9 x 13.5	*
92	1000	40 0	17.8 x 17.1 x 21.6	24.97 *
128	2000	63 0	24.1 x 21.6 x 15.2	41.25 *
129	3000	84 0	21.6 x 21.6 x 20.3	64.53 *
190	6000	178 0	31.1 x 35.6 x 17.1	105.89 *



440V 300VA ISOLATOR, Primary 440V Secondary 240V, Centre Tapped Screened and Shrouded, £11.40. P & P 67p.

AUTO SERIES (NOT ISOLATED)

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P
113	20	1 11	7.3 x 4.3 x 4.4	0-115-210-240	1.02 22
64	75	1 14	7.0 x 6.4 x 6.0	0-115-210-240	2.00 30
4	150	3 0	8.9 x 6.4 x 7.6	0-115-200-220-240	2.42 36
66	300	6 0	10.2 x 10.2 x 9.5	"	4.70 52
67	500	12 8	14.0 x 10.2 x 11.4	"	6.98 67
84	1000	16 0	11.4 x 14.0 x 14.0	"	12.69 82
93	1500	28 9	13.5 x 14.9 x 16.5	"	18.39 *
95	2000	40 0	17.8 x 16.5 x 21.6	"	24.00 *
73	3000	45 8	17.4 x 18.1 x 21.3	"	32.67 *

TOTALLY ENCLOSED 115V AUTO TRANSFORMERS
 115V 500 Watt totally enclosed auto transformer, complete with mains lead and two 115V outlet sockets. £9.49. P & P 67p
 Also available a 20 Watt version. £2.02. P & P 22p.

LOW VOLTAGE SERIES (ISOLATED) PRIMARY 200-250 VOLTS 12 AND/OR 24 VOLT RANGE

Ref. No.	Ampls.	Weight lb oz	Size cm.	Secondary Windings	P & P	
111	0.5	0.25	12	7.6 x 5.7 x 4.4	0-12V at 0.25A x2	1.02 22
213	1.0	0.5	12	8.3 x 5.1 x 4.0	0-12V at 0.5A x2	1.22 22
71	2	1	10	7.0 x 6.4 x 5.7	0-12V at 1A x2	1.60 22
18	4	2	2.4	8.3 x 7.0 x 7.0	0-12V at 2A x2	2.24 36
70	6	3	12	10.2 x 7.6 x 8.6	0-12V at 3A x2	2.70 42
108	8	4	5.4	10.0 x 8.3 x 8.2	0-12V at 4A x2	3.00 52
17	16	8	3	7.9 x 10.8 x 10.2	0-12V at 5A x2	3.55 52
17	16	8	7	8.9 x 9.5 x 10.2	0-12V at 10A x2	5.48 52
115	20	10	11.3	12.1 x 11.4 x 10.2	0-12V at 10A x2	6.98 67
187	30	15	16.12	13.3 x 12.1 x 12.1	0-12V at 15A x2	12.90 82
226	60	30	34	17.0 x 14.5 x 12.5	0-12V at 30A x2	23.72 *

30 VOLT RANGE

Ref. No.	Ampls.	Weight lb oz	Size cm.	Secondary Taps	P & P
112	0.5	1.4	8.3 x 3.7 x 4.9	0-12-15-20-24-30V	1.22 22
79	1.0	2.0	8.3 x 5.1 x 5.0	"	1.62 36
3	2.0	3.2	8.9 x 7.0 x 7.6	"	2.42 36
20	3.0	4.6	10.2 x 8.9 x 8.6	"	2.99 42
21	4.0	6.0	10.2 x 10.0 x 8.6	"	3.55 52
51	5.0	6.8	12.1 x 10.0 x 8.6	"	4.42 52
117	6.0	7.8	12.1 x 10.0 x 10.2	"	5.28 52
88	8.0	10.0	14.0 x 11.7 x 10.0	"	6.82 67
89	10.0	12.2	14.0 x 10.2 x 11.4	"	8.03 67

50 VOLT RANGE

Ref. No.	Ampls.	Weight lb oz	Size cm.	Secondary Taps	P & P
102	0.5	1.11	7.0 x 7.0 x 5.7	0-19-25-33-40-50V	1.60 30
103	1.0	2.10	8.3 x 7.3 x 7.0	"	2.34 36
104	2.0	5.0	10.2 x 8.9 x 8.6	"	3.25 42
105	3.0	6.0	10.2 x 10.2 x 8.3	"	4.41 52
106	4.0	9.4	12.1 x 11.4 x 10.2	"	5.84 52
107	6.0	12.4	12.1 x 11.1 x 13.3	"	8.63 67
118	8.0	18.9	13.3 x 13.3 x 12.1	"	11.27 97
119	10.0	19.12	16.5 x 11.4 x 15.9	"	14.13 97

60 VOLT RANGE

Ref. No.	Ampls.	Weight lb oz	Size cm.	Secondary Taps	P & P
124	0.5	2.4	8.3 x 9.5 x 6.7	0-24-30-40-48-60V	1.62 36
125	1.0	3.0	8.9 x 7.6 x 7.6	"	2.26 36
127	2.0	5.6	10.2 x 8.9 x 8.6	"	3.55 42
125	3.0	8.8	11.9 x 9.5 x 10.0	"	5.41 52
123	4.0	10.6	11.4 x 9.5 x 11.4	"	6.98 67
120	6.0	16.12	13.3 x 12.1 x 12.1	"	10.12 82
122	10.0	23.2	16.5 x 12.7 x 16.5	"	16.75 *

EQUIPMENT TRANSFORMER
 REF 238 PRI 0240 SCREEN SEC 3-0 3V RMS at 200mA SIZE CM 2.8 x 2.6 x 2.0 WEIGHT 2oz £1.19 P & P 10p.

LEAD ACID BATTERY CHARGER TYPES FOR CHARGING 6 OR 12VOLT BATTERIES

Ref. No.	Ampls.	Weight lb oz	Size cm.	P & P
45	1.5	1.9	7.0 x 6.0 x 6.0	1.61 30
5	4.0	3.11	10.2 x 7.0 x 8.3	2.45 42
86	6.0	5.12	10.2 x 8.9 x 8.3	3.70 52
146	8.0	6.4	8.9 x 10.2 x 10.2	4.22 52
50	12.5	11.14	13.3 x 10.8 x 12.1	6.29 67

All ratings are continuous. Standard construction: open with solder tags and wax impregnation. Enclosed styles to order.

TRANSISTORS

BC107/108/109 9-0p each	2N 3055 60p each	AD 161/162 60p pair
100+ 7.5p	with mica and bushes	with mica and bushes
25+ 5.5p	25+ 5.5p	25+ 5.5p
500+ 6.0p	100+ 4.5p	100+ 5.0p
Minimum order 10 pieces	500+ 4.0p	500+ 4.5p
this range.		1000+ 4.0p

★ **Quantity prices on application**
 Also stocked: SEMICONDUCTORS • VALVES
 AVOMETERS • ELECTROSIL RESISTORS

PLEASE ADD 10% FOR V.A.T. inc. P.&P.

*Carriage via B.R.S

BARRIE electronics

11 MOSCOW ROAD, QUEENSWAY
 LONDON W2 4AH Tel: 01-229 681/2

NEAREST TUBE STATIONS: BAYSWATER, QUEENSWAY

FOR THE STOCKS, THE DISCOUNTS AND THE SERVICE YOU NEED

ELECTROVALUE

Electronic Component Specialists

RESISTORS—10%, 5%, 2%

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	82Ω-220KΩ	E12	9	0	7.5
C	1/8W	5%	4.7Ω-470KΩ	E24	1	0.9	0.75 nett
C	1/4W	5%	4.7Ω-10MΩ	E12	1	0.9	0.75 nett
C	1/2W	5%	4.7Ω-10MΩ	E24	1.2	1	0.9 nett
C	1W	5%	4.7Ω-10MΩ	E12	2.5	2	1.6 nett
MO	1/2W	2%	10Ω-1MΩ	E24	4	3	2 nett
WW	1W	10% ± 1/20Ω	0.22Ω-3.9Ω	E12	7	7	6
WW	3W	5%	1Ω-10KΩ	E12	7	7	6
WW	7W	5%	1Ω-10KΩ	E12	9	9	8

Codes: C—carbon film, high stability, low noise.
MO—metal oxide, Electrosl TR5, ultra low noise.
WW—wire wound, Plessey.

Values:
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Priced in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.)

TRANSISTORS BY SIEMENS AND NEWMARKET

2N3055 npn silicon power	60p	BD135 npn medium power	37p
AC153K pnp germanium low power	32p	BD136 pnp medium power	38p
AC176K npn germanium low power	32p	DIODES	
AD161 npn germanium medium power	42p	OA90, OA91, OA95 each	6p
AD162 pnp germanium medium power	40p	OA200—9p; OA202—10p	
AF139 pnp germanium UHF	49p	Other semi-conductors	
BC107—13p; BC108—12p; BC109—13p	} npn	AC128—17p	AF117—32p
BC167—11p; BC168—10p; BC169—11p		} pnp	BFY51—19p
BC177—21p; BC178—19p; BC179—22p			
BC257—12p; BC258—11p; BC259—13p			

Standard groupings available.
Very many other types listed, described and illustrated in catalogue.

DIN CONNECTORS by Hirshmann 4A rating



2 way loudspeaker Socket	10p	Plug	12p
3 way audio Socket	10p	Plug	12p
5 way audio 180° Socket	12p	Plug	15p
5 way audio 240° Socket	12p	Plug	15p
6 way audio Socket	13p	Plug	15p

Lockable types, phono connectors, etc.


COVERS & HEATSINKS

T03 Transistor cover, clip-on 7p
HEATSINK
Type 6WV
Extruded aluminium
1°C/W, undrilled 60p
drilled 78p



TOGGLE SWITCHES

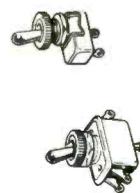1011C SPST toggle clip-on 7p
DPDT toggle 28p. (These are chrome plated, 2.5A rating). 7201 Sub-miniature DPDT 250V a.c./2A 48p



TTL ICs

IC	Price
7400	20p
7401	20p
7402	20p
7403	20p
7404	25p
7405	20p
7408	25p
7409	25p
7410	20p
7413	35p
7420	20p
7430	20p
7440	20p
74141 (16)	99p
7442 (16)	87p
7443 (16)	£1.00
7444 (16)	£1.36
7447	20p
7450	20p
7451	20p
7453	20p
7454	20p
7466	20p
7470	33p
7472	30p
7473	36p
7474	36p
7475 (16)	60p
7476 (16)	45p
7480	68p
7482	87p
7483 (16)	£1.32
7485	£1.70
7486	35p
7490	60p
7491AN	£1.00
7492	70p
7493	65p
7495	87p
7496 (16)	£1.00
74100 (24)	£1.64
74104	65p
74107	52p
74121	48p
74190 (16)	£1.80
74191 (16)	£1.80
74192 (16)	£1.74
74193 (16)	£1.74

POTENTIOMETERS carbon type

long spindles. Double wipers for low noise.

SINGLE GANG P20 linear 100Ω to 2.2MΩ, 12p, JP20 Log, 4.7KΩ, to 2.2MΩ 12p.


DUAL GANG linear 4.7KΩ to 2.2MΩ, 42p; Dual gang log, 4.7KΩ to 2.2MΩ, 42p; Log/antilog, 10K, 22K, 47K, 1MΩ only 42p; Dual antilog, 10K only, 42p. Any of above types with 2A D.P. mains switch, 12p extra. Only decades of 10, 22 & 47 available in ranges quoted.

DUAL CONCENTRIC DP20 in any combination of P20 values, 60p; with switch, 72p.

SLIDER POTS. In values from 4K7Ω to 1MΩ, linear or log, 26p. Escutcheon, white, grey, black, 10p. Knobs, flat, grip type, in 7 colours, 5p each.

SKELETON PRE-SETS. Small high quality, type PR linear only: 100Ω, 220Ω, 470Ω, 1K, 2K, 4K, 10K, 22K, 47K, 100K, 470K, 1M, 2M, 5M, 10MΩ. Vertical or horizontal mounting, 5p each.

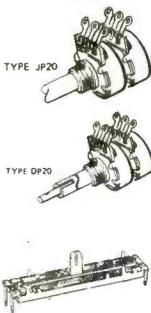NUTS, SCREWS, ETC. In lots of 100. Nuts 2BA—41p; 4BA—28p; 6BA—26p. Screws 1"—2BA—67p; 4BA—35p; 6BA—26p. 0.5"—2BA—50p; 4BA—23p; 6BA—19p. Screws roundheaded, cheese headed or countersunk. Other sizes available. Also tags, washers, spacers, etc.



ELECTROLYTICS

μF	Prices in pence							
	3V	6.3V	10V	16V	25V	40V	63V	100V
0.47							10	7
1.0						10	7	7
2.2					10	7	7	8
4.7				10	7	7	7	7
10				7	7	7	7	8
22			7	7	7	7	7	9
47	7		7	7	7	7	9	12
100	8	7	7	7	7	9	11	19
220	7	8	8	8	9	10	17	27
470	8	9	9	10	12	17	24	43
1000	10	12	12	17	20	24	40	
2200	14	17	22	25	36	40		
4700	25	28	37	41	54			
10,000	40	43						

Smallest size 3.7mm x 12mm. Largest size 25.5mm x 41mm. Full ranges of many other types of capacitors stocked.

ROTARY SWITCHES

Radiospares Miniature Maki-switch (in assembly kit form). Shaft 48p.
Wafers, MBB—2P5W, 1P 11W; BBM1P12W, 2P6W, 3P4W, 4P3W, 6P2W, each 32p.


Wavechange switches 1P12W, 2P6W, 3P4W, 4P3W, each 24p.

3 New Babani Books
BP.13 Electronic Novelties for the Motorist; BP.15 Constructor's Manual of Electronic Circuits for the Home; 200 Handbook of Electronic Musical Novelties: EACH 50p (no V.A.T.).



KNOBS

(for 0.25 shafts)

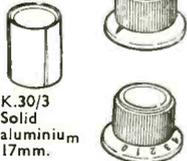

K.30/3 Solid aluminium 17mm.

F.14 skirt dia. 20mm.	32p
F.13 skirt dia. 26mm.	38p
F.12 skirt dia. 33mm.	40p
F.19 engraved 20mm.—two	32p
F.18 engraved. 26mm.—two	38p
F.17 engraved. 33mm.—two	40p



KB.4 Ribbed Skirt dia. 20mm. 4 in pack. 40p

Very many other types in stock—see Catalogue.



Minitron DIGITAL INDICATOR

TYPE 3015F Seven segment indicator compatible with standard logic modules and power supplies. Figs. 0-9 from well illuminated filament segments to give character of 9mm height plus decimal point. Power requirement 8mA from 5V D.C. per segment. A limited number of alphabetical symbols also available. In 16 lead DIL case £2.00
Suitable BCD decoder driver type FLL121T £1.36
DIL Socket; 16 lead 30p. No. 3015G showing + or — and fig. 1 and decimal point £2.00. nett

DISCOUNTS

Available on all items except those shown with NETT PRICES. 10% on orders from £5 to £15. 15% on orders £15 and over.

TERMS OF BUSINESS

All items are offered for sale in accordance with our standard terms of business, a copy of which is available on request. Prices subject to alteration without notice. Enquiries from quantity users invited.

PACKING & POSTAGE

FREE in U.K. For mail orders for £2 list value and under, there is an additional handling charge of 10p.

V.A.T.

Please add 10% to nett value of order to meet tax requirements.

Not applicable to overseas orders.

ZENER DIODES

Full range E24 values: 400m W: 2.7V to 36V, 14p each; 1W: 6.8V to 82V, 21p each; 1.5W: 4.7V to 75V, 48p each. Clip to increase 1.5W rating to 3 watts (type 266F) 4p.

SIEMENS THYRISTORS

0.8A 400V, 56p; 600V 70p. 3A 400V, 60p; 600V, 88p.

DE-SOLDER BRAID 6ft. nett 50p

S-DEC

Unsurpassed for "breadboard work" can be used indefinitely without deterioration. Components just push into plug holes and connect automatically. Slot for control panel. 70 holes. £1.80.

T-DEC

For more advanced work with 208 contacts in 38 rows. Will take one 16 lead carrier. £3.30. (Carriers supplied separately.)

BAXANDALL SPEAKER

As described originally in "Wireless World" and still one of the most brilliant designs in high quality low priced speakers. You save by assembling it yourself. 10 watts/15Ω.

Complete kit £14.90+60p part carr. Equaliser components £2.00. Speaker unit £2.45.

No. 6 CATALOGUE SUPPLEMENT

of latest price adjustments and new items. S.A.E. for your copy.

MAINS TRANSFORMERS

MT3 30V/2A plus 4 taps £2.85
MT103 50V/1A+4 taps £2.55
MT104 50V/2A+4 taps £3.50
MT127 60V/2A+4 taps £3.80
13T05 13V/1A, CT £1.25
28T05 12+12; 2.0-2V/1A £1.60

U.S.A. CUSTOMERS are invited to contact Electrovalue America, P.O. Box 27, Swarthmore, PA.

ELECTROVALUE LTD

(DEPT. WW.4), 28 ST. JUDES RD, ENGLEFIELD GREEN, EGHAM, SURREY, TW20 0HS
Hours: 9-5.30, 1.0 p.m. Saturdays.
Reg. offices at above address Business Reg. No. 1047769

ELECTRONIC ORGAN DIVIDER BOARDS built to high industrial/computer spec. 5 octave set £15. Complete with connection data and oscillator details.

COPPER LAMINATE P.C. BOARD
 8½ x 5½ x 1/16 in. 12½p sheet, 5 for 50p
 11 x 6½ x 1/16 in. 15p sheet, 4 for 50p
 11 x 8 x 1/16 in. 20p sheet, 3 for 50p
 16½ x 4 x 1/16 in. (Fibreglass), 30p sheet.
 Offcut pack (smallest 4 x 2 in.) 50p 300 sq. in.
 P&P single sheet 4p. Bargain packs 10p

SPEAKERS AND CABINETS
E.M.I. 13 x 8 in. (10 watt) with two tweeters and cross-over 3/8/15 ohm models. £3.75. P.P. 25p.
E.M.I. 20 watt (13 x 8 in.) with single tweeter and "X-over" 20 Hz to 20,000 Hz. Ceramic magnet 11,000gss. £8. P.P. 40p. 20 watt base unit only. £6. P.P. 40p.
CABINETS for 13 x 8 in. speakers manufactured in ½ in. teak-finished blockboard. Size 14 x 10½ x 9 in. £5 ea. P.P. 40p.
20W. CABINET. 18 x 11 x 10 in. £6. P.P. 50p.

HIGH-SPEED MAGNETIC COUNTERS. 4 digit (non reset) 24v. or 48v. (state which) 4 x 1 x 1 in. 40p. P.P. 5p.

5 digit (non-reset) 6-12-24-48v. (state which) 75p. P.P. 5p.

5 digit (Reset) 12v. £3. P.P. 5p.



PRECISION CAPACITANCE JIGS. Beautifully made with Moore & Wright Micrometer Gauge. Type 1. 18.5pf. to 1,220pf £10 each Type 2. 9.5pf. to 11.5pf. £6 each.

MULTICORE CABLE (P.V.C.).
 6 core (6 colours) 3 screened, 14/0048. 15p. yd. 100 yds. £12.50.
 24 core (24 colours) 20p. yd. 100 yds. £17.50.
 30 core (15 colours) 25p. yd. 100 yds. £18.50.
 34 core (17 colours) 22p. yd. 100 yds. £20.
 Minimum order 10 yds.

TELEPHONE DIALS (New) £1 ea.

RELAYS (G.P.O. '3000'). All types. Brand new from 37½p ea. 10 up quotations only. **EXTENSION TELEPHONES (Type 706)** New/Boxed. £5. 50p.
RATCHET RELAYS. (310 ohm) Various Types 85p. P.P. 5p.
UNISELECTORS (Brand new) 25-way 75 ohm. 8 bank ½ wiper £3.25. 10 bank ½ wiper £3.75. Other types from £2.25.



PRECISION A.C. MILLIVOLTMETER (Solartron) 1.5m.v. to 15v; 60db to 20db. 9 ranges. Excellent condition. £22.50. P.P. £1.50.

HIGH CAPACITY ELECTROLYTICS
 2,200µf. 100v. (1½ x 4in.) 60p. 3,150µf. 40v. (1½ x 4in.) 60p. 10,000µf. 25v. (1½ x 4½in.) 60p. 10,000µf. 100v. (2½ x 4½in.) £1. 12,000µf. 40v. (2 x 4in.) 75p. 16,000µf. 17v. (2 x 4in.) 60p. 21,000µf. 40v. (2½ x 4in.) £1. Post and packing 5p.

MINIATURE UNISELECTORS (A.E.I. 2203A). 3 bank. 12 position, non-bridging wipers. £4.25 ea. Brand new. Complete with base.

CD.1220 OSCILLOSCOPE, with dualtrace Plug-in. (CX1257) DC-24MHZ. £125.
 Wide band Plug-in (CX1256) DC-40MHZ. £25.

SOLARTRON OSCILLATOR (COS46) 25Hz-500KHz £50.

OVERLOAD CUT-OUTS. Panel mounting (1½ x 1½ x ½ in.) 800 M/A/1.8 amp/10 amp. 35p ea. P.P. 5p.

BULK COMPONENT OFFER. Resistors/Capacitors. All types and values. All new modern components. Over 500 pieces £2. (Trial order 100cps. 50p.) We are confident you will re-order

TWIN STABILISED POWER SUPPLIES (A.P.T.) +80v. @ 500 M/A. —80v @ 500 M/A (9 x 6 x 5½ in.) New. £8.50 with spec. & circuit.

TRANSFORMERS

L.T. TRANSFORMER. Prim. 240v. Sec. 24v. 1½ amp. £1. P.P. 20p.
250 WATT ISOLATION TRANSFORMER. 240v. double wound. £3.25. P.P. 50p.
E.H.T. TRANSFORMER. Prim. 240v. Sec. 2.5-0-2.5 kV. 12 mA. 7.5v. 1 amp. 2.5v. 2 amp. £2.50. P.P. 25p.
E.H.T. TRANSFORMER. Prim. 240v. Sec. 1800v. 50 mA. £2.50. P.P. 35p.
L.T. TRANSFORMER. (Shrouded) Prim. 200/250v. Sec. 20/40/60v. 2 amp. £2 ea. P.P. 40p.
L.T. TRANSFORMER (CONSTANT VOLTAGE). Prim. 200/240v. Sec. 1. 50v. at 2 amp. Sec. 2. 50v. at 100 mA £3. P.P. 50p.
L.T. TRANSFORMER. Prim. 110/240v. Sec. 2x32v. @ 4 amp. 20v. @ 5 amp.; 15v. @ 1.5 amp.; 7v. @ 2.5 amp. £3. P.P. 50p.
L.T. TRANSFORMER. Prim. 220/240v. Sec. 13v. 1.5 amp. 65p. P.P. 15p.
L.T. TRANSFORMER. Prim. 115/240v. Sec. 10-5v. at 1 amp. c.t. 28-0-28v. at 2 amp. shrouded type. £2. P.P. 40p.
2500 watt. ISOLATION TRANSFORMER (CONSTANT VOLTAGE). Prim. 190-260v. 50Hz. Sec. 230v. at 10-9 amps. £30. Carr. £2.
H.D. STEP-DOWN TRANSFORMER. Prim. 200/240v. Sec. 117v. at 19-8 amps. (2,300 watt). £22.50. Carr. £2.
H.T. TRANSFORMERS. Prim. 200/240v. Sec. 300-0-300v. 80 mA. 6.3v. c.t. 2 amp. £1.50 P.P. 40p. 350-0-350v. 60 mA. 6.3v. c.t. 2 amp. £1. P.P. 25p.
STEP-DOWN TRANSFORMERS: Prim. 22/240v. Sec. 115v. Double wound 500w. £5. P.P. £1. 700w. (with filters) £10. P.P. £1. 500w. (metal cased with socket output) and overload protection. £6.50.
AUTO-WOUND. 75W. £1. P.P. 25p. 300W. £1.50. P.P. 50p. 750W. £6. P.P. £1.
L.T. TRANSFORMER. Prim. 110/240v. Sec. 0/24/40v. 1.5A. (Shrouded type) £1.50. P.P. 25p.
HT/LT TRANSFORMER. Prim. 240v. (tapped) Sec. 1. 500-0-500v. 150 mA. Sec. 2. 31v. 5 amp. £2.75 P.P. 50p.
AUTOMATIC VOLTAGE STABILISER. (Claude Lyons) Input: 190-260v. Output 240v. ± 15%. 12.4 K.V.A. £60.

BLOWER FANS (Snail type) Type 1: Housing dia. 3½ in. Air outlet 1½ x 1 in. £2.25. P.P. 25p. Type 2: Housing dia. 6 in. Air outlet 2½ x 2½ in. £4. P.P. 50p. Both types 115/240v. A.C. (brand new).

"PAPST TAPE" MOTORS. (LZ. 20.50) New Boxed. £2. P.P. 25p.

RELAYS
SIEMENS/VARLEY PLUG-IN. Complete with transparent dust covers and bases. 2 pole c/o contacts 35p ea.; 6 make contacts 40p ea.; 4 pole c/o contacts 50p ea. 6-12-24-48v types in stock.
12 VOLT H.D. RELAYS (3x2x1 in.) with 10 amp. silver contacts 2 pole c/o 40p ea.; 2 pole 3 way 40p. P.P. 5p.
24 VOLT H.D. RELAYS (2x2x½ in.) 10 amp. contacts. 4 pole c/o 40p ea. P.P. 5p.
240v. A.C. RELAYS. (Plug-in type). 3 change-over 10 amp. contacts. 75p (with base). P.P. 5p.
SUB-MINIATURE REED RELAYS (1 in. x ½ in.) Wt. ½ oz. 1 make 3/12v. 40p. ea.
SILICON BRIDGES. 100 P.I.V. 1 amp. (½ x ½ x ½ in.) 30p 200 P.I.V. 2 amp. 60p.
24 VOLT A.C. RELAYS (Plug-in).
 3 Pole Change-over 60p.
 2 Pole Change-over 45p.

U.K. ORDERS 10% V.A.T. SURCHARGE

PATRICK & KINNIE
 191 LONDON ROAD · ROMFORD · ESSEX
 ROMFORD 44473 RM7 9DD

200-250V AC MAINS TO 27V 500mA D.C. STABILISED P.S.U.

With circuit. These interesting 27v 0.5A units (will happily provide 700mA indefinitely) are built into an attractive grey-finished instrument case, provision being made for base or side mounting. Cable entry grommets are mounted in the base of the unit. The choke capacity smoothed output is solid state stabilised against variation in input voltage and output current, and input and output fuses with spares are fitted. The output operates a built-in S.P.C.O. relay to switch for instance an alarm circuit. There is adequate room for other equipment within the ventilated case, which is 12" x 10" x 6" deep.

£4.15 EACH (P.Pd U.K.)

OVER 300,000 IN STOCK!
 Multiway and R.F. Connectors by twenty different companies!
 Send us your detailed requirements quoting Nato numbers if known. We are now on TELEX.

ELECTROSIL METAL OXIDE RESISTORS. Most values in stock, 2 or 5% tolerance as available. Type TR4/MR4 £5 per 100. Type TR5/MR5 £1.50 per 100 both inc. P. & P. U.K. Minimum order 100 of any value; for orders of over 1000 (up to 10 values above prices) see 103.

AMP PATCHBOARDS Type 695448-3 and 695365-2 £27.50 each. P.P.

EHT TRANSFORMER by Foster. Pri. 250v (tapped) Sec. 30kV CT earth at 1kV plus 8v (CTE) 12A £34.50 (C.Pd.)

PRESSURE TRANSDUCERS. We now have a wide range in stock. List on application, or send us your requirements.

PTFE INSULATED EQUIPMENT WIRES to DEF Specs. Various types available from £2 per 100 yds. We also have steel cored equipment wires designed for weapon applications.

FIELD STRENGTH METER Type CT10 covering 20-650 MHz with dipoles, tripod, mixer units and CRT Display.

RECORDERS of many types available; single and multi channel—even recorders—temperature recorders—pressure recorders. Please let us quote for your needs!

MARK IV MULTIWAY PLUGS AND SOCKETS

Size 1	Size 2	Size 3
2 way 19A	4 way 19A	18 way 5A
3 way 5A	6 way 5A 2kV	25 way 5A
4 way 5A	12 way 5A	

All poles rated at 250v.

The above are available for chassis mounting plug or socket with the free member fitted with straight or angle outlet. Prices: Size 1 £1 per pair. Size 2 £1.25 per pair. Size 3 £1.50 per pair. Cable type and diameter should be quoted when ordering. Alternatively please quote Mfrs' or Ministry Numbers. These connectors are also in stock in Brass shells. All types may be orientated in any one of six positions to prevent mismatch.

RACAL SSB CONVERTERS Type RA98A. Excellent used condition £35 each. (C.Pd. Eng. and Wales).

AERIAL DIRECTION INDICATING KIT
 This comprises a pair of Magslips to provide remote indication of aerial azimuth and comprises a transmitter and receiver. The transmitter is directly coupled to the remote aerial and the receiver can be mounted at the control point, to provide immediate and continuous indication of aerial position. Supply voltage required is 50v. 50Hz and the price £6.33. (P.Pd.) including a pointer for the receiver. The suggested use of these items would include a mains operated, geared motor to drive the aerial, controlled from the position to which is fed back information by the magslip link. Transformers to provide 50v 50Hz from 240v A.C. £2.15 each. (P.Pd.)

MIL SYNCHROS AVAILABLE EX-STOCK
 In sizes 08, 11, 15, 16, 18 and 23 for 50, 60 and 400 Hz operation.
Synchro Control Transformers
Synchro Control Differential Transmitters
Synchro Torque Transmitters and Receivers
Synchro Resolvers

WE ARE ANXIOUS TO BUY Synchro Test Equipment manufactured by Muirhead, Singer-Gertsch etc. Test Dials, Dividing Heads, Bridges, Standards etc. to expand our testing facilities.

EVERSHED AND VIGNOLLES special purpose and servo motors in stock also Velodyne Motor Generators and Split Field Motors by other Manufacturers for immediate delivery.

RADAR CABLEFORM INSULATION TESTER for checking insulation between individual conductors and each other and ground at preselected voltages. Full details on application.

DRI D150 Computer tape evaluation equipment, one installation in stock in excellent condition.

LEMANIA AIRCURE CHRONOGRAPHS, Stainless Steel case with screw back; luminous hands and markings. One fifth sec. sweep hand controlled independently of main movement by press to start, stop and return to zero button. 15 jewel movement. Many of these watches are as new but all have been cleaned and checked. Fitted strap. White face £18.55, Black Face £19.50 inc. P. & P.

GS WATCHES all with brushed stainless steel case with screw back and black faces. Manufactured by CYMA, VERTEX, TIMOR, GRANA, JWC, RECORD, SMITHS etc. to a common specification. We will try to meet your requirements for specific manufacturer and quantity orders will be of one manufacturer's production. All cleaned and checked. Fitted Strap. £8.95 inc. P. & P.

We also have limited quantities of these watches by OMEGA, LONGINES, BUREN, JAEGER LE COULTRE at £15.50 inc. P. & P.

LEMANIA STOPWATCHES fitted with one red and one black sweep hands independently controlled enabling elapsed periods forming part of the main period to be measured separately without stopping the measurement of the main time period. Absolutely mint condition but cleaned and checked £8.25 inc. P. & P.

WE HAVE ONE OF THE LARGEST STOCKS IN THE COUNTRY OF INSTRUMENTS AND COMPONENTS MANUFACTURERS. TELEX 965265. FOR AVAILABILITY CHECK.

ADVANCE RADIO INTERFERENCE MEASURING SETS CT535. These enable the frequency and level of equipment generated interference to be measured. The instrument is modern and portable and is offered at about 20% of the cost of similar equipment at present available. £49.50 (plus carriage at cost). Cover 50kHz to 30MHz.

VACTRIC SIZE 23 PULSE GENERATORS (Shaft Digitizers). Two outputs each of 250 square wave pulses per 360° displaced by 2 pitch. New with test chart. P.O.A.

STAINLESS STEEL VACUUM CONTAINERS FOR LIQUIDS. Capacity 2 U.S. galls. fitted with delivery taps. Brand new in cartons—£22.50 (C. Pd. U.K.)+10% V.A.T.

MULTICORE PVC COVERED TELEPHONE CABLE 24 core £24.20 per 100 yds, 12 core £19.80 per 100 yds, 8 core £13.20 per 100 yds, 4 core £11 per 200 yds, 2 core £3.30 per 100 yds. (All C. Pd. U.K. Mainland).

HEAVY DUTY PVC INSLTD. FLEXIBLE CABLE to DEF 12D Type 3 in following colours: violet, yellow, white, grey, orange, pink, red and brown 70/0076 conductors £3.25 per 100 yds (P.Pd.) also with 40/0076 conductors in grey, violet, white, pink and red at £2.50 per 100 yds. (P.Pd.)+10% V.A.T.

ALL PRICES INCLUDE 10% V.A.T.

DRY REED INSERTS



Overall length 1.85" (Body length 1.1")
Diameter 0.14" to switch up to 500 mA at up to 250V D.C. Gold clad contacts, 69p per doz.; £4.12 per 100; £30.25 per 1,000; £275 per 10,000. All carriage paid U.K.
 Heavy duty type (body length 2") diameter 0.22" to switch up to 1A. at up to 250V A.C. Gold clad contacts, £1.37 per doz.; £6.88 per 100; £52.25 per 1,000; £495 per 10,000. Changeover type £2.75 per doz. All carriage paid U.K.
Operating Magnets 61p per doz.; £4.40 per 100; £38.50 per 1000. All carriage paid.

SPECIALIST STOCKISTS OF SERVOMOTORS, SYNCHROS, MAGSLIPS & CONNECTORS

Servo and Electronic Sales Ltd

Post Orders and Technical enquiries to: "BAYS", HIGH ST., LYDD, KENT. Lydd 20252 (STD 0679)
 Or 67 LONDON ROAD, CROYDON, SURREY (Retail and Instrument Repairs). Phone: 01-688 1512
 V.A.T. Reg. No. 201-1296-23

BRAND NEW SEMICONDUCTORS & COMPONENTS GUARANTEED

WE SUPPLY NEARLY ALL THE COMPONENTS FOR PROJECTS ADVERTISED IN THIS MAGAZINE

TRANSISTORS

2G301	0.15	2N3403	0.19	40316	0.50	BC121	0.23	BDY18	1.75	BSX61	0.42
2G302	0.15	2N3404	0.24	40318	0.92	BC125	0.15	BDY19	1.97	BSX76	0.15
2G303	0.25	2N3405	0.27	40360	0.46	BC126	0.20	BDY20	0.05	BSX77	0.20
2G306	0.30	2N3414	0.10	40361	0.43	BC132	0.50	BDY38	1.65	BSX78	0.25
2G309	0.30	2N3415	0.10	40362	0.45	BC134	0.11	BDY60	0.90	BSW70	0.28
2G345B	0.25	2N3416	0.15	40363	0.88	BC135	0.11	BDY61	1.25	BSY24	0.20
2G371	0.15	2N3417	0.21	40389	0.46	BC136	0.15	BDY62	1.00	BSY25	0.15
2G374	0.15	2N3570	1.25	40394	0.56	BC137	0.15	BF115	0.23	BSY26	0.20
2N174	1.40	2N3571	1.12	40395	0.65	BC138	0.24	BF117	0.43	BSY27	0.15
2N404	0.43	2N3572	0.97	40406	0.44	BC140	0.34	BF119	0.58	BSY28	0.15
2N456	0.75	2N3702	0.11	40407	0.33	BC141	0.39	BF121	0.25	BSY38	0.20
2N456A	0.80	2N3703	0.10	40410	0.53	BC142	0.24	BF123	0.27	BSY39	0.20
2N457A	3.25	2N3704	0.14	40411	2.00	BC143	0.21	BF125	0.25	BSY51	0.25
2N491	0.15	2N3705	0.10	40414	3.55	BC144	0.24	BF152	0.20	BSY52	0.25
2N696	0.15	2N3706	0.09	40414	3.55	BC145	0.21	BF153	0.29	BSY53	0.25
2N697	0.15	2N3707	0.10	40414	3.55	BC147	0.12	BF154	0.16	BSY54	0.30
2N698	0.25	2N3708	0.70	40467	0.69	BC148	0.12	BF158	0.23	YS56	0.79
2N699	0.20	2N3709	0.09	40468A	0.44	BC149	0.12	BF159	0.27	BSY65	0.15
2N706	0.19	2N3710	0.12	40600	0.47	BC153	0.18	BF160	0.23	BSY78	0.40
2N706A	0.12	2N3711	0.09	40602	0.66	BC154	0.18	BF161	0.42	BSY79	0.40
2N708	0.13	2N3712	0.95	40603	0.58	BC158	0.14	BF163	0.20	BSY790	0.45
2N709	0.40	2N3713	1.95	40604	0.56	BC159	0.14	BF166	0.35	BSY95A	0.09
2N711	0.30	2N3714	2.29	40636	1.10	BC169	0.37	BF167	0.21	BU104	1.42
2N718	0.21	2N3715	2.16	40673	0.70	BC170	0.11	BF173	0.24	BU105	2.25
2N718A	0.30	2N3716	3.00	AC107	0.35	BC168B	0.13	BF177	0.29	C111	0.53
2N720	0.50	2N3773	3.96	AC113	0.16	BC168C	0.13	BF178	0.35	D40N3	0.55
2N721	0.55	2N3779	3.15	AC115	0.16	BC169B	0.13	BF179	0.43	GET111	0.45
2N914	0.15	2N3790	4.21	AC117	0.20	BC169C	0.11	BF180	0.35	GET113	0.40
2N916	0.17	2N3791	4.20	AC121	0.13	BC170	0.11	BF181	0.32	GET114	0.20
2N918	0.30	2N3792	5.04	AC126	0.25	BC171	0.13	BF182	0.40	GET115	0.50
2N929	0.14	2N3794	0.10	AC127	0.20	BC172	0.11	BF183	0.40	GET119	0.35
2N930	0.14	2N3819	0.32	AC128	0.20	BC182	0.10	BF184	0.17	GET120	0.25
2N1090	0.23	2N3820	0.47	AC141K	0.30	BC182L	0.12	BF194	0.14	GET535	0.20
2N1091	0.24	2N3823	1.42	AC142K	0.25	BC183	0.09	BF195	0.17	GET536	0.20
2N1131	0.20	2N3824	1.33	AC151V	0.14	BC183L	0.09	BF196	0.15	GET538	0.20
2N1132	0.20	2N3826	0.23	AC152V	0.17	BC184	0.11	BF197	0.15	GET783	0.20
2N1302	0.16	2N3854	0.16	AC153	0.22	BC184A	0.11	BF198	0.15	GET883	0.20
2N1303	0.16	2N3854A	0.16	AC153K	0.25	BC186	0.25	BF199	0.18	GET887	0.20
2N1304	0.20	2N3855	0.16	AC154	0.20	BC187	0.25	BF200	0.40	GET890	0.22
2N1305	0.20	2N3855A	0.16	AC176	0.18	BC207	0.12	BF224J	0.14	GET895	0.25
2N1306	0.22	2N3856	0.16	AC176K	0.20	BC208	0.11	BF225J	0.19	TIP29A	0.49
2N1307	0.22	2N3856A	0.16	AC187K	0.20	BC212K	0.10	BF237	0.22	TIP30A	0.58
2N1308	0.25	2N3858	0.16	AC188K	0.26	BC212L	0.18	BF238	0.22	TIP31A	0.62
2N1309	0.37	2N3858A	0.16	ACY17	0.35	BC214L	0.21	BF244	0.16	TIP32A	0.74
2N1463	0.30	2N3859	0.16	ACY18	0.24	BC237	0.09	BF245	0.33	TIP33A	1.01
2N1507	0.24	2N3859A	0.16	ACY19	0.27	BC238	0.09	BF246	0.43	TIP34A	1.51
2N1613	0.20	2N3860	0.16	ACY20	0.22	BC239	0.09	BF247	0.49	TIP35A	2.90
2N1631	0.35	2N3866	1.69	ACY21	0.26	BC251	0.20	BF254	0.16	TIP36A	3.70
2N1637	0.36	2N3877	0.25	ACY22	0.16	BC252	0.18	BF255	0.17	TIP41A	0.79
2N1638	0.32	2N3877A	0.26	ACY28	0.20	BC253	0.23	BF257	0.41	TIP42A	0.90
2N1701	1.10	2N3900	0.20	ACY30	0.42	BC257	0.09	BF258	0.46	TIP2955	0.98
2N1702	2.15	2N3900A	0.21	ACY39	0.65	BC258	0.09	BF259	0.45	TIP3055	0.60
2N1711	0.22	2N3901	0.32	ACY40	0.17	BC259	0.13	BF270	0.25	ME0401	0.18
2N1893	0.34	2N3903	0.24	ACY41	0.17	BC261	0.20	BF272	0.53	ME0402	0.20
2N2102	0.30	2N3904	0.27	AD136V	0.96	BC262	0.10	BF273	0.25	ME0404	0.13
2N2147	0.70	2N3905	0.24	AD142	0.54	BC263	0.23	BF274	0.28	ME0411	0.17
2N2148	0.94	2N3906	0.27	AD143	0.45	BC300	0.42	BF457	0.53	ME0412	0.18
2N2192	0.40	2N4036	0.46	AD149V	0.66	BC301	0.34	BF458	0.65	ME0413	0.14
2N2192A	0.40	2N4037	0.40	AD150	0.63	BC302	0.27	BF521A	2.30	ME1120	0.25
2N2193	0.40	2N4058	0.16	AD161	0.45	BC303	0.54	BFS28	0.92	ME4001	0.09
2N2193A	0.61	2N4059	0.09	AD162	0.45	BC307	0.10	SF561	0.27	ME4002	0.11
2N2194	0.27	2N4060	0.11	AD162	1.05	BC307A	0.10	BFS98	0.28	ME4003	0.14
2N2194A	0.30	2N4061	0.11	AF109R	0.40	BC308	0.09	BFW11	0.61	ME4101	0.10
2N2195	0.37	2N4062	0.11	AF114	0.25	BC308A	0.09	BFW15	0.35	ME4102	0.11
2N2195A	0.18	2N4302	0.25	AF115	0.24	BC308B	0.09	BFX13	0.23	ME4103	0.10
2N2218A	0.30	2N4303	0.47	AF116	0.25	BC309	0.10	BFX29	0.30	ME4104	0.11
2N2219	0.37	2N4916	0.20	AF117	0.20	BC309A	0.10	BFX30	0.30	ME6101	0.14
2N2219A	0.51	2N4917	0.17	AF118	0.50	BC309B	0.10	BFX37	0.30	ME6102	0.16
2N2220	0.20	2N4918	0.50	AF120	0.22	BC327	0.24	BFX44	0.33	ME8002	0.17
2N2221	0.20	2N4919	0.63	AF124	0.24	BC328	0.22	BFX63	2.48	ME8003	0.16
2N2221A	0.33	2N4920	0.71	AF125	0.20	BC327	0.19	BFX68	6.68	MJ400	0.78
2N2222	0.31	2N4921	0.50	AF126	0.19	BC338	0.19	BFX84	0.24	MJ420	0.86
2N2222A	0.41	2N4922	0.55	AF127	0.20	BCY30	0.43	BFX85	0.29	MJ421	0.88
2N2368	0.11	2N4923	0.60	AF139	0.38	BCY31	0.40	BFX86	0.24	MJ440	0.75
2N2369	0.15	2N5172	0.12	AF170	0.25	BCY32	0.15	BFX87	0.28	MJ443	0.71
2N2369A	0.17	2N5174	0.22	AF172	0.25	BCY33	0.34	BFX88	0.25	MJ480	0.75
2N2646	0.70	2N5175	0.26	AF178	0.55	BCY34	0.35	BFX89	0.45	MJ481	0.85
2N2711	1.20	2N5176	0.32	AF179	0.65	BCY38	0.53	BFY10	0.35	MJ490	0.94
2N2712	0.12	2N5190	0.92	AF180	0.50	BCY39	1.05	BFY11	0.45	MJ491	1.10
2N2713	0.12	2N5191	0.96	AF181	0.65	BCY40	0.50	BFY17	0.90	MJ802	14.2
2N2714	0.17	2N5192	1.24	AF186	0.40	BCY42	0.15	BFY18	0.35	MJ901	2.65
2N2904	0.28	2N5193	1.01	AF200	0.35	BCY43	0.15	BFY19	0.35	MJ1001	2.34
2N2904A	0.25	2N5194	1.10	AF211	0.55	BCY44	0.21	BFY20	0.50	MJ1800	1.88
2N2905	0.71	2N5195	1.46	AF239	0.41	BCY45	0.22	BFY29	0.40	MJ2500	2.92
2N2905A	0.88	2N5245	0.35	AF279	0.72	BCY71	0.22	BFY37	0.20	MJ2501	3.25
2N2906	0.24	2N5457	0.35	AF280	0.54	BCY72	0.13	BFY41	0.43	MJ2955	1.00
2N2906A	0.30	2N5458	0.33	AFY42	0.74	BCY87	3.47	BFY43	0.65	MJ3000	0.65
2N2907	0.32	2N5459	0.33	AL102	0.75	BCY89	0.97	BFY50	0.22	MJ3001	2.79
2N2907A	0.33	3N128	0.73	AL103	0.70	BCZ11	0.35	BFY51	0.15	MJ3701	0.9
2N2923	0.12	3N139	1.65	ASY26	0.30	BD115	0.75	BFY52	0.20	MJ4502	4.44
2N2924	0.12	3N139	1.42	ASY27	0.36	BD115	0.75	BFY53	0.15	MJE340	0.47
2N2924	0.12	3N140	0.92	ASY28	0.36	BD116	0.50	BFY56	0.34	MJE370	0.73
2N2925	0.15	3N141	0.81	ASY29	0.28	BD121	0.75	BFY76	0.40	MJE371	0.80
2N2926	0.12	3N142	0.58	ASY50	0.20	BD123	0.82	BFY77	0.24	MJE520	0.59
Green	0.12	3N143	0.75	ASY55	0.35	BD124	0.67	BFY78	0.36	MJE521	0.73
Yellow	0.10	3N152	0.92	BC107	0.15	BD130	0.57	BFY90	0.60	MJE1092	1.93
Orange	0.10	3N153	0.81	BC103	0.15	BD131	0.40	BFY99	0.60	MJE2801	1.57
2N3053	0.31	3N154	0.84	BC109	0.19	BD132	0.50	BSX19	0.30	MJE2901	1.56
2N3054	0.60	3N159	1.17	BC113	0.13	BD135	0.43	BSX20	0.14	MJE2955	1.65
2N3055	0.75	3N187	1.55	BC114	0.12	BD136	0.49	BSX21	0.20		
2N3390	0.20	3N200	2.49	BC115	0.15	BD137	0.55	BSX26	0.49		
2N3391	0.20	3N201	1.05	BC116	0.15	BD138	0.63	BSX27	0.34		
2N3391A	0.22	40050	0.78	BC117	0.18	BD139	0.71	BSX28	0.25		
2N3392	0.13	40251	0.81	BC118	0.18	BD140	0.83				

Trannies

I Dockyard, Station Road,
Old Harlow, Essex.
Telephone: 37739
(Saturday callers welcome)

VAT

PRICES DO NOT
INCLUDE VAT
ADD
10% TO THE TOTAL

74 Series TTL (National Semiconductors and I.T.T.) LOW PRICES, HIGH QUALITY



7400	1	25	100+	7450	1	25	100+	74141	1	25	100+
7401	16p	14p	12p	7451	16p	14p	12p	74142	71p	68p	66p
7402	16p	14p	12p	7453	16p	14p	12p	74145	£1.50	£1.40	£1.30
7403	16p	14p	12p	7454	16p	14p	12p	74150	£3.00	£2.69	£2.53
7404	16p	14p	12p	7460	16p	14p	12p	74151	£1.00	97p	92p
7405	16p	12p	12p	7470	16p	14p	12p	74153	£1.20	£1.12	99p
7406	36p	32p	28p	7472	29p	26p	25p	74154	£1.80	£1.71	£1.60
7407	36p	32p	28p	7473	38p	36p	32p	74155	£1.40	£1.30	£1.20
7408	18p	17p	16p	7474	38p	36p	32p	74157	£1.90	£1.81	£1.72
7409	18p	17p	16p	7475	45p	45p	42p	74160	£1.80	£1.71	£1.60
7410	16p	14p	12p	7476	40p	39p	36p	74161	£1.80	£1.71	£1.60
7411	24p	19p	16p	7480	68p	63p	59p	74162	£4.00	£3.76	£3.60
7412	30p	25p	20p	7481	£1.20	£1.15	£1.09	74163	£4.00	£3.76	£3.60
7413	29p	27p	25p	7482	86p	87p	86p	74164	£1.40	£1.30	£1.20
7414	44p	40p	38p	7483	£1.11	£1.07	97p	74165	£2.28	£2.22	£2.17
7415	44p	40p	38p	7484	£1.01	96p	91p	74166	£3.55	£3.28	£3.06
7416	14p	12p	12p	7485	£3.00	£2.45	£2.10	74174	£2.32	£2.22	£2.11
7422	50p	48p	45p	7486	32p	31p	30p	74175	£1.66	£1.55	£1.44
7423	50p	48p	45p	7489	£4.49	£4.24	£3.98	74176	£2.56	£2.44	£2.34
7425	50p	48p	45p	7490	58p	48p	59p	74177	£2.55	£2.44	£2.34
7426	46p	42p	40p	7491	£1.00	95p	90p	74180	£2.05	£1.66	£1.44
7427	46p	42p	40p	7492	68p	65p	59p	74181	£5.55	£5.10	£4.83
7428	70p	65p	60p	7493	68p	65p	59p	74182	£2.05	£1.83	£1.66
7430	16p	14p	12p	7494	78p	75p	69p	74184	£3.55	£3.28	£3.06
7432	45p	42p	40p	7495	78p	75p	69p	74190	£2.00	£1.94	£1.89
7433	80p	76p	71p	7496	88p	85p	79p	74191	£1.92	£1.97	£1.91
7437	66p	62p	60p	74100	£1.65	£1.60	£1.56	74192	£2.00	£1.94	£1.89
7438	66p	62p	60p	74104	97p	95p	89p	74193	£2.05	£1.66	£1.44
7440	16p	14p	12p	74105	97p	95p	89p	74194	£2.77	£2.66	£2.55
7441	68p	65p	60p	74107	41p	39p	37p	74195	£2.05	£1.66	£1.44
7442	68p	65p	60p	74110	56p	54p	51p	74196	£1.83	£1.75	£1.66
7443	£1.30	£1.25	£1.19	74111	£1.25	£1.18	£1.12	74197	£1.83	£1.75	£1.66
7444	£1.30	£1.23	£1.19	74116	£1.00	95p	90p	74198	£5.55	£5.10	£4.85
7445	£1.80	£1.76	£1.73	74119	£1.35	£1.25	£1.14	74199	£5.55	£5.10	£4.85
7446	97p	94p	88p	74121	40p	38p	35p				
7447	97p	84p	70p	74122	£1.40	£1.30	£1.12				
7448	£1.00	97p	95p	74123	£2.78	£2.67	£2.61				

Linear Integrated Circuits

709c DIL	1-49	50 plus	741c 14 Pin DIL	38p	31p
709c TO99	34p	29p	741c TO99	38p	31p
723c DIL	70p	55p	747c DIL	80p	68p
723c TO99	76p	58p	748c DIL	36p	31p
741c 8 Pin DIL	36p	34p	748c TO99	38p	32p

Many other types available.



General Purpose Miniature Electrolytic Capacitors (MULLARD & ERIE)

4 VOLT	47µf 6p	100µf 6p	220µf 6p	330µf 6p	470µf 6p	1000µf 6p	1500µf 6p	2200µf 6p	3300µf 6p	4700µf 6p
6.3 VOLT	33µf 6p	68µf 6p	150µf 6p	470µf 10p	680µf 12p	1000µf 16p	1500µf 18p	2200µf 18p	3300µf 25p	4700µf 30p
10 VOLT	22µf 6p	47µf 6p	100µf 6p	220µf 6p	470µf 6p	1000µf 6p	1500µf 6p	2200µf 6p	3300µf 6p	4700µf 6p
16 VOLT	15µf 6p	33µf 6p	68µf 6p	150µf 7p	220µf 8p	470µf 10p	680µf 12p	1000µf 16p	1500µf 18p	2200µf 20p
25 VOLT	10µf 6p	22µf 6p	47µf 6p	100µf 7p	220µf 8p	470µf 10p	680µf 12p	1000µf 16p	1500µf 18p	2200µf 20p
40 VOLT	6.8µf 6p	15µf 6p	33µf 6p	47µf 6p	100µf 6p	150µf 6p	220µf 6p	330µf 6p	470µf 6p	680µf 6p
63 VOLT	1µf 6p	2.2µf 6p	6µf 6p	10µf 6p	22µf 6p	68µf 6p	100µf 6p	150µf 6p	220µf 6p	330µf 6p

(Quantity discount 15%—25 plus. 20%—100 plus. 25%—250 plus.)

MULLARD POLYESTER CAPACITORS C280 SERIES

250v. D.C. mounting 0.01µf, 0.015, 0.022, 3p; 0.033, 0.047, 0.068, 3p; 0.1, 4p; 0.15, 0.22, 5p; 0.33, 8p; 0.47, 8p; 0.68, 11p; 1.0, 13p; 1.5, 20p; 2.2µf, 24p.

MULLARD POLYESTER CAPACITORS C296 SERIES

400v.: 0.001, 0.0015, 0.0022, 0.0033, 0.0047, 2p; 0.0068, 0.01, 0.015, 0.022, 0.033, 3p; 0.047, 0.068, 0.1, 4p; 0.15, 6p; 0.22, 7p; 0.33, 11p; 0.47, 13p; 0.68, 15p; 1.0, 0.015, 0.022, 0.033, 0.047, 0.068, 3p; 0.1, 3p; 0.15, 4p; 0.22, 5p; 0.33, 6p; 0.47, 7p; 0.68, 11p; 1.0, 13p.

AMTRON KITS

We have been appointed stockists of Amtron high quality Construction Kits. (20p P.P. on all kits).

Other Kits include:

UK65 Transistor tester	£2.50
UK110 Stereo Amplifier 5+5w	£11.07
UK120 Hi-Fi Amplifier 12w	£5.20
UK220 Signal Injector	£2.57
UK235 Acoustic Alarm for Absent minded drivers	£8.39
UK300 Four channel radio control transmitter	£6.55
UK310 Radio control Receiver	£3.28
UK325 'GCX2' channel splitting unit 1000 and 2000 Hz	£7.86
UK330 'GCX2' channel splitting unit 1500 and 2500 Hz	£7.86
UK345 Superhetrodyne radio control receiver	£6.55
UK515 mW Radio Receiver	£7.86
UK525 VHF Tuner 120 to 160 mHz	£12.44
UK705 Windscreen Wiper timer	£7.48
UK715 Photoelectric cell switch	£8.49
UK760 Acoustic switch	£11.85
UK875 Capacitive Discharge Electronic Ignition for internal combustion engines	£14.51
TRAT00 24 hour Electronic Digital Clock	£22.50

Many other kits available. Send for the Amtron Catalogue.

*THESE KIT PRICES INCLUDE V.A.T.

Veroboard

2 1/2 x 31	-15 matrix	17p	22p
2 1/2 x 32	-15 matrix	22p	24p
3 1/2 x 31	-15 matrix	28p	28p
3 1/2 x 5	-15 matrix	60p	79p
2 1/2 x 17	-15 matrix	81p	£1.05
3 1/2 x 17	-15 matrix	82p	82p
Pin insertion tool		52p	42p
Spot face cutter		20p	20p
Pack of 36 pins			

Silicon Rectifiers lamp miniature

Type	PIV	1-99	100 plus
IN4001	50	5p	31p
IN4002	100	5p	4p
IN4003	200	6p	5p
IN4004	400	6p	5p
IN4005	600	7p	6p
IN4006	800	9p	7p
IN4007	1000	10p	8p

Phone 37739 for IMMEDIATE despatch

MINITRON DIGITAL INDICATOR TYPE 3015F

Read 0.9 and decimals. ONLY £1.50.

400 mW Zener Diodes

BZ188 Series 3.3 volt to 33 volt.	100 plus
1.49	50-99
9p	7p

TRANSISTORS DIODES

(Quantity discount 25 plus 15%, 100 plus 20%)

AC126 14p	BC147 13p	OC36 65p
AC127 14p	BC148 13p	OC44 10p
AC128 11p	BC149 13p	OC45 10p
AC176 12p	BC154 17p	OC70 12p
AC187 14p	BC157 17p	OC71 12p
AC188 14p	BC158 14p	OC72 14p
AD149 60p	BC159 14p	2N706 12p
AD161 32p	BC182 12p	2N3055 49p
AD162 32p	BC183 12p	2N3702 13p
AF114 14p	BC184 12p	2N3704 13p
AF115 14p	BC212 12p	2N3819 30p
AF116 14p	BC213 12p	40361 31p
AF117 14p	BC214 14p	40362 36p
AF139 32p	BD131 69p	40366 78p
AF239 40p	BD132 69p	OA90 5p
BC107 10p	OC25 40p	OA91 5p
BC108 10p	OC28 52p	OA202 7p
BC109 10p	OC35 52p	IN4148 5p

(Many other types stocked)

EXPORT ORDERS A SPECIALITY!



SIGNAL INJECTOR

The UK 220 Signal Injector is a "must" for repairmen engaged in the repair and servicing of radio receivers and AF amplifiers. It permits a thorough check of the various stages to the antenna coupling circuit due to the signal it delivers, which has a frequency spectrum extending from the lowest acoustic frequencies to the highest short wave band frequencies. The unit is designed to perform quickly and efficiently all the operations involved in fault tracing, and many cases that would normally call for the set to be taken back to the repair-shop can be successfully carried out on the spot.

Specifications
Frequency: 500 Hz
Harmonics: up to approx. 30 MHz
Output voltage: 1 V peak-to-peak
Maximum voltage applicable to the probe: 500 V DC
Power supply: 1.4 V DC
Transistors: (2) BC208B
£2.57

UP TO 25% DISCOUNT OFF ALL OUR SEW CLEAR PLASTIC PANEL METERS



MR38P 1 21/32" Square fronts.	Normal Price	Our Price
0-500µA	£2.50	£2.15
0-1mA	£2.50	£2.10
0-10mA	£2.50	£2.10
0-100mA	£2.50	£2.10
S meter 1mA	£2.53	£2.10
4" Scale Rectangle fronts	£3.75	£2.90
0-30µA	£3.75	£2.90
0-100µA	£3.70	£2.90
0-500µA	£3.45	£2.88
'VU' Signal Strength meters	£3.85	£3.15
Edgewise meters 3 17/32" x 1 15/32"		
500µA	£3.50	£2.95
1mA	£3.50	£2.95

Resistors

1/2 watt 5% carbon	1p	100 plus
1 watt 5% carbon	1p	7p
1 watt 10% carbon	2p	7p
range 10 ohms to 4.7 megohms.		
1/2 watt m/o 2%	3p	2.4p
range 10 ohms to 1 megohms.		

Transformers

12-24 volt

Secondary Volts	Amps	Volts	Amps	Part No.	Price Inc. P.P.
12	500mA	24	250mA	MT111	£1.20
12	1	24	500mA	MT213	£1.28
12	2	24	1	MT71	£1.89

30 volt

Amps	Part No.	Secondary 12, 15, 20, 24, 30v.	Price Inc. P.P.
2	MT79		£2.02
2	MT3		£2.78
5	MT51		£5.21

50 volt

Amps	Part No.	Secondary 18, 25, 33, 40, 50 volts	Price Inc. P.P.
1	MT103		£2.54
2	MT104		£3.75
4	MT106		£8.00

Many other types available. See our Catalogue.

MAGNETIC HEADS P.O.A.

210028 RCA	9 TRACK	303462 RCA	7 TRACK
259019 RCA	7 TRACK	1215872 TYPE 1301	7 TRACK
257124 RCA	8 TRACK	5007821 POTTER	7 TRACK
282812 RCA	8 TRACK	19467 EPSYLON	8 TRACK
303489 RCA	7 TRACK	76815/948 BURROUGHS	9 TRACK
73927 RCA	7 TRACK	652623DRI 12/101	12 TRACK
303464 RCA	7 TRACK	L651922 DRI FR3000	16 TRACK

TRANSISTORS & DIODES

2N457	75p	AF116	25p	2N356/OC139	25p
2N1545	50p	AF117	25p	Get110	20p
2N1542	50p	BC107	8p	2G106/2N711B	43p
2N1557	50p	BC108	8p	OAS	20p
2N1908	£6.00	BC109	8p	OA10	25p
2N3054	40p	OC35	40p	RAS508AF	
2N3055	45p	OC42	40p	800PIV	50p
2N3442	£1.02	OC71	12p	RAS310AF 1000v Av.	
2N3553	£1.00	CV7006/OC72	20p	1.5a 2 for 50p	
2N5322	50p	OC75	25p	STC Wire ended 400PIV	
AC126	20p	OC77	45p	1a 4 for 50p	
AC127	25p	OC83	25p		
AC128	20p			IN3193	13p
AF115	25p			IN3194	14p
				IN3255	20p

RCA PHOTOMULTIPLIER C31005B

Checked and tested £37.50

BRIDGE RECTIFIERS

1B40KO5 50v 4a..... 95p

RECTIFIER STACKS

GEX541B1P2	£6.88
GEX541B1P1	£3.50
GEX541D2P1	£3.50
GEX541NB1P1F	£6.00
GEX541HP3F	£6.00
SX751N1B1P1F	£6.00

SWITCHES

Edwards High Vacuum "Speedivac" model VSK1B range 25-760 torr contact ratings 250v, 5a, volume 4-2 cu. cm, max. working pressure 15lb/sq. in. gauge net weight 17 ozs. £6.20
 Bailing Delay hand reset L415 £1.10
 Stackpole min. rocker 125v. 10a. 250v. 5a. 20p
 Tipalite Rocker 12v. 60p
 Securex 5000 press button 250v. ac. £1.20

DIGITAL COUNTERS

Veeder Root Zero Reset 6 dig. 110v. dc £4.75
 Veeder Root Mech. Reset 4 dig. 50p
 Hengstler Reset 6 dig. 210Ω 24v. £3.50
 Hengstler Reset 6 dig. 110v. Type 400 with suppressor £5.50

RELAYS

Varley Min. 700 Ω 12v. 50p
 Siemens Min. 12/15v. 50p
 Magnetic Dev. Type 596E £2.00
 BR Type M51 240v. 65p

KEYBOARDS

ICT Numerical. £3.50
 carr. 35p
 ICL Alpha Verifier (PN7035130) £27.50
 carr. £1.00

ELECTROACOUSTIC UNIT

6 watt (peak) Amplifier 240v. AC, with inputs for Radio, Tape Recorder, freq. response 80-12,500Hz, bass and treble controls, 2 speakers. Dimensions 265 x 235 x 580 mm. Net weight 10Kg. Ideal for education seminars etc. £00.00 incl. carriage.

INTEGRATED CIRCUITS

MC3544	£1.10
MC3533G	£2.00
MC358AG	£5.00
MC365G	£5.00
CA3020	93p
CA3021	£1.15
CA3028A	97p
CA3038A	£2.14
CA3055	£1.24
CA3085	78p
CD4035AE	£1.91
CD4017AE	£3.86

THYRISTORS

GE2N1774 200v. 5a.	£1.20
CR1-021C 20v. 1a.	25p
CR10-101B 100v. 10a.	£1.00
CR10-021 10a.	£1.00
CR10-40B 10a.	£1.00
CR10-051 10a.	£1.00
CR10-017 10a.	£1.00
BTX-82-300R 300v. 26a.	£2.00
STC 3/40 400v. 3a.	50p

CONNECTORS

McMurdo Red Range. Plug RP24	56p
McMurdo Red Range. SKT RS32	90p
Eng. Elect. Edge. 36 way 0.2mm	£1.00
Sylvania Edge. 48 way 0.1mm	pair £1.40
Ultra Gold-plated Contacts. 0.1mm Type 10M 54631263C 38 way.	pair £2.00
20 way.	pair £1.60

CAPACITORS

Daly Electrolytic 9000 uf 40v. 50p; Wego paper 4uf 400v 60p; Dublie Metallised Paper Type 426 100uf 150v. DC 50p; R.I.C. type 1297 1.8uf 440v AC 35p. TCC V13 Conol 3.1µf 1500VDC 50p

MOTORS

GEC fractional 1/12 hp 230/250v 1ph 50c 2850rpm. £3.50 carr. 67p
 E.E. ½hp 230v. 50c 1ph 50c. 1440rpm comp l ete with cap 80/100uf 275v. £13.00 carr. £1.00
 76813-393 Potter Instr. 110v. DC 4amp 0.2hp. Cont. flange mounting precision tape transport motor (£80 value) £25.00 incl. carr.

FANS, CENTRIFUGAL BLOWERS

Alrmax Type M1/Y3954 (3 blades) Cast Aluminium alloy impeller & casing (corresponds to current type 3965 7½") 230v. 1ph 50c 2900rpm Class "A" insulation 425cfm free air weight 9½lbs. incl. p.p. £21.00.

Woods Aerofoil short casing type "S" 2700rpm 220/250v 1ph 50c 6" plastic impeller incl. p.p. £11.50.

Woods Aerofoil Code 7.5 280K 200/250v. 1.0a 1ph 50c 2700rpm 7½" impeller 14 blades incl. p.p. £13.50.

Service Electric Hi-Velocity Fans, suitable for Gas combustion Systems. Steam exhausting, Pneumatic conveying, Cooling Electronic equipment, Air blast for Oil burners. **Secomak** Model 365 (corresponds to 575) Airblast Fan, 440v 3ph 50c 0.75hp 2850rpm continuous 160cfm 12 in. w.g. net weight 44lb price incl. carr. £41.00. **Secomak** model 350 250v 1ph 50c 0.166hp, 2800 rpm continuous 50cfm 2 in. w.g. net weight 34lbs, price incl. carr. £25.00.

Air Controls type VBL4 200/250v 1ph 50c. 110cfm free air weight 7½lbs price incl. p.p. £14.50.

William Allday Alcosa Two Stage Vacuum Pump Model HSP0B 8hp up to 29 in. mercury rpm 1420. E.E. 3 phase induction, motor ½hp cont. 220/250v. 380/440v. £21.00 incl. carr.

Gast MFG. Vacuum pump 0522-P702-R26X. Motor 110/120v. A.C. 1 ph. 60c 1725 rpm. Class E. Or as compressor 10psi int. or 15 psi cont. £25.00 incl. carr.

Where p.p. not advised add 10p per £ handling and post (in UK). Cash with order. Personal callers welcome. Open Mon-Wed. 9.30-5.00 Fri.-Sat. 9.30-5.00. Free Car Park adjacent.

PRICES SHOWN ARE EXCLUSIVE OF V.A.T.

W. & B. MACFARLANE


126 UXBRIDGE ROAD, HANWELL, LONDON W7 3SL

WW-108 FOR FURTHER DETAILS

BI-PRE-PAK

AUDIO BARGAINS

8 TRACK ONLY £11

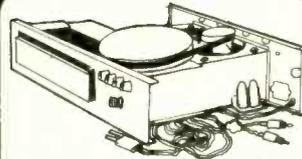

incl. P. & P. and VAT


The latest **B.S.R. 8 Track cartridge Replay Deck. Ready to install in your Hi-Fi Stereo System.**

This unit comes complete with Hi Gain Stereo Pre-Amplifier, 4-Programme Indicator Lamps, Track Selector Switch, all leads and plugs. etc. for 230 volt A.C. mains operation.

5W & 10W AMPS

5W ONLY £1.98

10W ONLY £2.49

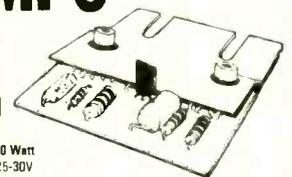

incl. P. & P. and V.A.T.

Specification:-	5 Watt	10 Watt
Normal Volts	12-14V	25-30V
Into 8 Ohms	5W	10W
Into 15 Ohms	2W	10W
Typical Distortion	1W	5W
Typical Distortion	5%	5%
Freq. response at 3dB	10Hz to 30KHz	10Hz to 30KHz
Sensitivity (Typical)	20mV	20mV
Full power consumption (30 Ohms)	650mA	580mA
Size	2½" x 1½"	2½" x 1½"


The **5W matchbox sized amplifier** will run satisfactorily from a 12V car battery. Can also be used for portable voice reinforcement such as public functions where mains supply is not accessible. A small mains unit kit is available.

Two amplifiers are ideal for Stereo. Complete connection details and treble, bass, volume and balance control circuit diagrams are supplied with each unit.

Discounts are available for quantity orders.

Cheapest in the U.K. Built and tested

STEREO DECODER £4.95

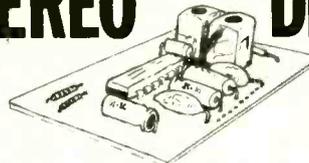

incl. P. & P. and VAT

A ready built unit, ready for connection to the I.F. stages of your existing FM Radio or Tuner. A tell tale light can be connected to show the presence of a Stereo transmission and correct operation.

The Unit is in the form of a small printed circuit, and no further alignment is necessary, as all preset adjustments have already been carried out at the factory.

It is recommended that a L.E.D. is used as the indicating light and a suitable device is available from us at 36½p.

Supplied with all necessary instructions.

I enclose £ for 8 Tracks/
 5W Amps/ 10W Amps/ Decoders
 (Please insert quantities and delete those not applicable.)
 Name
 Address

BI-PRE-PAK
 Co. Regn. No.820919

Dept. B, 222/224, West Road,
 Westcliff-on-Sea,
 Essex S50 9DF
 Tel: Southend (0702) 46344

G. F. MILWARD

ELECTRONIC COMPONENTS

Wholesale/Retail: **369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339**

Special Offer!!!—From Stock—New—Boxed—AND 60% Discount!

MULLARD ELECTROLYTIC CAPACITORS

071 and 072 Series



Type No.	Working Voltage Vdc.	Capacitance μ F	Max. Ripple Current at 50°C	Weight	Price
071 14472	10	4700	2.5 amps	1oz	15p
071 14682	10	6800	4 amps	1oz	17p
071 15332	16	3300	2.4 amps	1oz	15p
071 15472	16	4700	3.9 amps	1oz	17p
071 15682	16	6800	5.8 amps	1½oz	22p
071 15103	16	10000	7.9 amps	3oz	30p
071 18222	63	2200	5.8 amps	2½oz	27p
072 14113	10	11000 + 11000	10.6 amps	3oz	37p
072 14173	10	16500 + 16500	13.4 amps	4oz	49p
072 15752	16	7500 + 7500	10.5 amps	3oz	37p
072 15113	16	11000 + 11000	13.8 amps	4½oz	49p
071 18222	25	2200	2.2 amps	1oz	15p
072 16502	25	5000 + 5000	9.6 amps	3½oz	37p
072 16752	25	7500 + 7500	12.6 amps	4½oz	49p
072 17342	40	3400 + 3400	9.1 amps	3½oz	37p
072 17502	40	5000 + 5000	12.0 amps	4½oz	49p
071 18681	63	680	2.1 amps	1oz	15p
072 18172	63	1650 + 1650	7.8 amps	3oz	37p

106 and 107 Series

Type No.	Working Voltage Vdc.	Capacitance μ F	Max. Ripple Current at 50°C	Weight	Price
106 14153	10	15000	7 amps	4oz	57p
106 15103	16	10000	7 amps	2½oz	65p
106 16223	25	22000	17 amps	10oz	£1.12
106 17103	40	10000	12 amps	7½oz	94p
106 18153	63	15000	28 amps	18oz	£1.79
107 10222	100	2200	10 amps	5½oz	74p

Type No.	Voltage	Capacitance	Weight	Price
102 15163	16	16000	8oz	20p
104 90003	20	39000	16oz	30p
102 16802	25	8000	7oz	25p
104 17562	40	5600	5oz	25p
104 90001	45	20000	16oz	50p

A discount of 10% may be deducted from above prices on lots of 100 of any one type.

Please calculate the weight of your order and include appropriate postage.

Not over	Ordinary Parcels
1½lb	16p
2lb	21p
4lb	25p
6lb	29p
10lb	37p
14lb	47p
18lb	57p
22lb	67p



SMALL ELECTROLYTICS

Ref. No.	Capacity μ f	Voltage	Price	Ref. No.	Capacity μ f	Voltage	Price
H8/1	2.2	25v	4p	H7/4A	64	35v	5p
H8/2	3.3	25v	4p	H7/5	80	16v	4p
H8/2A	3.3	25v	4p	H7/6	100	25v	5p
H8/3	4.7	50v	4p	H7/6A	100	15v	4p
H8/3A	4.7	50v	4p	H7/7	100	25v	4p
H8/4	4.7	25v	4p	H7/8	125	16v	5p
H8/4A	5	64v	4p	H7/8A	100	35v	6p
H8/5	5	10v	4p	H7/9	100	63v	6p
H8/5A	5	150v	4p	H7/9A	125	4v	4p
H8/6A	10	10v	4p	H7/10	125	25v	6p
H8/7	10	70v	4p	H7/10A	150	2.5v	3p
H8/8	16	35v	4p	H7/11	180	25v	6p
H8/8A	16	16v	4p	H7/11A	150	16v	5p
H8/9	20	70v	2p	H7/13A	200	25v	8p
H8/9A	20	6v	2p	H7/14	220	50v	10p
H8/10	22	50v	4p	H7/14A	220	16v	6p
H8/10A	22	100v	4p	H7/15	220	25v	3p
H8/11	24	12v	4p	H7/15A	220	35v	19p
H8/11A	24	275v	4p	H6/1A	250	4v	3p
H8/12	32	15v	4p	H6/2			
H8/12A	30	10v	4p	H6/3A	320	2.5v	3p
H8/13A	32	50v	4p	H6/4	320	10v	4p
H8/14	40	25v	5p	H6/4A	330	16v	5p
H8/14A	40	16v	4p	H6/5	330	10v	5p
H8/15	47	50v	4p	H6/5A	330	35v	15p
H8/15A	40	35v	4p	H6/7	400	15v	5p
H7/1	50	6v	3p	H6/8	470	25v	10p
H7/1A	50	10v	4p	H6/8A	470	35v	20p
H7/2	50	50v	4p	H6/9			
H7/2A	64	2.5v	2p	H6/9A	400	40v	20p
H7/3A	64	25v	4p	H6/10	750	12v	5p
H7/4	64	15v	4p	H6/13A	1000	25v	16p
				H5/2A	2200	16v	15p

NEW! NEW! NEW! NEW!

An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.
 Method: Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner.
 Light sensitive aerosol spray £1.00 plus
 Developer and Etchant 50p postage
 Copper-clad Fibre-glass Board—50p so. ft. (max. 3' x 4')

NEWER THAN NEW!!!

Fibre Glass Board pre-treated with light-sensitive lacquer enabling you to produce prototype printed circuits within five minutes.
 75mm x 100mm 33p
 150mm x 100mm 66p
 150mm x 200mm £1.32
 250mm x 200mm £2.20
 Epoxy-Resin
 75mm x 100mm 22p
 100mm x 150mm 44p
 150mm x 200mm 88p

VEROBOARD

2½in x 1in x 0.15in	16p
3½in x 2½in x 0.15in	25p
5in x 3½in x 0.15in	25p
5in x 3½in x 0.15in	30p
17in x 3½in x 0.15in	55p
17in x 3½in x 0.15in	79p
3½in x 2½in x 0.1in	21p
3½in x 3½in x 0.1in	25p
5in x 2½in x 0.1in	29p
5in x 3½in x 0.1in	29p
Spot Face Cutter 38p. Pin Insert Tool 57p.	
Terminal Pins (0.1 or 0.15) 36 for 22p.	

MULLARD POLYESTER CAPACITORS

500,000 in STOCK!!!
 .001 μ f .0018 μ f .0056 μ f .015 μ f
 .0012 μ f .0022 μ f .0033 μ f .033 μ f
 .0015 μ f .0027 μ f .012 μ f .082 μ f
 20p dozen; 75p-100; £5-1,000; £40-10,000
 15 μ f 18 μ f 22 μ f 39 μ f 68 μ f
 20p dozen; £1-100; £6-50-1,000; £50-10,000

ERIE MONOLITHIC CERAMIC CAPACITORS

3p each; 24p dozen; £1.75 per 100
 10pf 68pf 560pf
 15pf 100pf 620pf
 22pf 150pf 680pf
 33pf 220pf 1,000pf
 39pf 330pf
 47pf 470pf

CLEARANCE CORNER

BAGS CONTAINING 1,000 ASSORTED DIODES, SILICON/GERMANIUM/ZENER. UNTESTED, BUT MAINLY O.K.

£1

MIXED COMPONENTS, ALL NEW, UNUSED. RESISTORS, CARBON/WIRE, POTS., DIODES, TRANSISTORS, CAPACITORS, ELECTROLYTIC/PAPER/CERAMIC/SILVER MICA. FANTASTIC VALUE. PRICE PER 2lb. MIXED BOX

£1

RECTIFIERS 1N4007 1200 peak volts, 30 amps peak current, 1 amp mean current. 100 for £7.50, 1,000 £50.

UNREPEATABLE BARGAIN BD112


TO3-NPN DIFFUSED SILICON PLANAR EPITAXIAL. VCBO COLLECTOR TO BASE—80 VOLTS. VCEO COLLECTOR TO EMITTER—80 VOLTS. VBE0 EMITTER TO BASE—5 VOLTS. 20 WATTS—2 AMPS—30 Mhz. FEATURES HIGH CURRENT GAIN OVER WIDE RANGE OF COLLECTOR CURRENT

25p!
ONLY

REMEMBER!


ALL GOODS PLUS 10% V.A.T.

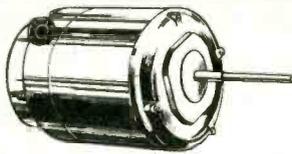G. F. MILWARD, Drayton Bassett, Tamworth, Staffs. Postage (minimum) per order 15p.



"SLO-SYN" 3-HEAD SYNCHRONOUS STEPPING MOTOR

Type SS15. These fine motors are easily reversed, starting and stopping in less than 5° without electrical or mechanical braking. Simple relay circuit can be applied to give DC., to winding for a maximum holding torque of 300oz/in with 35v at 0.35amps through winding. For A.C. (synchronous) operation at 120v., 50Hz. Speed 60 rpm at 60Hz., 72 rpm. STEPPING. Holding torque at 60 steps per second—100 oz/in. Can be wired to give 100 or 200 steps per revolution with accuracy of 0.1° per step non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions: dia. 4", body length 4 1/2", spindle length 2 1/2" x 1/8" dia. Weight 6 1/2 lbs. BRAND NEW in maker's packing. Offered at less than 1/2 maker's price. **£13.75**

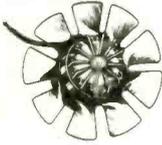

FAN/BLOWER

Precision-built in Germany. Dynamically balanced mains unit (200/240) continuous rated, reversible 60MA on run. Size: 5 1/2" dia. x 2 1/2" deep. Back plate is tapped for 4 fixing screws (supplied). Well under maker's price at £3. P. & P. 20p. Similar unit to above but 7 1/2" dia. x 3" deep. £4.50. P. & P. 25p.

SMITHS RINGER-TIMER

Reliable 15 minute times, spring wound (concurrent with time setting) 15x1min divisions, approximately 1/2" between divisions. Panel mounting with chrome bezel 3 1/2" dia. £1.30. 15p. P. & P.



GEARED MOTORS

"Parvalux" Reversible 100 rpm geared motor. Type SD14, 230/250v. A.C., 22 lb/in. 1/2" spindle. 1st class condition. £7.50 each. 50p P. & P. Also limited number only as above, BRAND NEW. £12.50 each. 50p P. & P.


OPEN FRAME shaded pole GEARED MOTORS

(Dural gear case) 240 A.C., 28rpm. NEW HIGH TORQUE, approx. overall size 3 1/2" x 2 1/2" x 2 1/2" + spindle 1/2" dia. as illustrated. £2.70. P. & P. 30p. Similar to above, 19rpm. £2.70. P. & P. 30p. 110rpm with pressed steel gear case (similar to above but slightly smaller). £2.70. P. & P. 30p.



SPIT MOTOR

5 1/2rpm. 2 1/2" x 1 1/2" x 6 1/2" high. 240v. A.C. Shaft 1/8" dia. 1 1/2" length with hexagon socket inside. £1.80. P. & P. 30p.

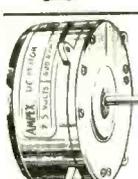

AMPEX 7.5v. DC MOTOR


This is an ultra precision tape motor designed for use in the AMPEX model AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 50ma on run. 600rpm ± speed adjustment. Internal AF/RF suppression. 1/2" dia. x 1" spindle, motor 3" dia. x 1 1/2". Original cost £16.50. OUR (special quotations). Mu-metal enclosure available. 75p each. FREE P. & P.

"CROUZET" MOTORS Type 965



115/240v. 50Hz. 48w. Stoutly constructed. 2.1116" dia. x 3 1/2" long plus spindle 1" x 1/8" dia. Anti-clock. £3 each. P. & P. 25p.

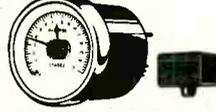SYNCHRONOUS AUTO-RESET PROCESS TIMER by LONDEX LTD.



Type IMP Mk. 2. BRAND NEW and boxed. These well known timers are already in world wide use and are perfect for Industrial Electronic Timing, Research and for all machine control timing problems. Repetitive accuracy better than 0.5% of full scale setting. Two or more can be interconnected to give control of a series of processes. 230/250V. 50Hz, also available 60Hz. 15mins. full scale 15secs. per division. Driven by self-starting sync. motor. Contact rating 5amp at 250V. A.C. Incorporates solenoid operated clutch, also lever actuated micro-switches. Normal probably in excess of £16. Complete with multi-pin connector as illustrated. £6.50. P. & P. 25p.

MAINS SOLENOID

This little unit gives vertical lift of approximately 1" through hinged "elbow". Bracket incorporates 2 fixing screws. Length of arm, 2 1/2". 240V A.C. Pull at coil is approximately 1lb. £1. FREE P. & P. Special quotes for quantities.



SOLENOIDS by WESTOOL

240AC type MM6. 3lb. pull, 2 1/2" x 1 1/2" x 1 1/2". Travel 1". 85p each. P. & P. 10p.



240AC type MM4. 2lb. pull, 1 1/2" x 1 1/2" x 1". Travel 3/4" 60p each. P. & P. 10p. Quantity discounts; 10-50 10%. 50 upwards 25%



"DECCO" MAINS SOLENOID

Compact and very powerful. 16lb. pull. 1" travel which can be increased to 1 1/2" by removing captive-end-plate. Overall size: 2" x 2 1/2" x 2 1/2" high. £2. P. & P. 20p.



7 DIGIT COUNTER by "Counting Instruments Ltd."

Non re-set, robust construction, 115V A.C. £1.20. P. & P. 10p.



3 BANK MAINS COUNTER NON RE-SET by "E.N.M. LTD." BRAND NEW.

6 digits per unit. Robust and neat. 200/240A.C. £5.80. P. & P. 25p. Limited supply.



"RE CIRK IT" Mains 10amp cut-out

by "Neimman Electric" Germany. Eliminates fuses. Size: 2" x 2 1/2" x 1 1/2" deep. 90p each. P. & P. 10p. 10 or more 70p each. P. & P. 20p.



PLUG-IN RELAYS by SCHRACK

(PERSPEX ENCLOSED)


OCTAL (2 c/o) 6 amp contacts at following voltages: 48 D.C., 60 D.C., 60 A.C., 110 D.C., 380 A.C. PRICE EACH 90p.

11 pin (3 c/o) 6 amp contacts: 12 A.C., 48 D.C., 48 A.C., 60 A.C., 60 D.C., 110 D.C., 115 A.C., 240 A.C. PRICE EACH £1.

RA and RN Series (4 c/o) 3 amp Gold Plated Contacts. Handsome modern construction 1/2" x 1 1/2" high. Following voltages: 6 A.C., 12 A.C., 24 A.C., 48 A.C., 48 D.C., 60 A.C., 110 D.C., 115 A.C., 120 A.C. PRICE EACH 80p.

Base sockets for all above types 10p. Please add 10p towards P&P on all orders.

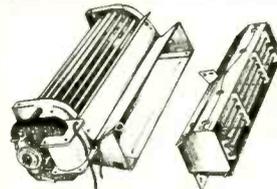From JAPAN, TAKAMISAWA Perspex enclosed relays. Type MQ 308. 24V. DC. 600 ohms (4c/o). Complete with base socket. 80p. P. & P. 10p.



TANGENTIAL HEATER

Silently driven by shaded pole Mycalex motor, powerful and smooth running with aluminium impeller (outlet 5/8" x 1/2"). Mains voltage PLUS matching heater unit with spiral element. May be switched for 500 or 1,000w. £1.80. P. & P. 30p.

DOUGLAS TRANSFORMERS

Full range in stock, SAE or phone for list please.

SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!


A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 3amp at 120v. 1amp at 240v. Size: (approx.) 1 1/2" long x 1/2" dia. Ideal for burglar alarms, security systems etc., and where non-mechanical switching is required. 10 for £1.80; P & P 15p. 50 for £8; 100 for £15. FREE P. & P. over 10.



NORPLEX

The famous American fibre-glass copper-clad laminate. Finest quality with woven glass base of Epoxy-resin. Excellent Mech. and Elec. conductive properties. Heat resistant, ideal for P.C.'s etc. THIS IS A SPECIAL PURCHASE AND ONLY AVAILABLE WHILE STOCKS LAST! Sizes: 12" x 12", 24" x 12", 24" x 24", FULL SHEET 43" x 37" (11 sq. ft.). Single-sided Copper with thickness of 1/32", 3/64", 3/32". Also double-sided 1/32", 1/16", 3/32". £1 per sq. ft. Cut sizes (1-10 sq. ft.) 25p. P. & P. Full Sheet £8 each. Carr. £1 for 1st sheet plus 25p each additional sheet.

"GOYEN" PRESSURE SWITCH

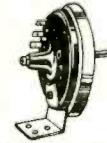

Incorporating differential adjustment between 2" and 12" water gauge (a max. of approx. 1/2 p.s.i.). A single pole change-over switch rated 15 amps. 250v. is actuated. Air inlet tube 7/8" dia. Projection 1 1/2". Overall size dia. 3 1/2", depth 2" plus 1/2" (air tube). £1.45. P. & P. 20p.

PYE MICROSWITCH OTEHALL Type.

This switch has a 1 1/2" x 15/32" dia. column plus 1/2" plunger—fractional travel actuates. 6 for £1 (Min. quantity). P. & P. 15p. Large stocks available.



PLEASE ADD 10% FOR V.A.T. ON ALL PRICES SHOWN INCLUDING P & P

Postal or carriage charges are for G.B. only. Orders welcomed from established companies, educational depts., etc. All orders under £2.50. C.W.O., please. Company orders under £2.50, surcharge 50p unless C.W.O.

ELECTRO-TECH

COMPONENTS LTD.

315/317, EDGWARE ROAD, LONDON, W2. Tel: 01-723 5667 01-402 5580

Transistor TELEPHONE AMPLIFIER



Our price ONLY

£3.99

Increase efficiency of Office, Shop and Workshop with this DELUXE TELEPHONE AMPLIFIER which enables you to take down long telephone messages or converse without holding the handset. Just moisten the suction pad and stick it to one side of the telephone. A useful office aid. On/Off switch. Volume control. Operates on one 9v battery. Size 3in. x 4in. Ready to operate. Complete with battery. P & P 9Kn.

4-STATION INTERCOM



£8.75

This NEW, versatile De Luxe 4-Station Transistorised Intercom (1 Master and 3 Subs) for desk or wall mounting can solve your communication problems instantly. Effective range 800ft. Call/talk/listen from Master to Subs and Subs to Master. With Selector switch. Ideally suitable for office, shop, home or surgery. Adaptable for Mains. Complete with three 66ft. connecting wires and accessories. On/Off switch volume control. P. & P. 44p.

WEST LONDON DIRECT SUPPLIES
169 KENSINGTON HIGH STREET, LONDON W8 6SN

GARBLED DATA? IS YOUR DATA LINK IMPOSSIBLE?

A CINORTCELE LOW COST, HIGH PERFORMANCE "BIT SYNCH" WILL GIVE CLEAN DATA FROM UNREADABLE SIGNALS. WORKS IN SIGNAL TO NOISE OF 0db. BIT RATES 25-2M. BITS P.C. MOUNTING.

CINORTCELE LTD.,
Oaklands House, Solartron Road,
Farnborough, Hants. Farnboro' 40554/5

SERVICE TRADING CO

MATSUNAGA VARIABLE VOLTAGE TRANSFORMERS

INPUT 230 v. A.C. 50/60
OUTPUT VARIABLE 0/260 v. A.C.
 Carriage extra if not shown.
 BRAND NEW. All types.

50 AMP 0-260 v. at 1 amp. (Post 50p)	£7-00
0-260 v. at 2.5 amps (Post 60p)	£8-05
0-260 v. at 5 amps (Post 75p)	£11-75
0-260 v. at 10 amps	£22-50
0-260 v. at 15 amps	£25-00
0-260 v. at 20 amps	£49-00
0-260 v. at 37.5 amps	£82-00
0-260 v. at 50 amps	£98-00

Special discount for quantity

OPEN TYPE (Panel Mounting)
 1 amp £7-00. Post 50p. 2½ amp £8-05. Post 60p.

L.T. TRANSFORMERS

All primaries 220-240 volts.

Type No.	Sec. Taps	Price	Post
1	30, 32, 34, 36 v. at 5 amps	£4-70	45p
2	30, 40, 50 v. at 5 amps	£6-90	60p
3	10, 17, 18 v. at 10 amps	£5-00	50p
4	6, 12 v. at 20 amps	£6-50	60p
5	17, 20 v. at 20 amps	£7-30	60p
6	6, 12, 20 v. at 20 amps	£6-90	60p
7	24 v. at 10 amps	£5-30	50p
8	4, 6, 24, 32 v. at 12 amps	£7-20	60p
9	6 and 12 v. at 10 amps	£3-80	40p

RING TRANSFORMERS

Functional Versatile Educational

These multi-purpose Auto Transformers, with large centre aperture, can be used as a Double wound current Transformer, Auto Transformer, H.T. or L.T. Transformer, by simply hand winding the required number of turns through the centre opening. E.g. Using the RT-100 V.A. Model the output could be wound to give 8V @ 12½ Amp., 4V @ 25 Amp. or 2V @ 50 Amp., etc. Price: RT-100VA 3.18 turns per volt, £3-00. Post 35p. RT-1KVA 1.82 turns per volt, £8-60. Post 50p. RT-2KVA 1.5 turns per volt £14-00. Post 75p. RT-3KVA 1.5 turns per volt. £19-00. Post £1.

VOLTAGE CHANGING TRANSFORMER

M.f. to highest W.D. spec. Auto wound, and tapped 0-130, 160-200-250 at least 2KVA. Can also be used as 230-240V. input, 115V. out for U.S.A. equipment, or reverse to obtain 240V. from 115V. The ideal transformer for making up solid state constant voltage unit, by use of taps the following voltages may be obtained: 30-40-50-70-90 Volts at 10 amps. Weight 40 lbs., length 260 mm., height 190 mm., width 230 mm. In original maker's wooden case, £8-00, carr. £1.

240 V A.C. SOLENOID OPERATED FLUID VALVE

Will handle liquids or gases up to 7 p.s.i. Forged brass body, stainless steel core and spring. ½ in. b.s.p. Inlet/outlet. Precision made. British mfg. PRICE: £1-75. Post 25p. Special quotation for quantity. NEW in original packing.

FOOT SWITCH

Suitable for Motors, Drills, etc., etc. 5 amp. 250 Volt. Price 75p. Post 15p.

PARVALUX TYPE: SDI.S/89400/OM

230/250v. A.C. 50 r.p.m. 22 lb/ins. Continuously rated. Incl. base £6-00. Post 30p. New and unused.

GENERAL ELECTRIC POWER-GLAS TRIACS

10 amp. Glass passivated plastic triac. Latest device from U.S.A. Long term reliability. Type SC 145D 10 amp. 400PIV £1-00. Post 5p. Type SC 146E 10 amp. 500PIV. £1-30. Post 5p. (Inclusive of data and application sheet) suitable Diac 18p.

'HONEYWELL' PUSH BUTTON MOUNTING MICRO SWITCH ASSEMBLY

Each bank comprises of a change-over rated at 10 amps 240 volt A.C. Black knob 1 in. dia. Fixing hole ½ in. Prices: 1-bank 30p., 2-bank 40p., 3-bank 50p. (Illustrated) Inc. P. & P. Special quotes for quantities.

VERY SPECIAL OFFER

MICRO SWITCH

5 amp. c/o contacts. M.f.g. bg. Honeywell. NEW. Twenty for £1-50. Post 10p (min. 20).

'HONEYWELL' LEVER OPERATED MICRO SWITCH

15 amps 250 volt A.C. c/o contacts. NEW In maker's carton. Price 10 for £1-90. Post 15p.

INSULATION TESTERS (NEW)

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L. 8 in., W. 4 in., H. 6 in., weight 6 lb. 500 VOLTS, 500 megohms £28-00. Post 50p. 1,000 VOLTS, 1,000 megohms £34-00. Post 60p.



STROBE! STROBE! STROBE!

* FOUR EASY TO BUILD KITS USING XENON WHITE LIGHT FLASH TUBES, SOLID STATE TIMING + TRIGGERING CIRCUITS. PROVISION FOR EXTERNAL TRIGGERING. 230-250V. A.C. OPERATION.

* EXPERIMENTERS "ECONOMY" KIT Adjustable 1 to 30 Flash per sec. All electronic components including Xenon Tube + instructions £8-30. Post 30p.

* NEW INDUSTRIAL KIT Ideally suitable for schools, laboratories etc. Roller tip printed circuit. Adjustable 1-80 f.p.s., approx. ½ output of Hy-Light. Price £10-50. Post 50p.

* HY-LIGHT STROBE Designed for use in large rooms, halls and utilizes a silica tube, printed circuit. Speed adjustable 1-20 f.p.s. Light output greater than many (so called 4 Joule) strobes. Price £12-00. Post 50p.

* 'SUPER' HY-LIGHT KIT Approx. 4 times the light output of our well proven Hy-Light strobe. Reactor control circuit producing an intense white light. ONLY £20-00. Post 75p.

* ATTRACTIVE, ROBUST, FULLY VENTILATED METAL CASE for the Super Hy-Light Kit including reflector. £7-00. Post 60p.

* FOR HY-LIGHT STROBE incl. reflector, £4-75. Post 25p.

* 7-INCH POLISHED REFLECTOR. Ideally suited for above Strobe Kits. Price 55p. Post 15p.

* RAINBOW STROBE FOUR LIGHT CONTROL MODULE

* Will operate four of our Hy-Light or Super Hy-Light Strobes in either 1, 2, 3, 4 sequence; 2+; or all together. Thoroughly tested and reliable. Complete with full connection instructions. Price: £18-00. Post 50p. Send S.A.E. for details.

COLOUR WHEEL PROJECTOR

* Complete with oil filled colour wheel. 100 watt lamp. 200/240V A.C. Features extremely efficient optical system. £18-50. Post 50p.
 * 6 INCH COLOURWHEEL As used for Disco lighting effects, etc. Price £5-00. Post 30p.



1 R.P.M. MOTOR

* 200/240 Volt A.C. 1 r.p.m. synchronous motor 2 watt. A/clock. Spindle 10 mm. long. 3 mm. dia. Motor only 20 mm deep. Fixing centres 44 mm. Price £1-10. Post 5p.

BIG BLACK LIGHT

* 400 Watt. Mercury vapour ultra violet lamp. Extremely compact and powerful source of u.v. innumerable industrial applications also ideal for stage, display, discos etc. P.F. ballast is essential with these bulbs. Price of matched ballast and bulb £16-00. Post £1. Spare bulb £7-00. Post 40p.



BLACK LIGHT FLUORESCENT U.V. TUBES

* 4ft. 40 watt. Price £5-50. Post 30p. 2ft. 20 watt £4-25. Post 25p. (For use in stan bi-pin fittings.). MINI. 12in. 8 watt £1-60. Post 15p. 9in. 6 watt £1-30. Post 15p. Complete ballast unit and holders for 9in., 12in. tube. £1-70. Post 25p. (9in. x 12in. measures approx.).

ELECTRONIC ORGAN KIT

Easy to build, solid state Two full octaves (less sharps and flats). Fitted hardwood case, powered by two penlite 1½v. batteries. Complete set of parts including speaker, etc., together with full instructions and 10 tunes. £3-25. Post 35p.

50 in 1 ELECTRONIC PROJECT KIT

50 easy to build Projects. No soldering, no special tools required. The Kit includes Speaker, meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier etc., etc. Price £8-80.

VAT

All prices are subject to 10% VAT. (10p in the £)

To all orders add 10% VAT to total value of goods including carriage/packaging.



INSULATED TERMINALS
 Available in black, red, white, yellow, blue and green. New 10p each. Incl. P. & P. Minimum order 6.

METER BARGAIN

BALANCE/LEVEL METERS
 100-0-100 Micro Amp. Size 1½in. x 1½in. x ½in. Price only 70p. Post 5p.



METERS NEW! 2½in. FLUSH ROUND
 available as D.C. Amps 1, 5, 10, 15, 20 or A.C. Amps 1, 5, 10, 15, 20. Both types £1-85. Post 15p.
VOLT/METER 0-300V. A.C. £2-00. Post 15p.



RELAYS				SIEMENS PLESSEY, etc. MINIATURE RELAYS			
1	2	3	4	1	2	3	4
52	4-6	6M	60p*	700	12-24	2 c/o	60p*
				700	15-35	2c/oHD	70p*
150	6-12	4 c/o	80p*	700	6-12	6 M	60p*
185	8-12	6 M	80p*	700	20-30	6 c/o	80p*
280	8-16	2 c/o	60p*	1250	24-36	4 c/o	60p*
410	10-18	4 c/o	70p*	2500	36-45	6 M	80p*
600	9-18	2 c/o	60p*	2400	30-48	4 c/o	50p*
700	16-24	4M2B	60p*	9000	40-70	2 c/o	50p*
700	16-24	4 c/o	80p*	15k	85-110	6 M	50p*

(1) Coil ohms; (2) Working d.c. volts; (3) Contacts; (4) Price HD=Heavy Duty. All Post Paid. (*Including Base)

9 VOLT D.C. RELAY

3 c/o 5 amp contacts. 70 ohm coil. 75p. Post 5p.

12 VOLT D.C. RELAY

3 c/o 5 amp contacts. 120 ohm coil. 75p. Post 5p.

230 VOLT A.C. 'DIAMOND H' RELAYS (Unused)

Three sets c/o contacts rated at 5 amps. Price 55p Inc. P. & P. (100 lots £40-00). 24 volt A.C. 3 c/o 55p. Post 5p.



230 VOLT A.C. RELAYS

One set c/o contacts rated at 7.5 amps. Boxed. Price 50p. Post 5p.

MINIATURE RELAYS

3-12 volt D.C. operation. 2 c/o 500 M.A. contacts. Size only 1 in. x ½ in. Price 60p. Post 5p.

30-36 v. D.C. operation. 2 c/o 500 M.A. contacts. 3,200 ohm coil. Size only 1 x ½ x ½ in. 40p. Post 5p.

MINIATURE LATCHING RELAY

Mfg. by Clare-Elliott Ltd. (Type F) 2 c/o permanent latching in either direction. Coil 1150 ohm. 15-30 v. D.C. New 85p. Post 5p.

BLOWER UNIT

200-240 Volt A.C. BLOWER UNIT Precision German built. Dynamically balanced, quiet, continuously rated, reversible motor. Consumption 60mA. Size 120mm. dia. x 60mm. deep. Price £3-00. Post 30p.

230V FAN ASSEMBLY

Continuously rated, special sealed bearing, removable aluminium blades. Price 80p. Post 20p.



4 BANK 3 c/o PUSH BUTTON ASSEMBLY

Complete with black rectangular buttons. 5 units 85p. Post 15p. (5 units min.).



POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.
 25 WATT 1/10/25/50/100/250/500/1k/2.5k ohm 85p. P. 10p.
 50 WATT 1/15/10/25/50/100/250/500/1k/1.5k/2.5k/5k ohm £1-35. Post 10p.
 100 WATT 1/15/10/25/50/100/250/500/1k/1.5k/2.5k/3.5k/5k ohm £1-95. Post 15p.
Black Silver Skirted knob calibrated in Nos. 1-9. 1 ½ in. dia brass bush. Ideal for above Rheostats, 22p ea.

UNISELECTOR SWITCHES-NEW

4 BANK 25 WAY FULL WIPER 25 ohm coil, 24 v. D.C. operation £6-90. Post 30p.
 6 BANK 25 WAY FULL WIPER 25 ohm coil, 24 v. D.C. £7-90. Post 30p.
 8 BANK 25 WAY FULL WIPER 24 v. D.C. operation £9-50. Post 40p.



BODINE TYPE N.C.I. GEARED MOTOR

(Type J) 71 r.p.m. torque 10 lb. In. Reversible 1/70th h.p. cycle 38 amp. (Type 2) 28 r.p.m. torque 20 lb. In. Reversible 1/80th h.p. 50 cycle 28 amp. The above two precision made U.S.A. motors are offered in 'as new' condition. Input voltage of motor 115v A.C. Supplied complete with transformer for 230/240v A.C. Input. Price, either type £4-84 or less transformer £2-75. These motors are ideal for rotating aerials, drawing curtains, display stands, vending machines, etc.



600 WATT DIMMER SWITCH

Easily fitted. Fully guaranteed by makers. Will control up to 600 watts of all lights except fluorescent at mains voltage. Complete with simple instructions. £2-75. Post 25p.



ALL MAIL ORDERS, ALSO CALLERS AT:

57 BRIDGMAN ROAD, CHISWICK, LONDON, W4 5BB. Phone: 01-995 1560
 Closed Saturdays.

SERVICE TRADING CO.

SHOWROOMS NOW OPEN
 AMPLE PARKING

PERSONAL CALLERS ONLY

9 LITTLE NEWPORT STREET, LONDON, WC2H 7JJ.
 Tel.: 01-437-0576

The largest selection

BRAND NEW FULLY GUARANTEED DEVICES

AC107	0-22	AD162	0 37	BC148	0-11	BD136	0-44	BF165	0-33	MPF105	0-41	2G344	0-20	2N2217	0-24	2N3053	0-19	2N4059	0-11
AC113	0-22	AD161	0	BC149	0-13	BD137	0-50	BF168	0-44	OC19	0-39	2G445	0-18	2N2218	0-22	2N3054	0-51	2N4060	0-13
AC115	0-26	AD162 (M)		BC150	0-20	BD138	0-55	BF194	0-13	OC20	0-70	2G471	0-18	2N2219	0-22	2N3055	0-55	2N4061	0-13
AC117K	0-22		0 61	BC151	0-22	BD139	0-61	BF195	0-13	OC22	0-42	2G371B	0-13	2N2220	0-24	2N3091	0-16	2N4062	0-13
AC122	0-13	AD114	0 55	BC152	0-19	BD140	0-66	BF196	0-16	OC23	0-48	2G373	0-19	2N2221	0-22	2N3391A	0-18	2N4284	0-19
AC125	0-19	AF114	0 27	BC153	0-31	BD155	0-88	BF197	0-16	OC24	0-62	2G374	0-19	2N2222	0-22	2N3392	0-16	2N4285	0-19
AC126	0-19	AF115	0 27	BC154	0-33	BD175	0-66	BF200	0-50	OC25	0-42	2G377	0-33	2N2223	0-22	2N3393	0-16	2N4286	0-19
AC127	0-19	AF116	0 27	BC157	0-20	BD176	0-66	BF222	1-05	OC26	0-58	2G378	0-18	2N2224	0-19	2N3394	0-16	2N4287	0-19
AC128	0-19	AF117	0 27	BC158	0-13	BD177	0-72	BF257	0-50	OC28	0-55	2G381	0-18	2N2225	0-16	2N3395	0-16	2N4288	0-19
AC132	0-16	AF118	0 39	BC159	0-13	BD178	0-72	BF258	0-56	OC29	0-55	2G382	0-18	2N2411	0-27	2N3402	0-23	2N4289	0-19
AC134	0-16	AF124	0 33	BC161	0-55	BD180	0-77	BF259	0-56	OC35	0-48	2G401	0-33	2N2412	0-27	2N3403	0-23	2N4290	0-19
AC137	0-16	AF125	0 28	BC162	0-13	BD185	0-83	BF262	0-61	OC36	0-55	2G414	0-33	2N2646	0-52	2N3404	0-31	2N4291	0-19
AC141	0-16	AF126	0 31	BC167	0-13	BD186	0-72	BF263	0-61	OC41	0-82	2G417	0-28	2N2711	0-23	2N3405	0-46	2N4292	0-19
AC141K	0-19	AF127	0 31	BC168	0-13	BD187	0-72	BF270	0-39	OC42	0-27	2N388	0-33	2N2712	0-23	2N3414	0-17	2N4293	0-19
AC142	0-16	AF129	0 33	BC169	0-13	BD188	0-77	BF271	0-33	OC44	0-37	2N388A	0-31	2N2714	0-23	2N3415	0-17	2N4294	0-19
AC142K	0-19	AF178	0 33	BC170	0-13	BD188	0-77	BF272	0-38	OC45	0-14	2N2904	0-16	2N2904A	0-23	2N3417	0-31	2N4295	0-19
AC151	0-17	AF179	0 55	BC171	0-16	BD189	0-99	BF273	0-39	OC49	0-11	2N2404A	0-31	2N2904B	0-23	2N3417	0-31	2N4296	0-19
AC154	0-22	AF180	0 55	BC172	0-16	BD190	0-83	BF274	0-38	OC71	0-11	2N524	0-46	2N2905	0-23	2N3525	0-31	2N5459	0-35
AC155	0-22	AF181	0 50	BC173	0-16	BD195	0-94	BF275	0-39	OC72	0-16	2N527	0-54	2N2905A	0-23	2N3646	0-10	2N5459	0-35
AC156	0-22	AF186	0 50	BC174	0-16	BD196	0-94	BF276	0-39	OC74	0-16	2N528	0-54	2N2906	0-17	2N3702	0-11	2N5459	0-35
AC157	0-27	AF239	0-41	BC175	0-24	BD197	0-99	BF277	0-39	OC75	0-17	2N529	0-54	2N2906A	0-20	2N3703	0-11	2N5459	0-35
AC165	0-22	AL102	0-72	BC177	0-21	BD198	0-99	BF278	0-39	OC79	0-17	2N530	0-54	2N2907	0-24	2N3705	0-11	2N5459	0-35
AC166	0-22	AL103	0-72	BC178	0-21	BD198	0-99	BF279	0-39	OC81	0-17	2N531	0-54	2N2923	0-16	2N3706	0-10	2N5459	0-35
AC167	0-22	ASV29	0-28	BC179	0-21	BD199	0-99	BF280	0-39	OC81D	0-17	2N532	0-54	2N2924	0-16	2N3707	0-12	2N5459	0-35
AC168	0-27	ASV27	0-33	BC180	0-27	BD205	0-88	BF281	0-39	OC82	0-17	2N533	0-54	2N2925	0-16	2N3708	0-08	2N5459	0-35
AC169	0-16	ASV28	0-28	BC181	0-27	BD206	0-88	BF282	0-39	OC82D	0-17	2N534	0-54	2N2926	0-16	2N3709	0-08	2N5459	0-35
AC176	0-22	ASV29	0-28	BC182	0-11	BD207	1-05	BF283	0-39	OC83	0-22	2N535	0-54	2N2927	0-16	2N3710	0-08	2N5459	0-35
AC177	0-27	ASV30	0-28	BC182L	0-11	BD208	1-05	BF284	0-39	OC84	0-22	2N536	0-54	2N2928	0-16	2N3711	0-08	2N5459	0-35
AC178	0-31	ASV31	0-28	BC183	0-11	BDY20	1-10	BF285	0-39	OC85	0-22	2N537	0-54	2N2929	0-16	2N3712	0-08	2N5459	0-35
AC179	0-31	ASV32	0-28	BC183L	0-11	BF15	0-27	BF286	0-39	OC89	0-22	2N538	0-54	2N2930	0-16	2N3713	0-08	2N5459	0-35
AC180	0-19	ASV34	0-28	BC184	0-13	BF17	0-50	BF287	0-39	OC91	0-22	2N539	0-54	2N2931	0-16	2N3714	0-08	2N5459	0-35
AC180K	0-22	ASV35	0-28	BC184L	0-13	BF18	0-77	BF288	0-39	OC92	0-22	2N540	0-54	2N2932	0-16	2N3715	0-08	2N5459	0-35
AC181	0-19	ASV36	0-28	BC186	0-31	BF19	0-77	BF289	0-39	OC93	0-22	2N541	0-54	2N2933	0-16	2N3716	0-08	2N5459	0-35
AC181K	0-22	ASV37	0-28	BC187	0-31	BF19	0-77	BF290	0-39	OC94	0-22	2N542	0-54	2N2934	0-16	2N3717	0-08	2N5459	0-35
AC187	0-24	ASV38	0-28	BC207	0-12	BF123	0-55	BF291	0-39	OC95	0-22	2N543	0-54	2N2935	0-16	2N3718	0-08	2N5459	0-35
AC187K	0-22	ASZ21	0-44	BC208	0-12	BF125	0-55	BF292	0-39	OC96	0-22	2N544	0-54	2N2936	0-16	2N3719	0-08	2N5459	0-35
AC189	0-24	BC107	0-10	BC209	0-12	BF127	0-55	BF293	0-39	OC97	0-22	2N545	0-54	2N2937	0-16	2N3720	0-08	2N5459	0-35
AC189K	0-22	BC106	0-10	BC212L	0-12	BF152	0-61	BF294	0-39	OC98	0-22	2N546	0-54	2N2938	0-16	2N3721	0-08	2N5459	0-35
ACV17	0-28	BC109	0-11	BC213L	0-12	BF153	0-60	BF295	0-39	OC99	0-22	2N547	0-54	2N2939	0-16	2N3722	0-08	2N5459	0-35
ACV18	0-22	BC113	0-11	BC214L	0-12	BF154	0-60	BF296	0-39	OC100	0-22	2N548	0-54	2N2940	0-16	2N3723	0-08	2N5459	0-35
ACV19	0-22	BC114	0-17	BC225	0-28	BF155	0-77	BF297	0-39	OC101	0-22	2N549	0-54	2N2941	0-16	2N3724	0-08	2N5459	0-35
ACV20	0-22	BC115	0-17	BC226	0-29	BF156	0-77	BF298	0-39	OC102	0-22	2N550	0-54	2N2942	0-16	2N3725	0-08	2N5459	0-35
ACV21	0-22	BC116	0-17	BC227	0-30	BF157	0-81	BF299	0-39	OC103	0-22	2N551	0-54	2N2943	0-16	2N3726	0-08	2N5459	0-35
ACV22	0-18	BC117	0-17	BCY30	0-27	BF158	0-81	BF300	0-39	OC104	0-22	2N552	0-54	2N2944	0-16	2N3727	0-08	2N5459	0-35
ACV27	0-20	BC118	0-11	BCY31	0-29	BF159	0-86	BF301	0-39	OC105	0-22	2N553	0-54	2N2945	0-16	2N3728	0-08	2N5459	0-35
ACV28	0-21	BC119	0-33	BCY32	0-33	BF160	0-44	BF302	0-39	OC106	0-22	2N554	0-54	2N2946	0-16	2N3729	0-08	2N5459	0-35
ACV29	0-39	BC120	0-88	BCY33	0-24	BF162	0-44	BF303	0-39	OC107	0-22	2N555	0-54	2N2947	0-16	2N3730	0-08	2N5459	0-35
ACV30	0-31	BC125	0-13	BCY34	0-28	BF163	0-44	BF304	0-39	OC108	0-22	2N556	0-54	2N2948	0-16	2N3731	0-08	2N5459	0-35
ACV31	0-31	BC126	0-20	BCY70	0-20	BF164	0-44	BF305	0-39	OC109	0-22	2N557	0-54	2N2949	0-16	2N3732	0-08	2N5459	0-35
ACV34	0-23	BC132	0-13	BCY71	0-20	BF165	0-44	BF306	0-39	OC110	0-22	2N558	0-54	2N2950	0-16	2N3733	0-08	2N5459	0-35
ACV35	0-23	BC134	0-20	BCY72	0-16	BF167	0-24	BF307	0-39	OC111	0-22	2N559	0-54	2N2951	0-16	2N3734	0-08	2N5459	0-35
ACV36	0-31	BC135	0-13	BCZ10	0-22	BF173	0-24	BF308	0-39	OC112	0-22	2N560	0-54	2N2952	0-16	2N3735	0-08	2N5459	0-35
ACV40	0-19	BC136	0-17	BCZ11	0-28	BF176	0-34	BF309	0-39	OC113	0-22	2N561	0-54	2N2953	0-16	2N3736	0-08	2N5459	0-35
ACV41	0-20	BC137	0-17	BCX12	0-28	BF177	0-39	BF310	0-39	OC114	0-22	2N562	0-54	2N2954	0-16	2N3737	0-08	2N5459	0-35
ACV44	0-39	BC139	0-44	BD121	0-86	BF178	0-33	BF311	0-39	OC115	0-22	2N563	0-54	2N2955	0-16	2N3738	0-08	2N5459	0-35
AD130	0-42	BC140	0-33	BD123	0-28	BF179	0-33	BF312	0-39	OC116	0-22	2N564	0-54	2N2956	0-16	2N3739	0-08	2N5459	0-35
AD140	0-53	BC141	0-33	BD124	0-66	BF180	0-33	BF313	0-39	OC117	0-22	2N565	0-54	2N2957	0-16	2N3740	0-08	2N5459	0-35
AD142	0-53	BC142	0-33	BD131	0-55	BF181	0-33	BF314	0-39	OC118	0-22	2N566	0-54	2N2958	0-16	2N3741	0-08	2N5459	0-35
AD143	0-43	BC143	0-33	BD132	0-66	BF182	0-44	BF315	0-39	OC119	0-22	2N567	0-54	2N2959	0-16	2N3742	0-08	2N5459	0-35
AD149	0-55	BC145	0-50	BD133	0-72	BF183	0-44	BF316	0-39	OC120	0-22	2N568	0-54	2N2960	0-16	2N3743	0-08	2N5459	0-35
AD161	0-37	BC147	0-11	BD135	0-44	BF184	0-28	BF317	0-39	OC121	0-22	2N569	0-54	2N2961	0-16	2N3744	0-08	2N5459	0-35

BD136	0-44	BF165	0-33	MPF105	0-41	2G344	0-20	2N2217	0-24	2N3053	0-19	2N4059	0-11
BD137	0-50	BF168	0-44	OC19	0-39	2G445	0-18	2N2218	0-22	2N3054	0-51	2N4060	0-13
BD138	0-55	BF194	0-13	OC20	0-70	2G471	0-18	2N2219	0-22	2N3055	0-55	2N4061	0-13
BD139	0-61	BF195	0-13	OC22									

-the lowest prices!

74 Series T.T.L. I.C.'S

BI-PAK STILL LOWEST IN PRICE FULL SPECIFICATION
GUARANTEED. ALL FAMOUS MANUFACTURERS



	1	25	100+		1	25	100+		1	25	100+
SN7400	0.17	0.16	0.13	SN7450	0.17	0.16	0.13	SN74141	0.74	0.71	0.64
SN7401	0.17	0.16	0.13	SN7451	0.17	0.16	0.13	SN74145	£1.65	£1.54	£1.43
SN7402	0.17	0.16	0.13	SN7453	0.17	0.16	0.13	SN74150	£3.30	£2.97	£2.75
SN7403	0.17	0.16	0.13	SN7454	0.17	0.16	0.13	SN74151	£1.10	£1.05	0.99
SN7404	0.17	0.16	0.13	SN7460	0.17	0.16	0.13	SN74153	£1.32	£1.21	£1.05
SN7405	0.17	0.16	0.13	SN7470	0.32	0.29	0.27	SN74154	£1.98	£1.87	£1.76
SN7406	0.39	0.34	0.31	SN7472	0.32	0.29	0.27	SN74155	£1.54	£1.43	£1.32
SN7407	0.39	0.34	0.31	SN7473	0.41	0.39	0.35	SN74156	£1.54	£1.43	£1.32
SN7408	0.20	0.19	0.18	SN7474	0.41	0.39	0.35	SN74157	£2.09	£1.98	£1.87
SN7409	0.20	0.19	0.18	SN7475	0.50	0.48	0.46	SN74160	£1.98	£1.87	£1.76
SN7410	0.17	0.16	0.13	SN7476	0.44	0.43	0.42	SN74161	£1.98	£1.87	£1.76
SN7411	0.28	0.27	0.26	SN7480	0.74	0.71	0.64	SN74162	£4.40	£4.13	£3.85
SN7412	0.39	0.34	0.31	SN7481	£1.32	£1.27	£1.21	SN74163	£4.40	£4.13	£3.85
SN7413	0.32	0.29	0.27	SN7482	0.96	0.95	0.94	SN74164	£2.43	£2.37	£2.31
SN7416	0.48	0.44	0.42	SN7483	£1.10	£1.05	0.99	SN74165	£2.48	£2.42	£2.37
SN7417	0.48	0.44	0.42	SN7484	£1.10	£1.05	0.99	SN74166	£3.85	£3.58	£3.30
SN7420	0.17	0.16	0.13	SN7485	£3.98	£3.85	£3.74	SN74174	£2.53	£2.42	£2.31
SN7422	0.55	0.53	0.50	SN7486	0.35	0.34	0.33	SN74175	£1.76	£1.65	£1.54
SN7423	0.55	0.53	0.50	SN7489	£6.05	£5.76	£5.50	SN74176	£2.75	£2.64	£2.53
SN7425	0.55	0.53	0.50	SN7490	0.74	0.71	0.64	SN74177	£2.75	£2.64	£2.53
SN7426	0.50	0.48	0.44	SN7491	£1.10	£1.05	0.99	SN74180	£2.20	£2.16	£2.12
SN7427	0.50	0.48	0.44	SN7492	0.74	0.71	0.64	SN74181	£6.05	£5.50	£5.23
SN7428	0.77	0.72	0.66	SN7493	0.74	0.64	0.64	SN74182	£2.20	£2.09	£1.98
SN7430	0.17	0.16	0.13	SN7494	0.85	0.82	0.75	SN74184	£3.85	£3.58	£3.30
SN7432	0.50	0.46	0.44	SN7495	0.85	0.82	0.75	SN74190	£2.15	£2.09	£2.04
SN7433	0.88	0.83	0.77	SN7496	0.96	0.93	0.86	SN74191	£2.09	£2.04	£1.98
SN7437	0.71	0.68	0.66	SN74100	£1.82	£1.76	£1.71	SN74192	£2.15	£2.09	£2.04
SN7438	0.71	0.68	0.66	SN74104	£1.07	£1.04	0.97	SN74193	£2.20	£2.16	£2.12
SN7440	0.17	0.16	0.13	SN74105	£1.07	£1.04	0.97	SN74194	£2.97	£2.86	£2.75
SN7441	0.74	0.71	0.64	SN74107	0.44	0.42	0.40	SN74195	£2.20	£2.09	£1.98
SN7442	0.74	0.71	0.64	SN74110	0.61	0.59	0.55	SN74196	£1.98	£1.87	£1.76
SN7443	£1.43	£1.38	£1.32	SN74111	£1.38	£1.27	£1.21	SN74197	£1.98	£1.87	£1.76
SN7444	£1.43	£1.38	£1.32	SN74116	£1.10	£1.05	0.99	SN74198	£6.05	£5.50	£5.23
SN7445	£1.98	£1.93	£1.83	SN74119	£1.40	£1.38	£1.21	SN74199	£6.05	£5.50	£5.23
SN7446	£1.07	£1.04	0.97	SN74121	0.49	0.41	0.38	3 Terminal Pos Volt Reg. TO-3			
SN7447	£1.20	£1.07	£1.05	SN74122	£1.54	£1.43	£1.21	Plastic O/P 1.5 Amps. uA7805			
SN7448	£1.10	£1.07	£1.05	SN74123	£3.08	£2.97	£2.86	5V. uA7812 12V. uA7812 each.			

The AL50 HI-FI AUDIO AMPL 50W pk 25w (RMS)

0.1% DISTORTION! HI-FI AUDIO AMPLIFIER

- Frequency Response 15Hz to 100,000—1dB.
- Load—3, 4, 8 or 16 ohms. • Supply voltage 10-35 Volts.
- Distortion—better than 0.1% at 1kHz.
- Signal to noise ratio 80dB.
- Overall size 63 mm x 105 mm x 13 mm.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry conceived to fill the need for all your A.F. amplification needs.

FULLY BUILT—TESTED—GUARANTEED.

BRITISH MADE. only £3.58 each



STABILISED POWER

MODULE SPM80

£3.25



AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 wats (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63 mm x 105 mm x 20 mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including: Disco Systems, Public Address, Intercom Units, etc. Handbook available, 10p.

TRANSFORMER BMT80 £2.15 p. & p. 25p

NUMERICAL INDICATOR TUBES

MODEL	CD66	GR116	3015F Minित्रon
Anode voltage (Vdc)	170min	175min	5
Cathodic Current (mA)	2-3	14	8
Numerical Height (mm)	16	13	9
Tube Height (mm)	47	32	22
Tube Diameter (mm)	19	13	12 wide
I.C. Driver Rec.	BP41/14 141	BP41 or 141	BP47
PRICE EACH	£1.87	£1.70	£1.50

All indicators 0-9 + Decimal point. All side viewing. Full data for all types available on request.

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

SPECIFICATION:

- Frequency response 20Hz—20kHz ±1dB
- Harmonic distortion better than 0.1%
- Inputs: 1. Tape head 1.2mV into 50KΩ
- 2. Radio, Tuner 35mV into 50KΩ
- 3. Magnetic P.U. 1.5mV into 50KΩ
- All input voltages are for an output of 250mV.
- Tape and P.U. inputs equalised to RIAA curve within ±1dB from 20Hz to 20kHz.
- Bass control ±15dB at 20Hz
- Treble control ±15dB at 20kHz
- Filters: Rumble (high pass) 8kHz
- Scratch (low pass) better than +65dB
- Signal/noise ratio -23dB
- Input overload +35 volts at 20mA
- Supply 292 x 82 x 35 mm
- Dimensions

SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £25.30 FREE p.&p. only £13.15



INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Part-Functional Units. These are classified as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	= 12 x 7400	0.55	UIC46	= 5 x 7446	0.55	UIC90	= 5 x 7490	0.55
UIC01	= 12 x 7401	0.55	UIC48	= 5 x 7448	0.55	UIC91	= 5 x 7491	0.55
UIC02	= 12 x 7402	0.55	UIC50	= 12 x 7450	0.55	UIC92	= 5 x 7492	0.55
UIC03	= 12 x 7403	0.55	UIC51	= 12 x 7451	0.55	UIC93	= 5 x 7493	0.55
UIC04	= 12 x 7404	0.55	UIC53	= 12 x 7453	0.55	UIC94	= 5 x 7494	0.55
UIC05	= 12 x 7405	0.55	UIC54	= 12 x 7454	0.55	UIC95	= 5 x 7495	0.55
UIC06	= 8 x 7406	0.55	UIC80	= 12 x 7460	0.55	UIC96	= 5 x 7496	0.55
UIC07	= 8 x 7407	0.55	UIC70	= 8 x 7470	0.55	UIC100	= 5 x 74100	0.55
UIC10	= 12 x 7410	0.55	UIC72	= 8 x 7472	0.55	UIC121	= 5 x 74121	0.55
UIC20	= 12 x 7420	0.55	UIC73	= 8 x 7473	0.55	UIC131	= 5 x 74131	0.55
UIC30	= 12 x 7430	0.55	UIC74	= 8 x 7474	0.55	UIC154	= 5 x 74154	0.55
UIC40	= 12 x 7440	0.55	UIC76	= 8 x 7476	0.55	UIC193	= 5 x 74193	0.55
UIC41	= 5 x 7441	0.55	UIC80	= 5 x 7480	0.55	UIC199	= 5 x 74199	0.55
UIC42	= 5 x 7442	0.55	UIC81	= 5 x 7481	0.55			
UIC43	= 5 x 7443	0.55	UIC82	= 5 x 7482	0.55			
UIC44	= 5 x 7444	0.55	UIC83	= 5 x 7483	0.55			
UIC45	= 5 x 7445	0.55	UIC86	= 5 x 7486	0.55			

Packs cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC X1.

NEW COMPONENT PAK BARGAINS

Pack No.	Qty.	Description	Price
C 1	250	Resistors mixed values approx. count by weight	0.55
C 2	200	Capacitors mixed values approx. count by weight	0.55
C 3	50	Precision Resistors 1%, mixed values	0.55
C 4	75	1/4 W Resistors mixed preferred values	0.55
C 5	3	Pieces assorted Ferrite Rods	0.55
C 6	2	Tuning Gangs, MW/LW/VHF	0.55
C 7	1	Pack Wire 50 metres assorted colours	0.55
C 8	10	Reed Switches	0.55
C 9	3	Micro Switches	0.55
C10	15	Assorted Pots & Pre-Sets	0.55
C11	5	Jack Sockets 3 x 3.5mm 2 x Standard Switch Types	0.55
C12	40	Paper Condensers preferred types mixed values	0.55
C13	20	Electrolytics Trans. Types	0.55
C14	1	Pack assorted Hardware—Nuts/Bolts, Grommets etc.	0.55
C15	4	Mains Toggle Switches, 2 Amp D/P	0.55
G16	20	Assorted Tag Strips & Panels	0.55
C17	10	Assorted Control Knobs	0.55
C18	4	Rotary Wave Change Switches	0.55
C19	3	Relays 6—24V Operating	0.55
C20	4	Sheets Copper Laminate approx. 10" x 7"	0.55

RTL MICROLOGIC CIRCUITS

	Price each		
	1-24	25-99	100 up
Epoxy TO-5 case uL900			
Buffer	38p	36p	29p
uL914 Dual 2i/p gate	38p	36p	28p
uL923 J-K flip-flop	55p	51p	46p

Data and Circuits Booklet for IC's Price 8p.

DUAL-IN-LINE IC'S. TWO RANGES	PROF. TYPE No.	1-24	25-99	100 up.
TSO 14 pin type		33p	30p	28p
"16 pin type		39p	35p	33p
LOW COST No.				
BPS 14		17p	15p	12p
BPS 16		18p	16p	13p

LINEAR I.C.'S—FULL SPEC.

Type No.	1-24	25-99	100 up
BP 201C—SL201C	70p	58p	50p
BP 701C—SL701C	70p	56p	50p
BP 702C—SL702C	70p	56p	50p
BP 702—72702	56p	50p	44p
BP 709—72709	40p	38p	33p
BP 709P—uA709C	40p	39p	33p
BP 710—72710	49p	46p	44p
BP 711—uA711	50p	48p	44p
BP 741—72741	55p	50p	45p
uA703C	31p	29p	27p
TAA 263—	77p	66p	61p
TAA 293—	99p	89p	77p
TAA 350	£1.87p	£1.74p	£1.66p

P. F. RALFE

10 Chapel St London N.W.1

Phone 01-723 8753

TELEVISION SWEEP GENERATOR

by Sweep systems type 505. Frequency coverage 450-940MHz. (Channels 15-80). Markers at 465/565/660/750/830 and 900MHz. Attenuated output in eight, five db steps and fine 0-10 db. Sweep width adjustable from 1-15MHz. The instrument is completely solid-state using variactor diodes and transistors throughout. Dims: 19 x 12 x 5ins. Wt.: 20lbs. Supplied in good working order, price **£59.50** + 50p carriage.



AERIAL CHANGE/OVER RELAYS of current manufacture designed especially for mobile equipments, coil voltage 12v., frequency up to 250MHz at 50 watts. Small size only, 2 in. x 1/2 in. Offered brand new, boxed. Price **£1.50**, inc. P.&P.

'ALCAD' Sealed rechargeable Nickel-cadmium batteries. Type Vv3.5, 1.2V at 3.5 Ah. Size as 'U2'. Offered new in packs supplying 12V, **£15**. Or separately at **£1.25**.

Automatic Constant current electronic battery chargers specially designed for nickel cadmium cells. Metered and fused. Up to twelve cells can be charged up to 750mA, variable 0-750mA. Size 7x6x5ins. Brand new units. Price each **£17**.

Smiths Ltd Weight indicators, self powered, measures 0 to 20 cwt in 1 cwt divisions on a 4" circular meter indicator, 30 feet of cable and heavy duty load cell use with bell crank or actual reading is 5 cwt for F.S.D. brand new units special price **£7.50** post 50p.

Cossor Electronic Invertors type CRA 200. A high quality device for producing a 115v 400Hz single phase output. Incorporating the following features: Input 23-28V D.C.
 * Full overload protection.
 * Sine wave output.
 * Remote control facilities.
 * Completely Solid State (Silicon transistors).
 * Built to Aircraft specifications.
 * 180VA of output continuous.
 May be run in series operation for 3 phase requirements. Offered brand new boxed units. Price **£17.50** Carriage 50p.

AUDIO OSCILLATORS AMERICAN TS-382/U

Covers 20 c/s-200 Kc/s in four ranges. Output voltage 1 micro volt to 10 v. in seven ranges. Built in calibrator. Sine wave O.P. is excellent over complete range. Supplied with transmit case, adaptors and circuits and transformer for 240 A.C. **£20**.

MINIATURE AEI UNISELECTORS 12 position x 3 bank 250 ohm coils, 1 bridging and 2 non-bridging wipers available now—Type 2200A complete with bases. Price **£4**.

BRAND NEW DIGITAL PANEL VOLTMETERS 10MV-1.99V. 199 Measuring points. Input impedance 100Mohm. Automatic zeroing. Measurements: 155mm x 72mm x 72mm. List price was **£52.00**. OUR PRICE **£24.50**.

DIGITAL MEASUREMENT Type 2003 Digital Voltmeter. 3 1/2 Digit display. Measuring up to 1000 Volts. AS NEW **£65**.

Noise Generator Model CT-82 Range 15kHz to 160MHz very useful noise for factor measurements of receivers/wide band I.F. amplifiers etc., the instrument is directly calibrated in noise factor and displayed on panel meter, also output meter calibrated in db, for 115-250 vac operation offered in good used condition, small size low price only **£8** Carr. 50p.

H. W. SULLIVAN STANDARD AIR SPACED CONDENSERS Capacitance range 0 to 100 pf fully screened with engraved vernier subdivided into 100 equal divisions complete with vernier index and original manufacturers seal offered brand new, at only **£25** each.

BARGAIN OFFER—LOW VOLTAGE STABILISED POWER SUPPLIES

*Voltage Range 16-24V.
 *Current Range to 6 Amps.
 *Full over-voltage and Current protection.
 *AC Ripple content better than 5mV. These PSUs are constructed to exacting standards and incorporate the very best of components and circuit design for long life and reliability. Employs Silicon transistors, thyristors, C-Core transformer etc. Offered in perfect condition, carefully checked before despatch. List price over **£125**. Our price only **£26.50**. Carriage **£1**.

Cossor Radio Telephones Type CC303

All Solid State except for O-P Valves 25 Watt A.M. offered brand new for high bond applications boot control console. Complete manual supply. Prices **£75** each + V.A.T.

SCHOMANDL PRECISION FREQUENCY METER TYPE FDI WITH FDMI ADAPTOR GPO approved equipment for Radio Telephone Marine servicing etc., offered in as new condition with calibration certificate.

G.E.C. Uniselectors, 8-banks, 25 position full wipe. 75 ohm coil. Not new but excellent working condition. Each **£2**.

Brand new GEC 3 banks of 25 position uniselectors with fitted suppressor. **£2.50** each.

SIX Level A.E.I. Uniselectors miniature plug in type 2216A coil 125 ohms, non-bridging wipers with index. 12 position 6 bank. Absolutely brand new in makers cartons sold complete with base. **£6.50**

CAMBRIDGE PORTABLE POTENTIOMETER type 44228. The ideal tool for checking thermocouples and auxiliary temperature measuring equipment. Accuracy $\pm 0.1\%$. BRAND NEW. **£75**.

TINSLEY type 4363D Vernier potentiometer. Good condition Price **£75**.

FRIGIDAIRE, AIR-CONDITIONING UNIT. Table-top model. 4 inch diameter pipe outlet. Complete and ready for use. Price **£125**.

WAYNE KERR type B521 Component bridge. Accurate measurement of LC & R. **£55**. Excellent order throughout.

TEKTRONIX OSCILLOSCOPES

Type 545A with 'CA' plug-in. (Or 'L'). DC—30MHz.
 Type 561A with 3A1 and 3B3 units. DC—10MHz.
 Type 535 with CA plug-in unit. DC—15MHz.
 Type 551. Double-beam with L&G units. DC—27MHz.



Also available:

Dynamco D7100 with 1Y2 and 1X2 plug-ins. Portable, DC—30MHz.
 Hewlett-Packard 175A, 1781 and 1755A plug-ins. DC—30MHz.
 Marconi TF1300. s/b. DC—15MHz. **£75**.
 Robard RO50A with 5G plug-in. DC—15MHz. Price **£125**.
 Solartron CD1400. With two CX1441 and a CX1443 units.

Extremely sensitive instrument. Twin differential inputs.

SIGNAL GENERATORS

Marconi type TF801D. 10-485MHz. Excellent. **P.U.R.**
 Marconi type TF867. 15KHz-30MHz. **£150**.
 Hewlett-Packard 616A. 1780-4000MHz. **£75**.
 Advance C2H. Spot-frequency production-line test instrument. 12 freqs. in bands 500KHz-30MHz. **£25**.
 Rohde & Schwarz U.H.F. 990-1900MHz. **P.U.R.**
 Rohde & Schwarz SMAF. A.M. & F.M. 4-300MHz. FM Dev. 0-100KHz in 2 ranges. Fundamental-frequency generator ideal for radio-telephone test equipment. **P.U.R.**



MARCONI TEST EQUIPMENT. All items have been calibrated, reconditioned and guaranteed.

Wave Analyser **TF455E**. Frequency range 20Hz. **£105**.
TF893 Audio Wattmeter. Range 20Hz-35KHz. Power range 20uW-10W. Impedance 2.5 Ω to 20K Ω in 48 steps. Direct calibration in Watts and dbm. Price **£45**.
TF2600 Sensitive Valve Voltmeter 1mV f.s.d. to 300V f.s.d. Accuracy $\pm 1\%$. Offered as new, price **£55**.
TF1370A Wide-range oscillator 10Hz to 10Mz. Squarewave up to 100KHz. High output—up to 1MHz 31 Volts. 75,100 or 600 Ω output. List price pre VAT—**£308**. Offered as new at **£125**.
TF2162 MF attenuator. DC-1MHz. 0-111db attenuation in 1db steps. Impedance 600 ohms unbalanced. Price **£50**.
TF2163 U.H.F. Attenuator. DC-1 GHz. 0-142db in 1db steps. Z, 50 ohms. Max. power input 0.5W. As new Price **£75**.
TF801D/I A.M. Signal Generator up to 470MHz.
TF1106 Noise Generator 1-200MHz. **£75**.
TF1041B Voltmeter. 300mV-300V. 20Hz-1500MHz. **£45**.
TF1301 Noise Gen. 200-1700MHz. 50 ohms. **£55**.
TF1099 20MHz Sweep Generator as new **£75**.
OA1094AHF Spectrum Analyser 100KHz-30MHz. As new.
TF1417 Counter, Frequency Meter 7 digits. Plus range extension unit TF1434/2 to 220MHz. As new.

JERROLD 900B Sweep Generator with SD8A sweep driver unit. V.H.F. and U.H.F. 0-1200MHz. centre frequency. 1, 10 and 100MHz markers. Built-in detector, attenuators etc. This instrument is probably the most comprehensive sweeper ever made. **P.U.R.**

ADVANCE AUDIO SIGNAL GENERATOR TYPE H1. 15Hz-50KHz in three ranges. Sine/square wave output. Supplied in first-class working condition. **£15**. Carriage **£1** each.

R216 V.H.F. AM/FM Communications receivers. Coverage 19-157MHz. Film scale dial 2 frequency crystal calibrator. Plus all other facilities. Complete with A.C. power supply connecting lead. Supplied in full working order in excellent secondhand condition.

PLEASE ADD 10% V.A.T. TO THE TOTAL AMOUNT WHEN ORDERING. INCORRECT AMOUNTS WILL CAUSE DELAY IN DESPATCH. THANK YOU.

VALVES

B12H	1.75	ECL82	0.31
CV31	0.40	ECL83	0.31
DAF96	0.40	ECL86	0.36
DF96	0.40	EF36	0.30
DK96	0.40	EF37A	0.35
DL92	0.32	EF40	0.32
DL86	0.45	EF41	0.35
DM70	0.40	EF80	0.25
DY86	0.28	EF83	0.31
DY87	0.28	EF85	0.27
DY802	0.30	EF89	0.25
E80CC/01	1.08	EF81	0.27
E180CC	0.37	EF92	0.31
E180CC	0.90	EF95	0.31
E182CC	1.08	EF188	0.26
EA50	0.18	EF184	0.31
EABC80	0.27	EF1200	0.67
EAF42	0.46	EL34	0.59
EB1	0.20	EL11	0.55
EB33	0.45	EL84	0.21
ECC41	0.50	EL85	0.44
ECC41	0.27	EL86	0.36
EBF80	0.36	EL90	0.31
EBF83	0.40	EL95	0.38
EBF89	0.27	EL500	0.76
ECC81	0.27	EL304	0.78
ECC82	0.25	EM31	0.22
ECC83	0.25	EM80	0.36
ECC84	0.27	EM84	0.31
ECC85	0.36	EM87	0.63
ECC86	0.30	EY31	0.36
ECC88	0.39	EY81	0.40
ECC189	0.48	EY88	0.40
ECP80	0.31	EZ41	0.45
ECP82	0.31	EZ80	0.22
ECP83	0.67	EZ41	0.24
ECP801	0.56	GZ41	0.52
ECH181	0.25	KT66	2.30
ECH183	0.40	KT88	2.25
ECH184	0.40	N78	1.80
ECH80	0.40	OA2	0.38

R17	0.45	UBF80	0.35	VR150/30	0.35
R19	0.35	UBF89	0.34	2800U	1.40
STV	0.41	UCC85	0.34	2801U	1.40
PC080	0.42	UCF80	0.60	2803U	1.10
PC084	0.38	UCH42	0.60	2900T	0.90
PC086	0.45	UCM1	0.35	1L4	0.13
PC089	0.49	UCM2	0.35	1R5	0.35
PC090	0.75	UCL82	0.35	1R4	0.30
PC092	0.27	UCM83	0.55	1T4	0.30
PC094	0.54	UCM84	0.35	1X2A	0.36
PC096	0.50	UCM85	0.35	1X2B	0.36
PC098	0.45	UL1	0.60	2K25	7.50
PC100	0.60	UL4	0.35	3A4	0.40
PC101	0.60	UL5	0.35	3D6	0.15
PC102	0.45	UL6	0.35	3A4	0.40
PC103	0.45	UL7	0.35	3D6	0.15
PC104	0.45	UL8	0.35	3A4	0.40
PC105	0.45	UL9	0.35	3D6	0.15
PC106	0.45	UL10	0.35	3A4	0.40
PC107	0.45	UL11	0.35	3D6	0.15
PC108	0.45	UL12	0.35	3A4	0.40
PC109	0.45	UL13	0.35	3D6	0.15
PC110	0.45	UL14	0.35	3A4	0.40
PC111	0.45	UL15	0.35	3D6	0.15
PC112	0.45	UL16	0.35	3A4	0.40
PC113	0.45	UL17	0.35	3D6	0.15
PC114	0.45	UL18	0.35	3A4	0.40
PC115	0.45	UL19	0.35	3D6	0.15
PC116	0.45	UL20	0.35	3A4	0.40
PC117	0.45	UL21	0.35	3D6	0.15
PC118	0.45	UL22	0.35	3A4	0.40
PC119	0.45	UL23	0.35	3D6	0.15
PC120	0.45	UL24	0.35	3A4	0.40
PC121	0.45	UL25	0.35	3D6	0.15
PC122	0.45	UL26	0.35	3A4	0.40
PC123	0.45	UL27	0.35	3D6	0.15
PC124	0.45	UL28	0.35	3A4	0.40
PC125	0.45	UL29	0.35	3D6	0.15
PC126	0.45	UL30	0.35	3A4	0.40
PC127	0.45	UL31	0.35	3D6	0.15
PC128	0.45	UL32	0.35	3A4	0.40
PC129	0.45	UL33	0.35	3D6	0.15
PC130	0.45	UL34	0.35	3A4	0.40
PC131	0.45	UL35	0.35	3D6	0.15
PC132	0.45	UL36	0.35	3A4	0.40
PC133	0.45	UL37	0.35	3D6	0.15
PC134	0.45	UL38	0.35	3A4	0.40
PC135	0.45	UL39	0.35	3D6	0.15
PC136	0.45	UL40	0.35	3A4	0.40
PC137	0.45	UL41	0.35	3D6	0.15
PC138	0.45	UL42	0.35	3A4	0.40
PC139	0.45	UL43	0.35	3D6	0.15
PC140	0.45	UL44	0.35	3A4	0.40
PC141	0.45	UL45	0.35	3D6	0.15
PC142	0.45	UL46	0.35	3A4	0.40
PC143	0.45	UL47	0.35	3D6	0.15
PC144	0.45	UL48	0.35	3A4	0.40
PC145	0.45	UL49	0.35	3D6	0.15
PC146	0.45	UL50	0.35	3A4	0.40
PC147	0.45	UL51	0.35	3D6	0.15
PC148	0.45	UL52	0.35	3A4	0.40
PC149	0.45	UL53	0.35	3D6	0.15
PC150	0.45	UL54	0.35	3A4	0.40
PC151	0.45	UL55	0.35	3D6	0.15
PC152	0.45	UL56	0.35	3A4	0.40
PC153	0.45	UL57	0.35	3D6	0.15
PC154	0.45	UL58	0.35	3A4	0.40
PC155	0.45	UL59	0.35	3D6	0.15
PC156	0.45	UL60	0.35	3A4	0.40
PC157	0.45	UL61	0.35	3D6	0.15
PC158	0.45	UL62	0.35	3A4	0.40
PC159	0.45	UL63	0.35	3D6	0.15
PC160	0.45	UL64	0.35	3A4	0.40
PC161	0.45	UL65	0.35	3D6	0.15
PC162	0.45	UL66	0.35	3A4	0.40
PC163	0.45	UL67	0.35	3D6	0.15
PC164	0.45	UL68	0.35	3A4	0.40
PC165	0.45	UL69	0.35	3D6	0.15
PC166	0.45	UL70	0.35	3A4	0.40
PC167	0.45	UL71	0.35	3D6	0.15
PC168	0.45	UL72	0.35	3A4	0.40
PC169	0.45	UL73	0.35	3D6	0.15
PC170	0.45	UL74	0.35	3A4	0.40
PC171	0.45	UL75	0.35	3D6	0.15
PC172	0.45	UL76	0.35	3A4	0.40
PC173	0.45	UL77	0.35	3D6	0.15
PC174	0.45	UL78	0.35	3A4	0.40
PC175	0.45	UL79	0.35	3D6	0.15
PC176	0.45	UL80	0.35	3A4	0.40
PC177	0.45	UL81	0.35	3D6	0.15
PC178	0.45	UL82	0.35	3A4	0.40
PC179	0.45	UL83	0.35	3D6	0.15
PC180	0.45	UL84	0.35	3A4	0.40
PC181	0.45	UL85	0.35	3D6	0.15
PC182	0.45	UL86	0.35	3A4	0.40
PC183	0.45	UL87	0.35	3D6	0.15
PC184	0.45	UL88	0.35	3A4	0.40
PC185	0.45	UL89	0.35	3D6	0.15
PC186	0.45	UL90	0.35	3A4	0.40
PC187	0.45	UL91	0.35	3D6	0.15
PC188	0.45	UL92	0.35	3A4	0.40
PC189	0.45	UL93	0.35	3D6	0.15
PC190	0.45	UL94	0.35	3A4	0.40
PC191	0.45	UL95	0.35	3D6	0.15
PC192	0.45	UL96	0.35	3A4	0.40
PC193	0.45	UL97	0.35	3D6	0.15
PC194	0.45	UL98	0.35	3A4	0.40
PC195	0.45	UL99	0.35	3D6	0.15
PC196	0.45	UL100	0.35	3A4	0.40

3B254M	2.75	6AQ5	0.38	6C4	0.25	6K7G	0.17
3B255M	3.10	6AQ5W	0.40	6C6	0.20	6K8GT	0.40
3R4GY	0.65	6AR6	0.30	6CH6	0.55	6K25	0.70
3U4G	0.90	6AT6	0.30	6CL6	0.50	6L6M	1.35
3V4G	0.45	6AU6	0.20	6D6	0.15	6SA7	0.40
3Y3GT	0.75	6AX4GT	0.60	6EA8	0.60	6SA7GT	0.25
5Z3	0.30	6AX5GT	0.60	6F29	0.80	6SC7GT	0.20
5Z4	0.30	6B7	0.35	6F33	1.35	6SN7	0.40
5Z4GT	0.75	6BK7	0.60	6H6M	0.25	6SJ7	0.40
6AB7	0.32	6BA6	0.25	6J4WA	0.65	6SJ7GT	0.28
6AB7B	0.45	6BE8	0.25	6J5	0.35	6SK7	0.45
6AH6	0.50	6BG6G	0.47	6J5GT	0.30	6SL7GT	0.35
6AK5	0.35	6BJ6	0.45	6J6	0.25	6SN7GT	0.35
6AKK	0.30	6B7A	0.43	6J7G	0.30	6SQ7	0.45
6AL5	0.18	6BR7	1.09	6J7M	0.35	6RQ7GT	0.30
6AL5W	0.35	6BW6	0.80	6K6GT	0.55	6X5GT	0.16
6AN8	0.60	6BW7	0.80	6K7	0.40	6Y6GT	0.35
						6X6G	0.25
						6X5GT	0.35
						6Y6G	0.75
						6-30L2	0.85
						6Z4	0.40
						7B7	0.50
						7Y4	0.60
						9D6	0.30
						12A2	3.70
						12E7	3.70
						12E7B	3.70
						12AX7	3.70
						12AV6	4.00
						12B6A	4.00
						12BE6	4.00
						12BH7	4.00
						12C6	4.00
						12E6	4.00
						12K5	4.00
						12L6	4.00
						12R6	4.00
						12X6	4.00
						12Y6	4.00
						12Z6	4.00
						12AB6	4.00
						12BE6	4.00
						12BH7	4.00
						12C6	4.00
						12E6	4.00
						12K5	4.00
						12L6	4.00
						12R6	4.00
						12X6	4.00
						12Y6	4.00
						12Z6	4.00
						12AB6	4.00
						12BE6	4.00
						12BH7	4.00
						12C6	4.00
						12E6	4.00
						12K5	4.00
						12L6	4.00
						12R6	4.00
						12X6	4.00
						12Y6	4.00
						12Z6	4.00
						12AB6	4.00
						12BE6	4.00
						12BH7	4.00
						12C6	4.00
						12E6	4.00
						12K5	4.00
						12L6	4.00
						12R6	4.00
						12X6	4.00
						12Y6	4.00
						12Z6	4.00
						12AB6	4.00
						12BE6	4.00
						12BH7	4.00
						12C6	4.00
						12E6	4.00
						12K5	4.00
						12L6	4.00

G.W. SMITH & CO (RADIO) LTD

AUDIOTRONIC MODEL ATM.1

Top value 1000 o.p.v. pocket multimeter.
 Ranges: 0/10/50/250/1000V AC and DC. DC Current 0-1mA/100mA. Resistance 0/150k ohms. Decibels -10 to +22dB. Size 90 x 60 x 25mm. Complete with test leads.
£2.50. Post 15p.



RUSSIAN 22 RANGE MULTIMETER

Model U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2.5/10/50/250/500/1000V D.C. 2.5/10/50/250/500/1000V A.C. D.C. Current 1000 uA/10/100 mA/1A. Resistance 300 ohms/30/300K/3M Ohm. Complete with batteries, test leads, instructions and sturdy steel carrying case.
Our Price £4.95. Post 25p.



MODEL 500

30,000 O.P.V. with overload protection, mirror scale. 0/2.5/10/25/100/250/500/1000 V. D.C. 0/2.5/10/25/100/250/500/1000 V. A.C. 0.30uA/5/50/500mA. 12 amp. D.C. 0/60K/5 meg/60 meg Ohm.
£9.95. Post paid. Leather case £1.75.



U4312 MULTIMETER

Extremely sturdy instrument for general electrical use. 607 o.p.v. 0/31.5/7.5/30/60/150/300/600/900 VDC and 75mV. 0/31.5/7.5/30/60/150/300/600/900 VAC. 0/300 uA/1.5/5/15/60/150/600mA/1.5/5 AMP. D.C. 0/1.5/5/15/60/150/600mA/1.5/5 AMP. A.C. 0/200 uA/30K/300K. Accuracy DC 1%. AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. **£9.75. Post 25p.**



HIOKI MODEL 700X

100,000 O.P.V. Overload protection. Mirror scale. 3/61.2/1-3/3/6/12/30/60/120/300/600/1200 VDC. 1.5/3/6/12/30/60/150/300/600/1200 VAC. 13/30uA/3/6/30/60/150/300 mA. 6/12 AMP DC. 2K/200 K/2 Meg/20 megohm. -20 to +63db.
£18.50. Post 20p.



MODEL C-7080 EN

Giant 6in. mirror scale. 20,000 o.p.v. Ranges: 0/2.5/12.5/50/150/250/1000/5000V D.C. 0/2.5/10/50/250/1000/5000V A.C. 0/500uA/1/10/100/500mA/10 amp. D.C. 0/2K/200K/20 meg. -20 to +50 db.
£13.95. Post 35p.



KAMODEN 72.200 MULTITESTER

High sensitivity tester. 200,000 o.p.v. Overload protection. Mirror scale. Ranges: 0/0.6/3/30/120/600/1200V D.C. 0/2/12/60/300/1,200V A.C. 0/5uA/1.2mA/120mA/600mA/12A D.C. 0/12A A.C. -20 to +63dB. 0/2K/200K/2 meg/200 meg ohms.
£16.95. Post 30p.



TMK LAB TESTER

100,000 O.P.V. 6 1/2 in. Scale Buzzer Short Circuit Check. Sensitivity: 100,000 O.P.V. D.C. 5K/Volt A.C. D.C. Volts: 5, 2.5, 10, 50, 250, 1,000V. A.C. Volts: 3, 10, 50, 250, 500, 1,000V. D.C. Current: 10/100uA, 10, 100, 500mA, 2.5, 10 amp. Resistance: 1K, 10K, 100K, 10MEG, 100MEG. Decibels: -10 to +49 db. Plastic Case with carrying handle. Size 7 1/2 x 6 1/2 x 3 1/2. **£18.95. P. & P. 25p.**



MODEL S-100TR MULTIMETER/TRANSISTOR TESTER

100,000 o.p.v. MIRROR SCALE/OVERLOAD PROTECTION. 0/12-6/3/12/30/120/600 VDC. 0/6/30/120/600 V. A.C. 0/12/600uA/12/300mA/12 Amp. DC. 0/10K/1 MEG/100 MEG. -20 to +40 db. 0-01 -2 mfd. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads. **£13.50. Post 25p.**



ALL PRICES ARE SUBJECT TO 10% V.A.T.


370 WTR MULTIMETER

Features A.C. current ranges. 20,000 o.p.v. Ranges: 0/2.5/10/50/250/500/1000 V DC 0/2.5/10/50/250/500/1000 V AC 0/50uA/1/10/100mA/1/10 Amp DC. 0/100mA/1/10 Amp AC. 0/5K/50K/500K/5MEG/50MEG. -20 + 62 db.
£15. Post 25p.



LB4 TRANSISTOR TESTER

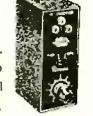Tests PNP or NPN transistors. Audio Indication. Operates on two 1.5v batteries. Complete with all instructions etc. **£4.50. Post 20p.**



LB3 TRANSISTOR TESTER

Tests ICO and B. PNP/ NPN. Operates from 9v. battery. Complete with all instructions etc. **£3.95. Post 20p.**



KAMODEN HM.350 TRANSISTOR TESTER

High quality instrument to test Reverse Leak current and DC current Amplification factor of PNP, PNP, transistors, diodes, SCR's etc. 4in. x 4 1/2in. clear scale meter. Operates from internal batteries. Complete with instructions leads and carrying handle. **£12.50 Post 30p.**



MODEL 449A IN CIRCUIT TRANSISTOR TESTER

Checks true A.C. beta In/out. Checks Iebo. Checks diodes in/out. Checks SCR etc. Beta HI 10-300. LO-2. Iebo 0-5000uA. 220/240V. A.C. operation. **£17.50. Post 25p.**



KAMODEN HM.700B F.E.T. V.O.M.

Input impedance 10 meg. ohms. Ranges: 0/2.5/12.5/50/150/250/1000V D.C. 0/2.5/10/50/250/1000V A.C. 0/25uA/2.5/25/250 MA D.C. -20 to +63dB. 0/5K/50K/500K/5 meg/500 meg ohms.
£14.95. Post 30p.



T.E.40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: 0/1/30/1.3/13/130/100/300 v. R.M.S. 4 cps-1.2 Mc/s. Decibels -40 to +50 dB. Supplied brand new complete with leads and instructions. Operation 230 v. A.C. **£17.50 Carr. 25p.**



TE-65 VALVE VOLTMETER

High quality instrument with 28 ranges. D.C. volts 1.5-1,500 v. A.C. volts 1.5-1,500 v. Resistance up to 1,000 megohms. 220/240V. A.C. operation Complete with probe and instructions. **£17.50. Post 30p.** Additional. Probes available: R.F. £2-12 H.V. £2-50.



MODEL U4311 SUB-STANDARD MULTI-RANGE VOLT AMPMETER

Sensitivity 330 ohms/Volt A.C. and D.C. Accuracy .5% D.C. 1% A.C. Scale length 165mm. 0/300/750uA/1.5/3/7.5/15/30/75/150/300/750mA/1.5/3/7.5/15/30/75/150/300/750V D.C. 0/3/7.5/15/30/75/150/300/750mA/1.5/3/7.5/15/30/75/150/300/750V A.C. 0/750mA/1.5/3/7.5/15/30/75/150/300/750V A.C. Automatic cut out. Supplied complete with test leads, manual and test certificates. **£49. Post 80p.**




TMK MODEL I17 ELECTRONIC VOLTMETER

Battery operated, 11 meg input. 20 ranges. Large 4 1/2in. mirror scale. Size 5 1/2 x 4 1/2 x 2 1/2in. DC Volts 0-3-1200V. AC Volts 3-300V R.M.S. 8-0-800V P-P. DC Current -12-12mA. Resistance up to 2000M ohm. Decibels -20 to +51 db. Complete with leads/instructions. **£17.50. P. & P. 20p.**




KAMODEN HMG-500 INSULATION RESISTANCE TESTER

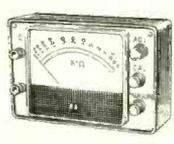Range 0-1000 Meg-ohms, 500 Volt. Battery operated. Wide range clear meter 4 1/2in. x 4in. Complete with de luxe carrying case, batteries, instructions. **£19.95. Post 30p.**




BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

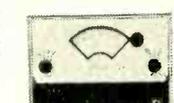Sine 15-200,000 Hz; Square 18-50,000 Hz. Output max. +10 dB (10 K ohms). Operation internal batteries. Attractive 2-tone case 7 1/2in. x 5in. x 2in. Price **£17.50. Carr. 17p.**



CI-5 PULSE OSCILLOSCOPE

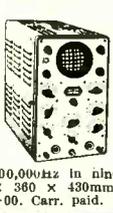For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP. Bandwidth 10MHz. Sensitivity at 100KHz VRMS/nm. 1-25; HOR. AMP. Bandwidth 500KHz. Sensitivity at 100KHz. V RMS/nm. 3-25; Preset triggered sweep 1-3,000usec.; free running 20-200,000Hz in nine ranges. Calibrator pips. 220 x 380 x 430mm. 115-230V. A.C. operation. **£39.00. Carr. paid.**



TO-3 PORTABLE OSCILLOSCOPE 3in. TUBE

Y amp. Sensitivity .1v p-p/CM. Bandwidth 1.5 cps -1.5 MHz. Input Imp. 2 meg Ohm. 25 PF. X amp sensitivity .5v p-p/CM. bandwidth 1.5 cps-800 KHz. Input Imp. 2 meg Ohm 20 PF. Time base 5 ranges 10 cps-300 KHz. Synchronization. Internal/external. Illuminated scale. 140 x 215 x 330mm. Weight 15 1/2lbs. 220/240 V. A.C. Supplied brand new with handbook **£47.50. Carr. 50p.**



RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPE

5 mc/s Pass Band. Separate Y1 and Y2 amplifiers. Rectangular 0in. x 4in. C.R.T. Calibrated triggered sweep from 2 usec. to 100 mill-sec. per cm. Free running time base 50 c/s-1 mcs. Built-in time base calibrator and amplitude calibrator. Supplied complete with all accessories and instruction manual. **£87 Carr. paid.**



MODEL AT201 DECADE ATTENUATOR

Frequency range: 0-200KHz. Attenuator: 0-111db., 0-1db. step. Impedance 600 ohms. Max. input power 30dbm. Size 180 x 90 x 55mm. **£12.50. Post 37p.**



ARF-300 AF/RF SIGNAL GENERATOR

All transistorised compact, fully portable. AF sine wave 18Hz to 220KHz. AF square wave 18Hz. to 100KHz. Output sine/square 10v. P-P. RF 100KHz. to 200 MHz. Output 1v. maximum. Operation 220/240V. A.C. Complete with instructions and leads. **£29.95. Post 50p.**



TE-20 D RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 Kc/s-500 Mc/s on 6 bands. Directly calibrated Variable R.F. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions. Size 140 x 215 x 170 mm. **£17.50. Carr. 37p.**



TE22 SINE SQUARE WAVE AUDIO GENERATORS

Sine: 20 cps to 200 kc/s. on 4 bands. Square 20 cps to 30 kc/s. Output Impedance 5,000 ohms, 500 250 v. A.C. operation. Supplied brand new and guaranteed with instruction manual and lead. **£17.50. Carr. 37p.**




230v/240v SMITHS SYNCHRONOUS GEARED MOTORS

Built-in gearbox. All brand new and boxed. 30 RPH CW; 2 RPH CW; 30 RPH CW; 2 RPH CW; 30 RPH CW. 50p each. Post 12p.



230 VOLT A.C. 50 c/s RELAYS

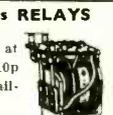3 sets of changeover contacts at 5 amp rating 40p each. Post 10p (100 lots £30) Quantities available.



MODEL TE-15 GRID DIP METER

Transistorised. Operates as Grid Dip, Oscillator, Absorption Wave Meter and Oscillating Detector. Frequency range 40Kc/s-280Mc/s in 6 coils. 500uA Meter. 9V. battery operation. Size 180 x 80 x 40mm. **£15.00. Post 20p.**




"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. All models—Input 230v. 50/60 c/s. Variable output 0-260v.


MODEL S-260 GENERAL PURPOSE BENCH MOUNTING

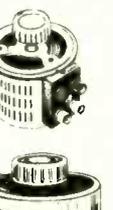1 Amp ... £7.00
 2.5 Amp ... £8.05
 5 Amp ... £11.75
 8 Amp ... £15.90
 10 Amp ... £22.50
 12 Amp ... £23.60
 20 Amp ... £48.00
 25 Amp ... £58.00
 40 Amp ... £82.50



MODEL S-260B

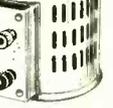Panel Mounting. 1 Amp ... £7.00
 2.5 Amp ... £8.05
Carriage and Packing Extra



AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded.
 80 W £2.35 P. & P. 18p
 150 W £3.00 P. & P. 18p
 300 W £4.00 P. & P. 23p
 500 W £5.80 P. & P. 33p
 1000 W £8.25 P. & P. 38p
 1500 W £11.25 P. & P. 43p
 2250 W £19.00 P. & P. 50p
 5000 W £40.00 P. & P. £1

MCA. 220 AUTOMATIC VOLTAGE STABILISER

Input 88-125 VAC or 175-250VAC. Output 120VAC or 240VAC. 200VA rating. **£11.97. Carr. 50p.**



PS.200 REGULATED P.S.U.

Solid state. Variable output 5-20 volt D.C. up to 2 amp. Independent meters to monitor voltage and current. Output 220/240 V. A.C. Size 7 1/2 x 5 1/2 x 6 1/2. **£19.95. Post 25p.**



PS.1000B REGULATED P.S.U.

Solid state. Output 6-9 or 12 V. D.C. up to 3 amps. Meter to monitor current. Input 220/240 V. A.C. Size 4 1/2 x 3 1/2 x 6 1/2. **£11.97. Post 25p.**



240° WIDE ANGLE 1mA METERS

MW1-6 60mm. square £3.97
 MW1-8 80mm. square £4.97
Post extra.



POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fitting. 1/2in. diameter. Bulk quantities available. 25 WATT. 10/25/50/100/250/500/1000 ohms. 95p. P. & P. 10p.
 50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. £1.35. P. & P. 10p.
 100 WATT. 1.5/10/25/50/100/250/500/1000 or 2500 ohms. £1.95. P. & P. 15p.





HIGH QUALITY CONSTRUCTION KITS
Appointed stockists at all branches
Complete with comprehensive, easy to follow instructions and covered by full guarantees
Post and packing 15p per kit

- AF20 Mono transistor amplifier. £4.80
- AF30 Mono transistor pre-amplifier. £2.61
- AF310 Mono amplifier (use two for stereo). £8.91
- AT5 Automatic light control. £2.58
- AT30 Photo cell unit. £5.70
- AT50 400W Triac light dimmer/speed control. £4.80
- AT55 1,300W Triac light dimmer/speed control. £5.70
- AT56 2,200W Triac light dimmer/speed control. £6.90
- AT60 Psychedelic light control, single channel. £7.80
- AT65 Psychedelic light control, 3 channel. £14.55
- HF1 Medium wave transistor radio. £3.33
- HF25 FM transistor receiver. £2.88
- HF310 FM tuner unit. £15.81
- HF325 Deluxe FM tuner unit. £24.12
- HF330 Stereo decoder for HF310/HF325. £9.96
- HF385 Aerial amplifier for AM/FM bands I, II, III. £1.77
- GP310 Stereo pre-amp for use with 2x AF310. £21.27
- GU330 Tremolo unit for guitars etc. £7.50
- NT10 Power supply 100 mA 9V stab. 12V unstab. £6.15
- NT300 Professional stabilized power supply 2x 30 Volt, 2.2 Amp. £12.51
- NT305 Transistor converter 12/15V AC/DC to 6V, 7.5V or 9V DC. £4.50
- NT310 Power supply 240V AC to 2x 18V DC at 2 Amps. £4.80
- NT315 Power supply 240V AC to 4.5-18V DC 500 mA. £9.57

TRIO TS515/PS515 TRANSCEIVER



High quality TS515 88B-CW amateur band receiver covering 80, 40, 20, 15 and 10 metre Transmitter/receiver frequency 3.5-29.7MHz. Output 1.5 watts. Power requirements 110-120-220-240V. A.C. Size: TS515 330 x 185 x 340mm. PS515 200 x 168 x 340mm.

OUR PRICE £210.00 Carr. Paid


TRIO JR310 SSB RECEIVER



Covers 3.5, 7, 14, 21, 28, 28.5 and 29.1MHz bands and WWV 14MHz. SSB, AM and CW. AF output more than 1 watt. Crystal controlled BFO for SSB. 8 meter. ANL etc. A.C. 110/120-220-240V. Size 330 x 178 x 310mm.

OUR PRICE £75.00 Carr. Paid

TRIO JR599 RECEIVER

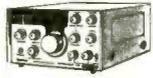

9 wavebands covering 1.8-29.7MHz, 144-146MHz and 10-60MHz WWV, SSB, CW, AM and FM. AF output more than 1 watt. 8 Meter. Squelch control. BFO. Variable IF and AF controls. 4-16 ohm output and phone jack. Power requirements 100-240V. A.C. 12-14V. D.C. Size 270 x 140 x 310mm.


OUR PRICE £155.00 Carr. Paid

TRIO TR2000 TRANSCEIVER

Fully transistorised portable VHF Transceiver. Will transmit and receive on 6 channels between 144-146 MHz. 1 watt transmitter. 12V D.C. Internal or external supply. Built in charger for nickel cells. Power/volume switch, squelch control, channel selector, mike socket, carbon/external speaker socket. Complete with microphone. 144-48, 144-72 and 145-32 crystals. Size 134 x 58 x 180mm.

OUR PRICE £210.00 Carr. Paid

BELTEK W5400 CAR TRANSCEIVER

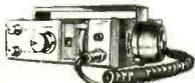

Solid state mobile transceiver for 12V D.C. neg. use. Transmits and Receives on any 12 of 26 channels between 144 and 146MHz. Power output 10w and 1w switchable. Controls: Volume on/off, squelch channel selector. Internal 3" speaker. Complete with dynamic mike, PTT switch, three sets of crystals for 144-48MHz, 144-60MHz, 145-00MHz, mounting bracket and instructions. Size approx. 170 x 50 x 220mm.

OUR PRICE £75.00 P. & P. 50p

SEW CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVT. DEPTS., EDUCATIONAL AUTHORITIES, etc.
Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

TYPE SW.100 100 x 80mm

100µA	£3.95
100-100µA	£3.90
300µA	£3.70
1mA	£3.60
20V. D.C.	£3.60
50V. D.C.	£3.80
300V. D.C.	£3.80
1 amp. D.C.	£3.60
5 amp. D.C.	£3.60
300V. A.C.	£3.70
VU Meter.	£4.30

TYPE SD.830 82.5mm x 110mm Fronts

10mA	£3.10
50mA	£3.10
100mA	£3.10
300µA	£3.10
1 amp.	£3.10
5 amp.	£3.10
10 amp.	£3.10
5V. D.C.	£3.10
16V. D.C.	£3.10
20V. D.C.	£3.10
30V. D.C.	£3.10
300V. D.C.	£3.10
1mA	£3.15
500µA	£3.15
1mA	£3.10
5mA	£3.10

TYPE SD.640 83.5mm x 85mm Fronts

50µA	£3.05
50-50µA	£3.05
100µA	£3.00
100-100µA	£3.00
200µA	£3.00
500µA	£2.95
1mA	£2.90
5mA	£2.90
10mA	£2.90
50mA	£2.90
100mA	£2.90


500µA	£2.90
1 amp.	£2.90
5 amp.	£2.90
10 amp.	£2.90
5V. D.C.	£2.90
20V. D.C.	£2.90
50V. D.C.	£2.90
300V. D.C.	£2.90
15V. A.C.	£3.00
300V. A.C.	£3.00
VU Meter.	£3.15

TYPE SD.460 46mm x 59.5mm Fronts

50µA	£2.80
50-50µA	£2.80
100µA	£2.75
100-100µA	£2.75
200µA	£2.70
500µA	£2.55
1mA	£2.60
5mA	£2.60
10mA	£2.60
50mA	£2.60
100mA	£2.60

500µA	£2.60
1 amp.	£2.60
5 amp.	£2.60
10 amp.	£2.60
5V. D.C.	£2.60
10V. D.C.	£2.60
20V. D.C.	£2.60
50V. D.C.	£2.60
300V. D.C.	£2.60
15V. A.C.	£2.70
300V. A.C.	£2.70
VU Meter.	£2.90

"SEW" EDGWISE METERS TYPE P.E.70

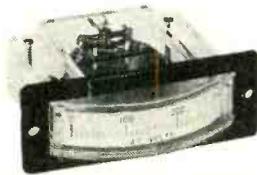

3 17/32in. x 1 15/32in. x 2 1/2 in. deep.

50µA	£3.75
50-50µA	£3.60
100µA	£3.60
100-100µA	£3.50
200µA	£3.40

500µA	£3.20
1mA	£3.25
5 amp. A.C.	£3.25
VU Meter	£3.85

*** MOVING IRON— ALL OTHERS MOVING COIL**

Please add postage

TYPE MR.85P 4 1/4in. x 4 1/4in. fronts.

10mA	£3.90
50mA	£3.90
100mA	£3.90
500mA	£3.90
1 amp.	£3.90
15 amp.	£3.90
30 amp.	£3.95
20V. D.C.	£3.90
50V. D.C.	£3.90
150V. D.C.	£3.90
300V. D.C.	£3.90
15V. A.C.	£3.90
300V. A.C.	£3.90
100-100µA	£4.05
5 Meter 1mA	£3.90
VU Meter	£4.55
1 amp. A.C.*	£3.90
5 amp. A.C.*	£3.90
10 amp. A.C.*	£3.90
20 amp. A.C.*	£3.90
30 amp. A.C.*	£3.90

TYPE MR.52P 2 1/2in. square fronts.

50µA	£3.50
50-50µA	£3.05
100µA	£3.00
100-100µA	£2.95
500µA	£2.65
1mA	£2.50
5mA	£2.50
10mA	£2.50
50mA	£2.50
100mA	£2.50
300mA	£2.50
1 amp.	£2.50
5 amp.	£2.50

10V. D.C.	£2.50
20V. D.C.	£2.50
50V. D.C.	£2.50
300V. D.C.	£2.50
15V. A.C.	£2.60
300V. A.C.	£2.60
8 Meter 1mA	£2.60
VU Meter	£3.60
1 amp. A.C.*	£2.50
5 amp. A.C.*	£2.50
10 amp. A.C.*	£2.50
20 amp. A.C.*	£2.50
30 amp. A.C.*	£2.50

TYPE MR.65P 3 1/4in. x 3 1/4in. fronts

50µA	£3.70
50-50µA	£3.15
100µA	£3.15
100-100µA	£3.10
200µA	£3.05
300µA	£2.75
500-500µA	£2.60
1mA	£2.60
5mA	£2.60
10mA	£2.60
50mA	£2.60
100mA	£2.60
500µA	£2.60
1 amp.	£2.60
5 amp.	£2.60
10 amp.	£2.60
15 amp.	£2.60
20 amp.	£2.60
30 amp.	£2.60
50 amp.	£2.60
5V. D.C.	£2.60

10V. D.C.	£2.60
20V. D.C.	£2.60
50V. D.C.	£2.60
160V. D.C.	£2.60
300V. D.C.	£2.60
15V. A.C.	£2.80
50V. A.C.	£2.80
150V. A.C.	£2.80
300V. A.C.	£2.80
500V. A.C.	£2.80
8 Meter 1mA	£2.85
VU Meter	£3.70
50mA A.C.*	£2.60
100mA A.C.*	£2.60
200mA A.C.*	£2.60
500mA A.C.*	£2.60
1 amp. A.C.*	£2.60
5 amp. A.C.*	£2.60
10 amp. A.C.*	£2.60
20 amp. A.C.*	£2.60
30 amp. A.C.*	£2.60

"SEW" EDUCATIONAL METERS

TYPE ED.107

Size overall 100mm x 90mm x 108mm.

A new range of high quality moving coil instruments ideal for school experiments and other bench applications. The meter movement is easily accessible to demonstrate internal working.

Available in the following ranges—

50µA	£2.90
100µA	£2.40
50-50µA	£2.40
1mA	£5.95
1-0-1mA	£5.95
1A D.C.	£5.95
5A D.C.	£5.95

10V. D.C.	£5.95
20V. D.C.	£5.95
50V. D.C.	£5.95
300V. D.C.	£5.95
Dual range	
500mA A.D.C.	£7.00
5V/50V. D.C.	£7.00

TYPE MR.38P 1 21/32in. square fronts.

130mA	£2.25
200mA	£2.25
300mA	£2.25
500mA	£2.25
750mA	£2.25
1 amp.	£2.25
2 amp.	£2.25
5 amp.	£2.25
10 amp.	£2.25
3V. D.C.	£2.25
15V. D.C.	£2.25
20V. D.C.	£2.25
50V. D.C.	£2.25
100V. D.C.	£2.25
150V. D.C.	£2.25
300V. D.C.	£2.25
500V. D.C.	£2.25
1mA	£2.25
1-4-1mA	£2.25
1mA	£2.25
5mA	£2.25
10mA	£2.25
20mA	£2.25
50mA	£2.25
100mA	£2.25

5 amp.	£2.40
10V. D.C.	£2.40
20V. D.C.	£2.40
50V. D.C.	£2.40
300V. D.C.	£2.40
15V. D.C.	£2.40
300V. D.C.	£2.40
8 Meter 1mA	£2.50
VU Meter	£2.70
1 amp. A.C.*	£2.40
5 amp. A.C.*	£2.40
10 amp. A.C.*	£2.40
20 amp. A.C.*	£2.40
30 amp. A.C.*	£2.40

TYPE MR.45P 2in. square fronts.

50µA	£2.70
50-50µA	£2.65
100µA	£2.60
100-100µA	£2.50
200µA	£2.50
300µA	£2.45
500-500µA	£2.40
1mA	£2.40
5mA	£2.40
10mA	£2.40
50mA	£2.40
100mA	£2.40
1 amp.	£2.40

5 amp.	£2.40
10V. D.C.	£2.40
20V. D.C.	£2.40
50V. D.C.	£2.40
300V. D.C.	£2.40
15V. D.C.	£2.40
300V. D.C.	£2.40
8 Meter 1mA	£2.50
VU Meter	£2.70
1 amp. A.C.*	£2.40
5 amp. A.C.*	£2.40
10 amp. A.C.*	£2.40
20 amp. A.C.*	£2.40
30 amp. A.C.*	£2.40

"SEW" BAKELITE PANEL METERS

TYPE MR.65 3 1/4in. square fronts.

1 amp.	£2.60
5 amp.	£2.60
15 amp.	£2.60
30 amp.	£2.60
50 amp.	£2.60
5V. D.C.	£2.60
10V. D.C.	£2.60
20V. D.C.	£2.60
50V. D.C.	£2.60
300V. D.C.	£2.60
30V. A.C.*	£2.65
50V. A.C.*	£2.65
150V. A.C.*	£2.65
300V. A.C.*	£2.65
500mA A.C.*	£2.60
1 amp. A.C.*	£2.60
5 amp. A.C.*	£2.60
10 amp. A.C.*	£2.60
20 amp. A.C.*	£2.60
30 amp. A.C.*	£2.60
50 amp. A.C.*	£2.60
50mA	£2.60
10mA	£2.60
500µA	£2.60
100µA	£2.60
100-100µA	£2.70
500-500µA	£2.60
1mA	£2.60
1-0-1mA	£2.60
5mA	£2.60
10mA	£2.60
50mA	£2.60
100mA	£2.60
500µA	£2.60

100-100µA	£3.30
500µA	£3.05
1mA	£3.00
20V. D.C.	£3.00
50V. D.C.	£3.00
300V. D.C.	£3.00
5 amp. D.C.	£3.00
300V. A.C.	£3.00
VU Meter	£3.70

TYPE S.80 80mm Square Fronts

50µA	£3.50
50-50µA	£3.40
100µA	£3.40

General coverage 150-400 kc/s. 550 kc/s-30 mc/s. FET front end, 2 mech. filters, product detector, variable B.F.O., noise limiter, 8 Meter Bandspread. RF Gain. 10in. x 9 1/2in. x 8 1/2in. 18 lb. 220/240 v. A.C. or 12 v. D.C. Brand new with instructions.

LAFAYETTE HA-600 RECEIVER

4 Bands covering 550 kc/s-30 mc/s. B.F.O. Built-in Speaker 220/240 v. A.C. Brand new with instructions.

OUR PRICE £15.75 Carr. 37p

UNR 30 RECEIVER

4 Bands covering 550 kc/s-30 mc/s. FET, 8 Meter. Variable BFO for SSB. Built-in Speaker, Bandspread, Sensitivity Control. 220/240 v. A.C. or 12 v. D.C. 12 1/2in. x 4 1/2in. x 7 1/2in. Brand new with instructions.

OUR PRICE £25.00 Carr. 37p

UNR-1A RECEIVER

4 Bands covering 550 kc/s-30 mc/s. FET, 8 Meter. Variable BFO for SSB. Built-in Speaker, Bandspread, Sensitivity Control. 220/240 v. A.C. or 12 v. D.C. 12 1/2in. x 4 1/2in. x 7 1/2in. Brand new with instructions.

OUR PRICE £25.00 Carr. 37p

HAND HELD 2 WAY TALKIES

Battery operation. Volume and Squelch controls. Call Button and Press to Talk Button. Telescopic Aerial. Complete with carrying cases.

SKYFON 100mW. Pair £24.95 Post 50p
P302 2 Channel 300mW. Pair £52.50 Post 50p
P1003 3 Channel 1 Watt. Pair £71.25 Post 50p

Licence required for operation in U.K.

3 STATION INTERCOM

Master and two sub stations. Can be used on desk or wall mounted. Complete with cable and batteries.

OUR PRICE £5.25 P. & P. 50p

TRIO 9R59DS RECEIVER

G.W. SMITH & CO (RADIO) LTD

BVD.5 VERNIER TUNING DIAL

Approx. 7:1 ratio planetary drive vernier dial. Log scale 0-180 degrees. Blank scales 1 to 5. Scale width 4". Dial size 5" x 3". Overall size 7 1/2" x 4 1/2" x 1 1/2" deep including knob and coupling. 1" dia. shaft.

OUR PRICE £1-62 P. & P. 15p

RUH.6 REFLEX HORN SPEAKER

Built in driver unit. Impedance 16 ohm. Power rating 10 watt. Response 380-7000 Hz. Approx. size 6 1/2" x 6". Weatherproof and shock proof.

OUR PRICE £4-97 P. & P. 30p

EMI LOUDSPEAKERS

Model 350. 13in. x 8in. with single tweeter crossover. 20-20,000 Hz. 15 watt RMS. Available 8 or 15 ohms. £7-25 each. P. & P. 37p.
Model 450. 13in. x 8in. with twin tweeters/crossover. 35-13,000 Hz. 8 watts RMS. Available 8 or 15 ohms. £3-82 each. P. & P. 25p.

HA-10 STEREO HEADPHONE AMPLIFIER

All silicon transistor amplifier operates from magnetic, iron magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9 v. battery. Inputs: 2mV-100mV. Output: 60mV per channel.

OUR PRICE £6-97 P. & P. 20p

MP7 MIXER PREAMPLIFIER

5 microphone inputs each with individual gain controls enabling mixing facilities. Battery operated. 9 1/2" x 5" x 3". Inputs: Mic: 3 x 2mV 30K; 2 x 2mV 600 ohm. Phono mag. 4 mV 50K. Phono ceramic 100mV 1 meg. Output 250mV 100K.

OUR PRICE £8-97 P. & P. 20p

1021 STEREO LISTENING STATION

For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets. din. x 4in. x 2 1/2in.

OUR PRICE £2-25 P. & P. 20p

EA41 REVERBERATION AMPLIFIER

Self contained, transistorised, battery operated. Simply plug in microphone, guitar, etc., and output into your amplifier. Volume control, depth of reverberation control. Beautiful walnut cabinet. 7 1/2 x 3 x 4 1/2in.

OUR PRICE £7-50 P. & P. 15p

ALL PRICES ARE SUBJECT TO 10% V.A.T.

SH628 STEREO HEADPHONES

Outstanding value. Soft pads, adjustable headband. 8-16 ohms. 20-20,000 Hz. Complete with lead and stereo plug.

OUR PRICE £1-87 P. & P. 30p

LIGER LH02S STEREO HEADPHONES

Lightweight headphones with padded earpieces. 4-16 ohms. 20-20,000 Hz. Complete with 6ft cord and plug.

OUR PRICE £1-95 P. & P. 30p

TE1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET

Sensitive magnetic headset with soft earpads. Impedance 2,600 ohms (d.c. 600 ohms). Frequency response 200-1000 Hz.

OUR PRICE £2-25 P. & P. 30p

SDH8V MONO/STEREO HEADPHONES

Two way stereo/mono with volume controls. Padded headband. 4-16 ohms. 20-18,000 Hz. Complete with lead and stereo plug.

OUR PRICE £4-97 P. & P. 30p

BH001 HEADSET AND BOOM MICROPHONE

Moving coil. Headphone imp. 16 ohms. Mike imp. 200 ohms. Ideal for language teaching, communications etc. Complete with leads and plugs.

OUR PRICE £4-95 P. & P. 30p

DH.08S Stereo Headphones

De luxe model with unique 2 way mechanical units and volume controls. 8 ohms. 20-20,000 Hz. Complete with coil lead and stereo jack plug.

OUR PRICE £7-97 P. & P. 30p

4-CHANNEL STEREO HEADPHONES

TTC G3600—Soft vinyl covered head cushion and earphones. Each earpiece incorporates two 2" speaker units. Padded 2 1/2 channel changeover switch. Impedance 4-16 ohm. Frequency response 20-20,000 Hz. Complete with 15ft. coiled lead fitted two stereo plugs.

OUR PRICE £9-95 P. & P. 30p

DH-02S STEREO HEADPHONES

Wonderful value and excellent performance combined. Adjustable headband. 8 ohm impedance. 20-12,000 cps. Complete with lead and stereo jack plug. ONLY £2.25. Post 30p.

AUDIOTRONIC

Audiotronic Products are manufactured exclusively for the Audiotronic Group of Companies and as a member of the group we are pleased to offer you this fabulous range of high quality equipment. Made to our own specifications each item provides outstanding performance and reliability at a value for money price!

TAPE CASSETTE

Top Hi-Fi quality in library cases

Type	5	10	25
C90	£1.20	£2.53	£5.99
C90	£1.65	£3.82	£8.59
C120	£2.29	£4.48	£10.63

CHROME DIOXIDE
CR40 £3-41 £6-72 £16-68
CR90 £4-93 £9-10 £22-88
TAPE HEAD CLEANER 30p each

P. & P. 35p for 5; 10 and over post free.

8-TRACK BLANK TAPES

Type	1	5	10
4M	75p	£3-50	£8-50
8M	99p	£4-70	£8-90

P. & P. 35p; 5 and over post free.

ACR.14 BATTERY/MAINS CASSETTE RECORDER

Portable twin track mono recorder with automatic reversing level control. Built-in speaker. Earpiece socket. Input for radio or record player. Fast forward and rewind. Output 500mW. AC 220-240v. or 6v. DC operation. Complete with remote control microphone, mains lead, earpiece and batteries.

OUR PRICE £10-50 P. & P. 50p

SPORTSMAN AM/FM PORTABLE RADIO MODEL AR.1000

5 wavebands covering AM 535-1065KHz. FM 88-107MHz. AIR 108-136MHz. PP 147-174MHz. WB 162.5MHz. Large horizontal slide dial with logging scale. Slider volume and squelch controls. 7 section telescopic aerial for FM and built-in ferrite bar for AM. AFC. 3in. speaker. Earpiece socket. Green leatherette covered cabinet with metal side panels. Size 152 x 79 x 216mm. Battery mains operation.

OUR PRICE £11-50 P. & P. 35p

MULTIBAND RADIO AMB 500

5 wavebands covering MW 535-1605KHz and FM 88-170MHz. All transistor. Battery or mains operation. Built-in aerial and 8 section telescopic aerial. Complete with batteries, shoulder strap and earpiece.

OUR PRICE £6-95 P. & P. 35p

PORTABLE RADIO AMR-9000 GLOBAL AM/FM

10 wavebands covering: AM: 535-1605 kHz. LW: 130-380 kHz. MR 1.3-4 MHz. SW1: 4.0-8 MHz. SW2: 8.0-1.6 MHz. SW3: 16-24 MHz. P8B1: 30-50 MHz. PSB2: 148-174 MHz. FM 88-108 MHz. AIR: 108-136 MHz. Features time zone map and timing dial. Large clear scale. Telescopic aerial and built in aerial. AFC on FM. 6in. x 4in. speaker and personal earpiece. Battery/mains operation. Size: 345 x 135 x 305mm.

OUR PRICE £36-00 P. & P. 50p

STEREO CASSETTE DECK ACD.660



A beautifully styled 4-track stereo deck with an outstanding specification offered at a remarkably low price. Incorporates a host of features including switchable noise filter, normal chrome tape selector, twin VU meters, slider record playback level controls, front panel headphone socket, recording indicator lamp, phono-Din line input sockets, 3.5 mm. mike input sockets etc. Frequency response 100-8KHz (100-12KHz. Cont'd) S/N -45dB. Crosstalk -45dB. Separation -55dB. Noise limiter -6dB at 10KHz. Complete with phono connecting leads.

OUR PRICE £39-50 P. & P. 50p

DIGITAL CLOCK RADIO ADC.1



Covers AM 540-1600KHz. FM 88-108 MHz with AFC. 24 hour lead time digital clock with one minute division time change. Illuminated dial. 24 hour alarm setting. Wake up to the sound of music or loud buzzer. Unique sleep switch will automatically turn off radio when you have gone to sleep. Slider volume control. Internal speaker plus socket for earpiece or pillow speaker. AC 240v. Size 254 x 92 x 178mm. Complete with earpiece, FM aerial and operating instructions.

OUR PRICE £12-50 P. & P. 50p

IN-CAR EQUIPMENT



ACP.8 8-TRACK PLAYER. Attractive black and silver finish. 12v. neg. earth. Slider controls for Volume, Tone and Balance. Channel selector button with red pilot lamp. Complete with speakers, mounting brackets and instructions.

OUR PRICE £12-50 P. & P. 40p



ACR 3500 CAR RADIO. Manual tuning of Medium and Long waves. 12v. pos. or neg. earth. Complete with speaker, mounting brackets and instructions.

OUR PRICE £6-50 P. & P. 50p

STEREO HEADPHONES

LSH.20 Individual volume controls. Stereo mono switch. 8 ohms. 40-19,000 Hz. £3-50. P. & P. 30p.

LSH.40 Two way speaker system. Individual volume controls. 8 ohms. 20-20,000 Hz. £8-95. P. & P. 30p.

LSH.50 Professional Quality Electrostatic. Complete with self powered energiser and control unit with headphone/speaker selector. 4-32 ohms. 20-24,000 Hz. £15.95. P. & P. 30p.



DOLBY 'B' NOISE REDUCTION UNITS

Reduce tape hiss by 3dB at 4000Hz. 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Size 163" x 8" x 3 1/2". AC 200-250v.

PROCESS TWO

For use with cassette and tape recorders. Freq. res. 30Hz-20KHz±2dB. Off tap monitoring. Switchable multiplex filter. Two Dolby calibration meters. S/N better than 70dB. Supplied with test cassette or tape as required.

OUR PRICE £34-50 P. & P. 50p

PROCESS FOUR

For use with semi professional tape recorders. Freq. res. 30Hz-20KHz±2dB. S/N better than 70dB. Full source tape monitoring. Record/Replay metering. Switchable multiplex filter. Supplied with test tape.

OUR PRICE £50-00 P. & P. 50p

AHP-8A 8-TRACK STEREO TAPE PLAYER



Incorporates built-in amplifiers giving 2 1/2-2 1/2 watts rms output. Push button track selector. Illuminated track indicators. Slide controls for volume, balance and tone. Attractive cabinet with black and silver trim. Output Impedance 8 ohms. AC 220-240v.

OUR PRICE £17-25 P. & P. 50p

AHP-8D 8-TRACK STEREO TAPE DECK



Can be used with most hi-fi amplifiers. Push button track selector and illustrated track indicators. Attractive cabinet with black and silver trim. Output level 750mV. AC 220-240v.

OUR PRICE £11-95 P. & P. 50p

AUDIOTRONIC LA.1700 SYSTEM



17-17 watt amplifier, Garrard AP76, plinth and cover, G800 cartridge, pair of Wharfedale Linton 2 speakers and all leads.

OUR PRICE £92-50 Carr. & Ins. £1-50

Matching LT1700 AM/FM Stereo Tuner £37-50.



SAVE UP TO 33 1/3% OR MORE! GWS

RECORD DECKS



Carriage & Packing 50p

B.S.R. McDONALD

C14 Mini	£3 95
C19 Mono	£5 50
C137	£7 00
510/TPD1	£13 95
610	£10 55
610/TPD1	£15 45
710	£21 15
810	£23 30
710/810 Plinth and Cover	£9 15
MP60	£8 25
MP60/G800	£10 90
MP60/TPD1	£13 20
MP60/TPD2	£11 25
HT70	£11 60
HT70/G800	£14 25
HT70/TPD1	£16 55

CONNISSEUR

BD1 Kit	£9 10
BD1 Chassis	£11 35
BD2/SAU2/Chassis	£22 70
BD2/SAU2/Plinth/Cover	£28 20

GARRARD

1025T Stereo	£4 95
2025 TC Stereo	£6 35
SP25 III	£9 25
SP25 III/Acos GP104 Ceramic	£8 50
SP25 III/G800	£10 95
SP25 M75-6	£13 90
AP76	£18 00
SL65B	£11 15
SL72B	£17 75
SL95B	£21 15
401	£24 35
ZERO 100	£24 10
ZERO 100B	£31 40

GOLDRING

G99	£22 50
G101P/C	£22 50
GL69/C	£15 75
GL72	£25 45
GL72/P	£23 75
GL75	£28 20
GL75P	£41 85
GL78P/C	£26 25
GL82P/C	£27 00

THORENS

TD125/II	£59 40
TD125A/II	£92 05
TD180C	£50 80
TD165	£43 80

RECORD DECK PACKAGES



Carriage and Packing 75p
Complete units with Stereo cartridge ready wired in plinth and cover.

GARRARD

2025 TC/9TA/ACD	£10 65
SP25 III/G800	£15 90
SP25 III/M44-7	£17 40
SP25 III/M44-7	£16 95
SP25 III/M55B	£17 85
SP25 III Module/M75-6	£19 45
AP76/G800	£25 50
AP76/G800F	£28 10
AP76/M44E	£27 05
AP76/M44-7	£26 90
AP76/M55E	£27 50
AP76/M75ED	£31 70
AP76/M75EJ	£30 30
AP76 Mobile M75-6	£29 10
AP96 Module M75-6	£33 20
ZERO 100S Module/M93E	£44 15

B.S.R. McDONALD

210/SC7M	£7 40
MP60/G800	£15 00
MP60/TPD1/G800	£15 90
MP60/M44-7	£16 90
HT70/TPD1/G800	£19 20

GOLDRING

GL72/G800	£31 50
GL75/G800	£36 65
GL75/G800E	£39 15

GOODMANS

TD100 G800 Teak	£46 95
TD100/G800 White	£48 60

LEAK

Delta/M75-6	£47 20
Truspee-d	£35 95

PHILIPS

GA105/GP200	£13 80
GA105/GP200 Teak	£19 50
GA308/GP400	£32 75
GA308 (Less cartridge)	£23 95
GA212/GP400	£48 05

PIONEER

PL12D (Less cartridge)	£31 75
PL15C (Less cartridge)	£44 95
PL14D (Less cartridge)	£104 75
PL50 (Less cartridge)	£98 90
PL61 (Less cartridge)	£110 30
PLA35 (Less cartridge)	£61 55

THORENS

TD150C/Ortofon M15E Super	£70 35
TD125 AB/II M15E Super	£112 05
T165 Ortofon M15E Super	£82 55

WHARFEDALE

Lint on/M44-7 Teak	£23 55
Lint on/M44-7 White	£24 70

SINCLAIR PROJECT 60 PACKAGE DEALS



2 x Z30 Stereo 60/P/Z5 £15 95. P. & P. 37p.

2 x Z30/Stereo 60/P/Z6 £18 00. P. & P. 37p.

2 x Z50/Stereo 60/P/Z8 £20 25. P. & P. 37p.

Transformer for PZ8 £3 65

Active Filter Unit £4 45

Pair of Q16 Speakers £10 70 P. & P. 50p.

Sinclair Project 605 £20 97. P. & P. 37p.

All other Sinclair Products in stock.

2000 Amplifier £22 95. P. & P. 50p.

3000 Amplifier £28 95. P. & P. 50p.

2000/3000 Tuner £28 30. P. & P. 50p.

Q830 Speaker £14 99. P. & P. 50p.

PHILIPS IC361 AM/FM MAINS/PORTABLE RADIO WITH AFC



Covers LW, MW, FM, SW1, SW2 and 49 metre band. Fine tuning of SW and Pre set tuning of three FM stations. Bass, treble and volume/on/off controls. Press button wave change. Tuning/battery indicator. AC 110-140v. or 6 x 1.5v. batteries. Size 14 1/2 in. x 4 in. x 3 1/2 in. approx. With main lead and instructions. Rec. List Price £69 18.

OUR PRICE £39 95 P. & P. 50p.



HANIMEC HRC 3061 CASSETTE RADIO

Record/Playback facilities plus slide rule tuning of AM 535-1620 KHz and FM 88-108 MHz. Slider volume controls. Built in condenser microphone plus separate hand/teak microphone. Telescopic aerial. Complete with earpiece, batteries and instructions. (Tape not supplied). (Rec. List price £55 50).

OUR PRICE £22 75 P. & P. 50p.

MINUTEMAN MM3M

As above with addition of memory key, percent key and a fixed or floating decimal. Complete with rechargeable batteries, AC adaptor, instructions and case.

OUR PRICE £34 95 P. & P. 25p.

BINATONE DS100 DIGITAL CLOCK

240v mains operation. Ivory case with large clear numbers for hours, minutes and seconds. Approx. size 14 1/2 x 3 1/2 x 3 1/2.

OUR PRICE £4 50 P. & P. 30p.

SUPER AKAI CASSETTE BARGAINS!



CS35 STEREO CASSETTE RECORDER

High quality cassette recorder with hysteresis synchronous outer-rotor motor. Has pause control with lock and selector for conventional or Chromium Dioxide tape. 4 track record/playback. Volume and tone controls. Frequency response 40-16kHz (using CrO2 tape), distortion better than 2%, wow and flutter better than 0.2% RMS. Complete with pair of matching Akai CSN8 speakers.

Rec. Price £96 10.

OUR PRICE £56 50 P. & P. 50p.

ADM MICROPHONES

Normally £11 80 pair.

OUR PRICE £7 50

Pair. P. & P. 25p.

AKAI CS35D STEREO CASSETTE DECK

4 track record/playback deck. Accepts chrome/regular tape cassettes.

Rec. Price £68 30.

OUR PRICE £44 45 P. & P. 50p.

NEW! SINCLAIR CAMBRIDGE CALCULATOR

To build yourself. Complete kit of parts with step by step instructions to build a full specification pocket sized calculator. (Rec. Price £27 23).

OUR PRICE £24 95 P. & P. 50p.

Also available ready built (Rec. Price £39 95).

OUR PRICE £27 20 P. & P. 25p.

FM TUNER CHASSIS

6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6in. x 4in. x 2 1/2in. 11 stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9 volt battery. Coverage 88-108 Mc/s. Ready built ready for use. Fantastic value for money.

OUR PRICE £5 95 P. & P. 20p.

Stereo Multiplex Adaptor £4 97.

A1018 FM TUNER

Specification as above chassis but complete in cabinet with on/off switch. Size 7 1/2 x 3 1/2 x 6".

OUR PRICE £9 65 P. & P. 30p.

Stereo Multiplex Adaptor £4 97.

MINUTEMAN MM3 POCKET CALCULATOR

Size only 4 1/2 x 3 x 1 1/2. 8 digit display with overflow and error indicators. Floating decimal. Adds, subtracts, multiplies and divides. Chain and mixed calculations. Constant factor for series multiplication or division. Complete with batteries, instructions and case.

OUR PRICE £27 50 P. & P. 25p.

FANTASTIC OFFER! PORTABLE CASSETTE RECORDER CT5050

Instant recording and playing. Piano key controls. Automatic level control. Built in speaker. Complete with remote control microphone, carrying case and shoulder strap.

OUR PRICE £8 50 P. & P. 50p.

DIGITAL CLOCK MECHANISM DT.55B

Features 24 hour alarm setting with built in buzzer. On/off and auto alarm sleep switch. Illuminated rotary dial with hours, minutes and seconds. Automatically turns off TV, radio, light etc. and with auto setting will switch on again when required. AC 240v. operation. Switch rating 250v. 3A.

OUR PRICE £5 95 P. & P. 30p.

BSR8 TRACK PLAYER CHASSIS

Famous BSR 8 track chassis as used in Model T188 complete with silver and black escutcheon ready to fit into cabinet. Output 125mV. AC 240v. Overall size approx. 185 x 215 x 80mm.

OUR PRICE £8 95 P. & P. 50p.

SPECIAL OFFER! STEREO SPEAKERS

Matched pair of bookshelf speakers. De luxe teak veneered finish. Size 14 1/2 in. x 9 in. x 7 1/2 in. 8 ohms. 8 watts RMS. 16 watts peak. Complete with DIN lead.

OUR PRICE £12 95 Carr. 50p.

ALBANY HOUSE AM 108 SYSTEM



8 + 8 watt amplifier MP60, plinth and cover. G800 cartridge, pair of Medway T138 speakers.

OUR PRICE £50 95 Carr. £1 25

TRIO KA 2000A SYSTEM



16+16 watt amplifier. SP25 or MP60 plinth and cover, G800 cartridge, pair of Denton 2 speakers and all leads.

OUR PRICE £70 95 Carr. £1 25

FERGUSON EXPORT MODELS



3408 Stereo Tuner Amplifier

Covers FM 88-108 MHz. Five push button tuning scales. 8-8 watts rms. Inputs for stereo ceramic cartridge and tape, etc. Separate bass, treble, balance and volume controls.

OUR PRICE £31 50 Carr. £50p.



3416 Stereo Tape Deck

4 track. 7 1/2, 3 1/2, 1 1/2 i.p.s. Stereo/mono record/play. 7 reels. Inputs for dynamic mikes, radio, gram. Complete with cover.

OUR PRICE £41 95 Carr. £75p.

LONDON'S LARGEST STOCKS INCLUDING PRODUCTS BY-

- ARMSTRONG
 - CAMBRIDGE
 - KEF LUX NIKKO
 - SANSUI SANYO
 - SONY TEAC
 - TRANSISTORS
 - TRIO-UHER
 - YAMAHA
- Prices on request or send S.A.E. for full Discount List

ALL EQUIPMENT IS FULLY GUARANTEED AND COVERED BY 12 MONTHS FREE SERVICE!

G.W.SMITH & CO (RADIO) LTD

- PERSONAL CALLERS WELCOME AT ANY OF OUR RETAIL BRANCHES
- CENTRAL LONDON**
- | | | | |
|--------------------------------|------------------|--------------------------------|--------------------|
| 257/8, Tottenham Court Rd, W.4 | Tel: 01-580 0670 | 311, Edgware Road, W.2 | Tel: 01-282 0387 |
| 10, Tottenham Court Rd, W.1 | Tel: 01-637 2232 | 382, Edgware Road, W.2 | Tel: 01-723 4194 |
| 27, Tottenham Court Rd, W.1 | Tel: 01-636 3715 | 152/3, Fleet Street, E.C.4 | Tel: 01-353 2833 |
| 87, Tottenham Court Rd, W.1 | Tel: 01-580 3739 | 378, Harrow Road, W.9 | Tel: 01-286 9530 |
| 21, Old Compton Street, W.1 | Tel: 01-437 9369 | ESSEX | |
| 3, Lisle Street, W.C.2 | Tel: 01-437 8204 | 86, South Street, Romford | Tel: Romford 20218 |
| 34, Lisle Street, W.C.2 | Tel: 01-437 9155 | SURREY | |
| 118, Edgware Road, W.2 | Tel: 01-723 9789 | 1046, Whitgift Centre, Croydon | Tel: 01-681 3027 |
| 193, Edgware Road, W.2 | Tel: 01-723 6211 | 27, Eden Street, Kingston | Tel: 01-546 7845 |
| | | 32, Hill Street, Richmond | Tel: 01-948 1441 |

ALL BRANCHES OPEN 9 a.m. - 6 p.m. MONDAY TO SATURDAY

HEAD OFFICE AND MAIL ORDER DEPARTMENT

UNIT 4, THE HYDE INDUSTRIAL ESTATE, THE HYDE, LONDON NW9 6JJ

TELEPHONE 01-205 3735

PRICES SUBJECT TO 10% VAT

Order with confidence by Post-but remember to add 10% VAT to total value of order including carriage and packing and send cash with order. PLEASE PRINT NAME & ADDRESS CLEARLY IN CAPITALS.

BARCLAYCARD

TELEPHONED ORDERS ACCEPTED FROM ACCESS and BARCLAYCARD HOLDERS

CREDIT TERMS FOR PERSONAL CALLERS (on sales of £50 and over).

All prices correct at 28.8.73 but subject to change without notice. E. & O.E.

TEKTRONIX STORAGE SCOPE type 564 with Time base and Y amplifier plug-ins £400.

TEKTRONIX 545A Oscilloscope with L plug-in £250; with CA plug-in £280.

TEKTRONIX 536 oscilloscope with T & CA plug-ins £325.

TEKTRONIX RM17 OSCILLOSCOPE £130.

TEKTRONIX TIME MARKERS type 181 £35.

ROHDE & SCHWARZ SYNTHESIZER Model BN 444462. 30 HZ to 30 MHz. Size 30 x 23 x 17in. MUST GO. £175.

ROHDE & SCHWARZ VIDEOSCOPE BN 424101/2 £750.

ROHDE & SCHWARZ Analyser BN 48302 £175.

AMERICAN SWEEP GENERATOR type 452. Covers from 5 to 100 MHz. Has built in display and 101 DB Push Button RF Attenuator in one DB steps, plus Calibrated Marker Generator covering 5 to 100 MHz continuous. American Government Contract, so quality is high. Supplied for 240V 50 HZ operation with plugs and leads. Size 13 1/2 x 9 1/2 x 19in. Price £70 each. Carriage £1-50.

AMERICAN SWEEP GENERATOR type TRM 3 15 to 400 MHz. £300.

AMERICAN POWER UNITS STANDARD 240V 50 HZ Input 28V 40 AMP OUTPUT. Size 22 x 16 x 9in. Supplied in original transit case £25.

AMERICAN AM GENERATOR type 497. 4 to 400 MHz. Supplied with leads, etc., for 240V 50 HZ operation £35.

AMERICAN RADIO INTERFERENCE AND FIELD INTENSITY METER/RECEIVER type NM22A (0-15 KHZ to 30 MHz) and NM30A (20 MHz to 400 MHz) £120 each or £180 10 pair.

POLARAD GENERATORS MODEL MSG 2, 2150-4600 MHz and Model MSG 34, 4200-11,000 MHz. The pair £130 or £75 each.

SPECIAL 40 MHZ SCOPE SOLARTRON CD1212 ONLY £50. Has to be a snag. There is—no plug-in Y amps available. TB-100 nanosecs per cm. to 5 secs. per cm. in 24 calibrated ranges. 20 nanosecs per cm. with times 5 expansion. 5" flat faced tube. Trace locator. 0-2 microsec. signal delay. Built in calibrator. 1 KHZ square wave. 200 micro volts to 100 volts in 18 calibrated ranges. Tube sensitivity 3 V/CM MAIN FRAM Y AMP boosts this to better than 200mV per cm. at 40 MHz. 240V. 50 HZ input. Complete with full manual including plug-in circuits. Come and see one working or Carriage £1-50!

***STILL at £42-50**
Solartron CD 711S.2 Double Beam Oscilloscope DC—9 mc/s; 3 mv/cm; trigger delay; crystal calibrator; 4" flat faced tube. In good working condition. Carr. £1-50.

SOLARTRON CD 523 Single Beam Oscilloscope 3db at 10 MHz; 1mV max sensitivity. DC coupled down to 1 volt. 4in. flat faced PDA tube. TB from 1 secs. per cm. to 0.1 microsecs. per cm. plus times 5 expansion £50.

MARCONI TF 428C. Measures AC 100MV to 150V 20HZ to 15 MHz. Measures DC 40MV to 300V. Complete with probe. Standard 240V operation £12-50 each.

MARCONI TF899. Measures 20MV to 2V AC. 50 HZ to 100 MHz. £10 each.

MARCONI TF 144H GENERATOR. In Very Good Condition £120.

MARCONI TF 195M-0/40 KHZ Sine Wave Generator 0/40 Volts output Metered. These must go £7-25.

MARCONI TF 891A AM GENERATOR 10 to 310 MHz £45.

MARCONI TF 801B. AM SIGNAL GENERATOR. 12 to 470 MHz. In good working condition £90.

MARCONI TF 938 (CT44). Absorption Wattmeter 10mW to 6 Watts. Input impedance 2-5 ohms to 20K ohms. Freq. response flat at 20KHZ. Calibrated in volts and db. 5in. mirror backed meter £9-50. P. & P. 75p.

MARCONI VVM TF 1041 £22-50.

MARCONI VVM TF 1041B £30.

MARCONI TF 1060/2. AM Generator 450-1200 MHz £140.

MARCONI VVM TF 1300. Measures AC 50MV to 100V, 20 HZ to 300 MHz, DC 100MV to 300V. Ohms 50 to 5 Meg Ohm. In fine condition £18 each.

AVO TRANSISTOR AND DIODE TESTER TYPE CT 537. In superb condition, in original crates with full instructions, circuit diagram, etc. New price £230 Plus. OUR PRICE £40 ea. Carr. £1-25.

EDDYSTONE 770 U. UHF RECEIVER £80.

RACAL RA 117 RECEIVERS. Brand new condition. Crated. £375 each.

RACAL RA17 RECEIVER £230.

SSB ADAPTOR for Racal RA 17 and RA117 £60 each.

TELEQUIPMENT S31 Rack mount Oscilloscope DC-6 MHz £40 each.

TELONIC 100 to 250 MHz Sweep Generator. Up to 4 watts output £120.

SURFACE PROFILE MONITOR by G. V. PLANNER type SPM 10 with recorder unit. MINT £140.

SLOPED CASES size 9 x 7in. with 8in. slope. 15in. long, in Hammer Grey. Brand New boxed £1. Packing and postage 37p.

BRAND NEW AMERICAN HIGH VOLTAGE CAPACITORS. 0-15mfd 120kV working. £20 each. Carriage at cost.

MODERN TELEPHONES type 706. Two tone grey. £3-75 ea. The same but black, £2-75 ea. P. & P. 25p ea.

Also **TOPAZE YELLOW** £4-50 ea. P. & P. 25p.

Ideal **EXTENSION** Telephones with standard GPO type dial, bell and lead coding. £1-75 ea. P. & P. 25p.

STANDARD GPO DIAL TELEPHONE (black) with internal bell, 87p ea. P. & P. 50p. Two for £1-50. P. & P. 75p.

All telephones complete with bell and dial.

POTENTIOMETERS
COLVERN 3 watt. Brand new, 5; 10; 25; 500 ohms; 1; 2-5; 5; 10; 25; 50k all at 13p ea.

MORGANITE Special Brand new, 2-5; 10; 100; 250; 500K; 1 in. sealed, 17p ea.

BERCO 2 1/2 Watt. Brand new, 5; 10; 50; 250; 500 ohms; 1; 2-5; 5; 10; 25; 50K at 15p ea.

STANDARD 2 meg. log pots. Current type 15p ea.

INSTRUMENT 3 in. Coivern 5 ohm 35p ea.; 50k and 100K 50p ea.

BOURNS TRIMPOT POTENTIOMETERS. 10; 20; 50; 100; 200; 500 ohms; 1; 2; 2-5; 5; 10; 25K at 35p ea. ALL BRAND NEW.

RELANCE P.C.B. mounting: 270; 470; 500 ohms; 10K at 35p ea. ALL BRAND NEW.

ALMA precision resistors 200K; 400K; 497K; 998K; 1 meg—0-1% 27p ea.; 3-25k, 5-6k, 13k-0-1% 20p ea.

**MULLARD
ELECTROLYTICS**
2200MFD 100V 10A (50°C)
BRAND NEW BOXED
70p each
13 off — 60p each
130 off — 45p each

RELAYS

S.T.C. Sealed 2 pole c/o 700 ohms (24V). 15p ea. 2,500 ohm (okay 24V) 13p ea. 6800 ohm coil 15p each.

Varley VP4 Plastic covers 4 pole c/o 5K—30p ea. 15K—33p ea.

CARPENTERS polarised Single pole c/o 20 and 65 ohm coil as new 37p each. 14 ohm coil 33p each. 45 ohm coil 33p each.

TRANSFORMERS. All standard inputs.

STEP DOWN ISOLATING trans. Standard 240V AC to 55-0-55V 300V, £3 ea. P. & P. 35p.

Nepiune Series. Multi 6.3 volts to give 48V at 3.5 amps etc. £3-50 incl. P. & P.

Large quantity LT, HT, EHT transformers and chokes.

3 TYPES ALL BRAND NEW HIGH QUALITY

(1) 3V 9 amp, 6V 9 amp, 12V 9 amp. Size 3 1/2 x 4 x 5 1/2in. £2 each. Packing and postage 47p.

(2) As above but 5-4 amp. Size 3 1/2 x 3 1/2 x 4 1/2in. £1-50 each. Packing and postage 37p.

(3) 3V 1-8 amp, 9V 1-8 amp, 27V 1-8 amp. Size 3 x 3 1/2 x 4 1/2in. £1-50 each. Packing and postage 37p.

All above 3 types also have 0-17V 1/2 amp and 17-0-17 1/2 amp. All windings are separate.

S.T.C. PUSH BUTTON ATTENUATORS. 0-9; or 0-90 in 1 db steps. State choice £3 ea. P. & P. 37p or £5 a pair P. & P. 57p.

MUIRHEAD Attenuator D239B. 85 db in 1 db steps. £3 each. P. & P. 37p.

COLVERN TEN TURN POTS. ex eq. 100K at 60p each. Complete with dial £1-50 each. P. & P. 15p.

CAPACITOR PACK 50 Brand new components only 50p. P. & P. 17p.

POTS 10 different values. Brand new. 50p. P. & P. 17p.

COMPONENT PACK consisting of 5 pots various values, 250 resistors 1/2 and 1/4 watt etc., many high stabs. All brand new. Fine value at 50p per pack. P. & P. 17p.

DELIVERED TO YOUR DOOR 1 cwt. of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY £3-50. N. Ireland £2 extra.

LOOSE LEAF BINDERS. Blue plastic cover, 4 ring. Standard size. 4 for £1. P. & P. 35p. 25 for £5. Carr. £1.

P.C.B. PACK S & D. Quantity 2 sq. ft.—no tiny pieces. 50p plus P. & P. 20p.

FIBRE GLASS as above £1 plus P. & P. 20p.

5 CRYSTALS 70 to 90KHZ. Our choice. 25p. P. & P. 15p.

MOTOR. min. synchronous. size 1 1/2 x 2 x 6in., 240V Operation 3-6 rpm, 25p each. P. & P. 5p.

TRIMMER PACK. 2 Twin 50/200 pf ceramic; 2 Twin 10/60 pf ceramic; 2 min strips with 4 preset 5/20 pf on each; 3 air spaced preset 30/100 pf on ceramic base. ALL BRAND NEW 25p the LOT. P. & P. 10p.

FLAT FACED 4" Twin Beam Tube. Type CV2193. Green Trace. Brand New. £4 each. P. & P. 37p.

GRATICULES. 12 cm. by 14 cm. in High Quality plastic. 15p each. P. & P. 5p.

PANEL mounting lamp holders. Red or green. 9p ea. Miniature. **PANEL** mounting lamp with holders—10V 15MA 5p ea.

BECKMAN MODEL A. Ten turn po complete with dial. 100K 3% Tol 0.25%—only £23 ea.

ELECTROSTATIC VOLTMETERS from 0-500 Volts to 0-10KV. S.A.E. with your requirements.

FIBRE GLASS PRINTED CIRCUIT BOARD. Brand new. Single sided up to 2 1/2" wide x 15" 1/2p per sq. in. Larger pieces 1p per sq. in. Double sided. Any size 1p per sq. in. Postage 10p per order.

INTEGRATED CIRCUIT test clip by AP inc. Gold Plated clip-on. Brand New individually boxed. £1-00 ea. P. & P. 10p.

DECADE DIAL UP SWITCH—5 DIGIT. Complete with esculcheon. Black with white figures. Size 4in. long x 1in. high x 1 1/2in. deep. Ex-Plessey. £1-40 each. P. & P. 15p.

LIGHT EMITTING DIODES (Red) from Hewlett-Packard. Brand New 38p ea. Holder 1p ea. Information 5p.

FIVE moving coil meters £2 P. & P. 37p.

VISCONOL EHT CAPACITORS

Size 1x2 1/2 ins.		
0.05mfd	2-5kV	50p ea.
0.01mfd	5kV	40p ea.
0.001mfd	10kV	50p ea.
Size 2 1/2 x 6 1/2 ins.		
0.05mfd	8kV	50p ea.
Size 1 1/2 x 5 1/2 ins.		
0.01mfd	10kV	50p ea.
0.002mfd	15kV	65p ea.
0.1mfd	4kV	35p ea.

DUBLIER 0.1mfd 5 KV; 0.1mfd 7.5 KV; 0.25mfd 7.5 KV; 0.5mfd 5 KV all at 50p ea. P. & P. 15p.

PHOTOCCELL equivalent OCP 71, 13p ea. Photo resistor type Clare 703 (TO5 case). Two for 50p.

MULLARD OCP70 10p each.

**20HZ to 200KHZ
SINE AND SQUARE WAVE GENERATOR**

In four ranges. Wien bridge oscillator thermistor stabilised. Separate independent sine and square wave amplitude controls. 3V max sine, 6V max square outputs. Completely assembled P.C. Board, ready to use. 9 to 12V supply required. £7.85 each. P & P 25p. Sine Wave only £5.85 each. P & P 25p.

NEW WIDE RANGE WOBBLULATOR

5 MHz to 150 MHz (Useful harmonics up to 1.5 GMZ) up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10-7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6-3V AC and use within minutes of receiving. All this for only £5 75. P. & P. 25p. Suitable miniature transformer for 240 Volt operation £1-25.

Unless stated—please add £1-50 carriage to all units.

VALUE ADDED TAX not included in prices—please add 10%

Official Orders Welcomed, Gov./Educational Depts., Authorities, etc., otherwise Cash with Order


Open 9 am to 6.30 pm any day (later by arrangement.)

CHILTMHEAD LTD

7/9 ARTHUR ROAD, READING, BERKS. (rear Tech. College, Kings Road) Tel.: Reading 582605/65916

Fantastic value in Test Equipment

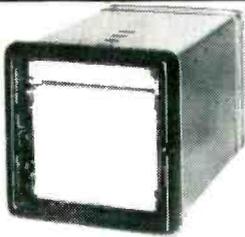
ALL EQUIPMENT BRAND NEW AND GUARANTEED FOR 6 MONTHS



**10 CHANNEL
EVENT RECORDER**

Designed for recording sequences of up to ten different operations, e.g. sequence of machine tool operation, switching sequences, etc. Record is presented in the form of square pulses. When energised, pen moves by approximately 4mm, to the right of zero line. Response time 100 milliseconds. Chart width 110mm. Chart length 50ft. Inv. capacity 72 hours. Chart speeds 20-60-180-600-1800-5400 mm/hour. Size 160x160x255mm. Weight 9 lbs. Price complete with accessories


£52.00

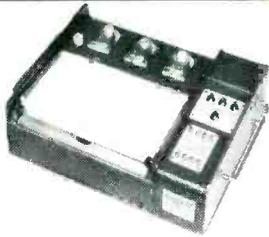

**THREE CHANNEL
HIGH SPEED RECORDER**

Strip Chart Recorder. Chart length 175ft. Footage indicator. Width of recording channel 80mm. Chart speeds (selected by pushbuttons) 1.2-12-30-60-120-300-600-3000 mm. per minute. Full deflection current 8mA. Internal impedance 210 ohms. External impedance 800 ohms. Dimensions 510x345x175 mm. Weight 44 lbs. Price complete with accessories


£90.00

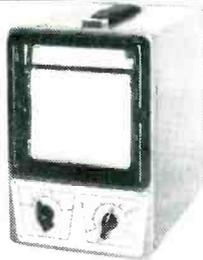

**PORTABLE AC/DC
RECORDING VOLTMETER**

Fitted with separate zero-marking pen. Accuracy 1.5% DC. 2.5% AC. Measurements ranges — AC and DC: 5-15-150-250-500mA. 1.5-5 Amps. 5-15-50-150-250-500V. DC only 150mV. Frequency range 45 to 1000 c/s. Chart width 100mm. Chart speeds 20-60-180-600-1800-5400 mm/hour. Weight 22 lbs. Price complete with accessories


£78.00

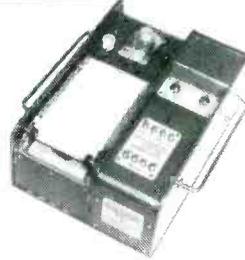

**SINGLE CHANNEL
HIGH SPEED RECORDER**

Chart length 175ft. Footage indicator. Width of recording channel 80mm. Chart speeds (selected by push buttons) 1.2-6-12-30-60-120-300-600-3000 mm per minute. Full deflection current 8mA. Internal impedance 210 ohms. External impedance 800 ohms. Dimensions 320x340x176mm. Weight 35 lbs. Price complete with accessories

£55.00

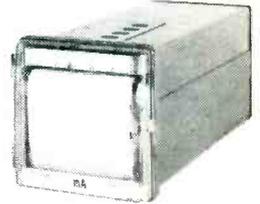

MINIATURE PEN RECORDER

Provides permanent record of DC currents up to 1mA. Eminently suitable for use where space is limited. Separate time marker pen provided. Chart width 80mm. Chart length 40ft. Chart speeds: Slow 20-60-180 mm/hour. Fast 600-1800-5400 mm/hour. Dimensions 120x120x285mm. Weight 7.7 lbs (3.5 Kg). Price complete with accessories

£39.00

Supertester 680R.

Buy it for what it is. Or buy it for what it can be.

ACCESSORIES TO CONVERT THE SUPERTESTER 680R TO THE FOLLOWING:

Amperclamp

For measuring a.c. currents from 250mA to 500 amps. **£11.95**



Signal Injector

Producing 1KHz and 500 KHz signals for circuit testing. **£5.95**



Temperature Probe

Covering the range -30 to +200°C. **£11.95**



Electronic Voltmeter

Input resistance of 11Mohms for d.c. and 1.6Mohms shunted by 10pF for a.c. **£18.00**



Transistor Tester

For transistors and diodes. **£11.00.**



£18.50
Complete with case & probes



SUPERTESTER 680R SPECIFICATION

Volts AC = 11 ranges from 2V to 2500V.
Volts DC = 13 ranges from 100mV to 2kV.
Amp DC = 12 ranges from 50µA to 10A.
Amp AC = 10 ranges from 200µA to 5A.
Ohms = 6 ranges from one tenth of 10m to 100MΩ.
Reactance = 1 range from 0 to 10MΩ.
Capacity = 6 ranges from 0 to 500pF and from 0 to 0.5µF and from 0 to 50,000pF.

Frequency = 2 ranges from 0 to 500Hz and from 0 to 5000Hz.
Output Voltage = 9 ranges from 10V to 2500V.
Decibels = 10 ranges from -24 to +70dB.

OTHER ACCESSORIES AVAILABLE SHUNTS
D.C. 25, 50 and 100 amps. **£4.50** each.
A.C. 25 and 100 amps. **£7.00** each. E.H.T. PROBE Extends d.c. voltage to 25,000V **£5.95.**



AC CLAMP VOLTMMETER

Clamp-on Voltmeter is used for measurements of AC voltages and currents without breaking circuits.

Specification

Measurement ranges:—Current 10-25-100-250-500 Amps. Voltage 300, 600 V. Accuracy 4%. Scale length 60mm. Overall dimensions 283x94x36mm. Weight 1.5 lbs.

£10.50


4-RANGE GENERAL PURPOSE TEMPERATURE RECORDER Type 01

Specially designed compact self-contained instrument for recording temperatures up to 500°C. The main design objectives were for an easy-to-use, robust instrument suitable for use in the laboratory and in the field. The four ranges are 10°C, 50°C, 100°C and 500°C. These are selected by push buttons allowing full use of the 3" wide chart. Two chart speeds 1" and 6" per hour are provided by the 240V 50Hz synchronous chart drive.

The 3% basic accuracy of the instrument, which is adequate for most applications, has been achieved without introducing stability problems in the d.c. amplifier, making the recorder ideal for use in schools, colleges and universities and by unskilled personnel. The recorder is complete with NiCh/NiAl thermocouple and mains lead. This product is brand new, and manufactured in our own laboratories with three month guarantee.

£95.00

plus £5.00 packing and carriage.

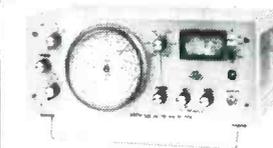

AM-FM GENERATOR Type AF 1065

Permits fast and accurate calibration of modern radio receivers. Suitable for calibration and testing in the laboratory. AM frequency range: from 140 KHz to 46 MHz in 6 ranges expanded range 430-530 KHz. FM frequency range: 9.5-12 MHz; 85-110 MHz. Frequency accuracy: better than 1%. RF output voltage: adjustable from 0.1 µV to 0.1V. Output impedance: 75 Ohm constant. Modulation: AM; FM; AM + FM. Amplitude modulation: 400 Hz; from 0-50% adjust. Frequency modulation: 1000 Hz adjust. Deviation from 0 - +/ - 50 KHz. External modulation: AM; FM; from 30 Hz to 15 KHz.

£225.00



MULTIMETER

0.1-1-10-100-1000mA. 2.5-10-20-250-500-1000V AC/DC. Sensitivity AC and DC all ranges except 10V-10,000 Ohm/V. Dimensions 212x118x75 mm. Weight 2.9 lbs. Price complete with steel carrying case and test leads

£4.95



AC/DC MULTIMETER

With taut band suspension movement. Sensitivity 20,000 ohms per volt on DC and 4,000 ohms per volt on AC.

Technical Data:
0.06-0.6-6-60-600mA-3 Amps DC.
0.3-3-30-300mA-3 Amps AC. 0.6-1.2-3-12-30-60-120-600 DC. 1200 Volts.
3-6-15-60-150-1300-600-900 Volts AC. 45 to 20,000 Hz.
500Ω. 5-50-500kΩ resistance. Decibel range 10 to -12dB. Accuracy (1% of F.S.D.):—DC and resistance measurements +2.5. Price with test leads, and storage case

£8.00



WIDE RANGE TRANSISTORISED R.F. SIGNAL GENERATOR

High stability low frequency generator. Basic circuit is a Wien-Bridge controlled sine wave oscillator and square wave is produced by means of a Schmitt trigger circuit. FREQUENCY RANGES: 4 from 10Hz to 100kHz. OUTPUT VOLTAGE: 1 millivolt p-p to 1 volt p-p ± 3% for sine and square wave. IMPEDANCE: 1k ohm. DISTORTION FACTOR: 0.2% for the sine wave output for the lower frequency range. < 1.0% for the upper frequency range. RISE TIME: < 0.1 microseconds for the square wave and 0.3 microseconds in the upper frequency range. WORKING VOLTAGE: 9 volt. 240mm x 140mm x 100mm. 2½ lbs. £27.



WIDE RANGE TRANSISTORISED R.F. SIGNAL GENERATOR

A low priced R.F. Generator. 8 ranges covers from 150kHz to 300MHz. The output can be unmodulated by means of an internal 400Hz oscillator. The A.F. signal is available from a separate output socket. Both output sockets are provided with an isolating capacitor (500 DC max.) FREQUENCY RANGES: 8 from 150kHz to 300MHz. ACCURACY: ± 2% R.F. OUTPUT VOLTAGE: 50 millivolts minimum. A.F. OUTPUT VOLTAGE: Approximately 1 Volt at 800Hz. WORKING VOLTAGE: 9 Volt. 240mm x 140mm x 100mm. 3½ lbs. £36.



WIDE RANGE TRANSISTORISED R.F. SIGNAL GENERATOR

The measuring ranges of this Capacity Resistance Bridge are 10pF to 100mfd capacity and 10ohms to 10 megohms. Bridge balance is shown by means of a luminous balance indicator tube. A further switch position permits measurement of capacity leakage current. RESISTANCE RANGES: 3 from 10 ohms to 10 megohms. CAPACITY RANGES: 3 from 10pF to 10mfd. WORKING VOLTAGE: 9 volt. 240mm x 140mm x 100mm. 2½ lbs. £19.50



TRANSISTORISED CAPACITY/RESISTANCE BRIDGE

A compact general purpose single beam solid state DC Y Amplifier — 5MHz. 3 db bandwidth D.C. coupled — dc — 5MHz. 100mV — 50V. 9 steps. Maximum input (a.c. coupled) 300Vp. Input impedance approx 1MΩ. 47pF. Sweep speeds ± 5%. 4 ranges 10mSec/cm to 10Sec/cm. Automatic operation. 3db bandwidth D.C. — 1MHz. Input impedance approx. 2.5 kΩ (220-240V 50-60Hz). Width 24cm. Depth 19cm. /lbs. £58.65.

Also available: function Gen 0.1Hz — 1MHz. frequency counter 5Hz — 9.999MHz. Ask for more details

ADD 10% VAT TO ALL PRICES ● PROMPT DESPATCH MAIL ORDER CALLERS WELCOME MON-FRI 9 A.M. to 5.30 P.M. SAT 9-30 A.M. to 2 P.M.

Add £2 towards the cost of packing and carriage on all items for U.K. delivery (except where packing and carriage are already indicated).



ELECTRONIC BROKERS LTD.

49-53 Pancras Road, London NW1 20B. Telephone 01-837 7781

WW-109 FOR FURTHER DETAILS

UNIQUE OPPORTUNITIES

GENERATORS

MARCONI TF867 STANDARD SIGNAL GENERATOR



Carrier Frequency Range: 15Kc/s-30Mc/s in 11 bands. Calibration Accuracy: $\pm 1\%$. Stability: After warm up the drift in a 10-minute period is, typically, less than 0.005% for carrier frequencies up to 3.2Mc/s and less than 0.01% from 3.2-30Mc/s. Output Voltage: 0.4V-4V. Impedance: 75 ohms nominal for outputs from 2.4 v. 75 ohms for outputs from 4V-2V. 13 ohms for outputs from 0.4V-0.4V.

Accuracy: below 3Mc/s $\pm 0.25dB$ of $\pm 0.1uV$. 3-10Mc/s $\pm 0.5dB$ or 0.02uV. 10-30Mc/s $\pm 1.0dB$ or $\pm 0.5uV$. Power Supply: 100-125V, 200-250V 40-100c/s. Dimensions: 18 in. high x 21 in. wide x 14 in. deep. Price **£165.00**

DOUBLE PULSE GENERATOR TYPE TF 1400/S
10 c/s-100 Kc/s. Complete with TM 6600. Pulse adjustable between 1.5 μ sec. before and up to 3,000 μ sec. Price **£145.00**

MARCONI A.M. SIGNAL GENERATOR TYPE TF801D

10-485Mc/s in five ranges. Output 0.1 μ V-1 Volt E.M.F. External Sine A.D. Frequency 30c/s-50Kc/s. Price **£195**

PHILIPS SQUARE WAVE GENERATOR MODEL GM2314

Range 15 c/s-200 Kc/s. Duration of square wave pulses between 0.75 μ sec and 40 m/sec. Square wave voltage 10V. Price **£75.00**

AMPLITUDE MODULATOR TF1102

100Kc/s-300Mc/s Sine-wave from 20 c/s-15 Kc/s and 20 x/s-500Mc/s. Price **£35.00**

MARCONI Type TF987/1 NOISE GENERATOR

1-200 Mc/s $\pm 0.5DB$ **£20.00**

MARCONI TF2092 NOISE GENERATOR **£295.00**

MARCONI VHF SIGNAL GENERATOR TF 1145

450-1900 Mc/s **£295.00**

PHILIPS VIDEO GENERATOR GM2887 **£95.00**

WAYNE-KERR VIDEO NOISE GENERATOR **£75.00**

MARCONI H.F. CIRCUIT MAGNIFICATION METER TF886A

A direct reading Q Meter 15-170 Mc/s Magnification 60-7200 Q **£45.00**

MARCONI DISTORTION FACTOR METER TF142F

100 c/s-8 Kc/s 0.05%-50% Measures all spurious components up to 30Kc/s **£35.00**

MARCONI PULSE GENERATOR TF675E

Repetition Frequency 50c/s-50Kc/s 0.15-40 μ Sec **£35.00**

MARCONI WIDE RANGE R.C. OSCILLATOR TF1130

Sine-waves 10c/s-Mc/s, square waves 10c/s-100Kc/s Direct outputs up to 31.6V. Attenuator with three impedances. **£120.00**

HETERODYNE UNIT TF1221

2Kc/s-100Mc/s **£45.00**

WAYNE-KERR NOISE GENERATOR CT410

A portable instrument for measuring the noise factor of radio receiving equipment, metric radar receivers, and radar wide-band i.f. amplifiers in the band 15KHz-160MHz. **£75.00**

MARCONI TYPE TF801A SIGNAL GENERATOR

Frequency range: 10MHz to 310MHz. O/P voltage: 0-100 db relative to 200 mV into 75ohm IV CW O/P available. Internal modulation: 400Hz, 1kHz and 5kHz to 80% sine or square. **£45.00**

ADVANCE TYPE D1/D SIGNAL GENERATOR

Frequency range: 10MHz-300MHz. O/P voltage: 1V-10mV. **£25.00**

ROHDE & SCHWARZ SIGNAL GENERATOR

BN4105 30-300 Mc $\pm 1\%$ Output 3 Volt. **£350.00.**

HEWLETT PACKARD 8690 SWEEP GENERATOR

plus 8693B Plug-in. 3.7-8.3 GHz. **£1,695.00.**

MARCONI TF995A/2M

AM/FM Generator. **£325.00.**

FANTASTIC VALUE IN OSCILLOSCOPES

TEKTRONIX

524AD **£125**

535A DC-30 Meg **£205**

545 Main Frame **£295**

545A With CA time base **£295**

545A **£295**


HEWLETT-PACKARD 185B

Sampling Oscilloscope DC-1000 Meg complete with 187C

Dual Trace AMP has 350

microsec. Rise time (1000

MC). **£395**

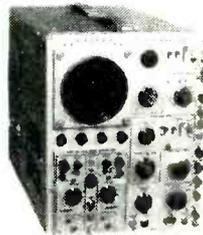

COSSOR CDU 110

Dual Channel Transistorised DC-25 MHz at 5mV/cm. 0.2 microsec. 0.5 3% 5X Magnification extends sweep speed to 40 nanosec./cm. Sweep delay 180 nanosec. **£249.50**



COSSOR CDU 120

Dual Channel fully transistorised 50 mV/cm to 10V DC-60 MHz. Rise time 6 nanosec. 1 mV/cm at 25 MHz. 0.1 microsec. **£349.50**

COSSOR CDU 150

Rugged Transistorised fully portable Dual Channel DC-35 MHz at 5mV/cm. As used by numerous government departments (c/f CT531) **£375**
COSSOR. The very latest Cossor 4000 Dual beam. 55 MHz at 50mV/cm Trigger. SCOP-ONE ONLY **£425**
DYNAMCO 7100 1Y2 7100 1x2 Oscilloscope. Dual channel with sweep delay, suitable for computer maintenance and most laboratory applications 30MHz. 1mV 10ys to 5s delay. BRAND NEW **£295.**

MINITRON

K.G.M. Type 3015F 7 Segment display showing figures 0-9 plus decimal point. Character of 9mm height. In 16 DIL case.

NEW LOW PRICE £1.40
SN7447N BCD Decoder Driver **£1.00**

SINE COSINE POTENTIOMETER 47K


Precision component by Pye Model 2002. Manufactured to rigid Ministry specification. The assembly consists of three units mounted in one frame. Each unit contains two sine and two cosine potentiometer sections, the sliders being ganged together. Electrical connections: 2 end taps, slider and centre tap. Mechanical IP: 30 r.p.m. Max. torque: 3/4 oz./in. Dimensions: W. 6 1/2 in. H. 5 in. D. 7 1/2 in. Wt. 7 1/2 lbs. Ex equipment. Good condition. Price **£5.** Carriage extra.



INFRA-RED SPECTROPHOTO-METER

A single beam instrument designed primarily to analyse the effluent from a gas chromatograph, however the fast response and fast scan capabilities make it suitable for fast reaction studies involving conventional gas, liquid, or solid samples. The wave length range is 2.5 to 14.5 microns. In excellent condition. Price **£175.00**

Beckman Type IR-102

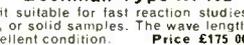

TRANSISTOR TEMPERATURE CONTROLLER TYPE 990

Completely transistorised self-contained direct deflecting units for indicating and controlling temperature accurately over a wide range. Suitable where a signal can be converted into d.c. Sensitivity 10 ohms per MV. Minimum F.S.D. 8 MV. Cold junction compensation. Calibrated scale length 6.5". 0-800°C. Accuracy $\pm 1\%$. Front panel size 10" x 8", weight 11 lbs. Mains supply 100-260 V. Control switching and thermo-couple connections all at back of case. Price **£18.50** plus **£2.00** packing and carriage.

ASCOP DIGITAL ENCODERS

Type 504A-8-001 Price **£20.** Type EDD8G Price **£20.**

SYNCHROVERTER SWITCH TYPE G1280


BY ELLIOTT **PRICE £3.**

POWER SUPPLIES

POWER SUPPLIES, IBM EX-COMPUTER HIGHLY STABILISED, TRANSISTORISED LOW VOLTAGE POWER SUPPLIES.

These modular units incorporate overload protection on both INPUT and OUTPUT. Load regulation of 1% or better. Low ripple and fast response time. Input voltage 120-130 50 Hz. Available in the following types:

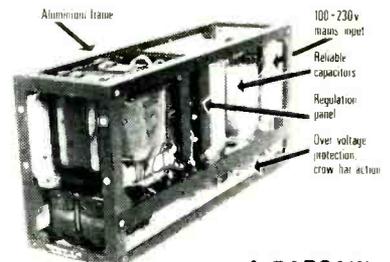- 6 Volt 8 Amp **£21.00**
- 8 Volt 12 Amp **£17.00**
- 9 Volt 16 Amp **£20.00**
- 12 Volt 4 Amp **£20.00**
- 12 Volt 12 Amp **£22.00**
- 12 Volt 20 Amp **£24.00**
- 30 Volt 7 Amp **£19.00**



A BARGAIN IN NEW POWER SUPPLIES. AT LESS THAN HALF MANUFACTURERS PRICES.

O/P Voltage 7.5V-9V. Max. load current 10 Amps. Max. ripple on full load approx. 60mV. p.p. Threshold current 10.5A. Overvolt protection. **OUR PRICE £12.50**

EX-COMPUTER HIGH GRADE FULLY STABILISED POWER SUPPLIES

- Input 200/250V.
- ADVANCE TYPE DC 207 **20 Volts 9 Amps.**
- 10 Volts 5 Amps.**
- 10 Volts 3 Amps.**
- 20 Volts 2 Amps.**
- ADVANCE TYPE DC 200 **20 Volts 13 Amps.**
- 10 Volts 5 Amps.**
- 20 Volts 2.5 Amps.**
- ADVANCE TYPE DC 202 **35 Volts 9 Amps.**
- 24 Volts 4 Amps.**
- 10 Volts 8 Amps.**
- ADVANCE TYPE DC 197 **6 Volts 7.5 Amps.**
- 6 Volts 11 Amps.**
- 28 Volts 9 Amps.**
- WESTINGHOUSE Fully Fused Input 200/220/240/10 **14 Volts 0.75 Amps**
- 20 Volts 4 Amps.**
- 25 Volts 2.5 Amps.**
- 30 Volts 0.75 Amps.**
- WESTINGHOUSE **6 Volts 7.5 Amps.**
- 6 Volts 11 Amps.**
- 28 Volts 9 Amps.**

£18 EACH. P. & P. £2.

EVERSHED SAFETY OHMMETER

For testing the continuity and resistance of circuits, consists of a hand-driven generator and a direct reading ohmmeter. Range in ohms 0-4, 0-5, 0-10, 0-100, 0-300. **£10**

IGNITION TESTER

Ideal for garages, this brand new instrument is used to display all ignition faults. Supplied complete with instruction manual showing photographs of displays, making use very simple. Sold complete with isolating transfer for use on 240V 50Hz supply. Display cards also available for garages and other places wishing to advertise this equipment in use. Made by British Physical Laboratories Ltd., originally for use on the Canadian market. Price **£75**

LOW OHMMETER MODEL RM155-BM VIII

Ideal for the measurement of low resistance. Low Current. 200mA at short circuit. Range 1m Ω to 152 in 2 Ranges ± 0.5 milliohms or $\pm 5\%$ whichever is the greater. **£20.00.**

SODECO IMPULSE PRINTING COUNTER

4 Digit Decimal Counter 10c/second Electrical Reset & Print-out 24 Volts Type PN117 Brand New. **£49.50.**

PHILIPS VALVE VOLTMETER

MODEL GM6014
Max. 300mV, 1000Hz-30MHz. **PRICE £30.00**



ELECTRONIC BROKERS LIMITED

49/53 PANCRAS ROAD : LONDON NW1 2QB. Tel: 01-837 7781

ADD 10% VAT TO ALL PRICES

to purchase some of the World's finest calibration instruments at savings of


33 1/3% AND MORE!

PEN RECORDERS

BRAND NEW MINIATURISED STRIP CHART RECORDER BY RUSTRAK



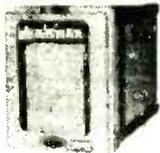of America. This Recorder indicates the magnitude of applied currents or voltages by a continuous distortion-free line on pressure sensitive paper. Moving coil movement, scale calibrated 0.1 milliamp d.c. Internal resistance 100 ohms. Chart drive motor 240 V 50Hz. Chart speed 1" per hour. Complete with handbook. Price £35.00 plus £5.00 packing and carriage.



SINGLE PEN RECORDER

by Record Electrical. 3" chart, sensitivity 1 milliamper, chart speed 1" and 6" per hour. Size 8" x 11" x 6". Offered complete with pen assembly and spare chart. Listed at over £100—this month's special price due to bulk purchase £39.50 plus £5.00 packing and carriage.

LEEDS & NORTHRUP STRIP CHART RECORDER

This well-known instrument is fitted with a Series 60 control unit servo amplifier 101041 BR EQ. Range: 5.571 to 19.855. Ref. junction 320F. Primary element: Pt. Pt. 12% RH JMC. Response time: 5 secs. for I.S.d. Chart width: 7 in. Chart speed: 1 in. per hour. Power supply: 120V 50 Hz (auto-transformer available). Dimensions: Ht. 18", width 11", depth 12 1/2". Weight 51 lbs. **PRICE £80.00**

POTENTIOMETERS

TEN TURN 3600 ROTATION

Res Ohms	Linearity Per cent	Manufacturers	Model	Price
100/100/100		Beckman	A	£4.00
100	0.5	Beckman	A.S	£2.00
200	0.5	Beckman	A	£2.00
500	0.1	Beckman	S	£2.50
500		Colvern	PX4	£2.25
500		Foxes	PX4	£2.00
500		Colvern	2610	£2.50
500		Colvern	2610/1000/11	£3.00
500	1.0	Relcon	HEL107-10	£2.25
1K		Relcon	HEL0710	£2.25
2K	0.5	Beckman	SA1101	£3.00
2K	0.25	Beckman	7216	£3.00
2K		Reliance	GPM15	£2.00
2K		General Controls	GP A154	£2.00
5K		Relcon	07-10	£2.50
5K		Colvern	CLR2503	£3.00
10K	0.5	Beckman	A	£3.00
10K	0.1	Beckman X	A	£3.50
10K	0.1	Colvern	CLR261/1001	£3.50
15K		Colvern	CLR2402	£3.00
18K		Beckman	A	£3.00
25K	0.5	Hellpot	SAJ337	£3.00
29K	0.05	Beckman	SA1244	£4.50
30K		Colvern	2402	£1.50
30K		Beckman	SA95C	£3.00
30K	0.1	Beckman	A.88	£3.50
30K	0.5	Beckman	SA1692	£3.00
30K	0.25	Beckman	SA1679	£3.25
30K	1.0	Colvern	2402/1	£1.50
50K		Reliance	07-10	£2.25
50K		Reliance	07-5	£2.25
50K		Colvern	2503	£2.25
50K		Foxes	PX4	£2.25
50K	0.5	Beckman	A	£3.00
50K	0.1	Beckman	A	£3.50
100K/100K		Ford	A	£5.00
100K	0.1	Beckman	A	£3.50
100K	0.5	Beckman	A	£3.00
100K		Colvern	2501	£2.25
100K		Colvern	2610	£2.50
298K	0.1	Beckman	8A3902	£3.50
300K	0.1	Beckman	A	£3.50

THREE TURN 780 ROTATION

100/100	0.5	Beckman	C	£3.00
100/100		Beckman	Type C	£3.00
300		Beckman	9303	£2.25
1K		Fox	PX2/H3	£2.25
10K	0.5	Beckman	C.S	£2.25
20K/20K	0.1	Beckman	C.S	£3.00
10K/10K	0.1	Beckman	C	£3.00
50K	0.5	Beckman	C.S	£1.75

FIFTEEN TURN 5400 ROTATION

25K/25K		Beckman B	10 watts	£6.50
46K/46K		Beckman B	10 watts	£6.50

TWENTY TURN 7200 ROTATION

1 Meg.		General Controls	PXM130	£4.00
50K		Reliance		£2.00

156 TURN 56/60 ROTATION

460		Kelvin Hughes	KTP0701	£9.50
-----	--	---------------	---------	-------

FIVE TURN 1800 ROTATION

200		Relcon	HEL07-05	£2.25
500		Colvern	CLR2505	£2.00
U1 5K		Colvern	CLR2605	£2.00

FIVE-AND-A-HALF TURN

500		Colvern	2405	£2.00
-----	--	---------	------	-------

OUR STOCKS ARE CONSTANTLY CHANGING—PLEASE LET US KNOW YOUR EXACT REQUIREMENTS

COMPUTER ACCESSORIES


80 COLUMN HAND PUNCHES



Ideal for stock control, sales analysis, back-up in existing computer installations, DP training centres, schools, etc. New low cost model £59.50 plus carriage.

DE LUXE MODEL

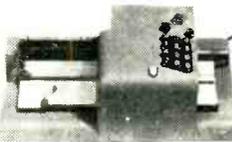Incorporating tabulating mechanism. £79.50 plus carriage.



ELECTRIC HAND VERIFIER

£89.50 plus carriage.

All machines supplied with numeric keytops and dust-covered by our three month guarantee. Delivery ex-stock. Optional extras alpha keytops and chip tray.

Special Computer Offer!

SAVE 75% OF LIST PRICE ON THIS DEC PDP SYSTEM

PDP-12C	4K CPU and Console	£3.50
DF32	32K Disk and Control	£3.50
DW08A	10 Bus Level Converter	£3.00
PC12 & PC05	High Speed Reader/Punch	£3.00
BA12	Peripheral Expander	£3.00
ASR33	Teletype	£3.00
PT08C	Dual Channel Interface	£3.00
KP12	Power Fall/Restart	£3.50
AF01A	A/D Converter/Multiplexer	£3.50

* Fully maintained by DEC since new
 * DEC maintenance available on resale
 * Available in our showroom now
 * Only three years old
 £5000
 Also available PDP 8F with ASR 33 £1150

TELETYPE PUNCH

BRPE High-speed punch Self-contained, consists of punch unit, base, motor unit. For use in many data communication systems. Operating speeds up to 100 characters per second (1100 words per minute). Available for punching 5, 6, 7, or 8 level codes, into 1/2" tape. Synchronous, parallel-wire input. £145



WELMEC 7 & 8 HOLE ELECTRO-MECHANICAL PUNCHES & READER

Models S110 and R82C. 17 char. per sec. Rebuilt, available from stock. £45.

ICT KEYBOARDS

In original packing—Numerical from £4.50

ICT KEYBOARDS

In original packing—Alpha-numeric Prices from £12.50

Magnetic Tape Transporters AMPEX TM4, TM2, TM7, FR300, IBM 7330, POTTER, ICL Magnetic Drums. From £75.

IBM PUNCH CARD EQUIPMENT FULLY GUARANTEED

024 Automatic alphanumeric keypunch	Prices from £340.00
026 Automatic alphanumeric printing keypunch	£820.00
056 Verifier features and operation same as 024, 026	£380.00
082 Sorter 500 cards per minute are sorted	£740.00

Carriage extra.

FREQUENCY CONVERTER MODEL B.40

50 KVA to 60 Hz power frequency converter. Fully overhauled.

Specification:
 Prime Mover: Electric Motor
 Input: 220/380V 50Hz 3ph
 Output: 220V 60Hz 3ph
 at 50 KVA with PF of 0.8. **PRICE £450.00**

HEWLETT PACKARD DIGITAL RECORDER MODEL 565A

Data Entry, parallel to 11 columns. Print speed 5 lines per second. **PRICE £85.00.**

HEWLETT PACKARD 200 CD Sine wave Oscillator

5Hz-600KHz 10 Volts. **£59.00.**

PYE HIGH RESISTANCE OHMMETER MODEL 10B

Range from 0.3-20,000 Megohms In 4 ranges at 500V. Used for the measurement of components or circuits having high parallel capacitance. **PRICE £20.00**



MULLARD VALVE VOLTMETER MODEL E7555/2

PRICE £20.00

COLVERN DIGITAL CODERS (Shaft Digitisers)

Digital Coders are electromechanical devices, which give a unique parallel digital code output representing the angular position of the shaft. The current handling capacity is sufficient to operate relay decodes and indicators direct without intermediate stage of amplification. 3 size magstrip, 256 divisions, max. torque for reflected binary code 4.5 oz. ins. **PRICE £10.00**

WIDE RANGE OSCILLATOR TYPE 400C by DAWE

1 c/s-1,000 c/s. **PRICE £35.00**

FANS BY PLAINAIR

115V-3 Phase 400 c/s-11,000 rpm. Type 1PL41-234 **PRICE £4.00**

R.C. OSCILLATOR TYPE G432 by FURZEHILL

Square and sine wave. 250 Kc/s. **PRICE £25.00**

SPECIAL OFFER SPECTRUM ANALYSER HEWLETT PACKARD 8551B

10MHz-12GHz and 851B Extension to 40GHz. With W/G Mixers and very little used Ex Calibration Lab. **£3,950.00.**

VENNER 3334

Digital Frequency Meter 0-1MHz **£45.00.**



VENNER 3336

Digital Counter Six Digit 0-1MHz **£55.00.** With 15 Meg Counter extension for above **£85.00.**



DYNAMCO 2001

Digital Voltmeter 50µV-2KV 0.05% **£175.00.**

DYNAMCO type 2022S

Long scale D.V.M. and Ratiometer. The 2022 is a high accuracy long scale instrument operating on the potentiometric principle. It features a very high input impedance with exceptionally low current errors, an external scaling facility, seven operating modes and digital output.

Scale	39999
Range	10µV to 2kV
Resolution	1 part in 40,000
Accuracy	0.0025% of F.S.D.
	0.01% of reading
	Optimum 0.0025% F.S.D.
	0.0025% of reading
Input impedance	> 25,000 M ohm
C.M.R.	160 dB at DC
	120 dB at 50Hz
	Typical
	£275.00

MEGGER CIRCUIT TESTING OHMMETER

For Measuring conductor resistance. By Evershed and Vignale. **£22.50.**

BELL & HOWELL

5-12 and 18 Channel U.V. Recorder **£395.00.**
 5-12 12 Channel **£350.00.**



ELECTRONIC BROKERS LIMITED

49/53 PANCRAS ROAD : LONDON NW1 2QB. Tel: 01-837 7781

ADD 10% VAT TO ALL PRICES

Samson's

(ELECTRONICS) LTD.
 9 & 10 CHAPEL ST., LONDON, N.W.1
 01-723 7851 01-262 5125

STEP DOWN 240/110v. AUTO TRANSFORMERS FOR AMERICAN EQUIPMENT. Fitted with 2 or 3 pin American sockets. All sizes from 80 to 25kva. available. Send s.a.e. for list. American sockets, plugs, adaptors also available.

DAVENSET ISOLATION TRANSFORMERS
 Pri. 10-0-200-220-240v. Sec. 240v. Centre tapped 1.2kva. Conservatively rated. Size 8½ x 7 x 8½ ins. Wgt. 59 lbs. Open frame type, terminal connections. Fraction of maker's price. £17.00 carr. £1.00.

PARMEKO ISOLATION TRANSFORMERS
 Pri. tapped. 100-110-200-220-230-240-250v. Sec. 115v. 13.5 amps. Conservatively rated, fully shrouded. Table top connections. Size 13 x 10 x 8½ ins. £32.50 carr. £2.00. Pri. tapped 200-210-220-230-240-250v. Sec. tapped 90-100-110-120v. 7.5 amps. Conservatively rated table top connections. Size 9 x 8 x 8 ins. £22.50 carr. £1.50.

T.E.C. HEAVY DUTY ISOLATION TRANSFORMERS
 Pri. 240v. Sec. 150v. 4kva. Size 9 x 8½ x 7 ins. Wgt. 70 lbs. £22.50 carr. £2.00.

RICH AND BUNDY. Pri. 220-230-240-250v. Sec. 265-270-275v. 1400 watts. Conservatively rated. Size 8 x 8 x 7 ins. Terminal block connections. £17.00 carr. £1.00.

ADVANCED COMPONENTS CONSTANT VOLTAGE TRANSFORMERS
 Input 190-260v. Output 230v. 150 watts. Type 140A £7.00 carr. 75p. Output 28v. 8 amps open frame type £4.50 carr. 75p. Output 4v. 3 watts 75p carr. 25p. Output 240v. 30 watts enclosed type £1.50 carr. 35p.

440 VOLT S.P. TRANSFORMERS
 No. 1 T.E.C. Pri. 380-400-415-440v. Sec. 33 60 amps. Size 9 x 9 x 8 ins. Terminal block connections. Conservatively rated. £20.00 carr. £2.00. No. 2 Davenset. Pri. 415-440-525v. Sec. 220v. 2kva. Size 9 x 8½ x 8 ins. £25 carr. £2.00. No. 3 Davenset. Pri. 380-400-415-440v. Sec. 110v. 6 amps. Size 6 x 6½ x 5½ ins. £8.50 carr. £1. No. 4 Davenset. Pri. 380-400-415-437v. Sec. tapped 110-270v. 0.15kva. Size 7 x 5½ x 5 ins. £8.50 carr. 75p. No. 5 Rich and Bundy. Pri. 380-400-420-440v. Sec. 240v. 40 watts. Size 4 x 4 x 4 ins. Terminal block connections. £2.50 carr. 50p. Drake. Pri. 440v. Sec. 220-240v. 100 watts. Shrouded. £3.25 postage 40p.

H.T. TRANSFORMERS BY FAMOUS MANUFACTURERS

PARMEKO. Potted type. Pri. 110-230-440v. Sec. 630-0-630v. 105mA. 5v. 4a., 5v. 2a. £3.50. carr. 50p. Pri. 110-220-240v. Sec. 1875v. 60mA. and 500v. 31mA. £4.00 carr. 50p. Pri. 110-220-240v. Sec. 300-250-0-250-300v. 80mA. £1.75 carr. 25p.

WODEN. Pri. 230v. Sec. 890-710-0-710-890v. 120mA. Open frame type table top connections, tropicalised. £3.00 carr. 50p. Pri. 220-240v. Sec. 350v. 150mA. 6.3v. 8a. 6.3v. 3a. 'C' core £2.50 carr. 40p. Pri. 220-240v. Sec. 240-0-240v. 90mA. 15v. 1a. 12.6v. 3a. £2.25 carr. 40p. Pri. 220-240v. Sec. tapped 150-165v. 4a. open frame type, table top connections £3.95 carr. 50p. Pri. 220-240v. Sec. 63v. 1.6a. and 24v. 0.8a. and 6.3v. 1a. open frame type table top connections £3.00 carr. 50p.

GARDNERS. Pri. 220-240v. Sec. 350-290-0-290-350v. 250mA. 6.3v. 4a., 6.3v. 4a., 5v. 3.5a., enclosed type table top connections £4.00 carr. 75p. Pri. 220-240v. Sec. 350-0-350v. 60mA. 6.3v. 4a., 5v. 2.5a. £2.00 carr. 50p.

GRESHAM. Pri. 220-240v. Sec. 710-0-710v. 120mA. open frame type table top connections £2.75 carr. 50p. Pri. 110-230-250v. Sec. 230v. 200mA. 6.3v. 7a. potted type £3.50 carr. 50p.

G.E.C. L.T. TRANSFORMERS

All Primaries 220-240v. Type 1 tapped. 63-68-74v. 3a. and 6.3v. 4a. terminal block connections. Unshrouded £3.00. P.P. 50p. Type 2 tapped. 59-61-65-67-69v. 10a. T blocks connections. Unshrouded £6.00 carr. 75p. Type 3 tapped. 56-58-60v. 3a. T block connections. £2.95. P.P. 50p. Type 4 100-0-100v. 65mA. and 61-64-67v. 150mA. and 6v. 1a. £1.75. P.P. 25p. Type 5 tapped. 11.5-13.5v. 14a. and 13.5v. 14a. twice. Unshrouded. T block connections. £4.50 carr. 75p. Type 6 10v. 2a. and 50v. 0.6a. T block connections. Unshrouded. £1.50 carr. 25p. Type 7 15v. 4a. and 13v. 6a. T block connections. Unshrouded. £3 carr. 50p. Type 8 17v. 2a. twice. unshrouded. £1.75. P.P. 30p.

AMOS 'C' CORE TRANSFORMERS

Pri. 220-240v. Sec. 53-6v. 6a. £3.75. P.P. 50p. Pri. 240v. 17.5v. 6a. £2.25. P.P. 35p.

L.T. TRANSFORMERS

Famous maker. Special offer. No. 1 Pri. 240v. Sec. 17v. 2a. twice. Open frame type £1.75. Postage 30p. No. 2 Pri. 220-240v. Sec. 12v. 10a. Open frame type £2.50. Postage 40p.

SPECIAL OFFER OF MULTI TAPPED L.T. TRANSFORMERS VERY CONSERVATIVELY RATED

Gresham Pri. 200-220-240v. Sec. 29.5v. 2.6a. twice. 20v. 5a. twice 15v. 0.1a. four times. 'C' Core. Table top connections £8.95 carr. 75p.
 Pri. 200-220-240v. Sec. 16.3v. 1a. twice. 10v. 1a. twice. 22.5-25-28.8v. 5a., 26.5v. 2.5a., 23.9v. 1a., 6.3v. 2a., 145-0-145v. 200 mA 'C' Core. Table top connections £4.95 carr. 75p.
 Pri. 200-220-240v. Sec. 20-21-22-23-24-25v. 6a., 20-21-22-23-24-25v. 3.5a., 18-19-20-21-22-23v. 2a., 11-12-13-14-15v. 0.5a. twice 100-0-100v. 150 mA 'C' Core. T. top connections. £7.25 carr. £1.

VAT PLEASE ADD 10% TO ALL ORDERS, INC. CARR./PACKING.

L.T. SMOOTHING CHOKES

GRESHAM 'C' core swinging types. 7.5 m/h. 6a-75 m/n 0.5a. £2.50 carr. 50p. 10 m/h. 4a-100 m/n 0.5a. £3.00 carr. 50p.
G.E.C. 150 m/h. 3a. unshrouded fully tropicalised £2.75 P.P. 35p.
REDCLIFFE. Oil-filled types 100 m/h. 2a. £2.50 P.P. 45p. 130 m/h. 1.5a. £1.50 P.P. 25p. Mains filter chokes 10 m/h. 2a. 50p P.P. 20p. All above chokes ½-1 ohm res.

G.P.O. RELAYS 3000 TYPE 10052 1.25 amp. Make contact. 80p. P.P. 10p. 75Ω 3 M. 1 B. 1 CO. Normal contacts. 40p. P.P. 10p.

H.T. TRANSFORMERS

PARMEKO. Pri. 240v. Sec. 250-0-250v. 50 mA. 6.3v. 1a. £1.25. P.P. 35p. Size 4 x 3 x 2½ ins.
GARDNERS. 'C' core. Pri. 240v. Sec. 300-0-300v. 66 mA. 6.3v. 4a. £1.50. P.P. 35p. Size 4 x 3 x 2½ ins.
A.C.I. Pri. 240v. Sec. 250v. 60 mA. 15v. 1.2a. 6.3v. 4.5a. £1.25. P.P. 35p., open type table top connections. Size 4 x 3½ x 3 ins.

T.C.C.-DUBILIER OIL-FILLED BLOCK CAPACITORS

4mfd. 4.5kv. D.C. wkg. £3.00 carr. 75p. 0.5mfd. 10kv. D.C. wkg. £2.50. P.P. 50p. 4mfd. 1250v. D.C. wkg. 50p. P.P. 20p. 4mfd. 2kv. wkg. 75p. P.P. 20p. 1mfd. 5kv. D.C. wkg. £1.00. P.P. 25p. 8mfd. 200v. D.C. wkg. Three for 75p. P.P. 25p. 8mfd. 750v. D.C. wkg. 50p. P.P. 20p. 6mfd. 750v. D.C. wkg. 40p. P.P. 20p. 4mfd. 500v. D.C. wkg. 30p. P.P. 10p. 1mfd. 2500v. D.C. wkg. 40p. P.P. 10p. 0.5mfd. 500v. D.C. wkg. Six for 50p. P.P. 25p.

TUBULAR MOTOR START CAPACITORS

HUNTS 20mfd. 275v. A.C. 75p. P.P. 25p. 15mfd. 250v. A.C. 50p. P.P. 15p. 7.5mfd. 250v. A.C. 60p. P.P. 15p. 6mfd. 440v. A.C. 60p. P.P. 15p. T.C.C. 3.5mfd. 250v. A.C. 40p. P.P. 15p. 2.2mfd. 250v. A.C. 35p. 2.5mfd. 300v. A.C. 40p. P.P. 15p. 4mfd. 250v. A.C. 40p. P.P. 15p. 8mfd. 400v. A.C. 50p. P.P. 20p. 10mfd. 250v. A.C. wkg. 50p. P.P. 15p. 48mfd. 275v. A.C. wkg. 75p. P.P. 15p. 2.6mfd. 500v.

AMERICAN OIL-FILLED BLOCK CAPACITORS

8+8+4mfd. 650v. wkg. D.C. £1.90. P.P. 25p. 4+4+4+4+1mfd. 600v. wkg. D.C. £1.90. P.P. 25p. 8mfd. 1000v. wkg. 75p. P.P. 25p. 6mfd. 1000v. D.C. wkg. 60p. P.P. 20p. 6mfd. 600v. D.C. wkg. 50p. P.P. 15p. 4mfd. 350v. D.C. wkg. 30p. P.P. 10p. 1.5mfd. 1500v. D.C. wkg. 35p. P.P. 15p.

H.T. SMOOTHING CHOKES

Parmeko potted types. 5h. 500mA. £3.00 carr. 50p. 10h. 300mA. £2.00 carr. 50p. 10h. 180mA. £1.50 carr. 30p. 15h. 180mA. £2.00 carr. 50p. Swinging type 5h. 0.4a. 4h. 0.25a. £1.50 carr. 35p. 10h. 120mA. 75p carr. 25p. 15h. 75mA. 10h. 75mA. 50h. 25mA. 50p carr. 20p.

A.C. GEARED MOTORS BY FAMOUS MAKERS


230/250v. 50 cycles induction type. 4/2 r.p.m. Cont. rating 5 lb. ins. Right angle worm drive. Overall size 7 ins. Dia. 3 ins. Spindle length 3 ins. Dia. ½ in. £4.75 carr. 45p. Gear motors 50v. D.C. Shunt wound. Cont. rating. 34 r.p.m. 2 lb. ins. Right angle worm drive. Overall size 6 x 3 ins. dia. Spindle 1 in. ½ in. dia. £3.75 carr.

BODINE ELECTRIC GEARED MOTORS

HP. 1/35 A.C. 115v. 50 cycles. RPM 137. Torque 9 in lbs. Ratio 10-1. Pulley Drive. Complete with Control Box containing Capacitor, On/Off Switch. Micro switch reversing connections. Ideal for electric door systems. £10.00 carr. £1.

HART ELECTRONICS

Audio Kits

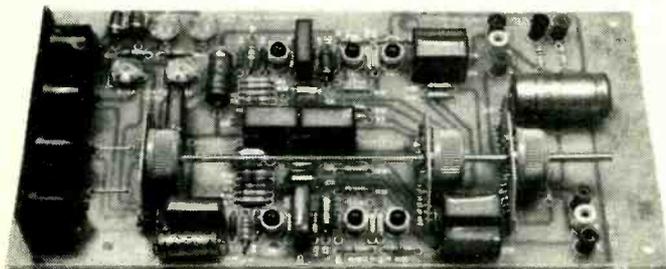

This is our Bailey/Burrows Stereo pre-amp front end. We think it is the best engineered kit of the best pre-amp circuit available, and there is a back end/tone control unit of similar advanced design to go with it which is only 1½" deep so it fits almost anywhere, but of course it's at its best in a Hart universal amplifier metalwork with a couple of Hart Bailey 30 watt power amps to keep it company. That's a recipe for real Hi-Fi with electronics you'll be too proud to cover up.

Also a delight to the connoisseur are our printed circuits and components for the Stuart tape circuits.

This is a most useful high quality circuit with the record, replay and bias functions on separate boards thus giving considerable versatility of use. For instance a stereo replay channel can be built for £6 for single speed use without external components or a switch may be added for multispeed operation.

Stuart reprints all three articles under one cover.
 Price 30p. No V.A.T.

Penylan Mill, Oswestry, Salop.

Personal callers are always welcome, but please note we are closed all day Saturday

WE ARE SUPPLYING

Printed Circuit Boards, Components and Kits for the

D. O'N. WADDINGTON DIGITAL MULTIMETER

This most interesting project fulfils the long-felt want for a Digital Multimeter with the added bonus of counter/timer functions, all at a price which makes it extremely attractive to the amateur, educational or commercial user.

Please send 9" x 4" SAE for full details:

TELEPRINTER EQUIPMENT LIMITED

Sales . . . Rentals . . . New . . . Refurbished . . . Installation . . .
Maintenance . . . Overhauls . . . Spare Parts . . . Prompt Deliveries

CREED EQUIPMENT

TELEPRINTERS Models 7B, 54, 75, 444
PERFORATORS 7PN, 85/86, PR75, 25
TAPE READERS 6S4, 6S5, 6S6, 6S6M, 92, 35, 71, 72, 74
HIGH-SPEED TAPE WINDERS 80-0-80V POWER SUPPLY UNITS, etc.

TELETYPE CORP. EQUIPMENT

TELEPRINTERS 15, 19, 20, 28, 32, 33, 35
all configurations
PERFORATORS 14, 19, 28 LPR, RECEIVE & MONITOR GROUP CABINETS
TAPE TRANSMITTERS 14, 20, 28 LBXD & LX D TRANSMIT GROUPS, etc.

SIEMENS EQUIPMENT

TELEPRINTERS T100 and T-68 in various configurations
PERFORATORS T-LOCH 12, T-LOCH 15, A, B, D & F, etc.

OTHER EQUIPMENT

KLEINSCHMIDT, OLIVETTI, LORENZ, COCQUELET, BRITISH, AMERICAN,
CONTINENTAL, ARABIC and other layouts, 5-8 track.

SPECIAL EQUIPMENT

SOLID STATE MOTOR CONTROLS, MODEM INTERFACE UNITS, TARRIFF J
INTERFACE UNITS, TEST EQUIPMENT, COMPUTER INTERFACE UNITS, DEC.
PDP8 and others. SILENCE COVERS AND CABINETS, TELEPRINTER TABLES,
SIGNALLING RECTIFIERS AND CONVERTORS, TAPE HOLDERS.

WW-101 FOR FURTHER DETAILS

COMMUNICATION ACCESSORIES & EQUIPMENT LIMITED

G.P.O. TYPE COMPONENTS FOR PROMPT DELIVERY

JACK PLUGS—201, 310, 316, 309, 404, 420, 609, 610, 1603 — 3201
JACK STRIPS—310, 320, 510, 520, 810
JACK SOCKETS—300, 500, 800, B3 and B6 mountings, 19, 84A and 95A
PATCH PANELS & RACKS—made to specifications
LAMPS, SWITCHBOARD NO. 2, BALLAST PO 11, LAMP STRIPS, 10-way PO 19, 20-way PO 17, Lamp Caps,
Holder No. 12
CORDS (PATCHING & SWITCHBOARD)—made to specifications
TERMINAL BLOCKS (DISTRIBUTION)—20-way up to 250-way
LOW PASS FILTERS—type 4B and PANELS, TELEGRAPH 71 (15 × 4B)
POLARISED TELEGRAPH RELAYS AND UNISELECTORS—various types and manufactures both P.O. and
miniature
LINE TRANSFORMERS/RETARDATION COILS—type 48A, 48H, 49H, 149H, 3/16, 3/216, 3/48A, 3/43A, 48J, etc.
FUSE & PROTECTOR MOUNTINGS—8064 A/B 4028, H15B, H40 and individual 1/2
COILS—39A, 40A, 40E, etc.
P.O.-TYPE KEYS—1000 and PLUNGER TYPES 228, 279, etc.
EQUIPMENT RACKS AND CONSOLES—made to specifications
RELAY ADJUSTING TOOLS, TOOL BAGS FOR MECHANICS, TENSION GAUGES, ARMATURE ADJUSTERS,
SPRING BENDERS ETC. VARIOUS SWITCHBOARD EQUIPMENT.

WW-102 FOR FURTHER DETAILS

MORSE EQUIPMENT LIMITED

The GNT Range of Automatic Morse Equipment is now manufactured in the U.K. and comprises complete equipment for Morse Training Schools and for Automatic Morse Transmission. Models available include:

KEYBOARD PERFORATORS for offline tape preparation
AUTOMATIC TAPE TRANSMITTERS with speeds up to 250 w.p.m.
MORSEINKERS specially designed for training, producing dots and dashes on tape
HEAVY DUTY MORSE KEYS
UNDULATORS for automatic record and W/T signals up to 300 w.p.m.
CODE CONVERTERS converting from 5-unit tape to Morse and vice versa
MORSE REPERFORATORS operating up to 200 w.p.m.
TONE GENERATORS and all Students' requirements
CREED, MORSE EQUIPMENT, PERFORATORS, REPERFORATORS, TRANSMITTERS, PRINTERS, MARCONI UG6 UNDULATORS, BUZZERS, ALDIS LAMPS, etc.

WW-103 FOR FURTHER DETAILS

77 AKEMAN STREET, TRING, HERTS., U.K.

Telephone: Tring 3476/8, STD: 0442-82 Telex 82362, Answerback: Batelcom Tring

MAINS TRANSFORMERS

SAFETY ISOLATING TRANSFORMERS

Primary 120/240 Volts. Secondary 120/240 Volts. Centre tapped with interwinding Screen.

VA (WATTS)	WEIGHT Lb.	SIZE CM.	TYPE No.	PRICE £	POST p
60	3½	9.9x7.7x8.6	149	2.86	38
100	5½	9.9x8.9x8.6	150	3.15	52
200	8	12.1x9.3x10.2	151	5.30	52
250	13½	12.1x11.8x10.2	152	7.05	65
350	15	14.0x10.8x11.8	153	9.40	80
500	19½	14.0x13.4x14.0	154	13.55	£1.20
1000	38	17.2x16.6x14.8	156	24.99	£1.20
2000	60	21.6x15.3x18.1	158	41.25	*
3000	85	23.5x17.8x19.7	159	64.54	*
6000	173	35.0x20.4x29.3	160	105.90	*

The above are also available cased with lead and socket. * On application.

MINIATURE & EQUIPMENT TRANSFORMERS

Pri. 240 Volts with interwinding Screen.

VA (WATTS)	WEIGHT Lb.	SIZE CM.	TYPE No.	PRICE £	POST p
3-0-3	200	2.8x2.6x2.0	238	1.12	10
0-6-0	500, 500	4.8x2.9x3.5	234	1.18	10
0-6-0	1000, 1000	6.1x5.8x4.8	212	1.28	22
0-9-9	100	3.9x2.6x2.9	13	63p	10
0-9-9	330, 330	4.8x2.9x3.5	235	1.28	10
0-8-9, 0-8-9	500, 500	6.1x5.4x4.8	207	1.70	22
0-8-9, 0-8-9	1000, 1000	7.0x6.4x6.1	208	2.30	30
15-0-15	40	2.8x2.6x2.0	240	1.28	10
0-15-0, 0-15	200, 200	4.8x2.9x3.5	236	1.28	10
0-20-0, 0-20	30	2.8x2.6x2.0	241	1.09	10
0-20-0, 0-20	150, 150	4.8x2.9x3.5	237	1.28	10
0-15-20, 0-15-20	500, 500	7.0x6.7x6.1	205	2.16	38
0-20-0, 0-20	300, 300	6.1x5.8x4.8	214	1.36	22
20-12-0-12-20	700 (DC)	11.0x8.1x6.1	221	1.21	30
0-15-20, 0-15-20	1000, 1000	8.3x7.7x7.0	206	3.10	38
0-15-27, 0-15-27	500, 500	8.3x7.0x7.0	203	2.38	38
0-15-27, 0-15-27	1000, 1000	8.9x7.7x7.7	204	2.40	38

AUTO TRANSFORMERS

TAPPED AT 114, 210, 240V.

VA (WATTS)	WEIGHT Lbs.	SIZE CM.	TYPE No.	PRICE £	POST p
20	1	5.8x5.1x4.5	113	1.00	22
75	2½	7.0x6.7x6.1	64	2.00	30

TAPPED AT 115, 200, 220, 240

VA (WATTS)	WEIGHT Lbs.	SIZE CM.	TYPE No.	PRICE £	POST p
150	3½	8.9x7.7x7.7	4	2.40	38
300	6½	9.9x9.6x8.6	66	4.70	52
500	12½	12.1x11.2x10.2	67	6.90	67
1000	19½	14.0x13.4x14.3	84	12.60	82
2000	32	17.2x16.6x14.0	95	24.00	£1.10
3000	40	21.6x13.4x18.1	73	32.60	£1.20

CASED AUTO TRANSFORMERS

220/240 VOLTS TO 115 VOLTS WITH LEAD AND 115 VOLT SOCKET

VA (WATTS)	WEIGHT Lb.	SIZE CM.	TYPE No.	PRICE £	POST p
20	1	8.0x5.1x6.4	113S	1.95	22
500	12	11.8x9.9x14.0	671S	9.46	67
1000	22½	13.7x11.5x25.4	841S	15.50	£1.00

LOW VOLTAGE TRANSFORMERS

PRIMARY 200/250 Volts. SECONDARY 12 and 12 Volts.

PRIMARY AMPS	WEIGHT Lb.	SIZE CM.	TYPE No.	PRICE £	POST p
0.5	0.25	4.8x2.9x3.5	111	1.00	22
1	0.5	6.1x5.8x4.8	213	1.23	22
2	1	7.0x6.4x6.1	71	1.60	22
4	2	8.3x7.7x7.0	18	2.25	38
6	3	8.9x8.0x7.7	70	2.70	42
8	4	9.9x8.9x8.6	108	3.00	52
10	5	9.9x9.6x8.6	72	3.55	52
12	6	9.9x10.2x8.6	116	4.50	52
16	8	12.1x9.9x10.2	17	5.50	52
20	10	14.0x9.6x11.8	115	6.95	67
30	15	14.0x12.1x11.8	187	12.90	97
40	20	14.0x14.7x11.8	232	18.30	£1.00
60	30	17.2x15.3x14	228	23.70	£1.10

30 VOLT TRANSFORMERS

PRIMARY 200/240. SECONDARY 12, 15, 20, 24, 30

PRIMARY AMPS	WEIGHT Lb.	SIZE CM.	TYPE No.	PRICE £	POST p
1	1½	6.1x5.8x4.8	112	1.20	22
1	2½	7.0x6.7x6.1	79	1.64	38
2	3	8.3x7.7x7.7	3	2.45	38
3	4½	9.9x8.3x8.6	20	3.00	40
4	6½	9.9x9.8x8.6	21	3.55	52
5	6½	12.1x8.6x10.2	51	4.40	52
6	8	12.1x9.3x10.2	117	5.28	52
8	12	12.1x11.8x10.2	88	6.80	67
10	13½	14.0x10.2x11.8	89	8.38	67

50 VOLT TRANSFORMERS


PRIMARY 200/240. SECONDARY 19, 25, 33, 40, 50

PRIMARY AMPS	WEIGHT Lb.	SIZE CM.	TYPE No.	PRICE £	POST p
1	1½	7.0x6.4x6.1	102	1.60	30
1	2½	8.3x7.4x7.0	103	1.35	38
2	5½	9.9x8.9x8.6	104	3.25	42
3	6½	9.9x10.2x8.6	105	4.40	52
4	10	12.1x10.5x10.2	106	5.48	52
6	12	14.0x10.2x11.8	107	8.65	67
8	18	14.0x12.7x11.8	118	11.27	97
10	25	17.2x12.7x14.0	119	14.15	97

60 VOLT TRANSFORMERS

PRIMARY 200/240. SECONDARY 24, 30, 40, 48, 60.

PRIMARY AMPS	WEIGHT Lb.	SIZE CM.	TYPE No.	PRICE £	POST p
1	2½	7.0x6.7x6.1	124	1.60	38
1	3½	8.3x7.7x7.7	126	2.25	38
2	6½	9.9x9.6x8.6	127	3.55	42
3	8½	12.1x9.9x10.2	125	5.40	52
4	13½	12.1x11.8x10.2	123	6.98	67
5	14	14.0x10.2x11.8	40	8.46	67
6	15½	14.0x12.1x11.8	120	9.20	82
8	25	14.0x14.7x11.8	121	11.60	£1.00
10	25	17.2x12.7x14.0	122	15.25	£1.00
12	29	17.2x14.0x14.0	189	29.62	£1.10

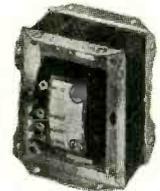

BRIDGE RECTIFIERS



ONE AMP	TWO AMP	FOUR AMP	SIX AMP
50 Volts	50 Volts	100 Volts	100 Volts
25p	35p	55p	65p
100 "	100 "	200 "	100 "
200 "	40p	400 "	70p
250 "	45p	600 "	80p
300 "	50p	800 "	90p
350 "	55p	1000 "	£1.00

PLEASE ADD 10% FOR VAT

A.S.P. LTD. BYRE HOUSE, No. 2 UNIT, WINCHEP, CANTERBURY, KENT

COLOMOR ELECTRONICS SALE

To clear our stores of surplus stock we are holding a sale of equipment and Components at give-away prices. It is impossible to list all the goods, the selection below is but a brief indication of items and prices. There is something for everyone to come and see, but hurry, many items are "one off" only.

- HEWLET PACKARD 5408 COUNTER £25—
- MARCONI OA1094 SPECTRUM ANALYSER £35—
- TF 144G £3—SIGNAL GENERATOR No. 1 £20—
- SIGNAL GENERATOR No. 2 £12—
- TF958VUM £12.50—TF 957 WATTMETER £10—
- AR88 £20—B 42 £15—P.C.R. £3.50—
- CR 100 £1—CT 160 VALVE TESTERS £15—
- TF 899 VmVM £1.50—SQUARE PULSE GENERATORS £7—
- B.F.'s £5—REG. H.T. POWER SUPPLIES £10—
- DM 2004 DVM £17—BERKELEY COUNTER £15—
- K/H PEN RECORDERS £7.50—
- THOUSANDS OF BRAND NEW METERS FROM 30p.
- LARGE METERS FROM 40p—
- COMPONENTS, SWITCHES, CONTROL BOXES, TESTERS, etc., etc., etc.

SALE COMMENCES 15th SEPTEMBER and will last a few weeks only. HOW TO GET THERE:— In the premises of Unigate Dairy Depot, entrance off Cromwell Road Extension (Cedars Rd.) towards London, first left (Sutton Lane North, W.4.) first entrance on left. Or write to:—

COLOMOR (ELECTRONICS) LTD.
170, Goldhawk Road, London W.12
01-743 0899

Newnes Radio Engineer's Pocket Book 14th Edition

Revised by H. W. Moorshead

A ready reference source for formulae, tables and definitions of electrical and electronic terms, including many mathematical tables. The book is very carefully indexed for quick and accurate selection of material.

1972 188 pp illustrated 0 408 00074 0 £1.20

Sound with Vision

Sound Techniques for Television and Film

E. G. M. Alkin

For the first time the methods developed by the BBC are here made available in book form for the benefit of television sound operators and production staff. The book discusses the problems of simultaneous production of sound and picture, giving practical instruction in methods of overcoming them. There are detailed discussions of operation equipment and trends which will be useful to designers and manufacturers of sound equipment.

1974 294 pp illustrated 0 408 70236 2 £6.00

Video Recording

Record and Replay Systems

Gordon White

This book describes the principles of video recording and discusses the various systems which are on the market or will soon make an appearance. Inevitably the book is technical, but it is designed so that people who have an interest in the subject should find no difficulty in understanding the principles, advantages and disadvantages of the various systems.

1972 216 pp illustrated 0 408 00085 6 £3.25

Obtainable through any bookseller or from

The Butterworth Group

88 Kingsway, London WC2B 6AB.
Trade counter: 4-5 Bell Yard, WC2.






AERO SERVICES LTD



D.C. STORAGE OSCILLOSCOPE TYPE C8-1

Made in U.S.S.R.

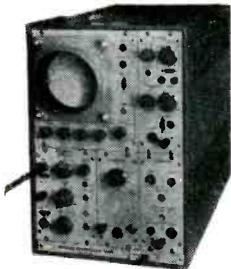

Differential Vertical Amplifier. Single shot, triggered or free-running time base. A.C. or D.C. coupling. Bandwidth: D.C. to 1MHz. Enhance or Normal Operation. Max. writing speed 4km/sec. Storage time: up to 1 week.

Price £240.00

Full details are contained in our Catalogue—see below.

ALL PRICES ARE EXCLUSIVE OF VALUE ADDED TAX. WHEN ORDERING BY POST PLEASE ADD £0.124 IN £ FOR HANDLING AND POSTAGE (SUBJECT TO A MINIMUM CHARGE £0.15) AND 10% OF THE TOTAL VALUE FOR VAT.

WIDE BAND OSCILLOSCOPE

TYPE C1-54

Made in U.S.S.R.



Bandwidth: D.C. to 20MHz. Max. sensitivity: 1mm/mV. Internal Amplitude Calibrator.

Crystal Controlled Time Marker Beam Locator. Push-button controlled single shot operation. Frequencies up to 30MHz can be displayed using direct-to-tube connections.

Price £140.00

NEW MULTIMETER TYPE U4323


Made in U.S.S.R.



Sensitivity 20000Ω/V. 23-range instrument providing: D.C. voltage: 0.5-1000V. A.C. voltage: 2.5-1000V. D.C. current: 0.05-500mA. A.C. current: 0.05mA. Resistance: up to 1MΩ. Multimeter contains an oscillator providing Audio Output of 1KHz and I.P. Output of 465KHz.

Price £7.00

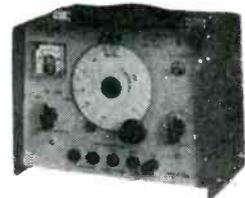TRANSISTORIZED AUDIO SINE-WAVE OSCILLATOR TYPE G3-36



Transistorized Audio R-C Oscillator covering a range of 20Hz to 200KHz in four decade bands. Calibration accuracy 3%. Four separate output sockets giving attenuation ratios of 1, 10, 100 and 1000. Microammeter output indicator. Output voltage 5V into 600Ω. £19.75

HIGH VOLTAGE NPN POWER TRANSISTORS TYPE BU105

For T.V. Line Deflection Circuit. V_{CEO} 750V D.C. or 1500V peak. £1.60

MINIATURE WIRE ENDED SILICON RECTIFIERS

1N4002	100 p.i.v.	1A	0.07
1N4004	400 p.i.v.	1A	0.08
1N4006	800 p.i.v.	1A	0.12

0A2	0.40	5Z4G	0.45	6DJ8	2.40
0A3	0.48	6X0L2	0.45	6DL6	0.60
0B2	0.40	6AB1	0.45	6DQ5	1.45
0B3	0.70	6AB5	1.00	6DQ6B	0.80
0C2	1.00	6AF1A	0.65	6DS4	1.35
0C3	0.40	6AG5	0.25	6DT6	0.60
0D3	0.40	6AG7	0.45	6EA8	0.70
0Z4	0.45	6AH8	0.90	6EN6	0.70
1A3	0.48	6AK5	0.40	6EP1	0.75
1A6GT	0.48	6AL5	0.25	6FP4	0.75
1A7GT	0.60	6AM5	0.50	6F6GB	0.60
1B6GT	0.48	6AM6	0.37	6F7	1.00
1C6GT	0.48	6AN5	1.80	6F8G	0.55
1H5GT	0.60	6AN8	0.65	6F11	0.50
1L4	0.28	6AQ5	0.25	6F13	0.50
1N6GT	0.60	6AQ6	0.70	6F14	0.40
1R5	0.45	6AR5	0.80	6F15	0.65
1R4	0.30	6AR6	0.68	6F17	1.00
1R5	0.30	6AS6	0.50	6F18	0.50
1T4	0.30	6AS7G	0.55	6P24	0.80
1U4	0.60	6AU5GT	0.60	6P25	1.00
1X2B	0.60	6AU6	1.30	6P28	0.70
2AP1	3.00	6AU8	0.70	6F32	0.80
2C26A	0.60	6AV6	0.45	6P33	3.25
2C24	0.55	6AV8	0.45	6P35	3.25
2C39	0.50	6AV4S	0.55	6P36	0.40
2C40	0.50	6B4G	1.00	6P37	0.40
2C51	0.50	6B7	0.80	6J4	0.40
2D21	0.45	6B9G	0.30	6J5GT	0.45
2E26	2.50	6BA6	0.28	6J6	0.30
3K25	8.00	6BE9	0.35	6J7	0.45
3A3	0.75	6B7S	1.50	6K6GT	0.75
3A4	0.50	6B6G	0.70	6K7	0.45
3B26	3.50	6BH6	0.75	6K8G	0.50
3BP1	3.50	6B6	0.55	6K8GT	0.50
3C45	5.00	6BR4B	1.25	6K23	0.75
3D6	0.48	6B7A	0.75	6K23	0.75
3D21A	4.00	6B7A	0.55	6L4GT	0.55
3E29	4.50	6BR7	1.00	6L18	0.50
3Q4	0.60	6BR8	0.80	6LD20	0.50
3Q6GT	0.55	6B87	1.35	6N7GT	0.55
3R4	0.40	6BV6	0.80	6Q7	0.50
3V4	0.70	6B7G	0.60	6R7G	0.60
4-125	9.00	6C26	0.45	6S47	0.45
4-250A	15.00	6C3	0.35	6SCT	0.35
4-400A	17.50	6C5GT	0.55	6P5	0.85
4CX1250B	13.00	6C8G	1.50	6R7	0.60
4X150A	9.00	6CB5A	0.50	6R7A	0.45
5CP1	5.00	6C6	0.50	6S17	0.50
5FP7	4.00	6C7A	1.00	6S17GT	0.48
5R4G	0.30	6C8	0.50	6S7	0.50
5Y3GT	0.45	6D6	0.40	6S7G	0.50
5Z3	0.75	6D6	0.55	6V6GT	0.50

FULLY GUARANTEED



FIRST QUALITY VALVES

6W4GT	0.70	12BY7	2	30F5	1.00	1500C	2	A2426	8.00	E88CC	2.75	ECF804	2	EL34	0.50	HL94	0.60
6W6GT	0.80	12CU6	0.80	30FL1	0.80	310A	1.75	A2500	3.00	E90F	1.50	EL36	1.65	EL38	0.50	KT8	2.50
6X5GT	0.45	12F5GT	0.45	30FL12	1.10	311A	2.00	AF3P8	0.25	E90P	1.50	ECH21	0.60	EL41	0.75	KT30C	1.00
6X8	0.55	12H6	0.35	30FL13	0.50	328A	2.00	AW6	0.60	E180F	1.00	ECH35	1.00	EL81	0.55	KT36	1.20
6Y6G	0.80	12J5GT	0.35	30FL14	0.90	329A	2.00	AZ1	0.60	E130L	5.00	ECH42	0.75	EL82	0.55	KT44	0.70
7B7	0.75	12K3	1.00	30L15	0.95	705A	4.50	AZ11	0.55	E180F	1.00	ECH81	0.30	EL83	0.50	KT45	2.00
7C7	0.70	12L6	0.65	30L17	0.95	715C	7.50	AZ12	0.60	E280F	2.85	ECH83	0.45	EL84	0.28	KT66	2.50
7D6	0.75	12M6	0.60	30P12	0.80	733A	7.00	AZ21	0.50	E910F	2.90	ECH84	0.45	EL85	0.43	KT77	1.00
7E6	0.75	12N6	0.60	30P13	0.80	801A	0.75	AZ31	0.55	EABC80	0.50	ECL80	0.53	EL86	0.40	KT88	2.90
7F6	0.75	12P6	0.60	30P19	0.95	807	0.50	AZ41	0.60	0.58	ECL81	0.55	EL85	0.40	ME1400	0.40	
7G6	0.75	12Q6	0.60	30PL1	0.95	811A	2.00	BT5	10.00	EAP42	0.60	ECL82	0.35	EL360	1.25	MT17	1.30
7H6	0.75	12R6	0.60	30PL13	1.10	812A	3.50	BT19	10.00	EAF801	0.50	ECL83	0.70	EL304	0.70	MH4	0.75
7J6	0.75	12S6	0.60	30PL14	1.10	813	4.50	BT36	10.00	0.50	ECL84	0.55	EL821	1.40	MH41	0.75	
7K6	0.75	12T6	0.60	30PL15	1.10	832A	3.50	CIK	7.50	0.50	ECL85	0.40	EL822	1.60	MH4	0.75	
7L6	0.75	12U6	0.60	35A3	0.65	833A	17.00	CJ1	7.60	0.65	EBC41	0.65	ELL80	0.85	MI4	0.75	
7M6	0.75	12V6	0.60	35A5	0.65	826A	1.00	CBL1	0.90	EBC81	0.33	ECL1800	0.75	EM71	0.80	ML6	0.60
7N6	0.75	12W6	0.60	35B5	0.65	872A	5.50	CBL3	1.20	EBF80	0.40	EM80	0.45	MT17	7.00	PF88	0.70
7O6	0.75	12X6	0.60	35C5	0.60	884	0.80	CC3L	0.25	EBF83	0.40	EM83	0.50	MT37	10.00	PF818	1.00
7P6	0.75	12Y6	0.60	35D5	0.75	889RA	50.00	CC3	1.50	EBF89	0.32	EF12	0.90	EM84	0.35	MU1214	0.75
7Q6	0.75	12Z6	0.60	35W4	0.50	2050	1.00	CY1	0.50	EBF81	1.00	EF36	0.60	EM85	1.00	PL38	0.40
7R6	0.75	12Z6	0.60	35Z3	0.75	5551A	18.00	CY31	0.50	EBL21	0.80	EF37A	1.00	EM87	0.70	N78	1.80
7S6	0.75	12Z6	0.60	35Z4G	0.40	5552A	24.00	DAF96	0.50	EBL31	1.50	EF39	0.75	EY31	0.40	NSP1	6.00
7T6	0.75	12Z6	0.60	35Z4GT	0.70	5553A	47.00	DET22	8.00	EC80	2.85	EF40	0.55	EY81	0.40	NSP2	7.50
7U6	0.75	12Z6	0.60	38A3	0.40	3557	7.00	DET23	8.00	EC81	1.30	EF41	0.65	EY83	0.55	OB1	7.00
7V6	0.75	12Z6	0.60	40K66A	0.55	5559	9.00	DET24	8.00	EC86	0.60	EF42	0.70	EY84	0.70	OM3	7.00
7W6	0.75	12Z6	0.60	50A5	1.50	5651	0.60	DF92	0.28	EC92	0.45	EF98	0.25	EY87	0.43	ORP12	0.50
7X6	0.75	12Z6	0.60	50B5	0.55	5654	0.60	DF96	0.50	EC93A	0.50	EF83	1.00	EY88	0.43	ORP60	0.60
7Y6	0.75	12Z6	0.60	50C5	0.60	5670	0.75	DG75	12.00	EC98	0.40	EF85	0.35	EZ40	0.50	ORP90	1.10
7Z6	0.75	12Z6	0.60	50CD6G	0.75	63	0.85	DH81	0.70	EC98C	0.33	EF89	0.28	EZ80	0.28	ORP93	1.10
8A6	1.20	6080	1.75	DH101	0.70	6146	2.00	DK40	0.35	EC98A	0.30	EF91	0.37	EZ81	0.29	PABC80	0.40
8B6	1.10	50L6GT	0.60	DK91	0.45	6146B	3.00	DK91	0.45	EC98S	0.40	EF92	0.35	GN4	1.50	PC86	0.60
8C6	0.50	52K0	0.45	DK96	0.60	6196	3.00	DK96	0.60	EC98E	0.40	EF94	0.30	GU50	5.00	PC88	0.60
8D6	0.50	75C1	0.50	DL96	0.55	7025	0.80	DL96	0.55	EC98F	0.50	EF95	0.40	GXU50	5.00	PC96	0.45
8E6	0.50	80	0.80	DM70	1.00	7189	1.00	DL810	3.20	EC98G	0.65	EF96	0.25	GXU51	6.00	PC97	0.50
8F6	0.50	7360	0.80	DM70	1.00	7360	0.80	DM70	1.00	EC98H	1.00	EF97	0.65	GY501	0.70	PC90	0.48
8G6	0.50	751A	1.00	DMK160	0.60	85A2	0.85	751A	2.00	EC98I	0.35	EF98	0.25	GZ30	0.45	PC98A	0.40
8H6	0.50	90A2	2.40	7591A	1.00	90A2	2.40	7591A	1.00	EC98J	0.35	EF183	0.35	GZ32	0.50	PC98S	0.40
8I6	0.50	90A2	2.40	7895	1.50	90A2	2.40	7895	1.50	EC98K	0.70	EF184	0.35	GZ34	0.65	PC98E	0.55
8J6	0.50	90C1	0.75	8136	0.60	90C1	0.75	8136	0.60	EC98L	0.35	EF184	0.35	GZ34	0.65	PC98F	0.55
8K6	0.50	90C2	0.40	90C3	0.40	90C3	0.40	90C3	0.40	EC98M	0.35	EF184	0.35	GZ34	0.65	PC98G	0.55
8L6	0.50	90C4	0.40	90C5	0.40	90C5	0.40	90C5	0.40	EC98N	0.35	EF184	0.35	GZ34	0.65	PC98H	0.55
8M6	0.50	90C6	0.40	90C7	0.40	90C7	0.40	90C7	0.40	EC98O	0.35	EF184	0.35	GZ34	0.65	PC98I	0.55
8N6	0.50	90C8	0.40	90C9	0.40	90C9	0.40	90C9	0.40	EC98P	0.35	EF184	0.35	GZ34	0.65	PC98J	0.55
8O6	0.50	90C10	0.40	90C11	0.40	90C11	0.40	90C11	0.40	EC98Q	0.35	EF184	0.35	GZ34	0.65	PC98K	0.55
8P6	0.50	90C12	0.40	90C13	0.40	90C13	0.40	90C13									

Europe at your fingertips

This is what you will have at your fingertips by purchasing the Kompass community package. All Kompass registers have the same format with extensive indexing and classification of up to 40,000 products and services with multilingual indices—every KOMPASS has an ENGLISH index.

To purchase the 16 volumes relating to the community would cost you £110.50 but as an E.E.C. package we are offering all volumes, if ordered at the same time, at a pre-publication discount of 18% . . . £90.00 post free.



KOMPASS PUBLISHERS LIMITED
RAC House, Lansdowne Road, Croydon CR9 2HE

Registered Address Registered in England No 329824

PLEASE SUPPLY:

KOMPASS BELGIUM—£11.00 DENMARK—£11.00

FRANCE—£16.50 ITALY—£16.50 HOLLAND—£11.00

U.K.—(Pre-Pub £15.75 Pub £18.75 CBI £9.75)

W. GERMANY—£25.75 E.E.C. PACKAGE—£90.00

Name

Address

.....

.....



MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—2 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 6 way, 1 pole, 12 way. All at 25p each.

TOGGLE SWITCHES

Metal, all standard types with metal dolly 240v, 3 amp: 8P, ST 17p 8P, DT, 22p DP, ST 22p DF, DT. 22p less 10% for ten of same type.

ROCKER SWITCH

13 amp self-fixing into an oblong hole. Size approximately 1 1/2 in. x 1/2 in., 5p each, 10 for 52p.

SLIDE SWITCHES

Slide Switch, 2 pole change over panel mounting by two B.A. screws. Size approx. 1 1/2 x 1 1/2 rated 250v lamp. 8p each, 10 for 72p.

Sub Miniature Slide Switch, DPDT 10mm (1/2 approx.) between fixing centres. 14p each or 10 for 126p.

DOUBLE LEAF CONTACT

Very slight pressure closes both contacts. 8p each, 10 for 72p. Plastic push-rod suitable for operating. 6p each, 54p for 10.

TELEPHONES

Complete as illustrated. Save your lines, time and temper simply by putting in some telephones. Ex. G.P.O. not new—but guaranteed in good condition and serviceable. Supplied with diagram and instructions showing how to connect. 3 types available as illustrated less internal bell 1.25 each. Ditto with bell but less dial 1.25 each. As illustrated with dial and bell 1.50 each.

Post etc. 50p each.

1 REV. PER MINUTE MOTOR WITH GEAR-BOX

Made by the famous Chamberlain & Hookham Ltd. These could be made to drive clock or similar. Really robust reliable unit Price 90p.

MINIATURE SEALED RELAY American made. Our Ref. No. REL A1. Measures only 1/2 wide x 1/2 thick and 1/2 high and it's a double change over, we don't know the contact rating but estimate this at 3/5 amps. The coil resistance is 600 ohms and 9-10 ohms. Ideal for models and miniaturised equipment. It's a plug in relay but we supply complete with base. Price 25p including base.

METAL CHASSIS

14 gauge sheet steel—size approx. 7 x 3 1/2 x 1 1/2 deep. Cadmium plated punched in the centre to take 3 P.O. 3000 type relays. There is also a removable cover over this section measuring 4 1/2 long x 3 1/2 x 2 1/2. The chassis also has a few holes and could take a small transformer and/or valve holders also some 1/2 holes for controls, pots etc. This is an ideal chassis for making up a relay unit or similar. There are ex-equipment but in excellent condition and may have a few resistors etc. still attached. Price 40p each.

12V CAR BLOWERS

Units made by Delco. 6 bladed 5" dia. fan inside heavy duty cylinder. These have really powerful series wound motors giving a terrific air flow suitable for ventilating or heating a car, boat, caravan, etc. Price 22-20 plus 40p post and insurance. (Note these are intended for 12V D.C. but can be run from A.C. up to 30V. The higher the voltage the more the air flow.)



DRILL CONTROLLER

New 1kW model. Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. Price 22-15 plus 13p post and insurance. Made up model also available 22-48 plus 13p p. & p.

BAKELITE INSTRUMENT CASE

Size approx. 6 1/2 x 3 1/2 x 2 1/2 deep with brass inserts in four corners and bakelite panel. This is a very strong case suitable to house instruments and special rigs, etc. Price 50p each. Paxlids 11p extra.

ISA ELECTRICAL PROGRAMMER

Learn in your sleep: Have radio playing and kettle boiling as you awake—switch on lights to ward off intruders—have warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp. on/off switch. Switch on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price 22-15 + 20p p. & p. or with glass front chrome bezel 83p extra.

WATERPROOF HEATING ELEMENT

13 yards length 35W. Self-regulating temperature control. 55p free.

HIGH ACCURACY THERMOSTAT

Uses differential comparator I.C. with thermistor as probe. Designer claims temperature control to within 1/7th of a degree. Complete kit with power pack 22-15.

TREASURE TRACER


Complete kit (except wooden battens) to make the metal detector as the circuit in Practical Wireless August issue. 23-85 plus 20p post and insurance.

AUTO TRANSFORMER

Primary 220-240v. Secondary 110-120v. Well built and varnish impregnated. 250 watt intermittent rating. Size approx. 3 1/2 x 3 in. 11-10 plus 20p post and insurance.

CENTRIFUGAL BLOWER

Miniature driven blower centrifugal type blower unit by Woods, powerful but specially built for quiet running—driven by cushioned induction motor with specially built low noise bearings. Overall size of blower is approx. 4 1/2 x 4 1/2 x 4. When mounted by its flange air is blown into the equipment but to suck air out mount it from the centre using a clamp. Ideal for cooling electrical equipment, or fitting into a cooker hood, film drying cabinet or for removing flux smoke when soldering etc., etc. A real bargain at 22-25.

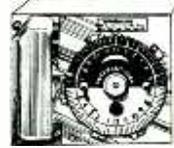

Made by Smiths these are A.C. mains operated. NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. 2 completely adjustable time periods per 24 hours, 5 amp changeover contacts will switch circuit on or off during these periods. 22-75 post and ins., 23p. Additional time contacts 55p pair.

ELECTRIC TIME SWITCH

MICROSWITCHES Button Operated

Ref. MS AU1. Made by Burgess, 250v, 15 amps, single pole, off/on, that is they are normally off until depressed. Price 17p each.

Ref. MS AU2. Made by Honeywell, 250v, 10 amp, change over. Price 25p each.

Ref. MS AU3. Ditto but 5 amp. Price 10p each, ex-equipment.

Ref. MS S1. Made by Burgess 15 amp on/off that is they are on until button is depressed. Price 17p each.

Sub Miniature Ref. MS S4. Made by Burgess, their type no V4 T6. These measure only 1/2 x 1/2 x 1/2 thick—have change contacts and tag compound. Price 32p each.

Ref. MS S3 two of V4 T6 mounted in light frame with roller for operating 75p each.

Lever Operated Ref. MS AU7. Made by Honeywell. Lever length approx. 2 1/2. 15 amp 250v change over. Price 28p each.

Ref. MS AU8. Made by Honeywell. This is an extra sensitive switch with a 4 lever. 10 amp 250v change over. Price 33p each.

Ref. MS S2. Made by reputable French company. 250v 5 amp off/on. Price 12p each.

Ref. MS S3 Made by Honeywell lever is a looped wire. 250v, 15 amp change-over. 35p each.

Ultra Sensitive Ref. MS D1. 1 amp change over at 230v. This has a wire lever attached and is so sensitive it will trigger with its own weight. Price 44p each.

Panel Mounted All made by Honeywell. These are 250v 10 amp change over microswitches fitted into a bracket with spring plunger and are operated by pushing a dished black knob. Mounting is through 1/2 hole and two locking nuts.

Ref. MS AU4. Single change over switch. Price 33p each.

Ref. MS AU5. Two bank, that is 2 change over 10 amp microswitches, both operated by the single plunger. Price 44p each.

Ref. MS AU6. Three bank, that is 3 change over microswitches all operated by one plunger. Price 55p each.

All subject to quantity discounts:—10-49=10%, 50-99=15%, 100-up=20%.

THRISTOR LIGHT DIMMER

For any lamp up to 250 watt. Mounted on switch plate to fit in place of standard switch. Virtually no radio interference. Price 22-95. Industrial model 5A 23-30.

10 AMP DIMMER CONTROL

For the control of lighting on stage or in a studio or for control of portable equipment in workshops, etc. This has two 13 amp socket outlets each is controlled by a 5 amp solid state regulator. The overall length is 1 1/2 in., width 3/4 in. and depth 1 1/4 in. In the end is fitted a master On/Off switch indicator, lamp and fuse. Price 22-25.

HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting animated and signs, Signalling, etc. Price from makers probably over 10 each. Special snip price 26-33 plus 25p post and insurance. Don't miss this terrific bargain.

TANGENTIAL HEATER UNIT

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters costing 2.15 and more. We have a few only Complies motor, impeller, 2kW, element and 1kW, element allowing switching 1, 2 and 2kW. and with thermal safety cut-out. Can be fitted into any metal case or cabinet. Only needs control switch. 23-85, 2kW. 21kW as above except 2kW. 22-75 Don't miss this. Control Switch 44p, plus VAT P. & P. 40p.

30KV EHT UNIT

This unit is self contained and on wheels. It stands approx. 6 ft high and 3 ft square. On the front panel is a Variac, Voltmeter, a 60 second timer as well as the normal overload trip on/off switch and cut outs, etc. The transformer itself is oil filled and rated at 7 KV A 30KV. The variac is in the primary so all voltages up to 35 KV are available. We believe the normal use for such a unit would be as a break down and flash tester. 1 only—not new but in good order. Price 289.

HORSTMANN "TIME & SET" SWITCH

(A 30 Amp Switch) Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost on period of up to 3 hours. Equally suitable to control processing. Regular price probably around 45. Special snip price 21-65. Post and ins. 23p.

SPLIT MOTOR

200-250v. Induction Motor, driving a carter gear box with 1 1/2 in. o output drive shaft running at 5 revs. per minute. Intended for roasting chickens, also suitable for driving models, windmills, coloured disc lighting effect, etc., etc. 22-05 plus 20p post and insurance.

DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 6 feet of heavy cable. Wired up ready to work. 22-48 plus 25p P. & P.

MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied. Model 1153 500mW power output 72p. Model 1172 750mW power output 84p. Model EP9000 4 watt power output 11-60. EP9001 twin channel or stereo pre amp. 11-99. 10% discount if 10 or more ordered.

WALL THERMOSTATS

This Month's Snip. Made by the famous Smiths Instrument Co. called Coloustrat. Wall mounting in a handsome plastic case. (Cream and beige) Adjustable by slider (lockable) may be set to control temperatures from around freezing through to 50°C. The slide panel is engraved and indicates (frost) (warm) (very warm) etc. The thermostat will control heaters etc. up to 10 amp at normal mains voltage and is ideal for living room, bedroom and greenhouse etc. Price 21-65. Don't miss this.

SPRING RETURN WAFER SWITCH

As used in intercom and other similar equipment a two wafer 8 pole 3 way switch, spring return from centre position when turned clockwise and permanent off or on when turned anti-clockwise. Price 55p each.

A.C. BUZZERS

12v. Fix these into a box which will resonate and they will give a loud piercing note. Suitable for alarms or signal. 33p each.

PUSH ON TAG CONNECTORS

These are being increasingly used on cars and domestic appliances. 2 sizes prevail, the most popular being for 1/2 tag. We offer these at attractive prices. 10 for 10p... 50 for 40p... 100 for 70p and 1,000 for 25p.

WALL THERMOSTATS

This Month's Snip. Made by the famous Smiths Instrument Co. called Coloustrat. Wall mounting in a handsome plastic case. (Cream and beige) Adjustable by slider (lockable) may be set to control temperatures from around freezing through to 50°C. The slide panel is engraved and indicates (frost) (warm) (very warm) etc. The thermostat will control heaters etc. up to 10 amp at normal mains voltage and is ideal for living room, bedroom and greenhouse etc. Price 21-65. Don't miss this.

AUTO TRANSFORMER

Primary 220-240v. Secondary 110-120v. Well built and varnish impregnated. 250 watt intermittent rating. Size approx. 3 1/2 x 3 in. 11-10 plus 20p post and insurance.



CAR PANEL SWITCH

Our Ref. No. 801. Arco made. Has a flat ended toggle black and chrome finish. Rated 2A. at 250v. and is double pole on/off. Listed at 40p. Our price 22p each.

CAR PANEL AUTO SWITCH

Ref. No. 803. Again a flat ended toggle. Made by Arrow. A 3 position double pole change over switch centre off for auto serials, reversing motors etc. 30p each.

6V D.C. POWER MOTOR MADE BY REDUND

For driving a bilge pump and similar applications. This motor we understand develops on 1/4 H.P. It is extremely powerful and although rated at 6v, this operates up to 12v. for short periods with very much increased power, (probably at least 1/2 H.P.) We understand that from the makers they cost over 45. At 22-20 each plus 25p post on one and then 15p each.

8 AMP VARIACS

These are variable voltage transformers. British made by the famous Zenith Co. Fully enclosed for bench use and fitted with calibrated scale and control knob. Zenith model No 100 M. 220-240v. A.C. output 0-240v. up to 8 amps. This model is listed at over 20. We have a limited quantity only, absolutely brand new, still in maker's cartons, offered to you at 21-75 each plus 1/4 carriage and insurance up to 400 miles.

MOTOR GENERATOR

Made for Admiralty. 24 volt D.C. input, 250v. 50 cps. output. Admiralty rating 80 watts but we have tested this to 50% overload voltage regulated so suitable to operate TV or instrument. In case with metal cover controls on front include voltmeter. Unused. Probably cost 200 each to make. Our price only 22-25 each plus carriage 24 up to 200 miles, 24 up to 400 miles.

MULLARD THRISTOR TRIGGER MODULE MY 5001

This produces pulses for phase control triggering, it has two isolated outputs, so one thyristor or two thyristors (in separate arms of bridge) may be controlled by one module. The timing circuit is synchronised to the mains frequency and control is by an external resistor or from a potentiometer or current source. Provision is made for feedback where automatic control is required. Price 24-95 each or for 10 245-00.

9V GRAMOPHONE UNIT

Battery operated on unit plate 2 Speed auto-stop. Price 22-50 plus 40p post and insurance.

BUY TIME SLOT METER

Made by Sangamo Weston. 3 types, one for each coin 24p, 5p or 10p. Price 21-75 each plus 25p post and ins.

4 STATION TRANSISTORISED INTERCOM

Solid State three transistor printed ckt. mater and tree sub station push button/press talk system. 200mW output, complete with installation accessories and 8v. Ever-ready power pack approx. 3 x 1 1/2 x 4 in. Price 28-50 plus 20p.

PHOTO ELECTRIC KIT

Contains photo cell, relay, transistor and all parts to make light operated switch. 21-75 plus 20p post and ins.

AC/DC MILLIAMMETERS 3 RANGE

Moving iron mirror scale laboratory instalate. Ranges from 10 to 100mA by selection switch (coil resistance marked) size 7 1/2 x 5 x 3 1/4 in. type 3599/1. Price 26-60.

GALVOMETER 7-0-7 UA F.S.D.

Moving coil precision laboratory instrument of extremely high sensitivity (3 x 10-7 A per division), size approx. 6 1/2 x 2 1/2 in. Price 27-50.

ACOS. 'G' METERS

For use with transducers and accelerometers. These are precision instruments they measure 'g' in three steps 0-10, 0-100 and 0-1000 directly on a large clear meter scale 0-1. Two models available:—Standard model (ID00L) price 212 and Auto cutout model (ID00L) which has a built in circuit with relay to trip the external circuit (trip level is adjustable by a control which is virtually linear with the meter scale). The trip load may be up to 2a. Once the circuit has been tripped it can be restored by a reset button. Price of this model is 218.

VOLTAGE CHANGING TRANSFORMERS MADE BY PARMEKO

Upright mounting, fully shrouded and with terminal blocks for input and output. For changing mains voltage, ideal for working low voltage equipment from 230/240 mains and for increasing voltage due to losses in long leads. Voltage up or down between 190-250v. 250 watt. Price 21-65 plus 30p post etc.

DOOR OPENING OR PLATFORM ROTATING MOTORS

Very powerful motors estimated rating at 1/4 H.P. Reversible with gearbox and 'V' belt drive wheel of 7" diameter. These are by a French maker using trade name LUXOR and name plated Moteur Asynchrone. Capacitor start but with 6 connections. At the time of writing this we haven't a connection diagram and if any reader has met this motor before and can tell us how to connect and anything about it would be obliged. Price of motor which weighs approx. 15 lbs. is 210.

SPRING RETURN WAFER SWITCH

As used in intercom and other similar equipment a two wafer 8 pole 3 way switch, spring return from centre position when turned clockwise and permanent off or on when turned anti-clockwise. Price 55p each.

A.C. BUZZERS

12v. Fix these into a box which will resonate and they will give a loud piercing note. Suitable for alarms or signal. 33p each.

PUSH ON TAG CONNECTORS

These are being increasingly used on cars and domestic appliances. 2 sizes prevail, the most popular being for 1/2 tag. We offer these at attractive prices. 10 for 10p... 50 for 40p... 100 for 70p and 1,000 for 25p.


WALL THERMOSTATS

This Month's Snip. Made by the famous Smiths Instrument Co. called Coloustrat. Wall mounting in a handsome plastic case. (Cream and beige) Adjustable by slider (lockable) may be set to control temperatures from around freezing through to 50°C. The slide panel is engraved and indicates (frost) (warm) (very warm) etc. The thermostat will control heaters etc. up to 10 amp at normal mains voltage and is ideal for living room, bedroom and greenhouse etc. Price 21-65. Don't miss this.

J. BULL (ELECTRICAL) LTD. (Dept. W.W.) 7, Park Street, Croydon, CR0 1YD Callers to 102/3, Tamworth Road, Croydon



100 WATTS!

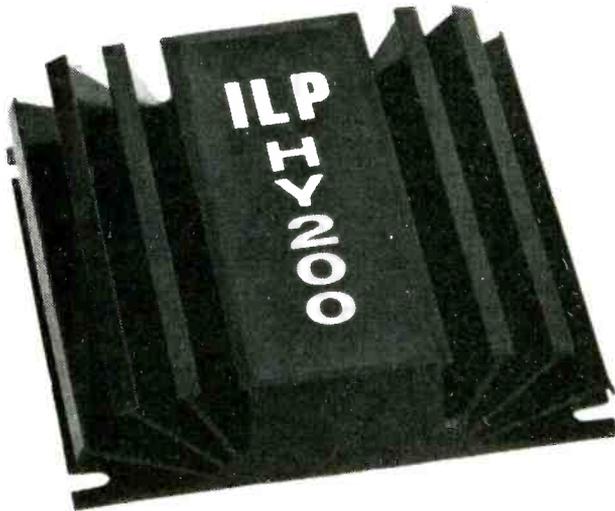

- ★ NO EXTERNAL COMPONENTS
- ★ MECHANICALLY & ELECTRICALLY ROBUST
- ★ INTEGRAL HEATSINK
- ★ HERMETICALLY SEALED UNIT
- ★ ATTRACTIVE APPEARANCE
- ★ LOW COST
- ★ BRITISH BUILT
- ★ 100 x 105 x 25mm

With the development of the HY200, ILP bring you the first COMPLETE Hybrid Power Amplifier.

COMPLETE: because the HY200 uses no external components!

COMPLETE: because the HY200 is its own heatsink!

By the use of integrated circuit technique, using 27 transistors, the HY200 achieves total component integration. The use of specially developed high thermally conductive alloy and encapsulant is responsible for its compact size and robust nature.

The module is protected by the generous design of the output circuit, incorporating 25amp transistors. A fuse in the speaker line completes protection.

Only 5 connections are provided, input, output, power lines and earth.

Output Power: 100 watts RMS; 200 watts peak music power into 8Ω

Input Impedance: $10K\Omega$

Input Sensitivity: 0Db (0.775volt RMS)

Load Impedance: 4- 16Ω

Total Harmonic Distortion: less than 0.1% at 100 watts typically 0.05%

Signal: Noise: Better than 75Db relative to 100 watts

Frequency response: 10Hz-50KHz ± 1 Db

Supply Voltage: ± 45 volts

APPLICATIONS: P.A., Disco, Groups, Hi-Fi, Industrial.

PRICE: £14.90 inc. VAT & P & P

Trade applications welcomed

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218



I.L.P. (Electronics) Ltd

SECOND GENERATION 25 WATT HYBRID



A brand new hybrid fabrication technique, recently perfected in our laboratories, has enabled us to achieve our latest range of completely integrated devices.

We have now finally reduced the modular amplifier to a simple input/output device requiring only the addition of a basic unstabilized (split line) power supply.

The HY50 takes medium power modules to their logical conclusion by incorporating with it a heatsink, which is designed in special high conductivity alloy, sufficient for normal audio use without additional chassis sinking. All this without significantly increasing the size of the module comparable in size to a packet of 'King-size' cigarettes.

Consistent with modern thinking a triple rated output circuit with a load fuse allows for peak transient response without distortion but ensures the necessary protection.

SPEC.

OUTPUT POWER: 25watts RMS, 50watts peak music power.
LOAD IMPEDANCE: 4-16Ω into 8Ω.
INPUT SENSITIVITY: 0db (0.775volts RMS).
INPUT IMPEDANCE: 47KΩ.
TOTAL HARMONIC DISTORTION: Less than 0.1% at 25watts typically 0.05 better than 75db.
SIGNAL/NOISE RATIO: 10Hz-50 KHz ± 1db
FREQUENCY RESPONSE: ± 25volts.
SUPPLY VOLTAGE: 105x50x25mm.
SIZE:

Price £5.40 mono £10.80 stereo.
Price inclusive of VAT & P & P.

NEW HY5 PRE-AMPLIFIER

Unchallenged for two years, the HY5, our unique multifunction preamplifier/tone hybrid, has been brought into line with the advancements in our power hybrids.

Like the HY50, the new HY5 has no external components & has been redesigned to run off a split power line with improvements in signal/noise, overload capability & reduced distortion. The output has been increased to match the power module (0db), and to share the same power supply.

Overall size is reduced by the use of a new thin film circuitry while the device still retains all the functions of the earlier device.

When combined with the HY50 & power supply only potentiometers are required to complete a simple mono amplifier with input & output facilities expected to be found on Hi-Fi amplifiers.

The combination of two HY5's two HY50's sharing a common power supply (PSU50) are linked by a balance control to form a complete stereo system.

INPUTS

Magnetic Pick-up 3mV (within 1db RIAA curve)
 Ceramic Pick-up up to 3mV.
 Microphone 10mV.
 Tuner 250mV.
 Auxiliary 3-100mV.
 Input impedance 47kΩ 1kHz

OUTPUTS

Tape 100mV.
 Main output. 0db (0.775volts).

ACTIVE TONE CONTROLS

Treble ± 12db at 10kHz
 Bass ± 12db at 100Hz

OVERLOAD CAPABILITY (equalization stage) 40db on most sensitive input.

OUTPUT NOISE LEVEL (below 10mV magnetic input) 68db.


DISTORTION 0.05% at 1kHz.

SUPPLY VOLTAGE ± 16-25volts.

SUPPLY CURRENT 15mA.

Price £4.51 mono £9.02 stereo

Price inclusive of VAT & P & P.

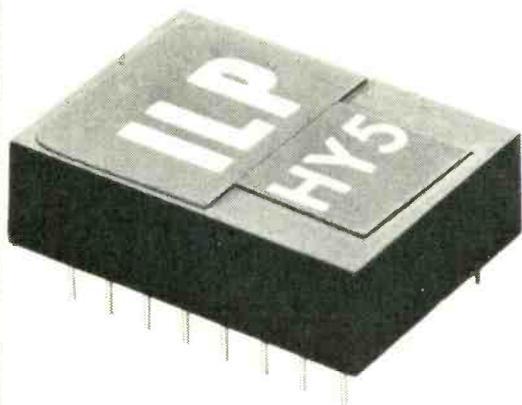

POWER SUPPLY PSU50

The new PSU50 has a low profile look being only 2¼ inches high and can be used for either mono or stereo systems.

SPEC.


OUTPUT VOLTAGE ± 25volts.

INPUT VOLTAGE 210-240volts.

SIZE L 70 D 90 H 60mm.

Price £5.23.

Price inclusive of VAT & P & P.

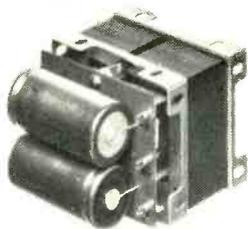

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

APPOINTMENTS VACANT

DISPLAYED APPOINTMENTS VACANT : £9.90 per single col. inch.
LINE advertisements (run-on) : 55p per line (approx. 7 words), minimum two lines.
BOX NUMBERS : 25p extra. (Replies should be addressed to the Box number in the advertisement, c/o Wireless World, Dorset House, Stamford Street, London, S.E.1.)
PHONE : Allan Petters on 01-261 8508 or 01-928 4597.
Classified Advertisement Rates are currently zero rated for the purpose of V.A.T.

Advertisement accepted up to 12 noon Thursday, October 4th for the November issue subject to space being available.

Test Engineers

Up to £2,600

Are you seeking a challenge?

The Post

To meet major growth requirements IAL seek experienced Test Engineers to be engaged in testing and trouble shooting on the most advanced solid state electronic assemblies and a wide variety of sophisticated systems.

The Company

International Aeradio Limited, a division of the British Airways Group is rapidly spreading it's interests in world markets with particular penetrations in the communications, electronics and data communications fields.

The Engineers

Will work within the company's fast expanding electronics engineering division which is concerned with the production of solid state transmitters and receivers and digital systems equipment aimed at the Computer market.

The Requirements

The scope and responsibilities offered within the post call for very competent engineers with proven practical experience. A technical qualification will of course be advantageous but will not be an essential requirement for the right man. Applications stating age and career to date should be addressed to: Mr. R. Radcliffe, Personnel Officer UK, International Aeradio Limited, Hayes Road, Southall, Middlesex.



Our Memories business at Towcester develops and manufactures Memory Stores and Systems for the computer industry.

Senior Electronic Engineer

to be responsible for the maintenance and calibration of a wide range of electronic/electromechanical equipment.

Applicants should be qualified to HNC level, have knowledge of logic techniques and be able to work from logic diagrams.

Towcester is a pleasant rural area, situated near the M1. Assistance will be given with re-location expenses.

Please apply to — The Personnel Officer, THE PLESSEY COMPANY LIMITED, Wood Burcote Way, Towcester, Northants. NN12. 7EG. Telephone — Towcester 50312

3048



SPANISH COMMUNICATIONS EQUIPMENT MANUFACTURER

Applications are invited from qualified design engineers specialized on:

- a) Ground/Air Communications
- b) TV Colour Transmitters
- c) Side Band Transmitters

At least 5 years experience desirable. Company located in Madrid. Salary open.

Send resumé to:

NORTRON
 Fernando el Católico, 63
 Madrid 15
 SPAIN

[2539

There is scope, variety and responsibility as a

Radio Technician

Join the National Air Traffic Services of the Civil Aviation Authority as a Radio Technician and you have the prospect of a steadily developing career in a demanding and ever expanding field.

ENTRANCE QUALIFICATIONS

You should be 19 or over, with at least one year's practical experience in telecommunications. Preference will be given to those having ONC or qualifications in Telecommunications.

Once appointed and trained, you will be doing varied and vital work on some of the world's most advanced equipment including computers, radar and data extraction, automatic landing systems, communications and closed circuit television.

Vacancies exist at locations near London (Heathrow), London (Gatwick) and Stansted Airports and for suitably qualified people at the Signals Training Establishment, Milton Keynes, Bucks.

Salary: £1383 (at 19) to £1836 (at 25 or over); scale maximum £2158 (higher rates at Heathrow). Some posts attract shift-duty payments. Promotion prospects are excellent and ample opportunity and assistance is given to study for higher qualifications.

To: Mrs Pat Norton, Civil Aviation Authority, Room 518, Aviation House, Kingsway, London WC2B 6NN.

Please send me application form for entry as Radio Technician.

Name _____

Address _____

ww/2



National Air Traffic Services

COMMERCIAL RADIO

TECHNICAL MANAGER / CHIEF ENGINEER**SWANSEA SOUND LIMITED**

If you believe you have suitable qualifications and/or the right practical experience, and you want to face the unusual challenge of heading up the engineering facility of the new commercial radio station in Swansea, we would like to hear from you.

Swansea Sound's new chief engineer will equip the station within the budgets and standards laid down, recruit and train the technical staff and bring the station to a fully operational state for an air-date in early summer 1974.

He will have full responsibility for his department.

The successful candidate could be a young man with a creative flair for audio electronics, or he could possess a broader experience of radio engineering but with a fresh and flexible approach to the job demanded by the particular workings of commercial radio.

In either case he will be expected to make his own contribution to the success of the station motivating and leading a compact team of technicians.

Salary will match the qualifications and abilities of the successful man.

Write in confidence to:

Keith Lunniss, Director
Radio Advertising Bureau Ltd.,
35 Curzon Street
London W1Y 7AE

[3068]

SPANISH COMMUNICATIONS EQUIPMENT MANUFACTURER

Has an immediate opening for
 An experienced Design and Development Engineer for Audio Equipment, including Highly Professional Mixing Desks, Compressors, Limiters, Audio Monitoring Amplifiers, etc. Systems Experience is desirable.

Salary open.

Send resumé to:

NORTRON
Fernando el Católico, 63
Madrid 15
SPAIN

[2540]

C.C.T.V. STUDIO TECHNICIAN

Hambro Life Assurance Limited are installing a high quality, three-camera colour television studio at their offices in Old Park Lane, W.1.

Facilities will include video recording, editing and telecine. Additionally, two black and white camera and U-matic recording chains have been acquired.

We now wish to add to the small, professional team working on this project an enthusiastic, hard working individual who will be responsible for the technical quality of the studio output, keeping equipment lined up and trouble shooting where necessary. Other aspects of the job are wide and varied, including establishment of studio sets, assisting during recordings (e.g. sound or vision mixing), liaison with suppliers, etc.

Enthusiasm and experience will be regarded as more important than technical qualifications for this position. We believe that a related engineering background with an inclination to turn a hand to all parts of the production of a video-recording are the most appropriate characteristics. Filming experience, either as an amateur or professional, would be an added advantage. Salary will be negotiable around £2,500. Working conditions are excellent and there are non-contributory pension, life assurance and B.U.P.A. schemes.

Telephone Harry Catton, 01-499 0031, for any further information and an appointment for interview.

[3098]

RADIO OFFICERS would you come ashore for £2,300 a year?

As a Radio Operator with the Post Office Maritime Service you can continue your career ashore in an interesting and expanding service. And earn over £2,000 a year, including compulsory pension contributions, at 25 years of age working only a 41-hour week of shift duties —with overtime this could rise to £2,300 and possibly more.

Post Office Radio Operators benefit from a shorter pay scale than sea-going officers. You have good opportunities for promotion to positions earning basic salaries of up to £3,290, and prospects of further advancement into Post Office Senior

Management.

To apply you need to be 21 or over and to hold a 1st class or General Certificate issued by the MPT or an equivalent certificate issued by a Commonwealth administration or the Irish Republic.

If you would like to know more, please write to the Inspector of Wireless Telegraphy, Post Office, IMTR/WTS1.1.3, Union House, St. Martin's-le-Grand, London EC1A 1AR. L52

Post Office
Telecommunications

91

Foreign and Commonwealth Office

Telecommunications Technicians

... at Hanslope Park, Milton Keynes, for work on various receivers and associated test equipment, recorders, telephone and teleprinter equipment, electronic ancillary equipment (some using analogue and digital techniques), voice frequency telegraph and other specialised equipment.

Candidates, normally aged at least 23, must have ONC or equivalent in electrical/electronic subjects *and* have served an apprenticeship or had equivalent training.

Starting salary £1,628 (at 21) — £1,810 (at 23) — £2,210 (at 28 or over on entry); scale maximum £2,418. Prospects of promotion up to £3,515. Non-contributory pension scheme.

For full details and an application form (to be returned by 12 October 1973), write to Civil Service Commission, Alencon Link, Basingstoke, Hants RG21 1JB, or telephone BASINGSTOKE 29222 ext. 500 or LONDON 01-839 1992 (24 hour answering service). Please quote T/8370

3055

cadac

The company specialise in the design and production of sound control equipment for the recording industries.

With the continued expansion of the company, vacancies arise for the following:

SENIOR TEST ENGINEER TEST ENGINEERS

Applicants should have a theoretical knowledge of electronics and/or experience in studio engineering techniques and practices.

It would be preferable that the Senior Test Engineer has had studio experience.

Salaries by negotiation and to be commensurate with that of the position.

Apply to:

**Cadac (London) Ltd.,
Lea Industrial Estate,
Batford,
HARPENDEN
Herts.**

Tel: **Harpندن (STD 05827) 64698**

2925

The best young Engineers have computers in mind.

Are you aged 21 to 25?

Do you want a flying start to a career in computers? Here is your chance. Train as a Field Engineer with ICL, Europe's leading computer manufacturer.

Training

You will be given thorough training on ICL electronic equipment leading to computers.

Qualifications

You should be aged between 21 and 25 and be on your final year or have attained City & Guilds electronic certificates or an HNC in electronics. You should have completed an electrical engineering apprenticeship or have at least two years' industrial experience on electronics.

Job satisfaction

As an ICL Field Engineer you have a high degree of responsibility for a customer's installation. You need technical expertise, tact and personality. So you are important as a representative of ICL.

There are opportunities of starting with us in several areas in the UK. Get the full details now by completing and returning this coupon today.

To: Mr A E Turner, International Computers Limited, 85/91 Upper Richmond Road, Putney, London SW15 2TQ.

Please send me an application form for job openings in Field Engineering.

Name

Address

International Computers



(WW8)

2589

THE OPEN UNIVERSITY SOUND RECORDING ENGINEER

A vacancy exists in The Open University for a sound recording engineer; five years minimum experience in the recording and editing of master tapes for radio, film, cassettes and discs. The successful candidate will be based in the sound studio (APRS member). The Open University is located in the new town of Milton Keynes and a housing scheme in conjunction with the Milton Keynes Development Corporation is operated.

Salary up to £2,241 per annum.

Applications should be made in writing stating full details of age, experience and qualifications and names and addresses of three referees to The Acting Personnel Manager, The Open University (RE2), P.O. Box 75, Walton Hall, Milton Keynes, MK7 6AL, as soon as possible.

[3023]

BERRY'S RADIO

has vacancies for

- (a) SENIOR SALESMEN
- (b) SENIOR ENGINEERS

TOP RATES OF PAY

5-DAY WEEK ● PERMANENCY

Apply: Mr. K. (405-6231)
319 High Holborn, London WC1

[97]

Electronics Test Engineers

Pye Telecommunications of Cambridge and Haverhill have immediate vacancies for Production Test Engineers. The work entails checking to an exacting specification VHF/UHF radio-telephone equipment before customer delivery: applicants must therefore have experience of fault finding and testing electronic equipment, preferably communications equipment. Formal qualifications while desirable, are not as important as practical proficiency. Armed service experience of such work would be perfectly acceptable. Pye Telecommunications is the world's largest exporter of radio-telephone equipment and is engaged in a major expansion programme designed to double present turnover during the next five years. There are, therefore, excellent opportunities for promotion within the company. Pye also encourages its staff to take higher technical and professional qualifications.

These are genuine career opportunities in an expansionist company, so write or telephone without delay for an application form to:

Mrs A E Darkin at
Cambridge Works, Elizabeth Way, Cambridge CB4 1DW.
Telephone: Cambridge 51351.
or Mrs C Dawe at
Colne Valley Road, Haverhill, Suffolk.
Telephone: Haverhill 4422.



Pye Telecommunications Ltd

A member of the Pye of Cambridge Group

96

Brighton Education Committee
Brighton Technical College

Senior C.C.T.V. Technician

Technician required as soon as possible to head a team responsible for the maintenance of closed circuit television equipment and other audio visual aids.

Applicants should possess a City & Guilds finals certificate in radio and television servicing and have had relevant practical experience.

SALARY ON GRADE T4 £1,530—£1,830.
(CURRENTLY UNDER REVIEW)

An additional allowance is payable for appropriate qualifications.

Application form and details available from:

Chief Administrative Officer,
Brighton Technical College,
Pelham Street,
Brighton, BN1 4FA.
Telephone: Brighton 685971.

[3057]

Electronics Engineers up to £4,000

Many jobs which would suit you down to the ground — either in the U.K. or overseas — are never advertised. Yet it will cost you nothing whatever to give yourself the opportunity to be considered for them. Join the Lansdowne Appointments Register — used by hundreds of employers to select electronics engineers. You have nothing to lose, everything to gain — and it's all conducted in strict confidence. So post the coupon — find out exactly how you can make use of a service which is all the more valuable for being free!

To: The Registrar, Lansdowne Appointments Register, Design House, The Mall, London W5 5LS. Tel: 01-579 6585 (anytime — 24 hour answering service). Please send me further details.

Name
Age (20-45 only)
Address

lansdowne WW 17/9
Appointments Register

3047

ENGINEER

to service
ELECTRONIC ORGANS
B & O AUDIO and C.T.V.

The work is interesting and varied, a Company vehicle is provided and there are vacancies in Birmingham and Manchester.

Telephone or write to:
W. Swan, Jnr. or Mr. D. C. Kay,
SWAN'S,
84-86 Oldham Street, Manchester M4 1LF
Tel: 061-228 3821

[2959

SERVICE ENGINEER

LKB INSTRUMENTS LTD.

requires an additional engineer to be resident in the South London, S.E. England area for field servicing of their Scientific and Technical instruments installed in Academic, Medical and Industrial Laboratories.

The successful applicant will possess a sound basic knowledge of modern electronics and will preferably have some field experience, although this is not essential.

The Company is internationally renowned for the quality of its products and offers excellent working conditions including company car, pension scheme, superannuation and profit sharing bonus scheme.

Write for application form to:
The Service Manager,
LKB Instruments Limited,
232 Addington Road,
South Croydon, Surrey, CR2 8YD
[3079

Telecommunications Technicians Looking for Variety?

The Ministry of Posts and Telecommunications needs skilled, suitably qualified Technicians to work in London on a broad range of projects.

These posts offer challenge, involvement in advanced new development, and the opportunity to develop your experience across a whole spectrum of sophisticated technology.

The Ministry is responsible for the planning of television and sound broadcasting, space communications, maritime and land mobile services; the technical monitoring of radio transmissions and radio regulatory control, together with the design of equipment for detecting, measuring and suppressing radio interference. There are opportunities to participate in the work of national and international conferences and there are good promotion prospects.

You should be at least 23, and must hold ONC Engineering with a pass in Electrical Engineering 'A', or ONC in Applied Physics, or a recognised equivalent such as C&G Telecommunications Technicians (No. 49). In addition you should have at least 5 years' experience of skilled work on radio, radar or electronics. Salary: Grade II £2,593 rising to £2,902; Grade III £1,985 at 23 — £2,385 at 28 or over on entry; scale maximum £2,593. Level of appointment will depend on age and experience. Non-contributory pension scheme.

For full details and an application form (to be returned by 10 October 1973), write to Civil Service Commission, Alencon Link, Basingstoke, Hants RG21 1JB, or telephone Basingstoke 29222 ext 500 or London 01-839 1992 (24 hour answering service). Please quote T/8349.



In order to keep pace with the ever increasing demand for large audio installations we require further staff. Specifically System planners, Supervisors, Wiremen and Test Technicians. If you consider your ability and experience suits you for one of these positions please phone or write to us. You will enjoy long term security and involvement in extensive contracts for the manufacture of technically advanced systems for use throughout the world.

GRAMPIAN REPRODUCERS LIMITED
Hanworth Trading Estate, Feltham, Middlesex.
Telephone: 01-894 9141.

HM PRISON AND BORSTAL SERVICE

TRAINING INSTRUCTOR £1,853 – £2,514

LEWES, Sussex and possibly elsewhere

Inmates of prisons and borstals are given vocational training so that they may earn their living when they leave. In addition, the training is used directly in industrial work contracted for by Prison Industries. Most of the training is to ITB specification and prepares people for City and Guilds or equivalent examinations. The service now needs the following additional instructor at HM Prison, Lewes, Sussex.

RADIO AND TELEVISION SERVICING

To train inmates in Radio and Television Servicing and to prepare them for City and Guilds examinations.

QUALIFICATIONS Applicants should have served a full apprenticeship or have had equivalent recognised training followed by at least five years industrial experience in the radio and television and/or electronic servicing industry. City and Guilds certificate (or equivalent) is desirable. Teaching or instructing experience are added advantages.

STARTING SALARY (Civilian Instructional Officer, Grade III) £1,853 at age 26; £2,082 at age 28 and above, rising to £2,514. Non-contributory pension scheme and prospects of promotion.

HOURS 40 hour week, excluding meal breaks. 4 weeks 2 days annual holidays plus 8½ days public and privilege leave.

FOR AN APPLICATION FORM Please phone or write to The Establishment Officer, Home Office, Portland House, Room 10/10 (17A) Stag Place, London, SW1E 5BX (telephone 01-828 9848 Ext. 666). Closing date 28 September 1973.

HOME OFFICE

Redland Tiles Development Department at Redhill VERSATILE ELECTRONICS TECHNICIAN

Required to construct and install a wide range of electronic and electrical control equipment using both contactor and integrated circuit techniques.

A good practical man is required capable of working on his own initiative from circuits and sketches when necessary. Good mechanical aptitude would be an advantage.

The applicant should be qualified to drive and be prepared to travel occasionally at short notice.

May suit EXPERIENCED PROTOTYPE WIREMAN following course of instruction leading to technician status. Write or telephone:

D. F. Matthews

REDLAND TILES LIMITED
Philanthropic Road, Redhill, Surrey
Telephone Redhill 64671 [3046

SOUND ENGINEER SOUTH AFRICA

Major South African Record Company are expanding their studio operations. They require an experienced Sound Recording Engineer to head up a team that will operate a new multitrack complex with the latest equipment. Salary negotiable. Write giving full details of professional background and experience to box WW 3067.

KEY SELECTION

Require for Clients

ELECTRONIC, DEV, TEST & SALES
ENGS. & TECHNICIANS
(All grades—all areas of U.K.)

Why not give your career that much needed boost by contacting Maurice Wayne on 01-487 3411, Key Selection, 126, Wigmore Street, London, W.1. [3029

Senior Quality Assurance Project Engineer

This new appointment in the Feltham Laboratories of our Systems and Weapons Division requires a qualified engineer who is able to supervise a wide range of Quality Assurance activities concerned with Instrumentation and Data Systems.

The duties will consist of liaison with development engineers from the project definition stage to production on Ministry Contracts.

Experience in Data Systems together with a sound knowledge of modern test equipment for functional test purposes, is essential.

Knowledge of Defence Standard 05-21/29 would be an advantage.

Applications should be made quoting reference number QA/11 to: **Mr. J. Morrison, Personnel Officer, EMI Electronics Ltd, Victoria Road, Feltham, Middlesex**
Tel. No. 01-890 3600 Extension 44



International leaders
in Electronics, Records
and Entertainment.

MARINE ELECTRONICS

Positions available for experienced, or trainee marine electronics engineers and operator technicians. Our work involves Oceanographic Surveys and will require personnel to work for periods overseas. This company is based at Yarmouth and for further information please write giving details of education and experience to:



OCEANEERING INTERNATIONAL SERVICES LTD.

Riverside Road,
GORLESTON
Norfolk

ilea

Education Television Service

Tennyson Street, London SW8

Mobile Section Engineer

£2907 - £3138

responsible for the technical operation and maintenance of one of the mobile control rooms, working with the Education Director and a crew of two. The MCRs are equipped with 3 monochrome Plumbicon cameras, an eight-channel sound desk and 2 inch or 1 inch videotape recorders as necessary. All members of the crew share rigging duties and the driving of vehicles. A current driving licence should be held and training will be given for the taking of an HGV driving test.

Applicants should possess a thorough knowledge of broadcast television engineering practices have appropriate qualifications and experience, and sound health.

Salary according to qualifications and experience.

Hours of work will be in accordance with the requirements of the service but the basic week is 35 hours. Hours are of necessity rather irregular, often involving overtime, but time off in lieu will be granted or, where that does not prove possible, overtime payment will be made. Weekend working is very seldom necessary. The annual leave entitlement, after qualifying service, is 5 weeks and 1 day.

Application forms and details from the Education Officer (Ref EC/Estab 2A/2). The County Hall, London SE8. Tel 01-633 7546 or 01-633 7456. Closing date for completed application forms October 1.

[3021

Lancashire County Council Health Department

The Health Education Service has a vacancy for a

TECHNICIAN (TV/PHOTOGRAPHY)

Grade Tech. 4
Salary £1,530-£1,803

Television is becoming an integral part of audio visual aids in the provision of health education. T.V. studio facilities are being developed and the Health Education Service requires a technician whose duties will include the technical operation of T.V. equipment.

The person appointed will, of course, be knowledgeable in the use of normal projection equipment. It will be an advantage for applicants to have some expertise in camera work and photography.

The post is full time, permanent, superannable and subject to medical clearance. Application forms obtainable from the County Medical Officer of Health, Serial No. 9693, East Cliff County Offices, Preston, to be returned by the 20th September, 1973.

[3097

MARCONI INSTRUMENTS LIMITED

ELECTRONIC TECHNICIANS

are required to work on calibration, fault-finding and testing of telecommunications measuring instruments. The work is varied and will enable technicians with experience of r.f. circuits to broaden their knowledge of the latest techniques employed in the electronics and telecommunications industries by bringing them into contact with a wide range of the most advanced measuring instruments embracing all frequencies up to u.h.f.

Entrants may be graded as Test Technicians. Senior Test Technicians or Technician Engineers according to experience and qualifications. Our servicing and production programme, geared to our recognised export achievement, provides employment combined with prospects of advancement, not only within these grades, but into other technical and supervisory posts within the Company at Luton and St. Albans.

Salaries are attractive and conditions excellent. A Pension Scheme includes substantial life assurance cover provided by the Company. Assistance with removal may also be given in appropriate cases. Please write or telephone, quoting reference WW178 for application form to:



Mr. M. Leavens, Works Manager
Telephone: Luton 33866. or
Mr P Elsip, Personnel Officer
Marconi Instruments Ltd
Longacres, St. Albans, Herts
Telephone: St. Albans 59292

Member of GEC-Marconi Electronics



95

Maintenance Engineers

Saudi Arabia

£4-£6500 (tax free)

Opportunities exist in Saudi Arabia for Engineers experienced in the installation, commissioning and maintenance of complex radar systems, on-line real time computer systems and their associated peripherals, other sophisticated digital hardware, tropospheric scatter systems and telecommunication systems. These posts involve 1-2 years unaccompanied tours for which inclusive salaries between £4000-£6500 will be paid. Free air-conditioned individual accommodation, and local

transportation is provided. U.K. leave entitlement is 16 days after each 24 weeks. Candidates, aged 23-50 years, should have extensive relevant practical experience (particularly experience of 3-D Radar), together with a formal qualification or services background. Excellent opportunities exist for career development and those selected will become permanent staff with all the benefits that this implies. Regional interviews will be conducted. Write or telephone for application form to:

**lansdowne
Recruitment Limited**

Chris Jamieson, Lansdowne
Recruitment Limited, Design
House, The Mall, London W5 5LS.
Tel 01-579 6585 (anytime - 24 hour
answering service)

TECHNICAL REPRESENTATIVES TO SELL TELEQUIPMENT EDUCATIONAL PRODUCTS

In order to satisfy the special needs of EDUCATION, three posts have been created. Successful applicants will be required to call on EDUCATION AUTHORITIES and COLLEGES in (1) England NORTH of the Wash and North Wales

(2) EASTERN counties Wash to Thames

(3) SOUTH England and South Wales

They will need sufficient knowledge of electronics to justify the product training provided by the company. Experience with oscilloscopes or knowledge of physics would be an advantage.

Basic salary £2,000 TOTAL EARNINGS with commission and company profit share will be in the region of £2,600-£2,900. Company car — Pension Scheme.


Contact Keith Retallic — SALES MANAGER

We also need TECHNICIANS at HARPENDEN, MANCHESTER and LIVINGSTONE (SCOTLAND) service centres.

CONTACT MR. R. M. GARRATT



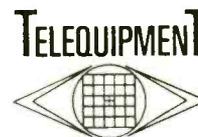TEKTRONIX UK LTD.
P.O. BOX 69, HARPENDEN, HERTS.
05827 61251




Customer Engineers Junior Engineers Testers

We require a wide range of staff for our expanding Customer Engineering Department. We design and produce Mobile Radio control equipment for a varied range of customer requirements, we need engineers to design, supervise production, test and commission a wide range of mobile radio telephone equipment.

If you are an engineer, an ambitious service engineer or tester who is looking for a career opportunity, and you have experience on one or more of the following:-

- 1 V.H.F. or U.H.F. radio equipment
- 2 Systems design
- 3 Circuit design of A.F., R.F., or D.C. switching circuits
- 4 Testing or servicing of Mobile Radio telephone equipment
- 5 If you can work with the minimum of supervision

Contact Mrs. L. Dyne, Personnel Dept.
ERITH 39121 Burndept Electronics (E.R.) Ltd.,
St. Fidelis Road, ERITH, Kent DA8 1AU.

SERVICE ENGINEER EXTRAORDINARY

We are seeking an unusual mixture to offer an exciting challenge, good prospects and pay. The service engineer sought should have both digital and analogue experience, mechanical aptitude and if possible knowledge of nuclear physics. He will cover the North of England, London and the South East, responsible for after-sales service of liquid scintillation equipment. Please reply in confidence to:

MANAGING DIRECTOR
INTERTECHNIQUE LIMITED
COTTRELL HOUSE
53-63 WEMBLEY HILL ROAD,
WEMBLEY HA9 8BE

[3095]

WIGGINS TEAPE RESEARCH AND
DEVELOPMENT LTD.

Butlers Court, Beaconsfield, Bucks.

SENIOR ELECTRONICS TECHNICIAN

Applications are invited for this post to lead a small team engaged in applying electronics to papermaking research and allied processes at the Central R. and D. Unit of an international papermaking group. Based at Beaconsfield the duties will include design, development, manufacture and maintenance of a wide variety of electronic, electro-mechanical and opto-electronic instrumentation.

Applicants should be of H.N.C. standard and have several years development experience with linear and digital circuits.

The salary is negotiable in the range £2,000 to £3,000. The unit provides excellent working conditions, a pension scheme and luncheon vouchers.

Application forms from Mr. A. W. Massey, Personnel Department. Tel: 0494 5652.

[3091]

CHIEF INSPECTOR

Thorn Consumer Electronics (Chigwell) Limited is the Audio division of the Thorn Group of Companies and in order to satisfy the continuing increase in demand for our products, both at home and abroad, it has become necessary to undertake an expansion programme. A new audio factory has been established at Harold Hill in Essex, which will ultimately be the largest manufacturing unit of its kind in Europe using sophisticated production techniques.

An exceptional opportunity occurs for a suitably qualified man to join the new organisation, which will be involved in quantity volume production of high wattage unit audio equipment, as Chief Inspector.

The job will be concerned with all aspects of the inspection, test and troubleshoot functions associated with the flowline production of the units. In addition, close liaison, with the Training Department in forward planning and training requirements will be necessary.

The successful candidate will hold suitable electronics qualifications, have experience of high volume production methods, be a capable staff motivator and will possess the drive and enthusiasm which the job will demand.

Written applications, setting out brief career details to date and current salary to:



**THE PERSONNEL MANAGER,
THORN CONSUMER ELECTRONICS,
62/70 FOWLER ROAD, HAINAULT, ILFORD, ESSEX**



A member of the Thorn Group

3053

LEEDS POLYTECHNIC
Educational Technology Unit

**Senior
Workshop Technician T5**

£1,803-£2,100 (under review) Ref. 13/14
This is a newly created post and the successful candidate will be required to service and maintain electronics equipment held by teaching departments of the Polytechnic.
Application forms (quoting reference number) together with further particulars, from the Administration Officer, Leeds Polytechnic, Calverley Street, Leeds, LS13 3HE, to be returned as soon as possible.

[3092

**CLOSED CIRCUIT
TELEVISION
TECHNICIAN**

£1,713 — £2,790

required in the London College of Printing, SE1, for the operation and first line maintenance of an extensive C.C.T.V. distribution system linking all the teaching areas of the college to a central control room.

Duties will include the central recording and routing of programmes as well as the setting up of a mobile programme origination "package", consisting of cameras and associated vision and sound equipment.

Applicants should have a basic knowledge of electronics and experience with the operation or installation of broadcast or closed circuit television equipment.

Starting salary according to qualifications and experience.

Application form returnable by October 2, from the Establishment Officer (E/635/) Room 163N, County Hall, London, SE1 7PB.

**Electrical Service
Engineering Group**

GLC GREATER LONDON COUNCIL

30/2

**Electronic
Calibration
Engineers**

G & E Bradley, part of the international Lucas organisation, develop and manufacture a unique range of electronic instruments and medical equipment. We can also boast the most comprehensive maintenance, calibration and repair service in the U.K.

So, to maintain our reputation and our current expansion programme, we're looking for more experienced Electronic Calibration Engineers with a maintenance background in telecommunications, radar, microwave, ECM systems, and all types of electronic test equipment.

Professionally competent Engineers, with or without relevant qualifications, will enjoy attractive salaries

plus the benefits normally associated with a major organisation.

And, for the ambitious, the promotional prospects to supervisory status are exceptional.

Please apply in writing or by telephone to:

**The Personnel Manager,
G & E Bradley Ltd.,
Electral House, Neasden Lane,
London N.W.10.
Tel: 01-450 7811**



A LUCAS COMPANY

3084

Computer Engineers

We're going to select a number of able, decisive, productive and logical minds to become expert on our very large computer systems.

We will train you for twelve to eighteen months in basic and advanced hardware and software; after this you will be responsible for ensuring that large computer systems of a particular type are kept in first-class order. This could lead to your being in charge of a team of high-calibre engineers.

Each assignment is unique and may be in Britain, Europe or elsewhere and would appeal to the young qualified engineer who wants a high degree of responsibility, has the personality, tact and resourcefulness required of a representative of ICL and who wishes to travel whilst broadening his knowledge of large computer systems.

Applications are welcomed from experienced Computer Engineers or graduates with highly logical minds and a degree in maths, physics or engineering science.

You will initially, and during training, be based in one of the following locations:

- Letchworth/Stevenage
- West Gorton, Manchester
- Kidsgrove, Staffordshire


Write for an application form, quoting reference WW496C, to A E Turner, International Computers Limited, 85/91 Upper Richmond Road, Putney, London SW15 2TQ.

International Computers
think computers - think ICL



ELECTRONIC ENGINEERS

required for equipment maintenance and associated engineering projects. Knowledge of professional tape recording equipment, studio operations, or high speed tape duplicating systems is desirable. Salary will be according to age and experience. Please write giving details of age, qualifications, experience and present salary to Chief Engineer, Rediffusion Redition Ltd., Cray Avenue, Orpington, Kent.

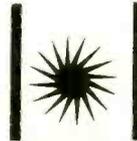

REDIFFUSION

SUPERVISOR

(EVENING SHIFT)

A music cassette/cartridge plant requires a man aged 28 or over to supervise their duplicating department. Applicants must have some practical experience in the audio field, and an understanding of tape recording principles is essential.

We can offer good working conditions and a salary in the region of £1750 p.a. dependant on ability and experience.

Apply to: Mr. R. A. Goodwin,
Trident Tape Services,
4/10, North Road,
Islington, N.7.
Tel: No. 609 0087.

[3058]

UNIVERSITY OF KENT
AT CANTERBURY

A

TECHNICIAN (Grade 3)

is required for the Audio Visual Aids Service. He must be experienced in present-day television servicing and, desirably, should also have a keen interest in cine-projection and other visual aids to teaching. The salary scale is £1539 - £1794. Further particulars and application forms may be obtained from R. Robson, Assistant Registrar, The Registry, The University, Canterbury, Kent quoting reference T73/10. The closing date for completed applications is 29th September, 1973.

[3061]

Storno

RADIO COMMUNICATION SYSTEMS

We have vacancies for:

SERVICE TECHNICIANS

based at Camberley, to work in a specialised Department dealing with miniaturised transmitter/receivers on fault diagnosis and correction. Technical experience of communications systems is an advantage.

FIELD SERVICE ENGINEERS

in the Greater London Area. Applicants should have experience in fault finding and testing of UHF/VHF radio equipment. Current driving licence essential, company vehicle provided.

The Company has much to offer those who are interested in the sophisticated, modern world of radiotelecommunications and who can demonstrate their ability in this field.

Please contact:

**The Personnel Officer,
STORNO LTD.,
Frimley Road, Camberley, Surrey.**

Telephone: 0276 29131

3081

Ulster—The New University

INSTITUTE OF
CONTINUING EDUCATION
MAGEE UNIVERSITY COLLEGE
LONDONDERRY

C.C.T.V. TECHNICIAN

Applications are invited for the above post. Duties will include the operation and maintenance of CCTV services and preparation of programme material.

Qualifications: HNC, or equivalent, plus at least seven years previous experience.

Salary scale: £1,881-£2,241 per annum.

Application forms and further particulars should be obtained from The Registrar, The New University of Ulster, Coleraine, Co. Londonderry, Northern Ireland (quoting Ref. No. 73/130/149/31/98) to whom completed applications, including the names and addresses of three referees, should be returned not later than 31st October, 1973.

[3088]

UNIVERSITY OF SHEFFIELD

**AUDIO
VISUAL
TECHNICIAN**

(Grade 3) responsible for maintenance and operation of audio visual equipment (film, slide and overhead projectors, tape recorders, P.A. systems, photo-copying, etc.).

Familiarity with photographic techniques an advantage. Salary scale £1,539 x £51 (5)—£1,794 p.a.

Write giving details of experience and qualifications, to the Deputy Director of Services (Ref. B.333/BW), The University, Sheffield, S10 2TN.

[3096]

**KING'S COLLEGE HOSPITAL
MEDICAL SCHOOL
(University of London)
Denmark Hill, London SE5 8RK**
**ELECTRONICS
EXPERIMENTAL OFFICER**

A vacancy exists in the Department of Biomedical Engineering for an Experimental Officer to work as part of a multi-disciplinary team on the development and construction of prototype electronic instruments for use in medical research. Salary will be in the range of £1,401 — £2,154 according to age and experience and the appointment will be for two years in the first instance. Candidates should have had adequate experience either in industry or in hospital and will be expected to hold an HNC in electronics or light current electronic engineering as a minimum. Applications to the Director, Department of Biomedical Engineering.

[3071]

**ELECTRONIC
ENGINEER**

Recording Studio of major Record Company require young Audio Electronic Engineer with a fresh approach to the problems of modern recording electronics.

**POLYDOR RECORDS
STUDIO LONDON
01-499 8686 ext 51**

[3077]

**IPSWICH AND DISTRICT
HOSPITAL MANAGEMENT COMMITTEE**
**ELECTRONICS
TECHNICIAN**

Applications are invited for the above post. Candidates should possess H.N.C. or equivalent qualifications, but consideration will be given to suitably qualified and experienced candidates in this field.

SALARY SCALE: £1,602 to £2,076 p.a. According to qualifications and experience.

Please note: that although the salary scale for this post rises from £1,602 to £2,076, new entrants to the Health Service are normally required to start on the lowest point of the scale. The successful candidate will be a member of a new and expanding department, servicing a wide range of electronic/bio-medical equipment.

For further details of this post, please telephone Ipswich 56481, Ext. 33 or write to: The Group Engineer, Ipswich and District Hospital Management Committee, 26 Broughton Road, IPSWICH, IPI 3QS.

[3038]

Draughtsmen!

EMI, one of the world's leading Companies in the fields of military and commercial Electronics, are forming teams to undertake several new and important projects in their divisions at Hayes, Middlesex — challenging work on the design of highly advanced electronic equipment. This opens up first class opportunities for

**Senior
Intermediate and
Junior Draughtsmen.**
with a mechanical, electrical
or electronics background.

To work in the following fields:

- * Radar and associated projects
- * Television and Aerial Systems
- * Microelectronics — thick and thin film work
- * Microwaves tubes and components

Starting salaries up to £2600 p.a. If you are looking for a good career in the forefront of Electronics technology, please write giving career details, or phone for an application form: **Richard Black, Personnel Department, EMI Electronics Ltd., 135 Blyth Road, Hayes, Middlesex. Tel: 01-573 3888 Ext. 2887.**



International leaders
in Electronics, Records
and Entertainment.

METROPOLITAN WATER BOARD

Assistant Communications Officer**(£2,733—£3,105)**

Applications are invited for the above-mentioned post which will be based at the Board's Head Offices.

Duties are to assist in project investigation, planning and development of mobile radio, telecommunications (telephone and telegraph) and data transmission networks.

The successful candidate should possess a suitable qualification, e.g. Degree, H.N.C., etc., and be experienced in Post Office procedures and have had practical experience at supervisory level in one of the following fields for at least five years.

- (1) V.H.F./U.H.F. mobile radio communications.
- (2) Telecommunications—privately switched networks, large P.A.B.X. installations (cross-bar type), transit switching techniques, Post Office telephone equipment, and data transmission.

An application form returnable by 5th October, 1973, may be obtained from the Establishment Officer, Metropolitan Water Board, New River Head, Rosebery Avenue, EC1R 4TP, or telephone 01-837 3300 Ext. 19.

[3090]



Telecommunications Engineer

With the expansion of the company's off-shore oil and gas production activities in UK and overseas areas, a further telecommunications engineer is required to work in our London Office.

Duties will include the design, development and implementation of remote control and supervisory systems with microwave/tropospheric scatter or cable links and telecommunications systems for normal correspondence and data. Some overseas travel will be involved for site surveys and equipment installation/commissioning.

Candidates, aged 30-40, must be qualified C. Eng. or B.Sc. in Electronic Engineering. Experience to include at least four years in a senior capacity on installation, testing or site maintenance of electronic telecommunications equipment and four years design and development in systems planning. At least one year's service in the oil or allied industries in this specialised field is desirable.

A realistic salary will be paid, with excellent terms and conditions.

■ Please write in the first instance, giving details of your experience, quoting reference AAG 604, to: The Manager, Central Recruitment, The British Petroleum Company Limited, Britannic House, Moor Lane, London, EC2Y 9BU.

3043

DYNAMIC SERVICE ENGINEERS DIGITAL ELECTRONICS

OHIO-NUCLEAR is the world's leading supplier of radio-isotope imaging equipment for use in diagnostic nuclear medicine. Due to continued rapid expansion we wish to recruit experienced field service personnel to undergo specialised technical training on our advanced systems to become **PRODUCT SPECIALISTS (SERVICE)**.

The work involves travel to install and service our range of digitally-oriented medical equipment throughout the U.K. (occasionally abroad).

DESIRABLE REQUIREMENTS for these positions are as follows:

- H.N.C. or equivalent
- wide, general electronics background
- thorough knowledge of 74 Series logic
- working knowledge of core and tape memory systems
- ability to work on own initiative with minimum supervision.

These are **KEY POSITIONS** offering real scope for advancement in a very exciting and rewarding field. The posts command an attractive salary, company car and extensive fringe benefits.

Detailed résumé, including age, education and experience, to:

The Service Manager, Ohio-Nuclear (U.K.)
Radix House, Central Trading Estate,
Staines, Middlesex.

SPANISH FIRM NEAR MADRID

is looking for design and development engineers with a minimum of three years of experience in the field of P.C.M. equipment to be used by the telephone industry.

Areas of interest are encoders and decoders, P.C.M. multiplexers and R.F. equipment to transmit P.C.M. data.

Salary open.

Send résumé to:

NORTRON
Fernando el Católico, 63
Madrid 15
SPAIN

2584

**HARTLEPOOL HOSPITAL
MANAGEMENT COMMITTEE**

Electronics Technician

Applications are invited for this new post to undertake the maintenance of electronic equipment in hospitals in and around Hartlepool.

The appointment is to the Staff of the Group Engineer, to whom the successful applicant will be accountable for the repair and planned preventive maintenance of a wide range of electronic equipment, including electro-medical and laboratory apparatus, H.F. pocket-paging receivers and transmitters, engineering controls, and audio/radio frequency distribution systems.

Applicants should preferably hold H.N.C. (Electronics or light current Electrical engineering) or City and Guilds Full Telecommunications Certificate.

National Health Service Conditions.

Starting Salary within the scale of £1,602-£2,076 p.a., depending on age, experience and qualifications.

Application forms are available from:—

**GROUP PERSONNEL OFFICER,
HARTLEPOOL HOSPITAL MANAGEMENT COMMITTEE,
CENTRAL ADMINISTRATION,
GENERAL HOSPITAL,
HARTLEPOOL.**

[3019]

**THE HOSPITAL FOR SICK CHILDREN
GREAT ORMOND STREET, LONDON, WC1N 3JH**

ELECTRONICS TECHNICIAN

required by the Medical Electronics Workshop to set and maintain high standards of serviceability and safety of a wide range of electronic apparatus used in the workshop and the Hospital.

Applicants must have sufficient constructional ability to enable them to assist with the modification and improvement of both existing and new apparatus. Experience of medical equipment would be an advantage but is not essential.

Salary on a fixed scale of £1,728 to £2,202.

Qualifications should be a minimum of O.N.C. or equivalent.

Day release for further study is available.

Application forms may be obtained from the Deputy Hospital Secretary.

[3031]

AUDIO SERVICE ENGINEERS

Lindair, London's leading Hi-Fi Retailers, require 2 Audio Service Engineers for their Service Dept. in the West End.

The Service Department deals with leading top-quality brands of Hi-Fi equipment, such as Amps., Receivers, Tape-Recorders, and Loudspeakers.

Applicants must be fully competent to work under the minimum of supervision. Ideally they should have appropriate City and Guild and/or "O" levels in Maths and Physics, but qualifications are not as important as the ability to complete a job once started.

Minimum age 22.

High Salaries will be paid, other attractive conditions of service include 3 weeks' paid holidays.

To arrange an interview write or phone:—

**Mr. George Welsh, Lindair, Kirkham House,
54a Tottenham Court Road, London, W1
Telephone: 01-637 1601**

LINDAIR

RADIO OFFICERS

**DO YOU HAVE PMG I PMG II MPT
2 YEARS OPERATING EXPERIENCE**

*POSSESSION OF ONE OF THESE QUALIFIES
YOU FOR CONSIDERATION FOR A RADIO
OFFICER POST WITH COMPOSITE SIGNALS
ORGANISATION.*

On satisfactory completion of a 7-month specialist training course, successful applicants are paid on a scale rising to £2,527 pa; commencing salary according to age — 25 years and over £1,807 pa. During training salary also by age, 25 and over £1,350 pa with free accommodation.

The future holds good opportunities for established status, service overseas and promotion.

Training courses commence at intervals throughout the year. Earliest possible application advised.


Applications only from British-born UK residents up to 35 years of age (40 years if exceptionally well qualified) will be considered.

Full details from

**Recruitment Officer, Government Communications
Headquarters, Room A/1105 Priors Road, Oakley,
Cheltenham, Glos GL52 5AJ, Telephone:
Cheltenham 21491 Ext 2270**

92

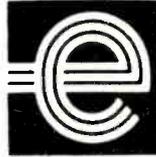**CENTRAL ELECTRICITY
GENERATING BOARD
SOUTH WESTERN REGION**



**SCIENTIFIC SERVICES DEPARTMENT
CONTROL & INSTRUMENTATION BRANCH**

**LABORATORY
TECHNICIAN**

A vacancy exists in the Instruments Section of the Scientific Services Department at Portishead, Somerset.

The work will be largely based at the laboratories at Portishead but site work at the Region's Power Stations will be necessary.

The successful candidate will join a new group, in a supporting role, to Research Officer involved in using mini computers and other logic devices to control, collect and analyse data from experiments. The group also provides a service in design and constructing electronic signal conditioning units.

The candidate's duties will be to construct electronic equipment and to generally assist in the production of both hardware and software associated with computer control and data collection. He will be expected to undertake some electronics development work.

Applicants should have an Ordinary National Certificate in Electrical/Electronic Engineering or Physics, and some practical experience in electronics and circuit construction. A working knowledge of digital and printed circuit techniques and workshop practices is desirable.

The terms and conditions of service will be in the National Joint Board Agreement for the Electricity Supply Industry. The salary will be within the range £1,446 to £2,376 per annum depending upon age, experience etc. In addition, allowances of £60 and £174 per annum are payable.

Applications on Form SF/1, obtainable from the Personnel Manager, 15-23 Oakfield Grove, Clifton, Bristol BS8 2AS, should be returned to him (quoting Vacancy No. 292/73) by not later than 1 October 1973.

3070

**LINCOLN No. 1 HOSPITAL
MANAGEMENT COMMITTEE**

Lincolnshire
Medical Physics Department
St. George's Hospital

**MEDICAL PHYSICS
TECHNICIAN GRADE V**

(Male or Female)

The Department is engaged upon providing diagnostic services, using radioactive isotopes including scanning, ultrasonic, electromyography, patient monitoring, etc.

Applicants must be qualified Radiographers or possess an ONC, two "A" levels in an appropriate science subject or HNC. Training for higher educational qualifications will be arranged in appropriate cases.

Salary £1,209 rising by annual increments to a maximum of £1,563 per annum.

Applications giving full details of education, qualifications and experience together with the names of two referees to the Hospital Secretary, St. George's Hospital, Lincoln.

[3028]

SITUATIONS VACANT

DO you require Indian representation? B.Sc. Honours in Electrical Eng. Resident Delhi, Bombay. Willing to act as local rep. for U.K. companies. Ref. available. Write Box WW3035.

ELECTRONICS TECHNICIANS. (1) Grade II £2,037-£2,634. To be accountable to the Group Engineer for the Department. (2) Grade III £1,725-£2,202. Salaries under review for payment of Government Phase II increase. The successful applicants will service and calibrate a wide range of equipment used in medical, surgical and engineering services, working closely with medical and other professional staff. Temporary single accommodation may be available. Further particulars and application forms returnable by October 8th from Mrs. J. Moore, Staffing Officer, Ext. 2202, Northwick Park Hospital and Clinical Research Centre, Watford Road, Harrow, Middlesex, HA1 3UJ. Telephone 01-864 5311. [3020]

FULLY experienced Audio Engineer required by leading importer of high fidelity equipment. The applicant should have working experience with most types of unit and be fully up-to-date with current techniques. 5 day week. Salary by negotiation. Applications to the Managing Director, Howland-West Ltd., 3-5 Eden Grove, London N7 8EQ. [3062]

HI-FI AUDIO ENGINEERS. We require experienced Junior and Seniors and will pay top rates to get them. Tell us about your abilities. 01-437 4607. [118]

IMPERIAL College of Science and Technology Technical Vacancy. **ELECTRONICS DEVELOPMENT ENGINEER** required, for a research project requiring development of electrical controls for high pressure hydraulic and mechanical systems. Qualifications: Degree or equivalent, mechanical background. Salary £2,229 to £2,715 plus £175 per annum London weighting, according to experience. Contract for a limited period. Application forms from Departmental Superintendent, Department of Geology, Imperial College, London SW7 2BP. [3044]

LEEDS (ST. JAMES'S) UNIVERSITY HOSPITAL MANAGEMENT COMMITTEE — **MEDICAL PHYSICS TECHNICIAN (GRADE I) (NEW POST)**. An electronics technician is required for the maintenance of x-ray image intensifiers and closed circuit television equipment in St. James's and other hospitals in Leeds. There are now 14 sets of equipment in use. The person appointed will work with the x-ray maintenance staff in the Medical Physics Unit. Candidates should have an O.N.C. or H.N.C. in electronic engineering or a science degree, followed by at least three years of relevant experience. Salary scale £1,602—£2,076. Application forms available from the Group Personnel Manager, St. James's Hospital, Leeds LS9 7TF. Closing date September 28th, 1973. [3045]

TEST Engineers and Installation Engineers—starting salary £1,400-£2,000. Electrosonic have vacancies for both test and installation engineers on audio, audio visual and lighting control equipment. Permanent and pensionable positions offering an excellent opportunity for applicants with initiative, experience and a sound knowledge of electronics. Starting salary according to experience. Electrosonic is an expanding international company and posts offer opportunities for travel. Apply Electrosonic Ltd., 815 Woolwich Road, Charlton, SE7 8LT. Telephone 01-855 1101 between hours 9 am-7 pm. [3087]

TECHNICIAN, GRADE 5 required for Electronics Section of Science Workshop. Applicants should be suitably qualified and be conversant with the maintenance and adaptation of electronic instruments and equipment and the design and construction of simple electronic apparatus for research and teaching. 5 day week. 5 weeks' annual leave. Pension Scheme. Commencing salary on scale £1,881 x 72—£2,241 plus £175 London Allowance, according to qualifications and experience. Application forms may be obtained from The Assistant Secretary (Personnel), (WW) Bedford College, Regent's Park, London, NW1 4NS. (Tel.: 01-486 4400 Ext. 313). [3060]

CLASSIFIEDS—Continued on p. 125

Are you interested in
**Communal Aerial Television
Systems Work?**

Then read on further.....

Due to continued expansion, EMI Service, part of EMI's Electronics and Industrial Operations group of Companies, has the following vacancies for engineers at Hayes, Middlesex.

SERVICE ENGINEERS required for bench and field work on Communal Television Aerial equipment. Must be capable of diagnosing faults and repairing wide range of aerial amplifying and distribution equipment.

SYSTEMS PLANNING ENGINEERS for the planning of Communal Television Aerial installations. Previous experience required to be capable of producing practical plans from building details and subsequently setting to work after installation.

Attractive starting salaries. Contributory Pension Scheme. Assistance with removal expenses in appropriate cases.

WANT TO TAKE THINGS FURTHER then write or telephone for an application form to:
R. N. L. Black, Personnel Department, EMI Limited, 135 Blyth Road, Hayes, Middlesex. 01-573 3888, Ext 2887.



International leaders in Electronics, Records and Entertainment.

SALES MANAGER

to market commercial sound products including the newly acquired 'Altec' Agency.

Salary negotiable: £3,000 plus.

Apply in writing to:

THEATRE PROJECTS SOUND LIMITED,
10 Long Acre, London, W.C.2

[3112]

Electronics Engineer

We are a London-based Studio and we are looking for a young Engineer who is capable and eager to learn. He will be working with Broadcast Colour cameras, VTR and Telecine.

Write or phone: Jon Hocking,
Technical Director,

ZOOM TELEVISION LIMITED
15-19 New Fetter Lane,
London E.C.4
Tel. 01-353 3641

[3110]

London Borough of Haringey
Education Service

Laboratory Technician

Salary £1,416—£1,635 per annum plus recent pay award. Commencing salary according to qualifications.

Full-time Laboratory Technician required at Stationers' Company's School, Mayfield Road, N.8, to work 36 hours per week X 52 weeks per annum.

Minimum qualifications: Ordinary National Certificate or Ordinary National Diploma; City and Guilds Laboratory Technicians Certificate; 4 G.C.E. passes with 2 at 'A' Level in appropriate subjects; Membership of Institute of Science Technology OR an equivalent suitable qualification OR 5 years suitable experience. Qualifications in Electronics would be an advantage.

Candidates will be responsible for the maintenance of the Language Laboratory and will be required to assist in the upkeep of Audio-Visual aids throughout the School and help monitor a computer link-line.

The post is ideal for a candidate who wishes to gain experience in the maintenance of a fairly wide range of equipment.

Application forms obtainable from Chief Education Officer, Somerset Road, N.17, returnable by 29 October, 1973.

[3111]

CLASSIFIEDS—Continued from p. 124

SITUATIONS WANTED

MARINE RADIO OFFICER: (Aged 27), eight years sea service seeks employment ashore within the electronics field in either field service, sales engineering or communications. PMG Certificate (2), DTI Radar Certificate. Willing to learn new fields and travel either at home or abroad. Permanent position, preferably in Scotland. Box WW 3099.

SURPLUS components and computer boards purchased for cash. 01-692 2009. [3108]

ARTICLES FOR SALE

A MPEX FR 1400 Instrumentation Tape Recorder/Reproducer, £375.00. EMI TR 52 two-channel audio Tape Recorder, £120.00. EMI magnetic drum Echo System (ex Abbey Road), £185.00. Hewlett Packard Series 3900 Tape Unit (new), £75.00. Kearfott Gyro T2502, £7.50. ERA solid-state 400Hz Inverter, 100VA, £15.00. Tinsley 50Hz Tuning Fork in polished wood case, £12.00. IBM Standard Electric Typewriter mounted on table, £55.00. IBM Selectric Typewriter on table, £95.00. Solartron CD 1400 d.b. Oscilloscope, £140.00. Solartron LM 903 a.c. Converter/Voltmeter, £12.00. ICT adjustable 6V Supply with twin meters, £16.00. Deltron 12V/20A Supply with twin meters, £12.00. Ekco M 5024 six-digit ttl Counter-Timer, £25.00. Advance TC 2A 1MHz Counter-Timer (Crystal Clock), £39.50. Raymond froulkes, Frensham Heights, Rowledge, Farnham, Surrey. Or phone Godstone 3106. [3074]

CLASSIFIEDS—Continued on p. 126



Senior Wireless Engineer

(£3237-£4098)

... to be responsible for the technical direction and control of staff engaged in the examination of problems associated with the planning, design, progressing installation and maintenance of a wide variety of telecommunications systems. These include mobile radio systems, message switching, networks to interface with large data processing computer systems, closed circuit television, radar and allied techniques, and control room design for fixed locations.

Candidates should have satisfied the academic and training requirements for corporate membership of an appropriate professional institution. They should have a broad knowledge of modern telecommunications, both radio and line, and have specialised in system planning and/or system research or have had experience in the control and management of a large-scale maintenance organisation.

Starting salary within the quoted scale. Promotion prospects. Non-contributory pension scheme.

For full details and an application form (to be returned by 10 October 1973) write to Civil Service Commission, Alencon Link, Basingstoke, Hants, RG21 1JB, or telephone BASINGSTOKE 29222 ext. 500 or LONDON 01-839 1992 (24 hour answering service), quoting T/8376.

HOME OFFICE Directorate of Telecommunications

3052



Marine Radio Design

IMRC is a leading company involved in the design and supply of radio communications equipment to the merchant shipping industries of the world.

We have the following vacancies in our development team working on new transmitter and receiver design projects.

Senior Electronics Development Engineer

Experience: A minimum of three years in circuit design for radio communications equipment, ideally with some time having been spent on projects in the MF and HF bands. A sound understanding of both linear and logic techniques associated with this field would be advantageous.

Qualifications: Degree or HNC standard — but ability and experience are our major concern.


Senior Design Draughtsman

Experience: At least five years in the layout, detailing and documentation of electro-mechanical designs including the layout and preparation of artwork for printed circuit boards.

Please write or phone with brief details of your experience or qualifications to:

Miss S. J. Lemmon
International Marine Radio Co. Ltd.,
Peall Road, Croydon CR9 3AX
Tel: 01-684 9771

3049

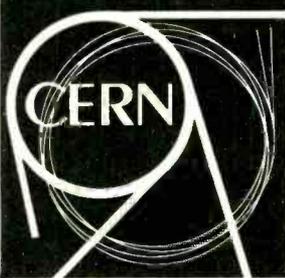

European Organization for Nuclear Research
Organisation Européenne pour la Recherche Nucléaire

CERN is a modern research laboratory, situated near Geneva, which offers first-class social and financial conditions of employment, and the opportunity to work in an international atmosphere.

A vacancy exists for a young

Electronics Technician (VHF)

to follow the progress of the construction, by external manufacturers, of the 200 MHz electronics equipment associated with beam position detectors of the 300 GeV proton synchrotron, now under construction. The successful candidate will also design and build circuits for reception tests, will perform these tests, will install the equipment and participate in its commissioning and maintenance.

Applicants should have a technical college diploma and some years of practical experience in the design and construction of HF and VHF circuits. Good knowledge of English or French desirable.

Please write for an application form to the address given below, quoting the reference: 8-051-CO-BM-361, to

Head of Personnel
CERN,
 1211 Geneva 23, Switzerland.

[3027

Marine Radio Engineers

The International Marine Radio Company, a leading company in the marine electronics field, have an immediate vacancy for one additional engineer to work from their Tilbury Depot on service and installation of marine radio and associated equipment.

Candidates must be ex-Merchant Navy Radio Officers with a minimum of three years' sea-service and preferably have had previous experience of installation and maintenance of equipment.

Please write, giving sufficient details of qualifications and experience to:

Miss S. J. Lemmon
INTERNATIONAL MARINE RADIO COMPANY LIMITED,
 1 Peall Road, Croydon, Surrey, CR9 3AX

[3030



BOOKS



ESSENTIAL BOOKS!

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES. Includes many thousands of British, USA and Japanese transistors. 78 pages. 40p. p.p. 5 pence.

HANDBOOK OF RADIO TUBE AND INDUSTRIAL TUBE & VALVE EQUIVALENTS. 40p. p.p. 5p.

PRINCIPLES OF ELECTRICITY & MAGNETISM. Page & Adams. A course in Electricity & Magnetism for student, technician and Electronics Engineer. As recommended to technical colleges, universities and polytechnics. Fully illustrated. 532 pages. Published at £4.50. Special offer of £2.25 per copy, p.p. 30p.

CONSTRUCTORS MANUAL OF ELECTRONIC CIRCUITS FOR THE HOME. Just published. Contains many interesting and useful gadgets for the home. Full circuits, data and instructions. 50p. post free.

HOW TO MAKE WALKIE-TALKIES FOR LICENSED OPERATION. 40p. p.p. 10p.

ELECTRONIC NOVELTIES FOR THE MOTORIST. 50p. post free.

HANDBOOK OF PRACTICAL ELECTRONIC MUSICAL NOVELTIES. 50p. post free.

PRACTICAL TRANSISTOR NOVELTY CIRCUITS. 40p. p.p. 5p.

THE THEORY OF GUIDED ELECTROMAGNETIC WAVES. R. Waldron. The most comprehensive book ever written about Waveguides, Transmission Lines, Cavity Resonators, Micro-Waves etc. Published at £11.50. Special offer of £6.25 p.p. 35p.

THE SCATTERING & DIFFRACTION OF WAVES. A goldmine of information for the experimenter, amateur and scientist. Published by Oxford Univ. Press. £1.60. p.p. 15p.

THE GOVERNMENT SURPLUS WIRELESS EQUIPMENT HANDBOOK. Gives circuits data and illustrations, plus valuable information for British/USA receivers, transmitters, trans/receivers. With modifications to sets and test equipment. Latest impression £3.25 including postage.

DIRECTORY OF GOVERNMENT SURPLUS WIRELESS EQUIPMENT DEALERS. Gives details of surplus wireless equipment stores and dealers including addresses and equipment that they are likely to have available. A valuable book only 40p. p.p. 10p.

NEW BOOKS. Publication date for these three titles is Nov. 15th. Order now to avoid disappointment as the first impression of each is expected to be a sell-out.

MOBILE RADIOTELEPHONE EQUIPMENT HANDBOOK. Gives circuits data, and illustrations plus some valuable modifications for commercial radiotelephone equipment including PYE and other popular makes. £4 including postage.

HOW TO MAKE 2 & 4 METRE CONVERTERS FOR AMATEUR USE. 50p. p.p. 10p. **ADVANCED BOOK OF CRYSTAL SET DESIGNS.** 35p. p.p. 5p.

A COMPREHENSIVE WORKING HANDBOOK OF SATELLITES AND SPACE VEHICLES. A handbook that provides important data both tabular and graphical enabling space scientists, technicians and telecommunication space vehicle design, launching, orbiting etc. Includes a detailed coverage of Communications in Space. An imposing book of 457 pages. Published at £8.20. Available at £6.50. post free.

HI-FI, P.A., GUITAR & DISCOTHEQUE AMPLIFIER DESIGN HANDBOOK. Includes circuits up to 1100 watts output. Tremolo, Vibrato, and Fuzz-Box Etc. 75p. post free. ANY BOOK IN PRINT OBTAINED FOR YOU. State Author, Title Publisher. SEND S.A.E. FOR FREE LISTS OF RADIO, TECHNICAL, SCIENTIFIC, ELECTRONICS, & GENERAL BOOKS. PLEASE STATE YOUR INTERESTS.

GERALD MYERS (W.W.)
18 SHAFESBURY STREET,
LEEDS LS12 3BT.

Bookseller & Publisher
 NEW SHOWROOM & TRADE COUNTER OPEN AT
 8 HARTLEYS YARD,
 OFF TOWN STREET.

ARMLEY, LEEDS 12. (near White Horse Inn) CALLERS WELCOME.

84

CLASSIFIEDS—Continued from p. 125 ARTICLES FOR SALE—Continued

ARVAK ELECTRONICS. 3-channel sound-light converters, from £18. Strobes, £25. Rainbow Strobes, £132.—12A Bruce Grove, N17 6RA. 01-808 9096. [23

BUILD IT in a DEWBOX quality plastic cabinet 2 in. x 2½ in. x any length. D.E.W. Ltd. (W.), Ringwood Rd., Fernwood, Dorset. S.A.E. for leaflet. Write now—Right now. [76

COMPUTER CONSTRUCTORS. I.B.M. 6420 Processor complete, working when removed from site, with documentation £40 (contains 296 P.C. cards). Mullard AW3767 10K x 4 bit Core Store (modern) £40. Electric Typewriter suitable for output printer £20. Fi-Cord miniature tape recorder (Swiss) £30. S-Band amplifier and power supply (Deneo) £20.—BRIGHTON (0273) 554992 after 6 p.m. [3036

CONSTRUCTION AIDS—Screws, nuts, spacers etc., in small quantities. Aluminium panels punched to spec. of plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit boards—masters, negatives and board, one-off or small numbers. Send 6p for list. Ramar Constructor Services, 29 Shelbourne Road, Stratford on Avon, Warwks. [28

BOOKS

PRACTICAL BOOKS

World Radio and TV Handbook 1973.....	£3.00
Integrated Circuit Pocketbook, 282 pp.....	£2.65
Electronic Engineers Ref. Book, 1532 pp. Illus.....	£7.90
Electronics Pocketbook, 314 pp. Illus.....	£1.55
Foundations of Wireless and Electronics, 552 pp.....	£1.98
110 Integrated Circ. Proj. for the Home Cons.....	£1.35
110 Semiconductor Proj. for the Home Cons. 134 pp.....	£1.35
Integrated Circuit Engineering, 406 pp. Illus.....	£11.30
Integrated Circuit Systems, 236 pp. Illus.....	£3.65
Aerials (P3) TV and FM Receiving Aerials, 112 pp. Illus.....	95p
Loudspeakers and Loudspeaker Cabinets, 120 pp.....	95p
Radio Valves, 134 pp. Illus.....	95p
Stereo Handbook, 150 pp. Illus.....	£1.10
Transistors in Local Circuits, 132 pp. Illus.....	95p
Practical Oscilloscope Handbook, 118 pp. Illus.....	£1.95
Principles of Feedback Design, 246 pp. Illus.....	£1.35
Principles of Transistor Circuits, 318 pp. Illus.....	£1.65
Ques. & Ans. on Electronics, 112 pp. Illus.....	75p
Ques. & Ans. on Transistors, 96 pp. Illus.....	75p
Radio & Electronic Laboratory Handbook, 628 pp.....	£4.95
Semiconductors: Basic theory & devices, 272 pp. Illus.....	£2.65
Simplified Modern Filter Design, 193 pp. Illus.....	£2.95
Telecommunications Pocketbook, 152 pp. Illus.....	£1.35
Transistor Circuit Design Tables, 128 pp.....	£2.95
Transistor Pocketbook, 312 pp. Illus.....	£1.55
Transistors for Technical Colleges, 210 pp. Illus.....	£1.55
20 Solid state Projects for the home, 114 pp. Illus.....	£1.10
Beginners Guide to Radio, 204 pp. Illus.....	£1.10
Dictionary of Radio & TV, 380 pp. Illus.....	£1.95
Everyman's Wireless Book, 368 pp. Illus.....	£1.65
FM Radio Servicing Handbook, 206 pp. Illus.....	£3.15
Guide to Broadcast Stations, 163 pp. Illus.....	85p
The Hi-fi and Tape-recorder Handbook, 304 pp. Illus.....	£2.15
Introduction to Radar and Radar Techniques, 136 pp.....	90p
Marine Radio Manual, 622 pp. Illus.....	£4.25
The Practical Aerial Handbook, 232 pp. Illus.....	£2.85
Practical Integrated Circuits, 144 pp. Illus.....	£1.00
Practical TV Circuits, 376 pp. Illus.....	£1.95
Practical Wireless Circuits, 192 pp. Illus.....	£1.35
Practical Wireless Service Manual, 288 pp. Illus.....	£1.65
Principles of Aerial Design, 182 pp. Illus.....	£1.35
Principles of PAL Colour TV, 162 pp. Illus.....	£1.35
Principles of TV Engineering, 188 pp. Illus.....	£1.65
Ques. & Ans. on Audio, 104 pp. Illus.....	75p
Ques. & Ans. on Colour TV, 104 pp. Illus.....	75p
Radio and Audio Serv. Handbook, 284 pp. Illus.....	£3.20
Radio and Electronic Handbook, 156 pp. Illus.....	£1.35
Radio Valve and Transistor Data, 240 pp. Illus.....	85p
Television Engineers Pocketbook, 304 pp. Illus.....	£1.55
Television Servicing Handbook, 358 pp. Illus.....	£3.95
Wireless Servicing Manual, 302 pp. Illus.....	£1.65
How to make Walkie Talkies for licensed operation.....	45p
Handbook of Trans. Equivalents & substitutes.....	50p
Handbook of Tested Transistor Circuits, 64 pp.....	50p
Sound and Loudspeaker Manual, 96 pp.....	55p
Practical Transistor Novelty Circuits, 64 pp.....	50p
Hi-fi, P.A., Guitar, Discotheque Ampl. Design Hand- book.....	85p
Electronic Novelties for the Car Owner.....	60p
2nd Book of Trans. Equivalents & Substitutes.....	85p
High Fidelity Loudspeaker Enclosures.....	50p
Radio Servicing for Amateurs.....	30p
Radio, T.V. and Electronics Data Book.....	30p
Transistor Circuits for Radio Controlled Models.....	50p
Modern Transistor Circuits for Beginners.....	50p
Manual of Transistor Audio Amplifiers.....	50p
Practical Car Radio Handbook.....	40p
1-2-3-4 Servicing Stereo Amplifiers, 240 pp. Illus.....	£2.65
Transistor TV Servicing Guide, 128 pp. Illus.....	£2.35
101 Ques. & Ans. about AM, FM & SSB. Illus.....	£1.90
99 Ways to improve your S.W. listening, 144 pp.....	£1.95
99 Electronic Projects, Illus.....	£1.65
Radio Handbook, 960 pp. Illus.....	£7.95
Transistorised Radio Control for Models.....	£2.65
Making and Using Electronic Oscillators, 128 pp.....	£2.15
Making and Repairing Transistor Radios, 128 pp.....	£1.15
ABC's of Hi-fi and Stereo.....	£1.40
ABC's of Electrical Soldering.....	£1.55
Car Radio Servicing Made Easy, Illus.....	£1.45
Electric Guitar Amplifier Handbook.....	£1.75
FM Multiplexing for Stereo.....	£1.65
Hi-fi Stereo Handbook.....	£2.25
Hi-fi Stereo Servicing Guide.....	£1.90
How to repair small Appliances.....	£1.35
Making and Repairing Transistor Radios, 128 pp.....	£1.25
Radio Spectrum Handbook, Illus.....	£3.30
Servicing Digital Devices.....	£1.45
Tape Recoding Servicing Guide.....	£1.95
Transistor Radio Servicing Made Easy, 144 pp.....	£1.85

WHEEL PUBLICATIONS (WWA)
41a Adelaide Grove, London W12 OJH.

CLASSIFIEDS—Continued from p. 126

ARTICLES FOR SALE—Continued

"KINGDOM ELECTRONICS" offers mono power amplifier, cca. 10 Watts, with gain control, meter and Test Oscillator, 0-100KHz, £20 and £3 carr. On view at "Westwoods", 49 George Street, Oxford. Mail orders to 4 Harberton Mead, Headington, Oxford. [3059]

LARGE quantity test equipment receivers transceivers, meters, various P.S.U.'s; over 1,000 items for immediate disposal. S.A.E., plus 25p, refunded on purchase over £2.00. F.J.C., Colnemill, Alvington, Glos. [2881]

LADDERS 8ft. 10in. closed—22ft. 6in. extended £15.64, delivered. Home Sales Ladder Centre, Haldane (North), Halesfield (1), Telford, Shropshire. Tel. 0952 586644. [122]

OLIVETTI P203 PROGRAMMA—OFFICE COMPUTER/TYPEWRITER, four years old. Regularly maintained by manufacturers, now surplus to requirement. Excellent condition. Reasonable offers to: Shirley Herridge, Mildenhall (0638) 713631. [3082]

CLASSIFIEDS—Continued on p. 128

CCTV, Audio and Projection Engineers

The opening of our York Theatre in September will see the opening of Europe's most sophisticated conference complex. Technically it offers the most comprehensive range of audio-visual equipment including broadcast quality cameras, helical Scan V.T.R.'s and simultaneous translation systems. Link this with back-up facilities that include social co-ordinators, secretarial services, bars, restaurants, solarium and sauna and you will see the degree of sophistication our conference delegates may expect.

We have found our Chief Engineer and we are now seeking the above people to assist him. They will be concerned with the operation and maintenance of the equipment and the provision of specialised knowledge to the team.

Applicants should also be sufficiently interested in the full range of audio-visual activities to become effective in production activities.

In return, we offer a salary on a scale between £3000 to £4000 p.a. depending on age, qualifications and experience, and excellent fringe benefits. These include non-contributory pension and sickness schemes, three weeks' holiday, and free meals whilst on duty.

Please phone or write to Mike Woolfe, Personnel Manager,
Heathrow Hotel, Bath Rd., Hounslow, Middx.
Tel: 01- 897 2419



The Heathrow
Cares for the people who count. You.



Medical & Biological Instrumentation Ltd.,
Brunswick Road, Cobbs Wood Estate,
Ashford, Kent.

Project Engineer

Required by a leading company in the new and expanding field of air ionization. Qualifications to BSc. or equivalent standard together with several years design experience in electronics. A knowledge of electrostatics, E.H.T. techniques, product and value engineering would be advantageous. The successful applicant will develop instrumentation from concept to production and be expected to become acquainted with relevant engineering and physical topics.

Development Engineer

Also required to assist project engineers in the design of a range of interesting products in the fields of faradic muscle stimulation, metal detection and ionization. Qualifications BSc. or HNC and practical electronics experience.

The above staff positions are with a rapidly expanding international company recently moved to larger premises in Ashford, London (Sales), and Ireland. The company operates a superannuation scheme, and a staff canteen.

Write giving relevant details to Mrs. H. Kennedy:

**Southall
College of Technology**

Beaconsfield Road, Southall,
Middlesex.

Telephone:
01-574 3448

CEI PART II
Options by
PART-TIME STUDY

in
Electronics — Telecommunications etc., The Engineer in Society
Apply: Head of Dept. of Electrical & Electronic Eng.

3017

**TRAIN FOR SUCCESS
WITH ICS**

Study at home for a progressive post in Radio, TV & Electronics. Expert tuition for C & G (Telecoms Techn's Cert and Radio Amateurs') RTEB, etc. Many non-exam courses including Colour TV Servicing, Numerical Control and Computers. Also self-build kit courses-valve and transistor.

Write for FREE prospectus and find out how ICS can help you in your career. ICS, (Dept 734 U) Intertext House, London SW8. [3000]

Middlesex Polytechnic

Technical Assistant T5

To work as a member of a research group in the field of telecommunication. Specialised knowledge and experience in audio systems, and electro-acoustics and familiarity with current electronic development practices is essential. You will be expected to assume some responsibility for circuit design in collaboration with consultants, and a capacity to integrate with an existing research fellow and his team is necessary.

Salary £1,908 - £2,205 (under review)

Write for an application form to the Senior Administrative Officer, Ref: WW/10, Middlesex Polytechnic, Crouch End Hill, London N8.

[3018]

ARTICLES WANTED

WANTED

PLUGS AND SOCKETS

Plessey/Painton Mk. IV,
Mk. VI, Mk. VII
UK-AN Multicon
H.D. Multicon
159 Series

Send lists to:

J. SALLIS,
Oatlands Farm, Brighton Road,
Shermanbury, Horsham, Sussex.
Tel: 710-515.

[2972]

**ELECTRO-TECH
COMPONENTS LTD.**

Are buyers of all types of electronic components and equipment. They will be pleased to view clearance stocks anywhere in Great Britain at one or two days notice
and negotiate on the spot!

**ELECTRO-TECH
COMPONENTS LTD.**

315/317 Edgware Road, London, W.2
Tel: 01-723 5667. 01-402 5580

[2977]

WE PURCHASE

All types of Electronic Components and Test Equipment. Cash waiting:

TRANNIERS

1 Dockyard, Station Road, Old Harrow, Essex.
Tel No. (027-96) 37739

[3080]

**WE BUY SURPLUS ELECTRONIC
COMPONENTS AND TEST EQUIPMENT,
IN QUANTITY.**

LINWAY ELECTRONICS

42 Spencer Avenue, Hayes,
Middlesex UB4 0QY.

CONTACT US - YOU'LL NOT REGRET IT!
Tel. No. 01-573 3677 [3078]

**CLASSIFIEDS—Continued from p. 127
ARTICLES FOR SALE—Continued**

COLOUR. UHF and TV SPARES. Colour and UHF lists available on request. New Philips G6 single standard convergence panels complete, incl. 16 controls, coils, P.B. switches, leads, etc. and circuit data £3.75, or with yoke £5.00. P/P 30p. New Colour Scan Coils, Mullard or Plessey plus convergence yoke and blue lateral, £10.00. P/P 40p. Mullard AT1025/05 Convergence Yoke, £2.50. P/P 25p. Mullard or Plessey Blue Laterals, £1.25. P/P 10p. BRC 3000 type Scan Coils, £4.00. P/P 40p. Delay Lines DL20, £3.50. DL1E, DL1, £1.50. P/P 25p. Lum. Delay Lines, 50p. P/P 15p. EHT Colour Quadrupler for Bush Murphy CTV 25 111/174 series, £8.25. P/P 25p. EHT Colour Tripler IIT TH25/1TH suitable most sets, £2.00. P/P 25p. KB CVCI Dual Stand. convergence panels complete incl. 22 controls, £3.75. P/P 35p. CRT Base Panel, £1.75. P/P 15p. Makers Colour surplus/salvaged Philips G8 panels part complete: Decoder incl. 1/C, £2.50. IF incl. 5 modules, £2.50. T. Base, £1.00. P/P 25p. CRT base, 75p. P/P 15p. GEC 2040 panels, Decoder, £3.50. T. Base, £1.00. RGB and Sound, £1.00. P/P 25p. Pye CT70 Colour LOPT assembly incl. EHT output and Focus Control, £3.50. P/P 35p. B9D valve bases 10p. P/P 6p. VARICAP TUNERS. UHF ELC 1043 NEW, £4.50. Philips VHF for Band 1 and 3, £2.85 incl. data. Salvaged VHF and UHF Varicap

tuners, £1.50. P/P 25p. UHF TUNERS NEW, Transistorised, £2.85 or incl. slow motion drive, £3.85. 4 position and 6 pos. push-button transistd., £4.95. UHF/VHF basic integrated tuners, £3.25. Cydon UHF valve tuners, £1.50. All tuners P/P 30p. Transistd. UHF/VHF IF panels salvaged, £2.50 P/P 25p. MURPHY 600/700 series complete UHF Conversion Kits incl. tuner, drive assy., 625 IF amplifier, 7 valves, accessories housed in cabinet plinth assembly, £7.50 P/P 50p. SOBELL/GEC 405 625 Dual standard switchable IF amplifier and output chassis incl. cct., £1.50 P/P 35p. THORN 850 Dual standard time base panel, £1.00 P/P 35p. PHILIPS 625 IF amplifier panel incl. cct., £1.00 P/P 30p. VHF turret tuners AT7650 incl. valves for K.B. Featherlight, Philips 19TG170, GEC 2010, etc., £2.50. PYE miniature incremental for 110 to 830, Pam and Invicta, £1.95. A.B. miniature with UHF injection suitable K.B., Baird, Ferguson, 75p. New fireball tuners Ferguson, HMV, Marconi, £1.90 P/P all tuners 30p. Large selection LOPTs, Scan Coils, FOPTs available for most popular makes. PYE/LABGEAR transistd. Masthead UHF Booster, £5.75. Power Unit, £4.65 P/P 30p or Setback battery operated UHF Booster, £4.65 P/P 30p. MANOR SUPPLIES, 172 WEST END LANE, LONDON, N.W.6 (No. 28, 59, 159 Buses or W. Hampstead Bakerloo and Brit. Rail). MAIL ORDER: 64 GOLDERS MANOR DRIVE, LONDON, N.W.11. Tel. 01-794 8751.

TENDERS

SLOUGH CORPORATION

**SALE OF
MOBILE RADIO
EQUIPMENT**

Offers are invited for the following equipment:—
One Base Station F.27 with 35 No. Cambridge FM.10 mobile radio sets and one portable hand set.

These sets are KHZ channel spacing and are not re-licensable for normal commercial use without modification. The equipment has been in use until recently, has been serviced regularly and is in good working order. The equipment can be inspected by arrangement with the Storekeeper, Highways Depot, Windmill Road, Slough—Phone Slough 23881, Ext. 315.

Offers to be made in a plain, sealed envelope endorsed "Mobile Radio Equipment" and addressed to the Borough Engineer, Town Hall, Slough, to be received not later than noon on 16th October, 1973.

[3025]

PRINTED CIRCUIT BOARD large supplies of glass fibre available. 1/16 in single sided one ounce copper 2p per 3 sq. inches (under 1 ft). 75p per sq. ft. (over 1 ft). 1/16 in double sided one ounce copper 1p per sq. inch (under 1 ft). £1 per sq. ft. (over 1 ft). Please add 10p per sq. foot postage and packing. We can cut to your size at 1p per cut. Solid State Lighting, (Dept. WW), 47 Hercules Rd., Norwich NOR 66M. [16]

PRINTED Circuit Board in 6 widths: 2 in., 2½ in., 3 in., 3½ in., 4 in. and 5 in. x any length; 1/16 in. single-sided fibreglass, 2p per 3 sq. in. Double-sided 1p per sq. in. P & P 5p per order. SAE quotations for other sizes and quantity discounts.—J. Knopp, 11 Connaught Gardens, Braintree, Essex, CM7 6LY. Tel. Braintree 25254. [15]

RADIO LABORATORY EQUIPMENT. Marconi Standard Signal Generator Type TF 867a. 15 KH to 30MH in first class condition with Terminating unit, this instrument is in laboratory accuracy. Price £130. Cintel Square wave and Pulse Generator 5H to 250KH. .05 to .3 Micro secs., variable impedance output, Sync. Input and CRO Sync. output. In first class condition. £30. Cossor 1039 Mk. 2 Oscilloscope. Price £10. All the above units have Manuals and are included in the prices. Airmec VTVM Type 784 with probe and in first class condition and accurate. £10. Kelvin Wheatstone Bridge 0.0001 ohm X by 10-1000. Incorporates light spot Mirror Reflecting Galvanometer. £45. Mechanical and neon BCD Scaling counter, incorporates 1 Volt Square wave 3CPS, also mains frequency reference indicator. £12. Stop Watch. £10. Pye Decade resistance box incorporates 4 decade switches 10 to 100K. Mullard RC Bridge. £10. Mombrex RC Bridge. £8. Phone for appointment. George Hill, Electrical Engineers, 19 Station Road, Tadcaster. Phone 2253. [3069]

SMALL electronic Manufacturing Company (mixers) with excellent record for sale. Ideal opportunity for technically experienced entrepreneurs. Approx. £2,500. Box WW 3114.

TELEVISION: Valves, tubes, UHF transistors, tuners. Any 10 valves 85p, 50 £3. ECC82, EY86/7, DY86/7, EF80/85/183/184. PCC84/89/189, PC97, PC86/88, PCF80/86/801/805, PCL82/84/85, PL36/504, PY81/82/800/801, 30L15, 30C15, 19ins. (47cm) tubes type A47-14W and equivalent £2.50 each. UHF transistor tuner £2.00 each. Postage 10p, carriage £1. Electronic Mailorder, Ramsbottom, Bury, Lancs. [3063]

For ££'s more profit just look at these prices!


Big Savings on Valves		Goods Price		Goods Price		Goods Price		Goods Price	
Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
DY 87	24p	PY 88	25.5p	AF 139	37p	BC 158	8p	BF 258	40p
DY 802	24p	PY 500A	54p	AF 178	43p	BC 159	12p	BF 337	28p
EB 91	14.5p	PY 800	24.5p	AF 180	40p	BC 173	18p	BFY 50	22p
ECC 82	25.5p	PC 900	22.5p	AF 181	40p	BC 178B	20p	BFY 52	20p
EF 80	27p	Semi-Conductors		AF 239	45p	BC 182L	12p	BSY 51	25p
EF 183	31.5p	AC 127	15p	BA 145	14p	BC 183L	12p	BY 126	11p
EF 184	31.5p	AC 128	12p	BC 107	10p	BC 214L	15p	BY 127	12p
EH 90	28.5p	AC 141K	30p	BC 109B	9p	BD 124	70p	E. 1222	30p
PCC 89	34p	AC 142K	30p	BC 109	11p	BD 131	45p		
PCC 189	35.5p	AC 151	20p	BC 113	22p	BF 115	20p		
PCF 80	29p	AC 154	18p	BC 116	22p	BF 160	20p		
PCF 86	35.5p	AC 155	16p	BC 117	20p	BF 167	19p		
PCF 801	39p	AC 156	19p	BC 125B	18p	BF 173	20p		
PCF 802	35p	AC 176	19p	BC 132	25p	BF 178	35p		
PCL 82	34p	AC 187	17p	BC 135	20p	BF 179	40p		
PCL 84	28.5p	AC 187K	20p	BC 137	25p	BF 180	30p		
PCL 85	32.5p	AC 188K	20p	BC 138	40p	BF 181	30p		
PCL 86	32.5p	AD 142	45p	BC 142	26p	BF 184	21p		
PFL 200	44.5p	AD 149	37p	BC 143	30p	BF 185	21p		
PL 36	49p	AD 161	34p	BC 147A	8p	BF 194	8p		
PL 84	22p	AD 162	34p	BC 147B	8p	BF 195	15p		
PL 504	1p	AF 114	22p	BC 148	8p	BF 196	20p		
PL 508	53.5p	AF 115	20p	BC 149	12p	BF 197	17p		
PL 509	86p	AF 116	20p	BC 153	20p	BF 200	25p		
		AF 117	22p	BC 154	20p	BF 218	35p		
		AF 118	42p	BC 157	10p	BF 224	35p		

EHT RECTIFIER TRAY ASSEMBLIES	
Type	Goods Price
1TH Decca Col.	£4.25
2TQ 1400 + 950 Mk II	£1.75
2TAK 1500 5 Stick	£1.90
2DAF 1500 3 Stick	£1.70
2HD 950 3 Stick M1	£1.65
TCQ Pye/Ekco	£3.35

12 MONTHS GUARANTEE

COLOUR TUBES	
Type	Goods Price
19" A49191X C.C.R.T.	£38.70
20" 510DJB22 C.C.R.T.	£39.80

FULLY GUARANTEED

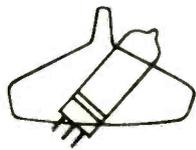

Valves packed individually subject to settlement Discount 5% of "Goods" content 7 days and 2% monthly.
 New Price List from 28th April 1973
 Combined Precision Components (Preston) Ltd.
 194-200 North Road, Preston PR1 1YP
 Telephone 55034 Telex No. 67129

"AGENTS FOR TOSHIBA"

PRICES SUBJECT TO 10% VAT

DIGITAL CLOCK COMPONENTS
 4/6 Digit Clock Chip £9.00; 6 Minitron Displays £6.00; 1 Digit Driver £1.50; 1 Segment Driver £1.50; Minitron Sockets 25p each; 2N 7447 Drivers £1.20 each.

LOW COST LED LAMPS
 Red 3mm dia. 25p each; Red 4.45mm dia. 35p each; Green 3mm dia. 68p each; Green 4.45mm dia. 68p each.

CALCULATOR DISPLAY
 0.12 inches Character Height Flatpack £2.00 each.

SLIDER SWITCHES
 1 pole 2 position—Miniature 14p each; 4 pole 2 position 14p each; 2 pole 3 position 21p each; 1 pole 4 position 23p each.
 U.K. Postage and packing 10p. Overseas 25p.

VAT 10%

PERDIX COMPONENTS LTD.
 Dept. WW73
 31 Green Lane, Chislehurst, Kent [3093]

Trampus electronic

Add 10% VAT to prices. All Brand New & Money Back Guaranteed.

DIGITAL INDICATORS 7 seg. DP 5v Filament type & socket £1.45. LED TYPE 1" 0.8 DP 14 pin DIL £2.49. 4" £2.29 ea 6" £2.19 ea 10" £2.15 ea 4 DIGIT LED DIL/magnifier £11.
LIGHT EMITTING DIODES & data 1" DIA type & panel clip RED 33p. GREEN 73p. TL209 1" DIA red 25p. INFRA RED £1.10. Dp9 isolator £2. TGS308 Gas/smoke detector £1.69. ULTRASONIC TRANSDUCERS £2.
 INTEGRATED CIRCUITS with data if req.



ic digital clock

MOS/LSI chip. 28 pin. 4 or 6 digit. 12 or 24 hr at flick of switch. Chip with DIL socket £13. PCD £1.69 KITS. 4 digit £21.49. 6 digit £25. IC LITF SWITCH 11-20v 40 ma relay/TTL drive. Photo amp/trigger/driver 87p ea. 10 77p ea. Photo amp only 39p. IC DIGITAL VOLTMETER £12. OVM 1P MPX £6. Data booklet 39p. 741 DIL 8 pin 28p. 709 19p. di1 29p. 710 33p. 748 29p. REGULATORS 1.5A 5 to 20v £1.49. 723 57p. 555 TIMER 89p. ZN414 RECEIVER Ferranti £1.19. Dual Pre amp £1.67. 3.5W AF AMP £1.24. STEREO DECODER IC FOR FM TUNERS MC1310P £2.69 KIT £3.45.

749 TTL BRAND NEW 100+ LESS 10%

Gates 7400/1/2/3/4/5/10/20/30/40/50 etc 14p ea 7413 27p. 7441 73p. 7447 99p. 7470 7472 28p. 7473 7474 36p. 7475 60p. 7476 32p. 7490 59p. 7492 67p. 7490 69p. 7483 £1.10. 7486 37p. 7493 73p. 7494 83p. 7495 83p. 7496 89p. 74121 45p. 74141 89p. 74150/31/32/33 £2.39. 74196 £1.59.

C.MOS logic in new lists. DIL PLUGS IC case 10mm high 16 pin 35p.
DIL SOCKETS low/high profile. 8/14/16 pin 13p. 100 10p ea. SEMICON-DIL SOCKETS low/high profile. 8/14/16 pin 13p. 100 10p ea. IN914 3p. DIACRS 25 — less 10%. ZENERS 02Y88 400 mW 7p. IN4001 3p. IN914 8p. 50v. "A Bridge 23n. 2N3055 40p. BC107 8p. BC108 8p. BC109 8p. BC147 8p. 10p. BC167/8/9 13p. BC3055/152 13p. BC182 3/4 10p. BC212 3/4 11p. BCY70 72 13p. BD131/2 55p. BF650S/152 13p. TIS43 UJT 24p. 2N708 11p. 2N2369 12p. 2N2926 8p. 2N3055 17p. 2N3055 40p. 2N3614 55p. 2N3702 3/4 5/8 7 8/9 10/11 11A 9p. FETS 2N3819 27p. 2N3823 29p. 2N3868 UHF 59p. 2N3904 400V 1A 23p. 4A 55p. TRANSFORMERS JA 6 8 12v. EI CAPACITORS 50v 10. 50. 100 of 5p ea. 50 — 4n ea. 22p of 0.1uf 3p. RESISTORS 1W 5% 13p ea. PRESETS 5p. CARBON POTS 12p ea. Dual 40p. Switch 12p.
 All DIL plugs 13p. sockets 5p. Veng at normal price. DILD PCB resist marking pen 69p. Copper board 12" x 8" SRBP 40p. FeCetchPAK 19p. All Antex ions at RRP

FLUORESCENT LIGHTS 12VOLT £2.79

8 WATT with diffuser, on/off switch. Fully built 13" long TRIO and COOAR communications and Hi Fi retailers. ELECTRONIC ORGANS imported. Full facilities from E67. ELECTRONIC CAR IGNITION KIT PW capacitor type E6.67. VAT customers MUST ADD 10% (1) to above prices.

FREE CATALIST S.A.E. DATA SHEETS 8p ea. S.A.E. P&P 8p CWO to PO BOX 29, BRACKNELL BERKS.


EDDYSTONE V.H.F. & U.H.F. COMMUNICATIONS RECEIVER TYPE 770R. 19 mc/s to 165 mc/s C.W. A.M. N.F.M. F.M. Mains, in as new condition, £95. carr. £3. 770U 150 mc/s to 500 mc/s F.M. or A.M., Mains, in as new condition, £95. carr. £3. **RACAL UNIVERSAL COUNTER/TIMER SA550 (CT488).** 8 digit inline readout, £85. carr. £3. **AVO MODEL 3 VALVE TESTER** in wooden Transit Case, £17.50. carr. £2.50p. **INDIVIDUAL POCKET DOSIMETERS.** Latest Government Release Type 2A and 3, 11,000 available individually wrapped in boxes of 50. Also 300 Charging Units No 1 for above Dosimeters, individually boxed, both are absolutely Brand New, supplied one box of 50 Dosimeters with one Charger £14, p/p £1. 25 and one Charger £9, p/p £1. Singly 50p, p/p 10p. Chargers £2.50, p/p 25p. Probable cost of one Dosimeter £10. Larger quantities by quotation.
MARCONI SIGNAL GENERATOR TYPE TF867 15KHz-30MHz. £75. carr. £3.
JOHNS RADIO
 424 BRADFORD ROAD, BATLEY, YORKS.
 Tel: Batley 7732 [35]

COMPUTER EQUIPMENT

Units available from RCA 301 computer: 3" Tape 2400' 70p (25p); 1/2" Tape 1800' 60p (20p); Also Peripherals, Tape Decks £16.50 (£1.50). Test equipment TF1449 Sig. gen. 85kHz-25MHz in 8 ranges. From £12 in average condition to £22 in excellent condition (£2). 5MHz Crystal calibrator £6 (£1); Field telephones complete in carrying case £2.50 (50p); pair for £4.50 (75p); Sig. gen. type 12/2 35kHz-18.3MHz in 8 bands AM-FM-CW, 36" long dial, inbuilt crystal calibrator at 100kHz & 2MHz; 8 diff modulation frequencies, £55 (£2); Tape amplifiers, 2x ECC83, EL84, E280, 20uV i/p for 3 watts into 30hm o/p. £1.80 (40p); or in case with 7x4" speaker & non-standard deck £3.30 (£1.10 up to 200 miles. £1.50 over; Isotope developments EHT supply type S32D. Provides stable 0-3kV @ 5mA, brand new £44 (£2); Assorted resistors in bulk: 500 £1.10 (15p); 20,000 £27.50 (£1.20); 100,000 £88 (£2); Computer panels: 71b £2.20 (40p); 561bs £13.20 (£1); High quality panels, 12 for £2.00 (30p); 100 for £16.50 (75p); 1,000 £82 (£3); 71b Bargain parcels, contain hundreds of R's, C's, xtals, pots, switches, panels, etc., £1.80 (40p); 561b ditto £12 (£1).

GREENWELD ELECTRONICS (W4), 24 Goodhart Way, W Wickham, Kent; 38 Lower Addiscombe Rd., Croydon. Shop at 21 Deptford Broadway, SE8. Tel: 01-692 2009. [311]

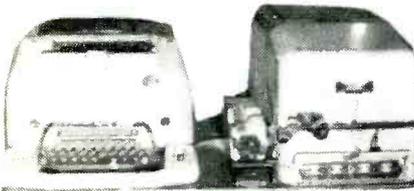**SURPLUS BARGAINS
KLEINSCHMIDT S.C.M.
TELEPRINTER OUTFITS**



Comprising Teletypewriter (page printer) type TT-2718/FG (known as Kleinschmidt 160) Reperforator-Transmitter (tape printer) type TT-272A/FG with table FN-65/FG. Both units are supplied with change wheels for 45 & 50 Bauds the whole equipment operates on 115 or 230V 50cycles in very choice condition £55. (carr £4).

VARIACS 25amp 0-270v as new less handle & cover £22.
(E2) TRANSFORMERS 240/110.3KVA New £15. (F1 50) Constant Voltage 500watt £18 (E1) ditto 125 watt £8 (75p). FRACMO MOTORS 240v AC 1/2hp 6000 rpm £4.50 (37p) AVCO CT38 Electronic Meters £18. (E1) BC221 £12. (E1) AMPEX VIDEO TAPE 2in x 1670 new £9 (50p) SINTERED NICKEL CADMIUM ACCUMULATORS 1.2v 7a.h. size 90x30x60mm with electrolyte and instructions 80p (8p) PRINTED CIRCUIT KITS £1.25. (21p). CT53 £10. (E1). FERRIC CHLORIDE 25p a1b (16p) 10lbs £2.50 (paid) KENT CHART RECORDERS 115vAC £20 (E1 50) MULTI-POINT £30. TF866 (Q Meter) Magnification Meter from £15. (E1). FRIEDEN FLEXOWRITERS £80 (E4) tape to suit £1. for 3. RACAL MA168 DUAL DIVERSITY Switch new £50. only VEEDER ROOT 4 Digit resettable counters 115v £1.25 (8p) ELECTRONIC TIMER KIT. 0.8secs to 100sec. comprises A.E.I. Transistors Module. Relay, & all electrical components for 115 or 240c. A.C. operation £1.75 (16p). Loads of surplus to clear. Large S.A.E. for list ALL PLUS VAT.

CASEY BROS.

233-237, Boundary Road, St. Helens, Lancs. 86

CARBON FILM RESISTORS

High Stab. 1/10 or 1/20 5%, 1p, 62p/100, £4.50/1000 (2252-2M2) E12
RESISTOR KITS 1052-1M E12 SERIES:
10E12KIT. 10 of each value (Total of 610) £3.10
25E12KIT. 25 of each value (Total of 1525) £7.20

FREE CATALOGUE ON REQUEST

Metal Film 1W 5%, 1p, £1.10/100; £8.25/1000
15E12 Kit (1052-1M) Total of 915 £8.00

C.W.O. P. & 2. 10p on orders under £5. Overseas extra.

BH COMPONENT FACTORS LTD.
Dept. WW, 61 Cheddington Road, PITSTONE,
Leighton Buzzard, Beds., LU7 9AQ. [3034]

PRINTED CIRCUITS

High Speed Prototype Service 1-10 Boards
—48 hours Door to Door.

WHELDON LIMITED
GREENFORD, WINDMILL HILL,
WROTHAM HEATH, KENT.

Hillfort STD 073287 222 Crayford 24530 [3042]

PRECISION

POLYCARBONATE CAPACITORS
Fresh stock — Fully tested

Close tolerance capacitors by well-known manufacturer. Good stability and very low leakage. All 63V d.c.

0.47µF:	±5%	30p;	±2%	40p;	±1%	50p
1.0µF:	±5%	40p;	±2%	50p;	±1%	60p
2.2µF:	±5%	50p;	±2%	60p;	±1%	75p
4.7µF:	±5%	70p;	±2%	90p;	±1%	115p
6.8µF:	±5%	95p;	±2%	115p;	±1%	150p
10µF:	±5%	110p;	±2%	140p;	±1%	180p
15µF:	±5%	160p;	±2%	210p;	±1%	270p

NEW! TRANSISTORS. BC 107, BC 108, BC 109. All at 9p each; 6 for 50p; 14 for £1.00. All brand new and marked. May be mixed to qualify for lower price. AF178 at 35p each; 3 for 95p.

POPULAR DIODES. IN914 at 7p each; 8 for 50p; 18 for £1.00. IN916 at 9p each; 6 for 50p; 14 for £1.00. 1S44 at 5p each; 11 for 50p; 24 for £1.00. All brand new and marked.

SPECIAL OFFER—400 MW ZENERS. Values available 4.7, 5.6, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15V. Tolerance ±5% at 5mA. All new and marked. Price 9p each; 6 for 50p; 14 for £1.00 SPECIAL 6 off EACH Voltage (66 ZENERS) £4.25.

RESISTORS—Carbon film 5% 1/2 watt at 40c. Range from 2.2Ω to 2.2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise —All at 1p each; 8p for 10 of any one value, 70p for 100 of any one value. Special development pack—10 off each value 2.2Ω to 2.2MΩ (730 resistors) £5.00.

TANTALUM BEAD CAPACITORS—Values available 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 35V, 10µF 25V, 15µF 20V, 22µF 15V, 33µF 10V, 47µF 6V, 100µF 3V—all at 9p each; 6 for 50p; 14 for £1.00. Special pack—6 off each value (78 capacitors) £5.00.

440V AC CAPACITORS—0.1µF. Size 1 1/2" x 1 1/2" 25p each. 0.25µF. Size 1 1/2" x 1 1/2". 30p each. 0.5µF. Size 1 1/2" x 1 1/2". 35p each. 1.0µF. Size 2" x 1 1/2". 45p each. 2.0µF. Size 2" x 1 1/2". 75p each.

SILICON PLASTIC RECTIFIERS 1.5 AMP—Brand new wire-ended DO27. 100PIV at 8p each or 4 for 30p; 400PIV at 9p each or 4 for 34p; 800PIV at 14p each or 4 for 50p.

P.E. SCORPIO—1µF 440V a.c. capacitor listed above as recommended by the Author for use in place of 2 x 0.47µF 1000V d.c. discharge capacitors C6 and C7. Improved reliability. Alternatively, 2 x 0.47µF 440V a.c. may be supplied at 35p each. These capacitors are also suitable for systems recently published in P.W. and W.W. 5p post and packing on all orders below £5.

MARGO TRADING
Dept. D9, THE MALTINGS, STATION ROAD, WEM
SALOP

Please add 10% V.A.T. to your order effective April 1st [3033]

Electronic Test Equipment

- ANALYSERS**
Airmec 248 Wave Analyser. 5-300MHz ... £85
Davian D100 IC Analyser. NEW. Complete with handbook ... £55
- AMPLIFIERS**
Cossor 1439 Wide Band. 40-220MHz ... £45
- DIGITAL COUNTERS**
Gresham Lion GFT.15 BRAND NEW. 6 digit. 0-15MHz. Solid state Counter/Timer. Measuring Freq. Pulse width. Period, Ratio, Time, Random and Regular counts, Scaling, Mark Space ratio, Totalising Phase angles etc. 3 Variable inputs. Complete with handbook and Input leads Normal price £325. Ask for full details
- Venner TSA334 4 Digit Counter/Timer. 9999. 15Hz-1.2MHz ... £45
- DIGITAL VOLTMETERS**
Solartron LM1620 NEW. 4 Digit. 0-1000V. Sensitivity 100µV. ... £85
Dynamco DM2001 5 Digit. 1999.5. 50µV-2kV. 0.025% f.s.d. ... £275
- METERS**
B.P.L. RM175LZ Megohmmeter. ... £75
H/P 410B Multi Function Meter. 1-300V AC. 1-1000V DC ... £50
H/P 400DR Vacuum Tube Voltmeter ... £45
Marconi TF1300 Vacuum Tube Voltmeter ... £40
Marconi TF142F Distortion Factor Meter ... £50
Phillips GM6012 True RMS Millivoltmeter ... £25
Radiometer BKF6 Distortion Meter. Distortion range 0.3%-100%. Freq. 18Hz-200kHz ... £150
- OSCILLOSCOPES**
Marconi TF1300 0-15MHz. Single Beam ... £60
Marconi TF1311 0-15MHz. Dual Beam ... £75
Solartron CD3220 0-40MHz. With wide band Amp. CX1259 ... £125
- PEN RECORDERS**
Bausch & Lomb SE VOM Flat Bed Chart Recorder. Voltage 1mV-500V. Current 0.01-100mA. Ohms. 1ohm-100kohms ... £175
H/P 17108 Plug on Recorder Time Base. Sweep ranges 0.1: 0.2: 2: 20mV/cm. ... £50
H/P 7701-04A Recorder complete with 8806B Plug in ... £300
- POTENTIOMETER**
Tinsley 4025 Potentiometer c/w MR4 Galvo ... £100
Tinsley 3387B Potentiometer ... £85
- POWER SUPPLIES**
Farnell TSV70 Variable P.S.U. 0-35V. 10A. 0-70V 5A ... £65
K.S.M. HVV5025 Stabilised P.S.U. Variable to 5kV. ... £75
- SIGNAL SOURCES**
H/P 962D Sweep Oscillator. Freq. 2GHz-4GHz ... £350
H/P Automatic and Manual sweep 0-200MHz ... £350
Optimization RCD1 5 Decade Oscillator. 0.1Hz-100kHz. 0.2% Solid State ... £85
10% VAT to be added on all items. Carriage extra at cost.

OTHER equipment available. Send for up-to-date list.
Good quality instrumentation always needed. Contact us before you dispose of your surplus equipment.

MARTIN ASSOCIATES
GREENSWARD LANE, ARBORFIELD,
NR. READING, BERKS.
TELEPHONE: Arborfield Cross (073 526) 610
or West Forest (0734) 74641. [3050]

NEW FROM ELBON

L.E.D.'s (Red Emitting) Ideally suited for panel Indicators
Price only: 33p each or £2.50 for 10

Light SENSITIVE SWITCHES
Two types available giving wide operating voltages:
LITE-IC2 11V-20V working — £1 each — £8.50 for 10
LITE-IC3 20V-30V working — £1 each — £8.50 for 10

Applications include: Relay, Triac or Logic Drive, automatic light switching and door control, beam break detection — burglar alarm, batch counting and code reading.

BARGAIN PACK!
2 LITE-IC2, 2 LITE-IC3 and 5 LED's all for £5.00

ALL PRICES INCLUDE VAT, PACKING AND CARRIAGE
Please send C.W.O. to:
LITE-IC, ELBON,
SUMMERFIELD, THE CRESCENT, WEST WITTING, SUSSEX

ECONOMISE ON SEMICONDUCTORS

All Prices include VAT

LED red Hewlett Packard	1+	10+	25+
709C Op Amp	8 or 14 pin DIL	32	30
723C Regulator	14 pin DIL	70	65
7741C Op Amp	8 pin DIL	34	32
48C Op Amp	8 pin DIL	37	35
BC 107	108	109	8
7400 02 03	17	7413	27
7404 05	18	7441	90
7410 20 30	17	7473	43
BC109C	9	BC212	11
BC177	13	BC214	11
BC178	13	BF244B	27
BC182	10	2N3055	47
BC184	10	IN914	5
TAD 100 Radio IC + IF Filter and Data	1+	5	7
5% 1/3W High stability Carbon film resistors 10-1M	E12 values 1p each. 10 mixed 9p. 10 same 8p.		

SILICON SEMICONDUCTOR SERVICES
41 Dunstable Road, Caddington, Luton, LU1 4AL [3086]

1/2 PRICE
SALE OF ANTI-WICKING TWEEZERS

Model 88
A.W.G 16, 18
20, 22, 24, 26.
28, 30

60p
30p

Model 77
A.W.G 16, 18
20, 26, 28.

10p
20p

ANTEX **order NOW!**
C.W.O. to...

ANTEX LTD, MAYFLOWER ST. PLYMOUTH, DEVON.

SILICON DIODES

FACTORY TESTED

IN4148	100 pcs for	£2.50
	500 pcs for	£9.00
	1000 pcs for	£14.00
	5000 pcs for	£52.50
IN4148E (40 volt version of IN4148)	100 pcs for	£1.50
	500 pcs for	£7.00
	1000 pcs for	£10.50
	5000 pcs for	£40.00

IMPORTANT NOTE: These devices are only cathode dipped and are not coded with part numbers.


EAST CORNWALL COMPONENTS
P.O. Box 4, Saltash, Cornwall [3032]

PEAK PROGRAM METERS TO BS4297

also 200kHz version for high speed copying.
Drive circuit. 35 x 80mm. for 1mA L.H. zero meters. Gold edge con supplies.

Complete kit	£9.00	£7.60	£7.20	£6.80
Built and aligned	£12.00	£11.40	£10.80	£10.20

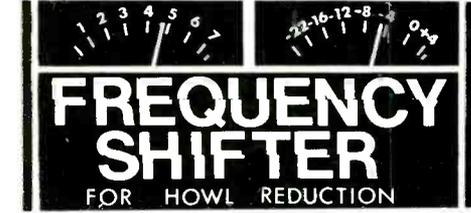ERNEST TURNER PPM meters. Below scalings stocked.
Type 642. 71 x 56mm £9.90; 643. 102 x 79mm £11.77



* Public address * Loudspeaker talkback * Telephone broadcast programmes when caller leaves receiver on. Unity gain mains powered box 190 x 55mm, with bypass switch, shifts input 5Hz up in frequency and allows 6-8dB more gain before howl-round.

* Other shift versions for weird music effects.
* SPECTRUM INVERTORS for speech security.
a Unbalanced 2-pole jack in and out Zout = 2Kohm £58
b Unbalanced 2-pole jack in and out Zout = 20 or 600 ohm £68
c Balanced 3-pole jack in and out Zout = 20 or 600 ohm £84

Post: Commonwealth 90p. Europe air and foreign £1.50
Shifter circuit boards for WW July '73 article:
Complete kit and board £18 Including p.s.u. and DESIGNER Board built and aligned £24 mains transformer APPROVED

SURREY ELECTRONICS
24 High Street, Merstham, Surrey
CASH WITH ORDER less 5% U.K. add VAT
Account 0197822 Lloyds Bank. Great Bookham, Surrey

CLASSIFIEDS—Continued from p. 128

PLUMBICON TV camera tubes type 5875 brand new. Klstrons type VA222A. K366A, KY366AU, KY366CDU, KY366BU. Pye Westminster radio-telephone type W25FM low band £100. Philips colour monitor type EL3560, suitable for spares, any offers. Colour monitor decoder units by leading British maker. Designed to BBC standards, units consist of chrominance module, P.A.L. filter and delay module, luminance module and encoded video input module. All units brand new and complete including edge connectors and service manual. £30. Also complete PAL/NTSC switchable decoder by same maker built in a 19in. Isep rack with power unit and sync separator. £75. Philips monitor decoder panels Type EL6818/50F PAL, £20. NTSC, £15. Advance stabilised power units type PM53.0-15 volt at 10 amp. Brand new, £35. Savage 600 watt audio amp. contains 12 x KT88's, no details. Offers, B. Bamber, 20 Wellington Street, Littleport, Cambs. Tel. 0353 860363. [3083]

ENAMELLED COPPER WIRE		
S.W.G.	1/2 Reel	1/2 Reel
10-14	£1.27	72p
15-19	£1.27	72p
20-24	£1.30	75p
25-29	£1.38	83p
30-34	£1.43	88p
35-40	£1.54	91p

Please add 10% to all above prices to cover V.A.T.
The above prices cover P. & P. In U.K. Supplied by
INDUSTRIAL SUPPLIES
102 Parrswood Road, Withington, Manchester M20 2JG
Tel.: 061-224-3553

VACUUM is our speciality. New and second-hand rotary pumps, diffusion outfits, accessories, coaters, etc. Silicone rubber or varnish outgassing equipment from £40. V. N. Barrett (Sales) Ltd., 1 Mayo Road, Croydon. 01-684 9917. [24]

VHF KIT 80-180 MHz receiver, tuner, converter. Transistorised, remarkable performance. £4 or s.a.e. for literature Johnssons (Radio), St. Martins Gate, Worcester. WR1 2DT. [13]

60 KHz MSF Rugby and 75 KHz Neuchatel Radio Receivers. Signal and Audio outputs. Small, compact units. Two available versions £35 and £60. Toolex, Bristol Road, Sherborne (3211), Dorset. [21]

HEWLETT PACKARD 9830A
Are you waiting delivery? New machine available at £3,500.
Also Counter HP5300/5303B with high stability time base (aging rate <1.2 parts in 10⁶/year) £700.
Ring Mr. Savage 01-340 7217 [3037]

ARTICLES WANTED

CASH paid for surplus transistors and all types of electronic components. Electronic Mailorder, Ramsbottom, Bury, Lancs. Tel. (STD 070 682) 3036. [3064]

CASH AVAILABLE for surplus semiconductors and I.C. Phone: 01-452 2583. [3095]

FRIDEN FLEXOWRITERS, all models urgently wanted for cash, also Friden Auxiliary Readers and Punches. Box No. WW 3005. [2938]

GEC METAL-CONE SPKR with/without cabinet, presence unit. 01-883 0748. [2938]

VORTEXION RECORDERS wanted. Models C.B.L. 5 or C.B.L. 6 Stereo. Also Ferrograph 632 models required. Best prices for spot cash. Ring West Mersea (020638) 3372. [2923]

WANTED, all types of communications receivers and test equipment.—Details to R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [63]

CAPACITY AVAILABLE

AIRTRONICS LTD., for Coil Winding—large or small production runs. Also PC Boards Assemblies. Suppliers to P.O., M.O.D., etc. Export enquiries welcomed. 3a Waterand Road, London, SE13 7PE. Tel. 01-852 1706. [61]

BATCH Production Wiring and Assembly to sample or drawings. Deane Electricals, 19B Station Parade, Ealing Common, London, W.5. Tel: 01-992 8976. [20]

DESIGN, development, repair, test and small production of electronic equipment. Specialist in production of printed circuit assemblies. **YOUNG ELECTRONICS**, 54 Lawford Road, London, N.W.5. 01-267 0201. [29]

CAPACITY available to the Electronic Industry. Precision turned parts, engraving, milling and grinding both in metals and plastics. Limited capacity available on Mathey SP33 JIG BORER. Write for lists of full plant capacity to C.B. Industrial Engineering Ltd., 1 Mackintosh Lane, E9 6AB. Tel. 01-985 7057. [14]

SMALL Batch Production, wiring, assembly, to sample or drawings. Specialist in printed circuit assemblies. D. & D. Electronics, 42 Bishopsfield, Harlow. Essex. Harlow 33018. [17]

COURSES

RADIO and Radar M.P.T. and C.G.L.I. Courses. Write: Principal, Nautical College, Fleetwood, FY7 8JZ. [25]

NEW GRAM AND SOUND EQUIPMENT

GLASGOW.—Recorders bought, sold, exchanged, cameras, etc., exchanged for recorders or vice-versa.—Victor Morris, 343 Argyle St., Glasgow, C.2. [11]

RECEIVERS AND AMPLIFIERS—SURPLUS AND SECONDHAND

HRO Rx5s, etc., AR88, CR100, BRT400, G209, S640, etc., etc., in stock.—R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [65]

SERVICE & REPAIRS

BRISTOL AND DISTRICT. Service to Hi Fi and electronic equipment. Public address installations. Stereo Centre, 309 Gloucester Road, Bristol. Tel: 0272 421395. [26]

EXPERIENCED ENGINEER offers field service facilities London area covering Electronic and Electro-Mechanical equipment—Box No. WW 2676. [26]

SCRATCHED TUBES. Our experienced polishing service can make your colour or monochrome tubes as new again for only £2.75, plus carriage 75p. With absolute confidence sent to Retube Ltd., North Somercote, Louth, Lincs, or 'phone 0507-85 300. [27]

SIGNAL generators, oscilloscopes, output meters, wave voltmeters, frequency meters, multi-range meters, etc., etc., in stock.—R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [64]

VALVES WANTED

WE buy new valves, transistors and clean new components, large or small quantities, all details, quotation by return.—Walton's. 55 Worcester St., Wolverhampton. [62]

TAPE RECORDING ETC.

IF quality, durability matter, consult Britain's oldest transfer service. Quality records from your suitable tapes. (Excellent tax-free fund raisers for schools.) Modern studio facilities with Steinway Grand.—Sound News, 18 Blenheim Road, London, W.4. 01-995 1661. [3041]

APPOINTMENTS—Continued from p. 126

Airline Radio Technicians

We require fully-trained and high-skilled Radio Technicians to work on the repair and overhaul of radio/radar equipment at Heathrow Airport (London). A high standard of theoretical knowledge is essential and at least 5 years' experience in radio maintenance. An approved apprenticeship is desirable.

Starting pay is £36.74 per week, plus shift allowance.

Additional benefits include a contributory pension scheme, sports and social facilities and opportunities for concessional holiday air travel worldwide.

Applications giving details of age and experience, quoting reference 68/WW/BW to:

Manager Selection Services
BOAC
PO Box 10
Heathrow Airport (London)
Hounslow TW6 2JA

2966

British airways

Assistant Electronics Engineer

A vacancy exists for an assistant Electronics Engineer within the Instrumentation Services Unit. The work of this unit is varied and interesting and will involve the person appointed in the construction of novel scientific equipment together with the repair and maintenance of existing instruments and apparatus. The successful candidate will probably be in the 21-25 age group with City and Guilds final qualifications or an ONC in electronic or electrical engineering. Some experience in similar work is necessary although specialised training will be given. (Ref. BP 176).

We offer a good progressive salary for this position, together with excellent conditions of service. Benefits include a subsidised canteen, active sports and social club. UK Staff Bonus Scheme and a non-contributory pension scheme.

Please reply quoting Ref. BP 176 to:—
Personnel Officer,
Beecham Research Laboratories,
Brockham Park, Betchworth, Surrey.
Tel: Betchworth 3202.




3109 1972

BOOKS ON ELECTRONICS

Basic Engineering Craft Studies— General (01)

Edited by
**P. H. M. Bourbousson, CIMarE, and
R. Ashworth, CEng, MIMechE, MIProdE**

Written for students studying for the City and Guilds of London Institute 500 Courses on Basic Engineering Craft Studies (Part I), this book together with a companion volume covers all the topics required for each of the courses. The General 01 volume contains basic material and should be used in conjunction with the appropriate complementary volume covering the syllabus relating to the required craft or trade bias.
0 408 00061 9 182 pages illustrated 1971

£1-50

F.M. Radio Servicing Handbook /2nd Edition

**Gordon J. King, RTechEng, MIPRE, FSRE,
MRTS, FISTC**

This handbook has been written by an experienced radio engineer with the aim of providing the theoretical and practical knowledge of FM radio receivers in a form helpful to all concerned with service work. The book is intended not only for professional service engineers, however, but also for amateur enthusiasts interested in the construction of FM equipment and for radio students. The style is straightforward and, as far as possible, non-mathematical.
0 408 00023 6 206 pages illustrated 1970

£3-00

Semiconductors: Basic Theory and Devices

Ian Kampel, C Eng, MIERE

Although this book covers a wider range of devices than is usually dealt with on any one course, it nevertheless provides a useful introductory text for students. All topics are explained in straightforward graphical terms without complicated formulae. It begins with an explanation of elementary atomic theory and gradually progresses through diodes, transistors and the more sophisticated devices that are available today.
0 408 00040 6 272 pages illustrated 1971

£2-50

Electroacoustics: Microphones, Earphones and Loudspeakers

(An STC Monograph)
M. L. Gayford, BSc., CEng, MIEE, ACGI, DIC

This book gives a unique insight into the audio and electroacoustics field dealing in particular with the theory, design and practical realisation of the various types of microphones, earphones and loudspeakers used in sound reproduction, telephony, broadcasting and acoustic measurements. It will be of special value to students, engineers and research workers engaged in telecommunications, broadcasting and sound reproduction.

0 408 00026 0 300 pages illustrated 1970

£4-50

Colour Television Servicing

**Gordon J. King, RTechEng, MIPRE, FSRE,
MRTS, FISTC**

This comprehensive book deals straightforwardly with the servicing of PAL receivers, using a minimum of mathematics. It is divided into three sections: the first surveys the colour TV system as a whole, the second studies the elements involved (e.g. picture tubes, conveyance systems, chroma channels) and the third is devoted exclusively to servicing.

0 408 00044 9 328 pages illustrated 1971

£4-40

Solid-State Devices and Applications

Rhys Lewis, BScTech, CEng, MIEE

Since the first appearance of the transistor in 1948, the field of solid-state devices has expanded so rapidly that it has become increasingly difficult to keep abreast of new developments. This book presents a concise summary of currently available devices, their theory, manufacture and applications.

0 408 00050 3 cased 264 pages illustrated 1971

£3-00

0 408 00051 1 limp

£2-00

A Simplified Approach to Solid State Physics

**M. M. Rudden, BSc, PhD, AInstP, and
J. Wilson, BSc, PhD, AInstP**

This book provides a broad survey of some of the more important concepts of solid state physics and will be suitable for first year university or technical college students. The approach throughout is essentially qualitative and the aim of the authors is to establish the fundamentals of the subject in as easy a manner as possible. To this end, frequent reference is made to experimental evidence in support of the theoretical concepts.

0 408 70003 3 cased 196 pages illustrated 1971

£2-90

0 408 70020 3 limp

£1-70

Available from leading booksellers or:

The Butterworth Group

88 Kingsway London WC2B 6AB

Showrooms and Trade Counter

4-5 Bell Yard, London WC2



Foundations of Wireless and Electronics

8th Edition

M. G. Scroggie

BSc CEng FIEE

1970 Reprinting 1973

552 pages, illustrated

Cased 0 592 05961 8 £3.00

Limp 0 592 00041 9 £1.80

"To the uninitiated all we have to say is that if you are seeking a thorough grounding in radio theory with a minimum use of mathematics in a style which is easy to assimilate, then this is a sound investment. It should be at the elbow of every aspiring technician."

Electrical and Electronic Trader

Available from leading booksellers or

The Butterworth Group


88 Kingsway London WC2B 6AB

Showrooms and Trade Counter


4-5 Bell Yard, London WC2



DIL Switch 16 in stock*

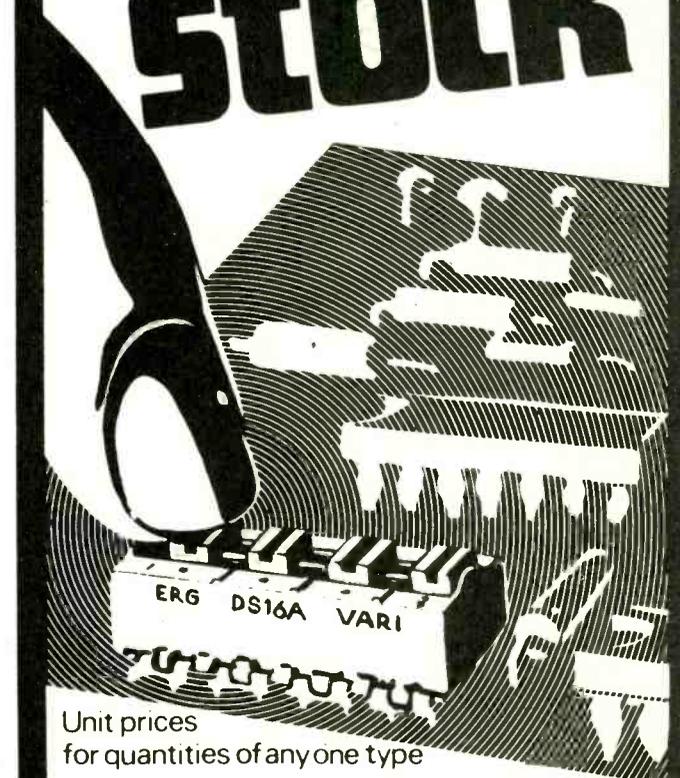

Unit prices
for quantities of any one type

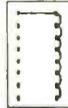Please indicate sample type required					
	Poles-Ways 1-8	1-6	2-4	4-2	VARI
10 off	£0.65	£0.65	£0.70	£0.77	£0.80
100 off	£0.56	£0.56	£0.61	£0.68	£0.71
1000 off	£0.48	£0.48	£0.53	£0.60	£0.63

Erg Components

Luton Road, Dunstable, Bedfordshire, LU5 4LJ, England.
Telephone: 0582-62241 (7 lines) Telex: 82349

*also stocked by Blueline, Farnell and others soon

For evaluation sample & technical data please complete

Name _____ Dept. _____

Company _____

Address _____

ww

WW-115 FOR FURTHER DETAILS

YATES ELECTRONICS

(FLITWICK) LTD.
DEPT. WW ELSTOW STORAGE DEPOT
KEMPSTON HARDWICK
BEDFORD

C.W.O PLEASE. POST AND PACKING
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the
components listed will be sent free on request.
10p stamp appreciated.

OPEN ALL DAY SATURDAYS
PLEASE ADD 10% V.A.T.

RESISTORS

1/2W Iskra high stability carbon film—very low noise—capless construction. 1/2W Mullard CR25 carbon film—very small body size 7.5 x 2.5 mm. 1/2W 2% ELECTROSIL TRS.

Power watts	Tolerance	Range	Values available	Price
1	5%	4.7Ω-2.2MΩ	E24	100+
1	10%	3.3MΩ-10MΩ	E12	1p
1	2%	10Ω-1MΩ	E24	3p
1	10%	1Ω-3.9Ω	E12	1p
1	5%	4.7Ω-1MΩ	E12	1p
4	10%	1Ω-10Ω	E12	6p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log 1/2W, lin 1/2W).
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch, 24p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C. mounting (0-1 matrix).
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 7p each.

TRANSISTORS

AC107	15p	AF126	20p	BF115	25p	OC42	12p	2N3707	12p
AC126	12p	AF139	32p	BF173	20p	OC44	12p	2N3708	10p
AC127	15p	AF178	32p	BF177	28p	OC45	12p	2N3709	11p
AC128	15p	AF180	40p	BF178	32p	OC70	12p	2N3710	11p
AC131	12p	AF181	40p	BF179	32p	OC71	12p	2N3711	11p
AC132	12p	BC107	12p	BF180	32p	OC72	12p	2N3819	32p
AC176	15p	BC108	12p	BF181	32p	OC81	12p	2N4062	12p
AC187	22p	BC109	12p	BF194	14p	OC82D	12p	2N4286	20p
AC188	22p	BC147	12p	BF195	14p	2N2646	60p	2N4289	20p
AD140	50p	BC148	12p	BF197	15p	2N2904	20p	40360	35p
AD149	45p	BC149	12p	BF200	32p	2N2926	10p	40361	35p
AD161	33p	BC157	14p	BF750	20p	2N3054	58p	40362	40p
AD162	36p	BC158	14p	BF751	20p	2N3055	60p	40408	40p
AF114	20p	BC159	14p	BF752	20p	2N3702	12p	ZTX108	15p
AF115	20p	BC187	22p	BU7105	225p	2N3703	12p	ZTX300	15p
AF116	20p	BD131	75p	OC26	45p	2N3704	12p	ZTX302	20p
AF117	20p	BD132	75p	OC28	50p	2N3705	12p	ZTX500	15p
AF118	38p	BD133	75p	OC35	50p	2N3706	11p	ZTX503	20p

ZENER DIODES

400mW 5% 3.3V to 30V, 12p.

WIRE WOUND POTS

3W, 10, 25, 50Ω and decades to 100kΩ, 35p.

DIODES

RECTIFIER

BY127	1250V	1A	12p
BZY10	800V	6A	25p
BZY13	200V	6A	20p
IN4001	50V	1A	7p
IN4004	400V	1A	8p
IN4007	1000V	1A	10p

SIGNAL

OA85	7p
OA90	5p
OA91	5p
OA202	7p
IN4148	5p
BA114	8p

BRUSHED ALUMINIUM PANELS

12in x 6in, 25p; 12in x 2 1/2in, 10p; 9in x 2in, 7p

SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of track 59mm.
SINGLE 10K, 25K, 100K log. or lin. 40p.
DUAL GANG, 10K + 10K etc. log. or lin. 60p.
KNOB FOR ABOVE, 12p.
FRONT PANEL, 65p.
18 Gauge panel 12in x 4in with slots cut for use with slider pots. Grey or matt black finish complete with fixings for 4 pots.

THERMISTORS

VA10555	15p
VA10665	15p
VA1077	15p
R53	£1.35

THYRISTORS

2N5060 50V 0.8A	30p
2N5064 200V 0.8A	47p
106F 50V 4A	40p
106D 400V 4A	55p

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 2 1/2p. 0.0068μF, 0.01μF, 0.015μF, 0.022μF, 0.033μF, 3p. 0.047μF, 0.068μF, 0.1μF, 4p. 0.15μF, 6p. 0.22μF, 7 1/2p. 0.33μF, 11p. 0.47μF, 13p.

160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p. 0.1μF, 33p. 0.15μF, 4 1/2p. 0.22μF, 5p. 0.33μF, 6p. 0.47μF, 7 1/2p. 0.68μF, 11p. 1.0μF, 13p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 3p. 0.033μF, 0.047μF, 0.068μF, 3 1/2p. 0.1μF, 4p. 0.15μF, 0.22μF, 5p. 0.33μF, 6 1/2p. 0.47μF, 8 1/2p. 0.68μF, 11p. 1.0μF, 13p. 1.5μF, 20p. 2.2μF, 24p.

ELECTROLYTIC CAPACITORS—MULLARD O15/6/7

(μF/v) 1/63, 1.5/63, 2.2/63, 3.3/63, 4.7/63, 6.8/40, 6.8/63, 10/25, 10/63, 15/16, 15/40, 15/63, 22/10, 22/25, 22/63, 33/6.3, 33/16, 33/40, 47/4, 47/10, 47/25, 47/40, 68/6.3, 68/16, 100/4, 100/10, 100/25, 150/6.3, 150/16, 220/4, 220/6.3, 220/16, 330/4, 6p. 47/63, 100/40, 150/25, 220/25, 330/10, 470/6.3, 7p. 68/63, 150/40, 220/40, 330/16, 1000/4, 10p. 470/10, 680/6.3, 11p. 100/63, 150/63, 220/63, 1000/10, 12p. 470/25, 680/16, 1500/6.3, 13p. 470/40, 680/25, 1000/16, 1500/10, 2200/6.3, 18p. 330/63, 680/40, 1000/25, 1500/16, 2200/10, 3300/6.3, 4700/4, 21p.

SOLID TANTALUM BEAD CAPACITORS

Value	Price	Value	Price	Value	Price
0.1μF 35V	—	2.2μF 35V	22p	22μF 16V	—
0.22μF 35V	—	4.7μF 35V	33p	33μF 10V	—
0.47μF 35V	—	6.8μF 25V	47p	47μF 6.3V	—
1.0μF 35V	—	10μF 25V	100p	100μF 3V	—

VEROBOARD

0.1	0.15
2 1/2 x 3 1/2	22p 16p
2 1/2 x 5	24p 24p
3 1/2 x 3 1/2	24p 24p
3 1/2 x 5	27p 27p
17 x 2 1/2	75p 573p
17 x 3 1/2	100p 78p
17 x 5 (plain)	— 82p
17 x 3 1/2 (plain)	— 60p
17 x 2 1/2 (plain)	— 42p
2 1/2 x 5 (plain)	— 12p
2 1/2 x 3 1/2 (plain)	— 11p
Pin insertion tool	52p 52p
Spot face cutter	42p 42p
Pkt. 50 pins	20p 20p

JACK PLUGS AND SOCKETS

Standard screened	18p	2.5mm insulated	8p
Standard insulated	12p	3.5mm insulated	8p
Stereo screened	35p	3.5mm screened	13p
Standard socket	15p	2.5mm socket	8p
Stereo socket	18p	3.5mm socket	8p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin
Plug 12p. Socket 8p.
4 way screened cable, 15p/metre.
6 way screened cable, 22p/metre.

BATTERY ELIMINATOR £1.50

9V mains power supply. Same size as PP9 battery.

LARGE (CAN) ELECTROLYTICS

1600μF 64V	74p	2500μF 64V	80p	4500μF 16V	50p
2500μF 40V	74p	2800μF 100V	£2.60	4500μF 25V	£1.68
2500μF 50V	58p	3200μF 16V	50p	5000μF 50V	£1.10

HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0.01μF 10p	0.047μF 13p	0.22μF 20p
0.022μF 12p	0.1μF 13p	0.47μF 22p

POLYSTYRENE CAPACITORS 160V 22%

10pF to 1,000pF E12 Series Values, 4p each.

SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs deoxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector.
Detector GDI, £2. Kit of parts for detectors including GDI and P.C. board but excluding case. Mains operated detector £5.20. 12 or 24V battery operated audible alarm £7.30. As above for PP9 battery, £6.40.

PRINTED BOARD MARKER

97p
Draw the planned circuit on to a copper laminate board with the P.C. Pen, allow to dry, and immerse the board in the etchant. On removal the circuit remains in high relief.

LARGE RANGE ITT/TEXAS IC's NOW IN STOCK

PRICES ARE CALCULATED ON TOTAL NUMBER ORDERED REGARDLESS OF MIX

IC	1-11	12-24	25-99	100+	7448	185	175	170	165	74118	100	82	73	64
7400	p	p	p	p	7450	18	16	14	13	74121	43	40	38	36
7401	18	16	14	13	7451	18	16	14	13	74141	100	95	90	85
7402	18	16	14	13	7453	18	16	14	13	74145	150	140	135	130
7403	18	16	14	13	7454	18	16	14	13	74150	330	280	250	220
7404	20	18	16	14	7460	18	16	14	13	74151	110	100	95	89
7405	20	18	16	14	7470	30	28	25	24	74153	120	110	105	95
7406	50	45	40	35	7472	30	28	27	23	74154	200	180	170	160
7407	56	50	44	38	7473	40	38	36	30	74155	150	120	100	86
7408	36	30	27	23	7474	40	36	32	28	74156	130	120	100	96
7409	36	30	27	23	7475	55	52	49	45	74180	155	136	112	105
7410	18	16	14	13	7476	40	36	32	30	74190	195	190	185	180
7411	23	21	20	18	7480	100	95	90	85	74191	195	190	185	180
7412	36	30	27	23	7481	125	115	110	105	74192	200	190	180	164
7413	34	28	26	22	7482	100	96	90	85	74193	200	180	170	150
7416	45	43	39	34	7483	100	97	95	92	74196	200	190	180	170
7420	18	16	14	13	7484	120	115	110	105	74197	200	195	180	170
7421	36	30	27	23	7485	250	245	240	230					
7426	32	29	23	20	7486	45	42	37	33					
7430	20	18	16	14	7490	75	67	60	52					
7432	40	36	32	28	7491A	100	92	85	79	709	14 pin DIL			40p
7440	20	18	16	14	7492	75	70	65	60	741	8 pin DIL			40p
7441	80	75	70	65	7493	75	68	60	52	741	14 pin DIL			38p
7442	80	75	70	65	7494	95	90	85	80	723	14 pin DIL			95p
7443	125	120	115	115	7495	105	100	95	90	747	14 pin DIL			85p
7447	175	165	150	120	7496	100	95	90	85	748	8 pin DIL			45p
					74100	250	240	235	230		DIL sockets	14 pin and 16 pin		16p

LINEAR IC's

14 pin DIL	40p
8 pin DIL	40p
14 pin DIL	38p
14 pin DIL	95p
14 pin DIL	85p
8 pin DIL	45p
14 pin and 16 pin	16p

Lodge Trading Company

For Amplifiers, Speakers with and without cabinets, Changer Units, Plinths and Covers, Tape Recorders, four and eight track for car or home, Car Radios, Colour TVs, Aerials, Flex, and Cables, Large stocks of components.

ALL AT WHOLESALE PRICES

A VISIT WILL SAVE YOU MONEY

5 Day Week 9-6. Easy Car Parking.

Sorry no lists.

21 LODGE LANE, N. FINCHLEY, LONDON, N.12
01-445 2713, 01-445 0749

QUARTZ CRYSTAL UNITS from

- 1.0-60.0 MHZ
- FAST DELIVERY
- HIGH STABILITY
- TO DEF 5271-A



WRITE FOR LEAFLET AT - 1

McKNIGHT CRYSTAL Co.
HARDLEY INDUSTRIAL ESTATE, HYTHE, SOUTHAMPTON SO4 6ZY.

TEL. HYTHE 8961
STD CODE 042 14

TRANSFORMER LAMINATIONS enormous range in Radiometal, Mumetal and H.C.R., also "C" & "E" cores. Case and Frame assemblies.

MULTICORE CABLE IN STOCK CONNECTING WIRES

Large quantities of miniature potentiometers (trim pots) 20 ohm to 25K. Various makes. Wholesale and Export only.

J. Black

OFFICE: 44 GREEN LANE, HENDON, NW4 2AH

Tel: 01-203 1855. 01-203 3033

STORE: LESWIN ROAD, N.16

Tel: 01-249 2260



THE ONLY COMPREHENSIVE RANGE OF RECORD MAINTENANCE EQUIPMENT IN THE WORLD!

Send P.O. 15p for 48 page booklet providing all necessary information on Record Care.

CECIL E. WATTS LIMITED
Darby House
Sunbury-on-Thames, Middx.

A guide to the better care of LP and Stereo Records

WE PURCHASE

OSCILLOSCOPES, SIGNAL GENERATORS, PEN RECORDERS, COMPUTERS, RECEIVERS.

PLEASE SEND US YOUR LISTS.
BEST PRICES PAID.

ELECTRONIC BROKERS LTD.
49 Pancras Road, London, N.W.1. 01-837 7781

TELERADIO SPECIAL PRODUCTS

LINSEY HOOD Low Distortion Amplifiers. (75 watt article re-print 40p) from £25.
TEXAN. Renowned 20+20 Stereo Kit (£28-50 basic).
DIGITAL NIXIE READ OUT CLOCKS (from £33).
RADIO CONTROL SYSTEMS (from £12).

Send S.A.E. (10 x 8), or stamp, for full data and prices to:
325-7 Fore St., London, N9 0PE.
01-807 3719

SOMMERKAMP

Our products are:

11m AM Walkie-Talkies, 0-2-1-2 and 5 Watt up to 24 channels. 11m AM Cartransceivers, 6 and 24 channels, 2-5 and 10 Watt, 2m FM 10 Watt, 12-22 channels Amateur, Industrial and Marine Transceivers. 11m SSB 24ch, 300W, 220V/12V-Transceivers. 8-track Stereo-Recorder with built-in AM and FM Stereo-Radio.

Wanted:

Qualified dealers and wholesalers of the technical line for the sale of the above highly sought-after products.

Delivery is effected immediately from stock in Switzerland or ex factory Japan.

SOKA SRL,

CH 6903 Lugano, Box 176
Tel: 0041 91 688543, Telex: 79314

BRAND NEW FULL SPEC. DEVICES

U.K. CUSTOMERS ADD 10% VAT TO TOTAL

MICROCIRCUITS: 709 24p; 710 36p; 723 51p; 741 (14 pin) 27p; 748 37p. FET OP. AMP. £1.62.
TRANSISTORS: 2N2926 (Brown) 6p; 2N3053 15p; 2N3055 35p; 2N3702 10p; 2N3704 10p; 2N3819 26p; 2N4058 12p; BC107A 8p; BC108B 8p; BC109B 8p; BC109C 8p; BCY70 15p; BFY50/51/52 15p; OC44/45/71/72 12p; AF114/5/6/7 14p; AC126/7/8 12p.

ZENERS: BZY88 Series 10p. I AMP. RECTIFIERS: 50V 3½p; 100V 4p; 200V 4½p; 400V 5p; 800V 6p; 1000V 7p. 14 pin IC SOCKETS 12p. SOLDER-CONS ½p per pin. DALO PC PEN 68p. ½W 5% Carbon Film Resistors, E12 values only: 10 of one value per 7p. Sub Min. Vertical Preset Pots (50mW) 100 ohms to 220K 4p each. LED with bush and data 24p.

ANTEX S. IRONS: 15W £1.70; 25W £1.75.

Prices at 25th July. Check our list.

Discounts start at 10% for 10+ Semiconductors of one type.

JEF ELECTRONICS (W.W. 10)

York House, 12 York Drive, Grappenhall, Warrington, WA4 2EJ.

Mail Order Only. C.W.O. P. & P. 10p per order minimum, or at cost if more. List free. Satisfaction or your money back.

SOWTER TRANSFORMERS

FOR SOUND RECORDING AND REPRODUCING EQUIPMENT
We are suppliers to many well-known companies, studios and broadcasting authorities and were established in 1941. Early deliveries. Competitive prices. Large or small quantities. Let us quote.

E. A. SOWTER LTD.

Transformer Manufacturers and Designers
7 Dedham Place, Fore Street, Ipswich IP4 1JP
Telephone 0473 52794

EXCLUSIVE OFFERS

NEVER BEFORE OFFERED WORLD-WIDE RANGE

PHILCO HC-150 POINT-TO-POINT STRIP RECEIVERS 2/30 m/cs. Ten fully tuneable channels to 0-5 kcs with synthesizers. Single and diversity reception on 18B, DSB, SSB with 4 sub-bands to each channel. Full details and prices on application.

INSTRUMENTATION TAPE RECORDER-REPRODUCERS

AMPEX

FR-100B 1" 14 tracks 6 speeds

FR-600 1" and ½" 14 and 7 tracks 4 speeds Transistorised

I.B.M.

729 ½" 7 tracks 6 speeds

CMP-100 ½" ½" 1" 7 tracks 6 speeds

E.M.I.

TD-1 ½" 4 tracks 7 speeds

Several other smaller decks.
Full details on request.
Prices of above are from £150 to £700.



COMPUTER HARDWARE

CARD READER 80 col. 600 c.p.m.
PRINTER, High speed 1000 lines p.m.
TAPE READER, High speed 5/8 track 800 c.p.m.

TALLY 5/8 track TAPE READERS
ADDO 5/8 track TAPE PUNCHES
BULL 80 col. HAND CARD PUNCHES

Prices on Application

FREE

40-page list of over 1,000 different items in stock available—keep one by you.

HIGHEST QUALITY 19" RACK MOUNTING CABINETS & RACKS

CABINETS

Our Ref.	Height in inches	Width in inches	Depth in inches	Rack Panel Space in in.	Price
CD	69	21	13	68	£10.00
CE	83	22	24	77	£14.00
CF	87	23	26	80	£12.50
CH	83	24	30	75	£14.00
CJ	83	24	24	75	£13.00
CK	83	24	12	75	£10.00
CL	30	60	36	42	£12.50
CM	19	22	18	17	£5.00
CP	69	24	26	61	£13.00
CR	69	30	26	—	£24.00
CT	70	69	27	—	£45.00
CU	87	26	17	—	£20.00
DE	82	40	24	91	£30.00
DF	75	22	26	68	£15.00
DH	70	23	24	122	£20.00
DK	85	22	26	79	£20.00
DL	54	24	19	69	£18.00
DP	74	24	24	66	£18.00
DR	14	21	12	10	£7.00
DS	69	30	20	63	£26.00
DT	84	24	22	80	£24.00

Also Consoles, twin and multi-way Cabinets.

OPEN RACKS

Our Ref.	Height in inches	Channel Depth	Rack Panel Space	Base Bolts	Price
RE	108	6	104	Bolts	£9.00
RD	80	8	77	24 Bolts	£8.00
RC	66	5	63	Bolts	£8.00
RE	78	7½	70	Bolts	£7.00

Full details of all above on request.

We have a large quantity of "bits and pieces" we cannot list—please send us your requirements we can probably help—all enquiries answered.

- ★ Ferragraph 3/CFN Tape Recorders £35.00
- ★ Ferragraph G.200 Tape Recorders £27.00
- ★ Racal RA-17L Receivers £225.00
- ★ CV-157 Hoffman 18B/SSB Converters £160.00
- ★ 10 foot Triangular Lattice Mast Sections £9.00
- ★ Casella Assmann Electric Hygrometers £24.00
- ★ Racal RA-17 Cabinets £14.00
- ★ Racal MA-150 Synthesizers £95.00
- ★ Racal MA-250 Decade Generators £125.00
- ★ vo Geiger Counters, new £7.00
- ★ Serrvomec 2KVA Voltage Regulators £34.00
- ★ Solartron CD-1016 d/b Oscilloscopes £34.00
- ★ Double Co-axial Blowers 6 x 6 220 v. A.C. £3.00
- ★ Amplex 8.E.10 Auto Degaussers £45.00
- ★ Uniselectors 10 bank 25 way full wipe £3.00
- ★ R.C.A. 6 element 420 m/cs Yagi Beams £4.00
- ★ Haynes 500 watt 230 v./115v. Isolation Transformers £9.00
- ★ Muirhead D.888 Analysers £80.00
- ★ Laboratory Radio Interference Filters £2.00
- ★ Fye Scalamp Galvos £14.00
- ★ Caswell Type 1471 Variable Filters £70.00
- ★ Adwell large Drafting Tables with parallel motions £24.00
- ★ 54in. dia. Meteorological Balloons £1.50
- ★ Flann Microwave Attenuators 4/12 EMC £40.00

PLEASE ADD V.A.T. TO ABOVE

P. HARRIS ORGANFORD — DORSET

BH16 6ER
BOURNEMOUTH-65051

ERRATA

The correct address of
BARRIE Electronics (page a79)
is 3, The Minories, London EC3N 1BJ. Telephone: 01-488 3316/8

STUDIO ELECTRONICS
 P.O. BOX No.18 HARLOW ESSEX CM18 6SH
 Telephone: Harlow 25457

SPECIALISED KITS

**HIGH STANDARD
 LOW FREQUENCY SOURCE**

(to article by J. M. Osborne, W.W. Jan. 73)

A Phase-Locked Loop designer approved kit to professional standards with Glass-Fibre P.C. Board, and all components including Hardware, case, etc. Full constructional details from the designer are included. Reference accurate to 2 parts in 10¹¹! Probably the most economic high precision signal source available. Kit **£24.67**
 Assembled and tested version. **£32.15**
 NE561B only each **£4.88**
 DE LUXE Kit **£30 + £3 VAT = £33.00**

**CBS-SQ QUADRAPHONIC
 IC DECODER**

To Motorola application for MC1312

as described by Geoffrey Shorter (WW March 73)

Our complete kit of professional quality components includes a glass-fibre edge connected printed circuit board and is absolutely complete, with full assembly and application notes.

As we also design and manufacture complete stereo and Quadraphonic systems, our wide applications experience is available to you to guarantee professional results.

Complete kit as described above **£8.80**
 Assembled and tested production board **£12.10**
 "AS USED IN P.E. RONDO"

**PHASE-LOCKED-LOOP
 STEREO DECODER**

To Motorola application for MC1310

as described in Wireless World, July 1972

1310 complete kit of professional quality including a glass-fibre edge connected printed circuit board and all components.

Complete kit which can be built in 1/2 hr. **£3.74**
 Assembled and tested production board **£4.84**
 MA2404 Professional LED 61p extra if required. Economy LED (physically small) 37p extra if required. A current limiting resistor is supplied free upon request with all LEDs. Self powered and special versions are available to order.

NEW PRODUCTS

1. Two tone test oscillator 1 & 2kHz, ideal for SSB setting up. Battery powered professional quality kit **£6.75**
2. Squelch board for FM tuners. Simple add-on advanced circuitry for effective muting. Tuner powered kit **£5.34**.

SPECIALIST SERVICES

Suppliers of products by Radiospares, Eagle, TTC, Sonax, Teleradio and RSGB publications. We welcome enquiries, irrespective of size or nature. A full technical and after-sales-service is provided, with licensed radio amateurs on the technical staff.

Communications acknowledged normally by return. MAIN DISTRIBUTORS FOR QUADRASONICS, THE PREMIER BRITISH QUADRAPHONIC SYSTEM.

**NO HIDDEN EXTRAS
 ALL PRICES INCLUDE VAT,
 CARRIAGE and INSURANCE**

PLEASE SUPPLY

£ enclosed.

	KITS	ASSEMBLED
CBS-SQ QUAD DECODER		
PLL STEREO DECODER		
L.F. SOURCE		
TWO TONE OSC.		
SQUELCH BOARD		
NAME		
ADDRESS		

WW10

**SEMICONDUCTOR
 CIRCUIT DESIGN
 Volume II**

A Texas Instruments Publication July 1973

£5.25

**THE TTL DATA BOOK FOR DESIGN
 ENGINEERS** by Texas Instruments. Price **£2.25**

**ELECTRONICS: CIRCUITS AND
 DEVICES** by R. J. Smith. Price **£6.75**

**MOS INTEGRATED CIRCUIT
 DESIGN** by E. Wolfendale. Price **£4.10**

**INSTALLING AND SERVICING
 ELECTRONIC PROTECTIVE
 SYSTEMS** by H. Swearer. Price **£1.45**

**HOW TO USE INTEGRATED
 CIRCUIT LOGIC ELEMENTS** by J. W. Streater. Price **£1.60**

**RADIO AND ELECTRONIC LABO-
 RATORY HANDBOOK** by M. G. Scroggie. Price **£5.50**

**THE RADIO AMATEUR'S HAND-
 BOOK 1973 A.R.R.L.** Price **£2.95**

COLOUR T.V. THEORY by Hudson. Price **£4.10**

**TRANSISTOR AUDIO AND RADIO
 CIRCUITS** by Mullard. Price **£1.90**

**UNDERSTANDING SOLID-STATE
 ELECTRONICS** by Texas Instruments. Price **£1.40**

★ALL PRICES INCLUDE POSTAGE★

THE MODERN BOOK CO.

SPECIALISTS IN SCIENTIFIC
 & TECHNICAL BOOKS

**19-21 PRAED STREET,
 LONDON, W2 1NP**

Phone 723 4185
 Closed Sat. 1 p.m.

Quartz Crystal Units
 ACCURATE
 RELIABLE

Private enquiries, send 5p in stamps for brochure

THE QUARTZ CRYSTAL CO. LTD.
 Q.C.C. WORKS, WELLINGTON CRESCENT,
 NEW MALDEN, SURREY. 01-942-0334 & 2968

CASH IMMEDIATELY AVAILABLE

for redundant and surplus stocks of radio, television, telephone and electronic equipment, or in component form such as meters, plugs and sockets, valves, transistors, semi conductors, capacitors, resistors, cables, copper wire, screws and nuts, speakers, etc.

The larger the quantity the better we like it.

**BROADFIELDS & MAYCO
 DISPOSALS**

21 Lodge Lane, London, N12.
 Telephone: 01-445 2713 01-445 0749
 Evenings: 01-958 7624

TRANSFORMERS

DOUGLAS GUARANTEED
 (Prices include 10% VAT and P. & P.)
 12 or 24 Volts

Output V. & Amps.	Ref. No.	Price	Output	Ref. No.	Price
12V x 2 250 mA x 2	MT 111 CS**	£1.15	4A	MT 21 AT	£2.02
12V x 2 500 mA x 2	MT 213 CT**	£1.56	5A	MT 51 AT	£5.73
12V x 2 1A x 2	MT 71 AT*	£1.97	8A	MT 88 AT	£7.87
12V x 2 2A x 2	MT 18 AT	£2.70	10A	MT 89 AT	£8.75
12V x 2 3A x 2	MT 70 AT	£3.34			
12V x 2 4A x 2	MT 108 AT	£3.74			
12V x 2 5A x 2	MT 72 AT	£4.30			

30 volts. All tapped at 0-12-15-20-30V.					
Output Amps.	Ref. No.	Price	Output Amps.	Ref. No.	Price
500 mA	MT 112 CT*	£1.47	4A	MT 21 AT	£2.02
1A	MT 79 AT*	£1.99	5A	MT 51 AT	£5.73
2A	MT 8 AT	£2.92	8A	MT 88 AT	£7.87
3A	MT 20 AT	£3.38	10A	MT 89 AT	£8.75

50 volts. All tapped at 0-19-25-33-40-50V.					
Output Amps.	Ref. No.	Price	Output Amps.	Ref. No.	Price
500 mA	MT 102 AT*	£1.92	3A	MT 105 AT	£4.98
1A	MT 103 AT	£2.67	4A	MT 106 AT	£6.50
2A	MT 104 AT	£3.98	5A	MT 107 AT	£9.11

60 volts. All tapped at 0-24-30-40-48-60V.					
Output Amps.	Ref. No.	Price	Output Amps.	Ref. No.	Price
500 mA	MT 124 AT*	£2.03	2A	MT 127 AT	£4.12
1A	MT 126 AT	£2.94	3A	MT 126 AT	£5.78

AUTO-WOUND RANGE					
Power output	Winding tapped at	Ref. No.	Price	Ref. No.	Price
20 VA	0-115-210-240	XMT 113 CT	£1.22		
75 VA	"	XMT 64 AT	£2.32		
150 VA	0-115-200-220-240	XMT 4 AT	£2.85		
200 VA	"	XMT 65 AT	£3.84		
300 VA	"	XMT 66 AT	£5.06		

SAFETY ISOLATORS. 105/120 V. or 200/240 V. In. 105/120 CT or 200/240 CT Out.					
VA	Ref. No.	Price	VA	Ref. No.	Price
60	MT 149 AT*	£2.86	250	MT 152 AT*	£7.75
100	MT 150 AT*	£5.51	350	MT 153 AT*	£10.18
200	MT 151 AT*	£8.22	500	MT 154 AT*	£14.55

400 V. Output at 50 Hz. Ref. IT3 AT Price
 C-D Ignition system by R. M. Marston Esq. **£2.98**
 Wireless World.

EQUIPMENT RANGE					
Sec. Output (r.m.s.)	200 mA	Ref. No.	Price	Ref. No.	Price
3-0-3 V.	200 mA	MT 238 CS**	£1.59		
9-0-9 "	100 mA	MT 15 CS**	£1.24		
12-0-12 "	100 mA	MT 239 CS**	£1.24		
20-0-20 "	30 mA	MT 241 CS**	£1.24		
0-20 x 2 "	300 mA x 2	MT 214 CT**	£1.59		
0-8-9 x 2 "	500 mA x 2	MT 207 CT**	£1.87		
0-15-20 x 2 "	500 mA x 2	MT 205 AT**	£2.55		
0-15-27 x 2 "	500 mA x 2	MT 203 AT*	£3.17		
0-15-27 x 2 "	1A x 2	MT 204 AT*	£4.55		
20-12-0-12-20 "	700 mA (d.c.)	MT 221 AT*	£1.58		

AT indicates open universal fixing with tags; CT is open U-clamp fixing with tags; CS is open U-clamp fixing with P.C. spalls; * with interwinding screen; † untapped 240V Primary; ‡ tapped at 210-240V; other Primaries tapped at 200-220-240V.

Over 200 types in stock through agents or direct. Send for lists. DOUGLAS ELECTRONIC INDUSTRIES LTD., Direct Sales Dept. Thames Street, LOUTH, Lincs. LN11-7AD

**LONDON CENTRAL
 RADIO STORES**

TELEPHONE CABLE. Plastic covered grey 4-core coloured coded. 7½p per yd.
 RECORD STORAGE UNITS. Brand new. Anti-warp. 'Compact 200' stores 200 records. £12.58. P.P. £1.40. 'Compact 100' stores 100 records. £5.97. P.P. 70p. Leaflets available. S.A.E.
 ELECTRICITY SLOT METERS (5p in slot) for A.C. mains. Fixed tariff to your requirements. Suitable for hotels, etc. 200/250v. 15 A. £7.25. 20 A. £7.75. P.P. 75p. Other amperages available. Reconditioned as new 2 years, guaranteed.
 MODERN DESK PHONES, red, green, blue or topaz, 2 tone grey or black, with internal bell and handset with 0-1 dial £5.00. P.P. 50p.
 5-WAY PRESS-BUTTON INTER-COM TELEPHONES in Bakelite case with junction box handset. Thoroughly overhauled, guaranteed. Price £5.25. Wiring diagram on request, send s.a.e.
 10-WAY PRESS-BUTTON INTER-COM TELEPHONES in Bakelite case with junction box handset. Thoroughly overhauled. Guaranteed. £6.75 per unit. Wiring diagram on request, send s.a.e.
 20-WAY PRESS-BUTTON INTER-COM TELEPHONES in Bakelite case with junction box handset. Thoroughly overhauled. Guaranteed. £7.75 per unit. Wiring diagram on request, send s.a.e.
 The "88" Set. This transceiver, weighs approx. 5½ lbs. and measures 3½in. x 5½in. x 9½in. It is a 4 frequency channel set 41-44 mc/s., Crystal Controlled and operates from a dry battery H.T./L.T. 94/1. v. I.E. Ruben Mallory Type No. 1 and employs the following 14 valves. 3A4, 1 off; 1L4, 6 off; 1T4, 4 off; 185, 1 off; 1A3, 2 off. £25.50 plus 76p P. & P.

**23 LISLE ST. (437)
 (2969) LONDON W.C.2**
 Open all day Saturday

**WE PURCHASE ALL FORMS
 OF ELECTRONIC EQUIPMENT
 AND COMPONENTS, ETC.**

**SPOT CASH
 CHILTMHEAD LTD.
 7, 9, 11 Arthur Road, Reading, Berks.
 Tel: 582 605**

WANTED FOR £ £ £ NOTES

ELECTRONIC TEST GEAR, COMPONENTS | SCOPES

THINKING OF RE-EQUIPPING, EXCHANGING OR JUST RAISING CASH — THINK OF US. WE WANT ANY TELEQUIPMENT, ADVANCE, MOST TEKTRONIX, SOLARTRONS FROM MODEL 1014, HEWLETT PACKARD CONSIDERED AND OTHERS. PHONE US OR BRING ANY TIME.

CHILTMEAD LTD

7-9 ARTHUR ROAD, READING, BERKS. (rear Tech. College) Tel.: Reading 582605

INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 110-131

	PAGE		PAGE		PAGE
Adeola Products Ltd.	21	Gale Electronics Ltd.	23	Racal Instruments Ltd.	45
Aeriplite Cables Ltd.	3	Gardners Transformers Ltd.	13	Raffe, P. F.	92
Aero Electronics Ltd.	80	General Instruments Ltd. (Microelectronics)	55	RCA Electronics Ltd.	28
A.I. Factors	137	Goldring Mfg. Co. Ltd.	56, 68	RCS Electronics	38
Ancom Ltd.	38	Grampian Reproducers Ltd.	30	Redifon Telecommunications Ltd.	40
Acoustical Mfg. Ltd.	39			Rilton Electronics	55
Anders Electronics Ltd.	7, 27	Harris Electronics (London) Ltd.	31	Rola Celestion Ltd.	32
Amtron U.K.	22	Harris, P.	135	R.S.C. Hi-Fi Centres Ltd.	76
Apollo Electronics	53	Hart Electronics	102	R.S.T. Valves Ltd.	80
Arrow Electronics Ltd.	2	Heath (Gloucester) Ltd.	11		
Audix B.B. Ltd.	14	Henry's Radio Ltd.	72, 73		
A.S.P. Ltd.	104	Henson, R. Ltd.	135, 136		
Aveley Electric Ltd.	35	Hi-Fi Year Book	29		
		I.C.S. Ltd.	46	Salford Electrical Insts. Ltd.	30
Barr & Stroud Ltd.	6, 56	I.L.P. Electronics Ltd.	108, 109	Samson (Electronics) Ltd.	102
Barris Electronics	79	Integrex Ltd.	59	Scott, James, Ltd.	36
B. & W. Electronics	34			S.E. Laboratories Ltd.	4, 5
Bedford Electronics	78	Jackson Bros. (London) Ltd.	32	Service Trading Co.	89
Bentley Acoustic	84	J.E.F. Electronics	135	Servo & Electronic Sales Ltd.	82
Bias Electronics Ltd.	43	J.H. Associates	56	Shure Electronics Ltd.	62
B.I.E.T.	27			Sinclair Radionics Ltd.	66, 67, 70, 71
Bi-Pak Semiconductors	90, 91	K.E.F. Electronics Ltd.	18	SME Ltd.	20
Bi-Pre-Pack Ltd.	78, 86	Keytronics Ltd.	137	Smith, G. W. (Radio) Ltd.	94, 95, 96, 97
Black, J.	135			SNS Communications Ltd.	26
Blore-Barton Ltd.	52	Luskys Radio Ltd.	76	Soka SRL	135
Brittec	50	Ledon Instruments Ltd.	36	Sonax Electronics	51
Bull. J. (Electrical) Ltd.	107	Leavers-Rich Equipment Ltd.	50	Sowler, E. A., Ltd.	135
		Levell Electronics Ltd.	1	Stramech Eng. Ltd.	46
		Light Soldering Developments Ltd.	33	Studio Electronics	136
Cardross Eng. Co. Ltd.	56	Limose Electronics Ltd.	54	Sugden, J. E., Ltd.	50
Cavern Electronics	59	Linstead Electronics	22		
Chilimead Ltd.	98, 136, 138	London Central Radio Stores	136	Teleprinter Equipment	103
Cinortelle Ltd.	88	Longs Ltd.	54	Teletype Products (Tektronix U.K.) Ltd.	60
Colomog Electronics	93, 104			Teleradio, The (Edmonton) Ltd.	135
Consumer Microcircuits	17, Readers Card	Macfarlane, W. & B.	86	Television Magazine	54
Cosmocord Ltd.	42	Manor Engineering	59	Telcon Metals Ltd.	26
Crichton, J.	79	Marconi Instruments	Cover ii	Telford Products Ltd.	21
Croydon Precision Inst. Co.	52	Marshall, A., & Sons (London) Ltd.	83	Texas Instruments Ltd.	37
C.T. Electronics	77	Mavis	69	Thorn Radio Valves and Tubes Ltd.	65
		McKnight Crystal Co.	135	Toyo Communication Equipment Co. Ltd.	38
		McLennan Eng. Co. Ltd.	58	Trader Year Book	47
		Mills, W.	75	Trannies	85
Decon Laboratories Ltd.	44	Milward, G. F.	87		
Dexter & Co.	137	Modern Book Co.	136	United-Carr Supplies Ltd.	44
Dixons Technical (CCTV) Ltd.	41	Motorola Semiconductors Ltd.	30		
Douglas Electronic Industries Ltd.	136	M.O. Valve Co. Ltd.	64	Valradio Ltd.	27
Drake Transformers Ltd.	28	Mullard Ltd.	15, 24, 25	Vitavox Ltd.	53
Dymar Electronics	12	Multicore Solders Ltd.	Cover iv	Vortexion Ltd.	57
		Nombrex Ltd.	46		
Eddystone Radio Ltd.	31			Walmore Electronics	68
Electronic Brokers	99, 100, 101, 135	Olson Electronics Ltd.	43	Watts, Cecil E., Ltd.	135
Electro-Tech Co.	88			Wayne Kerr, The, Co. Ltd.	10
Electrovalve	81	Parker, A. B.	36	West Hyde Developments Ltd.	76
English Electric Valve Co. Ltd.	63	Patrick & Kinnie	82	Westinghouse Electric S.A.	19
ERG Industrial Corp. Ltd.	133	Philips Electrical	48, 49	West London Direct Supplies	88
ESI Nuclear	43	Plessey (Garrard) Ltd.	8, 9	Wilkinson, L. (Croydon) Ltd.	80
		Powertran Electronics	74		
		Practical Wireless	53		
		Practical Electronics	84	Yates Electronics	134
Ferroglyph Co. Ltd.	16				
Fi-Comp Electronics	53	Quality Electronics Ltd.	36		
Future Film Developments	59	Quartz Crystal Co., Ltd.	136	Z. & I. Aero Services Ltd.	105
Fyde Electronic Laboratories Ltd.	31				

Printed in Great Britain by Southwark Offset, 25 Lavington Street, London, S.E.1, and Published by the Proprietors, I.P.C. ELECTRICAL-ELECTRONIC PRESS LTD., Dorset House, Stamford St., London, SE1 9LU telephone 01-261 8000. *Wireless World* can be obtained abroad from the following: AUSTRALIA and NEW ZEALAND: Gordon & Gotch Ltd. INDIA: A. H. Wheeler & Co. CANADA: The Wm. Dawson Subscription Service, Ltd. GORDON & GOTCH LTD. SOUTH AFRICA: Central News Agency Ltd.; William Dawson & Sons (S.A.) Ltd. UNITED STATES: Eastern News Co., 304 West 11th Street, New York 14. **CONDITIONS OF SALE AND SUPPLY.** This periodical is sold subject to the following conditions namely that it shall not without the written consent of the publishers first given be lent, re-sold, hired out or otherwise disposed of by way of Trade at a price in excess of the recommended maximum price shown on the cover, and that it shall not be lent, re-sold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or allied to or as part of any publication or advertising, literary or pictorial matter whatsoever.


"It's impossible."

*"Well, if I hadn't tested it myself,
I'd never have believed it."*

"It can't be done."

*"That small, that reasonable,
and that accurate
— it's quite fantastic!"*

*"I've never seen
anything like it."*

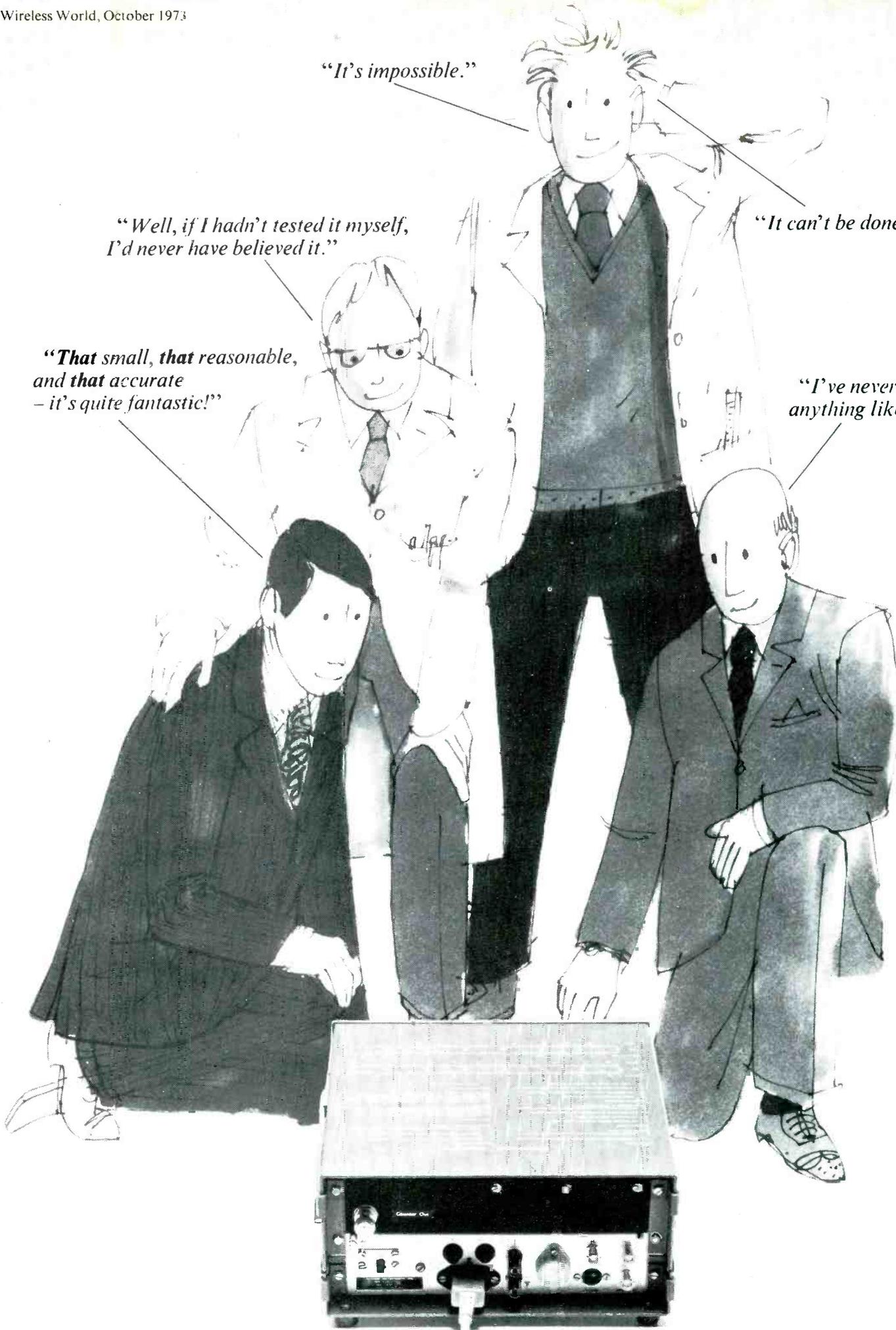

WW-002 FOR FURTHER DETAILS

Ersin Multicore- the international solder

Ersin Multicore 5-Core Solder


The proved superiority of ERSIN Multicore Solder for over thirty years is due to many factors. We have specialised throughout this period in the manufacture of cored solders. Consequently our research and manufacturing staff have been able to devote all their energies to the development of Multicore Solders. All alloys are of highest purity, carefully formulated and checked.

Our unsurpassed ERSIN flux is rigorously tested before and after it is incorporated in the solder wire. Our five separate cores of flux ensure flux continuity, leave only an ultra-thin layer of solder separating flux from work for instant wetting and provide a more accurate ratio of flux to solder. It is therefore possible to

use less solder and obtain greater reliability.

Our Quality Control at all stages of manufacture is guaranteed and recorded by the batch number on every reel.


Needle fine gauges

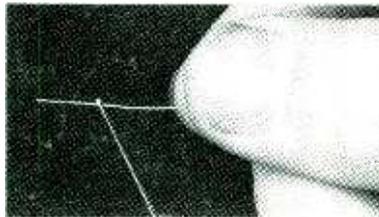

In addition to our standard range of wire diameters (10-22 swg: 3.2-0.7 mm) supplied on 2½ kg and ½ kg reels we also mass-produce needle-fine gauges (24-34 swg: 0.56-0.23 mm) on 250 g reels for microminiature soldering applications—still with 5 Cores of flux.

Savbit Solder

One of our most popular special ERSIN Multicore Solder alloys is SAVBIT alloy. Compared with ordinary tin/lead solders it dramatically reduces the erosion of soldering iron bits, copper wires and printed circuit conductors. It also saves costs and increases reliability. SAVBIT alloy containing 5-Cores ERSIN 362 flux has received special Ministry approval—under DTD. 900/4535 for Military applications.

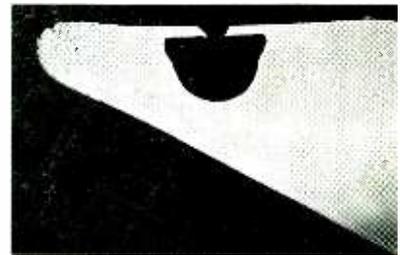

Sectioned iron-plated bit, after 40,000 simulated operations using 60/40 Solder.



Sectioned iron-plated bit, after 40,000 simulated operations using SAVBIT Solder.

ALLOY

Composition
(nominal major elements)

50/33/17 Sn/Pb/Cd
62/36/2 Sn/Pb/Ag
62/35.7/2/0.3 Sn/Pb/Ag/Sb
63/36.7/0.3 Sn/Pb/Sb
60/40 Sn/Pb
60/39.7/0.3
50/50 Sn/Pb
50/49.7/0.3 Sn/Pb/Sb
50/48.5/1.5 Sn/Pb/Cu
45/55 Sn/Pb
40/60 Sn/Pb
40/59.7/0.3 Sn/Pb/Sb
30/70 Sn/Pb
20/80 Sn/Pb
15/85 Sn/Pb
Pure Tin
95/5 Sn/Sb
5/93.5/1.5 Sn/Pb/Ag

Grade

Ti.C
LMP
Sn62
Sn63
K
Sn60
F
Sn50
Savbit 1
R
G
Sn40
J
V
—
P.T
95A
H.M.P.

Melting Temperature

Solidus Liquidus

°C °C
145 145
179 179
179 179
183 183
183 188
183 188
183 212
183 212
183 215
183 224
183 234
183 234
183 255
183 273
225 290
232 232
236 243
296 301

Specification

DIN 1707
DIN 1707
QQ-S-57 1E
QQ-S-57 1E
B.S. 219
QQ-S-57 1E
B.S.219
QQ-S-57 1E
DTD 900/4535
DIN 1707
B.S.219
B.S.219
QQ-S-57 1E
B.S.219
B.S.219
—
B.S.3252
B.S.219
B.S.219



For full information on these and a Selector Guide to other MULTICORE products please write on your Company's letterhead direct to:
Multicore Solders Limited, Maylands Avenue, Hemel Hempstead, Hertfordshire HP2 7EP.
Tel: Hemel Hempstead 3636 Telex: 82363