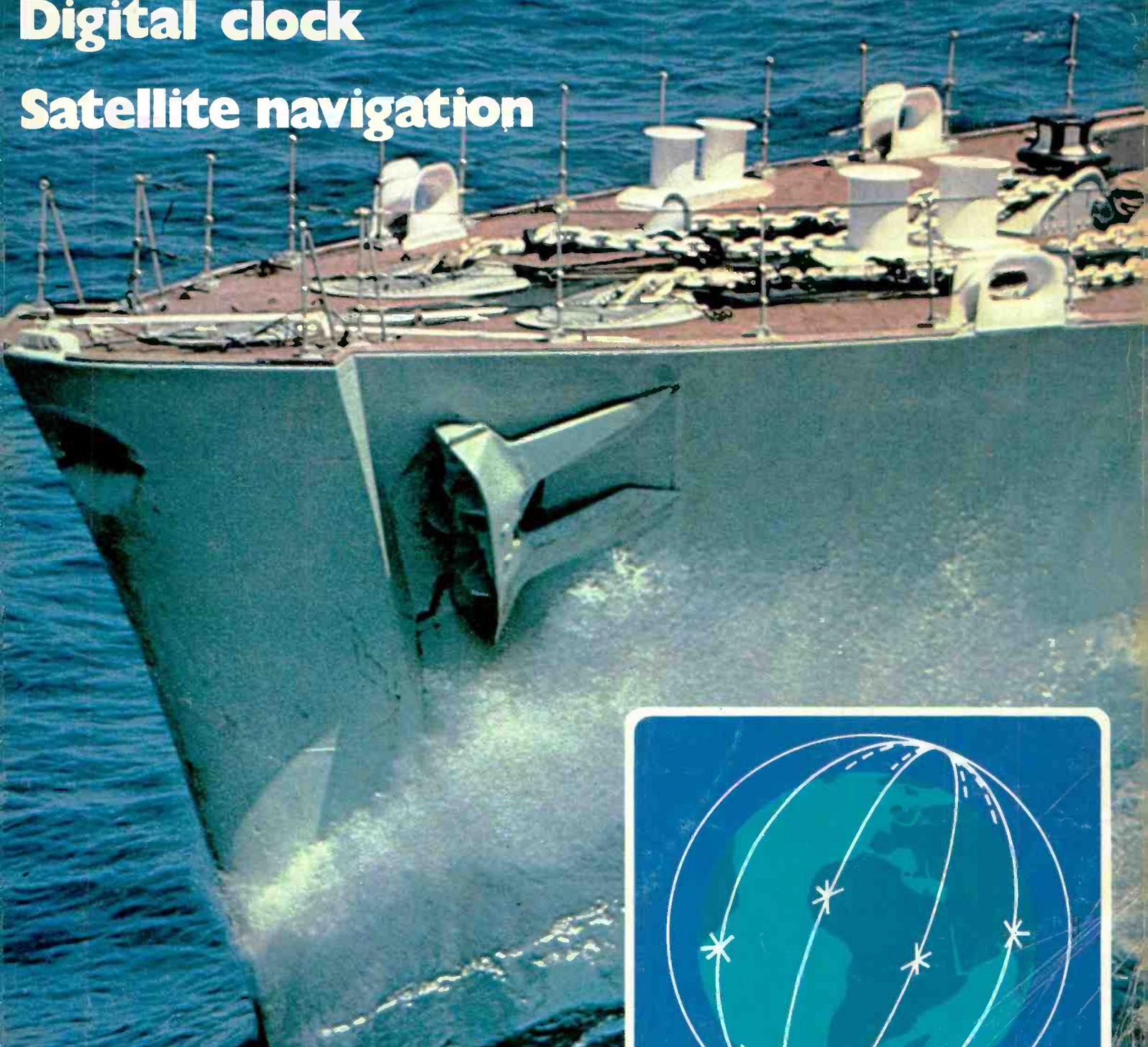


wireless world

FEBRUARY 1975 30p

Digital clock

Satellite navigation



Australia	80 Cents	Malaysia	M \$2.60
Belgium	Fr. 52.00	New Zealand	78 Cents
Canada	\$1.10	Norway	Kr. 7.50 inkl. Moms
Denmark	Kr. 9.00	South Africa	77 Cents
Finland	Fmk 4.50	Spain	Pras 65.00
Germany	Dm 4.00	Sweden	Kr. 5.35 inkl. Mom.
Holland	Dfl. 3.75	Switzerland	Fr. 4.70
Israel	1 ₪3.95	U.S.A.	\$1.10
Italy	L. 700		



Vital Issues

The issues are quite regular—and they discuss issues of vital importance to everyone who uses electronic test equipment.

The periodical, *Marconi Instrumentation*, which is mailed out free to all **mi** customers three times annually, contains technical articles about our latest instruments and up-to-the-minute information on their application to the solutions of measurement problems. It is written by engineers for engineers in English with summaries in four other languages.

And that's not all, by any means. **mi Contact** is a newspaper published six times a year to keep you

in touch with news and progress in the measurement business. Then there are our hardback publications, too. Already, there is a volume on TV Video Transmission Measurement written by the Head of BBC Measurement Systems Laboratory, and another book discusses the techniques and development of 'white noise' testing. Shortly we will be publishing a book on pulse code modulation, by a senior Post Office engineer.

There are technical data sheets, applications notes, catalogues, concise catalogues and product brochures, all aimed to help you measure.

Are you reading us?

mi: THE COMMUNICATORS

MARCONI INSTRUMENTS LIMITED

Longacres • St. Albans • Hertfordshire AL4 0JN • England • Telephone: St. Albans 59292 • Telex: 23350.

LOW COST VOLTMETERS



LEVELL

PORTABLE INSTRUMENTS


These highly accurate instruments incorporate many useful features, including long battery life. All A type models have $3\frac{1}{4}$ " scale meters, and case sizes 5" x 7" x 5". B types have 5" mirror scale meters and case sizes 7" x 10" x 6".



A.C. MICROVOLTMETERS

VOLTAGE & dB RANGES: 15 μ V, 50 μ V, 150 μ V... 500V f.s.d.
Acc. $\pm 1\% \pm 1\%$ f.s.d. $\pm 1\mu$ V at 1 kHz. - 100, - 90... + 50dB,
scale - 20dB/+ 6dB rel. to 1mW/600 Ω .
RESPONSE: ± 3 dB from 1 Hz to 3MHz, ± 0.3 dB
from 4Hz to 1MHz above 500 μ V. Type TM3B can be
set to a restricted B.W. of 10Hz to 10 kHz or 100 kHz.
INPUT IMPEDANCE: Above 50mV : > 4.3M Ω < 20pf.
On 50 μ V to 50mV : > 5M Ω < 50pf.
AMPLIFIER OUTPUT: 150mV at f.s.d.

type **£65** type **£80**
TM3A TM3B

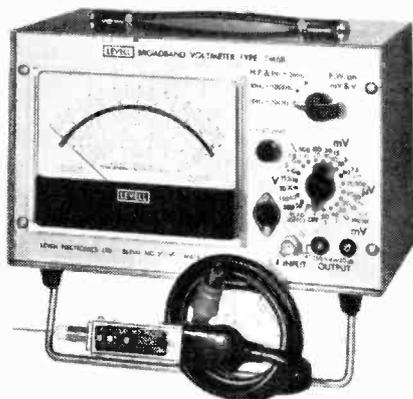

BROADBAND VOLTMETERS

H.F. VOLTAGE & dB RANGES: 1mV, 3mV, 10mV... 3V f.s.d.
Acc. $\pm 4\% \pm 1\%$ of f.s.d. at 30MHz. - 50dB, - 40dB, - 30dB
to + 20dB. Scale - 10dB/+ 3dB rel. to 1mW/50 Ω . ± 0.7 dB
from 1MHz to 50MHz. ± 3 dB from 300kHz to 400MHz.

L.F. RANGES: As TM3 except for the omission of 15 μ V and 150 μ V.
AMPLIFIER OUTPUT: Square wave at 20Hz on H.F. with
amplitude proportional to square of input. As TM3 on L.F.


type **£110** type **£125**
TM6A TM6B



D.C. MICROVOLTMETERS

VOLTAGE RANGES: 30 μ V, 100 μ V, 300 μ V... 300V.
Acc. $\pm 1\%$, $\pm 2\%$ f.s.d., $\pm 1\mu$ V. CZ scale.
CURRENT RANGES: 30 pA, 100 pA, 300 pA, 300 mA.
Acc. $\pm 2\%$, $\pm 2\%$ f.s.d., ± 2 pA. CZ scale.
LOGARITHMIC RANGE:
 $\pm 5\mu$ V at $\pm 10\%$ f.s.d., ± 5 mV at $\pm 50\%$ f.s.d., ± 500 mV at f.s.d.
RECORDER OUTPUT: ± 1 V at f.s.d. into > 1k Ω

type **£67**
TM10

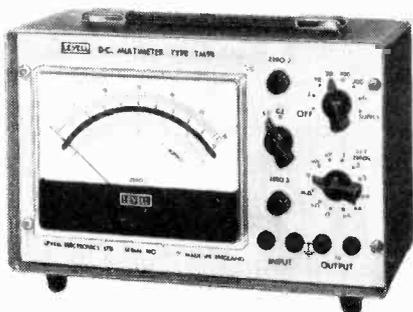

D.C. MULTIMETERS

VOLTAGE RANGES: 3 μ V, 10 μ V, 30 μ V... 1kV.
Acc. $\pm 1\% \pm 1\%$ f.s.d. $\pm 0.1\mu$ V. LZ & CZ scales.
CURRENT RANGES: 3pA, 10pA, 30pA... 1mA (1A for TM9BP)
Acc. $\pm 2\% \pm 1\%$ f.s.d. ± 0.3 pA. LZ & CZ scales.
RESISTANCE RANGES: 3 Ω , 10 Ω , 30 Ω ... 1kM Ω linear.
Acc. $\pm 1\%$, $\pm 1\%$ f.s.d. up to 100M Ω .
RECORDER OUTPUT: 1V at f.s.d. into > 1k Ω on LZ ranges.

type **£95** type **£114**
TM9A TM9BP

LEVELL ELECTRONICS LTD.

Moxon Street, High Barnet, Herts. EN5 5SD
Tel: 01-449 5028/440 8686

Prices include batteries and U.K. delivery. V.A.T. extra.
Optional extras are leather cases and mains power units.
Send for data covering our range of portable instruments.



Who else but the Italians could have produced the most sophisticated range of mixing and fading facilities ever offered in such a beautifully designed range of equipment.

Yet still apply the most precise and exacting manufacturing standards to provide the operational stability and reliability such complex electronics demand.

This is why we are able to guarantee all Goodmans/Galactron equipment for three years.

And your guarantee will be signed personally by the quality controller who tests it before it leaves the factory in Italy.

Galactron Mk 10 Stereo Integrated Amplifier

A remarkably compact pre and power amp combination with 90 watts RMS per channel. Features 5 mixable stereo inputs, 5 plug-in-modules—two of which can be cross-faded by slide potentiometer.

Galactron Mk 16 Stereo/Quad Amplifier

No comparable equipment has all these 3 functions. 5 inputs, independently mixable and equalised by plug-in modules. Twin graphic equalisers having

10 filters each ($\pm 16\text{dB}$) at octave intervals from 32Hz to 16kHz. Plug-in quadrophonic decoder panels for discrete and matrix systems allied to 4 output level controls.

Galactron Mk 100 Stereo Power Amplifier

Originally designed as a monitor amp for recording studios, the Mk 100 is designed for use with the Mk 16 preamplifier. 100 watts RMS per channel output.

Full facts and figures are available from Goodmans Loudspeakers Limited, Down Road, Havant, Hants.

 **Goodmans**
GALACTRON

WW—080 FOR FURTHER DETAILS


A member of The Thorn Group



Module
SP25 Mk IV

Module
Zero 100SB

Module 86SB

Hi-fi starts here

The quality of the sound you hear from your hi-fi depends on the quality of transcription from the record—so you won't want to skimp on quality. When you choose your turntable deck, you'll probably choose Garrard.

Fifty-five years of Garrard experience and know-how in producing top-quality record playing equipment is concentrated in the range of record playing units now available. There are three modules complete with attractive bases and lift-off covers, ready-wired for instant installation.

The SP25 mk IV is the most popular budget unit on the market. It features the famous Garrard four-pole synchronous motor to ensure smooth, constant speeds, the finely engineered pickup arm with resiliently mounted counterbalance weight, calibrated bias compensation and damped cueing.

The 86Sb represents just about the best buy in hi-fi today. It incorporates belt drive, the famous Garrard four-pole synchronous motor, high inertia turntable, contoured mat, precision pickup arm with fine stylus force adjustment and bias compensation calibrated for elliptical and conical styli.

The Zero 100SB has every quality feature you could expect to find on a record deck. What makes it truly unique is the tangential tracking pickup arm virtually eliminating tracking error and consequent harmonic distortion. Other features include, adjustable, resiliently-mounted, counterbalance weight, fine stylus force

adjustment, magnetic bias compensation calibrated for elliptical and conical styli, high inertia turntable with contoured mat, a record counter and the famous Garrard four-pole synchronous motor.

Use the coupon to obtain your free copy of the full-colour brochure on the complete range of Garrard record playing units.

Garrard
A PLESSEY QUALITY PRODUCT

Garrard, Newcastle Street, Swindon, Wiltshire.


Please send me your full-colour brochure describing the famous Garrard range of top-quality hi-fi equipment.

Name _____
Address _____

ANDERS MEANS METERS...


KESTREL RANGE

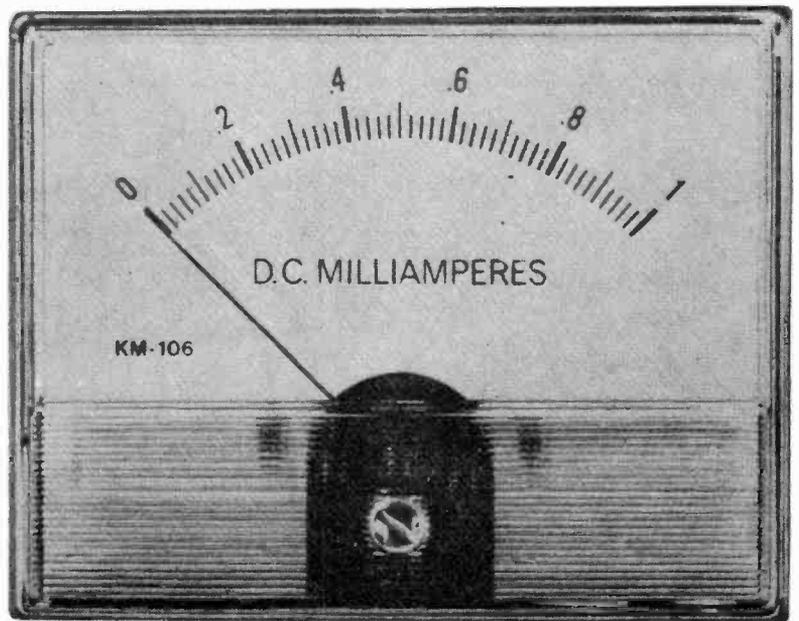- Modern styling, with clearfront plastic case.
- Seven models, scale lengths from 1.3" to 5.25".
- Extensively used by many leading manufacturers of electronic and electrical equipment.
- Available in all ranges, moving coil and moving iron.
- Competitive prices.



Anders provide what is probably the largest range of meters available from a single source in Europe: MC/MI, dynamometer, vibrating reed, electrostatic, etc. in over 100 case styles and sizes, a few of which are shown below.

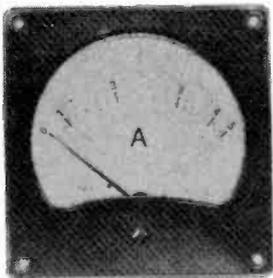
Popular models and ranges are stocked in depth while a specially equipped instrument department enables swift production of non-standard ranges and scales, to suit individual customer requirements, in large or small quantities.



Vulcan Moving Iron. 4 models, 1.5", 1.8", 2.7", 3.7" scales. Voltmeters, ammeters and motor starting meters.



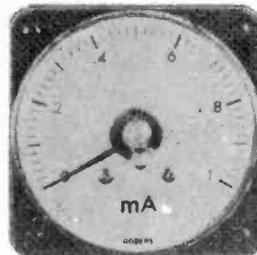
Profile 350 edgewise 4.3" scale. DC moving coil and AC moving coil rectified. Horizontal or vertical mounting.




Oxford Long Scale 240°. 2 models, 5.5", 8" scales. DC moving coil and AC moving coil rectified.



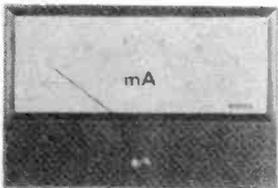Models KE1 and KE2 Miniature Edgewise Meters. Nominal scale lengths 1.2" and 2". Available in sensitivities from 50 microamps Moving Coil.



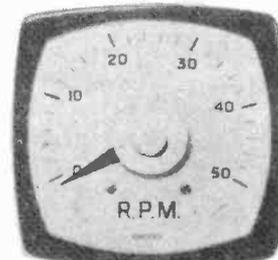Regal Range 100° flattened arc. 2 models 2.5" and 3.2" scales. Taut band. DC moving coil and AC moving coil rectified.



Stafford Long Scale 240 6 models, 3.5"—11.5" scales. DC moving coil, AC moving coil rectified, AC moving iron. Also 98° scale.



Lancaster Long Scale 240°. 2 models, 4", 5.5" scales. DC moving coil and AC moving coil rectified.

ANDERS ELECTRONICS LIMITED 48/56 Bayham Place, Bayham Street, London, N.W.1. Telephone 01-387 9092.

Manufacturers and distributors of Electrical Measuring Instruments. Sole U.K. distributors of FRAHM Resonant Reed Frequency Meters and Tachometers. Manufacturers of purpose built electrical and electronic equipment to customers requirements.

WW—145 FOR FURTHER DETAILS

New automatic digital bridge from Wayne Kerr



Wayne Kerr's new B900 is one of the best value-for-money bridges in the world.

It is universal, has a wide range, and gives immediate digital readout of resistive and reactive terms—simultaneously.

On all ten ranges, for every type of measurement available, the displays provide a complete indication of the numerical value (up to 19999), polarity, decimal points and units—automatically and in half a second.

Direct measurements of Q, dissipation and dc volts. 2, 3, & 4-terminal. Automatic lead compensation. 4-Quadrant: +ve or -ve C, L, 1/C, G and R.

Overall coverage:

10 $\mu\Omega$ - 200M Ω 1nH - 20 kH
 0.001pF - 20,000 μ F 10p Ω - 200 Ω

Accuracy: 0.1% (10 Ω -200M Ω), 0.3% (10m Ω -10 Ω) in all quadrants. Frequency: 1kHz Outputs: Analog and TTL.

For more information phone Bognor (02433) 25811, or fill in the coupon.

Please send me details of the B900.

For the attention of Mr. _____

Company name and address _____

WW—Feb

Post to Wayne Kerr, Durban Road, Bognor Regis, Sussex PO22 9RL

WAYNE KERR

A member of the Wilmot Breeden group.

WW—129 FOR FURTHER DETAILS

50mHz OSCILLOSCOPE TYPE C1-64

Made in USSR



Power supplies: 115/230V \pm 10%, 50-40 Hz.

Dimensions: 300 \times 200 \times 420 mm.

Weight: 19kg.

PRICE, complete with full complement of connectors, cables, adaptors and accessories **£470** exclusive of VAT.

Lightweight, portable, transistorized, dual trace oscilloscope.

Display:

Rectangular CRT 6 \times 10 div. (48 \times 80mm) with illuminated graticule.

Vertical deflection:

Two input channels operated in alternate or chopped modes or algebraically summed.

Bandwidth:

DC to 50mHz DC coupled.
3Hz to 50mHz AC coupled.

Sensitivity:

Channel I and II: 5mV/div. to 10V/div.
Summing mode: 1mV/div. max.

Horizontal deflection:

Sweep 'A'—0.1 μ s/div. to 1s/div.
Sweep 'B'—0.1 μ s/div. to 50ms/div.

Sweep delay:

1 μ s to 10s.

Time Base Modes:

'A' only; 'B' only; 'A' brightens 'B'.

'B' delayed by 'A'; 'A' and 'B' chopped or alternate.

Z & I AERO SERVICES LTD.,

44A WESTBOURNE GROVE, LONDON W2 5SF

Tel: 727 5641

Telex: 261306

WW—045 FOR FURTHER DETAILS

British...

Wherever there is appreciation of fine sound reproduction, insistence is upon British loudspeaker systems.



Renowned among the discerning for their outstanding quality, the products of Mordaunt-Short Ltd. are specified by professionals and by enthusiasts the world over. Choose them for your home - where the finest most concerns you.



...at its best.



Mordaunt-Short Ltd

Designers and Manufacturers of Quality Loudspeaker Systems

To receive immediately full information and the name and address of the Stockists nearest to you, please complete this coupon and return it to us direct.

Name


Address

Mordaunt-Short Ltd. The Causeway, Petersfield, Hampshire, GU31 4JT. Tel: Petersfield (STD 0730) 4631-5

WW—049 FOR FURTHER DETAILS

W2

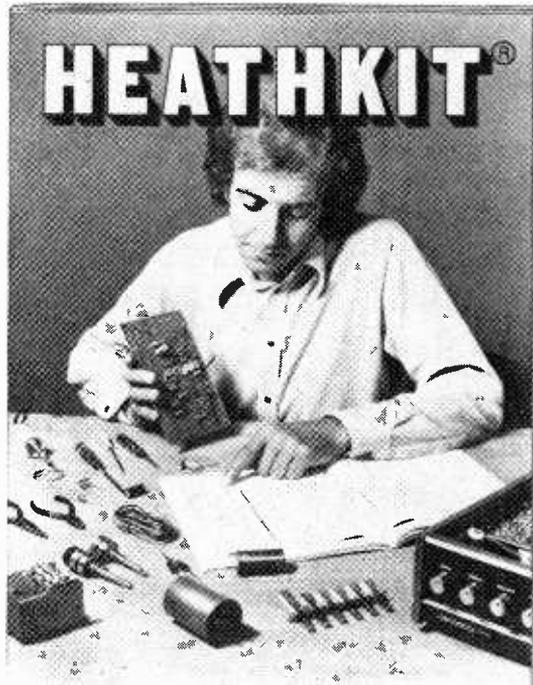Complete the coupon and we'll send you our new catalogue. Completely free.



The new Heathkit catalogue is now out. Full as ever with exciting, new models. To make building a Heathkit even more interesting and satisfying.

And, naturally, being Heathkit, every kit is absolutely complete. Right down to the last nut and bolt. So you won't find yourself embarrassingly short of a vital component on a Saturday evening—when the shops are shut.

You'll also get a very easy to understand instruction manual that takes you step by step through the assembly.

Clip the coupon now and we'll send you your free copy to browse through.

With the world's largest range of electronic kits to choose from, there really is something for everyone.

Including our full range of test equipment, amateur radio gear, hi-fi equipment and many general interest kits.

So, when you receive your catalogue you should have hours of pleasant reading.

And, if you happen to be in London or Gloucester, call in and see us. The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory in Bristol Road.

At either one you'll be able to see for yourself the one thing the catalogue can't show you.

Namely, how well a completed Heathkit performs.

Heath (Gloucester) Limited, Dept. WW-25, Bristol Road, Gloucester, GL2 6EE. Tel: Gloucester (0452) 29451.

The new solid-state SB-104 Transceiver.



An oscilloscope from the Heathkit range.



Digital electronic car clock/elapsed timer.



The new Heathkit catalogue. Out now. FREE.

To: Heath (Gloucester) Limited, Dept. WW-25 Gloucester, GL2 6EE. Please send me my free Heathkit catalogue.

Name _____ Address _____

Postcode _____

Remember easy terms are available with the Heathkit Monthly Budget Plan.



Three Ways To Easier Colour Servicing

1.



Colour Bar Generator

- * 10 test signals
- * Variable amplitude of colour burst signal
- * 4 preselected channels on the RF output
- * Small size, low weight

2.



Convergor

- * Battery operated
- * UHF output covers 10 channels
- * Video signal can be switched off for purity adjustment

3.



T.V. Visual Field Strength Meter

- * Varicap tuner with four channel selectors
- * High sensitivity
- * 6" picture tube
- * Mains or battery operation.

The speed and efficiency of your colour servicing with this Decca test equipment will save you time and therefore money. Send us the coupon or give us a call and we'll send you the full details



Decca Radio & Television Ltd.
Educational and Industrial Services Division
Ingate Place, Queenstown Road,
London SW8 3NT (01-622 6677)

Please send me further details of your colour TV test and service equipment:

Name.....

Address.....

WW2



Now suitable for U.K., European and American voltages...

Minimod, the versatile British made range of encapsulated power supplies first introduced in 1973, has now been extended to cover European and North American mains voltages (and is interchangeable with most American types). Normally available ex-stock, all units are fully stabilised with fold back current limiting – the 5V models have over voltage crowbar too!

STANDARD MODELS

Type Number	Output Voltage	Output Current Amps	Short Circuit Current mA (Typical)	% Regulation Line and Load (Typical)
PU01	5 ± 0.1	0.5	370	0.3
PU02	5 ± 0.1	1.0	770	0.5
PU03	15-0-15 ± 0.2	0.10	37	0.1
PU04	15-0-15 ± 0.2	0.20	84	0.1
PU05	12-0-12 ± 0.2	0.12	45	0.1
PU06	12-0-12 ± 0.2	0.24	120	0.2

Input voltage ranges 103 - 126V, 200 - 240V, 210 - 250V. Frequency 50 - 400 Hz all types.

Comprehensive specification given in brochure GT 29b which is available on request.

★SPECIAL DESIGN SERVICE

Custom built units for applications requiring different specifications are produced as part of our standard service. Try us first.



Specialists in Electronic Transformers & Power Supplies.


GARDNERS

TRANSFORMERS LIMITED


Gardners Transformers Limited, Christchurch, Dorset, BH23 3PN
Tel. Christchurch 2284 (STD 0201 5 2284) Telex. 41276 GARDNERS XCH
WW-056 FOR FURTHER DETAILS

Years of research...

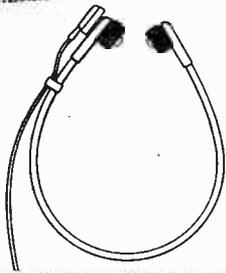
... on accessories for dictating machines, tape recorders,
tele-communications and electro-acoustic equipment, etc.




STETOCLIP
JUNIOR 60
HEADSET

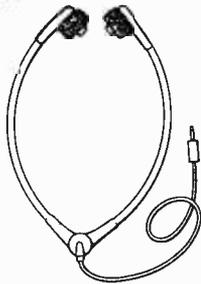

STETOCLIP
LIGHTWEIGHT
HEADSET

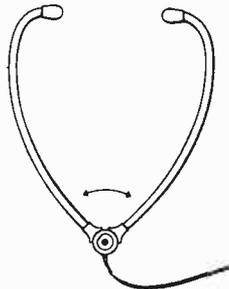


STETOCLIP
SENIOR
HEADSET

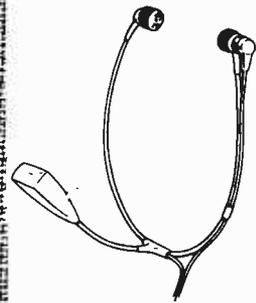


STETOMIKE
BOOM MICROPHONE
HEADSET




PLASTIC
EARHANGERS

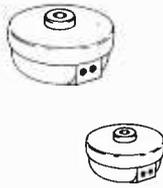

STANDARD &
SUB-MINOR
EARPHONES

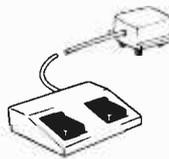

FOOTSWITCHES

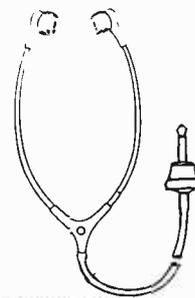


HDSPITAL
HEADSETS



2.5 mm and 3.5 mm
JACK PLUGS &
SOCKETS & SUB-
MINIATURE
SWITCHES



DANASOUND HEADSET

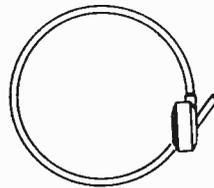

THROAT
MICROPHONE



DANASONIC
INDUCTION AUDIO
LOOP RECEIVER

Danavox
INTERNATIONAL

DANAVOX (GT. BRITAIN) LTD.

Electro-Acoustic Components and Hearing Aids
"BROADLANDS" BAGSHOT ROAD,
SUNNINGHILL, ASCOT, BERKS.
TEL: 0990 23732/6; TELEX 847584


WW-067 FOR FURTHER DETAILS

5 good reasons why Shibaden colour cameras are the best!




HV 1500
Compact, highly mobile unit, the only colour CCTV camera available with a single one-inch filter integrated colour vidicon tube.

FP 1500 As the HV 1500 but fitted with a 3" viewfinder for studio use.

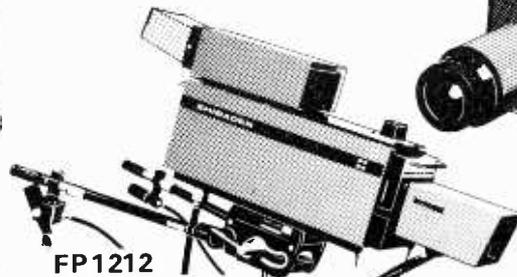

FP 1212
A one-inch three tube Plumbicon® Camera with freely detachable electronic viewfinder. Ideal for outside broadcast work and studio.

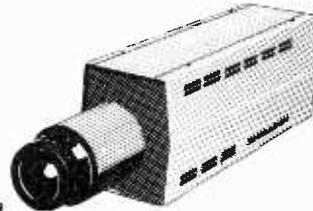

HV 1100
An extremely compact, lightweight three tube colour TV camera ideal for surveillance and observation applications.



FPC 1000
A vidicon/chalicon camera designed to meet all NTSC and PAL requirements.

® Trade Mark N.V. Philips



The Shibaden range of colour cameras are compact, easy to operate and versatile in their application through educational, medical, business and broadcasting studios. Shibaden Colour Cameras are designed with the customer in mind both from an application and performance stand point. They are fully backed by Shibaden's in-depth opto-electronic technology, which has proved to be superior through many years of application in a vast range of broadcasting equipment.

When you buy Shibaden you buy the best.
For further details on the Shibaden range of Colour Cameras, contact the Technical Service Department.

Hitachi Shibaden (UK) Limited
BROADCAST & CCTV EQUIPMENT MANUFACTURERS
Lodge House · Lodge Road · Hendon · London NW4 4DQ. Telephone: 01-203 4242/6

WW—122 FOR FURTHER DETAILS

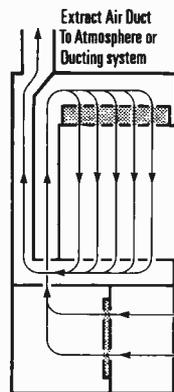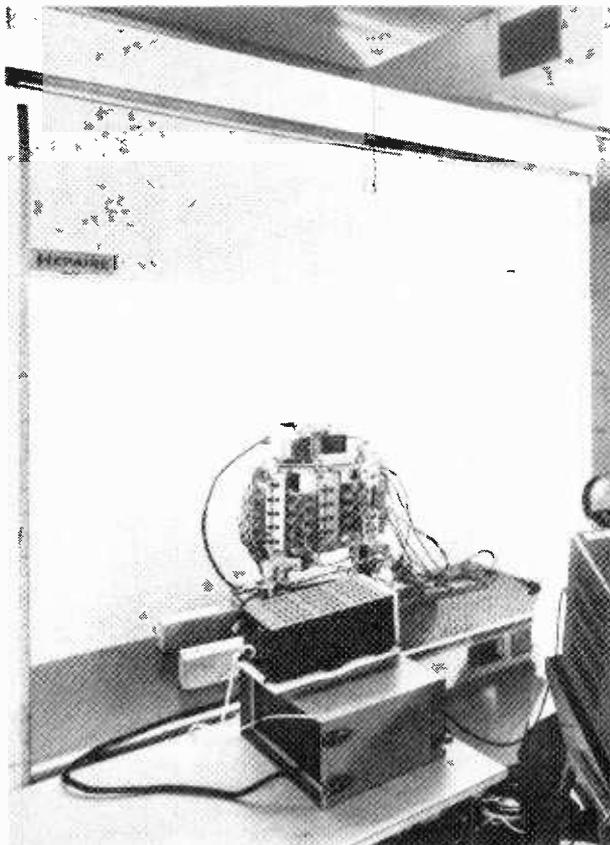Vertical Laminar Flow work stations by HEPAIRE



Provides vertical flow of filtered air. Free standing unit utilising minimum floor space. Uses standard single phase electrics. Clean design.

DESIGNED FOR SAFETY

Cabinet draws in air through pre-filter beneath work bench. Air is pressurised and passes through absolute filter vertically downwards and through perforated work surface. Dirty air is then extracted to atmosphere via extract duct mounted on top of cabinet.

Write for technical details.



HEPAIRE MANUFACTURING LTD
SPECIALISTS IN THE DESIGN AND MANUFACTURE OF INDUSTRIAL AND PHARMACEUTICAL CLEAN AIR EQUIPMENT
WATER LANE · STORRINGTON · SUSSEX RH20 3DN
Telephone: Storrington (STD 090-66) 2394

INCREASED PRODUCTION MEANS REPRESENTATION REQUIRED IN MANY U.K. AREAS
WW—051 FOR FURTHER DETAILS

The Greenwood guide to professional soldering.


The Ersa Multitip. A top-quality iron that's ultra-light, offering reliability so necessary to achieve constant production flow. A range of different shaped tips simply

push onto the stem of the iron. It has the unique advantage that you can change the element in seconds.



The Iso-Tip. A safe, high-powered iron which works anywhere without a mains lead. The breakthrough? Nickel Cadmium cells that are re-chargeable. (A charging stand is included for 240v or 115v A.C.) Each charge gives at least 60 soldering joints. Weight? Only 6oz.

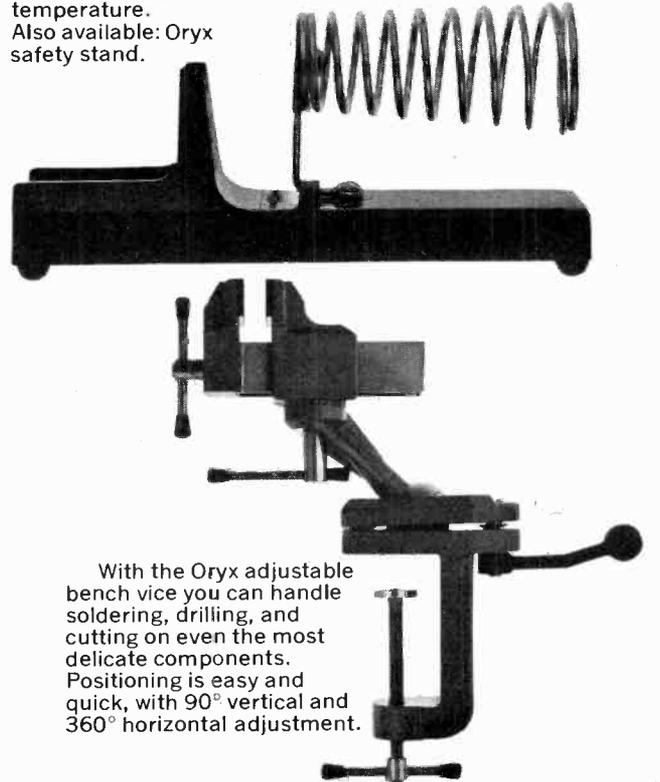
The Oryx 50. A temperature controlled mains soldering iron. (Temperature control within $\pm 2\%$.) Adjustment (200°-400°C) can be made whilst iron is operating using the same tip. Light, compact and easy to handle. A large 50W element loading gives rapid heating and high performance with constant tip temperature. Also available: Oryx safety stand.



The Ersa Sprint. Unique - it heats up to maximum temperature in only 10 seconds, and is the lightest gun on the UK market. Ideal for the service-man. With its lightweight (only 7oz.) and compact construction, it can be manoeuvred in even the most awkward areas.



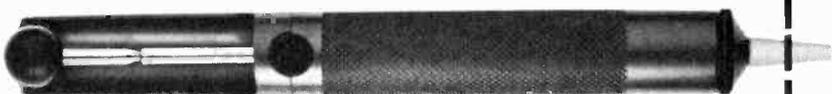Oryx SR3A desoldering tool. Ideal where components are tightly grouped. Instantly removes unwanted solder from printed circuits etc. Accurate, reliable, speedy, and safe.



Greenwood Electronics offer a range of highly advanced products specifically for professional soldering applications.

For more detailed information about the comprehensive Greenwood range, send us the coupon today.

Please send me more details about the Greenwood range of soldering equipment.

Name _____

Address _____

Greenwood Electronics

WW4


21 Germain Street, Chesham, Bucks, HP5 1LL
Tel: 02405 4808 Telex: 83647

Eddystone Radio



Economy! Simplicity! Reliability!

1830 Series C.W, M.C.W, A.M, S.S.B

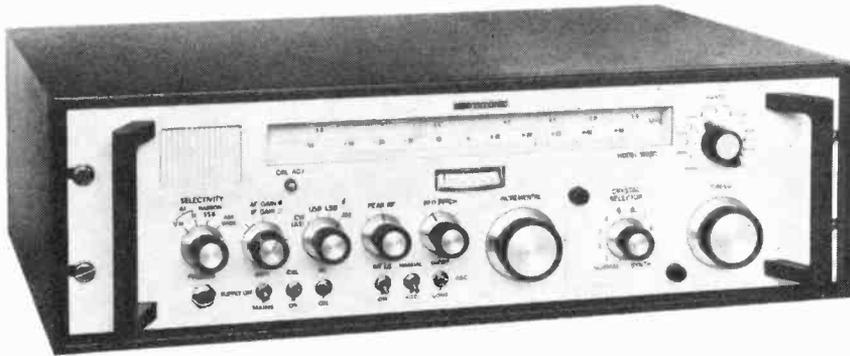

Crystal controlled
 Transistorized HF/MF
 general purpose receiver
 120 kHz – 30 MHz in 9 ranges
 Rack mounting as standard
 Cabinet optional extra
 AC or battery operation
 British MPT approved as
 ships reserve receiver
 DCA No. 10D/CA 10696

Illustrated brochure from:

Eddystone Radio Limited

Alvechurch Road, Birmingham B31 3PP. Tel: 021-475 2231. Telex 337081.

A member of Marconi Communication Systems Ltd

WW—047 FOR FURTHER DETAILS


However you view it...

...the choice is **Grampian**
 SOUND EQUIPMENT

GRAMPIAN REPRODUCERS LIMITED
 HANWORTH TRADING ESTATE, FELTHAM, MIDDLESEX.
 TELEPHONE: 01-894 9141. GRAMS: REAMP FELTHAM

X205

METER PROBLEMS?

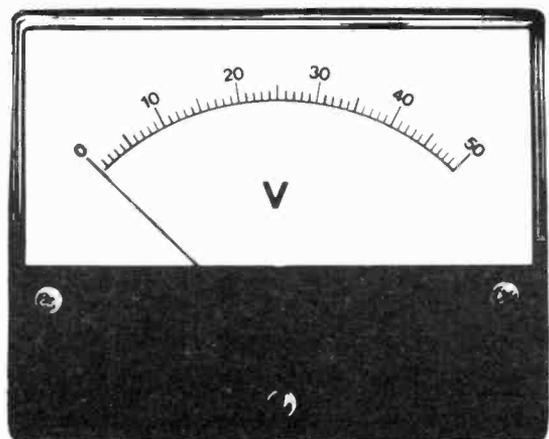


A very wide range of modern design instruments is available for 10/14 days' delivery.

Full Information from:

HARRIS ELECTRONICS (London)


138 GRAYS INN ROAD, W.C.1 Phone: 01/837/7937

WW—016 FOR FURTHER DETAILS

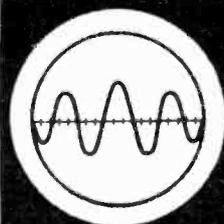


TUAC

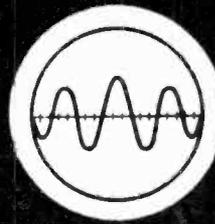TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
163 MITCHAM RD · LONDON SW17 9PG 01-672 3137/9080




MANUFACTURERS OF
ELECTRONIC &
AMPLIFICATION
EQUIPMENT, ALSO
QUALITY TRANSISTOR
EQUIPMENT.
OPEN MON-SAT
9.30am-6.00pm.


NEW TUAC POWER MODULES offering more power and quality than ever before

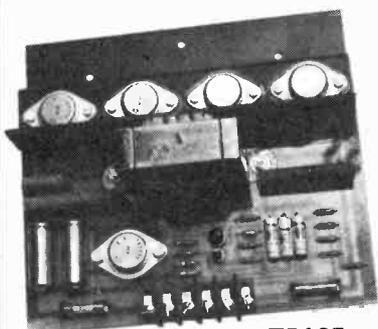

TP125
7 x 6½ x 3in.
★ 4 R.C.A. 150 watt 15 amp output transistors
★ 125 watts RMS continuous sine wave output
£17-00

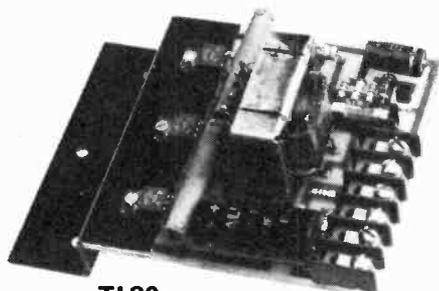

TL30
4 x 5½ x 2½ in.
£7-90
★ 30 watts RMS continuous sine wave output
★ 2 R.C.A. 40 watt output transistors

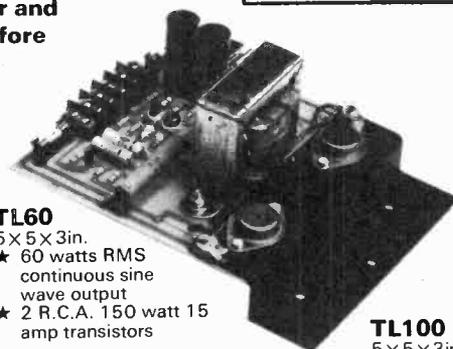

TL60
5 x 5 x 3in.
★ 60 watts RMS continuous sine wave output
★ 2 R.C.A. 150 watt 15 amp transistors
£11-50

TL100
5 x 5 x 3in.
★ 100 watts R.M.S. continuous sine wave output
★ 2 R.C.A. 150 watt 15 amp transistors
£13-20

TUAC DISCOTHEQUE MIXER WITH AUTO FADE **£26-50**

PANEL SIZE 18 x 4½ in. DEPTH 3 in.




Designed for the discerning D.J. of professional standard. Offering a vast variety of functions. Controls: Mic Vol; Tone, over-ride depth; auto/Manual Sw; Tape Vol; L & R Deck Faders; Deck Volume; Treble and Bass; H. Phon Vol Selector; Master Vol On/Off Sw. Max output 1V RMS.

Specification: Deck Inputs—50mV into 1mΩ; Deck Tone Controls *Treble +20 -10dB at 12kHz. Bass +22 -15dB at 40Hz; Mic input—200 ohms upwards. 2mV into 10kΩ; Mic Tone Control—Total Variation Treble 15dB. Total Variation Bass 10dB; Tape input—30mV into 47kΩ; Power Requirements—30-45 volts at 100mA.


- ★ Rugged layer wound driver transformer
- ★ Short—Open—and Thermal overload protection
- ★ Only 6 connections

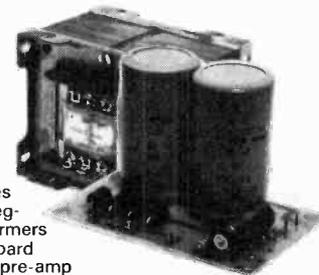Specification on all power modules: All output power ratings ±1dB; Output impedance 8-15 ohms; THD at full power 2% typically 1%; Input sensitivity 60mV into 10kΩ; Frequency response 20Hz-20kHz ±2dB; Hum and noise better than -70dB.



Power supplies vacuum impregnated Transformers with supply board incorporating pre-amp supply:

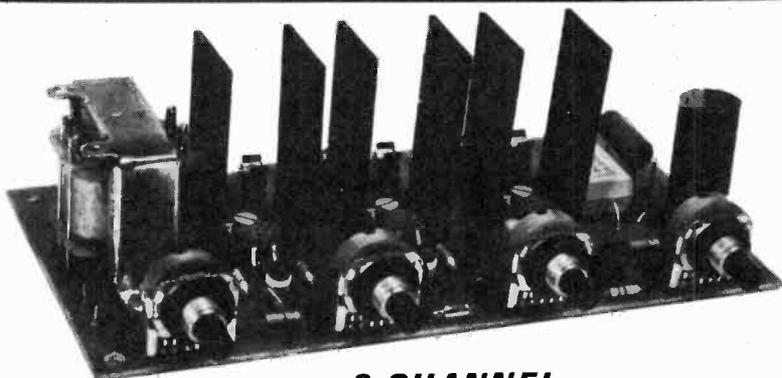PS 125 ±50 volts for one TP125 **£11-50**
PS 100 ±45 volts for one TL100 **£10-50**
PS 60 ±40 volts for one TL60 **£9-30**
PS 30 ±50 volts for one TL30 **£5-90**
PSU 2 for supplying disco mixer **£4-65**




3 CHANNEL LIGHT MODULATOR

- R.C.A. 8 Amp Triacs ● 1000W per channel
- Each channel fully suppressed and fused
- Master control to operate from 1W to 100W
- Full wave control—12 easy connections

£14-90

Single Channel Version 1500 watts **£6-60**

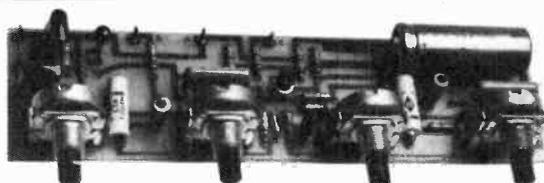ALL PRICES INCLUDE V.A.T. POST & PACKING FREE



PREAMPLIFIERS

All TUAC audio modules are constructed on glass fibre P.C. board, are ready assembled and fully tested. Low noise silicon and FET transistors together with H.S. carbon film resistors are used throughout. Extensive research has gone into various wide range tone control circuits producing superb sound quality from any signal.

VA08 Vol. Treble, Mid and Bass controls, Hi. IMP. FET. I/P. suitable Mid, Guitar, Radio, Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at 16kHz. Mid +20 -15dB at 1Hz. Bass +20 -10dB at 40Hz. **£4-90**

VA06 Vol. Treble and Bass controls. Sensitivity 8mV. Treble +28 -15dB at 12kHz. Bass +18dB at 40Hz. **£4-15**

Stockists, Callers only

ARTHUR SALLIS LTD, 28 Gardner St, BRIGHTON, Sussex. Tel. 65806
BRISTOL DISCO CENTRE, 86 Stokes Croft, BRISTOL 1. Tel. 41666
SODCOT, 9 The Friars, CANTERBURY. Tel. 60948
CALBARRIE AUDIO, 88 Wellington St, LUTON. Tel. 411733
A.1 MUSIC CENTRE, 88 Oxford St, MANCHESTER. Tel. 236 0340
DAMON ELECTRONICS, 99 Carrington St, NOTTINGHAM. Tel. 53880
MITCHELL ELECTRONICS, 64 Winchester St, SALISBURY. Tel. 23689
WEC LIGHTING, 35 Northam Road, SOUTHAMPTON. Tel. 28102

HOW TO ORDER BY POST

Make cheques/P.O.'s payable to TUAC (WW2). OR QUOTE ACCESS/BARCLAY CARD NO. and post to TUAC LTD (WW2) 163 MITCHAM ROAD, LONDON SW17 9PG. We accept phone orders against ACCESS/Barclay Card Holders. Phone 672-3137.

Infrared FILTERS

OCLI manufacture an extensive range of Infrared Filters covering the entire 1.0 to 30 micron spectral region.

Filters in these regions present an excellent solution to filtering out high-temperature radiation without appreciably limiting the signal from the source being observed. Moreover, they have proven capability over wide operating temperatures.

OCLI I.R. Filters are made to exact Customer specifications or a range can be supplied from stock.

Typical fields benefiting from OCLI I.R. Filters include:

- GAS ANALYSERS/DETECTION SYSTEMS
- INFRARED PASSIVE THERMAL IMAGING SYSTEMS
- FIRE DETECTION
- POLLUTION DETECTION
- OPTICAL PROXIMITY FUSES
- INFRARED SPECTROSCOPY
- INFRARED PHOTOGRAPHY
- SPACE RECONNAISSANCE

Write for the new OCLI catalogue and price list of stock I.R. Filters.

OCLI OPTICAL COATINGS LTD.
Hillend Industrial Estate,
Dunfermline, Fife KY11 5JE.
Tel. Inverkeithing 3631
(STD 038-34 3631).

OC-19D

WW-141 FOR FURTHER DETAILS

PRODUCTION TESTING


DEVELOPMENT

SERVICING

EDUCATION

POWER UNITS

NOW AVAILABLE WITH 3 VARIABLE OUTPUTS

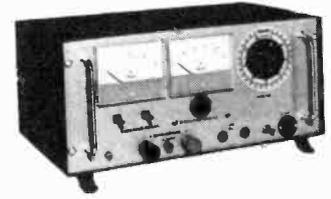

Type VRU/30/25—£166.75 + 8% VAT

Input 200–250V. 50Hz
or 100–120V. 60Hz to order
Output 1: 0–30V. 25A. D.C.
Output 2: 0–70V. 10A. A.C.
Output 3: 0–250V. 4A. A.C.

Other units are also available
with outputs of:
0–60V 12A.
0–120V 6A.
0–240V 3A.


ALL CONTINUOUSLY
VARIABLE

SEND FOR FURTHER DETAILS
OF THESE VERSATILE UNITS TO

Valradio LIMITED, BROWELLS LANE,
FELTHAM, TW13 7EN, MIDDLESEX.
TELEPHONE 01-890 4242

WW-110 FOR FURTHER DETAILS

nombrex

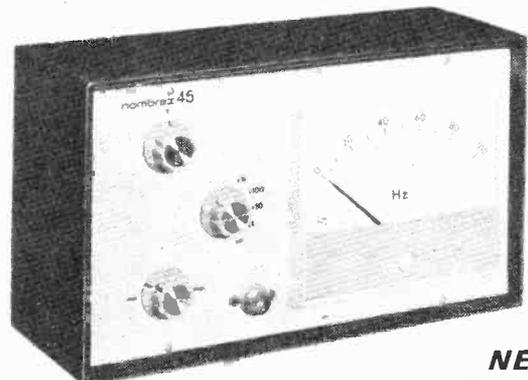

NEW
MODEL 45
DIRECT READING FREQUENCY METER
PRICE **£42.50** + VAT


- MEASURES FREQUENCY FROM 10 Hz TO 100 kHz.
- MEASUREMENT INDEPENDENT OF SIGNAL WAVE FORM.
- ACCEPTS INPUT LEVELS FROM 10mV TO 5V.
- FOUR DECADE SWITCH RANGES.
- SENSITIVITY CONTROL.
- CALIBRATION CONTROL.
- POWERED BY 9 VOLT BATTERY.

*Trade and Export enquiries welcome.
Send for full technical leaflets.
Post and Packing 50p extra.*

NOMBREX (1969) LTD., EXMOUTH, DEVON
Tel: 03-952 3515

WW-065 FOR FURTHER DETAILS

A WORLD FIRST* FROM CAMBRIDGE AUDIO

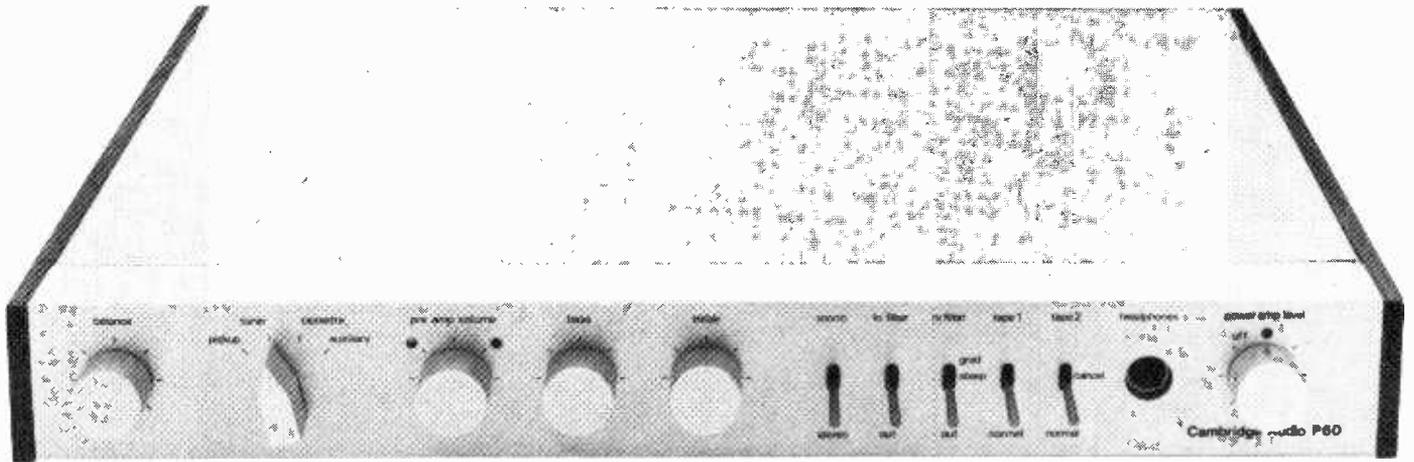

THE NEW P60 INTEGRATED STEREO AMPLIFIER

Low profile design only 2" high.
Recording with or without tone
correction.

*Peak level indicator for tape recording.
Suitable for continual high power
operation.

Dual independent tape operation.

*Light Emitting Diodes for level monitoring
in main and pre-amplifiers.
Toroidal mains transformer.

Facilities for three tape recorders.

*Separate main and pre-amp gain
controls.

Fully protected output stages.

RIAA phono correction unaffected by
cartridge inductance.

Ultra low distortion circuits.

*New tape monitoring, A-B and A-B-C
facilities.

International state-of-the-art circuitry
from Cambridge Audio in Britain.

*To the best of our knowledge these features have never been included in a comparable amplifier hitherto.



for people who listen to music


Cambridge Audio Limited
The River Mill, St. Ives, Huntingdon PE17 4EP
Telephone: St. Ives 62901

Please send me details of the revolutionary New
Cambridge P60 Integrated Stereo Amplifier.

Name _____
Address _____

WW 25

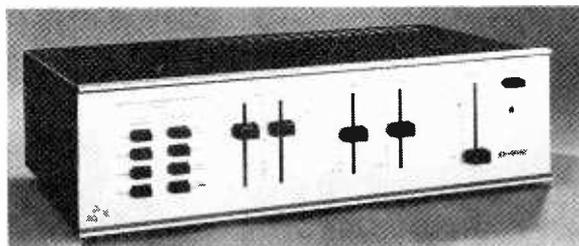A NEW STANDARD FOR SOUND REPRODUCTION HD250 High Definition Stereo Control Amplifier



Designed for disc and tuner input and two tape machines, with complete recording and reproducing facilities.

The HD250 amplifier establishes a new standard in amplifiers for sound reproduction in the home. Improvements have been made in respect of performance, engineering design and quality of construction. We believe that no other amplifier in the world can match the overall specification of the HD250. Look at extracts from the specification below.

Power output.

Rated: 50 watts average continuous power per channel, into any impedance from 4 to 8 ohms, both channels driven.

Maximum: 90 watts average power per channel into 5 ohms load.

Distortion.

Pre-amplifier: Virtually zero. (Cannot be identified or measured as it is below inherent circuit noise.)

Power amplifier:
at rated output: Less than 0.02% (typically 0.01% at 1kHz).
at 25w output: Typically 0.006%.

Overload margin.

Disc input 40 dB min.

Hum and noise output.

Disc: —83dBV Measured flat with noise bandwidth of 23kHz (ref. 5mV.)
—88dBV Measured with 'A' weighted characteristic (ref. 5mV.)

Line: —85dBV Measured flat (ref. 100mV.)
—88dBV 'A' weighted (ref. 100mV.)

Size: 17 inches X 4 3/4 inches X 11 inches deep overall.


Weight: 21 lb.

Write or phone for leaflet which describes the design philosophy and conception of the HD250 together with a complete specification.

RADFORD AUDIO LIMITED, BRISTOL, BS3 2HZ Telephone: 0272 662301

WW—060 FOR FURTHER DETAILS

DIOTESTOR IN-CIRCUIT TRANSISTOR TESTER

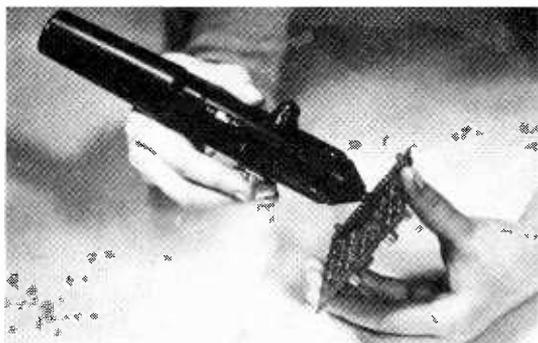

BRITEC LIMITED, 17 Devonshire Road, London SE23 3EN
Tel: 01-699 8844 Telex: 896161

WW—137 FOR FURTHER DETAILS



SPEEDSERVICE

A new service from one of the largest United Kingdom exporters of tubes and semiconductors

AEI · GATWICK HOUSE · HORLEY · SURREY · RH6 9SU
Telex 87116 · Cables Aerocon Telex Horley · Telephone Horley 5353

WW—107 FOR FURTHER DETAILS

JES AUDIO INSTRUMENTATION


Illustrated the Si453 Audio Oscillator

SPECIAL FEATURES:

- ★ very low distortion content—less than 0.03%
- ★ an output conforming to RIAA recording characteristic
- ★ battery operation for no ripple or hum loop
- ★ square wave output of fast rise time

£50.00

also available

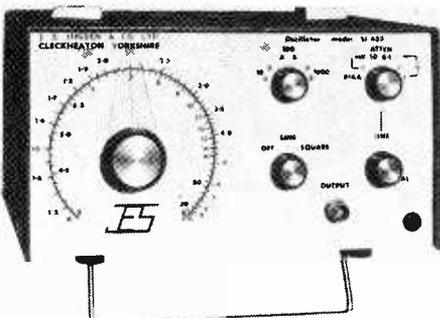

Si451 Millivoltmeter

★ 20 ranges also with variable control permitting easy reading of relative frequency response. **£42.50**

Si452 Distortion Measuring Unit

★ low cost distortion measurement down to 0.01% with comprehensive facilities including L.F. cut switch, etc. **£35.00**

ALL PRICES PLUS VAT


J. E. SUGDEN & CO. LTD., CARR STREET, CLECKHEATON, YORKS. BD19 5LA.

Tel: 09762-2501

WW—031 FOR FURTHER DETAILS

Four easy steps to improve your instructional video system.

1

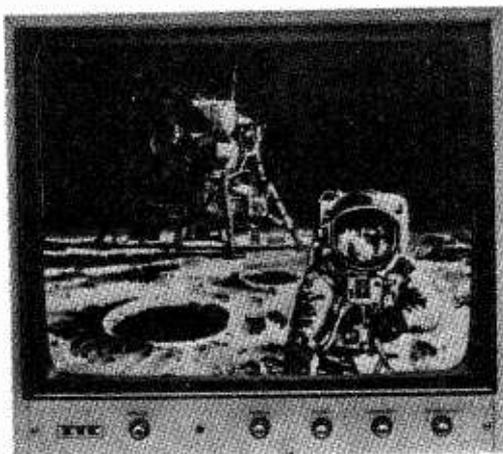

First purchase a good monitor. The ITC PM 171T for example, is perfect. It guarantees clarity, brilliance and definition; even if the picture comes straight from the moon. And our price is strictly earthbound, just £161. With the special video effects we have in mind, you'll need the ITC PM 171T monitor.

2



Next purchase the VTG-33F time and date generator. It gives legible reading from 100th of a second, through seconds, minutes, hour, day, month. Perfect for any countdown. The precise timing is provided by the electronic crystal control IC circuitry. This generator is compatible with any new or existing television system, colour or black and white. And costs just £322.

(Prices subject to VAT)

3



Now add the VP 315 video pointer. This advanced unit superimposes an arrow indication on your video system picture. The joy-stick control panel makes arrow positioning simple. And the arrow can be shown in black or white in a steady or flashing model either horizontal or vertical, in any size you want. We bring it to you at only £327.75.

4

Lastly, step into Dixons Technical. That's where you can buy all the above hardware. While you're in, look over all the other space-age equipment we have for improving your video system. We'll give you a personal demonstration, help you choose the equipment you need, then install it.

Please send full details for the

- ITC PM 171T Monitor
- The VTG-33F Video Display Generator
- The VP 315 Video Pointer

Name _____

Address _____

To: Dixons Technical,
3 Soho Square,
London W1.
Tel: 01-437 8811

Dixons
Technical Ltd
OF SOHO SQUARE

WW/35/2


*Also available showing seconds, minutes, hour, day, month, year. This model is very suitable for time lapse video recording.

THINK SCOPEX

... and life can become complicated. But think Scopex and you find practical, professional, dual-channel portables as easy-to-use as to carry. Sensible bandwidth, no-nonsense controls, trig level and polarity from one knob, and the ever-popular time-saving trace-locate feature. As an example, the Scopex 4D10 gives 10MHz over the full screen area, 5% accuracy, and all for £118*. It makes sense to ...

* Ex. VAT.

THINK SCOPEX

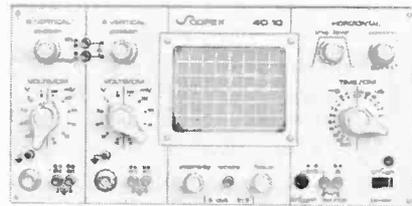

SCOPEX

Scopex Instruments Ltd,
Pixmore Industrial Estate,
Pixmore Avenue, Letchworth, Herts. SG6 1JJ
Tel: Letchworth (04626) 72771

Write or 'phone for details

WW—149 FOR FURTHER DETAILS

Measure airflow accurately for only £67.00

The AVM500 gives accurate and immediate metering of airflow. The standard scale is between 0 and 30 metres/second (70mph). Other calibrations can be supplied at cost.

Airflow is measured by a constant temperature bridge, supported on a lightweight probe, which is connected by cable to the meter. Operation is by battery. The AVM500 is therefore extremely quick and easy to move and instal. A recording instrument is available.

Please send details of your AVM500. I am interested in wind measurement for

Name Position

Company

Address



Prosser Scientific Instruments Ltd
Lady Lane Estate Hadleigh Suffolk
Tel Hadleigh (047-338) 3005

WW1

INSIST ON VERSATOWER



Acclaimed as the World's leading telescopic tiltover tower in the field of radio communication Models from 25' to 120'



Look for the name **STRUMECH**

Strumech Engineering Co Ltd
Coppice Side, Brownhills, Walsall, Staffs

WW—027 FOR FURTHER DETAILS


MEASURE FREQUENCY ANYWHERE WITH MULTIMETER SIZE INSTRUMENT POWERED BY FOUR PENCCELLS

Latest technology miniature device uses four 0.3" LED digits to display frequency. 5 ranges with coupled decimal point give resolution of 0.1Hz to 1kHz in decade steps.

TAKES UP ALMOST NO BENCH SPACE.

LOW PRICE. £79.50 inc p&p ex vat.

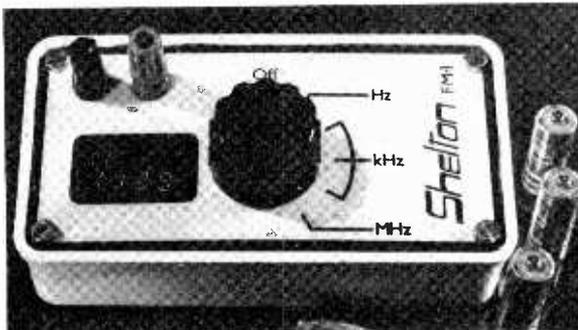Mains PSU available which fits inside ready drilled case.



* Also: FX-1 FREQUENCY MULTIPLIER (X 60, X 100) —see December W.W. £29.50 *

MINIATURE BATTERY FREQUENCY METER FM-1

FOUR-DIGIT MEMORY DISPLAY FIVE RANGES 4 ppm CRYSTAL

SIZE 6½ x 3½ x 2½ in —including knob and terminals

Shelton

INSTRUMENTS LTD., 24 Copenhagen Street, LONDON N1 Tel: 01-278 6273

WW—114 FOR FURTHER DETAILS

Icon Design

Electronic Design Specialists

NOW you can build our LUXURY F.M. STEREO TUNER Complete

As announced in advance last month, we can now offer a complete kit to build this superb design. The cabinet and chassis kit now available are up to the same high original design standards as the circuit design, and the same high quality of materials has been used. The metal work is in rustproof cadmium plated steel sheet, fully drilled and prepared. The front panel is in two tone gold and brown brushed anodised finish, while the drop over cabinet is made from high grade solid wood, finished in a light satin gloss varnish. The net result is a tuner of the very highest standards of performance and appearance.

(see W.W. APRIL/MAY 1974)

Kits now available	Price	Postage
K1-4 All parts to build the main receiver board	£24.95	30p
K5-7 Complete stereo decoder with anti-birdy filters	£9.95	30p
K8 A 4 way push button assembly for the function switching	£3.45	10p
K9 A 6 way pre-select push button unit, gold plated contacts, cermet trim-pots, P.C. Board with meter drive circuitry	£14.14	10p
K10 A regulated power supply including mains transformer (210-250v)	£5.82	30p
K11 Complete cabinet/metalwork set as described, including all plugs and sockets, mains lead, nuts and bolts, wire, etc.	£25.00	50p
Meter An edgewise meter with frequency calibration to suit K9	£6.50	20p
K1-11 All above parts, package price	£85.00	50p

PLEASE ADD V.A.T. TO TOTAL

Other individual parts available include the SL301B, SL3045, SBA750, MC1310P, Filter SFG10.7MA, etc. Also individual K1-7 prices available, other parts may be quoted on request. All parts and performance are guaranteed. Send a S.A.E. (9 x 4 preferred) for further details to:—


Icon Design

33, Restrop View,
Purton, WILTS
SN5 9DG




THE ULTIMATE IN TONE CONTROL

Teknik 27s Graphic Equaliser

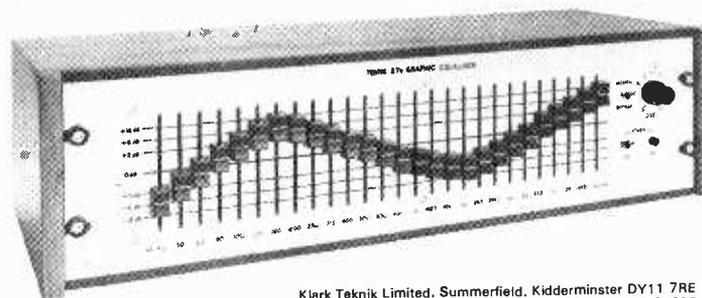

Clark Teknik Limited, Summerfield, Kidderminster DY11 7RE
Telephone: Kidderminster 64027

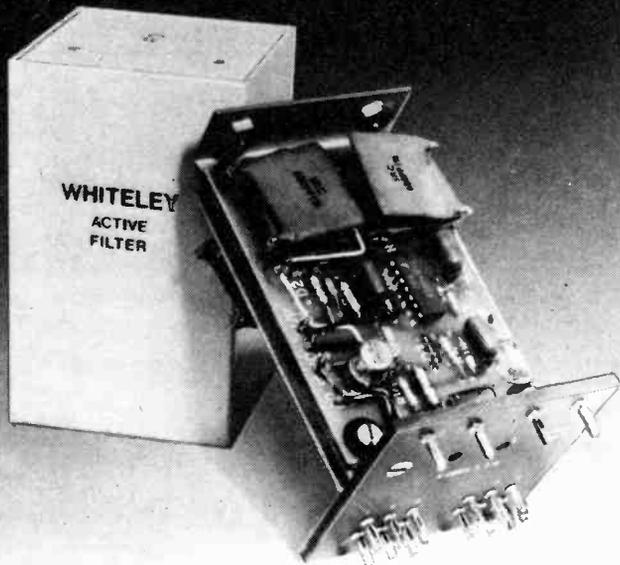New active filter takes over from passive networks



These active filters are designed to take over the functions of passive filter networks in audio telecommunications systems. They offer several advantages, in space-saving, economy and reliability.

As a size comparison, one active filter will take up the same space as two Post Office Type 3000 relays. By using the same fixing and terminal holes as the relays, it offers an extra convenience when baseboards are being prepared. By replacing inductive components with solid state devices, filter characteristics have been obtained at less cost, without insertion loss, and with increased flexibility and economy. These new active filters have B.P.O. approval, and have wide applications, in the audio area and in signalling and control systems.

Whiteley versatility...

ELECTRONIC & ELECTRICAL DESIGN

PRODUCTION CAPABILITY

CABINET MAKING

SHEET METAL FORMING/FINISHING

PLASTICS MOULDING


ENCAPSULATION

WHITELEY ELECTRICAL RADIO CO. LTD.
Mansfield, Notts, England. Tel. Mansfield 24762
London Office: 109 Kingsway, W.C.2. Tel. 01-405 3074

WW-042 FOR FURTHER DETAILS

Linstead Twin Stabilised Power Supplies

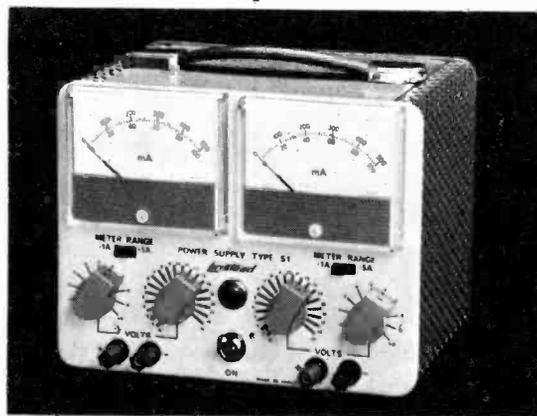Each comprising:
Two powerful bench supplies.
Continuously variable.
Independently operable, or in series, or parallel.
Fully protected against overload and short circuit.
In one compact robust case.



S1 2 x 0 to 20V 0 to 0.5A
with twenty 1 volt steps and fine control.
Voltage set by controls.
Current continuously monitored, 0 to 100mA, 0 to 0.5A.
Current limiting protection.

£78.80
plus VAT



S7 2 x 0 to 30V 0 to 1A.
Set by switches and fine control.
Meters switchable for volts.
0 to 100mA and 0 to 1A.
Re-entrant protection. Pilot indication of overload.

£87.70
plus VAT

Linstead

the best for less

BRITISH MADE BY Linstead

Linstead Electronics, Roslyn Works, Roslyn Road
London N15 5JB. Telephone 01-802 5144

Ireland, Lennox Laboratory Supplies Ltd., 3-4 South Leinster Street
P.O. Box 212A, Dublin 2
Denmark, Scanfysik, 13-15 Hjørtinggade, DK 2100, Copenhagen
Sweden, EMI Svenska A/B, Tritonvägen 17, Fack, 171 19 Solna 1
Norway, EMI Norak A/S, Postboks 42 Korsvoll, Oslo 8
Malaysia, Laboratory Equipment Sdn. Bhd., P.O. Box 60, Batu Pahat
Benelux, A.S.E. Ltd., Nationalestraat 38, B-2000 Antwerp

WW-057 FOR FURTHER DETAILS

100% MODULAR



SOLID STATE TELEVISION MONITORS


MODTEC solid state Series M monitors offer the most advanced design in video monochrome monitors available to date. 800 line resolution provides crisp, detailed pictures. The 100% modular chassis consists of five individually shielded circuit modules that plug in directly from the rear of the chassis. This unique and exclusive feature simplifies and speeds necessary maintenance with minimum down time. All plug-in circuit modules are common to 9, 12, 15, 19, and 23" CRT's.

LEE ENGINEERING LIMITED

Ashley House, Ashley Road
Walton-On-Thames, Surrey KT12-1JE
Phone: Walton-On-Thames 287-83/4
Telex: 928-475

WW-135 FOR FURTHER DETAILS

ELECTRONIC INDUSTRIAL THERMOMETER

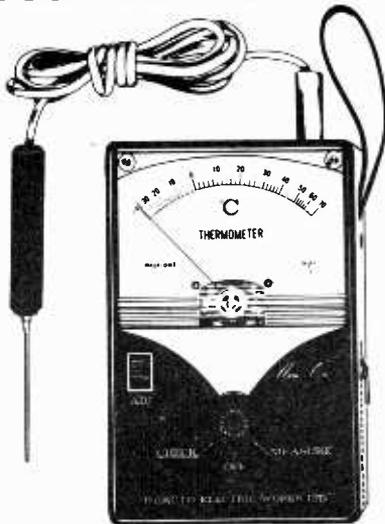


THE MODERN WAY TO MEASURE TEMPERATURE

A Thermometer designed to operate as an Electronic Test Meter. Will measure temperature of Air, Metals, Liquids, Machinery, etc., etc. Just plug-in the Probe, and read the temperature on the large open scale meter. Supplied in zippered vinyl case with transparent front and carrying loop, Probe, and internal 1½ volt standard size battery.
Model "Mini-On 1" measures from - 40°C to + 70°C, price £17.50
Model "Mini-On Hi" measures from + 100°C to + 500°C, price £20.00 (V.A.T. EXTRA)

Write for further details to

HARRIS ELECTRONICS (LONDON),
138 GRAY'S INN ROAD, LONDON WC1X 8AX
(Phone 01-837 7937)

WW-094 FOR FURTHER DETAILS

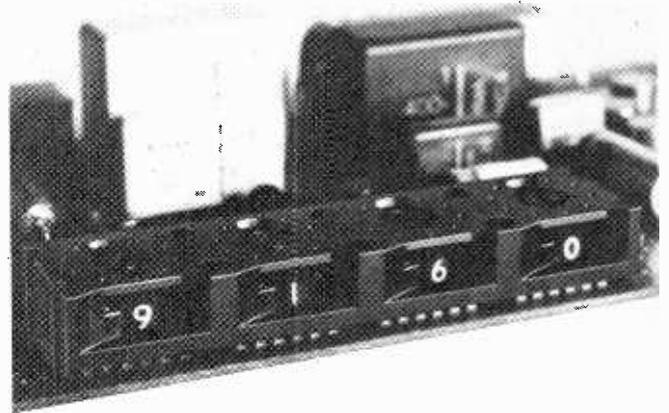

NOW! a thumb switch for direct PC mounting

EECo STRIPSWITCH

The Series 21 Stripswitch which is available in units comprising up to six stations is mounted directly to the printed circuit board. The switch solder tabs are used to provide the mechanical mounting to the circuit board and also the interconnection between the switch and the printed circuit.

Series 21 switch assemblies may be mounted horizontally or vertically and on either side of a P.C. board. The bezels offer a finished appearance if the switches are exposed through the equipment panel. Toothed wheels provide for a rapid setting of the switch positions but the Series 21 may also be used as a preset screwdriver operated switch. Knurled shafts which are available on request provide an alternative means of a rapid setting.

WAYCOM LIMITED

Wokingham Road, Bracknell, Berks RG12 1ND
Tel: Bracknell 22751 Telex: 848402

WW-140 FOR FURTHER DETAILS

P.C. BORED?

— not with the


DECON- DALO 33PC



A unique drafting aid for the electronics engineer enabling him to prepare in minutes a perfect PCB.

A fine-tipped marker charged with a free-flowing etch-resist ink. Simply draw the desired circuit onto copper laminated board—etch—clean.

The circuit is ready to use.

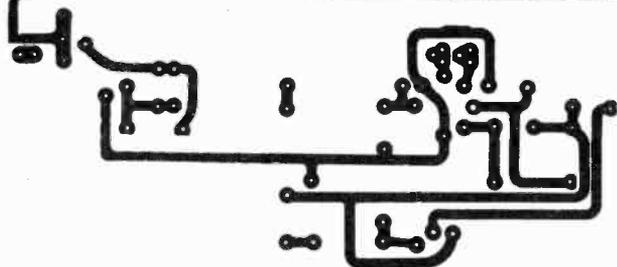

NO MESS — NO MASKING
A perfect circuit every time!

£1.00 for one-off, £4.00 for six, £8.00 for twelve plus VAT post included. Available now in every country in Europe.

Please send me further details on the 33PC:

Name _____

Address _____

Post to: **DECON LABORATORIES LTD.**
FREEPOST
PORTSLADE, BRIGHTON, ENGLAND
(No Stamp Needed) Phone 0273 414371

WW12



Make contact with Teonex

for electronic valves (a really comprehensive range), semi-conductors (a wide variety), integrated circuits. Prices on request.

Teonex offers more than 3,000 devices. They are competitively priced and they are superlative in performance, because the company imposes strict quality control. Teonex concentrates entirely on export and now operates in more than sixty countries, on Government or private contract. All popular types in Electronic valves, semi-conductors and integrated circuits available only for export.

the Teonex range are nearly always available for immediate delivery. Write now for technical specifications and prices to Teonex Limited, 2a Westbourne Grove Mews, London W11 2RY, England. Cables: Tosupply London W11. Telex: 262256



sounds international

WW—050 FOR FURTHER DETAILS

REVERSIBLE ASSEMBLY FRAME FOR PRINTED CIRCUITS

Simply assemble, turn over and solder



- ★ Takes one or more circuit boards
- ★ Fully adjustable foam cover
- ★ Also ideal for repairs and retouching

This apparatus allows fast, neat assembly of single circuit boards, or several smaller boards at a time.

You just insert the circuit boards between the holding bars, assemble components, clamp down the foam cover, invert the frame, then cut and solder connections.

Our special magnetic locking system ensures that components stay firmly in place.

Indispensable for any circuitry laboratory, repair shop, or production line use. Available in two sizes:

Max. area JA 500 — 220 x 170 mm.
area JA 1000 — 370 x 170 mm.


For full details, please contact:
Special Products Distributors Ltd.,
81 Piccadilly, London W1V 0HL.
Telephone: 01-629 9556.

WW—048 FOR FURTHER DETAILS

MAPLIN ELECTRONIC SUPPLIES

Get your 1975
CATALOGUE!

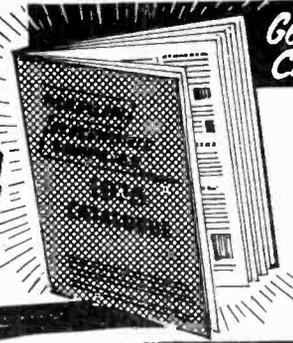Includes dozens of useful and interesting circuits you can build; data; hundreds of pictures, transistor equivalents list and hundreds of new lines. Packed with information. Only 35p



SUPERSONIC SAME-DAY-SERVICE-MEANS QUALITY COMPONENTS-FAST!

RESISTORS

CARBON FILM
1/4W 10 to 1M : 5% IM2 to 10M : 10% E12
1/2W 10 to 100 : 5% IM2 to 10M : 10% E12
110 to 910k : 5% E12 & E24 1p each.

METAL OXIDE
1/4W 100 to 1M : 2% E12 & E24 4p each

WIREWOUND
3W 0.22Ω, 0.27Ω, 0.33Ω, 0.47Ω : 10%
10:5% 17p each
1.2Ω to 270Ω : 5% E12 13p each

Other ranges stocked. See our catalogue for details.
E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades.
E24: 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades.

POTENTIOMETERS

Rotary miniature carbon track 1/2 spindle. Values available: 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M.

Log. single-gang 16p. Lin. single-gang 1+1k 16p
Log. or Lin. single-gang with switch 33p
Log. or Lin. dual-gang without switch 49p
Slider 60mm track. Metal-cased: overall length 86.15mm less knob (7p extra).

Log. or Lin. single-gang 1k, 5k, 10k, 25k, 50k, 100k, 36p each.
Log. or Lin. dual-gang 1k, 5k, 10k, 25k, 50k, 100k, 45p each.

Presets: 0.1W vertical or horizontal.
100Ω, 220Ω, 470Ω, 1k, 2k2, 4k7, 10k, 22k, 47k, 100k, 220k, 470k. 1M 7p each.



CAPACITORS

Sub-miniature Axial lead electrolytic

Mfd V	Price	Mfd V	Price
1.63 6p	68	6.3 6p	6p
1.5 63 6p	68	16 6p	40p
2.2 63 6p	68	63 14p	14p
3.3 63 6p	100	4 6p	Mfd V Price
4.7 63 6p	100	10 6p	470 6.3 6p
6.8 40 6p	100	25 6p	470 10 14p
6.8 63 6p	100	40 6p	470 25 16p
10 25 6p	100	63 16p	470 40 25p
10 63 6p	150	6.3 6p	680 6.3 14p
15 18 6p	150	16 6p	680 16 16p
15 40 6p	150	25 6p	680 25 25p
15 63 6p	150	40 14p	680 40 28p
22 10 6p	150	63 16p	1500 4 14p
22 25 6p	220	4 6p	1000 10 16p
22 63 6p	220	10 6p	1000 16 25p
33 6.3 6p	220	18 6p	1000 25 28p
33 16 6p	220	25 14p	1500 6.3 16p
33 40 6p	220	40 16p	1500 10 25p
47 4 6p	220	63 25p	1500 18 28p
47 10 6p	330	4 6p	2200 6.3 25p
47 25 6p	330	10 6p	2200 10 28p
47 40 6p	330	16 14p	3300 6.3 28p
47 63 6p	330	63 28p	4700 4 28p

SWITCHES

Rotary adjustable stop, 1 pole, 2 to 12 way; 2 pole, 2 to 6 way; 3 pole, 2 to 4 way; 4 pole, 2 or 3 way 36p each.

Slide Sub-min. DPDT 13p
Slide min. DPDT 13p
Push to make non-locking SPST 14p
Push on, push-off locking DPDT 250V 4A 48p
Rocker white DPST 250V 10A 40p
Rotary mains DPST 250V 2A 20p
Toggle with ON/OFF plate DPDT 250V 1.5A 25p

BCD OUTPUT SLIDE SWITCH
Marks the end of the old-fashioned thumb-wheel switch. With 7-segment type read-out. Full details in our catalogue £1.38



TRANSISTORS & DIODES

AC127	18p	BFY52	20p
AC12B	18p	BY126	13p
AC176	17p	BY127	13p
AD161/162MP	93p	BY164	49p
BA100	9p	BZY88	
BA145	22p	series	13p
BC107	12p	MPF102	36p
BC108	10p	OA91	6p
BC109	13p	OA200	7p
BC109C	15p	OC71	20p
BC142	23p	SC146D	88p
BC143	26p	T1S43	28p
BC147	10p	W005	30p
BC148	10p	W04	33p
BC149	12p	1N914	4p
BC168C	12p	1N4001	6p
BC169C	12p	1N4002	6 1/2p
BC178	17p	1N4003	7p
BC182L	10p	1N4004	7 1/2p
BC183L	12p	1N4005	8p
BC184L	12p	1N4006	8 1/2p
BC212L	14p	1N4007	9p
BC213L	15p	1N4148	4p
BC214L	18p	2N1302	20p
BCY71	22p	2N1303	20p
BD131	45p	2N1304	30p
BD132	54p	2N1711	24p
BD137		2N2219	25p
BD132MP		2N2646	45p
		2N2905	33p
	£1.20	2N2926 Or.	
BD135	36p	Ye. or Gn	11p
BD139	49p	2N3053	18p
BD140	69p	2N3055	49p
BF258	35p	2N3819	22p
BF259	25p	2N5459	51p
BFX29	30p	7400	16p
BFX30	33p	7413	39p
BFX84	30p	7447	£1.10
BFX85	36p	7473	54p
BFX87	30p	7474	45p
BFX88	25p	7490	93p
BFY50	20p	7493	93p
BFY51	22p	74121	39p

L.E.D. RED. 15p
2mcd 1/2" only
Panel mtg. clip 5p
(Other colours and 7-seg. displays in our catalogue.)

INTEGRATED CIRCUITS

CA3046 (14-pin DIL)	69p
LH0042CH (TO99)	£4.25
MC1310P (14-pin DIL)	£2.50
MC1496 (UA796) (14-pin DIL)	95p
MFC4000B	59p
MFC6040	83p
NE555V (8-pin DIL)	65p
SG1495 (14-pin DIL)	£2.70
SG3402 (14-pin DIL)	£1.69
µA741C (8-pin DIL)	36p
(14-pin DIL)	45p
µA747C (14-pin DIL)	£1.05
µA748C (8-pin DIL)	39p
ZNA14 (TO18)	£1.20

VOLTAGE REGULATORS

µA7805 5V 1.5A (TO3)	£2.30
µA7815 15V 1.5A (TO3)	£2.30
MVR 5V, 15V, 500mA (TO3)	£1.60
µA78M05 5V 100mA (Plastic power)	£1.30
µA78M05 15V 500mA (plastic power)	£1.30
µA78L05 5V 100mA (TO92)	60p
µA78L15 15V 500mA (TO92)	60p
µA723C variable 2 to 37V (TO99) or 14-pin DIL	75p

Our catalogue contains application circuits and data for all the above I.C.s and many more.

DISCOUNTS

Details in our catalogue. Start collecting MES Discount Vouchers NOW!

PLUGS AND SOCKETS

DIN	PLUG	CHASSIS SOCKET
2-pin	8p	6p
3-pin	9p	7p
4-pin	10p	7p
5-pin A(180°)	10p	7p
5-pin B(240°)	10p	7p
6-pin	10p	9p



JACK PLUGS

2.5mm plastic barrel	9p
2.5mm metal barrel	15p
3.5mm plastic barrel	9p
3.5mm metal barrel	15p
1/2 in. std. mono plastic barrel	13p
1/2 in. std. mono metal barrel	24p
1/2 in. std. stereo plastic barrel	18p
1/2 in. std. stereo metal barrel	30p



JACK CHASSIS SOCKETS

2.5mm open-type metal	9p
3.5mm open-type metal	9p
1/2 in. std. mono open-type metal	10p
1/2 in. std. mono moulded with 2 break contacts	14p
1/2 in. std. stereo open-type metal	15p
1/2 in. std. stereo moulded with 3 break contacts	18p



PHONO

Plastic-topped plug	5p
Screened plug	12p
Chassis socket single	4p
Chassis socket twin	6p



MAINS CONNECTORS

P360 3-pin 1.5A chassis plug with line socket	30p
SA2190 3-pin 5A chassis plug	22p
SA1862 Line socket for SA2190	25p
P437 3-pin 5A chassis socket with line plug	55p



TRANSFORMERS

LT700 min. output. Pri. 1k2: Sec. 5Ω 200mW	50p
Sub-min mains 6-0-6V 100mA 12-0-12V 50mA	95p
(Size both approx. 30x27x25mm)	
Min. mains 0-6V 500mA, 0-6V 500mA	£1.36
0-12V 250mA, 0-12V 250mA	£1.36
0-20V 150mA, 0-20V 150mA	£1.36
0-24V 125mA, 0-24V 125mA	£1.36
Mains MT3AT: Sec: 12-15-20-24-30V 2A	£3.60
Mains MT206AT: Sec: 0-15-20V 1A, 0-15-20V 1A	£3.98



ORGAN CONSTRUCTION

A Full-Scale Electronic Organ that you can build to your own specification.

FULL CONSTRUCTIONAL DETAILS IN OUR LEAFLETS

Leaflet MES 51: price 15p. describes a fully polyphonic basic organ which can later be used as the basis of a large sophisticated instrument. Leaflet MES 52: price 5p. continues the description of the MES 50 series organs and shows you how to add a second keyboard with lots more stops. Further leaflets to follow at approx. two-monthly intervals.



THE AMAZING DM02

A ready-built, tested and guaranteed digital master oscillator. Accurately generates the top 13 notes for your organ system and reduces the complete tuning of your organ to ONE SIMPLE adjustment. New design gives selectable C to C output ranges of (approx.) 4k to 8k (highest) or 2k to 4k or 1k to 2k. etc., right down to 16Hz to 32Hz! And this new compatible design is even smaller: only 3.5in. X 3.7in. including gold-plated edge connexion. DM02T includes built-in variable depth and rate frequency shift tremulant. DM02 £12.25 DM02T £14.25 SAJ 110: 7-stage frequency divider in 14-pin DIL package. Sine or square wave input. Square wave output may be converted to saw-tooth. £2.63 each or 6 for £14.14 or 12 for £25.

ORGAN COMPONENTS

Keyboards high quality, fully sprung.	
Flat-front 48-note F to E	£15.95
Sloping-front 49-note C to C	£15.95
Sloping-front 61-note C to C	£20.44
Swivel pedal with 10k log. pot	£5.93
*Spring line unit (short)	£3.05
*Spring line unit (long)	£7.59
*Reverberation driver module	£5.34
*S.a.e. please, for full details: leaflet MES 24.	
Gold-clad phosphor-bronze wire	30p per yd.
Palladium earth bar	15p per octave length
Contact blocks 2-make (GB2)	22p
Stop tabs, rocker type, not engraved (white, red, grey or black) with DPDT switch	49p

"ELECTRONIC TODAY INTERNATIONAL" 4600 SYNTHESISER

We stock all parts for this brilliantly designed synthesiser. This includes all the PCBs, metal-works and drilled and printed front panel giving a truly professional finish. Authoritative opinions agree the ETI International Synthesiser is technically superior to most of today's models. Complete constructional details in our booklet, available shortly. S.a.e. please, for price lists and specification. We also stock all parts for the P.E. Synthesiser and Minisonic.




P.O. Box 3, Rayleigh, Essex. Tel: Southend-on-Sea (0702) 44101.
VAT. Please add 8% to the final total. Post and packing FREE in U.K. (15p handling charge on orders under £1)
First-class post pre-paid envelope supplied free with every order.

Purpose-built servo and actuator systems using standard components

McLennan Engineering Ltd. have considerable experience in the solution of actuator and servo problems using synchronous, stepping and DC motor techniques, an important facet of our skill lying in purpose-designing around standard components for speed and economy.

The illustrations show a selection of modules from the standard range and include the new EM/ 100/100A servo drive system. All items are available individually or can be supplied engineered to custom-built systems.

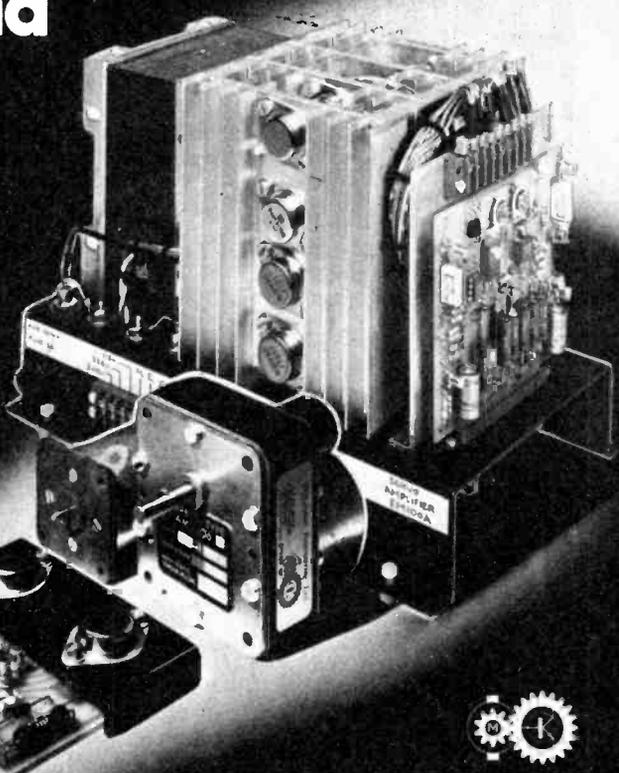1. EM 100/100A SERVO AMPLIFIER. A new addition to the range. A complete servo drive system including power supply which is eminently suitable for driving printed circuit motors and other servo motors up to 1/6 h.p. EM 100 - output $\pm 24V$, 4 amps continuous, 45 amps peak. EM 100A - output $\pm 24V$, 7 amps continuous, 75 amps peak.
2. DC SERVO AM 1006S. With integral potentiometer. Max continuous output Torque 14.6 kgcm at 7 r.p.m.
3. LOW INERTIA DC SERVO MOTOR Output 5W
4. CONTROL AMPLIFIER EM 40 Output $\pm 15V$ 0.5 amp
5. TYPICAL PRECISION GEARS 120 to 32 DP



McLennan
 McLennan Engineering Ltd
 Kings Road, Crowthorne, Berkshire.
 Tel: Crowthorne 5757/8

WW-106 FOR FURTHER DETAILS

TTL 74 SERIES INTEGRATED CIRCUITS				LINEAR ICs				SIGNAL DIODES		RECTIFIER DIODES		ZENER DIODES		SPECIAL OFFERS FOR POPULAR TRANSISTORS		
7400	14p	7432	37p	7486	41p	CA3046	55p	BA100	10p	BY100	15p	3.3V to 33V	100+	500+	AC 126	9p
7401	16p	7437	37p	7489	34p	LM301	40p	BAX13	5p	BY126	12p	400mW	9p	8p	AC 127	9p
7402	16p	7440	20p	7490	52p	LM307	50p	BAX16	6p	BY127	12p	1.3W	18p	8p	AC 128	9p
7403	22p	7441	75p	7492	65p	MFC6040	90p	OA47	7p	BY133	15p	1.5W	25p	8p	AC 128/AC 176 m.p.	18p
7404	18p	7442	70p	7493	55p	NE562	16p	OA70	9p	BYZ10	36p	10W	40p	8p	AC 176	9p
7405	25p	7445	216p	74100	200p	NE567	132p	OA79	10p	BYZ11	35p	20W	85p	8p	AC 187	10p
7406	42p	7447	95p	74107	45p	NE555	55p	OA81	8p	BYZ12	33p			8p	AC 188	9p
7407	42p	7448	120p	74121	34p	NE562	120p	OA85	10p	BYZ13	33p			8p	AF 114	11p
7408	20p	7450	34p	74122	75p	NE566	290p	OA90	7p	IN4001	5p			8p	AF 115	11p
7409	25p	7451	20p	74141	35p	NE560	290p	OA91	7p	IN4004	6p			8p	AF 117	11p
7410	15p	7460	20p	74142	200p	NE562	290p	OA95	7p	IN4007	7p			8p	BC 109C	9p
7412	30p	7470	30p	74145	150p	NE566	290p	OA200	8p	PL4004	10p			8p	BC 147B	6p
7413	28p	7472	30p	74160	180p	NE565	200p	OA202	10p	PL7004	20p			8p	BC 148B	6p
7414	90p	7473	36p	74161	180p	NE567	250p	1N914	4p					8p	BC 149C	7p
7416	36p	7474	34p	74184	225p	709	25p	1N4148	4p					8p	2N 2926 (TO-106)	6p
7417	36p	7475	34p	74185	225p	710	47p							8p	2N 2926 (TO-106)	6p
7420	16p	7476	37p	74186	220p	741	70p							8p	R B O	7p
7422	25p	7480	85p	74191	220p	747	28p							8p	G Y	6p
7425	37p	7482	87p	74192	220p	748	38p							8p		
7427	37p	7483	120p	74193	220p	74B	38p							8p		
7430	16p	7485	187p			ICL8038	290p							8p		

BRIDGE RECTIFIERS				SCR-THYRISTORS				TRIACS			
50V	100V	400V	600V	50V	100V	400V	600V	3 Amp	85p	95p	120p
250mA	16p	20p	24p	1 Amp	42p	48p	60p	6 Amp	88p	120p	150p
1 Amp	20p	21p	24p	3 Amp	43p	49p	78p	10 Amp	109p	154p	165p
2 Amp	30p	35p	45p	7 Amp	—	80p	84p	16 Amp	145p	180p	200p
4 Amp	47p	49p	60p	16 Amp	—	82p	98p	Other			
6 Amp	55p	60p	78p					0A43D	90p	40486	75p

PHOTO-TRANSISTORS		LED		SEVEN SEGMENT DISPLAYS	
OC70	50p	Red	18p	3015F (Filament)	120p
OC71	85p	Green	35p	MAN-3M (LED)	120p
2N5777	50p	Yellow	40p		

FIXED G/P + V _e VOLTAGE REGULATORS		VARIABLE G/P VOLTAGE REGULATOR	
1A (Plastic)	140p	ML723 2V to 37V	55p
MC7805 5V	140p		
MC7812 12V	140p		
MC7815 15V	140p		
MC7818 18V	140p		
MC7824 24V	140p		

ACCESSORIES		QUANTITY PRICES	
DIL SOCKETS	8 pin 12p, 14 pin 13p, 16 pin 14p	555	48p
Mica Washers + 2 Bushes (TO3 or TO66)	5p	723	48p
		741	25p
		7490	47p
		2N3819	19p

C-MOS LOGIC ICs		QUANTITY PRICES	
CD4001AE Quad 2 i/p NOR Gate	50p	555	48p
CD4009AE Hex Inverter/Buffer	50p	723	48p
CD4011AE Quad 2 i/p NAND Gate	50p	741	25p
CD4012AE Dual 4 i/p NAND Gate	50p	7490	47p
CD4013AE Dual 'D' Flip-Flop	120p	2N3819	19p
CD4017AE Decade Counter/Divider	300p		

SPECIAL OFFERS FOR POPULAR TRANSISTORS	
AC 126	9p
AC 127	9p
AC 128	9p
AC 128/AC 176 m.p.	18p
AC 176	9p
AC 187	10p
AC 188	9p
AF 114	11p
AF 115	11p
AF 117	11p
BC 109C	9p
BC 147B	6p
BC 148B	6p
BC 149C	7p
2N 2926 (TO-106)	6p
R B O	7p
2N 2926 (TO-106)	6p
G Y	6p

TGS GAS SENSOR	
Semiconductor	200p
Data Sheet	10p

C-MOS LOGIC ICs	
CA3048	Four Independent Amplifiers
CA3089	FM IF Amplifier
CA3090	FM Stereo Multiplex Decoder
LM377	2W/Channel Stereo Amp
LM380	2 Watt Amplifier
LM381	Stereo Pre-amplifier
MC1304	FM Stereo Multiplex Decoder
MC1307	FM Stereo Multiplex Decoder
MC1310	Coilless FM Multiplex Decoder
MC1312	Four Channel SQ Decoder
MFC4000	4 Watt Audio Amplifier
TBA800	5 Watt Audio Amplifier
TBA810	7 Watt Audio Amplifier
TBA820	2 Watt Audio Amplifier
ZN414	TRF Radio Receiver

All goods brand new. Money refunded if not satisfied. OEM, trade, colleges, inquiries welcome.

TECHNOMATIC LIMITED
54 SANDHURST ROAD, LONDON NW9. Tel. 01-204 4333



ERA

when reliability and quality count

Suppliers of Television Valves, Picture Tubes, Industrial and Transmitting Tubes to the Electronic Industry.

Available Ex Stock at advantageous prices. Enquiries from Agents and Importers welcome.


EDICRON LIMITED

Redan House, 1 Redan Place, London W2 4SA
Telephone: 01-727 0091/2 Telex: 265531
Cables: Edicron London W2

WW—108 FOR FURTHER DETAILS

TPA SERIES-D

integrated circuit power amplifier

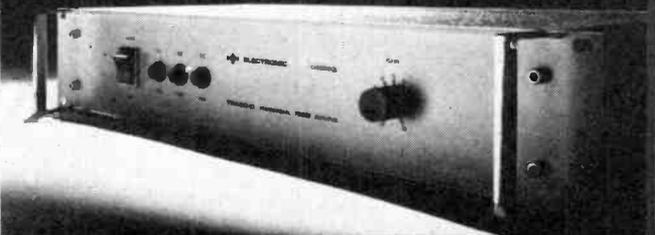

TPA 50 - D Specification

Power Output	100 watts rms into 4 ohms 65 watts rms into 15 ohms
Freq Response	±0.1dB 20Hz to 20KHz into 15 ohms. -1dB at 150KHz
Total harmonic distortion	Less than 0.04% at all levels up to 50 watts rms into 15 ohms
Input sensitivity	0dBm
Noise	-100dB
Rise time	2 u seconds
Price	£59 plus V.A.T.

100V Line (C.T.) and balanced inputs available.

For full technical information contact:

H H ELECTRONIC

CAMBRIDGE ROAD, MILTON, CAMBS
TELEPHONE CAMBRIDGE 65945/6/7

WW—006 FOR FURTHER DETAILS

QUARTZ CRYSTALS - FAST!




AEL

AEL GATWICK HOUSE, HORLEY, SURREY, ENGLAND
Tel: Horley (02934) 5353
Telex: 87116 (Aerocon Horley) · Cables: Aerocon Telex Horley

WW—026 FOR FURTHER DETAILS

STARWET

Spectrum Analyser Module ST858

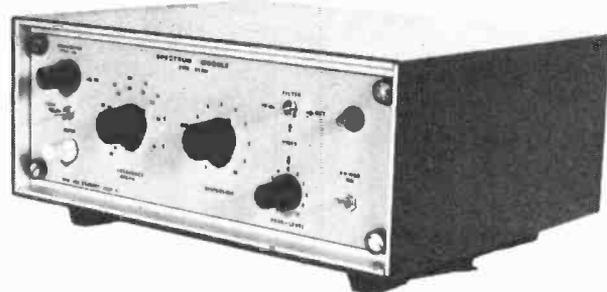

SPECIFICATION: Frequency range 10 MHz to 850 MHz in two calibrated ranges **Sensitivity** Better than 50 mv for 0.5V per cm **Resolution** Better than 25 KHz. **Dispersion** From less than 1 MHz to 400 MHz variable **Input** Via 50 ohm BNC connector on front panel **Output 1** Coax cable for connection to Y input on scope **Output 2** Coax cable for connection to sync. input on scope **Power requirements** 240 volts AC 50 Hz 10 watts. (Other voltages and frequencies available as required) **Size** Width 11in (28cm.) Height 4.375in. (11.2cm.) Depth 8.5in. (21.6cm.) **Nett weight** 7.5lbs (3.4 Kg) **Gross weight** 10lbs (4.5 Kg.)

For further details contact the sole distributors of
STARWET equipment:

CHILTMEAD LTD

7-9 ARTHUR ROAD, READING, BERKS
(rear Tech College) Tel. Reading 582605



sanwa

MULTI TESTERS

USED THROUGHOUT THE WORLD, SANWA'S EXPERIENCE OF 30 YEARS ENSURES ACCURACY, RELIABILITY, VERSATILITY, UNSURPASSED TESTER PERFORMANCE COMES WITH EVERY SANWA

MODEL P28	£9.78	MODEL F80TRD	£25.28
MODEL JPSD	£11.58	MODEL AT45	£21.52
MODEL BX 505	£29.12	MODEL 380CE	£29.12
MODEL 360YTR	£15.28	MODEL N101	£31.81
MODEL U50DX	£15.60	MODEL 460ED	£35.89
MODEL A303TRD	£17.45	MODEL EM800	£81.06
MODEL K30 THD	£24.01	MODEL R1000CB	£75.27

Excellent Repair Service

THESE PRICES ARE SUBJECT TO AN ADDITIONAL CHARGE OF 8% FOR V.A.T. Cases extra, available for most meters, but not sold separately.

MODEL U-50DX

Please write for illustrated leaflet of these and other specialised Sanwa meters

SOLE IMPORTERS IN UK
QUALITY ELECTRONICS LTD.
47-49 HIGH STREET, KINGSTON-UPON-THAMES, SURREY. KT1 1LP
Tel: 01-546 4585

WW—013 FOR FURTHER DETAILS

BYWOOD ELECTRONICS— ONE STOP SHOPPING FOR—

Clock Chips
 Calculator Chips
 Led Displays
 Liquid Crystals
 Phosphor-Diodes
 Gas Discharge
 Display Drivers
 MHI Kits
 Digitronic Clocks
 Customised Units

With Products from —
 Beckman, Brown-Boveri, Cal-Tex,
 Diacon, E.R.G., Fuji, Futaba,
 Imtech, Itoka, Jermyn, Litronix,
 Mostek, National, RCA, Siemens,
 Swarovski, Texas, 3M

Just about all you need to go digital is some of our ICs, some of our digits and drivers, some data and some advice. As they are all available at the end of a telephone line it would make sense to ring 0442-62757 before doing anything else.

Latest lists, prices and products are advertised each month in ETI.

EXTRACTUS DIGITUS, DIALUS and DIGITISE DIRECTLY!

BYWOOD

BYWOOD ELECTRONICS
 181 Ebbens Road
 Hemel Hempstead, Hertfordshire
 Tel: 0442-62757

WW—143 FOR FURTHER DETAILS

TAKE A CLOSE LOOK




at a professional recorder that offers high performance, excellent reliability and is very easy to maintain. Ask yourself why so many commercial radio stations and recording studios are doing their best to wear them out, and not having much success. Decide if you need mono or stereo, console transportable or rack mounting versions and then inquire about prices.

We are sure you will be very pleasantly surprised.

BIAS ELECTRONICS LTD. 01-540 8808
572 KINGSTON ROAD, LONDON SW20 8DR

WW—028 FOR FURTHER DETAILS

How much does Transit Damage cost you?

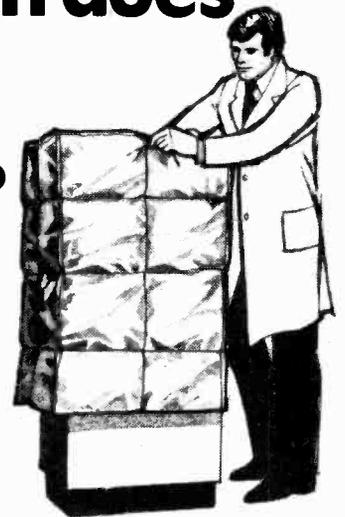

In damaged goods. In doubled delivery charges. It need not cost you a penny. Because it needn't happen. PROTECTOMUFFS are tough, padded, weather-proof, dustproof. They are tailored to fit your product. Slipped on in seconds by unskilled staff, they provide all the packing required. And because

they are re-useable again and again and again, packing costs become a non-recurring item. Be like Hoover, Ferranti, Rediffusion — use Protectomuffs and show your customers you care.

PROTECTOMUFFS

TRADE MARK

To **JOHN EDGINGTON & CO. LTD.**

47 Old Woolwich Road, Greenwich, London SE10 9PU (01-858 7014-6)

Send me details of Protectomuffs

Name


Address

W.W.2




I.L.P. (Electronics) Ltd

SHEER SIMPLICITY!

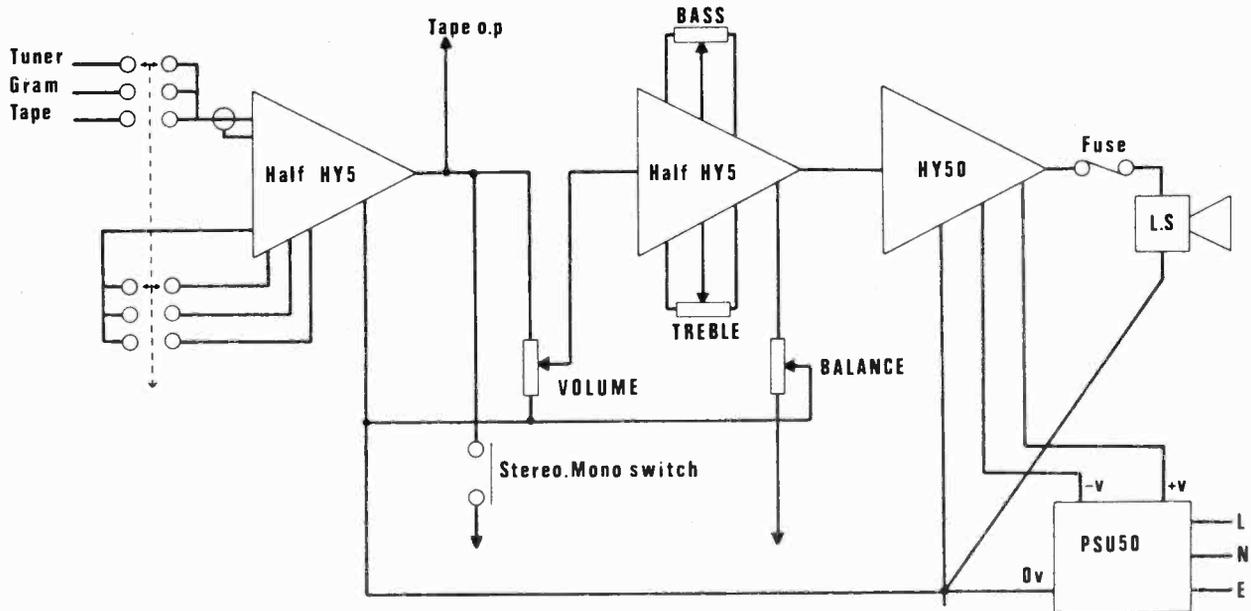

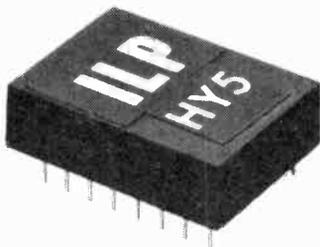Mono electrical circuit diagram with interconnections for stereo shown



The HY5 is a complete mono hybrid preamplifier, ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

TECHNICAL SPECIFICATION


Inputs
 Magnetic Pick-up 3mV, RIAA
 Ceramic Pick-up 30mV
 Microphone 10mV
 Tuner 100mV
 Auxillary 3-100mV
 Input impedance 47kΩ at 1kHz.

Outputs
 Tape 100mV
 Main output Odb (0.775 volts RMS)

Active Tone Controls:
 Treble ±12db at 10kHz
 Bass ±12db at 100Hz

Distortion 0.05% at 1kHz
Signal/Noise Ratio 68db
Overload Capability 40db on most sensitive input
Supply Voltage ±16-25 volts.

PRICE £4.50 + 0.36 V.A.T. P & P free.

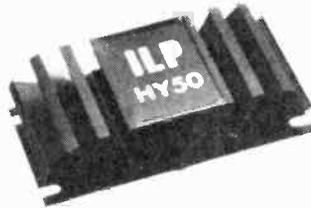


The HY50 is a complete solid state hybrid Hi-Fi amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided: Input, output, power lines and earth.

TECHNICAL SPECIFICATION

Output Power 25 watts RMS into 8Ω
Load Impedance 4-16Ω
Input Sensitivity Odb (0.775 volts RMS)
Input Impedance 47kΩ
Distortion Less than 0.1% at 25 watts typically 0.05%
Signal/Noise Ratio Better than 75db
Frequency Response 10Hz-50kHz ±3db
Supply Voltage ±25 volts
Size 105 x 50 x 25 mm.

PRICE £5.98 + 0.48 V.A.T. P & P free.

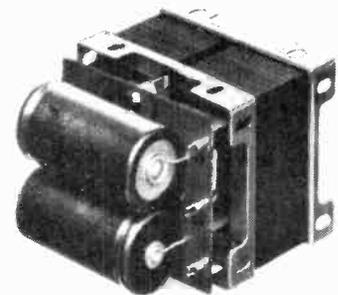

The PSU50 incorporated a specially designed transformer and can be used for either mono or stereo systems.

TECHNICAL SPECIFICATIONS

Output voltage 50 volts (25-0-25)
Input voltage 210-240 volts
Size L.70. D.90. H.60 mm.
 PRICE £6.00 + 0.48 V.A.T. P & P free.

TWO YEARS GUARANTEE ON ALL OUR PRODUCTS

**I.L.P. Electronics Ltd,
 Crossland House,
 Nackington, Canterbury,
 Kent CT4 7AD
 Tel (0227) 63218**

Please Supply _____
 Total Purchase Price _____
 I Enclose Cheque Postal Orders Money Order
 Please debit my Access account Barclay card account
 Account number _____
 Name & Address _____
 Signature _____

ELEKTOR

You told us you enjoyed
Elektor 1

Don't miss Elektor 2, out now

Elektor is a fund of well thought-out and thoroughly tested projects, new ideas using modern electronic components, objective comment on new developments.

Try it



ELEKTOR 2

mos tap
minidrum
dil logic probe
numeric displays
electronic
loudspeaker

Use the Elektor printed circuit board service for immediate delivery of high quality epoxy glass boards for all major projects.

In Elektor 2

- | | |
|----------------------------|----------------------------------|
| † Electronic drum kit | † Modulation systems – AM to CPM |
| † Touch sensitive switches | † 7-segment displays |
| † DIL Logic probe | † High-quality T.V. sound |

Write to us enclosing 35p P.O. or cheque for Elektor 2. If you would like a subscription for the next seven issues (£3.60 till end 1975), send no money, write or phone for subscription card.

Elektor Publishers Ltd.
6, Stour Street, Canterbury CT1 2XZ. Tel Canterbury (0227) 54439



naim audio
MANUFACTURERS OF AUDIO EQUIPMENT

have moved.

You can now find our factory and showroom at...
11 Salt Lane, Salisbury, Wilts, SP11DT
The telephone number remains the same...
SALISBURY 3746

WW—040 FOR FURTHER DETAILS

New LOGIC PROBE 340
Generates a single minus pulse of 0.2 ± 0.05 millisecond.
Built-in pulse generator

- RED & GREEN-LED APPLIED LOGIC LEVEL INDICATOR
- * Wrong polarity & overload protectors provided
- * Detection of the peak value of input waveform
- * Open circuit or faulty IC can be detected
- * All logic levels are visible at a glance
- * Unique high/low level probe

For use in detecting TTL, DTL flip-flop and other pulse circuits

Each **£14.00**
including pp + VAT
Discounts for quantity

JH
ASSOCIATES LIMITED
Bishop's Stortford, Herts. Tel: 0279 56347. Telex: 81657 Jaylamps Stort.

WW—020 FOR FURTHER DETAILS

ANALOGUE & HYBRID COMPUTERS

C60 FEATURES:

Eight low drift, high gain, IC operational amplifiers, 1% accuracy. Automatic function selection and meter switching. A four quadrant variable multiplier. Individual pot-set facilities, built-in stabilised power supplies plus all of the features expected in our precision machines. Price £475 complete with patching leads and instruction book.

We manufacture a wide range of analogue and hybrid computing equipment and can produce special machines built to your own specification. You will be pleasantly surprised at the cost of a computer built to your own requirements.

PHONE OR WRITE FOR DETAILS OF OUR ANALOGUE OR HYBRID APPARATUS

PHYSICAL & ELECTRONIC LABORATORIES LTD.
MANUFACTURERS OF PRECISION ELECTRONIC INSTRUMENTS & COMPUTERS
28 Athenæum Road, Whetstone, London N20. Tel. 01-445 7683

WW—134 FOR FURTHER DETAILS

this is Otari

Otari DP4050

Ideal for 1 cassette copy or 10,000

From Japan's biggest manufacturer of Tape Duplication equipment, the DP4050 reel to cassette copier.

Foolproof operation for non-skilled personnel.

Eight times copy speed.

Automatic cycle through Record-Rewind-Stop.

Absolute consistency in manufacture through large volume production.

Modular construction.

Servo-controlled direct capstan drive.



OTARI

NOTE NEW ADDRESS-

Industrial Tape Applications
5 Pratt Street, London NW1 OAE. Tel: 01-485 6162 Telex: 21879

ITA

WW-101 FOR FURTHER DETAILS

LOGIC LEISURE LTD

**build your
own t.v.
game**

**COMPLETE KIT AVAILABLE
OR P/C BOARD ONLY
STOP PRESS!!
OFFER LASTS ONLY
8 MORE WEEKS**

First time available, the real T.V. game in kit form as supplied to the amusement trade with five bat angles, fully automatic ball, digital score read out on screen and also simulated sound.
Please send stamped addressed envelope for details and prices to:
LOGIC LEISURE LIMITED, Kingfisher House, 68 Park Road, New Barnet, Herts.
Telephone: 01-440 9173/4, Telex: 264397.

THE NEW NELSON-JONES FM TUNER

PUSH-BUTTON VARICAP DIODE TUNING
(6 Position) (WW JUNE '73)



Exclusive Designer Approved Kits

What are the important features to look for in an FM tuner kit? Naturally it must have an attractive appearance when built, but it must also embody the latest and best in circuit design such as:—

- MDSFET** front end for excellent cross modulation performance and low noise.
- 3 GANG** tuning for high selectivity.
- VARICAP** tuning diodes in back to back configuration for low distortion.
- CERAMIC** filters for defined IF response.
- INTEGRATED** circuit IF amplifiers for reliability and excellent limiting/AM rejection.

- PHASE LOCKED** Stereo decoder with Stereo mute, see below
- LED** fine tuning indicators.
- PUSH BUTTON** tuning (with AFC disable) over the FM band (88-104).
- IC STABILISED** and S/C protected power supply.
- CABINET** double veneered against warp.

The Nelson-Jones Tuner has all of these features and many more, and more importantly the design is fully proven not just with a few prototypes but with many thousands of working tuners spread across the world.

Typ. Specn: 20 dB quieting 0.75uV. Image rejection —70dB.I.F. Rejection —85 dB

Basic tuner module prices start as low as **£12.31**, with **complete** kits starting at **£26.95** (mono) + P.P. 65p. and of course all components are available separately.

Our low cost **alignment service** is available to customers without access to a signal generator. Please send large SAE for our latest price lists which details all of the many options and special low prices for complete kits. All our other products remain available.

PORTUS AND HAYWOOD PHASE LOCKED DECODER (W.W. Sept. '70). Still the lowest distortion P.L. decoder available. THD typically 0.05% (at Nelson-Jones Tuner O/P level)! Supplied complete with Red LED.

Price **£7.02** when bought with a **complete** N-J tuner kit or **£8.29** if bought separately (P.P. 21p.)

PLEASE NOTE. Existing tuners are readily convertible and kits/parts are available for this purpose.

TEXAN AMPLIFIER. We have designed the tuner case and metalwork to match the Texan amplifier (see photograph). Complete designer approved Texan kits are available at **£30.78** plus P.P. 65p including Teak Sleeve.



NEW LOW COST STEREO TUNER Available as basic or complete kits

Basic stereo tuner **£15** post free.
Basic mono tuner **£12** post free.
6 position push button units with integral pots **£2.92**.



No alignment required. Mullard LP1186 front end module used with Ceramic IF and IC amplifier. Push button tuning (6 position) with **Interstation Mute**, restricted range **AFC**, single LED tuning indicator, phase locked IC decoder, and complete metalwork and veneered cabinet. Complete with IC regulated PSU and full assembly instructions. (Mechanically identical to N-J Tuner.)

TYP. SPECIFICATION
2µV for 30dB S/N
Image rejection 40dB
IF rejection 65dB


VAT at 8% is included in all prices

PRICE Complete stereo kit **£28.42**
Complete mono kit **£24.19**
P. & P. 65p



INTEGREX LIMITED, P.O. Box 45, Derby, DE1 1TW

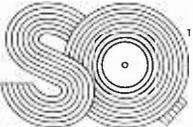Phone **Swadlincote (0283 87) 5432** Telex **377106**



SQ IS A TRADEMARK OF CBS INC.





SQ QUADRAPHONIC DECODERS

SQ the leading quadrasonic system, designed by CBS engineers, offers not only 4 channel ambiphony from the fast expanding range of SQ encoded discs but also immensely increased depth and fullness of sound from standard stereo recordings too.

Feed 2 channels (200-1000mV as obtainable from most pre-amplifiers) into your choice of any of our 3 decoders and take 4 channels out with no overall signal level reduction. On the logic enhanced decoders Volume, Front-Back, LF-RF, LB-RB and Dimension controls can all be implemented by simple single gang potentiometers—no need for exotic 4-gang units!

These state-of-the-art circuits, used under licence from CBS, are offered in kit form comprising first grade components only—fibre glass circuit boards of professional quality designed for edge connector insertion, all resistors 2% metal oxide, all polystyrene and polycarbonate capacitors 5% or better and in decoder L2 ultra low noise (MPS A18-0.5dB typ.) transistors used in each amplifying stage.

M1 Basic matrix decoder with fixed '10-40' blend. 10 Resistors, 14 Capacitors, 1 Integrated Circuit, Printed Circuit Board, **£8-84**.

L1 Full logic controlled decoder with 'wave matching' and 'front-back logic' for enhanced channel separation using three specially designed Integrated Circuits. 24 Resistors, 42 Capacitors, 3 Integrated Circuits, Printed Circuit Board, **£19-80**.

L2 More advanced full logic decoder with 'variable blend', extended frequency response, increased front-back separation. 43 Resistors, 44 Capacitors, 3 Integrated Circuits, 9 Transistors, 6 Diodes, Printed Circuit Board, **£28-20**. All kits include IC sockets and construction notes. Prices include CBS licence fee.

Please write for further details in FREE LIT.

United Kingdom: Post Free. Please add 8% VAT. Overseas: No VAT. Please add (per kit) £1-50 p & p AIR MAIL or 80p p & p SURFACE MAIL.

AMBIENTACOUSTICS

PO BOX 3000
ANDOVER, HANTS SP10 3EQ

WW—079 FOR FURTHER DETAILS

TELEVISION CAMERA KITS

Complete kits are available for both "Mullard" and "P.E." design. Each kit includes a comprehensive construction manual, and a completely FREE technical back-up service to ensure your success. VHF and UHF Modulator Kits also available to allow standard domestic T.V. to be used as monitor.

All parts available separately, including a wide range of lenses, vidicon tubes, special mains transformers and focus/scan coils. Also available P.W. tele-tennis game.

Send 5" x 7" S.A.E. for full details or come along for a demonstration and a chat with our technical staff.

CROFTON ELECTRONICS

124 Coine Road, Twickenham, Middlesex TW2 6QS.
Tel. 01-898 1569. Telex 934642 Cadanac LDN.

WW—105 FOR FURTHER DETAILS

ELECTRONIC ORGAN KITS




There are 5 superb models in kit-form specially designed for the D-I-Y enthusiast. With our free and generous after sales service you can build in sections, and the whole project can be extended over several months. All specialised components can be purchased separately.

We also stock keyboards, volume pedals, MOS master oscillators, ICs, transistors, ETC, for W/W synthesiser and W/W electronic piano. Send 50p for catalogue and vouchers worth 50p or send your own parts list, enclosing SAE for quotation.

ELVINS ELECTRONIC MUSICAL INSTRUMENTS

12 Brett Rd., Hackney, London E8 1JP. Tel: 01-986 8455
8 Putney Bridge Rd., London SW18 1HU. Tel: 01-870 4949
40A-42A Dalston Lane, Dalston Junction, London E8. Tel: 01-249 5624
Business Hours: Open 10 a.m. to 7 p.m. Mon. to Sat. Closed all day Thursday. Open 10 a.m. to 1 p.m. Sunday.

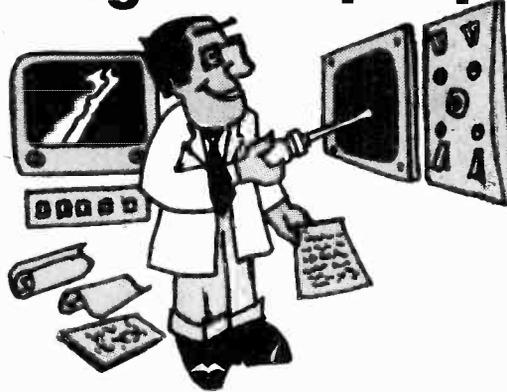We enjoy solving other peoples' problems!



Jasmin take a slightly different approach to their customers and they are proud of the rapport they attain with them. Research and development staff are always available to offer advice on technical issues. This in turn means that Jasmin are able to offer a unique service if you have problems in the following spheres

- Complex automatic text and evaluation apparatus.
- Digitalized video and Ceefax/Oracle display equipment.
- Mini computer orientated systems.
- Specialist contract engineering.


Jasmin ELECTRONICS LIMITED

BOSTON HOUSE, ABBEY PARK ROAD, LEICESTER LE4 5AN
TELEPHONE: 0533-58128/9 TELEX: 341581

ARISTOCRATS IN CONTROL

WW-144 FOR FURTHER DETAILS

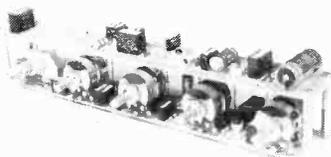HART ELECTRONICS Audio Kit Specialists since 1961



BAILEY/BURROWS/QUILTER PRE AMP This is the tone control section of the best pre-amp kit currently available. Consider the advantages:—*First quality fibreglass printed circuits with roller tinned finish and all component locations printed on reverse. *Low noise carbon film and metal film resistors throughout. *Finest quality low-noise ganged controls with matched tracks and shafts cut to length. *Well engineered layout for total stability. *Special decoupling and earthing arrangements to eliminate hum loops. *Controls, switches and input sockets mount directly on the boards to TOTALLY ELIMINATE wiring to these components. (We know of one pre-amp kit which claims its controls mount directly on the board—and so they do, by their shaft bushes! You still have to wire them up!!)

*We incorporate the Quilter modification which is most important as it reduces distortion and increases the bass and treble control range.

As can be seen from the photograph the tone control unit is very slim (only 1½" from front to back) and may therefore be used in many other applications than our Bailey metalwork which it is designed to fit.

METALWORK AND WOODEN CASES These have been under review for some time; please send for latest information.

F.M. TUNER This latest addition to our range is designed to offer the best possible performance allied to the ease of operation given by push button varicap tuning. We have taken great care to look after the constructors' point of view and there are no coils to wind, no RF circuits to wire and no alignment is required. In fact the whole unit can be easily completed and working in an evening as there are only 3 transistors, one IC and two ready built and aligned modules comprising the active components. We have abandoned the concept of having a tuner as large as the amplifier and this new unit has a frontal size of only 1½ in. X 4 in. It can be mounted on the side of our Bailey amplifier metalwork thus turning it into a tuner/amplifier whilst only increasing its width by 1½ in. Cost of tuner chassis (no case) is £22 for mono, £25.45 for stereo. Metal case £3.55. An extended wooden case to fit tuner and amplifier will be offered shortly.

STUART TAPE CIRCUITS Our printed circuits and components offer the easy way to convert any suitable quality deck into a very high quality Stereo Tape unit. Input and output levels suit Bailey pre amp. Total cost varies but around £35 is all you need. We can offer tape heads as well if you want new ones.

All above kits have fibreglass PCB's. Prices exclude VAT but P&P is included.

FURTHER INFORMATION ON ALL KITS FREE if you send us a 9 in. X 4 in. S.A.E. REPRINTS Post free, no VAT.

Bailey 30W 18p.


STUART TAPE RECORDER All 3 articles under one cover 30p.

BAILEY/BURROWS/QUILTER Preamp circuits, layouts and assembly notes 15p.

All prices exclude VAT.

Penylan Mill, Oswestry, Salop

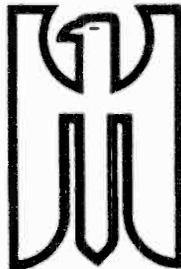Personal callers are always welcome, but please note we are closed all day Saturday



Phoenix Electronics (Portsmouth) Ltd

139-141 Havant Road,
Drayton, Portsmouth, Hants PO6 2AA

Full member of AFDEC—the industry's association of franchised electronic component distributors.

Our prices include VAT at the current rate—and carriage on all goods is free.

Send for our catalogue and price list—we'll mail that to you free, too.



THIS MONTH'S BARGAIN OFFER— Rectifier kit.

4 each—1N4148, AA144, 1N4004, 1N4006, 1N5402, 1N5406, SCR 0.6A/200V, Bridge 1A/400V + 4 voltages of 400mW Zeners—catalogue value £8.60.

BARGAIN PACK PEP4—£6.40

Please send your catalogue—free!

Name

Address

..... WW7

WW-084 FOR FURTHER DETAILS

Eliminate TV receiver distortion with Celestion *TELEFI*




TELEFI

At last you can enjoy TV entertainment with the added pleasure of true Hi-Fi sound. Telefi is a unique electronic invention which picks up VHF from the TV and relays this through your own Hi-Fi equipment. Telefi ensures crisp, full-range, distortion-free reproduction of music and speech providing an improvement over ordinary TV sound which will amaze you. Telefi is safe and requires no permanent connection to the TV set. Telefi is indispensable to the TV viewer who requires Hi-Fi TV sound.

"As selected for The Design Centre, London"

LOUDSPEAKERS

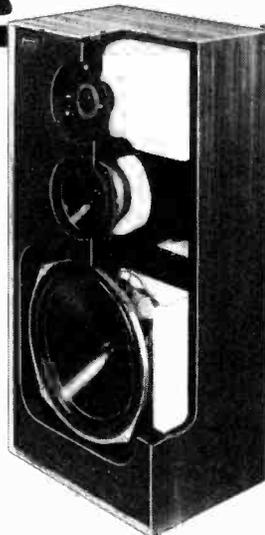Celestion Loudspeakers are engineered to the highest standard and provide superlative sound reproduction. The cut-away illustration shows the high, mid and bass speakers used in the Ditton 44 Monitor, one of the most popular loudspeakers available to the discerning listener. A range of models is available to suit your personal requirements, Celestion Hi-Fi Loudspeakers carry a five-year guarantee.



The Hadleigh loudspeaker, was specially created to meet a public demand for a high quality speaker of compact proportions. Not a difficult task for Celestion who produce the most popular bookshelf speaker ever (Ditton 15) – but we set out not only to produce an immaculate loudspeaker with a sparkling performance, but to do so at a budget price. For the enthusiast seeking a really excellent Hi-Fi system at reasonable outlay we recommend without hesitation the Hadleigh.

Celestion



Loudspeakers for the Perfectionist
DITTON WORKS, FOXHALL ROAD, IPSWICH, SUFFOLK IP3 8JP.

WW—059 FOR FURTHER DETAILS

RADFORD

AUDIO MEASURING INSTRUMENTS



LOW DISTORTION OSCILLATOR SERIES 3

A continuously variable frequency laboratory oscillator with a range 10Hz–100kHz, having virtually zero distortion over the audio frequency band with a fast settling time.

Specification:	
Frequency range:	10Hz–100kHz (4 bands)
Output voltage:	10 volts r.m.s. max.
Output source resistance:	150 ohms unbalanced (optional 150 ohms unbalanced, plus 150/600 ohms balanced/floating)
Output attenuation:	0–100dB (eight, 10dB steps plus 0–20dB variable)
Output attenuation accuracy:	1%
Sine wave distortion:	Less than 0.002% 10Hz–10kHz (typically below noise of measuring instrument)
Square wave rise and fall time:	40/60 n.secs.
Monitor output meter:	Scaled 0–3, 0–10, and dBV.
Mains input:	110V/130V, 220V/240V
Size:	17" (43cm) X 7" (18cm) high X 8 3/4" (22cm) deep
Price: 150 ohms unbalanced output:	£250
150/600 unbalanced/balanced floating output:	£300

DISTORTION MEASURING SET, SERIES 3

(illustrated above)

A sensitive instrument with high input impedance for the measurement of total harmonic distortion. Designed for speedy and accurate use. Capable of measuring distortion products down to 0.001%. Direct reading from calibrated meter scale.

Specification:	
Frequency range:	5Hz–50kHz (4 bands)
Distortion range (f.s.d.):	0.01%–100% (9 ranges)
Input voltage measurement range:	50mv–60V (3 ranges)
Input resistance:	47K ohms on all ranges
High pass filter:	12dB/octave below 500Hz
Power requirement:	2 X PP9, included.
Size:	17" (43cm) X 7" (18cm) high X 8 3/4" (22cm) deep
Price:	£200

Now available in reasonable delivery time

RADFORD LABORATORY INSTRUMENTS LIMITED

Bristol BS3 2HZ
Telephone 0272 662301

WW—049 FOR FURTHER DETAILS


wireless world

Electronics, Television, Radio, Audio

FEBRUARY 1975 Vol 81 No 1470

Contents

- 51 **Measuring what we perceive**
52 **Navigation by satellite** by *W. Blanchard*
58 **Project: Transformer phase reversal** by *T. Palmer*
59 **News of the month**
BBC research in quadraphonics
Electronics industry surveyed
Miniature solid-state TV camera
61 **Charge coupled devices—3** by *D. J. MacLennan*
65 **Letters to the editor**
Quad broadcasting—an alternative view
Using i.e.ds as photocells
Series and parallel feedback
69 **Solid-state digital clock** by *D. D. Clegg*
73 **About people**
74 **Electronic engineers' slide-rule** by *L. Nelson-Jones*
75 **Emergency power generator** by *J. M. Caunter*
77 **HF predictions**
78 **Space news**
79 **AF and r.f. speech clipping** by *D. A. Tong*
82 **Literature received**
83 **Figure of merit for f.m. tuner front ends** by *G. J. King*
85 **February meetings**
86 **World of amateur radio**
87 **Pseudo-random binary sequence generators** by *F. Butler*
92 **High capacity p.c.m. system**
92 **Sixty years ago**
93 **Circuit ideas**
DC level clamp
Analogue gate with no offset
Converting an electronic organ to piano sound
Ramp generator with independent slope and amplitude control
95 **Circuits 20: Transistor pairs** by *J. Carruthers, J. H. Evans, J. Kinsler and P. Williams*
97 **New products**
a74 **APPOINTMENTS VACANT**
a94 **INDEX TO ADVERTISERS**

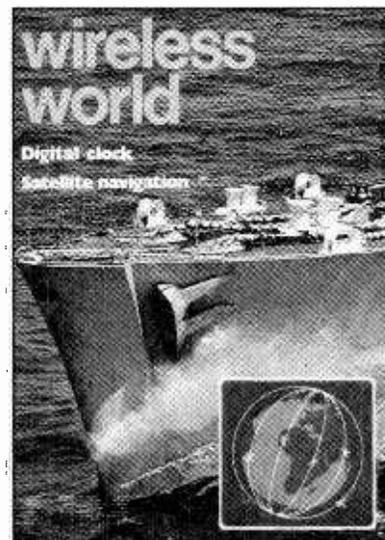

This month's front cover picture introduces the article on navigation by satellite in this issue and shows the polar orbits of the "Transit" satellites used in the system described.

IN OUR NEXT ISSUE

Simple f.m. tuner

Easy to build high quality design using commercial front end and new i.c. phase locked loop demodulator

Noise - confusion in more ways than one

Many special terms and ideas, seeming to have little in common, make it difficult to follow discussions about noise. This article looks at some of the basic ideas and prepares the ground for later articles

Using video tape recorders with domestic TV

The interface between video tape recorders and domestic receivers is examined, together with changes in receiver design to accommodate a reduced-quality video signal

SIXTY-FIFTH YEAR
OF PUBLICATION



Price 30p (Back numbers 50p)

Editorial & Advertising offices: Dorset House, Stamford Street, London SE1 9LU.

Telephones: Editorial 01-261 8620; Advertising 01-261 8339.

Telegrams/Telex, Wiworld Bisnespres 25137 London. Cables, "Ethaworld, London SE1."

Subscription rates: 1 year, £6 UK and overseas (\$15.60 USA and Canada); 3 years, £15.30 UK and overseas (\$39.80 USA and Canada). Student rates: 1 year, £3 UK and overseas (\$7.80 USA and Canada); 3 years, £7.70 UK and overseas (\$20.00 USA and Canada).

Distribution: 40 Bowling Green Lane, London EC1R 0NE. Telephone 01-837 3636.

Subscriptions: Oakfield House, Perrymount Rd, Haywards Heath, Sussex RH16 3DH. Telephone 0444 53281.

Subscribers are requested to notify a change of address four weeks in advance and to return envelope bearing previous address.

© I.P.C. Business Press Ltd, 1975



**For the Service Engineer
with dynamic performance
and terrific versatility**

The Telequipment D61 Oscilloscope

Service engineers, it's all for you in Telequipment's D61. In a robust, compact package you have all the tools of your trade. The D61 gives you single beam, dual-trace and X-Y modes; automatic selection for TV line or frame displays, and for chopped or alternate modes.

The lightweight easily portable D61 provides a wide ranging performance at the minimal cost of £125* — a sum quickly recoverable in the time saved by the simplicity and reliability of its operation.

A minimum of controls makes it extremely simple to use and gives room for a large bright 8 x 10cm display. These features, plus the superb triggering qualities built into the instrument make the D61 ideal for the discerning test engineer.

For full details contact

TELEQUIPMENT 

**Tektronix U.K. Ltd.,
Beaverton House, P.O. Box 69, Harpenden, Herts.
Telephone: Harpenden 63141 Telex: 25559**

*Exclusive of VAT

WW—083 FOR FURTHER DETAILS

T012 9/74

wireless world

Measuring what we perceive

Editor:

TOM IVALL, M.I.E.R.E.

Deputy Editor:

PHILIP DARRINGTON
Phone 01-261 8429

Technical Editor:

GEOFFREY SHORTER, B.Sc.
Phone 01-261 8443

Assistant Editors:

BILL ANDERTON, B.Sc.
Phone 01-261 8620
BASIL LANE
Phone 01-261 8043

Drawing Office:

LEONARD H. DARRAH

Production:

D. R. BRAY

Advertisements:

G. BENTON ROWELL (*Manager*)
A. PETERS (*Classified Advertisements*)
Phone 01-261 8508 or 01-928 4597
JOHN GIBBON (*Make-up and copy*)
Phone 01-261 8353

I.P.C. Electrical-Electronic Press Ltd
Managing Director: George Fowkes
Administration Director: George H. Mansell
Publisher: Gordon Henderson

An electronic reproduction system does not end at the acoustic or visual transducer but at the human brain, passing information via the human sense organs. Considering this, it's surprising how little work has been done on the psychology of perception in relation to electronic systems. The most familiar psychometric tests are of course the subjective assessment of sound quality from loudspeakers and of picture quality from television displays. With loudspeakers the commonest method is to make comparisons between two speakers at a time and from these derive an order of rank of the speakers under test. With television systems graded scales are often used, giving either grades of picture quality from "excellent" to "bad" or grades of picture impairment from "imperceptible" to "unusable". The trouble is that there are so many methods in use—for example eight different scales for picture assessment. It's unlikely that we shall make any important progress in the psychometry of electronic systems until international standardization of techniques is achieved.

The greatest prize to be won by improved methods of subjective assessment is the correlation of the subjective evaluations with objective data obtained from measurements. The aim, of course, is to be able to measure quality—hitherto a human experience—by instruments. With television systems this is not too difficult because picture quality can be largely defined by the magnitudes of various effects (e.g. noise) seen on the screen—which acts as a kind of oscilloscope—and these effects have direct electrical counterparts. With audio systems, as everyone knows, it is much more difficult, especially as subjective judgements are complicated by aesthetic responses of liking and disliking certain characteristics of the sound. Recently, however, there has been an interesting piece of research in Denmark* which claims to have derived two "psychological dimensions" from experimental data obtained through listening tests on loudspeakers. These "dimensions" cannot be explained by the subjects but are nevertheless composed of groups of the 35 subjective qualities (e.g. "brilliant") used in the listening tests. Correlations are claimed to exist between the subjective judgements made under the two "dimensions" and the measured sound pressure, power and phase responses of the loudspeakers.

Standardization of psychometric tests is needed first of all in the test conditions (e.g. room lighting for television, room acoustics for audio). Secondly, it is needed in the method of selecting subjects (e.g. whether experts or laymen or both). Then of course there must be standardization of the qualities to be assessed and standard terms to describe them, translatable into different languages. We also need standardization of the grading of scales and of the numerical "scores" assigned to particular grades. Finally there should be standardization of the statistical methods used, for example, to determine the uncertainty of the subjective data and the dependence of this data on the subjects and on the "programme" material. Only when such stringent controls are applied will it be possible to establish relationships between the results of different workers and so achieve real progress.

*Staffeldt, Henrik, "Correlation between subjective and objective data for quality loudspeakers." *J. Audio Eng., Soc.*, vol. 22, no. 6 (1974).

Navigation by satellite

Ship position finding using hyperbolic system and Doppler shift provided by orbiting satellite u.h.f. transmitters

By W. Blanchard

Redifon Telecommunications Ltd

The US Navy's navigation satellite system, using five "Transit" satellites, has been in operation for some years. This article, after explaining the basic principles of the system, describes modern British ship-borne equipment for navigating by it and discusses accuracy and uses.

Many radio navigation systems have been proposed in the last 50 years; quite a few of them never got any further than the files of patent offices, while of those that were actually built only a small number gained recognition as useful adjuncts to the navigator's stock-in-trade. Just about all the possible combinations and permutations of land-based systems have been investigated at some time or another, or so it seems when one goes through the files, and the emergence of a radically different system is a very rare event.

Examination of systems in current use reveals that as range is extended or accuracy requirements increase the problems become severe, particularly where both these features are demanded simultaneously. Very high accuracy at very short ranges is possible; moderate accuracy at moderate ranges is relatively easy; rather poor accuracy at very long ranges is also possible; but to give very high accuracy at very long ranges is beyond the capabilities of existing land-based techniques. It is not difficult to see why this should be so. The earth is approximately spherical, and to achieve long ranges means that whatever radio frequency is used must be capable of following the curve of the earth's surface. Medium and low frequency ground-waves do this to some extent, but changes in ground conductivity have a perturbing effect that can ruin any pretensions to high accuracy, as well as making sure that the wave does not get very far anyway. Ionospherically-reflected sky-waves also can follow the curve, sometimes without any great attenuation for many thousand of miles, but now the great variation in the reflecting medium itself from hour to hour is the agency that prohibits any serious attempt at good accuracy. The highest accuracies are obtained by the use of radio frequencies sufficiently high to operate in the space-wave mode, which by definition cannot follow the earth's curvature and consequently have a very limited range. So the would-be designer of a worldwide high-accuracy system faces fundamental physical limitations that, until the

advent of satellites, were insurmountable.

Satellites opened up new possibilities. Now it became possible to put u.h.f. transmitters out into space where they could "see" a large proportion of the earth's surface at one time, and the use of the virtually unperturbed space-wave from these transmitters allowed highly accurate measurements. It was not long before an experimental navigation satellite had been launched, and by 1964 the first complete system for marine navigation was in being.

Like so many other advances, the US Navy Navigation Satellite System (NNSS) did not happen as a result of an official committee being appointed to study the problem. Observation of the Doppler changes in the signals from the Russian Sputnik in 1957 ("Artificial satellites of the earth," *Wireless World*, December 1957, page 574) led to speculation that it should be possible to establish the position of the observer if the satellite orbit were already known, and preliminary experiments confirmed that this was indeed so. There were considerable practical problems in implementing the basic idea, one of them being the difficulty of designing an ultra-stable 5MHz frequency source for the satellite that would survive the launch and remain stable without human intervention for years afterwards. Naturally, if the satellite frequency was unstable, unpredictable apparent Doppler shifts would be measured by the receiver. The current satellites were designed as a result of lessons learnt in the earlier tests, and have proved to be very reliable. There are five of them, orbiting the earth at an altitude of about 600 miles. The satellites are in polar orbits, and the orbit planes are at angles of about 45° from each other.

One way of describing the principles of the NNSS system is by comparing it with the perhaps better-known hyperbolic radio systems, Loran, Omega, and Decca (see "Hyperbolic radio navigation systems" by F. S. Stringer, *Wireless World*, August 1969, page 353). In these the receiver establishes a difference of range between two transmitters by measuring the dif-

ference in time of reception of radio signals transmitted at precisely known intervals. It is usually assumed that the speed of radio wave propagation is known and therefore that time can be translated into distance (although this is not always a safe assumption in practice). The operational differences between these systems lie in the actual modes of transmission, the radiated frequencies, the format of the transmission, and the way in which the signals are detected and used in the receiver—the underlying principle always remaining the same. This fundamental principle also applies to satellite positioning systems. The earth-bound systems usually have little difficulty in locating their transmitters to a high degree of precision, but they have considerably more difficulty in translating time intervals into distances. Until comparatively recently it was impossible to know precisely, at a remote site, the exact time at which a transmitter emitted (say) a pulse, absolute time standards not being good enough. Direct range measurements could not be made, and a differential system requiring two transmitters was necessary. Because these two could only provide a single position line, the familiar triplet came into being to provide two position lines and hence a fix. Again, because difference of range was being measured the single position line was hyperbolic in form, and it was this that gave these systems their generic name. It should be noted that the familiar hyperbolae drawn on navigation charts are actually only the intersection of hyperboloids with the earth's surface, and if the receiver is not on the earth's surface the use of these hyperbolae can cause errors.

The same principles can be applied to satellite navigation by thinking of the satellite as a moving transmitter successively occupying the positions that the transmitters of a hyperbolic system might have used, as shown in Fig. 1. If the interval between the satellite's positions P_1 and P_2 is two minutes, then the "baseline" between P_1 and P_2 is about 960km, and a measurement of range difference between these points

produces a hyperboloid exactly as for a ground system. The intersection of two or more hyperboloids will uniquely locate the receiver, not only on the earth's surface, but also in the vertical plane (although this last measurement is not particularly accurate). Obviously, considerably more than three satellite transmitter positions will be available and the resultant fix will be that much more accurate.

But some basic problems remain. How do we know where the satellite is every two minutes (or whatever interval we choose), and how do we measure these range changes?

Superficially, the determination of a satellite's orbit is not particularly difficult, at least to the degree of accuracy sufficient for pointing aerials, but when a fix accuracy measured in metres is required something rather better is necessary. In fact, four tracking stations in the USA are engaged solely on the job of continuously tracking all the five satellites, known as Transit satellites, in the system described here. The resultant orbital data is used to compute, for some 16 hours ahead, where each satellite will be every two minutes throughout this period—or rather to compute the orbital parameters that will enable these positions to be calculated. There would be a massive logistics problem if this data had to be distributed to all potential users world-wide and renewed every few hours—in fact it would be an impossible task. So it is arranged that the satellites themselves broadcast the data. A ground station injects into them their orbital parameters, where they are retained in a store and broadcast as phase modulation of the transmitted carriers. Because of the bumps and bulges on the earth's surface, which cause the satellites to follow a somewhat wobbly path, there are two sets of numbers: a "fixed" set, describing the basic Keplerian average orbit for the next 16-hour period, and a second "ephemeral" set which changes every two minutes and describes the variations from basic at each two-minute interval (Fig. 2).

The only other thing necessary for satellite position determination is accurate timing. With the satellite travelling at some $7\frac{1}{2}$ km/s, a fraction of a second error could throw the fix out by several kilometres. It is still not possible to ensure precise absolute time world-wide to the required accuracy, so the satellite provides its own timing standard. Every two minutes it transmits a series of 23 digital ones, followed by a short burst of 400Hz audio modulation. The transition between these indicates an exact even minute of Greenwich Mean Time accurate to within 33µs, reducing the residual error from this source to the order of centimetres. This audio "beep" can be heard quite easily on the satellites' transmission and is an easy way of identifying the Transit satellites, as well as being a very accurate time check. The phase modulation is at a 50 bit/s rate, sounding rather like a subdued mains hum.

The only other measurement to be made is the difference of range. It might be possible to do this directly by using a pulsed

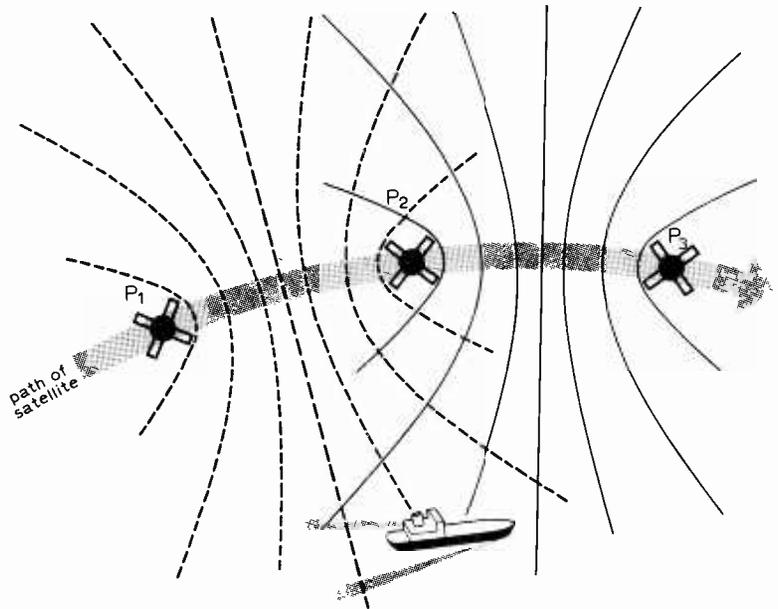


Fig. 1 Hyperbolae representing range differences measured in a ship between "transmitters" at P₁, P₂ and P₃, which are in fact successive positions of an orbiting satellite carrying a u.h.f. transmitter. Intersection of two (or more) hyperbolae locates the ship's receiver.

transmission but it would require the ground station mentioned above to transmit and would suffer the usual limitations of all such co-operative systems. If the ground station cannot transmit, the only course left open is to use the Doppler shift of the satellite's transmitted frequency. Since this is caused entirely by the motion of the satellite relative to the observer, integration over a fixed time period yields the necessary change of range measurement.

The requisites for this to work are that (a) the satellite's frequency does not drift appreciably over the measurement period, (b) the receiver's standard frequency reference does not either, and (c) the transmission path does not itself introduce any Doppler shift. Both (a) and (b) can be controlled to a sufficient degree

by careful design, but (c) cannot be controlled and is actually, for daylight satellite passes, the limiting factor on overall system accuracy. There are two causes of such unwanted shifts: an effect proportional to frequency caused by tropospheric bending, and an effect inversely proportional to frequency caused by the ionosphere. The tropospheric effect is unfortunately of the same character as the wanted Doppler shift, and cannot be separated from it, although a reasonable correction can be made by measuring local meteorological conditions and applying an empirical correction in the computing process. Fortunately, the effect is not very large and does not normally contribute more than a few tens of metres to the final fix error even without specific correction.

The ionospheric effect, which can cause much larger errors, is separable from the wanted shift provided that measurements on more than one frequency are available, and to this end the satellites transmit two frequencies. These two frequencies are controlled by the same reference oscillator and one is an exact multiple of the other (8/3). The actual frequencies transmitted are 400MHz offset by 32kHz (399.968 MHz), and 150MHz offset by 12kHz (149.988MHz). (The offsets are to prevent operation near nulls on crossovers, which would reduce the accuracy of the final Doppler count.) Under extreme conditions, a possible error of some 90 metres can be corrected in this way.

It is interesting to note that the correction falls to zero for most of the night hours, and hence the system is actually more accurate at night than by day—the reverse of most other radio navigation systems. When the system is being used only for normal marine navigation it is quite usual for only the 400MHz transmission to be utilized since, without highly accurate velocity sensors, the errors intro-

640232374	} ephemeral orbital parameters	} two-minute period
200172960		
210052942		
020072430		
030172633		
040272374		
050342053		
060331684		
422315120		
336697410		
303444370	} fixed orbital parameters	} Doppler count every 30 seconds
600196710		
300034390		
607462210		
327769320		
700000330		
300003040		
335366420		
300301300		
351003120		
310000000	} Doppler count every 30 seconds	
301470000		
600000000		
006000000		
000000000		
54315432		
200172960		
210052942		
020072430		
030172633		
040272374		
050342053		
060331684		
070371303		
422315120		
336697410		
303444370		

Fig. 2 Real-time printout of orbital parameters transmitted by a Transit satellite.

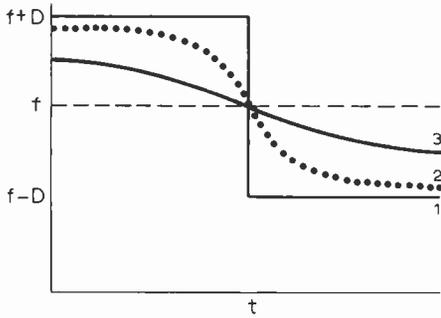


Fig. 3 Doppler shifts for observers at three different distances from the satellite's orbital path.

duced by unknown ships' motion will greatly outweigh ionospheric errors.

The actual Doppler shift to be expected on each of the two frequencies is not difficult to calculate for the extreme cases where the satellite is either directly approaching or receding from the observer. If the average orbital height is 600 miles (960km) then the orbital velocity will be about 7.37km/s, and since a frequency of 400MHz is a wavelength of 0.75 metre, the Doppler shift comes out at 9827Hz. At 150MHz it will be 3685Hz. If the observer were actually directly in the path of the satellite (equipped with a space suit,

no doubt!) this shift would stay constant at all times, the only change being a sudden one from $f+D$ to $f-D$ as it passed him, as shown in graph 1 of Fig. 3. If he is a little farther away from the orbital path, the change would not be quite as sudden (graph 2) and farther away still it would start taking on the character of an S-shaped curve (graph 3), until in the limiting case where he is so far away that there is no change of range at all, the curve would be a straight line. There is obviously direct correlation between change of range and the shape of this curve.

The transformation of these measurements into position is as follows:

The satellite transmits a stable frequency f_i which is received by the ship-borne navigator and designated f_r . This is compared to a stable local oscillator output frequency f_g to produce a frequency difference

$$\Delta f = f_g - f_r \dots \dots \dots (1)$$

Fig. 4 indicates the relationship between the frequencies. Over any time interval the number of beat cycles of the frequency difference are counted and integration accomplished.

From Fig. 4, using the first two intervals:

$$N_{1,2} = \int_{t_1}^{t_2} (f_g - f_r) dt = \int_{t_1}^{t_2} (f_g - f_i) dt + \int_{t_1}^{t_2} (f_i - f_r) dt \dots \dots \dots (2)$$

On the assumption that $f_i = f_r$, then $N_{1,2}$ is the Doppler count corresponding to the first and second time marks. Further, the time difference $\Delta t_2 - \Delta t_1$ is related to the slant range between satellite and receiver at P_1 and P_2 :

$$t_2 - t_1 = \frac{1}{c} (S_2 - S_1) \dots \dots \dots (3)$$

where c = vacuum speed of e.m. waves

S_1 = slant range from ship to satellite at P_1

S_2 = slant range from ship to satellite at P_2

Substituting (3) into (2) and solving for the difference in distance from the user to satellite yields the effective baseline, i.e.

$$\Delta S_{1,2} = S_2 - S_1 =$$

$$\frac{c}{f_g} N_{1,2} - (1 - \frac{f_i}{f_g}) c (t_2 - t_1) \dots \dots \dots (4)$$

Similarly

$$\Delta S_{2,3} = S_3 - S_2 = \frac{c}{f_g} N_{2,3} - (1 - \frac{f_i}{f_g}) c (t_3 - t_2) \dots \dots \dots (5)$$

Noting that $t_{i+1} - t_i$ where $i = 1, 2, \dots, n$ multiplied by c is the distance travelled by light in the time interval, allows some simplifying assumptions to be made. Further, note that $f_g = f_i + \Delta f$ and Δf is very small compared with f_i ; thus, to preserve computational accuracy, the above equations must be rearranged to avoid calculations of the form $\Delta f / f_g$. This is easily accomplished by using an additional point P_4 . Manipulating a third equation which is similar to the two above yields

$$-S_1 + 2S_2 - S_3 = \frac{c}{f_g} (N_{1,2} - N_{2,3}) \dots \dots \dots (6)$$

$$-S_2 + 2S_3 - S_4 = \frac{c}{f_g} (N_{2,3} - N_{3,4}) \dots \dots \dots (7)$$

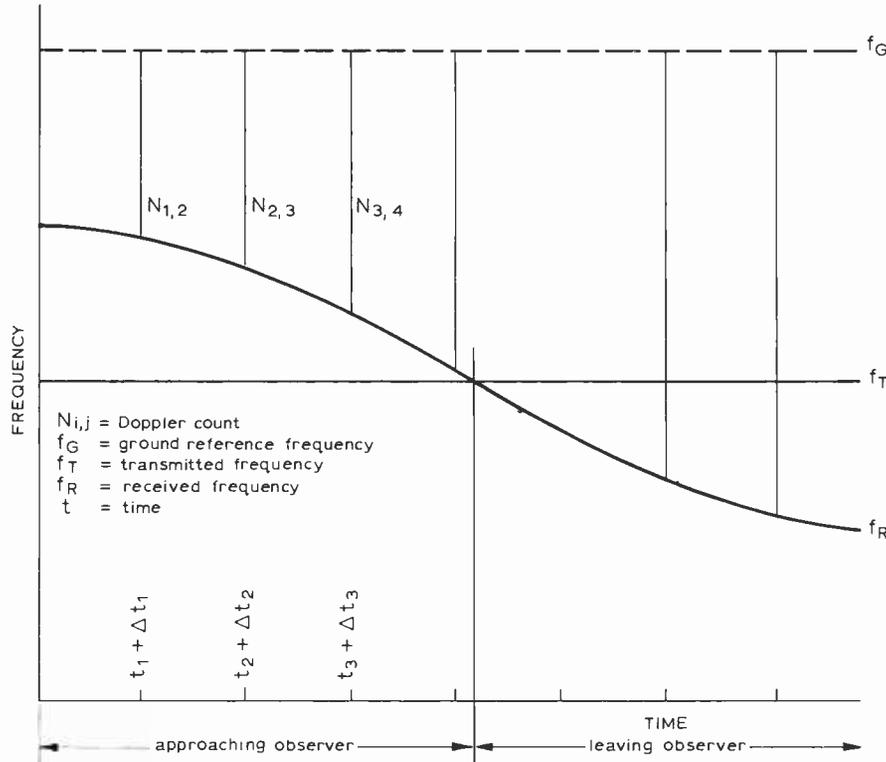


Fig. 4 Integrated Doppler count: f_T is the satellite's transmitted frequency; f_R the received frequency, f_G the ship's reference frequency; and $N_{1,2}$ etc. the Doppler count (t = time).

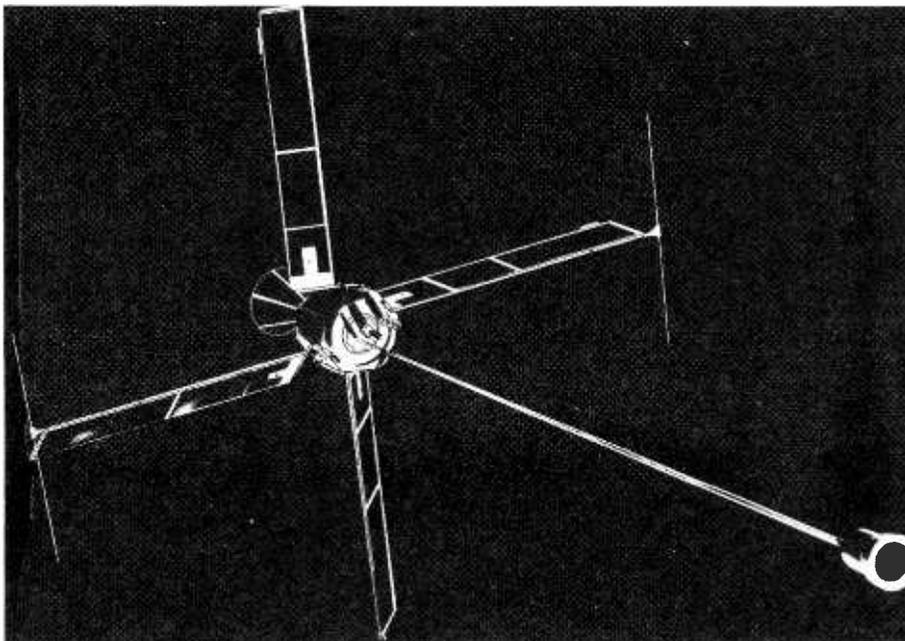


Fig. 5 Basic structure of a Transit satellite.

where S_i are functions of the ship and satellite positions at each point i where $i=1, 2, \dots, 9$. Hence two equations in two unknowns allow the determination of the ship's two unknown co-ordinates, latitude and longitude.

A usable maximum of nine two-minute data points is available during optimum satellite passes. However, many factors—low elevation, interference, etc.—can cause data to be missed or be invalid in this basic two-minute Doppler, least squares formulation. The situation can be improved by dividing the two-minute period into smaller data intervals, when temporary loss of data would only involve discarding one of the smaller data intervals instead of the whole two minutes. Thereby the number of data intervals is increased, and the inherent noise rejection properties of the least squares formulation permit a more accurate position computation, provided that the interval chosen is not too small. The optimum interval appears to be about 23–30 seconds, and when such an interval is chosen, it is known as the short Doppler formulation.

The "Transit" satellites

The five satellites, launched into nearly circular polar orbits by Scout rockets, orbit the earth at heights from 450 to 700 miles. The choice of orbit is determined by the need to maintain them in almost a circular path to minimise acceleration and deceleration characteristics of non-circular paths, and to negate the precession of orbital planes towards eventual overlap which might occur with non-polar orbits.

Each satellite contains a command receiver; a data decoder; switching logic and memory banks; readout control circuits, digital data to phase modulation encoder; stable 5MHz oscillators; and $1\frac{1}{2}$ -W 150 and 400MHz transmitters. They weigh about 150 pounds and measure 18in \times 12in excluding solar panels and a stabilisation boom. The last-mentioned is necessary to ensure that the satellite is always oriented with its aerials pointing at the earth, eliminating unwanted modulation effects and enabling the use of simple aerials for ships' receivers. It also allows the use of a directional aerial on the satellite itself which radiates a circularly-polarised signal with some concentration of power towards the edges of cover.

Primary power is provided by a set of nickel-cadmium cells, recharged by the solar panels, providing about 30 watts of power at launch, dropping to some 25 watts after five years. Mechanical design is relatively simple, with no moving parts other than a few relays which operate only very infrequently. There are no tape recorders, television cameras, or anything like that, and reliability has been very high, as is shown by the fact that three of the five satellites now in use have been operating uninterruptedly for over six years.

Electronically, they are quite sophisticated, containing some 35,000 magnetic store cores and 6,200 other electronic

Fig. 6 Phase modulation patterns for transmitting orbital data from satellite to ship in binary digital form. Patterns representing 1 and 0 digits are: 1, the (a) pattern followed by (b) pattern; 0, the (b) pattern followed by (a) pattern. These choices, avoiding (a) and (b), keep sidebands at a safe separation whatever bit sequences occur.


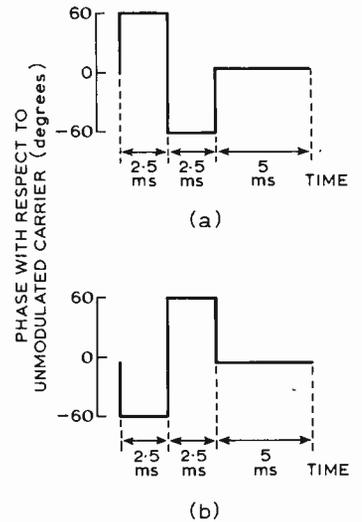


Fig. 7 Satellite navigation receiver (Redifon RSN-1) showing computer keyboard and printed circuit board.

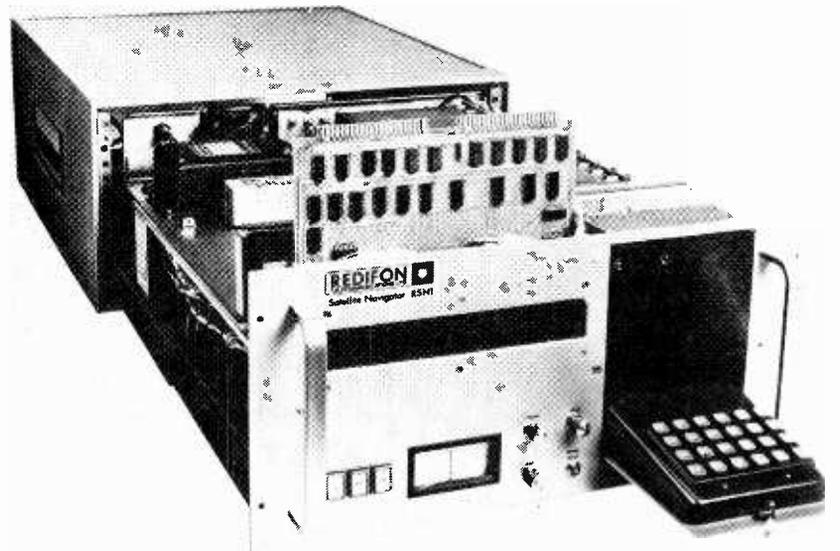

components. Of the 46,000 permanent joints, 40,000 are welds, and only 6,000 are solder connections. Generally, except for certain telemetry functions that could be lost without destroying operational usefulness, redundant wiring and solder connections are used, and where plugs have to be used, complete redundancy is provided.

The injected orbital data is stored in a magnetic core memory and transmitted as phase modulation on both frequencies that are radiated, these frequencies being derived from the stable 5MHz oscillator that provides the basic timing and frequency for the satellite. This phase modulation is symmetrical so as not to introduce offset errors in the Doppler measurement, typical waveforms being shown at Fig. 6. The memory, read out every two minutes, contains 156 words of 39 bits each, plus an additional 19 bits. There are 11 semi-fixed parameters describing the satellite's orbit, and a further eight words that are used to describe the corrections that must be made to these 11 parameters, as described earlier.

Receivers. At one time receivers for the system tended to be rather large and bulky, the practice being to include the receiver, computer, power supplies and controls within a standard 6-ft 19-in rack. This approach is now obsolete, the same

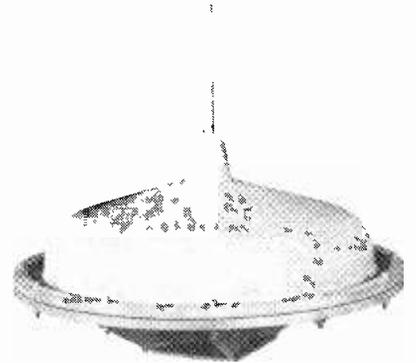


Fig. 8 Aerial used with receiver in Fig. 7.

facilities being obtainable within a much smaller space, as demonstrated by the Redifon equipment shown in Fig. 7. This requires only a single unit 19in wide and 10in high in addition to the aerial unit. The aerial itself sometimes surprises those who imagine that all satellite operations require aerials of the Goonhilly type, being only a small quarter-wave whip and ground plane (Fig. 8). Installation is correspondingly easy.

A block diagram of the receiver is shown in Fig. 9. The antenna signal is fed to a 400MHz filter with a bandwidth of 5MHz which is used to reject spurious

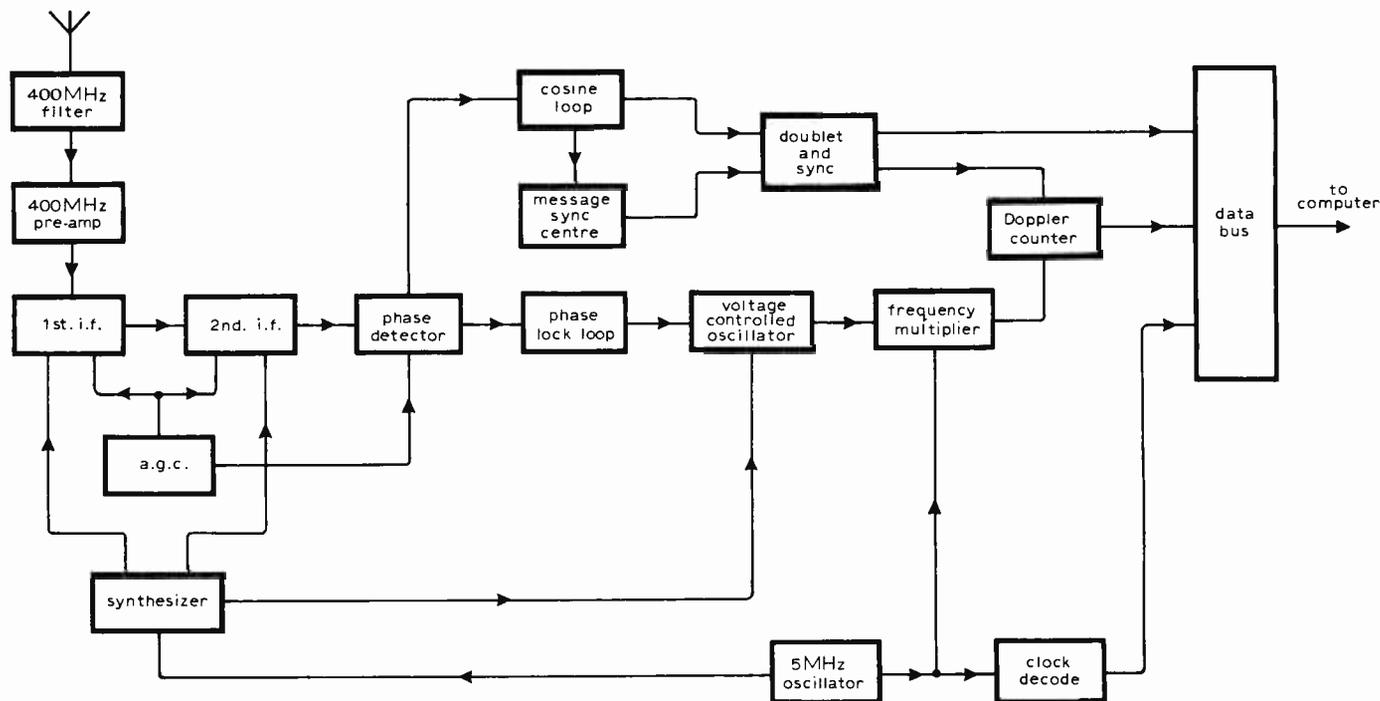


Fig. 9 Simplified receiver block diagram.

and unwanted signals. Signal output from the filter is received and amplified by a 400MHz amplifier with a gain of 30dB, a bandwidth of 15MHz, and 2.5dB noise figure. The overall sensitivity of these sub modules is -135dBm .

The i.f. section of the receiver is composed of two i.f. amplifiers. The inputs to the first, double balanced, i.f. amplifier/mixer are: (a) the received signal ($400\text{MHz} - 32\text{kHz} \pm \text{Doppler shift}$); (b) a 360MHz reference signal, and (c) an a.g.c. signal with 70dB range. The output of the module is therefore a signal of $40\text{MHz} - 32\text{kHz} \pm \text{Doppler shift}$. The second i.f. stage has a gain of 65dB and a 65dB a.g.c. signal. The output of this stage is an i.f. signal at a frequency of $15\text{MHz} \pm \text{Doppler shift}$. The crystal mixer contained within this module has a 1.5kHz bandwidth. This is followed by a phase detector, the output of which is a signal representing the Doppler shift frequency, the input signal from the second i.f. stage being compared to a $15\text{MHz} - 32\text{kHz}$ reference signal. The bandwidth of this stage is less than 3MHz but is immaterial as the overall bandwidth is controlled by the crystal mixer. The phase modulated data transmitted from the satellite is now detected and phase quadrature signals generated. The phase and correlation outputs are transmitted to the "cosine loop" and phase lock loop amplifier, respectively.

The phase lock loop amplifier inputs are the correlation and phase signal outputs of the phase detector and a d.c. to 200Hz reference signal. The primary purposes of this amplifier are to null the difference error of the phase detector input and provide the acquisition control signals.

This module is designed for either automatic or manual tuning.

The voltage controlled oscillator functions as a combination of a v.c.x.o. amplifier and an oscillator/multiplier

section. The bandwidth of the v.c.x.o. and amplifier is 20Hz with a second order loop implemented.

The basic functions of the cosine loop, message sync counter, doublet and sync modules, are to take the delayed acquisition, fast acquisition and correlation output signals from the phase lock loop and phase detector and to generate the demodulated signal information as well as forming the timing (or synchronization) signal. The cosine loop contains a phase locked crystal oscillator and a digital phase detector. The basic phase output frequency is 101Hz. The output of the doublet and sync module is the basic satellite orbital data signal at a 50Hz bit rate.

The frequency standard for the satellite receiver and the external real-time clock is a 5MHz crystal oscillator, featuring good short-term stability, low phase noise and ageing as low as 1×10^{-9} per day. It employs a 5MHz, third overtone metal-enclosed crystal mounted in an oven.

The software is responsible for the formation of the satellite message word and Doppler count accumulation. Some of the salient interface features include computer control via a strobe and clear command and a "hold while data transferring" feature to eliminate the possibility of writing one bit over one being transferred.

The computing operations for the Redifon satellite navigators are provided by a Data General Nova computer, fitted with memories appropriate to the user's requirements. This is a general purpose computer with a 16-bit word length and a 1.2 microsecond memory cycle time. It is organised around four accumulators, two of which can be used as index registers, providing efficiency and ease of programming. As part of its standard con-

figuration, it has a direct memory access data channel in which data passes to the memory without having to go through the central processing unit. With its console removed, the Nova is operated as an integral part of the satellite navigator, and is controlled by the operator via a small keyboard on the front panel of the main receiver unit (see Fig. 7). This eliminates any need for a teleprinter to be installed for the sole purpose of "talking" to the computer, and does not presuppose any expertise in computer operation on the part of the operator. The most-used functions are given separate keys—latitude, longitude, GMT, etc.—while the inclusion of numerical keys allows the use of auxiliary functions.

Operation. Due to the Doppler shift the received frequency can be anywhere within a 20kHz band centred on the actual transmitted frequency, and with only a 1.5kHz bandwidth provision has to be made for sweeping over the band of possible frequencies. This is done by applying a ramp signal to the voltage controlled oscillator, which is locked out when a transmission is detected. Lock-on is indicated both by a light and by the meter. Also incorporated in the receiver is a small loudspeaker to give aural indications. Once the signal is locked, the next step is to synchronise with the satellite message. Obviously, large errors could occur if the data stream were entered at the wrong point. This is done, as described earlier, by sensing an end-of-message signal. When this is achieved, a green lamp lights and the computer begins message acquisition. Every two minutes, the data stream is repeated, the number of repetitions actually received depending upon the length of time the satellite is above the horizon. At least three repetitions are required by the computer before

it will process the message, in order to provide a measure of redundancy in the face of possible noise bursts. Therefore, if part of one message is destroyed by noise it can be filled by a subsequent repetition, and even if lock is completely lost on the satellite the computer can still derive a fix provided either that lock is regained subsequently on the same satellite, or sufficient repetitions have already been received. The period of lost lock can be as long as four minutes.

The Doppler count itself is performed by the computer in 30-second blocks (see Fig. 2). Older equipments used a full two-minute period, which meant that fewer counts were obtained in any one pass and that the final fix was more liable to degradation due to noise. This 30-second count period has enabled a much higher proportion of satellite passes to be used than formerly.

Once the satellite signal is lost the computer suspends operations while the receiver searches for the signal in case the loss of lock has only been due to noise. After four minutes, if no signal reappears, the computer declares "end-of-pass" and starts to calculate the fix, although it has first to decide whether it has sufficient Doppler and orbital information. If not, it will not proceed further.

Initially, the programme uses the dead-reckoned position already stored in the computer as a starting point to calculate a Doppler shift curve, using the orbital parameters received from the satellite. This is compared with the curve actually measured, and unless they coincide, a new curve is computed using a slightly different position. This goes on until the two curves do actually coincide within certain limits, and the last position is assumed to be the actual true position. This takes no more than a few seconds, and the final fix is displayed to an accuracy of one-thousandth of a minute of arc (about 6 feet) of both latitude and longitude, together with the time of fix to one second. The fix can thus be plotted directly on to normal marine charts, without any need for special charts or conversion tables.

The part played by the operator in all this is quite small, since the receiver itself operates without intervention and the computer needs only a few initial settings when first switched on. The most important of these are approximate latitude, longitude, and GMT. None of these need be very accurate—latitude and longitude need be only within 3° (about 120 nautical miles at 50°N)—and time within 15 minutes.

After this, there is no absolute need for operator intervention at all. The navigator equipment can be switched into the "auto" mode, wherein it will produce GMT, latitude and longitude, updated every 18 seconds. The first usable satellite pass after switch-on will produce an accurate fix which will re-set the navigator's estimate to precise position—provided the two are not widely different (Fig. 10). This feature is incorporated so that in cases where a large difference exists the navigator

5501

```
+051,27.3457, -000,11.9570
FREQ + 1924439
ITER 0003
RES. 0009
11E1 1111 1111 1111 1000 0000 0000 0000
DLAT + 0000034 DLON - 0000276
```

Fig. 10 Satellite fix message: top line, satellite fix; second line, offset frequency; third, number of iterations; fourth, highest residual; fifth, Doppler string; bottom line, difference between dead reckoning and satellite fixes in feet.

can make his own decision whether or not to accept the satellite fix. There are other reasons why the computer may not automatically update the dead reckoned position, since it is programmed to perform mathematical tests on its computation and, if not satisfied, it will present the calculated fix together with an indication why it was not used for updating. The reason may be excessive noisiness of the data, inability to make calculated and actual Doppler curves fit precisely, insufficient data, and so on. But the navigator can always make the final decision.

System accuracy. Somebody once said that accuracies are just a matter of statistics, and after all the arguments about whether error curves have a Gaussian, exponential, square-law, or what-have-you distribution, or whether r.m.s., c.e.p., mean or standard deviations should be quoted, there sometimes seems to be little point in quoting anything at all.

But, anyway, of the ultimate accuracy of satellite navigation, it can be said that when used as a survey tool, put into a fixed position, and averaged over a period of some days, the repeatability accuracy has been shown to be better than 5 metres. Naturally, a receiver on board a moving vessel is not going to get anywhere near this figure, and it is interesting to see how the error budget is built up.

One of the errors used to be a rather imperfect knowledge of the earth's gravitational field, leading to errors in prediction of satellite position, but this knowledge has now been refined a great deal—over 415 parameters are now recognised as important in this respect—and this factor alone has led to a doubling of system accuracy over the last six years. Errors due to this do not now exceed 30 metres maximum for a single pass.

Another effect is refraction in the ionosphere and atmosphere, already mentioned. Tropospheric refraction is relatively unimportant, contributing only about 30 metres to the final error under worst-case conditions, but ionospheric refraction is more important, contributing about 90 metres error if uncorrected.

The major source of error for a ship at sea is uncertainty of the ship's velocity, particularly when this is in a north-south direction, and we are talking here of velocity over the ground, not through the water. Where greater accuracy is necessary, velocity-over-ground inputs are usually obtained either from Doppler sonar, or

from hyperbolic radio systems such as Loran-C.

One other correction has to be made, for aerial height. Actually, this is aerial height above the spheroid being used for calculation, and not simply height above sea-level, but the difference can be read directly off simple maps.

Usually, static accuracies of about 150 metres from a single pass for a single frequency, and about 50 metres for two-frequency equipment can be expected. Differences between individual equipments are very small—less than 15 metres.

Where a vessel is under way the additional errors due to movement are more complex to evaluate, but where sophisticated velocity-over-ground sensors are not installed, and only the standard ship's log and gyrocompass are available, a degradation of accuracy to some 500 metres may be expected. When these sensors are available, the accuracy reverts almost back to the static figures.

Uses. The strength of satellite navigation lies in its ability to provide virtually world-wide fixes to a high degree of accuracy, and its weakness in the fact that these fixes are not continuously available. The Redifon satellite navigation receivers overcome this latter problem by carrying on dead-reckoning between fixes, so that a position is always available. Provided that accurate inputs of speed and heading are available to the computer the accuracy of dead reckoning can be very high, but it is always time-dependent. Therefore satellite navigation becomes of less and less use as the vehicle velocity gets higher, and aircraft, for instance, make virtually no use of the system at all.

But slower vehicles such as ships are making excellent use of "satnav" for normal navigation as well as for the very demanding purposes of seismic and geophysical survey work. There is a growing trend for ships to carry automatic navigation systems to lessen the workload of the relatively few skilled officers they now carry, and satnav is an important ingredient of all such systems. In the field of geophysical exploration, the integration of a satellite navigator with hyperbolic systems is now common practice, the satnav providing ambiguity resolution for the hyperbolics. Satnav is even being used to provide remote location of buoys, a "bare-bones" receiver on board the buoy recording the Doppler curve as the satellite goes over, and transmitting it in digital form back to shore via another satellite link or via an h.f. link, where a central processor turns it into position.

Surveyors are using it, particularly in remote areas, for the location of control points. A portable receiver is set up at the point to be checked and records all satellite passes over perhaps two or three days. Later analysis results in a precise position that can be as good as 5 metres, referred to another known point. If a number of passes can be analysed, it is even possible to derive height above sea-level with a reasonable degree of accuracy.

Transformer phase reversal

An experimental demonstration for schools

by T. Palmer, B.A., Assoc. I.E.R.E.

Acton Technical College

After reading Cathode Ray's article*, I repeated some experiments I had performed on transformers at very low frequencies (0.1Hz) using centre-zero meters. Ordinary transformers do not have enough inductance to show the desired effects at 0.1Hz but a 45,000H coil sold by Unilab is satisfactory. It has two windings, A and B. Winding A has 20,000 turns and sits on one limb of a C-core. B has 17,000 turns and sits on the second limb. Coil A is used as the primary of a transformer.

The first step is to determine the sense of the windings. The C-core has a portion at the top, which I shall call the cap; it can be detached from the main body of the core. When this has been removed, and the transformer is placed in a horizontal position, we can use a compass needle to find that current entering the primary at *P* gives clockwise flux in the core; so does current entering the secondary at *C*. Since flux is the most important feature of a transformer, terminals *P* and *C* were regarded as analogous.

An advantage of using centre-zero meters is that we do not know how to connect them until we have thought about conventions. Here are mine: Primary voltage is positive when *P* is positive to *Q*. Secondary voltage is positive when *C* is positive to *D*.

Now we know how to connect the voltmeters in a consistent way: the positive terminal of the primary voltmeter, V_1 , is connected to *P*; that of the secondary voltmeter, V_2 , is connected to *C*, as shown in Fig. 2.

In later stages of the demonstration, we shall wish to connect centre-zero microammeters. Secondary voltage is positive when *C* is positive to *D*. Secondary current will be regarded as positive when current is flowing from *C* through the secondary load. We connect the positive terminal of the meter which measures secondary current, A_2 , to *C*.

Conditions are not the same in the primary. The reason why current flows at all in the primary is that an alternating voltage is applied to it. We regard the applied voltage as the "prime mover" and connect the positive terminal of the primary current meter to P_1 and the negative terminal to *P*.

Of course, no claim is made that these are the only suitable conventions; I think Cathode Ray would regret that they have been mentioned; but in demonstrations at 0.1Hz they seem unavoidable. Perhaps this is an argument for not performing experiments at low frequencies; but, by now, I am hooked.

With voltmeters V_1 and V_2 connected as shown in Fig. 2, when an alternating voltage is applied to the primary, it is easy to see that V_1 and V_2 swing in phase. On the basis of our conventions, there is no phase reversal.

Primary current shown on A_1 lags voltage by about 90° .

It is found that when the transformer is horizontal, compass needles placed at the junction of the cap and the main body of the core have sufficient leakage flux surrounding them to reverse their directions as the primary current passes through zero. It was the main purpose of the original experiments to draw attention to the alternation of the flux, which seems to me to be the most important feature of

transformer action that should be understood by elementary students. After the alternation of the flux has been shown by the compass needles, the transformer should be put in a vertical position. The weight of the cap reduces the minute air-gap at the junction and reduces leakage flux. When the transformer was horizontal, the cap had to be supported by a book at the correct height.

We can now go on to show that as the resistance of a secondary load is reduced, the secondary current increases, and so does the primary current. It must be admitted that the resistance of the primary and secondary windings does not allow a very large increase of primary current; but it can be seen.

Having shown the effects on centre-zero meters, with no electrical connection between primary and secondary, it seemed a pity not to show the waveforms for primary and secondary voltages on a double-beam oscilloscope. The Airmec display oscilloscope 252, with a very slow time base, is suitable. Since terminals *Q* and *D* on the transformer are analogous, they were strapped together and connected to the earth terminal of the scope. The input terminal for one trace was connected to *P*; that for a second trace, to *D*. The centre-zero meters can remain in circuit and the meters and the oscilloscope tell the same story in their own ways.

Almost the same story. The scope shows that secondary e.m.f. leads primary voltage by an angle too small to be detected on the meters. It is no doubt due to the voltage drop across the resistance of the primary winding (about $4k\Omega$). The small phase difference does not seem large enough to worry elementary students who, initially, are not concerned with primary resistance.

The oscilloscope shows that to avoid distortion in the transformer, the peak value of the voltage applied to the primary should not exceed 4V.

To appreciate the phase relationships on the centre-zero meters, it is convenient to have edgewise meters mounted one above another on a panel. We have a panel with four 50-50 μA meters. To use a meter as a voltmeter, a 220k Ω resistor was connected in series. To measure primary current, a meter was shunted by a 47 Ω resistor.

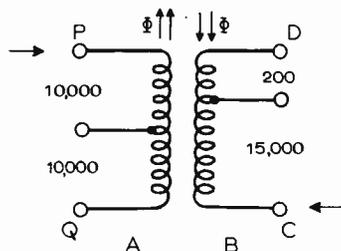


Fig. 1. Arrangement of Unilab transformer windings.

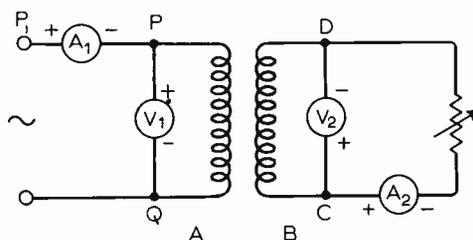


Fig. 2. Connection of meters to the transformer.

*Cathode Ray, "Transformer phase reversal". *Wireless World*, June 1971.

News of the Month

BBC demonstrate matrix system

Research Department work at the BBC into quadrasonic (four-speaker) surround-sound systems was made public at an "exposition of quadrasonic" during December. Organised by the IEE electronics division, demonstrations were given in separate rooms by the four commercial surround-sound proponents as well as by the BBC. Concentrating initially on two transmission channels, the research department have studied the commercial matrix systems (SQ, QS, BMX), finding that they suffered from poor stereo or mono compatibility or both. This led to the development of a matrix system that is similar to the Cooper/Nippon Columbia BMX matrix but modified in the light of experiments on directionality of the hearing system. The BBC say the coding gives improved stereo compatibility over other systems.

● We hear from Nippon Columbia that the BMX matrix is to be altered slightly, reducing the phase difference between channels for a centre front signal and improving stereo compatibility.

EEA promotions for 1975

The Electronic Engineering Association in the continuance of its policy to support industry operations concerned with overseas markets, will again sponsor and co-ordinate participations with the support of the British Overseas Trade Board during 1975. EEA-sponsored projects for UK based electronics companies will be on a world-wide basis. On the American continent groups will be organised to show at IEEE INTERCON in New York in April; The National Association of Broadcasters event, Las Vegas in April; SEMICON V, San Mateo in May and the WESCON Show, San Francisco in September. In late October there will be a group in Toronto attending the International Electrical-Electronic Conference and Exposition in October.

Other group participations are scheduled to be held at the Japan Electronics Show and Conference, Osaka in October;

in the same month a group will show at the Australian International Radio Electrical and Electronics event being held in Sydney in August. Nearer home, EEA will sponsor groups to Moscow Communications Exhibition, the Montreux TV event; both shows being held in May. In September another UK contingent will exhibit at MICROWAVE '75 due to take place in Hamburg. Further information can be obtained from The Electronic Engineering Association, Leicester House, 8 Leicester Street, London WC2H 7BN.

Troposcatter equipment for PO

Equipment has been ordered for two new radio stations to be set up near Peterhead in Aberdeenshire and on South Shetland to provide reliable high-quality world-wide communication for oil production platforms operating out of sight of land. The stations ordered from Marconi Communication Systems by the Post Office are expected to come into operation during October. The contract covers erection of 12 large dish aerials—four of 12m and two of 18m diameter near Peterhead and two of 12m and four of 18m diameter on South Shetland as well as the transmitters and receivers, switchgear and control equipment for operating a quadruple-diversity, space polarization system (see "Electronics in Oil" published in the January issue). The Frigg, Beryl, mid-pipeline and Piper platforms will act as "master" platforms in the North Sea network, providing communication for other platforms in their areas over microwave links.

The troposcatter links will operate in 1° beams between onshore aerials with a gain of 47dB and offshore aerials with a

41dB gain. At the distances to be bridged by the troposcatter links, the common volume or that part of the troposphere "visible" to the transmitting and receiving aerials, lies about 1km above sea level. Attenuation of the signal is about 210dB. Tropospheric turbulence varies almost continuously and the level of signal received is on average 130dB below 1W.


Miniature solid-state TV camera

A miniature solid-state television camera has been introduced which is the second in a planned series using charge-coupled device technology. The camera has a cylindrical body, three inches in diameter and just under two inches deep while the weight is 11 ounces. The usual, comparatively bulky Vidicon tube used in TV cameras has been replaced by a compact image-sensing device which contains 10,000 photosensors on a standard 24-pin dual-in-line integrated circuit unit.

Power consumption of the camera is 1.5 watts and it responds to illumination levels as low as two lux and is suitable for low-light applications such as night security and surveillance. Other applications include remotely piloted vehicles, space systems, periscopes and process control. Low geometrical distortion of the c.c.d. system allows its use in scientific measurement, medical instrumentation and microscopy.

The camera has a spectral response extending almost into the infrared range. It has a 100-line horizontal resolution and a bandwidth of 1MHz. Although a five-inch TV monitor adapted to the 123 frames per second c.c.d. camera sweep-rate is supplied as standard equip-

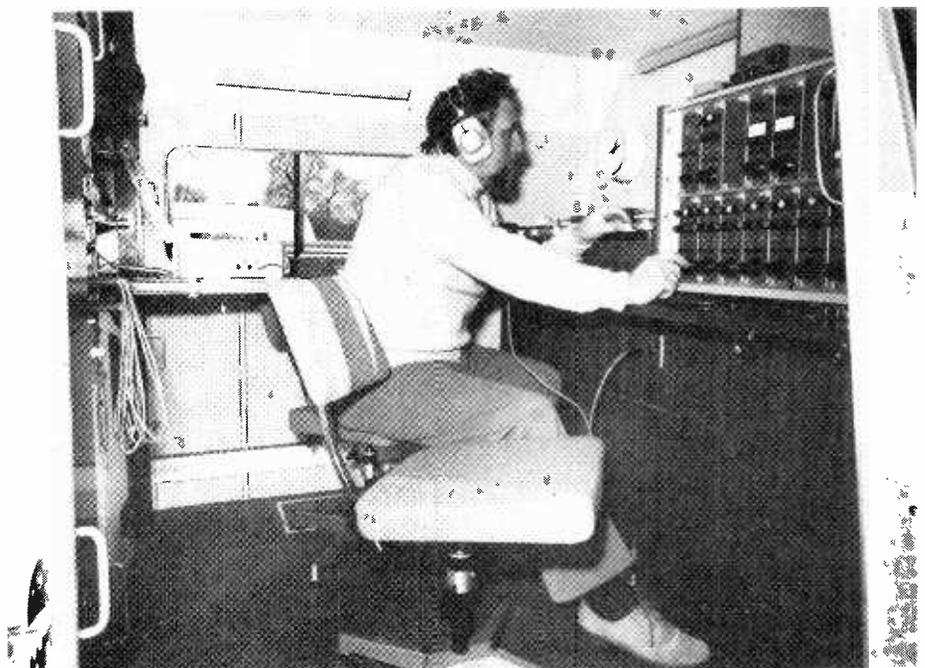Sound outside broadcast van during its test programme before shipment by Pye TVT to Sierra Leone. The vehicle is equipped with an eight-channel mixer, two transcription units, two tape-recorders, u.h.f. outside broadcast link, radiotelephone and is fully air-conditioned.



ment, the camera may be interfaced with any conventional monitor by a simple adjustment of the sweep-rate.

Operation is up to distances of 100 feet from the monitor and an optional battery pack is available when complete portability is required. The new camera is designated type MV101 and supersedes the MV100 which was introduced about 18 months ago by the Fairchild Camera and Instrument Corporation. (The MC100 was described in News of the Month, October 1973.)

Monitoring monitors

The US Electronic Industries Association announces the availability of two new standards for television monitors. They are RS-375-A, "Electrical Performance Standards for Direct View Monochrome Closed Circuit Television Monitors 525/60 Interlaced 2:1" and RS-412-A, "Electrical Performance Standards for Direct View High Resolution Monochrome Closed Circuit Television Monitors".

These new standards replace the earlier

versions, RS-375 and RS-412, which were the first developed by any standards organization relating to monochrome closed-circuit television monitors. They outline significant parameters describing the operation of closed-circuit monitors and also the minimum levels of performance desirable to develop an acceptable display. The standards will promote interchangeability of products from different manufacturers, thereby eliminating confusion on the level of performance that can be expected from an appropriately specified device. They will also assist the purchaser in selecting and obtaining the proper product for a particular need.

Electronics industry surveyed

The eighth edition of the annual statistical survey of the electronics industry* has been published by the Electronics Economic Development Committee. This charts the industry's progress in 1973 revealing that total sales reached over £2,600 million, a 12 per cent increase over 1972. After a brief pause in 1971/1972

the industry's expansion resumed but at a slower rate than before. Nevertheless it is clear that the industry's output has more than doubled since 1968.

The survey shows that the electronics industry's renewed growth was led by the components sector with an 18 per cent growth rate and the consumer goods sector with a 16 per cent rate.

While the industry re-established its pattern of growth in 1973, the home market underwent enormous expansion. The resulting trade deficit was £268 million, almost a four-fold deterioration over 1972. The largest deficits were in consumer goods (£219 million), active components (£68 million), and computers (£52 million). None of the sectors with positive trade balances improved their position although the instruments sector exported a slightly higher proportion of total sales.

*Available from Neddy Books, NEDO, Millbank Tower, Millbank, London SW1P 4QX, price £1.

New trade exhibition

The Board of the Association of Manufacturers of Domestic Electrical Appliances (AMDEA) and the Executive Council of the British Radio Equipment Manufacturers' Association (BREMA) have recently decided to sponsor a trade exhibition at the new National Exhibition Centre near Birmingham. The trade exhibition will open on Sunday May 23, 1976.

It will be organized as a single event, with separate exhibits for domestic electrical and electronic goods in adjacent halls with free access between the two areas. The BREMA section of the show will also be opened to the public for four days at its conclusion.


AMDEA's and BREMA's intention is to create a national electrical and electronic consumer goods trade show, of interest to retailers throughout the United Kingdom and which will also be of international standing to provide a world showcase for British goods.

AES Convention 1975

The fiftieth convention of the Audio Engineering Society will take place at the Cunard International Hotel, Hammer-smith, London W6, from Monday, March 3 to Friday, March 7, 1975. A comprehensive programme of technical papers on subjects connected with audio engineering and acoustics is being arranged. Anyone wishing to present a paper at the Convention should in the first instance submit an abstract of 200-250 words to: Dr J. M. Bowsher, Audio Engineering Society, Department of Physics, University of Surrey, Guildford, Surrey, England.

An exhibition of professional products will also be held at the Cunard International Hotel.

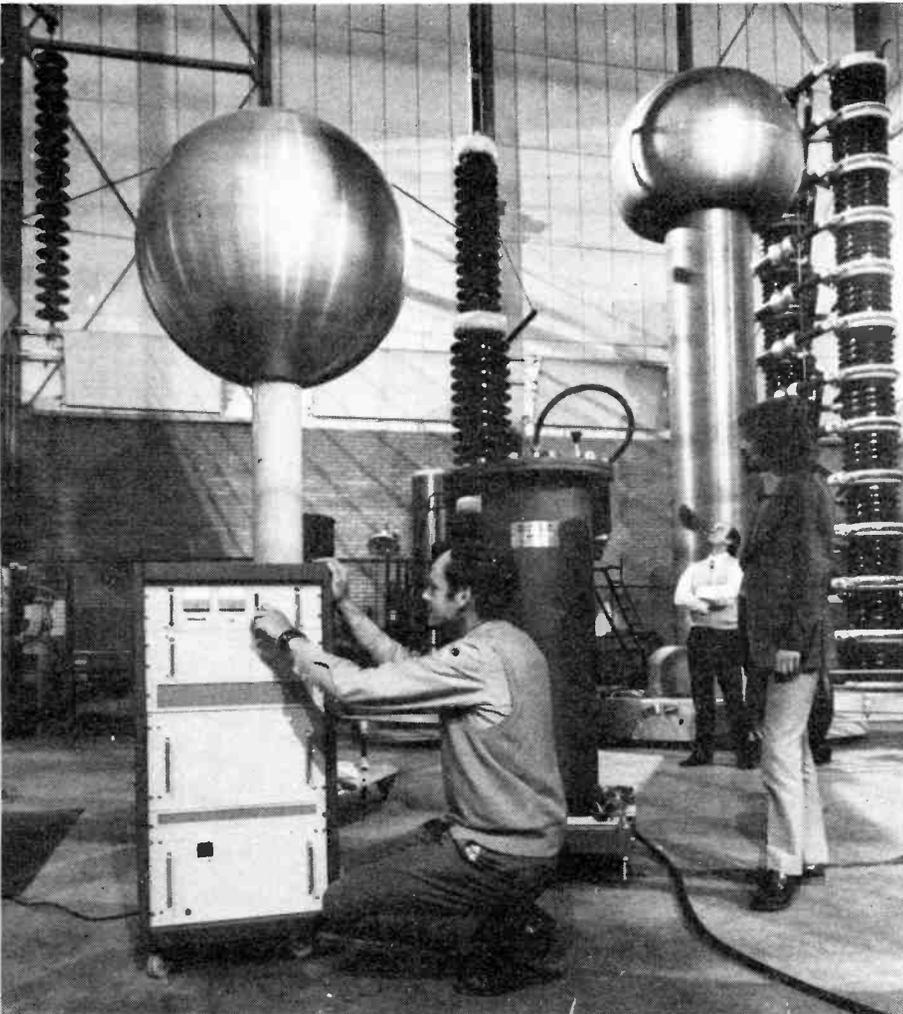Operating the control panel during a run of what is believed to be the first British all-solid-state precision 300kV d.c. power supply developed by Wallis Electronics. The high voltage assembly contains the r.f. power source and, in the tank, the voltage multiplier and feedback resistor chain. The high voltage output is available via a screened polythene cable.



Charge-coupled devices

3—Signal processing

by D. J. MacLennan

University of Edinburgh

Previous articles in this series have dealt with the basic operation of the c.c.d. as an analogue shift register (Dec., 1974) and the techniques for c.c.d. fabrication (Jan., 1975). This article outlines some of the primary considerations in designing c.c.d.s for signal processing, with some simple examples taken from the radar and communication fields. Comparisons with the alternatives to charge-coupled devices are made.

When charge is transferred from one capacitor or gate to the next, a small fraction of this charge is left behind under the previous gate. The result of this charge transfer inefficiency is a "smearing" or bandwidth reduction. This may be visualized by considering an impulse or a single "one" being applied to the input of the device. The output should ideally consist of one pulse. Due to the transfer not being complete, however, there will be trailing pulses which corrupt the output signal. The magnitude, and hence the degradation in the signal quality, is a function of the charge left behind at each transfer, or the transfer inefficiency. In simple mathematical terms^{1,2}, if we assume a fraction of charge ϵ is left behind, then the fraction of charge transferred is given by

$$\alpha = 1 - \epsilon$$

where α is known as the transfer efficiency, and ϵ the transfer inefficiency. Fig. 1, which shows the charge distribution within a single-phase, six-element c.c.d., demon-

strates the time sequence of charge packets at the output as

$$\alpha^6, 6\epsilon\alpha^5, 21\epsilon^2\alpha^4, \dots$$

As demonstrated by Vanstone² *et al*, this sequence is independent of the number of clock phases used, to a first approximation. The size of the trailing pulse relative to the required pulse is a function of both the inefficiency and the number of transfers.

Fig. 2 demonstrates the effect of inefficiency on both impulse and frequency response of a device. As can be seen, for $n\epsilon < 1$, the pulse immediately after the required signal is the largest residual, and its magnitude relative to the required signal is $n\epsilon$. The $n\epsilon$ product may thus be used as a criterion for device performance.

As an example, consider a device with $n\epsilon = 0.1$ used in a pulsed radar system. At the output there will be an echo of any return at a level of 20dB below the required signal, making it impossible to distinguish any target smaller than this within that range bin. For an application where pure analogue delay is required, the actual

bandwidth of the device is not only limited to half the sampling frequency by the Nyquist sampling criterion, but also by a factor depending on the $n\epsilon$ product, Fig. 2(b). It is thus obvious that an appropriate $n\epsilon$ product must be specified for

Clock phase		1	1	1	1	1	1	
Transfer element		1	2	3	4	5	6	Output
Discrete time	1							
	ϵ	α						
	ϵ^2	$2\epsilon\alpha$	α^2					
	ϵ^3	$3\epsilon^2\alpha$	$3\epsilon\alpha^2$	α^3				
	ϵ^4	$4\epsilon^3\alpha$	$6\epsilon^2\alpha^2$	$4\epsilon\alpha^3$	α^4			
	ϵ^5	$5\epsilon^4\alpha$	$10\epsilon^3\alpha^2$	$10\epsilon^2\alpha^3$	$5\epsilon\alpha^4$	α^5		
	ϵ^6	$6\epsilon^5\alpha$	$15\epsilon^4\alpha^2$	$20\epsilon^3\alpha^3$	$15\epsilon^2\alpha^4$	$6\epsilon\alpha^5$	α^6	
	ϵ^7	$7\epsilon^6\alpha$	$21\epsilon^5\alpha^2$	$35\epsilon^4\alpha^3$	$35\epsilon^3\alpha^4$	$21\epsilon^2\alpha^5$	$6\epsilon\alpha^6$	
	ϵ^8	$8\epsilon^7\alpha$	$28\epsilon^6\alpha^2$	$56\epsilon^5\alpha^3$	$70\epsilon^4\alpha^4$	$56\epsilon^3\alpha^5$	$21\epsilon^2\alpha^6$	

Fig. 1. Charge distribution within a six-element, single-phase c.c.d. when a single packet of charge is clocked from input to output.

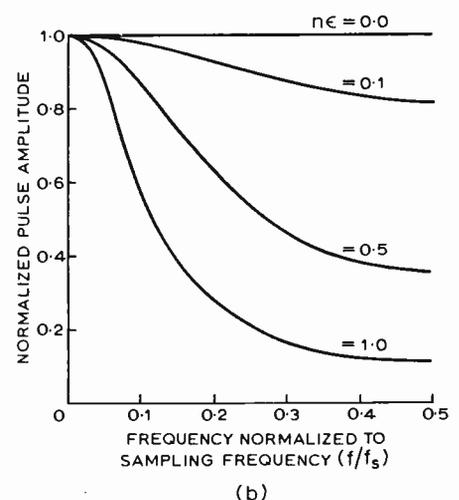
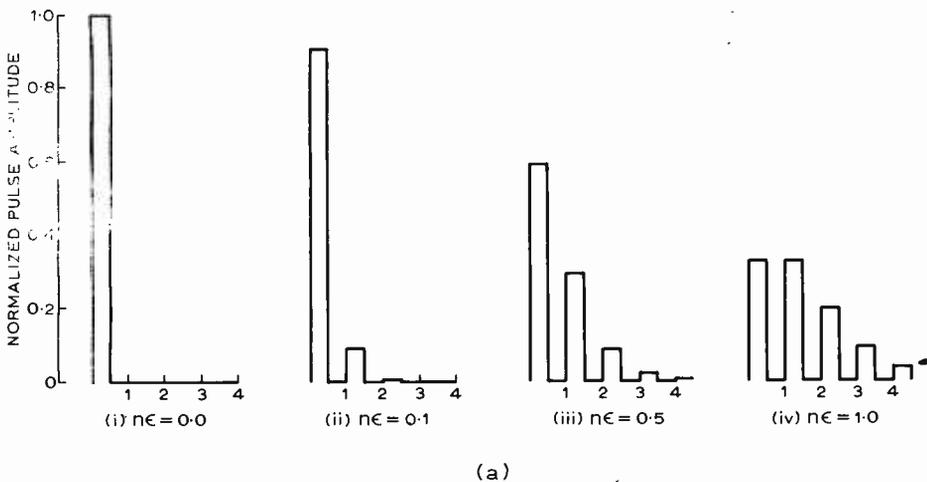


Fig. 2. Impulse response of a c.c.d. analogue delay line with varying $n\epsilon$ product (a). Frequency response modification for a c.c.d. analogue delay line with varying $n\epsilon$ product (b).

any given system application.

Transfer inefficiencies of the order of 10^{-5} have been obtained at frequencies of MHz and 10^{-4} at 125MHz. It should thus be possible to fabricate linear (meaning serial) devices with up to several thousand storage elements, which operate at several tens of MHz.

In addition to the incomplete transfer of charge, a small amount of charge is lost at each transfer due to recombination.

Device input

Several methods exist for putting charge into the c.c.d., each having its own advantages and disadvantages. All commonly-used techniques consist of a diode as a source of minority carriers (signal charge) and some form of gate structure, as in the m.o.s. transistor, to control the amount of charge, or the instant at which charge enters the c.c.d. register. A typical input structure for the linear injection of charge into a c.c.d. is shown in Fig. 3³. Operation of this input structure is as follows.

The input signal, V_{ig} , is applied to the input gate. When the first transfer electrode, ϕ_1 , is pulsed on the input diode is held at a voltage, V_{id} , which saturates the potential well under the first transfer electrode. The input diode voltage is then modified to empty the well. When the surface potential under the first electrode is equal to the surface potential below the input gate, no more charge will leave the well, thus setting the surface potential (and hence signal charge) under the transfer electrode to the potential under the input gate.

Signal detection

There are many methods for converting the signal charge stored in the c.c.d. to an

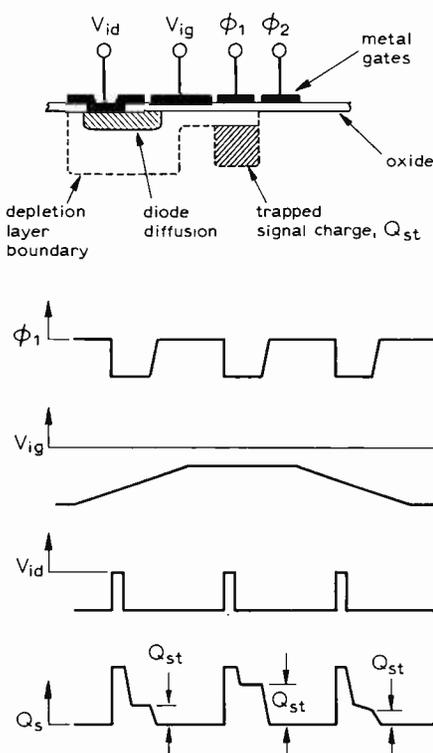


Fig. 3. Technique for the linear injection of charge into a c.c.d.

electrical signal. As for the input structure case, each technique has its own particular advantages and disadvantages. In this article it is intended to concentrate on three particular circuits. The first is in common use as an output circuit in the simple analogue delay type of applications. The second is for use in situations where multiple outputs with fixed weighting coefficients are required from the device, as in matched filtering applications. The third is similar to the previous method, but in this case the weighting coefficients are electrically programmable.

Floating diffusion reset. In this detection method⁴, a diode diffusion is reverse-biased by being charged to some appropriate potential, V_{gg} , through an m.o.s. transistor, Fig. 4.

Assuming negligible leakage current, the diode will remain at this potential when the charging transistor is switched off. If a charge signal is now clocked into the diffusion, at the end of the ϕ_3 pulse, the potential on the diode and sensing transistor will change due to the new charge distribution. This change may then be amplified by the sensing transistor. A reset pulse is then applied to the charging transistor prior to the arrival of the succeeding charge packet.

Split gate tapping. This technique for sensing the signal charge being clocked along a shift register is attributable to Buss⁵ *et al.* When charge is clocked under one of the split electrodes (Fig. 5), the current in each of the clock lines supplying this electrode is measured, i.e. I^+ and I^- ; output is proportional to the difference between the two. The magnitudes

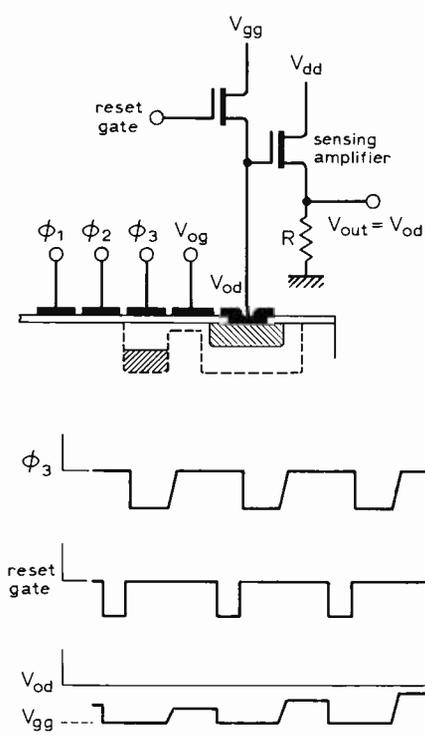


Fig. 4. Floating diffusion reset method of converting the charge present in a c.c.d. to an electrical signal.

of the currents are directly proportional to the quantity of signal charge present; the voltage on the gate is maintained constant and thus current must be supplied from the clock source to maintain charge equilibrium. The difference between the currents, for a given quantity of charge, is determined by the position of the split in the electrode. The smaller area "sees" a lesser portion of the signal than the larger area and as a result requires less current to maintain charge equilibrium.

A means has therefore been realized for not only sensing the signal charge present in the device but also for multiplying this signal by some fixed weighting coefficient. The usefulness of this technique is discussed later. One of the limitations is that the weighting coefficients cannot be modified subsequent to device fabrication. However, in situations where many identical filters are to be realized with fixed responses, this type of device is likely to be extremely useful.

Biased floating gate. This technique is basically similar in operation to the first technique, except that instead of charging a diffusion, a gate electrode is charged to an appropriate d.c. level, V_{gg} (Fig. 6).

When the preceding clock electrode, ϕ_1 , switches off, signal charge is injected into the depletion; well below the charged gate. The resultant redistribution of charge in the capacitive network results in a potential variation on the charged gate which may be sensed and amplified by an m.o.s. transistor. When the next clock electrode, ϕ_3 , is turned on, the gate potential reverts to its original potential. It is thus not necessary to reset the gate at every clock period. The signal charge is not destroyed or degraded, allowing other outputs to be taken at tapping points further along the register.

The moving target indicator

In many systems, it is required to monitor targets which are moving relative to the transmitter but may be surrounded by stationary objects. For this type of system it is necessary to eliminate the stationary clutter from the observer's display. To perform this a measurement of the phase changes due to Doppler shift in the frequency of the return signal in succeeding radar returns is required. It is therefore necessary to store one radar return, compare this with the succeeding return and subtract the two signals. Alternatively, in the frequency domain, it is necessary to build a notch filter which rejects frequencies of zero and multiples of the radar pulse repetition frequency. Both these methods of visualizing the problem are in fact identical and may be implemented as shown in Fig. 7⁷. Fig. 8 shows the performance of such a filter both in the time and frequency domain. The filter used was more complex than the simple schematic of Fig. 7—to obtain improved cancellation of clutter, steeper sides were required on the notch filter and this was achieved using three c.c.d. shift registers as delay elements in a three-pole Chebychev filter. The filled-in

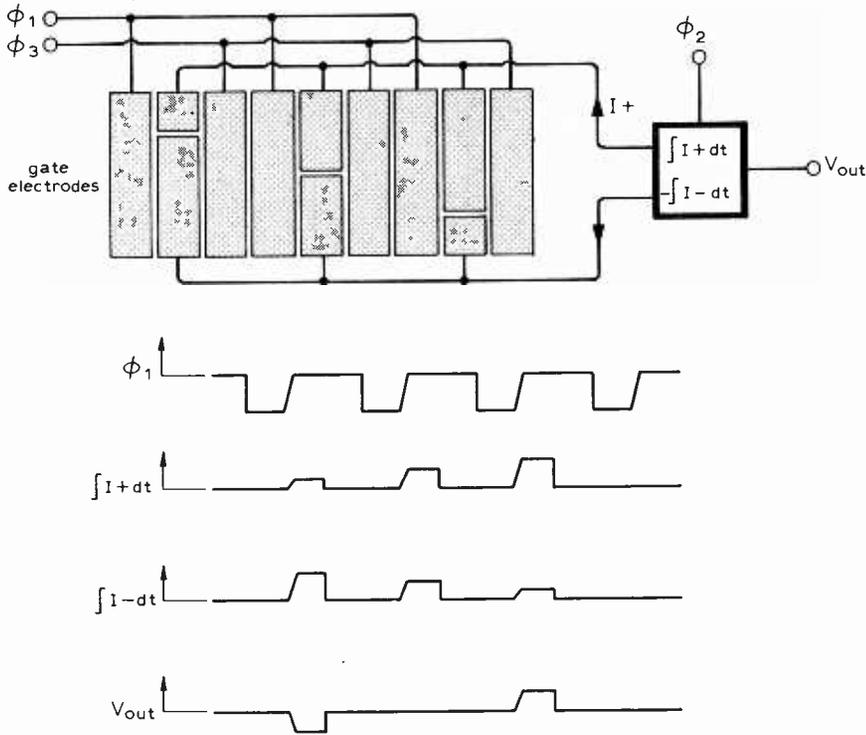


Fig. 5. Split-gate tapping technique for the fabrication of fixed weighting coefficient transversal filters.


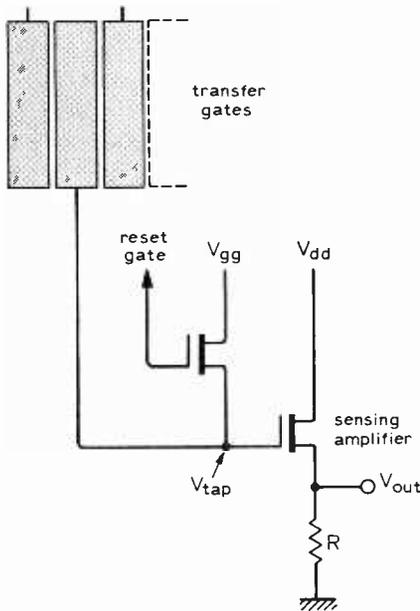


Fig. 6. Biased-gate tapping technique for the fabrication of transversal filters with electronically-variable weighting coefficients.

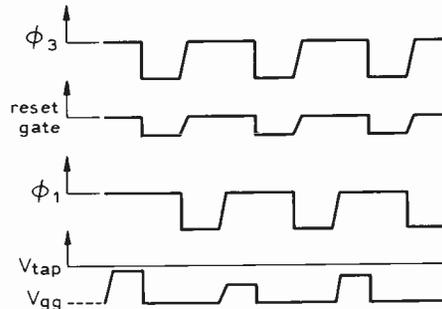

effect of the Doppler pulses on the simulated clutter cancellation photograph are due to many oscilloscope traces being photographed. As can be seen, the clutter has been effectively cancelled by the filter, there being >30dB of clutter rejection available.

Frequency filters

The filtering capabilities of a filter may be obtained by taking the Fourier transform of the time domain response, i.e. the response of the filter to an electrical impulse. It is thus possible, knowing the frequency response required of a filter, to define the necessary impulse response.

If we now consider a c.c.d. analogue delay line, constructed so that an output

may be taken at each bit without degrading the signal being clocked along the device, and connect each of the outputs as shown in Fig. 9, the response of this device to a charge impulse, will be the sequence of pulses

$$h_1, h_2, h_3, h_4, \dots, h_n.$$

This device is more commonly known as a transversal filter and by controlling the weighting coefficients at each tapping point, it is possible to fabricate a virtually infinite number of different filters. Unfortunately, the impulse responses to many desirable filters are of infinite duration and therefore have to be truncated in such a device—only a finite number of coefficients are available—resulting in

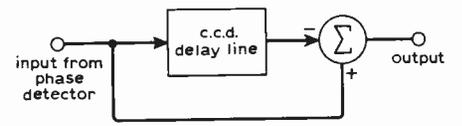


Fig. 7. Schematic diagram for the implementation of a m.t.i. filter.

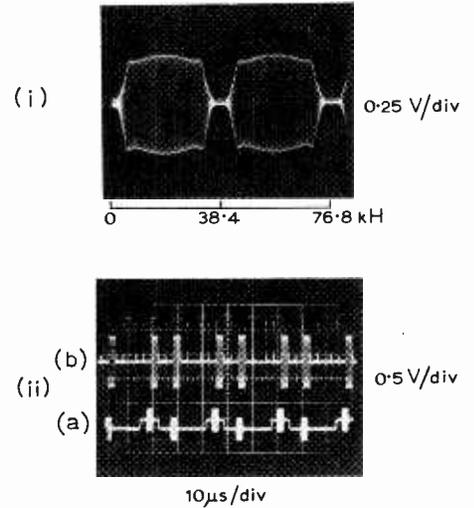


Fig. 8. Swept frequency response (i) and simulated clutter cancellation (ii) of a moving target indicator using c.c.ds. (Lower trace: filter input; upper trace: filter output.)

a non-ideal frequency response for the filter. In many cases, it is possible at the design stage to determine the impulse response required of any particular filter and ascertain the number of weighting coefficients necessary to specify the frequency response to any desired accuracy. Techniques are also available whereby the end weighting coefficients may be reduced to an insignificant level by speeding up the decay time of the impulse response.

This is not the only type of frequency filtering structure that may be realised using c.c.ds. The moving target indicator is an example of a recursive filter. In these types of filters the poles and zeros in the frequency domain response are determined by the weighting coefficients applied to the feedback loops used. In many situations, the loop feedback coefficients are critical to filter performance, leading to a requirement for extremely stable gain in the loop. Applications of c.c.ds in recursive filtering applications would at present appear to be limited and their use as transversal filters much more promising. The primary advantages in using a recursive filter rather than a transversal filter are that an infinite impulse response is achievable, because of the feedback, and a smaller number of delay elements is required using this technique. These advantages are at present offset by the need for highly stable on-chip amplification in a technology compatible with c.c.ds.

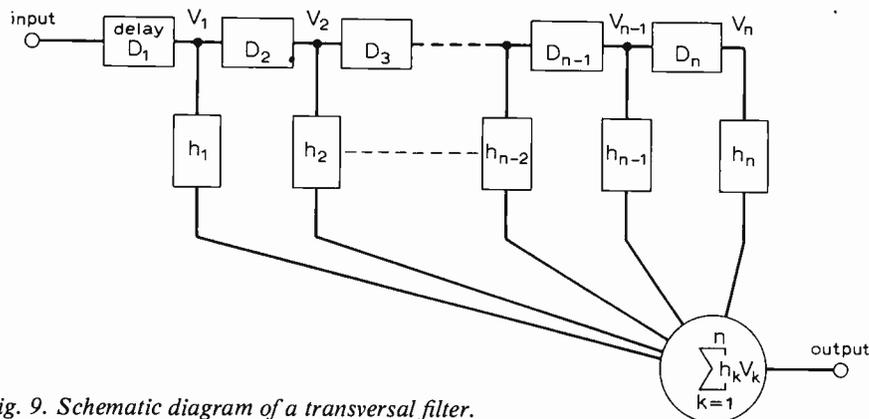


Fig. 9. Schematic diagram of a transversal filter.

Matched filtering

In matched filtering, a special case of transversal filtering, the signal is coded to increase its bandwidth by some predetermined amount prior to transmission. On reception the signal is decoded in a transversal filter which is matched to the coded waveform. As an example of matched filtering, consider the transmitted sequence as being

1,1,1,1,1,-1-1,1,1,-1,1,-1,1.

This sequence is commonly known as the 13-bit Barker code.

The impulse response of the filter which is matched to this waveform is the time reverse of the transmitted sequence, i.e. the weighting coefficients h_1 to h_{13} are given by the sequence

1,-1,1,-1,1,1,-1,-1,1,1,1,1,1.

Fig. 10 shows the effect of passing the received waveform into this filter. The output sequence is the autocorrelation function of a 13-bit Barker coded sequence

1,0,1,0,...0,13,0,1,...0,1.

One of the most important aspects of matched filtering is the improvement in signal-to-noise ratio obtained over conventional processing techniques.

Consider the filter described above with an input signal which includes white additive noise. The output noise power is the product of the number of taps (13) and the input noise power; the noise at each tap is summed. The output signal power however is proportional to output signal voltage squared. Hence the output signal to noise ratio has been improved by a factor of 13. Typical waveforms for this situation are shown in Fig. 11, where the received Barker sequence is totally immersed in noise. The output correlation peak from the c.c.d. matched filter can clearly be identified in the upper trace.

Charge-coupled or digital filters?

Some potential uses of charge-coupled devices have been discussed briefly in simplified terms. The fine detail of the design processes have been omitted in the interest of clarity and brevity.

It is essential at this stage to discuss the relevant advantages and disadvantages of the c.c.d. with respect to other techniques for performing such basic filtering functions as described in this article—the

simple lumped element filter, for example, along with some more exotic devices such as acoustic surface wave and digital filters.

The simple lumped filter is not discussed further due to its limitations with respect to critical alignment and bulk. Acoustic surface-wave devices have in the past few years created a visible impact on the radar and communications field at radio and

intermediate frequencies. The linear frequency-modulated matched filter has in particular been extremely successful in radar applications and a television i.f. filter has also been fabricated. However, at low frequencies and large time delays, acoustic surface-wave filters become impractical. Hence, at base-band, the c.c.d. has to compete with digital matched filters in cost, performance, power, weight, reliability and flexibility.

A comparison of the advantages relevant to the adoption of either c.c.d. or digital filters in system implementations is given in the following table:

Charge-coupled versus digital devices

CCD	Digital
Low cost	Flexible
Small size	Longer time delay possible
Low power	Proven technology
High reliability	
Standard m.o.s. production	

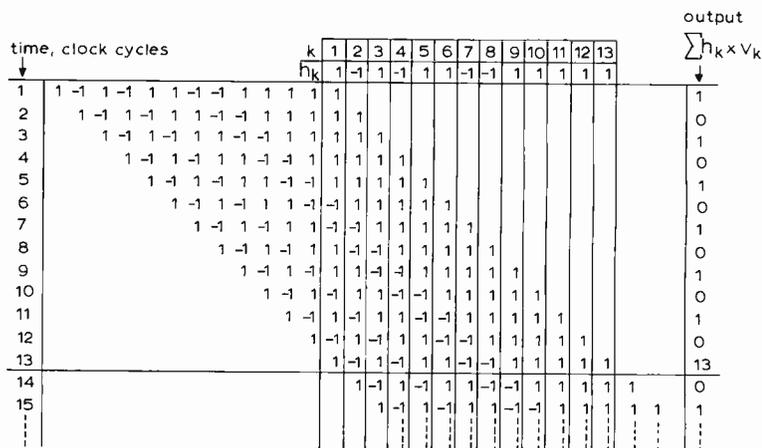


Fig. 10. Schematic of the operation of a matched filter when coded with a 13-bit Barker sequence. At clock cycle 1, the received sequence has just entered the matched filter. As the sequence progresses through the receiver filter, the auto-correlation function is output.

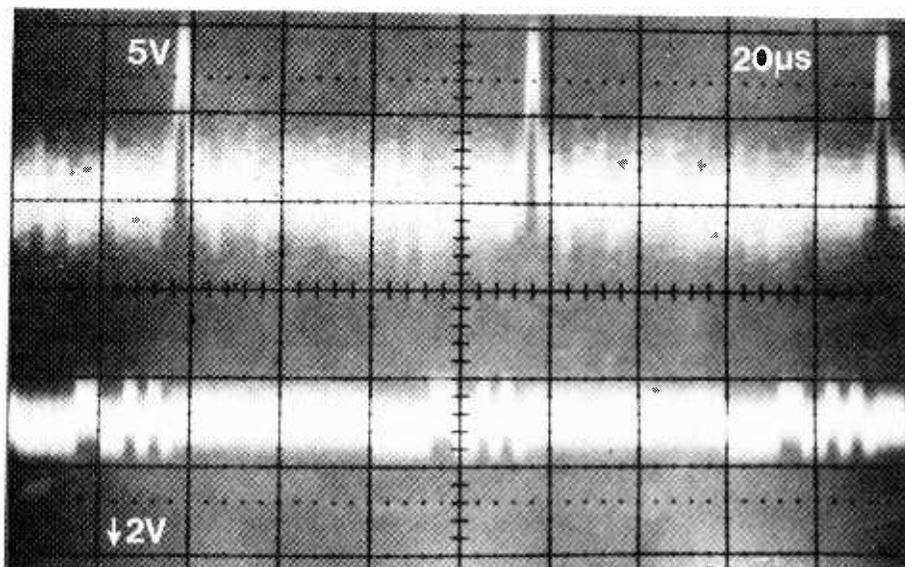


Fig. 11. Correlation of a 13-bit Barker sequence immersed in white additive noise. (Lower trace: input to c.c.d. matched filter; upper trace: filter output.)

Charge-coupled device performance

Sampling rate	≈ 10MHz
	> 100MHz with some techniques
Time delay	up to 1s
No. of storage elements	> 10^3 linear
	> 10^5 in array form
Transfer inefficiency	< 10^{-4} at 10MHz
Signal/noise ratio	> 70dB for a 256-bit linear device
Harmonic distortion	< -40dB
Time-bandwidth product	> 10^3

The potentially low cost of c.c.ds emphasized in this table is attributed to the inherently high level of integration obtainable. Elimination of analogue-to-digital and digital-to-analogue converters is one of the more obvious cost benefits along with a potential reduction in the number of packages required to implement a system.

Performance parameters for c.c.ds given above are typical of their present capabilities and the c.c.d. designer should be prepared to meet specifications within these capabilities.

The c.c.d. is an extremely high packing density, low power consumption, analogue shift register which is rapidly becoming accepted as an extremely useful device in many signal processing applications. In reasonable quantities, it is expected to be extremely cost effective. It can be considered as a means for realizing systems in other implementations. Commercial application potential in the signal processing field alone is enormous. Ability to produce lower cost, higher quality filters—both recursive and non-recursive—is of prime importance in the manufacture of modems. The c.c.d. can also potentially perform functions in the field of sonar similar to those performed by acoustic surface-wave devices in radar systems.

References

1. Joyce, W. B. and Bertram, W. J., *Bell Syst. Tech. J.*, vol. 50, 1971, p. 1741.
2. Vanstone, G. F., Roberts, J. B. G., and Long, A. E., *Solid-State Electronics*, vol. 17, 1974, p. 889.
3. Tompsett, M. F. CCD Applications Conference, San Diego, 1973, p. 147.
4. Kosonocky, W. F. and Carnes, J. E. *IEEE J. of Solid-State Circuits*, vol. SC-6, 1971, p. 314.
5. Buss, D. D., Collins, D. R., Bailey, W. H. and Reeves, C. R. *IEEE J. of Solid-State Circuits*, vol. SC-8, 1973.
6. MacLennan, D. J., Mavor, J., Vanstone, G. F. and Windle, D. J. *Elect. Lett.*, vol. 9, 1973, p. 610.
7. Bounden, J. E. and Tomlinson, M. J. *Elect. Lett.*, vol. 10, 1974, p. 89.

Letters to the Editor

QUAD BROADCASTING— AN ALTERNATIVE VIEW

With reference to the article by Messrs Carey and Sager on quadrasonic broadcasting (Nov. 1974 issue) I would like to discuss one or two of the points that were raised.

To say that the problem of quadrasonic broadcasting is where to put the third and fourth channels is to virtually ignore the many suggestions for matrixed quadrasonic systems (4-2-4) that only require two broadcast channels. In contrast broadcasters must give 4-2-4 systems very careful consideration as they might be able to provide a relatively inexpensive and more immediate answer to the problem. Not until it has been shown that all 4-2-4 systems are clearly incapable of providing both satisfactory quadrasonic and compatible stereophonic and monophonic reception, can such systems be cast aside in favour of the more technically difficult and expensive 4-3-4 and 4-4-4 systems.

Why are the 4-3-4 and 4-4-4 systems more difficult and expensive? In the first instance if the transmission occupies the same r.f. channel bandwidth and uses the same transmitter power then the overall signal-to-noise ratio for the listener is likely to suffer. While in the "fringe area" there might be a relatively slight loss of signal-to-noise ratio for the monophonic listener, the loss could be significant for the stereo listener and, in many cases, quadrasonic reception might not be worthwhile. The exact figures will depend on the system being broadcast, the mode of operation of the receiver (mono, stereo or quad), and the relative depth of modulation associated with each component of the composite signal. In this matter Carey and Sager's estimates may not be too far out.

On the other hand in the present circumstances, quadrasonic listeners might also be at risk from adjacent channel interference. Messrs Carey and Sager state that 4-3-4 and 4-4-4 systems "do not inhibit the optimum use of bandwidth by other stations". I agree that the addition of the second 38kHz channel or even

the 76kHz channel may not very greatly increase the maximum bandwidth occupied by the transmitted signal. However, this is not the whole story. For mono and stereo listeners with conventional receivers there would be an increase in the sensitivity to co- and adjacent-channel interference similar in magnitude to the decrease in signal-to-noise ratio, and largely for the same reason, viz. the reduction in the modulation depth of the components of the signal to which their receivers respond, and which has to be made to accommodate the additional quadrasonic information.

The corresponding increases in sensitivity to interference for the quad listener are less easy to predict but it is estimated that, relative to stereo reception of the existing pilot-tone system, quadrasonic reception of 4-3-4 would require about 6dB greater protection against co-channel and adjacent-channel interference at either 100kHz or 200kHz frequency spacing. With a 4-4-4 system, the increase in the required protection ratio against the adjacent channel could well amount to about 15dB. This particularly large penalty associated with the 4-4-4 system results not so much from the change in the transmitted signal spectrum as from the fact that the quadrasonic receiver is equipped with a 76kHz subcarrier detector. This produces an audible output from interference components in the range 61–91kHz to which a conventional stereo receiver does not respond.

The other technical difficulty which was unfortunately overlooked in the article is the problem of compatibility between the suggested new broadcast format and existing v.h.f. stereo receivers: in particular there is the problem of crosstalk between the two 38kHz subcarrier channels. In existing stereo receivers the phase accuracy of the regenerated 38kHz subcarrier determines the accuracy of eventual decoding but it is not very critical. If for example the phase error is 20°, this would introduce crosstalk between the left and right stereo channels at only -30dB, which is negligible in this context. If, however, the same receiver were used to receive stereo from a quadrasonic transmission using two quadrature 38kHz channels, the crosstalk between these for a phase error of 20° would be -9dB. The effect of this would depend on the design of the receiver. With an idealized square-wave-switching or synchronous-detector decoder the crosstalk would be substantially linear and the effect might be only a change in disposition of the audio images across the stereo sound stage; with many practical decoder circuits however the crosstalk could be appreciably distorted with rather more serious consequences.

With regard to cost, the susceptibility to noise and interference of the 4-3-4 and 4-4-4 systems implies that, with the present transmitter network, the stereo coverage of service areas could be prejudiced and, for quadrasonic, may be appreciably less than that required. A

substantial increase in transmitter powers could avoid the degradation caused by random noise but it would not solve the interference problem within the UK and could give rise to interference problems internationally.

These, then, are some of the reasons why a broadcasting organization may not readily share Carey and Sager's enthusiasm for the immediate adoption of a three or four channel solution to the quadrasonic broadcasting problem. If, however, further studies show that a 4-2-4 system cannot provide a sufficiently good quadrasonic service, whilst maintaining the present stereo and mono standards, then it may well be necessary to think again.

The other aspect of the article by Carey and Sager dealt with the possibility of a three-dimensional surround-sound system, i.e. quad plus height. Whilst it appears to be true that four suitable microphones arranged in a tetrahedral cluster can pick up and record the three dimensions of the original sound field, it is very doubtful whether four loudspeakers are sufficient to provide the wanted subjective result.


D. J. Meares,
BBC Research Department,
Tadworth,
Surrey.

USE OF LEDs AS PHOTO-CELLS

Light-emitting diodes made from gallium arsenide-phosphide or gallium phosphide have recently become available and are being made in very large numbers for sale at low prices. The question arises whether these devices can be used as photo-cells since they contain a semiconductor junction in an encapsulation designed to transmit visible light. It is not suggested that they are likely to perform better than properly designed cells; only that they may be more readily available to many readers.

Electrically the junctions have normal shaped diode characteristics but with forward conduction starting in the region of +2 volts, due to the wide energy-gap of the material, and reverse voltage limited to about -3 volts, since no special care is taken to prevent breakdown. The leakage current at this voltage, however, is extremely low provided the devices are kept dark. When light falls on them the leakage does indeed increase as expected, although the value must still be measured in nanoamps rather than milliamps.

The sensitivity varies considerably between different types of device, but every sample so far tested shows the effect to some extent. The diagram shows how two ordinary silicon transistors can be used as a simple Darlington pair to amplify the current and turn on a third transistor. Such an arrangement can be expected to switch tens of milliamps in the load with a threshold at about the normal indoor light level. The dark current of this sort of circuit is particularly low as the tran-

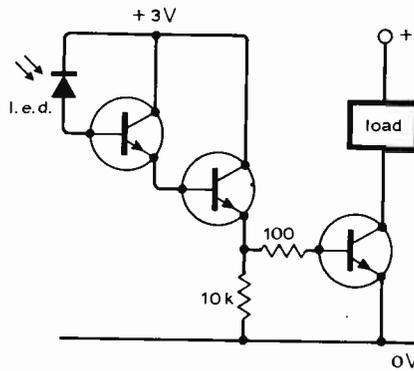

sistors lose gain at low currents, but the frequency response is poor as the stored charge can only be removed by internal recombination. There is no problem, though, in devising faster amplifier circuits, particularly if d.c. response is not required, and the inherent speed of the l.e.d. can be expected to be high.

The theory of energy levels tells us that the spectral response of the devices as photo-cells will be fairly broad and will lie on the high frequency (blue) side of the emission colour. If the normal emission process involves two or more quantum jumps in sequence, as I believe it does, then the absorption peak may be considerably more towards the blue than the emission. This leads to the idea that the major cause of the variations in the sensitivity between different types may perhaps be nothing more fundamental than the absorption characteristics of the dye which is put into the plastic lens to improve its appearance. There does seem to be some evidence that devices with paler plastic work better as photo-cells, and the manufacturers might perhaps consider this when selecting the mixture to be used in future designs.

K. C. Johnson,
Chedale,
Cheshire.

KEYPAD LAYOUT: TELEPHONES AND CALCULATORS

Mr Harold Barnard (Letters, December issue) is not justified in taking the Post Office or industry to task for the keypad layout of telephones.

Confusion is not likely to result from the co-existence of two different layouts. The great majority of telephone users are not, and never likely to be, users of calculators in close proximity to a telephone. For those who are, the British Post Office foresaw a potential clash between the requirements for the two devices before either keypad layout had become standardized. In consequence, the Post Office sponsored a research project at the Medical Research Council's Applied Psychology Unit at Cambridge.

The results (available in 1966 and confirmed by a further study carried out independently by the same body in 1968) provided significant evidence in favour of the

present telephone keypad layout. They showed that although there was little to choose between one arrangement and another in respect of keying speed, there was a statistically significant advantage in keying accuracy from the version in present use—even when users had already been conditioned to some other layout (such as the calculator layout standardized by ISO in 1967).

A standard layout for telephone keypads throughout the world is clearly desirable because of the growing volume of international travel. The International Telegraph and Telephone Consultative Committee recommended the current layout (which was already in use in America and due for early introduction in Japan and Latin America) and the British Post Office observes this international agreement.

R. E. Abbiss,
Director, Public Relations,
Post Office,
London, W1.

OPTICALLY COUPLED VFO

I was most interested in A. K. Langford's article in the November issue, "Optically coupled v.f.o.". What a perfect way to isolate a v.f.o., and a fairly cheap one at that! I was, however, a little unhappy about the idea of using the 5082-4350 optical isolator at 5MHz and above. There are two basic modes which the output transistor of the isolator can operate in: common collector, as used by Mr Langford, and common emitter. The former is only really suitable for low-frequency operation, and the response of the isolator in this mode effectively drops to zero by 3MHz, according to the spec. It is very likely that most devices will be comfortably within this spec., and will be usable at 5MHz, but it is not good design practice to assume this.

The common emitter mode, on the other hand, gives a usable response in excess of 10MHz with the same load resistor (470 ohms). So, I suggest the 470-ohm pot. is transferred to the collector circuit, and the emitter grounded. Assuming the gain and bandwidth of the output amplifier is sufficient, I see no reason why the circuit should not be used up to 15MHz reliably. Mr Langford does mention the common emitter mode, but in using the common collector mode, which offers no advantage in this circuit, he does not seem to have allowed for worst-case conditions.

Apart from that minor detail, I like it!
Richard Sterry, G4BLT,
Reading,
Berks.

Mr Langford replies:

I appreciate Mr Sterry's concern over the configuration of the isolator output transistor that was used in my final design. There were two reasons for choosing the common collector mode. First, the output

using the "high frequency" common emitter configuration offers no advantage when working into the low impedance broadband amplifier, and at 5MHz the output is actually less than that obtained using the "phototransistor" mode, with a crossover point at about 2MHz. Secondly, the high output impedance at the collector made matching into the broadband amplifier difficult, and susceptible to stray pick-up unless the connection was very short. Using the low output impedance of the common collector configuration eliminated this problem; which is very important if good isolation is to be achieved without having to contend with a critical layout.

However, as mentioned in the article, with a tuned circuit in the collector of the optically coupled isolator the useful output can be extended well beyond 5.5MHz.

FRONT PANEL LETTERING

For "one-off" jobs, the production of a nicely-lettered front panel is a considerable problem. One solution is the use of transparencies of the kind that are used on so-called overhead projectors in classrooms.

The transparency is made from a pencil drawing of the front panel lettering by passing this drawing and transparency film through a special heater. (One example is the 3M "Thermofax" machine.) The transparency may then be sandwiched between a thin, clear Plexiglass sheet and the metal front panel of the equipment. The Plexiglass sheet is retained on the panel by the potentiometer and switch fixing nuts.

The advantages of the process, provided one has access to a suitable machine, are: the front panel layout may be done in pencil; the layout may be easily revised; and special symbols and lines may easily be incorporated.

P. Hiscocks,
Ryerson Polytechnical Institute,
Toronto,
Canada.

SUICIDE SOLDERING

Our company has been soldering m.o.s. transistors and i.c.s with great success for some time now.

Mr Jack's letter in the November issue is of course rather worrying to us, as we too don't want to kill ourselves to protect our i.c.s, and we would like to know more of the precise nature of the hazard.

We use the earthed terminal on our oscilloscope or power supply as a convenient point to discharge any static electricity. Is this dangerous, and is the hazard still present if the equipment is used in normal circumstances?

Also, during cold weather some of our operators seat themselves on an ordinary domestic convector heater, to centrally heat themselves while working at the

bench. Apart from any medical side effects, is this practice electrically dangerous?

D. M. Parkins,
Greenbank Electronics,
Bebington,
Cheshire.

ELECTRONIC MUSIC JOURNAL

Interest in electronic music has grown and because of my wide experience in the medium—both theoretical and practical—I am starting a new journal entitled *Analog Sounds*.

Wireless World has been a great stimulus to me in the development of my own creative work with the electronic medium. To help spread the word, I intend including with each issue of *Analog Sounds* a cumulative directory of relevant articles published in electronic magazines including yours. This directory will take the form of a subject index with abstracts. *Analog Sounds* is a quarterly journal, depending solely on readers for support.

Jacob Meyerowitz,
Editor, *Analog Sounds*,
New York, U.S.A.

VARIABLE FREQUENCY DIVISION

I must congratulate Mr Winn of Racal Communications for his excellent article on the RA1772 synthesized communications receiver (October 1974).


In his discussion of the limitations of synthesizers, Mr Winn says that the present "state of the art" of digital integrated circuits makes it impossible to use variable frequency division at frequencies above 50MHz.

However, by using a two-modulus e.c.l. prescaler—say, the Plessey Semiconductors SP8645—in conjunction with t.t.l. programmable dividers, it is practical to directly synthesize from frequencies up to 500MHz.

The basic two modulus prescaler ($\div 10/11$), is usually combined with other e.c.l. counters to generate ratios of 20/21, 40/41 or 80/81—depending on the channel spacing required in the complete synthesizer. A typical scheme is shown below.

The total division ratio shown is:

$$N_{T,T} = P \cdot N + A$$

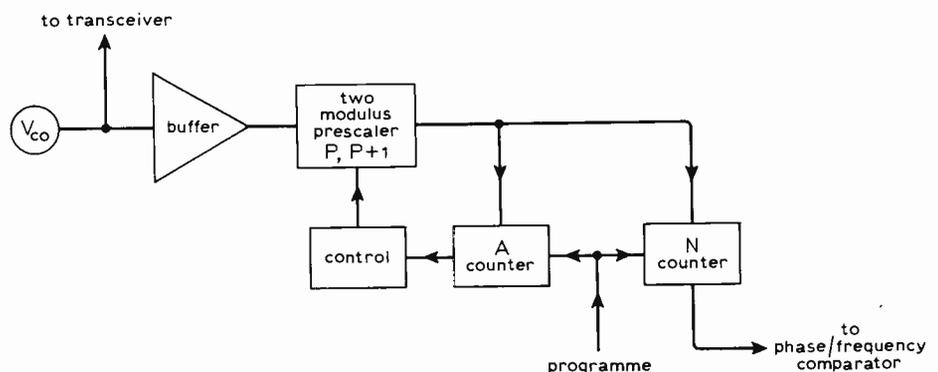

The only restriction is that A is less than N . If for any reason A must be greater than N , then a three-modulus counter, i.e. $\div 40/41/42$, can be used, thus halving the A count.

P. E. Battrick,
Plessey Semiconductors,
Swindon, Wilts:

Mr Winn replies:

It is agreed that recent developments have allowed an increase in the frequency at which variable division can take place, particularly by using the latest Plessey e.c.l. devices. As a small point, I did not state "impossible to use variable division above 50MHz" but that we divide directly from 50MHz and use a prescaler for higher output frequencies. It might still be preferable to do this since a hazard to be avoided in any digital-divider, phase-lock loop system is phase jitter. We find that a synchronous divider is essential to minimise the resulting noise sidebands produced by the division process as is also the need to restrict the division ratio of the final output loop as far as practicable.

ELECTRICITY AND MAGNETISM

The articles by "Cathode Ray" concerning fundamentals of electricity and magnetism (September, October) reminded me of a principle, if indeed it be a principle, that I deduced from purely practical considerations as an engineering student.

The principle is, briefly, that when one is wholly immersed together with one's instruments in a magnetic field (such as Mr O in the article) it is not possible to determine one's velocity through the magnetic field, even if its strength be known, by measuring an *e.m.f.* generated by a flux cutting conductor.

I should be most interested to know if "Cathode Ray" or your readers believe this crypto relativistic principle to be true, novel, or obvious.

C. P. J. Meade,
London, S.W.15.

"Cathode Ray" replies:

I am on record (in the September issue, p.348) as saying that observer O', moving in a magnetic field, finds also an electric field proportional to the magnetic flux density and his velocity. I discreetly refrained from explaining the means by


which he could find this. There is no doubt that he would be *subject to* an electric field caused by his motion through the magnetic field. Besides what the theory books say to this effect, there is a practical liquid flow meter which relies on precisely this principle. But the field is measured by a voltmeter that is *not* moving with the liquid. The observer O' , moving along with the liquid, could measure his velocity through the magnetic field by reading this meter as he went past it. Because of the relative velocity between himself and the meter there would be a relativistic correction. Our comparison of the observations of O and O' did indeed lead to the necessity for such a factor, β .

I cannot offhand think of any instruments that O' could take with him which would disclose his velocity through the magnetic field. Connecting a voltmeter to the ends of his conductor would form a closed loop embracing a constant magnetic flux, so there would be no reading. Whether this case could be extended to a general proof of Mr Meade's theorem I cannot say. Intuitively I feel it is true; I have no information on whether it is novel; and the last question reminds me of the story of the professor who, after saying that a certain statement was obvious, stopped abruptly, retired to his room for deep thought, and an hour later emerged to announce triumphantly to the by now empty lecture room "Yes, gentlemen, it is obvious".

SERIES AND PARALLEL FEEDBACK

Some time ago a debate was going on in your "Letters" columns about the virtues of parallel feedback as compared with series feedback. On that occasion Mr Linsley Hood stated that the distortion with operational amplifiers in the series-feedback mode was higher due to common-mode failure. Recently I have been able to verify his statement, although the distortion figures obtained were rather lower than those measured by Mr Linsley Hood. A Weston CD100 precision oscillator was used as a signal source. The output of this generator was filtered with a twin-T filter to suppress the last traces of the harmonic to be measured. The output of the test amplifiers was kept at 2V r.m.s. Twin-T and active notch filters were used to suppress the fundamental while harmonics were measured separately using synchronous detection methods.

With this test set-up it proved impossible to measure the distortion of the op-amps, connected as $-3\times$ amplifiers by parallel feedback, below 8kHz. Open-loop differential mode measurement yielded more useful results and from these distortion figures for the parallel-feedback connection were computed. They agreed well with the measured figures about 8kHz. The series-feedback connection, set for a gain of $+3$, produced harmonics that were readily measurable. Almost identical results were obtained from open-loop measurements

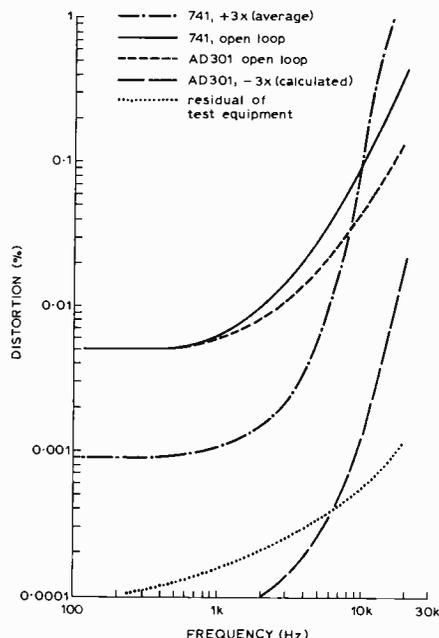

with common-mode signals of equal amplitude, proving Mr Linsley Hood's point about common-mode failure. It turned out that results varied widely between specimens, the best of the 20 op-amps tested producing about 0.001% at 2V output and the worst about 0.1%, when measured with series feedback at 8kHz ($A_v=3$). From this one can conclude that it is wise to avoid series feedback at gains of less than, say, $10\times$ when using these operational amplifiers in low-distortion circuits.

Unfortunately, the "error take-off" method of distortion reduction, as described by Mr Sandman in your October issue, suffers from the same drawback as the series-feedback arrangement, as can be seen in Mr Sandman's Fig. 2. Here the full input signal is present at the inputs of A_2 as a common-mode signal. Particularly when the circuit is set for a low gain, this can easily lead to an increase in distortion rather than a decrease. Incidentally, the "error take-off" method has been known for some time now as "feed-forward control". It has been thoroughly investigated at Delft University of Technology, where a more elegant circuit was devised that avoids the "floating" load, while preserving the advantages of feed-forward control.

T. Magchielse,
Almelo,
Netherlands.

Editor's note: Mr Linsley Hood asks us to state that his earlier figures were for a 1k Ω load, whereas those of Mr Magchielse could well be for a much higher output load (possibly the input impedance of his measurement equipment) and i.c.s, like most other similar amplifiers, give a lower distortion into a higher load impedance.

Mr Sandman replies:

Unfortunately Mr Magchielse has misunderstood the functioning of both the error take-off and Delft University circuits! A_2 in my Fig. 2 handles only a small signal and distorts only the distortion which is only a small effect and the Delft circuit

offends against the principle of "non-interaction" and as its A_1 has no negative feedback that of "rigidity of interconnection" as well.

ACTIVE CROSSOVER NETWORKS

As a designer of p.a. systems using active crossover networks, I was very interested to read the article by D. C. Read in your November, 1974, issue. However, I feel that readers may be confused by the graphs for the B110 unit in Fig. 1, and in particular by the conclusions drawn from them.

The graphs are obviously drawn for the free field responses, and predominantly show the effect not of internal cabinet volume, but of external cabinet dimensions. In fact the sound power output response for this unit is *improved* by the smaller cabinet, the 0.33cu. ft enclosure being near the optimum for the B110, the enclosure Q being just under 1 at around 75Hz, giving a response flat down to around 80Hz and dropping at 12dB/octave below this. Response curves for small speakers such as this should always be taken under the same conditions as their normal use, in this case almost certainly up against a wall, corresponding roughly to half-space conditions. Under these conditions the B110 will show a flat response up to around 600Hz, rising after this up to about 2kHz, where it levels out again. This unit should not be used on bass signals in as large a cabinet as 1cu. ft, as there will be almost no stiffness control over the low-frequency cone excursions.

A worthwhile improvement with these small enclosures is to provide, electronically, deliberate cross-talk between stereo channels below about 150Hz, thus cutting down considerably on cone excursions with bass signals predominantly in one channel or the other, unfortunately quite common with modern recording techniques. To the best of my knowledge, the first company to do this commercially was Servo-Sound.

K. C. Gale,
Poole,
Dorset.

THE STRIP IN BANK NOTES

A year or so ago, we were warned that spurious £5 and £1 notes were in circulation. I had a chance to examine some of these and one thing they all lacked was the metal strip. Surely (I thought) one of the metal detector circuits in the cashier's desk is all that is required. Then out of curiosity I tried to measure the resistance of the metal strip. It was infinity!

Question: what is the metal strip in a note made of?

A. Sproxtton,
Home Radio (Components) Ltd.,
Mitcham, Surrey.

Solid-state digital clock

1—Design

by David C. Clegg

With the increase in the number of educational programmes on both radio and television, the Open University programmes for example, many now have to be broadcast at both unsocial, and very often, inconvenient times. While there is no substitute for watching or listening to the programme live, the next best thing is to record* it. This requires some sort of time switch which must be both accurate and reliable, which implies that the time switch should be independent of the mains electricity supply. It was to solve this, and other similar problems, that the digital clock described in this article was designed.

The priorities which were considered when designing this clock are as follows:
Accuracy. Three frequency references were thought to be practical in this application; the mains 50Hz, an electronically maintained tuning fork, and a quartz crystal oscillator. The mains was rejected because it limits the uses to which the

clock can be put (it is no longer portable in the true sense of the word) and the stability (short term) and reliability of the mains leaves a lot to be desired, especially at the present time. A maintained tuning fork was rejected because of its high cost compared to the quartz crystal, which was finally adopted as the frequency reference. A good compromise between stability, size and power consumption was

obtained by using a frequency of about 200kHz with a c.m.o.s. maintaining amplifier and divider stages. Using an unovened crystal (frequency 204.8kHz) a stability of about one second per week was obtained.

Power consumption. The clock uses an l.e.d. display which does not result in low power consumption. Two supplies are, therefore, used: a main 12-volt supply and

*Subject to copyright regulations.

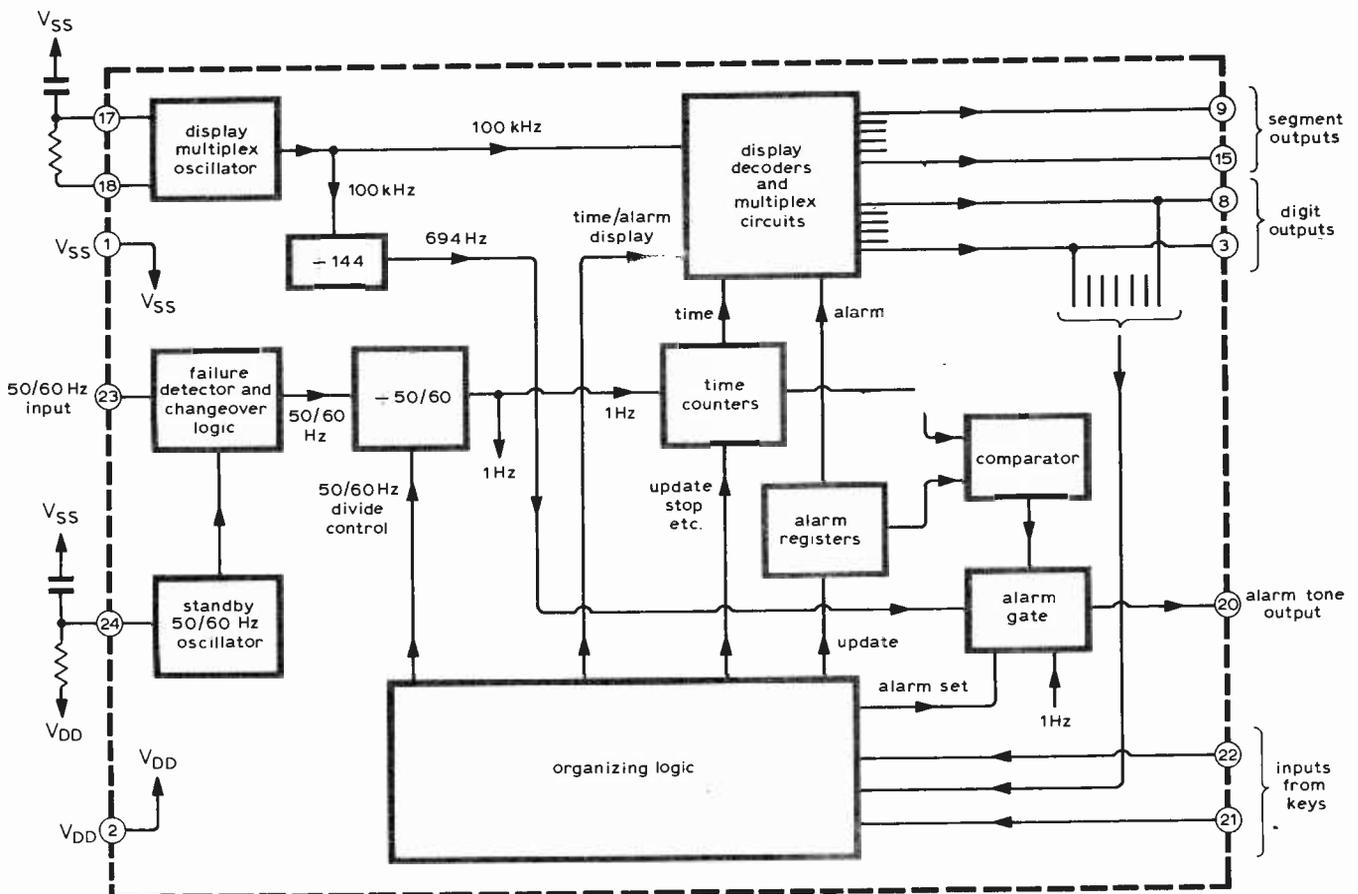


Fig. 1. Block diagram of the digital clock logic.

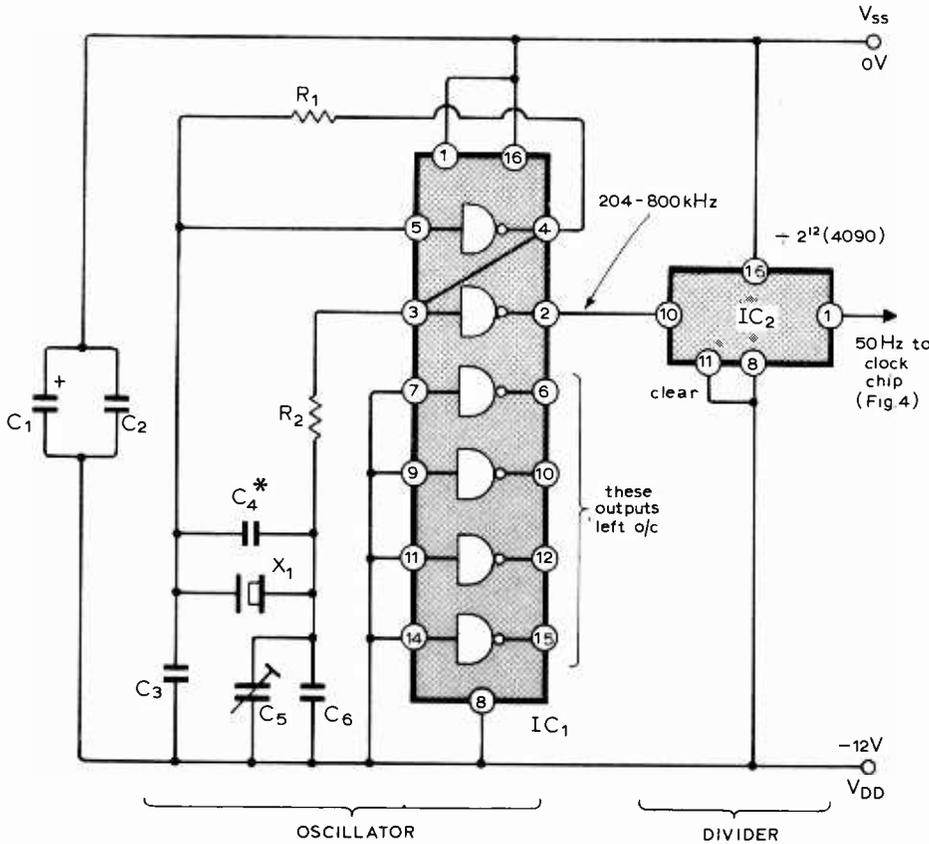


Fig. 2. Crystal oscillator and frequency divider. (For note on asterisked C_4 see next month.)

a standby 9-volt supply. The standby supply may consist of either nickel-cadmium re-chargeable cells or a dry battery. When the 12-volt supply is present, both the clock logic and the display are powered and if the standby cells are nickel-cadmium, these will be trickle charged. Under these conditions the current is a maximum of 120mA; i.e., a power consumption of 1.44W.

When the 12V supply is absent, the display is not powered and the standby supply powers the logic (and the crystal oscillator). Under these conditions the current is 8mA; i.e., a power consumption of 72mW.

A key is provided to enable the time to be read under standby conditions. Use of this key should be kept to a minimum since the current from the 9V supply rises to over 80mA.

Size. The overall dimensions of the printed circuit board are 6.75in \times 4.5in \times 1in. All the operator controls are push-buttons arranged as a 3 \times 4 keyboard. In the author's prototype the standby power supply consisted of nickel-cadmium cells and was mounted, together with the alarm speaker, in a perspex block under the p.c. board.

Circuit design

The clock was designed around the Mostek MK-5017-AA p.m.o.s.-l.s.i. integrated circuit, which contains all the logic required for a digital alarm clock. A block diagram is shown in Fig. 1.

The input to the chip may be either 50 or 60Hz, this being selected by the organizing logic. There is also a built-in relaxation oscillator which will generate a 50/60Hz waveform to keep the clock going in the event of failure of the external 50/60Hz. The frequency determining components for this oscillator are connected to pin 24. The stability is very poor, being dependent, both on temperature, and supply voltage.

In order to minimize the number of pins required on the package, the display is multiplexed. To further reduce the pin count, there are only two control inputs, but a matrix of diodes is formed with the two control inputs and four of the digit scanning outputs, making it possible to input the nine required control signals through these inputs. The frequency determining components for the display multiplex oscillator are external to the chip and consist of a resistor and capacitor chosen to give a frequency of 100kHz. This frequency is also divided by 144 to provide the alarm tone of 694Hz.

If the alarm has been enabled, pin 20 outputs the 694Hz alarm tone, interrupted at 1Hz intervals when the time counters and the contents of the alarm register agree.

Two additional facilities, which are not used in this design, are provided by the MK-5017-AA chip. Operation in the 12-hour mode is achieved by omitting diode D_9 ; an a.m./p.m. indication is available at pin 16, logic 1 (V_{ss}) indicating a.m. A 1Hz output is available at pin 19.

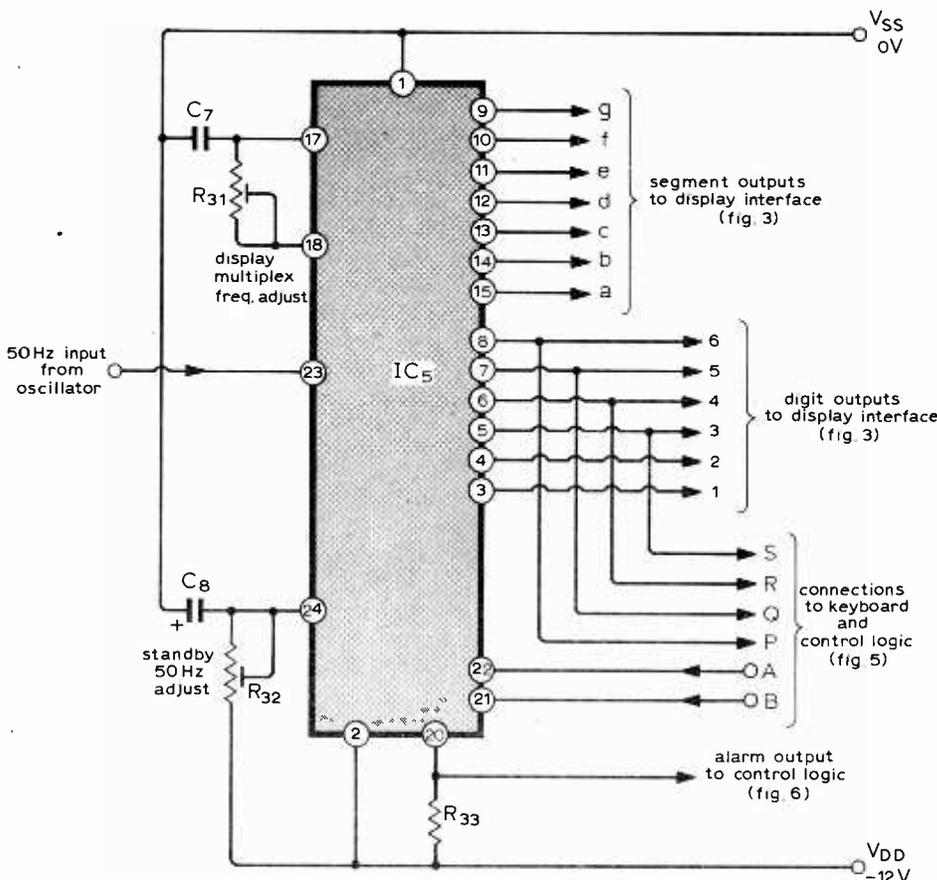


Fig. 4. The clock chip with its associated presets and outputs.

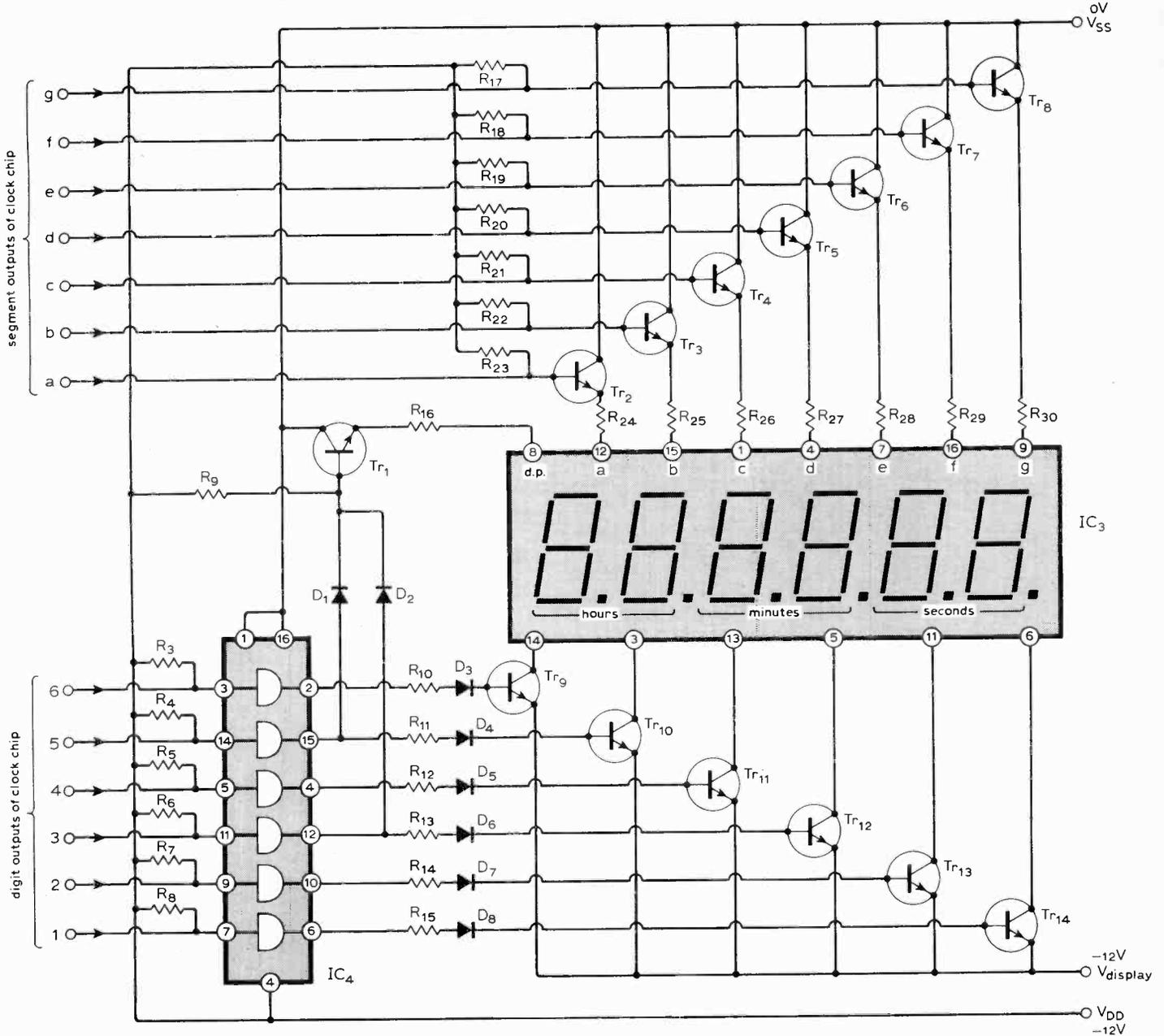


Fig. 3. Interface to enable the p.m.o.s. chip to drive the l.e.d. display.

Crystal oscillator. In order to minimize power consumption of the oscillator, shown in Fig. 2, it was decided to use both c.m.o.s. maintaining amplifier and a c.m.o.s. divider to provide the 50Hz required by the MK-5017-AA. At the time of designing this clock, there were no c.m.o.s. dividers capable of dividing by an integral power of 10—the next best thing was the RCA CD4040 which contains 12 binary dividers. Whilst it would have been possible, by the addition of external gating, to make the CD4040 divide by an integral power of 10, it was decided to use this device as a divide by 4096 and to choose a suitable crystal frequency. Since the MK-5017-AA can accept either 50 or 60Hz, there are two possible crystal frequencies to choose from: $50 \times 4096 = 204.800\text{kHz}$, or $60 \times 4096 = 245.760\text{kHz}$. The only reason for choosing the former

was that it is a “simpler” frequency. The cost of having a crystal manufactured to the design frequency of 204.800kHz is very little more than that of purchasing a crystal of, for example, 200kHz.

The crystal is not mounted in an oven because of the considerable power requirements. While the external supply could power a suitable oven, the drain on the standby supply would be unacceptable; not to power the oven under standby conditions would cause an unacceptable frequency shift. The crystal is cut for operation at room temperature (20°C) and provided the clock is used in an environment of reasonably constant temperature it will maintain a stability of one second per week.

The maintaining amplifier is a c.m.o.s. inverter biased into its linear mode by a 10MΩ feedback resistor. For a more com-

plete description of the design of such an oscillator, readers are referred to RCA application note ICAN-6539.

Display interface. The MK-5017-AA chip is not capable of driving an l.e.d. display directly, so the interface shown in Fig. 3 must be provided. The segment interface circuits consist of emitter followers with current defining resistors in the emitters.

The digit outputs from the clock chip are also used to scan the control logic and to preserve the logic levels, the digit outputs being buffered by IC₄. Diodes D₃ to D₈ are to protect the base/emitter junctions of the digit drive transistors from reverse breakdown when the display supply is removed. D₁, D₂ and Tr₁ illuminate the decimal points between the hours and minutes and between the minutes and seconds.

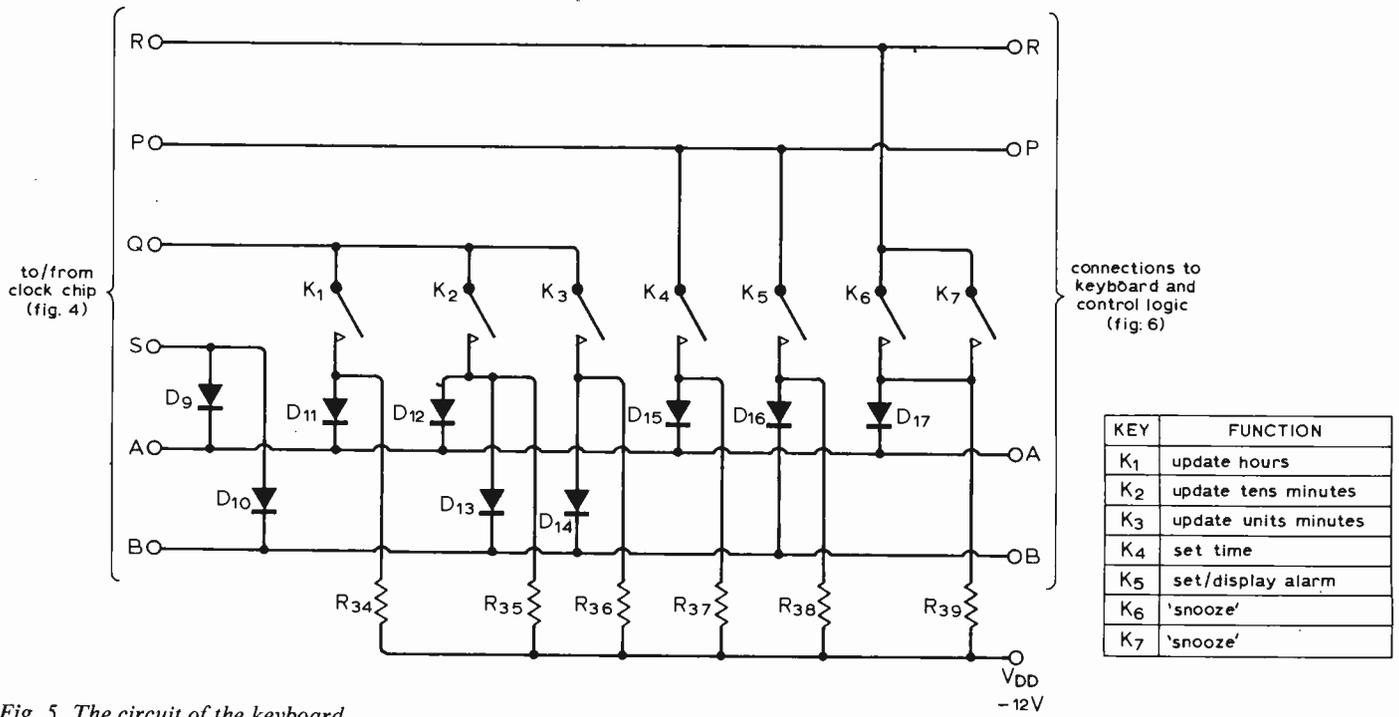


Fig. 5. The circuit of the keyboard.

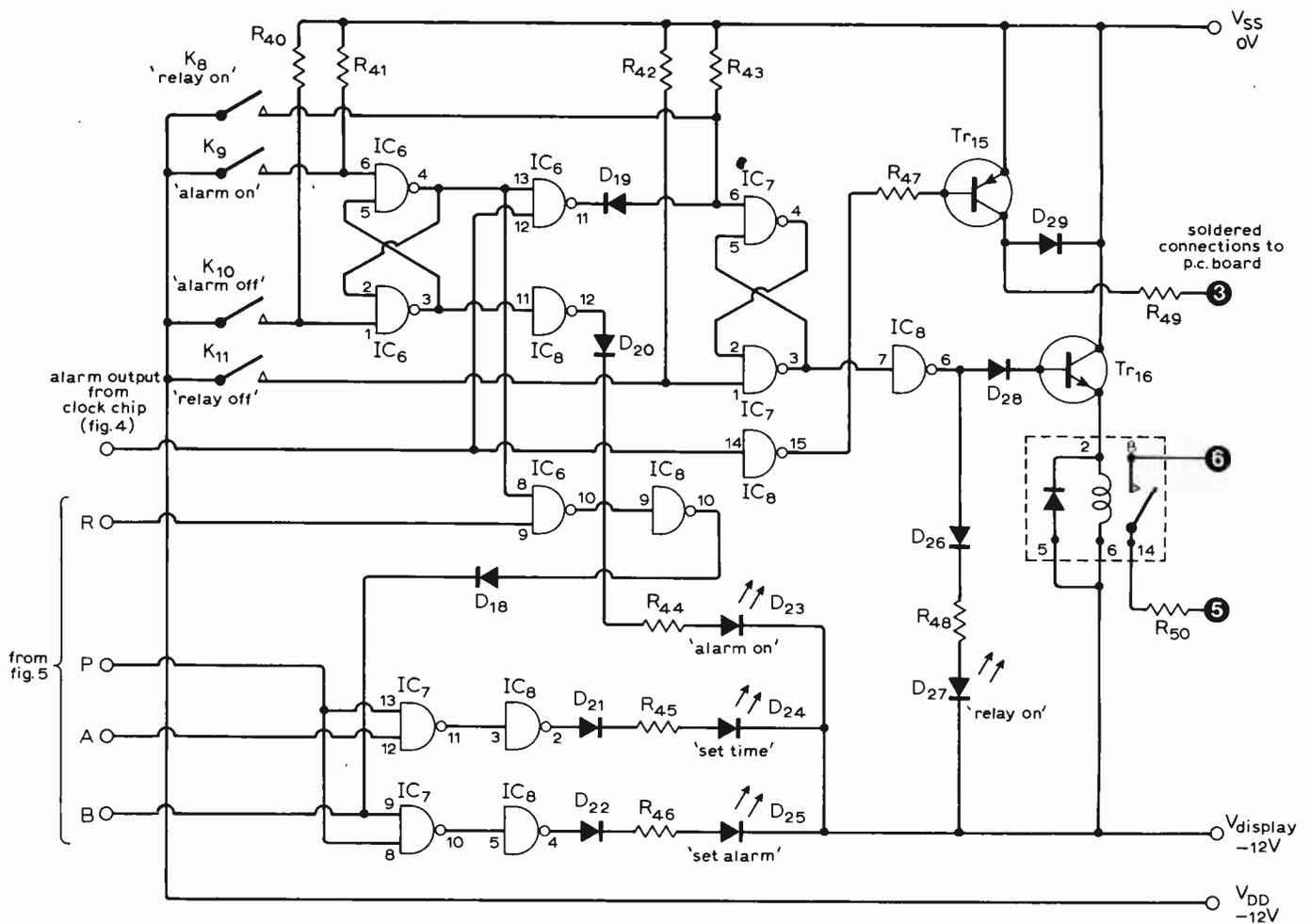


Fig. 6. Control logic circuit.

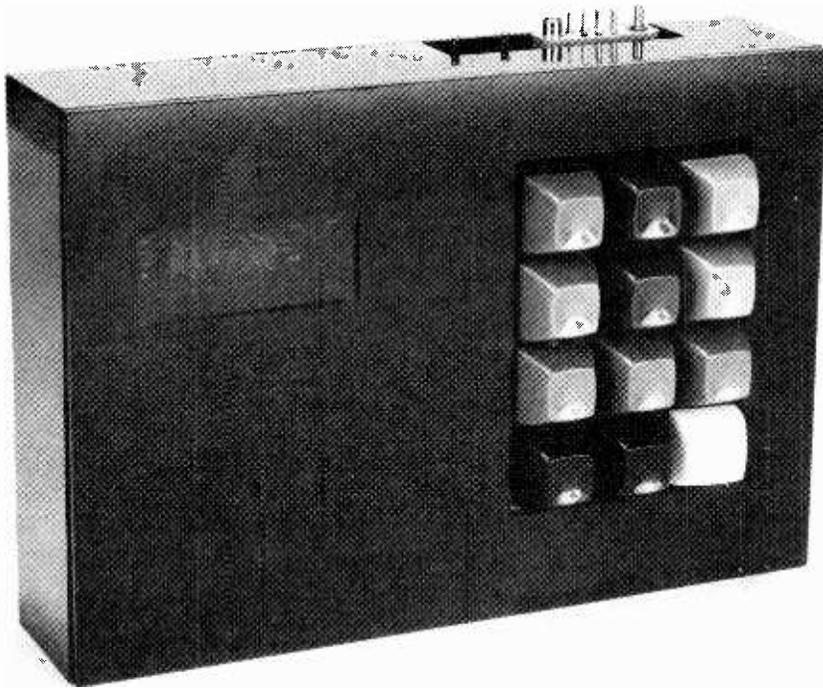


Fig. 7. The prototype clock. The unit is primarily intended as a timer, the display being of secondary importance. Connexions at top right are for an external power supply and switched output.

SPECIFICATION

Display. 6-digit 0.1 in l.e.d. display.

Displays time in the 24-hour mode with decimal point between hours and minutes and between minutes and seconds, e.g. 18.27.36

4 single l.e.ds indicate the following:

- 1) Alarm Set.
- 2) Relay On.
- 3) Display showing Alarm Time.
- 4) Count Stopped.

The display is not powered in the event of a supply failure.

Frequency

Reference. Quartz crystal, f_c 204.800kHz.

c.m.o.s. maintaining amplifier.

c.m.o.s. divider. Division ratio 2^{12} (4096).

Output of divider 50Hz.

Stability about $1\frac{1}{2}$ parts in 10^6

Power. Main supply 12V 120mA max. (1.44W)

Standby supply 9V Ni-Cd cells or dry

battery, providing 8mA max. (72mW) or 80mA with display on (720mW).

Alarm. Alarm time is adjustable in one-minute intervals.

Alarm tone is a 694Hz interrupted at 1Hz intervals.

When alarm sounds it may be completely cancelled or silenced for seven minutes after which time it will sound again.

Relay. When the alarm sounds the relay contact closes and remains closed even if the alarm is cancelled.

Independent control of the relay is also possible.

Contact rating: 100V max.

80mA max.

OFF resistance $\infty \Omega$

ON resistance 68 Ω

Dimensions

6 $\frac{3}{4}$ in \times 4 $\frac{1}{2}$ in \times 1 in.

Control logic. Most of the controls provided require only momentary closure of the control keys; diodes and resistors are, therefore, all that is required to connect the appropriate digit lines to the control inputs of the clock chip. This is shown in Fig. 5.

The alarm on/off and relay on/off functions require a bistable, to store the information supplied by momentary closure of the selected key. The bistables are formed by IC_6 and IC_7 in Fig. 6 which, as before, are c.m.o.s. integrated

circuits to reduce to a negligible amount the power required.

Single l.e.ds D_{25} and D_{27} indicate that the alarm has been enabled, and that the relay contact is closed, respectively.

Single l.e.d. D_{23} indicates that the display is showing the contents of the alarm register, i.e., the time for which the alarm has been set, D_{24} indicating that the count has been stopped.

A series resistor is connected in the relay contact circuit, to prevent damage to the reed relay due to large cable discharge

currents. This resistor, R_{50} , may be reduced in value, or removed altogether if the length of cable from the switched appliance to the relay is short. Without the series resistor the contact is rated at a maximum current of 250mA, to switch a load of not more than 10W.

The alarm output from the clock chip is buffered by an inverter in IC_8 and amplified by Tr_{15} to drive a medium impedance speaker, the impedance of which should be in the region of 1k Ω . The author used a miniature dynamic microphone, but better results were obtained by using a 3in 70 Ω moving coil speaker and a matching transformer. R_{49} is to prevent damage to Tr_{16} should the output be inadvertently shorted to V_{dd} .

(To be continued)

About People

Edward Fennessy, C.B.E., B.Sc., F.I.E.E., was made a Knight Bachelor in the New Year Honours List. Mr Fennessy is managing director of Post Office telecommunications and was formerly managing director of the electronics group at Plessey. As an RAF group captain on the staff of 60 Group he led the teams working on Gee, Oboe and other ground radar chains, becoming head of the Decca Navigator Company after the war. He later formed Decca Radar and in 1972 was awarded an honorary doctorate by the University of Surrey.

Also in the Honours List is the award of the O.B.E. to **John Scott-Taggart, M.I.E.E.** for "services to radio engineering". Mr Scott-Taggart has been a well-known innovator and writer on radio since the early years and, during the war, was Wing-Commander responsible for the majority of radar ground stations in England and Wales, including the training of their personnel. In 1963 he was made Knight Officer of the Order "Al Merito della Repubblica Italiana" by the Italian President.

Dr Per V. Bruel has received the Rayleigh Gold Medal of the Institute of Acoustics in recognition of his services to acoustics. Dr Bruel, one of the founders of Bruel and Kjaer, was presented with the Medal by the Hon. Guy Strutt, a descendant of Lord Rayleigh.

Godfrey Hounsfield, of the EMI Central Research Laboratories, has been awarded the Wilhelm Exner Medal by the Austrian Industrial Association for his work on the EMI-Scanner X-ray brain examination system. The system uses a computer to correlate a large number of readings from a narrow X-ray beam, the source rotating about the patient's head. Detailed cathode-ray tube displays can then be presented, giving about 100 times more information than a simple X-ray technique. Mr Hounsfield studied at the Faraday House College, obtaining a Diploma, and later joined EMI, working on radar and computers—in particular the EMIDEC 1100, for which he was head of the design team. He began work in the X-ray field in 1968, and in 1972 gained the McRobert Award for the work on EMI-Scanner.

Electronic engineers' slide rule

Designed for ease of calculation of commonly required parameters such as inductive and capacitive impedance and decibel ratios

by L. Nelson-Jones, F.I.E.R.E.

I have had a special slide rule for a number of years now which has a dB scale drawn up against the A and B scales of an otherwise standard slide rule, so that relative voltage dB ratios can be quickly calculated for any particular reference level. This rule has saved me many hours' work when drawing up response curves, both in audio and radio frequency work. Converting a table of readings to decibels can be a very tedious business using tables or logarithms; whereas, using the slide rule, one has only to move the slide to set the reference voltage against the "0dB" point of the dB scale and then all the other values are read off merely by moving the cursor to the voltage of each reading whose dB value is required.

Some months ago someone unknown stole the properly engraved version of the rule that I had been using, leaving me with only the very old hand-made wooden slide rule on which I first tried out the idea of the dB scale. Realizing how useful this rule had been to me, I decided to approach a slide rule manufacturer to put my ideas into practical form so that the idea could be made more widely available. This approach was made at the IEA exhibition and was received with interest, as the firm concerned was the one that had made the Units Converter for *Wireless World* (June 1969).

At that time I also had an *L/C* "slide

rule" originally distributed by the old A. H. Hunt (Capacitors) company as an advertising hand-out. This rule was made of stiff card and was very useful for quickly deriving the impedance of any *C* or *L*; however, it had very cramped scales since it tried to cover a quite unnecessarily wide range of frequency (0.000005Hz to 20GHz).

I decided therefore to aim at a double-sided rule having the dB scale added to the basic slide rule scales on one side and a simplified *L/C* calculator on the reverse. I tried many types of *L/C* scales using a large sized cardboard mock-up. With the scales chosen one first sets the slide against a triangular reference mark for the frequency of interest. The cursor is then moved to the value of the capacitor or inductor on the slide scale and the value of the impedance is read off from the appropriate scale on the body of the rule. The capacitive impedance scales have three ranges, for pF, for nF and for μ F. Likewise the inductive impedance scales have three ranges, for μ H, for mH, and for henrys. In this way, and by restricting the frequency range to 1Hz to 100MHz, the scales have been made relatively uncramped and will be quite accurate enough for most such calculations. I find the prototype of the new rule very easy to use for *L/C* calculations and it does not lend itself easily to misreading—quite an important point.


Reverting to the normal scales of the slide rule: The usual A,B,C, and D, scales (X^2 and X) are provided, together with the reciprocal scale $C1(1/X)$ used with the C and D scales, and the LL2 and LL3 ($e^{0.1x}$ and e^x). These provide all the necessary scales needed in everyday electronic circuit design work. I am sure some engineers will nevertheless find their favourite scale missing, but in the limited space available on a slide rule I had to choose those scales likely to be the greatest use to the greatest number of electronic engineers. In choosing the scales I was greatly assisted by the helpful comments and suggestions of the editorial staff of *Wireless World*.

I am sure many readers will at first wonder why I have chosen to introduce a new slide rule design at a time when calculators are getting so commonplace, and to this I would answer that, unless one has the price of a fully programmed calculator available (and few of us have), one cannot quickly do a dB calculation, or the *L/C* calculation for that matter. The slide rule on the other hand is quick and easy to use for these calculations, and its accuracy is usually more than adequate for everyday electronics. Until a simple and cheap electronic calculator capable of these calculations is available I, for one, shall be using the new slide rule.

Please do not think that I am anti-calculator, as some are. I most certainly am not. I have had a calculator of my own for some two years now, and it has proved invaluable in my work. Incidentally, on the occasions when I have been without it I find that I can add up much faster and more accurately than I used to be able to, before I had the calculator (critics of the "It gives you a lazy mind" school please note).

The new rule is available to *Wireless World* readers at a price of £2.50 + VAT and it is supplied complete with a full instruction book.

For a limited period until the end of February, 1975 the rule will be available at a special introductory price of £2.22 + VAT (equals £2.40 at the current rate of 8% VAT) to *Wireless World* readers. The above prices apply to UK and Eire only. Overseas please add appropriate carriage. Enquiries and orders (with cheque or Postal Order) should be sent to KEY Electronics, PO Box 7, Bournemouth BH7 7BS.

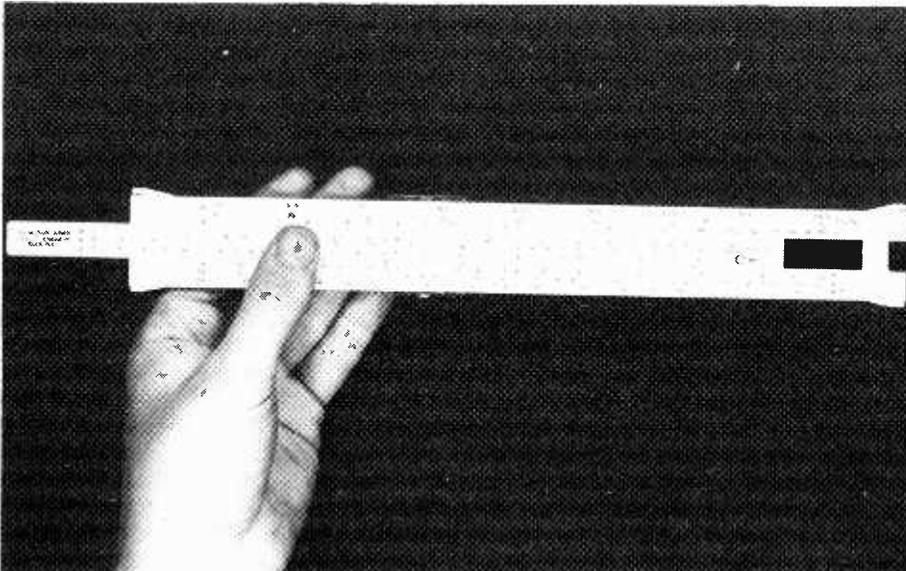

Low-cost emergency power generator

220V sine-wave generator using a lawn-mower engine and a scrap car dynamo

by J. M. Caunter

It has long been the dream of the author to become independent of the national grid during what seems to be the annual "silly season" of threatened disruptions in the supply of electricity. Inverters are attractive, being cheaper than petrol generating sets, but still expensive when one considers the batteries needed to run them. Most inverters have square-wave outputs, for optimum efficiency, which are not suitable for central heating pumps, 25% of the power being wasted in harmonics which could overheat the motors. Television sets should have the input taps changed because of the different peak-mean value of square waves. Sine-wave inverters are available at a price, but these are less efficient, and require even bigger batteries.

Alternative methods of generating low-cost power for the home have been investigated. The author's solution costs about £12 and makes use of a petrol mower. A 12V car dynamo rescued from a scrapyards provides an excellent skeleton for an alternator, and a transformer at about £8 saves a tedious winding process. A scrap 12V battery supplies the excitation current, and about £2.50 secures enough components to monitor the frequency of the output voltage and protect the field winding from setting fire to the garden shed when the motor stalls while you are in the bath (metaphorically speaking).

The armature of the dynamo is re-wound for a slightly higher voltage which does not cause insulation problems but keeps brush currents down, since the area of contact with the slip rings is less than that with the original commutator. The design to be described is by no means an optimum one and can easily be changed to suit the reader. For example, if the armature was wound for 110V a.c., it would require about 78 conductors of 22swg per slot. However, the insulation would need more careful selection than in this proposed design.

Armature construction

Remove the armature from the dynamo yoke and dismantle from the drive-end bearing plate. Push out the paper rope filler from the outer edge of each armature slot, and after cutting the wires at the commutator remove the windings.

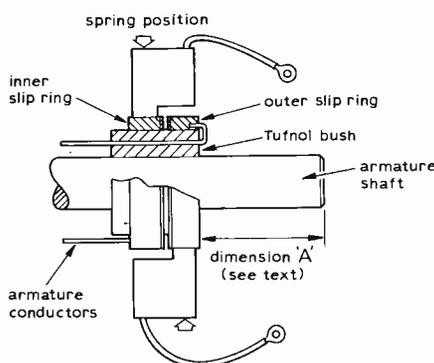


Fig. 1. Sectional view of slip-ring assembly and brushes.

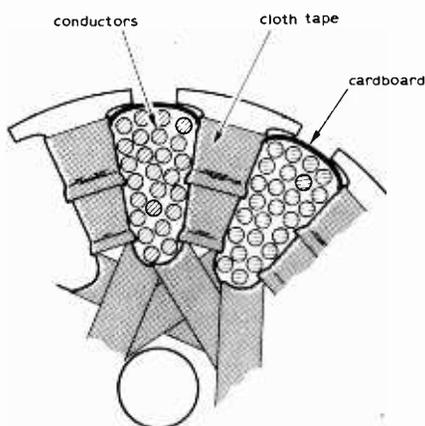


Fig. 2. Armature insulation.

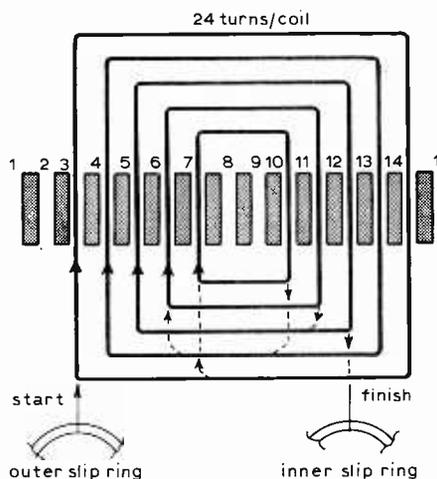


Fig. 3. Developed winding diagram.

Clean the armature core with paraffin and then dry. Before removing the commutator measure its major dimensions and its position relative to the end of the shaft which is shown as dimension A in Fig. 1. Note the width and relative position of the brush marks on its circumference. These dimensions are vital to ensure correct alignment between brushes and slip rings, especially on dynamos without brush inspection windows. With reference to Fig. 1, the author's slip-ring assembly was made to the following dimensions:

- overall diameter 37.25mm;
- insulating bush bore 15mm;
- width of each slip ring 8.5mm;
- gap between slip rings 3mm.

The remaining dimensions are less critical and can be varied to suit the reader. The commutator is now pulled off the shaft by brute force or ignorance.

Construction of the slip-ring assembly is shown sectioned in Fig. 1. The copper slip rings are retained on the Tufnol bush by Araldite or Loctite adhesive. When completed, the assembly is pressed or drifted on to the shaft to a position determined by dimension A. The old armature insulation must be removed from the slots and renewed. The most successful method was to wind single layers of black cloth insulation tape between adjacent slots and between diametrically opposite bottoms of the slots as shown in Fig. 2. This has the added advantage of building up a cone-shaped collar where the shaft enters the armature laminations and greatly aids the winding operation. One or two layers of tape are also wound tightly around the armature shaft between this collar and the slip-ring assembly.

Before commencing with the winding, Fig. 3, which shows the armature slots laid out flat for simplification, should be studied. Each pair of slots is wound with 24 turns of 18swg enamelled wire except the two outer pairs which are left empty. The slot nearest the hole through the slip-ring bush is designated slot 3; the remaining slots are numbered clockwise from this, through 14 and back to 2. When one is winding between slots 5 and 12 the coil is divided equally on each side of the armature shaft. Use thin but strong card cut into strips to insulate the open end of the armature slots as shown

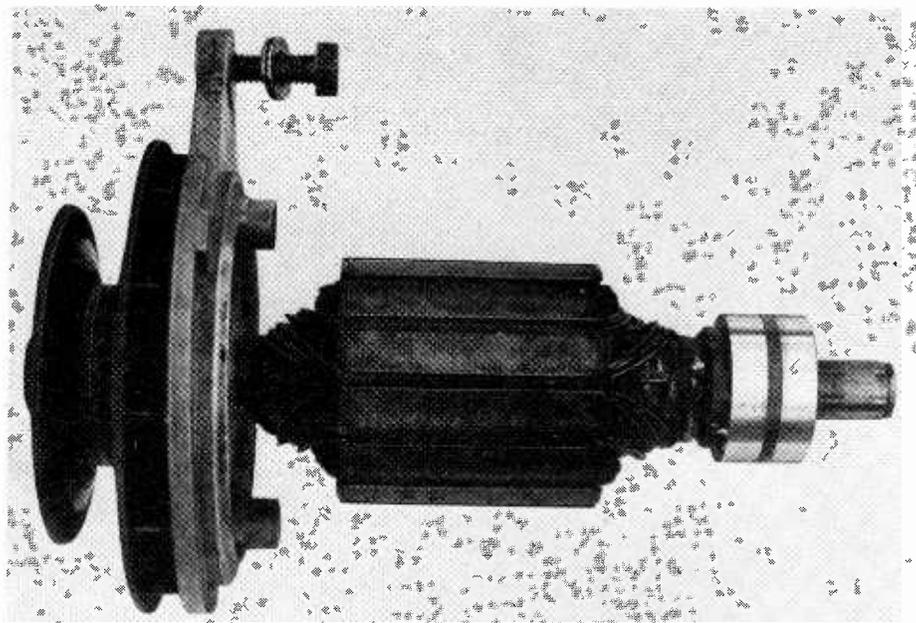


Fig. 4. Completed armature assembly.

in Fig. 2. By tapering one end, the cards slide into position fairly easily. Bind the armature shaft with thin string, where the conductors enter the slip-ring bush, and tie securely. Impregnate the whole winding with shellac applied by brush, ensuring that the liquid penetrates the slots. The completed armature is shown in Fig. 4.

The brush gear

The brushes are modified to contact the slip rings as shown in Fig. 1. In the author's model the brushes were filed back to a width of 6.5mm. If new brushes are used it may be necessary to bed them in with the aid of fine-grade carborundum paper wrapped around the slip rings. When finally fitting the brushes to the end plate it is important to position the pressure springs over the contact area as shown. The alternator may now be assembled.

Frequency indicator and control circuit

To ensure that the alternator is driven at the correct speed it is necessary to monitor the frequency of the output voltage. Fig. 5 shows the circuit of a suitable frequency meter. D_1 , R_1 , D_2 and C_2 provide a stabilized 10V d.c. supply to the circuit, derived from the input. The input voltage is squared by Tr_1 to minimize errors caused by changes in input amplitude. R_2 and D_3 protect Tr_1 from transients and reverse base-emitter potentials. A differentiating circuit— R_3 , C_1 and D_4 into Tr_2 is driven by Tr_1 whose collector current is limited by R_4 when discharging C_1 . The current pulses developed in the collector circuit of Tr_2 are of constant width and varying repetition rate depending on the input frequency. These pulses are integrated by the inertia of the meter movement and displayed as a steady reading, changing only with input frequency. The linearity of this circuit is dependent on the mark/space ratio of the current pulses at the maximum operating frequency. The values chosen for the differentiator in the author's circuit give a negligible error at the maximum meter reading of 100Hz. The meter scale is calibrated directly from 0 to 100Hz, and R_6 is adjusted to give a reading of 50Hz when the input is fed with 10V–60V a.c. from a mains-connected transformer. Fig. 6 shows the cut-out and output circuitry. The output from the alternator is stepped up to mains voltage by a transformer T_1 , which has a rating of 250W. An auto transformer would be ideal for this function on the basis of size and cost. It is important for safety reasons to connect the N and E terminals together on the output socket and return both to the metalwork of the complete unit. The output of the transformer is used to energize a 230V a.c. relay, the contacts of which complete the field circuit with the 12V excitation voltage. A separate set of contacts is used for the indicator lamp to prevent the back e.m.f. from the field winding fusing the bulb when the relay drops out. The lamp is positioned on the control panel to illuminate the frequency meter. The relay

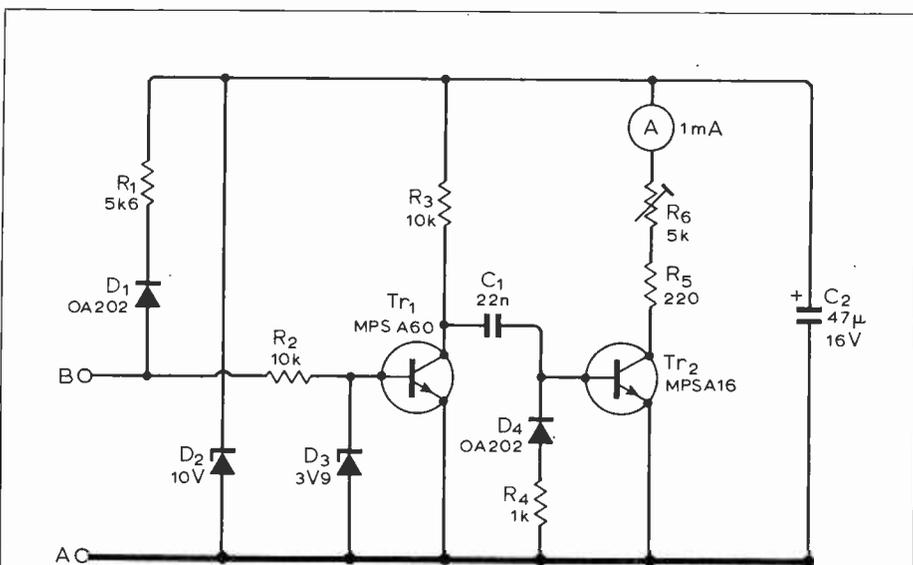


Fig. 5. Frequency-meter circuit diagram.

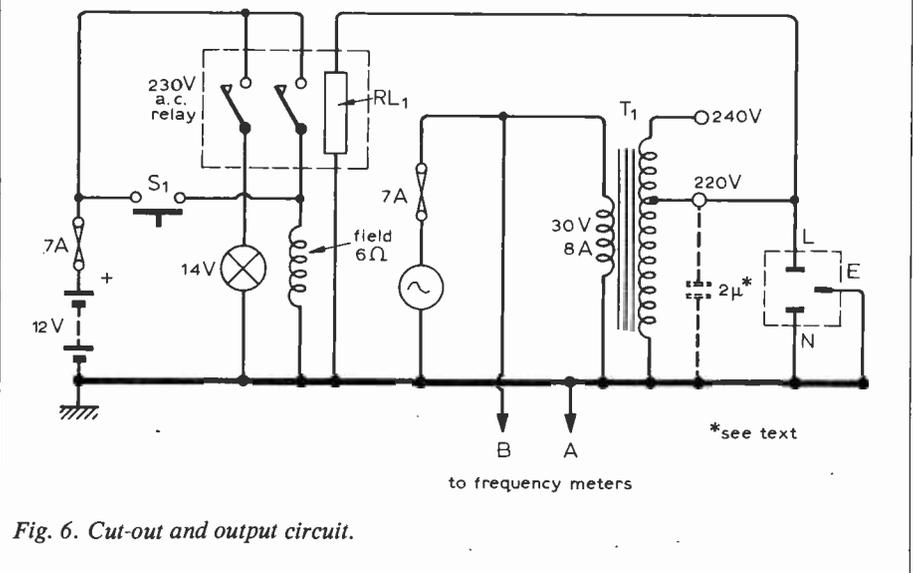


Fig. 6. Cut-out and output circuit.

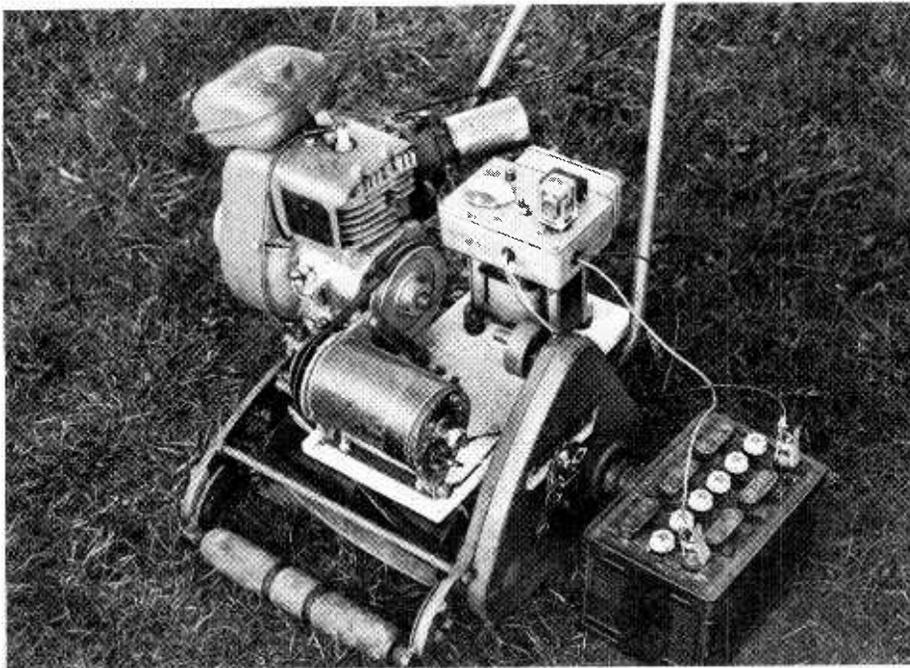


Fig. 7. Complete generator.

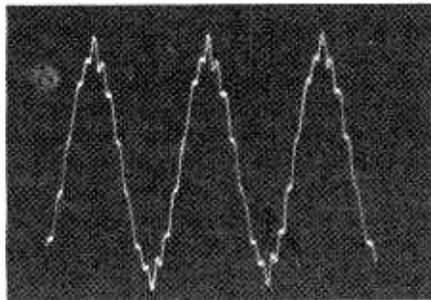


Fig. 8. Output waveform.

drops out if, for any reason, the output falls below 150V a.c., e.g. overload or engine failure, the latter causing loss of air cooling to the field coils. To reset the output S_f is depressed. A battery charger may be connected to the output to maintain battery charge if needed.

Driving the alternator

The unit is shown mounted on a motor mower in Fig. 7. This engine is ideal because it has a governor incorporated at the air intake of the cooling fan which maintains a fairly constant speed during changes in load. The drive pulley is five inches in diameter giving a step-up ratio of about 2:1. This ratio was chosen to give maximum economy with minimum noise. A further reduction in noise was effected by fitting a cocoa tin, suitably perforated and filled with glass wool, over the silencer and held in place by a capacitor clip. The engine, at full load, runs for one hour on one pint of petrol if the carburettor is correctly adjusted.

Performance

The output waveform is shown in Fig. 8. A component at 700Hz is present due to the variation in reluctance of the magnetic circuit as the armature slots rotate. This can be reduced by means of a $2\mu\text{F}$ 240V

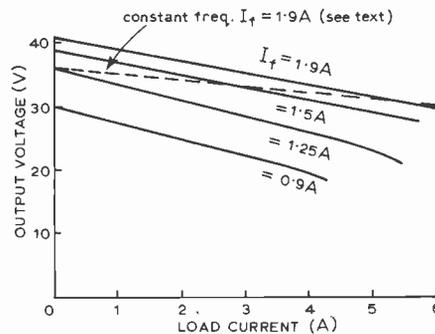


Fig. 9. Load characteristic for alternator.


a.c. capacitor connected at the output (Fig. 6) but some distortion of the waveform will result due to armature reaction on the field flux.

The open circuit output of the alternator at $I_f = 1.9\text{A}$ is 0.72V r.m.s./Hz and the load characteristic for varying excitation is shown in Fig. 9. The speed regulation of the engine is such that a load of 180W reduces the output frequency from 56Hz to 50Hz. The load characteristic of Fig. 9 includes the drop in output caused by the change in frequency. The broken line shows the output regulation at $I_f = 1.9\text{A}$ with the frequency held constant at 50Hz. For a full-load voltage of 200V at 50Hz, the no-load voltage is 265V at 56Hz.

This generating set, while crude in its concept, is quite adequate to supply the demands of a typical central-heating system and has been used to power a monochrome television set with good results. The performance tests have prompted the author to experiment with a higher-power, self-excited version incorporating electronic regulation, using the same alternator and output transformer.

HF predictions

Ionospheric attenuation and MUF are directly proportional to sunspot number so they are both low at sunspot minimum. Less attenuation gives in turn a lower LUF but the degree of MUF reduction is much greater. Normal undisturbed conditions thus give good communication but the available spectrum is small. Disturbed conditions lower MUF further but raise LUF so small disturbances have a great effect on communication at sunspot minimum.

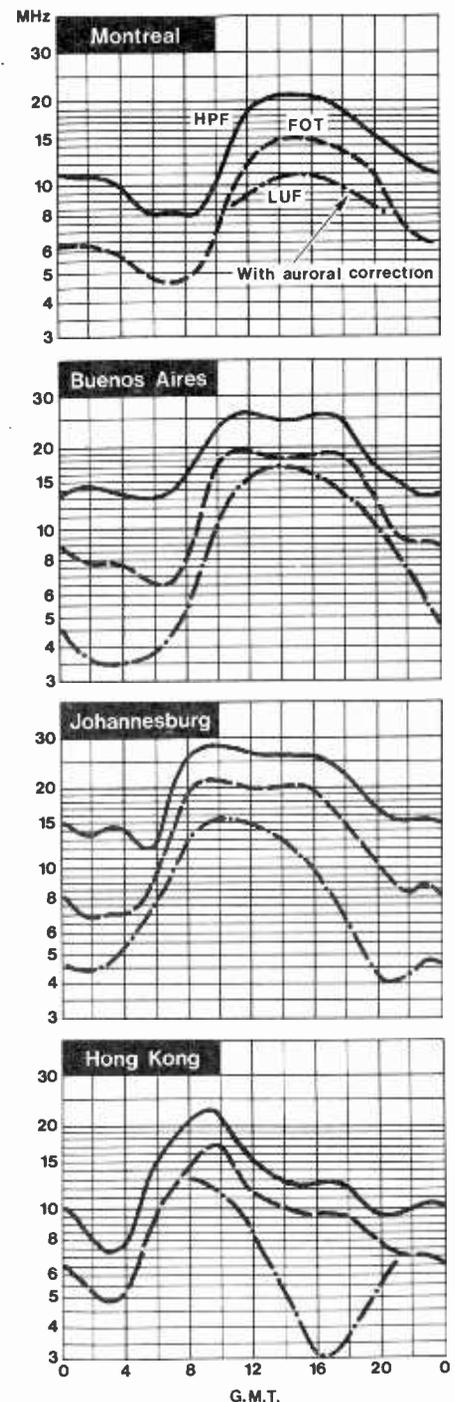



Solid state data recorder

A solid state NASA-developed data recorder with no moving parts may replace magnetic tape recorders aboard spacecraft in the 1980s. Other possible applications include use as aircraft flight data recorders. Failure of moving mechanical parts accounts for 70 per cent of magnetic tape recorder malfunctions aboard spacecraft. The new recorders offer high reliability and experimental models of the device have been pronounced successful.

Technology for such a recorder is based on the use of very small magnetic domains or spots known as "bubbles". These magnetic bubbles exist in specially prepared garnet chips. By applying a thin film of magnetic material in appropriate patterns over the chips, these bubbles can be moved and controlled to perform logic functions. The present experimental model has a 60-thousand bit data storage capacity. The overall objective of the present research programme is to provide a solid-state data storage system with a 100-million bit capacity by 1978. If successful, flight versions of such a recorder could be ready at the end of this decade.

Magnetosphere exploration

The International Sun Earth Explorer (ISEE) programme is a joint NASA/ESRO venture involving three satellites, two of which ISEE-A and ISEE-C are being developed under NASA auspices whereas ISEE-B is the responsibility of ESRO. The satellites will explore the Earth's magnetosphere and adjacent regions of interplanetary space close to Earth. As a result of previous satellite missions the main features of the magnetosphere are already known. However, there is still much to be discovered about its dynamic behaviour and the influence of the solar wind.

Satellites ISEE-A and ISEE-B, equipped with similar experiments will travel at a carefully controlled and variable distance from 100km to 5,000km between each other. These two satellites will be launched by a single Thor Delta Rocket in

Autumn 1977 and their orbit will be highly eccentric, close to the ecliptic plane. By this means, similar features will be seen by both spacecraft sequentially with a time interval between observations making it possible to distinguish between spatial and temporal variations of the physical and dynamic features recognized. A third spacecraft, ISEE-C will be launched one year later into a solar wind, undisturbed by the presence of Earth. Thus while A and B satellites are examining disturbances in the magnetosphere, the ISEE-C will provide vital information on the actual solar wind input to the magnetosphere.

New communications satellite

Contracts have been awarded for development of the communications payload of the ESRO maritime satellite MAROTS. This is to provide ship-to-shore communication vastly improved on the present, highly congested, conventional radio links. The launch of MAROTS is scheduled for the Autumn of 1977.

Marconi Space and Defence Systems, prime contractors for the communications payload, are also to study and define the basic parameters of the ship-borne and shore-based terminals. The former will be made as simple as possible and, to this end, MAROTS is to be equipped with a high-efficiency shaped-beam antenna coupled with a transistorized L-band power amplifier. Ships will use the L-band frequencies to communicate to and from the satellite. As shore terminals will be able to use more sophisticated equipment, the shore-to-satellite frequency will be in the 14GHz band while the satellite-to-shore communication will use the 11GHz band.

Radio and space research 1971-73

The triennial report of the Science Research Council's Appleton Laboratory was published during December. One section of the report is devoted to an outline of important developments in work during the period

1971-73; these include UK and co-operative satellites such as Ariel-IV, Ariel V, and UK contribution to the International Ultra-Violet Explorer satellite and the UK experiment on the American satellite Copernicus involving the use of four X-ray telescopes. A major high latitude rocket campaign late in 1973 in Andøya, Norway, involved the launching of Skylark and Petrel rockets in a co-ordinated programme which included the first trials of a new pulse code modulation telemetry system and Doppler range measurement system. The report describes the Laboratory's own research in space science and on the scientific aspects of the propagation of radio waves through the ionosphere and troposphere. Copies are available from HMSO at £1.25.

Also recently published is a comprehensive survey published by the European Space Research Organization which summarizes European activities in space research and technology and the skills and facilities developed by European industry in this field.


Crop inventory experiment

The launch of the second Earth Resources Technology Satellite (ERTS-B), scheduled for launch during January is to make possible the next steps of experimentation in the various earth resources disciplines.


Several experimental demonstrations designed to show the practical benefits to resource management of multispectral remote sensing from space have been selected to include water management, agriculture, land use planning, and monitoring ice conditions in navigable lakes. One of these experiments is a "Large Area Crop Inventory Experiment" to test whether the use of data gathered by spacecraft and analyzed with the aid of computers can improve the timeliness and accuracy of major crop forecasts. At the outset, LACIE will concentrate on wheat grown in the North American area. The experiment will combine crop acreage measurements obtained from ERTS-B data with meteorological information from NOAA satellites and from ground stations designed to relate weather conditions. If during the first year this activity proves useful, it will be extended in the second year to other regions and other crops.

Did you know?

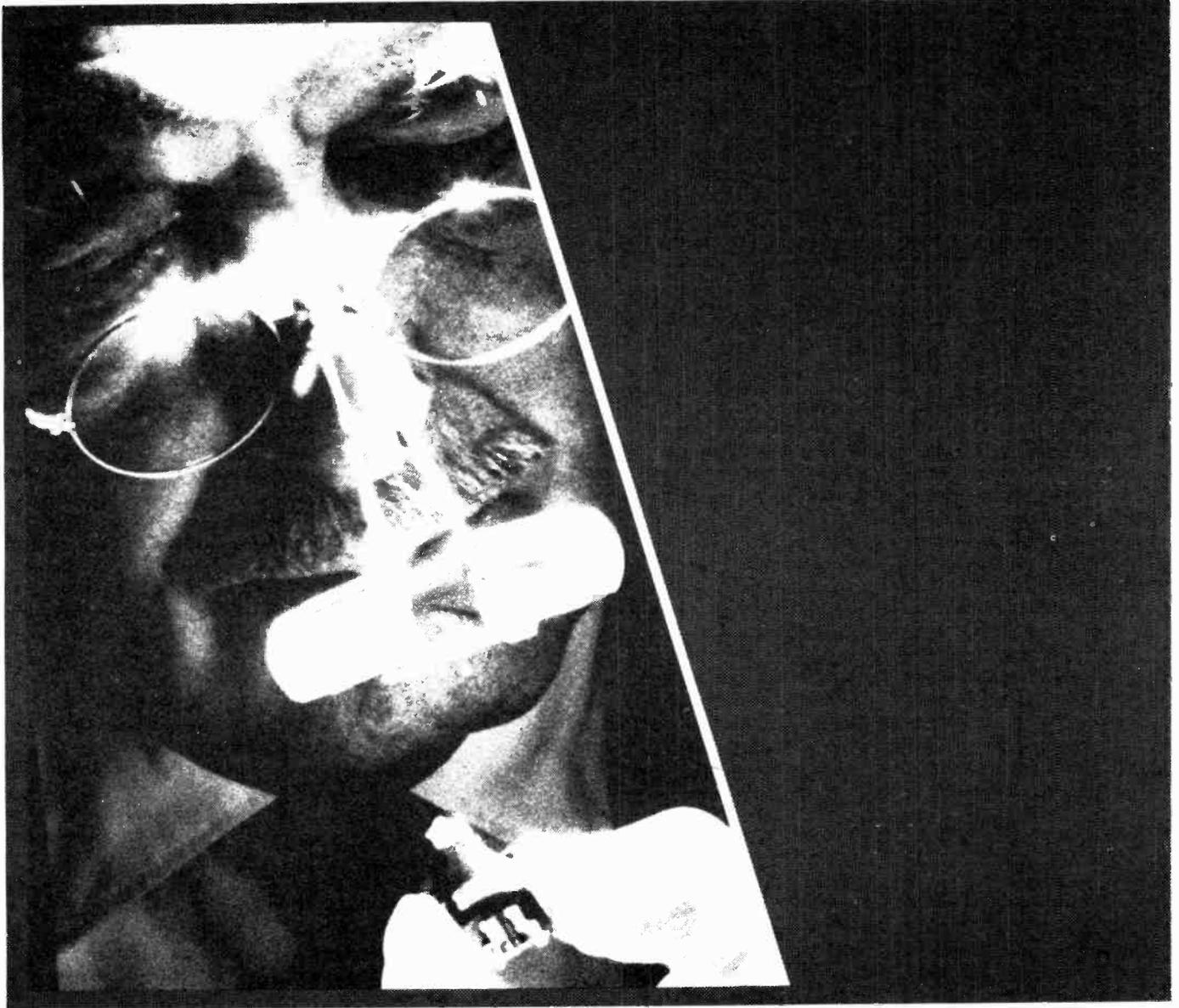Pioneer 11, latest Jupiter probe transmits an eight-watt radio signal which reaches NASA's antennas with a power of 1/100,000,000,000,000 watts. Collected for 19 million years, this energy would light a 7.5-watt Christmas tree bulb for one-thousandth of a second.



Our "U" and you.

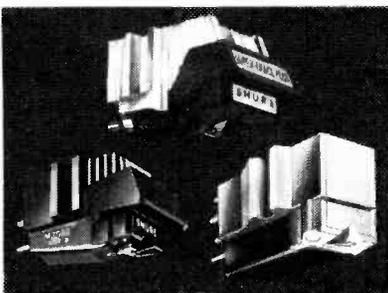

Every Shure cartridge comes equipped with its own "U" Factor. The "U" stands for *uniformity* in rigid production standards . . . tough quality control . . . and satisfying listening pleasure. By maintaining these high standards in every phase of engineering, production, and inspection, Shure provides a better cartridge . . . over, and over, and over. And, with routine maintenance, your Shure cartridge will continue to perform at the published specifications. You may not see the U Factor, but you'll always be grateful for it.

Shure Electronics Limited
Eccleston Road, Maidstone ME15 6AU
Telephone: Maidstone (0622) 59881



WW—138 FOR FURTHER DETAILS

NOW, more than ever,

S **single**
source
makes
sense

TO MINIMISE INVESTMENTS AND SOLVE STOCK PROBLEMS

You can increase your efficiency, too, by ordering large or small quantities of any one part, or making up an order of any number of assorted small quantities through the United-Carr Supplies service. We can deliver with more than usual promptitude because we carry such large and varied stocks of CINCH, DOT and FT electronic and electrical components. Fastenings and assemblies.

So, make United-Carr Supplies your SINGLE SOURCE for



Products, including Barrier terminal strips, Edge Connectors, Subminiature Connectors, Rocker switches, Indicator lights, Press fasteners and Metal & Plastic components.

Send now, stating possible requirements, for free and post free catalogue.

United-Carr Supplies Ltd., 112 Station Road, Ilkeston, Derbyshire DE7 5LF.
Tel: Ilkeston 78711 STD 06072 78711. Telex 377117. C.H.F.A.d.

WW-148 FOR FURTHER DETAILS

A.f. and r.f. clipping for speech processing

by D. A. Tong, B.Sc., Ph.D.

Datong Electronics Ltd

A comparison of audio and radio-frequency clipping for increased transmitter efficiency

If one examines the human voice using an oscilloscope, one of its most striking features is the low ratio of average amplitudes to peak amplitudes. An example is given in Fig. 1 which shows the first vowel sound in "hello". To the operators or designers of speech transmission equipment this small average-to-peak ratio can be an embarrassment because if the peak signal handling capability of the system (e.g., a radio transmitter or a public address system) is adequate to handle the peaks without distortion, it will be inefficiently utilized during the remaining sections of the speech waveform, that is, for most of the time. In a radio transmitter using any form of amplitude modulation (e.g., a.m. or s.s.b.) this means that for a given average radiated power a much higher peak power capability is required. Unfortunately the cost of a transmitter rises rapidly with its peak power capability. Additionally there is usually a statutory limit on the peak power that can be used. A radio transmitter using f.m. would similarly need a high peak deviation for a given average deviation, but here the cost is not in money but in frequency spectrum width.

For the above reasons there has long been much interest in "speech-processing" devices which raise the average-to-peak amplitude ratio of the speech waveform. In the remainder of this article we compare and contrast three speech-processing techniques which are at present quite extensively used. The techniques are audio-frequency clipping, audio-frequency compression, and radio-frequency clipping (that is, clipping of a single-sideband suppressed-carrier (s.s.b.) waveform). Reasons will be given for the marked superiority of r.f. clipping over the other methods.

A.f. clipping

This is probably the most obvious treatment and is probably also the simplest. As the name implies, one "clips" off any portion of the audio-frequency waveform which exceeds a given amplitude. Fig. 2 shows a sine wave at 500Hz after passage through an a.f. clipper and 3kHz low-pass filter at levels just below the clipping threshold (top) and with 20dB of clipping



Fig. 1. A section of the first vowel sound in the word "hello" as seen on an oscilloscope

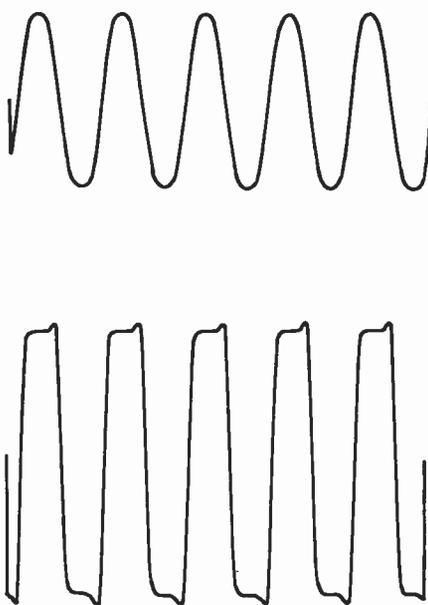


Fig. 2. Top: the output of an a.f. clipper when fed with a sine wave at a level just below the clipping threshold. Bottom: the same but with the input level increased by 20dB.

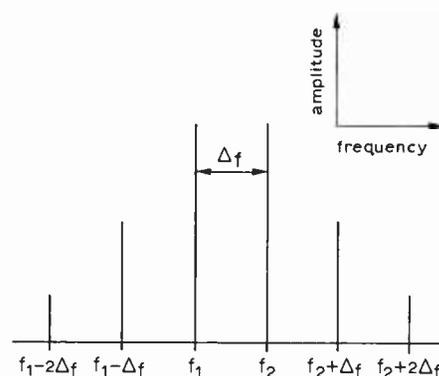


Fig. 3. Intermodulation products produced by clipping a two-equal-tone signal, omitting the products centred on harmonics of the two basic frequencies.

(bottom). The clipping effect is clearly visible and if the input were a speech waveform its average-to-peak ratio would be greatly increased.

But there are snags. Firstly, a lot of distortion is introduced; secondly, the output signal is for a fundamental reason unsuitable for feeding into a single sideband transmitter (the most common kind in use today).

The distortion comprises both harmonic and intermodulation distortion.¹ For example, if the input signal were simply two equal-amplitude sinusoids with frequencies f_1 and f_2 , the output would contain the intermodulation products

$$(f_1 + f_2)/2 + n(f_1 - f_2)/2$$

($n = 1, 3, 5 \dots$ etc.)

as shown in Fig. 3, together with other overlapping series of products centred on harmonics of f_1 and f_2 , i.e.,

$$m(f_1 + f_2)/2 + mn(f_1 - f_2)/2$$

where $n = 1, 3, 5 \dots$ etc.,

and $m = 2, 3, 4 \dots$ etc.

Thus if the two frequencies were 1kHz and 2kHz the output of the clipper would contain components every 0.5kHz. Obviously, when more than two input signals are present the number of possible intermodulation products becomes very large indeed. As a result speech passed through an audio-frequency clipper acquires an unnatural and characteristically "clipped" sound. Despite this the intelligibility is

hardly impaired. This kind of processor has been widely used in conventional a.m. or f.m. transmitters because of its simplicity: the gain in "talk-power" more than offsets the quite high distortion.

The reason that the technique is unsuitable for s.s.b. transmitters is that it generates "square" waveforms. An ideal s.s.b. modulator with a square wave input signal would produce s.s.b. with peaks of infinite amplitude. Obviously in a real situation this is impossible but the "square" waves from an a.f. clipper can result in a s.s.b. signal with no improvement in the average-to-peak ratio to offset the considerable distortion.

This effect is illustrated in Fig. 4 which contrasts the s.s.b. signal at 60kHz (a) produced from a sine wave (b) with that (c) produced from a "square" wave (d). These waveforms were obtained using a specially adapted commercial r.f. speech clipper made by Datong Electronics Ltd. Normally the s.s.b. signal shown is not accessible. Signals (d) and (b) were monitored at the output of the frequency-shaped preamplifier in the Datong r.f. clipper and this accounts for the distortion of the "square" wave. The point to note about these waveforms is that the peak amplitude ratio of the s.s.b. signals is 1.5 times that of the two input signals.

To some extent this difficulty can be partly circumvented by pre-emphasizing high frequencies in the speech bandwidth to such an extent that only speech components above 1kHz are clipped. The harmonics then fall outside the speech bandwidth and are cut out by the 3kHz low pass filter. But then, in addition to the distortion, the speech is excessively "toppy" and even more unnatural.

A.f. compression

Audio-frequency compressors use an automatic gain control system to ensure that if the input signal (the unprocessed speech waveform) exceeds a certain threshold, the gain is reduced rapidly (typically within 10ms). A second time constant, usually one second, allows the gain to recover much more slowly to its full value. Some devices of this type allow the gain to "hang" at a fixed value for a predetermined time if the input signal ceases. This avoids a distracting effect wherein the background noise rises to a high level between bursts of speech.

A.f. compressors are effective in maintaining a fairly constant peak signal level. Thus they can compensate nicely for unwitting changes in voice level or for different speakers. On the other hand they are not well suited to the task of raising the average-to-peak ratio of the speech waveform. In the limiting case of a compressor with zero "attack" and "decay" time constants there would be no difference between it and the audio clipper already discussed. But as soon as the time constants become non-zero (as they must to make the a.g.c. loop stable, and if distortion is to be less than that produced by an a.f. clipper) it is clear that, following a peak, the overall gain will be reduced for a time dependent on the decay time constant, and that this will reduce the amplitude of weaker signals following the peak. Unfortunately in speech, weak sounds which are important for intelligibility tend to closely follow strong peaks and therefore a compressor tends to affect adversely the intelligibility of the speech if its time constant is made low enough to increase the average-to-peak ratio².

R.f. clipping

An ideal speech-processing device would combine the instantaneous response of the a.f. clipper with the low distortion of a compressor with a long decay time con-

stant. This ideal is closely approached by the so-called r.f. clipper. The essence of the technique is not to clip the a.f. waveform directly, but to first translate it to some much higher frequency. It is then a single sideband suppressed carrier (s.s.b.) signal. If this signal is clipped a similar range of products is generated internally as in the a.f. clipper, but with the important difference that $(f_1 + f_2)$ is now very much greater than $(f_1 - f_2)$. It is then a trivial matter to filter out all the components with $m > 1$. In the example used earlier of two tones at 1kHz and 2kHz, if the r.f. clipping is carried out at say 60kHz, f_1 and f_2 will be 61 and 62kHz. Products associated with different m values will then be centred on integral multiples of 60kHz and the separate groups no longer overlap.

If the clipped s.s.b. signal is then heterodyned back to its original audio frequency range, the only frequencies left in the output will be

$$(f_1 + f_2)/2 + n(f_1 + f_2)/2.$$

$(n = 1, 3, 5 \dots \text{etc.})$

The harmonic frequencies which were produced by the a.f. clipper do not appear and with them disappear a large number of intermodulation products as well.

A commercial device for doing the whole operation, audio → s.s.b. → clipped s.s.b. → audio, the Datong Electronics Ltd "Universal r.f. Clipper", is shown in Fig. 5

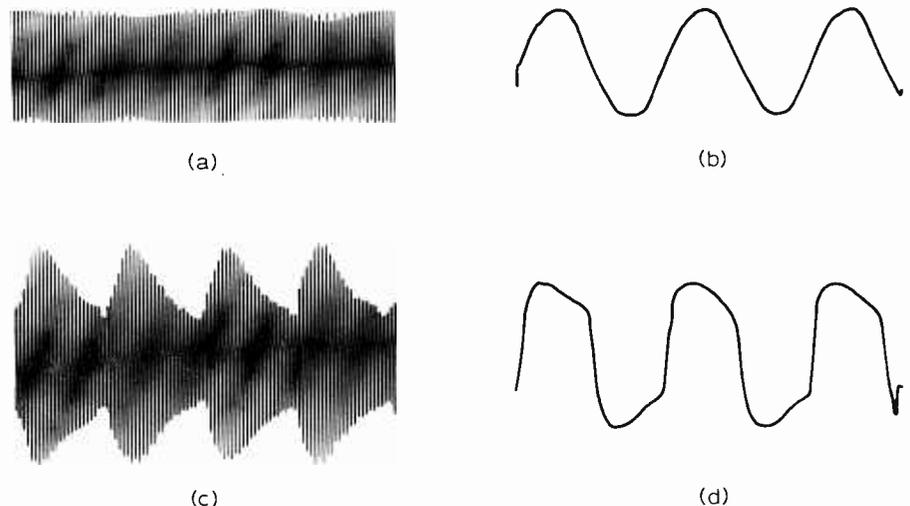


Fig. 4. S.s.b. signals produced from different input signals. A is given by B, and C by D. The peak amplitude ratio of the s.s.b. signals is greater than that of the inputs.

Fig. 5. Photograph of the Datong Electronics Ltd r.f. speech clipper. It is basically a closed-circuit s.s.b. transmitter, clipper, and receiver, operating at 60kHz. Thus both input and output are at audio frequencies and the device is designed simply to connect in series with the microphone lead on any transmitter.

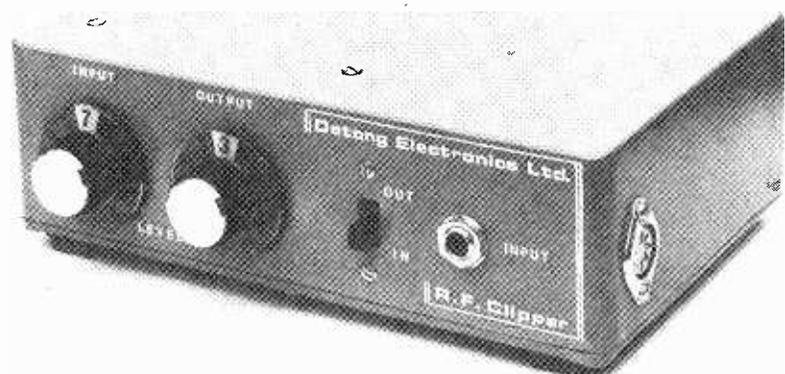





Fig. 6. Block diagram of the Datong Electronics Ltd r.f. speech clipper.

Fig. 7. Top: same speech sound as in Fig. 1 appearing at the output of the Datong r.f. clipper with peak amplitude just below the clipping threshold. Bottom: same but with 20dB of clipping, showing the absence of harmonic distortion.

and its block diagram is shown in Fig. 6. The device is intended for use as an accessory with existing communications transmitters and it is fitted simply by plugging in series with the microphone of the transmitter. The output waveform obtained using 20dB of r.f. clipping with a section of the same speech sound as in Fig. 1 is shown in Fig. 7. A comparison of the top and bottom traces shows the large gain in average-to-peak ratio which is obtained. (For the top trace the input level was reduced until the peaks were just below the threshold of clipping). The "non-clipped" appearance of the output waveform shows that the output is entirely compatible with s.s.b. transmitters. Fig. 8 shows the output of the Datong r.f. clipper when fed with a sinusoidal input at 500Hz and using 20dB of r.f. clipping. The absence of harmonic distortion is clearly shown.

Subjectively, speech sounds remarkably undistorted when processed in this way but becomes strikingly louder for the same peak amplitude. Indeed a similar kind of device to the Datong clipper has even been used for short-wave broadcasting³. The considerable increase in average-to-peak amplitude ratio which is possible using r.f. clipping allows the average side-band power output of an a.m. or s.s.b. transmitter (or deviation for an f.m. transmitter) to be greatly increased. It is generally agreed among the increasingly large number of radio amateurs who use r.f. clipping that it gives about the same improvement to a s.s.b. transmission as if its peak power rating were increased by a factor of ten, and at a far lower cost. Surprisingly perhaps, it also seems to be true that the intelligibility of the speech is actually increased by the r.f. clipping process so that there is a double benefit.

Obviously a s.s.b. transmitter already contains part of the circuitry shown in Fig. 6, therefore why duplicate it? In fact there are adaptors commercially available which allow the s.s.b. signal already produced inside the transmitter to be clipped, but contrary to what one might expect, there is almost invariably an extra cost penalty to add to the inconveniences of having to make connections internal to the transmitter and of the restriction to s.s.b. transmitters only. The reason is that in a device such as the one illustrated in Figs. 5 and 6, the internal s.s.b. signal is not radiated and therefore its spectral purity is irrelevant from the stand point of adjacent channel interference. Unwanted products close to the information bandwidth can be easily and cheaply re-

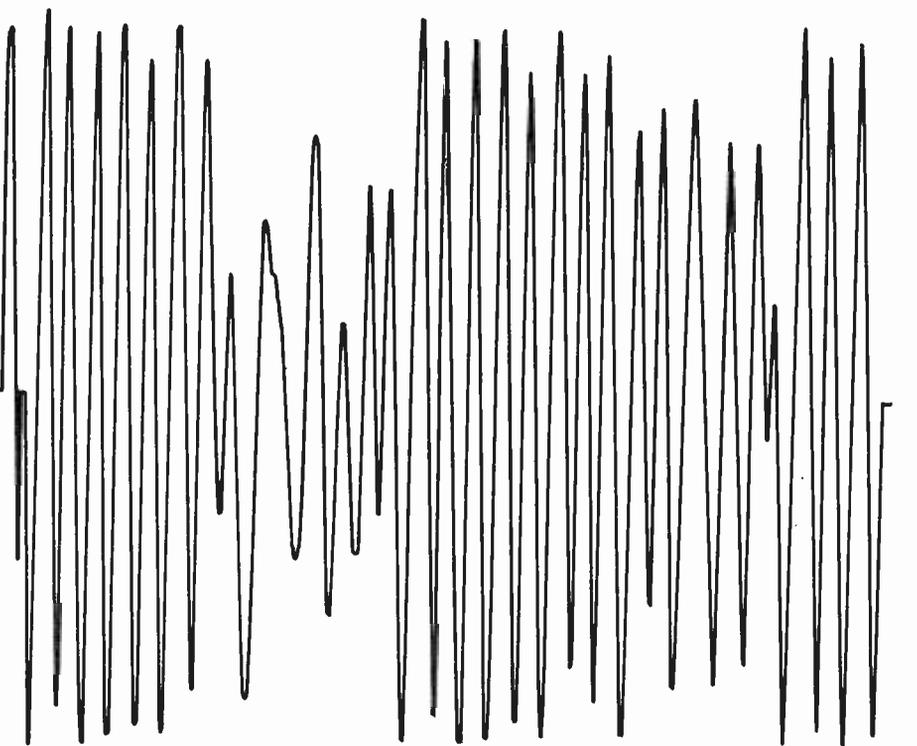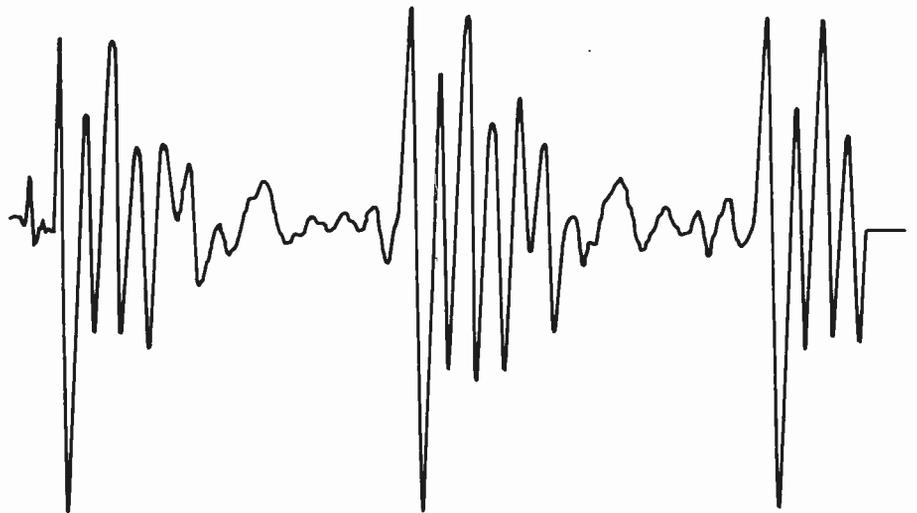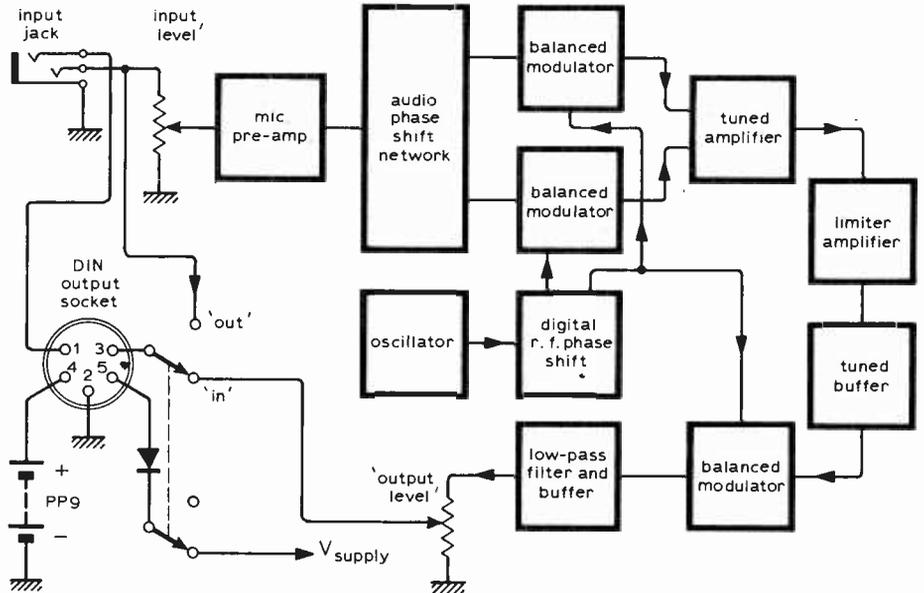

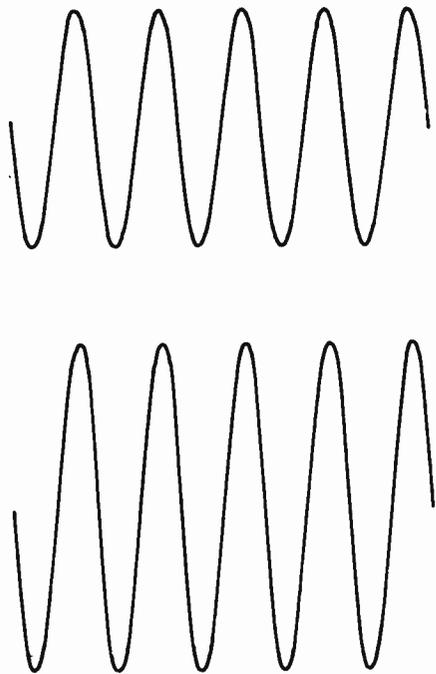


Fig. 8. Top: output of Datong r.f. clipper with input sinusoid just below clipping threshold. Bottom: same but input level 20dB above clipping threshold.

moved by an audio filter after the demodulator. In contrast, if the clipped s.s.b. signal is to be radiated directly, signals outside the information bandwidth must be reduced to a very low level to avoid radiating interference. This requires that a high-performance quartz crystal, ceramic, or mechanical filter be fitted. The high cost of such filters more than compensates for the cost of the duplicated circuitry in the "audio in/audio out" type of device.

To summarize, it can be said that a.f. clippers provide a useful improvement in average-to-peak ratios at the cost of quite severe distortion. They also have a fundamental disadvantage when used with s.s.b. transmitters.

A.f. speech compressors are good for maintaining a constant peak speech level despite different speech volume levels or different speakers, but are not very effective in raising the average-to-peak ratio.

R.f. speech clippers also compensate for different speech levels but at the same time give a big increase in average-to-peak ratio with negligible apparent distortion. Provided they are of the "a.f. in/a.f. out" type they are suitable for all modulation modes.

References

1. D. A. Tong, "Theoretical intermodulation distortion levels resulting from clipping a two-tone s.s.b. signal; with a note on the effects of crossover distortion", *Wireless World*, to be published.
2. L. R. Kahn, "The use of speech clipping in s.s.b. communications systems", (1957) *Proc. I.R.E.*, 45.2, 1148-9.
3. G. O. Herrick and H. W. Fallis, "A new approach to speech clipping for international broadcasters", I.E.E. Conference Publication No 69, International Broadcasting Convention (1970) 21-23.

Literature Received

ACTIVE DEVICES

A 24-page catalogue from EMI-Varian lists over 350 microwave devices, and includes information on the company's capabilities in p.c. aerials, ceramics, power supplies and pulse modulators. EMI-Varian Ltd, 248 Blyth Road, Hayes, Middx. WW401

Intel are to publish a bi-monthly technical magazine on their range of memories, microcomputers and m.o.s. devices. The magazine, *Intel News*, is available free from Intel Corp. (UK) Ltd, Broadfield House, 4 Between Towns Road, Cowley, Oxford WW402

Three leaflets from Brimar describe oscilloscope graticules, a 14-cm data display tube and a range of c.r.t. deflection yokes. Thorn Radio Valves & Tubes Ltd, Mollison Avenue, Brimsdown, Enfield, Middx. EN3 7NS WW403

Abridged data on the AEI range of microwave semiconductor and modules is contained in the new short-form catalogue from AEI Semiconductors Ltd, Carholme Road, Lincoln, LN1 1SG . . WW404

We are informed that Semiconductor Specialists have available the new Siliconix catalogues and price lists. New products include the dual-gate f.e.t.s and 3½-digit meter circuits. Semiconductor Specialists (UK) Ltd, Premier House, Fairfield Road, Yiewsley, West Drayton, Middx. WW405

A brochure from EMI describes a range of magnetically-focussed image intensifier tubes for use in spectroscopy, X-ray and electron diffraction and other low-light investigations. The publication is obtainable from EMI Electronics Ltd, Electron Tube Division, 243 Blyth Road, Hayes, Middx. . . WW406

PASSIVE DEVICES

Rastra have sent us a leaflet on the AUGAT range of individual pin sockets for i.c.s and a series of feed-through terminals. Catalogue 273 is obtainable from Rastra Electronics Ltd, 275-281 King Street, Hammersmith, London W6 9NF. WW407

A range of connectors for printed-circuit use and some multi-way plugs and sockets are illustrated on a wall-chart from Vareloco, which gives full specifications. Hand tools are also featured, as is a modular racking system. Vareloco Ltd, Exning Road, Newmarket, Suffolk. WW408

A leaflet-cum-wallchart, in colour, which is also a short-form catalogue of knobs, dials and turn-counting mechanisms, is obtainable from Argo Electronic Components Ltd, 28(b) Hamlet Court Road, Westcliff-on-Sea, Essex. WW409

The range of OT toroidal transformers by Avel Lindberg is described in leaflet AL4.71. The transformers are rated at between 15 to 500VA and are equipped with flying leads. Dimensions of the 15VA model are 57mm outside diameter, 36mm deep, with a central fixing hole. Avel-Lindberg, South Ockendon, Essex, RM15 5TD. WW410

A new brochure on the range of aerosol chemicals and lubricants has been published by Electrolube Ltd, Oxford Avenue, Slough, Bucks SL1 4LB. . . WW411

Aluminium "foil" or strip for coil winding is described on technical data sheet No. M204 from Rolled Products Division, British Aluminium Co. Ltd, Phelps House, Heath Road, Twickenham, Middx. WW412

GENERAL CATALOGUES

The new RS Components catalogue for Dec, 1974 to March, 1975 is now with us, new products this time including new 20VA transformers, plastic cabinets, displays, a voltage regulator and several others. RS Components Ltd, PO Box 427, 13-17 Epworth Street, London EC2P 2HA (on company letter-head).

The new Heathkit catalogue is now published. The kits are produced for a wide range of equipment for the consumer and for industrial and professional use. New models include a digital clock-cum-radio, a calculator, engine tuning equipment and several others. Heath (Gloucester) Ltd, Gloucester GL2 6EE. WW413

A publication entitled "Weir—The Facts" is a 16-page brochure on the company's capabilities in proprietary and custom-built electronic equipment. Available from Weir Electronics Ltd, Durban Road, Bognor Regis, Sussex. WW414

EQUIPMENT

A brochure giving specifications and installation information on the Data Sense 300 series of load cells has been sent to us by Transducers (CEL) Ltd, Trafford Road, Reading. WW415

Analogue multiplexers in the c.m.o.s. technology are fully described in a leaflet MPC80, MPC168 from Burr-Brown Research Corp. The units feature 7.5mW standby power, break-before-make switching and a two-microsecond settling time to within 0.1%. International Airport Industrial Park, Tucson, Arizona. WW416

The new catalogue of measuring instruments made by EIP, Exact, Cushman and Dana is now available from Dana Electronics Ltd, Collingdon Street, Luton, Beds. WW417

A guide to manufacturers and service organizations working in the field of digital electronic systems—the System Product Guide 1975—has been produced by Gershire Ltd, 103 Kent Road, Dartford, Kent, and is available from the publishers at £4.50.

The complete range of Pye and Philips broadcasting equipment, including cameras, telecine, audio gear and transmitters, is covered by the new Pye TVT catalogue, which is available from John Hawes, Publicity Manager, Pye TVT Ltd, Coldhams Lane, Cambridge. WW418

Oxford Electronic Instruments have sent us a leaflet on the Fenlow 710-A digital voltmeter—a 4½-digit instrument, which tracks the mains frequency to retain an 80dB series-mode rejection ratio from 49-51Hz. The leaflet is obtainable from Oxford at Osney Mead, Oxford OX2 0DX. . . WW419

We have received a brochure from D. A. Pitman on their range of Gastec gas detector tubes, including a new one for use with vinyl chloride. The Gastec system uses a piston-type volumetric pump, in conjunction with a range of 72 tubes. D. A. Pitman Ltd, Mill Works, Jessamy Road, Weybridge, Surrey. WW420

Standard impulse generators for the simulation of lightning and other transients in the range 200 to 3000kV are described in a leaflet by Hipotronics, Brewster, NY, USA. WW421

Modular r.f. shielded enclosures in the L3000 series are described in a brochure from Belling and Lee Ltd, Great Cambridge Road, Enfield, Middx. WW422

A wide range of strain gauge transducers and associated instrumentation for measurements of pressure, flow and level is dealt with in a 110-page catalogue from Marketing Services Department, Siemens Ltd, Great West House, Great West Road, Brentford, Middx. WW423

Univac signal processing equipment, a transient recorder and a power line disturbance monitor are briefly described in a short catalogue from Data Laboratories Ltd, 28 Wates Way, Mitcham, Surrey CR4 4HR. WW424

Performance characteristics and applications information on the DMC 800 series voltage-to-frequency converters (27 models) are given in an eight-page catalogue from Amplicon Electronics Ltd, Lion Mews, Hove BN3 5RA. WW425

We have received from MI two leaflets describing equipment in the Autotest range of automatic test systems, one covering r.f. testing and the other on printed-circuit boards. Marconi Instruments Ltd, St. Albans, Herts. WW426

Figure-of-merit for front-end selectivity of f.m. tuners

by Gordon J. King

Gordon J. King (Enterprises) Ltd

The documents of the British Standards Institution (BSI) and the Institute of High Fidelity (IHF, American) under BSI 4054:1966 and IHFM-T-100 respectively, along with others, describe methods for measuring and expressing the performance of a.m. and f.m. radio receivers and tuners, but in several areas these are dated with respect to state-of-art designs and the requirements for the contemporary f.m. tuner in particular.

With the advent of commercial radio broadcasting and the increasing utilisation of Band II for f.m. broadcasts, the ability of an f.m. tuner to respond, without interference, to a required signal in the presence of strong interfering signals is assuming increasing importance. A tuner hitherto operating from aerial signals of moderate level (*circa* 0.5 to 3mV p.d.) due to the three BBC transmissions and possibly the "local" f.m. station, might suddenly be subjected to an additional, more powerful signal due to the launching of a nearby commercial f.m. station, this being aggravated by lack of station co-siting.

The degree of susceptibility of a tuner in this respect is determined by both the large-signal handling performance of the r.f. stage and the selectivity and quality factors up to the mixer. A tuner with inadequate front-end selectivity, therefore, might exhibit spurious responses within the tuning range or coincident with the frequency of the wanted signal, a typical example being image response. Insufficient signal handling capability of the input devices can also encourage increasing intermodulation, due to decreasing linearity of the transfer characteristic. Cross-modulation in general is not such a big problem with f.m., of course, since this can only occur if the interfering signal has a.m. components, though this is not to imply that all interfering signals will be free from amplitude modulation. Moreover, if the i.f. selectivity is also poor, adjacent signal intermodulation products might encourage a warbling type of interference on stereo.

One solution, of course, would be to attenuate the aerial signal, but unless a frequency-selective attenuator is used, (and one writer has advocated the use of a tunable notch filter with a tuning control separate from that of the main

tuning for notching out a strong, unwanted adjacent channel signal!) required signals of moderate level could be reduced sufficiently in level to impair the signal-to-noise ratio, particularly on stereo. Another solution might be an aerial of greater directivity allowing orientation for maximum discrimination against an unwanted signal, but this is not always the answer because a different orientation may be required for the least multipath distortion.

The real solution, of course, lies in the design of the receiver or tuner. The chief offender is the simple receiver whose front-end consists of a not particularly linear r.f. amplifier operating at low emitter current with an aperiodic input from the aerial and proceeded by a solitary variable tuned circuit to the mixer. Such simplicity is not found in hi-fi tuner design, however, the least in this type of design being two variable-tuned circuits up to the mixer (three in all, including the local oscillator tuning). The next step up the scale is the design with three variable-tuned circuits from aerial to mixer with possibly dual-gate m.o.s. f.e.t.s for r.f. amplification and mixing. The square-law input characteristic of this type of transistor makes it particularly useful where a high degree of spurious response suppression is required and, of course, it is the ideal law for low-noise mixing. It has recently been demonstrated, however, that a bipolar transistor operating at 5mA, I_c can exhibit excellent linearity¹ and large-signal handling performance, though f.e.t.s, when carefully biased, are still regarded by some workers as the ultimate in the present state of the art. A dual-gate f.e.t. as mixer gives a good isolated input for the local oscillator signal and avoids oscillator pulling problems, but again¹ it has been demonstrated that a low cost Mullard BF245 f.e.t. can also be arranged for very acceptable results in this respect (see later).

Noise performance and hence usable sensitivity are not improved much by the use of two r.f. stages, but this technique is sometimes adopted to facilitate the introduction of an additional variable-tuned circuit or bandpass pair. Expensive f.m. tuners sometimes employ four or even five variable-tuned circuits in front of the mixer

and dual-gate m.o.s. f.e.t.s for r.f. amplification and mixing, along with an oscillator buffer stage to minimise oscillator pulling. Maximum usable sensitivity threshold (just below 1 μ V p.d. 75 Ω) is being achieved by some top-flight designs, and more recently, attention has been directed towards generally improving the input dynamic range.

The various tests for measuring the spurious responses of f.m. tuners are well known, as are those for measuring the IHF adjacent and alternate channel selectivity. To supplement the latter in terms of front-end selectivity performance the author, in collaboration with Ted Rule*, set out to devise a simple "figure of merit"-test based on the use of two generators with the result being referred to the IHF usable sensitivity. This test, of course, does not measure the intrinsic large-signal handling capability of the front-end (for this a more elaborate test setup with spectrum analyser is often used), but it does fairly reflect the overall goodness of the front-end selectivity and thus provide a fair impression of the spurious response interference likely from a front-end of given transistors and design. It is meant to complement rather than supersede the more conventional spurious response tests such as i.f. and image rejection ratios, half i.f. rejection, etc., and it has also been found to correlate more meaningfully with the interference obtained from a multiplicity of signals fed to tuners from a six-over-six aerial array.

The test set-up is given in Fig. 1 where two v.h.f. generators are combined in a matched T-pad to the input of the tuner under test. Tuner output is monitored on the y1 beam of an oscilloscope while being applied to the input of a distortion factor unit. The output of the distortion factor unit is coupled to an audio millivoltmeter through a decade attenuator, the signal at this point being monitored on the y2 beam of the oscilloscope.

IHF usable sensitivity

The first test is for IHF usable sensitivity, which is conducted with generator No. 1

*Armstrong Audio Ltd.

switched off. Generator No. 2 is adjusted for about 1mV, e.m.f. at f_2 which, as will become apparent later, should be around 88MHz†, and the signal is modulated 100% (i.e., ± 75 kHz deviation) at 400Hz or 1kHz. The distortion factor unit is switched on and set to the "set 100%" position and the decade attenuator adjusted for a convenient 0dB datum on the audio millivoltmeter, ensuring that the tuner is accurately adjusted to the generator

†IHF standard test frequencies are 90, 98 and 106MHz

signal. The distortion factor unit is then switched to the "read" position and its notch tuned and balanced to the frequency of the f_2 modulation, while reducing the audio millivoltmeter attenuation correspondingly.

The IHF usable sensitivity is the least p.d. at f_2 required at the tuner input for 30dB ratio (as established by the decade attenuator) between the "set 100%" and "read" positions. It is generally necessary to optimise the tuning for the least distortion factor (i.e., noise plus total harmonic distortion). The IHF usable

sensitivity (in μ V or dB) should be noted in terms of setting of the attenuator of generator No. 2.

Generator No. 1 is next switched on and its frequency (f_1) adjusted so that $f_1 - f_2$ equals the i.f., which is usually close to 10.7MHz, though some exploring may be necessary since tuners with ceramic i.f. filters may be slightly removed from the nominal. Attenuator No. 1 is adjusted for 50mV p.d. at the tuner input and, initially, attenuator No. 2 is adjusted likewise. If both generators are modulated and the tuner adjusted away from f_1 or f_2 the y1 trace will display a modulation beat when the mixer yields the i.f. from $f_1 - f_2$. The modulation of generator No. 1 is then switched off, leaving only the modulation of f_2 .

The scheme is then to run through the same exercise as for IHF usable sensitivity when the tuner is adjusted to $f_2 + 400$ kHz. A greater difference may be necessary where the i.f. selectivity is poor to avoid blocking. The dB ratio for the "figure of merit" can be obtained from attenuator No. 2 by subtracting the dB setting for the IHF usable sensitivity from the dB setting finally used.

The display on y2 trace is useful for ensuring that it is the noise-plus-distortion which is giving the readout!

A very simple tuner with aperiodic aerial coupling and single variable-tuned circuit to the mixer will exhibit little more than 20dB ratio. Two variable-tuned circuits increase the ratio to 30-35dB, while three variable-tuned circuits can take the ratio up to 60dB or more, depending on the quality factors of the selectivity. One tuner tested with four variable-tuned circuits (using mechanical capacitors as

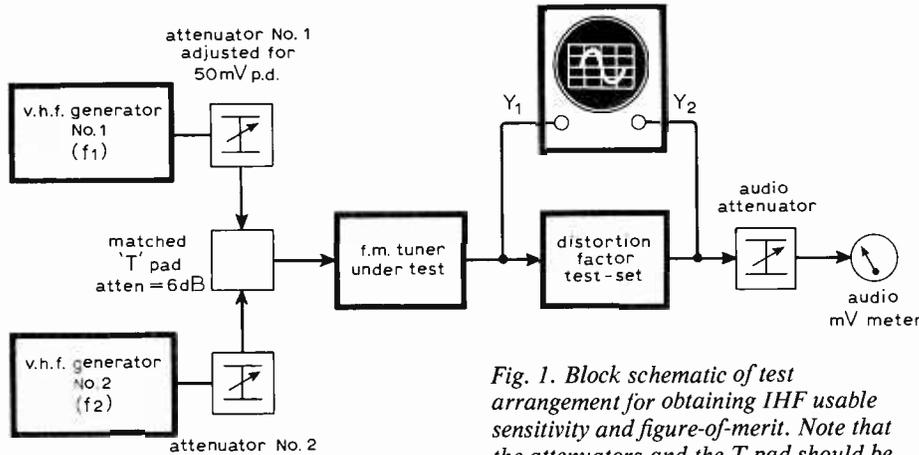


Fig. 1. Block schematic of test arrangement for obtaining IHF usable sensitivity and figure-of-merit. Note that the attenuators and the T-pad should be matched to each other and to the aerial input of the tuner.


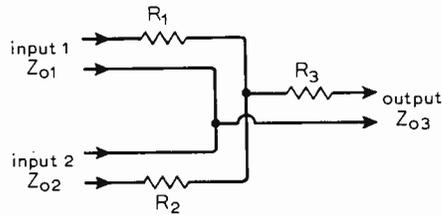


Fig. 2. Simple matched T pad for combining the outputs of two generators. When $Z_{01} = Z_{02} = Z_{03}$, $R = R_2 = R_3$, such that $R_1 = Z_{01}(n-1)/n+1$, where n is the number of inputs (two in this case). Insertion loss is 6dB.

Fig. 3. Mullard f.m. front-end referred to in the text.

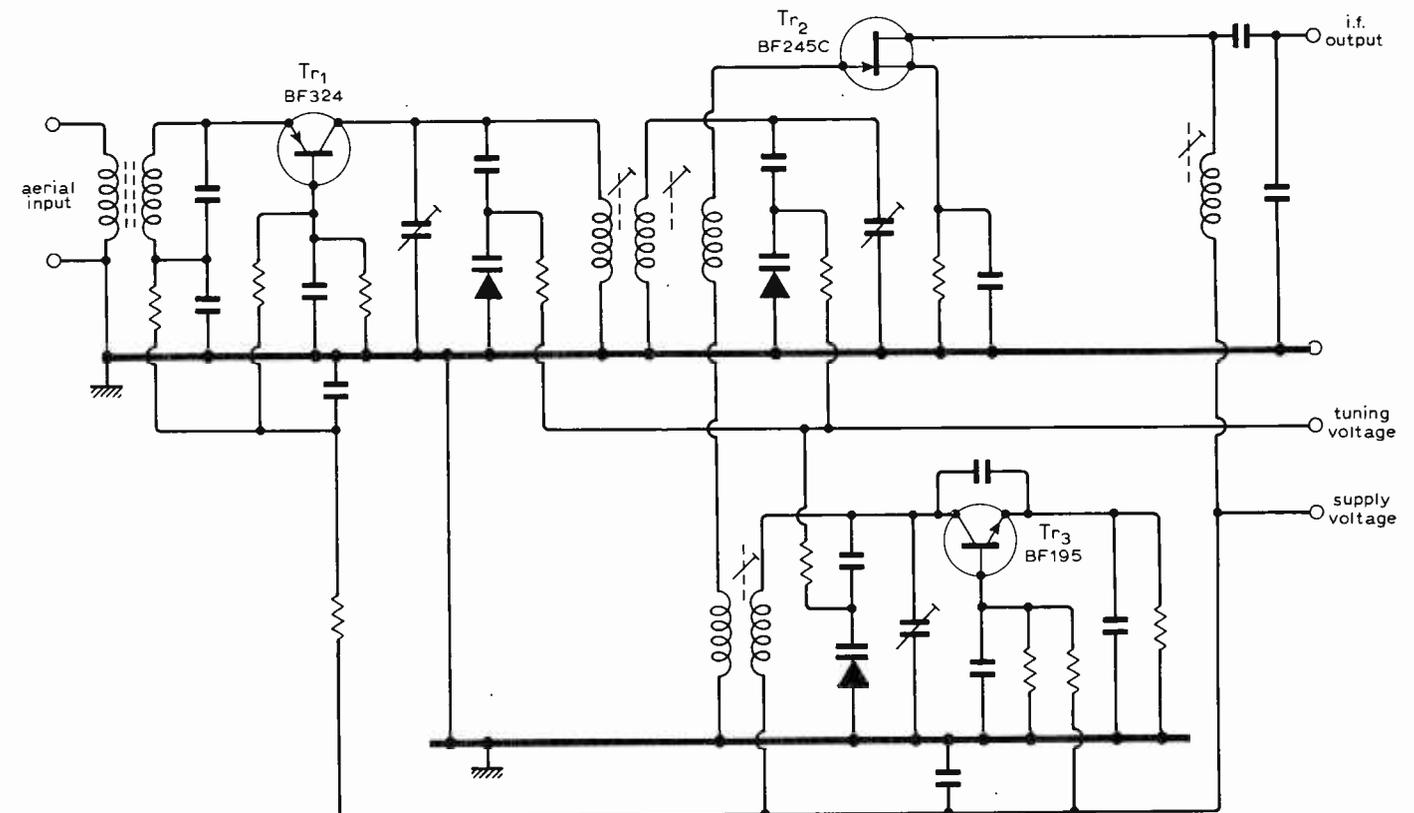

distinct from varicaps) up to the mixer, returned a ratio as high as 100dB.

Detailed evaluation of other second-order and higher-order intermodulation products, of course, requires different signal combination using the receiver (i.e. BS 4054:1966, 43.1) or a spectrum analyser to detect them. Reference 1 gives a set-up for measuring cross-modulation and hence intermodulation, since they are shown to be related effects, using three generators in a simulated single-sideband arrangement, in conjunction with a spectrum analyser.

One practical manifestation of third-order intermodulation arises from the three signals of Radios 2, 3 and 4 of f_2 , f_3 and f_4 , such that $f_2 + f_4 - f_3$ falls at f_3 . Thus tuners prone to third-order products will tend to exhibit Radio 3 interference when operating in areas where the signal fields of Radios 2, 3 and 4 are very strong.

The almost exactly square-law of f.e.t.s helps to reduce this trouble, and hi-fi tuners using correctly biased dual-gate f.e.t.s with good front-end selectivity are capable of operating in most areas without interference and without the need for aerial attenuation.

Another cause of interference on stereo results from the sensitivity of some decoders to near harmonics of the 38kHz switching frequency which can be present at the output of the f.m. detector under a number of interference conditions. As the audible note so produced is perturbed by the modulation, a warbling type of interference results, which has become known as "birdies". This problem is solved, or at least significantly reduced, by the inclusion of the low-pass filter (f_0 circa 55kHz) between the f.m. detector and the stereo decoder, and many manufacturers are now fitting this.

As already mentioned, local oscillators and oscillator pulling are other aspects of f.m. tuner design that are receiving attention. An interesting design by Mullard¹ for improving the signal handling capability and reducing oscillator pulling at relatively low cost includes a BF254C f.e.t. for almost square-law mixing, a loosely-coupled oscillator feed to the gate, giving freedom from oscillator pulling for aerial signals as high as 250mV e.m.f., 75 ohms; and a bipolar BF324 common-base r.f. amplifier which, at 5mA I_c , has a large signal-handling capability and excellent linearity, thereby—from the input overload point of view—obviating the need for input selectivity, which helps from the noise aspect. The oscillator uses a BF195 also in common-base mode and operates at 1mA, I_c and 9V, V_{ce} for low noise and good stability. As shown in the circuit in Fig. 3, varicaps are used for bandpass tuning while the r.f. input is aperiodic.

Reference

1. Mullard Technical Communications, Vol. 12, No. 119, July 1973. Also issued as Application Note TP1395.

Meetings

LONDON

4th IEE—"Earth survey and weather applications of satellites" by R. Watson-Laing at 17.30 at Savoy Pl., WC2.

4th IEE—"Air traffic control in the vicinity of a major airport" by S. Ratcliffe at 17.30 at Savoy Pl., WC2.

5th IEE—"Technology push versus market pull—the horns of the designer's dilemma" by D. A. E. Pannenberg at 17.30 at Savoy Pl., WC2.

5th IERE—"Hybrid computers and applications" by Dr R. L. Davey at 18.00 at 9 Bedford Sq., WC1.

6th RTS—"The role of law in today's environment of international broadcasting" by H. Bloom at 19.00 at London Weekend Television, South Bank TV Centre, Upper Ground, SE1.

11th AES—"Some acoustic thoughts on light-weight partitions" by P. Lord and "The use of acoustic scale models" by B. Day at 19.15 at the IEE, Savoy Pl., WC2.

12th IERE—"Channel approach aid for Milford Haven Conservancy Board" by A. P. Tuthill at 18.00 at 9 Bedford Sq., WC1.

18th IEE—Discussion on "Area Navigation" opened by J. Inglefield and G. Belcher at 17.30 at Savoy Pl., WC2.

19th IEE—Discussion on "Oil rig instrumentation" opened by K. Gibbs, J. Ingram, D. Lomas and G. Thurgood at 17.30 at Savoy Pl., WC2.

20th IEE—"The social computer", Faraday lecture by D. H. Pitcher at 18.00 at Central Hall, Westminster, SW1.

20th RTS—"A time multiplexed machine control system for broadcast television" by K. Allcock and J. Barrett at 19.00 at London Weekend Television, South Bank TV Centre, Upper Ground, SE1.

21st IEE—"The social computer", Faraday lecture by D. H. Pitcher at 18.00 at Central Hall, Westminster, SW1.

26th IEE—"Fast megavolt pulse generators" by J. C. Martin at 17.30 at Savoy Pl., WC2.

26th IERE—"A novel low attenuation waveguide" by Prof. P. J. B. Claricoats at 18.00 at 9 Bedford Sq., WC1.

BLANDFORD

11th IERE—"Autonull"—the suppression of large interfering signals in single- and multi-equipment installations" by M. M. Zepler at 18.30 at the School of Signals, Blandford Camp.

BIRMINGHAM

19th RTS—"The opening of a commercial radio station" by David Pinnell at 19.00 at the BBC Broadcasting Centre, Pebble Mill Road.

27th IEETE/IES/IHVE/ASEE—Symposium on "Integrated environmental design" at 19.00 at the Bing Kendrick Suite, University of Aston, Gosta Green.

CARDIFF

5th IERE/IEE—"Digital techniques in broadcasting" by Dr C. J. Dalton at 19.00 at the Chemistry Lecture Theatre, Room 164, U.W.I.S.T.

ENFIELD

25th IEE—"The generation of electricity from sunlight" by P. Howell at 18.30 at Middlesex Polytechnic, Queensway.

FARNBOROUGH, Hants

6th IERE—"Bubble memories" by Dr J. R. Fairholme at 19.00 at Farnborough Technical College.

GLASGOW

25th IEETE—"Emergency stand-by generators" by H. A. Smedley at 19.00 at the Royal Stuart Hotel, Jamaica Street.

GUILDFORD

12th IEE—"An Institution of Engineers?" by Dr G. F. Gainsborough at 19.30 at C.E.G.B., Burymead House, Portsmouth Road.

IPSWICH

5th IERE—"Radar approach to weather forecasting" by Prof. E. Shearman at 18.30 at Ipswich Civil College.

LEEDS

20th IERE/E & CS—"Oracle—information by domestic TV" by G. A. McKenzie and P. R. Hutt at 18.30 at Yorkshire TV Studios.

LEICESTER

6th IEE—"The social computer", Faraday lecture by D. H. Pitcher at 14.30 and 19.15 at the De Montford Hall.

LIVERPOOL

11th IEETE—"Thyristor controls for industry" by C. Smith at 19.30 at MANWEB Social Club, Thingwall Road.

12th IERE—"Solar energy" by W. R. Crooks at 19.00 at North East Liverpool Technical College.

LLANDAFF

12th SERT—"The RBM Z179 110° colour chassis" (lecturer from Rank Radio International) at 19.15 at Llandaff College of Technology.

MAIDSTONE

12th IEETE—"Protection against electrocution and electrical fires" (speaker from Allen West-EAC Ltd) at 19.30 at the Royal Star Hotel, High St.

MALVERN

5th IERE—"Active filters" by Dr D. R. Wilson at 19.30 at The Foley Arms.

PLYMOUTH

6th IERE/IEE—"Television engineering—a look into the future" by M. Cox at 19.00 at the Main Lecture Theatre, Plymouth Polytechnic.

PRESTON

17th IEETE—"The watchful eye—computer monitoring in colour" by B. Baker and D. Wood at 19.15 at Preston Polytechnic, Corporation St.

READING

12th IEE—"CAD of type 2 phase lock loops" by P. Atkinson and A. Allen at 19.30 at the J. J. Thomson Physical Laboratory, University of Reading, Whiteknights Park.

SHEFFIELD

11th IEE—"The social computer", Faraday lecture by D. H. Pitcher at 10.15, 14.30 and 19.30 at the City Hall.

SOUTHALL

27th IEETE—"Understanding noise" by L. Minikin at 19.30 at Southall College of Technology, Beaconsfield Road.

SOUTHAMPTON

12th IERE—"Electronic ignition—is it worth it?" by Dr. E. M. Stafford at 19.30 at Southampton College of Technology, East Park Terrace.

19th SERT—"Aspects of electronic copying" by R. Hickman at 19.30 at Southampton College of Technology.

26th IERE—"Time series feature detection" by Dr D. W. Thomas at 18.30 at the Lanchester Theatre, Southampton University.

STONE, Staffs

20th IERE/IEE/IPOEE—"Communications—bit by bit" by H. B. Law at 19.15 at P.O. Training Centre, Duncan Hall.

Tickets are required for some meetings: readers are advised therefore to communicate with the society concerned.

World of Amateur Radio

All-solid-state stations

Recently in contact on 7MHz with DJ6SI in Cologne I was interested to discover that his very good signals were coming from one of the small "Atlas 180" all-transistor transceivers. This particular unit provides up to 180 watts p.e.p. on 1.8 to 14MHz with an s.s.b. filter exciter on 5520kHz. It is one of several compact units employing multiple r.f. power transistors and broadband techniques that have appeared on the amateur market in the past year or so; others include the Swan SS-200 and the new Heathkit SB104 which has just been launched in the United States. This covers all the amateur h.f. bands from 3.5 to 29.7MHz with an r.f. power output of up to 100 watts p.e.p. (also providing a low-power output of 1 watt) for upper and lower sideband or 100 watts c.w. The transmitter and receiver tuned stages are broadbanded and it is claimed that, for example, it takes less than 10 seconds to change from c.w. on 3500kHz to s.s.b. on 29MHz. Another feature is direct six-digit read-out of frequency. With some 31 integrated circuits, 75 discrete transistors and 171 diodes and with a total of some 2800 components this unit must be one of the most ambitious kits ever produced for home construction; in its basic form it operates from 12-volt car batteries and measures only 6 by 14 by 14 inches.

Artificial radio aurora

In his 1966 inaugural address as president of the IEE, J. A. Ratcliffe noted that when the long-wave broadcasting station at Droitwich is switched on the temperature of the electrons at a height of about 100km increases by about 45°C. This technique of using radio transmitters to heat up the electrons in the ionosphere is being investigated in the United States and the USSR as a means of producing artificial radio aurora to permit scatter communication on frequencies up to u.h.f. over distances of some hundreds of miles. Details of this work, on behalf of the US Department of Defence, have recently been given in two American amateur journals with a view to further participation by amateurs. Much of the basic research

has been done by the Institute for Telecommunications Sciences (ITS) and the Stanford Research Institute and has already shown that this propagation mode could be of interest to amateurs. For example, on May 11, 1972 K7PXI in Phoenix was heard via ARA in Socorro, New Mexico. In these tests very high-power h.f. transmissions (typically about 5MHz) are beamed upwards with an e.r.p. of the order of 5 megawatts, raising the temperature of the electron gas, forcing it to expand along the magnetic field and so permitting scattering from the field-aligned irregularities.

The tests have shown that the effect on forward-scatter signals is almost coincident with the switching on and off of the "heater" transmitter both in the F-layer and the E-layer. High-power transmitters suitable for this work currently exist at Plateville, Colorado and at Arecibo, Puerto Rico and also in the USSR at Gorki.

Repeaters and beacons

With at least five 144MHz f.m. repeaters now operational or testing in the UK (GB3SN Four Marks, Hampshire; GB3BC Mynydd Machen, South Wales; GB3PI Barkway Ridge, Cambridge; GB3LO Crystal Palace, London; and GB3MH Malvern Hills, Gloucester) and half a dozen more proposals at various stages including a recent attempt to gain support for a repeater in the Chelmsford area of Essex, this is currently one of the fastest growing areas of amateur radio. But, for a variety of reasons, including the fear that the operation of repeaters with simple hand-held and mobile equipment may diminish interest in the more advanced equipment needed for tropospheric and other long-distance modes, a number of British amateurs appear to be firmly opposed to this development. One even hears persistent stories of deliberate interference to the operation of the repeaters. In the United States an important relaxation in the regulations now permits operation through more than one repeater simultaneously, thus opening the way to the establishment of v.h.f. trunk networks stretching across the Continent.

GB3SN, the repeater of the UK FM Group (Southern) at Four Marks, has been undergoing trials as a beacon on 145.725MHz before coming into operation as a repeater. At the time of writing this is controlled by a time-switch which switches it off for a couple of hours in the early morning and again from 1800 to 2015 GMT. Early reports indicate wide coverage and reliable operation.

Despite some lack of sensitivity the linear transposers on board Oscar 7 seem to be functioning well and one British amateur is reported to have been in contact with a station in California on the 432/145MHz unit. Frequencies for Oscar 7 are: Mode A uplink 145.85 to 145.95MHz, downlink 29.4 to 29.5MHz (beacon 29.5MHz); Mode B uplink 432.125 to 432.175MHz, downlink 145.925 to 145.975MHz (beacon 145.98MHz).

Additionally there is a beacon on 435.10-MHz. Mode A and Mode B repeaters are operated on alternate days.

A 28MHz beacon station, K6HME at Oceanside, California has been operating on 29.0MHz using a Swan SS-200 solid-state transmitter. A low-power 1-watt beacon operates on 28.150MHz from Hopkinton, Mass.

Slow-scan progress

Richard Thurlow, G3WW of March, Cambridgeshire, comments on the increasing interest in slow-scan television transmission in the United Kingdom. There are now at least 125 amateurs authorized for this type of transmission. In the first ten months of 1974, C. C. Robinson, G3IAI, had two-way s.s.t.v. contacts with amateurs in more than 70 different countries; the total for G3WW is now more than 60 and several overseas stations including VU2AIK and W4MS are over the 80 mark.

Although rather over 100 amateurs in Japan are permitted to use s.s.t.v., it is believed that the number will increase considerably quite soon as a large backlog of applications developed during some reorganization of the licensing departments.

In brief

Among the recent qualifiers for the 5-band DXCC award is Arthur Milne who recently celebrated holding his callsign G2MI for 50 years. The German amateur Rudolf Bluel, DL8AL also joined those with 50 years of operating. Originally TS4SAC, his callsigns have included EZ4SAB, D4BWT, D4QBT and 9S4AL and he was also one of the German amateurs who held German wartime licences in 1942-44 under circumstances that seem to have had something in common with the special G7 permits held by some prominent British amateurs in the closing stages of the war. According to *The Chiltern Carrier* (newsletter of the Chiltern Amateur Radio Club) a firm of Southampton stamp dealers has recently been offering for sale QSL cards commemorating the first 1.8MHz contacts between Tristan da Cunha and various other countries at prices between £4.50 (Brazil) and £7.50 (England)—the first time I have ever heard of anyone attempting to sell QSL cards in this way. A new 10kHz "window" for Japanese 3.5MHz stations, between 3793 and 3803kHz, is expected to increase the number of contacts on this band with European and American s.s.b. stations (normal Japanese 3.5MHz allocations are limited to 3500 to 3525kHz c.w. and 3525 to 3575kHz phone). The Australian amateur, Bill Hall, VK2XT, is believed to be the first station outside Japan to gain a JARL award for working all 644 Japanese cities. Several American states now have laws prohibiting the use of twin earphones while driving, although these regulations are apparently aimed at those using earphones for stereo and other entertainment.

PAT HAWKER, G3VA

Pseudo-random binary sequence generators

Used to construct fast, synchronous, programmable frequency dividers and a frequency synthesizer

by F. Butler, O.B.E., B.Sc., F.I.E.E., M.I.E.R.E.

A pseudo-random binary sequence generator (p.r.b.s.) alternatively known as a linear recursive sequence generator, (l.r.s.), is an assembly of bistables and exclusive-OR gates designed to produce a pulse sequence, of any desired length, in which individual pulses and spaces are randomly distributed over the sequence length. The bistables, in a shift-register configuration, are driven by a common clock pulse and each bistable drives the next in line. Outputs from certain stages, always including the last, are applied to an exclusive-OR gate, or to an array of such gates, the final output being taken back to the input of the shift register.

Illustrated in Fig. 1(a) is a general though not necessarily a practically useful method of connecting up such a system. The symbols for exclusive-OR gates have not been rigidly defined, nor has the terminology since the gates are also known as modulo-2 adders. Commonly-used symbols are shown in Fig. 1(b). Without using jargon, the properties of such a two-input gate are that when two identical inputs; 0 or 1, are applied the output is at one particular logic level and when the inputs are different, the opposite logic output appears. In tabular form these properties can be expressed digitally as:

1 + 1 = 0	or,	1 + 1 = 1
0 + 0 = 0	(equally)	0 + 0 = 1
1 + 0 = 1	valid)	1 + 0 = 0
0 + 1 = 1		0 + 1 = 0

A standardized way of writing the exclusive-OR addition or modulo-2 sum of two quantities has been agreed upon. It is expressed as $C = A \oplus B$ and is read as "C equals A circle-sum B". The above tables should be written in this way and, strictly speaking, one should differentiate between exclusive-OR and exclusive-NOR gates.

Before discussing practical circuits and applications, it will clear the ground if some of the statistical properties of linear recursive sequences are mentioned. The statements will be in the form of assertions, not backed by mathematical proofs, which would lead us into very deep water.

First, the maximum possible number of bits in the sequence generated by n bistables is $N = 2^n - 1$, one less than 2^n which might have been expected. The all-zero combination is inadmissible. If it occurs, the bistables latch or lock up and

the sequence stops. This condition must be avoided.

With large, but still practicable, numbers of bistables, very long sequences can be generated. For example, 60 stages give a sequence length of about 1.15292×10^{18} bits. Such long sequences can be used in enciphering digital signals. In any given sequence, remembering that the total number of bits is always odd, there are, as nearly as possible, equal numbers of 0's and 1's. There are half as many runs of two bits, one quarter as many runs of three, and so on. At the end of a cycle, the sequence starts again and gives another identical train of pulses. The student of Fourier will recognize that such a sequence is not truly random but is periodic with a period equal to the cycle length. It has a line spectrum with discrete frequencies which can be filtered out by suitable equipment.

Though superficially the l.r.s. resembles random noise, more so as the cycle length increases, true random noise has a band spectrum with components at infinitesimal frequency separation. If a complete sequence is compared, term by term, with a cyclically shifted version of itself, the number of pulse parity agreements and

disagreements, every possible pattern of n bits in the total sequence length N will appear once, and only once, at the outputs.

Exclusive-OR gates

Although these are available in packaged form, one integrated-circuit block containing four 2-input gates, it is instructive to see how they can be assembled from simple AND/OR or NAND/NOR gates. Fig. 2 shows in principle what has to be done, and how in practice, the scheme is implemented. By putting various inputs to the gate, the reader can verify that the exclusive-OR logical function is actually realized. If the two inputs A and B are taken from bistables, their complements \bar{A} and \bar{B} are normally accessible. The modulo-2 gate can then be simplified and assembled from three NAND gates only. A spare gate is then available in a quad package and can be used as an extra output buffer amplifier or inverter.

Practical generators

Integrated-circuit packages are currently available with quite large numbers of bistables assembled in shift-register form. Circuit blocks of this type, together with multiple modulo-2 gates will be used later

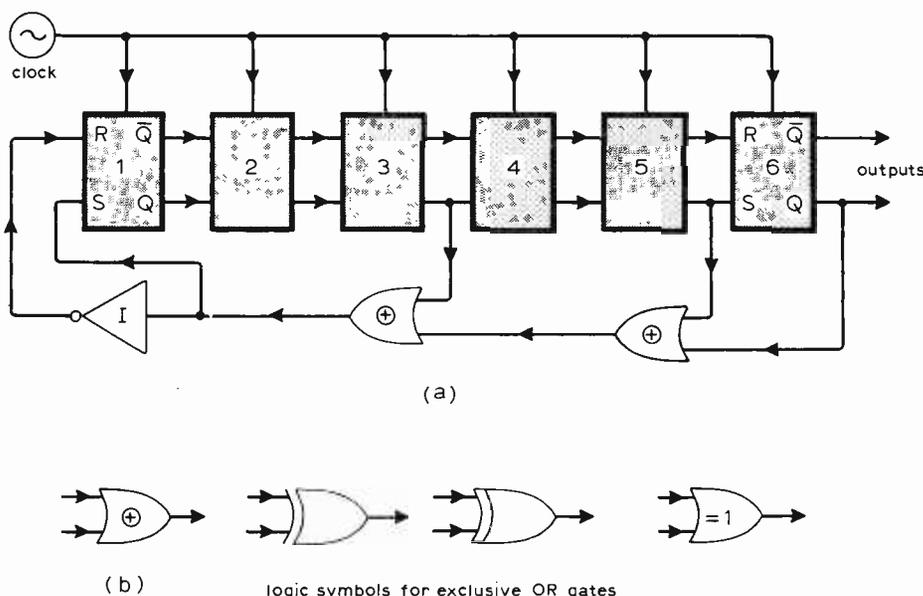


Fig. 1(a). P.r.b.s. generator using a shift register with exclusive-OR (modulo-2) feedback.

to produce long l.r.s. streams in an economical way but it is instructive to build one or two simple models with bistables and NAND-gates using d.t.l. logic. These blocks are inexpensive and readily available. Though slower than t.t.l. equivalents, they are fast enough for many purposes and are trouble-free in use. Clock frequencies up to 4MHz can be used with reasonably complex systems. A relatively simple but useful generator is shown in Fig. 3. Seven bistable stages are used to give a sequence length of 127 bits. Because both Q and \bar{Q} outputs are available from the bistables, the modulo-2 gate can be assembled from three of the four gates in a quad NAND-gate package, leaving one spare two-input gate for use as an inverter amplifier.

The d.t.l. bistables, SGS types 9945/9948, or their equivalents are basically R-S flip-flops but they can be used in the J-K mode by connecting the outputs back to the inputs. Direct set and clear inputs override other inputs, allowing the unit to be presented as required. The 945 unit has a higher value load resistor than the 948 and is better able to drive capacitive loads. The 948 has a faster pulse rise time.

The experienced user can wire up the complete generator directly on printed circuit board though it would be wise to check all units before assembly. Alternatively, plug-in holders can be used, making it easier to trace faults or to replace defective units. The clock source can be any type of oscillator, square-wave or sinusoidal, crystal-controlled or not, up to a frequency around 4MHz. Sinusoidal inputs must be squared up by Schmitt trigger or clipper circuits and must be

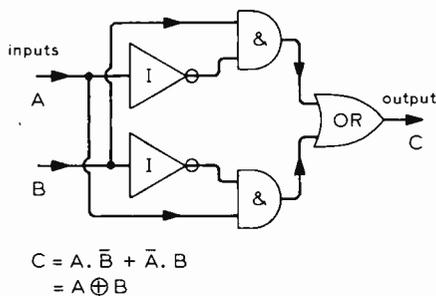


Fig. 2. Logic function and circuit realization of exclusive-OR (modulo-2) gate.

capable of driving the load presented by the seven bistables. The random sequence can be taken from any bistable output Q or \bar{Q} . Outputs from consecutive bistables are identical but delayed in time by one clock period. Because of its random nature it is rather difficult to lock the trace on an oscilloscope display but with perseverance it can be done, allowing the sequence to be examined visually.

It will be noticed that feedback to the exclusive-OR gate is taken from the sixth and last bistable in the register. The adjoining Table shows the requisite feedback connexions for sequences of different lengths. It should be mentioned that any feedback connexions will produce a sequence of sorts but to get the maximum possible length of $N=2^n-1$ bits, only certain arrangements are admissible. Those given are suitable though not unique. For example, in a seven-stage register, one feedback link must always be from the last stage. The other can be from stage 3, 4 or 6. Because both Q and \bar{Q} outputs


are accessible it is possible to use a simplified exclusive-OR gate. It will also be noticed that the output from this gate goes directly to one data input of the shift register. It is also applied to the other input through an inverter, which is in fact one of the four two-input NAND gates in a quad package. The other three gates form the modulo-2 adder.

Standard frequencies from pseudo-noise sources

The generator just described produces a pulse sequence which repeats after 127 bits, although the stream is random within this period. Suppose the clock frequency is exactly 127kHz, derived from a crystal-controlled source. Clearly a run of 127 bits repeats at 1,000 times per second and it follows that the fundamental frequency of the complex waveform is 1kHz. It has harmonics at all integral

Number of bistables n	Sequence length N	Feedback connexions
2	3	1, 2
3	7	2, 3
4	15	3, 4
5	31	3, 5
6	63	5, 6
7	127	6, 7
8	255	4, 5 and 6, 8
9	511	5, 9
10	1023	7, 10
11	2047	9, 11
12	4095	6, 8 and 11, 12
13	8191	9, 10 and 12, 13
14	16383	4, 8 and 13, 14
15	32767	14, 15

Fig. 3. Seven-stage p.r.b.s. generator.

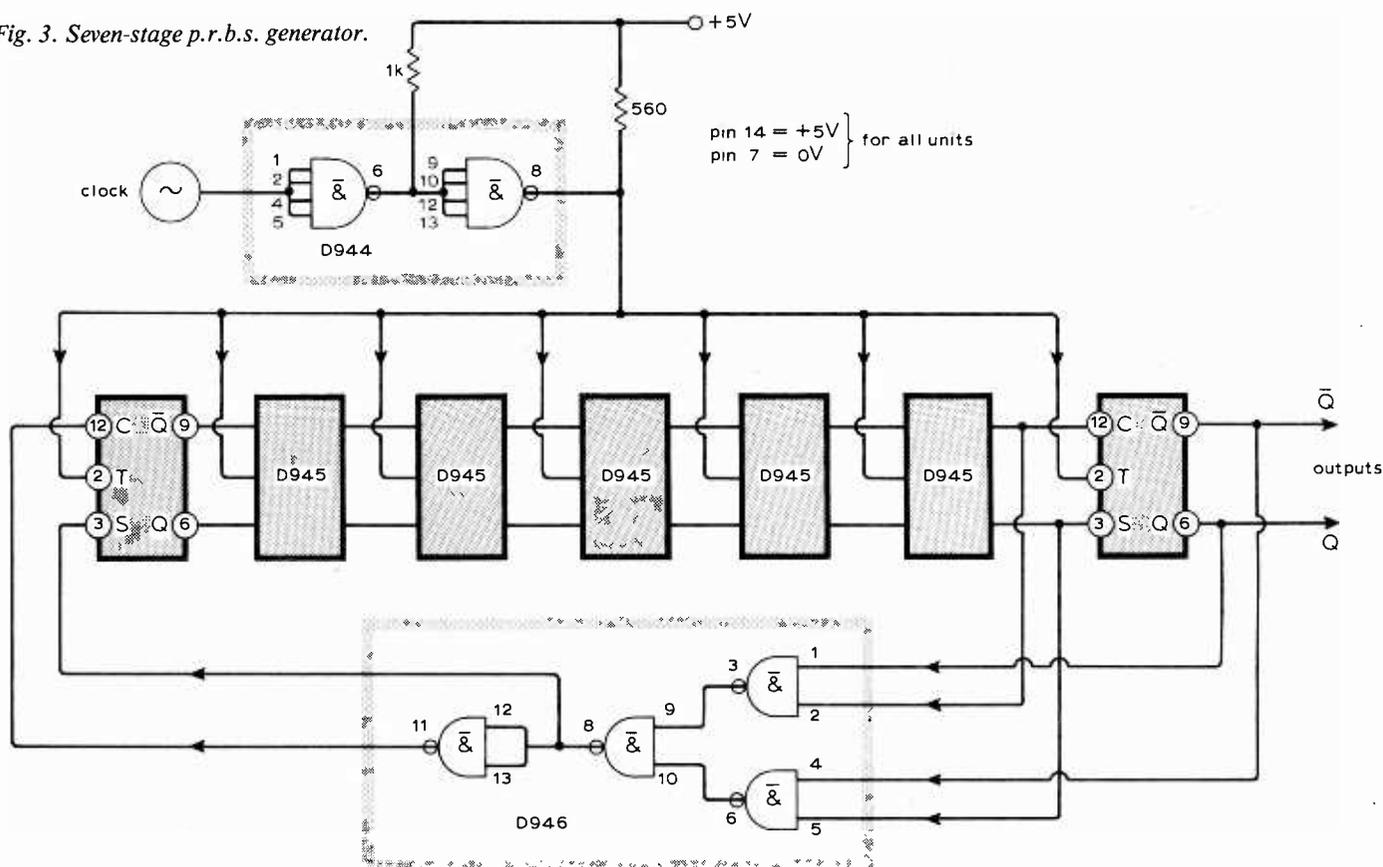

multiples of 1kHz and these can be picked out, one by one, using a sufficiently selective tunable amplifier or filter.

Mathematical analysis shows that the amplitude of the harmonics falls off in a predictable way, roughly as indicated in Fig. 4. The first zero occurs at 127kHz. It is well known that a train of narrow pulses with a stable recurrence frequency also has a spectrum of the same general form and the reader may well ask why one should construct a complex l.r.s. generator when something so much simpler would appear to do the same job. The advantage of the pseudo-noise source is that the harmonics are very much stronger because the power density of the noise spectrum is greater than that from a train of narrow pulses. Moreover, the amplitude of the higher harmonics falls off relatively slowly. Experience shows that with a clock frequency of 127kHz, strong harmonics up to 100kHz are available. Thus at least 100 standard frequencies of high stability can be picked out. The best equipment to do this is a wave analyzer. Such instruments commonly cover the band 0-50kHz with extremely high selectivity, bandwidths of ± 10 Hz to the -40dB points being typical.

If the 127kHz clock source is followed by several decade divider stages, the wave analyzer can easily pick out 100 frequencies between 0 and 1kHz in 10Hz steps, and 100 between 0 and 10kHz in 100Hz steps as well as the 1kHz series just discussed. The synthesized frequencies are extremely "clean", free from noise and undesirable modulation. A lower limit to the usable frequency separation of signals is set by the selectivity and calibration reliability of the wave analyzer. By using more decade dividers to achieve a low clock frequency, standard frequencies with periods of several minutes have been picked out by means of a gyrator, the waveform being checked with a chart recorder. The upper limit of frequency depends on the speed of the logic elements; 4MHz is easily achieved and 100MHz is not unreasonable as a clock frequency for use with the latest circuits.

Many laboratories already possess wave analyzers and the construction of a p.r.b.s. generator could hardly be simpler. The useful range of standard frequencies so derived is good enough for routine work such as checking receivers, calibrating oscillators and testing filters. The system can provide clock sources for digital work and can generate coherent signals on multiple frequencies, the freedom from spurious signals and responses being of particular value.

The wave analyzer functions basically as shown in Fig. 5, though a practical instrument incorporates many refinements. The complex signal to be filtered is fed to a mixer or balanced modulator along with a higher-frequency signal from a tunable oscillator. The difference frequency is picked out by a narrow-band crystal filter, amplified and applied to a second mixer, together with the same variable-frequency oscillator signal. The desired component of the complex signal is thereby restored

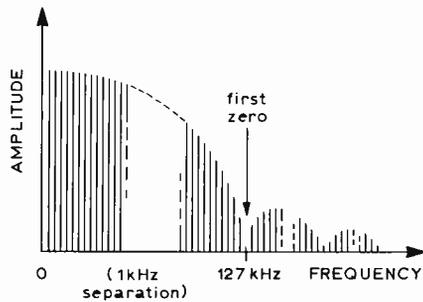


Fig. 4. Line spectrum of a 127-bit l.r.s. clocked at 127kHz.

to its original frequency but cleared of all other components. There is no degradation of signal frequency stability due to the v.f.o.. In the first mixer we derive $f_o - f_s$. In the second we recover $f_o - (f_o - f_s) = f_s$. This drift-cancelling technique is used in some communications receivers for much the same purpose.

It might be objected that the crystal-controlled clock frequencies are awkward, non-standard values but it is surprisingly easy to grind down readily-available crystals to the required size on a cast-iron lap using in turn coarse, medium and fine carborundum paste. Thus to produce 127kHz requires a stock 100kHz bar. Values such as 1023kHz are easily produced from a 1MHz standard, though of course it is impossible to modify glass-encapsulated units.

A solid state wave analyzer (illustrated), covering 0-150kHz has been built for use with l.r.s. sources as well as for the more usual applications of a tunable filter. A good deal of work is involved in the construction although, apart from the cost of the crystal filter, the instrument is not unduly expensive to build.

Programmable frequency dividers

The circuit of Fig. 3 is relatively easy to modify for use as a variable-ratio divider, programmable by a row of single-pole change-over switches, and hence adaptable for some forms of direct digital control.

In a normal shift register, initially loaded with a particular setting of bits, each clock pulse shifts the pattern along the register one bit at a time. This is also the case for a p.r.b.s. generator, except that the serial input to the register is derived by modulo-2 addition of selected outputs of the constituent bistables. An *n*-stage register displays in turn on its *n* outputs every

possible combination of bits, the pattern repeating after every $2^n - 1$ clock pulses.

If we could recognize some particular pattern as it appeared during the sequence we could then use this information to reset the register and start again without going through the remainder of the sequence. This is easily done. All we need for an *n*-stage register is an *n*-input AND or NAND gate with the inputs connected via switches to the *Q* or \bar{Q} terminals of successive stages of the register. When the selected pattern appears, the resulting gate output resets the shift register and the count starts again.

An arrangement which satisfies these requirements is shown in Fig. 6. Such a counter or frequency divider is fast, synchronous with the clock, easily set up or programmed and very reliable. It uses just about the minimum number of logic blocks and requires only simple precautions in construction. However, a race condition can come about in the following way. Suppose a particular pattern appears in the register and it satisfies the gate condition. A gate output pulse appears which attempts to reset all the bistables in the register. If one is much faster than the rest, it resets first, changes its output and destroys the gate condition before the remaining bistables are reset. To avoid this effect, the gate output can be used to trigger a pulse monostable, the output of which lasts long enough to reset all the bistables. At the same time the pulse must have disappeared before the arrival of the next clock pulse. Durations around one-tenth of a microsecond are about right for d.t.l. units at the fastest clock rates. The only other objectionable feature of the divider is that the natural output is a very narrow pulse, whereas a square wave would be preferable, particularly for synthesizer applications.

There is no obvious way of producing a square wave from a narrow pulse which is effective over a wide frequency range. A pulsed monostable can do this at a fixed frequency whereas if a bistable is used we get a true square wave but have to put up with a further division by two. We end up with a device which divides only by even numbers. This defect of course plagues other types of divider. One way out is to double the input frequency which allows us to end the chain with a bistable. Several aperiodic doublers are known but they will not work with square wave or pulse inputs.

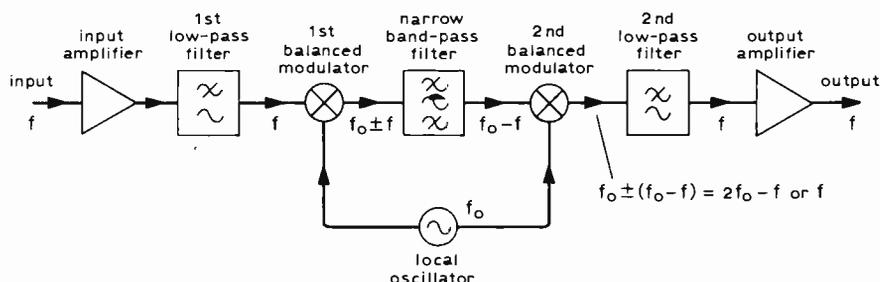


Fig. 5. Wave analyzer used in restored-frequency mode as a narrow-band tunable filter.

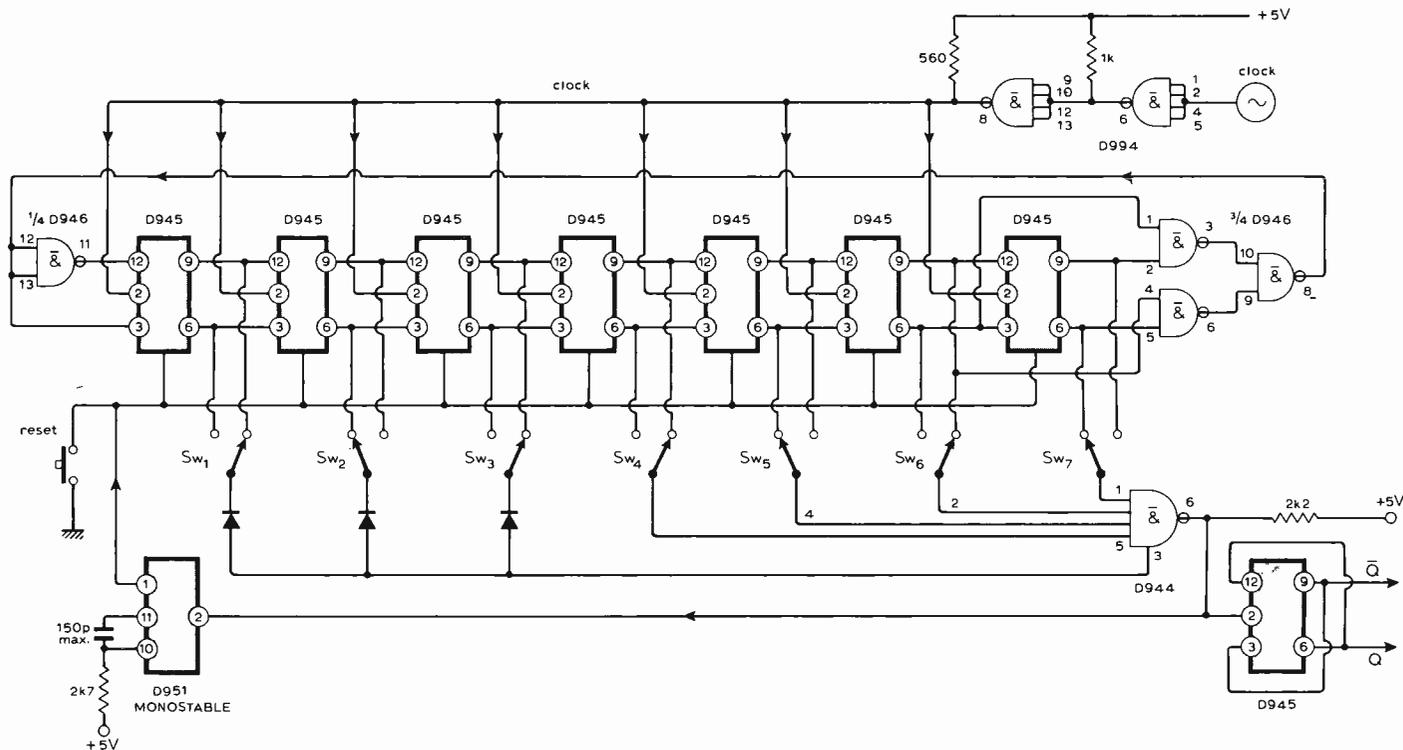


Fig. 6. Programmable frequency divider (all even divisions 2-254).

A seven-stage shift-register divider as in Fig. 6 will give a square wave output for every even divisor between 2 and 254. It will operate at clock frequencies up to 4MHz. Different divisors are selected by changing the switch settings. It is of course necessary to tabulate all these settings and this operation must be performed methodically. The equipment required is a counter and a stable oscillator. First, the switch settings must be found corresponding to division by two. Depending on the convention adopted for the switch positions, the pattern will be either 1000000 or 0111111, the switch positions along the line being counted from the input end of the register. To divide by four, the second switch along the line must be changed over, thus moving the pattern along one bit to the right. The first switch may or may not need to be altered.

The correct setting is that which gives the proper divisor as checked by the counter. Each successive change involves moving the switch pattern along, cyclically, one step at a time and, if necessary, changing the setting of the first switch to give the next even-number divisor in the sequence. The procedure sounds tedious and complicated when described in words but is quick and simple in practice. Naturally it is not so easy as setting up a row of decade switches but it is a less expensive system and it has the advantages of fast synchronous working and simple wiring. Preparing the table of switch settings does not call for particularly high accuracy of the clock source or counter. For example, a clock source of 1MHz divided by 200 gives an output of 5kHz. dividing by 202 gives a result about 1%, 50Hz, lower, a difference which is easily resolved.

Examination of the switch-setting table will bring out some interesting points. If we look down the first column we see the order of bits in a 127-pulse sequence. The second column down is a similar sequence, delayed by one clock pulse, and so on for the other columns. We notice to, that each switch setting pattern occurs once, and only once, as it should.

Referring again to Fig. 6, the seven bistable outputs eventually feed a seven-input NAND gate. This is not a standard

item. Instead, we use a four-input gate which has an expander or extender node to which other inputs may be connected, (through diodes with d.t.l. units). The diodes may be discrete components or may be contained in a special extender package, (SGS type 9933 or equivalent).

Generators using i.c. shift registers

One of the first published papers¹ giving practical information on random pulse

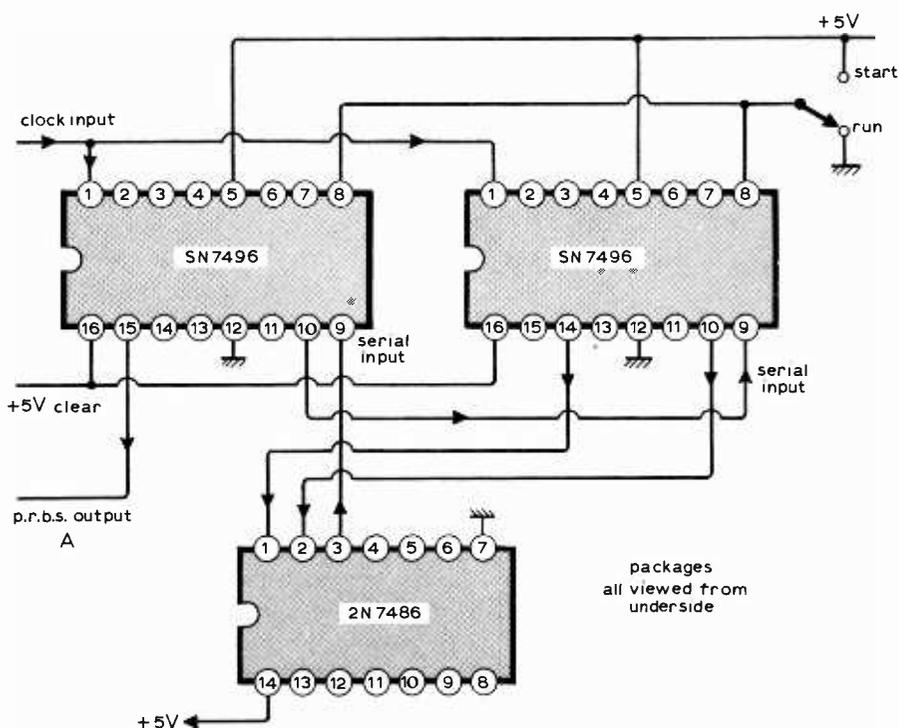


Fig. 7. 1023-bit l.r.s. generator using two five-bit t.t.l. shift registers and an exclusive-OR gate.

generators is still worth reading for the valuable background material it contains, its account of some applications, and because it shows the amount of effort required to construct such a generator from discrete components.

In contrast, an even more complex generator will now be described which can be built using only three integrated circuit packages.² These comprise two five-bit shift registers and one exclusive-OR gate from a quad package. Both these items are in the type 7400 t.t.l. range. The gate, SN7486, calls for no particular comment but reference must be made to the properties of the shift registers. To clear all stages, logic 0 must be applied to the clear input, pin 16. For normal use, apply logic 1. To preset the register for any particular starting sequence, the individual presets must be set to 0 or 1 as required. The sequence is read into the register by applying logic 1 to the master preset input, pin 8. During normal operation, pin 8 must be at logic 0. Shift in the register occurs when the clock input switches from 0 to 1.

The complete wiring diagram of the 1023-bit generator is shown in Fig. 7. The output may be taken from any of the *Q* terminals. In the diagram it is shown coming from the first. When clocked at 1023kHz, over 1,000 standard frequencies may be picked out by a suitable filter or selective amplifier.

Some extra packages are required to construct a programmable divider. Besides the multiple-input gate and bank of ten switches, we need ten inverter amplifiers to obtain the complements of the register outputs. Two standard packages provide twelve of these leaving two spares for use as buffers. Though unlikely, it may be necessary to drive a monostable from the gate output when resetting the register at the end of a count. Shorter sequences or simpler dividers can of course be built by omitting certain packages or units; in fact it is a simple matter to include switching to pick out runs of any length.

There is a growing interest in logic systems employing m.o.s. techniques. These i.c. packages are characterized by low power consumption, very high input impedance, tolerance to wide variations in supply voltage and high noise-immunity. Manufacturing processes are simpler than bipolar techniques and large-scale integration is possible. At present, speeds are rather lower than for t.t.l. but fast enough for most purposes.

Motorola has embarked on a big programme of complementary m.o.s. development and most logic requirements can be met by off-the-shelf units at moderate prices. The range includes modulo-2 gates and a variety of shift registers suitable for use in p.r.b.s. generators and frequency dividers of almost any degree of complexity.

A publication entitled "McMOS by Motorola", lists all the packages now in production and contains some useful, though brief, application notes. One of these refers to a 255-bit p.r.b.s. generator of the type under discussion.

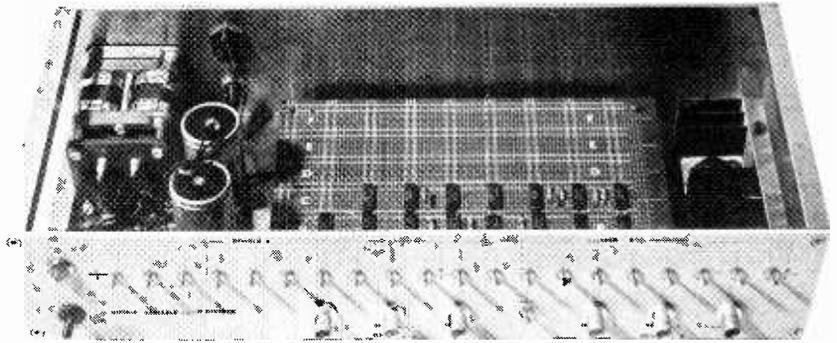


Fig. 8. Internal layout of the dual ten-stage 1023-bit p.r.b.s. generator/programmable frequency divider.

Miscellaneous uses of generators

Apart from their use as pseudo-noise sources and synchronous dividers these devices find application as test-signal sources, modulators in secure communication systems and as key generators for enciphered digital communications. A note on this last application may be of interest. Suppose that a plain text message in the form of a stream of binary digits is to be enciphered by the addition of a random bit stream, the key synchronous with the traffic. The two sequences can be added modulo-2 and securely transmitted by line or radio. At the receiving end an identical key stream is once more added (exclusive-OR), to the enciphered signal. It will be found that the original plain text is recovered. An example illustrates the principle:

Transmitting

Plain text	10110001111011001011011
Random key	00101100010000111011001
Enciphered text	01100010010100001111011

Receiving

Enciphered text	01100010010100001111011
Random key	00101100010000111011001
Plain text	10110001111011001011011

It will be seen that the last line is the same as the first and the plain text has been completely recovered. Security clearly depends on the random nature of the key which must have a very long sequence before repeating; indeed it should never repeat.

Referring back to the statistical properties of l.r.s. generators it is not difficult to see that if two identical sequences are produced and matched up pulse for pulse and space for space, then if they are exclusive-OR gated together the logical output will be 1 (continuous high). If a similar operation is conducted with one of the sequences displaced from the other by an amount corresponding to one clock period then the gate output will be almost zero (low), if averaged over the whole period of the sequence because, as already

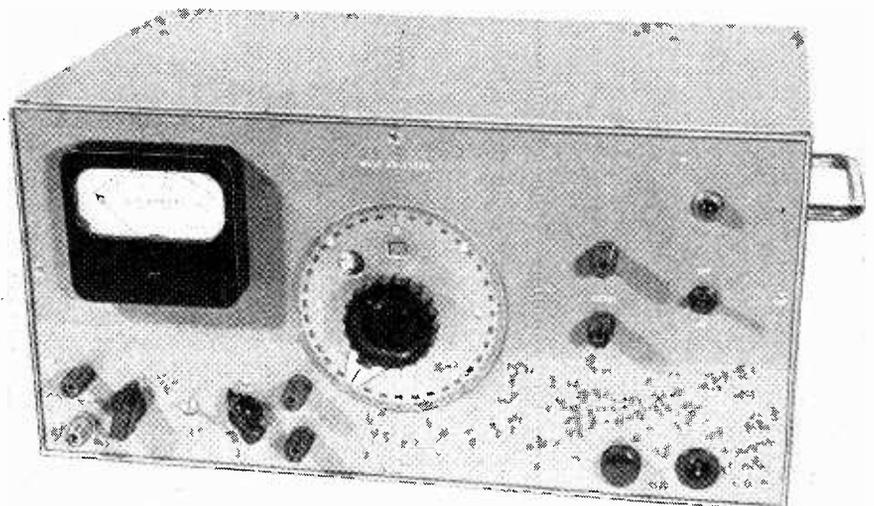


Fig. 9. Wave analyzer—used as a narrow-band tunable filter.

stated, the number of agreements and disagreements of the two patterns will, at most, differ only by unity. The same is true for any other relative shifts of the two patterns. This points to the possibility of developing a secure communications system.

If instead of transmitting a carrier, modulated or keyed in amplitude, frequency or phase, we transmit a random pulse train, this will sound like noise in the receiving telephones. If we switch from one sequence to a different one, or to a cyclically shifted version of the first, the transmission will still sound like noise, identical to the other. But if these digital streams are properly correlated with the outputs of similar generators at the receiving end, then intelligible communication becomes possible in Morse or in any normal printer code. There are obvious problems in setting up practical systems. Precise synchronization of the generators at each end of the link is required, the bandwidth of the transmission at high bit rates is very large and, in the h.f. band, multipath propagation effects cause difficulties.

An unauthorized interceptor hears nothing but noise during transmission. To read the traffic he must be in possession of l.r.s. generators exactly the same as those used on the link and even if he had such generators there is still the problem of synchronization and of finding the correct starting point in the sequence to give maximum correlation of the two bit streams. With 60-bit shift registers, the intercept task is a daunting one.

Few problems have been encountered in constructing the items so far discussed but, in the event of trouble, attention should be paid to the following points. Wiring runs should be as short as possible and a symmetrical layout of parts should be adopted. Some d.t.l. packages seem to work best with a supply voltage rather less than the nominal 5V. Capacitive decoupling at the unit power supply pins may sometimes be required. Mains transients can sometimes stop or interrupt the pulse sequence. Noise immunity of some units is not all it might be and it may occasionally be found that, after switching on, a sequence generator fails to start. This is because the shift registers lock up in the all-zero state. Though it is possible to incorporate logic to avoid this, it is simpler to switch off and start again.

References

1. "Random Pulse Generator Tests Circuits; Encodes Messages", B. K. Ericksen, J. D. Schmidt, *Electronics*, June 23, 1961, pp.56-59.
2. "A pseudo-Random Pulse Train Generator with Controllable Rate for Modelling of Audio-metric Systems", J. K. Moss, R. J. Simpson and W. Tempest, *Radio and Electronic Engineer*, Vol. 42, No. 9, September, 1972, pp.419-424.

High capacity p.c.m. system

A high bit-rate p.c.m. line transmission system, working at 120Mbit/s, has been put into field trial operation by the Post Office between Guildford and Portsmouth. Built by Standard Telephones and Cables, it is claimed to be the first of its kind in Europe and represents the Post Office's first step in developing a digital trunk network capable of carrying a variety of traffic. Of course there are p.c.m. systems already operating in the UK but these work at only 1.5Mbit/s, carrying 24 simultaneous telephone conversations over distances up to about 30km. The 120Mbit/s system is capable of accommodating 1,680 telephone channels, one colour television channel, 14 viewphone channels, 224 broadcast-quality sound channels, or a mixture of these types of traffic within its capacity.

The p.c.m. signals are transmitted along two coaxial "tubes" of an existing eight-tube cable which is already in use for 12MHz analogue carrier (f.d.m.) transmission. Repeater spacing and electrical power feeding are identical with those of the 12MHz system and in fact the 78 p.c.m. repeaters between Guildford and Portsmouth are installed in existing repeater stations—some of which are underground watertight and pressurized housings. Most of the repeaters' active functions are performed by the well proved BFY90 transistors. To allow maximum repeater spacing and remove d.c. component from the signal, the 120Mbit/s binary information is converted for transmission into a



A main repeater for the 120Mbit/s p.c.m. system between Guildford and Portsmouth.

90Mbaud ternary code consisting of the three voltage levels +6V, 0 and -6V.

At the Post Office's Portsdown repeater station near Portsmouth a demonstration was given, using a 30-channel p.c.m. terminal, of voice transmission over a distance of 130km from Portsmouth to Guildford and back. This used the system's multiplexing process for telephone channels. First, 30 channels are multiplexed to give a 2.048Mbit/s stream, then four such streams are multiplexed to give a 8.448Mbit/s stream and finally 14 of these are multiplexed to give the 120Mbit/s stream.

International discussion of the multiplexing of digital signals based on the 30-channel p.c.m. system has now resulted in the following hierarchy being adopted for use throughout Europe:

1st order	2.048Mbit/s	30 channels
2nd order	8.448Mbit/s	120 channels
3rd order	34.368Mbit/s	480 channels
4th order	139.264Mbit/s	1,920 channels

The first and second orders have already been adopted by the Post Office for the UK. Future plans for digital radio relay, and higher rate transmission on coaxial cable, will be based on the fourth order in the hierarchy, approximately 140Mbit/s, and multiples of this. The same basis will also be used for waveguide and optical fibre systems.

Sixty Years Ago

Humour was certainly an important component in the armoury of the wireless engineer of 1915. This was exemplified by a *Wireless World* reader's letter published in February of that year proposing a somewhat novel method of electric propulsion for ships, and reporting on several apocryphal experiments.

"Last week, after a short paper on 'Directional aerals', one of the members suggested that as action and re-action are equal and opposite there would certainly be in a directional aerial a force produced in the contrary direction to that in which the maximum energy was sent, therefore in his opinion if a good directional aerial were installed on a vessel, it would experience a force in the direction of the free end of the aerial, and so would be propelled. The free end, of course, would be generally over the bows of the vessel in order that she should move forward, but to move astern it could easily be arranged to shift the downleads to the other end. The speaker predicted that this would be the method of propulsion of the future—at any rate for small craft—and he became so excited, sir, over that prospect, that he wanted to communicate his idea to the Admiralty personally and without delay. He had great trouble, so we could hear at the porter's lodge, and was only persuaded to come quietly back on the promise of an extra bun for tea."


Circuit Ideas

D.C. level clamp


The need sometimes arises, e.g. after a stage of a.c. amplification, to clamp the minimum level of a signal voltage to a d.c. reference voltage. The circuit illustrated was developed to clamp, to the zero-volt level, signals having an amplitude of between 10mV and 10V. The familiar diode-and-capacitor clamp circuit is unsuitable here because of the diode's forward conduction characteristic.

In each cycle, the capacitor, C , charges to the peak negative value ($V_b = -V_p$) of the input voltage, V_i . The voltage V_a then follows the input voltage ($V_a = 2V_i + V_p$) while V_b remains at the level to which the capacitor was charged, decreasing only with a time constant
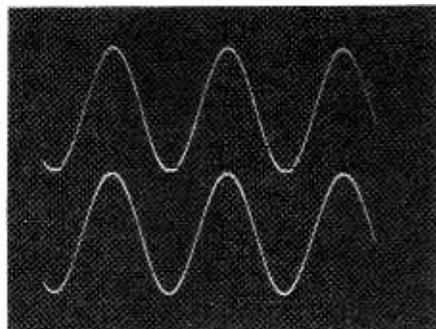
$$T \approx \frac{(R_4 + R_6) R_2 C}{R_4 + R_6 + 2R_2}$$



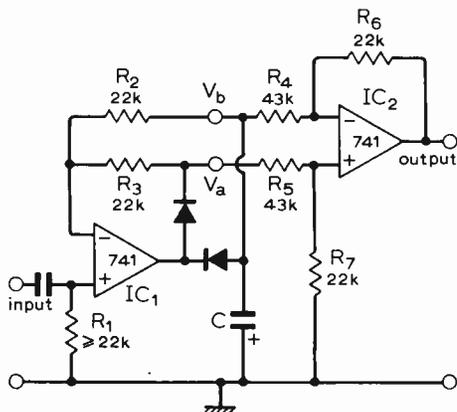Lower trace is the input signal; upper trace is the output from the restorer. Oscilloscope was obtained with the circuit operating on a 150Hz signal with an amplitude of 40mV peak-to-peak.



The required voltage waveform, with its minimum d.c. level restored to zero, appears as $V_a - V_b$. A low-impedance single-ended output is provided by IC_2 and, in this case, unity gain overall.


Using a 250- μ F electrolytic capacitor, the circuit clamps sinusoidal waveforms between 3Hz and 10kHz with little distortion. For use at higher frequencies, IC_1 should have a faster slew rate. Lower distortion can be achieved if IC_2 has a higher input impedance—allowing larger values of R_4 and R_5 to be used.

C. B. Mussell,
United Liverpool Hospitals.

Tolerant astable circuits

Some simple one-capacitor astable circuits are described below. They have none of the usual problems experienced with Eccles-Jordan and one-capacitor circuits, since they are reliable over a wide temperature and voltage range, and are substantially independent of transistor gain spreads.


Fig. 1 shows a 20-kHz astable which can have 50 p.p.m./deg C temperature coefficient of frequency if an NP0 capacitor, and low-coefficient wire-wound resistors are used, providing the transistors Tr_1 and Tr_2 are of the same type. Frequency varies by 0.05% over 6 to 12V supply, under these conditions.

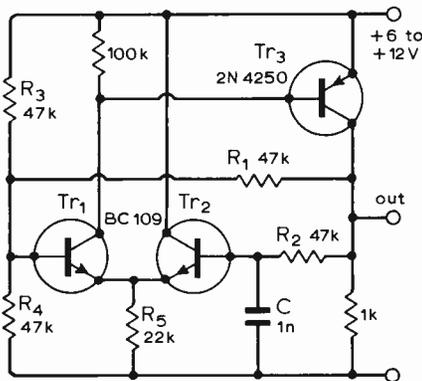

Timing may be varied with resistors R_1 and R_2 , and with capacitor C . Duty cycle is determined by the ratio of resistors R_3 and R_4 . The values shown give 50% duty cycle. Resistor R_5 may be decreased in value to allow higher output currents and/or high frequency operation; however, temperature stability is then slightly degraded.

Fig. 2 shows a high-performance pulser, capable of operating at from 10% to 1% duty cycle, approximately. The on current may be up to 50mA, and the off current drawn by the pulser is about 1μ A. This allows effective battery-power economy when operating at very low duty cycles. Standard Eccles-Jordan circuits cannot approach this performance.

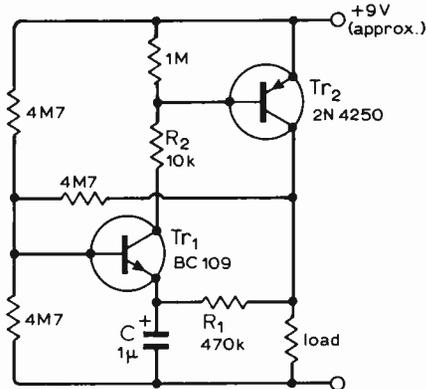Components R_2 and C determine the on time; however, the 4.7M Ω resistors and Tr_1 gain affects this time at short duty cycles. Components R_1 and C determine the off time. As shown, the circuit pulses about twice each second. This varies by



about 10% over the -20°C to $+100^\circ\text{C}$ temperature range. This variation may be reduced to about 1% by the addition of an emitter follower on the base of Tr_1 , of complementary polarity to Tr_1 , to cancel the V_{BE} temperature drift of this transistor.

This pulser circuit has been used for animal temperature and heart-rate studies. It is possible to have implanted transmitters operating from one mercury button cell for more than one year with a suitable choice of resistor values.

C. Horwitz,
University of Sydney,
Australia.


Analogue gate with no offset

An analogue gate capable of controlling audio signals by means of t.t.l. levels is shown. It is an improvement over existing gates in that when off there is negligible d.c. offset present at the output, thereby simplifying design of any subsequent stages in a large system.

Attenuation when off is approximately 66dB and negligible when on and fed into high impedance stages. The control should be logic 1 (+5V) to open the gate, and logic 0 (0V) to close it again.

There are many possible applications for such a circuit in the design of programmed channel selectors in the field of music synthesis for instance, for which it was designed.


L. Cook,
Prescot,
Lancs.

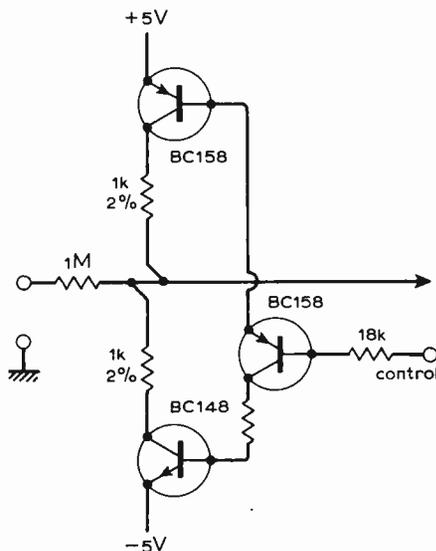

Electronic organ to piano

A circuit was needed which would simply convert an organ to a more piano-like instrument. It exponentially attenuates the output from an oscillator to zero in a manner adequate to mimic the waveform of a piano. In addition this circuit has the advantage of being self-triggering. Thus the exponential decay starts only when the waveform from a multivibrator is applied—dispensing with the need for extra contacts on the keyboard. It has been used in conjunction with the J. H. Asbery multiphonic organ published in the June 1973 issue of *Wireless World*, although it has many other applications.

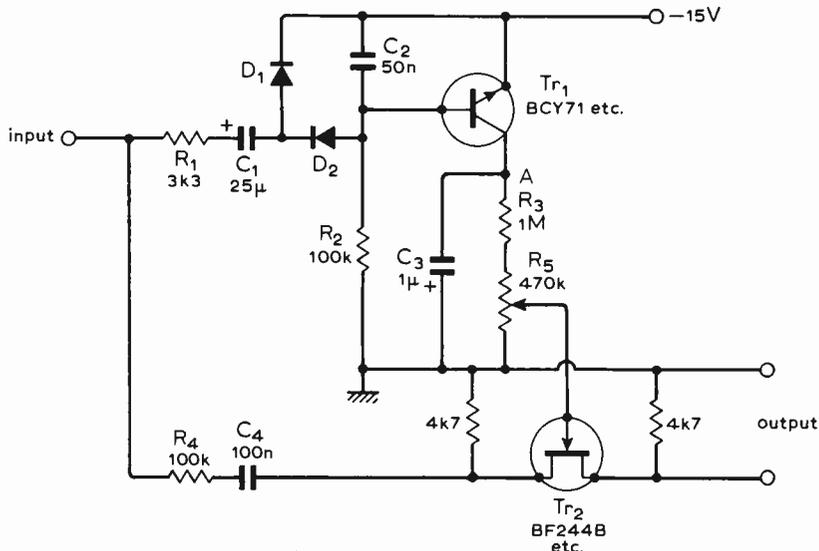Operation of the circuit is as follows: when no signal is being applied, R_2 draws a current through Tr_1 thus biasing it on and maintaining the voltage at A at supply potential. Application of a signal results in Tr_1 turning off—due to the rectifying and smoothing action of D_1, D_2 and C_2 . Capacitor C_3 then discharges through R_3 and R_5 .



The f.e.t. gate is controlled by this discharging capacitor. Potentiometer R_5 ensures the f.e.t. just switches off when C_3 is fully discharged. When the signal is removed Tr_1 conducts, C_3 charges and so

rapid manipulation of the keyboard is possible.
C. J. Outlaw,
Farnham,
Surrey.

Complementary ramp generator with independent amplitude/slope control

A circuit was required to generate two complementary ramps to be used to amplitude modulate auditory signals to either ear to create the impression of a left to right scan.

It is a simple matter using standard circuit techniques to either generate complementary ramps or to generate one ramp with independent control over amplitude and frequency. For this application, however, it was desirable to have control of amplitude and frequency of the two ramps at the same time, while avoiding interaction between the two controls. This is accomplished as follows: a ramp is generated between a reference voltage, V_{ref} and earth and its complement is generated by inversion through an operational amplifier and a level shift of V_{ref} .

The time taken to discharge a capacitor from an initial voltage V_{ref} to zero volts

depends on two parameters, discharge current and the initial voltage. If the discharge current is from a constant current source and if the current source is made voltage controlled, it can easily be shown that $T = CR$, which is independent of V_{ref} , the ramp amplitude. The ramp time is then independently controlled by R_5 . For the circuit shown, the output ramp amplitude and time are variable from 400mV to 8V, and 50ms to 2.0s, with negligible interaction between the two controls.

The capability of effecting this type of control described depends on a constant current source which avoids non-linearity due to V_{be} drops when V_{ref} becomes comparable to 0.7 volts. Hart* provides such a circuit which uses the high gain properties of operational amplifiers to reduce the effect of the V_{be} drop. It can be shown that this reduction is by a factor of $1/(1+A)$ where A is the open-loop forward voltage gain of the amplifier.


A conventional current mirror is then used to transfer the constant current to a

useful voltage level and this current is then used to discharge the ramp capacitor. Each time the capacitor reaches approximately zero volts, it is reset to V_{ref} by a switching transistor controlled by a comparator. At the same time, a positive feedback loop is changing the comparator switching voltage to V_{ref} so that when the capacitor voltage reaches this value, the shorting transistor is switched off and the capacitor again begins discharging towards zero volts.


Due to the very high impedance at the ramp output, effectively that of the current source, a voltage follower output stage is required as an impedance transformer. Another op-amp is used for the inversion and level shifting of the complementary ramp, and so both ramps are available from very low impedance sources.

L. J. Retallack,
Southampton University.

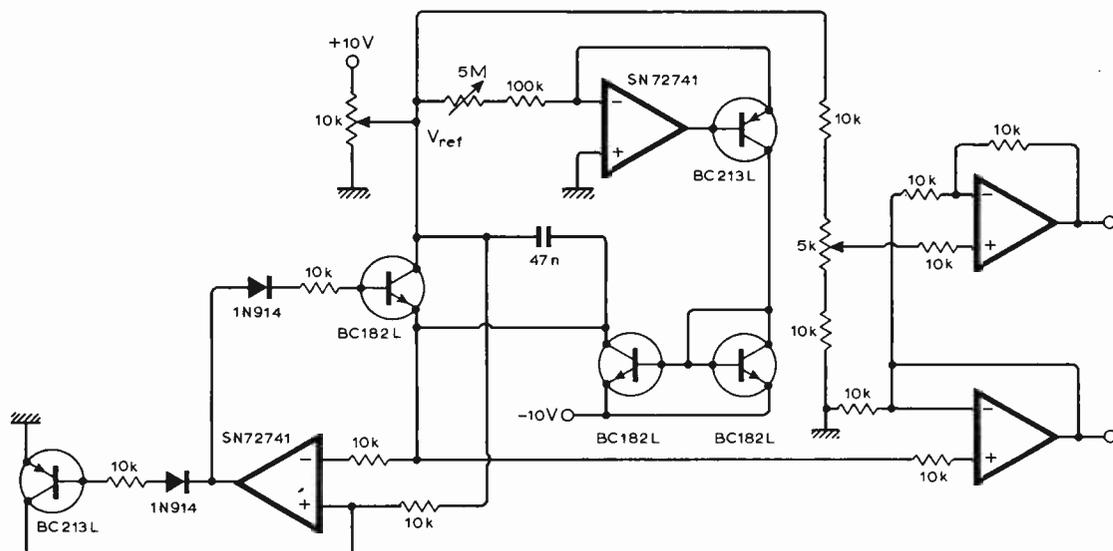*Hart, B. L., Current generators, *Wireless World*, vol. 27, 1970, pp. 511-4.



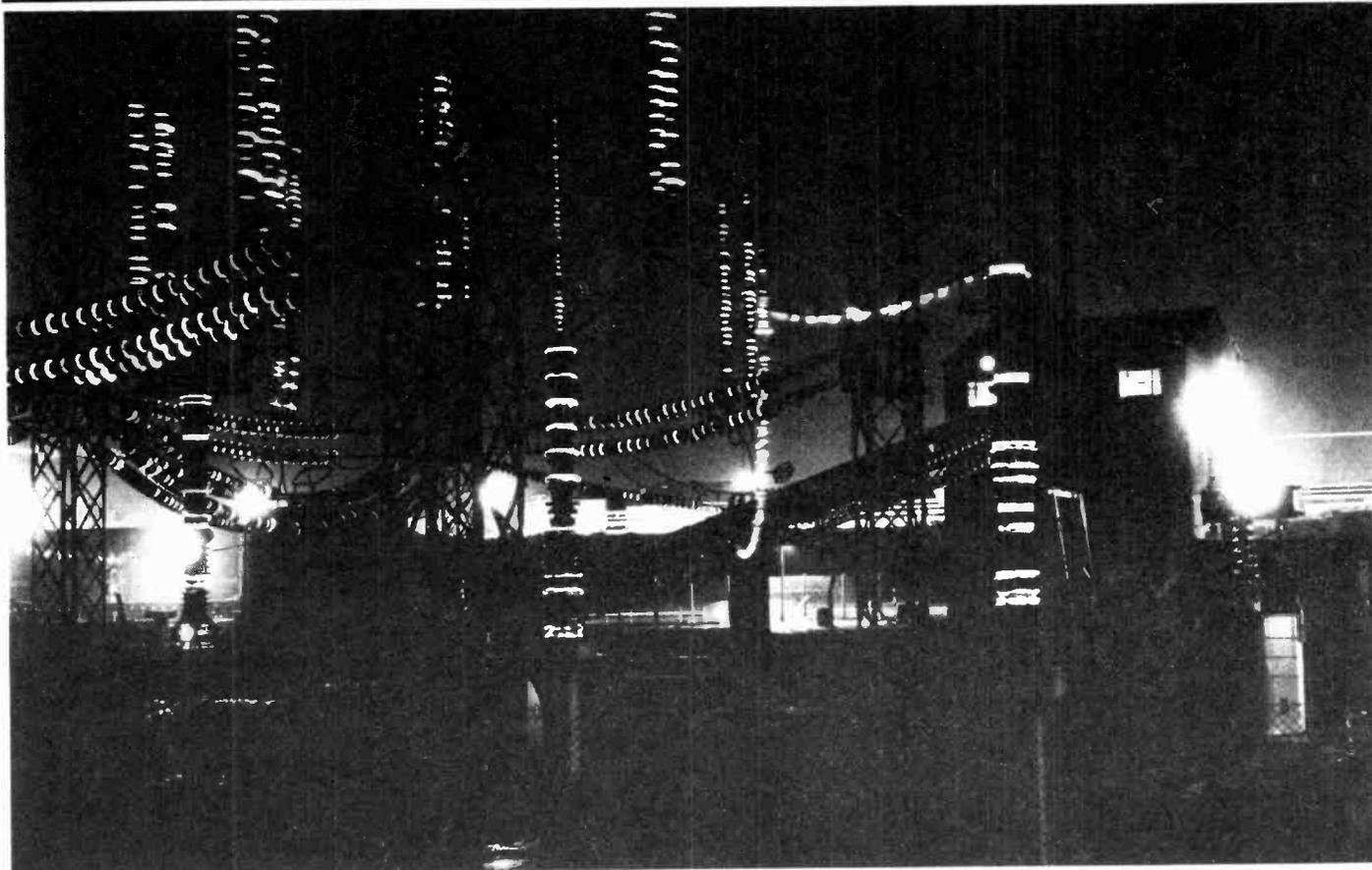When flashover is the danger. Use EEV spark gaps.



Photograph courtesy of C.E.G.B.

You name it. EEV spark gaps can stop it from happening.

Our range covers any voltage from 400-40,000V and handles powers up to 15 kilo joules. Types are available in glass or ceramic envelopes.

EEV spark gaps are very rugged and will work in any environment, unaffected by dust, damp or atmospheric changes. They are also compact, consistently dependable and long-lasting.

We make 2-electrode and 3-electrode types, and the whole range covers many applications including:

Flash-over protection. Crowbar protection circuits. Protection from transient phenomena. Protection circuitry for s/c drives for thermionic tubes.

Capacitor discharge circuits. Firing circuits. Relaxation oscillator circuits for gas ignition equipment. Quench circuits. TIG welding equipment.

For data and any help you need, write or 'phone EEV at the address below.

Right, GXQ400, a crowbar protection device and GXU40, for protection circuits in ground/air communications equipment.



LAP 93

EEV and M-OV know how.

THE M-O VALVE CO LTD, Hammersmith, London, England W6 7PE Tel: 01-603 3431. Telex: 234356. Grams: Thermionic London.
ENGLISH ELECTRIC VALVE CO LTD, Chelmsford, Essex, England CM1 2QU. Tel: 0245 61777. Telex: 99103. Grams: Enelectico Chelmsford



WW-007 FOR FURTHER DETAILS

Now—two fascinating ways to enjoy saving money!

NEW! Sinclair Scientific kit

£19.95
(INC. VAT)

Britain's most original calculator now in kit form

The Sinclair Scientific is an altogether remarkable calculator.

It offers logs, trig, and true scientific notation over a 200-decade range — features normally found only on calculators costing around £100 or more.

Yet even ready-built, the Sinclair Scientific costs a mere £32.35 (including VAT).

And as a kit it costs under £20!

Forget slide rules and four-figure tables!

With the functions available on the Scientific keyboard, you can handle *directly*

**sin and arcsin,
cos and arccos,
tan and arctan,
automatic squaring and
doubling,**

**log₁₀, antilog₁₀, giving quick
access to x^y (including square
and other roots),**

**plus, of course, addition,
subtraction, multiplication,
division, and any calculations
based on them.**

In fact, virtually all complex scientific or mathematical calculations can be handled with ease.

So is the Scientific difficult to assemble?

No. Powerful though it is, the Sinclair Scientific is a model of tidy engineering.


All parts are supplied — all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our Service Department will back you throughout if you've any queries or problems.

Of course, we'll happily supply the Scientific or the Cambridge already built, if you prefer — they're still exceptional value. Use the order form.

Components for Scientific kit (illustrated)

1. Coil
2. LSI chip
3. Interface chips
4. Case mouldings, with buttons, windows and light-up display in position
5. Printed circuit board
6. Keyboard panel
7. Electronic components pack (diodes, resistors, capacitors, etc.)
8. Battery assembly and on/off switch
9. Soft carrying wallet
10. Comprehensive instructions for use

Assembly time is about 3 hours.

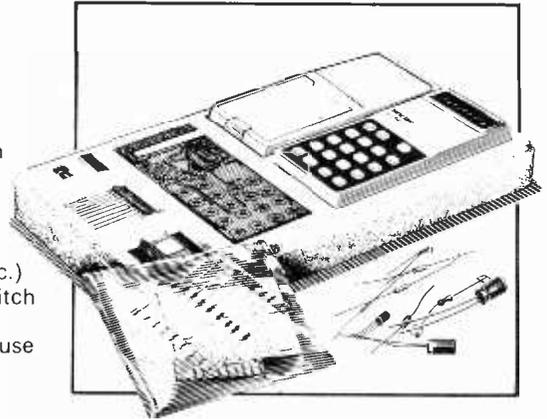

Features of the Sinclair Scientific



- **12 functions on simple keyboard**
Basic logs and trig functions (and their inverses), all from a keyboard as simple as a normal arithmetic calculator's. 'Upper and lower case' operation means basic arithmetic keys each have two extra functions.
- **Scientific notation**
Display shows 5-digit mantissa, 2-digit exponent, both signable.
- **200-decade range**
10⁻⁹⁹ to 10⁺⁹⁹
- **Reverse Polish logic**
Post-fixed operators allow chain calculations of unlimited length — eliminate need for an = button.
- **25-hour battery life**
4 AAA manganese alkaline batteries (e.g. MN 2400) give 25 hours continuous use. Complete independence from external power.
- **Genuinely pocketable**
4 1/3" x 2" x 11/16". Weight 4 oz. Attractively styled in grey, blue and white.

Sinclair Cambridge kit

Now only
£14.95
 (INC. VAT)

At its new low price, the original Sinclair Cambridge kit remains unbeatable value

In less than a year, the Cambridge has become Britain's most popular pocket calculator.

It's not surprising. Check the features below - then ask yourself what other pocket calculator offers such a powerful package at such a reasonable price.

Components for Cambridge kit

1. Coil
2. LSI chip
3. Interface chip
4. Thick film resistor pack
5. Case mouldings, with buttons, window and light-up display in position
6. Printed circuit board
7. Keyboard panel
8. Electronic components pack (diodes, resistors, capacitors, transistor)
9. Battery clips and on/off switch
10. Soft wallet

Assembly time is about 3 hours.

Take advantage of this money-back, no-risk offer today

The Sinclair Cambridge and Scientific kits are fully guaranteed. Return either kit within 10 days, and we'll refund your money without question.

All parts are tested and checked before despatch - and we guarantee any correctly-assembled calculator for one year. (This guarantee also applies to calculators supplied in built form.)

Simply fill in the preferential order form below and slip it in the post today.

Scientific

Price in kit form £19.95 inc. VAT.


Price built £32.35 inc. VAT.

Cambridge

Price in kit form £14.95 inc. VAT.

Price built £21.55 inc. VAT.

Features of the Sinclair Cambridge

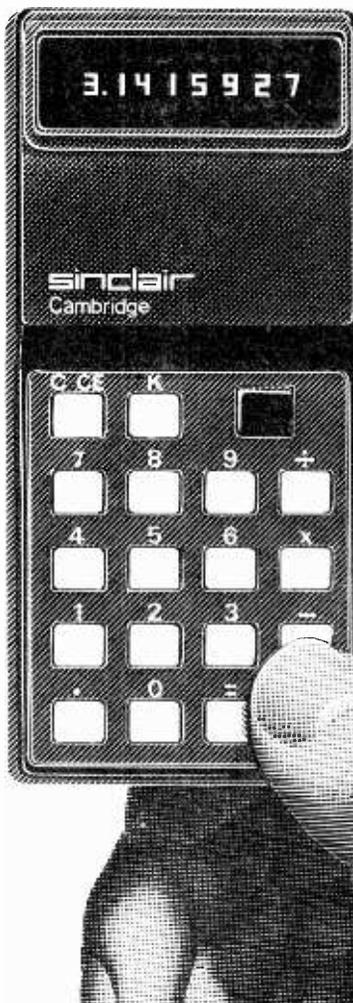

- Uniquely handy package. 4 1/3" x 2" x 1 1/16", weight 3 1/2 oz.
- Standard keyboard. All you need for complex calculations.
- Clear-last-entry feature.
- Fully-floating decimal point.
- Algebraic logic.
- Four operators (+, -, x, ÷), with constant on all four.
- Powerful constant with separate 'K' button.
- Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £15.
- Calculates to 8 significant digits
- Clear, bright 8-digit display.
- Operates for weeks on four AAA batteries.

**To: Sinclair Radionics Ltd,
 FREEPOST, St Ives,
 Huntingdon, Cambs. PE17 4BR**

Please send me
 Sinclair Scientific kit at £19.95
 Sinclair Scientific built at £32.35
 Sinclair Cambridge kit at £14.95
 Sinclair Cambridge built at £21.55

All prices include 8% VAT.

*I enclose a cheque for £
 made out to Sinclair Radionics Ltd,
 and crossed.

*Please debit my *Barclaycard/
 Access account. Account number

*Delete as required.

Signed _____

Name _____

Address _____

Please print. FREEPOST - no stamp needed.


ww/2/75

sinclair


Sinclair Radionics Ltd,
 FREEPOST, St Ives,
 Huntingdon, Cambs. PE17 4BR.

Reg. No: 699483 England. VAT Reg. No: 213 8170 88.

WW-142 FOR FURTHER DETAILS

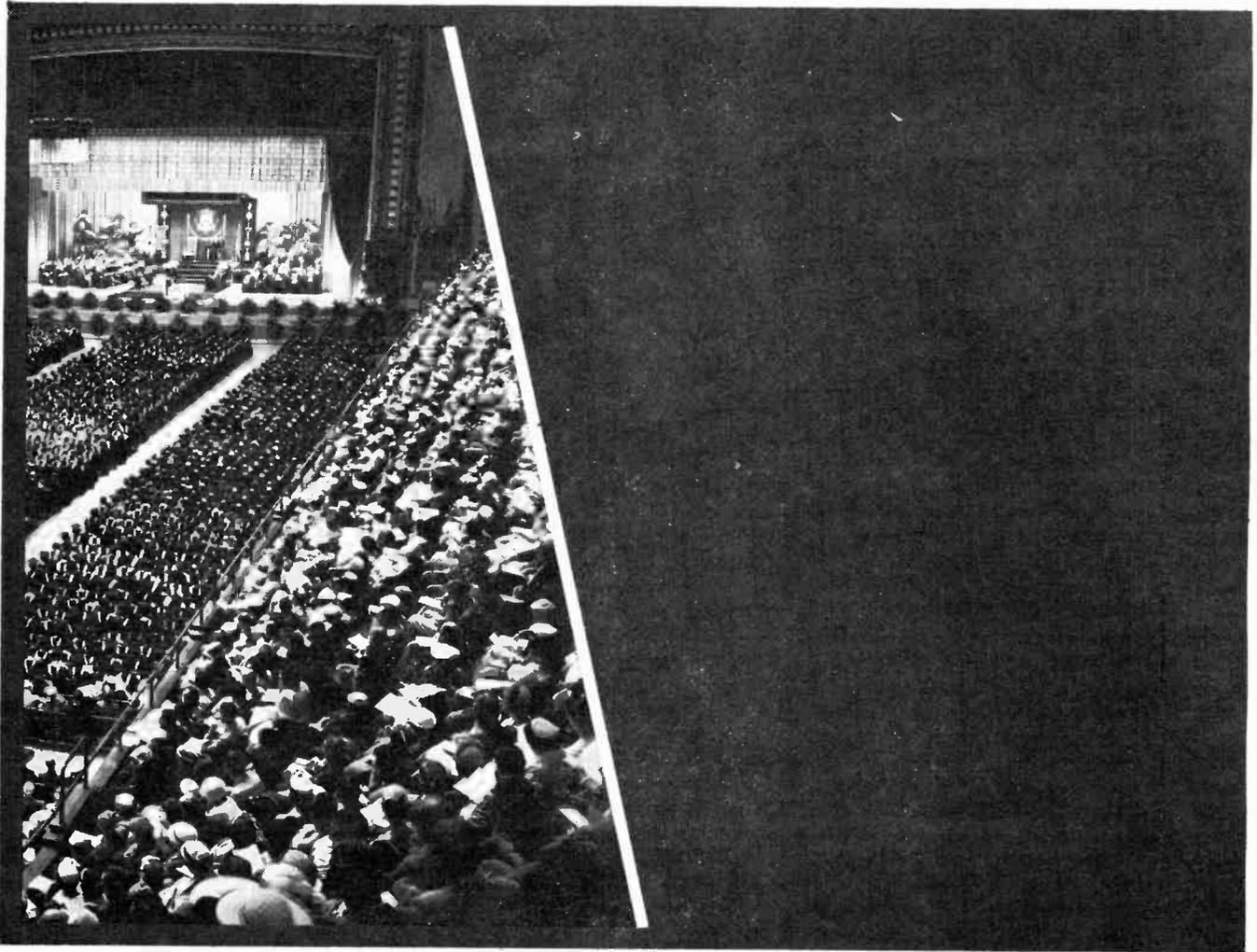

Vocal Master of Ceremonies

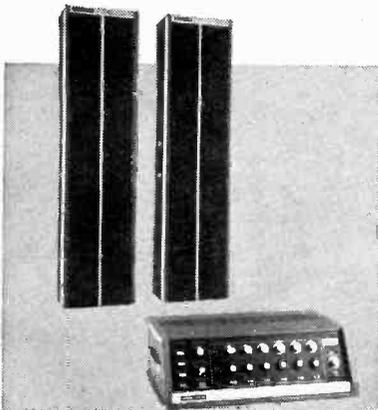

There are precious few ceremonies, functions, meetings or entertainment events that *Shure Vocal Master Sound Systems* can't cover — regardless of room size or apparent acoustic difficulties. The Vocal Master is designed to project the voice with intelligibility and authority to the rear of large areas without overwhelming the listeners up front. It's versatile, easy to operate, and totally reliable. It's the system that earned its reputation for superb sound amplification by meeting the standards of professional entertainers — and is now used in hotels, churches, schools, executive meeting rooms and entertainment facilities from Land's End to John O'Groats in preference to built-in "custom" systems costing *many* times more.

Shure Electronics Limited
 Eccleston Road, Maidstone ME15 6AU
 Telephone: Maidstone (0622) 59881



WW—147 FOR FURTHER DETAILS

Transistor pairs

The pros and cons of d.c.-coupled pairs, circuits for which are given in set 20 of Circards

by J. Carruthers, J. H. Evans, J. Kinsler and P. Williams

Paisley College of Technology

“Supplementary or complementary, opposites or composites?” asked Tweedledum. “Contrariwise”, said Tweedledee. It is not the intention to rewrite “Alice...”, but it is not always clear what the advantages are in d.c.-coupled pair configurations—voltage gain plus impedance change, super current-gains, p-n-p simulation, thermal compensation or perhaps a current source as a stabilizing network.

The *pièce de resistance* might be the long-tailed pair or differential amplifier (where would the linear i.c. be without it?) which provides some satisfying amplifying properties—some possible variations for small-signal operation are shown in Fig. 1. For example, the connection shown in Fig. 1(a) converts a signal difference between two inputs to equal, but antiphase collector signals. Signals common to both inputs (e.g. superposed noise signals from the same source) are reduced without affecting the differential gain, which is that due to a single transistor.

The ability of this amplifier to prevent amplification of a common signal is called the common-mode rejection ratio, being the ratio of the differential voltage gain to the common mode gain, usually expressed in dB. The single-ended inputs of Fig. 1(b) and (e) produce an output at Tr_2 collector, equivalent to Tr_1 as an emitter-follower driving Tr_2 as a common-base amplifier. In addition, the output of Tr_1 is equal in magnitude but antiphase to that of Tr_2 , on the assumption of constant total current (long-tail). Hence the differential output in Fig. 1(b) is twice the single-ended output. The voltage gains are approximately R/h_{ib} and $R/2h_{ib}$ for Fig. 1(b) and (e) respectively, where h_{ib} is the effective input resistance of the common base configuration. Fig. 1(c) and (f) are not used as amplifiers, but are useful as a means of determining the gain to common mode signals. This should be much less than unity to give good rejection.

The common-emitter, common-base, connection shown in Fig. 2(a) is the cascode amplifier, where the first stage transistor Tr_1 has current gain, and the second stage Tr_2 has voltage gain. The advantages are a large gain-bandwidth

product and also, for high voltage outputs, the high breakdown value of the common base transistor Tr_2 is essential.

The common collector-common collector pair of Fig. 2(b) is the familiar

Darlington connection, where the effective current would be approximately β^2 , if the transistors were identical. This would be true for short-circuit outputs, but a practical value for the β of each transistor

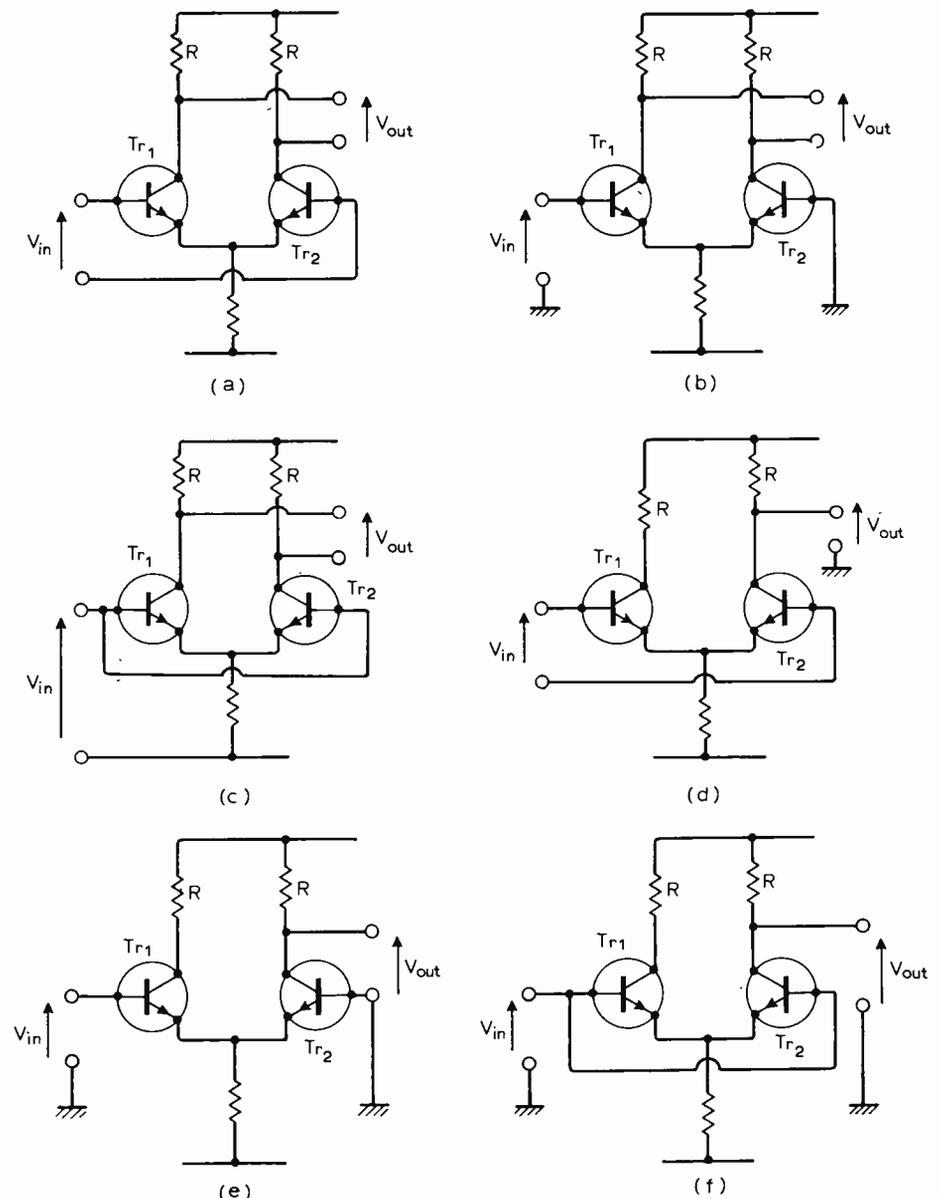


Fig. 1. Variations of the long-tailed pair include circuits with differential input, differential output (a), single-input, differential output (b) & (c), differential input, single output (d), and single input and output (e) & (f).

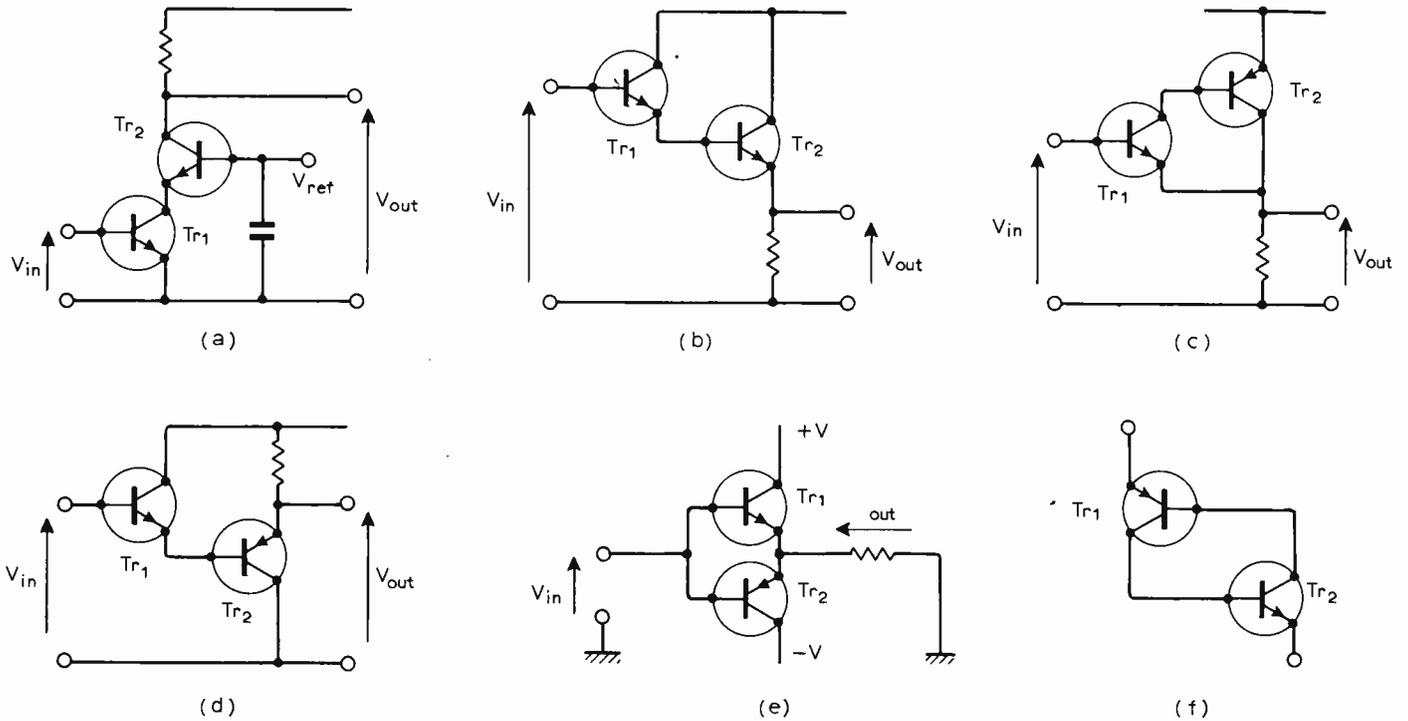


Fig. 2. Other ways of connecting two transistors are common-emitter, common-base i.e. cascode (a), common-collector pair i.e. Darlington (b), complementary pair with only one V_{be} drop (c), complementary pair with no V_{be} drop (d), symmetrical complementary pair i.e. class B amplifier (e), and the regenerative pair (f).

would be to specify the minimum value quoted by a manufacturer (assuming that discrete transistors are being discussed, because it must be remembered that super- β packages are also available with defined current gains). The complementary connection of Fig. 2(c) provides only one V_{be} drop compared with Fig. 2(b), and that of (d) cancels the V_{be} drops, but offers some second-order residual offset between input and output, and requires a separate bias path (not shown) for Tr_1 emitter current and Tr_2 base current. Complementary versions may provide an advantage, in that the transistor choice for the first stage can be that with the highest current gain at low currents.

When opposite types of transistors are connected in complementary form, such as Fig. 2(e), we have the basis of a class-B amplifier. The circuit for each half-cycle of signal is essentially identical, and the load is driven from a low-impedance source, because each transistor acts as an emitter follower. An advantage is that interstage and output transformers are not necessary when such a circuit is used at audio frequencies.

The interconnection of n-p-n and p-n-p transistors as in Fig. 2(f) provides a regenerative switching action due to the positive feedback between collectors and bases. It is similar in operation to a unijunction transistor, and there are of course similarities with the thyristor. Switching speeds can be faster than a single unijunction device because high-frequency transistors can be employed. The same arrangement is the basis for a constant-current circuit (Circards set 6, card 5), while those sources which may be classed as current controlled tend to use the current-mirror—no self-respecting

operational amplifier would be without one!

The complementary-symmetry m.o.s. pair has been an excellent addition to the pair family. Besides being the basis of several logic gates, it also has application in multivibrators and as a linear amplifier.

A close study of most linear integrated-circuits will reveal the use of two or more of the pairs mentioned, to provide a composite arrangement which offers advantages that no single transistor or pair can do.

Titles of cards in set 20 of Circards (available shortly)

are:

- High current gain I (Darlington)
- High current gain II
- Cascode
- Long-tailed pair
- Current mirror
- Complementary pair
- Complementary emitter follower
- CMOS pair
- Mixed pairs
- Triples

What are Circards?

Circards are a new method of collating and presenting data about circuits in a compact and easily retrievable way. The sets of 203 × 127mm (8 × 5 in) double-sided cards are designed for easy filing in standard boxes and for easy access at the desk or at the bench, where transparent plastic wallets keep the cards in good condition.

Each card normally describes operation of a selected circuit, gives *measured* performance data and graphs, component values and ranges, circuit limitations and modifications to alter performance. Suggestions for further reading are included

together with cross references to related circuits. The Circard concept was outlined more fully in the October 1972 issue of *Wireless World*, pp. 469/70.

How to get Circards

Order a subscription by sending £13.50 for a series of ten sets to:

Circards
IPC Electrical-Electronic Press Ltd
General Sales Department, Room 11
Dorset House
Stamford Street
London SE1 9LU

Specify which set your order should start with, if not the current one. One set costs £1.50, postage included (all countries). Make cheques payable to IPC Business Press Ltd.

Topics covered so far in Circards are:

- 1 active filters
- 2 switching circuits (comparator and Schmitt circuits)
- 3 waveform generators
- 4 a.c. measurement
- 5 audio circuits (equalizers, tone controls, filters)
- 6 constant-current circuits
- 7 power amplifiers (classes A, B, C & D)
- 8 astable multivibrator circuits
- 9 optoelectronics: devices and uses
- 10 micropower circuits
- 11 basic logic gates
- 12 wideband amplifiers
- 13 alarm circuits
- 14 digital counters
- 15 pulse modulators
- 16 current-differencing amplifiers—signal processing
- 17 c.d.as—signal generation
- 18 c.d.as—measurement and detection
- 19 monostable circuits

New Products

P.c.b. supports


Ilex pillars are designed to support and insulate p.c.bs from a chassis. The pillars are made from nylon and have a girder-shaped section with a spring-in fastening at the top and a push-in clip at the base.

The supports may be mounted horizontally or vertically and are available in sizes from $\frac{1}{4}$ in to $1\frac{1}{2}$ in from West Hyde Developments Ltd, Ryefield Crescent, Northwood Hills, Middx HA6 1NN.

WW300 for further details

Digital watch kit

A series of l.e.d. digital watch kits designated LWS-6120 has been announced by Litronix. The kits are all based on the LMC-6120 low-power c.m.o.s. chip which counts hours, minutes and seconds. Also included in the kits are two monolithic n-p-n bipolar arrays, the LBC-1060 digit driver and the LBC-1070 segment driver. All three circuits are supplied in chip form intended for hybrid assembly methods. Eight different display options are available which may be supplied either as monolithic l.e.d. chips or pre-packaged and

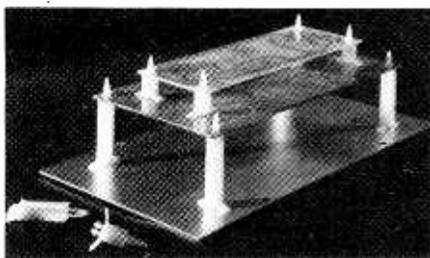

WW300

aligned for flow solder mounting to the watch module. The kits are priced from £16.62 in quantities of 100. Litronix, Bevan House, Bancroft Court, Hitchin, Herts SG5 1LW.

WW301 for further details

Digital X-Y plotter

The model WX511 plotter is designed for use with mini-computers or data output terminals. The instrument is compatible with a standard t.t.l. interface as well as t.t.l.-level pulses to give +x, -x, +y, -y, pen up and down (z axis), reset and chart change or feed operations. Specifications for the plotter are: a writing speed, in the x/y axis, of 400 steps/sec with a step width of 0.1mm. A maximum z axis speed of ten times/sec, and a rise time of 1µs with a pulse width of 1µs. The machine, which is claimed to have an overall accuracy to within $\pm 0.2\%$, has a writing area of 350 × 250mm and overall dimensions of 400 × 496 × 140mm. Environmental Equipments Ltd, Eastheath Avenue, Wokingham, Berkshire RG11 2PP.

WW302 for further details

I.c. heat sink

A heat sink suitable for use with d.i.l. i.cs is available from G.D.S. The dissipator, which is designated LIC214, has a "staggered finger" configuration with a top plate for securing the i.c. in position. The heat sink will dissipate approximately 400mW for every 10°C rise in junction temperature. Overall dimensions for the device are: width $\frac{3}{4}$ in, length 1.8in, and fixing holes 1.043in between centres. GDS Sales Ltd, Michaelmas House, Salt Hill, Bath Road, Slough, Berks.

WW303 for further details

Colour checker

Two colour checkers for shadowmask and Trinitron tubes have been introduced by BSP Ltd. The checkers, which are similar

in shape to a cheque card with a viewing window, are intended for use on static pictures such as test cards. The card is placed horizontally on the screen with the window over a selected part of the picture. The window area is a grid of lines in the Trinitron version and a matrix of black dots in the shadowmask type. This enables the colours to be analyzed separately.

Two colour checkers are supplied (mail order only) in a wallet with an instruction booklet for £2.58 including v.a.t. and postage. BSP Ltd, Sandwich, Kent CT13 9LP.

WW304 for further details

Hi-fi label kit


Bib Accessories are now marketing a pack of 76 printed-p.v.c. labels suitable for identifying audio leads. Each title has two labels and in the case of left and right leads the labels are printed in red and black. The kit also contains 38 blank labels enabling miscellaneous titles to be written. Bib Hi-Fi Accessories Ltd, Hemel Hempstead, Herts.

WW305 for further details


Liquid crystal display

A range of liquid crystal displays is now available from Hamlin Electronics. The range comprises 3½ digit types and one 8 digit type all operating in the dynamic scattering mode. The devices in the 3302 series are suitable for wrist-watch applications and have a power consumption of 30µW. Series 3400 consists of digital clock type displays and incorporate am/pm indication, while the 3600 series is suitable for instrument readouts. The eight digit devices in the 3500 series have been specifically designed for use in calculators and incorporate a floating decimal point. Hamlin Electronics Ltd, 14 New Road, Southampton, Hants SO2 0AA.


WW306 for further details

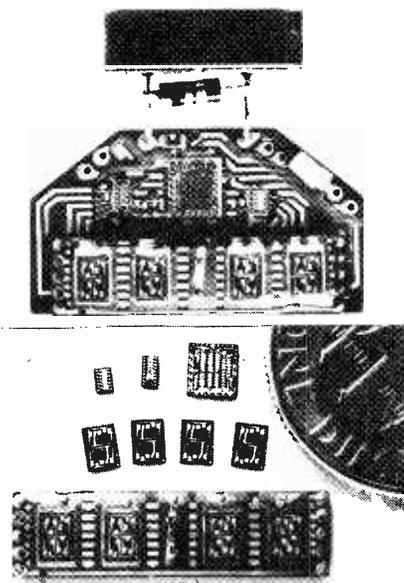

WW301

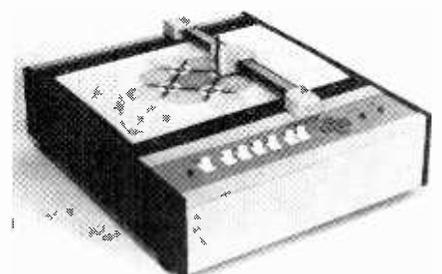

WW302

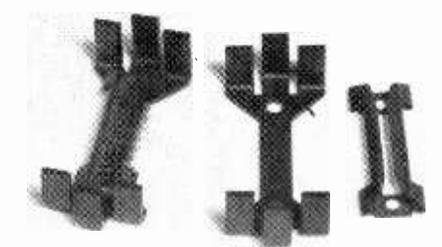

WW303

Instrument case handles

A range of 12 handles comprising heavy duty, folding, and flush types, each having variation of size and fixing, has been introduced by West Hyde Developments. All of the models have concealed spring clips which hold the hinged handles in either the open or closed position. Rubber buffers are also incorporated to ensure quiet operation. Apart from the smallest version, which is constructed from chromium plated steel, the handles are polished aluminium with metal base plates and are supplied either un-assembled and unpainted or complete and painted. West Hyde Developments Ltd, Ryefield Crescent, Northwood, Middx HA6 1NN.

WW307 for further details


Interference filters

The JX5100 series of filters is designed to protect equipment from mains-borne noise as well as protecting the mains from equipment noise. The filters are available for operation at +125°C and 250V a.c. in a range of current ratings from 1 to 30A. The series is claimed to withstand a test voltage of 2100V d.c. to ensure protection against high-voltage transients. Sprague Electric UK Ltd, 159 High Street, Yew-sley, West Drayton, Middx.

WW308 for further details

Digital multimeter

The DM2 multimeter from Sinclair is a five-function four-range instrument with a $3\frac{1}{2}$ digit l.e.d. display. The meter uses a m.o.s. l.s.i. chip which has built-in 7-segment decoding and provides an input impedance of typically 10M Ω . A chain of metal film resistors form a voltage divider to obtain ranges up to 1000V, and to provide current shunts for ranges up to 1A. A mean averaging a.c. to d.c. converter is also incorporated, to provide alternating voltage and current ranges; overload protection is provided. The meter is battery powered, measures 9 \times 6 \times 2in, and costs £59.00 plus v.a.t. Sinclair Radionics Ltd,

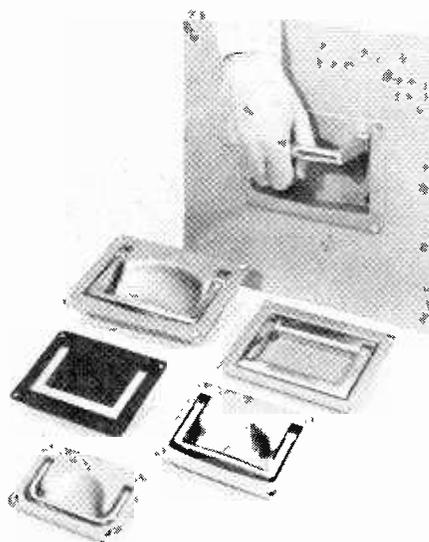

WW307

London Road, St. Ives, Huntingdon, Cambs PE17 4HJ.

WW309 for further details

Resistor modules

ITT have introduced a range of single-in-line packaged resistor modules comprising nine types in four package sizes. Resistor values between 10 Ω and 1M Ω \pm 10% are available with a power rating of 125mW per resistor in the temperature range -40 to +75°C. The networks cost between 6p and 13.5p and are available from ITT Components Group Europe, Film Circuit Operation, Brixham Road, Paignton, Devon.

WW310 for further details


Thermal wire-stripper

Litesold have introduced a pair of thermal wire-strippers suitable for removing p.v.c. and p.t.f.e. coverings up to 4mm diameter. The electrically heated V-shaped jaws melt the insulation material which is then drawn off the conductor. The model PVC is a 14W, 12 or 24V, tool for low temperature insulations while the model PTFE is a 48W 24V stripper suitable for p.t.f.e. insulations only. Light Soldering Developments Ltd, 97-99 Gloucester Road, Croydon, Surrey.

WW311 for further details

Ultrasonic transducer

The Linden Laboratories model 70100 ultrasonic transducer is available for operation at two standard frequencies. The 25kHz \pm 2kHz version has a bandwidth of 0.4kHz at -6dB, a receiving sensitivity of -50dB, relative to one volt per microbar, a capacitance of 150pF and a tuning inductance of 26mH. The 40kHz \pm 2kHz version also has a 0.4kHz bandwidth at -6dB but the receiving sensitivity is -60dB with a capacitance of 160pF and a tuning inductance of 10mH. Both types of transducer use a piezoelectric ceramic housed in an aluminium case measuring 20.6 \times 26mm. Linden Labora-

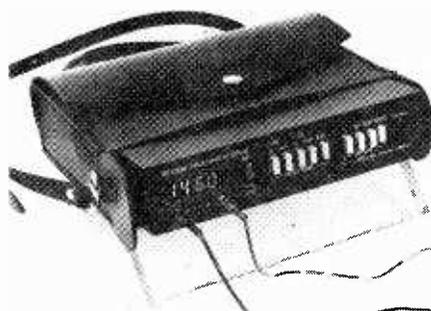

WW309

tories Inc., PO Box 920, State college, Pa. 16801, USA.

WW312 for further details

Waveform monitor

The EV4040 colour-television waveform monitor is available in PAL or NTSC versions and offers a bright display under high gain conditions. The instrument can also display remotely-commanded RGB signals, and has internal/external sync selection. A filter switch enables individual display of low frequency components, chrominance, differential gain and line time non-linearity. An active d.c. restorer may be selected to maintain the position of the back porch on the display regardless of average picture level. The illuminated graticule has ten divisions with major parameter lines emphasised. Electronic Visuals Ltd, PO Box 16, Staines, Middx.

WW313 for further details


Miniature transformer

The E75A is a recent addition to the 75 range of transformers from Belclere. This mains transformer will mount directly on to a p.c. board and occupy a volume of about 0.65 cubic in. The secondary winding, which is centre tapped, provides an output of 0.2VA and the makers claim that the temperature will not exceed 55°C when the secondary winding is shorted. Belclere Ltd, Cowley, Oxford OX4 2BU.

WW314 for further details

Digital signal generator

The DG2 is a crystal controlled signal generator providing a square wave output from 0.1Hz to 1MHz. The output can be set to three significant figures above 1Hz with an amplitude of either 5 or 2.5V. An accuracy of \pm 20 p.p.m. at 25°C with a stability of \pm 50 p.p.m. from 0 to +60°C is claimed for the instrument which can also be used to multiply an input frequency by factors from 0.001 to 1000. The generator, which has both internal battery and

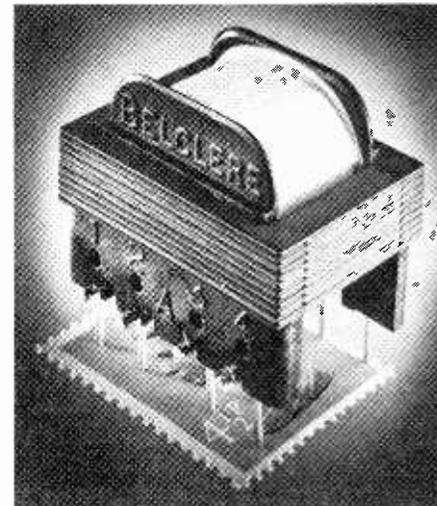

WW314

mains power supplies, measures 59 × 215 × 254mm and costs £140 from Jiskoot Auto-control Ltd, Tunbridge Wells, Kent.
WW315 for further details

Transistor covers

A range of insulating covers for T03 and T066 packages is available from Jermyn. There is a choice of either stretch on, screw hole or flange fixing types with different heights. All the covers are moulded from nylon and will withstand a temperature of 125°C. Jermyn Manufacturing, Sevenoaks, Kent.
WW316 for further details

Audio spectrum analyzer

The Amber Audio model 4550 analyzer provides visual representation of the spectral energy content of an audio signal. The unit is a relatively low-cost, compact instrument (13.3 × 21 × 27.9cm) whose application is in sound recording, mixdown of multi-channel recordings and broadcasting. The device may also be used for acoustic and vibration analysis. Audio input is divided into ten octave-width segments (20Hz to 20kHz), each octave being displayed on a vertical column of ten l.e.ds. The instrument includes two independent accumulating memories and four inputs can be displayed separately or in any combination by means of front panel push buttons. The display range may be set to either 10 or 20dB while a step type attenuator varies the input sensitivity in 2dB increments over a 20dB range. A sample button allows short spectra samples to be taken. Other main specifications are: centre frequencies 31.25, 62.5, 125, 250, 500Hz, 1, 2, 4, 8, 16kHz; centre frequency accuracy ±5%; filter slope 12dB/octave; accuracy of display dB steps ±0.25dB noncumulative; input impedance greater than 18kΩ. The display indicates within 1dB of actual value within 2ms above 1kHz or four cycles or less 1kHz and below (40ms at 100Hz, 80ms at 50Hz). Display decay time is 2.3 seconds for a fall of 20dB. The unit weighs 3.6kg and is priced at £815.00 net. Scenic Sounds Equipment, 27-31 Bryanston Street, London W1H 7AB.
WW317 for further details

Products seen at Electronica 74

Ion-implant r.a.m.


As well as showing single, two-chip and four-chip microprocessors, General Instrument Microelectronics announced their emphasis on static memories for use with microprocessors. The new 1024-bit random access memory for instance requires no external clock or peripheral refresh circuitry and its organization (4 × 256) means that a complete 256-word eight-bit memory can be assembled with two of the new chips (RA-3-4256) instead of eight



WW313



WW315

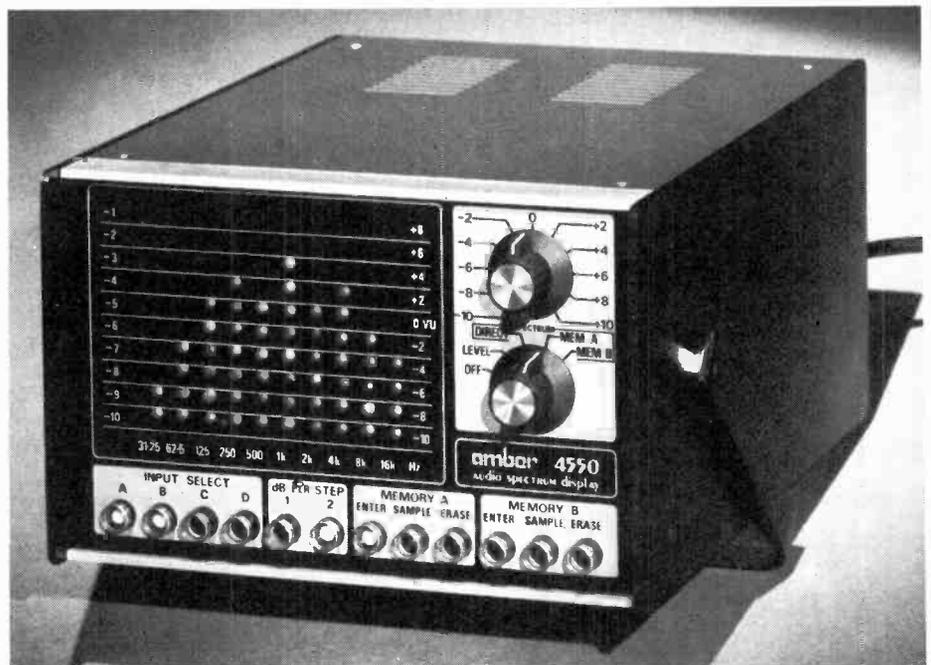

WW317

1024×1 bit r.a.ms. It has separate data input and output lines, eliminating the need for external multiplexing circuitry. Tri-state data outputs allow easy assembly of larger memories. Operated from a single +5V supply, read access and write cycle time is 1 μ s. The circuit is the first to use General Instruments Giant II n-channel ion-implantation facility at Glenrothes. General Instruments Microelectronics Ltd, 57 Mortimer Street, London W1N 7TD.

WW320 for further details

Dynamic r.a.m.

National Semiconductor 4096×1-bit random access read/write memory is a dynamic memory featuring a common input/output. The fully-decoded memory has an access time of 200ns and a cycle time of 400ns. The device is manufactured using the n-channel silicon gate technique with a single transistor cell providing a high memory density. It is housed in an 18-pin dual-in-line package. National Semiconductor GmbH, D808 Furstenfeldbruck, Industriestrasse 10, Germany.

WW321 for further details

Hybrid active filters

Tantalum thin-film active filters by Siemens feature a maximum temperature coefficient of 40×10⁻⁶ parts per Kelvin (e.g. a temperature change of 50 deg C will give a change in frequency of 0.2%). The close compensation of resistance and capacitance coefficients is achieved by using tantalum nitride resistors and beta-tantalum capacitors. Op-amp types TAA861, 761 or TBA 221 are used in these hybrid circuits. The synthesis technique used allows design of second-order filters with a Q factor of 100 from 100Hz to 1kHz and a Q of 50 up to 10kHz. Siemens Ltd, Great West House, Great West Road, Brentford, Middx.

WW322 for further details

Chalnicon TV tube

The Toshiba Chalnicon TV camera tube is claimed to have advantages over conventional vidicon and Plumbicon tubes in medicine, broadcasting, and industrial application. It has a target structure of photoconductive cadmium selenide, giving an almost-flat spectral response with a sharp cut off beyond 700nm. Toshiba say that the dark-current increase or decrease in light sensitivity that occurs in conventional vidicons, and the white spot growth that occurs in Plumbicons seldom occurs in the Chalnicon. Tubes are available with either magnetic or electrostatic focus in 18 or 25-mm sizes, having a 600mW heater. One tube, type E5095 intended for compact TV cameras, has a target to all-other-electrode capacitance of 2pF. Tube types E5001 and E5063, intended for use with image intensifiers in x-ray equipment and featuring a sensitivity of 1.5 times that of the Plumbicon and 3.5 times that of the vidicon, enables patient x-ray dose to be reduced proportionately. Toshiba (UK)

Ltd, Tube & Semiconductor Dept, Toshiba House, Great South West Road, Feltham, Middx TW14 0PG.

WW323 for further details

Semiconductor memory

A new type of semiconductor memory—the factory programmable read-only memory or f.r.o.m.—announced by Motorola offers advantages of a high-speed fusible-link p.r.o.m. but at lower cost. Like the standard p.r.o.m., programming is carried out by fusing nichrome resistor links, but in this case it is factory programmed. Because programming currents are applied using probes directly on the chip, the need for fuse-current steering and addressing circuitry is eliminated. The new device is produced in emitter-coupled circuitry with an organization of 256 word ×4 bits. Enable-to-output access time is 7ns, while address-to-output access time is 20ns. This speed is achieved with a 150-mA drain from a -5.2-Volt supply. Motorola Ltd, York House, Empire Way, Wembley, Middx.

WW324 for further details

Domestic infra-red headphone links?

The new photodiode type BPW34 from Siemens is developed especially for receiving modulated infra-red radiation over a room link from either television, radio or record players to headphones. The diffuse distribution of infra-red radiation means the head is free to turn in any direction. The problem in designing the photodiode is to collect as much radiation as possible whilst keeping capacitance small to obtain a high cut-off frequency. The Siemens diode can operate with modulation of a 100-kHz and a bandwidth of 50kHz despite the relatively large area of 9mm². An infra-red filter layer prevents visible light entering. Transmitter is an array of four LD241 luminescent diodes, the peak power of 60mW being adequate for medium-sized rooms. Siemens Ltd, Great West House, Great West Road, Brentford, Middx.

WW325 for further details

Counter for electronic watches

A silicon-on-sapphire timing circuit (TA6778) is the first s.o.s. device from RCA. Use of sapphire as an insulating substrate rather than silicon for m.o.s. structures results in smaller unwanted capacitances, leading to higher speeds and lower power dissipation than with standard c.m.o.s. circuits. The timing circuit is a ripple-counter for single-battery circuits. Voltage range is 1.1 to 5V but for a watch using a 4.195-MHz AT-cut crystal, range is 1.45 to 1.6V and for a 1.048-MHz SL-cut crystal range is 1.1 to 1.6V. Circuit is capable of operating up to 80MHz for 1.6mW at 5V. Consumption at 1MHz and 1.6V is about 2 μ W. RCA Ltd, Sunbury-on-Thames, Middx

WW326 for further details

Solid State Devices

The names of suppliers of devices in this section are given in abbreviation after each entry and in full at the end of the section.

Sample and hold

A sample and hold amplifier, model 4855, has an acquisition time of 250ns and conversion rates of over 250kHz with a claimed accuracy to within 0.01%. Bandwidth is 80kHz and aperture settling time is 0.2s.

WW350 for further details

Teledyne Philbrick

Switching transistors

Types BUY86 and BUY87 have a maximum current rating of 7.0A with collector-to-emitter saturation voltages of 1.0 and 1.3V respectively. Both transistors are n-p-n silicon planar, epitaxial types in TO-3 metal cases and have a V_{CEO} of 100 and 150V respectively.

WW351 for further details

Mullard

R.f. transistors

A range of r.f. power transistors, MRF230 to MRF234, for use in the 40–100MHz band have power outputs of 1.5, 3.5, 7.5, 15 and 25W respectively from a 12.5V supply. All devices purchased are tested at 30:1 v.s.w.r. at all phase angles.

WW352 for further details

Motorola

High speed p.r.o.m.

The type 3604 4k p.r.o.m. is organised as 512 words of 8 bits. The device has a typical power consumption of 0.3mW per bit, an address-to-output delay of 70ns, and a chip select-to-output delay of 30ns.

WW353 for further details

Walmore

High voltage op-amp

The new 3580 series of f.e.t.-input operational amplifiers provide output swings of up to 290V peak-to-peak. The devices, which are either encapsulated modules or integrated, have self-contained automatic thermal protection and will dissipate about three watts or up to 4.5W with a suitable heat sink.

WW354 for further details

Burr Brown

Suppliers

Teledyne Philbrick, Heathrow House, Bath Road, Cranford, Middx.

Mullard Ltd, Mullard House, Torrington Place, London WC1E 7HD.

Motorola Ltd, Semiconductor Products Division, York House, Empire Way, Wembley, Middx.


Walmore Electronics Ltd, 11–15 Betterton Street, Drury Lane, London WC2 9BS. Burr Brown, 25A King Street, Watford, Herts WD1 8BT.

New Course in Digital Design

Understand the latest developments in calculators, computers, watches, telephones, television, automotive instrumentation

Each of the 6 volumes of this self-instruction course measures 11¼" x 8¼" and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers.

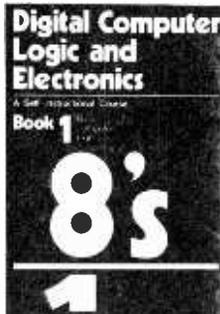After completing this course you will have broadened your career prospects and considerably increased your fundamental understanding of the changing technological world around you.



Digital Computer Logic and Electronics
A Self-Instructional Course
Book 1
8's

Also available — a more elementary course assuming no prior knowledge except simple arithmetic.

In 4 volumes:

1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flip flops and Registers

£3.95 inc p&p

Offer Order this together with Design of Digital Systems for the bargain price of £9.25.

Design of Digital Systems contains over twice as much information in each volume as the simpler course, Digital Computer Logic and Electronics. All the information in the simpler course is covered as part of the first volumes of Design of Digital Systems which, as you can see from its contents, also covers many more advanced topics.

Designer Manager Enthusiast Scientist Engineer Student

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.


Guarantee—no risk to you

If you are not entirely satisfied with Design of Digital Systems or Digital Computer Logic and Electronics, you may return them to us and your money will be refunded in full, no questions asked.

Design of Digital Systems

A Self-Instruction Course in 6 Volumes

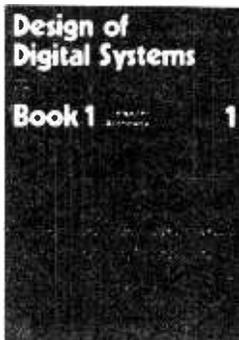- 1 Computer Arithmetic**
- 2 Boolean Logic**
- 3 Arithmetic Circuits**
- 4 Memories & Counters**
- 5 Calculator Design**
- 6 Computer Architecture**



£5.95

including packing and surface post anywhere in the world (VAT zero rated). Payments may be made in foreign currencies. Quantity discounts are available on request. Total packaged weight does not exceed 4lb —please allow enough extra for air mail.

To: Cambridge Learning Enterprises,
FREEPOST, St. Ives, Huntingdon, Cambs PE17 4BR.

*Please send me.....set(s) of Design of Digital Systems at £5.95 each,
*or.....set(s) of Digital Computer Logic and Electronics at £3.95 each,
*or.....combined set(s) at £9.25 each.

Name.....

Address.....

.....

.....

*delete as applicable.
No need to use a stamp—just print FREEPOST on the envelope.

E.H.T. POWERUNIT. 110/240v. 50Hz giving 5 K.V. at 50 m/a. METERED OUTPUT. £17.50.

COPPER LAMINATE P.C. BOARD
 8 1/2 x 6 x 1/8 inch 20p sheet. 3 for 55p. P.P. 10p.
 10 x 4 x 1/8 inch 12p sheet. 5 for 50p. P.P. 15p.
 10 1/2 x 5 1/2 x 1/8 inch 20p sheet. 3 for 55p. P.P. 10p.
 14 x 6 1/2 x 1/8 inch 30p sheet. 3 for 80p. P.P. 15p.
 Offcut pack (smallest 4 x 2 inch) 50p. 300 sq. in. P.P. 5p single sheet. 20p Bargain Packs.

TELEPHONE DIALS (New) £1 ea.

RELAYS (G.P.O. '3000'). All types. Brand new from 37p ea. 10 up quotations only.

EXTENSION TELEPHONES (Type 706) Various Colours £3.50. P.P. 50p. Excellent condition.

RATCHET RELAYS. (310 ohm) Various Types 85p. P.P. 15p.

UNISELECTORS (NEW) 25 way 12 Bank (Non Bridging) 68 ohms. £2. P.P. 30p.



PRECISION A.C. MILLIVOLTMETER (Solartron) 1.5m.v. to 15v. 60db to 20db. 9 ranges. Excellent condition. £22.50. P.P. £1.50.

HIGH CAPACITY ELECTROLYTICS
 2,200uf. at 50v. (2 x 1 1/4 in.) 40p. P.P. 5p. 2,200uf. 100v. (1 1/2 x 4 in.) 75p. 3,150uf. 40v. (1 1/2 x 4 in.) 60p. 10,000uf. 25v. (1 1/2 x 4 in.) 60p. 12,000uf. 40v. (2 x 4 in.) 75p. 16,000uf. 16v. (2 x 4 in.) 60p. 21,000uf. 40v. (2 1/2 x 4 in.) £1. 2,800uf. 100v. (4 x 2 in.) 80p. 35,000uf. 40v. (3 x 4 in.) £1. P.P. 15p.

H.D. ALARM BELLS. 6 in. Dome 6/8 volt D.C. £2.25. P.P. 50p.

OVERLOAD CUT-OUTS. Panel mounting (1 1/2 x 1 1/2 in.) 800 M/A/1.8 amp/10 amp. 35p ea. P.P. 5p.

BULK COMPONENT OFFER. Resistors/Capacitors. All types and values. All new modern components. Over 500 pieces £2. P.P. 20p. (Trial order 100pcs. 50p.) We are confident you will re-order.

REGULATED POWER SUPPLY. Input 110/240v. Output 9v. DC. 1 1/2 amp. 12v. D.C. 500 m/a. £4. P.P. 40p.

S. Q. C.B.S. DECODER MODULE
 Complete with I.C. M.C.1312P.
 With the removal of 6 components a direct electrical substitute for P. E. 'RONDO' Board. £4 each.

U.K. ORDERS 8% V.A.T. SURCHARGE

TRANSFORMERS

ADVANCE "VOLSTAT" TRANSFORMERS. Input 242v. A.C.

CV50. 38v. at 1 amp; 25v. at 100 m/a. 75v. at 200 m/a. £2 ea. P.P. 40p.

CV75. 25v. at 2 1/2 amp. £2.50. P.P. 50p.

CV100. 50v. at 2 amp; 50v. at 100 m/a. £3. P.P. 50p.

CV250. 25v. at 8 amp; 75v. at 1/2 amp. £5. P.P. £1.

CV500. 45v. at 3 amp; 35v. at 2 amp; 25v. at 3 amp. £7. P.P. £1.50.

L.T. TRANSFORMER "TOROIDAL": Prim. 240v. Sec. 30v. at 1.5 amp. Size 3 inch dia. 1/2 inch thick at £1.25. P.P. 10p.

L.T. TRANSFORMER: Prim. 240v. Sec. 27.0-27 at 800 m/a 7.5v. at 1.5 amp. £1.75. P.P. 25p.

L.T. TRANSFORMER. Prim. 240v. Sec. 24v. at 1 1/2 amp. £1.20. P.P. 30p.

L.T. TRANSFORMER. Prim. 110/240v. Sec. 0/24/40v 1 1/2 amp. (Shrouded). £1.50. P.P. 30p.

L.T. TRANSFORMER. Prim. 200/250v. Sec. 20/40/60v. at 2 amp. (Shrouded). £2.25. P.P. 40p.

L.T. TRANSFORMER (H.D.) Prim. 200/250v. Sec. 18v. at 27 amp; 40v. at 9.8 amp; 40v. at 3.6 amp; 52v. at 1 amp; 25v. at 3.7 amp. £15. P.P. £2.

H.T. TRANSFORMER. Prim. 110/240v. Sec. 400v. 100 m/a. £2. P.P. 50p.

E.H.T. TRANSFORMER. 240v. Sec. 1800v. 50 mA. £2.50. P.P. 50p.

L.T. TRANSFORMER. 110/240v. ('C. Core). Secs. 1/3/9/27v. at 10 amps. £6.50. P.P. £1.

L.T. TRANSFORMER. Prim. 240v. Sec. 16/0/16v. at 2 amp. £1.60. P.P. 30p.

L.T. TRANSFORMER. Prim. 110/240v. Sec. 23/0/23v. at 1.8 amp; 50v. at 300 m/a; 3.15/0/3.15v. at 300 m/a. £1.75. P.P. 30p.

L.T. TRANSFORMER. Prim. 200/240v. ('C. Core). Secs. 1v./3v./9v./8v. all at 1.5A; 50v. at 1 amp. £2. P.P. 30p.

L.T. TRANSFORMER. 110/240v. ('C. Core). Sec. 13.5v. 4A.; 39v. at 2A. £2.50. P.P. 30p.

L.T. TRANSFORMER. 110/240v. ('C. Core) 1v./3v./9v./20v./20v. all at 2 amp. £3. P.P. 40p. Same Secondaries but at 4 amp. £4.25. P.P. 50p.

L.T. TRANSFORMER. 110/240v. ('C. Core). Secs. 1v./3v./9v. all at 10 amp; 35v. at 1 amp; 50v. at 750 m/a £5.25. P.P. 75p.

HIGH-SPEED MAGNETIC COUNTERS. 4 digit (non reset) 24v. or 48v. (state which) 4 x 1 x 1 in. 40p. P.P. 10p.

5 digit (Non-reset) 24v. 75p. P.P. 10p.

3 digit 12v. (Rotary Reset) 2 1/2 x 1 1/2 x 1 1/2 in. £1 each. P.P. 10p.

6 digit (Reset) 240v. A.C. £3.50. P.P. 10p.



RIBBON CABLE (8 colours) £1.25. P.P. 15p. 10m: £10. P.P. 50p. 100m. 8 cores 7mm bonded side by side ribbon form.

1000 Type KEY SWITCHES. Single 2 x 4 c/o Locking 50p. P.P. 10p. Bank of 4. 2 x 4 c/o each switch (one biased). £1.20. P.P. 15p.

RELAYS

SIEMENS/VARLEY PLUG-IN. Complete with transparent dust covers and bases. 2 pole c/o contacts 35p ea.; 6 make contacts 40p ea.; 4 pole c/o contacts 50p ea. P.P. 5p ea. 6-12-24-48v. types in stock.

12 VOLT H.D. RELAYS. 2 pole 3 way 40p. P.P. 10p.

240v. A.C. RELAYS. (Plug-in type), 3 change-over 10 amp. contacts. 75p (with base). P.P. 10p.

P.A.R. BISTABLE RELAY (Latching) 24v. D.C. 4 c/o contacts 65p. P.P. 10p.

SILICON BRIDGES. 100 P.I.V. 1 amp 2 x 2 x 2 in. 30p. P.P. 5p. 200 P.I.V. 2 amp. 60p. P.P. 5p.

24 VOLT A.C. RELAYS (Plug-in). 3 Pole Change-over 60p. P.P. 5p. 2 Pole Change-over 45p. P.P. 5p.

S. T. C. CRYSTAL FILTERS. (10.7 Mhz) 445-LQU-901A (50Khz spacing) £3. 445-LQU-901B (25Khz spacing) £4.

WE REGRET THAT ALL ORDERS VALUE UNDER £5 MUST BE ACCOMPANIED BY REMITTANCE.

PATRICK & KINNIE
 191 LONDON ROAD · ROMFORD · ESSEX
 ROMFORD 44473 RM7 9DD

TRANSISTORS		Type Price (£)											
AC107	0.35	BC119	0.29	BD123	0.98	BF213	0.16	BUV79	0.43	ZT X500	0.17	2N3794	0.20
AC117	0.24	BC125	0.22	BD124	0.80	BF236	0.35	BUV79	0.43	ZT X502	0.17	2N3819	0.35
AC126	0.25	BC125B	0.25	BD130Y	1.42	BF485	0.48	CRS1/40	0.45	ZT X504	0.42	2N3820	0.49
AC127	0.25	BC126	0.20	BD131	0.45	BF459	0.51	CRS3/40	0.55	ZT X602	0.24	2N3823	1.45
AC128	0.25	BC132	0.15	BD132	0.50	BF596	0.40	D40N1	0.45	2N525	0.86	2N3877	0.25
AC141	0.26	BC134	0.20	BD135	0.40	BF597	0.15	ED122	0.55	2N596	0.25	2N3904	0.16
AC141K	0.21	BC135	0.15	BD137	0.48	BF611	0.30	ES024	0.20	2N597	0.15	2N3905	0.18
AC142K	0.19	BC136	0.20	BD138	0.50	BF624	0.35	ME6001	0.18	2N706	0.12	2N3906	0.15
AC151	0.24	BC137	0.20	BD139	0.55	BF710	0.55	ME6002	0.17	2N706A	0.15	2N4032	0.31
AC152	0.25	BC138	0.20	BD140	0.62	BF711	0.55	ME340	0.68	2N744	0.30	2N4036	0.52
AC153K	0.28	BC142	0.30	BD144	2.19	BF716A	1.70	ME341	0.72	2N914	0.19	2N4058	0.17
AC154	0.20	BC143	0.35	BD145	0.75	BF730	1.38	ME370	0.65	2N918	0.13	2N4123	0.16
AC176	0.25	BC147B	0.13	BD163	0.67	BF759	0.19	MJ E590	0.95	2N918	0.42	2N4124	0.15
AC187	0.25	BC148	0.12	BD183	0.58	BF760	0.20	MJ E521	0.95	2N930	0.35	2N4126	0.20
AC187K	0.25	BC149	0.14	BD234	0.75	BF790	0.28	ME2955	1.20	2N1304	0.21	2N4236	1.90
AC188	0.25	BC152	0.25	BD519	0.76	BFX16	2.25	MJ E3055	0.74	2N1305	0.21	2N4248	0.12
AC188K	0.26	BC153	0.20	BD520	0.76	BFX29	0.30	MM721	0.70	2N1306	0.31	2N4284	0.19
AC193K	0.30	BC154	0.20	BDX18	0.45	BFX30	0.35	MPF102	0.40	2N1307	0.22	2N4286	0.19
AC194K	0.32	BC157	0.15	BDX32	2.55	BFX85	0.25	MPS A05	0.47	2N1308	0.28	2N4288	0.13
AC198	0.25	BC158	0.15	BDY16A	0.38	BFY01	0.48	MPS A55	0.50	2N1309	0.38	2N4288	0.20
ACV39	0.68	BC159	0.15	BDY18	1.78	BFX86	0.26	MPS6566	0.21	2N1613	0.34	2N4290	0.14
AD140	0.50	BC161	0.48	BDY20	0.99	BFX87	0.28	MPSU05	0.68	2N1711	0.45	2N4291	0.18
AD142	0.52	BC167B	0.15	BF115	0.20	BFX88	0.24	MPSU06	0.76	2N1890	0.45	2N4292	0.20
AD143	0.51	BC168B	0.13	BF117	0.40	BFY18	0.53	MPSU55	1.28	2N1893	0.48	2N4871	0.24
AD149	0.50	BC169C	0.13	BF120	0.25	BFY40	0.40	MPSU56	1.28	2N2102	0.31	2N4902	1.30
AD161	0.48	BC170	0.15	BF121	0.25	BFY41	0.40	OC26	0.38	2N2117	0.36	2N4927	1.05
AD162	0.48	BC171	0.15	BF122	0.25	BFY50	0.25	OC28	0.65	2N2218	0.60	2N5066	0.32
AF114	0.25	BC172	0.14	BF125	0.25	BFY51	0.23	OC35	0.50	2N2219	0.50	2N5061	0.35
AF115	0.25	BC173	0.20	BF127	0.20	BFY52	0.23	OC36	0.55	2N2221A	0.41	2N5064	0.45
AF116	0.25	BC176	0.22	BF158	0.25	BFY57	0.32	OC42	0.35	2N2222A	0.50	2N5087	0.32
AF117	0.20	BC177	0.20	BF159	0.25	BFY64	0.42	OC44	0.15	2N2369A	0.42	2N5294	0.35
AF118	0.50	BC178	0.20	BF180	0.45	BFY72	0.31	OC45	0.15	2N2401	0.60	2N5296	0.37
AF121	0.30	BC178B	0.22	BF181	0.45	BFY90	0.70	OC70	0.15	2N2484	0.41	2N5298	0.38
AF124	0.25	BC179	0.20	BF182	0.45	BFY15A	0.79	OC71	0.15	2N2570	0.18	2N5322	0.85
AF125	0.20	BC179B	0.21	BF183	0.45	BPX25	1.65	OC72	0.15	2N2646	0.53	2N5449	1.90
AF126	0.20	BC182L	0.11	BF167	0.25	BPX29	1.60	OC73	0.51	2N2712	0.12	2N5457	0.30
AF127	0.20	BC183	0.11	BF173	0.25	BPX32	1.90	OC75	0.25	2N2904	0.22	2N5458	0.35
AF139	0.35	BC183K	0.12	BF177	0.30	BRCA4443	0.60	OC81	0.25	2N2904A	0.26	2N5494	1.85
AF147	0.35	BC183L	0.11	BF178	0.33	BRY39	0.42	OC81D	0.30	2N2905	0.72	2N5496	0.85
AF149	0.45	BC184L	0.13	BF179	0.33	BRY01	0.35	OC139	0.28	2N2905A	0.73	2N5497	0.85
AF178	0.55	BC186	0.25	BF180	0.35	BSWV64	0.38	OC140	0.30	2N2926G	0.13	2N6178	0.71
AF179	0.60	BC187	0.28	BF181	0.33	BSX19	0.13	OC170	0.25	2N2926V	0.12	2N6180	0.78
AF180	0.55	BC208	0.12	BF182	0.44	BSX20	0.19	OC171	0.30	2N29260	0.12	2SC643A	1.36
AF181	0.50	BC212L	0.12	BF183	0.44	BSX76	0.15	OCP71	0.43	2N3019	0.75	2SC1172Y	2.80
AF186	0.40	BC213L	0.12	BF184	0.28	BSX82	0.52	ONP188	0.68	2N3053	0.21	3N1140	1.21
AF239	0.40	BC214L	0.15	BF185	0.26	BSY19	0.52	ONP236A	0.15	2N3054	0.55	40250	0.60
AF273	0.84	BC238	0.10	BF194	0.15	BSY41	0.22	ORP12	0.55	2N3055	0.60	40327	0.67
AL100	1.10	BC261A	0.28	BF195	0.15	BSY54	0.50	R2008B	2.05	2N3133	0.54	40361	0.48
AL102	1.10	BC262A	0.18	BF196	0.15	BSY56	0.60	R2010B	2.10	2N3134	0.60	40362	0.50
AL103	1.10	BC263B	0.25	BF197	0.17	BSY65	0.15	TAG3/400	1.54	2N3232	1.32	40429	0.80
AL113	0.95	BC267	0.16	BF198	0.20	BSY78	0.40	TIC44	0.24	2N3235	1.10	40439	2.67
AU103	1.40	BC268C	0.14	BF199	0.25	BSY91	0.28	TIC46	0.58	2N3254	0.48	AC178/	0.52
AU110	1.40	BC294	0.27	BF200	0.35	BT101/300	1.05	TIC47	0.24	2N3255	0.48	AC176	0.52
AU113	1.70	BC300	0.58	BF218	0.38	BT101/500	1.15	TIC29A	0.49	2N3257	0.48	AC176K/	0.52
BC107	0.12	BC301	0.35	BF222	1.05	BT102/300	1.02	TIP30A	0.58	2N3702	0.13	AC142K	0.56
BC107A	0.13	BC303	0.60	BF224J	0.15	BT102/500	1.12	TIP31A	0.65	2N3703	0.15	AC187/	0.56

TELEPRINTER EQUIPMENT LIMITED

**Sales . . . Rentals . . . New . . . Refurbished . . . Installation . . .
Maintenance . . . Overhauls . . . Spare Parts . . . Prompt Deliveries**

CREED EQUIPMENT

TELEPRINTERS Models 7B, 54, 75, 444
PERFORATORS 7PN, 85/86, PR75, 25
TAPE READERS 6S4, 6S5, 6S6, 6S6M, 92, 35, 71, 72, 74
HIGH-SPEED TAPE WINDERS 80-0-80V POWER SUPPLY UNITS, etc.

TELETYPE CORP. EQUIPMENT

TELEPRINTERS 15, 19, 20, 28, 32, 33, 35
all configurations
PERFORATORS 14, 19, 28 LPR, RECEIVE & MONITOR GROUP CABINETS
TAPE TRANSMITTERS 14, 20, 28 LBXD & LXD TRANSMIT GROUPS, etc.

SIEMENS EQUIPMENT

TELEPRINTERS T100 and T-68 in various configurations
PERFORATORS T-LOCH 12, T-LOCH 15, A, B, D & F, etc.

OTHER EQUIPMENT

KLEINSCHMIDT, OLIVETTI, LORENZ, COCQUELET, BRITISH, AMERICAN,
CONTINENTAL, ARABIC and other layouts, 5-8 track.

SPECIAL EQUIPMENT

SOLID STATE MOTOR CONTROLS, MODEM INTERFACE UNITS, TARRIFF J
INTERFACE UNITS, TEST EQUIPMENT, COMPUTER INTERFACE UNITS, DEC.
PDP8 and others. SILENCE COVERS AND CABINETS, TELEPRINTER TABLES,
SIGNALLING RECTIFIERS AND CONVERTORS, TAPE HOLDERS.

WW 350 FOR FURTHER DETAILS

COMMUNICATION ACCESSORIES & EQUIPMENT LIMITED

G.P.O. TYPE COMPONENTS FOR PROMPT DELIVERY

JACK PLUGS—201, 310, 316, 309, 404, 420, 609, 610, 1603 — 3201
JACK STRIPS—310, 320, 510, 520, 810
JACK SOCKETS—300, 500, 800, B3 and B6 mountings, 19, 84A and 95A
PATCH PANELS & RACKS—made to specifications
LAMPS, SWITCHBOARD NO. 2, BALLAST PO 11, LAMP STRIPS, 10-way PO 19, 20-way PO 17, Lamp Caps,
Holder No. 12
CORDS (PATCHING & SWITCHBOARD)—made to specifications
TERMINAL BLOCKS (DISTRIBUTION)—20-way up to 250-way
LOW PASS FILTERS—type 4B and PANELS, TELEGRAPH 71 (15 × 4B)
POLARISED TELEGRAPH RELAYS AND UNISELECTORS—various types and manufactures both P.O. and
miniature
LINE TRANSFORMERS/RETARDATION COILS—type 48A, 48H, 49H, 149H, 3/16, 3/216, 3/48A, 3/43A, 48J, etc.
FUSE & PROTECTOR MOUNTINGS—8064 A/B 4028, H15B, H40 and individual.1/2
COILS—39A, 40A, 40E, etc.
P.O.-TYPE KEYS—1000 and PLUNGER TYPES 228, 279, etc.
EQUIPMENT RACKS AND CONSOLES—made to specifications
RELAY ADJUSTING TOOLS, TOOL BAGS FOR MECHANICS, TENSION GAUGES, ARMATURE ADJUSTERS,
SPRING BENDERS ETC. VARIOUS SWITCHBOARD EQUIPMENT.

WW 351 FOR FURTHER DETAILS

MORSE EQUIPMENT LIMITED

The GNT Range of Automatic Morse Equipment is now manufactured in the U.K. and comprises complete equipment for Morse Training Schools and for Automatic Morse Transmission. Models available include:

KEYBOARD PERFORATORS for offline tape preparation
AUTOMATIC TAPE TRANSMITTERS with speeds up to 250 w.p.m.
MORSEINKERS specially designed for training, producing dots and dashes on tape
HEAVY DUTY MORSE KEYS
UNDULATORS for automatic record and W/T signals up to 300 w.p.m.
CODE CONVERTERS converting from 5-unit tape to Morse and vice versa
MORSE REPERFORATORS operating up to 200 w.p.m.
TONE GENERATORS and all Students' requirements
CREED, MORSE EQUIPMENT, PERFORATORS, REPERFORATORS, TRANSMITTERS, PRINTERS, MARCONI UG6 UNDULATORS, BUZZERS, ALDIS LAMPS, etc.

WW 352 FOR FURTHER DETAILS

77 AKEMAN STREET, TRING, HERTS., U.K.

Telephone: Tring 4011, STD: 0442-82 Telex 82362, Answerback: Batelcom Tring

The largest selection

BRAND NEW FULLY GUARANTEED DEVICES

AC107 0-22	AD161 A	BC150 0-20	BD131 0-55	BF183 0-44	MJE3440 0-55	2G309 0-39	2N2194 0-39	2N3053 0-19	2N4058 0-13
AC113 0-20	AD162 (MP)	BC151 0-22	BD132 0-62	BF184 0-28	MFP102 0-46	2G339 0-22	2N2217 0-24	2N3054 0-51	2N4059 0-11
AC115 0-20	AD163 0-75	BC152 0-19	BD133 0-76	BF185 0-38	MFP104 0-41	2G349 0-18	2N2218 0-22	2N3055 0-45	2N4060 0-13
AC117K 0-22	AD170 0-55	BC153 0-31	BD135 0-44	BF187 0-30	MFP105 0-41	2G349 0-20	2N2219 0-22	2N3091 0-16	2N4061 0-13
AC122 0-13	AF114 0-27	BC154 0-35	BD136 0-44	BF188 0-44	OC19 0-70	2G345 0-18	2N2220 0-22	2N3304 0-18	2N4062 0-13
AC125 0-19	AF115 0-27	BC157 0-20	BD137 0-50	BF194 0-13	OC19 0-39	2G371 0-18	2N2221 0-22	2N3392 0-18	2N4284 0-19
AC126 0-19	AF116 0-27	BC158 0-13	BD138 0-55	BF195 0-13	OC29 0-62	2G371 0-18	2N2222 0-22	2N3393 0-16	2N4285 0-19
AC127 0-20	AF117 0-27	BC159 0-13	BD139 0-61	BF196 0-16	OC29 0-55	2G373 0-19	2N2268 0-18	2N3394 0-16	2N4286 0-19
AC128 0-20	AF118 0-39	BC160 0-50	BD140 0-86	BF197 0-16	OC24 0-82	2G374 0-18	2N2269 0-16	2N3395 0-19	2N4287 0-19
AC132 0-16	AF124 0-33	BC161 0-55	BD155 0-88	BF200 0-50	OC25 0-42	2G377 0-39	2N2369 0-16	2N3402 0-23	2N4288 0-19
AC134 0-18	AF125 0-39	BC162 0-13	BD175 0-66	BF202 1-00	OC26 0-32	2G378 0-19	2N2411 0-27	2N3403 0-23	2N4289 0-19
AC137 0-18	AF126 0-31	BC163 0-13	BD176 0-66	BF205 0-50	OC28 0-55	2G381 0-18	2N2412 0-27	2N3404 0-31	2N4290 0-19
AC141 0-30	AF127 0-31	BC169 0-13	BD177 0-72	BF208 0-66	OC29 0-55	2G382 0-18	2N2446 0-52	2N3405 0-46	2N4291 0-19
AC141K 0-32	AF139 0-33	BC170 0-13	BD178 0-72	BF209 0-64	OC35 0-46	2G401 0-33	2N2711 0-23	2N3414 0-17	2N4292 0-19
AC142 0-20	AF178 0-55	BC171 0-16	BD179 0-77	BF262 0-91	OC36 0-55	2G414 0-33	2N2712 0-23	2N3415 0-17	2N4293 0-19
AC142K 0-28	AF179 0-55	BC172 0-16	BD180 0-77	BF263 0-61	OC41 0-22	2G417 0-28	2N2714 0-23	2N3416 0-31	2N5172 0-13
AC151 0-17	AF190 0-55	BC173 0-16	BD185 0-78	BF270 0-39	OC42 0-27	2G437 0-39	2N2704 0-18	2N3417 0-31	2N5294 0-60
AC154 0-22	AF181 0-55	BC174 0-16	BD186 0-72	BF271 0-33	OC44 0-17	2G388A 0-31	2N2905 0-23	2N3555 0-53	2N5457 0-35
AC155 0-22	AF196 0-55	BC175 0-24	BD187 0-77	BF272 0-38	OC45 0-14	2N404 0-22	2N2906 0-23	2N3614 0-74	2N5458 0-35
AC156 0-22	AF239 0-41	BC177 0-21	BD188 0-77	BF273 0-33	OC70 0-11	2N404A 0-31	2N2906A 0-23	2N3615 0-82	2N5459 0-44
AC157 0-22	AL102 0-72	BC178 0-21	BD189 0-83	BF274 0-39	OC71 0-11	2N524 0-46	2N2906 0-23	2N3616 0-82	2N6121 0-75
AC165 0-22	AL103 0-72	BC179 0-21	BD190 0-83	BF275 0-33	OC72 0-16	2N527 0-45	2N2906A 0-20	2N3646 0-10	2N6301 0-55
AC166 0-22	AS236 0-28	BC180 0-27	BD195 0-94	BF276 0-33	OC74 0-16	2N538 0-46	2N2907 0-22	2N3702 0-13	2N6302A 0-46
AC167 0-22	AS237 0-33	BC181 0-27	BD196 0-94	BF277 0-33	OC75 0-17	2N538 0-46	2N2907A 0-22	2N3703 0-13	2N6302 0-46
AC168 0-27	AS238 0-28	BC182 0-16	BD197 0-99	BF278 0-33	OC76 0-17	2N538 0-46	2N2908 0-16	2N3704 0-13	2N6303 0-61
AC169 0-16	AS239 0-28	BC183 0-16	BD199 1-05	BF279 0-27	OC81 0-17	2N538 0-46	2N2925 0-16	2N3705 0-13	2N6304 0-77
AC176 0-22	AS240 0-28	BC184 0-22	BD200 1-05	BF280 0-24	OC81D 0-17	2N538 0-46	2N2926 0-16	2N3706 0-13	2N6305 0-88
AC177 0-27	AS241 0-28	BC185 0-22	BD201 0-88	BF281 0-22	OC82 0-17	2N538 0-46	2N2926(1)	2N3707 0-14	2N6306 0-86
AC178 0-31	AS242 0-28	BC186 0-22	BD202 1-05	BF282 0-22	OC82D 0-17	2N538 0-46	2N2926(1)	2N3708 0-03	2N6307 0-86
AC179 0-31	AS243 0-28	BC187 0-31	BD203 1-05	BF283 0-22	OC83 0-22	2N538 0-46	2N2926(1)	2N3709 0-10	2N6308 0-86
AC180 0-22	AS244 0-28	BC188 0-31	BD204 1-05	BF284 0-22	OC83 0-22	2N538 0-46	2N2926(1)	2N3710 0-10	2N6309 0-86
AC180K 0-32	AS245 0-28	BC189 0-31	BD205 1-05	BF285 0-22	OC84 0-17	2N538 0-46	2N2926(1)	2N3711 0-10	2N6310 0-86
AC181 0-22	AS246 0-28	BC190 0-31	BD206 1-05	BF286 0-22	OC85 0-22	2N538 0-46	2N2926(1)	2N3712 0-10	2N6311 0-86
AC181K 0-32	AS247 0-28	BC191 0-31	BD207 1-05	BF287 0-22	OC86 0-22	2N538 0-46	2N2926(1)	2N3713 0-10	2N6312 0-86
AC187 0-24	AS248 0-28	BC192 0-31	BD208 1-05	BF288 0-22	OC87 0-28	2N538 0-46	2N2926(1)	2N3714 0-10	2N6313 0-86
AC187K 0-25	AS249 0-28	BC193 0-31	BD209 1-05	BF289 0-22	OC88 0-17	2N538 0-46	2N2926(1)	2N3715 0-10	2N6314 0-86
AC188 0-24	AS250 0-28	BC194 0-31	BD210 1-05	BF290 0-22	OC89 0-17	2N538 0-46	2N2926(1)	2N3716 0-10	2N6315 0-86
AC188K 0-25	AS251 0-28	BC195 0-31	BD211 0-88	BF291 0-22	OC90 0-17	2N538 0-46	2N2926(1)	2N3717 0-10	2N6316 0-86
AC197 0-28	AS252 0-28	BC196 0-31	BD212 0-88	BF292 0-22	OC91 0-17	2N538 0-46	2N2926(1)	2N3718 0-10	2N6317 0-86
AC198 0-22	AS253 0-28	BC197 0-31	BD213 0-88	BF293 0-22	OC92 0-17	2N538 0-46	2N2926(1)	2N3719 0-10	2N6318 0-86
AC199 0-22	AS254 0-28	BC198 0-31	BD214 0-88	BF294 0-22	OC93 0-17	2N538 0-46	2N2926(1)	2N3720 0-10	2N6319 0-86
AC200 0-22	AS255 0-28	BC199 0-31	BD215 0-88	BF295 0-22	OC94 0-17	2N538 0-46	2N2926(1)	2N3721 0-10	2N6320 0-86
AC201 0-22	AS256 0-28	BC200 0-12	BD216 0-88	BF296 0-22	OC95 0-17	2N538 0-46	2N2926(1)	2N3722 0-10	2N6321 0-86
AC202 0-18	AS257 0-28	BC201 0-12	BD217 0-88	BF297 0-22	OC96 0-17	2N538 0-46	2N2926(1)	2N3723 0-10	2N6322 0-86
AC203 0-18	AS258 0-28	BC202 0-12	BD218 0-88	BF298 0-22	OC97 0-17	2N538 0-46	2N2926(1)	2N3724 0-10	2N6323 0-86
AC204 0-18	AS259 0-28	BC203 0-12	BD219 0-88	BF299 0-22	OC98 0-17	2N538 0-46	2N2926(1)	2N3725 0-10	2N6324 0-86
AC205 0-18	AS260 0-28	BC204 0-12	BD220 0-88	BF300 0-22	OC99 0-17	2N538 0-46	2N2926(1)	2N3726 0-10	2N6325 0-86
AC206 0-18	AS261 0-28	BC205 0-12	BD221 0-88	BF301 0-22	OC100 0-17	2N538 0-46	2N2926(1)	2N3727 0-10	2N6326 0-86
AC207 0-18	AS262 0-28	BC206 0-12	BD222 0-88	BF302 0-22	OC101 0-17	2N538 0-46	2N2926(1)	2N3728 0-10	2N6327 0-86
AC208 0-18	AS263 0-28	BC207 0-12	BD223 0-88	BF303 0-22	OC102 0-17	2N538 0-46	2N2926(1)	2N3729 0-10	2N6328 0-86
AC209 0-18	AS264 0-28	BC208 0-12	BD224 0-88	BF304 0-22	OC103 0-17	2N538 0-46	2N2926(1)	2N3730 0-10	2N6329 0-86
AC210 0-18	AS265 0-28	BC209 0-12	BD225 0-88	BF305 0-22	OC104 0-17	2N538 0-46	2N2926(1)	2N3731 0-10	2N6330 0-86
AC211 0-18	AS266 0-28	BC210 0-12	BD226 0-88	BF306 0-22	OC105 0-17	2N538 0-46	2N2926(1)	2N3732 0-10	2N6331 0-86
AC212 0-18	AS267 0-28	BC211 0-12	BD227 0-88	BF307 0-22	OC106 0-17	2N538 0-46	2N2926(1)	2N3733 0-10	2N6332 0-86
AC213 0-18	AS268 0-28	BC212 0-12	BD228 0-88	BF308 0-22	OC107 0-17	2N538 0-46	2N2926(1)	2N3734 0-10	2N6333 0-86
AC214 0-18	AS269 0-28	BC213 0-12	BD229 0-88	BF309 0-22	OC108 0-17	2N538 0-46	2N2926(1)	2N3735 0-10	2N6334 0-86
AC215 0-18	AS270 0-28	BC214 0-12	BD230 0-88	BF310 0-22	OC109 0-17	2N538 0-46	2N2926(1)	2N3736 0-10	2N6335 0-86
AC216 0-18	AS271 0-28	BC215 0-12	BD231 0-88	BF311 0-22	OC110 0-17	2N538 0-46	2N2926(1)	2N3737 0-10	2N6336 0-86
AC217 0-18	AS272 0-28	BC216 0-12	BD232 0-88	BF312 0-22	OC111 0-17	2N538 0-46	2N2926(1)	2N3738 0-10	2N6337 0-86
AC218 0-18	AS273 0-28	BC217 0-12	BD233 0-88	BF313 0-22	OC112 0-17	2N538 0-46	2N2926(1)	2N3739 0-10	2N6338 0-86
AC219 0-18	AS274 0-28	BC218 0-12	BD234 0-88	BF314 0-22	OC113 0-17	2N538 0-46	2N2926(1)	2N3740 0-10	2N6339 0-86
AC220 0-18	AS275 0-28	BC219 0-12	BD235 0-88	BF315 0-22	OC114 0-17	2N538 0-46	2N2926(1)	2N3741 0-10	2N6340 0-86
AC221 0-18	AS276 0-28	BC220 0-12	BD236 0-88	BF316 0-22	OC115 0-17	2N538 0-46	2N2926(1)	2N3742 0-10	2N6341 0-86
AC222 0-18	AS277 0-28	BC221 0-12	BD237 0-88	BF317 0-22	OC116 0-17	2N538 0-46	2N2926(1)	2N3743 0-10	2N6342 0-86
AC223 0-18	AS278 0-28	BC222 0-12	BD238 0-88	BF318 0-22	OC117 0-17	2N538 0-46	2N2926(1)	2N3744 0-10	2N6343 0-86
AC224 0-18	AS279 0-28	BC223 0-12	BD239 0-88	BF319 0-22	OC118 0-17	2N538 0-46	2N2926(1)	2N3745 0-10	2N6344 0-86
AC225 0-18	AS280 0-28	BC224 0-12	BD240 0-88	BF320 0-22	OC119 0-17	2N538 0-46	2N2926(1)	2N3746 0-10	2N6345 0-86
AC226 0-18	AS281 0-28	BC225 0-12	BD241 0-88	BF321 0-22	OC120 0-17	2N538 0-46	2N2926(1)	2N3747 0-10	2N6346 0-86
AC227 0-18	AS282 0-28	BC226 0-12	BD242 0-88	BF322 0-22	OC121 0-17	2N538 0-46	2N2926(1)	2N3748 0-10	2N6347 0-86
AC228 0-18	AS283 0-28	BC227 0-12	BD243 0-88	BF323 0-22	OC122 0-17	2N538 0-46	2N2926(1)	2N3749 0-10	2N6348 0-86
AC229 0-18	AS284 0-28	BC228 0-12	BD244 0-88	BF324 0-22	OC123 0-17	2N538 0-46	2N2926(1)	2N3750 0-10	2N6349 0-86
AC230 0-18	AS285 0-28	BC229 0-12	BD245 0-88	BF325 0-22	OC124 0-17	2N538 0-46	2N2926(1)	2N3751 0-10	2N6350 0-86
AC231 0-18	AS286 0-28	BC230 0-12	BD246 0-88	BF326 0-22	OC125 0-17	2N538 0-46	2N2926(1)	2N3752 0-10	2N6351 0-86
AC232 0-18	AS287 0-28	BC231 0-12	BD247 0-88	BF327 0-22	OC126 0-17	2N538 0-46	2N2926(1)	2N3753 0-10	2N6352 0-86
AC233 0-18	AS288 0-28	BC232 0-12	BD248 0-88	BF328 0-22	OC127 0-17	2N538 0-46	2N2926(1)	2N3754 0-10	2N6353 0-86
AC234 0-18	AS289 0-28	BC233 0-12	BD249 0-88</						

-the lowest prices!

74 Series T.T.L. I.C.'S

BI-PAK STILL LOWEST IN PRICE FULL SPECIFICATION
GUARANTEED. ALL FAMOUS MANUFACTURERS



Part No.	1	25	100+	Part No.	1	25	100+
SN7400	0.15	0.14	0.13	SN7453	0.16	0.15	0.14
SN7401	0.15	0.14	0.13	SN7454	0.18	0.18	0.14
SN7402	0.15	0.14	0.13	SN7460	0.16	0.15	0.14
SN7403	0.15	0.14	0.13	SN7470	0.32	0.29	0.27
SN7404	0.15	0.14	0.13	SN7472	0.32	0.29	0.27
SN7405	0.15	0.14	0.13	SN7473	0.41	0.39	0.35
SN7406	0.39	0.34	0.31	SN7474	0.41	0.39	0.35
SN7407	0.39	0.34	0.31	SN7475	0.60	0.58	0.56
SN7408	0.25	0.24	0.23	SN7476	0.44	0.43	0.42
SN7409	0.25	0.24	0.23	SN7480	0.16	0.15	0.14
SN7410	0.15	0.14	0.13	SN7481	£1.10	£1.05	£1.00
SN7411	0.25	0.24	0.23	SN7482	0.90	0.85	0.80
SN7412	0.28	0.27	0.26	SN7483	£1.20	£1.15	£1.05
SN7413	0.32	0.31	0.30	SN7484	£1.00	0.97	0.95
SN7415	0.30	0.29	0.28	SN7485	£1.60	£1.55	£1.50
SN7417	0.30	0.29	0.28	SN7486	0.25	0.24	0.23
SN7420	0.15	0.14	0.13	SN7489	£4.00	£3.75	£3.50
SN7422	0.30	0.29	0.28	SN7490	0.65	0.63	0.60
SN7423	0.40	0.39	0.38	SN7491	£1.10	£1.05	£1.00
SN7425	0.40	0.39	0.38	SN7492	0.74	0.71	0.64
SN7426	0.40	0.39	0.38	SN7493	0.74	0.71	0.64
SN7427	0.40	0.39	0.38	SN7494	0.85	0.82	0.75
SN7428	0.45	0.44	0.40	SN7495	0.85	0.82	0.75
SN7430	0.15	0.14	0.13	SN7496	0.98	0.93	0.88
SN7432	0.40	0.38	0.38	SN74100	£1.50	£1.45	£1.40
SN7433	0.42	0.40	0.38	SN74104	0.60	0.58	0.55
SN7437	0.35	0.32	0.30	SN74105	0.60	0.58	0.55
SN7438	0.35	0.32	0.30	SN74107	0.44	0.42	0.40
SN7440	0.15	0.14	0.13	SN74110	0.60	0.58	0.55
SN7441	0.74	0.71	0.64	SN74111	0.60	0.58	0.55
SN7442	0.74	0.71	0.64	SN74118	£1.00	0.95	0.90
SN7443	£1.20	£1.15	£1.10	SN74119	£1.50	£1.40	£1.30
SN7444	£1.20	£1.15	£1.10	SN74121	0.50	0.48	0.45
SN7445	£1.60	£1.55	£1.50	SN74122	0.70	0.68	0.65
SN7446	£1.20	£1.15	£1.10	SN74123	0.75	0.73	0.70
SN7447	£1.10	£1.07	£1.05	SN74141	0.85	0.82	0.79
SN7448	£1.10	£1.07	£1.05	SN74145	£1.80	£1.75	£1.70
SN7450	0.15	0.14	0.13	SN74150	£1.50	£1.40	£1.30
SN7451	0.15	0.14	0.13	SN74151	£1.10	£1.05	£1.00

NOW WE GIVE YOU 50w PEAK (25w R.M.S.) PLUS THERMAL PROTECTION!
The NEW AL60 Hi-Fi Audio Amplifier FOR ONLY £4.25



- Max Heat Sink temp. 90°C.
- Frequency Response 20Hz to 100KHz
- Distortion better than 0.1% at 1KHz.
- Supply voltage 15-50 volts
- Thermal Feedback
- Latest Design Improvements
- Load—3, 4, 8 or 16 ohms
- Signal to noise ratio 80dB
- Overall size 63mm x 105mm x 13mm

Especially designed to a strict specification. Only the finest components have been used and the latest solid state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

FULLY BUILT—TESTED and GUARANTEED

STABILISED POWER MODULE SPM80 £3.25



SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer BmT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 65 mm x 105 mm x 20 mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including: Disco Systems, Public Address, Intercom Units, etc. Handbook available, 10p.

TRANSFORMER BMT80 £2.15 p. & p. 25p

STEREO PRE-AMPLIFIER TYPE PA100



Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL60 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages.

Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

SPECIFICATION:
Frequency response 20Hz—20KHz ±1dB
Harmonic distortion better than 0.1%
Inputs: 1. Tape head 3.25mV into 50KΩ
2. Radio, Tuner 75mV into 50KΩ
3. Magnetic P.U. 3mV into 50KΩ
All input voltages are for an output of 250mV.
Tape and P.U. inputs equalised to RIAA curve within ±1dB from 20Hz to 20KHz.

only £14.25

MK 60 AUDIO KIT Comprising: 2 x AL60, 1 x SPM80, 1 x BMT80, 1 x PA100, 1 front panel, 1 kit of parts to include on-off switch, neon indicator, stereo headphone sockets plus instruction booklets. Complete Price: £29.75 plus 30p postage.

TEAK 60 AUDIO KIT Comprising: Teak veneered cabinet size 16 1/2" x 11 1/2" x 3 1/2", other parts include aluminium chassis, heatsink and front panel bracket, plus back panel and appropriate sockets etc. Kit price: £29.95 plus 30p postage.

INTEGRATED CIRCUIT PAKS

Manufacturers "Full Outs" which include Functional and Part-Functional Units. These are classed as 'out-of-spec' from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Part No.	Contents	Price	Part No.	Contents	Price
UIC01	—12 x 7400	0.54	UIC46	—5 x 7446	0.54
UIC01	—12 x 7401	0.54	UIC48	—5 x 7448	0.54
UIC02	—12 x 7402	0.54	UIC50	—12 x 7450	0.54
UIC03	—12 x 7403	0.54	UIC51	—12 x 7451	0.54
UIC04	—12 x 7404	0.54	UIC53	—12 x 7453	0.54
UIC05	—12 x 7405	0.54	UIC54	—12 x 7454	0.54
UIC06	—8 x 7406	0.54	UIC56	—12 x 7460	0.54
UIC07	—8 x 7407	0.54	UIC70	—8 x 7470	0.54
UIC10	—12 x 7410	0.54	UIC72	—8 x 7472	0.54
UIC20	—12 x 7420	0.54	UIC73	—8 x 7473	0.54
UIC30	—12 x 7430	0.54	UIC74	—8 x 7474	0.54
UIC40	—12 x 7440	0.54	UIC76	—8 x 7476	0.54
UIC41	—5 x 7441	0.54	UIC80	—8 x 7480	0.54
UIC42	—5 x 7442	0.54	UIC81	—5 x 7481	0.54
UIC43	—6 x 7443	0.54	UIC82	—5 x 7482	0.54
UIC44	—5 x 7444	0.54	UIC83	—5 x 7483	0.54
UIC45	—5 x 7445	0.54	UIC86	—5 x 7486	0.54

LINEAR I.C.'S—FULL SPEC.

Type No.	1	25	100+
72702	0.50	0.48	0.45
72709	0.25	0.23	0.20
72709P	0.20	0.19	0.18
72710	0.35	0.33	0.30
72711	0.30	0.29	0.28
72712	0.25	0.27	0.26
72714P	0.30	0.29	0.28
72717	0.85	0.80	0.75
72718P	0.38	0.36	0.34
SL20C	0.59	0.45	0.40
SL70C	0.50	0.45	0.40
SL702C	0.50	0.45	0.40
TAA263	0.80	0.70	0.60
TAA293	£1.00	0.95	0.90
TAA350A	£1.85	£1.80	£1.70
PA703C	0.28	0.28	0.24
PA709C	0.20	0.19	0.18
PA711	0.35	0.33	0.30
PA712	0.35	0.33	0.30
TBA800	£1.50	£1.45	£1.40
76003	£1.50	£1.45	£1.40
76023	£1.50	£1.45	£1.40
76060	0.95	0.93	0.90
LM380	£1.00	0.87	0.85
NE555	0.65	0.63	0.60
NE556	0.95	0.93	0.90

DTL 930 SERIES LOGIC I.C.'S

Type	1	25	100+
BP930	0.15	0.14	0.13
BP932	0.16	0.15	0.14
BP933	0.18	0.15	0.14
BP935	0.18	0.15	0.14
BP936	0.18	0.15	0.14
BP944	0.18	0.15	0.14
BP945	0.30	0.28	0.25
BP946	0.15	0.14	0.13
BP948	0.30	0.28	0.25
BP951	0.70	0.65	0.60
BP962	0.15	0.14	0.13
BP903	0.45	0.43	0.40
BP904	0.45	0.43	0.40
BP907	0.45	0.43	0.40
BP909	0.45	0.43	0.40

DUAL-IN-LINE SOCKETS

Part No.	Price
14 & 16 Lead Sockets for use with DUAL-IN-LINE I.C.'s. TWO Ranges PROFESSIONAL & NEW LOW COST. PROF. TYPE No. 1-24 25-39 100up	0.54
TSO 14 pin type	33p 30p 27p
TSO 16 pin type	38p 35p 32p
LOW COST No.	
BPS 14 pin type	16p 14p 12p
BPS 16 pin type	17p 15p 13p
BPS 8 pin type	15p 13p 11p

NUMERICAL INDICATOR TUBES

Type	Description	Price
5015F	Minitron	£1.50
MAN 3M	L.E.D. 7-segment 0-127"	£1.90

All indicators 0.9" x Decimal point. All side viewing. Full data for all types available on request.

SHPS80 STEREO HEADPHONES


1-16 ohms impedance. Frequency response 20 to 20,000Hz. Stereo/mono switch and volume controls. £4.95

1975 BI-PAK CATALOGUE & LISTS

Send S.A.E. and 10p

The STEREO 20

The 'Stereo 20' amplifier is mounted, ready wired and tested on a one-piece chassis measuring 20 cm. x 14 cm. x 6.5 cm. This compact unit comes complete with on/off switch volume control, balance, bass and treble controls, Transformer, Power supply and Power amps. Attractively printed front panel and matching control knobs. The 'Stereo 20' has been designed to fit into most turntable plinths without interfering with the mechanism or, alternatively, into a separate cabinet. Output power 20w peak. Input 1 (Cer.) 300mV into 1M. Freq. Res. 25Hz-25KHz. Input 2 (Aux.) 4mV into 30K. Harmonic distortion. Bass control ±12dB at 60Hz typically 0.25% at 1 watt. Treble con. ±14dB at 14KHz.

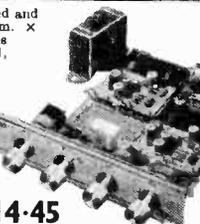

£14.45

EDGE 3166 TRIPLE 66 BIT DYNAMIC SHIFT REGISTER TTL Compatible. Low Clock Capacitance, High Speed Diode Protected Inputs Wired 'OR' Capability SPECIFICATION SHEET AVAILABLE £1 each

TEAK VENEERED CABINET for:

STEREO 20

TC 20. £3.95 p&p 30p

E.M.I. LEK 350 Loudspeaker System Enclosure kit in teak veneer, including speakers. Rec. our SPECIAL PRICE £38 per pair P. & P. £1.00p. WHILE STOCKS LAST!

3 TERMINAL POSITIVE VOLTAGE REGULATORS

Type	Price
µA7805/1.129 5V (Eqv. to MVR5)	£1.35
µA7812/1.130 12V (Eqv. to MVR12V)	£1.35
µA7815/1.131 15V (Eqv. to MVR15V)	£1.35
µA7818 18V	£1.35

TRANSFORMERS

T461 (Use with AL10) £1.60 P. & P. 15p.
T538 (Use with AL20 & AL30) £2.30 P. & P. 15p.
BMT80 (Use with AL60) £2.75 P. & P. 25p.

POWER SUPPLIES

PS 12. (Use with AL10, AL20 & AL30) 95p
SPM 80. (Use with AL60) £3.25

PA 12. PRE-AMPLIFIER SPECIFICATION

The PA 12 pre-amplifier has been designed to match into most budget stereo systems. It is compatible with the AL 10, AL 20 and AL 30 audio power amplifiers and it can be supplied from their associated power supplies. There are two stereo inputs, one has been designed for use with Ceramic cartridge sets the auxiliary input will suit most Magnetic cartridges. Full details are given in the specification table. The four controls are, from left to right: Volume and on/off switch, balance, bass and treble. Size 152mm x 84mm x 35mm

PRICE

£4.35

FRONT PANELS FP12 50p

FREQUENCY RESPONSE

20Hz-50KHz (-3dB)

Bass control—

±12dB at 60Hz

Treble control—

±14dB at 14KHz

*Input 1. Impedance

1 Meg. ohm

Sensitivity 300mV

†Input 2. Impedance

30 K ohms

Sensitivity 4mV

All prices inclusive of V.A.T. Gira No. 388 - 7006

Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 15p. Overseas add extra for airmail.

Minimum order 55p. Cash with order please.

Guaranteed Satisfaction or Money Back

CHROMASONIC electronics

Dept 5
56, Fortis Green Road, London, N10 3HN.
telephone: 01-883 3705

INDUCTORS

Denco Maxi-Q Coils

Ferrite Rod Aerials



FRA1 Long & Medium Wave band (300pf) 86p
FRA2 Long & Medium " (500pf) 86p

Tuning Coils in two series:
Range

1	150 kHz	to	400 kHz
2	515 kHz	to	1.545 MHz
3	1.67 MHz	to	5.3 MHz
4	5 MHz	to	15 MHz
5	10.5 MHz	to	31.5 MHz
6	30 MHz	to	50 MHz
7	45 MHz	to	78 MHz

* 50 pf tuning, all others based on 300 pf.

Series A Transistor - 48p each

Only available in ranges 1 to 5 inc.
4 Coils complete each range:

- Blue - Aerial Coil
 - Yellow - R.F. Interstage
 - Red - Osc. Coil for 465 kHz I.F.
 - White - Osc. Coil for 1.6 MHz I.F.
- give range number ; letter 'T' and colour.

Series B Dual Purpose Coils 48p each

For FET or Valve Circuits
All ranges available
5 Coils complete each range:

- Blue - Aerial
 - Yellow - Interstage R.F.
 - Green - R.F. plus reaction
 - Red - Osc. Coil for 465 kHz I.F.
 - White - Osc. Coil for 1.6 MHz I.F.
- (Note use Red instead of White for ranges 6 & 7).


Chokes



We stock from 1 μH to 19 mH
Check levels & prices when ordering

TUNING CONDENSERS

TYPE E

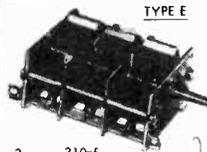

3 gang 310pf
£3.99

TYPE C804



83p
Slow Motion Drive
Ratio 6:1 Ref: 4511

TYPE O



365 pf £1.07
365 x 365 pf £1.30

TYPE OO




208 + 176 pf
with screen &
trimmers
£1.48

DILECON



100pf 69p
300pf 69p
500pf 69p

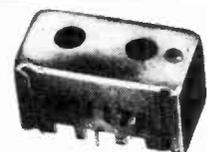

Tuned Block Filter incorporating a
Ceramic element. Pre-aligned
to 470 KHz. 3db bandwidth 5KHz.
Zin 100K. Zout 100K.

LP1175 £1.46

I.F. Transformers

I FT 13	465 kHz 1st & 2nd d/tuned	65p
I FT 14	465 kHz final single tuned	65p
I FT 15	10.7 MHz d/tuned	65p
I FT 16	1.6 MHz 1st & 2nd d/tuned	65p
I FT 17	1.6 MHz Final d/tuned	65p
I FT 18	465 kHz or 1.6 MHz d/tuned	75p

VEROBOARD



	COPPERCLAD	PLAIN	EXTRA
	0.1"	0.15"	0.15"
2 1/2" x 1"	7p	7p	-
2 1/2" x 3 1/2"	26p	21p	12p
2 1/2" x 5"	30p	25p	13p
3 1/2" x 3 1/2"	30p	25p	-
3 1/2" x 5"	34p	34p	25p
17" x 2 1/2"	90p	69p	45p
17" x 3 1/2"	£1.21	75p	57p
17" x 5"	-	99p	10p

D.I.P. Breadboard 4.15" x 6.15" £1.40
VEROSTRIP (State .1" or .15") 30p
Pin Insertion Tool (State .1" or .15") 63p
Spot Face Cutter 51p
Terminal Pins in Pkts. of 50 (State .1" or .15") 22p

Details of I.C.'s; Rectifiers; Diodes; Bridges; Passive Components; LED's; Clocks; Triacs etc. can be seen on other pages and/or issues of Wireless World; Practical Wireless; and Practical Electronics.

DIODES

AA119	10p	BY103	22p	OA91	8p
AA120	10p	BY105	16p	OA200	11p
AA129	10p	BY126	16p	OA202	12p
BA100	10p	BY127	16p	ZS120	8p
BA102	27p	BY133	23p	ZS140	25p
BA110	44p	BY164	54p	ZS141	42p
BA115	19p	BY176	£1.62	ZS142	32p
BA144	20p	BY182	£1.62	ZS170	10p
BA145	22p	BY250	25p	ZS270	11p
BA148	22p	BZX70	27p	ZS271	14p
BA154	20p	Series		ZS278	36p
BA155	15p	BZY88	11p	IN914	8p
BA156	16p	Series		IN916	10p
BAX16	10p	OA47	11p	IN4009	7p
BB104	45p	OA79	10p	IN4148	5p
BB105B	41p	OA81	8p	IN4448	9p
BY100	16p	OA85	10p	I ZS Series	18p
		OA90	8p		

Electrolytics

VUF	4V	6.3V	10V	16V	25V	40V	63V	100V	160V	450V
1							63p		83p	15p
1.5							63p			
2.2							63p		83p	
3.3							63p			
4.7							63p		83p	17p(40F)
6.8						63p	63p	83p		
8										21p
10						63p	63p	83p		
15						63p	63p	11p		
22						63p	63p			24p(160F)
33		63p		63p	63p	63p	8p			33p(320F)
47	63p		63p	63p	63p	8p	11p			25p(500F)
68		63p		63p		8p	14p			350V
100			63p	63p	63p	8p	14p	25p		
150				63p	8p	11p	14p			
220			63p	8p	11p	14p	19p	31p		
330			63p	8p	11p	14p	25p	44p		
470		8p	11p	14p	20p	26p	47p			
680		10p		14p	20p	25p	59p			
1000	13p		14p	19p	22p	25p	44p	79p		
1500		18p	19p	25p						
2200		18p	24p		39p	44p	79p	149p		
3300		26p								
4700				44p	68p	79p	149p	252p		
6800				75p						

TRANSISTORS

AC107	16p	BC213L	13p	D13V	52p	ZTX301	13p	2N3707	12p
AC126	13p	BC214L	13p	D40N3	59p	ZTX302	17p	2N3708	10p
AC127	13p	BC268	15p	MJ480	93p	ZTX303	14p	2N3709	10p
AC128	13p	BC407	16p	MJ481	£1.18	ZTX304	21p	2N3710	11p
AC176	15p	BCY70	17p	MJ490	£1.01 1/2	ZTX311	10p	2N3711	11p
AC187	20p	BCY71	22p	MJ491	£1.42 1/2	ZTX312	10p	2N3772	£2.00
AC187K	20p	BCY72	17p	MJ900	£1.42 1/2	ZTX341	22p	2N3791	£2.55
AC188	22p	BD115	73p	MJ1000	£1.22	ZTX384	18p	2N3819	27p
AC188K	25p	BD123	89p	MJ2955	£1.88 1/2	ZTX500	12p	2N3821	81p
ACY17	39p	BD124	80p	MJ3055	£1.21	ZTX501	13p	2N3823	99p
ADY17	38p	BD131	44p	MJ4000	£1.46 1/2	ZTX502	17p	2N3903	15p
ADY20	22p	BD132	52p	MJ4010	£1.95 1/2	ZTX503	14p	2N3904	15p
AD140	48p	BD131/2PR	£1.17	MJE340	45p	ZTX504	42p	2N3905	23p
AD149	48p	BD135	41p	MJE350	97p	ZTX531	22p	2N3906	25p
AD161	37p	BD136	43p	MJE2955	£1.20	ZTX550	17p	2N4056	13p
AD162	38p	BD201	£1.95 1/2	MJE3055	72p	2N697	16p	2N4059	19p
AD161/62MP	74p	BD202	£1.46 1/2	MPF102	27p	2N706	13p	2N4062	16p
AF114	17p	BF109	74p	MPF103	40p	2N708	16p	2N4289	19p
AF115	17p	BF115	25p	MPF104	44p	2N914	24p	2N4441	85p
AF116	17p	BF160	25p	MPF105	44p	2N930	22p	2N4442	£1.04 1/2
AF117	17p	BF167	24p	MPF106	49p	2N1302	20p	2N4443	£1.42 1/2
AF118	54p	BF173	24p	MPF111	22p	2N1303	24p	2N4444	£2.06 1/2
AF124	32p	BF178	28p	MPSU06	63p	2N1304	24p	2N4871	59p
AF139	34p	BF179	32p	MPSU56	77p	2N1305	24p	2N4901	£1.41 1/2
AF172	25p	BF180	32p	OC28	49p	2N1306	24p	2N5067	£1.07 1/2
AF239	40p	BF181	32p	OC35	49p	2N1307	27p	2N5129	16p
ASV26	32p	BF184	27p	OC36	49p	2N1308	34p	2N5172	11p
BC107	11p	BF185	27p	OC44	14p	2N1309	34p	2N5191	77p
BC108	11p	BF194	15p	OC45	14p	2N1711	26p	2N5194	91p
BC109	12p	BF195	17p	OC71	14p	2N1718	£4.37	2N5295	52p
BC117	22p	BF196	16p	OC72	14p	2N1893	52p	2N5447	16p
BC147	10p	BF197	16p	OC75	15p	2N2218	22p	2N5449	16p
BC148	10p	BF200	31p	OC76	27p	2N2219	38p	2N5457	16p
BC149	10p	BF2448	27p	OC81	14p	2N2646	54p	2N5458	43p
BC157	13p	BF262	25p	OC83	25p	2N2894	97p	2N5459	43p
BC158	12p	BF263	25p	OC170	27p	2N2904	32p	2N5485	52p
BC159	14p	BF272	£1.19	OC171	32p	2N2905	30p	2N5777	48p
BC167	17p			OC71	£1.54 1/2	2N2924	16p	2N6068	44p
BC168B	11p	BF597	23p	ORP12	65p	2N2925	18p	2N6069	51p
DC169	12p	BF598	20p	TIP29	53p	2N2926	10p	2N6070	57p
BC171	20p	BFW10	65p	TIP31	67p	2N3053	19p	2N6071	62p
BC172	17p	BFX 29	41p	TIP31A	67p	2N3054	50p	2N6073	67p
BC177	22p	BFY08	26p	TIP32A	79p	2N3075	51p	2N6075	£1.46 1/2
BC178	22p	BFY50	22p	TIP41A	79p	2N3355	£3.56 1/2	2N6076	16p
BC179	24p	BFY51	22p	TIP42A	97p	2N3442	£1.19	2N6111	54p
BC182	11p	BFY90	£1.09	11543	36p	2N3566	18p	2N6288	60p
BC1810	22p	BR100	42p	11588A	36p	2N3638	20p	3N140	99p
BC183L	12p	BRV39	43p	11591	32p	2N3702	13p	3N141	87p
BC184L	12p	BSX20	18p	ZTX107	10p	2N3703	12p	3N153	87p
BC187	27p	BSX21	22p	ZTX108	10p	2N3704	13p	40321	54p
BC204	14p	BSY95A	14p	ZTX109	15p	2N3705	12p	40430	£1.39
BC209	14p			ZTX300	12p	2N3706	14p	40673	55p
BC212L	12p								

REGULATORS

100mA (TO-39)	500mA* (TO-3)	500mA* (SOT-32)	1A (TO-220)		
		-20°C to +85°C	0°C to +70°C		
5V	TBA625A	L005T1 (MVR5V)	L129	TDA1405	7805UC
	£1.03	£1.45	£1.39	97p	£2.42
12V	TBA625B	L036T1 (MVR12V)	L130	TDA1412	7812UC
	£1.03	£1.45	£1.39	97p	£2.42
15V	TBA625C	L037T1 (MVR15V)	L131	TDA1415	7815UC
	£1.03	£1.45	£1.39	97p	£2.42

*600mA; 500mA and 450mA respectively.

DIGITAL SWITCH

BCD encoded digital switch
Reading 0 to 9. Suitable for
digital clock alarm setting
DVM input scaling etc.

1 to 9. £1.49 each.

ALUMINIUM BOXES



REF (No.)	(L)	(W)	(H)	PRICE	P&P
AB7	2 1/2"	5 1/2"	1 1/2"	45p	15

BI-PRE-PAK

Bargains in Semi-Conductors, components, modules & equipment.

**THIS MONTH'S
"BARGAIN COUNTER"**
Bi-Pre-Pak special pack
offers **ALL AT 50p EACH**
Tested and Guaranteed

B79	4	IN4007 Sil. Rec. diodes, 1,000 PIV lamp plastic
B81	10	Reed Switches, 1" long, 1/8" dia. High Speed P.O. type
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.
H38	30	Short lead Transistors. NPN Silicon Planar types
H39	6	Integrated Circuits, 4 Gates BMC 962, 2 Flip Flops BMC 945
H41	2	Sil Power transistors comp pair BD131/132
H63	4	2N3055 type NPN Sil. power transistors. Below spec. devices
H64	4	3819 N Channel FETs 2N3819 in plastic case

 **Unmarked untested packs ALL AT 50p EACH**

B1	50	Germanium Transistors PNP, AF and RF
B66	150	Germanium Diodes Min. glass type
B83	200	Transistors, manufacturers rejects, AF, RF, Sil. and Germs.
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202
B86	100	Sil. Diodes sub. min. IN914 and IN916 types
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.
H67	10	3819N Channel FETs plastic case type

Bi-Pre-Pak X-Hatch Generator Mk.2



Four-pattern selector switch
3" x 5 1/4" x 3"
Ready-built and tested

£9.93

In kit form

£7.93

Is invaluable to industrial and home user alike. Improved circuitry assures reliability and still better accuracy. Very compact; self-contained. Robustly built. Widely used by TV rental and other engineers. With strong metal case, instructions, but less batteries. (Three U2 type required.)



Stirling Sound

AMPLIFIER MODULES

SS100	Active tone control unit to provide Bass and Treble facilities (stereo).	£1.60
SS101	Pre-amp for stereo ceramic cartridges, radio tuners etc.	£1.60
SS102	Pre-amp for low-output stereo magnetic cartridges etc.	£2.25
SS103	Compact I.C. amp. 3 watts R.M.S. Single channel (mono). On P.C.B. size 3" X 2" with all components.	£1.75
SS1033	Stereo version of above. (Two I.Cs.)	£3.25
SS105	A compact all-purpose power amp. Can be run from 12V car battery. Size 2 1/2" X 1 3/4". Useful 5w output (mono). Excellent value.	£1.95
SS110	Similar in size to SS105 but will give 10w output (mono). Two in stereo five first class results, suitable for many domestic applications.	£2.40
SS140	Beautifully designed. Will give up to 40w R.M.S. into 4Ω. Excellent S.N.R. and transient response. Fine for P.A., disco use etc.	£6.26

FM Tuners

SS201	Front End Assembly. Ganged tuning condenser with well engineered slow motion geared drive in robust housing and diseminator stage. Excellent sensitivity. 88-108MHz.	£6.25
SS202	I.F. Stage (with I.C.). Designed to use with SS201 uses I.C. Carefully checked before despatch.	£5.25
SS203	Stereo Recorder. Designed essentially for use with SS201 and SS202, this excellent decoder can also make a stereo tuner of almost any single channel FM tuner. Supplied ready aligned. A L.E.M. can easily be fitted.	£5.62
SS300	Power Supply Stabiliser. Add this to your unstabilised supply to obtain a steady powerful working voltage for your audio system. Money saving and very reliable.	£5.62

- **ALL MODULES TESTED & GUARANTEED**
- **FULLY DETAILED & WELL PRINTED INSTRUCTIONS**
- **Postage—Add 15p for packing & postage (UK) + 8% VAT to total value.**

Plastic Power Transistors

IN TWO RANGES 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at irresistibly low prices. Sold under our Tested and Guaranteed terms.

Range 1. VCE Min 15. HFE Min 15.			Range 2. VCE Min. 40. HFE Min 40.				
40 Watt	1-12	13-25	26-50	40 Watt	1-12	13-25	26-50
90 Watt	20p	18p	16p	90 Watt	30p	28p	26p
	24p	22p	20p		35p	33p	30p

Please state NPN or PNP when ordering.



There's more in our latest catalogue: *More bargains—better price-values. Send large S.A.E. (6p stamp please) for your free copy. COMPONENTS, EQUIPMENT, AND OF COURSE, SEMI-CONDUCTORS.*

TERMS OF BUSINESS VAT Add 8% to total value of order including postage and packing charges. No VAT on overseas orders. **POST & PACKING** Add 15p for UK orders. Minimum mail order acceptable—50p. Overseas orders, add £1. Any difference will be credited or charged **PRICES** Subject to alteration without notice. **AVAILABILITY** All items available at time of going to press when every effort is made to ensure correctness of information.

To BI-PRE-PAK, 224-226 WEST RD, WESTCLIFF-ON-SEA, ESSEX

Please send
for which I enclose inc. VAT
NAME
ADDRESS

WWW2

BI-PRE-PAK LTD

C.O. Reg. No 820919

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SS0 9DF.


TELEPHONE: SOUTHEND (0702) 46344.

AMPLIFIER KITS OF *Distinction*

DESIGNER-APPROVED KIT

In Hi-Fi News there was published by Mr Linsley-Hood a series of four articles (November 1972-February 1973) and a subsequent follow-up article (April 1974) on a design for an amplifier of exceptional performance which has as its principal feature an ability to supply from a direct coupled fully protected output stage, power in excess of 75 watts whilst maintaining distortion at less than 0.01% even at very low power levels. The power amplifier is complemented by a pre-amplifier based on a discrete component operational amplifier referred to as the Liniac which is employed in the two most critical points of the system, namely the equalization stage and tone control stage, positions where most conventional designs run out of gain at the extremes of the frequency spectrum. Unusual features of the design are the variable transition frequencies of the tone controls and the variable slope of the scratch filter. There is a choice of four inputs, two equalized and two linear, each having independently adjustable signal level. The attractive slimline unit pictured has been made practical by highly compact PCBs and a specially designed Toroidal transformer.

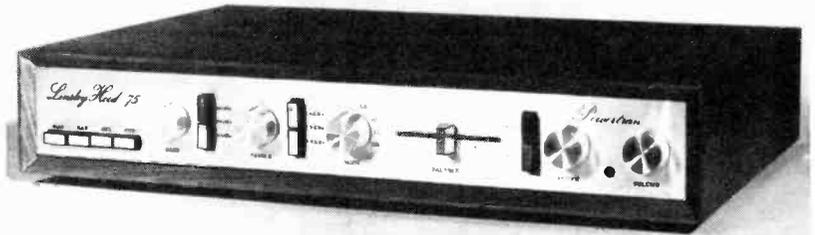Hi-Fi News Linsley-Hood 75 W Amplifier
Mk III Version (modifications as per Hi-Fi News April 1974)



Full circuit description
in handbook
(pack 15—price 30p)

FREE TEAK CASE WITH FULL KITS
£62.40 post free (U.K.)
KIT PRICE only

V.A.T. Please add 8%*
to all U.K. orders
(*or at current rate if changed)

for further information
please write for **FREE LIST**

POWERTRAN

SEE FOLLOWING PAGE

Pack	Price		Price
1 Fibreglass printed-circuit board for power amp.	£0.85	11 Fibreglass printed-circuit board for power supply	£0.65
2 Set of resistors, capacitors, pre-sets for power amp.	£1.70	12 Set of resistors, capacitors, secondary fuses, semiconductors for power supply	£3.50
3 Set of semiconductors for power amp. (now using BDY56, B0529, B0530)	£6.50	13 Set of miscellaneous parts including DIN skts, mains input skt, fuse holder, inter-connecting cable, control knobs	£4.25
4 Pair of 2 drilled, finned heat sinks	£0.80	14 Set of metalwork parts including silk screen printed fascia panel and all brackets, fixing parts, etc.	£6.30
5 Fibreglass printed-circuit board for pre-amp.	£1.30	15 Handbook	£0.30
6 Set of low noise resistors, capacitors, pre-sets for pre-amp.	£2.70	16 Teak cabinet	£7.35
7 Set of low noise, high gain semiconductors for pre-amp.	£2.40	2 each of packs 1-7 inclusive are required for complete stereo system	
8 Set of potentiometers (including mains switch)	£2.05	Total cost of individually purchased packs	£69.75
9 Set of 4 push-button switches, rotary mode switch	£3.70		
10 Toroidal transformer complete with magnetic screen/housing primary: 0-117-234 V, secondaries: 33-0-33 V, 25-0-25 V.	£9.15		



TRAMPUS ELECTRONICS LTD

58-60 GROVE ROAD,
WINDSOR, BERKS.

MONEY BACK IF NOT SATISFIED.
LARGE STOCKS. LOW PRICES.
ALL BRAND NEW TOP GRADE FULL
SPEC DEVICES. CALLERS WELCOME.

FAST SERVICE. SEND C.W.O. ADD VAT TO ALL PRICES IN U.K. P&P 15P. EUROPE 25P. OVERSEAS 65P. CATALOGUE/LIST FREE SEND S.A.E.

Digital Displays

MINITRON 3015F
0-9DP £1.15 ea
LED 0.3" digit
0-9DP £1.49 ea
JUMBO LED 0.6"
0-9DP £2.25 ea
LIQUID CRYSTAL
6 digit £18

LEDS 14p.

MINI PIN SOURCE OR RED DIFFUSE
LEDS, 209 STYLE, NO CLIP, 14P ea
FIL209 RED LED & CLIP 17P ea
BIG 1" RED LED & CLIP 18P ea
ORANGE & GREEN LEDES:
MINI 25P ea. BIG & CLIP 35P ea
INFRA RED LED £1.2N5777 33P.
PS12 PHOTO IC/amp/switch £1.

DIGITAL CLOCK

MOS INTEGRATED CIRCUITS.
AY51224 4 DIGIT CLOCK supplied
with 1pin socket & data £4.25
MM5311/14 6 DIGIT CLOCK with
28 pin socket & data £7.50
3 DIGIT DVM AY53500 £7.50
4 DIGIT COUNTER/DRIVER £7.50

CASSETTE mechanics £12.50

STEREO CASSETTE MECHANISM.
As used in imported types
costing £100. Only requires
a case & electronics heads
supplied. Send for data 15p.

IC's & Semiconductors

702 OPA 69p	MFC4000 1w AF 35p
703 RF/IF 28p	MFC4060 54p
709 1099 21p	MFC6030 52p
709 DIL 14 29p	MFC6040 90p
710 DIL 14 36p	MFC8010 11.10p
720 Radio £1.39	MFC8040 11
725 Regulator 67p	NE551 55V/us £2
741 1099 29p	NE536 FET OPA £2
741 DIL 8 51p	NE540 Driver 11
741 DIL 14 51p	NE546 AM Rxl 1.50p
747 Dual 741 89p	NE550 2v ref 75p
748 DIL 8 36p	NE555 11MLR 67p
1505 IC V/D Converter £-	NE556 Dual 11.50
7805 1A5V £1.59	NE560 PLL 35.15
7808 1A8V £1.69	NE561 PLL 35.15
7812 1A12V £1.69	NE562 PLL 35.19
7815 1A15V £1.69	NE565 PLL 32.69p
78009 1k AF 75p	NE566 Gen 32.49
76015 6k AF 1.59	NE567 Code 32.69
8058 Sig Gen 33	SN-2700 709 29p
CA5016 69p	SN-2711 711 51p
LH501 OPA 49p	SN-2748 748 56p
LH507 OPA 49p	SN-70151 11.20
LH508 11180Pa 95p	SN70660 ENIE 51
LH509K Reg. 32.29	SN76611 1F £1.25
LM571 RF/IF 12	FAD 100 & IF £2
LM572 AF/IF 12	2N100L 15
LM575 35	2N1021 11.75
LH577 2x2k 12.69	2N1055 Servo 2.50
LH580 2w AF 99p	2N114 AM Rxs 1.09
LM581) 2kpre. 12	
LM582) amp 12	
LM5900 1kOPA 69p	
IC1505 £1.20	7400 etc gates 16p
IC1506 49p	7413 Schmitt 31p
IC1510 & LED 32.69	7417 driver 11.09
IC1512 50amp 32.50	7170/72 52p
IC1530 69p	7173/7176 59p
IC1539 31	7175 48p
IC1550 55p	7190 Counter 63p
IC1551 1p	7422 Counter 69p
IC1552 1p	7424 mono 14p
IC1557 31	7411 driver 85p
IC1558 31	Full range in Cat.
IC1575 31.25	

SPECIAL OFFERS

741 29p MFC4000 35p
555 67p 2N114 11.09
BC107, BC108, BC109 9p ea
2N3055 39p Three for £1
115W/TO3 or 90W plastic
2N3819E 16p 2N3053 17p
BFY50/51/52/53 all 18p
1A50Vrect 4p ea IN914 4p

Price each:-

AC127/128 10p	FIP2955 90p
AC187/188 10p	FIP3055 55p
AD161/162 55p	FIS45 UJT 25p
BC107/8/9 9p	IN4001 4p
BC132/3/4 18p	IN4001 6p
BC147/8/9 10p	IN4148/911 4p
BC157/8/9 12p	2N697 15p
BC167/8/9 12p	2N706/8 10p
BC177/8/9 18p	2N2641 10p
BC182/3/4 11p	2N2904/5 20p
BC212/3/4 12p	2N2924 9p
*A or L	2N3053 17p
BCY 70/1/2 15p	2N3055 39p
BD151/2 59p	2N3614 49p
BFY50/1/2 18p	2N5702/3 9p
BFY55 17p	2N5703/5 10p
BSX20 12p	2N5706/7 9p
MJE2955 95p	2N5708/9 8p
2N1505 62p	2N5710/11 9p
MMP131put 19p	2N5565/64 10p
OA91 8p	2N5566/67 10p
FIP29A 18p	2N5658 10p
FIP50A 57p	2N5641/2 10p
FIP51A 61p	2N5819L 10p
FIP52A 75p	2N5852L 17p
FIP11A 78p	2N5904/6 11p
FIP42A 89p	2N1219 16p

vero NEW LOW PRICES!

VERO PINSx36 25p.
COPPER CLAD VEROBOARD 0.1"
2 1/2x5" 27p. 2 1/2x3 1/2" 24p. 3 1/2x3 1/2" 27p.
3 1/2x5" 29p. 3 1/2x17" 11.50
DIL IC's BOARDS 6x4 1/2" £1.50
24 way edge connector 60p
36way 90p. PLAIN 3 1/2"x17 11
FACE CUTTER 43p. FEC ETCHANT

DAL Open 69p

PRINTED CIRCUIT BOARD KIT £1.69
COPPER BOARD 6x4" 10p.
DESOLDER BRAID reel 59p
HEATSINKS
5T/TO5 & 18T/TO8 5p ea.
TV4 12p. IV3/TO5 16p. 4Y1/TO5 29p.

CAPACITORS

22pF to 0.1uF 4p ea. ELECTROLYTIC
25V 2/10/50/100uf op. 1000uf 20p
PRESETS VLRT: 5p. RL519 TORSES 11p

POTS A B or EGIN

ROTARY: 12p. SWITCH 13p. DUAL 38p.
SLIDERS: SINGLE: 26p. DOUBLE 48p.
SWITCHES: SPST 18p. DPDT 25p.
MINI 1P SPST 39p. PUSH 39p.

BENCH POWER SUPPLY 3-12V 55.

DIN PLUGS all 13p ea. Sockets 9p
TRANSFORMERS 1A 6/12V £1.34
BIA 10002 MODULE 15WATT AMP 35
EA1000 4W AF MODULE 32.49
8W/12V FLUORESCENT LIGHT 35.

Oil sockets

PROFESSIONAL
GOLD PLATED
& GREY NYLON.
8, 14 or 16 PIN
ONLY 15p each.



WW-029 FOR FURTHER DETAILS

FROM THE SPECIALISTS - POWERTRAN ELECTRONICS

WIRELESS WORLD AMPLIFIER DESIGNS

Component packs for a choice of three outstanding amplifiers are stocked together with packs for a regulated power supply suitable for use with a pair of any of them. Also stocked are packs for a very well-established pre-amplifier—the Bailey-Burrows design which features six inputs, a scratch and rumble filter and wide range tone controls which may be either rotary or slider operating.

30W BAILEY

- Pk. 1 F/Glass PCB £0.80
- Pk. 2 Resistors, capacitors, pots £1.75
- Pk. 3 Semiconductor set £4.70

30W BLOMLEY

- Pk. 1 F/Glass PCB £0.85
- Pk. 2 Resistors, capacitors, pots £2.15
- Pk. 3 Semiconductor set £5.60

20W LINSLEY-HOOD

- Pk. 1 F/Glass PCB £0.85
- Pk. 2 Resistors, capacitors, pots £2.40
- Pk. 3 Semiconductor set £3.35

60V REGULATED POWER SUPPLY

- Pk. 1 F/Glass PCB £0.75
- Pk. 2 Resistors, capacitors, pots £1.40
- Pk. 3 Semiconductor set £3.10

BAILEY-BURROWS PRE-AMP

- Pk. 1 F/Glass PCB £2.05
- Pk. 2 Resistors, capacitors, pre-sets, transistors £4.95
- Pk. 3R Rotary potentiometer set £1.60
- Pk. 3S Slider potentiometer set (with knobs) £2.70

STUART TAPE RECORDER

A set of three printed-circuit boards has been prepared for the stereo integrated circuit version of this high-performance Wireless World published design.

- TRRP Pk. 1 Reply amplifier F/Glass PCB £0.90
- TRRC Pk. 1 Record amp./meter drive cct. F/Glass PCB £1.40
- TROS Pk. 1 Bias/erase/stabilizer cct. F/Glass PCB £1.00

For details of component packs for this design please write for free list.

20 WATTS/CHANNEL



TOROIDAL T20 + 20

Developed from the famous Practical Wireless Texan

Designed by Texas engineers and published in a series of articles in **Practical Wireless**. The TEXAN was a remarkable breakthrough in delivering true Hi-Fi performance at exceptionally low cost. Now further developed to include a true Toroidal transformer, this slimline integrated circuit design, based upon a single F/Glass PCB, features all the normal facilities found on quality amplifiers, including scratch and rumble filters, adaptable input selector and headphones socket.

FREE TEAK CASE and HANDBOOK with full kits

ACTIVE FILTER CROSSOVER

An essential and critical component in a high-quality speaker system is the crossover unit conventionally comprising of a series of passive networks which unfortunately, though introducing reactive impedances between the amplifier and the speakers, result in the loss of the advantage of high amplifier damping factor and renders the speakers prone to overshoots and resonances. An elegant solution to this problem, described by D. C. Read in **Wireless World**, involves the use of a series of active filters splitting the output of the pre-amplifier into three channels, of closely defined bandwidth, each of which is fed to the appropriate speaker by its own power amplifier. A design for a suitable 20-watt amplifier, based on a proven Texas circuit, was also described by Mr Read. The printed-circuit board for this has been designed such that three amplifiers may be stacked and mounted together on a common heat sink to achieve a conveniently compact module.

KIT PRICE only **£28.25**
post free (U.K.)

- | | |
|--|-------|
| Pack | Price |
| 1 Set of all low noise resistors | £0.80 |
| 2 Set of all small capacitors | £1.50 |
| 3 Set of 4 power supply capacitors | £1.40 |
| 4 Set of miscellaneous parts including DIN sockets, fuses, fuse holders, control knobs, etc. | £1.90 |
| 5 Set of slide and push-button switches | £0.90 |
| 6 Set of potentiometers and selector switch | £1.45 |
| 7 Set of all semiconductors | £8.25 |
| 8 Special Toroidal Transformer | £4.95 |
| 9 Fibreglass PC Panel | £2.50 |
| 10 Complete chassis work, hardware and brackets | £4.20 |
| 11 Preformed cable/leads | £0.40 |
| 12 Handbook | £0.25 |
| 13 Teak Cabinet | £2.75 |

ACTIVE FILTER

- Pack 1 Fibreglass PCB (accommodates all filters for one channel) £1.05
 - 2 Set of pre-sets, solid tantalum capacitors, 2% metal oxide resistors, 2% polystyrene capacitors £4.20
 - 3 Set of semiconductors £2.65
- 2 off each pack required for stereo system

SUITABLE ALSO FOR FEEDING ANY OF OUR HIGH-POWER DESIGNS

READ/TEXAS 20w amp.

- Pack 1 Fibreglass PCB £0.70
 - 2 Set of resistors, capacitors pre-sets (not including O/P coupling capacitors) £1.10
 - 3 Sets of semiconductors £2.40
 - 6 off each pack required for stereo system
 - 4 Special heat sink assembly for set of 3 amplifiers £0.85
 - 5 Set of 3 O/P coupling capacitors £1.00
- 2 off packs 4, 5 required for stereo system

POWER SUPPLY

- FOR 20W/CHANNEL STEREO SYSTEM
- Pack 1 Fibreglass PCB £0.50
 - 2 Set of rectifiers, zener diode, capacitors, fuses, fuse holders £2.60
 - 3 Toroidal transformer £4.95

ENQUIRIES WELCOME For quality sets of speakers

SEMICONDUCTORS AS USED IN OUR RANGE OF QUALITY AMPLIFIERS

2N699 £0.25	2N4302 £0.60	BC182L £0.10	MJ481 £1.20	TIP29C £0.71
2N1613 £0.20	2N5087 £0.42	BC184L £0.11	MJ491 £1.30	TIP30C £0.78
2N1711 £0.25	2N5210 £0.54	BC212L £0.12	MJ521 £0.60	TIP31A £0.60
2N2926G £0.10	2N5457 £0.45	BC214L £0.14	MPSA05 £0.30	TIP32A £0.70
2N3053 £0.15	2N5459 £0.45	BCY72 £0.13	MPSA12 £0.55	TIP33A £1.00
2N3055 £0.45	2N5459 £0.30	BD525 £0.85	MPSA14 £0.35	TIP34A £1.50
2N3442 £1.20	40361 £0.40	BD530 £0.85	MPSA55 £0.35	TIP41A £0.74
2N3704 £0.10	40362 £0.45	BDY56 £1.60	MPSA65 £0.35	TIP42A £0.90
2N3707 £0.10	BC107 £0.10	BF257 £0.40	MPSA66 £0.40	IN914 £0.07
2N3711 £0.09	BC108 £0.10	BF259 £0.47	MPSU05 £0.60	IN916 £0.07
2N3819 £0.23	BC109 £0.10	BFR39 £0.25	MPSU55 £0.70	IS920 £0.10
2N3904 £0.17	BC125 £0.15	BFR79 £0.25	SN72721P £0.58	5805 £1.20
2N3906 £0.20	BC126 £0.15	BFY50 £0.20	SN72748P £0.58	
2N4058 £0.12	BC182K £0.10	TFY51 £0.20	TIP29A £0.50	
2N4062 £0.11	BC212K £0.12	BFY52 £0.20	TIP30A £0.60	

V.A.T. Please add 8%* to all U.K. orders

(*or at current rate if changed)

U.K. ORDERS—Post free (mail order only)

OVERSEAS—Postage at cost + 50p special packing

Dept. WW02

POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE ANDOVER, HANTS SP10 3NN

for further information please write for FREE LIST NOW!

FANTASTIC INSTRUMENT BARGAINS

A rare opportunity to purchase electronic instruments by leading manufacturers at rock bottom prices.

This high quality equipment, surplus to our present requirements, is in good working order and has been regularly maintained to the manufacturer's own standards.


One hundred different types of instruments are offered, representing more than £15,000 worth of equipment. Just look at the prices, the lowest ever for equipment of this quality.

Ask for the catalogue sheet of the full range today.

Instruments may be viewed by arrangement only at the address below. Please telephone for an appointment.

Please check availability of instruments by telephone when ordering. Calibration Service. Please ask for quotation.


	£ Sale Price Range
AUDIO (Professional)	
Crown	
High Power Loudspeaker Units (Altec)	70.00-80.00
Stereo Recorders	400.00-500.00
BRIDGES etc	
Radiometer	
CMB11B. Capacitance Comparator	30.00-35.00
Wayne Kerr	
601Z. LCR Bridge.	
Wide Frequency range	200.00-210.00
SR268. Source & Detector	300.00-320.00
B221/Q221. LCR Bridge	350.00-370.00
CALCULATORS	
Canon	
Briefcase size with charger and printer	20.00-25.00
COUNTERS & TIMERS	
Hewlett Packard	
5216 12MHz. 7 Digits	320.00-340.00
5246 50MHz. 6 Digit Counters	190.00-290.00
5252A 350MHz. Pre-scaler plug-ins	100.00-120.00
5253B 512MHz. Converter plug-ins	100.00-90.00
Marconi	
TF1417/2. 0-15MHz. 6 Digits	90.00-95.00
TF2401. Main Frames	On Application
TM7558. Plug-ins	On Application
TM8094/1. 0.3-2.5GHz. Plug-ins	On Application
DEVIATION METERS	
Marconi	
TF791D. 4-1024MHz.	182.00-220.00
DIGITAL VOLTMETERS	
Dana	
3800A Digital Multimeter.	
0.1%. 3 Digits	140.00-180.00

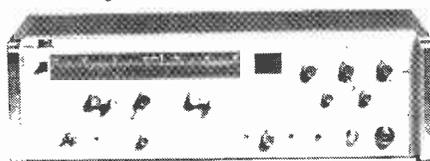

Dynamco	
DM2022. DV. 0.02% 10µV resolution to 2kV	130.00-290.00
DM2140/A1/B1. Mean AC. Converters	200.00-220.00
DM2140/A1/B3. RMS AC. Converters	64.00-78.00
Hewlett Packard	
3440 and range of plug-ins (Complete)	600.00-610.00
Solartron	
LM1420. 2. DC. 0.05% 2.5µV resolution to 1kV	110.00-190.00
LM1420. 2. BA-DC and RMS/Mean AC	350.00-400.00

OSCILLOSCOPES

	£ Sale Price Range
Cossor	
CDU150. DC-35MHz. 5mV-50V/DIV dual trace	400.00-410.00
Dynaco	
7100. DC-30MHz. Main Frames	100.00-150.00
1Y2. DC-30MHz. Dual Trace Amplifier Plug-ins	25.00-40.00
1Y4. 625 lines TV Monitor	60.00
1 X 1. Time Base plug-ins	20.00-40.00
1 X 2. Time Base plug-ins with Delay	30.00-60.00
Marconi	
TF2203. DC-15MHz. Single Trace. Battery/Mains	40.00-80.00
Tequipment	
D. 43. DC-25MHz. Main Frames with Time Base	60.00-70.00
A. DC-15MHz. Single Trace Amplifier plug-ins	10.00-20.00
J. DC-25MHz. Single Trace Amplifier plug-ins	20.00-30.00
D53S with 2 X 'A' amps. Storage. Dual Trace	290.00-310.00
POWER SUPPLIES	
Roband	
EGO 12/10. 0-12V. Pre-set	23.00-30.00
RECORDERS	
Bell & Howell	
5-124 Ultra Violet Light Beam. 18 Channels (Galvos to 13kHz available at extra charge)	60.00-66.00
5-127. As above with 12 channels	180.00-198.00
SIGNAL SOURCES	
Advance	
SG70. Audio Oscillator. 600 Ohms. 4 Watts	100.00-180.00

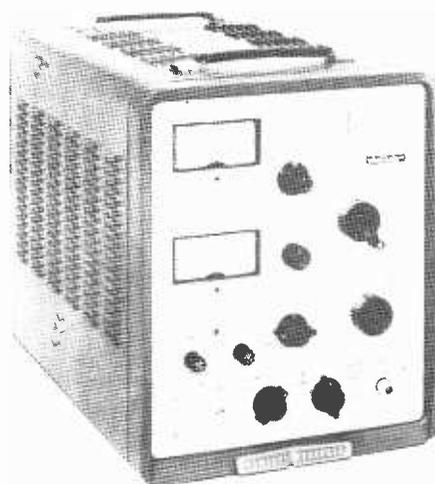

REMEMBER—these prices are unaffected by inflationary pressures. JUST COMPARE the 1974/75 replacement values.




Carston Electronics Limited

Shirley House, 27 Camden Road, London NW1.
Tel: 01-267 4257

£ Sale Price Range

General Radio		
1362. UHF Oscillator } both need a	{	80.00-88.00
1363. UHF Oscillator } power supply		
Hewlett Packard		
612A. 0.45-1.23GHz. Internal or External Amplitude Modulation		300.00-320.00
Marconi		
TF144H/4. 10kHz-72MHz. Xtal check Int/Ext. AM. 50 Ohms		290.00-320.00
TF801 D/1. 10MHz-470MHz. Int/Ext. AM and Pulse Modulation		320.00-350.00
TF2005. 20Hz-20kHz. Twin Oscillators		220.00-290.00
Radiometer		
HO 32C. 21kHz. Beat Frequency Oscillator		90.00-110.00
Wayne Kerr		
O.22D. 10kHz-10MHz. Video Oscillator		160.00-178.00
SPECTRUM ANALYSERS		
Hewlett Packard		
8551B/851B. 10MHz-12GHz.		2,400.00
SWEEP GENERATORS		
Hewlett Packard		

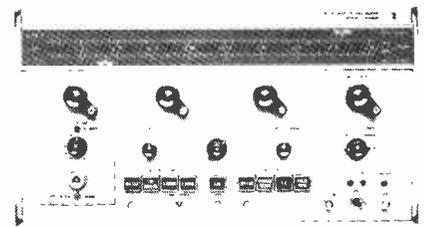


8690 Main Frames	260.00-300.00
8693B. 3.7-8.3GHz plug-ins (Other plug-ins on application)	300.00-450.00
TELEPHONE TV AND MICROWAVE	
Hewlett Packard	
423A. 12.4GHz Crystal Detectors	28.00-32.00
3701/02/03. Microwave Link Analyser	2,520.00-2,700.00
Marconi	
OA 2090A. White Noise Test Set (Filters also available at extra charge)	712.00-820.00
TF2909 TV Test Set. Grey Scale 625 lines	Price to be advised
Richmond Hill	
TSP. TV Studio Precision Signal Generator. Sin 2 P & B, Window. Staircase. (Requires all drives)	580.00-595.00
Siemens	
REL3K53. Contact Fault Locators. 1MHz Test Signal. Variable levels. High sensitivity	130.00-140.00
STC	
74166. Milliwatt Test Sets	41.00-49.00
74184B. Selective Measuring Sets	132.00-144.00
74216. Noise Generator. 20Hz-4kHz	230.00-260.00
74306B. Oscillators 10kHz-20MHz	110.00-135.00
74600. RF Attenuators. 10 steps each unit total Att: 0.9; 9.0; 90.0db.	15.00-25.00
74832B. Selective Level Measuring Set	80.00-100.00
Field Telephone (Hand Generators)	5.00-7.00
Wandel & Goltermann	
TFPS75. 1.3MHz. Selective Oscillators	140.00-160.00
TFPM43. 14MHz. Selective Meters	225.00-240.00
VXM1 Differential Phase Meters (TV)	318.00-330.00
VZMG1 Sampling Attachments	77.00-88.00
WAVE ANALYSERS	
Airmec/Racal	
248A. 5-300MHz. Harmonic Analysers	132.00-144.00
ASSOCIATED EQUIPMENT	
Hewlett Packard	
412A DC. Electronic Multimeter	On Application
Marconi	
TF893 Audio Power Meter 20µW-10W	90.00-98.00
TF2606 Differential Voltmeter. 0-1000V	120.00-140.00
Radiometer	
RV24. DC Electronic Multimeter	60.00-78.00
Siemens	
Multizet. RF Voltmeter. 0-100V. *Uncalibrated	5.00*7.00

Henry's

LARGEST SELECTION OF ELECTRONIC COMPONENTS AND EQUIPMENT. LOW PRICES MEAN LESS VAT.

VAT 8% EXTRA ON ALL ITEMS

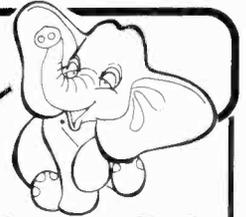

You can build the Texan and Stereo FM Tuner

TEXAN 20 + 20 WATT IC STEREO AMPLIFIER

Features fibre glass PC board. Gardeners low field transformer. 6-ICs. 10 transistors plus diodes etc. Designed by Texas Instruments engineers for Henry's and P.W. 1972. Supplied with full chassis work, detailed construction handbook and all necessary parts. Full input and control facilities. Stabilised supply, overall size 15 1/2 in. X 2 3/4 in. X 6 5/8 in. mains operated. Free teak sleeve with every kit. **£31.00** (Carr. 50p). Built and tested **£37.50**



HENELEC STEREO FM TUNER



Features capacity diode tuning, led and tuning meter indicators, stabilized power supply—mains operated. High performance and sensitivity with unique station indication IC stereo decoder. Overall size in teak sleeve 8 in. X 2 3/4 in. X 6 5/8 in. Complete kit with teak sleeve **£21.00** (Carriage 50p). Built and tested **£24.95**

JOIN THE LARGE BAND OF HAPPY CONSTRUCTORS!

TRANSISTORISED MODULES

Tuners - Power Suppliers - Amplifiers



Amplifiers (All single channel unless stated)

4-300	9 volt	300 MW	£1.75
2004	9 volt	250 MW	£2.70
104	9 volt	1 watt	£3.10
304	9 volt	3 watt	£3.95
555	12 volt	3 watt	£4.10
555ST	12 volt	1 1/2 watt	£3.95
E1208	12 volt	5 watt	£5.10
608	24 volt	10 watt	£4.95
410	28 volt	10 watt	£4.95
620	45 volt	30 watt	£9.95
240	30/35 volt	5 watt	£5.45
Z60	45/50 volt	25 watt	£6.95
SA6817	24 volt	6+6 watt	£10.20

Amplifiers with controls

E1210	12 volt	2 1/2+2 1/2 watts	8 ohms	£8.25
RE500	Mains	5 watts	4-16 ohms	£6.30
SAC14	Mains	7+7 watts	8 ohms	£11.75
SAC30	Mains	15+15 watts	8 ohms	£14.95
CA038	9 volt	1 1/2+1 1/2 watts	8 ohms	£6.95
CA068	12 volt	3+3 watts	8 ohms	£10.90

AM/FM Modules

Mullard LP 1186 FM tuner (front end) with data 10.7MHz o/p	£4.85
LP1157 AM/Module	£2.50
LP1171 AM/FM Module	£4.50
LP1179 AM/FM Front End	£4.85
Mullard LP 1185 10.7MHz IF unit	£4.50
Gorler Permeability FM tuner (front end) 10.7MHz o/p	£4.20

FM and AM tuners and decoders

FM 5231 (tu 2) 6 volt FM tuner	£7.95
TU3 12 volt version (FM use with decoder)	£7.95
SD4912 Stereo Decoder for Tu 3 12 volt	£7.95
SP62H 6 volt stereo FM tuner	£14.95
A1007 9 volt MW-AM tuner	£4.80
Sinclair 12/45 volt FM tuner stereo decoder for above	£7.45
A1019 9 volt FM tuner in cabinet	£13.95
A1005M (SI) 9-12 volt stereo decoder FM for above	£7.50
1062 12 volt stereo decoder. General purpose	£6.50

Preamplifiers

Sinclair Stereo 60 Preamplifier	£6.75
E1300 CART/TAPE/MIC INPUTS 9 volt	£2.95
E1310 Stereo 3-30mV mat cart 9 volt	£4.75
FF3 Stereo 3mV tape head 9 volt	£4.95
3402 Stereo 5-20mV Mag. cart, mains	£5.95
EQ25 Mono 3-250mV Input (Tape/cart/flat 9 volt)	£1.95

Power Supplies—Mains input (*chassis-rest cased)

470C 6.7/9V 300mA	*P1081 45 volt 0.9A	£7.80
with adapters	P12 41-12 volt	£2.25
P500 9 volt 500mA	0.4-1 amp	£7.15
HC244R 3/6.7/9 volt	SE101A 3/6/8/12 volt	£7.50
400mA stabilised	1 amp stabilised	£12.75
*P11 24 volt 1/2 amp	P1076 3/4/6/7/9/12	£3.30
*P15 28 volt 1/2 amp	1 amp 1/2	£4.20
*P1080 12 volt 1A	SE800A 1-15 volt	£4.70
	0-1/2A stabilised	£17.50

NOW OPEN SUPERMARKET

Come and browse round the new components supermarket at 404 Edgware Road. Bargains Galore. Goodie Bags. Components, etc.

SINCLAIR MODULES AND KITS



STR0 stereo pre amplifier	£11.95
Audio filter unit	£8.95
Z40 15 watt amplifier	£5.45
Z60 25 watt amplifier	£8.95
P25 power supplies for 1 or 2Z40	£4.98
P26 power supplies (STA3) for 1 or 2Z40	£7.98
P28 power supplies (STA3) for 1 or 2Z60	£7.98
Transformer for P28 FM tuner	£11.95
Stereo decoder	£7.95
IC20 power amp kit	£7.95
PZ20 power supply for 1 or 2 IC20	£5.45

Sinclair Project 80

Package Deals (Carriage/packing 35p)	
2XZ40, S780, P25	£25.00
2XZ60, S780, P26	£27.75
2XZ60, S780, P28	£34.40
+ Trans	£34.40
Sinclair Special Purchases	
* Project 80 stereo preamplifier	£6.75 post 20p
* Project 605	£19.95 post 25p
* Cambridge calculator	£13.50 post 15p

EMI SPEAKERS Special Purchase

13 x 8 chassis speakers (carr/packing 30p ea or 50p pr) *150 TC 10 watt 8 ohm twin cone **£2.20**



*450 10 watt 4, 8, 15 ohm with twin tweeters and crossover **£3.85** each
EW 15 watt 8 ohm with tweeter **£5.25**
350 20 watt 8, 15 ohm with tweeter **£7.80** each
*Polished wood cabinet **£4.80** carr., etc. 35p each or 50p pair

EXCLUSIVE 5 WATT IC AMPLIFIERS



Special purchase 5 watt output 8-16 ohm load. 30 watt max DC operation complete with data. Price **£1.50** ea. or 2 for **£2.85**. Printed Circuit Samples 50p.

UHF TV TUNERS

625-line receiver UHF transistorised tuners. UK operation. Brand new. (Post/packing 25p each)
TYPE C variable tuning **£2.50**
TYPE B 4-button push-button (adjustable) **£3.50**

PA-DISCO-LIGHTING EQUIPMENT



Without doubt UK's best range of modular and complete equipment. Lighting, mixing, microphones, accessories, speakers, amplifiers, lenses, etc. etc. FREE stock lists (Ref. No. 18) on request CALL IN AND SEE FOR YOURSELF AT HENRY'S DISCO CENTRE, 309 EDGWARE ROAD. 01-723 6963.

CALCULATORS

Sinclair Cambridge Kit	£13.50
Sinclair Cambridge Kit (built)	£17.50
Sinclair memory	£22.50
Sinclair scientific	£26.95
Sinclair scientific kit	£18.50

L450 RECHARGEABLE BATTERY

2v 400mA/HR 50p p.p. 15p.

PHILIPS 12V FLUORESCENT INVERTOR

for 8w fluorescent tube. Supplied with instr. and tube **£3.50** p.p. 30p.

TEST EQUIPMENT MULTIMETERS

(carr/packing 35p)

U4324 20KOV with case **£9.25**

U435 20KOV with steel case **£8.75**

U4313 20KOV with steel case **£12.50**

U4317 20KOV with case **£16.50**

U4341 33KOV plus transistor tester steel case **£10.50**

U4323 20KOV plus 1KHz 465KHz OSC with case **£7.70**

ITI-2 20KOV slim type **£5.95**

THL33D (L33DX) 2KOV robust **£7.50**

TP55N 20KOV (Case £2.00) **£8.25**

TP510S 2KOV **£6.25**

TW20S 20KOV **£10.00**

TW50K 50KOV **£11.25**

EP10KN 10KOV **£9.95**

AF105 50KOV De-luxe (Case £1.90) **£12.50**

S100TR 100KOV plus transistor tester **£22.50**

80R Revolutionary Supermeter **£18.50**

NEUR Multimeter **£19.75**

† T40 AC multivoltmeter **£19.95**

† T615 Grid dip meter **£19.95**

† T655 28-amp valve voltmeter **£22.50**

† T2000 RF generator **£18.95**

120KHz-500MHz **£18.95**

† T4220 AF generator 20Hz-200KHz **£19.95**

† T4220 AF generator 20Hz-200KHz **£19.95**

* HM350 In circuit transistor tester **£18.50**

† C125 De-luxe meter 1-300 MHz **£18.95**

† T145 Compact transistor tester **£14.75**

† G3-B/R osc. 20Hz-200KHz **£19.75**

† C3042 SWR Meter **£5.75**

* SE350A De-luxe signal tracer **£12.95**

* SE400 Mini-IB all in one tracer **£15.90**

† S-Scope 500.000Hz (lean £1.00) **£43.00**

* C3043 5 CH F/A meter 1-300MHz **£5.75**

† Resistance sub box + Post etc. **£2.40**

Capacitor 1 20p **£2.10**

2 amp variable transformers (carr £1) **£6.95**

Radio activity counter 0-10i (carr £1) **£9.97**

Mains unit for above (carr 50p) **£3.75**

TAPE HEADS

Mariot XRPS/17 1/2-track high **£2.50**

Mariot XRPS/18 1/2-track med **£3.50**

Mariot XRPS/36 1/2-track med **£5.00**

Mariot XRPS/63 1/2-track high **£1.75**

Mariot 1/2-tr. Erase 1.3 X 12E 343 **£0.75**

Mariot erase heads for XRPS 17/18/36 (XESI) **£0.75**

R/RP record/play 1/2-track **£0.45**

H/RP single-track rec/play **£0.35**

Bogen type UL290 erase **£1.50**

Miniature stereo cassette rec/play **£2.25**

pp 15p

STC & ITT MINIATURE RELAYS

150R 6/12v 2 p.c.o.	BRAND NEW
185R 12v 2 p.c.o.	NEW
1250R 12/55 2 p.c.o.	60p
1700R 12/24v 2 p.c.o.	pp
1800R 24v 4 p.c.o.	15p
2500R 18/24v 2 p.c.o.	
4000R 24v 2 p.c.o.	

10.7 MHZ MINIATURE CERAMIC

IF FILTER 40p per pair p.p. 15p
EP2 Low Cost Seven Segment Led. Digit Height 1/2 inch **£1.35** p.p. 15p.

SL414

Plessey 5w Power Amp IC **£1.65** p.p. 15p

40KHZ ULTRA SONIC TRANSDUCERS

£5.90 p.p. 25p
TAA 960 40KHz AMP IC **£1.75** p.p. 15p

EXTRA DISCOUNTS

Semi-conductors. Any one type or mixed SN 74 Series 'IC' 12 + EXTRA 10% 25 + EXTRA 15% 100 + EXTRA 20%


INTEGRATED CIRCUITS '74' SERIES

IC	£ p	IC	£ p
SN7400N	0.16	SN7492N	0.70
SN7401N	0.16	SN7493N	0.70
SN7402N	0.16	SN7494N	0.80
SN7403N	0.16	SN7495N	0.80
SN7404N	0.26	SN7496N	0.95
SN7405N	0.22	SN7497N	3.87
SN7406N	0.42	SN74100N	1.87
SN7407N	0.42	SN74104N	0.58
SN7408N	0.28	SN74105N	0.53
SN7409N	0.22	SN74107N	0.45
SN7410N	0.18	SN74110N	0.58
SN7411N	0.25	SN74111N	0.86
SN7412N	0.30	SN74116N	1.89
SN7413N	0.32	SN74118N	0.80
SN7414N	0.32	SN74120N	0.88
SN7416N	0.36	SN74120N	0.95
SN7417N	0.36	SN74121N	1.00
SN7419N	0.15	SN74122N	0.70
SN7421N	0.33	SN74123N	0.70
SN7422N	0.25	SN74125N	0.65
SN7423N	0.37	SN74132N	0.72
SN7425N	0.37	SN74142N	0.90
SN7426N	0.42	SN74149N	0.88
SN7427N	0.37	SN74150N	1.75
SN7428N	0.40	SN74151N	1.00
SN7430N	0.19	SN74153N	0.95
SN7432N	0.33	SN74154N	1.00
SN7433N	0.37	SN74155N	1.00
SN7437N	0.37	SN74156N	1.00
SN7438N	0.37	SN74157N	0.95
SN7439N	0.37	SN74157N	0.95
SN7441AN	0.92	SN74161N	1.38
SN7442N	0.79	SN74162N	1.38
SN7443N	1.27	SN74163N	1.38
SN7444N	1.27	SN74164N	1.76
SN7445N	1.60	SN74165N	1.76
SN7446N	1.89	SN74166N	1.60
SN7447AN	1.80	SN74167N	3.00
SN7448N	1.15	SN74170N	1.22
SN7450N	0.16	SN74173N	1.66
SN7451N	0.16	SN74174N	1.57
SN7453N	0.18	SN74175N	1.10
SN7454N	0.18	SN74176N	1.20
SN7460N	0.16	SN74177N	1.26
SN7470N	0.36	SN74180N	1.26
SN7472N	0.38	SN74181N	3.95
SN7473N	0.38	SN74182N	2.66
SN7474N	0.42	SN74184N	1.80
SN7475N	0.59	SN74185N	1.80
SN7476N	0.45	SN74190N	2.00
SN7477N	0.45	SN74191N	2.00
SN7481N	1.10	SN74192N	2.00
SN7482N	0.87	SN74193N	2.00
SN7483N	1.10	SN74194N	1.30
SN7484N	0.87	SN74195N	1.10
SN7485N	1.83	SN74196N	1.10
SN7486N	0.47	SN74197N	1.20
SN7489N			



92 Warwick Road, Ealing, London W5 5PT
Telephone: 01-567 0424

HE 100 100 WATT POWER AMP MODULE

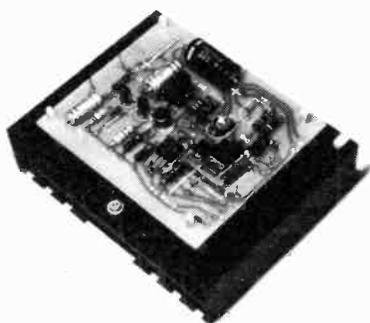

- ★ Includes large black anodised heatsink—no further heat-sinks required.
- ★ Top grade glass-fibre P.C.B.
- ★ Uses high quality components.
- ★ Fully protected—short/open circuit proof.
- ★ Only 5 external connections.
- ★ Fully guaranteed.

TECHNICAL SPECIFICATIONS

- ★ Power output : 106W. R.M.S. into 8Ω
- ★ Distortion : 0.8% at full O/P. Typ. 0.4%
- ★ Frequency response : 15 Hz–23 kHz
- ★ Signal to noise : Better than –96dB
- ★ Input sensitivity : 0dB (0.775V)
- ★ Input impedance : 10kΩ
- ★ Supply volts : 45–0–45V


Price **£15.98** inc. VAT. (ready built)

Power supply for HE100 (including transformer, capacitors, rectifier) **£9.40** inc. VAT. Postage & packing 85p.

Pre-amps etc., also available.
SAE for details.

CALLERS WELCOME

WW—132 FOR FURTHER DETAILS

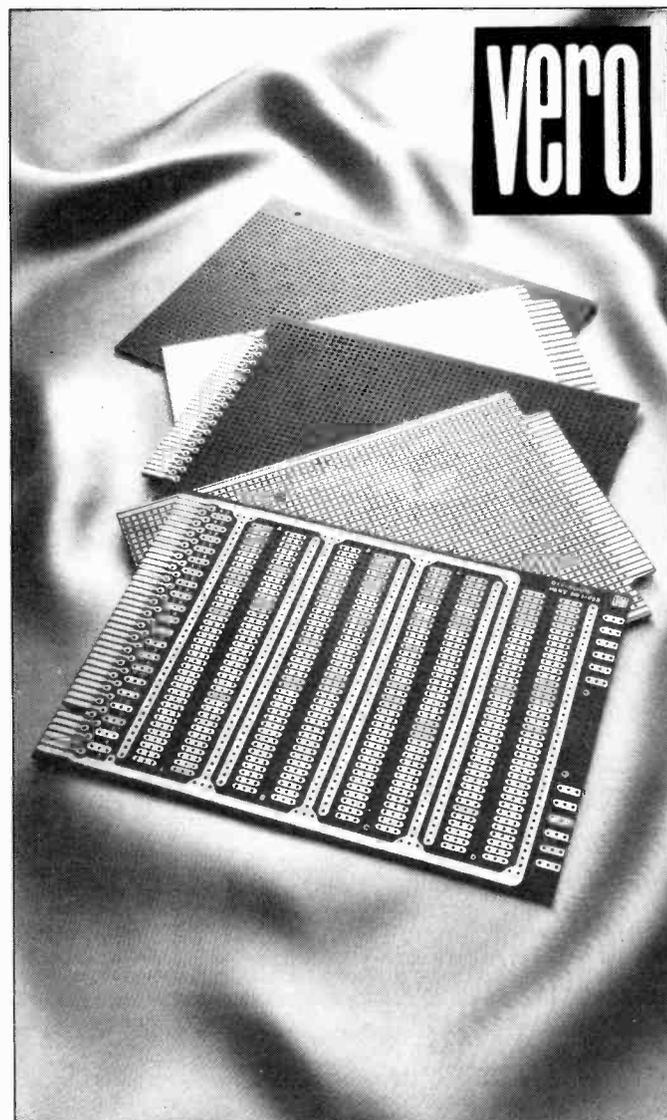

Universal Wiring Boards and Accessories

Plain Board – for use with pins and hard wiring.

D.I.Y. – etch your own circuit but use our contacts.

Finger Board – a plain board with gold plated contacts.

Veroboard – over 100 types for all development and short run production work.

D.I.P. boards – to mount I.C.'s, plug in and breadboard style available.

Vero Electronics Limited,
Industrial Estate, Chandler's Ford,
Eastleigh, Hants SO5 3ZR
Tel: Chandler's Ford 2952. Telex: 47551

World Leaders in Packaging Technology

WW—149 FOR FURTHER DETAILS

Marshall's

A. Marshall & Son (London) Limited Dept. W W
42 Cricklewood Broadway London NW2 3HD Tel: 01-452 0161
& 85 West Regent Street Glasgow G2 2QD Tel: 041-332 4133

Everything you need is in our new 1975 catalogue. Available now price 25p

Trade and export-enquiries welcome

PW TELETENNIS KIT

As featured on BBC Nationwide and in the Daily Mail, October 2, 1974. This exciting new game is now available in kit form. Due to popular demand we are now able to offer a fantastic saving on list prices. Ideal game for whole family. No need to modify your TV set, just plugs into aerial socket. Parts list as follows:

A. Resistor Pack **£1.00** p&p 20p **B.** Potentiometer Pack **£1.25** p&p 20p **C.** Capacitor Pack **£3.10** p&p 20p **D.** Semiconductor Pack **£14.50** p&p 20p **E.** IC Sockets **£4.00** p&p 20p **F.** Transformer **£1.15** p&p 25p **G.** PCBs **£7.50** p&p 20p **H.** Switches **£4.50** p&p 20p **I.** UHF Modular Kit **£7.20** p&p 20p. Special prices—Complete kit (excluding case) **£42.00** p&p 50p. Sections **A-F** incl. **£23.50** p&p 30p. Assembly instructions with complete kit or 75p on request.

SN7400 16p	SN7420 16p	SN7453 16p	SN7491 £1.10
SN7401 16p	SN7423 37p	SN7454 16p	SN7492 75p
SN7401AN 38p	SN7425 37p	SN7460 16p	SN7493 65p
SN7402 16p	SN7427 45p	SN7470 30p	SN7494 85p
SN7403 16p	SN7430 16p	SN7472 38p	SN7495 80p
SN7404 24p	SN7432 45p	SN7473 44p	SN7496 £1.00
SN7405 24p	SN7437 35p	SN7474 48p	SN74100 £2.16
SN7406 45p	SN7438 35p	SN7475 59p	SN74107 43p
SN7407 45p	SN7440 16p	SN7476 45p	SN74118 £1.00
SN7408 25p	SN7441 85p	SN7480 75p	SN74119 £1.92
SN7409 33p	SN7442 85p	SN7481 £1.25	SN74121 57p
SN7410 16p	SN7445 £1.59	SN7482 87p	SN74122 80p
SN7411 25p	SN7446 £2.00	SN7483 £1.20	SN74123 72p
SN7412 28p	SN7447 £1.30	SN7484 95p	SN74141 £1.00
SN7413 50p	SN7448 £1.50	SN7485 £1.58	SN74150 £1.44
SN7416 45p	SN7450 16p	SN7486 45p	SN74190 £1.95
SN7417 30p	SN7451 16p	SN7490 65p	

CMOS

CD4000 51p	CD4011 51p	CD4023 51p	CD4041 £2.11
CD4001 1p	CD4015 £2.66	CD4024 £1.90	CD4044 £2.11
CD4002 51p	CD4016 £1.02	CD4027 £1.56	CD4047 £1.65
CD4009 £1.07	CD4017 £2.66	CD4028 £2.34	CD4049 90p
CD4010 £1.07	CD4020 £2.96	CD4029 £3.74	CD4050 90p

Veroboard

2.5 x 3 1/2 in	Copper 0.1	0.15	Plain 0.1	0.15
2.5 x 5 in	36p	26p	—	17p
3 1/2 x 3 1/2 in	40p	40p	—	19p
3 1/2 x 5 in	45p	40p	—	—
3 1/2 x 17 in	45p	47p	—	32p
	£1.61	£1.26	£1.00	92p

TRY OUR GLASGOW SHOP

Popular Semi-conductors

2N696 22p	2N3707 13p	AD142 59p	BC309 10p	LM709 48p
2N697 16p	2N3708 70p	AD143 45p	BC327 21p	TO 99 38p
2N698 40p	2N3715 £1.50	AD161 45p	BC328 19p	BD1 40p
2N699 45p	2N3716 £1.80	AD162 45p	BC370 17p	14D1L 40p
2N1302 19p	2N3771 £2.20	AD161 pr	BCV71 22p	LM723C 90p
2N1303 19p	2N3772 £1.80	AD162 £1.05	BCY72 13p	LM741 40p
2N1304 24p	2N3773 £2.65	AF109R £1.05	BD123 32p	TO 99 40p
2N1305 24p	2N3819 37p	AF115 24p	BD131 40p	8D1L 40p
2N1306 31p	2N3820 38p	AF124 30p	BD132 50p	14D1L 38p
2N1307 22p	2N3823 £1.42	AF125 30p	BD135 42p	LM747 £1.00
2N1308 25p	2N3904 27p	AF126 28p	BD136 49p	LM7805 £2.00
2N1309 36p	2N3905 24p	AF127 28p	BD137 55p	MC1310 £2.92
2N1671 £1.44	2N4036 63p	AF139 39p	BD138 63p	MJ480 90p
2N1671A £1.54	2N4037 42p	AF178 55p	BD139 71p	MJ481 £1.14
2N1671B £1.72	2N4126 20p	AF179 65p	BD140 87p	MJ490 98p
2N1671C £4.32	2N4289 34p	AF180 58p	BD115 25p	MJ491 £1.38
2N2102 50p	2N4921 73p	AF239 51p	BF116 23p	MJE340 45p
2N2147 78p	2N4922 84p	AF240 72p	BF117 43p	MJE2955 £1.12
2N2148 94p	2N4923 83p	AF279 54p	BF154 16p	MJE3055 68p
2N2160 60p	2N5190 92p	AF280 54p	BF163 32p	MFC4000B 40p
2N2218A 22p	2N5191 95p	BC107 16p	BF180 35p	MFC4010A 49p
2N2219 24p	2N5192 £1.24	BC108 15p	BF181 34p	MFC4060 54p
2N2219A 26p	2N5195 £1.46	BC109 19p	BF184 30p	MFC6040 91p
2N2221 18p	2N5245 43p	BC147 12p	BF194 12p	NE55V 70p
2N2221A 21p	2N5457 49p	BC148 13p	BF195 12p	NE58D £4.48
2N2222 20p	2N5458 45p	BC149 12p	BF196 13p	NE531 £4.48
2N2222A 25p	2N5459 49p	BC167B 13p	BF197 15p	NE565A £4.48
2N2646 55p	40361 48p	BC168B 13p	BF198 18p	OC28 76p
2N2904 22p	40362 50p	BC168C 11p	BF200 40p	OC42 50p
2N2904A 24p	40363 88p	BC169B 13p	BF237 22p	OC71 17p
2N2905 24p	40406 44p	BC169C 13p	BF238 22p	OC72 25p
2N2905A 26p	40407 33p	BC182 12p	BFX29 30p	SL147A £1.80
2N2906 19p	40408 50p	BC182L 12p	BFX30 27p	TAA263 £1.00
2N2906A 21p	40409 52p	BC183 12p	BFX84 24p	TBA800 £1.50
2N2907 22p	40410 52p	BC183L 12p	BFX85 30p	TBA810 £1.50
2N2907A 25p	40411 £2.25	BC184 13p	BFX87 28p	TIP29A 49p
2N2926 11p	40602 46p	BC184L 13p	BFX88 25p	TIP30A 58p
2N3053 25p	40604 56p	BC212K 16p	BFX89 45p	TIP31A 62p
2N3054 60p	40669 £1.00	BC212L 16p	BFY19 62p	TIP328 74p
2N3055 75p	AC117 20p	BC214L 21p	BFY51 23p	TIP33A £1.01
2N3441 97p	AC126 20p	BC237 13p	BFY52 21p	TIP34A £1.51
2N3442 £1.61	AC127 20p	BC238 13p	BFY90 75p	TIP35A £2.90
2N3415 10p	AC128 20p	BC239 13p	BRY39 48p	TIP36A £3.70
2N3416 15p	AC151V 25p	BC257 14p	C1060 65p	TIP41A 79p
2N3417 21p	AC152V 17p	BC258 13p	CA3020A £1.80	TIP42A 90p
2N3702 11p	AC176 18p	BC300 36p	CA3046 70p	TIP295 93p
2N3703 12p	AC176 18p	BC300 36p	CA3048 £2.11	TIP3055 60p
2N3704 14p	AC176K 25p	BC301 34p	CA3089E £1.96	ZTX300 13p
2N3705 12p	AC187K 23p	BC307 11p	CA3090 £4.23	ZTX302 20p
2N3706 9p	AC188K 34p	BC308 12p	LM301A 46p	ZTX500 15p

Prices correct at October 1974, but all exclusive of V.A.T. Post and Package 20p

TRANSFORMERS

SAFETY MAINS ISOLATING TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	£	P & P
07	20	1 8	7.0x 7.0x 6.0	2.55	38
149	80	3 12	9.9x 7.7x 8.6	3.98	38
150	100	5 8	9.9x 8.9x 8.6	4.45	45
151	200	8 0	12.1x 9.3x 10.2	7.30	53
152	250	13 12	12.1x 11.8x 10.2	8.93	73
153	350	15 0	14.0x 10.8x 11.8	10.80	73
154	500	19 8	14.0x 13.4x 11.8	12.41	91
155	750	29 0	17.2x 14.0x 14.0	18.85	91
156	1000	38 0	17.2x 16.8x 14.0	26.50	91
157	1500	46 0	21.6x 13.4x 18.1	30.25	91
158	2000	60 0	21.6x 15.3x 18.1	33.70	91
159	3000	85 0	23.5x 17.8x 19.7	53.25	91



AUTO TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	£	P & P
113	20	1 0	5.8x 5.1x 4.5	0-115-210-240	1.52	30
64	75	2 4	7.0x 6.7x 6.1	0-115-210-240	2.64	38
4	150	3 4	8.9x 7.7x 7.7	0-115-200-220-240	3.75	45
66	300	6 4	9.9x 9.5x 8.6	0-115-200-220-240	5.20	53
67	500	12 3	12.1x 11.2x 10.2	0-115-200-220-240	8.02	67
84	1000	19 3	14.0x 13.4x 14.3	0-115-200-220-240	12.44	91
93	1500	30 4	14.0x 15.9x 14.3	0-115-200-220-240	18.65	91
95	2000	32 0	17.2x 16.8x 14.0	0-115-200-220-240	22.90	91
73	3000	40 0	21.6x 15.3x 18.1	0-115-200-220-240	31.90	91

CASEO AUTO TRANSFORMERS

115V mains lead input and U.S.A. 2 pin outlets. 20VA £2.85. P. & P. 38p. 500VA £9.50. P. & P. 80p. 1000VA £15.92. Via B.R.S.

LOW VOLTAGE TRANSFORMERS

Ref. No.	Amperes	Weight lb oz	Size cm.	Secondary Windings	£	P & P
111	0-0.25	1 4	4.8x 2.9x 3.5	0-12V at 0.25A x 2	1.34	23
213	1-0 0.5	1 4	6.1x 5.8x 4.8	0-12V at 0.5A x 2	1.58	30
71	2 1	1 12	7.0x 6.4x 6.1	0-12V at 1A x 2	2.09	38
18	4 2	2 12	8.3x 7.7x 7.0	0-12V at 2A x 2	2.60	38
70	6 3	3 8	8.9x 8.0x 7.7	0-12V at 3A x 2	3.75	45
108	8 4	5 8	9.9x 8.9x 8.6	0-12V at 4A x 2	4.15	45
72	12 6	6 12	9.9x 10.2x 8.6	0-12V at 5A x 2	4.67	53
116	16 8	8 12	12.1x 9.9x 10.2	0-12V at 8A x 2	6.62	60
115	20 10	18 8	14.0x 9.6x 11.8	0-12V at 10A x 2	9.45	73
187	30 15	15 8	14.0x 12.1x 11.8	0-12V at 15A x 2	12.29	85
226	60 30	32 8	17.2x 15.3x 14.0	0-12V at 30A x 2	15.30	91

36 VOLT RANGE


Ref. No.	Amperes	Weight lb oz	Size cm.	Secondary Taps	£	P & P
112	0-5	1 4	6.1x 5.8x 4.8	0-12-15-20-24-30V	1.65	30
79	1-0	2 4	7.0x 6.7x 6.1	0-12-15-20-24-30V	2.18	38
3	2-0	3 4	8.9x 7.7x 7.7	0-12-15-20-24-30V	3.18	38
20	3-0	4 5	9.9x 8.3x 8.6	0-12-15-20-24-30V	4.12	45
21	4-0	5 8	9.9x 9.5x 8.6	0-12-15-20-24-30V	4.67	53
51	5-0	6 12	12.1x 8.6x 10.2	0-12-15-20-24-30V	5.83	53
117	6-0	8 0	12.1x 9.3x 10.2	0-12-15-20-24-30V	6.51	60
88	8-0	12 0	12.1x 11.8x 10.2	0-12-15-20-24-30V	9.00	67
89	10-0	13 12	14.0x 10.2x 11.8	0-12-15-20-24-30V	8.97	73

50 VOLT RANGE

Ref. No.	Amperes	Weight lb oz	Size cm.	Secondary Taps	£	P & P
102	0-5	1 12	7.0x 6.4x 6.1	0-19-25-33-40-50V	2.35	30
103	1-0	2 12	8.3x 7.4x 7.0	0-19-25-33-40-50V	3.00	38
104	2-0	5 8	9.9x 8.9x 8.6	0-19-25-33-40-50V	4.26	45
105	3-0	6 12	9.9x 10.2x 8.6	0-19-25-33-40-50V	5.28	53
106	4-0	10 0	12.1x 10.5x 10.2	0-19-25-33-40-50V	6.91	67
107						

EX BEA CONTROL UNITS

THESE PROVIDE MESSAGE ASSEMBLY—BUFFER STORAGE-CHARACTER GENERATION AND CONTROL FOR OPERATION OF UP TO 20 PLUS DISPLAY STATIONS AND OR OTHER INPUT OUTPUT DEVICES. THESE CONTROL UNITS ARE SUPPLIED COMPLETE WITH INTERNAL POWER SUPPLIES FOR OPERATION FROM 240V 50HZ SIGNAL PHASE MAINS. THEY ARE NOT TESTED. LIMITED SPARES ARE AVAILABLE WITH EACH UNIT AND ADEQUATE INFORMATION. FURTHER DETAILS AVAILABLE IF REQUIRED

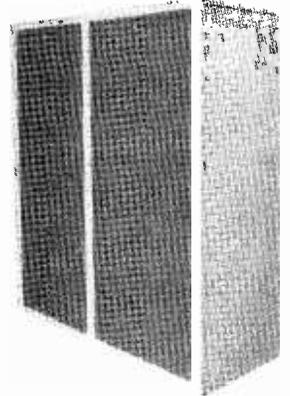

£250 each PLUS CARRIAGE

E.M.I. PROFESSIONAL RECORDERS. BTR2

COMPLETE EXCEPT FOR PLUG-IN HEADS
£35 each. CARRIAGE £2

Breaking some—limited amount of spares. Your enquiries please (be specific in requirements).

CLEARANCE LISTS AVAILABLE. S.A.E.

TELEPHONES

STANDARD 300 Series. BLACK only **£1.00** ea. P. & P. 50p.
MODERN STYLE 706 BLACK OR TWO-TONE GREY **£3.75** ea. P. & P. 35p. **STYLE 7006** TWO-TONE GREEN **£3.75** ea. P. & P. 35p. **HANDSETS**—complete with 2 insets and lead **75p** ea. P. & P. 37p. **DIALS ONLY.** **75p** ea. P. & P. 25p.
SCOOP FIRST TIME MODERN STANDARD TELEPHONES IN GREY OR GREEN WITH A PLACE TO PUT YOUR FINGERS LIKE THE 746. **A CHANCE NOT TO BE MISSED £3.00** ea. P. & P. 35p.

CAPACITOR PACK 50 Brand new components only **50p** P. & P. 17p.

P.C. MOUNT SKELETON PRE-SETS. Screwdriver adjust 10, 5 and 2.5M @ **2p** ea. 1M, 500, 250 and 25K @ **4p** ea. Finger adjust 10, 5 and 2.5M @ **3p** ea. 1M, 500, 250 and 25K @ **5p** ea. Min P. & P. 10p.

1000pf FEED THRU CAPACITORS. Only sold in packs of 10—**30p** P. & P. 10p.

RECTANGULAR INSTRUMENT FANS. American Ex-eq. Size $4\frac{1}{2} \times 4\frac{1}{2} \times 1\frac{1}{2}$ " 115 Volt. Very quiet **£3** ea. P. & P. 37p.

DELIVERED TO YOUR DOOR 1 cwt. of Electronic Scrap chassis boards, etc. No Rubbish. FOR ONLY **£4.** N. Ireland £2 extra.

P.C.B. PACK S & D. Quantity 2 sq. ft.—no tiny pieces. **50p** plus P. & P. 20p.

FIBRE GLASS as above **£1** plus P. & P. 20p.

TRIMMER PACK. 2 Twin 50/200 pf ceramic; 2 Twin 10/60 pf ceramic; 2 min strips with 4 preset 5/20 pf on each; 3 air spaced preset 30/100 pf on ceramic base. ALL BRAND NEW **25p** the LOT. P. & P. 10p.

PHOTOCCELL equivalent OCP 71. **13p** ea.

MULLARD OCP70 **10p** ea.

GRATICULES. 12 cm. by 14 cm. in High Quality plastic. **15p** each. P. & P. 5p.

FIBRE GLASS PRINTED CIRCUIT BOARD. Brand New. Single or Double sided. Any size **1½p** per sq. in. Postage **10p** per order.

CRYSTALS. Colour 4.43MHz. Brand New. **£1.25** ea. P. & P. 10p.

Beehive Trimmer 3/30 pf.

Brand new. Qty 1—9 **13p** ea. P. & P. 15p; 10—99 **10p** ea. P. & P. 25p; 100—999 **7p** ea. P. & P. free.

HF Crystal Drive Unit. 19in. rack mount. Standard 240V input with superb crystal oven by Labgear (no crystals) **£5** ea. Carr. **£1.50.**

ROTARY SWITCH PACK—6 Brand New switches (1 ceramic; 1—4 pole 2 way etc.). **50p** P. & P. 20p.

Vast quantity of good quality components—NO PASSING TRADE—so we offer **3 LB. of ELECTRONIC GOODIES** for **£1.50** post paid.

BOURNS TRIMPOT POTENTIOMETERS. 20; 50; 100; 200; 500 ohms; 1; 2; 2.5; 5; 10; 25K at **35p** ea. ALL BRAND NEW.

RELIANCE P.C.B. mounting. 270; 470; 500 ohms; 10K at **35p** ea. ALL BRAND NEW.

VENNER Hour Meters—5 digit, wall mount—sealed case. Standard mains. **£3.75** ea. P. & P. 45p.

TRANSFORMERS. All standard inputs. Gard/Parrr/Part. 450—400—0—400—450, 180 MA. 2 x 6 3v. **£3** ea.

FANTASTIC VALUE

Miniature Transformer. Standard 240V input. 3Volt 1 amp output. Brand New. **65p** ea. P. & P. 15p. Discount for quantity.

LOW FREQUENCY WOBBLATOR

Primarily intended for the alignment of AM Radios; Communication Receivers; Filters, etc., in the range of 250 KHZ to 5 MHZ, but can be effectively used to 30 MHZ. Can be used with any general purpose oscilloscope. Requires 12V AC input. Three controls—RF level; sweep width and frequency. Price **£8.50.** P. & P. 35p.
A second model is available as above but which allows the range to be extended down in frequency to 20 KHZ by the addition of external capacitors. Price **£11.50.** P. & P. 35p.
Both models are supplied connected for automatic 50 HZ sweeping. An external sweep voltage can be used instead. These units are encapsulated for additional reliability, with the exception of the controls (not cased, not calibrated).

DON'T FORGET YOUR MANUALS S.A.E. WITH REQUIREMENTS

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2 HZ to 8 MHZ. Hook up a 9 volt battery and connect to your scope and have two traces for ONLY **£6.25.** P. & P. 25p.
STILL AVAILABLE our 20 MHZ version at **£9.75.** P. & P. 25p.

20HZ to 200KHZ

SINE AND SQUARE WAVE GENERATOR

In four ranges. Wien bridge oscillator thermistor stabilised. Separate independent sine and square wave amplitude controls. 3V max sine, 6V max square outputs. Completely assembled P.C. Board, ready to use. 9 to 12V supply required. **£8.85** each. P. & P. 25p. Sine Wave only **£6.85** each. P. & P. 25p.

LARGE QUANTITY OF OSCILLOSCOPE & DISPLAY TUBES FROM 1" to 24" S.A.E. FOR COMPREHENSIVE LIST

All of our tubes can be supplied with nu-metal shields or Telcon nu-metal tape.

WIDE RANGE WOBBLATOR

5 MHZ to 150 MHZ (Useful harmonics up to 1.5 GHZ) up to 15 MHZ sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10·7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6·3V AC and use within minutes of receiving. All this for only **£6.75.** P. & P. 25p. (Not cased, not calibrated.)

TRANSISTOR INVERTORS

TYPE A
Input: 12V DC
Output: 1.3kV AC 1.5MA
Price **£3.45**

TYPE B
Input: 12V DC
Output: 1.3kV DC 1.5MA
Price **£4.70**

TYPE C
Input: 12V to 24V DC
Output: 1.5kV to 4kV AC 0.5MA
Price **£6.35**

TYPE D
Input: 12V to 24V DC
Output: 14kV DC 100 micro amps at 24V. Progressively reducing for lower input voltages
Price **£11**

Postage & Packing 36p

Unless stated – please add **£2.00** carriage to all units.

VALUE ADDED TAX not included in prices—please add **8%**

Official Orders Welcomed, Gov./Educational Depts., Authorities, etc., otherwise Cash with Order


Open 9 am to 6.30 pm any day (later by arrangement.)



CHILTMEAD LTD



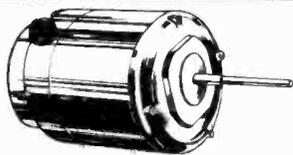7/9 ARTHUR ROAD, READING, BERKS. (rear Tech. College, Kings Road) Tel.: Reading 582605/65916



"SLO-SYN" 3-LEAD SYNCHRONOUS STEPPING MOTOR

Type SS15. These fine motors are easily reversed, starting and stopping in less than 5° without electrical or mechanical braking. Simple relay circuit can be applied to give D.C. to winding for a maximum holding torque of 300oz/in with 35v at 0.3amps through winding. For A.C. (synchronous) operation at 120v, 50Hz. Speed 60 rpm at 60Hz., 72 rpm. STEPPING. Holding torque at 60 steps per second—100 oz/in. Can be wired to give 100 or 200 steps per revolution with accuracy of 0.1° per step non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions: dia. 4", body length 4 1/2", spindle length 2 1/2" x 1/4" dia. Weight 3 1/2 lbs. BRAND NEW in maker's packing. Offered at less than 1/3 maker's price.

£15

OPEN FRAME shaded pole GEARED MOTORS

(Dural gear case) 240 A.C. 25rpm. NEW HIGH TORQUE, approx. overall size: 3 1/2" x 3 1/2" x 2 1/2" + spindle 1/2" dia. as illustrated. £3. P. & P. 30p. Similar to above, 19rpm. £3. P. & P. 30p. 110rpm with pressed steel gear case similar to above but slightly smaller. £3. P. & P. 30p.



CARTER ELECTRIC

Similar to above with alloy gear case, 60 r.p.m. This item is ex-equipment but perfect. £1.95. P & P 30p.



SMITHS RINGER-TIMER

Reliable 15 minute times, spring wound (concurrent with time setting) 15x1min divisions, approximately 1/2 between divisions. Panel mounting with chrome bezel 3 1/2" dia. £1.40. 15p. P. & P.

FEW ONLY

Fully stabilised "Labgear" Power Supply Unit. Input 90-240v, 50Hz. Outputs 6v. 6a D.C. and 6v+2v, 100mA. Hum and ripple at full load—less than 3mV peak to peak. Stability improvement ratio for 15% mains change—1/1000. Output impedance 0.005 ohms. 9 1/2" x 9 1/2" x 1 1/2". Weight 20lb. £26.00. Carr. & Pkg £1.50. In manufacturer's carton.

"LABGEAR ELIMINAC"

P.S.U. 200-250v, 40/60Hz. Alternative outputs fully variable (variac incorporated). Output 1.12v at 5a D.C. fully smoothed. Output 2.12v at 8a D.C. with ripple content. Output 3.20v at 10a A.C. 2 1/2" x 2 1/2" flush 0-20v D.C. m/c meter. In attractive grey hammer finish case. In maker's carton. £27.50. Carr. & Pkg. £1.50.

SHADED POLE MAINS MOTOR

A quality shaded pole motor. Open frame, 3" high x 2 1/2" x 2". Spindle 1" x 3/16". 1.420r.p.m. £1.95 P & P 20p.

SOLENOIDS by WESTOOL

240AC type MM6. 3lb. pull. 2 1/2" x 1 1/2" x 1 1/2". Travel 1" 90p each. F & P. 10p.



240AC type MM4. 2lb. pull. 1 1/2" x 1 1/2" x 1 1/2". Travel 3/4" 70p each. P. & P. 10p. Quantity discounts: 10-50 10%. 50 upwards 25%




MAINS SOLENOID


This little unit gives vertical lift of approximately 1" through hinged "elbow". Bracket incorporates 2 fixing screws. Length of arm 2 1/2". 240V A.C. Pull at coil is approximately 1lb. £1. FREE P. & P. Special quotes for quantities.



AMPEX 7.5v. DC MOTOR

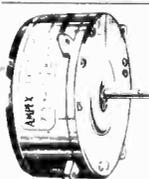

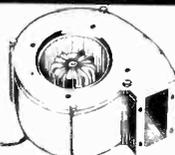An ultra precision tape motor designed for use in the AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 60ma on run. 600rpm ± speed adjustment. Internal AF/RF suppression. 1" dia. x 1 1/2" spindle motor 3" dia. x 1 1/2" Original cost £16.50. OUR PRICE £3.30. P. & P. 25p. Large quantities available (special quotations). Mu-metal enclosure available. 75p each. FREE P. & P.



ULTRA PRECISION CENTRIFUGAL BLOWER

by Air Control Ltd.

30 segments individually balanced in heavy cast alloy case. 2,300 r.p.m. 240v A.C. Very powerful and silent running. 5 1/2" dia. 3" inlet dia. Outlet flange 3" x 2 1/2".

Limited number only £8.95 P & P 40p

SILVANIA MAGNETIC SWITCH


Now complete with reference magnet!

A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 3amp at 120v. 1amp at 240v. Size: (approx.) 1 1/2" long x 1/2" dia. Ideal for burglar alarms, security systems etc., and wherever non-mechanical switching is required. 10 for £2; P & P 15p. 50 for £8.80; 100 for £16.50. FREE P.&P. over 10.

NORPLEX

The famous American fibre-glass copper-clad laminate. Finest quality with woven glass base of Epoxy-resin. Excellent Mech. and Elec. conductive properties. Heat resistant, ideal for P.C.'s etc. THIS IS A SPECIAL PURCHASE AND ONLY AVAILABLE WHILE STOCKS LAST! Sizes: 12" x 12", 24" x 12", 24" x 24", FULL SHEET 48" x 37" (11 sq. ft.) Single-sided Copper with thickness of 1/32", 3/64", 3/32". Also double-sided 1/32", 1/16", 3/32". £1 per sq. ft. Cut sizes (1-10 sq. ft.) 25p. P. & P. Full Sheet £8 each. Carr. £1 for 1st sheet plus 25p each additional sheet.

FAN/BLOWER

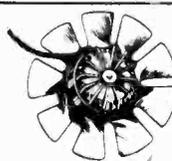

Precision-built in Germany. Dynamically balanced mains unit (200/240) continuous rated, reversible 60MA on run. Size: 5 1/2" dia. x 2 1/2" deep. Back plate is tapped for 4 fixing screws (supplied). Well under maker's price at £3. P. & P. 20p. Similar unit to above but 7 1/2" dia. x 3" deep. £4.50. P. & P. 25p.

ALL PRICES INCLUDE V.A.T.

Whilst we welcome official orders from established companies and Educational Departments, it is no longer practical to invoice goods under £5. Therefore, please remit cash with orders below this amount.

ELECTRO-TECH COMPONENTS LTD.

315/317, EDGWARE ROAD, LONDON, W2. Tel: 01-723 5667 01-402 5580

REDIFON TELEPRINTER RELAY UNIT NO. 12: ZA-41196 and power supply 200-250V a.c. Polarised relay type 3SEITR. 80-0-80V 25mA. Two stabilised valves CV 286. Centre Zero Meter 10-0-10. Size 8in. x 8in. New condition. £8.50. Carr. 75p.

AUTO TRANSFORMER: 230V 50c/s, 1000 watts. Mounted in strong steel case 5in. x 6 1/2in. x 7in. Bitumen impregnated. £10 each. Carr. £1.

TELEPRINTER TYPE 7B: Pageprinter 24V d.c. power supply, speed 50 bauds per min. 'as new' cond. in original packing case, £25 each; or second hand cond. (excellent order) no parts broken. £15 each. Carriage either type £3-00.

INSULATION TEST SET: 0-10 kV negative, earth with amplifier provision for checking ionisation. 110/230V a.c. input. S/hand good cond. £30 + £1 carr.

BRIDGE MEGGER: 250V. (Evershed Vignoles) series 2. £30 each. Carr. £1.

BRIDGE MEGGER: 2,500V., series 1. £30 each. Carr. £1.

CRYSTAL TEST SET TYPE 193: used for checking crystals in freq. range 3000-10,000KHz. Mains 230V 50Hz. Measures crystal current under oscillatory conditions and the equivalent resistance. Crystal freq. can be tested in conjunction with a freq. meter. £17.50. Carr. £1.50.

TYPE 174/1 FREQUENCY SHIFT ADAPTOR (Northern Radio Co.): Convert. mark and space frequencies from the output of one or two Receivers into d.c. pulses. Suitable to operate Teleprinters or similar devices. 110/220V. Further details on request, s.a.e. £55 each. Carr. £1.50.

TELEGRAPH TERMINAL UNIT (A.T.E.) TYPE TFS3: Converts signals from Receivers into d.c. pulses. Complete with monitor. £75 each. Carr. £2.

MUIRHEAD PAMETRADA WAVE ANALYSER D-489-EM: Primarily used for the analysis of complex vibration waveforms but will measure audio and power frequency waveforms from 19Hz-21KHz. Complete with power supply unit 230V 50Hz. Secondhand, good condition. £90. Carr. £3.

FURZHILL SENSITIVE VALVE VOLTMETER V.200: Freq. 10Hz-6MHz (can be used beyond 6MHz) Probe in circuit—voltage range 1mV-1kV in 6 decade ranges; full scale deflection 10mV, 100mV-1kV. Without probe 100µV-100V in 6 decade ranges; full scale deflection 1mV, 10mV-100V. Accuracy ± 5%. £30 each. Carr. £1.

NOISE FIGURE METER TYPE 113A (Magnetic AB, Sweden): £125 each. Carr. £1.

PRECISION PHASE DETECTOR TYPE 205: Freq. 0.1-15MHz in 5 ranges. Variable time delay microseconds 0-0.1c, 115V input. £55 each. Carr. £1.

ROHDE & SCHWARZ HF MILLIVOLTMETER: 30Hz-30MHz Type UVH, 1mV-1V in 7 ranges, 220V. £75 each. Carr. £2.

ROHDE & SCHWARZ VHF WATTMETER TYPE NAK: with matching indicator, 30 watts, 200-470MHz. £25 each. Post 70p.

ADVANCE PULSE GENERATOR PG55: £40 each. Carr. £1.

PHILLIPS VALVE VOLTMETER TYPE GM6014: 1-300mV in 6 ranges, 70-20dB, probe 1000Hz-30MHz, 300mV maximum. £35 each. Carr. £1.

TF-1345/2 DIGITAL FREQUENCY COUNTER: Range 10KHz-100MHz with extension units. Details on request, s.a.e. £100. Carr. £2.

ALL U.K. ORDERS SUBJECT TO 8% VALUE ADDED TAX. THIS MUST BE ADDED TO THE TOTAL PRICE (including post or carriage).

UHF MICROWAVE MILLIWATTMETER TYPE 14: Direct reading, can be used to measure power from 100MHz upwards. F.S.D. on 4in. scale meter 2.5mW. £40 each. Carr. £1.

MARCONI HF SPECTRUM ANALYSER OA. 1094/3. Further details on request. £250 each. Carr. £5.

Q METER: 30MHz-200MHz. £55. Carr. £1.

SIGNAL GENERATOR AIRMEC TYPE 701: 30KHz-30MHz, 7 ranges. £65. Carr. £1.50.

TF-1278/1 TRAVELLING TUBE WAVE AMPLIFIER: £125. Carr. £2.

BPL A.C. MILLIVOLTMETER TYPE VM.348-D Mk. 3: 2 millivolts-2 volts, 6 ranges. £30. Carr. £1.

WAYNE KERR WAVEFORM ANALYSER A.321: Low scale 0-1200 c/s. High scale 1-20 Kc/s, 600 ohms. Harmonic level is 0-55 dB in 12 steps. £75. Carr. £1.50.

SPECTRUM ANALYSER TYPE MW.69S (Decca): Further details on request. £200.

MARCONI DUAL TRACE UNIT TM-6456: £30. Post 60p.

AVO TRANSISTOR TESTER CT.446: £30. Carr. £1.

SIGNAL GENERATOR TS-403B/U (or URM-61A): (Hewlett Packard). A portable, self-contained, general-purpose test equipment designed for use with radio and radar receivers and for other applications requiring small amounts of RF power such as measuring standing-wave ratios, antenna and transmission line characteristics, conversion gain, etc. Both the output freq. and power are indicated on direct-reading dials. 115V, AC, 50 c/s. Freq.—1800-4000 Mc/s. CW, FM, Modulated Pulse—40-4000 pulses per sec. Pulse Width—0.5-10 microseconds. Timing—Undelayed or delayed from 3-300 microseconds from external or internal pulse. Output—1 milliwatt max. 0 to -127 dB variable. Output Impedance—50Ω. Price: £120 each + £2 carr.

H.V. TRANSFORMER: 8000/8000. Output 300mA. rms. Size: 12in. x 12in. x 36in. 230V input. £40. Carr. £4.

TELEPHONE CABLE: (Twin) 1,300ft. on metal reel. £7.50 per reel. Carr. £1

FIRE-PROOF TELEPHONES: £25.00 each, carr. £1 50.

TF.2000 A.F. SIGNAL SOURCE: £175.00, carr. £1.00.

POWER UNIT: 110/230 volts a.c. input. 28 volts d.c. at 40 amps output. £30.00 each, carr. £3-00.

SMOOTHING UNIT (for the above): £10.00 each, carr. £2.00.

X-BAND MODULATOR CALIBRATOR TYPE MC-4420-X: Mnfr. James Scott. £125 ea., Carr. £1.

HP-766D DUAL DIRECTIONAL COUPLER: 940-1975MHz. £35 ea., 75p post.

BACKWARD WAVE OSCILLATOR TYPE SE-215: 6.3 heater, 105V Anode, 79mA. Mnfr. Watkins & Johnson. £85 ea., Carr. £1.

LISTS OF EQUIPMENT AVAILABLE: MOTORS; TELEPRINTERS; AR88 SPARES; TEST EQUIPMENT ETC. Send 10p for above lists.

ALL CARRIAGE QUOTES GIVEN ARE FOR 50 MILE RADIUS OF LONDON ONLY.

If wishing to call at stores, please telephone for appointment.

W. MILLS

3-B TRULOCK ROAD, LONDON, N17 0PG
Phone: 01-808 9213 and Bedford 740605 (STD 0234).

JOHN CRICHTON

Electronic Equipment
558 Kingston Road,
London, SW20

Inland VAT add 8%
Prices shown include P & P, other prices gladly on request.
Carriage extra for overseas orders.
Viewing by appointment please.
Phone 01-540 9534

TEST SET FREQUENCY RESPONSE CT381

Consisting of: sweep generator, indicator response curve, flat-faced tube long persistence. Power supply. Calibrator frequency CT432. Frequency range: 10kc/s-33Mc/s in nine directly calibrated ranges. Accuracy $\pm 3\%$ of the indicated centre frequency. F.M. deviation: (nominal). 0-500kc/s above-4Mc/s. 0-400kc/s at 1.5Mc/s-4Mc/s. 0-165kc/s at 600kc/s-1.5Mc/s, falling to 3kc/s at 10kc/s. Output impedance: 75 ohms resistive. Power supplies: Mains 100-120V and 180-250V. Frequency 50-500c/s. Consumption 340W (nominal). Price **£195**. **Belling Lee** radio frequency interference filter type Y2005S. 100 Amps. 400W. 440V. Single wave **£15**.

HEWLETT PACKARD

185B. 1GHZ SAMPLING OSCILLOSCOPE.
Horizontal Sweep speeds: 10 ranges, 10 nsec/cm to 10 sec/cm, accuracy within $\pm 5\%$. Magnification: 7 calibrated ranges X1, X2, X5, X10, X20, X50 and X100. Increases maximum calibrated sweep speed to 0.1 nsec/cm; with vernier maximum sweep speed is further extended to 0.04 nsec/cm. Intensity and sampling intensity are not affected by magnification. High frequency: Input frequency: 50 to 1000 Mc for sweep speeds 200mv and 1000mv; $\pm 3\%$. Time: Approximately 5 sec burst of 50 Mc sine wave. Frequency accuracy $\pm 2\%$. In addition the Model 185B provides output signals for X-Y recorders and provides means for controlling the display either manually or externally. Full specification on request. Price **£295**.

- 430C Microwave power meter. **£60**
- H01-8401A Leveller amplifier. **£39**
- 8709A Synchronizer. **£120**
- 8734B Pin modulator 7.0-12.4GC. **£95**
- 8732A Pin Modulator 1.8-4.5 GC. **£85**
- 8431A Bandpass filter 2-4GC. **£40**
- 797D Directional Coupler 1.9-4.1GHz. **£30**
- 8436A Bandpass filter 8-12.4GC. **£95**
- 185A 800MHz Sampling oscilloscope.
- 185B Sampling oscilloscope.

L30047 CAMBRIDGE UNIVERSAL BRIDGE.
Measures DC resistance, self-inductance, mutual inductance, capacity and frequency. Full specification on request. **£95**.

Voltmeter Valve CT54 (Micovac), with mains power supply (power supply not available separately). In strong metal case with full operating instructions. 2.4V-480V AC or DC in 6 ranges. 1 ohm to 10 Megohm in 5 ranges. Indicated on 4 in. scale meter. Complete with probe. **£12.50** including p. and p. (Leads extra.)

MUIRHEAD FREQUENCY ANALYSER TYPE D-669-B.
Frequency range 30c/s-30kc/s. Accuracy better than 1.5%. Input voltage 300V-100V for full scale deflexion. Smallest indication 15µV. Maximum input voltage 300V r.m.s. Price **£95**. Full spec. on request.

TEKTRONIX

NON-PLUG-IN UNIT OSCILLOSCOPE.
524AD. DC-10MHz. **£100.**
MAIN FRAME OSCILLOSCOPES:
545. DC-30MHz. 545A. DC-30MHz. 545B. DC-33MHz.
PLUG-IN UNITS.
Type CA. 0.05V/cm to 20V/cm.
Type D. 1mV/cm to 50V/cm. Type G. 0.05V/cm to 20V/cm.
Type L. 5mV/cm to 2V/cm. 0.05V/cm to 20V/cm.
230 DIGITAL UNIT.
Digital readout parameters. Pulse amplitude, pulse risetime and falltime, pulse width, time interval.
R116. 10-NS PROGRAMMABLE PULSE GENERATOR
with Delay.
PASSIVE PROBE P6006 with 10X attenuation, designed for oscilloscopes having an input resistance of 1 megohm and input capacitance of up to 55pF. Price **£10.**
PROBE P6065 10X. 10 megohm 12.5pF. 500V D.C. max. Length 6ft. Price **£15.**

MUIRHEAD 2-PH. L.F. DECADE OSCILLATOR Type D880.
Frequency range 0.01c/s-11.2kc/s (continuously variable above 0.1c/s).

V.L.F. 0.01c/s-0.1c/s in steps of 0.01c/s. Hourly frequency stability.
Ranges X1, X10, X100 $\pm 0.05\%$ }
Ranges X0, 1, V.L.F. ± 0.1 } 3 hours.

T.F.801D/1/S.A.M. SIGNAL GENERATOR.
Freq. range: 10 MHz to 485 MHz. Built-in crystal calibrator. Internal and external sine a.m. External pulse modulation. Calibration Accuracy: Using crystal calibrator, within $\pm 0.2\%$ over entire frequency range. R.F. out-level 0.1µV to 1V source e.m.f.

OA.1094A/3 H.F. SPECTRUM ANALYSER
with L.F. extension unit type TM6448.
Freq. range: 100 Hz to 30 MHz. Measures relative amplitudes up to 60 dB. Spectrum width 0-30 KHz. Sweep duration: 0.1, 0.3, 1, 3, 10, 30 sec. and manual. Full spec on request. **£250** as seen condition, buyer to collect.

OA.1094A/S H.F. SPECTRUM ANALYSER. Freq. range: 3 MHz to 30 MHz in nine steps, spectrum width 0 to 30 KHz. Sweep distortion: 0.1, 0.3, 1, 3, 10, 30 secs. and manual. Full spec. on request. **£150** as seen condition, buyer to collect.

T.111 ROBAND TRANSISTORIZED SUPPLY. Mains input 110V or 230V, output 0-50V at 5 Amperes cont. variable, overload cut-out. As seen **£15**.

REMSCOPE S01/740 STORAGE OSCILLOSCOPE.
Fluorescence: Yellow, resolution: 40 lines/cm E.H.T.: 8kV, display time: 10 mins-1 hr approx., storage time: 1 week approx.

CD 1212 WIDE-BAND GENERAL-PURPOSE OSCILLOSCOPE.
Employing plug-in pre-amplifiers for single or dual trace displays.
Wide-band pre-amplifier CX 1251. Bandwidth: DC-40Mc/s (-3dB ± 1 dB); 2.5c/s-40Mc/s AC coupled (-3dB ± 1 dB). Rise time 8 nanosec approx. Sensitivity: 50mV/cm-500V/cm in nine calibrated ranges with fine gain control.
Dual trace pre-amplifier CX 1252. Bandwidth: DC-24Mc/s (-3dB ± 1 dB) AC coupled. Rise time: 14 nanosec approx. Sensitivity: 50mV/cm-500V/cm in nine calibrated ranges with fine gain control. Full specification on request. **£128**.

T.F.801B/3/S.A.M. SIGNAL GENERATOR.
Freq. range: 12 MHz to 485 MHz in five bands. Built-in crystal calibrator. Full spec. on request.

CT. 373 TEST SET. Oscillator: 17c/s-170kc/s $\pm 1\%$, ± 1 c/s at ambient temp. 0°C-45°C. Distortion Meter: Freq. range: 20c/s to 20kc/s, distortion range: 10%, 30%, 100% f.s.d. 0.5% readable. Signal input: approx. 500mV to 130V basic range. 250mV to 1300V extreme limits. Full spec. on request. **£30**.

AVO MODEL 3 VALVE TESTER. Enables comprehensive characteristics to be plotted or measures valves on a simple good/bad basis. **£55**.

AVO CT 160 VALVE TESTER. As above but in portable valise form. **£65**. Viewing by appointment only.

TINSLEY TYPE 4363E AUTO VERNIER POTENTIOMETER.
PYE Precision vernier potentiometer 7568. 1µV to 1.90100V in two ranges. Accuracy 0.002%.

DIE-CUT FOIL STRAIN GAUGES by DENTONICS TYPE M234C13L. Resistance in ohms 350 ± 5 . Gauge factor 2.13 $\pm 1\%$. Max Temp 350°F (173°C). Price **£2** per packet (5).


TF.937 F.M./A.M. SIGNAL GENERATOR.
Freq. range 85 KHz to 30 MHz. The carrier freq. can be standardized against a built-in dual freq. crystal calibrator, which is complete with miniature loudspeaker as an aural beat detector. **£87**.

TF.114H/S SIGNAL GENERATOR. Frequency range: 10 KHz-72 MHz. Stability: 0.002%. High discrimination, plus crystal calibrator. Good r.f. waveform at all frequencies. Protected thermocouple level monitor. Full spec. on request. **£220**.

TEST SET DEVIATION FM No 2. The carrier frequency range extends from 2.5Mc/s to 10Mc/s and from 20Mc/s to 100Mc/s in a total of eight bands: the deviation ranges are 0 to 5kc/s, 0 to 25kc/s and 0 to 75kc/s. **£48**.

RACAL UNIVERSAL COUNTER/TIMER SA550 (CT488)

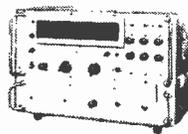8 digit in-line read-out. Facilities include: direct frequency measurement up to 100 MHz; pulse, period, ratio, time interval and totalising measurements. Input sensitivity variable from 300mV to 3V, three independent inputs self-check etc. Full spec on request.



TRANSISTORS AND DIODES

Type	Pc	VCBO	FT MHz	
BSV29 (SNPN)	300mw	15	20	15p
BD107 (SNPN)	11-5w	64	100	63p
2N711B/2G106 (SPNP)	150mw	18	120/150 Tot. Sw. Time 275 nS	43p
2N985 (GNPN)	300mw	15	Tot. Sw. Time 115 nS	95p
2N1304 (GNPN)	150mw	30		15p
2N1309 (GNPN)	150mw	30		30p
2N1046 (GNPN)	50w	100		£2.60
2N1146A (GNPN)	90w	70		45p
2N1542 (G)	106w	100	0.35	50p
2N1547 (G)	106w	100	0.35	75p
2N1557 (G)	106w	40	0.35	50p
2N2080 (G)	170w	70		£1.10
2N2082 (G)	170w	40	0.2	£1.10
2N2405 (SNPN)	1w	120		55p
2N3054 (SNPN)	29w	90	1.2	40p
2N3055 (SNPN)	115w	100		45p
2N3375 (SNPN)	11-6w	65	500	£3.46
2N4427 (SNPN)	3.5w	40	700	52p
2N5322 (SNPN)	10w	65	325	50p

ASZ16/OC28 **25p.** OC35 **40p.** OC42 **40p.** OC71 **12p.** CV7006/OC72 **20p.** OC75 **25p.** OC83 **25p.** GET110/NKT303 **20p.** OC702 **10p.** OA10 **25p.** RAS508AF **25p.** RAS310AF **25p.** STC Wire End 400P1V1A **4 for £50p.** IN3193 **13p.** IN3194 **14p.** IN3255 **20p.**

RCA PHOTOMULTIPLIER C310058

Checked and tested. **£37.50**

BRIDGE RECTIFIERS

1B40K05 50v 4a. **95p**

SWITCHES

Edwards High Vacuum "Speedivac" model VSK1B. Range 25-760 torr contact ratings 250v. 5a. volume 4-2 cu. cm. max. working pressure 15lb/sq. in. gauge net weight 17 ozs. **£6-20**
Belling Delay hand reset L415. **£1-10**
Stackpole min. rocker 125v. 10a. 250v. 5a. **20p**
Tippalite Rocker 12v. **60p**

CIRCUIT BREAKERS 250V AC

AMP	TRIP	TYPE	
2-0	D	Westingh. 550	
4-0	—	Securax 5000	
7-0	Inst.	Westingh. 550	
7-0	4	Heinemann (60c.) AM12	
8-0	Inst.	Westingh. 550	
9-0	Inst.	Westingh. 550	
10-0	—	Securax 5000	
20-0	—	ETA Magnetic	

DIGITAL COUNTERS

Veeder Root Mech. Reset 4 dig. **50p**

STABILIZED POWER SUPPLIES

Gresham Lion GX60/10a-60v. 10 amp. set to 30v. **£65.00** incl. carriage
Lambda CC28v-Inp 205-265v. output 28v dc $\pm 5\%$ 3-4 amp **£38.50** incl. p. & p.
Power Elect. Inp 240v outputs 20v 6-5a 10v 3-4 amp + 10v 300ma **£38.50** incl. carr.

RELAYS

Varley Min. 700 0.12v. **50p**
Siemens Min. 12/15v. **50p**
Magnetic Dev. Type 596E. **£2.00**

CONNECTORS

McMurdo Red Range. Plug RP24. **56p**
McMurdo Red Range. SKT RS32. **90p**
Eng. Elect. Edge. 36 way 0.2 inch pair **£1.00**
Sylvania Edge. 48 way 0.125 inch pair **40p**
Amphenol MS3106B-36-10. **£4.50**
Continental microminiature 2B 1080IN26 **£1.30**

CAPACITORS

Daly Electrolytic 9000µF 25v **50p** p/p 15p; 500µF 50v **30p** p/p 10p; TCC 16µF + 1µF + 8µF 450v **75p** p/p 15p; CCL 50µF + 50µF 275v **40p** p/p 10p; CCL Suppressor Unit Type SU103/1 comprising capacitor Diode and Resistor **40p** p/p 10p; Duplifer Metallised Paper type 426 100µF 150v **50p** p/p 25p; RIC 1-8µF 440v a.c. **35p** p/p 10p.

MOTORS

E.E. ½hp 230v. 50c 1ph 50c. 1440rpm complete with cap 80/100uf 275v. **£15.50** incl. carr.
3 phase 2HP motor 60/50c., 1800/1500 RPM. 208/220/440v. **£21.50** incl. Carriage
Cat. 2026391 Potter Instruments flange mounting capstan motor. 0.2HP cont. 110V DC 4 amp **£25.00** incl. carr.

FANS, CENTRIFUGAL BLOWERS

Airmax Type M1/Y3954 (3 blades) Cast Aluminium alloy impeller & casing (corresponds to current type 3965 7½") 230v. 1ph 50c 2900rpm Class "A" insulation 425cm free air weight 9½lbs. incl. p.p. **£21.00**.
Woods Aerofoil short casing type "S" 2700rpm 220/250v 1ph 50c 6" plastic impeller incl. p.p. **£11.50**.
Woods Aerofoil Code 7.5 280K 200/250v. 1.0a 1ph 50c 2700rpm 550cm free air. 7½" impeller 14 blades incl. p.p. **£13.50**.



Service Electric Hi-Velocity Fans, suitable for Gas combustion Systems. Steam exhausting. Pneumatic conveying. Cooling Electronic equipment. Air blast for Oil burners. **Secomak** Model 365 (corresponds to 575) Airblast Fan, 440v 3ph 50c 0.75hp 2850rpm, continuous 160cfm 12 in. w.g. nett weight 44lb, price incl. carr. **£41.00**. **Secomak** model 350 250v 1ph 50c 0.166hp, 2800 rpm continuous 50cfm 2 in. w.g. net weight 34lbs, price incl. carr. **£26.00**.
Air Controls type VBL4 200/250v 1ph 50c. 11 Ccfm free air weight 7½lbs price incl. p.p. **£14.50**.
Type VBL5 200/250v 1ph 50c. 172 cfm free air. Weight 10½lbs. price incl. p.p. **£18.50**.
William Allday Alcosa Single Stage Vacuum Pump Model HSP0B 8 HG. Rpm 1420. E.E. 3 phase induction motor 1/3 hp cont 220/250v 380/440v. Class E ins. **£21.00** incl. carriage
Gast MFG. Vacuum pump 0522-P702-R26X. Motor 110/120v. A.C. 1 ph. 60c 1725 rpm. Class E. 10cuft to 10in Mercury in 2 mins maintains vacuum 635mm Mercury. Or as compressor 10psi int. or 15 psi cont. **£25.00** incl. carr.



Where p.p. not advised add 10p per £ handling and post (in UK). Cash with order. Personal callers welcome. Open Mon.-Wed. 9.30-5.00 Fri.-Sat 9.30-5.00. Free Car Park adj. **PRICES SHOWN ARE EXCLUSIVE OF V.A.T.**

W. & B. MACFARLANE

126 UXBRIDGE ROAD, HANWELL, LONDON W7 3SL

WW-043 FOR FURTHER DETAILS

G. F. MILWARD

ELECTRONIC COMPONENTS

Wholesale/Retail:

369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339



CALLING ALL INDUSTRIAL BUYERS!!




We are glad to say that it is now possible to supply from stock the following integrated circuits. **ALL ARE BRANDED, FULL SPECIFICATION** devices offered at unbeatable prices! This is **YOUR** chance to cut manufacturing costs and greatly increase profit margins!

	1/99	100/499	500/1000		1/99	100/499	500/1000		1/99	100/499	500/1000
7400	£0-15	£0-125	£0-10	7442	£0-645	£0-537	£0-43	7494	£0-495	£0-412	£0-33
7401	£0-15	£0-125	£0-10	7443	£1-275	£1-062	£0-85	7495	£0-63	£0-525	£0-42
7402	£0-15	£0-125	£0-10	7445	£0-855	£0-712	£0-57	7496	£0-72	£0-60	£0-48
7403	£0-15	£0-125	£0-10	7446	£1-05	£0-875	£0-70	74104	£0-315	£0-262	£0-21
7404	£0-18	£0-15	£0-12	7446A	£1-05	£0-875	£0-70	74105	£0-315	£0-262	£0-21
7405	£0-18	£0-15	£0-12	7447	£1-05	£0-875	£0-70	74107	£0-315	£0-262	£0-21
7406	£0-375	£0-312	£0-25	7447A	£1-05	£0-875	£0-70	74121	£0-315	£0-262	£0-21
7407	£0-375	£0-312	£0-25	7448	£0-855	£0-712	£0-57	74122	£0-45	£0-375	£0-30
7408	£0-15	£0-125	£0-10	7450	£0-15	£0-125	£0-10	74123	£0-63	£0-525	£0-42
7409	£0-15	£0-125	£0-10	7451	£0-15	£0-125	£0-10	74141	£0-75	£0-625	£0-50
7410	£0-15	£0-125	£0-10	7453	£0-15	£0-125	£0-10	74151	£0-69	£0-575	£0-46
7412	£0-195	£0-162	£0-13	7454	£0-15	£0-125	£0-10	74153	£0-69	£0-575	£0-46
7413	£0-345	£0-287	£0-23	7460	£0-15	£0-125	£0-10	74155	£0-69	£0-575	£0-46
7416	£0-345	£0-287	£0-23	7472	£0-255	£0-212	£0-17	74156	£0-69	£0-575	£0-46
7417	£0-345	£0-287	£0-23	7473	£0-153	£0-262	£0-21	74160	£1-005	£0-837	£0-67
7420	£0-15	£0-125	£0-10	7474	£0-315	£0-262	£0-21	74161	£1-005	£0-837	£0-67
7423	£0-27	£0-225	£0-18	7475	£0-465	£0-387	£0-31	74162	£1-005	£0-837	£0-67
7425	£0-27	£0-225	£0-18	7476	£0-315	£0-262	£0-21	74163	£1-005	£0-837	£0-67
7426	£0-27	£0-225	£0-18	7480	£0-435	£0-362	£0-29	74166	£1-425	£1-187	£0-95
7427	£0-27	£0-225	£0-18	7482	£0-75	£0-625	£0-50	74174	£1-20	£1-00	£0-80
7430	£0-15	£0-125	£0-10	7483	£0-825	£0-687	£0-55	74175	£0-975	£0-812	£0-65
7432	£0-25	£0-225	£0-18	7485	£1-275	£1-062	£0-85	74192	£1-275	£1-062	£0-85
7437	£0-27	£0-225	£0-18	7486	£0-315	£0-262	£0-21	74193	£1-275	£1-062	£0-85
7438	£0-27	£0-225	£0-18	7490	£0-465	£0-387	£0-31	74198	£2-10	£1-75	£1-40
7440	£0-15	£0-125	£0-10	7492	£0-465	£0-387	£0-31	74199	£2-10	£1-75	£1-40
7441A	£0-825	£0-687	£0-55	7493	£0-465	£0-387	£0-31				

To secure the above prices, all orders for these devices must exceed £10 in total value. Price rating is established by TOTAL NUMBER OF DEVICES ORDERED. Any mix may be made. For special quotations for large orders ring 021-327 2339 NOW!!!

MICROWAVE DEVICES		
CL8300	Gunn effect oscillator	9-4GHz £40
CL8370	ditto	9-5GHz £10
CL8380	ditto	10-5GHz £10
CL8390	ditto	11-5GHz £10
CL8430	ditto	9-35GHz £40
CL8450	ditto	9-35GHz £40
CL8470	ditto	9-35GHz £40
BXY27	Varactor Diode, "S" Band, Cut-off	70GHz £1
BXY28	Varactor Diode, Cut-off	100GHz £1
BXY32	Frequency Multiplier, "X" Band	150GHz £1
BXY35A/C	ditto	25GHz £1
BXY36C/D	ditto	75GHz £1
BXY37C/D	ditto	100GHz £1
BXY38C/E	ditto	120GHz £1
BXY39C/D	ditto	150GHz £1
BXY40D/E	ditto	180GHz £1
BXY41C/D/E	ditto	200GHz £1

12 VOLT FLUORESCENT LIGHTING

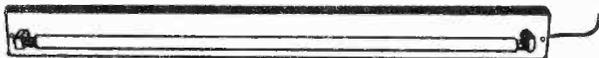

Inverter transformers 13/15W (circuit included) **70p**
 "Current economy" transistor (600 ma.) **50p**
 "Maximum light" transistor (1-3A) **50p**
 Resistors/capacitors to suit **15p**
 Lampholders (long lead) (needed with cases) Pair **30p**
 (short lead) Pair **20p**
 White enamel case 21in (postage 30p) **70p**
 Tube, 21in-13W **45p**
 (Note: tube only supplied if case ordered, to prevent postal damage).
 13W fitting ready built and tested—including tube (postage 30p) **£3.75**
 Post/packing, 25p per order except where shown.

NEW! NEW! NEW! NEW!

An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.
 Method: Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner.
 Light sensitive aerosol spray **£1.00** plus postage
 Developer and Etchant **50p** plus postage

Single-sided Copper-clad Fibreglass Board **75p** sq. ft.
 Double-sided Copper-clad Fibreglass Board **£1.00** sq. ft.
 Boards cut to any multiple of 6". Max. size 3' x 4'.

1,000,000 POTENTIOMETERS

We have bought a huge assortment of volume controls.

Pre-sets, sliders, etc. All are in manufacturer's original packing.

Manufacturing quantities of some types available.

Write or phone for details.

Sample bag 100 mixed £2.50

ELECTROLYTIC CAPACITORS

Several thousand of each of the following types. Silly price to clear!

ALL NEW STOCK

5µf 10V	35p dozen
10µf 10V	35p dozen
50µf 10V	35p dozen
100µf 10V	35p dozen
330µf 16V	45p dozen
330µf 25V	60p dozen
330µf 35V	80p dozen
2200µf 16V	£1 dozen
15000µf 25V	50p each

HOBBY CORNER!

BRAN TUB !!!

- ★ Resistors, Wire-wound and Carbon
- ★ Capacitors, Silver-mica, Paper, Ceramic, Polyester and Electrolytic
- ★ Controls, Volume, Pre-set, Carbon, Wire
- ★ Diodes, Silicon, Germanium, Zener
- ★ Transistors, Silicon, Germanium

All the above are new and unused stock.

We have made up packs of 2lb gross weight, all are different in content, and contain a mixture of components from the above list. This is a fantastic, unrepeatable offer that will enable you to get a good stock of spares at a tiny fraction of normal price!

To make things even more interesting — TWENTY OF THESE BAGS ALSO CONTAIN A POUND NOTE! TWENTY CUSTOMERS WILL BE VERY PLEASED INDEED!

And the price that we are asking? Only **£1.50** including both postage and VAT!

Rush your order now! This offer is only made to reduce our surplus stock! It is unlikely that in these days of rising prices we shall ever be able to repeat!

£1 100 1/2 WATT RESISTORS
 100 CERAMIC CAPACITORS
 100 DIODES

POSTAGE 25p PACK No. 1

£1 100 RESISTORS
 100 CERAMIC CAPACITORS
 100 POLYSTYRENE CAPACITORS

POSTAGE 25p PACK No. 2

£1 100 RESISTORS
 100 CERAMIC CAPACITORS
 50 MULLARD POLYESTER CAPACITORS

POSTAGE 25p PACK No. 4

£1 20 ASSORTED UNUSED MARKED, TESTED TRANSISTORS BC108 ETC.

POSTAGE 25p PACK No. 5

£1 1 TRANSISTORISED SIGNAL TRACER KIT
 1 TRANSISTORISED SIGNAL INJECTOR KIT

POSTAGE 25p PACK No. 6

£1 100 RESISTORS
 100 CAPACITORS (ASSORTED TYPES)

POSTAGE 25p PACK No. 8

REMEMBER! ALL GOODS PLUS 8% V.A.T.

G. F. MILWARD, 369 Alum Rock Rd., Birmingham B8 3DR. Postage (minimum) per order 25p.

VALVES

A1065	1.25	ECL80	0.55
AR8	0.55	ECL82	0.35
ATP4	0.50	ECL83	0.70
B12H	3.00	ECL86	0.50
CY31	0.50	EF36	0.85
DAF96	0.50	EF37A	1.20
DF96	0.55	EF40	0.75
DK96	0.55	EF41	0.65
DL92	0.40	EF80	0.30
DL96	0.60	EF83	1.25
DY86/87	0.40	EF85	0.35
DY802	0.45	EF86	0.35
E88CC/01	1.20	EF89	0.30
E180CC	0.70	EF91	0.45
E182CC	1.25	EF92	0.50
EA50	0.40	EF95	0.40
EAB3C0	0.40	EF183	0.35
EAF42	0.75	EF184	0.35
EB91	0.30	EFL200	0.75
EB33	1.00	EL33	2.30
EB41	0.75	EL34	0.70
EBF80	0.40	EL36	0.80
EBF83	0.50	EL41	0.80
EBF89	0.40	EL81	0.60
EC52	0.35	EL82	0.55
ECC81	0.40	EL84	0.30
ECC82	0.35	EL85	0.60
ECC83	0.35	EL86	0.45
ECC84	0.35	EL90	0.45
ECC85	0.40	EL504	0.60
ECC86	0.90	EM31	0.60
ECC88	0.50	EM80	0.55
ECC89	0.70	EM84	0.40
ECF80	0.40	EM87	1.00
ECF82	0.40	EY51	0.45
ECF801	0.75	EY81	0.45
ECH42	0.80	EY86	0.40
ECH81	0.35	EY88	0.50
ECH83	0.45	EZ40	0.70
ECH84	0.45	EZ41	0.75
		PL508	1.00

PL509	1.35	U191	0.75
PL802	0.95	U801	0.75
PY33	0.60	UABC80	0.40
GZ24	0.70	UAF42	0.85
GZ37	1.00	UY81	0.40
KT66	2.50	UY82	0.40
KT88	3.00	UY83	0.40
MH4	0.75	UY88	0.45
ML6	0.85	UY90	1.00
OA2	0.45	UCC85	0.45
OB2	0.75	UCC86	0.75
PC900	0.50	UCC87	0.45
PC901	0.50	UCC88	0.45
PC902	0.50	UCC89	0.45
PC903	0.50	UCC90	0.45
PC904	0.50	UCC91	0.45
PC905	0.50	UCC92	0.45
PC906	0.50	UCC93	0.45
PC907	0.50	UCC94	0.45
PC908	0.50	UCC95	0.45
PC909	0.50	UCC96	0.45
PC910	0.50	UCC97	0.45
PC911	0.50	UCC98	0.45
PC912	0.50	UCC99	0.45
PC913	0.50	UCC100	0.45

VR150/30	0.45	3D6	0.40
X66	0.85	3A4	0.60
Z800U	2.78	5V4G	0.55
Z801U	2.78	5Y3GT	0.55
Z800T	1.20	5B254M	4.00
Z801T	1.20	5B255M	3.50
IA3	0.55	5R4GY	0.50
IL4	0.25	5U4G	0.80

VAT 8% EXTRA

6AK5	0.40	6C6	0.50
6AK8	0.40	6CB6	0.50
6AL5	0.30	6CH6	1.45
6AL5 W	0.55	6CL6	0.75
6AM6	0.45	6D6	0.55
6AN8	0.45	6EA8	0.85
6AQ5	0.45	6F7	1.10
6AQ5W	0.70	6F8G	0.75
6AS6	0.80	6F23	1.00
6AT5	0.45	6F32	0.80
6AU6	0.40	6F33	3.50
6AV6	0.45	6H6	0.35
6AX4GT	0.75	6J4WA	1.25
6AX5GT	1.00	6J5	0.65
6B7	0.70	6J5GT	0.50
6B8	0.35	6K25	1.00
6BE6	0.40	6J7	0.80
6BG6G	0.90	6J7G	0.40
6BJ6	0.85	6K6GT	0.80
6BQ7A	0.60	6K7	0.35
6BR7	1.20	6K7G	0.58
6BW6	1.00	6K8GT	0.50
6BW7	1.00	6K25	1.00
6CA	0.40	6L6	1.25



THE VALVE WITH A GUARANTEE

VICIDON TUBES EMI types 9677A & 9677C £20.00 ea.

30F5	1.00	957	0.50
30FL1	1.00	1829	0.78
30FL12	1.10	2051	1.00
30FL14	0.80	5833	3.00
30L15	0.95	6057	0.75
30L17	0.95	6060	0.78
30P12	1.00	6064	0.60
30P19	1.00	6065	1.00
30PL1	0.95	9080	2.30
30PL3	1.10	6146	2.25
		6146B	3.25
		8020	5.00
		9001	5.00
		9002	8.50
		9003	0.70
		9004	0.35
		9006	0.35

30PL14	1.10	CG7-5	12.00
35FL12	0.75	DG13-2	18.00
35W4	0.50	DG13-34	12.00
35Z4GT	0.70	MM43-35	35.00
50C5	0.60	VCR138A	8.00
50D6G	1.10	3BP1	4.50
50D6G	1.10	88D	9.00
50D6G	1.10	88J	8.00
50D6G	1.10	88L	9.00

SPECIAL VALVES CV239 45.00 M503-2J42

TRANSISTORS

AC113	AF178	BF167	GET116
AC126	AF186	BF185	GEX66
AC127	AF212	BFY51	NKT222
AC128	AS226	BFY52	OA5
AC176	AS227	BFY90	OA47
AC178	AS228	BSY27	OA70
AC179	AS229	BSY38	OA71
AC180	AS230	BSY95A	OA73
AC181	AS231	BSY95B	OA79
AC182	AS232	BSY95C	OA91
AC183	AS233	BSY95D	OA200
AC184	AS234	BSY95E	OA202
AC185	AS235	BSY95F	OA2000
AC186	AS236	BSY95G	OC22
AC187	AS237	BSY95H	OC22
AC188	AS238	BSY95I	OC22
AC189	AS239	BSY95J	OC22
AC190	AS240	BSY95K	OC22
AC191	AS241	BSY95L	OC22
AC192	AS242	BSY95M	OC22
AC193	AS243	BSY95N	OC22
AC194	AS244	BSY95O	OC22
AC195	AS245	BSY95P	OC22
AC196	AS246	BSY95Q	OC22
AC197	AS247	BSY95R	OC22
AC198	AS248	BSY95S	OC22
AC199	AS249	BSY95T	OC22
AC200	AS250	BSY95U	OC22


Please write or phone for current price of any of the transistors, diodes shown below.

VALVES AND TRANSISTORS


Telephone enquiries for valves, transistors, etc., retail 749 3934; trade and export 743 0899.

OTHERS IN STOCK inc. integrated circuits, CRT & special valves. Min. Mail Order £1. U.K. Postage £1-£2, 17p. £2-3, 25p, over £3 free. C.O.D 25p extra.

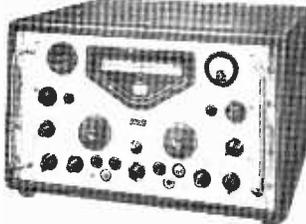A lot of these valves are imported and prices vary for each delivery, so we reserve the right to change prices for new stock when unavailable.



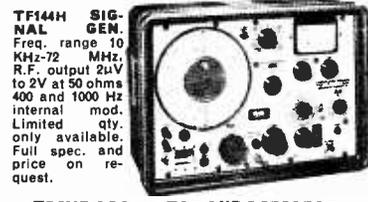RACAL RECEIVERS Models RA17, RA17 Mk. II, RA 17L, RA17W, RA17IE, in condition for working "as seen" to brand new in cabinets. Prices on application. DIVERSITY SWITCH TYPE MA168B, solid state, £45.00.




TF 520B OSCILLATOR AND DETECTOR UNIT £50.00.

TF 1228B, TF1225A, TF 577A. WHITE NOISE TEST SET £185.00. Full spec. on request.

MARCONI TF 995A/5 FM/AM SIGNAL GENERATOR. Four additional tuning controls facilitate narrow band measurements. 3 Int. A.M. mod. Freq. of 400, 1000 & 1500Hz at up to 50% F.M. deviation ± 5kHz - ± 120kHz. Output 0.1-20mV depending on termination. Freq. range 1.5-220MHz. P.O.A.

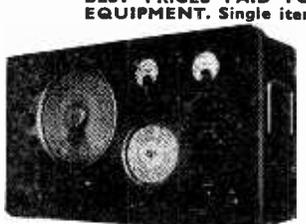TF 1258A VHF SPECTRUM ANALYSER for analysis and measurement of Radar equipment. Frequency range 190 to 230MHz with crystal check points. Sweep width 0.5 to 5MHz, output pulse delay (a) 85-175 µsec, (b) 0.7-1.4 mSec with x1 and x2 multiplier and -2, x1, x2 multiplier. Output 2µV to 20mV with x10 multiplier. £290.




TF 801D/1S SIGNAL GENERATOR. Range 10-95 MHz in five ranges. R.F. output 0.1 µV/V source s.m.t. Dial calibrated in volts, decibels and power relative to thermal noise. Pilot tone attenuator. 50Ω output impedance. Internal modulation at 1 kHz at up to 90% depth, also external sine and pulse modulation. Built-in 5MHz crystal calibrator. Separate R.F. and mod. meters. P.O.A.

TF 1400S DOUBLE PULSE GENERATOR WITH TM 6000/S SECONDARY PULSE UNIT. For testing radar, nucleonics, scopes, counters, filters etc. SPEC. TF 1400S. Rep. freq. 10Hz to 100kHz, pulse width 0.1 to 100µ sec., delay -1.5 to +3000µ sec., rise time 30N sec. SPEC. TM 6000/S. As for TF1400S except pulse width 0.5 to 25µ sec., delay 0 to +300µ sec. £230.

MARCONI OA 1094A/3 SPECTRUM ANALYSER with L.F. extension unit. Freq. range 100MHz. Full Spec & P.O.A.

ROHDE & SCHWARZ Z-g DIAGRAPH TYPE ZDU. 30-420 MHz. 50Ω. Directly measures multi-terminal networks, phase shift, phase angle etc. with complementary POWER SIGNAL GENERATOR TYPE SMLM High freq. resolution, internal/external mod., up to 3V out. P.O.A. POLYSCO SWOB 1. G.S-400MHz 75Ω. P.O.A. VHF WATTMETER & MATCHING INDICATOR 30/80W, 230MHz, 75Ω. P.O.A. VHF VOLTMEETER TYPE UDDN P.O.A. MICROWAVE POWER METER TYPE NRD. 0-3200MHz at 50Ω. Int. 0-200mW, 4 ranges, built-in calibration check with measuring head £125. FREQUENCY SYNTHESIZER TYPE XUA. 30Hz-30MHz with FREQUENCY INDICATOR TYPE FKM. 15-30MHz; 30-100MHz. P.O.A.

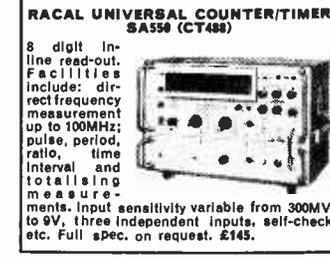BEST PRICES PAID FOR TEST AND COMMUNICATION EQUIPMENT. Single items or quantities. Private or industrial.



RACAL UNIVERSAL COUNTER/TIMER SA559 (CT488)

8 digit in-line read-out. Facilities include: direct frequency measurement up to 100MHz; pulse, period, ratio, time interval and totalling measurements. Input sensitivity variable from 300mV to 9V, three independent inputs, self-check etc. Full spec. on request. £145.

PLEASE NOTE Unless offered as "as seen"

ALL EQUIPMENT

ordered from us is completely overhauled mechanically and electrically in our own laboratories

FOR EXPORT ONLY TRANSMITTERS: BC 610 Hallicrafters. RCA ET 4336 also modified version of increased output to 700W. COLLINS TYPE 331D 415W, 10 channel, autotune and manual tuning. All above complete installation and spare parts. RECEIVERS: 19, 19HP, 38, 62. C-13 TRANSMITTERS: RACAL COMMUNICATIONS EQUIPMENT. We are able to offer a comprehensive selection from the range of this modern high class equipment including, receivers, L.F. Converters, SSB adaptors, panoramic adaptors, diversity switches, transmitter driver units, linear amplifiers can be built to customers' requirements. Please send us your enquiries.

AR88 SPARES. We hold the largest stock in U.K. Write for list. R.F. METER 0-8 amp. 2 1/2" (U.S.A.) £1-90 P. & P. 15p.

TELEPHONE TYPE "J" (Tropicalised) 10 line MAGNETO PHONE SWITCHBOARD 50 line AUTOMATIC PRIVATE TELEPHONE SWITCHBOARD Price of each of the above on application.

PLEASE ADD 8% VAT

COLOMOR (ELECTRONICS) LTD. 170 Goldhawk Rd., London, W.12 Tel. 01 - 743 0899

TEKTRONIX OSCILLOSCOPES

Oscilloscopes 585 DC to 100MHz. Separate time bases with delay and 5X magnifier. Time base A: 0.05 microseconds to 2 sec/cm in 24 stages also continuously variable between steps. Time base B: 2 microseconds to 10 sec in 18 stages. Delay 1 microsec to 10 sec. Complete with type 81 adaptor enabling use of all letter series plug-ins. Type 80 plug-in (less probe) also available.

541A-33MHz. Choice of plug-ins. P.O.A. LA265A(545A)-33MHz, separate time bases with delay. P.O.A.

545-15MHz. Separate time bases with delay. Price on application. PLUG-IN UNITS

CA-24 MHz dual trace 50MV-20V. G-20 MHz differential 50MV-20V. L-30 MHz fast rise time 5MV-20V. D-High gain differential 1MV-50V. N 600MHz sampling 10MV-cm. 53/54C. Dual trace 33MHz, 60MHz, 0.05-20V.

BOONTON FM/AM SIGNAL GENERATOR TYPE 202E. 54-216MHz in 2 ranges. complete with separate power supply £175. EHV POWER SUPPLY 115V input 100KV at 5mA output £150.

SOLARTRON AS 870.3 CURRENT LIMITING POWER SUPPLY

0-30V in steps of 10, 1.0.1V at up to 3A 250.

Open 9-12.30, 1.30-5.30 p.m. except Thursday 9-1 p.m.

HEWLETT - PACKARD

175A OSCILLOSCOPE with 1750A dual trace vert plug-in and 1781B delay time base plug-in. 50MHz minimum bandwidth at 50mV/cm. TR modes: main, main single, mixed, main delayed, delaying. Full Spec & P.O.A.

185A SAMPLING OSCILLOSCOPE. 800MHz. complete with 188A 1mV/cm dual trace plug-in. 1GHz probe and manual. Full spec & P.O.A.

524C ELECTRONIC COUNTER/TIMER direct reading to 10MHz. extended to 500MHz depending on converter plug-in. also period and time measurement. 8 digit in-line display on Nixie tubes. £165 with one plug-in (as below) 524B model, spec as for 524C but display on 6 neon lamp decades and 2 meters £115 with one of the following plug-ins: 526A Video amp. 525A: 10-100MHz, 525B: 100-220 MHz, (525C: 100-500MHz £45 extra).

616B SHF SIGNAL GENERATOR Freq 1.75GHz-4.2GHz. Mod: F.M., C.W., Pulse, Ext A.M., output 0.1µV-200mV. Full spec & P.O.A.

800AB AUDIO OSCILLATOR 19kHz. 600ohm balanced or unbalanced, small size. £25.

300A HARMONIC WAVE ANALYSER Freq. 0-16kHz. Full spec & P.O.A.

TELEQUIPMENT 543C & D43H OSCILLOSCOPES £80.

KAHN SSB ADAPTOR MODEL RSSB-62-1B. Designed for receivers with 455-500kHz I.F. (eg Collins 51J; AR88D etc) at 100mV (max) input. Features: Electronic A.F.C., carrier frequency diversity to combat fading; 20 sec R.C. memory to maintain tuning during severe fading; individual carrier meters; nuvistors; low distortion product demodulator. Full spec & P.O.A.

TEST EQUIPMENT for direct line for all enquiries regarding test equipment only, phone 01-748 5498.

BENTLEY ACOUSTIC CORPORATION LTD.

7A GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX. Tel. 6743

ALL PRICES SHOWN INCLUDE V.A.T.

0B2 0-40	6AX4 0-75	6K80 0-45	12AV6 0-50	30P4MR	ARP4 0-60	EC52 1-00	EL81 0-60	N339 1-10	PY80 0-40	UY32 0-45	Transistor AF121 0-33	BYZ13 0-28	OA211 0-75
0Z4 0-47	6B8G 0-30	6L1 2-00	12AX7 0-33	30P12 1-00	ATP4 0-50	EC53 1-00	EL83 0-55	P61 0-50	PY81 0-35	UY85 0-35	AF124 0-28	BYZ16 1-38	OC19 1-38
1A3 0-45	6BA6 0-28	6L9GT 0-58	12B7 0-70	30P12 0-80	AZ1 0-25	EC54 1-00	EL84 0-31	PABCR8 0-38	PY82 0-35	UY10 1-00	IN14744 0-58	AF125 0-10	CG128 0-45
1A5GT 0-60	6BC8 0-60	6L7M 0-50	12A6 0-45	30P19	AZ31 0-60	EC56 1-00	EL85 0-44	PC86 0-60	PY83 0-38	UY12/14 1-00	IN4952 0-55	AF126 0-20	CG64H 0-22
1A7GT 0-65	6BE6 0-35	6L18 0-55	12B6 0-65	30P4 0-75	AZ41 0-65	EC58 0-70	EL86 0-38	PC88 0-60	PY88 0-40	UY16 1-00	IN4952 0-55	AF129 0-75	PSY11A 0-25
1BGT 0-65	6BG6 1-05	6L19 2-00	12BE6 0-60	30P11 0-85	BL53 2-00	EC59 0-45	EL89 0-50	PC95 0-60	PY90 0-75	UY16 1-00	IN4952 0-55	AF130 0-75	PSY41A 0-25
1C2 0-70	6BH6 0-60	6L21 0-58	12BH7 0-50	30P13 0-85	CL33 1-60	EC60 0-20	EL90 0-20	PC97 0-38	PY90 0-85	UY17 0-75	IN4952 0-55	AF131 0-75	PSY41A 0-25
1G6 1-00	6BJ6 0-55	6L20 0-75	12E1 3-00	30P14 1-10	CV6 0-53	EC62 1-50	EL92 0-45	PC99 0-45	PY90 0-85	UY18/20 1-00	IN4952 0-55	AF132 0-75	PSY41A 0-25
1H5GT 0-60	6BK7A 0-60	6N7GT 0-60	12F5T 0-33	30P15 0-90	CV63 0-75	EC63 0-85	EL93 0-45	PC99 0-45	PY90 0-85	UY19 2-50	IN4952 0-55	AF133 0-75	PSY41A 0-25
1L4 0-28	6BQ5 0-81	6PL12 0-34	12J7GT 0-60	35A3 0-65	CV988 0-25	EC64 1-00	EL94 0-45	PC99 0-45	PY90 0-85	UY20 0-65	IN4952 0-55	AF134 0-75	PSY41A 0-25
1L5 0-28	6BQ7A 0-55	6Q7G 0-50	12K5 1-00	35C5 0-75	CV10 0-50	EC65 1-00	EL95 0-45	PC99 0-45	PY90 0-85	UY21 0-65	IN4952 0-55	AF135 0-75	PSY41A 0-25
1L5S 0-60	6BR7 1-00	6Q7G 0-50	12K7 0-50	35D5 0-75	CV10 0-50	EC66 1-00	EL96 0-45	PC99 0-45	PY90 0-85	UY22 0-65	IN4952 0-55	AF136 0-75	PSY41A 0-25
1N5GT 0-65	6BR8 1-50	6Q7M 0-55	12K7GT 0-45	35LGT 0-75	D63 0-25	EC67 0-33	EL97 0-45	PC99 0-45	PY90 0-85	UY23 0-65	IN4952 0-55	AF137 0-75	PSY41A 0-25
1R3 0-45	6C1 0-45	6A3GT 0-45	12M7GT 0-55	35Z3 0-75	DAF96 0-50	EC68 0-55	EL98 0-45	PC99 0-45	PY90 0-85	UY24 0-65	IN4952 0-55	AF138 0-75	PSY41A 0-25
1R4 0-33	6R6 0-60	4R7M 0-75	12N7GT 0-55	35Z3 0-75	DD4 1-00	EC68 0-55	EL99 0-45	PC99 0-45	PY90 0-85	UY25 0-65	IN4952 0-55	AF139 0-75	PSY41A 0-25
1R5 0-30	6R6 0-60	4R7M 0-75	12N7GT 0-55	35Z3 0-75	DD4 1-00	EC68 0-55	EL99 0-45	PC99 0-45	PY90 0-85	UY26 0-65	IN4952 0-55	AF140 0-75	PSY41A 0-25
1U4 0-60	6BX6 0-28	88Q7GT 0-33	12N7GT 0-55	35Z3 0-75	DD4 1-00	EC68 0-55	EL99 0-45	PC99 0-45	PY90 0-85	UY27 0-65	IN4952 0-55	AF141 0-75	PSY41A 0-25
1U5 0-75	6BY7 0-34	88Q7GT 0-33	12N7GT 0-55	35Z3 0-75	DD4 1-00	EC68 0-55	EL99 0-45	PC99 0-45	PY90 0-85	UY28 0-65	IN4952 0-55	AF142 0-75	PSY41A 0-25
2D21 0-45	6BZ6 0-48	88H7 0-44	12N7GT 0-55	35Z3 0-75	DD4 1-00	EC68 0-55	EL99 0-45	PC99 0-45	PY90 0-85	UY29 0-65	IN4952 0-55	AF143 0-75	PSY41A 0-25
2R5 0-45	6C1 0-45	88Q7GT 0-33	12N7GT 0-55	35Z3 0-75	DD4 1-00	EC68 0-55	EL99 0-45	PC99 0-45	PY90 0-85	UY30 0-65	IN4952 0-55	AF144 0-75	PSY41A 0-25
2X2 0-60	6C5G 0-40	88Q7GT 0-33	12N7GT 0-55	35Z3 0-75	DD4 1-00	EC68 0-55	EL99 0-45	PC99 0-45	PY90 0-85	UY31 0-65	IN4952 0-55	AF145 0-75	PSY41A 0-25
3A4 0-50	6C6 0-40	88Q7GT 0-33	12N7GT 0-55	35Z3 0-75	DD4 1-00	EC68 0-55	EL99 0-45	PC99 0-45	PY90 0-85	UY32 0-65	IN4952 0-55	AF146 0-75	PSY41A 0-25
3B7 0-45	6C9 1-00	88Q7GT 0-33	12N7GT 0-55	35Z3 0-75	DD4 1-00	EC68 0-55	EL99 0-45	PC99 0-45	PY90 0-85	UY33 0-65	IN4952 0-55	AF147 0-75	PSY41A 0-25
3D6 0-40	6CB8A 0-40	88Q7GT 0-33	12N7GT 0-55	35Z3 0-75	DD4 1-00	EC68 0-55	EL99 0-45	PC99 0-45	PY90 0-85	UY34 0-65	IN4952 0-55	AF148 0-75	PSY41A 0-25
3Q4 0-60	6C12 0-33	88Q7GT 0-33	12N7GT 0-55	35Z3 0-75	DD4 1-00	EC68 0-55	EL99 0-45	PC99 0-45	PY90 0-85	UY35 0-65	IN4952 0-55	AF149 0-75	PSY41A 0-25
3Y3GT 0-55	6C17 0-20	88Q7GT 0-33	12N7GT 0-55	35Z3 0-75	DD4 1-00	EC68 0-55	EL99 0-45	PC99 0-45	PY90 0-85	UY36 0-65	IN4952 0-55	AF150 0-75	PSY41A 0-25
3R4 0-45	6C18 0-25	88Q7GT 0-33	12N7GT 0-55	35Z3 0-75	DD4 1-00	EC68 0-55	EL99 0-45	PC99 0-45	PY90 0-85	UY37 0-65	IN4952 0-55	AF151 0-75	PSY41A 0-25
3V4 0-40	6C19 0-25	88Q7GT 0-33	12N7GT 0-55	35Z3 0-75	DD4 1-00	EC68 0-55	EL99 0-45	PC99 0-45	PY90 0-85	UY38 0-65	IN4952 0-55	AF152 0-75	PSY41A 0-25
4C86 0-55	6C1A 0-85	88Q7GT 0-33	12N7GT 0-55	35Z3 0-75	DD4 1-00	EC68 0-55	EL99 0-45	PC99 0-45	PY90 0-85	UY39 0-65	IN4952 0-55	AF153 0-75	PSY41A 0-25
5C8A 0-55	6C1A 0-85	88Q7GT 0-33	12N7GT 0-55	35Z3 0-75	DD4 1-00	EC68 0-55	EL99 0-45	PC99 0-45	PY90 0-85	UY40 0-65	IN4952 0-55	AF154 0-75	PSY41A 0-25
5R4G 0-40	6C17 0-20	88Q7GT 0-33	12N7GT 0-55	35Z3 0-75	DD4 1-00	EC68 0-55	EL99 0-45	PC99 0-45	PY90 0-85	UY41 0-65	IN4952 0-55	AF155 0-75	PSY41A 0-25
5T4 0-40	6C15 0-75	7A6 1-00	19G6 4-00	19H2 7-50	19M7 1-50	EC182 0-55	EL20 0-25	EC20 0-45	EC21 0-45	EC22 0-45	EC23 0-45	EC24 0-45	EC25 0-45
5U4G 0-40	6C15 0-75	7A6 1-00	19G6 4-00	19H2 7-50	19M7 1-50	EC182 0-55	EL20 0-25	EC20 0-45	EC21 0-45	EC22 0-45	EC23 0-45	EC24 0-45	EC25 0-45
5V4G 0-40	6C15 0-75	7A6 1-00	19G6 4-00	19H2 7-50	19M7 1-50	EC182 0-55	EL20 0-25	EC20 0-45	EC21 0-45	EC22 0-45	EC23 0-45	EC24 0-45	EC25 0-45
5Z3 0-75	6D15A 0-75	7H7 0-75	20P2 1-10	20P1 0-75	20P2 1-10	20P1 0-75	20P2 1-10	20P1 0-75	20P2 1-10	20P1 0-75	20P2 1-10	20P1 0-75	20P2 1-10
5Z4G 0-45	6E6 0-75	7H7 0-75	20P2 1-10	20P1 0-75	20P2 1-10	20P1 0-75	20P2 1-10	20P1 0-75	20P2 1-10	20P1 0-75	20P2 1-10	20P1 0-75	20P2 1-10
5Z4GT 0-45	6E5 1-00	7Y4 0-75	20P3 0-80	20P4 0-80	20P5 0-80	20P6 0-80	20P7 0-80	20P8 0-80	20P9 0-80	20P10 0-80	20P11 0-80	20P12 0-80	20P13 0-80
6A0L2 0-80	6F1 0-75	7Z4 0-80	20P4 0-80	20P5 0-80	20P6 0-80	20P7 0-80	20P8 0-80	20P9 0-80	20P10 0-80	20P11 0-80	20P12 0-80	20P13 0-80	20P14 0-80
6A8G 1-25	6F6G 0-50	9B9W6 0-75	20P5 1-30	1821 1-00	1822 1-00	1823 1-00	1824 1-00	1825 1-00	1826 1-00	1827 1-00	1828 1-00	1829 1-00	1830 1-00
6A8T 0-40	6F12 0-37	9D7 0-65	28A6G 0-60	3033X 0-50	3034 0-50	3035 0-50	3036 0-50	3037 0-50	3038 0-50	3039 0-50	3040 0-50	3041 0-50	3042 0-50
6A8G 0-40	6F12 0-37	9D7 0-65	28A6G 0-60	3033X 0-50	3034 0-50	3035 0-50	3036 0-50	3037 0-50	3038 0-50	3039 0-50	3040 0-50	3041 0-50	3042 0-50
6A8G 0-40	6F12 0-37	9D7 0-65	28A6G 0-60	3033X 0-50	3034 0-50	3035 0-50	3036 0-50	3037 0-50	3038 0-50	3039 0-50	3040 0-50	3041 0-50	3042 0-50
6A8G 0-40	6F12 0-37	9D7 0-65	28A6G 0-60	3033X 0-50	3034 0-50	3035 0-50	3036 0-50	3037 0-50	3038 0-50	3039 0-50	3040 0-50	3041 0-50	3042 0-50
6A8G 0-40	6F12 0-37	9D7 0-65	28A6G 0-60	3033X 0-50	3034 0-50	3035 0-50	3036 0-50	3037 0-50	3038 0-50	3039 0-50	3040 0-50	3041 0-50	3042 0-50
6A8G 0-40	6F12 0-37	9D7 0-65	28A6G 0-60	3033X 0-50	3034 0-50	3035 0-50	3036 0-50	3037 0-50	3038 0-50	3039 0-50	3040 0-50	3041 0-50	3042 0-50
6A8G 0-40	6F12 0-37	9D7 0-65	28A6G 0-60	3033X 0-50	3034 0-50	3035 0-50	3036 0-50	3037 0-50	3038 0-50	3039 0-50	3040 0-50	3041 0-50	3042 0-50
6A8G 0-40	6F12 0-37	9D7 0-65	28A6G 0-60	3033X 0-50	3034 0-50	3035 0-50	3036 0-50	3037 0-50	3038 0-50	3039 0-50	3040 0-50	3041 0-50	3042 0-50
6A8G 0-40	6F12 0-37	9D7 0-65	28A6G 0-60	3033X 0-50	3034 0-50	3035 0-50	3036 0-50	3037 0-50	3038 0-50	3039 0-50	3040 0-50	3041 0-50	3042 0-50
6A8G 0-40	6F12 0-37	9D7 0-65	28A6G 0-60	3033X 0-50	3034 0-50	3035 0-50	3036 0-50	3037 0-50	3038 0-50	3039 0-50	3040 0-50	3041 0-50	3042 0-50
6A8G 0-40	6F12 0-37	9D7 0-65	28A6G 0-60	3033X 0-50	3034 0-50	3035 0-50	3036 0-50	3037 0-50	3038 0-50	3039 0-50	3040 0-50	3041 0-50	3042 0-50
6A8G 0-40	6F12 0-37	9D7 0-65	28A6G 0-60	3033X 0-50	3034 0-50	3035 0-50	3036 0-50	3037 0-50	3038 0-50	3039 0-50	3040 0-50	3041 0-50	3042 0-50
6A8G 0-40	6F12 0-37	9D7 0-65	28A6G 0-60	3033X 0-50	3034 0-50	3035 0-50	3036 0-50	3037 0-50	3038 0-50	3039 0-50	3040 0-50	3041 0-50	3042 0-50
6A8G 0-40	6F12 0-37	9D7 0-65	28A6G 0-60	3033X 0-50	3034 0-50	3035 0-50	3036 0-50	3037 0-50	3038 0-50	3039 0-50	3040 0-50	3041 0-50	3042 0-50
6A8G 0-40	6F12 0-37	9D7 0-65	28A6G 0-60	3033X 0-50	3034 0-50	3035 0-50	3036 0-50	3037 0-50	3038 0-50	3039 0-50	3040 0-50	3041 0-50	3042 0-50
6A8G 0-40	6F12 0-37	9D7 0-65	28A6G 0-60	3033X 0-50	3034 0-50	3035 0-50	3036 0-50	3037 0-50	3038 0-50	3039 0-50	3040 0-50	3041 0-50	3042 0-50
6A8G 0-40	6F12 0-37	9D7 0-65	28A6G 0-60	3033X 0-50	3034 0-50	3035 0-50	3036 0-50	3037 0-50	3038 0-50	3039 0-50	3040 0-50	3041 0-50	3042 0-50
6A8G 0-40	6F12 0-37	9D7 0-65	28A6G 0-60	3033X 0-50	3034 0-50	3035 0-50	3036 0-50	3037 0-50	3038 0-50	3039 0-50	3040 0-50	3041 0-50	3042 0-50
6A8G 0-40	6F12 0-37	9D7 0-65	28A6G 0-60	3033X 0-50	3034 0-50	3035 0-50	3036 0-50	3037 0-50	3038 0-50	3039 0-50	3040 0-50	3041 0-50	3042 0-50
6A8G 0-40	6F12 0-37	9D7 0-65	28A6G 0-60	3033X 0-50	3034 0-50	3035 0-50	3036 0-50	3037 0-50	3038 0-50	3039 0-50	3040 0-50	3041 0-50	3042 0-50
6A8G 0-40	6F12 0-37	9D7 0-65	28A6G 0-60	3033X 0-50	3034 0-50	3035 0-50	3036 0-50	3037 0-50	3038 0-50	3039 0-50	3040 0-50	3041 0-50	3042 0-50
6A8G 0-40	6F12 0-37	9D7											

Samson's

(ELECTRONICS) LTD.
 9 & 10 CHAPEL ST., LONDON, N.W.1
 01-723 7851 01-262 5125
 ADJACENT TO EDGWARE ROAD MET. LINE STATION

CURRENT RANGE OF NEW L.T. TRANSFORMERS FULLY SHROUDED TERMINAL BLOCK CONNECTIONS ALL PRIMARIES 220/240v

Type	Sec. Taps	Amps	Price	Postage
1A	25-33-40-50v	15	£14 00	75p
1B	25-33-40-50v	10	£12 00	75p
1C	25-33-40-50v	6	£8 50	60p
1D	25-33-40-50v	3	£7 50	60p
2A	4-16-24-32v	12	£10 00	75p
2B	4-16-24-32v	8	£8 00	60p
2C	4-16-24-32v	4	£4 95	45p
2D	4-16-24-32v	2	£3 50	40p
3A	24-30-36v	10	£9 00	60p
3B	24-30-36v	5	£7 50	50p
3C	24-30-36v	2	£3 50	40p
4A	12-20-24v	20	£12 00	75p
4B	12-20-24v	10	£7 50	60p
4C	12-20-24v	5	£4 95	45p
5A	3-12-18v	20	£10 00	60p
5B	3-12-18v	10	£5 95	60p
5C	3-12-18v	5	£4 50	40p
6A	48-56-60v	2	£4 50	40p
6B	48-56-60v	1	£3 50	40p
7A	6-12v	20	£7 90	60p
7B	6-12v	10	£4 50	40p
7C	6-12v	5	£3 50	40p
8A	17-32v	8	£8 00	60p
9A	12-24v	1	£2 50	30p
10A	9-15v	2	£2 50	30p
11A	8-0-8v	2	£2 50	30p

PLEASE ADD 8% V.A.T.

HEAVY DUTY UNSHROUDED TYPES 9 INCH FLYING LEADS ALL PRIMARIES 240v.

Type No.	Sec. Volt Tap	Amps	Price	Carr.
1	24-30-36	20	£14 95	£1 00
2	12-20-24	30	£14 95	£1 00
3	3-12-18	30	£14 95	£1 00
4	6-12	50	£14 95	£1 00

TRANSFORMERS FOR LINSLEY HOOD AMPLIFIERS
 Fully shrouded, terminal block connections. Pri. 220-240v. Screen tap. Sec. 30-25-0-25-30v. 2 amps. £4 75, carr. 40p. Heavy duty type 36-25-0-25-36v. 5 amps. £7 75, carr. 50p.

STEP DOWN 240/110v AUTO TRANSFORMERS
 3000 watts. Built into steel case with two American 2 pin grounded socket outlets. Carry handle, 6 ft. mains lead. £29 50, carr. £2. Without case and fittings £22 00, carr. £1 50.
Other Types Available. 80-1500 watts, fully shrouded, with American socket outlet and 6 ft. mains lead. Let us know your requirements. Lists available.

HOWELLS "C" CORE TRANSFORMERS
 Pri. 200-220-240v. screen. Sec. 70-0-70v. 10 amp. table top connections. size 7x7x7 inches. £15 00, carr. £2 00. Pri. 220-240v. Sec. 18-0-18v 12.5 amps conservatively rated. Table top connections £10 00, carr. £2 00.

PARMEKO ISOLATION STEP DOWN TRANSFORMERS
 Pri. 200-220-240v. Sec. 90-100-110-120v 7.5 amps conservatively rated. Size 8x8x8 inches. Enclosed type. Table top connections. £19 50, carr. £2 00.

PARMEKO ISOLATION 1-1 TRANSFORMERS
 Pri. 190-260v in 10v steps. Sec. 240v 10 amp conservatively rated. Size 12x10x8 inches. Enclosed type. Table top connections. £29 50, carr. £3 00.

DRAKE ISOLATION 240/110v TRANSFORMERS
 Pri. Tapped 10-0-200-220-240 Sec. 110v 400 watts. Shrouded. £6 50 carr. 75p.
 Pri. 200-220-240v. Sec. 110v 50 watts unshrouded. Table top connections £2 25 P.P. 40p.

3 PHASE TRANSFORMERS
 Pri. 380-440v. Star Sec. Tapped 6-1-6-7-7-3v. 28 amps delta. £12 50. Carr. £2 00. Pri. 105-110-115-120-200-220-230-240-250 Star Sec. 12v. 58 amps Delta. C core. £25 00. Carr. £3 00. 3 Phase Isolation Transformer Pri. 415v. Sec. 415v. 2kVA £25 00. Carr. £3 00. Pri. 415 ± 3% Star Sec. 13-1v 150a. Star. £35 00. Carr. £5 00.

HEAVY DUTY HIGH INSULATION TRANSFORMER
 Pri. 230-240v. Sec. 10v 160 amp 50KV WKG. £25 00. Carr. £5 00.

ADVANCED COMPONENTS CONSTANT VOLTAGE TRANSFORMERS
 Pri. 240v Sec. 28v 10 amps. £7 50. Carr. £2 00.

GRESHAM EHT TRANSFORMERS
 Suitable for scope replacements.
 Pri. 240v. Sec. 2300v 10 M/A. 300-0-300v 50 M/A. 6.3v 4A. 6.3v 1.5A. Table top connections. Size 5x3 1/2 x 3 1/2 ins. £3 75. P.P. 45p.

GARDNERS C CORE HT TRANSFORMERS
 Pri. 110-220-230v. Sec. 250-0-250v. 60 M/A 2.8-0-2.8v 28 amps. 24v 3 amps. 6.3v 3 amps. 5v 2 amps. £4 75. P.P. 65p.

HEAVY DUTY ISOLATION TRANSFORMER
PARMEKO Admiralty Pattern. Pri. 230v. Sec. 230v. C.T. 20 amps. Very conservatively rated. Test to earth 2000 v. Size 17x14x16ins. Weight 320 lbs. £50 plus carriage.

RICH AND BUNDY. Pri. 220-230-240-250v. Sec. 265-270-275v. 1400 watts. Conservatively rated. Size 8x8x7 ins. Terminal block connections. £15 00, carr. £1 00.

GARDNERS C CORE L.T. TRANSFORMERS
 Table top connections. Primaries 200-220-240v. No. 1 Size 2 65-0-2 65v 42 amps. £4 50, P.P. 70p. No. 2 2.5v 10 amps and 2.5v 5 amps twice. £3 50, P.P. 60p. No. 3 24v 3 amps. £3 00, P.P. 40p. No. 4 25-0-25v 15A M/A and 7v 1.35 amps. £4 75, P.P. 25p. No. 5 36v 350 M/A £1 00, P.P. 25p. No. 6 73v tapped at 68v 0.6 amp and 6v 1 amp. £3 00, P.P. 35p. No. 7 4.2v 1 amp. 75p, P.P. 25p.

GRESHAM MULTI TAPPED L.T. TRANSFORMERS
 Pri. 110-220-240v. Sec. 21-22-23-27-28-30v 10a and 23-24-26v 2.5a. Two 6 and 15-16-18v 5A twice and 25-0-25v 50 M/A three times. C. core type. Table top connections £10 00, carr. £1 00.

PARMEKO L.T. TRANSFORMERS
 Open types. Pri. 110-220-240v. Sec. 30v 5.5 amps and 12v 2.2 amps. Table top connections. £4 95, P.P. 75p. Pri. 240v. Sec. 25v 10 amps and 12v 0.1 amp. Table top connections. £5 50, P.P. 75p. Potted types. Pri. 115-230v. Sec. 24-30-32v 2.5 amps. £2 75, P.P. 35p. Pri. 220-240v. Sec. 50v 0.4 amp. £1 50, P.P. 35p. Pri. 115-230v. Sec. tapped 40-45 50v 5 amps. £8 50, Carr. 75p.

G.E.C. Open frame. Terminal Block Connections Primaries 220-240v. No. 1 Sec. Tapped 51-61 65-67-69v. 10a. £8 00, carr. £1 00. No. 2 Sec. 58 63-69-74v 3a. and 6v 3a. £3 75, P.P. 50p.

GARDNERS L.T. TRANSFORMERS
 Pri. 110-220-240v. Sec. 30v 1 amp and 70v 1 amp. Enclosed type. £4 00, P.P. 75p. Pri. 110-220-240v. Sec. 12v 6 amps and 15.6v 1.5 amps. £3 75, P.P. 75p. Pri. 220-240v. Sec. 63v 1.5 amps. 20-22-24v 0.8 amp and 6.3v 1 amp. £2 50, P.P. 75p. Pri. 220-240v. Sec. 15v 2.5 amps and 13v 6 amps. £3 50, P.P. 75p. All types open construction table top connections.

H.T. TRANSFORMERS BY FAMOUS MAKERS
 No. 1. Pri. 110-210-230-250v. Sec. 230v 200 M/A and 6.3v 7A. potted type £3 00, P.P. 50p.
 No. 2. Pri. 110v-220-240v. Sec. 250v 80 M/A. 15v 1.2A 6.3v 4.5A. Open type £2 00, P.P. 35p.
 No. 3. Pri. 220-240v. Sec. 250-0-250v 75 M/A 6.3v 3A £1 75, P.P. 35p.
 No. 4. Pri. 200-220-240v. Sec. 400-375-350-0-350-375-400v 150 M/A 6.4v 7A twice 6.4v 3A. 6.4v 2A 6.4v 1A 6.4v 0.5A potted type £5 00, carr. 75p.
 No. 5. Pri. 110-220-240v. Sec. 70v 1A and 30v 1A potted type £3 75, P.P. 75p.
 No. 6. Pri. 220-240v. Sec. 187.5v 60 M/A and 500 31 M/A potted type £4 75, P.P. 75p.
 No. 7. Pri. 220-240v. Sec. 630-0-630v 105 M/A. 5v 4A 5v 2A £4 50, P.P. 75p.
 No. 8. Pri. 220-240v. Sec. 140v 195 M/A 6.3v CT 1.25A. 50v potted type 1A £3 50, P.P. 50p.
 No. 9. Pri. 220-240v. Sec. 385v 175 M/A and 218v 175 M/A potted type £3 50, P.P. 50p.
 No. 10. Pri. 220-240v. Sec. 480-0-480v 150 M/A 6.3v 2 BA. 6.3v 1.2A twice open type £4 50, P.P. 75p.

H.T. SMOOTHING CHOKES
GARDNER 'C' core types. 10H 250 M/A £2 00, post. 40p. 20H 180 M/A £2 00, post. 40p. 12H 100 M/A 85p, post. 25p. 50H 25 M/A 85p, post. 25p. **AR-MEKO** Potted types. 10H 180 M/A £2 00, post. 40p. 5H 250 M/A £2 50, post. 50p. 10H 300 M/A £2 50, post. 50p. 5H 100 M/A 75p, post. 25p. 15H 75 M/A 75p, post. 25p. 50H 25 M/A 75p, 25p.

L.T. SMOOTHING CHOKES
 C core types 140 M/H 5A £3 00, P.P. 75p. 10 M/H 25A £8 75, carr. £1 00. 15 M/H 3.8A £1 75, P.P. 35p. Potted types 4.6 M/H 11A £3 00, P.P. 50p. 100 M/H 2A £2 50, P.P. 50p. 130 M/H 1.5A £1 00, P.P. 25p. Open type 150 M/H 3A £3 00, P.P. 50p. 50 M/H 2A £1 50, P.P. 35p. 20 M/H 1A £1 00, P.P. 25p. 4.8 M/H 10A £2 50, P.P. 40p. Swinging types. C core. 7.5 M/H 6A-7.5 M/H 0.5A £3 75, P.P. 50p. 10 M/H 4A-7 M/H 0.5A open type £2 50, P.P. 25p. 50 M/H 5A-100 M/H 0.5A C core £2 25, P.P. 35p.

WODEN LT TRANSFORMERS
 Pri. 200-220-240v. SCR. Sec. 18-0-18v 12.5 amps 'C' core. Table top connections. Conservatively rated. Fraction of maker's price. £8 50, carr. £1 50.

SPECIAL OFFER OF RELAYS
 Omron relays: MK2P plug-in type. 230v AC 2 CO contacts. 75p. MK3P plug-in type. 12v DC 3 CO contacts. 75p. MK2P plug-in type. 12v DC 2 CO contacts. 65p. MK2P plug-in type. 24v DC 2 CO contacts. 65p. MK3 12v DC 3 CO contacts. MK3 24v AC 3 CO contacts. Single hole fixing. 60p. Postage: 1-3 relays. 20p; 4-6, 30p.
 Keyswitch relays: KMK3 230v AC 3 CO contacts. S hole fixing. 60p. KMK1 230v AC 1 CO contact. S hole fixing. 45p. KMK3 12v DC 3 CO contacts. S hole fixing. 60p. Diamond H relay 230v AC 3 CO contacts. S hole fixing. 60p. Postage: 1-3 relays. 20p; 4-6, 30p.

ROBINSON 240v. AC RELAYS. Two 5 amp change over contacts, single hole fixing. Size 2 1/2 x 1 1/2 x 1 1/2 ins. 60p. p.p. 10p.

RELAY CONTROL CO. American Miniature relays 6v. DC. 1 CO contact. Size 1 1/2 x 1 1/2 x 1 1/2 ins. 35p, post. 5p.

MINIATURE RELAYS. ITT, PLESSEY, VARLEY TYPES
 2802 125v DC 4 CO. 60p. 4305 125v DC 2 CO. 50p. 12502 4 CO 24-30v DC. 50p. 25002 35-45v DC. 50p. 50002 40-60v DC 2 CO. 50p. Postage 5p each.

G.P.O. RELAYS
 3000 type. 100Ω 1.25 amp. make contact 60p. 2004-1306 1 normal CO 40p. 753M 1B. 1 CO normal contacts 40p. post on all relays 10p.
 Diamond H relays type BR115AIT-3C. 150Ω 24v DC. Sealed type. 75p, P.P. 10p.

Dorman Loadmaster SP circuit breakers type M3. AC 240-440v 20 amps. Overall size 3x2x1 ins. £1 25, P.P. 20p.

ITT LEVER SWITCHES
 Type 601 A.A. 12-42 4 CO contacts. 2802 125v DC 4 CO. 60p. White lever gold flash contacts. 60p. Three for £1 50, post paid.

PLESSEY MINIATURE MICRO SWITCHES
 Type LIC 7134. One CO one break. Gold flash contacts. Size 1 1/2 x 1 1/2 x 1 1/2 ins. Three for 50p, post paid.

SANGAMO SYNCHRONOUS A.C. 240v MOTOR TYPE 7
 4 rev. per hour. Size 1 1/2 plus 1/2 spindle. 1 1/2 inch dia. £1 25, P.P. 25p.

GENTS ALARM BELLS
 6 volt DC 6 inch dia. Gong. Overall size 4 1/2 x 6 x 6 inches. £3 50, P.P. 50p.

MOVING COIL DC METERS
 0-8v DC. 3 in. square, 2 1/2 in. panel hole. £1 25, P.P. 25p.
 0-100 M/A DC. 3 1/2 in. round. 2 1/2 in. panel hole. £1 50, P.P. 25p.
 0-500 U.A. DC. 2 1/2 in. square. 2 in. panel hole. £1 75, P.P. 25p.

ACI AC 240V CONTACTORS
 Type LS-01-44. 4 make, 4 break contacts. 20 amps. £1 50, P.P. 20p. Type LS6-L11-02. 2 make, 2 break contacts. 20 amps. £3 50, P.P. 20p. Type LS6-L11-03 make, 1 break contacts. £1 25, P.P. 20p.

BENSON SOLENOIDS
 AC 240v 25% duty. Approx 2 ins. 1/2 in. pull. Size 2 1/2 x 1 1/2 x 1 1/2 ins. Res. 350Ω 75p P.P. 10p.

OIL-FILLED BLOCK CAPACITORS

MFD	DCV WKG	PRICE
8	2500	£3 00
8	800	75p
8	350	60p
8	300	40p
6	750	60p
6	600	50p
4	2000	£1 00
4	1000	60p
4	600	40p
4	350	30p
1	600	20p
1	200	10p


P.P. Add 5p each 1-4 MFD. 10p each 6-8 MFD. 25p each 8 MFD 2500v.
 Plessey 2+2+2 MFD 1500v. WKG 70°C. 75p, P.P. 10p.
 TCC block electrolytic capacitors 1000 MFD 100v DC WKG 50p, P.P. 15p.

MOTOR START CAPACITORS TUBULAR TYPES
 4 MFD 250v AC. 2.6 MFD 500v DC. 2.5 MFD 350v-AC. 2.2 MFD 250v AC. All at 50p, P.P. 10p. Eire Miniature 2.2 MFD 400v Size 1 1/2 x 1 1/2 x 1 1/2 inches. 25p post paid. TCC 8 MFD 800v DC WKG electrolytics 75p, P.P. 15p.

Dubilier 0.05 MFD 10,000v DC WKG Pri. 20v DEG C. £3 00, P.P. 50p. 10 MFD 750v DC WKG. 85p, P.P. 20p. AEI 12 MFD 250v WKG AC. 60p, P.P. 15p. TCC plastapack 2 MFD 350v DC WKG. 50p, P.P. 15p.

VAT PLEASE ADD 8% TO ALL ORDERS INC. CARR.

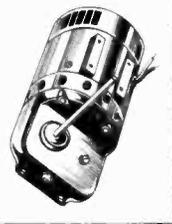AC GEARED MOTORS
 By famous makers 240v induction type, cont rating, 4.2 RPM £3 75 carr. 75p. Overall size 7 ins. Dia 3 1/2 ins. Length of spindle 2 1/2 ins.



AIR CONTROL LTD AIR BLOWERS 50-60v D.C. HP. 140th RPM 6000 cont rating. Size of motor 4x2x2 1/2 ins. Cowling 5 ins. dia. Outlet 1 1/2 x 1 1/2 ins. £2 50 carr. 45p.

UNIMAX SEQUENTIAL MICRO SWITCHES
 2 pole CO 15A contacts. 2nd pole actuates after 1st pole. Leaf roller action 60p, post 5p.



REDCLIFF C CORE HEAVY DUTY L.T. TRANSFORMERS
 Pri. 200-220-240v. Sec. 25v 30 amps twice. £15 00, carr. £2 00.

HEAVY DUTY HT CHOKES
 Parmeko potted type. 9 H 500 M/A 5 KV WKG. £8 50, carr. £2 00. Gardners enclosed type. 1 H 1 amp. £3 50, carr. £1 00. Gardner C core type. 10 H 350 M/A £3 00, carr. 75p.

CONSTANT VOLTAGE TRANSFORMERS
 Input 240v + 20% - 10% output 240v +/- or - 0.5% 30 watts enclosed in metal case. 5 1/2 x 4 x 4 ins. £2 00, P.P. 50p.

LEMARCK L.T. TRANSFORMERS
 Pri. 240v. Sec. 40v. 6a. 5.0-5v 2a. 5.0-5v 1a. Open frame design. £4 50, carr. 75p. Pri. 240v. 16-0-16v. 2.5a. 24v. 630 m/a twice. 24v. 65 m/a and 115v. 2a. auto tap on primary. Open frame table top connections £3 50, carr. 50p. Pri. 240v. Sec. 20-0-20 1/2a. 5-0-5 2a. £1 75, carr. 35p. All above transformers have a screen winding. Pri. 220-240v. Sec. 56v. C.T. 10a. Shrouded terminal block connections. £8 50, carr. 75p.

PARMEKO High Voltage Transformers. Pri. 220-250v. in 10v. steps. Sec. 1320-0-1320v. 250 mVA. 1.01 kv pk wkg. Open frame type. Terminal block connections. New in maker's carton. £12 00, carr. £1 00.

PARMEKO HT TRANSFORMERS POTTED TYPE
 Pri. 200-220-240v. SCR. Sec. 250-0-250v 240 M/A 6.3v 10A. £4 50, P.P. 75p. Pri. 115-230v SCR. Sec. 350-0-350v 200 M/A. 6.3v 5A. 5v 3A. Potted type. £4 50, P.P. 75p.

GRESHAM. Type 1 16.3v. 1a. twice 10v. 1a. twice. 22.5-25-28v. 5a. 26v. 2.5a. 23v. 1a. 6.3v. 2a. 145-0-145v. 200 mVA 'C' core £4 95, carr. 75p. Type 2 38v. 4a. 20v. 4a. 40v. 7a. 29v. 2a. 30v. 2.6a. 26v. 3.8a. 51v. 200 mVA. All separate windings. 'C' core £8 50, carr. £1. Type 3 25v. 2a. twice. 15v. 4a. twice. 25v. 5a. 31v. 7a., all separate windings. open frame table top connection. £8 50, carr. £1 00.

AMOS "C" CORE CHOKES
 10 M/H 25 amps., £8 75, carr. £1 00.

AUTO TRANSFORMERS
 Partridge Tapped. 0-220-230-240-250v 500 watts unshrouded table top connections £2 50, carr. 40p. Lemark tapped 0-240 115v 500 watts unshrouded table top connections £5 00, carr. 60p. 300 watts £3 50, carr. 50p.

12 volt 2 amp TRANSFORMER
 enclosed in metal case. Size 5x4 1/2 x 3 ins. with fitted input and output fuses. On/off switch. Output sockets and 4 ft. 240v. mains lead. £2 75 p.p. 35p.

DRAKE L.T. TRANSFORMERS
 Pri. 240v. E.S. Sec. 26v. 10A and 12v. 0.1A. open frame. table top connections. £5 50, carr. 50p. Pri. 200-220-240v. Sec. 1. 37v. 6A. Sec. 2. 37v. 2A. 21v. 11A. open frame table top connections. £9 50, carr. £1.

SERVICE TRADING CO

VARIABLE VOLTAGE TRANSFORMERS

Carriage extra
INPUT 230 v. A.C. 50/60
OUTPUT VARIABLE 0/260 v. A.C.
 BRAND NEW. All types.
200W (1 Amp) £9.00
0.5 KVA (Max. 2 1/2 Amp) £10.00
1 KVA (Max. 5 Amp) £14.70
2 KVA (Max. 10 Amp) £28.10
3 KVA (Max. 15 Amp) £31.25
4 KVA (Max. 20 Amp) £72.50
 (Max. 37.5 Amp) £102.50
1 Amp OPEN TYPE
 (Panel Mounting) £9.00

300 VA ISOLATING TRANSFORMER

115/230-230/230 volts. Screened. Primary two separate 0-115 volts for 115 or 230 volts. Secondary two 115 volts at 150 VA each for 115 or 230 volts output. Can be used in series or parallel connections. Fully tropicalised. Length 13.5 cm. Width 11 cm. Height 13.5 cm. Weight 15 lb. SPECIAL OFFER PRICE Only **£5.00**. Carr. 80p.

VENNER TIME SWITCH TYPE MSQP

200/250 Volt 2-ON/2-OFF every 24 hours at any manually pre-set time. 20 amp contacts. Fitted die-cast case. Tested and in good condition **£4.75** Post 25p.

A.C. MAINS TIMER UNIT

Based on an electric clock, with 25 amp. single-pole switch, which can be preset for any period up to 12 hrs. ahead to switch on for any length of time, from 10 mins to 6 hrs. then switch off. An additional 60 min. audible timer is also incorporated. Ideal for Tape Recorders, Lights, Electric Blankets, etc. Attractive satin copper finish. Size 135 mm X 130 mm X 60 mm. Price **£2.00**. Post 20p. (Total inc. VAT & Post **£2.38**)

UNISELECTOR SWITCHES - NEW

4 BANK 25 WAY FULL WIPER 25 ohm coil, 24v. D.C. operation £6.90. Post 30p.
8 BANK 25 WAY FULL WIPER 25 ohm coil, 24 v. D.C. £7.90. Post 30p.
8 BANK 25 WAY FULL WIPER 24 v. D.C. operation £9.50. Post 40p.

MINIATURE UNISELECTOR SWITCH

2 Bank, 12 position, 24 volt D.C. operation, full wiper with ancillary contacts. NEW Price **£2.50** Post 20p.
 As above but with 5 Bank, 12 position. Price **£3.50** Post 20p.

PROGRAMME TIMERS 230/240 Volt A.C. 15 Rpm Motors. Each cam operates a c/o micro switch. Ideal for lighting effects, animated displays etc. Ex equipment tested. 2 cam model **£2.00** post 30p. 4 cam model **£2.50** post 30p.

VERY SPECIAL OFFER

Miniature Roller Micro Switch. 5 amp c/o contacts. NEW. Price 10 for **£1.50**. Post 10p. (Min. order 10.)
 As above less roller/lever 20 for **£2.00**. Post 10p. (Min. order 20.)
 Ditto. Press to make. 20 for **£1.50** Post 10p.
 Ditto. Press to break. 20 for **£1.50** Post 10p.

'HONEYWELL' PUSH BUTTON, PANEL MOUNTING MICRO SWITCH ASSEMBLY

Each bank comprises of a change-over rated at 10 amps 240 volt A.C. Black knob 1 in. dia. Filing hole 1/2 in. Prices: 1-bank 30p., 2-bank 40p., 3-bank 50p. (Illustrated) inc. P. & P. Special quotes for quantities.

240 V.A.C. SOLENOID OPERATED FLUID VALVE

Rated 1 p.s.i. will handle up to 7 p.s.i. Forged brass body, stainless steel core and spring. 1/2 in. b.s.p. inlet/outlet. Precision made. British mfg. PRICE: **£2.00**. Post 25p. NEW original packing.

COIN MECHANISM (Ex-London Transport)

Unit containing selector mechanism for 1p, 2p & 5p coins. Micro switches, relays, solenoid-operated hopper. 24 volt D.C. Precision built to high standard. Incredible VALUE at only **£2.50** Post 60p.

230-250 VOLT A.C. SOLENOID

Similar in appearance to illustration. Approximately 1 1/2 lb. pull. Size of feet 1 1/2" X 1 1/2". Price **£1.00** Post 15p.

24 VOLT DC SOLENOIDS

UNIT containing: 1 heavy duty solenoid approx. 25 lb. pull at 1 in. travel, 2 solenoids of approx. 1 lb. pull at 1/2 in. travel, 6 solenoids of approx. 4 oz. pull at 1/4 in. travel. Plus 1 24V D.C. 1 heavy duty 1 make relay. Price: **£2.50**. Post 60p. **ABSOLUTE BARGAIN.**

High Visibility Panel Mounting LEDs

25 inch mounting, 16 inch lens. Typical parameters 2 volt 20 m.a. all types. Supplied complete with snap in mountings and data. Red 4 for **£1.00**, Green 3 for **£1.00**, Yellow 3 for **£1.00**. Post 10p. (Min. order 10.00.)

LED READOUTS

7 series 1/8 DP 3/4 high characters. 14-pin D.C.L. Available in red or green. **£1.65**, post 10p; 4 for **£6.00** post paid.

POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.
 25 WATT 10, 25, 100, 150, 500, 1k ohm, £1.15 Post 10p.
 50 WATT 1, 5, 10, 25, 50, 100, 500 ohm £1.60 Post 10p.
 100 WATT 1/10/25/50/100/250/500/1k/1.5k/2.5k/5k ohm £2.35 Post 15p.
Black Silver Skirted knob calibrated in Nos. 1-9. 1 1/2 in. dia brass bush. Ideal for above Rheostats, 22p ea.

STROBE! STROBE! STROBE!

* FOUR EASY TO BUILD KITS USING XENON WHITE LIGHT FLASH TUBES, SOLID STATE TIMING + TRIGGERING CIRCUITS, PROVISION FOR EXTERNAL TRIGGERING. 230-250v. A.C. OPERATION.
 * EXPERIMENTERS "ECONOMY" KIT Adjustable 1 to 30 Flash per sec. All electronic components including Xenon Tube + Instructions **£6.30**. Post 30p.
 * INDUSTRIAL KIT Ideally suitable for schools, laboratories etc. Roller tin printed circuit. Adjustable 1-80 i.p.s., approx. 1/2 output of Hy-Light. Price **£14.00**. Post 50p.
 * HY-LITE STROBE MK IV Designed for use in large rooms, halls and utilizes a silica tube, printed circuit. Speed adjustable 1-20 i.p.s. Light output greater than many (so called 4 Joule) strobes. Price **£14.00**. Post 50p.
 * 'SUPER' HY-LIGHT KIT Approx. 4 times the light output of our well proven Hy-Light strobe.
 * Variable speed from 1-13 flash per sec.
 * Reactor control circuit producing an intense white light. **ONLY £22.00**. Post 75p.
 * ATTRACTIVE, ROBUST, FULLY VENTILATED METAL CASE for the Super Hy-Light Kit including reflector. **£8.00**. Post 60p.
 * FOR HY-LYCHT STROBE incl. reflector, **£5.75**. Post 25p.

COLOUR WHEEL PROJECTOR

Complete with oil filled colour wheel. 100 watt lamp. 200/240V A.C. Features extremely efficient optical system. **£20.50**. Post 50p.

1 R.P.M. MOTOR AND COLOUR WHEEL

200/240 volt A.C. 1 r.p.m. motor, and wheel **£5.60**. Post 40p. (Motor not available separately.)

6 INCH COLOUR WHEEL ONLY. Price £4.50. Post 30p.

BIG BLACK LIGHT
 400 Watt. Mercury vapour ultra violet lamp. Extremely compact and powerful source of u.v. Innumerable industrial applications also ideal for stage, display discos etc. P.F. ballast is essential with these bulbs. Price of matched ballast and bulb **£16.00**. Post £1. Spare bulb **£7.00**. Post 40p.

BLACK LIGHT FLUORESCENT U.V. TUBES
 4ft. 40 watt. Price **£5.50**. (Callers only). 2ft. 20 watt **£4.25**. Post 25p. (For use in stan bin fittings.) MINI 12in. 8 watt **£1.60**. Post 15p. 9in. 6 watt **£1.30**. Post 15p. Complete ballast unit and holders for either 9" or 12" tube. **£1.70**. Post 25p. (9in. x 12in. measures approx.)

U.D.1. SINGLE CHANNEL. 750 watt MANUAL/AUTO DIMMER

750W Solid State Fader, with three functions. Manual cycling up and down. Auto fade-up. Automatic cycling up and down. Functions selected with 'three position' rocker switch. Two ranges of cycling for 'Flashing' or 'Slow blending'. Ready built module 6" X 3" glass fibre board incorporating 10 amp TRIAC. Two or more modules for top quality colour blending and flashing effects. PRICE **£15.00** Post 30p.

GENERAL ELECTRIC POWERGLAS TRIACS

10 amp. Glass passivated plastic Triac. Latest device from U.S.A. Long term reliability. Type SC 146E 10 amp. 600PIV. **£1.00**. Post 5p. (Inclusive of data and application sheet) suitable Diac 18p.

INSULATION TESTERS (NEW)

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L. 8 in., W. 4 in., H. 6 in., weight 6 lb.
 500 VOLTS, 500 megohms **£28.00**. Post 60p.
 1,000 VOLTS, 1,000 megohms **£34.00**. Post 60p.

All prices are subject to **8% VAT.** (8p in the £)

VAT

To all orders add 8% VAT to total value of goods including carriage/packaging.

INSULATED TERMINALS

Available in black, red, white, yellow, blue and green. New 12p

RELAYS				SIEMENS PLESSEY, etc. MINIATURE RELAYS			
1	2	3	4	1	2	3	4
58	5-9	6 c/o	80p	700	16-24	4 c/o	80p*
150	4-9	2 c/o	70p*	2500	36-45	6 M	60p*
185	8-12	6 M	60p	2500	31-43	2 c/o HD	60p*
308	9-14	4 c/o	75p*	9000	40-70	2 c/o	60p*
410	12-20	4 c/o	80p*	15k	85-110	6 M	60p*
700	16-24	4M2B	60p*				

(1) Coil ohms: (2) Working d.c. volts; (3) Contacts; (4) Price HD=Heavy Duty. All Post Paid. (*Including Base)

OPEN TYPE RELAYS

6 VOLT D.C. 1 make con. 35p. Post 10p.
9 VOLT D.C. RELAY
 3 c/o 5 amp contacts. 70 ohm coil **75p.** Post 10p.
12 VOLT D.C. RELAY
 3 c/o 5 amp contacts 120 ohm coil **75p.** Post 10p.
24 VOLT D.C. 3 c/o 600 ohm coil **75p.** Post 10p.
 2 HD c/o 700 ohm coil **75p.** Post 10p.
 4 c/o 300 ohm coil **85p.** Post 10p.
100 VOLT A.C.
 2 c/o sealed type, octal base **75p.** Post 10p.

PLASTIC COVERED RELAYS

24 VOLT D.C. 3 h.d. c/o contacts **95p.** Post 10p.
24 VOLT A.C. Mfg. by I.T. 2 h.d. c/o contacts. **55p.** Post 10p. 3 h.d. c/o **65p.** Post 10p.
240 VOLT A.C. RELAY IIT
 240V. A.C. heavy duty c/o contacts. Octal plug in base. Price **75p.** Post 10p.
220/240 VOLT AC RELAY
 3 c/o 5 amp contact. Sealed, incl 11-pin base. **£1.25**. Post 10p.
ARROW 230/240V AC 2 c/o 15 amp contacts. Amp connectors. **£1.00** Post 10p.
110 VOLT A.C. 2 c/o. 20 amp. **£1.25** Post 10p.
CLARE-ELLIOTT TYPE RP 7641 G8
 Miniature relay. 675 ohm coil. 24 volt D.C. 2 c/o. 70p. Post Paid.

MANY OTHERS FROM STOCK. PHONE FOR DETAILS.

BLOWER UNIT
 200-240 Volt A.C. BLOWER UNIT
 Precision German built. Dynamically balanced, quiet, continuously rated, reversible motor. Consumption 60mA. Size 120mm dia. x 60mm deep. Price **£3.00**. Post 30p.

PRECISION CENTRIFUGAL BLOWER
 Mfg. Airflow Developments Ltd. Heavy Duty, continuously rated, smooth running, 230/240v A.C. motor. Size: 16 X 14 cm. (case only), OAL 15 cm. Aperture 6 X 6 cm. **£6.50**. Post 50p.

230/240 VOLT A.C. EXTRACTOR FAN KIT
 Comprising of impeller, continuously rated motor, motor housing and fixings as illustrated. Price **£1.75**. Post 25p. (Total inc. VAT & Post **£2.16**)

230V FAN ASSEMBLY
 Continuously rated. Removable aluminium blades. Price **£1.00**. Post 20p.

230/240V SYNCHRONOUS GEARED MOTOR

BODINE TYPE N.C.I. GEARED MOTOR
 (Type 1) 71 r.p.m. torque 10 lb. in. Reversible 1/70th h.p. cycle -38 amp.
 (Type 2) 28 r.p.m. torque 20 lb. in. Reversible 1/30th h.p. 50 cycle 28 amp. The above two precision made U.S.A. motors are offered in 'as new' condition. Input voltage of motor 115v A.C. Supplied complete with transformer for 230/240v A.C. input. Price, either type **£6.25** Post 50p. or less transformer **£3.75** Post 40p.
 These motors are ideal for rotating aerials, drawing curtains, display stands, vending machines, etc. etc.

'FRACMO' 240VOLT A.C. 50 cycle SINGLE PHASE GEARED MOTOR
 33 r.p.m. 30 lb. ins. Reversible, fitted with mounting feet. Brand New. **£14.00** Post 60p. (Total price incl. VAT £15.77)

600 WATT DIMMER SWITCH
 Easily fitted. Fully guaranteed by makers. Will control up to 600 watts of all lighting except fluorescent at mains voltage. Complete with simple instructions. **£2.75**. Post 25p.

2000 WATT POWER CONTROL
 For Power tools, Heating, Lighting etc. incorporating 13 amp. outlet and mains lead. **£8.00** Post 27p.

'GENTS' 6" ALARM BELL
 200/250 volt AC/DC. Brand New. Price: **£5.00** Post 60p. (Illustrated)

'STC' 6" RED ALARM BELL
 Brand New. Price: **£4.00** Post 50p. 24/48V DC.

METERS NEW! 2 1/2 in. FLUSH ROUND
 available as D.C. Amps 1, 5, 10, 15 or A.C. Amps 1, 5, 10, 15, 20. Both types **£2.00**. Post 15p.
VOLTMETER 0-300V. A.C. £2.00. Post 15p.

ALL MAIL ORDERS, ALSO CALLERS AT:
 57 BRIDGMAN ROAD, CHISWICK,
 LONDON, W4 5BB. Phone: 01-995 1560
 Closed Saturdays.

SERVICE TRADING CO.
 SHOWROOMS NOW OPEN
 AMPLE PARKING

PERSONAL CALLERS ONLY
 9 LITTLE NEWPORT STREET,
 LONDON, WC2H 7JJ.
 Tel.: 01-437 0576

The big three from Wireless World

WIRELESS WORLD ANNUAL 1975


The first ever Wireless World Annual contains 140 pages of features covering all aspects of electronics and communications, including new and established techniques both practical and theoretical. Content includes constructional projects for a general purpose audio oscillator and a small boat echo sounder. There is a reference section packed with useful information.

HIGH FIDELITY DESIGNS

In response to demand for reprints of Wireless World constructional projects, we have collected fifteen of the most popular designs in one book. It covers tape, disc, radio, amplifiers, speakers and headphones. Where necessary, specifications have been updated to incorporate new components which have become available.

HI-FI YEAR BOOK 1975

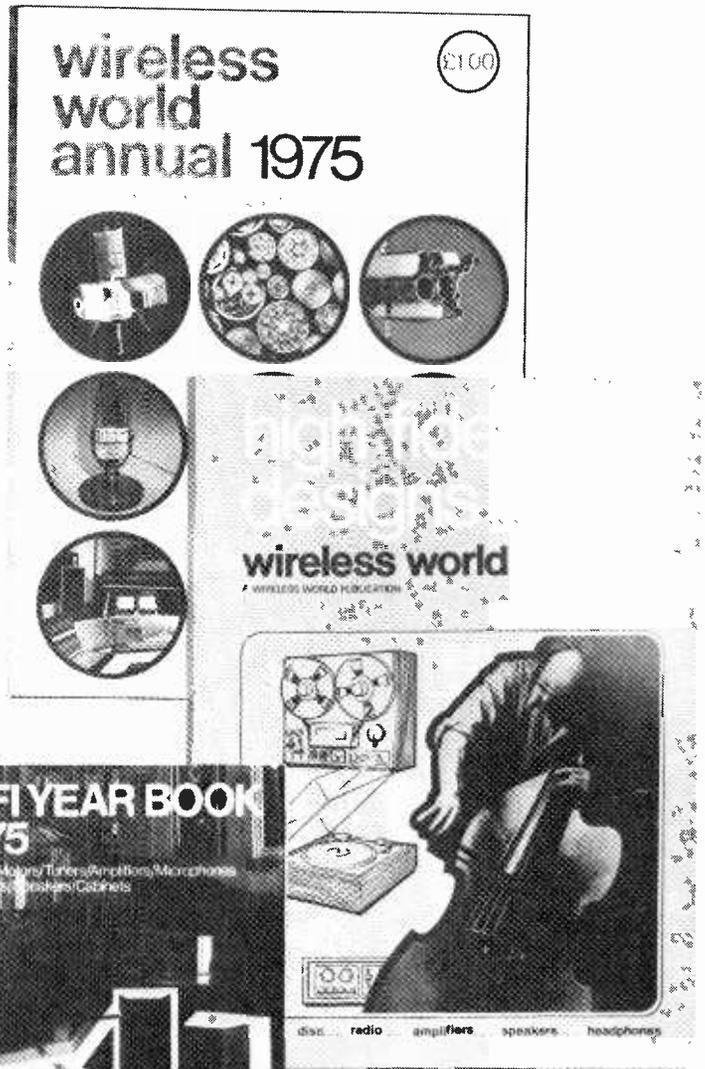This is the book that tells you everything you need to know about the hi-fi equipment on the market. Separate illustrated sections cover every major category, together giving prices and specifications of over 2,000 products. And it's got a directory of dealers/manufacturers – plus a host of articles on the latest hi-fi developments and their application.



ALSO AVAILABLE AT LEADING BOOKSTALLS

To: General Sales Department, Room 11, Dorset House, Stamford Street, London SE1 9LU

ORDER FORM

Please send me books as indicated below (state number of copies of each):

- Wireless World Annual 1975 (at £1.35 each incl.)
- High Fidelity Designs (at £1.35 each incl.)
- Hi-Fi Year Book 1975 (at £2.00 each incl.)

I enclose remittance value £
(cheques payable to IPC Business Press Ltd.)


Name
(please print)
Address

Regd. in England No. 877128 Regd. office Dorset House, Stamford Street, London SE1 9LU

ADVERTISEMENT

TEKTRONIX 515A OSCILLOSCOPE

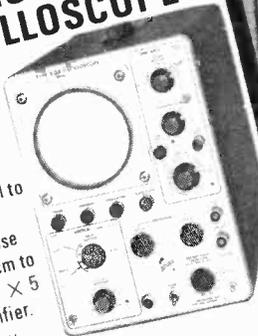Single Beam DC-15MHz risetime 24ns sensitivity 50mV/cm to 20V/cm Time Base 0.2us/cm to 2S/cm x 5 magnifier. Display area 6 x 10 cm plus internal calibrator



PRICE £125


OSCILLOSCOPE CT 436 Commercial Designation Solartron CD1014

General Purpose Dual Beam DC 6MHz flat faced double gun cathode ray tube operating at 1.6kV The time base velocity is continuously variable between 1cm/us.ec. and 1cm/sec. TIME BASE Free running or triggered from positive or negative pulses. Sweep speed 1cm/us.ec to 1cm/sec. Synchronisation: positive or negative going internal from either channel or external continuous waves. External 100mV/p.p. Sensitivity 100mV/cm: maximum on Y2 amplifier 1mV/cm. Size 9 1/2" x 11 1/2" x 15". Wt. 25 lb. PRICE: £69.50. Solartron 1014 2 & 3 £85. Tektronix Sampling Scope 661 £295.

ADD 8% VAT TO ALL PRICES

ADVANCE SQUARE WAVE GENERATOR SG21

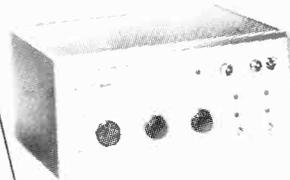
Frequency Range 9Kc/s to 100Mc/s. Rise time less than 1nS Ex-Demonstration. New condition in manufacturer's original carton.



9Kc/s to 100Mc/s continuously variable. Accuracy ±4% ±1% F.S. MAIN OUTPUT 20mV-1V into 50 ohm external termination continuously variable. Accuracy ±5%. Maximum output on open circuit 2V. RISE TIME less than 1nS up to 500mV. TRIGGER OUTPUT 0.2, 0.4, 1.0, 2.0V into 50 ohm external termination maximum output on open circuit 4V. Rise time normally 1.5nS. Fall time normally 3.5nS. Size 11inW 5 1/2inH. 9inD. Wt. 7.1 lb. LAST LISTED PRICE £95

OUR PRICE £35 p/p £1.50 Also available SG21A 100Kc/s-30Mc/s.

PRECISION DIFFERENTIAL VOLTMETERS

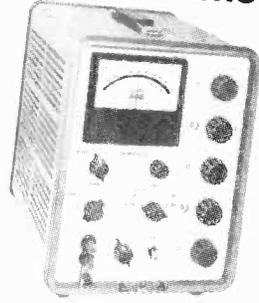


J. FLUKE 821A 0-500 Volts DC. 0.01% absolute accuracy.

Standard cell reference. Polarity Switch. Taut-band suspension meter. Infinite input resistance at null across entire range. J. Fluke 803B (AC/DC) £150. Marconi TF 2606 (DC) £150. Advance M500 (AC/DC) £150.

ALPHANUMERIC NIXIE TUBES B7971

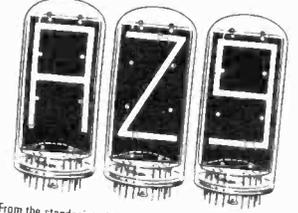The Alphanumeric NIXIE tube has the ability to display all the letters of the alphabet, numerals 0 thru 9 and special characters in a single tube.



From the standpoint of both readability and electrical characteristics, the Alphanumeric NIXIE tube provides many unique benefits including:

- ★ 170V-21mA ★ All DC operation
- ★ Uniform, continuous line characters of equal height
- ★ Memory with simple solid state drive circuits
- ★ Readability in high ambient light... 200 footcandle brightness ★ Long life with no loss of brightness
- ★ Character height 2 1/2 ins.

Price only 99p each plus 16p Bases for above 60p each DISCOUNT GIVEN FOR QUANTITY ORDER


JUST ARRIVED!! NUMERIC INDICATOR TUBES ultra-long life, high quality. 0-9 and 2 independent decimal points. Supply voltage 200V D.C. Current 14mA Pulse duration 1.4. Brand new, guaranteed. Surplus to manufacturers requirements. Type B5863st. Price 1-25 £1.00. 25+ 90p. 100+ 80p. 1000+ price on application.

THE REVOLUTIONARY SUPERTESTER 680R

FOUR INTERNATIONAL PATENTS - SENSITIVITY 20,000 Ohms per Volt 10 FIELDS OF MEASUREMENT AND 80 RANGES. ACCURACY 1% in D.C. 2% in A.C.

OUTSTANDING FEATURES:

- Fully screened against external magnetic fields
- Accuracy and stability 20,000 Ohms per Volt sensitivity
- Simplicity and ease of use and readability
- Scale width and small case dimensions (128 x 95 x 32mm)
- Printed circuit board, is removable (1% in D.C., 2% in A.C.) of indicated reading
- 1,000 times overload
- VOLTAGE A.C. = 11 ranges: 2000 Volts AMP D.C. = 12 ranges: 50µA-500µA-5 mA-50 mA-500 mA-50 Amp and 100µA-1 mA-2.5 mA-10 mA-100 mA-500 mA-500 mA-500 mA-5 Amp. OHMS REACTANCE = 6 ranges: x1-x10-100-x1000-x0.000 and Low Ohms. DETECTOR = 1 range: from 0 to 10 Megaohms. FREQUENCY = 2 ranges: from 0 to 500 and from 0 to 5000Hz. V. OUTPUT VOLTAGE = 9 ranges: 10-50-250-1000-2500 V and 20-100-500-2000 Volts. DECIBELS = 10 ranges: from -24 to +70 db. CAPACITY = 6 ranges: from 0 to 50,000 and from 0 to 500,000 pF using the mains and from 0 to 20, from 0 to 200, from 0 to 2,000 and from 0 to 20,000 Micro farad using the incorporated 3 Volts battery. **Bold figures indicate depress button.**

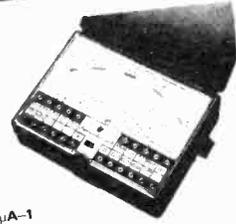

£18.50 with shockproof case

SPECIAL OFFER OF COLOUR T.V. AND F.M. MEASURING EQUIPMENT BY WANDEL AND GOLTERMANN

ZVM1 Measuring set for measuring phase and amplitude modulation distortion for Colour T.V. Sub carrier (PAL Systems) £495.00

ZVM2 Measuring set for measuring phase and amplitude modulation distortion for Multichannel FM radio systems with base bands up to 12 Mc/s. £295.00

ZVM3 Generator and Receiver used to measure transmission distortion on FM radio link systems. Superimposed signal 52/304/556kHz. £275.00

PROGRAMME BOARDS BY SEAELECTRO
These boards are basically a multi-pole multi-throw switch device consisting of a X-Y Matrix with two contact decks in the Z Plane running at 90 degrees to each other. Contact is made by either, shorting or plugging in pins. Ideal for prototype work, etc. Boards available in 2 planes. 24 x 50 £29. 20 x 11 £15. Pins now available at 15p each.

Stop Press

TEKTRONIX 453A Listed at over £1300. Special Offer this month £795.

SPECIAL OFFER OF TELEPHONE CARRIER TEST EQUIPMENT

An unusual offer of a system up to 15 Mc/s for the measurement of level attenuation on telephone carrier equipment and wide band radio relay systems.

SIEMENS sweep frequency system consisting of: 3W518 Level Oscillator 10 Kc/s-17 Mc/s; 3D335 Level Selective Meter 10 Kc/s-17 Mc/s; 3W933 Sweep Attachment; 3D346 Large Screen Level Tracing Receiver. Offered as a complete system as a 32M701. Special Offer less than Half-Price. Enquire for individual items P.O.A. £1950.00

Also available manual point to point system consisting of: 3W518 Selective Level Oscillator 10 Kc/s-17 Mc/s; 3D335 Selective Level Meter 10 Kc/s-17 Mc/s

Price Per Pair £950.00




TOP VALUE AC/DC MULTI-METER

With taut band suspension movement Sensitivity 20,000 ohms per volt on AC and 4,000 ohms per volt on DC

Technical Data:
 0.06-0.6-6-60-600mA 3 Amps DC
 0.3-3-30-300mA 3 Amps AC 0.6-1.2
 3-12-30-60-120-600 DC 1200 Volts.
 3-6-15-60-150-1300 600 900 Volts
 AC 45 to 20,000 Hz
 500Ω-5-50-500kΩ resistance Decibel
 range 10 to -12dB Accuracy (% of F.S.D.)—DC and resistance measurements -2.5. Price with test leads and storage case **£8.85**

UNIQUE MULTI-METER/SIGNAL GENERATOR

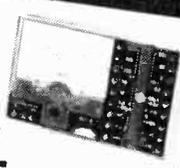

Taut suspension movement. Simple multimeter combined with audio/f. Test Oscillator providing AC and DC Voltage ranges D.C. current ranges and resistance ranges. 1kHz and 465kHz oscillator output makes the instruments suitable for general tuning of receivers etc.

Scale length: 65mm. D.C. voltage ranges: 0.5, 2.5, 10, 50, 1000V. D.C. current ranges: 2.5, 10, 15, 250, 500. Sensitivity 20,000Ω. Resistance ranges: 5-1000Ω mid-scale reading 50Ω 500Ω 10k, mid-scale reading 500Ω, 500Ω-reading 50kΩ. Accuracy: 5% of F.S.D. Internal battery: 3V dry cell. Oscillator output: 1kHz squarewave. 465kHz sinewave modulated by 1kHz squarewave signal. Output voltage: 1V minimum. Overall dimensions: 160 x 97 x 40mm. in carrying case. complete with test leads. **AMAZING VALUE £7.50**

Accessories available to convert Supertester 680R into following: SIGNAL INJECTOR, GAUSS METER, ELECTRONIC VOLTMETER, AMPERCLAMP, TRANSISTOR TESTER, TEMPERATURE PROBE, PHASE SEQUENCE INDICATOR. Send for details.

BUNNEN

LIMITED QUANTITY
Made to meet the most stringent Government Service Standards

DC-40MHz DUAL TRACE



Solatron C.T.484 oscilloscope.
3% accuracy. Dual Trace Displays.

DUAL TRACE Y AMPLIFIER Bandwidth: D.C.-24 Mc/s. Rise Time: 14 nanosecs. D.C.-24 Mc/s. Input Impedance: Sensitivity: 50 mV/cm. Accuracy: ±5% 1 M.ohm 26pF. Measuring Accuracy: ±5% direct. ±3% with calibrator. TIME BASE 100 nanosecs/cm-5 secs/cm or continuously variable up to 12 secs/cm. Sweep expansion X 5. Accuracy: ±3%. X AMPLIFIER. Bandwidth: D.C.-150 Kc/s. Sensitivity: 200 mV/cm and 1 V/cm. Input Impedance: 1 M.ohm 40 pF. INTERNAL CALIBRATOR. Accuracy: ±3%. WIDE BAND Y AMPLIFIER PLUG ALSO AVAILABLE. Bandwidth: D.C.-40 Mc/s. Rise Time: 8 nanosecs. Sensitivity: 50 mV/cm. Input Impedance: 1M ohm 22pF Measuring Accuracy: ±5% direct. ±3% with calibrator. **£149.50** P.O.A.

INCREDIBLE DIGITAL VOLTMETERS



Digital Voltmeters Type LM1420 **£195**
Type 1420 2 **£235**
Type 1420.2BC (Remote Ranging) **£325**
Type 1420.2BM (DC + Wide Band Mean AC Sensing DVM) **£395**
Wide Range of spares for Solatron Data Loggers Compact 1 and Series 2. Roband DM2004 **£75**
Dynamco 2001 mk2 **£175**

FABULOUS RANGE OF SIGNAL GENERATORS

H.P. VHF Signal Gen. 608B 10MHz to 400MHz **£175**
H.P. VHF Signal Gen. 608C 10MHz to 480MHz **£495**
H.P. UHF Signal Gen. 612A 450MHz to 1250MHz **£495**
H.P. UHF Signal Gen. 614A 800MHz to 2100MHz **£225**
H.P. Sweep Oscillator 693D 4GHz to 8GHz **£450**
Marconi VHF Signal Gen. 801B 12MHz to 485MHz **£125**
General Radio UHF Unit Oscillator + PSU 250MHz to 960MHz p.o.a.
Marconi PHM/AM Signal Generator TF2003 400KHz to 12.5MHz p.o.a.

VERY SPECIAL OFFER COSSOR

4000 50MHz Dual Trace Oscilloscope



5mV/cm Sensitivity, full delay sweep 1us to 100us/DIV. Timebase A sweep range 0.1us/DIV to 2S/DIV in 23 steps. X 10 magnified. Timebase 3%. Full triggering facilities. Use as XY Mode. Fully solid state. Limited quantity of ex-demonstration. Fully tested and guaranteed special offer. **£349.50** Manual **£7.50**. X 10 probes available **£8.50**.

6V 25A

Power Supplies

10% VARIABLE VOLTAGE HIGH CURRENT HIGH STABILITY HIGH RELIABILITY

These power supplies were designed for continuous operation in computer equipment. Manufactured to highest engineering standard for long-term reliability and stability. Independent voltage and current meters. C Core Transformer. Manufacturer's price probably in excess of £200.



£25

MULTI OUTPUT POWER SUPPLIES

Ex-Computer offered at mere fraction of original manufacturer's cost.

APT 13334 Mk III
Input 200/240V. +10V -5Amp. -10V -2Amp. +24V -2Amp. +20V -5Amp. -20V -2Amp. **PRICE £19.50**

Advances DC197
6V 7.5Amp. 6V 11Amp. 28V 9Amp. **PRICE £35**

BRAND NEW MINIATURISED STRIP CHART RECORDER BY RUSTRAK Model 88

This recorder indicates the magnitude of applied currents of voltages by a continuous distortion free line on pressure sensitive paper. Moving coil movement scale calibrated 1 milliamp D.C. internal resistance 100 ohms. Chart Drive motor 240V 50Hz. Chart speeds 90" per hour **£39** 1" per hour **£45** or 6" or 12".

SINGLE PEN RECORDER by Record Electrical

3" chart sensitivity 1 milliamp chart speed 1 and 6" per hr. Size 8" x 11" x 6". Offered complete with pen assembly. Listed at over £120—this month's special price due to bulk purchase.

1mA version **£50**
500µA version **£60**



AC CLAMP VOLTMMETER

Clamp-on Voltmmeter is used for measurements of AC voltages and currents without breaking circuits.

Specification
Measurement ranges:—Current 10-25-100-250-500 Amps. Voltage 300. 600 V. Accuracy 4%. Scale length 60mm. Overall dimensions 283 x 94 x 36mm. Weight 1.5 lbs.

£12.50

WIDE RANGE: Stroboscope—200 to 6,000 flashes per minute. Tachometer—200 to 6,000 RPM. **ACCURACY:** 3% or better. **CIRCUITRY:** 100% solid state. **BEAM ANGLE:** 80° **CALIBRATION:** At 3,600 FPM against any known synchronous speed—7200, 3600, 1800, etc. **FLASH DURATION:** Approximately 10 to 25 microseconds. **LIGHT COLOUR:** Xenon white 500°K. **COMPACT, LIGHTWEIGHT:** Can be carried in tool box, weighs only 27 oz. **EASY TO USE:** One on-off switch and one dial.

Carriage and packing charge extra on all items unless otherwise stated.

Please note: all instruments offered are second-hand and tested and guaranteed 12 months unless otherwise stated.

NEW CATALOGUE AVAILABLE EARLY IN THE NEW YEAR. WRITE IF YOU WISH TO RECEIVE A COPY. ADD 8% VAT TO ALL PRICES

ELECTRONIC BROKERS LIMITED

49-53 Pancras Road, London NW1 2QB. Telephone 01-837 7781

PROMPT DESPATCH MAILORDER. CALLERS WELCDME MON-FRI 9 A.M. to 5.30 P.M.

Potentiometers

TEN TURN 360° ROTATION

Res Ohms	Linearity Per cent	Manufacturers	Model	Price
100	0.5	Beckman	A.S.	£2.00
200	0.5	Beckman	A	£2.00
500	0.1	Beckman	S	£2.50
500	1.0	Relcon	HEL107.10	£2.25
1K		Relcon	HEL0710	£2.25
2K	0.5	Beckman	SA1101	£3.00
2K	0.25	Beckman	7216	£3.00
2K		Reliance	GPM15	£2.00
2K		General Controls	GPAL154	£2.00
5K		Relcon	07-10	£2.50
5K		Colvern	CLR2503	£3.00
10K	0.1	Beckman X	A	£3.50
15K		Colvern	CLR2402	£3.00
25K	0.5	Helipot	SAJ337	£3.00
30K	0.1	Beckman	A.88	£3.50
30K	0.5	Beckman	SA1892	£3.00
50K		Reliance	07.10	£2.25
50K		Reliance	07.5	£2.25
50K	0.5	Beckman	A	£3.00
100K	0.1	Beckman	A	£3.50
100K		Colvern	Z501	£2.25
298K	0.1	Beckman	8A3902	£3.50
300K	0.1	Beckman	A	£3.50

THREE TURN 780° ROTATION

250		Beckman	Type C	£2.25
100/100		Beckman	Type C	£3.00
1K		Fox	PX2/H3	£2.25
50K	0.5	Beckman	C.S.	£1.75

FIFTEEN TURN 5400° ROTATION

25K/25K		Beckman B	10 watts	£6.50
46K/46K		Beckman B	10 watts	£6.50

NEW "Strobette" STROBOSCOPE-TACHOMETER

What is "Strobette"? "Strobette" is complete combined Stroboscope-Tachometer available at a remarkable price. It's a stroboscope because it is capable of optically stopping, or slowing, any moving object while the object is in motion. And it's a tachometer since it can measure the speed, or rate of motion, of a rotating or moving object. "Strobette" is a tool, analyser, measuring device, fault detector for engineers, technicians, inspectors, teachers.



ONLY £49.50

SPECIAL PURCHASE OF ADVANCE EX-DEMONSTRATION TEST EQUIPMENT

Advance PG56 Double Pulse Generator

Independently variable. 2Hz-3MHz Pulse Width. Delay 70ns-0.2 sec. in 19 steps. Rise Time better than 10ns. External trigger and internal rate generator. **£120**

Advance PG52 Pulse Generator

Repetition frequency up to 20MHz and output pulses up to 20V into 5 ohms with rise and fall times of 5ns. Also produces complex ramp wave forms not obtainable from conventional pulse generators. Fully protected against short circuit. **£275**

Advance T.V. Dot and Cross Hatch Generator SG73


Output in form of modulated signal at VHF and UHF at level suitable for aerial sockets of receiver. Two Ranges
Band III on fundamental (MOD)
Band IV & V on Harmonics (-MOD)
Modulation 405 Lines or 625 Lines
£49.50 EX-DEMONSTRATION BRAND NEW

new from



ELECTRONICS

TUNERSET MODEL 7252

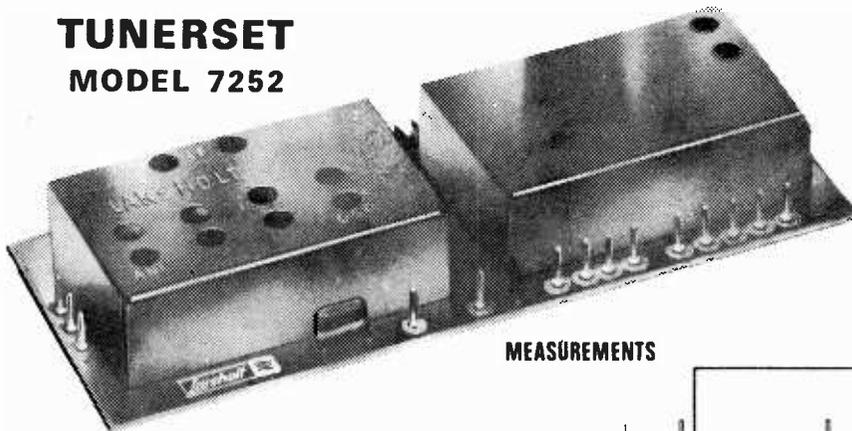


A new ELECTRONICALLY tuned FM radio receiver module, covering 88-108MHz

Featuring:

- 1uV sensitivity for 26 dB S/N 0.1% THD
 - 800 kHz AFC for 10uV signal
 - Twin audio preamp stages
 - AGC to input stage
 - 75/300 ohm input terminals
- Also available separately are the head alone (8319), stereo decoder and various control accessories.

Prices 7252 £20.00 8319 £7.74

MEASUREMENTS

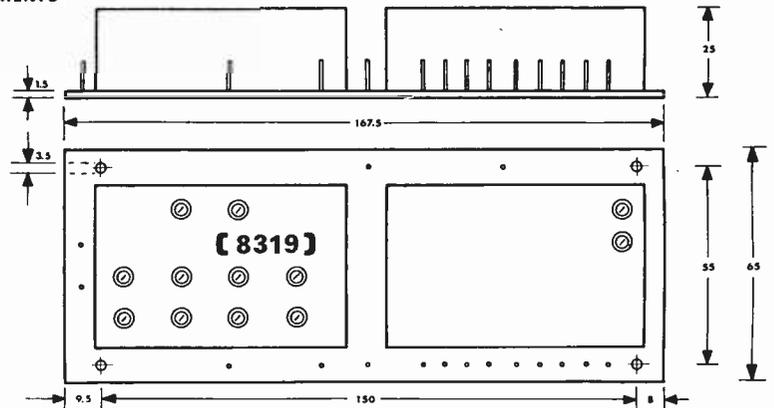


FM MODULE

Distributed in the UK by
AMBIT international
 37a HIGH STREET
 BRENTWOOD
 ESSEX CM14 4RH
 Telephone: (0277) 216029
 Enquiries S.A.E. please.

linear phase fm if (10.7MHz) filter

Size 23.5 x 23.5 x 18 mm.

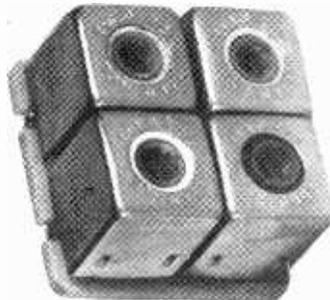

TYPE BBR 3125N

The new linear phase filter has negligible phase error across the relevant spectrum of the IF passband for MPX transmissions. Most ceramic filters introduce approx 60° of error across 10.69 - 10.72 — an error which cannot be permissible in true Hi-Fi FM stereo reception.

Centre Frequency 10.7 MHz ± 20kHz	Input/Output Impedance 330 ohms	Bandwidth -3dB = 250 kHz -30dB = 700 kHz
--------------------------------------	------------------------------------	--



O.E.M. Enquiries to:

Individual & sample enquiries to:

TOKO U.K.

**SHIRLEY LODGE
 470 LONDON RD
 SLOUGH
 BUCKS
 tel 48444
 tlx 847185 WWT SLOUGH**

PRICES:
 1 - 24 £1.30
 25 - 99 80p
 100+ 60p


ambit

INTERNATIONAL

**37a HIGH STREET
 BRENTWOOD
 ESSEX CM14 4RH
 Telephone: (0277) 216029
 Telex: 995194**

ELECTRONIC POWER UNITS

FOR XENON ARC AND MERCURY ARC LAMPS

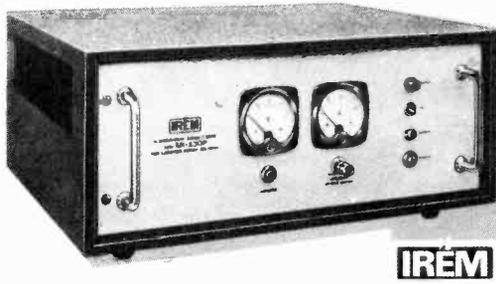

UNITS AVAILABLE FOR LAMPS RANGING FROM 75 TO 6500 WATTS.


Lamp housings and lens systems manufactured as standard off the shelf models or to specific design.

K. T. Manners Design Ltd.
33 Percy Street, London W1P 9FG
Telephone: 01-580 6361. Telex: 28604

TRANSFORMERS

CASED TRANSFORMERS

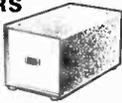Housed in smart resin-coated steel cases, with 3-core power cable and outlet socket, taped primary winding. Isolation types are fitted with 3-pin outlet sockets and are available with 110 volt or 240 volt output (Please state). Auto types are fitted with 2-pin (flat side sockets up to 500 VA 3-pin sockets from 750 to 3000 VA. See Auto and Isolation sections for prices. Plugs extra.



SAFETY ISOLATING

Prim. 120/240V. Sec. 120/240V. Centre Tap with screen

VA (WATTS)	REF. No.	PRICE Cased	PRICE Plugs 2 Pin+1 Earth	PRICE Open	Post
60	149	7.35	0.80	4.00	0.38
100	150	8.22	0.80	4.60	0.52
200	151	10.20	0.80	7.40	0.52
250	152	11.68	0.80	8.88	0.65
350	153	14.10	0.80	10.80	0.80
500	154	15.68	0.80	12.38	1.00
750	155	24.53	1.00	18.72	1.20
1000	156	32.19	1.00	25.50	1.20
1500	157	38.18	1.00	30.34	0.80
2000	158	45.20	2.40	34.68	0.80
3000	159	66.50	2.40	53.35	0.80

MINIATURE & EQUIPMENT

Primary 240V with Screen

VOLTS	Sec. 1	Sec. 2	MILLIAMPS	TYPE	PRICE	Post
3-0-3	200			238	1.23	0.10
0-6	500	500		234	1.30	0.10
0-6	1000	1000		212	1.95	0.22
9-0-9	100			13	1.23	0.10
0-9	330	330		235	1.43	0.10
0-8-9	500	500		207	1.75	0.22
0-8-9	1000	1000		208	2.30	0.30
15-0-15	40			240	1.23	0.10
0-15	200	200		236	1.30	0.10
20-0-20	30			241	1.23	0.10
0-20	150	150		237	1.43	0.10
0-15-20	500	500		205	2.47	0.38
0-20	300	300		214	1.72	0.22
0-20	3500	No Screen	1116		3.00	0.40
20-12-0	700			221	2.31	0.30
12-20	(D.C.)					
0-15-20	1000	1000		206	3.22	0.38
0-15-27	500	500		203	2.73	0.38
0-15-27	1000	1000		204	3.52	0.38

12 and 24 VOLTS PRIMARY 200-240 Volts.

12V AMPS	24V No.	TYPE	PRICE	Post
0.3	0.15	242	1.34	0.22
0.5	0.25	111	1.38	0.22
1	0.5	213	1.58	0.22
2	1	71	2.09	0.22
4	2	18	2.58	0.38
6	3	70	3.80	0.42
8	4	108	4.20	0.52
10	5	72	4.80	0.52
12	6	116	5.01	0.52
16	8	17	6.22	0.52
20	10	115	9.47	0.69
30	15	187	11.95	0.97
40	20	232	13.26	1.00
60	30	226	15.30	1.10

30 VOLTS

PRIMARY 200/240V. SECONDARY 12, 15, 20, 24, 30V.

AMPS	Ref. No.	Price	Post
0.5	112	1.72	0.22
1	79	2.21	0.38
2	3	3.26	0.38
3	20	4.10	0.42
4	21	4.68	0.52
5	51	5.80	0.52
6	117	6.50	0.52
8	88	8.50	0.67
10	89	8.47	0.67

50 VOLTS

PRIMARY 200/240V. SECONDARY 19, 25, 33, 40, 50V.

AMPS	Ref. No.	Price	Post
0.5	102	2.33	0.30
1	103	3.00	0.38
2	104	4.57	0.42
3	105	5.20	0.52
4	106	6.89	0.52
6	107	11.17	0.67
8	118	14.19	0.97
10	119	15.47	0.97

60 VOLTS

PRIMARY 240/240V. SECONDARY 24, 30, 48, 60V.

AMPS	Ref. No.	Price	Post
0.5	124	2.08	0.38
1	126	2.96	0.38
2	127	4.63	0.42
3	125	6.84	0.52
4	123	7.94	0.67
5	40	8.86	0.67
6	120	10.15	0.82
8	121	13.58	1.00
10	122	18.15	1.00
12	189	16.00	1.10

BRIDGE RECTIFIERS

ONE AMP	Price
50 P.I.V.	0.25
100 P.I.V.	0.25
200 P.I.V.	0.28
600 P.I.V.	0.30




FOUR AMP	Price
100 P.I.V.	0.55
200 P.I.V.	0.59
400 P.I.V.	0.65
600 P.I.V.	0.75

TWO AMP	Price
50 P.I.V.	0.35
100 P.I.V.	0.40
200 P.I.V.	0.45
400 P.I.V.	0.50

SIX AMP	Price
50 P.I.V.	0.65
100 P.I.V.	0.70
200 P.I.V.	0.80
400 P.I.V.	0.90

POWER UNIT TYPE CC12-05

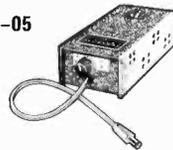

Output switched 3, 4.5, 6, 7.5, 9 and 12 Volts at 500 mA D.C. Operates from 240 V mains, suitable for Radios, Tape Recorders, Record Players etc. Size 7.5 X 5.0 X 14.0 cm. Price £3.95 Post 25p.

AUTO TRANSFORMERS

VA (Watts)	Ref. No.	PRICE Cased	PRICE Plugs 2 & 3 pin	PRICE Open	Post
Tapped at 115, 220, 240 Volts					
20	113	3.00	0.15	1.55	0.30
Tapped at 115, 200, 220, 240 Volts					
150	4	5.80	0.15	3.98	0.39
200	65	6.40	0.15	4.50	0.40
300	66	7.27	0.15	5.28	0.52
500	67	9.99	0.15	8.29	0.67
750	83	12.56	0.75	9.76	0.82
1000	84	15.70	0.75	12.40	0.82
1500	93	19.88	0.75	16.58	1.50
2000	95	30.10	1.44	22.05	1.50
3000	73	43.58	1.90	32.00	1.90

NEW! 2" AND 4" PANEL METERS

2"		4"	
SIZE: 45mm High	Wide X 40mm	SIZE: 110mm High	Wide X 43mm
0-50 micro A	1250	0-50 micro A	1400
0-100 micro A	580	0-100 micro A	730
0-500 micro A	170	0-500 micro A	200
0-1 mA	170	0-1 mA	200
0-5 mA	170	0-5 mA	200
0-10 mA	6	0-10 mA	6
0-50 mA	0.5	0-50 mA	0.5
0-100 mA	0.5	0-100 mA	0.5
0-500 mA	0.5	0-500 mA	0.5
0-1 AMP	0.5	0-1 AMP	0.5
0-2 AMP	0.5	0-2 AMP	0.5
0-25 Volt	15K	0-25 Volt	15K
0-50 Volt	50K	0-50 Volt	50K
0-300 Volt	300K	0-300 Volt	300K
g' Meter	170	g' Meter	200
VU Meter	5250	VU Meter	5250

VU Meters are complete with detectors. Modern wide view. Price 2" £3.15 Post 10p. Price 4" £3.95 Post 10p. Lamps 55p per set.

C1000 MULTI-METER

Compact General Purpose Mini Multimeter. Input Resistance 1000 ohms per volt. Ranges: AC Volts 0-15 50 250 1000 Volts. DC Volts 0-10 50 250 1000 Volts. DC Current 0-1 mA 0-100 mA. Resistance 0-150K ohms. Size 60 x 24 x 90 mm. Complete with Batteries, Test Prods, Instructions. Special price £3.20 Post 20p.



1-WATT CARBON FILM RESISTORS

also available 1/2 watt at 70°C E 12 range 10Ω-1MΩ. 5% tol. above 470KΩ 10% tol. at 95p per 100.

PLEASE ADD 8% FOR VAT

A.S.P. (Dept. WW2)

Byre House, Simmonds Road
Canterbury, Kent CT1 3RW

Tel: Canterbury (0227) 52436



CRYSTAL FREQUENCY STANDARD



LATEST IN THE RANGE TYPE 101 £80

OUTPUTS 1MHz, 100KHz, 10KHz
STABILITY 5 parts in 10¹⁰

8 DIGIT INSTRUMENTS WITH CRYSTAL OVENS

SENSITIVITY 10mV
STABILITY 3 parts in 10⁸



Directly coupled input and customers specific requirements to order

R.C.S. ELECTRONICS NATIONAL WORKS, BATH ROAD, HOUNSLOW, MIDDX, TW4 7EE. TEL: 01-572 0933.

WW-151 FOR FURTHER DETAILS

FREQUENCY COUNTERS

5 DIGIT TYPE 301 32MHz
SENSITIVITY 50mV
STABILITY 3 parts in 10⁶ **£75**



6 DIGIT TYPE 401 32MHz
SENSITIVITY 10mV
STABILITY 1 part in 10⁶ **£115**

TYPE 501 32MHz	£170	TYPE 701M 50MHz	Memory Version only £205
TYPE 501M 32MHz	£195	TYPE 801AM 300MHz	Memory Version only £285
TYPE 701 50MHz	£180	TYPE 901M 520MHz	Memory Version only £370

Electronic START/STOP version PLUS £12

Write for illustrated leaflet

Prices exclusive of VAT

ELECTROVALUE

IMPORTANT ANNOUNCEMENT PRICE STABILIZATION CATALOGUE DISCOUNTS

1975 is the year of challenge. Rather than sit back and wait for things to happen, we have produced our own policy to help stabilize price structure and maintain the services which have made ELECTRO-VALUE pre-eminent.

PRICES as shown in our latest catalogue (No. 7, issue 3) will be maintained at least until March 31st next (except in severe cases of market fluctuation) and then held after review for further 3-month periods instead of making day to day price changes.

CATALOGUE No. 7, ISSUE 3 is now ready with 108 pages of bargains and information. Price—30p post paid, including 25p refund voucher for use on orders for £5 or more.

DISCOUNTS apply on all items except the few where prices are shown NETT. 5% on orders from £5 to £14.99; 10% on orders value £15 or more.

FREE POST & PACKING in U.K. for pre-paid mail orders over £2 (except Baxandall cabinets). If under £2 there is an additional handling charge of 10p.

QUALITY GUARANTEE—All goods are sold on the understanding that they conform to makers' specifications. No rejects, seconds or sub-standard merchandise.

SUPPLIERS OF QUALITY COMPONENTS AND SEMI-CONDUCTORS AT COMPETITIVE PRICES

ELECTROVALUE LTD

All communications to Dept WW3.
28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB.
 Telephone Egham 3603. Telex 264475. Shop hours: 9-5.30 daily, 9-1 p.m. Sats.
NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester M19 1NA.
 Telephone (061) 432 4945. Shop hours: Daily 9-5.30 p.m.; 9-1 p.m. Sats.
U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081.

Wilkinsons P.O. type 3000 and 600 RELAYS



The best known of all Relays with a large variety of contact arrangements, all parts interchangeable known throughout the world. We have years of experience in building this type of Relay to your own specification. Complete banks of contacts made to order and component parts also supplied. Very highest quality at competitive prices with a quick delivery service. Quotations by return. We are Specialists in export orders.

DESK TYPE EXTENSION TELEPHONES complete with ringing £8.50 each.

P.O. type 2201a MINIATURE UNISELECTORS including Jack 12 outlet 2 bridging 1 non-bridging wipers. This compact ratchet-driven 3-level selector is of unique design and occupies no more space than a standard 3000 type Relay, £8.50 each. P.O. Type 2 Uniselectors 25 outlet 8-level non-bridging wipers 300 ohms, £14 each. Eleven-level 1 bridging 10 non-bridging 65 ohms, £17 each. P.O. Type 3 Uniselectors 25 outlet 4 level including single homing arc 1 bridging 3 non-bridging wipers 100 ohms, £10.50 each. Give us a phone call, we may have the Uniselector you require.

MINIATURE DIGITAL INDICATORS size of digit $\frac{3}{8}$ in illuminated by 28 volt midget flanged lamps, weight only 3½ ozs reading 0 to 9 with decimal points £4.50 each.

If you require a Pump for Water supply or Industrial use why not consult us, we are stockists of the World famous Stuart Turner Centrifugal Pump, types 10 and 12 in stock now for immediate delivery.

MINIATURE BUZZERS 6-12 volt with tone adjuster 50p each as illus. 15p each for lots of 50.

ROOM THERMOSTAT adjustable between 45-75 degrees F. 10 amp 250 volt bakelite case with control knob £2 each.

All prices shown are carriage paid UK only but subject to VAT at the standard rate.

**L. WILKINSON (CROYDON) LTD., LONGLEY HOUSE
 LONGLEY RD., CROYDON, CR0 3LH. Phone 01-684 0236. Grams: WILCO CROYDON**



WW—066 FOR FURTHER DETAILS

Principles and Calculations for Radio Mechanics Part 1

R. A. Bravery and A. P. Gilbert

Part of the Radio, Television and Electronics Servicing Series, this volume deals with the subject matter for Part 1 of the City and Guilds Radio Mechanics Course 222.

1974 152pp., illustrated 0 408 00119 4 £1.50

Obtainable through any bookseller or from

NEWNES-BUTTERWORTH

Borough Green, Sevenoaks,
 Kent TN15 8PH. Tel. Borough Green 2247.




Build up the network you need with Barr & Stroud Active Filter Modules

For maximum flexibility, the EF Series Active Filter Modules* are well worth your consideration. They give Bessel, Butterworth or Chebyshev responses, high-pass, low-pass, band-pass or band-stop filtering, are solid-state, compact and fully encapsulated. They are equally suitable for general laboratory functions or incorporation into standard equipment. Your own external components are used for tuning and response selection. Complete details are in pamphlets 1700 and 1732; ask for your copies today.

BARR & STROUD LIMITED
 London Office: 1 Pall Mall East,
 London SW1Y 5AU
 Tel: 01-930 1541 Telex: 261877



Glasgow and London

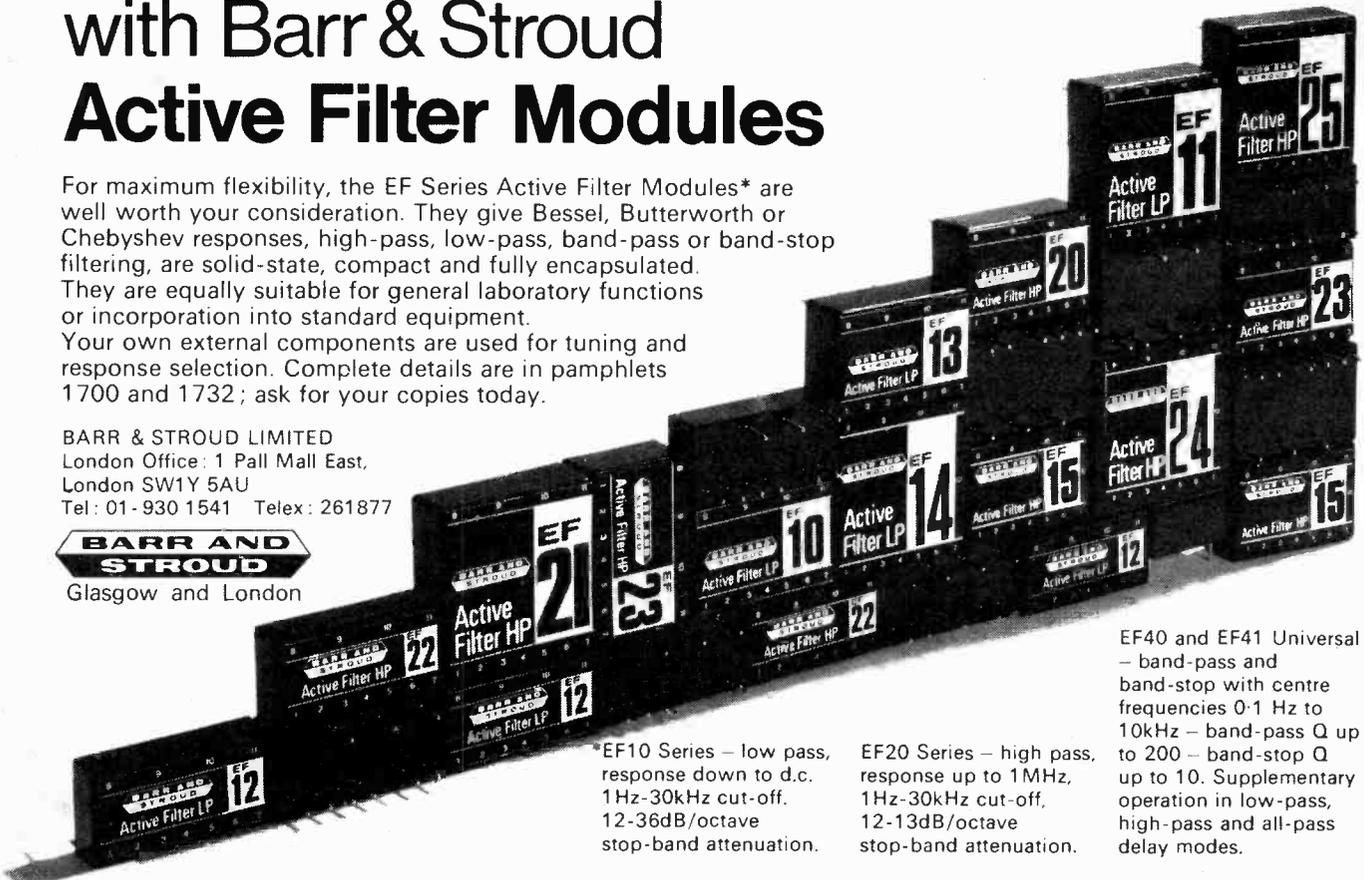

*EF10 Series — low pass, response down to d.c. 1Hz-30kHz cut-off. 12-36dB/octave stop-band attenuation.

EF20 Series — high pass, response up to 1MHz, 1Hz-30kHz cut-off, 12-13dB/octave stop-band attenuation.

EF40 and EF41 Universal — band-pass and band-stop with centre frequencies 0.1 Hz to 10kHz — band-pass Q up to 200 — band-stop Q up to 10. Supplementary operation in low-pass, high-pass and all-pass delay modes.

WW—008 FOR FURTHER DETAILS

ALL MAIL ORDER BY RETURN. C.O.D. SERVICE WELCOME

C. T. ELECTRONICS

We are open from 9.30 a.m.—6.00 p.m. Monday-Saturday

All mail order and enquiries to 270 Acton Lane, Chiswick, London W4 5DG.

V.A.T.
Unless otherwise stated all prices are EXCLUSIVE of V.A.T. Please add 8% to all orders. Carriage: orders under £5 plus 20p. Over £5 post free.

Tel: 01-994 6275

SEMICONDUCTORS

AC107	35p	BCY32	95p	MM1712	60p
AC125	25p	BCY34	60p	MPF102	45p
AC126	25p	BCY38	65p	(2N5457)	35p
AC127	27p	BCY39	£1-00	MPF103	
AC128	25p	BCY55	£1-50	(2N5457)	35p
AC176	25p	BCY70	22p	MPF104	
AC188	36p	BCY71	22p	(2N5458)	35p
ACY17	25p	BCY72	22p	MPF105	
ACY18	36p	BD151	75p	(2N5459)	40p
ACY19	36p	BD123	75p	OA47	10p
ACY20	25p	BD124	65p	OA70	10p
AD140	50p	BD131	40p	OA79	10p
AD142	50p	BD132	50p	OA80	10p
AD149	50p	BD158	75p	OA91	10p
AD181	44p	BDY11	£1-40	OA200	10p
AO182	44p	BDY17	£1-00	OA202	10p
AF114	25p	BDY19	£1-90	OA210	35p
AF115	25p	BDY20	£1-40	OA211	35p
AF116	25p	BF152	20p	OC16	60p
AF117	25p	BF194	14p	OC19	85p
AF118	25p	BF195	15p	OC22	55p
AS221	60p	BF196	15p	OC26	65p
AS223	30p	BF197	20p	OC28	60p
BA102	35p	BF200	30p	OC35	60p
BA112	50p	BF224J	30p	OC36	65p
BA114	16p	BFX29	30p	OC42	40p
BA156	15p	BFX34	30p	OC44	20p
BC107	12p	BFX85	30p	OC45	25p
BC108	12p	BFX86	30p	OC70	15p
BC109	14p	BFX88	30p	OC71	12p
BC113	15p	BFY10	35p	OC72	20p
BC115	15p	BFY44	50p	OC75	25p
BC116	16p	BFY50	25p	OC76	25p
BC117	30p	BFY51	35p	OC77	40p
BC118	12p	BFY52	25p	OC81	25p
BC147	11p	BFY53	25p	OC83	25p
BC148	11p	BFY90	65p	OC84	25p
BC149	12p	BSW63	65p	OC130	30p
BC153	15p	BSW68	60p	OC170	25p
BC157	14p	BSY127	20p	OC171	30p
BC158	15p	BY164	65p	OC200	60p
BC169	15p	IS100	15p	OC201	60p
BC182	12p	IS103	15p	OC202	75p
BC183	12p	MJ340	50p	TIP29A	45p
BC184	14p	MJ481	65p	TIP30	55p
BC186	25p	MJ2801	£1-25	TIP31A	57p
BC212	14p	MJ2901	£1-95	TIP32A	60p
BC212L	16p	MJE340	50p	TIP33A	£1-00
BC213	14p	MJE370	75p	TIP34A	£1-40
BC214	14p	MJE371	60p	TIP35A	£3-20
BC301	23p	MJE520	65p	TIP36A	£3-50
BC303	40p	MJE2955	£1-20	TIP41A	70p
BCY30	40p	MJE3055	75p	TIP42A	85p
BCY31	55p	MM1613	45p	TIP29B	54p
				TIP30B	60p

QTY. DISCOUNTS: 12+ 10%; 25+ 15%; 100+ 20%

METAL BOXES

TIP31B	85p	2N2218	25p
TIP32B	77p	2N2219	25p
TIP33B	£1-06	2N2222	20p
TIP34B	£1-62	2N2224	25p
TIP35B	£2-71	2N2306	70p
TIP36B	£3-50	2N2477	30p
TIP41B	78p	2N2640	50p
TIP42B	85p	2N2846	£1-50
TIP29C	60p	2N2904	25p
TIP30C	72p	2N2906	25p
TIP31C	80p	2N2907	25p
TIP32C	£1-00	2N2926	12p
TIP33C	£1-20	2N3053	25p
TIP34C	£1-80	2N3054	65p
TIP35C	£3-00	2N3055	50p
TIP36C	£3-74	2N3232	70p
TIP41C	60p	2N3252	85p
TIP42C	£1-00	2N3643	30p
TIS50	40p	2N3702	25p
ZTX107	15p	2N3703	12p
ZTX300	15p	2N3705	12p
ZTX501	20p	2N3706	12p
ZTX504	50p	2N3707	12p
ZTX531	30p	2N3708	12p
ZTX550	25p	2N3709	12p

ALUMINIUM BOXES IDEAL FOR VEROB-BOARD WITH BASE & P.K. SCREWS

AB7	2 1/2" Long	5 1/2" Wide	1 1/2" High	55p
AB8	4" "	4" "	1 1/2" "	55p
AB9	4" "	2 1/2" "	1 1/2" "	55p
AB10	4" "	5 1/2" "	1 1/2" "	55p
AB11	4" "	2 1/2" "	2" "	65p
AB12	3" "	2" "	1" "	50p
AB13	6" "	3" "	2" "	77p
AB14	7" "	5" "	2 1/2" "	90p
AB15	8" "	6" "	3" "	£1-16
AB16	10" "	7" "	3" "	£1-32
AB17	10" "	4 1/2" "	3" "	£1-10
AB18	12" "	5" "	3" "	£1-32
AB19	12" "	8" "	3" "	£1-80

★★SPECIAL OFFERS★★

MINIATURE MAINS TRANSFORMER.
PRI 240V. SEC. 12V, 100mA. Manuf.: Hinchley
LM723C 2-37V. 150mA
Voltage Reg... £1-05
Price 1-85p. 100-00p. ea. 1,000-50p. ea. 10,000-40p. ea.

3 CORE PVC INSULATED MAINS CABLE.
GREY ML650, 3 x 7/0.2mm. Price 100m-£4.50.
1,000m-£35. 10,000m-£330.

9-47 mfd. 50V MYLAR FILM CAPACITOR.
Size: 1" x 0.35" x 0.85" P.C. Mount. Price 100-6p
ea. 1,000-3p. ea.

LINEAR I.C.s

LM309K	5V. 1A.	Voltage Reg... £2-10
LM723C	2-37V. 150mA	Voltage Reg... £1-05
MFC4000	250mW	Audio ... 75p
TBA800	5 Watt	Audio ... £1-50
709C	Op Amp D.I.L./	TO99 ... 45p
741C	Op Amp 8/14	D.I.L./TO99 ... 35p
748C	Op Amp	D.I.L. ... 75p
747C	Dual Op	25 Amp. ... £1-20
ZN414	Radio I.C. £1-25	
TAD100	Radio I.C. Inc.	Filter ... £1-90
CA3014	...	£1-55
CA3018	...	£1-90
CA3028	...	£1-20
CA3036	...	£1-00
CA3046	...	85p
CA3048	...	£2-35
CA3075	...	£1-60
CA3090Q	...	£4-85
MC1303L	...	£2-20
MC1310P	...	£2-60

ALUMINIUM BOXES WITH SLOPING TOP PANEL IDEAL FOR PRE-AMPS, ETC., USING SLIDER CONTROLS

AB20	8" Long	9" Wide	3 1/2" High at back	£2-20
			2" High at front	
			With P.K. Screws	
AB21	As above	but 10" Long		£2-20
AB22	As above	but 12" Long		£2-60

ELECTRONIC COMPONENTS

BARGAIN COMPONENT PACKS
ALL COMPONENTS NEW & UNUSED
£1 plus 25p p.p. per pack, £5 for 5 packs p/Free
Pack No.

1 500 Carbon resistors, 3, 1/2, 1, 2 watt.
2 100 Electrolytic Condensers.
3 250 Ceramic, Polystyrene, Silver Mica, etc., Condensers.
4 250 Polyester, Polycarbonate, Paper, etc., Condensers.
5 25 Potentiometers, assorted.
6 750 High-stab. 1%, 2%, 5% resistors.
7 50 Assorted Tagstrips.
8 1lb. Assorted nuts, bolts, washers, spacers, toggled, etc.
9 25 Assorted switches, rotary, lever, micro, etc.
10 50 Preset Potentiometers.
11 Trial mixed component pack £1.
12 Jumbo mixed pack £5.

TRANSFORMER: DOUGLAS PRI. 0, 115, 200, 220, 240 SEC. 25-0-25-0-6V, 2 1/2A, £4-50 + 50p p.p.

MULTICORE CABLE. 25-way, Individually screened, 14/0076. £1-00 per yard + V.A.T. Postage by weight.

IMHOFF 19" RACKING CABINETS. 13 1/2" high, 22" wide, 13" deep. Brand new. £10-00 each + V.A.T. Carriage £1.00.

SIEMENS CONTRACTORS. Over 1,000 in stock. All types. Phone or write for details.

METAL OXIDE RESISTORS TR4/5/6 in stock. All values. 1-off price 3p each. Discount on quantity.

10 TURN TRIMPOTS by Bourns, Mec, Palnton, etc. All values in stock. 50p each. Discount on quantity.

TO3 VOLTAGE REGULATORS

LM05	5V 650mA
LM06	12V 600mA
LM07	15V 450mA

DIGITAL INTEGRATED CIRCUITS

SN7400	18p	SN7410	18p	SN7427	18p	SN7443	£1-00
SN7401	18p	SN7411	22p	SN7428	42p	SN7445	£1-70
SN7402	20p	SN7412	22p	SN7430	50p	SN7446	£2-00
SN7403	20p	SN7413	40p	SN7432	42p	SN7447	£1-50
SN7404	20p	SN7414	30p	SN7433	70p	SN7448	£1-75
SN7405	20p	SN7417	30p	SN7437	50p	SN7450	20p
SN7406	30p	SN7420	20p	SN7438	50p	SN7451	20p
SN7407	30p	SN7422	30p	SN7440	30p	SN7453	20p
SN7408	20p	SN7423	30p	SN7441A	75p	SN7454	20p
SN7409	40p	SN7425	30p	SN7442	75p	SN7460	20p

TAUT SUSPENSION MULTIMETERS

Made in USSR
For ex-stock delivery




U4312 £10.25*
U4313 £12.50*
U4315 £9.00*



U4324 £9.25*




U4341 £10.50*

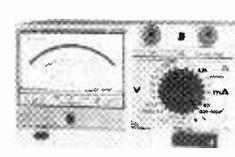

U4317 £16.50*



U4323 £7.70*

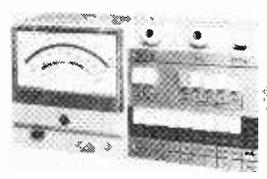

F4313 £22.00*

*Prices are exclusive of VAT
TRADE ENQUIRIES INVITED
PLEASE WRITE FOR FULL DETAILS

SPECIAL OFFER OF L.E.D.s

Twelve Light Emitting Diodes Type HP5082/4850, 0.20 mm dia., bright diffused red light. Operating current 20mA at 1.65V. ONLY £1.75 incl. P.P. and VAT

1-AMP SILICON RECTIFIERS

20 pieces	1N4001	50 p.i.v.	£1.12
"	1N4002	100 p.i.v.	£1.25
"	1N4003	200 p.i.v.	£1.35
"	1N4004	400 p.i.v.	£1.45
"	1N4005	600 p.i.v.	£1.55
"	1N4006	800 p.i.v.	£1.85
"	1N4007	1000 p.i.v.	£2.10

This is a special offer and minimum quantity of 20 pcs must be ordered. These prices are inclusive of P.P. and VAT.

11.5 AMP THYRISTORS

BTX47-1200R P-GATE Reverse blocking Thyristors. Peak reverse voltage 1200V. Trigger voltage 3.5V £2.00
Specials offer of 10 pcs £12.00
Inclusive of P.P. and VAT

PHOTO-CONDUCTIVE CELLS

ORP12	£0.60*	ORP69	£0.60*
ORP60	£0.60*	ORP90	£1.10*
ORP61	£0.45*	ORP93	£1.10*

Exclusive of P.P. and VAT
Please write for full catalogue and Price List of Valves, Semi-conductors, Test Equipment and Passive Components.

Minimum Account Order & Charge £10.00 + VAT, otherwise cash with order. Prices are exclusive of VAT unless indicated. When remitting cash with order please add £0.50 per Multimeter or £0.15 in £ for other items.

MINIMUM ACCOUNT ORDER CHARGE £10.00 PLUS VAT. OTHERWISE CASH WITH ORDER PLEASE

Z & I AERO SERVICES LTD

Tel. 727 5641 44A WESTBOURNE GROVE, LONDON W2 5JF Telex 261306



TRANSISTOR DATA ?



THE SEMICON

INTERNATIONAL TRANSISTOR DATA MANUAL

lists over 20,000 transistors of international origin alpha-numerically. Single line entries with major characteristics over 14 columns makes quick and easy reference. 400 pages. We update if you find an omission.

EXTENSIVE SUBSTITUTION GUIDE
CV NUMBERED DEVICES
OUTLINE DRAWINGS

ALTERNATIVE
MANUFACTURERS
AND AGENTS ADDRESSES


NEEDS SEEING TO BE APPRECIATED

ORDER NOW £8.80 includes postage
(TO COUNTRIES OUTSIDE UK ADD 60p POSTAGE)
FULL REFUND IF NOT COMPLETELY SATISFIED
PUBLISHED BY

SEMICON INDEXES LTD.,

2 DENMARK ST. WOKINGHAM, Berks. RG11 2BB
Tel: WOKINGHAM (STD 0734) 786161

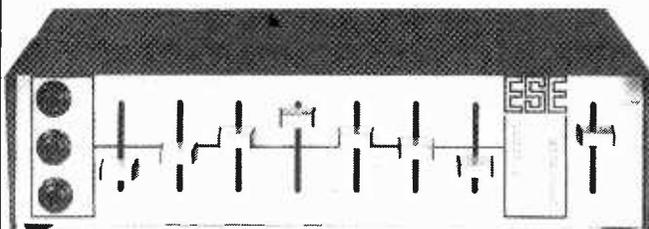NEW FROM E.S.E. A FULL FREQUENCY RANGE GRAPHIC EQUALISER YOU CAN AFFORD!!



FOR JUST £30.00
PLUS VAT

CONDENSED TECHNICAL
SPECIFICATION

YOU CAN TUNE OUT ALL UNWANTED NOISES AT SEVEN DIFFERENT FREQUENCIES! BRING ALL YOUR RECORDINGS, P.A., DISCOS, LEAD GUITAR, BASS GUITAR, ORGAN ANYTHING AMPLIFIED TO LIFE AT THE TOUCH OF A SLIDER!! NO MORE ANNOYING AMPLIFIER NOISES—JUST TRUE, CLEAR SOUND! FREQUENCIES FROM 60Hz TO 10KHz!

CUT OR BOOST EACH FREQUENCY BY MAXIMUM OF 15dB!

HIGH AND LOW GAIN INPUTS.

POWERED BY JUST TWO P.P.3 BATTERIES WHICH LAST FOR AGES. TRY IT AND YOU'LL BUY IT—IT WILL CHANGE YOUR CONCEPT OF SOUND.

TRADE ENQUIRIES WELCOMED.

MAX OUTPUT: + 13dBm INTO 600 OHMS
MAX INPUT: + 8dBm INTO 600 OHMS
SIGNAL TO NOISE RATIO: AT MAXIMUM,
BETTER THAN - 79dBm

FREQUENCY RESPONSE: ALL FILTERS
CENTRAL, BETTER THAN ± 2dBm.

FILTER RANGES: MAXIMUM ± 15dBm
AT 60, 180, 480Hz; 1, 2, 4, 5 AND 10KHz
DISTORTION: BETTER THAN 0.13% @ 0dBm

To E. S. Electronics, 2 Upper Fant Road,
Maidstone, Kent. Tel: 58903

Please send me 1 2 3 4 5 of
your Graphic Equalisers. I enclose cheque or
postal order for £ having
added 30p for P & P on each item ordered and
VAT at 8%. I understand that two batteries are
included.

NAME
ADDRESS

TEL. NO. W.W.1

P. F. RALFE

10 CHAPEL ST. LONDON NW1.

Phone 01-723 8753

SIGNAL GENERATORS

MARCONI TF801D/IS. 10-480 mHz P.O.A.
MARCONI TF801B/2S. 10-480 mHz £225.
MARCONI TF144H 10kHz-72 mHz P.O.A.
ADVANCE SG63D. AM/FM 7.5-230mHz £125.
HGN MS4U AM/FM 9.6-240mHz. N.Dev.Fac.
ROHDE & SCHWARZ SMLR 15-30mHz power generator. P.O.A.
RACAL/AIRMEC 201A. 30kHz-30mHz. As new. P.O.A.
ADVANCE SG21 VHF Square-wave generator 9kHz-100mHz. £25.



OSCILLOSCOPES

TEKTRONIX 661 Sampling scope with 4S1 & 5T1A
plug-in units. 3GHz. £200.

TEKTRONIX 545A with CA unit. DC-30mHz.
Price only £295.00.

TEKTRONIX 531 DC-15mHz with L type plug-in

TEKTRONIX 535 DC-15mHz with L type plug-in

TEKTRONIX 545B DC-30mHz with 'CA' plug-in.

NB: Due to the fragile nature of CRTs we regret that these oscilloscopes cannot be despatched by post. Collection only or delivery could be arranged.



MISCELLANEOUS TEST EQUIPMENT

MARCONI TF1400S double pulse generator with TM6600/S
secondary pulse unit. £105.

MARCONI TF791D deviation meter. 4-1024mHz. 0-100kHz
deviation.

MARCONI 455E Wave Analyser £120.

MARCONI TF2600 Valve Voltmeter 1mV-300V. Excellent. £75.

ROHDE & SCHWARZ USVD calibrated receiver 280-4, 600mHz.

ROHDE & SCHWARZ A.F. Wave Analyser type FTA 0-20kHz
plus log/lin AF meter incorporated. Excellent condition.

ROHDE & SCHWARZ URV milli-voltmeter BNI0913 (late type)
1mV-10V. With 'T' type insertion unit, free probe and attenuator
heads. 1kHz-1,600mHz. £175.

COSSOR I453 True RMS milli-voltmeter. Excellent. £75.

ADVANCE PG54 Pulse generator. AS NEW.

SOLARTRON EMI006 production-line resistance tolerance
check-set. 0-15Mohm digital read-out.

AIRMEC TYPE 210 modulation meter. Excellent condition.

WAYNE KERR B521 LCR Bridge. Excellent condition. £55.

RACAL SA520 Digital Frequency counter/timer. 300kHz. £47.50.

CAMBRIDGE A.C. Test Set. £75.00.

GAMBRELL Precision 4 Decade Resistance Box. 1-11, 110 ohms.
£24.50.

MUFFIN INSTRUMENT FANS

Dimensions 4.5 x 4.5 x 1.5 ins.
Very quiet running, precision fan
specially designed for cooling
electronic equipment, amplifiers
etc. For 110V. AC operation—
(practise is to run from split
primary of mains transformer or
use suitable mains dropper). CC
only 11 Watts. List price over £10
each. Our price, in brand new
condition, is £3.50.

AVO VALVE TESTERS

Brief-case type 160. Full working
condition throughout. £65.

AERIAL CHANGE/OVER RELAYS
of current manufacture designed especially
for mobile equipments, coil voltage
12v., frequency up to 250 MHz at 50 watts.
Small size only, 2 in. x 7/8 in. Offered
brand new, boxed. Price £1.50, inc. P.&P.

RACAL/AIRMEC VHF/UHF Milli-
voltmeter type 301A. Frequency
range 50Hz-900mHz. Voltage range
300µV-3V in eight ranges. Co-axial
input 50 and 75 ohms BNC con-
nectors. DC Ranges 100µV-10V in
ten ranges. Light-weight mains
operated instrument in as new con-
dition with handbooks. Other
makes of voltmeter also available
from stock.

POLARAD Model SA84WA SPECTRUM ANALYSER

10MHz-63GHz. I.F. Markers. Spec-
trum calibrator. Log/Lin scale.
NB. This is not the instrument
with the expensive TWT to
replace. Supplied in full working,
excellent condition. Guarantee.

MANY TYPES OF RF plugs and sockets in stock:—

BNC plugs 50Ω. 30p. BNC sockets
50Ω. 25p. N. Type plugs 50Ω. 50p.
Burndept plugs. 40p. Burndept
sockets. 40p. Miniature PYE. 20p.
Miniature sockets. 20p.

All connectors are brand new.
Immediate delivery. Please add
appropriate postage.

DURATRAK VARIACS type 100L.
230V. AC Input. 0-230V. AC Output, at
8 amps. Brand new units, less control
knobs. Price only £15.00. Carriage £1.

MINI HELIPOTS

500Ω Beckman Linearity Tolerance
0.075% (10 Turn). 1KΩ Beckman
Linearity Tolerance 0.25% (10 Turn).
20Ω Colvern CLR 26/6310/95 (3 Turn).
5KΩ Colvern (10 Turn).

EDDYSTONE U.H.F. RECEIVER type 770S.

Continuous coverage from 500-
1000mHz. AM/FM. Sensitivity
approx. 10µV absolute. Completely
self-contained with speaker. Excel-
lent condition.

HEWLETT PACKARD/ BOONTON TYPE 8900B

Peak-power calibrator. Measures
true peak power ±.6 db absolute.
Frequency range 50-2000mHz. RF
power range 200mV peak, full-
scale. RF Impedance 50 ohms.
P.O.A.

**MARCONI TF995A2/M AM/FM
R.F. SIGNAL GENERATORS.**
1.5-220mHz. 0-100kHz Deviation.
1µV-100mV output. Sold in excel-
lent condition. P.O.A.

PLEASE ADD 8% V.A.T. TO THE TOTAL AMOUNT
WHEN ORDERING. INCORRECT AMOUNTS WILL
CAUSE DELAY IN DESPATCH. THANK YOU.

How to stay ahead of demand in the electronics age

If you're an electrical or radio dealer you must have often pondered the above problem. You want to know what to stock and, of course, the best way to sell it. You need a regular source of information specially designed for retailers like you. And that's exactly what Electrical and Electronic Trader is. Its expert sales advice, shrewd comment and unrivalled technical intelligence service are used by thousands of successful retailers every week. Isn't it time you ordered it regularly too?

Regular features include:

Product News

Every week new merchandise is fully described to assist retailers in evaluating the products they will sell and service.

Tips about tax

Discusses the intricacies of tax and shows how you can save by adopting correct procedures.

Monitor

Monthly business round-up of retail statistics at national level and a report of trade trends within regions.

Hi-Fi this week

Weekly comment on hi-fi topics for dealers extending their hi-fi interests.

Dealer marketing

Every fortnight our business consultant describes methods of increasing profit with little expenditure.

Service Sheets

Free every week for the service technician, a full size service sheet covering a popular make of TV (including colour) or audio equipment.

ELECTRICAL AND ELECTRONIC Trader

Annual subscription £8.00

ELECTRICAL AND ELECTRONIC Price 15 November 1975, Vol 10 No 2

Trader

THE NEWSPAPER FOR RADIO AND ELECTRICAL DEALERS

Beauty your profits with Philips, the largest makers of electrical beauty aids

PHILIPS

THIS WEEK

Competence
PTES launch a new competence certificate for TV service

Earlier HP
Movers ensure the do covers the budget for fashion shops

Ajax
Slovakian visit treatment looks for VFT treatment as a report on the competition

Sales promotions
Including an evening book in Philips and consumer equipment

Aerial business
New Stephen Ward has the business for the past year in the UK

Aerial news
New about products and special events of interest in aerial centres

Tax
Our tax expert points out the dangers of not using the Home Office relief

Product news
Top-loading portable cassette from Sanyo

Chemical aids
A look at the new range of chemical aids for the hair

Company news
Dimple take a profit and look to better profits

Service sheet
310171 Four Philips colour television sets

Report on pay 'urgent'

GREATER ATTENTION should be given to the pay, conditions and career development of shop staff looking for long-term employment as retailing says a report published by the Distributive Trades Little Needs.

And among the comments is a recommendation that further work should be done on a study of staff in the retail sector.

The report published the week ending 10th of the past week by a working party on pay and conditions in retail distribution whose members include Lord Keshington managing director of Marks and Spencer.

Little Needs says that the study pointed out the need for a major problem, and it has decided to plan ahead with publication of the report in the next few weeks.

The report says that large councils have been ineffective in remedying the low pay for retail employees.

The legal minimum wage of 1.50 per hour is being raised to 1.60 per hour in 1975.

Attitude survey supported measures for improvements combined with an industry movement might be an appropriate means of remedying pay in relation to the report.

Among tasks to be tackled for the second phase of their contribution of the industry are that of the retailer of training and potential employees in the home and work, and motivating people in general.

The study also says to examine the role of the Government in the retail sector.



Breaking new territory

THESE are some of the names on the introductory course for the 'Retail International' first time colour receiver, the Book 10.100.

The new and better design has been built with reliability, ease of servicing and low cost as primary objectives, with improved 'reception' as a B21.

It is also equipped with a combined photo and front panel mounting for easy fitting. The colour shift control is also built into the front panel of the set to be easily reached by the viewer. The set is also built with the convenience of a built-in stand and a built-in speaker.

Consumer centres on the front of the set are an other feature - an all height-adjustable control and volume adjustment in a row at the top. Four great built-in buttons select station.

A built-in channel and a remote control allow the set to be used with a built-in stand and other sets as a replacement front panel and a V.I.T. of 22200. Chromium plated ends are featured.

'Biggest ever' Harrogate show

REPRESENTATIVES from the British electrical and retail trade.

The show will be held at the Harrogate Convention Centre from 11-15 January 1975. It will include special displays and guide which give a full list of exhibitors with details of products on display.

The show is organized by the Electrical Council's marketing department who are running the Council's annual marketing conference which will be held with the show on 11-15 January.

The show is organized by the Electrical Council's marketing department who are running the Council's annual marketing conference which will be held with the show on 11-15 January.

Selling an automatic washing machine or a dishwasher?

Then... include BCI in your sale the purpose designed stage venture

Write or phone now for special quantity terms



BCI Limited, 28 St. John Street, London E.C.4
Tel: 01-562 5555

To: Electrical and Electronic Trader, Room 15, Dorset House, Stamford St., London SE1 9LU

Please send me Electrical and Electronic Trader for one year. I enclose remittance value £8.00 (cheques should be made payable to IPC Business Press Ltd).

NAME _____
(please print)

ADDRESS _____

Registered in England No. 677128
Regd. office: Dorset House, Stamford St., London SE1 9LU


The SECOND-USER Computer Specialists

Peripherals and Systems for Data Processing Systems, Equipment and Components

COMPUTER SALES AND SERVICES

Mini-Computer Systems

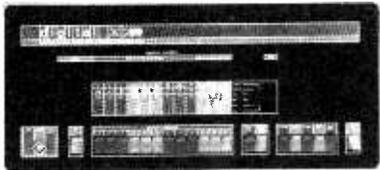Available for immediate delivery at greatly reduced prices due to special purchase



Little-used PDP8E 12K system including: High Speed Paper Tape Reader, High Speed Paper Tape Punch, Memory Drum, ASR33 Teletype.

Just arrived—PDP8L 4K processor with 8K extender box. A phone call could save you a bomb! Ring now for price. Other models becoming available all the time—let us know your requirements.

DEC High-Speed Paper Tape Reader Punch for PDP81. Hardly used. Our special price **£1,500**. DATA DYNAMICS 1114 RACK-MOUNTED 110 cps PUNCH. As new. Mounted in sound-reducing rack cabinet and complete with control and interface electronics and power supply unit with short circuit and overload protection. Asynchronous operation up to 110 cps.


OUR SPECIAL PRICE **£550** (list price £790). FACIT 4001 HIGH SPEED PAPER TAPE READER, rack-mounting version, 5/6/7/8 channel dielectric reader for speeds up to 500 cps (or 1000 cps using separate spooler). ONE BRAND NEW UNIT AVAILABLE IN ORIGINAL MANUFACTURER'S PACKING. OUR BARGAIN PRICE **£895** (list price £1,128).

One second-hand (little used) unit also available at **£650**. FACIT 4060 150 cps Rack-Mounted Paper Tape Punch. Suitable for all types of tape including Mylar. UNUSED SURPLUS—A BARGAIN AT **£595** (list price £1,056).

Add 8% VAT to all prices shown. Carriage extra—details on request

Keyboards

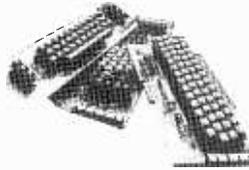Electro-mechanical numeric and alphanumeric keyboards originally designed for 80 column card punch and verifier machines. Numeric with 12 character keys and 8 instruction keys. Alphanumeric with 47 character keys and 8 instruction keys.



Price: Numeric **£4.50**, Alphanumeric **£15**.

Paper Tape punch/verifier keyboards. Full alphanumeric keyboard with 65 keys + 4 shift keys in 4-bank layout. ISO coded. Operating speed up to 25 ch./sec. Mounted in attractive case with control panel. Price **£25**.

Reed-Switch 4-bank Alphanumeric keyboard, mounted on PC board and housed in metal case. 43 character keys + 2 shift keys and 16 instructional keys. Ideal for data displays, computer programming, etc. Price **£30**.

Photo-electric Encoded Keyboards. No metallic switches or contacts. Generates any eight bit code to specification. Photo-electric keyboard combines Photoelectric encoders and power assisted solenoid actuators. 45 key alphanumeric keyboard + space bar + key interlock. Output—Photocells 500K to 2 Meg. for Logic 1, 800 Ohm-2 KOhm for Logic 2, -12V DC-OVDC Logic 1, Voltage requirements -26V DC mA, -12V 60 mA, + 6V 5mA. Price **£45**.

STOP PRESS!!!

JUST ARRIVED—FABULOUS BRAND NEW KEYBOARDS WITH READ ONLY MEMORY. Input Voltage -12V DC; positive logic; TTL compatible; odd parity 8-bit, two-key rollover; strobed ROM.

4-bank alphanumeric keyboard with 77 key positions + space bar. Ideal for communications equipment. Complete with associated integrated circuitry. Power supply connections and binary-coded outputs are made to a printed card connector at rear of keyboard. OUR INCREDIBLE PRICE **£49.50**

Peripherals

80 COLUMN HAND PUNCHES



Ideal for stock control, sales analysis, back-up in existing computer installations, DP training centres, schools, etc. New low cost model **£69.50** plus carriage.

DE LUXE MODEL

Incorporating tabulating mechanism. **£89.50** plus carriage.



ELECTRIC HAND VERIFIER



£96 plus carriage. All machines supplied with numeric keytops and dust-cover and covered by our three month guarantee. Delivery ex-stock. Optional extras alpha keytops and chip tray. Send for free descriptive leaflet NOW!

Punch Card

IBM Punch Card Equipment
024 Automatic alphanumeric keypunch
026 Automatic alphanumeric printing keypunch
056 Verifier (for use with 024, 026)

TERMINALS

BRAND NEW KSR33 Keyboard Send/Receive Terminal, complete with stand. Price **£525.00**
ASR 35 Heavy Duty Console Terminal, as new. Price **£700.00**
IBM Model B Input/Output Typewriter. Price **£125.00**
IBM Golfball Input/Output Typewriter. Price **£400.00**



COMPUTER SALES & SERVICES (EQUIPMENT) LIMITED
49/53 Pancras Road, London NW1 2QB. Tel: 01-278 5571

MIL SYNCHROS EX STOCK

WE ARE ANXIOUS TO BUY Synchro Test Equipment manufactured by Muirhead, Singer-Gertsch etc. Test Dials, Dividing Heads, Bridges, etc. to expand our test facilities.

SOLAR CELLS. Ferranti silicon MSIIBE, active area 390 sq. mm. Open CCT voltage 550mV at 3000 lumens/sq. ft. Sht. Cct. Current 60mA. Optimum load 90 ohms. Dia. 34mm. Thickness, 6mm. mtg thrd 1/4-28 unF 2A. Ex made up panel. **£1.35** (inc. P. & P. and VAT)

PANEL DISPLAY RECORDING CAMERA. Manufactured A.G.I. Specifically for the recording of complex instrument displays on 2 1/4in. x 2 1/4in. shots. Fitted 80mm F3.5 lens. Shutter speeds 1/100, 1/50, 1/25 sec. and time exp. Focusing at 1.75 to 50 ft. in 18 steps. Aperture stops F3.5 to F22. Prismatic viewfinder and facility for viewing direct on ground glass screen. Rotating filter attachment. Cord film advance and shutter cock with septe. Button control and electrical release facility (24V DC) Spool holds 40 exposures. Camera may be wall mounted on bracket supplied. Tripod mounting socket provided. In wooden case. Two grades available 'as new' Grade A **£25.10** (inc. P. & P. and VAT). 'Somewhat used but serviceable Grade B **£28.08** (inc. P. & P. and VAT).

Metal Oxide Resistors (ELECTROSIL & WELWYN) Tantalum Capacitors (KEMET, ITT, PLESSEY, ETC.) MANUFACTURING QUANTITIES

GAS CHROMATOGRAPHY RESEARCH OVEN PV4051/4056

A large capacity oven of low thermal mass for use between 35 and 400°C. Provides a forced air circulating system yielding 1000 changes of air per min. The oven has forced air cooled outer surfaces when the internal temperature is high. 210-250V, 50Hz. 2.6KW. **£29.50**. (C.P.D. England and Wales).



We are direct importers of Alps Keiki quality panel meters. We can thus offer these attractive meters at extremely competitive prices.

Range	TYPE No AND FRONT COVER DIMENSIONS IN MM												
	SR45	SR52	SR65	SA38	SA45	SA52	SA52W	TAD48	TAD66	TAD86	TAD118	TAD152	SA65E
50µA	72x56	78x63	92x72	43x43	51x51	61x61	3.96	48x42	66x60	86x70	118x106	150x110	82x78
1mA, 5mA	3.90	4.15	4.39	3.49	3.56	3.84	3.96	3.59	3.78	3.98	4.87	5.44	6.35
10mA, 50mA	3.10	3.70	3.95	3.08	3.15	3.40	3.55	3.23	3.41	3.61	4.50	5.20	5.90
100mA	3.57	3.81	4.06	3.15	3.23	3.51	3.63	3.34	3.52	3.72	4.61	5.31	6.00
1A, 5A, 10A	3.57	3.81	4.06	3.12	3.19	3.47	3.63	3.26	3.45	3.64	4.54	5.23	6.00
15V, 30V, 100V													
AC													
150V, 300V	3.70	3.94	4.19	3.36	3.36	3.64	3.76	3.43	3.62	3.81	4.70	4.85	6.15

Type SR is in an attractive modern case. Types SA and TAD are plainer with movement area louvred. All covers are exceptionally robust. NO HIDDEN EXTRAS! All prices include P&P & VAT. Quantity discounts offered. Full illustrated price list SAE please!

SPECIALIST STOCKISTS OF SERVOMOTORS, SYNCHROS, MAGSLIPS & CONNECTORS

Servo and Electronic Sales Ltd

Post Orders and Technical enquiries to: 24, HIGH ST., LYDD, KENT. TEL: Lydd 20252 (STD 0679) V.A.T. Reg. No. 201-1296-23 TELEX 965265

Also at 45a HIGH ST., ORPINGTON, KENT. TEL: ORP 31066

TELEPRINTER PAPER. Standard rolls. 1 ply **£3.80** per doz. 2 ply **£3.80** per doz. 3 ply **£4.10** per doz. 4 ply **£4.40** per doz. All P.Pd. U.K. Telex your order now!

A.C. SUPPLY PANEL for 19in. rack mounting carrying two 2kVA Variacs with double brush assemblies providing four individually fused and metered outputs of up to 4kVA and 270V in excellent condition at **£48.50** including carriage and V.A.T. (U.K. mainland).

TAPE STORAGE CANS. Brand new finished steel cans originally intended for 16mm film but ideal for storing 7 in. reels of tape. Our last supply of these items was quickly exhausted at 30p each but as a result of a massive new purchase we can now offer a case of 55 at **£5.25** inc. P. & P. and V.A.T. Sample order 10 for **£1.10** inc. P. & P. and V.A.T.

STAINLESS STEEL VACUUM CONTAINERS FOR LIQUIDS. Capacity 2 U.S. galls. fitted with delivery tap. Brand new in carton—**£25** (C. Pd. U.K.).

N.E.P. Mod. 1050 Channel UV Recorder. Fitted 5 gals. With P.S.U. for 230V. A.C. 14 x 10 x 12 in. (recorder) and 14 x 10 x 8 in. (P.S.U.). **£220.00** (inc. carr. & V.A.T.).

RADAR CABLEFORM INSULATION TESTER for checking insulation between individual conductors and each other and ground at preselected voltages up to 10kV. Full details on application.

WEE MEGGERS. 250V **£12.53**. RECORD MEGGERS. 500V **£15.12** (inc. P. & P. and VAT).

INDUCTION GENERATOR

Requires a supply voltage of 50V 50Hz and provides an output of 7V per 1,000 r.p.m. directly proportional to speed. This instrument has a wide variety of applications, e.g., anemometers, measuring shaft speed etc. In brand new condition **£5.25** post paid.

ALL PRICES INCLUDE 8% V.A.T.

LEMANIA AIRCREW CHRONOGRAPHS



Stainless Steel case with screw back; luminous hands and markings. One fifth sec. sweep hand controlled independently of main movement by press to start, stop and return to zero button. 15 jewel movement. Many of these watches are as new but all have been completely overhauled and checked for accuracy. Fitted strap. White face **£18.25**. Black face **£19.20** inc. P. & P. All watches: Inspection against remittance

GS WATCHES

all with brushed stainless steel case with screw back and black faces. Manufactured by CYMA, VERTEX, RECORD, etc. to a standard specification. Completely overhauled. Fitted strap. **£8.80** inc. P. & P. We also have limited quantities of these watches by OMEGA, LONGINES, BUREN, HAMILTON, JAEGER LE COULTRE and IWC at **£15.25** inc. P. & P.



DRY REED INSERTS

Overall length 1.85in. (Body length 1.1in.) Diameter 0.14in. to switch up to 500mA at up to 250V. D.C. Gold clad contacts **70p** per doz.; **£4.10** per 100; **£29.80** per 1,000; **£270** per 10,000. All carriage paid U.K.
Heavy duty type (body length 2in.) diameter 0.22in. to switch up to 1A, at up to 250V. A.C. Gold clad contacts, **£1.38** per doz.; **£8.78** per 100; **£51.40** per 1,000; **Changeover Heavy Duty type £2.70** per doz. All carriage paid U.K.
Operating Magnets **90p** per doz.; **£6.80** per 100; **£65** per 1000. All carriage paid U.K.
Operating Coils for 12v supply to accept up to four standard reeds **£2.20** per doz.; **£12.30** per 100. All carriage paid U.K.

OVER 300,000 IN STOCK!
MULTIWAY AND R.F. CONNECTORS by twenty different companies!
Send us your detailed requirements quoting Nato numbers if known. TELEX 965265.

Collect Wireless World Circards. And build a valuable dossier on circuit design.


Circards is a new and comprehensive system, launched by Wireless World, to provide professional engineers and enthusiasts with valuable and up-to-the-minute data on circuit design. Data not available from any other single source.

Each Circard is 8" x 5" and shows a specific circuit, a description of the circuit operation; component values and ranges; circuit limitations; circuit modifications; tested circuits; performance data and graphs.

The double-sided format enables the Circard to be filed in standard boxes for easy reference. And the plastic wallet provided keeps the cards well-protected.

Circard sets come in wallets and cost £1.50 per set. A subscription for 10 consecutive sets costs £13.50.

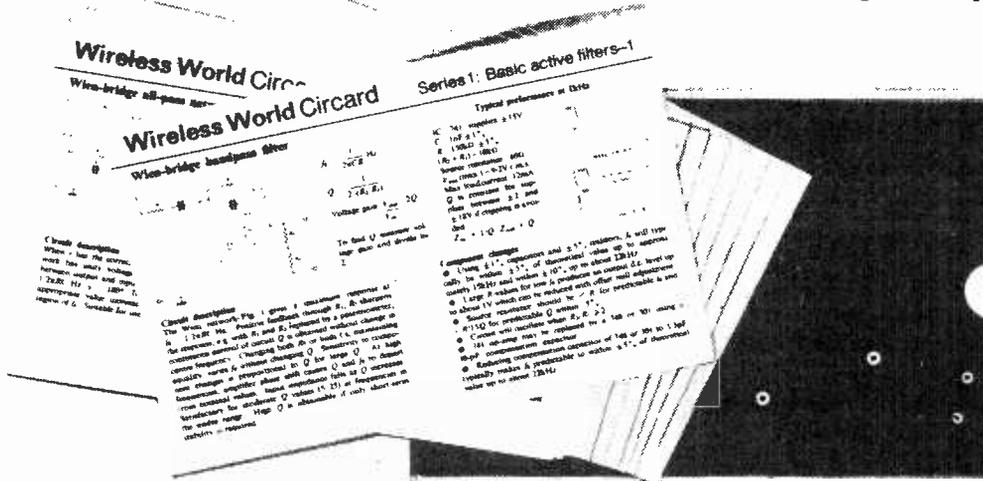Start your personal dossier on circuit design by completing and returning the coupon below.



Subjects already covered by Circards

1. Basic active filters. 2. Switching circuits, comparators and schmitts.
3. Waveform generators. 4. AC Measurements.
5. Audio circuits: preamplifiers, mixers, filters and tone controls.
6. Constant current circuits. 7. Power amplifiers.
8. Astables. 9. Opto-electronics.
10. Micropower circuits. 11. Basic logic gate circuits.
12. Wideband amplifiers. 13. Alarm circuits.
14. Digital counters. 15. Pulse modulators.
16. Current differencing amplifiers—Signal processing.
17. Current differencing amplifiers—Signal generation.
18. Current differencing amplifiers—Measurement and detection. 19. Monostable circuits.

Subjects planned

Two-Transistor circuits, Multipliers and Dividers, Code converters, DC Amplifiers and Choppers, Amplitude modulation and detection, Transistor arrays. Sets 18-25 will be sent to subscribers separately after publication. We shall be pleased to receive your order.

To: General Sales Dept., IPC Business Press Ltd., Room 11 Dorset House, Stamford Street, London SE1 9LU

Please send me set no(s) @ £1.50 each *
I wish to subscribe to set no(s) @ £13.50 *

I enclose cheque/money order for £

*Tick as required/Cheques to be made payable to IPC Business Press Ltd.

Name

Address

Company registered in England. Registered address, Dorset House, Stamford Street, SE1 9LU England. Registered Number 677128

APPOINTMENTS VACANT

DISPLAYED APPOINTMENTS VACANT: £6.08 per single col. centimetre (min. 3cm).


LINE advertisements (run-on): 86p per line (approx. 7 words), minimum three lines.

BOX NUMBERS: 35p extra. (Replies should be addressed to the Box number in the advertisement, c/o Wireless World, Dorset House, Stamford Street, London, SE1 9LU.)

PHONE: Allan Petters on 01-261 8508 or 01-261 8423.

Classified Advertisement Rates are currently zero rated for the purpose of V.A.T.

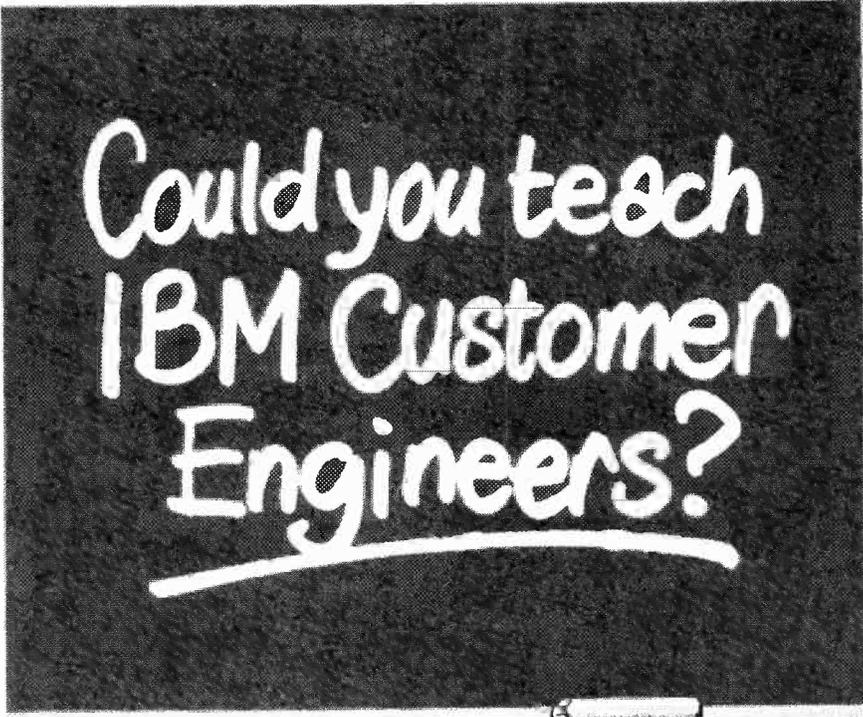Advertisements accepted up to 12 noon Wednesday, February 5th for the March issue subject to space being available.



Could you teach
IBM Customer
Engineers?

We have a number of opportunities for instructors to train our customer engineers to service and maintain data processing equipment including the latest 370 Systems and Software.


If you're an experienced or potential instructor with a background in software and/or electronics, educated to HNC, C & G standard or perhaps you've had similar service experience – now's the chance to find out more about these secure, well paid positions, based in NW London. Salaries start from £3000 and career development prospects and training are excellent.

If you are interested please write to:
Anne Dare, IBM United Kingdom Limited,
389 Chiswick High Road, London W4 4AL.
Quoting ref: WW/92418.

IBM

Radio/Electronics Officers

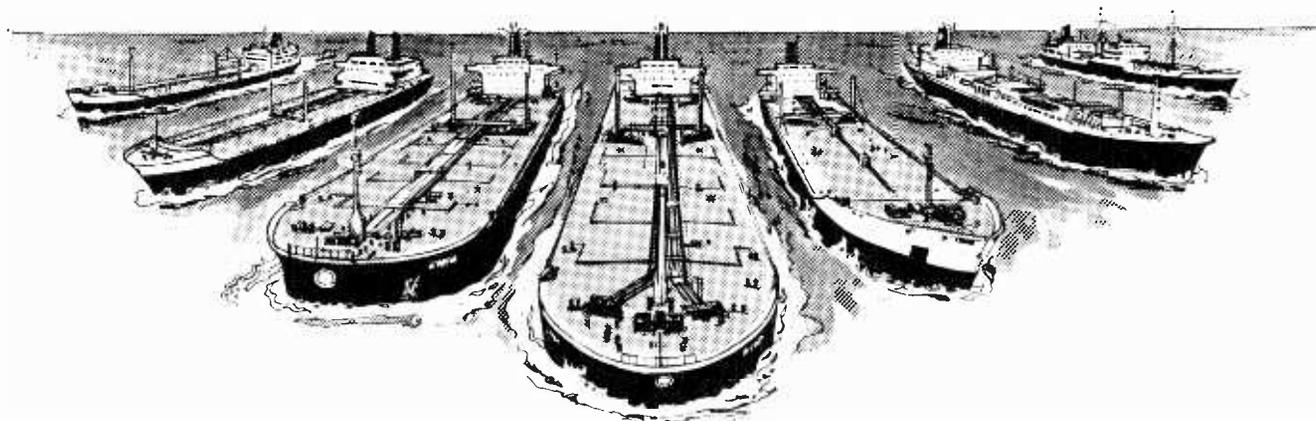Does it make sense to settle for second best?



When you're thinking about your family's future, it would be wise to think of Shell. Whether you're in the service now or ashore for the time being, you will already know a lot about us. Our British flag fleet of about 80 ships (with more on the way) is widely diversified, carrying many different cargoes—bitumen, luboils, crude, LNG, chemicals and black and white products. That means that you don't have to be stuck in one particular kind of tanker for long periods. You can move up and move around with equal familiarity. Our large and increasing investment in

training underwrites our determination to ensure that we will achieve our intended service periods of 4½ months, and underlines our confidence in the future of the Fleet. When it comes to pay you'll find our salaries are highly competitive. Providing you are holding current certificates (PMG 1 or 2 or MPT and Radar Maintenance) you will earn between £3207 and £6390. Your experience and qualifications will determine the point at which you can enter this scale. Leave too is generous—15¼ days for each month served. All Officers are members of the company

pension scheme and certificated officers can take their wives to sea whenever they wish and for this purpose wives are eligible for two free air passages a year. We will be pleased to tell you all about the extra benefits that Shell can offer you as a Radio/Electronics Officer in our fleet. Write or phone, reversing the charges:



Shell Tankers (UK) Limited,
STP/13, (WW/2/75)
Shell Centre,
London SE17PQ.

Tel: 01-934 4172 or 3968.

Radio Operators. How to see more of your wife without losing sight of the sea.



Join the Post Office Maritime Service. We have openings for Radio Operators at several of our coastal stations.

The work is just as interesting, just as rewarding as aboard ship, but you get home to see your wife and family more often. You need a United Kingdom General or First Class Certificate in Radiocommunications, or an equivalent certificate issued by a Commonwealth Administration or the Irish Republic.

Starting pay for a man of 25 or over is £2,270, plus cost of living allowance with further

annual increases after that. Though we're happy to take people from 19 up.

In addition to your basic salary, you'll get an average allowance of £450 a year for shift duties and there are opportunities for overtime.

Other benefits include a good pension scheme, sick pay and prospects of promotion to Senior Management.

For more information, write to: ETE Maritime Radio Services Division (L531), ET 17.1.1.2., Room 643, Union House, St. Martins-le-Grand, London, EC1A 1AS.

Post Office
Telecommunications

GOVERNMENT COMMUNICATIONS
HEADQUARTERS

RADIO TECHNICIANS

Applications are invited for posts in the London area.

Applicants must be at least 19, have had two years practical workshop experience, and hold

either C & G Telecomms Technicians Intermediate Certificate or equivalent technical qualifications or GCE 'O' Levels in English Language, Maths and Physics.

Salary is from £2,094 at age 19 to £2,974 including London Weighting Allowance and Cost-of-Living Supplements as appropriate. Posts are unestablished, but opportunities exist for establishment.

Applicants must be British, born of British parents and have resided in the U.K. for the last ten years.

APPLY TO:

Recruitment Officer, GCHQ, Block 2, Government Buildings, Eastcote Road, RUISLIP, Middx. HA4 8BS.

[4382

The Royal Fleet Auxiliary requires

Radio Officers

with 1st Class PMG or MPT General Certificate or (with previous experience) 2nd Class PMG Certificate and DOT Radio Maintenance Certificate.

Basic rates of pay at entry depend on experience e.g. less than six months sea service £2,312; over six months sea service £2,570. These rates are increased to take account of qualifications held.

Regular increments are awarded for Company service thereafter and there are excellent prospects for promotion into the senior grade with salaries rising to £6,156 per annum.

- * Leave 183 days per annum served.
- * Study leave on full pay.
- * Generous sick leave and welfare arrangements.
- * Non-contributory personal pension scheme.
- * Special training courses on full pay.
- * Opportunities for wives to travel.

The Royal Fleet Auxiliary is a career service offering an interesting and exciting way of life to young men of above average ability who seek a more challenging technical job at sea.

For further details write to:—
The Careers Office, Royal Fleet Auxiliary, DGST(N) 74A, Room 603, Empress State Building, London SW6 1TR. Or phone:—01-385 1244 ext. 2192.





Communications and Control Engineering

MIDDLE EAST

BP seek the following staff for service with Abu Dhabi Marine Areas Ltd. The work involves the maintenance of comprehensive telecommunications, instrumentation and computer-based telemetry systems, which are being installed as part of a major development programme for large-scale offshore oil production in the Arabian Gulf. Starting salaries indicated are presently free of tax and include provision of an annual service benefit in lieu of pension.

Control Engineer Offshore Telemetry

£7,500-£8,500 net p.a.

Based on a large offshore platform complex, he will be responsible for maintaining a computer-based remote control and supervisory system (dual Argus 500 computer installation, Ferranti 40,000 drive units and outstations, colour visual display units). Applicants, under 35 years of age, should have at least 7 years' experience in telemetry including 3 years working with similar systems. Preferred qualifications are those leading to Chartered Engineer, though a lower standard could be accepted if the candidate has had particularly relevant experience. Some knowledge of transducers and process control instrumentation is required. Preliminary specific training can be provided. Reference ZH.966.

Control Engineer Offshore Process Instrumentation

£7,500-£8,500 net p.a.

Based on a large offshore platform complex, he will head a small team of technicians in the maintenance of process control instrumentation (essentially pneumatic, but including electronic and hydraulic) covering gas/oil separation, water treatment and pumping, power generation and oil well-heads. Applicants, having HND/HNC and preferably under 35 years of age, should have at least 10 years' relevant experience in the oil refining or petrochemical industries. Some knowledge of TDM telemetry systems is required. Preliminary specific training can be provided. Reference ZH.967.

Control Engineer Computers

£8,500-£9,500 net p.a.

Based on the Abu Dhabi mainland, this specialist Engineer is to head the computer group which is responsible for the effective maintenance and operation of a number of Argus 500 machines located on large offshore platform complexes and used in conjunction with remote control and supervisory telemetry systems and associated display and data logging functions.

Technical leadership in the overall integration of these systems, in fault diagnosis and problem solving, is especially important. Applicants under 35 years of age should have had at least 5 years' experience with process control computer maintenance and operation, including 2 years in maintenance of Ferranti computers and their peripherals. Preferred qualifications are those leading to Chartered Engineer, though a lower standard could be accepted if the candidate has had particularly relevant experience. Reference ZH.968.

Telecommunications Technician Das

£5,500-£6,500 net p.a.

Based on Das Island in the Arabian Gulf, he will be responsible for maintaining HF, VHF and UHF, SSB, FM and AM single and switched channel radio equipment, radar, echo-sounders and marine electronic equipment, general audio systems and cinema projectors. Applicants, having OND/ONC or equivalent and aged 25-35, should have at least 5 years' experience in maintaining equipment as listed above. Knowledge of broadband radio systems and telephone multiplex or telephone exchanges would be advantageous. Reference ZH.969.

Telecommunications Technicians Rig/Marine

£6,500-£7,500 net p.a.

Based on the Abu Dhabi mainland, these two technicians will work within a team responsible for maintaining HF, VHF and UHF, SSB, FM and AM single and switched channel radio equipment, broadband microwave radio systems and associated multiplex equipment (up to 36 channels), MF radio beacons, small telephone exchanges and related line plant. Applicants, having OND/ONC and aged 25-35 years of age, should have at least 5 years' experience in maintaining most types of equipment listed above. Additional experience with teleprinter systems would be advantageous. Reference ZH.970.

Telecommunications Technicians Offshore

£5,500-£6,500 net p.a.


Based on a large offshore platform complex, these two technicians will be responsible to an engineer located on the mainland for, mainly, first line maintenance of the equipment listed under post reference 970 above, and should have similar qualifications and experience. Reference ZH.971.

All posts carry staff status and are offered as three-year (extendible) engagements. Terms include incremental salaries presently free of local tax, plus the usual benefits of employment with a major British oil company. Home leave is granted on full pay with fares paid to UK. Good sports and recreational facilities are provided on Das Island and the mainland. Offshore and Das Island posts are on an unaccompanied basis, with messing and air-conditioned accommodation provided free. Married and single accommodation at nominal rental (though without free catering) is provided on the mainland. Duty tours/UK leave entitlements are: mainland twelve months/60 days; Das Island 70 days/20 days; with very generous arrangements for offshore personnel.

Please send complete personal history, quoting the appropriate reference, to:

The Manager, Central Recruitment,
The British Petroleum Company Limited,
Britannic House, Moor Lane, London EC2Y 9BU
or phone 01-920 6344 for an application form.

4012

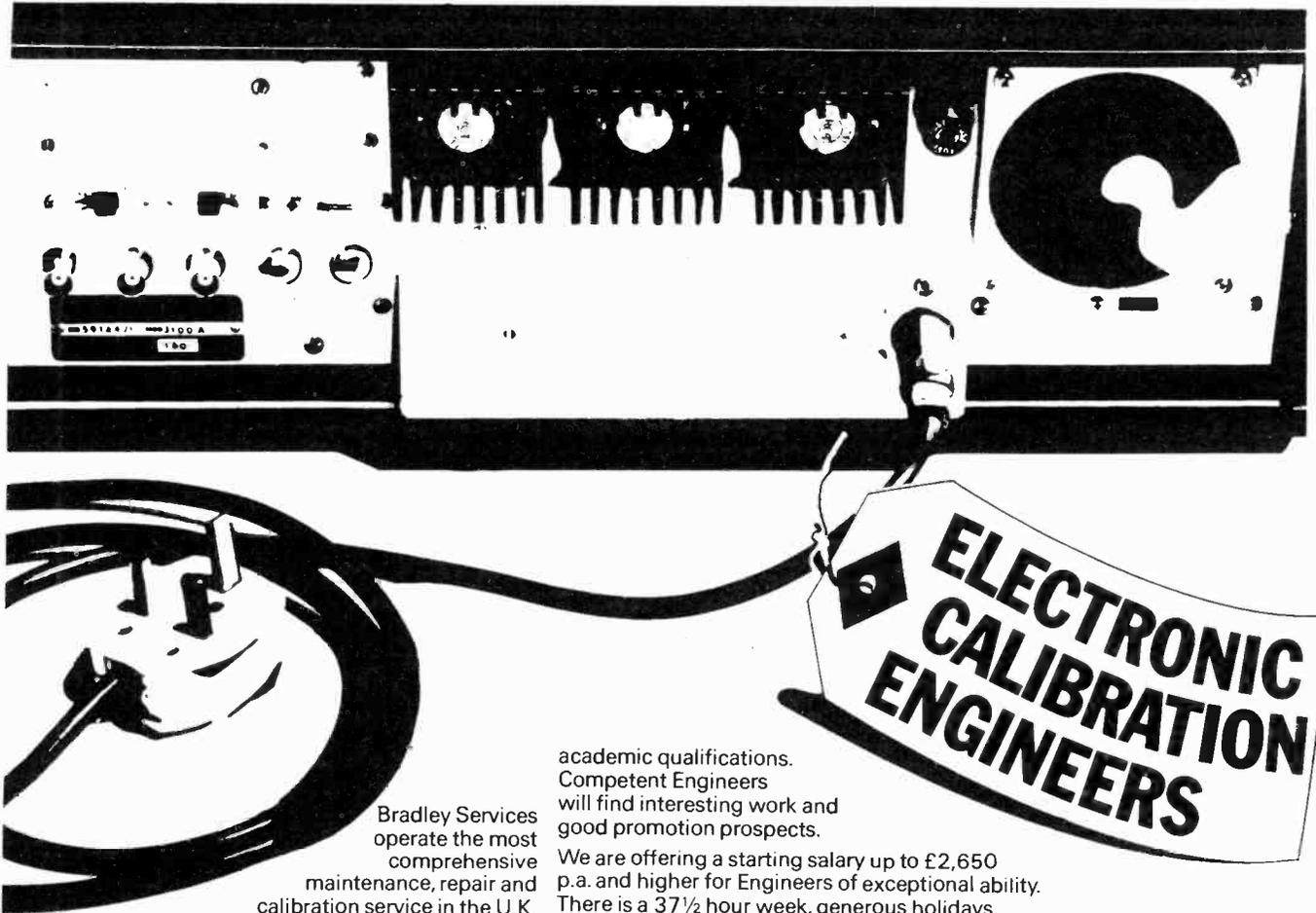

**ELECTRONIC
CALIBRATION
ENGINEERS**

Bradley Services operate the most comprehensive maintenance, repair and calibration service in the U.K.

New products and more service work means we need extra Electronic Technicians and Engineers experienced in maintaining a wide range of telecommunications, radar, microwave, ECM systems, and all types of electronic test equipment. We count practical experience more important than

academic qualifications. Competent Engineers will find interesting work and good promotion prospects.

We are offering a starting salary up to £2,650 p.a. and higher for Engineers of exceptional ability. There is a 37½ hour week, generous holidays, subsidised restaurant, the Lucas pension scheme and other fringe benefits.

For more details, please telephone, call or write to: R.F. Honnor, Personnel Manager, G & E Bradley Ltd., Electral House, Neasden Lane, N.W.10. 01-450 7811.

**BRADLEY
electronics**

4366

A LUCAS COMPANY

RADIO MAINTENANCE ENGINEER

An opportunity to work in a very small team in the Central Office of Information at Hercules Road, London SE1, as a Maintenance Engineer in their Overseas Press and Radio Division. The post is graded Assistant Information Officer. Applicants with suitable qualifications should have at least 5 years' experience which must include a thorough knowledge of mains and battery operated professional tape recording equipment and ancillary studio equipment. The ability to construct all kinds of audio amplifiers, equalisers and relay circuits, and experience in faultfinding in electromechanical equipment are also necessary. Knowledge of Post Office line plant would be an advantage.

Salary on a scale rising to £2,982 plus £410 London Weighting and £229.68 threshold payments. Non-contributory pension scheme. Please send postcard for full details and application form to Central Office of Information, Atlantic House, Room 53, Floor 1, Holborn Viaduct, London EC1N 2PD, quoting reference number COI/OPR/11/. Closing date for completed forms 5 February 1975.

[4397

ELECTRONIC VACANCIES

Engineers

Draughtsmen ● Designers

Service and Test Engineers

Technicians ● Technical Authors

Sales Engineers

£1,600-£5,000 pa
Permanent or Contract



01-387 0742
**MALLA TECHNICAL
STAFF LIMITED**
376 Euston Rd., London NW1 3BG

195

Electronic Engineers and Instructors: potent opportunity at Hemel Hempstead

Join the Company that invented the world's first electronic calculator, now expanding continuously as British leaders in both calculators and more complex systems. As you would expect from part of the Rockwell Organization, world famous for space and microelectronic technology, salaries are high while further benefits are extensive. And inevitably, there are few environments which can equal the career potential provided.

ELECTRONIC ENGINEERS can be at anything from Junior Technician level (day release training is available where appropriate) to a level where full qualifications and experience have been gained.

Instructors can have either: (a) C & G (Electronics) with a thorough knowledge of basic electricity plus teaching experience—for training Engineers in basic electricity and electronics; or (b) with qualifications/experience as specified in (a) plus calculating/computing techniques experience—for training engineers on Company products such as electronic and programmable calculators and business systems experience.

Please phone or write for more information and your application form to:

Mr. D. D. Davies
Sumlock Anita Ltd.,
1 Frogmore Road,
Apsley, Hemel Hempstead, Herts.
Tel: Hemel Hempstead 61771.



Sumlock Anita Ltd.
Rockwell International

4365

UNIVERSITY OF SOUTHAMPTON INSTITUTE OF SOUND AND VIBRATION RESEARCH

ELECTRONICS TECHNICIAN

required by the Wolfson Unit for Noise and Vibration Control to work in support of consultancy teams investigating a wide range of noise and vibration control problems.

The Unit's work involves the use of sophisticated noise measuring instruments and other electronic equipment which the technician appointed will operate, maintain, and precisely calibrate, and previous experience would be an advantage. He may be involved in laboratory investigations or required to take responsibility for the operation of equipment on field work involving his absence from base for short periods.

Candidates should have a recognised qualification in electronics or electrical engineering (O.N.C./H.N.C. or equivalent), and relevant experience in applied electronics.

The appointment, for one year initially, will be made at Grade 5 (non-established) on salary scale £2,439-£2,895 per annum.

Applications, stating age, qualifications and experience and giving the names of two referees should be sent to the Administrative Secretary's Section, The University, Southampton SO9 5NH, quoting reference 268/T/WW.

[4369]

Medical Physics Technician

required for servicing hospital and home-based kidney machines. Considerable travel in South East England, and there are opportunities for research. Previous experience of kidney machines is not essential but proven ability in this or similar fields of engineering is of greater importance. Academic achievement should at least be ONC or equivalent standard. Current driving licence essential. Salary according to qualifications and experience.

Apply, Personnel, Guy's Hospital, St. Thomas Street, London SE1 9RT.

Telephone: 01-407 3662 Ext. 68.

[4015]

Electronic Lecturers/Trainers

TELECOMMUNICATIONS

Principal Lecturer **c£4,000**

To investigate, develop and implement specialist software training courses to provide software training associated with processor systems. Desirable qualifications are a degree or equivalent in a numerate discipline together with considerable experience of software systems and programming in machine codes and high level languages.

Senior Lecturers & Lecturers **c£3,200**

To teach on a number of advanced courses on topics which include one or more of the following systems. Electromechanical electronic and digital switching systems. Time will be made available for course preparation and learning new systems as the need arises.

Desirable qualifications are a degree or possibly H.N.C. or Full Tech. Certificate in Electronics or Telecommunications together with considerable background experience in telecommunications design, development or installation.

These appointments are located in the East Midlands where the housing situation is good and generous relocation expenses will be paid where appropriate. Our client can also help to obtain mortgage.



PERSONNEL ADVERTISING LIMITED

Write in the first instance to David Macmillan, Personnel Advertising Limited, 22 Red Lion Street, London WC1R 4PX stating any companies to whom you do not wish your application forwarded and quoting reference GRS 309.

[4380

ELECTROSONIC LTD.
S.E. LONDON

Senior Test Engineer/Supervisor

Salary £2,600-£3,400

Electrosonic Ltd. a leading company in the rapidly expanding fields of lighting control, audio and audio-visual systems require a Senior Test Engineer.

Duties include the organisation and running of a production test shop employing 8-10 test engineers, the introduction and programming of automatic test equipment and the training of junior Test Engineers.

A capacity for work, a sound theoretical circuit knowledge, an appreciation of production engineering and organisation together with previous experience essential.

The company offers an attractive working environment, interesting work and excellent conditions of employment.

Apply: **Electrosonic Ltd.,
815 Woolwich Road,
Charlton, SE7 8LT.
Telephone: 01-855 1101.**

[4379

THE OPEN UNIVERSITY

ELECTRONIC ENGINEER/TECHNICIAN GRADE 6

We are looking for a person to design electronic equipment for use in teaching and research. Applicants should have experience of both digital and analogue circuit design. A degree in electronics is desirable, but applicants with H.N.C. or H.N.D. will also be considered. The person appointed will be expected to give design advice to academic and technical staff where necessary. Routine work with students is not part of the job function.

The appointment will be on the Technician Grade 6 Scale: £2,844 to £3,450 per annum.

Application forms and further particulars are available from the Personnel Manager (EE6), The Open University, P.O. Box 75, Walton Hall, Milton Keynes, MK7 6AL, and should be returned as soon as possible.

[4375

Electrical/Electronic Mechanic

required by the Trinity House Lighthouse Service to work in a small team involved in the prototype construction and testing of electrical/electronic equipment, including occasional travel within the U.K. to assist with field work.

Pay commences at £38.26 plus £3.44 bonus plus £4.40 threshold pay per week, and assistance may be provided with further technical education.

For further details and application form apply to:—

The Establishment Officer,
Trinity House Lighthouse Service,
Tower Hill,
London EC3N 4DH.

or 'phone 01-480 6601 Ext. 245.

[4403]

ROYAL FREE HOSPITAL
HAMPSTEAD

MEDICAL PHYSICS TECHNICIAN (ELECTRONICS)

A vacancy exists in the Electronics Workshop of this brand new major Teaching Hospital. Applicants should hold the final City and Guilds or an equivalent qualification. Some knowledge of analogue and digital circuit techniques desirable. Salary on a scale £2,314—£3,004 dependent on qualifications and experience.

Application forms to be returned by 15th February 1975, from the Personnel Department, Royal Free Hospital, 21 Pond Street, London, NW3. Tel: 01-794 0431.

[4402]

Electronics Engineers up to £5000

Many jobs which would suit you down to the ground – either in the U.K. or overseas – are never advertised. Yet it will cost you nothing whatever to give yourself the opportunity to be considered for them.

Join the Lansdowne Appointments Register – used by hundreds of employers to select electronics engineers. You have nothing to lose, everything to gain – and it's all conducted in strict confidence. So post the coupon – find out exactly how you can make use of a service which is all the more valuable for being free!

To: Stuart Tait, Lansdowne Appointments Register, Design House, The Mall, London W5 5LS. Tel: 01-579 6585 (anytime – 24 hour answering service).

Please send me further details.

Name.....

Age (20-45 only)

Address.....

.....

ww/23/1

Lansdowne
Appointments Register

97

PHILIPS CROYDON Electrical Design Engineer

An Engineer is required for electrical design and development of new mass production TV receivers, at Philips Croydon, an ultra modern TV manufacturing plant, within the international Philips Group of Companies.

The vacancy would suit an experienced graduate level electrical engineer, aged 23-32, wishing to broaden his career potential.

Good theoretical knowledge of circuits and experience of TV design is necessary.

Excellent conditions of employment apply, including more than 4 weeks holiday and annual bonus. Starting salary will match successful applicant's experience and qualifications. Substantial assistance will be provided towards removal costs where appropriate.

Applicants should submit brief details to:

Mr. L. H. Lewis, Personnel Officer, Phillips Croydon, Commerce Way, Purley Way, Croydon CR9 4JA, Telephone: 01-688 7766, ext. 2286.

[4383]



PHILIPS

Merton, Sutton and Wandsworth Area Health Authority (Teaching) Wandsworth & East Merton Teaching District ST. GEORGE'S HOSPITAL, LONDON, SW1 OPPORTUNITY IN ELECTRONICS

A vacancy exists in the Electronics Section of the Department of Medical Physics. The work involves the design, development and manufacture of a wide variety of medical and research instruments; in particular, the solution of problems arising from the use of cardiac pacemakers. Experience with digital integrated circuits very desirable. The salary is on the M.P.T. II scale, which is £2,727-£3,516 p.a. plus Threshold. Minimum qualification H.N.C. or the M.P.T. III scale, which is £2,316-£2,943 p.a. plus Threshold. Minimum qualification O.N.C. The salary point on the above scales depends on experience and qualifications.

Further information and application forms are available from the

Hospital Secretary's Office,
St. George's Hospital, Hyde Park Corner,
London SW1X 7EZ.

[4395]

Yorkshire
Regional Health
Authority

Regional Medical Physics Unit

MEDICAL PHYSICS TECHNICIAN (GRADE III)

A Medical Physics Department is to be set up at Grimsby, as an integral part of the new District General Hospital now under construction. In the first stage, a pilot scheme is to be operated with one Medical Physics Technician Grade III. Initially, the service, mainly relating to Radioactive Isotopes, will be provided at Grimsby General Hospital to the Consultant Staff in the District. Subsequently, the variety of work will be largely dependent upon the demands made upon the Service and the experience and initiative of the person appointed.

Applications are invited from persons qualified to H.N.C. standard in Medical Physics or Electronics, or equivalent, with three years' relevant experience, and preferably in hospital work. Persons with O.N.C. qualifications and broader experience will also be considered.

Starting salary within the range £2,190 to £2,355 rising by annual increments to £2,817 plus threshold of £13.92 per month.

The person appointed will work under the supervision of a Physicist and will receive training as necessary to provide the physics service.

Application forms to be obtained from and returned to the Regional Administrator, Yorkshire Regional Health Authority, Park Parade, Harrogate, HG1 5AH, within 14 days of the appearance of this notice.

[4378]

WEST BERKSHIRE HEALTH DISTRICT

AUDIO ENGINEER (SCIENTIFIC OFFICER)

to join busy group of surgeons, scientists and audiology technicians working with child and adult patients. Duties include running small well-equipped electro-acoustic laboratory, calibrating and maintaining audiometric instruments, assessing performance of hearing aids, with occasional CCTV, tape-recording and apparatus design jobs. Applicants should have HNC or degree (in physics, applied physics or electrical engineering) and relevant experience would be an advantage. Salary on scale £1,689-£2,994 + threshold payments (approx. £229 p.a.).

Further details from Dr. R. J. Bench, Audiology Unit, Royal Berkshire Hospital; applications to Hospital Secretary, Royal Berkshire Hospital, London Road, Reading.

[4377]

Telecommunications Engineer

Commercial Cable Company have a number of vacancies for Engineers experienced in telephony and data transmission. Salary according to experience and qualifications but not less than £3,700 per annum. Please telephone Chief Engineer, Commercial Cable Company. Telephone: 01-251 1577 for appointment.

[4399]

Harrow College of
Technology & Art

FILM AND TELEVISION TECHNICIAN

up to £2,677

A Technician/Engineer in Television and Sound is required for a post in the Film and Television Department of the School of Photography. Duties will include the technical operation and routine maintenance of a CC TV Studio requiring electronic and mechanical skills and knowledge in the television field.

Reasonable removal expenses reimbursed, lodging allowance of up to £6 per week and up to £500 towards legal and estate agents fees may be payable.

Good conditions of service including pension.

For more information and an application form telephone 01-864 4411 Ext. 31 or write to Harrow College of Technology & Art, Northwick Park, Watford Road, Harrow.

[4018]

**WEST SUSSEX COUNTY COUNCIL
INSTRUCTOR**

**Industrial Training Centre, College Road,
Crawley**

The person appointed will be required to give industrial training in electronics to First Year "Off the Job" trainees at both Craft and Technician level. Candidates for this post should possess qualifications of at least an appropriate Ordinary National Certificate level. The present salary scale is £1,900 x £54(3) x £57(9) to a maximum of £2,575 (under review) plus London Allowance. The commencing point on the scale is determined by qualifications and previous experience. Application forms and further particulars may be obtained from the Manager (Electrical) at the above Centre. Requests for application forms should be made within 14 days of this advertisement.

[4367]



University of Wales Institute of Science and Technology

**Department of Applied Physics
and Electronics**

**M.Sc./DIPLOMA COURSE
IN ELECTRONICS**

Applications are invited for places in the full-time one-year M.Sc./Diploma course in Electronics, commencing October 1, 1975.

Further details may be obtained from the Academic Registrar, UWIST, Cardiff CF1 3NU.

Application forms should be completed and returned to the College as soon as possible.

4371

**THE UNIVERSITY OF
MANCHESTER
INSTITUTE OF SCIENCE
AND TECHNOLOGY
DEPARTMENT OF
OPHTHALMIC OPTICS
ELECTRONICS
TECHNICIAN
(GRADE III)
(REF: 0/172/AU)**

Required in the electronics workshop of the visual sciences research section of the above department. The duties will be varied over a wide range including equipment repair, maintenance and prototype wiring and testing. Opportunities will exist for gaining experience in computer programming and electronic design. A sound knowledge of electronic techniques is essential and some experience in workshop practice would be an advantage. Qualifications required are O.N.C. or equivalent together with relevant experience.

Salary within the scale: £2,013-£2,343 per annum.

Write for application forms, quoting reference, to the Registrar, U.M.I.S.T., P.O. Box 88, Manchester, M60 1QD, to whom completed applications should be returned by 3rd February, 1975.

[4370]

**ARE YOU
LONDON'S
TOP
VIDEO
ENGINEER ?**

We need the very best there is to take complete charge of the Engineering Side of our busy Video Company.

We are probably the country's biggest independent systems house and already have top Grade Engineers so are looking for someone really special, capable of organisation and above all Technically Sound.

We are prepared to pay a super salary with fringe benefits, car, etc. commensurate with the responsibility of this situation. If you are capable of hard work and want to get right to the top in an Expanding Business this is the job for you. This sort of opportunity only comes once in a lifetime. Please contact:—


Ian Crammond, Managing Director,
Teletape Video,
76, Brewer Street,
London W1R 3PH.
Tel: 734/1319 434/1267.

[4394]

**KING'S COLLEGE LONDON
Department of
Electrical and Electronic Engineering
ELECTRONICS
TECHNICIAN**

Interesting new position for electronics technician, Grade 5, preferably with interest and experience in digital electronics. Some circuit design ability essential. The post offers good opportunity to acquire experience in computer systems. Four weeks annual holiday. Contributory Pension scheme. Salary on scale £2,849—£2,939 rising to £3,305 p.a. including London weighting. Apply in writing giving details of age, experience and qualifications to Head Clerk, (Ref. WW 138749) King's College London, Strand WC2R 2LS.

[4398]

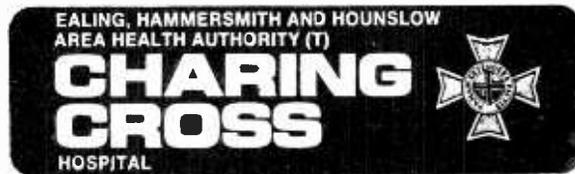

DEPARTMENT OF MEDICAL PHYSICS

Electronics Technician (Grade II)

Applicants should have a wide experience of analogue equipment and preferably a good working knowledge of digital techniques. Knowledge of Medical equipment an advantage but not essential.

ALSO

**Graduate Electronic
Engineer**

Knowledge of medical equipment an advantage but not essential. Whitley Council conditions of service apply. Salaries for both posts within the range of £1,689-£3,390 p.a. plus London Weighting at £126 p.a. (under review) and current Threshold payments. Point of entry on scale dependant upon qualifications and experience. Temporary single accommodation may be available for single men.

Application form and job description available from Mr. C. J. Hill, Personnel Department, Fulham Palace Road, Hammersmith, London W6 8RF. Te: 748 2050 Ext. 2992. Please quote ref. 106. Forms should be returned by 4th February 1975.

[4364]

INSTITUTE OF GEOLOGICAL SCIENCES

**Professional and Technology
Officer Grade IV**

Applications are invited for appointment as a Professional and Technology Officer Grade IV in the Geomagnetism Unit of the Institute.

DUTIES

The maintenance of equipment for the continuous monitoring of the Earth's Magnetic Field, to make the necessary calibrations and absolute observations and to assist in their reduction. There will be opportunities to assist in new development and proving.

Direct experience is not required as appropriate training will be given. Some electronic experience is, however, essential. The successful applicant may undergo a period of training at the Unit's geophysical observatory at Eskdalemuir, Dumfriesshire, prior to appointment to a permanent station.

QUALIFICATIONS

- (a) ONC or equivalent, in electrical engineering.
- (b) All candidates must have served an apprenticeship, or have had equivalent training, appropriate to the duties of the post, plus, normally, at least 3 years of suitable engineering experience (preferably assembly and testing of electronic equipment).
- (c) Ability to drive would be an advantage.

SALARY

£1845 (age 21)—£2260 (age 27 or over on entry)—£2625. In addition Cost-of-Living supplement of £19.14 per month is paid. Non-contributory superannuation arrangements are available.

Application forms and further particulars, including the location in the UK of the Institute's geophysical observatories, may be obtained from Establishments, Institute of Geological Sciences, Exhibition Road, London SW7 2DE. Please quote Ref. ESK/75.

Closing date for applications: 22 January, 1975.

NATURAL ENVIRONMENT RESEARCH COUNCIL

4407

AUDIO/VISUAL TECHNICIANS

(TWO POSTS)

The Commonwealth Institute has vacancies for two Audio Visual Technicians as follows:—

(A) A/V Officer to head small A/V Unit under Chief Exhibitions Officer.

The successful applicant will possess extensive knowledge of A/V equipment (slide/tape, video, cine, etc.) and have practical experience in the operation and maintenance of such equipment related to exhibitions. The vacancy offers a varied and interesting position in congenial atmosphere for a person of initiative.

(B) A/V Assistant with good working knowledge of operation and maintenance of all A/V equipment. Practical experience essential.

Post (A) is graded Scientific Officer with salary range £2,002 by 12 increments to £3,085 inclusive of London Allowance.

Post (B) is graded Technician III with salary range £1,997 by 7 increments to £2,436 inclusive of London Allowance. Both posts attract a cost of living supplement of £19.14 per month.

Good working conditions, 4 weeks' holiday.

Non-contributory pension scheme.

Some weekend working will be obligatory in both posts.

Application forms are obtainable from the Establishment Officer, Commonwealth Institute, Kensington High Street, London W8 6NQ. 01-602 3252.

TECHNICAL OPERATIONS MANAGER

(Television Service)

For the Educational Television Unit at Guildford County College of Technology. To be responsible for the daily operations of a team of technicians concerned with production and presentation of ETV material.

Applicants need a sound knowledge of closed-circuit television systems including colour, together with experience with helical-scan recorders and vidicon cameras. Organising ability, and an interest in the development of television and other audio-visual equipment as teaching aids, of considerable importance.

Salary (including Threshold and Surrey Allowance) £2,275-£2,947 according to age, qualifications and experience.

Application form and details from the Vice-Principal, Guildford County College of Technology, Stoke Park, Guildford.



SURREY
COUNTY COUNCIL

4024

ENGINEERING PUBLICITY WRITER

required for

BBC's ENGINEERING INFORMATION

DEPARTMENT in Central London

Salary according to experience, in the range £4,329-£4,725 rising to £5,319. Pensionable post.

Duties include writing leaflets and booklets, mainly about broadcast reception and drafting reports and letters. Some exhibition work may also be included.

The job requires an ability to write clearly and attractively on technical subjects—both for Engineers and the general public.

Applicants must have experience in the design and layout of printed material, also a good basic understanding of radio theory, television technology and audio reproduction allied to a natural flair for writing and public relations.

Requests for application forms to The Engineering Recruitment Officer, BBC, Broadcasting House, London, W1A 1AA, quoting reference no. 74.E.2417/WW and enclosing self-addressed envelope at least 9" x 4". Closing date for completed application forms 14 days after publication.



4013

RADIO OFFICERS

Do you have PMG I, PMG II, MPT 2 years operating experience?

Possession of one of these qualifies you for consideration for a Radio Officer post with composite signals organisation.

On satisfactory completion of a 7-month specialist training course, successful applicants are paid on a scale rising to £3,096 pa; commencing salary according to age—25 years and over £2,276 pa. During training salary also by age, 25 years and over £1,724 pa with free accommodation.

The future holds good opportunities for established status, service overseas and promotion.

Training courses commence at intervals throughout the year. Earliest possible application advised.

Applications only from British-born UK residents up to 35 years of age (40 years if exceptionally well qualified) will be considered.

Full details from:

**Recruitment Officer,
Government Communications Headquarters,
Room A/1105, Priors Road, Oakley,
Cheltenham, Glos GL52 5AJ
Telephone Cheltenham 21491 Ext 2270**

192

ELECTRONIC TECHNICIAN GRADE III

An electronic technician is required for the Electronics Department dealing with the maintenance of a wide variety of electronics and electro-medical apparatus./Applicants must possess HNC, HND or ONC in electronics or equivalent City and Guilds Certificate./General diagnostic maintenance experience in the electronic field is necessary. Training in maintenance experience in the electronic field is necessary. Training in maintenance of specialised hospital equipment will be given./Salary scale from £2,190 to £2,817 p.a. plus Threshold payment. Additional payments are made if overtime is required./Applications stating age, qualifications and experience, together with two referees should be sent to the Area Works Officer, Coventry Area Health Authority, The Birches, Tamworth Road, Keresley End, Coventry CV7 8NN

COVENTRY

Area Health Authority

4020

ELECTRONIC ENGINEER

aged 25—35 years, with knowledge of Logic and Audio equipment design, required by expanding Group of Companies. Must have H.N.C. or equivalent.

Write or telephone:

Personnel Department

SONTRONIC (C.H.C. GROUP)

LTD.

The Forum, High Street,

Edgware HA8 7HB

Telephone: 01-952 6666

[4022

TOP ARTISTS RECORDING STUDIO

Well established in the heart of Paris have an opening for experienced recording engineer who is also able to do some maintenance on electronic recording equipment. Excellent prospects for a bachelor age about 25. Living accommodation, bachelor flat, will be provided.

Please contact to-day
Loulou Gasté Studios
5 Rue du Bois de Bologne
Paris 16
France

[4386

Electronics Test Engineers: career openings that affect all sorts of people...



... you most of all, naturally. Mainly because, by joining the world's largest exporter of radio-telephone equipment you will inevitably open up for yourself career advantages that very few companies can provide. Pye Telecom is growing at an ever-increasing rate - and the potential for its products has as yet been only fractionally utilised.

But the work you do will also be vital to an incredible number of others. Very frequently, life itself depends on the efficiency of the UHF and VHF equipment you'll be working on. Police, firemen and ambulance staff are a small sample of the extensive range of users. Which explains the exacting specifications of the test procedures in operation - and why previous fault-finding and testing experience is an essential requirement. If it relates to communications equipment, so much the better, but this is not absolutely essential. More important is practical proficiency, which may well have been gained in the armed forces.

Find out more right now by phoning or writing to Mrs Audrey Darkin at:



Pye Telecommunications Ltd

Cambridge Works, Elizabeth Way,
Cambridge CB4 1DW. Tel: Cambridge 58985

A member of the Pye of Cambridge Group

4292

mi MARCONI INSTRUMENTS Ltd. AT ST. ALBANS AND LUTON ELECTRONIC TECHNICIANS

We are a company that manufactures precision electronic measuring instruments and have a range of technical career vacancies within our Production and Engineering departments at St. Albans and Service Division at Luton. To fill these posts we are looking for people with a good electronic background, but not necessarily qualified. Attractive salaries are offered for the right candidates along with the normal benefits of staff employment.

For further information and/or application forms contact John Prodger, **mi** Ltd., Longacres, St. Albans, Herts. Tel:59292.
A G. E. C. Marconi Electronics Company.

4356

LINK ELECTRONIC TEST ENGINEER TV CAMERAS


We are looking for another engineer to join our young team testing and commissioning TV studio equipment.

Link Electronics is a successful, independent company making a complete range of units for TV broadcasting, from monochrome and colour cameras to complete studio systems and Outside Broadcast mobiles. Our modern factory, on the edge of Andover, is currently being extended to help us meet the increasing demand for our products.

For this position formal qualifications are less important than direct experience of similar equipment and this means you are unlikely to be younger than 23. A knowledge of both digital and linear techniques is essential and you should be used to fault finding down to component level.

We offer a competitive salary with above average benefits including subsidised canteen, excellent pension scheme with free life assurance, free health insurance and financial assistance with re-location where necessary.

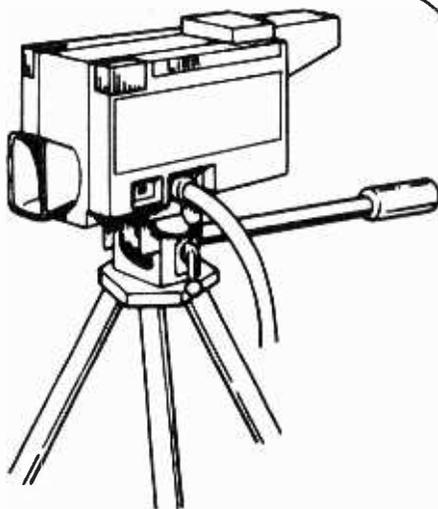Please write or telephone, giving brief details only at this stage, to M. D. Comber.



LINK
ELECTRONICS

LINK ELECTRONICS LTD.
Walworth Industrial Estate,
Andover, Hampshire, England Telephone: Andover (0264) 61345

4411

T.V. Engineers for New Zealand

Are you dissatisfied with your present position, feeling like a change of scene? Do something about it now! Be our guest—come down under and join the Tisco Team, N.Z.'s largest service organisation.

We are in service only and our engineers are all important people, every one of our 30 managers is an ex engineer.

We are now selecting staff to sponsor under the Immigration Scheme to arrive in N.Z. mid 1975.

If you,

- Have 5 years experience, preferably some in colour.
- Single or married with 3 children or less.

write now enclosing a photograph and details of past experience to:-
The Technical Staff Supervisor, Tisco Ltd, Private Bag, Royal Oak,
AUCKLAND, NEW ZEALAND.

[4070

LEEDS CITY COUNCIL Department of Education

Leeds Polytechnic
Educational Technology Unit

TELEVISION ENGINEER

(REF. 13/21)

T.3. £2,187—£2,538

plus Threshold payment

To work with media production team in the operation and maintenance of the colour television studio and related recorded facilities.

Application form (quoting ref. no.) together with further particulars from the Administration Officer, Leeds Polytechnic, Calverley Street, Leeds LS1 3HE. [4023

Radio Technicians

A secure future with Overseas Division of one of the world's largest airlines is within easy reach if you are interested in either aircraft or ground radio and have at least 5 years' experience.

The vacancies are at Heathrow Airport—London.

Starting pay is £49.66 per 40 hour week and there are chances of rapid promotion to £56.04 per week.


Additional benefits include a contributory pension scheme, a first-class sports and social club and opportunities for concessional holiday air travel world wide.

Please write, quoting reference 430/WW/BW, to:

Manager Selection Services, British Airways Overseas Division, PO Box 10, Heathrow Airport—London, Heathrow TW6 2JA

4021

**British
airways**

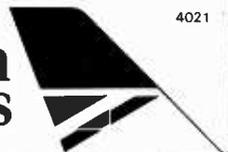

ARTICLES FOR SALE

B. BAMBER ELECTRONICS

20 WELLINGTON STREET, LITTLEPORT, CAMBS.
TEL: ELY (0353) 860185 (TUESDAY-SATURDAY)

TERMS OF BUSINESS: CASH WITH ORDER. ALL PRICES INCLUDE POST & PACKING (UK ONLY). EXPORT ENQUIRIES WELCOME. PLEASE ADD 8% VAT. MINIMUM ORDER £1
CALLERS WELCOME BY APPOINTMENT
PLEASE ENCLOSE STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES 4404

PYE AC10 POWER SUPPLY
240V input, 12V (nominal) at 10amp output, stabilized, fully enclosed, fused, used by tested **£30.00**

TEST EQUIPMENT

MARCONI UHF SIGNAL GENERATOR, TF762B, 300-600MHz, **£50.00**
MARCONI STANDARD SIGNAL GENERATOR, TF867/2, 15kHz-30MHz, **£100.00**
MARCONI TV SWEEP GENERATOR, TF1104/1, **£66.00**
MARCONI VALVE VOLTMETER, TF428C, **£28.00**
MARCONI AMPLITUDE MODULATOR, TF1102, **£35.00**
MARCONI VALVE MILLIVOLT-METER, TF899A, **£30.00**
MARCONI STANDARD SIGNAL GENERATOR, TF144H, 10kHz-72MHz, **£195.00**
WAYNE KERR VHF FREQUENCY STANDARD, 12-channel, **£20.00**
AIRMEC BRIDGE HETERODYNE DETECTOR, Type 775, **£65.00**
AIRMEC SIGNAL GENERATOR, Type 201, 30kHz-30MHz, **£75.00**
AVO PORTABLE TRANSISTOR ANALYSER, Mk II, **£45.00**
HEWLETT PACKARD UHF SIGNAL GENERATOR, Type 614A, 800-2300MHz, **£175.00**
SOLARTRON DIGITAL VOLTMETER, Type LM1420/2, with "TRUE RMS AC UNIT", 10mV-1000V, 5-digit display, new condition, **£400.00**
TEKTRONIC TYPE-526 VECTOR-SCOPE, 240V input, complete but needs slight attention, good external appearance.

Offers please

HIGH-QUALITY SPEAKERS

8 1/2 in. X 6 in. elliptical, 2 in. deep, 4 ohms, inverse magnet, rated up to 10Watts, **£1.50** each, or 2 for **£2.75** (quantity discount available).

ELECTROLYTIC CAPACITORS

AXIAL LEAD AND SINGLE ENDED
MFD 6.3V 10V 16V 25V 35V 50V
22 30p - - - - - 40p
33 - - 30p 35p 40p 40p 45p
47 - - - - - 40p 45p -
100 35p 40p - - 45p 60p -
220 40p 40p - - 50p 75p -
330 40p 45p 60p 75p 95p 95p
470 45p 60p - - 95p - -
1000 - - - 95p 95p - - -
3300 95p 95p - - - - -

PRICES PER PACK OF 5
Trade enquiries welcome for quantity

MAINS TRANSFORMERS

240V in, voltages quoted approx. RMS.
TYPE F27BS (ex Pye F27 base station TX) 500V at 350mA, 6.3V at 8A, **£6.00**.
TYPE 40/2 40V at 2A, **£1.00** each.
TYPE 18/8 18V at 8A, **£4.50** each, carriage 50p.
TYPE 16/6 16V at 6A, 45V at 100mA, **£4.00**, carriage 50p.
TYPE 28/4 28V at 4A, 125V at 500mA, **£4.00**, carriage 50p.
TYPE 63/1 6.3V at 1A, 85p each, 2 for **£1.50**.
TYPE 129 400V at 20mA, 200V at 10mA, 6.3V at 500mA, **£1.25**.
TYPE 70462 250-0-250V, 50-0-50V, 6.3V, £1.75.

RADIO SPARES 500-WATT AUTO TRANSFORMER, 100/110/150/200/220/240/250V tapped input and output, step up or step down facility, ex new equip, **£6.00**

MAINS ISOLATING TRANSFORMER, 375VA, tapped primary, 240V output, new, **£6.00**

MAINS ISOLATING TRANSFORMER, (ex equip), in metal cases, totally enclosed, tapped mains input, 110-240V etc., output 240V at 3A + 12V at 0.5A, **£11.00**.

AS ABOVE, output 240V at 12A + 12V at 3A + 22V at 2.5A, **£27.50**, carriage **£2**.

PLUGS AND SOCKETS

TV PLUGS (metal type) 6 for 50p
TV SOCKETS (metal type) 50p
TV LINE CONNECTORS 5 for 50p
PL259 (PTFE) PLUGS 50p each or 5 for **£2.25**
SO239 (PTFE) SOCKETS 50p each or 5 for **£2.25**
25-WAY ISEF PLUGS and SOCKETS 40p set (1 plug + 1 skt). Plugs and sockets sold separately at 25p each
CANNON Right-angled plugs XLR LNR15 75p
DIN SPEAKER SKTS, 2-pin, 4 for 30p
STANDARD JACK PLUGS, 1/4 in., 4 for 50p
ANDREWS 44AN FREE SKTS (N-TYPE) for FH4/50B or FHJ4/50B cable **£1.00** each
SO239 BACK-TO-BACK SOCKETS **£1.25** each
BNC INSULATED SOCKETS (single-hole type) 65p each

VALVES

QQV03/20A (ex equipment) **£2.10** each
QQV03/10 (ex equipment) **75p** each
2C39A (ex equipment) **£1.00** each
QQV02/6 (ex equipment) **£1.00** each
4X250B (ex equipment) **£2.10** each
4X250B (ex equipment) **£1.50** each
DET-22 (ex equipment) 2 for **£1.00**
EF80 (new) 25p, **EZ81** (new) 25p
ECC81 (new) 30p, **ECC83** (new) 30p

TEST EQUIPMENT

RACAL 125MHz DIGITAL FREQUENCY METER, Type 801R/2, 0.01V to 1V sensitivity, 8-digit readout, new condition, **£275.00**
ROHDE AND SCHWARZ SIGNAL GENERATOR, SMAF, 4-300MHz, AM/FM, attenuation to 0.05 microvolt, deviation and modulation metered, complete, but needs attention, **£300.00**
ROHDE AND SCHWARZ FREQUENCY DEVIATION METER, FMV, AM/FM, 20-300MHz **£300.00**

PYE RADIO-TELEPHONE EQUIPMENT

Cambridge, Westminster, Motofone, Europa series. Send s.a.e. for full details, stating requirements, frequency, channel spacing, etc.

MISCELLANEOUS

MAGNETIC DEVICES PROGRAMMERS, contain 9 microswitches with 9 adjustable drums for period switching (needs slow-motion motor to drive drum) many switching applications **£1.00** each.
ITT HIGH-GRADE ELECTROLYTICS, 6800 mfd at 25V, screw terminals, complete with capacitor clip for vertical mounting, **50p** each (quantity discount available).
MULTICORE CABLE, 1/2" dia, PVC covered, in 22ft lengths with plug and socket fitted, 24 core stranded + 1 screened + 1 twin screened (ideal mobile control lead) **£2.10** each.
TWIN HEAVY DUTY CABLE, PVC-covered, 50/0.25mm, **15p** per metre, or **£10.20** per 100 metre reel.
CURLY LEADS, 4-core telephone-type 18in. closed, approx. 5ft. extended, 2 for **20p**.

TEST EQUIPMENT

ROHDE AND SCHWARZ POWER SIGNAL GENERATOR, SMLM, 30-300MHz, up to 5V output, **£300.00**
GRESHAM LION 625-LINE PULSE/BAR/STAIRCASE GENERATOR, **£25.00**
TEKTRONIX 524D SCOPE, DC-10MHz, **£70.00**

PYE MF TRANSMITTERS

2 X 5B254Ms in final, VFO 340 to 540kHz (can be modded upward), 2 X 5B254Ms in Modulator, cw/mcw (can be modded for AM), units complete, but no PSUs, (supplied with circuits of TX and PSU) brand new, boxed, **£20.00**

We've got prices to put power in your profits

TOSHIBA VALVES

Type	Goods Price
DY87	30.0
DY802	30.0
ECC82	28.0
EF80	29.5
EF183	34.5
EF184	34.5
EH90	31.5
PCC900	24.5
PCC89	40.0
PCC189	41.0
PCF80	31.5
PCF86	39.0
PCF801	42.0
PCF802	40.0
PCL82	39.0
PCL84	34.0
PCL85	39.5
PCL86	41.0
PFL200	55.5
PL36	55.5
PL84	25.0
PL504	60.5

Goods	Type	Price
PL508	AF158	67.0
PY88	AF116	35.5
PY500A	AF117	85.0
PY800	AF118	29.0

SEMI-CONDUCTORS

Goods	Type	Price
AC127	AF178	17p
AC128	AF180	15p
AC141K	AF181	30p
AC142K	AF239	30p
AC151	BA145	20p
AC154	BC107	18p
AC155	BC108	18p
AC156	BC109	20p
AC176	BC113	22p
AC187	BC116	19p
AC187K	BC117	30p
AC188	BC125	20p
AC188K	BC132	30p
AD142	BC135	45p
AD149	BC137	40p
AD161	BC138	38p
AD162	BC142	38p
AF114	BC143	24p

Goods	Type	Price
BC147A	23p	
BC148	23p	
BC149	23p	
BC153	50p	
BC154	42p	
BC157	45p	
BC158	45p	
BC159	45p	
BC173	45p	
BC178B	14p	
BC182L	11p	
BC183L	11p	
BC187	12p	
BC214L	25p	
BD124	25p	
BD131	20p	
BD132	25p	
BD235	25p	
BD237	20p	
BDX32	25p	
BF115	40p	
BF160	26p	
BF167	30p	

Goods	Type	Price
BF173	08p	
BF178	08p	
BF179	12p	
BF180	20p	
BF181	22p	
BF184	12p	
BF185	10p	
BF194	14p	
BF195	18p	
BF196	20p	
BF197	12p	
BF198	12p	
BF200	28p	
BF218	15p	
BF224	70p	
BF258	45p	
BF336	45p	
BF337	49p	
BFX86	52p	
BFY50	£2.40	
BFY52	20p	
BSY52	20p	
BT106	20p	

Goods	Type	Price
BF173	08p	
BF178	08p	
BF179	12p	
BF180	20p	
BF181	22p	
BF184	12p	
BF185	10p	
BF194	14p	
BF195	18p	
BF196	20p	
BF197	12p	
BF198	12p	
BF200	28p	
BF218	15p	
BF224	70p	
BF258	45p	
BF336	45p	
BF337	49p	
BFX86	52p	
BFY50	£2.40	
BFY52	20p	
BSY52	20p	
BT106	20p	

Goods	Type	Price
BU108	£2.10	
BY126	11p	
BY127	12p	
E.1222	30p	
IN60	05p	
MJE340	45p	
OA202	7.5p	
OC71	15p	
OC72	15p	
BU105/02	£2.40	
ZSC1172B	£2.40	
R2008B	£2.00	
R2010B	£2.00	

Goods	Type	Price
TA550	49p	
TBA120AS	£1.00	
TBA120SQ	£1.00	
TBA540Q	£1.75	
TBA560CQ	£2.40	
TBA920Q	£2.90	
TBA990Q	£2.90	
SN76013ND	£1.50	

Goods	Type	Price
IN60	05p	
MJE340	45p	
OA202	7.5p	
OC71	15p	
OC72	15p	
BU105/02	£2.40	
ZSC1172B	£2.40	
R2008B	£2.00	
R2010B	£2.00	

Goods	Type	Price
TA550	49p	
TBA120AS	£1.00	
TBA120SQ	£1.00	
TBA540Q	£1.75	
TBA560CQ	£2.40	
TBA920Q	£2.90	
TBA990Q	£2.90	
SN76013ND	£1.50	

ENT RECTIFIER TRAY ASSEMBLIES

Type	Goods Price	Type	Goods Price
ITH Decca Col.	£4.50	11TAM Philips G8	£4.50
ITN GEC/Sobell	£4.50	TCQ Pye/Ekco	£3.50
2TQ 1400 + 950 Mk II	£1.85	11 TAG ITT/KB	£4.50
2TAK 1500 5 Stick	£2.00	3 TCU BRC 3000	£5.00
2DAF 1500 3 Stick	£1.85	11 TAZ GEC 2010	£5.35
2HD 950 3 Stick	£1.70		

12 MONTHS GUARANTEE

COLOUR TUBES

Type	Goods Price
19" A49/191X	48.00
20" 510DJ22	49.75
22" A56/120X	53.25

FULLY GUARANTEED

PRICES SUBJECT TO 8% VAT. All goods subject to settlement discount of 5% 7 days and 2% monthly. New Price List from 1st. May 1974.



COMBINED PRECISION COMPONENTS (PRESTON) LIMITED
194-200 North Road, Preston PR1 1YP
Telephone: 55034 Telex: 677122

ECONOMISE ON SEMICONDUCTORS

All prices include VAT

- * Lower 741C prices 100+ 24p
- * Plastic 3 terminal Regulators
- * Economical Digital Clock IC
- * Low price DIL sockets

	1+	10+	25+	
709C Op Amp + data 8 pin DIL	34	32	30	
723C Reg. + data 14 pin DIL	65	63	59	
741C Op Amp + data 8 pin DIL	30	28	26	
748C Op Amp + data 8 pin DIL	39	37	35	
NE555 Timer + data 8 pin DIL	65	62	59	
CA3046 Array 14 pin DIL	76	73	69	
TDA1405 Reg. 5V 650mA	100	92	85	
TDA1412 Reg. 12V 500mA	100	92	85	
TDA1415 Reg. 15V 450mA	100	92	85	
BC107, 108, 109	10	9.5	9	
BC182, 184	11	10.5	10	
BC212, 214	12	11.5	11	
HP Red LED 1/8"	18	16	15	
HP Red LED 0.2"	19	17	16	
DIL Sockets,	11	10	9	
low profile	12	11	10	
	13	12	11	

BC109C	11	BZX88C-	1N914	5
BC177	18	3V3-15V	1N4001	5
BC178	18	2N3702	1N4002	5
BF244	24	2N3704	1N4004	7
BF244B	27	2N3708	1N4148	5
BFY51	17	2N3055	48	

TTL Mixed prices

	1+	10+	25+
7400	17	16	15
7402	17	16	15
7403	17	16	15
7404	18	17	16
7405	18	17	16
7410	17	16	15
7413	36	34	32
7420	17	16	15
7442	70	66	63
7447	90	85	80
7473	38	36	34
7474	35	33	31
7476	38	36	34
7486	30	28	26
7490	55	52	49
7492	55	52	49
7493	55	52	49
74121	44	42	40

AY-5-1224 Digital Clock IC, 12 or 24hr, 7 segment or BCD outputs, drives LED Minित्रon. LED displays. Simple interfacing. 16 pin DIL. IC + data + circuits £4.65. HP 5082-7740 0.3" digits £2.00. IC + 4 0.3" digits £12. IC + 4 0.3" digits + transistors + transformer £14.00

TBA810AS 7W Audio Amp, Thermal protection + data + circuit £1.60
TCA940 10W Audio Amp, Thermal protection, current limit + data + circuit £2.60

Carbon film High Stability 1/2W 5% resistors 10 ohm-2m2 1p ea. 10 9p, 100 80p same value.

By return service. Prices include VAT. P & P 8p (UK) overseas at cost. All items new Tl. Motorola, Mullard, SGS etc. SAE lists, enquiries. Data sheets 4p. Colleges etc. supplied.

SILICON SEMICONDUCTOR SERVICES

41 Dunstable Road, Caddington, Luton LU1 4AL

DOUGLAS For Transformers

- ★ Comprehensive stock range
- ★ Rapid prototype service
- ★ Quantity production orders.

Douglas Electronic Industries Ltd.,
Eastfield Road, Louth, Lincolnshire LN11 7AL.
Tel: Louth (05-07) 3643 Telex: 56260

4007

S.I.G.A.

TOROIDAL TRANSFORMERS

- ★ LOW PROFILE
- ★ LOW LEAKAGE FLUX

Especially suitable for Audio Amplifier Power Supplies.

Our comprehensive coil winding service also includes inductors, A.C. and D.C. Current Transformers.

S.I.G.A. ELECTRONICS LIMITED

Sunderland Road, Sandy, Beds SG19 1QY. Tel: Sandy (0767) 81266.

4349

MINI ACCUMULATORS

2 volt MULTI-USE Sealed Lead Acid Rechargeable Cells.
Size L450—1.4" x 1.1" x 0.44".
3 for £1.85 inc. P. & P.
Size GA2—1.7" x 1.3" x 0.5".
3 for £2.35 inc. P. & P.

GARFIELDS, 269 Rye Lane, London, SE15 14017

ENAMELLED COPPER WIRE

S.W.G.	1lb reel	1/2lb reel
10 to 14	£1.90	£1.05
15 to 19	£2.00	£1.10
20 to 24	£2.05	£1.15
25 to 29	£2.10	£1.20
30 to 34	£2.20	£1.28
35 to 40	£2.35	£1.35

All the above prices are inclusive in U.K.

COPPER SUPPLIES

102 Parswood Rd., Withington, Manchester 20
Telephone 061-224 3553

185

WE SELL

CONSTRUCTION PLANS

Phonevision, Television Camera, Police Radar Detector, Voice typewriter, Scrambler, Answering machine, Wireless quarter mike. Plans: £7.50 each.

COURSES

Detective-Electr. \$36.50. Security-Electr. \$43.50. Telephone Eng. \$59.

OVER 750 ITEMS

Ask for Catalogue—Airmailed \$0.75

T. STRIK.

Postbox 618, Rotterdam, Holland.

144

CRYSTALS

Fast delivery of prototype and production military quality crystals. Competitive prices all frequencies; LF crystals a speciality. Details from

INTERFACE INTERNATIONAL
29 Market Street, Crewkerne, Somerset
Tel: (046031) 2578. Telex: 46283.

135

PARTRIDGE ELECTRONICS

MANUFACTURERS OF AUDIO MIXER SYSTEMS

NEW PEAK READING

★ VU METER SYSTEMS

Which gives the advantages normally only associated with PPM systems at much lower cost.

REF. W.W.

21/25, Hart Road, Benfleet, Essex.

(Established 23 years)

143

CARBON FILM RESISTORS—E12 SERIES

High Stab. 1/2W OR 1/4W 5%. 1p, 75p/100, £5-50/1000 (22Ω-1MΩ).

RESISTOR KITS 22Ω-1MΩ E12 SERIES
10E12 KIT 10 of each value (Total of 570) 1/2W, £3-65;
1/4W, £2-85; 25E12 KIT 25 of each value (Total of 1425)
1/2W, £8-35; 1/4W, £8-45.

EQUIPMENT SALE

Regulated power supply modules. New in original packing. ATC 24V/2A, £18. Fenlow ± 1% (1A), with F/Panel, £12-50. NGN Vacuum Meters PRU3 (Used) £15. Marconi D-A Converters TF2402, £20. Code Converter TF2403, £20. Limits Indicator TF2404, £20. HAAKE Const Temp. Water Circulators type F-Junior (± 0.10) Used, £50. Transformers 50V/30A £20. 7-5KV/0-015A, £7. Honeywell Chart Recorders £30. Solarton VF252 Precision Millivoltmeter £35. Solarton CA512 V.S.W.R. Indicators £25. 400V, 250mA Bench Power Supplies £15. Hatfield Ins. PUM1/16 400 cycle Generators £30. Multhead 2PH. Dec. Osc., £30. Many other items available. Please add £1 carriage and 8% VAT.

METAL FILM KITS ALSO AVAILABLE.

CATALOGUE No. 3 (Approx. 2000 Parts) 20p.

C.W.O. P. & P. 10p on orders under £5. Overseas at cost.

B.H. COMPONENT FACTORS LTD
Dept. WW, 61 Cheddington Road, PITSTONE,
Nr. Leighton Buzzard, Beds. LU7 9AQ.
Cheddington (0296) 688448

132

SURPLUS BARGAINS

EASTER LINE ANGUS

chart recorders, model A601R
500-0-500u.a. f.s.d. 110v AC,
as new, with manual. £35.00
(carr. £1)



Kent Chart recorders single point £20, multipoint £30 (£1.50).

A.E.I. 4-stage sequential transistorised electronic timer, many applications, inc 3 channel auto-light flasher (750 watts 240v). Circuits provided for fully interrupted and dim/bright flashing. Modification instructions and mains transformer. £4.50 only (50p).

Printed circuit Kits. £1.25 (30p)
Instant Heat Soldering Irons, 240v 100 watt £2.65 (30p)

Veedor root 4 digit resettable counters 115v AC £1.25 (10p)

AMPEX VIDIO Tape 2" x 1670'. New £9 (50p).

Ferric Chloride 25p lb (20p), 10 lbs for £2.50 (45p).

TELEPRINTER PAPERS and TAPES, 8 1/2" wide, 3-ply carbon, buff manilla 60p (35p), ditto 7-ply NCR, no carbon required £1 (35p). TAPES, 1/8", white £2 per 8 rolls (65p). 1/4" buff £2 per 10 rolls (65p). 1" tape suit Friden, etc. £2 per 7 rolls (65p).

VARIC Transformers 240 volt input. 0-270v output. 2 amp £3.50 (75p), 8 amp £9 (£1).

20 amp £18 (£2), 5 amp 110v input 0-130v output £3.50 (75p).

All prices plus (p&p) total plus VAT 8%.

Large S.A.E. for list.


CASEY BROS., 235 Boundary Rd, St Helens, Lancs.

LOST—BELIEVED STOLEN

—a prototype model of the *Wireless World* noise reducer as sketched below. Dimensions are approximately 15in wide, 3in high and 7in front-to-back. Front panel is brushed aluminium with lettering in black, spun aluminium control knobs and twin VU meters. Cabinet is teak veneered.

Anyone who has seen this unit or knows of its whereabouts please contact the Editor, *Wireless World*, Dorset House, Stamford Street, London SE1 9LU (Tel. 01-261 8425). A reward will be offered for information leading to the recovery of the unit and the apprehension of the persons concerned.

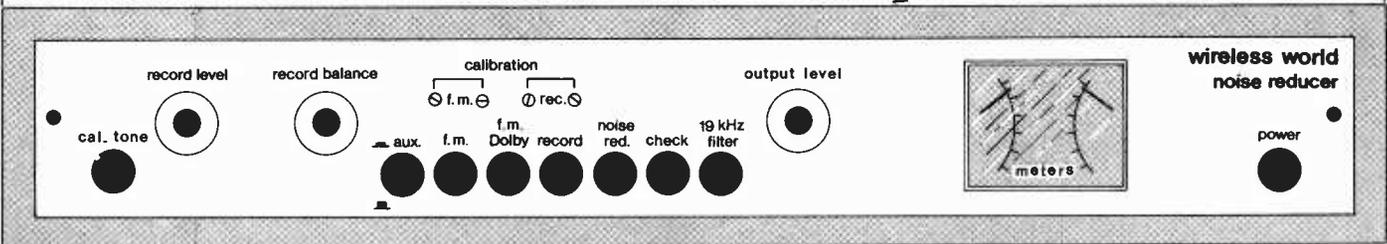teak-looking box 10in approx. front to rear



ARTICLES WANTED

TOP PRICES PAID

for semiconductor and component redundant or excess inventories

P.R.S. ELECTRONICS

126 Headstone Road
Harrow, Middlesex
Tel: 01-965 6864

[34]

CAPACITY AVAILABLE

WANTED SURPLUS

★ FACTORIES CLEARED ★

MACK'S ELECTRONICS
283 EDGWARE ROAD
LONDON WV 1BB
Tel: 01-262 8614

[4014]

OPPORTUNITY FOR GRADUATE IN ELECTRONICS

with some experience of industry to join fast expanding firm specializing in power supply and logic signalling equipment.

ALPHA OMETRIC LTD.,
HOLMDALE, SIDMOUTH, DEVON.
TEL: Sidmouth 5151.

[4319]

ELECTRO-TECH COMPONENTS LTD.

Are buyers of all types of electronic components and equipment. They will be pleased to view clearance stocks anywhere in Great Britain at one or two days notice
and negotiate on the spot!

ELECTRO-TECH COMPONENTS LTD.

315/317 Edgware Road, London, W.2
Tel: 01-723 5667. 01-402 5580

[37]

BUSINESS OPPORTUNITIES

Hair Transplant

For free brochure, clip this ad. and send to:

Room 6
HAIR TRANSPLANT INTERNATIONAL
502 Eccleshell Road, Sheffield

[4224]

APPOINTMENTS

ELECTRONIC EXPERIENCE WANTED. Engineers, technicians or testers required to assist teams preparing electronic equipment manuals. Writing experience preferable but not essential. Interesting work on sites in London and Home Counties. Impex Publications, 37, Alexandra Street, Southend-on-Sea, Essex. [4273]

PROFITABLE and interesting part-time assignment for knowledgeable and enthusiastic Hi-Fi journalist. Apply giving brief details of experience to Box No. WW 4374.

REDIFON TELECOMMUNICATIONS LTD., London, S.W.18, have a vacancy for an enthusiastic, practical man with some experience of Volume Production Testing in the electronics industry. Phone: 01-874 7281 and ask for Len Porter. [4288]

SAFFRON WALDEN COLLEGE, ESSEX. Technician required for Educational Technology Department from 1 March 1975 or as soon after as possible. The technician is responsible for management and maintenance of C.C.T.V. aural and visual equipment, making of aids and resources, demonstrating to students. The salary is on N.J.C. Technicians' division according to qualifications and experience. The post is likely to be for a minimum of two years. Application forms and further particulars from the Principal. Applications should be returned as soon as possible. [4392]

SERVICE ENGINEERS for audio visual equipment needed to supplement our present team. Salary negotiable. Burgess Lane & Co. Ltd., Thornton Works, Thornton Avenue, Chiswick W.4. 994 5752/5953. [4388]

TECHNICAL OFFICER—INSTRUMENT AND MEASUREMENT. An interesting opportunity is offered for a Physicist or electronics/instrumentation Engineer to join a project commissioned by the Medical Research Council on the calibration and measurement of medical ultrasonic equipment. Candidates should have a degree, H.N.C. or equivalent qualification in Physics or Engineering and, preferably, some practical experience in instrumentation work. The project will be located at Guildford and the appointment will run to 30th June 1977 in the first instance. Salary according to qualifications and experience either in Junior Technical Officer scale (£1,494-£2,592) or Technical Officer scale (£2,688-£2,895) plus Threshold payments. Detailed applications in duplicate, giving addresses of two referees to the Secretary, Institute of Cancer Research, 34 Sumner Place, London SW7 3NU, quoting ref. 301/B/538. [4368]

SITUATIONS WANTED

FREE LANCE professional Author/Communications Engineer invites technical writing commissions. Full time employment also considered. Box No. WW 4384.

Classifieds continued on page 90

TAPE RECORDING ETC.

RECORDS MADE TO ORDER

DEMO DISCS
MASTERS FOR
RECORD COMPANIES

VINYLLITE
PRESSINGS

Single discs, 1-20, Mono or Stereo, delivery 4 days from your tapes. Quantity runs 25 to 1,000 records PRESSED IN VINYLLITE IN OUR OWN PLANT. Delivery 3-4 weeks. Sleeves/Labels. Finest quality NEUMANN STEREO/Mono Lathes. We cut for many Studios UK/OVERSEAS. SAE list.

DEROY RECORDS
PO Box 3, Hawk Street, Carnforth, Lancs.
Tel. 2273

[182]

EDUCATIONAL

C AND G EXAMS

Make sure you succeed with an ICS home study course for C and G Electrical Installation Work & Technicians Radio/TV/Electronics Technicians. Telecomms Technicians and Radio Amateurs.

COLOUR TV SERVICING

Make the most of the current boom! Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers.

TECHNICAL TRAINING

Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self-build radio kits. Get the qualifications you need to succeed.

Free details from:
INTERNATIONAL CORRESPONDENCE SCHOOLS
Dept 734, Intertext House, London SW8 4UJ.
Or Phone 01-622 9911 (all hours). [4391]

APPOINTMENTS

Television International Operations Limited

9-11 Windmill Street
London W1P 1HF

A vacancy exists for a Planning and Installation Senior Engineer within the Engineering Department of Television International Ltd. Working with a small group of engineers he would be responsible for the planning and installation of Studio and Outside Broadcast television equipment.

Applications in writing to **Director of Engineering, Television International Ltd., 9-11 Windmill Street, London W.1.**

4029

Classifieds continued from page 89

SITUATIONS VACANT

ELECTRONIC engineer to design equipment for use of the physically handicapped. Knowledge/interest in medical electronics, digital systems, communications, computers preferred. Interesting range of work with small Company in pleasant location. Grange Electronics Ltd., Stone Lane, Wimborne, Dorset. [4408]

HI-FI AUDIO ENGINEERS. We require experienced Junior and Seniors and will pay top rates to get them. Tell us about your abilities. 01-437 4607. [19]

ARTICLES FOR SALE

AARVAK ELECTRONICS. 3 Channel Sound-Light Converters from £17; Strobes, £21; Rainbow Strobes, £133. Free catalogue 98A (W), West Green Road, (Side Door), London N13 5NS. 01-800 8656. [23]

500,000 CAPACITORS-POLYESTER C280-250v & 400v, values from 0.01UF to 2.2UF mixed 100-£1.00, 1000-£8.00. Electrolytics from 1UF to 1000UF, 10v to 63v mixed, 100-£1.50, 500-£6.00. Electronic Mailorder, Ramsbottom, Bury, Lancs. [4396]

COLOUR. UHF and TV SPARES. Colour and UHF lists available on request. 625 TV. If unit, suitable for Hi-Fi amp or tape recording, £6.75, P/P 35p. Television construction cross hatch kit, £3.85, P/P 15p. Bush CTV 25. New convergence panels plus yoke and blue lat., £3.85, P/P 40p. New Philips single standard convergence panels complete, incl. 16 controls, coils, P.B. switches, leads and yoke £5.00, P/P 40p. New Colour Scan Coils, Mullard or Plessey plus convergence yoke and blue lateral, £10.00, P/P 40. Mullard AT1025/05 Convergence Yoke, £2.50, P/P 35p. Mullard or Plessey Blue Laterals, 75p P/P 20p. BRC 3000 type Scan Coils, £2.00 P/P 40p. Delay Lines DL20, £3.50, DLIE, DL1. £1.50, P/P 25p. Lum Delay Lines, 50p, P/P 15p. EHT Colour Quadrupler for Bush Murphy CTV 25 11/174 series, £8.25, P/P 35p. EHT Colour Tripler IIT TH25/1TH suitable most sets, £2.00 P/P 25p. KB CVC1 Dual Stand, convergence panels complete incl. 22 controls £2.75, P/P 35p. CRI Base panel, 75p, P/P 15p. Makers Colour surplus/salvaged Philips G8 panels part complete; Decoder, £2.50, IF incl. 5 modules, £2.25. T. Base, £1.00, P/P 25p. CRT base, 75p, P/P 15p. GEC 2040 panels, Decoder, £3.50, T. Base £1.00, P/P 15p. CRT Base 75p, P/P 20p. B9D valve bases 10p, P/P 6p. VARICAP TUNERS. VHF ITC 1043 NEW £4.50. Philips VHF for Band 1 and 3, £2.85 incl. data. Salvaged VHF and UHF Varicap tuners, £1.50, P/P 25p. UHF TUNERS NEW, Transistorised, £2.85 or incl. slow motion drive, £3.85. 4 position and 6 pos. push-button transistorised, £4.95. All tuners P/P 35p. MURPHY 600/700 series complete UHF Conversion Kits incl. tuner, drive assy., 625 IF amplifier, 7 valves, accessories housed in cabinet plinth assembly, £7.50 P/P 50p. GEC 405/625 Dual standard switchable IF amplifier and output chassis incl. cct., £1.50 P/P 35p THORN 850 Dual standard time base panel, 75p P/P 35p. PHILIPS 625 IF amplifier panel incl. cct., 75p, P/P 30p. VHF turret tuners AT7650 incl. valves for K.B. Featherlight, Philips 19TG170, GEC 2010, etc., £2.50. PYE miniature incremental for 110 to 830, Pam and Invicta, £1.00. A.B. miniature with UHF injection suitable K.B. Baird, Ferguson, 75p. New fireball tuners Ferguson, HMV, Marconi, £1.80 P/P all tuners 30p. Mullard 110° mono scan coils, new suitable all standard Philips, Stella, Pye, Ekco, Ferranti, Invicta, £2.00, P/P 35p. Large selection LOPTs. FOPTs available for most popular makes. 200+200+100 Microfarad 350v Electrolytic, £1.00 P/P 20p. MANOR SUPPLIES, 172 WEST END LANE, LONDON, N.W.6. Shop premises, callers welcome. (No. 28, 59, 159 Buses or W. Hampstead Bakerloo and Brit. Rail). MAIL ORDER: 64 GOLDERS MANOR DRIVE, LONDON. N.W.11. Tel. 01-794 8751.

CONSTRUCTION AIDS—Screws, nuts, spacers, etc., in small quantities. Aluminium panels punched to spec. or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit boards—masters, negatives and board, one-off or small numbers. Send 9p for list. Ramar Constructor Services, 29 Shelbourne Road, Stratford on Avon, Warwks. Tel. Stratford on Avon (std 0789) 4879. [28]

CONSTRUCTION AIDS—Screws, nuts, spacers, etc., in small quantities. Aluminium panels punched to spec. or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit boards—masters, negatives and board, one-off or small numbers. Send 9p for list. Ramar Constructor Services, 29 Shelbourne Road, Stratford on Avon, Warwks. Tel. Stratford on Avon (std 0789) 4879. [28]

COSSOR CDU120 60MH3 Solid-State scope. Dual-Trace 1mv/cm. 2 Timebases. Full delay sweep. With probe and manual. £220. 01-346 1103 [4410]

ERNEST TURNER 1.5m/a PPMs, £3. Unused ex BBC equalizers (bass, treble, presence) £3.75 each. Pair Mullard switchable audio high & low pass filters £8.50. Optical PPM £6.50. Details—Leeds 683618. [4389]

HAVE YOU HAD YOUR CHIPS? AY-5-1224 Digital Clock chip+data and circuit diagram £3.66 —Details SAE. Jumbo 0.6" DL 747 seven segment L.E.D. display now only £2.04. All post free, add standard VAT.—GREENBANK ELECTRONICS, 94 New Chester Road, Wirral, Merseyside L62 5AG. [4405]

HEATH IG-37 FM Stereo Generator, brand new, factory aligned, £60. I. G. Bowman, 35 Park Hill Road, Torquay, S. Devon. [4401]

I CREATE, 51 Midhurst Road, London W13 9XS. Zero—X Relays 8A 240V AC. Epoxy Encapsulated. Integral Heatsink. Input 10UA 2V. £5.40 each. [4385]

PHILIPS PM3232 Oscilloscope for sale. Used only twice, one year old, £160. MEC Electronics Ltd., 327B Hedon Road, Hull, Humberside. [4403]

PYE INDUSTRIAL CAMERA MARK IV, type 2048. Ser. 69, with lens change attachment type 2081. Ser. 46. Camera control panel type 3716 Ser. 90. Industrial camera control unit type 2332c. Ser. 85. One tripod to fit and three lengths of cable. £400 o.n.o. Telephone Cambridge 55081. [4381]

VACUUM is our speciality. New and second-hand rotary pumps, diffusion outfits, accessories, coaters, etc. Silicone rubber or varnish outgassing equipment from £40. V. N. Barrett (Sales) Ltd., 1 Mayo Road, Croydon. 01-684 9917. [24]

VALVES, TRANSISTORS, STYLI. Valves 1930 to 1975, 1500 types in stock. Many obsolete; List 5p. Diamond Styli, list 10p; transistors, list 15p. S.A.E. for quotation. Cox Radio (Sussex) Ltd., The Parade, East Wittering, Sussex. West Wittering 2023. [4027]

WIRELESS WORLD 100 copies 1919 to 1937 offers? BBC Year Books 9 copies 1928 to 1934 £5; Amplion Horn Speaker Type AR23 New £15; Valves (50), Coils, Transformers, all new 84 components £15. 01-882 0638 Palmers Green N.13.

60 KHz MSF Rugby and 75 KHz Neuchatel Radio Receivers. Signal and Audio outputs. Small, compact units. Two available versions. Toolex, Bristol Road, Sherborne (3211), Dorset. [21]

ARTICLES WANTED

SCOPE TUBES. 1" Tube 1cP1 or DH3/91 preferably with bases and screws. Price up to £5.00 according to age and condition. Cheque or P.O. by return. Barry Childe, 370, Charmingston Rd. Bournemouth BH8 9RX. Tel: 516565. Closed Mondays. [4413]

WANTED, all types of communications receivers and test equipment.—Details to R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [63]

WANTED in good working condition. Philips Pal Colour T.V. Lattern generator tupe PM 5508. Similar generators would also be suitable. Box No. WW 4411.

WANTED. Ericsson Counting Tubes Type GC/12/4B. Ricardo and Co. Ltd., Blidge Works, Shoreham-By-Sea. Phone 5611. [4016]

WE BUY modern 16mm sound projectors. Burgess Lane & Co. Ltd., Thornton Works, Thornton Avenue, Chiswick W.4. 994 5752/5953. [4387]

CAPACITY AVAILABLE

AIRTRONICS LTD., for Coil Winding—large or small production runs. Also PC Boards Assemblies. Suppliers to P.O., M.O.D., etc. Export enquiries welcomed. 3a Walerand Road, London, SE13 7PE. Tel. 01-852 1706. [61]

AVAILABLE Capacity for Electronic Electro-Mechanical Assembly Wiring of P.C.B.'s Panels cableforms, design work undertaken if required. Jackson Instruments, 74 Western Road, Leicester, 0533-546649. [4026]

BATCH Production Wiring and Assembly to sample or drawings. Deane Electricals, 19B Station Parade, Ealing Common, London, W.5. Tel: 01-992 8976. [20]

CAPACITY available to the Electronic Industry. Precision turned parts, engraving, milling and grinding both in metals and plastics. Limited capacity available on Mathey SP33 JIG BORER. Write for lists of full plant capacity to C.B. Industrial Engineering Ltd., 1 Mackintosh Lane, E9 6AB. Tel. 01-985 7057. [14]

COMPLETE PRINTED CIRCUIT DOCUMENTATION including artwork masters, assembly drawings, mechanical drawings, circuit diagrams etc. prepared from your basic design details. Single and double sided PC boards. Assembled prototypes supplied. J. T. Electronics, Box No. WW 4390.

COMPREHENSIVE Electronics Service from design and manufacturer to installation of the finished product. Specialists in Audio-Visual equipment. Zeta Electronics. Box No. WW 4412.

DESIGN, development, repair test and small production of electronic equipment. Specialist in production of printed circuit assemblies. YOUNG Electronics Ltd., 54 Lawford Road, London, NW5 01-267 0201. [29]

ENGINEER makes anything unusual. Inventors models, displays. Special tools and equipment. Seymour, 30 Devonshire Drive, Stapleford, Nottingham. [4229]

SMALL Batch Production, wiring assembly, to sample or drawings. Specialist in printed circuit assemblies. D. & D. Electronics, 42 Bishopfield, Harlow, Essex. Harlow 33018. [17]

COURSES

RADIO and Radar M.P.T. and C.G.L.I. Courses. Write: Principal, Nautical College, Fleetwood, FY7 8JZ. [25]

LITERATURE WANTED

RADIOTELEPHONE INFORMATION. Collector is interested in books and other information on radiotelephone pioneers and experiments. Ronald Phillips, 1925 Baltimore, Kansas City, Missouri, 64108. [4376]

NEW GRAM AND SOUND EQUIPMENT

GLASGOW HI FI, Recorders, Video, Communications Receiver always available we buy sell and exchange for photographic equipment. Victor Morris Audio Visual Ltd., 340 Argyle Street, Glasgow, G.2; 31 Sauchiehall Street, Glasgow, G.1; 8/10 Glassford Street, Glasgow, G.2. Tel: 041-221 8958. [11]

RECEIVERS AND AMPLIFIERS—SURPLUS AND SECONDHAND

HRO Rx5s, etc., AR88, CR100, BRT400, G209, S640, etc., etc., in stock.—R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [65]

SIGNAL generators, oscilloscopes, output meters, wave voltmeters, frequency meters, multi-range meters, etc., etc., in stock.—R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [64]

SERVICE AND REPAIRS

SCRATCHED TUBES. Our experienced polishing service can make your colour or monochrome tubes as new again for only £2.75, plus carriage £1. With absolute confidence send to Retube Ltd., North Somercote Louth, Lincs, or 'phone 0507-85 300. [27]

TV Audio, Radio Servicing. Most spares 1930-1975. Equipment designed, tested and maintained. Technical Services (Luton), Ltd., 111, Cutenhoe Road, Luton, Beds. LU1 3NG. 0582-29673/27601. [8025]

TAPE RECORDING ETC.

IF QUALITY, durability matter, consult Britain's oldest transfer service. Quality records from your suitable tapes. (Excellent fund raisers for schools). Modern studio facilities with Steinway Grand.—Sound News, 18 Blenheim Road, London, W.4. 01-995 1661. [4302]

VALVES WANTED

WE buy new valves, transistors and clean new components, large or small quantities, all details, quotation by return.—Walton's, 55 Worcester St., Wolverhampton. [62]

Wilmslow Audio

THE firm for speakers!



Baker Group 25, 3, 8 or 15 ohm	£7.75
Baker Group 35, 3, 8 or 15 ohm	£8.50
Baker Deluxe, 8 or 15 ohm	£10.75
Baker Major, 3, 8 or 15 ohm	£8.50
Baker Regent, 8 or 15 ohm	£7.75
Baker Superb, 8 or 15 ohm	£14.50
Celestion PST8 (for Unilex)	£3.25
Celestion MH 1000 horn, 8 or 15 ohm	£10.95
EMI 13 x 8, 3, 8 or 15 ohm	£2.25
EMI 13 x 8, 150 d/c, 3, 8 or 15 ohm	£2.50
EMI 13 x 8, 450 t/w, 8 ohm	£3.75
EMI 13 x 8, 350, 8 or 15 ohm	£8.25
EMI 13 x 8, 20 watt bass	£6.60
EMI 2 1/2" tweeter 8 ohm	£0.65
EMI 8 x 5, 10 watt, d/c, roll/s 8 ohm	£2.50
Elac 59RM 109 15 ohm, 59RM 1148 ohm	£2.80
Elac 6 1/2" d/cone, roll/s 8 ohm	£3.50
Elac TV4 4" tweeter	£1.50
Fane Pop 15 watt 12"	£5.25
Fane Pop 25T 30 watt 12"	£7.25
Fane Pop 50 watt, 12"	£12.00
Fane Pop 55, 12" 60 watt	£12.50
Fane Pop 60 watt, 15"	£13.25
Fane Pop 100 watt, 18"	£24.50
Fane Crescendo 12A or B, 8 or 15 ohm	£29.00
Fane Crescendo 15, 8 or 15 ohm	£36.00
Fane Crescendo 18, 8 or 15 ohm	£51.95
Fane 807T 8" d/c, roll/s, 8 or 15 ohm	£3.85
Fane 801T 8" d/c, roll/s, 8 ohm	£7.00
Goodmans 8P 8 or 15 ohm	£5.00
Goodmans 10P 8 or 15 ohm	£5.30
Goodmans 12P 8 or 15 ohm	£12.95
Goodmans 12P-D 8 or 15 ohm	£16.75
Goodmans 12P-G 8 or 15 ohm	£15.75
Goodmans Audiom 100 8 or 15 ohm	£12.00
Goodmans Axent 100 8 ohm	£7.25
Goodmans Axiom 401 8 or 15 ohm	£17.25
Goodmans Twinaxiom 8" 8 or 15 ohm	£8.25
Goodmans Twinaxiom 10" 8 or 15 ohm	£9.00
Kef T27	£5.25
Kef T15	£6.00
Kef B110	£7.25
Kef B200	£8.25
Kef B139	£14.75
Kef DN8	£2.00
Kef DN12	£4.95
Kef DN13	£3.30
Richard Allan CG8T 8" d/c roll/s	£6.35
STC 400 1 G super tweeter	£6.19
Fane 701 twin ribbon horn	£35.00
Baker Major Module each	£10.75
Goodmans Mezzo each	£45.00
Goodmans DIN 20 4 ohm each	£9.75
Helme XLK25 (pair)	£22.00
Helme XLK30 (pair)	£14.95
Helme XLK50 (pair)	£39.95
Kefkit 1 each	£20.95
Kefkit 3 each	£36.75
Peerless 3-15 (3 sp. system) each	£15.00
Richard Allan Twinkit each	£8.95
Richard Allan Triple 8 each	£13.75
Richard Allan Triple each	£19.95
Richard Allan Super Triple each	£23.75
Wharfedale Linton 2 kit (pair)	£19.25
Wharfedale Glendale 3 kit (pair)	£34.50
Wharfedale Dovedale 3 kit (pair)	£52.50

PRICES INCLUDE VAT

Cabinets for PA and HiFi, wadding, vynair, etc.

Send stamp for free booklet "Choosing a Speaker"

FREE with orders over £7—"HiFi loudspeaker enclosures" book.

All units guaranteed new and perfect.

Prompt despatch.


Carriage: Speakers 38p each, tweeters and crossovers 20p each, kits 75p each (pair £1.50).

WILMSLOW AUDIO

Dept WW
Swan Works, Bank Square, Wilmslow,
Cheshire SK9 1HF Tel. Wilmslow 29599
(Discount HiFi, PA and Radio at
10 Swan St, Wilmslow.)

WW—139 FOR FURTHER DETAILS

The Young Generation Relay

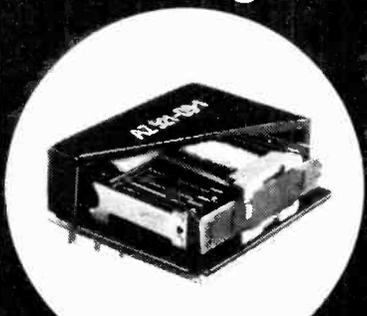

Platform Relay AZ 521

Cradle relay with 4 change-overs, dustproof cover, with single or bifurcated contacts.

Contact material:

Fine silver, silver palladium, gold nickel, fine silver with hard gold flashing, silver cadmium oxide.

Switching 2 A/2.5 A capability
110 V/125 V D.C. ~
30 W/100 VA

Operating power ca. 400 mW
Coil voltage maximum 60 V
Surface area 36 x 30 mm
Height 11 mm

ZETTLER

Zettler UK Division



Equitable House,
Lyon Rd., Harrow,
Middx. HA1 2DU
Tel. (01) 863 6329

WW—023 FOR FURTHER DETAILS

Quartz Crystal Units

ACCURATE RELIABLE

Private enquiries, send 5p in stamps for brochure

THE QUARTZ CRYSTAL CO. LTD.

Q.C.C. WORKS, WELLINGTON CRESCENT,
NEW MALDEN, SURREY. 01-942-0334 & 2988

TRANSFORMER LAMINATIONS enormous range in Radiometal, Mumetal and H.C.R., also "C" & "E" cores. Case and Frame assemblies.

MULTICORE CABLE IN STOCK CONNECTING WIRES
Large quantities of miniature potentiometers (trim pots) 20 ohm to 25K. Various makes. Wholesale and Export only.

J. Black

OFFICE: 44 GREEN LANE, HENDON, NW4 2AH
Tel: 01-203 1855. 01-203 3033
STORE: LESWIN ROAD, N.16
Tel: 01-249 2260

EXCLUSIVE OFFERS

WORLD-WIDE RANGE NEVER BEFORE OFFERED

COMPLETE TRANSPORTABLE H.F. COMMUNICATIONS CENTRE housed in Air Conditioned TRAILER fitted two COLLINS KWT-6 500W S.S.B. Transmitter-Receiver and one COLLINS Receiver all fully tuneable 2 to 30 m/c digital readout synthesised frequency control, with line amplifiers and inputs, operating position and remote control facilities and ancillary equipment. Power Input 115V or 230V A.C. Full details on application.

PHILCO HC-150 POINT-TO-POINT STRIP RADIO HF RECEIVERS 2/30 m/c. Ten fully tuneable channels to 9.5 kcs with synthesizers. Single and diversity reception on ISB, DSB, SSB with 4 sub-hands to each channel. Full details and prices on application.

HIGHEST QUALITY 19" RACK MOUNTING CABINETS & RACKS CABINETS

Our Height Ref. in inches	Width in inches	Depth in inches	Rack Panel Space in ins.	Price
CD 69	21	13	68	£10.00
CL 30	60	36	42	£12.50
CR 69	30	20	—	£24.00
DM 70	20	26	138	£21.00
FA 85	22	36	160	£22.00
FC 52	25	22	47	£17.00
FD 40	22	24	72	£14.00
FG 11	19	18	10	£11.00
FH 15	21	17	11	£12.00
FJ 15	21	15	12	£12.00
FN 70	24	20	68	£17.00
FL 84	22	17	80	£21.00
LL6 11	21	17	9	£15.00
LL7 16	20	12	14	£15.00
LL8 10	20	10	9	£15.00
LL9 17	21	17	14	£15.00

Also Consoles, twin and multi-way Cabinets.

OPEN RACKS

Our Height Ref. in inches	Channel Depth in inches	Rack Panel Space	Base	Price
RF 85	3	79	15	£11.00
RG 57	2	51	14	£9.00

Full details of all above on request.

We have a large quantity of "bits and pieces" we cannot list—please send us your requirements we can probably help—all enquiries answered.

- ★ 15" dia. Reel fibreboard Transit Cases, strapped, 10 for £5.00
- ★ Rustrak Chart Recorders 1-0-1 m/s (New) £30.00
- ★ Marconi Marine Speech Inverters £30.00
- ★ URA 8 Teletypewriter Converters £85.00
- ★ Portable Marine Battery Floodlights £24.00
- ★ 400 channel Pulse Height Spectrum Analyser P.U.R. £30.00
- ★ Airmec 245 L.F.150 watt Oscillators £24.00
- ★ Solartron 5/25000 cyc. Oscillators £24.00
- ★ Southern Inst. 1800 F.M. Meters £24.00
- ★ Belling Lee T.V. Relay Equipment P.U.R.
- ★ Addo 5/8 track Tape Punches £48.00
- ★ Tally 5/8 track Tape Readers £48.00
- ★ 80 column Card Hand Punches £40.00
- ★ 75 foot sectional self supporting Towers £300.00
- ★ Auto Electric Carillon Chimes £250.00
- ★ 10 foot Triangular Lattice Mast Sections 6 inch sides £12.00
- ★ Ditto 15 foot with 15 inch sides £24.00
- ★ Casella Asemann Electric Hygrometers £24.00
- ★ Racal RA63 SSB Adapters £50.00
- ★ WW Vol 1 No. 1 Bound P.U.R.
- ★ Hi-fi News, Vol. 1, No. 1 to date P.U.R.
- ★ Ampex Audio Stereo Tape Machines £50.00
- ★ Astrodial 5130 Time Code Generators £60.00
- ★ Geotech 4983 Hello Amplifiers £3.00
- ★ 18" Chrome trims 1 1/2" to 1 1/2" from £0.25
- ★ Hi-fi Sounds Practical Wireless P.U.R.
- ★ DG * 7 * 5 CRJs 2 1/2" £3.00
- ★ SAZ P/31 CRTs 3 1/2" £8.00
- ★ GOCZ Lightweight Teletypewriter £30.00
- ★ FX * 1 Fuelless Transistor Receivers £35.00
- ★ Teletype 28, 3-speed tape printers £35.00

We have a varied assortment of industrial and professional Cathode Ray Tubes available. List on request.

FREE

40-page list of over 1,000 different items in stock available—keep one by you.

INSTRUMENTATION-TAPE RECORDER-REPRODUCERS

AMPEX

FR-600 and FR-100 1" and 1/2" 14 and 7 tracks 4 speeds Transistorised



MINCOM

CMP-100 1/2" 1" 7 tracks 6 speeds

E.M.I.

BTR-1 Several other smaller decks. Full details on request.

Prices of above are from £100 to £400.


COMPUTER HARDWARE

- ★ CARD READER 80 col. 600 c.p.m.
- ★ PRINTER, High speed 1000 lines p.m.
- ★ TAPE READER, High speed 5/8 track 800 c.p.m.

Prices on Application

PLEASE ADD V.A.T. TO ABOVE

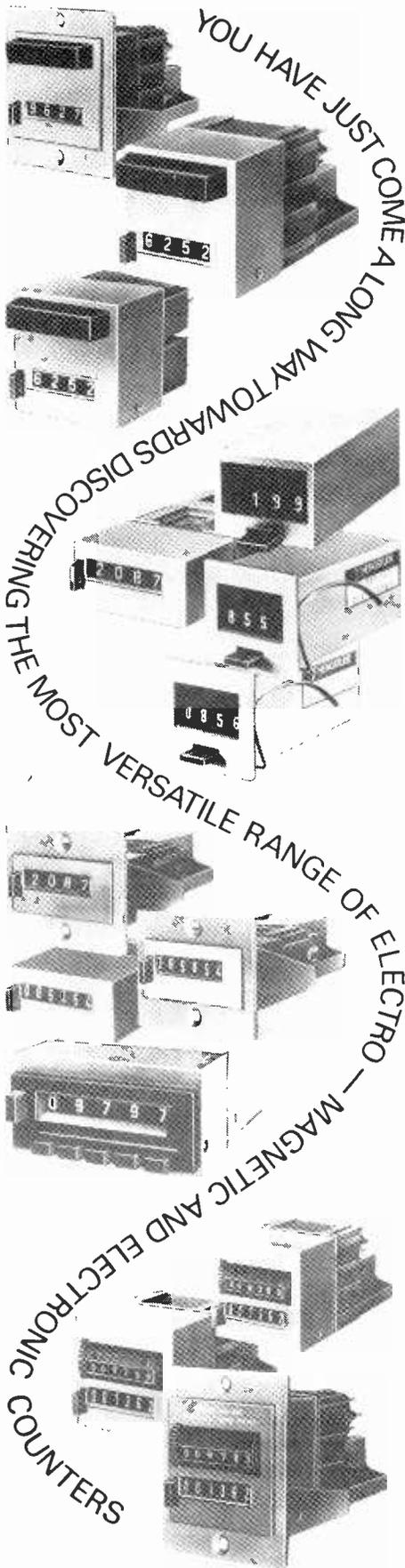P. HARRIS
ORGANFORD-DORSET
BHI6 6ER
BOURNEMOUTH-785051



YOU HAVE JUST COME A LONG WAY TOWARDS DISCOVERING THE MOST VERSATILE RANGE OF ELECTRO-MAGNETIC AND ELECTRONIC COUNTERS

EX-COMPUTER STABILISED POWER SUPPLIES

RECONDITIONED, TESTED AND GUARANTEED

Ripple <10mV. Over-voltage protection 120-130v. 50 c/s input. Stepdown transformer to suit about £3.

Post & Packing £1-70

5-6v. 8A. £12 5-6v. 16A. £16
5-6v. 12A. £14

PAPST FANS 4 1/2 x 4 1/2 x 2in. 100 cfm. 240v. 50/60 Hz. £3-50 (30p).

PAPST FANS 6in. dia. x 2 1/2in. deep Type 7576 £5-00 (30p). Few only 6in. PAPST £4 (30p)

TRANSISTORS p & p 10p
BC107/8/9 BC147/8/9 BC157/8/9 all 9p
BF180 25p BF182/3/40p BF184 17p BC167 13p
BFW10 55p BF336 35p 741 8 DIL 34p
2N3771 £1-10, 2N3441 50p, BD131 40p
NE555 67p, 2N3055 45p

ELECTROLYTICS
30,000µ 25v, 68,000µ 16v, 15,000µ 30v 65p (20p)
4000µ 70v., 3,600µ 40v., 4 1/2 x 2in. dia. 55p (15p)
5,000µ 35v., 40p (12p)
2,000µ 50v + clip 35p (8p)
2,200µ 63v 35p (8p)

EX-COMPUTER PC PANELS 2 x 4in. 25 boards for £1 (30p).
QH Bulbs, 12v. 55w. 50p (7p)
150 mixed HI-STABS 60p (11p)
250 Mixed Resistors 60p (13p)
250 Mixed Capacitors 60p (11p)
200 SI Planar Diodes 50p (8p)
Min. Glass Neons 8 for 50p (7p)
2N3055 EQUIV 4 for £1 (10p)

Postage and packing shown in brackets

Please add 8% VAT to TOTAL


KEYTRONICS

Mail Order only.

44 EARLS COURT ROAD, LONDON, W.8
01-478 8499

QUARTZ CRYSTAL UNITS from

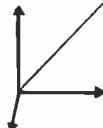- 1.0-60.0 MHZ
- FAST DELIVERY
- HIGH STABILITY
- TD DEF 6271-A



TEL. HYTHE 848961
STD CODE 0703

WRITE FOR LEAFLET AT-1

McKNIGHT CRYSTAL Co.
HARDLEY INDUSTRIAL ESTATE, HYTHE, SOUTHAMPTON SO4 6ZY.

BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, N. Finchley, London, N12 8JG.

Telephone :

01-445 0749 01-445 2713 01-958 7624

MAY WE ASSIST YOU TO DISPOSE OF YOUR SURPLUS AND REDUNDANT STOCKS.

We will call anywhere in the British Isles, and pay SPOT CASH for Electronic Components and Equipment.

SINTEL

Data and circuits supplied with orders, or available separately (4 1/2p stamp each).

3 Digit DIP LED Calculator display (12" ht) £1-35
High Quality 3" LED 7 segment display 95p
MK50250N Alarm Clock IC £6 90
Send for our new simple MK50250N circuit diagrams
MK50250N + 4 DL704 3" LED's £10-20, + 6 x DL704 £12-10
Soldercon IC socket pins 300 pins for £1-50
(Instructions supplied) 1000 pins for £4-00
—send s.a.e. for sample 3000 pins for £10-50
ADD VAT @ 8%—Add 10p p&p for orders under £2
SINTEL, 53c ASTON STREET, OXFORD Tel: 0865 43203

Illustrations in Applied Network Theory

F. E. Rogers

A hundred numerical and algebraic illustrations designed to exemplify practical circuit problems and introduce, in analysis, principles consistent with studies of synthesis that may be pursued later.

1973 240 pp., illustrated
0 408 70425 X cased £5.00
0 408 70426 8 limp £2.50

Obtainable through any bookseller or from

The Butterworth Group

88 Kingsway, London WC2B 6AB
Showroom: 4-5 Bell Yard, WC2.



WE PURCHASE ALL FORMS OF ELECTRONIC EQUIPMENT AND COMPONENTS, ETC. SPOT CASH

CHILTMEAD LTD.

7, 9, 11 Arthur Road, Reading, Berks. Tel: 582 605

EXPRESS

PRINTED CIRCUITS - ROLLER TINNING - GOLDPLATING - FLEXIBLE FILMS, ETC.

Electronic & Mechanical Sub-Assembly Co. Ltd

Highfield House, West Kingsdown Nr. Sevenoaks, Kent
Tel: West Kingsdown 2344

J. LINSLEY-HOOD

New Phase Locked Loop F.M. TUNER (As per Wireless World Annual).

Basic kit of parts *£29.95 (tax £2.40)

Available in pack form as follows:

Pack 1. Res. and capacitors £2.95 2. Semi conductors and IC's £5.50 3. Tuner head £5.50 4. P.C. boards and drawings £1.50 5. Chassis and tuning mechanism £5.00 6. Ceramic filters £1.50 7. Teak finish sleeve £3.00 8. Meter and muting module £2.50 9. Regulator power supply £5.00 10. Stereo decoder. Ready made £7.50 11. Push button and trimmer pack £2.50 *Excludes packs No. 8, 10 and 11. VAT extra, p.p. 20p (pks. 5 and 7 50p)

TELERADIO ELECTRONICS

325 Fore Street, Edmonton, London N9 OPE. 01-807 3719. Closed Thursdays.

S.A.E. for further details of above and other Linsley-Hood superior designs.

SOWTER TRANSFORMERS

FOR SOUND RECORDING AND REPRODUCING EQUIPMENT We are suppliers to many well-known companies, studios and broadcasting authorities and were established in 1941. Early deliveries. Competitive prices. Large or small quantities. Let us quote.

E. A. SOWTER LTD.

Transformer Manufacturers and Designers
7 Dedham Place, Fore Street, Ipswich IP4 1UP
Telephone 0473 52794

Housing problems?

West Hyde will have a case to meet your needs. Check now. Ring WEST HYDE

CONTIL MOD-2 MOD-3, SAMOS BRIGHTCASE AMTRON, MINOS ENVIRONMENTAL HEAVY DUTY CASES WEST HYDE DEVELOPMENTS LIMITED

Ryefield Crescent, Northwood Hills, Northwood, Middx. HA6 1NN. Tel. Northwood 24941/26732. Telex: 923231

HENGSTLER

Manufacturers of counters and counting systems



HENGSTLER GB LIMITED, NAZEING NEW ROAD, BROXBORNE, HERTS, EN10 6SX. TELEPHONE: HODDESDON 68451. TELEX: LONDON 263243

WW-150 FOR FURTHER DETAILS

WW-136 FOR FURTHER DETAILS

STILL ON SPECIAL OFFER

LOW FREQUENCY ANALYZER
50Hz-50KHz
ASSEMBLY AND INSTRUCTION
INFORMATION S.A.E.

PRICE **£27** p&p 75p

Board, modules and all
components (excluding
P.U.).

V.A.T. at 8%

CHILTMEAD LTD

7-9 ARTHUR ROAD, READING, BERKS. (rear Tech. College). Tel. Reading 582605

100MHz SCOPE TUBES

MULLARD D13-450GH-03. P31 PHOSPHOR.
INTERNAL GRATICULE—6CM X 10CM RECT-
ANGULAR. Y SENSITIVITY 3V PER CM X 11V
PER CM. SINGLE GUN. DISTRIBUTED Y PLATES,
TRACE ROTATE COILS.

BRAND NEW BOXED. £30 each.
CARRIAGE £2.

INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 74-90

	PAGE		PAGE		PAGE
Aero Electronics Ltd.	16, 25	Gardners Transformers Ltd.	8	Patrick & Kinnie	42
Ambientacoustics	30	Garrard Eng. Ltd.	3	Phoenix Electronics (Portsmouth) Ltd.	31
Ambit International	66	Goodmans Loudspeakers Ltd.	2	Physical & Elec. Labs. Ltd.	28
Anders Electronics Ltd.	4	Grampian Reproducers Ltd.	12	Powertran Electronics	48, 49
A.S.P. Ltd.	67	Greenwood Electronics	11	Prosser Scientific Insts.	18
Barr & Stroud Ltd.	68	Harris Electronics (London) Ltd.	12, 21	Quality Electronics Ltd.	25
Barrie Electronics Ltd.	53	Harris, P.	91	Quartz Crystal Co. Ltd.	91
Bentley Acoustic Corp. Ltd.	60	Hart Electronics	31		
Bi-Pak Semiconductors	44, 45	Heath (Gloucester) Ltd.	7		
Bi-Pre Pak Ltd.	47	Hengstler G.B. Ltd.	92	Radford Audio Ltd.	16, 32
Bias Electronics Ltd	26	Henry's Radio Ltd.	51	Ralfe, P.	70
Black, J.	91	Hepaire Manufacturing Ltd.	10	Rola Celestion Ltd.	32
Britec Ltd.	16	H.H. Electronics	25	R.C.S. Electronics	67
Broadfields & Mayco Disposals	92	Hitachi-Shibaden (U.K.) Ltd.	10	R.S.T. Valves Ltd.	54
Bull, J. Electrical Ltd.	60	Hurst Electronics	52		
Bywood Electronics	26				
Cambridge Audio Ltd.	15	Icon Design	19	Samsons (Electronics) Ltd.	61
Cambridge Learning	41	I.L.P. (Electronics) Ltd.	27	Scopex Instruments Ltd.	18
Carston Electronics	50	Industrial Tape Applications Ltd.	29	Semicon Indexes Ltd.	70
Chiltmead Ltd.	25, 55, 92, 94	Integrex Ltd.	30	Service Trading Co.	62
Chromasonic Electronics Ltd.	46			Servo & Electronic Sales Ltd.	72
Circards	73	Jasmin Electronics Ltd.	31	Shelton Instruments Ltd.	19
Colomor (Electronics) Ltd.	59	J.H. Associates Ltd.	28	Shure Electronics Ltd.	35, 40
Computer Sales & Services	72			Sinclair Radionics Ltd.	38, 39
Consumer Association "Which" Magazine Loose Insert		K.T. Manners Design	67	Sintel	92
Crichton, J.	57	Keytronics Ltd.	92	Sowater, E. A., Ltd.	92
Crofton Electronics	30	Klark Teknik	19	Special Product Distributors Ltd.	22
C.T. Electronics Ltd.	69			Strumech Eng. Co. Ltd.	18
				Sugden, J. E., & Co. Ltd.	16
				Surrey Electronics	93
Danavox (G.B.) Ltd.	9	Lee Eng. Ltd.	21	Technomatic Ltd.	24
Decca Radio & Television	8	Levell Electronics Ltd.	1	Teleprinter Equipment Ltd.	43
Decon Labs. Ltd.	22	Linstead Electronics	20	Telegroup Products (Tektronix U.K.) Ltd.	34
Dixons Technical CCTV Ltd.	17	Logic Leisure Ltd.	29	Teleradio Special Products	92
				Teonex Ltd.	22
				Toko U.K. Ltd.	66
				Trampus Electronics	48
				T.U.A.C. Ltd.	13
East Cornwall Components	42	Macfarlane, W. & B.	57	United-Carr Supplies	36
Eddystone Radio Ltd.	12	Maplin Electronic Supplies	23		
Edgington, John & Co. Ltd.	26	Marco Trading Co.	93		
Edicron Ltd.	25	Marconi Instruments Ltd.	cover ii		
Electronic Brokers Ltd.	64, 65	Marshall, A., & Sons (London) Ltd.	53	Valradio Ltd.	14
Electronic Mech. Sub Assembly Co. Ltd.	92	McKnight Crystal Co.	92	Verd Electronics Ltd.	52
Electro-Tech. Components Ltd.	56	McLennan Eng. Ltd.	24	Vortexion Ltd.	cover iii
Electrovalue	68	Mills, W.	56		
Elektor Publications Ltd.	28	Milward, G. F.	58		
Elvins Electronic Musical Insts.	30	Modern Book Co.	6	Waycom Ltd.	21
English Electric Valve Co. Ltd.	37	Mordaunt-Short Ltd.	6	Wayne, Kerr, The, Co. Ltd.	5
E.S. Electronics	70	Multicore Solders Ltd.	cover iv	West Hyde Developments Ltd.	92
				Whiteley Electrical Radio Co. Ltd.	20
				Wilkinson, L. (Croydon) Ltd.	68
				Wilmslow Audio	91
Fi-Comp Electronics	54	Naim Audio Ltd.	28		
Future Film Development Ltd.	54	Nombrex (1969) Ltd.	14		
		Ocli Optical Coatings Ltd.	14	Z. & I. Aero Services Ltd.	6, 69
				Zettler GmbH	91

Printed in Great Britain by Hazells Offset Ltd., Leigh Road, Slough, Bucks., and Published by the Proprietors I.P.C. ELECTRICAL-ELECTRONIC PRESS LTD., Dorset House, Stamford St., London, SE1 9LU telephone 01 8000. *Wireless World* can be obtained abroad from the following: AUSTRALIA and NEW ZEALAND: Gordon & Gotch Ltd. INDIA: A. H. Wheeler & Co. CANADA: The Wm. Dawson Subscription Service, Ltd. & Gotch Ltd. SOUTH AFRICA: Central News Agency Ltd.; William Dawson & Sons (S.A.) Ltd. UNITED STATES: Eastern News Distributors Inc. 155 West 15th Street, New York, N.Y. 10011. CONDITIONS OF TRADE: This periodical is sold subject to the following conditions namely that it shall not without the written consent of the publishers first given be lent, re-sold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised form of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.



50/70 watt all silicon amplifier with built-in 5-way mixer using F.E.T.'s.

SOUND SENSE = VORTEXION

VORTEXION Design and manufacture public address equipment to meet a range of specific requirements for AIRPORTS, HOTELS, THEATRES, GOVERNMENT AUTHORITIES, LOCAL AUTHORITIES, SUPERMARKETS, SCHOOLS, SPORTING COMPLEXES, POP GROUPS AND THE LOCAL VILLAGE HALL.

The high fidelity amplifier illustrated has bass cut controls on each of the three low impedance balanced line microphone stages and a high impedance gram stage with bass and treble controls, plus the usual line or tape input. All the input stages are protected against overload by back to back low self capacity diodes and all use F.E.T.'s for low noise, low intermodulation distortion and freedom from radio breakthrough.

A voltage stabilised supply is used for the pre-amplifiers making it independent of mains supply fluctuations and another stabilised supply for the driver stages is arranged to cut off when the output is overloaded or over temperature. The output is 75 % efficient and 100 V balanced line or 8-16 ohms output are selected by means of a rear panel switch which has a locking plate indicating the output impedance selected.

The mixer section has an additional emitter follower output for driving a slave amplifier, phones or tape recorder, output 0.3 V out on 600 ohms upwards.

50/70 WATT ALL SILICON AMPLIFIER WITH BUILT-IN 4-WAY MIXER using the circuit of our reliable 100 Watt Amplifier with its elaborate protection against short and overload, etc. To this is allied our latest development of F.E.T. Mixer Amplifier, again fully protected against overload and radio breakthrough. The mixer is arranged for 2-30/60 Ω balanced line microphones, 1-HiZ gram input and 1-auxiliary input followed by bass and treble controls. 100 volt balanced line output OR 5-15 Ω and 100 volt line.

100 WATT ALL SILICON AMPLIFIER. A high quality amplifier with 8 ohms-15 ohms or 100 volt line output for A.C. Mains. Protection is given for short and open circuit output over driving and over temperature. Input 0.4 V on 100 K ohms.

THE 100 WATT MIXER AMPLIFIER with specification as above is here combined with a 4-channel F.E.T. mixer. 2-30/60 Ω balanced microphone inputs, 1-HiZ gram input and 1-auxiliary input with tone controls and mounted in a standard robust stove enamelled steel case. A stabilised voltage supply feeds the tone controls and pre amps, compensating for a mains voltage drop of over 25 % and the output transistor biasing compensates for a wide range of voltage and temperature. Also available in rack panel form.

20/30 WATT MIXER AMPLIFIER. High fidelity all silicon model with F.E.T. input stages to reduce intermodulation distortion to a fraction of normal transistor input circuits. Standard model 1-low mic. balanced input and HiZ gram. Outputs available 8/15 ohms OR 100 volt line.

CP50 AMPLIFIER. An all silicon transistor 50 watt amplifier for mains and 12 volt battery operation, charging its own battery and automatically going to battery if mains fail. Protected inputs, and overload and short circuit protected outputs for 8 ohms-15 ohms and 100 volt line. Bass and treble controls fitted.

Models available with 1 gram and 2 low mic. inputs, 1 gram and 3 low mic. inputs or 4 low mic. inputs.

200 WATT AMPLIFIER. Can deliver its full audio power at any frequency in the range of 30 c s-20 Kc s. Can be used to drive mechanical devices for which power is 120 watts on continuous sine wave. Input 1 mW 600 ohms. Output 100-120 V or 200-240 V. Additional matching transformers for other impedances are available.

F.E.T. MIXERS and PPM's. Various types of mixers available. 3, 4, 6 and 8 channel with Peak Programme Meter. 4, 6, 8 and 10 Way Mixers. Twin 3, 4 and 5 channel Stereo, also twin 4 and 5 channel Stereo with 2 PPM's.

VORTEXION

Vortexion Ltd., 257-263 The Broadway, Wimbledon, SW19 1SF.

Telephone : 01-542 2814 and 01-542 6242 3/4.

Telegrams : "Vortexion London SW19"

For further information and technical leaflets write to Vortexion
Name _____ Address _____

P.E. 723E (not included) for Savbit
 5,000µF 50V
 +12V 500mA
 with artificial earth
 for testing

Multicore- the complete answer for printed circuit soldering.

Most printed circuit soldering problems can be avoided by using quality products and seeking quality advice. Naturally, we suggest ours. First, let's talk about quality products.


Extrusol and Multipure.

EXTRUSOL Extruded Bars and MULTI-PURE Cast Bars are made from specially processed ultra high purity solder. EXTRUSOL bars and pellets are protected by plastic film from the moment they are made to the moment they are used. And MULTI-PURE bars are probably the smoothest and brightest solder bars you will ever see.



Ersin Multicore Savbit.

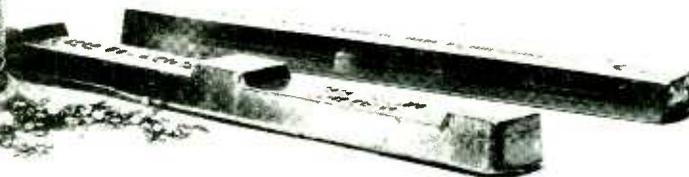This cored solder has countless uses. For instance, it avoids erosion of copper plating and wires as well as prolonging the life of soldering iron bits.



Liquid Fluxes.

We have a whole family of them, so you're bound to find the right one for your job. One of our latest is PC 26, exceptionally fast but non-corrosive and non-conductive. Eliminates "icicles" and "bridging."

Right, those are the products. Now for the advice. And we can't really say any more than: if you've a soldering problem or question, call us. We really do have all the answers and the widest range of problem soldering test equipment.

ROSIN BASE

ERSIN Flux No.	Type	Solids Content w/w	Specifications
0360	non-activated	38%	MIL-F-14256D Type R; DTD 599A DIN 8527 F-SW 31
5381	mildly activated Chloride and Bromide free	25%	MIL-F-14256D Type RMA; DTD 599A
304D } 304W }	mildly activated Halide Free	10% } 25% }	DIN 8527 Type F-SW 32 DTD 599A
PC. 21A	activated	38%	DTD 599A; DIN 8527.F-SW 26
PC. 26	activated (extra fast)	15%	DTD 599A; DIN 8527.F-SW 26
366	activated (extra fast)	38% }	Meet DIN 8511 Type F-SW 26 and pass DTD 599A Corrosion Test
366A-25	activated (extra fast)	25% }	
ORGANIC ACID			
PC. 101	water base	12% }	Water soluble residues must be removed after soldering.
PC. 112	solvent base, fast drying	9.5% }	
INORGANIC ACID			
ARAX	water base extremely active	40%	Used with most "very difficult to solder" metals. Not for electronics assembly joints.

Solderability Test Instrument.

Already used by major electronic companies throughout the world, this novel instrument saves production costs by controlling solderability of component leads which, unlike a printed circuit, cannot be assessed by a simple "immersion and inspection" test.



Multicore Soldering Chemicals.

We make a complete, compatible range to assist in soldering processes. They clean, protect and preserve.



For full information on these or any other Multicore products, please write on your company's letterhead direct to:
Multicore Solders Limited, Maylands Avenue, Hemel Hempstead, Hertfordshire HP2 7EP
 Tel: Hemel Hempstead 3636. Telex: 82363.