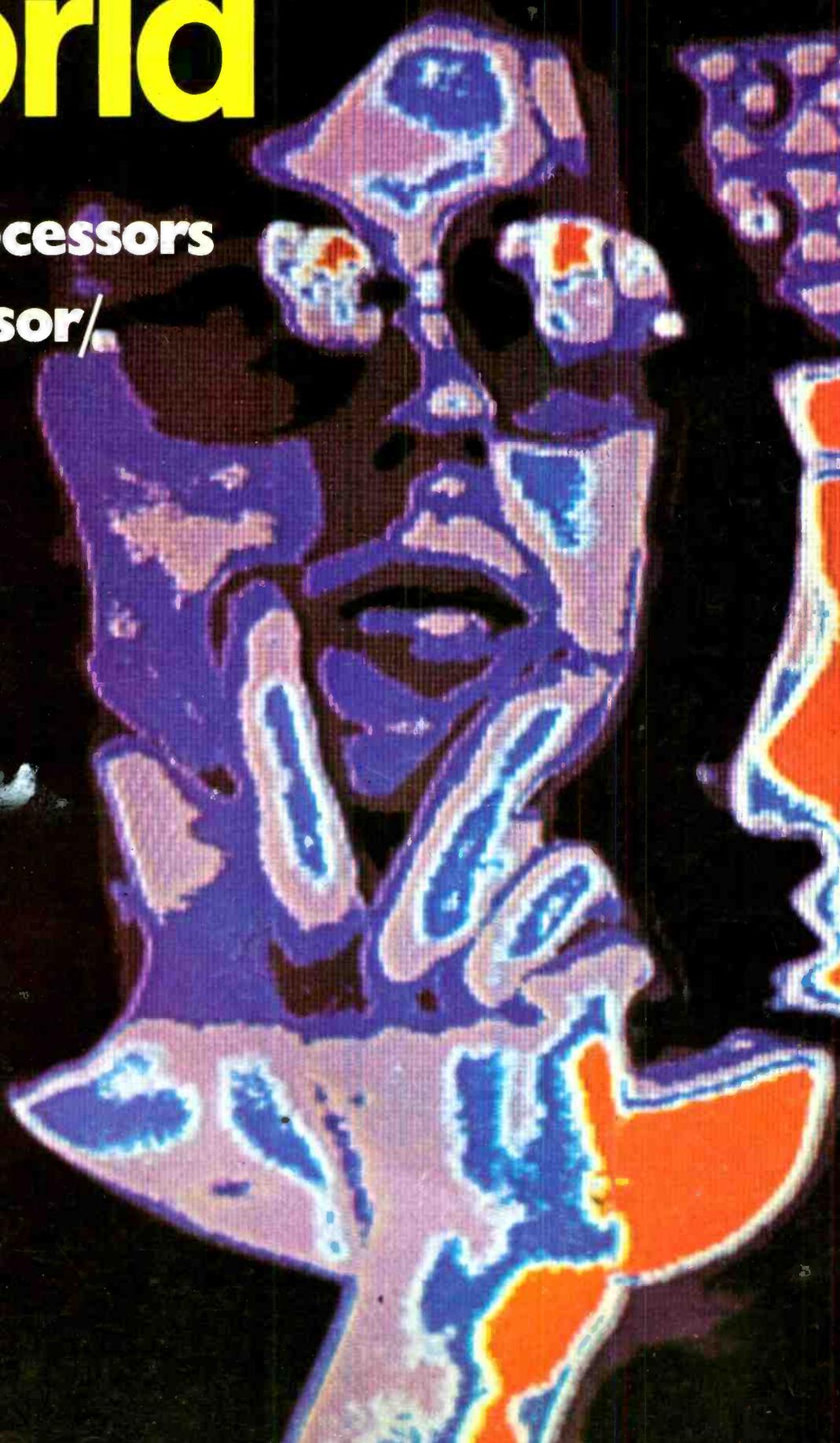



# wireless world

DECEMBER 1975 35p

**Microprocessors**  
**Compressor/  
limiter**



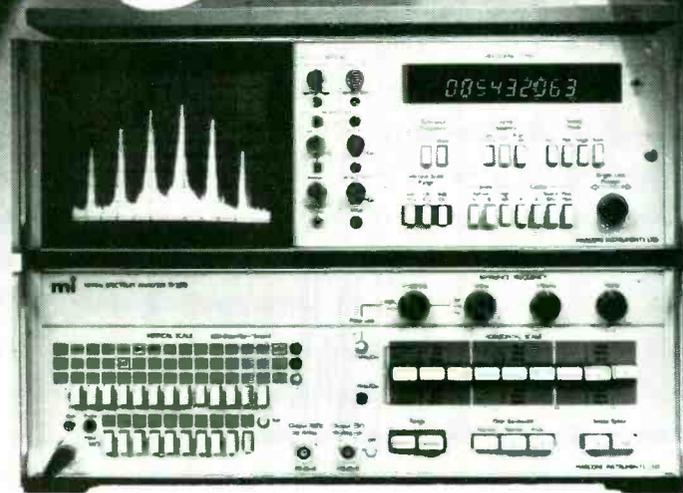Australia SA1.20  
Belgium Fr. 61.50  
Canada \$1.50  
Denmark Kr. 11.00  
Finland Fmk. 6.20  
Germany Dm. 4.50  
Greece Dr. 45.00  
Holland Dfl. 4.50  
Italy L. 900  
Malaysia MS3.25  
New Zealand \$NS1.20  
Norway Kr. 10.00 incl. moms  
Portugal Esc. 40.00  
South Africa R. 1.10  
Spain Ptas 80.00  
Sweden Kr. 6.90 incl. moms  
U.S.A. \$1.50



# The Production Test Bottleneck Smasher!

You've never seen a faster, more accurate way of measuring frequency response from 30Hz to 110MHz

Slash your production-test times and divert your skilled engineers to more important work with our TF 2370 Spectrum Analyser. It will reduce to simple operations, complicated measurements such as response, level, gain, signal purity, modulation and many more, with a speed and degree of accuracy that has to be seen to be believed. Forget everything you have heard about spectrum analysers. The TF 2370 is unique. It employs advanced technology to make it reliable and as easy to operate as a multimeter. The facts speak for themselves.

- \* Flicker-free display of frequency response from 30 Hz to 110 MHz on a high-brightness c.r.t.
- \* Electronic graticule, with a  $\pm 15\%$  variation of horizontal divisions for pin-point positioning against waveform display.
- \* Press-button selection of three amplitude scales: one linear and two logarithmic with expansion to 1 dB/div. with an accuracy of  $\pm 0.1$  dB/dB.
- \* 9-digit electronic counter automatically gives centre frequency, reads any other frequency corresponding to manually-adjusted 'bright line' position on display, or the

- difference frequency between the two, at the press of a button. All to an accuracy of  $\pm 2$  Hz  $\pm$  reference frequency accuracy on high resolution and manual. Internal reference frequency provided with setting accuracy of 1 in  $10^7$ .
- \* Internal generator supplies synchronous signal source for measuring such items as networks and filters.
- \* For comparative measurements, unique memory storage system will retain one display indefinitely as required, for simultaneous display with waveform produced by items under test.
- \* Automatic adjustment of amplifier gain to give optimum lowest-noise performance with full protection against input overloading.
- \* Automatic selection of optimum sweep speed.
- \* With the 5 Hz filter, signals 100 Hz from a response at 0dB can be measured to  $-70$  dB.

Now ask for a demonstration. It could prove that the TF 2370 is a better cure for your headaches than aspirin. We are standing by for your call.

## mi: THE INNOVATORS

MARCONI INSTRUMENTS LIMITED,



Longacres, St. Albans, Hertfordshire, AL4 0JN, England. Telephone: St. Albans 59292. Telex: 23350.

A GEC-Marconi Electronics Company  
[www.americanradiohistory.com](http://www.americanradiohistory.com)

# LOW COST RC OSCILLATORS



**LEVELL**  
PORTABLE INSTRUMENTS

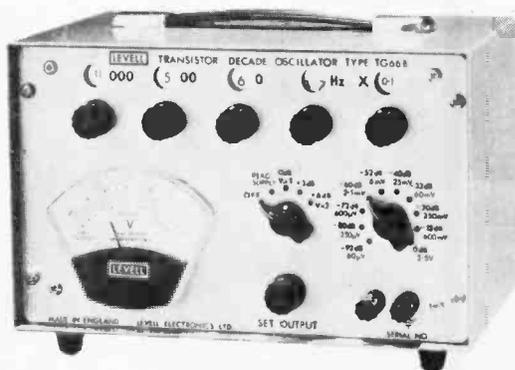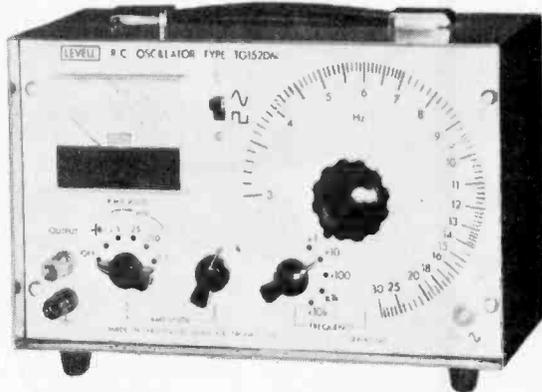

## ANALOGUE

**FREQUENCY** 3Hz to 300kHz in 5 decade ranges  
**ACCURACY**  $\pm 2\% \pm 0.1\text{Hz}$  up to 100kHz, increasing to  $\pm 3\%$  at 300kHz.  
**SINE OUTPUT** 2.5V r.m.s. down to  $< 200\mu\text{V}$ .  
**DISTORTION**  $< 0.2\%$  from 50Hz to 50kHz.  
**SQUARE OUTPUT** 2.5V peak down to  $< 200\mu\text{V}$ .  
**SYNC. OUTPUT** 2.5V r.m.s. sine.  
**METER SCALES** 0/2.5V &  $-10/+10\text{dB}$  on TG152DM.  
**SIZE & WEIGHT** 7" high x  $10\frac{1}{2}$ " wide x  $5\frac{1}{2}$ " deep. 8 lbs.

**TG152D**  
Without meter. **£53**

**TG152DM**  
With meter. **£63**

**FREQUENCY** 1Hz to 1MHz in 12 semi-decade ranges. 0 to 1% fine control included on TG200DMP  
**ACCURACY**  $\pm 2\% \pm 0.03\text{Hz}$ .  
**SINE OUTPUT** 7V r.m.s. down to  $< 200\mu\text{V}$  with  $R_s = 600\Omega$   
**DISTORTION**  $< 0.1\%$  to 5V,  $< 0.2\%$  at 7V from 10Hz to 100kHz.  
**SQUARE OUTPUT** TG200D, DM & DMP only. 7V peak down to  $< 200\mu\text{V}$ . Rise time  $< 150\text{nS}$ .  
**SYNC. OUTPUT**  $> 1\text{V}$  r.m.s. sine in phase with output.  
**SYNC. INPUT**  $\pm 1\%$  freq. lock range per volt r.m.s.  
**METER SCALES** TG200M, DM & DMP only. 0/2V, 0/7V &  $-14/+6\text{dBm}$ .  
**SIZE & WEIGHT** 7" high x  $10\frac{1}{2}$ " x  $5\frac{1}{2}$ " deep. 10 lbs.

**TG200** **TG200D** **TG200M** **TG200DM** **TG200DMP**  
**£63** **£66** **£73** **£76** **£80**

## DIGITAL

**FREQUENCY** 0.2Hz to 1.22MHz on four decade controls.  
**ACCURACY**  $\pm 0.02\text{Hz}$  below 6Hz  
 $\pm 0.3\%$  from 6Hz to 100kHz  
 $\pm 1\%$  from 100 kHz to 300 kHz  
 $\pm 3\%$  above 300 kHz.  
**SINE OUTPUT** 5V r.m.s. down to  $30\mu\text{V}$  with  $R_s = 600\Omega$   
**DISTORTION**  $< 0.15\%$  from 15Hz to 15 kHz.  
 $< 0.5\%$  at 1.5Hz and 150kHz.  
**METER SCALES** 2 Expanded voltage &  $-2/+4\text{dBm}$ .  
**SIZE & WEIGHT** 7" high x  $10\frac{1}{2}$ " wide x 7" deep. 12 lbs.

**TG66B**  
Battery model. **£170**


**TG66A**  
Mains & battery model. **£190**

**LEVELL ELECTRONICS LTD.**  
Moxon Street, High Barnet, Herts. EN5 5SD  
Tel: 01-449 5028/440 8686

Prices include batteries and U.K. delivery. VAT extra. Optional extras are leather cases and mains power units. Send for data covering our range of portable instruments.

WW-004 FOR FURTHER DETAILS

# 'Phone-in Programme

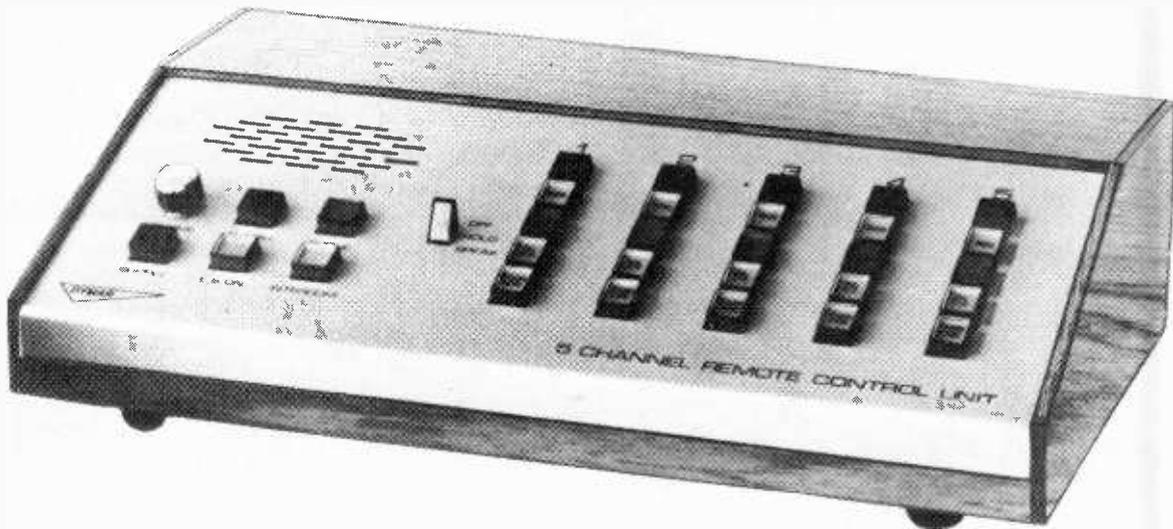

**When you can reach them. And they can reach you.  
Any time. You've got a Dymar system.**

Computer controlled VHF radiotelephone network. Sounds great. The coming thing. At Dymar it's come! And that's the Dymar difference.

Dymar designs systems that take all the local conditions into account. Terrain. Geographical distribution of the labour and the customers available to the user. Emergency situation control. Channel congestion. The lot.

Dymar does it with common frequency coverage using quasi-synchronous transmitters. With a CCIR compatible selective calling system. With automatic signal level selection. With computer control of signal routing.

Tomorrow's systems today. It's what you'd expect from a company 100% devoted to the radiotelephone business... and nothing else.


Discover the Dymar difference. Make contacting Dymar part of today's programme.

**DYMAR**

**the name in radiotelephone systems**

Dymar Electronics Limited, Colonial Way, Radlett Road, Watford,  
Herts. WD2 4LA. Tel. Watford 37321. Telex: 923035.  
Cables: Dymar Watford

WW-070 FOR FURTHER DETAILS

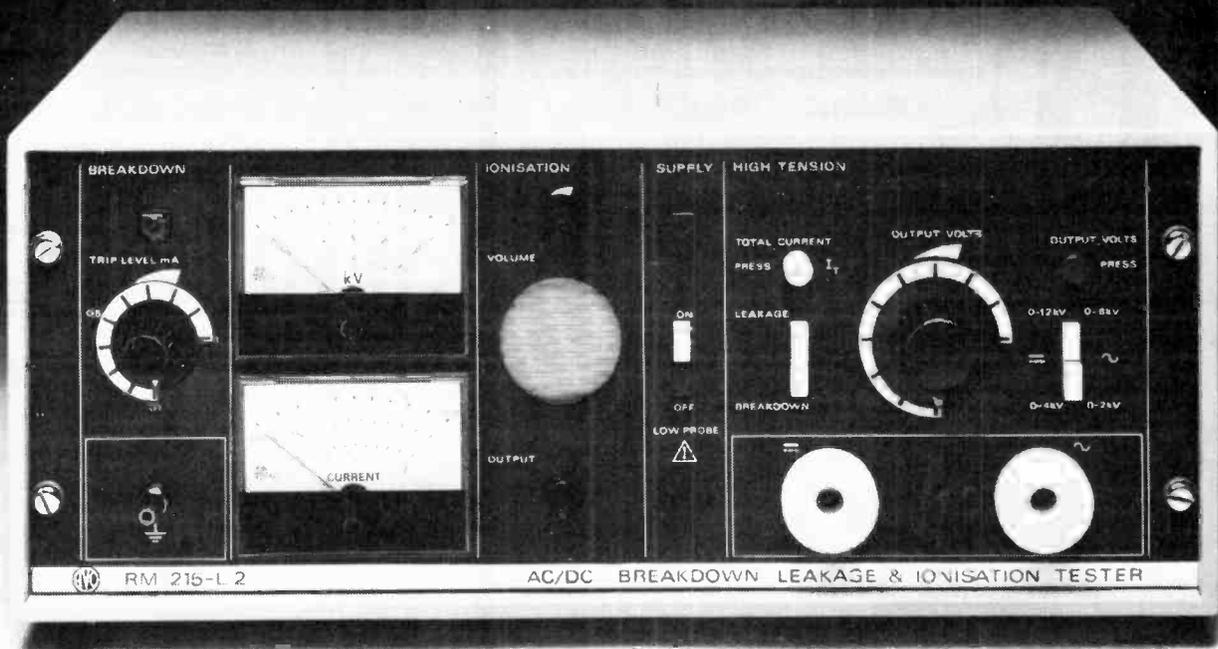

# Ion out your quality control problems

The AVO Breakdown and Ionisation Tester RM215-L/2 is specifically designed to help solve all manner of quality control problems.

It measures resistive leakage current under both AC & DC voltage testing conditions as well as total AC leakage current. Test voltages up to 12 kV DC and 6 kV AC are continuously variable and breakdown current level is adjustable up to 1 mA. A built-in loudspeaker gives audible detection of ionisation and there are connections for earphone or an oscilloscope.

The circuit features low internal resistance yet at the same time limits the maximum output current, even at short circuit.

With the RM215-L/2 you can carry out general flash testing, measurement of breakdown voltage – even after breakdown – and the detection (and counting) of spurious flashovers.

Equally suited to both destructive and non-destructive testing, the RM215-L/2 is a piece of test equipment you cannot afford to be without. If you have some problems that need to be 'ionised' out, get in touch for full details.

## APPLICATIONS

- Flash testing of electrical components.
- Measurement of breakdown voltage on electrical components and materials.
- Measurement of insulation resistance at high voltage.
- Measurement of d.c. leakage current.
- Measurement of a.c. leakage current and total current.
- Non-destructive insulation testing of materials and components.
- Detection of ionisation in electrical assemblies.

Designed to meet B.S., V.D.E. and I.E.C. Safety Requirements.



Avo Limited, Dover, Kent.  
Tel: Dover (0304) 202620.

Thorn Measurement Control  
and Automation Division.

WW — 056 FOR FURTHER DETAILS

[www.americanradiohistory.com](http://www.americanradiohistory.com)




# P.B. ELECTRONICS LTD.

SCOTLAND

ELECTRONIC - SCIENTIFIC - INSTRUMENTS

57 High Street, Saffron Walden, Essex CB10 2DP, England.  
Telephone: Saffron Walden 22876 Telex: 817201.

## S-DEC Solderless Breadboard 25p Off.

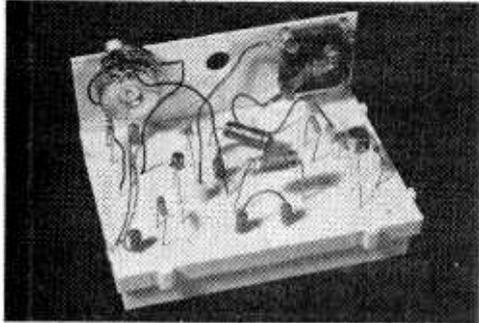

The world proved S-DEC can now be yours with 25P off list price take this coupon to your local dealer or send direct to us for immediate delivery.

S-DEC just plug components directly in, no soldering, use components over and over again.

With your S-DEC you receive FREE a booklet which gives a range of circuits which can be quickly assembled on the S-DEC including Radio-Receiver, VHF Radio-Microphone, 3 Stage Amplifier and many others, also FREE control panel for mounting switches, lamps etc.

S-DEC normally £1.98 with this advertisement £1.73

(When ordering direct send £2.08 to cover Post & VAT)


T-DEC normally £3.63 with this advertisement £3.38

(When ordering direct send £3.87 to cover Post & VAT)

U-DEC - A for discreet and use with I.C. send £4.31

(Mr. Troder for every coupon received PB will refund 25p)
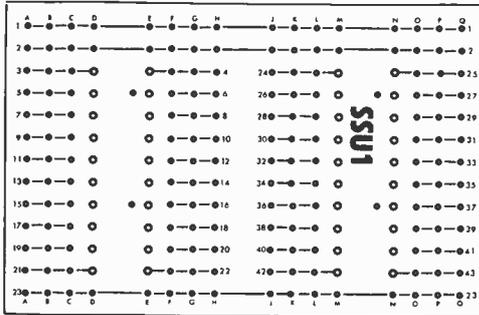
## NEW NEW PB DEC Super-Solder Boards. Low Cost.



Matched to the world famous range of DEC breadboard layouts PB introduce a new concept into printed circuit board assembly. Now you can buy off the shelf professional circuit boards which have the following features.

DEC SUPER - SOLDER BOARD SSU. Roller Tinned for super soldering.

Carefully engineered layout for maximum assembly efficiency bus-bars for power supplies.

No cutting and drilling of contact rails required.

The 208 contacts are identified by a letter number system.

SIZE OF BOARDS 5" x 3" APPROX, fibreglass, drilled, roller tinned.

Lay the prototype out on DEC-breadboards and then for small or large production runs use SUPER - SOLDER Boards.

Super - Solder Boards are available in packs of 1 or 3 off.


SUPER SOLDER BOARD SST1 for discreet circuits 1 off £0.59, 3 off £1.60.

SUPER SOLDER BOARD SSU1 for discreet and dil circuits 1 off £0.59, 3 off £1.60.

SUPER SOLDER BOARD SSN1 for discreet and dil circuits up to 40 lead .6" DIL and for direct insertion of TO5 .1" lead out sockets and packages 1 off £0.69, 3 off £2.00.

When ordering please add £0.40 for Post and VAT.
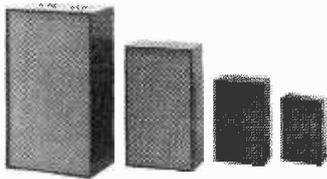
## Zippy Cabinets Ideal For All Assembly Cabinets.



Robust ABS plastic assembly boxes, front panel designed to be cut and drilled, slots inside for mounting circuit boards attractive colouring and styling.

TP 1 80 x 50 x 30 mm £0.72 1 OFF

TP 2 115 x 65 x 40 mm £1.27 1 OFF

TP 3 155 x 90 x 50 mm £1.62 1 OFF

TP 4 210 x 125 x 70 mm £2.27 1 OFF

Discount for quantity prices include Post & VAT.

Resist Coated Circuit Board Lowest price in U.K.

12" x 12" Glass Fibre 1/16 coated with resist £1.50 each.

Circuit Board Manufacture, Fast delivery, low Price, any circuit board made in days.

S DEC - T DEC - U DEC Accessories.

16 DIL ADAPTOR ..... £0.99

16 DIL with socket ..... £1.92

Single ended leads (packs of ten) £0.90

Double ended leads ..... £0.90

EXPERIMENT GUIDES used by all to teach electronics with DEC breadboards.

GUIDE A ..... 8 Projects ..... £1.50

GUIDE B ..... 10 Projects ..... £1.77

GUIDE C ..... 3 ADVANCED .. £0.90

GUIDE D ..... 10 Projects ..... £2.40

GUIDE E ..... 23 Projects ..... £4.20

NIGHT GUARD.

Dimmer with a difference, Guards your home from theft, SET, darkness comes, lights come on, dawn, lights go off.


Dims room lights up to 500 watts. £5.95 + £1.05 VAT & POST.

PB ELECTRONICS (SCOTLAND) LTD.  
57 HIGH STREET, SAFFRON WALDEN, ESSEX, CB10 1AA  
TEL: 0799 22876

ALL STOCKISTS OF DEC BREADBOARDS  
PLEASE NOTE PB ARE THE  
MANUFACTURERS AND SUPPLIERS,  
PLEASE SEND ALL ORDERS  
COMMUNICATIONS DIRECT.

# Stable companions
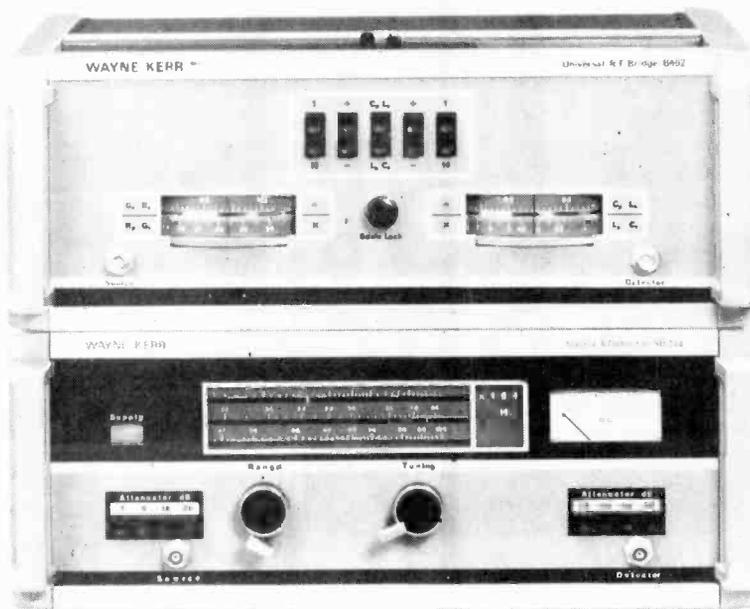
## Wide-range universal bridge **B602** 0.1-100MHz source/detector **SR268** from Wayne Kerr



The B602 transformer ratio arm bridge measures impedance in all four quadrants of the complex plane over the frequency range 100kHz to 10MHz. Because of novel features incorporated in the design, values from virtually a short circuit to an open circuit can be measured. This bridge has established a standard of performance and flexibility which is unobtainable from any other radio frequency bridge.

A standard inductor is included in the bridge network in addition to standards of capacitance and resistance enabling a periodic calibration of the scales which are correct at any frequency between 100kHz and 10MHz.

There are only two balance controls. One is direct reading in resistance and conductance, the other in capacitance and inductance and there is no interaction between them.

The stability realised allows a discrimination of 0.1% to be obtained for all types of measurement with a general accuracy of 1% over most of the impedance and frequency range.

The bridge is shown together with the SR268 Source and Detector which can also be used with other bridges in the Wayne Kerr range over the frequency band 100kHz to 100MHz. Nine frequency ranges are provided by this instrument and a single tuning control adjusts both source and detector to the exact frequency required.

Meticulous screening between the two sections provides freedom from bridge measurement errors due to leakage of the source signal into the detector. Common mode rejection transformers are incorporated in the input and output networks to reduce interference from unwanted signals, and push button attenuators are included to assist the logarithmic detector circuit to indicate approach of the bridge balance point.

### SPECIFICATION

#### B602

Frequency range:	100kHz to 10MHz
Accuracy:	1% up to 3MHz, 1pF to 10nF 10 $\Omega$ to 100k $\Omega$ 1 $\mu$ H to 10mH
Overall impedance range:	1fF to 1mF 100 $\mu\Omega$ to 100M $\Omega$ (10n $\Omega$ to 10k $\Omega$ ) 10pH to 10H

#### SR268

Frequency Range:	100kHz to 100MHz in 9 bands (SR268L 46.5kHz to 46.5MHz)
Frequency accuracy:	2-3% according to band used.
Short Term Frequency Stability:	0.01%
Output level:	0.5-2.0V according to band used
Output attenuator:	3, 6, 10, 20 dB additive steps, 75 $\Omega$
Input sensitivity for 10% meter deflection:	1 to 30 $\mu$ V according to frequency setting
Input attenuator:	4 steps of 20 dB, 75 $\Omega$
Detector bandwidth:	2-3% according to band used

For more information, either phone Bognor Regis (02433) 25811 or write to the address below:


## WAYNE KERR

Durban Road, Bognor Regis, Sussex  
Telex: 86120. Cables: Waynkerr, Bognor

*A member of the Wilmot Breeden group*

# 100 WATTS !

## HY200

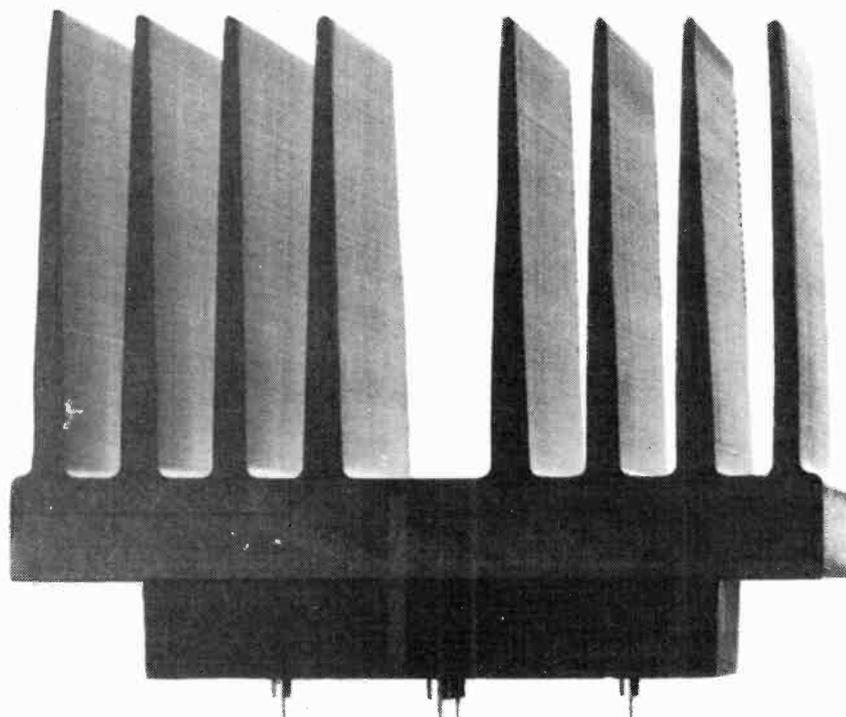

The HY200 is the latest hybrid amplifier from I.L.P. It has been designed to be virtually indestructible lending itself to domestic and industrial applications. Latest design techniques including thermal shutdown make the HY200 the most advanced amplifier of its kind in the World. Only five connections are required, input, output, power lines and earth.

#### Features:

Short Circuit Protection  
No External Heatsinking  
Thermal Shutdown  
Only Five Connections  
Low Distortion

Price £21.20 +VAT £5.30  
P&P free

#### Specifications:

Output Power 100 watts R.M.S. into  $8\Omega$   
Input Impedance  $100K\Omega$   
Input Sensitivity 500mV R.M.S.  
Distortion 0.05% Typical  
Signal: Noise 96dB  
Power Band Width 10Hz - 45KHz  $\pm 3$ dB  
Power Supply 45-0-45v D.C. at 2 Amps  
Weight 1 Kilo (2.2lb)  
Power Supply PSV90 suitable for one HY200  
Price £10.56 + VAT £2.64  
P&P free

TWO YEARS GUARANTEE ON ALL OUR PRODUCTS

**I.L.P. Electronics Ltd,**  
**Crossland House,**  
**Nackington, Canterbury,**  
**Kent CT4 7AD**  
**Tel (0227) 63218**

Please Supply \_\_\_\_\_  
Total Purchase Price \_\_\_\_\_  
I Enclose Cheque  Postal Orders  Money Order   
Please debit my Access account  Barclay card account   
Account number \_\_\_\_\_  
Name & Address \_\_\_\_\_  
Signature \_\_\_\_\_

# Now the Alpha costs less than the A\*\*\* will the 1567 engineers who are still without one please identify themselves?



It was two years ago that Alpha one was launched by Advance.

As a brand new concept in low cost digital multimeters.

Now, many thousands of instruments later, Alpha I and II are everywhere.

You, too, should claim your Alpha. And to help you, we're listing the advantages engineers of competing firms enjoy:

- ★ Low, low prices. Alpha I now costs only **£49** and Alpha II is now only **£57** including a mains power supply but excluding VAT.
- ★ Extraordinary battery longevity. One PP9 lasts up to a year in an Alpha I.
- ★ No backache. Alphas are small, light, but in a tough as blazes carrying case.
- ★ No problems – reliability is superb with long periods between recalibration.
- ★ No squinting. Our LEDs give bright, clear, unambiguous readouts.

**Do get the Gould Advance data on Alpha. You see, it's so much better.**

Gould Advance Limited  
Roebuck Road, Hainault, Essex, England.  
Telephone: 01-500 1000 Telex: 263785

**GOULD ADVANCE**

# BARR & STROUD **MODULAR FILTERING**

## EF3-04 Low Pass

Cut-off frequency variable from 0.1Hz to 100kHz

## EF3-03 High Pass


Cut-off frequency variable from 0.1Hz to 100kHz

## EF3-02 Low Pass

Cut-off frequency variable from 0.01Hz to 10kHz
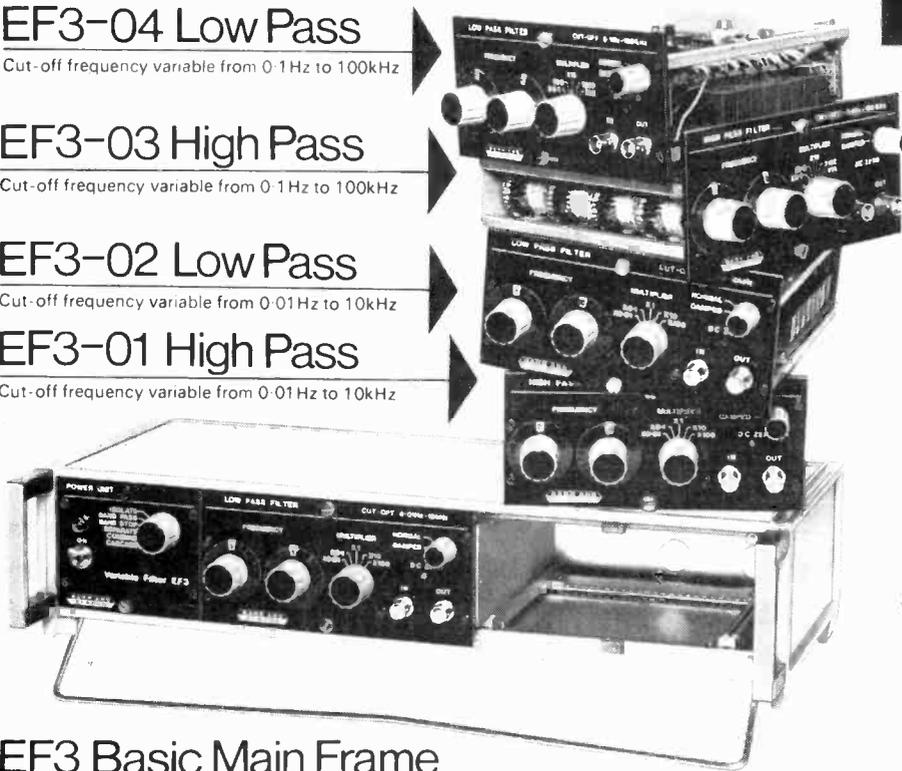
## EF3-01 High Pass

Cut-off frequency variable from 0.01Hz to 10kHz



EF3 Basic Main Frame

WW-059 FOR FURTHER DETAILS

Now **FOUR** Modules—and more to come!

The introduction of our EF3 Electronic Filter System was a breakthrough in electronic filtering, a System with options and interchangeability.

Now we introduce two additional modules to extend the scope and versatility of the EF3. To appreciate fully the technical and economic merits of the EF3 System you ought to have our detailed literature which we will be pleased to send. Continuing development of the EF3 System means that we will be announcing yet more modules in the near future.

Send now for full details to:



Glasgow and London

Barr & Stroud Limited,  
1 Pall Mall East, London SW1Y 5AU.  
Tel: 01-930 1541 Telex: 261877

# There's more scope in Scopex

The Scopex 4D25 is a portable 25 MHz dual-trace instrument suitable for all laboratory and field applications. It features a guaranteed measuring accuracy of 3% — and yet at £225\* is in a price bracket below any comparable instrument. Check these features and see why the 4D25 is a must for the discerning buyer.



- \* DC-25 MHz, full screen
- \* 3% accuracy
- \* Signal delay (both channels)
- \* One control for Trig Level and Polarity
- \* Timebase 200ms to 200ns  
    × 5 expansion
- \* Sensitivity 50V/cm to 10mV/cm

**SCOPEX** Write or telephone today:-  
Scopex Instruments Ltd., Pixmore Industrial Estate,  
Letchworth, Herts. Tel: Letchworth (04626) 72771

\*UK List ex VAT

WW-066 FOR FURTHER DETAILS

# Join the Digital Revolution

## Teach yourself the latest techniques of digital electronics

Computers and calculators are only the beginning of the digital revolution in electronics. Telephones, wristwatches, TV, automobile instrumentation — these will be just some of the application areas in the next few years

Are you prepared to cope with these developments?

This four volume course — each volume measuring 11 3/4" x 8 1/4" and containing 48 pages — guides you step-by-step with hundreds of diagrams and questions through number systems, Boolean algebra, truth tables, de Morgan's theorem, flipflops, registers, counters and adders. All from first principles. The only initial ability assumed is simple arithmetic


At the end of the course you will have broadened your horizons, career prospects and your fundamental understanding of the changing world around you

### Digital Computer Logic and Electronics

A Self-instructional Course

C. P. Gange MA (Cantab)  
A. W. Lunn BA (Cantab)

<b>Book 1</b>	Basic computer logic
<b>Book 2</b>	Logical circuit elements
<b>Book 3</b>	Designing circuits to carry out logical functions
<b>Book 4</b>	Flipflops and registers

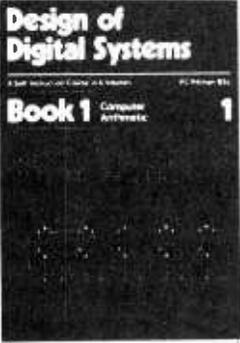

**Design of Digital Systems**  
Book 1 Computer Arithmetic

**£5.95** plus 50p p&p

Design of Digital Systems contains over twice as much information in each volume as the simpler course Digital Computer Logic and Electronics. All the information in the simpler course is covered as part of the first volumes of Design of Digital Systems which, as you can see from its contents, also covers many more advanced topics

*Also available — a more advanced course in 6 volumes:*

1. Computer Arithmetic
2. Boolean Logic
3. Arithmetic Circuits
4. Memories & Counters
5. Calculator Design
6. Computer Architecture

*Offer.* Order this together with Digital Computer Logic & Electronics for the bargain price of £9.25, plus 50p p&p.

**Designer  
Manager  
Enthusiast  
Scientist  
Engineer  
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

### Guarantee — no risk to you

If you are not entirely satisfied with Digital Computer Logic and Electronics or Design of Digital Systems, you may return them to us and your money will be refunded in full, no questions asked.



**£3.95**

plus 50p packing and surface mail anywhere in the world.

Quantity discounts available on request.

Payment may be made in foreign currencies.

VAT zero rated.

To: Cambridge Learning Enterprises,  
FREEPOST, St. Ives, Huntingdon, Cambs.  
PE17 4BR

\*Please send me . . . . . set(s) of Digital Computer Logic and Electronics at £4.45 each, p&p included  
\*or . . . . . set(s) of Design of Digital Systems at £6.45 each, p&p included  
\*or . . . . . combined set(s) at £9.75 each, p&p included

Name . . . . .

Address . . . . .


. . . . .

. . . . .

\*delete as applicable  
No need to use a stamp — just print FREEPOST on the envelope.

WW '2

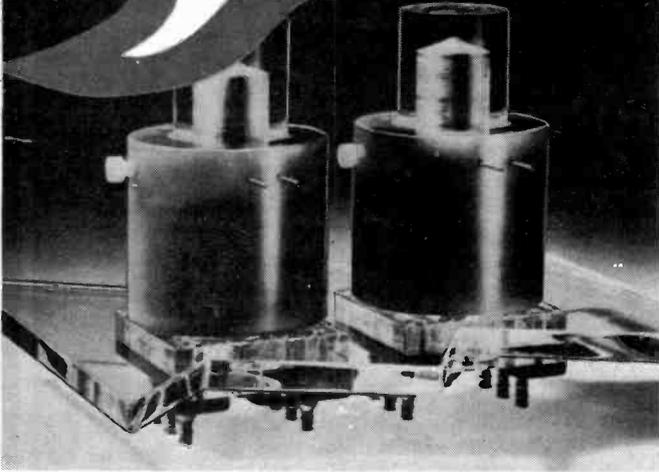*"He's asking  
for a  
reed relay  
assembly  
with a 30kV  
isolated coil"*



People often bring their need to us. They know the Whiteley speciality. Being helpful! And the item that started life as a customer request, joins the Whiteley product list, ready to help other designers over a problem. You, perhaps? Consider a neat relay assembly — one or two dry reed switches with a rating of 25W, housed in a mounting tube, with either 'normally open' or 'change-over' contacts. Around them, a coil operating from 8, 12, 24 or 50V supply, 30kV isolated from the contacts. The whole unit mounting on a 0.25" insulating plate with a couple of 3 way tag strips. If you're interested, ask for a data sheet. But more, keep Whiteley in mind as the people who make useful things.

*Surprising how often you'll find*

# Whiteley make it.

Whiteley Electrical Radio Co. Ltd.

Mansfield, Notts NG18 5RW, England. Tel: 0623 24762.

WW—010 FOR FURTHER DETAILS



**STABILISED TWIN POWER  
SUPPLIES TO 30V AT 2AMP**

# LINSTEAD ELECTRONICS

ROSLYN RD, LONDON N15 5JB  
01-802-5144

MAIN AGENTS

IRELAND:	LENNOX LTD P.O. BOX 212A DUBLIN 2
DENMARK:	SCANFYSIK AB 13/15 HJORRINGADE DK-2100 COPENHAGEN
SWEDEN:	EMI SVENSKA AB TRITONVAGEN 17 FACK S-171 19 SOLNA 1
NORWAY:	EMI NORSK AS POSTBOKS 42 KORSVOLL OSLO 8
MALAYSIA:	LEC Sdn Bhd P.O. BOX 60 BATU-PAHAT
SOUTH AFRICA:	PROTEA (PTY) 38 FARADAY STREET JOHANNESBURG

WW—076 FOR FURTHER DETAILS

# Audio Laboratory Instruments

To expand the distribution of Audio Laboratory Instruments RADFORD are looking for new dealer/agents outside the United Kingdom. If you are a supplier of laboratory instruments to professional and industrial end users it could be to your advantage to learn more about RADFORD audio measuring equipment.

Write today for leaflets and details of franchised dealership.


Radford Laboratory Instruments Ltd  
Ashton Vale Road  
Bristol BS3 2HZ England



- LDO3. Low Distortion Oscillator**  
Frequency range: 10Hz – 100kHz.  
Distortion: Distortion less than 0.002% over audio band.  
Size: 17" x 7" x 8 3/4". £275.00
- LDO3B. Low Distortion Oscillator**  
As LDO3 but additionally fitted with output amplifier and transformer providing a 600 ohm floating balanced output.  
Unbalance: –80dB, 1kHz. –60dB 10kHz. £375.00
- DMS3. Distortion Measuring Set**  
Frequency range: 5Hz – 50kHz.  
Measurement down to 0.001%. £225.00
- HSV1. High Sensitivity Voltmeter**  
Average reading: 10µV to 300V f.s.d. £125.00
- HSV2. High Sensitivity Voltmeter**  
True r.m.s. reading. 10µV to 300V f.s.d. £175.00
- ANM1. Audio Noise Meter and High Sensitivity Voltmeter**  
Average reading: 10µV to 300V f.s.d.  
Includes Wide band, Audio band, IEC curve 'A' and CCIR weighting networks. Illustrated above. £150.00
- ANM2. Audio Noise Meter and High Sensitivity Voltmeter**  
As ANM1 but true r.m.s. reading. £200.00

WW-051 FOR FURTHER DETAILS

## METER PROBLEMS?

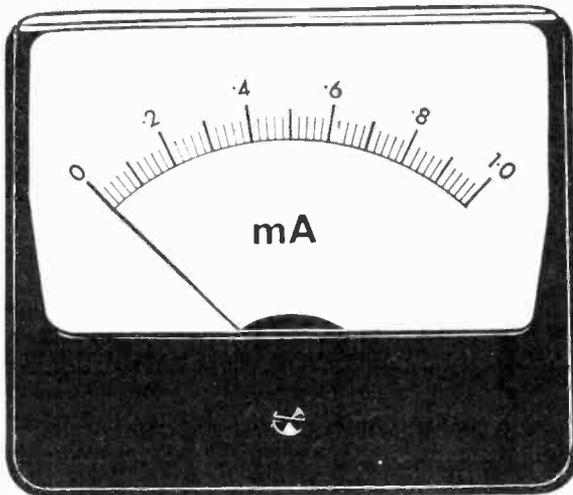

137 Standard Ranges in a variety of sizes and stylings available for 10-14 days' delivery. Other ranges and special scales to order.

Full Information from:

**HARRIS ELECTRONICS (London)**

138 GRAYS INN ROAD, W.C.1 Phone: 01/837/7937

WW-053 FOR FURTHER DETAILS

## \*AUTOCRAT

Farnell offer the only Digital Multimeter with all these features:-

AUTORANGING AUTOPOLARITY AUTOZERO

SIX RESISTANCE RANGES LARGE DISPLAYS

A.C. AND D.C. VOLTS AND CURRENT

TEMPERATURE MEASUREMENT

at £140 (mains powered version)  
or £165 (mains/battery version)

*\*The absolute leader in its class*

Details from:  
Farnell Instruments Ltd.  
Wetherby, W. Yorks, LS22 4DH  
Tel: 0937-3541 or 01-864 7433



WW-074 FOR FURTHER DETAILS

# PETITE PRECISION!

A 12V DC POWER TOOL FOR THE DESIGN AND RESEARCH ENGINEER

AVAILABLE IN KIT FORM OR SEPARATES

Diameter 33mm  
Weight 160g  
Length 125mm  
Torque 105cmg  
RPM  
approx. 3000  
at 12V DC  
Power 9/14V DC  
Batteries  
or AC/DC  
transformer



Drill. £7.00 P&P 35p

## EXAMPLE OF FRENCH PRECISION ENGINEERING



Flexible drive.  
£5.00  
P&P 35p

Now in use by the following:  
GPO, BBC, Atomic Energy  
Authority, British Nuclear  
Fuels, Weekend TV, Ministry  
of Defence, Hospitals,  
Opticians, etc.



Stand £3.76  
P&P 58p

UK DISTRIBUTOR  
**PRECISION PETITE LTD**  
(Les Applications Rationelles Paris)  
119A HIGH STREET  
TEDDINGTON, MIDD. UK  
TEL. 01-977 0878

SAE for leaflets, price list and order form

WW—043 FOR FURTHER DETAILS

# Inland motors do the things most motors can't do

Inland direct drive torque motors, tachogenerators and DC servo motors respond in milliseconds to rapidly programmed commands and give precise control of position, speed or tension. Their high quality and extreme accuracy makes them particularly suitable for instrumentation, data handling and computer peripheral sub-systems like magnetic tape drives, incremental transport drives and high speed printout systems.

Sizes range from a tiny "inch-cube" torque motor which will give 7oz.in., to larger motors capable of 3,000 lb. ft. Speeds from zero to 10,000 r.p.m. are typical. And all models have high thermal capacity under severe duty cycles. We offer competitive prices, prototype services and application engineering support.

Get in touch and see what Inland can do for you.



## INLAND MOTOR DIVISION

Kollmorgen (UK) Limited,  
219 Kings Road, Reading, Berks.  
Tel: Reading (0734) 68980/65929  
Telex: 847032

For larger motors for machine tool applications contact:  
Merit House, Edgware Road, Colindale, London NW9  
Tel: 01-205 0500/0538 Telex: 923416



WW — 017 FOR FURTHER DETAILS

# Telford Oscilloscope cameras

Type A modular system with widest range of film backs, lenses, viewing systems and adaptors to meet virtually all requirements.

Plus inexpensive Type P (prices from £50) utilising coaterless Polaroid® film and Type C with economical 35mm film for continuous feed.

More complete details available on request from:

## Telford PRODUCTS LTD.

WADSWORTH ROAD PERIVALE GREENFORD MIDD. ENGLAND Telephone: 01-998 1011 Telex: 935524

DAVALL A MEMBER COMPANY OF BENTHAM INDUSTRIES LIMITED

®Reg. Trade Mark.

WW—041 FOR FURTHER INFORMATION

# TELCON

**soft magnetic shields  
magnetic alloys  
and cores**

### SHIELDS




We manufacture a wide range of Mumetal shielding cans and boxes and fabricate shields for CRT's, transformers etc., to customers' own designs. These are made to the highest standards and have optimum properties (as sole UK/European manufacturers of Mumetal we have years of experience). For large quantities we recommend the 'Telform' process which provides maximum uniformity, extra close tolerance and maximum performance. For R & D and prototype work - try 'Telshield', do-it-yourself, wrap-around foil. Supplied in handy packs costing around £5.00 - it's simple and quick to use.

### ALLOYS

Typical magnetic properties	Initial permeability (dc μs)	Maximum permeability	Saturation ferric induction (Tesla)	Remanence from saturation (Tesla)	B <sub>100</sub> (Tesla)	Coercivity H <sub>c</sub> (A/m)	Hysteresis Loss (J/m <sup>3</sup> /cycle)	Curie point (°C)
Mumetal	55 000	240 000	0.77	0.37	1.0	3.2	350	
Mumetal Plus	69 000	300 000	0.77	0.37	0.8	1.3	350	
Supermumetal	127 000	350 000	0.77	0.4	0.55	0.9	350	
Orthomumetal				0.8	0.7	2.4	7.5	350
Satmumetal	65 000	240 000	1.5	0.7	2.0	12	550	
Radiometal 50	6 000	30 000	1.6	1.0	8.0	40	525	
Super Radiometal	11 000	100 000	1.6	1.1	3.2	20	525	
Radiometal 36	3 000	20 000	1.2	0.5	16.0	75	275	
Hyrb Radiometal	3 500	30 000	1.4	1.0	8.0	45	525	
Hyrb Radiometal		70 000	1.5	1.35	8.0	50	525	
HCR Alloy		100 000	1.54	1.5	10	65	525	
Permendur	1 000	7 000	2.35	1.5	135	1270	975	
Supermendur		70 000	2.35	2.05	19.0	170	975	
Permendur 24	250	2 000	2.35	1.65	950	925		
Vicalloy			1.5	1.0	20 000	12 x 10 <sup>4</sup>		


### CORES

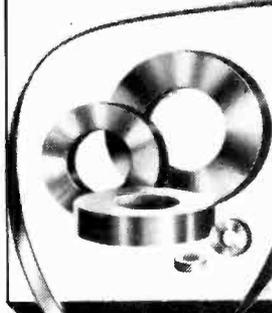

We manufacture a wide range of strip wound, high permeability cores in the Mumetal, Radiometal, Permendur and HCR groups of alloys. These cover a wide range of applications including: current, pulse, telecommunication, earth leakage transformers, relays, magnetic amplifiers, synchros, high speed generators, and transducers. All Telcon products are made to the highest standards and undergo stringent testing before despatch.


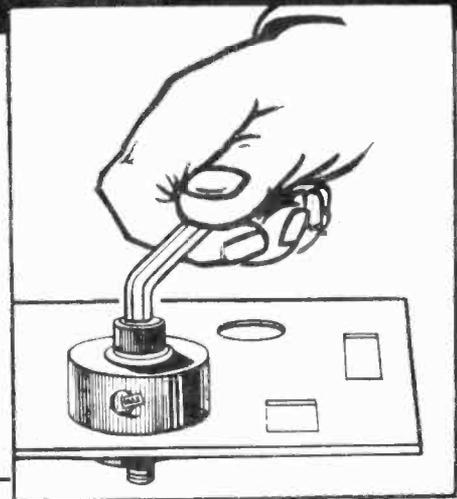
## SHEET METAL PUNCHES FOR QUICK CLEAN HOLES



- Easiest and quickest way of punching holes in sheet metal (up to 1.625mm).
- Simple operation ● **100% British**
- Burr-free holes — no jagged edges
- **57 Metric and Linear sizes** (Lists on application)

**Used all over the world by:** Government services — Atomic, Military, Naval, Air, G.P.O. and Ministry of Works; Radio, Motor and Industrial manufacturers, Plumbing and Sheet Metal Trades, Garages, etc.

*Obtainable from leading tool factors*

*Wholesale & Export enquiries to:*


**"Q-MAX" (ELECTRONICS) LTD**  
44 PENTON STREET · LONDON N19QA Tel: 01-278 2500

WW-028 FOR FURTHER DETAILS

**TELCON**  
Telcon Metals Ltd. Manor Royal,  
Crawley, Sussex, Crawley: 28800

WW-065 FOR FURTHER DETAILS

# brandenburg's Olympian view.

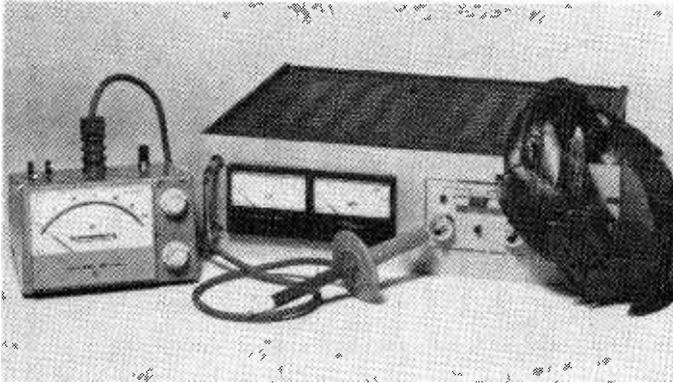

## Our Ensign range and HV meters.

Brandenburg produce a wider range of power supplies and associated equipment than any other British manufacturer.

There's our high technology Ensign range of HV power supplies. Featuring the exceptionally high stability level of 10 parts in  $10^{-6}$  at voltage outputs from 3—30kV at 500  $\mu$ A to 6—60 kV at 250  $\mu$ A, the Ensign is designed for 19" rack mounting. Operation is from 200—250V r.m.s. 50 Hz supply at ambient temperatures between 0°C and 35°C.

And our HV meters. Designed for accurate measurements of line voltages in the ranges 0—5kV; 0—15kV and 0—30kV at better than 1% accuracy at full scale or 1% f.s.d. Our probe and cable assemblies are available separately.

*We at Brandenburg believe Britain does not do enough at or for the Olympic Games. So, as we are British through and through, we thought we would get our industry involved.*

Please use our enquiry number and, apart from receiving full information on our Ensign range and meters, it could be the first step in your winning a free trip to the Montreal Olympics. We'll send you an entry form for our Olympian Competition which is, we are sure you'll agree, great fun. Get in training; use your pen now.

# brandenburg

Due to our continued expansion, we have vacancies for sales engineers, development engineers and production personnel.


WW 079 FOR FURTHER DETAILS

For printed circuit boards . . .

## It pays to know the right drill

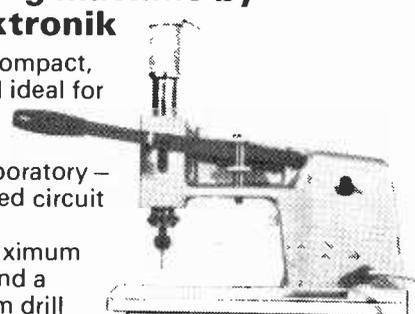**KB-2 drilling machine by Kema Elektronik**

The KB-2 is a compact, high-speed drill ideal for all precision drilling tasks in workshop or laboratory — especially printed circuit board work. With a 2mm maximum drill diameter, and a 20mm maximum drill depth, it runs at 15,000 rpm with voltage (variable) 220 volts and maximum power 25 VA. Measuring  $13\frac{1}{2}'' \times 5\frac{1}{2}'' \times 10''$ , the KB-2 is Swiss precision engineered, extremely reliable and moderately priced.



For full details, contact:  
**SPECIAL PRODUCTS DISTRIBUTORS LTD.**  
81 Piccadilly, London W1V 0HL. (01-629 9556)

WW—011 FOR FURTHER DETAILS



## sanwa MULTI TESTERS

USED THROUGHOUT THE WORLD, SANWA'S EXPERIENCE OF 30 YEARS ENSURES ACCURACY, RELIABILITY, VERSATILITY, UNSURPASSED TESTER PERFORMANCE. COMES WITH EVERY SANWA.

6 Months' Guarantee		Excellent Repair Service	
MODEL P2B	£11.75	MODEL F80TRD	£26.40
MODEL JP50	£12.80	MODEL AT45	£23.15
MODEL BX 505	£22.90	MODEL 380CE	£29.12
MODEL YX360TR	£14.90	MODEL N101	£31.85
MODEL U50DX	£16.10	MODEL 460ED	£35.13
MODEL A303TRD	£19.15	MODEL EM800	£74.50
MODEL K3D THD	£24.20	MODEL R1000CB	£75.27


**THESE PRICES DO NOT INCLUDE V.A.T.**  
Cases extra, available for most meters, but not sold separately

Please write for illustrated leaflet of these and other specialised Sanwa meters

**SOLE IMPORTERS IN U.K.**  
**QUALITY ELECTRONICS LTD.**  
47-49 HIGH STREET, KINGSTON-UPON-THAMES, SURREY. KT1 1LP  
Tel: 01-546 4585

WW—014 FOR FURTHER DETAILS

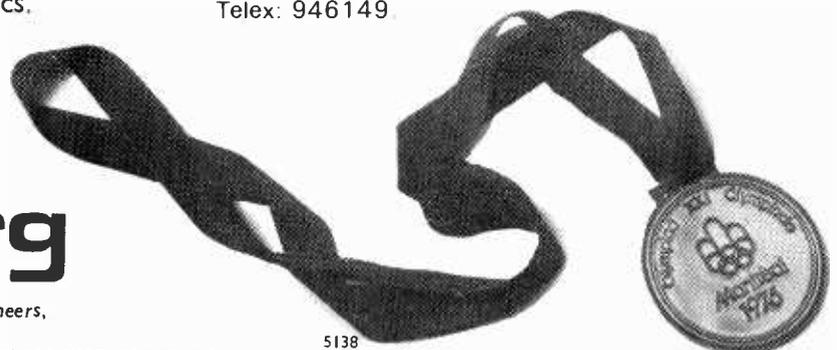Brandenburg Limited,  
939 London Road,  
Thornton Heath,  
Surrey CR4 6JE  
England.  
Telephone: 01-689 0441.  
Telex: 946149.



5138

*Litesold*

New - Thermostatic - Compact  
Fast - Accurate - Self Contained  
Adjustable

# TC50

## Thermostatic Soldering Iron



The new Litesold TC50 thermostatic soldering iron is specially designed for production line use in the electronics industry.

- |   |   |
|---|---|
| <ul style="list-style-type: none"> <li>* <b>COMPACT</b> Only 3" from tip to handle. Weighs only 2½ oz. without flex. Less tiring to use.</li> <li>* <b>SELF CONTAINED</b> Mains version requires no power unit. 24 volt version uses existing soldering iron power units.</li> <li>* <b>ADJUSTABLE</b> Simple Allen screw adjustment between 180°C and 420°C whilst running without changing bits.</li> <li>* <b>ECONOMIC</b> Better performance at lower cost than many other thermostatic irons.</li> </ul> | <ul style="list-style-type: none"> <li>* <b>FAST</b> Reaches 350°C in less than 90 secs. Recovery from 300°C to 350°C in 10 secs.</li> <li>* <b>ACCURATE</b> Holds set temperature in any attitude with no overshoot.</li> <li>* <b>VERSATILE</b> Slip-on long-life bits in 6 shapes and sizes.</li> <li>* <b>SAFE</b> Indicator lamp in handle shows operation of control.</li> <li>* <b>DETAILS</b> Leaflet giving full details and specification available now.</li> </ul> |
|---|---|

# LIGHT SOLDERING DEVELOPMENTS LTD


97-99, Gloucester Road, Croydon, CRO 2DN. 01-689 0574

34b

WW-084 FOR FURTHER DETAILS
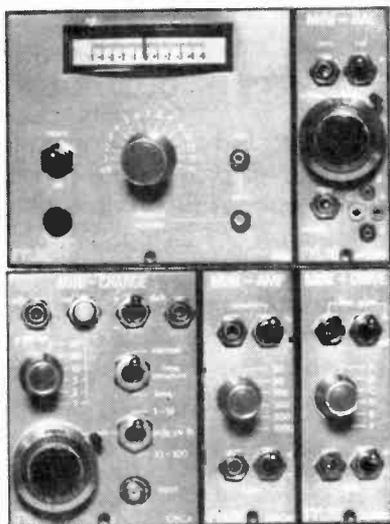
# FYLDE

TRANSDUCER and RECORDER  
AMPLIFIERS and SYSTEMS



reliable high performance & practical controls. individually powered modules—mains or dc option single cases and up to 17 modules in standard 19" crates small size—low weight—realistic prices.


# FYLDE

Fylde Electronic Laboratories Limited.

49/51 Fylde Road Preston  
PR1 2XQ  
Telephone 0772 57560

WW-026 FOR FURTHER DETAILS

# GROOVAC

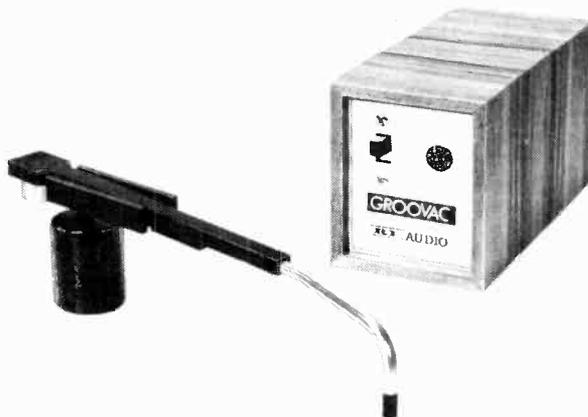

## vacuum record cleaner

Vacuum cleaning is the best way to remove dust, especially fine dust. Now with the Groovac, vacuum cleaning is available for extracting the particles from inside record grooves which are responsible for record and stylus wear — while your record is playing.

For full details please write to:—


# RI AUDIO

Kernick Road, Penryn  
Cornwall TR10 9DQ, England  
Telephone: Penryn 72753

WW-040 FOR FURTHER DETAILS
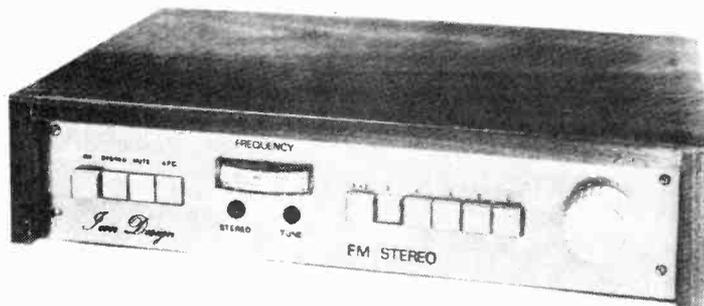
## ARE YOU HAVING TROUBLE WITH THE WIRELESS WORLD TUNER?

The kits we supply are fully guaranteed to work, and if trouble should arise we can, and do, put it right. But there are possibly thousands of tuners about which we know nothing, because the parts were not purchased from us. If you have one of these tuners and are having any sort of trouble with its construction or operation, we would like to help. Why? Well, we believe in our design, and know that if it is built correctly it will work, and work better than most. Unfortunately, things are not always as simple as they seem; there were misprints in the article, 'equivalent' devices are not always the same, and a simple dry joint can take a long time to trace. So, if you have built our tuner, or are thinking of doing so, why not write now for your—



### FREE TROUBLE-SHOOTING KIT

This includes:

- 11-page article reprint
- Full list of errors, etc.
- Voltage check chart
- Checking routine and
- Diagnostic hints

In fact all you need to know to get it working the way it was intended to work. Please send a S.A.E. size A5 (6 x 8½ min) today, as this offer is only open up to 1st Jan.

If you haven't started yet, why not avoid all possibility of trouble and buy one of our kits. You will get an immediate acknowledgement, prompt delivery ex-stock, a guarantee of success or free repair, in fact a complete after-sales service by the designers.

All our sub-assemblies are available ready built and tested for even less trouble, or you may have a fully assembled tuner with a **five year** guarantee. Send today for full details (S.A.E., please) to:


Main Tuner Board Kit . . . £24.55  
 Decoder Board Kit . . . . . £7.05  
 Full Tuner Kit . . . . . £85.00  
 Ready built . . . . . £102.00  
 (+25% VAT)

*Icon Design*

33 RESTROP VIEW  
 PURTON, WILTS., SN5 9DG

A PEACEFUL CHRISTMAS TO YOU ALL

## HIGH POWER DC-COUPLED AMPLIFIER

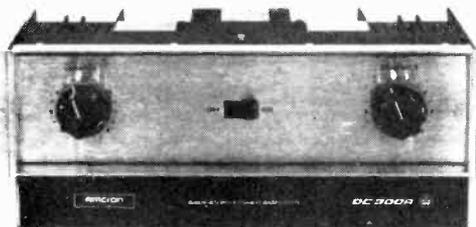

- ★ UP TO 500 WATTS RMS FROM ONE CHANNEL
- ★ DC-COUPLED THROUGHOUT
- ★ OPERATES INTO LOADS AS LOW AS 1 OHM
- ★ FULLY PROTECTED AGAINST SHORT CCT, MISMATCH, ETC.
- ★ 3 YEAR WARRANTY ON PARTS AND LABOUR

The DC300A Power Amplifier is the successor to the world famous DC300 which is so widely used in Industrial, and Research applications in this country. It is DC-coupled throughout so providing a power bandwidth from DC to over 20,000Hz. The ability of the DC300A to operate without fuss into totally reactive loads while delivering its full power, and maintaining its faithful reproduction of Pulse or complex waveforms has established the DC300A as the world's leading power amplifier. Each of the two channels will operate into loads as low as 1 ohm, and the amplifier can be rapidly connected as a single ended amplifier providing over 650 watts RMS into a 4 ohms load, and still providing a bandwidth down to DC. Below is a brief specification of the DC300A, but if you require a data sheet, or a demonstration of this fine equipment please let us know.

Power Bandwidth	DC-20kHz @ 150 watts + 1db, - 0db.
Power at clip point (1 chan)	500 watts rms into 2.5 ohms
Phase Response	+0. -15° DC to 20kHz, 1 watt 8Ω
Harmonic Distortion	Below 0.05% DC to 20kHz
Intermod. Distortion	Below 0.05% 0.01 watt to 150 watts
Damping Factor	Greater than 200 DC to 1kHz at 8Ω
Hum & Noise (20-20kHz)	At least 110db below 150 watts
Other models in the range: D60 — 60 watts per channel	

Slewing Rate	8 volts per microsecond
Load impedance	1 ohm to infinity
Input sensitivity	1.75 V for 150 watts into 8Ω
Input Impedance	10K ohms to 100K ohms
Protection	Short, mismatch & open cct. protection
Power supply	120-256V, 50-400Hz
Dimensions	19" Rackmount, 7" High, 9½" Deep
D150 — 150 watts per channel	



**MACINNES LABORATORIES LTD**

MACINNES HOUSE, CARLTON PARK INDUSTRIAL ESTATE,  
 SAXMUNOHAM, SUFFOLK IP17 2NL  
 TEL: (0728) 2262 2615

WW-064 FOR FURTHER DETAILS


## S-2020TA STEREO TUNER/AMPLIFIER KIT

### NEW PRODUCT

*A high-quality push-button FM Varicap Stereo Tuner combined with a 20W r.m.s. per channel Stereo Amplifier.*

**Brief Spec.** Amplifier: Low field Toroidal transformer, Mag. input, Tape In/Out facility (for noise reduction unit, etc), THD less than 0.1% at 20W into 8 ohms. All sockets, fuses, etc. are PC mounted for ease of assembly. Tuner section: uses Mullard LP1186 module requiring no RF alignment, ceramic IF, INTERSTATION MUTE, and phase-locked IC stereo decoder. LED tuning and stereo indicators. Tuning range 88–104MHz. 30dB mono S/N @ 1.8µV. THD typ. 0.4%.

**PRICE: £47.95 + 99p p&p + VAT.**

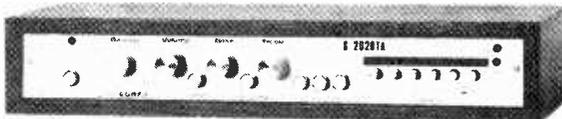

**SOLID MAHOGANY CABINET**



## NELSON-JONES STEREO FM TUNER

*A very high performance tuner with dual gate MOSFET RF and Mixer front end, triple gang varicap tuning, and dual ceramic filter/dual IC IF amp.*

**Brief Spec.** Tuning range 88–104MHz. 20dB mono quieting @ 0.75µV. Image rejection—70dB. IF rejection—85dB. THD typically 0.4%.

IC stabilized PSU and LED tuning indicators. Push-button tuning and AFC unit. Choice of either mono or stereo with a choice of stereo decoders.

**PRICE: Mono £25.46 + 85p p&p + VAT;**

**With Portus-Haywood Decoder £31.96 + 85p p&p + VAT;**

**With ICPL Decoder £29.73 + 85p p&p + VAT.**


### NEW PRODUCT

## S-2020A AMPLIFIER KIT

*Developed in our laboratories from the highly successful "TEXAN" design. PC mounting potentiometers, switches, sockets and fuses are used for ease of assembly and to minimize wiring.*

**Typ. Spec.** 20 + 20W r.m.s. into 8-ohm load at less than 0.1% THD. Mag. PU input S/N 60dB. Radio input S/N 72dB. Head-phone output. Tape In/Out facility (for noise reduction unit, etc). Toroidal mains transformer.

**PRICE: £29.95 + 99p p&p + VAT.**

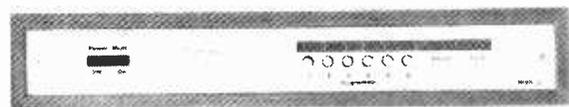

## STEREO MODULE TUNER

*A low-cost Stereo Tuner based on the Mullard LP1186 RF module requiring no alignment. The IF comprises a ceramic filter and high-*

*performance IC. Variable INTERSTATION MUTE. PLL stereo decoder IC.*

**Typ. Spec.** Sens. 30dB S/N mono @ 1.8µV. Tuning range 88–104MHz. LED sig. strength indicator. LED Stereo indicator. THD typically 0.4%.

**PRICE: Stereo £26.32 + 85p p&p + VAT. Mono £22.40 + 85p p&p + VAT.**

**ALL THE ABOVE KITS ARE SUPPLIED COMPLETE WITH ALL METALWORK, SOCKETS, FUSES, NUTS AND BOLTS, KNOBS, FRONT PANELS, SOLID MAHOGANY CABINETS AND COMPREHENSIVE INSTRUCTIONS.**

## SUB ASSEMBLIES

### BASIC NELSON-JONES TUNER

Supplied as a printed circuit board with all components and screening box to build a varicap tuner module. Performance spec as above for complete N-J Tuner. For suitable stereo decoders see below. (Illustrated without screening box.)

**PRICE: £12.88 + 25p p&p + VAT.**



### BASIC MODULE TUNER

Supplied as a printed circuit board with all components and screened Mullard LP1186, to build a mono or stereo tuner module. Performance spec as above for Stereo Module Tuner complete kit.

**PRICE: Mono £11.11 + 25p p&p + VAT; Stereo £13.89 + 25p p&p + VAT.**



### PORTUS-HAYWOOD PHASE-LOCKED STEREO DECODER

Mk II version of this design (WW Sept. 1970). The lowest distortion phase-locked stereo decoder kit available (Typ. 0.05% @ N-J Tuner O/P level). Separation 40dB up to 15KHz. Complete kit comprises PCB and all components, inc. stereo LED.

**PRICE: £7.68 + 25p p&p + VAT.**



### PHASE-LOCKED IC DECODER

Integrated circuit phase-locked stereo decoder based on the MC1310. THD typically 0.3%. Separation 40dB @ 1KHz.

**PRICE: £4.27 + 20p p&p + VAT.**



### PUSH-BUTTON UNIT

The six-position push-button unit used in our tuners and tuner/amp. Each track has the required diode law for stability of tuning. There are approx. 40 turns on each button and there are six separate moving pointers. An AFC disable switch is incorporated with each button. The unit is finished in black with red pointers.

**PRICE: £3.00 + 20p p&p + VAT.**



*Please send SAE for complete lists and specifications.*

**INTEGREX LIMITED,** Portwood Industrial Estate, Church Gresley, Burton-on-Trent, Staffs, DE11 9PT.  
Tel. Swadlincote (0283 87) 5432. Telex 377106.


## A message for dealers in exclusive high quality audio equipment — everywhere.

It is now proposed to expand the distribution of RADFORD products by supplying from the factory in BRISTOL direct to franchised dealers outside the United Kingdom.

If you have a discriminating clientele looking for the finest audio equipment and loudspeaker components available, you could profit from a direct RADFORD franchise.

Write today for details and leaflets.

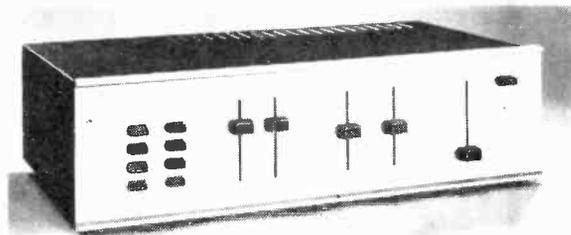Radford Audio Ltd  
Ashton Vale Road  
Bristol BS3 2HZ England



### ZD22

#### Stereo Pre-amplifier Control Unit

A stereo pre-amplifier of virtually zero distortion. Inputs for disc, tuner, and two tape machines. Size 17" x 4 $\frac{3}{4}$ " x 10" deep.

£145.00

### HD250 Stereo Integrated amplifier

Incorporates ZD22 pre-amplifier with low distortion power amplifier of 50 watts per channel into 4-8 ohms load. Headphone output. Illustrated above. Size 17" x 4 $\frac{3}{4}$ " x 11".

£195.00

### ZD100 Power amplifier

Power output 120 watts in 4 ohms and 75 watts into 8 ohms. Distortion less than 0.004% up to clip level. Size 17" x 4 $\frac{3}{4}$ " x 13".

£175.00

### ZD200 Power amplifier


Power output 250 watts into 4 ohms and 150 watts into 8 ohms. Distortion less than 0.004% up to clip level. Size 17" x 7" x 13".

£295.00

WW—052 FOR FURTHER DETAILS

## FAST RESPONSE STRIP CHART RECORDERS


Made in USSR

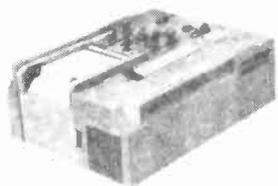

Type H3020-1  
Single pen

### Specification

Basic error.....	2.5%
Sensitivity.....	8mA F.S.D.
Response.....	0.2 sec.
Width of each channel.....	80mm
Chart speeds, selected by push buttons.....	0.1—0.2—0.5—1—2.5— —5—12.5—25mm/sec.
Chart drive.....	200-250v 50Hz

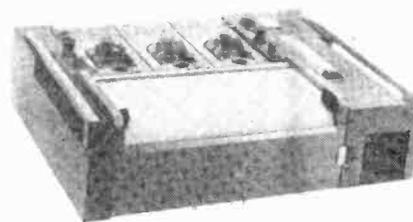

Type H3020-3  
Three-pen

### Recording:

Syphon pen directly attached to moving coil frame, curvilinear co-ordinates

### Equipment:

Marker pen, Timerpen, Paper footage indicator, 10 rolls of paper, connectors, etc.

### Dimensions:

H320-1: 285x384x16.5mm  
H320-3: 475x384x16.5mm

PRICE: H320-1 £80.00

H320-3 £130.00

Exclusive of VAT

Available for immediate delivery

## Z & I AERO SERVICES LTD.


44A WESTBOURNE GROVE, LONDON W2 5SF

Tel. 01-727 5641

Telex: 261306

WW—008 FOR FURTHER DETAILS

## ELECTRONIC INDUSTRIAL THERMOMETER

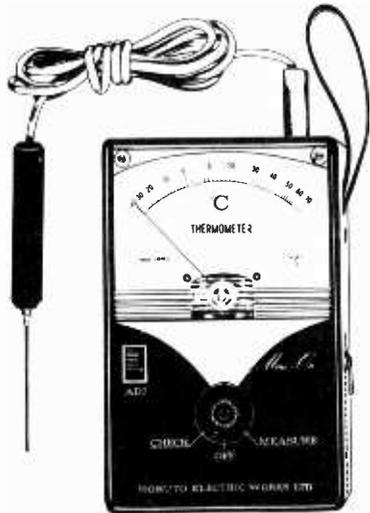

### THE MODERN WAY TO MEASURE TEMPERATURE

A Thermometer designed to operate as an Electronic Test Meter. Will measure temperature of Air, Metals, Liquids, Machinery, etc., etc. Just plug-in the Probe, and read the temperature on the large open scale meter. Supplied in zippered vinyl case with transparent front and carrying loop, Probe, and internal 1½ volt standard size battery. Model "Mini-On 1" measures from - 40°C to + 70°C, price £17.50 Model "Mini-On Hi" measures from + 100°C to + 500°C, price £20.00 (V.A.T. EXTRA)

Write for further details to

**HARRIS ELECTRONICS (LONDON),**  
138 GRAY'S INN ROAD, LONDON. WC1X 8AX  
(\*Phone 01-837 7937)

WW-054 FOR FURTHER DETAILS

## FREQUENCY COUNTERS

HIGH PERFORMANCE REASONABLY PRICED ELECTRONIC INSTRUMENTS



CRYSTAL OVEN

TWO TONE BLUE CASE

£370 **520** MHz

Sensitivity 10mV. Stability 5 parts 10<sup>10</sup>

301M 32MHz 5 Digit £75  
501 32MHz 8 Digit £175  
801A/M 300MHz 8 Digit £295  
801B/M 250MHz 8 Digit £260

Start/Stop versions plus £12

Type 101 1MHz 100KHz 10KHz Crystal Standard £80  
Type 103 On/Air Standard £78

SUPPLIERS TO: Ministry of Defence, G.P.O., B.B.C., Government Depts.,  
Crystal Manufacturers and Electronic Laboratories world-wide

401 32MHz 6 Digit £118  
701A 80MHz 8 Digit £195  
901M 520MHz 8 Digit £370  
Memory versions available if not  
suffixed M £25 extra



**R.C.S. ELECTRONICS**  
NATIONAL WORKS, BATH ROAD  
HOUNSLOW, MIDDX. TW4 7EE  
Telephone: 01-572 0933/4

WW-039 FOR FURTHER DETAILS

# Anti-reflection coatings for high-power laser systems

Check your requirement from this list:

VERY LOW REFLECTIVE COATINGS

Reflectance equal to less than 0.05% at specified wavelength.

HIGH-EFFICIENCY REFLECTIVE COATINGS

Details on request.

ANTI-REFLECTION WIDE BAND COATINGS


Visible to Near Infrared.

POLARISING COATINGS AND BEAMSPLITTERS

Details on request.

NARROW BAND FILTERS

0.9 microns and above.

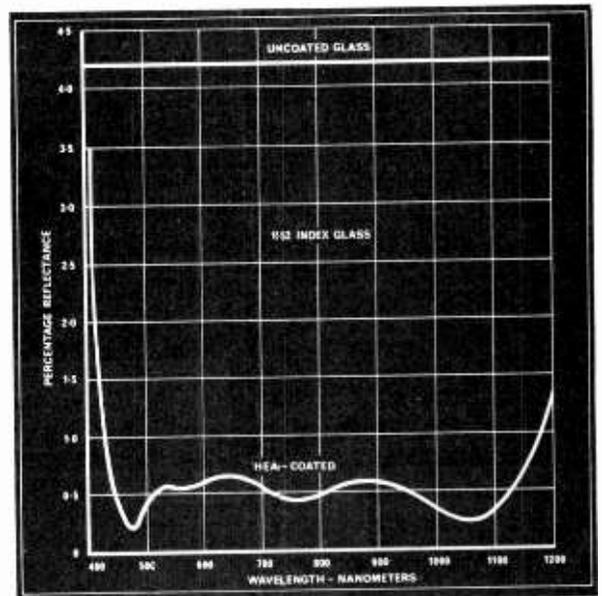

Comparison between OCLI Wide Band 'HEA'-coated and uncoated 1.52 index glass (measured performance).

For more information, send this advertisement to:

**OCLI**

OCLI Optical Coatings Ltd.,  
Hillend Industrial Estate,  
Dunfermline, Fife, Scotland KY11 5JE.  
Tel Inverkeithing 3631 (038-34 3631).  
Telex. 72307.

OC-52C

**SPANNING EUROPE**

WW-061 FOR FURTHER DETAILS




**sound equipment**  
by **Grampian**

**GRAMPIAN REPRODUCERS LTD.** HANWORTH TRADING ESTATE FELTHAM, MIDDLESEX TELEPHONE 01-894 9141

x209

WW-085 FOR FURTHER DETAILS

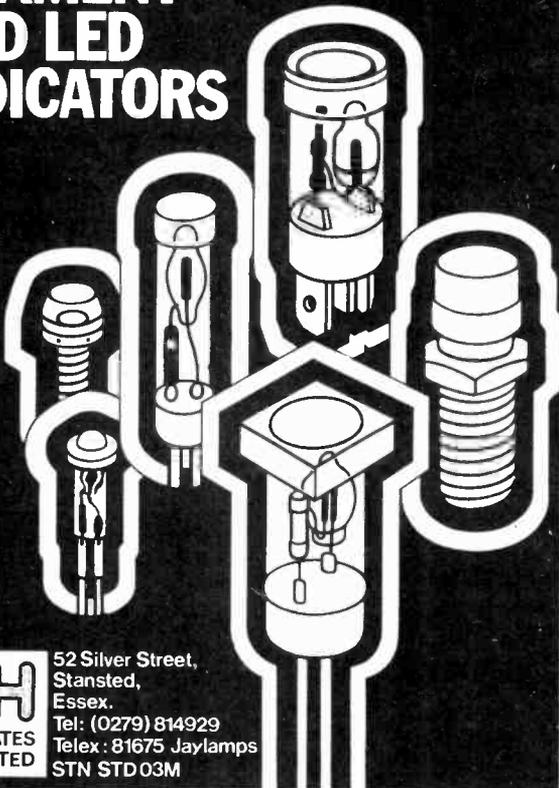**NEON  
FILAMENT  
AND LED  
INDICATORS**




**JH**  
ASSOCIATES  
LIMITED

52 Silver Street,  
Stansted,  
Essex.  
Tel: (0279) 814929  
Telex: 81675 Jaylamps  
STN STD 03M

WW-022 FOR FURTHER DETAILS

**QUARTZ  
CRYSTALS  
-FAST!**

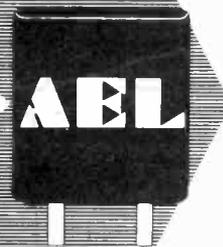

**AEL** GATWICK HOUSE, HORLEY, SURREY, ENGLAND  
Tel: Horley (02934) 5353  
Telex: 87116 (Aerocon Horley) Cables: Aerocon Telex Horley

WW-048 FOR FURTHER DETAILS

**Your choice of  
Live Sockets-  
Instantly!**

A Lexor DIS-BOARD gives you up to 6 sockets from one power outlet. Portable or permanent fixing, compact units, with safety neon. Over 1,000 socket combinations available from stock. All types of fittings and finishes.

Brochure from  
LEXOR DIS-BOARDS LIMITED  
Allesley Old Road, Coventry  
Telephone 72614 or 72207



WW-047 FOR FURTHER DETAILS

# Our noise reducer is something to shout about!



## Wireless World Dolby noise reducer

Complete kits for the *Wireless World* Dolby B noise reducer are available through the address given below. The two-channel design features:

- a weighted noise reduction of 9dB
- switching for both encoding (low-level h.f. compression) and decoding
- a switchable f.m. stereo multiplex and bias filter
- provision for decoding Dolby f.m. radio transmissions (as in USA)
- no equipment needed for alignment
- suitability for both open-reel and cassette tape machines
- check tape switch for encoded monitoring in three-head machines

The kit includes:

- complete set of components for a stereo processor
- regulated power supply components
- board-mounted \*DIN sockets and push-button switches
- fibreglass board designed for minimum wiring
- solid mahogany cabinet, chassis, two meters, front panel, knobs, mounting screws and nuts.

Price is £43 inclusive.

A single-channel printed-circuit board, with f.e.t. costs £2.50 or £8.63 with all components inclusive (excluding edge connector, £1.37 extra). Selected field-effect transistors cost 68p each inclusive, £1.20 for two and £2.20 for four.

Calibration tapes are available, costing £1.94 inclusive for 9.5cm/s open-reel use and for cassette (specify which).

**Send cash with order, making cheques payable to IPC Business Press Ltd. to:  
Wireless World noise reducer  
General sales department  
Room 11, Dorset House  
Stamford Street  
London SE1 9LU**

### DOLBY KIT ORDER FORM

Please supply me with the complete Wireless World kit for a Dolby noise reducer.

I enclose remittance value £43.00 inclusive

Name .....

Address .....

Additional items required .....

I enclose remittance value £ ..... payable to I.P.C. Business Press Ltd.

# FANTASTIC OFFER—DIGITAL CLOCK KIT SAVE £££s

- Fast building
- Easy to follow instructions
- No knowledge of electronics required
- The most comprehensive kit and instructions you have ever seen



KIT COMPRISES or separately at:—	£
1 MOS Clock Chip 12-24 hr option MM5314N	2.95
4 0.63" LED Displays NSN61L	6.60
1 Segment Driver Chip	0.50
1 Pack Resistors, Caps., Transistors, switch	1.60
1 Double Sided Glass Fibre P.C. Board	0.95
1 Double Wound Mains Transformer	1.50
1 Circuit/Assembly Manual	0.50
1 Futuristically styled Case (state colour), Red, Black, White, Mauve, Green, Blue.	4.40
*NB All Prices INCLUDE VAT & p&p	

NOW ONLY **£12.50**

+ £1.50 VAT & p&p

## COMET CLOCK DATA

Size 6¼ x 3 x 2½  
Mains Operation  
50/60HZ  
12/24 hour mode

OR READY BUILT & FULLY TESTED  
ELECTRONIC ASSEMBLY Excl. Case

**£11.88 INC.**

C.W.O. to:

ALL WOOD CASE 70p EXTRA


## Pulse Electronics Ltd



Dept. WW3, 202 Shefford Road, Clifton, Beds.  
Tel. Hitchin 0462 814477



# nombrex

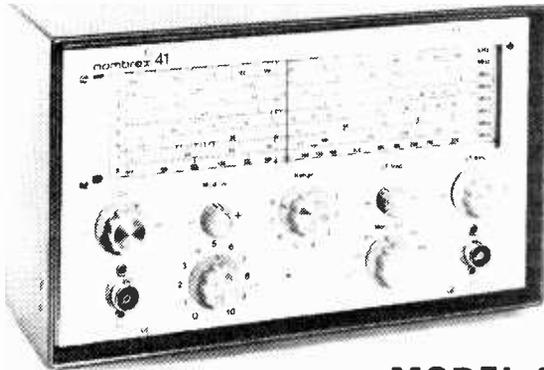

## MODEL 41 R.F. SIGNAL GENERATOR Price £54.85

PLUS V.A.T.


- ★ 150 KHz — 220 MHz on fundamentals.
- ★ 8 clear scales — Total length 130mm.
- ★ Spin-Wheel Slow Motion Drive 11 — 1 ratio.
- ★ Overall Accuracy — 2½%.
- ★ Modulation, Variable depth and frequency.
- ★ Internal Crystal Oscillator providing calibration checks throughout all ranges.
- ★ Mechanical scale adjustment for accurate alignment against internal 1MHz crystal oscillator.
- ★ Powered by 9V Battery.

Trade and Export enquiries welcome  
Send for full technical leaflets  
Post and Packing £1 00 extra

**NOMBREX LTD., POUND PLACE, WOLBOROUGH STREET,  
NEWTON ABBOT, DEVON, TQ12 1NE  
Tel. Newton Abbot 68297**

WW—012 FOR FURTHER DETAILS

## JES AUDIO INSTRUMENTATION

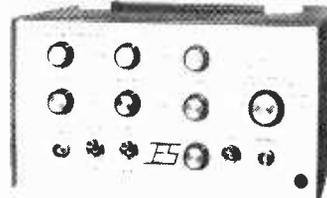

Illustrated the Si452  
Distortion Measuring  
Unit—low cost distortion  
measurement down to  
.01% **£40.00**

Si451	<b>£50.00</b>	Si453	<b>£50.00</b>
Comprehensive Millivoltmeter	20 ranges	Low distortion Oscillator	sine — square — RIAA
350µ Volts			

prices plus VAT

**J. E. SUGDEN & CO. LTD. Tel. Cleckheaton (0274) 872501  
CARR STREET, CLECKHEATON, W. YORKSHIRE B19 5LA**

WW—013 FOR FURTHER DETAILS



## OSCILLOSCOPES

- BATTERY PORTABLE
- 10 MHz BANDWIDTH
- 0.1µS-0.1 Sec. TIME-BASE
- SINGLE AND DOUBLE BEAM
- PRICES FROM £95

**meteronic Ltd.**


114/116 Shipbourne Road  
Tonbridge, Kent  
Tel. Tonbridge 61448

WW—045 FOR FURTHER DETAILS

## SPECIALISTS IN COIL AND TRANSFORMER WINDING:

Torroidal: c core: high  
speed high turn bobbin  
winding: chokes and wave  
winding  
any quantity, any rating.

Send for new catalogue.

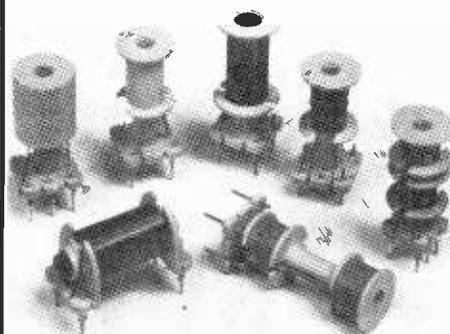


WW—020 FOR FURTHER DETAILS



Electronics Limited

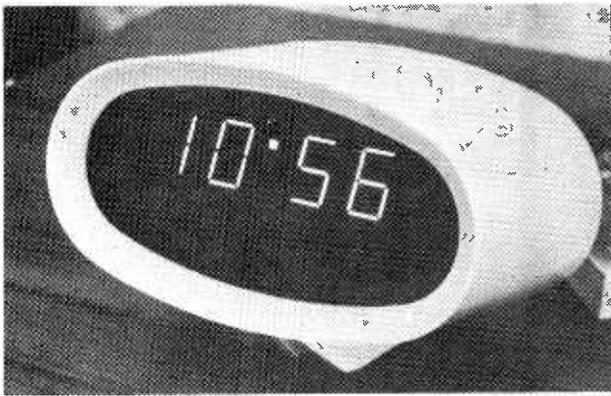**27 STATION ROAD  
BRIMINGTON  
CHESTERFIELD  
DERBYSHIRE, ENGLAND  
TEL: 0246 70297/8/9  
TELEX 54284**



**ENHANCE YOUR HOME WITH A SOPHISTICATED DIGITAL ALARM CLOCK**

An all solid state digital alarm clock in an attractive brilliant white plastic case. Pleasing 4-digit orange displays with brightness control together with a flashing colon for seconds and a p.m. indicator. Gentle alarm with snooze facility — Tip it forward and it stops. With a reminder every five minutes.


**SPECIAL OFFER PRICE £12.99**

(Plus VAT £1.04, Post & Packing 50p)

Remittance with order, please, to:  
**TYME & GEAR**  
 Eastern Towers, 30 Eastway, Morden, Surrey  
 Telephone: 01-540 1898


WW — 083 FOR FURTHER DETAILS

**LOW-COST INSTRUMENTS**

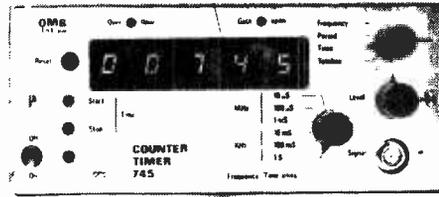


**VALUE!**  
**£82**  
 + £1.50 p.p.  
 + VAT

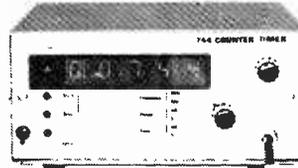**745 COUNTER TIMER**  
 Measures frequency, period, time and totalises  
 32 MHz frequency range (DC coupled)  
 5-digit .3" LED display  
 6 Gate times/Time units, 10µs to 1 S in decades  
 Sensitive, protected FET input



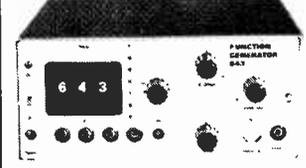**744 COUNTER TIMER**  
**£74 + £1.50 p.&p. + VAT**  
 Measures frequency, period and time  
 30MHz frequency range (DC coupled)  
 5-digit, long-life incandescent display  
 Sensitive, protected FET input




**643 FUNCTION GENERATOR**  
**£86 + £1.50 p.&p. + VAT**  
 Accurate, digital frequency setting  
 .01Hz-1MHz  
 Wide range external control of frequency  
 Triangle, Squarewave and Low Distortion  
 Sinewave outputs  
 50Ω + simultaneous outputs  
 DC offset

*Delivery is normally ex-stock—telephone for confirmation  
 Prices correct at time of going to press, subject to change without notice*

**OMB ELECTRONICS**  
 Riverside, Eynsford, Kent DA4 0AE  
 Tel. Farningham (0322) 863567

WW—034 FOR FURTHER DETAILS

**Alice Broadcasting STM6**

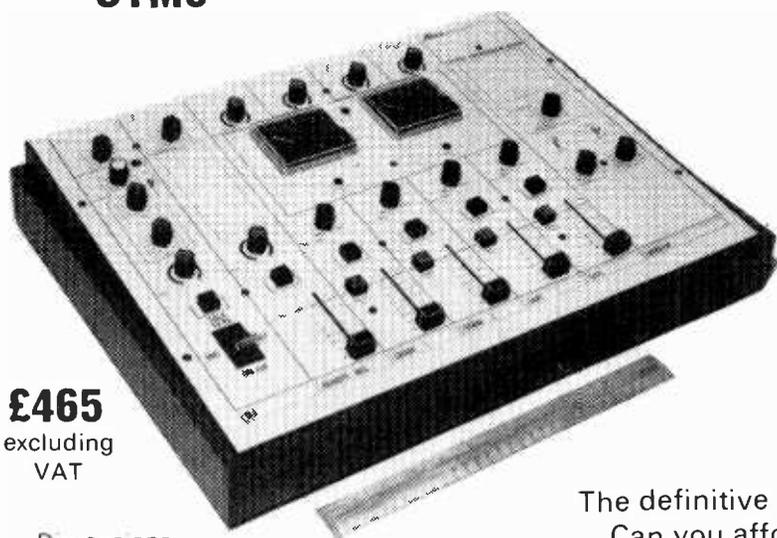

**£465**  
 excluding  
 VAT

Dimensions  
 20" x 15" x 4½"

**Six Channel Stereo Transmission Mixer (ALICE'S BABY)**

- |                  |                |
|------------------|----------------|
| <b>INPUTS</b>    | <b>OUTPUTS</b> |
| Microphones      | Lines          |
| Lines/Tape/Carts | P.A.           |
| Pick-ups         | Headphones     |
| Off Air          | Recording      |

The definitive DJ / OB / Production Mixer  
 Can you afford to use anything use?

Contact Chris Walden on Windsor 51056 / 7

**ALICE (STANCOIL LTD.), 38 ALEXANDRA ROAD, WINDSOR, BERKS, ENGLAND**

Also available from Roger Squires, London and Manchester

WW—016 FOR FURTHER DETAILS

# Low-cost phasemeter



**Only £160**

The A200 is an analogue phasemeter which directly displays the phase difference between two inputs - both input channels are carefully matched internally so that phase shift within the instrument is negligible. Lead/lag indicators automatically register polarity.



**Prosser Scientific Instruments Ltd**  
Lady Lane Estate Hadleigh Suffolk  
Tel Hadleigh (0473-38) 3005


WW-023 FOR FURTHER DETAILS



**Hard-to-find tubes and semiconductors are normally included in our quotations. We try to give a complete answer.**

**AEL GATWICK HOUSE HORLEY SURREY RH6 9SU**  
Telex 87116 Cables Aerocon Telex Horley Telephone Horley 5353

WW-049 FOR FURTHER DETAILS

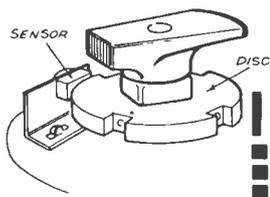

**Capacitor Discharge IGNITION**  
 ■ MAXIMUM PERFORMANCE  
 ■ MAXIMUM ECONOMY  
 ■ EASY COLD START

**SYSTEM I**

Professional photoelectric ignition using L.E.D. light source and reflective disc. This machined aluminium disc gives a timing accuracy far superior to other methods and is simple to fit. Unit housed in diecast box 4 1/2" x 3 1/4" x 2 1/4" Price £18.80 (Kit £16.80) State car/model/measurement across cam lobes.

**SYSTEM II**

Contact breaker model as above less sensor. Price £12.80 (Kit £10.80) M/C Twin unit Price £15.00. S.A.E. for descriptive leaflet - ALL UNITS IN STOCK. Mail orders to CDI Electronic Systems Ltd, 275 Vale Road, Ash Vale, Aldershot, Hants. Demonstration/Callers to Hillside Motors, 292 Carshalton Road, Carshalton, Surrey, telephone 01-642 9973.

WW-082 FOR FURTHER DETAILS

## A NEW DIMENSION IN SOLDERING



### Iso-Tip Cordless Soldering Iron

Ideal for factory, field servicing, laboratory or home, the Iso-Tip Cordless offers a great advance in soldering. It is completely portable, heats in 5 seconds and recharges automatically in its own stand.

The Iso-Tip is powered by long-life nickel cadmium batteries giving tip performance up to 50 watts with a temperature of 370°C. Tips are available in five different sizes ranging from Micro to Heavy Duty to meet all soldering requirements.


**Greenwood Electronics**  
Portman Rd, Reading RG3 1NE, England  
Telephone: Reading (0734) 595844.  
Telex: 848659

WW-037 FOR FURTHER DETAILS
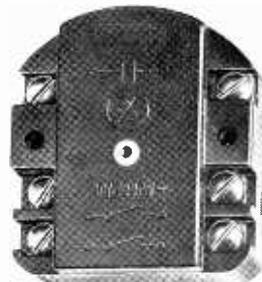
## Switching problems? Rely on Zettler.

Producing 30 basic types of relay and 15,000 variants with regard to contact stacks, terminals, energizing current and contact material, Zettler is among the largest manufacturers of electro-mechanical components.

Our product range comprises:  
 Low profile (platform) Timing · Miniature · Low contact capacity · Hermetically sealed · Stepping Mains switching · Latching Contact stacks · Solenoids



### Impulse Latching Relay AZ 340


**Make contacts:**  
 Resistive load: 10 A/240 V AC.  
 Lamp load: 8 A/240 V AC.  
 Compensated fluorescent tubes: 3.7 A/240 V AC.  
**Break contacts:**  
 Resistive load: 8 A/240 V AC.  
 Lamp load: 5 A/240 V AC.  
 Compensated fluorescent tubes: 3.7 A/240 V AC.

We resolve your switching problems rapidly and expertly. Please contact us for further details.



**ZETTLER** Zettler UK Division  
 Brember Road  
 Harrow, Middx. HA2 8AS. Tel. (01) 422 0061  
 A member of the worldwide ZETTLER electrical engineering group, est 1877


WW-007 FOR FURTHER DETAILS

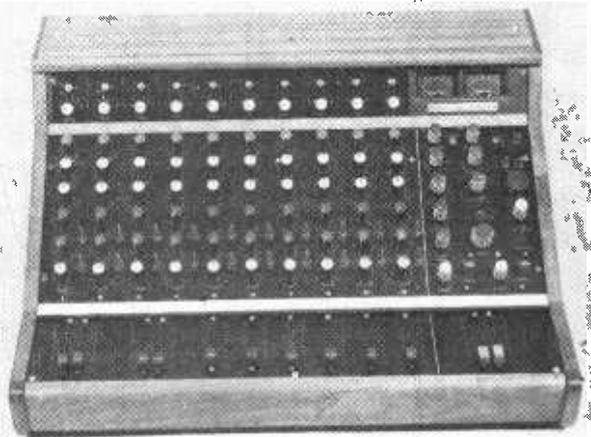

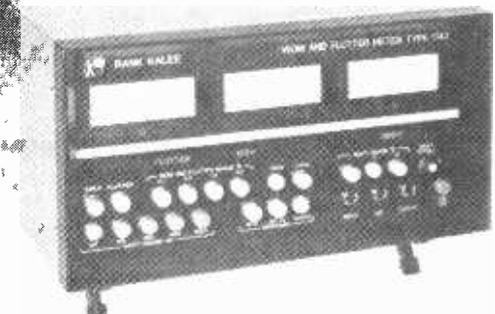**IS CHILTON'S MIXER THE BEST FOR YOUR USE?**

Magnetic tapes Ltd make the 10/2 above as well as a 16/2 and a 12/4 with all the inherent flexibility and quality customarily found in big studio mixers. Most of our mixers are constructed to meet the varying demands of the customer, perhaps we can do one for you. Prices start at £365 for the basic 10/2 + VAT @ 8%.

**MAGNETIC TAPES LTD.**  
 Chilton Works, Garden Road, Richmond  
 Surrey TW9 4NS - 01-876 7957



**\* The new Rank**

**WOW & FLUTTER Meter**  
**Type 1742**

Fully transistorised for high reliability

Versatile  
 Meets in every respect all current specifications for measurement of Wow, Flutter and Drift on Optical and Magnetic sound recording/reproduction equipment using film, tape or disc

High accuracy  
 with crystal controlled oscillator

Simple to use  
 accepts wide range of input signals with no manual tuning or adjustment

Two models available:  
 Type 1742 'A' BS.4847: 1972 DIN 45507 CC1R 409-2 Specifications  
 Type 1742 'B' BS 1988: 1953 Rank Kalee Specifications

For further information please address your enquiry to  
 Mrs B. Nodwell  
 Rank Film Equipment, PO Box 70  
 Great West Road, Brentford  
 Middlesex TW8 9HR  
 Tel: 01-568 9222 Telex 24408 Cables Rankaudio Brentford

**RANK FILM EQUIPMENT**

# NEW!...the decon-dalo 33 PC Quick -Dri etch -resist marker



A unique drafting aid for the electronics engineer enabling him to prepare in minutes a perfect PCB. A fine-tipped marking pen charged with free-flowing etch-resist ink — new formulation QUICK-DRI ink is ready for etching in just two minutes! Simply draw the desired circuit onto copper laminated board — etch — clean. The circuit is ready to use

**NO MESS — NO MASKING**  
**A perfect circuit every time!**  
 Still only £1.08 for one-off, £4.42 for six, £8.80 for twelve, post and VAT paid! Available now in every country in Europe. **AND FROM YOUR LOCAL COMPONENT SUPPLY SHOP!**  
 Decon Laboratories Ltd., Ellen Street, Portslade, Brighton BN4 1EQ Phone: 0273 414371

Please send me further details on the 33 PC Quick-Dri

Name .....


Address .....

Post to: **DECON LABORATORIES LTD.**  
**FREEPOST**  
**PORTSLADE, BRIGHTON, ENGLAND**  
 (No Stamp Needed) Phone 0273 414371

WW-067 FOR FURTHER DETAILS

# TEAC

TEAC A3340(S)  
4-CHANNEL  
RECORDER

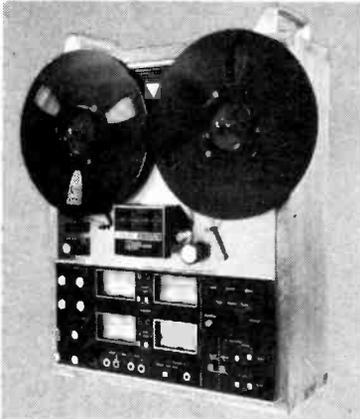

Industrial version upgraded to studio requirements, with increased signal to noise performance and improved reliability. Four totally independent channels each with sel sync, input mixing, switchable VU's and all the facilities for easy multitracking. This industrial model is in more studios than any other version.

Available only from ITA  
(Semi-pro version also available)  
IMMEDIATE DELIVERY

# REVOX

REVOX A-700 SERIES



The new big Revox — ideal for all studio requirements. Highly sophisticated design features include servo tape tension, full deck logic, crystal controlled servo electronics, 3 speeds, tape footage counter.

£595 IMMEDIATE DELIVERY


The famous A77 has been consistently improved over the past 8 years and is now available in the latest Mk 4 version. The wide choice of specifications includes versions for duplicating and logging applications. Backed by UK's latest fastest service.



Hire service Check our prices from IMMEDIATE DELIVERY £275

# ITA

ITA 10-4  
MODULAR MIXER

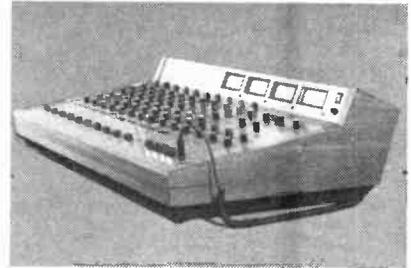

Ten balanced inputs, four output groups, 4 limiters, bass mid and treble EQ, modular construction, headphone monitoring. Extremely high quality construction only matched by mixers costing around £1,000.

10-4 £647

20-4 £990

EIGHT OUTPUT £1260

IMMEDIATE DELIVERY  
Also available for hire

PRICES EXCLUSIVE OF V.A.T.

## Industrial Tape Applications




5 Pratt Street, London NW1 OAE  
Telephone: 01-485 6162. Telex: 21879

WW-088 FOR FURTHER DETAILS

## brenell

### PROFESSIONAL TAPE TRANSPORTS and multi-channel electronics for studio and industrial use

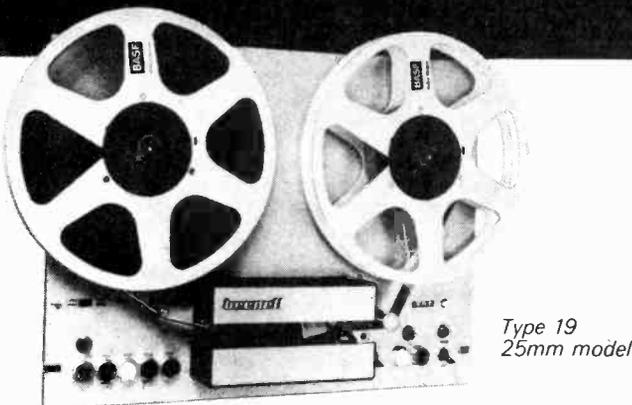

Type 19  
25mm model

Finance available

- \* Tapewidths up to 25mm
- \* Speeds: 3mm/s minimum up to 152cm/s max 2 and 4 speed models
- \* Reel Capacity up to 29cm
- \* Remote Control Facility
- \* Tape Tension Control
- \* Automatic Interlock against misuse
- \* Special models to customer requirements

### BRENELL ENGINEERING CO LTD

231-5 Liverpool Road, London N1 1LY. Tel: 01-607-8271

## servos synchronous steppers dc motors



## gearboxes and control systems



Stockists for IMPEX Motors

McLennan

McLENNAN ENGINEERING LIMITED

Kings Road Crowthorne Berks Telephone: Crowthorne 5757/8

WW-027 FOR FURTHER DETAILS

# BUILD YOURSELF A 25W AMP FOR ONLY

**£29-95**  
+ 4-05 VAT

## COMPLETE KIT SUPPLIED

DORAM, one of Britain's leading mail-order distributors of audio accessories & components brings you the 'INTERNATIONAL 25' - a 25W per channel Stereo Amp. - that you can build yourself!

This 'real-value-for-money' kit is supplied with clear assembly instructions and reliable components to give you a big sound to be proud of.

Overseas orders  
£34-50

- \* Triple Op-amp pre-amplifier
- \* Power 'Darlington's' in output stage
- \* 25W per channel into 8 ohms
- \* Modern, elegant styling

GENUINE  
BIG-SOUND VALUE!


MANY MORE INTERESTING  
AUDIO KITS AND COMPONENTS  
LISTED IN DORAM'S CATALOGUE  
PRICED AT ONLY 60p



# DORAM

DORAM ELECTRONICS LTD  
P.O. Box 118, Leeds, LS12 2UF  
Tel. Leeds. (0532) 34222
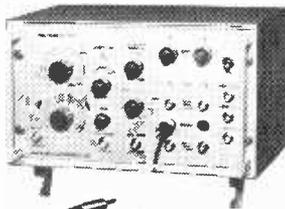
## THE DINOSAUR ELECTRONICS LTD. MULTISWEEP ED3 SWEEP-GENERATOR



- WIDE RANGE**  
20 KHz to 70 MHz in 10 switched ranges
  - DIRECT GENERATION**  
For low spurious and high stability
  - DUAL TRACE**  
With most simple oscilloscopes
  - COMPREHENSIVE MARKERS**  
Crystal marker combs as standard fitting
  - MAXIMUM UTILITY**  
Just connect oscilloscope and attenuators
- £490.00 + VAT

MARKETED by

**aspen electronics limited**

18A HIGH STREET, NORTHWOOD, MIDDLESEX HA6 1BN  
Tel.: Northwood 27688/9

WW-078 FOR FURTHER DETAILS



# professionally canned from ear to ear

The DT 100 is only one of an extensive range of headphones manufactured by Beyer Dynamic, in use in studios throughout the world . . . . setting a new sound standard.

- \* Frequency Response: 30-20,000 Hz
- \* Output Level at 100 HZ and 1 mW: 110 db over 2. 10<sup>-4</sup> μ bar
- \* Rated Input: appr. 600m V per cartridge
- \* Peak Power Load 1W or 20V per cartridge
- \* Impedance: 2 x 400 Ω (2 x 8, 2 x 100, 2 x 800, 2 x 2,000 Ω upon request)

## BEYER DYNAMIC

BEYER DYNAMIC (GB) LIMITED  
1 Clair Road, Haywards Heath, Sussex. Tel: Haywards Heath 51003

WW-096 FOR FURTHER DETAILS

# BI-PAK

# BARGAIN BUNDLES

Send to: **BI-PAK SEMICONDUCTORS**  
DEPT. W.W.2, P.O. BOX 6, WARE, HERTS.

Bi-Pak bring you, for 2 months only a fantastic **inflation beating offer** designed to help you, the customer. With every **Pak** comes a useful **FREE GIFT**. In addition to this, our star attraction is the **D.I.Y. Printed Circuit Kit**. With every kit sold during this offer comes a voucher to the value of £1.50 to be spent on any items from our Retail Catalogue.



**PRINTED CIRCUIT KIT:** Containing 6 sheets of 6" x 4" single sided laminate, a generous supply of etchant powder, etching dish, etchant measure, tweezers, etch resistant marking pen, high quality pump drill with spares, cutting knife with spare blades, 6" metal ruler, plus full easy-to-follow instructions. £7.80.



### 3 for the PRICE of 2

Buy 2 x C60 cassettes for 72p per pair  
— GET 1 x C60 ABSOLUTELY FREE  
Buy 2 x C90 cassettes for 96p per pair  
— GET 1 x C90 ABSOLUTELY FREE

**I.C. BUNDLE**  
2 x 7400                    2 x 7474  
2 x 74121                2 x 74141  
2 x 741

**PLUS FREE** 2 x BPS8 and  
2 x BPS16 I.C. Sockets

**ALL FOR ONLY**  
**£1.50**  
**OFFER WORTH £3.27**

**TRANSISTOR BUNDLE**  
2 x BC108C                2 x BC178  
2 x OC71                    2 x BC107  
2 x BF115                   2 x BC109  
2 x 2N3819                2 x BFX84  
2 x 2N3646                2 x BFX29

**PLUS FREE**  
**ONE SHEET OF VEROBOARD**

**ALL FOR ONLY**  
**£1.50**  
**OFFER WORTH £3.00**

**S.C.R. BUNDLE**  
2 x 0.6 100v              2 x 3A 50v  
2 x 1A 50v                2 x 5A 400v  
2 x 1A 400v

**PLUS FREE**  
**2 METERS OF 18SWG MULTICORE SOLDER**

**ALL FOR ONLY**  
**£1.50**  
**OFFER WORTH £3.00**

**DIODE + RECTIFIER BUNDLE**  
20 GERM G.P. DIODES DIRECT REPLACEMENTS FOR (OA81-85 OA91-95)

2 x BY100	4 x 1.5A	50v
4 x IN4001	4 x 1.5A	400v
4 x IN4004	4 x 1N	4148

**PLUS FREE BOOK**  
No. BP9 "38 PRACTICAL TESTED DIODE CIRCUITS FOR THE HOME CONSTRUCTOR"

**ALL FOR ONLY £1.50 OFFER WORTH £3.00**

**CAPACITOR + RESISTOR BUNDLE**  
100 1/4w Resistors in assorted values ranging from 100 ohm to 1M ohm  
50 C 280 Capacitors in assorted values ranging from .01uF to 2.2uF

**PLUS FREE**  
**COLOUR CODE CHARTS**

**ALL FOR ONLY £1.50**  
**OFFER WORTH £3.00**

**WATCH THIS SPACE FOR THE GREAT BI-PAK CHRISTMAS COMPETITION WITH A FIRST PRIZE OF A COLOUR TV PLUS 52 OTHER PRIZES**

## You edit the tape. We edit the prices. VIDEO TAPE AT DIXONS TECHNICAL

	RECOMMENDED PRICE	DIXON PRICE
SCOTCH 1/2 361 - 2400 ft	£11.99	£8.50
SCOTCH 1/2 8174 - 3550 ft	£19.43	£14.50
SCOTCH 1/2 461 - 2400 ft	£14.41	£11.00
BASF 1/2 - 2400 ft	£10.50	£8.50
SHIBADEN 1/2 - 2400 ft	£10.50	£8.50
U-MATIC KC60 Cassettes	£14.50	£12.00
PHILIPS VC60 Cassettes	£17.00	£14.50
DIXTEC 1/2 2400 ft 7" spool	£5.50	£5.50
DIXTEC 1/2 2000 ft 7" spool	£3.00	£3.00
DIXTEC 1/2 1200 ft 7" spool	£2.00	£2.00

We will gladly supply you with a quotation for any tapes not listed above.

**PLUS VAT**

Please send me \_\_\_\_\_ reels of \_\_\_\_\_ Tape.

Size \_\_\_\_\_ Length \_\_\_\_\_ Dixons Price \_\_\_\_\_

**TOTAL PRICE**  
(Please remember to calculate VAT at 8% before sending off your cheque)

And please send me a quotation for \_\_\_\_\_  
(any tape not listed)  
I enclose a cheque made payable to Dixons Technical Limited  
3 Soho Square London W1

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_

**Dixons**  
Technical Ltd  
OF SOHO SQUARE

WW/66A/12

## SOUND INSTALLATIONS

Design, installation and commissioning of recording and broadcast studios, sound reinforcement equipment, theatre communication and other systems.

## SOUND EQUIPMENT

Supply and, where required, manufacture of equipment to customers' specifications.

We also specialise in television, lighting and other systems.

## PHILIP DRAKE ELECTRONICS LTD.

165 LANCASTER ROAD, NEW BARNET, HERTS.  
Telephone: 01-445 1144

WW-063 FOR FURTHER DETAILS



**FREE Brochure**  
on New **KITS**

Whether professional, student, teacher or amateur, the field of electronics can open up a new world for you.



CROFTON don't just sell kits, we offer you a technical back up service to ensure your success

The following is a selection of some of the more popular kits -


- ★ Mullard CCTV Camera
- ★ PE CCTV Camera
- ★ PE Rondo Quadraphonic Four Channel Sound (Designer Approved!)
- ★ Electronic Ignition
- ★ Sound Operated Flash
- ★ P.W. Tele-Tennis Game
- ★ UHF Modulator
- ★ Bench Power Supply
- ★ Wobblator
- ★ All E.T.I. Top Projects
- ★ Many of the Elektor Projects

NOTE: PCBs for most published projects available to order

**CROFTON ELECTRONICS LTD**  
Dept. D, 124-Golne Road, Twickenham, Middx. 01-898 1569

WW-046 FOR FURTHER DETAILS

## TAKE A CLOSE LOOK

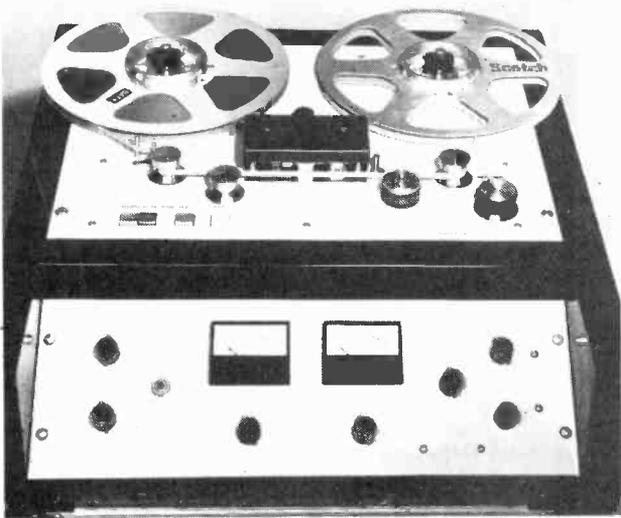


at a professional recorder that offers high performance, excellent reliability and is very easy to maintain. Ask yourself why so many commercial radio stations and recording studios are doing their best to wear them out, and not having much success. Decide if you need mono or stereo, console transportable or rack mounting versions and then inquire about prices. We are sure you will be very pleasantly surprised.

**BIAS ELECTRONICS LTD.** 01-540 8808  
**572 KINGSTON ROAD, LONDON SW20 8DR**

WW-021 FOR FURTHER DETAILS.

## —TURNER—

### STEREO POWER AMPLIFIERS

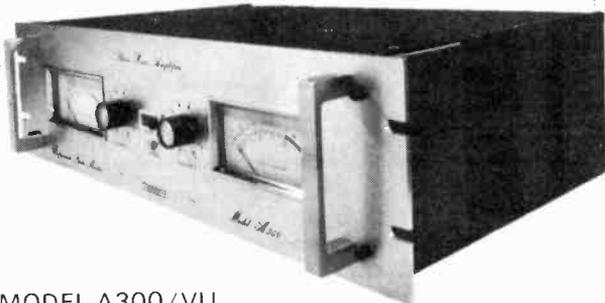

MODEL A300/VU

A range of professional stereo power amplifiers designed and manufactured to a very high standard.

The A Series (Professional Studio Monitor) amplifiers feature dual power supplies to maintain full RMS power on both channels.

The B Series (Professional) amplifiers feature single power supplies suitable for most music applications.

		STANDARD	WITH VU's
MODEL A500	250+250 watts RMS 4 ohms	£380.00	£440.00
MODEL A300	150+150 watts RMS 4 ohms	£262.50	£322.00
MODEL B300	150 watts RMS per channel	£210.00	£250.00
MODEL B200	100 watts RMS per channel	£170.00	£210.00


The above prices are list and exclusive of VAT.

Overseas Import Agents are invited to make their final applications for allocation of areas for 1976 exports.

**TURNER ELECTRONIC INDUSTRIES LTD.**  
**175 Uxbridge Road, London W7 3TH**  
 Tel. 01-567 8472


WW-025 FOR FURTHER DETAILS

## NT 3302 · fet fm tunerhead + AM gang

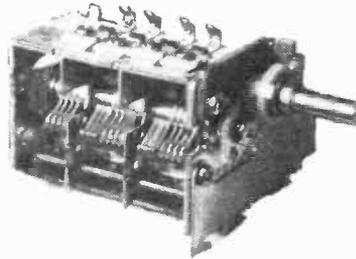

- \* FET input stage
- \* 3 stage tuning
- \* 3:1 gearing
- \* 335pF AM gangs
- \* AFC facility

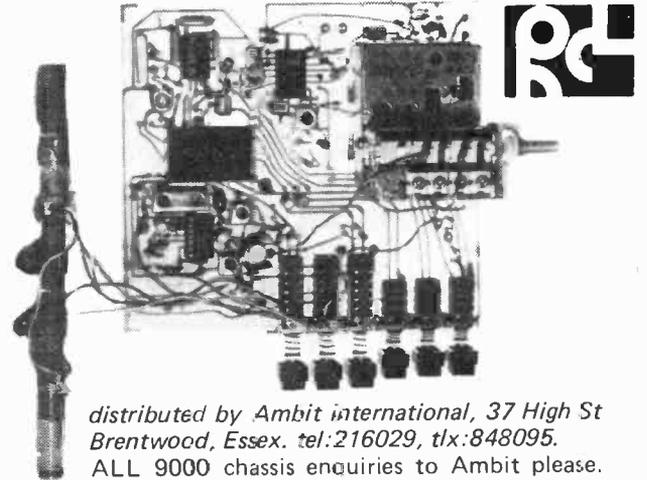TOKO's latest FM tunerhead is available for immediate evaluation with the Broadcasting 9000 tuner chassis- an AM (LW/MW) and mpX FM chassis, with switches inc.




*distributed by Ambit international, 37 High St Brentwood, Essex. tel:216029, tlx:848095.*

ALL 9000 chassis enquiries to Ambit please.

OEM enquiries to TOKO UK, Ward Royal Parade, Alma Road, Windsor, Berkshire. tel:54057, tlx:848095.

## INSIST ON VERSATOWER

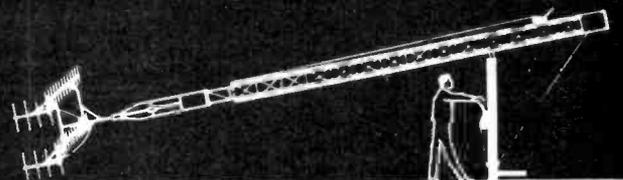

Acclaimed as the World's leading telescopic tiltover tower in the field of radio communication  
 Models from 25' to 120'




Look for the name  
**STRUMECH**

Strumech Engineering Co Ltd  
 Coppice Side Brownhills, Walsall, Staffs

WW-032 FOR FURTHER DETAILS

# Spot the Difference

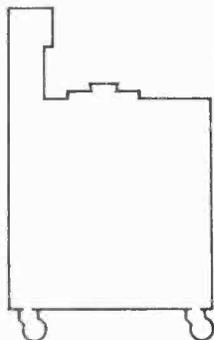

**TYPICAL STEREO MASTER RECORDER at around £3,000.00**

**Wow & Flutter** less than .05%

**Start Time** less than .5 sec

**Frequency Response** 40 - 18KHz ± 2.0dB


**Erasure** 75dB

**Full Servo Tension**

**Noise** 60dB below 320 nWb/m

**Servo Controlled Capstans**

**Electronic Tape Timer**

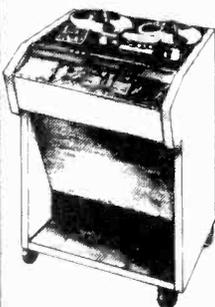

**TEKNIK SM2 STEREO MASTER RECORDER at \*£1,750.00 complete**

**Wow & Flutter** less than .05% (Typically .02% at 15 ips)

**Start Time** less than .3 sec

**Frequency Response** 40 - 20KHz ± 2.0dB

**Erasure** 75dB

**Full Servo Tension**

**Noise** 60dB below 320 nWb/m at all speeds

**Servo Controlled Capstans**

with panel operated or remoteable varispeed

**Electronic Tape Timer**

Switchable NAB/DIN equalization

V.U. metering plus L.E.D. peak level indicators

\* U.K. Trade Price



**Klark-Teknik Ltd**  
Summerfield Kidderminster  
Worcestershire DY11 7RE  
Tel Kidderminster 64027

WW-062 FOR FURTHER DETAILS



## naim audio the power amplifier

### BE FAIR TO YOUR MUSIC

Reproduction of sound and its acceptability is dependent on a combination of physical parameters not yet fully explored. We believe that only a compatible combination of specifications will enable a system to

reproduce music. We have taken care that the NAC 12 and NAP 160 pre and power amplifier will do so faithfully, while accepting the output of any pickup cartridge and driving any loudspeaker.



Naim Audio Ltd. 11 Salt Lane, Salisbury, Wilts. Tel: (0722) 3746

WW-038 FOR FURTHER DETAILS

## EXCLUSIVE OFFER

### EXCERPT from our SPECIAL OFFER 1975

KITS with circuit diagram and parts list enclosed	Net Prices £
<b>KIT No. 3A</b> for transformerless A.F. Full-Amplifier 10W complete with printed circ. panel, drilled, dim. 80 x 160 mm	4.70
<b>KIT No. 12A</b> for stabiliz. Mains supply unit 30V max. 700mA complete with printed circ. panel, drilled, dim. 110 x 115 mm	4.50
Price for transformer	2.80
<b>KIT No. 3B</b> for 2 transformerless A.F. Full-Amplifiers 10W for stereo operation, complete with 2 print circ. panels, drilled, dim. 80 x 160 mm	9.70
<b>KIT No. 13A</b> for stabiliz. Mains supply unit 30V max. 1.5A for <b>KIT No. 3B</b> complete with printed circ. panel, drilled, dim. 110 x 115 mm	4.50
Price for transformer	3.60
<b>KIT No. 5A</b> for transformerless A.F. Amplifier 5W with treble adjusting complete with printed circ. panel, drilled, dim. 80 x 120 mm	2.50
<b>KIT No. 11A</b> for stabiliz. Mains supply unit 12V max. 700mA for <b>KIT No. 5A</b> complete with printed circ. panel, drilled, dim. 80 x 115 mm	2.20
Price for transformer	1.90
<b>KIT No. 5B</b> for 2 transformerless A.F. Amplifier 5W with treble adjusting for stereo operation complete with 2 print. circ. panels, drilled, dim. 80 x 120 mm	5.15
<b>KIT No. 4</b> for stabiliz. Mains supply unit 12V max. 1.5A for <b>KIT No. 5B</b> complete with printed circ. panel, drilled, dim. 65 x 120 mm	2.40
Price for transformer	2.00
<b>KIT No. 16</b> Line Voltage Regulator complete with printed circ. panel, drilled, dim. 65 x 115 mm	3.35
Potentiometer turning knob	0.15
Radio interference suppression set for <b>KIT No. 16</b>	1.10
<b>KIT No. 22</b> Line Voltage Regulator (Brightness Control) 220V 200W complete with printed circ. panel, drilled, dim. 50 x 50 mm	1.45
Potentiometer turning knob	0.15
Radio interference suppression set for <b>KIT No. 22</b>	0.90
<b>KIT No. 23</b> Line Voltage Regulator (Brightness Control) 220V 600W complete with printed circ. panel, drilled, dim. 60 x 70 mm	1.80
Potentiometer turning knob	0.15
Radio interference suppression set for <b>KIT No. 23</b>	1.10
<b>KIT No. 24</b> Line Voltage Regulator (Brightness Control) 220V 1,000W complete with printed circ. panel, drilled, dim. 60 x 70 mm	2.20
Potentiometer turning knob	0.15
Radio interference suppression set for <b>KIT No. 24</b>	1.10

Description and technical data: see our SPECIAL OFFER 1975. The above are but a few of the many KITS and articles available ex stock Nürnberg/F.R.G. Deliveries C.O.D.; postage will be charged at self-costs. Only brand new goods of high quality, fully guaranteed. Subject to prior sale.

Please request our complete free SPECIAL OFFER 1975!




## EUGEN QUECK

Augustenstr. 6  
D-85 Nürnberg/f.r.g.

Ingenieur-Büro  
Import-Transit-Export  
Tel. 46'35'83

WW-093 FOR FURTHER DETAILS

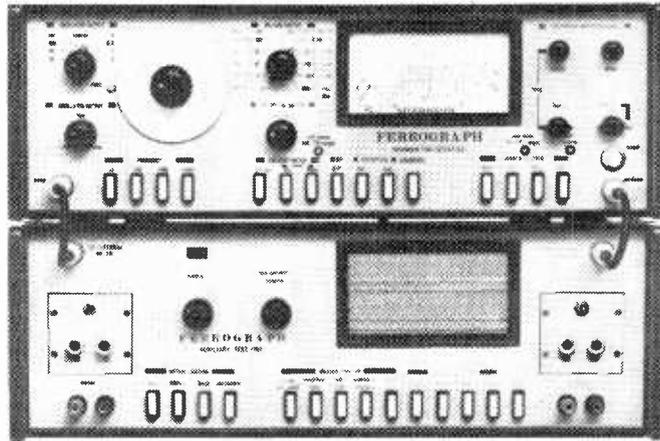

## Comprehensive Audio Measurements...

... from ONE compact unit comprising low-distortion audio oscillator, eleven-range millivoltmeter, wow and flutter meter (which also measures mean speed drift), and a distortion meter with seven full-scale ranges from 100% to 0.1%. The RTS2 Audio Test Set is used daily in fifty-nine countries throughout the World and is accepted as essential equipment by designers, manufacturers, test engineers, studio staffs and hi-fi reviewers.

Auxiliary Unit ATU1 extends the field of application by providing balanced input and output connections (in stereo pairs), a number of loading and weighting facilities, further amplification and attenuation of the oscillator signal from the RTS2, and loudspeaker monitoring of recorded announcements on test tapes.

**Audio Test Set RTS2 (Upper)**  
**Auxiliary Test Unit ATU1 (Lower)**

### FERROGRAPH

A member of the Wilmot Breeden Group

The Ferrograph Co. Ltd., 442 Bath Road, Slough, Bucks., SL1 6BB, England.

Telephone: Burnham (06286) 62511. Telex: 847297.

WW-095 FOR FURTHER DETAILS

## NEW 180MHz DFM from CATRONICS LTD.



The latest addition to the range of Digital Frequency Meters is model DFM5 — a full 7 digit instrument reading up to beyond 180MHz (typically 220MHz), i.c. memory to give 'non-blinking' display.

For quality of construction, unflinching efficiency and sheer good value this new model is unequalled. Built as it is to the high standards of all Catronics equipment and backed by their Guarantee. The sturdy metal case is custom styled and finished in Chip-proof light metallic Green. Approx 8½ x 6½ x 3in. For operation on 210-260v mains or 12v battery.

**Special Introductory Offer — only £121 + £10.75 VAT & carr.**  
Delivery generally from stock. Send SAE for Free illustrated leaflet.




Also available: The Catronics VHF Prescaler to convert HF D.F.M.s to read up to VHF. Still only £39.00 + £3.65 VAT & carr.

**CATRONICS LTD.** (Dept. 520), 39 POUND ST., CARSHALTON, SURREY, SM5 3PG Phone: 01-869 6701

WW-095 FOR FURTHER DETAILS
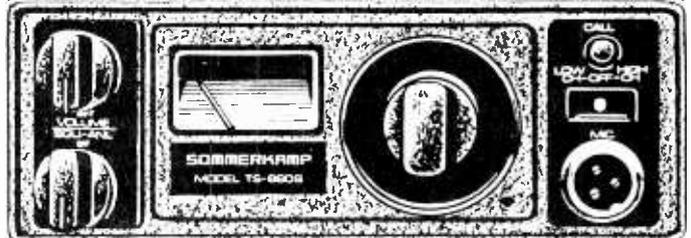
## GET THE MESSAGE with SOMMERKAMP

As Europe's most experienced Citizen Band specialists we can meet all your needs in 2-way equipment from our complete line of hand-held and mobile transceivers. Transmitting powers of 0.2 watts on 2 channels to 15 watts on 60 channels are available now. Not licensable in the U.K.



For full details contact the Sole U.K. agent

**COMMUNIQUE, 129 PARK ROAD, LONDON, N.W.8. Tel. 262 4707**

WW-075 FOR FURTHER DETAILS



## Audio Connectors

Broadcast pattern jackfields, jackcords, plugs and jacks.

Quick disconnect microphone connectors  
Amphenol (Tuchel) miniature connectors with coupling nut.



Hirschmann Banana plugs and test probes  
XLR compatible in-line attenuators and reversers

Low cost slider faders by Ruf.



**Future Film Developments Ltd.**  
**90 Wardour Street**  
**London W1V 3LE**  
**01-437 1892/3**

WW-050 FOR FURTHER DETAILS

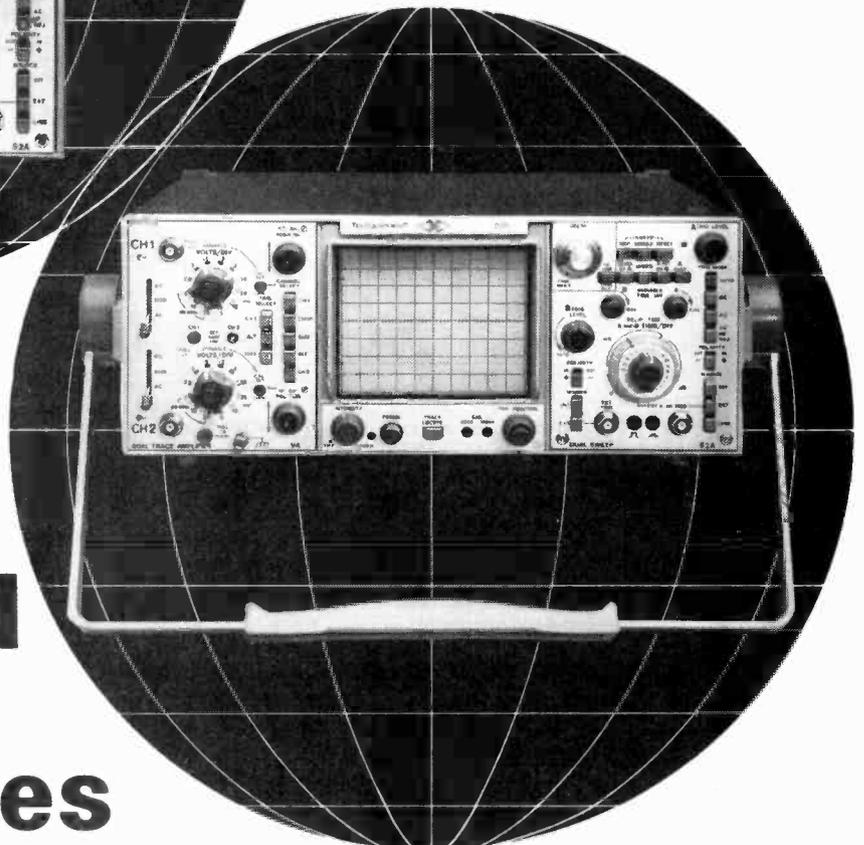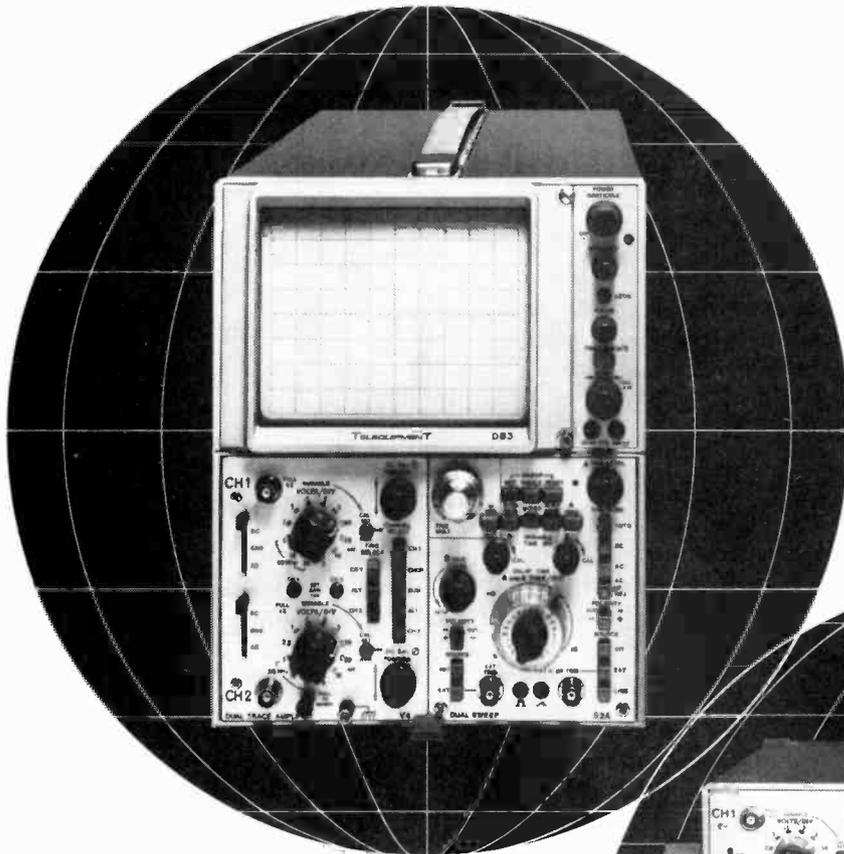

# Unequaled in their own spheres

Whether the need is for a high performance portable for field use or for a laboratory-grade oscilloscope with plug-in flexibility the Telequipment D83 and D75 instruments can meet that need at highly competitive prices. Common features are a full 50MHz bandwidth at 5mV/div sensitivity, choice of single, dual, and mixed sweep operation, internal graticule CRT's, and a brilliant 15kV trace.

The D83 is designed around a 6½" CRT which provides 50% more viewing area than the usual 8x10cm CRT's. The mainframe contains one vertical and one horizontal plug-in compartment. Five vertical plug-in amplifiers cover a wide range of applications, from single channel, dual channel and high-gain differential operation to specialised

television measurements. The dual time base plug-in incorporates sweep intensifying, delaying, mixed sweep and single-shot facilities, whilst the simpler single time base unit provides the same basic sweep rates with the addition of X-Y operation.

The D75 is essentially a portable version of the D83 and offers the same high performance in applications not requiring full plug-in facilities. Optional versions are available which provide a choice between dual vertical channels with single time base, high gain differential amplifier with dual-trace or single time base. This compact, highly portable instrument is equipped with an 8x10cm CRT, and is supplied with a protective front panel cover.

**Write or telephone for leaflets and a demonstration:**

**TELEEQUIPMENT**



**Telequipment gives you more scope for your budget**

**Tektronix UK Ltd.,  
Beaverton House, P.O. Box 69, Harpenden, Herts.  
Telephone: Harpenden 63141 Telex: 25559**

WW 081—FOR FURTHER DETAILS

TQ20


# wireless world

**Electronics, Television, Radio, Audio**

DECEMBER 1975 Vol 81 No 1480
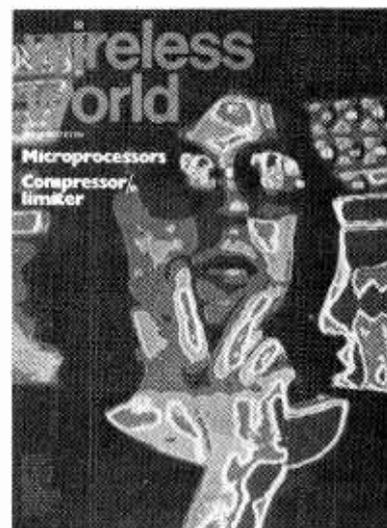
## Contents

- 549 **A star for India**
- 550 **Microprocessors** by D. E. O'N. Waddington
- 556 **News of the month**  
A-level electronics  
Advance in i.c. fabrication  
Component giants integrate
- 560 **Current dumping audio amplifier** by P. J. Walker
- 563 **Wireless World Teletext decoder — 2** by J. F. Daniels
- 567 **Applying "magnetic Ohm's law" to permanent magnets**  
by P. E. K. Donaldson
- 568 **Letters to the editor**
- 571 **Interference from pocket calculators** by Charles Thomas Ristorcelli
- 575 **Circuit ideas**  
Frequency doubler  
Linear current/rotation control  
Balanced output amplifier
- 577 **Advances in microwaves** by M. W. Hosking
- 578 **H.F. predictions**
- 579 **High resolution satellite cloud cover pictures** by P. E. Baylis
- 580 **Space news**
- 581 **Television tuner design — 3** by D. C. Read
- 585 **Announcements. Books received**
- 586 **World of amateur radio**
- 587 **High quality compressor/limiter** by D. R. G. Self
- 590 **Literature received**
- 591 **New products**
- 594 **Instruments in Bloomsbury**
- 596 **1975 Index**
- a84 APPOINTMENTS VACANT
- a 00 INDEX TO ADVERTISERS



This month's front cover shows a television monitor picture of a human face after digital processing in a video synthesizer made by Electronic Music Studios (London) Ltd.

## IN OUR NEXT ISSUE

**Phase changes in loud-speakers** — are they audible, and do they affect sound quality and stereo image formation?

**A-level electronics.** Introducing a new tutorial series based on a course that has been on trial in schools for three years.

**Television history.** On the 50th anniversary of Baird's Royal Institution demonstration a disclosure about his early apparatus.

Price 35p (Back numbers 50p, from Room 11, Dorset House, Stamford Street, London SE1 9LU.)  
Editorial & Advertising offices: Dorset House, Stamford Street, London SE1 9LU.  
Telephones: Editorial 01-261 8620; Advertising 01-261 8339.  
Telegrams/Telex. Wiworld Bisnespres 25137 London. Cables. "Ethaworld, London SE1."  
Subscription rates: 1 year, £6 UK and overseas (\$15.60 USA and Canada); 3 years, £15.30 UK and overseas (\$39.80 USA and Canada). Student rates: 1 year, £3 UK and overseas (\$7.80 USA and Canada); 3 years, £7.70 UK and overseas (\$20.00 USA and Canada).  
Distribution: 40 Bowling Green Lane, London EC1R 0NE. Telephone 01-837 3636.  
Subscriptions: Oakfield House, Perrymount Rd, Haywards Heath, Sussex RH16 3DH. Telephone 0444 53281. Subscribers are requested to notify a change of address.

© IPC Business Press Ltd, 1975

SIXTY-FIFTH YEAR  
OF PUBLICATION



# Introducing Powerlab: a revolutionary concept in precision power supply

Exit the panel  
meter:  
enter the  
push button

Powerlab represents an entirely new approach to bench power supplies. Designed not only for electronics laboratories but for general use as well, Powerlab does away with the conventional panel meter, replacing this with simple push-button selection of precision voltages.

These give selection of 5, 12 and 15 volts, in isolated series or parallel mode interlocked to give zero voltage at range change and half depressed point.

Voltages are adjustable if necessary  $\pm 10\%$  by a precision calibrated slide potentiometer. For series operation,  $B\Delta V$  tracks  $A\Delta V$  to  $\pm 0.1\% A\Delta V$ .

Good things come in  
pairs

Powerlab has dual twin isolated power outputs, with push-button mode selection of internal connection in Series or in Parallel. So Powerlab provides an ideally flexible power source.

We're a little remote...

And we mean to be, with Powerlab's built-in remote sense which overcomes variance in voltage between source and board, so that you know you're getting  $\pm$  precisely the right voltage.

Put it in...cut it out

The jack plugs on Powerlab ensure perfect connection and the screened cable reduces extraneous pick-up.

Repeatability

You don't need to use a DVM to recheck settings. Output voltages can be reset to within 20 mV on 5 Volt range.



**£75**

Nothing  
new-fangled  
about Powerlab

The concept of Powerlab may be unconventional – but its circuitry is safely conventional. So there's no worry about problems cropping up through untested innovations in this area.

Practical design makes  
for practical use

Powerlab doesn't just look smart – it is smart. Its flat top means that it can easily be stacked. Its clear instrumentation

makes for simple operation. And its push-button controls promise fool-proof handling.

The right price for  
the right package

Powerlab will cost you £75. That's all – for the most radical advance in power supply equipment for generations. Its capability, flexibility and ease of operation put it way ahead of conventional power supply apparatus.

For fuller information send the coupon to: ITT Components Group Europe, Standard Telephones and Cables Limited, Electrical Products Division, Edinburgh Way, Harlow, Essex CM20 2DE.

Name \_\_\_\_\_  
 Position \_\_\_\_\_  
 Company \_\_\_\_\_  
 Address \_\_\_\_\_

Components **ITT**  
www12

# wireless world

## A star for India

**Editor:**

TOM IVALL, M.I.E.R.E.

**Deputy Editor:**

 PHILIP DARRINGTON  
 Phone 01-261 8435

**Technical Editor:**

 GEOFFREY SHORTER, B.Sc.  
 Phone 01-261 8443

**Assistant Editors:**

 BILL ANDERTON, B.Sc.  
 Phone 01-261 8620  
 BASIL LANE  
 Phone 01-261 8043  
 MIKE SAGIN  
 Phone 01-261 8429

**Production:**

D. R. BRAY

**Advertisements:**

 G. BENTON ROWELL (*Manager*)

 KEVIN BURNAL  
 Phone 01-261 8515

 ROGER PORT  
 Phone 01-261 8037

 O. BAILEY (*Classified Advertisements*)  
 Phone 01-261 8508 or 01-261 8423

 JOHN GIBBON (*Make-up and copy*)  
 Phone 01-261 8353

 IPC Electrical-Electronic Press Ltd  
 Publisher: Gordon Henderson

India is irradiated. Since August 1, an entire sub-continent has been lit with a beam of u.h.f. television signals from a single source, the Applications Technology Satellite ATS-6 now positioned in synchronous orbit over Lake Victoria in East Africa (see Space News, September).

Looking back over 1975, this must surely be the most important project of the year in the application of electronics to human welfare. Important on two counts. Technically, it is the first example of direct broadcasting from a satellite providing coverage of a whole country. (Earlier the ATS-6 had been used for a direct broadcasting experiment in America to isolated communities in Appalachia, the Rocky Mountain region and Alaska.) Socially, it is an ambitious attempt to help the backward, underprivileged people of rural India to understand how they can improve the material conditions of their life. Programmes giving instruction on modern agricultural methods, nutrition, health, hygiene and birth control (as well as other educational and cultural programmes) are being transmitted by All India Radio, via the satellite, to 2400 remote villages in 20 districts spread over the country. There are in fact six clusters of villages, each with about 400 communal receiving stations. Signals on 860MHz from the satellite are picked up by 10ft diameter dish aerials made cheaply of chicken wire, and pass through frequency converters to television sets installed in public buildings for communal viewing.

All this comes, incidentally, just 30 years after Arthur C. Clarke suggested the possibility of direct broadcasting from satellites in his prophetic article "Extra-terrestrial relays" in the October 1945 issue of *Wireless World*.

Unfortunately the Satellite Instructional Television Experiment, as it is called, is indeed just an experiment. It is to last only a year, after which the ATS-6 satellite will be moved on to a new position in the western hemisphere. Considering the enormous problems of rural India – poverty, illiteracy, epidemics, fragmented and inefficient agriculture, all made worse by a caste system which condemns most people to automatic inferiority – it is futile to imagine, as the Indian broadcasters admit, that one year's exposure to television will make any real difference. And for this brief experiment, the expenditure on the ground hardware and facilities has been very high for a poor nation – about £6 million. One year is barely enough to sort out the operating problems, both technical and in the presentation of programmes, let alone derive useful social knowledge from the experiment. It's a pity that NASA, who provided the satellite, could not have been persuaded to leave their vital relay in place for at least another year. One can only echo the expressed hope of All India Radio that this "mammoth" experiment will help to create a "climate for development" in the backward areas of the country. Centuries-old patterns of life and work will not be changed in a few months but expectations may be.

India already has its own scientific satellite, built in Bangalore and launched by the USSR. The need for its own direct broadcasting satellite is much more pressing.

# Microprocessors

## An introductory discussion of the principles of design, programming and application

by D. E. O'N. Waddington, M.I.E.R.E.

Computer control! These two words conjure up visions of intelligent automatic systems far beyond the reach of us ordinary mortals. Until recently this has been true but it will not be long before microprocessors will be appearing in all sorts of unexpected and even mundane applications. Originally, digital computers were somewhat ponderous and unreliable, using many thousands of thermionic valves, kilo-amps of heater current, were built in large racks and housed in air-conditioned rooms to prevent them from dying of heat exhaustion! This was changed, to a large extent, by the introduction of semiconductor technology. The use of transistors enabled smaller and more efficient computers to be designed, although the need for some form of air conditioning has remained. Silicon integrated circuits allowed further size reduction, as it was now possible to put many logical functions into a very small volume.

This led to the design of the "mini-computer" which is small in size, in comparison with earlier computers, but is usually comparable in performance to much larger machines. A basic form exists which is, in effect, a mini-computer without all the mechanical frills and may even consist of a few, albeit rather large, printed circuit cards. New semiconductor production techniques together with improved quality control are now making true large-scale integration possible so that, although Isaac Asimov's positronic robot is still in the future, the "computer on a chip" has arrived under the alias of Microprocessor. Admittedly, it is not the equal of the large computer or even the mini, but it does represent a new generation of pseudo-intelligent circuits which will change the design and operation of machines ranging from cookers, cars and traffic lights to measuring instruments, automatic landing systems and process control.

One of the main attractions of microprocessors is price. Full size computers can cost tens of thousands of pounds and even minis cost in the order of one to ten thousand. The faster microprocessors cost between £100 and £500 and

### Using microprocessors

One of the prime reasons for using a microprocessor in a control system is its flexibility. Many systems which use these devices could, in theory at least, be made with smaller-scale logic packages in a purpose-designed form, but any changes needed in an operational sequence would involve expensive changes in logic design and printed-circuit layout. Changes in a system using a microprocessor only require a programme change, and the reliability of the system gains from the reduction in the number of integrated circuits.

A typical application for a microprocessor would be the operation of a supermarket cash-point where, together with its input/output devices (keyboard, display, tally-roll printer, etc.), the microprocessor would display the price total, check prices against codes, count the total number of articles, deduct these from stock and inform stock control, dispense change, issue a receipt and send the total to the accounts department.

Possible domestic use of microprocessors includes the control of central heating, taking into account external temperatures, time of day, and internal temperatures desired and achieved. Simulating the occupation of a house when the owner is absent is also a possibility; lights would be switched on and off at relevant times, curtains would be drawn and it is even suggested that the sound of water music could be caused to issue from the bathroom from time to time.

Cars are particularly receptive to microprocessor control. When fed with information derived from sensors on engine temperature, exhaust gas composition, piston position, road speed, engine speed, accelerator depression, road wheel forces, seat belt connexion, etc., the optimum adjustment of mixture and timing to obtain efficient running and least pollution can be maintained, braking can be controlled in such a way as to reduce skidding and the car can be made to refuse to go at all unless the driver has fastened his seat belt. No doubt a breath "sniffer" could also be incorporated in the system.

simple 4-bit machines now cost from £30 to £100, depending on volume and complexity. Prices are still falling, and the new Texas Instruments TMS1000, a one-chip 4-bit machine, primarily intended for calculator type applications but also suitable for use in small control systems, is reputed to cost less than ten dollars. However, this low price applies only to large quantities and does not include the initial charges for the design and manufacture of programming masks, which could be in the order of £10,000. If microprocessors continue to follow the same price trend as most other semiconductor devices, the minimum prices will not be reached for some time yet, so there will probably be substantial price reductions over the next few years.

Before discussing microprocessors in more detail, it is as well to try to answer the question: "What is a computer?". The full definition is very wide ranging but, in the electronics world it has come to mean an electronic machine which is capable of carrying out a set of instructions (programme), either arithmetical or logical, without the need for operator intervention other than to specify which programme is required. In its simplest form, shown in Fig. 1, a computer consists of three main parts; a central processor unit (c.p.u.), a memory or store and input/output ports. The programme or set of instructions which control the operation of the computer is stored in the programme memory and is "read" in sequence by the c.p.u. which carries out each instruction as it is received. The data memory is used to store the data which is to be operated on and the c.p.u. can gain access to the locations in this memory either to read the data stored there or to write new information. As a computer is only capable of recognising 1's or 0's it carries out all its operations in binary code, although frequently instructions are in binary-coded octal, decimal or hexadecimal. In order that the computer may serve a useful function it has to be able to communicate and this is done via the input/output ports. Typical inputs are derived from tape-readers, teletypes and trans-

ducers while outputs may go to line-printers, video display units, control valves, etc.

The basic operating sequence for a computer is as follows: (a) send to the programme memory the address of the instruction to be carried out; (b) read and decode the instruction; (c) implement the instruction. This sequence, illustrated in Fig. 2, is usually known as a machine cycle or micro-cycle and the time taken for its completion is frequently used to define the speed of the computer. This can be misleading as some computers have far more powerful instruction sets than others.

**Central processing unit**

This description is obviously an over-simplification, so we will look at the architecture (the "in" word used by computer men to describe the layout) of the c.p.u. in more detail as it is this which defines the character of the

computer. Fig. 3 shows a typical c.p.u., which is likely to consist of the following main units.

**Accumulator register.** This usually contains one of the operands to be processed by the arithmetic and logic unit (a.l.u.). A typical instruction could tell the a.l.u. to add the contents of some other register location to the accumulator register and to store the result in the accumulator. Thus the accumulator could be regarded as the main working register into which data and results are written and processed, and from which they are subsequently despatched to memory or output ports.

**Programme counter.** The instructions which form a programme are stored in the programme storage memory in sequence so that, in order to carry out an operation correctly, the c.p.u. has to keep a count of where it is in the

programme. This, then, is the main function of the programme counter. However, programmes frequently contain subroutines which may be called for at any point during the execution of the main programme. Subroutines are sets of instructions used to carry out specific tasks which may be needed several times during the execution of a programme. In a desk calculator type of environment, for example, the calculation of functions such as square, sine, logarithm or root, might each call for a separate subroutine which might, in turn, call for subroutines to add, subtract, multiply and divide. In a control system, the operation of each function might call for a separate subroutine, while the overall operation is unified by a main programme calling for the subroutines as required.

When a jump-to-subroutine instruction occurs in a programme, the address of the next sequential instruction must

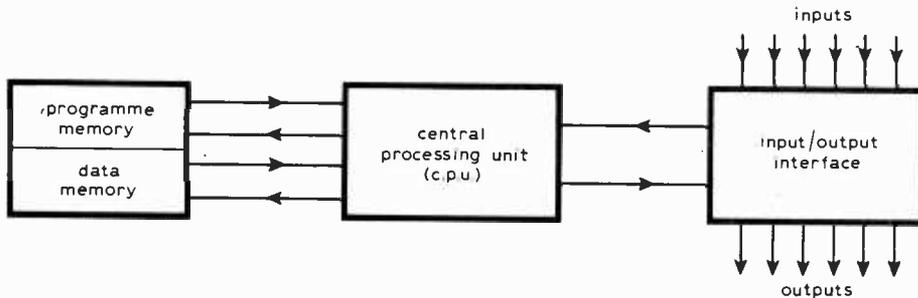


Fig. 1. Basic computer system.

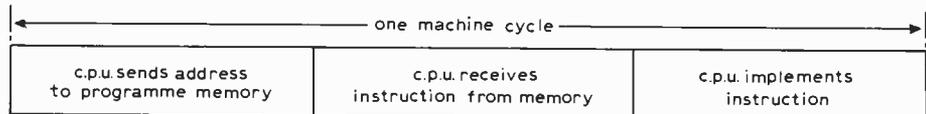


Fig. 2. Computer machine cycle.

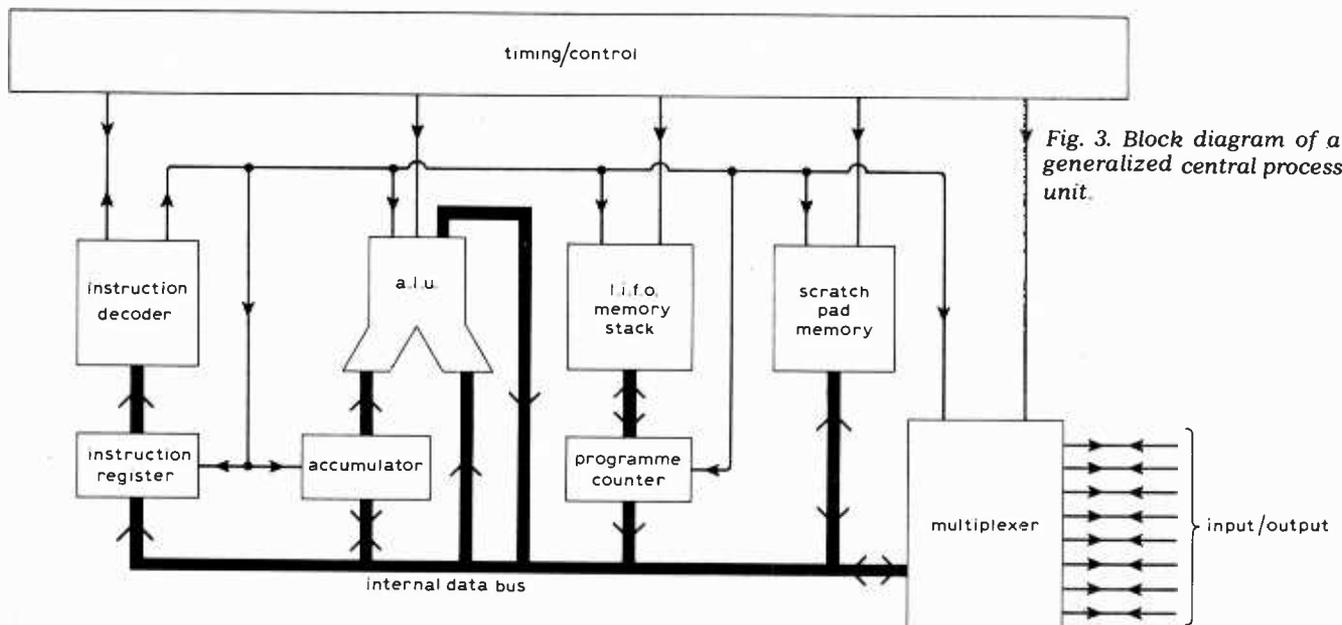


Fig. 3. Block diagram of a generalized central processor unit.

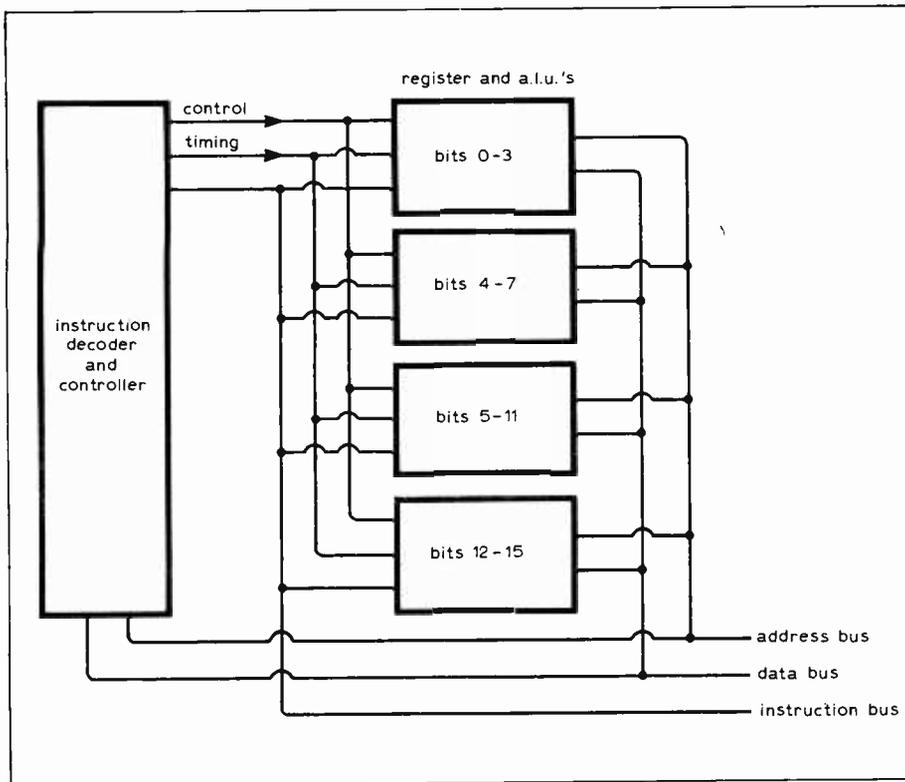


Fig. 4. "Bit slice" c.p.u. configuration.

be stored so that the processor will know where to return at the end of the subroutine, and the address of the first instruction in the subroutine must be inserted into the programme counter. In a microprocessor, this operation is usually done by means of a "push down stack" memory which is also sometimes called a "l.i.f.o." or last-in, first-out memory. Thus the jump-to-subroutine instruction causes the current address to be pushed down one step and the new address is written into the top location. A further jump instruction might cause both of these addresses to be pushed down another step. This occurs when nested subroutines, i.e., subroutines which call for further subroutines, are used. Obviously, the number of subroutines which can be nested before losing the original return address will depend on the depth of the stack, which will vary from one type of microprocessor to the next. At the end of the subroutine the programme "branches back" and the last return address stored is replaced in the programme counter register. This causes the processor to resume its programme from the point immediately following that at which the branch occurred.

**Instruction register.** When the c.p.u. receives an instruction from memory, it stores it in the instruction register, which holds it for decoding. The length of the instruction will depend on the type of processor. A simple processor, for example, will probably use an 8-bit instruction code. This will give a capacity of up to 256 separate instructions, each of which will consist of a series of 1's and 0's. In practice this is more than sufficient, although some machines use variable-length instruction codes which not only tell the c.p.u.

what operation is required, but also specify one or more addresses for fetching data or writing results.

**Instruction decoder.** The function of this is to decode the instructions and tell the c.p.u. what to do with them — a task which, though appearing formidable, is no more difficult, in principle, than a b.c.d. to 7-segment display decoder, although a different technique is usually used. Generally, the instructions are grouped so that those associated with a particular portion of the c.p.u. have the same "signatures". The four most significant bits in the instruction might be used to define a separate section such as "data transfer", "arithmetic functions" or "logical operations", etc. In this way the decoding can be simplified considerably.

**Scratch pad memory.** This section is used for all sorts of temporary storage as it is usually more easy to gain access to than the main memory area. One of its main uses in the simpler machines is to store addresses of working memory locations or input/output ports which the c.p.u. will need to use. These addresses can usually be incremented by single instructions so that successive memory locations can be addressed for iterative operations.

**Arithmetic/logic unit (a.l.u.).** All processors include some form of arithmetic/logic unit which is often known as the a.l.u., although sometimes the registers are included in the description when it is called the r.a.l.u. The a.l.u. is the section which actually performs the computation and it will normally be

expected to be able to carry out the following operations as a minimum requirement:

- addition with carry
- subtraction with carry
- left and right shift
- count up/down
- logical AND and OR
- digital word comparison for conditional branching. This may be simple zero/non-zero detection or full word comparison.

More sophisticated a.l.us will include additional functions such as hard-wired multipliers or dividers and more comprehensive logical operations.

As the a.l.u. is based on digital processing techniques, it will carry out all of its operations in binary notation so that the programmer will need to understand binary arithmetic techniques. However some processors which have been designed for calculator type applications will include binary/b.c.d. (binary-coded decimal) conversion instructions.

**Clock and control circuitry.** The clock generates the timing information for the whole processor system. Its frequency is usually determined by the speed at which the various parts of the c.p.u. can function, although the speed of the memories is also a factor which may have to be taken into account. The actual sequence of events in the c.p.u. is organized by the control circuits. Normally the sequence is fixed, but the control circuit will usually be able to respond to an external request for attention. This is known as an "interrupt" and it will cause the programme to jump to a subroutine which will identify the source of the interruption, service it and return control to the main programme.

These then are the main parts of the c.p.u. In the past they have ranged from several racks of valved equipment down to a single printed-circuit card containing a series of l.s.i./m.s.i. chips. The idea of putting a c.p.u. on a single chip has been around for many years, but for a long time it was not practical. The number of transistors necessary to make a practicable processor is such that a relatively large piece of silicon (about 4mm square) is necessary for the integrated circuit. Both the Intel 8080 and the Motorola 6800 use well over 5000 transistors! Of necessity, this means that unless the crystal slice into which the transistors are to be diffused is perfect, the manufacturing yield will be low and prices correspondingly high. The use of m.o.s. technology has helped the situation considerably, although some small processors using bipolar transistors are now available. Two types of m.o.s. circuit are generally in use; p.m.o.s. which is the least difficult to make and n.m.o.s. which needs tighter production control but which has the advantage that the transistors can be smaller and, as a result, can work at a higher speed.

Most surprisingly it is not the number of transistors which determines the size of the final integrated circuit chip but the amount of interconnection. Usually, the transistors take up less than 10% of the surface area. C.m.o.s. would appear to be an ideal medium for microprocessors as it combines good speed performance with low power consumption. However, it also requires a relatively large area, so that it is not as attractive to make. Nevertheless, at least two manufacturers are now offering c.m.o.s. processors. Bipolar transistor processing, as the oldest-contender in the field of integrated circuits, would appear to be ideal as it has the advantage of the best speed performance. It also, however, has the disadvantage that it uses considerably more power than m.o.s. and this sets an additional limitation on the size of processor which can be made. In order to overcome this, devices known as "bit-slice" processors have appeared. The basic processors are made as two or four bit slices which can be connected in parallel to make up the required word length as in Fig. 4. The major advantage of these

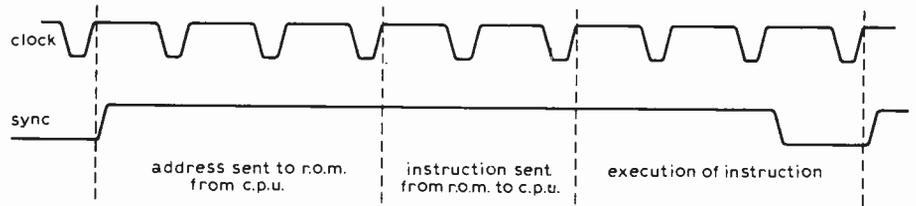


Fig. 5. One machine cycle using a 4-bit bus, illustrating the limitation when compared to higher-capacity buses.

processors is speed. They can be designed to have a cycle time of 200ns or less — an order faster than n.m.o.s.


In all processors the number of bits in the bus system is an important factor in determining the effective speed. With a 4-bit bus, addresses can only be sent in 4-bit "nibbles". This means that in order to address 4k (4096) words of store, it will be necessary to send three 4-bit nibbles of address ( $4096 = 2^{12}$ ). If the instructions are each eight bits long it

will then take a further two clock cycles to read the instruction. Thus a minimum of five clock cycles is necessary to carry out the first two parts of the machine cycle. It could then take a further three clock cycles to implement the instruction, so that one machine cycle will take eight clock cycles or, with a 1MHz clock, 8  $\mu$ s as in Fig. 5. However, if the data bus were 12 bits wide, this same operation could be carried out in three or four clock cycles, i.e., twice as fast.

**Programme storage**

In the past, magnetism has played a great part in computer memories or stores. Core stores are still very widely used, as they have no mechanical

Fig. 6. Basic 4 x 4 read-only memory array.

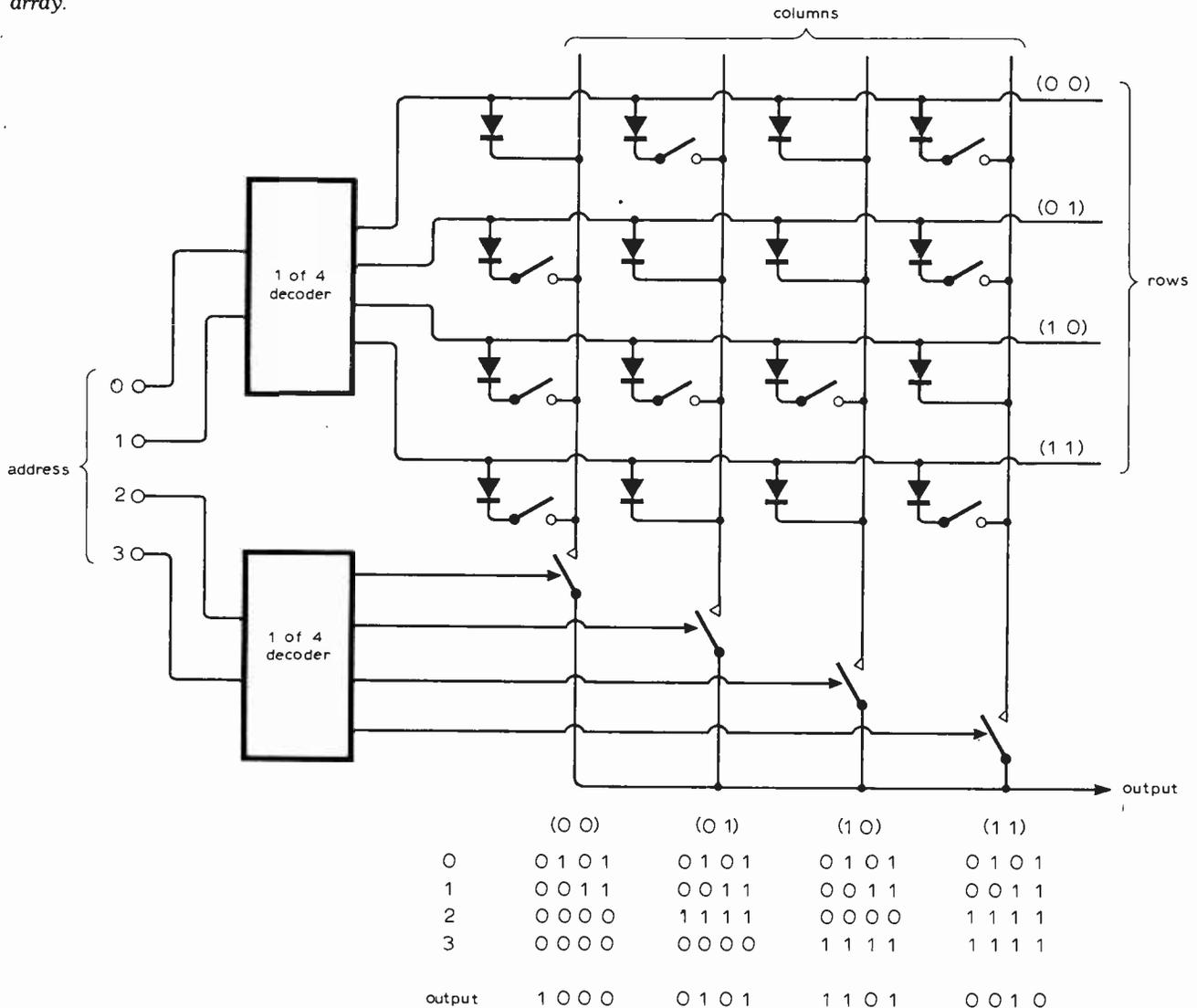

moving parts, they are non-volatile, i.e., they retain their information when switched off, and they can be made to occupy a relatively small volume. In fact, for a computer which is to be reprogrammed periodically, they form an ideal storage medium. Most micro-processor systems work with fixed programme control, i.e., the programme need seldom if ever be changed as the processor is dedicated to a single task. For these, core stores are an "overkill" as they require a considerable amount of drive circuitry and provide a facility which will never be used. Thus another kind of store, the read-only memory or r.o.m. is generally used. These consist of logic circuit arrays which can be programmed to give either a 1 or 0 as each location is addressed. Read-only memories can be made in all the various semiconductor technologies. The main differences between these are size, i.e., the number of bits which can be stored, logic levels, reprogrammability and access time. In general bipolar memories are faster than their m.o.s. counterparts, but the latter usually have more capacity.

In its simplest form, a read-only memory is an array of open or closed unidirectional contacts, the state of the contact determining whether the location contains a "1" or a "0". In the 16-bit array shown in Fig. 6, half of the address lines are decoded to energize one of the rows. This activates those column lines which have closed contacts to the selected row. The other address lines are decoded and used to select a column. Thus a selected closed contact will result in a "1" at the output. In a memory for a microprocessor, r.o.ms are usually arranged so that an address selects eight locations in parallel, so that a single address will locate an 8-bit word.

One of the main distinctive features of a r.o.m. is the method by which it is programmed.

**Mask-programmable r.o.ms.** As implied by the name, these are programmed by a metallization pattern which is either deposited on the surface of the r.o.m. through a mask or selectively etched through a mask. This method of manufacture has a lot to commend it, as the manufacturer can hold stocks of r.o.ms which only need their final masking to provide any memory pattern required. Thus the process of making a r.o.m. need only take the time necessary to produce the final mask and metal pattern. This reduces the time necessary to produce a r.o.m. to about six weeks. However, the disadvantages are that the system designer has no control over the manufacture and there is no room for any error. He must be right!

**Electrically-programmable r.o.ms.** These fall into two main types; those which, when programmed, cannot be changed and those which can. The first

Table 1

Manufacturer	General Instruments	Fairchild	Advance	Intel	Intel	Intel	Intersil	Motorola	MOS Technology	National	National	MOSTEK	Plessey	RCA	Texas Instruments
Type	1600	F8	Two chip	4040	8080	IM6100	M6800	MCS6501	IMP 4	IPC-16A/500D (PACE)	MK5065P	MIPROC	TA6889/90 (COSMAC)	TMS1000	
Package	d.i.l.	d.i.l.	d.i.l.	d.i.l.	d.i.l.	d.i.l.	d.i.l.	d.i.l.	3 chip set	d.i.l.	d.i.l.	Printed circuit	two chip	d.i.l.	
Number of pins	40	40	24 & 28	24	40	+5, -12	+5	40	+5, -12	+5, +3, -12	40	+5	+5	4/40	
Supply voltages	+5, -12	+5, -12	+5, -12	1W	1W	1W	1MHz	1MHz	1W	700mW	+5, -5, -12	+5	60mW	15	
Power	350mW	350mW	350mW	740kHz	2.083MHz	2MHz	1MHz	1MHz	500kHz	500kHz	1.4MHz	2MHz	2MHz	600mW	
Clock frequency	55kHz	55kHz	55kHz	2	2	1	2	2	2	2	2	1	1	400kHz	
Phases	2	2	2	2	2	1	2	2	2	2	2	2	2	15µs	
Register cycle time	400ns	2µs	400ns	10.8µs	2µs	5µs	2	2	12µs	2µs	350ns	8	8	4	
Data word (bits)	16	8	16	4	8	12	8	8	4	8/16	8	8	8	8	
Programme word (bits)	16	8	16	4	8	12	8	8	4	16	8	8	8	8	
Programme addresses	384	64k	64k	8k	64k	4k	64k	64k	64k	64k	32k	64k	64k	1k	
Interrupt	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	
d.m.a. ability	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	
b.c.d. arithmetic	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	
Comments	Manufactured by G.I. to Advance design calculator	Calculator oriented. 4004 is earlier version!	Calculator oriented. 4004 is earlier version!	c.m.o.s. type compatible with PDP8/E software	Full range of peripheral drivers	Similar to M6800 and 16 bit version available soon	8 and 16 bit versions available	Also manufacture FB	c.m.o.s. type	Single chip system includes ROM and RAM					

**Bit slice microprocessors**

Manufacturer	Advanced Micro Devices	Intel	Monolithic Memories	Texas Instruments	Motorola
Type	AM2901	3002	5701/6701	SBP 400	M10800
Technique	Schottky t.t.l.	Schottky t.t.l.	Schottky t.t.l.	i <sup>2</sup> L	e.c.l.
Cycle time	100ns	100ns	200ns	530ns	55ns
Data word	4	2	4	4	4

type contain some form of fuse which is "blown" by the application of a suitable pulse during the programming process. One type includes links of either nichrome or polysilicon. It is claimed that the latter are more reliable as there is a tendency for nichrome to "grow" back and connect once more. A variant on the fusible link is the shorted-junction where transistors with no physical connection to their bases are diffused into the substrate. By applying a high potential between the collector and emitter, the transistor is forced to break down and a short is formed between the emitter and base, changing the transistor into a diode. This process is a critical one and needs precise control. These p.r.o.ms are all made using bipolar technology.

Two main types of p.r.o.m. are made using m.o.s. transistor arrays. Unlike their bipolar counterparts they are erasable so that they can be reprogrammed, a facility which makes them ideal for development of microprocessor systems. One of the best known types uses f.a.m.o.s. or floating-gate avalanche injection m.o.s. which was introduced in 1971 by Intel. In this type, shown in Fig. 7, a floating gate is induced into the silicon dioxide separating the source and drain of an m.o.s. transistor by applying an excessive voltage to the device. As no discharge path is available for this gate, the charge remains unchanged and it is predicted that if the device is maintained at a temperature of 125°C for 10 years, at least 70% of the charge will remain. At lower temperatures the charge would remain even longer. However, if the device is exposed to strong ultra-violet radiation, the charge may disperse in 5 minutes, when the p.r.o.m. can be reprogrammed. This type is easily recognisable, as the chip is covered by a transparent quartz window.

Another type of m.o.s. p.r.o.m. is known as the e.a.r.o.m. or electrically-alterable r.o.m. Actually, it uses m.n.o.s. in which an additional gate insulation layer of silicon nitride is used. During programming, which is done electrically, a charge is trapped in the gate region and it is possible to sense this charge up to 10<sup>9</sup> times before there is any uncertainty. This is not sufficient for programme storage but, if it is provided as a back up to a read/write memory it may be used to provide a non-volatile store for data. However, it takes an appreciable time, of the order of 2ms, to save data in an e.a.r.o.m. so that these are not in general use.

In addition to the programme storage, a microprocessor system usually contains a memory to store results or data. This is normally known as r.a.m. or random-access memory which, strictly speaking, is a misnomer as the access to r.o.m. may be equally random. It is probably better to call this read/write memory as it is used in this fashion. Just as the amount of r.o.m. used in a system depends on the programme

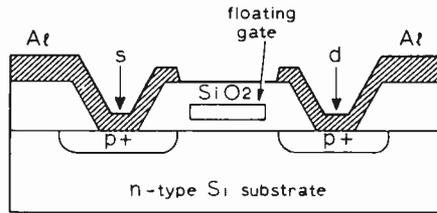


Fig. 7. Cross section through an idealised f.a.m.o.s. transistor.

requirement, the amount of r.a.m. needed will depend on the data storage requirement. R.a.ms consist of arrays of flip-flops which are set or cleared according to the data stored. As with r.o.ms they are made in both bipolar or m.o.s. form. Bipolar devices are generally very much faster but they absorb an appreciable amount of power. M.o.s. r.a.ms may be either static or dynamic: in the former, the data is stored in normal flip-flop type circuits, but in the latter it is stored as electrical charges holding transistors "on" or "off". As the charges leak away gradually, dynamic r.a.ms are refreshed by "clocking" them periodically to replenish the charge.

**Programming**

Like computers, microprocessors need to be programmed if they are to serve any useful purpose. The processor recognises ones and zeros. However, although a human programmer can learn all the machine codes, it is a very tedious business to try to write a complete programme in machine code. Thus various computer languages have evolved. The simplest type is known as assembly language or assembler code and consists of groups of two, three or four letters, known as mnemonics, which relate directly to the machine codes and describe the instructions. For example:

NOP .....	no operation
ADD X .....	add the contents of the register X to the accumulator with carry.
XCH X .....	exchange the contents of register X with the accumulator.
RD Y .....	read the contents of register Y into the accumulator.

This type of language is relatively easy to use once all the implications and limitations of each instruction is understood. This is very important as the c.p.u. has no intuition. It can only carry out instructions which it is given and not guess at those which have been left out. In order to convert a programme written in assembly language into machine code, one of two courses is available. The first is to do it very patiently and inefficiently by hand, a procedure which is not recommended for more than about 20 commands. The

second is to make use of a programme known as an assembler, which examines the source programme (i.e., assembly language) and converts into machine code. In most machines a "two pass" assembler is used, feeding the source programme to the assembler twice. The first time, the assembler converts the mnemonics to machine code, looks for syntax errors and allocates addresses to the instructions. The second time it fills in all the addresses for the "jump" instructions. Assembly language programming is probably the most efficient when it comes to making the optimum use of memory space and, as such, is most generally used for small to medium sized systems. However, it can be tedious for large programmes, so that high level languages are being developed to allow programmes to be written using a limited English/mathematical vocabulary. One such language is PL/M, which has been developed by Intel for their 8080 system and no doubt other manufacturers are developing their own languages. Programmes written in these languages are then converted into machine code using a programme known as a compiler. Although this method provides a degree of built in "intuition", so that the programmer does not need to worry about all the minor details, compilers do produce programmes which take up to 40% more storage than the corresponding assembly language programme. Another approach is to use an "interpreter" which is a programme which converts the programme to be executed directly into machine code as it is used. As this implies, the processor has to have two programmes built into it, the interpreter and the programme which is to be executed. This approach is only really suitable for very large machines at present but, as microprocessors get "smarter," we may see them with built-in interpreters. Interpreters, however, are inevitably rather slow.

**Microprocessor circuits**

The first microprocessor was introduced by Intel in 1971 and was a 4-bit machine called the 4004. This was the first of its kind; a 4-bit machine, oriented towards calculators but capable of very much wider application. Shortly it was followed by an 8-bit model, the 8008. The latter has been superseded by the 8080, a n.m.o.s. machine with a 2µs instruction cycle and 70 instructions. The power dissipation is only 600 mW and there is a full range of r.o.ms and r.a.ms, clock and interface receivers and drivers so that a complete system can easily be built. Intel have also introduced the 4040 which is primarily a calculator-oriented machine which has an instruction cycle of 10.2 µs, 47 instructions and which can be used for many other applications.

Some of the types known to me are shown in Table 1.

# Meetings

## DECEMBER

### LONDON

3rd. BKSTS — "Impressions of television and film in the USA and Canada by A. B. Palmer at 19.30 at Thames Television Theatre, 308-316 Euston Rd., NW1.

4th. IEE — Discussion on "Are fibre optics the answer to aircraft signal transmission problems?" at 17.30 at the Royal Aeronautical Society, 4 Hamilton Pl., W1.

4th. IERE — "Dynamic system checkout" by Prof. D. R. Towill at 18.00 at 9 Bedford Sq., WC1.

4th. RTS — "Progress in colour receiver design" by M. F. Bowers at 19.00 at the Conference Suite, London Weekend Television, South Bank TV Centre, Upper Ground, SE1.

5th. IEE — Colloquium on "Communication for the deaf and dumb" at 10.30 at Savoy Pl., WC2.

5th. RI — "Acoustics regained" by Eric A. Ash at 20.45 at The Royal Institution of Great Britain, 21 Albemarle St., W1.

8th. IEE/IERE — Colloquium on "Computer aids to software and system design" at 10.30 at Savoy Pl., WC2.

8th. IEE — Discussion on "Ultra-violet and infra-red curing of printed and coated materials and ultra-violet sterilisation" at 17.30 at Savoy Pl., WC2.

10th. I.Phys./IEE — One-day meeting on "Light detection" at 10.00 at Imperial College, SW7.

10th. IERE — Colloquium on "The electronics of electronic organs" at 14.00 at Engineering Theatre G6, University College, Torrington Pl., WC1.

10th. IEE — "On-line capture and analysis of transient phenomena" by C. Buffam at 18.30 at Savoy Pl., WC2.

10th. BKSTS — "Specialised techniques in television film production" by G. Anderson at 20.30 at NFT2, National Film Theatre, South Bank, Waterloo, SE1.

11th. RTS — The Shoenberg Memorial Lecture on "The history of videotape recording" by J. Roizen at 19.00 at The Royal Institution, Albemarle St., W1.

11th. IEETE. — "Electrotechnology in offshore oil fields" by D. S. Townend at 18.00 at the IEE, Savoy Pl., WC2.

12th. IEE — Colloquium on "Technological developments in the fabrication of MOS integrated circuits" at Savoy Pl., WC2.

15th. IEE — "The NPL reference volt" by C. H. Dix at 17.30 at Savoy Pl., WC2.

16th. IEE — Discussion on "Intelligent instruments" at 17.30 at Savoy Pl., WC2.

17th. IEE — "Engineering for biomedical research" by D. Rothwell at 17.30 at Savoy Pl., WC2.

18th. IEE — Colloquium on "Review of digital signal processing" at 9.30 at Savoy Pl., WC2.

18th. IEE — "The development of the Doppler microwave landing system" by K. Kelly at 18.30 at Savoy Pl., WC2.

30th. IEE — "Electronics in crime prevention" by G. Phillips at 14.30 at Savoy Pl., WC2.

31st. IEE — "Electronics in crime prevention" by G. Phillips at 14.30 at Savoy Pl., WC2.

### ARBORFIELD

4th. IERE — "Terotechnology" by H. Lukes at 19.30 at the Lecture Theatre, School of Electronic Engineering, R.E.M.E., Arborfield.

### BELFAST

2nd. IERE — Discussion on "The role of the engineer in society" at 19.00 at Cregagh Technical College, Montgomery Road.

### BIRMINGHAM

10th. RTS — "Optical fibre communications" by M. R. Mathews at 19.00 at the ATV Centre, Broad Street, Birmingham 1.

### BLANDFORD

2nd. IERE — "Opto-electronics — illuminating the future" by R. J. Abraham at 18.30 at School of Signals, Blandford Camp.

### BOURNEMOUTH

3rd. IEE — "Microprocessor technique" by R. Savage at 19.30 at Durlston Court Hotel.

11th. IEE — A Christmas lecture on "Computers and users" by Peter Clarke at the College of Technology, Lansdowne.

### BRISTOL

1st. IEE/IERE — "Open University technology courses — an outsider's view" by Dr S. L. Hurst at 18.00 at Queens Building, Bristol University.

### CAMBRIDGE

11th. IEE — One-day seminar on "Unexpected inter-action in electronic equipment" at 10.00 at the University Engineering Dept., Trumpington St.

### CARDIFF

10th. IERE/I.Phys. — "Solar energy and its applications" by B. J. Brinkworth at 18.30 at Room 164, Dept. of Chemistry, UWIST.

### CHELMSFORD

10th. IERE — "Teletext — information display on the home television receiver" by P. L. Mothersole at 18.30 at the Civic Centre.

### COLCHESTER

4th. IEE — "Machine — master or slave of man?" by Prof. M. W. Thring at 18.30 at University of Essex, Wivenhoe Park.

### COVENTRY

3rd. IEE — "Computer numerical control of machine tools" by K. W. Norman and I. W. Smith at 18.30 at Lanchester Polytechnic.

### DUBLIN

10th. IEE — "The Institution and the future of the Irish branch" by J. L. Dobie at 18.00 at the Physics Theatre, Trinity College.

### GLOUCESTER

10th. IEE — "Colour TV — a popular approach" by G. D. Barnes at 19.30 at CEGB Barnwood.

### GUILDFORD

10th. IERE — "Aspects of v.h.f. reception" by R. S. Broom at 19.00 at Lecture Theatre 'F', University of Surrey.

### LEEDS

9th. IEE — "Automobile electronics" at 18.30 at Leeds University.

16th. IEE — "Computers and communications, convergence or conflict" by J. R. Pollard at 18.30 at Leeds University.

18th. IERE — Colloquium and exhibition on "Microprocessing" at 9.30 at Leeds Polytechnic.

### LEICESTER

9th. RTS — "Radio and television interference problems" by F. C. Ward at 19.30 at The Post House, Braunstone Lane East.

### LIVERPOOL

1st. IEE — "Artificial vision — past, present and prospect" by P. E. K. Donaldson at 18.30 at the Dept. of Electrical Engineering, Liverpool University.

10th. IERE — "Progress in medical instrumentation" by Dr D. W. Hill at 19.00 at the Dept. of Electrical Engineering and Electronics, University of Liverpool.

### LOUGHBOROUGH

10th. IERE/I.Phys. — "Sector scanning sonar" by Dr A. R. Pratt at 19.00 at Lecture Theatre W.O.01, Loughborough University of Technology.

### MALVERN

8th. IEE — "Electronic aids for detection and prevention of crime" by G. Phillips at 19.30 at the Winter Gardens.

10th. IERE — "Electronics in seismic exploration" by M. J. Hughes at 19.30 at the Foley Arms Hotel.

### MANCHESTER

10th. BKSTS/RTS — "Slide and sound versus cine and sound" by L. E. Slater at 19.00 at Preview Theatre, Granada Television.

11th. IEE/IERE — "Communications in oil rigs" at 17.45 at Renold Building, UMIST.

### NEWCASTLE-ON-TYNE

1st. IEE — "Microcomputers — control systems application" by J. Gallacher, at 18.15 at Rm M421 Merz Court, University of Newcastle-on-Tyne.

9th. IERE — "Practical uses of pattern recognition" by Dr J. R. Parks at 18.00 at YMCA Lecture Theatre, Ellison Place.

### PLYMOUTH

11th. IEE — Student papers evening at 19.00 at Plymouth Polytechnic.

### SHEFFIELD

11th. IEE — Faraday lecture on "The entertaining electron" by F. H. Steele at 10.30, 14.30 and 19.30 at the City Hall.

### SOUTHAMPTON

3rd. IERE/IEE — "Impact of behaviour science in management" by P. Sadler at 18.30 at Southampton Technical College.

### STONE, Staffs

8th. IERE/IEE/IPOEE — "My dear Watson" by G. Phillips at 19.00 at the P.O. Training Centre.

### SWANSEA

11th. IEE — "Technology aids the police" by G. Phillips at 18.15 at University College of Swansea.

*Tickets are required for some meetings: readers are advised therefore to communicate with the society concerned.*

## Quarter million "Foundations"

With the ninth edition of M. G. Scroggie's "Foundations of Wireless and Electronics" this famous book, from which many engineers have received their grounding in our subject, will have sold a quarter of a million copies. Since it was first published in 1936 the book has been closely associated with *Wireless World* because its author has been a much valued contributor to the journal for the whole of this period (indeed over 50 years) under his own name and as "Cathode Ray".

To commemorate the occasion the publishers of "Foundations", Newnes-Butterworths, have produced two handsome crimson leather-bound gold-embossed copies of the ninth edition. One of these has been presented to the author and the other, autographed by M. G. Scroggie, is to be the prize in a competition open to all buyers of the new edition, just out. Competitors are invited to write an explanation of "why Scroggie's Foundations of Wireless and Electronics is so popular". Details of the competition are given on leaflets inside copies of the new edition.

# News of the Month

## "A" level electronics

A conference on the pilot "A" level course in electronic systems was recently held at City University by the National Electronics Council in association with the IERE, the IEE, and the Institute of Physics. The course is not intended to be vocational training and will not replace the existing maths and physics courses. "Systems" is the area of interest, in its widest sense, and one gains the impression that electronics is used as an illustration of computer, communication and feedback systems, encountered in any sphere of living, be it biological, mechanical or, one imagines, political and social. Each type of system can be treated as a unit, and taught separately and the course material includes a selection of lecture notes and experimental hardware (an ingenious breadboard particularly caught the eye) designed by a team at the University of Essex, led by Prof. G. B. B. Chaplin. Speakers at the conference included two teachers, G. F. Bevis (Richard Taunton College) and D. Thompson (Welbeck College) who were loud in their praise of the course material, Mr Thompson being particularly encouraging to those teachers present who looked upon electronics with trepidation; he himself, he explained, was until a couple of years ago more at home with a rugby football than an integrated circuit.

## IEE's "Factual Salary Survey"

The Council of the Institution of Electrical Engineers, at its meeting on October 2, 1975, endorsed the recommendation of its newly formed Professional Services Board, to undertake a "Factual Salary Survey" beginning January 2, 1976, with the results being produced about six weeks later. The IEE thinks that a survey of this nature is both timely and vital in view of the present inflationary situation and the £6 per week maximum pay increase. The

normal questions of age, qualifications, grade of membership and field of employment will be supplemented by questions covering the employment status of IEE members; number employed/unemployed at the beginning of January 1976; number of weeks/months employment during 1975 and if while unemployed the engineer was advised to take part in a government retraining scheme.

## TV by tropo-scatter

A television programme has been successfully transmitted via a tropo-scatter communication system across the Mediterranean from Crete in Greece to Dernah in Libya. The 320-km system is capable of transmitting one monochrome television channel and 300 telephone channels. Transmission of television via a long-distance tropo-scatter system has been considered almost impossible due to deep selective fading characteristics in tropo-scatter propagation. Nippon Electric Company has developed a quadruple i.f. combining system to overcome this drawback. The trans-Mediterranean system is connected at Dernah to the border-to-border microwave system, completed by NEC in 1974, running along the Mediterranean Sea from Bengardane in Tunisia to Musaid near the Egyptian border. It will be further linked to microwave systems now being built by NEC in Algeria and Egypt to form a pan-African communications network. The newly completed tropo-scatter system linking Greece and Libya is expected to contribute to the development and furthering of friendly relations between the two countries.

## Royal president for IERE

In its 50th year of existence (see News, Oct.) the Institution of Electronic and Radio Engineers has installed as its president a member of the Royal Family, the Duke of Kent. At the end of a wide-ranging presidential address on the applications of electronics, including a look into the future, the Duke sounded a warning about "inherent dangers" to personal liberty in the use of electronic systems for management: "... it will be our task, together with the planners of management systems, to ensure that the privacy of the individual is preserved, that he or she is not reduced to the status of a 'human terminal' in a central management complex. I see great strides in the whole field of 'management' by the electronic devices in the future but I hope also to see an industry profoundly concerned with ensuring preservation of the essential human liberties. The almost limitless

scope for extending 'management by electronics' must be accompanied by rigorous safeguards against deliberate or accidental abuse."


The Duke's cousin Charles, Prince of Wales, has just been made an Honorary Fellow of the IERE.

## Facsimile future forecast

"Facsimile transmission over ordinary telephone lines will be much more useful and will play a much more important part in the office of the future than was previously thought. Picture telephones and other video facilities, in which executives can see the person at the other end of the line, do improve the quality of judgments made but they require very expensive telecommunications links and the extra cost is not justified by the degree of improvement obtained." These are two of the main conclusions of a new research report on the use of telephone facsimile in business which was published at the beginning of October.

The report "Telephone facsimile for business" which is a new and enlarged edition of one published early in 1973, finds that the changes in equipment and practice in the last two or three years have been more substantial than those

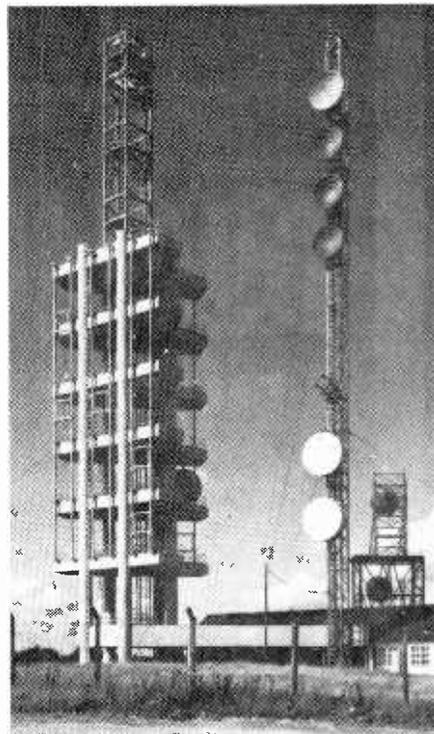*To meet increasing demands on telecommunications between the UK and Europe, the Post Office have built a new radio tower to replace the existing guyed mast and tower at their radio relay station near Folkestone. Concrete was chosen as the most suitable material for the 42m high main structure of this 64m high tower.*



that had occurred in the previous decade. This means that they have been very substantial indeed because the earlier developments converted facsimile from an expensive, specialised tool suitable only for sending very urgent information such as news photographs and weather charts into a simple, inexpensive one suitable for use on the executive desk of the smallest business. The report costs £29 and is available from Ronald Brown, FREE-POST, Stoke-sub-Hamdon, Somerset TA14 6BR.


---

## Advance in i.c. fabrication

---

A major advance in the fabrication of integrated circuits has been claimed at Bell Telephone Laboratories by the development of an "electron beam exposure system" known as EBES. By using a beam of electrons to generate the microscopic patterns from which integrated circuits are manufactured, EBES can produce integrated circuit master pattern masks faster, more reliably, with fewer defects and at lower cost than masks made by existing photographic systems. Because electrons have a smaller equivalent wavelength than light, a much "sharper" writing beam can be generated for use in the mask-making process. Circuit design instructions on magnetic tape are fed into the EBES computer which controls both the electron beam and the movable stage on which the mask blank is mounted so that the writing operation is entirely automatic.

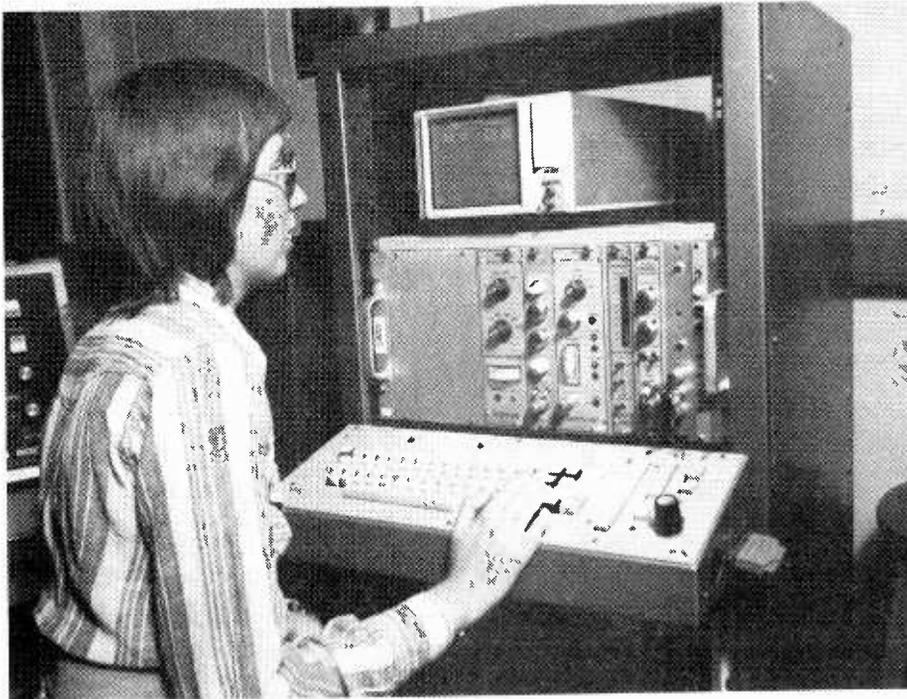*At Mullard Research Laboratories near Redhill, Surrey, a data communication network has been built which shares the computing power among a number of users distributed within a laboratory building. The results of one experiment can then be used in setting up the next with no need to provide expensive intermediate storage.*




---

## Microcircuit copyright lawsuit

---

General Instrument Microelectronics Ltd have instituted proceedings against the Plessey Company Ltd and their subsidiary LSI (Electronic Systems) Ltd alleging copyright infringement and breach of confidence.

The proceedings stem from Plessey's introduction of certain m.o.s. integrated circuits which GIM claim were copied from their designs. General Microelectronics also assert that Plessey improperly obtained process and design information from several of GIM's former employees.

The first hearing of GIM's application for a temporary injunction restraining Plessey from marketing the microcircuits was heard in the High Court of Justice Chancery Division on October 10, 1975. The circuits in question are Plessey's MP9100 push-button telephone dialler, MP9200 repertory telephone dialler store and MP1013A UAR/T which GIM claim were improperly derived from their AY-5-9100, AY-5-9200, AY-5-1013A respectively.

---

## NRDC wants more proposals

---

Despite the pressures of increased expenditure, interest charges and operating costs, a surplus of £845,000 is recorded by the National Research Development Corporation in its 26th Annual Report published on October 9.

The achievement of this surplus emphasizes the present health of the Corporation. Interest charges of £1.12M have been paid to the Department of Industry, the Corporation's interest relief grant having again been reduced this year to £0.43M.

The effects of the generally depressed state of British industry have inevitably been reflected in the Corporation's development activities during the year ended March 31, 1975. Expenditure on development rose to £3.17M (compared with £2.49M last year) but amounts authorized for investment fell from £5.21M to £4.30M. NRDC state that "Although we can appreciate that companies are reluctant, in the present financial climate, to embark on new development activities, the Corporation is concerned that it is not receiving more proposals for substantial projects involving an appropriate degree of technological innovation."

---

## Component giants integrate

---

From November 1, 1975 responsibility for all UK Signetics sales operations will be undertaken by Mullard Ltd. This follows the acquisition of the Signetics Corporation by the United States Phillips Trust earlier this year. From the beginning of November the entire Signetics range of digital and linear integrated circuits became part of the range of solid-state devices available from Mullard. This includes the recently announced Signetics 2650 microprocessor and the Mullard LOCOS4000 series of digital integrated circuits.

Sales of all Signetics i.c.s will be the responsibility of a new integrated circuit marketing group being set up within Mullard which will not only be concerned with Signetics products but also with the maintenance and expansion of the sales of all other Mullard industrial i.c.s.

According to Bill Everden, general manager of the Mullard Data Processing Division with overall responsibility for the Signetics operation "Under no circumstances do we intend to cause Signetics customers any concern whatsoever. . . . Basically all it means is that instead of contacting the Penge office they will now deal with the same team based in Mullard House."

---

## Indonesian television update

---

New transmitters, film and processing equipment for the Republic of Indonesia's television authority and radio communications equipment for use by its radio broadcasting authority will be part of an ambitious scheme to expand and update Indonesia's television and broadcasting system. Transmitters and

antennas are to be installed at six of the television authority's stations on the islands of Java and Madura as part of a plan to ensure that the majority of inhabitants of the two islands will be able to receive television programmes. At the eastern end of Java, Surabaya, an important city and port, will have its television station's existing low power transmitters replaced by a pair of 10kW v.h.f. transmitters which will radiate more than 100kW of power. Surabaya will then feed three relay stations each supplied with a pair of 1kW v.h.f. transmitters.

The contract for this work has been awarded to Marconi Communication Systems Ltd who will supply the v.h.f. television transmitters. These are self-contained and from their B7103 series of i.f. modulated equipment. Modulation at i.f. has several potential advantages, paramount amongst these being the possibility of applying at i.f. corrections which are asymmetrical about the vision carrier. Emphasis in the design of the series has been placed on the need to reduce the number of valves to a minimum in order to obtain the sort of reliability which is associated with high grade solid-state devices.



*Position Location Reporting System seen in use here was developed for the US Marine Corps by Hughes Aircraft Company's ground systems group at Fullerton, California. The set, which weighs 15 pounds, continuously and automatically exchanges information with a master unit back at the command post.*

---

## Holographic videodisc

---

The fifth method of recording video signals on disc (and the first from Japan) has been announced by Hitachi. The recording method is holographic, each frame of the television picture being concentrated in a 1mm diameter hologram on a 12in disc. All three pieces of television information — chrominance, luminance and sound — are superimposed in one hologram, and are "read out" by one laser beam inspected at three different angles. The disc spins at only 6 r.p.m. and can contain 54,000 frames — enough information for 30 minutes playing time in the NTSC standard. This seems to be a playback-only machine and will depend for its success on the supply of programme material. We hope to give more information in a future issue.

---

## Broadcasting for Pakistan villages

---

Isolated village communities throughout Pakistan are to be provided with news, entertainment and educational programmes broadcast in their own dialect. The low powered broadcasting equipment to be supplied consists of small, self-contained community radio stations, simple to operate and totally self-sufficient in power supply. Until now, many remote country villages in Pakistan have been without any form of radio broadcast communications. The national radio programmes of the Pakistan Broadcasting Corporation

could not reach these isolated districts because there was no mains power supply nor any suitable landlines to transmit a programme. The "Village Broadcaster" supplied by Standard Telephones and Cables Pty. is a fully duplicated radio station with two 25kVA diesel generators, two transmitters and two sets of studio desks plus ancillary equipment. Depending on the terrain, a range of 8 to 12 kilometres radius with good quality reception is expected. The contract is part of the Australian Government's aid programme to Pakistan.

---

## Well oiled

---

An advanced remote control and monitoring system to link Burmah Oil Developments' giant £3000M Thistle "A" drilling platform with the towing and laying vessels during the platform's deployment in the Thistle field is to use a radio communications link between the platform and support vessel during tow out. A cable link will be used as well during the deployment phase. Governing the operation will be the transmission of 150 control signals and the monitoring of over 40 analogue levels and more than 240 indications of platform status. The system, developed by EMI, also includes a unit for attitude measurement during the turnover manoeuvre and an acoustic measuring system for checking leg-to-sea-bed distances during the final touch-down phase. There is complete duplication of the encoding/decoding and radio equipment, with automatic changeover

to achieve maximum reliability. Using a 13ft model of the platform, EMI is undertaking extensive tests at its Feltham laboratories which are designed to simulate the radiation patterns that will be encountered. Similarly the entire system will be subjected to full environmental testing with vibration and temperature cycling prior to delivery.

---

## Briefly

---

**5th Salon International "Audiovisuel et Communication."** This will be held in Paris from January 24 to 30, 1977. In addition to professional and semi-professional equipment and systems, the Salon will present for the first time "light audiovisual systems". These are intended for a wide public but are of quality suitable for, among other applications, teaching, training, information and commercial promotion.

**British radio helps conquer Everest.** A Hacker Super Sovereign, RP75MB five-waveband radio was chosen by Chris Bonnington's successful British Everest expedition as its principal portable broadcast receiver.

**Computer's Esperanto.** Texas Instruments has announced a new micro/minicomputer family with the capability of operating with the same software language throughout, from a microprocessor chip up to the full-size minicomputer.

# Current dumping audio amplifier

Output power transistors' non-linearity does not appear in amplifier transfer characteristic

by P. J. Walker

*Acoustical Manufacturing Co. Ltd.*

**If Harold Black did not actually invent negative feedback, he was certainly the first to show a comprehensive understanding of the subject in his famous patent of 1937. Nine years earlier he took out a patent on feed-forward error correction'. Relatively small variations on this nearly 50 year old concept have led to the development of a new type of audio output circuit with attractive properties. The circuit was the subject of a paper presented to the 50th convention of the A.E.S. by M. P. Albinson and the writer earlier this year.**

An audio power amplifier is required to produce an output signal that differs from the input signal in magnitude only. It must therefore have occurred to every circuit designer that it should be a simple matter to take a portion of the output, compare it with the input to derive an error signal. It is then only necessary to amplify this error signal and add it to the output in the correct amplitude and phase to cancel completely the distortion of the primary amplifier. Of course, one is left with distortion of the error amplifier but being of very low power this can be made negligibly small without much difficulty.

There is a special appeal in feed forward error correction for transistor power circuits. Because of thermal limitations, the output transistors in the majority of audio amplifiers operate in

class B, in which alternate output transistors handle the negative and positive signal excursions. The output transistors are carefully biased to obtain a reasonably smooth transition from one to the other. If the bias is insufficient there will be a discontinuity in the transfer characteristic. If the bias is too great, there will be a region of overlap when the mutual conductance will be doubled. The curvature of the characteristic near cut-off precludes there being a perfect bias condition and this is further aggravated by the fact that the junction temperature and hence the bias is a varying factor depending upon both the long term and immediate past history of the programme dynamics. A compromise is


selected and overall feedback is applied to obtain an acceptably linear characteristic. Excellent amplifiers have been produced along these lines. Nevertheless, whereas feedback reduces distortion to a small and no doubt negligible amount, feed-forward carries the promise of reducing to zero the distortion of that part of the amplifier over which it is applied. If this is the class B stage, then not only does the distortion itself disappear but all the paraphernalia of quiescent current adjustment and thermal tracking disappears with it.

Feed-forward has only really flourished in areas where stability problems prohibit the use of feedback<sup>2</sup>. In the field of domestic audio amplifiers, it has failed to fire the imagination of all but a few<sup>3</sup>; presumably due to the extra complications and the undoubted practical problems of adding the error channel to the main 'stiff' output in an elegant manner.

If feed-forward is applied within the loop of a feedback amplifier, its stability advantage is necessarily forfeit. Nevertheless, in return, the need for a separate error amplifier can disappear and mutual loading problems disappear with it. A circuit developed on these lines carries an error component bypassing the main output transistors and so largely releasing them of linearity requirements. This technique has become known as 'current dumping' since this is descriptive of the rather mundane functions they are called upon to perform.

The basis of the new approach is shown in Fig. 1. Amplifier A is a small class A amplifier capable of providing the total required output voltage swing but with limited output current capability. Tr<sub>1</sub> and Tr<sub>2</sub> are current dumping transistors which supply the major part of the load current.

Fig. 1. Basic circuit parameters.

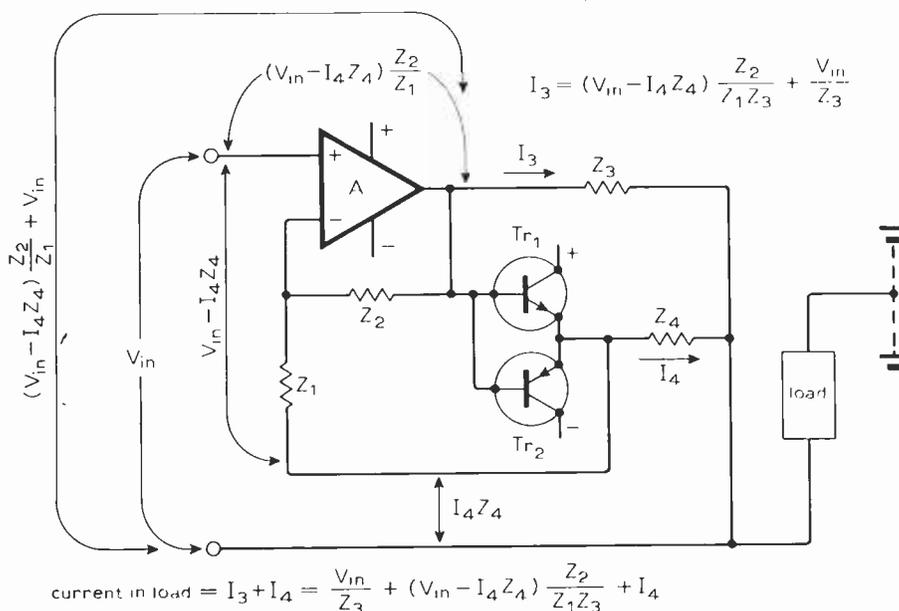

It will help in visualising the operation if the impedances are assumed to be resistors of values  $Z_1=1k\ \text{ohm}$ ;  $Z_2=100k\ \text{ohm}$ ;  $Z_3=100\ \text{ohm}$ ; and  $Z_4=1\ \text{ohm}$ . In the interest of simplicity we have assumed  $Z_4$  to be negligibly small compared to  $Z_1$ , and for the time being we will assume that the voltage output of amplifier A is completely defined by the external impedances.

With  $Tr_1$  and  $Tr_2$  turned off, amplifier A will deliver current to the load via  $Z_3$ . The current with the values suggested will be 1.01 amps/volt because the second term in the brackets is zero (no  $I_4$  current from the dumpers). When half a volt or thereabouts appears across  $Z_3$ , one or other of the dumpers  $Tr_1$  or  $Tr_2$  will begin to turn on and pass some current  $I_4$  into the load. We have selected resistor values such that  $Z_4Z_2/Z_1Z_3$  is unity so that the second term in the expression for the  $I_3$  current is exactly equal and opposite to  $I_4$  (this second term is the feed-forward error correction component). Currents  $I_3$  and  $I_4$  add in the load so that no matter what the magnitude of  $I_4$ , the overall mutual conductance remains constant. We can say that any distortion in  $Tr_1$  and  $Tr_2$  produces perturbations in the current  $I_4$  and since this causes the exactly equal and opposite perturbations in  $I_3$ , no distortion appears in the load.

$Tr_1$  and  $Tr_2$  have only one function to perform and that is to dump current into the load sufficiently accurately and sufficiently fast to come to the rescue of the class A amplifier and prevent it from overloading. If this is achieved then the class A amplifier, although it may have considerable gymnastics to perform, will be in complete control of the load current at all times.

Fig. 1 does not look like a practical hi-fi amplifier since its output is constant current and the input is floating relative to the power supply. Nevertheless it is obvious that if the input is returned to the other end of the load all the unique properties of Fig. 1 will still apply though perhaps a little less simple to visualise. This done, we have an amplifier whose output source impedance is  $Z_4$  and  $Z_3$  in parallel.

Two further changes are desirable. A practical amplifier is required to have an internal impedance small compared to the load at audio frequencies and stability requires that the internal loop gain falls with frequency. Both these conditions are met by the use of an inductor for  $Z_4$ , a capacitor for  $Z_2$  and resistors for  $Z_1$  and  $Z_3$ . The requirement for zero distortion from the dumpers is that  $Z_4Z_2/Z_1Z_3$  is unity at all frequencies of interest. This is achieved if  $L=RRC$ . Fig. 2 shows the circuit with the modifications carried out. (In order to keep the system operating at all frequencies it is necessary for a resistor in series with the inductor to have a conjugate match with a parallel resistor across the capacitor. This has been omitted for simplicity.)

Fig. 2 begins to look very familiar, in fact just like a conventional amplifier with the biasing removed and a small inductor added. Is this really all that is necessary to produce the perfect amplifier? The answer, of course, is no, not quite; the circuit is over-simplified. We have pushed all the problems back

into the class A stage and whilst the distortion would indeed be zero if the class A stage were perfect, this cannot be completely so in practice. We assumed in our analysis that amplifier A was completely controlled by the external impedances, that it had a perfect virtual earth at its input which implied perfect regulation at its output. The effect of departure from this ideal can be assessed by calculation from a deliberate unbalance of the four component bridge, whether this is due to tolerances of any of the components or to inadequate 'stiffness' at the output of amplifier A. With the values shown in Fig. 2, a 5% error in any component value will produce maximum intermodulation products of around  $5\mu\text{V}$  at 1kHz; maximum possible i.m. of 0.01%, the maximum absolute level of these components being some 140dB below full power. Although frequency dependent, it is clear that balance is by no means critical and standard tolerance fixed components can be used without adjusting facilities.

We have said that the dumpers have

Fig. 2. Basic diagram of principal elements.


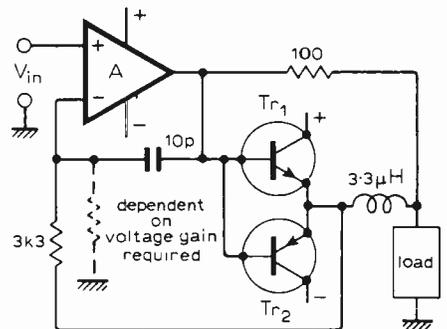


Fig. 3. Simplified diagram showing Class A stage, current dumpers and bridge components.

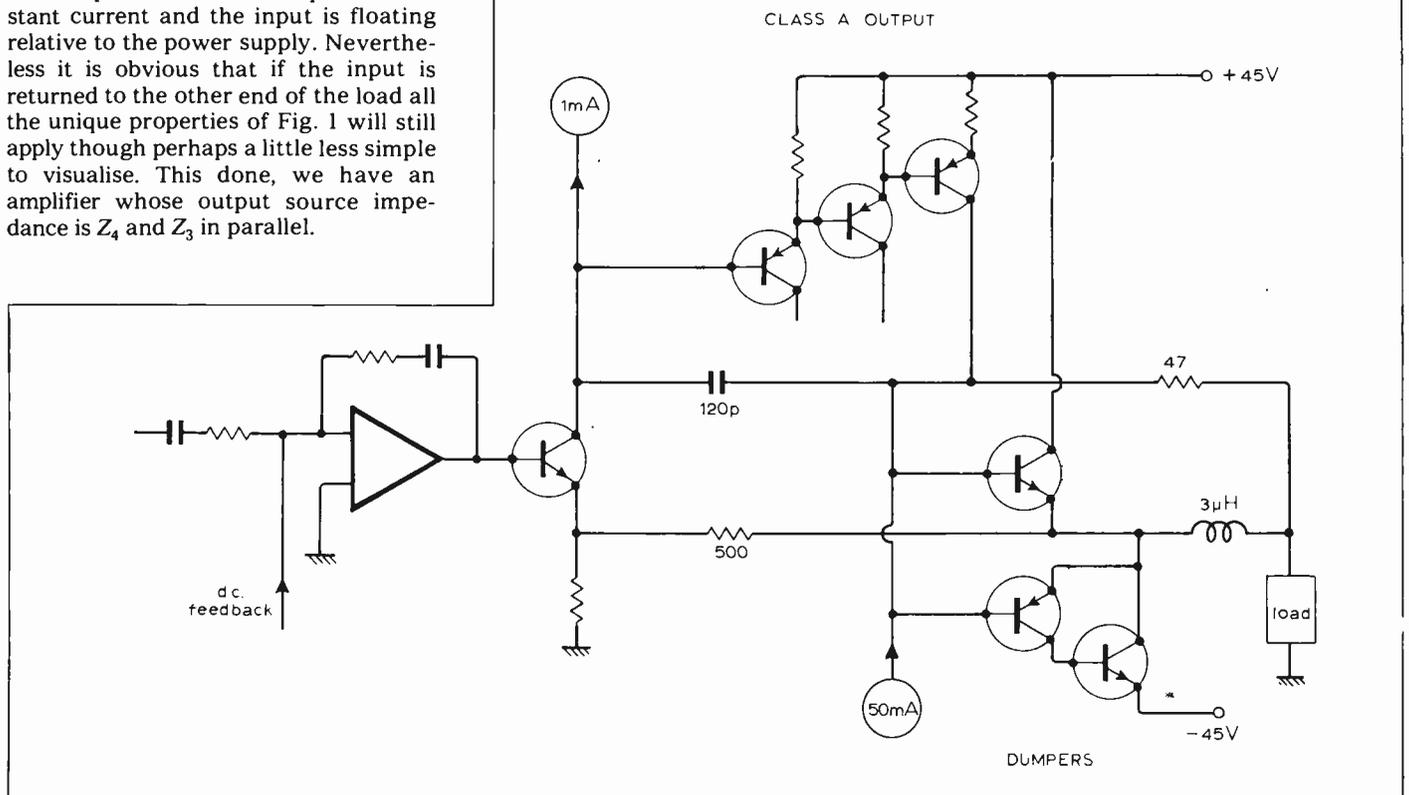

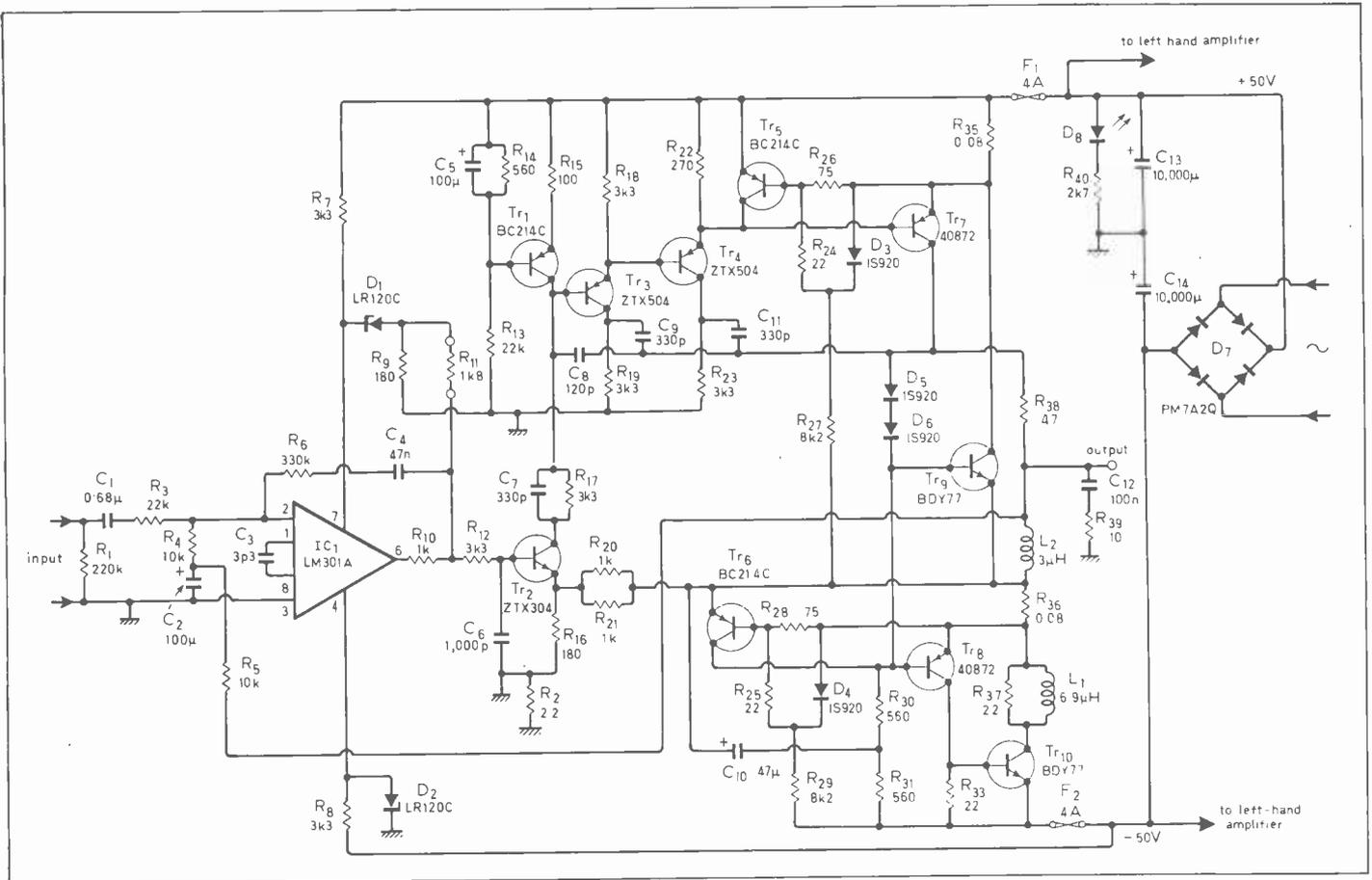


Fig. 4. Full circuit diagram. Resistor  $R_2$  is a protective connection provided to ensure earth continuity in the event that  $Tr_2$  and its associated component panel are disconnected from the common earth chassis.

Fig. 5. The Quad 405, a commercial realization of the circuit design.

to be sufficiently fast to come to the rescue of the class A amplifier to prevent its overloading. Clearly they must be sufficiently fast to achieve this over the audio spectrum of the programme. There is, however, nothing whatever to say that they must do so at frequencies outside the audio range provided that steps are taken in the design of the whole amplifier to ensure that any such frequencies that may be present do not embarrass the amplifier performance within the audio range. If the system is properly designed it is possible to use relatively slow devices – inherently more rugged than fast devices – and to show in theory and


practice that they will never fail to come to the rescue of the low powered amplifier to any programme. If, however, the criteria are thought to be response to step functions, square waves and other factors not relevant to programme, then of course faster dumpers must be used commensurate with the rise times involved.

Fig. 4 shows a commercial amplifier circuit (the Quad 405) developed along these lines, Fig. 3 being a simplified diagram to indicate the relevant areas. The class A amplifier serves also as the driver for the top dumper. To counter this extra burden, the class A amplifier is a triple to give a very effective virtual earth. The mid frequency distortion of this amplifier measures about 0.005%, a region where slight component non-linearities etc. tend to deprive such measurements of any true meaning.

An extremely attractive factor of the technique is the complete absence of adjustments or alignment requirements and no thermal problems. Nothing to set up in manufacture and nothing to go out of adjustment during life. One may expect that after several years there will be far less variation, set to set, than is presently realised with most conventional circuits.

**References**

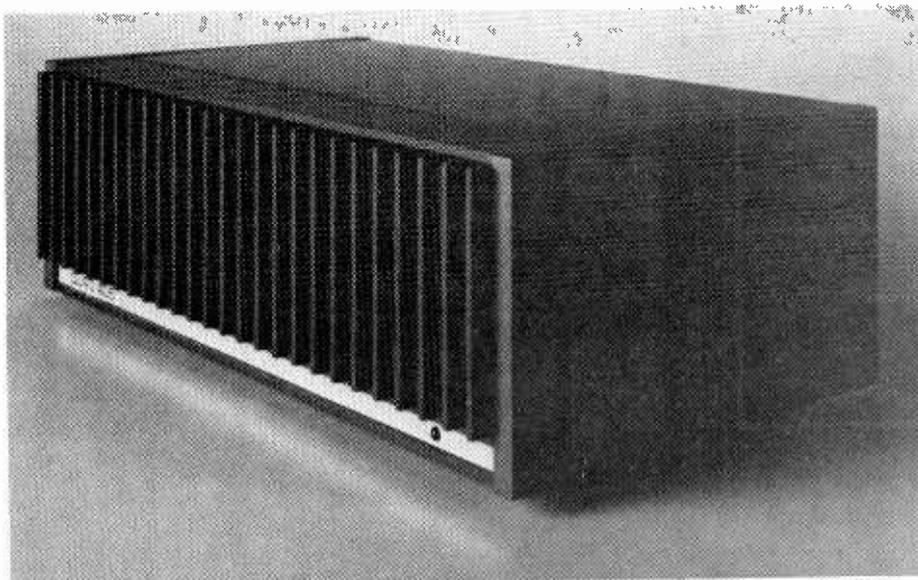
1. Black. US Pat. 1,686,792. 9th Oct. 1929.
2. Feedforward error control. *Wireless World*, May 1972, p.232.
3. Sandman, A. M. Reducing amplifier distortion. *Wireless World* October 1974, pp.367-371.



**For the first time someone's measured up to  
your real need in a measurement system...**


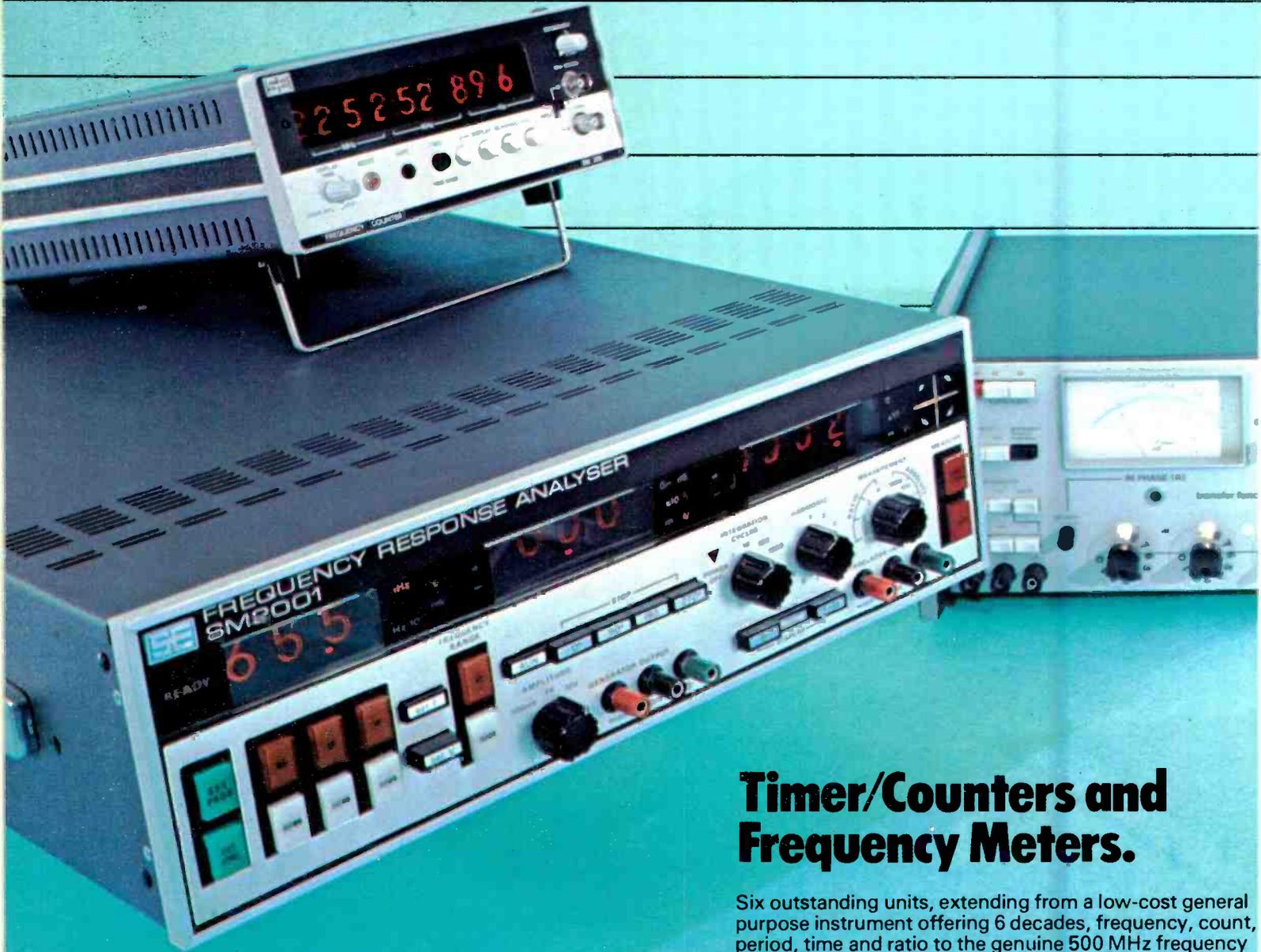
# True value as reflected in SE digital instruments



## Multimeters/Voltmeters.

SE provide a wide range of instruments, each one providing an outstanding price/performance package. The range includes the most versatile 5 1/2 decade, high performance multimeter available and runs up to the most accurate portable dc voltmeter in the world with true 0.001% three month stability *without* recalibration. Instruments in the range feature every facility you could require including autoranging, full programming capability, BCD and printer outputs, and stored display.

SE provide an economic solution to your measurement problem from this twelve instrument range. Send for our literature and find out more about SE value.

## Timer/Counters and Frequency Meters.

Six outstanding units, extending from a low-cost general purpose instrument offering 6 decades, frequency, count, period, time and ratio to the genuine 500 MHz frequency measurement in the SM 209.

The range also includes the fully automatic SM 205 and the SM 202M with every worthwhile feature to be found in a very high performance general purpose universal counter/timer, in a compact unit.

Find out more about SE instruments — value you can count on.

## Dynamic Analysis.

Our SM 2001 Digital Frequency Response Analyser has one competitor. Both equipments offer similar facilities. We're convinced that ours has the edge in performance and convenience. *It also costs some £1,500 less.* This is what value is all about—equating performance and convenience with cost. We also provide a range of complementary units to extend the range of usefulness of SM 2001, including frequency extension and modulator/demodulator units, plotter and computer interfaces. Exceptional value too is our SM 272 Transfer Function Analyser. Capable of processing all but the lowest frequencies, it provides a flexible reliable unit at very low cost indeed.

Find out more about Dynamic Analysis and more about SE instruments.

The SE range of digital instruments includes highly sophisticated devices for research and systems use as well as general purpose units for bench and portable operation.

Whatever your application, all SE instruments have the same premium to offer — GUARANTEED VALUE — the optimum interface between quality and price.

For you this means a range of instruments to meet your precise needs — instruments with a stated accuracy that is always attainable — at a sensible price. The SE range of

multimeter, voltmeter, counter/timer, and dynamic analysis instruments provides effective and economic solutions to a wide range of measurement problems.

Send for further information on specification and prices.



# ...with the first class service back-up you need.

SE provide a quick reacting service back-up that measures up fully to your requirements, through our calibration/ service centres at Feltham, Nottingham, Wells, Manchester and Glasgow.

Where on-site service is required a service engineer can visit anywhere in England, Wales and Scotland within 48 hours of your call. Overseas, SE companies and selected agents offer a similar capability.


When you buy SE instruments you get the right price/performance ratio, reliability, ease of operation and first-class after-sales service facility.

Oscillographs, Transducers, Signal Conditioning, Analogue & Digital Tape Recorders, Multimeters, Voltmeters, Counters, Dynamic Analysis, Modems, Medical Instrumentation.
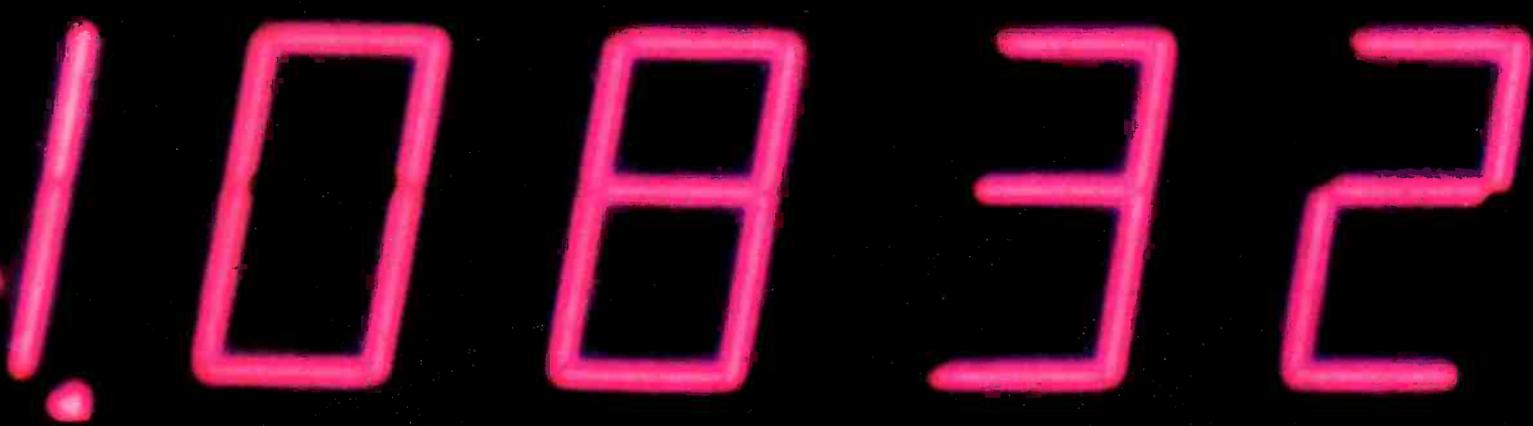
## EMI SE LABS

SE Labs (EMI) Ltd., Spur Road, Feltham, Middlesex TW14 0TD England.  
Telephone: 01-890 1166. Telex: 23995.

A member of the EMI Group of companies  
International leaders in music, electronics and leisure



Send coupon for details by return.

To: SE Labs (EMI) Ltd.,  
Spur Rd., Feltham, Middlesex. TW14 0TD.  
Telephone: 01-890 1166 Telex 23995.

- Please send me full details of:-
- Digital Multimeters/Voltmeters
  - Dynamic Analysis Capability
  - Timer/Counters, Frequency Meters
  - Instrument Hire Facilities
  - Please arrange for your applications engineer to contact me
  - Contract Service Agreements

Name/Title \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

Tel. No. \_\_\_\_\_ WW/A/1

### European Sales & Service

- Holland:** ANRU B. V., Wijnhaven 80, Rotterdam 1. Phone: 137-395  
Telex: 25175
- France:** Emitronics, 18, Rue des Bluets, 75011 Paris 11e. Phone: 357-58-45,  
357-58-46 Telex: OMITEL 68461 F ext. 196
- Belgium:** Régulation-Mesure S.P.R.L., Av R Vandendriessche 73, 1150  
Brussels Phone: 771-2020 Telex: 21520 Mereg-Brux
- Germany:** Kontron Elektronik GMBH, D8051 Eching, Postfach 105.  
Phone: (08165) 77-1 Telex: 05 26 719
- Italy:** Marconi Italiana, 20135 Milano, via Comelico 3  
Phone: 54-65-541/542/543 Telex: 32467  
and: Via Adige 39, 00198 Roma, Phone: 86 17 13, 86 33 41 Telex 61272
- Norway:** EMI Norsk A/S., Postboks 42, Korsvoll, Oslo 8. Phone: 23-14-88  
Telex 16294 EMIAS
- Sweden:** EMI (Sweden) Ltd., Svenska AB., Tritonvägen 17, Fack S-171, 19  
Solna 1. Phone: 08-730-0060 Telex: 10046

Also represented by EMI companies and agents throughout the world.

▶ Enquiry No. 295

Printed in England

# Wireless World Teletext decoder

## 2—The decoder system

by J. F. Daniels\*

**This article describes the facilities offered by the Wireless World decoder and also covers, in general terms, the methods of installation in a commercial colour receiver. The problems likely to be encountered with such a project are also discussed.**

When contemplating the design of a project as complex as this one, there are many factors which have to be considered. For instance, to build a single Teletext decoder with cost and size virtually no object and expensive test equipment available is comparatively easy, but this is of little interest to the home constructor. What is needed is something which can be built relatively cheaply, can be mounted in a small, attractive cabinet, and can be installed and made to work with only the minimum of adjustments, preferably requiring only a cheap multimeter.

This design will fulfil these requirements. This does assume, however, that the unit is constructed without any wiring errors and with no faulty components — in a unit using around '85 i.cs and their interconnexions, there is some room for error!

Not to be too discouraging at such an early stage, however, it should be pointed out that printed circuit boards will be made available, from normal sources, which should eliminate most wiring error problems. Further, digital i.cs tend to be very reliable, in my experience anyway, as long as they are not obtained from one of the sources of unmarked, untested devices. The use of such i.cs in this project must be strongly discouraged, as even if they appear satisfactory on a d.c. test, they may well be out of tolerance on delay time or fan-out, which could have disastrous effects in some parts of the circuit, where correct delay time through i.cs is an important factor.

For the constructor who has access to an oscilloscope, waveform diagrams will be given at various points in the circuit to help those wishing fully to understand the circuit operation.

It is not intended, in this series of articles, to give full constructional details, and the choice of suitable box, and method of mounting p.c.bs etc. is

left to the individual constructor. Details of how the unit may be connected into various types of commercial colour receiver will, however, be fully covered and this should leave only problems of a mechanical nature to the individual.

The cost of the decoder will be in the region of £85, and although this may seem a great deal of money to pay, people who have seen the resulting display of pages on the TV screen agree that the service is well worth while and has great potential for the future. The *Wireless World* decoder will be capable of utilising most of the features currently offered by the system, including display in six colours and white, alphanumeric characters, graphic characters, and flashing display. Two circuit options will be described; one which includes both upper and lower case characters, and another, slightly simpler circuit, with upper case characters only — a worthwhile option for cost conscious constructors. The circuit does not include any form of interpolation (character rounding) because it was thought that the extra cost of about £15-20 was not justified in a discrete-component decoder of this type.


Before going on to describe some problems, which can be encountered when dealing with commercial TV receivers, it is necessary to describe in more detail the performance of the Teletext decoder.

### Operation

The decoder can be built into a box measuring about 8.5×10.5×2in, which is a convenient size to rest on top of a normal domestic TV receiver. The power supply is not included in this box for a number of reasons, some electrical, but mainly to keep down the size and heat dissipation in the decoder unit. Space can usually be found in the cabinet of most domestic TV receivers to take the decoder power supply.

The front panel of the decoder carries two sets of thumbwheel switches, and various other function switches. In the latest version, the function switches take the form of a row of pushbuttons as shown in Fig. 1. The bank of three thumbwheel switches are for magazine and page number selection, the one on the left being for magazine number; the other two for page number tens and units. The bank of four thumbwheel switches are for the selection of timed pages, which may only be transmitted for a one-minute period during each day, and therefore require selection by means of time code and storing, for viewing later. The switches can be set to any given time during a 24-hour period, and in this mode of operation a page will only be written into the store at the time shown on the thumbwheel switches. It should be pointed out here that at the time of writing, no pages are being transmitted in this manner, although the operation of the circuitry can easily be checked, because all pages carry time coding information. However, a cost saving of the order of £6 could be made by omitting this facility.

Fig. 1. Suggested front panel layout of the *Wireless World Teletext decoder*.

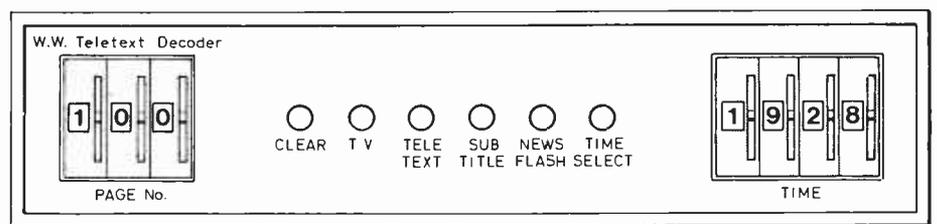

\*Designer of the Teletext decoder

The row of pushbutton switches mainly controls the form of display on the TV screen. The four in the centre are all interlocked, latching pushbuttons, the one of the left is an individually-operating, momentary-action type and the right-hand one is individually latching. The "TV" button merely selects the picture on the screen in the normal manner, although the decoder will still be operative and can store pages in the usual way, ready for instant viewing when the "Teletext" button is pushed. The latter merely replaces the picture with the video output of the decoder and, in this mode, all the normal features of Teletext display are available.

The page header contains a continuously changing time indication in the top right-hand corner, but a fixed page number display — the number of the page selected. When a different page is required on the display, the momentary-action, left-hand button marked "clear" is pushed. This clears all the information from the display except for the page header row, which then starts "rotating" i.e., reading out all the page headers as they are transmitted until the new page number selected is reached, whereupon the new page is read out into the screen.

The next button is marked "subtitle" and is used to select the "insert" mode of operation. When this button is selected, the TV picture is displayed on the screen until the subtitle page, the number of which has been selected on the thumbwheel switches, is detected, when the subtitle message will be read out in a box inserted in the picture. If a new subtitle, or indeed a continuous stream of different subtitles is trans-

mitted, the displayed subtitles will automatically change as they are transmitted. This may be a very useful facility for the future, as subtitles take up very little transmission time in the Teletext waveform, consisting of only a few rows of information. However, at the present time they are only transmitted in test form.

The operation of the "newsflash" button is somewhat similar to the subtitle button, but with an added facility. After selecting the newsflash page number on the thumbwheel switches, the current newsflash — which may have first been transmitted some time ago — is displayed in a box in the TV picture in the normal manner. If, however, the clear button is then pushed, the picture returns to normal, and no data are then displayed until a new newsflash is transmitted, whereupon this is displayed in the usual way in its box. If the current newsflash is required to be seen again, after pushing the clear button, the newsflash button is simply released and reselected.

The next button, marked "time" brings the time-select thumbwheel switches into operation, when the selected page will only be written into the decoder store during the one-minute period displayed on the thumbwheel switches. This page will then be held in the store until either the clear button is depressed or a different mode of operation is selected. This button is not

interlocked with the other buttons so that time-selected pages can be written into the store while watching a TV programme — possibly for later reading during the commercials! The time selection facility is not operative when subtitle or newsflash buttons are selected.

No facility is provided for superimposing the complete Teletext display on the picture, as in the author's opinion this gives a meaningless display which makes both the picture and the Teletext display difficult to interpret.

These, then, are the basic facilities offered by the *Wireless World* decoder. Without doubt, as the Teletext system progresses, more facilities will be offered by the service, and it should not be difficult to add extra facilities to the decoder as required.


### Installation

There is really only one satisfactory way to connect the decoder to a domestic colour receiver if all the facilities described earlier are required, and this is shown in Fig. 2. It can be seen from the diagram that there are only four points of connexion into the set: a feed of composite video from the output of the receiver i.f. strip, and feeds of red, green and blue (or possible R-Y, G-Y and B-Y) to and from the inputs to the receiver video amplifiers. It is possible that a fifth connexion, from the set's flywheel oscillator, will be required if the set is in use in a low signal area and displays a noisy picture, as this can be used to remove horizontal jitter on the Teletext display caused by the noise on the video signal. However, this possibility will be considered later during the circuit description.

The interface board is a small video switch unit, mounted inside the receiver, fairly close to the video amplifiers, and serves to switch electronically between the picture and the Teletext display, when commanded by either the function switches, or by "hole-cutting information from the decoder. The design of this unit will vary slightly, depending on the type of receiver used, some sets having, R, G and B feeds to the video amplifiers and others using colour difference signals (R-Y, G-Y and B-Y). If the facility of putting newsflashes and subtitles in boxes is not required, then this unit could probably be replaced by a three pole change-over relay, controlled solely by the function switches.

This, then, is the only practical way in which a decoder can be installed into an existing TV set, if a coloured display is required and this is the only method that will be described in detail in this series of articles. However, for those who rent a colour set, there is another, somewhat less attractive possibility, shown in Fig. 3. Here, a separate tuner and i.f. strip are used to provide video for the Teletext decoder. The R, G and B outputs of the decoder are then matrixed together, and fed to a u.h.f.

Fig. 2. Suggested method of connexion into a domestic colour receiver, using an interface board containing three simple electronic video switches.

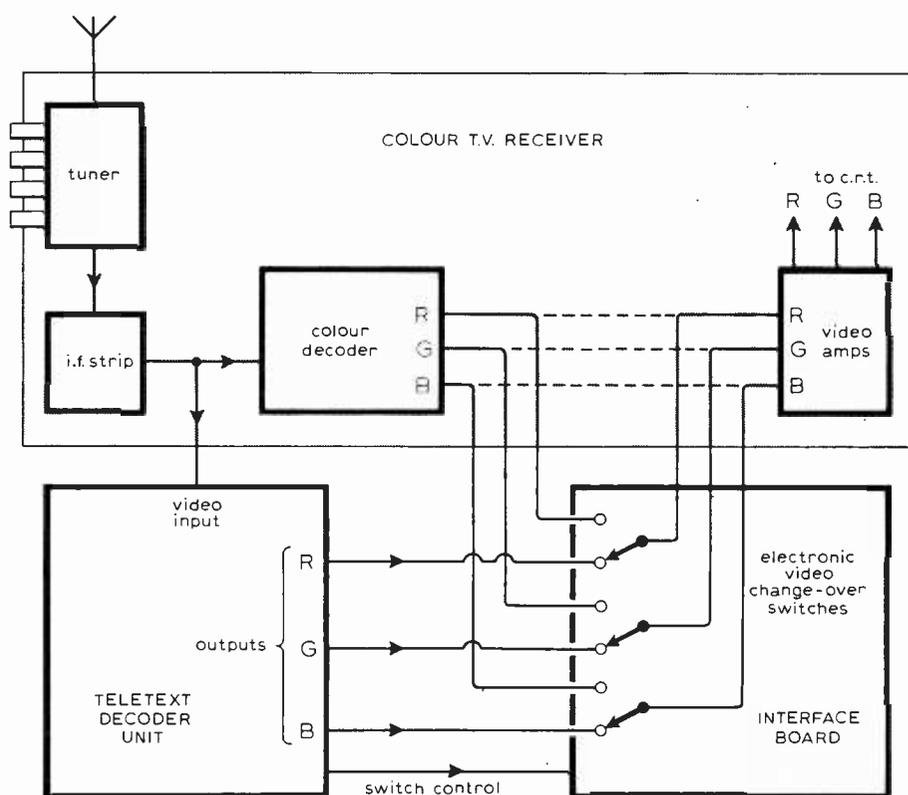

modulator. This in turn feeds the aerial socket of the receiver, which is tuned in to the modulator on an unused channel. This will, of course, only give a monochrome display, but would at least have different shades of grey to represent different transmitted colours.

It is not practical to modulate the decoder display into PAL colour form, partly because of the high cost of a colour coder, but mainly because the results would be unsatisfactory due to the fact that the bandwidth of the PAL system would be insufficient to cope with the Teletext display waveform.

### Data signal

Before starting a description of the decoder block diagram, there are two more important points to be made to prospective constructors. Firstly, there is the question of obtaining a suitably undistorted data signal from the TV receiver.

Distortion of the data waveform can be caused in a number of ways; poor bandwidth or non-linear phase response in the receiver i.f. strip; reflections (ghosting) on the picture, caused either by external multipath interference or aerial mismatching; co-channel interference; and finally noise. All these can cause errors to be made in the data display and, in extreme cases, prevent operation of the decoder at all.

Generally speaking, however, satisfactory results can be expected from the majority of colour sets displaying a ghost-free picture. Noise on the picture, unless of sufficient amplitude to be objectionable, is unlikely to be a problem, as the decoder employs circuits capable of detection and correction of errors caused by noise spikes.

Secondly, the performance of the decoder in the presence of interference in various forms is determined almost solely by the performance of the front end, i.e., the circuitry which separates the data from the video waveform, and converts it into t.t.l.-compatible form. It is proposed to describe first a fairly simple data separator, which is extremely easy to set up and which will be adequate under good reception conditions. This will enable the rest of the digital circuitry to be tested and set up. In a later article a more complex form of data separator will be described which will give an improved performance under adverse signal conditions although it will be rather more difficult to set up initially.

### Safety

The most important problem of all is one of safety. If the decoder is to be installed in the manner to be described rather than by using a u.h.f. modulator, as mentioned earlier, then a direct connexion must be made to the receiver chassis, which could under some circumstances be live.

There is only one way to prevent the decoder itself from becoming live, and that is to use a mains isolating trans-

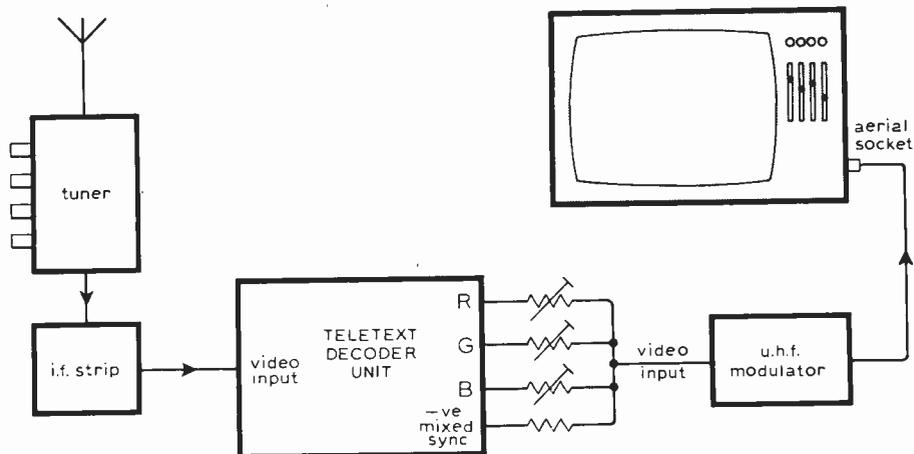


Fig. 3. Alternative arrangements for rented television sets. This has the disadvantage that only a black and white display will be obtained.

former in the mains supply to the TV receiver, and I would strongly recommend this course of action for anyone who does not regularly work with live equipment. If, however, the constructor feels absolutely confident that he can carry out the installation without electrocuting himself, then there are two important points to note. The first is to ensure that the receiver chassis is connected to the neutral side of the mains and not the live — this should be a simple matter of connecting the plug the correct way round but it must be checked with a multimeter. The second is to make sure that the decoder cabinet (if made of metal) or any metallic parts on it such as switches, etc. are not connected to the decoder electrical earth.

A three core mains lead must be used, with the earth connexion taken to the decoder cabinet, if this is made of metal. Probably the best solution, though, is to use a wooden cabinet and ensure that the thumbwheel switches and pushbutton switches are suitably insulated from their electrical contacts. The earth connexion should only be made after the decoder has been tested and set up, as it could create a hazard while actually working on the decoder. Of course, after testing is finished, when the earth is connected, protection is ensured against the decoder box becoming live due to faulty insulation.

### Construction

Prototype decoders were constructed on  $12 \times 7$ in pieces of ordinary Veroboard 0.1in matrix sheets. There is no reason why this method of construction should not be used, apart from the fact that it is very laborious, and wiring errors can easily be made.

For those who have less time to spare, printed circuits will be available in the form of two large p.c.bs for the digital circuitry, and a smaller p.c.b. for the analogue circuits. The overall size of the

unit has been kept down by splitting up the boards in this way.

The large boards measure  $9\frac{1}{2} \times 5\frac{1}{2}$ in., and are arranged to mount one above the other, spaced about  $\frac{1}{2}$ in apart. The analogue board measures  $5\frac{1}{2} \times 3$ in and is spaced  $\frac{1}{2}$ in above the digital boards. This gives an overall size for the decoder electronics of about  $9\frac{1}{2} \times 5\frac{1}{2} \times 1\frac{1}{2}$ in. The digital boards, which each hold about 40 i.c.s, are double sided, but for cheapness do not have plated-through holes. The "plating through" process is carried out by the constructor, using tinned copper wire soldered on both sides of the board.

This simplified block diagram in Fig. 4 shows the main functions contained in the decoder, only the main data paths being shown for simplicity. The heart of the circuit is contained in the clock and line divider blocks, and there are many waveforms from these sources which are distributed to the rest of the circuit blocks. This initial description is only intended as a guide to circuit operation, so that an overall picture can be obtained, before starting a detailed description of each circuit block.

The function of the analogue board is to take the composite wide-band video signal from the receiver i.f. strip, and produce from it t.t.l.-compatible mixed syncs, data, and clock waveforms. The single clock line includes the outputs of two clock generators, one derived from the incoming data, and another free-running oscillator used during the display time. Switching between the oscillators is achieved by using a waveform from the line divider circuits, which switches from the display oscillator to the "data locked" oscillator during part of the field blanking interval (between lines 10 and 20). The free-running oscillator has a preset frequency adjustment which controls the width of the Teletext display, and is also triggered by a line blanking waveform to ensure that it starts up in the same phase at the start of each television line.

Clock and data waveforms from the analogue board are fed to the serial-to-parallel converter, which in turn feeds the data latches and the framing-code detector. The output of the framing code detector is used to reset the clock

dividers, and a +8 clock waveform is in turn used to operate the data latches.

It should be explained at this point that the clock and line dividers perform the dual role of data acquisition and data display dividers, and this constitutes quite a saving in circuit components.

Bits 1-7 from the data latches are fed straight to the inputs of the data store, while all eight bits are fed to the parity checker and Hamming-code corrector. The output of the Hamming corrector consists of bits 2, 4, 6 and 8, suitably corrected in the case of a single error, and also an output which indicates an even number of errors. If an even error is detected during a row address group, then the even error output of the Hamming corrector is used to inhibit any data from being written into the store on this row.

Bits 2, 4, 6 and 8 from the Hamming corrector are fed to the row and page recognition circuitry, and also to the line divider circuits. The line divider circuits count line syncs during the display period, but when data lines are detected during field blanking, the counters are preset to the correct row number, indicated by the Hamming-corrected bits. The five-bit row-address output of the line dividers is fed, together with the six-bit column-ad-

dress output of the clock dividers, to the code convertor circuit. ("Column address" refers to the 40 vertical character columns and "row address" to the 24 horizontal character rows.)

The divider circuits are both arranged so that the data on these eleven wires is correct during both data acquisition and data display, and this obviates the necessity of complicated switching in the address inputs to the store. The code convertor is required for the following reason: the 1024-bit random-access memories are arranged in a  $32 \times 32$  matrix which can, of course, be addressed in any of its store positions by a 10-bit address input. Our display matrix, though, is arranged in a  $40 \times 24$  pattern as previously described, and this requires an 11-bit (6 + 5) code to address each individual position. However, there are many unused positions which can be addressed by the 11-bit code and by a suitable rearrangement of the addresses, the 11-bit code can be reduced to 10 bits, without actually losing any of the  $40 \times 24$  matrix positions. A simple calculation showing that 40 multiplied by 24 comes to less than 1024 indicates this possibility.


Fig. 4. Teletext decoder simplified block schematic.

The data store consists of seven 1024-bit random-access memories, addressed in parallel — one for each of the seven bits of data. The other input to the store is the read/write input. This input is normally in the read condition, when data already in the store is read out onto the screen, but changes to the write condition during Teletext data lines 17 and 18, when instructed to do so by the read/write control logic.

The seven-bit output of the data store is fed in parallel to three circuit blocks, as shown. Alphanumeric characters and graphic characters are generated for each of the 960 display positions on the screen. The control codes decoder decides which will actually be displayed, what colour it should be, and whether or not it ought to be flashing or boxed. It does this by suitable switching in the output control unit, which also blanks control characters.

This, then, is a necessarily brief introduction to the *Wireless World* Teletext decoder. In the following articles, detailed descriptions of each of the circuit blocks will be given, with waveform diagrams and explanations where these are relevant. Finally, circuits will be given for various types of "interface" board.

(To be continued)

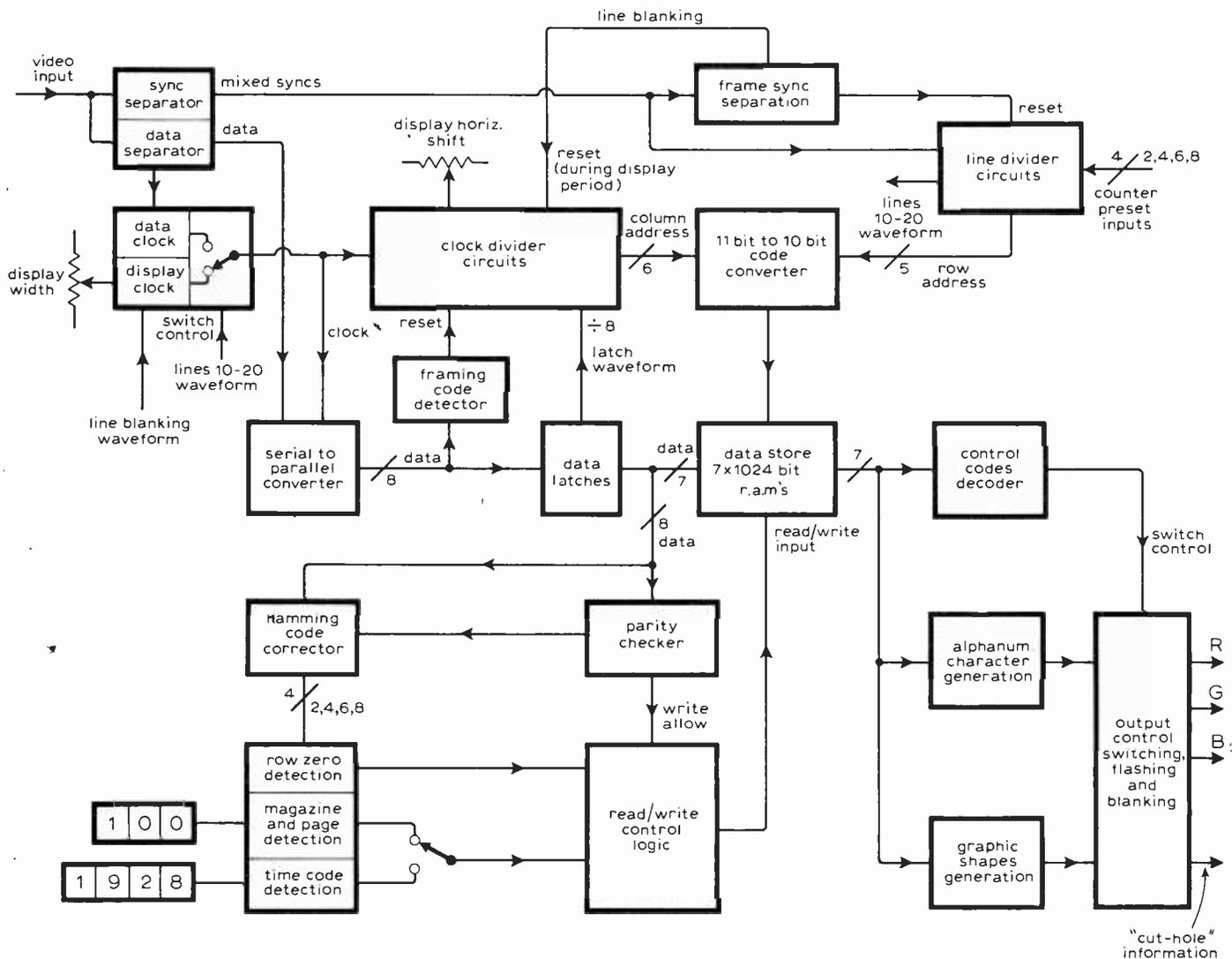

# Applying "magnetic Ohm's law" to permanent magnets

by P. E. K. Donaldson  
Medical Research Council

The entertaining article last year by M. G. Scroggie in which he replaces the notion of e.m.f. by a counter electric field ("What is e.m.f.?", August 1974 issue) reminded me forcibly of another area in which a motive force is inclined to be consigned to limbo: the application of the "magnetic Ohm's law" to magnetic circuits excited by a permanent magnet. The textbooks follow a well-worn path in defining magnetomotive force as the line integral of a magnetizing force, but then press quickly on to consider a magnetic circuit excited by a coil carrying a current, developing the familiar relation

$$\text{flux} = \frac{\text{m.m.f.}}{\text{total circuit reluctance}}$$

which parallels neatly the even more familiar

$$\text{current} = \frac{\text{e.m.f.}}{\text{total circuit resistance}}$$

perhaps leaving the student with the notion that m.m.f. is something made only by a coil carrying a current.

What does happen to a magnetic circuit if the electromagnet is replaced by a permanent magnet? Is the "magnetic Ohm's law" model still relevant? The textbooks are maddeningly inexplicit on this point, but seem in general to abandon the notion, switching abruptly to an "ad hoc" graphical solution to find the flux in the permanent magnet case. "Cathode Ray" (*Wireless World*, February 1973) evidently believes in m.m.f. for permanent magnets, but uses the graphical solution. Another author<sup>1</sup> states clearly that, in the absence of a wound coil, "the m.m.f. in the circuit is zero," and concludes that a flux is able to exist because the reluctance of the permanent magnet is negative. Now this is perfectly legitimate; it is analogous to looking at the terminals of the dotted box in Fig. 1 and concluding that, since there is a p.d. of 1.4V between them, and a current of 0.1A flowing in at the negative terminal and out at the positive, the box must contain a resistance of -14 ohms. But I feel sure it is more useful to think of a real cell as an e.m.f. in series with an internal (positive) resistance, and would like to suggest, in the magnetic case, that it is useful to think of a real permanent magnet as a m.m.f. in series with an internal (positive) reluctance.

Choosing a ceramic magnetic material for the conveniently constant reluctance such materials have, we find for Mullard<sup>2</sup> Magnadur 1 that the B-H curve cuts the B=0 axis at  $H = -140 \times 10^3$  ampere turns/metre, the H=0 axis at  $B = 210$  milliwebers/metre<sup>2</sup> and is straight between. Plotting this data for a magnet of length  $l = 3$  cm and a cross-section  $A = 4$  cm<sup>2</sup> gives us Fig. 2. If the magnet were to be immersed in a very highly reluctant medium, there can be no flux,  $\phi = 0$ , so the working point is  $\alpha$ . Because there is no flux, the "open circuit" magnetic potential difference will give the m.m.f.; in this case  $4.2 \times 10^7$  ampere-turns. If the magnet were immersed in a very high- $\mu$  (low-reluctance) medium, the magnet would be short-circuited, there can be no magnetic potential difference, the working point is  $\beta$  and the short-circuit flux is  $8.4 \times 10^{-5}$  webers. The internal reluctance (cf. Fig. 1) is given by

$$\frac{\text{open-circuit m.m.f.}}{\text{short-circuit flux}} = 5 \times 10^7 \frac{\text{ampere-turns}}{\text{weber}}$$

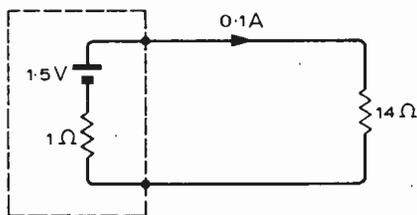


Fig. 1 Electrical circuit analogy for a permanent magnet with negative reluctance: the box can be said to contain a resistance of -14 ohms.

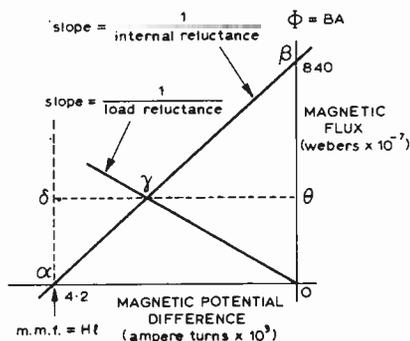


Fig. 2 Plot of magnetic flux against magnetic potential difference for a ceramic magnetic material.

These two quantities, m.m.f. and internal reluctance, entirely characterize the magnet.

In general the working point will be between  $\alpha$  and  $\beta$ , at some point  $\gamma$ , where  $O\gamma$  is a load line representing the reluctance of the air-gap, pole pieces etc.:

$$\frac{l_1}{A_1 \mu_1} + \frac{l_2}{A_2 \mu_2} \dots \dots$$

The flux is given by

$$\frac{\text{m.m.f.}}{\text{load reluctance} + \text{internal reluctance}} = \frac{4.2 \times 10^7 \text{ ampere-turns}}{\frac{l_1}{A_1 \mu_1} + \frac{l_2}{A_2 \mu_2} \dots + 5 \times 10^7 \frac{\text{ampere-turns}}{\text{weber}}}$$

If the only significant load is an air gap 0.5 cm long and of cross-section 1 cm<sup>2</sup>, then its reluctance is

$$\frac{l}{A \mu_0} = \frac{0.5 \times 10^{-2}}{10^{-4} \times 4\pi \times 10^{-7}} = \frac{1.25}{\pi} \times 10^8 = 4 \times 10^7 \frac{\text{ampere-turns}}{\text{weber}}$$

and the flux is

$$\frac{4.2 \times 10^7}{4 \times 10^7 + 5 \times 10^7} = 4.7 \times 10^{-5} \text{ weber}$$

or 4,700 "lines" or maxwells.

The distance  $\delta\gamma$  is the magnetic potential dropped in the internal reluctance of the magnet, leaving  $\gamma\theta$  available for pushing flux through the external load. When the load reluctance is equal to the internal reluctance,  $\gamma$  bisects  $\alpha\beta$  and the product  $HLBA$  is maximal. For a given magnet, that is,  $lA$  fixed, we have therefore the well-known  $(BH)_{\text{max}}$  condition ("Cathode Ray," *Wireless World*, February 1973, p. 73) for optimum use of the magnetic material. We see that the condition corresponds to conditions for maximum power transfer in the analogous electrical case.

It seems that some useful insights are to be had by pushing the "magnetic Ohm's law" notion into the realm of permanent magnetism. Is there a catch to it, or have I been looking in the wrong books? Oh, and let nobody say that the graphical solution, rather than the simple Ohm's law solution, is necessitated by the fact that, for many permanent magnet materials, the reluctance is not very constant, but is a function of  $H$  (or  $B$ ). The  $\beta$  of a bipolar transistor is not very constant either, being a function of  $I_c$ . But the concept of  $\beta$  is far too useful to be discarded on that account. And so, it seems to me, are the m.m.f. and internal reluctance of a permanent magnet.

**References**

1. Bennet, G. A. G., *Electricity & Modern Physics*, Edward Arnold, 1971.
2. Mullard Ltd data sheet, *Permanent Magnets*, March 1971.

# Letters to the Editor

---

## TELEVISION TUNER DESIGN

---

I am writing to advise you and forewarn potential constructors of D. C. Read's television tuner (Oct., Nov., Dec.) that the design, as shown, with the Mullard ELC1043 varicap tuner, will not be suitable for use in those areas served by group C/D or E transmitters. The tuning voltage is derived from an 11V line and therefore the varicap tuner cannot be tuned above channel 50, some 24V being required to reach channel 68. Indeed, the values shown for resistors  $R_{89}$  to  $R_{97}$  inclusive preclude the tuner from being used even on group B, for the potentiometers  $R_{90}$ ,  $R_{93}$  and  $R_{96}$  will allow channels 21 to 26, 23 to 29, and 33 to 40, respectively, to be tuned. These will be satisfactory for the Crystal Palace transmissions but different component values may be required for some group A or any group B transmitters. A mechanical tuner will be required if coverage of the whole u.h.f. television spectrum is required.

It would also be helpful if Mr Read could advise which version of the ELC1043 is required, as there have been six versions: the two models in current production, the ELC1043/05 and ELC1043/06, have differing i.f. coil arrangements which may require alteration to the matching components  $C_5$  and  $R_3$  to optimise the response shape. I am also advised that early versions of the ELC1043, as are currently available from many discount dealers, had an i.f. output which was not isolated from the 12V supply, which might result in  $R_3$  expiring along with the i.f. coil in the tuner.

P. A. Moore,  
London E3.

### Mr Read replies:

I am indebted to Mr Moore for his timely reminder that television channel numbers and radiated frequencies in use move ever upward towards the limit of Band V and that some changes (even additions) to the tuner circuit published in Part 1 of the article would be

necessary to receive signals from the newer transmitters. To allay Mr Moore's possible suspicion that we who live in the shadow of the Crystal Palace transmitter had forgotten everyone else, I refer him to steps 2 and 11a of the line-up procedure in Part 4 which deal with this aspect of construction, specifically relating it to a curve (Fig. 21) showing tuning voltage against channel numbers/frequencies for the ELC1043 and ELC 1043/05 modules. Re-stated briefly, the point is made that the published circuit will enable reception up to channel 50; for channels 51 to 68 one or two extra zener diodes are needed in the  $Tr_{20}$  collector circuit to provide up to 22.5 V for the tuning supply.

At the time of writing it seems that channel 69 is being reserved for the "Fourth Programme" transmissions ready for when (and if) the Government decides on allocation. The highest-numbered channel at present in use is 67, which is allocated to the IBA transmitter at Henley. In the event that a tuner is required to receive channel 67, and also happens to have an ELC1043 or an ELC1043/05 version with a characteristic at the top of the manufacturer's quoted spread (see Fig. 21), the necessary extra tuning voltage — perhaps 25V — could be obtained by bypassing the MC7824CP ( $IC_3$ ) regulator and driving the  $Tr_{19}/Tr_{20}$  circuit directly from the 30V rail, using an extra zener diode.

Regarding the specific version of the tuner module to be used, I am similarly grateful for the information from Mr Moore, particularly his point about the lack of i.f. output isolation on early models; I had not previously heard of this. In reply, it is simply necessary to say that: (i) as indicated in the parts list (Part 3), the u.h.f. module fitted to the prototype tuners was coded ELC1043, i.e. *without* suffix numbers; the ELC1043/05 version should be suitable but has yet to be tried; and (ii) if one of the early un-isolated u.h.f. tuners is to be used, the only modification required will be to break the copper track leading from the i.f. output roundel on the board and to bridge the break with a small disc ceramic capacitor (e.g. 2.2nF).

---

## AUDIO AMPLIFIER LOAD SPECIFICATION

---

Since amplifier specifications rarely call for any "wattless" output capability and since loudspeakers are not required to reflect a purely resistive load, it is not surprising that some amplifiers of excellent paper specification fail to live up to their promise when auditioned.

The situation has deteriorated in recent years because of the indiscriminate use of voltage-dependent current limiting.  $V-I$  limiting restricts the amplifier's ability to cope with the

reactive component of the load but it does enable faster output transistors to be safely used, with the implied assumption of a "better" specification.

I would like to suggest that a power amplifier must be capable of providing its full output *voltage* without exceeding its specified distortion when loaded by  $R \pm jX$ , where  $R$  is the rated load for which the amplifier is designed and  $X$  is any value from zero to several times  $R$ .

In practice only a single additional measurement is really necessary. Set up the amplifier in the usual way to measure power output and distortion just below clipping into the resistive load  $R$ . Then, without changing the input level, a reactance equal to  $R$  at the frequency of measurement is added in series with the  $R$ . The distortion at the amplifier output terminals should not increase.

The choice of  $R \pm jX$  seems to me a reasonable compromise because it is the form of the load of any single moving-coil speaker and it is very representative of the load imposed by the majority of loudspeaker systems. It allows a sensible degree of  $V-I$  limiting in the amplifier. (Constant voltage to  $R \pm jX$  implies that the amplifier shall be able to deliver half peak current at zero volts.)

There are a few loudspeakers (our ESL is one) which place a more severe load on the amplifier than their rated impedance implies. However, the prudent loudspeaker designer will only allow this to happen in areas of the frequency band where full power is unlikely to occur on programme.

Meeting the requirement outlined in this letter is no real hardship for amplifier or loudspeaker designer and can result in nothing but better sound for the listener.

P. J. Walker,  
Acoustical Mfg. Co. Ltd.,  
Huntingdon.

*The following is an invited response to Mr Walker's letter. Other invited comments will be published later.*

I applaud Mr Walker's letter as a useful and correct attempt to arrive at a standard to be agreed and achieved by loudspeaker and power amplifier designers. As a target the notion of a load  $R \pm jX$  where the magnitude of  $X$  varies from 0 to  $\infty$  is suitable.

However, in the present world loudspeakers tend not to be so well behaved and the amplifier designer is obliged to consider more stringent loads. I would suggest that a power amplifier of rated load impedance  $R$  ohms should maintain its performance into loads of  $R/2$  and  $R/jX$ , i.e.  $(jR-X)/XR$ . This requires, of course, twice the resistive load current and a zero voltage current sink of rated peak current. This is not of course an ideal state of affairs and is only necessary because monitor quality loudspeakers are not designed to Mr Walker's suggested impedance limits

and do not always exhibit the defects outside the speech band.

In the second paragraph of his letter it is suggested that  $V-I$  limiting is a device for enabling fast transistors to be used with reduced reactive power capability. There is an economic factor not made clear; there is no reason for  $V-I$  limiting, particularly delayed limiting, to deteriorate the performance of the power amplifier, nor is there any reason why this should preclude the use of fast or slow devices. All that is important is the time nature of the  $V-I$  limiting and the  $V-I$  co-ordinates used, bearing in mind the loads already discussed. Of course, faster transistors e.g. triple-diffused devices, may need to be used in larger numbers and because they are already more expensive than the rugged single diffused or epi-base parts a given  $V-I$  characteristic will cost more with the faster part. Whether or not this actually improves the specification or the performance is too dependent on the circuit and too complicated to discuss here.

How do we propose to achieve this standard?

J. R. Stuart,  
Boothroyd/Stuart and Partners,  
Cambridge.

---

## ANALOGUE vs DIGITAL READOUT

---

Your editorial on analogue versus digital measuring instruments in the July issue strikes a chord in my thought which I should like to express. My home laboratory has only analogue meters for d.c. and low frequency a.c.; and with 1-2% or 3-4% moving iron types for a.c., and a few 1% d.c. meters, I try to stay that close to true voltages and currents over a fairly wide range. Every five years or so I purchase a (British-made) standard cell and check over my d.c. instruments, assisted by a Wheatstone bridge and sufficient precision resistors to set up a potentiometer. But I am not unaware of the relatively-phenomenal accuracies of the digital multimeters available for a few hundred dollars; in fact, I read all the advertisements, wondering when I will jump that way. What stops me is their evident limited life at their initial accuracy, unless re-calibrated. Decades pass, and my analogue meters (when properly treated) continue to live up to the standard cell checks and other means of calibration I am able to borrow.

What use would it be to me to have a meter that would display impressive rows of digits, when after a year or so it may have drifted way beyond my modest, but dependable, 1%, and thereby require re-calibration to a degree of accuracy entirely out of reach of the home laboratory, budget-wise? And I am not at all anti-digital; my "upstairs" scientific calculator uses reverse Polish logic, while my "downstairs" ditto

employs algebraic logic with two pairs of nested parentheses. I could hardly be happy without both of them, technically speaking. I would be interested to hear comments from experts on digital multimeters which might help to resolve my doubts.

F. A. B. Smith,  
Washington DC,  
USA.

---

## CONTROLLING STAGE LIGHTING

---

I have read with very great interest the letter from Paul M. Hodgson in the October issue on the amateur's problem in using triacs for stage lighting. The points he made on using triacs with T class lamps were extremely relevant and enlightening. However, he is misinformed on the point that these triacs are not available on the British market.

Allen Bennett components Ltd (Orgrave Crescent, Sheffield S13 9NR) supply a range of triacs up to 50 amps r.m.s. on-state current which are extremely reliable and at a price between £5 and £10 each. I have approached the company and have received the assurance that if any bona fide amateur group who are building their own stage lighting equipment would write to the company they are prepared to supply these triacs at a much reduced price.

C. D. Naylor,  
Sheffield.

---

## ELECTRODYNAMICALLY INDUCED E.M.F.

---

For those readers who are interested in the continuing discussion of "electrodynamically induced e.m.f." (Letters, Feb., May, July, Sept., Oct. 1975) which was prompted by your earlier two-part series on electricity and magnetism and who would like to augment their general understanding of electromagnetic theory, I would like to recommend the lucid paper by Professor Chen-To Tai entitled, "On the Presentation of Maxwell's Theory" (*Proc. IEEE*, Aug. 1972).

This important contribution identifies some typical ambiguities found in most textbooks on the subject, explains their origins and resolves them in a scholarly way. However one has become acquainted with electromagnetic theory, Professor Tai's paper is indeed both a necessary and enlightening supplement.

Douglas H. Preis,  
Harvard University,  
USA.

The continuing controversy concerning electrodynamically induced e.m.f., as expressed by the letters from Dr Smith and Mr Masson in your September 1975 issue, prompts me to refer once again to my relevant correspondence in your

May 1975 issue. This is in broad agreement with Colin Masson's suggestion that only a relativistic consideration is satisfactory; but I must disagree with Mr Masson's statement that the electric field seen from the aeroplane is as real as the earth's magnetic field itself. Such a statement is at variance with one of the two axioms upon which Einstein based the special theory of relativity, namely that uniform and non-rotational velocity of a system cannot be detected within that system, and is in fact meaningless.

In contrast, the first reference of my May 1975 letter postulates relative motion between a conductor and the system within which the conductor e.m.f. is to be detected as a basic requirement for electrodynamic induction of e.m.f. in the conductor. Perhaps "Cathode Ray" will also accept my note of disagreement as being equally valid for his footnote in your September issue, with rotation discounted in the interest of simplicity.

John Gray,  
College of Technology,  
Belfast.

---

## "THE CONSULTANTS"

---

We have read with great interest the contribution by Mr Dwyer in the November issue on the subject of consultants.

It is a source of considerable dismay to us that there are several points which can be regarded as little short of gross misrepresentation — not only regarding the activities of our own company, Angus McKenzie Facilities Limited, but also those of several of our highly respected colleagues also mentioned in the article.

One specific source of concern to us is the very superficial discussion of fees, which most unjustly gave the impression that the better established audio consultants charged exorbitant fees, with the sole justification of personal greed for big houses and fast cars! In order to maintain a high standard of instrumentation to avoid Mr Raymond Cooke's true picture of some "consultants with just an Avo with a bent needle", the capital investment involved in a properly organised and equipped audio laboratory runs well into tens of thousands, and the feeblest level of schoolboy accountancy points to the need to amortizing this high level of expenditure. In our own concern, for example, we have had to re-equip with approaching £10,000 worth of capital gear over the last 12 months in order to keep the standard of our test equipment at least one step ahead of the increasingly more sophisticated products which we are called upon to assess. Our particular rates of charge are by no means rigid and depend upon facilities and personnel required to complete the job of work — the article made no

reference to the fact that as a firm we are not a "one-man-band"; there are indeed six of us regularly employed with extra staff enrolled as necessary for work calling for more hands.

Our second major worry is with regard to the holding of shares in companies in the audio industry. It can hardly be construed as a sin for an investor to have shares in any particular large public company in any industry — and the Managing Director, Mr McKenzie, is by no means unique in holding a relatively small proportion of his shares in major electrical companies. The point which Mr McKenzie was endeavouring to put over was that our existence depends entirely upon our being unbiased and being seen to be such and that we are most prepared to disclose any associations financial or otherwise with clients; the same state of affairs we know to be true of others amongst our respected colleagues.

Finally we would request that such an apparently irresponsibly composed article receive closer scrutiny before publication in order to maintain the very high standard and integrity of reporting to which we have previously been accustomed in *Wireless World* and also to avoid the upset which has been caused to ourselves and undoubtedly to more than a few of our colleagues.

A. P. B. Faulkner,  
Angus McKenzie Facilities Ltd,  
London, N3.

Mr Dwyer replies:

Consultants seem to find no difficulty in expressing the inestimable advantages of using their services, as Mr McKenzie well knows. Therefore, if I attempt to tell readers what to look out for if they are thinking of employing a consultant, what I have to do is to try to discover the pitfalls. I feel sure that Angus McKenzie, for whom I have the highest regard, would not countenance the design, or even the use, of a digital or analogue system which fed merely the non-errors in the output back to the input, for such a system would be unstable. Yet he is not alone among electronics engineers in being willing to entertain just such an idea in relation to examination of his own activities by the press and others.

As I pointed out in the article, PATS charge about the same as Angus McKenzie Facilities and yet they support a staff of 100, many of them Ph.Ds, as well as a laboratory and office complex covering several thousand square feet. The capital employed would be many times that employed by Mr McKenzie's company. That part of the article alluded to by Mr Faulkner merely said that consultants who have large houses and expensive cars must be successful, yet they still resent competition from university departments. I find this resentment puzzling, but I said nothing about greed, nor did I mean to imply it.

I had no intention when I started the

article of mentioning anyone's shareholdings, since normally these are the business of no-one but the person concerned. That is why I did not ask Mr McKenzie about this when I first interviewed him. But in subsequent interviews with others it was put to me that holding shares in a company might prejudice a consultant in favour of pushing the client in the direction of that company's products. I felt I could not write the article without touching on the subject and so I phoned Mr McKenzie to ask him about it. I knew that he had in the past been annoyed by remarks he said had been made about his shareholdings and thought it a good opportunity to make clear exactly what his position was. The morality of the thing is his concern. I made it clear in the article that he would tell clients of his shareholdings.

With reference to John Dwyer's article "The consultants" in the November issue, it was stated that B & W employed consultants and as implied I should like to absolutely deny this and would point out that we have a staff of five engineers in the Research and Development Department and the only outside services we call on are for styling and visual design and climatic testing for reliability of components, the two consultants being Pentagram Design Partnership, 61 North Wharf Road, London W2, and Yarsley Research Laboratories Limited, The Street, Ashstead, Surrey.

John Bowers,  
B & W Loudspeakers,  
Worthing,  
Sussex.

## INSULATION TESTERS

Mr King's reply (October Letters) to my letter in the March issue shows he quite missed my point. Far from suggesting that d.c. testing of a.c. circuits was ridiculous, I wanted to imply that the Americans were only just beginning to do it — with this "new product".

I would, however, apologise for using the name "Megger" to describe the instrument illustrated, which still looks to me very like the genuine Megger we have, and which has given yeoman service almost every day for many years. We could not manage without these tests. How could anyone?

J. G. C. Fox,  
Royal Postgraduate Medical School,  
London, W12.

## RAILWAY FAIL-SAFE?

Mr Anderton, in his interesting article on railway electronics (August issue), reproduced an example of supposedly fail-safe circuitry. The design included a traditional two transistor astable, but

did not show any provision for recovering from the stable state in which both transistors are hard on. Such a state can be reached when the power is turned on. The probability of this event depends largely on the match of transistor gains, a parameter which changes with time and temperature.



I hope that human safety does not depend on this circuit.

I would also question the use of high value resistors and capacitors in timing circuits. The 15 $\mu$ F unit, which must be a plastic film type if the quoted 5% accuracy is to be maintained, probably costs as much as the other fifty components together, and five times as much as a single integrated circuit which could perform the whole timing function.

David Cockerell,  
New York,  
USA.
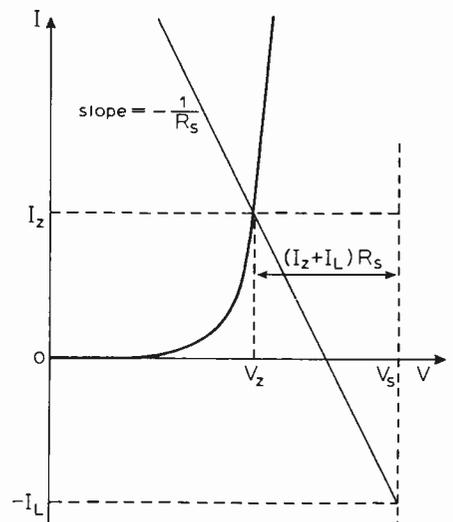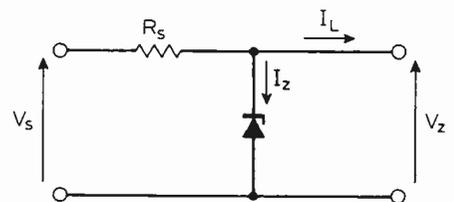
## ZENER DIODE LOAD LINE

In the case of a zener-regulated supply, students often have difficulty in relating zener voltage and current to input voltage and output current. The following simple graphical construction clar-



ifies the interrelation between these quantities. From Kirchhoff's law:

$$V_s = V_z + (I_z + I_L) R_s$$

A load line of slope  $-1/R_s$  is drawn through the point  $(V_s, -I_L)$ . Its intersection with the zener diode characteristic gives the operating point. It is immediately obvious how changes in  $V_s$  and  $I_L$  affect  $V_z$  and  $I_z$ .

N. H. Sabah,  
American University of Beirut,  
Lebanon.

# Interference from pocket calculators

## Electromagnetic radiation tests on three commercial instruments

by Charles Thomas Ristorcelli

Postgraduate School, US Navy

**This article reports an investigation into the near field electromagnetic interference caused by pocket calculators. American regulations on permissible levels of interference from portable electronic equipment are reviewed, then the results of measurements on three pocket calculators are presented. Results indicate that near field radiation levels are sufficiently large to make questionable the unrestricted operation of a pocket calculator in an electromagnetically sensitive environment, such as an aircraft flight deck. A simple and inexpensive way of eliminating the interference is suggested.**

Electromagnetic interference caused by portable electronic equipment is receiving attention in many circles, including the US Department of Defense, because of the profusion of devices such as calculators, digital test instruments and digital processors which are being used in modern electronic systems. Of particular interest is the possibility of interference to electronic sensors from these devices in electromagnetically sensitive areas such as aircraft flight decks, especially if the operation of a digital device causes r.f. emissions of significant magnitude in the near field. This increased interest is not limited to United States agencies alone, as is demonstrated by the following excerpt:

### "A Word To The Wise"

Recent tests by the Canadian Department of Communications have established that handheld calculators cause a degree of interference in a.d.f. signals when the calculator is operated in close proximity to the a.d.f. antennas. It is not necessary that operations be performed on the calculator, only that the calculator be turned on.

Pilots should be aware of this and use a.d.f. indications cautiously when handheld electronic calculators are being used in the cockpit."

The only US government regulation establishing permissible e.m. interference levels for pocket calculators is expressed in Article 15.7.(c) of the Rules and Regulations of the Federal Communications Commission:

"That in any event the total electromagnetic field produced at any point distance of  $157,000/f$  (kHz) (equivalent to  $\lambda/2\pi$ ) from the apparatus shall not exceed 15 microvolts per meter."

This regulation is applicable to all

"miscellaneous" electronic equipment, that is, equipment not specifically designed for the purpose of radiation of electromagnetic energy.

Another American organization which establishes guidelines pertaining to r.f. emission from portable electronic equipment, with emphasis on equipment to be used aboard aircraft, is the Radio Technical Commission for Aeronautics at Washington, DC.\* The following excerpt from a RTCA report emphasizes the nature of the problem:

"Unfortunately, detailed factual data upon which to base precise limits for the levels of r.f. energy which can be permitted to radiate from portable equipment are not available. However, safety considerations and general experience with r.f. interference problems indicate that the levels of radiated r.f. energy from portable electronic devices should be at least 6dB below those which cause malfunction of airborne electronic equipment during the tests conducted by the FAA. On this basis, the maximum level of permissible r.f. energy emission from any portable electronic device operated aboard aircraft in flight should not exceed the following values within the frequency bands indicated:

Frequency	Maximum emission
110 kHz	3.5 $\mu$ V/m at 64 cm
350 kHz	1.8 $\mu$ V/m at 64 cm
1750 kHz	1.7 $\mu$ V/m at 64 cm
10.0 MHz	1.15 $\mu$ V/m at 64 cm
18.0 MHz	0.63 $\mu$ V/m at 64 cm"

**Theory.** The following derivation from classical electromagnetic theory is provided as a mathematical basis for understanding the terms "near field" and "far field" in these studies.

\* RTCA is not an official agency of the US Government. It is a co-operative association of government, aeronautical industry, and telecommunications agencies. Its objectives are the resolution of aeronautical-telecommunications problems through mutual agreement.

For an elementary electric dipole of vanishingly small length relative to the wavelength  $\lambda$  of its conducted current, the electric field at an observation point  $P_{(x,y,z)}$  in the spherical co-ordinate system, as a function of angular displacement  $\theta$  from the z axis, is given by Fig. 1(a):

$$E_{\theta} = -\frac{IdB_0^2}{2\pi} \sqrt{\frac{\mu}{\epsilon}} \sin \theta \left[ \frac{1}{jB_0 r} + \frac{1}{(jB_0 r)^2} + \frac{1}{(jB_0 r)^3} \right] e^{-jB_0 r}$$

where:  $I$  = conducted current;  $B_0$  = free space phase constant;  $d$  = dipole length;  $\mu$  = permeability of free space;  $\epsilon$  = permittivity of free space; and  $r$  = radial distance from dipole centre.

For the case where  $B_0 r \ll 1$  the expression given above may be simplified to read:

$$E_{\theta} = -\frac{IdB_0^2}{2\pi} \sqrt{\frac{\mu}{\epsilon}} \sin \theta \left[ \frac{1}{(jB_0 r)^3} \right] e^{-jB_0 r} \quad (1)$$

whereas for the case  $(B_0 r) \gg 1$  a similar simplification yields:

$$E_{\theta} = -\frac{IdB_0^2}{2\mu} \sqrt{\frac{\mu}{\epsilon}} \sin \theta \left[ \frac{1}{(jB_0 r)} \right] e^{-jB_0 r} \quad (2)$$

Expressions (1) and (2) are commonly considered the near field and far field electromagnetic radiation terms, respectively. Similar derivations for all other electromagnetic field components are possible.

Consider the ratio

$$\frac{E_{\theta \text{ near field}}}{E_{\theta \text{ far field}}} = \frac{1}{B_0^2 r^2} = \frac{1}{\mu \epsilon \omega^2 r^2}$$

where  $\omega = 2\pi f$ . If a unity value for the above ratio is chosen as a convenient indicator of the radial distance  $r$  at

which a crossover between the near field and far field radiation components applies, then  $r$  may be expressed as

$$r = \frac{\lambda}{2\pi} \quad (3)$$

The ratio given by expression (3) is the radial distance chosen by the FCC in establishing the permissible interference levels described by article 15.7.(c) of FCC regulations.

The emphasis in this investigation was to determine the interference levels from near field measurements during the operation of three different portable calculators. The models chosen were two Texas Instruments SR-50 calculators and one Hewlett-Packard HP-45. The reasons for choosing these calculators were their availability, and the fact that their light emitting diode displays are blanked during the performance of certain calculations. The desirability of this feature will be explained later.

Two possible sources of electromagnetic interference believed associated with the operation of a pocket calculator are: strobing of data into the l.e.d. display; and digital switching operations associated with the streams of pulses found in all operating digital devices. The digital switching operations are believed to provide the broadband r.f. emissions when the calculator is in operation. If streams of symmetrical pulses such as shown in Fig. 1(b) are assumed in these switching operations, Fourier analysis of the waveform leads to the following Fourier coefficients in frequency domain:

$$C_k = \sum_{k=-\infty}^{+\infty} \frac{V}{\pi k} \sin \frac{k\omega_0(a)}{2};$$

$(k=0, \pm 1, \pm 2, \dots)$

These coefficients may be associated with the power spectrum of the pulse stream. If we assume a fundamental frequency of 100kHz for the calculator functions, the broadband nature of the possible radiated interference is immediately apparent.

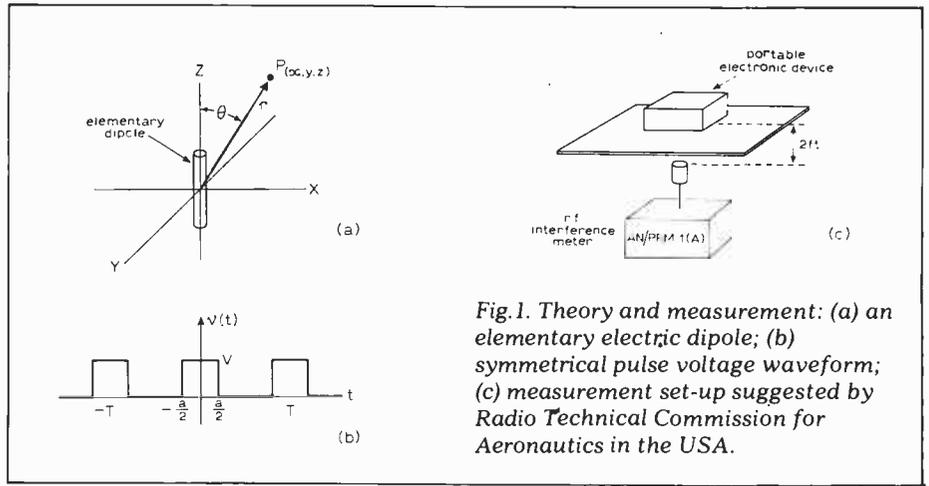


Fig. 1. Theory and measurement: (a) an elementary electric dipole; (b) symmetrical pulse voltage waveform; (c) measurement set-up suggested by Radio Technical Commission for Aeronautics in the USA.

**Measurement procedures.** The measurements in this investigation were performed according to the method suggested by RTCA, except that a radio frequency interference meter type AN/PRM-1(A) was substituted for the 390-ohm terminated valve-voltmeter suggested by RTCA (Fig. 1(c)). The frequencies of interest are those in the 110-1750 kHz band because of their importance to long range navigation systems.

The measurements obtained have been examined with the following questions in mind:

- Can the calculator's emission of e.m. interference be attributed principally to the l.e.d. display strobing, or to the internal processing? It was consideration of this question that made the chosen calculators desirable, because while the devices perform certain mathematical functions such as the determination of large factorials the l.e.d. display remains blanked, allowing

measurement of interference levels associated with the internal processing.

- Can unusual r.f. emission patterns be detected during performance of certain calculator functions?

- Is there a difference between the levels of interference from the two makes of calculator which may indicate certain construction features preferable in order to eliminate, or reduce, electromagnetic radiation?

**Operating modes.** The calculator operating modes used to measure their interference levels as indicated in the graphs and tables are defined as:

**Display.** The constant pi (3.141592654) was displayed, providing measurement of emitted r.f. energy when l.e.d. display data strobing was in progress.

**Undefined.** Division by zero was performed to provide measurement of r.f. energy emitted with a pulsating display.

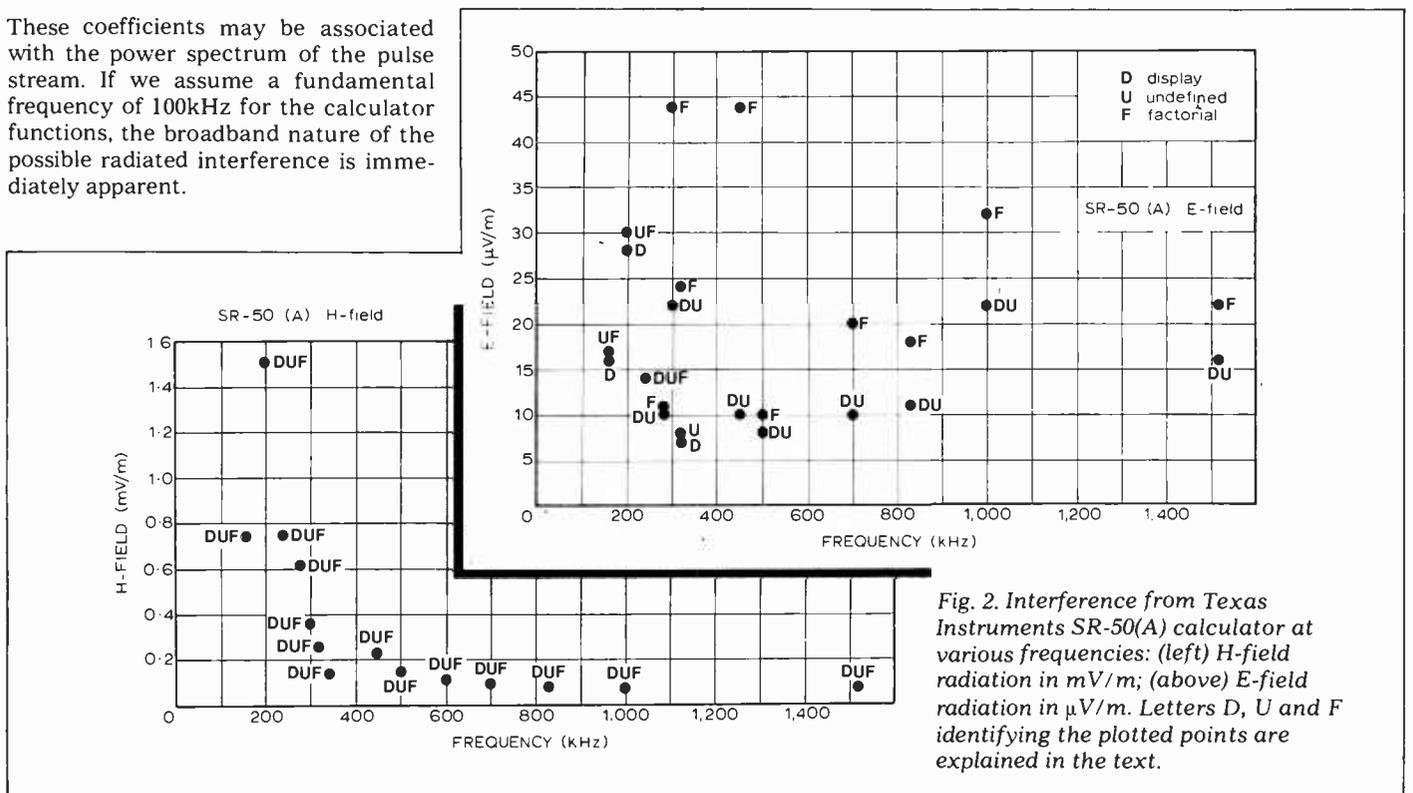



Fig. 2. Interference from Texas Instruments SR-50(A) calculator at various frequencies: (left) H-field radiation in mV/m; (above) E-field radiation in µV/m. Letters D, U and F identifying the plotted points are explained in the text.

**Table 1: H-field interference levels from three calculators ( $\mu\text{V}/\text{m}$  at 64cm). Operating modes: D — display, U — undefined, F — factorial**

frequency (MHz)	Texas Instruments SR-50 (A)				Texas Instruments SR-50 (B)				Hewlett-Packard HP-45			
	operating mode				operating mode				operating mode			
	ambient noise ( $\mu\text{V}/\text{m}$ )	D ( $\mu\text{V}/\text{m}$ )	U ( $\mu\text{V}/\text{m}$ )	F ( $\mu\text{V}/\text{m}$ )	ambient noise ( $\mu\text{V}/\text{m}$ )	D ( $\mu\text{V}/\text{m}$ )	U ( $\mu\text{V}/\text{m}$ )	F ( $\mu\text{V}/\text{m}$ )	ambient noise ( $\mu\text{V}/\text{m}$ )	D ( $\mu\text{V}/\text{m}$ )	U ( $\mu\text{V}/\text{m}$ )	F ( $\mu\text{V}/\text{m}$ )
0.160	62.0	750.0	750.0	750.0	90.0	240.0	300.0	310.0	135.0	9000.0	1050.0	1050.0
0.200	60.0	1500.0	1500.0	1500.0	90.0	450.0	630.0	510.0	120.0	2700.0	585.0	150.0
0.240	90.0	750.0	750.0	750.0	90.0	150.0	300.0	210.0	90.0	600.0	420.0	420.0
0.280	75.0	600.0	600.0	600.0	60.0	60.0	110.0	60.0	90.0	2100.0	360.0	120.0
0.300	75.0	360.0	360.0	360.0	70.0	240.0	300.0	210.0	60.0	3000.0	225.0	90.0
0.320	60.0	225.0	225.0	225.0	30.0	30.0	60.0	100.0	45.0	600.0	150.0	60.0
0.340	60.0	150.0	150.0	150.0	45.0	60.0	100.0	45.0	45.0	1050.0	180.0	240.0
0.450	60.0	210.0	210.0	210.0	60.0	1500.0	720.0	2100.0	60.0	1500.0	180.0	60.0
0.500	60.0	165.0	165.0	165.0	60.0	70.0	1800.0	80.0	55.0	600.0	150.0	55.0
0.600	54.0	126.0	126.0	126.0	60.0	65.0	90.0	75.0	60.0	660.0	80.0	60.0
0.700	54.0	105.0	105.0	105.0	48.0	75.0	90.0	120.0	55.0	2850.0	300.0	600.0
0.830	20.0	35.0	35.0	35.0	20.0	200.0	140.0	240.0	20.0	450.0	60.0	20.0
1.000	20.0	30.0	30.0	30.0	20.0	120.0	90.0	190.0	20.0	175.0	60.0	20.0
1.520	20.0	45.0	45.0	45.0	20.0	100.0	70.0	120.0	20.0	80.0	30.0	20.0
2.100	40.0	40.0	40.0	40.0	40.0	100.0	130.0	100.0	40.0	160.0	50.0	60.0

**Table 2: E-field interference levels from three calculators ( $\mu\text{V}/\text{m}$  at 64cm). Operating modes: D — display, U — undefined, F — factorial**

frequency (MHz)	Texas Instruments SR-50 (A)				Texas Instruments SR-50 (B)				Hewlett-Packard HP-45			
	operating mode				operating mode				operating mode			
	ambient noise ( $\mu\text{V}/\text{m}$ )	D ( $\mu\text{V}/\text{m}$ )	U ( $\mu\text{V}/\text{m}$ )	F ( $\mu\text{V}/\text{m}$ )	ambient noise ( $\mu\text{V}/\text{m}$ )	D ( $\mu\text{V}/\text{m}$ )	U ( $\mu\text{V}/\text{m}$ )	F ( $\mu\text{V}/\text{m}$ )	ambient noise ( $\mu\text{V}/\text{m}$ )	D ( $\mu\text{V}/\text{m}$ )	U ( $\mu\text{V}/\text{m}$ )	F ( $\mu\text{V}/\text{m}$ )
0.160	3.0	16.0	17.0	17.0	2.0	12.0	11.0	50.0	3.0	20.0	160.0	28.0
0.200	3.0	28.0	30.0	30.0	2.0	6.0	6.0	6.0	3.0	11.0	20.0	18.5
0.240	3.0	14.0	14.0	14.0	1.8	5.5	4.0	8.0	3.0	11.0	12.0	6.0
0.280	3.0	10.0	10.0	11.0	2.0	4.5	4.0	9.0	2.9	11.0	12.0	6.0
0.300	3.0	22.0	22.0	44.0	2.5	5.0	4.5	19.0	3.0	180.0	180.0	200.0
0.320	3.0	8.0	7.0	24.0	4.1	7.5	7.0	14.0	3.0	100.0	80.0	100.0
0.340	3.0	9.0	9.0	32.0	4.0	6.0	6.0	6.0	3.0	70.0	120.0	70.0
0.450	3.0	10.0	10.0	44.0	2.0	4.0	4.5	5.0	3.0	24.0	60.0	20.0
0.500	3.2	8.0	8.0	10.0	2.0	6.0	7.0	16.0	3.0	100.0	180.0	110.0
0.600	3.2	9.5	9.5	11.0	1.9	3.5	3.0	10.0	3.0	16.0	18.0	16.0
0.700	3.2	10.0	10.0	20.0	2.0	4.0	4.0	5.0	3.2	100.0	240.0	120.0
0.830	4.0	11.0	11.0	18.0	2.0	10.0	8.0	14.0	4.0	10.0	44.0	8.0
1.000	6.0	22.0	22.0	32.0	2.0	4.0	4.0	8.0	3.6	6.0	55.0	10.0
1.520	5.7	16.0	16.0	22.0	2.0	2.0	3.0	5.0	3.9	9.0	80.0	9.0
2.100	5.7	6.0	6.0	9.5	1.0	2.0	2.0	4.0	2.0	4.0	20.0	4.0

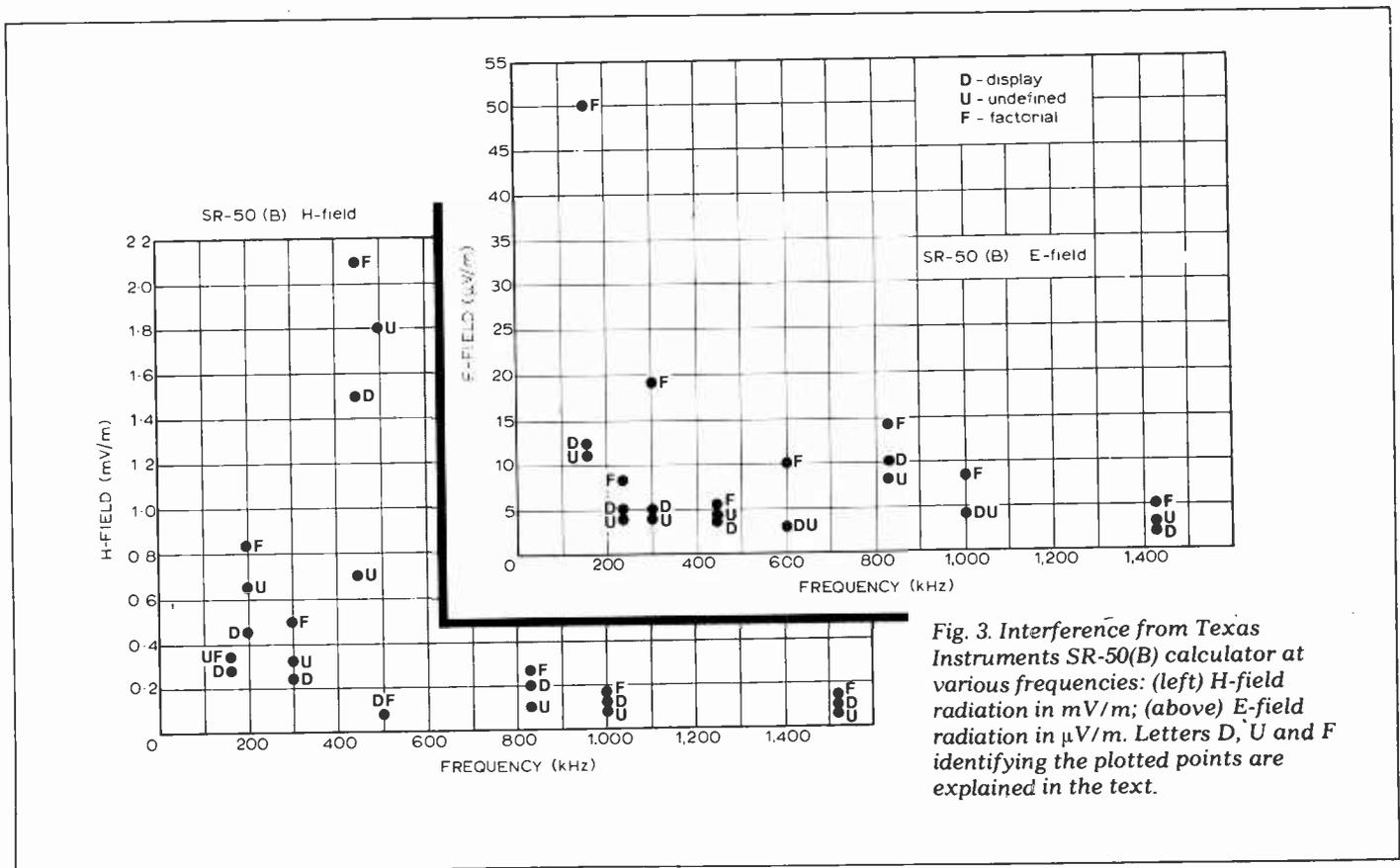

**Fig. 3. Interference from Texas Instruments SR-50(B) calculator at various frequencies: (left) H-field radiation in mV/m; (above) E-field radiation in  $\mu\text{V}/\text{m}$ . Letters D, U and F identifying the plotted points are explained in the text.**

**Factorial.** 69! was calculated. In this manner the display was blanked for approximately 4 seconds, allowing the measurement of emitted r.f. as a result of the internal digital processing.

The frequencies for measurement were randomly chosen. The r.f. energy emission was not confined to discrete frequencies, however, but was observed to cover a very broad spectrum. The non-automated measuring technique prevented a continuous measurement of interference vs. frequency, thus making necessary a discrete set of measurements. The results of all measurements are listed in the tables and selected data are presented graphically in Figs. 2, 3 and 4.

**Conclusions.** As expected before the measurements were performed, the levels of e.m. interference detected as a result of the calculator operations were below the limits established by the FCC for such interference. However, these limits address the interference detected at a range  $r = \lambda/2\pi$ , a distance which our theoretical development indicates is a crossover point for near vs. far field considerations. In the near field the measurements indicate a level of interference which exceeds the limits suggested by RTCA for electromagnetically sensitive environments such as aircraft in flight.

From the above considerations it seems advisable to re-examine the regulations establishing permissible interference levels from portable electronic equipment. The fact that significant levels of interference are present in the near field of an operating portable calculator becomes a problem only if the environment in which the device is

operated cannot safely tolerate the interference. If instances of this problem are identified, then either restrictions on the use of portable calculators may be imposed, or a cure for the radiated interference must be found (a possible solution is offered below):

The E-field interference intensity measurements associated with the operation of the SR-50 calculators would indicate that the resulting interference levels are principally caused by the internal digital processing in the strobing of the i.e.d. display. This type of interference should be expected from any digital processor, and the power level of the interference should be directly related to the power levels found within the device.

The measurements indicated that for near field considerations the interference levels associated with the H-field electromagnetic components are orders of magnitude greater than those associated with the E-field. Further investigation may reveal that this phenomenon is a result of component layout within the calculator, permitting circular current flows to create a "loop antenna" radiation effect.

As a subject of amusing interest, the AN/PRM-1(A) r.f. interference meter provides the operator with an audio output for monitoring purposes, and the interference signals resulting from

operation of the calculators presented significantly different "audio signatures" as a function of calculator brand. The differences were sufficiently pronounced to allow the meter operator to identify the calculator brand name from the audio output.

Finally, a means was sought which would reduce the levels of interference emitted from these calculators. Some form of shielding seemed a likely solution, and this approach was briefly examined. The calculators were surrounded by one sheet of aluminium kitchen foil and then operated in the various modes described above. The shielding proved so effective that the r.f. interference meter was then only capable of detecting the ambient noise level of electromagnetic radiation. This suggests that, at least where portable calculators are concerned, perhaps either selectively or collectively as a general cure, providing a foil or other type of shield around the interior of the calculator case would eliminate the possibility of interference from these devices in environments where it cannot safely be tolerated.

**Reference**

1. United States Department of the Navy, *Approach, The Naval Aviation Safety Review*, December 1974, p.28. Washington, United States Government Printing Office, 1974-635 022/7.


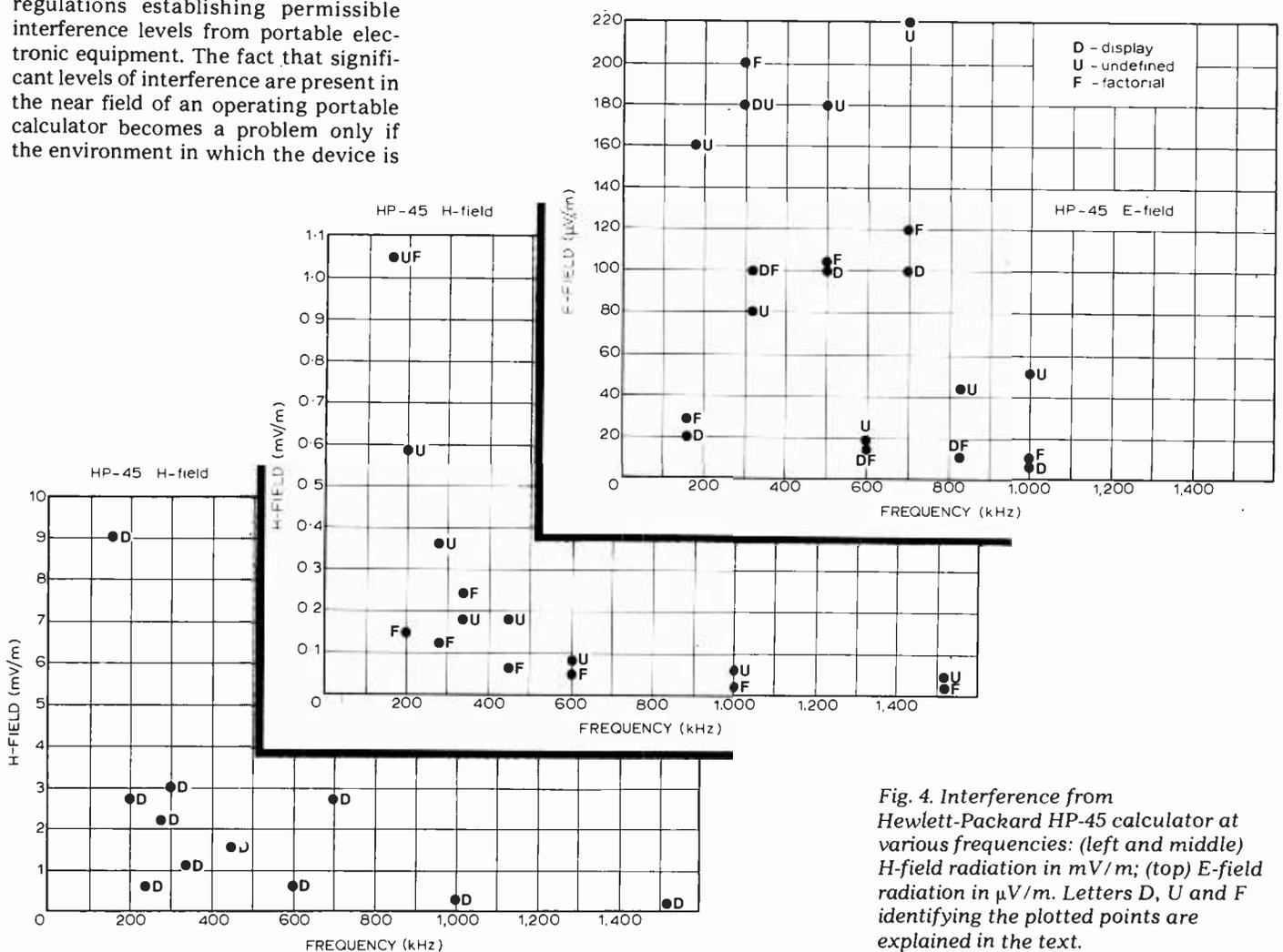


Fig. 4. Interference from Hewlett-Packard HP-45 calculator at various frequencies: (left and middle) H-field radiation in  $mV/m$ ; (top) E-field radiation in  $\mu V/m$ . Letters D, U and F identifying the plotted points are explained in the text.

# Circuit Ideas
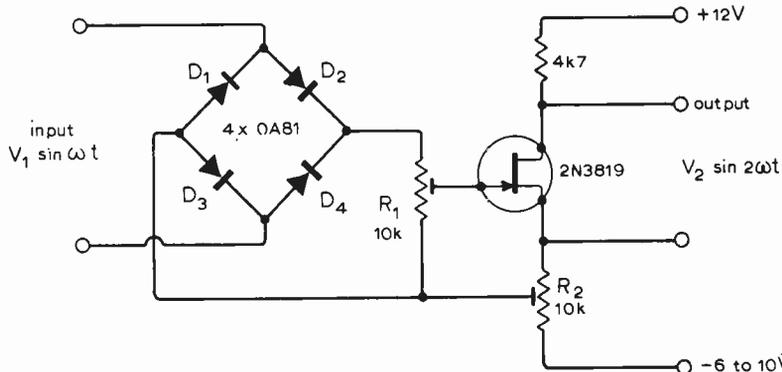
## Frequency doubler

This circuit was devised to show that theory can be put into practice; we hope that readers may find other uses for it. The theory is simply the trigonometric identity  $\frac{1}{2}(1 + \cos 2\theta) = \cos^2 \theta$ . Replacing  $\theta$  by  $\omega t$  produces a frequency doubler. Probably the easiest way of obtaining a square law characteristic, at least over half the input range, is to use



a f.e.t. because the drain current is determined by

$$I_d = \left(1 - \frac{V_{gs}^2}{V_p^2}\right) \cdot I_{dss} \text{ for } |V_{gs}| \leq |V_p|.$$

In practice,  $D_{1,2,3,4}$  ensure that a positive-going pulse is applied to the f.e.t. gate so that the device operates with a square law effect on both cycles ( $\cos^2 \theta = |\cos \theta|^2$ ).

Potentiometer  $R_1$  is adjusted to operate the device at the correct input level, a compromise between overloading and a good output.

Potentiometer  $R_2$  sets the f.e.t. to just-cut-off under no-signal conditions,

which operates the device in the square law region. The potentiometers may be adjusted, while the device is in operation, with the use of an oscilloscope or t.h.d. monitor to obtain minimal distortion. Correctly set up, the harmonic content of the output for a sine wave input can be made to approach that of the input. It will of course considerably distort any other input waveform. The circuit shown performed well up to about 10kHz, but this could probably be bettered with good construction and higher speed diodes.

R. Williams & J. Dunne  
Brentwood School,  
Essex.

## Clock generator for electronic calculators


The *Wireless World* desk calculator (Sept./Oct. 1972) uses a hybrid thick-film integrated circuit for its clock generator. An alternative, and inexpensive (around 50p) way of producing the clock waveform is by means of two readily available t.t.l. integrated circuits, as shown.

NAND gates A, B, C, D and E are connected to form a free-running multivibrator, with a self starting gate,

C, to ensure that the clock waveform is available as soon as the supply is applied to the calculator-chip. The multivibrator output (gate D) swings approximately from  $-7.2$  to  $-2.1V$ , and this signal is applied to the input of a voltage level changing gate, F, which is an open-collector type having its output connected to  $+7.2V$  via a  $1k\Omega$  resistor. When the input to F is  $-7.2V$  (logical 0) this gate is effectively an open

circuit and its corresponding output is  $+7.2V$ . Alternatively, when the input to F is  $-2.1V$  (logical 1) this gate is effectively a short-circuit and its corresponding output is  $-7.2V$ . Therefore the output swings between  $+7.2$  and  $-7.2V$  at approximately 320kHz for a 1000 pF capacitor. This frequency was found to be satisfactory in practice.

T. J. Terrell,  
Preston Polytechnic.

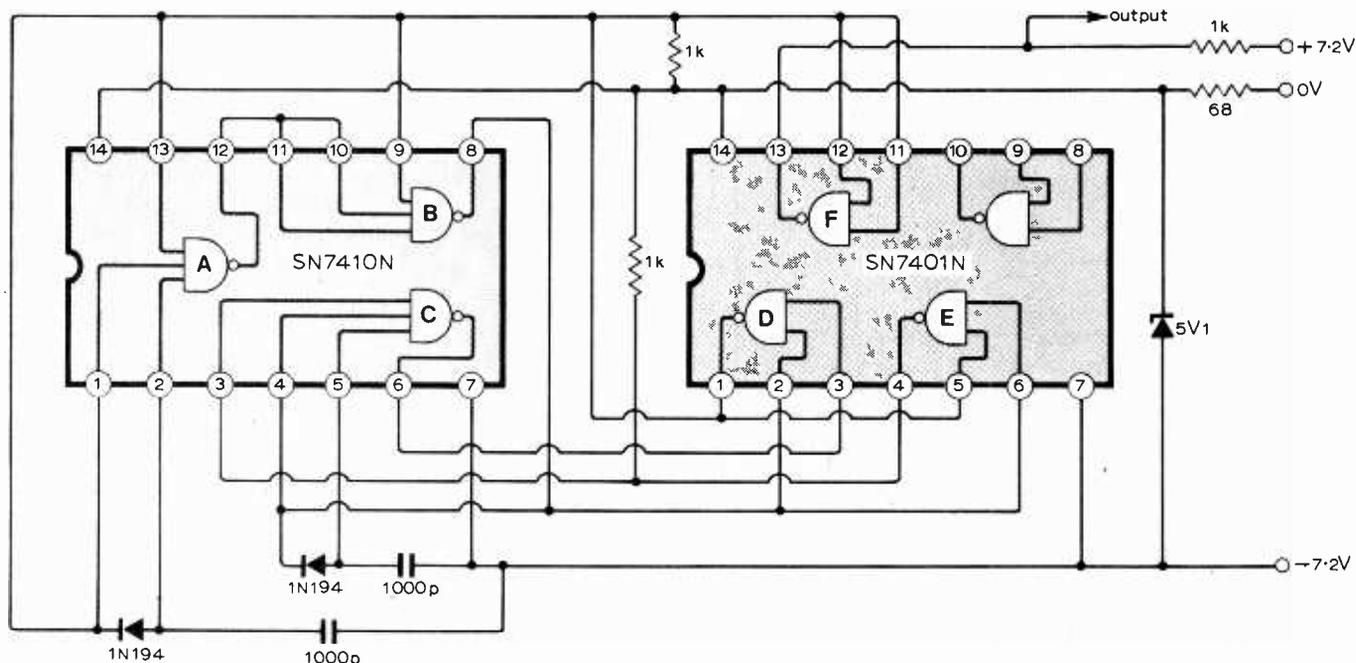

## Linear current/rotation control

In the circuit described, the current through a linear potentiometer is made a linear function of the rotational angle of the potentiometer. Consider the circuit of Fig. 1, in which

$$i_1(R_1 + R_2 + R_3 + R_4) = i(R_3 + R_4).$$

The linear relationship between angle of turn and current  $i_1$  is achieved by making current  $i$  constant and by using a double potentiometer for  $R_1$  and  $R_4$ , connected so that  $R_1 + R_4$  is constant and equal to the value of the potentiometer  $R$ , therefore

$$i_1 = \frac{i}{R + R_2 + R_3} (R + R_3 - R_1)$$

showing the linear relationship between current  $i_1$  and the variable resistance  $R_1$ . Because  $R_1$  has a maximum value of  $R$  the ratio of maximum to minimum current is

$$\frac{i_{1 \max}}{i_{1 \min}} = \frac{R + R_3}{R_3}$$

This ratio may be altered by adjusting  $R_3$ .

For any setting of the potentiometer, current  $i_1$  is proportional to  $i$  so the latter may be adjusted to set up a particular  $i_{1 \max}$  or  $i_{1 \min}$ . Appropriate adjustment of both  $i$  and  $R_3$  allows setup of  $i_{1 \max}$  and  $i_{1 \min}$ . In designing a practical circuit we must allow for the voltage across the arms (assuming still that  $v_1 = v_2$ ):

$$v - v_1 = i_1(R_1 + R_2)$$

$$= \frac{i}{R + R_2 + R_3} (R_1 + R_2) (R + R_3 - R_1)$$

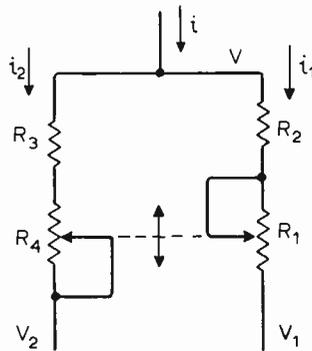


Fig. 1

which is dependent upon angle of rotation and is at maximum

$$(v - v_1)_{\max} = \frac{i(R + R_2 + R_3)}{4}$$

Shown in Fig. 2 is a practical circuit in which the current  $i_1$  is used to charge capacitor  $C$  which is periodically discharged by the unijunction transistor when the trigger voltage is reached. Because the charging time is inversely proportional to charge current, the frequency of the output sawtooth is proportional to current  $i_1$  and hence to the potentiometer's angle of rotation. The setup sequence is:

Adjust potentiometer to give maximum frequency sawtooth and adjust preset  $R_5$  to give the required maximum frequency.

Set potentiometer to the other extreme and adjust preset  $R_3$  to give the required minimum frequency.



The sequence may need repeating because the two adjustments are coupled. The preset  $R_6$  is adjusted to setup working voltages, and in a final design may be replaced by a fixed resistor.

A multi-way switch can be included to select different  $R_5$  and  $C$  values.

Andrew Armit,  
Clifton,  
Bedfordshire.
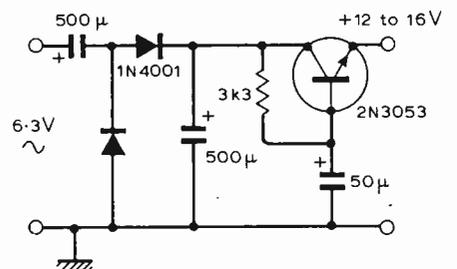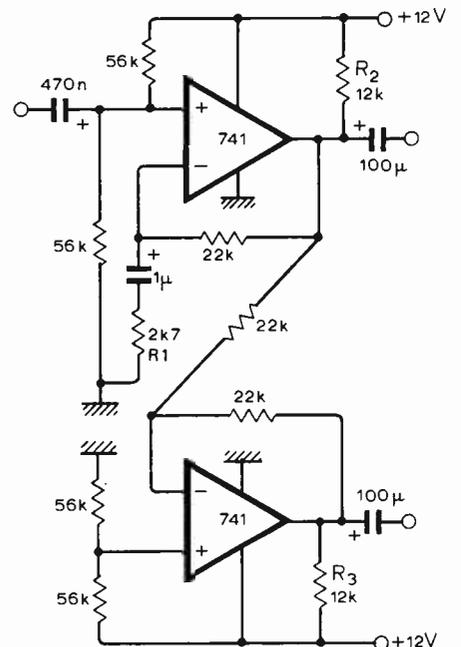
## Balanced output amplifier

This low-cost amplifier provides a low impedance balanced output from an unbalanced input. The modest power supply requirements can be met by a voltage doubler and filter working from a valve filament supply; this enables a balanced output to be added to a valve preamplifier. In the original design 741



amplifiers were used but similar types such as the LM307 or dual 741 (747) can be used. Response is flat from 10Hz to 20kHz and the distortion is less than 0.1% at 800Hz + 20dBm into a 600ohm load. Crossover distortion is minimized by the addition of  $R_2$ , and  $R_3$ . The gain is 20dB but can be reduced by increasing  $R_1$ .

K. D. James,  
Dunedin,  
New Zealand.

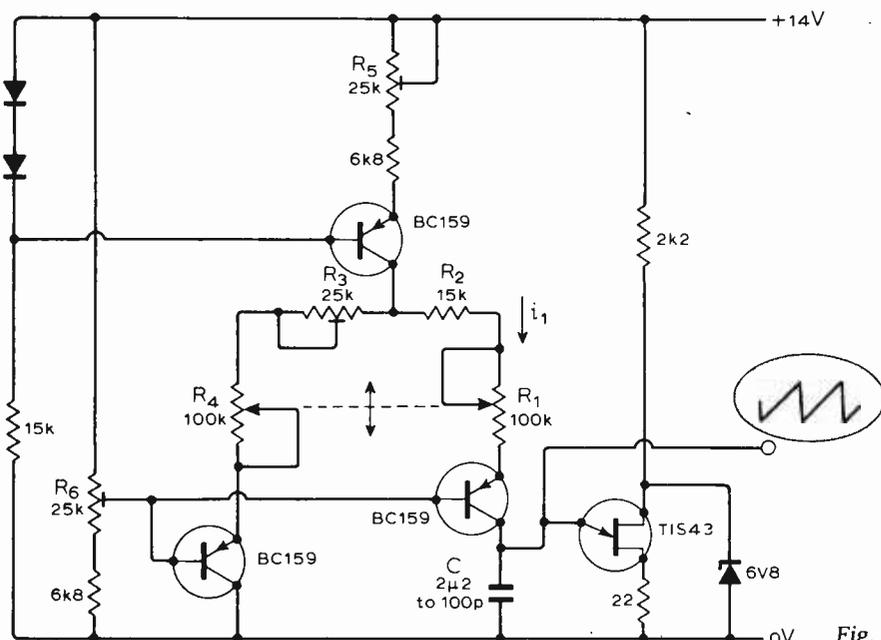


Fig. 2

Contributors to Circuit Ideas are urged to say what is new or improved about their circuit early in the item, preferably in the first sentence.

# Advances in microwaves


5th European microwave conference held last September in Hamburg is reported by M. W. Hosking, author of the Realm of Microwaves articles

**This conference has grown in size over the years and also in composition, starting as a biennial event held first in London in 1969, then in Stockholm in 1971 where it was amalgamated with the Microwave and Optical Generation and Amplification Conference (MOGA), Brussels in 1973, and Montreux in 1974. From 1974 the conference became associated with an organised exhibition and is now the largest microwave event of its kind.**

In recognition of the advances being made in opto-electronics, together with the use of the laser and infra-red sources in communications, Prof. H. G. Unger's invited paper on optical waveguides gave a very comprehensive survey of this vital area of technology. There are two main areas of development, one being the types of transmission line suitable for the design of components and interconnections, and the other being long-distance waveguide. In the first category, the most widely-used type of transmission line is the film guide. This consists of a thin dielectric film on top of a dielectric substrate of lower refractive index. A trapped light wave then propagates down the thin film in a zig-zag fashion by total internal reflection at the boundaries. Phase conditions can exist for both low and high-order modes but, as the attenuation losses arise from general dispersion and scattering at film imperfections, the higher order modes suffer greater loss. Transparent glass-film guide with suitable boron and silicon doping can provide low-order mode losses of less than 1dB/cm and a value of 0.04dB/cm has been achieved.

Instead of coating the complete substrate, the film can be made as a narrow raised or recessed strip and can still provide total internal reflection at the side walls. This looks very similar in section to the microstrip type of microwave transmission line and, in fact, many of the design principles can be used directly to fabricate beam splitters, directional couplers, filters and other passive components.

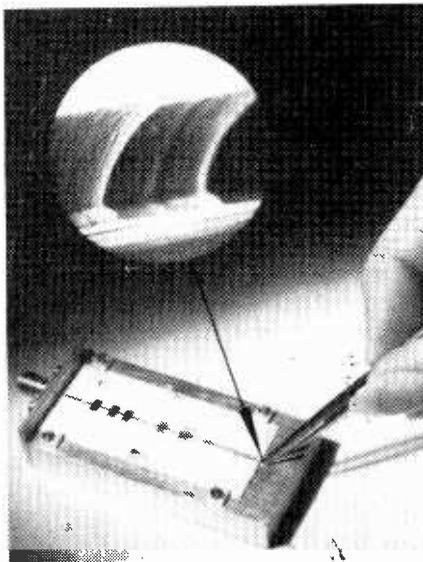A laser beam can be coupled into and out of the film guide by various types of coupler. One efficient method is to form a series of grating strips in the film which, with proper phase design, will radiate a coherently scattered beam into the guide. Another technique, the prism coupler, consists of bringing a



*Microstrip pulsed Trapatt oscillator producing about 100W peak power at 2.5GHz with 32.5% efficiency. Key circuit element is a matching low-pass filter. Inset shows the device mesa structure. (Mullard Research Laboratories).*

slab of different refractive index material into close proximity with the film guide. An evanescent mode is set up in the gap which in turn excites a plane wave in the prism and, for the correct laser intensity distribution, can vary efficiently couple out power.

For long-distance signal transmission, single-mode fibres are used consisting of a central core and a slightly lower refractive index cladding. The wave is confined by total internal reflection and parameters are adjusted so that usually only the dominant HE<sub>11</sub> mode propagates. Fibres with a graded index of refraction, decreasing from the centre outwards, are being developed

to reduce signal dispersion and high-silica fibres have been made with 1dB/km loss and less than 1ns/km pulse dispersion.

This is still a new and rapidly expanding area and many problems remain to be overcome in circuit design and basic technology. Not least is the interconnection of optical fibres which individually range in diameter from about 10<sup>-2</sup>mm to 10<sup>-1</sup>mm.

In the design of array antennas, commonly-used individual elements are the half-wave dipole and radiating slot and most attention is paid to the overall radiation pattern, together with problems of mutual coupling. In a paper presented by A. Clavin of Hughes Aircraft, a basic improvement in the design of the individual array element was described, consisting of a conventional slot radiator with two short wires placed one either side and normal to the slot. The total radiation pattern is a combination of a slot plus an array of two dipoles (monopole plus image). By adjusting the phase of excitation of the wires by their length and spacing, the slot pattern can be modified. In particular, its endfire radiation can be cancelled, with the result that the E-plane pattern of the element can be made equal to the H-plane slot pattern. The new element thus has a symmetrical radiation pattern. Beamwidth was increased by bending over the top of each wire to form an inverted-L. Practical results with an array of these new elements at X-band have shown a reduction in mutual coupling, elimination of back radiation, general improvement in sidelobe structure and a slight increase in gain.

Complementary to the radiating aperture side of phase array antennas was a session devoted to the heart of the system — the microwave phase-shifter circuitry itself. This, as usual, splits into the two areas of ferrite and p-i-n diode

devices where the competition still exists for the best low weight, low loss and low cost device. On the ferrite side the papers were mainly theoretical and included a useful survey of the properties and performance of dual-mode reciprocal phasers. A further advance in the design of high power, low loss p-i-n diode phase shifters was reported from ITT in the form a 4-bit ( $22.5^\circ$ ,  $45^\circ$ ,  $90^\circ$ ,  $180^\circ$ ) device on a sapphire substrate capable of handling 440 watts at a 17dB insertion loss level.

On the solid-state oscillator and amplifier front, one of the most rapidly advancing areas is that of the microwave field-effect transistor. This device is already competing strongly on noise performance with microwave mixer diodes and looks likely to offer higher c.w. powers and higher efficiency than Impatt devices. In a paper read by J. A. Angus of Plessey, results on some designs of GaAs power m.e.s.f.e.t.s. were presented. Using some novel gate and drain configurations, a four-cell,  $2\mu\text{m}$  gate device gave 700mW of c.w. power output at 3GHz with 6dB gain and 25% efficiency. A six-cell f.e.t. of slightly different geometry and a  $3.5\mu\text{m}$  gate length gave 1.3 watt at 2GHz with 6.2dB gain and 32% efficiency. With multiple-cell devices already reported as giving saturated output powers of this order at X-band (8 to 12GHz), f.e.t. development over the next few years should prove to be very interesting.

At the low-noise end of the scale, an impressive GaAs m.e.s.f.e.t. amplifier was described by C. A. Liechti *et al.* of Hewlett Packard. Operating in the 11.7 to 12.2GHz satellite communication band, the three-stage amplifier using  $1\mu\text{m}$  gate chips on a microstrip circuit gave a noise figure of 5.3dB with 18dB gain. This compares very favourably indeed with achievable mixer figures. On cooling to  $40^\circ\text{K}$ , the noise figure improved to 1.6dB ( $130^\circ\text{K}$  noise temperature) and the gain increased to 31dB. Considering that uncooled and cooled parametric amplifiers provide about  $150^\circ\text{K}$  and  $50^\circ\text{K}$  respectively of noise figure, improved performance of this type of m.e.s.f.e.t. is expected to provide keen competition.

Acoustic-wave technology is another area wherein steady progress is being made and a paper from France by P. Hartemann of Thomson-CSF described a range of surface-wave components produced on lithium niobate and quartz substrates. Operating in the region of 1000MHz, a range of wide-band delay lines, filters and oscillators had been constructed. One of the main technological advances was the production of transducer patterns with linewidths down to  $0.3\mu\text{m}$ . The Royal Radar Establishment continues its world leadership in bulk acoustic-wave technology and T. M. Mason described the design of a complete delay module containing delay line, amplifiers, p-i-n switches, circulators and power supplies. Spinel ( $\text{MgAl}_2\text{O}_4$ ) crystal formed

the delay line and the module operated at 1000MHz with a 3dB bandwidth of 500MHz,  $22\mu\text{s}$  delay and unity gain.

Finally, a session this year was devoted to the biological effects of microwaves. The most apparent and obvious effect of microwave power has always been the absorption of energy by living tissue, leading to heating. However, in experiments on animals, nervous system effects, blood cell production and glandular performance have all proved to be influenced by microwave exposure. On the cheerful side, there appears to be no definite evidence of attributable health defects among microwave workers. But a disturbing inconsistency prevails in that the USSR specifies  $0.01$  to  $1\text{mW}/\text{cm}^2$  as a safe power density whilst the USA specifies  $10\text{mW}/\text{cm}^2$ .

This, the second year of a combined conference and exhibition, was well supported in terms of exhibitors with over 100 companies being represented on stands. Components of all sorts were on show ranging from connectors to integrated sub-systems and semiconductor devices. A full range of instruments was also present, including advanced sweep generators, power monitors and spectrum analysers. There never appeared to be much danger of being trampled underfoot by visitors to the exhibition and a light attendance was confirmed by many of the people on the stands. However, a general comment was that those that did attend were serious visitors and several reported fresh business openings.

The 1976 European Microwave Conference will be held from 14 to 17 September at the Pallazzo di Congressi in Rome with Professor Peitro de Santis as chairman. Particular attention will be paid to microwave acoustics and integrated optics.

#### "Facsimile scanner"

We regret that an error occurred in the diagram of Fig. 5, p.460, in the October issue. The two  $1\text{k}\Omega$  resistors should be returned to the gate inputs, not to 5V. This biases the gates in the "linear" part of their characteristic and ensures starting.


#### "Transmitter power amplifier design"

We regret that it has been necessary to postpone publication of the fourth, and final part of this series.
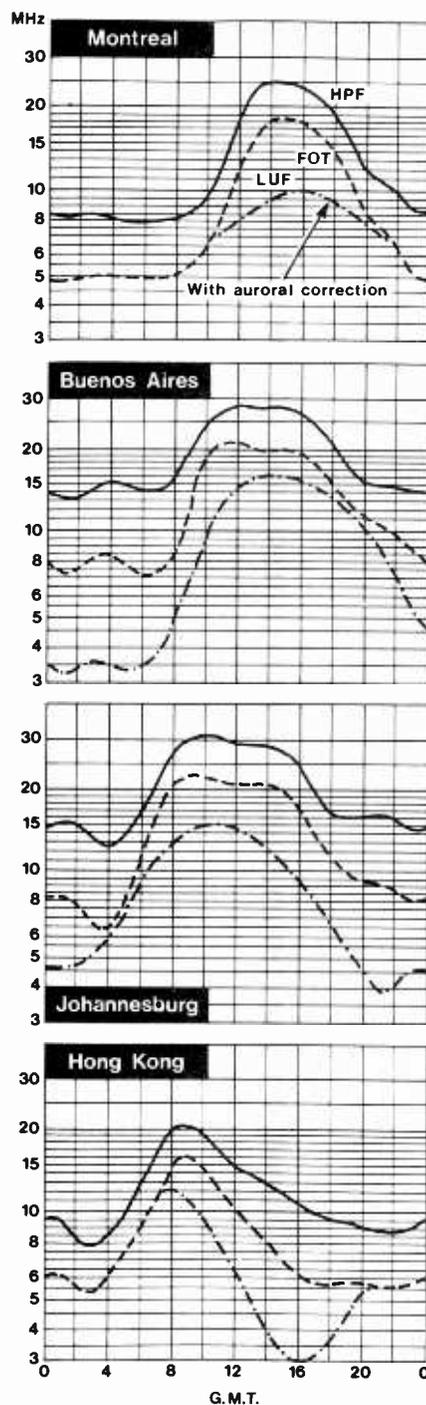
## HF predictions

Ionospheric absorption or skywave loss is greater during winter than in summer months. This is known as the winter anomaly as it is the opposite effect to that deduced from simple reasoning of the seasonal changes in sun/Earth relationship.

The high absorption is continuously present over a large area for several days and then shifts to another area, for example Europe to Western Russia. This results in short routes having "patchy" conditions and long routes having day-to-day variations in signal strength about four times greater than during summer. However, with the availability of higher frequencies (compare this month's Montreal chart with that for June) winter daytime communication is overall better than that experienced during summer.



# High resolution satellite cloud cover pictures

Report from a unique ground receiving station

by P. E. Baylis

*University of Dundee*

The Department of Electrical Engineering and Electronics, University of Dundee has recently completed the construction of a ground receiving station for the acquisition of Very High Resolution Radiometer (VHRR) cloud cover picture data from the American NOAA satellites. It is thought to be the only station in the UK with this capability. This type of data transmission is similar to that on 137.5 and 137.62MHz from the low resolution scanning radiometers on the same spacecraft. The chief difference lies in the nearly ten-fold increase in resolution and consequent hundred-fold increase in data rate. The VHRR scanning rate is 400 lines of visible and 400 lines of infra red channel per minute, time multiplexed. The resolution of both channels is 0.9km. The analogue signal from the radiometer which has a video bandwidth of 35kHz, frequency modulates a 99kHz subcarrier with peak deviation of  $\pm 29$ kHz. The subcarrier frequency modulates the main carrier of 1697.5MHz with peak deviation of  $\pm 300$ kHz. Total r.f. bandwidth is approximately 1MHz and the transmitter power is 5W (+37dBm).


The Dundee receiver front end consists of a two stage transistor preamplifier, balanced diode mixer and first i.f. mounted at the focus of a 12ft diameter fully steerable parabolic reflector antenna. Local oscillator power is derived from a v.h.f. crystal controlled oscillator followed by a power amplifier, a times-12 varactor multiplier and an interdigital bandpass filter fabricated in triplate configuration from p.c.b. The first i.f. is at 137MHz so that it can be fed into existing v.h.f. satellite equipment for the reception of APT (Automatic Picture Transmission) compatible WE-FAX type transmissions from either Meteosat or SMS when they become available in the future. The low noise two stage transistor preamplifier was fabricated from microstrip on three  $2 \times 2$ in alumina substrates and has a noise figure of approximately 3dB. The transistors are type 35876E, made by Hewlett Packard. It is mounted in a sealed tube bolted on to the back of a 5in diameter circular waveguide primary

feed at the reflector focus. Right hand circular polarization is transmitted by the spacecraft so the circular waveguide contains a polarizer to convert from circular to linear before the probe transition into a coaxial feed to the receiver. Matching into the first transistor is for optimum noise. A bandpass filter is included in the preamplifier to attenuate the second channel and discourage local v.h.f. mobile signals which are frequently over 70dB stronger than the satellite signals.

When the satellite is at an elevation of  $5^\circ$  the slant range is 2180 miles and the space loss  $(\lambda/4\pi R)^2$  is -169dB. With a receiver n.f. of 3dB and bandwidth 1MHz the resultant predemodulator carrier/noise ratio is 14dB assuming the gain of the 12ft reflector antenna to be 33.7dB (55% aperture efficiency). In fact, the receiver will produce usable data from horizon to horizon.

The remaining parts of the receiver are quite conventional. A second mixer, manually tuned v.f.o. and 10.7MHz second i.f. amplifier are followed by a bandpass limiter and phase lock discriminator. Doppler shift has a maximum of  $\pm 25$ kHz so a.f.c. to the second i.o. is included. A separate i.f. is used to drive an S meter and to produce a signal for the possible implementation of auto-track at some future date.

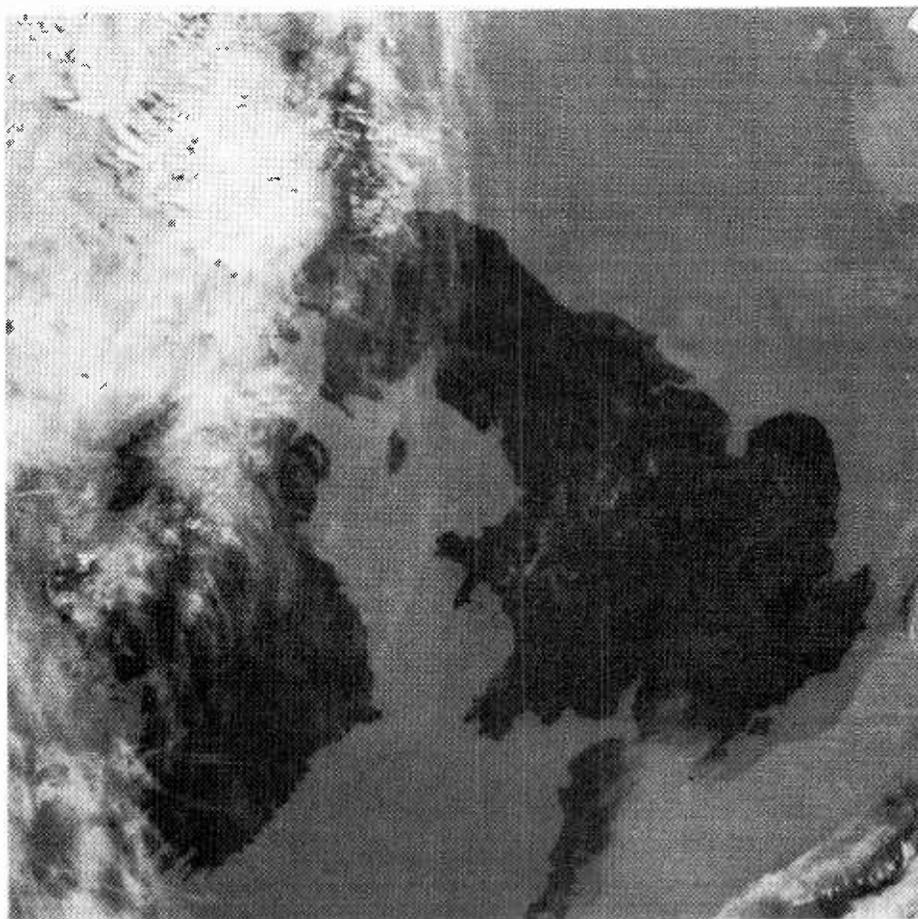*Satellite NOAA 4, orbit no 2313, date 19.5.75, time 09.40, height 31km.*






## ESA's first satellite

The first satellite to be launched by the new European Space Agency (ESA) was placed in orbit on August 9, 1975 from the Western Test Range, California. A scientific satellite designed to study extraterrestrial gamma-radiation, COS-B is the eighth satellite developed by European industry for ESA's predecessor, the European Space Research Organization. COS-B carries a single payload which can be considered as a remotely-controlled astronomical laboratory designed to study radiation emitted from known and assumed sources of gamma rays. The payload has been assembled by six institutes in France, Germany, Italy, Netherlands.

The experiment electronics unit plays a central role in the payload in that it generates and accepts most of the internal payload signals and controls the flow of data from the sub-systems to the telemetry encoder. These signals

consist of time, position and energy data produced by gamma and pulsar synchronizer events in the sub-systems of the payload. A built-in inflight test sequencer generates four main programmes which are capable of testing and calibrating other parts of the payload according to a preset pattern. Other functions of the experiment electronics are concerned with basic interpretation of data produced by the spark chamber. The objective of this chamber is the accurate measurement of the arrival direction of gamma quanta in the energy range from 30MeV to above 3GeV. Tracks of electron-positron pairs produced when gamma quanta in this energy range pass through conversion plates are traced out in the chamber by sparks produced by applied high voltage fields. The position co-ordinates of the sparks generated are stored on ferrite cores and from there are transferred to a buffer memory for telemetering to ground.

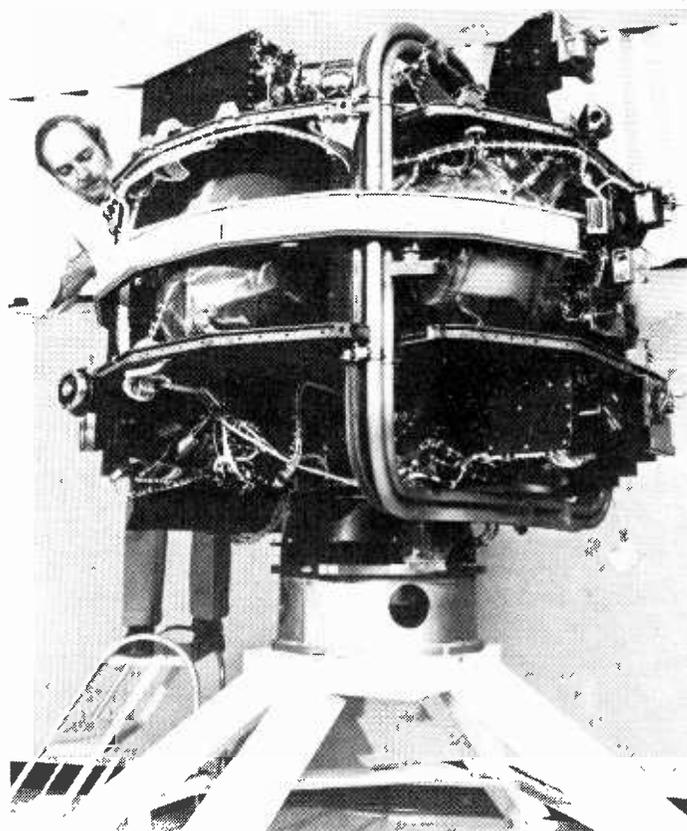

*Installing an ozone sounding instrument on NASA's Atmosphere Explorer-E satellite that will be investigating the possibility of ozone depletion in the stratosphere.*

## Radar probes Ganymede

Jupiter's largest moon, Ganymede, has been probed by radar for the first time and found to have a rougher surface than the inner planets. The big Jovian satellite, slightly larger than the planet Mercury, is considerably rougher than Mercury, Mars or Venus, the most likely possibility for the surface being rocky and/or metallic material embedded in a top layer of ice. The Ganymede test over a distance of 600 million kilometres was conducted on six nights, employing the 64-metre antenna at the NASA-Jet Propulsion Laboratory deep space network tracking station at Goldstone, California. The finding is particularly interesting in view of verification by Pioneer 10 and 11 flybys that Jupiter itself is gaseous with no solid surface that could sustain a radar echo.

The material on Ganymede is probably meteoric in origin. Ganymede scatters to Earth 12 per cent of the power expected from a conducting sphere of the same size and distance. Roughness is made evident in this experiment by the presence of echoes away from the centre of the disc. A perfectly smooth disc would reflect only a glint from the centre. A rough one reflects power from the entire disc. A 400-kilowatt beam of microwaves with a wavelength of 12.6cm was directed at Ganymede.

## Mars probe launched

America's most ambitious unmanned space venture is underway with the launch during August and early September of two Viking spacecraft. The year long 815-million-kilometre journey will culminate with the landing of an automated laboratory on the surface of Mars in the summer of 1976. The instrument-laden craft will take pictures and conduct a detailed scientific examination of the planet, including a search for life. Viking 2 will arrive at Mars seven weeks after Viking 1. Each will divide into an orbiter and lander vehicles. The main orbiter communications system is a two-way S-band, radio link providing Earth command, radio tracking and scientific data return. This link uses either a steerable 1.5m high-gain dish antenna or an omni-directional low-gain antenna. Transmission rates at S-band vary from 8.3 to 33.3 bits per second for engineering data to 2,000 to 16,000 bits per second for Lander and Orbiter science data. The radio science investigations will make use of Orbiter and Lander communications equipment to measure Mars' gravitational field, determine its axis of rotation, measure surface properties, conduct certain relativity experiments and pinpoint the locations of both Landers on Mars. An X-band radio link will be used to study charged ion and electron particles.

# Television tuner design — 3

## Construction and sound-only version

by D. C. Read, B.Sc.

**Parts 1 and 2 of this article dealt with important aspects of the tuner design, particularly where it differs from the more conventional arrangements, explained circuit operation, and gave oscillograms to illustrate typical performance. Description continues with constructional points and modifications for a varned-capacitor-tuned version and a sound-only unit. Part 4 will detail alignment and use of an optocoupler for mains isolation.**

To help readers build the tuner, a component location diagram, provided with the printed-circuit board\* carries important information concerning specific processes in construction; the uses of this diagram are explained below.

Inspection of the printed-circuit board will show that it has an earth plane covering the whole of the component side; there are also a number of "earth-plane" zones on the wiring side, and it is essential that in the course of wiring-in components these zones are connected through to the main earth plane.

Each of the points at which a through connection must be made (before

mounting near-by components) is indicated in the location diagram by a small triangle; at such points on the board, a short wire link is passed through the hole provided and firmly soldered to both sides. Most, but not all, of the large squares representing inductors in the drawing are flanked by triangles. In these instances, the links ensure that the screening-can lugs and the associated wiring-side zones are properly connected to earth. Sometimes, as with resistors  $R_5$  and  $R_{56}$ , a through connec-

\*Board diagram is available from the editorial office, together with location diagram. Drilled boards are available from the address given in the components list.

tion can be arranged simply by feeding the component lead itself through the board and soldering this on each side.

Several of the through connection points are associated with short sections of copper track which are needed:

- on the wiring side of the board, to provide earth connections for  $C_{59}$ ,  $C_{65}$ ,  $L_{18}$ ,  $Tr_7$  and  $IC_2$ . Both pins 4 of the 8-pin d.i.l. packaged SN72748P and the SN72741P (See Fig.14) require an earth; these two i.c.s replace the SN72747 shown in Fig.2.
- on the component side of the board, to complete the 24-volt supply rail circuit. These are shown in the diagram as broken lines across the top of  $C_{35}$  and along the edge of the board below  $R_{25}$  and  $R_{26}$ .

Two other symbols used in the location diagram to indicate particular aspects of construction are:

- a diagonal cross drawn at one end of some components. This shows that the appropriate connecting "leg" in each instance has to be shortened and bent so that it can be soldered directly to the earth plane (on the component side).
- a square, which shows the position of a monitor point, provided with stand-off resistor for oscilloscope measurement.

In addition to the copper-track links already mentioned, a long wire link must be fitted to carry the a.g.c. circuit output to the  $Tr_1/Tr_2$  i.f. stage. The two points which require this interconnection are terminated in copper "pads" on the board; one of these is beneath  $C_{65}$  (the large  $1\mu F$  component to the right of the u.h.f. module) and the other is marked "a.g.c." (at the junction of  $C_{13}$  and  $R_6$ ). A further long wire link is needed if the group-delay equalizer has been omitted from the circuit. This is required to join the output of the  $Tr_4/Tr_5$  stage to the input of  $Tr_6/Tr_7$ , and runs from  $R_{28}$  to  $C_{34}$ .

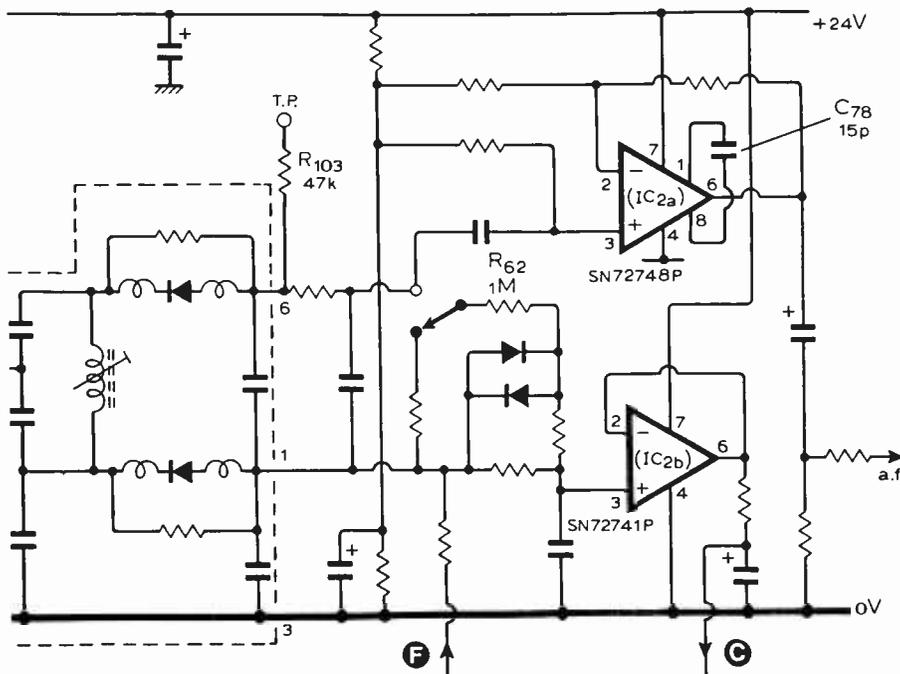


Fig. 14. Changes and corrections to the sound/a.f.c. circuit given in Fig. 2 (Part 1). Separate components in the  $IC_{2a}$  and  $IC_{2b}$  positions take advantage of better noise performance available from the SN72748P acting as the audio output amplifier.

L<sub>19</sub>; 40 turns 30 s.w.g. enamel, 15mm  
 L<sub>20</sub>; 12 turns 20 s.w.g. enamel, 15mm  
 L<sub>21</sub>; 2 $\frac{3}{4}$  turns 30 s.w.g. enamel, interwound

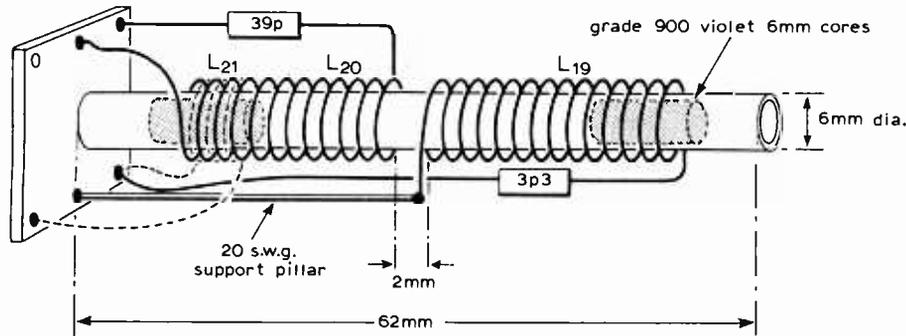


Fig. 15. Dimensions and form of L<sub>19</sub>/L<sub>20</sub>/L<sub>21</sub> coil construction.

In the circuit of Fig. 2 the following components were omitted: C<sub>77</sub>, which should decouple the junction of R<sub>1</sub> and R<sub>2</sub> to earth, C<sub>40</sub>, which should decouple Tr<sub>9</sub> base to earth, R<sub>108</sub>, which should be in series with the tuning voltage line at point F, and R<sub>109</sub>, which feeds the sound a.f.c. discriminator output on pin 6 to a test point.

### Pre-assembly of inductor circuits

In addition to winding the coils (see parts list), further assembly work is required for some inductors before they are mounted on the circuit board. In most instances, these sub-assemblies are formed simply by adding a capacitor which is mounted inside the screening can in one of the two ways outlined below. Construction of the L<sub>19</sub>/L<sub>20</sub>/L<sub>21</sub> assembly and of the L<sub>18</sub> discriminator circuit, however, is more involved, and requires separate description.

For the more simple inductors the choice of construction depends on whether the inductor and its associated capacitor are in series or parallel. For series combinations use diagonally opposing base pins; from Fig. 2 and the parts list it can be seen that L<sub>1</sub>, L<sub>3</sub>, L<sub>11</sub> and L<sub>13</sub> need to be assembled in this way. Inductors L<sub>7</sub>, L<sub>14</sub>, L<sub>15</sub> and L<sub>17</sub> are parallel-connected to their capacitors and wired to adjacent base pins. Inductors L<sub>9</sub>, L<sub>10</sub> and L<sub>12</sub> also have parallel capacitors, and as the Neosid type E-2 formers used for these have an off-centre stack, there is room for the added component inside the can. But for these components it is just as convenient to solder the capacitors across the inductor connection pins which will be proud on the wiring side of the board.

As explained more fully elsewhere, proper operation of the sound trap/sound take-off circuit obtains when phase cancellation occurs precisely at the sound carrier (i.f.) frequency, and this in turn depends on the degree of coupling between L<sub>19</sub> and the L<sub>20</sub>/L<sub>21</sub> pair. Fig. 15 shows how the three coils are wound on the common former and are connected to associated capacitors C<sub>19</sub> and C<sub>20</sub>. Typical dimensions for the coils and their spacing are also given. To facilitate a change in spacing which may be advantageous during adjust-


ment of the circuit as described in step 7 of the line-up instructions (part 4), the upper coil can be wound over a paper tube wrapped round the former stack, and subsequently fixed by a coating of Denfix or clear Bostic when the optimum coupling conditions have been established by measurement.

Rigid construction of the discriminator assembly (L<sub>18</sub> and components enclosed by broken lines in Fig. 2) before installation on the board is essential: any change in circuit parameters here, such as might be caused by relative movement, could spoil the performance of the tuner.

Two views of the coil and its associated circuitry are given in Fig. 16, which shows diagrammatically the assembly from opposite corners of the former base. The assembly should be built up in three stages, as detailed below.

— Insert an 18 s.w.g. wire through hole 5 in the former base, solder it to the metal insert and cut it so that it reaches nearly to the top of the stack; this wire simply acts as a support and is not part of the circuit. Wind the 10 $\frac{1}{2}$ -turn coil as shown and temporarily secure the ends by wrapping them round the support wire so that

Fig. 16. Opposing views of L<sub>18</sub> assembly identifying associated components and their positions.

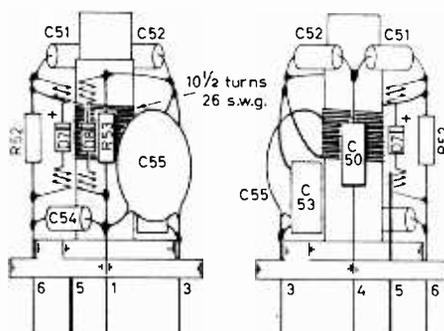

the coil turns are held tightly in position. Completely coat the coil in cement (Denfix) and leave overnight to dry thoroughly.

- Free the coil ends and cut back the support wire to a length roughly as in the drawing. Now connect and arrange into the positions shown, resistors R<sub>52</sub> and R<sub>53</sub>, ceramic capacitors C<sub>53</sub> and C<sub>55</sub>, and diodes D<sub>7</sub> and D<sub>8</sub>, each with leads formed into miniature coils as explained in part 1. Cover these components with cement, making sure that wiring points to which the remaining capacitors will be soldered are kept clear. Leave the assembly to dry.
- Finally, connect C<sub>50</sub>, C<sub>51</sub>, C<sub>52</sub> and C<sub>54</sub> so that they are held in position as firmly as possible but do not cement them because the polystyrene dielectric might then be dissolved.

The assembly is then connected into the circuit, (making sure that pin numbers on the base correspond with those marked on the board) where it is held by means of 6BA screws in the tapped holes provided. The screening can is added later and held separately by 6BA screws and nuts passing through two more holes in the board.

### Tuning-voltage supply arrangements

The later steps in the line-up procedure, to be given in part 4, require reception of a transmitted signal, and therefore the switched voltages available from the tuning supply circuit (shown in part 1) must be pre-set to the appropriate values for the required transmissions. Values given for the fixed resistors feeding the pre-set controls R<sub>90</sub>, R<sub>93</sub>, R<sub>96</sub> are suitable for the London area (Crystal Palace) transmitter; for other localities, these values will have to be changed as follows.

From Fig. 17 the tuning voltages which correspond to the channels chosen. If a wanted channel has a number more than 45 to 50, add one or two 5.6-volt zener diodes in series with those at D<sub>12</sub> and D<sub>13</sub> to increase the tuning supply-rail voltage. Calculate new fixed-resistor values (for R<sub>89</sub>/R<sub>91</sub>, R<sub>92</sub>/R<sub>94</sub>, etc), taking the current through each resistor chain to be 0.5mA, so that suitable voltages are then available for final adjustment by the pre-sets to the precise values found above.

Current from Tr<sub>20</sub> through the zener circuit should be held at about 6.5mA to give the required zero temperature coefficient of the zeners. Therefore, the resistance of each pre-set control divider chain must be increased to maintain a total supply to the four chains of about 2mA. The increase will be up to, say, 40kΩ for a 22V rail with each variable changed to 10kΩ to give the same control range.

For added convenience of operation, push-button units can be obtained (from Manor Supplies) in which each button also actuates a separate multi-turn variable resistor and a common



# Antex Soldering Irons are Presents worth receiving

Even Santa Claus would be delighted with a present like this. Antex Soldering Irons are about the most versatile gifts you could receive and are as reliable as Christmas itself.

### Model X.25

- Near-perfect insulation Breakdown voltage 1500A.C. Leakage current 3.5µA.
- Top efficiency in heat transfer. Element slides inside the soldering bit. 25 watts but equivalent in heat capacity to 60 watts.
- Highgrade phenolic handle (own moulding!) Stainless steel shaft -3 core 0.4mm flexible lead.
- Iron-coated bits that do not stick to the shaft but slide on and off easily. 3 tip sizes 2.4, 3.2 and 4.7mm.
- For dual-in-line de-soldering the model X.25 can be fitted with special bits 14A and 14B.

PRICE £2.67 (0.22)

Our catalogue gives further particulars.



## The Antex Range

All prices include V.A.T. P.&P. in brackets



**MODEL C** - 15 watt miniature soldering iron  
Bits slide on and off stainless steel shaft. Elements fitted inside steel shaft for efficient heat transfer. Length 16 cm. Complete iron with 2.3 mm. iron-coated bit £2.67 (0.22) Spare elements £1.20 Spare bits £0.35 (nickel) £0.45 (iron-coated).



**MODEL G** - 18 watt miniature soldering iron  
Looks exactly like model C, but because of the extra 3 watts should be kept going all day on repairs or production. Stainless steel shaft - fitted with standard iron-coated bit 2.3 mm. £2.94 (0.22) Spare elements £1.47 Spare bits 2.3, 3 or 4.7 mm. £0.45.




**MODEL CCN** - 15 watt miniature soldering iron  
Unique - ceramic shaft - no measurable leakage - capacitance 30 pf. Tested at 2000 volts A.C. Length 16 cm. Complete with standard iron-coated bit 2.3 mm. £3.15 (0.22) . 4 other slide-on and-off bits available from £0.45 Spare elements £1.69. Suitable for the most delicate soldering job imaginable.



**MODEL X.50 T.C.** - 50 watt temperature controlled soldering iron  
Leakage current negligible - Temperature controlled to 2°C either way. Ceramic shaft inside stainless steel shaft. Tested at 2000 volts A.C. Complete with 3 mm. iron-coated bit £9.69 (0.27) Normally set at 370°C Length 20 cm. Weight 50 gr.

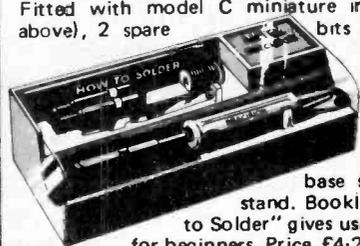**MODEL SK.1 - SOLDERING KIT**  
Fitted with model C miniature iron (see above), 2 spare bits 2.3 and 4 mm., heat sink, reel of solder. Plastic base serves as stand. Booklet "How to Solder" gives useful tips for beginners. Price £4.25 (0.42)



**MODEL MLX** - 12 volt - 12 watt Soldering iron with 4½ mtrs. lead and crocodile clips Useful for repairs on motor cars, boats, model trains, etc. Can be worked off car-type battery. Complete with 3.2 mm. bit £3.27 (0.30) Two other bits available 2.4 and 4.7 mm. £0.47 each. Packed in a plastic wallet with guide "How to Solder".



**STAND S.T.3**  
High grade insulation material. chromium plated steel spring. Suitable for all our models. Replaceable sponges, space for spare bits. Complete £1.21 (0.24)




Please send the following: \_\_\_\_\_

Please send the ANTEX colour catalogue.

I enclose cheque/P.O./Cash (Giro No. 258 1000) \_\_\_\_\_

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

From radio or electrical dealers, car accessory shops or in case of difficulty direct from: ANTEX LTD. FREEPOST, PLYMOUTH PL1 1BR (no stamp required) Tel. 0752 67377.

WW12

WW-091 FOR FURTHER DETAILS

From Canada's largest manufacturer of video monitors, Bell & Howell present the extensive Electrohome range.

# Questions to ask before buying a video monitor

## It's an impressive number of models but what about the performance?

The performance price ratio is equally impressive – perhaps the best in the CCTV business. More than 80% of the screen has a resolution capability greater than 1,000 lines and on the large monitors the minimum brightness in the white area is 130ft lamberts (under accepted test conditions). Other features include high video input impedance and external sync input.

## I need a large screen. For what application has Electrohome's 23 in monitor been designed?

The long-term reliability of the EVM23 and EVM23AG make either ideal for surveillance systems in banks, factories and department stores. They are equally at home in the message centres of the world's airports, in schools and broadcast studios. Both models have a durable outer casing and the EVM23AG has a special tube face to reduce reflections – important where lights or windows may reflect on to the screen. Lockable front panels make them ideal for unattended locations.

## What about mounting? I need the utmost flexibility.

There is no problem. Electrohome have wall and ceiling mount assemblies that allow a monitor to be swivelled or tilted about its centre of gravity. For mobile work like presentations and exhibitions there is an adjustable stand to support the EVM23 at four different heights – 63in, 55½in, 54in, and 46½in. If your requirement is for rack mounting versions, all sizes below 23in are available in rack mount options.

## How do I decide the screen size to suit my application and do Electrohome have a complete range?

Screen size depends largely on viewing distance and available space. If the minimum viewing distance is 10ft then you should use a large monitor – 17in or above. At closer distances or where space is limited a 9in or 11in screen may be more suitable. If you intend TV to teach or persuade, avoid the mistake of sacrificing visual impact for the sake of economy. Electrohome's range is one of the most comprehensive available with seven different sizes from 9in to 25in (two in colour).

## What facilities do Electrohome's small screen monitors offer?


To complement this outstanding specification we have not forgotten the importance of switchable A-B inputs, switchable underscan, DC restoration and good geometry. Also the wide input sensitivity range and the input ground which can be 'floated' will look after less favourable operating conditions. Input power requirement is also tolerant within 95–130V 185–265V, 50 60Hz.

## When should I use a colour monitor?

We'll ask a question which will help you decide. Everything you show on TV will be shown with a purpose. Will colour help to achieve that purpose? If so, use colour – and choose an Electrohome colour monitor because, simply, you cannot make a better choice. (This is only part of the answer to a complex question which we would enjoy discussing with you in proper depth.)
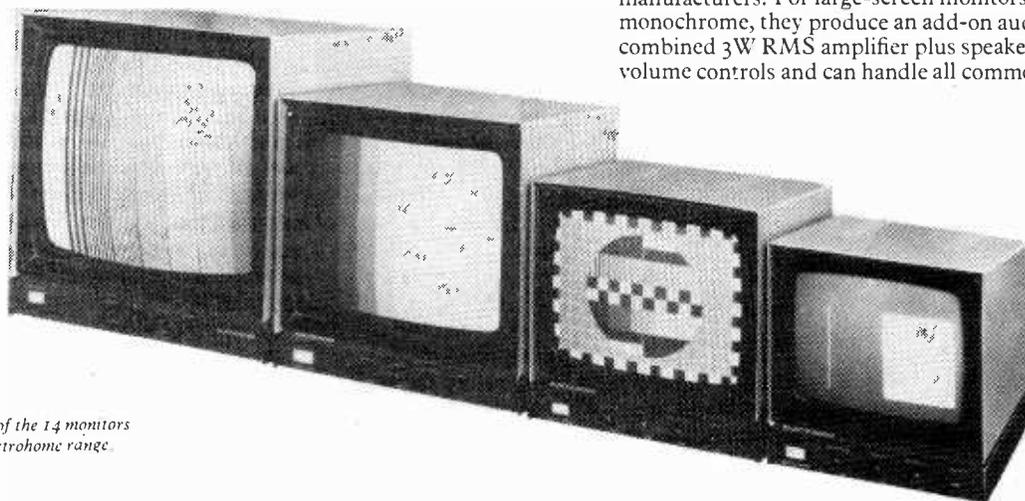
## What about audio? You have convinced me that the video signal is first-class, but I need to hear the sound.

Electrohome haven't overlooked audio, like some manufacturers. For large-screen monitors, both colour and monochrome, they produce an add-on audio pod with a combined 3W RMS amplifier plus speaker unit. It has tone and volume controls and can handle all common audio inputs.



Just four of the 14 monitors in the Electrohome range.

Bell & Howell A-V Ltd.,  
Freepost, Wembley, Middlesex HA0 1BR  
(no stamp required).



**BELL & HOWELL**

More questions? Write to us for the address of your nearest Bell & Howell Video Centre. You'll get the answers in the most convincing way possible – by seeing and hearing how Electrohome's monitors perform.

# Specifications: the Electrohome monitor range from Bell & Howell

Models	Screen size	Specification	Individual features
<b>EVM-910</b> (freestanding) <b>EVM-910R</b> (rack mounted) <b>EVM-910R2</b> (double rack mounted)	9in (21.7cm) 38in <sup>2</sup> (245cm <sup>2</sup> )	Input sensitivity 0.25V - 4V pp composite or separate sync. signal (sync. negative). Resolution in excess of 1,000 lines in central 80% of display area at 5ft lamberts; more than 860 lines at 30ft lamberts brightness; capability 55f. lamberts in white area of test pattern (23 in monitor 130ft lamberts). EHT regulation, switchable scan size, selectable black level clamp and 15Mhz bandwidth ± 3dB. Operating temperature 0-50°C, humidity 0-98% non-condensing.	2 composite video inputs or 1 video blanked input plus sync.
<b>EVM-1110</b> (free standing) <b>EVM-1110R</b> (rack mounted)	11in (26.3cm) 61in <sup>2</sup> (393.5cm <sup>2</sup> )		
<b>EVM-1410</b> (free standing) <b>EVM-1410R</b> (rack mounted)	14in (32.2cm) 82in <sup>2</sup> (529cm <sup>2</sup> )		
<b>EVM-1710</b> (free standing) <b>EVM-1710R</b> (rack mounted)	17in (41.3cm) 149in <sup>2</sup> (961cm <sup>2</sup> )		
<b>EVM-23</b>	23in (57.5cm) 282in <sup>2</sup> (1819.3cm <sup>2</sup> )		Lockable control cover
<b>EVM-23AG</b>	23in (57.5cm) 282in <sup>2</sup> (1819.4cm <sup>2</sup> )		Special tube face to reduce reflections. Lockable control cover
<b>ECV-19P</b> (colour)	19in (48.26cm) 185in <sup>2</sup> (1193.25cm <sup>2</sup> )		Input sensitivity 0.5V - 2V pp composite or separate sync. signal (sync. negative). D.C. restoration: keyed clamp back porch maintains black level shift to less than 2% of peak luminance from 10% to 90% APL. Colour temperature: 6500°K. Continuously adjustable to 9300°K.
<b>ECV-25P</b> (colour)	25in (62.5cm) 315cm <sup>2</sup> (2032cm <sup>2</sup> )		

## Accessories for EVM-23, ECV-19P and ECV-25P

<b>ECM-2</b>	Ceiling mount
<b>EWM-1</b>	Wall mount
<b>EVSA-2</b>	Speaker/amplifier pod. 3W RMS amplifier available for large monochrome and colour monitors.
<b>EPC-1</b>	Pulse-Cross kit. Allows VTR users to optimise tracking and tape tension (EVM-23 only).



# BELL & HOWELL

WW-087 FOR FURTHER DETAILS

# IF THE NAKAMICHI CAN CAPTURE HIM, THINK WHAT IT'LL DO FOR BEE THOVEN.

Most portable cassette decks are quite happy recording the odd pop song.

But give them something truly challenging, and you soon realize their shortcomings. Fine, if you're content to be unambitious. But at Nakamichi we think you should be able to record any sound you want. Which is the reason why we produced the Nakamichi 550.

From a mouse squeak to the triumphant sounds of Beethoven, you can record it all on a Nakamichi 550.

Its peak level meters have a range of 45dB. Its signal-to-noise ratio is more than 60dB. Its microphone inputs have a dynamic range of 125dB.

Wider ranges than any other portable cassette deck in the world.

And that's not all. The 550 is also the only portable cassette deck with 3 microphone inputs. And a tape end alarm with pre-set timer.

The only one too, with a button that shows how much of your cassette you've used.

And Nakamichi's exclusive record/playback head. And it's the only one with a battery life that can give you up to 15 hours continuous playing.

When you try the Nakamichi 550, you'll know why it costs £236+ VAT. Suddenly, other portable cassette decks look like toys.




NAKAMICHI

THE WORLD'S MOST VERSATILE PORTABLE CASSETTE DECK

Natural Sound Systems Limited,  
Strathcona Road, North Wembley, Middx. HA9 8QL. 01-904 0141.

WW-092 FOR FURTHER DETAILS

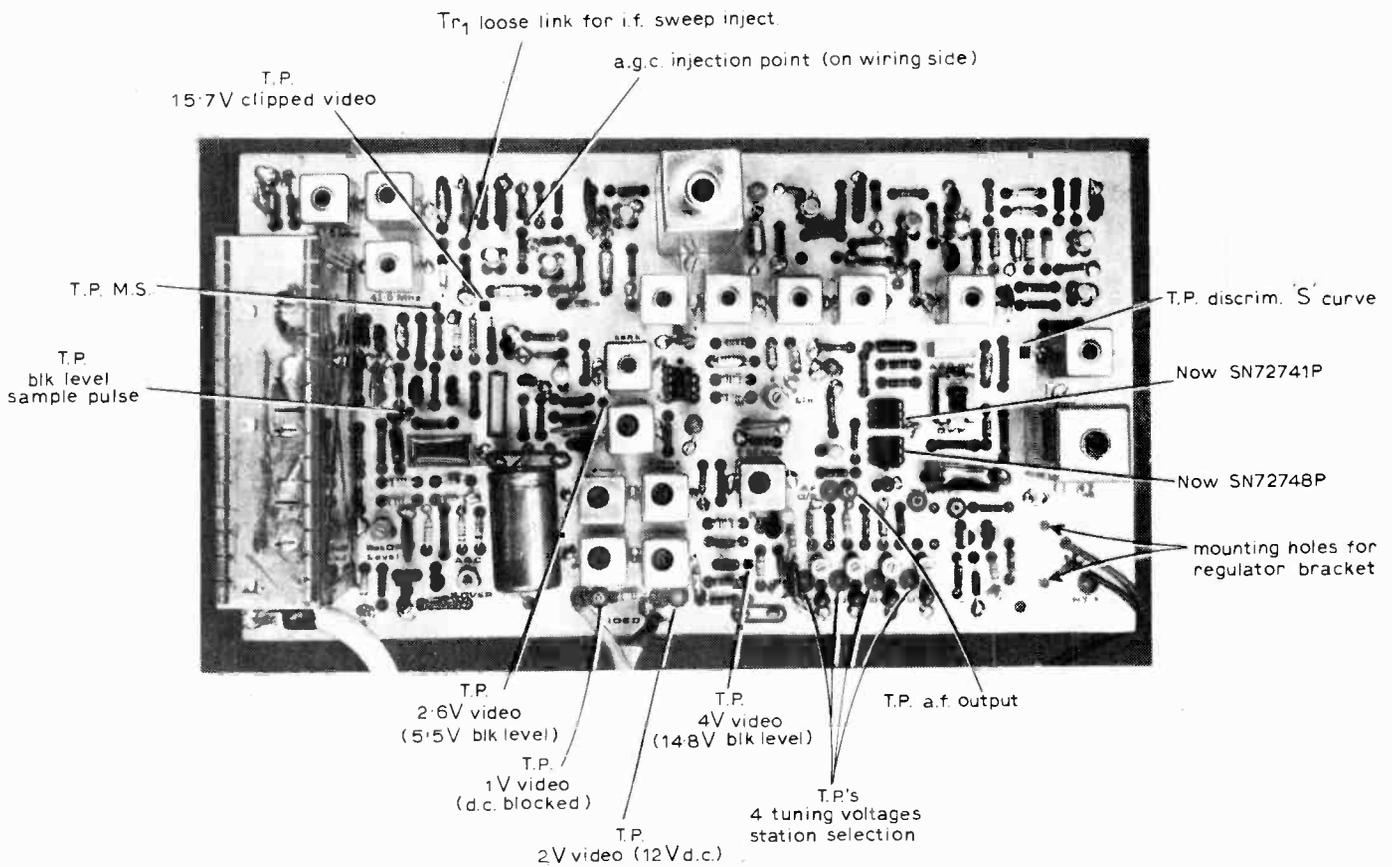

a.f.c.-inhibit switch. When a button is pressed, it can then be rotated, acting as a fine-tuning control, to give any voltage up to the maximum available.

The pre-set variables in these units have resistance values around 50kΩ, and hence draw a much smaller current than the control chains specified in the published tuner circuit. To compensate for this, the standing zener current must again be adjusted to 6.5mA, in this instance by adjusting the value of R<sub>88</sub> feeding Tr<sub>20</sub> emitter (an increase in value causes a decrease in current).

**MODIFICATIONS**


**Varied-capacitor module**

Although varicap-operated u.h.f. tuner circuits such as the Mullard ELC1043/05 used here are very convenient, especially for remote-control arrangements, they do have disadvantages, mainly in that they are prone to spurious phase modulation.

The ELC1043 circuit principally consists of four half-wave tuned lines in cascade, each with a fixed capacitor at one end and a capacitance diode at the other acting as the control variable responding to the separately-applied tuning voltage (which is push-button switched and includes a slowly-varying a.f.c. correction signal). The incoming r.f. signal, with its main spectral components as illustrated in Fig. 18, passes through these lines superimposed on the direct control voltage; the varicap diodes can thus be affected by amplitude changes in the vision carrier

Photograph of component side of board showing approximate positions of test points and the signals they carry. When completed, the board is fitted on pillars into the bottom of a U-section aluminium sheet screen which covers the whole of the wiring side and extends above the components.

Fig. 17. Broken line indicates tuning voltage versus frequency and channel number for ELC1043 u.h.f. tuner. Shaded area shows spread quoted for the ELC1043/05.

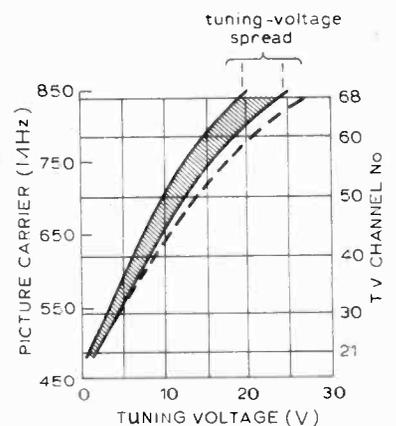

envelope as well as by the control-voltage.

Thus, if the incoming vision carrier amplitude is very high, it causes detectable sympathetic changes in the resonance of the lines, and hence variations in the phase of their output. In practice, the rate of phase change will be mainly at the 50-Hz field frequency (2 fields = 1 picture) which predominates at the low end of the spectrum. Such phase variation does not usually affect the a.m. picture information (unless a phase-locked-loop demodulator is being used), but it does interfere with the sound because it is detected as frequency modulation. Given a sufficiently large phase variation, the result is the well-known sound 'buzz.'

This type of interference may be prevented by suitably arranging the

r.f./i.f. a.g.c. overlap (see Fig. 13 in part 2) to give as small an r.f. signal amplitude as possible. But if the amplitude is reduced too much, the signal-to-noise performance is degraded.

To test the relative merits of varicap and varied-capacitor u.h.f. tuners, and especially to sample the possible improvements in tuner performance with regard to the problem mentioned above, a second circuit to this overall design was constructed but with the varicap module replaced by a "mechanical" module taken from a commercial receiver and connected to the board by means of flying leads. (The component used was a Mullard type AT6382 -41-PB.)

Extensive tests were carried out, using locally-generated r.f. feeds as well as 'off-air' signals and with both high

## Components

Resistors		
qty	value	reference
Mullard MR25 metal film $\pm 2\%$ 0.4W, or equivalent metal film $\pm 5\%$ 0.25W.		
1	10	107 <sup>1</sup>
2	47	13, 18
1	75	88
9	100	11, 41, 45, 47, 50, 51, 58, 66, 108
3	150	31, 32, 68
2	180	3, 14
1	300	4
1	390	8
3	470	6, 48, 74
2	750	2 <sup>5</sup> , 28
1	820	46
8 <sup>2</sup>	1k	1, 7, 9, 20, 102, 104, 105
3	1.5k	25, 29, 30
2	1.8k	77, 79
2	2k	26, 91 <sup>3</sup>
2	2.2k	5, 67 <sup>4</sup>
3	3.3k	27, 40, 106
1	3.6k	22
1	4.3k	94 <sup>3</sup>
4	4.7k	24, 59, 63, 70
1	5.6k	67 <sup>7</sup>
2 <sup>2</sup>	6.2k	95
1	6.8k	21
6	10k	10, 39, 55, 56, 64, 73
1	11k	97 <sup>3</sup> , 3, 5
1	12k	84
1	13k	92 <sup>3</sup>
1	15k	43
1	16k	89 <sup>3</sup>
2	18k	23, 71
6	22k	16, 34 <sup>5</sup> , 44
4	33k	49, 86, 87
1	39k	37, 38, 42, 81
3	47k	12
5	100k	35, 36, 103 <sup>6</sup>
		15, 33, 52, 53, 82
Mullard MR30 metal film or equivalent $\pm 5\%$ 0.25W		
3	150k	72, 80, 85
1	220k	61, 65
1	270k	69
2	470k	54, 101
1	560k	57
2	1M	62 <sup>5</sup> , 75
Erie carbon $\pm 5\%$ 0.33W		
1	1.5M	62 <sup>8</sup>
2	2.2M	60, 76 <sup>5</sup>
Carbon potentiometer		
1	2k	see note 2
Cermet potentiometers		
1	50k	19
1	1k	78
4	5k	90, 93, 96, 99
1	10k	17
1	50k	83

## Notes:

- Used with MC7824CP regulator.
- One used for a.g.c. test point.
- For London transmissions.
- Used when D<sub>9</sub> is used.
- Changed value from that shown in Fig. 2 (part 1).
- Additional component to those in Fig. 2 (see text).
- Used when D<sub>9</sub> is not used.
- Used with mechanical vane tuner, see inset Fig. 2.

Capacitors		
qty	value	reference
0.5p inter-track on p.c.b.		
Erie tubular ceramic NO33AD		
2	2.2p	41, 53
2	3.3p	8, 19
polystyrene $\pm 2\%$ 125V (Sufflex, Salford, Lemco)		
1	10p	23 <sup>1</sup>
1	12p	50
2	15p	78 <sup>4</sup>
3 <sup>2</sup>	20p	49
1	22p	32
3	27p	30, 39, 42
4	33p	6, 26 <sup>6</sup> , 44, 62
2	39p	20 <sup>4</sup> , 29
2	51p	51, 52
1	68p	33
3	100p	22, 28, 54
1	120p	56
2	150p	5, 64
1	200p	31
1	220p	46
1	470p	24
1	680p	21 <sup>4</sup>
3	1n	7, 11, 14
disc ceramic $\pm 25\%$ 500V Erie K7004/831		
11	2.2n	13, 15, 16, 18, 37, 40 <sup>6</sup>
		43, 45, 47, 48, 76 <sup>3</sup>
5	10n K7004/811	9, 12, 17, 66, 38
8	100n K7004/811/T/30V	1-4, 27, 55, 68, 77 <sup>5</sup>
polyester metallized $\pm 10\%$ 100 or 250V (Mullard)		
1	10n type 344 41103	58
1	330n type 344 25334	63
2	1 $\mu$ type 344 25105	59, 65
tantalum $\pm 20\%$ Union Carbide or RS Components		
1	4.7 $\mu$ 35V	61
9	10 $\mu$ 25V	25, 36, 60, 67, 70-73 <sup>4,5,7,5</sup>
1	22 $\mu$ 15V	57
2	47 $\mu$ 6V	34, 74
electrolytic, Erie, Mullard or equivalent		
1	150 $\mu$ 25V	69 <sup>4</sup>
1	1000 $\mu$ 25V	35

## Notes

- Removed when c.r.o. connected.
- One used for C<sub>5</sub> a.o.t., another to resonate L<sub>16</sub> in test procedure.
- Used with regulator.
- Changed value from that shown in Fig. 2.
- Additional component to those in Fig. 2 (see text).
- Shown as C<sub>36</sub> in Fig. 2, part 1.
- The 22 $\mu$ F/15V tantalum capacitors may be retained for channels requiring less than 15V.

Semiconductor devices		
qty	type	reference
<i>diodes</i>		
4	1N916	7, 8, 15, 16
2	AAZ13 or OA47	5, 6
1	BZY88 C3V3	14
2	BZY88 C5V1	10, 11
5 <sup>1</sup>	BZY88 C5V6	2-4, 12, 13
1	BZY88 C12V	1
1	BZY88 C16V	9
<i>transistors</i>		
1	BF167	2
7	BF173	1, 3, 8-12
3	2N3904 or BC107-8-9	4, 6, 15
8	2N3906 or BCY70-1-2	5, 7, 13, 14, 17-20
1	2N3819	
<i>integrated circuits</i>		
1	MC1330P 8-pin d.i.l. (Motorola)	1
1	SN72748P 8-pin d.i.l. (Motorola)	2a
1	SN72741P 8-pin d.i.l. (Motorola)	2b
1	MC7824CP (optional)	3
1. Up to three extra zener diodes are needed for higher tuning voltages.		
<i>Inductors (all require cans) reference</i>		
Neosid 4mm dia. 6mm leg spacing		
18mm tall, grade 900 violet core		
(u=11), Neosid or equivalent		
15	turns 26s.w.g.	
8	turns 34s.w.g.	2
30	turns 34s.w.g.	3
40	turns 40s.w.g.	4
5 $\frac{1}{4}$	turns 26s.w.g.	6
9	turns 26s.w.g.	7
4	off, 11 turns 26s.w.g.	14-17
6mm dia.		
10	turns 26s.w.g. 35mm tall	18 (Fig. 16)
See Fig. 15 for detail. 62mm 19-21 tall		
Neosid E2 assemblies		
9 $\frac{1}{2}$	+ 9 $\frac{1}{2}$ turns 16/48 litz	8
pile wound		
18	turns 16/48 litz	9
wound		
33	+ 33 turns 16/48 litz	10
wound		
27	turns 16/48 litz	11
wound		
19	+ 19 turns 16/48 litz	12
wound		
31	turns 16/48 litz	13
wound		

## Other parts

u.h.f. tuner Mullard ELC1043. (If ELC1043/05 is used drill extra hole in board next to test point position.)

a.f.c. switch 1 pole 2way photocoupler Mullard CNY48 printed board (available at £6 inclusive from M. R. Sagin, 11 Villiers Road, London NW2, together with component location diagram). Kits, or parts separately, including a sound-only version, are available from Manor Supplies, 172 West End Lane, London NW6 1SD, telephone 01-794 8751.

Vision monitor used with prototype was Decca CS2240/L, costing about £280 including 8% v.a.t.

and low incoming levels. From these tests, it was evident that the performance benefits — as distinct from possible financial ones — were not as marked as expected.

The first main improvement was in signal-to-noise — of 3 to 4dB — obtained from transmissions received at high aerial-strength (e.g. the signal from a transmitter at 'line-of-sight' distance). Reception conditions as beneficial as this, however, are the exception rather than the rule; generally, the limiting factor in respect of noise performance is already realized as a function of received signal level, and the signal-to-noise figure which can be achieved using a varicap-tuned front end is the best possible given that input level. Hence, the noise cannot be further reduced by changing the input circuit to one using a varned capacitor.

The second main improvement was discussed earlier regarding r.f./i.f. a.g.c. overlap setting. Remember, with low r.f. but high i.f. gain, the problem is r.f.-circuit mixer noise whereas with gain conditions reversed, the result is buzz-on-sound. Higher r.f. levels could be permitted in the mechanical tuner so allowing greater level range to be accommodated between the onset of adverse effects. But, except in places where reception conditions for wanted stations are greatly different (or change considerably with time), this extra range is of no particular advantage because the a.g.c. circuit can so easily be set for a satisfactory compromise which includes the highest and lowest levels normally received.

Under certain conditions, then the different operating characteristics of mechanical tuners could be useful in obtaining the best possible video signal-to-noise figure. Added to this is the saving in component cost which would be made if a mechanical module were already to hand or cheaply available.

In choosing such a module, check that it includes a varicap diode for a.f.c. correction. For constructors who wish to take up this option, therefore, the necessary circuit changes have been detailed in Fig. 2. They involve the small differences in value for  $C_5$  (which could accommodate the capacitance introduced by about 6 inches of connecting cable),  $R_3$ , the alternative a.f.c. circuit catching diodes as detailed by the inset diagram in Fig. 2,  $Tr_{19}$  and  $Tr_{20}$  plus,  $R_{87}$  to  $R_{100}$  and associated capacitors with the zener diodes omitted.

### Sound-only tuner

Some readers may wish, at least initially, to build only those parts of the circuit necessary for producing a sound signal; the vision side could be added at a later date. The circuit changes necessary are as follows. Referring separately to the four sections of circuitry in Fig. 2

—**top section** — retain except for  $R_9$ ,  $Tr_3$  and  $L_4$ . The i.f. output from  $C_{14}$  is then connected directly to the emitter of

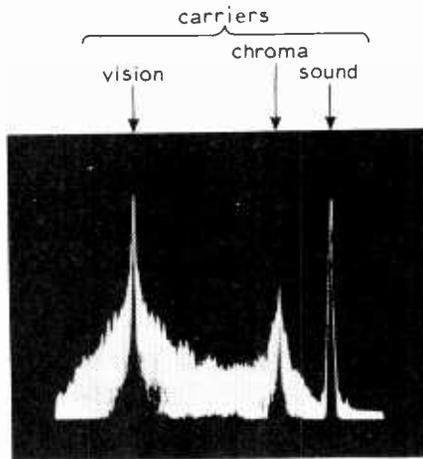


Fig. 18. Spectrum of r.f. television transmission showing distribution and relative energy content of side bands about the vision carrier (left), the colour subcarrier (centre), and the sound carrier (right).

$Tr_8$ , via a short wire link on the wiring side of the board.

- second section** — omit entirely ( $C_{17}$  to  $C_{35}$ ,  $R_{13}$  to  $R_{33}$  etc).
- third section** — retain all this section, making sure  $R_{34}$  is  $22k\Omega$ , not as incorrectly shown in Fig. 2, and incorporating the changes to the sound and a.f.c. output circuits already called for.
- bottom section** — omit the part up to the  $R_{80}/R_{81}$  divider, retaining all the circuit including, and to the right of,  $C_{66}$ . The temporary divider chain marked 'a.g.c. test' in Fig. 2 becomes a permanent part of the circuit and is used to set the gain of the sound-only tuner.

Line-up of this simplified tuner is very easy and details will be given subsequently.

## Announcements

Allen-Bradley Electronics Ltd, Pilgrimsway, Bede Industrial Estate, Jarrow have announced that they are to phase out production at Jarrow of the "Morganite" range of carbon composition resistors, the last of their important products supplied to the consumer goods sector.

National Semiconductor U.K. Ltd, 19 Goldington Road, Bedford MK40 3LF has formed a new group to produce **electronic subsystems**. Known as The Module Products Group, it will produce modules to meet the needs of home appliances, entertainment systems, automotive products, telecommunications and military equipment.

Reaching decisions on the technical merits of introducing hybrid microelectronics into equipment, assessing alternative approaches, estimating likely costs and identifying the right suppliers can be difficult problems for electronic equipment designers and manufacturers. Now available is a comprehensive, independent report dealing with these problems which has just been completed by the Electronics Technology Department of the Electrical Research Association Ltd, Cleeve Road, Leatherhead, Surrey KT22 7SA.

Plastro Plastics Ltd, 38 Wates Way, Mitcham, Surrey now offer a service for the manufacture of **control knobs**. These can be produced in any thermosetting or thermoplastic material with hot foiled or paint filled legend, metal inserts and bright trimmed discs.

**Sifam Ltd**, Accessories Division, Torquay, Devon has appointed Townsend Coates Ltd, Lunsford Road, Leicester, stockists and distributors for the Sifam range of professional collet knobs.

Bosch Ltd has changed its company name to **Robert Bosch Ltd**, P.O. Box 166, Rhodes Way, Watford, Herts.

As a result of a six-year research programme the Allen Clark Research Centre of the Plessey Company Ltd at Caswell, near Towcester, Northants has now established a complete facility for the design and production of **surface acoustic wave devices** to customers' requirements.

Electroplan Ltd, P.O. Box 19, Orchard Road, Royston, Herts, has been appointed sole UK distributor for the "Powercube" range of power supplies manufactured by Integrated Photomatrix.

**Amateur Computer Club**, 7 Doordells, Basildon, Essex has commenced the design and construction of a low cost computer which appears in a series of articles in the club's newsletter. Membership to the ACC costs £1 and details of the club's activities can be obtained from the above address.

Guest International Ltd, Redlands, Coulsdon, Surrey CR3 2HT, is establishing manufacturing facilities for **carbon film resistors**.

## Books Received

**Radio Construction for Amateurs** by R. H. Warring is a plain-man's guide to understanding and (hopefully) building a receiver. The book contains 27 working circuit designs ranging from a simple crystal set to a f.e.t. receiver and i.c. amplifier. Transistor circuitry is used in all the discrete designs and the text is supplemented with pictorial diagrams for the identification of components. Price £2. Pp. 120 (paperback). Pitman Publishing Ltd, 39 Parker Street, London WC2B 5PB.

**Videotape Recording** by Joseph F. Robinson is aimed at providing a readable exposition for readers with a basic engineering knowledge. The book starts with chapters on tape recording principles and basic requirements of videotape recording. Having gently led the reader up the video path, broadcast and c.c.t.v. formats, f.m. theory, signal systems, and servo-mechanisms are discussed. The book concludes with chapters on errors and correction, cassettes and cartridges, editing, magnetic video discs and slow motion techniques. Pp. 303. Price £5.75. Focal Press Ltd, 31 Fitzroy Square, London W1P 6BH.

**Radio and Line Transmission A** (second edition) by D. C. Green. This is a textbook covering the second-year requirements of the telecommunication technicians' course. The contents have been revised to include chapters on f.e.t.s and i.c.s. and omit those dealing with aerials and power supplies. A number of new questions have also been added to the exercises at the end of each chapter. Price £4.00. Pp. 318. Pitman Publishing Ltd, 39 Parker Street, London WC2B 5PB.

# World of Amateur Radio

## Amateur radio on Oracle

Amateur radio information is now frequently transmitted on the experimental Oracle Teletext service (London region only except when London programmes are networked) on the ITV channel. A multiple-page (often up to 5 pages transmitted sequentially on page 167) provides, typically, details of Oscar 6 and Oscar 7 orbits, information on beacon and repeater stations, and news items. An introduction states: "These pages of information are being transmitted as a service to radio amateurs who have access to, or have built, Oracle decoders." The service was initiated and is being updated by members of the London Weekend Television Radio Club (G4AOT). It is hoped to include h.f. propagation information.

## More countries with novice licences

The Australian Post Office, with the full support of the Wireless Institute of Australia, has now begun issuing "novice licences" to applicants who pass a simple theory examination and a 5 w.p.m. Morse test. The licence permits the use of crystal-controlled transmitters between 3525-3575, 21125-21200 and 26960-27230 kHz with up to 10 watts input (double sideband) or 30 watts p.e.p. single sideband. Licences cost \$A6 plus \$A2 examination fee, half the usual cost of an Australian amateur licence. Purpose of the new facility is to allow applicants "to engage in radio as a hobby on a restricted basis and gain the knowledge and experience necessary to qualify for a normal licence".

Holland is introducing shortly a "D-licence" (communicators) which allows the holder to operate on six crystal-controlled channels in the 144MHz band using n.b.f.m. for fixed or mobile operation with a maximum input of 20 watts. It will be issued to people over 18 years old who have passed a simple technical examination. The Dutch society VERON opposes what it believes is "an ill-considered plan" in conflict with the aims and definition of the amateur service. It would seem that the introduction of the

D-licence is linked with efforts to suppress illegal use in Holland of the 27MHz "citizens band".

The Federal Republic of Germany is making it possible for youngsters between 14 and 18 years old to obtain revocable amateur licences; these permit operation of club stations (under supervision) and, after reaching 16 years, home stations under normal regulations.

## Repeater problems

Although a number of v.h.f. and u.h.f. repeater stations are now licensed and operational in the United Kingdom, there appears to be some dissatisfaction with the way in which the Home Office is regulating these facilities. In particular the ruling that v.h.f. repeaters must normally be spaced at least 100 miles apart is provoking the criticism that little or no account is being taken of the topography: an example is the turning down of the proposed Dover repeater although the area it would cover is screened by hills from the London repeater service area. One result is the recent formation of a UK Repeater Users' Council to act as a ginger group.

## ARRL opposes Docket 20282

The American Radio Relay League in its official submission on the proposed "restructuring" of the amateur radio service criticises FCC Docket 20282 on the grounds that "Whilst idealistic in its goals, it is so unrealistic and potentially diverse as to be unworkable". The ARRL however favours some more moderate revision and improvement of the present licence structure. Instead of the suggested Morse-code-free "communicator" licence, the League puts forward a new suggestion: the idea that applicants should have "familiarity with the Morse code without requiring the ability to send or receive at any speed".

"Amateur radio" ARRL comments "has reached its present high level of technical excellence under a licensing philosophy based upon learning by doing — there must be a balance between the attractiveness of an entry level licence and the motivation of those entering to advance to higher grades".

In view of the recent resignation of Mr A. Prose Walker, W4BW, chief of the FCC Amateur and Citizens Division, it may well mean that FCC will revise its proposals and that some of the more controversial elements of the restructuring will be dropped altogether.

## In brief

With Oscar 6 now in its fourth year of operational service, it is available for use on ascending orbits on Mondays, Thursdays and Saturdays and on descending orbits on Sundays. Oscar 7, one-year-old on November 19, is avail-

able for general use daily except Wednesdays when orbits are reserved for special experiments. It is not necessary to use more than 80 watts effective radiated power, for Oscar communication and excessive power harms the batteries. . . . A supplementary instruction guide to the use of the London v.h.f. repeater, covering recently-added facilities, is available under the title "GB3LO what you hear and why" from Richard Street, UKFM Group (London), "Code 12", 3 White Ledges, London W13 8JB. Price 7p plus large stamped-addressed envelope; add 5p for a copy of the original "GB3LO without tears" and change address to "Code 23". . . . According to William Orr, W6SAI, the original prototype of the famous HRO communications receivers was given the factory designation "HOR" standing for "Hell of a rush" and finally rechristened HRO just in time for its first announcement in the December 1934 issue of QST. Over 10,000 HRO receivers were manufactured during World War II (many of them still in use) . . . World Radio Club — broadcast on the BBC's World Service — has recently enrolled its 23,000th member . . . Address of Rev. G. C. Dobbs (G3RJV) who is secretary of the G-QRP Club and produces the newsletter "Sprat" devoted to low power radio communication is now 8 Redgates Court, Calverton, Nottingham NG14 6LR . . . Several instances of Sporadic E propagation extending up to beyond 144 MHz occurred during the Summer but an outstanding example in the United States was the "fantastic day" of July 20th when widespread Sporadic E lasted many hours on 144 MHz . . . Customs & Excise in turning down RSGB efforts to reduce VAT on amateur radio equipment admit the educational value of amateur radio but nevertheless state that "their considered view is that the activities of ham radio operators are essentially of a recreational nature" — clearly the Customs do not set much store by "learning by doing" . . . Winner of the 1975 BERU contest for British Commonwealth stations was Yuri Blanarovich, VE3BMV who made over 400 contacts. Leading British station was that of Al Slater, G3FXB who was a close second in a hard fought contest that has encouraged the RSGB Contest Committee to retain many of the features of the "BERU" contest for 1976 after originally deciding that a complete overhaul was needed . . . RSGB president for 1976 will be Dr E. J. Allaway, MB, ChB, MRCS, LRCP, G3FKM who for many years has been a noted enthusiast for long-distance operation on the h.f. bands. Membership of the Society at the end of July totalled just over 18,500 of which 1,827 were overseas members. In the year to the end of June 1975, the Society overspent its income by a staggering £18,000 (less a £5,000 VAT refund) which the treasurer says is "the worst year in our history".

PAT HAWKER, G3VA

# High-quality compressor/limiter

A variable law, low distortion attenuator incorporating second harmonic cancellation circuitry

by D. R. G. Self, B.A.

University of Sussex

Compression and limiting play an increasingly important role in the resources of a modern sound studio. The conventional function of signal level control is to avoid overload, but it can be used in the realm of special effects. To date, however, relatively few designs for high-fidelity compressor/limiters have been published.

The main design problem is the voltage-controlled attenuator, v.c.a., which increases attenuation of the input signal in response to a voltage from a control loop as shown in Fig. 1. In limiting, this circuit block continuously monitors the peak output level from the v.c.a. and acts to maintain an almost constant level if it exceeds a threshold value, or, in compression, allows it to increase more slowly than the v.c.a. input signal. This is illustrated in Fig. 2., which shows the input-amplitude/output-amplitude characteristic for both compression and limiting. Note that limiting makes use of a much tighter slope to ensure that the output voltage cannot exceed the chosen limit, and that the threshold (point of onset of attenuation) takes place at a higher level than for compression.

Traditionally, studio-quality compressor/limiters (as the two functions are so similar it is logical to produce a system that can be used for either compression or limiting) used one of two types of v.c.a. Either the audio signal was chopped at an ultrasonic frequency by a variable mark/space square wave - which requires complex circuitry and careful filtering of the audio output to avoid beats with tape-recorder bias frequencies - or it was attenuated by an electronic potential divider, one arm of which was a photoresistor, the control signal being applied via a small filament bulb. The last-mentioned has disadvantages because photoresistors are non-linear devices, therefore noticeable distortion is introduced into the audio signal, and the thermal inertia of the bulb filament limits the speed of attenuation onset.

Most modern compression systems use field-effect transistor operated below pinch-off as a voltage-variable resistance in a potential divider. This

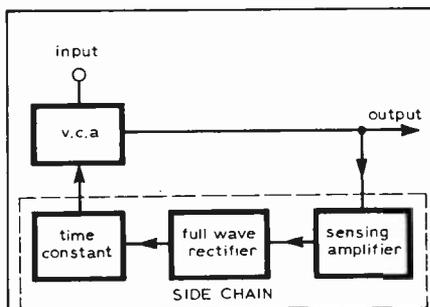


Fig. 1. Voltage-controlled attenuator with d.c. control loop.

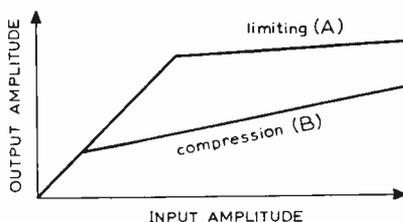


Fig. 2. Amplitude characteristics for compression and limiting—the last-mentioned uses an almost zero slope to prevent the output exceeding a preset level.

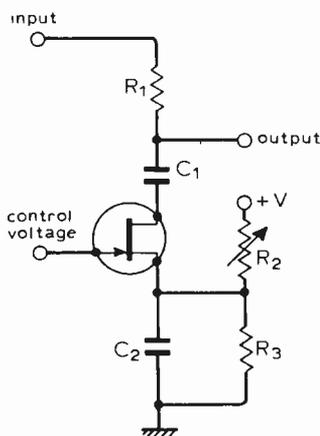


Fig. 3. Basic v.c.a. circuit providing up to 45dB of attenuation. This configuration introduces second-harmonic distortion which is greatest at 6dB of attenuation.

technique has many advantages; it is a simple, cheap, and fast-acting configuration that can provide an attenuation variable between 0 and 45dB. The only problem is that an f.e.t. is a square-law device, and tends to generate a level of second-harmonic distortion that increases rapidly with signal amplitude. A typical arrangement is shown in Fig. 3 -  $R_2$ ,  $R_3$  and  $C_2$  allow the source of the f.e.t. to be set at a d.c. level above ground, so that a control-voltage that moves positive with respect to ground can be used, to avoid level-shifting problems in the control loop. This d.c. level is isolated from the input and output by  $C_1$ .

The distortion introduced by this circuit is at its worst for the 6dB attenuation condition, because at this point the drain-source resistance equals  $R_1$ , and the maximum power level exists in the f.e.t. Table 1 shows the level of second-harmonic distortion introduced into a sine-wave signal of 100mV r.m.s. amplitude, under the 6dB attenuation condition, for three different f.e.t. types. Measurements were made with a Marconi TF2330 wave analyser, higher-orders of harmonic distortion proved to be negligible amplitude in all cases. These measurements were made on one sample of each type of f.e.t. and, because production spreads are large, the results should be treated with some caution. However, it is clear that these levels of distortion are unacceptable for high-quality applications.

Fortunately, a technique\* exists for reducing f.e.t. distortion to manageable levels, if the control-voltage is applied to the f.e.t. gate and summed with a signal consisting of one-half the voltage, from drain to source, then the distortion level is dramatically lowered. The configuration in Fig. 4 shows a simple way of realising this; the signal fraction fed back is not critical and 10% resistors can be used for  $R_4$  and  $R_5$ . Surprisingly, this distortion cancellation procedure leaves the attenuation/control-voltage characteristic almost unchanged. Table 1 shows the new maximum distortion values for 100mV r.m.s. input. (Note that the maximum no longer occurs at 6dB attenuation, but at a point that

varies with the f.e.t. type, where cancellation is least effective.) From these results the 2N5457 and 2N5459 are superior, the 2N5459 was used in the final version of the v.c.a.

To determine appropriate signal levels in the v.c.a., measurements were made of maximum distortion generated, ie the v.c.a. was set to 2dB attenuation, against r.m.s. input voltage; results are shown in Table 2. The question now arises as to whether this distortion performance is adequate for a high-quality compressor/limiter. There is no general agreement as to the amount of second harmonic distortion that can be introduced into a program signal before it becomes aurally detectable, but 0.1% is a figure that is quoted. This means that the permissible input voltage to the v.c.a. would be restricted to below 100mV r.m.s. In practice, however, the attenuation level will be constantly changing, and because distortion level peaks fairly sharply with attenuation change, this level of distortion will only be present for a very small percentage of the time. In any case, second harmonic distortion alone has a relatively low "objectionability factor". The proof of the pudding is in listening to the compressor output signal; inputs of music around 200mV r.m.s. produced no trace of audible distortion. (Good class A power amplifiers and headphones were used for monitoring).

The control loop consists of an amplifier which senses the v.c.a. output level. A full-wave rectification system is normal practice because program waveforms have positive and negative peaks that can vary by as much as 8dB, and an 8dB uncertainty in the output level is usually unacceptable. A time-constant arrangement is used with the rectification circuit to control the attack and decay rates.

The output sensing amplifier in the system is a non-inverting op-amp which allows a high input impedance because the output impedance of the v.c.a. stage reaches a maximum of about 39kΩ at zero attenuation. The full-wave rectification system consists of a transistor phase-splitter driving two op-amp precision-rectifier stages in antiphase. The principle of a precision rectifier is illustrated in Fig. 5. The rectifying element is placed in the feedback loop of an op-amp, so that the effect of the forward voltage drop on the output voltage is divided by the open-loop gain. During positive half-cycles, if the input voltage exceeds the d.c. level stored on the capacitor C, the op-amp output swings positive and C is charged through diode D until its stored voltage is equal to the input voltage. Thus C takes up a voltage across it equal to that of the positive peak of the input signal. During negative half-cycles, and while the input is less than the voltage on C during positive half-cycles, the op-amp saturates negatively and D remains firmly reverse-biased. Obviously this is only a half-wave rectification circuit, the

**Table 1.** Second-harmonic distortion level introduced into a sine-wave of 100mV r.m.s.

Device	2N3819	2N5457	2N5459
2nd harmonic at -6dB	13%	10%	8.9%
2nd harmonic with cancellation attenuation shown	0.39% 2dB	0.12% 10dB	0.12% 2dB

**Table 2.** Maximum distortion generated by various input voltages at 2dB attenuation.

Input (mV, r.m.s.)	2nd harmonic (%)
20	0.005
50	0.10
100	0.12
200	0.19
500	0.34
1,000	0.56


**Table 3.** Prototype calibration data and compression ratios

VC <sub>2</sub> (V)	Threshold (mV, pk)	Compression ratio
2.9	10	2.3
3.5	20	5.1
5.0	50	10
6.7	100	20
8.5	200	35
9.8	500	50


full-wave version uses two of these driven in antiphase, and charging a common capacitor. A resistance through which the charging currents flow determines the attack time, and another in parallel with C defines the decay time-constant.

The complete circuit is shown in Fig. 6. The v.c.a. is essentially as described above and the attenuation threshold is set by the variable resistance R<sub>2</sub>. As the resistance is increased the level of control voltage required for attenuation to begin is reduced, and the system's input/output characteristic moves smoothly from A to B on Fig. 2. The threshold decreases and the compression slope becomes less flat as the system turns slowly from a limiter into a compressor by the manipulation of a single control. The output sensing amplifier consists of IC<sub>1</sub> and has a gain of 19 over the audio band. This is rolled off to unity at d.c. by C<sub>5</sub>. Transistor Tr<sub>2</sub> and its associated components form a conventional phase-splitter driving IC<sub>2</sub> and IC<sub>3</sub>, the precision rectifiers. The rectifier circuitry is more complex than implied above, three modifications have been made to improve the performance. Firstly, IC<sub>2</sub> and IC<sub>3</sub> charge C<sub>9</sub> via current amplifier stages Tr<sub>5</sub> and Tr<sub>6</sub> otherwise the current-limited 741 outputs would be unable to provide enough current for the faster attack times (less than 1ms). Secondly, the feedback loop from C<sub>9</sub> to the inverting inputs of IC<sub>2</sub> and IC<sub>3</sub> is completed via a f.e.t. source-follower. Without this, C<sub>9</sub> would be loaded by the two 741 inputs, and this would severely limit the maximum decay times available. Incorporating the source-follower allows decay times of several minutes by using large resistance values for R<sub>27</sub>. The conventional source-follower has a large negative offset voltage and is unusable in this application because due to their rectifying action IC<sub>2</sub> and IC<sub>3</sub> are unable to provide a voltage on C<sub>9</sub> that is negative of ground. This would be required to allow the source-follower output to be at ground when there is no input to the rectifiers. However, if a modified source-follower is used, with a constant-current source and resistance combination in the source circuit, the offset voltage can be varied on either side of zero by manipulation of R<sub>24</sub> which varies the driving current. The offset voltage is arranged to be plus 0.3V, to allow a large safety margin for thermal variations, component ageing, etc. This means that under no-signal conditions C<sub>9</sub> takes up a standing quiescent voltage of plus 0.3V. The effect of this is taken up in the calibration of R<sub>2</sub>.


The third modification is the addition of R<sub>21</sub>, D<sub>3</sub> and R<sub>22</sub>, D<sub>4</sub>. These two networks prevent IC<sub>2</sub> and IC<sub>3</sub> from saturating negatively, during negative half-cycles of their input voltage, by allowing local negative feedback through D<sub>3</sub> and D<sub>4</sub>. This limits the negative excursion of the IC outputs to

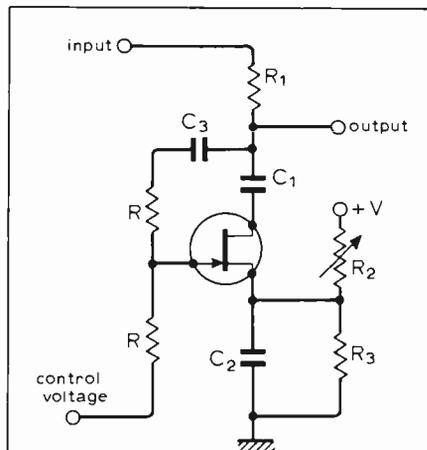

**Fig. 4.** Standard circuit technique for reducing f.e.t. distortion by summing half of the drain/source voltage with the control voltage.

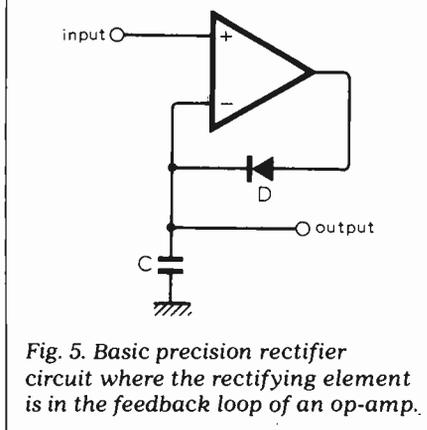

**Fig. 5.** Basic precision rectifier circuit where the rectifying element is in the feedback loop of an op-amp.

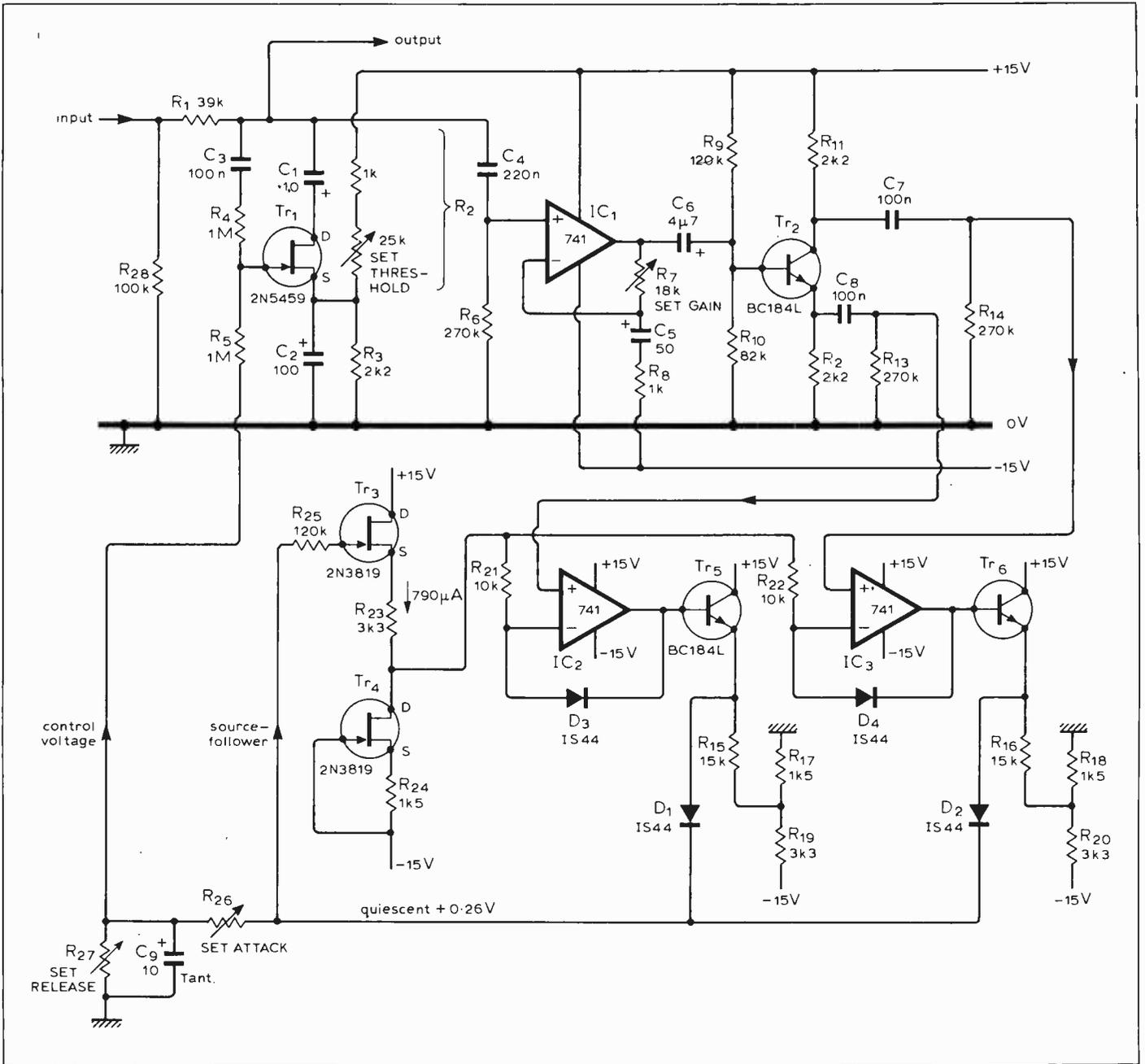

about two Volts. The prevention of saturation is necessary because the recovery time of the 741s causes the frequency response of the precision rectifier circuit to drop off at about 1kHz. The addition of the anti-saturation networks provides a frequency response that starts to fall off significantly above about 12kHz which is ample for our purposes as program signals have very little energy content above this frequency.

The final part of the circuit defines the attenuation time constants. Resistor R<sub>26</sub> sets the attack time constant and R<sub>27</sub> the decay time constant; these can range between zero and 1MΩ (220µs and 10s) for R<sub>26</sub>, and 1kΩ and infinity (10ms and 20min) for R<sub>27</sub>. They can be either switched or variable resistances, depending on the range of variation required.

The circuit in Fig. 6 shows the compressor output being taken directly from the v.c.a. This is only suitable if the minimum load to the output is greater

Fig. 6. Complete circuit where the output is taken directly from the v.c.a.—this may be buffered for loads greater than 100kΩ.

than 100kΩ, otherwise the v.c.a. attenuation characteristic will be distorted by excessive loading. If lower resistance loads are to be driven a buffer amplifier stage must be interposed. The IC<sub>1</sub> amplifier stage is suitable for most applications, and its gain is  $(R_7 + R_8) / R_8$ . For the unity gain case R<sub>8</sub> & C<sub>5</sub> can be eliminated and R<sub>7</sub> replaced by a direct connexion.

The compressor should be driven from a reasonably low impedance output (less than 5kΩ).

Construction is straightforward; the layout is not critical and the prototype was assembled on 0.1in matrix Vero-board. To set up the circuit R<sub>24</sub> is adjusted so that the voltage across C<sub>9</sub> is about plus 0.3V with no signal input.

The value required will vary due to production spreads in the f.e.t.s. To calibrate R<sub>2</sub> it is necessary to relate the level of input signal at which attenuation commences, with the voltage across C<sub>2</sub>. This can be done with an oscilloscope, or preferably an a.f. millivoltmeter. As a guide the calibration data for the prototype is shown in Table 3, along with the values of the compression ratio (number of dBs the input must increase by to increase the output by 1dB). This data must be regarded as only a guide. It is worth noting that as the controlling factor setting the compression/limiting function is the voltage across C<sub>2</sub> R<sub>2</sub> could be replaced by a 1kΩ resistor connected to a remote voltage source.

The compressor/limiter is quite straightforward in use, provided a few points are kept in mind. Firstly, if it is being used in the limiting mode to prevent overload of a subsequent device, the fastest possible attack time should be used, to catch fast transients, and a

fast decay time (say 100ms;  $R_{27} = 10k\Omega$ ), to allow the system to recover rapidly when the transient has passed. Secondly, if a noisy programme signal is being compressed a long decay time should be employed, otherwise the noisy background will be faded up during quiet passages, and the familiar compressor "breathing noises" will be heard. Finally, signals with a large v.l.f. content should be avoided or filtered, otherwise v.l.f. modulation of the signal will result, if a fast decay time is in use.

If a stereo compressor/limiter is constructed from two of the systems described above it is necessary to gang together  $R_{27}$ ,  $R_{26}$ , and  $R_{27}$  between the two channels. A direct connexion between the non-grounded sides of the two  $C_9$ s is also needed. It might be necessary to select matched f.e.t.s to avoid stereo image shift during compression, due to differing attenuation characteristics in the two v.c.as. A well-smoothed p.s.u. providing  $\pm 15V$  should be used to power the compressor/limiter.

#### Components list

IC <sub>1, 2, 3</sub>	741	
Tr <sub>2, 5, 6</sub>	BC184L or equivalent	
Tr <sub>1</sub>	2N5459	
Tr <sub>3, 4</sub>	2N3819	
D <sub>1, 2, 3, 4</sub>	IS44 or low-leakage equivalent	
R <sub>1</sub>	39k	
R <sub>2</sub>	25k variable, with 1k in series	
R <sub>3</sub>	2.2k	
R <sub>4, 5</sub>	1M	
R <sub>6</sub>	270k	
R <sub>7</sub>	18k	
R <sub>8</sub>	1k	
R <sub>9</sub>	120k	
R <sub>10</sub>	82k	All resistors
R <sub>11, 12</sub>	2.2k	(except R <sub>2</sub> ) ¼W
R <sub>13, 14</sub>	270k	
R <sub>15, 16</sub>	15k	
R <sub>17, 18</sub>	1.5k	
R <sub>19, 20</sub>	3.3k	
R <sub>21, 22</sub>	10k	
R <sub>23</sub>	3.3k	
R <sub>24</sub>	see text	
R <sub>25</sub>	120k	
R <sub>26, 27</sub>	see text	
R <sub>28</sub>	100k	
C <sub>1</sub>	10µF 25V electrolytic	
C <sub>2</sub>	100µF 25V electrolytic	
C <sub>3</sub>	100nF 250V polyester	
C <sub>4</sub>	220nF 250V polyester	
C <sub>5</sub>	50µF 40V electrolytic	
C <sub>6</sub>	4.7µF 40V electrolytic	
C <sub>7, 8</sub>	100nF 250V polyester	
C <sub>9</sub>	10µF 16V tantalum bead	

#### Printed circuit boards

Wireless World has arranged a supply of stereo glass fibre p.c.bs. One off price is £3 inclusive; make cheques or postal orders payable to M. R. Sagin, 11 Villiers Road, London NW2.

### "Electronic circuit calculations simplified"

We apologize that once again it has been necessary to postpone publication of Part 6 of this series, on LC circuits. The seventh, and final, part will be on active devices.

## Literature Received

A British Standard, BS E 9111, on the quality assessment of low-power, fixed-value, non-wirewound resistors has recently been published, being the English text of a European Standard CEEC 40 100, with additions. Copies are available from BSI Sales Department, 101 Pentonville Road, London N1 9ND at £2.70.

Television distribution equipment from Wolsey is briefly described in their new short-form catalogue, available from Wolsey Electronics, Cymmer Road, Porth, Mid Glamorgan ..... WW401

Full descriptions of a range of analogue and digital thermometers, recorders and associated equipment, thermocouples and application information are given in a new catalogue from Comark Electronics Ltd, Brookside Avenue, Rustington, Sussex BN16 3LF ..... WW402

Moore Reed have sent two new leaflets, which give technical data and general descriptions of the company's ranges of stepping motors and rotary contact encoders. The leaflets contain useful descriptions of general interest on each of the classes of device. Moore Reed & Company Ltd, Walworth, Andover, Hants SP10 5AB. .... WW404

The Annual Report and Accounts of the Independent Broadcasting Authority are now published, giving details on the financial position, technical developments, programmes and programming, advertising and engineering information. The Report is obtainable from H.M. Stationery Office or booksellers at £1.00.

General transducer techniques are described and specific information is given relating to a range of transducers for the measurement of pressure, displacement, acceleration and force in a new brochure from Sales Department, S.E. Labs (EM1) Ltd, Feltham, Middx. The publication is entitled "A guide to your transducer requirements" .. WW405

We have received a copy of the new catalogue of gears from Davall, which, in addition to data on a vast range of gear products, contains a technical section providing tabular information, conversions, glossary and bibliography. Davall Gear Company Ltd, Welham Green, Hatfield, Herts AL9 7JB ..... WW406

Hewlett-Packard have prepared an eight-page guide to their range of optoelectronic devices, including red, green and yellow l.e.ds, alphanumeric displays and opto-couplers. P.i.n. diodes are also included. The brochure is obtainable from GDS Sales Ltd, Michaelmas House, Salt Hill, Bath Road, Slough, Bucks ..... WW407

Self-balancing chart recorders which use fan-fold chart paper and feature  $\pm 1\%$  accuracy, the SM range from Channel Electronics can provide up to six-point dotting with colour and a wide range of speeds. Channel Electronics (Sussex) Ltd, Cradle Hill Industrial Estate, Seaford, Sussex BN25 3JE ..... WW408

A brochure on the E.E.V. range of travelling-wave tubes is now available, which gives descriptions of t.w.t.s for high-capacity microwave links, including 10W and 20W types working at 4, 6, 8 and 11GHz. E.E.V., Chelmsford, Essex CM1 2QU ..... WW409

A book on the design and use of heat pipes has been produced by Solek. Costing £17.50, the publication includes information on the theory and design of heat pipes, testing, wick materials and applications in 300 pages. The price includes one 12in, ¾in diameter heat pipe with its data sheet. Solek Ltd, 16 Hollybush Lane, Sevenoaks, Kent ..... WW410

Unitrode have published a 32-page semiconductor selection guide which presents information, in tabular form, on rectifying devices, transistors, diodes and i.c.s. There is also a section on reliability, a list of application notes and mechanical details. Walmore Electronics Ltd, 11-15 Betterton Street, Drury Lane, London WC2 9BS ..... WW411

We have received a copy of Pye Ether's new brochure on their range of transducers for industrial measurement. Descriptions are offered of devices for the electrical measurement of displacement, pressure, force, acceleration, vibration, speed, torque and temperature, and associated signal-conditioning, display and recording equipment is illustrated. Pye Ether Ltd, Caxton Way, Stevenage, Herts ..... WW412

Highland Electronics have sent us a leaflet on an over-voltage trip circuit breaker, designed to operate within 2% of the setting in four ranges centred on 25V d.c., 50V d.c., 118V a.c. and 242V a.c. Contact rating of load-switching controls is 50A at 250V a.c. Highland Electronics Ltd., 33-41 Dallington Street, London EC1V 0BD ..... WW413

A booklet from Fairhurst Instruments forms an introduction to a logic tutor and Karnaugh mapper, describing the construction and use of the equipment. It is available, on payment of 15p for postage and packing, from Fairhurst at Dean Court, Woodford Road, Wilmslow, Cheshire ..... WW414.

A booklet from Marconi presents specifications and applications information on two precision signal sources, employing signal generators and associated digital synchronizers, with which frequencies locked in 10Hz steps to 88MHz and 100MHz steps up to 520MHz can be generated at crystal stabilities. Marconi Instruments Ltd, St. Albans, Herts AL4 0JN ..... WW415

### Speed detection alternative

An alternative method of speed detection on the roads has been proposed, based on the Doppler effect in vehicular noise. \* The method correlates the noise frequency spectrum as the vehicle approaches an observer with the spectrum as it moves away. The results of empirical investigation demonstrate that the Doppler shift can be extracted from a motor vehicle's noise and related to the vehicle's speed. Although sources of inaccuracy are significant at lower speeds, a resolution of  $\pm 5\%$  was easily achieved at 60 m.p.h. Such a technique might be found useful in large scale traffic speed and density monitoring systems and may prove to be practical with the use of dedicated mini- or micro-processors. A single computation centre could simultaneously serve a large number of inexpensive microphone sensors. There is considerable interest in computer controlled traffic systems, and it's possible that the acoustic speed measuring technique could become economically competitive with the widely used radar method.

\*Jakus, K. & Čoe, D. S. "Speed Measurement Through Analysis of the Doppler Effect in Vehicular Noise." *IEEE Trans. on Vehicular Technology*, Vol. VT-24, Aug. 1975.

# New Products

## Test meter

The LT 801 is a small multimeter with the unusual feature that the meter movement lifts to an inclined angle to improve viewing. Fifteen switched ranges are available together with three current ranges. The meter is  $20k\Omega/V$  and is overload protected. Alternating voltages from 10V to 1kV f.s.d. may be measured, together with direct voltages from 5V to 2.5kV, f.s.d. Two resistance scales are offered with  $50k\Omega$ , f.s.d. and  $5M\Omega$  f.s.d. West Hyde Developments Ltd, Ryefield Crescent, Northwood, Middlesex HA6 1NN.

**WW 301 for further details**

## Cartridge heated soldering iron

The Quick-Shot soldering iron is designed for use in situations where no power supply is available. The iron bit encloses a replaceable cartridge of "thermit" compound which, when fired by a spring loaded pin in the handle, generates about 10,000 calories of heat, raising the bit temperature to over  $860^{\circ}F$  in a few seconds. Soldering temperatures are maintained for 8 to 10 minutes.

The cartridge is non-inflammable and non-explosive and produces no sparks or chemical fumes during use. A range of copper bits are available. Tele-production Tools Ltd, 28B Hamlet Court Road, Westcliff-on-Sea, Essex.

**WW 302 for further details**

## Static inverter

Designed primarily for aircraft use, the ATR500 is a static inverter rated at 500VA and generates 200V, three phase, 400Hz from a 28V d.c. source. The system comprises two 250VA inverters, a master and a slave, mounted in a tray which interconnects them to give a 3-phase output. The output voltage regulation is 4% worst case with a typical figure of 2%. Up to 167VA load may be applied to each phase with a

power factor of one for unbalanced loads and 0.7 for balanced loads. Industrial Instruments Ltd, Stanley Road, Bromley, Kent BR2 9JF.

**WW 303 for further details**

## Pico and micro-fuses

Pico fuses are  $3/32in \times 9/32in$  and weigh approximately  $1/5g$ . Available in fusings from 62mA to 15A these are designed for use in circuits below 125V. They have a ceramic body hermetically sealed by a heat-shrunk transparent sleeve and are made with two lead configurations. Type 275 have tinned copper axial leads for direct soldering and type 276 have tinned copper radial leads either for soldering or plugging into AMP type tubular receptacles.

Microfuses are plug-in types and are available in 24 fusings from 2mA up to 5A. Designed to have a very fast fusing action, the short-circuit interruption capacity is 10kA d.c. at 125V. Seven types of holders are available including p.c.b. mounting, panel mounting and indicating types. G. E. Electronics (London) Ltd, Eardley House, 182/4 Campden Hill Road, Kensington, London W8 7AS.

**WW 304 for further details**

## P.m. synchronous motors

The range of Memotrace motors is based on a permanent magnet face rotor design, offering ungeared torque ratings from 80-3000g-cm in a variety of options. At 50Hz the motors will operate synchronously at 250, 375 or 500 r.p.m. with gear heads available for a wider range of speeds from 10 r.p.m. The single coil construction type have a random initial starting direction, but will automatically reverse when driven against a mechanical end stop. The double coil, capacitor start motors are directionally controllable and provide greater torque, a stepping mode by d.c. pulsing the winding and variable speed operation also from d.c. pulses. Unimatic Engineers Ltd, Granville Road Works, 122 Granville Road, Cricklewood, London NW2 2LN.


**WW 305 for further details**

## Sound level meter


The PSI 203A is a data-logging sound level meter with a total of 72dB linear dynamic range. The meter is designed to meet the IEC 179 Standard and can be fitted with filters for either octave band or other analysis. Weighting characteristics such as the three standard A, B and C curves are incorporated with an externally fitted option of a D weighting filter. Three dynamic responses may be selected, slow, fast or impulse. Normally supplied with a 1in micro-




**WW 301 for further details**

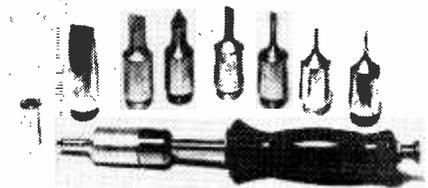


**WW 302 for further details**

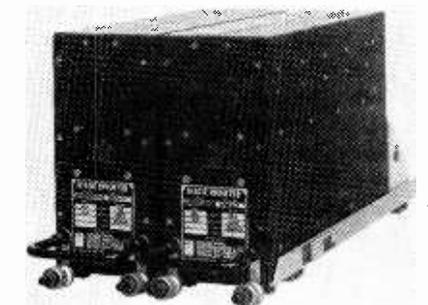

**WW 303 for further details**

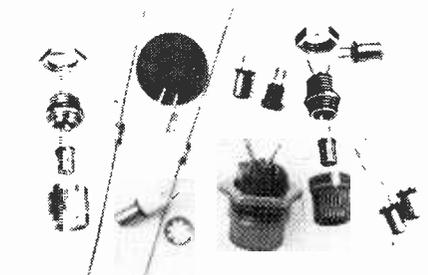

**WW 304 for further details**

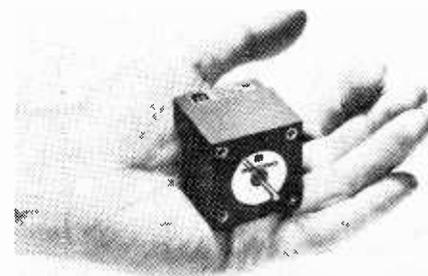

**WW 305 for further details**

phone, the meter can also be fitted with 0.5in or 0.25in capsules, permitting measurements up to 40kHz. A linear d.c. output is provided for connexion to a recorder, with a dynamic range of 0 to 3.5V d.c. Power is supplied from either five 1.5V primary or NiCd rechargeable cells or an accessory a.c. power unit. A wide range of optional accessories is also available. Castle Associates, Redbourn House, North Street, Scarborough, Yorkshire YO11 1DE.

**WW 306 for further details**

### Real-time analyzer

Two real-time spectrum analyzers have been announced by Wessex, the distributors for Rockland Systems. These are the FFT 512/S and the FFT 512/C. The former is a single-channel analyzer using fast Fourier transform techniques to calculate 512 spectral lines of which only 400 are displayed. In addition thirty one-third octave filters from 25Hz to 20kHz are optionally available together with a selectable mode enabling two 200-line analyses to be made and simultaneously displayed. Either digital or analogue data can be accepted and an analogue display and digital data output are provided.

The display is in the form of a 10 × 8cm c.r.t. with cursor readout built in.

Real-time analysis to 5kHz is offered as a standard, but an extension to 10kHz is offered as an option. The Model 512/C cross-channel adaptor provides for the combination of two 512/S units to perform cross-channel analysis. Wessex Electronics Ltd, Stover Trading Estate, Yate, Bristol BS17 5QP.

**WW 307 for further details**

### NiCd charger module

An extended range of modular chargers is available ex-stock from Electroplan. These units provide true constant current operation and are available with output currents ranging from 10mA to 400mA with up to 10 cells being simultaneously charged in a series connexion. Two case sizes are offered, this being dependent upon the power output. Electroplan Ltd, P.O. Box 19, Orchard Road, Royston, Herts SG8 5HH.

**WW 308 for further details**

### Anti-static plastic

A range of anti-static plastic products are being offered by Dage Intersem. These include plastic and foam packages for the transportation and storage of c.m.o.s. devices and assembled

boards, together with anti-static plastic sheeting for work tops, trays etc, and grounding straps for use with either the plastic sheeting or for use by production line staff. Dage Intersem Ltd, Haywood House, Pinner, Middlesex.

**WW 309 for further details**


### Extractor tool

The user of l.s.i. circuits is often faced with the problem of extracting these 24, 36 or 40 pin d.i.p. packages from a tight socket. The l.s.i. extractor tool is a simple stainless steel device with a vinyl coated handle designed to make this task easier. Rastra Electronics Ltd., 275-281 King Street, Hammersmith, London W6 9NF.

**WW 310 for further details**
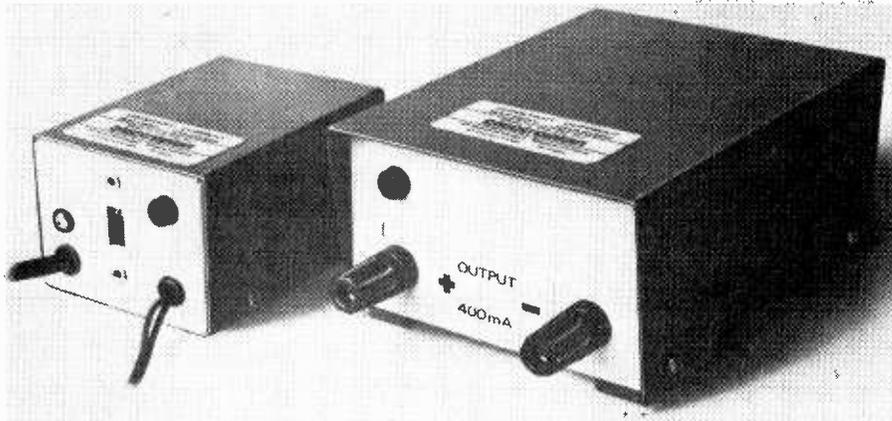
### D.i.p. boards


A range of high density d.i.p. cards have been introduced by Vero. Initially they have been introduced in two versions, the international card size of 114.3 × 165.1mm and the Eurocard size of 100 × 160mm. The former has forty three 2.54mm pitch gold plated contacts on both sides and will accept a maximum of thirty six, 14 or 16 pin i.c.s. The Eurocard will take a 64 way indirect




**WW 308 for further details**



**WW 307 for further details**

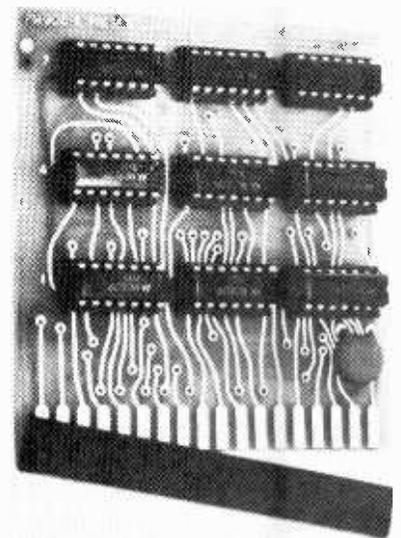

**WW 309 for further details**

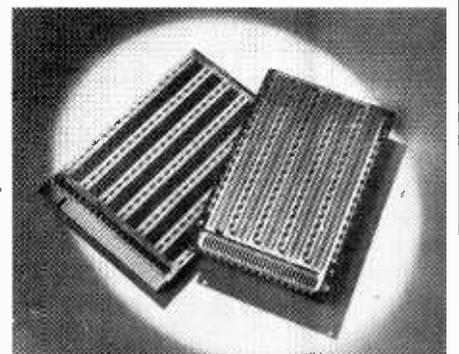

**WW 311 for further details**

**NOW, more than ever,**

**S** **single**  
**source**  
**makes**  
**sense**

**TO MINIMISE INVESTMENTS AND SOLVE STOCK PROBLEMS**

You can increase your efficiency, too, by ordering large or small quantities of any one part, or making up an order of any number of assorted small quantities through the United-Carr Supplies service. We can deliver with more than usual promptitude because we carry such large and varied stocks of CINCH, DOT and FT electronic and electrical components. Fastenings and assemblies.

**So, make United-Carr *Supplies* your SINGLE SOURCE for**



Products, including Barrier terminal strips, Edge Connectors, Subminiature Connectors, Rocker switches, Indicator lights, Press fasteners and Metal & Plastic components.

**Send now, stating possible requirements, for free and post free catalogue.**

United-Carr Supplies Ltd., 112 Station Road, Ilkeston, Derbyshire DE7 5LF.

Tel: Ilkeston 78711 STD 06072 78711. Telex: 377117.

H.F.A.d.

WW — 057 FOR FURTHER DETAILS

Now...the most exciting Sinclair kit ever


# The Black Watch kit

At £17.95, it's

★ **practical** – easily built by anyone in an evening's straightforward assembly.

★ **complete** – right down to strap and batteries.

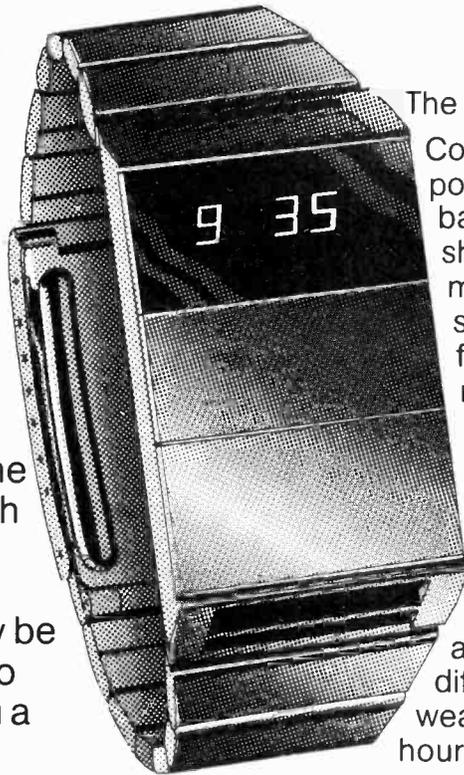★ **guaranteed.** A correctly-assembled watch is guaranteed for a year. It works as soon as you put the batteries in. On a built watch we guarantee an accuracy within a second a day – but building it yourself you may be able to adjust the trimmer to achieve an accuracy within a second a week.



The Black Watch by Sinclair is unique. Controlled by a quartz crystal... powered by two hearing aid batteries... using bright red LEDs to show hours and minutes and minutes and seconds... it's also styled in the cool prestige Sinclair fashion: no knobs, no buttons, no flash.

The Black Watch kit is unique, too. It's rational – Sinclair have reduced the separate components to just four.

It's simple – anybody who can use a soldering iron can assemble a Black Watch without difficulty. From opening the kit to wearing the watch is a couple of hours' work.




## The special features of The Black Watch

Smooth, chunky, matt-black case, with black strap. (Black stainless-steel bracelet available as extra – see order form.)

Large, bright, red display – easily read at night.

Touch-and-see case – no unprofessional buttons.

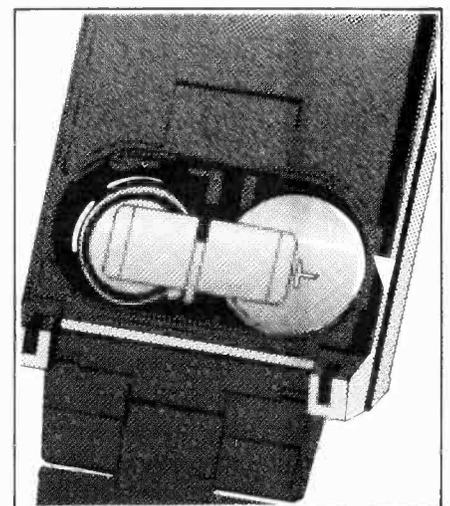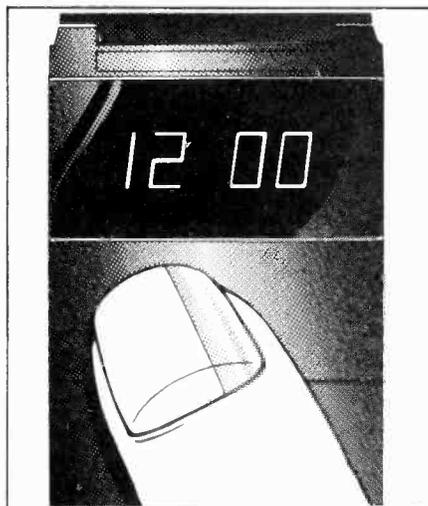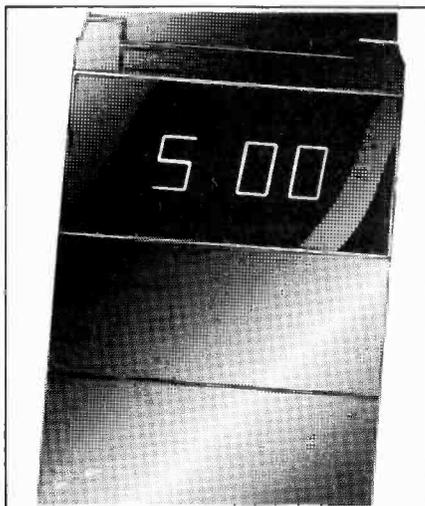Runs on two hearing-aid batteries (supplied). Change your batteries yourself – no expensive jeweller's service.



## The Black Watch – using the unique Sinclair-designed state-of-the-art IC.

### The chip...

The heart of the Black Watch is a unique IC designed by Sinclair and custom-built for them using state-of-the-art technology – integrated injection logic.

This chip of silicon measures only 3 mm x 3 mm and contains over 2000 transistors. The circuit includes

- a) reference oscillator
- b) divider chain
- c) decoder circuits
- d) display inhibit circuits
- e) display driving circuits.

The chip is totally designed and manufactured in the UK, and is the first design to incorporate *all* circuitry for a digital watch on a single chip.

### ...and how it works


A crystal-controlled reference is used to drive a chain of 15 binary dividers which reduce the frequency from 32,768 Hz to 1 Hz. This accurate signal is then counted into units of seconds, minutes, and hours, and on request the stored information is processed by the decoders and display drivers to feed the four 7-segment LED displays. When the display is not in operation, special power-saving circuits on the chip reduce current consumption to only a few microamps.

# Complete kit £17.95!

### The kit contains

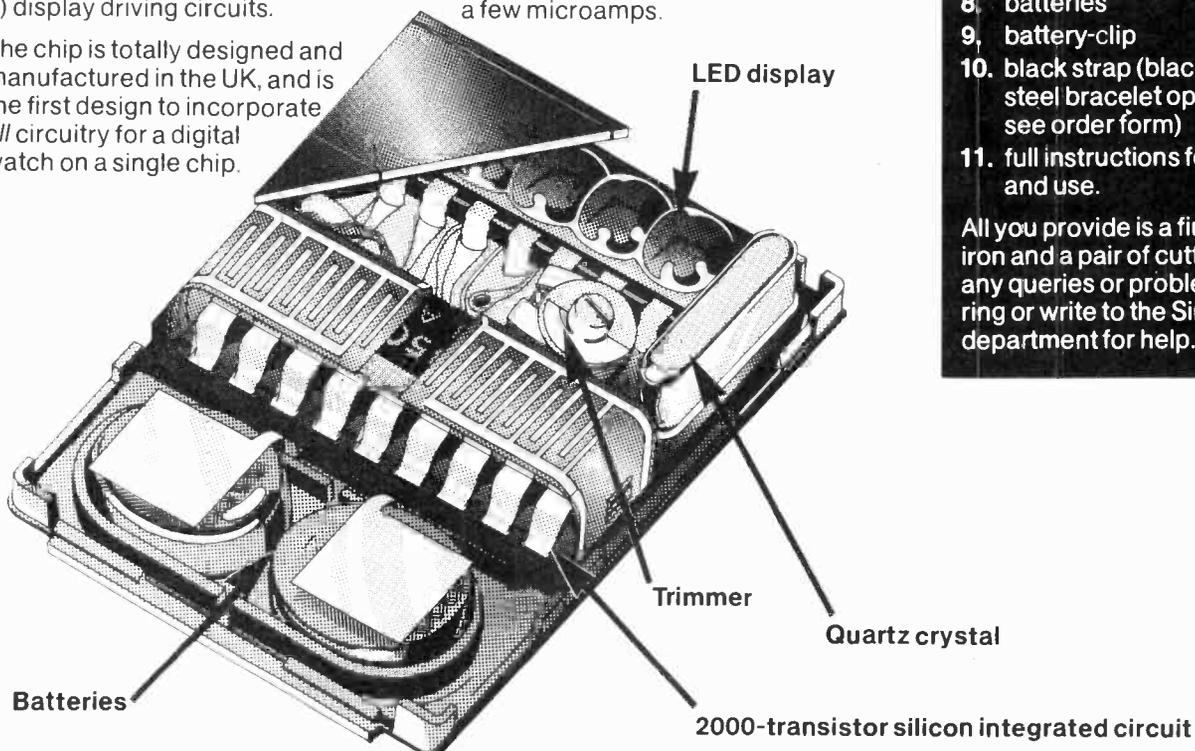1. printed circuit board
2. unique Sinclair-designed IC
3. encapsulated quartz crystal
4. trimmer
5. capacitor
6. LED display
7. 2-part case with window in position
8. batteries
9. battery-clip
10. black strap (black stainless-steel bracelet optional extra – see order form)
11. full instructions for building and use.

All you provide is a fine soldering iron and a pair of cutters. If you've any queries or problems in building, ring or write to the Sinclair service department for help.



### Take advantage of this no-risks, money-back offer today!

The Sinclair Black Watch is fully guaranteed. Return your kit within 10 days and we'll refund your money without question. All parts are tested and checked before despatch – and correctly-assembled watches are guaranteed for one year. Simply fill in the FREEPOST order form and post it – today!

**Price in kit form: £17.95 (inc. black strap, VAT, p&p).**

# sinclair

Sinclair Radionics Ltd,  
London Road, St Ives,  
Huntingdon, Cambs., PE17 4HJ.  
Tel: St Ives (0480) 64646.

Reg. no: 699483 England. VAT Reg. no: 213 8170 88.

To: Sinclair Radionics Ltd, FREEPOST, St Ives, Huntingdon, Cambs., PE17 4BR.

Please send me

Total £

..... (qty) Sinclair Black Watch kit(s) at £17.95 (inc. black strap, VAT, p&p).

\* I enclose cheque for £..... made out to Sinclair Radionics Ltd and crossed.

..... (qty) black stainless-steel bracelet(s) at £2.00 (inc. VAT, p&p).

\* Please debit my \*Barclaycard/Access/American Express account number


Name \_\_\_\_\_

Address \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

WW 12

Please print. FREEPOST – no stamp required.

\*Delete as required

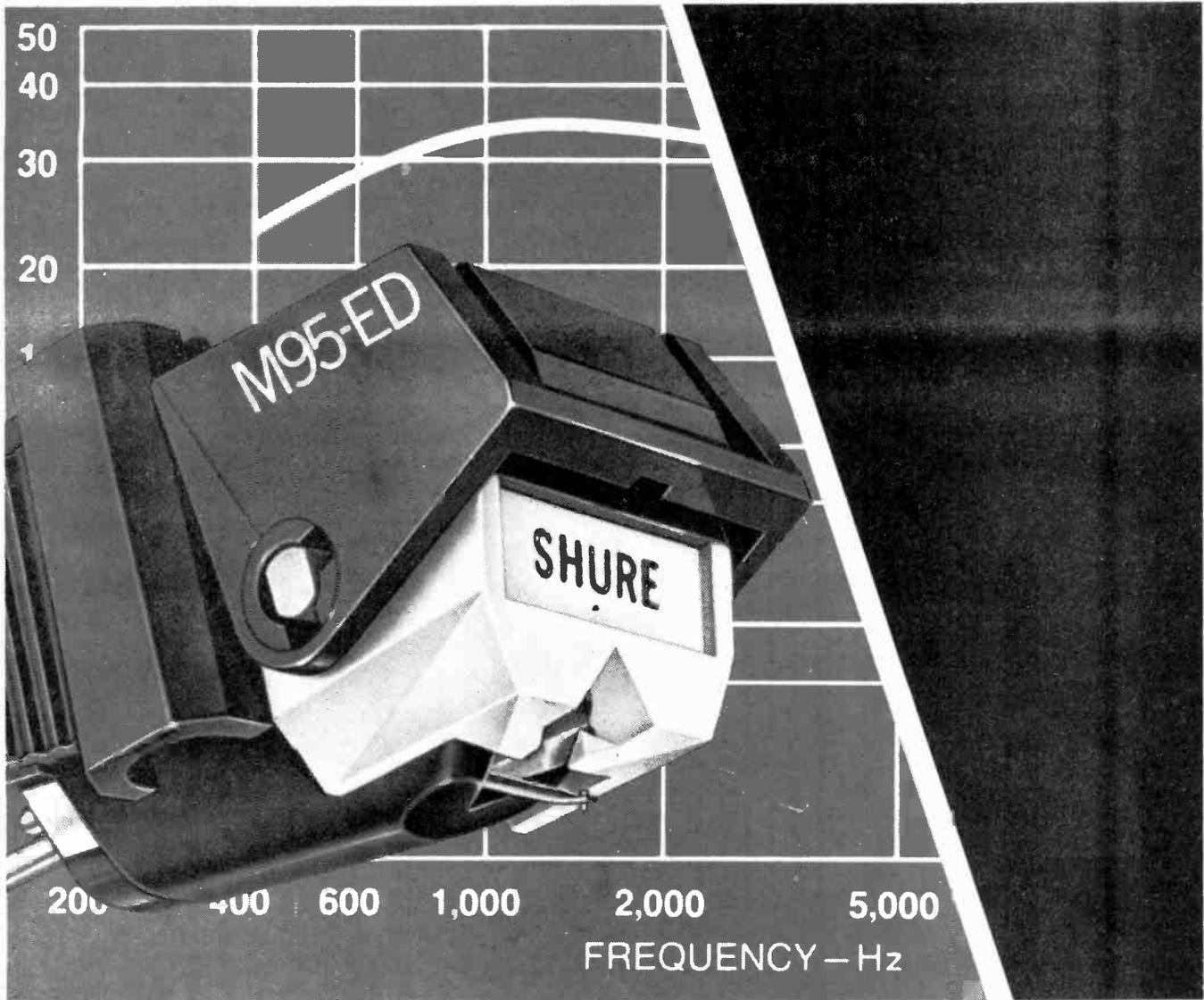

## M95ED: A Significant Technological Innovation



Shure now introduces a superb, moderately priced pick-up cartridge with a performance second only to the renowned V-15 Type III. The technologically advanced electromagnetic structure with a newly designed pole-piece virtually eliminates hysteresis loss. The frequency response from 20 to 20,000 Hz remains essentially flat. Operating at extremely light tracking forces of between  $\frac{3}{4}$  and  $1\frac{1}{2}$  grams, the exceptional trackability of the M95ED enables it to trace the very high recorded velocities encountered on many modern recordings with the result that in addition to providing faithful reproduction of the recorded sound, stylus and record wear are reduced to minimum proportions. The M95ED: A notable addition to the Shure range with a performance never before available at such a competitive price.

Shure Electronics Limited  
Eccleston Road, Maidstone ME15 6AU  
Telephone: Maidstone (0622) 59881



WW-018 FOR FURTHER DETAILS

connector to DIN 41612 specification and will accept a maximum of thirty 14 or 16 pin packages.

The copper pattern is carried on three separate planes, two voltage planes on the wiring side and a ground plane on the component side. Interconnection of devices is either through soldering or by wire wrapping. Vero Electronics Ltd, Industrial Estate, Chandlers Ford, Eastleigh, Hants.

**WW 311 for further details**

## Centre fed dipole

The CD95/3 is a single dipole claimed to produce the same 3dB gain in a single dipole, that is normally obtained from a stacked and phased two way system. Frequency range is from 70-480MHz with maximum gain between 165 and 175MHz. Impedance is 50Ω, and the v.s.w.r. better than 1.5:1. Radiomasts Ltd, Pond Wood Close, Moulton Park, Northants.

**WW 312 for further details**

## Solid State Devices

Names of suppliers of devices in this section are given in abbreviation after each entry and in full at the end of the section.

### M.o.s. drivers


The AM0026 and AM0056 are two dual high-speed clock drivers for use in large m.o.s. memory systems. They consist of two independent circuits suitable for driving loads of high capacitance and providing clock pulse widths down to 125ns. Both standard and Schottky t.t.l. input levels are accepted and converted to m.o.s. compatible outputs. Output current drive is rated to 1.5A and output voltage swing up to 20V. The devices are identical in all but one respect, the AM0056 having a  $V^{BB}$  terminal to provide a higher voltage to the output stage.

Advance Micro Devices Inc.

**WW 350 for further details**
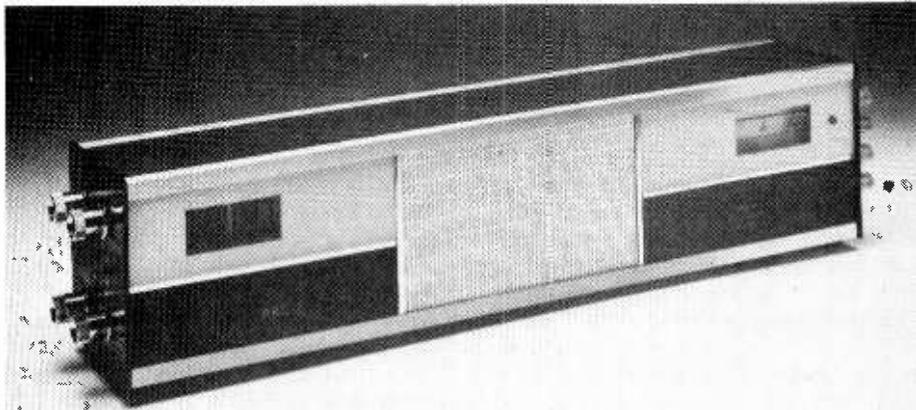
### Dual op-amp

The Harris HA-2655 features, in each half, a minimum slew rate of  $2V/\mu s$ , a minimum full-power bandwidth of 30kHz and a  $\pm 13V$  output voltage swing. The slew rate capability is maintained typically above  $4V/\mu s$  even when supply voltages are permitted to drop to  $\pm 3V$ . The average input offset



**WW 313 for further details**

## Audio-video receiver

This unit features a three day digital timer/clock and is designed to be used in conjunction with video cassette recorders. Up to 72 hrs pre-selection of record start with a one-minute accuracy is available for periods up to 9 hrs 57 minutes. Tuning is effected without the use of a monitor, by using a combina-

tion of an l.e.d. display and the integral monitor loudspeaker. Video and audio outputs are available from off-air u.h.f. transmissions together with a switched mains outlet. Power supply is 200-240V, 50Hz, with a standby battery for the digital timer/clock. Radio Rentals Contracts Ltd, Apex House, Twickenham Road, Feltham, Middlesex TW13 6JQ.

**WW 313 for further details**

voltage drift is said to be  $8\mu V/\beta C$  and the maximum offset current 60nA. Minimum input resistance is 5MΩ.

GDS Sales Ltd

**WW 351 for further details**

## Tuner diodes

The ZC100 Series are a range of variable capacitance tuner diodes claimed to provide a high Q at low cost. The devices are encapsulated in the standard E-line package. Sets of devices with matched parameters are obtainable and also a selection based on parameter tolerance.

Ferranti

**WW 352 for further details**

## Microwave transistor

A family of Class A amplifying microwave transistors has been introduced by AEI. These devices make use of an overlay emitter structure and the high power versions incorporate emitter ballast resistors. The series comprises three types, the DC5621, 5623 and 5631 with gains of 9dB, 8dB and 7.5dB respectively and 1dB gain compression points of 60mW, 150mW and 300mW, measured at 2GHz.

AEI Semiconductors

**WW 353 for further details**

## Germanium power transistors

A series of germanium power transistors with peak current capabilities of 25A at up to 80V have been introduced by the American company, Germanium

Power Devices Corp. Designed as p-n-p transistors and for use in a wide variety of switching and analogue situations they are designated 2N575 and 2N575A and are available in a standard MT-7 package.

Germanium Power

**WW 354 for further details**

## Yellow, orange, red l.e.ds

Twelve high intensity discrete l.e.ds are now available from Vitality. Available in yellow, orange, red and green, the devices have intensities ranging up to 45mcd and viewing angles from a spot for backlighting, a  $24^\circ$  dispersion for directional indicators to  $65^\circ$  for general panel uses. All the l.e.ds are encapsulated in cylindrical packs with 0.75in tin-plated leads.

Vitality

**WW 355 for further details**

## Suppliers

Advance Micro Devices Inc., 901 Thompson Place, Sunnyvale, California 94086, U.S.A.

GDS Sales Ltd, Michaelmas House, Salt Hill, Bath Road, Slough, Bucks.

Ferranti Ltd, Electronic Components Division, Gem Mill, Chadderton, Oldham, Lancs.

AEI Semiconductors Ltd, Carholme Road, Lincoln, LN1 1SG.

Germanium Power Devices Corp., P.O. Box 65, Shawsheen Village Station, Andover, Ma. 01810, U.S.A.

# Instruments in Bloomsbury

In the present economic uncertainty, instrument manufacturers can hardly be blamed for appearing less than complacent about the coming year. The development which must have been undertaken before the situation began to worsen is now, however, bearing fruit in the shape of a variety of new equipment from a large number of manufacturers, who anticipate that the new crop will modify recessive tendencies to manageable proportions. New equipment shown at the 15th EPG electronic instruments exhibition in London takes full advantage of semiconductor developments to achieve a high degree of automatic operation and superlative performance. But the introduction at the less complicated end of the market is equally worthwhile.

**Scopex** showed two new single-beam oscilloscopes, both continuing the company's policy of simplicity in design and operation. The 4S-6 has a reduced cost and performance specification, compared with the earlier models, and is intended for use in schools and servicing roles. It is evident that very careful thought has been applied to the controls, the result being a horizontal sweep controlled in time, trigger level, trigger polarity and internal/external trigger selection by two knobs and a 4mm switching socket. Bandwidth is 6MHz and the maximum sweep is  $1\text{cm}/\mu\text{s}$  — a little slow for the bandwidth. The other instrument, the IS-10, is a 1-in.-tube, 10MHz instrument, which is smaller than the standard car radio. The front panel is  $5\frac{1}{4} \times 2\frac{3}{8}$  inches and the unit weighs just over 3lb.

Among the customary exoticism at the **Tektronix** stand were the DM40 and DM43 digital add-on units for time measurements when used in conjunction with the 465 and 475 portable oscilloscopes. Time measurement is carried out by selecting the two points by means of a bright-up spot with the delay-time position control. Time between the two is then displayed digitally on the add-on unit, which can also be used independently of the oscilloscope for voltage, resistance and temperature measurement.

The 314 portable storage oscilloscope, also shown by Tektronix, possesses a bistable storage screen with a four-hour viewing time. Sensitivity is  $1\text{div}/\text{mV}$  at 10MHz (1 division is 0.25in). Maximum sweep speed is  $10\text{div}/\mu\text{s}$  and a full complement of triggering and dual-beam switching modes is provided. The unit can be powered by a.c. mains, by 24V d.c. at 800mA or 12V d.c. at 1.6A.

Oscilloscopes newly introduced by **Dynamco** are the 7500 and 8500. The former is a mains/battery portable instrument with a bandwidth of

0-40MHz at  $0.1\text{cm}/\text{mV}$  ( $1\text{cm}/\text{mV}$  at 5MHz) sweep delay (which operates in the "mixed" mode) and gated trigger. It is a dual-trace unit with the same general approach as the older Dynamco types, but has no facilities for plug-in X and Y modules. This does help to keep costs down and is sensible in a general-purpose instrument with a specification high enough to be useful in the majority of applications. A rather more advanced specification was adopted for the 8500, which is a 100MHz unit, reverting to the more conventional shape from the long, low look previously used by Dynamco. It boasts an extremely fast timebase (5ns/cm with magnifier in use) and delayed sweep. Sensitivity of the dual-channel Y amplifier is  $0.1\text{cm}/\text{mV}$  or  $1\text{cm}/\text{mV}$  at 40MHz. Both instruments possess sufficient signal delay to enable leading pulse edges to be seen.

The development of digital measuring instruments continues to advance rapidly, the pace being determined, to a large extent, by the integrated-circuit designer rather than the instrument engineer, although there will always be the ingenious method of sailing round limitations instead of battering through them. The **EIP** Autohet digital frequency meter, for instance, is capable of measuring frequencies up to 18GHz with a basic 300MHz counter. This instrument, shown by **Dana**, uses three different techniques to cover the band, that employed from 20Hz to 300MHz being straightforward counting, with either  $50\Omega$  or  $1\text{M}\Omega$  input impedance. From 100MHz to 850MHz, a divide-by-four prescaler precedes the counter, while at higher frequencies a heterodyne approach is used. The 10MHz crystal oscillator used for the gating circuitry is also used to phase-lock a 200MHz oscillator, which feeds an yttrium-iron-garnet comb filter. This produces a series of harmonics of 200MHz and is automatically tuned, selecting successive harmonics until one of them, when mixed with the unknown signal, generates a frequency within the range of the counter. The converter circuit, which step-tunes the filter, provides information to the display on which harmonic was selected and the heterodyne frequency is added to this. Operation is completely automatic, once the correct input is chosen, and the method of measurement confers the advantage that a high degree of f.m. will not affect the result.

A digital method of generating a variety of waveforms (sinusoid as standard) is used by **Farnell** in the DSG1 digital signal generator, which covers the range of  $10^4\text{Hz}$  to  $10^5\text{Hz}$ . The frequency of a multivibrator is phase-locked to a crystal oscillator for

stability and the square-wave output is used as the clock, addressing a read-only memory. The r.o.m. is programmed to contain the waveshape of interest (other programmes are available) in 120 steps, giving a minimum of 0.1% harmonic distortion at mid frequencies. T.h.d. figures rise to 0.3% and 1.5% at top and bottom of the frequency range. The clock waveform and a square wave at twice this frequency are provided at a separate output. A feature of this method of signal generation is that two such instruments can be run together to provide a precise phase relationship.

Carrying this approach several steps further the **Fluke 601DA** (£1650) is a signal synthesizer, covering 10Hz to 11MHz at a resolution of 0.1Hz and a stability of better than 3 p.p.m. after one year. A microprocessor is used to programme the unit with up to ten frequencies, modulation modes and output levels, controlled by push-button. The unit is interfaced for use with automatic test systems.

The use of digital methods in voltage measurement are in use at comparatively less advanced levels of work than was the case a few years ago, two new examples being shown by **Advance** and **Farnell**. Both are digital multimeters, designed for general use in the sort of work that ordinary moving-coil test meters were, and still are, used but with greater resolution and accuracy. The **Advance DMM7** uses p.m.o.s. large-scale i.c.s to provide direct voltage measurement from  $199.9\text{mV}$  full scale to 1200V full scale, at an accuracy of  $0.1\% \pm 0.05\%$  f.s.d. and a c.m.r.r. of more than 120dB at 50Hz; alternating voltage in the same ranges; direct current from  $199.9\mu\text{A}$  f.s.d. to 1999mA and resistance from  $199.9\Omega$  f.s.d. to  $19.99\text{M}\Omega$ . **Farnell's DM131** is a similar type of instrument, but offers auto-ranging and temperature measurement from  $-55^\circ\text{C}$  to  $+125^\circ\text{C}$  at a resolution of 0.1°C.

Turning to communications, the automatic modulation meter Type 9008, shown by **Racal**, is able to measure amplitude modulation depth or frequency deviation without the critical manual tuning process and level-setting that is a common feature to these instruments. The carrier frequency range is 1.5MHz - 2GHz, tuned completely automatically, and levels from 5mV r.m.s. to 1V r.m.s. can be accepted, depending on frequency. The level of signal is also adjusted automatically if it lies within the acceptable range. Mod. depths up to 100% f.s.d. in six ranges and deviations of up to 100kHz in eight ranges (50Hz - 30kHz) can be displayed.

A similar instrument was on the **Marconi Instruments** stand, the TF2304, which covers 25-1000MHz and accepts

modulation frequencies (a.m. and f.m.) of 50Hz to 9kHz.

Even more impressively automatic in operation is the OA2090C white noise test set by M.I., for the measurement of noise-power ratio, channel power and signal-to-noise ratio in multi-channel, frequency-multiplex communications systems. The set consists of a noise generator and receiver, which can be used separately, covering the frequency range 6kHz to 12.36MHz. The generator contains a programmable filter unit with plug-in filters, which is remotely selectable, as is the output level. Selection of a band-stop filter in the generator automatically selects the receiver bandpass frequency, and several functions on the generator




(filter switching, noise on/off) can be controlled from the receiver.

As an example of the analogue equipment on show, Racal had the

9301 — a true r.m.s. millivoltmeter for the range 10kHz to 1.5GHz at 1mV fullscale. It is a sampling type, which converts the product of the sampling process to the r.m.s. value, giving correct readings in the presence of distortion. Remote programming has been provided.

High-power signals for r.f. testing are provided by the AIL model 446, which puts out 70W in the range 10kHz-2.5GHz by means of plug-in r.f. sections. Up to 1000MHz, frequency calibration is by means of a five-digit l.e.d. display, while frequencies above this point are dial-calibrated. Load mismatch protection is incorporated and there is metering for both forward and reflected power.

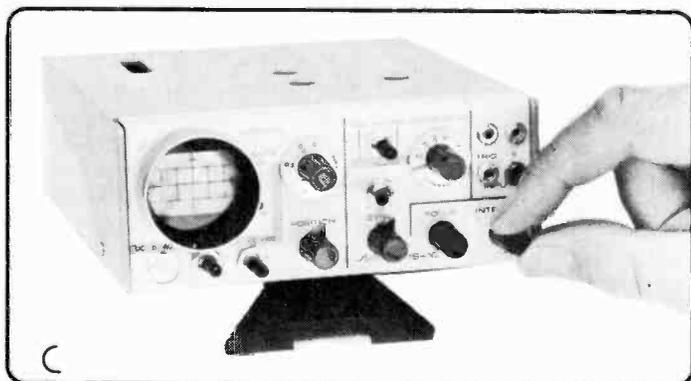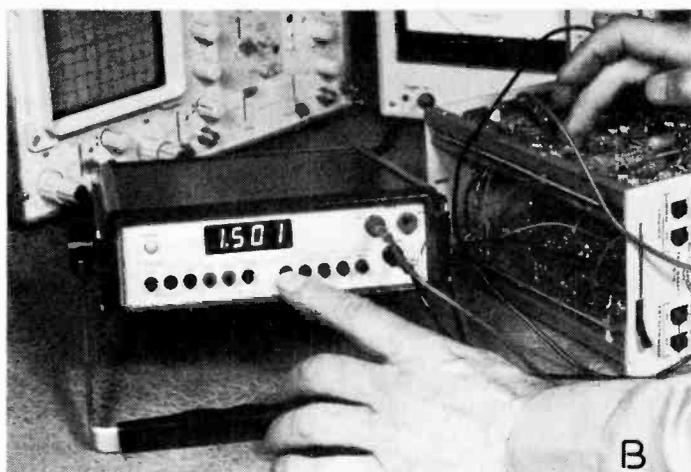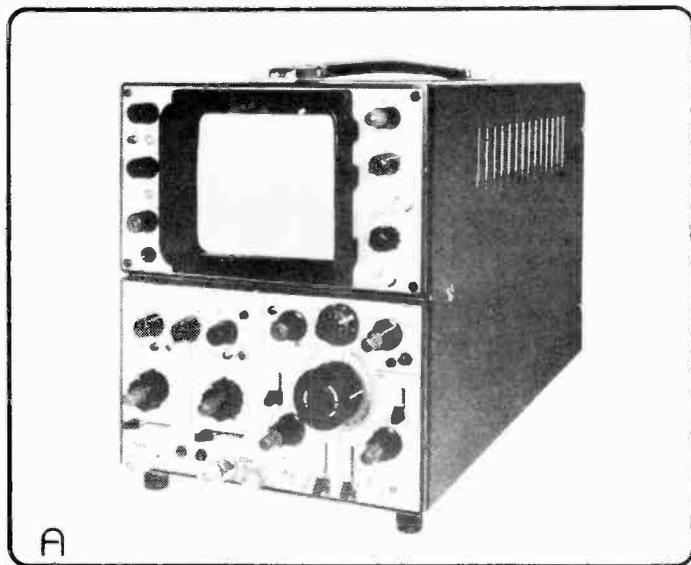A: Dynamco 8500 100MHz oscilloscope. B: Advance digital multimeter. C: Scopex IS-10 miniature oscilloscope. D: Racal true r.m.s. millivoltmetre. E: Farnell digital multimeter. F: Racal modulation meter.



# General index

Volume 81, January-December 1975

The general index is followed by classified and authors' sections. The classified index is divided into the following sections: audio and acoustics, circards, circuit ideas, circuitry and circuit design, communications, constructional designs, editorials, education and instructional, exhibitions and conferences, letters to the editor, measurement and test, news of the month, research notes, space news and world of amateur radio.

- A.f. and r.f. clipping for speech processing, D.A. Tong, 79 Feb.
- APRS 75, 254 June
- ABOUT PEOPLE, 73 Feb.
- Active notch filters, Y. Nezer, 307 July, *Letters*, 467 Oct.
- Advances in microwaves, M. W. Hosking, 577 Dec.
- Aerial rotator servo, D. J. Telfer, 177 Apr.
- Aerials, v.l.f. transmitting, R. B. C. Copsey, 427 Sept.
- Aid for drivers, 269 June
- Amplifier, "current dumping" audio, P. J. Walker, 560 Dec.
- design, transmitter power, W. P. O'Reilly, 417 Sept., 479 Oct., 541 Nov.
- , low-noise wideband, J. A. Grocock, 117 Mar.
- Amplitude modulators, J. Carruthers, J. H. Evans, J. Kinsler & P. Williams, 287 June
- ANNOUNCEMENTS, 120 Mar., 158 Apr., 206 May, 325 July, 482 Oct., 585 Dec.
- Applying "magnetic Ohm's law" to permanent magnets, P. E. K. Donaldson, 567 Dec.
- Artificial vision progresses, T. E. Ivall, 156 Apr.
- Audio Engineering Society 50th convention, W. E. Anderton & B. Lane, 207 May
- Fair new products, 49 Jan.
- preview, 515 Nov.
- level indicator, peak-reading, S. F. Bywaters & J. E. West, 357 Aug., *Letters*, 468 Oct., 512 Nov., Note, 492 Oct.
- Berlin show, more from the, 539 Nov.
- Binary sequence generators, pseudo-random, F. Butler, 87 Feb.
- BOOKS RECEIVED, 205 May, 311 July, 440 Sept., 453, 458 Oct., 539 Nov., 585 Dec.
- Broadcasting, digital techniques in recording and, J. Dwyer, 248 June, *Letters*, 365 Aug.
- Cables in buildings and city streets, radiating, R. Johannessen & P. K. Blair, 398 Sept.
- Calculations simplified, electronic circuit, S. W. Amos, 273 June, 323 July, 387 Aug., 423 Sept., 475 Oct., Correction, 532 Nov.
- Calculators, interference from pocket, C. T. Ristorcelli, 571 Dec.
- Capacitance meter, oscilloscope, H.v.Z. Smit, 238 May
- Cassette and cartridge recorders, vision, 185 Apr.
- Centenary of the crystal rectifier, 141 Mar.
- Charge-coupled devices, J. Mavor, 13 Jan., D. J. MacLennan, 61 Feb., E. Williams, 133 May
- Circuit calculations simplified, electronic, S. W. Amos, 273 June, 323 July, 387 Aug., 423 Sept., 475 Oct., Correction, 532 Nov.
- CIRCUIT IDEAS, 12 Jan., 93 Feb., 175 Apr., 226 May, 391 Aug., 413 Sept., 473 Oct., 519 Nov., 575 Dec.
- Classifying f.e.t.s, B. L. Hart, 2 Jan.
- Clipping for speech processing, a.f. and r.f., D. A. Tong, 79 Feb.
- Clock, solid-state digital, D. D. Clegg, 69 Feb., 129 Mar., *Letters*, 221 May
- Coastguard v.h.f. repeaters, J. B. Tuke, 240 May
- Comparator, resistance, D. Griffiths, 331 July, *Letters*, 415 Sept.
- Components show, Paris, 271 June
- Compressor/limiter, high quality, D. R. G. Self, 597 Dec.
- Computer monitoring of TV signals, J. Schaffer, 37 Jan.
- Computers, communication and high speed railways, W. E. Anderton, 348 Aug., *Letters*, 570 Dec.
- CONFERENCES & EXHIBITIONS, 17 Jan.
- Consultants, J. Dwyer, 505 Nov., *Letters*, 569 Dec.
- Consumer electronics in the U.S.A., 369 Aug., *Letters*, 514 Nov.
- Convention, Audio Engineering Society 50th, W. E. Anderton & B. Lane, 207 May
- Converters, voltage-to-frequency, J. Carruthers, J. H. Evans, J. Kinsler & P. Williams, 183 Apr.
- Crossover networks and phase response, S. K. Pramanik, 529 Nov.
- "Current dumping" audio amplifier, P. J. Walker, 560 Dec.
- Decoder, Wireless World Teletext, P. R. Darrington, 498 Nov., J. F. Daniels, 563 Dec.
- Delayed switching, power supply, P. J. Briody, 139 Mar.
- Digital clock, solid-state, D. D. Clegg, 69 Feb., 129 Mar., *Letters*, 221 May
- frequency-synthesis - a new approach, D. C. Ayre & K. G. Woodard, 216 May, *Letters*, 365 Aug., 468 Oct.
- techniques in recording and broadcasting, J. Dwyer, 248 June, *Letters*, 365 Aug.
- waveform synthesizer, R. A. J. Youngson, 431 Sept.
- wristwatch, solid-state, D. D. Clegg, 298 July, 371 Aug.
- Display devices, 229 May
- Dolby noise reducer, Wireless World, G. Shorter, 200 May, 257 June, 314 July, *Letters*, 415 Sept.
- Domestic equipment, new, 354 Aug.
- Drivers, aid for, 269 June
- EDITORIALS, 1 Jan., 51 Feb., 101 Mar., 151 Apr., 199 May, 247 June, 297 July, 347 Aug., 397 Sept., 447 Oct., 497 Nov., 549 Dec., *Letters*, 126 Mar., 313 July, 414 Sept.
- Electrical safety, standards and the law, B. Lane, 401 Sept., *Letters*, 513, 514 Nov.
- Electronic circuit calculations simplified, S. W. Amos, 273 June, 323 July, 387 Aug., 423 Sept., 475 Oct., Correction, 532 Nov.
- engineers' slide rule, L. Nelson-Jones, 74 Feb., *Letters*, 165 Apr.
- watches, big demand for, 532 Nov.
- Electronics in oil, W. E. Anderton, 4 Jan.
- Emergency power generator, low-cost, J. M. Caunter, 75 Feb., *Letters*, 165 Apr., 265 June, 514 Nov.
- F.e.t.s, classifying, B. L. Hart, 2 Jan.
- F.m. tuner, high-quality, J. B. Dance, 111 Mar., *Letters*, 312 July
- Facsimile scanner, J. M. Osborne, 459 Oct.
- Ferrite pot-cores, using, D. E. O'N. Waddington, 152 Apr.
- 50MHz oscilloscope, C. M. J. Little, 211 May, 266 June, 319 July, 381 Aug.
- Figure-of-merit for front-end selectivity of f.m. tuners, G. J. King, 83 Feb.
- Filters, active notch, Y. Nezer, 307 July, *Letters*, 467 Oct.
- Frequency-synthesis, digital - a new approach, D. C. Ayre & K. G. Woodard, 216 May, *Letters*, 365 Aug., 468 Oct.
- Generator, low-cost emergency power, J. M. Caunter, 75 Feb., *Letters*, 165 Apr., 265 June, 514 Nov.
- Generators, pseudo-random binary sequence, F. Butler, 87 Feb.
- H. F. PREDICTIONS, 30 Jan., 77 Feb., 138 Mar., 173 Apr., 239 May, 272 June, 302 July, 376 Aug., 412 Sept., 478 Oct., 508 Nov., Dec.
- Hermetic plastics i.c.s, 322 July
- High capacity p.c.m. system, 92 Feb.
- quality f.m. tuner, J. B. Dance, 111 Mar., *Letters*, 312 July
- High quality compressor/limiter, D. R. G. Self, 587 Dec.
- High resolution satellite cloud cover pictures, P. Bayliss, 579 Dec.
- How speech can be compressed and expanded, S. L. Silver, 433 Sept.
- I.c. telephone tone generator, R. Ball, 119 Mar.
- Ignition system, optical sensor, H. Maidment, 533 Nov.
- , transistor-aided, G. F. Nudd, 191 Apr.
- Indicator, peak-reading audio level, S. F. Bywaters & J. E. West, 357 Aug., *Letters*, 468 Oct., 512 Nov., Note 492 Oct.
- Interference from pocket calculators, C. T. Ristorcelli, 571 Dec.
- Instruments in Bloomsbury, 594 Dec.
- International radio and television exhibition, 521 Nov.
- Kirchhoff's voltage law, M. G. Scroggie, 143 Mar.
- Lectures, Wireless World, 30 Jan.
- LETTERS TO THE EDITOR, 18 Jan., 65 Feb., 126 Mar., 165 Apr., 219 May, 264 June, 312 July, 365 Aug., 414 Sept., 465 Oct., 512 Nov., 568 Dec.
- Linear c.m.o.s. circuits - I, J. Carruthers, J. H. Evans, J. Kinsler & P. Williams, 581 Dec.
- LITERATURE RECEIVED, 35 Jan., 82 Feb., 155, 190 Apr., 215 May, 286 June, 356 Aug., 422 Sept., 537 Nov., 590 Dec.
- London electronic component show 1975, 227 May
- Loudspeaker developments, recent, 182 Apr.
- Low-cost emergency power generator, J. M. Caunter, 75 Feb., *Letters*, 165 Apr., 265 June, 514 Nov.
- noise wideband amplifier, J. A. Grocock, 117 Mar.
- M.o.s. centre, new, 218 May
- Magnetic recording, 75 years of, B. Lane, 102 Mar., 161 Apr., 222 May, 283 June, 341 July, *Letters*, 365 Aug.
- Magnets, applying "magnetic Ohm's law" to, P. E. K. Donaldson, 567 Dec.
- MEETINGS, 30 Jan., 85 Feb., 125 Mar., 155 Apr., 206 May, 464 Oct., 509 Nov., 556 Dec.
- Meter, oscilloscope capacitance, H.v.Z. Smit, 238 May
- Microprocessors, D. E. O'N. Waddington, 550 Dec.
- Microwaves, advances in, M. W. Hosking, 577 Dec.
- Modulators, amplitude, J. Carruthers, J. H. Evans, J. Kinsler & P. Williams, 287 June
- Monitoring of TV signals, computer, J. Schaffer, 37 Jan.
- Monostable . . . doth give us pause, J. Carruthers, J. H. Evans, J. Kinsler & P. Williams, 27 Jan.
- More from the Berlin show, 539 Nov.
- Multiphonic organs, progress in, J. H. Asbery, 456 Oct.
- National Electronics Council Link scheme, 192 Apr.
- Navigation by satellite, W. Blanchard, 52 Feb., *Letters*, 264 June
- New domestic equipment, 354 Aug.
- m.o.s. centre, 218 May
- NEW PRODUCTS, 47 Jan., 97 Feb., 146 Mar., 194 Apr., 243 May, 293 June, 343 July, 392 Aug., 443 Sept., 493 Oct., 545 Nov., 591 Dec.
- NEWS OF THE MONTH, 10 Jan., 59 Feb., 114 Mar., 159 Apr., 209 May, 255 June, 303 July, 367 Aug., 405 Sept., 454 Oct., 510 Nov., 556 Dec.
- Noise - confusion in more ways than one, K. L. Smith, 107 Mar., 169 Apr., 235 May, 326 July, *Letters*, 264 June
- reducer, Wireless World Dolby, G. Shorter, 200 May, 257 June, 314 July, *Letters*, 415 Sept.
- Notch filters, active, Y. Nezer, 307 July, *Letters*, 467 Oct.
- Oil, electronics in, W. E. Anderton, 4 Jan.
- Optical sensor ignition system, H. Maidment, 533 Nov.
- Organs, progress in multiphonic, J. H. Asbery, 456 Oct.
- Oscillator for the amateur, variable frequency, I. J. Dilworth, 407 Sept.
- Oscillators, RC, J. Carruthers, J. H. Evans, J. Kinsler & P. Williams, 483 Oct.
- Oscilloscope capacitance meter, H.v.Z. Smit, 238 May
- , 50MHz, C. M. J. Little, 211 May, 266 June, 319 July, 381 Aug.
- P.c.m. system, high capacity, 92 Feb.
- Paris components show, 271 June
- Peak-reading audio level indicator, S. F. Bywaters & J. E. West, 357 Aug., *Letters*, 468 Oct., 512 Nov., Note, 492 Oct.
- Phase response, crossover networks and, S. K. Pramanik, 529 Nov.
- reversal, transformer, T. Palmer, 58 Feb.
- shift in loudspeakers, 482 Oct.
- Pot-cores, using ferrite, D. E. O'N. Waddington, 152 Apr.
- Power amplifier design, transmitter, W. P. O'Reilly, 417 Sept., 479 Oct., 541 Nov.
- generator, low-cost emergency, J. M. Caunter, 75 Feb., *Letters*, 165 Apr., 265 June, 514 Nov.
- supply delayed switching, P. J. Briody, 139 Mar.
- , twin voltage stabilized, J. L. Linsley Hood, 43 Jan., *Letters*, 127 Mar., 167 Apr.
- Processing, a.f. and r.f. clipping for speech, D. A. Tong, 79 Feb.
- Products seen at Hi-Fidelity 75, 345 July
- at LECS, 395 Aug.
- Progress in multiphonic organs, J. H. Asbery, 456 Oct.
- Pseudo-random binary sequence generators, F. Butler, 87 Feb.
- RC oscillators, J. Carruthers, J. H. Evans, J. Kinsler & P. Williams, 483 Oct.
- Radiating cables in buildings and city streets, R. Johannessen & P. K. Blair, 398 Sept.
- Radio and television exhibition, international, 521 Nov.
- telescope project at Frensham Heights School, J. H. Duncan, 289 June
- , time by, D. A. Bateman, 277 June
- waves, "Cathode Ray", 469 Oct.
- Railways, computers, communication and high speed, W. E. Anderton, 348 Aug., *Letters*, 570 Dec.
- REAL & IMAGINARY, "Vector", 150 Mar., 198 Apr., 296 Aug., 396 Aug., 496 Oct.
- Realm of microwaves, M. W. Hosking, 334 July
- Recent loudspeaker developments, 182 Apr.
- Recorders, vision cassette and cartridge, 185 Apr.
- with domestic TV, use of video tape, A. C. Smaal, 121 Mar.
- Recording and broadcasting, digital techniques in, J. Dwyer, 248 June, *Letters*, 365 Aug.
- 75 years of magnetic, B. Lane, 102 Mar., 161 Apr., 222 May, 283 June, 341 July, *Letters*, 365 Aug.
- Rectifier, Centenary of the crystal, 141 Mar.
- Reference and regulator circuits, J. Carruthers, J. H. Evans, J. Kinsler & P. Williams, 377 Aug.
- Repeater, coastguard v.h.f., J. B. Tuke, 240 May
- RESEARCH NOTES, 36 Jan., 106, 110 Mar., 430 Sept., 538 Nov.
- Resistance comparator, D. Griffiths, 331 July, *Letters*, 415 Sept.
- Resistors, R. A. Fairs, 487 Oct.
- Rotator servo, aerial, D. J. Telfer, 177 Apr.
- Rule, electronic engineers' slide, L. Nelson-Jones, 74 Feb., *Letters*, 165 Apr.
- Safety, standards and the law, electrical, B. Lane, 401 Sept., *Letters*, 513, 514 Nov.

Satellite cloud cover pictures, high resolution, P. Bayliss, 579 Dec.  
 --- ground station, weather, G. R. Kennedy, 21 Jan., Correction 145 Mar.  
 --- navigation by, W. Blanchard, 52 Feb., *Letters*, 264 June Scanner, facsimile, J. M. Osborne, 459 Oct.  
 Selectivity of f.m. tuners, figure-of-merit for front-end, G. J. King, 83 Feb.  
 Servo, aerial rotator, D. J. Telfer, 177 Apr.  
 75 years of magnetic recording, B. Lane, 102 Mar., 161 Apr., 222 May, 283 June, 341 July, *Letters*, 365 Aug.  
 Signs, sorting out, A. T. Morgan, 436 Sept., *Letters*, 512 Nov.  
 Silent switch for stereo-pair comparisons, K. Moulana, 31 Jan., *Letters*, 312 July, Correction, 145 Mar.  
 SIXTY YEARS AGO, 92 Feb., 125 Mar., 155 Apr., 241 May, 339 July, 368 Aug., 404 Sept., 458 Oct., 538 Nov.  
 Slide rule, electronic engineers', L. Nelson-Jones, 74 Feb., *Letters*, 165 Apr.  
 Solid-state digital clock, D. D. Clegg, 69 Feb., 129 Mar., *Letters*, 221 May  
 --- --- wristwatch, D. D. Clegg, 298 July, 371 Aug.  
 Sorting out signs, A. T. Morgan, 436 Sept., *Letters*, 512 Nov.  
 SPACE NEWS, 78 Feb., 174 Apr., 291 June, 441 Sept., 580 Dec.  
 Speech can be compressed and expanded, how, S. L. Silver, 433 Sept.  
 --- processing, a.f. and r.f. clipping for, D. A. Tong, 79 Feb.  
 Stabilized power supply, twin voltage, J. L. Linsley Hood, 43 Jan., *Letters*, 127 Mar., 167 Apr.  
 Standards and the law, electrical safety, B. Lane, 401 Sept., *Letters*, 513, 514 Nov.  
 Switch for stereo-pair comparisons, silent, K. Moulana, 31 Jan., *Letters*, 312 July, Correction, 145 Mar.  
 Switcher, vision network, 325 July  
 Switching, power supply delayed, P. J. Briody, 139 Mar.  
 Synthesis, digital frequency - a new approach, D. C. Ayre & K. G. Woodard, 216 May, *Letters*, 365 Aug., 468 Oct.  
 Synthesizer, digital waveform, R. A. J. Youngson, 431 Sept.  
 TV signals, computer monitoring of, J. Schaffer, 37 Jan.  
 Telephone tone generator, i.c., R. Ball, 119 Mar.  
 Teletext decoder, Wire World, P. R. Darrington, 498 Nov., J. F. Daniels, 563 Dec.  
 --- receivers, 45 Jan.  
 Television exhibition, international radio and, 521 Nov.  
 --- --- solid-state and digital, 362 Aug.  
 --- tuner design, D. C. Read, 448 Oct., 525 Nov., 581 Dec., *Letters*, 568 Dec.  
 Tidal-wave warnings from the ionosphere? 206 May  
 Time by radio, D. A. Bateman, 277 June  
 Tone generator, i.c. telephone, R. Ball, 119 Mar.  
 Transformer phase reversal, T. Palmer, 58 Feb.  
 Transistor-aided ignition, G. F. Nudd, 191 Apr.  
 --- pairs, J. Carruthers, J. H. Evans, J. Kinsler & P. Williams, 95 Feb.  
 Transmitter power amplifier design, W. P. O'Reilly, 417 Sept., 479 Oct., 541 Nov.  
 Transmitting aerials, v.l.f., R. B. C. Copey, 427 Sept.  
 Tuner design, television, D. C. Read, 448 Oct., 525 Nov., 581 Dec., *Letters*, 568 Dec.  
 ---, high-quality f.m., J. B. Dance, 111 Mar., *Letters*, 312 July  
 Tuners, figure-of-merit for front-end selectivity of f.m., G. J. King, 83 Feb.  
 Twin voltage stabilized power supply, J. L. Linsley Hood, 43 Jan., *Letters*, 127 Mar., 167 Apr.  
 Use of video tape recorders with domestic TV, A. C. Smaal, 121 Mar.  
 Using ferrite pot-cores, D. E. O'N. Waddington, 152 Apr.  
 VAT rates - details, 386 Aug.  
 V.h.f. repeaters, coastguard, B. J. Tuke, 240 May  
 V.l.f. transmitting aerials, R. B. C. Copey, 427 Sept.  
 Variable frequency oscillator for the amateur, I. J. Dilworth, 407 Sept.  
 "Vector" articles:  
 The first book of Vector, 150 Mar.  
 The second book of Vector, 198 Apr.  
 Ode to colour television and Tuppence coloured, 296 June  
 Noonday upon the market-place, 396 Aug.  
 On committees, 496 Oct.  
 Video tape recorders with domestic TV, use of, A. C. Smaal, 121 Mar.  
 Viewdata on trial soon, 532 Nov.  
 Vision cassette and cartridge recorders, 185 Apr.  
 --- network switcher, 325 July  
 --- progresses, artificial, T. E. Ivall, 156 Apr.  
 Voltage law, Kirchhoff's, M. G. Scroggie, 143 Mar.  
 Voltage-to-frequency converters, J. Carruthers, J. H. Evans, J. Kinsler & P. Williams, 183 Apr.  
 Waveform synthesizer, digital, R. A. J. Youngson, 431 Sept.  
 Waves, radio, "Cathode Ray," 469 Oct.  
 Weather satellites ground station, G. R. Kennedy, 21 Jan., Correction, 145 Mar.  
 Wideband amplifier, low-noise, J. A. Grocock, 117 Mar.  
 Wireless World Dolby noise reducer, G. Shorter, 200 May, 257 June, 314 July, *Letters*, 415 Sept.  
 --- --- Teletext decoder, P. R. Darrington, 498 Nov., J. F. Daniels, 563 Dec.  
 WORLD OF AMATEUR RADIO, 46 Jan., 86 Feb., 142 Mar., 193 Apr., 242 May, 292 June, 340 July, 380 Aug., 442 Sept., 486 Oct., 540 Nov., 586 Dec.  
 Wristwatch, solid-state digital, D. D. Clegg, 298 July, 371 Aug.

## CLASSIFIED INDEX

## AUDIO &amp; ACOUSTICS

Amplifier, "current dumping" audio, P. J. Walker, 560 Dec.  
 --- low-noise wideband, J. A. Grocock, 117 Mar.  
 Audio level indicator, peak-reading, S. F. Bywaters & J. E. West, 357 Aug., *Letters*, 468 Oct., 512 Nov., Note, 492 Oct.  
 Compressor/limiter, high quality, D. R. G. Self, 587 Dec.  
 Crossover networks and phase response, S. K. Pramanik, 529 Nov.  
 "Current dumping" audio amplifier, P. J. Walker, 560 Dec.  
 Delayed switching, power supply, P. J. Briody, 139 Mar.  
 Dolby noise reducer, Wireless World, G. Shorter, 200 May, 257 June, 314 July, *Letters*, 415 Sept.

F.m. tuner, high-quality, J. B. Dance, 111 Mar., *Letters*, 312 July  
 Figure-of-merit for front-end selectivity of f.m. tuners, G. J. King, 83 Feb.  
 High-quality f.m. tuner, J. B. Dance, 111 Mar., *Letters*, 312 July  
 High quality compressor/limiter, D. R. G. Self, 587 Dec.  
 How speech can be compressed and expanded, S. L. Silver, 433 Sept.  
 Low-noise wideband amplifier, J. A. Grocock, 117 Mar.  
 Magnetic recording, 75 years of, B. Lane, 102 Mar., 161 Apr., 222 May, 283 June, 341 July, *Letters*, 365 Aug.  
 Noise reducer, Wireless World Dolby, G. Shorter, 200 May, 257 June, 314 July, *Letters*, 415 Sept.  
 Peak-reading audio level indicator, S. F. Bywaters & J. E. West, 357 Aug., *Letters*, 468 Oct., 512 Nov., Note, 492 Oct.  
 Phase response, crossover networks and, S. K. Pramanik, 529 Nov.  
 Power supply delayed switching, P. J. Briody, 139 Mar.  
 Progress in multiphonic organs, J. H. Asbery, 456 Oct.  
 Selectivity of f.m. tuners, figure-of-merit for front-end, G. J. King, 83 Feb.  
 75 years of magnetic recording, B. Lane, 102 Mar., 161 Apr., 222 May, 283 June, 341 July, *Letters*, 365 Aug.  
 Silent switch for stereo pair comparisons, K. Moulana, 31 Jan., *Letters*, 312 July, Correction, 145 Mar.  
 Speech can be compressed and expanded, how, S. L. Silver, 433 Sept.  
 Switching, power supply delayed, P. J. Briody, 139 Mar.  
 Tuner, high-quality f.m., J. B. Dance, 111 Mar., *Letters*, 312 July  
 Tuners, figure-of-merit for front-end selectivity of f.m., G. J. King, 83 Feb.  
 Wideband amplifier, low-noise, J. A. Grocock, 117 Mar.  
 Wireless World Dolby noise reducer, G. Shorter, 200 May, 257 June, 314 July, *Letters*, 415 Sept.

## CIRCARD ARTICLES

Amplitude modulators, 287 June  
 Converters, voltage-to-frequency, 183 Apr.  
 Liner c.m.o.s. circuits - 1, 581 Dec.  
 Modulators, amplitude, 287 June  
 Monostable . . . doth give us pause, 27 Jan.  
 RC oscillators, 483 Oct.  
 Reference and regulator circuits, 377 Aug.  
 Transistor pairs, 95 Feb.  
 Voltage-to-frequency converters, 183 Apr.

## CIRCUIT IDEAS

A balanced output amplifier, K. D. James, 576 Dec.  
 Accurate current generator, R. Morcom, 226 May  
 Amplifier for oscilloscopes, deflection, G. A. Johnston, 175 Apr.  
 Analogue gate with no offset, L. Cook, 93 Feb.  
 Antenna switch, passive solid state, A. Lieber, 12 Jan.  
 Astable circuits, tolerant, C. Horwitz, 93 Feb.  
 Battery charger, N. H. Sabah, 520 Nov.  
 --- voltage indication, low, P. R. K. Chetty, 175 Apr.  
 Binary counter for division by one or two, control of, J. M. Firth, 12 Jan.  
 Cancellation by negative resistance provides alternative to Wheatstone bridge, D. R. Schaller, 391 Aug.  
 Charger, battery, N. H. Sabah, 520 Nov.  
 Clamp, d.c. level, C. B. Mussell, 93 Feb.  
 C-free switching for audio filters, J. S. Wilson, 12 Jan.  
 Clock generator for electronic calculators, T. J. Terrell, 575 Dec.  
 Complementary ramp generator with independent amplitude/slope control, L. J. Retallack, 94 Feb.  
 Constant amplitude sawtooth generator, J. N. Paine, 473 Oct.  
 Continuous dividing of two pulse rates, J. Sabol, 391 Aug.  
 Control of a binary counter for division by one or two, J. M. Firth, 12 Jan.  
 Converter, variable voltage-ratio transistor, R. M. Carter, 519 Nov.  
 Current generator, accurate, R. Morcom, 226 May  
 Cut-out, thermal overload, C. Woolf, 520 Nov.  
 D.c. level clamp, C. B. Mussell, 93 Feb.  
 Deflection amplifier for oscilloscopes, G. A. Johnston, 175 Apr.  
 Dividing of two pulse rates, continuous, J. Sabol, 391 Aug.  
 Electronic organ to piano, C. J. Outlaw, 94 Feb.

F.m. tuning indicator, simpler, H. Hodgson, 413 Sept.  
 Filter, rumble stereo, M. L. G. Oldfield, 474 Oct.  
 Filters, click-free switching for audio, J. S. Wilson, 12 Jan.  
 Frequency doubler, J. Dunne & R. Williams, 575 Dec.  
 Gate with no offset, analogue, L. Cook, 93 Feb.  
 Generator, accurate current, R. Morcom, 226 May  
 ---, constant amplitude sawtooth, J. N. Paine, 473 Oct.  
 --- with independent amplitude/slope control, complementary ramp, L. J. Retallack, 94 Feb.  
 Indication, low battery voltage, P. R. K. Chetty, 175 Apr.  
 Indicator, simpler f.m. tuning, H. Hodgson, 413 Sept.  
 Limiter, stereo dynamic noise, J. W. Richter, 474 Oct.  
 Linear current rotation control, A. Armit, 576 Dec.  
 Low battery voltage indication, P. R. K. Chetty, 175 Apr.  
 Meter, tach-dwell, N. Parron, 413 Sept.  
 Modulator, pulse height, M. D. G. Dabbs, 176 Apr.  
 Noise limiter, stereo dynamic, J. W. Richter, 474 Oct.  
 One-shot timer circuit, J. L. Linsley Hood, 520 Nov.  
 Organ to piano, electronic, C. J. Outlaw, 94 Feb.  
 Oscillator uses c.d.a., sine, T. J. M. Rossiter, 176 Apr.  
 --- uses passive voltage-gain network, W. R. Jackson, 175 Apr.

Oscilloscopes, deflection amplifier for, G. A. Johnston, 175 Apr.  
 Overload cut-out, thermal, C. Woolf, 520 Nov.  
 Passive solid-state antenna switch, A. Lieber, 12 Jan.  
 Power supply, voltage stabilizing a symmetrical, O. Holmskov, 226 May, *Letters*, 415 Sept.  
 --- --- with zener stabilization, variable, L. J. Baughan, 520 Nov.  
 Protection circuit, thyristor, S. G. Pinto, 473 Oct.  
 Pulse height modulator, M. D. G. Dabbs, 176 Apr.  
 --- --- rates, continuous dividing of two, J. Sabol, 391 Aug.  
 Ramp generator with independent amplitude/slope control, complementary, L. J. Retallack, 94 Feb.  
 Rumble filter, stereo, M. L. G. Oldfield, 474 Oct.  
 Sawtooth generator, constant amplitude, J. N. Paine, 473 Oct.  
 Simpler f.m. tuning indicator, H. Hodgson, 413 Sept.  
 Sine oscillator uses c.d.a., T. J. M. Rossiter, 176 Apr.  
 Stabilizing a symmetrical power supply, voltage, O. Holmskov, 226 May, *Letters*, 415 Sept.  
 Stereo dynamic noise limiter, J. W. Richter, 474 Oct.  
 --- rumble filter, M. L. G. Oldfield, 474 Oct.  
 Supply with zener stabilization, variable power, L. J. Baughan, 520 Nov.  
 Switch, passive solid-state antenna, A. Lieber, 12 Jan.  
 Switching for audio filters, click-free, J. S. Wilson, 12 Jan.  
 Tach-dwell meter, N. Parron, 413 Sept.  
 Thermal overload cut-out, C. Woolf, 520 Nov.  
 Thyristor protection circuit, S. G. Pinto, 473 Oct.  
 Timer circuit, one-shot, J. L. Linsley Hood, 520 Nov.  
 Tolerant astable circuits, C. Horwitz, 93 Feb.  
 Transistor converter, variable voltage-ratio, R. M. Carter, 519 Nov.  
 Tuning indicator, simpler f.m., H. Hodgson, 413 Sept.  
 Variable power supply with zener stabilization, L. J. Baughan, 520 Nov.  
 --- voltage-ratio transistor converter, R. M. Carter, 519 Nov.  
 Voltage-gain network, oscillator uses passive, W. R. Jackson, 175 Apr.  
 --- ratio transistor converter, variable, R. M. Carter, 519 Nov.  
 --- stabilizing a symmetrical power supply, O. Holmskov, 226 May, *Letters*, 415 Sept.  
 Wobulator, E. C. Lay, 226 May

## CIRCUITRY &amp; CIRCUIT DESIGN

Active notch filters, Y. Nezer, 307 July, *Letters*, 467 Oct.  
 Aerial rotator servo, D. J. Telfer, 177 Apr.  
 Amplifier, "current dumping" audio, P. J. Walker, 560 Dec.  
 --- design, transmitter power, W. P. O'Reilly, 417 Sept., 479 Oct., 541 Nov.  
 ---, low-noise wideband, J. A. Grocock, 117 Mar.  
 Artificial vision progresses, T. E. Ivall, 156 Apr.  
 Audio level indicator, peak-reading, S. F. Bywaters & J. E. West, 357 Aug., *Letters*, 468 Oct., 512 Nov., Note, 492 Oct.  
 Binary sequence generators, pseudo-random, F. Butler, 87 Feb.  
 Calculations simplified, electronic circuit, S. W. Amos, 273 June, 323 July, 387 Aug., 423 Sept., 475 Oct., Correction, 532 Nov.  
 Capacitance meter, oscilloscope, H. V. Z. Smit, 238 May  
 Circuit calculation, simplified, electronic, S. W. Amos, 273 June, 323 July, 387 Aug., 423 Sept., 475 Oct., Correction, 532 Nov.  
 Clock, solid state digital, D. D. Clegg, 69 Feb., 129 Mar., *Letters*, 221 May  
 Comparator, resistance, D. Griffiths, 331 July, *Letters*, 415 Sept.  
 Compressor/limiter, high quality, D. R. G. Self, 587 Dec.  
 Crossover networks and phase response, S. K. Pramanik, 529 Nov.  
 "Current dumping" audio amplifier, P. J. Walker, 560 Dec.  
 Decoder, Wireless World Teletext, P. R. Darrington, 498 Nov., J. F. Daniels, 563 Dec.  
 Delayed switching, power supply, P. J. Briody, 139 Mar.  
 Digital clock, solid-state, D. D. Clegg, 69 Feb., 129 Mar., *Letters*, 221 May  
 --- frequency-synthesis - a new approach, D. C. Ayre & K. G. Woodard, 216 May, *Letters*, 365 Aug., 468 Oct.  
 --- waveform synthesizer, R. A. J. Youngson, 431 Sept.  
 --- wristwatch, solid-state, D. D. Clegg, 298 July, 371 Aug.  
 Dolby noise reducer, Wireless World, G. Shorter, 200 May, 257 June, 314 July, *Letters*, 415 Sept.  
 Electronic circuit calculations simplified, S. W. Amos, 273 June, 323 July, 387 Aug., 423 Sept., 475 Oct., Correction, 532 Nov.  
 Emergency power generator, low-cost, J. M. Caunter, 75 Feb., *Letters*, 165 Apr., 265 June, 514 Nov.  
 F.m. tuner, high-quality, J. B. Dance, 111 Mar., *Letters*, 312 July  
 50MHz oscilloscope, C. M. J. Little, 211 May, 266 June, 319 July, 381 Aug.  
 Filters, active notch, Y. Nezer, 307 July, *Letters*, 467 Oct.  
 Frequency-synthesis, digital - a new approach, D. C. Ayre & K. G. Woodard, 216 May, *Letters*, 365 Aug., 468 Oct.  
 Generator, low-cost emergency power, J. M. Caunter, 75 Feb., *Letters*, 165 Apr., 265 June, 514 Nov.  
 Generators, pseudo-random binary sequence, F. Butler, 87 Feb.  
 High-quality f.m. tuner, J. B. Dance, 111 Mar., *Letters*, 312 July  
 High quality compressor/limiter, D. R. G. Self, 587 Dec.  
 I.c. telephone tone generator, R. Ball, 119 Mar.  
 Ignition system, optical sensor, H. Maidment, 533 Nov.  
 ---, transistor-aided, G. F. Nudd, 191 Apr.  
 Indicator, peak-reading audio level, S. F. Bywaters & J. E. West, 357 Aug., *Letters*, 468 Oct., 512 Nov., Note, 492 Oct.  
 Low-cost emergency power generator, J. M. Caunter, 75 Feb., *Letters*, 165 Apr., 265 June, 514 Nov.  
 Low-noise wideband amplifier, J. A. Grocock, 117 Mar.

Meter, oscilloscope capacitance, H. v. Z. Smit, 238 May  
Multiphonic organs, progress in, J. H. Asbery, 456 Oct.

Noise reducer, Wireless World Dolby, G. Shorter, 200 May,  
257 June, 314 July, *Letters*, 415 Sept.

Notch filters, active, Y. Nezer, 307 July, *Letters*, 467 Oct.

Optical sensor ignition system, H. Maidment, 533 Nov.  
Organs, progress in multiphonic, J. H. Asbery, 456 Oct.

Oscillator for the amateur, variable frequency, I. J. Dilworth,  
407 Sept.

Oscilloscope capacitance meter, H. v. Z. Smit, 238 May  
---, 50MHz, C. M. J. Little, 211 May, 266 June, 319 July, 381  
Aug.

Peak-reading audio level indicator, S. F. Bywaters & J. E.  
West, 357 Aug., *Letters*, 468 Oct., 512 Nov., Note, 492  
Oct.

Phase response, crossover networks and, S. K. Pramanik,  
529 Nov.

Power amplifier design, transmitter, W. P. O'Reilly, 417  
Sept., 479 Oct., 541 Nov.

--- generator, low-cost emergency, J. M. Caunter, 75 Feb.,  
*Letters*, 165 Apr., 265 June, 514 Nov.

--- supply delayed switching, P. J. Briody, 139 Mar.

--- --, twin voltage stabilized, J. L. Linsley Hood, 43  
Jan., *Letters*, 127 Mar., 167 Apr.

Progress in multiphonic organs, J. H. Asbery, 456 Oct.

Pseudo-random binary sequence generators, F. Butler, 87  
Feb.

Radio, time by, D. A. Bateman, 277 June  
Resistance comparator, D. Griffiths, 331 July, *Letters*, 415  
Sept.

Resistors, R. A. Fairs, 487 Oct.  
Rotator servo, aerial, D. J. Telfer, 177 Apr.

Satellites ground station, weather, G. R. Kennedy, 21 Jan.,  
Correction, 145 Mar.

Servo, aerial rotator, D. J. Telfer, 177 Apr.

Silent switch for stereo-pair comparisons, K. Moulana, 31  
Jan., *Letters*, 312 July, Correction, 145 Mar.

Solid-state digital clock, D. D. Clegg, 69 Feb., 129 Mar.,  
*Letters*, 221 May

--- -- -- wristwatch, D. D. Clegg, 298 July, 371 Aug.

Stabilized power supply, twin voltage, J. L. Linsley Hood, 43  
Jan., *Letters*, 127 Mar., 167 Apr.

Switch for stereo-pair comparisons, silent, K. Moulana, 31  
Jan., *Letters*, 312 July, Correction, 145 Mar.

Switching, power supply delayed, P. J. Briody, 139 Mar.

Synthesis, digital frequency -- a new approach, D. C. Ayre &  
K. G. Woodard, 216 May, *Letters*, 365 Aug., 468 Oct.

Synthesizer, digital waveform, R. A. J. Youngson, 431 Sept.

Telephone tone generator, i.c., Rll, 119 Mar.  
Teletext decoder, Wireless World, P. R. Darrington, 498  
Nov., J. F. Daniels, 563 Dec.

Television tuner design, D. C. Read, 448 Oct., 525 Nov., 581  
Dec., *Letters*, 568 Dec.

Time by radio, D. A. Bateman, 277 June  
Tone generator, i.c. telephone, R. Ball, 119 Mar.  
Transistor-aided ignition, G. F. Nudd, 191 Apr.  
Transmitter power amplifier design, W. P. O'Reilly, 417  
Sept., 479 Oct., 541 Nov.

Tuner design, television, D. C. Read, 448 Oct., 525 Nov., 581  
Dec., *Letters*, 568 Dec.

---, high-quality f.m., J. B. Dance, 111 Mar., *Letters*, 312  
July

Twin voltage stabilized power supply, J. L. Linsley Hood, 43  
Jan., *Letters*, 127 Mar., 167 Apr.

Variable frequency oscillator for the amateur, I. J. Dilworth,  
407 Sept.

Vision progresses, artificial, T. E. Ivall, 156 Apr.

Waveform synthesizer, digital, R. A. J. Youngson, 431 Sept.  
Weather satellites ground station, G. R. Kennedy, 21 Jan.,  
Correction, 145 Mar.

Wideband amplifier, low-noise, J. A. Grocock, 117 Mar.  
Wireless World Dolby noise reducer, G. Shorter, 200 May,  
257 June, 314 July, *Letters*, 415 Sept.

--- -- Teletext decoder, P. R. Darrington, 498 Nov., J. F.  
Daniels, 563 Dec.

Wristwatch, solid-state digital, D. D. Clegg, 298 July, 371  
Aug.

**COMMUNICATIONS**

Advances in microwaves, M. W. Hosking, 577 Dec.  
A.f. and r.f. clipping for speech processing, D. A. Tong, 79  
Feb.

Aerial rotator servo, D. J. Telfer, 177 Apr.  
Aerials, v.l.f. transmitting, R. B. C. Copsey, 427 Sept.  
Amplifier design, transmitter power, W. P. O'Reilly, 417  
Sept., 479 Oct., 541 Nov.

Broadcasting, digital techniques in recording and, J. Dwyer,  
248 June, *Letters*, 365 Aug.

Cables in buildings and city streets, radiating, R.  
Johannessen & P. K. Blair, 398 Sept.

Cassette and cartridge recorders, vision, 185 Apr.  
Clipping for speech processing, a.f. and r.f., D. A. Tong, 79  
Feb.

Coastguard v.h.f. repeaters, J. B. Tuke, 240 May  
Computer monitoring of TV signals, J. Schaffer, 37 Jan.  
Computers, communication and high speed railways, W. E.  
Anderton, 348 Aug., *Letters*, 570 Dec.

Consultants, J. Dwyer, 505 Nov.

Decoder, Wireless World Teletext, P. R. Darrington, 498  
Nov., J. F. Daniels, 563 Dec.

Digital techniques in recording and broadcasting, J. Dwyer,  
248 June, *Letters*, 365 Aug.

Electronics in oil, W. E. Anderton, 4 Jan.

Facsimile scanner, J. M. Osborne, 459 Oct.  
Figure-of-merit for front-end selectivity of f.m. tuners, G. J.  
King, 83 Feb.

High capacity p.c.m. system, 92 Feb.  
High resolution satellite cloud cover pictures, P. Bayliss, 579  
Dec.

I.c. telephone tone generator, R. Ball, 119 Mar.

Microwaves, advances in, M. W. Hosking, 577 Dec.  
Monitoring of TV signals, computer, J. Schaffer, 37 Jan.

Navigation by satellite, W. Blanchard, 52 Feb., *Letters*, 264  
June

Oil, electronics in, W. E. Anderton, 4 Jan.

P.c.m. system, high capacity, 92 Feb.  
Power amplifier design, transmitter, W. P. O'Reilly, 417  
Sept., 479 Oct., 541 Nov.

Processing, a.f. and r.f. clipping for speech, D. A. Tong, 79  
Feb.

Radiating cables in building and city streets, R. Johannessen  
& P. K. Blair, 398 Sept.

Radio, time by, D. A. Bateman, 277 June  
--- waves, "Cathode Ray", 469 Oct.

Railways, computers, communication and high speed, W. E.  
Anderton, 348 Aug., *Letters*, 570 Dec.

Recorders, vision cassette and cartridge, 185 Apr.  
--- with domestic TV, use of video tape, A. C. Smaal, 121  
Mar.

Recording and broadcasting, digital techniques in, J. Dwyer,  
248 June, *Letters*, 365 Aug.

Repeaters, coastguard v.h.f., J. B. Tuke, 240 May  
Rotator servo, aerial, D. J. Telfer, 177 Apr.

Satellite cloud cover pictures, high resolution, P. Bayliss, 579  
Dec.

---, navigation by, W. Blanchard, 52 Feb., *Letters*, 264  
June

Satellites ground station, weather, G. R. Kennedy, 21 Jan.,  
Correction, 145 Mar.

Scanner, facsimile, J. M. Osborne, 459 Oct.  
Selectivity of f.m. tuners, figure-of-merit for front-end, G. J.  
King, 83 Feb.

Servo, aerial rotator, D. J. Telfer, 177 Apr.  
Speech processing, a.f. and r.f. clipping for, D. A. Tong, 79  
Feb.

TV signals, computer monitoring of, J. Schaffer, 37 Jan.  
Telephone tone generator, i.c., R. Ball, 119 Mar.  
Teletext decoder, Wireless World, P. R. Darrington, 498  
Nov., J. F. Daniels, 563 Dec.

--- receivers, 45 Jan.

Television tuner design, D. C. Read, 448 Oct., 525 Nov., 581  
Dec., *Letters*, 568 Dec.

Time by radio, D. A. Bateman, 277 June  
Tone generator, i.c. telephone, R. Ball, 119 Mar.  
Transmitter power amplifier design, W. P. O'Reilly, 417  
Sept., 479 Oct., 541 Nov.

Transmitting aerials, v.l.f., R. B. C. Copsey, 427 Sept.  
Tuner design, television, D. C. Read, 448 Oct., 525 Nov., 581  
Dec., *Letters*, 568 Dec.

Tuners, figure-of-merit for front-end selectivity of f.m., G. J.  
King, 83 Feb.

Use of video tape recorders with domestic TV, A. C. Smaal,  
121 Mar.

V.h.f. repeaters, coastguard, J. B. Tuke, 240 May  
V.l.f. transmitting aerials, R. B. C. Copsey, 427 Sept.  
Video tape recorders with domestic TV, use of, A. C. Smaal,  
121 Mar.

Viewdata on trial soon, 532 Nov.  
Vision cassette and cartridge recorder, 185 Apr.

Waves, radio, "Cathode Ray", 469 Oct.  
Weather satellites ground station, G. R. Kennedy, 21 Jan.,  
Correction, 145 Mar.

Wireless World Teletext decoder, P. R. Darrington, 498 Nov.,  
J. F. Daniels, 563 Dec.

**CONSTRUCTION DESIGNS**

Aerial rotator servo, D. J. Telfer, 177 Apr.  
Audio level indicator, peak-reading, S. F. Bywaters & J. E.  
West, 357 Aug., *Letters*, 468 Oct., 512 Nov., Note, 492  
Oct.

Capacitance meter, oscilloscope, H. v. Z. Smit, 238 May  
Clock, solid-state digital, D. D. Clegg, 69 Feb., 129 Mar.,  
*Letters*, 221 May

Comparator, resistance, D. Griffiths, 331 July, *Letters*, 415  
Sept.

Decoder, Wireless World Teletext, P. R. Darrington, 498  
Nov., J. F. Daniels, 563 Dec.

Digital clock, solid-state, D. D. Clegg, 69 Feb., 129 Mar.,  
*Letters*, 221 May

--- waveform synthesizer, R. A. J. Youngson, 431 Sept.

--- wristwatch, solid-state, D. D. Clegg, 298 July, 371 Aug.

Dolby noise reducer, Wireless World, G. Shorter, 200 May,  
257 June, 314 July, *Letters*, 415 Sept.

Emergency power generator, low-cost, J. M. Caunter, 75  
Feb., *Letters*, 165 Apr., 265 June, 514 Nov.

F.m. tuner, high-quality, J. B. Dance, 111 Mar., *Letters*, 312  
July

Facsimile scanner, J. M. Osborne, 459 Oct.  
50MHz oscilloscope, C. M. J. Little, 211 May, 266 June, 319  
July, 381 Aug.

Generator, low-cost emergency power, J. M. Caunter, 75  
Feb., *Letters*, 165 Apr., 265 June, 514 Nov.

High quality f.m. tuner, J. B. Dance, 111 Mar., *Letters*, 312  
July

I. c. telephone tone generator, R. Ball, 119 Mar.  
Ignition system, optical sensor, H. Maidment, 533 Nov.  
---, transistor-aided, G. F. Nudd, 191 Apr.

Indicator, peak-reading audio level, S. F. Bywaters & J. E.  
West, 357 Aug., *Letters*, 468 Oct., 512 Nov., Note, 492  
Oct.

Low-cost emergency power generator, J. M. Caunter, 75  
Feb., *Letters*, 165 Apr., 265 June, 514 Nov.

Meter, oscilloscope capacitance, H. v. Z. Smit, 238 May  
Multiphonic organs, progress in, J. H. Asbery, 456 Oct.

Noise reducer, Wireless World Dolby, G. Shorter, 200 May,  
257 June, 314 July, *Letters*, 415 Sept.

Optical sensor ignition system, H. Maidment, 533 Nov.  
Organs, progress in multiphonic, J. H. Asbery, 456 Oct.  
Oscillator for the amateur, variable frequency, I. J. Dilworth,  
407 Sept.

Oscilloscope capacitance meter, H. v. Z. Smit, 238 May  
---, 50MHz, C. M. J. Little, 211 May, 266 June, 319 July, 381  
Aug.

Peak-reading audio level indicator, S. F. Bywaters & J. E.  
West, 357 Aug., *Letters*, 468 Oct., 512 Nov., Note, 492  
Oct.

Power generator, low-cost emergency, J. M. Caunter, 75  
Feb., *Letters*, 165 Apr., 265 June, 514 Nov.

--- supply, twin voltage stabilized, J. L. Linsley Hood, 43  
Jan., *Letters*, 127 Mar., 167 Apr.

Progress in multiphonic organs, J. H. Asbery, 456 Oct.

Radio, time by, D. A. Bateman, 277 June  
Resistance comparator, D. Griffiths, 331 July, *Letters*, 415  
Sept.

Rotator servo, aerial, D. J. Telfer, 177 Apr.

Satellites ground station, weather, G. R. Kennedy, 21 Jan.,  
Correction, 145 Mar.

Scanner, facsimile, J. M. Osborne, 459 Oct.  
Servo, aerial rotator, D. J. Telfer, 177 Apr.

Silent switch for stereo-pair comparisons, K. Moulana, 31  
Jan., *Letters*, 312 July, Correction, 145 Mar.

Solid-state digital clock, D. D. Clegg, 69 Feb., 129 Mar.,  
*Letters*, 221 May

--- -- -- wristwatch, D. D. Clegg, 298 July, 371 Aug.

Stabilized power supply, twin voltage, J. L. Linsley Hood, 43  
Jan., *Letters*, 127 Mar., 167 Apr.

Switch for stereo-pair comparisons, silent, K. Moulana, 31  
Jan., *Letters*, 312 July, Correction, 145 Mar.

Synthesizer, digital waveform, R. A. J. Youngson, 431 Sept.

Telephone tone generator, R. Ball, 119 Mar.  
Teletext decoder, Wireless World, P. R. Darrington, 498  
Nov., J. F. Daniels, 563 Dec.

Television tuner design, D. C. Read, 448 Oct., 525 Nov.  
Time by radio, D. A. Bateman, 277 June  
Tone generator, i.c. telephone, R. Ball, 119 Mar.  
Transistor-aided ignition, G. F. Nudd, 191 Apr.  
Tuner design, television, D. C. Read, 448 Oct., 525 Nov.  
---, high-quality f.m., J. B. Dance, 111 Mar., *Letters*, 312  
July

Twin voltage stabilized power supply, J. L. Linsley Hood, 43  
Jan., *Letters*, 127 Mar., 167 Apr.

Variable frequency oscillator for the amateur, I. J. Dilworth,  
407 Sept.

Waveform synthesizer, digital, R. A. J. Youngson, 431 Sept.  
Weather satellites ground station, G. R. Kennedy, 21 Jan.,  
Correction, 145 Mar.

Wireless World Dolby noise reducer, G. Shorter, 200 May,  
257 June, 314 July, *Letters*, 415 Sept.

--- -- Teletext decoder, P. R. Darrington, 498 Nov., J. F.  
Daniels, 563 Dec.

Wristwatch, solid-state digital, D. D. Clegg, 298 July, 371  
Aug.

#### EDITORIALS

A star for India, 549 Dec.  
Broadcasting and communications, 447 Oct.  
Computers and us, 199 May, *Letters*, 313 July  
Consumerism and the Common Market, 397 Sept.  
Measuring what we perceive, 51 Feb.  
Not always the spice of life, 347 Aug.  
Off the record, 247 June  
Outlook for cable television, 151 Apr.  
Professional advice, 101 Mar.  
Sharing the spectrum, 1 Jan., *Letters*, 126 Mar.  
The analogue to digital conversion, 297 July, *Letters*, 414  
Sept., 569 Dec.  
The dugs of war, 497 Nov.

#### EDUCATION & INSTRUCTIONAL

A.f. and r.f. clipping for speech processing, D. A. Tong, 79  
Feb.

Active notch filters, Y. Nezer, 307 July, *Letters*, 467 Oct.  
Advances in microwaves, M. W. Hosking, 577 Dec.  
Aerials, v.l.f. transmitting, R. B. C. Copsey, 427 Sept.  
Aid for drivers, 269 June  
Amplifier design, transmitter power, W. P. O'Reilly, 417  
Sept., 479 Oct., 541 Nov.

Applying "magnetic Ohm's law" to permanent magnets, P.  
E. K. Donaldson, 567 Dec.

Artificial vision progresses, T. E. Ivall, 156 Apr.

Broadcasting, digital techniques in recording and, J. Dwyer,  
248 June, *Letters*, 365 Aug.

Calculations simplified, electronic circuit, S. W. Amos, 273  
June, 323 July, 387 Aug., 423 Sept., 475 Oct.,  
Correction, 532 Nov.

Calculators, interference from pocket, C. T. Ristorcelli, 571  
Dec.

Cassette and cartridge recorders, vision, 185 Apr.  
Charge coupled devices, J. Mavor, 13 Jan., D. J. MacLennan,  
61 Feb., E. Williams, 133 Mar.

Circuit calculations simplified, electronic, S. W. Amos, 273  
June, 323 July, 387 Aug., 423 Sept., 475 Oct.,  
Correction, 532 Nov.

Classifying f.e.t.s, B. L. Hart, 2 Jan.  
Clipping for speech processing, a.f. and r.f., D. A. Tong, 79  
Feb.

Coastguard v.h.f. repeaters, J. B. Tuke, 240 May  
Computer monitoring of TV signals, J. Schaffer, 37 Jan.  
Computers, communication and high speed railways, W. E.  
Anderton, 348 Aug., *Letters*, 570 Dec.

Consultants, J. Dwyer, 505 Nov., *Letters*, 569 Dec.

Digital techniques in recording and broadcasting, J. Dwyer,  
248 June, *Letters*, 365 Aug.

Display devices, 229 May  
Dolby noise reducer, Wireless World, G. Shorter, 200 May,  
257 June, 314 July, *Letters*, 415 Sept.

Drivers, aid for, 269 June

Electrical safety, standards and the law, B. Lane, 401 Sept.,  
*Letters*, 513, 514 Nov.

Electronic circuit calculations simplified, S. W. Amos, 273  
June, 323 July, 387 Aug., 423 Sept., 475 Oct.,  
Correction, 532 Nov.

Electronics in oil, W. E. Anderton, 4 Jan.

F.e.t.s. classifying, B. L. Hart, 2 Jan.  
 Ferrite pot-cores, using, D. E. O'N. Waddington, 152 Apr.  
 Figure-of-merit for front-end selectivity of f.m. tuners, G. J. King, 83 Feb.  
 Filters, active notch, Y. Nezer, 307 July, *Letters*, 467 Oct.  
 How speech can be compressed and expanded, S. L. Silver, 433 Sept.  
 Interference from pocket calculators, C. T. Ristorcelli, 571 Dec.  
 Kirchhoff's voltage law, M. G. Scroggie, 143 Mar.  
 Magnetic recording, 75 years of, B. Lane, 102 Mar., 161 Apr., 222 May, 283 June, 341 July, *Letters*, 365 Aug.  
 Magnets, applying "magnetic Ohm's law" to, P. E. K. Donaldson, 567 Dec.  
 Microprocessors, D. E. O'N. Waddington, 550 Dec.  
 Microwaves, advances in, M. W. Hosking, 577 Dec.  
 Monitoring of TV signals, computer, J. Schaffer, 37 Jan.  
 Navigation by satellite, W. Blanchard, 52 Feb., *Letters*, 264 June  
 Noise — confusion in more ways than one, K. L. Smith, 107 Mar., 169 Apr., 235 May, 326 July, *Letters*, 264 June  
 — reducer, *Wireless World* Dolby, G. Shorter, 200 May, 257 June, 314 July, *Letters*, 415 Sept.  
 Notch filters, active, Y. Nezer, 307 July, *Letters*, 467 Oct.  
 Oil, electronics in W.E. Anderton, 4 Jan.  
 Phase reversal, transformer, T. Palmer, 58 Feb.  
 Pot-cores, using ferrite, D. E. O'N. Waddington, 152 Apr.  
 Power amplifier design, transmitter, W. P. O'Reilly, 417 Sept., 479 Oct., 541 Nov.  
 Processing, a.f. and r.f. clipping for speech, D. A. Tong, 79 Feb.  
 Radio waves, "Cathode Ray", 469 Oct.  
 Railways, computers, communication and high speed, W. E. Anderton, 348 Aug., *Letters*, 570 Dec.  
 Recorders, vision cassette and cartridge, 185 Apr.  
 — with domestic TV, use of video tape, A. C. Smaal, 121 Mar.  
 Recording and broadcasting, digital techniques in, J. Dwyer, 248 June, *Letters*, 365 Aug.  
 —, 75 years of magnetic, B. Lane, 102 Mar., 161 Apr., 222 May, 283 June, 341 July, *Letters*, 365 Aug.  
 Repeaters, coastguard v.h.f., J. B. Tuke, 240 May  
 Resistors, R. A. Fairs, 487 Oct.  
 Safety, standards and the law, electrical, B. Lane, 401 Sept., *Letters*, 513, 514 Nov.  
 Satellite, navigation by, W. Blanchard, 52 Feb., *Letters*, 264 June  
 Selectivity of f.m. tuners, figure-of-merit for front-end, G. J. King, 83 Feb.  
 75 years of magnetic recording, B. Lane, 102 Mar., 161 Apr., 222 May, 283 June, 341 July, *Letters*, 365 Aug.  
 Sorting out signs, A. T. Morgan, 436 Sept., *Letters*, 512 Nov.  
 Speech can be compressed and expanded, how, S. L. Silver, 433 Sept.  
 — processing, a.f. and r.f. clipping for, D. A. Tong, 79 Feb.  
 Standards and the law, electrical safety, B. Lane, 401 Sept., *Letters*, 513, 514 Nov.  
 TV signals, computer monitoring of, J. Schaffer, 37 Jan.  
 Teletext receivers, 45 Jan.  
 Transformer phase reversal, T. Palmer, 58 Feb.  
 Transmitter power amplifier design, W. P. O'Reilly, 417 Sept., 479 Oct., 541 Nov.  
 Transmitting aerials, v.l.f., R. B. C. Copsy, 427 Sept.  
 Tuners, figure-of-merit for front-end selectivity of f.m., G. J. King, 83 Feb.  
 Use of video tape recorders with domestic TV, A. C. Smaal, 121 Mar.  
 Using ferrite pot-cores, D. E. O'N. Waddington, 152 Apr.  
 V.h.f. repeaters, coastguard, J. B. Tuke, 240 May  
 V.l.f. transmitting aerials, R. B. C. Copsy, 427 Sept.  
 Video tape recorders with domestic TV, use of, A. C. Smaal, 121 Mar.  
 Vision cassette and cartridge recorders, 185 Apr.  
 — progresses, artificial, T. E. Ivall, 156 Apr.  
 Voltage law, Kirchhoff's, M. G. Scroggie, 143 Mar.  
 Waves, radio, "Cathode Ray", 469 Oct.  
 Wireless World Dolby noise reducer, G. Shorter, 200 May, 257 June, 314 July, *Letters*, 415 Sept.

#### EXHIBITIONS & CONFERENCES

APRS 75, 254 June  
 Audio Engineering Society 50th Convention, W. E. Anderton & B. Lane, 207 May  
 — Fair preview, 515 Nov.  
 Berlin show, more from the, 539 Nov.  
 Components show, Paris, 271 June  
 Consumer electronics in the U.S.A., 369 Aug., *Letters*, 514 Nov.  
 Convention, Audio Engineering Society 50th, W. E. Anderton & B. Lane, 207 May  
 Domestic equipment, new, 354 Aug.  
 Instruments in Bloomsbury, 594 Dec.  
 International radio and television exhibition, 521 Nov.  
 London Electronic Component Show 1975, 227 May  
 More from the Berlin show, 539 Nov.  
 New domestic equipment, 354 Aug.  
 Paris components show, 271 June  
 Radio and television exhibition, international, 521 Nov.  
 Television exhibition, international radio and, 521 Nov.  
 — solid-state and digital, 362 Aug.

#### LETTERS TO THE EDITOR

Active crossover networks, K. C. Gale, 68 Feb.,  
 — notch filters, P. Bowron, 467 Oct.  
 American insularity, J. G. C. Fox, 128 Mar.  
 Amplifier claims, T. de Paravicini, 19 Jan., R. A. J. Glowacki, 165 Apr.  
 Analogue vs digital readout, E. J. Williams, 414 Sept., F. A. V. Smith, 569 Dec.  
 Audio amplifier load specification, P. J. Walker, R. J. Stuart, 568 Dec.  
 Blattnerphone, G. Dann, 365 Aug.  
 Blowers on amplifiers, I. M. Marshall, 514 Nov.  
 Broadcasting duplication, C. Higham, 126 Mar.  
 Capacitors as transmission lines, A. Azelickis, 219 May, R. A. Fairs, 265 June  
 Circuit diagram layout, D. Williams, P. V. J. Adkins, 18 Jan.  
 Computer power, D. P. C. Thackeray, 313 July  
 Confusion about noise, H. Sutcliffe, 264 June  
 Contacts requested, Mrs. I. David, 264 June  
 Controlling stage lighting, P. D. Hiscocks, 366 Aug., P. M. Hodgson, 466 Oct., C. D. Naylor, 569 Dec.  
 dB conversion on a slide-rule, R. A. Scott, 165 Apr.  
 dB to ratio on a calculator, R. J. Isaacs, 468 Oct.  
 Digital frequency synthesis, J. P. Martinez, 365 Aug., G. Bates, 468 Oct.  
 — speedometer, G. B. Weston, 166 Apr.  
 Directory of audio courses, J. Borwick, 313 July  
 Distortion transmuted?, T. Marshall, 128 Mar.  
 Dolby kit filter adjustment, M. S. Maisey, 415 Sept.  
 Doppler distortion, C. F. Coleman, 416 Sept.  
 — effect, D. H. Edgar, 220 May  
 Easier to become a radio amateur?, J. F. Dunglein, 219 May  
 Electricity and magnetism, C. P. J. Meade, 67 Feb.  
 Electrodynamically induced e.m.f., J. Gray, 221 May, D. C. E. Todd & N. G. S. Taylor, 313 July, K. L. Smith, C. R. Masson, "Cathode Ray", 414 Sept., C. S. Evans, 467 Oct., D. H. Preis, J. Gray, 569 Dec.  
 Electrolytic capacitors, P. D. Habermel, 168 Apr.  
 Electronic component retailers, A. Sproton, 467 Oct.  
 — music journal, J. Meyerowitz, 67 Feb.  
 Emergency power generator, I. R. Sinclair, 165 Apr., M. W. Garman, 265 June  
 F.m. tuning indicator, R. D. Post, 220 May  
 Front panel lettering, P. Hiscocks, 67 Feb.  
 Good service, F. V. Mourant, 415 Sept.  
 High quality f.m. tuner, J. E. Marshall, 312 July  
 Horn loudspeaker output, D. R. Schaller, 126 Mar.  
 Impedance of a transmission line, R. Aratari, 168 Apr.  
 Instrument read-out in Braille?, J. M. Osborne, 313 July  
 Insulation testers, E. A. King, 466 Oct., J. G. C. Fox, 570 Dec.  
 Interference from pocket calculators, C. T. Ristorcelli, 219 May  
 Keypad layout: telephones and calculators, R. E. Abbiss, 66 Feb.  
 Lawn mower powered generator, L. Streatfield, 513 Nov.  
 Liquid-cooled power amplifier, P. Lenartowicz, 220 May  
 Low-cost practice electronic organ, K. J. Young, 167 Apr., 466 Oct.  
 More things in Heaven and Earth, C. G. Warren, 128 Mar.  
 Multi-rate VAT, J. C. Nuttall, 366 Aug.  
 Music without movement, R. G. Young, 365 Aug., J. C. Sager, 467 Oct.  
 Navigation by satellite, J. R. Watkinson, 264 June  
 Novel class B amplifier?, T. Bennett, 366 Aug.  
 — — — — — output?, N. M. Visch, 166 Apr.  
 Optically coupled v.f.o., R. Sterry, 66 Feb.  
 Peak reading level meter, J. Dawson & C. Evans, 468 Oct., S. F. Bywaters & J. E. West, 512 Nov.  
 Peril of publishing, W. B. Henniker, 265 June, D. A. Bailes, 465 Oct.  
 Power supply protection, L. Bischoff & D. W. Branston, 415 Sept.  
 Quad broadcasting — an alternative view, D. J. Meares, 65 Feb.  
 Quadraphonic quandary, B. J. Shelley, 19 Jan.  
 Railway fail-safe?, D. Cockerell, 570 Dec.  
 Read-out for the visually handicapped, A. J. Croft, 514 Nov.  
 Reducing amplifier distortion, W. T. Cocking, 18 Jan., G. W. Short, 127 Mar.  
 Resistance comparator, D. Griffiths, 415 Sept., A. Sandman, 513 Nov.  
 Ribbon microphones, D. Ireland, 165 Apr.  
 Safety regulations, R. C. Whitehead, 513 Nov.  
 Series and parallel feedback, T. Magchielse, 68 Feb., 265 June  
 "Settling time" in audio amplifiers, J. L. Linsley Hood, 18 Jan., G. J. King, 127 Mar.  
 Silent stereo switch, S. F. Bywaters, 312 July  
 Single lamp f.m. tuning indicators, J. A. Skingley, 219 May  
 Small shops care, G. J. Badman, 513 Nov.  
 Solid state digital clock, D. D. Clegg, R. M. Sinden, 221 May  
 Sorting out signs, M. G. Scroggie, 512 Nov.  
 Sound broadcasting dynamic range, J. M. Hughes, 167 Apr.  
 Suicide soldering, D. M. Parkins, 67 Feb., P. S. Reckless, 416 Sept.  
 Teletext demonstration, M. A. E. Butler, 415 Sept.  
 Television tuner design, P. A. Moore, 568 Dec.  
 "The consultants", A. P. B. Faulkner, J. Bowers, 569 Dec.  
 The strip in bank notes, A. Sproton, 68 Feb.  
 Tracking filters, G. D. Dawson, 19 Jan.  
 Transistor circuit diagrams, R. C. Whitehead, 221 May  
 Transmission line impedance, P. I. Somlo, 467 Oct.  
 Twin voltage-stabilized power supply, L. Cook, D. Boxall, 127 Mar., J. F. K. Nosworthy, 167 Apr.  
 Use of l.e.ds as photo-cells, K. C. Johnson, 66 Feb.

Vanishing component shops, B. W. B. Pethers, 512 Nov.  
 Variable frequency division, P. E. Batrick, 67 Feb.

Wide-band local networks, R. Gabriel, 465 Oct.

#### MEASUREMENT & TEST

Binary sequence generators, pseudo-random, F. Butler, 87 Feb.  
 Capacitance meter, oscilloscope, H. v. Z. Smit, 238 May  
 Comparator, resistance, D. Griffiths, 331 July, *Letters*, 415 Sept.  
 Computer monitoring of TV signals, J. Schaffer, 37 Jan.  
 Electronic engineers' slide rule, L. Nelson-Jones, 74 Feb., *Letters*, 165 Apr.  
 50MHz oscilloscope, C. M. J. Little, 211 May, 266 June, 319 July, 381 Aug.  
 Figure-of-merit for front-end selectivity of f.m. tuners, G. J. King, 83 Feb.  
 Generators, pseudo-random binary sequence, F. Butler, 87 Feb.  
 Monitoring of TV signals, computer, J. Schaffer, 37 Jan.  
 Oscillator for the amateur, variable frequency, I. J. Dilworth, 407 Sept.  
 Oscilloscope capacitance meter, H. v. Z. Smit, 238 May  
 — 50MHz, C. M. J. Little, 211 May, 266 June, 319 July, 381 Aug.  
 Pseudo-random binary sequence generators, F. Butler, 87 Feb.  
 Radio, time by, D. A. Bateman, 277 June  
 Resistance comparator, D. Griffiths, 331 July, *Letters*, 415 Sept.  
 Rule, electronic engineers' slide, L. Nelson-Jones, 74 Feb., *Letters*, 165 Apr.  
 Selectivity of f.m. tuners, figure-of-merit for front-end, G. J. King, 83 Feb.  
 Slide rule, electronic engineers', L. Nelson-Jones, 74 Feb., *Letters*, 165 Apr.  
 TV signals, computer monitoring of, J. Schaffer, 37 Jan.  
 Time by radio, D. A. Bateman, 277 June  
 Tuners, figure-of-merit for front-end selectivity of f.m., G. J. King, 83 Feb.  
 Variable frequency oscillator for the amateur, I. J. Dilworth, 407 Sept.  
 Zener diode load line, N. H. Saban, 570 Dec.

#### NEWS OF THE MONTH

AES Convention 1975, 60 Feb.  
 Advance in i.c. fabrication, 558 Dec.  
 "A" level electronics, 577 Dec.  
 Antenna system for AEROSAT, 304 July  
 Association of research contractors formed, 305 July  
 Audio/visual show for the Midlands, 116 Mar.  
 BBC demonstrate matrix system, 59 Feb.  
 Bell Laboratories celebrate fifty years, 160 Apr.  
 Bouncing ball detector, 405 Sept.  
 Breakthrough in quartz oscillators, 454 Oct.  
 BREMA on VAT, 304 July  
 Bristol community TV experiment concluded, 209 May  
 Broadcasting for Pakistan villages, 559 Dec.  
 Bureau of Higher Degrees, 405 Sept.  
 Buy British audio, 510 Nov.  
 CCTV in Westminster Abbey, 406 Sept.  
 Ceefax, Oracle — now Tifax, 306 July  
 Celtic communications covered, 114 Mar.  
 Chart recorder controls furnace, 406 Sept.  
 Colour TV deliveries down, 455 Oct.  
 — — — examinations, 11 Jan.  
 Communications '76, 210 May  
 Component giants integrate, 558 Dec.  
 Computers respond to human voice, 114 Mar.  
 Crystals for calculators, 405 Sept.  
 Data buoy commissioned, 511 Nov.  
 DICE throws a double, 159 Apr.  
 Direct-drive a.c. motor, 306 July  
 EEA promotions for 1975, 59 Feb.  
 Electronics at 'A' level, 255 June  
 — industry surveyed, 60 Feb.  
 Errors reduced on radio-teleprinters, 114 Mar.  
 Facsimile future forecast, 557 Dec.  
 Fingerprint file, 406 Sept.  
 First production c.c.d. memory, 159 Apr.  
 — quadruplex Nowell, 210 May  
 Flexible speaker, 116 Mar.  
 Gulf radar, 256 June  
 High Fidelity 75 expands, 116 Mar.  
 — — — success, 256 June  
 High-speed waveform recorder, 160 Apr.  
 Holographic videodisc, 559 Dec.  
 IEE recommends reconstruction of engineering profession, 159 Apr.  
 — to resign from CEI, 510 Nov.  
 IEE's "Factual Salary Survey", 557 Dec.  
 ITU first I.F./M.F. conference session, 10 Jan.  
 Indonesian television update, 558 Dec.  
 Integrated circuit in stitches, 454 Oct.  
 Is circularly polarized TV coming? 304 July  
 Josephson faster than transistors, 303 July  
 Large-area liquid crystal display, 367 Aug.  
 Laser pulses connect i.c.s, 116 Mar.  
 Liquid crystals for electron observation, 10 Jan.  
 Live stereo from Japan, 367 Aug.

Memory store for coloured weather display, 209 May  
Microcircuit copyright lawsuit, 558 Dec.  
Microwave Conference overwhelmed, 306 July  
Miniature solid-state TV camera, 59 Feb.  
Monitoring monitors, 60 Feb.

NRDC wants more proposals, 558 Dec.  
Navel television, 256 June  
New communications device, 11 Jan.  
-- computer breed, 511 Nov.  
-- trade exhibition, 60 Feb.  
-- video system, 116 Mar.  
1975 Spring trade shows, 303 July  
No interference from experimental tube train, 511 Nov.

Optical stereo for cinema films using Dolby, 255 June

Paging service for London, 255 June  
-- the dead, 10 Jan.  
Parrot power, 11 Jan.  
Perth to Adelaide by microwave, 455 Oct.  
Push-button 'phones introduced, 510 Nov.

Quadraphonic cassettes, 10 Jan.  
Queen's awards to electronics, 305 July  
Quintophonic Tommy, 256 June

Radio range increased twentyfold, 115 Mar.  
Rescue radio system, 209 May  
Royal president for IERE, 557 Dec.

Safety for school TVs, 115 Mar.  
Satellite interference suppressed, 454 Oct.  
Satellite navigator helps food search, 210 May  
Ship simulator innovations, 368 Aug.  
Solid state radio transmitter, 256 June  
Standstill brake tester, 455 Oct.  
Stockholm's buses computerized, 367 Aug.  
Study on teleconferencing, 160 Apr.  
Symposium on broadcasting satellites, 210 May

TV by tropo-scatter, 557 Dec.  
-- deliveries down, 11 Jan.  
-- -- -- again, 306 July  
-- -- -- still down, 160 Apr.  
-- landmark disappears, 367 Aug.  
Telegram a second, 454 Oct.  
Telemetry brings in North Sea oil, 405 Sept.  
Test transmissions curtailed, 115 Mar.  
Tower Bridge won't fall down, 368 Aug.  
Trading boom at LECS, 368 Aug.  
Transistor assembly automated, 305 July  
Troposcatter equipment for PO, 59 Feb.

VAT muddle, 303 July  
Video first, 209 May

Well oiled, 559 Dec.  
World markets decline, 305 July  
Worldwide telephone link, 115 Mar.

#### RESEARCH NOTES

At last! The solid-state radio valve, 106 Mar.

Bat sonar is best, 538 Nov.  
Better propagation forecasts? 430 Sept.  
Black holes: radiation transformers? 110 Mar.  
-- -- -- to solve the energy crisis, 538 Nov.  
Come back, Geller, all is forgiven? 538 Nov.

Dielectric waveguide materials, 106 Mar.  
Digital filters reveal weather trends, 430 Sept.

E.E.G. test for telepathy? 430 Sept.  
Ear temperature clue to brain-damage, 430 Sept.  
Enter the white hole, 36 Jan.

First binary pulsar, 36 Jan.

Gravity waves: more problems for detection, 106 Mar.

Holes in the ionosphere to aid radio astronomy? 430 Sept.

Insect tracking by radar, 106 Mar.

Just a second . . . , 538 Nov.

LDEs - not from alien space probes, 106 Mar.  
Lasers detect paint-peeling masterpieces, 110 Mar.

Meteorites: poor man's intelsat? 538 Nov.

New thermal imaging tube, 110 Mar.

Optical fibre modulators? 106 Mar.

Power from ocean waves, 36 Jan.  
Psi particle, 110 Mar.

Sound waves to hold liquids in space lab? 538 Nov.  
Sunspots, Jupiter, and earthquakes, 36 Jan.

Tailpiece, 106 Mar.

Thermistor-stabilized oscillators, 36 Jan.  
Towards the 12GHz consumer f.e.t., 430 Sept.

Watching high-speed transistors in slow motion, 36 Jan.  
Wave power looks good, 430 Sept.

#### SPACE NEWS

ASTP's ranging system, 441 Sept.

Communications satellite moves to India, 441 Sept.  
Conference on spacecraft antennas, 291 June  
Crop inventory experiment, 78 Feb.  
Crystals grown in space, 291 June

Did you know?, 78 Feb.

ESA's first satellite, 580 Dec.  
European Space Days, 441 Sept.

First African Landsat station, 291 June  
Future of satellite communications, 291 June

Jovian magnetic influences, 291 June

Last Intelsat IV launch, 441 Sept.

Magnetosphere exploration, 78 Feb.  
Mars probe launched, 580 Dec.

New communications satellite, 78 Feb.

Radio and space research 1971-73, 78 Feb.

Self-repairing memories, 174 Apr.  
Seventh Intelsat IV launch, 174 Apr.  
Solid state data recorder, 78 Feb.

Weather satellite for Western states, 174 Apr.

#### WORLD OF AMATEUR RADIO

Across the Channel, 292 June  
All-solid-state stations, 86 Feb.  
Amateur production line, 292 June  
-- television, 46 Jan.  
Amateurs and emergencies, 340 July  
American opinions, 486 Oct.  
Artificial radio aurora, 86 Feb.

Commonwealth microwave record?, 46 Jan.

End of "BERU", 242 May

FCC Docket 20282, 380 Aug.  
50 years of REF, 193 Apr.  
From all quarters, 193 Apr.

G-line pioneer, 380 Aug.  
Good winter for "Top Band", 193 Apr.

Hourly propagation forecasts from WWV, 340 July

IARU celebrates 50 years, 142 Mar.  
Inflated awards?, 540 Nov.  
Italian FAX, 142 Mar.

Less television interference, 442 Sept.  
Licence trends, 242 May  
Look no batteries, 340 July  
Low-cost s.s.b. generation, 242 May

Milliwatts and coherent c.w., 142 Mar.  
Mixed grill, 242 May  
Moonbounce, 486 Oct.

On the bands, 540 Nov.  
Oscar 7 up and working, 46 Jan.

Powers low and high, 292 June  
Preparing for 1979, 292 June  
President from Wales, 46 Jan., *Letters*, 219 May  
Proposed changes to American licences, 193 Apr.

R.t.t.y. facilities at ZS3B, 193 Apr.  
Repeaters and beacons, 86 Feb.

SOE's suitcase sets, 442 Sept.  
Slow-scan progress, 86 Feb.  
Sun shines on 28MHz, 442 Sept.

Television topics, 540 Nov.  
Transatlantic link severed, 486 Oct.  
200-mile microwave contacts, 380 Aug.  
Typewriters rampant, 486 Oct.

Using the London repeater, 292 June

Warsaw and v.h.f., 380 Aug.  
What goes wrong?, 540 Nov.  
When portable is fixed, 442 Sept.  
Whose finger on the rule book?, 380 Aug.  
World Radio Club, 142 Mar.

#### AUTHORS

Amos, S. W., 273 June, 323 July, 387 Aug., 423 Sept., 475 Oct.  
Anderton, W. E., 4 Jan., 207 May, 348 Aug.  
Asbery, J. H., 456 Oct.  
Ayre, D. C. & Woodard, K. G., 216 May, *Letters*, 365 Aug.

Bail, R., 119 Mar.  
Bateman, D. A., 277 June  
Bayliss, P., 579 Dec.  
Blair, P. K. & Johannessen, R., 398 Sept.  
Blanchard, W., 52 Feb., *Letters*, 265 June  
Briody, P. J., 139 Mar.  
Butler, F., 87 Feb.  
Bywaters, S. F. & West, J. E., 357 Aug., *Letters*, 512 Nov.

Carruthers, J., Evans, J. H., Kinsler, J. & Williams, P., 27 Jan.,  
95 Feb., 183 Apr., 287 June, 377 Aug., 483 Oct., 581 Dec.  
"Cathode Ray", 469 Oct.  
Caunter, J. M., 75 Feb., *Letters*, 166 Apr.  
Clegg, D. D., 69 Feb., 129 Mar., 298 July, 371 Aug., *Letters*,  
221 May  
Copsey, R. B. C., 427 Sept.

Dance, J. B., 111 Mar., *Letters*, 312 July  
Daniels, J. F., 563 Dec.  
Darrington, P. R., 498 Nov.  
Dilworth, I. J., 407 Sept.  
Donaldson, P. E. K., 567 Dec.  
Dwyer, J., 248 June, 505 Nov.

Evans, J. H., Kinsler, J., Williams, P. & Carruthers, J., 27 Jan.,  
95 Feb., 183 Apr., 287 June, 377 Aug., 483 Oct., 581 Dec.

Fairs, R. A., 487 Oct.

Griffiths, D., 331 July  
Grocock, J. A., 117 Mar., *Letters*, 264 June

Hart, B. L., 2 Jan.  
Hosking, M. W., 334 July, 577 Dec.

Ivall, T. E., 156 Apr.

Johannessen, R. & Blair, P. K., 398 Sept.

Kennedy, G. R., 21 Jan.  
King, G. J., 83 Feb., *Letters*, 128 Mar.  
Kinsler, J., Williams, P., Carruthers, J. & Evans, J. H., 27 Jan.,  
95 Feb., 183 Apr., 287 June, 377 Aug., 483 Oct., 581 Dec.

Lane, B., 102 Mar., 161 Apr., 208 & 222 May, 283 June, 341  
July, 401 Sept.  
Linsley Hood, J. L., 43 Jan., *Letters*, 18 Jan., 127 Mar., 167  
Apr.  
Little, C. M. J., 211 May, 266 June, 319 July, 381 Aug.

MacLennan, D. J., 61 Feb.  
Maidment, H., 533 Nov.  
Mavor, J., 13 Jan.  
Morgan, A. T., 436 Sept., *Letters*, 513 Nov.  
Moulana, K., 31 Jan.

Nelson-Jones, L., 74 Feb.  
Nezer, Y., 307 July  
Nudd, G. F., 191 Apr.

O'Reilly, W. P., 417 Sept., 479 Oct., 541 Nov.  
Osborne, J. M., 459 Oct.

Palmer, T., 58 Feb.  
Pramanik, S. K., 529 Nov.

Read, D. C., 448 Oct., 525 Nov., 581 Dec.  
Ristorcelli, C. T., 571 Dec.


Schaffer, J., 37 Jan.  
Scroggie, M. G., 143 Mar.  
Self, D. R. G., 587 Dec.  
Shorter, G., 200 May, 257 June, 314 July  
Silver, S. L., 433 Sept.  
Smaal, A. C., 121 Mar.  
Smith, K. L., 107 Mar., 169 Apr., 235 May, 326 July, *Letters*,  
264 June, 414 Sept.

Telfer, D. J., 177 Apr.  
Tong, D. A., 79 Feb.  
Tuke, J. B., 240 May

"Vector", 150 Mar., 198 Apr., 296 June, 396 Aug., 496 Oct.

Waddington, D. E. O'N., 152 Apr. 550 Dec.  
Walker, P. J., 560 Dec.  
West, J. E. & Bywaters, S. F., 357 Aug., *Letters*, 512 Nov.  
Williams, E., 133 Mar.  
Williams, P., Carruthers, J., Evans, J. H. & Kinsler, J., 27 Jan.,  
95 Feb., 183 Apr., 287 June, 377 Aug., 483 Oct., 581 Dec.  
Woodard, K. G. & Ayre, D. C., 216 May, *Letters*, 365 Aug.  
Youngson, R. A. J., 431 Sept.

Abraham Lincoln  
1809-1865

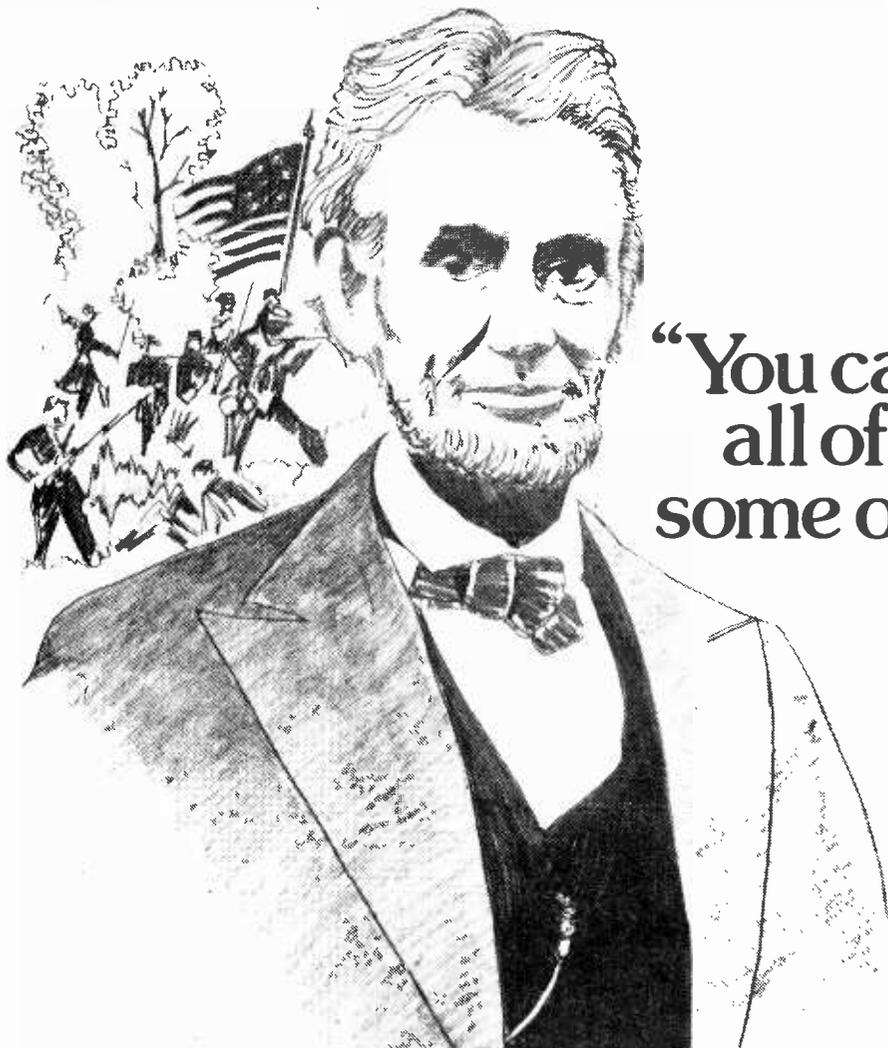

“You can fool  
all of the people  
some of the time”...

Born in Hodgenville, Kentucky, he came from humble origins. His descendants have been traced back to Puritans who emigrated to Massachusetts from England in 1637. His father was an illiterate farmer and Lincoln himself had irregular schooling.

After a succession of jobs over ten years, a friend encouraged him to study law and he practiced as a lawyer during the 1830's/40's. In 1861 he became the sixteenth president of the U.S.A.

During the American Civil War he preserved the Union and on January 1st 1863, he emancipated negro slaves.

On 14th April 1865, John Wilkes Booth, an actor and fanatical southern sympathiser, shot Lincoln through the head, he died the next day.

“But you cannot fool all  
of the people all of the time”...

We're not suggesting that our competitors try to, but . . . . . International Rectifier is the only company producing Solid State Relays offering all these advantages, from 120 to 240V up to 40 amperes, and 8 and 12 amperes up to 480V. All International Rectifier SSR's are photo-isolated, have zero-voltage switching, are I/C compatible and can be made to withstand either 1500VAC or 2500VAC isolation between output terminals and base.

But what is important, when you are not trying to fool even some of the people any of the time, is that ALL I.R. SSR's use POWER THYRISTOR JUNCTIONS not triacs.

Why not send for details and find out for yourself.



**INTERNATIONAL RECTIFIER**

HURST GREEN OXTED SURREY RH8 9BB TELEX RECTIFIER OXTED 95219 TELEPHONE OXTED 3215/4231



# IT MAKES SENSE TO

## SEW PANEL METERS

STOCKED AT  
481 Oxford Street, 311 Edgware Road  
42 Tottenham Court Rd., 3 Lisle Street  
branches or by mail order.

USED EXTENSIVELY BY  
INDUSTRY, GOVERNMENT  
DEPARTMENTS, EDUCATIONAL  
AUTHORITIES ETC.

Over 200 ranges in stocked—other ranges to  
order. Quantity discounts available. Send  
for fully illustrated brochure.

### CLEAR PLASTIC MODEL S0640

Size 85 x 64mm

50uA	£4.20		
100uA	£4.15		
200uA	£4.10		
500uA	£4.05		
50 0 500uA	£4.15		
100 0 1000uA	£4.00		
1mA	£4.05		
5mA	£4.05		
10mA	£4.05	10V DC	£4.05
50mA	£4.05	20V DC	£4.05
100mA	£4.05	25V DC	£4.05
500mA	£4.35	50V DC	£4.05
1A DC	£4.35	300V DC	£4.25
5A DC	£4.05	15V AC	£4.15
10A DC	£4.05	30V AC	£4.15
5V DC	£4.05	VU Meter	£4.45

### CLEAR PLASTIC MODEL SW100

Size 100 x 80mm

50uA	£5.05		
100uA	£4.95		
500uA	£4.75		
50 0 500uA	£4.90		
100 0 1000uA	£4.90		
1mA	£4.75		
1A DC	£4.75		
5A DC	£4.75		
20V DC	£4.75	150V AC	£4.90
50V DC	£4.75	300V AC	£4.90
300V DC	£4.05	VU Meter	£6.25

### MODEL ED107 EDUCATIONAL METER

Size 100 x 90 x 150mm including terminals

A range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working.

50uA	£9.35		
100uA	£8.70		
50 0 500uA	£8.70		
1mA	£8.40	20V DC	£8.40
1 0 1mA	£8.40	50V DC	£8.40
1A DC	£8.40	300V DC	£8.40
5A DC	£8.40	500mA 5A DC	£9.50
5V DC	£8.40	5V 50V DC	£9.50
10V DC	£8.40	5V 15V DC	£9.50
15V DC	£8.40	1A 15A DC	£9.50

### CLEAR PLASTIC MODEL S0460

Size 59 x 46mm

50uA	£3.85		
100uA	£3.80		
200uA	£3.75		
500uA	£3.70		
50 0 500uA	£3.80		
100 0 1000uA	£3.75		
1mA	£3.65	5V DC	£3.65
5mA	£3.65	10V DC	£3.65
10mA	£3.65	20V DC	£3.65
50mA	£3.65	50V DC	£3.65
100mA	£3.65	50V DC	£3.65
500mA	£3.65	300V DC	£3.65
1A DC	£3.65	15V AC	£3.80
5A DC	£3.65	30V AC	£3.80
10A DC	£3.65	VU Meter	£4.65

### CLEAR PLASTIC MODEL MR 38P

Size 42 x 42mm

50uA	£3.45		
100uA	£3.40		
200uA	£3.30		
500uA	£3.10		
50 0 500uA	£3.40		
100 0 1000uA	£3.30		
500 0 5000uA	£3.05		
1mA	£3.05		
1 0 1mA	£3.05		
2mA	£3.05		
5mA	£3.05	10V DC	£3.05
10mA	£3.05	15V DC	£3.05
20mA	£3.05	20V DC	£3.05
50mA	£3.05	50V DC	£3.05
100mA	£3.05	100V DC	£3.05
300mA	£3.05	150V DC	£3.10
500mA	£3.05	300V DC	£3.10
1A DC	£3.05	50V AC	£3.15
2A DC	£3.05	150V AC	£3.15
5A DC	£3.05	300V AC	£3.15
10A DC	£3.05	500V AC	£3.20
3V DC	£3.05	5 Meter 1mA	£4.50
		VU Meter	£3.40

\*Items with asterisk are Moving Iron type, all others are Moving Coil

### CLEAR PLASTIC MODEL S0830

Size 110 x 83mm

50uA	£4.75		
100uA	£4.65		
200uA	£4.60		
500uA	£4.55		
50 0 500uA	£4.65		
100 0 1000uA	£4.60		
1mA	£4.50		
5mA	£4.50		
10mA	£4.60	10V DC	£4.50
50mA	£4.50	20V DC	£4.50
100mA	£4.50	20V DC	£4.50
500mA	£4.50	50V DC	£4.50
1A DC	£4.50	300V DC	£4.60
5A DC	£4.50	15V AC	£4.60
10A DC	£4.50	30V AC	£4.60
5V DC	£4.50	VU Meter	£5.60

### CLEAR PLASTIC MODEL MR 45P

Size 50 x 50mm

50uA	£3.55		
100uA	£3.50		
200uA	£3.45		
500uA	£3.40		
50 0 500uA	£3.50		
100 0 1000uA	£3.45		
500 0 5000uA	£3.25		
1mA	£3.25		
5mA	£3.25		
10mA	£3.25		
50mA	£3.25	15V AC	£3.40
100mA	£3.25	300V AC	£3.40
500mA	£3.25	5 Meter 1mA	£3.75
1A DC	£3.25	VU Meter	£4.30
5A DC	£3.25	1A AC	£3.25*
10V DC	£3.25	5A AC	£3.25*
20V DC	£3.25	10A AC	£3.25*
50V DC	£3.25	20A AC	£3.25*
300V DC	£3.25	30A AC	£3.25*

### CLEAR PLASTIC MODEL MR 85P

Size 120 x 110mm

50uA	£6.00		
100uA	£5.95		
200uA	£5.90		
500uA	£5.80		
50 0 500uA	£5.95		
100 0 1000uA	£5.90		
500 0 5000uA	£5.65		
1mA	£5.75		
5mA	£5.75	50V DC	£5.75
10mA	£5.75	150V DC	£5.75
50mA	£5.75	300V DC	£5.75
100mA	£5.75	300V AC	£5.85
500mA	£5.75	5 Meter 1mA	£6.65
1A DC	£5.75	VU Meter	£7.10
5A DC	£5.75	1A AC	£5.75*
15A DC	£5.75	5A AC	£5.75*
30A DC	£5.75	10A AC	£5.75*
10V DC	£5.75	20A AC	£5.75*
20V DC	£5.75	30A AC	£5.75*

### BAKELITE MODEL S80 Enlarged Window

Size 80 x 80mm

50uA	£4.95		
100uA	£4.90		
500uA	£4.85		
50 0 500uA	£4.80		
100 0 1000uA	£4.85		
1mA	£4.80		
1A DC	£4.60		
5A DC	£4.60		
20V DC	£4.60		
50V DC	£4.60		
300V DC	£4.60		
10V AC	£4.75		
30V AC	£4.75		
300V AC	£4.75		
VU Meter	£5.95		

### CLEAR PLASTIC MODEL MR 52P

Size 60 x 60mm

50uA	£4.10		
100uA	£3.85		
200uA	£3.70		
50 0 500uA	£3.85		
100 0 1000uA	£3.70		
1mA	£3.65		
5mA	£3.65		
10mA	£3.65		
50mA	£3.65		
100mA	£3.65		
500mA	£3.65		
1A DC	£3.65	5 Meter 1mA	£4.20
5A DC	£3.65	VU Meter	£4.85
10V DC	£3.65	1A AC	£3.65*
20V DC	£3.65	5A AC	£3.65*
50V DC	£3.65	10A AC	£3.65*
300V DC	£3.65	20A AC	£3.65*
15V AC	£3.75	30A AC	£3.65*
30V AC	£3.75	30A AC	£3.65*

### BAKELITE MODEL MR 65

Size 80 x 80mm

25uA	£5.80		
50uA	£4.40		
100uA	£4.35		
500uA	£4.05		
90 0 500uA	£4.35		
100 0 1000uA	£4.30		
500 0 5000uA	£3.95		
1mA	£3.95		
1 0 1mA	£3.95		
5mA	£3.95		
10mA	£3.95		
50mA	£3.95	300V DC	£3.95
100mA	£3.95	30V AC	£3.95
500mA	£3.95	50V AC	£3.95
1A DC	£3.95	100V AC	£3.95
2A DC	£3.95	300V AC	£3.95
5A DC	£3.95	500V AC	£3.95
10A DC	£3.95	1A AC	£3.95*
15A DL	£3.95	5A AC	£3.95*
30A DC	£3.95	10A AC	£3.95*
50A DC	£3.95	20A AC	£3.95*
5V DC	£3.95	30A AC	£3.95*
10V DC	£3.95	100V AC	£3.95*
15V DC	£3.95	50A AC	£3.95*
20V DC	£3.95	500V AC	£3.95*
50V DC	£3.95	500V DC	£4.15
150V DC	£3.95	1000V DC	£4.75

### EDGWISE MODEL PE70

Size 90 x 34mm

50uA	£4.55		
100 A	£4.50		
200uA	£4.45		
500 u	£4.30		
50 0 50 A	£4.50		
100 0 100 A	£4.45		
1 A	£4.25		
10V DC	£4.25		
300V DC	£4.35		
VU Meter	£5.50		

### CLEAR PLASTIC MODEL MR 65P

Size 96 x 78mm

50 A	£4.35		
100 A	£4.25		
200 A	£4.20		
500 A	£4.15		
50 0 500 A	£4.25		
100 0 100 A	£4.20		
500 0 500 A	£4.10		
1 u A	£4.10		
5 mA	£4.10	300V DC	£4.10
10 A	£4.10	15V DC	£4.20
100 A	£4.10	150V AC	£4.20
500 A	£4.10	300V AC	£4.20
1A DC	£4.10	500V AC	£4.30
5A DC	£4.10	5 Meter 1mA	£4.85
10A DC	£4.10	VU Meter	£5.20
15A DC	£4.10	1A AC	£4.10*
20A DC	£4.20	5A AC	£4.10*
30A DC	£4.25	10A AC	£4.10*
50A DC	£4.10	20A AC	£4.10*
5V DC	£4.10	30A AC	£4.10*
10V DC	£4.10	50A AC	£4.10*
15V DC	£4.10	500A AC	£4.10*
20V DC	£4.10	1000A AC	£4.10*
50V DC	£4.10	2000A AC	£4.10*
150V DC	£4.10	5000A AC	£4.10*

### POSTAGE / PACKING & INSURANCE 15p

240" Wide Angle  
1mA METERS  
MW1 6 60 x 60 mm  
£7.00 P & Ins 15p  
MW1 B 80 x 80 mm  
£7.45 P & Ins 15p

### BATTERY LEVEL PANEL INDICATOR

18mm  
18mm Panel mounting  
OUR PRICE 95p P & Ins 15p  
& Ins 15p Discounts for quantity

### VU METER TYPE 3

250uA Size 33mm 20mm  
£1.55 P & Ins 15p

### REDUCED TO CLEAR

#### YAMABISHI VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. Input 230V 50/60Hz. Output 0-260V. P.P.P. Mounting

1A	£7.30	£1.50
2.5A	£10.35	£1.50
5A	£12.95	£1.50
8A	£19.45	£1.50
10A	£23.75	£1.50
12A	£25.90	£1.50
20A	£60.45	£1.50
25A	£64.45	£1.50
40A	£73.40	£1.50

### MODEL C720ZEN

20,000opv DC  
10 50 100 500 1000  
V AC DC Resistance  
- 10 1000 300  
centre scale DC  
Current 500uA  
2 5mA 250mA 20  
to - 63dB  
OUR PRICE £7.50 P & Ins 30p

### U4323 MULTIMETER

20,000opv Simple unit with audio/F oscillator. Suitable for general receiver tuning. Ranges: 0.5/1/10/50/250/500/1000V DC. 2.5/10/15/250/500/1000V AC. 0.05/0.5/5/50/500mA DC Resistance x 10, x 100, x 1,000, x 10,000 (50k). 500k, 5k(1, 50k) centre scale. Battery operated. Size 160 x 97 x 40mm. Supplied in carrying case complete with test leads.  
OUR PRICE £8.60 P & Ins 60p

### HIOKI 730X

30,000 opv. Overload protection. 6 30/60/300/600/1200V DC. 12/60/120/600/1200V AC. 60uA/30mA/300mA/2K/200K/2 Meg Ohm. 10 to 63dB.  
OUR PRICE £8.10 P & Ins 30p

### TMK 500 MULTIMETER KIT

Build yourself a quality 20000 opv multimeter and save money. Complete kit with meter scale, movement and rotary range selector ready mounted in cabinet. All parts, batteries, test leads and instructions. Ranges 0 0.6 6 30 120 600 1200V DC. 0 0.6 6 30 600mA Resistance 0 10 100K 1 10 Meg ohms. Decibels 20 to +63dB. Size 90 x 150 x 35mm.  
OUR PRICE £9.65 P & Ins 30p

### MODEL C720BFM

30,000 opv DC  
15,000 opv AC  
6 3 15 60 300 600  
1200V DC 6 30  
120 600 1200V AC  
DC Resistance x 1, x 10, x 100, x 1000  
(50k) centre scale  
DC Current 300uA  
3 30 600mA 20 to +63dB  
OUR PRICE £9.65 P & Ins 30p

### U4324 MULTIMETER

High sensitivity. 20,000opv. Ranges 0.6/1.2/3/12/30/60/120/600/1200V DC. 30/60/150/300/600/900V AC. Current: 0.06/0.6/6/60/600mA/2.5/25/250 DC. 0.3/3/30/300mA/3A AC. Resistance: 25/500 ohms/0.5/5/50/500 ohms/5 Mohms. Decibels - 10 to +12dB. Size 167 x 98 x 63mm. Supplied complete with test leads, spare diode and instructions.  
OUR PRICE £10.60 P & Ins 60p

### U91 Clamp VOLT AMMETER

For measuring AC voltage and current without breaking circuit. Ranges 3000/600V AC. Current 10/25/100/250/500A. Accuracy 4%. Size 283 x 94 x 36mm. Complete with carrying case, leads and fuses.  
OUR PRICE £15.10 P & Ins 60p

### HIOKI 750X VOLT-OHM-MILLIAMETER

43 ranges. 0-0.3/0.6/1.5/3/12/30/60/150/300/600/1200V DC. 0-3/6/15/30/60/120/300/600/1200V AC. Current: 0-30/60/300mA. 1.5/3/15/30/150/300mA/2.5/25/250/500mA/2.5/25/250/500V AC. Accuracy: 3% DC, 4% AC. Sensitivity: 50,000 opv DC, 5,000 opv AC. 4 inch meter. Built in protection. Size 57 x 102 x 53mm.  
OUR PRICE £12.90 P & Ins 60p

### U4312 MULTIMETER

extremely sturdy instrument for general electrical use. 667opv. 0/0.3/1.5/7.5/30/60/150/300/600/900V DC & 75mV. 0/0.3/1.5/7.5/30/60/150/300/600/900V AC. 0/300mA/1.5/6/15/150/600/600mA/

# BUY AT LASKYS

**KAMODEN 72.200 Multimeter**  
High sensitivity tester. 200,000 opv. Overload protected. Mirror scale. Ranges: 0/06/3/3/30/120/600/1200V DC. 0/3/12/60/300/11200 V AC. 0/6uA/12mA/120mA. 600mA/12A DC. 0/12A AC. -20 to +35dB. 0/2u/200u. 2 Meg/200 Megohms.  
**OUR PRICE £24.30 P & Ins 60p**

**U4341 Multimeter & Transistor Tester**  
27 ranges. 16 7000uv. Overload protected. Ranges: 5/5/5/30/60/150/300/900V DC. 1.5/7.5/30/150/300/750V AC. Current: 0.06/0.6/6/60/600mA DC. 0.3/3/30/300mA AC. Resistance: 0/06/0.6/2/20/200/200k ohms/2 Mohms. Battery operated. Supplied complete with probes, leads and steel carrying case. Size: 115 x 215 x 90mm.  
**OUR PRICE £11.85 P & Ins 60p**

**TRANSISTORISED I.C.R. AC BR 8 MEASURING BRIDGE**  
A new portable bridge offering excellent range and accuracy at low cost. Resistance: 6 ranges. 0.1 ohm-11.1 megohm. 1 inductance: 6 ranges. 1 microhenry-111 henries. 2 Capacity: 6 ranges. 10pt 1110 mfd. 2 Turns Ratio: 6 ranges. 1:1 1000:1 11100:1. Bridge Voltage at 1000cps. Operated from 9 volt battery. 100 microamp meter indication. Size: 71 x 5 x 2.  
**OUR PRICE £29.70 P & Ins 60p**

**SENN SOUND 4-CHANNEL ADAPTOR**  
Simple couple this unit to your existing stereo amplifier and add a pair of speakers and enjoy the realism of the concert hall.  
**OUR PRICE £4.95 P & Ins £1.35**

## AUDIOTRONIC EXCLUSIVE TO LASKYS

**AUDIOTRONIC HEADPHONES LSH20** Individual volume controls. Mono stereo switch. 40-19000 Hz. 8 ohms.  
**OUR PRICE £6.50 P & Ins 50p**

**AUDIOTRONIC DIGITAL CLOCK RADIOS**  
**ADC22** 24-hour clock radio covering MW FM wave bands. 60 minute sleep timer. Choice of Grey or White cabinet.  
**OUR PRICE £17.50 P & Ins £1.00**

**LSH30** Individual tone and volume controls. Mono stereo switch. 30-20,000Hz. 8ohms.  
**OUR PRICE £10.50 P & Ins 30p**

**ADC33** Deluxe 24-hour clock radio covering MW FM wavebands. 180 minute sleep timer. Buzzer alarm. Tone control.  
**OUR PRICE £19.95 P & Ins £1.00**

**LSH40** Two-way speaker system. Individual volume controls. 20-20,000 Hz. 8 ohms.  
**OUR PRICE £12.95 P & Ins 30p**

**AUDIOTRONIC HIGH ENERGY LOW NOISE CASSETTES**  
MODEL 5 10 15  
C60LN £3.59 £6.80 £9.64  
C90LN £5.13 £9.72 £13.77  
C120LN £6.15 £11.66 £16.52  
p & ins 15p per order

**AUDIOTRONIC ACO 7700** Cassette Deck with Dolby. Twin VU meters, program counter. DIN and phono input outputs. level slider controls. in sleek black brushed aluminium and teak. Freq. response 40-12kHz on normal tape and 40-16kHz on CrO<sub>2</sub> tape. W/F 0.2" and with the Dolby Noise Reduction System - a signal to noise ratio of 57dB.  
**OUR PRICE £79.95 P & Ins £1.65**

**AUDIOTRONIC MODEL ATM5** Jewel movement attractively moulded case with edgewise ohms adjustment. Ranges: 0.3/15/150/300/1200V AC. (2500 opv). 0.6/30/300/600V DC. (5000 opv). 0.300 uA/0.300mA DC. Resistance: x10 & x100 - 10 to -16dB. Supplied with battery test leads and data booklet. Size: 121 x 73 x 29mm.  
**OUR PRICE £5.40 P & Ins 25p**

**FANTAVOX FMT1 STEREO FM TUNER** 9v Battery operated FM Stereo Tuner with C.F.M. 108 MHz. Select section telescopic aerial. Edgewise Tuning and volume controls. Size only 151x66x108mm. Socket for external power supply. Simple connections.  
**OUR PRICE £12.40 P & Ins £1.65**

**AUDIOTRONIC LOW NOISE CASSETTES**  
MODEL 5 10 15  
C60 £2.05 £3.88 £5.50  
C90 £2.81 £5.34 £7.57  
C120 £3.59 £6.80 £9.64

**AUDIOTRONIC AHA101 Stereo Headphone Amplifier** All silicon. 30 watt amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. INPUTS: 5mV and 100mV. OUTPUT: 50mV per channel.  
**OUR PRICE £10.65 P & Ins 30p**

**AUDIOTRONIC Model ATM1** Top value 1,000 opv pocket multimeter. Ranges: 0.1/0.5/250/1,000 volt AC and DC. DC current 0.1mA/100mA. Resistance 0/150k ohms. Decibels 10 to -22dB. Size 90 x 60 x 28mm. Complete with test leads.  
**OUR PRICE £4.60 P & Ins 25p**

**ELECTRONIC CALCULATORS**  
We carry a tremendous range of both pocket and desk calculators by Sinclair, Hammett, Texas Instruments, Hewlett Packard, Novus, Casio, Univex, Litronic, etc. etc. Owing to the demand it is not possible to include them in this advertisement so send for our latest price list or call into any branch.

**ABSOLUTELY FREE** and available from any branch of LASKYS or by post (complete coupon below). Our brochure includes a complete price list, list of components, Calculators, Tapes, Cassette Decks, Tuners, Amplifiers, Televisions, Record Decks, Electronic Kits, Video, and a host of other accessories. A must for every hi-fi/electronics enthusiast.  
**COMING SOON! DON'T MISS OUR BUMPER 36-PAGE NOVEMBER DECEMBER CHRISTMAS CATALOGUE, STUFFED WITH GREAT BARGAINS AND GIFT IDEAS!**

**SINCLAIR PROJECT 805** Now available at special low LASKYS prices - the famous project 805 no-solder amplifier kit. Included are all necessary wires, push-on connectors, P80 pre-amp, two Z40 power boards giving 12w rms. P25 power supply and a comprehensive manual. List Price £49.97.  
**OUR PRICE £17.50 P & Ins £1.65**

**FREE HI-FI BROCHURE**

**KAMODEN HM7208 FET VOM** Input impedance 10 Megohms. Ranges: 0.25/1/2.5/10/50/1000V DC. 0/2.5/10/50/250/1000V AC. 0/25uA/2.5/25/250 mA DC. 0/5k/50k/500k/5M 500 Megohms.  
**OUR PRICE £24.30 P & Ins 60p**

**TE 200 RF SIGNAL GENERATOR** Accurate wide range signal generator covering 120 kHz-500 MHz on 6 bands. Directly calibrated. Variable R.F. attenuator audio output. Xtal socket for calibration. 220-240V a.c. Brand new with instructions. Size: 140mm x 215mm x 170mm.  
**OUR PRICE £24.30 P & Ins 60p**

**SINCLAIR Project 80 Modules** 240 Power Amp £6.60 P & Ins 15p. 260 Power Amp £6.95 P & Ins 15p. Stereo 80 Pre Amp £13.10 P & Ins 15p. 400 Pre Amp £7.40 P & Ins 15p. FM Tuner £13.10 P & Ins 15p. Stereo Decoder £8.40 P & Ins 15p. P25 Power Supply £4.85 P & Ins 30p. P26 Power Supply £4.80 P & Ins 30p. P28 Power Supply £7.90 P & Ins 30p. Walkie Talker for P28 £10 P & Ins 30p.

**BELTEK C6260 CAR AM FM RADIO & 8 TRACK CARTRIDGE PLAYER** 12V Neg earth. Has tone and balance controls. Cartridge programme indicator, automatic headlocking and comes complete with installation kit, suppressors and instructions. (No cartridge included).  
**OUR PRICE £22.50 P & Ins £1.35**

**SWR METER Model SWR3** Handy SWR meter for transmitter antenna alignment, with built-in field strength meter. Accuracy 5%. Impedance 52. Indicator 100uA DC. Full scale 5 section collapsible antenna. Size 145 x 50 x 60mm.  
**OUR PRICE £4.55 P & Ins 60p**

**L84 TRANSISTOR TESTER** Tests PNP or NPN transistors. Audio indication. Operates on two 1.5V batteries. Complete with instructions etc.  
**OUR PRICE £4.85 P & Ins 20p**

**WALKIE TALKIES SKYFON NV7** Super low cost transmitter-receivers. 100MW. With call buzzer and on/off volume control. 7 transistors. Telescopic aerial.  
**OUR PRICE £43.60 per PAIR P & Ins 50p. NOT LICENSABLE IN THE UK**

**FANTAVOX FMT1 STEREO FM TUNER** 9v Battery operated FM Stereo Tuner with C.F.M. 108 MHz. Select section telescopic aerial. Edgewise Tuning and volume controls. Size only 151x66x108mm. Socket for external power supply. Simple connections.  
**OUR PRICE £12.40 P & Ins £1.65**

**MODEL TE26 RF SIGNAL GENERATOR** Six bands. 120kHz-260MHz. Dual output RF terminals. Separate variable audio output. Accuracy ± 2%. Audio output to 8V. Power requirements 105-125V, 220-240V AC. Size 193 x 265 x 150mm. Complete with test leads etc.  
**OUR PRICE £20.45 P & Ins 60p**

**TE22 SINE SQUARE WAVE AUDIO GENERATOR** Six bands. 20cps to 200kHz on 4 bands. Sine wave 20cps to 30kHz. Output impedance with instructions. 5000 Ohms. 200/250V AC operation. Supplied brand new guaranteed, with instruction manual and leads.  
**OUR PRICE £26.90 P & Ins 60p**

**MINIATURE ORGAN MUSIC MASTER AM100** Spanning nearly two octaves, including semi-tones. This instrument will give hours of enjoyment to all the family. Beautifully finished. The keyboard range can be adjusted to be in tune with any instrument. Operates from internal 9V battery. Fitted with an on/off switch, vibrator switch, earphone socket and external 9V DC socket. Size 229mm x 127mm x 64mm.  
**OUR PRICE £9.95 P & Ins 50p**

**ELECTRONIC CALCULATORS**  
We carry a tremendous range of both pocket and desk calculators by Sinclair, Hammett, Texas Instruments, Hewlett Packard, Novus, Casio, Univex, Litronic, etc. etc. Owing to the demand it is not possible to include them in this advertisement so send for our latest price list or call into any branch.

**KAMODEN TT35 TRANSISTOR TESTER** High quality instrument to test reverse leak current and DC current. Amplification factor of NPN, PNP diodes, transistors, SCR's etc. 4" square clear scale meter. Operates from internal batteries. Complete with instructions, leads carrying handle.  
**OUR PRICE £18.90 P & Ins 60p**

**ARF 300 AF/RF SIGNAL GENERATOR** All transistorised compact fully portable. AF sine wave 18Hz to 220 kHz. AF square wave 18Hz to 100kHz. Output Square/RF. Sine wave 10V. P.P. RF 100kHz to 200MHz. Output 1V. 220/240V AC operation. Complete with instructions and leads.  
**OUR PRICE £40.50 P & Ins 60p**

**SAVE £14.00**

**ELECTRONIC CALCULATORS**  
We carry a tremendous range of both pocket and desk calculators by Sinclair, Hammett, Texas Instruments, Hewlett Packard, Novus, Casio, Univex, Litronic, etc. etc. Owing to the demand it is not possible to include them in this advertisement so send for our latest price list or call into any branch.

**SI01TR MULTIMETER TRANSISTOR TESTER** 100,000opv. Mirror scale. Overload protection 0/0.12/0.6/3/12/30/120/600V DC. 0/6/30/120/600V AC. 0/12/600uA/12/300mA/6/12A DC. 0/10k/1 Meg/100 Meg. 20Ω - 50dB. 0.01 - 0.2 MFD. Transistor tester measures Alpha, Beta and ICO. Complete with instructions, batteries and leads.  
**OUR PRICE £22.65 P & Ins 60p**

**SINCLAIR DM2 DIGITAL MULTIMETER** Will measure AC and DC volts, AC and DC current and resistance in a total of 20 ranges. The large light emitting diode display will read up to 1999 and automatically indicate polarity. Indication of positive and negative overload is also provided. The instrument is fitted with a combined carrying handle and hench stand and sockets are provided for the connection of an external power supply.  
**OUR PRICE £63.70 P & Ins 50p**

**ELIZABETHAN 8/LZ-1** 8 Track Stereo Player. Home 8 Track player with automatic and manual programme change and illuminated channel indicators for use with your hi-fi system. Size 71 x 112 D x 21. List Price £28.90.  
**OUR PRICE £14.90 P & Ins £1.35**

**SINCLAIR PROJECT 805** Now available at special low LASKYS prices - the famous project 805 no-solder amplifier kit. Included are all necessary wires, push-on connectors, P80 pre-amp, two Z40 power boards giving 12w rms. P25 power supply and a comprehensive manual. List Price £49.97.  
**OUR PRICE £17.50 P & Ins £1.65**

**CIS PULSE OSCILLOSCOPE** For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP Bandwidth 10MHz. Sensitivity at 100kHz VRMS/mm. 0.1-25 HOR. AMP. Bandwidth 500kHz. Sensitivity at 100kHz VRMS/mm. 0.3-25. Preset triggered sweep 1-3000uSec. Free running 20-200 kHz in nine ranges. Calibrator pips 220 x 360 x 430mm. 115-230V AC.  
**OUR PRICE £47.50 P & Ins £1.50**

**ELIZABETHAN 8/LZ-1** 8 Track Stereo Player. Home 8 Track player with automatic and manual programme change and illuminated channel indicators for use with your hi-fi system. Size 71 x 112 D x 21. List Price £28.90.  
**OUR PRICE £14.90 P & Ins £1.35**

**ELIZABETHAN 8/LZ-1** 8 Track Stereo Player. Home 8 Track player with automatic and manual programme change and illuminated channel indicators for use with your hi-fi system. Size 71 x 112 D x 21. List Price £28.90.  
**OUR PRICE £14.90 P & Ins £1.35**

**SINCLAIR PROJECT 805** Now available at special low LASKYS prices - the famous project 805 no-solder amplifier kit. Included are all necessary wires, push-on connectors, P80 pre-amp, two Z40 power boards giving 12w rms. P25 power supply and a comprehensive manual. List Price £49.97.  
**OUR PRICE £17.50 P & Ins £1.65**

**ELIZABETHAN 8/LZ-1** 8 Track Stereo Player. Home 8 Track player with automatic and manual programme change and illuminated channel indicators for use with your hi-fi system. Size 71 x 112 D x 21. List Price £28.90.  
**OUR PRICE £14.90 P & Ins £1.35**

**ELIZABETHAN 8/LZ-1** 8 Track Stereo Player. Home 8 Track player with automatic and manual programme change and illuminated channel indicators for use with your hi-fi system. Size 71 x 112 D x 21. List Price £28.90.  
**OUR PRICE £14.90 P & Ins £1.35**

**ELIZABETHAN 8/LZ-1** 8 Track Stereo Player. Home 8 Track player with automatic and manual programme change and illuminated channel indicators for use with your hi-fi system. Size 71 x 112 D x 21. List Price £28.90.  
**OUR PRICE £14.90 P & Ins £1.35**

**ELIZABETHAN 8/LZ-1** 8 Track Stereo Player. Home 8 Track player with automatic and manual programme change and illuminated channel indicators for use with your hi-fi system. Size 71 x 112 D x 21. List Price £28.90.  
**OUR PRICE £14.90 P & Ins £1.35**

- CENTRAL LONDON** (01)  
481 Oxford Street W1 493 8641  
10 Tottenham Court Rd W1 637 2232  
33 Tottenham Court Rd W1 636 2605  
42/45 Tottenham Ct Rd W1 636 0845  
257/8 Tottenham Ct Rd W1 580 0670  
3 Lisie Street. WC2 437 8204  
118 Edgware Road W2 723 9789  
193 Edgware Road W2 723 6211  
207 Edgware Road W2 723 3271  
311 Edgware Road W2 262 0387  
346 Edgware Road W2 723 4453  
382 Edgware Road W2 723 4194  
109 Fleet Street EC4 353 5812  
152/3 Fleet Street EC4 353 2833
- BIRMINGHAM**  
116 Corporation Street 021-236 3503
- BRISTOL**  
16-18-20 Penn Street 20421
- CROYDON**  
1046 Whitgift Centre 681 3027
- KINGSTON** 38/40 Eden St 546 1271
- LEICESTER** 45 Market Pl 537678

- LEWISHAM**  
29 Riverdale. Lewisham Centre Opening Soon
- NORTHAMPTON**  
78 Abington Street 457/5
- NOTTINGHAM**  
5-7 Lower Parliament St 489K7  
OXFORD 16 Westgate Centre 727K70
- READING**  
6 Friars Walk, Friar Street 0734 595459
- RICHMOND** 32 Hill Street 948 1411
- ROMFORD** 86 South Street 7021X
- SLOUGH**  
Unit 65, Queensmere Centre Opening Soon
- SOUTHEND**  
705 206 Churchill West 611/41
- TUNBRIDGE WELLS**  
53 57 Camden Road 2/4
- WOLVERHAMPTON**  
30 Wulfrun Way 233K4
- CHATHAM, DARTFORD, SWINDON** Opening Soon

All prices correct at 30/9/75 but subject to change without notice E. & O. E.

**TO LASKYS CUSTOMER SERVICES DIVISION (Dept. WW11)**  
Audiotronic House, The Hyde, London NW9 6JJ. Tel: 01-200 1321

Please send me the following items

Name \_\_\_\_\_

Address \_\_\_\_\_

Signature \_\_\_\_\_


TOTAL PURCHASE PRICE \_\_\_\_\_ (inc. P.P.&Ins)

Please send me your Free 32 page Hi-Fi catalogue price list   
I enclose cheque  postal order  money order

I wish to pay by Barclaycard/Access and my number is \_\_\_\_\_

Registered in England No. 347947 at 12 Lower Grosvenor Place, London SW1 0EX.

# For just £1\* the world is yours!

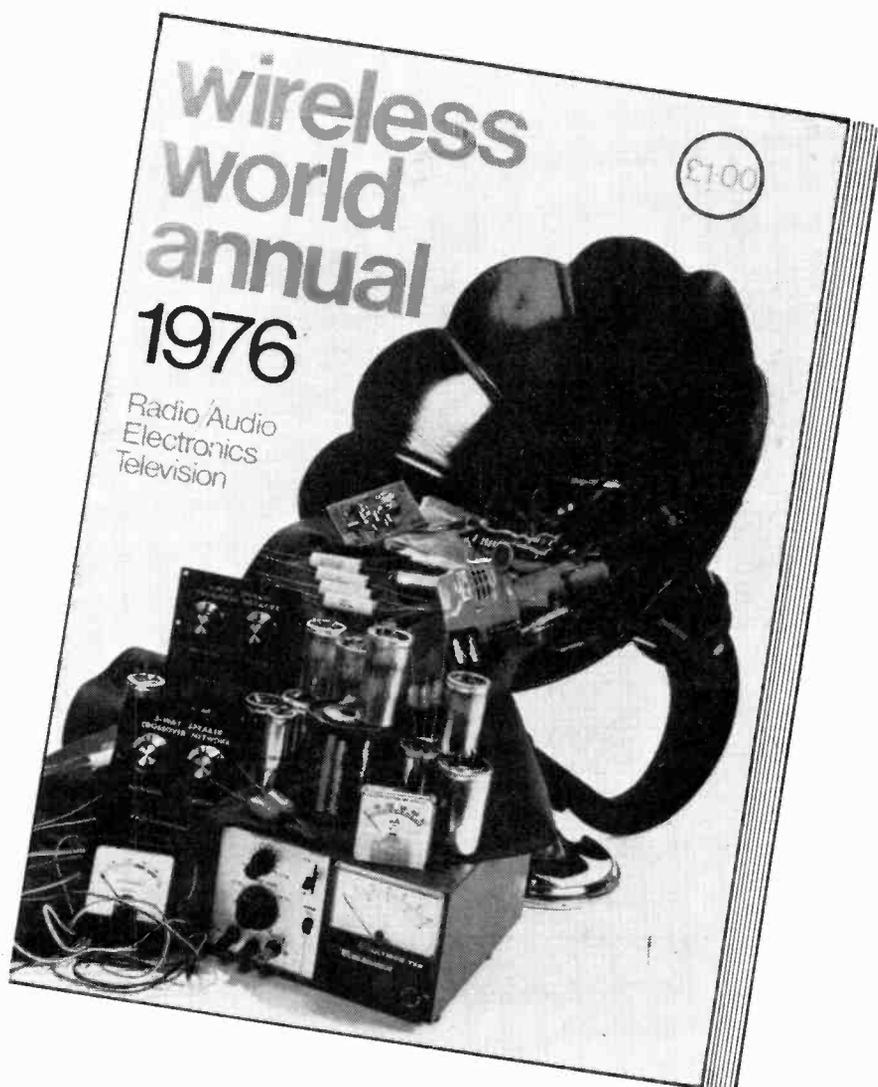

The world of electronics, television, radio/audio is on parade in the second great Wireless World annual. Constructional articles include making a photographic timer. Surveys cover video, magnetic tape compatibility, electronic ignition and radio astronomy in schools. 'How to . . .' features range from using oscilloscopes to making printed circuit boards. And there's a reference section listing standard frequency transmissions and much, much more. All written with the clarity, authority and expertise you'd expect from Wireless World.

**\*£1 from newsagents or £1.35 inclusive by post from the publishers.**

Order Coupon  
To General Sales Dept., Room 11, Dorset House, Stamford St.,  
London SE1 9LU.  
Please send me . . . . . copy/copies of Wireless World Annual 1976 at  
£1.35 inclusive.  
I enclose remittance value £ . . . . . (Cheques payable to IPC Business  
Press Ltd).

Name (please print) .....

Address .....

Company regd. in England No. 677128  
Regd. office: Dorset House, Stamford St.,  
London SE1 9LU.

# CHROMASONIC electronics

Dept. 5, 56, Fortis Green Road,  
Muswell Hill, London, N10 3HN.  
telephone: 01-883 3705

C - MOS			
	1-24	25-99	100up
CD4000AE	19p	17p	14p
CD4001AE	19p	17p	14p
CD4002AE	19p	17p	14p
CD4006AE	£1.59	£1.33	£1.06
CD4007AE	23p	19p	15p
CD4008AE	£1.75	£1.46	£1.17
CD4009AE	Use	CD4049*	
CD4010AE	Use	CD4050*	
CD4011AE	19p	17p	14p
CD4012AE	19p	17p	14p
CD4013AE	59p	50p	46p
CD4014AE	£1.75	£1.46	£1.17
CD4015AE	£1.75	£1.46	£1.17
CD4016AE	55p	48p	44p
CD4017AE	£1.29	£1.07	93p
CD4018AE	£1.89	£1.05	£1.25
CD4019AE	80p	66p	53p
CD4020AE	£1.97	£1.64	£1.31
CD4021AE	£1.75	£1.46	£1.17p
CD4023AE	19p	17p	14p
CD4022AE	£1.83	£1.53	£1.27
CD4024AE	£1.26	£1.05	84p
CD4025AE	19p	17p	14p
CD4026AE	£2.79	£2.33	£1.86
CD4027AE	98p	82p	65p
CD4028AE	£1.53	£1.28	£1.02
CD4029AE	£1.89	£1.56	£1.15
CD4030AE	71p	59p	47p
CD4035AE	£1.75	£1.46	£1.17
CD4040AE	£2.01	£1.69	£1.34
CD4042AE	£1.49	£1.24	99p
CD4046AE	£2.15	£1.79	£1.44
CD4049AE	69p	58p	46p
CD4050AE	69p	58p	46p
CD4051AE	£2.78	£2.32	£1.85
CD4052AE	£2.78	£2.32	£1.85
CD4056AE	£2.12	£1.76	£1.41
CD4060AE	£2.39	£1.99	£1.55
CD4066AE	£1.13	94p	75p
CD4068AE	28p	24p	19p
CD4069AE	28p	24p	19p
CD4070AE	28p	24p	19p
CD4071AE	28p	24p	19p
CD4077AE	71p	59p	47p
CD4081AE	28p	24p	19p
CD4082AE	28p	24p	19p
CD4085AE	£1.28	£1.06	85p
CD4086AE	£1.28	£1.06	85p
CD4093AE	£1.56	£1.20	£1.04
CD4099AE	£2.95	£2.46	£1.96
CD4511AE	£2.36	£1.79	£1.44
CD4528AE	£1.30	£1.08	87p

### I.C. SOCKETS

Pin Sockets, pins in strips of 100. Just snip off what you need. 65p per strip.

Dual in line \*

8 pin 13p.	24 pin 26p.	TO5
14 pin 15p.	28 pin 30p.	8 pin 31p.
16 pin 15p.	36 pin 39p.	10 pin 35p.

### FREE CIRCUITS

Our 8 Page A4 Audio I.C. Booklet is supplied FREE with purchases of Linear I.C.'s worth £1. or more (35p. if sold alone) Contains circuits and pin connections

- 15 Amplifiers 250 mW to 20 watts
- 5 Audio Pre-Amplifiers
- 1 Tape Pre-Amplifier
- 1 Power Driver
- 1 Instrument Amplifier (Bifet)
- 1 General Purpose Mini Amplifier
- 1 D.C. Controlled Gain Control
- 1 Micro-mini radio (2 I.C.'s)

### PHOTO-DARLINGTON

V<sub>ceo</sub> 25v 2N5777  
V<sub>ceo</sub> 25v  
V<sub>ceo</sub> 8v  
I<sub>t</sub> 250 mA  
Pd 200 mW  
Hfe 2500

35p

### LINE-O-LIGHT

NEW LED Linear Cursors each device contains 10 light emitting diodes in a 20 pin dual in-line package. Ideal for solid state analogue meters or dials. Type 101 RED £2.26. \* Complete with leaflet.

74 TTL			
	1-24	25-99	100+
7400	14p	12p	10p
7401	14p	12p	10p
7402	14p	12p	10p
7403	15p	12p	10p
7404	16p	13p	11p
7408	16p	13p	11p
7409	16p	13p	11p
7410	16p	13p	11p
7413	29p	24p	20p
7417	27p	22p	20p
7420	16p	13p	11p
7427	27p	22p	18p
7430	16p	13p	11p
7432	27p	22p	18p
7437	27p	22p	18p
7441	75p	62p	50p
7442	65p	55p	43p
7445	85p	71p	57p
7447	81p	75p	65p
7448	75p	62p	50p
7447A	95p	83p	67p
7470	30p	25p	20p
7472	25p	21p	17p
7473	30p	25p	20p
7474	32p	26p	21p
7475	47p	39p	31p
7476	32p	26p	21p
7487	75p	62p	50p
7485	£1.30	£1.09	87p
7486	32p	26p	21p
7489	£2.92	£2.80	£2.10
7490	49p	40p	32p
7491	65p	55p	45p
7492	57p	49p	39p
7493	45p	40p	33p
7495	67p	55p	45p
74100	£1.08	87p	72p
74107	35p	28p	22p
74121	34p	28p	23p
74122	47p	39p	31p
74141	78p	63p	53p
74145	68p	58p	48p
74154	£1.62	£1.48	84p
74174	£1.00	83p	67p
74180	£1.06	89p	71p
74181	£3.20	£2.50	£1.90
74192	£1.35	£1.14	90p
74193	£1.35	£1.14	90p
74196	£1.64	£1.34	97p

### 3 1/2 DECADE DVM I.C.

This state-of-the-art MOS LSI chip contains all the logic necessary for a 3 1/2 decade, dual slope integrating, automatic polarity detecting DVM. Supplied with free data and circuit booklet. AY-5-3507

OUR PRICE ONLY £6.59.\*  
(Data and Circuit Booklets alone 20p.)

### The AY-5-1224 tick-tock

Another marvel from G.I. A 16 pin 12-24 hr. Clock I.C. with 25 pin capability and low external parts count. Supplied with manufacturers detailed leaflet £3.95p\*(inc. VAT) (Leaflet alone 20p.) Full Kit (excluding case) available towards end of 1975. Phone Clive for details.

### MULLARD MODULES

Still make the simplest, highly reliable F.M. tuner

LP1186	Varactor front end	£8.60
LP1185	1 F. Stg	£6.95
LP1400	Multiplex decoder	£9.02

LINEAR I.C.'s			
555 (8 pin dip) IV	55p	AY-1-0212	£6.93
555 (10-99)T	81p	AY-1-5051	£1.44
556 (14 pin dip)	£1.29	AY-5-1224	£3.95
		AY-5-3500	£6.59
		AY-5-3507	£6.59
		AY-5-4007	£7.94
703 (RF/IF Amp)	68p	BHA0002	£3.01
709 (8 pin dip)	38p	CA2111	£1.19
709 (10-99)	45p	CA3045	£1.69
709 (14 pin dip)	39p	CA3046	88p
710 (8 pin dip)	39p	CA3053	59p
710 (10-99)	45p	CA3065	£1.60
710 (14 pin dip)	44p	CA3075	£1.64
711 (10-99)	51p	CA3078	£1.26
711 (14 pin dip)	44p	CA3080	59p
720 (A.M. Radio)	£1.76	CA3081	£1.86
723 (10-99)	£1.09	CA3082	£1.86
723 (14 pin dip)	55p	CA3089E (TDA1200)	£2.43
741 (8 pin dip)	30p	CA3097E	£1.67
741 (10-99)	43p	CA3123E	£1.76
741 (14 pin dip)	36p	CA3130	84p
747 (8 pin dip)	42p	CA3401E (LM3900)	68p
748 (10-99)	42p	CA3600E	£1.44
748 (14 pin dip)	49p		
753 (F.M. 1st I.F.)	£1.08		
75491	88p		
75492	£1.10		
Regulators 100 mA		LM2111	£1.12
78L105WC (TO-92)	60p	LM3900	69p
78L12WC (TO-92)	60p	LM3909	66p
78L15WC (TO-92)	60p	MC1306P	£1.94
		MC1306P	85p
Regulators 100mA		MC1310P	£2.10
78L05A WC (TBA625A)	90p	MC1312P	£2.52
78L12A WC (TBA625B)	90p	MC1314P	£4.34
78L15A WC (TBA625C)	90p	MC1315P	£4.95
Regulators 500mA		MC1327P	£1.48
78M05HC	£1.35	MC1330P	89p
78M12HC	£1.35	MC3401P	81p
78M15HC	£1.35	MC1339P	£1.60
78M18HC	£1.35	MC1350	68p
78M24HC	£1.35	MC1351	92p
		MC1352	92p
Regulators 1A		MC1357	£1.60
7805KC (TO-3)	£2.09	MC1358(CA3065)	£1.23
7812KC (TO-3)	£2.09	MC1375	£1.56
7815KC (TO-3)	£2.09	MC1455 (555T)	65p
7818KC (TO-3)	£2.09	MC1456C	£1.77
7824KC (TO-3)	£2.09	MC1458CP1	89p
		MC1468G	£2.30
		MC1495L	£4.48
		MC1496G	£1.01
		MC3302P	£1.65
		MC3401P	81p
ICL8030	£3.52	MFC4000B	87p
		MFC4060A	85p
		MFC6030A	85p
		MFC6040	£1.01
		MMS5314	£4.80
		MMS5316	£9.99
		MVRSV (TO-3)	£1.45
		MVR12V (TO-3)	£1.45
		MVR15V (TO-3)	£1.45
		NE5401	£1.25
		NE546A	£1.16
		NE555V	69p
		NE556	£1.29
		NE560B	£5.06
		NE561B	£5.06
		NE563	£2.96
		NE565N	£2.63
		NE566V	£1.87
		NE567V	£2.63
		SD6000	£1.22
		SL414A	£2.09
		SL415A	£2.75
		SL437D	£7.50
		SL440	£2.84
		SN75491N	88p
		SN75492N	£1.10
		ZN414	£1.26
		ZN414 Leaflet free with devices (10p alone)	
		MC1310; 2, 4 & 5 Leaflet free with devices (10p alone)	

### LED DISPLAYS

Litronix Double Digit Displays 0.5" Common Anode; 2 R/H Decimal Points DL721 ± 1.9 DL727 0.0 to 9.9 Suitable for Clocks, Meters, Instruments, Channel Indicators Our price £4.75 \* each

### DIGITAL SWITCH

BCD encoded digital switch Reading 0 to 9. Suitable for digital clock alarm setting DVM input Scaling etc. 1 to 9. £1.49 each \*

Low cost Red GaAsP Motorola MLED 500 in a TO92 package 15p.\*

0.33" Litronix DL 707 Series  
0.33" Monsanto MAN 50/70/80/3600  
0.43" Xcitan XAN 70 Series  
0.63" Litronix DL747 'Jumbo' Series

all £1.82\* each (Red only)  
all £1.82\* Each (Red, green, yellow, Orange)  
all £1.49\* Each (Red, Green, yellow)  
all £2.32\* Each (Red, Green, Yellow, Orange)  
all £2.42\* Each (Red only)  
Common Cathode as Common Anode (Red only).

### LIGHT EMITTING DIODES

Free snap-on plastic retainers

0.125" dia. lens (TIL 209)	0.16" dia. lens	0.2" dia. lens (MLED 650)
1+ 10+ 100+	1+ 10+ 100+	1+ 10+ 100+

Red	16p	15p	13p*	27p	24p	23p*	18p	16p	14p*
Green	27p	24p	22p*	33p	30p	27p*	30p	27p	25p*
Orange	27p	24p	22p*	33p	30p	27p*	30p	27p	25p*
Yellow	34p	31p	29p*	35p	32p	29p*	35p	33p	30p*

### OPTO-ISOLATORS

Our Bulk Buying Power enables a repeat of our special Offer. 0.33" (LIT 707) 90p. \*(inc. VAT) 0.63" (LIT 747) £1.99. \*(inc. VAT)

IL1 AN25 or TIL116  
6 pin industry standard package  
2.5KV isolation £1.00.\*

### MAINS TRANSFORMERS

Secondaries	VA	1A	2A	4A	
6-0-6V 100 mA	97p.*	0-9-17 V	£1.95	£2.27	£2.64
9-0-9V 100 mA	97p.*	0-12-15-20-24-30V	£2.48	£4.15	-
12-0-12V 100 mA	97p.*	0-24-30-40-48-60V	£5.18	£7.02	-
20-0-20V 1 A	£4.55	0-19-25-33-40-50V	£2.70	£3.40	£4.53
24-0-24V 500 mA	£2.48				
28-0-28V 1 A	£6.18				

p.p. on transformers 10% of price min. 20p

### VAT INC

Items followed by a \* inc. VAT at 8% all others include 25%

Overseas Customers deduct 2/27 from \* items. 1/3 from others

postage & packing 20p  
Orders for over £6. post free. Except transformers

Data Sheet and photocopy service available 10p. per page  
Advert No. 1A of Series B CALLERS WELCOME

# More than just a catalogue!


## PROJECTS FOR YOU TO BUILD

4-digit clock, 6-digit clock, 10W high quality power amp., High quality stereo pre-amp., Stereo Tuner, F.M. Stereo decoder, etc., etc.

CIRCUITS . . . Frequency Doublers, Oscillators, Timers, Voltmeters, Power Supplies, Amplifiers, Capacitance Multiplier, etc., etc. . . .

Full details and pictures of our wide range of components, e.g. capacitors, cases, knobs, veroboards, edge connectors, plugs and sockets, lamps and lampholders, audio leads, adaptor plugs, rotary and slide potentiometers, presets, relays, resistors (even 1% types!), switches, interlocking pushbutton switches, pot cores, transformers, cable and wire, panel meters, nuts and bolts, tools, organ components, keyboards, L.E.D.'s, 7-segment displays, heatsinks, transistors, diodes, integrated circuits, etc., etc., etc. . . .


Really good value for money at just 40p.

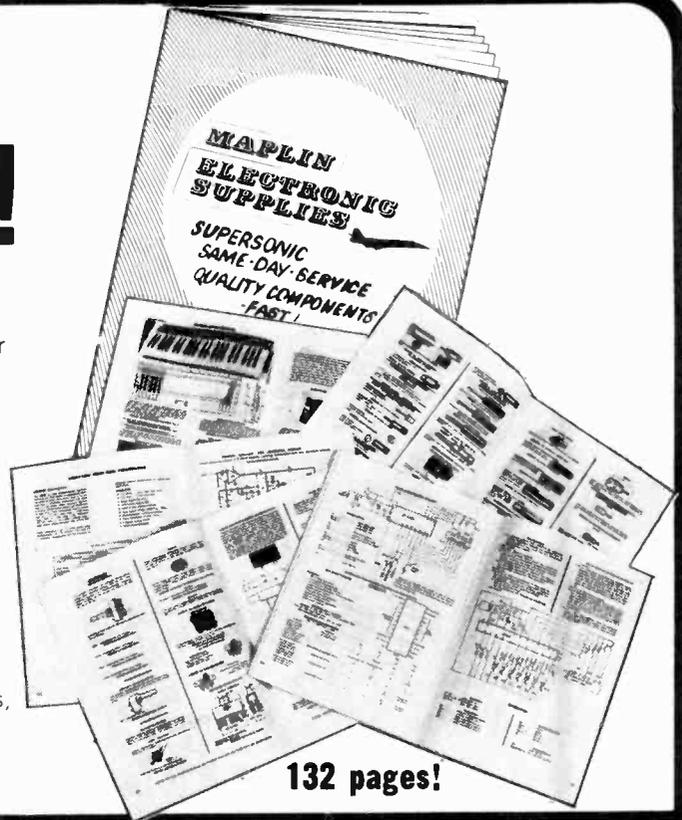

132 pages!
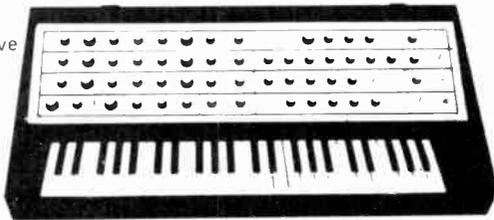
### The 3600 SYNTHESISER


The 3600 synthesiser includes the most popular features of the 4600 model, but is simpler. Faster to operate, it has a switch patching system rather than the matrix patchboard of the larger unit and is particularly suitable for live performance and portable use.



S.A.E. please for price list

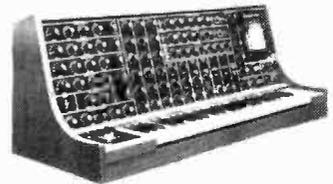
### The 4600 SYNTHESISER

We stock all the parts for this brilliantly designed synthesiser, including all the PCBs, metalwork and a drilled and printed front panel, giving a superb professional finish.



Opinions of authority agree the ET1 International Synthesiser is technically superior to most of today's models. Complete construction details available now in our booklet price £1.50. or S.A.E. please for specification

### GRAPHIC EQUALIZER

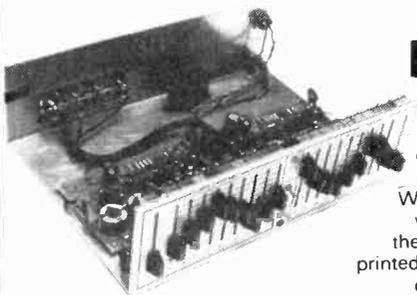

A really superior high quality stereo graphic equaliser as described in Jan. 1975 issue of ET1. We stock all parts (except woodwork) including all the metal work drilled and printed as required to suit our components and PCBs. Complete reprint of article — price 15p.

### ELECTRONIC ORGAN

Build yourself an exciting Electronic Organ. Our leaflet MES51, price 15p, deals with the basic theory of electronic organs and describes the construction of a simple 49-note instrument with a single keyboard and a limited number of stops. Leaflet MES52, price 15p, describes the extension of the organ to two keyboards each with five voices and the extension by an octave of the organ's range.



Solid-state switching and new footages along with a pedal board and a further extension of the organ's range are shown in leaflet MES53, price 35p. (Pre-publication price 15p).

### NO MORE DOUBTS ABOUT PRICES

Now our prices are GUARANTEED (changes in VAT excluded) for two month periods. We'll tell you about price changes in advance for just 30p a year (refunded on purchases). If you already have our catalogue send us an s.a.e. and we'll send you our latest list of GUARANTEED prices. Send us 30p and we'll put you on our mailing list — you'll receive immediately our latest price list then every two months from the starting date shown on that list you'll receive details of our prices for the next GUARANTEED period before the prices are implemented! — plus details of any new lines, special offers, interesting projects — and coupons to spend on components to repay your 30p

NOTE: The price list is based on the Order Codes shown in our catalogue so an investment in our super catalogue is an essential first step.

Call in at our shop, 284 London Road, Westcliff on Sea, Essex. Please address all mail to



MAPLIN ELECTRONIC SUPPLIES  
P.O. Box 3 Rayleigh Essex SS6 8LR

I enclose Cheque/P.O. value \_\_\_\_\_ ww  
For \_\_\_\_\_ copy/copies of your Catalogue  
Name \_\_\_\_\_  
Address \_\_\_\_\_

MAPLIN ELECTRONIC SUPPLIES P.O. Box 3 Rayleigh Essex SS6 8LR

# Collect Wireless World Circards. And build a valuable dossier on circuit design.


Circards is a unique and comprehensive system, launched by Wireless World, to provide professional engineers and enthusiasts with valuable and up-to-the-minute data on circuit design — data not available from any other single source.

Each Circard is 8" x 5" and usually shows a specific tested circuit, a description of the circuit operation; component values and ranges; circuit limitations and modifications; performance data and graphs.

The double-sided format enables the Circard to be filed in standard boxes for easy reference. And the plastic wallet provided keeps the cards well protected.

Circard sets (10 cards) come in wallets and cost £2.00. A subscription for 10 consecutive sets costs £18.

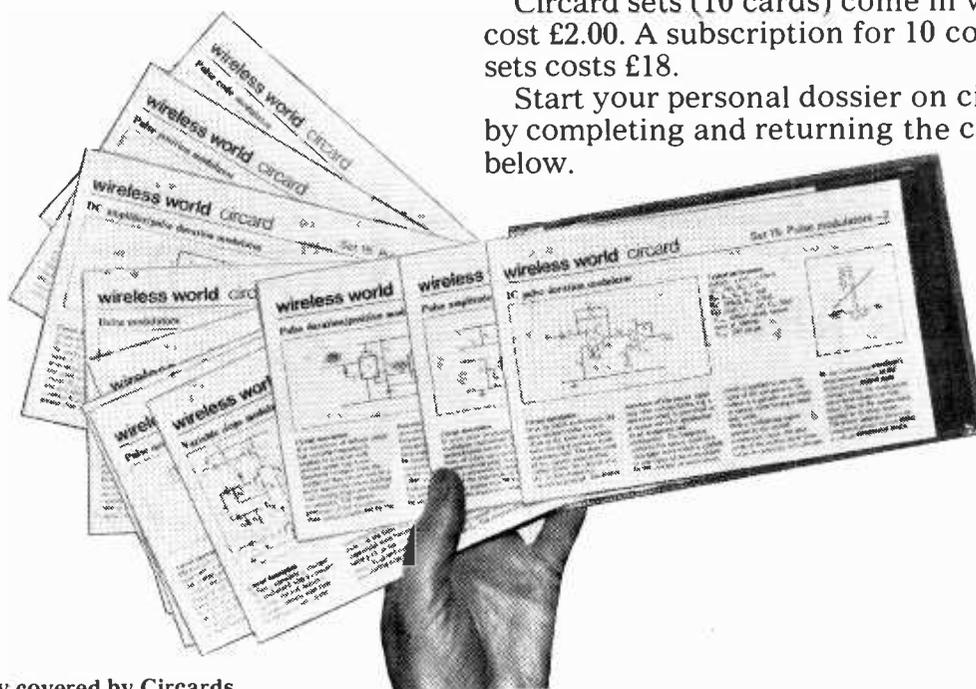Start your personal dossier on circuit design by completing and returning the coupon below.



### Subjects already covered by Circards

1. Basic active filters. 2. Switching circuits comparators and schmitts.
3. Waveform generators. 4. AC measurements.
5. Audio circuits: preamplifiers, mixers, filters and tone controls.
6. Constant current circuits. 7. Power amplifiers.
8. Astables. 9. Opto-electronics.
10. Micropower circuits. 11. Basic logic gate circuits.
12. Wideband amplifiers. 13. Alarm circuits.
14. Digital counters. 15. Pulse modulators.
16. Current differencing amplifiers — signal processing.
17. Current differencing amplifiers — signal generation.
18. Current differencing amplifiers — measurement and detection.
19. Monostable circuits. 20. Transistor pairs.
21. Voltage to frequency converters.
22. Amplitude modulators. 23. Reference circuits.
24. Voltage regulators
25. RC oscillators — I. 26. RC oscillators — II.
27. Linear C.M.O.S.—I.

To: General Sales Dept., IPC Business Press Ltd., Room 11 Dorset House, Stamford Street, London SE1 9LU

Please send me set no(s) @ £2.00 each \*  
I wish to subscribe to set no(s) @ £18.00 \*

I enclose cheque/money order for £  
\*Tick as required/Cheques to be made payable to IPC Business Press Ltd.

Name .....

Address .....

Company registered in England. Registered address, Dorset House Stamford Street, SE1 9LU, England. Registered Number 677128

# TRANSFORMERS

## CASED TRANSFORMERS

Used in smart resin coated steel cases with 3 core power cable and outlet socket. fused primary winding. Isolation types are fitted with 3-pin outlet sockets and are available with 110 volt or 240 volt output (Please state). Auto types are fitted with 2-pin trial style sockets up to 500 VA. 3-pin sockets from 750 to 3000 VA. See Auto and Isolation sections for prices. Plugs extra.



## SAFETY ISOLATING

Prim. 120/240V. Sec. 120/240V. Centre Tap with screen

VA (WATTS)	REF No.	PRICE Cased £	PRICE Plugs 2 Pin + 1 Earth £	PRICE Open £	Post £
60	149	8.60	0.88	4.37	0.56
100	150	9.40	0.88	4.90	0.64
200	151	11.70	0.88	8.14	0.80
250	152	13.15	0.88	9.80	0.88
350	153	15.75	0.88	11.88	0.95
500	154	17.50	0.88	13.62	1.13
750	155	27.35	1.10	20.59	1.04
1000	156	35.65	1.10	29.15	1.04
1500	157	42.25	1.10	33.27	1.04
2000	158	49.95	2.64	37.10	1.04
3000	159	73.50	2.64	58.55	1.04

## MINIATURE & EQUIPMENT

Primary 240V with Screen.

VOLTS		MILLIAMPS		TYPE	PRICE	Post
Sec. 1	Sec. 2	Sec. 1	Sec. 2	No.	£	£
3-3	—	200	—	238	1.50	0.25
0-6	0-6	500	500	234	1.38	0.25
0-6	0-6	1000	1000	212	1.90	0.47
9-9	—	100	—	13	1.40	0.25
0-9	0-9	330	330	235	1.50	0.25
0-8-9	0-8-9	500	500	207	1.93	0.34
0-8-9	0-8-9	1000	1000	208	2.75	0.47
15-0-15	—	40	—	240	1.35	0.25
0-15	0-15	200	200	236	1.38	0.25
20-0-20	—	30	—	241	1.35	0.25
0-20	0-20	150	150	237	1.38	0.25
0-15-20	0-15-20	300	300	205	1.93	0.47
0-20	0-20	3500	No Screen	1116	3.30	0.64
20-12-0	—	700	—	221	2.20	0.47
12	—	[D.C.]	—	—	—	—
0-15-20	0-15-20	1000	1000	206	3.50	0.56
0-15-27	0-15-27	500	500	203	3.00	0.56
0-15-27	0-15-27	1000	1000	204	3.85	0.56

## 12 and 24 VOLTS PRIMARY 200-240 Volts

VA (Watts)	Ref No.	PRICE Cased £	PRICE Plugs 2 & 3 pin £	PRICE Open £	Post £
12V	24V	—	—	—	—
0.3	0.15	242	1.58	0.34	—
0.5	0.25	111	1.38	0.34	—
1	0.5	213	1.74	0.47	—
2	1	71	2.30	0.47	—
4	2	18	2.96	0.56	—
6	3	70	4.18	0.64	—
8	4	108	4.56	0.64	—
10	5	72	5.20	0.72	—
12	6	116	5.51	0.72	—
16	8	17	7.00	0.80	—
20	10	115	10.42	0.88	—
30	15	187	13.25	1.01	—
40	20	232	14.85	1.04	—
60	30	226	16.83	1.04	—

## 30 VOLTS

AMPS	Ref.	Price	Post
0.5	112	1.90	0.47
1	79	2.40	0.56
2	3	3.50	0.56
3	20	4.50	0.64
4	21	5.15	0.72
5	51	6.40	0.72
8	117	7.16	0.88
8	88	9.55	0.95
10	89	9.67	0.95

## 50 VOLTS

AMPS	Ref.	Price	Post
0.5	102	2.58	0.47
1	103	3.48	0.56
2	104	5.03	0.64
3	105	5.81	0.72
4	106	7.58	0.88
6	107	12.30	0.95
8	118	13.20	1.13
10	119	17.02	1.13

## 60 VOLTS

AMPS	Ref.	Price	Post
0.5	124	2.30	0.56
1	126	3.41	0.56
2	127	5.09	0.72
3	125	7.52	0.80
4	123	8.75	0.95
5	40	9.75	0.95
6	120	11.20	1.01
8	121	15.00	1.19
10	122	18.20	1.19
12	189	18.50	1.19

## AUTO TRANSFORMERS

VA (Watts)	Ref No.	PRICE Cased £	PRICE Plugs 2 & 3 pin £	PRICE Open £	Post £
Tapped at 115, 220, 240 Volts					
20	113	4.10	0.20	1.71	0.47
Tapped at 115, 200, 220, 240 Volts					
150	4	6.65	0.20	4.12	0.56
200	65	7.30	0.20	4.95	0.64
300	66	8.25	0.20	5.81	0.72
500	67	11.25	0.20	8.85	0.88
750	83	14.10	0.20	10.80	0.95
1000	84	17.50	0.85	13.68	1.13
1500	93	22.15	0.85	18.31	1.13
2000	95	33.40	1.60	24.25	1.13
3000	73	48.20	2.10	35.10	1.13

## BRIDGE RECTIFIERS

ONE AMP	Price	FOUR AMP	Price
50 P.I.V.	0.25	100 P.I.V.	0.65
100 P.I.V.	0.25	200 P.I.V.	0.59
200 P.I.V.	0.28	400 P.I.V.	0.65
600 P.I.V.	0.30	600 P.I.V.	0.75


**SPECIAL OFFER!**  
**2 KVA ISOLATORS**  
 Fully impregnated & screened  
 2 primary windings 110V each  
 2 secondary windings 115V each  
 (2 matching transformers)  
**£29.50 plus carr. & VAT.**

TWO AMP	Price	SIX AMP	Price
50 P.I.V.	0.35	50 P.I.V.	0.65
100 P.I.V.	0.40	100 P.I.V.	0.70
200 P.I.V.	0.45	200 P.I.V.	0.80
400 P.I.V.	0.50	400 P.I.V.	0.90

Mid 25% VAT on all prices

## POWER UNIT

TYPE CC12-05  
 British Made

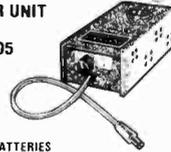

## SAVES BATTERIES

## SAVES MONEY

Housed in smart steel case, finished in hard epoxy coating. Screened for safety.  
 Output switched 3, 4.5, 6, 7.5, 9 and 12 Volts at 500 mA D.C. Operates from 240V mains, suitable for Radios, Tape Recorders, Record Players, etc.  
 Size 7.5 x 5.0 x 14.0 cm. Price £4.05 Post 30p. Plus 25% VAT.

## NEW! 2" AND 4" PANEL METERS

2"		4"	
SIZE: 60mm Wide x 45mm High x 40mm Deep.	Movement	SIZE: 110mm Wide x 82mm High x 43mm Deep.	Movement
0-50 micro A	1250	0-50 micro A	1400
0-100 micro A	580	0-100 micro A	730
0-500 Micro A	170	0-500 micro A	200
0-1 mA	170	0-1 mA	200
0-5 mA	170	0-5 mA	200
0-10 mA	6	0-10 mA	6
0-50 mA	0.5	0-50 mA	0.5
0-100 mA	0.5	0-100 mA	0.5
0-500 mA	0.5	0-500 mA	0.5
0-1 AMP	0.5	0-1 AMP	0.5
0-2 AMP	0.5	0-2 AMP	0.5
0-25 Volt	15K	0-25 Volt	15K
0-50 Volt	50K	0-50 Volt	50K
0-300 Volt	300K	0-300 Volt	300K
"g" Meter	170	"g" Meter	200
VU Meter	9250	VU Meter	5250

VU Meters are complete with detectors. Modern wide view. Price 2" £3.20 Post 10p. Price 4" £4.00 Post 10p. Lamps 60p per set. Plus 8% VAT

## C1000 MULTI-METER

Compact General Purpose Mini Multimeter  
 Input Resistance 1000 ohms per volt  
 Ranges AC Volts 0-15 50 250 1000 Volts  
 DC Volts 0-10 50 250 1000 Volts  
 DC Current 0-1 mA 0-100 mA  
 Resistance 0-150K ohms  
 Size 60 x 24 x 90 mm  
 Complete with Batteries, Test Prods. Instructions



Special price £3.35 Post 30p Plus 8% VAT.

## 1/4-WATT CARBON FILM RESISTORS

also available 1/4 watt at 70°C E 12 range 10Ω - 1MΩ. 5% tol above 470KΩ 10% tol at 95p per 100. Plus 25% VAT

## MINIATURE NEONS

6mm dia., 12mm length leads length approx. 20mm. Recommended ballast resistor: 150K ohms for 240 Volt operation. Price: Packet of 10 for 60p. Postage 15p. Plus 8% VAT

## PLEASE ADD 8% VAT ON ALL TRANSFORMERS

Send 25p for Catalogue

**A.S.P. LTD.**  
 [DEPT. WW9], SIMMONDS ROAD, WINCHEAP  
 CANTERBURY, KENT. Tel: [0227] 52436


# DATA AND COMMUNICATIONS TERMINALS

Teletype 28, 32, 33, 35, 40  
 Termino 30, 300 & 1200 (30 and 120 cps)  
 Teleterm 1030 & 1132 (portable 30 cps with integral coupler and RS 232C)  
 Other page printers (by Siemens, ITT Creed, etc.)  
 Termino 120 line printer

- ★ Spares, repairs, overhauls and maintenance
- ★ Other types and models available
- ★ Refurbished units also available
- ★ Short and long period rentals
- ★ Minicomputer interfaces
- ★ Quantity discounts
- ★ Immediate delivery

**TELEPRINTER EQUIPMENT LTD.**  
 70-80 AKEMAN STREET,  
 TRING, HERTS., U.K.

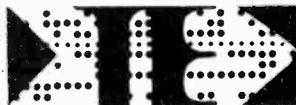Telephone 0442-82-4011  
 Cables RAHNO Tring  
 Telex 82362  
 A/B Batelcom Tring



WW-044 FOR FURTHER DETAILS

## STEREO IC DECODER

HIGH PERFORMANCE PHASE LOCKED LOOP  
 (as in 'W.W.' July '72)

## MOTOROLA MC1310P EX STOCK DELIVERY SPECIFICATION

Separation: 40dB 50Hz-15kHz  
 I/P level: 560mV rms  
 Input impedance: 50kΩ  
 Distortion: 0.3%  
 O/P level: 485mV rms per channel  
 Power requirements: 8-14V at 16mA  
 Will drive up to 75mA stereo 'on' lamp or LED.

**KIT COMPRISES FIBREGLASS PCB**  
 (Roller tinned), Resistors, I.C. Capacitors,  
 Preset Potm & Comprehensive Instructions  
**LIGHT EMITTING DIODE**  
 Suitable as stereo 'on' indicator for above

**ONLY £3.98**  
**RED GREEN**  
**WHY PAY MORE? post free 29p 59p**


**MC1310P only £2.15 plus p.p. 10p**

## NOTE

As the supplier of the first MC1310P decoder kit, of which we have sold literally thousands, our customers can benefit from our wide experience.

V.A.T.  
 Please add V.A.T. to all prices  
**FI-COMP ELECTRONICS**  
 PORTWOOD INDUSTRIAL ESTATE, CHURCH GRESLEY  
 BURTON-ON-TRENT, STAFFS. DE11 9PT

## 8 DECADE RESISTANCE BOX

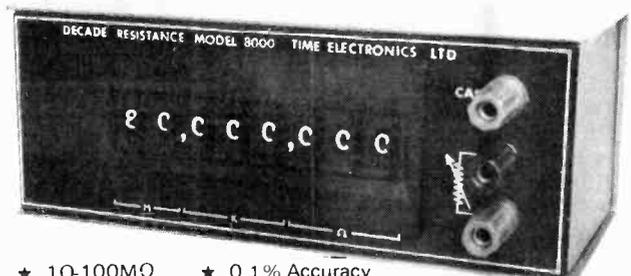


- ★ 1Ω-100MΩ
- ★ 0.1% Accuracy
- ★ Colour coded digits, Ω yellow, KΩ white, MΩ red

**TIME ELECTRONICS LTD.**  
 Botany Industrial Estate Tonbridge, Kent  
 Tel. Tonbridge (07322) 5993 (3 lines)

WW-042 FOR FURTHER DETAILS

Pack	Price	Pack	Price
1 Fibreglass printed circuit board for front end, 1 F strip, demodulator, AFC and mute circuits	£2.15	9 Function switch, 10 turn tuning potentiometer, knobs	£5.30
2 Set of metal oxide resistors, thermistor, capacitors, cermet preset for mounting on pack 1	£4.80	10 Frequency meter, meter drive components, fibreglass printed circuit board	£8.60
3 Set of transistors, diodes, LED, integrated circuits for mounting on pack 1	£6.25	11 Toroidal transformer with electrostatic screen. Primary: 0-117V-234V	£4.45
4 Pre-aligned front end module, coil assembly, three-section ceramic filter	£8.80	12 Set of capacitors, rectifiers, voltage regulator for power supply	£2.95
5 Fibreglass printed circuit board for stereo decoder	£1.10	13 Set of miscellaneous parts, including sockets, fuse holder, fuses, inter-connecting wire, etc.	£1.50
6 Set of metal oxide resistors, capacitors, cermet preset for decoder	£2.60	14 Set of metal work parts including silk screen printed fascia panel, acrylic silk screen printed tuning indicator panel insert, internal screen, fixing parts, etc.	£6.50
7 Set of transistors LED, integrated circuit for decoder	£3.45	15 Construction notes (free with complete kit)	£0.25
8 Set of components for channel selector switch module including fibreglass printed circuit board, push-button switches, knobs, LEDs preset adjusters, etc.	£8.30	16 Teak cabinet	£9.85
		One each of packs 1-16 inclusive are required for complete stereo FM tuner.	
		Total cost of individually purchased packs	£76.85

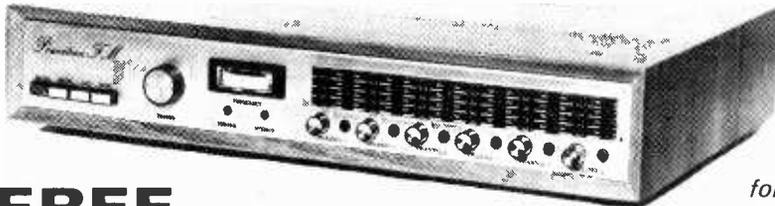

## STEREO FM TUNER KIT

In the April and May issues of *Wireless World* there was published a novel design for an f.m. tuner which combines consistent high performance with the elimination of the critical setting-up procedure required by too many earlier tuners. This original circuit has been developed further and is used as the basis for our new slimline unit. The front end is a ready built pre-aligned module which then feeds an amplifier driven screened three section ceramic filter leading to an integrated circuit five-stage limiting amplifier providing excellent a.m. rejection. This is followed by a single coil integrated balanced demodulator from which the audio output may be taken. Temperature compensated varicap tuning allows stations to be selected either by a ten-turn tuning potentiometer or by a choice of six preset push-button controls. Each of the preset controls can be adjusted on the front panel with the settings being indicated by six LED lamps behind an acrylic silk screen printed fascia panel insert. Additional circuitry includes temperature compensated AFC restricted to less than station spacing, inter-station muting, a single-lamp LED tuning indicator and a linear scale frequency meter. The stereo decoder, built on a separate board, is based on a well-proven integrated circuit phase-locked-loop to which has been added active filters to remove sub-carrier harmonics and 'birdies'. The power supply, to ensure station holding stability, uses an integrated circuit-voltage regulator which is powered via a low-hum field specially designed TOROIDAL TRANSFORMER.

STYLED TO COMPLEMENT THE WORLD-WIDE ACCLAIMED LINSLEY-HOOD 75W AMPLIFIER

for further information please write for FREE LIST

**FREE** TEAK CASE WITH FULL KITS  
 KIT PRICE only **£66.75** carriage free (U.K.)

**MORE KITS ON NEXT PAGE!**



Typical P. & P. charges at November 1st (E & OE)

	L.H. 75 Watt		F.M. Tuner		T20+20	
	Air	Sea	Air	Sea	Air	Sea
Australia	£42.60	£11.40	£26.05	£7.25	£17.05	£4.65
Canada	£23.50	£8.00	£14.40	£5.05	£9.60	£3.45
Denmark	£10.50	£7.40	£6.00	£4.65	£4.75	£3.25
Germany	£10.50	£7.65	£6.00	£4.80	£4.75	£3.35
New Zealand	£41.60	£10.75	£25.25	£6.85	£16.85	£4.40
Norway	£11.40	£7.30	£6.70	£4.50	£5.20	£3.30
Rep. S. Africa	£25.00	£7.80	£15.15	£4.85	£10.35	£3.45
Sweden	£10.90	£7.25	£6.45	£4.50	£4.95	£3.25
Switzerland	£8.90	£6.85	£5.30	£4.25	£4.10	£3.10
U.S.A.	£23.20	£9.85	£14.25	£6.30	£9.45	£4.05

## EXPORT NO PROBLEM £'s NOW HEAP CHEAP!


By special arrangement the U.K. government has continued its policy of industrial sabotage and stimulation of inflation ensuring the rapid decline in value of sterling, making it even easier for overseas readers to purchase the Powertran range of high-quality audio kits (down 12% against U.S. \$ in last 6 months!). Write now for postage quote.


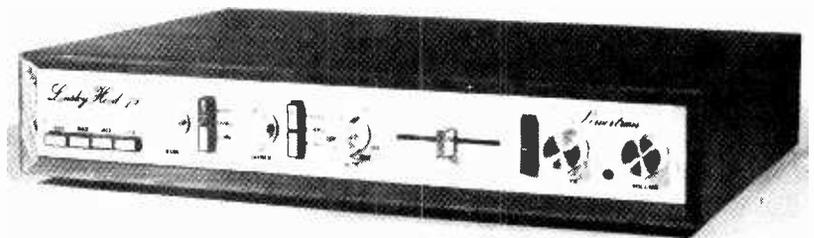
## 75W AMPLIFIER KIT

In *Hi-Fi News* there was published by Mr Linsley-Hood a series of four articles (November 1972-February 1973) and a subsequent follow-up article (April 1974) on a design for an amplifier of exceptional performance which has as its principal feature an ability to supply from a direct coupled fully protected output stage, power in excess of 75 watts whilst maintaining distortion at less than 0.01% even at very low power levels. The power amplifier is complemented by a pre-amplifier based on a discrete component operational amplifier referred to as the Linciac which is employed in the two most critical points of the system, namely the equalization stage and tone control stage, positions where most conventional designs run out of gain at the extremes of the frequency spectrum. Unusual features of the design are the variable transition frequencies of the tone controls and the variable slope of the scratch filter. There is a choice of four inputs, two equalized and two linear, each having independently adjustable signal level. The attractive slimline unit pictured has been made practical by highly compact PCBs and a specially designed Toroidal transformer.

Hi-Fi News Linsley-Hood 75W/Channel Amplifier Mk III Version (modifications as per *Hi-Fi News* April 1974)



Full circuit description in handbook (pack 15—price 30p)

**FREE** TEAK CASE WITH FULL KITS  
 KIT PRICE only **£62.40** carriage free (U.K.)

V A T Please add 25%\* to all U.K. orders

(\*or at current rate if changed)  
 U.K. ORDERS — Carriage free (MAIL ORDER ONLY)

SECURICOR DELIVERY: For Securicor delivery to mainland—add £2 + VAT per kit.  
 OVERSEAS—Postage at cost + 50p special packing, handling (remittance in sterling please)

Dept. WW12  
**POWERTRAN ELECTRONICS**  
 PORTWAY INDUSTRIAL ESTATE  
 ANDOVER, HANTS SP10 3NN

Pack	Price	Pack	Price
1 Fibreglass printed-circuit board for power amp.	£0.85	11 Fibreglass printed-circuit board for power supply	£0.65
2 Set of resistors, capacitors, pre-sets for power amp.	£1.70	12 Set of resistors, capacitors, secondary fuses, semiconductors for power supply	£3.50
3 Set of semiconductors for power amp. (now using BDY56, BD529, BD530)	£6.50	13 Set of miscellaneous parts including DIN skts, mains input skt, fuse holder, inter-connecting cable, control knobs	£4.25
4 Pair of 2 drilled, finned heat sinks	£0.80	14 Set of metalwork parts including silk screen printed fascia panel and all brackets, fixing parts, etc.	£6.30
5 Fibreglass printed-circuit board for pre-amp.	£1.30	15 Handbook	£0.30
6 Set of low noise resistors, capacitors, pre-sets for pre-amp.	£2.70	16 Teak cabinet	£9.85
7 Set of low noise, high gain semiconductors for pre-amp.	£2.40	2 each of packs 1-7 inclusive are required for complete stereo system	
8 Set of potentiometers (including mains switch)	£2.05	Total cost of individually purchased packs	£72.25
9 Set of 4 push-button switches, rotary mode switch	£3.70		
10 Toroidal transformer complete with magnetic screen/housing primary: 0-117-234 V secondaries: 33-0-33 V, 25-0-25 V.	£9.15		

WW-072 FOR FURTHER DETAILS

# BYWOOD

BYWOOD ELECTRONICS  
68 Ebbens Road  
Hemel Hempstead  
HP3 9RD  
Tel 0442 62757.

To Whom it may concern,

Please note that as from mid-November we are able to offer Litronix Class II displays in addition to our range of Litronix full-spec devices. With the Class II displays all segments are guaranteed to work but have no guaranteed match in output spec. Device availability and prices are -

FULL SPEC DISPLAYS		CLASS II DISPLAYS		* Prices Exclude VAT!
Type	Price	Type	Price	
DL701/4/7	148p	DL707E	70p	
DL721/7/8	375p	DL727E	180p	
DL746/7/750	245p	DL747E	150p	

Quantity prices for either type are available upon request.

We are also able to offer the full range of National Semiconductors Clock chips, most Mostek and Caltech clock chips, Mostek MK5039 series counter/timer chips, our MHI modular kit system, Fluorescent and other technology displays.

We accept Access and Barclay cards or CWO or accounts to accredited customers. A SAE sent to us will be returned with our latest catalogue and price list enclosed.

As we are the experts in our field why bother to contact anybody else? Call us today on 0442-62757.

P.S. 5314 Clock chip, CA3081 display driver, PCB, 4x 747E, 2x 707E = 5314EE Kit - £15 + VAT.

  
Jane Kirkpatrick,  
Managing Director.

## STANDARD TRANSFORMERS

The following types are stock items:

### Mains:

Primary 120v + 120v. Two identical secondaries

Type	Each Sec.	Total VA	Quantity	£ p
SM15-6	0-6v	15	1-9	1.92
SM15-12	0-12v		10-49	1.82
SM15-15	0-15v		50-99	1.75
SM15-20	0-20v	24	100-499	1.69
SM24-6	0-6v		1-9	2.30
SM24-12	0-12v		10-49	2.20
SM24-15	0-15v	50	50-99	2.15
SM24-20	0-20v		100-499	2.10
SM50-6	0-6v		1-9	3.75
SM50-12	0-12v	50	10-49	3.60
SM50-15	0-15v		50-99	3.49
SM50-20	0-20v		100-499	3.40

### Sub-miniature mains:

Primary 240v. Electrostatic screen. CT Secondary 1.2VA, PCB or clamp mounting

Type	Sec.	Quantity	£ p Clamp	£ p No clamp
SMS3	3-0-3v	1-9	1.60	1.56
SMS6	6-0-6v	10-49	1.50	1.47
SMS12	12-0-12v	50-90	1.43	1.40
SMS20	20-0-20v	100-499	1.37	1.34

Data sheets are available. Minimum order charge £5, post & packing extra.

## WOUND ELECTRONIC COMPONENTS LTD.

Excelcis Works, Gogmore Lane  
Chertsey, Surrey K16 9AP  
Phone: Chertsey 65147

WW-098 FOR FURTHER DETAILS

# Look AT THESE PRICES AND BUY QUALITY

TOSHIBA VALVES		Type	Price Each (p)	Type	Price Each (p)
Type	Price (p)	8C125B	15	R2008B	£2 00
DY87	30 0	BC132	25	R2010B	£2 00
DY802	30 0	8C135	15	RCA16334	80
ECC82	28 0	BC137	19	RCA16335	80
EF80	29 5	BC138	26	TIP31A	57
EF183	34 5	BC142	23	TIP32A	67
EF184	34 5	BC143	25	TIP41A	67
EH90	35 5	BC147	11	TIP42A	80
PC900	24 5	8C147A	11	2N3055	55
PCC89	40 0	8C148	10	<b>DIODES</b>	
PCC189	41 0	BC149	10	BA115	7
PCF80	31 5	8C153	15	BA145	14
PCF86	39 0	BC154	15	BA148	19
PCF801	42 0	8C157	14	BA154/201	11
PCF802	40 0	BC158	10	8Y126	11
PCL82	39 0	BC159	11	8Y127	12
PCL84	39 0	8C173	18	8Y199	27
PCL85	44 5	BC178B	20	8Y206	21
PCL86	41 0	8C182L	12	8Y238	25
PFL200	59 5	8C183L	12	OA90	6
PL36	55 5	BC187	25	OA202	7 5
PL84	25 0	8C214L	15	IN60/OA91	5
PL504	64 5	8C328	28	IN914	6
PL508	67 0	8C337	19	IN4002	5
PL519	£1.20	BD124	75	<b>INTEGRATED CIRCUITS</b>	
PY88	35 5	8D131	45	Type	Price Each (p)
PY800	33 0	8D132	39	EYTR6016	£2 00
PY500A	85 0	8D160	£1 39	MC1351P	70
		8D235	49	SN76003N	£2 35
		8D237	52	SN76013N	£1 50
		BDX32	£2 40	SN76013ND	£1 50
		8F115	20	SN76023N	£1 50
		8F160	15	SN76023ND	£1 45
		8F167	20	SN76033N	£2 35
		8F173	20	SN76227N	£1 45
		8F178	35	SN76532N	£1 45
		8F179	40	SN76660N	58
		8F180	31	SN76666N	87
		BF181	32	TAA550	49
		BF184	25	TAA700	£2 95
		BF185	25	TBA120AS	£1 00
		BF194	9	TBA120SQ	£1 00
		BF195	8	TBA480Q	£1 40
		BF196	10	TBA520Q	£2 35
		BF197	12	TBA530Q	£1 75
		8F198	23	TBA540Q	£1 75
		8F200	25	TBA550Q	£2 90
		8F218	30	TBA560CQ	£2 40
		BF224	23	TBA800	£1 50
		8F258	34	TBA920Q	£2 90
		BF336	28	TCA2700	£2 90
		BF337	35	<b>EHT MULTIPLIERS MONOCHROME (BRC) Price Each</b>	
		BF355	54	2HD 950MK1	960
		BFX86	28	2TQ 950MK2	1400
		BFY50	19	(17" & 19")	£1 85
		BFY52	20	(23" & 24")	£2.00
		BSY52	55		
		BT106	£1 20		
		BU105/02	£1 95		
		BU108	£2 10		
		BU208	£2 95		
		E1222	30		
		MJE340	45		
		OC71	15		
		OC72	16		

**EPIC**  
PRICE QUALITY SERVICE



**COMBINED PRECISION COMPONENTS (PRESTON) LTD**

Department W.  
194-200 North Rd.  
Preston PR1 1YP  
Tel: 55034  
Telex: 677122.

EHT MULTIPLIERS COLOUR		Type	Price Each
11TAQ	ITT CVC	1, 2 & 3	£4 50
11TN	GEC Sobell		£4 50
11TAZ	GEC 2110		£4 85
11TAM	Philips G8		£4 50
11TBD	Philips 550		£4 50
3TCW	Pye 691/693		£3 50
11TH	Decca 30 Series		£4 50
11TAQ	Decca Bradford		£4 50
3TCU	Thorn 3000/3500		£5 00
11HAA	Thorn 8000		£1 90
11HAB	Thorn 8500		£4 25

## New TOSHIBA TUBES

with 12 months in service guarantee

19" A49-191X equivalents	
A49-192 and A49-120X	£48 95
20" 510DJB22 equivalent	
A51-110X	£50 75
22" A56/120X	£54.25

PRICES SUBJECT TO 25% V.A.T.

All goods subject to settlement discount of 5% 7 days and 2% monthly

No postage charges or minimum order values

Write or phone for full details now.

# QUALITY AMPLIFIER KITS by POWERTRAN ELECTRONICS

## 20 WATTS/CHANNEL

Pack	Price
1 Set of all low noise resistors	£0.95
2 Set of all small capacitors	£1.50
3 Set of 4 power supply capacitors	£1.40
4 Set of miscellaneous parts including DIN sockets, fuses, fuse holders, control knobs, etc.	£1.90
5 Set of slide and push-button switches	£1.20
6 Set of potentiometers and selector switch	£2.00
7 Set of all semiconductors	£7.25
8 Special Toroidal Transformer	£4.95
9 Fibreglass PC Panel	£2.50
10 Complete chassis work, hardware and brackets	£4.20
11 Preformed cable/leads	£0.40
12 Handbook	£0.25
13 Teak Cabinet	£4.50

## TOROIDAL T20 + 20

Developed from the famous Practical Wireless Texan

Designed by Texas engineers and published in a series of articles in **Practical Wireless**. The TEXAN was a remarkable breakthrough in delivering true Hi-Fi performance at exceptionally low cost. Now further developed to include a true Toroidal transformer, this slimline integrated circuit design, based upon a single F/Glass PCB, features all the normal facilities found on quality amplifiers, including scratch and rumble filter, adaptable input selector and headphones socket.



**KIT PRICE STILL ONLY £28.25**  
post free (U.K.)

**FREE TEAK CASE and HANDBOOK** with full kits

## AND NOW OUR NEW T30 + 30 30 WATT VERSION!

The T20+20, already a development from the very successful Texan, has been developed still further to include all the improvements suggested in the P.W. July 1975 follow-up article and our new model offers RF interference filters, tape monitor facility and an additional 10 watts/channel of power

Pack	Price
1 Set of all low noise resistors	£1.05
2 Set of all small capacitors	£2.10
3 Set of 4 power supply capacitors	£2.05
4 Set of miscellaneous parts including DIN sockets, fuses, fuse holders, control knobs, etc.	£1.90
5 Set of slide and push button switches	£1.20
6 Set of potentiometers and selector switch	£2.00
7 Set of all semiconductors	£7.75
8 Special Toroidal Transformer	£6.80
9 Fibreglass PC Panel	£2.90
10 Complete chassis work, hardware and brackets	£4.80
11 Preformed cable leads	£0.40
12 Handbook (free with complete kit)	£0.25
13 Teak Cabinet	£4.50

**FULL KIT (WITH FREE TEAK CASE) ONLY £32.95**

## WIRELESS WORLD AMPLIFIER DESIGNS

Component packs for a choice of three outstanding amplifiers are stocked together with packs for a regulated power supply suitable for use with a pair of any of them. Also stocked are packs for a very well-established pre-amplifier—the Bailey-Burrows design which features six inputs, a scratch and rumble filter and wide range tone controls which may be either rotary or slider operating.

### 30W BAILEY

Pk. 1 F/Glass PCB	£1.00
Pk. 2 Resistors, capacitors, pots	£2.35
Pk. 3 Semiconductor set	£4.70

### 20W LINSLEY-HOOD

Pk. 1 F/Glass PCB	£1.05
Pk. 2 Resistors, capacitors, pots	£3.20
Pk. 3 Semiconductor set	£3.35

### 60V REGULATED POWER SUPPLY

Pk. 1 F/Glass PCB	£0.95
Pk. 2 Resistors, capacitors, pots	£1.95
Pk. 3 Semiconductor set	£3.10

### BAILEY-BURROWS PRE-AMP

Pk. 1 F/Glass PCB	£2.35
Pk. 2 Resistors, capacitors, pre-sets, transistors	£6.10

Pk. 3R Rotary potentiometer set	£2.00
Pk. 3S Slider potentiometer set (with knobs)	£2.70

### STUART TAPE RECORDER

A set of three printed-circuit boards has been prepared for the stereo integrated circuit version of this high-performance *Wireless World* published design.

TRRP Pk. 1 Replay amplifier F/Glass PCB	£1.10
TRRC Pk. 1 Record amp./meter drive cct. F/Glass PCB	£1.60

TROS Pk. 1 Bias/erase/stabilizer cct. F/Glass PCB	£1.20
---	-------

For details of component packs for this design please write for free list.

## ACTIVE FILTER CROSSOVER

An essential and critical component in a high-quality speaker system is the crossover unit conventionally comprising of a series of passive networks which unfortunately, though introducing reactive impedances between the amplifier and the speakers, result in the loss of the advantage of high amplifier damping factor and renders the speakers prone to overshoots and resonances. An elegant solution to this problem, described by D. C. Read in *Wireless World*, involves the use of a series of active filters splitting the output of the pre-amplifier into three channels, of closely defined bandwidth, each of which is fed to the appropriate speaker by its own power amplifier. A design for a suitable 20-watt amplifier, based on a proven Texas circuit, was also described by Mr Read. The printed-circuit board for this has been designed such that three amplifiers may be stacked and mounted together on a common heat sink to achieve a conveniently compact module.

### ACTIVE FILTER

Pack	Price
1 Fibreglass PCB (accommodates all filters for one channel)	£1.05
2 Set of pre-sets, solid tantalum capacitors, 2% metal oxide resistors, 2% polystyrene capacitors	£4.20
3 Set of semiconductors	£2.65
2 off each pack required for stereo system	

SUITABLE ALSO FOR FEEDING ANY OF OUR HIGH-POWER DESIGNS

### READ/TEXAS 20w amp.

Pack	Price
1 Fibreglass PCB	£0.70
2 Set of resistors, capacitors pre-sets (not including O/P coupling capacitors)	£1.10
3 Sets of semiconductors	£2.40
6 off each pack required for stereo system	
4 Special heat sink assembly for set of 3 amplifiers	£0.85
5 Set of 3 O/P coupling capacitors	£1.00
2 off packs 4, 5 required for stereo system	

### POWER SUPPLY

FOR 20W/CHANNEL STEREO SYSTEM	
Pack	Price
1 Fibreglass PCB	£0.50
2 Set of rectifiers, zener diode, capacitors, fuses, fuse holders	£2.60
3 Toroidal transformer	£4.95

**MORE KITS ON PAGE 51**

## SEMICONDUCTORS

as used in our range of quality amplifiers

2N699	£0.25	BFY51	£0.20
2N1613	£0.20	BFY52	£0.20
2N1711	£0.25	CA3046	£0.70
2N2926G	£0.10	LF1186	£5.50
2N3055	£0.45	MC1310	£2.90
2N3442	£1.20	MC1351	£1.05
2N3711	£0.09	MFC4010	£0.95
2N3904	£0.17	MJ481	£1.20
2N3906	£0.20	MJ491	£1.30
2N4062	£0.11	MJE521	£0.60
2N4302	£0.60	MPSA05	£0.25
2N5087	£0.42	MPSA12	£0.55
2N5210	£0.54	MPSA14	£0.35
2N5457	£0.45	MPSA55	£0.25
2N5459	£0.45	MPSA65	£0.35
2N5461	£0.50	MPSA66	£0.40
2N5830	£0.30	MPSU05	£0.60
40361	£0.40	MPSU55	£0.70
40362	£0.45	SB4750A	£2.50
BC107	£0.10	SL301	£1.30
BC108	£0.10	SL3045	£1.60
BC109	£0.10	SN72741P	£0.40
BC109C	£0.12	SN72748P	£0.40
BC125	£0.15	TIL209	£0.30
BC126	£0.15	TIP29A	£0.50
BC182	£0.10	TIP30A	£0.60
BC212	£0.12	TIP29C	£0.71
BC182K	£0.10	TIP30C	£0.78
BC212K	£0.12	TIP41A	£0.74
BC182L	£0.10	TIP42A	£0.90
BC184L	£0.11	TIP41B	£0.82
BC212L	£0.12	TIP42B	£0.98
BC214L	£0.14	1N914	£0.07
BCY72	£0.13	1N916	£0.07
BD529	£0.85	1S920	£0.10
BD530	£0.85	5805	£1.20
BDY56	£1.60		
BF257	£0.40	FM4	£0.80
BF259	£0.47	SF610 7MA	£2.80
BFR39	£0.25		
BFR79	£0.25		

V.A.T. Please add 25%\* to all U.K. orders

(\* or at current rate if changed)

U.K. ORDERS—Post free (mail order only)

SECURICDR DELIVERY—for this optional service (Mainland only) add £2.00 + VAT per kit

OVERSEAS—Postage at cost + 50p special packing, handling (remittance in sterling please)

Dept. WW12

**POWERTRAN ELECTRONICS**

PORTWAY INDUSTRIAL ESTATE ANDOVER, HANTS SP10 3NN

# TRAMPUS



**58-60 GROVE ROAD, WINDSOR, BERKS, SL4 1HS**  
 ADD 8% VAT TO PRICES MARKED\*. ADD 25% VAT TO ALL OTHER PRICES  
 SEND C.W.O. (EXCEPT GOV'T DEPTS. ( POST & PACKING 20p IN U.K.  
 NEW FAST SERVICE LOW PRICES. MONEY BACK IF NOT SATISFIED. ALL BRAND  
 NEW TOP SPEC. DEVICES. CALLERS WELCOME.  
 NEW LIST FREE. SEND S.A.E. BARCLAYCARD & ACCESS WELCOME

## INTEGRATED CIRCUITS



DL707 COM. ANODE &  
 DL704 COM. CATH.  
 0.3" 0-9dp £1\* ea  
 747 JUMBO 0.6" CA  
 LED DISPLAY £2.25\*  
 3015F 0-9dp £1\*  
 DL33 MINI 3 DIGIT  
 & MAGNIFIER £1.50\*  
 STROBE TUBE £5\*

## LEDS red 12p.

209 STYLE OR 0.2" NO CLIP 12p\*  
 TIL209 or 0.2" RED & CLIP 14p\*  
 GREEN LARGE/SMALL & CLIP 19p\*  
 ORANGE LARGE/SMALL & CLIP 19p\*  
 ORP12 57p\* 2N5777 33p\*  
 TEC12 PHOTO IC SC\*ITT £1\*  
 IC AY51224 4 DIGIT CLOCK £3.75\*  
 MM5316 £5. OR MM5314 6 DIGIT £4.00\*

**CAPACITORS**  
 CERAMIC 22pf-0.1uf 50v 5p.  
 ELECTROLYTIC:10/50/100 uf in  
 25V 7p. 50V 9p. 2uf/10V 6p.  
 1000uf 25V 18p. 200/500uf 9p.  
 POTENTIOMETERS LIN/LOG 14p.  
 PRESETS 6p. RESISTORS 14p ea

703 RF/IF 26p MC1303 £1.50  
 709 T099 22p\* MC1310 £2.20  
 709 DIL 14 28p\* MC1312 SQ £2.50  
 710 DIL 14 31p\* MC1318 £2.50  
 723 Regul'r 45p\* MC1330 75p  
 741 DIL 8 21p\* MC1339 £1.40  
 741 DIL 14 31p\* MC1350/1/2 75p  
 741 T099 31p\* MC1466 /9 £3  
 747 2x741 67p\* MC4000 1W 49p  
 748 DIL 8 27p\* NE536 FETOPA £2\*  
 7805 5V £1.25\* NE540 £1.10\*  
 7812 12V £1.25\* NE550 2v7 £1\*  
 7815 15V £1.25\* NE555 TIMER 42p\*  
 7900 Series £2\* NE556 2x" 88p\*  
 76013 6W 4F 75p NE560 PLL £4.00  
 CA3046 54p NE561 PLL £4.00  
 CA3048 £2 NE562 PLL £4.00  
 CA3054 £1.50 NE563 £2.25  
 ICL8038 SGEN £3\* NE565 £2.50  
 LM300 £1.50\* NE566 £1.55  
 LM301 OPA 41p\* NE567 £2.20  
 LM304 0-40V £3\* SN72741 741 21p\*  
 LM308 HI Bo 95p\* SN76660 IF 75p  
 LM309K 5V £1.75\* SN76611 IF £1  
 LM372 IF £2.00 TAD100 & IF £2  
 LM377 2x2W £3 TBA800 89p  
 LM380 60745 89p TBA810 7WAF 99p  
 LM381 £1.50 TBA820 75p  
 LM3900 40PA 63p\* ZN414 RX 99p

## TRANSISTORS

PRICE EACH:-  
 AC127 & 128 11p\*  
 AC176 9p\*  
 AC187 & 188 11p\*  
 AD149 45p\*  
 AD161 & 162 33p\*  
 BC107 8p\*  
 BC107B 12p\*  
 BC108 8p\*  
 BC108B 12p\*  
 BC109 9p\*  
 BC109C 12p\*  
 BC147/8/9 2p  
 BC157/8/9 12p  
 BC167/8/9 12p  
 BC177/8/9 18p  
 BC182/3/4A&L10p  
 BC212/3/4A&L12p  
 BCY70/1/2 16p\*  
 BD131 & 132 39p\*  
 BFR88 250V 35p  
 BFY50 14p\*  
 BFY51 14p\*  
 BFY52 & 53 14p\*  
 BSX19/20/21 16p\*  
 MJ2955 T03 75p\*  
 MJE2955 99p\*  
 MJE3055 67p\*  
 YPU131 PUT 49p

**MATCHING** 20p\*  
 INS. BUSH SET 6p\*  
 TIP29 & 30 43p\*  
 TIP31 & 32 54p\*  
 TIP41 68p\*  
 TIP42 74p\*  
 TIP2955 99p\*  
 TIP3055 67p\*  
 TIS43 UJCT' 32p  
 ZTX107/8/9 11p  
 ZTX300 & 304 20p  
 ZTX500 & 504 42p  
 ZN706 & 708 11p\*  
 2N2646 UJT 38p\*  
 2N2904 & 5 20p\*  
 2N2926b broyg 9p  
 2N3053 16p\*  
 2N3054 42p\*  
 2N3055 115V 37p\*  
 2N3055 RCA 60p\*  
 2N3702/3/4/5 9p  
 2N3706/7/8/9 9p  
 2N3710 & 11 10p  
 2N3819E FET 14p  
 2N3820 FET 4p  
 2N3823E FET 16p  
 2N3904/5/6 15p  
 2N4289 mini 31p  
 2N5457 FET 45p

## DIODES

0A91 & 0A91 GERMANIUM 5p.  
 1N4001 1A50V & 1N4002 5p\*  
 1N4004 6p\* 1N4007 9p\*  
 1N4148 & 1N914 SILICON 4p.  
 ZENERS 4ZY88 400mW 9p.  
 ZENERS 14" 17P. 21Jmoteef1  
 BRIDGE RECTIFIER 1A50 18p  
 1A400V 25p. 4A100V 45p

## SCR's TRIACS

SCR's TAG1/400 1A400V 50p\*  
 1A50V 38p\* 1A 600V 70p\*  
 C106D 1A400V SCR ONLY 47p\*  
 TRIAC SC146D 10A400V £1\*  
 TRIAC DISCO 15A400V £2\*  
 DIACS: ST2 20p. BR100 25p

## vero

36PINS 28p\* FACE CUTTER 19p\*  
 COPPERCLAD 0.1 PITCH VERO  
 2 1/2"x5" 32p\* 2 1/2"x3 1/2" 29p\*  
 3 1/2"x5" 37p\* 3 1/2"x3 1/2" 32p\*  
 3 1/2"x17" £1.70\*  
 3 1/2"x17" PLAIN 0.1" £1.06\*  
 DIL BREARBOARD 6x4" £2\*

## DALO pen 69p

DALO ETCH RESIST PEN 69p\*  
 PEC ETCH PAK 500gm 89p\*  
 6x4" COPPER BOARD 50p\*  
 PCB KIT 3 ITEMS £2\*  
 CASSETTE MECHANISM £9 & £13  
 TGS GAS DETECTORS 308etc £2\*

## DIL sockets

TOP QUALITY NYLON  
 SOCKETS SPIN 12p\*  
 14PIN 13p. 16PIN 14p  
 SOLDERCON PINS:  
 100 65p. 1000 £4\*

## 740 TTL



HEATSINKS: T05 & T015 5p\* TV4 15p\*  
 TV3/T03 16p\* EXTRUDED 4" 4Y1 29p\*

SWITCHES: SPST 18p. DPDT 25p.  
 DIN PLUGS ALL 12p. SOCKETS ALL 9p  
 ALL CASES ABS/AB7 50p. AB13 65p\*  
 TRANSFORMERS 1/1A 6 or 12V £1.50\*

TRAMPUS FULL SPEC PAKS ALL £1 ea  
 PAK A 10 RED LEDS our choice £1\*  
 PAK B 5 741C OP A/P 9 PIN £1\*  
 PAK C 4 2N3055 £1\*. D 12 BC109E £1\*  
 PAK E 10 BC182 £1\*. F 11 2N3704 £1  
 PAK G 8 BFY51 £1\*. H 9 2N3819e £1  
 PAK J 9 2N3053 £1\*. K 40 1N914 £1



7400 11p\* 7474 29p\*  
 7401 13p\* 7476 29p\*  
 7402 13p\* 7490 39p\*  
 7404 15p\* 7491 73p\*  
 7410 13p\* 7492 43p\*  
 7413 29p\* 7493 39p\*  
 7420 13p\* 7494 46p\*  
 7430 13p\* 7496 74p\*  
 7440 13p\* 74100 £1\*  
 7441 34p\* 74121 27p\*  
 7442 67p\* 74123 65p\*  
 7470 26p\* 74141 64p\*  
 7472 24p\* 74173 £2\*  
 7473 29p\* 74174 £1\*  
 7475 35p\* 74175 35p\*

## CMOS LOGIC

CD4000 MC14 & 145K AVAILABLE.  
 CD4000 15p\* CD4028 £1.29\*  
 CD4001 16p\* CD4046 £2\*  
 CD4002 16p\* CD4047 £1.49\*  
 CD4009 65p\* CD4049 59p\*  
 CD4011 20p\* CD4054 £1.89\*  
 CD4013 53p\* CD4055 £1.89\*  
 CD4016 49p\* CD4060 £2.25\*  
 CD4017 £1.15\* CD4071 23p\*  
 CD4018 £1.69\* CD4081 23p\*  
 CD4022 £1.55\* CD4510 £1.49\*  
 CD4023 18p\* CD4511 £2.25\*  
 CD4024 £1.15\* CD4528 £1.10\*  
 CD4027 89p\* CD4558 £2.35\*

WW-019 FOR FURTHER DETAILS

# TRANSISTORS + DIODES

Type	Price excluding VAT	Price including VAT	Type	Price excluding VAT	Price including VAT
BC 107	0.090	0.113	2N 930	0.200	0.250
BC 107A	0.130	0.163	2N 1132	0.240	0.300
BC 107B	0.140	0.175	2N 2129	0.240	0.300
BC 108	0.090	0.113	2N 2218A	0.220	0.275
BC 108A	0.130	0.163	2N 2219	0.220	0.275
BC 108B	0.130	0.163	2N 2219A	0.220	0.275
BC 108C	0.140	0.175	2N 2221	0.180	0.225
BC 109	0.090	0.113	2N 2221A	0.210	0.263
BC 109B	0.140	0.175	2N 2222	0.200	0.250
BC 109C	0.140	0.175	2N 2222A	0.250	0.313
BC 184(K)	0.120	0.150	2N 2904	0.190	0.238
BC 212A(K)	0.110	0.138	2N 2905A	0.230	0.288
BC 212B(K)	0.110	0.138	2N 2906	0.170	0.213
BC 213C(K)	0.110	0.138	2N 2906A	0.170	0.213
BC 214B(K)	0.110	0.138	2N 2907	0.220	0.275
BCY 71	0.220	0.275	2N 2907A	0.240	0.300
BFY 50	0.200	0.250	2N 3053	0.180	0.225
BFY 51	0.200	0.250	2N 4037	0.250	0.313
BD 131A	0.360	0.450	1N 4001	0.050	0.054
BD 135	0.360	0.450	1N 4002	0.065	0.070
BD 136	0.396	0.495	1N 4003	0.070	0.076
BD 137	0.432	0.540	1N 4004	0.075	0.081
BD 138	0.450	0.563	1N 4005	0.080	0.086
BD 139	0.495	0.619	1N 4006	0.085	0.092
2N 929	0.230	0.288	1N 4007	0.090	0.097
			1N 4148	0.040	0.050

**REPLECOMPS Ltd.** Telephone: Hastings 427914  
 123 Bohemia Road, ST. LEONARDS-ON-SEA, Sussex TN376RL

## quality

Manufactured strictly to stringent specifications.  
 12 months guarantee.

## service

Orders actioned in 24 hours.  
 Over one million transistors in stock.

## special discounts

For large quantities ordered by retailers, educational establishments and hobby clubs.


## terms

Cash with order, please.  
 Post and Packing 20p.  
 Minimum order 50p.


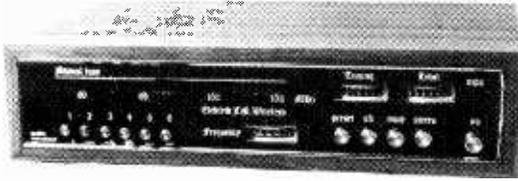
# BY POPULAR DEMAND.


Yes indeed. We get asked to do it so often, so that we went out and really did it. A complete series of FM tuner systems in sleek teak cases, with eggshell finish mild steel chassis, and really durable front panel. We think that we have provided an FM tuner for most tastes and budgets. In fact, a three meter receiver, if you'll pardon the pun. (100MHz = 3 metre wavelength, get it, eh?)



The Elektrik FM Wireless System: a brief specification is shown in the following order, beneath each system description:

Input for 26dB S/N	Image rejection	AF output	THD	
Larsholt 7252† + 993090†	.. .. .	.. .. .	.. .. .	£60.75
1uV	-56dB	1.5v	0.3% typ. mpx.	
Larsholt 7253† + BLR3107 mpx filter	.. .. .	.. .. .	.. .. .	£50.75
1.2uV	-55dB	80mV	0.55% typ. mpx.	
EF5603 + 8001 IF & decoder*	.. .. .	.. .. .	.. .. .	£48.00
0.9uV	-85dB	80mV	0.5% typ. mpx.	
EC3302 + 8001 IF & decoder*	.. .. .	.. .. .	.. .. .	£40.00
1.2uV	-52dB	80mV	0.5% typ. mpx.	

† Built and tested modules \* Parts kits

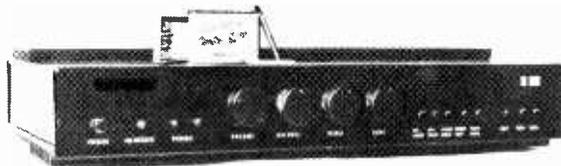

The U66 25+25W amplifier, with mpx tuner. A superb low look receiver kit, with aluminium extrusion case, one piece PCB construction, toroidal transformer, modular tuner section. The features include tape monitor, loudness (volumer section) and a fully fuse protected PSU and output section. . . . . £76.00

Varicap tuned MW/LW receiver modules - the 7003 series. The latest development - with FET input, ferrite rod, electronic switching for MW/LW, ceramic filter. 9003 kit - £9.85, 9003 built £11.85.

### SGS audio amplifiers and applications PCBs.

- TDA2020 20w rms with sufficient heatsink .. . . . 2.99.
- TDA2020k 2xTDA2020 with PCB and R's&C's .. . . . 7.85.
- TCA940 10w rms IC with heatsink .. . . . 1.85.
- TCA940k 1xTCA940, PCB, R's,C's heatsink .. . . . 3.05.
- TBA810s 7 w rms IC .. . . . 1.30.
- TBA810k 1xTBA810, PCB, R's, C's, heatsink .. . . . 2.75.

All SGS approved PCBs, all devices overload protected.

### More new things:

Birdy filter for stereo radio. Flat to 55kHz, whereupon the slope dives off to -33dB at 200kHz. Fit between the detector and stereo decoder. . . . . 1.75.

3000 series stereo control amp/4000 series PU amp/ 2000 series AFU/ Ferranti small signal devices/Motorola power discretes (BD165-609-etc).


Postage £2.50 per tuner system. VAT extra at 25%. Full catalogue 40p, postage for general component orders is 22p - Shortform price list available FOC with an SAE.

**ambit** int  
**37 High Street**  
**BRENTWOOD Essex**

Post code: CM14 4RH, telephone 216029; tlx 995194.

## HART ELECTRONICS

### Audio Kit Specialists since 1961

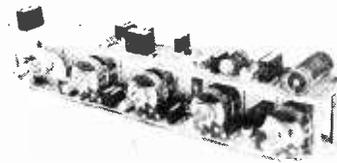

**BAILEY/BURROWS/QUILTER PRE AMP** This is the tone control section of the best pre-amp kit currently available. Consider the advantages:—\*First quality fibreglass printed circuits with roller tinned finish and all component locations printed on reverse \*Low noise carbon film and metal film resistors throughout. \*Finest quality low-noise ganged controls with matched tracks and shafts cut to length. \*Well engineered layout for total stability. \*Special decoupling and earthing arrangements to eliminate hum loops. \*Controls, switches and input sockets mount directly on the boards to TOTALLY ELIMINATE wiring to these components. (We know of one pre-amp kit which claims its controls mount directly on the board—and so they do, by their shaft bushes! You still have to wire them up!!)

\*We incorporate the Quilter modification which is most important as it reduces distortion and increases the bass and treble control range.

As can be seen from the photograph the tone control unit is very slim (only 1 1/2" from front to back) and may therefore be used in many other applications than our Bailey metalwork which it is designed to fit.

**F. M. TUNER.** Several useful modifications have been made to our compact tuner. The mechanical layout with all its advantages is retained and four important electrical extras are now offered: 1. Multi-turn preset pots for easier tuning. 2. MPX filter for trouble free taping. 3. Extra thermal stabilisation for tuning line to eliminate drift. 4. Provision for remote control tuning of as many stations as you require.

**STUART TAPE CIRCUITS** Our printed circuits and components offer the easy way to convert any suitable quality deck into a very high quality Stereo Tape unit. Input and output levels suit Bailey pre amp. Total cost varies but around £35 is all you need. We can offer tape heads as well if you want new ones.

All above kits have fibreglass PCB's. Prices exclude VAT but P&P is included.

**FURTHER INFORMATION ON ALL KITS FREE** if you send us a 9 in. x 4 in. S.A.E.

**REPRINTS** Post free, no VAT.

**Bailey 30W 18p.**

**STUART TAPE RECORDER** All 3 articles under one cover 30p.

**BAILEY/BURROWS/QUILTER** Preamp circuits, layouts and assembly notes 15p.

All prices exclude VAT.

## Penylan Mill, Oswestry, Salop

Personal callers are always welcome, but please note we are closed all day Saturday

# THE RADIO SHOP

16 CHERRY LANE  
 BRISTOL BS1 3 NG



TELEPHONE  
 0272-421196

### TRIACS

1.6AMP PLASTIC		6AMP ISOLATED TAB		10AMP ISOLATED TAB	
NAS0161W	100V .28	NAS0651W	100V .85	NAS1001W	100V .72
NAS0161X	100V .28	NAS0651X	100V .85	NAS1001X	100V .72
NAS0162W	200V .30	NAS0652W	200V .81	NAS1002W	200V .78
NAS0162X	200V .29	NAS0652X	200V .81	NAS1002X	200V .78
NAS0164W	400V .40	NAS0654W	400V .72	NAS1004W	400V 1.09
NAS0164X	400V .38	NAS0654X	400V .70	NAS1004X	400V 1.04
NAS0166W	600V .50	NAS0656W	600V .88	NAS1006W	600V 1.36
NAS0166X	600V .48	NAS0656X	600V .78	NAS1006X	600V 1.36

3.5AMP CLIPPED TAB		8.5AMP ISOLATED TAB		15 AMP ISOLATED TAB	
NAS0351W	100V .82	NAS0851W	100V .88	NAS1501W	100V 1.05
NAS0351X	100V .82	NAS0851X	100V .88	NAS1501X	100V .98
NAS0352W	200V .56	NAS0852W	200V .78	NAS1502W	200V 1.02
NAS0352X	200V .56	NAS0852X	200V .78	NAS1502X	200V 1.02
NAS0354W	400V .68	NAS0854W	400V .88	NAS1504W	400V 1.51
NAS0354X	400V .67	NAS0854X	400V .85	NAS1504X	400V 1.48
NAS0356W	600V .86	NAS0856W	600V 1.10	NAS1506W	600V 1.89
NAS0356X	600V .84	NAS0856X	600V 1.08	NAS1506X	600V 1.84

Devices with Internal Trigger have 'W' suffix. 'X' denotes Standard Triac.

### THYRISTORS

1.6AMP T05		4AMP ISOLATED TAB		6AMP ISOLATED TAB	
NAS006P	50PIV .25	NAS106P	50PIV .26	NAS206P	50PIV .37
NAS006Q	100PIV .28	NAS106Q	100PIV .30	NAS206Q	100PIV .42
NAS006R	200PIV .31	NAS106R	200PIV .36	NAS206R	200PIV .50
NAS006S	400PIV .40	NAS106S	400PIV .57	NAS206S	400PIV .77
NAS006T	600PIV .52	NAS106T	600PIV .80		

8AMP ISOLATED TAB		16AMP ISOLATED TAB	
NAS306P	50PIV .41	NAS806P	50
NAS306Q	100PIV .47	NAS806Q	58
NAS306R	200PIV .59	NAS306R	73
NAS306S	400PIV .86	NAS806S	1 15

Quantity Prices on Application. SAE

THYRISTORS C106 SERIES 4AMP  
 50V .32; 100V .37; 200V .48; 400V .56; 600V .70

### INTEGRATED CIRCUITS

TAA550	T018	54	●TBA600	78	●709	14 Pin	.27
TAA263	T018	82	●TBA810AS	1 08	●741	8 Pin	.35
555	8 pin	40	●ZN414T018	75	●748	14 Pin	.50
555	8 pin	1 05			723	14 Pin	.67

### CLOCK CHIPS

CT7001	28 Pin Skt	28 Pin	£4.95	AY-5-1224	16 Pin	£3.75
Data			55	16 Pin Skt		16
			15	Data		15

707 LED 3" Common Cathode Display £1 00  
 704 LED 3" Common Anode Display 90  
 747 LED 6" Common Anode Display £185

● Please add 25% VAT, remainder 8%. Postage and Packing 20p per order  
 Phone in your Access and Barclaycard Order Catalogue 20p Callers welcome

PRICES ★ RCA SLASH PRICES ★ RCA SLASH PRICES ★ RCA  
CMOS from the leading manufacturers at the new manufacturers' 1 off prices

## SINTEL for CMOS

CD4000AE 0.17	CD4021AE 0.63	CD4039AD 7.47	CD4057AD 20.35	CD4082BE 0.18
CD4001AE 0.17	CD4022AE 0.79	CD4040AE 0.88	CD4059AD 10.64	CD4083BE 0.57
CD4002AE 0.17	CD4023AE 0.17	CD4041AE 0.69	CD4060AE 0.92	CD4084BE 0.57
CD4003AE 0.97	CD4024AE 0.84	CD4042AE 0.69	CD4061AD 16.43	CD4085BE 0.66
CD4007AE 0.17	CD4025AE 0.17	CD4043AE 0.83	CD4062AT 7.33	CD4086BE 0.86
CD4008AE 0.79	CD4026AE 1.42	CD4044AE 0.77	CD4063BE 0.90	CD4086BE 0.86
CD4009AE 0.46	CD4027AE 0.46	CD4045AE 1.15	CD4066AE 0.58	CD4099BE 1.50
CD4010AE 0.46	CD4028AE 0.74	CD4046AE 1.10	CD4068BE 0.18	CD4501BE 0.32
CD4011AE 0.17	CD4029AE 0.74	CD4047AE 0.74	CD4069BE 0.18	CD4502BE 1.02
CD4012AE 0.17	CD4030AE 0.46	CD4048AE 0.46	CD4070BE 0.18	CD4508BE 4.20
CD4013AE 0.46	CD4031AE 1.81	CD4049AE 0.46	CD4071BE 0.18	CD4510BE 1.26
CD4014AE 0.83	CD4032AE 0.88	CD4050AE 0.46	CD4072BE 0.18	CD4511BE 1.95
CD4015AE 0.83	CD4033AE 1.14	CD4051AE 0.77	CD4073BE 0.18	CD4518BE 1.03
CD4016AE 0.46	CD4034AD 7.83	CD4052AE 0.77	CD4075BE 0.18	CD4520BE 1.03
CD4017AE 0.83	CD4035AE 0.97	CD4053AE 0.77	CD4076BE 1.27	CD4522BE 1.18
CD4018AE 0.83	CD4036AD 7.47	CD4054AE 0.95	CD4077BE 0.18	CD4555BE 0.74
CD4019AE 0.46	CD4037AE 0.78	CD4055AE 1.08	CD4078BE 0.18	CD4585BE 1.45
CD4020AE 0.92	CD4038AE 0.88	CD4056AE 1.08	CD4081BE 0.18	

**RCA 1975 CMOS Databook** 400 pages of data sheets and 200 pages of circuits, applications and other useful information **£2.30** (No VAT) + 37p P&P

**ATTRACTIVE ALARM CLOCK KITS** — all components including attractive slim case, to build a 6-digit alarm clock with snooze, intensity control, 12- or 24-hour format.

Complete kit with DL704E 0.3" LED displays **£22.80**  
Complete kit with FND500 0.5" LED displays **£26.70**

**32.767 kHz Min. Quartz Crystal** for watch or clock **£3.60**  
**Xtal Timebase Kit:** Will provide stable 50cps for clock IC's giving time accurate to a few secs a month; contents: small PCB, 32.768 kHz Xtal, 3 CMOS IC's, trimmer, C's R's, IC shts **£6.40**

### COMMON CATHODE LED DISPLAYS

DL704E 0.3" only	85p
FND500 0.5" only	£1.50
MAN3M 0.13" only	48p
DL33MMB 3 digits in DIL	£2.00

<b>FLIXCO</b> 3½ digit Liquid Crystal 0.5" display, with socket	<b>£9.40</b>
<b>5LT01</b> 0.5" 4 digit clock display with AM/PM; green phosphor diode	<b>£5.80</b>

**IC's**  
MK50253 4 or 6 digit 12 or 24 hr Alarm Clock IC with snooze **£5.60**  
MK50250 Identical to MK50253 except that it is 24 hr only **£5.00**  
MK5030M CMOS watch IC for LED display with date and seconds **£19.50**  
MM5314 4/6 digit 12/24 hr clock **£4.44**. **AY51224** 4 digit clock **£4.25**

**HARDWARE**  
**SOLDERCON PINS** for Lowest Cost IC sockets for TTL, CMOS, IC's, displays. Strip of 100 for **50p**, 400 for **£2**, 1000 for **£4**, 3000 for **10.50**  
**LSI Sockets** (Soldercon Pins with nylon supports) 22, 24, 28 or 40 pin **30p**.  
**20 way Colour-Coded Flexible Flat Cable** £1 per m. **£8.50** for 10m.  
**7-way Boss Switch:** 7 ultra-min toggle sws in 14 pin DIL **£2.60**  
**ADD VAT AT 8%** — new 25% rate does not apply to any of the above goods.  
75p P&P on orders under £3. All orders processed on the day of receipt.  
**Official orders welcomed**, written, phoned or telexed, from Polys., Univs. Schools, Govt. Dept. Nat. Inds., Rated Cos: **Fastest delivery for R & D.**  
Exports: No VAT 35p (Europe), £1 (Overseas) for Air Mail P&P  
Full Price List and Data with any order, or free on request

**SINTEL** 53c Aston Street, Oxford  
Tel: 0865 43203. Tlx: 837650 A/B ELECTRONIC OXFORD

## Servodata Limited

Advanced Technology  
in Servo Control Components



DC Torque Motors and Tachometers

- ★ High performance, brush and brushless versions and complementary tachometers.
- ★ 840 Standard Models ranging from 15 oz-in to 120 lb-ft.
- ★ Military, Industrial or Space Qualified models are already used by most European Nations.

### Servodata

Is able to offer a technical design service utilising these devices in control systems as well as supplying amplifiers, solid state synchro/resolver to digital converters, readouts and other servo control transducers.

## Servodata Limited

Highclere, Newbury  
Berkshire RG15 9PU  
Telephone: Highclere (STD 0635) 253579  
Telex: 847054

WW—029 FOR FURTHER DETAILS

# TRANSFORMERS

ALL EX-STOCK — SAME DAY DESPATCH

### MAINS ISOLATING

PRI 120/240V SEC 120/240V  
CENTRE TAPPED AND SCREENED

Ref. No.	VA (Watts)	£	P&P p
07*	20	4.10	58
149	60	4.69	72
150	100	5.33	85
151	200	8.54	112
152	250	10.32	141
153	350	12.47	141
154	500	14.33	161
155	750	21.94	BRS
156	1000	30.51	BRS
157	1500	34.89	BRS
158	2000	38.92	BRS

### 50 VOLT RANGE

SECONDARY TAPS  
01-19-25-33-40-50V

Ref. No.	Amps.	£	P&P p
102	0.5	2.71	58
103	1.0	3.55	72
104	2.0	4.95	85
105	3.0	6.10	97
106	4.0	7.98	112
107	6.0	12.71	125
118	8.0	13.53	161
119	10.0	17.75	BRS

### 60 VOLT RANGE

SECONDARY TAPS  
0-24-30-40-48-60V

Ref. No.	Amps	£	P&P p
124	0.5	2.48	72
126	1.0	3.68	72
127	2.0	5.33	85
125	3.0	7.90	97
123	4.0	9.19	141
40	5.0	10.25	125
120	6.0	12.07	141
121	8.0	15.75	BRS
122	10.0	19.40	BRS
189	12.0	20.26	BRS

### HIGH VOLTAGE

MAINS ISOLATING  
PRI 200/220 OR 400/440  
SEC 100/120 OR 200/240.

VA	Ref.	£	P&P p
60	243	4.37	97
350	247	10.93	141
1000	250	26.31	BRS
2000	252	44.12	BRS

### SPECIAL OFFER

Cased Isolator & Transformer  
1KVA PRI 240v sec 115V  
Few only £33.50. BRS

## PLUS

### BRIDGE RECTIFIERS

50v 2A	35p
100v 2A	40p
200v 1A	45p
400v 4A	65p
600v 2A	50p
PM7A6 500v 10A	£2.35

### METERS

AV08 Mk 5	£55.88
AV072	£21.72
U4313	£13.85
U4315	£11.80

### MAGNETIC TO CERAMIC CARTRIDGE CONVERTER

Operating Voltage 2D/45v  
ONLY £2.65 p&p 18p

### BSR MINI-DECK

4-speed autochanger **£6.00**.  
P&P 51p

### 12 and/or 24-VOLT

PRIMARY 220-240 VOLTS

Ref. No.	AMPS	£	P&P p
111	0.5 0.25	1.54	28
213	1.0 0.5	1.86	58
71	2 1	2.41	58
18	4 2	2.97	72
70	6 3	4.43	72
108	8 4	5.09	85
72	10 5	5.50	85
116	12 6	5.80	97
17	16 8	7.48	97
115	20 10	10.91	161
187	30 15	14.20	141
226	60 30	17.67	BRS

### 30 VOLT RANGE

SECONDARY TAPS  
0-12-15-20-25-30V

Ref. No.	Amps	£	P&P p
112	0.5	1.90	58
79	1.0	2.52	72
3	2.0	3.77	72
20	3.0	4.70	85
21	4.0	5.56	85
51	5.0	6.73	97
117	6.0	7.52	112
88	8.0	10.20	125
89	10.0	10.36	141

### AUTO TRANSFORMERS

Ref. No.	VA (Watts)	AUTO TAPS	P&P p
113	20	0-115-210-240	1.75 51
64	75	0-115-210-240	3.05 72
4	150	0-115-210-220-240	4.33 72
66	300		6.11 85
67	500		9.36 125
84	1000		14.36 161
93	1500		19.02 BRS
95	2000		25.41 BRS
73	3000		36.84 BRS

### SCREENED MINIATURES

Ref.	mA	Volts	£	P&P p
238	200	3-0-3	1.62	39
212	1A1A	0-6-0-6	1.93	46
13	100	9-0-9	1.56	25
235	330 330	0-9-0-9	1.64	25
207	500 500	0-8-9-0-8-9	2.02	51
208	1A 1A	0-8-9-0-8-9	3.07	58
236	200, 200	0-15-0-15	1.56	25
214	300, 300	0-20-0-20	2.03	58
221	700 (DC)	20-12-0-12-20	2.38	58
206	1A 1A	0-15-20-0-15-20	3.63	72
203	500, 500	0-15-27-0-15-27	3.15	72
204	1A 1A	0-15-27-0-15-27	4.14	72
S112	500	12 15 20 24 30	1.97	58

### CASED AUTO. TRANSFORMERS

240v mains lead input and USA 2-pin outlets  
20VA **£3.29**, P&P 72p Ref. 113V  
150VA **£6.37**, P&P 85p Ref. 4W  
500VA **£10.97**, P&P £1.25p Ref. 67W  
1000VA **£18.39** BRS. Ref. 84W

### HIGH QUALITY MODULES

3 watt RMS Amplifier	£2.30
5 watt RMS Amplifier	£2.65
10 watt RMS Amplifier	£2.95
25 watt RMS Amplifier	£3.95
Pre-Amp for 3-5-10w	£4.08
Pre-Amp for 25w	£13.20
Power Supplies for 3-5-10w	88p
Power Supplies for 25w	£3.00
Transformer for 3w	£1.48
Transformer for 5-10w	£2.13
Transformer for 25w	£2.60
P&P Amps/Pre-Amps/Power Supplies	18p
P&P Transformers	37p

### POWER UNITS

CC12-05. Output switched  
3-4-5-6-7-5-9-12v at 500mA  
£4.08. P&P 40p

### ANTEX SOLDERING IRONS

15W **£2.68**. 18W **£2.45**. 25W **£2.26**.  
Soldering iron kit **£3.61**  
Stand for above **£1.13**. P&P 25p

PLEASE ADD VAT AFTER P&P  
ELECTROSIL AND SEMICONDUCTOR  
STOCKISTS — CALLERS WELCOME (MON.-FRI.)  
OR SEND STAMP FOR LISTS

## Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/8

EAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.

THE NEW SEMICONDUCTOR SOURCE

ALL PRICES ARE VAT EXCLUSIVE. PLEASE ADD THE APPROPRIATE AMOUNT OF VAT TO YOUR ORDER

ALL ITEMS IN THIS SECTION RATED AT 25% VAT

Table listing various semiconductor components such as diodes, transistors, and thyristors with their respective part numbers and prices.

ITEMS IN THIS SECTION RATED AT 8% VAT

Table listing various semiconductor components such as diodes, transistors, and thyristors with their respective part numbers and prices.

DL704 7-segment led (0.3") £1.20
DL707 7-segment led (0.3") £1.20
DL750 7-segment led (0.6") £2.00
Large leds 0.2" dia (clear) £0.07

THYRISTORS (PLASTIC TO-220 PKGE)

Table listing thyristor specifications including current ratings (3 Amp, 6 Amp, 8 Amp, 10 Amp) and prices.

TRIACS (PLASTIC TO-220 PKGE. ISOLATED TAB)

Table listing triac specifications including current ratings (4A, 6.5A, 8.5A, 10A, 15A) and prices.

N B Triacs without internal trigger diac are priced under column (a). Triacs with internal trigger diac are priced under column (b). When ordering please indicate clearly the type required

Matching charge 20p per pair P & P (U.K. only) 20p P & P (Overseas) 80p.

LYNX ELECTRONICS LTD.

92 BROAD STREET, CHESHAM, BUCKS
TEL: 02405-75154

MUIRHEAD PAMETRA WAVE ANALYSER D-489-EM: Primarily used for the analysis of complex vibration waveforms but will measure audio and power frequency waveforms from 19Hz-21KHz. Complete with power supply unit 230V 50Hz. Secondhand, very good condition. £110. Carr. £3.

REDIFON TELEPRINTER RELAY UNIT No. 12: ZA-41196 and power supply 200-250V a.c. Polarised relay type 3SEITR. 80-0V 25mA. Two stabilised valves 'CV 286. Centre Zero Meter 10-0-10. Size 8in. x 8in. x 8in. New condition. £105. Carr. 75p.

SOLARTRON PULSE GENERATOR TYPE G1101-2: £75.00 each. Carr. £2.00. TELEPRINTER TYPE 7B: Pageprinter 24V d.c. power supply, speed 50 bauds per min. second hand cond. (excellent order) no parts broken. £20 each. Carriage £3.

INSULATION TEST SET: 0-10 kV negative, earth with amplifier provision for checking ionisation. 110/230v a.c. input. S/hand, good cond. £35 + £1 carr.

BRIDGE MEGGER: 250V. (Evershed Vignoles) series 2. £30 each. Carr. £1. BRIDGE MEGGER: 2500V., series 1. £30 each. Carr. £1.

CRYSTAL TEST SET TYPE 193: used for checking crystals in freq. range 3000-10,000KHz. Mains 230V 50Hz. Measures crystal current under oscillatory conditions and the equivalent resistance. Crystal freq. can be tested in conjunction with a freq. meter. £25. Carr. £1.50.

SOLARTRON VARIABLE POWER UNIT S.R.S. 1535: 0-500 volts at 100 mA and 6.3 volts C.T. 3 amps d.c. 110/250 volts a.c. input. £18.50. Carr. £1.50.

FURZHILL SENSITIVE VALVE VOLTMETER V.200: Freq. 10Hz-6MHz (can be used beyond 6MHz). Probe in circuit - voltage range 1mV-1kV in 6 decade ranges; full scale deflection 10mV, 100mV-1kV. Without probe 100µV-100V in 6 decade ranges; full scale deflection 1mV, 10mV-100V. Accuracy ±5%. £30 each. Carr. £1.

NOISE FIGURE METER TYPE I13A (Magnetic AB, Sweden): Complete with Noise Source 121 and 122. £125. Carr. £1.

PRECISION PHASE DETECTOR TYPE 205: Freq. 0.1-15MHz in 5 ranges. Variable time delay microseconds 0-0.1c. 115V input. £55 each. Carr. £1.

RHODE & SCHWARZ HF MILLIVOLTMETER: 30Hz-30MHz Type UVH, 1mV-1V in 7 ranges, 220V. £75 each. Carr. £2.

PHILIPS VALVE VOLTMETER TYPE GM6014: 1-300mV in 6 ranges, 70-20dB; probe 1000Hz-30MHz, 300mV maximum. £35 each. Carr. £1.

CT.343 VALVE VOLTMETER: in ruggedised steel case. Range 1.2mV to 400V. 6 ranges indicated on 3" meter. 230v a.c. input. £25. Carr. £2.

UHF MICROWAVE MILLIWATTMETER TYPE 14: Direct reading, can be used to measure power from 100MHz upwards. F.S.D. on 4in. scale meter 2.5mW. £40 each. Carr. £1.

S-BAND RADAR TEST SET MW69S (Decca) Oscilloscope and Spectrum Analyser. Further details on request. £200.

Q METER: 30MHz-200MHz. £55. Carr. £1.

AVO TRANSISTOR ANALYSER CT.446: £35. carr. £1.50.

ALL CARRIAGE QUOTES GIVEN ARE FOR 50-MILE RADIUS OF LONDON ONLY.

CT.420 SIGNAL GENERATOR: 200-8000c/s Variable tuning. Two fixed frequencies 9000 and 10,000. Internal calibrator 100 & 500 c/s. £75 each carr. £2.

NOISE GENERATOR TF-1106: Frequency 1 to 200 Mc/s Direct noise factor calibration. Output impedance 70 ohms £65 each. Carr. £1.50.

COUNTER EXTENSION UNIT TF-1434/2: Complete with plug-in units £75 carr. £1.50.

MW-59 UNIVERSAL KLYSTRON POWER SUPPLY: £85. Carr. £3.

TF-1278/1 TRAVELLING TUBE WAVE AMPLIFIER: £25. Carr. £2.

BPL A.C. MILLIVOLTMETER TYPE VM.348-D Mk. 3: 2 millivolts-2 volts, 6 ranges. £30. Carr. £1.

MARCONI DUAL TRACE UNIT TM-6456: £30. Post 60p.

SIGNAL GENERATOR TS-403B/U (or URM-61A): (Hewlett Packard). A portable, self-contained, general-purpose test equipment designed for use with radio and radar receivers and for other applications requiring small amounts of RF power such as measuring standing-wave ratios, antenna and transmission line characteristics, conversion gain, etc. Both the output freq. and power are indicated on direct-reading dials. 115V, AC, 50 c/s. Freq. - 1800-4000 Mc/s. CW, FM, Modulated Pulse - 40-400 pulses per sec. Pulse Width - 0.5-10 microseconds. Timing - Undelayed or delayed from 3-300 microseconds from external or internal pulse. Output - 1 milliwatt max., 0 to -127 dB variable. Output Impedance - 500. Price: £120 each + £2 carr.

H.V. TRANSFORMER: 8000/8000. Output 300mA. rms. Size: 12in. x 12in. x 36in. 230V input. £40. Carr. £4.

FIREPROOF TELEPHONES: £25.00 each, carr. £1.50.

POWER UNIT: 110/230 volts a.c. input. 28 volts d.c. at 40 amps output. £30.00 each, carr. £3.00.

SMOOTHING UNIT (for the above): £10.00 each, carr. £2.00.

X-BAND MODULATOR CALIBRATOR TYPE MC-4420-X: Mnfr. James Scott. £125 each. Carr. £1.

HP-766D DUAL DIRECTIONAL COUPLER: 940-1975MHz. £35 each, 75 post.

BACKWARD WAVE OSCILLATOR TYPE SE-125: 6.3 heater, 105V Anode, 7.9mA. Mnfr. Watkins & Johnson. £85 each. Carr. £1.

TEKTRONIX TIME MARK GENERATOR TYPE 180-S1: 5, 10, 50 MHz. £65. Carr. £2.

MARCONI SIGNAL GENERATOR TYPE TF-144G: Freq. 85 Kc/s-25 Mc/s in 8 ranges. Incremental: ±1% at 1 Mc/s. Output: continuously variable 1 microvolt to 1 volt. Output Impedance: 1 microvolt to 100 millivolts, 10 ohms 100mV-1 volt - 52.5 ohms. Internal Modulation: 400 c/s sinewave 75% depth. External Modulation: Direct or via internal amplifier. A.C. mains 200/250V, 40-100 c/s. Consumption approx. 40 watts. Measurements 29in. x 12 1/4in. x 10in. Secondhand condition. £32.50 each. Carr. £2.50.

ROTARY INVERTERS: TYPE PE.218E - input 24-28V d.c., 80 Amps. 4,800 rpm. Output 115V a.c. 13 Amp 400 c/s. 1Ph. P.F.9. £20.00 each. Carr. £2.50.

FREQUENCY METER BC-221: 125-20,000 Kc/s complete with original calibration charts. Checked out. working order £20 + £1.50 carr.

ALL U.K. ORDERS SUBJECT TO VALUE ADDED TAX. THIS MUST BE ADDED TO THE TOTAL PRICE (including post or carriage)

If wishing to call at stores, please telephone for appointment

W. MILLS

3 & 3a BALDOCK STREET, WARE, HERTS. SG12 9DT
WARE 66312 (STD 0920)
and at ELSTOW STORAGE DEPOT. Phone: Bedford 740605 (STD 0234)

# BI-PRE-PAK Makers of Stirling Sound audio equipment

The people for component bargains

ORIGINATORS OF PRE-PACKED COMPONENTS IN BRITAIN — AND STILL LEADING!

## YOUR CHANCE TO SAVE £12

ON THIS MODULAR STEREO FM/AMP ASSEMBLY

- \* TOTAL VALUE AT REGULAR ADVERTISED PRICE (INC. VAT) **£30**
- \* ALL 4 UNITS PURCHASED TOGETHER INC. VAT & P&P IN U.K. **£18**
- \* IF YOU BUY UNITS SEPARATELY YOU STILL SAVE **33 1/3%**
- \* ORDER NOW FOR DELIVERY BY RETURN

### 1. THE FRONT END

Ganged tuning: AFC facility. Reduction-gear drive. 88-108 MHz.

Usual price inc. VAT **£8.01** **£5.34**

### 3. STEREO DECODER USING I.C.

Designed for use with the above modules, can also be used with other mono F.M. tuners. Ready aligned. (L.E.D. for stereo beacon available at 18p.)

Usual price inc. VAT **£7.22** **£4.82**

### 2. THE I.F. BOARD

Using I.C. Designed for use with above front end.

Usual price inc. VAT **£6.76** **£4.50**

### 4. 5 + 5 WATT MUSIC POWER I.C. AMPLIFIER

Useful stereo power amplifier with good performance, at economy price

Usual price inc. VAT **£8.01** **£5.34**

### 3 SPECIAL OFFERS

**LM 380 AUDIO IC** (Marked 60745). Brand new and to spec. 3 watts R.M.S. out. With data. **75p**  
**Three SN 7490**. Brand new I.C. to spec. decode counters. **3 for £1.20**  
**Five SN 7400 Quad 2** input Nan gate ICs. **60p**

### SUNDRY

**P.1 PAK** — Approx. 170 short-lead semi-conductors and components. PNP, NPN, diodes, rectifiers, etc. on ex-computer panels. At least 30% factory marked. Some data supplied. **50p**.  
 UHF 625 line tuner, rotary. **£2.50**.  
 Rev Counter (for cars) (8%). **£1.00**.  
 Books by Bernard's Publications. Newnes-Butterworth's, etc.

### THE FREE CATALOGUE

New edition better than ever. It's your's for free and well worth getting — only please send large S.A.E. with 10p stamp if we have to post it to you.

### V.A.T. — IMPORTANT

Rates quoted in good faith in accordance with Customs & Excise rulings. In the event of overpayment by customers the difference will be credited.

### TERMS OF BUSINESS:

VAT at 25% must be added to total value of order, except for items marked \* or (8%). when VAT is to be added at 8%. No VAT on overseas orders. **POST & PACKING** Add 25p for UK orders except where shown otherwise. Minimum mail order acceptable — £1. Overseas orders add £1 for postage. Any difference will be credited or charged. **PRICES** Subject to alteration without notice. **AVAILABILITY** All items available at time of going to press when every effort is made to ensure correctness of information.

## NEW RANGE TRANSISTOR & COMPONENT PACKS

### TP SELECTION

- TP5** 20 Transistors. PNP Germanium, Red Spot A.F.
- TP6** 20 Transistors. PNP Germanium, White spot RF
- TP7** 1 2N174 150w 80Vce Power Transistor, with mounting assembly.
- TP19** 100 diodes, mixed Germanium, Gold-bonded, etc. Marked/Unmarked.
- TP23** Twenty NPN Silicon uncodded T05. Similar to BFY50/2, 2N696, 2N1613, etc. Complementary to TP24.
- TP24** Twenty PNP Silicon, uncodded T05. Similar to BFY64, 2N2904/5.
- TP29** 8 power diodes 400V. 1 25A Silicon FST 3/4.

### UT SELECTION

- UT1** 50 PNP's Germanium, AF & RF.
- UT2** 150 Germanium diodes, min glass.
- UT4** 100 Silicon diodes, min. glass, similar to IN914, IN916.
- UT5** 40 250mW Zener diodes OAZ '240 range; average 50% good.
- UT7** 30 Silicon rectifiers 750mA, mixed voltages. Top Hats, etc.
- UT9** 40 NPN Silicon planers. Similar to 2N3707-11 range. Low noise amps.
- UT12** 25 2N3702/3 Transistors. PNP Silicon. Plastic to 92.

### CP SELECTION

- CP1** Mixed bag of capacitors — Electrolytic, Paper, Silver Mica (Approx. 150 — sold by weight).
- CP2** 200 (approx.) Resistors, various types, values, watts. (Sold by weight.)
- CP3** 40 Wire-wound resistors, mixed.
- CP4** 12 pots — pre-set, w/wound, carbon, dual, with/without switches — all mixed.
- CP7** Heat sinks, assorted. To fit SO-2 (OC72) TO-1 (AC128), etc.

**ALL ABOVE PACKS — 60p EACH** TP Tested & Guaranteed. UT Untested, unmarked. CP Components

### CAPACITOR DISCHARGE IGNITION KIT

Simple to assemble and fit. Improves car performance. **£7.50** \*

### BI-PRE-PAK X-HATCH GENERATOR MK. 2

Four-pattern selector switch 3" x 5 1/4" x 3"  
**Ready-built and tested** **£9.93** \*  
**In kit form** **£7.93** \*



*Please add 50p for postage and packing*  
 Is invaluable to industrial and home user alike. Improved circuitry assures reliability and still better accuracy. Very compact, self-contained. Robustly built. Widely used by TV rental and other engineers. With reinforced fibreglass case, instructions, but less batteries. (Three U2 type required.)

### TV SIGNAL STRENGTH METER \*

Complete kit as described in "Television" £19.50 plus 40p for P&P

### SS300 POWER SUPPLY STABILISER

Add this to your un stabilised supply to obtain a steady working voltage from 12 to 50V for your audio system, workbench, etc. Money saving and very reliable. **£3.25** \*

### PLASTIC POWER TRANSISTORS

40 WATT SILICON *			
Type	Polarity	Gain	VCE
40N1	NPN	15	15
40N2	NPN	40	40
40P1	PNP	15	15
40P2	PNP	40	40

90 WATT SILICON *			
Type	Polarity	Gain	VCE
90N1	NPN	15	15
90N2	NPN	40	40
90P1	PNP	15	15
90P2	PNP	40	40

If you prefer not to cut coupon out, please mention WW12 when writing.

To BI-PRE-PAK, 222-224 WEST ROAD WESTCLIFF-ON-SEA, ESSEX

Please send \_\_\_\_\_ inc. VAT  
 for which I enclose \_\_\_\_\_  
 NAME \_\_\_\_\_  
 ADDRESS \_\_\_\_\_

WW12

## BI-PRE-PAK LTD


Co Reg No B20319

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.  
 TELEPHONE: SOUTHEND (0702) 46344.

FOUNDED IN 1959
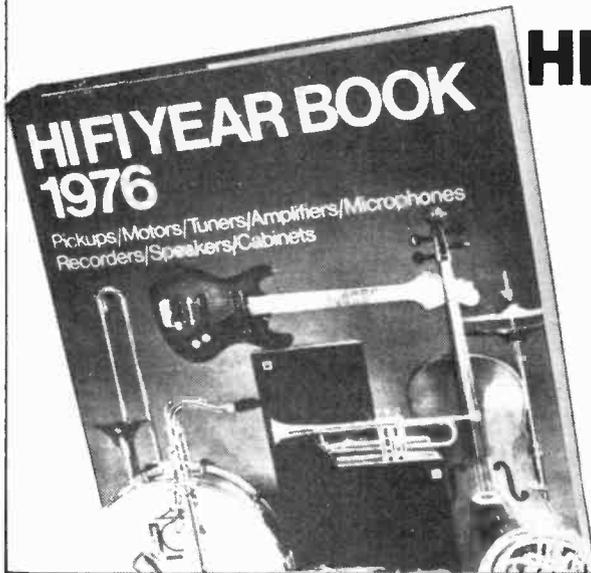
# Where the facts are

Hi-Fi Year Book tells you everything you need to know about Hi-Fi equipment on the market — what it does, who makes it, what it costs and where to buy it. The directory section alone lists prices and specifications of over 2,000 audio products. Included are authoritative articles by leading experts on the latest Hi-Fi developments and their application. So if you want information like you want Hi-Fi, order your copy today — before it sells out!



## HI-FI YEAR BOOK 1976

Available direct from the publishers at £2.35 inclusive  
or from leading booksellers & newsagents price £2.00.

### ORDER FORM

To: Room 11, IPC Electrical-Electronic Press Ltd., Dorset House,  
Stamford Street, London SE1 9LU

Please send me .....copy/copies of Hi-Fi Year Book 1976 at  
£2.35 per copy inclusive. I enclose remittance of £.....  
(cheque/P.O. payable to IPC Business Press Ltd).

Name (please print) .....

Address .....

Registered in England No. 677128 Regd. Office Dorset House, Stamford Street, London SE1 9LU



**TO: AMPLICON ELECTRONICS LIMITED**  
Lion Mews, Hove, BN3 5RA. Tel. Brighton (0273) 723175

Please send .....

for which I enclose £..... inc VAT

Name .....

Address .....

## AMATEUR OR PROFESSIONAL

### WITH THE LM3 DIGITAL MULTIMETER

Now everyone can afford to make highly accurate ( $\pm 0.1\%$ ) and reliable measurements.

The big, bright numerical readout has three full digits, shows the decimal point in the right place and eliminates memorising the confusing full scale range values. You don't even have to operate a switch or reverse leads to get both positive and negative DC voltage readings. Polarity indication is automatic with a big LED + or - sign displaying complete readings.

It has one millivolt sensitivity and resolution for AC and DC with readings from one mv to 500v or one ohm resolution and readings from one ohm to 10 megohms. Automatic zeroing means no drift. It also has built-in protection on all functions.

With four ranges of volts DC and AC and high input impedance the LM3 is powered by 3 internal batteries each set being capable of over 2000 readings. Probably the smallest in the World (1.9"H x 2.7"W x 4.0"D) it is extremely rugged with optional shunts which plug into the input jacks, to provide current measurement from 100 micro-amperes full scale to one ampere.

This MOS/LS1 construction multimeter has a low, low price of £65.50 including batteries + £1.00 postage and packing + 8% VAT.

Tremendous value for money from NLS the originators of the digital voltmeter, you should order now with confidence with a 10-day money back guarantee.

WW—090 FOR FURTHER DETAILS

# Celestion Dittons get the best out of any system

Buy a really good set of speakers and you've got yourself a better hi-fi system... buy a set of Celestion Dittons and you've got one of the best.



Whether you already own or are thinking of buying either a 'package' hi-fi system or are selecting your own individual units, a pair of good speakers will pay dividends in terms of sound quality.

Some people pay least attention to selecting their speakers. Given first priority they will vastly improve the performance of most systems.

Celestion Dittons have a long standing reputation among enthusiasts for their outstanding achievements in high quality sound reproduction.

From left to right, the Ditton 11, 44 and 33.

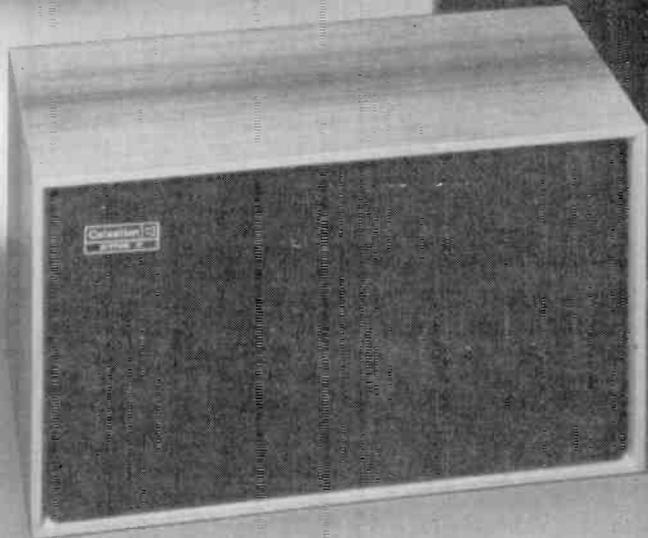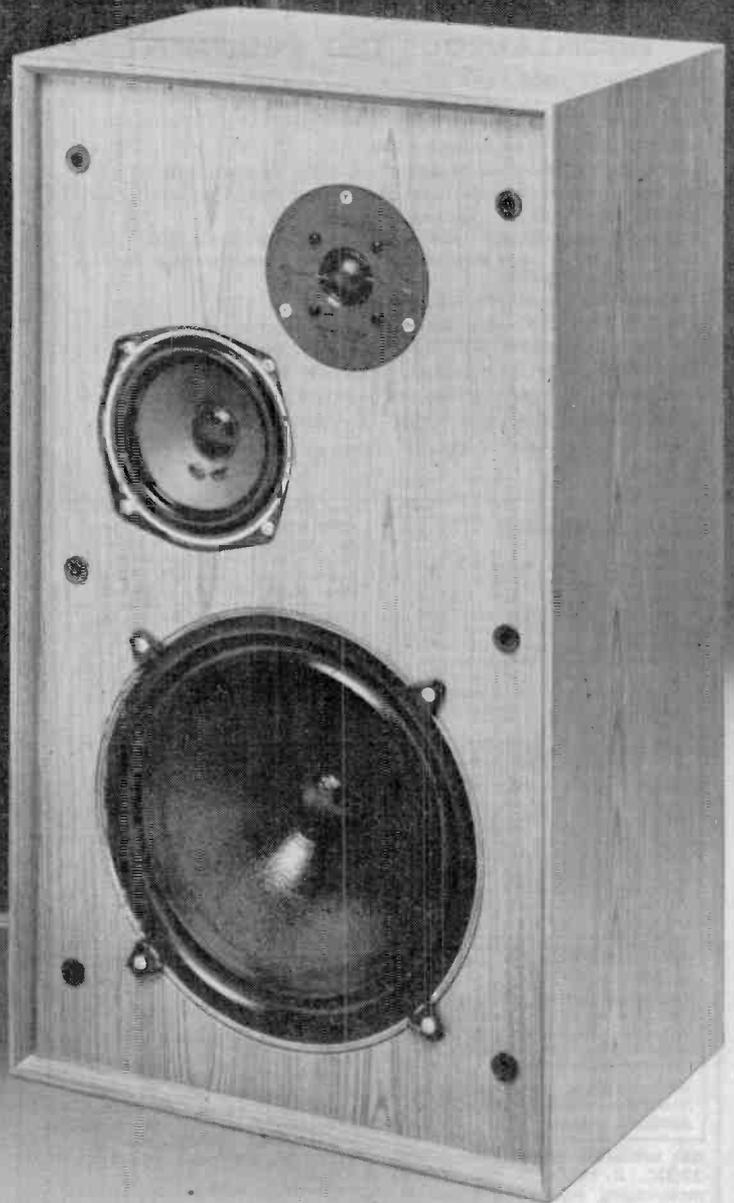Visit your Celestion dealer. See the beautiful appearance and hear the new sounds of the very latest Dittons. Full details on request.



Rola Celestion Limited, Ditten Works,  
Foxhall Road, Ipswich, Suffolk IP3 8JP.  
Telephone: Ipswich (0473) 73131.  
Cables: Voicecoil Ipswich. Telex: 98365.

Please send full details of Ditton 11  Ditton 33  Ditton 44  W6  
(tick appropriate box/boxes)

Name \_\_\_\_\_

Address \_\_\_\_\_

# P. F. RALFE

10 CHAPEL ST. LONDON NW1.  
Phone 01-723 8753

## SIGNAL GENERATORS



**MARCONI TF801D/IS.** 10-480 mHz P.O.A.  
**MARCONI TF801B/2S.** 10-480 mHz £225.  
**HGN MS3/U.** 9.7-11.9 and 77-109 mHz. AM/FM.  
**ADVANCE SG63D.** AM/FM 7.5-230mHz £125.  
**RACAL/AIRMEC 201A.** 30kHz-30mHz. As new. P.O.A.  
**ADVANCE SG21** VHF Square-wave generator 9kHz-100mHz. £25.

## OSCILLOSCOPES



**SOLARTRON CD1400** DC-15mHz.  
**COSSOR CDU110.** DC-80mHz.  
**TEKTRONIX 545A** with CA unit. DC-30mHz. Price only £295.00  
**TEKTRONIX 531** DC-15mHz with L type plug-in  
**TEKTRONIX 535** DC-15mHz with L type plug-in  
**TEKTRONIX 545B** DC-30mHz with 'CA' plug-in.  
**TEKTRONIX 585A.** DC-80mHz with type 82 plug-in.  
**TEKTRONIX 654B.** Storage oscilloscope.  
**TEKTRONIX 502.** 200uV. Sens. X-Y.  
**TEKTRONIX C27** Polaroid Camera. Series 125 with 560 series adapter.

## MISCELLANEOUS TEST EQUIPMENT

**MARCONI TF1400S** double pulse generator with TM6600/S secondary pulse unit. £105.  
**MARCONI TF791D** deviation meter. 4-1024mHz. 0-100kHz deviation.  
**MARCONI 455E** Wave Analyser £120.  
**MARCONI TF2600** Valve Voltmeter 1mV-300V. Excellent. £75.  
**ROHDE & SCHWARZ** USVD calibrated receiver 280-940mHz (4600mHz)  
**LEVELL TG200 DM.** RC Oscillator.../w case. £65.  
**ROHDE & SCHWARZ** URV milli-voltmeter BN10913 (late type) 1mV-10V. With 'T' type insertion unit, free probe and attenuator heads. 1kHz-1.600mHz. £175.  
**COSSOR 1453** True RMS milli-voltmeter. Excellent. £75.  
**AIRMEC TYPE 210** modulation meter. Excellent condition.  
**ROHDE & SCHWARZ** "SCR" V.H.F. Signal Generator 1000-1900 mHz.  
**MARCONI** type TF936 Impedance Bridge. £85.00.  
**GERTCH** Phase Angle V. Meters. Range 1mV-300V, in 12 ranges.  
**SOLARTRON** oscillator type CO 546. 25Hz-500kHz. £30.00.  
**GAMBRELL** Precision 4 Decade Resistance Box. 1-11, 110 ohms. £24.50.

### BOXER INSTRUMENT

**FANS**  
Dimensions 4.5 x 4.5 x 1.5 ins. Very quiet running, precision fan specially designed for cooling electronic equipment, amplifiers etc. For 110V. AC operation—(practise is to run from split primary of mains transformer or use suitable mains dropper). CC only 11 Watts. List price over £10 each. Our price, in brand new condition, is £4.50.

### POWER SUPPLIES

**WEIR** Electronics modular unit. Model OCAR. Regulated & stabilised. 0-7V @ 2A. £9.50.

Centrifugal blowers by **WOODS**. 8 inch snail type. Outlet 2 3/4 x 2in. 24V DC 2.8A. 2400 r.p.m. Grey stove finish. All brand new. Price is £10.50 + carriage.

### MANY TYPES of RF plugs and sockets in stock:—

**BNC** plugs 50Ω. 30p. BNC sockets 50Ω. 25p. N. Type plugs 50Ω. 50p. Burndept plugs. 40p. Burndept sockets. 40p. Miniature PYE. 20p. Miniature sockets. 20p.  
All connectors are brand new. Immediate delivery. Please add appropriate postage.

**AEI** miniature uniselectors. Type 2200C. 3 banks. 1 bridging. 2 non-bridging wipers. 12 positions. Coil resistance 50 ohms. Complete with bases. Brand new. £4.50 each.  
**20-way BPO Jack strips** to accept 316 type Jack plugs. Also quantity of 316 plugs available. All good condition.

**GENTS/FRIEDLAND** fire alarm bells. Operating voltages 12v dc/24v dc. All in as new condition and tested before despatch. Sizes 6/8/12 inch. Prices £4.80, £5.20 and £6.50 resp.

**COMPUTER PERIPHERALS.** Tape punches. 8 hole by Westrex and other well known manufacturers. Tape readers by Elliot. All virtually brand new. Prices are better than one half the maker's. Write or phone for quotation.

An exceptional buy enables us to offer stabilised and regulated power supplies by APT at a very cheap price. 16-24v dc @ 10 Amps, and 8-10v dc @ A. Both supplies are extremely stable with low ripple voltage. Price each £18.50 + carriage.

**MINIATURE DEAC** Ni-Cad. batteries type 700K. 3 cells in package 25x17x15mm. 75p, post paid.

**GEC** Courier Walkie-Talkies. 3 Channel. Re-chargeable batteries. Mid-band. £55 pair.

E.M.I. oscilloscopes model WM16 with type 7/1 W.B.A. plug-in unit. Supplied in perfect condition complete with trolley. £125.00.

**HEWLETT PACKARD/BOONTON TYPE 8900B**  
Peak-power calibrator. Measures true peak power ±.6 db absolute. Frequency range 50-2000Mhz. RF power range 200mW peak, full-scale. RF Impedance 50 ohms. P.O.A.

**MARCONI TF995A2/M AM/FM R.F. SIGNAL GENERATORS.** 1.5-220mHz. 0-100kHz Deviation. 1µV-100mV output. Sold in excellent condition. P.O.A.

**PLEASE ADD 8% V.A.T. TO THE TOTAL AMOUNT WHEN ORDERING. INCORRECT AMOUNTS WILL CAUSE DELAY IN DESPATCH. THANK YOU.**

SQ IS A TRADEMARK OF CBS INC.

## NEW LOW PRICES!

### SQ QUADRAPHONIC DECODERS

SQ the leading quadraphonic system, designed by CBS engineers, offers not only 4 channel ambiphony from the fast expanding range of SQ encoded discs but also immensely increased depth and fullness of sound from standard stereo recordings too.  
Feed 2 channels (200-1000mV as obtainable from most pre-amplifiers) into your choice of any of our 3 decoders and take 4 channels out with no overall signal level reduction. On the logic enhanced decoders Volume, Front-Back, LF-RF, LB-RB and Dimension controls can all be implemented by simple single gang potentiometers—no need for exotic 4-gang units!  
These state-of-the-art circuits, used under licence from CBS are offered in kit form comprising first grade components only—fibre glass circuit boards of professional quality designed for edge connector insertion, all resistors 2% metal oxide all polystyrene and polycarbonate capacitors 5% or better and in decoder L2 ultra low noise (MPS A18-0.5dB typ.) transistors used in each amplifying stage.  
M1 Basic matrix decoder with fixed '10-40' blend. 10 Resistors, 14 Capacitors, 1 Integrated Circuit. Printed Circuit Board £5.90.  
L1 Full logic controlled decoder with 'wave matching' and 'front-back logic' for enhanced channel separation using three specially designed Integrated Circuits. 24 Resistors, 42 Capacitors, 3 Integrated Circuits. Printed Circuit Board £17.20.  
L2 More advanced full logic decoder with 'variable blend', extended frequency response increased front-back separation. 43 Resistors, 44 Capacitors, 3 Integrated Circuits, 9 Transistors, 6 Diodes. Printed Circuit Board. £24.60.  
All kits include IC sockets and construction notes. Prices include CBS licence fee.  
Please write for further details in FREE LIST.  
United Kingdom: Post Free. Please add 25% VAT. Overseas: No VAT. Please add (per kit) £2 00 p & p (AIR MAIL or £1.00 p & p SURFACE MAIL

PO BOX 3000  
ANDOVER, HANTS SP10 3LQ

WW-071 FOR FURTHER DETAILS

## NEW PRACTICAL PAPERBACKS FROM FOULSHAM-TAB

<p><b>ELECTRONIC TEST EQUIPMENT</b> — and how to use it. by <i>Joe Risse</i> £1.85</p> <p><b>COLOUR TV TROUBLES</b> — Problems &amp; Solutions (FactBook) by the Editors of Electronic Technician/Dealer £2.30</p> <p><b>ELECTRONICS UNRAVELLED</b> — A New Commonsense Approach by <i>James Kyle</i> £1.90</p> <p><b>SIMPLIFIED COMPUTER PROGRAMMING</b> — The Easy RPG Way by <i>Keith Carson</i> — £1.95</p> <p><b>INSTALLING TV &amp; FM ANTENNAS</b> by <i>Leo G. Sands</i> £1.75</p> <p><b>JAPANESE CONSUMER ELECTRONICS SCHEMATIC/MANUAL SERVICING</b> by <i>TAB Editorial Staff</i> £2.50</p>	<p><b>MODERN GUIDE TO CAR TUNEUP AND EMISSION CONTROL SERVICING</b> by <i>Paul Dempsey</i> £1.95</p> <p><b>SERVICING TRANSISTOR RADIOS</b> by <i>Leonard D'Airo</i> £1.95</p> <p><b>PRACTICAL TRIAC/SCR PROJECTS FOR THE EXPERIMENTER</b> by <i>R. W. Fox</i> £1.80</p> <p><b>BASIC COLOUR TELEVISION COURSE</b> by <i>Stan Prentiss</i> £2.20</p> <p><b>ELECTRONIC CIRCUIT DESIGN HANDBOOK</b> by <i>Editors of EEE Magazine</i> £4.50</p>
---	---

For free catalogue please write to Dept. WW

## FOULSHAM-TAB LTD.

YEOVIL ROAD, SLOUGH, BERKS.

**NEW PRODUCTS**

**PROTO BOARDS**

Build & test circuits as fast as you think!

PB100	10 IC cap breadboard kit, 4 5 x 6 x 1 3"	£17.55
PB101	10 14-DIP cap, 5-way post, 940 solderless tie points, 5 8 x 4 5"	£26.35
PB102	12 14-DIP cap, like PB101 with 1 240 tie points, 7 0 x 4 5"	£35.15
PB103	24 14-DIP cap, 4 5-way posts, 2 250 tie points, 6 0 x 9 0"	£52.75
PB104	32 14-DIP cap, 3 060 solderless tie points, 8 0 x 9 7 6"	£70.35

**LOGIC MONITOR**

Simultaneously displays static and dynamic logic states of DTL TTL HTL or CMOS DIP ICs. Pocket size. £84.95.

**PROTO-CLIP**

For power on/hands off signal tracing. Bring IC leads up from PC board surface for fast trouble shooting.

PC14	14-pin	£3.25
PC16	16-pin	£3.75

**SOCKETS & BUS STRIPS**

Plug-in wire, test, modify or expand without patch cords or solder. Snap together to form breadboard needed.

PN/Description	Hole-to-Hole	Term's	1+	10+
Q159S	1.3"			
Socket	6.5"	6.2"	118	£10.91
Q159B	6.5"	6.2"	20	£2.20
Q147S				
Socket	5.3"	5.0"	94	£8.73
Q147B	5.3"	5.0"	16	£1.98
Q147S				
Socket	4.1"	3.8"	70	£7.42
Q135B	4.1"	3.8"	12	£1.73
Q11S				
Socket	2.4"	2.1"	36	£4.16
Q112S				
Socket	1.8"	1.5"	24	£3.28
Q18S	1.4"	1.1"	16	£2.83
Q17S	1.3"	1.0"	14	£2.63

**7400 Series TTL**

	1	25	100+		0.48	0.45	0.40
SN7400	0.14	0.13	0.12	SN7494	0.60	0.56	0.50
SN7401	0.14	0.13	0.12	SN7495	0.70	0.67	0.60
SN7402	0.14	0.13	0.12	SN7496	0.70	0.67	0.60
SN7403	0.14	0.13	0.12	SN74100	1.35	1.30	1.25
SN7404	0.15	0.14	0.13	SN74104	0.31	0.29	0.26
SN7405	0.15	0.14	0.13	SN74105	0.31	0.29	0.26
SN7406	0.30	0.29	0.28	SN74107	0.31	0.29	0.26
SN7407	0.30	0.29	0.28	SN74109	0.55	0.50	0.45
SN7408	0.15	0.13	0.12	SN74110	0.44	0.41	0.37
SN7409	0.15	0.13	0.12	SN74111	0.81	0.80	0.76
SN7410	0.14	0.13	0.12	SN74114	1.00	0.97	0.95
SN7411	0.23	0.22	0.21	SN74115	1.00	0.97	0.95
SN7412	0.19	0.18	0.17	SN74118	1.00	0.95	0.90
SN7413	0.30	0.29	0.28	SN74121	0.31	0.29	0.26
SN7414	0.14	0.13	0.12	SN74122	0.44	0.41	0.37
SN7415	0.30	0.29	0.27	SN74123	0.62	0.58	0.50
SN7416	0.28	0.27	0.26	SN74125	0.70	0.65	0.60
SN7417	0.28	0.27	0.26	SN74126	0.75	0.70	0.65
SN7420	0.14	0.13	0.12	SN74128	1.40	1.35	1.30
SN7421	0.95	0.94	0.93	SN74132	2.10	2.05	2.00
SN7422	0.26	0.25	0.23	SN74136	0.95	0.90	0.85
SN7423	0.26	0.25	0.22	SN74140	2.50	2.45	2.40
SN7425	0.26	0.25	0.22	SN74141	0.75	0.70	0.62
SN7426	0.26	0.25	0.22	SN74145	1.15	1.10	1.05
SN7427	0.26	0.25	0.22	SN74147	2.95	2.90	2.85
SN7428	0.39	0.38	0.37	SN74148	2.30	2.25	2.20
SN7429	0.14	0.13	0.12	SN74150	1.35	1.30	1.25
SN7432	0.25	0.24	0.22	SN74151	0.68	0.62	0.55
SN7433	0.36	0.35	0.34	SN74152	1.55	1.50	1.45
SN7437	0.27	0.26	0.22	SN74153	0.68	0.62	0.55
SN7438	0.27	0.26	0.22	SN74154	1.55	1.50	1.45
SN7439	1.10	1.08	1.06	SN74155	0.68	0.62	0.55
SN7440	0.14	0.13	0.12	SN74156	0.68	0.62	0.55
SN7441	0.70	0.69	0.66	SN74157	0.90	0.85	0.80
SN7442	0.63	0.60	0.53	SN74158	1.50	1.45	1.40
SN7443	1.00	0.99	0.90	SN74160	0.95	0.90	0.80
SN7444	1.08	1.07	1.05	SN74161	0.95	0.90	0.80
SN7445	0.85	0.83	0.70	SN74162	0.95	0.90	0.80
SN7446	1.03	1.00	0.85	SN74163	0.95	0.90	0.80
SN7447	1.03	1.00	0.85	SN74164	1.60	1.55	1.50
SN7448	0.85	0.83	0.70	SN74165	1.60	1.55	1.50
SN7450	0.14	0.13	0.12	SN74166	1.40	1.30	1.15
SN7451	0.14	0.13	0.12	SN74170	2.40	2.30	2.20
SN7453	0.14	0.13	0.12	SN74173	1.65	1.60	1.55
SN7454	0.14	0.13	0.12	SN74174	1.15	1.10	1.00
SN7455	0.40	0.39	0.38	SN74175	0.97	0.90	0.80
SN7460	0.14	0.13	0.12	SN74176	1.10	1.05	1.00
SN7462	0.45	0.44	0.42	SN74177	1.10	1.05	1.00
SN7464	0.45	0.44	0.42	SN74180	1.10	1.05	1.00
SN7465	0.45	0.44	0.42	SN74181	3.50	3.45	3.35
SN7470	0.30	0.27	0.25	SN74192	1.10	1.05	1.00
SN7471	0.60	0.59	0.58	SN74184	1.60	1.55	1.50
SN7472	0.25	0.24	0.21	SN74185	2.30	2.25	2.20
SN7473	0.30	0.27	0.26	SN74188	4.90	4.85	4.80
SN7474	0.31	0.29	0.26	SN74190	1.75	1.70	1.65
SN7475	0.40	0.39	0.38	SN74191	1.70	1.65	1.60
SN7476	0.31	0.29	0.26	SN74192	1.25	1.05	1.00
SN7478	0.65	0.63	0.61	SN74193	1.25	1.05	1.00
SN7480	0.43	0.41	0.36	SN74194	1.10	1.05	1.00
SN7481	1.00	0.95	0.90	SN74195	0.90	0.85	0.80
SN7482	0.75	0.70	0.62	SN74196	1.05	1.00	0.95
SN7483	0.81	0.80	0.85	SN74197	1.05	1.00	0.95
SN7484	0.90	0.86	0.85	SN74198	2.05	2.00	1.70
SN7485	1.25	1.15	1.00	SN74199	2.05	2.00	1.70
SN7486	3.01	3.28	3.00	SN74200	6.00	5.95	5.80
SN7489	3.50	3.20	3.00	SN74221	1.80	1.75	1.70
SN7490	0.45	0.42	0.35	SN74251	1.80	1.75	1.70
SN7491	1.00	0.95	0.90	SN74278	3.00	2.90	2.80
SN7492	0.45	0.42	0.35	SN74279	1.20	1.15	1.10
SN7493	0.45	0.42	0.35	SN74293	1.00	0.95	0.90
				SN74298	2.60	2.55	2.50

'H', 'L', 'S', and 'LS' TTL also available

**HIGH-SPEED TTL**

	1	25	100+		0.36	0.35	0.33
SN74H00	0.34	0.33	0.30	SN74H51	0.36	0.35	0.33
SN74H01	0.34	0.33	0.30	SN74H52	0.36	0.35	0.33
SN74H04	0.38	0.37	0.34	SN74H53	0.36	0.35	0.33
SN74H05	0.37	0.36	0.33	SN74H54	0.36	0.35	0.33
SN74H08	0.40	0.39	0.37	SN74H55	0.36	0.35	0.33
SN74H10	0.36	0.35	0.33	SN74H60	0.36	0.35	0.33
SN74H11	0.36	0.35	0.33	SN74H61	0.36	0.35	0.33
SN74H20	0.36	0.35	0.33	SN74H62	0.36	0.35	0.33
SN74H21	0.36	0.35	0.33	SN74H71	0.80	0.78	0.75
SN74H22	0.36	0.35	0.33	SN74H72	0.74	0.73	0.70
SN74H30	0.36	0.35	0.33	SN74H73	0.90	0.88	0.85
SN74H40	0.36	0.35	0.33	SN74H74	0.87	0.85	0.81
SN74H50	0.36	0.35	0.33	SN74H76	0.90	0.88	0.85
				SN74H101	0.80	0.78	0.75
				SN74H102	0.80	0.78	0.75
				SN74H103	1.10	1.09	1.05
				SN74H106	0.95	0.93	0.90

**LOW-POWER TTL**

	1	25	100+		0.34	0.33	0.30
SN74L00	0.34	0.33	0.30	SN74L10	0.34	0.33	0.30
SN74L02	0.34	0.33	0.30	SN74L20	0.39	0.37	0.34
SN74L03	0.39	0.37	0.34	SN74L42	1.62	1.58	1.50
SN74L04	0.39	0.37	0.34	SN74L51	0.34	0.33	0.30
				SN74L73	0.74	0.71	0.68
				SN74L74	0.89	0.87	0.80
				SN74L90	1.62	1.58	1.50
				SN74L93	1.74	1.71	1.65

**WAVEFORM GENERATOR KITS**



Here's a highly versatile instrument at a fraction of the cost of conventional units. Kit includes two XR205 IC's, data & applications, PC board (etched & drilled ready for assembly) and detailed instructions.

The Function Generator Kit features sine, triangle and square wave, 1HD 0.5% typ. AM/FM capability.

**XR-2206KA FUNCTION GENERATOR KIT** £11.50

Includes monolithic function generator IC, PC board, and assembly instruction manual.

**XR-2206KB FUNCTION GENERATOR KIT** £16.00

Same as XR-2206KA above and includes components for PC board.

**PICO-PALLET**

THE SMALLEST AC/DC POWER SUPPLY EVER!  
Only 1 70" x 1 00" x 0 85" output pre-set - 5% 9 models.  
£14.50 each

**PREMIUM QUALITY COMPONENTS**

We've been buying and selling top quality components for nearly ten years. We handle only original parts, from the world's leading manufacturers and our customers include some of the largest and most quality-conscious companies. Now you can take advantage of our component buying skills and power and select from a broad range of advanced circuits.

**FIRST QUALITY ONLY**

**HIGH-BRIGHTNESS L.E.D.s**

	.200" dia.	.125" dia.
ED 5053 RED	0.24	ED 209 RED 0.18
ED 5053 YELLOW	0.24	ED 209 YELLOW 0.27
ED 5053 GREEN	0.24	ED 209 GREEN 0.27
ED 5053 ORANGE	0.24	

**NEW Solar Powered Watch**

with 100-YEAR CALENDAR



Solar cells draw power from the sun (10 to 15 minutes per day) or from ambient light (slightly longer) to keep batteries fully charged. Batteries operate up to 10 years. LSI circuitry is programmed to provide a calendar to the year 2100, automatically adjusting for 30 and 31 day months, even leap years. Automatic brightness control adjusts LED for perfect viewing even in outdoors. Shows minutes and hours, counts out seconds or shows the date. Easily adjusts to reset hour or date without affecting calendar. Shock and water resistant. Accurate to 5 seconds per month. Price: £298.50 each.

**STANDARD MICROSYSTEMS**

	1-up	25-up	10
--	------	-------	----



**ALL MAIL ORDER BY RETURN. C.O.D. SERVICE WELCOME**

# C. T. ELECTRONICS

**Tel: 01-994 6275**

**All mail order and enquiries to 270 Acton Lane, Chiswick, London W4 5DG.**

**VAT**  
Unless otherwise stated all prices are exclusive of VAT. Please check whether the goods you are ordering are 25% or 8% Carriage orders under £5 please add 33p. Order over £10 post free in U.K. only. This is to be at our discretion.

## SEMICONDUCTORS

AAZ12 25p	BC214 14p	IS100 15p	TIP42A 85p
AC107 35p	BC214L 15p	IS103 15p	TIP298 54p
AC125 25p	BC238 15p	MJ340 50p	TIP308 60p
AC126 25p	BC239 15p	MJ481 95p	TIP318 65p
AC127 25p	BC300 30p	MJ481 95p	TIP388 £1.06
AC128 25p	BC301 30p	MJ2801 £1.25	TIP348 £1.62
AC176 25p	BC302 30p	MJ2901 £1.95	TIP358 £2.71
AC187 27p	BC303 35p	MJE340 50p	TIP368 £3.50
AC188 27p	BCY31 35p	MJE370 75p	TIP428 95p
ACV17 25p	BCY32 95p	MJE371 90p	TIP29C 68p
ACV18 25p	BCY33 60p	MJE520 65p	TIP30C 72p
ACV19 25p	BCY34 65p	MJ2955 £1.20	TIP31C 80p
ACV20 25p	BCY38 65p	MJE3055 75p	TIP32C £1.00
AD140 60p	BCY39 95p	MM1513 85p	TIP33C £1.20
AD142 60p	BCY55 £1.50	MM1712 60p	TIP340C £1.80
AD161 45p	BCY70 20p	MPF102 45p	TIP35C £3.00
AD162 45p	BCY72 20p	MPF103 45p	TIP38C £3.74
AF114 25p	BD121 75p	MPF104 35p	TIP41C 90p
AF115 25p	BD123 85p	(ZNS457) 35p	TIP42C £1.00
AF116 25p	BD124 70p	(ZNS458) 35p	TIP50 40p
AF117 25p	BD131 40p	(ZNS459) 40p	ZTX107 15p
AF118 50p	BD132 50p	OA47 10p	ZTX300 15p
AF124 30p	BD135 50p	OA70 10p	ZTX500 16p
AGP39 60p	BD136 50p	OA79 10p	ZTX501 20p
BA102 30p	BD139 75p	OA81 10p	ZTX504 50p
BA112 25p	BD140 87p	OA90 10p	ZTX531 30p
BA114 16p	BD153 80p	OA91 10p	ZTX580 25p
BA155 16p	BD156 80p	OA200 10p	IN659 8p
BA156 15p	BDY17 £1.50	OA202 10p	IN914 8p
BC107 13p	BDY18 £1.75	OA210 35p	IN916 8p
BC108 12p	BDY19 £1.90	OA211 35p	IN4001 8p
BC109 14p	BDY20 £1.20	OC16 90p	IN4002 9p
BC109c 16p	BF152 20p	OC19 85p	IN4003 9p
BC113 13p	BF166 30p	OC22 55p	IN4005 12p
BC114 13p	BF178 35p	OC26 65p	IN4008 14p
BC115 15p	BF180 35p	OC28 60p	IN4007 16p
BC116 15p	BF194 16p	OC35 80p	IN4148 7p
BC117 16p	BF195 16p	OC38 65p	2N696 25p
BC118 15p	BF196 16p	OC42 40p	2N697 25p
BC119 30p	BF197 16p	OC44 20p	2N698 25p
BC143 25p	BF200 35p	OC45 25p	2N706 12p
BC147 12p	BF224 18p	OC70 15p	2N706A 14p
BC148 12p	BF244J 18p	OC71 12p	2N708 15p
BC149 12p	BF245 45p	OC72 20p	2N829 20p
BC149c 14p	BF251 55p	OC75 25p	2N930 20p
BC157 14p	BFX29 30p	OC76 25p	2N1132 25p
BC158 14p	BFX34 30p	OC77 40p	2N1302 30p
BC159 15p	BFX85 30p	OC81 25p	2N1303 30p
BC167 14p	BFX86 30p	OC83 25p	2N1304 30p
BC168 14p	BFX88 30p	OC84 25p	2N1305 30p
BC169 14p	BFY10 35p	OC139 30p	2N1306 30p
BC169c 15p	BFY44 50p	OC170 25p	2N1307 30p
BC172 13p	BFY50 25p	OC171 30p	2N1308 30p
BC182 12p	BFY51 25p	OC200 60p	2N1309 30p
BC182L 12p	BFY52 25p	OC201 60p	2N1613 30p
BC183 12p	BFY53 25p	OC202 75p	2N1711 30p
BC183L 12p	BSW21 65p	TIP29A 45p	2N1890 60p
BC184 12p	BSW68 70p	TIP30 55p	2N2146 15p
BC184L 12p	BSW63 65p	TIP31A 57p	2N2147 90p
BC185 35p	BSW68 80p	TIP32A 69p	2N2160 80p
BC186 27p	BSX19 15p	TIP33A £1.00	2N2217 25p
BC212 12p	BSX20 15p	TIP34A £1.40	2N2218 25p
BC212L 12p	BSY10 35p	TIP35A £3.20	2N2219 25p
BC213 12p	BY127 20p	TIP36A £3.50	2N2222 20p
BC213L 12p	BY164 65p	TIP41A 70p	2N2222A 25p

QTY. DISCOUNTS 12+10% 25+15% 100+20%

## TTL (full stocks available)

SN7400 18p	SN7411 23p	SN7430 20p	SN7447 £1.50
SN7401 18p	SN7412 22p	SN7437 50p	SN7448 £1.75
SN7402 20p	SN7413 40p	SN7438 50p	SN7449 20p
SN7403 20p	SN7414 30p	SN7439 50p	SN7450 20p
SN7404 20p	SN7415 30p	SN7440 20p	SN7451 20p
SN7405 20p	SN7420 20p	SN7441 20p	SN7452 20p
SN7406 30p	SN7422 38p	SN7442 75p	SN7453 20p
SN7407 30p	SN7423 38p	SN7443 £1.00	SN7454 20p
SN7408 20p	SN7425 38p	SN7444 £1.70	SN7455 20p
SN7409 40p	SN7427 42p	SN7445 £1.70	SN7456 20p
SN7410 18p	SN7428 50p	SN7446 £2.00	SN7457 20p

## METAL BOXES

**ALUMINIUM BOXES IDEAL FOR VEROBOARD WITH BASE & P.K. SCREWS**

AB7 2 3/8" Long	5 1/4" Wide	1 1/2" High	55p
AB8 4" "	4" "	1 1/2" "	55p
AB9 4" "	2 3/4" "	1 1/2" "	55p
AB10 4" "	5 1/4" "	1 1/2" "	55p
AB11 4" "	2 1/2" "	2" "	65p
AB12 3" "	2" "	1 1/2" "	50p
AB13 6" "	4" "	2" "	70p
AB14 7" "	5" "	2 1/2" "	90p
AB15 8" "	6" "	3" "	£1.16
AB16 10" "	7" "	3" "	£1.32
AB17 10" "	4 1/2" "	3" "	£1.10
AB18 12" "	5" "	3" "	£1.32
AB19 12" "	8" "	3" "	£1.80

**ALUMINIUM BOXES WITH SLOPING TOP PANEL - IDEAL FOR PRE-AMPS, ETC., USING SLIDER CONTROLS**

AB20 8" Long 9" Wide 3 1/2" High at back	£2.20
2" High at front 6" Slope to front	
With P.K. Screws	
AB21 As above but 10" long	£2.20
AB22 As above but 12" long	£2.60

## HIGH PERFORMANCE MODERN SCOPE TUBES

By Telefunken Limited, qty. only 5" rectangular display Type No. D14/131. Price £25,000 each + VAT 8%. All extras provided free whilst remaining in stock. Postage £1.00. All brand new.

## REXINE COVERED ALUMINIUM CASES WITH SCREWS & FEET

RB1 6" x 4" x 1 1/2"	£1.05	RB4 11" x 6" x 1 1/2"	£1.85
RB2 8" x 5" x 2"	£1.20	RB5 11" x 7 1/2" x 1 1/2"	£2.35
RB3 9" x 5" x 3 1/2"	£1.35		

+ 8% Postage 35p

## S.C.R.s

CRS1/05 40p	2N2306 70p
CRS1/10 56p	2N2369A 50p
CRS1/20 60p	2N2477 30p
CRS1/40 65p	2N2661 50p
CRS1/60 90p	2N2846 £1.50
CRS3/10 62p	2N4904 25p
CRS3/20 62p	2N2905 30p
CRS3/40 90p	2N2906 25p
CRS7/400 £1.00	2N2907 25p
CRS16/100 85p	2N2926 13p
CRS16/200 90p	2N3053 25p
CRS16/600 £1.60	2N3055 50p
C106B 45p	2N3232 £1.35
C106D 70p	2N3553 £1.40
40669 90p	2N3643 30p
TIC44 35p	2N3702 12p
2N4444 £1.90	2N3703 12p
BT10/500A 90p	2N3704 12p
	2N3705 12p
	2N3706 12p
	2N3707 12p
	2N3708 14p
	2N3709 14p

## BRIDGE RECTIFIERS

W02 1A 200V 38p	2N3711 £1.50
BY164 1.4A 200V 57p	2N3772 £1.80
MDA952/2 6A 100V 80p	2N3792 £1.80
	2N3794 30p
	2N3819 35p
	2N3820 55p
	2N3823 70p
	2N3866 85p
	2N3904 22p
	2N3905 25p
	2N3906 25p
	2N4014 80p
	2N4035 62p
	2N4037 44p
	2N4058 14p
	2N4059 14p
	2N4080 12p
	2N4288 30p
	2N4289 30p
	2N4290 25p
	2N4126 18p
	2N4286 25p
	2N4287 25p
	2N4288 27p
	2N4289 30p
	2N4290 25p
	2N4291 32p
	2N4302 35p
	2N4444 £1.90
	2N4871 35p
	2N4903 £1.30
	2N4919 90p
	2N5069 £1.30
	2N5191 96p
	2N5192 £1.20
	2N5194 £1.10
	2N5195 £1.40
	2N5245 45p
	2N5296 55p
	2N5298 50p
	2N5457 35p
	2N5458 35p
	2N5459 40p
	2N5485 55p
	2N5490 55p
	2N5555 65p
	2N5777 40p

## ZENER DIODES

BZY88 Series 400mW	11p
3.3V-33V, 5%	25p
15W range	25p
10W range	45p

## L.E.D.

TIL 209 38p
HFS082 28p
MA2082R 20p

## L.D.R.

ORP12 60p
NE555 Timer 80p

## TO3 VOLTAGE REGULATORS

L005 5V 650mA	£1.60 ea.
L036 12V 600mA	
L037 15V 450mA	

## VEROBOARD

17 x 2 1/2"	0.15
17 x 3 1/4"	£1.18
17 x 5"	£1.66
	£1.30

PIN INS TOOL	72p
SP F CUTTER	65p
100 PINS SS	40p
100 PINS DS	40p
2 1/2 x 3 1/4"	30p
2 1/2 x 5"	35p
3 1/4 x 5"	40p
PIN INS TOOL	72p
500 PINS SS	£1.55
500 PINS DS	£1.55

## POTENTIOMETERS

Linear or Log Rotary Pots	Single 17p	Double 45p
Rotary Switched	25p	-

## TRIACS

TXL228B 400V 85p
SC400 £1.40
SC405 £1.65
SC45D £1.70
SC45E £2.10
SC50D £2.42
SC50E £2.70
DIAC 25p

## LINEAR I.C.s

LM304 Neg Voltage Reg	£2.10
LM309K 5V 1A Voltage Reg.	£2.10
LM723C 2.37V 150mA Voltage Reg	75p

## MFC4000 250mW

Audio	75p
TB800K 5 Watt Audio	99p
709C Op Amp	15p
D I L / T099	8/14
741C Op Amp	35p
D I L / T099	Op.
747C Dual Op Amp	£1.20
748C Op Amp	75p
D I L	£1.25
ZN414 Radio I.C.	£1.90

## TAD100 Radio I.C. inc. Filter

CA3014	£1.55
CA3018	£1.00
CA3029	£1.20
CA3036	£1.00
CA3046	95p
CA3048	95p
CA3075	£1.60
CA3098E	£1.90
CA3090Q	£4.85
MC1303L	£2.20
MC1310P	£2.80
SN76660EQ	65p
TBA120	65p

## ★★ SPECIAL OFFERS ★★

**MINIATURE MAINS TRANSFORMER. PRI240V**  
SEC. 12V. 100Ma Manuf. Hinchley Size. 36 x 45 x 40mm. F.C. 53mm.

Price 1.65p. 100 60p ea. 10,000 40p ea. 8% VAT.

**MINIATURE MAINS TRANSFORMER.**

**EMI**  
FUJI  
MAXELL

**BASF**  
TDK  
UP TO **50%** OFF  
MEMOREX  
SCOTCH  
★★★ LEADING BRANDS OF CASSETTES - REPLACEMENT GUARANTEE ★★★

**PHILIPS**  
pyral

## Stereo Tape Recorders

### Stereo Cassette Recorders      Stereo Car Cassette Players

**SPECIAL AUDIO & VIDEO TAPES SUPPLIED. PRICES ON REQUEST**

PLASTIC SNAP PACK	BASF LH		BASF Super S/M		BASF CR02		Memorex MRX		Memorex CR02		REEL TO REEL	BASF Low Noise in Plastic Box		BASF LH Super in Plastic Box		Scotch Hi-Fi Boxed		Agfa Low Noise in Plastic Box		Agfa PFM in Plastic Box		
	One	10	One	10	One	10	One	10	One	10		One	10	One	10	One	10	One	10	One	10	One
C60	42p	£4.15	60p	£5.90	90p	£8.89	57p	£5.63	77p	£7.68	LONG PLAY	5" x 900'	£1.75	£17.00	£1.97	£19.00	—	—	£1.27	£12.65	£1.95	£19.10
C90	62p	£6.07	76p	£7.20	£1.12	£10.50	76p	£7.53	96p	£9.75		5 1/2" x 1200'	£2.20	£20.00	£2.25	£20.50	—	—	£1.60	£15.90	—	—
C120	82p	£8.14	£1.09	£10.80	£1.54	£15.40	£1.08	£10.70	—	—		7" x 1800'	£2.75	£26.50	£3.10	£29.00	£3.20	£31.10	£1.19	£11.85	£2.90	£28.60
PLASTIC SNAP PACK	TDK DYNAMIC		TDK Super Dynamic		TDK Extra Dynamic		TDK CR02		Agfa LH		DOUBLE PLAY	10 1/2" x 3600' NAB	—	—	—	—	—	—	—	—	—	—
	One	10	One	10	One	10	One	10	One	10		10 1/2" x 4200' NAB	—	—	—	—	—	—	—	—	—	—
	One	10	One	10	One	10	One	10	One	10		10 1/2" x 4200' 9NE	—	—	—	—	—	—	—	—	—	—
C60	54p	£5.30	75p	£7.35	95p	£9.30	£1.20	£11.80	33p	£3.25	TRIPLE PLAY	5" x 1200'	£2.20	£20.00	£2.35	£22.50	£1.95	£18.50	£1.49	£14.50	—	—
C90	75p	£7.35	95p	£9.20	£1.60	£15.70	£1.60	£15.70	53p	£5.14		5 1/2" x 1800'	£2.85	£28.00	£3.50	£33.00	£2.50	£23.50	£2.19	£21.10	—	—
C120	99p	£9.70	£1.38	£13.50	—	—	—	—	73p	£7.20		7" x 2400'	£3.50	£34.00	£4.35	£41.00	£2.75	£26.50	£2.89	£28.85	£3.95	£35.50
PLASTIC SNAP PACK	Agfa Super		Agfa CR02		EMI HMV Soundbag		EMI High Dynamic		EMI X1000 UD		REEL TO REEL	5" x 1800'	£2.95	£28.00	—	—	£2.50	£24.50	£2.46	£23.80	—	—
	One	10	One	10	One	10	One	10	One	10		5 1/2" x 2400'	£3.50	£34.00	—	—	£3.10	£29.50	£2.96	£28.80	—	—
	One	10	One	10	One	10	One	10	One	10		7" x 3610'	£4.30	£42.00	—	—	£3.50	£32.50	£3.76	£35.50	—	—
PLASTIC SNAP PACK	Philips LN		Scotch High Energy		Scotch CR02		Scotch Classic		Maxell Super		LONG PLAY	5" x 900'	£1.30	£12.90	£1.40	£13.50	—	—	—	—	—	—
	One	10	One	10	One	10	One	10	One	10		5 1/2" x 1200'	£2.85	£28.00	£2.75	£27.00	£3.20	£30.50	£3.20	£30.50	—	—
	One	10	One	10	One	10	One	10	One	10		7" x 1800'	£2.10	£20.95	£2.25	£22.00	£3.20	£30.50	£3.20	£30.50	—	—
C60	41p	£4.05	—	—	—	—	£1.24	£12.00	55p	£5.45	DOUBLE PLAY	5" x 1200'	£1.55	£14.90	£1.50	£14.95	—	—	—	—	—	—
C90	57p	£5.65	85p	£8.45	96p	£9.75	£1.68	£16.75	69p	£6.30		5 1/2" x 1800'	£2.59	£25.00	£2.50	£24.95	—	—	—	—	—	—
C120	78p	£7.75	—	—	—	—	—	—	94p	£8.50		7" x 2400'	—	—	—	—	—	—	—	—	—	—
PLASTIC SNAP PACK	Maxell Ultra Dynamic		Fuji Super LN		Fuji Extra Dynamic		Pyral Hi-Fi LN		C-A De Luxe		SPECIAL OFFER	<b>FREE</b> Cassette Head Cleaner with every C.A. cassette order over £15.										
	One	10	One	10	One	10	One	10	One	10		<b>MUSIC</b> Cassettes and Cartridges										
	One	10	One	10	One	10	One	10	One	10		Send large (9" x 4") S.A.E. to R/C Dept. for catalogue.										
B-TRACK CARTRIDGES	BASF		Memorex		TDK		EMI		Scotch		Prices shown include VAT at 8%, but are subject to change without notice. Mail Order Only - Cash with orders. For postage and packing, add 10p every 10 cassettes, 10p every reel-to-reel tape. Minimum 20p. Maximum 70p. Offers apply to U.K. Mainland only. <b>CITY AUDIO. STRAND HOUSE</b> <b>GREAT WEST ROAD, BRENTFORD</b> <b>MIDDLESEX (Tel. 01-560 4191)</b>	One		One		One		One		One		If you wish to use Barclaycard or Access, simply quote name, address and card number when ordering. <div style="text-align: right;"> </div>
	40/45 mins.	£1.12	£10.70	£1.10	£10.70	40/£1.25	£11.60	89p	£8.60	£1.12		£10.60	One		One		One		One			
	80/84 mins.	£1.25	£11.60	£1.25	£11.60	—	—	93p	£9.20	—		—	One		One		One		One			
90/100 mins.	£1.42	£13.50	£1.42	£13.50	50/£1.65	£15.10	£1.95	£10.80	£1.35	£12.70	One		One		One		One					

## KINNIE COMPONENTS

10 NELMES WAY,  
HORNCHURCH, ESSEX RM11 2QZ  
HORNCHURCH 45167

ALL PRICES INCLUDE V.A.T. EXCEPT WHERE SURCHARGE IS INDICATED

QUADROPHONIC DECODER MODULE. C.B.S./S.Q. Type, using I.C. MC 1312P. With slight modification direct substitute for P.E. "RONDO" Board. Complete with Data. £4 each.

15% V.A.T. Surcharge

S.T.C. CRYSTAL FILTERS (10.7 Mhz). 445-LQU-901A (50 Khz spacing). £3. P.P. 20p. 445-LQU-901B (25 Khz spacing). £4. P.P. 20p.

V.H.F./U.H.F. POWER TRANSISTORS (type BLY38). 3 watt output at 100-500 Mhz. £2.25. P.P. 10p.

HIGH CAPACITY ELECTROLYTICS  
 1,000µf/100v (4 x 1 1/2in.) 80p. P.P. 20p. 2,200µf/100v (4 x 1 1/2in.) 90p. P.P. 20p. 2,200µf/100v (4 x 1 1/2in.) 90p. P.P. 20p.  
 2,500µf/100v (4 x 2in.) 90p. P.P. 20p. 10,000µf/25v (4 1/2 x 1 1/2in.) 75p. P.P. 20p. 25,000µf/40v (4 1/2 x 2 1/2in.) £1. P.P. 20p.  
 47,000µf/40v Powerlytic (5 1/2 x 3in.) £2. P.P. 50p. 100,000µf/10v Powerlytic (4 1/2 x 3in.) £1.50. P.P. 30p. 160,000µf/10v Powerlytic (6 x 3in.) £2. P.P. 50p.

MULTICORE CABLE. 6-core (6 colours) 14/0076 Screened P.V.C £22p per yard. 100 yards at £16.50. P.P. 2p a yard. 7-core (7 colours) 7/22mm. Screened P.V.C £22p per yard; 100 yards £16.50. P.P. 2p per yard. 30-core (15 colours) 25p per yard; 100 yards £20. P.P. 2p per yard

RIBBON CABLE (8 colours) 10m £1.65. P.P. 20p 100m 8-core 7/ mm Bonded side by side £11.50. P.P. £1

COPPER LAMINATE P.C. BOARD  
 8 1/2 x 6 3/16 inch, 3 for 75p. P.P. 25p  
 10 x 4 x 1/16 inch, 5 for 75p. P.P. 25p  
 10 1/2 x 5 1/2 x 1/16 inch, 3 for 75p. P.P. 25p  
 10 x 8 1/2 x 1/16 inch, 3 for £1. P.P. 25p  
 17 x 9 1/2 x 1/16 inch, 2 for £1.20. P.P. 25p

PRECISION A.C. MILLIVOLTMETER (SOLARTRON). 1.5mv. to 15v. 60dB to 20dB. 9 ranges. Excellent condition. £24. P.P. £2.

TELEPHONE DIALS (new) £1. P.P. £15p.  
 EXTENSION TELEPHONES (Type 706). Various colours. £3.95. P.P. 75p  
 RATCHET RELAYS (310 ohm). Various types £1.20. P.P. 20p  
 UNISELECTORS (New) 25 way, 12 Bank (Non bridging). 68 ohms £6.50. P.P. 50p  
 1,000 TYPE KEY SWITCHES.  
 Single 2 x 4 c/o Locking. 50p. P.P. 10p Bank of 4—2 x 4 c/o each switch (one biased). £1.20. P.P. 15p

OVERLOAD CUT-OUTS. Panel mounting (1 1/4 x 1 1/4 x 1/2in.). 800 M/A/1.8 amp. 10 amp. 45p. P.P. 5p.

ADVANCE TRANSFORMERS "VOLSTAT". Input 242v. A.C.  
 C.V.50. 38v. at 1 amp; 25v at 100 m/a; 75v. at 200 m/a. £2.50. P.P. 65p.  
 C.V.75. 25v. at 2 1/2 amp. £3. P.P. 75p.  
 C.V.100. 50v. at 2 amp.; 50v. at 100 m/a. £3.75. P.P. 75p.  
 C.V.250. 25v. at 8 amp; 75v. at 1/2 amp. £6.50. P.P. £1.50.  
 C.V.500. 45v. at 3 amp; 35v. at 2 amp. £10. P.P. £1.75.  
 H.T. TRANSFORMER. Prim. 110/240v. Sec. 400v. 100 m/a. £2.50. P.P. 65p.  
 L.T. TRANSFORMER "TOROIDAL". Prim. 240v. Sec. 30v. at 1/2 amp. Size 3 in. dia. thick. £1.65. P.P. 20p.  
 L.T. TRANSFORMER. Prim. 240v. Sec. 27-0-27 at 800 m/a. 7.5 amp. £2.25. P.P. 50p.

TRANSFORMERS  
 L.T. TRANSFORMER. Prim. 110/240v. Sec. 0/24/40v. 1 1/2 amp. (Shrouded) £1.95. P.P. 50p.  
 L.T. TRANSFORMER. Prim. 200/250v. Sec. 20/40/60v. at 2 amp. (Shrouded) £3. P.P. 50p.  
 L.T. TRANSFORMER (H.D.). Prim. 200/250v. Sec. 18v. at 27 amp.; 40v. at 9.8 amp.; 40v. at 3.6 amp.; 52v. at 1 amp; 25v. at 3.7 amp. £17.50. P.P. £2.50.  
 L.T. TRANSFORMER prim. 240v. Sec. 18v @ 1.5 amp. & 12v @ 1 amp. £2. p.p. 50p.  
 L.T. TRANSFORMER PRIM. 120-0-120v. Sec. 12v. at 1 amp. 70p. P.P. 20p.  
 L.T. TRANSFORMER PRIM. 240v. Sec. 18v. 1 amp. £1. P.P. 20p.

WE REGRET THAT ALL ORDERS VALUE UNDER £5 MUST BE ACCOMPANIED BY THE REMITTANCE.

HIGH-SPEED MAGNETIC COUNTERS. 4 digit (non reset) 24v or 48v (state which). 4 x 1 x 1in 65p. P.P. 15p  
 5 digit (non reset) 24v £1.15. P.P. 15p  
 3 digit 12v (Rotary Reset) 2 1/4 x 1 1/4 x 1 1/4in. £1.30. P.P. 15p  
 6 digit (Reset) 240v A.C. £3.50. P.P. 25p



H.D. ALARM BELLS. 6in. Dome. 6/8v. d.c. Heavy cast housing for exterior/interior use. £2.75. P.P. 75p. Connecting wire (twin/twisted) 220yd. reel £3. p.p. 75p.  
 MINIATURE REED RELAYS (3/6v). 1 make (30 x 8mm) 20p; 2 make (32 x 12mm) 30p  
 12v. 2 c/o 5 amp. H.D. RELAY, 65p. P.P. 15p  
 240v. A.C. RELAY (PLUG-IN TYPE). 3 c/o 10 amp. contact with base. 85p. P.P. 25p.  
 10 TURN POTENTIOMETERS (M.P.C.). 10 K ohm. 0.5% Lin. 38mm x 22mm. 14mm Standard Spindle. £2. P.P. 15p. (Dials 50p each.)

GARRARD PLINTH & COVER. For "Zero-100" etc. beautifully finished in brushed aluminium and black with hinged smoke/grey perspex lid. £9.75 P.P. £1.

24v. A.C. RELAY (PLUG-IN). 3 pole c/o 75p. P.P. 15p. 2-pole change over. 55p. P.P. 15p.  
 BULK COMPONENTS OFFER. Resistors/Capacitors. 600 new components. £2.50. P.P. 35p. Trial order 100pcs. 60p. P.P. 20p. 15% V.A.T.  
 REGULATED POWER SUPPLY. Input 110/240v. output 9v. D.C. 1 1/2 amp.; 12v. D.C. 500 m/a. £4.75. P.P. 75p.  
 D.C. SUPPLY. Input 240v a.c. giving 17 1/2v d.c. @ 1 1/2 amp. (unsmoothed) 2 1/4 x 2 1/4in. £2.25p. p.p. 45p  
 MINIATURE "ELAPSED TIME" INDICATORS. (0-5000 hours). 45 x 8mm. 75p.

L.T. TRANSFORMER prim. 240v. Sec. 20v @ 2.5 amp. £2. p.p. 50p.  
 L.T. TRANSFORMER ("C" CORE). 200/240v. Secs. 1-3-8-9v. All at 1.5 amp. 50v. at 1 amp. £2.50. P.P. 50p.  
 L.T. TRANSFORMER ("C" CORE). 200/240v. Secs. 1-3-9-27v. All at 4 amp. £4. P.P. 50p.  
 L.T. TRANSFORMER ("C" CORE). 200/240v. Secs. 1-3-9-27v. All at 10 amp. £7.50. P.P. £1.50.  
 L.T. TRANSFORMER ("C" CORE). 200/240v. Secs. 1-3-9-20v. All at 4 amp. £5.50. P.P. 75p.  
 L.T. TRANSFORMER ("C" CORE). 120/120v. Secs. 1-3-9-9v. All at 10 amp. £6.50. P.P. 75p.  
 L.T. TRANSFORMER ("C" CORE). 110/240v. Secs. 1-3-9v. 10 amp. 35v. 1a.: 50v. 750 M/A. £8.50. P.P. 75p.

# ELECTROVALUE



**Why hunt around when there's Catalogue 7 issue no 3?**

- UP-DATED PRODUCT & PRICE INFORMATION
- REFUND VOUCHER

We have made it just about as comprehensive and up-to-the-minute as possible. Thousands of items from vast ranges of semi-conductors including I.C.s to components, tools, accessories, technical information and diagrams are included as well as a refund voucher worth 25p for spending on orders list value £5 or more. SEND NOW FOR YOUR COPY BY RETURN. It's an investment in practical money-saving and reliability! **30p** post paid

**+ E.V. PRICE STABILIZATION POLICY**

This is one of reviewing prices every 3 months rather than trying to keep up with day by day changes as they occur. We have in fact held prices for two such periods (Jan. 1-July 1) and our next price review is due October 1st

**+ E.V. DISCOUNT PLAN**

Applies to all items except the few where prices are shown NETT. 5% on orders from £5 to £14.99; 10% on orders value £15 or more

**+ FREE POST & PACKING**

In UK for pre-paid mail orders over £2 (except Baxandall cabinets). If under there is an additional handling charge of 10p.

**+ QUALITY GUARANTEE**

All goods are sold on the understanding that they conform to makers' specifications. No rejects, seconds or sub-standard merchandise

## ELECTROVALUE LTD

All communications to Section 2/8  
**28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB**  
 Telephone Egham 3603, Telex 264475. Shop hours: 9-5.30 daily, 9-1 p.m. Sats  
**NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester M19 1NA**  
 Telephone (061) 432 4945. Shop hours: Daily 9-5.30 p.m., 9-1 p.m. Sats  
**U.S.A. CUSTOMERS** are invited to contact **ELECTROVALUE AMERICA**, P.O. Box 27, Swarthmore PA 19081

The

\* A Complete Kit \*  
or fully built.

## 'MISTRAL' Digital Clock



Kit £12.50 (incl)

Built £18.00.

- Pleasant green display ◦ 24 Hour readout
- Silent Synchronous Accuracy ◦ Fully electronic
- Pulsating colon ◦ Push button setting
- Building time 1Hr ◦ Attractive acrylic case
- Easy to follow instructions ◦ Size 10.5 x 5.7 x 8cm
- Ready drilled PCB to accept components

Exetron Time Ltd. offer this unique transformerless design at a substantial saving on retail price. The kit is complete less mains lead - all you require is a soldering iron, solder, and screw driver to assemble your own digital clock.



**EXETRON Time Ltd**  
 Regal House,  
 Penhill Road,  
 LANCING, Sussex.

Payment: CWO, Cheque, Access, Barclaycard. (Quote Number)

# YOU COULD SAVE UP TO £1,000 PER ENGINEER \* WITH THIS BOOK


★ With the Colour Faults Guide system of rapid, on-the-spot diagnosis of colour set faults the originating firm, Colour Vision Rentals Ltd, reported savings of the order of **well over £1,000 per engineer per year.**

**HOW IT IS DONE . . .** A tabulated index of fault symptoms and the most common circuit troubles causing them quickly enables the engineer in the customer's home to locate the cause of the breakdown and the panel or assembly in which it has occurred. He can then change the panel (etc) on the spot from his van stock and return the faulty item for repair subsequently, and return to stock. The originating firm calculates that an average of about 3 hours a week per engineer is saved, plus an average of one workshop uplift less per engineer — hence the £1,000-plus per year saving.

The Colour Faults Guides, E R T's top innovation of 1974-5, covering 14 widely used chassis, are now collected in book form for sale at £1.70 inclusive per issue.

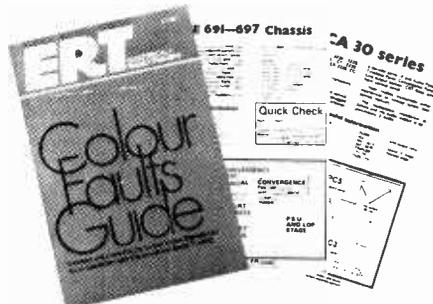**CAN YOU AFFORD YOUR MEN NOT TO HAVE A COPY WITH THEM ON EVERY JOB?**

The fourteen chassis covered in the book comprise:- Decca 30 series; GEC 2210 series; GEC Hybrid 2040 series; Hitachi range — CAP 160, CEP 180, CNP 190; ITT CVC5; Philips G8; Pye CT200 series, Pye 691-697; Rank R I A823/A; Thorn C E 3000 & 3500; Thorn (BRC) 8000/8500 series; Bang & Olufsen 39 series — Beovision 3500, 3600, 400, 600; Skantic — all models except earlier 22in. hybrid.



Order Coupon  
 To General Sales Dept., Room 11, ERT, Dorset House, Stamford St., London SE1 9LU

Please send me . . . . . copy/copies of Colour Faults Guide at £1.65 inclusive.

I enclose remittance value £ . . . . . (Cheques payable to IPC Business Press Ltd.)

Name (please print) . . . . .

Address . . . . .

Company regd. in England No 677128  
 Regd. office Dorset House, Stamford St., London SE1 9LU



# TELETYPE 28 — NEW SPECIAL PRICE

**TELETYPE 28** without keyboard. Good condition (can be used as receive only) **£32.50** ea.

**TELETYPE 28** with housing, keyboard and Power supply **£45** ea.

Limited quantities — information in process of being obtained — this may not be available when orders are dispatched but we guarantee to forward comprehensive information at the earliest possible time.

# TEKTRONIX OSCILLOSCOPE

Type 536 with T time base and IL20 plug-ins

**£675**

**MARCONI** Signal Generator. TF801B 12 - 470MHZ **£120** ea.  
**MARCONI** Valve Voltmeter type TF1041B **£45**.

**MARCONI** TF934/2 FM Deviation Meter **£35**.  
**MARCONI** TF1020A RF Power Meter 150 and 300 Watts. As New. **£60** ea

**MARCONI** TF1020A RF Power Meter 50 and 100 Watts. As New. **£45** ea.

**MARCONI** TF1094A/S HF Spectrum Analyser. Late model. Must go. **£160**.

**MARCONI** TF1434/2 Counter Range extension unit 10-100MHZ **£25** ea.

**KELVIN & HUGHES** Single Channel Recorders with spare paper **£18** ea.

**FURZEHILL** Valve Voltmeter V200. 10mv full scale. **£18** ea. Nice condition.

**NOT OUR SCENE — Large Lathe Cardiff — Buck & Hickman £150**

**MARCONI OSCILLOSCOPES**  
TF1330 - DC - 15MHZ. Single Beam. **£65** ea.  
TF 1331 - DC - 15MHZ. Double Beam. **£85** ea.

**RHODE & SCHWARZ** Admittance Meter VLUK-BN3511. As new, **£110**.

**BRUEL & KJOER** Voltmeter type 2409 2 cs to 200k/cs. **£85** ea.

**DUAL TRACE PLUG-IN** units for CD1212 Scopes DC-24MHZ **£35** ea.

**TELONIC** Sweep Generator SM2000/1. Main frame with 0-20kHz plug-in **£300**.

**TEKTRONIX** Oscilloscope type 516 **£240**.  
**MARCONI** TF 455E Wave Analyser. Excellent condition. **£55** ea.

**MARCONI** TF 867 Signal Generator 15KHZ to 30MHZ. **£50** ea.

**MARCONI** TF 885 Video Oscillator. **£30** ea.

**MARCONI** TF 791D Deviation Meter. **£90**.  
**MARCONI** TF 791C Deviation Meter. **£60** ea.

**EDDYSTONE RECEIVER** type 770U. **£90** ea.

**ROHDE & SCHWARZ** Receiver ESM180 BN 15073/2 **£425**.

**ROHDE & SCHWARZ** Generator 300-1000 MHZ. Type SDR BN 41022. **£300**.

**SE LABS** Oscilloscope type SM112 Double Beam DC-100MHZ **£295**.

**FLANN** Signal Generator type 501 0.8-3 GC/S **£90** ea.

**DATAPULSE** Generator 101 by Systron-Donner Corporation, **£90** ea.

**★ AB POTENTIOMETERS**  
100K + 100K LIN DUAL GANG **25p** ea.  
Discount for quantities. P. & P. extra

**EX-MINISTRY** CT436 Double Beam Oscilloscope DC-6 megs. Max Sensitivity 10mv/cm. Small compact. Size 10 X 10 X 16 in. Suitable for Colour TV servicing. Price **£85** each including copy of manual.

**FHACHI RAMP MODULE FX21 24** Volt DC input for 18 volt saw tooth output. Requires only external capacitor and 100K ohm potentiometer to control frequency range up to 100KHZ (eg 50 mfd electrolytic gives sweep of approx. 1 cm per second). In or out sync capability. Price **£5.75**. P. & P. 20p.

**★ TELEPHONES**  
**MODERN STYLE 706** BLACK OR TWO-TONE GREY **£3.75** ea. P. & P. 45p.  
**STYLE 7006** TWO-TONE GREEN OR GREY **£3.75** ea. P. & P. 45p.  
**HANDSETS**—complete with 2 insets and lead **£1.25** ea. P. & P. 37p.  
**DIALS ONLY**. 50p ea. P. & P. 30p.  
**STILL AVAILABLE** MODERN STANDARD TELEPHONES IN GREY OR GREEN WITH A PLACE TO PUT YOUR FINGERS LIKE THE 746. **£3.00** ea. P. & P. 45p.

**★CAPACITOR PACK** 50 Brand new components only **50p**. P & P 27p  
**★P.C. MOUNT SKELETON PRE-SETS.** Screwdriver adjust 10. 5 and 2.5M a **2p** ea. 1M. 500. 250 and 25K a **4p** ea. Finger adjust 10. 5 and 2.5M a **3p** ea. 1M 500. 250 and 25K a **5p** ea. Min. P. & P. 15p

25p the LOT. P & P. 15p.  
**★PHOTOCELL** equivalent OCP71. **13p** ea  
**GRATICULES**. 12 cm. by 14 cm. in High Quality plastic. **15p** each. P. & P. 8p.

**VENNER** Hour Meters—5 digit. wall mount —sealed case Standard mains. **£3.75** ea P. & P. 55p.

**RESETTABLE COUNTERS**—4 digit by Stonebridge/Sodeco 1,000 ohm coil. **£2** ea. P. & P. 35p.

**★Beehive Trimmer 3/30 pf.** Brand new Qty 1-9 **13p** ea. P. & P. 15p. 10-99 **10p** ea. P. & P. 25p. 100-999 **7p** ea. P. & P. free.

**★Vast quantity of good quality components —NO PASSING TRADE—so we offer 3 LB. of ELECTRONIC GOODIES for £1.70 post paid**

**TRANSFORMERS.** All standard inputs. Gard/Par/Part. 450-400-0-400-450. 180 MA. 2 x 6.3v. **£3** ea.

**E.H.T. CAPACITORS**  
1 mfd 7.5KV working. 2 mfd 5KV working  
8 mfd 2.5KV working. 0.5 mfd 10KV working **£2** each.

**DELIVERED TO YOUR DOOR** 1 cwt. of Electronic Scrap chassis, boards etc No Rubbish. FOR ONLY **£4**. N. Ireland **£2** extra  
**P.C.B. PACK** S & D Quantity 2 sq. ft.—no tiny pieces. **50p** plus P. & P. 25p

**HF Crystal Drive Unit.** 19 in. rack mount. Standard 240V input with superb crystal oven by Labgear (no crystals) **£5** ea. Carr. **£2**.

**FANTASTIC VALUE**  
Miniature Transformer. Standard 240V input. +3V 1 amp output. Brand New. **65p** ea. P. & P. 20p Discount for quantity.

**RAPID DISCHARGE**  
1 mfd 5.6KV **£2.50** ea. 0.9 mfd 15KV **£3.50** ea. 0.15 mfd 120KV **£7** ea. Carriage extra.

**★TRIMMER PACK**. 2 Twin 50/200 pf ceramic. 2 Twin 10/60 pf ceramic. 2 min strips with 4 preset 5/20 pf on each. 3 air spaced preset 30/100 pf on ceramic base ALL BRAND NEW

**BOURNS TRIMPOT POTENTIOMETERS.** 20; 50; 100; 200; 500 ohms: 1; 2; 2.5; 5; 10; 25K at **35p** ea ALL BRAND NEW  
**RELIANCE P.C.B.** mounting. 270; 470; 500 ohms: 10K at **35p** ea. ALL BRAND NEW.  
**TENTURNPOTS.** Ex. equ. As new Micropot Model 205 Two point nine ohms 0.1% @ **£1.50** ea. P&P 20p.  
Bourns Model 3507S-3-101 100 ohms. **£1.25** ea P&P 15p

**FIBREGLASS PRINTED CIRCUIT BOARD.** Brand New Single or Double sided. Any size **1 1/2p** per sq. in. Postage 20p per order.

**FHACHI VCC MODULE FX11—10HZ-100KHZ**  
Size 2 x 1 1/2 x 3/8" H. Input 12V to 24V DC (not centre tapped) 18V input giving 10V constant amplitude output. Requires only a 1 meg ohm potentiometer to tune entire range — or can be swept with a saw tooth input. Price **£5.75**. P. & P. 20p.

**★HIGH VALUE PRINTED BOARD PACK.** no two boards the same—no short leaded computer boards. **£1.75** post paid

**★METER PACKS**—3 different meters for **£2**. P. & P. 55p.

## LOW FREQUENCY WOBBULATOR

For alignment of Receivers, Filters, etc. 250KHz to 5MHz, effective to 30MHz on harmonics. Three controls—RF level, sweep width and frequency. Order LX63. Price **£8.50** P. & P. 35p.  
As above but can have extended cover range down to 20KHz by addition of external capacitors. Order LX63E. Price **£11.50** P. & P. 35p.  
Both models can be used with any general-purpose oscilloscope. Requires 6.3V AC input. Supplied connected for automatic 50Hz sweeping. An external sweep voltage can be used instead. These units are encapsulated for additional reliability, with the exception of the controls (not cased, not calibrated).

**DON'T FORGET YOUR MANUALS S.A.E. WITH REQUIREMENTS**

## 20HZ to 200KHZ SINE AND SQUARE WAVE GENERATOR

In four ranges. Wien bridge oscillator thermistor stabilised. Separate independent sine and square wave amplitude controls. 3V max sine 6V max square outputs. Completely assembled P.C. Board, ready to use. 9 to 12V supply required. **£8.85** each. P. & P. 25p. Sine Wave only **£6.85** each. P. & P. 25p.

## WIDE RANGE WOBBULATOR

5 MHz to 150 MHz (Useful harmonics up to 1.5 GHz) up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10-7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6-3V AC and use within minutes of receiving. All this for only **£6.75**. P. & P. 25p. (Not cased, not calibrated.)

## TRANSISTOR INVERTORS

**TYPE A**  
Input: 12V DC  
Output: 1.3kV AC 1.5MA  
Price **£3.45**

**TYPE B**  
Input: 12V DC  
Output: 1.3kV DC 1.5MA  
Price **£4.70**

**TYPE C**  
Input: 12V to 24V DC  
Output: 1.5kV to 4kV AC D.5MA  
Price **£6.35**  
Postage & Packing 36p


**TYPE D**  
Input: 12V to 24V DC  
Output: 14kV DC 100 micro amps at 24V. Progressively reducing for lower input voltages  
Price **£11**

**MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH.** 2 HZ to 8 MHz. Hook up a 9 volt battery and connect to your scope and have two traces for ONLY **£6.25**. P. & P. 25p.  
**STILL AVAILABLE** our 20 MHz version at **£9.75**. P. & P. 25p.

Unless stated — please add **£2.00** carriage to all units.

**VALUE ADDED TAX not included in prices—Goods marked with ★ 25% VAT, otherwise 8% Official Orders Welcomed, Gov./Educational Depts., Authorities, etc., otherwise Cash with Order**

Open 9 a.m. to 5.30 p.m. Mon. to Sat.

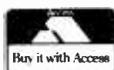

# CHILTMHEAD LTD



7/9 ARTHUR ROAD, READING, BERKS. (rear Tech. College, Kings Road)

Tel.: Reading 582605

# SERVICE TRADING CO

## RELAYS

SIEMENS PLESSEY, etc. MINIATURE RELAYS			
1	2	3	4
52	4-8	2c/o	75p*
58	5-9	6c/o	85p*
185	8-12	6M	65p*
230	9-18	2c/o/HD	75p*
430	15-24	4c/o	85p*
700	18-24	2c/o	65p*

(1) Coil ohms; (2) Working d.c. volts; (3) Contacts; (4) Price HD=Heavy Duty. All Post Paid. (\*Including Base)

### OPEN TYPE RELAYS

**6 VOLT D.C.** 1 make con. 35p Post 15p.  
**9 VOLT D.C. RELAY**  
 3 c/o 5 amp contacts 70 ohm coil 75p Post 15p  
**12 VOLT D.C. RELAY**  
 3 c/o 5 amp contacts 120 ohm coil 75p Post 15p  
**24 VOLT D.C.** 3 c/o 600 ohm coil 75p Post 15p  
 2 HD c/o 700 ohm coil 75p Post 15p  
 4 c/o 300 ohm coil 85p Post 15p

### ENCLOSED TYPE RELAYS

24V D.C. 3 c/o 75p. Post 20p Base 15p  
**24 VOLT A.C.** Mfg. ITT 3 h.d. c/o contacts 55p. Post 20p. Base 15p extra  
**55 VOLT A.C.**  
 3 heavy duty c/o contacts. Price 55p. Post 20p. Base 15p  
**100 VOLT A.C.**  
 2 c/o sealed type. octal base 75p. Post 20p. Base 15p  
**240 VOLT A.C. RELAY**  
 240V. A.C. heavy duty 3 c/o contacts. Price 75p. Post 20p. Octal base 15p extra  
**220/240 VOLT AC RELAY**  
 3 c/o 5 amp cont. Sealed M.f.g. ISKRA. £1.25. Post 20p Base 15p extra  
**ARROW 230/240V AC** 2 c/o 15 amp contacts. Arrow connectors. £1.00. Post 20p.  
**110 VOLT A.C.** 2 c/o. 20 amp. £1.25. Post 15p.  
**CLARE-ELLIOT Type RP 7641 G8**  
 Miniature relay. 675 ohm coil. 24 volt D.C. 2 c/o. 70p. P.P.  
**MANY OTHERS FROM STOCK, PHONE FOR DETAILS**

## PRECISION CENTRIGUGAL BLOWERS

Mfg. by Smiths Industries Miniature model. Series SF/200. Size 95mm x 82mm x 82mm. Aperture 38mm x 31mm. 12 c.f.m. £2.75. Post 50p.  
 Mfg. by Airflow Developments Ltd  
 Precision made, continuously rated, smooth running 230/240v A.C. motor 80c.f.m. As illustrated but with round aperture. £6.50. Post 75p.  
 Mfg. by Woods.  
 Extremely powerful 220/250v A.C. 0.3 amp. 2,700 r.p.m. continuously rated. Capacitor start. Cast construction. Aperture 66mm x 50mm. O/A 200mm. £12.00. Post £1.00

## 230 VOLT FAN ASSEMBLY

Continuously rated, removable aluminium blades. Price £1.25. Post 50p.  
**VAT 25%**

## C/O MICRO SWITCH

VERY SPECIAL OFFER. Mfg. by C.E.M. 3 amp 250 volt. 10 amp 125 volt. 50 for £3. Post 36 100 for £5. Post 50p. 1,000 for £45. Post paid.  
**DOUBLE POLE C/O or 2 make/2 break micro switch** 10 amp 250 v A.C. With detachable roller assembly. 10 for £2.50. Post 50p. (Min order 10)

## LATCHING RELAY

Twin latching relay. Flip-flop. 2c/o each relay. Mains contacts 115 volts A.C. or 50 volt D.C. operation or 240 volts A.C. with 2.5K resistor. 85p. Post 20p

## COIN MECHANISM (Ex-London Transport)

Unit containing selector mechanism for 1p, 2p & 5p coins. Micro switches, relays, solenoid-operated hopper. 24 volt D.C. Precision built to high standard. Incredible VALUE at only £2.80. Post £1. VAT 25% (Total price inc. VAT & Post £4.21)

## 230-250 VOLT A.C. SOLENOID

Similar in appearance to illustration. Approximately 1 1/2 lb. pull. Size of feet 1 1/8" x 1 1/8". Price £1.00. Post 25p.

## SOLENOID HEAVY DUTY MODEL

230/250v A.C. Apprx. 10lb. pull. 4" long x 2 1/2" wide x 3" high. £2.50. Post 50p.

## 24 VOLT DC SOLENOIDS

UNIT containing: 1 heavy duty solenoid approx 25 lb pull at 1 in. travel, 2 solenoids of approx. 1 lb. pull at 1/2 in. travel, 6 solenoids of approx. 4 oz. pull at 1/2 in. travel. Plus 1 24V D.C. 1 heavy duty 1 make relay. Price: £2.50. Post £1.00. **ABSOLUTE BARGAIN.**

## 240 V.A.C. SOLENOID OPERATED FLUID VALVE

Rated 1 p.s.i. will handle up to 7 p.s.i. Forged brass body, stainless steel core and spring 3/8 in. b.s.p. inlet/outlet. Precision made. British mfg. PRICE £2.25. Post 50p. NEW original packing

## 600 WATT DIMMER SWITCH

Easily fitted. Fully guaranteed by makers. Will control up to 600 watts of all lighting except fluorescent at mains voltage. Complete with simple instructions. £2.75. Post 25p

1000 watt model	£4.00. Post 25p
2000 watt model	£8.00. Post 40p

## VARIABLE VOLTAGE TRANSFORMERS

Carriage extra  
**INPUT 230 v. A.C. 50/60**  
**OUTPUT VARIABLE 0/260 v. A.C.**  
**BRAND NEW. All types.**  
 200W (1 Amp) £10.00  
 0.5 KVA (Max. 2 1/2 Amp) £11.50  
 1 KVA (Max. 5 Amp) £16.50  
 2 KVA (Max. 10 Amp) £30.00  
 3 KVA (Max. 15 Amp) £33.00  
 4 KVA (Max. 20 Amp) £80.00  
 (max. 37.5 Amp) £102.50

## LT TRANSFORMERS

0 6, 12 volt r. 10 amp	£5.60 Post 70p
0 10, 17 18 volt r. 10 amp	£7.90 Post £1.00
0 6, 12 volt r. 20 amp	£9.00 Post £1.00
0 12, 24 volt r. 10 amp	£9.20 Post £1.00
0 4, 6, 24, 32 volt r. 12 amp	£9.90 Post £1.00
0 6, 12 17 18 20 volt r. 20 amp	£10.40 Post £1.00

Other types to order at short notice - Phone your enquiries

## AUTO TRANSFORMERS

Step up step down 0 115 200 220/240 volts  
 At 75 watt £2.64 Post 40p 150 watt £3.50 Post 50p 300 watt £6.20 Post 60p 500 watt £9.20 Post 75p 1000 watt £12.00 Post 90p.

## STROBE! STROBE! STROBE!

- ★ FOUR EASY TO BUILD KITS USING XENON WHITE LIGHT FLASH TUBES, SOLID STATE TIMING + TRIGGERING CIRCUITS. PROVISION FOR EXTERNAL TRIGGERING. 230-250v. A.C. OPERATION.
- ★ HY-LITE STROBE Mk IV  
 ★ Designed for use in large rooms, halls and utilizes a silica tube printed circuit. Speed adjustable 1/20 f.p.s. Light output greater than many (so called 4 Joule) strobes. Price £14.00. Post 75p
- ★ RANGE OF THREE OTHER STROBE KITS FROM STOCK.  
 FROM: £6.30 to £22.00 S.A.E. (Foolscap) for details.
- ★ **BIG BLACK LIGHT**  
 400 Watt. Mercury vapour ultra violet lamp. Extremely compact and powerful source of u.v. Innumerable industrial applications also ideal for stage - display discos etc. P.F. ballast is essential with these bulbs. Price of matched ballast and bulb £21.00. Post £1.50. Spare bulb £8.00. Post 65p.
- ★ **BLACK LIGHT FLUORESCENT U.V. TUBES**  
 4ft. 40 watt £5.50 (callers only) 2ft. 20 watt £4.25. Post 60p (For use in stan. bi-pin fittings) MINI 12in. 8 watt £1.60. Post 25p 9in. 6 watt £1.30. Post 25p. Complete ballast unit and holders for either 9" or 12" tube £1.70. Post 30p (9" x 12" measures approx.)

## U.D.I. SINGLE CHANNEL. 750 watt MANUAL/AUTO DIMMER

750W Solid State Fader. with three functions. Manual fade. Auto fade-up. Auto fade-down. Automatic cycling up and down. Functions selected with three position rocker switch. Two ranges of cycling for 'Flashing' or 'Slow blending'. Ready built module 6" x 3" glass fibre board incorporating 10 amp TRIAC. Two or more modules for top quality colour blending and flashing effects. PRICE £15.00. Post 65p.

## SQUAD LIGHT

A new conception in light control. Four channels each capable of handling 750 watts of spotlights, floodlights or dozens of small mains lamps. Seven programs all speed controlled plus flash modulation, effectively giving 14 different displays. Makes sound-to-light obsolete. Completely electrically and mechanically noise free. Can be used on same circuit as radio mikes or sensitive amplifiers. A whole new range of lighting effects possible with astounding results. Already in use in London's foremost theatres, night clubs and discos. Conforms to all R.F.I. tests, including Common Market regulations. Supplied in tough, well designed case with embossed front panel. Price only £60.00. Post 75p. S.A.E. (Foolscap) for further details.

## WHY PAY MORE?!

MULTI RANGE METER. A.C. volts 2.5-500. D.C. volts 2.5-500 (Sensitivity 2000Ω/V DC & AC). DC current 0.1/10/100 mA. Ohms range. Sturdy compact moving coil instrument with 21 ranges. dimensions 120x80x44mm. Weight 0.32 kg. SERVICE TRADING CO. Price £5.00. Post 50p. (Total price inc. VAT & Post £5.94).

## METERS NEW

90mm Diameter.  
 Type 65C5 2A DC M/C. 5A DC M/C. 10A DC M/C. 20A D.C. M/C.  
 Type 62T2 1A A.C. M/I. 20A A.C. M/I. 300V A.C. M/I. ALL ABOVE £2.50. Post 30p  
 Type 65L5 300V A.C. R/M/C. £2.75. Post 30p

## VAT

VAT at 8% MUST BE ADDED TO ALL ORDERS FOR THE TOTAL VALUE OF GOODS INCLUDING POSTAGE UNLESS OTHERWISE STATED

## GEARED MOTOR

230/240 volt A.C., smooth powerful, continuously rated. Two types 32 r.p.m. or 110 r.p.m. Either type £4.75. Post 50p

## REVERSIBLE MOTOR

General Electric, 230V A.C. 1,600 r.p.m. 0.25 amp. Complete with anti-vibration mounting bracket and capacitor. O/A size 110mm x 95mm. Spindle 5/16" dia. 20mm long. Ex-equipment tested. £3.00. Post 50p

## 20 r.p.m. GEARED MOTOR

230/240 volt 20 r.p.m. motor £1.00. Post 20p

## BODINE TYPE N.C.I. GEARED MOTOR

(Type 1) 71 r.p.m. torque 10 lb. in. Reversible 1/70th h.p. cycle 38 amp. (Type 2) 28 r.p.m. torque 20 lb. in. Reversible 1/80th h.p. 50 cycle 28 amp. The above two precision made U.S.A. motors are offered in 'as new' condition, input voltage of motor 115v A.C. Supplied complete with transformer for 230/240v A.C. input. Price, either type £6.25. Post 75p or less transformer £3.75. Post 65p  
 These motors are ideal for rotating aerials, drawing curtains, display stands, vending machines, etc. etc

## BENDIX MAGNETIC CLUTCH

A superb example of Electro-mechanics! The main body is in two sections. The coil section is fixed and has a 3/8 in. sleeve. The drive section rotating on the outer perimeters. The uniting plate has 3/8 in ID bearing concentric with main section and 18-tooth cog wheel.  
 When energized transmission is extremely powerful. 24V d.c. at 240 MA. OUR PRICE JUST £2.50 Post 45p

## ROTARY VACUUM AIR COMPRESSOR AND PUMP

Carbon vane, oil-less, 100/115v A.C. 1/12 h.p. motor. 50/60 cycle 2875/3450 r.p.m. 20" vacuum 1.25 c.f.m. 10 p.s.i. (approx. figures). New unused surplus stock, with elect connection data. Fraction of maker's price £12.00. Post £1.00. Suitable transformer £3.50. Post 50p

## UNISELECTOR SWITCHES - NEW

4 BANK 25 WAY FULL WIPER 25 ohm coil, 24v. D.C. operation £6.90. Post 50p.  
 6 BANK 25 WAY FULL WIPER 25 ohm coil, 24 v. D.C. £7.90. Post 50p.  
 8 BANK 25 WAY FULL WIPER 24 v. D.C. operation £9.50. Post 65p.

## TIME SWITCH

Horstmann Type V Mk II Time Switch. 200/250 volt A.C. Two on/two off every 24 hours, at any manually pre-set time. 30 amp contacts. 36-hour spring reserve in case of power failure. Day omitting device. Fitted in heavy high impact case, with glass observation window. Built to highest Electricity Board spec. individually tested. Price £7.75. Post 50p. (Total inc. VAT £8.91)

## A.C. MAINS TIMER UNIT

Based on an electric clock, with 25 amp single pole switch, which can be preset for any period up to 12 hrs ahead to switch on for any length of time, from 10 mins. to 6 hrs. then switch off. An additional 60 min. audible timer is also incorporated. Ideal for Tape Recorders, Lights, Electric Blankets, etc. Attractive satin copper finish. Size 135 mm x 130 mm x 60 mm. Price £2.25. Post 40p. (Total inc. VAT & Post £2.87.)

## PROGRAMME TIMERS

230/240 Volt A.C. 15 RPM Motors. Each cam operates a c/o micro switch. Ideal for lighting effects, animated displays etc. Ex equipment - tested similar to illustration.  
 2 cam model 15 r.p.m. £2.00 post 35p  
 4 cam model 15 r.p.m. £2.50 post 40p  
 8 cam model 20 r.p.m. £4.75 post 60p  
 8 cam model each cam fully adjustable. 6 r.p.m. M.f.g. by Magnetic Devices. £7.50. Post 60p.

## POWER RHEOSTATS

new ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.  
 25 WATT 10, 25, 100, 150, 250, 500, 1k, 1.5k ohm £1.70. Post 20p. 50 WATT 1, 5, 10, 25, 50, 100, 500, 1k ohm £2.10. Post 25p. 100 WATT W/10, 25, 50/100/250/500/1k/1.5k/2.5k/5k ohm, £3.30. Post 35p.  
 Black Silver Skirted knob calibrated in Nos. 1-9. 1 1/2 in. dia. brass bush. Ideal for above Rheostats, 22p ea.

## 'GENTS' 6" ALARM BELL

200/250 volt AC/DC. Brand New. Price: £5.00. Post 75p (illus.). VAT 25%.

## 'STC' 6" RED ALARM BELL

Brand New. Price: £4.00. Post 50p. 24/48V DC. VAT 25%

## INSULATION TESTERS (NEW)

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L. 8 in., W. 4 in., H. 6 in., weight 6 lb.  
 500 VOLTS 500 megohms £30.00 Post 80p.  
 1000 VOLTS 1000 megohms £36.00. Post 80p.

ALL MAIL ORDERS, ALSO CALLERS AT: 57 BRIDGMAN ROAD, CHISWICK, LONDON, W4 5BB. Phone: 01-995 1560. Closed Saturdays.

SHOWROOMS NOW OPEN AMPLE PARKING

PERSONAL CALLERS ONLY 9 LITTLE NEWPORT STREET, LONDON, WC2H 7JJ. Tel.: 01-437 0576

### Fully guaranteed Individually packed VALVES

A1065	1.25	ECL82	0.35	GZ37	1.00	PY33	0.60
ARR	0.55	ECL83	0.70	KT66	2.50	PY80	0.40
ATP4	0.50	ECL86	0.60	KT88	3.85	PY81	0.40
B12H	3.00	EF36	0.65	MH4	0.75	PY82	0.40
CY31	0.50	EF37A	1.20	MH6	0.85	PY83	0.40
DAF96	0.55	EF40	0.75	OA2	0.45	PY86	0.40
DF96	0.55	EF41	0.65	OB2	0.45	PY80	1.00
DK96	0.70	EF80	0.30	PABC80	0.40	PY800	0.45
DL92	0.40	EF83	1.25	PC97	0.80	PY801	0.60
DL96	0.60	EF85	0.35	PC900	0.50	QQV03-10	1.40
DY86/87	0.40	EF86	0.35	PCC84	0.40	QQV06-40A	0.40
EY802	0.45	EF89	0.30	PCC85	0.40		
EB8CC/01	1.20	EF92	0.50	PC89	0.50		
E180CC	0.70	EF95	0.40	PCF189	0.80	R19	0.75
E182CC	1.25	EF183	0.35	PCF80	0.40	SC1/400	3.00
EASO	0.40	EF184	0.35	PCF82	0.40	SC1/600	5.00
EABC80	0.40	EFL200	0.75	PCF84	0.80	SP61	0.75
EAF42	0.75	EL34	0.70	PCF86	0.80	TT21	5.00
EB91	0.30	EL36	0.60	PCF200	0.75	U25	0.85
EBC33	1.00	EL37	1.80	PCF201	0.75	U26	0.75
EBC41	0.75	EL41	0.80	PCF801	0.55	U27	0.65
EBF80	0.40	EL81	0.60	PCF802	0.50	U191	0.75
EBF83	0.50	EL82	0.55	PCF805	0.90	U801	0.75
EBF89	0.40	EL84	0.30	PCF806	0.75	UABC80	0.40
ECC52	0.35	EL85	0.60	PCF808	0.90	UAF42	0.65
ECC81	0.40	EL86	0.45	PCH200	0.80	UBC41	0.80
ECC82	0.35	EL90	0.45	PCL81	0.55	UBF80	0.40
ECC83	0.35	EL504	0.80	PCL82	0.40	UBF89	0.40
ECC84	0.35	EM31	0.60	PCL83	0.65	UBL1	1.00
ECC85	0.40	EM80	0.55	PCL84	0.45	UBL21	0.70
ECC86	0.80	EM84	0.40	PCL86	0.50	UCC85	0.45
ECC88	0.50	EM87	1.00	PCL85	0.80	UCF80	0.75
ECC189	0.70	EY51	0.45	PFL200	0.70	UCH42	0.75
ECCF80	0.40	EY81	0.45	PL36	0.60	UCH81	0.45
ECCF82	0.40	EY86	0.40	PL81	0.50	UCLR2	0.45
ECCF801	0.75	EY88	0.50	PL82	0.45	UCLR3	0.65
ECH35	1.40	EZ40	0.70	PL83	0.45	UF41	0.70
ECH42	0.80	EZ41	0.75	PL84	0.45	UF80	0.35
ECH81	0.35	EZ80	0.30	PL504	0.80	UF85	0.45
ECH83	0.45	EZ81	0.30	PL508	1.00	UFR9	0.50
ECH84	0.45	GY501	0.75	PL509	1.35	UL41	0.70
ECL80	0.55	GZ34	0.70	PL802	1.75		

A lot of these valves are imported and prices vary for each delivery, so we reserve the right to change prices for new stock when unavoidable

UL84	0.40	3A4	0.60	6AL5	0.30	6AX5GT	1.00	6C6	0.50	6J7G	0.40
UY41	0.45	3BP1	7.00	6AL5W	0.55	6B7	0.70	6CB6	0.50	6K6GT	0.80
VR105/300.45		3D6	0.40	6AM6	0.60	6BA6	0.35	6CH6	1.45	6K7	0.55
VR150/300.45		354	0.40	6AN8	0.45	6BE6	0.40	6CL6	0.75	6K7G	0.30
X81M	1.40	3V4	0.85					6D6	0.55	6KRGT	0.80
X66	0.65	5B-254M	4.50					6E4B	0.85	6K25	1.00
Z800U	2.70	5D255M	4.50					6F7	1.10	6L6	1.90
Z801U	2.70	5R4GY	1.10					6FBG	0.75	6L6G	0.60
Z900T	1.20	5U4G	0.50					6F23	0.90	6L7G	0.40
1A3	0.55	5V4G	0.55					6F32	0.75	6SA7	0.60
114	0.26	5Y3GT	0.85	6AQ5	0.45	6BG6G	0.90	6F33	3.50	6SA7GT	0.40
1R5	0.40	5Z1	0.50	6AQ5W	0.70	6B6U	0.85	6J4WA	1.25	6SG7	0.50
154	0.30	5ZAGT	0.55	6AS6	0.60	6BQ7A	0.60	6J5	0.65	6SJ7	0.55
1T4	0.30	6AB7	0.60	6AT6	0.50	6BR7	1.20	6J5GT	0.50	6SJ7GT	0.35
1X2A	0.75	6AC7	0.60	6AU6	0.70	6BW6	1.00	6J6	0.30	6SK7	0.55
1X2B	0.75	6AH6	0.70	6AV6	0.45	6BW7	1.00	6J7	0.60	6SL7GT	0.50
2D21	0.50	6AK5	0.40	6AX6	0.45	6C4	0.40				
2K25	9.00	6AKR	0.40	6AX6GT	0.75						

VAT  
Please add 25%  
to all orders



ALL valves guaranteed


### TRANSISTORS, DIODES etc.

AC113	AF178	BSY38	OA2200	OC206	2N3054
AC126	AF186	BSY95A	OC22	SX754	2N3055
AC127	AF239	BV16	OC25	ZR11	2N3391
AC128	AF212	CRS1/10	OC26	ZR21	2N3638A
AC176	ASV26	CRS1/20	OC28	1N23A	2N3730
ACY16	ASV27	CRS1/30	OC29	1N25	2N3819
ACY19	ASV28	CRS1/40	OC35	1N32A	2N403R
ACY20	BC108	CRS3/10	OC36	1N39A	2N405R
ACY39	BC118	CRS3/20	OC42	1N43	2N4061
ACY40	BC119	CRS3/30	OC44	1N70	2N4785
AD149	BC136	CRS3/40	OC45	1N717	2N5295
AD161	BC137	CRS25/C25	OC70	1N415C	3N12R
AD162	BC148A	GET115	OC73	1N414R	3N154
AD211	BC172	GET116	OC78	2N456A	3N159
AD212	BC172A	GEX66	OC78D	2N70R	2S303
AF114	BC212A	NKT222	OC81	2N91R	2OR2
AF115	BCY31	OA5	OC82	2N130A	40Z50
AF116	BCY33	OA47	OC82D	2N130S	40Z51
AF117	BCY72	OA70	OC82DM	2N1307	40310
AF118	BF115	OA71	OC83	2N1309	4066R
AF124	BF167	OA73	OC139	2N2062	
AF125	BF185	OA79	OC140	2N2147	
AF126	BFV51	OA91	OC170	2N2411	
AF127	BFV52	OA200	OC172	2N2989	
AF139	BSV27	OA202	OC200	2N3053	

MINIMUM POSTAL ORDER £1. PERSONAL CALLERS WELCOME.  
MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves  
U.K. Postage £1-£2 20p, £2-£3 30p, £3-£5 40p, over £5 free

65N7GT	0.50	30C17	1.00	6064	0.60
65O7	0.55	30C18	0.90	6065	1.00
65V6GT	0.55	30F5	1.00	6067	0.70
6X4	0.40	39FL1	1.00	6080	2.30
6X5	0.40	30FL12	1.10	6146	3.35
6X6GT	0.50	30FL14	0.80	6146B	3.85
6Y6G	0.90	30L15	0.85	8020	5.00
6Z4	0.65	30L17	0.95	9001	5.00
6-30L2	0.90	30P12	1.00	9002	0.60
7B7	0.80	30P19	1.00	9003	0.70
7Y4	0.80	30P1	0.95	9004	0.35
9D6	0.40	30PL13	1.10	9006	0.35
11E2	6.00	30PL14	1.10		
12A6	0.65	35L6GT	0.75		
12A7E	0.45	35W4	0.50		
12AT7	0.40	35Z4GT	0.70		
12AU7	0.35				
12AV6	0.50	50C06G	1.10	DG7-5	12.00
12AX7	0.35	75	1.00	DG13-2	18.00
12BA6	0.45	75C1	0.75	MW13-353	8.00
12BE6	0.80	76	0.75	VC139A	4.00
12BH7	0.50	78	0.70	88J	8.00
12CR	0.55	80	0.75	88L	9.00
12E1	3.50	85A2	0.75		
12K5	1.10	723A/b	9.00		
12K7G	0.50	803	6.00		
12K8GT	0.70	805	14.00		
12Q7G	0.70	807	0.85		
12SA7GT	0.70	813	8.50		
12SG7	0.55	865A	1.20		
12SJ7	0.55	931A	6.00		
12Y4	0.40	954	0.50		
1457	1.00	955	0.50		
19A05	0.65	956	0.50		
19G3	8.00	957	0.50		
19G6	6.00	1305	0.20		
19H5	14.00	1629	0.70		
20P3	0.50	2051	1.00		
20P4	1.10	5933	3.00		
25L6GT	0.70	6057	0.75		
30C15	1.00	6060	0.70		

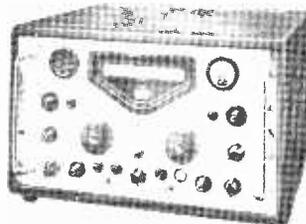VALVES AND TRANSISTORS  
Telephone enquiries for valves, transistors, etc., retail 749 3934 trade and export 743 0899



**RACAL RECEIVERS**  
Models RA17, RA17 Mk II, RA 17L, RA17W, RA117E, in condition from working "as seen" to brand new in cabinets. Prices on application  
**DIVERSITY SWITCH TYPE**  
MA168B, solid state, £45.00.  
RA98A SSB ADAPTOR, P.O.A.

**KAHN SSB ADAPTOR MODEL RSSB 62 1B** Designed for receivers with 455 500kHz IF (eg Collins 51J, AR88D etc) at 100mV (max) input. Features: Electronic A.F.C. carrier frequency diversity to combat fading 20 sec R.C. memory to maintain tuning during severe fading individual carrier meters nuvisitors low distortion production demo dular. Full spec & P.O.A.

**TEKTRONIX OSCILLOSCOPES**  
545-33 MHz. Separate time bases with delay. Price on application.  
**PLUG-IN UNITS**  
G-20 MHz differential 50MV-20V.  
D-High gain differential 1MV-50V.

**CT 480 SIGNAL GENERATOR** 70KMc/s to 12KMc/s £160  
**DIGITAL VOLTMETER DM 2003** 1kV peak input, 2v to 1kV £75.

**TECHNICAL MATERIAL CORP. EXCITER/TRANSMITTING MODE SELECTOR** Freq 2-32MHz M.O. and 10 crystal positions. Vernier tuning USB L.S.B. var carrier insertion etc £200.  
**F.S.K. EXCITER.** Freq 1-8.5MHz 0-100Hz continuous frequency shift. Up to 600Hz switched frequency correction. Modes F.A.X. F.S. M.S.C. C.W. £50.

**BOONTON FM/AM SIGNAL GENERATOR TYPES 202E & 202H.** 54-216 MHz in two ranges, complete with separate power supply unit £275.

**EHV POWER SUPPLY** 115V input 100KV at 5mA output £150.

**SOLARTRON CD 1400 Oscilloscope.**  
Few left, only £110.

Open 9-12.30, 1.30-5.30 p.m.  
except Thursday 9-1 p.m.



**TF 526B OSCILLATOR AND DETECTOR UNIT** £50.00.

**TF 1226B, TF1225A, TF 577A. WHITE NOISE TEST SET** £185.00. Full spec. on request.

**TF 1400S DOUBLE PULSE GENERATOR WITH TM 6600/S SECONDARY PULSE UNIT.** For testing radar, nucleonics, scopes, counters, filters etc. **SPEC. TF 1400S.** Rep. freq. 10Hz to 100kHz, pulse width 0.1 to 100u sec., delay -1.5 to +3000u sec., rise time 30N sec. **SPEC. TM 6600/S.** As for TF1400S except pulse width 0.5 to 25u sec., delay 0 to +300u sec. £175.

**TF 893 AUDIO OUTPUT METERS** £55.

**NOISE GENERATOR TF1053 (CT207).** Range 100-600MHz Noise factor up to 150 (21.7db) at 75 ohms Audio power up to 500MW £95.

**MARCONI TF893 AUDIO OUTPUT METERS** Price on application

**MARCONI HR23 TRIPLE DIVERSITY IS RECEIVERS.** Freq 3.275 MHz VFO or Extal positions Reception of independent single or double side band transmissions. Full specification and price on application

### HEWLETT - PACKARD

**175A OSCILLOSCOPE** with 1750A dual trace vert plug in and 1781B delay time base plug in 50MHz minimum bandwidth at 50mV/cm TM TB modes main, main single mixed main delayed delaying. Full Spec & P.O.A.

**540B TRANSFER OSCILLATOR.** Measures frequency up to 12.4GHz. May be used on its own or with freq counter. P.O.A.


**200AB AUDIO OSCILLATOR** 19kHz 600ohm balanced or unbalanced small size £25.

**300A HARMONIC WAVE ANALYSER** Freq 0-16kHz Full spec & P.O.A.

**MULLARD PRECISION VARIABLE CAPACITOR TYPE F.2.** 15pF to 336pF Supplied with individual calibration certificate Brand new in original packing £12. Carriage £1

**MS 111D DANISH PRODUCTION SIGNAL GENERATOR** 10Kc - 110Mc £150.
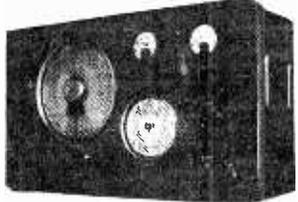
### BEST PRICES PAID FOR TEST AND COMMUNICATION EQUIPMENT. Single items or quantities. Private or Industrial.



**RF 801D/1/S SIGNAL GENERATOR.** Range 10-485 MHz in five ranges. R.F. output 0.1 uV-1V source e.m.f. Dial calibrated in volts, decibels and power relative to thermal noise. Piston type attenuator. 50Ω output impedance. Internal modulation at 1 kHz at up to 90% depth, also external sine and pulse modulation. Built-in 5MHz crystal calibrator. Separate R.F. and mod. meters. P.O.A.

**TF801B/2.** Spec as for TF801D but minor circuit differences. Working order £95.

**TF 1370 R.C. OSCILLATOR** sine/square wave 10Hz to 10MHz £140.

**TF995 A/1 or A/2 or A/2M SIGNAL GENERATORS.** AM/FM freq 1.5-220MHz Prices on application

**TF 934 DEVIATION METER**

# BENTLEY ACOUSTIC CORPORATION LTD.

7A GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX. Tel. 6743  
ALL PRICES SHOWN INCLUDE V.A.T.

0B2	0.45	6BC6	0.40	6L12	0.47	12B26	0.50	30P4	0.88	AZ31	0.80
0Z4	0.55	6BE6	0.41	6L18	0.64	12B7H	0.50	30P16	0.43	AZ41	0.50
1A3	0.55	6BG6G	1.23	6L19	2.00	12B7Y	0.85	30P18	0.50	D31	2.34
1ASGT	0.50	6BH6	0.75	6LD12	0.45	12E1	3.51	30P11	1.00	CL33	1.85
1A7GT	0.80	6BU6	0.64	6LD20	0.88	12J5GT	0.30	30P12L	0.45	EC32	1.00
1BSGT	0.50	6BK7A	0.85	6N7GT	0.70	12J7GT	0.70	30P13L	1.20	CV63	1.00
1C2	1.15	6BQ5	0.36	6P12	0.45	12K5	1.17	30P14L	1.20	CV988	1.20
1G6	1.17	6BQ7A	0.64	6PL15	0.36	12K7GT	0.50	30P15L	0.90	CY1C	1.00
1H5GT	0.50	6BR7	1.20	6Q7G	0.50	12K8	0.85	35A2	0.78	CY31	0.70
1LA	0.25	6BR8	1.25	6Q7GT	0.60	12L8	0.50	35C5	0.85	D63	0.50
1LD5	0.70	6CA	0.47	6Q7(M)	0.64	12S47	0.64	35D5	0.90	DAC32	1.80
1LN5	0.70	6BW6	1.00	6R7G	0.70	12S7GT	0.70	35F8GT	0.88	DAF91	0.40
1NSGT	0.70	6BW7	0.85	6R7(M)	0.88	12SC7	0.50	35W4	0.60	DAF96	0.80
1R5	0.50	6BX6	0.30	6SA7	0.55	12SG7	0.55	35Z3	0.88	DC90	0.70
1S4	0.30	6BY7	0.40	6SC7GT	0.50	12SH7	0.50	35Z4GT	0.82	DD4	0.90
1S5	0.40	6BZ6	0.57	6SG7	0.52	12S17	0.60	35Z5GT	0.90	DF33	0.78
1T4	0.30	6C4	0.47	6SH7	0.55	12S17	0.64	42	1.90	DF91	0.30
1U4	0.70	6CG5	0.59	6SJ7	0.64	12SN7GT	0.64	50R5	1.00	DF96	0.65
1U5	0.88	6C6	0.47	6SK7GT	0.52	12SQ7	0.75	50C5	0.70	DF98	0.50
2D21	0.90	6C9	2.00	6SQ7GT	0.50	12SQ7GT	0.50	50CD6G	1.46	DH76	0.50
2GK5	0.75	6C10	0.80	6U4GT	0.82	12SR7	0.78	50EH5	0.88	DH77	0.53
2X2	0.70	6CB6A	0.47	6U7G	0.55	12SR7	0.78	50L6GT	1.00	DH81	0.88
3A4	0.60	6C12	0.40	6V6G	0.30	14H7	0.64	72	2.00	DK32	0.80
3B7	0.53	6C17	2.34	6V6GT	0.53	14T7	1.10	77	0.70	DK40	0.82
3D6	0.47	6CD8G	1.00	6X4	0.47	18	1.17	85A2	0.75	DK91	0.50
3Q4	0.85	6CG8A	0.88	6XS5GT	0.50	19A05	0.65	85A3	0.75	DK92	1.15
3Q5GT	0.70	6CL6	0.78	6Y8G	0.94	19B6G	0.65	90AG	2.83	DK96	0.70
3S4	0.47	6CL8A	0.94	6Y7G	1.17	19C7	1.17	90CC	2.81	DL32	0.47
3V4	0.52	6CM7	0.98	7A7	1.00	19G6	7.00	90CV	2.81	DL94	0.62
4C86	0.75	6CU5	0.88	7B6	0.88	19H1	4.00	90C1	0.88	DL96	0.64
5C68	0.75	6CW4	1.17	7B7	0.82	20D1	0.90	150B2	1.00	DM70	0.80
5R4G	0.94	6D3	0.75	7F8	1.76	20D4	2.34	2155G	0.58	DM71	1.76
5T4	0.47	6DE7	0.88	7H7	0.88	20F2	0.88	301	1.17	DW4/350	1.17
5U4G	0.50	6DT8A	0.88	7H7	2.00	20L1	1.29	302	1.17	ECL86	0.47
5V4G	0.50	6E4G	0.88	7A7	1.76	20P1	1.90	303	1.17	EF22	1.17
5Y3GT	0.55	6E5	1.17	7Y4	0.80	20P3	1.90	305	1.17	EF80	0.47
5Z3	0.88	6F1	0.90	7Z4	0.80	20P4	1.17	807	1.17	EF83C	2.57
6A2G	0.55	6F6G	0.90	9B6W	0.88	20P5	1.50	956	0.60	EF87	2.20
5Z4GT	0.55	6F12	0.50	9D7	0.70	25A6G	0.70	1821	1.17	EF87	2.20
6B0L2	0.80	6F13	0.90	10C2	0.76	25L6G	0.70	4033X	7.61	EF88CC	1.20
6B3G	1.46	6F14	0.98	10D1	0.82	25Y5	0.80	5702	1.20	EF88	1.40
6AC7	0.60	6F15	0.76	10D2	0.88	25Y5G	0.60	5783	1.76	EF89	0.60
6AG5	0.35	6F18	0.84	10F1	0.88	25Z4G	0.50	6057	1.00	EF89	0.60
6AC6	0.80	6F23	0.90	10F3	1.17	25Z5	0.75	6060	1.00	EF89	0.60
6AJ5	0.76	6F24	1.00	10F9	0.70	25Z6G	0.80	6067	1.00	EF91	0.50
6AJ8	0.40	6F25	1.17	10F18	0.60	28D7	2.00	7193	0.62	EF92	0.60
6AK5	0.47	6F26	0.90	10L14	0.53	30A5	0.78	7475	1.17	EF93	0.41
6AK6	0.70	6F28	0.78	10L11	0.82	30C1	0.47	9003	0.50	EF94	0.40
6AK8	0.45	6F32	0.70	10L12	0.45	30C15	0.80	9006	0.50	EABCB80	0.45
6AL5	0.33	6G6G	0.60	10P13	0.88	30C17	0.85	A1834	1.17	EAC91	0.45
6AMB8A	0.70	6G8BA	0.88	10P14	2.34	30C18	0.85	A2134	3.00	EAF42	0.88
6AN8	0.82	6GK5	0.78	10P18	0.40	30P5	0.75	A3042	0.60	EAF801	0.80
6AG5	0.53	6G07	0.88	12A6	0.50	30FL1	1.10	AC2PEN1	1.17	EB34	0.35
6AG6	0.47	6H8GT	0.29	12A6C	0.90	30FL2	1.10	AC2PEN2	1.00	EB91	0.25
6AR5	0.80	6J5GT	0.53	12AD6	0.90	30FL12	1.05	AC3PEN	1.00	EB91	0.25
6AR6	1.17	6J6	0.35	12AE6	0.90	30FL13	0.64	AC6/PEN	0.80	EB91	0.25
6AT7	0.53	6J7(M)	0.65	12A7H	0.47	30FL14	0.82	AC/PEN(7)	0.60	EB91	0.25
6AU6	0.40	6J8A	0.88	12AUB	0.53	30L15	0.82	AC/TH1	1.00	EBP80	0.40
6AV6	0.53	6K7G	0.35	12AUG	0.30	30L17	0.78	AL80	1.17	EBP89	0.40
6AW8A	0.90	6K9G	0.53	12AV6	0.50	30P4MR	0.80	ARP3	0.80	EBL21	2.34
6AX4	0.88	6L1	2.34	12AX7	0.30	30P12	0.90	ATP4	0.50	EL83	0.70
6B8G	0.35	6L8G	0.88	12A7Y	0.94	30P19	0.80	AZ1	0.50	EL84	0.38
6BA6	0.41	6L7(M)	0.59	12BA6	0.53	30P19	0.80				


EL86	0.60	PC95	0.70	PY88	0.47	U18/20	1.17	2N404	0.23	AF186	0.71	GDB	0.28	OC43	1.52
EL90	0.53	PC97	0.42	PY301	0.50	U19	4.00	2N966	0.88	AF239	0.49	GDR	0.26	OC44	1.13
EL360	1.90	PC900	0.30	PY500	1.11	U22	0.85	2N1756	0.64	ASY27	0.55	GD11	0.26	OC45	0.14
EL506	1.20	PC884	0.40	PY500A	1.11	U25	0.70	2N2147	1.10	ASY28	0.42	GD12	0.26	OC46	0.20
EL150	2.50	PC855	0.50	PY800	0.45	U26	0.65	2N2257	0.29	ASY29	0.64	GD14	0.64	OC65	1.45
EM80	0.53	PC858	0.65	PY801	0.45	U31	0.50	2N289A	0.18	BA102	0.58	GD17	0.52	OC70	0.16
EM81	0.78	PC889	0.50	PZ30	0.50	U33	1.75	2N2613	0.50	BA115	0.84	GD16	0.26	OC71	1.14
EM83	0.64	PC1189	0.60	QP21	1.10	U35	1.75	2N3053	0.42	BA116	0.23	GET113	0.26	OC72	1.14
EM84	0.47	PC805	0.82	QQV03/10	U37	2.03	2N3121	3.22	BA129	0.16	GET118	0.26	OC74	0.29	
EM85	1.20	PC806	0.76	QV03/12	1.76	U78	0.47	2N3703	0.25	BA130	0.13	GET119	0.33	OC75	0.14
EM87	1.10	PCF80	0.47	QV04/7	1.17	U81	0.80	2N3709	0.26	BA133	0.20	GET173	0.49	OC76	0.20
EM9M803	0.50	PCF82	0.50	QV04/10	1.00	U82	0.50	2N3710	0.26	BA135	0.50	GET387	0.55	OC77	0.35
EV51	2.50	PCF84	0.70	QV04/15	U50	0.55	2N3988	0.64	BC112	0.64	GET392	0.26	OC78	0.20	
EV81	0.50	PCF86	0.50	QV03/12	1.76	U78	0.47	2S232	0.64	BCY33	0.29	GET373	0.20	OC78D	0.20
EV83	0.70	PCF200	1.00	QV03/12	1.76	U78	0.47	AA119	0.20	BCY34	0.29	GET382	0.49	OC79	0.52
EV84	0.82	PCF201	1.05	QV06/20	3.50	U153	0.40	AA120	0.20	BCY38	0.29	GET387	0.29	OC81	0.14
EV87/8	0.50	PCF800	0.82	R104	0.50	U191	0.50	AA129	0.20	BCY39	0.33	GET389	0.29	OC81D	0.14
EV91	0.50	PCF82	0.50	R17	1.00	U193	0.47	AA213	0.23	BC107	0.16	GET390	0.29	OC82	0.14
EV93	0.50	PCF85	0.85	R18	0.92	U251	0.94	AC113	0.33	BC109	0.16	GET396	0.29	OC83	0.26
EZ40	0.55	PCF86	0.80	R19	0.75	U281	0.75	AC114	0.52	BC113	0.33	GET398	0.29	OC84	0.31
EZ41	0.55	PCF808	0.82	R20	0.85	U282	0.70	AC126	0.16	BC115	0.20	GET399	0.29	OC23	0.29
EZ42	0.80	PCF810	0.82	R21	0.85	U291	0.94	AC127	0.22	BC116	0.33	GET399	0.29	OC140	1.23
EZ81	0.35	PCF830	1.00	RK34	1.00	U301	0.85	AC128	0.26	BC118	0.29	GET396	0.64	OC169	0.29
EZ90	0.47	PCL83	0.50	SP13C	0.74	U329	0.94	AC132	0.26	BCZ11	0.49	GET395	0.42	OC172	0.46
FC4	1.00	PCL84	0.50	TH4B	1.00	U339	0.50	AC154	0.33	BF154	0.33	GET395	0.42	OC172	0.46
FW4/500	1.17	PCL86	0.35	TH233	1.00	U381	0.50	AC156	0.26	BF158	0.23	G13	0.33	OC201	0.59
FW4/800	1.17	PCL88	1.29	TP220	1.00	U403	0.90	AC157	0.33	BF159	0.33	MT1	0.20	OC202	0.55
FW4/800	1.17	PCL88	1.29	TP220	1.00	U403	0.90	AC165	0.33	BF163	0.26	MAT100	0.50	OC203	0.39
FW4/800	1.17	PC180	1.11	TP22	1.00	U404	0.75	AC166	0.33	BF173	0.49	MAT101	0.55	OC204	0.39
FW4/800	1.17	PC185	0.70	UAB30	0.47	U402	0.75	AC167	0.77	BF180	0.30	MAT120	0.50	OC205	0.55
FW4/800	1.17	PC185	0.70	UAB30	0.47	U402	0.75	AC168	0.40	BF182	0.52	OA9	0.16	OC206	1.17
FW4/800	1.17	PC185	0.70	UAB30	0.47	U402	0.75	AC169	0.42	BF185	0.52	OA10	0.55	OC212	0.52
FW4/800	1.17	PC185	0.70	UAB30	0.47	U402	0.75	AC176	0.71	BF194	0.20	OA47	0.13	ORP12	0.66
FW4/800	1.17	PC185	0.70	UAB30	0.47	U402	0.75	AC177	0.26	BF195	0.20	OA70	0.20	S8M1	0.33
FW4/800	1.17	PC185	0.70	UAB30	0.47	U402	0.75	AC177	0.26						




# ELECTRONIC BROKERS

## OSCILLOSCOPES & PLUGS INS

HEWLETT PACKARD

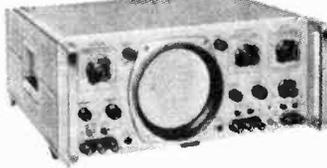

Model 130C 200µV/cm Oscilloscope. This scope is a versatile all purpose instrument for laboratory, production line, industrial process measurements and medical applications. The outputs of rf detectors, strain gauges, transducers, and other low level devices may be viewed directly without preamplification. The Model 130C is easy to operate even by inexperienced personnel. Specification: Time Base: Range — 1 µs/cm to 5 s/cm, 21 ranges in a 1,2,5 sequence, accuracy ± 3%, vernier provides continuous adjustment between steps and extends the 5 s/cm step to at least 12.5 s/cm. Automatic triggering (baseline displayed in the absence of an input signal). Vertical and horizontal amplifiers. Bandwidth: d.c. coupled, dc to 500 KHz; ac coupled (input), 2 Hz to 500 KHz; ac coupled (amplifier), 25 Hz to 500 KHz at 0.2 mV/cm deflection factor. **£175**  
Model 185B Sampling Scope DC — 3.5 GHz. **£300**  
**ROBAND** R050 DC — 25 MHz c/w. 5c Plug Dual Trace. Rise Time 13 n secs 50mV/cm min sensitivity, 5" display. Superb condition. **£220**

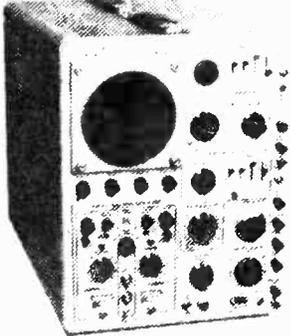

TEKTRONIX

MAIN FRAMES ONLY

546 **£275**  
547 **£325**

Plug ins available include:  
TA1, 1A2, CA, 90, 86, B, D, GL, M, N, Q, R, S, T, P.O.A. 661 c/w with plug ins **£300**

EQUIPMENT

Dual Beam Scope D31R DC-6MHz **£75**  
DM — 64 storage) **£320**  
**SOLARTRON** CD 1400 (main frame) with plug ins, price dependant on choice **£165-£180**  
Types available cx1441, cx1443, cx1444, DC-15 MHz, 5" Display. Portable. Good condition.

## HEATHKIT

10-12µ Scope Single Beam 50mV/cm DC — 4.5 MHz 5" Tube. Assembled Refurbished.

OUR PRICE **£49.50**  
**HURRY . . . Only a few left in stock!**


## INSULATION TESTERS

EVERSHED & VIGNOLES

Circuit Tester Ohmmeter 0-3 ohms 0-39 ohms **£18**  
Circuit Tester Ohmmeter 0-1000 ohms, 100-200 kohms **£18**  
Megger Series II 250V **£12**  
Megger Series III Mk. 3 250V **£20**  
Megger 250V **£20**

## SIGNAL SOURCES

FM AM SIGNAL-GENERATOR TYPE 202H

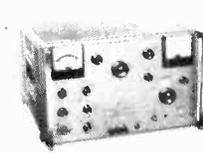


This superb generator in grade one condition, F.M., A.M., C.W. & pulse coverage 54 to 216MHz. Used to testing and calibration of

F.M. receiving systems, V.H.F., T.V., Mobile and general Communications. Freq. range 54-216MHz + 2 Bands. R.F. stability 0.01%. R.F. output 0.1 µV-0.2V. V.S. W.R. 1.2. Signal to noise ratio 50dB below 10KHz. Dimensions 16 3/4" x 10 1/4" x 18 3/4".

PRICE NEW OVER **£1,000!**

OUR PRICE **£495**

MARCONI INTS.

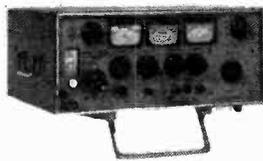

Phase/AM Signal Generator TF 2003. 0.4-12 MHz. Bargain price — super condition **£150**

FM/AM Signal Generators

TF995A **£185**  
TF995A/2 **£225**  
TF995A/2M **£385**

FM/AM Signal Generator TF 995A/3S. 1.5 Mhz-220 MHz. 2µ V-200mV. Superb condition.

A.M. SIGNAL GENERATOR

TF 801 B/3S **£125**  
TF 801D/1s **£350-£600**  
TF 801D/1 **£350-£450**

RC OSCILLATOR TF 1101 P.O.A.

R.C. OSCILLATOR TF 1370 **£90**

LEVELL Decade Oscillator TG 66A (new condition) **£40**

ADVANCE A.F. Generator J2B **£45**

AIRMEC H.F. Sig. Gen. 201 **£75-£115**

# END OF YEAR SALE!

The following equipment is being sold off cheap due to our shortage of storage space.

## BARGAINS GALORE!

These devices listed are sold as received and without our normal guarantee. Purchasers will have to collect from our premises between 9 a.m. and 5.30 p.m. (weekdays only).

**SOLARTRON** Solarscope CD 513 **£40**

**ADVANCE** Voltmeter VM 80 **£25**

Superb mechanical condition

**MARCONI** Decade Potentiometer TF 221 **£12**

**MARCONI** Sig. Gen. CT320 **£40**

35 KHz - 18 MHz. 1 only **£40**

**MARCONI** Distortion Factor Meter TF 142F **£40**

STC Push Button Attenuators 74600 series **£9** each

A.E.I. Miniature Scope CT 52 **£19**

**MARCONI** Scope TF 1330 **£34**

**ADVANCE** Recorder Calibrator HC 20 **£20**

**MARCONI** Sig. Gen. TF 801A **£15**

**HEWLETT PACKARD** Microwave Power Meter 430C Without Bolometers **£18**

**MARCONI** Variable Attenuator TF 338B **£12**

LEVELL AC Voltmeter TM 2B **£8**

**MARCONI** VHF Alignment Scope TF 1104 **£20**

**SOLARTRON** Power Supply SRS 151 **£8**

**SOLARTRON** Millivoltmeter VF 252 **£12.50**

Memory Planes **50p** each

# RECENTLY OUT!


The most Comprehensive Test Equipment Catalogue ever compiled in the U.K.

FREE COPIES now available for U.K. companies. Please apply on letter-headed paper.

Private individuals please remit 50p towards cost & carriage.

Overseas Customers please remit £1 for air-mailed copy.

## COMPONENTS

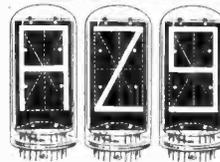


**NIXIE TUBES** B 5853 ST 0.9 Numeric 1 2" high density 0.510" 2 independently operable decimal points in tube. 1-25 **£1** each  
26-100 **90p** each  
100+ **80p** each  
Large quantities in stock.

B 7971 ALPHA NUMERIC 0.9 and all letters of the alphabet. 4 1/2" high x 2.065" wide. Display 2 1/2" high. Can be read at distances of 25 to 100 feet **99p** each  
Bases for Tube **60p**  
Please add VAT at 8% P&P 40p

MAGNETIC DEVICES

Cam Timer Type 8303B/8H/3C6A/240. Cyclic Time 8Hrs. Division Value 8Mins. Complete with Crouzet Motor 230V 3 Relay positions at 10A 250V Rating **£4** ea. + 75p P&P

## TELEPHONE TEST EQUIPMENT

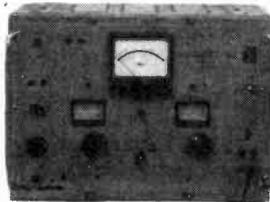

Siemens Level Meter 3D 335 10KHz-17MHz. Complete system by Siemens comprising: 3W 518 Level Oscillator, 3D 335 Level Meter, 3W 933 Sweep Attachment, 3D 346 Screen Level Tracing Receiver. P.O.A.  
Siemens Level Meter 3D 332. 0.3-1200KHz. Level Oscillator 3W 29. 0.3-1200KHz P.O.A.

S.T.C.

Octave Filter 74143A. 37.5-12,800Hz. For analysing noise and interference on comms systems, particularly useful with 74142 psophometer P.O.A.

Selective level Measuring Set 74184B P.O.A.

60-1364KHz P.O.A.

Measuring Set 74831A P.O.A.


A.T.&E.

Telegraph Distortion Measuring Set. Various types 5BV, 5BV3 68V 6A P.O.A.

MURPHY RADIO

Receiver VHF field strength RX 506 & interference measuring set c/w Power Unit P.O.A.

## MISCELLANEOUS

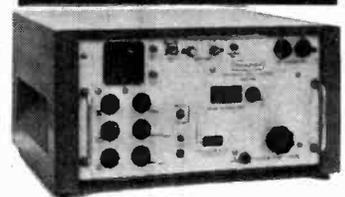

Transfer Oscillator Type 7580Hb Beckman. DC-15GHz with counter, 7.5MHz-15GHz without counter. Sensitivity 100mV (R.M.S.) **£350**

**MARCONI** Distortion Factor Meter TF 142F. Fundamental Freq. Range 100Hz-8KHz. Dist. measurement ranges 0-5% & 0-50% **£60**

Portable Recener Tester TF 888/3. 7DKHz-70MHz. Xtal check 500KHz & 5MHz. 1KHz A.F. Oscillator, A.F. Power 10mW, 100mW & 1W **£69**

Wave Analyser TF 455E **£95**

Noise Generator TF 1301. 200-1700 MHz **£60**

Amplitude Modulator TF 1102. Basic Carrier Frequency Range 100KHz-300MHz/500MHz CW or FM output of any conventional signal generator can be amplitude modulated, including sine waves, square waves pulses, picture signals **£25**

**SOLARTRON** Resolved Component Indicator VP 253.3 P.O.A.

Low Freq. Decade Oscillator OS 103.3 P.O.A.

**EKCO INSTS** (Nucleonics) Ratemeter N 600B P.O.A.

S.T.C. Level Measuring Set 74307A P.O.A.

**RADIOMETER** 1MHz Capacitance Comparator Type CMB 11bS2 P.O.A.

**BELL** Gaussmeter 120 P.O.A.

**HEWLETT PACKARD** Microwave Link Analyser 3701/02/03 **£2000**

Distortion Analyser 380C P.O.A.

Ratio Meter 416B P.O.A.

Inverter 207H (for use with 202H and J Generators) P.O.A.

**MUIRHEAD** Facsimile Transmitter Receiver Type 900. Easily convertible to receive weather pictures from satellite systems **£850**

**SAVAGE** Amplifier Mark II Star Model 1KM2Z, 1 KW output. Freq. 50-10 KHz. Good condition **£1650**

**WAYNE KERR** Video Noise Level Meter M 131 **£75**

B.P.L. Component Comparator CZ457/5. P.O.A.

**AIRMEC** Modulation Meter 210 **£75**

Modulation Meter 210A **£135**

**HEWLETT PACKARD** Time Domain Reflectometer 140A + 1415A **£750**

Trolley for 175A scope **£50**

Digital Recorder 561B **£150**

**MARCONI** Blank & Sync. Mixer TF 2908 **£95**

VHF/UHF Probe TM 9650 (New) **£30**

**TEKTRONIX** Scope Camera C-13 P.O.A.

**MUIRHEAD** Various Pametrada Analysers P.O.A.

**SOLARTRON** Analogue Tutor TY 1351. Ask for details P.O.A.

AC/DC Converter LM 1219 **£200**

P.R.D. Noise Generator 904A P.O.A.

**TELEMAX-SOUTHERN** TD1 Freq. Meter/Generator. 10KHz-3000 MHz P.O.A.

## POTENTIOMETERS

Manuf.	Type	Turns	Value	Price
Relcon	0705/1001/A	5	100 ohm	<b>£1.75</b>
Relcon	0705/05/F11	5	200 ohm	<b>£1.75</b>
Beckman	7246/5019	10	50 ohm	<b>£2.00</b>
Bourns	35005-2-500	10	50 ohm	<b>£1.95</b>
Bourns	35005	10	1K	<b>£2.00</b>
Beckman	A/S303	10	5K	<b>£1.00</b>
Beckman	72212/5	10	10K	<b>£2.00</b>
Relcon	0710-1-1-001A	10	10K	<b>£2.00</b>
Beckman	A	10	20K	<b>£3.00</b>
Borg	KS1302512	10	20K	<b>£2.00</b>
Beckman	7223	10	50K	<b>£3.50</b>

WW — 099 FOR FURTHER DETAILS

# the test equipment people

Come and visit Europe's first Electronic Instrumentation Centre

49-53 Pancras Road  
London NW1 2QB  
Tel: 01-837 7781

Next to KING'S CROSS ST. PANCRAS



## SELF-SCAN

PANEL DISPLAY  
Model SSD1000-0030

DIRECT VISUAL PRESENTATION  
OF ALPHA-NUMERIC DATA


LIMITED QUANTITY ONLY

### TYPICAL APPLICATIONS:

- Read-out of Operator Instructions and Results from digitally controlled machines, and test-equipment complexes.
- Display of specific data inserted into pre-programmed messages. Examples include the presentation of Commercial information, such as Share Prices and Exchange Rates. Industrial uses may include Stock Control and Stores Movements.
- Presentation of key information where the full message writing capability of a V.D.U. is not warranted, or where space is at a premium.

Each panel is a self-contained package, providing 16 or 18 display positions, each of which may be instructed by a 6-bit coded signal to display one of 64 pre-programmed characters as a 5 X 7 dot-matrix, formed by special gas discharge units. Alternatively, other characters may be synthesised by the application of the appropriate signals. Each character is 0.4 inches high providing a bright image, visible over a wide viewing angle.

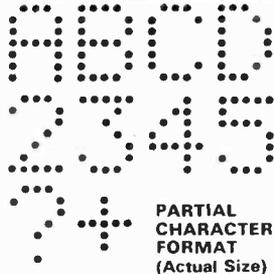Full applications data is available, giving all necessary information.



PARTIAL CHARACTER FORMAT (Actual Size)

**Abridged Specification**  
Size: 8 1/2" x 2 1/4" x 1 1/2" approx.  
Input signals: 6-bit data, clock, reset, etc.  
Power Supplies: +5v, -12v & +250v.  
Auxiliary data input available to permit generation of additional symbols, etc.  
Internal repertoire: A to Z, 1 to 0, @, 0, 7, /, %, =, -, ., etc.

Brand New . . . . . £60  
Secondhand . . . . . £50  
P&P . . . . . £2



## DIGITAL TACHOMETER

Measures RPM instantly

TO MEASURE RPM

- Motors ● Gears ● Fans ● Mixers  
Turbines ● Drills ● Centrifuges  
Grinders ● Wheels ● Pumps  
Pulleys ● Anything that rotates


### SPECIFICATION

DIGITS	4 1/2
RANGE	1 to 19999
INDICATOR	Red Luminescent
BATTERIES	4 "A" cells
ACCESSORIES	2 Rubber tips and carrying case
MEASURING TIME	1 Second
ON-OFF SWITCH	Push Button
ACCURACY	0.1 of 1% ± 1 Digit
WEIGHT	Approx. 15 oz.

£99.50 P&P £1

## STROBETTE STROBOSCOPE - TACHOMETER

Two Units In One

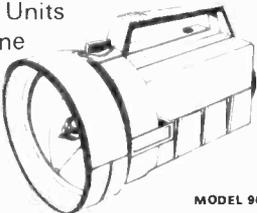

MODEL 964

### SOME SPECIFIC APPLICATIONS

- To check and analyze motion while designing data processing units.
- To check register in printing presses.
- To check balance in balancing machines.
- To check speed of motors, gear reducers, etc.
- To check speed of pulleys, gears, fans, shafts or anything that rotates over 200 RPM.
- To observe motion of packages, bottles, cans, envelopes, etc. while they are being manufactured.
- To observe belt slippage.
- To demonstrate strobe action to students.

**SPECIFICATIONS**  
STROBOSCOPIC FLASH RATE—200 to 6,000 flashes per minute  
TACHOMETER SPEED RATE—200 to 6,000 R.P.M.  
ACCURACY—3% better  
CALIBRATION—At 3,600 F.P.M. against any known synchronous speed—7200, 3600, 1800, 1200, 900 RPM, etc.  
CIRCUITRY—100% solid state  
FLASH DURATION—Approximately 10 to 25 microseconds  
FLASHLIGHT COLOR—Xenon white 6,500 K  
FLASH ENERGY—40 Watts-second (Joules)  
DUTY CYCLE—Below 1,000 FPM = 30 minutes  
1,000 to 3,600 FPM = 1/2 duty cycle  
3,600 FPM and above = 1/4 duty cycle  
BEAM ANGLE—80°

**PHYSICAL**—High impact case. Plastic lens. Mirror type reflector.  
SIZE—3" x 3" x 7" with 4" diameter reflector  
WEIGHT—27oz (76 Kg). Shipping weight 4 lb. (1.8 Kg)  
TRIPOD MOUNTING—Built-in 1/4-20 thread tripod socket.  
POWER—220 VOLTS 50/60 Hz 22 watts.

FANTASTIC VALUE  
£49.50



Only £89.50

## "TOUCHLESS" RETRO-REFLECTIVE TACHOMETER

### FEATURES


- Reads RPM from as far as 24" away!
- Four ranges: 0-1,000, 3,000, 10,000, 30,000 RPM.
- Instant field calibration
- Reads low or high speed on any type of machinery
- Battery powered—built-in voltage checker
- "Touchless" (no torque loss) measurements.
- Direct reading: mirror type scale
- Hand portable (only 32 oz.) (0.9 Kg)
- Accuracy: 1 1/2% of full scale
- Aluminum case—baked enamel finish
- Reads on marked shafts as small as 1/16" diameter
- Marking tape provided
- Complete solid-state circuitry
- Push-button reading
- Hidden probe cable, extends to 24" (60cm).

### SPECIFICATIONS

Photocell: Photo transistor. Lamp: GE No. 222X  
Batteries: One 5.4 V type TR-134R. Except Model B. 912  
Accuracy: 1 1/2% of full scale. Meter: Shock-proof movement, large clear-face dial.  
Calibration: From any fluorescent light 50 to 60 cycles.  
Dimensions: 5 1/2" (130.0 mm) wide, 7 1/2" (190.0 mm) high, 2 1/2" (63.5 mm) deep.

Carrying case . . . . . £12.50

## MULTIMETERS

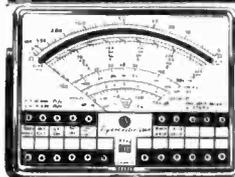

**SUPER-TESTER 680R ICE**  
20,000 Ohm per Volt sensitivity. Fully screened against external magnetic fields.

Scale width and small case dimensions (128 x 95 x 32mm). Accuracy and stability (1% in D.C., 2% in A.C.) of indicated reading. Simplicity and ease of use and readability. Full ranges of accessories. 1000 times overload. Printed Circuit board is removable without desoldering. More ranges than any other meter. Ask for free catalogue . . . . . £18.50

## FANTASTIC NEW MICROTEST 80

MEASURES ONLY

90 x 70 x 18mm  
Electronic zero Ω

Amazing Value at £11.95  
8 fields of measurement and 40 ranges

PRINTED CIRCUIT BOARD IS REMOVABLE WITHOUT SOLDERING


Volts d.c. 6 ranges: 100mV, 2V, 10V, 50V, 200V, 1,000V (20kΩ/V) 2% precision on d.c. and a.c.  
Volts a.c. 5 ranges: 1.5, 10V, 50V, 250V, 1,000V (4kΩ/V)  
Amp. d.c. 6 ranges: 50μA, 500μA, 5mA, 50mA, 500mA, 5A  
Amp. a.c. 5 ranges: 250μA, 2.5mA, 25mA, 250mA, 2.5A  
Ohms 4 ranges: Low Ω, Ω x 1, Ω x 10, Ω x 100 (from 1/10 Ω to 5MΩ)  
V Output 5 ranges: 1.5V, 10V, 50V, 250V, 1,000V  
Decibels 5 ranges: +6dB, +22dB, +36dB, +50dB, +62dB.

Capacity 4 ranges: 25μF, 250μF, 2,500μF, 25,000μF

Accessories (extra) available to convert Microtest 80 & SuperTester 680R into following: SIGNAL INJECTOR, GAUSS METER, ELECTRONIC VOLTMETER, AMPER-CLAMP, TRANSISTOR TESTER, TEMPERATURE PROBE, PHASE SEQUENCE INDICATOR—Send for details
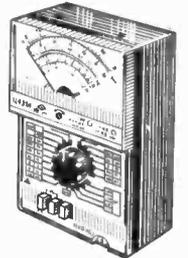
### MORE RANGES FOR LESS MONEY!

AC/DC Multi-meter type U4324. A-DC 0.06-3A — 6 Ranges. A-AC 0.3A — 5 Ranges. V-DC 0.6-1200V — 9 Ranges. V-AC 3.900V — 8 Ranges. Freq. In the range of 45 to 20kHz Resistance 500 ohm to 5 Mohm — 5 Ranges. Decibel: -10 to +12dB. Accuracy: ± 2.5%



DC ±4% AC Dimensions: 167 x 98 x 63mm  
Only £9.50

All above Multimeters (except AVO) are brand new.

POST & PACKING 50p

Shown on these pages are just a few samples of our huge stock. If the item you require is not shown please give us a ring.



# ELECTRONIC BROKERS LIMITED

Carriage and packing charge extra on all items unless otherwise stated.

Please note: All instruments offered are secondhand and tested and guaranteed 12 months unless otherwise stated.

ADD 8% VAT TO ALL PRICES

FOR FURTHER DETAILS

# Samson's

(ELECTRONICS) LTD.

9 & 10 CHAPEL ST., LONDON, N.W.1  
01-723 7851 01-262 5125  
ADJACENT TO EDGWARE ROAD MET. LINE STATION

**CURRENT RANGE OF NEW L.T. TRANSFORMERS FULLY SHROUDED TERMINAL BLOCK CONNECTIONS ALL PRIMARIES 220/240v**

Type	Sec. Taps	Amps	Price	Postage
1A	23-33-40-50v	15	£15.50	£1.00
1B	25-33-40-50v	10	£13.25	£1.00
1C	25-33-40-50v	6	£9.50	85p
1D	25-33-40-50v	3	£8.25	85p
2A	4-16-24-32v	2	£11.25	£1.00
2B	4-16-24-32v	8	£8.75	85p
2C	4-16-24-32v	4	£5.25	65p
2D	4-16-24-32v	2	£3.85	60p
3A	24-30-36v	10	£10.00	85p
3B	24-30-36v	5	£8.25	65p
3C	24-30-36v	2	£3.85	60p
4A	12-20-24v	20	£13.25	£1.00
4B	12-20-24v	10	£8.25	85p
4C	12-20-24v	5	£5.25	65p
5A	3-12-18v	2D	£11.25	£1.00
5B	3-12-18v	10	£7.75	85p
5C	3-12-18v	5	£4.95	65p
6A	48-56-60v	2	£4.95	65p
6B	48-56-60v	1	£3.85	60p
7A	6-12v	20	£8.50	65p
7B	6-12v	10	£5.25	65p
7C	6-12v	5	£3.85	60p
8A	17-32v	8	£8.50	85p
9A	12-24v	1	£2.70	50p
10A	9-15v	2	£2.70	50p
11A	8-0-8v	2	£2.70	50p

**HEAVY DUTY UNSHROUDED TYPES 9 INCH FLYING LEADS ALL PRIMARIES 240v**

Type No.	Sec. Volt	Tap	Amps	Price	Carr.
1	24-30-36	20	20	£15.75	£1.25
2	12-20-24	30	30	£15.75	£1.25
3	3-12-18	30	30	£15.75	£1.25
4	6-12	50	50	£15.75	£1.25

**CENTRE TAPPED L.T. TRANSFORMERS**  
Fully shrouded. Terminal block connections Pr. 220-240v. Screen. Tapped sec. 30-25-0-25-30v. 2 amps £4.95, carr. 60p. 35-25-0-25-35v 5 amps £9.95, carr. 85p. 28-0-28v 10a £12.50, carr. £1

PLEASE ADD 8% TO ALL ORDERS INC. CARR.

**UNIMAX SEQUENTIAL MICRO SWITCHES**  
2 pole CO 15 amp contacts. 2nd pole actuates after 1st pole. Leaf roller action. 75p. P.P. 25p.

**A.E.I. 240AC CONTACTORS**  
20 amp CONTACTS  
Type 0659. 3 makes. 1 break. Type 0658 2M. 2B. £1.25, P.P. 25p. 110v AC types Type 0651. 3M. 1B. Type 0654. 2M. 2B. Type 0653. 4M. £1.00, P.P. 25p.

**RELAY CONTROL CO.** American Miniature relays 6v. DC. 1 CO contact. Size 1 1/4 x 1 1/4 x 1/2 ins 35p, post 10p.

**MINIATURE RELAYS**  
**ITT, PLESSEY, VARLEY TYPES**  
280Q 12-15DC 4CO. 60p. 430Q 15-24v DC 2CO. 50p. 1250Q 4 CO. 24-30v DC. 50p. 2500Q 35-40v DC. 50p. 5000Q 40-60v DC. 2CO. 50p. Postage 15p each.

**G.P.O. RELAYS**  
3000 type. 100Q 1 25 amp. make contact 60p. 2000+1300 1 normal CO 40p. 75Q 3M 1B. 1CO normal contacts 40p. Post on all relays 10p.  
Diamond H relays type BR115AIT-3C. 150Q 24v DC. Sealed type. 75p, P.P. 10p.

**ITT LEVER SWITCHES**  
Type 601 AAO 72 42 4 CO contacts. overall size 1 1/4 x 2 1/2 ins. White lever gold flash contacts. 60p. Three for £1.50, P.P. 20p.

**PLESSEY MINIATURE MICRO SWITCHES**  
Type LIC 7134. One CO one break. Gold flash contacts. Size 7/8 x 3/4 x 1/2 ins. Three for 50p. P.P. 20p.

**SANGANO SYNCHRONOUS A.C. 240v MOTOR TYPE 7**  
4 rev. per hour. Size 1 1/4 plus 1/2 spindle. 1 1/2 inch dia. £1.25, P.P. 50p.

**GENTS ALARM BELLS**  
6 volt DC 6 inch dia. Gong. Overall size 4 1/2 x 6 inches. £3.50, P.P. 75p.

**DIAMOND H** Double pole toggle switches type 712 250v 20 amps. centre single hole fixing. 80p. P.P. 15p.

**BENSON SOLENOIDS**  
AC 240v 25% duty. Approx. 2 in. dia. 1/2 in. pull. Size 2 1/2 x 1 1/2 ins. Res. 350Q 75p. p.p. 25p.

**L.T. SMOOTHING CHOKES**  
C core type 15 M/H 3.8A £2.00, P.P. 50p. 50 M/H 2.5A £2.00, P.P. 50p. 12 M/H 7A £3.00, P.P. 60p. 140 M/H 1A £3.50, P.P. 85p. 10 M/H 25A £8.75, Carr. £1.25. Open type top panel connections. 4.8 m/H 10A £3.00, P.P. 50p. Potted type 100 M/H 2A £3.50, P.P. 75p. C core swinging types 7.5 M/H 6A 7.5 M/H 0.5A £3.95, P.P. 75p. 10 M/H 4A-100 M/H 0.5A £3.95, P.P. 50p. 50 M/H 5A-100 M/H 0.5A £2.75, P.P. 50p.

**H.T. SMOOTHING CHOKES**  
Core types 10H 350M/A £3.50, carr. £1.20H 180M/A £2.50, carr. 75p. 5H 180M/A £1.75, P.P. 50p. Potted types 15H 180M/A £2.00, carr. 75p. 10H 250M/A £2.00, carr. 75p. 20H 40M/A 75p. top 25p. Parmeko Potted type 10H 180M/A £2.00, carr. 75p.

**AMOS 'C' CORE CHOKES**  
10 M/H 25 amps. £8.75, carr. £1.00.

**HOWELLS 'C' CORE TRANSFORMERS**  
Pr. 200-220v. screen. Sec. 70-0-70v. 10 amp. table top connections. Size 7x7 1/2 inches. £15.00, carr. £2.00. Pr. 220-240v. Sec. 18-0-18v. 12.5 amps conservatively rated. Table top connections £10.00, carr. £2.00.

**GEC L.T. TRANSFORMERS**  
Pr. 220-240v. Sec. tapped 51-61-65-67-69v. 10A Unshrouded terminal block connections. £8.75, carr. £1.25. Pr. 220-240v. Sec. tapped 58-63-69-74v. 3A. £3.75, carr. 75p.

**WODEN MULTI-TAPPED L.T. TRANSFORMERS**  
Pr. 200-220-240v secs. All separate windings 31v 7A. 26v 5A. 16v 4A. 16v 4A. 25v 2A. 25v 2A open frame type. Table top connections. £8.50, carr. £1.50.

**CRESHAM MULTI-TAPPED L.T. TRANSFORMERS**  
Pr. 200-220-240v Sec. No. 1. 22.5-25-28v 5A. No. 2 26v 2.5A. No. 3 16v 1A twice. No. 4 10v 1A twice. No. 5 6.3v 2A. No. 6 145-0-145v 200 M/A C core type table top connections. Brand new.

**GRESHAM E.H.T. TRANSFORMERS**  
Pr. 240v. 2500 M/A. 6.3v 1.5A. Table top connections. Size 5 1/4 x 3 1/4 ins. £3.00, carr. 60p.

**PARMEKO L.T. TRANSFORMERS**  
Open types. Pr. 110-220-240v. Sec. 30v 5.5A and 12v 2A. Table top connections. £4.95, P.P. 95p. Pr. 240v. Sec. 26v 10A and 12v 0.1A. Table top connections. £5.50, P.P. 95p. Pr. 230-240-250v. Sec. 6.4-0-6.4v 12A. Shrouded table top connections. £4.50, P.P. 95p. Potted types. Pr. 115-230v. Sec. tapped 24-30-32v 2A. £2.95, P.P. 50p. Pr. 115-220-230v. Sec. 6.6v 6A twice and 5v 6A. £4.95, P.P. 95p. Pr. 110-220-240-250v. Sec. 2.0-2v 24A and 6.4v 0.5A. High voltage insulation. £5.75, P.P. £1.25.

**WODEN H.T. TRANSFORMERS**  
Pr. 200-220-240v. Sec. 250v-250v 60M/A. 6.3v CT 3A. 5v 2A. Enclose type. Table top connections. £3.00, P.P. 50p. Parmeko potted type. Pr. 115-220-240v. Sec. 6.6v 6A twice and 5v 6A. £4.95, P.P. 95p. Pr. 110-220-240-250v. Sec. 2.0-2v 24A and 6.4v 0.5A. High voltage insulation. £5.75, P.P. £1.25.

**SPECIAL OFFER OF PAPER BLOCK CAPACITORS**  
6mld 1000v DC wkg. 75p. P.P. 35p. 4mld 1000v DC wkg. £65p. P.P. 35p. 4mld 400v AC wkg. 65p. P.P. 35p. 4mld 800v DC wkg. 50p. P.P. 35p. 8mld 750v DC wkg. 75p. P.P. 35p. 1mld 600v DC wkg. 25p. P.P. 10p. 2mld 100v DC wkg. 51a for £1, P.P. 35p. 0.001mld Mica 6000v DC wkg. £1, P.P. 35p. 0.001mld 2000v DC wkg. £75p. P.P. 35p. 0.003mld Mica. 1250v RMS Pulse wkg. 75p. P.P. 35p. 0.1+0.1mld 600v DC wkg. 25p. P.P. 10p. One only large block cap 40mld 500v DC wkg + 40mld 400v DC wkg + 6mld 600v DC wkg. £8.50, P.P. £1.50.

**COIN OPERATION TV METERS**  
An ideal component unit, comprising of 1 1/2 battery motor, coin mechanism. 240v 5A micro switch, gear wheels etc. Housed in bakelite case. 75p, P.P. 25p.

**COMPUTER FANS AC 230v**  
Size 4 1/2 x 4 1/2 ins. 100 CFM. Ex-equipment. Perfect condition. £3.50, P.P. 50p.

**POTTED H.T. TRANSFORMERS BY FAMOUS MAKERS**  
No. 1 Pr. 110-220-240v. Scr. Sec. tapped 408-0-200-408v. High taps 165M/A. Low taps 500M/A. £5.50, carr. £1. No. 2 Pr. 115-220-240v. Scr. Sec. 400-0-400v. 400M/A. £5.75, carr. £1. No. 3 Pr. 115-220-240v. Scr. Sec. 350-0-350v. 200M/A. 6.3v 6A. 5v 3A. £4.50, carr. £1.

# 1st GRADE COMPONENTS

We hold £250,000 worth of components and all items listed in this advertisement are ex-stock at the time of going to press. All products guaranteed. No minimum order charge.

**SIGNETICS 74 series TTL**

N7400	14p	N7453	18p	N74148	£1.26
N7401	14p	N7454	18p	N74150	£2.45
N7402	14p	N7460	18p	N74151	£1.44
N7403	18p	N7470	36p	N74152	£1.44
N7404	18p	N7472	24p	N74154	£1.44
N7405	20p	N7473	36p	N74155	72p
N7406	41p	N7474	30p	N74156	72p
N7407	41p	N7475	54p	N74158	68p
N7408	41p	N7476	37p	N74161	99p
N7409	20p	N7480	50p	N74180	99p
N7410	15p	N7483	99p	N74162	99p
N7411	21p	N7485	£1.17	N74163	99p
N7413	29p	N7486	32p	N74164	£1.26
N7414	45p	N7490	63p	N74165	£1.26
N7416	27p	N7491	90p	N74166	£1.26
N7417	27p	N7492	63p	N74170	£1.80
N7420	15p	N7493	48p	N74171	£1.13
N7421	21p	N7494	90p	N74175	81p
N7426	23p	N7495	72p	N74180	90p
N7430	15p	N7496	£1.63	N74181	£3.24
N7432	23p	N74100	£1.35	N74190	£1.44
N7433	27p	N74107	32p	N74182	90p
N7437	27p	N74109	54p	N74191	£1.44
N7440	18p	N74116	£1.35	N74192	£1.44
N7442	70p	N74121	36p	N74193	£1.44
N7443	£1.35	N74122	50p	N74194	£1.08
N7444	£1.35	N74123	90p	N74195	90p
N7445	£1.35	N74125	43p	N74198	£1.98
N7446	£1.35	N74126	43p	N74199	£1.80
N7447	£1.12	N74128	45p	N74221	90p
N7448	£1.35	N74132	45p	N74279	72p
N7450	18p	N74145	90p	N74298	£1.28
N7451	18p	N74147	£1.44		

**MULLARD CONSUMER I.C.s**

*TA4350A	£1.96	*TB4540Q	£2.97	*TB4990Q	£3.77
*TA4550	60p	*TB4550	£4.14	*TC160B	£2.84
TA4570	£2.19	*TB4550Q	£4.23	*TC160C	£1.93
*TA4700	£3.80	*TB4560C	£4.14	*TC1210	£4.09
*TA4700A	£4.03	*TB4560CQ	£4.23	*TC2700	£4.19
*TA0100	£1.35	*TB4570	£1.38	*TC290A	£2.76
*TB4480	£1.75	*TB4570Q	£1.47	*TC420A	£1.96
*TB4600	£2.84	TA673	£2.19	*TC4730	£3.22
*TB4600	£2.42	*TB4690	£2.23	*TC4740	£2.88
*TB4600Q	£2.53	*TB4690Q	£2.35	TC4750	£2.19
*TB4510	£2.42	*TB4700	£1.84	*TC4760	£1.73
*TB4510Q	£2.35	*TB4700Q	£1.95	*TC4800	£5.75
*TB4520	£2.99	*TB4700Q	£2.23	TD1002	£1.61
*TB4520Q	£3.08	*TB4750	£2.23	TD1003	£1.38
*TB4530	£2.53	*TB4750Q	£2.35	TD1004	£2.99
*TB4530Q	£2.62	*TB4820	£3.68	*TB41005	£3.45
*TB4540	£2.88	*TB4820Q	£3.77	TD2640	£1.96

\*% Carbon Resistors; Mullard, CR 37 Series - 1 ohm 1M ohm. 1p each.

**VOLTAGE REGULATORS**

**Motorola Variable**  
MC1723CP2 pos. or neg. 2-37v 150mA d.c. 49p  
MC1461G positive 0-40v 500mA d.c. £1.81

**Motorola Fixed**  
MC7805CP 5V positive £1.28 MC7905CP 5V negative £1.80  
MC7812CP 12V positive £1.28 MC7912CP 12V negative £1.80  
MC7815CP 15V positive £1.28 MC7915CP 15V negative £1.80  
MC7818CP 18V positive £1.28 MC7918CP 18V negative £1.80  
MC7824CP 24V positive £1.28 MC7924CP 24V negative £1.80  
MLM309K 5V positive TO-3 can £1.72

**G.I.M. CONSUMER CIRCUITS**

'AY-5-1224	12-24 hour digital clock circuit	£4.25
'AY-3510	3 1/2 digit 0VM circuit	£8.10
'AY-1-0212	Master tone generator	£5.65
'AY-1-5051	4 stage divider	£1.20
'AY-1-6721	5 stage divider	£1.30
'AY-1-6721	6 stage divider	£1.45
'AY-1-5050	7 stage divider	£1.75

**TRIACS**

MAC92-2	60v 0.8A	29p
MAC92-6	400v 0.8A	47p
2N6089	60v 4A	59p
2N6073	400v 4A	74p

**SCRs**

2N5060	30v 0.8A	27p
2N5061	80v 0.8A	27p
MCR107-6	400v 4A	47p

**MULLARD AUDIO AND RADIO MODULES**

*LP1162	5W Audio Amp	£4.20
*LP1173	10W Audio Amp	£6.88
*LP1181	RF-IF	£3.94
*LP1183	2 Stereo Pre-amp Module	£6.32
*LP1184	2 Very low distortion pre-amp stereo	£7.18
*LP1185	FM IF Amplifier	£6.56
*LP1186	FM Tuner Module	£6.88
*LP1400	Stereo Decoder Module	£7.22

Data and suggested circuits available price 5p per Module.

**FERRANTI ICs**

ZN1040E	Universal counter/display cct	£12.00
ZN1034E	Precision timer cct	£2.99
ZN414 A.M.	radio circuit	£1.00

Data and circuits on ZN414 5p

**LEDS**

ML5074B	red (300R)	15p
MV5174B	orange	32p
MV5274B	green	32p
MV5374B	yellow	32p

**THE HALF-POUND SALE**

TO CLEAR OUR STOCKS OF BIN-ENDS ANY PACKAGE - 50p INC. V.A.T THIS SECTION ONLY. Post and packing 20 pence per order.

DEVICE	QTY/PACK	DEVICE	QTY/PACK	DEVICE	QTY/PACK	DEVICE	QTY/PACK	PRICE	
1N283	2	2N3808	5	BC121	2	BD597	3	HS7027	3
1N629	2	2N3924	5	BC125A	2	BD598	3	IT744	15
1N935	2	2N3906	8	BC131	4	BD687	2	MC1312P	1
1N938A	1	2N4059	1	BC136	3	BD688	3	MC1314P	1
1N3323RB	1	2N5089	5	BC137	3	BF121	4	MC1315P	1
1N3595	3	2N5128	5	BC153	6	BF125	4	MC1357P	1
1N4392	2	2N5447	10	BC157	8	BF153	2	ME0411	2
1N5398	15	2N5485	2	BC160	3	BF160	3	ME0414	10
2N1304	3	2N5691							

**REED SWITCH INSERTS**



Overall length 1.85in (Body length 1.1in). Diameter 0.14in. To switch up to 500mA at up to 250VDC. Gold clad contacts 74p per doz. £4.15 per 100. £29.95 per 1,000. £272 per 10,000. All carriage paid U.K. Operating Magnets 95p per doz. £6.95 per 100. £67 per 1,000. All carriage paid U.K. Operating Coils for 12v supply to accept up to four standard reeds £2.50 per doz. £12.80 per 100. All carriage paid U.K. Heavy duty type (Body length 2in) Diameter 0.22in. To switch up to 1A at up to 250VAC. Gold clad contacts £1.45 per doz. £6.95 per 100. £52.00 per 1,000. Changeover Heavy Duty type £2.80 per doz. All carriage paid U.K. Magnets for HD reeds £1.50 doz. A few coils available for HD reeds P.O.A.

**C-SCOPE METAL DETECTORS**

Represent today's BEST VALUE in metal detection equipment

BF050 integral speaker	£26.24
BF060 integral speaker and meter	£33.59
IB100 with headphones	£52.59
IB300 with headphones and meter	£68.24
TR200 with headphones	£59.90
TR400 with headphones and meter	£78.43

Full information on receipt of 10p stamp

**INDUCTION GENERATOR.** Requires a supply voltage of 50V 50Hz and provides an output of 7V per 1,000 r.p.m. directly proportional to speed. This instrument has a wide variety of applications, e.g. anemometers, measuring shaft speed, etc. In brand new condition £5.60 post paid

**ITT OFFICE INTERCOM.** 20 way with modern manual SWB and facilities. Lightweight desk set. Brand new in cartons £160 inc. P & P and VAT. Spare telephones £7.50 ea

**TELEPRINTER PAPER.** Standard rolls. 1 ply £5.00 per doz. 2 ply £5.00 per doz. 3 ply £5.40 per doz. 4 ply £5.70 per doz. All P Pd U.K. Telex your order now

**TAPE STORAGE CANS.** Brand new finished steel cans originally intended for 16mm film but ideal for storing 7in. reels of tape. Our last supply of these items was quickly exhausted at 30p each but as a result of a massive new purchase we can now offer a case of 55 at £6.80 inc. P & P and VAT

**SOLAR CELLS.** Ferranti silicon MS18E, active area 390 sq. mm. Open CCT voltage 550mV at 3000 lumens/sq. ft. Sht. Cct. Current 60mA. Optimum load 90 Ohms. Dia. 34mm. Thickness 6mm. Ex. made up panel £1.35 (inc. P & P and VAT)

**CONTINENTAL CUSTOMERS** — we have a direct link by air from Lydd to Beauvais (also Channel Islands) and are 35.45 minutes drive from Dover. Folkestone with direct hovercraft and sea links with France and Belgium

SPECIALIST STOCKISTS OF SERVO MOTORS, SYNCHROS, TEST EQUIPMENT, METERS AND CONNECTORS

**Servo and Electronic Sales Ltd**  
(Established 1953)

24 HIGH ST., LYDD, KENT TN29 9AS. Tel. Lydd 20252 (STD 0679) VAT No. 201-1296-23 TELEX 965265

**PLESSEY GROUND BASED U.H.F. GROUND/AIR TX/RX FOR EXPORT ONLY OR SALE TO LICENSED USERS**  
Single Channel Receiver 5820-99-932-5694  
Single Channel Transmitter 5820-99-932-5698  
Single Channel Amplifier 5820-99-932-5701  
Power Unit for Amplifier 5820-99-932-5700  
Cooler Unit 5820-99-932-3995  
These assemble into free standing rack unit providing UHF communications over 225 0 to 399 9MHz. The TX Amplifier unit giving 100 Watts R.F. output into 50 Ohms. Spare sub-units available. All are guaranteed new and unused. Full details on request

**SOLARTRON OSCILLOSCOPES** in stock CD1183 CD1212 CD1220 CD1400 P.O.A. and INSTRUMENTS SR151 152 VP253 OS103 C0546 JX641 JX641A VF252 JX746 LM1420 T0960 JX603 JM1600 etc. P.O.A.

**HEWLETT PACKARD SAMPLING 'SCOPE HP185A.** £324 inc. carr. and V.A.T. HP185B £357.

**STAINLESS STEEL VACUUM CONTAINERS FOR LIQUIDS.** Capacity 2 U.S. GALLONS. FITTED WITH DELIVERY TAPS. Brand new in cartons—£25 (inc. P & P U.K.)

**PANEL DISPLAY RECORDING CAMERA.** Manufactured A.G.I. Specifically for the recording of complex instrument displays on 2 1/4" x 2 1/4" shots. Fitted 80mm F3.5 lens. Shutter speeds 1/100 1/50 1/25 sec. and time exp. Focusing at 1.75 to 50ft. in 18 steps. Aperture stgts. F3.5 to F22. Prismatic viewfinder and facility for viewing direct on ground glass screen. Rotating filter attachment. Cord film advance and shutter cock with septa. Button control and electrical release facility (24V DC). Spool holds 40 exposures. Camera may be wall mounted on bracket supplied. Tripod mounting socket provided. In wooden case. Two grades available: as new, Grade A £35.50 (inc. P & P and VAT). Somewhat used but serviceable Grade B £28.40 (inc. P & P and VAT).

**POLAROID SPECTRUM ANALYSER, SAR4W** 10 MHz to 40 RRHz. With handbooks P.O.A.

**ETHER TRANSISTORISED A.C. MAINS STABILISER.** 190-260V 50 Hz. in. output 220-240V (adjustable) 1000 VA 17" x 7" x 11" £42.50 (inc. carr. U.K. Mainlands & VAT).

**BRUSH CLEVEIT 2-CHANNEL RECORDER.** 4" sprocketless chart. Push button gearbox 1.5 2.5 125 min. Twin int'l. amprhs. Giving 10mV 10V range. variable sensy. elect. zeroing. twin event markers. 13" x 13" x 12" 115v 60Hz input. £82.50 (inc. carr. & VAT)

**Metal Oxide Resistors (ELECTROSIL & WELWYN) Tantalum Capacitors (KEMET, ITT, PLESSEY, ETC.)**

ALL AVAILABLE EX STOCK IN MANUFACTURING QUANTITIES

**MIL SYNCHROS AND SERVO MOTORS EX STOCK**

**AIRCREW CHRONOGRAPHS**



Stainless steel case with screw back, luminous hands and markings. One-fifth sec. sweep hand controlled independently of main movement by press to start stop and return to zero button. 15 jewel movement. Many of these watches are as new but all have been completely overhauled and checked for accuracy. Fitted strap. White face £18.30. Black face £19.25 inc. P & P. All watches: Inspection against remittance.

**GS WATCHES** all with brushed stainless steel case with screw back and black face. Manufactured by CYMA VERTEX RECORD, etc. to a standard specification. Completely overhauled. Fitted strap £8.85 (inc. P & P). We also have limited quantities of these watches by OMEGA, LONGINES, BUREN, Hamilton, JAEGER LE COULTRE and IWC at £15.30 inc. P & P



**ANALYTICAL EQUIPMENT**

**GAS CHROMATOGRAPHY RESEARCH OVEN PV4051/4056 (other GC items in stock)**  
A large capacity oven of low thermal mass for use between 35 and 400 C. Provides a forced air circulating system yielding 1000 changes of air per min. The oven has forced air cooled outer surfaces when the internal temperature is high. 210-240V, 50Hz. 2.6KW. £31.50 (C. Pd. England and Wales)

**IONISATION AMPLIFIER PV4075**  
A modern high grade low noise solid state amplifier to feed a potentiometer recorder. 18 input ranges from 10<sup>-15</sup> to 5 x 10<sup>-1</sup> A with 5 outputs of 1mV to 100mV. Linearity 0.1% 1s. Noise less than 0.5% 1s at max sensitivity. Back off facility. Dimensions 28 x 10 x 43 cm deep. With operating information £28.50. (C. Pd. U.K.)  
Details of these three and other gas chromatography items price 25p (C. W. O. only). Handbooks (complete) available

**COMPUTER PROCESSORS AND PERIPHERALS.** Printers Readers, Core Stores, etc.

**AIRCRAFT INSTRUMENTS** for industrial and educational use. Released items available for flight use

**COMMUNICATIONS RECEIVERS.** Hammarlund SP600 JX in superb condition £160.


**400Hz ROTARY CONVERTERS.** Both DC & AC input available. E.g. 415v 50Hz to 115v 400Hz 1ph 50w AJ £27.50.

**MULTIWAY CABLES** in stock up to 50 way or up to 750 amp. Also PTFE insulated types

**MARCONI SPECTRUM ANALYSERS OA1094A/S.** Listed at £2700. Our price £865.

**ACTUATORS, RELAYS, FLOODLAMPS, POWER UNITS, TRIMPOTS FANS MICROWAVE EQUIPMENT.** All ex-stock

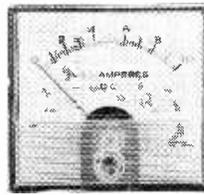**REACH FOR THE PEAKS OF MEASURING INSTRUMENT ENGINEERING!**



**TYPE TAD**

Dim's	48	66	85	118	150
in	x	x	x	x	x
mm	42	50	70	108	110
50 μA	£3.63	£3.81	£4.00	£4.90	£5.46
500 μA	£3.34	£3.51	£3.72	£4.62	£5.32
1 mA	£3.27	£3.44	£3.64	£4.53	£5.23
15vDC	£3.30	£3.49	£3.67	£4.57	£5.26
300vAC	£3.47	£3.66	£3.84	£4.73	£5.30

**TYPE SA**

Dim's	43	51	61	82
in	x	x	x	x
mm	42	51	61	78
50 μA	£3.52	£3.59	£3.87	£4.12
500 μA	£3.21	£3.28	£3.53	£3.76
1 mA	£3.11	£3.18	£3.43	£3.72
15vDC	£3.15	£3.22	£3.50	£3.76
300vAC	£3.39	£3.46	£3.67	£3.92



**FOR YOUR PRODUCTION REQUIREMENTS USE ALPS PANEL METERS FULL RANGE PRICE LIST—SAE PLEASE!**  
Substantial quantity discounts to manufacturers  
Remember! We are the sole importers!



**TYPE SR**

Dim's	73	78	92
in	x	x	x
mm	56	63	72
50 μA	£3.93	£4.18	£4.42
500 μA	£3.58	£3.83	£4.08
1 mA	£3.48	£3.73	£3.98
15vDC	£3.60	£3.84	£4.09
300vAC	£3.73	£3.87	£4.22

**LABORATORY TYPE SA65E**

Metric size 82 x 78mm

50 μA	£6.51
500 μA	£6.26
1 mA	£6.06
1 A	£6.16
15vDC	£6.16
300vAC	£6.16



ALL ABOVE PRICES INCLUDE P. & P. and VAT

**NEW ADDITIONS to our range of PANEL METERS available at present only in MANUFACTURING QUANTITIES**

SE45	64 x 52 mm
SE52	80 x 60 mm
SE65	100 x 80 mm
SE85	120 x 100 mm



SU45	69 x 53 mm
SU55	87 x 63 mm
SU65	105 x 77 mm

Above meter forms are for moving coil movements only and may house S-meter and VU-meter instruments.

**VU METERS**

SF100	72 x 66 mm
SF104	63 x 60 mm
SF106	63 x 60 mm



All meters can be supplied with special or personalised scales, internal illumination, coloured front lenses, mirror scales, special pointer forms, etc.

Full details and prices on request

**AUTOMOBILE TEST EQUIPMENT**


**SERVO AUTOTESTER No. 1.** 0-3.2 & 0-16v. 0-80 A-DC & 0-20K Ohms dwell angle and speed for 4 b & 8 cyc engines and E.H.T. SEC. VOLTS. A substitute capacitor is incorporated. Size 26.5 x 14 x 16.5cm. wt 3.25kg. With handbook £30.37 inc. P & P & V.A.T.

**SERVO AUTOTESTER No. 2.** 0-16v. 0-80A dwell angle and speed for 4 6 & 8 cyc engines. Size 16 x 9.5 x 6.5 cm. Wt. 0.45kg. With instrns. £11.15 inc. P & P & V.A.T.

**SERVO AUTOTESTER No. 3.** Simultaneously on separate meters 0-16v & 0-BOA. Size 17 x 10 x 7 cm. Wt. 0.45kg. Price £9.76 inc. P & P & V.A.T.

**SERVO AUTOTESTER No. 4.** Dwell angle and engine speed. Hand held instt. Size 14 x 8 x 5 cm. Wt. 0.26kg. Price £6.35 inc. P & P & V.A.T.

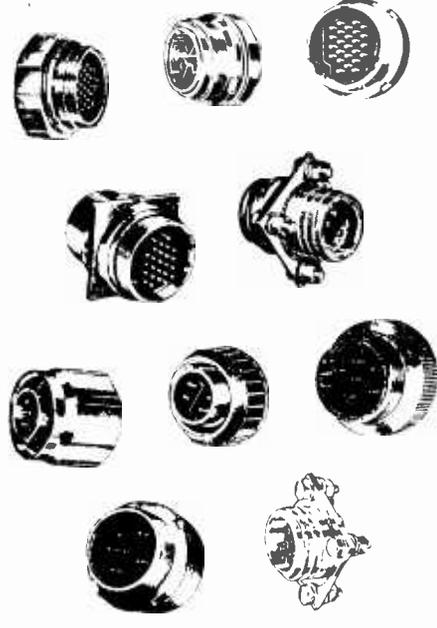**OVER 300,000 RF AND MULTI-WAY CONNECTORS IN STOCK. TELEX YOUR REQUIREMENTS NOW.**



WWW-089 FOR FURTHER DETAILS

TTLs by TEXAS			C-MOS LOGIC		OP. AMPS		TRANSISTORS		
7400 13p	7483 80p		CD4000AE 19p	1458 Dual Op Amp Int Comp 8 pin DIL 70p	AC126 11p	BF182 33p	ZTX502 18p	2N4060 13p	OA90 7p
7401 14p	7484 95p		CD4001AE 19p	301A Ext. Comp 8 pin DIL 36p	AC127 12p	BF184 22p	2N697 13p	2N4289 20p	OA91 7p
7402 14p	7485 120p		CD4002AE 19p	3130 COSMOS/BI-Polar MosFet 8 pin DIL 100p	AC128 11p	BF185 22p	2N698 30p	2N4347 130p	OA95 7p
7403 16p	7486 30p		CD4003AE 19p	3900 Quad Op Amp 14 pin DIL 70p	AC141 18p	BF194 10p	2N706 12p	2N4348 160p	OA200 8p
7404 16p	7489 270p		CD4004AE 19p	J361 FET Op Amp 10-99 275p	AC142 18p	BF195 9p	2N708 18p	40360 40p	OA202 10p
7405 16p	7490 40p		CD4005AE 19p	709 Ext. Comp 8/14 pin DIL 30p	AC176 11p	BF196 14p	2N918 40p	40361 38p	IN914 4p
7406 38p	7491 75p		CD4006AE 19p	741 Int. Comp 14/14 pin DIL 25p	AC187 13p	BF197 15p	2N928 20p	40362 40p	IN4148 4p
7407 36p	7492 45p		CD4007AE 19p	747 Dual 741 14 pin DIL 70p	AC188 12p	BF200 32p	2N930 18p	40364 120p	
7408 14p	7493 40p		CD4008AE 19p	748 Ext. Comp 8 pin DIL 36p	AD149 43p	BF257 32p	2N1131 18p	40369 55p	
7409 20p	7494 75p		CD4009AE 19p	776 Programmable Op. Amp. TO-5 140p	AD162 36p	BFR39 30p	2N1302 18p	40410 55p	
7410 13p	7495 65p		CD4011AE 19p		AF114 18p	BFR40 30p	2N1304 21p	40411 225p	RECTIFIER
7411 23p	7496 78p		CD4012AE 19p		AF115 18p	BFR79 30p	2N1305 21p	40594 75p	BY100 25p
7413 32p	74107 30p		CD4013AE 19p		AF116 18p	BFR80 30p	2N1306 28p	40595 85p	BY126 12p
7414 60p	74121 30p		CD4014AE 19p		AF117 18p	BFR88 30p	2N1307 28p		BY127 12p
7416 33p	74122 46p		CD4015AE 19p		AF139 33p	BFX30 30p	2N1308 28p		BY210 45p
7420 14p	74123 68p		CD4016AE 19p		AF239 38p	BFX84 26p	2N1309 28p		BY211 45p
7422 18p	74141 65p		CD4017AE 19p		BC107 9p	BFX85 25p	2N1613 20p		BY212 45p
7423 34p	74151 72p		CD4018AE 19p		BC108 9p	BFX86 25p	2N1711 20p		BY213 45p
7425 30p	74153 85p		CD4019AE 19p		BC109 10p	BFX87 20p	2N1893 30p		BY214 45p
7427 37p	74154 160p		CD4020AE 19p		BC109C 12p	BFX88 24p	2N2218 21p		BY215 45p
7430 14p	74155 76p		CD4021AE 19p		BC147 7p	BFY50 16p	2N2219 20p		IN4001 5p
7432 25p	74156 76p		CD4022AE 19p		BC148 8p	BFY51 15p	2N2220 19p		IN4004 6p
7437 25p	74160 99p		CD4023AE 19p		BC149C 7p	BRX39 34p	2N2222 20p		IN4007 7p
7440 14p	74161 99p		CD4024AE 19p		BC158 10p	BSX19 16p	2N2369 14p		
7441 85p	74162 99p		CD4025AE 19p		BC159 11p	BSX20 18p	2N2484 30p		
7442 60p	74163 99p		CD4026AE 19p		BC177 18p	BU105 140p	2N2490 20p		
7447 75p	74164 120p		CD4027AE 19p		BC178 17p	BU108 250p	2N2905 20p		
7448 70p	74165 126p		CD4028AE 19p		BC179 18p	MJE340 45p	2N2906 20p		
7450 15p	74174 120p		CD4029AE 19p		BC182 10p	MJE295599p	2N2926R 7p		
7451 16p	74175 85p		CD4030AE 19p		BC183 10p	MJE305565p	2N2926B 7p		
7453 18p	74180 100p		CD4031AE 19p		BC184 11p	MPSA12 50p	2N2926O 8p		
7454 16p	74181 298p		CD4032AE 19p		BC187 30p	MPSA12 50p	2N2926Y 9p		
7456 16p	74182 82p		CD4033AE 19p		BC212 11p	MPSA56 62p	2N2926C 9p		
7470 70p	74185 135p		CD4034AE 19p		BC213 10p	MPSU06 62p	2N3053 18p		
7472 25p	74190 144p		CD4035AE 19p		BC214 14p	OC28 55p	2N3054 40p		
7473 30p	74191 144p		CD4036AE 19p		BC478 30p	OC35 48p	2N3439 67p		
7474 30p	74192 120p		CD4037AE 19p		BCY70 18p	OC36 56p	2N3442 140p		
7475 45p	74193 120p		CD4038AE 19p		BCY71 22p	OC41 / 2 15p	2N3702 11p		
7476 30p	74194 108p		CD4039AE 19p		BD123 100p	OC45 11p	2N2703 11p		
7480 50p	74195 75p		CD4040AE 19p		BD124 65p	OC71 20p	2N3704 11p		
7481 95p	74198 198p		CD4041AE 19p		BD131 36p	TIP29A 40p	2N3705 11p		
7482 70p	74199 180p		CD4042AE 19p		BD132 40p	TIP30A 48p	2N3706 10p		
			CD4043AE 19p		BD135 43p	TIP31A 52p	2N3707 11p		
			CD4044AE 19p		BD139 63p	TIP32A 58p	2N3708 9p		
			CD4045AE 19p		BD140 70p	TIP33A 90p	2N3709 9p		
			CD4046AE 19p		BF115 22p	TIP34A 115p	2N3773		
			CD4047AE 19p		BF167 23p	TIP35A 290p			
			CD4048AE 19p		BF170 25p	TIP36A 370p	2N3866 90p		
			CD4049AE 19p		BF173 25p	TIP41A 65p	2N3903 18p		
			CD4050AE 19p		BF177 26p	TIP42A 70p	2N3904 18p		
			CD4051AE 19p		BF178 28p	TIP2955 70p	2N3905 18p		
			CD4052AE 19p		BF179 33p	ZTX108 10p	2N3906 18p		
			CD4053AE 19p		BF180 33p	ZTX300 13p	2N4058 15p		
			CD4054AE 19p		BF181 33p	ZTX500 15p	2N4059 10p		
			CD4055AE 19p						
			CD4056AE 19p						
			CD4057AE 19p						
			CD4138AE 19p						

Designer-approved

# TEXAN AMPLIFIER AND TUNER KITS

... from Henry's Radio. The Sole UK Distributors.


Here is your opportunity to build the superb Texan amplifier and tuner! Designed especially for Henry's by Richard Mann of Texas Instruments, the Texan amplifier was featured in Practical Wireless. Through bulk buying, Henry's are able to offer both these kits of quality components at low cost. Naturally, as sole appointed UK distributors, Henry's offer a full after sales service - so if your kits don't result in properly functioning units, we'll help you sort them out!

## TEXAN AMPLIFIER


Incorporating fully integrated stereo preamp and power amp, with 6 IC's, 10 transistors, 6 rectifiers and zener diodes. Plus stabilised, protected circuitry, glass fib pcb; Gardener's low-field low-line mains transformer; and all facilities and controls. Slim design, chassis 14 1/2" x 6" x 2" overall. Professional appearance and performance - 20 watts per channel RMS, less than 0.1% distortion at 1 kHz.
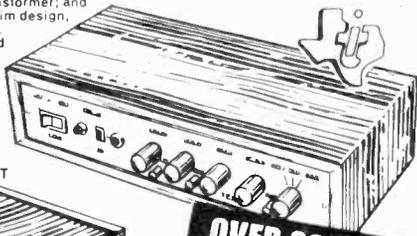
### KIT PRICE

**£29.50** inc. VAT  
 +£1.00 p & p  
 Built & tested £39.50 inc. VAT  
 +£1.00 p & p.



**OVER 30,000 ALREADY SOLD**

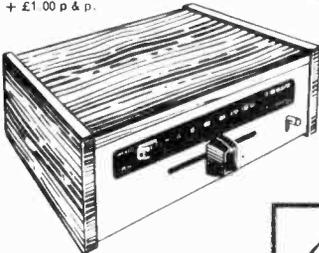


## TEXAN TUNER

Featuring varicap tuning and phase lock loop decoder in a professionally designed circuit, this tuner has a glass fibre pcb, built-in AFC, 9 transistors, 1 IC, 9 diodes; and a teak cabinet. Aerial sensitivity 2.5 uV; stereo separation 40 dB; frequency response on stereo 20 - 15,000 Hz ± 3 dB (upper limit set by transmitter), on mono 20 - 22,000 Hz ± 3 dB. Circuit can be altered to cover amateur and aircraft bands. Mains operated.
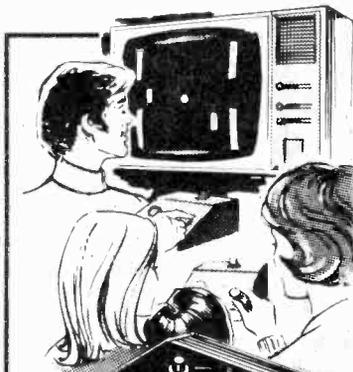
### KIT PRICE £25.95

inc. VAT +£1.00 p & p  
 Built & tested £30.95 inc. VAT  
 +£1.00 p & p.



## ELECTRONIC FOOTBALL & TENNIS

# VIDEO SPORT

### ON YOUR OWN TV

Play three exciting electronic ball games ● FOOTBALL ● TENNIS ● HOLE IN THE WALL on your own TV! Just plug Video Sport into the aerial socket of your TV and away you go. Completely safe for you, your children and your TV. Mains operated.

### HENRY'S PRICE ONLY

**£27.50** inc. VAT + £2.50 p & p.

**IDEAL GIFT**  
**10,000 ALREADY SOLD!**

**HENRY'S**

404/6 EDGWARE ROAD  
 LONDON W.2 01-402 8381

LOWER SALES FLOOR

231 TOTTENHAM COURT ROAD LONDON W.1 01-636 6682

NEW MIDLANDS STORE

94/96 UPPER PARLIAMENT STREET, NOTTINGHAM 0602-40403

All mail to Henry's Radio, 303 Edgware Road, London W.2

**Benefit from our 30 years' experience in retail electronics!**

# DEMA ELECTRONICS INTERNATIONAL

## ELECTRONIC COMPONENTS DISTRIBUTOR FOR INDUSTRY AND HOBBYIST

### MONTHLY SPECIALS - from DEMA ELECTRONICS

CT5001	12 Digit 4-Funct	£ 99	1101	256 Bit Ram Mos	£ 1.05
CT5002	Battery Oper. 5001	1.19	1103	1024 Bit Ram Mos	1.95
CT5005	12 Digit 4-Funct w/Mem	1.49	5261	1024 Bit Ram L/Power	1.95
MM5314	24-Pin 6-Digit Mux	2.75	5203	2048 Bit U/Violet PROMS	9.95
CT7001	4 or 6 Digit Alarm	3.75	2101	1024 Bit Status Ram	2.95

555	Timer	0.40			
556	Dual Timer	0.70	9-Digit LED Display Comm		
1CL8038	Funct Gen Volt Contr Oscillator, Sine, Sq.	1.95	Cathode Compatible with 8 Digit Ck Chips, 12" Char.		1.95

### TTL 7400 SERIES

7400	£ 0.11	7440	£ 0.11	7485	£ 0.85	74155	£ 0.69
7401	0.11	7441	0.60	7486	0.24	74156	0.69
7402	0.11	7442	0.55	7488	2.50	74157	0.69
7403	0.11	7443	0.55	7489	1.50	74158	0.69
7404	0.13	7444	0.60	7490	0.40	74160	0.89
7405	0.13	7445	0.75	7491	0.55	74162	0.89
7406	0.22	7446	0.85	7492	0.43	74163	0.89
7407	0.22	7447	0.75	7493	0.43	74164	1.05
7408	0.14	7448	0.85	7494	0.49	74165	1.05
7409	0.14	7450	0.12	7495	0.49	74166	1.05
7410	0.11	7451	0.13	7496	0.55	74170	1.65
7411	0.16	7453	0.13	74100	0.89	74175	0.90
7413	0.26	7454	0.14	74107	0.27	74180	0.80
7416	0.22	7460	0.11	74121	0.27	74181	2.50
7417	0.22	7470	0.24	74122	0.37	74182	0.80
7420	0.11	7472	0.21	74123	0.49	74192	0.90
7426	0.23	7473	0.25	74145	0.57	74193	0.85
7430	0.12	7474	0.25	74150	0.59	74194	0.85
7432	0.22	7475	0.37	74151	0.59	74195	0.80
7437	0.25	7476	0.26	74153	0.69	74198	1.70
7438	0.25	7483	0.69	74154	1.05	74199	1.70

### HIGH SPEED 74H00

74H00	£ 0.16	74H20	£ 0.16	74H52	£ 0.16	74H71	£ 0.21
74H01	0.16	74H21	0.16	74H53	0.16	74H72	0.26
74H04	0.16	74H22	0.16	74H54	0.21	74H74	0.28
74H05	0.21	74H30	0.16	74H55	0.16	74H76	0.28
74H08	0.16	74H40	0.16	74H60	0.16		
74H10	0.16	74H50	0.16	74H61	0.16		
74H11	0.16	74H51	0.21	74H62	0.16		

### CMOS 4000 SERIES

4000A	£ 0.19	4014	£ 1.10	4028	£ 0.95	4071	£ 0.23
4001	0.19	4015	1.10	4030	0.50	4072	0.25
4002	0.19	4016	0.55	4042	0.95	4073	0.25
4006	0.90	4019	0.67	4043	1.20	4075	0.25
4007	0.19	4020	1.10	4044	1.20	4078	0.25
4008	1.30	4021	1.10	4049	0.48	4081	0.25
4009	0.49	4023	0.19	4050	0.48	4082	0.29
4010	0.49	4024	0.85	4066	0.75	4528	0.85
4011	0.19	4025	0.19	4068	0.23	4585	1.25
4013	0.39	4027	0.75	4069	0.23		

### DTL

930	£ 0.10	936	£ 0.10	944	£ 0.10	962	£ 0.10
932	0.10	937	0.10	946	0.10	963	0.10

### LINEARS

LM300	TO99	£ 0.45	340U	TO92	£ 1.25	739	A DIP	£ 0.65
301	V DIP	0.29	380	A DIP	30	741	V DIP	0.22
302	TO99	0.45	381	A DIP	1.05	747	A DIP	0.44
304	TO100	0.50	546	V DIP	0.51	748	V DIP	0.27
305	TO99	0.60	550	A DIP	0.55	5556 (2456)	V DIP	0.65
307	V DIP	0.38	555	V DIP	0.45	5558 (1458)	V DIP	0.65
307	TO99	0.45	556	B DIP	0.75	ULN 2111	A DIP	0.95
308	A DIP	0.59	560	B DIP	2.55	LM3900	A DIP	0.35
	TO99	0.79	561	B DIP	2.55	75450	V DIP	0.45
309K	TO3	1.45	562	B DIP	2.55	75451	V DIP	0.45
310	T pkg	0.65	565	A DIP	1.25	75452	V DIP	0.45
311	V DIP	0.90	566	V DIP	1.20	75453	V DIP	0.45
320K	TO 3 NEG	567	V DIP	1.25	75454	V DIP	0.45	
	5, 2, 12, 15	1.25	709	A DIP	0.22	75491	A pkg	0.65
324	A DIP	1.07	710	A DIP	0.25	75492	A pkg	0.75
339	A DIP	1.49	711	A DIP	0.30			
340K	TO3	2.10	723	A DIP	0.38			

V - Mini Dip A - 14L Dip B - 16 Dip TO99 - 8 Pin Header TO100 - 10 Pin Header  
 Data sheets supplied on request. Add 20 ea. excepted as noted

MEMORIES w/DATA	CALCULATORS & CLOCKS w/DATA
1101 256 Bit Ram Mos £ 1.79	5001 Cal Chip £ 0.99
1103 1024 Bit Ram Mos 2.25	5002 Cal Chip 1.19
7499 (8225) 64 Bit Ram TTL 1.50	5005 Cal Chip 1.49
8223 Programmable ROM 2.50	5311 Clock Chip 2.95
5260 1024 Bit Ram Low Power 1.95	5312 Clock Chip 2.95
	5313 Clock Chip 2.95
	5314 Clock Chip 3.45
	5316 Clock Chip 3.95
	Data only for any of above
	Refundable Against Purchase.

LEDS	TRANSISTORS
MV 5020 Jumbo Red or Clear £ 0.15	2N 2219A TO5 £ 0.37 2N 4124 TO92 0.10
MAN 1 Red 7 Seg. 270' 1.30	2N 2222 TO18 0.15 2N 4126 TO92 0.10
MAN 3A Red Seg. 127 35	2N 2369 TO18 0.10 2N 4401 TO92 0.10
MAN 5 Green 7 Seg. 270 1.75	2N 2905A TO5 0.38 2N 5225 TO92 0.10
MAN 6 6 Solid Seg. 2.50	2N 3227 TO18 0.32 2N 5226 TO92 0.10
9 Digit Array Fairchild 37 with clear magnifying lens 2.95	

DISCOUNTS:	MIN ORDER	All Items New Branded Guaranteed By DEMA ELECTRONICS
10% on orders over £ 10	£ 2.5	
15% on orders over £ 15		

TERMS: PRICES LISTED ARE BRITISH POUNDS & PENCE. SEND CHEQUE WITH ORDER. MASTERCHARGE, BANKAMERICARD, BARCLAY CARD ACCEPTED. TERMS OFFERED TO SCHOOLS & INSTITUTIONS.

POSTAL AND HANDLING CHARGES		
under 4.99	add 0.35	£ 10 and over
5.00-9.99	add 0.25	No Charge

DEMA ELECTRONICS INTERNATIONAL  
 P.O. Box 407 San Ramon, Ca. 94583 USA  
 Cable DEMAEINTL

# AMERICAN SEMICONDUCTORS

## TRANSISTORS

BRAND NEW, FULLY GUARANTEED			
AC107	0.20	HC171	0.15
AC113	0.20	BF172	0.15
AC115	0.20	BF173	0.15
AC117K	0.30	BC174	0.15
AC122	0.12	BC175	0.22
AC125	0.18	BC177	0.19
AC126	0.18	BC178	0.19
AC127	0.19	BC179	0.19
AC128	0.19	BC180	0.25
AC132	0.15	BC181	0.25
AC134	0.15	BC182	0.15
AC137	0.15	BC182L	0.15
AC141	0.19	BC183	0.15
AC141K	0.30	BC183L	0.15
AC142	0.19	BC186	0.20
AC142K	0.26	BC184L	0.20
AC151	0.16	BC194	0.29
AC154	0.20	BC187	0.29
AC155	0.20	BC207	0.11
AC156	0.20	BC208	0.11
AC157	0.25	BC209	0.20
AC165	0.20	BC212L	0.13
AC166	0.20	BC213L	0.13
AC167	0.20	BC214L	0.17
AC168	0.25	BC225	0.26
AC169	0.15	BC226	0.36
AC176	0.20	BC2601	0.28
AC177	0.25	BC302	0.25
AC178	0.29	BC303	0.31
AC179	0.29	BC304	0.37
AC180	0.20	BC440	0.31
AC180K	0.30	BC460	0.37
AC181	0.20	BC490	0.25
AC181K	0.37	BC491	0.27
AC187	0.22	BCY32	0.31
AC187K	0.23	BCY33	0.22
AC188	0.22	BCY34	0.26
AC188K	0.23	BCY70	0.15
AC17	0.26	BCY71	0.20
AC18	0.20	BCY72	0.15
AC19	0.20	BCY10	0.20
AC20	0.20	BCZ11	0.26
AC21	0.20	BCZ12	0.26
AC22	0.17	BD115	0.63
AC27	0.19	BD116	0.81
AC28	0.19	BD121	0.61
AC29	0.36	BD123	0.67
AC30	0.29	BD124	0.70
AC31	0.29	BD131	0.51
AC32	0.21	BD132	0.61
AC33	0.21	BD133	0.67
AC36	0.29	BD134	0.67
AC40	0.18	BD137	0.36
AC41	0.19	BD138	0.51
AC44	0.36	BD139	0.56
AD130	0.39	BD140	0.61
AD140	0.39	BD155	0.81
AD142	0.61	BD156	0.61
AD143	0.39	BD176	0.61
AD149	0.51	BD177	0.67
AD161	0.36	BD178	0.67
AD162	0.36	BD179	0.71
AD161 & AD162 (MP)	0.69	BD180	0.71
AD170	0.51	BD186	0.67
AD174	0.25	BD187	0.71
AD175	0.25	BD188	0.71
AD176	0.25	BD189	0.77
AD177	0.25	BD190	0.77
AD178	0.25	BD191	0.77
AD405	0.25	BD418	0.77

**VISIT OUR COMPONENT SHOP**  
 18 BALDOCK STREET, WARE, Herts (A10)  
 Open Mon.-Sat. 9-5.30 p.m. Tel. 61593  
 Late night shopping till 7 p.m. Fri.

# PO BOX 6 WARE HERTS

**AL 60**


**ONLY £3.95**

**50w. PEAK (25w. R.M.S.)**



● Max Heat Sink temp 90°C ● Frequency Response 20Hz to 100K Hz ● Distortion better than 0.1 at 1KHz  
 ● Supply voltage 15-50 volts ● Thermal Feedback ● Latest Design Improvements ● Load — 3, 4, 5 or 16 ohms ● Signal to noise ratio 80dB ● Overall size 63mm x 105mm x 13mm. Especially designed to a strict specification. Only the finest components have been used and the latest solid state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

## STABILISED POWER MODULE SPM80

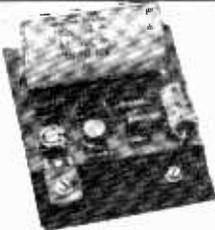


SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm x 105mm x 30mm.

These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Disco Systems. Public Address Intercom Units, etc. Handbook available 10p.

**TRANSFORMER BMT80 £2.60**

**PRICE £3.00**

## STEREO PRE-AMPLIFIER TYPE PA100

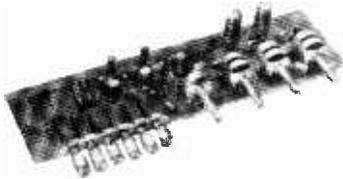

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages.

Three switched stereo inputs, and rumble and scratch filters are features of the PA100 which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

**£13.20**

**GUARANTEE SATISFACTION OR YOUR MONEY REFUNDED**

### MK 60 AUDIO KIT

Comprising: 2 x AL60, 1 x SPM80, 1 x BTM80, 1 x PA100, 1 front panel, 1 kit of parts to include on-off switch, neon indicator, stereo headphone sockets plus instruction booklets.

COMPLETE PRICE: £27.55 plus 45p postage.

### TEAK 60 AUDIO KIT

Comprising: Teak veneered cabinet size 16 1/2" x 11 1/2" x 3 3/4", other parts include aluminium chassis, heatsink and front panel bracket, plus bar panel and appropriate sockets, etc.

KIT PRICE: £9.20 plus 45p postage.

## STEREO 30 COMPLETE AUDIO CHASSIS

**7 + 7 WATTS R.M.S.**

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This with only the addition of a transformer or overwind, will produce a high quality audio unit suitable for use with a wide range of inputs, i.e. high quality ceramic pickup, stereo tuner, stereo tape deck, etc.


Simple to install, capable of producing really first-class results, this unit is supplied with full instructions, black front panel, knobs, mains switch, fuse & fuse holder and universal mounting bracket, enabling it to be installed in a record plinth, cabinets of your own construction or the cabinet available.

Ideal for the beginner or advanced constructor who requires Hi-Fi performance with a minimum of installation difficulty. Can be installed in 30 mins.

**PRICE £15.75** Plus 45p postage & packing

**TRANSFORMER £2.45** plus 45p postage & packing **TEAK CASE £3.65** plus 45p postage & packing

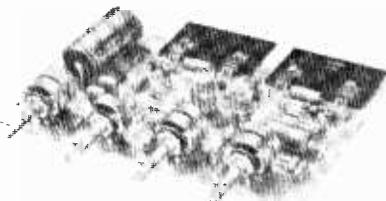**PLEASE ADD V.A.T. AT 25% TO ALL ITEMS EXCEPT**  
 \* ADD 8%  
 # NO V.A.T.  
 GIRO NUMBER 388-7006




## AL 10/AL 20/AL 30

The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S.

The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home.

**AL10 £2.30, AL20 £2.65, AL30 £2.95**

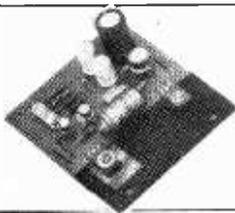

### SPEAKERS

E.M.I. LEK 350 Loudspeakers Enclosure kit in teak veneer, including speakers. Rec. retail price £4.50 per pair.

OUR SPECIAL PRICE ONLY £27.75 per pair P&P £3 WHILE STOCKS LAST!

### HEADPHONES

4-16 ohms impedance frequency response 20 to 20,000 Hz stereo/mono switch and Volume Control £4.55

### FRONT PANEL

FOR PA100. Attractive matt silver. Finish with black trim and lettering. Adds that professional touch. £1.10 only.

### M.P.A.30

Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the new Bi-Pak M.P.A.30 which is a high-quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only.

Used in the construction are 4 low noise, high gain, silicon transistors. It is provided with a standard DIN input socket for ease of connection.

Supplied with full, easy-to-follow instructions.

**PRICE £2.65**

### STORAGE-CARRY CASES

**RECORD CASES**  
 7 in E.P. 18 3/8th in. x 7 in x 8 in (50 records) \*£2.48  
 12 in L.P. 13 1/2 in x 7 3/8th in x 12 1/2 in (50 records) \*£3.30

**CASSETTE CASES**  
 Holds 15. 10 in x 3 1/2 in x 5 in. Lock and handle \*£1.50

**8-TRACK CARTRIDGE CASES**  
 Holds 14. 13 in x 5 in x 6 in. Lock and handle \*£2.20  
 Holds 24. 13 3/8th in x 8 in x 5 3/8th in Lock and handle \*£3.20

### CARTRIDGES

ACOS GP91-1SC 200mV at 1.2cms/sec £1.11  
 GP93-1 280mV at 1cm/sec £1.43  
 GP96-1 100mV at 1cm/sec £2.31  
 TTC J-2005 Crystal/Hi Output £0.97  
 J-2010C Crystal/Hi Output £1.11  
 Compatible £1.52  
 J-2006S Stereo/Hi Output £1.81  
 J-2105 Ceramic/Med Output  
 J-2203 Magnetic 5mV/5cm/sec £4.78  
 including stylus £2.88  
 J-22038 Replacement stylus for above  
 AT-55 Audio-technica magnetic £3.06  
 cartridge 4mV/5cm/sec

### DYNAMIC MICROPHONE

TYPE B1223 200 ohms impedance. Complete with stand, on/off switch and 2.5mm and 3.5mm plugs. Suitable for cassette tape recorders. **PRICE £1.67.**


**JUST OUT!**

**STEREO FM TUNER**

**WRITE NOW FOR FULL DETAILS**

**TAUT SUSPENSION MULTIMETERS**

Made in USSR

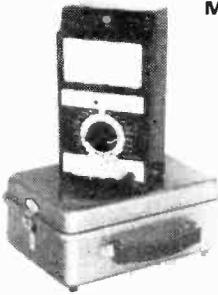

U4312: 41 ranges 0.3mA — 6A D.C., 1.5mA — 6A A.C., 0.3-900v A.C./D.C., 0.2-50kΩ; Mirror scale. Sensitivity 667Ω/v; Accuracy 1% D.C.; 1.5% A.C. £10.75.

U4313: 40 ranges 0.06mA — 1.5A D.C., 0.6-1.5A A.C.; 1.5-600v A.C./D.C., 0.06-60kΩ; Mirror scale. Sensitivity 20kΩ/v D.C., 2kΩ/v A.C. Accuracy 1.5% D.C., 2.5% A.C. £13.80.

U4315: 43 ranges 0.05mA-2.5A D.C.; 0.5mA-2.5A A.C.; 1-1000v D.C./A.C., 0.3-500kΩ; Sensitivity 20kΩ/v D.C., 2kΩ/v A.C. Accuracy 2.5% D.C., 4% A.C. £10.00.



U4324: 33 ranges 0.06mA — 3A D.C., 0.3mA — 3A A.C., 0.6-1200v D.C., 3-900v A.C., 0.5-500kΩ; Sensitivity 20,000Ω/v D.C., 4000Ω/v A.C. Accuracy 2.5% D.C., 4% A.C. Re-chargeable cadmium cell operation. £9.85.

**LINEAR I.C. AMPLIFIERS**

TAA263 — 3 stage low level amplifier. Bandwidth DC to 600kHz. Supply voltage 6-8V. Output power 10mW. TO 72 4-lead £0.65.

TAA293 — Med. freq. amplifier up to 600kHz. Supply voltage 6V. Output 10mW into 150Ω. TO 74 10-lead case £0.65.

TAA320 — Most stage followed by a bi-polar transistor. Gate-to-source voltage 9-14V. Power dissipation 200mW. Drain current 1μA. TO 18 3-lead £0.60.

**DIGITAL 7400 SERIES I.C.**


Made in USSR

7400	£0.14	7440	£0.14
7401	£0.14	7450	£0.14
7410	£0.14	7453	£0.14
7420	£0.14	7455	£0.14
7422	£0.20	7460	£0.14
7430	£0.14	7472	£0.30
		7474	£0.25

A minimum of 10 assorted I.C. must be ordered. Discount of 10% for any mix, up to 25 and 20% for larger quantities.

**OSCILLOSCOPE CI-5**

Made in USSR

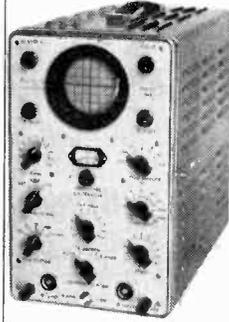


Extremely simple and easy to use single beam oscilloscope. Well proved design based on standard octal valves makes servicing and maintenance straightforward and inexpensive. Because of its bandwidth of 10 MHz the instrument is suitable for general electronic applications and educational purposes where a sophisticated instrument would be both too expensive and delicate. 3-in. tube giving a 50 x 50mm clear display. Amplitude and time base calibrations. Sensitivity 30mm/v max. Triggered and free-running time base, suitable for displaying pulses from 0.1μ sec. to 3 m sec. A.C. mains operation.

Price £44.00 ex. works

Packing and carriage (U.K. only £2.50)

**EDUCATIONAL METERS**

Made in USSR

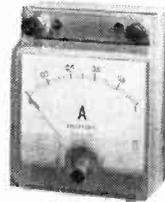

A range of small portable free-standing meters suitable for experiments and demonstration work. Moving coil movements with centre-pole pieces. 69mm long open scale. Basic calibration accuracy 4%. The following ranges are available: 1, 2, 5, 10 Amps D.C., 6, 15, 30 Volts D.C. Overall dimensions: 80 x 100 x 48mm.

Price £1.80 ex. works

Packing and postage £0.20 per meter

**SPECIAL TELEVISION BARGAINS**

**FIRST GRADE TRANSISTORS**

R2008B	£0.95
R2010B	£1.85
BU126	£1.55
BU133	£1.55
BU208	£2.00

Have you already got our illustrated 1975 catalogue / price list of valves, semiconductors, test equipment and passive components? If not, please send £0.20 for your copy now.

Prices are exclusive of VAT and unless stated otherwise, packing and postage. When remitting cash with order please add £0.80 per multimeter, or £0.20 in £ for other items, as well as VAT (25% for valves, semiconductors and linear I.C.s. and 8% for other equipment).

**Z & I AERO SERVICES LTD.**


Head Office: 44A WESTBOURNE GROVE, LONDON W2 5SF  
Tel.: 727 5641 Telex: 261306

Retail Branch:  
85 Tottenham Court Road  
London W1. Tel: 580 8403

WW—009 FOR FURTHER DETAILS

**RADFORD HD250**

High Definition Stereo Amplifier

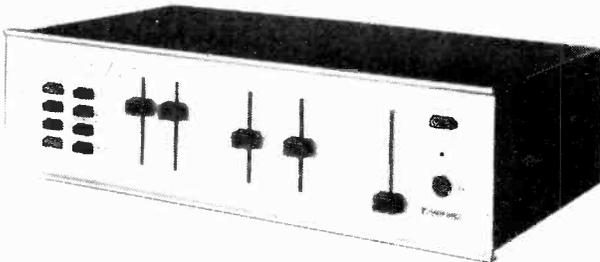

A new standard for sound reproduction in the home! We believe that no other amplifier in the world can match the overall specification of the HD250.

Rated power output: 50 watts av. continuous per channel into any impedance from 4 to 8 ohms, both channels driven.

Maximum power output: 90 watts av. per channel into 5 ohms.

Distortion, preamplifier: Virtually zero (cannot be identified or measured as it is below inherent circuit noise).

Distortion, power amplifier: Typically 0.006% at 25 watts, less than 0.02% at rated output (Typically 0.01% at 1 KHz)

Hum and noise: Disc.—83dBV measured flat with noise band width 23 KHz (ref 5mV); —88dBV "A" weighted (ref. 5mV)

Line —85 dBV measured flat (ref 100v)  
—88dBV "A" weighted (ref 100v)

Hear the HD250 at

**SWIFT OF WILMSLOW**

Dept. WW

5 Swan Street, Wilmslow, Cheshire (Tel. 26213)  
Mail Order and Personal Export enquiries: Wilmslow Audio, Swan Works, Bank Square, Wilmslow (Tel. 29599)

In stock: All Radford speaker drive units and crossovers, ZD22 preamp, Low Distortion oscillator L003 and Distortion Measuring set DMS3.

WW — 024 FOR FURTHER DETAILS

**SINCLAIR CALCULATORS**

Cambridge £9.95. Cam Mem £13.95. Scientific £13.95. Oxford 100 £9.95. Oxford 200 £14.95. Oxford 300 £22.98. Mains units (state model) £3.19.

**CBM CALCULATORS**

774D 7-digit 4 function model £5.99. 385R 8 digit rechargeable with charger £10.99. 8120D £20.95. SR9120D £26.95. SR6120R £35.95. SR4148R £43.95. Mains unit for D models £2.95.

**S-DECS AND T-DECS**

S-DeC £2.34  
T-DeC £4.15  
α-DeCA £4.55  
α-DeCB £7.85

IC carriers:  
16 dit: plain £1.18  
With socket £2.21  
10TDS: plain £1.09. With socket £2.08




**SINCLAIR IC20 AMPLIFIERS**

IC20 10+10W stereo amp. kit with free booklet and printed circuit £8.58.  
PZ20 power supply kit for above £5.91.  
VP20 volume, tone control and preamp kit including printed circuits £7.95.

SEND SAE FOR FREE DATA

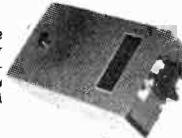**BATTERY ELIMINATORS**

**6-WAY SPECIAL**  
The most versatile battery eliminator ever offered. Switched output of 3, 4½, 6, 7½, 9 and 12V at 500mA £4.95.



**3-WAY MODEL**  
Switched output of 6, 7½ and 9V at 250 mA with unique 4 way jack plug and socket output connector £2.95.



**RADII MODELS**  
50mA with poppet battery terminals for radios, etc. 6V £2.95. 9V £4.05. Double 4½+4½V £3.95. 6+6V £3.95. 9+9V £4.43.




**CASSETTE MAINS UNITS**  
7½V output complete with 5-pin DIN plug to run cassette tape recorders from the AC mains £4.61.

**SINCLAIR PROJECT 80**

AFU £7.55 FM tuner £13.25  
Z40 £5.75 Stereo decoder £8.55  
Z60 £7.10 Trans. for PZ B £5.40  
Q16 £9.71 Stereo 80 £13.25  
PZ25 £6.50 Project 80 £34.95  
PZ6 £8.70. PZ8 £8.20

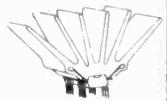**JC12 AMPLIFIER**

6W IC Audio amp with free data and printed circuit £2.80. Special offer: only £2.45 if bought with deluxe kit.



**DELUXE KIT FOR JC12**

Includes all parts for the pcb and vol. bass and treble controls for mono version £2.52. Stereo version with balance control £5.20.

**JC12 POWER KIT**

Supplies 28V 0.5 amp £4.77.

**JC12 PREAMP KITS**

Type 1, for magnetic pickups, mics and tuners. Mono model £2.15. Stereo £3.70. Type 2 for ceramic or crystal pickups. Mono £1.27. Stereo £2.33.

SEND SAE FOR FREE DATA

Prices include post and VAT. Official credit orders from schools, etc., welcome. No VAT charged on overseas orders. All prices are special offers.

**SWANLEY ELECTRONICS**  
P.O. BOX 68, SWANLEY, KENT BR8 8TQ


WW—033 FOR FURTHER DETAILS

# Appointments

Advertisements accepted up to 12 noon Monday, December 1st, for the January issue subject to space being available.

**DISPLAYED APPOINTMENTS VACANT:** £6.99 per single col. centimetre (min. 3cm).  
**LINE advertisements (run on):** 99p per line (approx. 7 words), minimum three lines.  
**BOX NUMBERS:** 40p extra. (Replies should be addressed to the Box numbers in the advertisement, c/o Wireless World, Dorset House, Stamford Street, London SE1 9LU).  
**PHONE:** Allan Petters on 01-261 8508 or 01-261 8423.

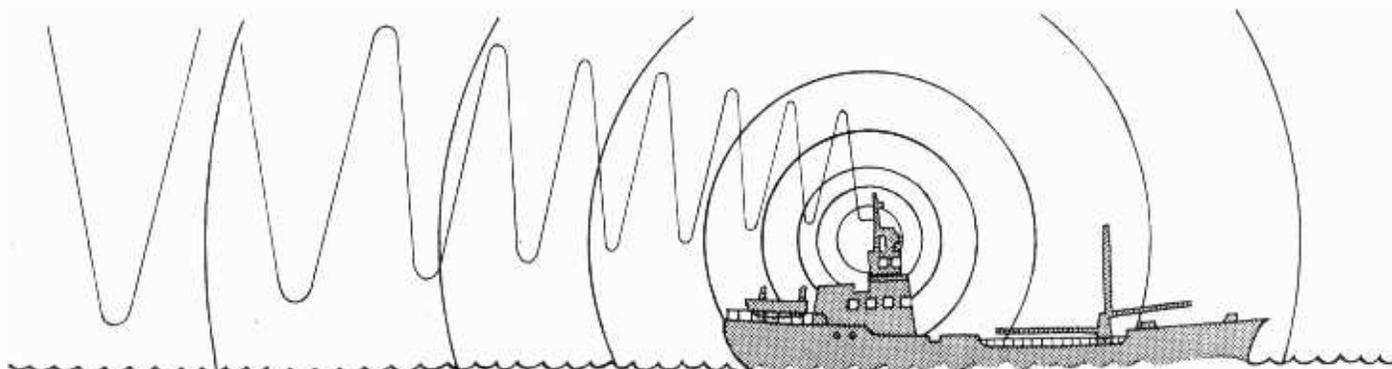*Classified Advertisement Rates are currently zero rated for the purpose of V.A.T*



## Radio Officers—now you can enjoy the comforts of home.

Working for the Post Office Maritime Services really makes sense. You still do the work that interests you, but with all the advantages of a shore-based job: more time to enjoy home life, job security and good money. To qualify, you need a United Kingdom Maritime Radiocommunication Operator's General Certificate or First Class Certificate of competence in Radiotelegraphy, or an equivalent certificate issued by a Commonwealth Administration or the Irish Republic.

Starting salaries, at 25 or over, are £2905 rising to £3704 after three years service. Between 19 and 24, the starting salary varies from £2234 to £2627

according to age. You'll also receive an allowance for shift duties which at the maximum of the scale averages £900 a year and there are opportunities to earn overtime. There's a good pension scheme, sick pay benefits and prospects of promotion to senior management.

Right now we have vacancies at some of our coastal radio stations, so if you're 19 or over, write to: ETE Maritime Radio Services Division (R/B/12), ET 17.1.1.2., Room 643, Union House, St. Martins-le-Grand, London EC1A 1AR.

Post Office Telecommunications

UNIVERSITY OF ST. ANDREWS  
 Department of Psychology


### TECHNICIAN GRADE 5 (ELECTRONICS)

Applications are invited for the above post in the Electronics Workshop of the Psychology Department tenable from November, 1975. Applicants should have a good electronics background together with practical experience in the development and construction of digital equipment and the design of computer interfaces.

The person appointed will work together with other members of the technical staff on the development of on-line experimental facilities using the Department's Data General computers. Experience with small general purpose digital computers and a knowledge of programming languages is desirable. The duties will also involve the use and maintenance of other electronic equipment in the Department.

Salary on scale £2439 - £2895. Applications, with full details of career to date, and the names of two referees, should be sent to the Establishment Officer, of the University, College Gate, St. Andrews, Fife, by 21st November, 1975.

(4970)

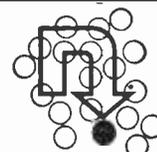

### Opportunities in the ELECTRONICS FIELD

Men with analogue or digital qualifications / experience seeking higher paid posts in: TEST - SERVICE - DESIGN - SALES

Phone: Mike Gernat, Ref. W.W.

**NEWMAN APPOINTMENTS**  
 360 Oxford Street, W.1.  
 01-629 0501

(94)

## ENGINEERS

### Electronic Instruments

W. LONDON

#### PRODUCT SUPPORT ENGINEER

£3,500 + car + comm.

Essentially a sales orientated position covering the UK. The successful applicant should be able to do a service engineer's job, but will concentrate on product applications, interfacing of systems etc., with existing technical staff.

Formal qualifications are not required, but an HNC or equivalent in Electronic Engineering is desirable, as is a knowledge and experience of signal analysis, nuclear and automatic isotope counting techniques. Age range 20's to 30's

#### SERVICE ENGINEER

£3,000 + car + comm.

To cover over 50 client installations — mainly hospitals and universities — in the London area. You need technical product and applications knowledge and at least two years' experience of servicing scientific instruments in a laboratory environment. Ideally, applicants should have experience in fast digital pulse techniques, isotope counting techniques or computer based systems. Age range 25-40.

Telephone Valerie Jenner  
London (01) 235 7030 Ext. 221

**PER** PROFESSIONAL  
and EXECUTIVE  
RECRUITMENT

Rediffusion Reditune Ltd., Britain's leading background music service, require the following technical staff:

## PRODUCTION LIAISON ENGINEER

Duties involve quality control and inspection of both incoming and outgoing goods.

Applicants should preferably have an HNC or equivalent and not less than 5 years' experience in industry. An interest in music is essential.

## LABORATORY TECHNICIAN

A wide variety of duties include layout drawing, construction and test of prototype printed circuits. The person envisaged is young and enthusiastic with ONC or equivalent, and some industrial experience in the audio field.

The positions, which are pensionable, are based at Orpington, where a 37½-hour week is worked.

There is a subsidised canteen and annual holidays are 3 weeks and 3 days.

The salaries are negotiable according to age and experience.

Please apply to:

Personnel Manager  
Rediffusion Reditune Limited  
Cray Avenue  
Orpington  
Kent

(5005)

## PIONEER®

Shiro (UK) Limited are leaders in the field of advanced, high fidelity equipment with their superior "Pioneer" range.

To keep pace with our continued expansion in this all important growth market we now require the following qualified engineers.

### SENIOR AUDIO ENGINEERS

The people we are looking for will have a sound experienced background in hi-fi servicing, dealing with our wide range of audio products. This is interesting and well paid work for people with potential.

### COLOUR TV AND VCR ENGINEERS

As part of our new expansion, we are introducing new lines to our already extensive range. These will include the Loewe-Opta range of colour televisions and video cassette recorders: and to help service this range we require a highly experienced VCR and CTV Engineer, with 3-5 years' relevant experience, preferably qualified to HNC (Elec.) or equivalent. It is a responsible post as he will be taking charge of this new division.

We also require another engineer to work with him on this range.

For an experienced and competent person, this position is ideal for progression in this challenging new area.

For all the above vacancies we offer:-

- ★ Excellent negotiable salaries
- ★ 37½-hour week
- ★ 3 weeks' paid holiday
- ★ LVs
- ★ Special staff discount scheme

Apply to: **The Service Manager, Shiro (UK) Limited, Shiro House, The Ridgeway, IVER, Bucks SL0 9JL.**

Tel: Iver 652222.

5019



## MEDICAL PHYSICS TECHNICIAN GRADE IV

### Area Medical Physics Department

Required for duties in the INTENSIVE CARE UNIT and in the wards primarily at Leicester General Hospital.

The work involves close contact with patients. It will include care, use and maintenance of intensive care equipment and sophisticated monitoring systems both in the Unit and throughout the hospital.

A technician qualified ONC/HNC (Electronics) will be required. Experience whilst desirable is not essential, as training in this aspect of work will be provided.

Salary: Technician IV, £2346-£3267. New entrants would normally start at minimum.

Applications stating age, qualifications and previous experience together with the names of two referees to the **Sector Administrator, Leicester General Hospital, Gwendolen Road, Leicester LE5 4PW.**  
Closing date: 24th November, 1975

5013



**Leicestershire  
Health Service**

LEICESTERSHIRE AREA HEALTH AUTHORITY (TEACHING)

# Area Sales Manager

**Challenge and  
opportunity with an  
international leader  
in T.V. Broadcast  
Equipment.**



Pye TVT Ltd., world-wide supplier of professional broadcasting equipment, has a vacancy in the Sales Department for an Area Sales Manager.

The position, which calls for an extensive knowledge of TV broadcasting, and colour cameras in particular, involves the marketing of a wide range of products including cameras, video and audio switchers and mixers, pulse and distribution equipment and complete outside broadcast vehicles. Essential requirements will be the ability to discuss the products at an appropriate technical level with existing and potential customers; the preparation of comprehensive quotations and approval of complex specifications; liaison with other departments and companies within the Pye and Philips groups – in short, someone who can make a major contribution to our marketing programme.

We shall expect the successful candidate to be of HNC or equivalent educational standard.

The position, based in Cambridge, offers many opportunities for travelling in the U.K. and, occasionally, abroad. A company car will be provided.

In addition to a very competitive salary, there is a company pension scheme and a wide range of fringe benefits, including relocation expenses in approved cases.

Applications, giving brief details, should be sent to:

Mrs. J.A. Macnab, Personnel Manager,  
Pye TVT Limited, Coldhams Lane,  
Cambridge CB1 3JU.



**Pye TVT Ltd**

Pye TVT Ltd., Coldhams Lane, Cambridge CB13JU  
Tel. Cambridge (0223) 451115. Telex: 81103

A member of the Pye of Cambridge Group

## G.R. INTERNATIONAL ELECTRONICS LTD.

requires

# AUDIO TEST and SERVICE ENGINEERS and TESTERS

The Company, currently 300 strong and embarked on a programme of expansion, is based in one of the most attractive parts of Central Scotland. It is seeking experienced test engineers and testers to become members of or to take control of a number of production test, fault-finding and repair sections concerned with a variety of projects but with particular emphasis on consumer audio products.

Applicants for the more senior positions should ideally possess appropriate technical qualifications and be capable of giving assistance in maintenance and calibration of special purpose test equipment, but the Company considers the principal necessities to be relevant practical experience coupled with enthusiasm and integrity. There are exceptionally good prospects of advancement for hard-working and ambitious people, particularly for anyone able to contribute ideas on future test equipment to be designed in-house.

Current technical capabilities and experience of applicants will obviously be taken into account in offering initial appointments, but the opportunities described will be open to all.

The social and sporting amenities and general living environment of Perth are outstanding and the Company offers assistance with rehousing and payment of all removal costs.

Good wages and salaries are offered, consistent with age, experience and responsibilities.

Please apply in writing for interview, giving details of age, marital status, qualification (if any), experience to date and current salary to:

**Mr. J. Bandeen, Executive Director (Administration)**  
**G.R. International Electronics Ltd.**  
**Almondbank, Perthshire, PH1 3NQ**  
Interview expenses would be fully reimbursed

(4984)

**Birmingham Area Health Authority (Teaching)**  
**Central Birmingham Health District**  
**BIRMINGHAM MATERNITY HOSPITAL**  
**Queen Elizabeth Medical Centre**

## Senior Electronics Technician

to work with Senior Physicist and Electronics Technician in well-equipped laboratory in Department of Medical Physics and Biomedical Engineering.

Duties will be concerned with servicing, calibration, design and construction of electronic equipment used in obstetrics, paediatrics and associated laboratories.

Applicants should possess O.N.C., H.N.C. or equivalent qualification together with some experience of analogue and digital circuit techniques, preferably in the medical field.

Salary Scale (Medical Physics Technician Grade III)  
£2,931-£3,834.

Please write to the Personnel Officer, Queen Elizabeth Hospital, Edgbaston, Birmingham 15, for further particulars and application forms.

4993

## The Polytechnic of North London

Department of Chemistry

Applications are invited for the following appointment:

### Laboratory Technician (Grade 4)

required immediately by the spectroscopy laboratories of the Department. The main duties will involve the maintenance and development of electronic instrumentation. Applicants should have practical experience in electronics but specific knowledge of spectroscopic instruments is not essential.

Normally candidates should hold C & G/IST Ordinary Certificate, ONC or C & G Part 2 (or equivalent) in Electronics subjects, and have seven years' experience.

Salary Scale: Grade 4 £2247-£2628 plus £411 London Allowance.

Apply for further details and application form to the Head of the Department of Chemistry, The Polytechnic of North London, Holloway Road, London, N7 8DB.

## THE NATIONAL THEATRE on the South Bank

Required for maintenance of control systems for hoists, revolves and stage lighting, all using new computer technology.

### ASSISTANT SYSTEMS ENGINEER

Knowledge of electro-mechanical and audio is an advantage.

Write now with full details to: Dept. W/W12 Building Services, The National Theatre, Upper Ground, South Bank, London, SE1 9PX. 5004

University of Reading

## ELECTRONICS TECHNICIAN

required in the Department of Chemistry. Duties include the maintenance of a very wide range of electronic instruments and help with the design and construction of electronic devices. Salary in scale £2,439-£2,895 p.a. (under revision).

Apply in writing, quoting Ref. T.48A, with full details and names of two referees, to Assistant Bursar (Personnel), University of Reading, Whiteknights, Reading RG6 2AH.

(4978)

DEPARTMENT OF PSYCHOLOGY  
UNIVERSITY OF GLASGOW

Applications are invited for the post of

### ELECTRONICS TECHNICIAN

Experience with the design of Digital Circuitry essential, and experience with NOVA-line Computers desirable. Grade and salary negotiable. Apply Head of Department of Psychology. (4956)


*Looking  
for  
a  
new  
job?*

## Perhaps we can help!

We have regular contact with hundreds of electronics and electrical companies needing qualified electronics engineers and technicians and TV service engineers.

We can, therefore, help you to find an interesting and well paid job. All you need to do is to return the coupon below or give us a ring. Our service is confidential and costs you nothing.

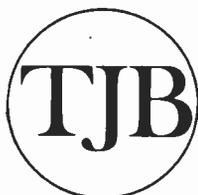**TJB Technical Services Bureau,  
3A South Bar,  
Banbury, Oxfordshire.  
Banbury (0295) 53529**



Technical Services Bureau is a division of Technical & Executive Personnel Ltd and is solely concerned with job placement in the Electronics and Electrical Industries

Please send me an "Application for Registration" form

NAME .....

ADDRESS .....

.....

..... 4992

### HER MAJESTY'S GOVERNMENT COMMUNICATIONS CENTRE

HANSLOPE PARK, MILTON KEYNES MK19 7BH

has vacancies in the following fields of R & D work:

- (a) VHF/UHF COMMUNICATIONS EQUIPMENT DESIGN
- (b) ACOUSTICS
- (c) MICROWAVE COMMUNICATION SYSTEMS
- (d) GENERAL CIRCUIT DESIGN — ANALOGUE, DIGITAL
- (e) STATISTICS/OPERATIONAL ANALYSIS
- (f) RELIABILITY — FROM COMPONENTS TO OVERALL SYSTEMS
- (g) SMALL SCALE MECHANICAL ENGINEERING — HYDRAULICS/SMALL MECHANISMS

Post (e) will be in London and will attract London allowance of £410 p.a. Appointments will be made within the grades of:

### Scientific Officer

£2149-£3527 (Candidates under age 27)

- Qualifications:-
- (a) Scientific or Engineering Degree
  - or (b) Degree standard membership of a Professional Institution
  - or (c) HNC or HND in a scientific or engineering subject or equivalent qualification.

### Higher Scientific Officer

£3254-£4454 (Candidates under age 30)

Qualifications: As for Scientific Officer, with the following experience since qualifying:

- (a) Candidates with 1st or 2nd class honours degree or equivalent qualifications — at least 2 years post graduate experience.
- or
- (b) Other Candidates — at least 5 years of appropriate experience.

### Senior Scientific Officer

£4185-£5778 (Candidates at least age 25 and under age 32)

Posts (c) and (e) only.

Qualifications: 1st or 2nd class honours degree in a scientific subject and a minimum of 4 years appropriate post-graduate experience.

For further details and application form please write to:

Administration Officer  
HM Government Communications Centre  
Hanslope Park  
Hanslope  
MILTON KEYNES MK19 7BH

## Engineers — Telecommunications Link Equipment

powerful prospects, extensive benefits

Compare this with your present circumstances. This Company has a remarkable on-going growth record in home and export markets. And consequently, a history of continuing internal promotion. The salaries must interest you, and the benefits package comes complete with flexible hours and generous relocation assistance to a most attractive country town.

Experience of low/medium capacity multiplex bearer equipment up to 2GHz and/or in higher frequency RF techniques is the major requirement for:

### Senior Electronics Designers

Complete involvement from basic development through to responsibility for manufacturing continuity with particular emphasis on specific custom design and engineering of medium capacity multiplex systems. Necessary experience level is around 6 years and experience of RF techniques above 2GHz is helpful.

### Systems Engineers

To plan, quote for and engineer communications systems (particularly link equipment) at all project stages. Involvement in total system planning and implementation makes this unusually attractive.

### Senior Development Engineers

To join the link development team you should preferably have BSc, HND or HNC and 3 years related experience, although if you have less experience you should still apply. Useful experience would be on IF and RF filter design or base-band supervisory techniques.

Please write initially with brief details and in strict confidence, to

**Alan Wellbrook, Bartlett Jeffress  
Advertising Ltd., 23/28 Fleet Street,  
London EC4Y 1NE**

Please indicate any company to whom you do not wish to apply.



## ENGINEERING DESIGNS DEPARTMENT

A number of posts are available in Central London for enthusiastic and forward thinking young students to train as

## TECHNICIANS

in the laboratories of the BBC's Designs Department. Their work will include assisting engineering and laboratory staff in the development, construction and testing of units of sound and television broadcasting equipment.

The successful candidates will probably be aged 18-20 and have a keen interest in, and possibly some experience of, electronics.

They will have some 'O' levels — two preferably will be scientific — and they will be either recently qualified to ONC or C & G Part II standard or have recently started the final year of such a course. Day release to complete the course will be given. Subsequent training to IEEET standard is by full-time BBC courses at its Engineering Training Centre.

The salary offered would depend upon experience and qualification on appointment and would be between £2202 p.a. and £2394 p.a. It would also rise by £96 p.a. to a maximum of £2682 p.a. Salaries under review. Satisfactory trainees could expect to be selected within two years for more senior Laboratory Technician posts.

Requests for further information and application forms to The Engineering Recruitment Officer, BBC, Broadcasting House, London W1A 1AA, quoting reference 75.E.4056.WW, and enclosing addressed foolscap envelope. Application forms to be returned by 14 days after publication.

(4958)



**CAPITAL  
APPOINTMENTS LTD**

## FIELD SERVICE ENGINEERS (ELECTRONICS)

If you're not earning over **£3,500** p.a. plus a car — then you had better contact us! (4982)

**34 Percy Street, London, W.1  
01-636 9659 (day) or  
550 0836 (evg.)**

## THE UNIVERSITY OF HULL TECHNICAL MANAGER

Audio Visual Centre  
(Re-Advertisement)

Applications are invited for the above post. The Audio Visual Centre is a central academic service unit with some teaching responsibilities and comprises sophisticated, broadcast standard, television and sound studios, a distribution system and a busy VTR suite, a film unit and the usual A.V. activities.

Scale: National Salary Scale for academic-related staff Grade II, £4932-£6134 (under review).

Applications (four copies) giving details of age, qualifications and experience, together with the names of three referees, should be sent by 1st December, 1975, to the Registrar, The University of Hull, Hull HU6 7RX, from whom further particulars may be obtained.

5008

## CITY OF LONDON POLYTECHNIC

## ELECTRONICS TECHNICIAN I

GRADE 3

The person appointed would be involved with the development and construction of electronic equipment for teaching and research purposes, together with some servicing and maintenance of existing apparatus. Applicants should be familiar with standard test equipment and its uses, and hold relevant qualification in electronics.

Salary scale: £2,424 to £2,754 including London Allowance.

Further information on the above post can be obtained by an application in writing to the Head of Department of Psychology, City of London Polytechnic, Calcutta House, Old Castle Street, London, E1 7NT.

5017

## THE UNIVERSITY OF LIVERPOOL DEPARTMENT OF PHYSICS VAN DE GRAAFF OPERATOR

OPERATOR required to assist with running a 12 MeV Tandem Van de Graaff Accelerator. Candidates must possess an HNC, Final C. & G. or equivalent qualification. Practical experience of installation and maintenance of one of the following is essential: Electrical machinery, electrical equipment, vacuum systems. Salary on the scale £2,439-£2,895 p.a. (under review), plus a bonus for shift work (at present 30%). Application forms can be obtained from the Registrar, The University, P.O. Box 147, LIVERPOOL, L69 3BX. Quote Ref. RV/612/WW. (4977)

## MEDICAL LINEAR ACCELERATORS WILL TAKE YOU ROUND THE WORLD!

In its role as the professional electronic equipment division of the International Philips Group, the MEL Equipment Company Limited produces advanced linear accelerators for use in the treatment of cancer.

The SL 75 series is the latest development in a successful line of accelerators which are installed in major hospitals throughout the world.

Our continued success in gaining new markets has led to an expansion in our team of

## SERVICE AND INSTALLATION ENGINEERS

who will be engaged in the installation and technical support of the accelerators and associated equipment both at home and abroad.

We are looking for adaptable self-reliant engineers who are prepared to spend periods of up to approximately 3 months overseas. The successful candidates will have a good knowledge of semi-conductors circuitry, be qualified to at least ONC standard and will preferably have worked on such equipment as modern high-power radar systems.

The company offers a progressive salary, bonus and pension scheme, generous expenses and at least 4 weeks 3 days holiday. Assistance in moving to Crawley will be given if appropriate.

Please write or telephone for an application form (quoting ref no WW/44), to Diana Hill, Personnel Officer, The MEL Equipment Company Limited, Manor Royal, Crawley, Sussex. Tel; Crawley 28787.

(4979)

**MEL**

**Royal Holloway College  
(University of London)  
Egham Hill, Egham, Surrey**

### EXPERIENCED ELECTRONICS TECHNICIAN (GRADE 4)

required in the Physics Department for one year only, preferably with experience in digital and computer electronics. Salary on the scale £2,247-£2,628 plus £260 London allowance.

Applications, together with the names and addresses of two referees, should be sent to the Personnel Officer (WW) as soon as possible. (4971)

### SERVICE ENGINEER MEDICAL ELECTRONICS

Based at our office in Crawley, Sussex. To service Medical Ultrasonic Diagnostic equipment in our own workshops and in hospitals throughout the U.K. The post carries a very high degree of responsibility with an appropriate salary. Application for an interview in writing quoting brief career details to: The Managing Director, Kretztechnik (U.K.) Limited, Alpine Works, Oak Road, Crawley, Sussex (4951)

### MECHANICAL DESIGN/DRAUGHTSMAN

A senior Design Draughtsman is required preferably having experience in the radio communications field.

The work involves design and development of portable and mobile radio type equipment and a knowledge of drawing office practice and procedures is essential. Qualifications to HNC level or equivalent would be an advantage.

### DESIGN LABORATORY TECHNICIAN


A position exists for a Technician in the Design Engineering Laboratory. Duties would cover the various tasks necessary in the day-to-day running of a laboratory, but the primary function would be to give technical support to the team engaged in design projects.

The salaries and benefits offered for these posts reflect the best of modern practice. Assistance with housing relocation will be offered to the successful applicants if applicable.

Please apply in writing, giving brief details of qualifications and experience, or telephone for an application form to:

The Personnel Manager, Motorola Limited, Chesford Grange, Warrington, Cheshire, WA1 4RG. Tel. Warrington 52306. (4981)

**MOTOROLA  
COMMUNICATIONS  
DIVISION**

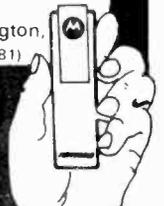

## R & D. IN TELECOMMUNICATIONS & NIGHT VIEWING SYSTEMS

### — Fresh opportunities for Scientists and Engineers

The Signal Research and Development Establishment, situated near Christchurch, Dorset, is concerned with a wide range of development work in the growth subjects of telecommunications and night viewing systems. Although the work is done mainly to satisfy Ministry of Defence needs, some of the developments also have important civil applications.

To help continue its advanced and challenging work, the establishment currently needs Scientists and Engineers in the following fields:—

- ★ Dedicated computer applications: switching and control of multi-connected communications networks, including research into software structure.
- ★ Assessment and mathematical modelling: communications and electro-optical systems for night vision.
- ★ Applications of microprocessors: data transmission and communication terminals.
- ★ Man/system interface: communications and night vision.
- ★ Electromagnetic theory: vehicular aeriels and multipath propagation.

Candidates should normally have a good honours degree or equivalent in an appropriate scientific or engineering subject and be aged under 32. Appointments will be as Senior Scientific Officers (over £4,180 to £5,775), Higher Scientific Officers (£3,250 to £4,450) or Scientific Officers (2,150 to £3,525), according to age, qualifications and experience.

For further details, conditions of service, and an application form (to be returned by 5 December, 1975), please write to J. R. Mills, Signals Research Establishment, Christchurch, Dorset, or telephone the Personnel Officer on 042-52 71311. Please quote SA/3/FEA.



SIGNALS RESEARCH & DEVELOPMENT ESTABLISHMENT, CHRISTCHURCH, DORSET

(4915)

# AIRFIELD NAVAIDS

## Training courses starting soon

IAL is a world leader in communications and aviation services and we will be running a series of UK training courses in the New Year to meet our expanding overseas commitments. Successful completion will lead to interesting, highly-paid postings abroad and opportunities to expand with the company.

To qualify for a place on the course, you should have several years' experience in the maintenance and operation of ILS, VOR and DME, together with a knowledge of associated ground-to-

air communications systems. We offer attractive tax-free salaries overseas and additional benefits include free furnished accommodation; an excellent pension scheme; opportunities for accompanied postings; education/child allowance. The next course starts January 5th, 1976. Secure your place by contacting the Senior Recruitment Engineer, International Aeradio Limited, Aeradio House, Hayes Road,



Southall, Middlesex  
Telephone: 01-571 1808 or 01-571 0678.

4996

### GUY'S HOSPITAL MEDICAL PHYSICS TECHNICIANS Grade II and Grade IV Department of Clinical Physics and Bioengineering

The Grade II Technician is a member of a team of Physicists and Technicians engaged in a variety of clinical instrumentation projects. ONC/HNC or higher qualification required together with 2 years' electronics experience in Technician Grade III or other relevant technical experience. Salary from £3,558-£4,581 plus £312 London Weighting.

The Grade IV Technician will be engaged upon maintenance, repair and calibration of a wide range of electro-medical equipment. Candidates should have 2 'A' levels plus technical experience OR City and Guilds OR an ONC Science Laboratory Technician Certificate. Salary £2,346 - 3,267 plus £312 London Weighting

Apply to Personnel, Guy's Hospital, London SE1 9RT. Telephone 01-407 7600 Extn. 3462.

(4967)

### UNIVERSITY OF LEICESTER

## ELECTRONICS TECHNICIAN

(Grade 5)

Required for the Department of Chemistry. The person appointed will be required to work on the design and development of electronic apparatus for use in teaching and research laboratories and the modification and maintenance of a variety of existing electronic equipment. A knowledge of data logging and digital equipment would be useful.

Good conditions of appointment including generous holidays, superannuation and sick leave schemes. Salary (under review) not less than £2439 p.a. rising to £2895 p.a. Subject to qualifications and/or practical experience an appointment can be made above the minimum of the scale.

Applications in writing should be sent as soon as possible to Professor R. D. Peacock, Department of Chemistry, The University, Leicester LE1 7RH

(4956)

**SOUND & VIDEO TECHNICIAN REQUIRED.** We are AV Distributors (London) Limited importers and distributors of cine camera and projectors, sound recorders and video equipment. We are situated in close proximity to Baker Street Tube and Main Line Station as well as Marylebone Station. We offer amicable working conditions, good salary, holidays honoured, flexible hours and air conditioned premises. We would like to hear from you. Please contact Mrs Schlaen on 01-935 8161. AV Distributors (London) Limited, 26 Park Road, Baker Street, London NW1 4SH. (4965)

**ELECTRICAL / ELECTRONIC ENGINEERS & MECHANICAL ENGINEERS** are required by company engaged in shock and vibration physics, pneumatics, hydraulics, electronics, control systems, instrumentation design and use and non-destructive testing. Applicants must be aged between 22 and 30, qualified to HNC or equivalent. Must have willingness to accept challenging work, learn other disciplines and perform field work for limited periods. Write to Dr. Savage, Search Engineering Ltd., Unit 19, Randalls Road Estate, Leatherhead, Surrey. (4961)

**ROYAL FREE HOSPITAL SCHOOL OF MEDICINE** (University of London). A CCTV engineer is required to supervise installation and operation of a new recording and distribution service in the new Royal Free Hospital, Hampstead. A substantial part of the work will be in colour and the system will ultimately include full studio facilities when all building phases are complete. HNC or equivalent qualifications desirable. Salary in range of IMLT Technician £2,511-£3,738 plus London Weighting of £312, but initial salary will not exceed £3,102 gross. Apply in writing with names of two referees to Professor H. A. B. Simons, Department of Medical Physics, Royal Free Hospital, Pond Street, London NW3 2QG. (4959)

**UNIVERSITY OF SUSSEX**

**SCHOOL OF MOLECULAR SCIENCES  
ELECTRONICS ENGINEER**

To carry out repairs and construction of electronic circuitry connected with analytical equipment. Preference will be given to applicants having sound knowledge and experience of logic circuits. Some knowledge of conventional circuit fault clearing is also required. Applicants must have had a minimum of three years' practical experience and hold a City and Guilds Full Technological certificate or equivalent.

Salary is within the range £2439-£2895 per annum (under review) Sixteen days' holiday plus University closures at Christmas and Easter; superannuation and sickness benefit schemes.

Applications giving full details of experience and qualifications to Mr. P. J. Gilliver, Laboratory Superintendent, School of Molecular Sciences, University of Sussex, Falmer, BRIGHTON BN1 9QJ.

5007

**ELECTRONIC ENGINEER**

Young man (18-22) with experience of Digital Logic required to work on Electronic Display & Printing Calculators and Electronic Cash Registers.

Phone: 01-580 1614 or write:  
J. Norman

Geller Business Equipment Ltd.  
15 Percy Street, London, W1

5009

**ARTICLES FOR SALE**

**COLOUR, UHF and TV SPARES.** Colour and UHF lists available on request. New cross hatch kit Ancl Sync and UHF Modulator units aerial in-put type £11 p&p 45p. CRT reactivator kit for colour and mono £16.80 p&p 60p. Signal strength meter kit £18.00. P/P 45p. 625 TV. IF unit, suitable for Hi-Fi amp or tape recording, £6.75 P/P 35p. Bush CTV 25. New convergence panels plus yoke and blue lat., £3.85. P/P 40p. New Philips single standard convergence panels complete, incl. 16 controls, coils, P.B. switches, leads £3.75 P/P 50p. New Colour Scan Coils, Mullard or Plessey plus convergence yoke and blue lateral, £9.20. P/P 55p. Mullard AT 1023/05 Convergence Yoke £2.30 p/p 50p. Mullard or Plessey Blue Laterals, 75p P/P 20p. BRC 3000 type Scan Coils, £2.00 P/P 40p. Delay Lines DL20, £3.50, DLIE, DLI, £1.00, P/P 35p. Lum Delay Lines, 50p, P/P 15p. EHT Colour Quadrupler for Bush Murphy CTV 25 111/174 series, £7.50. P/P 60p. ERT. Colour Tripler ITT TH25/1TH suitable most sets, £2.00 P/P 35p. GEC 2040 colour tripler £1.75 P/P 35p. Colour surplus/salvaged Philips G8 panels part complete; Decoder, £2.50. IF incl. 5 modules, £2.25. T. Base, £1.00. P/P 25p. CRT base, 75p, P/P 15p. GEC 2040 panels, for spares Decoder £3.50, Time Base £1.00 P/P 50p. B9D valve bases 10p, P/P 6p. VARICAP TUNERS. UHF ELC 1043 NEW, £4.20. ELC1043/05 £5.00. ELC1042 (VHF) £5.50. Salvaged VHF and UHF Varicap tuners, £1.40, P/P 25p. UHF TUNERS NEW, Transistorised. Incl. slow motion drive, £3.80. 4 position and 6 pos. push-button transistorised £4.20. P/P 45p. Philips, Bush, Decca, Integrated UHF/VHF transd tuners £4.50 P/P 60p. Murphy 600/700series com. UHF conversion kits incl. tuner, drive assy, 625 IF amplifier, 7 valves, access., housed in cabinet plinth assembly, £5.50 P/P 65p. THORN 850 Dual standard time base panel. 50p, P/P 50p. PHILIPS 625 IF amplifier panel incl. cct., 50p P/P 45p. VHF turret tuners AT7650 incl. valves for K.B. Featherlight, Philips 19TG170, GEC 2010, etc., £2.50. PYE miniature incremental for 110 to 830, Pam and Invicta, £1.00. A.B. miniature with UHF injection suitable K.B. Baird, Ferguson, 75p. New fireball tuners Ferguson, HMV, Marconi, £1.00 P/P all tuners 50p. Mullard 110° mono scan coils, new suitable all standard Philips, Stella, Pye, Ekco, Ferranti, Invicta, £2.00, P/P 35p. Large selection LOPTS, FOPTS available for most popular makes. 200+200+100 MFD 350v Electrolytic, £1.00 P/P 20p. MANOR SUPPLIES 172 WEST END LANE, LONDON, N.W.6. Shop premises, callers welcome. (No. 28, 59, 159 Buses or W. Hampstead Bakerloo and Brit. Rail). MAIL ORDER: 64 GOLDERMANOR DRIVE, LONDON, N.W.11. Tel. 01-794 8751. VAT PLEASE ADD 25% TO ALL PRICES.

## TELEVISION ENGINEERS

Doric Radio is a fast growing member of the Rediffusion group of companies, selling monochrome and colour T.V. receivers to the retail trade through an increasing network of dealers. A small but effective team is being established to provide a technical service to our customers at home and overseas. This team provides service back up facilities by direct contact with our Doric dealers, helping to solve their problems and completing the link back to our factories where necessary.

Attitude, ability, thoroughness, tact and a willingness to get involved are essential requirements for these positions. This is a challenging opportunity for experienced engineers who wish to become important members of a small successful team working on the latest receivers employing advanced electronic techniques. Prospects for promotion are excellent. Formal qualifications, whilst desirable, are not essential where adequate practical experience on modern colour television receivers can be demonstrated.

Successful applicants will be based at our Chessington laboratories, with their excellent facilities and equipment, but occasional visits to our factories in the North of England and to our dealers' premises, both at home and abroad, may be necessary.

Salaries will depend on ability and experience, but will reflect the importance of these new posts. Assistance with relocation expenses will be given where appropriate.

Interested? then write to:-

H. Brearley,  
Head of Technical Services,  
Doric Radio Ltd.,  
Fullers Way South,  
Chessington,  
Surrey. KT9 1HJ.  
Telephone 01-397-5411



## DORIC RADIO

5012

## DESIGN/DEVELOPMENT/TEST ENGINEER

An Engineer is required for the development, design and testing to B.S.S. of audio equipment. The ideal candidate should have qualifications to HND or degree level and should have a number of years' relevant experience in this type of work and industry. Salary by negotiation, depending on qualifications and experience.

Reply stating present salary to: **The Personnel Manager  
J. Parker & Company (London) Limited  
Parker House, 1 Beresford Avenue, Wembley, Middx. HA0 1YX**

(4976)

**ARTICLES FOR SALE**

**DIGITAL CLOCK CHIP, AY-5-1224,** with data and circuit diagram £3.66 plus VAT, 'Jumbo' LED digits (16mm high) type economy DL747 only £2.04 each plus VAT, post free. Greenbank Electronics, 94 New Chester Road, Wirral Merseyside L62 5AG. (83)

**LADDERS** unvarnished 14ft lin. closed, 25ft 4in extd. £21.40 delivered. Tel: Telford 586644. (16)

**16MM B & H 631** Sound projectors c/w speaker and transformers £135. — Hilton Cine, 9 West Hill, Dartford - T. 20009. (15)

**C.R.T. REGUNNING PLANT.** New and second-hand reconditioned training, demonstration, colour or B/W. Barretts, Mayo Road, Croydon, Surrey, CRO 2QP. (36)

**LOW COST IC MOUNTING.** Use Soldercon IC socket pins for 8 to 40 pin DILs, 70p (plus 5p VAT) for strip or 100 pins, £1.50 (plus 12p VAT) for 3 strips of 100, £4 (plus 32p VAT) for 1,000. Instructions supplied. Send for sample. Sintel, 53c Aston Street, Oxford. Tel: 0865 43203. (67)

**VACUUM** is our speciality, new and second-hand rotary pumps, diffusion outfits, accessories, coaters, etc. Silicone rubber or varnish outgassing equipment from £40. V. N. Barrett (Sales) Ltd., 1 Mayo Road, Croydon. 01-684 9917. (24)

**SURPLUS TEST EQUIPMENT AND RADIO AMATEUR GEAR.** Bench power supplies 200/400 v. Precision millivolt meters, chart recorders. Vanguard, Cambridges, etc., etc. recorder standards room equipment. B&H COMPONENT LTD., Dept. WW, Leighton Electronics Centre, 59 North Street, Leighton Buzzard, Beds, LU7 7EG. (05253 2316). (49)

# AIRFIELD ILS TRAINING

## Course starts early January

If you've a sound technical background in Airfield Radio and Navigation Aids and preferably knowledge of ILS, this training will bring you up-to-date for a highly rewarding position in Saudi Arabia.

On successful completion you will qualify for a 2½ year Lockheed contract. That means £4500+ p.a. and attractive end of contract

bonus — both free of local tax. Free accommodation and generous home leave. *Act NOW to make sure of your place* — 'phone our Senior Recruitment Engineer on **01-571 1808 or 01-571 0678.**

If you can't 'phone, write to the Senior Recruitment Engineer, International Aeradio Limited, Aeradio House, Hayes Road, Southall, Middlesex.



## LABORATORY TECHNICIANS

### Equipment Dept. W. London

Interesting work testing new electronic equipment made by the BBC for its colour television and stereo radio services, involving analogue and digital techniques over a frequency range from D.C. to U.H.F.

Qualifications O.N.D., O.N.C., or C. & G. Part II in Telecommunications or Electrical Technician certificate. Initial salary range normally £2514 to £2706 rising to £3339. Good opportunities for promotion to Senior Laboratory and Engineering Technicians with salaries rising to £4149. Further promotion to Engineer grades is also possible.

Staff will be based at Equipment Department, Chiswick which is within easy reach of British Rail and London Transport services and the M4, North and South Circular roads.

Good club and canteen facilities are available.

Requests for application forms to The Engineering Recruitment Officer, BBC, Broadcasting House, London W1A 1AA, quoting reference 75 E4057/WW. Please enclose an addressed envelope at least 9" x 4" with your application; no stamp is required. Closing date for completed application forms is 14 days after publication.




4972

### ARTICLES FOR SALE
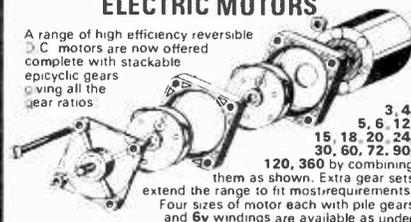
#### MARX-LÜDER STACKABLE EPICYCLIC GEARED ELECTRIC MOTORS

A range of high efficiency reversible D.C. motors are now offered complete with stackable epicyclic gears giving all the gear ratios



EM136P 1½ watts: 5000rpm size 24 x 24 x 14mm	£
Max. gearbox torque 2kg.cm	6.55
EM136P/1 Spare gear set with 3.4.5.6 ratios	1.95
EM141P 8 watts: 5000rpm size 35 x 35 x 109mm	
Max. gearbox torque 5kg.cm	7.40
EM141P/1 Spare gear set with 3.4.5.6 ratios	2.10
EM145P 20 watts: 7000rpm size 52 x 52 x 180mm	
Max. gearbox torque 10kg.cm	9.55
EM146P 30 watts: 4000rpm size 52 x 52 x 200mm	
Max. gearbox torque 10kg.cm	11.80

<b>SPECIAL OFFER</b>	
'Gearbox pack'. All items above	34.00
<b>MOTORS without gearboxes</b>	
EM131 0.8 watts 20g cm 8000rpm ø17mm	4.65
EM136 1.2 watts 40g cm 5000rpm ø21mm	4.35
EM139 4.2 watts 160g cm 5000rpm ø30mm	4.15
EM141 8 watts 320g cm 4500rpm ø30mm	4.85

<b>SPECIAL OFFER</b>	
'Motorpack'. All motors above	16.00
Suggested applications. Laboratory equipment, stirrers, pump drives, servo systems, positioning of aenais, dampers, doors, power for models, trains, boats, drills, cutting wheels etc. SAE for DATA SHEETS. All prices are inclusive in U.K.	

MAILORDER ONLY FROM  
**AID-US PRODUCTS**  
Dept. WW10, 8 Hillview Road, Pinner  
HA5 4PA, Middlesex 4987

### THE SCIENTIFIC WIRE CO.

Copper — Nickel — Chrome — Eureka —  
Litz — Manganin Wires.  
Enamelled — Silk — Cotton — Tinned  
Coverings.

- ★ No minimum charges or quantities.
- ★ Trade and export enquiries welcome.
- ★ S.A.E. brings list.

P.O. BOX 30, LONDON E4 9BW

### BUDGET MINI AUDIO MIXERS

With Professional Facilities

Silver sliders ★ Tone Controls ★ Monitoring ★  
VU Meter  
Mono or Stereo ★ Ready to use or kits

Details Ref. WW

PARTRIDGE ELECTRONICS  
21-25 Hart Road, Benfleet, Essex

**60 KHz MSF RUGBY RECEIVERS.** BCD TIME-OF-DAY OUTPUT. High performance, phase locked loop radio receiver. 5V operation with LED indication. Kit complete £9.50; assembled and tested unit £11.12 (prices include postage and V.A.T.) Also available low power receiver with signal and audio outputs. Send for details Toolux, Sherborne (4359) Dorset. (21

**VALVE BARGAINS.** Any 5-45p. 10-75p. 50-£3.60. ECC 82 ECL 80 EF 80/183/184 PC 86/88 PCF 80/802 PCL 82/84/85/805 PL 36/504 PY 33/81/800/88 30PL14. COLOUR VALVES 12p each PL508/509 PY 500A. No VAT required. P&P under £1/10p. £1 to £3/15p. Above £3/20p. Money back guarantee. — LANCASHIRE MAIL ORDER, 6 WILLIAM STREET, STUBBINS, RAMSBOTTOM, BURY, LANCs. (4987)

**SCOOP! CAPACITORS / RECTIFIERS.** 10mfd/12V. 80mfd/150V 10/20p. 100/£1. 10mfd/70V. 22mfd/50V 10/25p. 100 £1.25 100mfd/16V. 1000mfd/6V 10/30p. 50/75p. 1N4002 10/30p. 1N4004 10/40p. 1N4007 10/50p. Bridges 1A/200V 2/50p. 2A/200V 2/65p. P&P 20p. Audio-Optics, 19 Middleway, Chinnor, Oxon. (4955)

**HUNDREDS, YES HUNDREDS** of turntable units, pick-up cartridges, plinths, covers, and speaker cabinets Wholesale/Retail. Ring or write for lists. SPA-RADIO. 335-337 High Street Cheltenham. Phone 54357. (4952)

**HUNDREDS** of Dual Standard Colour TV's for sale. Contact: S. H. C. Televisions Ltd., 024-026 (Radnage) 3321. (20

**SITUATIONS VACANT**

# TEST GEAR ENGINEERS

Rediffusion, a major British company in television manufacture, is developing a new, state of the art receiver at its Chessington laboratories. To support this project we require additional Test Equipment Design and Development Engineers at senior and intermediate levels to help produce our sophisticated production test equipment. Rediffusion test equipment leads the industry and uses both analogue and digital techniques along with an up-to-date approach to jiggling.

Applications are invited from well qualified and experienced test equipment engineers, who will be offered the opportunity to join a young and energetic team. Our work is usually demanding, often under pressure but always stimulating, using new ideas to speed production whilst reducing the demands on our test operators.

Salaries, which will depend on experience, are excellent and assistance with relocation will be given where appropriate. Some travelling to our production factories in Co. Durham will be necessary from time to time to assist in the installation and commissioning of new equipment since our design engineers are expected to be responsible for all aspects of their project.

If you are a high calibre engineer and wish to have your ability recognised and rewarded, come and join us.

Write or 'phone to:

A. J. Litteck,  
Test Equipment Group Leader,  
Rediffusion Consumer Electronics Ltd.,  
Fullers Way South,  
Chessington, Surrey.  
Phone 01-397-5411

## REDIFFUSION

5011

**ARTICLES FOR SALE**

### fibre optic suppliers

**MARE'S TAIL** Decorative Display, 22" dia. 7.000 + Fibres. Looks absolutely immaculate £10.00. Glass fibres — requires cover.  
**FIBROFLEX SIZE 1** 440 Strand Flexible Glass Light Conduit. 1 1/4mm Active Dia. Black Sheath. 10m £3.00; 100m £21.00  
**CROFFON 1610** Flexible 64 Strand Plastic Light Conduit. Active Dia 1 8mm, O.D. 3 3mm £1.20 per M. 10m £9.00  
**PLASTIC OPTICAL MONOFIBRE** Flexible Light Guide Dia. 10, 20, 40, 60 thou. FP10 100m £4.00. FP20 (Ø 5mm) 100m £8.00. FP40 10m £4.00; 100m £32.00. FP60 10m £8.00; 100m £55.00  
**OPTIKIT 103** 2m CROFFON 1610 + 3m each FP20, FP40, FP60 + Polishing Compound, ideal laboratory pack £5.50  
**OPTIKIT L6** 6 Convex Glass Lenses Dia 7/14/21/26/47/51mm £3.00. (Lenses also available separately)  
**OPTIKITS RRS** Five Retro-Reflectors for Optical/Infra-Red beam systems. Dia. 22/36/44/62mm + 150mm Strip £2.50  
**ULTRASONIC TRANSDUCERS SE05B-40T/R** Sensitive 40kHz Tx/Rx pair (Suitable for 'Practical T.V.' Remote Control System) £3.50  
**ULTRASONIC TRANSDUCERS SE04B-25T/R** 25 kHz Tx/Rx Pair. (Better Sensitivity Lower Bandwidth than SE05B-40) £4.00  
**CIRCULAR POLARISERS** Reduce glare on all types of instrument. RED/AMBER/GREEN or NEUTRAL 50 mm sq 70p; 75 mm sq £1.40; 150 mm sq £4.50. Linear Polarizers also available  
**OPTOELECTRONICS LIGHT SOURCES & DETECTORS**  
MV54 2mm Red LED 20p. MLED500 T092 Red LED 20p.  
XC209-Red (3mm) 20p. XC209-Y, XC209-G (Amber, Green) 30p.  
MLED92 Infra Red Emitter 30p. MLS203 Photo-Thyristor £1.20.  
2N5777 High Sensitivity Photo-Darlington 25V 50p.  
MRD 150 2mm High Speed Photo-Transistor (4 uS) 40V 70p

Please add 8% VAT to prices. S.A.E. please for short form/datasheet  
**FIBRE OPTIC SUPPLIERS (NW)**, 2 LOUDOUN ROAD NEWS, LONDON NW8 0DN 5016

**CLAUDE LYONS TS2** Stabilisers 240V 2750W as new £25 + £2 cam. S.A.E. for lists. M. Bond, 38 The Orchard, Market Deeping, Peterborough PE6 8JR. (4952)

**NINE IIN** tapes scotch video 360-1-3000 R97B Slightly used, five as above unopened twelve in Hitachi Video tape R716 unopened. Offers to Perth High School, Oakbank Road, Perth, Scotland. (4969)

**"MOTIVATOR"** Curtain Cord Controllers. Mains battery models and kits for use with corded domestic curtains. From £18-20. Aid-Us Products, Dept. WW10, 8 Hillview Road, Pinner HA5 4PA, Middlesex. (4988)

**MOBILE RADIO CRYSTALS.** All specs except glass types. Competitive price and delivery. Secondhand mobile radio equipment bought and sold. Vehicle mounting and hand held sets. Write to: Radio Ancillaries Ltd., 30 Craven St., London WC2N 5NT. (4985)

**TEST EQUIPMENT.** 1 x Airmec' 409 AM/FM Modulation Meter, £100. 2 x Advance J1 AF Signal Gen., £45 each. 1 x Clark Pump Up Mast, condition as new, £50. Write to: Radio Ancillaries Ltd., 30 Craven St., London WC2N 5NT. (4986)

**GRIMSBY ELECTRONICS.** For components relays, sirens, surplus equipment, etc. Bargains list send 9p. Lambert Road, Grimsby, Humberside. (5010)

**SCOPE TUBES D14-121-GH 50 MHZ.** 4.2 v/cm 'Y' sensitivity, with bases and mumetal shields. Also suitable unassembled cases. £30 the package. Suitable mains transformers, regulator P.C.Bs (no components inverter transformers, multipliers, deflection amps etc. available to tube purchasers at virtually scrap prices. Everything brand new. Phone 01-202 6282. (5000)

**WEATHER SATELLITE PICTURES.** Electrosensitive, chemical recording paper ALFAX Type A. Ideal for experiments. Carton of 12 rolls, each 5 1/4 x 120ft, £4.25 post paid. Suggestions for use included. SAE for further details. Branson, 111 Park Road, Peterborough. (5018)

**MULLARD FERRITE CORES** LA3 100 to 500 KHZ 54p, LA4 10 to 30KHZ 81p, LA5 30 to 100 KHZ 81p, LA13 for W.W. oscilloscope £1.50. Transistors BD 124 55p AD 149, matched pair 65p. Diodes by 100 10 for £1.50. BY/127 10 for £1.08. Special offer Mullard electrolytic capacitors 2200 MFD 100V type 107-10222 £1.25 each. All prices include post and VAT at appropriate rate. Mail order only.

Xeroza Radio,  
1 East Street, Bishops Tawton, Devon (5020)

**NEW FULL SPEC SPARES** for Linsley-Hood 75 watt amplifiers sescosem BDY 56 £2.00, Motorola BD529, 530 65p each, 2N5459 45p, BF 258 45p. Tantulum bead 100/3V 20p. Filter switch click and mains/rf interference suppression kit, with instructions, £1.35. Rapid delivery. SAE for list. P & P 10p. I. G. Bowman, 59 Fowey Avenue, Torquay, S. Devon. (4999)

**GEARED MOTORS** Drayton type RQR, 1RPM 90 lbs/in torque, 220-250V 50 cps. In-line sound shaft. Reversible by two-way sw. or relay. Any mounting position. Ideal servos. Brand new. Boxed half price, £17.50 including PP. Nigel O'Brien, 189 West Hendon Broadway, London, NW9. (5001)

**ARTICLES FOR SALE**

#### ENAMELLED COPPER WIRE

S.W.G.	1 lb. reel	1/2 lb. reel
10 to 19	2.40	1.35
20 to 29	2.45	1.40
30 to 34	2.60	1.50
35 to 40	2.85	1.60

All the above prices are inclusive of postage and packing in U.K.

#### COPPER SUPPLIES

102 Parrwood Road, Withington, Manchester 20  
Telephone 061-445 8753

**HIGHLY EXPERIENCED T.V. BROADCAST ENGINEER,** many years overseas in Technical/Sales/Marketing backgrounds seeks challenging, responsible position. Experienced in systems design, planning and installation for studios O.B. vehicles, etc. Contact: R. Brown, c/o 26 Hill Grove, Romford, Essex. (4994)

#### CRYSTALS

Fast delivery of prototype and production quantities to your specification. EG:

100 KHz	0.005%	HC13/U	£2.50 each: £1.900 per 1,000
1 MHz	0.005%	HC6/U	£2.50 each: £1.600 per 1,000
2.097152 MHz	0.0025%	HC6/U	£3.05 each: £1.550 per 1,000
3.2768 MHz	0.0025%	HC6/U	£2.70 each: £1.500 per 1,000
10 MHz	0.002%	HC18/U	£2.00 each: £1.100 per 1,000

Also, Stahk LF. crystals in T0-5 package, many stock frequencies in the range 10-240 KHz, e.g. 10, 12.8, 16.384, 32.768 & 100 KHz, prices from £2.55 each: £1.400 per 1,000.

Please send for further details  
**INTERFACE QUARTZ DEVICES LTD.**, 29 Market Street, Crewkerne, Somerset. Telephone: (046031) 2578 Telex: 46283.

#### TAPE RECORDING ETC.

#### RECORDS MADE TO ORDER

DEMO DISCS MASTERS FOR RECORD COMPANIES	VINYLLITE PRESSINGS
---	------------------------

Single disc: 1.20. Mono or Stereo, delivery 4 days from your tapes. Quantity runs 25 to 1,000 records PRESSED IN VINYLITE IN OUR OWN PLANT. Delivery 3-4 weeks. Sleeves/Labels. Finest quality NEUMANN STEREO/Mono Lathes. We cut for many studios UK/OVERSEAS. SAE list.

#### DEROY RECORDS

PO Box 3, Hawk Street, Camforth, Lancs. Tel. 2273 (82)

**EX-GOV'T MOMO** to multi-track tape recorders, "E.M.I.," Perrograph-rich, etc. S.A.E. details A. Wright, 10 Church Street, Dowlais, Glamorgan. 4991

HIGH STABILITY  
**QUARTZ  
CRYSTALS**

4 KHZ TO 105 MHZ  
CUSTOM DESIGNED OR  
PRODUCED IN A FULL  
RANGE OF INDUSTRIAL  
AND MOBILE SPECS.

WRITE OR TELEPHONE FOR DETAILS:

**TRISDENE LTD.**  
46 CRANK ROAD, BILLINGE, WIGAN, LANCs, WN5 7EZ  
ENGLAND. Tel: Billinge (0744) 894295

4960

**CASE CLEARANCE.** Mullard C280 polyester film 250v 0.1 microfarad. 20 per cent tol. Perfect mechanically but untest surplus, £2 per thousand. Also tested 250v c 280 caps. 0.47 uf £1.50 per 100, 0.33 uf £1.20 per 100, 0.22 uf £1.10 per 100, 0.33 uf 80p per 100, all perfectly printed. Price includes P.P. Brand new E.C.L. gates MC 10101L, MC 10102L, MC1015L at 65p each. TD 253 tunnel diodes at £2.00 each. N. O'Brien, 189 West Hendon Broadway, London, NW9. (5002)

## ARTICLES FOR SALE

### B. BAMBER ELECTRONICS

5 STATION ROAD, LITTLEPORT, CAMBS, CB6 1QE  
TEL: ELY (0353) 860185 (TUESDAY-SATURDAY)

**A Merry Xmas  
and a  
Prosperous New Year  
to All our Customers**

**HELLERMAN LUBRICANT GRADE C.** The ideal lubricant for all rubber goods. Good electrical insulator. **75p** per bottle.

**WE NOW STOCK SPIRALUX TOOLS** for the electronics enthusiast. Screwdrivers, nut spinners, BA and Metric sizes, pop rivet guns, etc. SAE for list.

**PHOTOMULTIPLIERS, E.M.I. TYPE 6094.** Brand new with base. **£20** each.

#### PLUGS AND SOCKETS

**25-WAY ISEP PLUGS AND SOCKETS, 40p** set (1 plug + 1 skt). Plugs and sockets sold separately at **25p** each.

**ANDREWS 44AN FREE SKTS.** (N-type) for FH4/50B or FHJ4/50B cable, **£1.00** each.

**BULGIN ROUND FREE SKTS.** 3 pin, for mains input on test equipment, etc., **25p** each.

**SO239 BACK TO BACK SOCKETS, £1.25** each.

**PL259 PLUGS (PTFE).** Brand new. **50p** each or 5 for **£2.25**.

Reducers for above **15p** each.

**SO239 SOCKETS (PTFE).** Brand new (4 hole fixing type), **50p** each, or 5 for **£2.25**.

**N-TYPE SKTS.** (4 hole chassis mounting, 50ohms, small coax lead type), **50p** each.

**N-TYPE PLUGS 50ohm, 60p** each.

**GREENPAR (GE35012) CHASSIS LEAD TERMINATIONS** (These are the units which bolt on to the chassis, the lead is secured by screw cap, and the inner of the coax passes through the chassis), **30p** each, 4 for **£1.00**.

**BULGIN FLAT 2 pin FLEX CONNECTORS.** Non-reversible. **40p** each.

**SPECIAL OFFER.** Miniature 50 ohm coax, high quality, PTFE insulation and blue PTFE cover, solid silver-plated inner, and silver-plated braid, approx 3mm overall diameter, (ideal for unit wiring of RF stages up to 23cms. etc.) 4 metres for **50p**.

#### ALL BELOW — ADD 8% VAT

**PYE WESTMINSTER W15 AM.** 12½kHz channel spacing, G.P.O. approved. High Band AM. Dash mount, less crystals. Good condition. **£100.00.**

**PYE BASE STATION F30M.** TX 100mHz Rx 140 mHz, low power **MID BAND**, good condition. **£200.00.**

**MANUFACTURERS — SEND SAE FOR OUR LATEST BARGAIN CAPACITOR LIST**

**PLESSEY COLOUR SCAN COILS.** 90° brand new. **£4.00** each.

**COLOUR MONITOR DECODER PANELS.** By leading British manufacturer. Designed to B.B.C. standards. Units consist of chrominance module, PAL filter and delay module, luminance module and encoded video input module. All units brand new and complete including edge connectors and service manual. **£30.00.** Manual supplied separately. **£1.00** each.

**PHILIPS STAB. POWER** 0.35 volt, 3 amp. Metered type PE 4806. **£65.00** each.

**TINNED COPPER WIRE.** 0.234mm. Looks like 15a fuse wire. 12 oz. reel. **30p.**

**CHART RECORDER PAPER.** 10¼in x 120ft. Type M1299. **£1.00** per roll.

**MINIATURE** Panel mounting Rocker Switches, bolt-on type, smart appearance. 3 for **50p**.

**MAINS TRANSFORMERS**

All 240V input voltages quoted approx. RMS

(Please quote Type No. only when ordering)

**TYPE 10/2** 10.0-10V at 2A. **£1.50.**

**TYPE 18/2** 18V at 2A. **£1.65.**

**TYPE 28/4** 28V at 4A, 125V at 500mA. **£4.00.**

**TYPE 129** 400V at 20mA, 200V at 10mA. 6.3V at 500mA. **£1.25.**

**TYPE 72703** 400V at 10mA. 200V at 5mA. 6.3V at 400mA. **£1.25.**

**TYPE 70462** 250-0.250V. 50-0-50V. 6.3V. **£1.75.**

**TYPE 125BS,** approx. 125V at 30mA. **65p.**

**MAINS ISOLATING TRANSFORMER** (ex. equip), in metal cases, totally enclosed, tapped mains input, 110-240V etc., output 240V at 3A + 12V at 0.5A. **£11.00.**

**AS above,** output 240V at 12A + 12V at 3A + 22V at 2.5A. **£27.50.**

#### ALL BELOW — ADD 8% VAT

**MULLARD TUBULAR CERAMIC TRIMMERS.** 1-18pf, 6 for **50p.** (as featured in Rad. Comm. Jan. p.25)

**ICs,** some coded, 14DIL type, untested, mixed, 20 for **25p.**

**T03 TRANSISTOR INSULATOR SETS,** 10 for **50p.**

**24V MIN. REED RELAYS,** encapsulated single-pole make, 2 for **50p.**

**CHASSIS TAGS,** 25p pack

**RELAYS,** single pole, changeover, 12 DC, approx ¾in x ½in x 1¼in, **35p** each.

**MINIATURE SLIDER SWITCHES,** 2 pole, 2 way, 5 for **50p.**

**2-6PF., 10MM CIRCULAR; CERAMIC TRIMMERS** (for VHF/UHF work), 3 pin mounting, 5 for **50p.**

**CERAMIC HIGH VOLTAGE PILLARS** (metal ends, tapped 4BA), approx. 1in. long. 10 for **50p.**

#### PYE RADIO-TELEPHONE EQUIPMENT

Cambridge, Westminster, Motofone, Europa series. Send s.a.e. for full details

**WELLER STOCKIST.** All irons and spares available. S.A.E. for list.

#### VALVES

**QV03/20A** (ex. equipment). **£3.00.**

**QV03/10** (ex. equipment) **75p** or 2 for **£1.20.**

**2C39A** (ex. equipment). **£1.00** each.

**QV02/6** (ex. equipment). **£1.00** each.

**4CX250B** (ex. equipment). **£2.10** each.

**4X250B** (ex. equipment). **£1.50** each.

**DET22** (ex. equipment). 2 for **£1.00.**

**TRANSISTOR HEATSINKS,** to take 2 x TO18 transistors, screw-in clamps, block size 1in. x ½in. x ¼in. with 2 holes for mounting. 3 for **50p.**

**RADIOPARES 500WATT AUTO TRANSFORMER,** 100 / 110 / 150 / 200 / 220 / 240V tapped input and output step up or step down facility, ex. new equip., **£6.00.**

**MULLARD SCOPE TUBE DN7-78.** 3in face complete with base and mu-metal screen. **£6.50** each.

#### ALL BELOW — ADD 25% VAT

**HIGH QUALITY SPEAKERS.** 8½in x 6in. elliptical, 2in. deep, 40ohms, inverse magnet, rated up to 10W. **£1.50** each, or 2 for **£2.75** (Quantity discount available).

**T.V. PLUGS** (metal type). 6 for **50p.**

**T.V. SOCKETS** (metal type). 5 for **50p.**

**T.V. LINE CONNECTORS** (back-to-back skt.) 5 for **50p.**

**MIXED ELECTROLYTICS,** large bag. **£1.00.**

**OC200 TRANSISTORS,** 6 for **50p.**

**BSY95A TRANSISTORS,** 6 for **50p.**

**BCY72 TRANSISTORS,** 4 for **50p.**

**PNP AUDIO TYPE T05 TRANSISTORS,** 12 for **25p.**

**STUD RECTIFIERS,** BYX42/300R. 300V at 10A. **30p** each, or 4 for **£1.00.**

**DIN SPEAKER SKTS,** 2-pin, 4 for **50p.**

**IF CANS,** ½in square, suitable for rewind, 6 for **30p.**

**DUBILIER ELECTROLYTICS.** 50uF, 450V, 2 for **50p.**

**DUBILIER ELECTROLYTICS.** 100uF, 275V, 2 for **50p.**

**PLESSEY ELECTROLYTICS.** 470uF, 63V, 3 for **50p.**

**TCC ELECTROLYTICS.** 1000uF, 30V, 3 for **60p.**

**PLESSEY ELECTROLYTICS.** 1000uF, 180V, **40p** each (3 for **£1.00**).

**DUBILIER ELECTROLYTICS.** 5000mfd, at 35V. **50p** each.

**DUBILIER ELECTROLYTICS.** 5000mfd at 50V. **60p** each.

**DUBILIER ELECTROLYTICS.** 5000mfd at 70V. **65p** each.

**ITT ELECTROLYTICS.** 6800mfd at 25V, high grade, screw terminals, with mounting clip. **50p** each.

**PLESSEY ELECTROLYTICS.** 10000mfd, at 63V. **75p** each.

**MULLARD BLACK/WHITE C.R.T.** A65-11W Brand new. **£11.00.**

**T.V. LINE SOCKETS.** 18p each, 5 for **75p.**

**T.V. SOCKETS.** Mounted on Bakelite panel, 6 for **50p.**

**DIN 3 pin LINE SOCKETS.** 15p each.

**E.H.T. V/HOLDERS B9A.** (Both PHILIPS and PYE types available.) **20p** each.

### Economise on Semiconductors

All prices include VAT

- ★ Low Price CMOS
- ★ Low price OIL sockets
- ★ Lower Price 741C
- ★ Plastic 3 terminal Regulators

709C + data 8 pin OIL	38	36	34	7400	14	12	4000	18	17
723C + data 14 pin OIL	70	68	64	7402	14	12	4001	18	17
741C + data 8 pin OIL	26	25	24	7403	14	12	4002	18	17
748C + data 8 pin OIL	39	37	35	7404	16	13	4006	102	95
ME555 + data 8 pin OIL	48	47	46	7405	16	13	4007	18	17
CA3046 14 pin OIL	84	81	77	7410	14	12	4008	102	95
TDA1405 5v 650mA	80	76	74	7413	29	24	4009	50	46
TDA1412 12v 500mA	80	76	74	7420	14	12	4010	50	46
TDA1415 15v 450mA	80	76	74	7430	14	12	4011	18	17
BC107, 108, 109	11	10.5	10	7442	64	54	4012	18	17
BC182, 184	12	11.5	11	7447	90	80	4013	50	46
BC212, 214	13	12.5	12	7473	30	25	4014	90	82
H-P 0.2" LED red	19	18	17	7474	32	26	4015	90	82
H-P 0.125" LED red	18	17	16	7476	32	26	4016	50	46
OIL Low profile 8	11	10	9	7486	32	26	4017	90	82
Sockets 14	12	11	10	7490	48	39	4020	97	88
Sockets 16	13	12	11	7492	55	50	4023	18	17
				7493	48	39	4024	68	62
				74121	34	28	4025	18	17
							4027	50	45
							4028	78	71
							4030	50	43
							4040	93	84
							4042	74	67
							4046	117	107
							4049	50	45
							4050	50	45
							4068	18	17
							4071	18	17
							4078	18	17
							4081	18	17
							4507	50	45
							4511	138	126
							4518	109	99
							4520	109	99
							4527	138	126
BC109C	11	BZY88C		IN914	5				
BC177	21	3V3-15V	12	IN4001	5				
BC179	22	2N3702	12	IN4002	6				
BF244B	30	2N3704	13	IN4004	7				
BFY51	18	2N3708	10	IN4148	4				
		2N3055	49						
AY-5-1224 16 pin DIL clock IC + data + circuit									4.00
Clock kit IC + 4 digits									11.00
Clock kit IC + 4 digits, transistors & transformer									13.00
TBA810AS 7W Audio Amp + circuit + data									1.15
TCA940 10W Audio Amp + circuit + data									2.20
TA0100 Radio IC + IF filter + data									1.70
Carbon film resistors ¼W 5% E12, 1.2 ea. 10 11p. 100 95p.									

By return service. P&P 10p (UK). SAE enquiries, lists. Schools, Colleges supplied

**SILICON SEMICONDUCTOR SERVICES**  
41 Dunstable Road, Caddington, Luton LU1 4AL

# SMI MUSICAL INSTRUMENTS LIMITED

Terms of business — Cash with order  
All prices include V.A.T., Post and Packing (U.K. only)  
Minimum order £1 No personal callers  
Subject to stock availability

<b>DIODES</b>		<b>CAPACITORS</b>		<b>RESISTORS</b>	
IN 914e	.03p	Polystyrene		Wire Wound	
IN 4001	.05	3000 pf 63v 5%	.05p	.5 Ohm	.12p
IN 4002	.06	Mullard C280		¼ watt 5%	
IN 4148	.02	.022 uf	.04	470 Ohm	.01
BZY 88 5.6v	.17	.033 uf	.04	18k	.01
BZY 88 C3V3	.10	.047 uf	.05	15k	.01
		.1 uf	.03	56k	.01
		.15 uf	.04	330k	.01
		.22 uf	.04	25k Slider LIN	.27
<b>TRANSISTORS</b>				Var. 470 Ohm	.04
BC 108	.10			Preset 500 Ohm	.42
BC 109	.11	Electrolytic		Preset 200k	.04
BC 109A	.11	.10 uf 25v	.05	25k Linear	.12
BC 109B	.16	50 ml Reversible	.07		
BF 195	.11	47 ml 25v	.04		

## EDUCATIONAL

## C AND G EXAMS

Make sure you succeed with an ICS home study course for C and G Electrical Installation Work & Technicians, Radio/TV/Electronics Technicians, Telecomms Technicians and Radio Amateurs.

## COLOUR TV SERVICING

Make the most of the current boom! Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers.

## TECHNICAL TRAINING

Home study courses in Electronics and electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self-build radio kits. Get the qualifications you need to succeed.

Free details from:

## INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 734, Intertext House, London SW8 4UJ  
or phone 01-622 9911 (all hours)

(4962)

## CAPACITY AVAILABLE

**DESIGN**, development, repair, test and small production of electronic equipment. Specialist in production of printed circuit assemblies. **YOUNG ELECTRONICS LTD.**, 184 Royal College Street, London NW1 9NN. 01-267 0201. (29)

**BATCH** Production Wiring and Assembly to sample or drawings. Deane Electricals, 19B Station Parade, Ealing Common, London, W.5. Tel: 01-992 8976. (13)

**CAPACITY** available to the Electronic Industry. Precision turned parts, engraving, milling and grinding both in metals and plastics. Limited capacity available on Mathey SP33 jig borer. Write for lists of full plant capacity to C.B. Industrial Engineering Ltd., 1 Mackintosh Lane, E9 6AB. Tel: 01-985 7057. (14)

**AIRTRONICS LTD.**, for Coil Winding — large or small production runs. Also PC Boards Assemblies. Suppliers to P.O., M.O.D., etc. Export enquiries welcomed. 3a Waterand Road, London, SE13 7PE. Tel: 01-852 1706. (61)

**A.A.A. SERVICE.** Small batch production wiring, assembly to sample or drawings. Specialists in printed circuit assembly. Cable-forms to order. Rock Electronics Ltd., 42 Bishopsfield, Harlow, Essex. Tel. Harlow (0279) 33018. (37)

**AVOMETERS** repaired and calibrated, traceable calibration certificate given if required. **AVOMETERS and ELECTRONIC COMPONENTS** wanted, good prices paid. 'Q' Services Electronic (Camberley) Ltd., Yateley (0252) 871048 any time. (4998)

**FARNBOROUGH ELECTRONIC SERVICES.** Electronic prototype wiring, printed circuit board assembling, at competitive prices. Design, Manufacture and finishing of metal work for the Electronic/Electrical fields. Tel. Farnborough 44592. (4964)

**PRINTED CIRCUIT BOARDS** — Quick deliveries, competitive prices, quotations on request roller tinning, drilling, etc., speciality small batches, larger quantities available. Jamiesons Automatics Ltd, 1-5 Westgate, Bridlington, N. Humberside, for the attention of Mr. J. Harrison. Tel: (0262) 4738/77877. (18)

**LABELS, NAMEPLATES, FASCIA**s on aluminium or plastic. Speedy delivery. **G.S.M. GRAPHICS LTD.**, 1-5 Rectory Lane, Guisborough (02873-4443) Yorks. (26)

**PCB ASSEMBLY** by professional females accurate high quality work. Phone 0256-3858 NOW for quotation and delivery. (4953)

**TRANSFORMERS:** Capacity available for manufacture of small mains transformers. Art Metal Engineers Ltd. Blatchford Road, Horsham, Sussex. Tel: Horsham 2215. (4968)

**PRINTED CIRCUITS**, we will make your P.C.B.'s for at least 25 per cent less than what you are now paying. Prototypes welcome. 4990

**FREELANCE TECHNICAL AUTHOR** and design engineer seeks commissions for handbook writing, preparation of test specs, etc. 0276-33479 (Camberley). (4997)

## AUCTIONS

## SALE BY AUCTION

By order of the Receiver and Manager, W. G. Mackey, Esq.

Re R.S.D. Systems Limited

PUBLIC ADDRESS  
AND  
STAGE EQUIPMENT

including: SPEAKER AND AMPLIFIER CABINETS, SPEAKERS AND SPEAKERS IN CABINETS. 14 ACOUSTIC, H.H. YAMAHA AND OTHER AMPLIFIERS. Yamaha YH S100 horn unit, Yamaha bass stack. 16 AKG and other microphones. HAYMAN DRUM KIT, VOX electric piano, 13 Hayman, Jedson, Yamaha and other guitars, 3 WURLITZER MODEL 200 PROFESSIONAL PORTABLE ELECTRONIC PIANOS. A 30-CHANNEL MIXER CONSOLE.

Guitar cases, drum skins, spotlights.

## COMPONENT STOCK

including Capacitors, jack plugs and sockets, resistors, etc.

which

## FRANK G. BOWEN LIMITED

(established 1824)

will include in their Sale by Auction  
on Thursday, November 27th, 1975  
at 2 p.m. precisely at their salerooms at  
15 GREEK STREET, LONDON, W.1

ON VIEW DAY PRIOR AND MORNING OF SALE

Catalogues 15p from the Auctioneers 01-437 3244/5

## SERVICE AND REPAIRS

**AUDIOMASTER BACKGROUND MUSIC** . . . service, sales. Tape programmes. P. J. Equipments, 3 Onslow Street, Guildford 4801. (12)

**THOR-HOLE CONVENTIONAL P.C.B.'s** gold plating, roller tinning, prototypes, silk screening, drilling. All or part service. — **ELECTRO CIRCUITS (P.C.) LTD.**, Delamare Road, Chesnut, Herts. Tel. Waltham Cross 38600 or 20344 (64)

**TUBE POLISHING**, mono, £5.63, colour £5.94. C.W.O. Return carriage and VAT paid. Phone: N.S. 300, Retube Limited, North Somercotes, Lough, Lincs. (27)

## ARTICLES WANTED

**WANTED**, all types of communications receivers and test equipment. Details to R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley 4986. (63)

**WANTED SECOND A/F** real time analyser HP 8054 or GR 1921. Duo or single cassette or floppy disc hardware. Wang 720C or similar mini computer. Nagra Kudelski III or IV S. M.A.A. 3 Rue de la Gendarmerie Marie B 1338, Lasne, Belgium. Tel. 02 633 1804. (5021)

**B-D ELECTRONICS** offer prompt settlement for your surplus components. Our main field of interest is consumer electronics. Please telephone our Miss Hughes, Sandy (0767) 81616. (22)

**COIL WINDERS WANTED.** Any type considered including toroidal. For one application we would prefer Avo Macadie or newer equivalent. We specialise in audio inductors wound to your specification. Falcon Acoustics Ltd, 26 Station Road, Bexhill-on-Sea. 0424-219950. (4963)

## RECEIVERS AND AMPLIFIERS —

**HRO** Rx5s, etc., AR88, CR100, BRT400, G209, S640, etc., etc., in stock. R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E11. Ley 4986. (65)

**SIGNAL** Generators, Oscilloscopes, Output Meters, Wave Voltmeters, Frequency Meters, Multi-range Meters, etc., etc., in stock. R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley 4986. (64)

## BUSINESS FOR SALE

**HI-FI/AUDIO SHOWROOMS.** Superb trading position in a busy pedestrian shopping precinct, near Croydon in Surrey. 2,000 sq. ft. premises with electronic compressor, acoustic tiling, subdued lighting, etc. All better class agencies held. Turn-over £50,000 plus per annum under management. Obvious scope for enterprising owner to increase. Realistically priced at £8,000 plus S.A.V. — Full details from sole agents, Latimer Laurence Ltd., Leslie House, 238 High Street, Poole, Dorset. Tel. Poole (02013) 71037, 24 hour service. (4950)

## NEW GRAM AND SOUND EQUIPMENT

**GLASGOW.** Hi Fi, Cassette Decks, Tape Recorders, Video Equipment, always available we buy, sell and exchange for Hi Fi sets and photographic equipment. **VICTOR MORRIS** Audio Visual Ltd, 340 Argyle Street, Glasgow, G1, 8/10 Glassford Street, Glasgow, G2, 31 Sauchiehall Street, Tele: 041-221 8958. (11)

## VALVES WANTED

**WE BUY** new valves, transistors and clean new components, large or small quantities, all details, quotation by return — Walton's, 55 Worcester St., Wolverhampton. (62)

## COURSES

**RADIO** and Radar M.P.T. and C.G.L.I. Courses. Write: Principal, Nautical College, Fleetwood, FY7 8JZ. (25)

1. VHF Signal Generator Type TF 801A 10-300mcs. £50.00 pp £3.00
2. VHF Sweep Generator 450-900mcs (Telonic). £40.00 pp £2.00
3. Noise Generator CT 410 15kcs-160mcs in 3 bands. £40.00 pp £2.00
4. Pulse Generator Type Go 1005 (Solatron). £35.00 pp £2.00
5. Signal Generator (Airmec) 300kcs-30mcs in 7 bands. £45.00 pp £3.00
6. Signal Generator CT 202 6-75mcs. £25.00 pp £1.50
7. Microsecond Chronometer (Cintel) 12vDc or 240 Ac. £30.00 pp £2.00
8. Frequency Calibrator Type 221.125-20,000 kcs. Ac Power Supply. £40.00 pp £1.50
9. High Resistance measuring set Type 6625. £25.00 pp £2.50
10. Calibrator Type TC 99 100-205mcs. £25.00 pp £2.00
11. Frequency Period Counter (Beckman) Type 7360JH. £25.00 pp £2.00
12. VHF Frequency Standard (Wayne Kerr). £15.00 pp £1.50
13. TV Line Selector Type L 190 (Mullard) £40.00 pp £2.00
14. High Speed Valve Tester (Mullard). £30.00 pp £2.00
15. Klystron Power Supply Model Z816B (Elliot). £45.00 pp £2.00
16. Voltage Regulator (Lang & Thompson) 1000w 220/240v. £50.00 pp £4.00
17. Wide Range Oscillator Type 400C (Dawe). £20.00 pp £2.00
18. Video Oscillator (Marconi) TF 885 Rough External. £40.00 pp £2.00
19. Universal Impedance Bridge (Marconi) TF 373C. £15.00 pp £1.25
20. Adjustable Phase Corrector (Rank Cintel). £20.00 pp £1.00
21. Wave Analyser Type 705B. £30.00 pp £2.50
22. Valve Voltmeter TF 428B. £15.00 pp £1.25
23. RF X Band Test Set Type TC 118. £50.00 pp £2.00
24. Storage Scope (Remscope) Type SO1 £70.00 pp £3.00
25. Sweep Generator .005-100 cycles, square sine & sawtooth. Advance Type SG 88. £360.00 pp £4.00
26. VHF Receiver (GEC) Type R 1294 500-300mcs. 3 bands. £25.00 pp £1.50
27. Radio Telephones, Mobile, VHF, Under Dash Mounting £25.00 ea. or Built-in Speaker and coil lead mic. Transistorized, 12v DC. £40.00 pair pp £1.50 ea.
28. Transceiver (Walkie talkie) Type 88's. £30.00 per pair pp £2.00
29. Power & Modulator Unit Type 4 04 LRV 3B Built in Rotary Converter 24v DC in. 3 HT out. £8.00 pp £1.50
30. 2nd VFO units with film scale for RA 17. £40.00 pp £1.50
31. RA 17 L. £295.00 pp £3.00
32. RA 17 Mk 2. £285.00 pp £3.00
33. RA 17 A. £275.00 pp £3.00
34. RA 117 E. £385.00 pp £3.00
35. RA 1217 Transistorized. £400.00 pp £3.00
36. RA 6217 Transistorized North American. £410.00 pp £3.00
37. Universal Counter Timer, Rcal Type CT 488. £140.00 pp £3.00
38. RA 98 Single Side Band with AFC. £85.00 pp £1.50
39. RA 121 Single Side Band with AFC and Tuning Scope. £145.00 pp £1.50
40. RA 218 Single Side Band Fine Tune unit for RA117. £45.00 pp £1.50
41. RA 63 Single Side Band Fine Tune. £100.00 pp £1.50
42. RA 298 Single Side Band Transistorized £160.00 pp £1.50
43. RA 316 F.S.K. Teletypewriter Terminal Unit £150.00 pp £1.50
44. Rcal Teat Rig Type MA 91 for RA17's £45.00 pp £1.50
45. MA 79 Universal Drive Unit. £450.00 pp £1.50
46. TA 349C 1 K.W. Linear Amplifier. £2500.00 pp £1.50
47. MA 152 S.W.R. Bridge 1 K.W. £80.00 pp £1.50
48. TA 104H S.S.B. Transmitter 100w. £150.00 pp £1.50
49. Lorenz Teletypewriter with tape feature, send/receive Similar to 444. £80.00 pp £3.00
50. Creed 75 Mk 4 Receive Teletypewriters. £60.00 pp £1.50
51. Paper Winders for above. £25.00 pp £1.50
52. Sperry Gryro's Compass Mk 4. £18.00 pp £1.00
53. Inverter Type 100B-22-28v DC in 115v 3 Phase 400 cycles out 150 VA PF.8. £25.00 pp £1.00
54. Dial Telephones. £3.50 pp £0.75
55. Klaxton Horns 24v. 240v. £5.00 pp £1.00
56. Geared motors with built in 600-1 gearing: Electronic brake, reversible, limiting switches. Rough Appearance 12-24v DC. £15.00 pp £1.50
57. Electric Hand Dryers. £4.00 pp £1.00
58. Ferrograph Series 6 Tape Recorder 100-240vAC Strong Durel Case. £70.00 pp £3.00
59. Ferrograph Series 3 Tape Recorder 100-240vAC. Strong Durel Case. £40.00 pp £3.00
60. Phamphenic 25 watt High/Low Impedance input switchable output 15 ohms-70v. Wooden Case. £10.00 pp £2.00
61. Tape Cartridge Player built in 10 watt amp. £10.00 pp £1.50
62. Radar Aircraft (No indicator). £40.00 pp £2.00
63. Radar (Decca) Type: Marine. £350.00 pp £10.00
64. Decca Navigator Mark 5 Complete £1000.00 pp £8.00

CATALOGUES 50p each

Mail order only please to:  
Dept. MO2

**SOUTHERN AVIATION**

Station Approach, Epsom, Surrey

Telephone (03727) Epsom 2691

**BROADFIELDS & MAYCO DISPOSALS**

21 Lodge Lane, N. Finchley  
London, N12 8JG


Telephone:  
01-445 0749 01-445 2713 01-958 7624

MAY WE ASSIST YOU TO DISPOSE OF YOUR SURPLUS AND REDUNDANT STOCKS.

We will call anywhere in the British Isles, and pay **SPOT CASH** for Electronic Components and Equipment.

**QUARTZ CRYSTAL UNITS from**

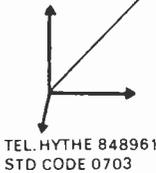- 1.0-80.0 MHZ
- FAST DELIVERY
- HIGH STABILITY
- TO DEF 5271-A



WRITE FOR LEAFLET AT 1

**McKNIGHT CRYSTAL Co. Ltd.**

HARDLEY INDUSTRIAL ESTATE, HYTHE, SOUTHAMPTON SO4 6ZY

TEL. HYTHE 848961  
STD CODE 0703

**"SAVE IT" BARGAIN**

**500 WATT DIMMER SWITCH**

(not suitable for fluorescent lights)

- Basic Module with 1" Knob. £2.00
  - Complete on MK switch plate. £2.50
  - Larger 2" knob (BULGIN) 25p extra, P&P 25p.
- Please add 8% VAT to all orders inc. P&P.

**FRASER-MANNING LTD.**  
40 TUDDENHAM ROAD, IPSWICH, IP4 2SL

**IBM GOLFBALL**

COMPUTER INPUT/OUTPUT

**TYPEWRITERS**

STANDARD EBCDIC CODING

Will accept normal or sprocketed paper. Supplied in working order with data sheets, circuit diagram and application notes. Each machine serviced and tested

£100 + 8% VAT

**PAPST** (or similar) **FANS** 4 1/2 x 4 1/2 x 2" 100 c.f.m. 50/60 c/s £4 (40p).

**PAPST FANS** Type 7576, new, 6" dia x 2 3/16 deep £5 (45p).

**LIGHT DIMMERS** 250w £2.70 (16p). BC107/B/9, BC147/B/9, BC157/B/9 all 9p ea. (11p).

**ELECTROLYTICS**

10,000 µ 63v £1 (25p). 2800 µ 100v £80p (25p) 2240 µ 100v 75p (25p). 1000 µ 63v £1 (25p) 4500 µ 35v 60p (15p). 2000 µ 50v 35p (11p). 4000 µ 70v 80p (20p). 4700 µ 63v 80p (15p) 2500 µ 60v 50p (12p)

**EX-COMPUTER PC PANELS.** 2 x 4" 50 boards for £2.40 (62p).

**OPCOA SCA7** 7mm 7-seg. led display. £1 (12p)  
OH bulbs 12v 55w. 60p (10p)  
250 mixed resistors. 60p (18p)  
250 mixed capacitors. 60p (18p)  
Si recs 20A 100piv. 4 for £1 (15p)  
2N3055 equiv. 4 for £1 (15p)

**EXTRUDED HEAT SINK** for 2 x TO3. 50p (15p)

**SMALL ELECTROLYTICS**

2.2 µ 10v, 10 µ 35v, 50 µ 40v, 100 µ 40v, 100 µ 6v, 150 µ 10v, 64 µ 10v, 300 µ 10v, 200 µ 10v 12 for 45p (12p)

**PINER PRESETS** 100mW

220. 470 1k, 4k7, 10k, 47k, 100k, 220k 12 for 50p (12p)

6v 0.5A Transformer. 75p (18p)

**REED RELAYS** 6v coil h/d contacts. 5 for £1 (15p)

**REED INSERTS** h/d contacts. 10 for £1 (12p)

**WATER-COOLED HEATSINKS** ex. eqpt. £1.20 (40p)

**CHROMED HANDLES**

5" mtg. centres. per pair £1 (20p)

8" mtg. centres. per pair £1.50 (25p)

P&P shown in brackets

ADD 25% VAT to TOTAL


8% VAT on PSUs, FANS, DIMMERS, BOARDS

**KEYTRONICS**

Please note new address:

332 LEY STREET, ILFORD, ESSEX  
01-553 1863 till 2 p.m.  
01-478 8499 after 2 p.m.

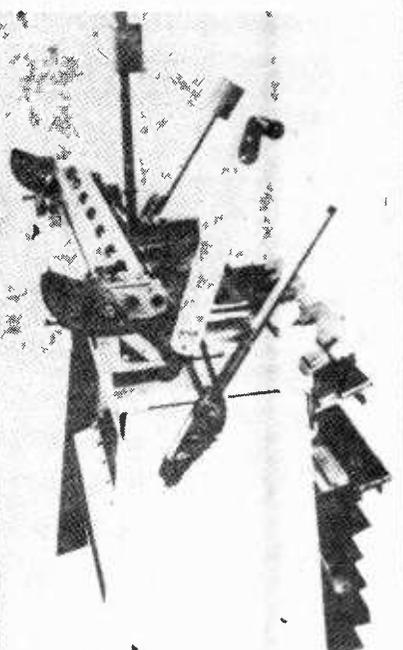**ANNOUNCING THE NEW T36" METAL BENDER BOX AND TRAY FORMING**



**A WORKSHOP IN ITSELF AS VERSATILE AS OUR EVER POPULAR RXX-26**

- ★ AMAZINGLY POWERFUL
- ★ EASY TO OPERATE
- ★ IDEAL FOR STAINLESS STEEL
- ★ A MUST FOR TRAINING

For full details contact sole manufacturers

**A.A. TOOLS**

WHITEACRE ROAD, HURST ASHTON-UNDER-LYNE LANCs.



PATENTERS AND MAKERS OF TOOLS FOR SHEET METAL & WIRE WORKERS

# QUARTZ CHRONOMETERS & TIMERS



Additions to our range of electronic timing instruments include a precision timer with START/STOP and RESET facilities, and a combined Chronometer/Timer with completely independent timing circuits and a shared digital display.

Send S.A.E. for full details. Telephone Penn 4661 (STD Code 049481). Trade and overseas enquiries welcome.

Model Number and Description	Price
401-6 (hours, minutes, seconds) Chronometer	£54.60
401-6-R (As 401-6, with Ni Cd battery) Chronometer	£68.90
402-6 (Hours, minutes, seconds) Timer	£65.90
402-6-R (As 402-6, with Ni Cd battery) Timer	£79.90
403-6 (Hours, minutes, seconds) Chronometer/Timer	£77.00
403-6-R (As 403-6, with Ni Cd battery) Chronometer/Timer	£92.00

Add 8% VAT UK only, postage and packing included. No VAT for overseas orders, but add £6.50 per unit for air parcel post.

If an instrument is to be used in a motor vehicle or boat with the engine running, an additional internal voltage surge protection network is necessary, and is available for £1.50 extra (+VAT if applicable).

Marine versions also available — waterproof construction

- \* One second per month accuracy at 20°C
- \* High frequency AT-cut quartz crystal for best possible temperature stability
- \* All versions provide security against timing inaccuracies caused by mains-borne interference and short-term mains frequency variations
- \* Rechargeable nickel-cadmium battery versions offer not only portability but also protection against outright mains failure, may be left on charge continuously
- \* Rugged mechanical design ensures reliability for portable use
- \* Large, bright and easy to read LED display, 24-hour or 12-hour modes optional
- \* 220/240V mains or external battery operation 110V version also available
- \* Weight 0.5kg, Width 13cm, depth 5cm, height 10cm (12cm with stand)
- \* No-cost extras include precision engineered adjustable metal stand and power unit/battery charger
- \* Kits available for 401 models (all components and full instructions supplied)
- \* Many special options available to industrial purchasers including 1 second output pulses, relay operated start/stop etc
- \* One-year full guarantee, which applies also to correctly-assembled kits

To: **ELECTRO SYSTEMS AND TIMING CO.**  
48 Robinson Road, Loudwater  
High Wycombe, Bucks., HP13 7BJ  
ENGLAND

Please supply

401-6     401-6-R     402-6     403-6  
 401-6 Kit     401-6-R Kit     402-6-R     403-6-R  
 Over voltage protection

U.K. residents add 8% VAT

Name \_\_\_\_\_  
Address \_\_\_\_\_

Enclose cheque/p.o. for £ \_\_\_\_\_

# BRIDGE ELECTRONICS COMPONENTS

AC 128 .13	BF 180 .25	2N2904 .18
AC 127 .13	BF 181 .25	2N2905 .18
AC 128 .11	BF 200 .25	2N2906 .18
AC 151 .18	BF 194 .09	2N2907 .18
AC 152 .25	BF 195 .09	2N2926G .09
AC 153 .27	BF 198 .12	2N3053 .20
AC 176 .14	BF 199 .12	2N3054 .40
AC 187K .27	BF 257 .34	2N3055 .45
AC 188K .27	BF 258 .34	2N3393 .12
AD 161 .35	BF 219 .24	2N3441 .56
AD 162 .36	BFX 20 .22	2N3442 .96
BA 102 .10	BFX 30 .22	2N3638 .10
BAX 13 .03	BFX 84 .20	2N3702 .10
BAX 16 .04	BFX 85 .27	2N3702 .10
BC 107 .09	BFX 88 .20	2N3703 .10
BC 108 .09	BFY 50 .19	2N3104 .10
BC 109 .09	BFY 51 .19	2N3105 .10
BC 107 .09	BFY 52 .19	2N3106 .10
BC 148 .09	BY126 .11	2N3708 .10
BC 149 .09	BY127 .11	2N3771 .125
BC 187 .10	OA47 .06	2N3772 .135
BC 188 .10	OA50 .04	2N3773 .200
BC 189 .10	OA91 .04	2N3904 .11
BC 182 .09	OA200 .05	2N3906 .12
BC 183 .09	OA202 .06	2N5294 .35
BC 184 .09	IN914 .04	2N5296 .35
BC 212 .095	IN4004 .05	2N5298 .35
BC 213 .095	IN4007 .06	2N3794 .20
BC 214 .095	IN4148 .03	2N3819 .30
BC 237 .08	1S920 .05	2N3820 .55
BC 238 .08	1S921 .05	2N4036 .55
BC 239 .08	1S923 .05	2N4037 .40
BC 307 .09	2N697 .15	2N4286 .20
BC 308 .09	2N698 .14	2N4287 .20
BC 309 .09	2N706 .10	2N5060 .25
BC 327 .12	2N708 .10	2N4289 .12
BC 328 .12	2N916 .23	2N5447 .25
BCY 70 .13	2N1305 .25	2N5449 .12
BCY 71 .13	2N1307 .25	2N5457 .30
BCY 72 .12	2N1308 .25	2N5458 .27
BD 131 .30	2N1613 .15	2N6277 .40
BD 132 .30	2N1711 .15	40361 .45
BD 135 .25	2N2218 .175	40362 .40
BD 136 .25	2N2218A .18	40408 .42
BD 137 .27	2N2219 .175	40409 .42
BD 138 .28	2N2219A .18	40410 .42
BD 139 .28	2N2221 .175	40602 .88
BD 140 .32	2N2221A .18	40636 .100
BDY 56 1.00	2N2222 .175	40673 .60
BF 115 20	2N2646 .30	

## FULLY GUARANTEED

Mail order only V.A.T. extra p&p 20p  
Bridge Electronics  
PO Box No. 10 Fishponds Bristol BS16 2LX

# J. LINSLEY HOOD


HIGH QUALITY AMPLIFIERS AND TEST EQUIPMENT available from

Examples: **TELERADIO HI FI**

75 Watt Amplifier, PA Module	£12.00 (Kit)	£15.95 (Made)
Pre-amp Module	£10.25 (Kit)	£14.50 (Made)
P.S.U. from	£18.50 (Kit)	£21.00 (Made)
F.M. Tuner, basic kit	£32.00 (p.p. 70p)	
de luxe p.b. version	£37.50 (p.p. 70p)	
Stereo Decoder	£4.85 (Kit)	£5.85 (Made)
Millivoltmeter Kit	£15.25 (Kit) (Tax 8%)	
Low Distortion Audio Osc.	£9.50 (Kit) (Tax 8%)	
Third Harmonic Analyser	£20.25 (Kit) (Tax 8%)	
Reg. P.S.V. 0/60v 1A	£17.50 (Kit), Tax 8%	

Tax extra 25% where unmarked. P/P extra (min. 25p)

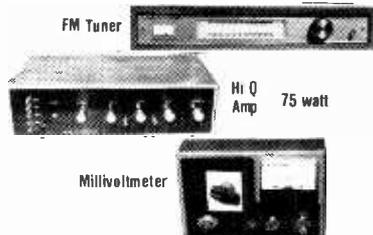FOR DETAILED AND ILLUSTRATED LISTS SEND S.A.E.



325 Fore St, Edmonton, London, N.9  
01-807 3719 Closed Thursdays

**SOWTER TYPE 3678 MULTITAP MICROPHONE TRANSFORMER**  
Primary windings for 600 ohm, 200 ohm and 60 ohm with Secondary loadings from 2K ohm to 10 K ohm. Frequency response plus/minus 1/2 dB 20 Hz to 25 KHz. Contained in well finished Mumetal box, 33mm diameter by 22mm high, with colour coded end leads, low distortion DELIVERY (small quantities) EX STOCK. HIGHLY COMPETITIVE PRICE FULL DETAILS ON REQUEST.  
E. A. SOWTER LTD., Dedham Place, Ipswich IP4 1JP. Telephone 0473 52794

WWW — 030 FOR FURTHER DETAILS

## EXCLUSIVE OFFERS

### WORLD-WIDE RANGE NEVER BEFORE OFFERED

COMPLETE TRANSPORTABLE H.F. COMMUNICATIONS CENTRE housed in Air Conditioned TRAILER fitted two COLLINS KWT-6 500W 8.S.B. Transmitter-Receiver and one COLLINS Receiver all fully tuneable 2 to 30 mcs digital readout synthesised frequency control, with line amplifiers and inputs, operating position and remote control facilities and ancillary equipment. Power input 115V or 230V A.C. Full details on application.

PHILCO HC-150 POINT-TO-POINT STRIP RADIO HF RECEIVERS 2/30 mcs. Ten fully tuneable channels to 0-5 kes with synthesisers, single and diversity reception on 1SB, DSB, SSB with 4 sub-bands to each channel. Full details and prices on application.

### HIGHEST QUALITY 19" RACK MOUNTING CABINETS & RACKS

Our Ref.	Height in inches	Width in inches	Depth in inches	Rack Panel Space in ins.	Price
CL	30	60	36	42	£12.50
CR	30	30	20	—	£24.00
DM	70	20	26	138	£21.00
FA	85	22	36	160	£22.00
FC	52	25	22	47	£17.00
FG	11	19	18	10	£11.00
FH	15	21	17	11	£12.00
FJ	15	21	15	12	£12.00
FN	70	24	20	68	£17.00
LL6	11	21	17	9	£15.00
LL7	16	20	12	14	£15.00
LL8	10	20	10	9	£15.00
LL9	17	21	17	14	£15.00
LL10	52	21	19	46	£15.00
MM	75	22	26	68	£22.00

Also Consoles, twin and multi-way Cabinets.

### OPEN RACKS

Our Ref.	Height in inches	Channel Depth	Rack Panel Space	Base	Price
RF	85	3	79	15	£11.00
RG	57	2	51	14	£9.00

Full details of all above on request.

We have a large quantity of "bits and pieces" we cannot list—please send us your requirements we can probably help—all enquiries answered.

- \* Collins KWT-6 SSB Transceivers P.U.R. £45.00
- \* Rhode and Schwarz HUZ Field Strength Measurer P.U.R. £45.00
- \* Intertechnique SA40 Spectrum Analysers P.U.R. £40.00
- \* Telegon D-33 d/b Oscilloscopes £30.00
- \* Inside Cabinet Shelf Sliders £3.00
- \* DG-7/32 C.R.T.'s £15.00
- \* Remscope Storage Scope with tracer £45.00
- \* Textronic 519 Scope 1GHZ £47.00
- \* Telegon D-33 Oscilloscopes C Amp P.U.R. £2.00
- \* M.V.R. Action Replay 20 sec. Videocassette P.U.R. £2.00
- \* Gresham quality enclosed chokes, 5H 200 m/a £3.00
- \* Dow Keu Co-ax. Relays SPST 12 to 110v A.C. P.U.R. £18.00
- \* Racal 1KW S.S.B. Linear amplifiers 1.5/30 mcs P.U.R. £40.00
- \* Advance HI Signal Generators. 15/50Kcs P.U.R. £48.00
- \* Varian VA175EA Backward Wave Oscillators P.U.R. £48.00
- \* Kinel Standard Voltmeter .001/600 Vx .001v £65.00
- \* Tally 5/8 Track Tape Readers 120 cps £22.00
- \* 2 KVA Auto-Transformers £30.00
- \* Coutant 40v 30A Power Supplies £29.00
- \* 15 foot 15 inch Lattice Steel Mast Sections £35.00
- \* Cintel 2 KV Power Supplies £22.00
- \* Valradio 400 watt Inverters 24v to 230 VAC £60.00
- \* Cavkell FU 4 Band Pass Filter Testers

We have a quantity of Power Transformers 250 watts to 15KVA at voltages up to 40KV. Best quality at low prices. List available.

- \* Racal RA-63 SSB Adaptors, new £70.00
- \* Racal RA-237 L-W Converters, new £70.00
- \* 19" Blank Rack Panels 8 1/2 inch high £1.00
- \* Ampco Electro-Stat Photo Copier Electrostatic £40.00
- \* Ampco Dial a Copy Photo Copier Electrostatic £60.00
- \* Hewlett Packard 524C Digital Counter P.U.R. £23.00
- \* Airmec 702 Sig. Generators 30 cve/30 k/cve £24.00
- \* Portable Mains Battery Floodlights £24.00
- \* 400 channel Pulse Height Spectrum Analysers P.U.R. £24.00
- \* Solarton 5/25000 cve. Oscillators £24.00
- \* Addo 5/8 track Tape Punches £48.00

We have a varied assortment of industrial and professional Cathode Ray Tubes available. List on request.

## INSTRUMENTATION-TAPE RECORDER-REPRODUCERS

- \* Ampex TM-2 1/4", 4 speeds, 7 tracks
  - \* Ampex 501 1/4", 6 speeds, 2 tracks
  - \* Ampex FR600 1/2", 4 speeds, 7 tracks
  - \* Ampex FR600 1", 4 speeds, 14 tracks
  - \* D.R.I. RM-1 1/4", 4 speeds, 4 tracks
  - \* EMI BTR-1 1/4", 1 speed, 1 track
  - \* EMI R301G 1/4", 2 speeds, 2 tracks
  - \* Mincom CMP-100 1/4", 1, 1, 6 speeds, 7 tracks
  - \* Racal T.5000, 1/2" speed, 7 tracks
  - \* Leavers Rich DA-2P, 1/4", 2 speeds, 2 tracks
- Prices of above £70 to £400

## COMPUTER HARDWARE

- \* PRINTER, High speed 1000 lines p.m.
- \* TAPE READER, High speed 5/8 track 800 c.p.m.

Prices on Application

PLEASE ADD V.A.T. AT APPROPRIATE RATE TO ABOVE

**P. HARRIS ORGANFORD-DORSET**  
BH16 6BR  
BOURNEMOUTH-785051

# Wilmslow Audio

**THE firm for speakers!**



Baker Group 25, 3, 8, or 15 ohm	£8.64
Baker Group 35, 3' 8 or 15 ohm	£10.25
Baker Deluxe, 8 or 15 ohm	£13.75
Baker Major, 3, 8 or 15 ohm	£11.87
Baker Regent, 8 or 15 ohm	£10.00
Baker Superb, 8 or 15 ohm	£18.12
Celestion HF1300 8 or 15 ohm	£7.75
Celestion MH 1000 horn, 8 or 15 ohm	£13.50
Decca London and X over	£42.25
Decca DK30 and X over	£24.06
EMI 13 x 8, 150 d/c, 3, 8 or 15 ohm	£2.94
EMI 13 x 8, Type 350	£9.56
EMI 13 x 8, 25 watt bass	£9.00
EMI 8 x 5, 10 watt, d/c, roll/s 8 ohm	£3.95
EMI 14" x 9" Base 80	£13.25
Elac 59RM 109 15 ohm, 59RM 1148 ohm	£3.44
Elac 6 1/2" d/c roll/s 8 ohm	£4.06
Fane Pop 15 watt 12"	£5.25
Fane Pop 25T 30 watt 12"	£7.50
Fane Pop 50 watt, 12"	£12.00
Fane Pop 55, 12" 60 watt	£13.95
Fane Pop 60 watt, 15"	£17.25
Fane Pop 70 watt 15"	£18.75
Fane Pop 100 watt, 18"	£29.95
Fane Crescendo 12A or B, 8 or 15 ohm	£34.50
Fane Crescendo 15, 8 or 15 ohm	£47.50
Fane Crescendo 18, 8 or 15 ohm	£62.95
Fane 807T 8" d/c, roll/s, 8 or 15 ohm	£5.75
Fane 801T 8" d/c roll/s 8 ohm	£9.95
Goodmans 8P 8 or 15 ohm	£5.50
Goodmans 10P 8 or 15 ohm	£5.80
Goodmans 12P 8 or 15 ohm	£13.95
Goodmans 12P-D 8 or 15 ohms	£16.95
Goodmans 12P-G 8 or 15 ohms	£15.95
Goodmans Audiom 100 15-ohm	£13.90
Goodmans Audiom 200 8 ohm	£13.90
Goodmans Axent 100 8 ohm	£8.44
Goodmans Axiom 402 8 or 15 ohm	£20.00
Goodmans Twinaxiom 8" 8 or 15 ohm	£10.14
Goodmans Twinaxiom 10" 8 or 15 ohm	£10.75
Kef T27	£6.06
Kef T15	£6.94
Kef B110	£8.37
Kef B200	£9.50
Kef B139	£16.95
Kef DN8	£2.31
Kef DN12	£5.99
Kef DN13	£4.50
Richard Allan HP88 8" 45 watt	£13.25
Richard Allan CG8T 8" d/c roll/s	£7.50
STC 400 1 G super tweeter	£6.56
Baker Major Module, each	£13.44
Goodmans Mezzo Twinkit, pair	£47.19
Goodmans DIN 20, 4 ohm, each	£14.75
Helme XLK35, pair	£24.00
Helme XLK40, pair	£35.00
Helme XLK30, pair	£19.00
Helme XLK50, pair	£56.00
Kefkit 1, pair	£53.00
Kefkit III, each	£48.00
Richard Allan Twinkit, each	£10.95
Richard Allan Triple 8, each	£16.50
Richard Allan Triple, each	£23.95
Richard Allan Super Triple, each	£28.75
Richard Allan RA8 kit, pair	£42.00
Richard Allan RA82 kit, pair	£63.00
Wharfedale Linton 2 kit (pair)	£23.12
Wharfedale Glendale 3 kit, pair	£40.62
Wharfedale Dovedale 3 kit, pair	£63.12
All Radford, Gauss, Castle, Jordan Watts, Eagle, Lowther, Peerless Tannoy units in stock	

Prices correct at 29.10.75  
**INCLUDING VAT AT 25% ON HI-FI**  
**8% ON PRO AND PA**

Cabinets for PA AND HiFi, wadding, Vynair, etc.  
 Send stamp for free booklet "Choosing a Speaker"  
**FREE with all orders over £7 — HiFi**  
**Loudspeaker Enclosures book**  
**All units are guaranteed new and perfect.**  
 Prompt despatch  
 Carriage: Speakers 50p each, 12" and up 75p each,  
 tweeters and cross-overs 30p each, kits 80p each  
 (£1.60 pair).

## WILMSLOW AUDIO

Dept. vvvv  
**Loudspeakers & Export Dept: Swan Works,**  
**Bank Square, Wilmslow, Cheshire SK9 1HF.**  
**Discount HiFi, PA etc: 10 Swan Street,**  
**Wilmslow. Radio, HiFi, TV, Radio: Swift of**  
**Wilmslow, 5 Swan Street, Wilmslow. Tel.**  
**(Loudspeakers) Wilmslow 29599, (HiFi, etc.)**  
**Wilmslow 26213**

WW-058 FOR FURTHER DETAILS

**When you need to hire Video-**  
**it pays to contact the most experienced**  
**video company in the business**




**R.E.W. HOUSE**  
**10, 12 HIGH STREET**  
**COLLIERS WOOD**  
**LONDON SW19 2BE**  
**PHONE: 01-540 9684**

Also at **CENTRE POINT**  
**20/21 ST. GILES HIGH STREET**  
**LONDON, WC2**  
**PHONE: 01-240 3066**

**Quartz Crystal Units**  
 ACCURATE RELIABLE  
 Private enquiries, send 10p in stamps for brochure  
**THE QUARTZ CRYSTAL CO. LTD.**  
 Q.C.C. WORKS, WELLINGTON CRESCENT,  
 NEW MALDEN, SURREY. 01-942-0334 & 2988

**EURO CIRCUITS**  
 Printed Circuit Boards - Master layouts -  
 Photography - Legend printing - Roller tinning -  
 Gold plating - Flexible films - Conventional  
 fibre glass - No order too large or too small -  
 Fast turnaround on prototypes.  
 All or part service available NOW.....  
**EURO CIRCUITS LTD**  
 Highfield House  
 West Kingsdown  
 Nr. Sevenoaks, Kent. WK2344

**STABILIZER**  
 With two years' experience of frequency shifters the new Stabilizer includes all the features which have shown themselves to be desirable in 3 unit for noise reduction. It provides shifts between 1 and 10 Hertz either upwards or downwards and has a front panel gain control signal overload LED and SHIFT/BYPASS switch as well as a mains switch and neon. This unit has a considerably lower noise level than any previous shifter and hum pickup within the small case is avoided by the mains transformer and input transformer in the balanced version being in mu-metal screening cans. The input amplifier is protected from high voltage spikes on the signal line whether from the valve equipment or occurring through static or earth leakage voltages while a system is being plugged up. The output line driving amplifier is preceded by a 24Hz high pass filter which not only provides further rejection of the shifting oscillator but is general good practice before feeding into a power amplifier.  
 Available as a boxed unit with either balanced or unbalanced signal lines. Rack mounting version also available offering studio quality slider. SHIFT control duplicated jack and XLR connectors and a smart anodised finish with an engraved front panel.

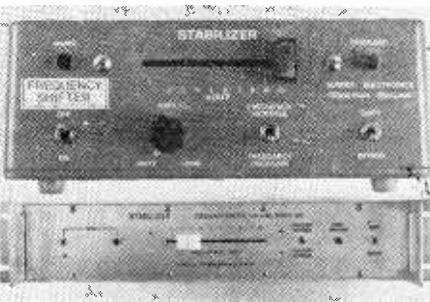

Shifters are proving effective in the following situations  
 Sound reinforcement for television studio audiences  
 Foldback monitoring on stage  
 Live microphone telephone conference systems with a 5Hz shift each way giving 10Hz round the loop, which is effective in the small non-reverberant rooms involved  
 Group hearing aid systems for teaching deaf children  
 Microphones or radio microphones for discussion groups or floor questioners who are within the intended coverage of the PA loudspeakers as well as for straightforward sound reinforcement and public address  
**+5Hz FIXED SHIFT CIRCUIT BOARDS FOR WW**  
**July 1973 article**  
 Small enough to be built inside the cabinets of many amplifiers  
 Complete kit and board £24 including psu and mains transformer DESIGNER APPROVED  
 Board built and aligned £31

Write or ring for leaflet giving full specifications for this or any other item -  
**STEREO DISC AMPLIFIER 10 OUTLET DISTRIBUTION AMPLIFIER**  
**MICROPHONE PREAMPLIFIER PPM DRIVE CIRCUITS and Ernest Turner**  
**PPM MOVEMENTS 642 643 and TWIN** all meeting IBA requirements  
**SPECTRUM SHIFTER:**  
 Variable shifts 0.1 - 1000Hz for weird special effects on speech or music  
**SURREY ELECTRONICS**  
**The Forge, Lucks Green, Cranleigh**  
**Surrey GU6 7BG (STD 04866) 5997**  
 CASH WITH ORDER less 5% UK post free add VAT at 8%

**the audio amateur?**  
 The brain boggles at what old Johann could have done with his own console, preamp, 8-in-2 out mixer, octave equalizer, electrostatic speakers, or 24 inch woofer.  
 Come boggle with us.  
**theAudio Amateur?** Yellow Oak Cottage  
 Tillington nr. Hereford HR48LQ  
 Send now for a free prospectus.  
 Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 W

**Housing problems?**  
 West Hyde will have a case to meet your needs. See last or next issue Check now. Ring **WEST HYDE**  
**CONTIL MOD-2 MOD-3, SAMOS BRIGHTCASE AMTRON, MINOS ENVIRONMENTAL HEAVY DUTY CASES**  
**WEST HYDE DEVELOPMENTS LIMITED**  
 Ryefield Crescent, Northwood Hills Northwood, Middx. HA6 1NN  
 Tel. Northwood 24941/26732. Telex: 923321

**SOWTER TRANSFORMERS**  
 FOR SOUND RECORDING AND REPRODUCING EQUIPMENT  
 We are suppliers to many well-known companies, studios and broadcasting authorities and were established in 1941. Early deliveries. Competitive prices. Large or small quantities. Let us quote.  
**E. A. SOWTER LTD.**  
 Transformer Manufacturers and Designers  
 12 Dedham Place, Waterworks Street Ipswich IP4 1JP. Telephone 0473 52794  
**WW-030 FOR FURTHER DETAILS**

**WE PURCHASE ALL FORMS OF ELECTRONIC EQUIPMENT AND COMPONENTS, ETC.**  
**SPOT CASH**  
**CHILTMead LTD.**  
 7, 9, 11 Arthur Road, Reading, Berks.  
 Tel: 582 605

**NEW EDITION  
RADIO VALVE AND  
SEMICONDUCTOR  
DATA**

by A. M. Ball **PRICE £2.50**

**TTL COOKBOOK** by D. E. Lancaster. Price **£5.75**

**SCR MANUAL** inc. Trides by G. E. Price **£2.00**

**PRINCIPLES OF TRANSISTOR CIRCUITS** by Amos S. W. Price **£3.55**

**SOLID STATE HOBBY CIRCUITS** by R.C.A. Price **£1.25**

**UNDERSTANDING CMOS INTEGRATED CIRCUITS** by R. Melen. Price **£2.89**

**TRANSISTOR CIRCUIT DESIGN** by Texas. Price **£5.60**

**FOUNDATIONS OF WIRELESS AND ELECTRONICS**. 9th Edition. Scroggie, M. G. Price **£4.25**

**DATA COMMUNICATIONS**. An introductory guide by Hebditch, D.L. Price **£4.55**

**LINEAR I.C. PRINCIPLES, EXPERIMENTS & PROJECTS** by Noll, E. N. Price **£5.00**

**MODERN RECORDING TECHNIQUE** by Runstein, R.E. Price **£5.35**

★ PRICES INCLUDE POSTAGE ★

**THE MODERN BOOK CO.**

SPECIALISTS IN SCIENTIFIC & TECHNICAL BOOKS

19-21 PRAED STREET LONDON W2 1NP

Phone 723 4185  
Closed Sat 1 p.m.

**DIRECT COMMUNICATIONS**

division of

**DIRECT ELECTRONICS LTD.  
INTERCOMMS & TELEPHONES**

- Simple 2-way wall/desk with 100ft. cable. 6v Batt. or Power Supply. £16 (£1 P&P).
- Similar but 2 to 7-way instrument only. Installation Diagram. £8.50 each (50p).
- Superior 2 to 6-way Siemens & Halske. Wall/desk conversion kit, term block and cord. £10 (50p).
- AUTOMATIC INSTRUMENTS. Strowger compatible or PX working. New/refurbished/2nd hand. 232 332 706 746 722 (Trimfone) etc. Special and foreign types.
- ULTRA MODERN TYPES. "Gondola" International: Touch-Button-Dial: Charleston (Candlestick), etc. from £32.85.
- Jacks: Plugs: Cords: Term. Blocks: Cables (up to 25-way and 50 pair) etc.
- Entrance Phones & Electric Latches, with or without Intercomm. Facility.
- Telephone Amplifier (1-way) £6-95 (35p); Hands-free Tele. Amp. (2-way conversation) £9-50 (50p).
- ★ TRANSISTORISED UNITS. Simple 2-way Batt. Intercomm. £7.75 (50p): Batt. Baby Alarm £5.25 (50p): Intercomm. with Roving Master £9.50 (50p).
- ★ Wireless Intercomm. (Just plug into mains) 2-way £20 (£1): Master plug 3 subs (4-way) Batt.-op. Mains adaptor £2.95 (35p).

Add V.A.T. ● = 8%, ★ = 25% on post paid price

TRADE ENQUIRIES WELCOMED

MANY SURPLUS ELECTRONIC BARGAINS FROM OLD STOCK STILL LEFT — COME AND DO A DEAL!

34 LITTLE STREET  
LONDON WC2H 7BD  
Tel. 01-437 2524

**PRECISION  
POLYCARBONATE CAPACITORS**

440V All High Stability — Extremely Low Leakage

RANGE: DIMENSIONS	VALUE (F)	1 (mm)	2 (mm)	PRICE EACH:	± 1%	± 2%	± 5%
0.1µF	27	12.7	51p	0.47µF	67p	50p	43p
0.22µF	33	16	64p	1.0µF	82p	62p	52p
0.25µF	33	16	67p	2.2µF	96p	75p	61p
0.47µF	33	19	80p	4.7µF	£1.62	£1.13	94p
0.5µF	33	19	87p	6.8µF	£1.96	£1.38	£1.13
0.68µF	50.8	19	93p	10µF	£2.40	£1.95	£1.64
1.0µF	50.8	19	£1.03	15µF	£3.22	£2.79	£2.24
2.0µF	50.8	25.4	£1.44	22µF	£4.78	£3.68	£3.08

\*TANTALUM BEAD CAPACITORS — Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.8, 6µF at 15V/25V or 35V; 10µF at 16V/20V or 25V; 22µF at 6V or 16V; 33.0µF 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. ALL at 10p each, 10 for 95p, 50 for £4.

TRANSISTORS & I.C.'s

AC128 14p	BC268A/384* 10p	OC71 12p
AC176 16p	BC547/558A 12p	*2N2928G 12p
AD149 40p	BCY72 12p	*2N2928O 11p
AF178 36p	BD131/132 39p	*2N2928Y 11p
AF238 38p	BF115/167 22p	2N3054 85p
BC107/8/9 9p	BF173 24p	2N3055 50p
*BC114 12p	BF178 26p	2N3702/ 3704 11p
*BC147/8/9 10p	BF184 22p	*TIP30A 52p
*BC153/154 12p	*BF194/195* 12p	TIP31A 55p
*BC157/8/9 12p	*BF196/197* 12p	TIP32A 64p
BC177 18p	BF200 22p	TIP3055 55p
*BC182/183L 11p	*BF262/263* 60p	*MPU131 40p
*BC183/183L 11p	BFY50/51/52 20p	NE555 61p
*BC184/184L 12p	BFX84/86/88 20p	741C 32p
*BC212/212L 14p	BFX85 26p	ZN414 11.15
*BC213/213L 11p	BR101 41p	SN76013ND 1.50
*BC214/214L 11p	GET872 25p	
BC267 12p	OC44/OC45 14p	

POPULAR DIODES — 1N914 8p, 8 for 45p, 18 for 90p; 1N916 8p, 8 for 45p, 14 for 90p; 1S44 5p, 11 for 50p, 24 for £1.00; 1N4148 5p, 6 for 27p, 12 for 46p; 1N4001 5p; 002 6p; 003 6p; 004 7p; 006 8p; 007 8p.

LOW PRICE ZENER DIODES — 400mW. Tol. ± 5% at 5mA. Values available: 3V, 3.3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13V, 13.5V, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V. All at 7p each; 5 for 33p; 10 for 65p. SPECIAL OFFER: 100 Zeners for £6.00.

\*RESISTORS — High stability, low noise carbon film 5%, ¼W at 40°C, ½W at 70°C. E12 series only — from 2.2Ω to 2.2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value. SPECIAL PACK. 10 of each value 2.2Ω to 2.2MΩ (730 resistors) £5.

SILICON PLASTIC RECTIFIERS — 1.5 amp, brand new wire ended DO27; 100 P.I.V. 7p (4 for 26p), 400 P.I.V. 8p (4 for 30p).

BRIDGE RECTIFIERS — ½ amp, 200V 40p, 350V 45p, 600V 55p.

\*SUBMINIATURE VERTICAL PRESETS — 0.1W only. ALL at 5p each: 50kΩ, 100kΩ, 220kΩ, 470kΩ, 680kΩ, 1kΩ, 2.2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 68kΩ, 100kΩ, 250kΩ, 680kΩ, 1MΩ, 2.5MΩ, 5MΩ.

PLEASE ADD 15p POST AND PACKING ON ALL ORDERS BELOW £5. ALL EXPORT ORDERS ADD COST OF SEA/AIR MAIL.

PLEASE ADD 8% VAT to all items except those marked with \* which are 25%.

Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona fide companies.

**MARCO TRADING**  
(Dept. D12)  
The Old School, Edstaston, Nr. Wem, Shropshire  
Tel. Whixall (Shropshire) (STD 094872) 464/5  
(Proprs: Minicost Trading Ltd.)

**Now! The  
day-by-day  
yearbook.**

Day-by-day usefulness throughout 1976—that's the keynote of our new, completely revised Yearbook. New features include a week-at-a-glance desk diary, and a fact-packed Serviceman's Section. Plus the industry's most comprehensive buyers' guide, big legal and technical sections, and pages of valuable trade names and addresses. Order your copy now!


To: General Sales Dept., IPC Electrical & Electronic Press Ltd., Room 11, Dorset House, Stamford St., London SE1 9LU. Please send me.....copies of Electrical & Electronic Trader Year Book and Diary 1976 @ £5.50 each, inclusive of postage and packaging. I enclose cheque p.o. for.....

Name.....  
Address.....

\* Cheques should be made payable to IPC Business Press Ltd.

**Electrical and Electronic  
Trader**  
Company registered in England Registered No. 677128.  
Registered address Dorset House, Stamford St., SE1 9LU.

**TIME SIGNAL RECEIVERS**

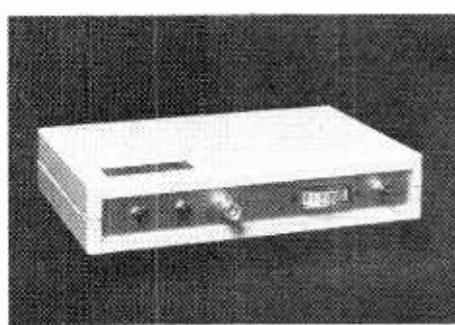

**TOOLEX 60 KHz MSF RUGBY  
RADIO RECEIVERS**

**MODEL MSFI**  
Low Power Unit; 1500 hrs independent operation from Internal Battery; Case 8" x 5" x 1 ½"; External Aerial; assembled and tested circuit alone available if required.

**MODEL MSF.T1**  
Phase locked Loop System; 10/20 hrs independent operation; External Aerial; External Supply; Case 4 ½" x 2 ½" x 1 ½"; also available in Kit Form or assembled and tested circuit only.

Full specifications from:

**TOOLEX**  
BRISTOL ROAD, SHERBORNE, DORSET  
TEL. 093-581 4359

WW-101 FOR FURTHER DETAILS

# LOW FREQUENCY ANALYSER

50Hz-50kHz  
ASSEMBLY AND INSTRUCTION  
INFORMATION S.A.E.

PRICE £27 p&p 75p

Board, modules and all components (excluding P.U.).

# 12" CRT

Magnetic Deflection. Blue Trace Yellow Afterglow (P7). Information and recommended circuits with all purchases. Brand new, boxed, **£4 each**. Carriage £2.

V.A.T. at 8%

# X-Y RECORDERS

Advance, Moseley  
Hewlett Packard

Price from:  
**£80 each**

## CHILTMEAD LTD

7-9 ARTHUR ROAD, READING, BERKS. (rear Tech. College). Tel. Reading 582605

# INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 83-95

	PAGE		PAGE		PAGE
A.A. Tools	96	Foulsham-Tab Ltd.	62	Q-Max Electronics Ltd.	13
Aero Electronics Ltd.	20, 24	Fraser-Manning Ltd.	96	Quality Electronics Ltd.	14
Alice Broadcasting (Stancoil Ltd.)	23	Fulton Electronic Labs. Ltd.	31	Quartz Crystal Co. Ltd.	98
Ambientacoustics	62	Future Film Developments Ltd.	31	Queck, Eugen	30
Ambit International Ltd.	29, 56	Fyde Electronic Labs. Ltd.	15		
Amplicon Electronics Ltd.	60			Radford Audio Ltd.	18
Antex Ltd.	35	Gould Advance Ltd.	7	Radford Laboratories Ltd.	11
A.S.P. Ltd.	50	Grampian Reproducers Ltd.	20	Radio Shop, The	56
A. & S. T.V. Components	64	Greenwood Electronics Ltd.	24	Ralfe, P.	62
Audio Amateur	98			Rank Film Equipment	25
Aspen Electronics Ltd.	27	Harmsworth Townley & Co. Ltd.	Readers Card	Rastra Electronics Ltd.	63
Avo Ltd.	3	Harris Electronics (London) Ltd.	11, 19	R.C.S. Electronics	19
		Harris P.	97	Replecomps Ltd.	54
Barr & Stroud Ltd.	8	Hart Electronics	56	R.E.W. Audio Visual Co.	98
Barrie Electronics Ltd.	57	Henry's Radio Ltd.	72, 79	R.I. Audio	15
Bell & Howell Ltd.	36, 37	Hi-Fi Yearbook	60	Rola Celestion Ltd.	61
Bentley Acoustic Corp. Ltd.	72			R.S.T. Valves Ltd.	64
Beyer Dynamic (G.B.) Ltd.	27	I.L.P. (Electronics) Ltd.	16		
B.H. Component Factors Ltd	73	Icon Design	6	Samsons (Electronics) Ltd.	76
Bias Electronics Ltd.	29	Industrial Tape Applications Ltd	26	Scopex Ltd.	8
Bi-Pak Semiconductors Ltd.	28, 80, 81	Inland Motor Services (Reading) Ltd.	12	S.C.S. Components	76
Bi-Pre Pak Ltd.	59	Integrex Ltd.	17	S.E. Laboratories Ltd.	Bound-in Insert
Bradley, G. & E. Ltd.	Cover iii	International Rectifier Co.	43	Service Trading Co.	70
Brandenburg Ltd.	14	I.T.T. Components Group	34	Servo Data Ltd.	57
Brenell Eng.	26			Servo & Electronics Sales Ltd.	77
Bridge Electronics	97	J.H. Associates Ltd.	20	Shure Electronics Ltd.	42
Broadfields & Mayco Disposals	96			Sinclair Radionics Ltd.	40, 41
Bull, J., Electrical Ltd.	68	Keytronics Ltd.	96	Sintel	57
Bywood Electronics	52	Kinnie Components Ltd.	66	Sowter, E. A., Ltd.	97, 98
		Klark Teknik Ltd.	30	Southern Aviation	96
Cambridge Learning	9			Special Products Ltd.	14
Catronics	31	Laskys	44, 45	Strumech Eng. Ltd.	29
CDI Electronic Systems Ltd.	24	Levell Electronics Ltd.	1	Sugden, J. E. & Co. Ltd.	22
Chiltmead Ltd	69, 98, 100	Lexor Electronics Ltd.	20	Surrey Electronics	98
Chromasonic Electronics	47	Light Soldering Developments Ltd.	15	Swanley Electronics Ltd.	82
City Audio	66	Linstead Electronics	10	Swift of Wilmslow	82
Colomar (Electronics) Ltd.	71	Lynx (Electronics) London Ltd.	58		
Combined Precision Components Ltd.	52			Technomatic Ltd.	78
Computer Sales & Services	78	Macinnes Labs. Ltd.	16	Telcon Metals Ltd.	13
Crofton Electronics Ltd.	28	Magnetic Tapes Ltd.	25	Teleprinter Equipment Ltd.	50
C.T. Electronics Ltd.	65	Maplin Electronic Supplies	48	Teleguide Products (Tektronix U.K.) Ltd.	32
		Marco Trading Co.	99	Teleradio Special Products	97
Decon Laboratories Ltd.	25	McKnight Crystal Co.	96	Telford Products Ltd.	12
Dema Electronics International	79	McLennan Eng. Ltd.	26	Time Electronics Ltd.	50
Direct Electronics Ltd.	99	Marconi Instruments Ltd.	Cover ii	Toko U.K.	29
Dixons Technical Ltd.	28	Marshall, A., & Sons (London) Ltd.	55	Toolex	99
Dolby Noise Unit	21	Meteronic Ltd.	22	Trampex Electronics	54
Doram Electronics Ltd.	27	Mills, W.	58	Turner Electronics	29
Drake, Philip Electronic Ltd.	28	Modern Book Co.	99	Tyme & Gear	23
Dymar Electronics Ltd.	2	Multicore Solders Ltd.	Cover iv		
				United-Carr Supplies Ltd.	39
East Cornwall Components	68	Naim Audio	30	Wayne, Kerr, The, Co. Ltd.	5
Electrical & Electronic Year Book	99	Natural Sound Systems Ltd.	38	West Hyde Developments Ltd.	98
Electronic Brokers Ltd.	74, 75	Nombrex Ltd.	22	Whiteley Electrical Radio Co. Ltd.	10
Electro Systems & Timing Co.	97			Wilmslow Audio	98
Electrovalue Ltd	67	OCLI Optical Coatings Ltd.	19	Wilkinson, L. (Croydon) Ltd.	64
E/R/T Colour Faults Guide	67	OMB Electronics	23	Wireless World Annual	46
Euro-Circuits	98			Wireless World Circuit Designs	49
European Electronics Suppliers Guide	73	PB Electronics (Scotland) Ltd.	4	Wireless World Wallchart	83
Exetron Time Ltd	67	Powertan Electronics	51, 53	Wound Electronic Components Ltd.	52
		Precision Petite Ltd.	12	Wye Electronics Ltd.	22
Farnell Instruments Ltd.	11	Prosser Scientific Instruments	24		
Ferroglyph, The Co. Ltd.	31	Pulse Electronics Ltd.	22	Z. & I. Aero Services Ltd.	18, 82
Fi-Comp Electronics	50	Purnell Books.	Loose insert	Zettler (U.K.) Division	24



*We're experts on all of these*



HEWLETT



PACKARD

SOLARTRON

Schlumberger



RACAL instruments



ADVANCE  
*and many more.*

# For the Great Names a Great Service

Bradley Electronics are well known as manufacturers of precision electronic instrumentation. But there's another important aspect of our business – we're also experts on other people's products.

For 21 years our Services Division has been providing a first-class repair and recalibration service for all types and makes of electronic test and measuring equipment – from simple meters to complicated systems. Any manufacturer's instrument in the frequency range DC to 18 GHz – and to

36 GHz in some cases – collected and delivered back to your door ready to plug-in.

The Services Division has its own 35,000 sq ft factory, expert staff, comprehensive spares, and a Standards Laboratory approved by the British Calibration Service. It will supply calibration certificates for AC, DC and RF measurements. And, of course, our standards are directly traceable to NPL and NBS.

So – when your calibrator won't calibrate anymore, your generator

refuses to generate, or your counter stops counting – you know who to contact.

G & E BRADLEY LIMITED  
Electral House, Neasden Lane,  
London NW10 1RR  
Telephone: 01-450 7811  
Telex: 225583

A Lucas Company

**BRADLEY**  
electronics

The life and efficiency of any piece of electronic equipment can rest entirely on the solder used in its assembly. That is why for utmost reliability leading electronic manufacturers in the USA and in 106 other countries throughout the world insist on using Ersin Multicore Solder. It's the solder they have depended on for consistent high quality for more than 30 years.

If you are not already using Ersin Multicore Solder it must be to your advantage to investigate the wide range of Specifications which are available. Besides achieving better joints – always – your labour costs will be reduced and subsequently savings in overall costs of solder may be possible.

There are well over 1,000 Specifications, made to all International Standards to choose from, and here are just a few of the special solders that we manufacture:

**Savbit Alloy** – dramatically reduces erosion of copper wires and printed circuits and also reduces the wear of soldering iron bits.

**96S Silver Solder** – highest strength soft solder. Melting point 221°C. Bright and non-toxic. Replaces high temperature brazing alloys.

**95A alloy** – Melting range 236–243°C. For electrical connections subjected to peak temp. of approx. 240°C.

**H.M.P. alloy** – Melting range 296–301°C. Highest melting point soft solder for high service temperature applications.

**T.L.C. alloy** – Melting point 145°C. Lowest melting point Ersin Multicore solder for making joints on top of other solders and for heat sensitive components.

**L.M.P. alloy** – Melting Point 179°C. For soldering silver plated surfaces such as ceramic capacitors and soldering gold.

**Alu-Sol Multicore Solder** – for soldering aluminium.

**Arax acid-cored solder** – for non-electrical applications or pre-tinning of parts of difficult solderability (flux residue must be removed) which can then be assembled with Ersin Multicore Solder.

Write for Technical Bulletins, on your Company's letterhead, for products which interest you to:



## Multicore Solders Ltd.

Maylands Avenue,  
Hemel Hempstead, Hertfordshire, HP2 7EP  
Tel: Hemel Hempstead 3636 Telex: 82363



**Why have leading  
USA manufacturers specified  
British made Ersin Multicore  
solder for over 30 years?**