


wireless world

JANUARY 1976 35p

Speaker phase
A-level electronics



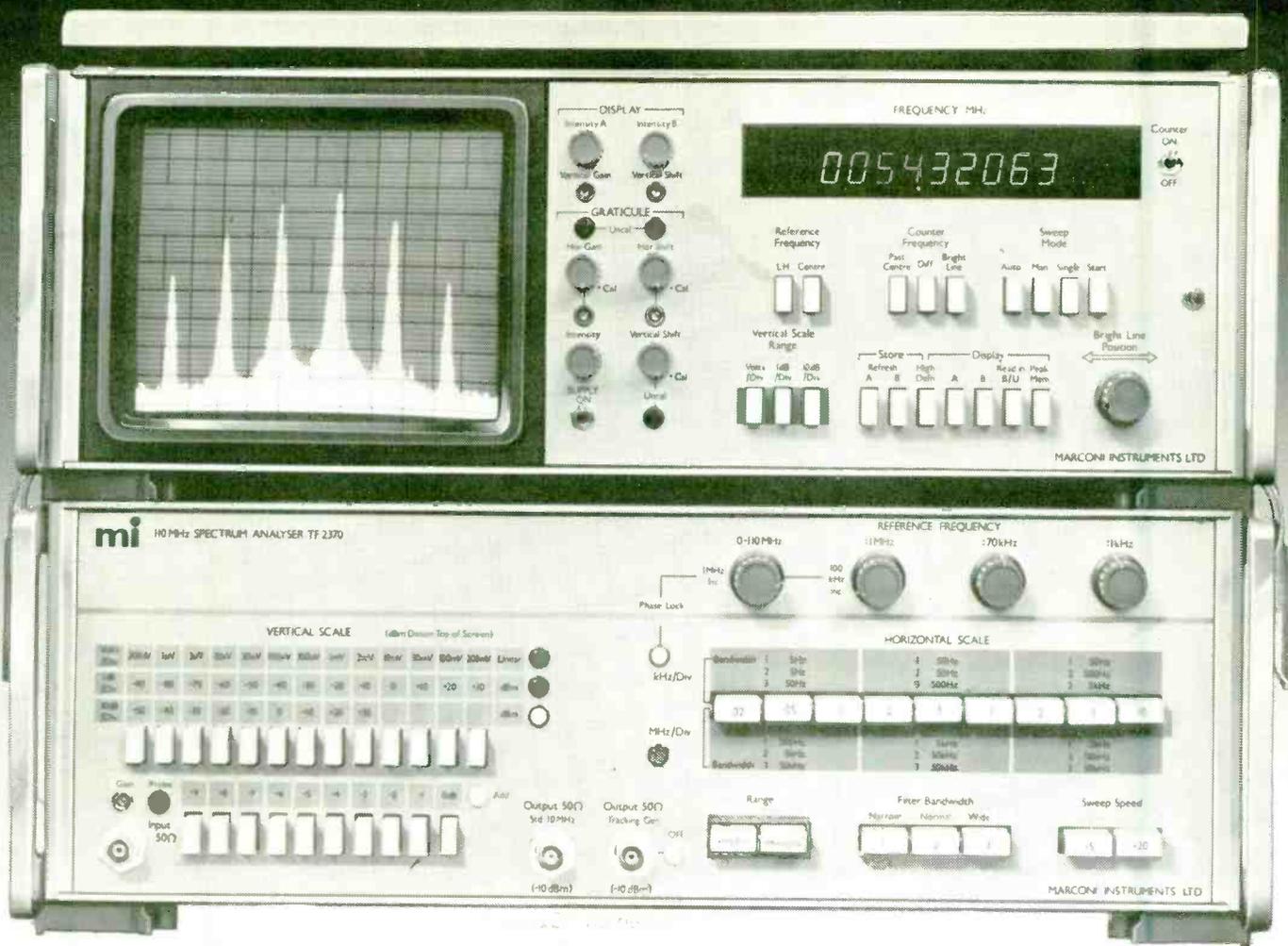Australia \$A1.20
Belgium Fr. 61.50
Canada \$1.50
Denmark Kr. 11.00
Finland Fmk. 6.20
Germany Dm. 4.50
Greece Dr. 45.00
Holland Dfl. 4.50
Italy L. 900
Malaysia M\$3.25
New Zealand \$NS1.20
Norway Kr. 10.00 incl. moms
Portugal Esc. 40.00
South Africa R. 1.10
Spain Ptas 80.00
Sweden Kr. 6.90 incl. moms
U.S.A. \$1.50



The Most Advanced Spectrum Analyser

You've never seen a faster, more accurate way of measuring frequency response from 30Hz to 110MHz

The TF 2370 Spectrum Analyser employs advanced technology to provide a complete system for measuring response, level, frequency, signal purity, modulation and much more, with a speed and degree of accuracy previously unobtainable. A digital memory permits the use of a standard monitor tube and internal logic selects gain ratios and sweep speeds for optimum performance. The specification speaks for itself:

- * Flicker-free 100 dB display of frequency response from 30 Hz to 110 MHz on a high brightness c.r.t.
- * Electronic graticule, with a $\pm 15\%$ variation of horizontal divisions for pin-point positioning against waveform display.
- * Three amplitude scales: one linear and two logarithmic with expansion to 1 dB/div. with an accuracy of ± 0.1 dB/dB.
- * 9-digit electronic counter automatically gives centre frequency, reads any other frequency corresponding to manually-adjusted 'bright line' position on display, or the difference frequency between the two, at the press of a

button. All to an accuracy of $\pm 2\text{Hz} \pm$ reference frequency accuracy on high resolution and manual. Internal reference frequency provided with setting accuracy of 1 in 10^7 .

- * Internal generator supplies synchronous signal source for measuring such items as networks and filters.
- * For comparative measurements, unique memory storage system will retain one display indefinitely as required, for simultaneous display with response produced by items under test.
- * Automatic adjustment of amplifier gains to give optimum lowest-noise performance with full protection against input overloading.
- * Automatic selection of optimum sweep speed.
- * With the 5 Hz filter, signals 100 Hz from a response at 0 dB can be measured to -70 dB.

Please send for full information or ask for a demonstration - seeing is believing!

mi: THE INNOVATORS

MARCONI INSTRUMENTS LIMITED,

Longacres, St. Albans, Hertfordshire, England, AL4 0JN. Telephone: St. Albans 59292 Telex: 23350.




A GEC-Marconi Electronics Company

WW-001 FOR FURTHER DETAILS

LEVELL

PORTABLE INSTRUMENTS

LOW COST OSCILLATORS

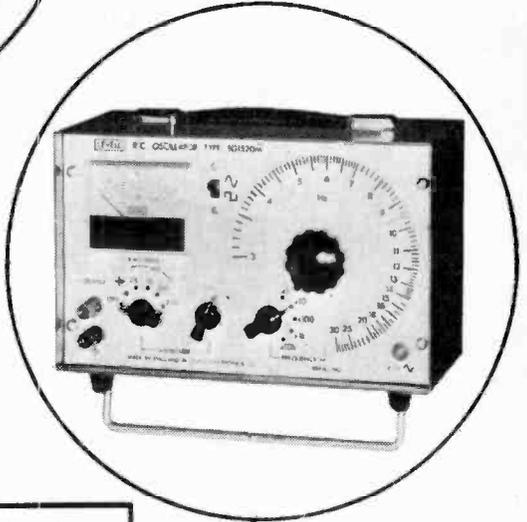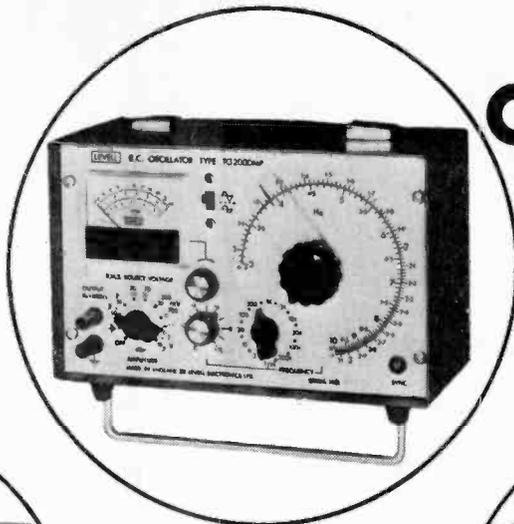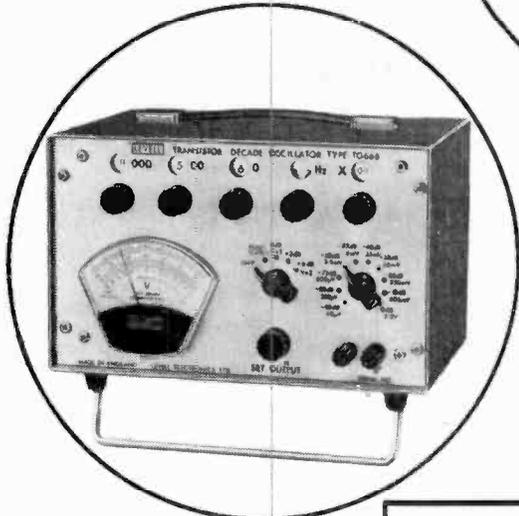

FREQUENCY	1 Hz to 1 MHz in 12 semi-decade ranges. 0 to 1% fine control included on TG200DMP.
ACCURACY	$\pm 2\% \pm 0.03\text{Hz}$.
SINE OUTPUT	7V r.m.s. down to $< 200\mu\text{V}$ with $R_s = 600\Omega$.
DISTORTION	$< 0.1\%$ to 5V, $< 0.2\%$ at 7V from 10Hz to 100kHz.
SQUARE OUTPUT	TG200D, DM & DMP only. 7V peak down to $< 200\mu\text{V}$. Rise time $< 150\text{nS}$.
SYNC. OUTPUT	$> 1\text{V}$ r.m.s. sine in phase with output.
SYNC. INPUT	$\pm 1\%$ freq. lock range per volt r.m.s.
METER SCALES	TG200M, DM & DMP only. 0/2V, 0/7V & $-14/+6\text{dBm}$.
SIZE & WEIGHT	260mm x 130mm x 180mm. 4.3kg.

TG200	TG200D	TG200M	TG200DM	TG200DMP
£63	£66	£73	£76	£80

FREQUENCY	0.2Hz to 1.22MHz on four decade controls.
ACCURACY	$\pm 0.02\text{Hz}$ below 6Hz. $\pm 0.3\%$ from 6Hz to 100kHz. $\pm 1\%$ from 100kHz to 300 kHz. $\pm 3\%$ above 300 kHz.
SINE OUTPUT	5V r.m.s. down to $30\mu\text{V}$ with $R_s = 600\Omega$.
DISTORTION	$< 0.15\%$ from 15Hz to 15kHz. $< 0.5\%$ at 1.5Hz and 150kHz.
METER SCALES	2 Expanded voltage & $-2/+4\text{dBm}$.
SIZE & WEIGHT	260mm x 190mm x 180mm. 5.6kg.

TG66B	TG66A
Battery model £170	Mains & battery model £190

FREQUENCY	3Hz to 300kHz in 5 decade ranges.
ACCURACY	$\pm 2\% \pm 0.1\text{Hz}$ up to 100kHz, increasing to $\pm 3\%$ at 300kHz.
SINE OUTPUT	2.5V r.m.s. down to $< 200\mu\text{V}$.
DISTORTION	$< 0.2\%$ from 50 Hz to 50kHz.
SQUARE OUTPUT	2.5V peak down to $< 200\mu\text{V}$.
SYNC. OUTPUT	2.5V r.m.s. sine.
METER SCALES	0/2.5V & $-10/+10\text{dB}$ on TG152DM.
SIZE & WEIGHT	260mm x 130mm x 180mm. 3.4kg.

TG152D	TG152DM
Without meter £53	With meter £63

LEVELL ELECTRONICS LTD.
 Moxon Street, High Barnet, Herts. EN5 5SD
 Tel. 01-449 5028/440 8686

Prices include batteries and U.K. delivery. VAT extra. Optional extras are leather cases and mains power units. Send for data covering our range of portable instruments.

**Teonex are
better known abroad...
because we don't sell
in the U.K.**



Electronic valves (a really comprehensive range), semi-conductors (a wide variety), integrated circuits.

Teonex offers more than 4,000 devices.

They are competitively priced and they are superlative in performance, because the company imposes strict quality control. Teonex concentrates entirely on export and now operates in more than 70 countries, on Government or private contract.

All popular types in the Teonex range are nearly always available for immediate delivery.

Write now for technical specifications and prices to Teonex Limited, 2a Westbourne Grove Mews, London W11 2RY, England.

Cables: Tosupply London W11. Telex: 262256



ELECTRONIC VALVES + SEMI CONDUCTORS

for Teonexexport only

WW-006 FOR FURTHER DETAILS



For faster delivery try these sources

Our Appointed Distributors have been ordering instruments on your behalf for over a year now. This means they can deliver your order quicker than any other source. They can help you choose the right instrument, too. Here's where to contact them:

LONDON AREA

London

Edmundson Electric Ltd.
Tel: 01-891 1331

ERD(South East) Ltd.
Tel: 01-928 5620

Lugton & Co. Ltd. Tel: 01-348 8247

R.T. & I. Electronics Ltd.
Tel: 01-539 4986

ITT Distributors Ltd.
Tel: 01-803 6522

Harlow

ITT Instrument Services
Tel: 0279 29522

Welwyn Garden City
Ellistons(Welwyn) Ltd.
Tel: 07073 26344

MIDLANDS

Coventry

Mercia Electronics Ltd.
Tel: 0203 24091

Birmingham

ITT Distributors Ltd.
Tel: 021-236 5030

ERD(Midlands) Ltd. Tel: 021-236 5060

Northampton

E.M.F.(Electrical) Ltd. Tel: 0604 21711

Norwich

Newey & Eyre Ltd. Tel: 0603 49341

Nottingham

Newey & Eyre Ltd. Tel: 0602 866531

NORTHERN IRELAND

Belfast

Eirco Ltd. Tel: 0232 42911

NORTH EAST

Hull

Edmundson Electric Ltd
Tel: 0482 20691

Leeds

Farnell Electronic Components Ltd.
Tel: 0532 636311

Wetherby

Farnell Instruments Ltd.
Tel: 0937 3541

Newcastle upon Tyne

J. Gledson & Co. Ltd. Tel: 0632 860955

NORTH WEST AND N. WALES

Salford

Hirst Ibbetson & Taylor Ltd.
Tel: 061-832 9711

J. Walton (Electrical) Ltd.

Tel: 061-872 4224

SCOTLAND

Glasgow

ERD(Scotland) Ltd. Tel: 041-647 7141

Elesco-Fraser Ltd. Tel: 041-221 9301

SOUTH WEST AND S. WALES

Bristol

Black Arrow (Electronics) Ltd.
Tel: 0454 315824

Cardiff

Newey & Eyre Ltd. Tel: 0222 45831

Bath

ERD(South West) Ltd. Tel: 0225 63281

You will still be able to buy our instruments through your usual wholesaler, although he may not be an Appointed Distributor.



Thorn Measurement Control and Automation Division, Archcliffe Road, Dover, Kent. Telephone: Dover (0304) 202620

Avo Limited
Evershed & Vignoles Limited MEGGER Instruments Division
H. W. Sullivan Limited
Taylor Electrical Instruments Limited

WW - 093 FOR FURTHER DETAILS.

Audio Laboratory Instruments

To expand the distribution of Audio Laboratory Instruments RADFORD are looking for new dealer/agents outside the United Kingdom. If you are a supplier of laboratory instruments to professional and industrial end users it could be to your advantage to learn more about RADFORD audio measuring equipment.

Write today for leaflets and details of franchised dealership.

Radford Laboratory Instruments Ltd
Ashton Vale Road
Bristol BS3 2HZ England

 **RADFORD**



LDO3. Low Distortion Oscillator

Frequency range: 10Hz - 100kHz.

Distortion: Distortion less than 0.002% over audio band.

Size: 17" x 7" x 8 $\frac{3}{4}$ ".

£275.00

LDO3B. Low Distortion Oscillator

As LDO3 but additionally fitted with output amplifier and transformer providing a 600 ohm floating balanced output.

Unbalance: -80dB. 1kHz. -60dB 10kHz.

£375.00

DMS3. Distortion Measuring Set

Frequency range: 5Hz - 50kHz.

Measurement down to 0.001%.

Size: 17" x 7" x 8 $\frac{3}{4}$ ".

£225.00

HSV1. High Sensitivity Voltmeter

Average reading: 10 μ V to 300V f.s.d.

£125.00

HSV2. High Sensitivity Voltmeter

True r.m.s. reading. 10 μ V to 300V f.s.d.

£175.00

ANM1. Audio Noise Meter and High Sensitivity Voltmeter

Average reading: 10 μ V to 300V f.s.d.

Includes Wide band, Audio band, IEC curve 'A' and CCIR

weighting networks. Illustrated above.

£150.00

ANM2. Audio Noise Meter and High Sensitivity Voltmeter


As ANM1 but true r.m.s. reading.

£200.00

WW — 047 FOR FURTHER DETAILS

FAST RESPONSE STRIP CHART RECORDERS


Made in USSR

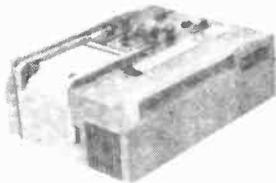

Type H3020-1
Single pen

Specification

Basic error	2.5%
Sensitivity	8mA F.S.D.
Response	0.2 sec.
Width of each channel	80mm
Chart speeds, selected by push buttons	0.1-0.2-0.5-1-2.5- -5-12.5-25mm/sec.
Chart drive	200-250v 50Hz

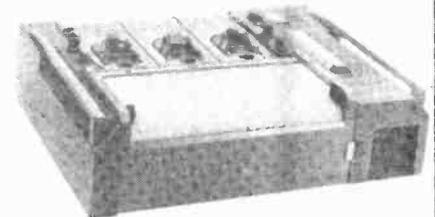

Type H3020-3
Three-pen

Recording:

Syphon pen directly attached
to moving coil frame.
curvilinear co-ordinates

Equipment:

Marker pen, Timerpen, Paper footage
indicator, 10 rolls of paper, connectors,
etc.

Dimensions:

H320-1: 285x384x16.5mm

H320-3: 475x384x16.5mm

PRICE: H320-1 £80.00

H320-3 £130.00

Exclusive of VAT

Available for immediate delivery

Z & I AERO SERVICES LTD.

44A WESTBOURNE GROVE, LONDON W2 5SF

Tel. 01-727 5641

Telex: 261306

WW — 058 FOR FURTHER DETAILS

Join the Digital Revolution


Teach yourself the latest techniques of digital electronics

Computers and calculators are only the beginning of the digital revolution in electronics. Telephones, wristwatches, TV, automobile instrumentation — these will be just some of the application areas in the next few years.

Are you prepared to cope with these developments?

This four volume course — each volume measuring 11 3/4" x 8 1/4" and containing 48 pages — guides you step-by-step with hundreds of diagrams and questions through number systems, Boolean algebra, truth tables, de Morgan's theorem, flipflops, registers, counters and adders. All from first principles. The only initial ability assumed is simple arithmetic.

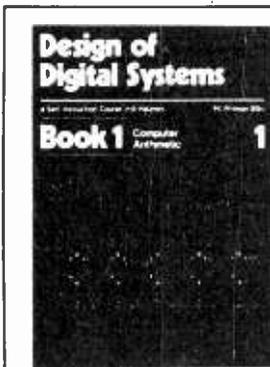At the end of the course you will have broadened your horizons, career prospects and your fundamental understanding of the changing world around you.



Also available — a more advanced course in 6 volumes:

1. Computer Arithmetic
2. Boolean Logic
3. Arithmetic Circuits
4. Memories & Counters
5. Calculator Design
6. Computer Architecture

Offer. Order this together with Digital Computer Logic & Electronics for the bargain price of £9.25, plus 50p p&p.

£5.95 plus 50p p&p

Design of Digital Systems contains over twice as much information in each volume as the simpler course Digital Computer Logic and Electronics. All the information in the simpler course is covered as part of the first volumes of Design of Digital Systems which, as you can see from its contents, also covers many more advanced topics.

**Designer
Manager
Enthusiast
Scientist
Engineer
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

Guarantee — no risk to you

If you are not entirely satisfied with Digital Computer Logic and Electronics or Design of Digital Systems, you may return them to us and your money will be refunded in full, no questions asked.

Digital Computer Logic and Electronics

A Self-instructional Course

C. P. Gore MA (Cantab)
A. W. Linn BA (Cantab)

Book 1 Basic computer logic

Book 2 Logical circuit elements

Book 3 Designing circuits to carry out logical functions

Book 4 Flipflops and registers



£3.95

plus 50p packing and surface mail anywhere in the world.

Quantity discounts available on request.

Payment may be made in foreign currencies.

VAT zero rated.

To: Cambridge Learning Enterprises,
FREEPOST, St. Ives, Huntingdon, Cambs.
PE17 4BR

*Please send me set(s) of Digital Computer Logic and Electronics at £4.45 each, p&p included

*or set(s) of Design of Digital Systems' at £6.45 each, p&p included

*or combined set(s) at £9.75 each, p&p included

Name

Address

.

.

*delete as applicable
No need to use a stamp — just print FREEPOST on the envelope.

WW 1




sound equipment by **Grampian**

GRAMPIAN REPRODUCERS LTD. HANWORTH TRADING ESTATE FELTHAM, MIDDLESEX TELEPHONE 01-894 9141

X209

WW-029 FOR FURTHER DETAILS

brenell PROFESSIONAL TAPE TRANSPORTS and multi-channel electronics for studio and industrial use

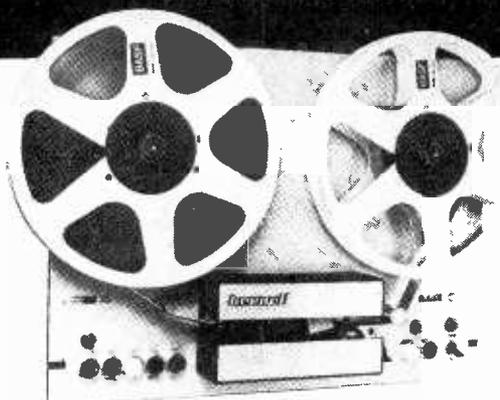

Type 19
25mm model

**Finance
available**

- * Tapewidths up to 25mm
- * Speeds: 3mm/s minimum up to 152cm/s max
2 and 4 speed models
- * Reel Capacity up to 29cm
- * Remote Control Facility
- * Tape Tension Control
- * Automatic Interlock against misuse
- * Special models to customer requirements

BRENELL ENGINEERING CO LTD
231-5 Liverpool Road. London N1 1LY. Tel: 01-607-8271

Valradio TRANSVERTORS

Valradio sinewave and square wave transvertors now incorporate SILICON transistors resulting in greater reliability and more stable performance at high ambient temperatures, including tropical climates.



TYPE D12/400S

A wide selection of types are available to drive practically any equipment within the power rating.


A random selection of types:

	Input	Output
C24/60S	24v DC	115/230v 60watts Sine wave
D12/400S	12v DC	115/230v 400watts Sine wave
D12/500T	12v DC	115/230v 500watts Square wave
D24/150T	24v DC	115/230v 150watts Square wave
D12/250/24	12v DC	24v DC 8A

Please send for literature WW675

VALRADIO LIMITED
BROWELLS LANE, FELTHAM, MIDDLESEX, TW13 7EN
Tel: 01-890 4242/4837

WW-065 FOR FURTHER DETAILS

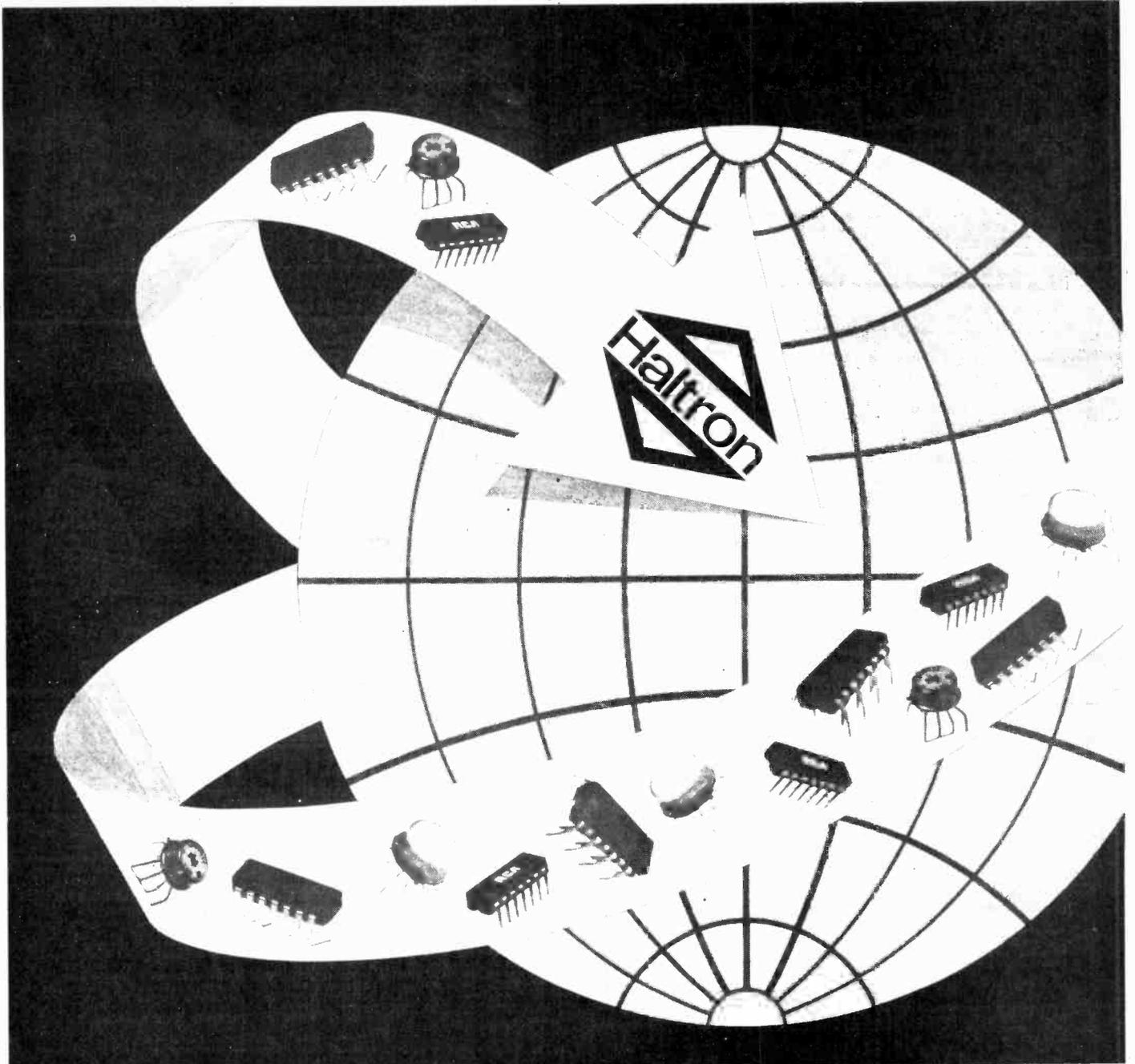

**The world over-
You get the
best service
from Haltron**

For high quality electronic valves, semiconductors and integrated circuits – and the speediest service – specify Haltron. It's the first choice of Governments and many other users throughout the world. Haltron product quality and reliability are clearly confirmed. The product range is very, very wide. And Haltron export expertise will surely meet your requirements. Wherever you are, get the best service. From Haltron.




Hall Electric Limited,
Electron House,
Cray Avenue, St. Mary Cray,
Orpington, Kent BR5 3QJ.
Telephone: Orpington 27099
Telex: 896141

At Home Soldering?

You should be — with the LITESOLD CONQUEROR

A superbly handling lightweight iron, fully insulated and earthed for safety. Bits are interchangeable, non-seize, and are available in 16 different shapes and sizes, from 1/16" up to 1/4", in copper and long-life types. (Standard fitting, 1/8" copper single chisel shape). Covers a range of work often needing several different irons. A special spring stand gives safe, easy location of the iron and spare bits. The heavy heat-resistant base is complete with non-slip pads and bit cleaning sponge.

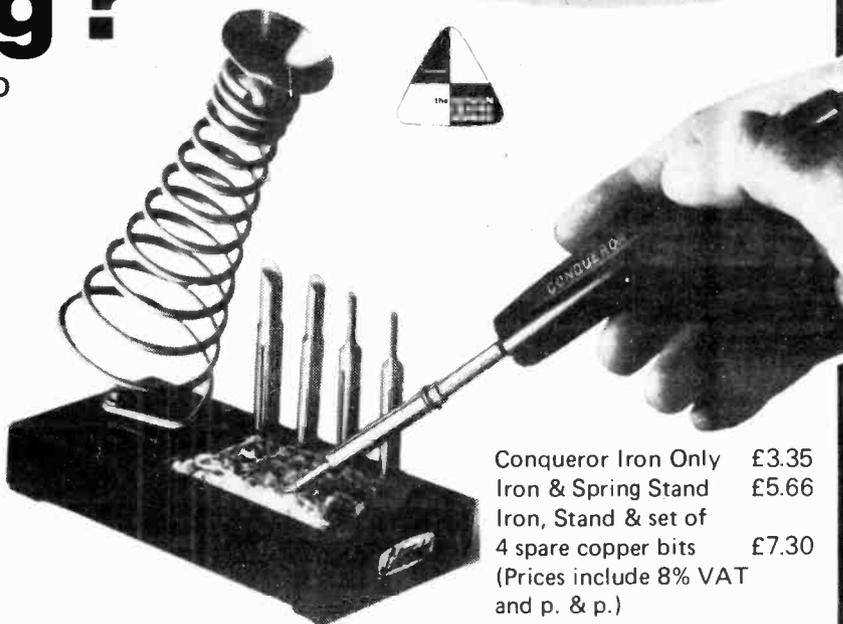Send cheque/PO direct, or ask for leaflet.



Conqueror Iron Only £3.35
 Iron & Spring Stand £5.66
 Iron, Stand & set of 4 spare copper bits £7.30
 (Prices include 8% VAT and p. & p.)


LIGHT SOLDERING DEVELOPMENTS LTD

97-99, Gloucester Road, Croydon, CRO 2DN. 01-689 0574

LS/M

WW-063 FOR FURTHER DETAILS

ELECTRONIC INDUSTRIAL THERMOMETER

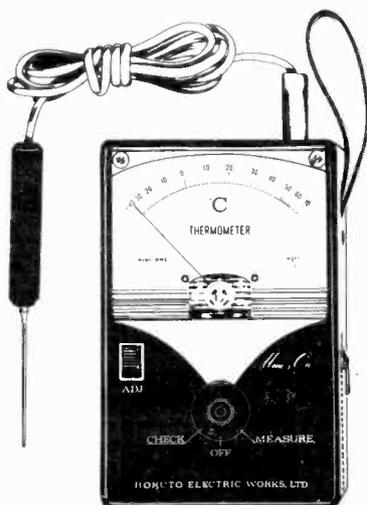

THE MODERN WAY TO MEASURE TEMPERATURE

A Thermometer designed to operate as an Electronic Test Meter. Will measure temperature of Air, Metals, Liquids, Machinery, etc., etc. Just plug-in the Probe, and read the temperature on the large open scale meter. Supplied in zippered vinyl case with transparent front and carrying loop, Probe, and internal 1 1/2 volt standard size battery.

Model "Mini-On 1" measures from - 40°C to + 70°C, price £17.50

Model "Mini-On Hi" measures from + 100°C to + 500°C, price £20.00 (V.A.T. EXTRA)

Write for further details to

HARRIS ELECTRONICS (LONDON),
 138 GRAY'S INN ROAD, LONDON. WC1X 8AX
 ('Phone 01-837 7937)

WW-035 FOR FURTHER DETAILS




SR45 72 x 56
 SR52 78 x 63
 SR65 95 x 75




TAD48 48 x 42
 TAD66 66 x 60
 TAD86 86 x 78
 TAD118 118 x 106
 TAD152 150 x 110



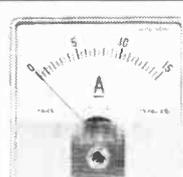SU45 69 x 53
 SU55 87 x 63
 SU65 105 x 77



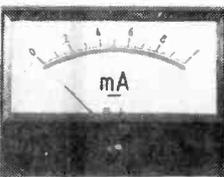SA38 43 x 43
 SA45 51 x 51
 SA52 61 x 61
 SA65 82 x 78



SE45 64 x 52
 SE52 80 x 60
 SE65 100 x 80
 SE85 120 x 100



SA65 82 x 78
 For laboratory use

A selection from our Range Competitive Prices! High Quality! Personal Service! Full Electrical and Mechanical Information on Request!

All dimensions in mm.



SERVO AND ELECTRONIC SALES LTD.
 24 High St., Lydd, Kent. TN29 9AJ
 Tel: Lydd 20252 Telex: 965265

WW-072 FOR FURTHER DETAILS

Make light work of wiring with the **NEW SELF ADHESIVE WIRE STAPLES**



Countless uses in industry and offices


- *QUICK AND EASY TO APPLY – EVEN IN AWKWARD PLACES
- *SAVES DAMAGE TO WOOD AND PAINTWORK
- *STICKS ON INSTANTLY : HOLDS WIRE FIRMLY

You'll save enormous time and trouble with the new Brandauer adhesive staple. Just peel off the backing strip and press staple into place. Then bend clips over to hold wire firmly in position. No messing with pins, tacks, soldering or drilling. No damage to woodwork, e.g. skirting boards. Use the Brandauer Staple for any wall, frame or cabinet wiring jobs — it's wonderfully easy for fitting in those awkward corners.

Send now for details to:

SPECIAL PRODUCTS DISTRIBUTORS LTD.
81 Piccadilly, London W1V 0HL. Tel: 01-629 9556.

WW-054 FOR FURTHER DETAILS

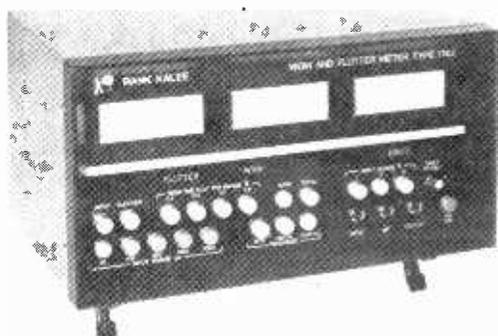

The new Rank

WOW & FLUTTER Meter Type 1742

Fully transistorised for high reliability

Versatile

Meets in every respect all current specifications for measurement of Wow, Flutter and Drift on Optical and Magnetic sound recording/reproduction equipment using film, tape or disc

High accuracy

with crystal controlled oscillator

Simple to use

accepts wide range of input signals with no manual tuning or adjustment

Two models available:

- Type 1742 'A' BS-4847: 1972 DIN 45507 CC1R 409-2 Specifications
- Type 1742 'B' BS 1988: 1953 Rank Kalee Specifications

For further information please address your enquiry to Mrs B. Nodwell

Rank Film Equipment, PO Box 70
Great West Road, Brentford
Middlesex TW8 9HR

Tel: 01-568 9222; Telex 24408; Cables Rankaudio Brentford

RANK FILM EQUIPMENT

Gardners

The Best of British



ENCAPSULATED POWER SUPPLIES
DC Input – NV Converter Series

- Fully stabilized
- Input/output isolation
- Short circuit protection
- Fully shielded, low radiation
- Commutation spikes less than 20 mV P-P

Cat. No.	Nominal DC Input Voltage	OUTPUT		TYPICAL REGULATION (Volts)	
		Volts	Amps	LINE	LOAD
NV7300	5	2x15	0.25	.006	.006
NV7308	5	180	0.05	2.5	2.5
NV7312	12	5	1.00	.005	.024
NV7314	12	2x 5	1.00	.005	.024
NV7317	12	6	1.00	.009	.021
NV7319	12	2x 6	1.00	.009	.023
NV7323	12	2x12	0.50	.014	.011
NV7328	12	2x15	0.50	.019	.011
NV7336	12	24	0.5	.07	.09
NV7342	24	5	1.00	.004	.024
NV7344	24	2x 5	1.00	.004	.024
NV7349	24	2x 6	1.00	.008	.023
NV7353	24	2x12	0.50	.010	.012
NV7357	24	15	1.00	.024	.021
NV7358	24	2x15	0.50	.015	.012
NV7366	24	24	0.5	.07	.09
NV7368	24	50	0.25	.3	.2
NV7372	50	5	1.00	.002	.024
NV7383	50	2x12	0.50	.007	.011
NV7388	50	2x15	0.50	.010	.012
NV7396	50	24	0.5	.07	.09
NV7398	50	50	0.25	.3	.2

Based on ambient 20°C, 100sq. in heatsink
*modules facilitating polarity changes
Additional designs are fully described in GT.21B.

AC Input – Minimid Series

- P.C. mounting interchangeable with most American types
- Linear stabilization
- Foldback current limiting
- Wide temperature range
- Modules available for U.K. (210-250v), European (200-240v) and American (106-121v) requirements
- Supply Frequency 50-400Hz




Type number	OUTPUT		Short Circuit Current mA (Typical)	% Regulation line & load (Typical)
	Voltage*	Amps		
PU01	5	0.5	370	0.3
PU02	5	1.0	770	0.5
PU03	15-0-1E	0.10	37	0.1
PU04	15-0-1E	0.20	84	0.1
PU05	12-0-12	0.12	45	0.1
PU06	12-0-12	0.24	120	0.2
PU11	18-0-1E	0.15	50	0.1
PU10	15	0.10	37	0.1
PU12	12	0.10	45	0.1
PU13	18	0.065	23	0.1

* Voltage tolerance 5v models ± 0.1v. All other models ± 0.2v.

Nickel-Cadmium Cell Charger Units

Constant current outputs permitting up to 10 cells to be charged in series. DC INPUT - NV7304 AC INPUT - PU07

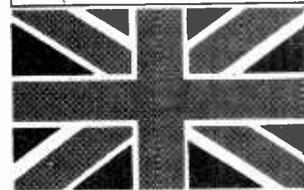ALL UNITS DESCRIBED ARE NORMALLY AVAILABLE FROM STOCK. **SPECIAL DESIGN SERVICE.** CUSTOM BUILT UNITS FOR APPLICATIONS REQUIRING DIFFERENT SPECIFICATIONS ARE PRODUCED AS PART OF OUR STANDARD SERVICE. TRY US FIRST.



Gardners

Gardners Transformers Limited
Christchurch · Dorset BH23 3PN
Telephone 0201-5 2284
Telex 41276 Gardners XCH

Approved manufacturers of electronic transformers, modular power supplies, inverters and converters to Defence Standard 05-21

WW-067 FOR FURTHER DETAILS

They use them here, they use them there, those engineers use them everywhere.



WW — 025 FOR FURTHER DETAILS

Being completely self contained, the Sullivan Multi-Purpose Potentiometer, Type 44228 is equally at home in a laboratory, on a production line or on-site.

This versatile unit is intended for the calibration and testing of thermocouples and associated indicators and recorders. It can measure or supply potentials up to 101 mV (to an accuracy of +0.1%)! An optional Voltage Ratio Box type 44763 extends measurements up to 500 V.

The Sullivan Multi-Purpose Potentiometer incorporates a solid state d.c. null detector which carries a centre zero logarithmic scale with sensitivity at 12 μ V per division, for small deflections.

And to cap it all, this precision engineered unit is rugged enough to go anywhere and give accurate readings. Get in touch to-day for fully detailed literature.

Sullivan

H. W. Sullivan Limited, Dover, Kent.
Tel: Dover (0304) 202620 Telex: 96283.

Thorn Measurement Control and Automation Division

Problem.

Where to obtain devices for push-pull audio power amplifiers which give good linearity and don't blow up on the slightest overload.

Solution.

M-OV audio beam tetrodes. A pair of KT66s will give up to 50W and a pair of KT88s will give up to 100W. And M-OV audio triodes, too: a pair of DA42s gives up to 200W and a pair of DA 100s gives up to 300W.



LAP81

EEV and M-OV know how.

THE M-O VALVE CO LTD, Hammersmith, London, England W6 7PE.
Tel: 01-603 3431. Telex: 23435. Grams: Thermionic London. **SBC** 

WW—015 FOR FURTHER DETAILS

Switching problems? Rely on Zettler.

Producing 30 basic types of relay and 15,000 variants with regard to contact stacks, terminals, energizing current and contact material, Zettler is among the largest manufacturers of electro-mechanical components.

Our product range comprises:
Low profile (platform) · Timing · Miniature · Low contact capacity · Hermetically sealed · Stepping · Mains switching · Latching Contact stacks · Solenoids



Stepping Relay AZ 170

Contacts are mechanically latched and thus unaffected by supply interruption. Regular contact configurations from 1 make up to 3 changeovers. Heavy duty version with 1 make or 1 changeover. Switching capability: 3 A at 125 V AC. Coil voltages: 6 to 110 V DC.

We resolve your switching problems rapidly and expertly. Please contact us for further details.



ZETTLER Zettler UK Division

Brember Road
Harrow, Middx. HA2 8AS, Tel. (01) 422 0061

A member of the worldwide ZETTLER electrical engineering group, est. 1877

WW—011 FOR FURTHER DETAILS


A message for dealers in exclusive high quality audio equipment – everywhere.

It is now proposed to expand the distribution of RADFORD products by supplying from the factory in BRISTOL direct to franchised dealers outside the United Kingdom.

If you have a discriminating clientele looking for the finest audio equipment and loudspeaker components available, you could profit from a direct RADFORD franchise.

Write today for details and leaflets.

Radford Audio Ltd
Ashton Vale Road
Bristol BS3 2HZ England

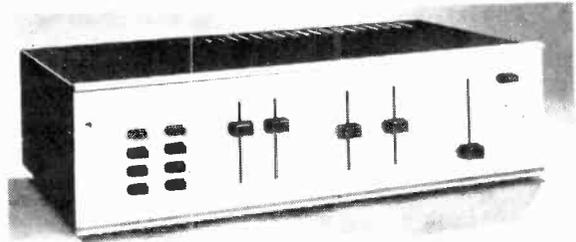

ZD22
Stereo Pre-amplifier Control Unit
A stereo pre-amplifier of virtually zero distortion. Inputs for disc, tuner, and two tape machines. Size 17" x 4 3/4" x 10" deep. £145.00

HD250 Stereo Integrated amplifier
Incorporates ZD22 pre-amplifier with low distortion power amplifier of 50 watts per channel into 4-8 ohms load. Headphone output. Illustrated above. Size 17" x 4 3/4" x 11". £195.00

ZD100 Power amplifier
Power output 120 watts in 4 ohms and 75 watts into 8 ohms. Distortion less than 0.004% up to clip level. Size 17" x 4 3/4" x 13". £175.00

ZD200 Power amplifier
Power output 250 watts into 4 ohms and 150 watts into 8 ohms. Distortion less than 0.004% up to clip level. Size 17" x 7" x 13". £295.00

WW – 046 FOR FURTHER DETAILS

Your choice of Live Sockets- Instantly!

A Lexor DIS-BOARD gives you up to 6 sockets from one power outlet. Portable or permanent fixing, compact units, with safety neon. Over 1 000 socket combinations available from stock. All types of fittings and finishes.

Brochure from
LEXOR DIS-BOARDS LIMITED
Allestey Old Road, Coventry
Telephone 72614 or 72207



WW-033 FOR FURTHER DETAILS



MODEL
U-50DX

sanwa MULTI TESTERS

USED THROUGHOUT THE WORLD, SANWA'S EXPERIENCE OF 30 YEARS ENSURES ACCURACY, RELIABILITY, VERSATILITY, UNSURPASSED TESTER PERFORMANCE COMES WITH EVERY SANWA.

6 months Guarantee	£11.75	MODEL K30THD	£24.20
MODEL P2B	£12.80	MODEL F80TRD	£26.40
MODEL JPSD	£14.90	MODEL 380CE	£29.12
MODEL YX36DTR	£16.10	MODEL M101	£31.85
MODEL U50DX	£19.15	MODEL 460ED	£35.13
MODEL A303TRD	£22.90	MODEL EM800	£74.50
MODEL BX505	£23.15	MODEL R1000CB	£75.27

Excellent Repair Service

THESE PRICES DO NOT INCLUDE V.A.T.

Cases extra, available for most meters, but not sold separately


Please write for illustrated leaflet of these and other specialised Sanwa meters

SOLE IMPORTERS IN UK

QUALITY ELECTRONICS LTD.

47-49 HIGH STREET, KINGSTON-UPON-THAMES, SURREY, KT1 1LP
Tel: 01-546 4585

WW-007 FOR FURTHER DETAILS

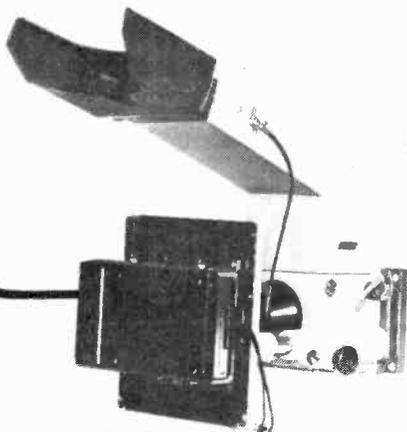

Telford Oscilloscope cameras

Type A modular system with widest range of film backs, lenses, viewing systems and adaptors to meet virtually all requirements.

Plus inexpensive Type P (prices from £50) utilising coaterless Polaroid film and Robot with economical 35mm film for continuous feed.

More complete details available on request from:

Telford PRODUCTS LTD.


WADSWORTH ROAD PERIVALE GREENFORD MIDDIX, ENGLAND Telephone: 01-998 1011 Telex: 935524

DAVALL A MEMBER COMPANY OF BENTIMA INDUSTRIES LIMITED

©Reg. Trade Mark.

WW – 026 FOR FURTHER INFORMATION

HIGH POWER DC-COUPLED AMPLIFIER

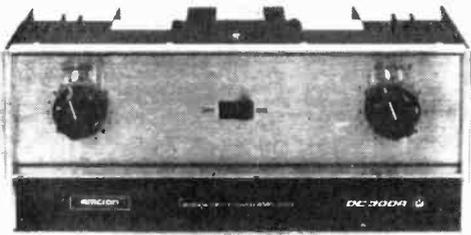

- ★ UP TO 500 WATTS RMS FROM ONE CHANNEL
- ★ DC-COUPLED THROUGHOUT
- ★ OPERATES INTO LOADS AS LOW AS 1 OHM
- ★ FULLY PROTECTED AGAINST SHORT CCT, MISMATCH, ETC.
- ★ 3 YEAR WARRANTY ON PARTS AND LABOUR

The DC300A Power Amplifier is the successor to the world famous DC300 which is so widely used in Industrial, and Research applications in this country. It is DC-coupled throughout so providing a power bandwidth from DC to over 20,000Hz. The ability of the DC300A to operate without fuss into totally reactive loads while delivering its full power, and maintaining its faithful reproduction of Pulse or complex waveforms has established the DC300A as the world's leading power amplifier. Each of the two channels will operate into loads as low as 1 ohm, and the amplifier can be rapidly connected as a single ended amplifier providing over 650 watts RMS into a 4 ohms load, and still providing a bandwidth down to DC. Below is a brief specification of the DC300A, but if you require a data sheet, or a demonstration of this fine equipment please let us know.

Power Bandwidth	DC-20kHz @ 150 watts + 1db. - 0db.	Slewing Rate	8 volts per microsecond
Power at clip point (1 chan)	500 watts rms into 2.5 ohms	Load impedance	1 ohm to infinity
Phase Response	+0. - 15° DC to 20kHz. 1 watt 8Ω	Input sensitivity	1.75 V for 150 watts into 8Ω
Harmonic Distortion	Below 0.05% DC to 20kHz	Input Impedance	10K ohms to 100K ohms
Intermod. Distortion	Below 0.05% 0.01 watt to 150 watts	Protection	Short, mismatch & open cct. protection
Damping Factor	Greater than 200 DC to 1kHz at 8Ω	Power supply	120-256V. 50-400Hz
Hum & Noise (20-20kHz)	At least 110db below 150 watts	Dimensions	19" Rackmount. 7" High. 9 3/4" Deep
Other models in the range: D60 — 60 watts per channel		D150 — 150 watts per channel	



MACINNES LABORATORIES LTD

MACINNES HOUSE, CARLTON PARK INDUSTRIAL ESTATE,
SAXMUNDHAM, SUFFOLK IP17 2NL
TEL: (0728) 2262 2615

WW—031 FOR FURTHER DETAILS

Contractors to H.M. Govt. P.O.

REPAIRS

OF ELECTRICAL MEASURING INSTRUMENTS

7-14 DAYS SERVICE

◀ MODEL 8 MK.V



STOCKISTS
ALSO SUPPLIERS OF GEC
RISSO AND OTHER
MULTI-RANGE TEST SETS


WE SPECIALISE IN ASSEMBLIES, AND IN THE
REPAIR, CALIBRATION AND CONVERSION
OF ALL TYPES OF INSTRUMENTS, INDUSTRIAL
AND PRECISION GRADE

LEDON INSTRUMENTS LTD.

**GLADSTONE WORKS, GLADSTONE RD,
FOLKESTONE, KENT.
TEL: (STD) 0303 57555**

WW — 024 FOR FURTHER DETAILS

NEON FILAMENT AND LED INDICATORS

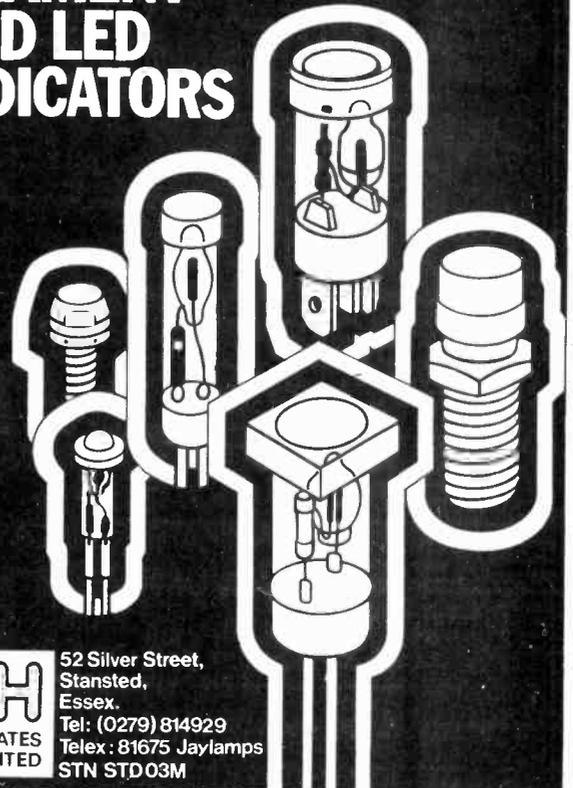

JH
ASSOCIATES
LIMITED

52 Silver Street,
Stansted,
Essex.
Tel: (0279) 814929
Telex: 81675 Jaylamps
STN STD03M

WW—034 FOR FURTHER DETAILS

AEL 3030

The AEL 3030 is a compact, fully solid-state 150 watt PEP output Transmitter-Receiver covering 2.16 MHz on 4 or 6 channels.

Rugged construction for today's tough environments. Easily accessible for simple maintenance.

Ten plug-in modules give maximum insurance against loss of service.

The advanced technology used in the AEL 3030 provides unmatched efficiency in point to point or mobile communication, minimises size and cost and maximises reliability!

DESIGNED FOR RELIABILITY



For further information and colour brochure write to:

AEL GATWICK HOUSE
 HORLEY, SURREY, ENGLAND
 TELEPHONE: HORLEY (02934) 5353

Telex: 87116 (Aerocon Horley)
 Cables: Aerocon. Telex: Horlev

WW — 085 FOR FURTHER DETAILS

A NEW DIMENSION IN SOLDERING



Iso-Tip Cordless Soldering Iron

Ideal for factory, field servicing, laboratory or home, the Iso-Tip Cordless offers a great advance in soldering. It is completely portable, heats in 5 seconds and recharges automatically in its own stand.

The Iso-Tip is powered by long-life nickel cadmium batteries giving tip performance up to 50 watts with a temperature of 370°C. Tips are available in five different sizes ranging from Micro to Heavy Duty to meet all soldering requirements.

Greenwood Electronics
 Portman Rd, Reading RG3 1NE, England.
 Telephone: Reading (0734) 595844.
 Telex: 848659.

WW—036 FOR FURTHER DETAILS

FREQUENCY COUNTERS

HIGH PERFORMANCE REASONABLY PRICED ELECTRONIC INSTRUMENTS



CRYSTAL OVEN
 TWO TONE BLUE CASE

£370 **520** MHz

Sensitivity 10mV. Stability 5 parts 10¹⁰

301M	32MHz 5 Digit £78	401	32MHz 6 Digit £121
501	32MHz 8 Digit £178	701A	80MHz 8 Digit £195
801A/M	300MHz 8 Digit £305	901M	520MHz 8 Digit £375
801B/M	250MHz 8 Digit £262	Memory versions available if not suffixed M £25 extra	

Start/Stop versions plus £12

Type 101 1MHz 100KHz 10KHz Crystal Standard £85
 Type 103 Off/Air Standard £85

SUPPLIERS TO: Ministry of Defence, G.P.O., B.B.C., Government Depts.,
 Crystal Manufacturers and Electronic Laboratories world-wide




R. C. S. ELECTRONICS
 NATIONAL WORKS, BATH ROAD
 HOUNSLOW, MIDDX. TW4 7EE
 Telephone: 01-672 0933/4

WW — 048 FOR FURTHER DETAILS

SPECIALISTS IN COIL AND TRANSFORMER WINDING:

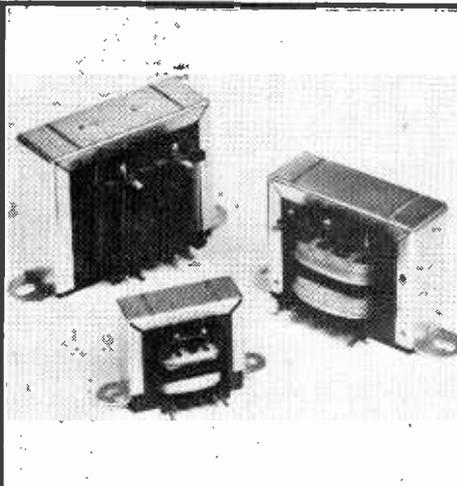Torroidal: c core: high speed high turn bobbin winding: chokes and wave winding
any quantity, any rating.



**27 STATION ROAD
BRIMINGTON
CHESTERFIELD
DERBYSHIRE, ENGLAND
TEL: 0246 70297/8/9
TELEX 54284**


Send for new catalogue.

WW-009 FOR FURTHER DETAILS

THE TUNER YOU CAN TRUST

(W.W. APRIL/MAY 1974)

This tuner has been designed for use with high quality audio equipment. It has therefore been designed so that only high quality, audio signals may be heard. There are no interstation noises, distorted or mis-tuned stations, spurious tuning responses, or other unwanted effects. There are only clear stereo programmes set against a background of silence. When the tuning lamp is out - silence; tuning lamp on - one of a multitude of receivable stations, in perfect tune, and held by powerful a.f.c.

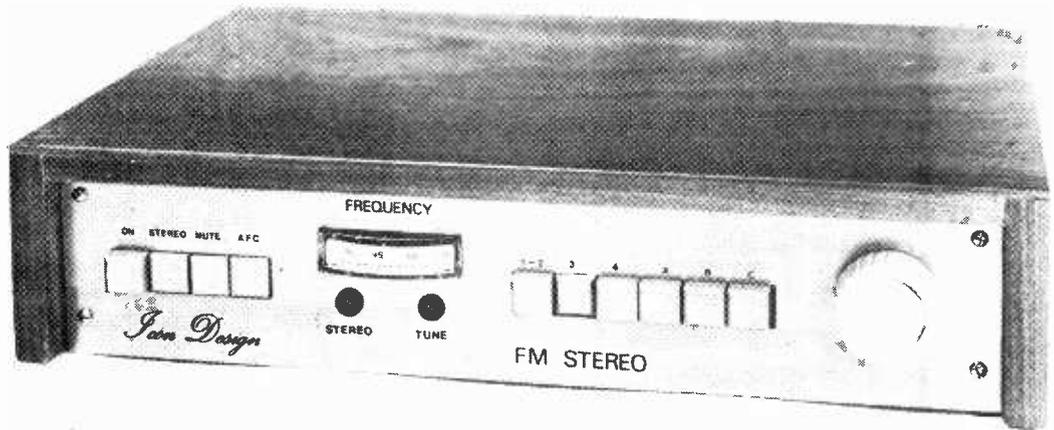

Kits 1 to 12 listed below supply you with all you need to build this high quality tuner, including every nut and bolt, plug, socket, and mains lead. A complete after-sales service is available for fault finding, and a full guarantee provided. All sub-assemblies are available ready built and tested to simplify construction, or you may purchase the completed tuner with a five-year guarantee.

NEW REVISED PRICES (EXC. VAT)

VAT Rate 25%

K1-4 Main receiver board	£24.55
K5-7 Stereo decode board	£7.05
K8 Function Switches	£4.95
K9a Pre-set station unit	£13.75
K10 Power supply unit	£5.59
K11 Cabinet and all else	£27.70
K12 Meter with drive components	£11.00
K1-12 PACKAGE PRICE	£85.00
	saving £9.59

U.K. postage 30p per kit, free over £15.

INDIVIDUAL PARTS

(included in Kits 1-12)

LP1186 front end	£4.53
MC1310P decoder	£3.15
SBA750B i.f. amp	£2.95
SL3046B trans. array	£1.70
SL301B dual trans.	£1.40
Filter SFG10.7MA	£2.95
Coil with wire	£0.50
Ten turn pot. 50K	£3.55
Postage per item U.K.	£0.20

S.A.E. please for details to:

Icon Design

33 RESTROP VIEW, PURTON, WILTS SN5 9DG

J. A. SKINGLEY & N. C. THOMPSON

Ready built and tested £102.00. Securicor delivery (mainland only). £3 extra

DIGITAL CLOCK KITS : ALARM AND STANDARD



- Fast Building.
- Easy to follow Instructions.
- No knowledge of electronics needed
- The most comprehensive kit and instructions you have ever seen.

ALARM VERSION £16.00
(including P&P, VAT)

STANDARD CLOCK KIT. STILL £14.00

READY-BUILT, TESTED ELECTRONICS FOR STANDARD CLOCK £11.88

Clock Chip MM5314N	£2.95
0.63" LED Displays NSN61L	£1.65
Segment Driver Chip DM8865N	£0.50
Mains Transformer (8.5/15v)	£1.50
Assembly Manual	£0.50
Futuristically Styled Case	£4.40
White, Black, Red, Blue, Green, Mauve	
All wood case extra 70p	
Standard Kit, excluding case	£11.60

Pulse Electronics Ltd.


Dept. WW4, 202 Shefford Road, Clifton, Beds.
Tel. Hitchin (0462) 814477



6 1/4" x 3" x 2 1/2"
Mains operated

12-24 hour

METER PROBLEMS?

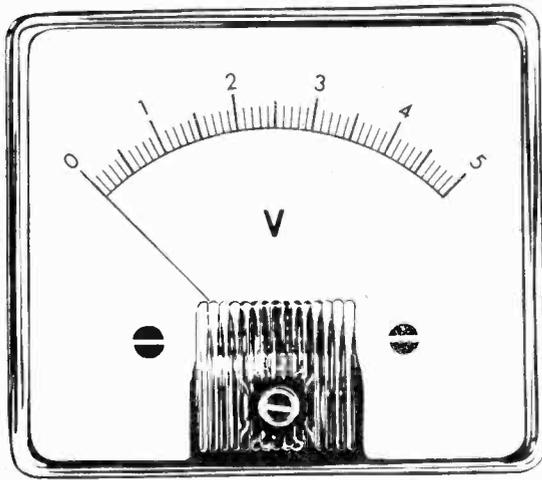

137 Standard Ranges in a variety of sizes and stylings available for 10-14 days delivery. Other Ranges and special scales can be made to order.


Full Information from:

HARRIS ELECTRONICS (London)

138 GRAYS INN ROAD, W.C.1 Phone: 01/837/7937

WW - 021 FOR FURTHER DETAILS

LOW-COST INSTRUMENTS

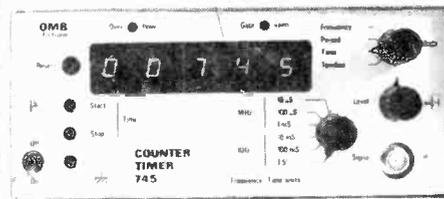

VALUE!

£82

+ £2.00 p.p.
+ VAT

745 COUNTER TIMER


Measures frequency, period, time and totalises
32 MHz frequency range (DC coupled)
5-digit .3" LED display
6 Gate times/Time units, 10µs to 1 S in decades
Sensitive, protected FET input



744 COUNTER TIMER

£79 + £2.00 p.&p. + VAT

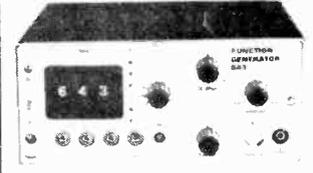Measures frequency, period and time
30MHz frequency range (DC coupled)
5-digit, long-life incandescent display
Sensitive, protected FET input



643 FUNCTION GENERATOR

£86 + £2.00 p.&p. + VAT

Accurate, digital frequency setting
0.1Hz-1MHz
Wide range external control of frequency
Triangle, Squarewave and Low Distortion
Sinewave outputs
50Ω + simultaneous outputs
DC offset

Delivery is normally ex-stock—telephone for confirmation
Prices correct at time of going to press, subject to change without notice

OMB ELECTRONICS

Riverside, Eynsford, Kent DA4 0AE

Tel. Farningham (0322) 863567

WW - 027 FOR FURTHER DETAILS

ERA

when reliability and quality count


Magnetrons, Klystrons, T.W. Tubes, Transmitting Valves, Industrial Valves, T.V. Picture Tubes, Cathode Ray Tubes, High Reliability Valves and a full range of Receiving Valves always available.
Professional import and export enquiries welcomed.

EDICRON LIMITED

Redan House, 1 Redan Place, London W2 4SA
Telephone: 01-727 0101 Telex: 265531
Cables: Edicron London W2
WW-010 FOR FURTHER DETAILS


NT 3302 · fet fm tunerhead

+ AM gang

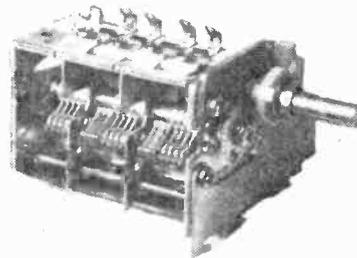

- * FET input stage
- * 3 stage tuning
- * 3:1 gearing
- * 335pF AM gangs
- * AFC facility

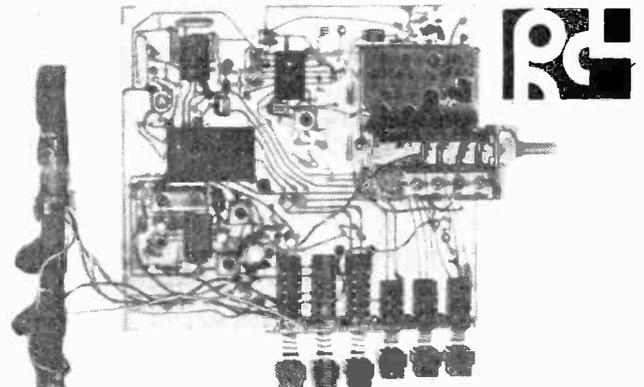
TOKO's latest FM tunerhead is available for immediate evaluation with the Broadcasting 9000 tuner chassis- an AM (LW/MW) and mpX FM chassis, with switches inc.



distributed by *Ambit International*, 37 High St
Brentwood, Essex. tel:216029, tlx:848095.

ALL 9000 chassis enquiries to Ambit please.

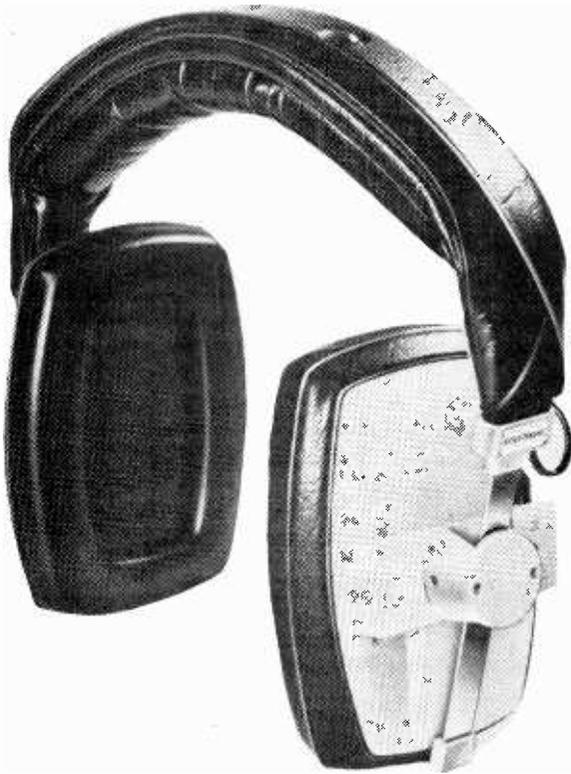OEM enquiries to TOKO UK, Ward Royal Parade,
Alma Road, Windsor, Berkshire. tel:54057, tlx:848095.



**professionally
canned from
ear to ear**

The DT 100 is only one of an extensive range of headphones manufactured by Beyer Dynamic, in use in studios throughout the world setting a new sound standard.

- Frequency Response: 30-20,000 Hz
- Output Level at 100 HZ and 1 mW: 110 db over 2. 10⁻⁴ μ bar
- Rated Input: appr. 600m V per cartridge
- Peak Power Load: 1W or 20V per cartridge
- Impedance: 2 x 400 Ω (2 x 8, 2 x 100, 2 x 800, 2 x 2,000 Ω upon request)

BEYER DYNAMIC

BEYER DYNAMIC (GB) LIMITED

1 Clair Road, Haywards Heath, Sussex. Tel: Haywards Heath 51003

WW-068 FOR FURTHER DETAILS

**servos
synchronous
steppers
dc motors**



**gearboxes and
control systems**



Stockists for **IMPEX** Motors

McLennan

McLENNAN ENGINEERING LIMITED


Kings Road Crowthorne Berks Telephone: Crowthorne 5757/8

WW-043 FOR FURTHER DETAILS

FOUR CHANNEL

**Recorder . £385
Replay only £237**

VAT and carriage extra

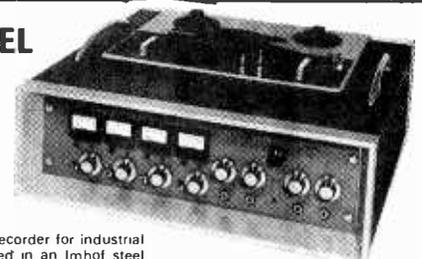

A new rugged four channel recorder for industrial or university use mounted in an Imhof steel case size 21" wide x 19" x 10" high overall Weight 25Kg.

In line record and replay heads with ability to erase and record on individual tracks. Mk 5 Brenell Deck — 3 $\frac{3}{4}$, 7 $\frac{1}{2}$ and 15 i p s — 8 $\frac{1}{4}$ " spools — $\frac{1}{4}$ " tape — —Papst Motors

This equipment, which has simple controls, is specially designed for reliability and easy maintenance. All the amplifiers plug in. Features include jack sockets for input and output lines on the front panel with extra D I N sockets at the back. Built in four x 8 watt power amplifiers available. Price £46

DEIMOS LIMITED

Simmonds Road, Wincheap, Canterbury, Kent. Tel. 0227 68597

meteronic



OSCILLOSCOPES

- BATTERY PORTABLE
- 10 MHz BANDWIDTH
- 0.1 μ S-0.1 Sec. TIME-BASE
- SINGLE AND DOUBLE BEAM
- PRICES FROM £95

meteronic Ltd.

114/116 Shipbourne Road
Tonbridge, Kent
Tel. Tonbridge 61448

WW-032 FOR FURTHER DETAILS

RACAL COMMUNICATION EQUIPMENT

34	RA 117E High Stability H F Receiver Frequency Range 1 to 30 MHz	
	34a New condition	£400 00 + £5 00 p.p.
	34b Good clean condition	£350 00 + £6 00 p.p.
31	RA 17 Frequency range 500KHz to 30MHz	
	31 In good, clean condition	£315 00 + £5 00 p.p.
38	RA 98 Single side band with A F C. and tuning	£83 00 + £2 00 p.p.
39	RA 121 Single side band with A F C. and tuning scope	£143 00 + £2 00 p.p.
40	RA 218 Single side band line tune unit for RA 117	£43 00 + £2 00 p.p.
41	RA 63 Single side band fine tune	£100 00 + £2 00 p.p.
30	SECOND V F O's with film scale for RA 17s No guarantee	£20 00 + £1 50 p.p.
44A	RACAL Test Rig Type MA 91 for RA 17s	£30 00 + £1 50 p.p.
44B	L F Converter Type TRA 137A	£75 00 + £2 00 p.p.

FULL SPEC. UPON REQUEST

TELECOMMUNICATION EQUIPMENT

27a	PYE Mobile Radio Telephones High/low band available V H F Under-dash mounting Microphone on coil lead. Built-in speaker	£25.00 ea. or £40 00 pair + p.p. £1 50 ea.
27b	PYE Mobile Radio Telephones Boot mounting C/W Control Box, wiring loom built-in speaker, microphone on coil lead. High power	£30 00 ea. or £50 00 pair + p.p. £2 00 ea.
27c	MURPHY High Band Base Station 240v	£95 00 + £5 00 p.p.
27d	MURPHY High Band Base Station, 240v + 10 High Band PYE Mobile Units (as in 27a above)	£260 00 + £10 00 p.p.
27e	PYE High Band Base Station, 240v	£100 00 + £5 00 p.p.
27f	PYE High Band Base Station, 240v + PYE High Band Mobile Units (as in 27a above)	£285 00 + £10 00 p.p.

MOUNTING TRAYS/AERIALS ALSO AVAILABLE

JANUARY CLEARANCE

ITEM		
28a	Walkie Talkie Type 88 (Transceiver)	£25.00 pair + £2.00 p.p.
28b	Walkie Talkie Type 18 (Transceiver) 6-10 MHz Inaudible, built-in check meter	£10.00 each + £2.00 p.p.
28c	Walkie Talkie Type 38 (Transceiver), Tunable	£15.00 each + £2.00 p.p.
29	Power & Modulator Unit Type 440 LRV 3B, Rotary converter 24v, DC in SHT out. (Ex-Airline)	£4.00 + £1.50 p.p.
49	LORENZ Telegraph with punch tape feature built in. Send/recv. Similar to Creed 444, 240v, 50 cycles. Clean appearance	£55.00 + £3.00 p.p.
50a	Creed 75 Mk. 4	£25.00 + £3.00 p.p.
50b	Terminal Unit Type DFS/AF/3/1 Built in 1" CAT	£20.00 + £1.50 p.p.
50c	Telegraph (Terminal Unit) Tape Transmitter	£25.00 + £2.00 p.p.
52a	Sperry Gyro Compass Mk. 4	£14.00 + £1.00 p.p.
52b	Navigator Indicator Units for above	£12.00 + £1.00 p.p.
53	Inverter Type 100B 22-28v, DC working in 115v, 3 Phase 400 cycles out. 150 VA FF-8 for Sperry Gyro Equipment	£15.00 for 10 + £1.50 p.p.
54	Olai Telephones, working order, clean appearance, 6 P.O. type	£10.00 for 10 + £3.00 p.p.
55	Klaxon Horns, 24v, or 240v	£8.00 + £1.00 p.p.
56	Geared Motors. These motors have a 600-1 elliptical gearbox built onto the end. High torque 6rpm. Electronic brake. Ideal for aerial, door, etc., rough externally, 12-24v.	£4.00 + £2.00 p.p.
57	Electric Hot Air Hand Dryers, very effective	£8.00 + £1.00 p.p.
58	FERROGRAPH Series 5 Tape Recorder, 100-240v, AC, 1/2 track, built in a strong dural case. Built-in speaker and amplifier	£70.00 + £3.00 p.p.
59	FERROGRAPH Series 3 Tape Recorder. As above, but smaller	£25.00 + £2.50 p.p.

ITEM		
61	TAPE Cartridge Player, built-in 10w amp, Belt driven, 240v, 50 cycles	£5.00 + £1.50 p.p.
84	15 Watt Amplifier, in strong polished wood oak case, 2 input. Base/Treble controls. (Switched output 3 ohm/15 ohm/70v.) 240v, 50-60 cycles. Manufactured by Clarke & Smith	£5.00 + £1.50 p.p.
85	QUAD 2 power amps, rough appearance, minus valves. Sold with circuit	£6.00 + £1.50 p.p.
86	QUAD 22 Control Units, pre-amp	£25.00 + £1.50 p.p.
87	Close circuit fully transistorised video TV cameras, 240v.	£40.00 + £1.50 p.p.
88	QUARTZ Digital Watches, Day, date, hours, mins., secs. Remarkable accuracy. Complete with bracelet and power cell	£15.00 + £2.00 p.p.
89	B 41 Communication Receiver. If version, rough condition	£15.00 + £2.00 p.p.
90	8 62 Communication Receiver. Rough condition	£20.00 + £2.50 p.p.
62	Aircraft Radar (no indicator)	£45.00 + £3.00 p.p.
63	DECCA 404 Marine Radar. Very clean condition. Console display, 220v, DC	£400.00 + £10.00 p.p.
64	DECCA Marine Navigator Mk. 5. Complete 110v, 240v, 50-60 cycles	£1000 + £10.00 p.p.

TEST EQUIPMENT

2	VHF Sweep Generator, 450-900 mcs (Telonic)	£50.00 + £1.50 p.p.
3	Noise Generator, CT 410, 15kcs-160 mcs in 3 bands	£30.00 + £2.00 p.p.
4	Pulse Generator Type 60 100S (Solartron)	£30.00 + £2.00 p.p.
5	Signal Generator 300kcs-30mcs in 7 bands, (Airvac)	£45.00 + £3.00 p.p.
6	Signal Generator CT 202 6-75 mcs	£25.00 + £2.00 p.p.
7	Microsecond Chronometer (Cintel), 12v, DC or 240v, AC	£25.00 + £2.00 p.p.

ITEM		
8	Frequency Calibrator Type 221, 125-20,000 kcs, AC power supply	£30.00 + £1.50 p.p.
9	High resistance measuring set, Type 6625	£20.00 + £2.50 p.p.
10	Calibrator Type TC 99 100-205 mcs	£20.00 + £2.00 p.p.
11	Frequency period counter (Beckman), Type 7360 JH, Teble model, AC power 110-240v	£15.00 + £2.00 p.p.
12	VHF Frequency Standard (Wayne Kerr)	£10.00 + £1.50 p.p.
13	TV line selector Type L 130 (Mullard)	£25.00 + £2.00 p.p.
14	High speed valve tester (Mullard)	£30.00 + £2.00 p.p.
15	Klystron power supply Model 28168 (Elliott)	£35.00 + £2.00 p.p.
16	Voltage Regulator (Lang & Thompson), 100w 220/240v	£40.00 + £4.00 p.p.
17	Wide range oscillator Type 400 C (Dawes)	£15.00 + £2.00 p.p.
18	Video oscillator (Marconi), TF 885, Rough external	£30.00 + £2.00 p.p.
20	Adjustable Phase Corrector (Rank Cintel)	£10.00 + £1.50 p.p.
21	Wave Analyser, Type 7058	£25.00 + £2.50 p.p.
22	Valve Voltmeter TF 4286	£10.00 + £1.50 p.p.
23	RF X Band Test Set Type CT 118	£35.00 + £2.00 p.p.
24	Storage Scope Type SD1 (Hemacope)	£55.00 + £5.00 p.p.
25	Sweep Generator by ADVANCE, 005-100 cycles, square sine and saw tooth, Type SG 88, Very good condition	£250.00 + £5.00 p.p.
91	CR 100 Communication Receiver, Rough condition	£15.00 + £2.00 p.p.
92	Nagard Oscilloscope	£10.00 + £2.00 p.p.
93	A.F. Analyser, 75 cycles to 7.5 kcs, Type 1401 C	£10.00 + £1.50 p.p.
94	Casor D/B Oscilloscope, 110 240v., working, Dirty condition	£15.00 + £3.00 p.p.

ITEM		
95	Beckman Digital Voltmeter (Ratio), Fully transistorised, 240v. No other information available	£18 00 + £2.50 p.p.
96	Solartron Digital Voltmeter Type LM 202.2, Transistorised	£20.00 + £2.50 p.p.
97	Fuel Analyser Type 13171 'United Control Corporation'	£60.00 + £3.00 p.p.
98	Regulated power supply, Model 503, Manul. 'All Power Transformers Ltd., Post. 0-500v, controlable, Reg. 0-250v Built-in check meter, 6.3v. @ 10 amps. Table model	£25.00 + £3.00 p.p.
99	Constant Voltage Transformer, 190-260v, 50 cycles in output, 240vms 75 watts p.l.l	£10.00 + £1.50 p.p.
100	Pen Recorder, 'Record' make, Type MC DC, Decibelmeter 38A/CTA, New condition, 240v.	£50.00 + £1.50 p.p.
101	Twin Pen Recorder, Eveready & Vignoles, ex London, 200-250v, drive 50 cycles, working	£35.00 + £3.00 p.p.
102	Hand Magneto, Mounted on rubber feet	£2.50 + 50p p.p.
103	Reflection co-efficient meter, 2-30 Mc/s	£100.00 + £2.50 p.p.
104	Valve Voltmeter, Type 613 B, Dawes Instruments	£10.00 + £1.50 p.p.
105	Signal Generator Type CT345, 4.5 Khz, 150KHz in 8 switch bands, Built-in calibrator	£15.00 + £3.00 p.p.
106	Solartron Component Indicator (Resolved), Model VP 253.2	£150.00 + £3.00 p.p.
107	Low Frequency Decade Oscillator (Solartron), Model OS 103.2 A	£100.00 + £3.00 p.p.
108	TFA Carrier Converter, Solartron, Type JX 641 A	£100.00 + £3.00 p.p.
109	Solartron Feedback Voltmeter, Type VF 252	£30.00 + £2.50 p.p.
110	Transistor Test Set, Type CT 537 (AVO), New condition	£50.00 + £1.50 p.p.
111	Transceiver, 6 channel (Ex-Airline), Plessey Type PR 160F	£40.00 + £1.50 p.p.

Mail Order only please to **SOUTHERN AVIATION**
 Station Approach, Epsom, Surrey, Telephone: Epsom (03727) 20691

WW-070 FOR FURTHER DETAILS

AEL SPEEDSERVICE




Hard-to-find tubes and semiconductors are normally included in our quotations. We try to give a complete answer.

AEL GATWICK HOUSE HORLEY SURREY RH6 9SU
 Telex 87116 Cables Aerocon Telex Horley Telephone Horley 5353

WW-039 FOR FURTHER DETAILS

ANALOGUE & HYBRID COMPUTERS

Illustrated is the C180, one of our standard range of analogue and hybrid computers which offer high performance and extremely good value for money. This model has 18 i.c. operational amplifiers all of which may be switched for use as integrators, automatic function selection and meter switching, 3-Four quadrant Multipliers, Individual Pot-Set Facilities, 1% accuracy, built-in Stabilised Power Supplies, D.V.M optional extra. Many other features at this very low price of £1,150 complete with patching leads and instruction Book

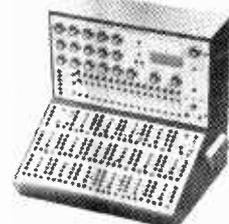

We are specialists in producing computers designed for your own specific research or engineering requirements at prices which are very little more than those for our standard range

Phone or write for details of our Analogue or Hybrid apparatus.


PHYSICAL & ELECTRONIC LABORATORIES LTD.
 MANUFACTURERS OF PRECISION ELECTRONIC EQUIPMENT
 28 Athenaeum Road, Whetstone, London N20 9AE Tel 01-445 7683

WW-023 FOR FURTHER DETAILS

PETITE PRECISION!

A 12V DC POWER TOOL FOR THE DESIGN AND RESEARCH ENGINEER
 AVAILABLE IN KIT FORM OR SEPARATES

EXAMPLE OF FRENCH PRECISION ENGINEERING

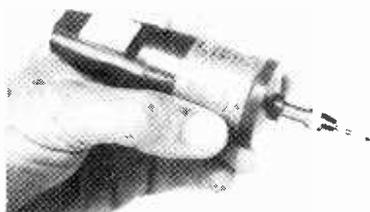

Diameter 33mm
 Weight 160g
 Length 125mm
 Torque 105cmg
 RPM approx. 3000
 at 12V DC
 Power 9/14V DC
 Batteries or AC/DC transformer

Drill, £7.00 P&P 35p




Flexible drive, £5.00
 P&P 35p
 Now in use by the following:
 GPO, BBC, Atomic Energy Authority, British Nuclear Fuels, Weekend TV, Ministry of Defence, Hospitals, Opticians, etc.



Stand £3.76
 P&P 58p

UK DISTRIBUTOR
PRECISION PETITE LTD
 (Les Applications Rationnelles Paris)
 119A HIGH STREET
 TEDDINGTON, MIDDX. UK
 TEL. 01-977 0878

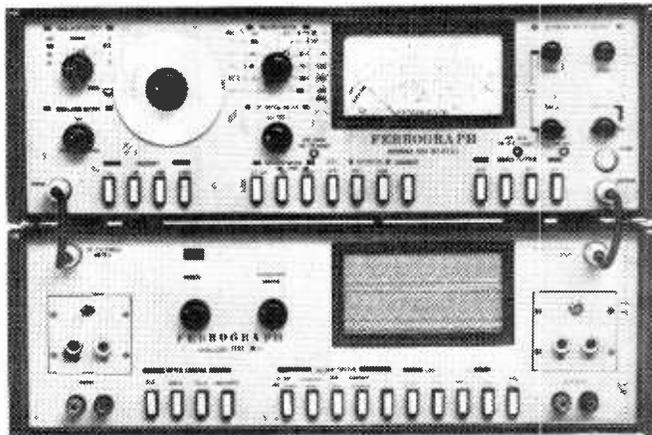SAE for leaflets, price list and order form



Comprehensive Audio Measurements....

... from ONE compact unit comprising low-distortion audio oscillator, eleven-range millivoltmeter, wow and flutter meter (which also measures mean speed drift), and a distortion meter with seven full-scale ranges from 100% to 0.1%. The RTS2 Audio Test Set is used daily in fifty-nine countries throughout the World and is accepted as essential equipment by designers, manufacturers, test engineers, studio staffs and hi-fi reviewers.

Auxiliary Unit ATU1 extends the field of application by providing balanced input and output connections (in stereo pairs), a number of loading and weighting facilities, further amplification and attenuation of the oscillator signal from the RTS2, and loudspeaker monitoring of recorded announcements on test tapes.

Audio Test Set RTS2 (Upper)
Auxiliary Test Unit ATU1 (Lower)

FERROGRAPH


A member of the Wilmot Breeden Group

The Ferrograph Co. Ltd., 442 Bath Road, Slough, Bucks., SL1 6BB, England.
 Telephone: Burnham (06286) 62511. Telex: 847297.

WW — 091 FOR FURTHER DETAILS

Where the facts are

Hi-Fi Year Book tells you everything you need to know about Hi-Fi equipment on the market—what it does, who makes it, what it costs and where to buy it. The directory section alone lists prices and specifications of over 2,000 audio products. Included are authoritative articles by leading experts on the latest Hi-Fi developments and their application. So if you want information like you want Hi-Fi, order your copy today—before it sells out!

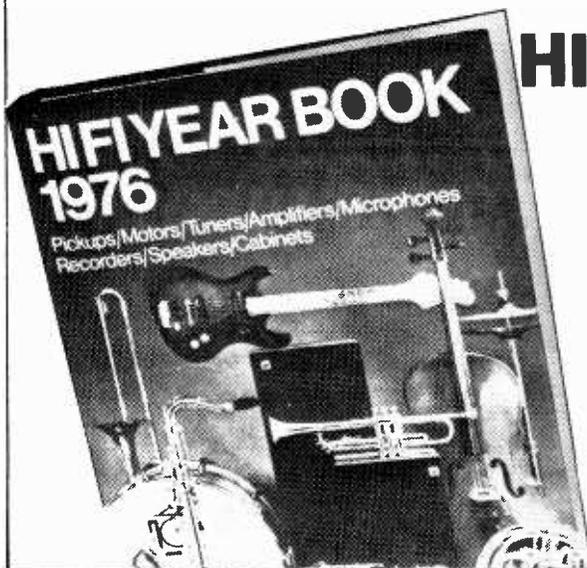

HI-FI YEAR BOOK 1976

Available direct from the publishers at £2.35 inclusive
 or from leading booksellers & newsagents price £2.00.

ORDER FORM

To: Room 11, IPC Electrical-Electronic Press Ltd., Dorset House, Stamford Street, London SE1 9LU

Please send me.....copy/copies of Hi-Fi Year Book 1976 at £2.35 per copy inclusive. I enclose remittance of £..... (cheque/P.O. payable to IPC Business Press Ltd).


Name (please print)

Address

.....

Registered in England No. 677128 Regd. Office Dorset House, Stamford Street, London SE1 9LU

INSIST ON VERSATOWER

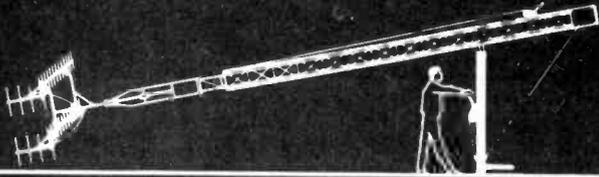

Acclaimed as the World's leading
telescopic tiltover tower in the
field of radio communication.
Models from 25' to 120'



Look for the name
STRUMECH

Strumech Engineering Co Ltd
Coppice Side, Brownhills, Walsall, Staffs

WW-042 FOR FURTHER DETAILS

*AUTOCRAT

Farnell offer the only Digital Multimeter with
all these features:-

AUTORANGING AUTOPOLARITY AUTOZERO

SIX RESISTANCE RANGES LARGE DISPLAYS

A.C. AND D.C. VOLTS AND CURRENT

TEMPERATURE MEASUREMENT

at £140 (mains powered version)
or £165 (mains/battery version)

**The absolute leader in its class*

Details from:
Farnell Instruments Ltd.
Wetherby, W. Yorks, LS22 4DH
Tel: 0937-3541 or 01-864 7433



WW-017 FOR FURTHER DETAILS




naim audio the power amplifier

BE FAIR TO YOUR MUSIC


Reproduction of
sound and its acceptability
is dependent on a combination
of physical parameters not yet
fully explored. We believe that
only a compatible combin-
ation of specifications will
enable a system to

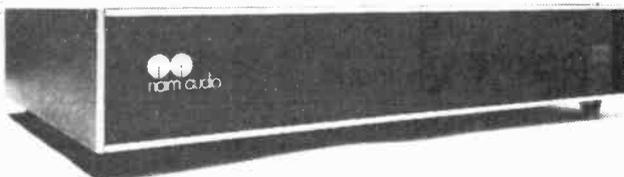reproduce music. We
have taken care that the
NAC 12 and NAP 160 pre
and power amplifier will do
so faithfully, while accepting
the output of any pickup
cartridge and driving
any loudspeaker.



Naim Audio Ltd, 11 Salt Lane, Salisbury, Wilts. Tel: (0722) 3746

WW-055 FOR FURTHER DETAILS

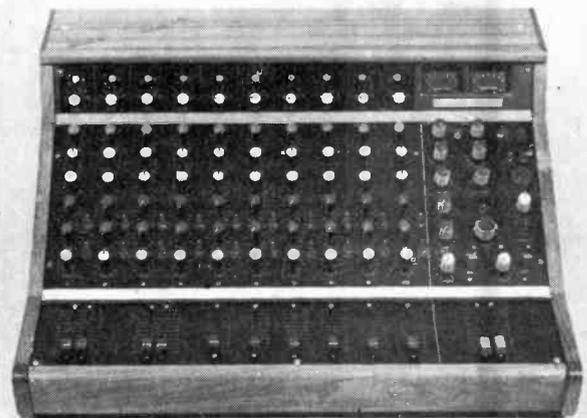

IS CHILTON'S MIXER THE BEST FOR YOUR USE?

Magnetic tapes Ltd make the 10/2 above as well as
a 16/2 and a 12/4 with all the inherent flexibility
and quality customarily found in big studio mixers.
Most of our mixers are constructed to meet the
varying demands of the customer, perhaps we can
do one for you. Prices start at £365 for the basic
10/2 + VAT @ 8%.

MAGNETIC TAPES LTD.
Chilton Works, Garden Road, Richmond
Surrey TW9 4NS - 01-876 7957

Bridge in a thousand



One part in one thousand is the accuracy of Universal Bridge B224 from 10 ohms to 1 gigohm, 0.1pF to 10 microfarads and 1 nanomho to 100 millimhos. Monitor its 1592Hz source frequency and also get 0.1% from 1mH to 10kH. With reducing accuracy, coverage extends above and below the ranges quoted, on R, C, G and L. Resistive and reactive terms read simultaneously. Sockets for 200Hz — 50kHz operation. Internal rechargeable battery. Many other valuable features detailed in Data Sheet B224.

WAYNE KERR


A member of the Wilmot Breedon group

For more information phone Bognor (02433) 25811 or write to Wayne Kerr, Durban Rd., Bognor Regis, Sussex PO22 9RL

WW — 090 FOR FURTHER DETAILS

itam

ITAM 305 (8TRACK) MASTER RECORDER

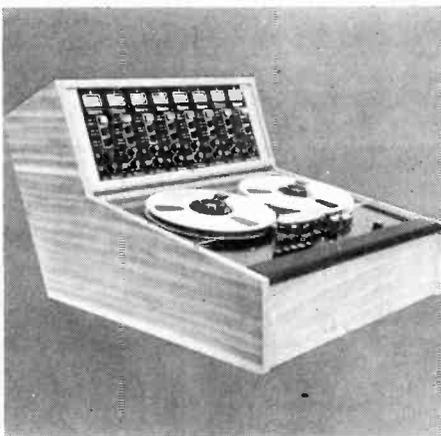

Fully modular electronics using plug-in PCB's through-out. Separate sync and replay amps give identical levels. Switchable VU's with slow decay. Individual oscillator for each channel. Dolby A switching facility. Comprehensive facilities include sync on all channels, servo controlled capstan, modular electronics, variable speed (optional), relay-solenoid operation. Compact presentation for easy portability.

£1790 + VAT Full console optional extra

Compatible 8-output Mixer available

£1260 + VAT

OTARI

OTARI DP-4050 CASSETTE COPIER



Ideal for one copy or ten thousand. Eight times copy speed, foolproof operation for non-skilled personnel, modular construction, servo-controlled direct capstan drive.

Immediate delivery


THESE ITEMS ARE INDUSTRIAL PRODUCTS AND SUBJECT TO 8% VAT

Industrial Tape Applications



5 Pratt Street, London NW1 0AE
Telephone: 01-485 6162. Telex: 21879

WW — 075 FOR FURTHER DETAILS

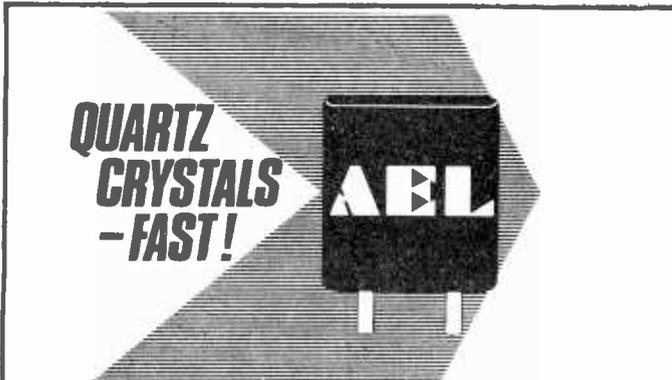

QUARTZ CRYSTALS - FAST!

AEL

AEL GATWICK HOUSE, HORLEY, SURREY, ENGLAND
 Tel: Horley (02934) 5353
 Telex: 87116 (Aerocon Horley) Cables: Aerocon Telex Horley

WW-038 FOR FURTHER DETAILS

BUILD YOURSELF A 25W AMP FOR ONLY

£29-95 + 4-05 VAT

COMPLETE KIT SUPPLIED

DORAM, one of Britain's leading mail-order distributors of audio accessories & components brings you the 'INTERNATIONAL 25' - a 25W per channel Stereo Amp. - that you can build yourself!

This 'real-value-for-money' kit is supplied with clear assembly instructions and reliable components to give you a big sound to be proud of.

Overseas orders £34-50

- * Triple Op-amp pre-amplifier
- * Power Darlington's in output stage
- * 25W per channel into 8 ohms
- * Modern, elegant styling

GENUINE BIG-SOUND VALUE!

MANY MORE INTERESTING AUDIO KITS AND COMPONENTS LISTED IN DORAM'S CATALOGUE PRICED AT ONLY 60p



DORAM


DORAM ELECTRONICS LTD
 P.O. Box TR8, Looe, LS12 2UF
 Tel: Looe (0532) 34222

CJL C.J.L. LTD. P.O. BOX 34, CANTERBURY, CT1 1YT

ALL PRICES INCLUDE P&P AND V.A.T.

SOLDERING IRONS (ANTEX)		'X25' Dual-in-line de-soldering bits, 14A, 14B - each	£3.50
15W, 'C' miniature irons, slide on & off 3/32" bit	£2.30	50W, 'X.50 T.C' temperature controlled irons, low leakage, 1/8" bit	£8.50
3/32", 1/8", 3/16" bits-each	£0.45	12V, 25W, 'MLX' battery operated irons - slide on & off 1/8" bit, wallet, booklet	£2.95
'C' Elements	£1.10	3/32", 1/8", 3/16" bits-each	£0.47
18W, 'G' miniature irons, slide on & off 3/32" bit	£2.50	Soldering Kits, 'SK1', 'C' iron, 2 spare bits 3/32" & 5/32", heat sink, solder, base, booklet	£3.85
3/32", 1/8", 3/16" bits-each	£0.45	Stands (all models), High grade base, spring, sponges, bit space	£1.10
'G' Elements	£1.35	25W, 'X25' De-soldering irons	£6.50
15W, 'CCN' miniature irons, low leakage, slide on & off 3/32" bit	£2.70	18W, 'GSS' De-soldering irons	£6.50
3/32", 1/8", 3/16" bits-each	£0.45	Foot pump	£1.70
'CCN' Elements	£1.50	'KEYNECTORS' Rapid connect to mains, Piano switches, neon, 13A fuse	£3.55
25W, 'X25' irons, low leakage, slide on & off 1/8" bit	£2.30		
3/32", 1/8", 3/16" bits-each	£0.47		
'X25' Elements	£1.15		

GROOVAC

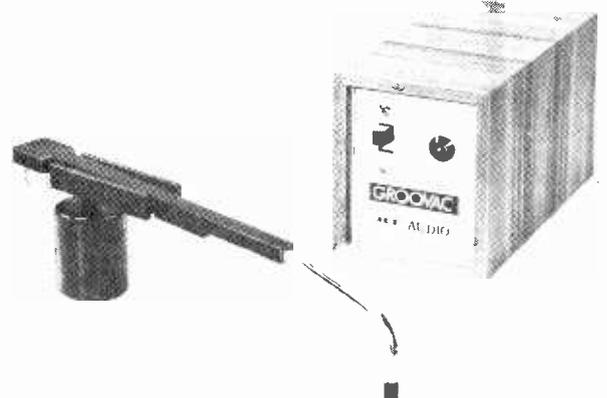

vacuum record cleaner

Vacuum cleaning is the best way to remove dust, especially fine dust. Now with the Groovac, vacuum cleaning is available for extracting the particles from inside record grooves which are responsible for record and stylus wear - while your record is playing.

For full details please write to:-

RI AUDIO Kernick Road, Penryn, Cornwall TR10 9DQ, England
 Telephone Penryn 72753

WW - 045 FOR FURTHER DETAILS

JES AUDIO INSTRUMENTATION

Illustrated the Si453 Audio Oscillator

SPECIAL FEATURES:

- ★ very low distortion content—less than 0.03%
- ★ an output conforming to RIAA recording characteristic
- ★ battery operation for no ripple or hum loop
- ★ square wave output of fast rise time

£50.00

also available

Si451 Millivoltmeter
 ★ 20 ranges also with variable control permitting easy reading of relative frequency response **£50.00**


Si452 Distortion Measuring Unit
 ★ low cost distortion measurement down to 0.01% with comprehensive facilities including L.F. cut switch, etc **£40.00**

ALL PRICES PLUS VAT

J. E. SUGDEN & CO. LTD., CARR STREET, CLECKHEATON, W. YORKS. BD19 5LA. Tel. 0274-872501

WW-013 FOR FURTHER DETAILS

MULTI-PEN RECORDERS

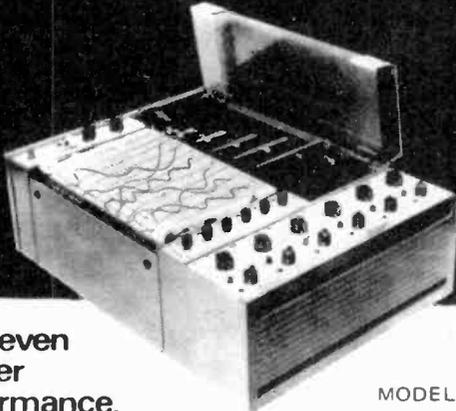

with even greater performance.

MODEL MC 641

100 μ Vf.s. 0.3 sec.f.s.

MULTICORDER


- Multi-channel, 2-6 with full range zero set.
- Multi-pen - fibre tip. 6 colours. ● 16 switched chart speeds.
- Choice of Z fold or roll chart. ● Five plug-in preamplifiers switched ranges 100 μ v - 500 Vf.s. ● 250mm(10") chart width



ENVIRONMENTAL EQUIPMENTS LTD.
Eastheath Avenue, Wokingham,
Berks. RG11 2PP. Tel: Wokingham 784922.

WW - 020 FOR FURTHER DETAILS

nombrex

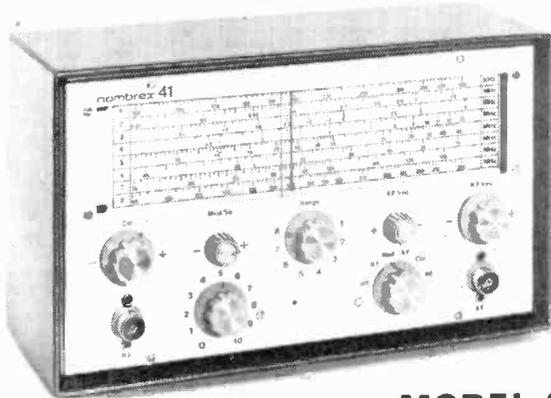

MODEL 41
R.F. SIGNAL GENERATOR
Price £54.85


- ★ 150 KHz - 220 MHz on fundamentals. PLUS V.A.T.
- ★ 8 clear scales - Total length 130mm.
- ★ Spin-Wheel Slow Motion Drive 11 - 1 ratio.
- ★ Overall Accuracy - 2 1/2 %.
- ★ Modulation, Variable depth and frequency.
- ★ Internal Crystal Oscillator providing calibration checks throughout all ranges.
- ★ Mechanical scale adjustment for accurate alignment against internal 1MHz crystal oscillator.
- ★ Powered by 9V Battery.

*Trade and Export enquiries welcome.
Send for full technical leaflets.
Post and Packing £1.00 extra*

**NOMBREX LTD., POUND PLACE, WOLBOROUGH STREET,
NEWTON ABBOT, DEVON, TQ12 1NE
Tel. Newton Abbot 68297**

WW-028 FOR FURTHER DETAILS

* £88.00

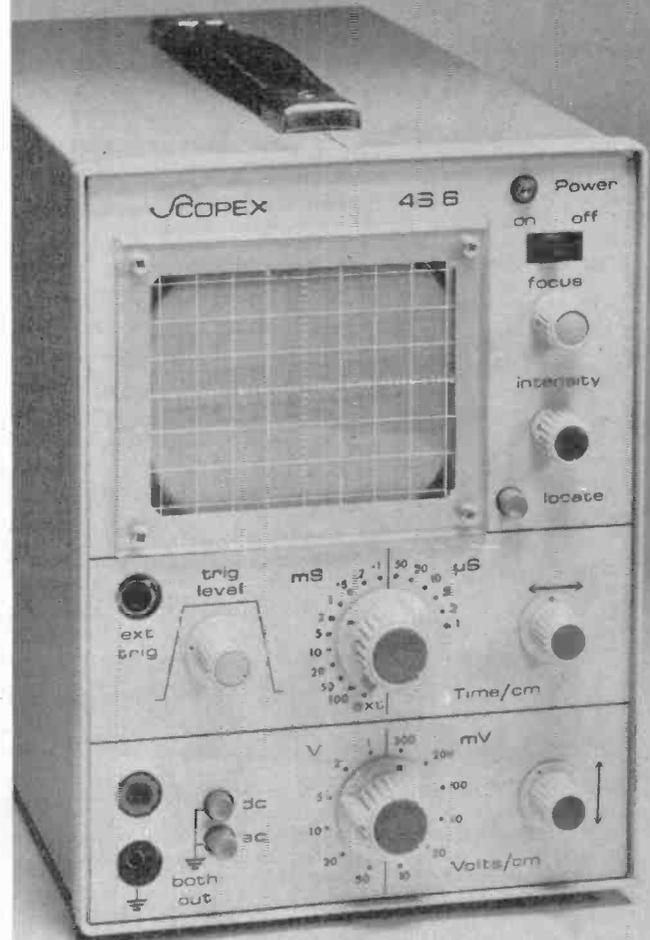

The Scopex 4S-6 Single Beam Oscilloscope

- 6 MHz Bandwidth
- 10 mV/cm Sensitivity
- 1 μ S/cm - 100 mS/cm Timebase (16 Calibrated Ranges)

For immediate attention write or telephone



Scopex Instruments Ltd., Pixmore Industrial Estate,
Pixmore Avenue, Letchworth, Herts SG6 1JJ
Tel: Letchworth (04626) 72771

*UK List exVAT (at time of going to press)

WW-087 FOR FURTHER DETAILS

BY POPULAR DEMAND.


Yes indeed. We get asked to do it so often, so that we went out and really did it. A complete series of FM tuner systems in sleek teak cases, with eggshell finish mild steel chassis, and really durable front panel. We think that we have provided an FM tuner for most tastes and budgets. In fact, a three meter receiver, if you'll pardon the pun. (100MHz = 3 metre wavelength, get it, eh?)



The Elektrik FM Wireless System: a brief specification is shown in the following order, beneath each system description:

Input for 26dB S/N	Image rejection	AF output	THD	
Larsholt 7252† + 993090†	-56dB	1.5v	0.3% typ. mpx.	£60.75
Larsholt 7253† + BLR3107 mpx filter	-55dB	80mV	0.55% typ. mpx.	£50.75
EF5603 + 8001 IF & decoder*	-85dB	80mV	0.5% typ. mpx.	£48.00
EC3302 + 8001 IF & decoder*	-52dB	80mV	0.5% typ. mpx.	£40.00

† Built and tested modules * Parts kits

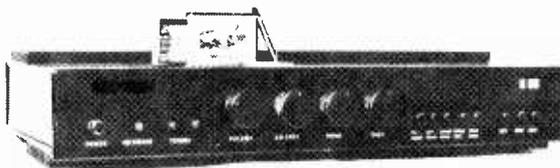

The U66 25+25W amplifier, with mpx tuner. A superb low look receiver kit, with aluminium extrusion case, one piece PCB construction, toroidal transformer, modular tuner section. The features include tape monitor, loudness (volume related) and a fully fuse protected PSU and output section... £76.00

Varicap tuned MW/LW receiver modules - the 7003 series. The latest development - with FET input, ferrite rod, electronic switching for MW/LW, ceramic filter. 9003 kit - £9.85, 9003 built £11.85.

SGS audio amplifiers and applications PCBs.

- TDA2020 20w rms with sufficient heatsink... 2.99.
- TDA2020k 2xTDA2020 with PCB and R's&C's... 7.85.
- TCA940 10w rms IC with heatsink... 1.85.
- TCA940k 1xTCA940, PCB, R's,C's heatsink... 3.05.
- TBA810s 7 w rms IC... 1.30.
- TBA810k 1xTBA810, PCB, R's, C's, heatsink... 2.75.

All SGS approved PCBs, all devices overload protected.

More new things:

Birdy filter for stereo radio. Flat to 55kHz, whereupon the slope dives off to -33dB at 200kHz. Fit between the detector and stereo decoder... 1.75.
3000 series stereo control amp/4000 series PU amp/ 2000 series AFU/ Ferranti small signal devices/Motorola power discretes (BD165-609-etc).


Postage £2.50 per tuner system. VAT extra at 25%. Full catalogue 40p, postage for general component orders is 22p - Shortform price list available FOC with an SAE.

ambit int
37 High Street
BRENTWOOD Essex
Post code: CM14 4RH, telephone 216029; tlx 995194.

SOUND AND COMMUNICATION EQUIPMENT

from

CRYSLON

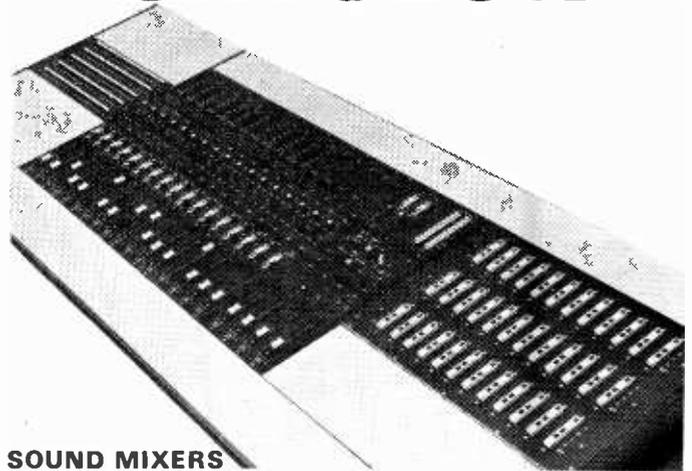

SOUND MIXERS
TALKBACK UNITS
STAGE MANAGERS SYSTEMS
POWER AMPLIFIERS 100 WATT

CRYSLON ELECTRONICS LTD.

Berrington Road
Leamington Spa, Works.

Tel. Leamington Spa (0926) 37628/9

WW-084 FOR FURTHER DETAILS

See our Ad. in Everyday Electronics for a superb 4-Digit Clock CMOS from the leading manufacturers at the new manufacturers' 1 off prices

SINTEL for CMOS

CD4004AE 0.17	CD4021AE 0.83	CD4039AE 2.86	CD4057AD 20.35	CD4082BE 0.18
CD4011AE 0.17	CD4022AE 0.79	CD4040AE 0.88	CD4069AD 10.84	CD4085BF 0.39
CD4013AE 0.17	CD4023AE 0.17	CD4041AE 0.69	CD4080AE 0.82	CD4086BE 0.59
CD4008AE 0.37	CD4024AE 0.64	CD4042AE 0.69	CD4081AD 16.43	CD4087BE 0.46
CD4017AE 0.17	CD4025AE 0.17	CD4043AE 0.83	CD4082AT 7.33	CD4088BE 0.86
CD4009AE 0.79	CD4026AE 1.42	CD4044AE 0.77	CD4083BE 0.30	CD4089BE 0.86
CD4010AE 0.46	CD4027AE 0.46	CD4045AE 1.15	CD4084BE 0.58	CD4090BE 1.50
CD4011AE 0.17	CD4028AE 0.74	CD4046AE 1.10	CD4085BE 0.18	CD4501BE 0.32
CD4012AE 0.17	CD4029AE 0.94	CD4047AE 0.74	CD4086BE 0.18	CD4502BE 1.02
CD4013AE 0.46	CD4030AE 0.46	CD4048AE 0.46	CD4070BE 0.18	CD4503BE 4.20
CD4014AE 0.83	CD4031AE 1.81	CD4049AE 0.46	CD4071BE 0.18	CD4510BE 1.28
CD4015AE 0.83	CD4032AE 0.88	CD4050AE 0.46	CD4072BE 0.18	CD4511BE 1.85
CD4016AE 0.46	CD4033AE 1.14	CD4051AE 0.77	CD4073BE 0.18	CD4512BE 1.83
CD4017AE 0.83	CD4034AE 1.56	CD4052AE 0.77	CD4075BE 0.18	CD4520BE 1.83
CD4018AE 0.83	CD4035AE 0.97	CD4053AE 0.77	CD4076BE 1.27	CD4537BF 1.18
CD4019AE 0.46	CD4036AE 1.82	CD4054AE 0.95	CD4077BE 0.18	CD4550BE 0.74
CD4020AE 0.82	CD4037AE 0.78	CD4055AE 1.08	CD4078BE 0.18	CD4558BE 1.45
	CD4038AE 1.82	CD4056AE 1.08	CD4081BE 0.18	MC14558CP 4.07

RCA 1975 CMOS Databook 400 pages of data sheets and 200 pages of circuits, applications and other useful information 2.30 (No VAT) + 37p P&P

ATTRACTIVE ALARM CLOCK KITS - all components including attractive slim case, to build a 6-digit alarm clock with snooze, intensity control, 12- or 24-hour format

Complete kit with DL704E 0.3" LED displays £22.80

Complete kit with FND500 0.5" LED displays £26.70

32.768kHz Min. Quartz Crystal for watch or clock £3.60

Xtal Timebase Kit: Will provide stable 50cps for clock IC's giving time accurate to a few secs a month, contents small PCB, 32 768 kHz Xtal 3 CMOS IC's, trimmer C's R's, IC skts £6.40

COMMON CATHODE LED DISPLAYS

DL704E 0.3"	only 85p
FND500 0.5"	£1.50
MAN3M 0.13"	48p
DL33MMB 3 digits in OIL	£2.00

ILIXCO 3½ digit Liquid Crystal 0.5" display, with socket £9.40
5LT01 0.5" 4 digit clock display with AM/PM, green phosphor diode £5.80

IC's MK50253 4 or 6 digit 12 or 24 hr Alarm Clock IC with snooze £5.60

MK50250 identical to MK50253 except that it is 24 hr only £5.00

MK5030M CMOS watch IC for LED display with date and seconds £19.50

MM5314 4/6 digit 12/24 hr clock £4.44. AY51224 4 digit clock £4.25

SN75491 81p. SN75492 £1.02

SOLDERCON PINS for Lowest Cost IC sockets for TTL, CMOS, I-L displays Strip of 100 for 50p, 400 for £2, 1000 for £4, 3000 for £10.50.

LSI Sockets (Soldercon Pins with nylon supports) 22, 24, 28 or 40 pin 30p.

20 way Colour-Coded Flexible Flat Cable £1 per m. £8.50 for 10m

7-way Boss Switch: 7 ultra-min toggle sws in 14 pin DIL £2.60

ADD VAT AT 8% - new 25% rate does not apply to any of the above goods 15p P&P on orders under £3. All orders processed on the day of receipt

Official orders welcomed, written, phoned or telexed, from Polys. Univs. Schools, Govt. Dept. Nat. Inds., Rated Cos. Fastest delivery for R & O.

Exports No VAT 35p (Europe), £1 (Overseas) for Air Mail P&P

Full Price List and Data with any order, or free on request

SINTEL 53c Aston Street, Oxford
Tel: 0865 43203. Tlx: 837650 A/B ELECTRONIC OXFORD

PROFESSIONAL - FREQUENCY COUNTERS BY HOYMITZ

Up-to-the-minute design. All five of our range of frequency-period-ratio counters are **directly gated**. For best resolution — FAST.

Stability. Electronic controlled crystal oven 3 parts 10^6

Bright. .63" character height display. (All Nine)

CHOICE. Filament or LED with Polaroid Filter.

All counters have suppressed leading zeros and auto decimal point positioning for easy positive readings. The memory is also standard.

Suffix F— Filament

Suffix L— LED

Type DG100L
Type DG100F
Sensitivity 10mV
Frequency 100 Mhz
PRICE £199.00

Type DG32L
Type DG32F
(8 digit only)
Sensitivity 10mV
Frequency 32 Mhz
PRICE £169.00

Type DG700L
Type DG700F
Sensitivity AMP 1.0C-200 Mhz. 10mV. PRICE £569.00
Sensitivity AMP 2.40-700 Mhz. 10mV

Type DG400L
Type DG400F PRICE £349.00
Sensitivity AMP 1.0C-150 Mhz. 10mV
Sensitivity AMP 2.40 Mhz-400 Mhz. 10mV

Type DG500L
Type DG500F PRICE £475.00
Sensitivity AMP 1.0C-150 Mhz. 10mV
Sensitivity AMP 2.40 Mhz-500 Mhz. 10mV

SPECIALS TO ORDER

Telephone Today 0642-43124
Telex No. 587238


Hoymitz Electronics Ltd.

7-9 Albert Terrace, Middlesbrough
Cleveland, TS1 3PA, England

Prices exclusive of VAT

WW—077 FOR FURTHER DETAILS

Trip Amplifiers

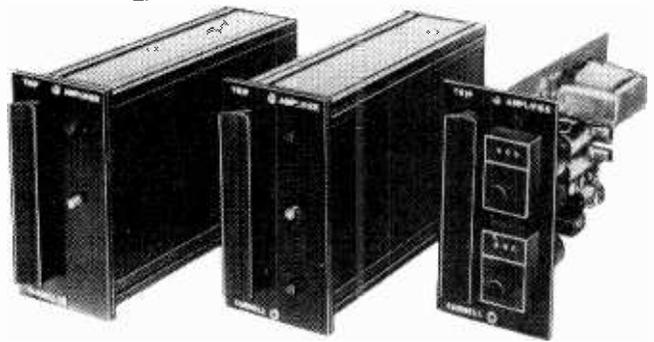

SET-POINT CONTROL OF VOLTAGE, CURRENT & TEMPERATURE

When input signals derived from voltage, current or temperature sources, fall outside pre-determined limits, relay changeover contacts (rated at 30V d.c. 5A) operate within this unit to control peripheral equipment.

Single or twin trip levels are available set by lockable 3 digit dials or alternatively by multi-turn screwdriver operated controls. Units are ready for panel mounting or can be supplied to fit a standard I.S.E.P. rack. Both versions incorporate a regulated power supply. A compatible range of Alarm Annunciators and Digital Panel Meters is available.



Farnell

INDUSTRIAL
CONTROL
DIVISION

FARNELL INSTRUMENTS LIMITED
WETHERBY · WEST YORKSHIRE LS22 4DH · TEL: 0937 3541 or 01-864 7433

WW—082 FOR FURTHER DETAILS

POWER AMPLIFIER


120 watts RMS into 4 ohms



For full details on our range of mixers, amplifiers and light control units, contact:

ICELECTRICS LTD
15 ALBERT ROAD, ALDERSHOT
HANTS. TEL: 0252 28514

WW—078 FOR FURTHER DETAILS

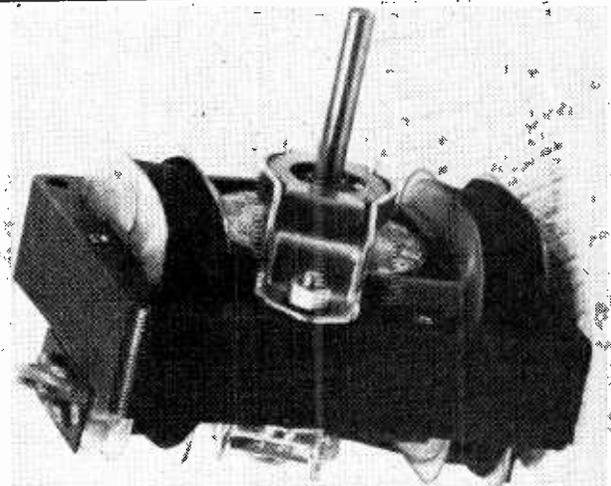

SHADED 4 POLE AC MOTORS

Slow drive speed.

Smooth running and freedom from 50 Hz vibration.

Low magnetic leakage field.

No electrical interference.

Speed torque characteristics adaptable to individual requirements.

Full load power up to 4 watts.

Particularly suitable for tape recorders, record players, instrumentation.

Also DC Motors up to 10 watts output

A. D. Bayliss & Son Ltd.

PFERA WORKS

REDMARLEY

GLOUCESTER GL19 3JU

Tel. Bromesberrow 364 & 273

STD 053-181-364 & 273

WW—076 FOR FURTHER DETAILS

Telequipment's new dual trace 10 MHz battery operated oscilloscope




...and that's about the size of it

4 x 9 x 11 inches! Weight, less than 10lb!
Price, only £275*.

Small in all but specification, Telequipment pack into the tiny frame of the D32 features normally associated with instruments twice its size.

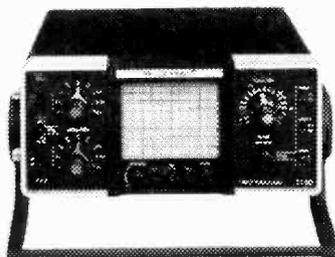Easily carried on any assignment the D32 is probably the smallest and least expensive scope of its kind in the world.



*Exclusive
of VAT

Priced at £275* (including re-chargeable batteries) this dual trace scope offers 10MHz bandwidth at 10mV/div sensitivity; automatic selection of chopped or alternate modes; automatic selection of TV line or frame displays; and the choice of battery or mains operation.

Size up the D32 for yourself and write or phone for a demonstration of this truly remarkable instrument now.

Telequipment gives you more scope for your budget

TELEQUIPMENT



**Tektronix U.K. Ltd.,
Beaverton House, P.O. Box 69, Harpenden, Herts.
Telephone: Harpenden 63141 Telex: 25559**

TQ4

wireless world

Electronics, Television, Radio, Audio

JANUARY 1976 Vol 82 No 1481

Contents

- 29 **Models of behaviour**
- 30 **Audibility of phase effects in loudspeakers** by *H. D. Harwood*
- 32 **Books received**
- 33 **Electronic systems** — 1 by *W. E. Anderton*
- 35 **News of the month**
 - Atomic heart power
 - London honours Blumlein
 - Microprocessor comes clean
- 37 **Wireless World Teletext decoder** — 3 by *J. F. Daniels*
- 42 **New m.w./l.w. broadcasting plan**
- 43 **John Logie Baird and the Falkirk transmitter** by *P. Waddell, W. V. Smith and J. Sanderson*
- 47 **What's in a name?** by "*Cathode Ray*"
- 48 **Letters to the editor**
 - Citizens' Band in Europe
 - Audio amplifier load specification
 - The consultants
- 51 **Television tuner design** — 4 by *D. C. Read*
- 58 **Circuit ideas**
 - MSF receiver using a tone decoder
 - Resistance modulator or periodic switch
 - Sequence generator for radio control
- 61 **Transmitter power amplifier design** — 4 by *W. P. O'Reilly*
- 65 **January meetings**
- 66 **World of amateur radio**
- 71 **Electronic circuit calculations simplified** — 6 by *S. W. Amos*
- 74 **H. F. predictions**
- 75 **Circards 27: linear c.m.o.s. circuits** by *J. Carruthers, J. H. Evans, J. Kinsler and P. Williams*
- 77 **New products**
- 81 **1976 conferences and exhibitions**
- 82 **Real and imaginary** by "*Vector*"
- 121 **APPOINTMENTS VACANT**
- 136 **INDEX TO ADVERTISERS**

Price 35p (Back numbers 50p, from Room 11, Dorset House, Stamford Street, London SE1 9LU.)
Editorial & Advertising offices: Dorset House, Stamford Street, London SE1 9LU.
Telephones: Editorial 01-261 8620; Advertising 01-261 8339.
Telegrams/Telex: Wiworld Bisespres 25137 London. Cables: "Ethaworld, London SE1?"
Subscription rates: 1 year: £7.00 UK and overseas (\$18.20 USA and Canada). Student rate: 1 year, £3.50 UK and overseas (\$9.10 USA and Canada).
Distribution: 40 Bowling Green Lane, London EC1R 0NE. Telephone 01-837 3636.
Subscriptions: Oakfield House, Perrymount Rd, Haywards Heath, Sussex RH16 3DH. Telephone 0444 53281. Subscribers are requested to notify a change of address.

© IPC Business Press Ltd. 1976



This month's front cover shows a group of Plumbicon* lead oxide photoconductive television camera tubes available from Mullard Ltd.

*registered trade mark for television camera tubes.

IN OUR NEXT ISSUE

Radio controlled clock. Design for self-setting digital clock operated by time-of-day code now transmitted by MSF Rugby.

Novel waveguide. New type of structure for dipole-mode propagation of microwaves offers practical advantages of smaller size and lower attenuation.

Sensing temperature. Principles and characteristics of the thermistor and the somewhat neglected thermocouple, outlining basic measurement methods.

SIXTY-SIXTH YEAR
OF PUBLICATION

ibpa
International Business
Press Associates

A good image gets around.



EEV's Leddicon[®] is the consistent colour tube.

The EEV Leddicon[®] is the advanced lead oxide colour tube made with high purity materials to the most precise standards.

Ease and speed of line-up are exceptional. Perfect colour registration can be achieved in seconds. Geometry is precise. Manufacture is consistent. Tube dependability is excellent.

EEV Leddicons are in use with most major colour networks. A good image gets around - and so does EEV service. All EEV camera tubes are available across the world from local representatives.

For your nearest contact, please write to EEV at Chelmsford, Essex, England.

Leddicon Type	Application	Features	Leddicon Type	Application	Features
P8000	Monochrome Luminance + Chrominance channels	30mm diameter Integral mesh construction	P8130	Monochrome Luminance + Chrominance channels	30mm diameter, coaxial construction Separate or integral mesh Fixed integral light bias
P8001	Monochrome Luminance + Chrominance channels	30mm diameter Separate mesh construction	P8131 *	Monochrome Luminance + Chrominance channels	Similar to P8130 series but with variable integral light bias
P8003	Red channel Luminance/green channels Monochrome channel	30mm diameter Separate mesh with extended red response, with or without IR faceplate filter	P8132	Red Channel Luminance/green channels Monochrome channel	Similar to P8130 series but with extended red response, with or without IR faceplate filter
P8005 *	Monochrome Luminance + Chrominance channels	30mm diameter Separate mesh Improved lag under low-light conditions	P8133 *	Red Channel Luminance/green channels Monochrome channel	Similar to P8131 series but with extended red response, with or without IR faceplate filter

* Uses integral light bias but requires socket modification and bias supply

[®] Leddicon is a Registered Trade Mark of English Electric Valve Co Ltd

EEV and M-OV know how.

ENGLISH ELECTRIC VALVE CO LTD, Chelmsford, Essex, England CM1 2QU. Tel: 0245 61777. Telex: 99103. Grams: Enelectico Chelmsford. **SBC** 

WW — 083 FOR FURTHER DETAILS

wireless world

Models of behaviour

Editor:
TOM IVALL, M.I.E.R.E.

Deputy Editor:
PHILIP DARRINGTON
Phone 01-261 8435

Technical Editor:
GEOFFREY SHORTER, B.Sc.
Phone 01-261 8443

Assistant Editors:
BILL ANDERTON B.Sc.
Phone 01-261 8620
BASIL LANE
Phone 01-261 8043
MIKE SAGIN
Phone 01-261 8429

Production:
D. R. BRAY

Advertisements:
G. BENTON ROWELL (*Manager*)

KEVIN BURNAL
Phone 01-261 8515

O. BAILEY (*Classified Advertisements*)
Phone 01-261 8508 or 01-261 8423

JOHN GIBBON (*Make-up and copy*)
Phone 01-261 8353

IPC Electrical-Electronic Press Ltd
Publisher: Gordon Henderson

The turn of the year sees the world in the trough of an economic recession, the deepest for Britain since the second world war. We are told there may be an upturn in 1976. Will there be another boom? We recognize, at any rate, that we are in the grip of another business cycle — and people have been experiencing these now for over a hundred years. Thoughtful engineers observe that if these events really are cyclical there must be a system at work somewhere, or rather a complex of interacting system. And systems can be measured, analysed and controlled to make them do what we want. But are the politicians, economists, business leaders, trade union officials and others who run our affairs really aware of this? Are they capable of even conceiving that there are mechanisms at work, let alone trying to make use of this knowledge?

A small elite, of course, is aware. In the writings of the econometrists, for example, you will find plenty of talk of input, output, gain, positive and negative feedback loops, damping, stability and the like. The fact that many of these terms are consciously or unconsciously borrowed from electronics is no accident, for electronic engineering has provided a whole universe of concepts and analogies which are highly flexible and readily adaptable to the complexities of economic systems.

In this issue we introduce a new series of articles which may make a small contribution to the understanding of systems in human affairs (economic, biological, sociological and so on) in terms of the models provided by electronic physical processes, circuits, systems and engineering concepts. It is based on Professor Chaplin's pioneering work on A-level electronics courses for schools — and this is a significant point. In the sixth form, young people's ideas about the world are still reasonably fluid. They are not yet bound to the conceptual framework of the historian, the economist, the physicist, the geographer, the biologist or the engineer. At this age it's not a bad idea for our future politicians, etc., to study a set of physical models embodying universal principles. In this respect the subject is rather like the classics. It certainly provides a better mental frame of reference for understanding the systems in human activities than those offered by the conventional disciplines.

Electronics, of course, has also given us instruments by which our models can be quantified — analogue and digital computers. We have, for example, Professor Stone's input-output model of the British economy at Cambridge, handling about 300 identities and 700 relationships on a digital computer, by which it is hoped to forecast the state of the economy in 1980. Other computer models have been concerned with the activities of man on a global scale, predicting quantitatively the interaction of population growth, industrialization, malnutrition, depletion of natural resources and deterioration of the environment.

We must be very careful, though, not to lead people astray by simple deterministic models which don't take account of all the variables. Processes in the real world are often non-linear, probabilistic rather than deterministic, have time delays, and include behaviour caused by such things as human panic and euphoria. The impractical ideal is for our electronic models to provide ways of representing all these characteristics. The practical realization is never to accept that the ideal has been achieved.

Audibility of phase effects in loudspeakers

Are "linear phase" loudspeakers a gimmick?

by H. D. Harwood, B.Sc.

BBC Research Department

The fact that most loudspeakers have a non-uniform phase-frequency response has long been known and the audibility of the effects of the phase changes in loudspeakers has been debated in the literature many times. This article reviews the position in the light of present-day knowledge and especially of the fact that some manufacturers are now selling loudspeakers in which it is claimed that particular attention has been paid to the phase-frequency response. The article is concerned with the effects of phase from two aspects — that of sound quality and that of stereo image formation.

Taking the question of sound quality first, it is a commonplace observation that the polarity of the connection to the loudspeaker has almost no effect on sound quality. A few observers have claimed to be able to detect such a change on particular types of programme but even if this is accepted as correct the effect is so small that no programme producer, disc manufacturer, pickup manufacturer or loudspeaker manufacturer has ever thought it worthwhile to attempt to specify which polarity is correct. Furthermore, no producer attempts to bother about polarities when mixing the outputs of single multi-microphone pickups for light music programmes. This result is at first sight somewhat surprising, as a programme waveform is well known to be appreciably asymmetrical and it is not at all obvious that polarity should have so little effect on such items as the beating of a drum.

This lack of perception of phase over the whole band can be confirmed by changing the relative phase of the loudspeaker output by means of two all-pass type networks. This can be done on an A-B basis using one loudspeaker and if the circuits are carefully constructed for both amplitude, phase and distortion, the effect is quite inaudible. This has recently been checked at the BBC Research Department using a modern high quality loudspeaker and various types of programme. These included a violin piano sonata, informal speech with mixed voices, light orchestra, choir and symphonic orchestra. On this stringent type of test it is essential to hold the amplitude response to very close limits and for the non-linearity distortion to be of a very low order if the comparison is not to be invalidated by such factors.

The effect on sound quality of relative phase changes over the whole audio band of 90°, 60° and 30° was also tested and in no case was any audible effect produced.

In all these experiments of relative phase shift, the absolute phase shift introduced is very much greater than the relative shift and varies smoothly with frequency as shown in Fig. 1. The change in phase between 30Hz and 10kHz is of the order of 500° yet the effect of this on sound quality is still inaudible. Note that this change does not even correspond to a simple time delay, the delay at the bass is roughly 6ms while that in the treble is 0.15ms.

The inaudibility of such phase changes has been confirmed by Bauer¹, yet the distortion produced by such a network on the waveform of a rectangular wave was clearly shown in his article. The need for a loudspeaker to be able to reproduce accurately a square wave² is therefore more than doubtful.

From these observations it is concluded that sound quality is not affected either by constant or by smoothly varying phase changes over the range normally met in loudspeakers. It is quite likely that such changes produced by

the use of very long horns would produce audible effects, but such devices are rare in practice.

In contrast, the effects of rapid local phase changes on sound quality must now be considered. Various workers, such as de Boer and Craig & Jeffress, have shown that audible effects can be produced when using artificial signals, by what are, in essence, rapid local phase changes. The conditions which are necessary to achieve this audibility are not clear, except that authors such as Goldstein³ have suggested that, for example, the difference between an amplitude modulated signal and a frequency modulated signal (which differ only in phase) is only audible within the critical bandwidth, at the corresponding carrier frequency.

On the other hand examination⁴ of the audibility of resonant peaks of various Qs and frequencies for minimum phase shift networks has shown that under certain conditions the audibility of a peak of given height actually decreases as the Q increases, that is as the rate of change of phase increases. This surprising result, since confirmed by Moulana⁷, was accompanied by evidence that under these particular circumstances the subjects were listening to the steady-state condition. On reversing the phase of the resonant channel relative to that of the straight through channel it was possible, by adjusting the level of the signal in the resonant circuit, to cancel out the coloration so that the effect of the resonance was inaudible. This cancellation can only occur for the steady state condition; the time response cannot so be cancelled. Under these conditions the effects of phase were obviously inaudible.

Attention has also been drawn⁶ to the

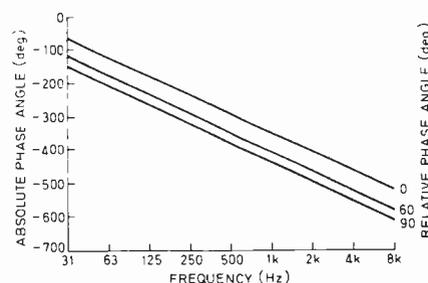


Fig. 1. Absolute phase-frequency response curve of all-pass networks used for phase shift experiments.

anomaly that under other conditions, which again cannot yet be specified, subjects arrive at precisely the opposite conclusion, namely that the audibility of a resonant peak of given height increases with increasing Q. Whether in this last-mentioned case it is the phase change or the amplitude-time response which is audible might be thought to be immaterial, as for these networks the two are obviously irrevocably tied together. On the other hand if a simple resonant element such as a tuning fork is struck, the audibility clearly falls with the amplitude and does not follow the constant phase changes.

It is also a matter of common observation that narrow interference crevasses are inaudible. However, these by their very nature must contain very sharp phase changes as well as the more obvious amplitude changes, yet they appear to have no effect on sound quality. One rather interesting example of this was tested at BBC Research Department by P. C. J. Hill in connection with another investigation. The amplitude-frequency response curve of the circuit used is shown in Fig. 2. For reasons connected with the original experiment the bandwidth was limited to 6 kHz, and the effect of this circuit was compared with that of an otherwise unadulterated programme restricted to the same bandwidth. Recordings of speech, piano music and dance band were used in the assessment; in the associated subjective grading of 1 to 5, one unit represented only "slightly worse than the standard." The ratings obtained were 0.6 for speech, 0.8 for piano and an improvement of 0.3 for the dance music! Obviously the overall effect of the irregularities due to the combined effects of phase and amplitude was very small indeed, even though the phase response must have been irregular.

Again, no one objects to listening in a live room, yet the effects on phase of the first reflections and of the eigentone structure must be devastating and vary rapidly with the position of the source or listener. The effects of even appreciable changes in head position are however inaudible.

If now we revert to the condition of lumped constants with high Qs, the question arises as to the limit on Q, or rate of phase change, which is inaudible. For example I have often found it necessary to damp cross-over networks of second and third order to remove audible coloration. However if adequate damping is used the cross-over frequencies are completely inaudible even though the users in the BBC have the advantage of direct comparison with the live programme. This condition appears to be all that is necessary subjectively even though the phase changes are considerable.

In this connection the BBC monitoring loudspeaker type LS5/5 (ref. 8) is recognised to possess a sound quality of the very highest order yet the phase

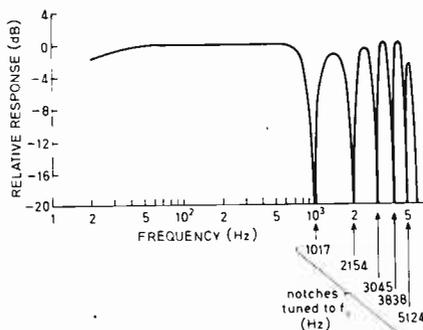


Fig. 2. Amplitude-frequency response curve of circuit used in Dr Hill's experiment.

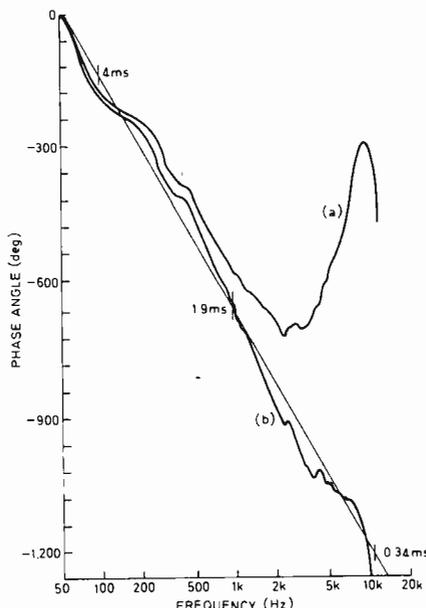


Fig. 3 (a) Phase-frequency response curve of monitoring loudspeaker type LS5/5 (b) Phase response plus 1/4ms time delay.

response, measured at 1m, is as shown in Fig. 3(a). The loudspeaker is a three-unit design with cross-over frequencies at 400Hz and 3kHz. The phase irregularity at the first frequency is small but that at the last is large, the high frequency unit being acoustically in front of the middle frequency unit, although mechanically the front surfaces of all three units are in the same plane. The major phase irregularity caused by this is totally inaudible and no complaints of the sound quality in this region are made.

The phase irregularity shown in curve 3(a) can be largely removed by the addition of a 1/4ms time delay applied to the whole loudspeaker. The results are shown in Fig. 3(b). The curve is now a rough approximation to a straight line, and this in turn was shown earlier to be inaudible. It is also well known that changing the listening distance by about 3in on the axis of a loudspeaker produces no audible change. This confirms the innocuous nature of curve (a). This experiment also makes nonsense of absolute phase angle curves, for the addition of a small time delay has completely changed the shape of the curve. If on the other hand time

delay itself were plotted such an addition would merely result in a small vertical shift; the axial time delay/frequency response curve is shown in Fig. 4. It is clear that this has an innocuous shape.

It seems therefore that the situation as far as the effect of phase on sound quality is concerned, is rather like that of the old lady passenger flying for the first time. Some time after take-off she looked out of the window and noticed that the wings were flapping up and down. Calling the steward she complained that the plane was unsafe and demanded that it should be stopped. The steward assured her that the plane was quite in order and proceeded to pull down the cabin blind, asking the lady if she could now feel any effects due to the wing movement. She could not and was quite happy. As regards the effects of phase on sound quality therefore until someone can demonstrate that they are audible on programme items as opposed to artificial signals, I shall proceed to pull down the blind and pretend that such a factor does not exist.

The second aspect of phase in relation to loudspeakers is connected with the formation of stereo images. Here our ignorance is even more marked than for sound quality as we do not know just what factors are necessary to determine image sharpness.

It would appear at first sight that if the two loudspeakers of a pair were identical in amplitude and phase response the image sharpness would not depend on how uniform with frequency either of the characteristics were. In practice the situation does not seem to be as simple as this. Pairs of differing types of loudspeaker even when matched for amplitude-frequency response do not all give the same sharpness of image even for a symmetrically placed listener. Thus in two types designed by the author the same bass units and high frequency units were used for the two unit system. One design employed the units in a vertical array but for the other design the tweeters were mounted concentrically in the centre of the bass unit on a perforated panel. This last-mentioned design is reckoned by the users to have appreciably better image forming properties than the in-line design even though the same units and similar cross-over networks are used. That the improvement is not due to the concentric arrangement is shown by the fact that a later design⁸ which uses three units in a vertical array gives a sharper image still. It is this last loudspeaker whose phase-frequency response is given in Fig. 3(a). Furthermore, another commercial concentric design gives the worst image sharpness yet known.

A further experiment has been carried out inserting one of the all-pass phase delay networks whose response is shown in Fig. 1 in series with each of the type LS5/5 loudspeakers and determining the effect both on the sharpness of a

central image, and, in view of the non-constant time delay, on possible chromatic aberration effects when using male speech as the input signal. No effect was discernible, even on an A-B test.

From this result it is not clear how the use of a circuit to make the phase-frequency response linear would help to improve the image width.

In this connection it is worthwhile recalling data published some years ago⁹, which show that for a central image the image width from a pair of loudspeakers is actually narrower under live conditions than under free-field conditions. The only obvious explanation of this is that the reflection from the floor in the live room assists in the detection of the direction of the apparent source. This has been confirmed recently during recent tests in a free-field room.

Under these last-mentioned conditions subjects complained that the stereophonic image was more diffuse than that to which they were accustomed using the same loudspeakers in a normal live listening room. At my suggestion, a floor of 6mm hardboard was put down in the free-field room, and all the subjects were then content. The acoustic axis of the loudspeakers was about 1 metre from the floor and if the distance of the observer from the loudspeaker is taken as 2 metres then under the simplifying assumption of no phase change on reflection from the floor there will be an interference crevasse at the listener's ear at 115Hz and at intervals of 230Hz thereafter. The phase irregularities corresponding to this kind of interference must be very large, but far from destroying the stereo image it is seen to actually assist in improving the sharpness.

This does however raise the interesting question as to whether the loudspeaker amplitude response at, say, -45° in the vertical plane (which is usually ignored) is important in this regard.

Even if it were eventually found that phase had a second-order effect on image formation, it is difficult to see how it can be effective above about 2kHz. It is known from studies of the stereo effect that the relative phase between the stereo signals is important up to about this frequency, but above this the ear appears to use the envelope of the signal rather than the absolute phase. It is therefore once again extremely difficult to imagine that producing a phase-linear loudspeaker will assist in any way in improving the production of a stereo image above 2kHz.

A further piece of evidence is coming to light in experiments I have started to measure the image width produced by various designs of loudspeaker. This work has only just commenced but preliminary results indicate that when using male speech as the source material the image width for wide range material is narrower than that obtained for any

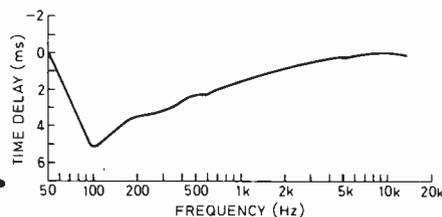


Fig. 4. Axial time delay/frequency response corresponding to Fig. 3(a).

one octave band of the same material, indicating that the brain is using some form of summation of the information received.

To conclude, any effect either of wide band or narrow band variations of phase on sound quality is at most of a second order, and is certainly minute compared with first-order effects such as coloration, and compared with these can be ignored by loudspeaker designers and users even though not by psycho-acousticians. Until, therefore, someone can demonstrate that phase effects of this nature affect the sound quality of loudspeakers on programme, and not just on highly artificial signals, the appropriate treatment appears to be to pull down the blind and pretend that phase, in this sense, does not exist.

From the aspect of stereo image formation we must admit our ignorance as to all the factors involved, but in view of the data presented earlier, I will continue to listen to the siren voices of the manufacturers, but again until some audible effect can be demonstrated I will remain absolutely agog — with indifference!

Thanks to the Director of Engineering, BBC for permission to publish.

References

1. Bauer, B.B. Audibility of phase distortion. *Wireless World* vol. 80, 1974. p.27/8.
2. Baekgaard, E. Loudspeakers, the missing link. 50th AES Convention, London 1975, paper 6.
3. Wall, P. K. Active and passive loudspeaker cross-over networks without transient distortion. 50th AES Convention, London 1975, paper 16.
4. de Boer, E. Observations on inharmonic signals. *JASA*, vol. 29, 1975. p.780. 53rd Meeting ASA. Paper 01.
5. Craig, J. H. and Jeffress. Effect of phase on a two component tone. *JASA*, vol. 34, 1962. p.1752, also vol. 31, 1959. p.1584.
6. Goldstein, J.L. Auditory spectral filtering and monaural phase perception. *JASA*, vol. 41, 1967. p.458.
7. Harwood, H.D. Audibility of an irregularity in the frequency response of a transmission channel. To be published.
8. Harwood, H.D. Some of the factors affecting sound quality in loudspeakers. 50th AES Convention, London 1975, invited paper.
9. Moulana, K. Ph.D. Thesis University of Surrey 1975.
10. Harwood, H.D. New BBC monitoring loudspeaker, *Wireless World*, vol. 74, 1968. pp.2-5, 74-8, 114-7.
11. Harwood, H.D. Stereophonic image sharpness, *Wireless World*, vol. 74, 1968, pp.207-11.

Books Received

Foundations of Wireless and Electronics, 9th edition by M. G. Scroggie. The first edition was published in 1936 and since then, nearly 250,000 copies have been sold, which in itself is a recommendation for the current ninth edition. Like previous editions, the book covers basic theory, starting with elementary "first principles" where no previous technical knowledge is assumed. Subsequent chapters discuss a.c. theory, valve and transistor theory, equivalent circuits and oscillators. The book then covers radio senders, transmission lines, radiation and aerials, and detection.

Final chapters deal with low and high frequency amplification, selectivity and tuning, the superheterodyne receiver, cathode-ray tubes, electronic waveform generators and switches, computers, and power supplies. As with all of the author's work, the text is clear, concise and very readable with many circuit and pictorial diagrams where necessary. Price £3.75. Pp.521. Newnes-Butterworth, Borough Green, Sevenoaks, Kent TN15 8PH.

The Autumn 75 series of D.A.T.A. books is now available which covers relays, microwave tubes, memories, linear and digital integrated circuits, current/discontinued diodes and transistors, power semiconductors, thyristors and, a new addition to the range, opto electronics. Most of the books have two editions a year and contain a section with suppliers' names and addresses. The books are also provided with a cross index which speeds up the location of a device, and devices with similar characteristics are listed together. London Information (Rowse Muir) Ltd, Index House, Ascot, Berkshire SL5 7EU.

We have recently been able to examine the **Bugbook system** of teaching the use of digital integrated circuits. Bugbooks I and II are intended to lead a student from a state of complete innocence, via an extremely methodical procedure, to an understanding of fairly complex t.t.l. functions (registers, counters, memories, etc.). Each section consists of an introduction to the subject area, a statement of objectives, definitions and symbols when necessary, discussion of the subject and experiments. The section finishes with a review of the work. Teachers' course books are available.

Experiments are carried out with the aid of a universal socket board and a selection of small printed-board assemblies (clocks, indicators, power units, etc) which plug into it, a rather neat idea being the application of pin-identifying stickers to the integrated-circuit packages (bugs).

Books and hardware are expensive. The two books cost £12.82 and a typical accessory board, consisting of a p.c.b. about 32 x 20mm, two resistors and an l.e.d., two lengths of wire and two croc. clips, costs £7.36. The course material is exhaustive (but not exhausting, if a case quoted in the foreword is typical) and, with reservations over the price, can be recommended for examination. The books, produced by E & L Instruments, Derby, Connecticut, can be obtained from Hepworth Electronics, Kidderminster, Worcs.

Electronic systems — 1

An introduction to the nature of the Universe (or an atom)

by W. E. Anderton
Assistant Editor, *Wireless World*

This article heralds the beginning of a series of tutorial articles on the subject of electronic systems, their theory, applications and consequences. The content will be based on a proposed Advanced Level course for schools which has been undergoing a trial at nine schools for a period of three years. This course is the culmination of six years' preparation by Professor G. B. B. Chaplin of the University of Essex, who, with the assistance of his colleagues, has detailed most of the proposed syllabus. *Wireless World* will use this course as a basis for the forthcoming series. We shall, however, diversify and expand its content where we feel necessary, with the hope that a contribution will be made to what we believe is an excellent cause.

The subject matter of "Electronic systems" is split into (a) communication systems, (b) computer systems and (c) feedback systems. The theory is applicable to almost any subject and helps the student to appreciate that apparently unrelated phenomena are often embodiments of fundamental principles with universal application. The articles will also aim towards a more rigorous and academic knowledge of these fundamental principles through study of their application to electronics.

Since the human body itself is made up of many systems and man throughout his life is surrounded by systems, an understanding of them (whether they are biological, sociological, environmental, mechanical or electronic) is necessary so that science can benefit our society and enable it to progress. All systems have certain fundamental principles in common, and it so happens that they can be described particularly easily and effectively in terms of electronic systems. Electronic experiments to illustrate these principles can be set up quickly and cheaply and their flexibility encourages initiative on the part of the pupil.


Each section of the series is to be introduced by relating man and his needs, including his relevant physical and mental characteristics, to the electronic system under discussion. The content will not emphasize technology,



but will rather seek to establish in the reader a knowledge and understanding of fundamental principles such as feedback, stability, storage and retrieval of information, signals and noise, information content and decision making. Some current technologies will also be discussed as applications of these basic principles.

The word "system" seems vague at first as it can apparently be applied to

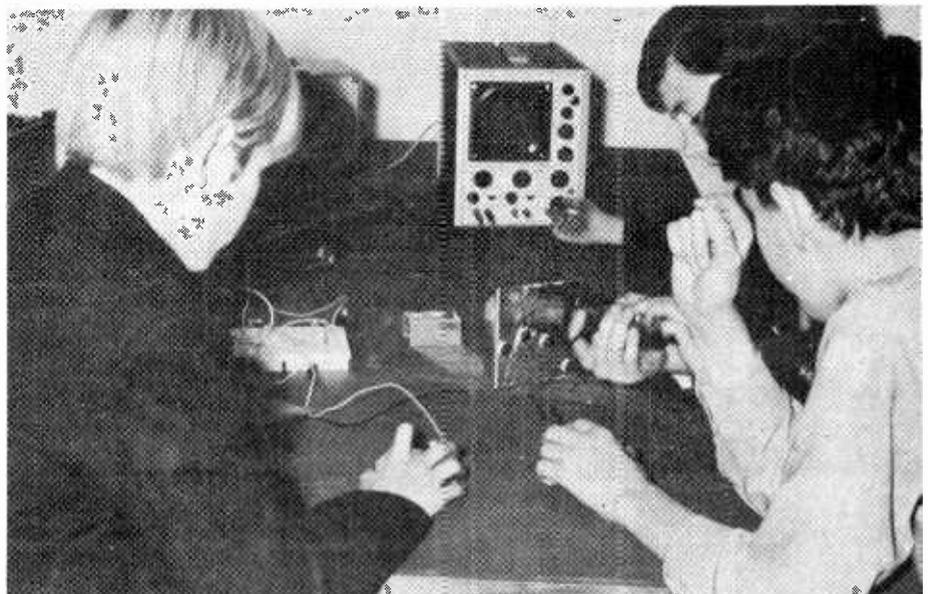Sixth form students working on one of the A-level electronic systems course experiments.



any subject under the sun without explaining anything useful about it. But this is not at all true as a definite theory of systems, how they work and how they can be usefully manipulated has been evolved. This theory can be applied to politics, chemistry, biology, sociology, evolution and so on ad infinitum, the system being defined to encompass just what parameters may be involved with a particular problem. The largest system imaginable is the Universe and one of the smallest is the atom, but no matter how large or small, the same theory can be applied. Our concern will naturally be with electronic systems theory and with the consequences and benefits that can be achieved.

First, the starting point must be a definition. According to the Concise Oxford Dictionary, a system is "a complex whole, a set of connected things or parts, an organized body of material or immaterial things."

The first point to note is that a system is a complete entity and can thus be represented pictorially by a box (Fig. 1) within which everything is subject to the laws of how a system operates. To determine what these laws are it is necessary to divide the system into its basic component parts, and these can be

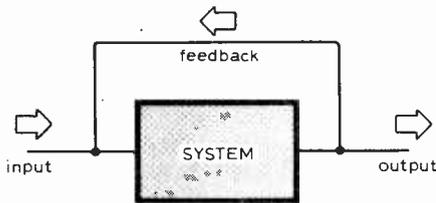


Fig. 1. A system can be represented as a single box in its most simplified form.

obtained simply by examining the dictionary definition. A system is complex and therefore needs to be capable of **processing** or working out its complexities so that they are ordered and not disordered. It is a set of connected things and therefore needs **communication** to make the connections. Finally, it is organized and therefore needs **control** to achieve organization.

One more factor must be added to the list of processing, communication and control and this is the application of feedback, which is involved with all three. Here information is fed back from output to input so that a close watch can be kept on the way things are going within the system. If they are going astray then the information fed back to tell this to whoever or whatever is in control can be used to adjust the system's operation and straighten out any problems that have arisen. More rigorously, feedback is the process whereby a measured portion of information is taken from the output of a system or its component parts and is fed back to the input where it is added in such a way as to increase the input (positive feedback) or decrease the input (negative feedback).

As an example of how a system can be split into its relevant component parts for analysis, consider Fig. 2. This is a block diagram of the system representing a town's community, with the problem of controlling the numbers of its population to a comfortable level. The elements of feedback, control, communication and processing can be identified as follows:

At the "input" to the town there are births and immigrants who swell the population and at its output there are deaths and emigrants who diminish it. The problem is to maintain a balance

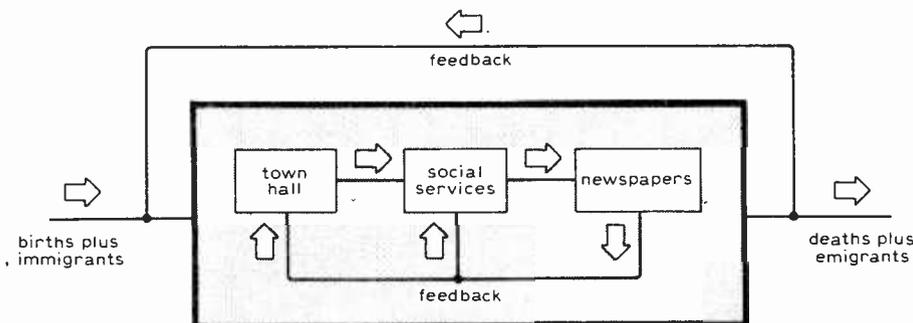


Fig. 2. Simple analysis of a social system. There would be many more factors to take into account which have not been considered here.

Suggested reading

Two books which will develop a greater understanding of the interdisciplinary nature of systems are:

Wiener, N. "The Human use of Human Beings," Sphere Books, London.
 Wiener, N. "Cybernetics: or Control and Communication in the Animal and the Machine," The M.I.T. Press, Cambridge, Massachusetts.

The following topics will be covered in subsequent issues:

Introduction to communication systems
 Modulation
 Transmission
 Reception and demodulation
 Audio perception and bandwidth
 Audio systems and transducers

Audio systems and amplifiers
 Measurement in audio systems
 Visual perception
 Visual systems — scanning and detection
 Television systems

These describe the "communications" part of the syllabus and will be followed by related experiments:

- Frequency response of audio systems
- Amplitude demodulation
- Power in electronic circuits
- Television waveforms

Topics continuing from this will be under the main headings of feedback and control systems, computer systems and basic electronics.

between the actual population and the facilities that are provided in the town such as housing, hospitals, shops and parks.

Information is fed from output to input so that all relevant facts can be supplied to the town hall where they are processed. The results are communicated to the town's services such as police, hospitals, etc., who are then able to control to maximum efficiency of services which they offer. Communication between the town hall, the social services and the town's population is effected by means of newspapers and radio broadcasts. This briefly shows how a social system is built of the prime factors. It will be the aim of the following series of articles to examine each in turn in terms of electronic systems.

Fundamental to the analysis of a system is the recognition of whether it is deterministic (entirely predictable according to formal laws) or stochastic (not entirely deterministic, but subject to probability). This means recognizing the fact that we may be able to say from one analysis that "a system definitely does this" and from another "a system definitely does this, but . . ." For practical purposes, electronics is exact

enough to forget about the "buts" and this is why the application of systems theory to electronics is such a powerful and important tool.

Sixty Years Ago

Wireless World has always been conscious of the need to make instructional material as interesting as possible — there is never anything wrong with a little humour in even the weightiest piece of reasoning. But we have never approached the level of popularization advocated by Mr Stephen Leacock, as reported in our issue of January 1916. One wonders what he would have made of avalanche diodes and buffer stages.

"A matter under discussion at the moment is the actual value to the student of a mathematical training, and whether it is necessary to go deeply into the subject in order to become a competent electrical engineer. Many have complained that the ordinary methods of imparting mathematical knowledge are far from interesting, and the famous Canadian humourist, Mr Stephen Leacock, in his new book Moonbeams from a Larger Lunacy, particularly emphasises this point of view. He writes as follows:

"Here, for example, you have Euclid writing in a perfectly prosaic way all in small type such an item as the following:

"A perpendicular is let fall on a line BC so as to bisect it at the point C, etc., etc."

"... just as if it were the most ordinary occurrence in the world. Every newspaper man will see at once that it ought to be:

**"AWFUL CATASTROPHE.
 PERPENDICULAR FALLS
 HEADLONG ON A GIVEN
 POINT.**

The Line at C said to be
 Completely Bisected.
 President of the Line makes
 Statement."

News of the Month

Atomic heart power

A nuclear-powered pacemaker that could bring a new lease of life to thousands of people suffering from certain types of heart trouble is to be made at the Harwell Atomic Energy research Establishment. Conventional pacemakers with chemical batteries have to be replaced surgically about every three years. Trials indicate that the implanted lifetime of the Harwell units could reach 10 or even 20 years.

The nuclear battery that powers the pacemaker consists of a heat-producing nuclear source, containing less than a fifth of a gramme of plutonium oxide, and a miniature thermocouple, all in a strong metal housing. The assembly is encapsulated in an epoxy resin known to have lasting compatibility with living tissue. Internationally agreed safety standards require stringent tests on the batteries. These ensure that there is no radiation hazard and that they will withstand the most severe accident — including cremation. The isotope plutonium 238 has been chosen for the heat source because its power output falls by only one per cent per year, and its radiation, mainly alpha particles, requires a minimum of shielding for implantation. This isotope is specially prepared for the pacemaker batteries and is markedly different from the very long-lived plutonium isotopes associated with nuclear fuel.

Braille information service

A pilot scheme to produce a monthly braille information service for blind computer programmers and analysts has been started by INSPEC, the information services division of the Institution of Electrical Engineers, and the Warwick Research Unit for the Blind. Each month, INSPEC supplies the Warwick Research Unit with a computer-readable magnetic tape containing abstracts of recently published

articles from computer science journals. The Research Unit uses an RXDS Sigma 5 computer system with a braille embosser on-line to produce selective listings from the tapes, which are converted into contracted braille by an automatic translation programme. The pilot service has now been running for several months with a limited group of users. Both the INSPEC source tapes and the service operated by the Warwick Research Unit are being made available free to the blind user or his employers. Computing has been able to offer particularly good opportunities for the employment of blind staff on equal terms with their sighted colleagues, and there is now a significant group of blind computer programmers and analysts in the UK. It's in the hope of finding a solution to their information needs that the INSPEC/Warwick project has been started.

London honours Blumlein


The Greater London Council is to erect a commemorative plaque on the wall of the house where Alan Dower Blumlein was living at the time he met his death in a Halifax bomber crash in 1942. In bestowing this honour, Blumlein's native city of London is placing him among the immortals in recognition of his many achievements in science and technology. Blumlein's inventions

included modern gramophone stereo recording techniques, the closely-coupled inductive ratio-arm bridge, the cathode follower circuit and the so-called "Miller" integrator. The BBC adopted the television broadcasting specification on which Blumlein worked in the 1930's, in preference to Baird's, when they opted for the 405-line, 50 frames/s interlaced system still in use today. During his short working life, Blumlein was awarded an average of one patent each six working weeks, a record not yet equalled. The official unveiling of the plaque, which is to be placed on a house in Ealing, West London, will be in 1977 on June 7, the anniversary date of Blumlein's death near Ross-on-Wye, Herefordshire.

Microprocessor comes clean

A new range of dedicated microprocessors just introduced is suitable for all types of washing machines and offers the seven main wash programmes recommended by the International Standards Organization's system of fabric care labelling, together with additional pre-wash, rinse and spin, biological and fast wash programmes. Another feature of the circuit is that it allows for the automatic release of a fabric conditioner during the final rinse. It replaces the conventional electromechanical timer and various safety

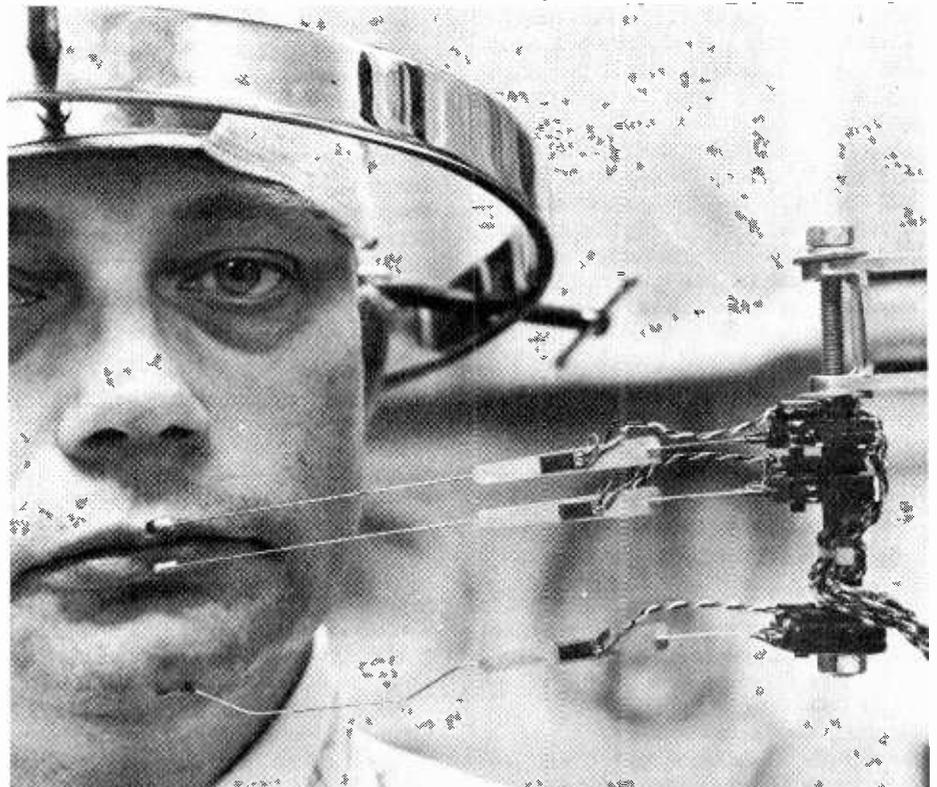Monitoring speech. Strain gauges mounted on flexible metal sensors are used to obtain information on lip and jaw movements made while speaking. Honeywell tape and oscillograph instrumentation records the facial movements for analysis in Seattle, USA, at the University of Washington's Speech Physiology Laboratory.



features are incorporated, including door interlocks, no machine action or heating without water present, and a "child-proof" programme lock-out which, after a programme has been selected, inhibits change of programmes in mid-operation without first resetting.

The heart of the processor, the ITT 7150, is contained within a 28-pin d.i.l. package and consists of two r.o.ms which perform the control functions. Up to ten machine functions can be controlled by means of a maximum of 20 different programme steps which provide the various combinations of fill, wash, heat, pump and spin. The package has been designed for m.o.s. applications and is capable of withstanding adverse conditions, e.g. 85°C at 85% relative humidity under reverse bias.

Head-up for Harrier

The electronics content of military aircraft continues to grow. A system incorporating an integrated head-up display and weapon aiming computer, with cursive and raster outputs and designed specifically for carrier aircraft, is to be supplied for the Sea Harrier. The display system will consist of three units; a computer which generates a very wide range of air-to-air and air-to-surface weapon aiming and display generation functions; a pilot's display which presents the pilot with all the appropriate flight data and weapon aiming symbology superimposed on his view of the outside world; a pilot's control panel for mode selection and display control. The computer unit will contain: a high-speed digital processor having an associated store of 20,000 words of which 16,000 words will be fully reprogrammable core store; hybrid analogue and digital input and output peripherals, to interface with other aircraft systems and sensors; and a symbol generator to provide deflection wave forms to the pilot's display unit. There will also be a video synthesizer section which, under control of the central processor, will give symbology outputs in raster form for use with raster type displays. The inclusion of a core store will give considerable flexibility during development and will greatly simplify changes to the role of the aircraft during service. Smiths Industries is to supply the display system.

Single-tube colour TV camera

Work is continuing on the single-tube television camera developed by Siemens and demonstrated at the Montreux television symposium. The "Interplex" camera, as it is called, uses a new type of dichroic strip filter. In contrast to a normal three-tube camera,



Market research has told us that the average age of our readership is getting lower. Is Richard Tucker of Lutterworth in Leicestershire the youngest reader at 2¼?

the colour analyser used to break down the image arriving from the lens into red, green and blue components is integrated within the complex pick-up tube itself. This has made it possible to reduce the size of the camera by dispensing with the accessories for colour registration.

Signal information supplied by the television camera tube in the 4.43MHz subcarrier band is converted into standard PAL signals in a decoder using comb filter systems and other circuitry. Black-and-white and colour information is separated by the comb filters, the spectral lines of the video signals being broken down into chrominance and luminance information. The silicon tube is said to achieve a resolution of approximately 6MHz in red-green-blue operation. The signal produced by the camera is compatible with black-and-white sets, and can be recorded without decoding on conventional video tape recorders with colour capability, preserving a claimed 6MHz resolution.

Traffic information service

The BBC is still working on its m.f. system for broadcasting traffic information bulletins to road users (see May 1973 issue p. 239). They claim it is more economical than other schemes and will not involve depriving car radio listeners of their normal programmes.

A network of about 80 low-power medium wave transmitters would be set up in the pattern of a grid covering the whole country. They would all operate on one frequency just within the tuning range of a medium-wave receiver. Each station would only transmit for perhaps

half a minute in every eight, and neighbouring stations would always transmit at different times from one another. At regular intervals, therefore, every motorist could be provided with a bulletin containing information about the area through which he was travelling. The motoring receiver could either be separate from the normal car radio or cassette-player, or, for drivers who wished, special receivers could be fitted to either machine so that it could be played in the normal way and would be interrupted by the strongest local traffic signal.

This system is rather similar in principle to a radio paging scheme for national coverage, using one frequency and a cellular transmitter layout, developed by the Martin Marietta Corporation in the USA.

The BBC say they would be willing to develop and operate the service in collaboration with a motoring organization. Cost of establishing the transmitters would be about £2½ million. The BBC thinks that a project of this nature should not be a charge on the licence fee — the finance would have to come from some other source.

There is a well established system of traffic information broadcasting operating in West Germany, called Autofahrer-Rundfunk-Information (see May 1973 and April 1974 issues).

Rogers packs up

It's sad to record the demise of yet another small British company making high quality products. Rogers Developments (Electronics) Ltd, manufacturers of audio equipment including amplifiers, tuners and monitor loudspeakers, ceased operating on October 31 1975. The company was formed by J. D. Rogers in 1947 and came to considerable prominence during the hi-fi boom. Following changes in the firm's management on June 17, 1975, when the founder was made chairman and technical director, Mr Rogers "was compelled to resign" (as he writes to us) on August 27. At the time of writing we understand the company will be put into liquidation. Farewell to a much respected and friendly firm.

Licence for Teletext?

In a recent memorandum to the Annan Committee on the future of broadcasting the BBC says it would expect its CEEFAX part of the Teletext service to attract an incremental licence fee in much the same way as colour television does.

Viewdata, the Post Office's television screen information service using the domestic telephone line, will of course be charged for on a subscriber basis (November issue, p.532).

Wireless World Teletext decoder

3 — Line and clock dividers

by J. F. Daniels

Last month we looked briefly at the overall operation of the decoder by considering a simplified block schematic diagram. I also mentioned that the heart of the circuit lay in the design and operation of the clock and line divider circuits. This month we shall look in greater detail at the operation of these two circuit blocks, as these together provide most of the waveforms used elsewhere in the decoder circuitry. We shall begin by looking at the operation of the line dividers.


The main function of this part of the circuit is to provide row-address information for the store during the operation of writing data into the store and when reading it; i.e., when the data is


displayed as characters on the screen. Other outputs are also obtained from this part of the circuit, namely separated field syncs, line address information for the character generator read-only memory, the vertical component of the display blanking waveform and a field blanking waveform which goes to "1" during the period from lines 11 to 21 and 324 to 334. This latter waveform is used extensively elsewhere in the decoder to

discriminate between data acquisition and data display: i.e., data is only "looked for" during the periods just mentioned. If all 625 lines were examined for data, false framing codes would be detected at random during the video information, and cause lines of "rubbish" to be read into the store. It would of course be possible to look for data only on lines 17-18 and 330-331, but it is possible that broadcasters may change the positions, or increase the number, of data lines transmitted, and so the above method was adopted to avoid later modification in this respect.

It may appear, from a quick glance at the circuits, that the i.c.s are numbered somewhat erratically, but this is

Fig. 1. The line divider circuitry. IC₃ is a 74121 monostable, IC₅ and IC₁₄ are 7490 decimal counters, IC₁₁ is a 7474 dual D-type edge-triggered flip-flop and IC₂₀ is a 74177/74197 binary counter.

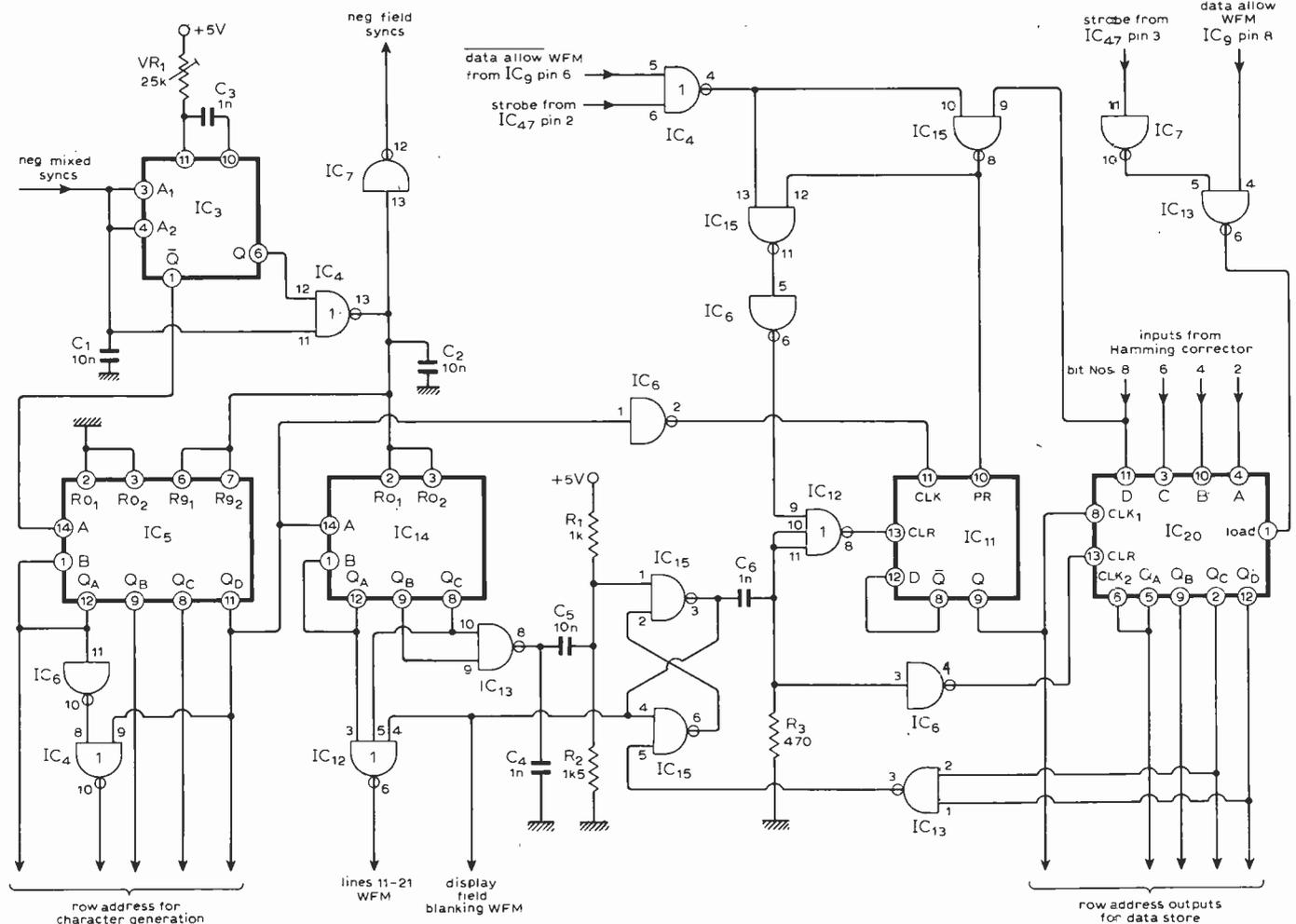

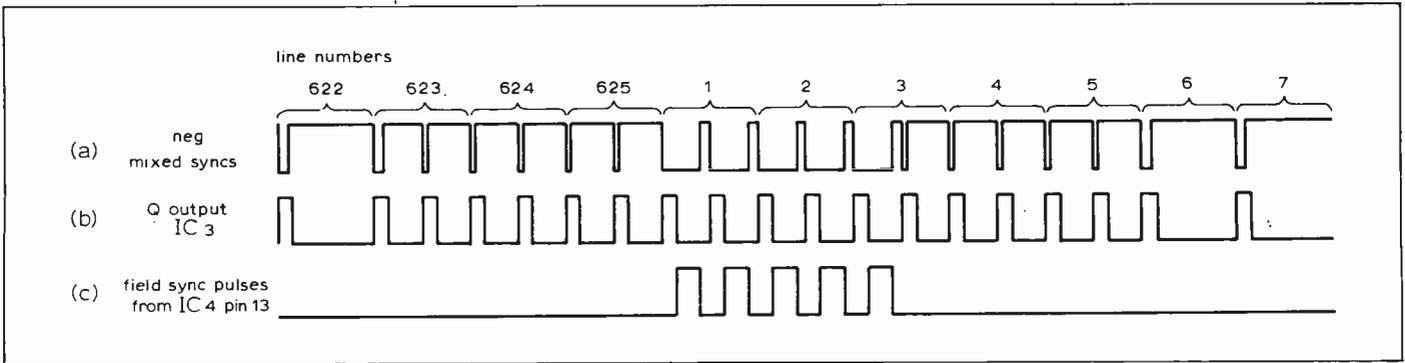

because they are designated according to their position on the p.c. boards - IC₁₋₄₀ being on the uppermost board and IC₄₁₋₈₀ on the lower circuit. During circuit descriptions, multigate i.c.s will be referred to by their IC number, and output pin number. For example (7, 12.) indicates the inverter gate for field sync pulses in Fig. 1.

Line dividers

Negative-going mixed syncs from the analogue board trigger monostable 3, which is adjustable by means of a preset potentiometer. Elsewhere in the circuit the variable width of the output pulse is used to shift the display horizontally, but for this part of the circuit the output pulse width is not critical, so long as the pulse is wider than the input sync pulse. By gating together the input and output waveforms of this i.c. in a NOR gate (4,13), the broad pulses during the field blanking interval are separated from the mixed sync waveform. Capacitor C₂

Fig. 2. Waveforms from Fig. 1, showing the detection of broad pulses.

removes spikes which are caused by the delay through IC₃. The method by which the broad-pulse separation is achieved is more clearly shown by Fig. 2. waveforms (a), (b) and (c).


The broad pulses are used to reset the first part of the line-divider chain, which consists of two i.c.s forming a divide-by-80 circuit. The first i.c., a divide-by-10 counter, provides line-address information for the character generator r.o.m. and sets the height of each "character box" at 10 lines per field.

In the "upper case only" version of the decoder, only seven of these lines

are used for the display of alphanumeric characters, and gates (6,10) and (4,10) serve to inhibit character generation during three of the ten lines. These gates are not required when the upper and lower case version is built, as the blanking of unused character lines is achieved in a later part of the decoder.

The operation of the rest of the circuit is best understood by referring to Fig.3, which shows some of the more important waveforms through the circuit. The divide-by-8 counter IC₁₄ is fed with one pulse every 10 lines from IC₅ and its outputs Q_B and Q_C are gated in (13, 8) to provide a start pulse for the display period at line 51 (also 364). C₄ removes any spikes caused by timing differences between the Q_B and Q_C outputs of the counter, and C₅, R₁ and R₂ shorten the pulse into a narrow negative spike to set the vertical display-blanking flip-flop, formed from gates (15, 3) and (15, 6). The positive transition at the output of gate (15, 3) is coupled via C₆ and R₃ into gates (12, 8) and (6, 4), which has the

Fig. 3. Waveforms in the circuit of Fig. 1.

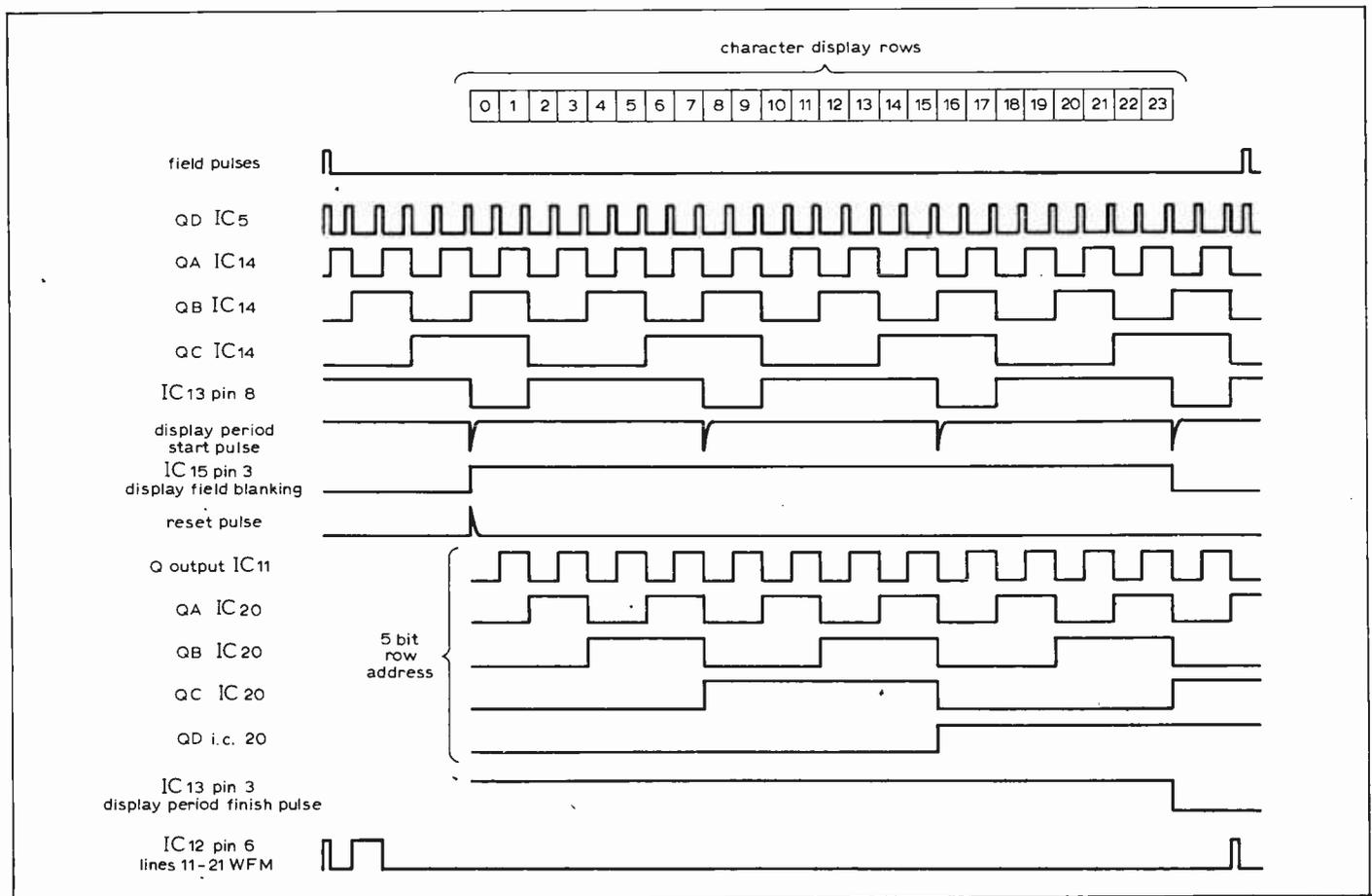

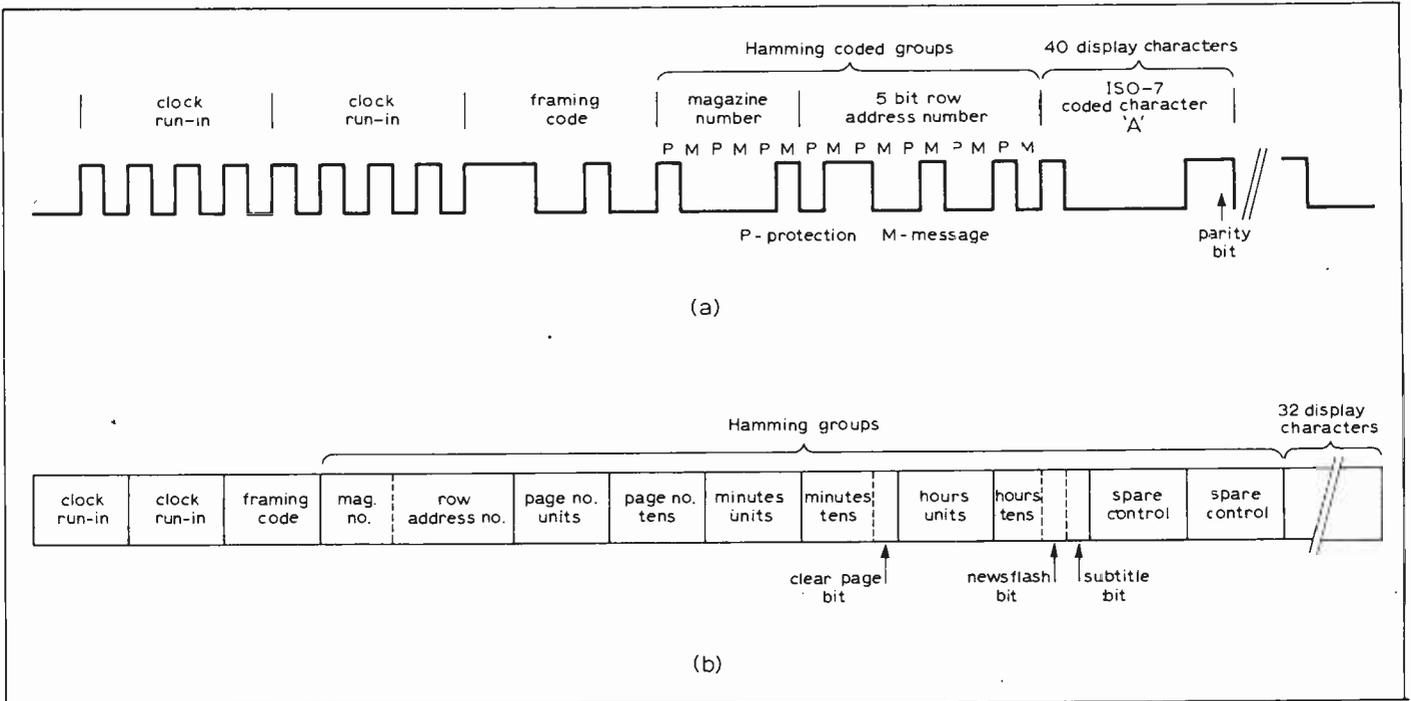


Fig. 4. Layouts of typical rows of data bits. A display row (row 5 of magazine 1) is shown at (a) and at (b) is a page-header row.

effect of setting the outputs of the 5-bit counter, formed from ICs 11 and 20, to zero. From this point onwards, the 5-bit counter counts through the character-display rows until the counter reaches 24 (the end of the page display). This point is detected by gate (13, 3) and its output is used to reset the vertical display-blanking flip-flop.

During lines containing data the 5-bit counter is preset to the correct row number, which is available in binary form at the output of the Hamming corrector during the control and row address groups, at the start of each data line.

The time at which this data is entered into the presettable counter is controlled by gates (4, 4) and (13, 6). The least significant bit of the row address arrives first, and a strobe pulse from the clock divider circuits (to be described later in this article) set IC₁₁ at the appropriate time. The next data group to arrive contains the remaining four bits of row address information and this is written into IC₂₀, again at a time determined by a strobe pulse from the clock divider circuits. The other inputs to gates (4, 4) and (13, 6) are waveforms which only allow the strobe pulses to set the counters during lines which have been confirmed as containing valid information. These waveforms are used in a number of places in the decoder and we shall call them data allow (DA), for a waveform going to "1" when a framing code is detected and returning to "0" at the end of that line and \overline{DA} for its inverse.

A 3-input NOR gate (12, 6), provides the field blanking waveforms which goes to "1" during lines 11 - 21 (324 - 334), by gating together the Q_A and Q_C outputs of IC₁₄ together with the vertical display-blanking waveform. It can be seen from the waveform diagram in Fig.3. that this waveform also goes to

"1" during the equalizing and broad pulses. This is of little consequence, however, as no video is present on these lines so that no false framing codes could be detected here.

Before continuing with a description of the clock divider circuits, it would be as well to consider in greater detail how each of the data rows is made up.

Data row format

Display row. The data bits are transmitted in groups of eight, and each line of data contains 45 of these groups, or bytes. The first five groups have the same function on all rows and a typical row is shown in Fig. 4(a). The following 40 groups consist of ISO-7 coded characters, the eighth bit in each group being used as an odd parity bit. The magazine number and row address information are coded in a different manner from the display data, being more heavily protected in a form of Hamming coded. Only four useful bits of data can be extracted from each of these eight-bit groups, but a single error in the group can be corrected and an even number of errors i.e., 2, 4 or 6 bits in error, can be detected.

Page header row. The page-header row (row zero) contains eight more of these Hamming protected groups following the row address number, and only 32 groups of ISO-7 coded data for display, as shown in Fig. 4(b). The two groups immediately following the row address number contain the page number units and tens respectively and these together with the three bits allocated to

the magazine number, enable any combination of page numbers between 100 and 899 to be selected.

The next four groups contain information indicating the time of day. The first group contains four bits of "minutes units" information and the second, three bits for the minutes tens. The spare bit in this second group is used as a "clear page" control, which goes to "1" whenever the following page contains new information and the old page must be erased from the store. The next group contains a 4-bit "hours units" message and the fourth group contains a 2-bit "hours tens" indication. There are two unused bits in this group, the first being used to indicate a newsflash page, and the second a subtitle page.

Clock dividers

There are two more groups of Hamming-protected data before the page header display starts, and these will eventually contain more control information.

The clock-divider circuit block provides a large number of pulses and waveforms for use elsewhere in the decoder, as follows: a display line-blanking waveform which goes to "1" during the 40-character-wide display period; the "data allow" waveform which goes "1" on detection of a framing code and returns to zero 42 bytes later; 6-bit column-address for addressing the store, which is used when writing data into the store, and when reading from display; strobe pulses which discriminate between the Hamming-coded words in normal rows and in the page header row and finally, groups of pulses used elsewhere for the formation of the vertical elements of the alphanumeric characters.

Figure 5 shows the clock-divider circuit diagram, and Fig. 6 the associated waveform diagrams.

done by the Q output of monostable 3. This reset is combined with the "write" mode reset by gate (18,11).

The first of the clock-divider i.cs feeds a binary-to-decimal decoder (IC₄₂) of which only eight of the ten outputs are used. Each output is a negative-going pulse, which occurs at every eighth clock pulse and is used to time the vertical components of the characters. Each character box is eight clock pulses wide, and for the formation of alphanumeric characters, five of these eight-clock-pulse intervals are used, the other three forming the space between characters.

Experiments were carried out with prototype decoders to reduce the character boxes to six pulses wide, with only one pulse space between characters. However, the extra circuit complexity was not thought to be worthwhile, as the display seemed as good with a character-to-space ratio of 5:3 as with 5:1. Graphic characters, however, fill the complete character box, in both the vertical and horizontal directions.

Address generator. This is common to "read" and "write" modes, i.cs 11 and 19, together with the inverted Q_D output of IC₁, providing the 6-bit address for the store, obtaining reset by the output of the line blanking flip-flop formed from (18,3) and (18,6). This flip-flop is set by output 3 of decoder 47 and reset at the end of the line, 40-character boxes later in the display mode, or 40 bytes of data later during the write mode. This same reset pulse is also used to return the data allow waveform to "0". The data allow waveform may also be reset to zero by another input to gate (9,6), taken from the Hamming corrector circuit, which gives a negative-going pulse if an even error is detected during the row address group and inhibits the writing of any data which may occur on such a row. During the read mode of operation the clock dividers and column-address dividers are both reset by the Q output of monostable 3, and by adjusting the width of this pulse, the display can be shifted horizontally to the centre of the TV screen. Also in the read mode, the clock input to the dividers is switched to the output of an adjustable frequency oscillator, to enable the overall width of the display to be adjusted.

This concludes the description of the divider circuits. In the next article we shall look at the operation of the serial-to-parallel converter, framing-code detector, data latches, and data store.

The Teletext decoder will also be usable with Viewdata (November issue, p.532) when this Post Office service becomes available. Later in the year we shall be publishing details of the Viewdata system and how it is compatible with Teletext.

New medium- and long-wave broadcasting plan

Better long-wave coverage of the UK and better reception of Radio London are two of the few benefits for Britain to be expected from the 1975 Geneva Plan for l.f./m.f. broadcasting just completed under the auspices of the International Telecommunication Union. Due to take effect in three years' time on November 23, 1978, the Plan covers frequency assignments in the 120 m.f. channels available for broadcasting in ITU Regions 1 and 3 (which means all the world except the Americas — see map in August 1974 issue, p.266) and in the 15 l.f. channels available at present for Region 1 only. It supersedes the Copenhagen Plan of 1948 — which was for the European broadcasting area only — and is to last for eleven years. The Plan is in fact a thick book listing stations, frequencies, transmitter powers etc., and is an "Annex" to the "Final Acts of the Regional Administrative l.f./m.f. Broadcasting Conferences (Region 1 and 3)", part of which took place at Geneva in October-November 1974 (Dec. 1974 issue, p.481; Jan. 1975 issue, p.10) and part in October-November 1975. J. G. Spencer's article "The future of medium- and long-wave broadcasting" in the August 1974 issue explained the technical problems involved in the re-planning.

Britain's improved l.f. coverage will come partly from an additional assignment for 200kHz, 50 kW transmitter at Burghead, Scotland, to be synchronized with the existing 200kHz station at Droitwich. This will give improved long-wave reception in the north of Scotland. For the central, heavily populated area of Scotland around Glasgow and Edinburgh there is a further l.f. assignment, for a 227kHz transmitter at Westerglen, also with a power of 50kW. (Both Burghead and Westerglen are m.f. stations at present.) Thus England and the Scottish mainland will have complete coverage from two frequencies in the l.f. band. Unfortunately this gain has to be "paid for" in the Plan by the assignment of a new 200kHz frequency to Warsaw, at 200kW, for day-time operation. This will not worry us within the UK but will interfere with reception of Droitwich on the Continent. At the moment the BBC has not decided whether the new UK coverage on l.f. will be used for Radio 2 or Radio 4.

Radio London, the m.f. 1457kHz local radio station at Brookmans Park, will under the new Plan give better reception because a co-channel transmitter at present sited on the coast of Albania at Durres is planned to be moved 60km inland to Lushnje, where it will lose the benefit of "sea gain", and the night-time interference with Radio London will be reduced by 4-5dB. Unfortunately some

of the other UK local radio stations are likely to suffer worse co-channel interference at night, particularly Radio Solent at Fareham which may be 10dB worse off.

Night-time co-channel interference could also be worse for listeners to the Radio 3 647kHz, 150kW transmitter at Daventry, for under the Plan there are three new assignments on this frequency, for stations in Albania, Greece and Libya, and all for 300kW transmissions. To obtain protection against this interference it will be necessary to increase the power of Daventry, and the UK delegation stated at Geneva that it reserves the right to do this when the new transmitters come on the air. (Theoretically 2 megawatts would be needed but this is unlikely to be achieved because of cost.) These three new assignments in Radio 3's "province" well illustrate the principle adopted by the conference that existing stations should not have priority over new claims for the channels just because they are well established. However, the prospect of next-door neighbours Albania and Greece both transmitting 300kW on the same frequency seems somewhat unlikely.

Two further problems for the UK from the Plan: the power of Radio Ulster (1340kHz) will have to be increased from 100kW to 250kW to cope with increased co-channel interference power from Budapest; and the power of Radio 4 Wales (881kHz) will have to be increased from 150kW to 300kW to deal with increased co-channel power from East German and Yugoslav stations.

As mentioned in the January 1975 issue, the channel spacing will remain at 9kHz throughout the l.f. and m.f. bands. The actual frequencies assigned in the Plan at m.f., however, are slightly adjusted to make them integral multiples of the channel spacing; for example Radio 3, Daventry, at present 647kHz, will become 648kHz; Radio Ulster's 1340kHz will become 1341kHz; Radio London's 1457kHz will become 1458kHz.

Some commentators have described the 1975 Geneva Plan as a bad plan. "It started as a shopping list and it ended as a shopping list but everyone signed it and called it a plan" were the remarks of one delegate. Criticisms centre around the "power race" (of competitively increasing transmitter powers) and the fact that the Plan carries with it a long and untidy list of 72 reservations and 30 counter-reservations by different countries, claiming rights to change frequencies, powers etc. if they wish to after the Plan has come into force. Perhaps it's as well the Geneva Plan is to last for a maximum of only eleven years.

John Logie Baird and the Falkirk Transmitter

The activities of the pioneer of television between 1925 and 1928


by P. Waddell, W. V. Smith and J. Sanderson

Dr. Waddell and Mr Smith are at the University of Strathclyde. Mr Sanderson is Curator of the Falkirk Museum

On the evening of Tuesday, the twenty-sixth of January 1926, John Logie Baird demonstrated television to an audience of Members of the Royal Institution. No detailed description, with photographic evidence, of the equipment used for the demonstration seems to exist, although many authors have made guesses¹. It has been suggested that the instrument now at the South Kensington Science Museum was used, or that a very large disc unit with a single spiral of lenses was seen, but Baird had suddenly become secretive and information is hard to come by. The next two and a half years are poorly recorded and this article is an attempt to discover what Baird was working with during this period.

April 1925 is the beginning of the relevant period in Baird's activities. A. S. Goodchild and R. Best, both employed by Will Day Ltd of Leicester Square, had constructed a television transmitter to Baird's design². The instrument was to be used in the first public demonstration of television, given by Baird at Selfridge's in Oxford Street, and was delivered to him at 22 Frith Street, Soho, in late 1924. This unit was first described in *Wireless World*³ by Baird and some indication of his canniness can be obtained from the fact that he attempted to deceive his readers into thinking he was less advanced than he was. He gave a diagram of a large, basically unbalanced, single-spiral lens disc, which he knew would give a low-grade picture due to a necessarily low speed of rotation and vibration, which would blur the picture. Photographs, and a further article⁴, show that he was really using a double spiral of lenses, which made possible a higher speed and smoother running, and a radially-slotted disc subdivided each of the eight lines into 50 elements to produce a 400-element picture. (As a comparison, a modern television display contains about 450,000 elements.)

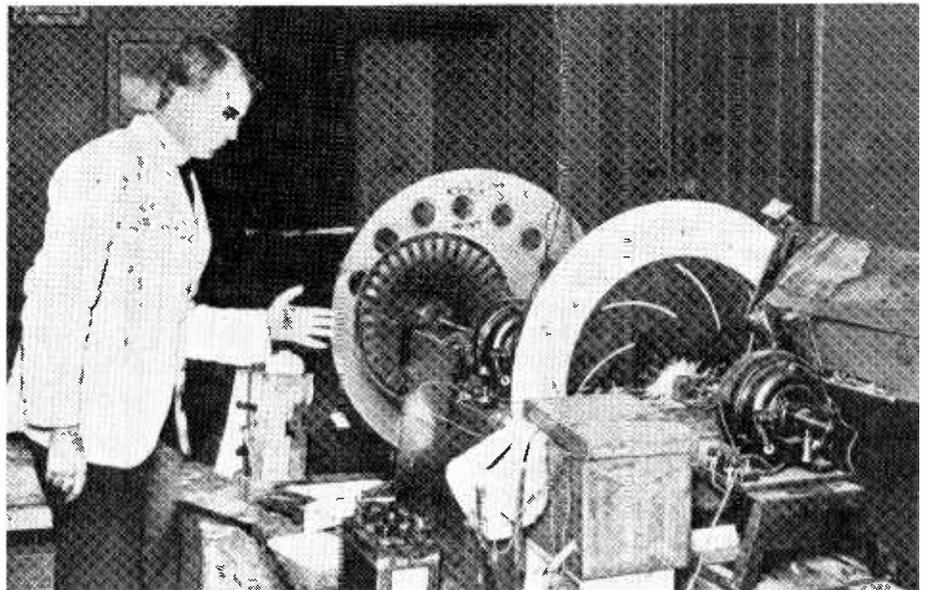
Later in 1925, in June, Television Ltd was formed as a means of financing Baird's research, Day and relatives of Baird supplying much of the capital. Day had also found the Frith Street laboratory and his name appears on



1A. J. L. Baird at 22 Frith Street, Soho, London, Dec. 1924, with his "original" television transmitter and receiver.

Science Museum, Kensington, London. Note the white painted double spiralled receiver disc has been removed, and that a rotary slot has been placed over the photocell, necessitating a change in the chopper disc mounting arrangement.

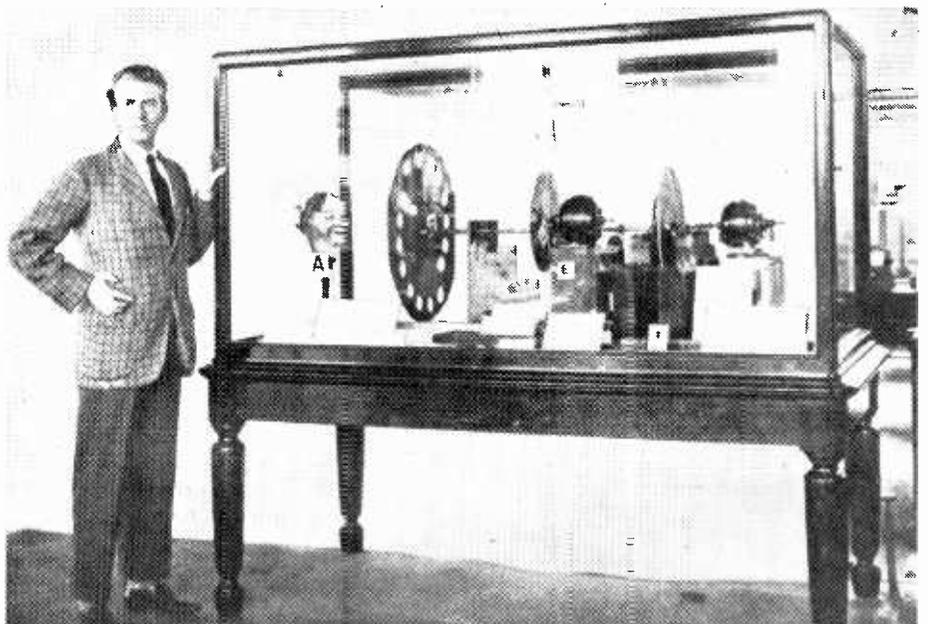1B. J. L. Baird, Sept. 1926, his "original" transmitter now presented to the




some patents which he had helped to finance from July 1923, while Baird was at Hastings.

In this way, the work was able to continue at Frith Street and further experiments and demonstrations took place. The face of William Taynton, an office-boy from another floor of the building, was televised by equipment of unknown design and in January 1926 Baird and Capt. O. G. Hutchinson (who had bought Day's share of Television Ltd) demonstrated televised human faces to the Press^{5,6}. Then, after the R.I. demonstration⁷, Baird clamped down and details of the equipment used were lost.

Newspaper reports and magazine articles are of some assistance, though words and pictures in some of these are at variance and serve only to cloud the image, many of them not giving details of equipment used. Tracing the development of the equipment, the first reference is found in the *Daily Telegraph*⁸, in which mention is made of a lensed-disc transmitter, with no further information.

A step forward is indicated by a report in *The Engineer*⁹ of June 18th 1926 which describes and illustrates a grid being used to subdivide the image, the "grid" being a bundle of optical fibres with which Baird claimed to have eliminated the need for a lensed disc. A full description of this transmitter was not seen until June, 1927¹⁰ and the patent on the use of optical fibres was not applied for until 1927, being obtained the following year – a further instance of Baird's reticence. Discrepancies between the description of the optical fibre system and the photographs of Capt. Hutchinson's televised face exist; the photograph which illustrated a number of articles of this period, showed the usual picture made up of vertical strips – a fibre system would have given a cellular appearance. Deception again, perhaps?

In September 1926, Baird gave a double-spiral lens-disc transmitter (two sets of eight lenses) to John Hart of Hart Radio Supplies in Falkirk and, six days later, donated the transmitter/receiver now on display at the South Kensington Science Museum. The authors have found no references to the Falkirk transmitter, except in the Falkirk Museum records. One difference between this unit and the Science Museum transmitting section is that the Falkirk unit has two, interlaced spirals of eight holes, providing a 16-line picture, while the Science Museum transmitter has two non-interlaced spirals, giving an 8-line picture. Further small differences include the use of three lens-retaining screws for each lens on the Falkirk unit – two for most lenses on the S.M. transmitter. Both units are provided with a rotary spiral slot over the photocell, which increases the number of picture lines, with no increase in the number of lenses. This slot was patented in January 1925,

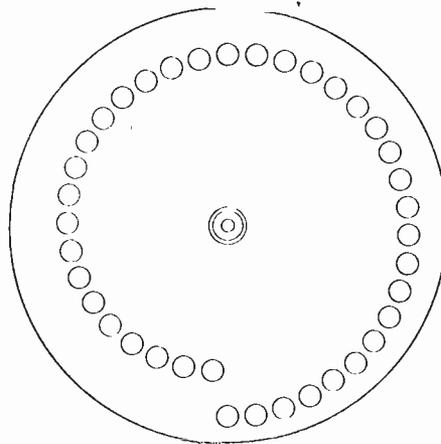

2. Suggested 32 lensed disc as used at Royal Institution demonstration by E. Larner¹ in 1929; book carries a foreword by J. L. Baird.



3. First ever televised photograph, Captain O. G. Hutchinson, business manager and director of Television Ltd and friend of Baird's since 1911 in Glasgow, when they were apprentices together at the Argyll Motor Works, Alexandria, Dunbartonshire. Photograph published in various magazines from June 1926. Photograph has peculiar aspects, one half of the image is apparently a profile, the other half being a frontal view.

although it does not appear in magazine articles or newspaper photographs of the first half of 1925.

In the first full description of the rotary slot – an article in *Electrical Review*¹¹ – Baird still discusses an 8-line transmitter and the diagrams in the article match the S.M. transmitter. A second article in December¹² also shows these features. Then, in 1927, Baird began to talk of 16-line transmitters, using choppers and rotary slots, as in

the Falkirk and S.M. units. In a paper¹³ read by Baird in March 1928 he describes, in words and in diagrams, a 16-line transmitter and clearly states "using equipment similar to that shown . . . I gave a demonstration of true television to the Royal Institution on January 27th, 1926". (Baird always referred to January 27th, not 26th). He also says that a London to Glasgow television demonstration, using G.P.O. lines, was performed on May 24th and 26th 1927 using the same equipment, i.e., the Royal Institution transmitter.

It is interesting to note that in the Falkirk Museum register of entries it states that the Falkirk transmitter was used by Baird to transmit human faces from Glasgow to London on 27th January 1927. Newspaper articles from April 22nd 1927¹⁴ talk of Baird sending his first batches of television signals to New York from London; other articles talk of signals from London, Hull, Leeds, Birmingham and Glasgow to New York. It should be remembered that Baird's publicized transatlantic demonstration was on February 8th 1928, so once again he was ahead of his well publicized public events, making sure nothing would go wrong on the big day.

Another article from March 1928 clearly talks of images from Glasgow to London¹⁵. A photograph of Baird (Fig. 6) standing beside the Falkirk transmitter, somewhere in the West of Scotland, has been traced. Four people date it to 1928 and almost certainly to Mr Hart's radio show exhibition in Falkirk. The photograph, reproduced in this article, clearly states "radio engineers" and the word "Glasgow" also appears on the board behind Baird's head. The dummy is unlike any seen in published work by Baird. Interestingly enough, one author, P. Waddell, has seen a photograph of Baird wearing the same overcoat on a visit to Scotland, dated January 1927. It should be noted that Baird did visit Scotland in early 1927, arriving in Glasgow on February 1st 1927 for his lecture in the St. Andrews Halls, Glasgow on February 3rd 1927.

Other mysterious events concerning Baird at this period and the equipment he was using are seen in the following articles. In *Nature*, January 15th 1927¹⁶ it was stated that Baird had lectured on January 6th 1927 to the 17th Annual Exhibition of the Physical and Optical Societies at Imperial College, London. A "model" of the transmitting portion of the lecturers "original" apparatus was displayed. Which one? The one from the Science Museum reborrowed, or the one given to J. Hart (still not sent to Falkirk), or a new and third unit? Backing up the third model concept it is clearly stated in a book by S. A. Mosely and H. T. Barton Chapple from 1931¹⁷ that Mr Baird had given a model of his original transmitter to Glasgow University, sometime in early 1927. This is also mentioned in *Nature* July 1927, and some parts of this transmitter are still in existence.

4. J. L. Baird's "original" 16-lensed disc transmitter and receiver. Note spiral slot over the photocell in the transmitter to increase number of TV lines, without increasing number of disc lenses. In the receiver light from a lamp at K is allowed through rotary slot on disc H then through the lensed disc, to be focused on screen F.



It would appear from the above evidence, and from other information we are not at liberty to disclose, that Baird was working in secrecy in Scotland on television well away from his main competitors. The reason for his secrecy from mid 1925 until early 1928 may never be fully known, but why did he never reveal in later years exactly what had been used in January 1926? The authors, having further information, can make educated guesses and assumptions as to Mr Baird's movements at this period.

Baird stated in *Radio News*, June 1927, that he had abandoned 16-line lensed disc transmitters since his last article in *Radio News*, which was September 1926. He also had abandoned fibre optics by the time of writing reference 12, i.e. June 1927, and was now investigating multiple-lensed-disc "optical levers". The optical lever enables a rapid scan of the image but only required low speed discs - in general up to five discs were used, four of which had a circle of lenses and not a spiral. The fifth disc could either be a single spiral or an oscillating or notching mirror in order to move the images over the photocell. A full description of such a system is given in a reference¹⁸. However, in *Modern Wireless* May 1928¹⁹ it is clearly stated that "they would have to wait and see if it worked."

The transatlantic TV demonstration by Baird on February 8th 1928 meanwhile had taken place using a lensed-disc transmitter. A photograph in *Illustrated London News* at the time clearly shows one lens with three screws at 120° around the lens, but what style of disc, two spirals or one, is not clear. In July 1928²⁰ *Television* revealed a photograph of an optical lever using mainly slotted discs and not lensed discs; no large single-spiralled lensed disc can be seen. Shortly afterwards Baird abandoned lensed discs and went over to small aluminium discs having 30 small holes in a single spiral.


One further mystery remains. Mr Baird donated the so called Royal Institution receiver to the Science Museum in 1930. The receiver consists of a disc having 30 holes in a single spiral and one's immediate reaction is that he must have used a 30-lensed disc, lenses in a single spiral. Why he left the receiver presentation until 1930 is not known.

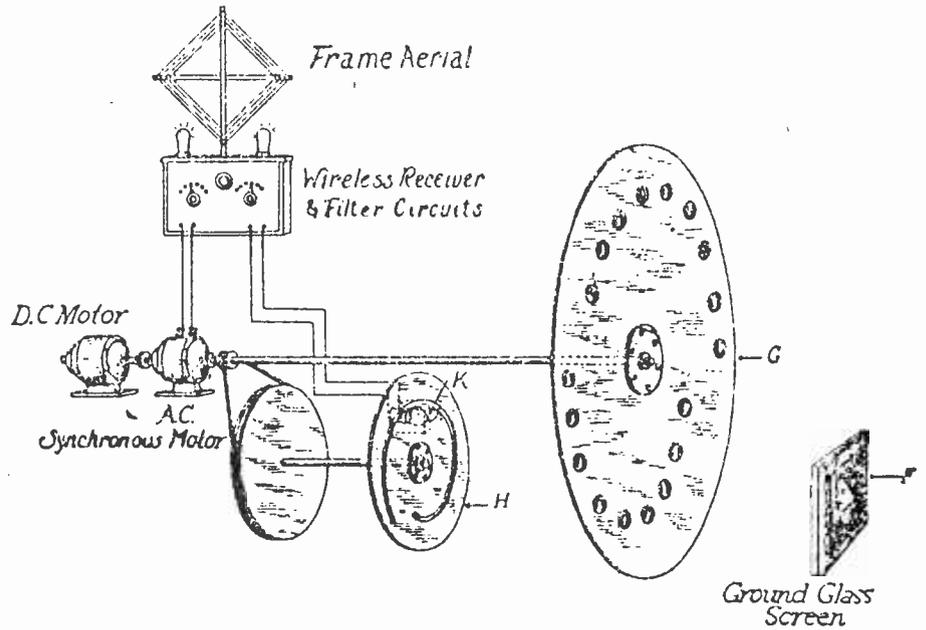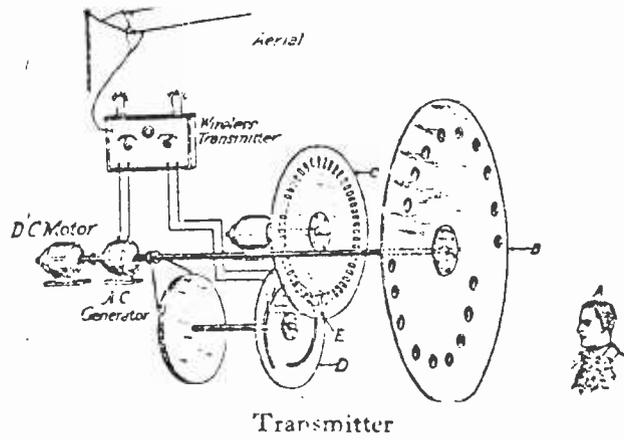Highlighting the utter confusion as to what Baird used in late 1925 into 1926



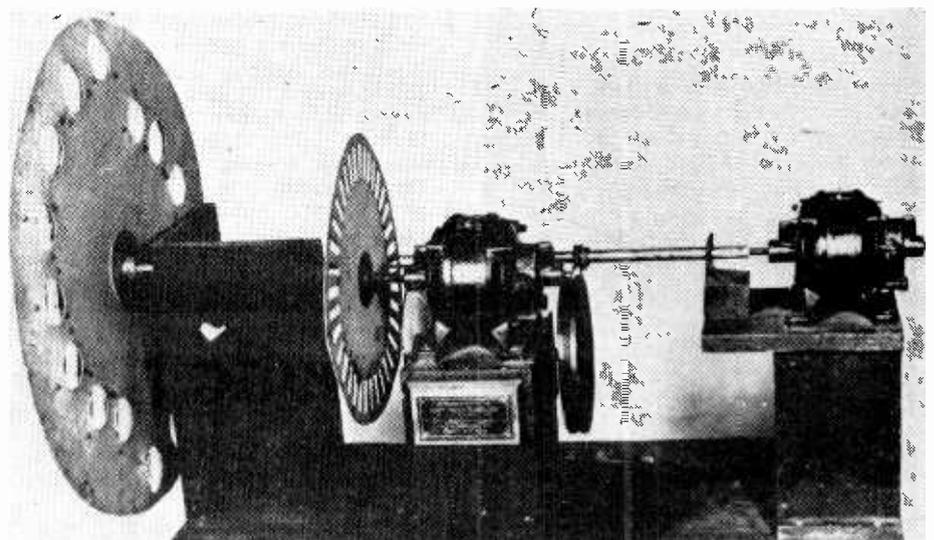5. Falkirk Museum transmitter, given by J. L. Baird to "Hart Radio Supplies" of Falkirk on 5th September, 1926. Mr J. Hart of Falkirk has apparently no

connection with Hart Batteries of London who gave Mr Baird £200 of batteries free of charge in June 1925.




are shown in two references. In a reference from January 1926⁶, Capt. Hutchinson describes the transmitter as having a nine-foot diameter disc with 50 lenses in spiral formation (single or double?) and rotating at a high speed. A

reference from late 1926²¹ describes Baird as using a large single-spiralled lensed disc transmitter in February 1926, although they could not be sure since "unpatented devices appear to have been used". A third reference from

September 1926²² shows a diagrammatic visualization of Baird's equipment at 2TV studios; what appears to be either a large-diameter single spiral or a circle of lenses is shown, followed by the rotary spiral slot over the photocell.

Baird only provisionally patented the double spiral system in late 1926, for an obvious reason. The double spiral with its well-balanced characteristics and small diameter enabled high rotational speeds to be achieved and was a commercial proposition. In the Spring of 1928 Baird started selling the double-spiralled small aluminium disc "Televisors" at Selfridge's, the spirals being of small holes and not lenses. One

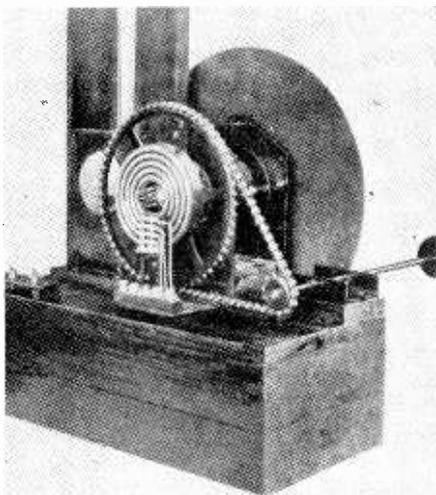

6. Baird with "Falkirk" transmitter (3 screws around each lens) in West of Scotland. Photograph dates to either early 1927 (Jan.) or by witnesses to 1928.



7. Royal Institution demonstration television receiver? Donated in 1930 by J. L. Baird to the Science Museum, Kensington. 30 holes in a single spiral.

spiral acted as a flying-spot transmitter and the other spiral, on the same disc, acted as the receiver. No synchronization problems existed and the units provided a lot of interest for the amateur TV enthusiasts. He was, in fact, creating a television market! So once again Baird in late 1924 with his double-spiralled lensed disc arrangement was 3½ years ahead of such a system being fully patented.

The authors would be delighted to hear from anyone with photographic or first-hand evidence on the actual equipment used by Mr Baird.

John Logie Baird, with 178 patents in his own name, is under serious study by several people at the moment and will undoubtedly emerge as one of Britain's finest researchers in tackling not only the technical but the business aspects of creating a television audience.

References

1. Lerner, E. T. 'Practical Television', (foreword by J. L. Baird), Benn, 1929, Chapter 8 'The Baird Televisor', pp.132-146. Describes a single-spiral 32-lens disc and a 64-slot (spiral) chopper disc.
2. Waddell, P. Private correspondence, November 1975.
3. Baird, J. L. 'Television, a description of the Baird System by its Inventor', *Wireless World and Radio Review*, 21st January, 1925, pp.534-5.
4. Baird, J. L. 'Wireless Television', *Engineering*, 119, Part 1, 29th May, 1925, pp.661-662.
5. Baird, J. L. 'Broadcast Picture of Derby', *Daily Express*, 8th Jan., Friday, 1926.
6. Baird, J. L. 'Television', *Manchester Guardian*, Saturday, 9th Jan., 1926.
7. Baird, J. L. a) 'The Televisor', *The Times*, Thursday, January 28, 1926. b) Photograph of receiver, *The Times*, Tuesday, 2nd Feb., 1926.
8. Baird, J. L. 'Television Problem', *Daily Telegraph*, 28th April, 1926, p.14.
9. Baird, J. L. 'Television', *The Engineer*, 18th June, 1926, p.641.
10. Dinsdale, A. 'Television Sees in Darkness and Records its Impressions' *Radio News* (USA), June 1927, pp.1422, 3 - 1490, 1, 2.
11. Dinsdale, A. 'Television', *The Electrical Review*, 5th November, 1926, p.748.
12. Baird, J. L. 'Television', *Experimental Wireless & Wireless Engineer*, December 1926, pp.730-737.
13. Baird, J. L. 'Television', *Trans. Inst. of Engrs. and Shipbuilders of Scotland*, 71, Mar. 1928, pp.604-614.
14. Baird, J. L. 'Faces Across the Sea', *Daily Herald*, 22nd April, 1927.
15. Baird, J. L. 'The Baird Television System', *Modern Wireless*, March 1928, pp.259-262.
16. Baird, J. L. 'Annual Exhibition of the Physical and Optical Societies', *Nature*, 15th Jan. 1927, p.101.
17. Moseley, S. A., Barton-Chapple, H. J. 'Television, Today and Tomorrow', Pitman, 1931, p.8.
18. Baird, J. L. 'Baird's Television Apparatus', *The Wireless Constructor*, Oct. 1928, pp.407-408.
19. Baird, J. L. 'Television Notes of the Month', *Modern Wireless*, May 1928, p.531.
20. Baird, J. L. 'Television', July 1928, p.22.
21. Baird, J. L. 'Television', *Encyclopaedia Britannica*, 1926, pp.756-7.
22. Baird, J. L. '2TV Studios', *Illustrated London News*, 11th Sept. 1926, p.145.

Meetings

MANCHESTER

20th. IEE — "Minicomputers — wherever next" by M. Judd at 17.45 at UMIST, Sackville Street.

28th. IEE — "Advanced developments and miniaturization in the telecommunications field" by J. G. L. Rhodes at 17.45 at Renold Building, UMIST.

MIDDLESBROUGH

29th. IEE/IMC — "Application of microcomputers to industrial control systems" by J. Gallacher at 18.30 at Cleveland Scientific Institute, Corporation Road.

NEWCASTLE-ON-TYNE

5th. IEE — "The manufacture of thick-film, precision active filters" by A. W. Greenwell at 18.15 at M4 21 Merz Court, University of Newcastle-on-Tyne.

12th. IEE — "My Dear Watson" by G. Phillips at 18.30 at The Refectory, The University, Newcastle-on-Tyne, Kings Road.

NEWPORT, I.o.W.

31st. IEE/IERE — "Microwave landing systems" by R. Barrett and J. M. H. Chambers at 19.30 at the Isle of Wight College of Arts and Technology.

OXFORD

14th. IEE — "More and more on less and less (integrated circuit design)" by P. C. Newman at 19.00 at Oxford Polytechnic, Headington.

POOLE

14th. IEE — "Hi-Fi" at 19.30 at Arndale Library.

PRESTON

14th. IEE — "Inertial navigation" by Cmdr. C. J. G. Young at 19.30 at Torella Restaurant, 76 Friargate.

20th. IEE — "Reduction in hi-fi noise" by K. J. Gundry at 19.30 at Preston Polytechnic.

RUGBY

20th. IEE — "Cinema engineering" by H. Rigby at 18.15 at Lanchester Polytechnic.

SHEFFIELD

21st. IEETE — "Electronics in rolling mills" by D. Turner at 19.30 at Granville College of Further Education, Granville Road.

SOUTHAMPTON

21st. IEE/IERE — "Electronics in schools" by G. F. Bevis at 19.30 at Southampton College of Technology, East Park Terrace.

SWINDON

6th. IEE/IERE — "Automobile electronics" by C. S. Rayner at 18.15 at The College, Regent Circus.

WEYMOUTH

22nd. IEE — "Data processing and recording" at 18.30 at South Dorset Technical College, Newstead Road.

Binding WW volumes

To have your volume of *Wireless World* bound by our company, send the copies to: Press Binders Ltd, 4-4a Iliffe Yard, Crampton Street, Walworth, London SE17, with your name and address enclosed. Confirm your order and send it with the remittance (£6.05 for each volume) to IPC Electrical-Electronic Press Ltd, Binding Department, Room 11, Dorset House, Stamford Street, London SE1 9LU.

What's in a name?

More views on technical terms

By Cathode Ray

As long ago as 1934 (Nov. 23 issue) I took it upon myself to attack, by ridicule, the many absurd and inappropriate "technical terms" that had come into use in the world of wireless. The attack was renewed in 1945 (April issue), "non-linear" (distortion) being one of the targets. It was encouraging to note that by 1954 the British Standards Institution had admitted "non-linearity" to BS.2065 as an alternative, and by 1955 "non-linear" had been banished from BS.661. Although I have continued to fire at "targets of opportunity" whenever they arose, the fact that an article devoted wholly to misconceived terms has not seemed needful for the last three decades is evidence of an improvement in this respect, though how much (if any) is due to my campaign and how much to a growing sense of logic among electronic engineers I can't say — nor can anyone else.

But seeing (in *WW*, May 1975, and elsewhere) the word "slew" used in a sense apparently quite unconnected with its actual meaning, has stirred the old instinct once more. I do not, of course, refer to the past tense of "slay", but to a type of movement. (It can alternatively be spelt "slue".) The origin of the word is obscure, but there is no doubt that an essential feature of the movement it refers to is turning or twisting. A sailor might use it to refer to the swinging round of a boom, or even a turning movement of the whole vessel. So it could hardly change in an unchanging direction, as applied, for example, to deflect a cathode ray (you see why I am affronted by this usage!) across an oscilloscope screen. I hope that whoever started misusing this word will kindly explain why he did so. He would make an interesting case history in psychology, no doubt under the heading "Humpty Dumpty complex". (Mr H. Dumpty was, of course, the character who claimed the right to make words mean just what he chose.)

Since I first protested against the use of "ground" (instead of "earth") by non-Americans, and in particular such expressions as "grounded base", or even "earthed base" (instead of "common base") by anybody at all, there has been a marked reduction in the latter offending usage. I won't repeat the whole story; the nub of the matter is that in this context the description "grounded"

or "earthed" is not the essential feature of the type of connection so described. A transistor (or triode valve) used for amplification has a pair of input and a pair of output points, and its performance depends very largely on which of its three electrodes is common to both pairs. The fact that quite often this electrode is also earthed, directly or indirectly, is beside the point; it need not be, in order to qualify as any one of the three possible configurations. It is quite possible for a transistor to have one electrode common and a different one earthed. So the usage complained of is clearly wrong.

Incidentally, it is meaningless to apply a common-electrode distinction to an oscillator, but the Editor considers this too obvious to need explaining. I hope he is right.

My impression is that there has been a noticeable improvement in rejection of such absurdities as "d.c. current", "d.c. voltage", and "i.f. frequency". I wish I could say the same of "at d.c." (meaning "at z.f.") and "d.c. to 10 MHz" (meaning "0-10 MHz"). Why should frequency be stated in terms of current? I'm afraid "mixer" (applied to frequency changers) is a lost cause. If this wrong term were abolished, students would be more likely to grasp that just adding together signals of different frequencies (as in the correctly-named audio mixer) does not create other frequencies, any more than just mixing nitrogen and hydrogen produces ammonia.

My only other complaint just now is of a misusage that is far more widely distributed than in technical literature, being spoken by broadcasters and written in *Times* leaders, to give but two examples. But whereas in these examples it can often be dismissed as mere poetic fancy, in technical contexts ambiguity must be avoided at all costs. It happens that in English there is one word, and one word only, to mean "one or the other but not both". That word is "either". When one wants to include two alternatives there is the correct word "each". Or, if you prefer, "both". As if the choice of these two were not enough, however, certain lewd fellows of the baser sort, as St Luke might well have described them (Acts, ch.17, v.5), perversely reject both of these and see fit to use (or rather misuse) instead the only word that means *not* both. (Again

the Bible provides a fitting comparison, with the rich man who wantonly took the poor man's only lamb rather than kill one from his own flock. David declared indignantly that this man — actually himself — should surely die.) People who say or write "on either side" when what they mean is "on each side" or "on both sides" are guilty of murdering the English language. As a result of this, when one wants to make quite sure that "either" (correctly) is meant there is no way left of doing it. To this day I'm not sure what the writer of an article in *Electronics & Power* meant when, describing a new electric train, he wrote that there was a motor unit "at either end". Was he using or misusing the word? Only he could tell, and if he really meant "either" he was not to blame for the failure to communicate his meaning unambiguously; the blame would lie on those who won't use either of the words provided but have to steal the one word available for conveying a certain different meaning.

There are of course quite a number of English words which through ignorance or carelessness are so often wrongly used that one is forced to abandon them altogether for fear that they would probably not be rightly understood. Such words as "infer" (in place of "imply") and "protagonist" (supposing it to be the opposite of "antagonist"). But they are not very relevant to *Wireless World*, so I refrain from further comment.

English is a wonderful language for precise communication — if it is used with due care.

Editor's footnote: Our respect for the English language has to be tempered sometimes by the overriding need for effective communication in a complicated subject. This means that we have to follow common usage in technical language, just as everyone has to in ordinary language. Common usage may not produce the most elegant or logical expressions but it's what everyone understands. And, of course, it does bring changes in terminology. The term "antenna", for example, is gradually replacing "aerial" in the UK, and although some people may deplore this as an Americanism it is in fact a perfectly good, and descriptive, English word to be found in the Oxford Dictionary. We apologise to readers if our terminology is not always consistent, but we live in a rapidly changing world.

Letters to the Editor

CITIZENS' BAND IN EUROPE

November's World of Amateur Radio mentioned the increased sales of Citizens' Band transceivers in the USA. You may be unaware that Citizens' Band is not limited to the USA. Here in West Germany we have a flourishing CB system and in Scandinavia and several other European countries CB is well established. The German authorities have allocated frequencies from 26.965 to 27.275 MHz at a spacing of 10 kHz, which gives about twenty-six channels, with certain exclusions. Power is limited to two watts input, and two types of transceivers are available, one type being licence and payment free and the other costing DM5 per month (about £1, but in cost-of-living terms more like 50p).

There is a considerable number of CB clubs in Germany, several of them American with USA forces constituting the members. The club to which I belong has roughly 100 members. Basic operating procedure is to allocate one frequency as a "monitoring" frequency and when you contact your party you shift to one of two "conversation" frequencies. Callsigns are generated by the CB-ers themselves. Traffic on CB is totally dissimilar to amateur radio traffic; although there are the keen DX-ers, most people use mobile-to-mobile or mobile-to-fixed transceivers for convenience and assistance.

Despite the dire fears of the British Post Office, little interference with television is caused by the licence-free or the registered users, and the Bundespost has gained rather than lost revenue from the CB-ers, who mostly use CB in addition to the telephone rather than instead of it. It does indeed seem a pity that the B.P.O. are so down on CB. Driving through England, the deadly silence of my CB set was a miserable contrast to the many interesting chats I have had with fellow German and American CB-ers in Germany, not to mention the useful information one can get about traffic jams,

fog, snow, and "Smokey the Bear" sitting at the side of the road with his "Camera Machine"!

Robin Adrian Flood,
Darmstadt,
West Germany.

Pat Hawker comments:

Although Citizens' Band Radio has become an anathema to very many radio amateurs (we have learned to fear that recruits and frequencies may be spirited away from our side of the fence) it constantly surprises me that there is not a more persistent and vocal demand for CB facilities in the UK. Many countries now have such facilities, and it would surely not be beyond the wit of the Home Office to devise a system that would avoid most of the well-recognised abuses yet still give the British citizen the advantages of two-way radio at low cost.

But in his reference to "Smokey Bear and his camera machine" Robin Flood rather gives the game away — and the Home Office is not likely to be anxious to see a British CB system used for the dubious purpose of giving other motorists advance warning of police speed traps — for that is the meaning of such Smokey Bear messages, and one of the reasons for the current CB boom in the United States. Officially in Germany the CB channels are intended for specific purposes, including police, fire, Red Cross, small businesses, sports clubs, etc. The problem that many countries have found is that once you grant CB facilities there is no easy way to check how they are being used — hence Smokey Bear.

EXPLOITATION OF VIEWDATA?

I was much interested by the review in your November issue ("Wireless World Teletext decoder" by P. Darrington) of methods which have been used to transmit additional information over a standard television channel.

If they do not already know it, your readers might like to have the discussion of this topic by Prof. Stafford Beer brought to their notice. In his book "Platform for Change" (Wiley 1975, p. 236) he discusses the social and political implications of systems which could, in effect, allow electronic monitoring of what pages of the newspaper an individual chooses to read. There are obvious possibilities for exploitation by advertisers and propagandists.

Stafford Beer does not advocate the abolition of Viewdata and other developments (such as data banks of personal information) which threaten to infringe personal freedom. The potential benefits are enormous if the developments are properly handled. What he argues is that attention should be given urgently to deciding what constitutes proper

handling and to bringing it about. Systems should be designed, right from the start, so that decisions about access to information can be made according to proper democratic procedures, and enforced.

Your presentation of this series of articles and a design for a decoder is an admirable way of bringing the possibilities to the notice of a responsible section of the community.

A. M. Andrew,
Department of Engineering
and Cybernetics,
University of Reading.

The Government is about to issue a White Paper on the question of personal privacy and the use of data banks and other electronic systems. — Ed.

AUDIO AMPLIFIER LOAD SPECIFICATION

Now that voltage-dependent current limiters are in widespread use, it is important that users and reviewers should be aware that such circuits, when made too potent, can severely restrict the output-voltage-producing capability of an amplifier when feeding partially-reactive loads of the type presented by normal loudspeakers. I find myself in agreement with every word of Peter Walker's letter in the December issue, and I think the only controversial point is whether his practical criterion, that a good amplifier should be capable of feeding a load of $R \pm jX$, without increase in distortion, is the most sensible choice of criterion. In the absence of detailed information on the complex impedances of numerous commercial loudspeakers, it does, indeed, seem to me to be a reasonable and sensible compromise.

It is really commercial pressures and trends that have given rise to the widespread use of voltage-dependent current limiting, for it enables a manufacturer, with little increase in cost, to increase substantially the (resistive load) power rating of an amplifier, without sacrificing reliability. Sometimes it is deemed to permit the use of faster, though less robust, output transistors. Though this may lead to impressive-looking figures and square-wave photographs in reviews, it may well represent a step in the wrong direction nevertheless, for there will inevitably have been some sacrifice in reliability, and excessively wide bandwidths are in any case quite pointless in an audio amplifier.

It is an unfortunate, but quite inherent, feature of voltage-dependent current limiters, that they tend to make the audible effects of overloading, with some types of load impedance, much more pleasant. This is because the limiter, while operating, gives the amplifier a negative incremental output resistance — an increase in the collec-

tor-to-emitter voltage of the "on" transistor reduces the current it can turn on. If the load has an impedance at some frequency of the same nature as that of a tuned circuit, oscillation will occur while the limiter is acting, giving unpleasant squittery sounds.

There is much to be said for making nice simple, robust amplifiers, without voltage-dependent current limiters, even though, for a given price, these may offer less spectacular power-rating and bandwidth figures; but commercial pressures tend to be against this philosophy.

It has sometimes been said that, even in the absence of voltage-dependent current limiters, reactive, or partially-reactive, loads are "difficult" for amplifiers to cope with, and are liable to give feedback distortion. In a well-designed and conservatively-rated feedback amplifier, without limiter, even a fully reactive load gives rise to no particular distortion difficulties and is, indeed, likely to give less distortion than does a purely resistive load of the same value. I gave the results of some measurements verifying this theoretically-predictable result in a letter to the editor in January 1955. If the distortion does increase on reactive loads, it is usually because the feedback stability margin is insufficient, giving oscillation, or near-oscillation, during part of the cycle. The transient testing technique described by R. C. Bowes in the December 1962 issue, applied with loads of appropriate phase angles, is helpful here.

Peter J. Baxandall,
Malvern,
Worcs.

"THE CONSULTANTS"

It is clear from John Dwyer's very comprehensive article on consultants that he invested a considerable amount of time in research and discussions with individuals in the industry. Unfortunately, the very range of his discussions seems to have led to some quoted comments being abbreviated to the point where a degree of distortion has resulted. Since one of the things which emerges strongly from his article is the controversy surrounding the role and relevance of consultants, it is important to make sure that the complex issues involved are not muddled by incorrect attributions (November issue).

Mr Dwyer devoted considerable space to the very important question of whether learning by the consultant is carried out at the client's expense or his own. How you tackle this question depends partly upon what is included as "learning". In routine situations a consultant should be fully briefed already. If he is not, he should most certainly acquire the necessary skill and background in his own time and not at the client's expense. This point hardly

needs stating. However, my comment, which he paraphrased as "if you're working for the government they don't mind your learning at their expense" was made to emphasise a particular point. This was that a different type of learning is involved when a client, which may often be a government agency, retains a consultant to carry out a specific type of work for him, involving the breaking of new ground. Examples include the development of a new technology or provision of an independent assessment of an existing technology unbiased by any preconceptions. In such cases familiarisation with the technology and so development of the consultant — learning — are inevitable consequences of the work which the client is sponsoring. He himself is well aware of this and happy that it should be so.

John Dwyer also implies that the receivership (not bankruptcy) of the group to which Cambridge Consultants belonged may still be having its effect: this anxiety could be quickly dispelled by considering our financial and technical success since that time. However, a consequence of that experience has been to make us at CCL crucially aware of the essential need for really solid product development and production engineering if a product is to be successful in the market. This is a very important lesson which we have not forgotten and I regret that John Dwyer seems to have done so by mislaying the essential point of my comment on that topic!

My comment he quoted on the section reproduced from my article in *Communications International* (referring to the accessibility of consultants) was that specialist skills which a client may need may often exist within the large corporations, such as Marconi. However, these skills often cannot be tapped from outside the organisation. They may not even be available to other members of the corporation, because of competing demands for the time of the specialists involved. In such cases, consultants with the appropriate skills can provide a source of the necessary know-how which is accessible to all.

I fear that the very comprehensiveness of the article, covering the range of companies, establishments and styles which it did, will not have given a possible user of consultants much guidance or help in deciding whether a consultant might be of help to him personally, and if so whom to select.

My own views on this are that use of a consultant can be indicated if the development is short term, if internal development effort or appropriate skills are not available, or if long term commitments resulting from the recruitment of new permanent staff are unacceptable.

The question of whom to select to undertake the work is more difficult. Clearly, in addition to personal competence to carry out the work, a consul-

tant should also have adequate equipment and resources to ensure that time is not wasted as a result of a half-baked approach. But in addition, and equally important, he should have a clear and detailed perception of the client's needs and proven ability to deliver results efficiently. This requires much experience of managing development programmes. This is a difficult and absolutely essential art and did not receive, in my view, nearly enough exposure in an article which paid attention to so many other aspects. It is management ability which really distinguishes and singles out the competent contract research and development activity and failures in this same area which have given rise to perhaps the most cogent criticisms of consultants quoted in John Dwyer's article. Effective management and control of projects is of equal importance to technical competence and this fact can hardly be over-emphasised.

R. J. Smith-Saville,
Cambridge Consultants Ltd,
Cambridge.

DOPPLER DISTORTION AGAIN

In the September issue Mr Coleman raises the question of the audibility of Doppler distortion in loudspeakers and feels that it is rather surprising that the listeners should be able to recognise "such subtly camouflaged distortions." I rather take the opposite view: "how can they fail to recognise them?" Reference to the test results quoted on page 67 of the April, 1974 issue show that when using an 8 inch speaker the Doppler distortions are some 16dB higher than the amplitude intermodulation distortions. As the distortions components arising from Doppler and amplitude intermodulation are at exactly the same frequencies it is reasonable to believe that the Doppler distortion will be more significant when the distortions are judged subjectively. I believe that the "dirty reproduction" generally thought to be due to amplitude intermodulation is largely due to Doppler distortion.

It may only be coincidence but if one notes the order of merit for the seven pairs of high quality loudspeakers recently panel tested by *Hi-Fi News*, it will be seen that there is a significant measure of agreement between the measured Doppler distortions and the listening panel opinion about the quality of reproduced music.

Mr Coleman's suggestion that room effects may make Doppler distortion more obvious is well based. When reproducing two test tones in a room, head positions can be found where the distortions are either very audible or almost inaudible, particularly if one ear

Television tuner design — 4

Alignment and use of coupler

by D. C. Read, B.Sc.

These instructions cover all aspects of adjustment and even though most of the operations described are simple to carry out — many are virtually standard practice for equipment of this type — the same degree of detail is maintained throughout because the listed sequence is a step-by-step diary of actions taken and measurements made when lining-up two tuners to this design (one with a varicap front end and the other fitted experimentally with vared-capacitor tuner). Hence, the instructions given are all essential and practical and, if followed closely, should lead to a circuit performance well within tolerance.

1. Connect +24 V to the board and measure the total current delivered which should be about 140 mA. If the on-board regulator is fitted, the supply to this should be at 30 V nominal.

2. Using an Avometer Model 8, or voltmeter of similar sensitivity, check that the d.c. values measured through the circuit agree with those listed in the Table. Ensure particularly that — the separate u.h.f. tuner supply feeds taken through D_1 and D_2 , D_3 are both at $12 \pm 0.7V$.

— the tuning voltage supply at the collector of Tr_{20} is +11 V (within the zener tolerance). If, as mentioned in step 11(a), one of the higher-numbered television channels is required for selection, a supply voltage of +16.5 or +22 may be derived by adding extra zeners to the D_{12}/D_{13} circuit.

3. Set adjustable resistors R_{17} if fitted, R_{19} and R_{83} to mid-range; set R_{78} fully counter-clockwise to give about 15.5 V on the slider.

4. Disconnect one end of R_{74} (connected to the junction of C_{65} , R_{75} and R_{76}) to disable the a.g.c. circuit — but make sure that the wire link feeding a.g.c. signals to the i.f. stages is in position. Thus the control voltages fed to the u.h.f. tuner module and to the Tr_2/Tr_3 i.f. amplifier are basically set by the fixed values of R_{85}/R_{86} and R_{80}/R_{81} . (Subsequently, the full range of gain control is tested by connecting three extra resistors to the a.g.c. circuit so as to form a temporary adjustable divider as shown dotted in Fig. 2.)

For i.f. alignment, start with an a.g.c. feed of +4.5 V as measured at the injection link wire (D in Fig. 2); this gives a gain reduction of about 12dB as

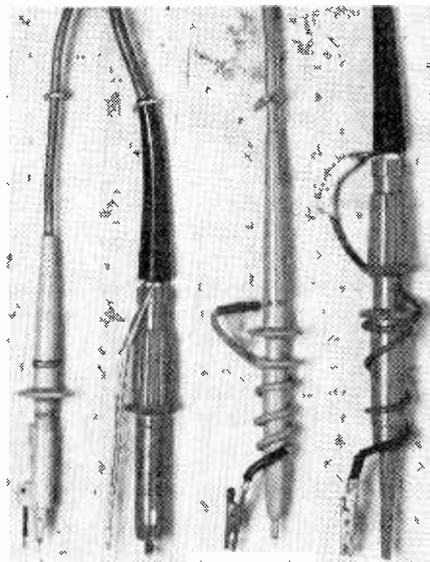


Fig. 19. Oscilloscope test probes: (left) "twin-legged" (Hewlett Packard) type; (next) home-made version constructed from "standard" probe. The two other examples — with earth

leads coiled round the probe body — are simpler usable alternatives. Care in the use of probes is necessary in the 30-40 MHz region to avoid measurement error and confusing radiations.

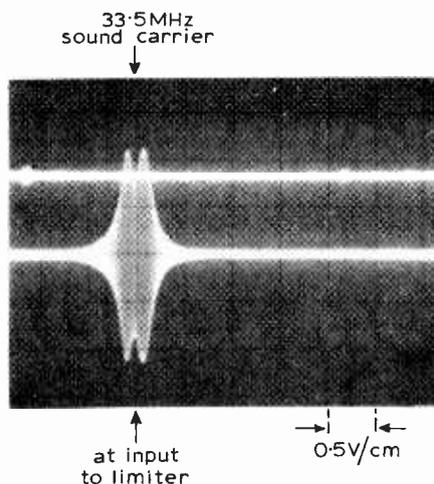


Fig. 20. Sweep response of Tr_9 output showing sound i.f. band.

shown in Fig. 13 of Part 2. Note that an increase of a.g.c. voltage results in a decrease of main-circuit gain because the transistor current gain falls as the collector current rises.

5. Disconnect the wire link feeding the incoming signal to Tr_1 base. Inject a signal from a sweep generator directly into Tr_1 via small (2.2 nF) disc ceramic capacitor connected to the base and with a 75-ohm terminating resistor across the end of the generator outlet cable having one end soldered to the earth plane of the board. Remove C_{23} from the i.f. output test pins; feed the output from across C_{22} to the display oscilloscope.

It is essential in this operation that the oscilloscope probe should not cause too much change in circuit constants normally obtaining at the measuring point, neither should it distort the observed response by virtue of added reactance in the output test feed-line itself. Ideally, a two-legged probe such as that provided with Hewlett-Packard equipment — see Fig. 19 (top) — could be used; failing this, it is worthwhile constructing a home-made version, using a standard type of probe without the clip attachment and modified as suggested by the second example shown in Fig. 19. The two other lower examples show probes with their earth leads round the body; these would be usable alternatives.

The injected signal sweep should be from about 29 to 44MHz, preferably having the swept range set so that the horizontal scale on the oscilloscope graticule fits in with the important frequencies in the anticipated pass band. Typically, this would require having the sound carrier at 33.5MHz spaced two divisions left of centre and the vision carrier at 39.5MHz two divisions right of centre. The response oscillograms in part 2 have such a spacing. Set the signal amplitude at Tr_1 base to give an output r.f. envelope measured across C_{22} (at the MC1330P input) of 100 to 120 mV pk-pk.

6. Adjust L_4 and L_6 to obtain a response shape which is shown in Fig. 4 of part 2; Fig. 3 was obtained with the sound

trap/sound take-off disconnected. Adjusting L_4 alters the position of the pass-band (tuned so that the required range of frequencies is covered) and L_6 controls the in-band shape (set so that the double-humped response is as flat and level as possible).

7. Adjust the $L_{19}/L_{20}/L_{21}$ circuit as follows. The drawing of this inductor assembly (Fig. 15) shows a 2-mm gap between the upper coil, L_{19} , and the overwound pair, L_{20}/L_{21} . This is a typical spacing for the required degree of coupling but because it is a critical factor in circuit operation it may need slight alteration, possibly making use of the sliding paper tube arrangement mentioned earlier.


It is essential to use a non-metallic tool (e.g. a filed-down knitting needle) when making core adjustments otherwise there will be a marked change in notch response each time the tool is withdrawn and it will be virtually impossible to achieve the necessary tuning accuracy. For similar reasons, the shielding cans must be fitted and screwed down in position before any adjustment is made.

To start the procedure, initially fit only the lower tuning core. Observing the sweep output as in step 5, use this core to set the tuning of L_{20}/L_{21} so as to obtain a dip in the response at 33.5MHz. Now add the second core, screwing it only a short way into the stack until the L_{19} circuit resonates to give the deep narrow response null which is created by phase cancellation between the two circuits. Next, readjust the lower (L_{20}/L_{21}) core to find two such null points which, typically, should occur within $\frac{3}{4}$ turn of the core and be separated by about 300 to 500kHz; this double-null condition shows, in fact, that optimum coupling exists. (If only one null is obtained — which may be quite shallow — this indicates over-coupling, and the coil spacing of 2mm must be increased slightly; alternatively, a decrease in spacing is desirable if the two null points are more than 500kHz apart.)

L_{20}/L_{21} core is then screwed out to select the null at the higher frequency (and which is further identified by having a noticeably steeper slope towards the video pass band as illustrated by the response shapes in Figs 5, 6 and 7 of part 2). Finally, move the two cores simultaneously and very gently together along the former, maintaining the shape of this steep-sided notch, until the null point is set exactly at 33.5MHz.

8. Loosely couple the signal from the sweep generator to the i.f. injection test point (drawn in Fig. 2 as an unconnected pin to the left of the u.h.f. tuner i.f. output connection) by putting a plastic sleeve over the test point and winding two or three turns of wire round it with one end soldered to the

Test conditions

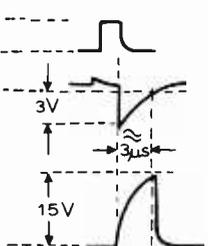Circuit point	D.C. condition (V)	A.C. condition
r.f. stage (u.h.f. tuner)	+ 12 (± 0.7)	
osc. stage (u.h.f. tuner)	+ 11.5 (± 0.7)	
Tr1 base	+ 4.5 (approx.)	
Tr2 base	+ 3 for max. gain + 6.7 for min. gain	
Tr3	+ 4.6	
IC1 input (measured across C22)		100 to 120mV pk-pk i.f. envelope; see Figs 6 & 12
IC1 output (measured at pin 4 via R102)	blanking level $\approx + 5.5$ (depends on R19 setting)	2.6Vpk-pk comp. video
Tr4 base	blanking level $\approx + 7$	1.8V pk-pk comp. video
Feed to a.g.c. circuit (measured at R27)	blanking level $\approx + 14.8$	4V pk-pk comp. video
Video output (75 ohms) (medium Z)	blanking level $\approx + 12$	1V pk-pk terminated 2V pk-pk
Tr8 emitter	$\approx + 11$	
base	$\approx + 11$	
collector	+ 24	
Tr9 emitter	+ 12.4	
base	+ 12.9	
collector	+ 24	
Tr10 emitter	+ 2	
base	+ 2.7	
collector	+ 12.4	
Tr11/Tr12 emitter	+ 5.4	
base	+ 5.7	
collector	+ 24	
IC2a	pin 1 compensating $C = \frac{R_{59} \times 30}{R_{59} + R_{63}}$ pF	'C' must be set for gain used (6dB C = 15pF)
(ex $\frac{1}{2}$ SN72747 now SN72748)	pin 8 pin 2 pin 3 pin 4 pin 5	a.f. $\approx 0.25V$ r.m.s.
IC2a (SN72748P) cont.	pin 6 pin 7	a.f. $\approx 0.5V$ r.m.s.
IC2b (ex $\frac{1}{2}$ SN72747 now SN72741P)	pin 1 pin 2 pin 3 pin 4 pin 5 pin 6 pin 7 pin 8	n.c. n.c. tuning + a.f.c. correct tuning + a.f.c. (hi-Z) 0 n.c. as pins 2 and 3 + 24 n.c.
Tr13 base	blanking level $\approx + 15$ white level $\approx + 18$	4V pk-pk comp. video
emitter	blanking level + 15 to + 15.7 video clipped at 0.4 to 0.7V above blanking	1.6-1.9V pk-pk (syncs + clipped video)
Tr14 base	bottom of syncs at $\approx 0.7V$ below supply	4V pk-pk comp. video
collector (M.S.)	+ 24	
Tr15 base	$\approx + 19$	
collector	0	
Tr16 source	see Tr13 emitter	see Tr13 emitter
gate	see Tr15 collector	see Tr15 collector
drain	blanking level 15 to 15.7	
Tr17 emitter	+ 0.7V w.r.t. the sampled-and-held blanking level voltage	
base	see Tr16 drain	
collector:	$\approx + 4.5$ (depends on incoming sig. strength; from 2.9 to 5 see Tr17 collector typically + 4.35 in the range: + 2.8 for low sig. + 4.7 for high sig.)	If incoming sig. 'flutters' then inverse a.c. comp appears here.
Tr18 emitter		
base		
collector		

inner of the generator output co-axial cable. The braid of the cable is connected to the board earth plane, and the generator is terminated by a 75-ohm resistor between the cable inner and the earth plane.

Replace the link to Tr_1 base which was previously disconnected. With the same sweep range and output across C_{22} established in step 5 — preferably adjusting the generator output if necessary to obtain the required 100 to 120mV pk-pk signal amplitude specified, and leaving the temporary a.g.c. divider variable at the 4.5 V setting given in step 4 — adjust the u.h.f. module tuning slug for pass-band position and the core of L_2 for band shape to obtain a response as illustrated in Fig. 5 of Part 2. Here, it may be advisable to temporarily tune out the adjacent-vision trap (L_1) and the adjacent-sound trap (L_3) so that the effect of these circuits can be disregarded when making the main pass-band adjustments.

To do this, tune L_1 well below 31.5MHz and L_3 well above 41.5MHz; after making the main-circuit setting, re-tune L_1 and L_3 to give notches at these frequencies. Observe that L_3 , particularly, has an effect on the pass-band shape itself; in fact, the L_3 response skirt completes the shaping at the 6dB-down region around the wanted vision carrier at 39.5MHz. Ideally, the pass-band response here should be symmetrical about the carrier frequency such that the curvature towards the notch is an inverted mirror image of the curvature towards the flat part of the pass-band — the 39.5MHz point being at the 6dB-down level; this is, of course, a particular requirement of the vestigial side-band reception system as specified by the idealised curve of Fig. 8.

9. With the sweep test signal still being fed at the same level as in step 8 via the u.h.f. tuner i.f. injection test point coupling, disconnect C_{44} from Tr_9 collector and transfer the oscilloscope probe to between Tr_9 collector and earth; the oscilloscope must be operated in the a.c.-coupled mode for this next measurement. Remember to re-connect C_{23} across C_{22} , and note that the value of the replaced component must be as nearly as possible the same as the probe capacitance, typically 10pF, if the circuit conditions as indicated on the oscilloscope are to remain undisturbed.

Connect a 20pF capacitor across L_{16} (this, added to the 10pF or so of the probe, gives the tuning capacitance required for L_{16}). Fig. 20 shows the response shape which should be obtained at this point. The 33.5MHz sound carrier is at the centre of a 1MHz pass-band (only ± 50 kHz of this being occupied by the sound-modulation side-bands, the remainder of the bandwidth is needed to develop an a.f.c. voltage of sufficient range). Adjust L_{14} , L_{15} and L_{16} to obtain this response. L_{14} and L_{15} together produce a lop-sided sound i.f. pass-band shape — with

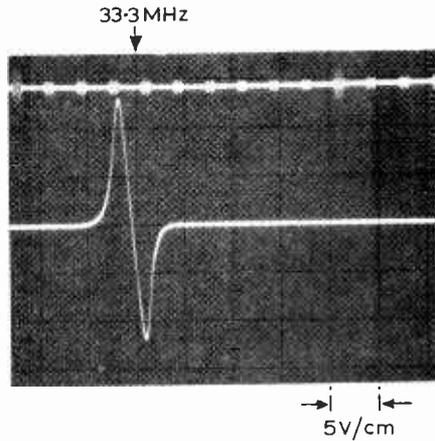


Fig. 21. Sound/a.f.c. discriminator S curve at L_{18} output test point.

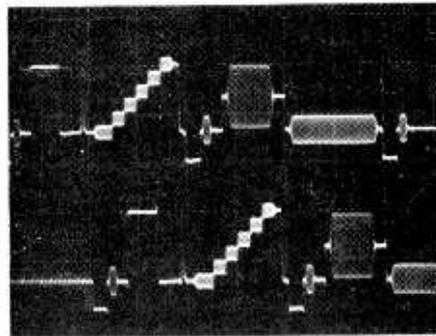


Fig. 22. Insertion test signal (i.t.s.) waveforms as generated (top), and as received showing added distortion (bottom).

greater response at low frequencies — which counteracts the slope of the main i.f. circuits which affect the signal taken from L_{19} and L_{20} ; L_{16} fills in the dip around the sound carrier frequency at the pass-band centre. The dip is caused by stray-capacitance top-C coupling of the L_{14} and L_{15} circuits. In practice, the response shape in this region is relatively unimportant because signals within the band are clipped by the limiting action of Tr_{12} and Tr_{11} . The energy transferred by the circuit should be equally distributed on either side of the carrier frequency and this requires that the sides and skirts of the response curve, not the peaks, should be as symmetrical as possible about the carrier point.

10. Remove the added capacitor and the probe. Re-connect C_{44} to establish the circuit as in Fig. 2. Connect the probe via R_{103} and the test point provided to the junction of R_{54} and pin 6 of the L_{18} assembly to observe the discriminator response curve which ultimately should appear as in Fig. 21. To obtain this shape, first adjust L_{18} to set the S-curve centre exactly at 33.5MHz; accurate adjustment here is necessary because it determines the frequency point about which the a.f.c./tuner combination settles. Second, adjust L_{17} and L_{16} to obtain a symmetrical S-shape. The high peak-peak voltage of the curve, as illustrated in Fig. 21 (15 to 20 V), is

needed to give a sufficient amplitude of recovered audio — taken from the 100kHz middle region — and a wide a.f.c. range.

Beware of a possible measurement error which can occur and which might not be detected without advance warning. The error is caused by the phase-shifting effect at l.f. given by many oscilloscope a.c.-coupled X-drive circuits; it does not occur therefore, if the oscilloscope and the generator are d.c.-coupled throughout. If the applied frequency sweep is at a slow rate, and of saw-tooth form with a fast fly-back stroke, the displayed curve is effectively delayed along the frequency axis by the coupling and will therefore be artificially displaced with respect to either second-trace marker pips or the graticule scale, whichever is being used for measurement. This means that although the S-curve may apparently be set with its zero-crossing exactly at 33.5MHz, the actual setting will be different. In more comprehensive sweep generators, the sweep rate is arranged to be the same in both directions, and this usually results in a double response display showing two S-curves which are displaced by an amount which increases as the sweep rate decreases. The technique for correct adjustment using such equipment is to estimate a mean between the two curves and set the circuit accordingly. Failing this, i.e. when using one of the simpler types of sweep generator and a.c.-coupled oscilloscope, set the displayed curve symmetrically about the indicated carrier frequency — accepting any error which this introduces — and subsequently make compensating adjustment when setting up the a.f.c. system as described in step 20. Further small adjustment will be needed in any case at that point to compensate for the offset voltage created by the input biasing current to the SN72741P op-amp.

11. The information originally given in this step was transferred to Part 3 of the article where it appears in the section headed "Tuning-voltage supply arrangements". Also, Fig. 21 became Fig. 17.

12. Disconnect the oscilloscope probe from the discriminator (R_{103}) test point and transfer it to the IC_1 pin-4 test point, which is fed via a 1k Ω resistor as a protection because, if pin 4 is accidentally earthed, the i.c. would almost certainly be damaged beyond repair. Connect a suitable u.h.f. aerial to the tuner input. The display required is that of the i.t.s. (insertion test signal) waveform which is included in the television signal radiated by all stations in the U.K. on lines 19/332 and 20/333 of the field-blanking interval. The top trace of Fig. 22 shows this waveform as generated and the bottom trace is the received signal with distortion added by the transmitter and the tuner.

At this point, i.e. with the a.f.c. system inoperative, it may be necessary to

check the adjustment of the appropriate pre-set control to obtain a satisfactory display. There may also be some difficulty in obtaining a stable trace of the i.t.s. waveform. If so, a suitable triggering signal for the oscilloscope can be obtained from the sync separator circuit formed by Tr_{13} and Tr_{14} ; from the last-mentioned, a feed of inverted mixed sync pulses is made available via R_{105} which protects Tr_{14} from accidental damage. If the set-up procedure detailed here is being carried out at a time when a test card transmission is available, there should be no problem in obtaining a stable trace by means of the oscilloscope internal trigger signal.

As the a.g.c. circuit is not working, in addition to the pre-set tuning adjustment just mentioned, it will be necessary to set the tuner gain using the temporary divider circuit installed in step 4. To do this, first check that R_{78} is set to a minimum, ensuring that Tr_{17} is not conducting, then adjust the divider variable to give about 4 V at the i.f. a.g.c. injection point. It may also be worthwhile adjusting R_{83} , the r.f. a.g.c. pre-set control, to obtain optimum noise performance. Finally, by manually setting the tuning voltage, it should be possible to fit the received sound carrier precisely in the notch created by the $L_{19}/L_{20}/L_{21}$ circuit; if this is not done the displayed waveform will be obscured by a superimposed 6MHz fuzz.

13. The MC1330P (IC₁) tank circuit inductor L_7 must initially be adjusted to obtain maximum amplitude of the displayed signal and then more precisely for best possible linearity of the overall transfer characteristic by observing the 6-step staircase waveform of the i.t.s. (Because each staircase carries a block of colour subcarrier, it is necessary to imagine a sawtooth line running diagonally through each block, and make adjustments until this line is as straight as possible.)

Observe also the 10 μ s rectangular pulse to white level — the so-called luminance bar at the beginning of the line; an added criterion in the adjustment of L_7 is that overshoots should occur only at the bottom-left and top-right corners of the bar (compare the form of upper and lower traces in Fig. 22). Overshoot at these points is caused by h.f. signal components arriving early with respect to those at l.f. and is also the reason for the ringing in front of the 0.2 μ s (= 2T) sine-squared pulse which follows the bar; the effect is shown in more detail by the expanded waveform in Fig. 23. Correction for this type of distortion is obtained by adjustments to be made in step 15.

14. Transfer the oscilloscope probe to the base of Tr_4 and then tune L_8 for minimum 6MHz "fuzz". To do this effectively, it is helpful to de-tune the receiver slightly, using R_{93} or R_{96} as appropriate, to temporarily upset the notching conditions mentioned at the

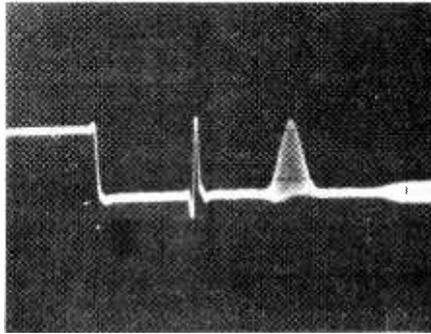


Fig. 23. Detail of 2T and 10T i.t.s. pulses showing effect of gain and delay inequality distortion.

end of step 11; the displayed signal then contains a larger sound-carrier component which makes it easier to check the effect of tuning L_9 .

15. Connect the probe to the output of the video strip, i.e. to the 75ohm output terminal. This will allow adjustment of the group-delay equalizer. The curves in Fig. 11 show that in this circuit the first stage L_{10}/L_{11} corrects for delay difference between the lower and middle video frequencies whereas the L_{12}/L_{13} stage has its main effect at the top end of the band. Adjustment of the two pairs of inductors is best carried out by inspection of the first i.t.s.-line waveforms. Initially, L_{10} and L_{11} are tuned for minimum overshoot on the luminance bar corners (see step 13), and to reduce ringing before and after the 2T pulse. Figs. 24(a) and 24(b) are expanded i.t.s. waveform traces which, in comparison with Fig. 23, illustrate the improvements in delay response typically effected by these adjustments. Two oscillograms are given — taken with the same tuner tuned to different channels — to show that the transmitted signal itself has differing imperfections such as can be seen in the examples on inspection of the trace shape around the bar corners and on either side of the 2T pulse.

Set the L_{12}/L_{13} stage for best symmetry of the 1 μ s (= 10T) chrominance-plus-luminance pulse, between the 2T pulse and the staircase in the waveform, illustrated in more detail by the expanded traces of Figs. 24(a) and 24(b).

When adjusting for symmetry, ensure that the pulse base is as flat as possible; specifically, L_{12} and L_{13} are tuned so that any ripples present in the base line (i.e. departures from the blanking-level line as seen in the Fig. 23 example) are reduced in amplitude, and those remaining are disposed symmetrically about the pulse-base centre, as in Figs. 24(a) and 24(b). Having achieved best symmetry, even better flatness can sometimes be obtained by adjusting the variable resistor in the series-tuned circuit which is optionally connected across R_{25} in the Tr_4/Tr_5 amplifier stage; an improvement of 1 to 2dB in chrominance-luminance gain inequality — which shows up as a symmetrical bump or dip in the pulse base — should be possible.

16. It may be necessary to adjust L_9 to reduce the amount of colour subcarrier second harmonic (8.866MHz) present in the tuner output. Do this by inspecting the 14 μ s block of 100% amplitude subcarrier (often called the chrominance minibar) which occupies the first half of the second i.t.s. line on lines 20 and 333. Make the subcarrier sit symmetrically about the 50% luminance pedestal which carries it. Ideally, the block should also extend fully between blanking and white level; however, if there is a difference in circuit amplification between upper and lower halves of the video band — i.e. chrominance-luminance gain inequality — which remains even after the step 14 adjustments, then L_9 must be set simply for best symmetry of the chrominance minibar. This setting is important because an unfortunate side-effect of the group-delay equalizer will be to increase asymmetry of the chrominance component if this contains an appreciable amount of second harmonic.

Step 16 completes the adjustment of inductors in the circuit. The final processes in the line-up procedure are concerned with the a.g.c. and a.f.c. systems.

17. The a.g.c. buffer amplifier, Tr_{13} , should receive a video signal of 4 V pk-pk from the Tr_4/Tr_5 stage. If neces-

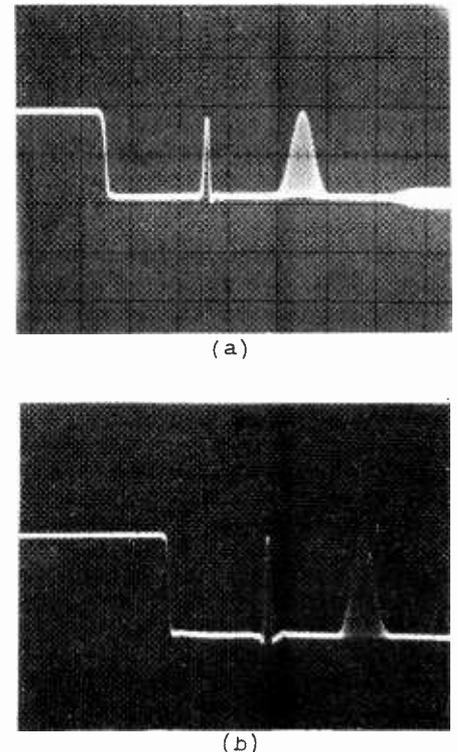


Fig. 24. Distorted 2T and 10T pulses mainly corrected by tuner group-delay equalizer but comparing remaining distortion caused by different transmitter characteristics.

sary, arrange this by means of the temporary a.g.c. divider variable; also, set the blanking-level voltage between 15 and 15.7 V by adjusting R_{19} in the supply voltage feed to IC_1 (MC1330). The requirement here is for D_9 to slice the picture component just above blanking level. To check that this slicing action is correct, connect the oscilloscope to the Tr_{13} emitter (R_{104}) test point provided and observe the i.t.s. staircase waveform in which slicing should occur between the second and third stairsteps. In practice, because the component called for in the D_9 position has a zener-point spread quoted from 15.2 to 16.9 V — for a current of 1mA — adjustment of R_{19} will also be necessary to create the required conditions for the zener diode actually being used. As a simplifying alternative, D_9 could be omitted and slicing will then be achieved by ordinary potential division in the remaining circuit if R_{67} is changed to 5.6k Ω . In reception conditions where aircraft flutter is a particular problem, however, the stabilizing effect of the zener is of such benefit that it is worth retaining.

18. Use the oscilloscope to check the timing and size of the sampling pulses fed to the gate of the f.e.t., Tr_{16} . These should be of about 3 μ s duration and should extend between 0 V and the voltage appropriate to video blanking level in the signal appearing at the source; a typical amplitude is 15.5 V.

19. Reconnect R_{74} ; disconnect "a.g.c. test" divider. The threshold of a.g.c. action is controlled by Tr_{17} emitter potential, i.e. it depends on the setting of R_{78} . However, the overall requirement here is to obtain optimum r.f./i.f. signal conditions by setting the a.g.c. crossover — using R_{83} to determine Tr_{18} base bias — so that there is minimum buzz on sound consistent with minimum video noise. The last-mentioned can be observed either by using an oscilloscope display of the tuner output signal waveform, or by viewing appropriate areas of the resulting picture on a television screen. Captions are best used for such inspection because some programme signals, particularly those originating at outside broadcasts, are themselves affected by noise and thus

confuse adjustment. Ref to Fig. 13 in part 2, where comparison of curve (a) with curve (b) gives the conditions which obtain with maximum i.f./r.f. a.g.c. overlap and (b) compared with (c) shows minimum overlap. The practical compromise will, of course, be somewhere between these two limits.

20. To set up the a.f.c. system, first with a.f.c. off and the relevant station-selection buttons pressed in sequence, check that the settings of R_{90} , R_{93} , R_{96} and R_{99} give as nearly as possible correct tuning for the chosen stations.

Accurate manual tuning is best achieved by connecting the oscilloscope to the MC1330P pin-4 test point via R_{102} and observing each selected transmission, particularly checking for equality of amplitude between the 2T pulse and luminance bar and for absence of 6MHz "fuzz". Now switch a.f.c. on and slightly re-adjust the core of L_{18} if necessary to correct for any change in tuning caused by spurious a.f.c. error signals which may occur (for reasons already discussed in the note to step 10). By checking again the output i.t.s. waveform and setting L_{18} for minimum 6MHz component, the sound carrier is accurately positioned at the zero-crossing point of the discriminator S curve. After this re-adjustment of L_{18} remember that it is most important to fix the core firmly (use p.t.f.e. tape or elastic band) to prevent movement and the resulting disturbance in these critical tuning conditions. Note that, with the a.f.c. switch off, the f.m. de-emphasis time-constant is incorrect because R_{62} and R_{61} are out of circuit. The effect of this error is too small to be of any consequence and will certainly not be detected in the sound output.

Sound-only tuner line-up

Line-up of the sound-only tuner is a much simpler process than for the full circuit because there is no need for care in the adjustment of video i.f. pass-band shape, the position of notches or the phase-cancellation point. Thus, after


checking that direct voltages agree with the appropriate values given in the table, the following operations should be sufficient to obtain a satisfactory sound output. It is assumed initially that a signal generator capable of giving a single-frequency output in the 30 to 45MHz range is available; subsequently, an alternative method is suggested for use in the absence of a generator.

1. Set the circuit gain provisionally by adjusting the a.g.c. test divider variable to give a +4.5 V input at point D in Fig. 2.
2. Panel-mounting variables of 2k Ω are not readily available and as this resistor is now required as a permanent control, it could be changed to one of 5k Ω . The two fixed resistors in the divider chain must then also be changed to 10k Ω (at the top) and 2.2k Ω .
2. Loosely couple the signal generator to the u.h.f. module i.f. injection point in the manner already explained in step 8 of the full line-up. Set the frequency of the injected signal as accurately as possible to 33.5MHz.

3. Connect a voltage-measuring instrument to the R_{64} test point to inspect the output of the discriminator circuit. Ideally, an oscilloscope or an electronic voltmeter should be used here because it is a high-impedance point and therefore cannot accept additional loading without confusing change in the measured parameters. Failing the ideal, a low-current meter such as an Avo Model 8 or similar can be used, connected between the test point and the tuning-voltage supply — point F in Fig. 2 — but remember that the indicated voltage only represents the true circuit output when it is at or near 0V, i.e. when the meter is taking no current.

4. Adjust the core of L_{18} to find the sharp negative and positive voltage peaks which show the limits of the S curve. The voltage peaks will probably not be equal about zero, because the overall amplitude-frequency response of the preceding band-pass circuits has yet to be optimized, and the maximum values obtained will depend on the extra loading involved. If an Avo 8 is being used, the maxima will be in the region of ± 4.5 to 5V. Having located these

Fig. 25. Audio feed isolator circuit up to coax link is housed within tuner or receiver; circuit may be live up to isolator. Pins are numbered looking from top.

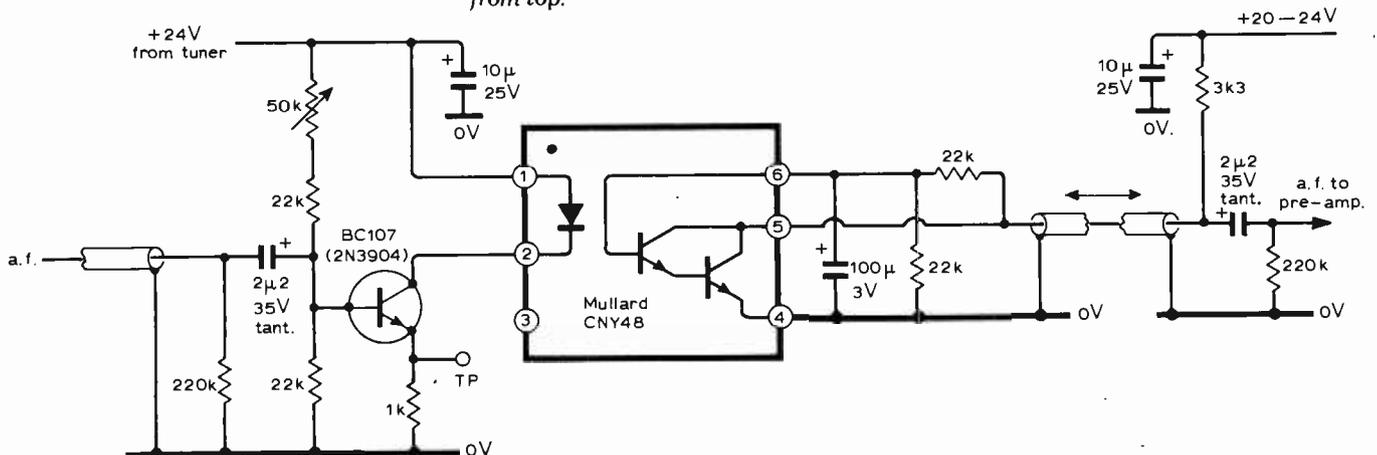

positive and negative peaks, set L_{18} core so that the discriminator output is at 0V between them for the injected sound i.f., of 33.5MHz.

5. Remove the generator coupling and connect an aerial to the tuner. With the a.f.c. switch off, manually set the tuning voltage fed to the u.h.f. module so as to receive a transmission. The discriminator output should remain at about 0V and, as a check on the L_{18} setting just made, the tuning voltage can be varied slightly to sweep this output through to its positive and negative limits. By listening to the incoming programme the i.f. circuits can be adjusted, tuning for maximum sound level. Start with the high-Q coupled pair L_{14}/L_{15} , followed by L_{17} , L_{16} and finally the i.f. coil in the ELC1043 module. With these circuits roughly set in this way, final adjustment is made as follows. Reduce the r.f./i.f. gain by increasing the a.g.c. voltage. With the narrow-band sound carrier signal now at lower level, the wide-band circuit noise has greater effect and the i.f. coils can be re-adjusted, this time seeking best signal-to-noise ratio. This occurs when the overall pass-band is as narrow as possible consistent with proper recovery of the modulation.

6. With the circuit response set as described, the a.g.c. voltage is then reduced, allowing the gain to rise with a consequent decrease in the audible noise. The programme sound should

first rise and then stay at the same level after the onset of limiting. The change in a.g.c. is continued until just beyond the point where no further difference in noise level can be detected. The limiter, of course, maintains a reasonably constant level of audio r.f. carrier against varying r.f./i.f. signals. The optimum degree of limiting is 15 to 18dB; if more is used, the effective sound i.f. bandwidth (Fig. 20) increases with a consequent worsening of signal-to-noise ratio. For even greater amounts of limiting, there is also the possibility that energy from the video luminance or chrominance sidebands (see the spectral distribution shown in Fig. 17), or even from the lower adjacent-channel transmission, could intrude into the widened passband and add unwanted background to the programme signal.

The remaining adjustment is the tuning of the adjacent-channel traps, L_1 and L_3 , and this ideally requires the use of a signal generator. Fortunately, in most locations, adjacent-channel interference on sound is not a problem and these circuits can normally be omitted.

If a signal generator is not available for establishing the correct tuning point for L_{18} as in steps 3 and 4 above, this can be achieved by listening to the noise generated in the r.f./i.f. circuits. With no aerial connected and as much gain as necessary, the sound output will be white noise at a low level. As L_{18} core is adjusted, the sound noise level

increases; when at maximum, the noise energy accepted through the i.f. pass-band is being demodulated along the greatest discriminator slope — the S curve is then positioned with its centre in the middle of the i.f. band. Once the discriminator is set in this way, the rest of the line-up then proceeds as explained in steps 5 and 6.

The i.f. response is maintained to 10Hz and tuner output-signal frequencies as low as this could be something of an embarrassment if the sound equipment being used is capable of fully responding to them. To prevent problems arising, therefore, it would be worthwhile feeding the audio signal via an op-amp connected as an active high-pass filter cutting off sharply at, say, 20Hz. If this extra circuit is connected in the pre-amplifier then it would also take care of unwanted high-amplitude i.f. signals from other possible sources, e.g. pick-up handling noises and d.c. thumps from f.m. tuners when station re-selection takes place. Suitable circuit for such filters, including design calculations, have appeared in several recent articles (e.g. Active crossover networks, *Wireless World*, November, 1974).

Audio connection through coupler

Picture display equipment can be either of the monitor type such as the Decca model CS2240L or modified conventional receiver. The first represents the

Performance

Video bandwidth: see Fig. 12.
Pulse & bar performance: see Fig. 23.
Chrominance/luminance delay inequality: see 10T pulse, Fig. 23.
Signal-to-noise ratio: see Fig. 25.
Differential gain: 3%.
Differential phase: $\pm 3^\circ$.

Performance of sound-only tuner

Harmonic distortion: -50dB (0.3%)
(Figure limited by u.h.f. modulator)
Overload margin: 20dB over 0.5V r.m.s.
for t.h.d. -40dB (1%)
Signal-to-noise ratio: 50dB for ± 50 kHz
Amplitude response: 20Hz to 20kHz
 ± 0.5 dB

Performance using coupler

11mA standing current (50k Ω pot. at min)
Harmonic distortion: -46dB (0.5%)
Overload margin: 20dB
Signal-to-noise ratio: -50dB
Amplitude response: as above

6.5mA standing current (50k Ω pot. at half)

Harmonic distortion: -40dB (1%)
Overload margin: 14dB
Signal-to-noise ratio: -54dB

Differential gain results in colour subcarrier amplitude change with luminance level, seem as colour saturation as brightness changes. 14% is just perceptible. Differential phase results in colour subcarrier phase change with luminance level, seen as hue/colour change. $\pm 25^\circ$ is just perceptible for delay-line PAL decoders (which convert phase errors into desaturation). $\pm 6^\circ$ is just perceptible for simple PAL decoders, used on some Japanese sets, and shows as a hue-colour change or alternate lines (Hanover bars).

In interpreting the performance figures given, remember that in television productions, sound is inherently at a disadvantage because the picture always takes precedence. Exceptionally, then, the ambient noise level at the source could be as high as -45 to -40dB with respect to the wanted signal.

To test the noise performance of the tuner, both varicap and mechanical versions were measured off-air using locally-generated signals (tested on empty lines 12 and 325 gated from field-blanking interval). The curves in Fig. 26 were plotted from the results of these tests and show that to take full advantage of the tuner's high performance, particularly its overall bandwidth capability, the r.m.s. carrier level at the aerial input should not be less than 1.5 mV. At the other end of the r.f. signal range, the Mullard data sheet on the ELC 1043 shows that an input level of 8mV gives 1% (40 dB) cross-carrier intermodulation, i.e. the spurious 1.57MHz signal caused by beating of sound and chroma carriers, which results in the annoying herring-bone patterning on the picture; a 1% level is, incidentally, just perceptible. For even larger inputs, there are the added problems of compression — Mullard quote 30% for a 15 mV r.m.s. input — and u.h.f. local-oscillator pulling.

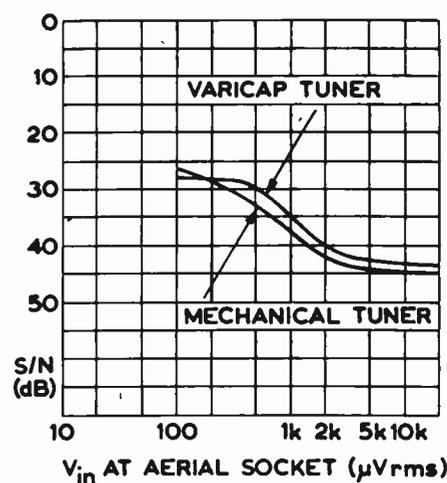


Fig. 26. Curves show satisfactory noise performance (on a "just perceptible" basis at 38dB) is obtained for inputs as low as 700 μ V at the aerial socket. Sound signal-to-noise ratio is better than 50dB over the whole range.

The narrow window of input levels to be aimed at is between 2 and 5 mV r.m.s. vision carrier. Obviously, proper measuring equipment provides the best means of checking that the optimum conditions obtain, but for home constructors a good indication of signal-to-noise performance can be gained by

ideal, not only because it is specifically designed to accept, and do justice to, a fully-corrected, colour-coded video signal, but because it is powered through a double-wound transformer, thus avoiding the interconnection difficulties associated with the live chassis common in domestic receivers. But the expense involved in buying specialist equipment of this sort makes it a daunting prospect, and the alternative idea of using a standard receiver is an attractive compromise despite the extra work needed in modifying the decoder and in making sure that the installation is safely isolated from the mains.


Assuming that an existing set is to be used, the problem of isolation mainly concerns the tuner outputs, because co-axial isolators for the u.h.f. aerial input are easily obtained — they are fitted to many commercial receivers not only to protect against mains voltages on the chassis but also against aerial static.

Considering first the video output feed, this necessarily requires a direct earth connection to the decoder and display circuits; there is no practical way of avoiding it, mainly because isolators currently available do not have sufficient bandwidth to handle video signals. The simplest solution here is to accept the fact that the tuner could be live and install it and its power supply with the rest of the TV equipment in the cabinet. This option obviously precludes the possibility of using the tuner

comparing the vision noise observed on electronically-generated captions against that on ordinary camera pictures. If the caption noise is noticeably less, then it shows that the receiving system is not introducing the majority of the noise.

To obtain a higher input level, better aerial or aerial siting is called for, or even investment in a mast-head amplifier such as the Antiference type MA102 with PU102 power unit, together costing £8 in mid-1975. A directional aerial is sometimes needed to reduce multipath effects which give rise to ghost images on the screen; if so, the incoming wanted signal might then be at too great a level and a co-axial attenuator (e.g. the Belling-Lee components with values of 3, 6, 12 and 18 dB) would be required. The caption-noise test can be used to ascertain optimum attenuation; tuner input should be reduced until noise on captions starts to increase, and then raised by 6 to 12 dB so that the applied level is within the recommended range.

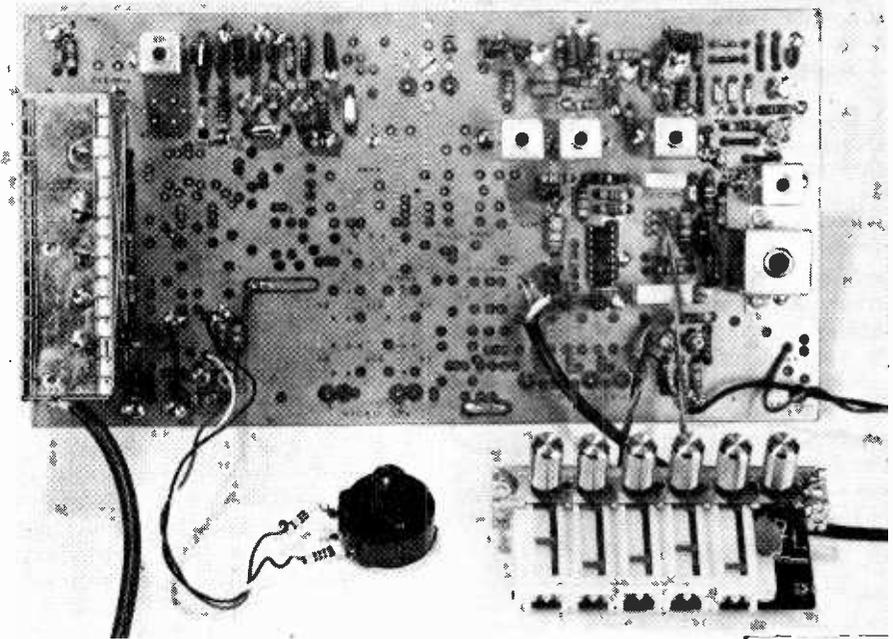Tests on sound signal-to-noise were also done, and the acceptable window of r.f. input level was much greater than for video. The test showed a ratio better than 50 dB over the range 100 μ V–10mV α , and worse than this only when the input sound carrier level was reduced below 100 μ V).



Sound-only tuner with alternative push-button tuning control.

as a sort of remote-control box, but is strongly recommended as the only way to ensure complete safety in operation.

Warning: never uncover the TV set chassis without first disconnecting it from the mains supply. If in any doubt about what is or is not safe practice, have the completed tuner installed by an experienced service engineer or seek advice from Manor Supplies.

The remaining connection to be made is the feed to the audio units and, for this, a reasonably straightforward isolating circuit can be built using a coupler (Fig. 25). These devices, called photocouplers, or optocouplers, provide an additional benefit in that, unlike transformers, they prevent the circulation of mains-frequency earth currents; low-level signal runs are thus better protected against hum interference. The component used in the circuit shown is the Mullard Darlington photocoupler CNY48 which provides input-to-output isolation up to 4000 volts.

The circuit must be installed with the tuner in the receiver cabinet. The BC107 transistor provides a current-source to the infra-red-emitting diode in the coupler. Both devices are fed from the tuner d.c. supply which, as already explained, could have its 0V rail at the full a.c. mains voltage carried through from the display-circuit earth. The Darlington pair in the coupler package receives d.c. via the audio co-ax inner from the pre-amp power supply, and will be free of mains connection.

Three of the circuit components are added at the pre-amplifier input to provide part of the collector load for the Darlington pair, to couple the audio signal and to keep a charge on the coupling capacitor so that d.c. surges and consequent loudspeaker thumps do not occur each time the TV sound output is selected.

The CNY48 gives a very reasonable performance as shown by the appended figures. The 50k Ω variable resistor allows adjustment of the diode standing current and is provided because there is some spread in the operating characteristics of couplers and the setting used will be a compromise between best signal-to-noise and least distortion. There have been reports which suggest possible ageing difficulties with these diodes, so note that the lower the standing current used, the less these ageing effects should be.

Literature Received

All published information on the Motorola M6800 microprocessor is now available from Celdis Data Centre, 37/39 Loverock Road, Reading.

Mark 3 Emicron geared motor units are described in a new publication from Emicron Industrial Devices Ltd, 9a Annette Road, London N7 6ET ... WW401

New and used test equipment is listed and described in a catalogue produced by Electronic Brokers Ltd, 49/53 Pancras Road, London NW1 2QB. The catalogue costs 50p or £1 for overseas readers.

Burr-Brown have sent us a leaflet on the Micromux data acquisition system, which consists of a 16-input, remotely-sited multiplexer and encoder, communicating with a central receiver by ordinary twisted pair. The leaflet is obtainable from Burr-Brown Ltd, Permanent House, 17 Exchange Road, Watford WD1 7EB ... WW402

Automatic inspection of printed-board assemblies is explained and its application in a variety of manufacturing situations examined in a new publication from Marconi Instruments "Getting to the point". Copies can be obtained from the publicity department, Marconi Instruments Ltd, Longacres, St. Albans, Herts. ... WW403

We have received from the IEE a list of available publications, including periodicals, conference publications, colloquium digests and many others. Marketing Department, Institution of Electrical Engineers, PO Box 8, Southgate House, Stevenage, Herts SG1 1HQ ... WW404

Circuit Ideas

MSF receiver using a tone decoder


Using a tuned aerial, preamplifier, and a Signetics tone decoder, type NE567V, the time signals broadcast on 60kHz from MSF Rugby may be detected. The tone decoder is a phase locked loop device containing an oscillator which, when set to 60kHz, will lock to an input signal greater than 20mV r.m.s. at this frequency causing the output to switch rapidly from high to low.

The time signals, which are directly related to the national time and frequency standard, consist of 100ms interruptions in the r.f. signal each second, with a 500ms break at the minute mark; the call sign is given twice just before the hour. Depending on the application, receiver design is a compromise between wide bandwidth with accurate resolution of the carrier on/off transition, and narrow bandwidth with good signal to noise ratio. Conventional heterodyne or "straight" receivers with b.f.o. may render the signal audible and the ear can assist in noise discrimination, but this method gives the time signals as pauses in a tone. This circuit produces the opposite situation where the rectified output is inverted and used to switch an audio oscillator so that pips may be heard instead. The tone decoder is well suited to this application because, having adjustable bandwidth, it will accept a large dynamic range of

Current limited stabilizer with switch-down

The modification suggested by P. C. Bury (WW July 1974, page 239) to the circuit originally due to A. E. T. Nye (WW June 1973, page 285) gives fold-back characteristics and, as he states, is probably the most generally useful. If, however, a switch-down action is required, it is possible to achieve this by a similar modification in which a p-n-p transistor is connected as shown. This will reduce the output current to a low value once the limit is reached, and will hold it down until the output load resistance rises to several thousand ohms. Action is similar to that of the additional diode except that when the limit is reached, the collector of Tr_3 draws current from the resistor R which lowers the effective current limit so that a regenerative process suddenly reduces the output voltage to a low value.

If a reset switch is needed a

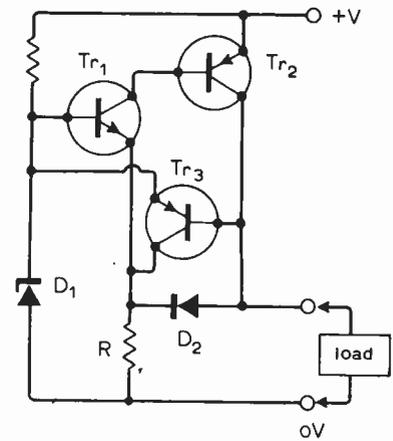

normally-closed push button switch in the collector of Tr_3 may be used, with the advantage that fold-back limiting remains in action through the Tr_3 base-emitter diode during the switch on process.

R. G. T. Bennett,
Christchurch,
New Zealand.

input signals, and avoids the need for tuned r.f. or i.f. stages.


The aerial consists of a $7 \times \frac{3}{8}$ in. ferrite rod fully wound (about 360 turns) with 26 s.w.g. enamelled copper wire, tuned with a total of about 1900pF. A 40 turn step-down transformer wound at one end feeds the two stage amplifier. With a 9V supply the amplifier has a gain of 4700 giving an r.f. output of 400mV r.m.s. at 140km from the transmitter. The zener diode improves oscillator stability with voltage and permits the supply to exceed the 9V maximum of the tone decoder.

Frequency selection of the tone decoder is by means of R_1 and C_1 which have values of 16.6k Ω and 1000pF for 60kHz. The bandwidth may be selected by C_2 and C_3 , but this is complicated by the input stage limiting of 200mV, and the fact that, in this

application, the time markers are given when the r.f. signal goes off. With $C_2 = 10nF$ and $C_3 = 100nF$, and an input signal of 400mV, the output change follows the r.f.-off by 4ms and the r.f.-on by 1ms without any output chatter. By reducing the r.f. signal to between 20 and 100mV, both off and on delays are less than 2ms. The output may be taken from pin 8 and a suitable load resistor to switch an audio oscillator or drive an l.e.d. as shown.

The complete circuit may be assembled on Veroboard, taking care to minimise coupling between the amplifier and the tone decoder by earthing all unconnected copper strips, and keeping the aerial at least 1m from the unscreened circuit.


D. A. Bateman,
Crowthorne,
Berks.

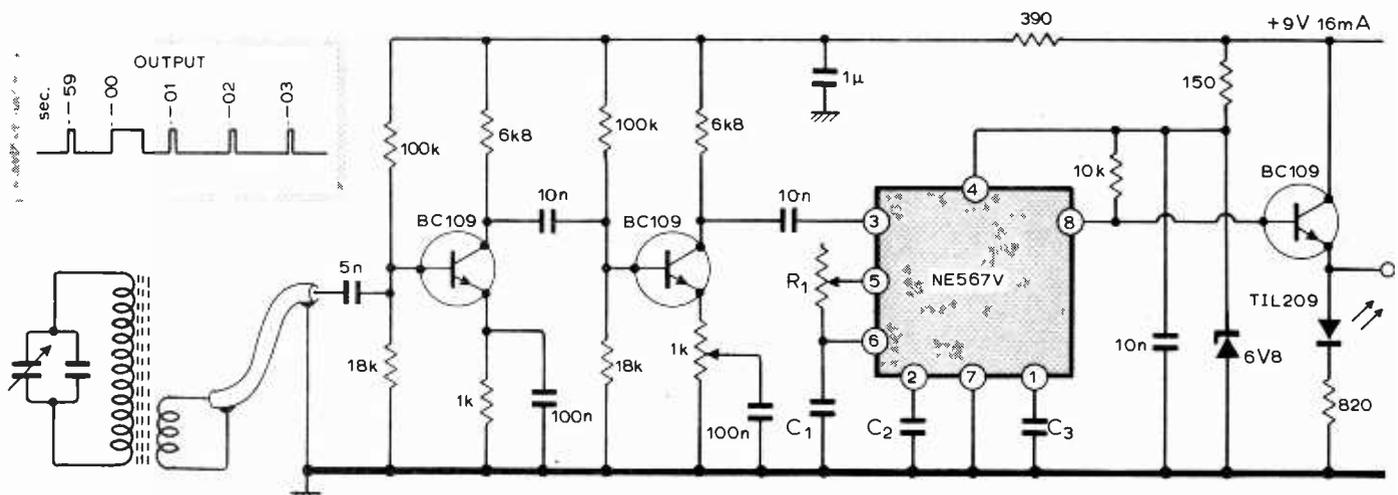

Synthesizer chord-maker

To play chords on a synthesizer, v.c.os run from a common voltage source plus the appropriate off-sets to each oscillator. To do this all the oscillators must be matched to the same voltage/frequency curve. A more satisfactory solution is to use a configuration similar to that shown in the diagram. The advantages are that only a single v.c.o. is necessary in order to get an octave of notes. The circuit is basically a phase-locked loop frequency multiplier with the divide by N section a master divider. Unfortunately the range is limited by the phase-locked loop locking range.

H. A. Thomas,
Hatfield,
Herts.

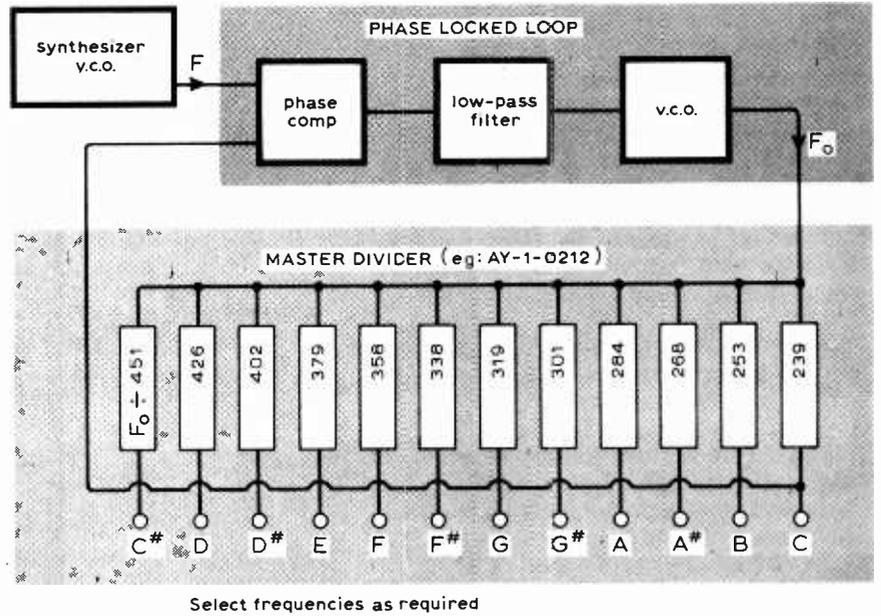


Resistance modulator or periodic switch

This circuit can be used either as an a.c. switch which makes and breaks for approximately equal times at an adjustable frequency, or to produce a modulated resistance at an adjustable frequency. The interesting feature is that both the oscillator and the switch can be made using a single CD4007 c.m.o.s. integrated circuit. This i.c. contains two complementary pairs of transistors, and a complementary transistor inverter. Transistors Tr_1 and Tr_4

are used as a normal inverter. Transistor Tr_5 has a $10k\Omega$ load and forms a single ended output inverter. Transistors Tr_2 and Tr_6 are connected back-to-back to form a transmission gate. The input and output of inverter $Tr_{1,4}$ drive the gates of Tr_6 and Tr_2 respectively to obtain correct operation of the transmission gate, which acts as an a.c. switch. The inverter is also used, in conjunction with the inverter Tr_5 , to form an astable oscillator whose frequency is controlled by the time constant CR. Because the two inverters are dissimilar and do not necessarily switch

at 50% of V_{DD} a mark-space ratio of unity cannot be guaranteed; but the prototype, which ran at switched frequencies of 10, 30 and 50Hz had almost equal on and off times. To obtain a modulated resistance characteristic, resistors R_1 and R_2 are connected, as shown. The resistance seen at the output terminals is then modulated between $(R_1 + R_2)$ and R_1 , at the frequency of the oscillator.

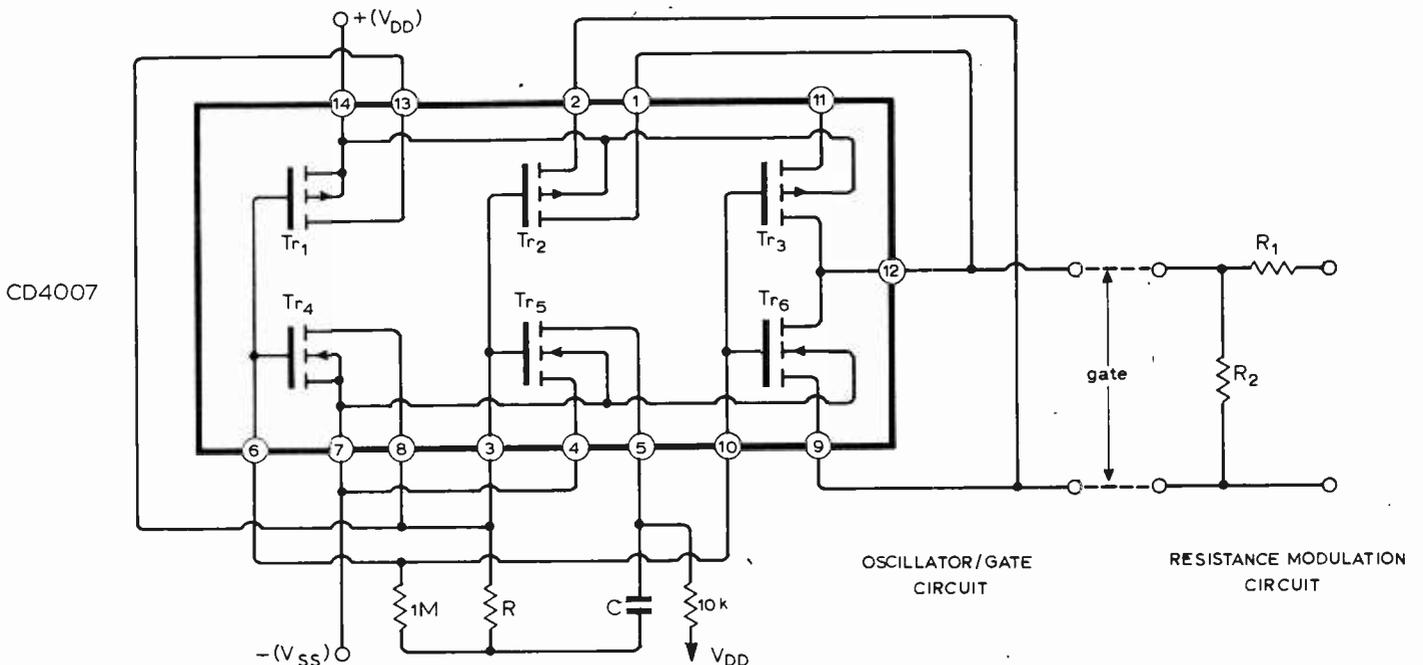D. K. Fryer,
Hydraulics Research Station,
Wallingford.



L.e.d. clip indicator


The circuit seen here was devised as a simple and economical way of detecting the clipping point in audio amplifiers. The values shown are suitable for a 50W power amplifier. Transistor Tr_1 is normally turned hard on, because of the d.c. potential at the output, and Tr_2 , with the l.e.d., are turned off. When the collector-emitter voltage of the lower output transistor approaches saturation (i.e. it drops below about 5V) Tr_1 begins to turn off, C_1 charges up through D_1 and the l.e.d. turns on. The attack time of the circuit is about 3ms, determined by R_3 and C_1 , which approximates to the time taken by the ear to first detect clipping distortion in a good amplifier. The decay time of approximately 50ms is determined by C_1 and R_4 in parallel with βR_5 , where β is the current gain of Tr_2 . 50ms is long enough to make a single 3ms overload transient visible but provides adequate resolution to detect more severe overloads where several pulses are clipped in rapid succession.

Because the circuit is referenced to the negative power rail, the detection level is substantially independent of fluctuating supply voltages, hence the circuit works equally well for instantaneous, music or continuous signals.

Transistors Tr_1 and Tr_2 should have a voltage rating of at least 0.5 supply V for dual-rail amplifiers or at least supply V for single-rail amplifiers. With the last mentioned, Tr_2 and the top of R_3 must be connected to the positive power rail.

If two indicators are used, one for the negative rail as shown plus one referenced to the positive rail using p-n-p transistors, the circuit can be used to detect short-circuited output transistors because one l.e.d. will be permanently on.

J. Dawson & K. Northover, Cambridge.

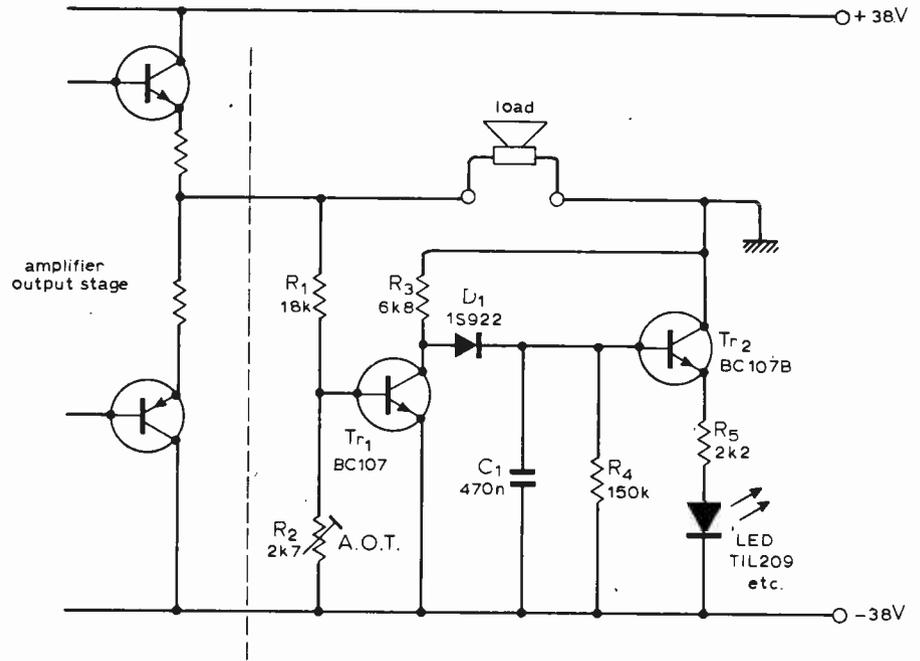


Sequence generator for radio control

This coder generates a sequence of pulses suitable for the blip-and-hold actuators used in radio control. During the stand-by period, the oscillator formed by NAND gate 1 runs continuously at a frequency of 0.5Hz which can be adjusted by altering C_1 or R_1 , and the four outputs from the 7490 are held at zero by the presence of 5 volts on pins 2 and 3. If push-button A is depressed the voltage on pins 2 and 5 falls to zero and the 7490 is clocked by the negative edge of the oscillator waveform. When a level 1 appears at outputs A and C

concurrently, transistor Tr_1 will be forward biased and the output of NAND gate 2 will fall to zero. This will stop the oscillator and thus outputs A and C at 1. If the transmitter modulator is driven from output A the signal will consist of two blips of 1:1 mark space ratio by a continuous transmission until button A is released. On release of button A all outputs from the 7490 will again fall to zero. By suitable arrangement of switches and gates a multitude of blip-and-hold combinations can be achieved.

G. D. Southern, Cronton, Nr Widnes.

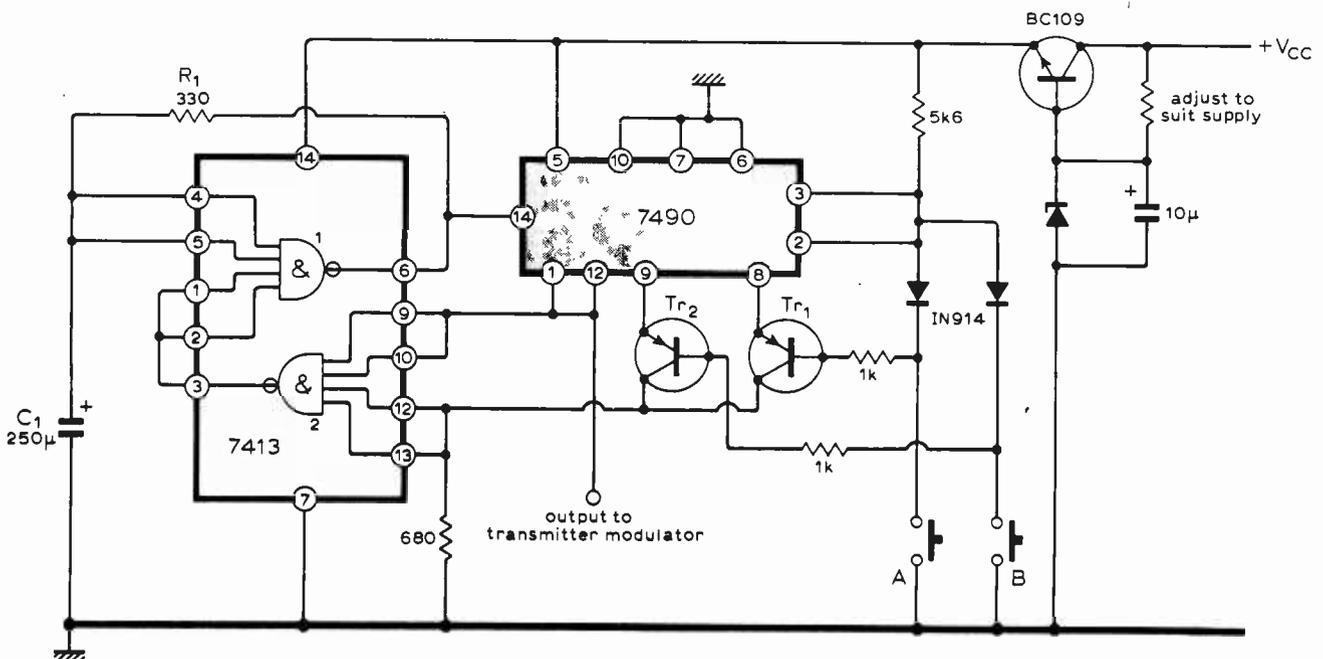

Transmitter power amplifier design — 4

Conclusion of the practical circuit described in November; also different strip-line constructions

by W. P. O'Reilly, M.Sc., M.I.E.E.

The Plessey Company Ltd

A spectrum analyser is extremely useful when the first prototype of a new design is being evaluated. The harmonic content of the output signal and any tendency for spurious or sub-harmonic instabilities under conditions of varying supply voltage, drive level or load mismatch may be monitored.

In the design which has been described stability is ensured by careful supply line filter design and the use of low-Q base return chokes. This ensures that a low source impedance is presented to the transistors at frequencies well below the operating band where the gain is much higher. Due to the inherent inductance of the low-value resistors R_4 and R_6 very little gain at v.h.f. is sacrificed.

Considering the amplifier's input/output characteristic shown in Fig. 5 of the previous article, a saturated power approaching 25W is obtained for a total current consumption of 3.3A at 13.6V. This corresponds to an overall efficiency in excess of 50%. The collector efficiency of the output stage is over 75% when operating into a matched load. As with most mobile radio transmitters the possibility of a mismatched antenna must be considered. A prototype amplifier has been operated for prolonged periods into both open and short circuit loads at 10, 12.5 and 14.5V supply without damage. The power transistors will only tolerate these stress levels if they are properly mounted on an adequate heatsink. The maximum safe drive level is 200mW. Excessive drive could damage the input device and will reduce the tolerance of the amplifier to load mismatch conditions.

At full drive the input v.s.w.r. is typically 1.3:1 and, due to the Class B bias of the input stage, the input impedance does not vary rapidly when drive level is reduced as would be the case if a Class C design were employed. Second harmonic output is -35dB relative to the fundamental, while third and higher harmonics are below -60dB. These levels should not represent an interference hazard when an antenna matching filter is in use. It is normal to

employ a bandpass filter common to both receive and transmit circuits and several suitable designs have been published.^{1,2}

When operated with the correct drive level and supply voltage a power amplifier of this type has a predicted mean - time - between - failure (m.t.b.f.) in excess of 100,000 hours. (More than ten years of continuous operation.) The amplifier is thus essentially free from routine maintenance.

The power amplifier described makes use of microstrip transmission-lines. Other useful v.h.f. components can be made using strip-lines of different constructions and some of these will now be discussed.

Tri-plate striplines

Fig. 1 shows a transmission line consisting of a three layer sandwich in which

the inner "live" conductor is equally spaced, by means of dielectric sheets, between two conducting earth planes. In this tri-plate structure the field is entirely contained within the dielectric and so, unlike the microstrip transmission lines previously considered, a true transverse electromagnetic (t.e.m.) wave can exist on the tri-plate line. The guided wavelength, λ , is no longer dependent upon the characteristic impedance of the line, but is simply related to the free-space wavelength, λ_0 by

$$\lambda/\lambda_0 = 1/\sqrt{\epsilon_r} \quad (1)$$

where ϵ_r is the relative permittivity of the dielectric. The earth planes above and below a tri-plate stripline act to confine the field. As a result tri-plate is more suitable for filter applications

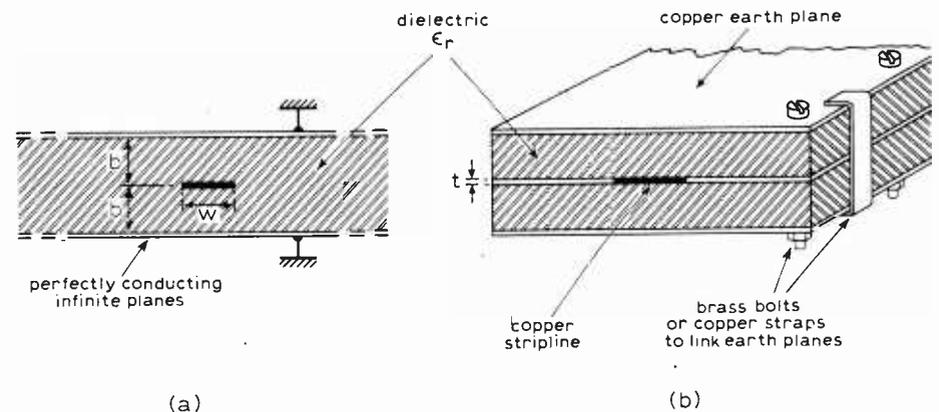


Fig. 1. Tri-plate stripline (a) ideal tri-plate line (b) practical realization.

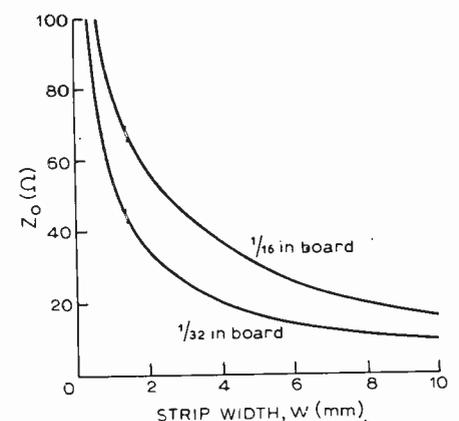


Fig. 2. Characteristic impedance of tri-plate striplines in p.t.f.e./glass dielectric ($\epsilon_r \approx 2.5$).

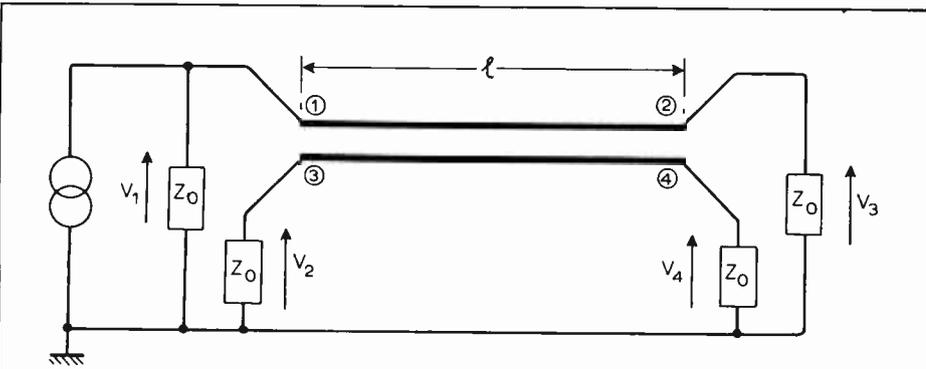


Fig. 3. Coupled transmission lines.

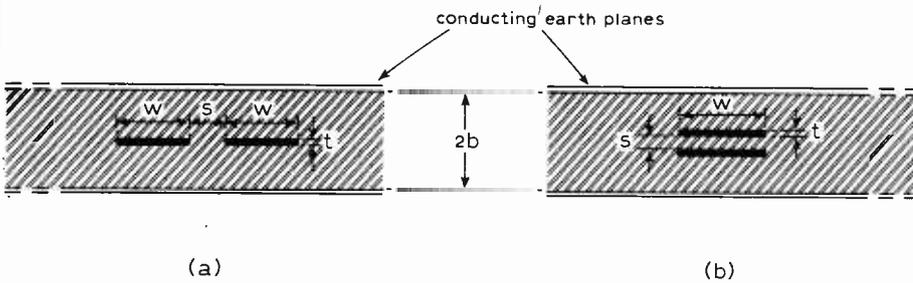


Fig. 4. Tri-plate coupling structures (a) edge coupling (b) broadside coupling.

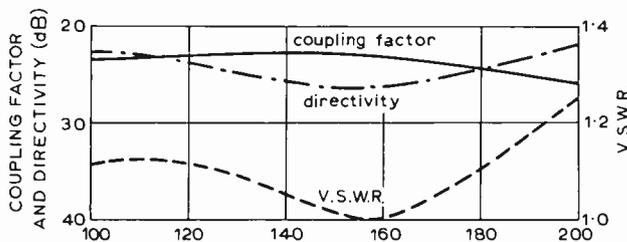
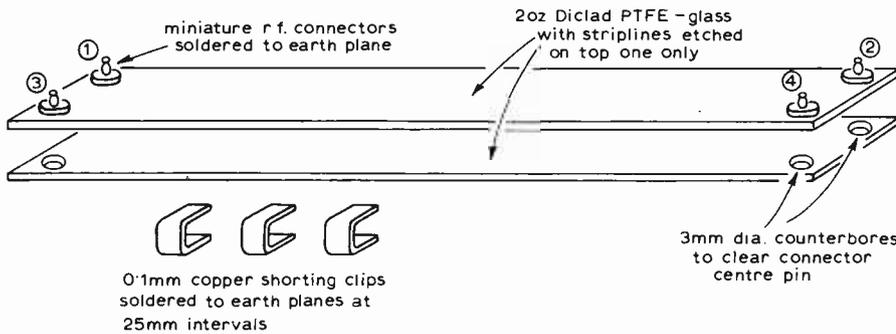
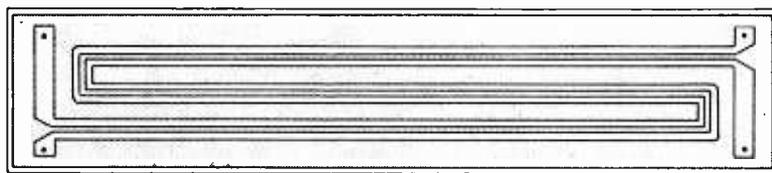


Fig. 5. Tri-plate 26dB directional coupler (a) construction (b) performance curves.

requiring a high degree of stopband rejection.

The characteristic impedance of a low impedance tri-plate line in a dielectric of relative permittivity ϵ_r is given by reference three and is shown graphically in Fig. 2 for two common dielectric layer thicknesses. Cross-reference to Fig. 7 in Part 2 of this series reveals that tri-plate conductors of a particular width yield a lower characteristic impedance than would be obtained with a similar width microstrip conductor. This and also the shorter guided wavelength in tri-plate structures tend to compensate for the increase in size and weight resulting from the extra layer of dielectric. Both microstrip and tri-plate striplines are used in modern communications equipment, the choice for any particular application being determined by performance requirements.

Coupled striplines

Many v.h.f. components make use of the phenomenon of backward-wave directional coupling between striplines which are in close proximity to one another. Fig. 3 shows a pair of coupled transmission lines of length l . The electrical length of the lines is given by

$$\theta = 2\pi l / \lambda \quad (2)$$

It can be shown that if all four ports are terminated in the system characteristic impedance, Z_0 , the coupled voltage at port three is given by

$$V_3 = V_1 \cdot \frac{j k \sin \theta}{\sqrt{1 - k^2} \cos \theta + j \sin \theta} \quad (3)$$

The voltage at the output port on the main line is:-

$$V_2 = V_1 \cdot \frac{\sqrt{1 - k^2}}{\sqrt{1 - k^2} \cos \theta + j \sin \theta} \quad (4)$$

In an ideal coupler no output appears at port four, which is termed the isolated port. In practice due to manufacturing imperfections there is always a small output at port four, and the expression $20 \log (V_3/V_4)$ is termed the directivity of the coupler (in dB). Constant k is the coupling factor, generally expressed in dB, and is related to the degree by which the characteristic impedance of one line is affected by the presence of the other. This inter-dependence is characterised in terms of the odd mode and even mode impedances, Z_{oe} and Z_{oo} , of the lines. Z_{oo} is the impedance of one line when the adjacent line is at the same potential but 180° out of phase, and Z_{oe} is the impedance of one line when both lines are at the same potential in phase and magnitude. The coupling factor and system characteristic impedance are related to the even and odd mode impedances by the relationships:-

$$k = \frac{Z_{oe} - Z_{oo}}{Z_{oe} + Z_{oo}} \quad (5)$$

$$Z_0 = \sqrt{Z_{oe} Z_{oo}} \quad (6)$$

Once the required values of even and odd mode impedances are known the physical dimensions of a particular line structure may be calculated.⁴

It can be seen from equations (3) and (4) that the coupling reaches a maximum when the length of the coupled lines is an odd multiple of $\lambda/4$. The phase difference between the outputs of the main line and coupled line is 90° at all frequencies.

Two commonly used arrangements of tri-plate coupled striplines are shown in Fig. 4. The edge-coupled structure is suitable for coupling factors up to 10dB. For tighter coupling the spacing, s , becomes very small and presents manufacturing difficulties. The broadside coupling structure of Fig. 5 (b) is more suitable for producing close coupling such as in two-way equal power (3dB) dividers.

Power measurements

It has been seen that a directional coupler may be used to bleed off a sample of the signal flowing in one direction along a line. If a pair of similar couplers are connected with their main lines in series it is possible to monitor both the forward power component and reflected power component on the main line. Such an arrangement used in the output circuit of a transmitter can provide useful information both for tuning an antenna and for controlling the output power to a safe value for the

A member of the *Wireless World* staff has made available a printed circuit board for the stripline r.f. power amplifier. The board, which measures approximately 23×11 cm is supplied roller-tinned and drilled. The one-off price is £4.50 inclusive. All cheques and postal orders should be made payable to M. R. Sagin and sent to 11 Villiers Road, London N.W.2.

particular value of load mismatch present. The net output power is simply the forward power less the reflected power. Thus if the coupling factors are accurately known this arrangement may be used to produce an accurate wattmeter. A dual directional coupler may also be used to measure reflection coefficient or v.s.w.r., since

$$\rho = \frac{V_R}{V_F} \text{ and v.s.w.r.} = \frac{1 + |\rho|}{1 - |\rho|} \quad (7)$$

The measurement of r.f. voltage involves the use of specialized equipment and so it is normal to employ diode detectors with the couplers. The d.c. output of the detectors may then be processed to provide $|\rho|$ and v.s.w.r. indications. Coupling factors of between 20dB and 40dB are suitable for

this application. Fig. 5 (a) shows the construction of a 23dB directional coupler suitable for use in the two-metre band. The characteristic impedance is 50 ohms. This coupler is manufactured from 0.8mm (1/32 inch) di-clad p.t.f.e. - glass material and uses edge coupling. The required dimensions are: conductor width, $w = 1.10$ mm; conductor spacing, $s = 0.70$ mm; conductor thickness, $t = .071$ mm (2oz/sq. ft.); and length of coupled lines = 370mm.

The insertion loss of the coupler is approximately 0.2dB over the frequency band 100MHz to 200MHz. The directivity is mainly determined by the dimensional accuracy of the dielectric material and printed conductors. Fig. 5 (b) shows the performance obtained from a prototype coupler made to this design. To modify the design for any other frequency band it is merely necessary to alter the length of the coupled lines using the formula:-

$$l_c = \frac{47.5}{\text{frequency in MHz}} \text{ metres} \quad (8)$$

Power combining at v.h.f.

When the required output power cannot be obtained from a single transistor the designer must consider combining the outputs of two or more transistors. Most v.h.f. amplifiers having output



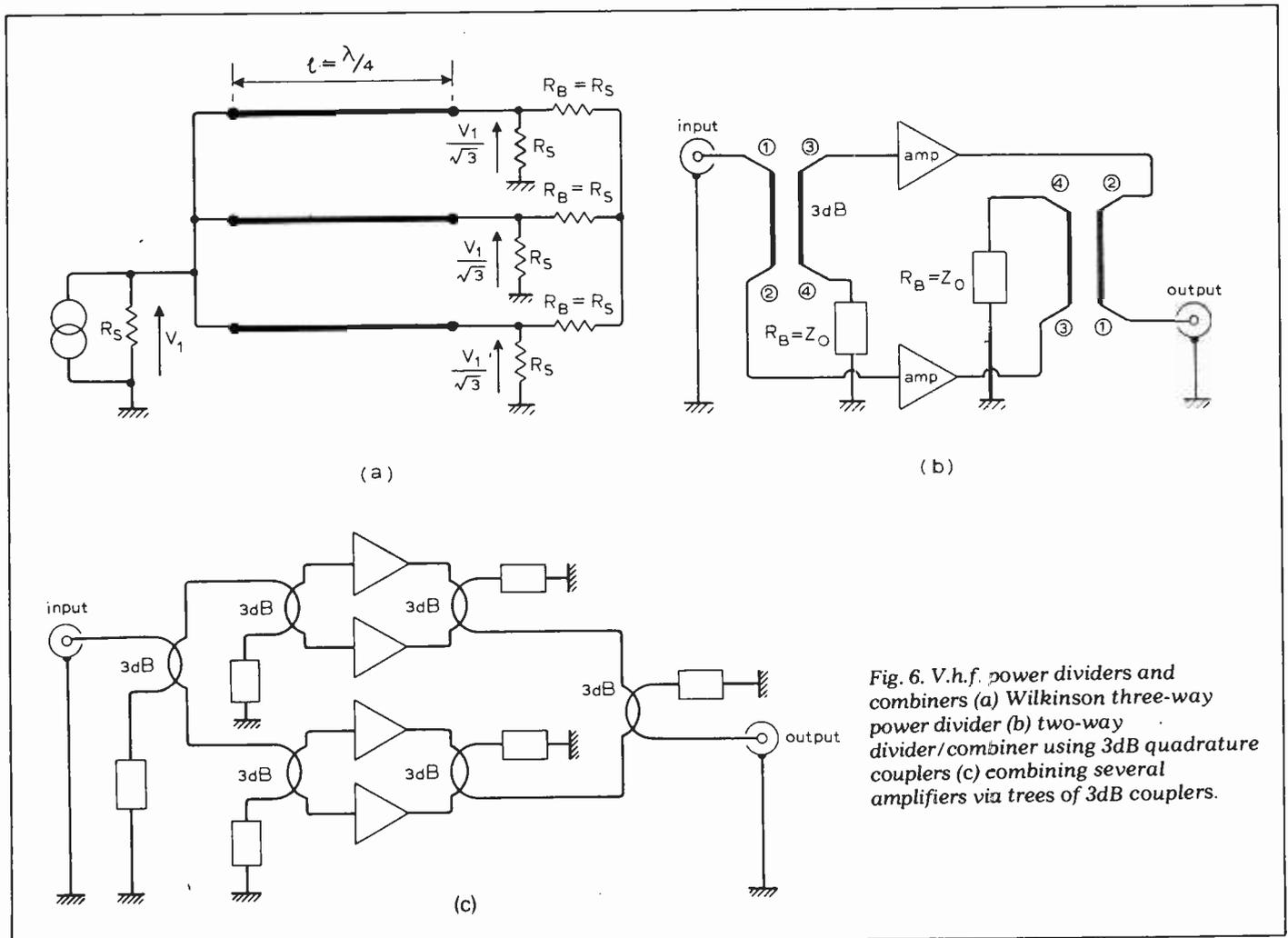


Fig. 6. V.h.f. power dividers and combiners (a) Wilkinson three-way power divider (b) two-way divider/combiner using 3dB quadrature couplers (c) combining several amplifiers via trees of 3dB couplers.

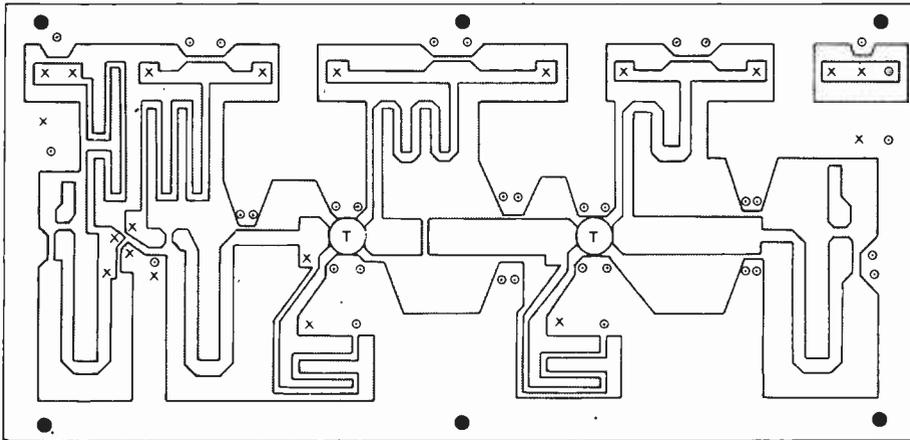

- x = 0.8mm holes for components
 o = 1mm holes for "Z" link through connections
 ● = 3.5mm holes for p.c.b. mounting
 T = 11mm holes for transistors

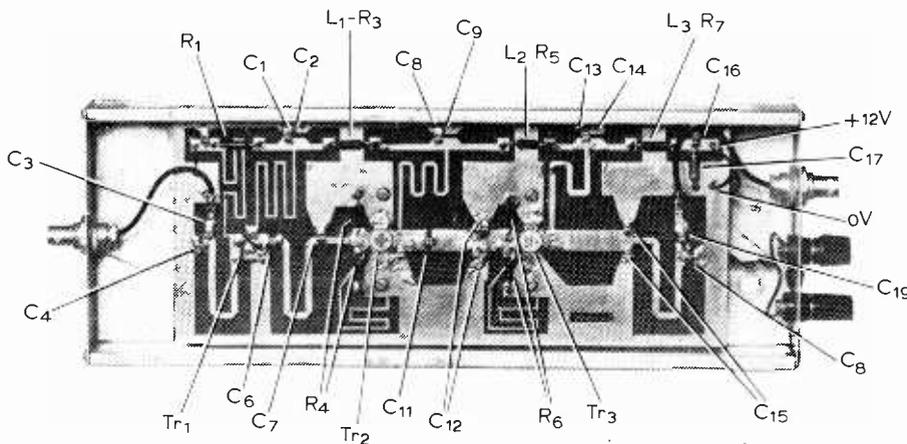Printed-circuit pattern and a view of the amplifier, showing the location of major components for the stripline board. The pattern is approximately half-size—a full-size drawing can be obtained from this office.



capability in excess of 100 watts make use of one of the following combining techniques.

Parallel connection. Simply connecting r.f. power transistors directly in parallel is rarely successful. Unless the two devices are nearly identical in input impedance and current gain one transistor will accept more than its share of the drive power. This causes its internal temperature to rise, thus lowering the turn-on voltage, V_{BE} , and increasing the conduction angle. As a result the input impedance and collector efficiency fall, causing extra heat dissipation and eventual failure. Extra stress is then imposed upon the surviving transistors so that it is not uncommon for all of the output devices to fail successively in circuits of this type.

When parallel connection is used it is advisable to provide a separate matching network to the base of each transistor in order to help stabilise the drive power. If a relatively narrow bandwidth is required then drive stability may be greatly enhanced by designing base matching networks having electrical length $\lambda/4$. As the input impedance of one device falls the

impedance at the input to its matching network rises and accepts a smaller fraction of the available drive power.

Wilkinson hybrid combiner. The n-way in-phase power divider/combiner devised by Wilkinson⁵ is a narrow band system using quarter wave transmission lines. Fig. 6 (a) shows a three-way power divider of this type. The ballast resistors, R_B , provide a high degree of isolation between the output ports at the centre frequency. The isolation and v.s.w.r. fall off to typically 20dB and 2:1 respectively for frequencies 30% removed from the band centre. Variations on this principle have been devised using multiple sections of transmission line to obtain wider bandwidths.

Wilkinson divider/combiners may be constructed using stripline techniques. The optimum line characteristic impedance is

$$Z_0 = \sqrt{n} \cdot R_s \quad (9)$$

where R_s is the system characteristic impedance. If a large number of amplifier modules are to be combined it may be necessary to employ a system characteristic impedance lower than 50 ohms so that the required matching line impedance can be realised in stripline form.

90° combiners. Two power transistors or amplifier modules may be combined using 3dB quadrature couplers as shown in Fig. 6(b). This combining system has the useful property that, provided the input impedance of the two amplifiers are nearly identical, a very low input v.s.w.r. is obtained at port 1. Any reflected power at ports 2 and 3 is routed to the ballast resistor at port 4. By using matching networks which provide increasing v.s.w.r. to lower frequencies in the passband of the amplifier it is possible to remove the inherent gain/frequency slope of the transistors. Pitzalis⁶ has determined element values for gain slope compensation networks of 4, 5 and 6dB per octave.

The output impedance of a 3dB quadrature coupled amplifier usually has a v.s.w.r. of less than or equal to 1.3 and provides an accurately matched source impedance for an antenna coupling network or output filter. This type of combiner provides typically 20 to 30dB of isolation between the two amplifiers. Should a fault develop in one amplifier the surviving unit continues to drive a matched load provided the output and ballast ports are accurately terminated.

Using coupled pairs of amplifiers as modules 2ⁿ amplifiers may be combined via a tree network of 3dB quadrature couplers as outlined in Fig. 6(c). Typical combining efficiency of 95% per step can be obtained using commercially available stripline 3dB quadrature couplers.

180° combiners. Push-pull operation of power transistors at v.h.f. demands accurate control of the phase characteristics of the phase-splitting networks which is difficult to achieve using conventional transformers. Transmission-line transformers provide a means of obtaining the required accuracy at frequencies up to several hundred MHz.⁷ The conventional push-pull configuration does not provide isolation between the power transistors, but 180° hybrid combiners may be used to obtain the push-pull effect with its associated advantage of greatly reduced second harmonic output. The 180° combiner is essentially a 90°, 3dB coupler with the addition of a fixed 90° phase shifter in series with one output port. Isolation is at least as good as that obtained using quadrature couplers, but insertion loss, phase error and v.s.w.r. are usually significantly greater.

Future developments

It has not been possible in this brief series to cover all of the r.f. power amplifier design techniques in use today. The last few years have seen great improvements in frequency coverage, and power output capability of transistors. Recently introduced devices are much more rugged than the transistors of three or four years ago, so that now with careful design very high reliability may be achieved in cost-effective

mobile radio systems. The future will see further improvements in power-frequency capability of transistors which are presently at least 10dB below the theoretical limitation. For broadband applications some manufacturers are including part of the input matching circuitry inside the transistor package, and for some medium power requirements full input and output matching is included. This trend is likely to increase and, as high permeability materials — originally pioneered for microwave hybrid integrated circuits — become less expensive and more readily available, complete power amplifier chains may be available on a custom design basis.

There is little reason to doubt that as manufacturing technology conquers present equipment requirements so the necessity for additional communication channel capacity will be Mother to the invention of new modulation processes which will present a challenge to the designers of radio equipment in the years ahead.

References

1. Jessop, G.R. "A Compact Bandpass Filter for 144MHz", *Radio Communication*, Vol. 7, No. 6, June 1971, p.390.
2. Mullard Technical Communication No. 115, July 1972, P.167.
3. Cohn, S.B. "Problems in Strip Transmission Lines", *Trans. IEEE PGMTT3*, 1955, p.119.
4. Matthaei, G.L., Young L. and Jones, E.M.T. "Microwave Filters, Impedance Matching Networks and Coupling Structures", McGraw-Hill, 1969.
5. Wilkinson, E.J. "An N-way Hybrid Power Divider", *Trans. IEEE PGMTT*, January 1960, pp.116-118.
6. Pitzalis, Jr., O. and Gilson, R. A. "Tables of Impedance Matching Networks which Approximate Prescribed Attenuation", *Trans. IEEE Microwave Theory and Techniques*, Vol. MTT-19, No. 4, April 1971, pp.381-386.
7. RCA Application Note AN6126.

The author has asked us to point out that a correction is needed to Fig. 7 published in Part 2 of this series (October issue). The upper curve of Z_0 vs. strip width has been plotted for air spaced microstrip and not for p.t.f.e. as stated in the text. The following co-ordinates can be used from which the true p.t.f.e. curve can be plotted.

Z_0 (ohms)	width (mm)
120	0.7
80	2.0
50	4.2
25	11.0

Transistors Tr_2 and Tr_3 in the components list of Part 3 in the November issue should be 2N5590 and 2N5591 respectively and not 2N5990 and 2N5991 as stated. Also Fig. 4(g) shows coaxial braid soldered to earth with a "pigtail" made prior to soldering instead of the braid soldered *directly* to earth as it should be to avoid degrading the v.s.w.r. of the coaxial to stripline transition.

Meetings

LONDON

- 6th. IEE — "Role of government in support of automation in the UK" by J. H. Major at 17.30 at Savoy Place, WC2.
- 8th. IEE — 11th Appleton lecture on "Ionospheres of dead stars and living galaxies" by Prof. R. L. F. Boyd at 17.30 at Savoy Place, WC2.
- 9th. IEE — Colloquium on "Solid state transmitters for radar" at 11.00 at Savoy Place, WC2.
- 13th. IEE/RTS — Colloquium on "Broadcast and wired Teletext systems — Ceefax, Oracle, Viewdata, at 10.00 at Savoy Place, WC2.
- 14th. IEE/I.Phys. — One-day meeting on "Integrated optics" at Imperial College, SW7.
- 14th. IERE — Colloquium on "Current trends in surface acoustic waves" at 14.00 at 9 Bedford Square, WC1.
- 14th. IEE — "Electronics as an aid to off-shore operations" by R. Nesbit at 17.30 at Savoy Place, WC2.
- 15th. IEE — "Underwater remote controlled vehicles" by R. T. Holmes and R. M. Dunbar at 17.30 at Savoy Pl., WC2.
- 15th. IEE — Discussion on "Private telecommunications networks — value for money?" at 17.30 at Savoy Place, WC2.
- 20th. IEE — Colloquium on "The technology of instrumentation in off-shore applications" at 10.30 at Savoy Place, WC2.
- 21st. IEE — "Surround sound technology" by Prof. P. B. Fellgett at 17.30 at Savoy Place, WC2.
- 21st. IERE — Two lectures on "Security systems — intruder alarms" at 18.00 at 9 Bedford Square, WC1.
- 22nd. IEE — "Antistatic — active and passive methods for removal of static electricity" by Prof. A. W. Bright at 17.30 at Savoy Place, WC2.
- 22nd. IERE — "Integrated injection logic — efficiency and versatility in solid state" by C. S. den Brinker at 18.00 at 9 Bedford Square, WC1.
- 28th. IEE — Colloquium on "Stability theory and non-linear oscillations" at 10.30 at Savoy Place, WC2.
- 28th. IERE/IEE Colloquium on "The impact of l.s.i. components on logic design" at 14.00 at 9 Bedford Square, WC1.
- 29th. IEE — Colloquium on "Pattern recognition — fact or fiction?" at 14.30 at Savoy Place, WC2.

ABERDEEN

- 15th. IEE — "Understanding lasers" by M. Kears at 14.00 at Robert Gordon's Institute of Technology, Schoolhill.

ARBORFIELD

- 22nd. IERE/IEE — "Recent developments in electro-chemical energy storage devices" by Prof. P. Dunn at 19.30 at the Lecture Theatre, School of Electronic Engineering, REME, Arborfield, Berks.

BELFAST

- 13th IEE — "The metallurgy and application of solder" by Peter King at 18.30 at Ashby Institute.

BIRMINGHAM

- 5th. IEE — "Public radio 'phone services in the UK" by P. J. Linney at 18.00 at Rm SG31, Sumpner Building, University of Aston, Gosta Green.
- 21st. IEE — "Engineering starts in the schools — implications for manpower planning" by G. B. Harrison at 18.15 at Sumpner Building, University of Aston.
- 22nd. RTS/IERE — "Radio Communications" by Prof. W. Gosling at 19.00 at Birmingham University.
- 26th. IEE — Faraday lecture on "The entertaining electron" by F. H. Steele in the evening at the Town Hall.
- 27th. IEE — Faraday lecture on "The entertaining electron" by F. H. Steele in the morning, afternoon and evening at the Town Hall.

BLANDFORD

- 21st. IEE — "Assessment is more difficult than it looks" by P. McVey at 18.30 at School of Signals, Blandford Camp.

CAMBRIDGE

- 29th. IERE/IEE — "Tropospheric scatter communications" by B. S. Skingley at 18.00 at the University Engineering Laboratories, Trumpington Street.

CARLISLE

- 13th. IEE — "My Dear Watson" by G. Phillips at 19.00 at Carlisle Technical College, Victoria, Carlisle.

CHATHAM

- 21st. IERE — "Managing your P's and Q's" (P = profit, Q = Quality) by P. Daisley at 19.00 at Medway and Maidstone College of Technology, Maidstone Road.

CHELMSFORD

- 14th IEE/IERE — "Charge coupled devices" by D. J. Burt at 18.30 at the King Edward VI Grammar School, Broomfield Road.

CREWE

- 12th IEE — "Stereophonic and ambisonic reproduction of sound" by Prof. P. B. Fellgett at 19.00 at MANWEB, Crewe.

DERBY

- 6th. IEE — "Signal processing using surface acoustic wave and charge coupled devices" by J. H. Collins at 19.00 at Main Lecture Theatre, Derby College of Art and Technology.

DUBLIN

- 15th. IEE — "The RTE Tullamore high power m.f. transmitting station" by M. J. C. Curley and P. Doyle at 18.00 at Physics Theatre, Trinity College.

DUNDEE

- 27th. IEE — "Electronic calculators" by Dr Priestland at 19.30 at Ewing Building, The University, Dundee.

EASTBOURNE

- 20th. IEE/CEI — "Choice and use of calculators" by D. W. Glover at 18.30 at SEEBoard, Westlords, Willingdon Road.

EDINBURGH

- 6th. IEE — "North sea oil telecommunications" by W. N. Lang at 18.00 at SSEB Offices, George Street.
- 22nd. IEE — "Liquid crystals" by Prof. Davies at 18.00 at King's Building, Edinburgh University, Mayfield Road.

EVESHAM

- 12th IEE/IERE — "Air traffic control in the vicinity of a major airport" by S. Ratcliffe at 19.30 at BBC Club, High Street.

HATFIELD

- 7th. IERE — Colloquium on "Contemporary teaching of electronics" at 10.00 at Hatfield Polytechnic.
- 14th. IERE — "A look at classical and modern control theory" by P. Murdoch at 19.45 at Hatfield Polytechnic.

HULL

- 21st. IEETE — "TEC — The introduction of new course structures for technician education" by J. W. M. McKain at 19.30 at Ernest Bullock Lecture Theatre, College of Technology, Queens Gardens.

LEEDS

- 6th. IEE — "My Dear Watson" by Dr D. N. S. Peach at 18.30 at Leeds University.

LIVERPOOL

- 6th. IEE — "Electronics in crime prevention" by G. Phillips at 18.30 at the Dept. of Electrical Engineering, Liverpool University.
- 21st. IEE/I Mech.E — "Ergonomics" by P. Crawley at 18.30 at The Polytechnic, Byrom Street.

Meetings continued on page 46

World of Amateur Radio

Outlook costly

The effects of inflation and 25% VAT continue to hoist the costs of operating an amateur radio station. The Home Office has proposed a 60% rise in all fees for standard radio licences (other than broadcast reception) with effect from December 1, 1975. This includes all amateur and model radio control licences, taking the basic annual fee for a Class A or B amateur licence in the UK from £3 to £4.80. The Home Office states that the income from the former fees no longer covers costs of issue and administration. Combined total of Class A and B licences recently passed the 21,000 mark. The RSGB is similarly proposing to raise its subscriptions by a roughly similar percentage in an attempt to offset the £18,000 deficit in 1973-74.

Attendance at the recent Leicester amateur exhibition appears to have been a little lower than in 1974 and a general comment was the effect of 25% VAT on equipment prices.

As an educational and scientific hobby, however, the costs of amateur radio remain very much what the individual enthusiast wishes to make them.

Satellite plans

With the highly successful and long living Oscars 6 and 7 still continuing to provide amateurs throughout the world with active transponders for 144/28 MHz and 432/144 MHz operation, the various "AMSAT" groups in a number of countries, including the UK, are planning ahead for a new phase of operations.

AMSAT-UK, for example, is hoping to provide the first British amateur-built equipment for an Oscar in the form of a 21/28 MHz repeater which, if successful, will provide the first "all-h.f." activity in the Oscar series.

It is also hoped that the next Oscar may be replaced in either a synchronous or highly elliptical orbit (i.e. as used in the Russian Molniya satellites) and so would be capable of providing improved coverage over long periods of time, although at the cost of much greater path losses. With a possible launch date

around mid-1978, the next Oscar is expected to be equipped with high-power transponders for the 145.9 and 435.1 MHz bands. German, Canadian and Australian groups are all co-operating with the Americans in planning for this new phase.

The recent RSGB meeting on AMSAT activities included an interesting account of the building and operation of the Oscar 6 ground control station that has been working since last February at the University of Surrey, Guildford, and plays an important role in conserving the state of batteries on board the satellite. An ambitious new Oscar communications and control station is currently being built there involving the use of an ex-ASWE tracking dish which, although weighing several tons, is being installed on the roof of one of the university buildings.

Television topics

The first slow-scan television convention at Aston University brought over 100 s.s.t.v. enthusiasts to Birmingham in this specialised field of amateur radio. Highlights included the keyboard s.s.t.v. character generators of Richard Thurlow, G3WW and Keith Clarke, G3KRC; four fast-to-slow scan converters; a flying spot scanner built by R. G. Dobbins, G3RGD and the extremely interesting slow-to-fast converter by Volker Wrasse, DL2RZ which allows s.s.t.v. pictures to be displayed on conventional television receivers — thus helping to bridge the gap between slow scan and "normal" television enthusiasts. This German amateur from Keil "stole the show" with frozen s.s.t.v. pictures displayed on 9 and 16-inch monitors, and Richard Thurlow is one of those who believe that after seeing this form of presentation "s.s.t.v. can never be the same again" though the necessary electronic storage is expensive at present, with a requirement for some 64 type 1404 ics costing some £5 each.

John Wood, G6AH/T, adds some additional calls to the November list of active 70cm amateur tv transmitters: G6NOX/T Saffron Walden; G6AMB/T Manchester; G6AAD/T Newcastle-under-Lyne; and F5VA. Several enthusiasts are anxious to establish a recognised "calling frequency" on 144MHz as a preliminary meeting point for both fast- and slow-scan enthusiasts. Suggestions have included 144.23 and 144.75 MHz. Membership secretary of the British Amateur Television Club is now Brian Summers, G6AJU/T, 13 Church Street, Gainsborough, Lincs (telephone 3940).

On the bands

A tune across 3.5MHz on November 1 unexpectedly brought in GB2BP on Platform C in the Forties Field, 110 miles east of Scotland. This was the first amateur radio operation from a North Sea oil rig as part of the celebrations

marking the official start of oil flowing ashore. The size of the rig permitted the use of a vertical half-wave aerial on 3.5MHz and the international nature of these oil fields was underlined by the fact that the operation on GB2BP was G5APC/W5WC who doubtless learned the oil business in Texas!

The long and intense "tropo" opening over the last weekend in October resulted in enormous numbers of 144 and 432 MHz contacts at distances up to about 1500km with ducts extending from Sweden in the north to Switzerland in the south; for example Scottish amateurs were able to work into Poland, Czechoslovakia and possibly for the first time Switzerland.

For many years one of the outstanding amateur signals from Angola has been those of Joao Chaves, CR6AI and it was painful to read in the South African *Radio-ZS* a letter from the 66-year-old amateur enquiring about possible work there — one of the many amateurs caught up in political turmoil that has greatly reduced the number of amateurs operating in the African continent.

The annual Top Band transatlantic tests, with emphasis on "first-time" contacts across the Atlantic on 1.8MHz, began this season on November 16 and the other dates are December 21, January 11 and February 8 with times of 0500 to 0730 GMT.

President 1976

To be formally installed as the 1976 president of the Radio Society of Great Britain on January 23 at Edgbaston, Birmingham is Dr E. J. Allaway, MB, ChB, MRCS, LRCP, G3FKM.

John Allaway is thus one of those whose hobby of amateur radio is something entirely apart from his profession and who has no qualms in showing clearly that he is keenly interested in such traditional amateur radio pursuits as h.f. operation, "dx chasing" and awards and certificates. His year as president is his 30th year as a member of the Society and his licence dates from 1949. He is a member of the First Class Operators Club, the Certificate Hunters Club and the International Short Wave League.


Dr Allaway seems destined to be a well-liked, well-respected president though it will surely tax his own professional skills to help cure the poor health of the Society's finances which are currently so strained, in spite of a membership which now exceeds 18,000.

In brief

American amateurs are facing a marked increase in the difficulties of buying one-off components specified for constructional projects, with firms imposing "minimum-billing fees" and claiming that the amateur component market is "too miniscule to warrant stocking specialised small parts."

PAT HAWKER, G3VA

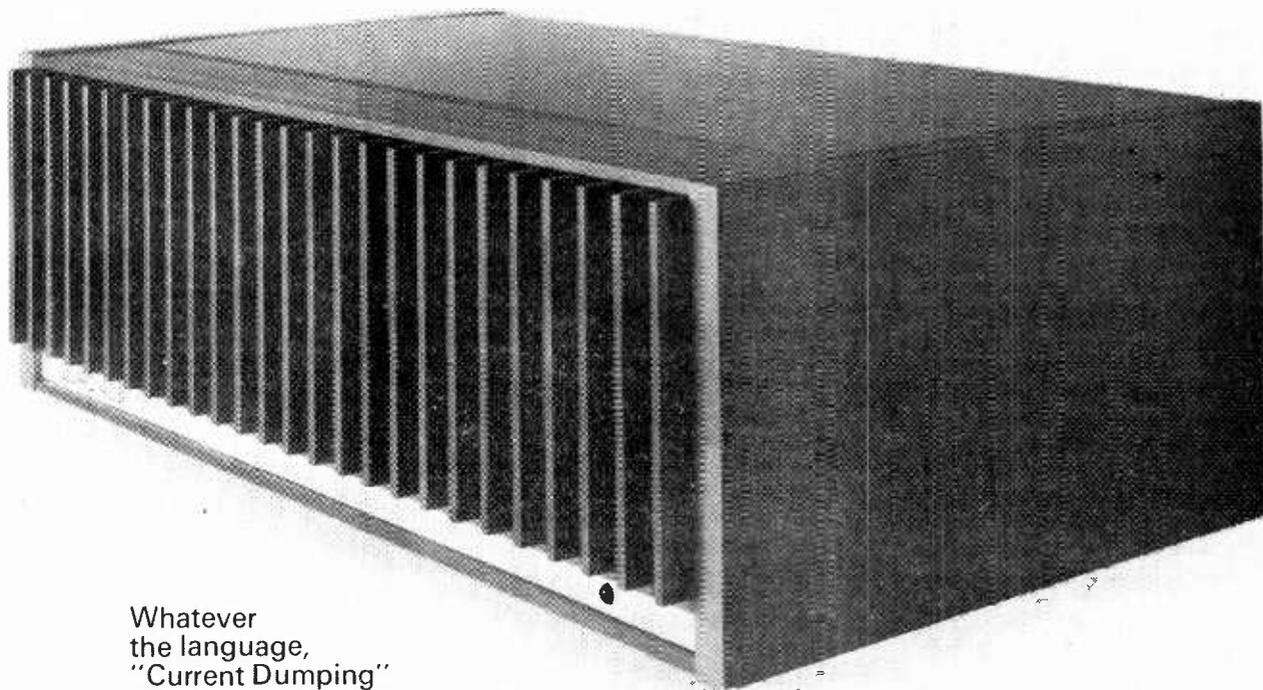**Current Dumping
Strom Ablade
Asservissement des étages générateurs de courant
Stroomtoelevering**



Whatever the language, "Current Dumping" is a term that is rapidly becoming familiar to audio engineers and hi-fi enthusiasts.

To the engineer it means an end to such problems as crossover, crossover distortion, quiescent current adjustment, thermal tracking and transistor matching.

To the hi-fi enthusiast it means an

absolutely predictable and impeccable performance which cannot change with time.

Current dumping is another QUAD development.

Details from your nearest QUAD retailer or write directly to Dept. WW Acoustical Manufacturing Co. Ltd., Huntingdon, Cambs., PE18 7DB.

QUAD

for the closest approach to the original sound

QUAD is a Registered Trade Mark

Now...the most exciting Sinclair kit ever


The Black Watch kit

At £17.95, it's

★ **practical** – easily built by anyone in an evening's straightforward assembly.

★ **complete** – right down to strap and batteries.

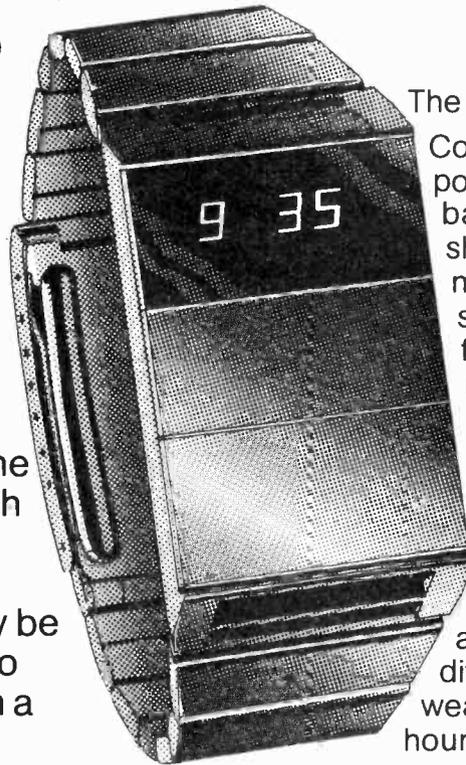★ **guaranteed.** A correctly-assembled watch is guaranteed for a year. It works as soon as you put the batteries in. On a built watch we guarantee an accuracy within a second a day – but building it yourself you may be able to adjust the trimmer to achieve an accuracy within a second a week.



The Black Watch by Sinclair is unique. Controlled by a quartz crystal... powered by two hearing aid batteries... using bright red LEDs to show hours and minutes and minutes and seconds... it's also styled in the cool prestige Sinclair fashion: no knobs, no buttons, no flash.

The Black Watch kit is unique, too. It's rational – Sinclair have reduced the separate components to just four.

It's simple – anybody who can use a soldering iron can assemble a Black Watch without difficulty. From opening the kit to wearing the watch is a couple of hours' work.




The special features of The Black Watch

Smooth, chunky, matt-black case, with black strap. (Black stainless-steel bracelet available as extra – see order form.)

Large, bright, red display – easily read at night.

Touch-and-see case – no unprofessional buttons.

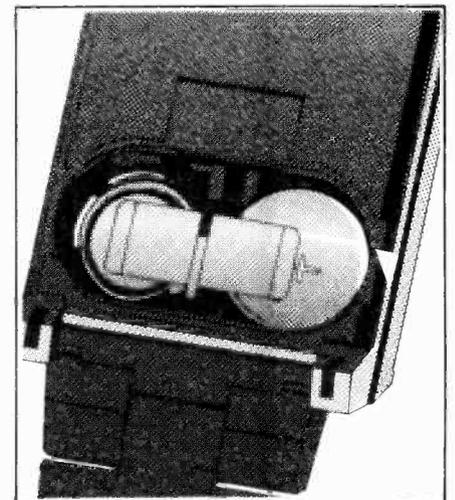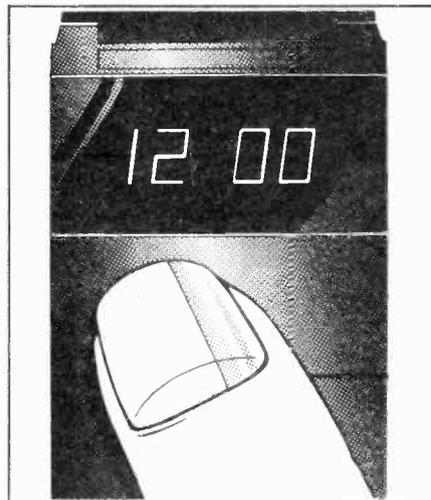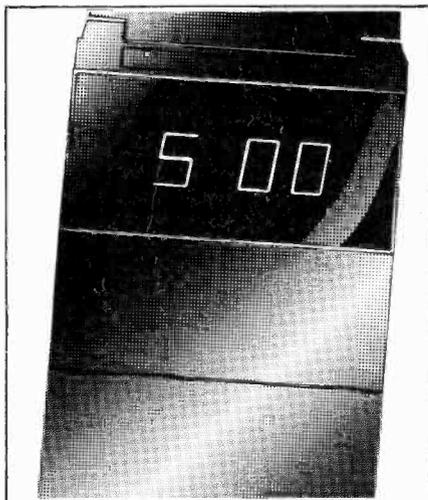Runs on two hearing-aid batteries (supplied). Change your batteries yourself – no expensive jeweller's service.



The Black Watch – using the unique Sinclair-designed state-of-the-art IC.

The chip...

The heart of the Black Watch is a unique IC designed by Sinclair and custom-built for them using state-of-the-art technology – integrated injection logic.


This chip of silicon measures only 3 mm x 3 mm and contains over 2000 transistors. The circuit includes

- a) reference oscillator
- b) divider chain
- c) decoder circuits
- d) display inhibit circuits
- e) display driving circuits.

The chip is totally designed and manufactured in the UK, and is the first design to incorporate *all* circuitry for a digital watch on a single chip.

...and how it works

A crystal-controlled reference is used to drive a chain of 15 binary dividers which reduce the frequency from 32,768 Hz to 1 Hz. This accurate signal is then counted into units of seconds, minutes, and hours, and on request the stored information is processed by the decoders and display drivers to feed the four 7-segment LED displays. When the display is not in operation, special power-saving circuits on the chip reduce current consumption to only a few microamps.

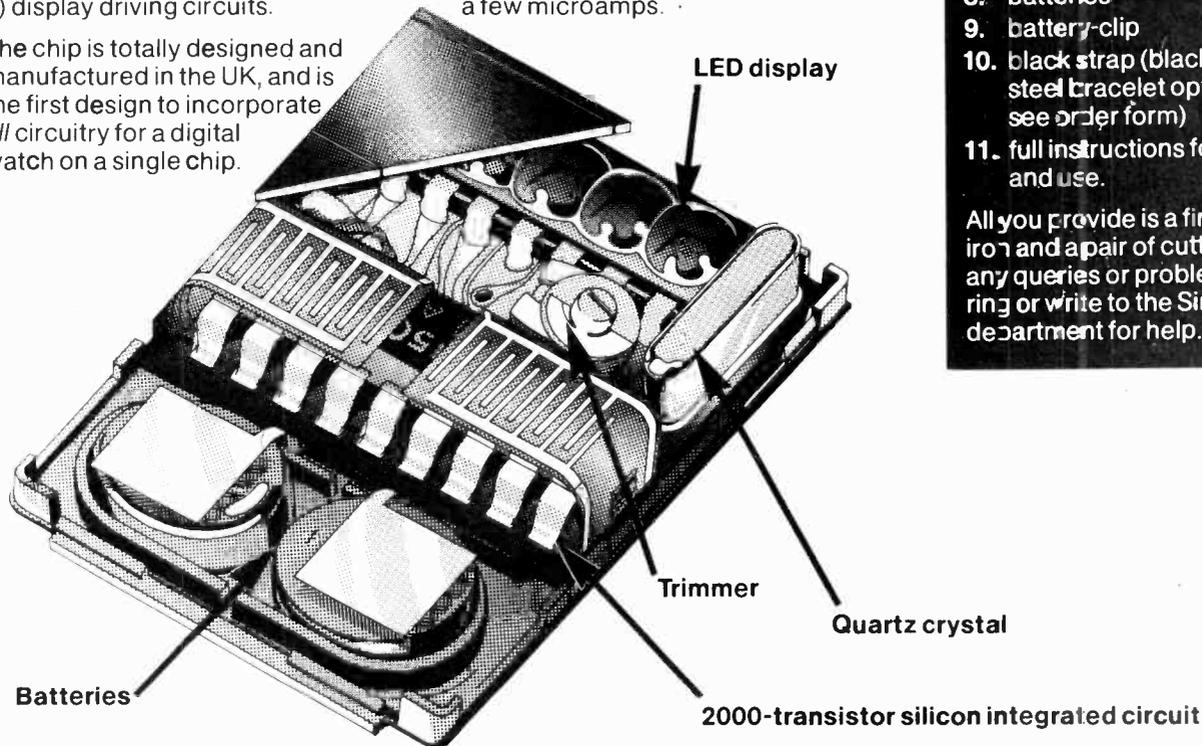

Complete kit £17.95!

The kit contains

1. printed circuit board
2. unique Sinclair-designed IC
3. encapsulated quartz crystal
4. trimmer
5. capacitor
6. LED display
7. 2-part case with window in position
8. batteries
9. battery-clip
10. black strap (black stainless-steel bracelet optional extra – see order form)
11. full instructions for building and use.

All you provide is a fine soldering iron and a pair of cutters. If you've any queries or problems in building, ring or write to the Sinclair service department for help.

Take advantage of this no-risks, money-back offer today!

The Sinclair Black Watch is fully guaranteed. Return your kit within 10 days and we'll refund your money without question. All parts are tested and checked before despatch – and correctly-assembled watches are guaranteed for one year. Simply fill in the FREEPOST order form and post it – today!

Price in kit form: £17.95 (inc. black strap, VAT, p&p).

sinclair

Sinclair Radionics Ltd,
London Road, St Ives,
Huntingdon, Cambs., PE17 4HJ.
Tel: St Ives (0480) 64646.

Reg. no: 699483 England. VAT Reg. no: 213 8170 88.

To: Sinclair Radionics Ltd, FREEPOST, St Ives, Huntingdon, Cambs., PE17 4BR.

Please send me

Total £

..... (qty) Sinclair Black Watch kit(s) at £17.95 (inc. black strap, VAT, p&p).

..... (qty) black stainless-steel bracelet(s) at £2.00 (inc. VAT, p&p).

* I enclose cheque for £..... made out to Sinclair Radionics Ltd and crossed.

* Please debit my *Barclaycard/Access/American Express account number

Name _____

Address _____

Please print. FREEPOST – no stamp required.

*Delete as required

ww1

Now ready!

**A new line of VHF tetrodes with PYROBLOC® grids...
for super-reliable FM-radio transmitters**

- 3 kW to 30 kW of output power.
- Only one power tetrode needed.
- Direct solid-state drive for the output stage.

With a big extra plus: THOMSON-CSF's own RF line-circuit designs for optimum overall amplifier performance and reliability!



THOMSON-CSF

THOMSON-CSF ELECTRONIC TUBES LTD
RINGWAY HOUSE / BELL ROAD / DANESHILL / BASINGSTOKE RG24 0QG / TEL. (0256) 29155 / TELEX. 84 9171

WW-005 FOR FURTHER DETAILS

Electronic circuit calculations simplified

6 — LC circuits

by S. W. Amos, B.Sc., M.I.E.E.

The resonance frequency f_o of an LC circuit, whether parallel-connected as in Fig. 1(a) or series-connected as in Fig. 1(b), is given by the well-known expression

$$f_o = \frac{1}{2\pi\sqrt{LC}}$$

In this form the expression is suitable for calculating f_o by direct substitution of numerical values for L and C . Problems of this type occur: for example it can happen, in designing a circuit, that an inductor and a capacitor are accidentally connected in series or in parallel. It is important then to know the resonance frequency of the combination because the low or high resistance presented by the LC circuit at resonance could have a great effect (beneficial or disadvantageous) on the performance of the circuit.

Knowing L and C we could determine f_o quite readily by the use of abacs, but in this series we are concerned only with arithmetical methods such as direct substitution in the expression for f_o . As an example of such a calculation let us suppose that in an attempt to build a very small medium-wave receiver, a tuning capacitor of 100pF maximum capacitance is chosen together with an inductor of 800 μ H (taken from a 465kHz i.f. transformer possibly). The problem is to calculate the maximum and minimum extremes of the waveband likely to be achieved with this combination. We can estimate the effective total minimum capacitance as 20pF, made up of contributions from the tuning capacitor, coil self-capacitance and strays. The maximum capacitance we can take as 110pF. For the minimum capacitance direct substitution in the expression for resonance frequency gives

$$f_o = \frac{1}{6.284 \times \sqrt{(800 \times 10^{-6} \times 20 \times 10^{-12})}} \text{ Hz}$$

$$= 1.26 \text{ MHz}$$

somewhat short of the 1.6MHz hoped for. The determination of the other tuning limit is carried out later.

The above calculation was hardly

simple but fortunately needs to be done only rarely: there are simpler methods which do not require direct substitution in the expression for f_o . These methods depend on two observations which can be deduced from the expression. The first is that if C is fixed, the resonance frequency is inversely proportional to the square root of the inductance. This can also be expressed by saying that the inductance is inversely proportional to the square of the frequency, e.g. if the inductance is quadrupled the resonance frequency is halved. The second observation is that, for a given inductance, the resonance frequency is inversely proportional to the square root of the capacitance: that is to say the capacitance is inversely proportional to the square of the frequency, e.g. if the capacitance is reduced to one quarter of its former value the resonance frequency is doubled.

The simpler method of calculating f_o requires a knowledge of the resonance frequency for particular values of L and C . A convenient result to know is that if $L=100\mu\text{H}$ and $C=100\text{pF}$, the resonance frequency is 1.6MHz. This can readily be checked by direct substitution in the expression for f_o .

As a numerical example we will complete the calculation started above: the problem now is to determine the resonance frequency for a circuit in which $L=800\mu\text{H}$ and $C=110\text{pF}$. We know that if $L=100\mu\text{H}$ and $C=100\text{pF}$ the resonance frequency is 1.6MHz. Frequency is inversely proportional to

the square root of inductance and to the square root of capacitance: thus the required value of f_o is given by

$$1.6 \times \sqrt{\left(\frac{100}{110} \times \frac{100}{800}\right)} \text{ MHz} = 537 \text{ kHz}$$

very near the required value. But there is difficulty, as shown above, in achieving the desired high-frequency extreme of the medium waveband unless the minimum capacitance in the circuit can be reduced.

The problem of calculating the resonance frequency for given values of L and C is, however, not so frequently encountered as that of calculating the value of C needed to tune a given value of L to a particular frequency (or alternatively of calculating the value of L , needed to tune a given value of C to a particular frequency). Such calculations could, of course, be performed by recasting the above expression for f_o so as to give an expression for C (or L) and by substituting numerical values in this. It is, however, simpler to make use of the observation that inductance and capacitance are inversely proportional to the square of resonance frequency.

As a numerical example, suppose we wish to use a medium-wave tuning inductor of 160 μH in an i.f. wavetrapp in the aerial circuit of a receiver. What value of tuning capacitance is required for resonance at 465kHz?

We can begin with the same basic statement as before. If $L=100\mu\text{H}$ and $C=100\text{pF}$, $f_o=1.6\text{MHz}$. Capacitance is inversely proportional to inductance and to the square of the frequency. Therefore the required value of C is given by

$$C = 100 \times \frac{100}{160} \times \left(\frac{1.6}{0.465}\right)^2 = 740 \text{ pF}$$

Reactance method. There is an alternative method of calculating values of L and C which can sometimes be useful. This makes use of the fact that at the resonance frequency of an LC circuit, the inductive and capacitive reactances are equal. Thus if we know or can calculate the reactance of an inductor at the resonance frequency, the required C value is that which has the same value

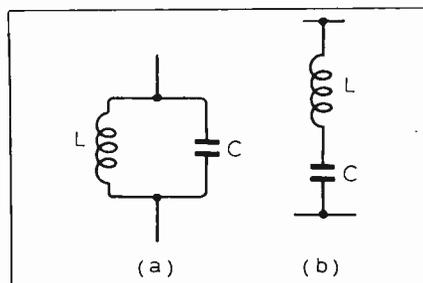


Fig. 1. For given values of L and C parallel-connected circuits (a) and series-connected circuits (b) have the same resonance frequency.

of reactance at the resonance frequency. To use this method it is necessary to know or to calculate reactance. Calculation is possible by numerical substitution in the expressions

$$\text{inductive reactance} = 2\pi fL$$

and

$$\text{capacitive reactance} = \frac{1}{2\pi fC}$$

It is however simpler and more convenient to calculate reactance from a knowledge of its value for a particular inductance (or capacitance) at a particular frequency. Useful results to remember are that an inductor of $100\mu\text{H}$ has a reactance of 628 ohms at 1MHz (and that inductive reactance is directly proportional to inductance and to frequency) and that a capacitor of 100pF has a reactance of 1.6 kilohms at 1MHz (and that capacitive reactance is inversely proportional to capacitance and to frequency).

The relationship between reactance and resonance is well illustrated in the circuit diagram of Fig. 2. This represents the frequency changer of an f.m. receiver. The transistor is d.c. stabilised by the potential divider R_1R_2 and emitter resistor R_3 . The circuit is basically that of a Colpitts oscillator (C_3 and C_4 being the two fundamental capacitors and C_5 being the tuning capacitor). To enable C_3 to be ganged with other tuning capacitors, the moving vanes of C_3 must be earthed. Thus the transistor base must also be earthed. Clearly therefore the emitter cannot also be earthed and the inductor L_2 is introduced into the emitter circuit to permit r.f. signals at the emitter. An advantage of including L_2 is that the emitter now becomes a convenient point at which the signal-frequency input can be applied to the transistor. L_3 is the primary winding of an i.f. transformer and this cannot be tuned by the usual parallel-connected capacitor because such a capacitor would decou-

ple the collector at r.f., so preventing oscillation. Instead therefore the tuning capacitor (C_5) is connected between collector and earth via L_1 which has negligible reactance at the intermediate frequency.

This circuit is a good example of the possibility mentioned earlier, that of forming an LC circuit by accident, for L_2 and C_7 constitute an unintentional series-connected resonant pair in the emitter circuit. The negative feedback introduced by these components will seriously reduce the conversion gain of the transistor if L_2 and C_7 have any net reactance at the intermediate frequency. Such feedback can be avoided, however, by making L_2 and C_7 resonate at the intermediate frequency and the problem is to calculate suitable values for these two components.

First decide a value for C_7 . To minimise feedback the reactance of C_7 at the oscillation frequency must be small compared with the emitter a.c. resistance of the transistor. A likely value for the emitter a.c. resistance is 25 ohms and thus the reactance should ideally not exceed 2 ohms at 100MHz. We know that 100pF has a reactance of 1.6 kilohms at 1MHz, and thus of 16 ohms at 100MHz. C_7 could hence be 1000pF which has a reactance of 1.6 ohms at 100MHz. As C_7 must resonate with L_2 at the intermediate frequency we also need to know its reactance at 10.7MHz; this is equal to $1.6 \times 100/10.7$ about 15 ohms. Thus the reactance of L_2 must also be 15 ohms at 10.7MHz. We know that an inductance of $100\mu\text{H}$ has a reactance of 628 ohms at 1MHz and thus the required value of L_2 is given by,

$$L_2 = 100 \times \frac{15}{628} \times \frac{1}{10.7} = 0.23\mu\text{H}$$

The reactance of L_2 at 100MHz will be nearly ten times the value at 10.7MHz

Fig. 2. A v.h.f. self-oscillating mixer circuit. The calculations of values for L_2 and C_7 are discussed in the text.

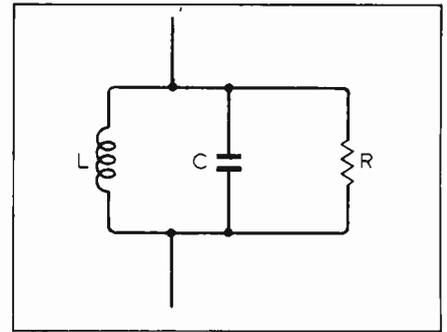
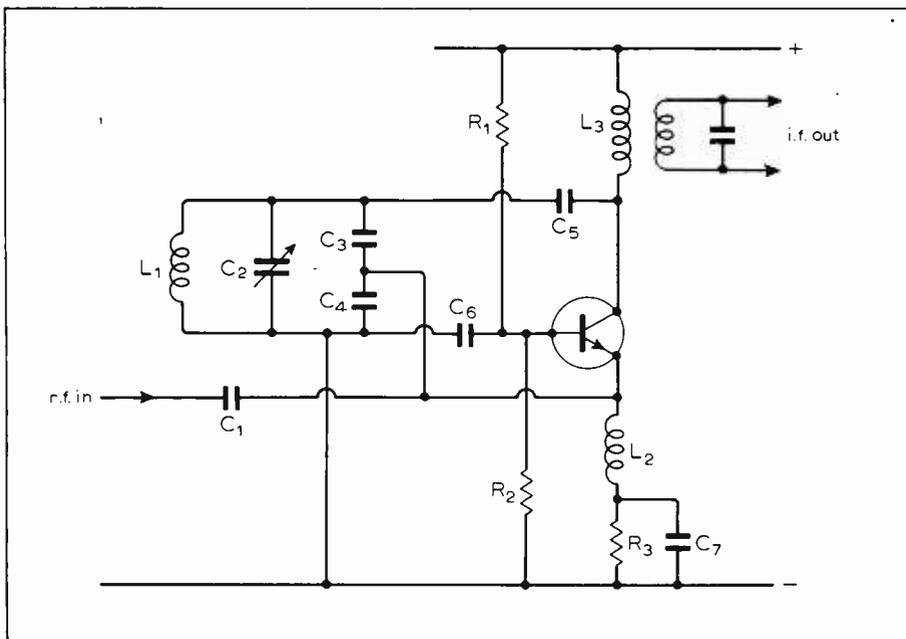


Fig. 3. A parallel-tuned circuit damped by a parallel resistor R.

and will be thus approximately 150 ohms, many times the emitter a.c. resistance of the transistor and this is the required condition.

Bandwidth of single tuned circuits.

Bandwidth is often stated as the range of frequency between the points at which the response is 3dB down, and for a single tuned circuit the bandwidth is simply related to the Q factor of the inductor thus

$$\text{bandwidth} = \frac{f_0}{Q}$$

where f_0 is the centre frequency. For an inductor with $Q=100$ tuned to 465kHz the bandwidth is 4.65kHz and if there are three such circuits in the i.f. amplifier of a medium-wave receiver the response is 9dB down at 4.65kHz bandwidth i.e. at 2.325kHz from the centre frequency. This represents a serious loss in high-frequency audio response due to sideband cutting in the i.f. amplifier and the effect may be reduced by damping each tuned circuit by a parallel-connected resistor as shown in Fig. 3. Suppose we decide that the loss of 9dB can be accepted at 5kHz. Then the bandwidth of each tuned circuit is 10kHz and the Q value required for each inductor is 46.5. What value of parallel resistance is required to reduce the natural Q of 100 effectively to 46.5? If we knew the dynamic resistance of the undamped LC circuit at 465kHz the problem is a simple one of two resistances in parallel. The dynamic resistance R_d of an LC circuit is given by

$$R_d = \text{reactance of } L \text{ (or } C) \times Q$$

We are more likely to know the capacitance of C than the inductance of L so, to pursue this numerical example, let us assume that C is 200pF. This has a reactance of 1700 ohms at 465kHz and thus the dynamic resistance is 1700×100 , i.e. 170 kilohms. The required, damped, value of dynamic resistance is given by 1700×46.5 which is approximately 80 kilohms. From Part 1 we can now calculate the required value of damping resistor thus:

$$R = \frac{\text{product of damped and undamped dynamic resistances}}{\text{difference between damped and undamped dynamic resistances}}$$

$$\begin{aligned} &= \frac{170k \times 80k}{170k - 80k} \\ &= 150 \text{ kilohms} \end{aligned}$$

In a practical circuit there is no need to add a parallel resistor as indicated in Fig. 3 to achieve the required bandwidth. Bipolar transistors have a low input resistance and this can be used to provide the required damping. For a mean emitter current of 1mA, a bipolar transistor has typically an input resistance of 2000 ohms. If the base of the transistor is connected to a tapping point on the inductor, as shown in Fig. 4, the required Q value can be achieved by correct positioning of the tapping point. For the example in question we need the effect of a parallel resistance of 150,000 ohms and we have an input resistance of 2000 ohms. The position of the tapping point should be such that there is a turns ratio between the whole coil and that part presented to the transistor of n:1 where

$$\begin{aligned} n &= \sqrt{\left(\frac{150,000}{2,000}\right)} \\ &= 8.7 \end{aligned}$$

Thus if the inductor has 150 turns, then the tapping point should be 150/8.7, i.e. 17 turns from one end.

It is alternatively possible to use a capacitive tapping instead of an inductive one. To do this the tuning capacitance of 200pF is made up of two capacitors in series, the ratio of the two being chosen to give the step-down ratio necessary to provide the required damping. The method of calculating the values of the two capacitors was given in Part 3.

In this calculation it was assumed that there is no contribution to the damping from the collector circuit of the transistor preceding the tuned circuit. This is normally justified because it is common practice to connect the tuned circuit to the preceding transistor via a coupling coil or a tapping point chosen to present the transistor with a resistance equal to its optimum load resistance. The collector a.c. resistance of the transistor is usually very large compared with the optimum load so that damping of the tuned circuit is negligible. The position of the tapping point can be calculated in the following manner.

As shown in Part 1 the optimum load resistance is given by

$$\frac{\text{collector voltage swing available}}{\text{collector current swing available}}$$

and for a transistor with a 9V supply and a mean emitter current of 1mA is approximately 7000 ohms.* To present the transistor with this value of resistance the position of the collector

* 2V being assumed lost across the emitter resistor and the base-emitter junction of the transistor.


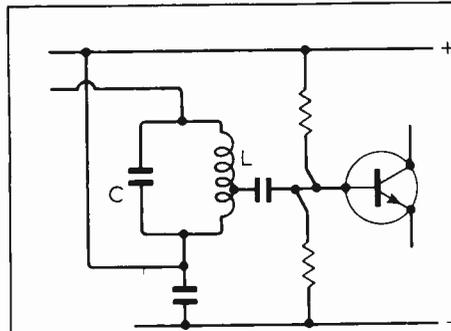


Fig. 4. Damping of a parallel-tuned circuit by the input resistance of a bipolar transistor.

Fig. 5. Method of matching the input resistance of a transistor to the optimum load of the preceding transistor via an LC circuit and of obtaining a desired working Q value.

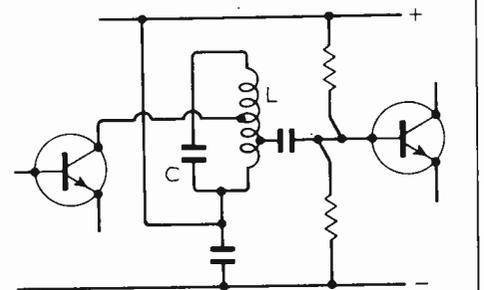

tapping point must be such that the turns ratio between the winding presented to the collector circuit and that presented to the base circuit of the following transistor is n:1 where

$$n = \sqrt{\left(\frac{7000}{2000}\right)} = \sqrt{3.5} = 1.87$$

The base winding has 17 turns and thus the collector winding must have 17 x 1.87, i.e. 32 turns. Thus the circuit can take the form shown simplified in Fig. 5. The collector circuit could alternatively be connected to a separate winding of 32 turns closely coupled to the tuning inductor.

There is an alternative solution to the problem of obtaining a required Q value using a given value of damping resistance. This is to connect the resistor across the tuned circuit, as shown in Fig. 3, and to choose the values of L and C so that:

(a) they tune to the required centre frequency

(b) the required Q value is obtained. We can illustrate the method by a numerical example on the i.f. circuit for a 625-line television receiver. The standard centre frequency is 36.5MHz and the bandwidth (to include the vision and accompanying sound channel) is required to be 6MHz. Thus we have

$$Q = \frac{\text{centre frequency}}{\text{bandwidth}} = \frac{36.5}{6} = 6.1.$$

Practical undamped Q values are likely to be very large compared with this. Therefore practical values of undamped dynamic resistance are likely to be very large compared with the damped value. When a high-value resistor is connected

in parallel with a low-value resistor, the net resistance is slightly less than that of the low-value resistor and, with little error, can be taken as equal to the low-value resistor. Thus the damped value of the dynamic resistance can be taken as equal to the external damping resistor, i.e. 2000 ohms. Now we know that

dynamic resistance = inductive or capacitive reactance x Q
and this gives

$$\begin{aligned} &\text{inductive or capacitive reactance} \\ &= \frac{\text{dynamic resistance}}{Q} \end{aligned}$$

Substituting the numerical values appropriate to our example

$$\begin{aligned} &\text{inductive or capacitive reactance} \\ &= \frac{2000}{6.1} \\ &= 328 \text{ ohms} \end{aligned}$$

The problem now is to determine the L and C values which have a reactance of 328 ohms at 36.5MHz. The method of doing this has already been described; the results are:

$$\begin{aligned} L &= 1.43 \mu\text{H} \\ C &= 13.3 \text{ pF} \end{aligned}$$

Bandwidth of two coupled circuits. A better approximation to the ideal square-topped frequency response can be obtained from two similar coupled LC circuits tuned to the same frequency and many receivers incorporate such pairs of LC circuits in the i.f. amplifier. The shape of the frequency response of such a pair is determined by the degree of coupling between them and this is measured by the coupling coefficient k, defined as M/L if the coupling is

HF predictions

Following its first signs of life in September last the new sunspot cycle should become clearly established this month. Sunspot number will rise with increasing rate during 1976 and may be as high as 50 by the end of the year.

In retrospect of 1975 it was most noticeable that transfer of international circuits from h.f. to satellite systems over the past decade had drastically reduced co-channel interference problems previously encountered during a sunspot minimum year. However did we manage with about 300 unstable channels for the whole world?

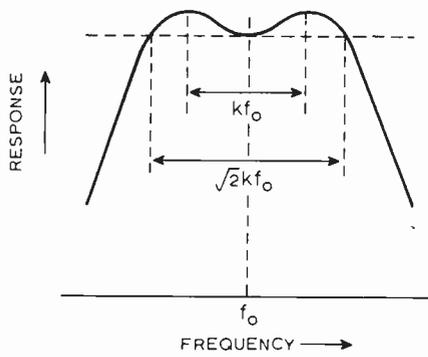
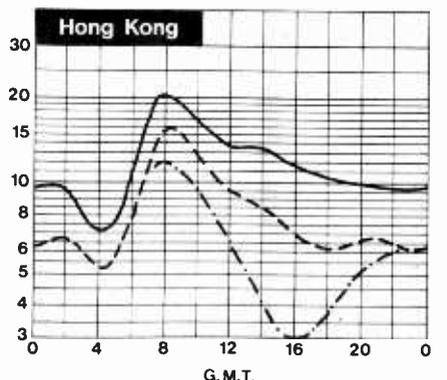
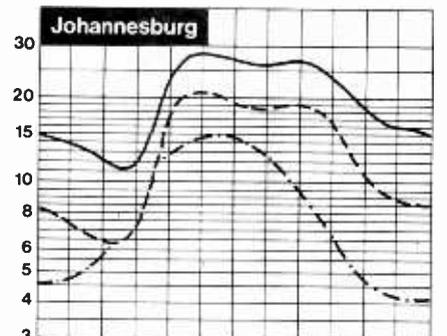
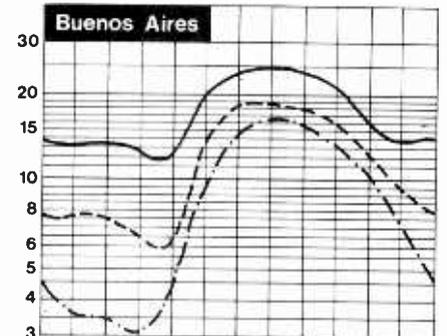
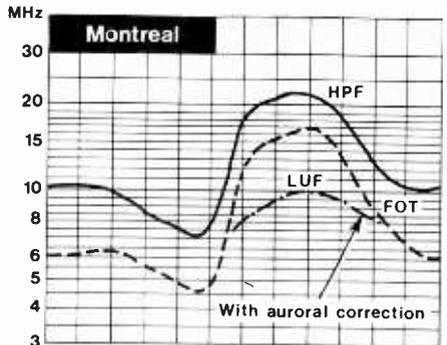


Fig. 6. Illustrating the response of a pair of overcoupled tuned circuits.

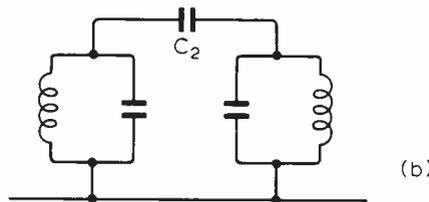
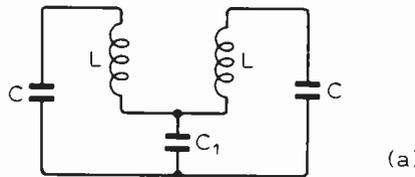


Fig. 7. Two simple methods of coupling two tuned circuits (a) by shunt capacitance and (b) by series capacitance.

achieved, as in i.f. transformers, by mutual inductance between the coils. For a signal injected into one of the tuned circuits, maximum response is obtained from the other when $k=1/Q$, known as critical coupling. The frequency response is also the flattest for critical coupling. If k is less than critical the response is low and is single-peaked. If k is greater than critical the response has two peaks of equal height, the frequency separation between them being approximately kf_0 . Values of k slightly greater than critical are often employed in i.f. circuits and for such values the passband can be taken as $\sqrt{2}kf_0$, as indicated in Fig. 6.

There are many ways of coupling coils to achieve the response of Fig. 6, and for a number of these there is a simple expression for the coupling coefficient so that it is easy to achieve a desired value of passband. Two coupling methods are shown in Fig. 7: at (a) coupling is achieved by a common shunt capacitor C_1 and at (b) by a common series capacitor C_2 . For circuit (a) the coupling coefficient is given approximately by

$$k = \frac{C}{C_1}$$

and for circuit (b)

$$k = \frac{C_2}{C}$$

As a numerical example we will consider the design of a pair of coupled

coils for use in the i.f. stage of an f.m. receiver. The standard centre frequency is 10.7MHz and the bandwidth required is 200kHz. Thus from Fig. 6 we have

$$k = \frac{\text{bandwidth}}{\sqrt{2}f_0} = \frac{0.2}{\sqrt{2} \times 10.7} = 0.013$$

If we assume the tuning capacitors to be 200pF then we have, for shunt-capacitance coupling

$$C_1 = \frac{C}{k} = \frac{200}{0.013} \text{ pF} = 0.015 \mu\text{F}$$

and for series-capacitance coupling

$$C_2 = kC = 0.013 \times 200 \text{ pF} = 2.6 \text{ pF}$$

shape of the response curve achieved by either of these two methods of coupling depends on the Q value for the inductors. For $k=0.013$ coupling is critical if $Q=1/k=75$. For this value of Q therefore the response is flat near f_0 but the required bandwidth is not achieved. The Q values must exceed 75 to give the bandwidth wanted and the response then has two peaks. The height of the peaks should not exceed the centre-frequency response by too great an amount but the difference will be less than 1dB provided Q does not exceed 110.

Linear c.m.o.s. circuits

This article gives background to the linear use of c.m.o.s. circuits which appear in set 27 of Circards.

by J. Carruthers, J. H. Evans, J. Kinsler and P. Williams.

Paisley College of Technology

By considering the various families of logic circuits one can deduce what parameters, designed-in to optimize digital operation, result in adverse performance if the circuits are used in the analogue mode. The most interesting family that is available at a low cost is complementary symmetry metal oxide semiconductor logic or c.m.o.s. By adding an extra diffusion to the processing steps needed for a single type of device, Fig. 1, the complementary type can be produced. Thus the p-channel device is obtained by diffusing p⁺ source and drain into the n-type substrate; a deeper p-type well is diffused to contain the n-channel device.

In addition to the conducting channels between the respective sources and drains, there are a number of p-n junctions. Though these are normally reverse-biased by the selected operating mode, their parasitic effects cannot always be ignored. Other p-n junctions are deliberately introduced at the inputs to prevent damage to the thin oxide films by high voltages that might be produced electrostatically or due to external transients.

The conductivity of the channels is increased by a forward bias on the gates. For an n-channel device this corresponds to a gate voltage positive with respect to the source. The conductivity tends to zero for zero gate-source voltage because the doping of the channel is such that there are virtually zero current carriers available. At a particular value of gate voltage, called the threshold voltage, charges induced in the channel by the resulting field allow conduction to commence. No gate current flows because of the insulation provided by the oxide layer. Drain-source conductivity continues to increase with rising gate-source voltage, while the current flow depends on both V_{gs} and V_{ds} . At low values of V_{ds} , the slope resistance is reasonably linear and is controlled by V_{gs} . Ultimately, the output current reaches a limiting value again set by V_{gs} i.e. the output slope resistance becomes very high making the device suitable for various forms of constant-current circuits.

The basic inverter is shown in

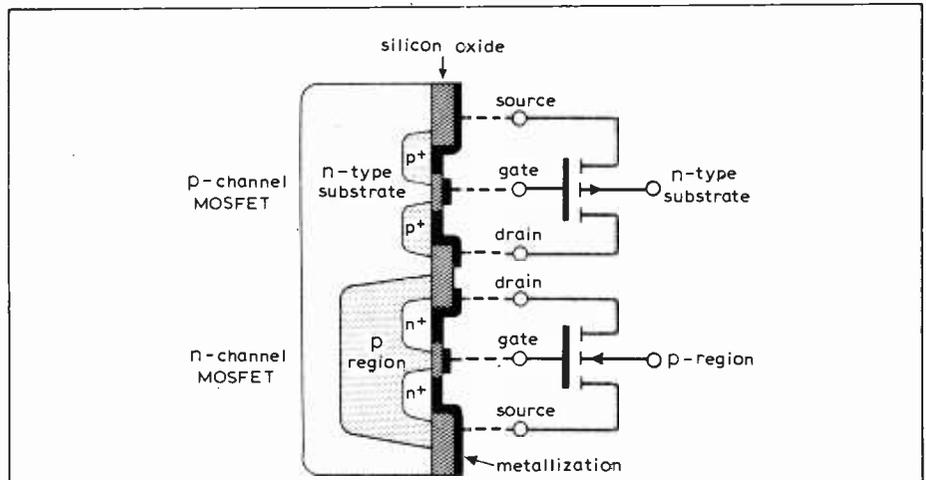


Fig. 1. Structure of c.m.o.s. inverter.

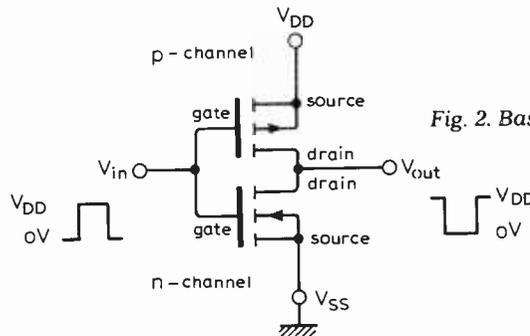


Fig. 2. Basic c.m.o.s. inverter.

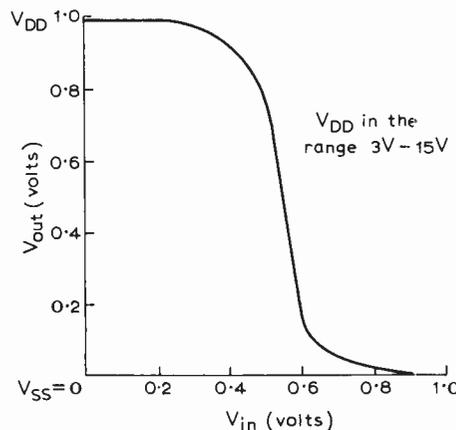


Fig. 3. Transfer function of c.m.o.s. inverter.

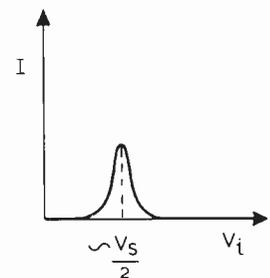


Fig. 4. Variation of inverter current with input voltage.

Fig. 2 and the transfer function in Fig. 3. When the input voltage is low, there is insufficient forward bias on the n-channel device to bring it above the threshold of conduction. The reverse is true for the p-channel device which has a high conductivity i.e. the output is virtually equal to $+V_s$. Conversely a very positive input voltage pushes the output close to zero. When lightly loaded the output swings to within 1% of the supply voltage. At voltages in the region of $+V_s/2$ both transistors are conducting. This region is traversed rapidly when the inverter is used as a logic level inverter, but the transient current pulse as shown in Fig. 4 is then the only significant contribution to current drain, as one or other of the transistors is non-conducting in each of the logic states. (At high pulse rates power consumption is associated with the multiple charge/discharge of internal and load capacitances.)

For analogue systems this central region of the characteristic is of great interest. The slope is moderately high, corresponding to a voltage gain of the order -10 to -100 with the unusual property that the gain is greater at lower values of supply voltage (both transconductance and output conductance fall, the last-mentioned more rapidly than the first).

Although not designed for high d.c. stability, temperature dependence of the transfer function is small. Recently c.m.o.s. i.c.s have been produced designed specifically for analogue applications; though the configurations may be identical to particular logic circuits, the processing is optimized for linear operation.

Because each m.o.s. transistor can be used as a voltage-controlled resistor, packages containing several devices offer interesting possibilities. The drain-source resistance characteristic remains approximately linear for small values of reverse voltage and current, making a.c. operation feasible. The devices on a common chip will be similar and will be subject to the same temperature variations. Thus, operated from a common gate-source voltage supply, they offer closely-matched resistance characteristics for use in amplifiers etc.

An interesting extension of this technique is possible even where single devices are not accessible separately. By grounding the positive supply line of a package containing multiple inverters, the p-channel devices are kept out of conduction provided the p.d. applied between output and ground of each device is small. Thus a hex buffer inverter i.c. can be used as a set of six matched n-channel f.e.t.s.

Any inverting amplifier can be used with n.f.b. to give a see-saw amplifier of reduced but well-defined voltage gain. As only a single gain-stage is involved external compensation against high-frequency stability is not required even

Linear c.m.o.s. circuit cards

Set 27 of Circards, available now from the address given below, contains 10 cards with the following titles

- devices and characteristics
- linear circuit characteristics
- device configurations
- d.c. amplifiers
- a.c. amplifiers
- gain-controlled amplifiers
- controlled resistances
- non-linear circuits-1
- non-linear circuits-2
- square triangle generator

How to get Circards

Order a subscription by sending £18 for a series of ten sets to:

Circards
IPC Electrical-Electronic Press Ltd
General Sales Department, Room 11
Dorset House
Stamford Street
London SE1 9LU

Specify which set your order should start with, if not the current one. One set costs £2.00, postage included (all countries). Make cheques payable to IPC Business Press Ltd.

New circuit book

"Circuit design — 1, Collected Circards" brings together the first ten sets of Circards, introductory articles to each of the subjects, and ten pages of additional circuits. The hardback A4 book contains 168 pages, in which 120 cards are rearranged so that each is laid out on one page. A brief introduction precedes the articles, which were previously published in *Wireless World*, and each of the ten subjects is followed by an up-dating page. Corrections have been incorporated where appropriate. "Circuit designs" is obtainable through leading bookstalls at £10 per copy. In case of difficulty order direct by sending remittance for £10.40 (includes postage and packaging) to the address given later, making cheques payable to IPC Business Press Ltd.

with 100% negative feedback. The bandwidth is not particularly high though well above the audio-frequency range, with some gain to beyond 1 MHz. High values of resistors may be used without loading effects due to amplifier input impedance, though the resulting RC time constants due to strays can further reduce the bandwidth.

A recent example of the way in which device technologies change forces a warning note at this point. To improve the performance of gates/inverters for their main functions in purely digital applications, some manufacturers pro-

Topics covered so far in Circards are:

- 1 active filters
- 2 switching circuits (comparator and Schmitt circuits)
- 3 waveform generators
- 4 a.c. measurement
- 5 audio circuits (equalizers, etc.)
- 6 constant-current circuits
- 7 power amplifiers (classes A, B, C, D)
- 8 astable multivibrator circuits
- 9 optoelectronics: devices and uses
- 10 micropower circuits
- 11 basic logic gates
- 12 wideband amplifiers
- 13 alarm circuits
- 14 digital counters
- 15 pulse modulators
- 16 current-differencing amplifiers—signal processing
- 17 c.d.as — signal generation
- 18 c.d.as — measurement and detection
- 19 monostable circuits
- 20 transistor pairs
- 21 voltage to frequency converters
- 22 amplitude modulators
- 23 reference circuits
- 24 voltage regulators
- 25 RC oscillators-1
- 26 RC oscillators-2
- 27 Linear c.m.o.s.-1
- 28 Linear c.m.o.s.-2

Circards are a unique way of collating and presenting data about circuits in a compact and easily retrievable way. The sets of 203×127 mm (8×5 in) doublesided cards are designed for easy filing in standard boxes and for easy access at the desk or at the bench, where transparent plastic wallets keep the cards in good condition.

Each card normally describes operation of a selected circuit, gives measured performance data and graphs, component values and ranges, circuit limitations and modifications to alter performance. Suggestions for further reading are included together with cross references to related circuits. The Circard concept was outlined more fully in the October 1972 issue of *Wireless World*, pp.469/70.

duce "fully-buffered" versions. These might contain three inverters in cascade to perform the function previously using a single inverter. The improved response is welcome to users with critical requirements in the digital field; those wishing to adapt them for analogue circuits, as described in Circards Set 27, would find high-frequency instability resulting from the much-increased loop gain and multiple phase-shifts. Remember to check the characteristics of any device or circuit rather than assume that similar titles guarantee identical performance.

New Products

Wire wrapping tool

The model EW-7D-48U is an electrically driven wire wrapping and unwrapping tool. Particularly designed for use in telecommunications, the motor operates from a 48-50V d.c. power source. Conversion from the wrapping to unwrapping mode is achieved through the operation of a switch in the handle of the tool.


The chuck will accept two types of bit, defined by the wire gauges involved. These are the PUW-2226 for 20-26 a.w.g. and the PUW-2830 for 26-32 a.w.g. (American wire gauge). Vero Electronics Ltd, Industrial Estate, Chandlers Ford, Eastleigh, Hants.

WW 301 for further details

Band-reject filters

Telonic has introduced six tunable band-rejection filters which will cover the 50-1000MHz frequency spectrum in one-octave bands.

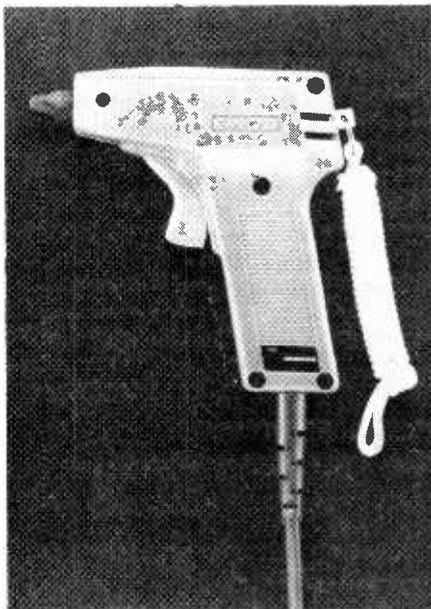Designated the Series TTR, the new filters are tuned by a single knob, which has direct frequency readout marked on the dial. The filters are suited for



WW 301 for further details

electromagnetic compatibility testing, or for many other laboratory functions. Each filter is tunable over a one-octave tuning range (up to 1GHz) and offers an insertion loss of less than 1dB. The passband v.s.w.r. is less than 1.5 over the entire tuning range, the notch bandwidth being 4-6MHz wide at the 50dB bandwidth and a minimum of 100kHz at the 1dB bandwidth. Ultimate attenuation is claimed to be a minimum of 50dB with typical values of 60-70dB. The power rating is 50W. Telonic Altaire UK, 2 Castle Hill Terrace, Maidenhead, Berks.

WW 302 for further details

Watch-timer


Designed to check the accuracy of all types of wrist-watch, the Quartz-timer II is fitted with three types of probe to effect a suitable signal coupling to the watch. It will also provide a power supply for electric watches under test, should this be required. The measuring amplifier can be bandwidth-limited by selecting the appropriate mode switches, and measuring periods of 2, 4, 6 and 12 seconds are also available.

A two-figure digital display with plus or minus error signals is provided, together with an analogue meter which is switchable to read the power supply voltage or average current consumption, and which can also be used to measure the signal level obtained from the probe. Greimer Electronic (GB) Ltd, 182 Upper Richmond Rd, Putney, London SW15 2SH.


WW 303 for further details

Soldering pistol

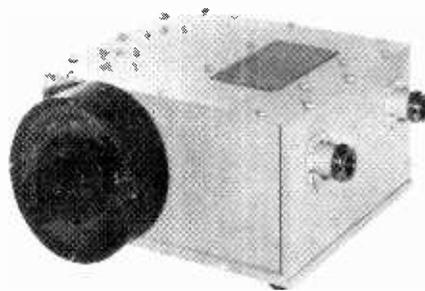The Kager soldering iron pistol features the automatic application of solder to the iron tip, in measured quantities. The tips used in the range are nonscaling and recent trials by the manufacturer



WW 302 for further details

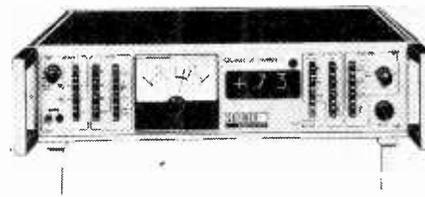

WW 303 for further details

have produced the claim that the life of each tip is well in excess of 10,000 joints. The Kager 3000 range of pistol irons is available in various wattages and voltages and an additional option of electronic temperature control is offered. Park Star Engineering Ltd, 62, High St, Croydon CR9 2UT, Surrey.

WW 304 for further details.

Op-amp tester

The THETA operational amplifier tester type 255 is a semi-automatic system for the measurement of the characteristics of d.c. operational amplifiers. It will measure bias current, offset voltage, supply current and the transfer function of the device under test, with a minimum of adjustments, and may be used either for laboratory quantitative measurements, for quality assurance tests or for production limit testing.


The instrument is powered by 110/240V mains and provides the stabilized supplies, waveforms and solid-state switching needed to make the tests. The 255 is designed to be used in conjunction with a directly-coupled oscilloscope for display purposes.

Plug-in modules are used to interface the device to be tested with the tester, these carrying any frequency compensation or other networks necessary for correct operation. Expander modules are also available for 24, 28 and 36-pin packages. THETA, PO Box 10, Martock, Somerset, TA12 6LT.


WW 305 for further details

R.f test system

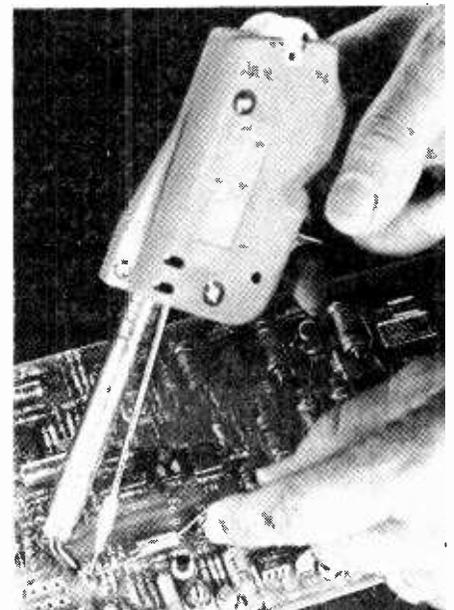
The models 9600/9650 are two versions of a radio-frequency tracking sweeper-analyser, designed for operation in the frequency range from 1MHz to 350MHz. The unit incorporates a sweep generator and tracking spectrum




WW 304 for further details

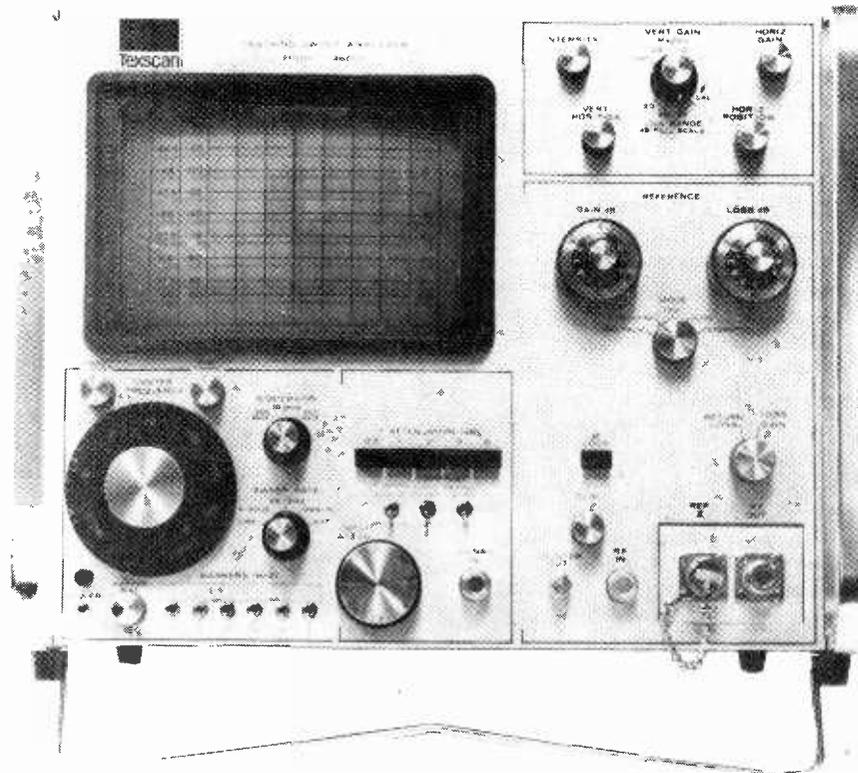


WW 306 for further details

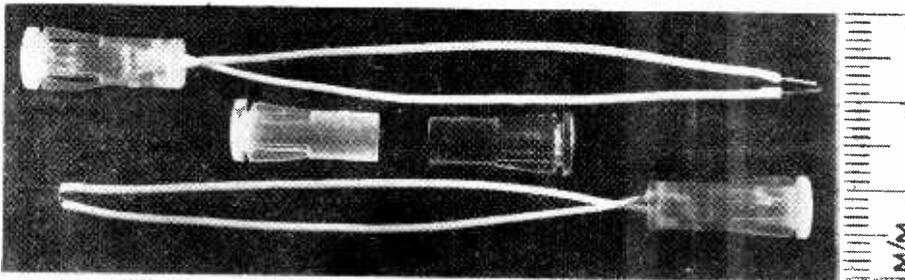

WW 307 for further details

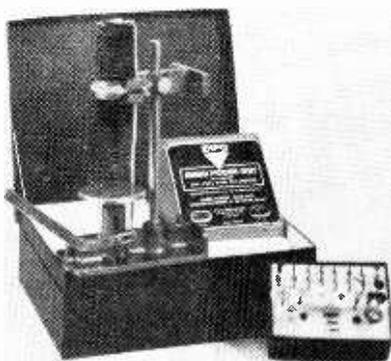

WW 308 for further details

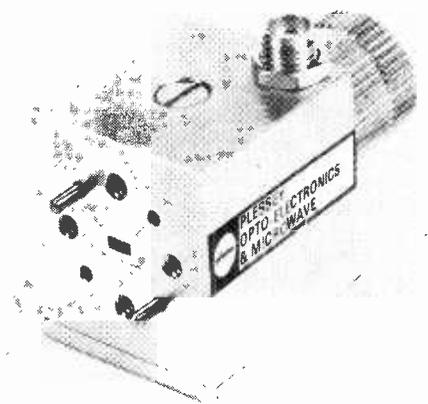

WW 309 for further details

analyser together with a display unit, reflection-coefficient bridge, comparator and gain and loss measuring attenuators.

The two versions of the system available are for 75Ω operation (Model 9600) and 50Ω operation (Model 9650). Both units have an 80dB dynamic range, a sensitivity of 1μV and a sweep-system level accuracy of ±0.25dB over the whole frequency range. Additional features include automatic phase lock, a 50dB bridge balance for return loss measurements, a 120dB range for isolation and crosstalk and provision for up to six plug-in crystal markers. Texscan Instruments Ltd, 1 North Bridge Rd, Berkhamsted, Herts.

WW 306 for further details

Panel indicator

Details have been received of a front-mounting panel indicator, from H. F. Collison-Goodwell. These are miniature-tungsten filament or neon bulbs, encapsulated in a clear plastic holder which is designed to clip directly into a 6mm hole. Types available include 5V, 60mA; 12V, 30mA; 28V, 40mA and 120-240V with integral resistor. A variety of colours are also offered and the lamps are fitted with insulated and tinned leads. H. F. Collison-Goodwell Ltd, Coleshill, Birmingham B46 3BL.

WW 307 for further details

Mini drills

The Expo Titan and Reliant are miniature 12V d.c. drills suitable for printed circuit boards, jewellery, model making, etc. The first mentioned measures 114×41mm and is supplied with four collets of up to 3mm capacity, while the Reliant measures 76×34mm and is supplied with three collets of up to 2.4mm capacity. With the aid of a tool kit (20 or 40 piece) the drills can polish, brush, burr, saw and grind almost any material at speeds up to 9000 rev/min. Both drills can be fitted to a multipurpose drill stand which can also be used as a miniature lathe or horizontal bench stand. For operation from 240V a.c. supplies, a mains power unit is available. These accessories can be obtained with the drills in various kit options from A. D. Bayliss & Son Ltd, Pfera Works, Redmarley, Gloucester GL19 3JU.

WW 308 for further details

IMPATT oscillator

The ATO range of c.w. millimetre wavelength IMPATT signal sources from Plessey has now been extended to include the frequency band 60-90GHz. These devices are designated the ATO 260 series and three basic models provide 20, 50 and 100mW c.w. Designed

for fixed frequency operation, the sources can be supplied to any specified frequency in the range, with small adjustments, typically 0.5%, made possible by means of a tuning screw.

Standard units are provided with a UG387/U output waveguide flange and an SMA connector for bias. Typical bias requirements are 20V at 100mA. Plessey Optoelectronics and Microwave, Wood Burcote Way, Towcester, Northants.

WW 309 for further details

Scope probe kit

The latest addition to the Interprobe range of oscilloscope passive probe kits, is the triple-function Interprobe-3, giving $\times 10$ attenuation up to 80MHz, $\times 1$ attenuation up to 15MHz and an earth reference check selected by a three-position switch built into the probe body.

Features include a very flexible cable, a fixed earth-lead, a sprung hook tip and an input capacitance range of 15-50pF. Intertek, 15 Ennerdale Avenue, Dunstable, Beds, LU6 3AR.

WW 310 for further details

Non-flam capacitors

Designed to conform with B415, Clause 20 (Fire prevention in TV receivers), this range of plastic encapsulated, metallised film capacitors will self-extinguish in one second after being subjected to the BS flame test.

The capacitance range is from 0.01-4.7 μ F in working voltages from 100V to 200V, a.c. and tolerance ranges ± 5 , 10 and 20%.

The capacitors also carry all the BS and PO approvals granted to the PMT range. ITT Components, Capacitor Division, Brixham Rd, Paignton, Devon.

WW 311 for further details

Low-current dry-reed relays

The ARME series of dry-reed relays are sealed in a d.i.l. 14-pin package, suitable for socket or p.c.b. mounting. Satisfactory operation is claimed from small-signal sources, up to a maximum rating of 10VA. The initial contact resistance is typically 200 Ω and the contact life expectancy is said to be 100 million operations at low signal levels, to 5 million operations at the maximum rated load.

Response time for the relays is typically 500 μ s, the coil drawing 13mA from a standard 5V logic supply rail. The standard version is designated Form A and has a single contact, normally open. Other variants are offered featuring electrostatic shielding between the coil and the capsule and/or an integrated diode which is cathode

connected to the coil, the anode being connected to an otherwise unused pin. Elliot Relays, 70 Dudden Hill Lane, London NW10 1DJ.

WW 312 for further details

Pyrometer

A pyrometer has been developed to check the temperature of soldering iron bits. It uses an iron-constantan thermocouple in conjunction with a moving coil meter, incorporating automatic cold junction compensation. The meter scale ranges from zero to 500°C with a scale mark every 20°C. The pyrometers are supplied with a calibration certificate having been tested against the standard e.m.f. of iron-constantan to BS4937, part 3. Light Soldering Developments Ltd, 97-99 Gloucester Road, Croydon CR0 2DH.

WW 313 for further details

Capacitance meter

The DCM302 is a portable capacitance meter ranging over six decades of measurement from 1999pF to 199.9 μ F with a resolution of 0.05% being given by the 3½ digit display.

The only control is a touch-pad used to start measurement, turn off occurring automatically after about 10s. Power is derived from two 9V, PP3 batteries giving an operating life of 6,000 measurements. The i.e.d. display has 7.5mm high characters, full scale range being indicated by a separate i.e.d. Price is £89 direct from the manufacturers. Aim Cambridge Ltd, Nuffield Road Industrial Estate, St. Ives, Huntingdon, Cambs.

WW 314 for further details

Sweep generator

The ED3 is a sweep generator covering the frequency range from 20kHz to 70MHz in ten overlapping bands. Sockets are fitted for external sweep control, an external marker generator, an external r.f. generator and d.c. level shift. Outputs include the video signal, sync and the time base signal.


An internal marker generator provides for a selection of up to seven crystal derived frequency combs from 10kHz to 10MHz. Aspen Electronics Ltd, 18a High St, Northwood, Middlesex HA6 1BN.

WW 315 for further details


Cycle counter/timer

Capable of counting at rates up to 5kHz, the Koyo KCD 5H is a counter timer, with pre-setting obtained from a five digit thumbwheel indicator.

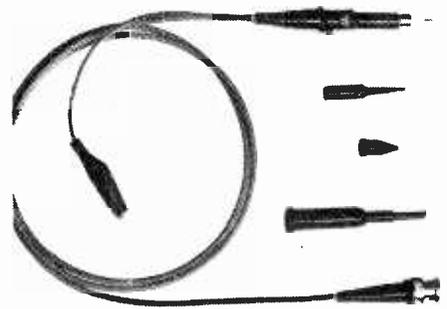Signal sources may be from a variety of transducers and the counter can be



WW 310 for further details

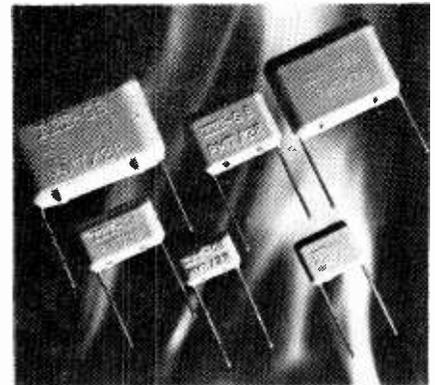


WW 311 for further details



WW 312 for further details



WW 313 for further details

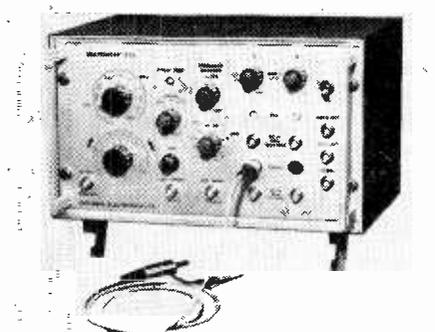

WW 315 for further details

reset from an external source. Two types of output are available, a 50ms pulse or a d.c. level, either of which appears when the count equals the thumbwheel setting.

Noise immunity is improved by filtering and the supply voltage is mains derived (220/240V, 50/60Hz). Tempatron Ltd, 5 Loverock Rd, Reading, Berks.

WW 316 for further details

Jacketed flat cable

Thomas & Betts have introduced a jacketed flat cable as an addition to the Ansley flat cable and connector system. The cable has been developed for external cabinet-to-cabinet wiring requiring low crosstalk characteristics, such as in high-speed data processing equipment.

To terminate the cable, a small length of outer jacket is removed and the insulated core of the cable is fitted into a standard Ansley insulation-piercing connector. Termination is effected using either a bench or hand type Ansley tool.

The inner construction of the cable is ribbed, making location of the connector simple and every fifth conductor is colour coded as a method of identifying conductors. The number one conductor is identified by a dark-blue strip, which also provides a "polarity" check. The cable is available in 10 to 50 wire sizes and has a UL temperature rating of 75°C and a voltage rating of 90V. Thomas & Betts Ltd, Sedgewick Rd, Luton LU4 9DT.

WW 317 for further details

Solid State Devices

Names of suppliers of devices in this section are given in abbreviation after each entry and in full at the end of the section.

Darlington transistors

The RCA 2N 6534/5/6/7 are a range of monolithic n-p-n silicon Darlington power transistors produced in TO-66 packages. The devices are made using the double epitaxial construction to produce good forward and reverse second breakdown characteristics; they are suited to power applications at low and medium frequencies.

Since they have gains up to 1000 at 5A, the devices can be operated directly from integrated circuit outputs without

the use of a pre-driver. Versions are available for 80, 100 and 120V all with power dissipation of 36W. They can handle a continuous collector current of 8A, with peak collector current up to 15A.

RCA

P.s.u. transistor

The latest addition to the Mullard range of transistors for use in high-frequency switched-mode power supplies operating directly from a "rectified mains" input, is the type BUX82. It is intended for use in 400W push-pull or 100W to 200W single-ended circuits. The BUX82, in common with the other types in the range will accommodate the 10% voltage variations found on mains supplies.

To meet these requirements, the device has an open base, collector-emitter rating of 400V and a collector breakdown rating of 800V ($V_{BE} = 0$). The d.c. and peak collector current ratings are 5A and 8A respectively.

The switching characteristics are designed to minimize switching losses and to facilitate operation in the 25-50kHz region.

Mullard

Microprocessor

The Am2901 is the first of a family of low-power Schottky circuits planned by Advanced Micro-Devices for use in a variety of applications, including micro-programmed computers. This particular device is a four-bit micro-programmable data chip containing an eight-function arithmetic logic unit, a two-port 16-word scratch pad memory, an additional accumulator register and shifting and control logic. This circuit can execute a total of 12992 instructions and performs a read-modify-write cycle in less than 100ns.

Advanced

Decoder/driver

The CD4511 is a b.c.d. decoder/driver with an integral latch on a single chip. The decoding functions and the latch use the c.m.o.s. process and the output devices are bipolar. This enables the device to supply up to 25mA to drive a display segment. The CD4511 provides the functions of a 4-bit storage latch, a b.c.d.-to-seven-segment decoder and seven high-current drivers. Lamp test, blanking and latch inputs are provided for display testing, turning off or brightness modulation of the display and storing a b.c.d. code respectively.

The CD4511 is available in either 16-pin epoxy-B d.i.l. or 16-pin ceramic packages.

National

GaAs light source

The type GL-504 lamp is designed to produce a power dissipation of 140mW

at room temperatures and is a hermetically-sealed unit in a metal can, fitted with a glass window. The peak emission wavelength is 2Å and when used with a pulse circuit delivering a pulse width of 10µs, repeated at 100Hz, will produce an output capable of detection over a distance of 100 metres.

The device measures 4.6mm dia, by 6.6mm high, including the glass window. Price is £2 to £3 each according to quantity. (Plus VAT at 8%)

Photain

High voltage op-amp

The HA2-2645-5 operates from dual supply rails between 10V and 40V (up to 80V total) and incorporates a temperature sensing circuit for output current limiting. Slew rate is 5V/µs in the unity-gain configuration, 23kHz full power bandwidth is 23kHz and the device provides a typical 12mA output current. Up to plus and minus 35V can be produced across a 5kΩ load.

Input characteristics for the internally-compensated op-amp include 40nA maximum bias and offset currents over the full temperature range from 0°C to +75°C, a 40MΩ minimum input resistance and plus and minus 35V common mode range.

GDS

8k r.a.m. board

Motorola have announced the introduction of an 8k r.a.m. card comprising two 4k byte blocks of dynamic random access memory. This memory is for use with their M6800 evaluation and development systems and features a standby battery power supply enabling the contents of the memory to be retained for more than a week from a 12V battery of 4.5Ah capacity.

The memory card is designed to provide a temporary store for the assembly of programmes, prior to loading where high speed loading arrangements such as a floppy disc with direct memory access, or a high speed cassette reader are not available.

Motorola

Suppliers

RCA Ltd, Solid State Europe, Sunbury-on-Thames, Middlesex.

Mullard Ltd, Mullard House, Torrington Place, London WC1.

Advanced Microdevices Inc. 901, Thompson Place, Sunnyvale, California 94086, USA.

National Semiconductor UK Ltd, 19 Coldington Rd, Bedford MK40 3LF.

Photain Controls Ltd, Unit 18, Hangar 3, The Aerodrome, Ford, Sussex.

GDS Sales Ltd, Michaelmas House, Salt Hill, Bath Rd, Slough, Bucks.

Motorola Semiconductor Products Division, York House, Empire Way, Wembley, Middx.

Conferences & Exhibitions

LONDON

Mar. 23-25 Imperial College
CAD 76 (Computer Aided Design)
 (Tom McGowran, CAD 76, IPC Science & Technology Press, 32 High Street, Guildford, Surrey GU1 3EW)

Mar. 30-31 Savoy Place
Small Electrical Machines
 (IEE Conference Department, Savoy Place, London WC2R 0BL)

Apr. 13-15 Grosvenor House
The All-Electronics Show
 (The All-Electronics Show, 34-36 High Street, Saffron Walden, Essex)

May 3-7 Savoy Place
Subscriber Loops and Services
 (IEE Conference Department, Savoy Place, London WC2R 0BL)

May 10-14 Royal Lancaster Hotel
7th IMEKO Congress
 (The Institute of Measurement and Control, 20 Peel Street, London W8 7PD)

June 22-25 Savoy Place
On-line Operation and Optimisation of Transmission and Distribution Systems
 (IEE Conference Department, Savoy Place, London WC2R 0BL)

July 5-8 Savoy Place
Automobile Electronics
 (IEE Conference Department, Savoy Place, London WC2R 0BL)

Sept. 1-3 Savoy Place
Advances in Magnetic Materials and their Applications
 (IEE Conference Department, Savoy Place, London WC2R 0BL)

Sept. 16-18 Savoy Place
Optical Fibre Communication
 (IEE Conference Department, Savoy Place, London WC2R 0BL)

Sept. 20-24 Grosvenor House
International Broadcasting Convention
 (IEE Conference Department, Savoy Place, London WC2R 0BL)

Nov. 9-12 Savoy Place
Millimetric Waveguide Systems
 (IEE Conference Department, Savoy Place, London WC2R 0BL)

Nov 22-25 Savoy Place
The Future of Aircraft All-weather Operations
 (IEE Conference Department, Savoy Place, London WC2R 0BL)

Nov. 30-Dec. 2 Mount Royal Hotel
Electronic Displays '76
 (Network, 84 High Street, Newport Pagnell, Bucks MK16 8EG)

AVIEMORE

Sept. 20-24 Coultrybridge Hotel
Impact of New Technologies in Signal Processing
 (IEE, Savoy Place, London WC2R 0BL)

BIRMINGHAM

May 3-7 National Exhibition Centre
IEA-Electrex
 (Industrial and Trades Fairs Ltd., Radcliffe House, Blenheim Court, Solihull, West Midlands, B91 2BG)

May 23-31 National Exhibition Centre
HEDA followed by Sound & Vision '76
 (Montbuild Ltd., 11 Manchester Square, London W1M 5AB)

July 20-22 University of Birmingham
Video and Data Recording
 (IERE, 8-9 Bedford Square, London, WC1B 3RG)

BRIGHTON

Mar. 29-30 University of Sussex
Materials and Processing Effects in Semiconductor Devices
 (The Institute of Physics, 47 Belgrave Square, London SW1X 8QX)

June 8-11 Metropole Convention Centre
Communications '76
 (IEE Conference Department, Savoy Place, London WC2R 0BL)

BRISTOL

July 12-16 University of Bristol
Liquid Metals
 (The Institute of Physics, 47 Belgrave Square, London SW1X 8QX)

CAMBRIDGE

Apr. 17-19 Churchill College
Quantimet Image Analysis Techniques
 (Miss E. J. Jones, Image Analysing Computers Ltd., Moat House, Melbourn, Royston, Herts SG8 6EJ)

June 28-July 2 University of Cambridge
IERE Golden Jubilee Convention
 (IERE, 8-9 Bedford Square, London WC1B 3RG)

EDINBURGH

Sept. 19-22 University of Edinburgh
Gallium Arsenide and Related Compounds
 (Institute of Physics, 47 Belgrave Square, London SW1X 8QX)

MANCHESTER

Jan. 5-7 University of Manchester
Solid State Physics
 (The Institute of Physics, 47 Belgrave Square, London SW1X 8QX)

SOUTHAMPTON

Apr. 6-8 Southampton University
Applications of Electronics in Medicine
 (IERE, 8-9 Bedford Square, London WC1B 3RG)

STONELEIGH

Feb. 24-26 National Agricultural Centre
Audio/Visual in the Midlands
 (D. L. Ford Exhibitions (1968) Ltd., National Agricultural Centre, Stoneleigh, Warwickshire)

SWANSEA

Sept. 7-9 Univeristy College of Swansea
Gas Discharges
 (IEE Conference Department, Savoy Place, London WC2R 0BL)

YORK

Sept. 21-23
Optics
 (The Institute of Physics, 47 Belgrave Square, London SW1X 8QX)

OVERSEAS

Jan. 20-22 Las Vegas
Reliability and Maintainability
 (The American Society of Mechanical Engineers, 345E 47th Street, New York, N.Y.10017, U.S.A.)

Feb. 18-20 Salzburg
Software Engineering for Telecommunication Switching Systems
 (IEE Conference Department, Savoy Place, London WC2R 0BL)

Mar. 2-5 Zurich
53rd AES Convention
 (Audio Engineering Society, 60 East 42nd Street, New York, N.Y.10017, U.S.A.)

Mar. 8-14 Paris
Festival International du Son
 (S.D.S.A., 20 rue Hamelin, 75116, Paris, France)

Apr. 5-10 Paris
Paris Components Show
 (Société pour la Diffusion des Sciences et des Arts, 20 rue Hamelin, F75116 Paris, France.)

Apr. 22-26 Budapest
Acoustics
 (Optical, Acoustical and Filmtechnical Society, H-1061 Budapest, Anker Koz 1, Hungary)

Apr. 28-May 6 Hanover
Hanover Fair
 (Deutsche Messe- und Ausstellungs-AG, P.O. Box 283, 78 Riddlesdown Road, Purley, Surrey CR2 1YB)

May 1-9 Hanover
11th German Aerospace Show
 (Deutsche Messe- und Ausstellungs-AG, P.O. Box 283, 78 Riddlesdown Road, Purley, Surrey CR2 1YB)

May 4-7 Los Angeles
54th AES Convention
 (Audio Engineering Society, 60 East 42nd Street, New York, N.Y.10017, U.S.A.)

May 11-24 Boston
Electro 76
 (IEEE, 3600 Wilshire Boulevard, Los Angeles, California 90010, U.S.A.)

May 22-26 Brussels
Euromation (Instrumentation and Automation)
 (BIRA, Jan Van Rijswijklaan 58, B-2000 Antwerp, Belgium)

June 2-4 Atlantic City
30th Annual Frequency Control Symposium
 (Department of the Army, Headquarters United States Army Electronics Command, Fort Monmouth, New Jersey 07703, U.S.A.)

June 15-18 Basle
Medex 76
 (Sekretariat Medex 76, Postfach, CH-4021 Basle, Switzerland)

Aug. 3-6 Toronto
Computer Communication
 (Dr Pramode K. Verma, Programme Chairman, ICC-76, P.O. Box 365, Station 'A', Ottawa, Ontario, Canada K1N 8V3)

Aug. 27-Sept. 5 Amsterdam
Firato 76
 (RAI, Europaplein, Amsterdam, The Netherlands)

Sept. 6-11 Namur
International Congress of Cybernetics
 (Association Internationale Cybernetics, Palais des Expositions, Place Andre Rijckmans, BM-5000 Namur, Belgium)

Sept. 7-10 Geneva
European Conference on Circuit Theory and Design
 (Istituto Elettrotecnico Nazionale Galileo Ferraris, Corso Massimo d'Azeglio, 42, 10125 Torino, Italy)

Sept. 14-17 Rome
Sixth European Microwave Conference 76
 (Prof. Ing. P. de Santis, Conference Chairman, Selenia S.p.A., Via Tiburtina Km. 12.400, 00131 Rome, Italy)

Sept. 13-15 Eindhoven
Magnetic Bubbles
 (P. F. Bongers, Philips Research Laboratories, Eindhoven, The Netherlands)

Oct. 5-8 Geneva
3rd European Electro-Optics Conference and Exhibition
 (Mack-Brooks Exhibitions Ltd., 62-64 Victoria Street, St. Albans, Herts AL7 3XT)

Oct 18-22 Amsterdam
Fiarex 76
 (RAI, Europaplein, Amsterdam, The Netherlands)

Real and Imaginary

by "Vector"

"CHRISTMAS IS COMING . . ." (or, The Haunted Power Station)

In days of yore it was the pleasant custom for journals to produce what were invariably described as Bumper Xmas Numbers. Large dollops of snow adorned the title on the front cover and holly ran riot everywhere. Inside, normally staid contributors let their hair down and a jolly time was had by all.

With a deferential tug of the forelock I suggested to the Editor that he might revive the practice and combine amusement with instruction. Perhaps Cathode Ray, I said, who has in time past clarified so many matters that perplexed us, might be persuaded to direct his genius to unravelling that Law, known to all electronics engineers by a name which Sir won't let me use. You know — the one which states "That if anything can possibly go wrong it assuredly will, and at the most inconvenient time". And as another feature, I said, why not include the scenario of a pantomime? Heaven knows, the electronics industry writes its own, year after year, complete with cast . . .

At this point the Editor was stricken with apoplexy and had to be revived by his retinue of ravishing secretaries. I won't touch on his subsequent diatribe, which, shorn of its adjectival content, was to the effect that he didn't agree with me.

Tell you what, fellow traditionalists. Christmas Eve is the time for gathering around the log fire and telling ghost stories, so leave what follows until Dec. 24 and then read it.

All right, then. Everybody comfy around the oil-fired radiator? Good. Well then, you may remember that in the November '74 issue I wrote about the odd experiences of Jim, a friend of mine, while investigating an old woollen mill site in the West Country, where his forebears lived. In all, he's now made three visits on successive annual holidays. On the first occasion

he removed a piece of stone from the ruins; this was subsequently psychometrised under experimental conditions and in due course an astonishingly accurate description of the site was given. This mentioned "a strong atmosphere of decay" and described it as "a place of sinister happenings", with death by drowning as a specific instance.

Jim recalled that his mother had told him of the drowning of a little girl in the mill leat and had said that the cottage was haunted. On one occasion she'd been taken, as a small child, to visit her grandparents at the mill cottage. One afternoon, she and her mother had been alone in the house when they heard footsteps cross the bedroom above and descend the stairs. A pause, and then the latch of the stair door lifted — at which her mother snatched her up and ran out of the house.

On his second visit Jim, more or less by chance, found that the granite wall surrounding the site was markedly radioactive — not to anywhere near a dangerous degree but very much higher than the norm for the area. As he wasn't able to get into the site on that occasion, the question of whether the wall represented the peak of radiation or whether a higher source lay inside had to remain unanswered.

This old mill site was, as long ago as 1891, acquired by an electricity supply undertaking, which installed a water-driven generator. The original plant has long since disappeared but the Central Electricity Generating Board still have a water-driven generator there; it's almost certainly the smallest CEGB station in the country. This occupies only a part of the old mill site; the rest being mostly wilderness, but it does explain the granite wall and the need to keep people out.

On his first visit Jim had obtained permission from the SWEB area representative, who, he'd been astonished to find, was a school-fellow of almost half-a-century ago. On the second visit, circumstances forbade a prior arrangement, but this year, on making application, he found that his old school acquaintance had retired and that the succeeding SWEB representative was the son of another old school-fellow! Coincidence number three occurred on the site when, in conversation, he found that in 1930 the power station had been acquired by an electrical firm in his home-town, 250 miles away.

As to the gamma radiation tests on the third visit, nothing sensational materialised. The highest reading was obtained from the ruined wall of the cottage; no peaks were obtained from the ground itself, which is not surprising as I believe that even a few feet of earth will severely attenuate gamma radiation. Possibly then, a local quarry may be the "hot" source, rather than the site itself.

So much for facts as registered by an electronic instrument, but now for the relative quicksands of the unknown. On this occasion the party visiting the site was eleven strong and included the SWEB representative, a professor of electrical engineering and an electronics research engineer, the last-mentioned being a colleague of Jim's.

In the course of the tests it was noticed that the West Highland terrier belonging to Jim's colleague was avoiding the cottage area, although happily trotting around the rest of the site. On several occasions her master stood by the cottage wall and called her; normally obedient, each time she'd approach to within 20 yards, then slow and stop; her tail would droop, she'd exhibit signs of distress and on no account would she come nearer.


Sinister happenings? Well, there was the drowning in the leat. Then there's the grisly circumstance related by an elderly villager. His father had told him that in the woollen mill days there'd been a girl who'd transferred her affections from her intended to one of the mill operatives; the rejected suitor thereupon consulted a "wise woman" who'd cast a spell for him. A couple of days later the mill-worker was caught in the machinery and was so thoroughly dismembered that (to quote the narrator) "they brought him out in one of the big wicker baskets used in the mill".

Another story, which has achieved print, concerns two ladies from London, on holiday in the area. They came across a cottage which looked so delightful that they called, with intent to try to stay there if possible. The door was opened by a pretty little girl, who invited them into the parlour to await her mother. In the room was a white cat curled up on a chair and a black bird in a cage; both of them seemed to regard the visitors with hostility. When the lady of the house arrived she was apologetic, but no rooms were available at the moment. Perhaps later in the year?

In the Autumn the two ladies returned. The cottage had gone; all that was left was a pile of rubble, overgrown with trees and bushes.

Returning to the firm ground of technology, you might be interested to know that the electrical plant of 1891 provided a public supply at 2kV, 100Hz, with stepdown transformers at each drop-out point. One wonders what problems were encountered with line surges caused by resonance and how they were dealt with. The pioneers of high-voltage a.c. transmission lines were S.Z. de Ferranti and Professor J.A. ("diode") Fleming; in 1890 they were just about the only two people in the country with any theoretical knowledge and practical experience of the matter, so it is at least feasible that either or both might have had some part in the enterprise. Perhaps their ghosts haunt the site also!

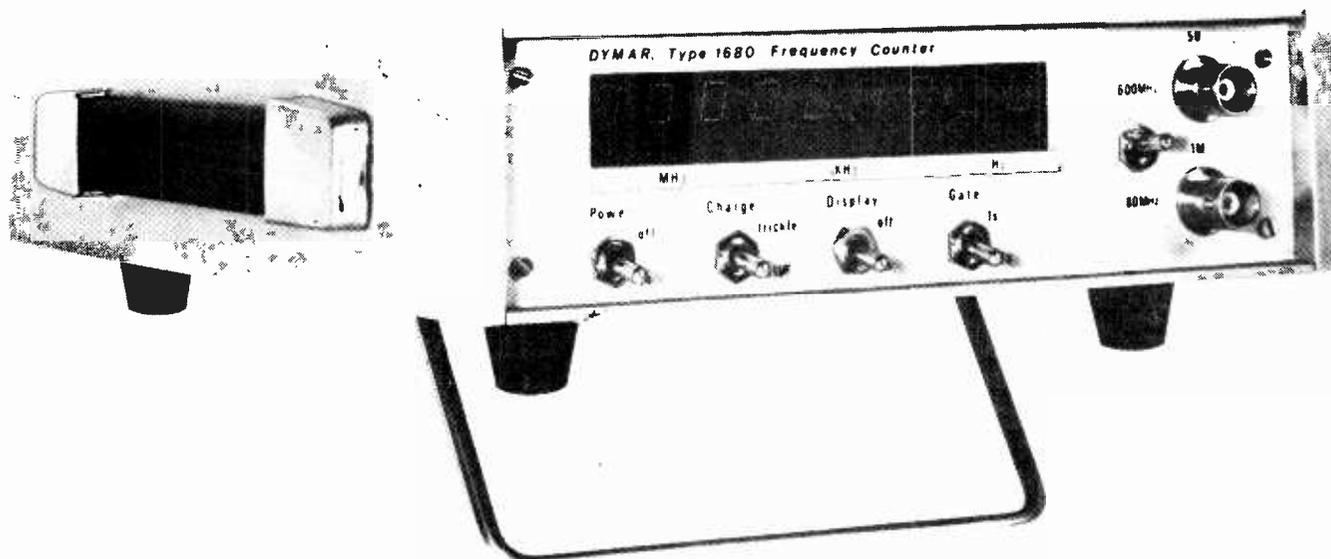The Dymar 1680 portable frequency counter



You're working miles from base,
there's no power handy, and enough AM about
to drive you crazy...

You don't have to have problems in order to appreciate the Dymar 1680 frequency counter. But if they arise you'll know you've got a friend.

At home or away, the 1680 offers a frequency range of from 30Hz to 600MHz with exceptionally high sensitivity right across the range.

A high stability crystal time base provides laboratory standard accuracy in workshop or on location - accuracy which is maintained even in the presence of a large proportion of AM on the carrier wave.

The eight-digit LED display reads in MHz, kHz and Hz, with automatically positioned decimal point, and the front panel controls are simple and easy to use.

In the field, the 1680 really comes into its own. Operating from AC mains supply or its own rechargeable batteries, it provides genuine portability at only 5.5lbs weight and 7.2 x 10.6 x 1.9in dimensions.

Want to know more? Use the Reader Reply Service or contact Dymar direct.

DYMAR

the name in radiotelephones

Designed for the mobile land, marine and air communications industry.

DYMAR ELECTRONICS LIMITED,
Colonial Way, Radlett Road, Watford,
Herts. WD2 4LA. Tel: Watford 37321.
Telex: 923035. Cables: Dymar Watford.

TRANSISTORS + DIODES

Type	Price excluding VAT	Price including VAT	Type	Price excluding VAT	Price including VAT
BC 107	0.090	0.113	2N 930	0.200	0.250
BC 107A	0.130	0.163	2N 1132	0.240	0.300
BC 107B	0.140	0.175	2N 2129	0.240	0.300
BC 108	0.090	0.113	2N 2218A	0.220	0.275
BC 108A	0.130	0.163	2N 2219	0.220	0.275
BC 108B	0.130	0.163	2N 2219A	0.220	0.275
BC 108C	0.140	0.175	2N 2221	0.180	0.225
BC 109	0.090	0.113	2N 2221A	0.210	0.263
BC 109B	0.140	0.175	2N 2222	0.200	0.250
BC 109C	0.140	0.175	2N 2222A	0.250	0.313
BC 184(K)	0.120	0.150	2N 2904	0.190	0.238
BC 212A(K)	0.110	0.138	2N 2905A	0.230	0.288
BC 212B(K)	0.110	0.138	2N 2906	0.170	0.213
BC 213C(K)	0.110	0.138	2N 2906A	0.170	0.213
BC 214B(K)	0.110	0.138	2N 2907	0.220	0.275
BCY 71	0.220	0.275	2N 2907A	0.240	0.300
BFY 50	0.200	0.250	2N 3053	0.180	0.225
BFY 51	0.200	0.250	2N 4037	0.250	0.313
BD 131A	0.360	0.450	1N 4001	0.050	0.054
BD 135	0.360	0.450	1N 4002	0.065	0.070
BD 136	0.396	0.495	1N 4003	0.070	0.076
BD 137	0.432	0.540	1N 4004	0.075	0.081
BD 138	0.450	0.563	1N 4005	0.080	0.086
BD 139	0.495	0.619	1N 4006	0.085	0.092
2N 929	0.230	0.288	1N 4007	0.090	0.097
			1N 4148	0.040	0.050

REPLECOMPS Ltd. Telephone: Hastings 427914
 123 Bohemia Road, ST. LEONARDS-ON-SEA, Sussex TN376RL

quality

Manufactured strictly to stringent specifications. 12 months guarantee.

service

Orders actioned in 24 hours. Over one million transistors in stock.


special discounts

For large quantities ordered by retailers, educational establishments and hobby clubs.

terms

Cash with order, please. Post and Packing 20p. Minimum order 50p.

TAUT SUSPENSION MULTIMETERS Made in USSR

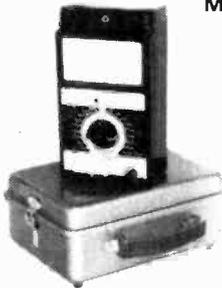

U4312: 41 ranges 0.3mA — 6A D.C., 1.5mA — 6A A.C., 0.3-900v A.C./D.C., 0.2-50kΩ; Mirror scale. Sensitivity 667Ω/v. Accuracy 1% D.C., 1.5% A.C. £10.75.

U4313: 40 ranges 0.06mA — 1.5A D.C., 0.6-1.5A A.C., 1.5-600v A.C./D.C., 0.06-60kΩ; Mirror scale. Sensitivity 20kΩ/v D.C., 2kΩ/v A.C. Accuracy 1.5% D.C., 2.5% A.C. £13.80.

U4315: 43 ranges 0.05mA-2.5A D.C., 0.5mA-2.5A A.C., 1-1000v D.C./A.C., 0.3-500kΩ; Sensitivity 20kΩ/v D.C., 2kΩ/v A.C. Accuracy 2.5% D.C., 4% A.C. £10.00.

U4324: 133 ranges 0.06mA — 3A D.C., 0.3mA — 3A A.C., 0.6-1200v D.C., 3-900v A.C., 0.5-500kΩ; Sensitivity 20,000Ω/v D.C., 4000Ω/v A.C. Accuracy 2.5% D.C., 4% A.C. Re-chargeable cadmium cell operation. £9.85.



LINEAR I.C. AMPLIFIERS

TAA263 — 3 stage low level amplifier. Bandwidth DC to 600kHz. Supply voltage 6-8V. Output power 10mW. TO 72 4-lead £0.65

TAA293 — Med. freq. amplifier up to 600kHz. Supply voltage 6V. Output 10mW into 150Ω. TO 74 10-lead case £0.65


TAA320 — Most stage followed by a bi-polar transistor. Gate-to-source voltage 9-14V. Power dissipation 200mW. Drain current 1μA. TO 18 3-lead £0.60.

DIGITAL 7400 SERIES I.C. Made in USSR

7400	£0.14	7440	£0.14
7401	£0.14	7450	£0.14
7410	£0.14	7453	£0.14
7420	£0.14	7455	£0.14
7422	£0.20	7460	£0.14
7430	£0.14	7472	£0.30
		7474	£0.25

A minimum of 10 assorted I.C. must be ordered. Discount of 10% for any mix, up to 25 and 20% for larger quantities.

OSCILLOSCOPE CI-5 Made in USSR

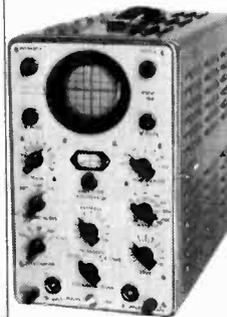

Extremely simple and easy to use single beam oscilloscope. Well proved design based on standard octal valves makes servicing and maintenance straightforward and inexpensive. Because of its bandwidth of 10 MHz the instrument is suitable for general electronic applications and educational purposes where a sophisticated instrument would be both too expensive and delicate. 3-in. tube giving a 50 x 50mm clear display. Amplitude and time base calibrations. Sensitivity 30mm/v max. Triggered and free-running time base, suitable for displaying pulses from 0.1μ sec. to 3 m sec. A.C. mains operation.

Price £44.00 ex. works

Packing and carriage (U.K. only £2.50)

EDUCATIONAL METERS Made in USSR



A range of small portable free-standing meters suitable for experiments and demonstration work. Moving coil movements with centre-pole pieces. 69mm long open scale. Basic calibration accuracy 4%. The following ranges are available: 1, 2, 5, 10 Amps D.C.; 6, 15, 30 Volts D.C. Overall dimensions: 80 x 100 x 48mm.

Price £1.80 ex. works

Packing and postage £0.20 per meter

SPECIAL TELEVISION BARGAINS

FIRST GRADE TRANSISTORS

R2008B	£0.95
R2010B	£1.65
BU126	£1.55
BU133	£1.55
BU208	£2.00

Have you already got our illustrated 1975 catalogue/price list of valves, semiconductors, test equipment and passive components? If not, please send £0.20 for your copy now.


Prices are exclusive of VAT and unless stated otherwise, packing and postage. When remitting cash with order please add £0.80 per millimeter, or £0.20 in £ for other items, as well as VAT (25% for valves, semiconductors and linear I.C.s, and 8% for other equipment)

Z & I AERO SERVICES LTD.

Head Office: 44A WESTBOURNE GROVE, LONDON W2 5SF
 Tel.: 727 5641 Telex: 261306

Retail Branch:
 85 Tottenham Court Road
 London W1. Tel: 580 8403

Pack	Price	Pack	Price
1 Fibreglass printed circuit board for front end, I.F. strip, demodulator, AFC and mute circuits	£2.15	9 Function switch, 10 turn tuning potentiometer, knobs	£5.30
2 Set of metal oxide resistors, thermistor, capacitors, cermet preset for mounting on pack 1	£4.80	10 Frequency meter, meter drive components, fibreglass printed circuit board	£8.60
3 Set of transistors, diodes, LED, integrated circuits for mounting on pack 1	£6.25	11 Toroidal transformer with electrostatic screen, Primary: 0-117V-234V	£4.45
4 Pre-aligned front end module, coil assembly, three-section ceramic filter	£8.80	12 Set of capacitors, rectifiers, voltage regulator for power supply	£2.95
5 Fibreglass printed circuit board for stereo decoder	£1.10	13 Set of miscellaneous parts, including sockets, fuse holder, fuses, inter-connecting wire, etc.	£1.50
6 Set of metal oxide resistors, capacitors, cermet preset for decoder	£2.60	14 Set of metal work parts including silk screen printed fascia panel, acrylic silk screen printed tuning indicator panel insert, internal screen, fixing parts, etc.	£6.50
7 Set of transistors LED, integrated circuit for decoder	£3.45	15 Construction notes (free with complete kit)	£0.25
8 Set of components for channel selector switch module including fibreglass printed circuit board, push-button switches, knobs, LEDs preset adjusters, etc.	£8.30	16 Teak cabinet	£9.85
		One each of packs 1-16 inclusive are required for complete stereo FM tuner.	
		Total cost of individually purchased packs	£76.85

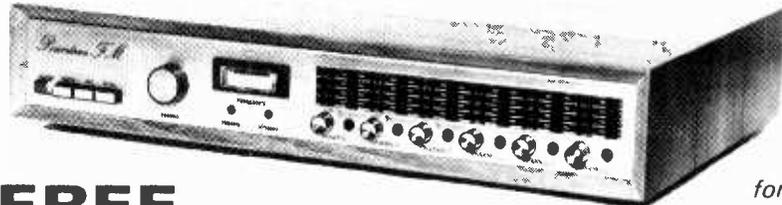

STEREO FM TUNER KIT

In the April and May issues of *Wireless World* there was published a novel design for an f.m. tuner which combines consistent high performance with the elimination of the critical setting-up procedure required by too many earlier tuners. This original circuit has been developed further and is used as the basis for our new slimline unit. The front end is a ready built pre-aligned module which then feeds an amplifier driven screened three section ceramic filter leading to an integrated circuit five-stage limiting amplifier providing excellent a.m. rejection. This is followed by a single coil integrated balanced demodulator from which the audio output may be taken. Temperature compensated varicap tuning allows stations to be selected either by a ten-turn tuning potentiometer or by a choice of six preset push-button controls. Each of the preset controls can be adjusted on the front panel with the settings being indicated by six LED lamps behind an acrylic silk screen printed fascia panel insert. Additional circuitry includes temperature compensated AFC restricted to less than station spacing, inter-station muting, a single-lamp LED tuning indicator and a linear scale frequency meter. The stereo decoder, built on a separate board, is based on a well-proven integrated circuit phase-locked-loop to which has been added active filters to remove sub-carrier harmonics and 'birdies'. The power supply, to ensure station holding stability, uses an integrated circuit voltage regulator which is powered via a low-hum field specially designed TOROIDAL TRANSFORMER.

STYLED TO COMPLEMENT THE WORLD-WIDE ACCLAIMED LINSLEY-HOOD 75W AMPLIFIER

for further information please write for FREE LIST

FREE TEAK CASE WITH FULL KITS

KIT PRICE only **£66.75** carriage free (U.K.)

MORE KITS ON NEXT PAGE!

Typical P. & P. charges at November 1st (E & OE)

EXPORT NO PROBLEM £'s NOW HEAP CHEAP!


By special arrangement the U.K. government has continued its policy of industrial sabotage and stimulation of inflation ensuring the rapid decline in value of sterling, making it even easier for overseas readers to purchase the Powertran range of high-quality audio kits (£ down 12% against U.S. \$ in last 6 months!) Write now for postage quote

	L.H. 75 Watt		F.M. Tuner		T20+20	
	Air	Sea	Air	Sea	Air	Sea
Australia	£42.60	£11.40	£26.05	£7.25	£17.05	£4.65
Canada	£23.50	£8.00	£14.40	£5.05	£9.60	£3.45
Denmark	£10.50	£7.40	£6.00	£4.65	£4.75	£3.25
Germany	£10.50	£7.65	£6.00	£4.80	£4.75	£3.35
New Zealand	£41.60	£10.75	£25.25	£6.85	£16.85	£4.40
Norway	£11.40	£7.30	£6.70	£4.50	£5.20	£3.30
Rep. S. Africa	£25.00	£7.80	£15.15	£4.85	£10.35	£3.45
Sweden	£10.90	£7.25	£6.45	£4.50	£4.95	£3.25
Switzerland	£8.90	£6.85	£5.30	£4.25	£4.10	£3.10
U.S.A.	£23.20	£9.85	£14.25	£6.30	£9.45	£4.05

75W AMPLIFIER KIT

In *Hi-Fi News* there was published by Mr Linsley-Hood a series of four articles (November 1972-February 1973) and a subsequent follow-up article (April 1974) on a design for an amplifier of exceptional performance which has as its principal feature an ability to supply from a direct coupled fully protected output stage, power in excess of 75 watts whilst maintaining distortion at less than 0.01% even at very low power levels. The power amplifier is complemented by a pre-amplifier based on a discrete component operational amplifier referred to as the Linciac which is employed in the two most critical points of the system, namely the equalization stage and tone control stage, positions where most conventional designs run out of gain at the extremes of the frequency spectrum. Unusual features of the design are the variable transition frequencies of the tone controls and the variable slope of the scratch filter. There is a choice of four inputs, two equalized and two linear, each having independently adjustable signal level. The attractive slimline unit pictured has been made practical by highly compact PCBs and a specially designed Toroidal transformer.

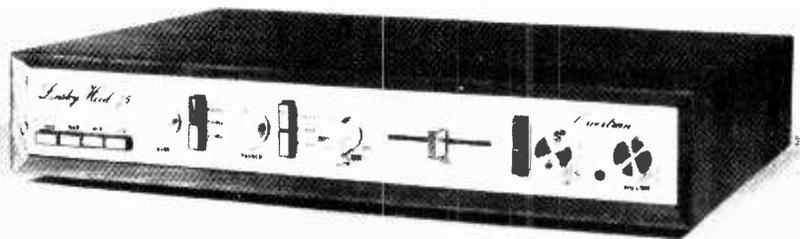Hi-Fi News Linsley-Hood 75W/Channel Amplifier
Mk III Version (modifications as per *Hi-Fi News* April 1974)



Full circuit description in handbook (pack 15—price 30p)

FREE TEAK CASE WITH FULL KITS

KIT PRICE only **£62.40** carriage free (U.K.)

Pack	Price	Pack	Price
1 Fibreglass printed-circuit board for power amp.	£0.85	11 Fibreglass printed-circuit board for power supply	£0.65
2 Set of resistors, capacitors, pre-sets for power amp.	£1.70	12 Set of resistors, capacitors, secondary fuses, semiconductors for power supply	£3.50
3 Set of semiconductors for power amp, inow using BDY58, BD523, BD530	£8.50	13 Set of miscellaneous parts including DIN skts, mains input skt, fuse holder, inter-connecting cable, control knobs	£4.25
4 Pair of 2 drilled, finned heat sinks	£0.80	14 Set of metalwork parts including silk screen printed fascia panel and all brackets, fixing parts, etc.	£8.30
5 Fibreglass printed-circuit board for pre-amp.	£1.30	15 Handbook	£0.30
6 Set of low noise resistors, capacitors, pre-sets for pre-amp.	£2.70	16 Teak cabinet	£9.85
7 Set of low noise, high gain semiconductors for pre-amp	£2.40	2 each of packs 1-7 inclusive are required for complete stereo system	
8 Set of potentiometers (including mains switch)	£2.05	Total cost of individually purchased packs	£72.25
9 Set of 4 push-button switches rotary mode switch	£3.70		
10 Toroidal transformer complete with magnetic screen/housing primary: 0-117-234 V, secondaries: 33-0-33 V, 25-0-25 V.	£9.15		

V A T Please add 25%* to all U.K. orders

(*or at current rate if changed)

U.K. ORDERS — Carriage free (MAIL ORDER ONLY)

SECURICOR DELIVERY: For Securicor delivery to mainland—add £2 + VAT per kit.

OVERSEAS—Postage at cost + 50p special packing, handling (remittance in sterling please)

Dept. WW1

POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE
ANDOVER, HANTS SP10 3NN

Designer-approved

TEXAN AMPLIFIER AND TUNER KITS

... from Henry's Radio. The Sole UK Distributors.

Here's your opportunity to build the superb Texan amplifier and tuner! Designed especially for Henry's by Richard Mann of Texas Instruments, the Texan amplifier was featured in Practical Wireless. Through bulk buying, Henry's are able to offer both these kits of quality components at low cost. Naturally, as sole appointed UK distributors, Henry's offer a full after sales service - so if your kits don't result in properly functioning units, we'll help you sort them out!

TEXAN AMPLIFIER


Incorporating fully integrated stereo preamp and power amp, with 6 IC's, 10 transistors, 6 rectifiers and zener diodes. Plus stabilised, protected circuitry, glass fib pcb, Gardener's low-field low-line mains transformer; and all facilities and controls. Slim design, chassis 14 1/2" x 8 1/2" x 2" overall. Professional appearance and performance. 20 watts per channel RMS, less than 0.1% distortion at 1 kHz.

KIT PRICE

£29.50 inc. VAT
+ £1.00 p & p.
Built & tested £39.50 inc. VAT
+ £1.00 p & p.



**OVER 30,000
ALREADY SOLD**

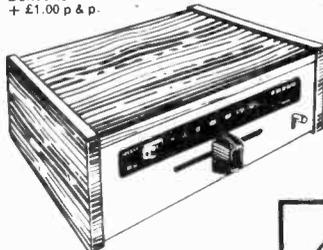

TEXAN TUNER

Featuring varicap tuning and phase lock loop decoder in a professionally designed circuit, this tuner has a glass fibre pcb; built-in AFC; 9 transistors, 1 IC, 9 diodes; and a teak cabinet. Aerial sensitivity 2.5 uV; stereo separation 40 dB; frequency response on stereo 20 - 15,000 Hz ± 3 dB (upper limit set by transmitter), on mono 20 - 22,000 Hz ± 3 dB. Circuit can be altered to cover amateur and aircraft bands. Mains operated.

KIT PRICE £25.95

inc. VAT + £1.00 p & p.
Built & tested £30.95 inc. VAT
+ £1.00 p & p.



ELECTRONIC FOOTBALL & TENNIS VIDEO SPORT

ON YOUR OWN TV

Play three exciting electronic ball games ● FOOTBALL ● TENNIS ● HOLE IN THE WALL on your own TV! Just plug Video Sport into the aerial socket of your TV and away you go. Completely safe for you, your children and your TV. Mains operated.

HENRY'S PRICE ONLY
£27.50 inc. VAT + £2.50 p & p.

IDEAL GIFT
**10,000
ALREADY SOLD!**

Henry's

404/6 EDGWARE ROAD
LONDON W.2 01-402 8381

LOWER SALES FLOOR
231 TOTTENHAM COURT ROAD LONDON W.1 01-636 6682
NEW MIDLANDS STORE
94/96 UPPER PARLIAMENT STREET, NOTTINGHAM 0602-40403

All mail to Henry's Radio, 303 Edgware Road, London W.2

**Benefit from our 30 years' experience
in retail electronics!**

SINCLAIR CALCULATORS

Cambridge **£9.95**. Cam Mem **£13.95**.
Scientific **£13.95**. Oxford 100 **£9.95**.
Oxford 200 **£14.95**. Oxford 300 **£22.98**.
Mains units (state model) **£3.19**.


CBM CALCULATORS

774D 7-digit 4 function model **£5.99**.
385R 8 digit rechargeable with charger
£10.99. 8120D **£20.95**. SR9120D
£26.95. SR6120R **£35.95**. SR4148R
£43.95. Mains unit for D models **£2.95**.

S-Dec **£2.34**
T-Dec **£4.15**
u-DecA **£4.55**
u-DecB **£7.85**

S-DECS AND T-DECS

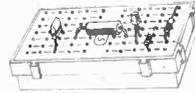IC carriers:
16 dit: plain **£1.18**
With socket **£2.21**
10T05: plain **£1.09**. With socket **£2.08**



SINCLAIR IC20 AMPLIFIERS

IC20 10+10W stereo amp. kit with free booklet and printed circuit **£8.58**.
PZ20 power supply kit for above **£5.91**.
VP20 volume, tone control and preamp kit including printed circuits **£7.95**.

SEND SAE FOR FREE DATA

BATTERY ELIMINATORS

6-WAY SPECIAL

The most versatile battery eliminator ever offered. Switched output of 3, 4 1/2, 6, 7 1/2, 9 and 12V at 500mA **£4.95**.



3-WAY MODEL

Switched output of 6, 7 1/2 and 9V at 250 mA with unique 4 way jack plug and socket output connector **£2.95**.



RADIO MODELS

50mA with poppet battery terminals for radios, etc. 6V **£2.95**.
9V **£4.05**. Double 4 1/2 + 4 1/2V **£3.95**.
6+6V **£3.95**. 9+9V **£4.43**.



CASSETTE MAINS UNITS

7 1/2V output complete with 5-pin DIN plug to run cassette tape recorders from the AC mains **£4.61**.

SINCLAIR PROJECT 80

AFU **£7.55** FM tuner **£13.25**
Z40 **£5.75** Stereo decoder **£8.55**
Z60 **£7.10** Trans for PZ **£5.40**
Q16 **£9.71** Stereo 80 **£13.25**
PZ25 **£6.50** Project 805 **£34.95**
PZ6 **£8.70** PZ8 **£8.20**

JC12 AMPLIFIER

6W IC Audio amp with free data and printed circuit **£2.80**. Special offer: only **£2.45** if bought with deluxe kit.



DELUXE KIT FOR JC12

Includes all parts for the pcb and vol, bass and treble controls for mono version **£2.52**. Stereo version with balance control **£5.20**.

JC12 POWER KIT

Supplies 28V 0.5 amp **£4.77**.

JC12 PREAMP KITS

Type 1 for magnetic pickups, mics and tuners. Mono model **£2.15**. Stereo **£3.70**. Type 2 for ceramic or crystal pickups. Mono **£1.27**. Stereo **£2.33**.
SEND SAE FOR FREE DATA

Prices include post and VAT. Official credit orders from schools, etc., welcome. No VAT charged on overseas orders. All prices are special offers.

SWANLEY ELECTRONICS
P.O. BOX 68, SWANLEY, KENT BR8 8TQ

HART ELECTRONICS

Audio Kit Specialists since 1961



BAILEY/BURROWS/QUILTER PRE AMP This is the tone control section of the best pre-amp kit currently available. Consider the advantages:—*First quality fibreglass printed circuits with roller tinned finish and all component locations printed on reverse. *Low noise carbon film and metal film resistors throughout. *Finest quality low-noise ganged controls with matched tracks and shafts cut to length. *Well engineered layout for total stability. *Special decoupling and earthing arrangements to eliminate hum loops. *Controls, switches and input sockets mount directly on the boards to TOTALLY ELIMINATE wiring to these components. (We know of one pre-amp kit which claims its controls mount directly on the board—and so they do, by their shaft bushes! You still have to wire them up!!)

*We incorporate the Quilter modification which is most important as it reduces distortion and increases the bass and treble control range. As can be seen from the photograph the tone control unit is very slim (only 1 1/2" from front to back) and may therefore be used in many other applications than our Bailey metalwork which it is designed to fit.

F.M. TUNER. Several useful modifications have been made to our compact tuner. The mechanical layout with all its advantages is retained and four important electrical extras are now offered: 1. Multi-turn preset pots for easier tuning. 2. MPX filter for trouble free taping. 3. Extra thermal stabilisation for tuning line to eliminate drift. 4. Provision for remote control tuning of as many stations as you require.

STUART TAPE CIRCUITS Our printed circuits and components offer the easy way to convert any suitable quality deck into a very high quality Stereo Tape unit. Input and output levels suit Bailey pre amp. Total cost varies but around **£35** is all you need. We can offer tape heads as well if you want new ones. All above kits have fibreglass PCB's. Prices exclude VAT but P&P is included.

FURTHER INFORMATION ON ALL KITS FREE if you send us a 9 in. x 4 in. S.A.E.

REPRINTS Post free, no VAT.

Bailey 30W 18p.

STUART TAPE RECORDER All 3 articles under one cover 30p.

BAILEY/BURROWS/QUILTER Preamp circuits, layouts and assembly notes 15p.

All prices exclude VAT.

Penylan Mill, Oswestry, Salop

Personal callers are always welcome, but please note we are closed all day Saturday

QUALITY AMPLIFIER KITS by POWERTRAN

ELECTRONICS

20 WATTS/CHANNEL

Pack	Price
1 Set of all low noise resistors	£0.95
2 Set of all small capacitors	£1.50
3 Set of 4 power supply capacitors	£1.40
4 Set of miscellaneous parts including DIN sockets, fuses, fuse holders, control knobs, etc.	£1.90
5 Set of slide and push-button switches	£1.20
6 Set of potentiometers and selector switch	£2.00
7 Set of all semiconductors	£7.25
8 Special Toroidal Transformer	£4.95
9 Fibreglass PC Panel	£2.50
10 Complete chassis work, hardware and brackets	£4.20
11 Preformed cable/leads	£0.40
12 Handbook	£0.25
13 Teak Cabinet	£4.50

TOROIDAL T20 + 20

Developed from the famous Practical Wireless Texan

Designed by Texas engineers and published in a series of articles in **Practical Wireless**. The TEXAN was a remarkable breakthrough in delivering true Hi-Fi performance at exceptionally low cost. Now further developed to include a true Toroidal transformer, this slimline integrated circuit design, based upon a single F/Glass PCB, features all the normal facilities found on quality amplifiers, including scratch and rumble filters, adaptable input selector and headphones socket.



KIT PRICE STILL ONLY £28.25
post free (U.K.)

FREE TEAK CASE and HANDBOOK with full kits

AND NOW OUR NEW T30 + 30 30 WATT VERSION!

The T20+20 already a development from the very successful Texan, has been developed still further to include all the improvements suggested in the P.W. July 1975 follow-up article and our new model offers RF interference filters, tape monitor facility and an additional 10 watts/channel of power

Pack	Price
1 Set of all low noise resistors	£1 05
2 Set of all small capacitors	£2 10
3 Set of 4 power supply capacitors	£2 05
4 Set of miscellaneous parts including DIN sockets, fuses, fuse holders, control knobs, etc.	£1 90
5 Set of slide and push button switches	£1 20
6 Set of potentiometers and selector switch	£2 00
7 Set of all semiconductors	£7 75
8 Special Toroidal Transformer	£6 80
9 Fibreglass PC Panel	£2 90
10 Complete chassis work, hardware and brackets	£4 80
11 Preformed cable leads	£0 40
12 Handbook (free with complete kit)	£0 25
13 Teak Cabinet	£4 50

FULL KIT (WITH FREE TEAK CASE) ONLY £32.95

WIRELESS WORLD AMPLIFIER DESIGNS

Component packs for a choice of three outstanding amplifiers are stocked together with packs for a regulated power supply suitable for use with a pair of any of them. Also stocked are packs for a very well-established pre-amplifier—the Bailey-Burrows design which features six inputs, a scratch and rumble filter and wide range tone controls which may be either rotary or slider operating.

30W BAILEY

Pk. 1 F/Glass PCB	£1.00
Pk. 2 Resistors, capacitors, pots	£2.35
Pk. 3 Semiconductor set	£4.70

Pk. 3R Rotary potentiometer set	£2 00
Pk. 3S Slider potentiometer set (with knobs)	£2 70

20W LINSLEY-HOOD

Pk. 1 F/Glass PCB	£1.05
Pk. 2 Resistors, capacitors, pots	£3.20
Pk. 3 Semiconductor set	£3.35

STUART TAPE RECORDER

A set of three printed-circuit boards has been prepared for the stereo integrated circuit version of this high-performance *Wireless World* published design.

60V REGULATED POWER SUPPLY

Pk. 1 F/Glass PCB	£0.95
Pk. 2 Resistors, capacitors, pots	£1.95
Pk. 3 Semiconductor set	£3.10

TRRP Pk. 1 Replay amplifier F/Glass PCB	£1 10
TRRC Pk. 1 Record amp./meter drive cct. F/Glass PCB	£1 60

BAILEY-BURROWS PRE-AMP

Pk. 1 F/Glass PCB	£2.35
Pk. 2 Resistors, capacitors, pre-sets, transistors	£6 10

TROS Pk. 1 Bias/erase/stabilizer cct. F/Glass PCB	£1 20
---	-------

For details of component packs for this design please write for free list.

ACTIVE FILTER CROSSOVER

An essential and critical component in a high-quality speaker system is the crossover unit conventionally comprising of a series of passive networks which unfortunately, though introducing reactive impedances between the amplifier and the speakers, result in the loss of the advantage of high amplifier damping factor and renders the speakers prone to overshoots and resonances. An elegant solution to this problem, described by D. C. Read in *Wireless World*, involves the use of a series of active filters splitting the output of the pre-amplifier into three channels, of closely defined bandwidth, each of which is fed to the appropriate speaker by its own power amplifier. A design for a suitable 20-watt amplifier, based on a proven Texas circuit, was also described by Mr Read. The printed-circuit board for this has been designed such that three amplifiers may be stacked and mounted together on a common heat sink to achieve a conveniently compact module.

ACTIVE FILTER

Pack	Price
1 Fibreglass PCB (accommodates all filters for one channel)	£1.05
2 Set of pre-sets, solid tantalum capacitors, 2% metal oxide resistors, 2% polystyrene capacitors	£4.20
3 Set of semiconductors	£2.65
2 off each pack required for stereo system	

READ/TEXAS 20w amp.

Pack	Price
1 Fibreglass PCB	£0.70
2 Set of resistors, capacitors pre-sets (not including O/P coupling capacitors)	£1.10
3 Sets of semiconductors	£2.40
6 off each pack required for stereo system	
4 Special heat sink assembly for set of 3 amplifiers	£0.85
5 Set of 3 O/P coupling capacitors	£1.00
2 off packs 4, 5 required for stereo system	

POWER SUPPLY

FOR 20W/CHANNEL STEREO SYSTEM	
Pack	Price
1 Fibreglass PCB	£0.50
2 Set of rectifiers, zener diode, capacitors, fuses, fuse holders	£2.60
3 Toroidal transformer	£4.95

SUITABLE ALSO FOR FEEDING ANY OF OUR HIGH-POWER DESIGNS

MORE KITS ON PAGE 85

SEMICONDUCTORS

as used in our range of quality amplifiers

2N699	£0.25	BFY51	£0.20
2N1613	£0.20	BFY52	£0.20
2N1711	£0.25	CA3046	£0.70
2N2926G	£0.30	LP1186	£5.50
2N3055	£0.85	MC1310	£2.90
2N3442	£1.30	MC1351	£1.05
2N3711	£0.09	MFC3010	£0.95
2N3904	£0.17	MJ481	£1.20
2N3906	£0.20	MJ491	£1.30
2N4062	£0.11	MJE521	£0.60
2N4302	£0.60	MPSA05	£0.25
2N5087	£0.42	MPSA12	£0.55
2N5210	£0.54	MPSA14	£0.35
2N5457	£0.45	MPSA55	£0.25
2N5459	£0.45	MPSA65	£0.35
2N5461	£0.50	MPSA66	£0.40
2N5830	£0.30	MPSU05	£0.60
40361	£0.40	MPSU55	£0.70
40362	£0.45	SBA750A	£2.50
BC107	£0.10	SL301	£1.30
BC108	£0.10	SL3045	£1.60
BC109	£0.10	SN72741P	£0.40
BC109C	£0.12	SN72748P	£0.40
BC125	£0.15	TIL209	£0.30
BC126	£0.15	TIP29A	£0.50
BC182	£0.10	TIP30A	£0.60
BC212	£0.12	TIP29C	£0.71
BC182K	£0.10	TIP30C	£0.78
BC212K	£0.12	TIP41A	£0.74
BC182L	£0.10	TIP42A	£0.90
BC184L	£0.11	TIP 41B	£0.82
BC212L	£0.12	TIP 42B	£0.88
BC214L	£0.14	1N914	£0.07
BCY72	£0.13	1N916	£0.07
BD529	£0.85	1S920	£0.10
BD530	£0.85	5B05	£1.20
BDY56	£1.60		
BF257	£0.40	FILTERS	
BF259	£0.47	FM4	£0.80
BFR39	£0.25	5FG10 7MA	£2.80
BFR79	£0.25		

V.A.T. Please add 25%* to all U.K. orders

(*or at current rate if changed)

U.K. ORDERS—Post free (mail order only)

SECURICOR DELIVERY—for this optional service (Mainland only) add £2.00 + VAT per kit

OVERSEAS—Postage at cost + 50p special packing, handling (remittance in sterling please)

Dept. WW1

POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE
ANDOVER, HANTS SP10 3NN

CASED TRANSFORMERS

Housed in smart resin coated steel cases with 3 core power cable and outlet socket, fused primary winding. Isolation types are fitted with 3 pin outlet sockets and are available with 110 volt or 240 volt output (Please state). Auto types are fitted with 2-pin flat style sockets up to 500 VA. 3 pin sockets from 750 to 3000 VA. See Auto and Isolation sections for prices. Plugs extra.



SAFETY ISOLATING

Prim. 120/240V Sec. 120/240V Centre Tap with screen

VA (WATTS)	REF No.	PRICE Cased	PRICE Plugs 2 Pin + 1 Earth	PRICE Open	Post
20	148	5.25	0.98	3.75	0.72
60	149	9.03	0.98	4.70	0.72
100	150	9.87	0.98	5.35	0.85
200	151	12.29	0.98	8.61	0.97
250	152	13.81	0.98	10.31	1.18
350	153	16.54	0.98	12.50	1.28
500	154	18.38	0.98	14.31	1.44
750	155	28.72	1.25	22.12	0.84
1000	156	37.44	1.25	30.57	0.84
1500	157	44.37	1.25	34.98	0.84
2000	158	52.45	2.95	38.91	0.84
3000	159	77.18	2.95	61.51	0.84

MINIATURE & EQUIPMENT

Primary 240V with Screen

VOLTS		MILLIAMPS		REF No.	PRICE	Post
Sec. 1	Sec. 2	Sec. 1	Sec. 2			
3-0.3	—	200	—	238	1.56	0.34
0-6	0-6	500	500	234	1.56	0.34
0-6	0-6	1900	1000	212	2.12	0.46
9-0.9	—	100	—	13	1.60	0.34
0-9	0-9	330	330	235	1.62	0.34
0-9	0-9	500	500	207	1.69	0.46
0-9	0-9	1000	1000	208	2.79	0.46
15-0.15	—	40	—	240	1.55	0.34
0-15	0-15	200	200	236	1.56	0.34
20-0.20	—	30	—	241	1.55	0.34
0-20	0-20	150	150	237	1.56	0.34
0-15-20	0-15-20	500	500	205	2.88	0.58
0-20	0-20	300	300	214	2.03	0.61
0-20	—	3500	No Screen	1116	3.45	0.97
20-12-0	—	700	—	221	2.50	0.61
12-20	—	(D.C.)	—	—	—	—
0-15-20	0-15-20	1000	1000	206	2.85	0.72
0-15-27	0-15-27	500	500	203	3.16	0.58
0-15-27	0-15-27	1000	1000	204	4.55	0.72

12 and 24 VOLTS PRIMARY 200-240 Volts

AMPS	REF No.	PRICE	PRICE Plugs 2 & 3 pin	PRICE Open	Post
12V	24V				
0.3	0.15	242	1.66	0.34	
0.5	0.25	111	1.60	0.46	
1	0.5	213	1.90	0.61	
2	1	71	2.47	0.61	
4	2	18	3.07	0.62	
6	3	70	4.50	0.72	
8	4	108	5.11	0.85	
10	5	72	5.63	0.85	
12	6	116	5.80	0.85	
20	8	11	7.26	0.97	
30	10	115	10.96	1.18	
40	15	187	14.06	1.36	
60	20	232	15.63	0.84	
3000	30	226	17.70	0.84	

TRANSFORMERS

30 VOLTS

PRIMARY 200/240V
SECONDARY 12, 15, 20, 24, 30V

AMPS	Ref. No.	Price	Post
0.5	112	2.04	0.61
1	79	2.57	0.66
2	3	3.91	0.72
3	20	4.80	0.85
4	21	5.58	0.85
5	51	6.75	0.95
6	117	7.52	0.97
8	88	9.93	1.18
10	89	10.27	1.18

50 VOLTS

PRIMARY 200/240V
SECONDARY 19, 25, 33, 40, 50V

AMPS	Ref. No.	Price	Post
0.5	102	2.71	0.61
1	103	3.58	0.66
2	104	5.30	0.85
3	105	6.10	0.85
4	106	7.97	1.08
6	107	12.93	1.18
8	118	13.75	1.44
10	119	17.79	1.86

BRIDGE RECTIFIERS

ONE AMP	Price	FOUR AMP	Price
50 P.I.V.	0.25	100 P.I.V.	0.55
100 P.I.V.	0.25	200 P.I.V.	0.59
200 P.I.V.	0.28	400 P.I.V.	0.65
600 P.I.V.	0.30	600 P.I.V.	0.75


SPECIAL OFFER!
2 KVA ISOLATORS
Fully impregnated & screened
2 primary windings 110V each
2 secondary windings 115V each
(2 matching transformers)
£29.50 plus carr. & VAT.

TWO AMP	Price	SIX AMP	Price
50 P.I.V.	0.35	50 P.I.V.	0.65
100 P.I.V.	0.40	100 P.I.V.	0.70
200 P.I.V.	0.45	200 P.I.V.	0.80
400 P.I.V.	0.50	400 P.I.V.	0.90

Add 25% VAT on all prices

POWER UNIT

TYPE
CC12-05
British
Made

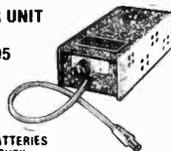

**SAVES BATTERIES
SAVES MONEY**
Housed in smart steel case, finished in hard epoxy coating. Screened for safety.

Output switched 3, 4.5, 6, 7.5, 9 and 12 Volts at 500 mA D.C. Operates from 240 V mains, suitable for Radios, Tape Recorders, Record Players, etc. Size 7.5 x 5.0 x 14.0 cm. Price £4.05 Post 30p. Plus 25% VAT.

AUTO TRANSFORMERS

VA (Watts)	Ref No.	PRICE	PRICE Plugs 2 & 3 pin	PRICE Open	Post
Tapped at 115, 220, 240 Volts					
20	113	4.31	0.25	1.88	0.61
Tapped at 115, 200, 220, 240 Volts					
150	4	6.99	0.25	4.28	0.72
200	65	7.67	0.25	5.21	0.78
300	66	8.67	0.25	6.11	0.85
500	67	11.82	0.25	9.48	1.18
750	83	14.81	0.95	11.30	1.28
1000	84	18.38	0.95	14.35	1.44
1500	93	23.26	0.95	19.22	0.84
2000	95	35.07	1.80	25.49	0.84
3000	73	50.61	2.35	36.12	0.84

NEW! 2" AND 4" PANEL METERS

2"		4"	
SIZE: 60mm Wide x 45mm High x 40mm Deep.	Movement	SIZE: 110mm Wide x 82mm High x 43mm Deep.	Movement
0.50 micro A	1250 Ohms	0.50 micro A	1400 Ohms
0.100 micro A	580	0.100 micro A	730
0.500 micro A	170	0.500 micro A	200
0.1 mA	170	0.1 mA	200
0.5 mA	170	0.5 mA	200
0.10 mA	6	0.10 mA	6
0.50 mA	0.5	0.50 mA	0.5
0.100 mA	0.5	0.100 mA	0.5
0.500 mA	0.5	0.500 mA	0.5
0.1 AMP	0.5	0.1 AMP	0.5
0.2 AMP	0.5	0.2 AMP	0.5
0.25 Volt	15k	0.25 Volt	15k
0.50 Volt	50k	0.50 Volt	50k
0.300 Volt	300k	0.300 Volt	300k
VU Meter	170	VU Meter	200
	9250	VU Meter	5250

VU Meters are complete with detectors. Modern wide view. Price 2" £3.20 Post 10p. Price 4" £4.00 Post 10p. Lamps 60p per set plus 8% VAT

C1000 MULTI-METER

Compact General Purpose Mini Multimeter
Input Resistance 1000 ohms per volt
Ranges AC Volts 0-15 50 250 1000 Volts
DC Volts 0-10 50 250 1000 Volts
DC Current 0.1 mA 0-100 mA
Resistance 0-150k ohms
Size 65 x 24 x 90 mm
Complete with Batteries, Test Prods. Instructions



Special price £3.35 Post 30p Plus 8% VAT

1/4-WATT CARBON FILM RESISTORS

also available 1/4 watt at 70°C E 12 range 100-1MΩ 5% tol above 470KΩ 10% tol. at 95p per 100. Plus 25% VAT.

MINIATURE NEONS

6mm dia. 1.2mm length leads length approx. 20mm. Recommended ballast resistor: 150K ohms for 240 Volt operation. Price: Packet of 10 for 60p. Postage 15p Plus 8% VAT

PLEASE ADD 8% VAT ON ALL TRANSFORMERS

Send 25p for Catalogue

A.S.P. LTD.

DEPT. WW1, SIMMONDS ROAD, WINCHEAP, CANTERBURY, KENT. Tel: (0227) 52436

KINNIE COMPONENTS

10 NELMES WAY,
HORNCHURCH, ESSEX RM11 2QZ
HORNCHURCH 45167

COPPER LAMINATE P.C. BOARD

8.4 x 7.7 inch. 3 for 75p. P.P. 25p.
9.45 x 8.15 inch. 3 for 90p. P.P. 30p.
10.10 x 7.90 inch. 3 for £1. P.P. 30p.
13.1 x 9.4 inch. 3 for £1.20. P.P. 30p.
17 x 9.5 inch. 2 for £1.20. P.P. 30p.

MONSTER PACK

10 PIECES 10.1in x 7.90in PLUS FREE BOTTLE OF CIRCUIT ETCHANT £2.50. P.P. 50p.

TELEPHONE DIALS (new) £1. P.P. 15p

EXTENSION TELEPHONES (Type 706) Various colours. £3.95. P.P. 75p.

RATCHET RELAYS (310 ohm) Various types £1.20. P.P. 20p.

UNISELECTORS (New) 25 way. 12 Bank (Non bridging). 68 ohms. £6.50. P.P. 50p.

MINIATURE UNISELECTOR (Ex. Equip.) 6 Bank (5 non bridging, 1 bridging) 100 ohms 24-30 V.D.C. £1.50. P.P. 50p.



OVERLOAD CUT-OUTS. Panel mounting (1 1/4 x 1 1/4 x 1/2in.). 800 M/A/1.8 amp-10 amp 45p. P.P. 5p

ADVANCE TRANSFORMERS "VOLSTAT". Input 240v. A.C.

C.V.50. 38v at 1 amp. 25v at 100 m/a. 75v at 200 m/a £3. P.P. 65p

C.V.75. 25v at 2 1/2 amp £3.25. P.P. 75p

C.V.100. 50v at 2 amp. 50v at 100 m/a £4. P.P. 75p

C.V.250. 25v at 8 amp. 75v at 1/2 amp £6.50. P.P. £1 50

C.V.500. 45v at 3 amp. 35v at 2 amp £12. P.P. £1 75

H.T. TRANSFORMER. Prim. 110/240v Sec. 400v 100 m/a £3. P.P. 65p

L.T. TRANSFORMER "TOROIDAL". Prim. 240v Sec. 30v. at 1/2 amp Size 3 in dia. 1 thick £1.65. P.P. 20p

L.T. TRANSFORMER. Prim. 240v. Sec. 27-0-27 at 800 m/a 7.5 amp £2.25. P.P. 50p

L.T. TRANSFORMER. Prim. 110/240v Sec. 50v at 10 amp £10. P.P. £1 50

L.T. TRANSFORMER. Prim. 240v. Sec. 18v. at 1.5 amp & 12v @ 1 amp £2.25. P.P. 50p

L.T. TRANSFORMER. Prim. 240v. Sec. 18v. 1 amp. £1. P.P. 20p

L.T. TRANSFORMER. Prim. 240v. Sec. 12v at 1 amp. 70p. P.P. 25p

ALL PRICES INCLUDE V.A.T. EXCEPT WHERE SURCHARGE IS INDICATED

QUADROPHONIC DECODER MODULE. C.B.S./S.Q. Type. using I.C. MC 1312P. With slight modification direct substitute for P.E. "RONDO" Board. Complete with Data. £4 each

15% V.A.T. Surcharge

S.T.C. CRYSTAL FILTERS (10.7 Mhz). 445-LQU-901A (50 Khz spacing). £3. P.P. 20p. 445-LQU-901B (25 Khz spacing). £4. P.P. 20p. 10.7 M.H.Z. Canned I.F.s Size 1 x 1/2 x 1/2in (with data) 65p. P.P. 10p

3 GANG TUNING CAPACITOR 8.5 PF to 320 PF 80p. P.P. 20p

V.H.F./U.H.F. POWER TRANSISTORS (type BLY3B) 3 watt output at 100-500 Mhz. £2.25. P.P. 10p

MINIATURE METERS 500 Micro amp. (level/stereo beacon etc.) scaled half black/half red. Size 1 x 1 inch 65p. P.P. 15p

HIGH CAPACITY ELECTROLYTICS

2,200.µf/100v (4 x 1 1/4in) 90p. P.P. 20p. 2,500.µf/100v (4 x 2in) 90p. P.P. 20p. 4,700.µf/25v (2 x 1 1/4in) 65p. P.P. 15p. 10,000.µf/25v (4 1/2 x 1 1/2in) 75p. P.P. 25p. 6,800.µf/63v (3 x 2in) £1. P.P. 20p. 25,000.µf/40v (4 3/4 x 2 1/2in) £1.25. P.P. 25p. 47,000.µf/40v Powerlytic (5 1/2 x 3in) £2. P.P. 50p. 100,000.µf/10v Powerlytic (4 1/2 x 3in) £1.50. P.P. 30p. 160,000.µf/10v Powerlytic (6 x 3in) £2. P.P. 50p

MULTICORE CABLE. 6-core (6 colours) 14/0076 Screened P.V.C. 22p per yard; 100 yards at £16.50. P.P. 2p a yard. 7-core (7 colours) 7/22mm Screened P.V.C. 22p per yard; 100 yards £16.50. P.P. 2p per yard. 30-core (15 colours) 25p per yard; 100 yards £20. P.P. 2p per yard

RIBBON CABLE (8 colours). 10m £1.65. P.P. 20p. 100m 8-core 7/.mm Bonded side by side £11.50. P.P. £1

TRANSFORMERS

L.T. TRANSFORMER. Prim. 110/240v Sec. 23/24/25v at 10 amps £7. P.P. £1

L.T. TRANSFORMER. Prim. 110/240v Sec. 20/21/22v at 8 amp £6. P.P. £1


L.T. TRANSFORMER. Prim. 110/240v Sec. 0/24/40v at 1 1/2 amp (Shrouded) £1.95. P.P. 50p

L.T. TRANSFORMER. Prim. 200/250v Sec. 20/40/60v at 2 amp (Shrouded) £3. P.P. 50p

L.T. TRANSFORMER. (H.D.) Prim. 200/250v Sec. 18v at 27 amp. 40v at 9.8 amp. 40v at 3.6 amp. 52v at 1 amp. 25v at 3.7 amp £17.50. P.P. £2 50

100 WATTS !

HY200

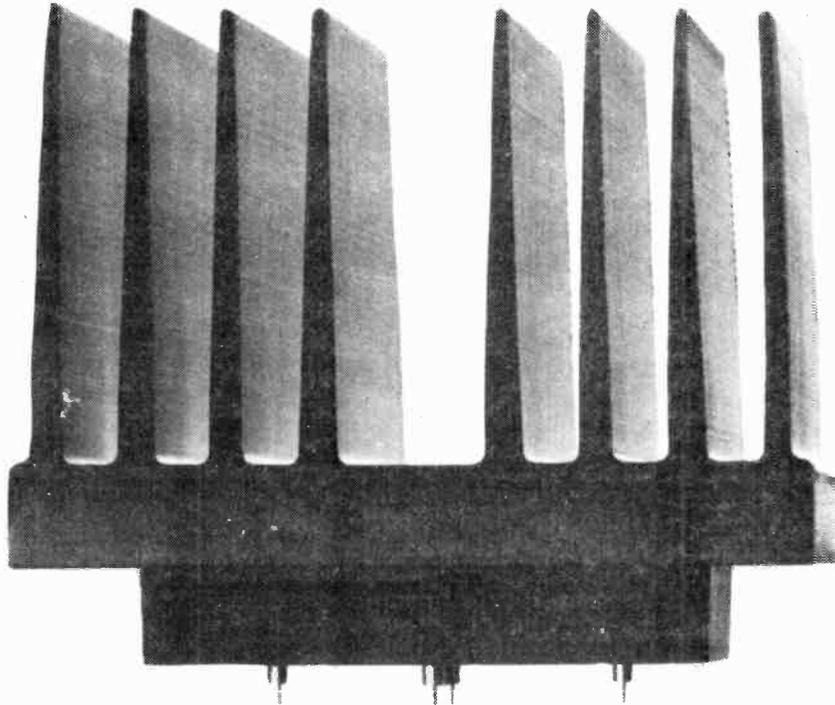

The HY200 is the latest hybrid amplifier from I.L.P. It has been designed to be virtually indestructible lending itself to domestic and industrial applications. Latest design techniques including thermal shutdown make the HY200 the most advanced amplifier of its kind in the World. Only five connections are required, input, output, power lines and earth.

Features:

Short Circuit Protection
No External Heatsinking
Thermal Shutdown
Only Five Connections
Low Distortion

Price £21.20 + VAT £5.30
P&P free

Specifications:

Output Power 100 watts R.M.S. into 8Ω
Input Impedance $100K\Omega$
Input Sensitivity 500mV R.M.S.
Distortion 0.05% Typical
Signal: Noise 96dB
Power Band Width 10Hz - 45KHz ± 3 dB
Power Supply 45-0-45v D.C. at 2 Amps
Weight 1 Kilo (2.2lb)
Power Supply PSV90 suitable for one HY200
Price £10.56 + VAT £2.64
P&P free

TWO YEARS GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd,
Crossland House,
Nackington, Canterbury,
Kent CT4 7AD
Tel (0227) 63218

Please Supply _____
Total Purchase Price _____
I Enclose Cheque Postal Orders Money Order
Please debit my Access account Barclay card account
Account number _____
Name & Address _____
Signature _____

More than just a catalogue!


PROJECTS FOR YOU TO BUILD

4-digit clock, 6-digit clock, 10W high quality power amp., High quality stereo pre-amp., Stereo Tuner, F.M. Stereo decoder, etc., etc.

CIRCUITS . . . Frequency Doublers, Oscillators, Timers, Voltmeters, Power Supplies, Amplifiers, Capacitance Multiplier, etc., etc. . . .

Full details and pictures of our wide range of components, e.g. capacitors, cases, knobs, veroboards, edge connectors, plugs and sockets, lamps and lampholders, audio leads, adaptor plugs, rotary and slide potentiometers, presets, relays, resistors (even 1% types!), switches, interlocking pushbutton switches, pot cores, transformers, cable and wire, panel meters, nuts and bolts, tools, organ components, keyboards, L.E.D.'s, 7-segment displays, heatsinks, transistors, diodes, integrated circuits, etc., etc., etc. . . .


Really good value for money at just 40p.

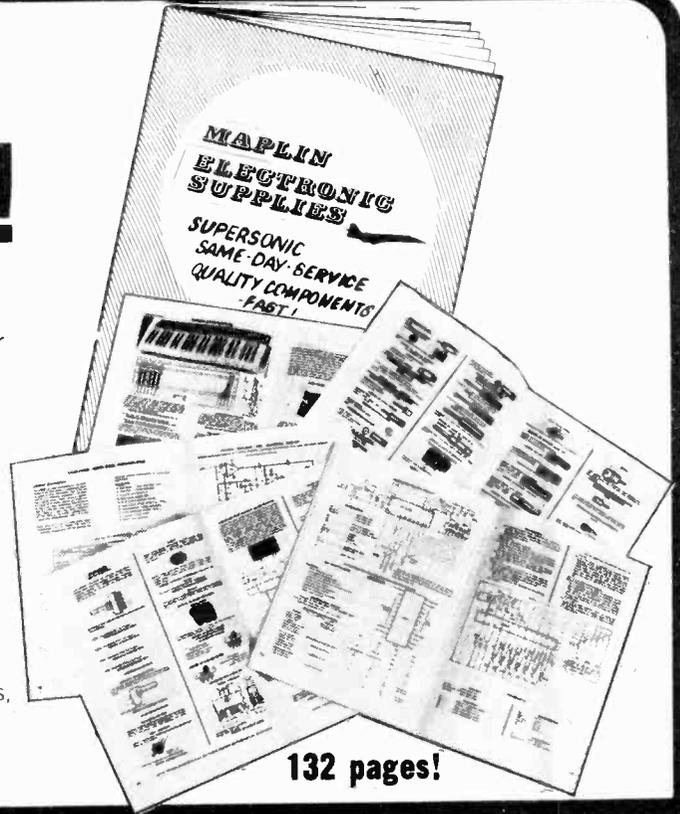

132 pages!

The 3600 SYNTHESISER

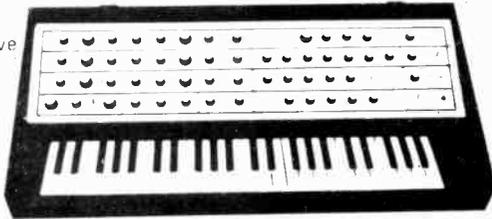
The 3600 synthesiser includes the most popular features of the 4600 model, but is simpler. Faster to operate, it has a switch patching system rather than the matrix patchboard of the larger unit and is particularly suitable for live performance and portable use.



S.A.E. please for price list


The 4600 SYNTHESISER

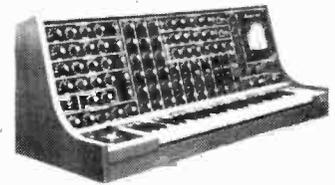We stock all the parts for this brilliantly designed synthesiser, including all the PCBs, metalwork and a drilled and printed front panel, giving a superb professional finish.



Opinions of authority agree the ETI International Synthesiser is technically superior to most of today's models. Complete construction details available now in our booklet price £1.50, or S.A.E. please for specification

GRAPHIC EQUALIZER

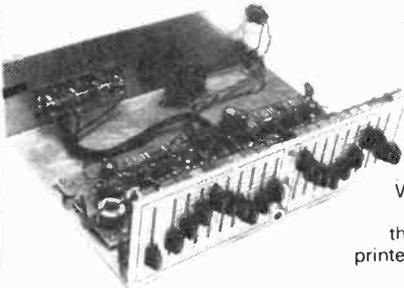

A really superior high quality stereo graphic equaliser as described in Jan. 1975 issue of ETI. We stock all parts (except woodwork) including all the metal work drilled and printed as required to suit our components and PCBs.

Complete reprint of article — price 15p.

ELECTRONIC ORGAN

Build yourself an exciting Electronic Organ. Our leaflet MES51, price 15p, deals with the basic theory of electronic organs and describes the construction of a simple 49-note instrument with a single keyboard and a limited number of stops. Leaflet MES52, price 15p, describes the extension of the organ to two keyboards each with five voices and the extension by an octave of the organ's range.

Solid-state switching and new footages along with a pedal board and a further extension of the organ's range are shown in leaflet MES53, price 35p. (Pre-publication price 15p).



NO MORE DOUBTS ABOUT PRICES

Now our prices are GUARANTEED (changes in VAT excluded) for two month periods. We'll tell you about price changes in advance for just 30p a year (refunded on purchases). If you already have our catalogue send us an s.a.e. and we'll send you our latest list of GUARANTEED prices. Send us 30p and we'll put you on our mailing list — you'll receive immediately our latest price list then every two months from the starting date shown on that list you'll receive details of our prices for the next GUARANTEED period before the prices are implemented! plus details of any new lines, special offers, interesting projects and coupons to spend on components to repay your 30p

NOTE: The price list is based on the Order Codes shown in our catalogue so an investment in our super catalogue is an essential first step.

Call in at our shop, 284 London Road, Westcliff on Sea, Essex. Please address all mail to



MAPLIN ELECTRONIC SUPPLIES
P.O. Box 3 Rayleigh Essex SS6 8LR.

I enclose Cheque/P.O. value _____
For _____ copy/copies of your Catalogue
Name _____
Address _____

ww

MAPLIN ELECTRONIC SUPPLIES P.O. Box 3 Rayleigh Essex SS6 8LR

DEMA ELECTRONICS INTERNATIONAL

ELECTRONIC COMPONENTS DISTRIBUTOR FOR INDUSTRY AND HOBBYIST

MONTHLY SPECIALS from DEMA ELECTRONICS

CT5002 Battery Oper 5001	£ 1.19	555 Timer	£ 0.40
CT5005 12 Digit 4 Funct w/Mem	1.49	556 Dual Timer	0.70
MM5314 24 Pin 6 Digit Mux	2.75	1CL8038 Funct Gen Volt Contr	
MM5375 4 or 6 Digit Alarm	1.95	Oscillator Sine, Sq	1.95
CT7001 4 or 6 Digit Alarm	3.75	9-Digit LED Display Comm Cath Comp	
1101 256 Bit Ram Mos	1.05	w/8 Digit Clk Chips 12' Char	1.95
1103 1024 Bit Ram Mos	1.95	7446	65
5261 1024 Bit Ram L/Power	1.95	7448	45
1702A 2KE Prom U/Violet	9.95	7475	27
5203 2048 Bit U/Violet PROMS	9.95	7490	30
2102 1024 Bit Status Ram	2.95	7493	33
		74123	39

TTL 7400 SERIES

7400	£ 0.11	7440	£ 0.11	7485	£ 0.85	74155	£ 0.69
7401	0.11	7441	0.60	7486	0.24	74156	0.69
7402	0.11	7442	0.55	7488	2.50	74157	0.69
7403	0.11	7443	0.55	7489	1.50	74158	0.69
7404	0.13	7444	0.50	7490	0.40	74160	0.89
7405	0.13	7445	0.75	7491	0.55	74162	0.89
7406	0.22	7446	0.85	7492	0.43	74163	0.89
7407	0.22	7447	0.75	7493	0.43	74164	1.05
7408	0.14	7448	0.65	7494	0.49	74165	1.05
7409	0.14	7450	0.12	7495	0.49	74166	1.05
7410	0.11	7451	0.13	7496	0.55	74170	1.65
7411	0.16	7453	0.13	74100	0.89	74175	0.90
7413	0.26	7454	0.14	74107	0.27	74180	0.80
7416	0.22	7450	0.11	74121	0.27	74181	2.50
7417	0.22	7470	0.24	74122	0.37	74182	0.80
7420	0.11	7472	0.21	74123	0.49	74192	0.90
7426	0.23	7473	0.25	74145	0.57	74193	0.85
7430	0.12	7474	0.25	74150	0.59	74194	0.85
7432	0.22	7475	0.37	74151	0.59	74195	0.80
7437	0.25	7476	0.26	74153	0.69	74198	1.70
7438	0.25	7483	0.69	74154	1.05	74199	1.70

HIGH SPEED 74H00

74H00	£ 0.16	74H20	£ 0.16	74H52	£ 0.16	74H71	£ 0.21
74H01	0.16	74H21	0.16	74H53	0.16	74H72	0.26
74H04	0.16	74H22	0.16	74H54	0.21	74H74	0.28
74H05	0.21	74H30	0.16	74H55	0.16	74H76	0.28
74H08	0.16	74H40	0.16	74H60	0.16		
74H10	0.16	74H50	0.16	74H61	0.16		
74H11	0.16	74H51	0.21	74H62	0.16		

CMOS 4000 SERIES

4000A	£ 0.19	4014	£ 1.10	4028	£ 0.95	4071	£ 0.23
4001	0.19	4015	1.10	4030	0.50	4072	0.25
4002	0.19	4016	0.55	4042	0.95	4073	0.25
4006	0.90	4019	0.67	4043	1.20	4075	0.25
4007	0.19	4020	1.15	4044	1.20	4078	0.25
4008	1.30	4021	1.10	4049	0.48	4081	0.25
4009	0.49	4023	0.19	4050	0.48	4082	0.29
4010	0.49	4024	0.85	4066	0.75	4528	0.85
4011	0.19	4025	0.19	4068	0.23	4585	1.25
4013	0.39	4027	0.75	4069	0.23		

DTL

930	£ 0.10	936	£ 0.10	944	£ 0.10	962	£ 0.10
932	0.10	937	0.10	946	0.10	963	0.10

LINEARS

LM300	TO99	£ 0.45	340U	TO92	£ 1.25	739	A DIP	£ 0.65		
301	V DIP	0.29	380	A DIP	80	741	V DIP	0.22		
302	TO99	0.45	381	A DIP	1.05	747	A DIP	0.44		
304	TO100	0.50	546	V DIP	0.51	748	V DIP	0.27		
305	TO99	0.60	550	A DIP	0.55	5558 (1456)	V DIP	0.65		
307	V DIP	0.38	555	V DIP	0.45	5558 (1458)	V DIP	0.65		
			TO99	0.45	556	B DIP	0.75	ULN 2111	A DIP	0.95
308	A DIP	0.59	560	B DIP	2.55	LM3900	A DIP	0.35		
	TO99	0.79	561	B DIP	2.55	75450	V DIP	0.45		
309K	TO3	1.45	562	B DIP	2.55	75451	V DIP	0.45		
310	T pkg	0.65	565	A DIP	1.25	75452	V DIP	0.45		
311	V DIP	0.90	566	V DIP	1.20	75453	V DIP	0.45		
320K	TO 3 NEG	567	V DIP	1.25	75454	V DIP	0.45			
	5.2, 12, 15	1.25	709	A DIP	0.22	75491	A pkg	0.65		
324	A DIP	1.07	710	A DIP	0.25	75492	A pkg	0.75		
339	A DIP	1.49	711	A DIP	0.30					
340K	TO3	2.10	723	A DIP	0.38					

V = Mini Dip, A = 14L Dip, B = 16 Dip, TO99 = 8 Pin Header, TO100 = 10 Pin Header
Data sheets supplied on request. Add 20p ex. excepted as noted.

MEMORIES w/DATA

1101 256 Bit Ram Mos	£ 1.79	5001 Cal Chip	£ 0.99
1103 1024 Bit Ram Mos	2.25	5002 Cal Chip	1.19
7489 (8225) 64 Bit Ram TTL	1.50	5005 Cal Chip	1.49
8223 Programmable ROM	2.50	5311 Clock Chip	2.95
5260 1024 Bit Ram Low Power	1.95	5312 Clock Chip	2.95
		5313 Clock Chip	2.95
		5314 Clock Chip	3.45
		5316 Clock Chip	3.95

LEDS

MV 5020 Jumbo Red or Clear	£ 0.15		
MAN 1 Red 7 Seg. 270'	1.30		
MAN 3A Red Seg. 127	35		
MAN 5 Green 7 Seg. 270	1.75		
MAN 6 Solid Seg	2.50		
9 Digit Array Fairchild 37 with clear magnifying lens	2.95		

DISCOUNTS:

10% on orders over £ 10	MIN ORDER £ 2.5	All Items New Branded
15% on orders over £ 15		Guaranteed By DEMA ELECTRONICS

TERMS: PRICES LISTED ARE BRITISH POUNDS & PENCE. SEND CHEQUE WITH ORDER. MASTERCHARGE, BANKAMERICARD, BARCLAY CARD ACCEPTED. TERMS OFFERED TO SCHOOLS & INSTITUTIONS.

POSTAL AND HANDLING CHARGES SHIPMENT VIA AIR MAIL under 4.99 add 0.35 £ 10 and over 5.00-9.99 add 0.25 No Charge

DEMA ELECTRONICS INTERNATIONAL P.O. Box 407 San Ramon, Ca. 94583 USA Cable DEMAELINTL

TRANSFORMERS

ALL EX-STOCK - SAME DAY DESPATCH

MAINS ISOLATING VAT 8% **12 and/or 24-VOLT**
PRI 120/240V SEC 120/240V
CENTRE TAPPED AND SCREENED

Ref. No.	VA (Watts)	£	P&P p	Ref. No.	AMPS 12v	AMPS 24v	£	P&P p
07	20	3.77	58	111	0.5	0.25	1.54	28
149	60	4.69	72	213	1.0	0.5	1.86	58
150	100	5.33	85	71	2	1	2.41	58
151	200	8.54	1.12	18	4	2	2.97	72
152	250	10.32	1.41	70	6	3	4.43	72
153	350	12.47	1.41	108	8	4	5.09	85
154	500	14.33	1.61	72	10	5	5.50	85
155	750	21.94	BRS	116	12	6	5.80	97
156	1000	30.51	BRS	17	16	8	7.48	97
157	1500	34.89	BRS	115	20	10	10.91	1.61
158	2000	38.92	BRS	187	30	15	14.20	1.41
159	3000	61.48	BRS	226	60	30	17.67	BRS

50 VOLT RANGE

SECONDARY TAPS 01-19-25-33-40-50V

Ref. No.	Amps	£	P&P p
102	0.5	2.71	58
103	1.0	3.55	72
104	2.0	4.95	85
105	3.0	6.10	97
106	4.0	7.98	1.12
107	6.0	12.71	1.25
118	8.0	13.63	1.61
119	10.0	17.75	BRS

30 VOLT RANGE

SECONDARY TAPS 0-12-15-20-25-30V

Ref. No.	Amps	£	P&P p
112	0.5	1.90	58
79	1.0	2.52	72
3	2.0	3.77	72
20	3.0	4.70	85
21	4.0	5.56	85
51	5.0	6.73	97
117	6.0	7.52	1.12
88	8.0	10.20	1.25
89	10.0	10.36	1.41

60 VOLT RANGE

SECONDARY TAPS 0-24-30-40-48-60V

Ref. No.	Amps	£	P&P p
124	0.5	2.48	72
126	1.0	3.68	72
127	2.0	5.33	85
125	3.0	7.90	97
123	4.0	9.19	1.41
40	5.0	10.24	1.25
120	6.0	12.07	1.41
121	8.0	15.75	BRS
122	10.0	19.40	BRS
189	12.0	20.25	BRS

AUTO TRANSFORMERS

Ref. No.	VA (Watts)	AUTO TAPS	£	P&P p
113	20	0-115-210-240	1.75	5T
64	75	0-115-210-240	3.05	72
4	150	0-115-210-220-240	4.33	72
66	300		6.11	85
67	500		9.36	1.25
84	1000		14.36	1.61
93	1500		19.02	BRS
95	2000		25.41	BRS
73	3000		36.84	BRS

SCREENED MINIATURES

Ref. No.	mA	Volts	£	P&P p
238	200	3-0-3	1.62	39
212	1A1A	0-6-0-6	1.93	46
13	100	9-0-9	1.56	25
235	330 330	0-9-0-9	1.64	25
207	500 500	0-8-9-0-8-9	2.02	51
208	1A 1A	0-8-9-0-8-9	3.07	58
236	200 200	0-15-0-15	1.56	25
214	300 300	0-20-0-20	2.03	58
221	700 (DC)	20-12-0-12-20	2.38	58
206	1A 1A	0-15-20-0-15-20	3.63	72
203	500 500	0-15-27-0-15-27	3.15	72
204	1A 1A	0-15-27-0-15-27	4.14	72
S112	500	12-15-20-24-30	1.97	58*

HIGH VOLTAGE

MAINS ISOLATING
PRI 200/220 OR 400/440
SEC 100/120 OR 200/240

VA	Ref.	£	P&P p
60	243	4.37	97
350	247	10.93	1.41
1000	250	26.31	BRS
2000	252	44.12	BRS

SPECIAL OFFER

Cased Isolator & Transformer 1KVA, PRI 240v, sec. 115V
Few only £33.50 BRS

PLUS

P. F. RALFE

10 CHAPEL ST. LONDON NW1.

Phone 01-723 8753

SIGNAL GENERATORS

MARCONI TF801D/IS. 10-480 mHz P.O.A.
MARCONI TF801B/2S. 10-480 mHz £225.
HGN MS3/U. 9.7-11.9 and 77-109 mHz. AM/FM.
ADVANCE SG63D. AM/FM 7.5-230mHz £125.
RACAL/AIRMEC 201A. 30kHz-30mHz. As new. P.O.A.
ADVANCE SG21 VHF Square-wave generator 9kHz-100mHz. £25.



OSCILLOSCOPES

SOLARTRON CD1400 DC-15mHz.
COSSOR CDU110. DC-80mHz
TEKTRONIX 545A with CA unit. DC-30mHz. Price only £295.00
TEKTRONIX 531 DC-15mHz with L type plug-in
TEKTRONIX 535 DC-15mHz with L type plug-in
TEKTRONIX 545B DC-30mHz with 'CA' plug-in.
TEKTRONIX 585A. DC-80mHz with type 82 plug-in.
TEKTRONIX 654B. Storage oscilloscope.
TEKTRONIX 502. 200uV. Sens. X-Y.
TEKTRONIX C27 Polaroid Camera. Series 125 with 560 series adapter.



MISCELLANEOUS TEST EQUIPMENT

MARCONI TF1400S double pulse generator with TM6600/S secondary pulse unit. £105.
MARCONI TF791D deviation meter. 4-1024mHz. 0-100kHz deviation.
MARCONI 455E Wave Analyser £120.
MARCONI TF2600 Valve Voltmeter 1mV-300V. Excellent. £75.
ROHDE & SCHWARZ USVD calibrated receiver 280-940mHz (4600mHz)
LEVELL TG200 DM. RC Oscillator. c/w case. £65.
ROHDE & SCHWARZ URV milli-voltmeter BN10913 (late type) 1mV-10V. With 'T' type insertion unit, free probe and attenuator heads. 1kHz-1,600mHz. £175.
COSSOR 1453 True RMS milli-voltmeter. Excellent. £75.
AIRMEC TYPE 210 modulation meter. Excellent condition.
ROHDE & SCHWARZ "SCR" V.H.F. Signal Generator 1000-1900 mHz
MARCONI type TF936 Impedance Bridge. £85.00.
GERTCH Phase Angle V. Meters. Range 1mV-300V, in 12 ranges.
SOLARTRON oscillator type CO 546. 25Hz-500kHz. £30.00.
GAMBRELL Precision 4 Decade Resistance Box. 1-11, 110 ohms. £24.50.

BOXER INSTRUMENT

FANS
 Dimensions 4.5 x 4.5 x 1.5 ins.
 Very quiet running, precision fan specially designed for cooling electronic equipment, amplifiers etc. For 110V. AC operation—(practise is to run from split primary of mains transformer or use suitable mains dropper). CC only 11 Watts. List price over £10 each. Our price, in brand new condition, is £4.50.

POWER SUPPLIES

WEIR Electronics modular unit. Model OCAR. Regulated & stabilised. 0-7V @ 2A. £9.50.

Centrifugal blowers by WOODS. 8 inch snail type. Outlet 2 1/4 x 2 in 24V DC 2.8A. 2400 r.p.m. Grey stove finish. All brand new. Price is £10.50 + carriage.

MANY TYPES of RF plugs and sockets in stock:—

BNC plugs 50Ω. 30p. **BNC** sockets 50Ω. 25p. **N**. Type plugs 50Ω. 50p. **Burndep** plugs. 40p. **Burndep** sockets. 40p. **Miniature** PYE. 20p. **Miniature** sockets. 20p.

All connectors are brand new. Immediate delivery. Please add appropriate postage.

AEI miniature uniselectors. Type 2200C. 3 banks. 1 bridging. 2 non-bridging wipers. 12 positions. Coil resistance 50 ohms. Complete with bases. Brand new. £4.50 each.
20-way BPO Jack strips to accept 316 type Jack plugs. Also quantity of 316 plugs available. All good condition.

PLEASE ADD 8% V.A.T. TO THE TOTAL AMOUNT WHEN ORDERING. INCORRECT AMOUNTS WILL CAUSE DELAY IN DESPATCH. THANK YOU.

GENTS/FRIEDLAND fire alarm bells Operating voltages 12v dc/24v dc. All in as new condition and tested before despatch. Sizes 6/8/12 inch. Prices £4.80, £5.20 and £6.50 resp.

COMPUTER PERIPHERALS. Tape punches. 8 hole by Westrex and other well known manufacturers. Tape readers by Elliot. All virtually brand new. Prices are better than one half the maker's. Write or phone for quotation.

An exceptional buy enables us to offer stabilised and regulated power supplies by APT at a very cheap price. 16-24v dc @ 10 Amps, and 8-10v dc @ A. Both supplies are extremely stable with low ripple voltage. Price each £18.50 + carriage.

MINIATURE DEAC Ni-Cad. batteries type 70DK. 3 cells in package 25x17x15mm. 75p, post paid.

GEC Courier Walkie-Talkies 3 Channel Re-chargeable batteries. Mid-band. £55 pair.

E.M.I. oscilloscopes model WM16 with type 771 W.B.A. plug-in unit. Supplied in perfect condition complete with trolley. £125.00.

HEWLETT PACKARD/BOONTON TYPE 8900B
 Peak-power calibrator. Measures true peak power ±.6 db absolute. Frequency range 50-2000Mhz. RF power range 200mW peak, full-scale. RF Impedance 50 ohms. P.O.A.

MARCONI TF995A2/M AM/FM R.F. SIGNAL GENERATORS. 1.5-220mHz. 0-100kHz Deviation. 1μV-100mV output. Sold in excellent condition. P.O.A.

SQ IS A TRADEMARK OF CBS INC.

**NEW
LOW
PRICES!**

SQ QUADRAPHONIC DECODERS

SQ the leading quadraphonic system, designed by CBS engineers offers not only 4 channel ambiphony from the fast expanding range of SQ encoded discs but also immensely increased depth and fullness of sound from standard stereo recordings too

Feed 2 channels (200-1000mV as obtainable from most pre amplifiers) into your choice of any of our 3 decoders and take 4 channels out with no overall signal level reduction. On the logic enhanced decoders Volume Front Back LF RF LB RB and Dimension controls can all be implemented by simple single gang potentiometers—no need for exotic 4-gang units!

These state-of-the-art circuits used under licence from CBS are offered in kit form comprising first grade components only—fibre glass circuit boards of professional quality designed for edge connector insertion all resistors 2% metal oxide all polystyrene and polycarbonate capacitors 5% or better and in decoder L2 ultra low noise (MPS A18-0 5dB typ) transistors used in each amplifying stage

M1 Basic matrix decoder with fixed 10/40 blend 10 Resistors 14 Capacitors 1 Integrated Circuit. Printed Circuit Board £5.90.
L1 Full logic controlled decoder with 'wave matching and front back logic' for enhanced channel separation using three specially designed Integrated Circuits 24 Resistors 42 Capacitors 3 Integrated Circuits Printed Circuit Board £17.20.
L2 More advanced full logic decoder with variable blend extended frequency response increased front back separation 43 Resistors 44 Capacitors 3 Integrated Circuits 9 Transistors 6 Diodes Printed Circuit Board £24.60.
 All kits include IC sockets and construction notes. Prices include CBS licence fee
 Please write for further details in FREE LIST
 United Kingdom Post Free Please add 25% VAT Overseas No VAT Please add (per kit) £2 00 p & p AIR MAIL or £1 00 p & p SURFACE MAIL


AMBIENTACOUSTICS

PO BOX 3000
ANDOVER, HANTS SP10 3LQ.

WW—040 FOR FURTHER DETAILS

RADFORD HD250

High Definition Stereo Amplifier

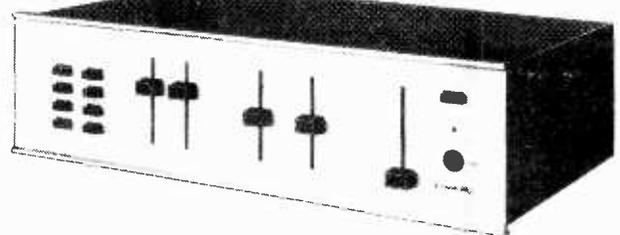

A new standard for sound reproduction in the home! We believe that no other amplifier in the world can match the overall specification of the HD250.

Rated power output: 50 watts av. continuous per channel into any impedance from 4 to 8 ohms, both channels driven.

Maximum power output: 90 watts av. per channel into 5 ohms.

Distortion, preamplifier: Virtually zero (cannot be identified or measured as it is below inherent circuit noise.)

Distortion, power amplifier: Typically 0.006% at 25 watts, less than 0.02% at rated output (Typically 0.01% at 1 KHz)

Hum and noise: Disc.—83dBV measured flat with noise band width 23 KHz (ref 5mV); —88dBV "A" weighted (ref. 5mV)

**Line —85 dBV measured flat (ref 100v)
 —88dBV "A" weighted (ref 100v)**

Hear the HD250 at

SWIFT OF WILMSLOW

Dept WW

5 Swan Street, Wilmslow, Cheshire (Tel. 26213)
 Mail Order and Personal Export enquiries: Wilmslow Audio, Swan Works, Bank Square, Wilmslow (Tel. 29599)

In stock: All Radford speaker drive units and crossovers, ZD22 preamp, Low Distortion oscillator LD03 and Distortion Measuring set DMS3.

WW—041 FOR FURTHER DETAILS

CHROMASONIC electronics

Dept. 5, 56, Fortis Green Road,
Muswell Hill, London, N10 3HN.
telephone: 01-883 3705

C - MOS

	1-24	25-99	100up
CD4000AE	19p*	17p*	14p*
CD4001AE	19p*	17p*	14p*
CD4002AE	19p*	17p*	14p*
CD4006AE	£1.59	£1.33	£1.06
CD4007AE	23p*	19p*	15p*
CD4009AE	£1.75	£1.46	£1.17
CD4010AE	Use	CD4049*	
CD4011AE	Use	CD4050*	
CD4012AE	19p*	17p*	14p*
CD4013AE	19p*	17p*	14p*
CD4014AE	£1.75	£1.46	£1.17
CD4015AE	£1.75	£1.46	£1.17
CD4016AE	55p*	48p*	44p*
CD4017AE	£1.29	£1.07	93p*
CD4018AE	£1.89	£1.56	£1.25
CD4019AE	80p*	66p*	53p*
CD4020AE	£1.97	£1.64	£1.31
CD4021AE	£1.75	£1.46	£1.17p
CD4022AE	19p*	17p*	14p*
CD4023AE	£1.83	£1.53	£1.22
CD4024AE	£1.26	£1.05	84p*
CD4025AE	19p*	17p*	14p*
CD4026AE	£2.79	£2.32	£1.86
CD4027AE	98p*	82p*	65p*
CD4028AE	£1.53	£1.28	£1.02
CD4029AE	£1.89	£1.56	£1.15
CD4030AE	71p*	59p*	47p*
CD4035AE	£1.75	£1.46	£1.17
CD4040AE	£2.01	£1.69	£1.34
CD4042AE	£1.49	£1.24	99p*
CD4046AE	£2.15	£1.79	£1.44
CD4049AE	69p*	58p*	46p*
CD4050AE	69p*	58p*	46p*
CD4051AE	£2.78	£2.32	£1.85
CD4052AE	£2.78	£2.32	£1.85
CD4056AE	£2.12	£1.76	£1.41
CD4060AE	£2.39	£1.99	£1.55
CD4066AE	£1.13	94p*	75p*
CD4068AE	28p*	24p*	19p*
CD4069AE	28p*	24p*	19p*
CD4070AE	28p*	24p*	19p*
CD4071AE	28p*	24p*	19p*
CD4077AE	71p	59p*	47p*
CD4081AE	28p*	24p*	19p*
CD4082AE	28p*	24p*	19p*
CD4085AE	£1.28	£1.06	85p*
CD4086AE	£1.28	£1.06	85p*
CD4093AE	£1.56	£1.20	£1.04
CD4099AE	£2.95	£2.46	£1.96
CD4511AE	£2.36	£1.79	£1.44
CD4528AE	£1.30	£1.08	87p*

I.C. SOCKETS



Pin Sockets, pins in strips of 100. Just snip off what you need. 65p per strip.

Dual in line

8 pin 13p.	24 pin 26p.	TOS
14 pin 15p.	28 pin 30p.	8 pin 31p.
16 pin 15p.	36 pin 39p.	10 pin 35p.

FREE CIRCUITS

Our 8 Page A4 Audio I.C. Booklet is supplied FREE with purchases of Linear I.C.'s worth £1. or more (35p. if sold alone) Contains circuits and pin connections

15 Amplifiers 250 mW to 20 watts

5 Audio Pre-Amplifiers

1 Tape Pre-Amplifier

1 Power Driver

1 Instrument Amplifier (Bifet)

1 General Purpose Mini Amplifier

1 D.C. Controlled Gain Control

1 Micro-mini radio (2 I.C.'s)

PHOTO-DARLINGTON



V_{ceo} 25v 2N5777

V_{ceo} 25v

V_{be} 6v

I_b 250 mA

P_d 200 mW

Hfe 2500

35p

LINE-O-LIGHT



NEW LED Linear Cursors each device contains 10 light emitting diodes in a 20 pin dual-in-line package. Ideal for solid state analogue meters or dials. Type 101 RED £2.26. Complete with leaflet.

74 TTL

	1-24	25-99	100+
7400	14p*	12p*	10p*
7401	14p*	12p*	10p*
7402	14p*	12p*	10p*
7403	15p*	12p*	10p*
7404	16p*	13p*	11p*
7408	16p*	13p*	11p*
7409	16p*	13p*	11p*
7410	16p*	13p*	11p*
7413	29p*	24p*	20p*
7417	27p*	22p*	20p*
7420	16p*	13p*	11p*
7427	27p*	22p*	18p*
7430	16p*	13p*	11p*
7432	27p*	22p*	18p*
7437	27p*	22p*	18p*
7441	75p*	62p*	50p*
7442	65p*	55p*	43p*
7445	85p*	71p*	57p*
7447	81p*	75p*	65p*
7448	75p*	63p*	50p*
7447A	95p*	83p*	67p*
7470	30p*	25p*	20p*
7472	25p*	21p*	17p*
7473	30p*	25p*	20p*
7474	32p*	26p*	21p*
7475	47p*	39p*	31p*
7476	32p*	26p*	21p*
7482	75p*	62p*	50p*
7485	£1.30	£1.09	87p*
7486	32p*	26p*	21p*
7489	£2.92	£2.80	£2.10
7490	49p*	40p*	32p*
7491	65p*	55p*	45p*
7492	57p*	46p*	36p*
7493	45p*	40p*	33p*
7495	67p*	55p*	45p*
74100	£1.08	89p*	72p*
74107	35p*	28p*	22p*
74121	34p*	28p*	23p*
74122	47p*	39p*	31p*
74141	78p*	63p*	53p*
74145	68p*	58p*	48p*
74154	£1.62	£1.48	86p*
74174	£1.00	83p*	67p*
74180	£1.06	88p*	71p*
74181	£3.20	£2.50	£1.90
74192	£1.35	£1.14	90p*
74193	£1.35	£1.14	90p*
74196	£1.64	£1.34	99p*

REGULATORS 100 mA

78105WC (TO-92)	60p*
78L12WC (TO-92)	60p*
78L15WC (TO-92)	60p*

REGULATORS 100mA

78L05AWC (TBA625A)	90p*
78L12AWC (TBA625B)	90p*
78L15AWC (TBA625C)	90p*

REGULATORS 500mA

78M05HC	£1.35
78M12HC	£1.35
78M15HC	£1.35
78M18HC	£1.35
78M24HC	£1.35

REGULATORS 1A

7805KC (TO-3)	£2.09
7812KC (TO-3)	£2.09
7815KC (TO-3)	£2.09
7818KC (TO-3)	£2.09
7824KC (TO-3)	£2.09

REGULATORS 1A

7805UC (TO-220)	£1.72
7812UC (TO-220)	£1.72
7815UC (TO-220)	£1.72
7818UC (TO-220)	£1.72
7824UC (TO-220)	£1.72

ICL8030 £3.52

LINEAR I.C.'s

AY-1-0212	£6.93
AY-1-5051	£1.44
AY-5-1224	£3.95
AY-5-3500	£6.59
AY-5-3507	£6.59
AY-5-4007	£7.94


BHA0002 £3.01

CA2111	£1.19
CA3045	£1.69
CA3046	88p
CA3053	59p
CA3065	£1.60
CA3075	£1.64
CA3078	£1.26
CA3080	59p
CA3081	£1.86
CA3082	£1.86
CA3089E (TDA1200)	£2.43
CA3097E	£1.67
CA3123E	£1.76
CA3130	84p
CA3401E (LM390C)	68p
CA3600E	£1.44

LM2111	£1.12
LM3900	69p
LM3909	66p*
MC1303L	£1.94
MC1306P	85p
MC1310P	£2.10
MC1312P	£2.52
MC1314P	£4.34
MC1315P	£4.85
MC1327P	£1.48
MC1335P	89p
MC3401P	81p
MC1339P	£1.60
MC1350	68p
MC1351	92p
MC1352	92p
MC1357	£1.60
MC1358(CA3065)	£1.23
MC1375	£1.56
MC1455 (555T)	85p*
MC1456C	£1.77
MC1458C(1)	89p
MC1468G	£2.30
MC1495L	£4.48
MC1496G	£1.01
MC3302P	£1.65
MC3401P	81p

MFC4000B	87p
MFC4050A	85p*
MFC6030A	85p*
MFC6040	£1.01
MM5314	£4.80
MM5316	£9.99
MVRSV (TO-3)	£1.45
MVR12V (TO-3)	£1.45
MVR15V (TO-3)	£1.45
NE540	£1.25
NE542A	£1.16
NE555V	69p*
NE556	£1.29
NE560B	£5.06
NE568	£5.06
NE568B	£5.06
NE568C	£5.06
NE568D	£5.06
NE568E	£5.06
NE568F	£5.06
NE568G	£5.06
NE568H	£5.06
NE568I	£5.06
NE568J	£5.06
NE568K	£5.06
NE568L	£5.06
NE568M	£5.06
NE568N	£5.06
NE568O	£5.06
NE568P	£5.06
NE568Q	£5.06
NE568R	£5.06
NE568S	£5.06
NE568T	£5.06
NE568U	£5.06
NE568V	£5.06
NE568W	£5.06
NE568X	£5.06
NE568Y	£5.06
NE568Z	£5.06
SD6000	£1.22
SL414A	£2.09
SL415A	£2.75
SL437D	£7.50
SL440	£2.84
SN75491N	88p*
SN75492N	£1.10
TDA1054	£1.50
TDA1200	£2.43
TDA1405	80p*
TDA1412	80p*
TDA1415	80p*
TDA2010	T.B.A.
TDA2020	T.B.A.
ULN2111A	£1.52
ZN414	£1.26

3 1/2 DECADE DVM I.C.

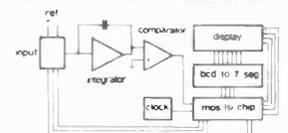

This state-of-the-art MOS LSI chip contains all the logic necessary for a 3 1/2 decade, dual slope integrating, automatic polarity detecting DVM. Supplied with free data and circuit booklet. AY-5-3507


OUR PRICE ONLY £6.59* (Data and Circuit Booklets alone 20p.)

The AY-5-1224 tick-tock

Another marvel from G.I. A 16 pin 12-24 hr. Clock I.C. with 25 pin capability and low external parts count. Supplied with manufacturers detailed leaflet £3.95p*(inc. VAT) (Leaflet alone 20p.) Full Kit (excluding case) available towards end of 1975. Phone Clive for details.

MULLARD MODULES

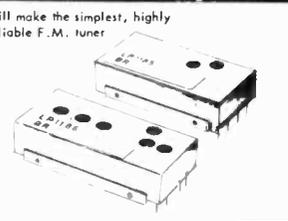Still make the simplest, highly reliable F.M. tuner



LP1188 Varactor front end £8.80
LP1185 1F Strip £6.95
LP1400 Multiplex decoder £9.02

REGULATORS 100 mA

78105WC (TO-92)	60p*
78L12WC (TO-92)	60p*
78L15WC (TO-92)	60p*

LED DISPLAYS

Litronix Double Digit Displays 0.5" Common Anode, 2 R/H Decimal Positions DL721 ± 1.9 DL727 0.0 to 9.9 Suitable for Clocks, Meters, Instruments, Channel Indicators Our price £4.75 * each



Low cost Red GaAsP 0.33" Litronix DL 707 Series
Matsushita MLED 500 in a TO92 package 0.33" Monsanto MAN 50/70/80/3600
Xciton XAN 70 Series 0.33" Monsanto MAN 4000 Series
0.63" Litronix DL747 'Jumbo' Series

REGULATORS 100mA

78L05AWC (TBA625A)	90p*
78L12AWC (TBA625B)	90p*
78L15AWC (TBA625C)	90p*

DIGITAL SWITCH

BCD encoded digital switch Reading 0 to 9. Suitable for digital clock alarm setting DVM input Scaling etc.

1 to 9. £1.49 each *



LIGHT EMITTING DIODES

Free snap-on plastic retainer

0.125" dia. lens (TIL209)	10p*	100p*	10p*	100p*
0.16" dia. lens (MLED 650)	10p*	100p*	10p*	100p*
0.2" dia. lens (MLED 650)	10p*	100p*	10p*	100p*

Red 18p 15p 13p 27p 24p 23p 18p 10p 14p
Green 27p 24p 22p 33p 30p 27p 30p 27p 25p
Orange 27p 24p 22p 33p 30p 27p 30p 27p 25p
Yellow 34p 31p 29p 35p 32p 29p 35p 33p 30p

OPTO-ISOLATORS

Our Bulk Buying Power enables a repeat of our Special Offer.

0.33" (LIT 707) 90p*(inc. VAT)
0.63" (LIT 747) £1.99*(inc. VAT)

11L 4N25 or TIL116 6 pin industry standard package 2.5KV isolation £1.00*

MAINS TRANSFORMERS

6-0-6V 100 mA	97p*	0-9-17 V	£1.95	£2.27	£2.64
9-0-9V 100 mA	97p*	0-12-15-20-24-30 V	£2.48	£4.15	-
12-0-12V 100 mA	97p*	0-24-30-40-48-60 V	£5.18	£7.02	-
20-0-20V 1 A	£4.55	0-19-25-33-40-50 V	£2.70	£3.40	£4.53
24-0-24V 500 mA	£2.48				
28-0-28V 1 A	£6.18				

p.p. on transformers 10% of price. min. 20p

SECONDARIES

6-0-6V 100 mA	97p*
9-0-9V 100 mA	97p*
12-0-12V 100 mA	97p*
20-0-20V 1 A	£4.55
24-0-24V 500 mA	£2.48
28-0-28V 1 A	£6.18

VAT INC

Items followed by * inc. VAT at 8% all others include 25%

Overseas Customers deduct 2/7 from * items. 1/5 from others

postage & packing 20p
Orders for over £6. post free. Except transformers

Data Sheets and photocopy service available 10p. per page
Advert No. 1A of Series B

CALLERS WELCOMED

Look AT THESE PRICES AND BUY QUALITY

VALVES Type	Price (p)	Type	Price Each (p)	Type	Price Each (p)
DY87	30.0	BC125B	15	R2008B	£2.00
DY802	30.0	BC132	25	R2010B	£2.00
ECC82	28.0	BC135	15	RCA16334	80
EF80	29.5	BC137	19	RCA16335	80
EF183	34.5	BC138	26	TIP31A	57
EF184	34.5	BC142	23	TIP32A	67
EH90	35.5	BC143	25	TIP41A	67
PC900	24.5	BC147	11	TIP42A	80
PCC89	40.0	BC147A	11	2N3055	55
PCC189	41.0	BC148	10	DIODES	
PCF80	31.5	BC149	10	BA115	7
PCF86	39.0	BC153	15	BA145	14
PCF801	42.0	BC154	15	BA148	19
PCF802	40.0	BC157	14	BA154/201	11
PCL82	39.0	BC158	10	BY126	11
PCL84	39.0	BC159	11	BY127	12
PCL85	44.5	BC173	18	BY199	27
PCL86	41.0	BC178B	20	BY206	21
PFL200	59.5	BC182L	12	BY238	25
PL36	55.5	BC183L	12	QA90	6
PL84	25.0	BC187	25	QA202	7.5
PL504	64.5	BC214L	15	IN60/OA91	5
PL508	67.0	BC328	28	IN914	6
PL519	£1.20	BC337	19	IN4002	5
PY88	35.5	BD124	75	INTEGRATED CIRCUITS	
PY800	33.0	BD131	45		
PY500A	85.0	BD132	39		
		BD160	£1.39	Type	Price
		BD235	49	ETTR6016	£2.00
		BD237	52	MC1351P	70
		BDX32	£2.40	SN76003N	£2.35
		BF115	20	SN76013N	£1.50
		BF160	15	SN76013ND	£1.50
		BF167	20	SN76023N	£1.50
		BF173	20	SN76023ND	£1.45
		BF178	35	SN76033N	£2.35
		BF179	40	SN76227N	£1.45
		BF180	31	SN76532N	£1.45
		BF181	32	SN76660N	58
		BF184	25	SN76666N	87
		BF185	25	TAA550	49
		BF194	9	TAA700	£2.95
		BF195	8	TBA120AS	£1.00
		BF196	10	TBA120SQ	£1.00
		BF197	12	TBA480Q	£1.40
		BF198	23	TBA520Q	£2.35
		BF200	25	TBA530Q	£1.75
		BF218	30	TBA540Q	£1.75
		BF224	23	TBA550Q	£2.90
		BF258	34	TBA560CQ	£2.40
		BF336	28	TBA800	£1.50
		BF337	35	TBA9200	£2.90
		BF355	54	TBA99CQ	£2.90
		BFX86	28	TCA270Q	£2.90
		BFY50	19	EHT MULTIPLIERS MONOCHROME (BRC) Price Each	
		BFY52	20	2HD 950MK1	960
		BSY52	35		£1.70
		BT106	£1.20	2TQ 950MK2	1400
		BU105/02	£1.95		£1.85
		BU108	£2.10	2DAK 1500	
		BU208	£2.95	(17" & 19")	£1.85
		E1222	30	2TAK 1500	
		MJE340	45	(23" & 24")	£2.00
		OC71	15		
		OC72	16		

EHT MULTIPLIERS COLOUR	Price Each
11TAQ ITT CVC 1, 2 & 3	£4.50
11TAN GEC Sobell	£4.50
11TAZ GEC 2110	£4.85
11TAM Philips G8	£4.50
11TBD Philips 550	£4.50
3TCW Pye 691/693	£3.50
11TH Decca 30 Series	£4.50
11TAQ Decca Bradford	£4.50
3TCU Thorn 3000/3500	£5.00
11HAA Thorn 8000	£1.90
11HAB Thorn 8500	£4.25

New TOSHIBA TUBES

with 12 months in service guarantee	Price
19" A49-191X equivalents	£48.95
A49-192 and A49-120X	
20" 510DJB22 equivalent	£50.75
A51-110X	£54.25
22" A56/120X	

PRICES SUBJECT TO 25% V.A.T.

All goods subject to settlement discount of 5% 7 days and 2% monthly

No postage charges or minimum order values

Write or phone for full details now.



PRICE QUALITY SERVICE



COMBINED PRECISION COMPONENTS (PRESTON)LTD

Department W.
194-200 North Rd.
Preston PR1 1YP
Tel: 55034
Telex: 677122.

ATTENTION— ALL COMMERCIAL RADIO USERS!

MOBILE AERIALS

Big Economy News!
Catronics now stock

a wide range of whip type aerials and a variety of bases including types that **do not require a fixing hole on the car.** We can, therefore, supply virtually ANY frequency aerial for mounting on ANY car!

These aerials are particularly suitable for MINICabs, Breakdown Trucks, and other radio-controlled service vehicles.

The range of frequencies extends from 50MHz to 476 MHz ALL AT THE MOST COMPETITIVE PRICES

Write for illustrated leaflet

VHF DIGITAL FREQUENCY METER



New 200MHz, 7 digit, D.F.M. for direct readings up to the mobile radio VHF 'High Band'. Will operate on mains or 12V supply, **making it ideal for use with mobile equipment. Price Only £121 + £1 carriage + VAT (currently 8%)**


CATRONICS LTD. (Dept. 521)

39 Pound Street,
Carshalton, Surrey
Tel: 01-669 6700



WW — 074 FOR FURTHER DETAILS

ELECTROVALUE

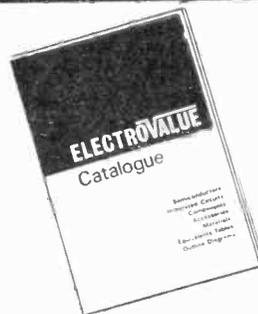

READY NOW CATALOGUE 8

- 144 pages
- New lines
- UP-DATED PRODUCT & PRICE INFORMATION
- 40P REFUND VOUCHER

We have made it just about as comprehensive and up-to-the-minute as possible. Thousands of items from vast ranges of semi-conductors including I.C.s to components, tools, accessories, technical information and diagrams are included as well as a refund voucher worth 40p for spending on orders list value £5 or more. **SEND NOW FOR YOUR COPY BY RETURN.** It's an investment in practical money-saving and reliability!

40p post paid

+E.V. PRICE STABILIZATION POLICY FOR EA

This is one of reviewing prices every 3 months rather than trying to keep up with day by day changes as they occur. We have in fact held prices better than we anticipated in 1975. Next review period starts January 1st, 1976.

+E.V. DISCOUNT PLAN

Applies to all items except the few where prices are shown NETT. 5% on orders from £5 to £14.99; 10% on orders value £15 or more.

+FREE POST & PACKING

In UK for pre-paid mail orders over £2 (except Baxandall cabinets). If under there is an additional handling charge of 10p.

+QUALITY GUARANTEE

All goods are sold on the understanding that they conform to makers' specifications. No rejects, seconds or sub-standard merchandise.

ELECTROVALUE LTD

All communications to Dept. 4/1

28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Telephone Egham 3603. Telex 264475. Shop hours: 9-5.30 daily, 9-1 p.m. Sats.

NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester M19 1NA
Telephone 061 432 4945. Shop hours: Daily 9-5.30 p.m., 9-1 p.m. Sats.

U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081

EMI
FUJI
MAXELL

BASF
TDK

UP TO **50% OFF**

MEMOREX
SCOTCH

PHILIPS
pyral

Stereo Tape Recorders

Stereo Cassette Recorders Stereo Car Cassette Players

SPECIAL AUDIO & VIDEO TAPES SUPPLIED. PRICES ON REQUEST

PLASTIC SNAP PACK	BASF LH		BASF Super S/M		BASF CR02		Memorex MRX		Memorex CR02		REEL TO REEL		BASF Low Noise in Plastic Box		BASF LH Super in Plastic Box		Scotch Hi-Fi Boxed		Agfa Low Noise in Plastic Box		Agfa PFM in Plastic Box			
	One	10	One	10	One	10	One	10	One	10	One	10	One	10	One	10	One	10	One	10	One	10		
C60 C90 C120	42p 62p 82p	£4.15 £6.07 £8.14	60p 76p £1.09	£5.90 £7.20 £10.80	90p £1.12 £1.54	£8.89 £10.50 £15.40	57p 76p £1.88	£5.63 £7.53 £10.70	77p 96p —	£7.68 £9.75 —	LONG PLAY		£1.75 £2.20 £2.75	£17.00 £20.00 £26.50	£1.97 £2.25 £3.10	£19.00 £20.50 £29.00	— — £3.20	— — £3.10	£1.27 £1.60 £1.19	£12.65 £15.90 £11.85	£1.95 £2.90 £7.30	£19.10 — £72.50		
C60 C90 C120	54p 75p 99p	£5.30 £7.35 £9.70	75p 95p £1.38	£7.35 £9.20 £13.50	95p £1.60 —	£9.30 £15.70 —	£1.20 £1.60 —	£11.80 £15.70 —	33p 53p 73p	£3.25 £5.14 £7.20	DOUBLE PLAY		£2.20 £2.85 £3.50	£20.00 £28.00 £34.00	£2.35 £3.50 £4.35	£22.50 £33.00 £41.00	£1.95 £2.50 £2.75	£18.50 £23.50 £26.50	£1.49 £2.19 £2.89	£14.50 £21.10 £28.85	— — £3.95	— — £35.60		
C60 C90 C120	55p 68p 93p	£5.45 £6.75 £9.25	66p 85p £1.24	£6.55 £8.45 £12.35	30p 44p —	£2.75 £4.35 —	40p 54p 66p	£3.90 £5.35 £6.55	48p 67p —	£4.75 £6.65 —	TRIPLE PLAY		£2.95 £3.50 £4.30	£28.00 £34.00 £42.00	— — —	£2.50 £3.50 £3.50	£24.50 £29.50 £32.50	£2.46 £2.96 £3.76	£23.00 £28.00 £35.50	— — —	— — —			
C60 C90 C120	41p 57p 78p	£4.05 £5.65 £7.75	— — —	— £8.45 —	90p — —	£9.75 — —	£1.24 £1.68 —	£12.00 £16.75 —	55p 69p 94p	£5.45 £6.30 £8.50	REEL TO REEL		£1.30 £2.10 £4.70	£12.90 £20.95 £46.10	£1.40 £1.75 —	£13.50 £17.00 —	— — —	£3.20 £3.50 £3.50	£29.50 £30.50 £78.00	SPECIAL OFFER FREE Cassette Head Cleaner with every C.A. cassette order over £15.				
C60 C90 C120	78p 57p £1.32	£7.20 £9.35 £11.20	43p 59p 80p	£4.20 £5.60 £7.95	40/63p 91p —	£6.28 £9.05 —	35p 49p 64p	£3.45 £4.85 £8.38	47p 52p 71p	£4.60 £5.00 £7.00	DOUBLE PLAY		£1.55 — £2.59	£14.90 — £25.00	£1.50 £1.90 £2.50	£14.95 £13.50 £24.95	MUSIC Cassettes and Cartridges Send large (9" x 4") S.A.E. to R/C Dept. for catalogue.							
40/45 mins. 60/64 mins. 90/100 mins.	£1.12 £1.25 £1.42	£10.70 £11.60 £13.50	£1.10 £1.25 £1.42	£10.70 £11.60 £13.50	40/£1.25 £1.25 50/£1.65	£11.60 £11.60 £15.10	89p 93p —	£8.60 £9.20 —	£1.12 £9.20 £1.35	£10.60 — £12.70	8-TRACK CARTRIDGES		One	10	One	10	One	10	One	10	One	10	One	10
<p>Prices shown include VAT at 8%, but are subject to change without notice. Mail Order Only - Cash with orders. For postage and packing, add 10p every 10 cassettes, 10p every reel-to-reel tape. Minimum 20p. Maximum 70p. Offers apply to U.K. Mainland only.</p> <p>CITY AUDIO, STRAND HOUSE GREAT WEST ROAD, BRENTFORD MIDDLESEX (Tel. 01-560 4191)</p>												<p>If you wish to use Barclaycard or Access, simply quote name, address and card number when ordering</p> <p>Buy it with Access</p>												

CROFTON don't just sell kits, we offer you a technical back up service to ensure your success

The following is a selection of some of the more popular kits -

- ★ Mullard CCTV Camera
- ★ PE CCTV Camera
- ★ PE Rondo Quadraphonic Four Channel Sound (Designer Approved)
- ★ Electronic Ignition
- ★ Sound Operated Flash
- ★ P.W. Tele Tennis Game
- ★ UHF Modulator
- ★ Bench Power Supply
- ★ Wobulator
- ★ A.I.E.T. Top Projects
- ★ Many of the Elektor Projects

NOTE: PCBs for most published projects available to order

CROFTON ELECTRONICS LTD
Dept. D, 124, Colne Road, Twickenham, Middx. 01-898 1569

FREE Brochure on New KITS

Whether professional, student, teacher or amateur, the field of electronics can open up a new world for you.

WW-053 FOR FURTHER DETAILS

STEREO IC DECODER

HIGH PERFORMANCE PHASE LOCKED LOOP
(as in 'W.W.' July '72)

MOTOROLA MC1310P EX STOCK

DELIVERY SPECIFICATION

Separation: 40dB 50Hz-15kHz	Distortion: 0.3%
I/P level: 560mV rms	O/P level: 485mV rms per channel
Input impedance: 50kΩ	Power requirements: 8-14V at 16mA
Will drive up to 75mA stereo 'on' lamp or LED	

KIT COMPRISES FIBREGLASS PCB (Roller tinned), Resistors, I.C., Capacitors, Preset Potm. & Comprehensive Instruction.

LIGHT EMITTING DIODE
Suitable as stereo 'on' indicator for above

MC1310P only £2.15 plus p.p. 10p

ONLY £3.98 (RED 29p, GREEN 59p)

WHY PAY MORE? post free

NOTE
As the supplier of the first MC1310P decoder kit, of which we have sold literally thousands, our customers can benefit from our wide experience V.A.T.

Please add V.A.T. to all prices

FI-COMP ELECTRONICS
PORTWOOD INDUSTRIAL ESTATE, CHURCH GRESLEY
BURTON-ON-TRENT, STAFFS. DE11 9PT

COMPUTER APPRECIATION OFFER THE LATEST IN AUTOMATIC TYPEWRITERS!


If you need a Paper Tape IBM 'Golfball' for Correspondence, Standard Texts or Computer Input; Computer Appreciation can SAVE YOU MONEY! New ITEL Word Processors from £680; ex-demo from £450. All with guarantees and full maintenance backup.

Computer Appreciation, Castle Street, Bletchingley, Surrey, RH1 4NX.

Telephones: Godstone 3106, Otford 3256.

WW-088 FOR FURTHER DETAILS

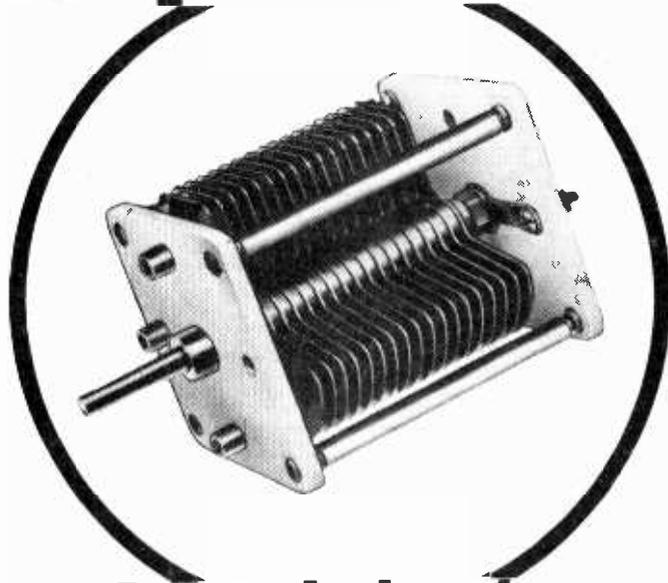Looking for high voltage air dielectric capacitors?



Turn to Jackson's for versatility

The Jackson's range of high voltage air dielectric capacitors has been specially developed for modern transmitting and aerial tuning applications.

It's a versatile range. Some give a capacity of up to 1,000pF. Others accept up to 6Kv. d.c. Proof Voltage.

It's a smooth range. Plain bearings for high torque. Ball bearings for low torque. Single stator, differential and split stator configurations.

All backed by 50 years' experience in the communications field. Highly skilled men. And Jackson Brothers' good name.



Write for further information to:

JACKSON BROTHERS (LONDON) LIMITED


Kingsway, Waddon, Croydon CR9 4DG
 Tel: 01-681 2754/7 Telex: 946849
 U.S. Office: Swedgal Electronics, Inc.,
 258 Broadway, New York, N.Y. 10007

B. S. 9000 Approved

WW-062 FOR FURTHER DETAILS

OLSON

MINICASES

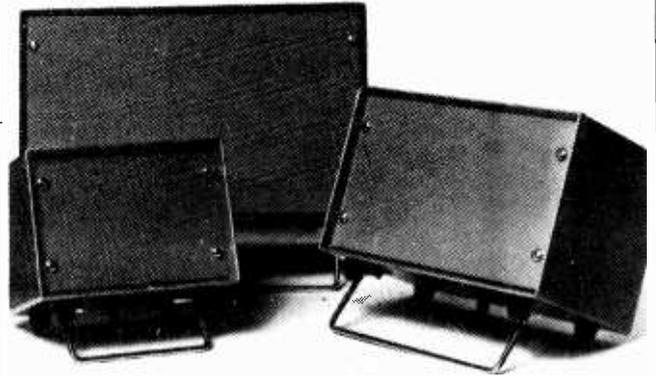

Standard minicases are made from 20g. mild steel sheets zinc-coated and finished in silver grey hammer-tone stove enamel. Front panels made from 18g. steel, finished in light grey high gloss enamel.

Type	Overall Dimension			Case no vents	Case with vents	Chrome leg
	Width	Height	Depth			
21	6½"	4½"	4½"	—	3.92	0.90
22	8½"	5½"	5½"	—	4.40	0.90
23	10½"	6½"	6½"	—	5.25	0.95
24	12½"	7½"	7½"	—	5.74	0.95
25A	6½"	4½"	4½"	3.80	4.28	0.90
25B	6½"	4½"	6½"	4.00	4.48	0.90
26A	8¾"	5¾"	6½"	5.37	5.85	0.95
26B	8¾"	5¾"	8½"	5.62	6.10	0.95
27A	12¼"	7½"	5½"	5.75	6.35	0.95
27B	12¼"	7½"	8"	6.35	6.95	0.95
28A	14"	10½"	6½"	6.95	7.55	—
28B	14"	10½"	8½"	7.55	8.15	—
29A	10"	4"	6"	4.85	5.33	0.95
29B	10"	4"	8"	5.15	5.63	0.95
30A	12"	5"	6"	5.25	5.85	0.95
30B	12"	5"	8"	5.56	6.16	0.95
31A	14"	6"	6"	5.75	6.35	0.95
31B	14"	6"	8"	6.05	6.65	0.95
61	15½"	7½"	9½"	—	8.75	—
62	17½"	8½"	9½"	—	10.15	—
63	16½"	9½"	9½"	—	10.15	—
64	15½"	7½"	12½"	—	10.15	—
65	17½"	8½"	12½"	—	11.60	—
66	16½"	9½"	12½"	—	11.60	—

Types 21, 22, 23 and 24 are finished in olive green hammertone with front panels in light straw gloss enamel. Fitted with ventilated rear panels only. No louvres in the base.

PORTABLE POWER DISTRIBUTION



COMPLETE WITH 8FT CABLE AND 13AMP PLUG

4 SOCKETS 13A.	£8.80
6 SOCKETS 13A.	£10.45
4 SOCKETS 13A/SW	£10.05
6 SOCKETS 13A/SW.	£11.11

Please add for postage and packing and VAT @ 8%.

Trade Counter is open for personal callers from 9 a.m. to 5.00 p.m. Monday-Friday

OLSON ELECTRONICS LTD., 5-7 LONG ST., LONDON, E.2. TEL: 01-739 2343

WW-057 FOR FURTHER DETAILS

Introducing the small speaker with 'big' ideas Celestion UL6

Compact Shape

How small? 11½ x 16 x 8¾ in. to be precise, these measurements are the only 'small' thing about UL6.

Expansive Sound

UL gives expansive, open, natural sound; only Celestion have truly conquered the technical problems which have previously been held to be insurmountable.

An intensive three year development programme has crystalized a life times know-how of speaker design and given birth to UL.

Superior Performance


Inside the beautiful exterior are the new 'acoustic motor units' which make these designs possible. New soft dome 'tweeters' of impeccable design to give smooth sweet treble sounds; bass units built on to diecast chassis, with small ultra-low distortion bextrene diaphragm, extra large voice coil (1½ in.) and magnet for high accuracy and ability to handle wide dynamic range and high peak music levels when required. The third diaphragm is Celestions auxiliary bass radiator 'ABR' which comes into its own on the extreme low notes of instruments

such as organ and double bass.

UL means ultra linear; UL also represents unlimited quality of sound; Celestion experience makes possible a prestige product at an ordinary cost.

The UL6 speaker has precise and beautiful balance both aurally and visually.

Celestion

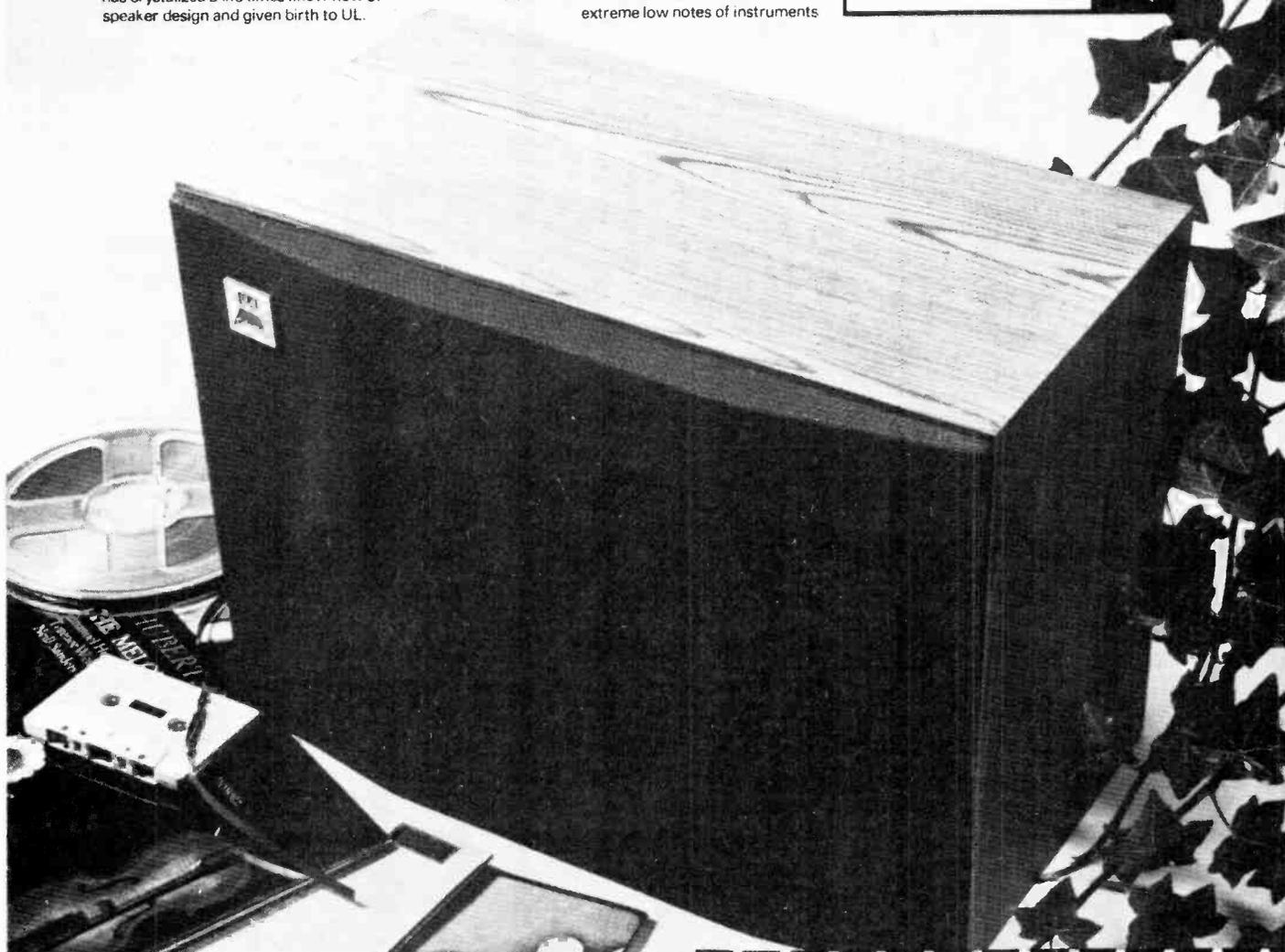


Hear the full range speak for itself:

Please send me full details of UL6 UL8 UL10 and inform me of my nearest franchised demonstration centre.

Name _____

Address _____

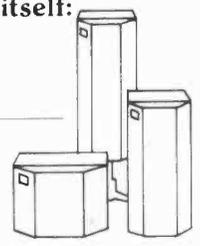

W7

Rola Celestion Limited, Ditton Works, Foxhall Road, Ipswich, Suffolk IP3 8JP
Telephone Ipswich (0473) 73131 Cablax Voicecoil Ipswich Telex 98365

Fully guaranteed Individually packed VALVES

A1065	1.25	ECL82	0.35	G237	1.00	PY33	0.80
ARR	0.55	ECL83	0.70	KT66	2.50	PY80	0.40
ATP4	0.50	ECL86	0.50	KT88	3.85	PY81	0.40
B124	3.00	EF35	0.65	MH4	0.75	PY82	0.40
CY31	0.50	EF37A	1.20	ML6	0.65	PY83	0.40
DAF96	0.55	EF40	0.75	OA2	0.45	PY88	0.45
DF96	0.55	EF41	0.65	OB2	0.45	PY500	1.00
DK96	0.70	EF80	0.30	PABC80	0.40	PY800	0.45
DL92	0.40	EF83	1.25	PC97	0.50	PY801	0.50
DL96	0.60	EF85	0.35	PC900	0.50	QOV03-10	1.40
DY86/87	0.40	EF86	0.35	PCC84	0.40	QOV06-40A	1.40
DR02	0.45	EF89	0.30	PCC85	0.40		
E88CC/01.120	0.50	EF92	0.50	PCC89	0.50		
E180CC	0.70	EF95	0.40	PCC189	0.60	R19	0.75
E182CC	1.25	EF183	0.35	PCF80	0.40	SC1/400	3.00
EA50	0.40	EF184	0.35	PCF82	0.40	SC1/600	3.00
EABC80	0.40	EF200	0.75	PCF86	0.80	SP81	0.75
EAF42	0.75	EL34	0.70	PCF86	0.80	TT21	0.50
EB91	0.30	EL36	0.60	PCF200	0.75	U25	0.85
EBC33	1.00	EL37	1.80	PCF201	0.75	U26	0.75
EBC41	0.75	EL41	0.80	PCF801	0.55	U27	0.65
EBFR0	0.40	EL81	0.60	PCFR02	0.50	U191	0.75
EBFR3	0.50	EL82	0.55	PCFR05	0.90	UB01	0.75
EBFR9	0.40	EL83	0.60	PCFR06	0.75	UABC80	0.40
EC52	0.35	EL85	0.60	PCFR08	0.90	UAF42	0.65
ECC81	0.40	EL86	0.45	PCH200	0.80	UBC41	0.60
ECC82	0.35	EL90	0.45	PCL81	0.55	UBF80	0.40
ECC83	0.35	EL504	0.80	PCL82	0.40	UBF89	0.40
ECC84	0.35	EM31	0.80	PCL83	0.85	UBL1	1.00
ECC85	0.40	EM80	0.55	PCL84	0.45	UBL21	0.70
ECC86	0.90	EM84	0.60	PCL86	0.50	UCC85	0.45
ECC88	0.50	EM87	1.00	PCL805	0.60	UCF80	0.75
ECC189	0.70	EY51	0.45	PEL200	0.70	UCH42	0.75
ECR80	0.40	EY81	0.45	PL36	0.60	UCH81	0.45
EFR82	0.40	EY86	0.40	PL81	0.50	UCL82	0.45
EFR01	0.75	EY88	0.50	PL82	0.45	UCL83	0.65
ECH35	1.40	EZ40	0.70	PL83	0.45	UL41	0.70
ECH42	0.80	EZ41	0.70	PL84	0.45	UF80	0.85
ECH81	0.35	EZ80	0.30	PL504	0.80	UF85	0.45
ECH83	0.45	EZ81	0.30	PL508	1.00	UF89	0.50
ECH84	0.45	EY501	0.75	PL509	1.35	UL41	0.70
ECL80	0.55	EZ34	0.70	PL802	1.75		

A lot of these valves are imported and prices vary for each delivery so we reserve the right to change prices as seen to brand new in cabinets. Prices on application

UL84	0.40	3A4	0.60	6AL5	0.30	6AX5GT	1.00	6C6	0.50	6J7G	0.40
UY41	0.45	3BP1	7.00	6AL5W	0.55	6B7	0.70	6CB6	0.50	6K6GT	0.80
VR105/300.45		3DE	0.40	6AM6	0.80	6BA6	0.35	6CH6	1.45	6K7	0.55
VR150/300.45		354	0.40	6AN8	0.45	6BE6	0.40	6CL6	0.75	6K7G	0.30
X61M	1.40	3V4	0.85					6D6	0.55	6K8GT	0.50
X66	0.85	5B/254M	4.50					6E8R	0.85	6K25	1.00
Z800U	2.70	5B255M	4.50					6F7	1.10	6L6	1.90
Z801U	2.70	5R4YG	1.10					6FRG	0.75	6L6G	0.60
Z900T	1.20	5U4G	0.60					6F23	0.90	6L7G	0.40
1A3	0.55	5V4G	0.55					6F32	0.75	6SA7	0.50
1L4	0.25	5Y3GT	0.60					6F33	3.50	6SA7GT	0.40
1R5	0.25	5Z3	0.80					6H6	0.40	6SC7GT	0.40
1S4	0.30	5Z4GT	0.55					6J4WA	1.25	6S67	0.50
1T4	0.30	6AB7	0.50					6J5	0.65	6S7	0.55
1X2A	0.75	6AC7	0.60					6J5GT	0.50	6SJ7GT	0.35
1X2B	0.75	6AH6	0.70					6J6	0.30	6SK7	0.55
2D21	0.50	6AK5	0.40					6J7	0.60	6SL7GT	0.50
2K25	0.50	6AK8	0.40								

VAT
Please add 25%
to all orders

TRANSISTORS, DIODES etc.

AC113	AF17R	BSY38	OA2200	OC206	2N3054
AC126	AF186	BSY95A	OC22	OC22	2N3055
AC127	AF239	BV216	OC25	OC26	2N3055
AC128	AF212	CRS1.10	OC28	OC28	2N3391
AC176	ASV26	CRS1.20	OC29	OC29	2N3391A
ACY18	ASV27	CRS1.30	OC35	OC35	2N3819
ACY19	ASV28	CRS1.40	OC42	OC42	2N4038
ACY20	BC108	CRS3.10	OC44	OC44	2N4058
ACY39	BC118	CRS3.20	OC45	OC45	2N4061
ACY40	BC119	CRS3.30	OC47	OC47	2N4785
AD149	BC136	CRS3.40	OC78	OC78	2N4785
AD161	BC137	CRS25.C25	OC81	OC81	2N5295
AD162	BC148A	GET115	OC82	OC82	2N5295
ADZ11	BC172	GET116	OC83	OC83	2N5295
ADZ12	BC172A	GET116	OC83	OC83	2N5295
AF114	BC121A	NK1222	OC139	OC139	2N1309
AF115	BCY31	OA5	OC140	OC140	2N1309
AF116	BCY33	OA7	OC170	OC170	2N2411
AF117	BCY72	OA70	OC172	OC172	2N2989
AF118	BF115	OA71	OC200	OC200	2N3053
AF124	BF167	OA73			
AF125	BF185	OA79			
AF126	BFV51	OA91			
AF127	BFV52	OA200			
AF139	BSY27	OA202			

MINIMUM POSTAL ORDER £1. PERSONAL CALLERS WELCOME.
MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves
U.K. Postage £1-£2 20p, £2-£3 30p, £3-£5 40p, over £5 free

COLOMOR

ALL valves guaranteed

6SN7GT	0.50	30C17	1.00	6064	0.60
6S07	0.55	30C18	0.90	6065	1.00
6V6GT	0.55	30F5	1.00	6067	0.70
6X4	0.40	39F11	1.00	6080	2.30
6X5G	0.40	30R12	1.10	6146	3.35
6X5GT	0.50	30R14	0.90	6146B	3.85
6Y6G	0.90	30L15	0.95	8020	5.00
6Z4	0.65	30L17	0.95	9001	5.00
6-30L2	0.90	30P12	1.00	9002	0.50
7B7	0.80	30P19	1.00	9003	0.70
7Y4	0.80	30P11	0.95	9004	0.35
906	0.40	30P13	1.10	9006	0.35
11E2	0.60	30P14	1.10		
12A6	0.55	35L6GT	0.75		
12A7	0.45	35V4	0.50		
12A7T	0.40	35Z4GT	0.70		
12AU7	0.35	50C5	0.60		
12AV6	0.50	50CDB6G	1.10		
12AX7	0.35	75	1.00		
12BA6	0.45	75C1	0.75		
12BE6	0.50	76	0.75		
12BH7	0.50	78	0.70		
12CR	0.55	80	0.75		
12E1	0.50	85A2	0.75		
12K5	1.10	723A/b	0.90		
12K7GT	0.50	803	0.60		
12KRGT	0.70	805	1.40		
12O7GT	0.70	807	0.65		
12SA7GT	0.70	813	0.50		
12SG7	0.55	865A	1.20		
12SJ7	0.55	85A2	0.75		
12Y4	0.40	954	0.50		
1457	1.00	955	0.50		
19A05	0.65	956	0.50		
19C3	0.80	957	0.50		
19G6	6.60	1305	0.20		
19H5	14.00	1629	0.70		
20P3	0.60	2051	1.00		
20P4	1.10	5933	3.00		
2516GT	0.70	6057	0.75		
30C15	1.00	6060	0.70		


C. R. TUBES

DG7-5	12.00
DW13-2	18.00
MW13-3535	8.00
VCR139A	8.00
3BP1	4.50
8R1	8.00
8R1	9.00


SPECIAL VALVES

CV239	45.00
M503-2J42	6.00
	42.00
K301	7.00
KRN2A	2.00
OY4-250	19.00
TY4-500	30.00
725A	23.00
2J192	140.00

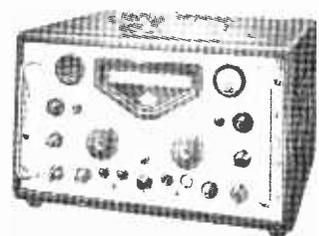VALVES AND TRANSISTORS
Telephone enquiries for valves, transistors etc retail 749 3934 trade and export 743 0899



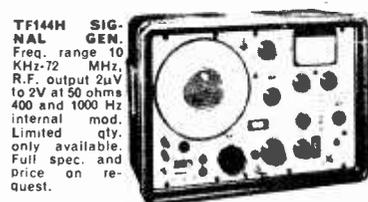RACAL RECEIVERS
Models RA17, RA17 Mk II, RA 17L, RA17W, RA117E, in condition from working as seen to brand new in cabinets. Prices on application



TF144H SIGNAL GEN.
Freq. range 10 KHz-72 MHz, R.F. output 2uV to 2V at 50 ohms 400 and 1000 Hz internal mod. Limited qty. Only available. Full spec. and price on request.




TF526B OSCILLATOR AND DETECTOR UNIT £50.00

BEST PRICES PAID FOR TEST AND COMMUNICATION EQUIPMENT. Single items or quantities. Private or Industrial.

RACAL UNIVERSAL COUNTER/TIMER SA550 (CT488)

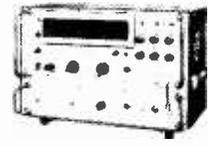8 digit in-line read-out. Frequency range 10 Hz to 100 MHz. Direct frequency measurement up to 100MHz; pulse, period, ratio, time interval and totalising measurements. Input sensitivity variable from 300mV to 9V, three independent inputs, self-check. Full spec. on request, £145.



KAHN SB ADAPTOR MODEL RSSB 62 1B Designed for receivers with 455 500kHz IF (eg Collins 51J, AR88D etc) at 100mV (max) input Features Electronic A F C carrier frequency diversity to combat fading 20 sec R C memory to maintain tuning during severe fading individual carrier meters navigators low distortion production demodulator Full spec & P O A

TF 1229B, TF1225A, TF 577A. WHITE NOISE TEST SET £185.00. Full spec. on request.

TF 1400S DOUBLE PULSE GENERATOR WITH TM 6000/S SECONDARY PULSE UNIT. For testing radar, nucleonics, scopes, counters, filters etc. **SPEC. TF 1400S.** Rep. freq. 10Hz to 100kHz, pulse width 0.1 to 100u sec, delay -1.5 to +3000u sec, rise time 30n sec. **SPEC. TM 6000/S.** As for TF1400S except pulse width 0.5 to 25u sec., delay 0 to +300u sec. £175.

TF 801D/1/S SIGNAL GENERATOR. Range 10-485 MHz in five ranges. R.F. output 0.1 uV-V source e.m.f. Dial calibrated in volts, decibels and power relative to thermal noise. Piston type attenuator. 50u output impedance. Internal modulation at 1 kHz at up to 90% depth, also external sine and pulse modulation. Built-in 5MHz crystal calibrator. Separate R.F. and mod. meters. P.D.A.

TF801B/2. Spec as for TF801D but minor circuit differences. Working order £95.

TF 1370 R.C. OSCILLATOR sine/square wave 10Hz to 10MHz £140.

TF995 A/1 or A/2 or A/2M SIGNAL GENERATORS. AM/FM freq 1.5-220MHz. Prices on application

TF 934 DEVIATION METER 250MHz/FM £55.

TM 8517 VIDEO AMPLIFIER £60.

500/250W MEDIUM WAVE BROADCAST TRANSMITTERS. Price and details on application.

PLEASE NOTE
Unless offered as "as seen"
ALL EQUIPMENT
ordered from us is completely overhauled mechanically and electrically in our own laboratories

FOR EXPORT ONLY TRANSMITTERS:

BC 610 Hallicrafters.
RCA ET 4336 also modified version of increased output to 700w.
COLLINS TYPE 231D 4/5kw., 10 channel, autotune and manual tune, full coverage complete installation and spare parts.
TRANSCEIVERS
19, 19HP, 38, 62.
C-13 TRANSMITTERS
RACAL COMMUNICATIONS EQUIPMENT
We are able to offer a comprehensive selection from the range of this modern high class equipment including receivers, L.F. Converters, SSB adaptors, panoramic adaptors, diversity switches, transmitter driver units, linear amplifiers can be built to customers' requirements. Please send us your enquiries.

ARRS SPARES. We hold the largest stock in U.K. Write for list.

R.F. METER 0-8 amp. 2 1/2" (U.S.A.) £1-80 P. & P. 15p.

TELEPHONE TYPE "J" (Tropicalised) 10 line MAGNETO TELEPHONE SWITCHBOARD

50 line AUTOMATIC PRIVATE TELEPHONE SWITCHBOARD
Price of each of the above on application.

TEST EQUIPMENT
for direct line for all enquiries regarding test equipment only, phone 01-748 6486

S-2020TA STEREO TUNER/AMPLIFIER KIT

NEW PRODUCT

A high-quality push-button FM Varicap Stereo Tuner combined with a 20W r.m.s. per channel Stereo Amplifier.

Brief Spec. Amplifier: Low field Toroidal transformer, Mag. input, Tape In/Out facility (for noise reduction unit, etc), THD less than 0.1% at 20W into 8 ohms. All sockets, fuses, etc. are PC mounted for ease of assembly. Tuner section: uses Mullard LP1186 module requiring no RF alignment, ceramic IF, INTERSTATION MUTE, and phase-locked IC stereo decoder. LED tuning and stereo indicators. Tuning range 88–104MHz. 30dB mono S/N @ 1.8µV. THD typ. 0.4%.

PRICE: £47.95 + 99p p&p + VAT.



SOLID MAHOGANY CABINET



NELSON-JONES STEREO FM TUNER

A very high performance tuner with dual gate MOSFET RF and Mixer front end, triple gang varicap tuning, and dual ceramic filter/dual IC IF amp.

Brief Spec. Tuning range 88–104MHz. 20dB mono quieting @ 0.75µV. Image rejection—70dB. IF rejection—85dB. THD typically 0.4%.

IC stabilized PSU and LED tuning indicators. Push-button tuning and AFC unit. Choice of either mono or stereo with a choice of stereo decoders.

PRICE: Mono £25.46 + 85p p&p + VAT;

With Portus-Haywood Decoder £31.96 + 85p p&p + VAT;

With ICPL Decoder £29.73 + 85p p&p + VAT.



NEW PRODUCT

S-2020A AMPLIFIER KIT

Developed in our laboratories from the highly successful "TEXAN" design. PC mounting potentiometers, switches, sockets and fuses are used for ease of assembly and to minimize wiring.

Typ. Spec. 20+20W r.m.s. into 8-ohm load at less than 0.1% THD. Mag. PU input S/N 60dB. Radio input S/N 72dB. Head-phone output. Tape In/Out facility (for noise reduction unit, etc). Toroidal mains transformer.

PRICE: £29.95 + 99p p&p + VAT.

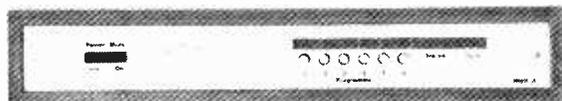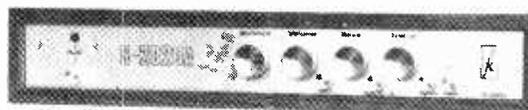

STEREO MODULE TUNER

A low-cost Stereo Tuner based on the Mullard LP1186 RF module requiring no alignment. The IF comprises a ceramic filter and high-performance IC. Variable INTERSTATION MUTE. PLL stereo decoder IC.

Typ. Spec. Sens. 30dB S/N mono @ 1.8µV. Tuning range 88–104MHz. LED sig. strength indicator. LED Stereo indicator. THD typically 0.4%.

PRICE: Stereo £27.80 + 85p p&p + VAT. Mono £24.70 + 85p p&p + VAT

ALL THE ABOVE KITS ARE SUPPLIED COMPLETE WITH ALL METALWORK, SOCKETS, FUSES, NUTS AND BOLTS, KNOBS, FRONT PANELS, SOLID MAHOGANY CABINETS AND COMPREHENSIVE INSTRUCTIONS.

SUB ASSEMBLIES

BASIC NELSON-JONES TUNER

Supplied as a printed circuit board with all components and screening box to build a varicap tuner module. Performance spec as above for complete N-J Tuner. For suitable stereo decoders see below. (Illustrated without screening box.)

PRICE: £12.88 + 25p p&p + VAT.



BASIC MODULE TUNER

Supplied as a printed circuit board with all components and screened Mullard LP1186, to build a mono or stereo tuner module. Performance spec as above for Stereo Module Tuner complete kit.

PRICE: Mono £13.00 + 25p p&p + VAT: Stereo £15.00 + 25p p&p + VAT



PORTUS-HAYWOOD PHASE-LOCKED STEREO DECODER

Mk II version of this design (WW Sept. 1970). The lowest distortion phase-locked stereo decoder kit available (Typ. 0.05% @ N-J Tuner O/P level). Separation 40dB up to 15KHz. Complete kit comprises PCB and all components, inc. stereo LED.

PRICE: £7.68 + 25p p&p + VAT.



PHASE-LOCKED IC DECODER KIT

Integrated circuit phase-locked stereo decoder based on the MC1310. THD typically 0.3%. Separation 40dB @ 1KHz.

PRICE: £4.27 + 20p p&p + VAT.



PUSH-BUTTON UNIT

The six-position push-button unit used in our tuners and tuner/amp. Each track has the required diode law for stability of tuning. There are approx. 40 turns on each button and there are six separate moving pointers. An AFC disable switch is incorporated with each button. The unit is finished in black with red pointers.

PRICE: £3.30 + 20p p&p + VAT



Please send SAE for complete lists and specifications.

INTEGREX LIMITED,

Portwood Industrial Estate, Church Gresley, Burton-on-Trent, Staffs, DE11 9PT.
Tel. Swadlincote (0283 87) 5432. Telex 377106.



TRAMPUS

ELECTRONICS LTD. WINDSOR

58-60 GROVE RD.
WINDSOR, BERKS, SL4 1HS.
ADD 8% VAT TO PRICES MARKED *
ADD 25% VAT TO ALL OTHER PRICES
SEND C.W.O. (EXCEPT GOVT DEPTS)
POST & PACKING 20P FOR THE UK

NEW FAST SERVICE. LOW PRICES.
MONEY BACK IF NOT SATISFIED.
ALL BRAND NEW TOP GRADE FULL
SPEC DEVICES. CALLERS WELCOME
NEW CATALOGUE LIST FREE SAE.
BARCLAYCARD & ACCESS BY POST.
SORRY NO SALES TELEPHONE.

FAST SERVICE



DL707 COM. ANODE &
DI704 COM. CATH.
0.3 0-9dp 85p*ea.
747 JUMBO 0.6" CA
LED DISPLAY £1.89*
3015F 0-9dp £1.20*
DL33 MINI 3 DIGIT
& MAGNIFIER £1.25*
STROBE TUBE 50p*

LEDS red 12p.

209 STYLE OR 0.2" 5V CLIP 12p*
TIL209 or 0.2" RFD & CLIP 14p*
GREEN LARGE/SMALL & CLIP 19p*
ORANGE LARGE/SMALL & CLIP 19p*
ORP12 57p* 2N5777 33p* TEC12 50p*
DIGITAL CLOCKS MM5316 £5*
MM5314 £3.39* MM5311 £5*
AY51224 £3.49* PCB £1*
CAPACITORS
CERAMIC 22pf-0.1uf 50v 5p.
ELECTROLYTIC: 10/50/100 of 1n
25V 7P. 50V 2p. 2uf/10V 6p.
1000uf 25V 18p. 200/300uf 9p.
POTENTIOMETERS 1kV/LOG 11p.
PRESETS 6p. RESISTORS 14p ea

HATSINKS: TL1 1.015 10p TV4 13p*
TV3/103 11p. LXTUBED 4" 1Y1 29p*
SWITCHES: SPST 15p. DPDT 25p.
915 PLUGS ALL 12p. SOCKETS ALL 9p
ALL CASES: MS5/M2 10p. M13 65p*
TRANSFORMERS 1/1A 6 or 12V £1.50*

TRAMPUS FULL SPEC PAKS ALL £1 ea
PAK A 10 20 30 40S our choice £1*
PAK B 10 20 30 40S 1IN £1*
PAK C 10 20 30 40S 1.5IN £1.10*
PAK D 10 20 30 40S 1.5IN £1.10*
PAK E 10 20 30 40S 1.5IN £1.10*
PAK F 10 20 30 40S 1.5IN £1.10*
PAK G 10 20 30 40S 1.5IN £1.10*
PAK H 10 20 30 40S 1.5IN £1.10*

IC's LOW PRICES

703 RF/IF	26p	MC1303	£1.50
709 T099	22p*	MC1310	£2.20
709 DIL 11	28p*	MC1312 SQ	£2.50
716 DIL 14	31p*	MC1318	£2.50
723 Regul'r	35p*	W1330	70p
741 DIL 8	31p*	W1339	£1.10
711 DIL 14	31p*	MC1350/17	75p
11 T099	11p*	W1466/70	£3
747 2x741	47p*	MC14000 1V	49p
44 DIL 8	27p*	NE536 FITOPA	£2
7805 5V	£1.38*	NE340	£1.10
7812 12V	£1.20*	NE550 5V	71p
7816 15V	£1.35*	NE555 TIMER	42p*
7900 Series	52p*	NE556 5V	88p*
76013 6W AF	75p*	NE560 PLL	£4.00
CA3048	94p	NE561 PLL	£4.00
CA3049	£2	NE562 PLL	£4.00
CA3074	£1.50	NE505	£2.25
LM3878 SGEN	£3*	NE506	£2.50
LM300	£1.50*	NE566	£1.55
LM301 OPA	41p*	NE567	£2.21
LM304 0-10V	£3*	SN72741 741	21p*
LM308 HI Bo	95p*	SN76660 IF	70p
LM309K 5V	£1.25*	SN76611 IF	£1
LM372 IF	£2.00	TA1000 I&P	£3
LM377 2x2W	£3	TA8900	80p
LM380 2x245	89p	TB8110 7VAF	99p*
LM381	£1.50	TB820	75p
LM3900 40PA	65p*	ZN414 RX	80p

740 TTL

7400	11p*	7471	29p*
7401	11p*	7476	30p*
7402	11p*	7490	31p*
7403	11p*	7491	73p*
7404	11p*	7492	13p*
7405	11p*	7493	20p*
7406	11p*	7494	70p*
7407	11p*	7495	71p*
7408	11p*	7410	£1
7409	11p*	7411	27p*
7410	11p*	7412	27p*
7411	11p*	7413	60p*
7412	11p*	7414	60p*
7413	11p*	7415	75p*
7414	11p*	7416	75p*
7415	11p*	7417	75p*
7416	11p*	7418	75p*
7417	11p*	7419	75p*
7418	11p*	7420	75p*
7419	11p*	7421	75p*
7420	11p*	7422	75p*

TRANSISTORS ALL FULL SPEC

PRICE EACH	MATCHING	20p*	
AC127 & 128	11p*	75 40 20 20 6p*	
AC170	9p*	TIP29 & 30	43p*
AC187 & 188	11p*	TIP31 & 32	54p*
AD110	45p*	TIP41	60p*
AD101 & 102	33p*	TIP12	77p*
BC107	8p*	11N935	80p*
BC107B	12p*	TIP2055	87p*
BC108	8p*	15A1 JCT	15p*
BC108B	12p*	7TV1 07/8/9	11p*
BC109	8p*	ZTX204	£3.30
BC109C	12p*	ZTX205	£3.30
BC117/8/9	11p*	ZTX206	£3.30
BC117/7/9	11p*	ZTX207	£3.30
BC117/8/9	11p*	ZTX208	£3.30
BC117/8/9	11p*	ZTX209	£3.30
BC117/8/9	11p*	ZTX210	£3.30
BC217/3/4/4/1/1	11p*	ZTX211	£3.30
CVT 1/1	11p*	ZTX212	£3.30
BD131 & 132	30p*	ZTX213	£3.30
BF188	250V 35p*	ZTX214	£3.30
BFY50	11p*	ZTX215	£3.30
BFY51	11p*	ZTX216	£3.30
BFY52 & 53	11p*	ZTX217	£3.30
BSY19/20/21	11p*	ZTX218	£3.30
BJ2955 T03	73p*	ZTX219	£3.30
NJ1955	94p*	ZTX220	£3.30
NJ3055	87p*	ZTX221	£3.30
PU131 PCT	40p*	ZTX222	£3.30

DIODES

0A81 & 0A91 GERMANIUM 5p.
1N4001 1A50V & 1N100 5p*
1N1001 6p* 1N4007 9p*
1N114 & 1N914 SILICON 4p.
ZENER 8ZV88 400mW 3p.
ZENER 11V 17V 21V 0.5W 6p.
BRIDGE RECTIFIER 1A50 18p.
1A100V 25p. 4A100V 45p.

SCR'S TRIACS

SCR'S TAG1/400 1A400V 50p*
1A50V 38p* 1A 600V 70p*
C1060 4A400V SCR ONLY 17p*
TRIAC SC1480 10A400V £1*
TRIAC DISCO 16A400V £1.75*
DIACS-ST2 20p. BR100 25p

vero

36PINS 28p*FACE CUTTER49p*
COPPERCLAD 0.1 PITCH VERO
2 1/2" x 5" 30p* 2 1/2" x 3 1/2" 29p*
3 1/2" x 5" 37p* 3 1/2" x 3 1/2" 32p*
3 1/2" x 17" £1.70*
3 1/2" x 17" PLAIN 0.1" £1.06*
DIL BREADBOARD 6x4" £2*

DALO 69P

DALO ETCH RESIST PEN 69p*
ETC ETCH PAK 500gm 89p*
6x1" COPPER BOARD 50p*
PCB KIT 3 ITEMS 50p*
CASSETTE MECHANISM 19 & AS12
TGS GAS DETECTORS 308-tcf £2

Oil sockets

POP QUALITY NYLON
SOCKETS SPI 100p*
14PIN 1.5" 16PIN 14p*
SOLDERING PINS:
100 0.75x10.00 1.50*

WW-060 FOR FURTHER DETAILS

AIRMEC FREQUENCY METER TYPE 265: 0-6000 rpm and 0-100Kc/s £35. Carr. £2.
RACAL L.F. CONVERTER UNIT RA-37B: £35. Carr. £1.
RACAL I.S.B. ADAPTER RA-95A: £65. Carr. £2.
MUIRHEAD ATTENUATORS: 75 ohms 0-8 Mc/s 3V MAK 3 ranges 0-5, 0-25, 0-50 DB £3.00 + 75p post.
CREED MODEL 54 TELEPRINTER: £37.50 each. Carr. £4.
CREED MODEL 75 TELEPRINTER: Receiver only £30.00. Carr. £3.
CREED MODEL 75 TELEPRINTER: Receiver, Transmitter and perforator — £50. Carr. £4.
MULLARD VALVE VOLTMETER: E/7555/3 A.C./D.C. 2 ranges 0-5 and 0-500v. £35. Carr. £2.
EDDYSTONE TELEPRINTER ADAPTOR TYPE 937: £45. Carr. £1.
COLLINS RECEIVER TYPE 51J4: 500Kc/s to 30Mc/s. £250.00. Carr. £4.
WAVEMETER CLASS 'D' NO. 2: 1.2 to 20Mc/s 12 volts d.c. input or 240v a.c. £12.50. Carr. £3.
WILD BARFIELD ELECTRIC FURNACE MODEL CCI.22X: With either indicating temperature controllers Model 990°-1400° C. £250. Carr. £5.
A.E.I. MASS SPECTROMETER TYPE MS.10: £300. Carr. £6.
METROVAC IONIZATION GAUGE MODEL V.C.3: £55. Carr. £3.
MUIRHEAD PAMETRADA WAVE ANALYSER D-489-EM: Primarily used for the analysis of complex vibration waveforms but will measure audio and power frequency waveforms from 19Hz-21KHz. Complete with power supply unit 230V 50Hz. Secondhand. very good condition, £110. Carr. £3.
REDIFON TELEPRINTER RELAY UNIT No. 12: ZA-41196 and power supply 200-250V a.c. Polarised relay type 3SEITR. 80-0V 25mA. Two stabilised valves CV 286. Centre Zero Meter 10-0-10. Size 8in. x 8in. x 8in. New condition. £107. Carr. 75p.
SOLARTRON PULSE GENERATOR TYPE GI101-2: £75.00 each. Carr. £2.00.
TELEPRINTER TYPE 7B: Pageprinter 24V d.c. power supply. speed 50 bauds per min. second hand cond. (excellent order) no parts broken. £20 each. Carriage £3.
INSULATION TEST SET: 0-10 kV negative, earth with amplifier provision for checking ionisation. 110/230v a.c. input. S/hand. good cond. £35 + £1 carr.
BRIDGE MEGGER: 250V. (Evershed Vignoles) series 2. £30 each. Carr. £1.
BRIDGE MEGGER: 2500V. series 1. £30 each. Carr. £1.
CRYSTAL TEST SET TYPE 193: used for checking crystals in freq. range 3000-10,000KHz. Mains 230V 50Hz. Measures crystal current under oscillatory conditions and the equivalent resistance. Crystal freq. can be tested in conjunction with a freq. meter. £25. Carr. £1.50.
SOLARTRON VARIABLE POWER UNIT S.R.S. 1535: 0-500 volts at 100 mA and 6.3 volts C.T. 3 amps d.c. 110/250 volts a.c. input. £18.50. Carr. £1.50.
ALL CARRIAGE QUOTES GIVEN ARE FOR 50-MILE RADIUS OF LONDON ONLY.

NOISE FIGURE METER TYPE 113A (Magnetic AB, Sweden): Complete with Noise Source 121 and 122. £125. Carr. £1.
PRECISION PHASE DETECTOR TYPE 205: Freq. 0.1-15MHz in 5 ranges. Variable time delay microseconds 0-0.1c. 115V input. £55 each. Carr. £1.
RHODE & SCHWARZ HF MILLIVOLTMETER: 30Hz-30MHz Type UVH, 1mV-1V in 7 ranges. 220V. £75 each. Carr. £2.
PHILIPS VALVE VOLTMETER TYPE GM6014: 1-300mV in 6 ranges, 70-20dB, probe 1000Hz-30MHz, 300mV maximum. £35 each. Carr. £1.
CT.343 VALVE VOLTMETER: in ruggedised steel case. Range 1.2mV to 400V. 6 ranges indicated on 3" meter. 230v a.c. input. £25. Carr. £2.
UHF MICROWAVE MILLIWATTMETER TYPE 14: Direct reading, can be used to measure power from 100MHz upwards. F.S.D. on 4in. scale meter 2.5mW. £40 each. Carr. £1.
S-BAND RADAR TEST SET MW695 (Decca) Oscilloscope and Spectrum Analyser. Further details on request. £200.
Q METER: 30MHz-200MHz. £55. Carr. £1.
AVO TRANSISTOR ANALYSER CT.446: £35. carr. £1.50.
CT.420 SIGNAL GENERATOR: 200-8000c/s Variable tuning. Two fixed frequencies 9000 and 10,000. Internal calibrator 100 & 500 c/s. £75 each carr. £2.
NOISE GENERATOR TF-1106: Frequency 1 to 200 Mc/s Direct noise factor calibration. Output impedance 70 ohms £65 each. Carr. £1.50.
COUNTER EXTENSION UNIT TF-1434/2: Complete with plug-in units £75 carr. £1.50.
MW-59 UNIVERSAL KLYSTRON POWER SUPPLY: £85. Carr. £3.
TF-1278/1 TRAVELLING TUBE WAVE AMPLIFIER: £25. Carr. £2.
BPL A.C. MILLIVOLTMETER TYPE VM.348-D Mk. 3: 2 millivolts-2 volts, 6 ranges. £30. Carr. £1.
MARCONI DUAL TRACE UNIT TM-6456: £30. Post 60p.
500. Price: £120 each + £2 carr.
H.V. TRANSFORMER: 8000/8000. Output 300mA. rms. Size: 12in. x 12in. x 36in. 230V input. £40. Carr. £4.
FIREPROOF TELEPHONES: £25.00 each. carr. £1.50.
POWER UNIT: 110/230 volts a.c. input. 28 volts d.c. at 40 amps output. £30.00 each. carr. £3.00.
SMOOTHING UNIT (for the above): £10.00 each. carr. £2.00.
X-BAND MODULATOR CALIBRATOR TYPE MC-4420-X: Mnfr. James Scott. £125 each. Carr. £1.
HP-766D DUAL DIRECTIONAL COUPLER: 940-1975MHz. £35 each. 75 post.
BACKWARD WAVE OSCILLATOR TYPE SE-125: 6.3 heater. 105V Anode. 7.9mA. Mnfr. Watkins & Johnson. £85 each. Carr. £1.
TEKTRONIX TIME MARK GENERATOR TYPE 180-SI: 5, 10, 50 MHz. £65. Carr. £2.
ROTARY INVERTERS: TYPE PE.218E — input 24-28V d.c., 80 Amps. 4,800 rpm. Output 115V a.c. 13 Amp 400 c/s. 1Ph. P.F.9. £20.00 each. Carr. £2.50.
FREQUENCY METER BC-221: 125-20,000 Kc/s complete with original calibration charts. Checked out, working order £20 + £1.50 carr.

ALL U.K. ORDERS SUBJECT TO VALUE ADDED TAX. THIS MUST BE ADDED TO THE TOTAL PRICE (including post or carriage)

If wishing to call at stores, please telephone for appointment

W. MILLS

3 & 3a BALDOCK STREET, WARE, HERTS. SG12 9DT
WARE 66312 (STD 0920)
and at ELSTOW STORAGE DEPOT. Phone: Bedford 740605 (STD 0234)

ALL MAIL ORDER BY RETURN. C.O.D. SERVICE WELCOME

C. T. ELECTRONICS

Tel: 01-994 6275

All mail order and enquiries to 270 Acton Lane, Chiswick, London W4 5DG.

VAT
Unless otherwise stated all prices are exclusive of VAT. Please check whether the goods you are ordering are 25% or 8% Carriage orders under £5 please add 33p. Order over £10 post free in U.K. only. This is to be at our discretion.

SEMICONDUCTORS

AAZ12 25p	BC214 14p	IS100 15p	TIP29B 54p
AC107 35p	BC214L 15p	IS103 15p	TIP30B 60p
AC125 25p	BC238 15p	MJ340 50p	TIP31B 65p
AC126 25p	BC239 15p	MJ481 95p	TIP32B 77p
AC127 25p	BC300 30p	MJ2801 £1.25	TIP35B £2.71
AC128 25p	BC301 30p	MJ2901 £1.95	TIP36B £3.50
AC176 25p	BC302 30p	MJE340 50p	TIP41B 70p
AC187 27p	BC303 35p	MJE370 75p	TIP42B 95p
AC188 27p	BCY31 35p	MJE371 90p	TIP29C 68p
ACY17 25p	BCY32 95p	MJE520 65p	TIP30C 72p
ACY18 25p	BCY33 60p	MJE525 75p	TIP32C 1.00
ACY19 25p	BCY34 65p	MJE3055 1.50	TIP33C 1.20
ACY20 25p	BCY38 65p	MM1613 45p	TIP33C 1.20
ACY21 25p	BCY39 95p	MM1712 60p	TIP34C 1.80
AD140 60p	BCY55 £1.50	MPI103 45p	TIP35C £3.00
AD142 60p	BCY70 20p	MPI103 45p	TIP35C £3.74
AD161 45p	BCY71 20p	MPI104 35p	TIP42C 1.00
AD162 45p	BCY72 20p	MPI104 35p	TIP42C 1.00
AF114 25p	BO121 75p	MPI104 35p	TIP42C 1.00
AF115 25p	BO123 85p	(2N5458) 35p	TIS50 40p
AF116 25p	BO124 70p	MPI105 40p	ZIX107 15p
AF117 25p	BO131 40p	(2N5459) 40p	ZIX300 15p
AF118 50p	BO132 50p	OA47 10p	ZIX500 16p
AF124 30p	BD135 50p	OA70 10p	ZIX501 20p
AF129 40p	BD136 50p	OA79 10p	ZIX504 50p
BA102 30p	BD139 75p	OA81 10p	ZIX531 30p
BA112 50p	BD140 87p	OA90 10p	ZIX550 25p
BA114 16p	BD153 80p	OA91 10p	IN659 8p
BA155 16p	BD156 80p	OA200 10p	IN914 8p
BA156 15p	BDY17 £1.50	OA202 10p	IN916 8p
BC107 13p	BDY18 £1.75	OA210 35p	IN4001 8p
BC108 12p	BDY19 £1.90	OA211 35p	IN4002 9p
BC109 14p	BDY20 £1.20	OC16 90p	IN4003 9p
BC109c 16p	BF152 20p	OC19 85p	IN4004 10p
BC113 13p	BF166 30p	OC22 55p	IN4005 12p
BC114 13p	BF178 35p	OC26 65p	IN4008 14p
BC115 15p	BF180 35p	OC28 60p	IN4007 16p
BC116 15p	BF194 15p	OC35 60p	IN4148 7p
BC117 20p	BF195 16p	OC36 65p	2N696 25p
BC118 15p	BF196 16p	OC42 40p	2N697 25p
BC119 30p	BF197 16p	OC44 20p	2N698 25p
BC143 25p	BF200 35p	OC45 25p	2N706 12p
BC147 12p	BF224 18p	OC70 12p	2N706A 14p
BC148 12p	BF244J 24p	OC71 12p	2N708 15p
BC149 12p	BF245 45p	OC72 20p	2N929 22p
BC149c 14p	BF259 55p	OC75 25p	2N930 20p
BC157 14p	BFX29 30p	OC76 25p	2N1132 25p
BC158 14p	BFX34 30p	OC77 40p	2N1302 30p
BC159 15p	BFX85 30p	OC81 25p	2N1303 30p
BC167 14p	BFX86 30p	OC83 25p	2N1304 30p
BC168 14p	BFX88 30p	OC84 25p	2N1305 30p
BC169 14p	BFY10 35p	OC139 30p	2N1306 30p
BC169c 15p	BFY44 50p	OC170 25p	2N1307 30p
BC172 13p	BFY50 25p	OC171 30p	2N1308 30p
BC182 12p	BFY51 25p	OC200 60p	2N1309 30p
BC182L 12p	BFY52 25p	OC28 60p	2N1613 30p
BC183 12p	BFY53 25p	OC202 75p	2N1711 30p
BC183L 12p	BFY90 65p	TIP29A 45p	2N1890 60p
BC184 12p	BSV68 70p	TIP30 55p	2N2146 15p
BC184L 12p	BSW63 65p	TIP31A 57p	2N2147 90p
BC185 35p	BSW68 80p	TIP32A 69p	2N2160 80p
BC186 27p	BSX19 15p	TIP33A 50p	2N2217 25p
BC212 12p	BSX20 15p	TIP34A £1.40	2N2218 25p
BC212L 14p	BSX21 25p	TIP35A £3.20	2N2219 25p
BC213 12p	BY127 20p	TIP36A £3.50	2N2222 20p
BC213L 12p	BY164 65p	TIP41A 70p	2N2222A 25p

QTY DISCOUNTS 12 + 10% 25 + 15% 100 + 20%

TTL (full stocks available)

SN7400 18p	SN7411 23p	SN7430 20p	SN7447 £1.50	SN7481 £1.25
SN7401 18p	SN7412 22p	SN7432 42p	SN7448 £1.75	SN7482 87p
SN7402 20p	SN7413 40p	SN7433 70p	SN7450 20p	SN7483 £1.00
SN7403 20p	SN7416 30p	SN7434 50p	SN7451 20p	SN7484 90p
SN7404 20p	SN7417 30p	SN7438 50p	SN7452 20p	SN7486 45p
SN7405 20p	SN7420 20p	SN7440 20p	SN7453 20p	SN7490 75p
SN7406 30p	SN7422 38p	SN7441A 75p	SN7454 20p	SN7491A 1.00
SN7407 30p	SN7423 38p	SN7442 75p	SN7455 20p	SN7492 75p
SN7408 20p	SN7425 38p	SN7443 £1.00	SN7456 20p	SN7493 75p
SN7409 40p	SN7427 42p	SN7445 £1.70	SN7457 45p	SN7494 80p
SN7410 18p	SN7428 50p	SN7446 £2.00	SN7458 45p	SN7495 £1.00
			SN7459 45p	SN7496 £1.00
			SN7460 80p	SN7497 £2.25

METAL BOXES

ALUMINIUM BOXES IDEAL FOR VEROBOARD WITH BASE & P.K. SCREWS

AB7	2 3/4" Long	5 1/4" Wide	1 1/2" High	55p
AB8	4"	4"	1 1/2"	55p
AB9	4"	2 3/4"	1 1/2"	55p
AB10	4"	5 1/4"	1 1/2"	55p
AB11	4"	2 1/2"	2"	65p
AB12	3"	2"	1"	55p
AB13	6"	4"	2"	77p
AB14	7"	5"	2 1/2"	90p
AB15	8"	6"	"	£1.16
AB16	10"	7"	3"	£1.32
AB17	10"	4 1/2"	3"	£1.10
AB18	12"	5"	3"	£1.32
AB19	12"	8"	3"	£1.80

ALUMINIUM BOXES WITH SLOPING TOP PANEL — IDEAL FOR PRE-AMPS, ETC., USING SLIDER CONTROLS

AB20	8" Long 9" Wide 3 1/2" High at back 2" High at front 6" Slope to front With P.K. Screws	£2.20
AB21	As above but 10" long	£2.20
AB22	As above but 12" long	£2.60

S.C.R.s

2N2306 70p	CRS1/05 40p
2N2369A 50p	CRS1/10 56p
2N2477 30p	CRS1/20 60p
2N2646 50p	CRS1/40 65p
2N2846 £1.50	CRS1/60 60p
2N4904 25p	CRS3/10 62p
2N2905 30p	CRS3/20 62p
2N2906 25p	CRS3/40 90p
2N2907 25p	CRS7/400 £1.00
2N2926 13p	CRS16/100 85p
2N3053 25p	CRS16/200 85p
2N3055 50p	CRS16/600 £1.60
2N3232 £1.35	CR106B 45p
2N3553 30p	C106D 70p
2N3702 12p	40669 90p
2N3703 12p	TIC44 35p
2N3704 12p	2N4444 £1.90
2N3705 12p	BT10/500A 90p
2N3706 14p	
2N3707 14p	
2N3708 14p	
2N3709 14p	
2N3771 £1.50	
2N3772 £1.60	
2N3792 £1.80	
2N3794 30p	
2N3819 30p	
2N3820 55p	
2N3823 70p	
2N3856 85p	
2N3904 22p	
2N3905 25p	
2N3906 25p	
2N4014 80p	
2N4035 62p	
2N4037 44p	
2N4058 14p	
2N4059 16p	
2N4060 12p	
2N4061 12p	
2N4062 12p	
2N4126 18p	
2N4286 25p	
2N4287 25p	
2N4288 27p	
2N4289 30p	
2N4290 25p	
2N4291 32p	
2N4302 45p	
2N4444 £1.90	
2N4871 35p	
2N4903 £1.30	
2N4919 90p	
2N5069 £1.30	
2N5191 96p	
2N5192 £1.20	
2N5194 £1.10	
2N5195 £1.40	
2N5245 45p	
2N5296 55p	
2N5298 50p	
2N5457 35p	
2N5458 35p	
2N5459 40p	
2N5485 55p	
2N5490 55p	
2N5555 65p	
2N5777 40p	

BRIDGE RECTIFIERS

W02 1A 200V 38p
BY164 1A 200V 57p
MDA952/2 6A 100V 80p

ZENER DIODES

BZY88 Series 400mW
3.3V-33V 5% 11p
1.5W range 25p
10W range 45p

L.E.D.

TL 209 38p
HP50B2 28p
MA2082R 20p

L.D.R.

ORP12 60p
NE555 Timer 80p

TO3 VOLTAGE REGULATORS

L005 5V 650mA	£1.60 ea.
L036 12V 600mA	
L037 15V 450mA	

VEROBOARD

17 x 2 1/2"	0.15
17 x 3"	£1.18
17 x 5"	£1.66
17 x 7"	£1.30
PIN INS TOOL	72p
SP F CUTTER	65p
100 PINS SS	40p
100 PINS DS	40p
2 1/2 x 3"	32p
2 1/2 x 5"	35p
3 1/4 x 3 1/4"	35p
3 1/4 x 5"	40p
PIN INS TOOL	72p
500 PINS SS	£1.55
500 PINS DS	£1.55

POTENTIOMETERS

Linear or Log	Single	Double
Rotary Pots	17p	45p
Rotary Switched	25p	

HIGH PERFORMANCE MODERN SCOPE TUBES

By Telefunken Limited. qty only 5" rectangular display. Type No. D14/131 Price £25,000 each + VAT 8%. All extras provided free whilst remaining in stock. Postage £1.00. All brand new

REXINE COVERED ALUMINIUM CASES WITH SCREWS & FEET

RB1 6" x 4" x 1 1/4"	£1.05	RB4 11" x 6" x 3"	£1.85
RB2 8" x 5" x 2"	£1.20	RB5 11" x 7 1/2" x 3 1/2"	£2.35
RB3 9" x 5" x 2 1/2"	£1.35		

+ 8% Postage 35p

★ SPECIAL OFFERS ★

MINIATURE MAINS TRANSFORMER. PRI240V.
SEC. 12V. 100Ma Manuf. Hinchley Size. 36 x 45 x 40mm. F.C. 53mm.
Price 1.65p. 100 60p ea. 10 000 40p ea. 8% VAT.

MINIATURE MAINS TRANSFORMER. Primary 115/240V. Sec. 18V/250 Ma at 80p ea. + VAT & postage 33p. 8% VAT

MULLARD POT CORE TYPE FX2241 at 60p ea. + 33p p.p. 8% VAT

24V D.C. SOLENOID by MAGNETIC DEVICES 60p each. 2 1/2" long x 3/8" x 3/8" in. + 8% VAT

240V. A.C. SOLENOID. Reversible operation. twin coil. Size approx. 2 1/4" x 1 1/2" x 1 1/2" in. 90p.

30 unmarked OC71 transistors £1.00
25 unmarked 250mW Zener diodes. 4.7V. 5.1V. 6.2V. 7.5V. 9.1V. 10V. Measured and tested £1.00
Please state voltage required
50 GE Diode OA47 equivalent £1.00

8µF 600V WKG PAPER CAPACITORS, ideal for Strobe Constructors. £1.50 each + 8% VAT + 33p post

Many other values of PAPER CAPACITORS in stock. Phone for details

JACKSON AIRSPACED CAPACITORS to suit 1/4" spindle.
100pF Two Gang at 55p + 25% VAT
500pF Two Gang at 75p + 25% VAT

MULLARD TUBULAR CERAMIC UHF TRIMMERS (PROFESSIONAL)
Type 092 0.8-2.2p } Price 10p ea.
801 0.8-2.2p }
991 0.5-1.3p }

QUANTITY DISCOUNTS PLEASE TELEPHONE
1000pF Feedthrough capacitor 5p ea.
Miniature tubular P.C. trimmers 3.5-13pF
6.30pF 10p ea.
4p c/o Varley 700 Ω relay 50p ea.

Gold Flashed professional TRANSISTOR SOCKETS. To suit small signal TO18. etc. 30 for £1.00 + 8% VAT

W. WOUND POTS 1 Ω-100K Ω at 30p each Colvern or Reliance styles + 25% VAT

VERO EDGE CONNECTOR 24 way 1" pitch 30p each + VAT. All

Marshall's

A. Marshall (London) Ltd Dept. WW
42 Cricklewood Broadway London NW2 3ET Tel: 01-452 0161/2
Telex: 21492
& 85 West Regent St Glasgow G2 2DD Tel: 041-332 4133
& 1 Straits Parade Fishponds Bristol BS16 2LX
Tel: 0272 654201/2
& 27 Rue Danton Issy Les Moulineaux Paris 92 Tel: 644 2356

Catalogue price 25p Trade and export enquiries welcome

**OUR RANGE COVERS OVER 7,000 ITEMS
THE LARGEST SELECTION IN BRITAIN
TOP 200 IC'S TTL, CMOS & LINEARS**

CA3020A	1.80	CD3130	0.88	NE561	4.48	SN7448	0.90	SN74160	1.10
CA3028A	0.79	CD4510	1.25	NE565	4.48	SN7450	0.16	SN74161	1.10
CA3035	1.37	CD4511	1.94	SN414	1.80	SN7451	0.16	SN74162	1.10
CA3046	0.70	CD4516	1.25	SN410C	1.70	SN7453	0.16	SN74163	1.10
CA3048	2.11	CD4518	1.87	SN611C	1.70	SN7454	0.16	SN74164	2.01
CA3052	1.62	CD4520	1.87	SN612C	1.70	SN7456	0.16	SN74165	2.01
CA3089E	1.96	LM301A	0.48	SN624E	2.60	SN7476	0.33	SN74167	4.10
CA3090Q	4.23	LM308	2.50	SN621C	2.60	SN7472	0.28	SN74174	1.25
CD4000	0.36	LM005TL	1.50	SN623C	4.59	SN7473	0.38	SN74175	0.90
CD4001	0.36	LM380	1.10	SN640C	3.10	SN7474	0.38	SN74176	1.44
CD4002	0.36	LM381	2.20	SN7400	0.16	SN7475	0.50	SN74180	1.40
CD4003	1.58	LM702C	0.75	SN7401	0.16	SN7476	0.38	SN74181	1.88
CD4007	0.36	LM709	0.90	SN7401AN	0.38	SN7483	0.50	SN74190	2.30
CD4008	1.63	TO99	0.38	SN7402	0.16	SN7481	1.25	SN74191	2.30
CD4009	1.18	8DIL	0.45	SN7403	0.16	SN7482	0.75	SN74192	1.15
CD4010	1.18	14DIL	0.38	SN7404	0.18	SN7483	0.95	SN74193	1.15
CD4011	0.36	LM710	0.47	SN7405	0.18	SN7484	0.95	SN74196	1.60
CD4012	0.36	LM723C	0.90	SN7406	0.45	SN7485	1.25	SN74197	1.58
CD4013	0.66	LM741C	0.90	SN7407	0.45	SN7486	0.32	SN74198	2.25
CD4014	1.72	TO99	0.40	SN7408	0.18	SN7489	0.45	SN74199	2.25
CD4015	1.72	8DIL	0.40	SN7409	0.22	SN7491	0.85	SN76003N	2.92
CD4016	0.66	14DIL	0.38	SN7410	0.16	SN7492	0.45	SN76013N	1.95
CD4017	1.72	LM747	1.05	SN7411	0.25	SN7493	0.45	SN76033N	1.60
CD4018	2.56	LM748	0.60	SN7412	0.28	SN7494	0.82	SN76033N	2.92
CD4019	0.88	8DIL	0.73	SN7413	0.35	SN7495	0.72	AA200	1.80
CD4020	1.91	14DIL	0.73	SN7414	0.35	SN7496	0.75	TAA300	1.80
CD4021	1.72	LM3900	0.70	SN7417	0.35	SN74100	1.28	TAA350A	1.0
CD4022	1.66	LM7805	2.00	SN7420	0.16	SN74107	0.38	TAA550	0.60
CD4023	0.36	LM7812	2.50	SN7423	0.28	SN74110	1.00	TAA611C	2.18
CD4024	1.26	LM7824	2.50	SN7425	0.28	SN74113	1.92	TAA621	2.03
CD4025	0.32	LM7815	2.50	SN7427	0.28	SN74119	0.37	TAA661B	1.32
CD4027	0.43	MC1303L	0.50	SN7430	0.16	SN74122	0.58	TBA5418	2.25
CD4028	1.50	MC1303P	2.50	SN7432	0.28	SN74123	0.60	TBA651	1.68
CD4029	3.50	MC1330P	0.90	SN7437	0.35	SN74141	0.85	TBA800	1.40
CD4030	0.87	MC1351P	0.80	SN7438	0.35	SN74145	0.90	TBA810	1.40
CD4031	5.15	MC1466L	3.50	SN7440	0.16	SN74150	1.50	TBA820	1.15
CD4037	1.88	MC1469B	2.75	SN7441AN	0.85	SN74151	0.85	TBA830	4.00
CD4041	1.88	MC14553	4.07	SN7442	0.65	SN74153	0.85	14DL5KT	0.12
CD4042	1.38	NE555V	0.70	SN7445	0.90	SN74154	1.50	16DL5KT	0.13
CD4049	0.81	NE556	1.30	SN7446	0.95	SN74155	1.50		
CD4050	0.66	NE560	4.48	SN7447	0.95	SN74157	0.85		

LONDON, GLASGOW, PARIS — AND NOW
BRISTOL
IT'S OUR SERVICE THAT MAKES US GROW

POPULAR SEMICONDUCTORS

2N989F	0.22	2N3906	0.27	4FJ39	0.65	BD139	0.71	MPSA46	0.31
2N989G	0.22	2N4037	0.67	4F239	0.65	BD140	0.77	OC29	0.25
2N989H	0.82	2N4036	0.67	4F240	0.65	BD115	0.38	OC35	1.60
2N695	0.59	2N4058R	0.18	4F278	0.70	III117	0.55	OC42	0.50
2N706	0.14	2N4062	0.15	4F280	0.79	III154	0.20	OC45	0.32
2N708	0.17	2N4289	0.34	AL102	1.00	III159	0.27	TIP29A	0.49
2N911C	0.28	2N4920	1.10	III107	0.14	III180	0.35	TIP29C	0.58
2N915E	0.32	2N4921	0.83	III108	0.14	III181	0.36	TIP31A	0.82
2N1302	0.185	2N4923	1.00	III109	0.14	III184	0.30	TIP32A	0.74
2N1304	0.26	2N5245	0.47	III147B	0.14	III194	0.12	TIP33A	1.01
2N1306	0.31	2N5294	0.48	BC148B	0.15	III195	0.12	TIP34A	1.51
2N1308	0.47	2N5296	0.48	BC149B	0.15	III196	0.13	TIP35A	2.90
2N1711	0.45	2N5457	0.48	BC157A	0.16	III197	0.15	TIP36A	3.70
2N2102	0.60	2N5458	0.48	BC158A	0.16	III198	0.16	TIP41A	0.79
2N2147	0.78	2N5459	0.46	BC167B	0.15	II214A	0.21	TIP42A	0.90
2N2148	0.94	2N6027	0.46	BC168B	0.15	II257	0.47	TIP2955	0.98
2N2218A	0.22	3N128	0.73	BC169B	0.15	II258	0.53	TIP3055	0.50
2N219A	0.76	3N140	1.00	BC182	0.12	II259	0.55	TIS43	0.28
2N2220	0.25	3N141	0.81	BC182L	0.12	II261	0.27	ZTX300	0.13
2N2221	0.18	3N200	2.49	BC183	0.12	II265B	0.25	ZTX301	0.13
2N2222	0.20	40361	0.40	BC183L	0.13	II269	0.24	ZTX500	0.14
2N2369	0.20	40362	0.46	BC183L	0.13	II275	0.24	ZTX501	0.13
2N2646	0.55	40406	0.44	BC184L	0.13	II279	0.30	ZTX502	0.18
2N2904	0.22	40407	0.35	BC212A	0.16	II280	0.27	1N914	0.07
2N2905	0.25	40408	0.50	BC212LA	0.16	II281	0.24	1N375A	0.16
2N2906	0.19	40409	0.52	BC213A	0.15	II282	0.30	1N4007	0.10
2N2907	0.22	40410	0.52	BC214B	0.18	II283	0.25	1N4148	0.07
2N2924	0.20	40411	3.00	BC237B	0.16	II284	0.225	1N4504	0.22
2N2926G	0.12	40594	0.74	BC238C	0.15	II285	0.23	1N5408	0.30
2N3053	0.25	40595	0.84	BC239C	0.15	II286	0.205	AA119	0.08
2N3054	0.60	40836	1.10	BC257A	0.16	II287	0.48	BA102	0.26
2N3055	0.75	40873	0.73	BC257B	0.16	II288	0.20	BA145	0.18
2N3391	0.28	AC126	0.20	BC259B	0.17	II289	0.18	BA154	0.12
2N3392	0.15	AC127	0.20	BC301	0.34	II290	0.11	BA155	0.12
2N3393	0.15	AC128	0.20	IC307B	0.17	II291	0.95	BB103B	0.23
2N3440	0.59	AC151	0.27	IC308A	0.15	II292	1.20	BB104B	0.45
2N3442	1.40	AC152	0.48	BC309C	0.20	II293	1.05	BY126	0.12
2N3638	0.15	AC153	0.35	BC327	0.23	II294	1.45	BY127	0.15
2N3702	0.12	AC176	0.30	BC328	0.22	II295	1.00	BZ211	0.51
2N3703	0.13	AC187K	0.35	BCY70	0.35	II296	0.48	BZ212	0.51
2N3704	0.16	AC188K	0.40	BCY71	0.22	II297	0.55	OA47	0.06
2N3706	0.15	AD143	0.68	BCY72	0.15	II298	0.75	OA81	0.18
2N3708	0.14	AD161	0.50	BD121	1.00	II299	0.60	OA90	0.06
2N3714	1.38	AD162	0.50	BD123	0.82	II300	0.70	OA91	0.06
2N3716	1.80	AF106	0.40	BD124	0.67	II301	1.20	OA200	0.08
2N3721	2.20	AF109	0.40	BD131	0.40	II302	0.75	BY164	0.57
2N3723	2.65	AF115	0.35	BD132	0.50	II303	0.47	ST2	0.20
2N3789	2.06	AF116	0.35	BD135	0.43	II304	0.39	AO669	1.00
2N3819	0.37	AF117	0.35	BD136	0.47	II305	0.25	TC44	0.29
2N3820	0.64	AF118	0.35	BD137	0.53	II306	0.31	C106D	0.55
2N3904	0.27	AF124	0.30	BD138	0.63	II307	0.31	OPR12	0.60

Prices correct at December 1975, but all exclusive of V.A.T Post & Packing 25p


DATA AND COMMUNICATIONS TERMINALS

Teletype 28, 32, 33, 35, 40
TermiNet 30, 300 & 1200 (30 and 120 cps)
Teleterm 1030 & 1132 (portable 30 cps
with integral coupler and RS 232C)
Other page printers (by Siemens, ITT Creed, etc.)
TermiNet 120 line printer

- ★ Spares, repairs, overhauls and maintenance
- ★ Other types and models available
- ★ Refurbished units also available
- ★ Short and long period rentals
- ★ Minicomputer interfaces
- ★ Quantity discounts
- ★ Immediate delivery

TELEPRINTER EQUIPMENT LTD.
70-80 AKEMAN STREET,
TRING, HERTS., U.K.

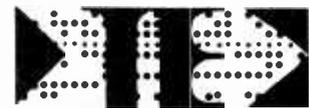Telephone 0442-82-4011
Cables RAHNO Tring
Telex 82362
A/B Batelcom Tring



WW—080 FOR FURTHER DETAILS

Semiconductor Data ?

ESSENTIAL FOR ALL TESTING, INSPECTION AND MAINTENANCE.

THE SEMICON INTERNATIONAL TRANSISTOR INDEX 1975/6 (6th Edition) NOW AVAILABLE

Easy reference alpha-numeric listings of about 24,000 transistors of international origin, European, Japanese, USA etc.. Maximum ratings and basic characteristics. 400+ pages of invaluable data.

EXTENSIVE SUBSTITUTION GUIDE
CV & BS NUMBERED DEVICES
TERMINATION OUTLINE DRAWINGS

ALTERNATIVE MANUFACTURERS AND AGENTS ADDRESSES

ORDER NOW, £10.60 includes postage in the UK
(Elsewhere £11.90 by surface mail)

FROM SEMICON INDEXES LTD

2(W) DENMARK ST. WOKINGHAM, Berks. RG11 2BB
Tel: Wokingham (STD 0734) 786161

This is Vol.1 of the Semicon Index Series.
Vol.2 (Diodes & SCRs) and Vol.3 (ICs) available soon. Same price
ORDER NOW AND AVOID DISAPPOINTMENT
WW—079 FOR FURTHER INFORMATION

REED SWITCH INSERTS



Overall length 1.85in (Body length 1.1in.) Diameter 0.14in to switch up to 500mA or 250VDC. Gold clad contacts 74p per doz. £4.15 per 100. £29.95 per 1,000. £272 per 10,000. All carriage paid U.K.
Operating Magnets 95p per doz. £6.95 per 100. £67 per 1,000. All carriage paid U.K.
Operating Coils for 12v supply to accept up to four standard reeds. £2.50 per doz. £12.60 per 100. All carriage paid U.K.
Heavy duty type. (Body length 2in.) Diameter 0.22in to switch up to 1A at up to 250VAC. £1.45 per doz. £6.95 per 100. £52.00 per 1,000.
Changeover Heavy Duty type £2.80 per doz. All carriage paid U.K.
Magnets for HD reeds £1.50 per doz. A few coils available for HD reeds P.O.A.

C-SCOPE METAL DETECTORS

Represent today's BEST VALUE in metal detection equipment
 BF050 integral speaker £26.24
 BF060 integral speaker and meter £33.59
 IS100 with headphones £52.59
 IS300 with headphones and meter £68.24
 TR200 with headphones £59.90
 TR400 with headphones and meter £78.43

Full information on receipt of 10p stamp

HUNT THAT TREASURE!

INDUCTION GENERATOR. Requires a supply voltage of 50V 50Hz and provides an output of 7V per 1,000 r.p.m. directly proportional to speed. This instrument has a wide variety of applications, e.g. anemometers, measuring shaft speed, etc. In brand new condition £5.60 post paid.

ITT OFFICE INTERCOM. 20 way with modern manual SWB and facilities. Lightweight desk sets. Brand new in cartons £160 inc. P & P and VAT. Spare delaylines £7.50 ea

TELEPRINTER PAPER. Standard rolls. 2 ply £5.00 per doz. 3 ply £5.40 per doz. 4 ply £5.70 per doz. All P. Pd. U.K. Telex your order now.

TAPE STORAGE CANS. Brand new finished steel cans originally intended for 16mm film but ideal for storing 7in. reels of tape. Our last supply of these items was quickly exhausted at 30p each but as a result of a massive new purchase we can now offer a case of 55 at £6.80 inc. P & P and VAT.

SOLAR CELLS. Ferranti silicon MS18E active area 390 sq. mm. Open circuit voltage 550mV at 3000 lumens/sq. ft. Sht. Cct. Current 60mA. Optimum load 9.0 ohms. Dia 34mm. Thickness 6mm. Ex. made up panel £1.35 (inc. P & P and VAT).

CONTINENTAL CUSTOMERS — we have a direct link by air from Lydd to Beauvais (also Channel Islands) and are 35-45 minutes drive from Dover-Folkestone with direct overcraft and sea links with France and Belgium



LEMANIA AIRCREW CHRONOGRAPHS

Stainless steel case with screw back, luminous hands and markings. One-fifth sec. sweep hand controlled independently of main movement by press to start stop and return to zero button. 15 jewel movement. Many of these watches are as new but all have been completely overhauled and checked for accuracy. Fitted strap. White face £18.80. Black face £19.75 inc. P & P

GS WATCHES all with brushed stainless steel case with screw back and black faces. Manufactured by TIMOR, ETERNA, LEMANIA, VERTEX, RECORD, CYMA, etc. to a standard specification. Completely overhauled. Fitted strap. £9.05 (inc. P & P). We also have limited quantities of these watches by OMEGA, BUREN, HAMILTON and IWC at £15.30 inc. P & P. SMITHS GS watch with sweep second hand £9.25 inc. P & P & VAT. All watches: Inspection against remittance.



ANALYTICAL EQUIPMENT

GAS CHROMATOGRAPHY RESEARCH OVEN PV4051/4056 (other GC items in stock)
 A large capacity oven of low thermal mass for use between 35 and 400°C. Provides a forced air circulating system yielding 1000 changes of air per min. The oven has forced air cooled outer surfaces when the internal temperature is high. 210-240V. 50Hz. 2.6KW. £31.50 (C. Pd. England and Wales)

IONISATION AMPLIFIER PV4075
 A modern high grade low noise solid state amplifier to feed a potentiometer recorder. 18 input ranges from 10⁻¹² to 5 x 10⁻¹ A with 5 outputs of 1mV to 100mV. Linearity 0.1% f.s. Noise less than 0.5% f.s. at max sensitivity. Back off facility. Dimensions 28 x 10 x 43 cm deep. With operating information £28.50. (C. Pd. U.K.)
 Details of these three and other gas chromatography items, price 25p (C. W. O. only). Handbooks (complete) available.

AIRCRAFT INSTRUMENTS for industrial and educational use. Released items available for flight use.

400Hz ROTARY CONVERTERS. Both DC & AC input available. E.g. 415v 50Hz to 115v 400Hz 1ph 50w AJ. £27.50.

MULTIWAY CABLES in stock up to 50 way or up to 750 amp. Also PTFE insulated types.

MARCONI SPECTRUM ANALYSERS OA1094A/S. Listed at £2700. Our price £565.

ACTUATORS, RELAYS, FLOODLAMPS, POWER UNITS, TRIMPOTS FANS MICROWAVE EQUIPMENT. All ex-stock

SOLARTRON OSCILLOSCOPES in stock CD1183, CD1212, CD1220, CD1400 P.O.A. and **INSTRUMENTS** SR151 & 152, VP253, OS103, CS046, JX641, JX641A, VF252, JX746, LM1420, TD960, JX603, JM1600, etc. P.O.A.

SPECIALIST STOCKISTS OF SERVOMOTORS, SYNCHROS, TEST EQUIPMENT, METERS AND CONNECTORS

Servo and Electronic Sales Ltd
 Established 1953

24 HIGH ST., LYDD, KENT TN29 9AJ. Tel. Lydd 20252 (STD 0679) VAT No. 201-1296-23. TELEX 965265

PLESSEY GROUND BASED U.H.F. GROUND/AIR TX/RX FOR EXPORT ONLY OR SALE TO LICENSED USERS
 Single Channel Receiver 5820-99-932-5694
 Single Channel Transmitter 5820-99-932-5698
 Single Channel Amplifier 5820-99-932-5701
 Power Unit for Amplifier 5820-99-932-5700
 Cooler Unit 5820-99-932-3995
 These assemble into free standing rack unit providing U.H.F. communications over 225 0 to 399 9MHz. the TX/Amplifier unit giving 100 Watts R.F. output into 50 Ohms. Spare sub-units available. All are guaranteed new and unused. Full details on request.

HEWLETT PACKARD SAMPLING SCOPE HP185A, £324 inc. carr and V A T HP185B £357.

STAINLESS STEEL VACUUM CONTAINERS FOR LIQUIDS. Capacity 2 U.S. GALLS. FITTED WITH DELIVERY TAPS. Brand new in cartons—£25 (C. Pd. U.K.)

PANEL DISPLAY RECORDING CAMERA. Manufactured A.G.I. Specifically for the recording of complex instrument displays on 2 1/4 in x 2 1/4 in shots. Fitted 50mm F3.5 lens. Shutter speeds 1/100, 1/50, 1/25 sec. and time exp. Focusing at 1.75 to 50ft. in 1B steps. Aperture stops F3.5 to F22. Prismatic viewfinder and facility for viewing direct on ground glass screen. Rotating filter attachment. Cord film advance and shutter cock with septe. Button control and electrical release facility (24V DC). Spool holds 40 exposures. Camera may be wall mounted on bracket supplied. Tripod mounting sockets provided. In wooden case. Two grades available, as new. Grade A £35.50 (inc. P and VAT). Somewhat used but serviceable Grade B £28.40 (inc. P & P and VAT).


COMPUTERS AND PERIPHERALS

ICL 1904 CPU (complete) — documentation will be available with 32K 7.5 Plessey core store £1000. ICL 7070 2 UNIFLEXER (complete) £150. BRPE 110 ch. sec. 8 chan. paper tape punches, some silence covers £120. Plessey 68/1339 32K (13 bit) 1uS corestore £35. Mullard AW 3331 16K (25 bit) 2uS corestore £40. Mullard AW 3795 corestore £30. IBM 729/IV M T U s — documentation available £200. ICL mainframe PSUs 6V 25A and 28V 20A £25 & £40. ICL peripheral PSUs — 10V and 20V £20. Ampex & D.R.I. digital tape heads (7 & 9 track) P.O.A. ICL 1971 & 1973 servo motors & vacuum blowers P.O.A. CDC, ICL 2802 (EDSB) disc drives — mechanical spares P.O.A. RCA ICL 1500 series — electrical & mechanical spares P.O.A. Belling-Lee R.F.I. suppressors — 3ph 20A (50Hz) £30. STC Senterical fire (smoke) detectors — data available £15. Vactric Shaft position encoders type 110P101 (10 bit) £15. Tolana B channel F.M. instrumentation recorder (complete) £350.
 We can also design and construct non-standard interfaces between computers instrumentation and control equipment etc. and we have a large number of one-off pieces of test equipment. If you have any problems in this field, do not hesitate to get in touch with us. Contact O.P. Manager Chris Seton (Ext'n 3).

GE Optical Tape Readers 5, 7 and 8 track. 300 ch/sec. built-in amps and cond. ccts. Excellent condn. Tested. £70 inc. P & P and VAT


Metal Oxide Resistors (ELECTROSIL & WELWYN) Tantalum Capacitors (KEMET, ITT, PLESSEY, ETC.) ALL AVAILABLE EX STOCK IN MANUFACTURING QUANTITIES

MIL SYNCHROS AND SERVOMOTORS EX STOCK

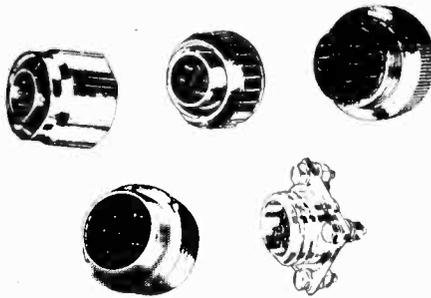

OVER 300,000 RF AND MULTIWAY CONNECTORS IN STOCK. TELEX YOUR REQUIREMENTS NOW!

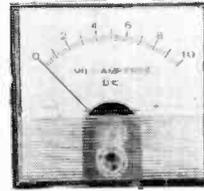REACH FOR THE PEAKS OF MEASURING INSTRUMENT ENGINEERING!



TYPE TAD


Dim's	48	66	85	118	150
in	x	x	x	x	x
mm	42	50	70	106	110
500 μA	£3.73	£3.91	£4.10	£5.00	£5.55
500 μA	£3.44	£3.61	£3.82	£4.72	£5.42
1mA	£3.37	£3.54	£3.74	£4.63	£5.33
15vDC	£3.40	£3.59	£3.77	£4.67	£5.36
300vAC	£3.57	£3.76	£3.94	£4.83	£5.40

TYPE SA

Dim's	43	51	61	82
in	x	x	x	x
mm	43	51	61	78
500 μA	£3.62	£3.69	£3.87	£4.22
500 μA	£3.31	£3.36	£3.63	£3.86
1mA	£3.21	£3.28	£3.53	£3.82
15vDC	£3.25	£3.32	£3.60	£3.86
300vAC	£3.49	£3.55	£3.77	£4.02



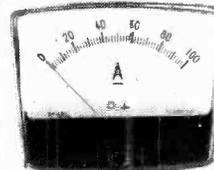FOR YOUR PRODUCTION REQUIREMENTS USE ALPS PANEL METERS FULL RANGE PRICE LIST—SAY PLEASE! Substantial quantity discounts to manufacturers! Remember! We are the sole importers!



TYPE SR

Dim's	73	78	92
in	x	x	x
mm	56	63	72
500 μA	£4.03	£4.28	£4.52
500 μA	£3.68	£3.93	£4.18
1mA	£3.58	£3.83	£4.08
15vDC	£3.70	£3.94	£4.19
300vAC	£3.83	£3.97	£4.32

LABORATORY TYPE SA65E

Metric size 82 x 78mm


50 μA	£6.69
500 μA	£6.44
1mA	£6.24
1A	£5.34
15vDC	£5.34
30vDC	£5.34



ALL ABOVE PRICES INCLUDE P. & P. and VAT

NEW ADDITIONS to our range of PANEL METERS available at present only in MANUFACTURING QUANTITIES

SE45	64	×	52	mm
SE52	80	×	60	mm
SE65	100	×	80	mm
SE85	120	×	100	mm

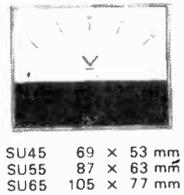

Above meter forms are for moving coil movements only and may house S-meter and VU-meter instruments.

VU METERS

SF100	72	×	68	mm
SF104	63	×	60	mm
SF106	63	×	60	mm



With A or B Scales. Linear Movements or to B.S.T.J. spec. Also available in most standard cases. All meters can be supplied with special or personalised scales, internal illumination, coloured front lenses, mirror scales, special pointer forms, etc.

Full details and prices on request

AUTOMOBILE TEST EQUIPMENT

SERVO AUTOTESTER No. 1. 0.32 & 0.16v. 0.80 A-DC & 0.20K Ohms. dwell angle and speed for 4 b & b cyc engines and E.H.T. SEC. VOLTS. A substitute capacitor is incorporated. Size 26.5 x 14 x 16.5cm. wt 3.25kg. With handbook £30.37 inc. P & P & V A T

SERVO AUTOTESTER No. 2. 0-16v. 0.80A dwell angle and speed for 4, 6 & B cyc engines. Size 16 x 9.5 x 6.5 cm. Wt 0.45Kg. With instrns £11.15 inc. P & P & V A T

SERVO AUTOTESTER No. 3. Simultaneously on separate meters 0-16v & 0.80A. Size 17 x 10 x 7 cm. Wt 0.45kg. Price £9.78 inc. P & P & V A T

SERVO AUTOTESTER No. 4. Dwell angle and engine speed. Hand held instr. Size 14 x 8 x 5 cm. Wt 0.26kg. Price £6.35 inc. P & P & V A T


BENTLEY ACOUSTIC CORPORATION LTD.

7A GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX. Tel. 6743

ALL PRICES SHOWN INCLUDE V.A.T.

0B2	0.45	6BC8	0.90	6L12	0.47	12BA6	0.53	30P4	0.88	AZ31	0.80	EC53	1.00		
0Z4	0.53	6B8A	0.88	6L18	0.48	12BE6	0.59	30P6	0.43	AZ41	0.50	EC54	1.00		
1A3	0.65	6BG6G	1.23	6L19	2.00	12BH7	0.59	30P8	0.50	B1B3	2.34	EC66	0.90		
1ASGT	0.59	6BH6	0.75	6LD12	0.45	12BY7	0.85	30P11	1.00	CL33	1.85	EC88	0.90		
1B7GT	0.60	6B16	0.64	6LD20	0.88	12E1	3.51	30P12	0.45	CV6	0.62	EC92	0.55		
1B3GT	0.59	6BK7A	0.85	6N7GT	0.70	12J5GT	0.39	30P13	1.20	CV63	1.00	EC93	1.00		
1C2	1.15	6K05	0.36	6K12	0.70	12J7GT	0.70	30P14	1.28	CV988	0.29	EC93	2.00		
1G6	1.17	6BQ7A	0.64	6P15	0.36	12K5	1.17	30P15	0.90	CY1C	1.00	EC93	2.00		
1H5GT	0.90	6BR7	1.20	6Q7G	0.50	12K7GT	0.50	35A3	0.76	CY31	0.70	EC93	2.00		
1L4	0.25	6BR8	1.25	6Q7G1	0.60	12K8	0.85	35C5	0.85	D1	0.50	EC93	2.00		
1LD5	0.70	6B8T	1.64	6Q7(M)	0.64	12Q7GT	0.50	35D5	0.90	D63	0.30	EC93	2.00		
1LN5	0.70	6RW6	1.00	6R7G	0.70	12SA7GT		35L6GT	0.88	DAC32	0.80	EC93	2.00		
1NSGT	0.76	6BW7	0.65	6RT(M)	0.88			35W4	0.60	DAF91	0.40	EC93	2.00		
1U5	0.50	6BX6	0.30	6SA7	0.55	12S7	0.70	35Z3	0.88	DAP90	0.60	EC93	2.00		
1S4	0.39	6BY7	0.48	6SC7GT	0.50	12S7G7	0.55	35Z4GT	0.82	DC90	0.70	EC93	2.00		
1T5	0.40	6BZ6	0.57	6SG7	0.52	12SH7	0.50	35Z5GT	0.80	D04	0.80	EC93	2.00		
1U4	0.30	6C4	0.47	6SH7	0.55	12S17	0.60	42	1.00	DF33	0.76	EC93	2.00		
1U5	0.70	6C5G	0.59	6S17	0.64	12SK7	0.64	50C5	1.00	DF91	0.30	EC93	2.00		
1LN5	0.70	6RW6	1.00	6R7G	0.70	12S7GT		50C5	0.70	DF96	0.65	EC93	2.00		
2D21	0.60	6C9	2.00	6SQ7GT	0.30			50C6DG	1.46	DH63	0.50	EC93	2.00		
2GK5	0.75	6C10	0.80	6U4GT	0.82	12SQ7	0.76	50E15	0.88	DH76	0.50	EC93	2.00		
2X2	0.70	6C8BA	0.64	6V7G	0.55	12SQ7GT		50L9GT		DH77	0.53	EC93	2.00		
3A4	0.60	6C12	0.40	6V8G	0.30			50M7	0.70	DH81	0.88	EC93	2.00		
3B7	0.53	6C17	2.34	6V8GT	0.53	12SR7	0.76	77	0.70	DK32	0.66	EC93	2.00		
3D6	0.47	6CD6G	1.60	6X4	0.47	14H7	0.64	85A2	0.75	DK40	0.82	EC93	2.00		
3Q4	0.85	6C8A	0.88	6X5GT	0.50	14S7	1.10	85A3	0.70	DK91	0.50	EC93	2.00		
3Q5GT	0.70	6C16	0.76	6Y7	0.94	18	1.17	90AG	2.93	DK92	1.15	EC93	2.00		
3S4	0.47	6CL8A	0.84	6Y7G	1.17	18A05	0.65	90CG	2.81	DK96	0.70	EC93	2.00		
3V4	0.82	6CM7	0.88	7A7	1.00	18B6G	1.17	90CV	2.81	DL92	0.47	EC93	2.00		
4CB6	0.75	6C15	0.88	7B6	0.88	19G6	7.00	90C1	0.88	DL94	0.82	EC93	2.00		
5C8G	0.75	6CW4	1.17	7B7	0.82	19H1	4.00	150B2	1.00	DL96	0.64	EC93	2.00		
5R4G	0.94	6D3	0.75	706	2.00	20D1	0.80	2155G	0.59	DM70	0.80	EC93	2.00		
5T4	0.47	6DE7	0.88	718	1.76	20D4	2.34	301	1.17	DM71	1.76	EC93	2.00		
5U4G	0.59	6DT8A	0.88	7H7	0.88	20F2	0.88	302	1.17	DX96	0.70	EC93	2.00		
5V4G	0.59	6E16	0.88	7R7	2.00	20Y1	1.29	303	1.17	DW4/350	1.17	EC93	2.00		
5Y3GT	0.55	6E5	1.17	7V7	1.76	20P1	1.00	305	1.17	DY87	0.41	EC93	2.00		
5Z3	0.88	6F1	0.80	7Y4	0.80	20P3	0.94	807	1.17	EF40	0.88	EC93	2.00		
5Z4G	0.55	6F6G	0.60	7Z4	1.00	20P4	1.17	956	0.60	E80C2	2.57	EC93	2.00		
5Z4GT	0.55	6F12	0.50	98W6	0.88	20P5	1.50	1821	1.17	E80F	2.20	EC93	2.00		
6.30L2	0.80	6F13	0.90	9D7	0.70	25A6G	0.70	4033X	7.61	E83F	1.60	EC93	2.00		
6A9G	1.46	6F14	0.88	10C2	0.76	25L9G	0.70	5702	1.20	E88C	1.20	EC93	2.00		
6AC7	0.60	6F15	0.76	10D1	0.42	25Y5	0.80	5783	1.76	E92C	0.70	EC93	2.00		
6AG5	0.35	6F18	0.64	10DE7	0.88	25Y5G	0.60	6057	1.00	E180C	0.82	EC93	2.00		
6AH6	0.80	6F23	0.80	10F1	0.88	25Z4G	0.50	6060	1.00	E180F	1.17	EC93	2.00		
6AJ5	0.76	6F24	1.00	10F3	1.17	25Z5	0.75	6067	1.00	E182C	3.00	EC93	2.00		
6AK8	0.40	6F25	1.17	10F9	0.76	25Z6G	0.80	7193	0.62	E290F	0.50	EC93	2.00		
6AK5	0.47	6F26	0.80	10F18	0.80	28D7	2.00	7475	1.17	E148	0.62	EC93	2.00		
6AK8	0.70	6F28	0.78	10L14	0.53	30C1	0.47	9002	0.59	EAS0	0.40	EC93	2.00		
6AK8	0.45	6F32	0.70	10L11	0.82	30C11	0.47	9006	0.50	EAT6	1.40	EC93	2.00		
6AL5	0.23	6G6G	0.60	10P12	0.45	30C15	0.80	A1834	1.17	EAB00	0.45	EC93	2.00		
6AM8A	0.70	6G8BA	0.88	10P13	0.88	30C17	0.85	A2134	3.00	EAC91	0.65	EC93	2.00		
6AN8	0.82	6GK5	0.76	10P14	2.34	30C18	0.85	A3042	6.00	EAF42	0.88	EC93	2.00		
6AQ5	0.53	6G17	0.88	10P18	0.49	30F5	0.75	AC2PEN17		EAF801	0.80	EC93	2.00		
6AQ6	0.47	6H6GT	0.29	12A6	0.75	30F11	1.10	AC2PEN2D		EB34	0.35	EC93	2.00		
6AR5	0.80	6H9GT	0.53	12AC6	0.90	30F12	1.10	1.00		EB91	0.23	EC93	2.00		
6AR6	1.17	6J6	0.35	12A6E	0.90	30F12	1.05	AC6/PEN		EB41	0.88	EC93	2.00		
6B5A	1.17	6J7G	0.35	12A6E	0.90	30F13	0.64	AC/PEN(7)		EB41	0.45	EC93	2.00		
6AT6	0.53	6J7(M)	0.85	12A76	0.47	30L14	0.82	AC/PEN(7)		EB30	0.53	EC93	2.00		
6AV6	0.40	6J8A	0.88	12A77	0.40	30L14	0.40	1.17		EB91	0.53	EC93	2.00		
6AV8	0.53	6K7G	0.35	12A78	0.53	30L15	0.82	AC/ATH1		EBF80	0.40	EC93	2.00		
6AW8A	0.90	6K8G	0.53	12A79	0.39	30L17	0.76	AL80	1.17	EBF83	0.50	EC93	2.00		
6AX4	0.88	6L1	2.34	12AV6	0.59	30P12	0.80	ARP3	0.60	EBF89	0.40	EC93	2.00		
6B8G	0.35	6L6CG	0.68	12AX7	0.30	30P12	0.80	ATP4	0.50	EBL21	2.34	EC93	2.00		
6BA6	0.41	6L7(M)	0.59	12Y7	0.94	30P19		AZ1	0.50	EC52	1.00	EC93	2.00		
EL84	0.36	PC95	0.70	PY88	0.47	U18/20	1.17	2N404	0.23	AF186	0.71	GD11	0.26	OC45	0.14
EL86	0.60	PC97	0.42	PY901	0.59	U19	4.00	2N2966	0.68	AF239	0.49	GD12	0.26	OC46	0.20
EL90	0.53	PC98	0.30	PY902	1.11	U25	0.70	2N1757	0.64	ASV27	0.55	GD14	0.64	OC47	1.45
EL93	0.60	PC98A	0.47	PY900A	1.11	U29	0.70	2N147	0.20	ASV28	0.42	GD15	0.26	OC70	0.16
EL96	1.20	PC985	0.50	PY800	0.45	U26	0.55	2N2297	0.29	ASV29	0.64	GP16	0.26	OC71	0.14
EL98	0.50	PC988	0.65	PY801	0.45	U31	0.50	2N2369A	0.18	BA102	0.59	GET113	0.26	OC72	0.14
EM80	0.53	PC989	0.50	PZ30	0.50	U33	1.75	2N2613	0.50	BA115	0.18	GET118	0.26	OC74	0.29
EM81	0.76	PC989	0.60	QZP21	1.10	U35	1.75	2N3053	0.42	BA116	0.23	GET119	0.33	OC75	0.14
EM83	0.84	PC985	0.82	QV03	1.10	U37	2.95	2N3121	3.22	BA129	0.16	GET173	0.49	OC76	0.20
EM84	0.47	PC980	0.76	QV06/20	3.50	U45	1.17	2N3703	0.25	BA135	0.13	GET187	0.55	OC77	0.16
EM85	0.60	PC980	0.47	QV75/20	1.00	U47	0.70	2N3709	0.20	BA138	0.20	GET187	0.29	OC78	0.20
EM86	1.10	PCF82	0.50	QV85/10	1.00	U49	0.65	2N3866	1.29	BCY10	0.59	GET183	0.20	OC78L2	0.20
EM87	0.50	PCF84	0.70	QV150/15	1.00	U50	0.55	2N3888	0.64	BCY12	0.64	GET182	0.64	OC79	0.52
EM88	0.55	PCF86	0.50			U51	1.90	25323	0.64	BCY33	0.26	GET187	0.29	OC81	0.14
EM89	0.76	PCF87	0.90	OV03/12	1.76	U78	0.47	AA119	0.20	BCY34	0.29	GET188	0.29	OC81D	0.14
EM90	0.84	PCF200	1.00	U37	2.95	U81	0.80	AA120	0.20	BCY38	0.29	GET189	0.29	OC82	0.14
EM91	0.47	PCF201	1.05	U45	1.17	U81	1.17	AA129	0.20	BCY39	0.33	GET186	0.29	OC82D	0.14
EM92	1.10	PCF80	0.82	U81	0.80	U81	0.80	AA213	0.23	BC107	0.16	GET187	0.29	OC83	0.26
EM93	0.50	PCF80	0.65	R16	2.05	U82	0.40	AC107	0.20	BC108	0.16	GET188	0.29	OC84	0.31
EM94	0.39	PCF80	0.85	R17	1.00	U83	0.47	AC113	0.33	BC109	0.16	GET189	0.29	OC85	0.26
EM95	0.55	PCF80	0.85	R18	0.92	U84	0.47	AC114	0.52	BC113	0.33	GET189	0.29	OC86	0.26
EM96	0.55	PCF80	0.85	R19	0.75	U85	0.47	AC126	0.16	BC115	0.20	GET189	0.29	OC87	0.26
EM97	0.55	PCF80	0.85	R20	0.65	U86	0.47	AC127	0.33	BC117	0.33	GET189	0.29	OC88	0.26
EM98	0.55	PCF80	0.85	R21	0.65	U87	0.47	AC128	0.26	BC118	0.33	GET189	0.29	OC89	0.26
EM99	0.55	PCF80	0.85	R22	0.65	U88	0.47	AC129	0.26	BC119	0.33	GET189	0.29	OC90	0.26
EM100	0.55	PCF80	0.85	R23	0.65	U89	0.47	AC130	0.26	BC120	0.33	GET189	0.29	OC91	0.26
EM101	0.55	PCF80	0.85	R24	0.65	U90	0.47	AC131	0.26	BC121	0.33	GET189	0.29	OC92	0.26
EM102	0.55	PCF80	0.85												

For just £1* the world is yours!

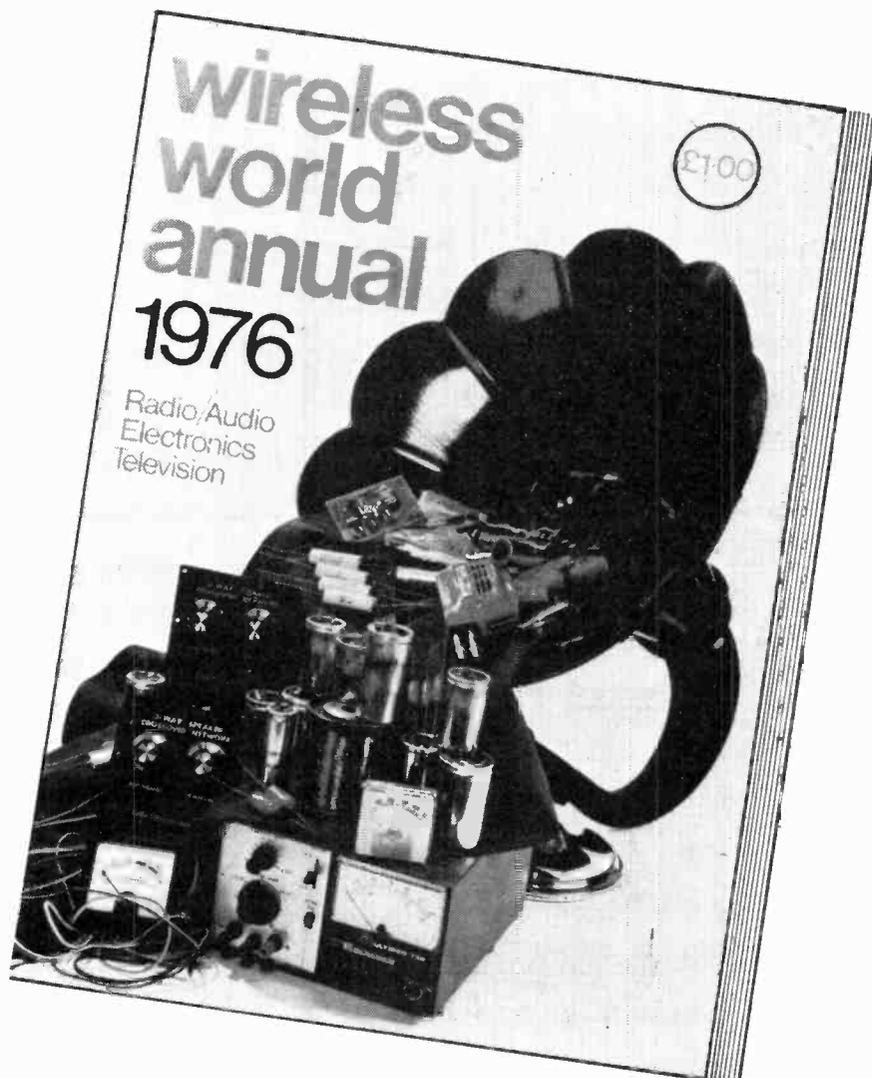

The world of electronics, television, radio/audio is on parade in the second great Wireless World annual. Constructional articles include making a photographic timer. Surveys cover video, magnetic tape compatibility, electronic ignition and radio astronomy in schools. 'How to ...' features range from using oscilloscopes to making printed circuit boards. And there's a reference section listing standard frequency transmissions and much, much more. All written with the clarity, authority and expertise you'd expect from Wireless World.

***£1 from newsagents or £1.35 inclusive by post from the publishers.**

Order Coupon
To General Sales Dept., Room 11, Dorset House, Stamford St.,
London SE1 9LU.
Please send me copy/copies of Wireless World Annual 1976 at
£1.35 inclusive.
I enclose remittance value £ (Cheques payable to IPC Business
Press Ltd).

Name (please print)

Address

Company regd. in England No. 677128
Regd. office: Dorset House, Stamford St.,
London SE1 9LU.

BI-PAK SEMICONDUCTORS

COMPONENTS

CARBON RESISTOR PAKS
These Paks contain a range of Carbon Resistors, assorted into the following groups:—

R1	50	Mixed	100 ohms	—
			820 ohms 1/8th W.	0.60
R2	50	Mixed	1K ohms	—
			82Kohms 1/8th W.	0.60
R3	50	Mixed	10K ohms	—
			82Kohms 1/8th W.	0.60
R4	50	Mixed	100K ohms	—
			820Kohms 1/8th W.	0.60
R5	30	Mixed	100 ohms	—
			820 ohms 1/2 W.	0.60
R6	30	Mixed	1K ohms	—
			8.2Kohms 1/2 W.	0.60
R7	30	Mixed	10K ohms	—
			82Kohms 1/2 W.	0.60
R8	30	Mixed	100K ohms	—
			820Kohms 1/2 W.	0.60

These are unbeatable prices.

LOW COST CAPACITORS

500 µF	50V Elect	0.09 each
100 µF	400 V	0.83 each

REPANCO CHOKES & COILS

RF Chokes	CH1 2.5mH	0.27
	CH3 7.5mH	0.29
	CH5 1.5mH	0.26
	CH2 5.0mH	0.28
	CH4 10mH	0.31
COILS	DRXT Crystl set	0.29
	DRR2 Dual range	0.42

CARBON POTENTIOMETERS

Log and Lin	4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M.
VC 1	Single Less Switch 0.14
VC 2	Single D.P. Switch 0.26
VC 3	Tandem Less Switch 0.43
VC 4	1K Lin Less Switch 0.14
VC 5	100K Log anti-Log 0.43

HORIZONTAL CARBON PRESETS

0.1 Watt	0.06 each
100, 220, 470, 1K, 2.2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4.7M.	

REPANCO TRANSFORMERS

240V. Primary. Secondary voltages available from selected tappings 4V, 7V, 8V, 10V, 40V, 50V and 25V-0.25V.

Type	Amps	Price	P&P
MT50/1/2	1/2	£1.79	0.45p
MT50/1	1	£2.24	0.48p
MT50/2	2	£3.06	0.80p

COIL FORMERS & CORES

NORMAN 1/4" Cores & Formers	0.07p
3/4" Cores & Formers	0.09p

SWITCHES

DP/DT Toggle	0.28p
SP/ST Toggle	0.22p

FUSES

1 1/4" and 20mm, 100mA, 200mA, 250mA, 500mA, 1A, 1.5A, 2A QUICK BLOW	*0.5p each
Anti-surge 20mm only	*0.8p each

VEROBORDS

VB 1 containing approx. 50 sq. ins. various sizes all 0.1 matrix	*0.60p
VB 2 containing approx. 50 sq. ins. various sizes all 0.15 matrix	*0.60p

DECON-DALO 33PC Marker *

Etch resistant printed circuit marker pen. Full instructions supplied with each pen *0.92p

BATTERY HOLDERS *

Takes 6 H.P. 7s complete with terminal clip and lead *0.31p each

CABLES *

CP #	Description	Per Metre
CP 1	Single lapped screen	*0.08
CP 2	Twin Common Screen	*0.11
CP 3	Stereo Screened	*0.12
CP 4	Four Core Common Screen	*0.21
CP 5	Four Core individually screened	*0.28
CP 6	Microphone Fully Braided Cable	*0.11
CP 7	Three Core Mains Cable	*0.11
CP 8	Twin Oval Mains Cable	*0.08
CP 9	Speaker Cable	*0.06
CP 10	Low Loss Co-Axial	*0.14

SEE OUR COMPLETE RANGE IN

PRACTICAL ELECTRONICS, PRACTICAL WIRELESS, RADIO CONSTRUCTOR, EVERYDAY ELECTRONICS, WIRELESS WORLD

OR SEND 5p FOR THE FULL LIST OF ALL BI-PAK PRODUCTS

INSTRUMENT CASES



(In 2 sections, Black Vinyl covered top and sides and bezel)

No.	Length	Width	Height	Price
BV1	8" x	5 1/4" x	2"	*£1.25
BV2	11" x	6" x	3"	*£1.62
BV3	6" x	4 3/4" x	1 1/2"	*0.92
BV4	9" x	5 1/4" x	2 1/2"	*£1.39

ALUMINIUM BOXES

No.	Length	Width	Height	Price
BA1	5 1/2" x	2 1/4" x	1 1/2"	*0.45
BA2	4" x	4" x	1 1/2"	*0.45
BA3	4" x	2 1/4" x	1 1/2"	*0.45
BA4	5 1/4" x	4" x	1 1/2"	*0.54
BA5	4" x	2 1/2" x	2"	*0.45
BA6	3" x	2" x	1"	*0.39
BA7	7" x	5" x	2 1/2"	*0.79
BA8	8" x	6" x	3"	*£1.02
BA9	6" x	4" x	2"	*0.65

(Each complete with 1/2" deep lids & screws)

PLEASE ADD 20p POSTAGE AND PACKING FOR EACH BOX

COMPONENT PAKS

Pak No.	Description	Price
C1	200 Resistors mixed values approx. count by weight	.60
C2	150 Capacitors mixed values approx. count by weight	.60
C3	50 Precision Resistors mixed values	.60
C4	75 1/8th width Resistors mixed preferred values	.60
C5	5 Pieces assorted Ferrite Rods	.60
C6	2 Tuning Gangs. MW/LW VHF	.60
C7	1 Pak Wire 50 metres assorted colours	.60
C8	10 Reed Switches	.60
C9	3 Micro Switches	.60
C10	15 Assorted Pots & Pre-Sets	.60
C11	5 Jack Sockets 3 x 3.5m, 2 x standard Switch Type	.60
C12	30 Paper Condensers preferred types mixed values	.60
C13	20 Electrolytics Trans. types	.60
C14	1 Pack assorted Hardware - Nuts/Bolts, Grommets, etc.	.60
C15	5 Mains Slide Switches, 2 Amp	.60
C16	20 Assorted Tag Strips & Panels	.60
C17	10 Assorted Control Knobs	.60
C18	4 Rotary Wave Change Switches	.60
	2 Relays 6-24V Operating Sheets Copper Laminate. approx. 200 sq. ins.	.60

Please add 20p post and packing on all component packs, plus a further 10p on pack nos. C1, C2, C19 & C20.

AVDEL BOND

SOLVE THOSE STICKY PROBLEMS! with 

CYANOACRYLATE C2 ADHESIVE

The wonder bond which works in seconds bond plastic rubber transistors components permanently immediately!

OUR PRICE ONLY 60p

for 2gm phial

BIB HI-FI ACCESSORIES

REF	Description	PRICE
B	Stylus and turntable cleaning kit	
J	Tape head cleaning kit	*31p
P	Hi-Fi cleaner	*30p
9	Wire stripper/Cutter	*94p
31	Cassette head cleaner	*58p
32	Tape editing kit	*£1.64
32A	Stylus balance	*£1.24
36A	Record stylus cleaning kit	*32p
42	De Luxe Groov-Kleem	*£1.84
43	Record care kit	*£2.68
45	Auto changer groove cleaner	*98p
46	Spirit level	*68p
56	Hi-Fi stereo hints & tips	*38p
60	Chrome finish as above	*£1.72

ANTEX EQUIPMENT

SOLDERING IRONS

x25. 25 watt	*£2.45
Model G. 18 watt	*£2.70
CCN 240. 15 watt	*£2.90
SK2. Soldering Kit	*£3.90

BITS AND ELEMENTS *

Bit No.	Price
102 for model CN240	3/32" *42p
104 for model CN240	3/16" *42p
1100 for model CCN240	3/32" *42p
1101 for model CCN240	3/8" *42p
1102 for model CCN240	1/4" *42p
1020 for model G240	3/32" *42p
1021 for model G240	1/8" *42p
1022 for model X25	3/16" *42p
50 for model X25	3/32" *44p
51 for model X25	1/8" *44p
52 for model X25	3/16" *44p

ELEMENTS *

Model ECN 240	£1.10*
Model EG 240	£1.35*
Model ECN 240	£1.55*
Model EX 25	£1.20*

SOLDERING IRON STAND

ST3 Suitable for all models	*£1.10
Antex heat shunt	*10p

PLUGS

PSI	Description	PRICE
PS 1	D.I.N. 2 Pin (Speaker)	0.10
PS 2	D.I.N. 3 Pin	0.11
PS 3	D.I.N. 4 Pin	0.14
PS 4	D.I.N. 5 Pin 180°	0.15
PS 5	D.I.N. 5 Pin 240°	0.15
PS 6	D.I.N. 6 Pin	0.16
PS 7	D.I.N. 7 Pin	0.17
PS 8	Jack 2.5mm Screened	0.17
PS 9	Jack 3.5mm Plastic	0.11
PS 10	Jack 3.5mm Screened	0.17
PS 11	Jack 1/2" Plastic	0.14
PS 12	Jack 1/2" Screened	0.20
PS 13	Jack Stereo Screened	0.33
PS 14	Phono	0.09
PS 15	Car Aerial	0.14
PS 16	Co-Axial	0.14

INLINE SOCKETS

PS	Description	PRICE
PS 21	D.I.N. 2 Pin (Speaker)	0.13
PS 22	D.I.N. 3 Pin	0.19
PS 23	D.I.N. 5 Pin 180°	0.19
PS 24	D.I.N. 5 Pin 240°	0.19
PS 25	Jack 2.5mm Plastic	0.15
PS 26	Jack 3.5mm Plastic	0.15
PS 27	Jack 1/2" Plastic	0.28
PS 28	Jack 1/2" Screened	0.32
PS 29	Jack Stereo Plastic	0.28
PS 30	Jack Stereo Screened	0.35
PS 31	Phono Screened	0.17
PS 32	Car Aerial	0.20
PS 33	Co-Axial	0.20

SOCKETS

PS	Description	PRICE
PS 35	D.I.N. 2 Pin (Speaker)	0.07
PS 36	D.I.N. 3 Pin	0.09
PS 37	D.I.N. 5 Pin 180°	0.09
PS 38	D.I.N. 5 Pin 240°	0.10
PS 39	Jack 2.5mm Switched	0.11
PS 40	Jack 3.5mm Switched	0.11
PS 41	Jack 1/2" Switched	0.19
PS 42	Jack Stereo Switched	0.18
PS 43	Phono Single	0.07
PS 44	Phono Double	0.09
PS 46	Co-Axial Surface	0.09
PS 47	Co-Axial Flush	0.19

P.C.B. KITS & PENS

PROFESSIONAL D.I.Y. PRINTED CIRCUIT KIT

Containing 6 sheets of 6" x 4" single sided laminate, a generous supply of etchant powder, etching dish, etchant measure, tweezers, etch resistant marking pen, high quality pump drill with spares, cutting knife with spare blades, 6" metal ruler, plus full easy to follow instructions.

*£7.80 per kit

Spare container of etchant for above, complete with instructions *£60p

P.C.B. MARKING PENS

2 x quality market pens, specifically designed for drawing fine etchant resistant circuits on copper laminate. Complete with full instructions *£1.53 per pair

LOW-NOISE CASSETTES

C60	*33p
C90	*44p
C120	*56p

SLIDER PAK

Containing a range of slider pots.

SP1 6 mixed values sliders	0.60
SP2 6 470K Lin. sliders	0.60
SP3 6 10K Lin. sliders	0.60
SP4 6 22K Lin. sliders	0.60
SP5 6 47K Lin. sliders	0.60
SP6 6 47K log. sliders	0.60

AUDIO LEADS

S221	5 pin DIN plug to 4 phono plugs length 1.5m	£1.08
S222	5 pin DIN plug to 5 pin DIN socket length 1.5m	.68p
S237	5 pin DIN plug to 5 pin DIN plug, mirror image length 1.5m	£1.20
S238	2 pin DIN plug to 2 pin DIN socket length 5m	.68p
S268	5 pin DIN plug to 3 pin DIN plug 1 & 4 and 3 & 5 length 1.5m	£1.00
S270	2 pin DIN plug to 2 pin DIN socket length 10m	.80p
S271	5 pin DIN plug to 2 phone plugs connected to pins 3 & 5 length 1.5m	.70p
S275	5 pin DIN plug to 2 phono sockets connected to pins 3 & 5 length 23cm	.68p
S318	5 pin DIN socket to 2 phono plugs connected to pin 3 & 5 length 23cm	.68p
S404	Coiled stereo headphones extension cord extends to 7m	£1.40
S217	3 pin DIN plug to 3 pin DIN plug length 1.5m	.80p
S219	5 pin DIN plug to 5 pin DIN plug length 1.5m	.80p
S474	3.5mm Jack to 3.5mm Jack length 1.5m	.68p
S600	5 pin DIN plug to 3.5mm Jack connected to pins 3 & 5 length 1.5m	.80p
S700	5 pin DIN plug to 3.5 Jack connected to pins 1 & 4 length 1.5m	.80p

CROSSOVER NETWORK

K4007 1/P Impedance 8 ohms. (2-way) Insertion Loss 3dB. Crossover Frequency 3 KHz. PRICE £1.12

3-WAY-STEREO H/PHONE JUNCT BOX

H 1012 Enables change-over from loudspeaker to headphone listening. Also has a centre position for both outputs. PRICE £1.73

HANDBOOKS

TRANSISTOR DATA BOOK, DTE 2
227 Pages packed with information on European Transistors. Full specification including outlines. Price *£2.95 each

TRANSISTOR EQUIVALENT BOOK
BPE 75 256 Pages of cross references and equivalents for European, American and Japanese Transistors. This is the most comprehensive equivalents book on the market today and has an introduction in 13 languages. Price *£2.68 each

DIODE EQUIVALENT BOOK DE 74
144 Pages of cross references and equivalents for European, American and Japanese Diodes, Zeners, Thyristors, Triacs, Diacs and L.E.D.'s. Price *£1.98 each

MULLARD DATA BOOK 1974/75 MDB 74
The latest edition of this popular handbook contains information on Semiconductors, Integrated Circuits, Television Picture Tubes, Valves, Capacitors and Resistors. Included in the 161 informative pages are 21 pages on Semiconductor Comparables. Price *£0.40 each

TTL DATA BOOK DIC 75
Now complete Data book of 74 series TTL (7400-74132). Covering 13 main manufacturers in the U.S.A. and Europe, this book gives full data as well as equivalents. Price *£3.74

THE WORLD'S BROADCAST

VISIT OUR COMPONENT SHOP
 18 BALDOCK STREET, WARE, Herts (A10)
 Open Mon.-Sat. 9-5.30 p.m. Tel. 61593


PO BOX 6 WARE HERTS

AL 60

ONLY £3.95

50w. PEAK (25w. R.M.S.)

- Max Heat Sink temp 90°C ● Frequency Response 20Hz to 100K Hz ● Distortion better than 0.1 at 1KHz
- Supply voltage 15-50 volts ● Thermal Feedback ● Latest Design Improvements ● Load — 3, 4, 5 or 16 ohms ● Signal to noise ratio 80dB ● Overall size 63mm x 105mm x 13mm. Especially designed to a strict specification. Only the finest components have been used and the latest solid state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

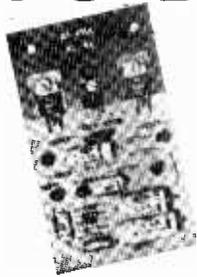


STABILISED POWER MODULE SPM80

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm x 105mm x 30mm.

These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Disco Systems. Public Address Intercom Units, etc. Handbook available 10p.

TRANSFORMER BMT80 £2.60

PRICE £3.00

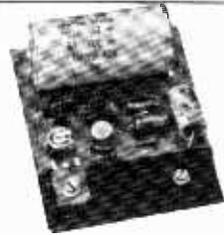


STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages.

Three switched stereo inputs, and rumble and scratch filters are features of the PA100 which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

£13.20

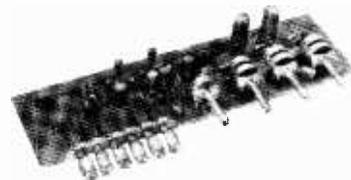

GUARANTEE SATISFACTION OR YOUR MONEY REFUNDED

MK 60 AUDIO KIT

Comprising: 2 x AL60, 1 x SPM80, 1 x BTM80, 1 x PA100, 1 front panel, 1 kit of parts to include on-off switch, neon indicator, stereo headphone sockets plus instruction booklets.

COMPLETE PRICE: £27.55 plus 45p postage.

TEAK 60 AUDIO KIT

Comprising: Teak veneered cabinet size 16 3/4" x 11 1/4" x 3 3/4", other parts include aluminium chassis, heatsink and overwind, will produce a high quality audio unit suitable for use with a wide range of inputs, i.e. high quality ceramic pickup, stereo tuner, stereo tape deck, etc.

KIT PRICE: £9.20 plus 45p postage.

STEREO 30 COMPLETE AUDIO CHASSIS

7 + 7 WATTS R.M.S.


The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This with only the addition of a transformer or overwind, will produce a high quality audio unit suitable for use with a wide range of inputs, i.e. high quality ceramic pickup, stereo tuner, stereo tape deck, etc.

Simple to install, capable of producing feally first-class results, this unit is supplied with full instructions, black front panel, knobs, mains switch, fuse & fuse holder and universal mounting bracket, enabling it to be installed in a record plinth, cabinets of your own construction or the cabinet available.

Ideal for the beginner or advanced constructor who requires Hi-Fi performance with a minimum of installation difficulty. Can be installed in 30 mins.

PRICE £15.75 Plus 45p postage & packing

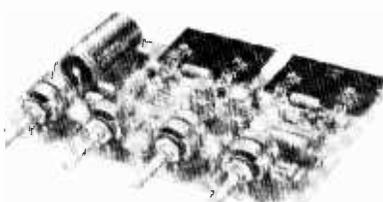TRANSFORMER £2.45 plus 45p postage & packing **TEAK CASE £3.65** plus 45p postage & packing



PLEASE ADD V.A.T. AT 25% TO ALL ITEMS EXCEPT * ADD 8% # NO V.A.T.


GIRO NUMBER 388-7006

AL 10/AL 20/AL 30

The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S.

The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home.

AL10 £2.30, AL20 £2.65, AL30 £2.95

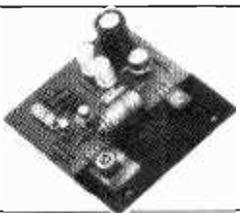

SPEAKERS

E.M.I. LEK 350 Loudspeakers Enclosure kit in teak veneer, including speakers. Rec. retail price £4.50 per pair.

OUR SPECIAL PRICE ONLY £27.75 per pair P&P £3 WHILE STOCKS LAST!

HEADPHONES

4-16 ohms impedance frequency response 20 to 20,000 Hz stereo/mono switch and Volume Control £4.55

FRONT PANEL

FOR PA100. Attractive matt silver. Finish with black trim and lettering. Adds that professional touch. £1.10 only.

M.P.A.30

Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the new Bi-Pak M.P.A.30 which is a high-quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only.

Used in the construction are 4 low noise, high gain, silicon transistors. It is provided with a standard DIN input socket for ease of connection.

Supplied with full, easy-to-follow instructions.

PRICE £2.65

STORAGE-CARRY CASES

- RECORD CASES**
 7 in E.P. 18 3/8th in. x 7 in x 8 in (50 records) *£2.48
 12 in L.P. 13 3/8 in x 7 3/8 in x 12 1/2 in (50 records) *£3.30
- CASSETTE CASES**
 Holds 15. 10 in x 3 3/4 in x 5 in. Lock and handle *£1.50
- 8-TRACK CARTRIDGE CASES**
 Holds 14. 13 in x 5 in x 6 in. Lock and handle *£2.20
 Holds 24. 13 3/8 in x 8 in x 5 3/8 in Lock and handle *£3.20

CARTRIDGES

- ACOS GP91-1SC 200mV at 1.2cms/sec £1.11
 GP93-1 280mV at 1cm/sec £1.43
 GP96-1 100mV at 1cm/sec £2.31
 TTC J-2005 Crystal/Hi Output £0.97
 J-2010C Crystal/Hi Output £1.11
 Compatible £1.52
 J-2006S Stereo/Hi Output £1.81
 J-2105 Ceramic/Med Output
 J-2203 Magnetic 5mV/5cm/sec including stylus £4.78
 J-2203S Replacement stylus for above £2.88
 AT-55 Audio-technica magnetic cartridge 4mV/5cm/sec £3.06

DYNAMIC MICROPHONE

TYPE B1223 200 ohms impedance. Complete with stand, on/off switch and 2.5mm and 3.5mm plugs. Suitable for cassette tape recorders. **PRICE £1.67.**

JUST OUT!

STEREO FM TUNER

WRITE NOW FOR FULL DETAILS

Collect Wireless World Circards. And build a valuable dossier on circuit design.


Circards is a unique and comprehensive system, launched by Wireless World, to provide professional engineers and enthusiasts with valuable and up-to-the-minute data on circuit design — data not available from any other single source.

Each Circard is 8" x 5" and usually shows a specific tested circuit, a description of the circuit operation; component values and ranges; circuit limitations and modifications; performance data and graphs.

The double-sided format enables the Circard to be filed in standard boxes for easy reference. And the plastic wallet provided keeps the cards well protected.

Circard sets (10 cards) come in wallets and cost £2.00. A subscription for 10 consecutive sets costs £18.

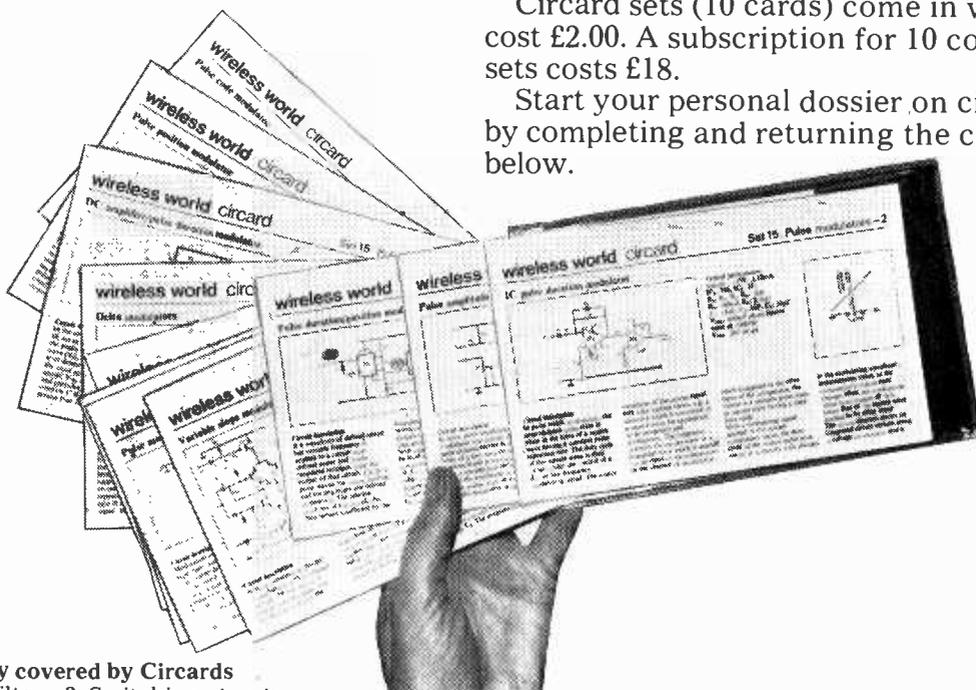Start your personal dossier on circuit design by completing and returning the coupon below.



Subjects already covered by Circards

1. Basic active filters. 2. Switching circuits comparators and schmitts.
3. Waveform generators. 4. AC measurements.
5. Audio circuits: preamplifiers, mixers, filters and tone controls.
6. Constant current circuits. 7. Power amplifiers.
8. Astables. 9. Opto-electronics.
10. Micropower circuits. 11. Basic logic gate circuits.
12. Wideband amplifiers. 13. Alarm circuits.
14. Digital counters. 15. Pulse modulators.
16. Current differencing amplifiers — signal processing.
17. Current differencing amplifiers — signal generation.
18. Current differencing amplifiers — measurement and detection.
19. Monostable circuits. 20. Transistor pairs.
21. Voltage to frequency converters.
22. Amplitude modulators. 23. Reference circuits.
24. Voltage regulators
25. RC oscillators — I. 26. RC oscillators — II.
27. Linear C.M.O.S.—I.
28. Linear C.M.O.S. II.

To: General Sales Dept., IPC Business Press Ltd., Room 11
Dorset House, Stamford Street, London SE1 9LU

Please send me set no(s) @ £2.00 each *

I wish to subscribe to set no(s) @ £18.00 *

I enclose cheque/money order for £

*Tick as required/Cheques to be made payable to IPC Business Press Ltd.

Name

Address

Company registered in England. Registered address, Dorset House
Stamford Street, SE1 9LU, England. Registered Number 677128

TTLs by TEXAS 7400 13p 7483 80p 7401 14p 7484 95p 7402 14p 7485 120p 7403 16p 7486 30p 7404 16p 7489 270p 7405 16p 7490 40p 7406 38p 7491 75p 7407 36p 7492 45p 7408 14p 7493 40p 7409 20p 7494 75p 7410 13p 7495 65p 7412 23p 7496 78p 7413 32p 74107 30p 7414 60p 74121 30p 7416 33p 74123 40p 7422 18p 74141 65p 7423 34p 74151 72p 7425 30p 74153 85p 7427 37p 74154 150p 7430 14p 74155 76p 7432 25p 74157 75p 7437 25p 74160 99p 7440 14p 74161 99p 7441 65p 74162 99p 7442 60p 74163 99p 7447 75p 74164 120p 7448 70p 74166 60p 7450 15p 74175 120p 7451 16p 74175 85p 7453 16p 74180 100p 7454 16p 74181 28p 7460 15p 74182 82p 7470 27p 74185 135p 7472 25p 74190 144p 7473 30p 74191 144p 7474 30p 74192 120p 7475 45p 74193 120p 7476 30p 74194 108p 7480 50p 74195 50p 7481 95p 74198 195p 7482 70p 74199 180p		C-MOS LOGIC I.C.s NEW LOW PRICES CD4000AE 19p CD4001AE 19p CD4002AE 19p CD4009AE 67p CD4011AE 19p CD4012AE 19p CD4013AE 55p CD4016AE 50p CD4020AE 19p CD4018AE 175p CD4020AE 250p CD4022AE 170p CD4023AE 19p CD4024AE 120p CD4025AE 19p CD4026AE 19p CD4027AE 75p CD4028AE 140p CD4029AE 175p CD4030AE 55p CD4042AE 137p CD4043AE 202p CD4046AE 140p CD4047AE 154p CD4049AE 83p CD4054AE 196p CD4055AE 196p CD4056AE 135p CD4060AE 229p CD4069AE 37p CD4071AE 27p CD4081AE 19p CD4082AE 27p CD4510AE 130p CD4511AE 200p CD4528AE 120p		OP. AMPS 1458 Dual Op Amp Int Comp 8 pin DIL 70p 301A Ext. Comp 8 pin DIL 35p 3130 COSMOS Bi-Polar MosFet 8 pin DIL 100p 3900 Quad. Op Amp 14 pin DIL 70p 336T FET Op Amp TO-99 275p 709 Ext. Comp 8/14 pin DIL 30p 741 Int. Comp 8/14 pin DIL 25p 747 Dual 741 14 pin DIL 70p 748 Ext. Comp 8 pin DIL 36p 776 Programmable Op. Amp TO-5 140p		TRANSISTORS AC126 12p AC127 12p AC128 11p AC141 18p AC142 18p AC176 11p AC187 13p AC188 12p AD149 42p AD161 36p AD162 36p AF114 18p AF115 18p AF116 18p AF117 18p AF139 33p AF239 33p BC107 9p BC108 9p BC109 10p BC109C 12p BC147 7p BC148 7p BC149C 8p BC157 11p BC158 10p BC159 11p BC169C 12p BC177 18p BC178 17p BC179 18p BC182 10p BC183 10p BC184 11p BC187 30p BC212 11p BC213 10p BC214 14p BC478 30p BCY70 18p BCY71 22p BD123 100p BD124 65p BD131 36p BD132 40p BD135 43p BD139 63p BD140 70p BF115 22p BF167 23p BF170 23p BF173 25p BF177 26p BF178 28p BF179 33p BF180 33p BF181 33p ZTX502 18p ZTX507 13p ZTX508 13p ZTX509 13p ZTX510 13p ZTX511 13p ZTX512 13p ZTX513 13p ZTX514 13p ZTX515 13p ZTX516 13p ZTX517 13p ZTX518 13p ZTX519 13p ZTX520 13p ZTX521 13p ZTX522 13p ZTX523 13p ZTX524 13p ZTX525 13p ZTX526 13p ZTX527 13p ZTX528 13p ZTX529 13p ZTX530 13p ZTX531 13p ZTX532 13p ZTX533 13p ZTX534 13p ZTX535 13p ZTX536 13p ZTX537 13p ZTX538 13p ZTX539 13p ZTX540 13p ZTX541 13p ZTX542 13p ZTX543 13p ZTX544 13p ZTX545 13p ZTX546 13p ZTX547 13p ZTX548 13p ZTX549 13p ZTX550 13p		LINEAR I.C.s CA3028 Diff. Cascade Amp TO5 90p CA3046 5 Transistor Array 14 pin DIL 50p CA3048 Quad. Low Noise Amp 16 pin DIL 200p CA3089E FM IF System 16 pin DIL 200p CA3090E FM Stereo Multi. Dec. 16 pin DIL 160p ICL8038CC VCO Fun. Gen. 14 pin DIL 275p LM380 2W Audio Amp 14 pin DIL 90p LM381 Stereo Preamp 14 pin DIL 160p M252 Thyristor Generator 16 pin DIL 900p MC1310P FM Stereo Dec. 14 pin DIL 175p MC1314 SQ Quad. Dec. 14 pin DIL 1100p MC1315 MFC4000B 1/4W Audio Amp PCB 70p MFC9040 Electronic Attenuator PCB 90p NE555 Timer 8 pin DIL 45p NE555 Dual 555 14 pin DIL 100p NE561 PLL with AM Demod. 16 pin DIL 325p NE562 PLL with VCO 16 pin DIL 325p NE563 PLL FM/IF Demod. 16 pin DIL 300p NE565 PLL 14 pin DIL 200p NE566 PLL Fun. Gen. 8 pin DIL 150p NE567 PLL Tone Dec. 8 pin DIL 150p 2567 Dual 567 14 pin DIL 370p SN72733 Video Amp 14 pin DIL 120p TBAR00 5W Audio Amp QIL 90p TBAR10 7W Audio Amp QIL 100p TBAR20 2W Audio Amp QIL 80p XR2240 Prog. Timer/Counter 16 pin DIL 370p ZN414 TRF Radio Receiver TO-18 110p		OTHER 100V 400V 500V 3 Amp 85p 120p 150p 40430 99p 6 Amp 88p 150p 180p 40486 99p 10 Amp 109p 180p 195p 40689 95p 15 Amp 145p 210p 250p BR100 Diac 21p		TRIACS 100V 400V 500V 3 Amp 85p 120p 150p 40430 99p 6 Amp 88p 150p 180p 40486 99p 10 Amp 109p 180p 195p 40689 95p 15 Amp 145p 210p 250p BR100 Diac 21p		SCR-THYRISTORS BT106 1A/700V Stud 140p C106D 1A 50V TO5 40p 1A100V TO5 42p 1A400V TO5 52p 1A800V TO5 70p 3A100V Stud 49p 3A400V Stud 75p 7A100V TO5+HS 84p 7A400V TO5+HS 90p 8A 50V Plastic 130p 12A400V Plastic 180p 16A100V Plastic 160p 16A400V Plastic 180p 16A600V Plastic 220p MCR101 TO-92 25p 2N3525 TO-18 92p 2N4444 TO-18 92p 2N5602 TO-92 34p 2N5604 TO-92 37p 2N5606 TO-92 40p		VOLTAGE REGULATORS FIXED PLASTIC - 3 Terminals 1 Amp +Ve -Ve 200mA (TO5) 5V 7805 140p 7905 200p 12V 7812 140p 7912 200p 15V 7815 140p 7915 200p 18V 7818 140p 7918 200p 24V 7824 140p 7924 200p VARIABLE 723 14 PIN DIL 45p Data sheets on regs at 10p each + s.a.e.		OPTO-ELECTRONICS SEVEN SEGMENT DISPLAYS OCPT71 30p OCPT71 90p ORP12 50p ORP60 60p ORP61 60p 2N5777 40p 3015F 0.3 in DIL 120p MAN3M 0.127 in PCB 110p DL704 0.3 in DIL 135p DL707 0.3 in DIL 135p DL747 0.6 in DIL 225p		LED'S: TIL209 Red 14p; TIL211 Green 30p LOW PROFILE DIL SOCKETS BY TEXAS 8 pin 13p, 14 pin 14p, 16 pin 15p, 24 pin 50p. INSULATORS: Mica + 2 Bushes for TO3 & TO66 5p.		DIODES Rectifier Diodes 1N 4001 Series 1 AMP £0.04 1N 4002 100V £0.06 1N 4003 200V £0.07 1N 4004 400V £0.08 1N 4005 600V £0.09 1N 4006 800V £0.10 1N 4007 1000V £0.13 MR 501 Series 3 AMP £0.16 MR 500 50V £0.17 MR 501 100V £0.17 MR 502 200V £0.18 MR 504 400V £0.20 MR 506 600V £0.25 MR 508 800V £0.29 MR 750 Series 6 AMP £0.27 MR 750 50V £0.29 MR 751 100V £0.33 MR 752 200V £0.33 MR 745 400V £0.40 MR 756 600V £0.54 Zener Diodes 400mW BZY 88 Series 2.7 to 33 volts £0.10 General Purpose Diodes 1N 4148 £0.04 Tuning Diodes *BB105 A VHF £0.59 *BB105 B VHF £0.63 *BB105 C VHF £0.44 MVAM - 1M MW/LW £0.70		MULLARD TRANSISTORS/DIODES AC 126 £0.21 BAX 17 £0.14 BD 160 £2.00 BF 180 £0.33 AC 127 £0.18 BC 107 £0.12 B0 11 £0.65 BF 181 £0.33 AC 128 £0.13 BC 107A £0.13 BD 182 £0.70 AC 153 £0.08 BC 1073 £0.09 BD 183 £0.80 AC 176 £0.18 BC 108 £0.10 BD 201 £1.00 AC 188 £0.32 BC 108A £0.11 BD 203 £1.00 ZN 3055 £0.70 ACY 19 £0.30 BC 108B £0.08 BD 232 £0.82 MJ 2501 £1.80 ACY 20 £0.17 BC 109B £0.13 BD 233 £0.50 MJ 2955 £0.80 ACY 22 £0.08 BC 109C £0.14 BD 234 £0.52 MJ 3001 £1.56 ACY 220 £0.08 *BC 147 £0.08 BD 235 £0.57 *MJ 340 £0.51 AD 140 £0.36 *BC 148 £0.06 BD 237 £0.62 MJ 371 £0.75 AD 149 £0.50 *BC 148B £0.08 BD 238 £0.72 MJ 521 £1.18 AF 114 £0.25 *BC 149 £0.06 BF 175 £0.14 MJ 2995 £0.72 AF 115 £0.22 *BC 157 £0.08 BF 187 £0.22 MSA 06 0.17 AF 116 £0.20 *BC 158 £0.07 BF 173 £0.22 MSA 06 0.33 AF 117 £0.19 *BC 159 £0.09 BF 177 £0.43 MSA 12 £0.37 AF 121 £0.10 *BC 327 £0.18 BF 178 £0.32 *MPSU 06 0.30 AF 125 £0.24 *BC 328 £0.18 BF 179 £0.38 *MPSU 56 £0.39 AF 126 £0.20 *BC 337 £0.20 AF 139 £0.31 BC 372 £0.18 ME 0411 £0.30 AF 178 £0.40 B0 115 £0.22 ME 0414 £0.07 AF 229 £0.60 *BD 124 £0.70 ME 0462 £0.30 AF 102 £0.16 BD 131 £0.37 ME 0492 £0.17 BA 154 £0.06 BD 133 £0.50 ME 1002 £0.50 BA 155 £0.07 BD 135 £0.27 ME 4003 £0.17 BA 156 £0.07 BD 136 £0.26 ME 4102 £0.07 BA 182 £0.17 BD 137 £0.30 ME 4104 £0.06 BAT 10 £0.65 BD 138 £0.34 T1P 29A £0.30 BAV 10 £0.08 BD 139 £0.38 T1P 30B £0.50 BAW 62 £0.06 BD 140 £0.41 T1P 31A £0.50 BAX 13 £0.06 BD 144 £2.00 TP 42A £0.50		RECTIFIER BY100 25p BY126 12p BY127 12p BY210 45p BY211 45p BY212 45p BY213 45p BY214 55p BY215 55p BY216 55p BY217 55p BY218 55p BY219 55p BY220 55p BY221 55p BY222 55p BY223 55p BY224 55p BY225 55p BY226 55p BY227 55p BY228 55p BY229 55p BY230 55p BY231 55p BY232 55p BY233 55p BY234 55p BY235 55p BY236 55p BY237 55p BY238 55p BY239 55p BY240 55p BY241 55p BY242 55p BY243 55p BY244 55p BY245 55p BY246 55p BY247 55p BY248 55p BY249 55p BY250 55p		FETs BF244 25p MPF102 30p MPF103 30p MPF104 30p MPF105 30p MPF109 22p ZNR3819 57p ZNR3820 50p ZNR3821 50p ZNR3822 50p ZNR3823 50p ZNR3824 50p ZNR3825 50p ZNR3826 50p ZNR3827 50p ZNR3828 50p ZNR3829 50p ZNR3830 50p ZNR3831 50p ZNR3832 50p ZNR3833 50p ZNR3834 50p ZNR3835 50p ZNR3836 50p ZNR3837 50p ZNR3838 50p ZNR3839 50p ZNR3840 50p ZNR3841 50p ZNR3842 50p ZNR3843 50p ZNR3844 50p ZNR3845 50p ZNR3846 50p ZNR3847 50p ZNR3848 50p ZNR3849 50p ZNR3850 50p		ZENER 3.3V to 33V 400mW 9p 1W 18p		TUNNEL AEY11 50p		MOSFETS 3N128 85p 3N140 85p 3N141 85p 40603 58p 40673 58p		VARIABLE Data sheets on regs at 10p each + s.a.e.		NOISE ZIJ 100p		BRIDGE RECTIFIERS 25A 100V20p 1A 50V 22p 1A 100V 24p 1A 400V 27p 1A 600V 30p 2A 50V 30p 2A 100V 35p 2A 400V 45p 6A 50V 60p 6A 100V 65p		DIODES SIGNAL OA47 7p OA70 9p OA81 8p OA85 10p		VAT RATES ALL ITEMS AT 8% EX-CEPT where marked which are rated at 25%	
--	--	--	--	--	--	--	--	---	--	---	--	--	--	--	--	---	--	--	--	---	--	--	--	---	--	--	--	--	--	---	--	----------------------------	--	---	--	---	--	--------------------------	--	---	--	---	--	---	--

Minimum Order £2 P&P 20p Please add VAT to total

All first grade devices Visitors, by appointment, welcome. Govt. Colleges, etc. orders accepted

TECHNOMATIC LTD.
54 SANDHURST ROAD, LONDON, NW9
Tel: 01-204 4333

VOLTAGE REGULATORS Variable Output MC 1469 R 500 mA 2.5-37.0 V Positive £1.83 MC 1483 R 500 mA 3.3-37.0 V Negative £2.50 MC 1723 CP2 150 mA 2.0-37.0 V Positive £0.50 MLM 305 G 20 mA 4.5-40.0 V Positive £1.25 MLM 304 G 20 mA 0.1-40.0 V Negative £1.25 MC 1466 L Floating Current/Voltage regulator £3.53 Fixed Output 1 Amp Positive Voltage—£1.20 Negative Voltage—£1.60 5 volt MC 7805 CP MC 7912 CP 12 volt MC 7812 CP MC 7915 CP 15 volt MC 7815 CP MC 7918 CP 18 volt MC 7818 CP MC 7924 CP 24 volt MC 7824 CP 0.7 Amp Positive Voltage—£0.77 5 V MC 7705 CP TO3 Volt Positive Regulators 15 V MC 7715 CP Internal thermal shut down 18 V MC 7718 CP MLM 309 K — £1.53		DISPLAYS AND LED'S All from Monsanto MAN Series 7 segment displays — Red, yellow, green, orange Type 1 Common anode RH decimal 0.3 inch £1.34 Type 2 Common anode (overlaid) 0.4 inch £1.66 Type 3 Common cathode LH decimal Please specify colour, height and type number reqd. Light 4 0.12" Red display £0.35 Type 1 0.2 inch diameter panel mounting £0.38 Type 2 0.125 inch diameter PCB mounting £0.15 Red only Type 3 0.125 inch diameter high intensity £0.32 Please specify colour and type number reqd Unless otherwise specified alternate colours will be shipped if ordered colour is not available 7 segment decoder drivers — CMOS common cathode MC 14511 CP £1.23 TTL common anode N 7447 B £0.75 TTL common cathode N 7448 B £0.85		DIODES Rectifier Diodes 1N 4001 Series 1 AMP £0.04 1N 4002 100V £0.06 1N 4003 200V £0.07 1N 4004 400V £0.08 1N 4005 600V £0.09 1N 4006 800V £0.10 1N 4007 1000V £0.13 MR 501 Series 3 AMP £0.16 MR 500 50V £0.17 MR 501 100V £0.17 MR 502 200V £0.18 MR 504 400V £0.20 MR 506 600V £0.25 MR 508 800V £0.29 MR 750 Series 6 AMP £0.27 MR 750 50V £0.29 MR 751 100V £0.33 MR 752 200V £0.33 MR 745 400V £0.40 MR 756 600V £0.54 Zener Diodes 400mW BZY 88 Series 2.7 to 33 volts £0.10 General Purpose Diodes 1N 4148 £0.04 Tuning Diodes *BB105 A VHF £0.59 *BB105 B VHF £0.63 *BB105 C VHF £0.44 MVAM - 1M MW/LW £0.70		FERRANTI INTEGRATED CIRCUITS ZN 1040 E Universal counter/display driver £12.00 ZN 1034 E Precision timer £2.99 *ZN 414 A N Radio circuit £1.00		SOLDERING IRONS Litesold soldering irons 240 A.c. Model 90 12 watt £2.75 Model 142 20 watt £2.80 Model 187 24 watt £2.95 Conqueror - light weight (35 gm) high efficiency iron £2.83 Spring stand for above irons £2.14 Desoldering attachment—fits Conqueror only £4.55 Desoldering braid 5 foot reel £0.79		from MOTOROLA • MULLARD • SIGNETICS MONSANTO • FERRANTI • GIM Mullard Audio and Radio Modules *LP 1173 10 Watt Audio Amp £6.68 *LP 1184 2 Very low distortion stereo pre-amp £7.16 *LP 1185 FM IF Amplifier £5.56 *LP 1188 FM Tuner Module £6.88 *LP 1400 Stereo Decoder Module £7.22 Special 'kit' offers (1) 10 Watt Stereo amplifier comprising — 1 x LP 1184 2 ND 2 x LP 1173 *NORMAL PRICE £20.52 *KIT PRICE £15.00 (2) FM Tuner comprising — 1 x LP 1185 1 x LP 1186 1 x LP 1400 *NORMAL PRICE £19.66 *KIT PRICE £15.00 Data Sheets on each module 10p extra		MULLARD TRANSISTORS/DIODES AC 126 £0.21 BAX 17 £0.14 BD 160 £2.00 BF 180 £0.33 AC 127 £0.18 BC 107 £0.12 B0 11 £0.65 BF 181 £0.33 AC 128 £0.13 BC 107A £0.13 BD 182 £0.70 AC 153 £0.08 BC 1073 £0.09 BD 183 £0.80 AC 176 £0.18 BC 108 £0.10 BD 201 £1.00 AC 188 £0.32 BC 108A £0.11 BD 203 £1.00 ZN 3055 £0.70 ACY 19 £0.30 BC 108B £0.08 BD 232 £0.82 MJ 2501 £1.80 ACY 20 £0.17 BC 109B £0.13 BD 233 £0.50 MJ 2955 £0.80 ACY 22 £0.08 BC 109C £0.14 BD 234 £0.52 MJ 3001 £1.56 ACY 220 £0.08 *BC 147 £0.08 BD 235 £0.57 *MJ 340 £0.51 AD 140 £0.36 *BC 148 £0.06 BD 237 £0.62 MJ 371 £0.75 AD 149 £0.50 *BC 148B £0.08 BD 238 £0.72 MJ 521 £1.18 AF 114 £0.25 *BC 149 £0.06 BF 175 £0.14 MJ 2995 £0.72 AF 115 £0.22 *BC 157 £0.08 BF 187 £0.22 MSA 06 0.17 AF 116 £0.20 *BC 158 £0.07 BF 173 £0.22 MSA 06 0.33 AF 117 £0.19 *BC 159 £0.09 BF 177 £0.43 MSA 12 £0.37 AF 121 £0.10 *BC 327 £0.18 BF 178 £0.32 *MPSU 06 0.30 AF 125 £0.24 *BC 328 £0.18 BF 179 £0.38 *MPSU 56 £0.39 AF 126 £0.20 *BC 337 £0.20 AF 139 £0.31 BC 372 £0.18 ME 0411 £0.30 AF 178 £0.40 B0 115 £0.22 ME 0414 £0.07 AF 229 £0.60 *BD 124 £0.70 ME 0462 £0.30 AF 102 £0.16 BD 131 £0.37 ME 0492 £0.17 BA 154 £0.06 BD 133 £0.50 ME 1002 £0.50 BA 155 £0.07 BD 135 £0.27 ME 4003 £0.17 BA 156 £0.07 BD 136 £0.26 ME 4102 £0.07 BA 182 £0.17 BD 137 £0.30 ME 4104 £0.06 BAT 10 £0.65 BD 138 £0.34 T1P 29A £0.30 BAV 10 £0.08 BD 139 £0.38 T1P 30B £0.50 BAW 62 £0.06 BD 140 £0.41 T1P 31A £0.50 BAX 13 £0.06 BD 144 £2.00 TP 42A £0.50		INTEGRATED CIRCUITS µA 741 Cv Op Amp £0.42 µA 709 Cv Op Amp £0.30 Signetics Linear MC 1458 V Dual comp op amp £0.80 *NE 540 L Audio power driver £1.17 NE 555 V Timer £0.44 NE 556 A Dual Timer £0.95 NE 561 B P.L.L. with AM demod £2.70 NE 562 B P.L.L. with V.C.O £2.70 NE 566 V P.L.L. function gen. £1.50 Signetics Memories N 82506 8 256 bit bipolar RAM £4.50 2102 B 1024 bit MOS RAM £2.85 Special Offer: Motorola 14 pin 741 C £0.10	
--	--	---	--	--	--	--	--	---	--	--	--	---	--	--	--

Dept. WW, Wellington Road London Colney, St. Albans Herts. AL2 1EZ

Terms of Business: Cash with order. MAIL ORDER ONLY

PRICES EXCLUSIVE OF V.A.T. WHICH MUST BE ADDED AS SHOWN BELOW

Postage/Packing 30p + VAT V.A.T. 8% except where marked * These items 25%

WW—070 FOR FURTHER DETAILS

NEW PRODUCTS

PROTO BOARDS

Build & test circuits as fast as you think!

PB100	10 IC cap breadboard kit, 4.5 x 6.0 x 1.3"	£17.55
PB101	10 14-DIP cap, 5-way post, 940 solderless tie points, 5.8 x 4.5"	£26.35
PB102	12 14-DIP cap, like PB101 with 1,240 tie points, 7.0 x 4.5"	£35.15
PB103	24 14-DIP cap, 4 5-way posts, 2,250 tie points, 6.0 x 9.0"	£52.75
PB104	32 14-DIP cap, 3,060 solderless tie points, 8.0 x 9.76"	£70.35



LOGIC MONITOR

Simultaneously displays static and dynamic logic states of DTL, TTL, HTL or CMOS DIP ICs. Pocket size. £84.95.




PROTO-CLIP

For power on/hands off signal tracing. Bring IC leads up from PC board surface for fast trouble shooting. PC14 14-pin £3.25 PC16 16-pin £3.40



SOCKETS & BUS STRIPS

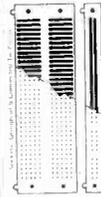Plug-in wire, test, modify or expand without patch cords or solder. Snap together to form breadboard needs.



PN/Description	Hole-to-Hole	Terminals	Price
QT595 Socket	1.3" 6.5"	118	£1.91
QT598 Bus	6.5" 6.2"	20	£2.20
QT475 Socket	5.3" 5.0"	94	£1.98
QT178 Bus	5.3" 5.0"	16	£1.98
QT135 Socket	4.1" 3.8"	70	£1.42
QT358 Bus	4.1" 3.8"	12	£1.73
QT185 Socket	2.4" 2.1"	36	£4.16
QT175 Socket	1.8" 1.5"	24	£3.28
QT85 Socket	1.4" 1.1"	16	£2.83
QT75 Socket	1.3" 1.0"	14	£2.63

7400 Series TTL

PN	25	100+	PN	0.48	0.45	0.40	
SN7400	0.14	0.13	0.12	SN7494	0.48	0.45	0.40
SN7401	0.14	0.13	0.12	SN7495	0.60	0.56	0.50
SN7402	0.14	0.13	0.12	SN7496	0.70	0.67	0.60
SN7403	0.14	0.13	0.12	SN7497	0.70	0.69	0.68
SN7404	0.15	0.14	0.13	SN74100	1.35	1.30	1.25
SN7405	0.15	0.14	0.13	SN74104	0.31	0.29	0.26
SN7406	0.30	0.29	0.28	SN74105	0.31	0.29	0.26
SN7407	0.30	0.29	0.28	SN74107	0.31	0.29	0.26
SN7408	0.15	0.13	0.12	SN74109	1.00	0.97	0.95
SN7409	0.15	0.13	0.12	SN74110	0.55	0.50	0.45
SN7410	0.14	0.13	0.12	SN74111	0.81	0.80	0.76
SN7411	0.23	0.22	0.21	SN74114	1.00	0.97	0.95
SN7412	0.19	0.18	0.17	SN74115	1.00	0.97	0.95
SN7413	0.30	0.29	0.28	SN74118	1.00	0.95	0.90
SN7414	0.71	0.70	0.69	SN74121	0.31	0.29	0.25
SN7415	0.30	0.29	0.27	SN74122	0.44	0.41	0.37
SN7416	0.28	0.27	0.26	SN74123	0.62	0.58	0.50
SN7417	0.28	0.27	0.26	SN74125	0.70	0.65	0.60
SN7420	0.14	0.13	0.12	SN74126	0.75	0.70	0.65
SN7421	0.95	0.94	0.93	SN74132	2.10	2.05	2.00
SN7422	0.25	0.24	0.23	SN74136	0.95	0.90	0.85
SN7423	0.26	0.25	0.22	SN74140	2.50	2.45	2.40
SN7425	0.26	0.25	0.22	SN74141	0.75	0.70	0.62
SN7426	0.26	0.25	0.22	SN74145	1.15	1.10	1.05
SN7427	0.26	0.25	0.22	SN74147	2.95	2.90	2.85
SN7428	0.39	0.38	0.37	SN74148	2.30	2.25	2.20
SN7430	0.14	0.13	0.12	SN74150	1.35	1.30	1.25
SN7432	0.25	0.24	0.22	SN74151	0.68	0.62	0.55
SN7433	0.36	0.35	0.34	SN74152	1.55	1.50	1.45
SN7437	0.27	0.26	0.22	SN74153	0.68	0.62	0.55
SN7438	0.27	0.26	0.22	SN74155	1.55	1.50	1.45
SN7439	1.10	1.08	1.06	SN74156	0.68	0.62	0.55
SN7440	0.14	0.13	0.12	SN74157	0.90	0.85	0.80
SN7441	0.70	0.69	0.66	SN74158	1.50	1.45	1.40
SN7442	0.63	0.60	0.53	SN74159	1.15	1.10	1.05
SN7443	1.00	0.99	0.90	SN74160	0.95	0.90	0.80
SN7444	1.08	1.07	1.05	SN74161	0.95	0.90	0.80
SN7445	0.85	0.83	0.70	SN74162	0.95	0.90	0.80
SN7446	1.03	1.00	0.85	SN74163	0.95	0.90	0.80
SN7447	1.03	1.00	0.85	SN74164	1.60	1.55	1.50
SN7448	0.85	0.83	0.70	SN74165	1.60	1.55	1.50
SN7450	0.14	0.13	0.12	SN74166	1.40	1.30	1.15
SN7451	0.14	0.13	0.12	SN74170	2.40	2.30	2.20
SN7453	0.14	0.13	0.12	SN74173	1.65	1.60	1.55
SN7454	0.14	0.13	0.12	SN74174	1.15	1.10	1.00
SN7455	0.40	0.39	0.38	SN74175	0.97	0.90	0.80
SN7460	0.14	0.13	0.12	SN74176	1.10	1.05	1.00
SN7462	0.45	0.44	0.42	SN74177	1.10	1.05	1.00
SN7464	0.45	0.44	0.42	SN74180	1.10	1.05	1.00
SN7465	0.45	0.44	0.42	SN74181	3.50	3.45	3.35
SN7470	0.30	0.27	0.25	SN74182	1.10	1.05	1.00
SN7471	0.60	0.59	0.58	SN74184	1.60	1.55	1.50
SN7472	0.25	0.24	0.21	SN74185	2.30	2.25	2.20
SN7473	0.30	0.27	0.26	SN74186	4.90	4.85	4.80
SN7474	0.31	0.29	0.26	SN74190	1.75	1.70	1.65
SN7475	0.40	0.39	0.38	SN74191	1.70	1.65	1.60
SN7476	0.31	0.29	0.26	SN74192	1.25	1.05	1.00
SN7478	0.65	0.63	0.61	SN74193	1.25	1.05	1.00
SN7480	0.43	0.41	0.36	SN74194	1.10	1.05	1.00
SN7481	1.00	0.95	0.90	SN74195	0.90	0.85	0.80
SN7482	0.75	0.70	0.62	SN74196	1.05	1.00	0.95
SN7483	0.81	0.80	0.68	SN74197	1.05	1.00	0.95
SN7484	0.90	0.86	0.85	SN74198	2.05	2.00	1.70
SN7485	1.25	1.15	1.00	SN74199	2.05	2.00	1.70
SN7486	0.31	0.28	0.25	SN74200	6.00	5.95	5.80
SN7489	3.50	3.20	3.00	SN74221	1.80	1.75	1.70
SN7490	0.45	0.42	0.35	SN74251	1.80	1.75	1.70
SN7491	1.00	0.95	0.90	SN74278	3.00	2.90	2.80
SN7492	0.45	0.42	0.35	SN74279	1.20	1.15	1.10
SN7493	0.45	0.42	0.35	SN74293	1.00	0.95	0.90
				SN74298	2.60	2.55	2.50

'LS' and 'S' Series TTL also available

HIGH-SPEED TTL

PN	1	25	100+	PN	0.36	0.35	0.33
SN74H00	0.34	0.33	0.30	SN74H51	0.36	0.35	0.33
SN74H01	0.34	0.33	0.30	SN74H52	0.36	0.35	0.33
SN74H04	0.38	0.37	0.34	SN74H53	0.36	0.35	0.33
SN74H05	0.37	0.36	0.33	SN74H54	0.36	0.35	0.33
SN74H06	0.40	0.39	0.37	SN74H55	0.36	0.35	0.33
SN74H10	0.36	0.35	0.33	SN74H60	0.36	0.35	0.33
SN74H11	0.36	0.35	0.33	SN74H61	0.36	0.35	0.33
SN74H20	0.36	0.35	0.33	SN74H62	0.36	0.35	0.33
SN74H21	0.36	0.35	0.33	SN74H71	0.80	0.78	0.75
SN74H22	0.36	0.35	0.33	SN74H72	0.74	0.73	0.70
SN74H30	0.36	0.35	0.33	SN74H73	0.90	0.88	0.85
SN74H40	0.36	0.35	0.33	SN74H74	0.87	0.85	0.81
SN74H50	0.36	0.35	0.33	SN74H76	0.90	0.88	0.85
				SN74H101	0.80	0.78	0.75
				SN74H102	0.80	0.78	0.75
				SN74H103	1.10	1.09	1.05
				SN74H106	0.95	0.93	0.90

LOW-POWER TTL

PN	1	25	100+	PN	1.60	1.55	1.50
SN74L00	0.34	0.33	0.30	SN93101	3.20	3.10	2.90
SN74L02	0.34	0.33	0.30	SN93108	1.80	1.75	1.70
SN74L03	0.39	0.37	0.34	SN93109	1.80	1.75	1.70
SN74L04	0.39	0.37	0.34	SN93110	2.80	2.75	2.65
SN74L08	0.34	0.33	0.30	SN93111	4.20	4.10	3.90
SN74L10	0.34	0.33	0.30	SN93112	1.80	1.75	1.70
SN74L20	0.39	0.37	0.34	SN93134	1.70	1.65	1.60
SN74L40	1.62	1.58	1.50	SN93116	3.20	3.10	2.95
SN74L51	0.34	0.33	0.30	SN93121	1.50	1.46	1.42
SN74L73	0.74	0.71	0.68	SN93122	1.80	1.76	1.70
SN74L74	0.89	0.87	0.80	SN93124	2.80	2.72	2.60
SN74L80	1.62	1.58	1.50	SN93128	3.70	3.60	3.42
SN74L95	1.62	1.58	1.50	SN93138	4.20	4.10	3.90
SN93L00	1.50	1.45	1.40	SN93140	6.50	6.30	5.90
				SN93141	6.50	6.30	5.90
				SN93160	3.00	2.90	2.70
				SN93166	2.70	2.65	2.55

WAVEFORM GENERATOR KITS

Here's a highly versatile instrument at a fraction of the cost of conventional unit. Kit includes two XR205 IC's, resistors & applications. PC board (etched & drilled, ready for assembly) and detailed instructions.



XR-205K £12.30

The Function Generator Kit features sine, triangle and square wave, 1MHz 0.5% typ., AM/FM capability.

XR-2206KA FUNCTION GENERATOR KIT £11.50

Includes monolithic function generator IC, PC board, and assembly instruction manual.

XR-2206KB FUNCTION GENERATOR KIT £16.00

Same as XR-2206KA above and includes components for PC board.

PICO-PAC

THE SMALLEST AC/DC POWER SUPPLY EVER! Only 1.70" x 1.00" x 0.85" output preset: 5% 9 models £14.50 each




PREMIUM QUALITY COMPONENTS

We've been buying and selling top quality components for nearly ten years. We handle only original parts, from the world's leading manufacturers and our customers include some of the largest and most quality-conscious companies. Now you can take advantage of our component buying skills and power and select from a broad range of advanced circuits.



NEW

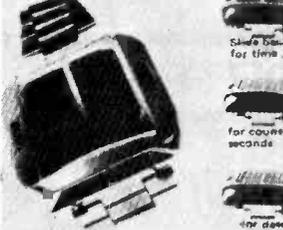Solar Powered Watch with 100-YEAR CALENDAR



Solar cells draw power from the sun (10 to 15 minutes per day) or from ambient light (slightly longer) to keep batteries fully charged. Batteries operate up to 10 years. LSI circuitry is programmed to provide a calendar to the year 2100, automatically adjusting for 30 and 31 day months, even leap years. Automatic brightness control adjusts LED for perfect viewing even in outdoors. Shows minutes and hours, counts out seconds or shows the date. Easily adjusts to reset hour or date without affecting calendar. Shock and water resistant. Accurate to 5 seconds per month. Price: £298.50 each.

HIGH-BRIGHTNESS L.E.D.s

PN	200" dia.	125" dia.
ED 5053 RED	0.24	ED 209 RED 0.18
ED 5053 YELLOW	0.24	ED 209 YELLOW 0.27
ED 5053 GREEN	0.24	ED 209 GREEN 0.27
ED 5053 ORANGE	0.24	

STANDARD MICROSYSTEMS

PN	1-up	25-up	100-up
COM2502	£6.60	£5.30	£4.62
COM2502F	£4.65	£3.95	£3.50
COM2017	£7.05	£6.00	£5.00
COM2017F	£4.75	£4.15	£3.75
COM2502H	£12.80	£11.25</	

Samson's

(ELECTRONICS) LTD.

9 & 10 CHAPEL ST., LONDON, N.W.1
01-723 7851 01-262 5125
ADJACENT TO EDGWARE ROAD MET. LINE STATION

CURRENT RANGE OF NEW L.T. TRANSFORMERS FULLY SHROUDED TERMINAL BLOCK CONNECTIONS ALL PRIMARIES 220/240V

Type	Sec. Taps	Amps	Price	Postage
1A	23-33-40-50v	15	£15.50	£1.00
1B	25-33-40-50v	10	£13.25	£1.00
1C	25-33-40-50v	6	£9.50	85p
1D	25-33-40-50v	3	£8.25	85p
2A	4.16-24-32v	12	£11.25	£1.00
2B	4.16-24-32v	8	£8.75	85p
2C	4.16-24-32v	4	£5.25	65p
2D	4.16-24-32v	2	£3.85	60p
3A	24-30-36v	10	£10.00	85p
3B	24-30-36v	5	£8.25	85p
3C	24-30-36v	2	£3.85	60p
4A	12-20-24v	20	£13.25	£1.00
4B	12-20-24v	10	£8.25	85p
4C	12-20-24v	5	£5.25	65p
5A	3-12-18v	20	£11.25	£1.00
5B	3-12-18v	10	£7.75	85p
5C	3-12-18v	5	£4.95	65p
6A	48-56-60v	2	£4.95	65p
6B	48-56-60v	1	£3.85	60p
7A	6-12v	20	£8.50	65p
7B	6-12v	10	£5.25	65p
7C	6-12v	5	£3.85	60p
8A	17-32v	8	£8.50	85p
9A	12-24v	1	£2.70	50p
10A	9-15v	2	£2.70	50p
11A	8-0-8v	2	£2.70	50p

HEAVY DUTY UNSHROUDED TYPES 9 INCH FLYING LEADS ALL PRIMARIES 240V

Type No	Sec. Volt	Tap	Amps	Price	Carr
1	24-30-36	20	15	£15.75	£1.25
2	12-20-24	30	10	£15.75	£1.25
3	3-12-18	30	5	£15.75	£1.25
4	6-12	50	5	£15.75	£1.25

CENTRE TAPPED L.T. TRANSFORMERS Fully shrouded Terminal block connections Pr 220-240v Screen Tapped sec 30-25-0-25-30v, 2 amps £4.95, carr 60p. 36-25-0-25-36v 5 amps £9.95, carr 85p. 28-0-28v 10a £12.50, carr £1

PLEASE ADD 8% TO ALL ORDERS INC. CARR.

UNIMAX SEQUENTIAL MICRO SWITCHES
2 pole CO 15 amp contacts. 2nd pole actuates after 1st pole. Leaf roller action. 75p. P.P. 25p

A.E.I. 240AC CONTACTORS
20 amp CONTACTORS
Type 0659. 3 makes. 1 break. Type 0658. 2M. 2B. £1.25. P.P. 25p. 110v AC types. Type 0651. 3M. 1B. Type 0654. 2M. 2B. Type 0653. 4M. £1.00. P.P. 25p

RELAY CONTROL CO. American Miniature relays 6v DC. 1 CO contact. Size 1 1/4 x 1 1/4 ins. 35p, post 10p

MINIATURE RELAYS
ITT, PLESSEY, VARLEY TYPES
280J 12-15DC 40C. 60P. 430P. 15-24V DC 2CO. 50P. 1250J 4 CO. 24-30V DC. 50P. 2500J 35-40V DC. 50P. 5000J 40-60V DC. 50P. Postage 15p each

G.P.O. RELAYS
3000 type. 100J. 1 25 amp make contact 60p. 2000+130J. 1 normal CO 40p. 75J. 3M. 1B. 1CO normal contacts 40p. Post on all relays 10p.
Diamond H relays type BR115A1T-3C. 150J. 24v DC Sealed type 75p. P.P. 10p

ITT LEVER SWITCHES
Type 601 AAO 72-42 4 CO contacts overall size 1 1/2 x 2 1/2 ins. White lever gold flash contacts. 60p. Three for £1.50. P.P. 20p

PLESSEY MINIATURE MICRO SWITCHES
Type LIC 7134 One CO one break. Gold flash contacts. Size 1 1/2 x 1 1/2 ins. Three for 50p. P.P. 20p

SANGANO SYNCHRONOUS A.C. 240V MOTOR TYPE 7
4 rev. per hour. Size 1 1/4 plus 1/2 spindle. 1 1/4 inch dia. £1.25. P.P. 50p

GENTS ALARM BELLS
6 volt DC 6 inch dia. Gong. Overall size 4 1/2 x 6 x 6 inches. £3.50. P.P. 75p

DIAMOND H Double pole toggle switches type 712 250v. 20 amp. centre single hole fixing. 60p. P.P. 15p

BENSON SOLENOIDS
AC 240v. 25% duty. Approx 2 ins. 1/2 in. pull. Size 2 1/2 x 1 1/2 ins. Res 350J. 75p. p.p. 25p.

L.T. SMOOTHING CHOKES
C core type 15 M/H 3 BA £2.00. P.P. 50p. 50 M/H 2.5A £2.00. P.P. 50p. 12 M/H 7A £3.00. P.P. 60p. 140 M/A 140 M/H 5A £1.25. Carr 85p. 10 M/H 2.5A £8.75. Carr £1.25. Open type top panel connections. 4 B m/H 10A £3.00. P.P. 50p. Potted type 100 M/H 2A £3.50. P.P. 75p. C core swmgng types 7.5 M/H 6A-75 M/H 0.5A £3.95. P.P. 75p. 10 M/H 4A-100 M/H 0.5A £3.00. P.P. 50p. 50 M/H 5A-100 M/H 0.5A £2.75. P.P. 50p

H.T. SMOOTHING CHOKES
Core types 10H 350M/A £3.50. carr £1. 20H 180M/A £2.50. carr 75p. 5H 180M/A £1.75. P. 50p. Potted types 15H 180M/A £2.00. carr 75p. 10H 250M/A £2.00. carr 75p. 20H 40M/A 75p. pp. 25p. Parmeko Potted type 10H 180M/A £2.00. carr 75p

AMOS "C" CORE CHOKES
10 M/H 25 amps £8.75. carr £1.00

HOWELLS "C" CORE TRANSFORMERS
Pri. 200-220v. screen. Sec. 70-0-70v 10 amp table top connections. size 7 1/2 x 7 inches. £15.00. carr £2.00. Pri. 220-240v. Sec. 18-0-18v. 12.5 amps conservatively rated. Table top connections £10.00. carr £2.00

GEC L.T. TRANSFORMERS
Pri. 220-240v. Sec. tapped 51-61-65-67-69v. 10A Unshrouded terminal block connections. £8.75. carr £1.25. Pri. 220-240v. Sec. tapped 58-63-69-74v. 3A. £3.75. carr 75p

WOODEN MULTI-TAPPED L.T. TRANSFORMERS
Pri. 200-220-240v secs. All separate windings. 31v 7A. 26v 5A. 16v 4A. 16v 4A. 25v 2A. 25v 2A. open frame type. Table top connections. £8.50. carr £1.50

FRESHAM MULTI-TAPPED L.T. TRANSFORMERS
Pri. 200-220-240v Sec. No. 1 22.5-25-28v 5A. No. 2 25v 2.5A. No. 3 16v 1A twice. No. 4 10v 1A twice. No. 5 6.3v 2A. No. 6 145-0-145v. 200 M/A. C core type table top connections. Brand new

GRESHAM E.H.T. TRANSFORMERS
Pri. 240v. Sec. 2300 M/A. 6.3v 1.5A. Table top connections. Size 5 3/4 x 3 3/4 ins. £3.00. carr 50p

PARMEKO L.T. TRANSFORMERS
Open types Pri. 110-220-240v. Sec. 30v 5.5A and 12v 2.2A. Table top connections. £4.95. P.P. 95p. Pri. 240v. Sec. 26v 10A and 12v 0.1A. Table top connections. £5.50. P.P. 95p. Pri. 230-240-250v. Sec. 6.4-0-6.4v 12A. Shrouded table top connections. £4.50. P.P. 95p. Potted types. Pri. 115-230v. Sec. tapped 24-30-32v 2A. £2.95. P.P. 50p. Pri. 115-220-230v. Sec. 6.6v 6A twice and 5v 6A. £4.95. P.P. 95p. Pri. 110-220-240-250v. Sec. 2-0-2v 24A and 6.4v 0.5A. High voltage insulation. £5.75. P.P. £1.25

WOODEN H.T. TRANSFORMERS
Pri. 200-220-240v. Sec. 250 0-250v 60M/A. 6.3v CT. 3A. 5v 2A. Enclose type table top connections. £3.00. P.P. 50p. Parmeko potted type. Pri. 110-220-240v. Sec. 1185-0-1185v 365M/A. Choke input filter. £10.00. carr £2

SPECIAL OFFER OF PAPER BLOCK CAPACITORS
6mld 1000v DC wkg. 75p. P.P. 35p. 4mld 1000v DC wkg. 65p. P.P. 35p. 4mld 400v AC wkg. 65p. P.P. 35p. 6mld 750v DC wkg. 75p. P.P. 35p. 1mld 600v DC wkg. 25p. P.P. 10p. 2mld 100v DC wkg. Six for £1. P.P. 35p. 0.01mld Mica 6000v DC wkg. £1. P.P. 35p. 0.1mld 2000v DC wkg. £75p. P.P. 35p. 0.03mld Mica. 1250v RMS Pulse wkg. 75p. P.P. 35p. 0.1-0.1mld 600v DC wkg. 25p. P.P. 10p. One only large block cap 40mld 500v DC wkg + 40mld 400v DC wkg + 6mld 600v DC wkg. £8.50. P.P. £1.50

COIN OPERATION TV METERS
An ideal component unit, comprising of 1 1/2v battery motor, gear mechanism 240v 5A micro switch, coin wheels etc. Housed in bakelite case. 75p. P.P. 25p

COMPUTER FANS AC 230v
Size 4 1/2 x 4 1/2 ins. 100 CFM. Ex-equipment. Perfect condition. £3.50. P.P. 50p

POTTED H.T. TRANSFORMERS BY FAMOUS MAKERS
No. 1 Pri. 110-220-240v. Sec. Sec. tapped 408-0-200-408v. High taps 165M/A. Low taps 500M/A. £5.50. carr £1. No. 2 Pri. 115-220-240v. Sec. 400-0-400v. 400M/A. £5.75. carr £1. No. 3 Pri. 115-220-240v. Sec. 350-0-350v. 200M/A. 6.3v 6A. 5v 3A. £4.50. carr £1

GIRO NO. 331 7056. Access accepted and Barclaycard. C.W.O. only p&p 25p.
Vat discount: £15 - 10% (except net items)
Export Order enquiries welcome £5 min.

Official Orders accepted from Educational & Government Departments
E. & O. E. ALL PRICES include vat at 8%

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. Mounting. 0.01µF. 0.015µF. 0.022µF. 0.033µF. 0.047µF. 4p; 0.068µF. 0.1µF. 4 1/2p. 0.15µF. 5p; 0.22µF. 6p; 0.33µF. 8p; 0.47µF. 10p; 0.68µF. 13p; 1µF. 17p; 1.5µF. 26p; 2.2µF. 28p.

MULLARD POLYESTER CAPACITORS C296 SERIES
400V. 0.01µF. 0.01µF. 0.022µF. 0.033µF. 0.047µF. 0.068µF. 0.01µF. 0.015µF. 0.022µF. 0.033µF. 4p; 0.047µF. 0.068µF. 0.1µF. 5p; 0.15µF. 8p; 0.22µF. 10p; 0.33µF. 15p; 0.47µF. 18p.

160V. 0.01µF. 0.015µF. 0.022µF. 0.047µF. 0.068µF. 4p; 0.1µF. 5p; 0.15µF. 6p; 0.22µF. 7p; 0.33µF. 8p; 0.47µF. 10p; 0.68µF. 14p; 1µF. 17p.

MINIATURE CERAMIC PLATE CAPACITORS
50V (pF) 27. 33. 39. 47. 56. 68. 82. 100. 120. 150. 180. 220. 270. 330. 390. 470. 560. 680. 820. 1K. 1K5. 2K2. 3K3. 4K7. 6K8. (pF) 0.01. 0.015. 0.022. 0.033. 0.047. 2 1/2p each. 0.1. 30V. 5p.

POLYSTYRENE CAPACITORS 160V 5%
(pF) 10. 15. 22. 33. 47. 68. 100. 150. 220. 330. 470. 680. 1000. 1500. 2200. 3300. 4700. 6800. 10000. 4p

VAT
Please add 15% extra VAT to total order. except for test meters and Vero Board. We would appreciate separate listing of 8% and 25% items to avoid delay

SPECIAL RESISTOR KITS (Prices include post and packing)
10E12 1/2 W KIT 10 of each E12 value. 22 ohms-1M. a total of 570 (CARBON FILM 5%) £4.60 net
25E12 1/2 W KIT 25 of each E12 value. 22 ohms-1M. a total of 1425 (CARBON FILM 5%) £10.99 net
1/2 W Kit also available at the same prices

RESISTORS — High Stab Carbon Film 5% MF — High Stab Metal Film 5%
1/2 W Type Range 1-99 100-499 500-999 1000+ Size mm
1/4 CF 12-1M 1 0.90 0.85 0.80 2.4 x 7.5
1/4 CF 22-2M2 1 0.90 0.85 0.80 3.9 x 10.5
1/4 MF 10-2M2 1.7 1.4 1.2 3 x 7
1/2 MF 10-2M2 1.6 1.3 1.1 4.2 x 10.8
1 MF 10-10M 3 1.98 1.81 1.65 6.6 x 13
2 MF 10-10M 4 3.52 3.08 2.75 8 x 17.5

(Price in pence each)
VALUES AVAILABLE — E12 Series only (Net price above 100)

PRESET SKELETON POTENTIOMETERS
MINIATURE 0.25V Vertical or horizontal 7p each. 1K. 2K. 4K. 7.5K. etc. up to 1M Ω
SUB-MIN 0.05V Vertical. 100 Ω to 220K Ω. 7p each

ALL STOCK SUBJECT TO AVAILABILITY

MULTIMETER U4324
34 Ranges. High sensitivity. 20,000 Ω/Volt. Overload protected. Vdc. 0-6. 1200v in 5 ranges. Vac. 3. 900v in 8 ranges. Idc. 0-0.6-3A in 6 ranges. Iac. 0-3. 3A in 5 ranges. Resistance—25 Ω-5M Ω in 5 ranges. Accuracy—dc and R—2% of F.S.D. ac and db—4% of F.S.D.
Size—167 x 98 x 63mm
Supplied complete with storage case, test leads, spare diode, and battery. PRICE £10.64 net + P & P 50p. U4324

SPECIAL OFFER
10E12 1/2 W resistor kit
£4.00 net
(+ 15% VAT)
Offer ends 30th January

B. H. COMPONENT FACTORS LTD.

(W.W.), LEIGHTON ELECTRONICS CENTRE, 59 NORTH STREET, LEIGHTON BUZZARD LU7 7EG. Tel: Leighton Buzzard 2316 (Std. Code 05253)

Miniature Mullard Electrolytics
1.0µF 63V 7p 68µF 63V 14p
1.5µF 63V 7p 100µF 10V 7p
2.2µF 63V 7p 100µF 25V 7p
3.3µF 63V 7p 100µF 50V 17p
4.7µF 63V 7p 150µF 16V 7p
6.8µF 63V 7p 150µF 63V 17p
10µF 63V 7p 220µF 6.4V 7p
10µF 16V 7p 220µF 10V 7p
10µF 25V 7p 220µF 16V 8p
10µF 63V 7p 220µF 63V 25p
15µF 16V 7p 330µF 63V 14p
15µF 63V 7p 330µF 63V 28p
16µF 40V 7p 470µF 6.4V 8p
22µF 25V 7p 470µF 40V 25p
32µF 63V 7p 680µF 16V 17p
32µF 10V 7p 680µF 40V 28p
33µF 16V 7p 100µF 16V 25p
33µF 40V 7p 100µF 25V 28p
47µF 63V 7p 1500µF 6.4V 17p
47µF 25V 7p 1500µF 16V 28p
47µF 63V 8p 2200µF 10V 28p
68µF 16V 7p 3300µF 64V 26p

VEROBOARD 0.1 0.15
2 1/2 x 5 1/2 45p 45p
2 1/2 x 3 1/2 41p 30p
3 1/2 x 5 1/2 51p 53p
3 1/2 x 3 1/2 45p 45p
2 1/2 x 1 1/2 11p 10p
2 1/2 x 5 1/2 (Plain) 22p
2 1/2 x 3 1/2 (Plain) 60p
5 x 3 1/2 (Plain) 37p
Insertion tool 87p 87p
Track cutter 68p 68p
Pins Pk1 25 25p 25p

TRANSISTORS
AC127 13p BC212L 21p
AC128 13p BC213L 22p
BC107 16p BC214L 12p
BC108 12p OC44 12p
BC109 13p OC71 13p
BC148 17p OC81 13p
BC149 29p OC170 13p
BC182L 34p TIS43 45p
BC183L 13p 2N2926 13p
BC184L 14p 2N3702 14p

POTENTIOMETERS
Carbon track 5K Ω to 2M Ω log or lin (and 1K lin) Single. 17 1/2p. Dual Gang 48p. Log Single with switch 26p. Slider pots 60mm. 5K to 500K log or lin. 45p. Dual 55p. Knob 10p.

DIDDES
IN4001 6p Din 2 Pin 12p
IN4002 7p 3 Pin 16p
IN4003 9p 5 Pin 18p
IN4004 9p Sid Jack 20p
IN4005 12p 2.5mm Jack 13p
IN4006 14p Phono 7p
IN914 7p Din 2 Pin 10p
IN916 7p 3 Pin 10p
BA100 10p Din 2 Pin 12p
OAS 42p 5 Pin 18p
GA47 9p Sid Jack 18p
GA81 11p 2.5mm Jack 13p
GA200 8p Phono 7p

ELECTROLYTIC CAPACITORS Tubular and Large Cans
(µF/V) 125 225 425 470/10. 525 825 1010. 1050. 1625 2263
2525 2550. 3225 5025. 10010. 10025 7p. 5050 8p. 10050 10p
20025. 10p. 25050. 18p. 50010 10p. 50025 17p. 50050 25p
100010 17p. 100025 25p. 100050 40p. 200010 20p. 100010. £1.10
200025 35p. 2000100. £1.20 2500 25. 38p. 250050 68p. 500025 69p.
500050 £1.20

HY-VOLT 4350. 20p. 8350. 23p. 100100. 20p. 16350. 35p. 16450. 38p.
32350. 38p. 50250. 27p. 100250. 40p.

METALISED PAPER CAPACITORS
250V. 0.05µF. 0.1µF. 6p. 0.25µF. 7p. 1µF. 9p. 500V
0.025. 0.05. 0.1. 6p. 0.25. 7p. 0.5. 9p. 1000V. 0.01. 12p. 0.022.
13p. 0.047. 0.1. 19p. 0.22. 28p. 0.47. 36p.

HAVE YOU GOT YOURS?

66 PAGES 3000 ITEMS 600 PICTURES

YOUR COMPLETE ELECTRONIC STORES MAIL ORDER AND SHOP

CATALOGUE NO. 4A FULLY ILLUSTRATED

COMPLETE WITH DISCOUNT VOUCHERS WORTH 20p

20p

★ DISCOUNTS ★ ALL NEW STOCK ★ SATISFACTION GUARANTEE ★ DEPENDABLE SERVICE

Please send S.A.E. for supplement No. 1

MULTIMETER U4323
22 Ranges plus AFIF Oscillator. 20,000 Ω/Volt. Overload protected. Vdc. 0-6. 1200v in 7 ranges. Vac. 2.5-1000v in 6 ranges. Idc. 0-0.05-500mA in 5 ranges. Resistance—5 Ω-1M Ω in 4 ranges. Accuracy—5% of F.S.D.
OSCILLATOR—1kHz and 455kHz (A.M.) at approx. 1 Volt. Size—160 x 97 x 40mm. Supplied complete with carrying case, test leads and battery. PRICE £8.64 net + P & P 50p

MULTIMETER U4341
27 Ranges plus Transistor Tester. 16,700 Ω/Volt. Overload protected. Vdc. 0-3. 900v in 8 ranges. Vac. 1.5-750v in 6 ranges. Idc. 0-0.06-600mA in 5 ranges. Resistance—2K Ω-2M Ω in 4 ranges. Accuracy—dc—2% ac—4% of F.S.D.
Hz—10-350 in 2 ranges. Size—115 x 215 x 90mm. Complete with steel carrying case, test leads and battery. PRICE £11.88 net + P & P 50p

NEW CAPACITOR KITS
C280 Kit PC Mounting polyester. 250V 5 of each value 0.01. 0.022. 0.047. 0.1. 0.22µF. 2 of 0.47µF. £1.40 net
C296 Kit Tubular polyester. 400V 5 of each value 0.01. 0.022. 0.047. 0.1. 0.22µF. 2 of 0.47µF. £1.40 net
Ceramic Kit—square platelets. 50V 5 of each value 22. 33. 47. 100. 220. 330. 470. 1000pF. 2200. 4700pF. 0.1µF. £1.40 net
250V Paper Kit—Tubular metal case. 3 of each value 0.05. 0.1. 0.25. 0.5. 1µF. £1.00 net
500V Paper Kit—Tubular metal case. 3 of each value 0.025. 0.05. 0.1. 0.25. 0.5µF. £1.00 net
1000V Paper Kit—Tubular metal case. 3 of each value 0.01. 0.025. 0.05. 0.1µF. £1.20 net

You've asked for it!

Time and again we are asked for reprints of Wireless World constructional projects: tape, disc, radio, amplifiers, speakers, headphones. Demand continues long after copies are out of print. To meet the situation we have collected fifteen of the most sought after designs and put them in one inexpensive book. And we've updated specifications where necessary to include new components which have become available. A complete range of instruments is presented, from the Stuart tape recorder and Nelson-Jones f.m. tuner, through the Bailey, Blomley and Linsley Hood amplifiers, to the Bailey and Baxandall loudspeakers – some of which have been accepted as standard in the industry.

high fidelity designs

£1 from newsagents and bookshops
or £1.35 (inclusive) by post from the publishers.

A book from

Wireless World



To: General Sales Department, Room 11, Dorset House,
Stamford Street, London, SE1 9LU

Please send me _____ copy copies of High Fidelity Designs

at £1.35 inclusive. I enclose remittance value £
(cheques payable to IPC Business Press Ltd.).

NAME
(please print:)

ADDRESS

Company registered in England No. 577128
Regd. office; Dorset House, Stamford Street, London SE1 9LU

YOU COULD SAVE UP TO **£1,000** *pa* PER ENGINEER * with THIS BOOK


* With the Colour Faults Guide system of rapid, on-the-spot diagnosis of colour set faults the originating firm, Colour Vision Rentals Ltd, reported savings of the order of **well over £1,000 per engineer per year.**

HOW IT IS DONE . . . A tabulated index of fault symptoms and the most common circuit troubles causing them quickly enables the engineer in the customer's home to locate the cause of the breakdown and the panel or assembly in which it has occurred. He can then change the panel (etc) on the spot from his van stock and return the faulty item for repair subsequently, and return to stock. The originating firm calculates that an average of about 3 hours a week per engineer is saved, plus an average of one workshop uplift less per engineer — hence the £1,000-plus per year saving.

The Colour Faults Guides, E R T's top innovation of 1974-5, covering 14 widely used chassis, are now collected in book form for sale at £1.70 inclusive per issue.

CAN YOU AFFORD YOUR MEN NOT TO HAVE A COPY WITH THEM ON EVERY JOB?

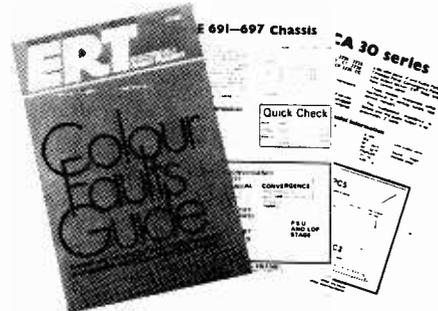The fourteen chassis covered in the book comprise:- Decca 30 series; GEC 2210 series; GEC Hybrid 2040 series; Hitachi range — CAP 160, CEP 180, CNP 190; ITT CVC5; Philips G8; Pye CT200 series, Pye 691-697; Rank R I A823/A; Thorn C E 3000 & 3500; Thorn (BRC) 8000/8500 series; Bang & Olufsen 39 series — Beovision 3500, 3600, 400, 600; Skantic — all models except earlier 22in. hybrid.



Order Coupon

To General Sales Dept., Room 11, ERT, Dorset House, Stamford St., London SE1 9LU

Please send me copy/copies of Colour Faults Guide at £1.65 inclusive.

I enclose remittance value £ (Cheques payable to IPC Business Press Ltd.)

Name (please print)

Address

Company regd. in England No. 677128
Regd. office: Dorset House, Stamford St., London SE1 9LU

OUR ALL SINGING, ALL DANCING MODEL! FLIGHT LINK CONTROL LTD. 01-570 4065



"Coppelia" — shown on "Tomorrow's World" by master puppeteer Martin Granger.

You're a professional puppeteer, and you need a 16 function radio control system, including miniature proportional servos, for a self-contained puppet?

CONTACT FLIGHT LINK!

You need 200 precise reliable long life dual axis joystick controllers every month, starting next month?

CONTACT FLIGHT LINK!

You're a Hi-Fi specialist building a music room for an Arab Sheik — and you want a one-off remote control system?

CONTACT FLIGHT LINK!

You're building a 30 foot dia. demonstration model of a new airship and you want a radio control system in 14 days?

CONTACT FLIGHT LINK!

You're planning a submersible reconnaissance vehicle for the North Sea, and you want joystick controllers, plus 30-way analogue multiplex system to send all the controls along one conductor?

CONTACT FLIGHT LINK!

You're planning a 12-boat coin-operated radio control attraction for a seaside promenade and you want a GPO approved system?

CONTACT FLIGHT LINK!

Your Middle East customer requires radio-controlled target drones?

CONTACT FLIGHT LINK!

Your ship hull model requires control and telemetry equipment?

CONTACT FLIGHT LINK!

You need to speed control a 48v 1/2hp D.C. motor from reverse through stop to full ahead? **CONTACT - FLIGHT LINK!**

We have 12 years experience of remote control equipment of all kinds. Our standard products include joysticks, miniature DC servos, 2 to 30 way multiplex systems (radio and cable), motor speed controllers, high quality RF links, etc. and we are happy to supply anything from one transistor to a complete system costing many thousands of pounds. Whatever your problem in control systems — ask us to solve it for you quickly at surprisingly low cost. Don't write for standard literature — our products are so varied there isn't much. Ring us!

**FLIGHT LINK CONTROL LTD., BRISTOW WORKS
BRISTOW ROAD, HOUNSLOW, MIDDX. 01-570 4065**



FLC Dual and Triple axis joysticks

Our noise reducer is something to shout about!



Wireless World Dolby noise reducer

Complete kits for the *Wireless World* Dolby B noise reducer are available through the address given below. The two-channel design features:

- a weighted noise reduction of 9dB
- switching for both encoding (low-level h.f. compression) and decoding
- a switchable f.m. stereo multiplex and bias filter
- provision for decoding Dolby f.m. radio transmissions (as in USA)
- no equipment needed for alignment
- suitability for both open-reel and cassette tape machines
- check tape switch for encoded monitoring in three-head machines

The kit includes:

- complete set of components for a stereo processor
- regulated power supply components
- board-mounted DIN sockets and push-button switches
- fibreglass board designed for minimum wiring
- solid mahogany cabinet, chassis, two meters, front panel, knobs, mounting screws and nuts.

Price is £43 inclusive.

A single-channel printed-circuit board, with f.e.t. costs £2.50 or £8.63 with all components inclusive (excluding edge connector, £1.37 extra). Selected field-effect transistors cost 68p each inclusive, £1.20 for two and £2.20 for four.

Calibration tapes are available, costing £1.94 inclusive for 9.5cm/s open-reel use and for cassette (specify which).

Send cash with order, making cheques payable to IPC Business Press Ltd, to: Wireless World noise reducer General sales department Room 11, Dorset House Stamford Street London SE1 9LU

DOLBY KIT ORDER FORM

Please supply me with the complete Wireless World kit for a Dolby noise reducer.

I enclose remittance value £43.00 inclusive

Name

Address

Additional items required

I enclose remittance value £ payable to I.P.C. Business Press Ltd.

RST VALVE MAIL ORDER CO.

16a Wellfield Rd., London, SW16 2BS
Tel: 01-677 2424 Telex: 946 708.

VALVES										INDUSTRIAL VALVES																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
ECH35 1.50	EZ80 0.30	PEN45DD	UCL83 0.70	6CD6G 1.60	12BH7 0.60	6060	CV131	CV3986	EF54	OD1	6061	CV132	CV3988	EF55	OD3	6062	CV133	CV3991	EF56	OZ4	6063	CV134	CV3998	EF804	OZ24A	6064	CV135	CV4001	EL91	PT15	6065	CV136	CV4002	EN30		6066	CV137	CV4003	EN31	QA2400	6067	CV138	CV4004	EN32	QA2403	6068	CV139	CV4005	EN91	QA2404	6069	CV140	CV4006	ESU74	QA2406	6070	CV141	CV4007	ESU76	QA2407	6071	CV142	CV4008	ESU77	QB3300	6072	CV143	CV4009	F6057	Q515-750	6073	CV144	CV4010	F6058	Q6080	6074	CV145	CV4011	F6059	Q84-1100	6075	CV146	CV4012	F6061	QF41	6076	CV147	CV4013	F6062	QF45	6077	CV148	CV4014	F6063	QV02-6	6078	CV149	CV4015	F6064	QV03-10	6079	CV150	CV4016	F6065	QV03-20A	6080	CV151	CV4017	F6066	QV03-40	6081	CV152	CV4018	F6067	QV04-10	6082	CV153	CV4019	F6068	QV06-40A	6083	CV154	CV4020	F6069	G102/10B	6084	CV155	CV4021	F6070	G150/2B	6085	CV156	CV4022	F6071	G180/2M	6086	CV157	CV4023	F6072	G240/2D	6087	CV158	CV4024	F6073	G400/1K	6088	CV159	CV4025	F6074	G500/1K	6089	CV160	CV4026	F6075	G500/1K	6090	CV161	CV4027	F6076	G500/1K	6305	CV376	CV4242	F6291	G500/1K	6306	CV377	CV4243

Fashionable Leatherwear

A Wireless World special offer

We show four models from our new range of top grade leather clothing. Hand-cut by craftsmen, these soft, light and supple garments are a pleasure to wear and will give years of service. Items are exchangeable, warranted for six months under fair wear and tear and carry a money-back guarantee if returned unworn within seven days of receipt. They are easily cleaned at specialist cleaners — we will recommend one if required. This special price offer closes on 31st January, 1976.

JB 53 A stylish Norfolk jacket, fully lined and incorporating a number of distinctive features. Available in pigskin (illustrated), leather or suede. Colours: **Pigskin**—Pastel Blue, Golden Tan, Truffle; **Leather**—Golden Brown, Dark Brown, Maroon, Bottle Green, Dark Blue, Black; **Suede**—Pastel Blue, Beige, Avocado Green, Milk Chocolate Brown, Dark Brown.

JB 265 A smart, suede-fronted cardigan, lined inside, twin pockets, single breasted fastening and featuring a detachable collar. An ideal 'all round' leisure garment. Colour: Dark Brown.

JB 304 A distinctive men's full length (41in) sheepskin coat which is both luxurious and hard wearing. Leather bound, large feature collar, double breasted styling with leather buttons and vertical slit-pockets in seams. For the man who wants style and comfort without being too "trendy". Colours: White Wool/Mid-Brown, 2-tone Brown.

JB 307 A classic sheepskin coat for men. Leather bound edges, twin pockets and side vents, inset sleeves, single breasted styling. Colour: 2-tone Brown.




(JB 307)



(JB 53)



(JB 304)

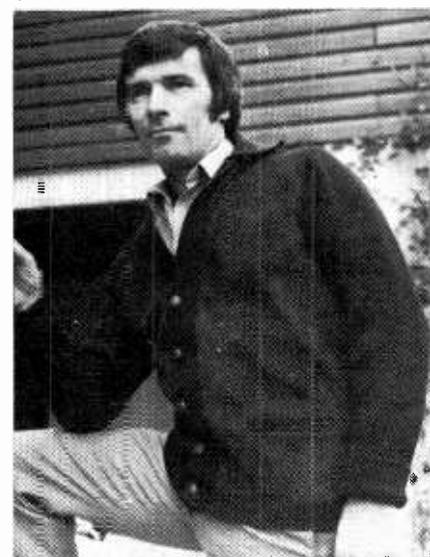

(JB 265)

SIZES: Chest measurement in inches	Extra		Approx. Ret. Value
	34-42	44-46	
PRICE CHART			
JB 53	£56.80	£59.99	£80.00- £85.00
JB 265	£15.93	£17.37	£25.00- £27.00
JB 304 White/M. Brown	£90.59	£96.07	£130.00-£145.00
2-tone Brown	£100.98	£107.32	
JB 307	£70.28	£75.76	£90.00- £95.00

SPECIAL OFFER CATALOGUE

We are able to supply a wide range of leather, suede, pig-skin and sheepskin coats, dresses, skirts, tunics, jackets, rugs, seat covers at preferential prices. Please tick box on order form to receive free catalogue and price list.



(JB 256)

To: Wireless World Offers
GPO Topsham, Topsham, Devon

Please send me the following items:

Style No.	Size	Colour	Finish	Price
.....
.....
.....

I enclose cheque/P.O. value £.....

Please send me your free catalogue (tick if required)

NAME (please print)

ADDRESS

.....

.....

Prices include postage, packing and VAT. Cheque or PO payable to Wireless World Special Offers must accompany all orders for goods. Offer applies to U.K. only. Allow 28 days for delivery.

Registered in England No. 677128 and a subsidiary of Reed International Limited.
Regd. Office: Dorset House, Stamford Street, London SE1 9LU



POWER RESISTORS

EX STOCK to 6 weeks Delivery

- * Low cost
- * Rated up to 210 watts
- * Custom designs are our speciality

Data on our standard ranges is available on request

Erg Components Telephone: 0582-62241
Luton Road, Dunstable, Bedfordshire, LU5 4LJ, England.

WW-069 FOR FURTHER DETAILS


NEW! AMERICAN STYLE CRADLE TELEPHONE AMPLIFIER



ONLY
£12.95
+ VAT £1.04

Latest transistorised Telephone Amplifier is completely automatic with detachable plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the hand-set. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting. On/Off switch, volume control. Model with tape-recording facility £13.95 + VAT £1.12 P. & P. 70p. C.W.O. 10-day price refund guarantee.

NEW IMPROVED MAINS INTERCOM

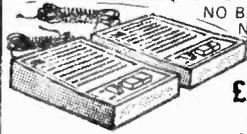

NO BATTERIES
NO WIRES

ONLY
£24.99
per pair
+ VAT £6.25

Made to British Safety and Telecommunications Standards. The modern way of instant 2-way communications. Supplied with 3-core wire. Just plug into power socket. Ready for use. Crystal clear communications from office to office. Operates over ¼-mile range on the same mains phase. On/off switch. Volume control. Useful as office intercom, surgery and hospitals, between office and warehouse. No GPO licence required. Full price refund if returned in 10 days. **Six months' service guarantee.** P. & P. 75p.

WEST LONDON DIRECT SUPPLIES (W/W)
169 Kensington High Street, London W.8

Audio Connectors



Broadcast pattern jackfields, jackcords, plugs and jacks.

Quick disconnect microphone connectors
Amphenol (Tuchel) miniature connectors with coupling nut.

Hirschmann Banana plugs and test probes
XLR compatible in-line attenuators and reversers.

Low cost slider faders by Ruf.

Future Film Developments Ltd.
90 Wardour Street
London W1V 3LE
01-437 1892/3

WW-081 FOR FURTHER DETAILS

Now the European electronics industry is an open book

It's the European Electronics Suppliers Guide—the only reference book of its kind you can buy.


(And, in fact, the only multi-lingual, multi-national buyers guide in the electronics world.)

Every feature is designed to take you fast to the name of the supplier you need, whatever the country, whatever the product concerned.

Products and manufacturers are broken down into 26 distinct market sectors. Over 600 types of products are listed, cross-referenced with over 1700 manufacturers. Principal Trade Associations in every country are included too. And all essential information appears in three languages—English, German and French.

The price is £18.50, including post and packaging. Not much for opening up a continent.

Post this coupon—with your cheque—today.

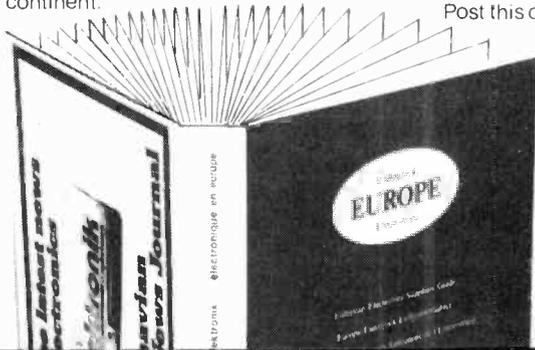

To: General Sales Dept., IPC
Electrical-Electronic Press Ltd., Room 11,
Dorset House, Stamford St., London
SE1 9LU, England.

Please send me a copy of The European
Electronics Suppliers Guide. I enclose
cheque/money order for £18.50 (100
Swiss Francs) inclusive.

Name _____

Address _____

*Cheques should be made payable to IPC
Business Press Ltd.

Registered in England, No. 677128
Registered Office: Dorset House, Stamford
Street, London SE1 9LU, England.

BI-PRE-PAK Makers of Stirling Sound audio equipment

The people for component bargains

ORIGINATORS OF PRE-PACKED COMPONENTS IN BRITAIN — AND STILL LEADING!

YOUR CHANCE STILL TO SAVE £12

ON THIS MODULAR STEREO FM/AMP ASSEMBLY

- * TOTAL VALUE AT REGULAR ADVERTISED PRICE (INC. VAT) **£30**
- * ALL 4 UNITS PURCHASED TOGETHER INC. VAT & P&P IN U.K. **£18**
- * IF YOU BUY UNITS SEPARATELY YOU STILL SAVE **33 1/3%**
- * ORDER NOW FOR DELIVERY BY RETURN

1. THE FRONT END

Ganged tuning: AFC facility. Reduction-gear drive. 88-108 MHz.

Usual price inc. VAT **£8.01** **£5.34**

3. STEREO DECODER USING I.C.

Designed for use with the above modules, can also be used with other mono F.M. tuners. Ready aligned. (L.E.D. for stereo beacon available at 18p.)

Usual price inc. VAT **£7.22** **£4.82**

2. THE I.F. BOARD

Using I.C. Designed for use with above front end.

Usual price inc. VAT **£6.76** **£4.50**

4. 5 + 5 WATT MUSIC POWER I.C. AMPLIFIER

Useful stereo power amplifier with good performance, at economy price

Usual price inc. VAT **£8.01** **£5.34**

3 SPECIAL OFFERS

- LM 380 AUDIO IC** (Marked 60745). Brand new and to spec. 3 watts R.M.S. out. With data. **75p**
- Three SN 7490**. Brand new I.C. to spec. decode counters. **3 for £1.20** (8%)
- Five SN 7400** Quad 2 input Nan gate ICs. **60p** (8%)

SUNDRY

P.I. PAK — Approx. 170 short-lead semi-conductors and components. PNP, NPN, diodes, rectifiers, etc. on ex-computer panels. At least 30% factory marked. Some data supplied. **50p**.
 UHF 625 line tuner, rotary **£2.50**.
 Rev Counter (for cars) (8%) **£1.00**.
 Books by Bernard's Publications, Newnes-Butterworth's, etc.

NEW RANGE TRANSISTOR & COMPONENT PACKS

TP SELECTION

- TP5** 20 Transistors, PNP Germanium, Red Spot A.F.
- TP6** 20 Transistors, PNP Germanium, White spot RF
- TP7** 1 2N174 150w 80Vce Power Transistor, with mounting assembly.
- TP19** 100 diodes, mixed Germanium, Gold-bonded, etc. Marked/Unmarked.
- TP23** Twenty NPN Silicon uncodded T05. Similar to BFY50/2, 2N696, 2N1613, etc. Complementary to TP24
- TP24** Twenty PNP Silicon, uncodded T05. Similar to BFY64, 2N2904/5
- TP29** 8 power diodes 400V, 1.25A Silicon FST 3/4.

UT SELECTION

- UT1** 50 PNP's Germanium, AF & RF.
- UT2** 150 Germanium diodes, min. glass
- UT4** 100 Silicon diodes, min. glass, similar to IN914, IN916.
- UT5** 40 250mW Zener diodes OAZ 240 range, average 50% good.
- UT7** 30 Silicon rectifiers 750mA, mixed voltages, Top Hats, etc.
- UT9** 40 NPN Silicon planers. Similar to 2N3707-11 range. Low noise amps
- UT12** 10 2N3819 N channel FETs, plastic case type

CP SELECTION

- CP1** Mixed bag of capacitors — Electrolytic, Paper, Silver Mica (Approx. 150 — sold by weight).
- CP2** 200 (approx.) Resistors, various types, values, watts. (Sold by weight.)
- CP3** 40 Wire-wound resistors, mixed.
- CP4** 12 pots — pre-set, w/wound, carbon, dual, with/without switches — all mixed.
- CP7** Heat sinks, assorted. To fit SO-2 (OC72) TO-1 (AC128), etc.

ALL ABOVE PACKS — 60p EACH, TP Tested & Guaranteed, UT Untested, unmarked, CP Components.

CAPACITOR DISCHARGE IGNITION UNIT

Simple to assemble and fit. Improves car performance. saves on fuel. P/P 50p. **Kit £7.95, Built £10.50***

BI-PRE-PAK X-HATCH GENERATOR MK. 2



Four-pattern selector switch 3" x 5 1/4" x 3"
Ready-built and tested £9.93*
In kit form £7.93*

Please add 50p for postage and packing. Is invaluable to industrial and home user alike. Improved circuitry assures reliability and still better accuracy. Very compact, self-contained. Robustly built. Widely used by TV rental and other engineers. With reinforced fibreglass case, instructions, but less batteries. (Three U2 type required.)

TV SIGNAL STRENGTH METER*

Complete kit as described in "Television" £19.50 plus 40p for P&P

SS300 POWER SUPPLY STABILISER

Add this to your unregulated supply to obtain a steady working voltage from 12 to 50V for your audio system, workbench, etc. Money saving and very reliable. **£3.25***

PLASTIC POWER TRANSISTORS

40 WATT SILICON				
Type	Polarity	Gain	VCE	Price
40N1	NPN	15	15	20p
40N2	NPN	40	40	30p
40P1	PNP	15	15	20p
40P2	PNP	40	40	30p

90 WATT SILICON				
Type	Polarity	Gain	VCE	Price
90N1	NPN	15	15	25p
90N2	NPN	40	40	35p
90P1	PNP	15	15	25p
90P2	PNP	40	40	35p

THE FREE CATALOGUE

New edition better than ever. It's yours for free and well worth getting — only please send large S.A.E. with 10p stamp if we have to post it to you.

V.A.T. — IMPORTANT

Rates quoted in good faith in accordance with Customs & Excise rulings. In the event of overpayment by customers the difference will be credited.

TERMS OF BUSINESS:

VAT at 25% must be added to total value of order, except for items marked or (8%) when VAT is to be added at 8%. No VAT on overseas orders. **POST & PACKING** Add 20p for UK orders except where shown otherwise. Minimum mail order acceptable — £1. Overseas orders, add £1 for postage. Any difference will be credited or charged. **PRICES** Subject to alteration without notice. **AVAILABILITY** All items available at time of going to press when every effort is made to ensure correctness of information.

BI-PRE-PAK LTD

Co Reg. No R27019

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.

TELEPHONE: SOUTHEND (0702) 46344.

If you prefer not to cut coupon out please mention WW1 when writing

To BI-PRE-PAK, 222-224 WEST ROAD WESTCLIFF-ON-SEA, ESSEX SSO 9DF

Please send

for which I enclose

inc VAT

NAME

ADDRESS


WW1

For all who want to know about electronic circuits

Here's a book of very special appeal to all concerned with designing, using or understanding electronic circuits. It comprises information previously included in the first ten sets of Wireless World's highly successful Circards – regularly published cards giving *selected* and *tested* circuits, descriptions of circuit operation, component values and ranges, circuit limitations, modifications, performance data and graphs. Each of the ten sets – including additional circuits – in this magazine size hard cover book has been updated where necessary, and is preceded by an explanatory introduction. Circuit designs (1) is the first collection of its kind.

Circuits covered are:

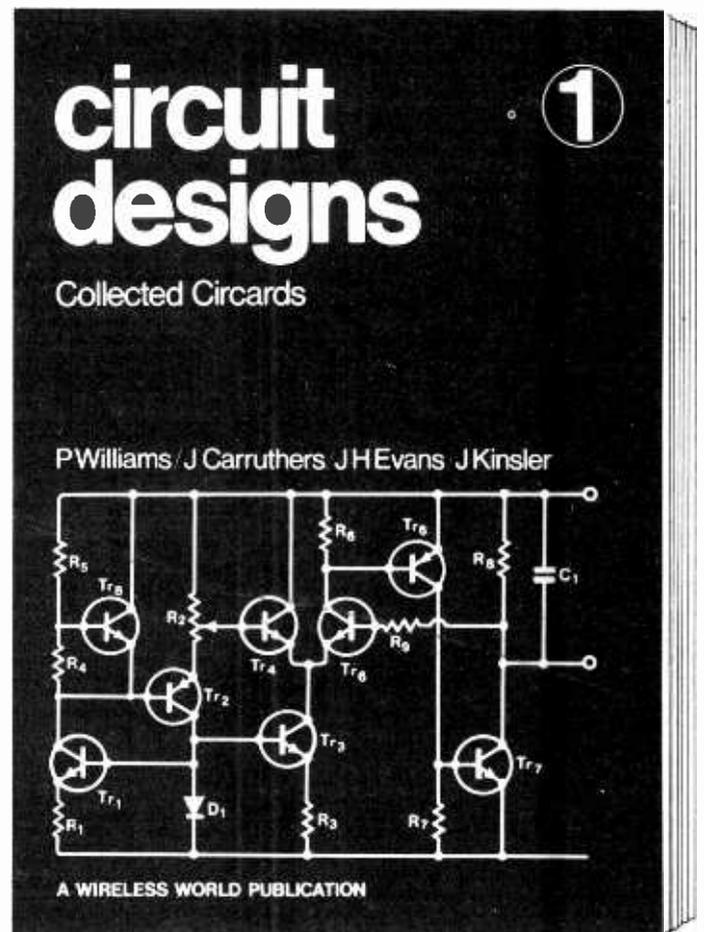- Basic active filters**
- Switching circuits**
- Waveform generators**
- AC measurements**
- Audio circuits**
- Constant-current circuits**
- Power amplifiers**
- Astable circuits**
- Optoelectronics**
- Micropower circuits**



A new book from Wireless World

ORDER FORM

To: General Sales Department,
IPC Business Press Limited,
Room 11, Dorset House,
Stamford Street, London SE1 9LU.

Please send me copy/copies of
Circuit Designs – Number 1 at £10.40
each inclusive. I enclose remittance
value £. (cheques payable to
IPC Business Press Ltd.)

NAME (please print)

ADDRESS

Company registered in England and a subsidiary of Reed
International Limited Registered No 677128 Regd. office
Dorset House, Stamford Street, London SE1 9LU.

Don't buy Test Equipment

Until you've sent off for our Test Equipment Catalogue



If you are in the market for Test Equipment, you owe it to yourself and your Company to find out all about Electronic Brokers Ltd.

We have the largest stocks of Second Hand Test Equipment in Europe as well as a selected range of new products.

Our present customers include: GEC-Marconi, Plessey, ICAO, NPL, British Rail, Post Office and various Government Departments at home and abroad.

Electronic Brokers' comprehensive catalogue of Test Equipment offers big savings in cost and time.

Send 50p towards printing, postage, etc. (Overseas customers £1) and a catalogue will be sent by return.

Electronic Brokers Ltd. will then keep the catalogue updated by forwarding monthly revision sheets free of charge.

ELECTRONIC BROKERS LTD.

The Test Equipment People

49-53 Pancras Road, London NW1 2QB

Tel. 01-837 7781



A MEMBER OF THE EB GROUP OF COMPANIES

TELETYPE 28 — NEW SPECIAL PRICE

TELETYPE 28 without keyboard. Good condition (can be used as receive only) **£32.50** ea.

TELETYPE 28 with housing, keyboard and Power supply **£45** ea.

Limited quantities — information in process of being obtained — this may not be available when orders are dispatched but we guarantee to forward comprehensive information at the earliest possible time.

POLARAD SPECTRUM ANALYZER

Type TSA covering 10MHz-1 GHz: 25KHz resolution. **£325**.

Can be extended to 44GHz with additional plug-in units at nominal cost.

MARCONI Signal Generator. TF801B 12.470MHz **£120** ea.

MARCONI Valve Voltmeter type TF1041B **£45**.

MARCONI TF934/2 FM Deviation Meter **£35**.

MARCONI TF1020A RF Power Meter 150 and 300 Watts. As New. **£60** ea.

MARCONI TF1020A RF Power Meter 50 and 100 Watts. As New. **£45** ea.

MARCONI TF1094A/S HF Spectrum Analyser. Late model. Must go. **£160**.

MARCONI TF1434/2 Counter Range extension unit 10-100MHz **£25** ea.

KELVIN & HUGHES Single Channel Recorders with spare paper **£18** ea.

FURZEHILL Valve Voltmeter V200. 10mv full scale. **£18** ea. Nice condition.

NOT OUR SCENE — Engraver
Buck & Hickman - £75

MARCONI OSCILLOSCOPES
TF1330 - DC - 15MHz. Single Beam. **£65** ea.
TF 1331 - DC - 15MHz. Double Beam. **£85** ea.

RHODE & SCHWARZ Admittance Meter VLUK-BN3511. As new, **£110**.

BRUEL & KJOER Voltmeter type 2409 2 cs to 200k/cs. **£85** ea.

DUAL TRACE PLUG-IN units for CD1212 Scopes DC-24MHz **£35** ea.

TELONIC Sweep Generator SM2000/1. Main frame with 0-20kHz plug-in **£300**.

TEKTRONIX Oscilloscope type 516 **£240**.

MARCONI TF 455E Wave Analyser. Excellent condition. **£55** ea.

MARCONI TF 867 Signal Generator 15KHz to 30MHz. **£50** ea.

MARCONI TF 885 Video Oscillator. **£30** ea.

MARCONI TF 791D Deviation Meter. **£90**.
MARCONI TF 791C Deviation Meter. **£60**
MARCONI TF1370 R.C. Oscillator. **£80**.

MARCONI TF1245A Circuit Magnification Meter with TF1246. **£140**.

EDDYSTONE RECEIVER type 770U. **£90**

ROHDE & SCHWARZ Receiver ESM180 BN 15073/2. **£425**.

ROHDE & SCHWARZ Generator 300-1000 MHz. Type SDR BN 41022. **£300**.

FLANN Signal Generator type 501 0.8-3 GC/S **£90** ea.

DATAPULSE Generator 101 by Systron-Donner Corporation. **£90** ea.

★ AB POTENTIOMETERS
100K + 100K LIN DUAL GANG **25p** ea.
Discount for quantities. P. & P. extra

EX-MINISTRY CT436 Double Beam Oscilloscope DC-6 megs. Max Sensitivity 10mv/cm. Small compact. Size 10 x 10 x 16 in. Suitable for Colour TV servicing. Price **£85** each including copy of manual.

FHACHI RAMP MODULE FX21 24 Volt DC input for 18 volt saw tooth output. Requires only external capacitor and 100K ohm potentiometer to control frequency range up to 100KHz (eg 50 mfd electrolytic gives sweep of approx. 1 cm per second). In or out sync capability. Price **£5.75**. P. & P. 20p.

★ TELEPHONES

MODERN STYLE 706 BLACK OR TWO-TONE GREY **£3.75** ea. P. & P. 45p.

STYLE 7006 TWO-TONE GREEN OR GREY **£3.75** ea. P. & P. 45p.

HANDSETS—complete with 2 insets and lead **£1.25** ea. P. & P. 37p.

DIALS ONLY. **50p** ea. P. & P. 30p.

STILL AVAILABLE MODERN STANDARD TELEPHONES IN GREY OR GREEN WITH A PLACE TO PUT YOUR FINGERS LIKE THE 746. **£3.00** ea. P. & P. 45p.

***CAPACITOR PACK** 50 Brand new components only **50p**. P. & P. 27p.

***P.C. MOUNT SKELETON PRE-SETS**. Screwdriver adjust 10, 5 and 2.5M Ω **2p** ea.

1M, 500, 250 and 25K Ω **4p** ea. Finger adjust 10, 5 and 2.5M Ω **3p** ea. 1M, 500, 250 and 25K Ω **5p** ea. Min. P. & P. 15p.

***Beehive Trimmer 3/30 pf.**

Brand new. Qty 1-9 **13p** ea. P. & P. 15p; 10-99 **10p** ea. P. & P. 25p; 100-999 **7p** ea. P. & P. free.

DELIVERED TO YOUR DOOR 1 cwt. of Electronic Scrap chassis boards, etc. No Rubbish. For ONLY **£4.50**. N. Ireland \pm 2 extra P.C.B. **PACK S & D**. Quantity 2 sq. ft.—no tiny pieces. **50p** plus P. & P. 25p.

***TRIMMER PACK**, 2 Twin 50/200 pf ceramic; 2 Twin 10/60 pf ceramic; 2 min strips with 4 preset 5/20 pf on each; 3 air spaced preset 30/100 pf on ceramic base. ALL BRAND NEW.

***PHOTOCCELL** equivalent OCP71. **13p** ea.

GRATICULES. 12 cm. by 14 cm. in High Quality plastic. **15p** each. P. & P. 8p.

***Vast quantity of good quality components — NO PASSING TRADE — so we offer**

3 LB. of ELECTRONIC GOODIES

for **£1.70** post paid

HF Crystal Drive Unit. 19 in. rack mount. Standard 240V input with superb crystal oven by Labgear (no crystals) **£5** ea. Carr. **£2**.

BOURNS TRIMPOT POTENTIOMETERS. 20: 50; 100; 200; 500 ohms; 1, 2; 2.5; 5, 10; 25k at **35p** ea. ALL BRAND NEW.

RELIAANCE P.C.B. mounting. 270: 470; 500 ohms; 10K at **35p** ea. ALL BRAND NEW.

TENTURN POTS. Ex. equ. As new. Micropot Model 205. Two point nine ohms 0.1% @ **£1.50** ea P&P 20p.

Bourns Model 3507S-3-101. 100 ohms **£1.25** ea. P&P 15p.

VENNER Hour Meters—5 digit. wall mount —sealed case. Standard mains. **£3.75** ea. P. & P. 55p.

TRANSFORMERS. All standard inputs. Gard/Param/Part 450-400-0-400-450. 180 MA. 2 x 6.3v. **£3** ea.

FANTASTIC VALUE

Miniature Transformer. Standard 240V input. +3V 1 amp output. Brand New. **65p** ea. P. & P. 20p. Discount for quantity.

FIBREGLASS PRINTED CIRCUIT BOARD. Brand New. Single or Double sided. Any size **13p** per sq. in. Postage 20p per order.

***HIGH VALUE PRINTED BOARD PACK**, no two boards the same—no short leaded computer boards. **£1.75** post paid.

***METER PACKS**—3 different meters for **£2**. P. & P. 55p.

RESETTABLE COUNTERS—4 digit by Stonebridge/Sodeco. 1,000 ohm coil. **£2** ea. P. & P. 35p.

E.H.T. CAPACITORS

1 mfd 7.5KV working. 2 mfd 5KV working. 8 mfd 2.5KV working 0.5 mfd 10KV working **£2** each.

RAPID DISCHARGE

1 mfd 5.6KV **£2.50** ea. 0.9 mfd 15KV **£3.50** ea. 0.15 mfd 120KV **£7** ea. Carriage extra.

FHACHI VCC MODULE

FX11—10HZ-100KHZ
Size 2 x 1 1/4 x 3/4" H. Input 12V to 24V DC (not centre tapped) 18V input giving 10V constant amplitude output. Requires only a 1 meg ohm potentiometer to tune entire range — or can be swept with a saw tooth input. Price **£5.75**. P. & P. 20p.

DON'T FORGET YOUR MANUALS S.A.E. WITH REQUIREMENTS

LOW FREQUENCY WOBBLATOR
For alignment of Receivers, Filters, etc. 250KHz to 5MHz, effective to 30MHz on harmonics. Three controls—RF level, sweep width and frequency. Order LX63. Price **£8.50** P. & P. 35p.
As above but can have extended cover range down to 20KHz by addition of external capacitors. Order LX63E. Price **£11.50** P. & P. 35p.
Both models can be used with any general-purpose oscilloscope. Requires 6.3V AC input. Supplied connected for automatic 50Hz sweeping. An external sweep voltage can be used instead. These units are encapsulated for additional reliability, with the exception of the controls (not cased, not calibrated).

20HZ to 200KHZ SINE AND SQUARE WAVE GENERATOR

In four ranges. Wien bridge oscillator thermistor stabilised. Separate independent sine and square wave amplitude controls. 3V max sine 6V max square outputs. Completely assembled P.C. Board, ready to use. 9 to 12V supply required. **£8.85** each. P. & P. 25p. Sine Wave only **£6.85** each. P. & P. 25p.

WIDE RANGE WOBBLATOR

5 MHz to 150 MHz (Useful harmonics up to 1.5 GHz) up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10:7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6.3V AC and use within minutes of receiving. All this for only **£6.75**. P. & P. 25p. (Not cased, not calibrated.)

TRANSISTOR INVERTORS

TYPE A Input: 12V DC Output: 1.3kV AC 1.5MA Price £3.45	TYPE B Input: 12V DC Output: 1.3kV DC 1.5MA Price £4.70	TYPE C Input: 12V to 24V DC Output: 1.5kV to 4kV AC 0.5MA Price £6.35	TYPE D Input: 12V to 24V DC Output: 14kV DC 100 micro amps at 24V. Progressively reducing for lower input voltages Price £11
Postage & Packing 36p			

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2 HZ to 8 MHz. Hook up a 9 volt battery and connect to your scope and have two traces for ONLY **£6.25**. P. & P. 25p.
STILL AVAILABLE our 20 MHz version at **£9.75**. P. & P. 25p.

Unless stated — please add **£2.00** carriage to all units.

VALUE ADDED TAX not included in prices—Goods marked with ★ 25% VAT, otherwise 8% Official Orders Welcomed, Gov./Educational Depts., Authorities, etc., otherwise Cash with Order

Open 9 a.m. to 5.30 p.m. Mon. to Sat.



CHILTMHEAD LTD



7/9 ARTHUR ROAD, READING, BERKS. (rear Tech. College, Kings Road)

Tel.: Reading 582605

Appointments

Advertisements accepted up to
12 noon Monday, December 29,
for the February issue subject
to space being available.

DISPLAYED APPOINTMENTS VACANT: £6.99 per single col. centimetre (min. 3cm).
LINE advertisements (run on): 99p per line (approx. 7 words), minimum three lines.
BOX NUMBERS: 40p extra. (Replies should be addressed to the Box numbers in the
advertisement, c/o Wireless World, Dorset House, Stamford Street, London SE1 9LU).
PHONE: Allan Petters on 01-261 8508 or 01-261 8423.

Classified Advertisement Rates are currently zero rated for the purpose of V.A.T.

KING'S COLLEGE HOSPITAL MEDICAL SCHOOL

(University of London)

Denmark Hill, London, SE5 8RX

ENGINEERING IN MEDICINE ELECTRONICS TECHNICIAN

A vacancy exists within the Department of Biomedical Engineering for an Electronics Technician to join a multidisciplinary team engaged on research into the application of engineering to medicine. The successful applicant will be involved in the development, construction and maintenance of electronic signal processing systems using both analogue and digital techniques. Applicants should have some relevant experience and preferably possess an HNC or equivalent in electronics as a minimum.

The post is tenable for one year in the first instance but is renewable up to a maximum of three years. Initial salary will be within the range £2823-£4050, including London Allowance, commensurate with experience and qualifications.

RESEARCH STUDENTSHIP

A second vacancy exists within the Department for a Research Student to work on a project, funded by the Department of Health and Social Security, on non-invasive methods of measuring blood flow and cardiac function. Applicants should possess a first or second class degree in physics, electrical or mechanical engineering, or an equivalent qualification.

The successful applicant will join a multidisciplinary team which has been active in the field of haemodynamics and flow measurement for several years, and will be expected to register for a higher degree. The post is tenable for one year in the first instance but is renewable up to a maximum of three years. Salary will be in accordance with the normal SRC Research Studentship scales and will depend on age and qualifications.

Further information on both of these posts may be obtained from The Secretary, King's College Hospital Medical School, to whom applications, giving details of age, qualifications and experience, together with the names and addresses of two referees, should be sent as soon as possible quoting reference WW (5028)

SHEFFIELD POLYTECHNIC

DEPARTMENT OF HISTORY AND
COMMUNICATION STUDIES

TECHNICAL OFFICER

required immediately to be responsible for the Communications Laboratory of the Department of History and Communication Studies. The successful applicant's duties will include the installation, operation and maintenance of CCTV video/audio and some linguistic and psychological equipment. It is hoped that the technician will play a role in short courses on television familiarisation and practical video workshops.

An appropriate qualification in electronics would be an advantage as would previous television and educational experience.

Salary scale T1 1215-2529 plus qualification allowance.

Application forms and further details obtainable from the Personnel Officer, Sheffield Polytechnic, Halfords House, Fitzalan Square, Sheffield S1 2BB, to whom completed forms should be returned within fourteen days.

TECHNICAL OPERATIONS MANAGER (TELEVISION SERVICE)

£3546-£3882

For the Education Television Unit of Guildford County College of Technology. To be responsible for the daily operations of a team of technicians concerned with production and presentation of ETV material.

The successful applicant will have a sound knowledge of closed-circuit television systems including colour, together with experience of helical-scan recorders and vidicon cameras. Organising ability important as is an interest in the development of television and other audio-visual equipment as teaching aids.

Salary quoted inclusive — starting point depending on age, qualifications and experience.

**Application form and details from the Vice Principal,
Guildford County College of Technology, Stoke Park,
Guildford, Surrey. Tel: Guildford 73201, Ext. 41.**



SURREY COUNTY COUNCIL

(5029)

AMPEX


WANTED Field Service Engineers

- IF YOU —
- Have at least five years' experience in a maintenance capacity with a professional broadcast television system . . .
 - Have at least three years' maintenance experience on quadruplex videotape recorders . . .
 - Have maintenance or installation experience on broadcast quality colour television systems . . .
 - Are interested in basing yourself in sunny Greece . . .
 - Are interested in travelling extensively in the African and Middle East countries, and working without direct supervision . . .
 - Are interested in being trained on state of the art third generation videotape and colour camera equipment for installation commissioning and maintenance services at our customer sites . . .

THEN WRITE TO OUR Service Manager, Ampex World Operations, SA, P.O. Box 45, Halandri (1) Athens, Greece (Include your telephone number).

- WE—
- Assist with relocation expenses for yourself and immediate family . . .
 - Assist with local schooling expenses . . .
 - Provide a medical insurance coverage . . .
 - Provide a Pension Scheme after a qualifying period . . .
 - Offer an interesting salary.

(5041)

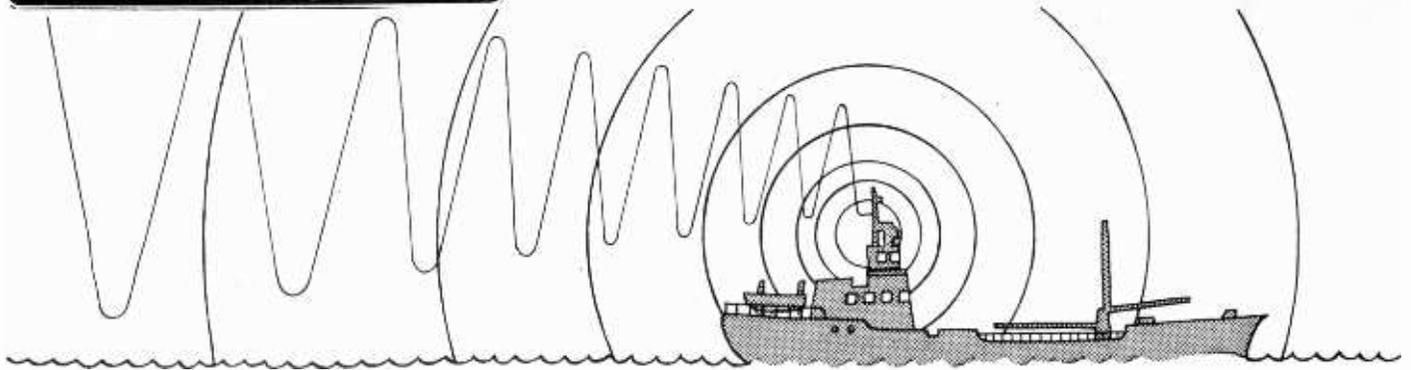

Radio Officers—now you can enjoy the comforts of home.

Working for the Post Office Maritime Services really makes sense. You still do the work that interests you, but with all the advantages of a shore-based job: more time to enjoy home life, job security and good money. To qualify, you need a United Kingdom Maritime Radiocommunication Operator's General Certificate or First Class Certificate of competence in Radiotelegraphy, or an equivalent certificate issued by a Commonwealth Administration or the Irish Republic.

Starting salaries, at 25 or over, are £2905 rising to £3704 after three years service. Between 19 and 24, the starting salary varies from £2234 to £2627

according to age. You'll also receive an allowance for shift duties which at the maximum of the scale averages £900 a year and there are opportunities to earn overtime. There's a good pension scheme, sick pay benefits and prospects of promotion to senior management.

Right now we have vacancies at some of our coastal radio stations, so if you're 19 or over, write to: ETE Maritime Radio Services Division (R/B/1), ET 17.1.1.2., Room 643, Union House, St. Martins-le-Grand, London EC1A 1AR.

Post Office Telecommunications

93



Wideband Radio Assistant Project Engineer

£3700 - £4500

The CABLE AND WIRELESS Group, leaders in global telecommunications, has an interesting career opening for a young Wideband Radio Engineer.

Based at our central London Head Office, there will be short periods spent elsewhere in the UK and overseas. Duties will include specifying, evaluating, and testing wideband radio equipment and systems; also cost estimating and detailed engineering planning.

Applicants should have had experience of equipment and system design or installation planning work on UHF, microwave and tropospheric scatter systems.

Excellent conditions of service are offered, with commencing pay of between £3700 p.a. and £4500 p.a. including allowances, on career sales rising to over £6000 p.a. Generous leave and pension arrangements. Sports and Social Club.

Please write or telephone for an application form to:



CABLE & WIRELESS

Personnel Officer (Recruitment),
Cable and Wireless Limited,
Dept. A.18/447,
Theobalds Road, LONDON, WC1X 8RX.
TEL: 01-242 4433 Ext. 211.

ELECTRONICS ENGINEER

We manufacture a range of highly sophisticated scientific instruments of advanced design embodying many aspects of the electronic art ranging from high-power RF to high-speed digital switching.

We are looking for a first-class Electronics Engineer to carry out installation, commissioning and after-sales service at customers' premises.

The ideal applicant will be aged 25-35, have a minimum qualification of HNC (electronics) and some industrial experience, preferably in a design/development environment, and be capable of working with minimum supervision.

The job is both rewarding and demanding and requires a high degree of technical ability, as well as a keen sense of responsibility. In return a good salary and excellent prospects are coupled with an unusual amount of personal freedom.

Extensive travel in the U.K. is involved with occasional trips abroad. Knowledge of the German language though not essential would be an advantage.

If you want a job which will really give you something to think about, then apply in writing giving fullest possible details of age, qualifications, career to date, salary, etc., to:



R. F. Ladbury
BRUKER SPECTROSPIN LIMITED
Unit 3, 209 Torrington Avenue
Coventry, CV4 9HN

(5046)

audix SALES MANAGER

Audix Limited are leading designers and manufacturers of audio broadcast systems for both the sound reinforcement and radio/T.V. industries. Due to continued expansion the post of Sales Manager is now made available to take total responsibility for the sale of company products both for the home and overseas markets.

Ideally the post is suited to a person aged 30/40 years with considerable knowledge of the commercial audio industry, who would enjoy organising and motivating a small internal sales team as well as identifying and securing new market and product opportunities. The applicant must be familiar with modern industrial marketing techniques and have a successful record of selling and sales management.

Exceptional opportunities exist here for an ambitious man who has the drive and application to satisfy the requirements of this post.

Applications should in the first instance be in writing to:—

AUDIX LIMITED
Station Road
Wenden
Saffron Walden
Essex CB11 4L9

Tel: Saffron Walden (0799) 40888

(5031)

THE RADIO AND ELECTRONIC COMPONENT
MANUFACTURERS FEDERATION INVITE APPLICATIONS
FOR APPOINTMENT AS

DIRECTOR-DESIGNATE

from candidates whose qualifications and experience should enable them to succeed the present Director, Mr. Arnold Bentley, who is due to retire in May 1976.

The commencing salary will be related to Civil Service and Industrial rates for senior executives.

Industrial experience combined with imagination, initiative and personality, will be regarded as important qualifications.

Applications should give full details of the candidate's academic record, qualifications and experience, and should be addressed, marked 'Personal' to:

Mr. C. Robert Jennings
Chairman
Radio and Electronic Component Manufacturers Federation
Liberty House
222 Regent Street
London. W1R 5EE

Every application will be treated as entirely confidential and will be acknowledged.


*Looking
for
a
new
job?*

Perhaps we can help!

We have regular contact with hundreds of electronics and electrical companies needing qualified electronics engineers and technicians and TV service engineers.

We can, therefore, help you to find an interesting and well paid job. All you need to do is to return the coupon below or give us a ring. Our service is confidential and costs you nothing.

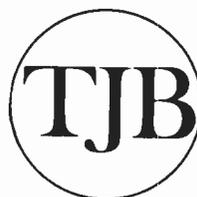**TJB Technical Services Bureau,
3A South Bar,
Banbury, Oxfordshire.
Banbury (0295) 53529**



Technical Services Bureau is a division of Technical & Executive Personnel Ltd and is solely concerned with job placement in the Electronics and Electrical Industries

Please send me an "Application for Registration" form

NAME

ADDRESS

.....

.....

TELEVISION PROJECT AND SYSTEM ENGINEERS

PROWEST ELECTRONICS, a leading international manufacturer of TV Mixing and Switching systems, have vacancies for Senior, Intermediate and Junior Engineers in the Projects department. Responsibilities will cover all aspects of customer liaison, design, manufacture, test and installation of a wide variety of custom-built vision/ audio mixing and switching equipment for the professional Broadcast market. We are looking for energetic and enthusiastic engineers aged 18 to 35, to join a rapidly expanding Projects team. Applicants for the Senior positions should ideally be qualified to degree standard or equivalent, with some knowledge of television engineering.

Salaries, dependent on age and experience, but above average.
Day-release considered for further studies.

Applicants should write or telephone to:

The Projects Manager
PROWEST ELECTRONICS LTD.
Alma Road, Windsor, Berks. SL4 3JA
Tel: Windsor 53111/8

(5023)

GRANADA TELEVISION LIMITED ELECTRONIC ENGINEERS

We are looking for young, experienced electronic engineers to fill a number of interesting jobs at our Manchester studios. The duties cover the operation and maintenance of the whole range of broadcast electronics, including television cameras, videotape recorders, telecine projectors and video switching, distribution and display equipment. The kind of people we need will have a formal qualification in electronics engineering but more important, will have an understanding of basic electronics and colour television principles arising from their genuine interest in the medium. They must be fit, with normal colour vision and prepared to work irregular hours including weekends.

Salary whilst training £2998 increasing to £3269 after one year and by annual increments to £4357 after 5 years. Four weeks leave, pension and free life assurance.

Write with full details of education and experience to: Robert Connell, Granada Television Ltd., Quay Street, Manchester M60 9EA.

(5034)



POLICE - CIVILIAN
GLASGOW SUB REGION

WIRELESS TECHNICIAN

GW/POL/21

£2922-£3282

Turnbull Street, Glasgow

The successful applicant will require to install and maintain a wide range of wireless equipment. City and Guilds Certificate in Telecommunications an advantage but emphasis is on ability and experience. Applicants must hold a current driving licence.

Application forms may be obtained from the Assistant Director of Manpower Services, 21 Gordon Street, Glasgow G1 3PL, to whom completed forms should be returned within 10 days of this advertisement.

R. M. O. McCULLOGH
Director of Manpower Services

(5049)

UNIVERSITY OF SURREY ELECTRONIC ENGINEER £2751-£3762

Applications are invited for the above position in the Electronic Workshop of the Physics Department. The person appointed will work, together with two other members of the technical staff, under the general direction of a Chief Technician.

The successful applicant will have a good electronics background, a sound theoretical knowledge and should be capable of developing and constructing computer interfacing circuits.

Applicants should possess HNC or equivalent, and salary will be according to qualifications and experience.

Further details and application forms may be obtained from the Staff Officer, University of Surrey, Guildford, Surrey, GU2 5XH, or Tel Guildford 71281. Ext. 452 Closing date for applications 9th January, 1976.

(5025)

CHELSEA COLLEGE University of London ELECTRONICS TECHNICIAN

GRADE 5 required for a new SRC research contract to work on a wide band tuning range microwave solid state oscillator. A high level of skill in electronic design and construction, and experience in microwave techniques is essential. The appointment is for two years. Salary in the range £3,161 - £3,617 inclusive. Application forms and further information from Mr. M. E. Cane (5ER), Department of Electronics, Chelsea College, Pulton Place, London SW6 5PR.

(5040)

NATIONAL AUDIO VISUAL AIDS CENTRE

254 Belsize Road, Kilburn
London, N.W.6

Television and Sound Production and Training Studios require an Engineer to support Lecturer staff on courses in CCTV and Audio-Visual media for teachers and training officers.

Further details from
Head of Training Dept.
(Tel. 01-624 8812)

(5037)



**CAPITAL
APPOINTMENTS LTD**

Recession?

Don't you believe it!

We have more jobs for good Electronic Design Development and Test Engineers than ever before. All areas UK, all applications Salaries to £5 000

(5073)

34 Percy Street, London, W.1
01-636 9659 (day) or
550 0836 (evg.)

RECEIVERS AND AMPLIFIERS —

HRO Rx5s, etc., AR88, CR100, BRT400, G209, S640, etc., etc., in stock. R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E11. Ley 4986. (65)

SIGNAL Generators, Oscilloscopes, Output Meters, Wave Voltmeters, Frequency Meters, Multi-range Meters, etc., etc., in stock. R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E11. Ley 4986. (64)

Electronics Engineers

Hewlett-Packard: the world's leading manufacturer of electronic instrumentation is expanding into the Middle East.

Challenging positions are now available in Iraq and Saudi Arabia for electronic engineers with at least 3 years experience in the field of electronic maintenance.

The selected candidates will be responsible for the installation and maintenance of electronic, medical and chemical instrumentation as well as calculator and

computer systems. Extensive training provided. Salaries and benefits competitive. All applications will be considered with preference given to candidates with compatible cultural background.

Send résumé in full confidence to:
Hewlett-Packard,
Mediterranean and Middle East
Operations, 35 Kolokotroni Street,
Kifissia - Greece.



Sales and service from 172 offices in 65 countries.

5051

UNIVERSITY OF SALFORD

ELECTRONICS TECHNICIAN

Required as part of an active research team in the Department of Chemistry and Applied Chemistry. Duties include the operation and maintenance of specialised electronic instrumentation and associated equipment as well as circuit design and construction. HNC in electronics essential. The appointment offers excellent experience for a young ambitious electronics technician.

Salary scale: £2751-£3207

Letters of application stating age, qualifications and experience should be sent to the Registrar, University of Salford, Salford M5 4WT by 16 December 1975, quoting reference CH-192 WW.

(5036)



Opportunities in the ELECTRONICS FIELD

Men with analogue or digital qualifications / experience seeking higher paid posts in: TEST - SERVICE - DESIGN - SALES.

Phone: Mike Gernat, Ref. W.W.

NEWMAN APPOINTMENTS
360 Oxford Street, W.1,
01-629 0501

(94)

CHARING CROSS HOSPITAL ELECTRONICS TECHNICIAN Medical Physics Department

Applications are invited for the above post from candidates with several years' experience, not necessarily in the medical field. Minimum qualifications are Ordinary National Certificate in electrical engineering or equivalent. This is a challenging opportunity for the right person, to be concerned with maintaining and servicing to a high standard a wide range of electronic equipment. They will also assist with the work of ordering components. Opportunities will arise for development work.

Salary will be within the ranges £2658 to £3579 or £3243 to £4146 depending on experience.

Further details of this post may be obtained from Warren Hills (01-748 2040, ext. 2665) and application forms are available from Heather Dann, Personnel Department, Charing Cross Hospital, Fulham Palace Road, London, W6 8RF (ext. 2997).

TELEVISION ENGINEER

A vacancy has arisen at our O.B. Units at Hanworth in Middlesex, for an engineer. Suitably qualified and experienced candidates should apply to the Personnel Officer at our Euston Studios whereby further information may be obtained.

Excellent conditions of employment including 21 days' annual leave and restaurant facilities.

Closing date: 29th December, 1975.

Thames Television, 306 Euston Road, London, NW1 3BB.
Tel. 01-387 9494.

THAMES

(5070)

APPOINTMENTS

SENIOR AUDIO VISUAL ENGINEER

London Airport c. £3,500 p.a.


The Heathrow Hotel features Europe's most sophisticated conference complex, complementing the hotel's fine restaurants, bars and first-class accommodation.

The finest audio-visual facilities are available to clients using our conference complex. We have a vacancy for a Senior Audio Visual Engineer to operate and maintain a wide range of CCTV and colour studio equipment including broadcast cameras and one-inch helical scan VTRs. Duties also include preparing and operating equipment for specific conference requirements.

Applicants should be aged 25-35 and have several years' experience of studio work in broadcasting or education and possess relevant technical qualifications.

Excellent company benefits include 20 days' holiday and a non-contributory pension scheme.

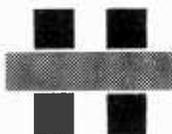Please apply with brief personal and career details to: The Personnel Department, The Heathrow Hotel, Bath Road, Heathrow, Hounslow, Middlesex TW6 2AQ, or telephone 01-897 6363/2419 for an application form.



The Heathrow Hotel

The only hotel on London Airport.

(5027)

CAPACITY AVAILABLE

DESIGN, development, repair, test and small production of electronic equipment. Specialist in production of printed circuit assemblies. **YOUNG ELECTRONICS LTD.**, 184 Royal College Street, London NW1 9NN. 01-267 0201. (29)

CAPACITY available to the Electronic Industry. Precision turned parts, engraving, milling and grinding both in metals and plastics. Limited capacity available on Mathey SP33 jig borer. Write for lists of full plant capacity to C.B. Industrial Engineering Ltd., 1 Mackintosh Lane, E9 6AB. Tel: 01-985 7057. (14)

AIRTRONICS LTD., for Coil Winding — large or small production runs. Also PC Boards Assemblies. Suppliers to P.O. M.O.D., etc. Export enquiries welcomed. 3a Waterland Road, London, SE13 7PE. Tel: 01-852 1706. (61)

PRINTED CIRCUIT BOARDS — Quick deliveries, competitive prices, quotations on request roller tinning, drilling, etc., speciality small batches, larger quantities available. Jamiesons Automatics Ltd, 1-5 Westgate, Bridlington, N. Humberside, for the attention of Mr. J. Harrison. Tel: (0262) 4738/77877. (18)

A.A.A. SERVICE. Small batch production wiring, assembly to sample or drawings. Specialists in printed circuit assembly. Cable-forms to order. **Rock Electronics Ltd.**, 42 Bishopshfield, Harlow, Essex. Tel. Harlow (0279) 33018. (19)

AVOMETERS repaired and calibrated, traceable calibration certificate given if required. **AVOMETERS** and **ELECTRONIC COMPONENTS** wanted, good prices paid. "Q" Services Electronic (Camberley) Ltd., Yateley (0252) 871048 any time. (4998)

BATCH Production Wiring and Assembly to sample or drawings. **Deane Electricals**, 19B Station Parade, Ealing Common, London, W.5. Tel: 01-992 8976. (13)

LABELS, NAMEPLATES, FASCIAS on aluminium or plastic. Speedy delivery **G.S.M. GRAPHICS LTD.**, 1-5 Rectory Lane, Guisborough (02873-4443) Yorks. (26)

PRINTED CIRCUITS, we will make your P.C.B.'s for at least 25 per cent less than what you are now paying. Prototypes welcome. 4990

ARTICLES FOR SALE

CAPACITORS mixed bags of electrolytics, approximately 500 untested for £1. Mullard metalised polyester, mixed bags of 50, 1µF and 2.2µF (250 d.c.), cosmetic imperfections so £1. Add 40p p&p to all orders. — R. Wardle, 3 Erpingham Road, SW15 1BE. (5069)

JACKFIELDS. Few only. 1 x 20 way and 3 x 20 way, to clear cheaply. Details 0532 683618. (5063)

OCILLOSCOPE HEATH KIT 10/18, new, good condition, £45. — Phone 427 4020 (Harrow Area). (5071)

VACUUM is our speciality, new and second-hand rotary pumps, diffusion outfits, accessories, coaters, etc. Silicone rubber or varnish outgassing equipment from £40. **V. N. Barrett (Sales) Ltd.**, 1 Mayo Road, Croydon. 01-684 9917. (24)

60 KHz MSF RUGBY RECEIVERS. BCD TIME-OF-DAY OUTPUT. High performance, phase locked loop radio receiver. 5V operation with LED indication. Kit complete £9.50; assembled and tested unit £11.12 (prices include postage and V.A.T.) Also available low power receiver with signal and audio outputs. Send for details **Toolex, Sherborne (4359) Dorset.** (21)

SITUATIONS VACANT

UNIVERSITY COLLEGE CARDIFF. Department of Physics, Electronic Music Studio. A **TECHNICIAN** Grade IV is required to maintain, supervise and build equipment for the Electronic Music Studio in the Department of Physics. The applicant should be interested in digital and audio electronics and be able to maintain analogue and digital equipment and tape recorders. The main studio is a working 4 channel unit using Studer A80 (1 inch) and TEAC (1/2 inch) 4 channel recorders, one UHER and 6 Revox machines. There is a SYNTHI 100 and several other synthesizers. The main mixer has eighteen channels with 6 groups and there is also other portable performance equipment. The Studio runs postgraduate courses for M.A and Diploma in electronic sound and also provides facilities for visiting composers. Among his other duties the technician will be required to help students with any construction projects if they arise. Salary range £2,559-£2,940 (which includes a supplement of £312 P.A. on the basic rate). Applications giving the names of two referees should be forwarded to the Vice-Principal (Administration) and Registrar, University College, P.O. Box 78, Cardiff CF1 1XL, not later than 9th February, 1976, please quote ref 0427. Anyone wishing further information, or who would like to discuss the possibilities further is cordially invited to get in touch with Mr Keith Winter, Electronic Music Studio, Physics Department, University College, P.O. Box 78, Cardiff CF1 1XL. (5047)

ARTICLES FOR SALE

PHOTO ETCH LIMITED

9 LOWER QUEEN STREET
PENZANCE, CORNWALL, TR18 4DF

Prototype or long run — we will supply your printed circuit requirements
Also facilities for Design, Assembly and Test

Prompt and efficient service assured

contact David Webster

☎ PENZANCE (0738) 4472

COLOUR UHF and TV SPARES. Lists available on request "Wireless World" TV tuner project, by D. C. Read. Kits of parts available. New cross hatch kit, Aerial input type. No other connections. Battery operated, portable. Incl. Sync & UHF Modulator units. £11.00 P/P 45p. CRT Reactivator kit for colour and mono £17.48 p/p 70p. Signal strength meter kit £18.00 p/p 60p. 625 TV I.F. Unit suitable for Hi-Fi amp on tape recording £6.80 p/p 60p. Bush CTV 25 new convergence panels + yoke and blue lateral £3.60 p/p 65p. New Philips single standard convergence panels complete, incl. 16 controls, coils, P.B. switches, leads £3.75 p/p 65p. New colour scan coils, Mullard or Plessey, plus convergence yoke and blue lateral £9.20 p/p 70p. Mullard at 1023/05 convergence yoke £2.50 p/p 50p. Mullard or Plessey blue laterals 75p p/p 25p. BRC 3000 type scan coils £2.00 p/p 60p. Bush CTV25 scan coils, new. £2.50 p/p 60p. Delay lines DL20 £3.50, DL40 £1.50, DLIE, DL1 £1.00 p/p 35p. Lum Delay Lines 50p p/p 20p. EHT colour quadrupler for Bush/Murphy CTV25 3/174 Series £8.50 p/p 60p. Special offer, colour triplers: ITT TH25/ITH £2.00 p/p 40p. GEC 2040 tripler £1.75 p/p 40p. Philips G8 panels, part complete, surplus/salvaged: decoder £2.50, IF, incl. 5 modules £2.25, T-Base £1.00 p/p 50p, CRT base 75p p/p 20p, G.E.C. 2040 panels for spares. Decoder £3.50. Timebase £1.00 p/p 55p. VARICAP TUNERS. UHF ELC 1043, new £4.20. ELC 1043/05, £5.00. VHF ELC 1042, new £5.00. Salvaged VHF and UHF Varicap tuners £1.50 p/p 25p. **SPECIAL OFFER:** RBM 6psn. Varicap control units £1.00 p/p 25p. UHF tuners, new, transistorised, incl. slow motion drive, £3.80. 4-position and 6-position push-button transistorised, £4.20 p/p 60p. Philips, Bush, Decca integrated UHF/VHF transd. tuners £4.50 p/p 65p. Thorn 850 dual Standard time base panel 50p p/p 50p. Philips 626 I.F. amp incl. cct. 50p p/p 50p. VHF turret tuners at 7650 incl. Valves for K.B. Featherlight, Philips 19TG170, GEC 2010 ETC. £2.50. Pyc miniature incremental for 110 to 830. Pam and INVICTA £1.00. New Fireball tuners, Ferguson, HMV, Marconi, £1.00 p/p all tuners 50p. Mullard 1100 Mono scan coils, new, suitable all standard Philips, Stella, Pyc, Ekco Ferranti, Invicta £2.00 p/p 55p. Large selection. LOPTS, FOPTS available for most popular makes. 200 + 200 = 100 MFD 350V Electrolytic £1.00 p/p 30p. **MANOR SUPPLIES.** 172 West End Lane, London, N.W.6. Shop Premises. Callers welcome. (No. 28, 159, 59 buses or W. Hampstead-Bakerloo and Brit. Rail). Mail Order: 64 Golders Manor Drive, London NW11. Tel: 01-794 8751. VAT. Please ADD 25% TO ALL PRICES (EXCEPT KITS. VAT 8%).

APPOINTMENTS

Central Birmingham Health District

**CHIEF
ELECTRONICS
TECHNICIAN**

required by the Regional Radiation Physics and Protection Service located at the Queen Elizabeth Medical Centre. The successful applicant will be involved in the design and construction of special devices and will be responsible for the electronic equipment in the department. Candidates should possess considerable experience in electronics and ONC/HNC or equivalent. Salary scale £3,558-£4,581. Further details on request by telephoning Dr. B. L. Reece, 021-472 1311, ext. 316. Application forms from the Personnel Officer, Queen Elizabeth Medical Centre, Edgbaston, Birmingham B15 2TH.

ARTICLES FOR SALE

**SCOPES
AVAILABLE**

Absolutely perfect condition. Most as new.

Tele-equipment S 51b	3 meg.	£60
S 54	10 meg.	£85
D 43	15 meg.	£90
D53	15 meg.	£135
D54	10 meg.	£125
DM 53	15 meg. storage	£225

Ring: Mr. Lewis at 01-882 1644 now and avoid disappointment

(78)

RECORDS MADE TO ORDER

DEMO DISCS MASTERS FOR RECORD COMPANIES	VINYLLITE PRESSINGS
---	------------------------

Single disc: 1 20. Mono or Stereo, delivery 4 days from your tapes. Quantity runs 25 to 1,000 records PRESSED IN VINYLLITE IN OUR OWN PLANT. Delivery 3-4 weeks. Sleeves/Labels. Finest quality NEUMANN STEREO/Mono Lathes. We cut for many studios UK/OVERSEAS. SAE list.

DEROY RECORDS

PO Box 3, Hawk Street, Carnforth, Lancs. Tel. 2273

(82)

100,000 C280 CAPACITORS, good mixed selection from .01uf to 2.2uf-250v/w & 400v/w, price 100/£1.25, 1,000/£10. AC128 transistors marked unused but require testing, price per 50/£1.50. Prices include VAT, P&P 25p. Electronic Mail-order Ltd., Ramsbottom, Bury Lancs. (5024)

"MOTIVATOR" Curtain Cord Controllers. Mains battery models and kits for use with corded domestic curtains. From £18.20. Aid-Us Products, Dept. WW10, 8 Hillview Road, Pinner HA5 4PA, Middlesex. 4988

THE SCIENTIFIC WIRE CO.

Copper — Nickel — Chrome — Eureka — Litz — Manganin Wires.
Enamelled — Silk — Cotton — Tinned Coverings.

- * No minimum charges or quantities.
- * Trade and export enquiries welcome.
- * S.A.E. brings List.

P.O. BOX 30, LONDON E4 9BW

CRYSTALS
Fast delivery of prototype and production quantities to your specification EG

100 KHz	0.005*	HC13/U	£2.50 each: £1,900 per 1,000
1 MHz	0.005*	HC6/U	£2.50 each: £1,600 per 1,000
2.097152 MHz	0.0025*	HC6/U	£3.05 each: £1,550 per 1,000
3.2768 MHz	0.0025*	HC6/U	£2.70 each: £1,500 per 1,000
10 MHz	0.002*	HC18/U	£2.00 each: £1,100 per 1,000

Also. Statek L.F. crystals in TO-5 package, many stock frequencies in the range 10-240 KHz, e.g., 10, 12.8, 16.384, 32.768 & 100 KHz, prices from £2.55 each: £1,400 per 1,000.
Please send for further details.
INTERFACE QUARTZ DEVICES LTD., 29 Market Street, Crewkerne, Somerset. Telephone: (046031) 2578 Telex: 46283.

ENAMELLED COPPER WIRE

S.W.G.	1 lb. reel	1/2 lb. reel
10 to 19	2 40	1 35
20 to 29	2 45	1 40
30 to 34	2 60	1 50
35 to 40	2 85	1 60

All the above prices are inclusive of postage and packing in U.K.

COPPER SUPPLIES
102 Parrwood Road, Withington, Manchester 20
Telephone 061-445 8753

HIGH STABILITY
**QUARTZ
CRYSTALS**
4 KHZ TO 105 MHz
CUSTOM DESIGNED OR PRODUCED IN A FULL RANGE OF INDUSTRIAL AND MOBILE SPECS.

WRITE OR TELEPHONE FOR DETAILS
TRISDENE LTD.
46 CRANK ROAD, BILLINGE WIGAN, LANCs. WN5 7EZ ENGLAND. Tel: Billinge (0744) 894295

DIGITAL CLOCK CHIP, AY-5-1224, with data and circuit diagram, £3.66 plus VAT. "Jumbo" LED digits (16mm high) type economy DL/747 only £2.04 each plus VAT, post free. Greenbank Electronics, 94 New Chester Road, Wirral Merseyside L62 5AG. (83)

C.R.T. REGUNNING PLANT. New and second-hand reconditioned training, demonstration, colour or B/W. Barretts, Mayo Road, Croydon, Surrey, CR0 2QP. (36)

OSCILLOSCOPE, Solartron CD711S.2. Any reasonable offer. St. Leonards House, Ashtree Close, Worlingham, Suffolk. Tel: Beccles 713786 (5032)

16MM B & H 631 Sound projectors c/w speaker and transformers £135. — Hilton Cine, 9 West Hill, Dartford -T. 20009. (15)

ARTICLES FOR SALE

RTTY AUDIO FREQUENCY SHIFT CONVERTOR CV-89A/URA-8A. This must be the first quantity release of this most sought after Ritty Converter. Brief description uses 15 BG9 & BG7 Valves, with a 2" C.R. Tuning Tube. Housed in a Grey Alloy Case size 17" x 5" x 15" deep Input supply fully filtered for interference Requires 105 - 125 Volts A.C. A two position Selectivity or Filter Switch that enables to set up for any Narrow Shift from 10-200 Cycles or any Wide Shift from 200-1000 Cycles. The Mean or Centre Freq for the Narrow Shift is 1000 Cycles, for the Wide Shift is 2550 Cycles Normal Audio Input from Receiver is 600 OHMS The Converter will operate with an input of 60 Microwatts to 60 Milliwatts or about -14 to plus 18 DBM Has Internal Tone OSC Freq 595-1785 CPS Mark Space Switch Normal or Reverse Supplied in good used condition, checked complete, but not tested Electronically £22.50. Carr. £2.50 onwards

We also have a few COMPARATORS CM-22A/URA-8A same colour and size, using 13 BG7 and BG9 Valves Made for use with above for Dual Diversity, Reception. 105-125 V.A.C Supply fully filtered for interference. Used Good condition, checked complete but not tested Electronically £10 00 Carr. as above.

We have in stock a Clip on Fan Blower Cooler complete with Filter & Heat Switch that only switches on when Units get to a preselected heat. Normally if Units are used up to 24 hours a day Housed in Alloy case £2 50 Post or carr. 50p

TELEPRINTER CREED 7B. New or rebuilt as new by Gov. in original Gov Transit Case Power 100 - 250V D.C. Few only at £22.50 ea. Carr. £3 50 or carr. £3 50

SUPPLY UNIT 7. Input Voltage 12V d.c. or 100-250 A.C. Output 70-100 Volts 30M/A twice. 30-45V A.C. 40 M/A. 11.5-14V d.c. 2-4 amps In small box. These are mainly for supplying Relay Voltage for the Teleprinters. Brand New at £3.50. Carr or post £1 00.

If possible collect ex Warehouse by appointment, and save carr. cost also delivery time.
Terms cash with order, VAT at 8%.
Phone Morley Code 0532-531179

JOHNS RADIO
424 BRADFORD ROAD, BATLEY, YORKS.
(5045)

fibre optic suppliers

MARE'S TAIL 22" dia 7000 + Fibres £10.00. Glass fibres - requires cover
FIBROFLEX SIZE 1 440 Strand Flexible Glass Light Conduit. 1 14mm Active Dia. Back Sheath 10m £3.00; 100m £21.00
FIBROFLEX SIZE 4 1760 strand £1.50
CROFFON 1610 Flexible 64 Strand Plastic Light Conduit Active Dia 1 8mm OD 3 3mm £1.20 per M 10m £9.00
PLASTIC OPTICAL MONOFIBRE Flexible Light Guide Dia 10 20 40 60 thou FP10 100m £4.00. FP20 (0 5mm) 100m £8.00 FP40 10m £4.00 100m £32.00. FP60 10m £8.00; 100m £65.00
OPTIKIT 103 2m CROFFON 1510 + 2m each FP20 FP40 FP60 + Polishing Compound, ideal laboratory pack £5.50
OPTIKIT L6 6 Convex Glass Lenses Dia 7/14 21 26/47/51mm £3.00. (Lenses also available separately)
OPTIKITS RRS Five Retro-Reflectors for Optical/beam systems Dia 22/36/44/83mm + 150mm Strip £2.80.
ULTRASONIC TRANSDUCERS SE05B-40T/R Sensitive 40kHz Tx/Rax 3w (Suitable for Doppler Remote Control) £3.50
ULTRASONIC TRANSDUCERS SE04B-25T/R 25 kHz Tx/Rax Pair (Better Sensitivity Lower Bandwidth than SE05B 40) £3.50
CIRCULAR POLARISERS Reduce glare on all types of instrument RED AMBER or NEUTRAL 50 mm sq 70p; 75 mm sq £1.40; 150 mm sq £4.50; Lenses Polarisers also available.
OPTOELECTRONICS LIGHT SOURCES & DETECTORS
MV54 2mm Red LED 20p. MLED500 T092 Red LED 20p.
XC209 Red (3mm) 20p. XC209 Y XC209-G Amber Green 30p.
MLED92 Infra Red Emitter 30p. MLED203 Photo Thyristor £1.20.
2N5777 High Sensitivity Photo-Darlington 25V 50p.
MRD 150 2mm High Speed Photo Transistor 4 US: 40V 70p
Please add 8% VAT to prices. S.A.E. please for short form data.
FIBRE OPTIC SUPPLIERS (WW), 6 CHIPPENHAM MEWS, LONDON W9. (5048)

500 DUAL STANDARD COLOUR TV's. In stock From £30. Contact: S.H.C. Television Ltd, 024-026 (Radnage) 3321. (20)

E.C.L. LOGIC I.C.s. Mc10101L; Mc101002L; Mc10105L all first grade, guaranteed. 50p per gate, post free. Discounts: £4.20 for 10 pieces; £38 for 100. Tunnel diodes TD253 at £1.50 each post free. Capacitor clearance: 0.1 micro-farad 250v polyester films tape C280 at £1.80 per thousand. (These are physically perfect but are surplus untested). Tested C280s: 0.47 at £1.20 per 100; 0.33 at £1.00 per 100; 0.22 at 90p per 100; 0.033 at 70p per 100. N. O'Brien, 189 West Hendon, Broadway, London. NW9. (5042)

OSCILLOSCOPE TUBES Mullard type D14-121-GH complete with shields, and base. Suitable case. C Core mains transformer and multi-rail regulator P.C.B. Inverter transformer and E.H.T. multiplier. Twin plug-in deflection amplifiers. All at £35 per package. All brand new. Circuits supplied phone 01-202 6282, very limited stock. (5043)

SUPERB INSTRUMENT CASES by Bazelli. manufactured from heavy duty PVC faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range, competitive prices start at a low 75p. Over 400 models to choose from. Prompt despatch. Free literature (stamp would be appreciated). Bazelli, Dept No 22, St Wilfrid's Foundry Lane, Halton, Lancaster, LA2 6LT. (5052)

ARTICLES FOR SALE

B. BAMBER ELECTRONICS

5 STATION ROAD, LITTLEPORT, CAMBS, CB6 1QE
TEL: ELY (0353) 860185 (TUESDAY-SATURDAY)

TERMS OF BUSINESS: CASH WITH ORDER

ALL PRICES INCLUDE POST AND PACKING (UK ONLY)
EXPORT ENQUIRIES WELCOME. CALLERS WELCOME TUES.-SAT.
PLEASE ADD VAT. MINIMUM ORDER £1
PLEASE ENCLOSE STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES (5030)

ALL BELOW — ADD 8% VAT

BFY51 TRANSISTORS 4 for 60p.
BSX20 TRANSISTORS 3 for 50p.
BC108 (metal can) 4 for 50p.
PBC108 (plastic BC108) 5 for 50p.
BSY95A TRANSISTORS 6 for 50p.
BCY72 TRANSISTORS 4 for 50p.
MINIATURE 2 PIN PLUGS & SOCKETS
(Fit into 1/4" hole pins enclosed, with covers for chassis mounting or can be used for in-line connectors) Bargain pack of 3 plugs + 3 sockets + covers 50p.
PROGRAMMERS (Magnetic Devices) Contain 9 microswitches (suitable for mains operation) with 9 rotating cams all individually adjustable, ideal for switching disco lights displays, etc. or industrial machine programming. (Need slow motion motor to drive cams, not supplied) 9 switch version £1.50, or 15 switch version £2.00.
10 WAY PUSH-BUTTON UNITS, 1/2" square buttons marked 0-9 cancelling type, mounted on one PCB for easy fixing, ex-equip. 50p.
HEAVY DUTY HEATSINK BLOCKS, undrilled base area 2 1/4" x 2", with 6 fins, total height 2 1/4". 50p each.
9V RELAYS, Continental type, 2 pole change over 35p.
RUBBER MAGNETS 1/2" square, with mounting hole, 20 for 30p.
PYE CAMBRIDGE PC BOARDS (Removed from high band AM10).
RF and MIXER BOARD £7.00
10.7 MHz IF BOARD £1.50
10.7 MHz OSCILLATOR/MIXER BOARD (with 11 155 Xtal) £1.25.
455 KHz IF BOARD £2.00
AM AUDIO BOARD £1.20
AM SQUELCH BOARD 50p
6 CHANNEL LEDEX SWITCHES, 12V, complete with all trimmers and coils (removed from high band AM10) £4.00.
PYE WESTMINSTER W30 AM MANUALS (shop soiled) £1.20 (Zero rated VAT).
T03 TRANSISTOR INSULATOR SETS, 10 for 50p.
SPECIAL OFFER. Miniature 50 ohm coax, high quality, PTFE insulation and blue PTFE cover, solid silver-plated inner, and silver-plated braid, approx. 3mm overall diameter, (ideal for unit wiring of RF stages up to 23cms, etc.) 4 metres for 50p.

ALL BELOW — ADD 8% VAT

24V MIN. REED RELAYS, encapsulated single-pole make, 2 for 50p.
CHASSIS TAGS, 25p pack
REALYS, single pole changeover, 20 DC, approx 1/4in x 1/2in x 1 1/4in 35p each

MANUFACTURERS — SEND SAE FOR OUR LATEST BARGAIN CAPACITOR LIST.

PLESSEY COLOUR SCAN COILS, 90° brand new £4.00 each
COLOUR MONITOR DECODER PANELS. By leading British manufacturer. Designed to B.B.C. standards. Units consist of chrominance module, PAL filter and delay module, luminance module and encoded video input module. All units brand new and complete including edge connectors and service manual. £30.00. Manual supplied separately. £1.00 each

WE NOW STOCK SPIRALUX TOOLS for the electronics enthusiast. Screwdrivers, nut spinners, BA and Metric sizes, pop rivet guns, etc. SAE for list

PLUGS AND SOCKETS

25-WAY ISEP PLUGS AND SOCKETS, 40p set (1 plug + 1 skt). Plugs and sockets sold separately at 25p each.
ANDREWS 44AN FREE SKTS. (N-type) for FH4/50B or FHJ4/50B cable. £1.00 each.
BULGIN ROUND FREE SKTS. 3 pin, for mains input on test equipment, etc. 25p each.
SO239 BACK TO BACK SOCKETS, £1.25 each.
PL259 PLUGS (PTFE). Brand new. Packed with reducers 65p each, or 5 for £3.50.
SO239 SOCKETS (PTFE). Brand new (4 hole fixing type), 50p each, or 5 for £2.25.
N-TYPE SKTS. (4 hole chassis mounting, 50ohms, small coax lead type), 50p each.
N-TYPE PLUGS 50ohm, 60p each
GREENPAR (GE35012) CHASSIS LEAD TERMINATIONS (These are the units which bolt on to the chassis, the lead is secured by screw cap, and the inner of the coax passes through the chassis), 30p each, 4 for £1.00.
BULGIN FLAT 2 pin FLEX CONNECTORS. Non-reversible 40p each.

ALL BELOW — ADD 8% VAT

MINIATURE Panel mounting Rocker Switches, bolt-on type, smart appearance, 3 for 50p.

MAINS TRANSFORMERS

All 240V input voltages quoted approx RMS
(Please quote Type No. only when ordering)
TYPE 10/2 10.0-10V at 2A, £1.50.
TYPE 72703 400V at 10mA, 200V at 5mA, 6.3V at 400mA, £1.25.
TYPE 28/4 28V at 4A, 125V at 500mA, £4.00.
TYPE 125BS, approx. 125V at 30mA, 65p.
RADIO SPARES 500WATT AUTO TRANSFORMER, 100 / 110 / 150 / 200 / 220 / 240V tapped input and output step up or step down facility, ex. new equip., £6.00.

MULLARD TUBULAR CERAMIC TRIMMERS

1-18pf, 6 for 50p.
(as featured in Rad. Comm. Jan p.25).
ICs, some coded, 14DIL type, untested, mixed, 20 for 25p.
2-6PF, 10MM CIRCULAR CERAMIC TRIMMERS (for VHF/UHF work), 3 pin mounting, 5 for 50p.
CERAMIC HIGH VOLTAGE PILLARS (metal ends, tapped 4BA), approx 1in long, 10 for 60p.

PYE RADIO-TELEPHONE EQUIPMENT

Cambridge, Westminster, Motofone, Europa series. Send s.a.e. for full details

WELLER STOCKIST. All irons and spares available. S.A.E. for list.

VALVES

QQV03/20A (ex-equipment) £3.00.
QQV03/10 (ex-equipment) 75p or 2 for £1.20.
2C39A (ex. equipment) £1.00 each
4X202/6 (ex. equipment) £1.00 each
QQV250B (ex. equipment), £1.50 each
DET22 (ex. equipment), 2 for £1.00.

ALL BELOW — ADD 25% VAT

HIGH QUALITY SPEAKERS, 8 1/2in x 6in, elliptical, 2in. deep, 4ohms, inverse magnet, rated up to 10W £1.50 each, or 2 for £2.75 (Quantity discount available)
T.V. PLUGS (metal type) 6 for 50p.
T.V. SOCKETS (metal type) 5 for 50p.
T.V. LINE CONNECTORS (back-to-back skt.), 5 for 50p.

MIXED ELECTROLYTICS, large bag £1.00.
PNP AUDIO TYPE T05 TRANSISTORS, 12 for 25p.
STUD RECTIFIERS, BYX42/300R, 300V at 10A, 30p each, or 4 for £1.00.
DIN SPEAKER SKTS. 2-pin, 4 for 50p.
IF CANS, 1/2in square, suitable for rewind, 6 for 30p.

DUBILIER ELECTROLYTICS, 50uF, 450V, 2 for 50p.
DUBILIER ELECTROLYTICS, 100uF, 275V, 2 for 50p.
PLESSEY ELECTROLYTICS, 470uF, 63V, 3 for 50p.
TCC ELECTROLYTICS, 1000uF, 30V, 3 for 60p.
PLESSEY ELECTROLYTICS, 1000uF, 180V, 40p each (3 for £1.00).

DUBILIER ELECTROLYTICS, 5000mfd at 35V 50p each
DUBILIER ELECTROLYTICS, 5000mfd at 50V 60p each
DUBILIER ELECTROLYTICS, 5000mfd at 70V 65p each
ITT ELECTROLYTICS, 6800mfd at 25V, high grade, screw terminals, with mounting clip 50p each
PLESSEY ELECTROLYTICS, 10000mfd at 63V 75p each.

MULLARD BLACK/WHITE C.R.T. A65-11W. Brand new, £11.00.
T.V. LINE SOCKETS, 18p each, 5 for 75p.
T.V. SOCKETS. Mounted on Bakelite panel 6 for 50p.
DIN 3 pin LINE SOCKETS, 15p each
E.H.T. V/HOLDERS B9A. (Both PHILIPS and PYE types available.) 20p each

Economise on Semiconductors

All prices include VAT

- ★ Low Price CMOS
- ★ Low price DIL sockets
- ★ Lower Price 741C
- ★ Plastic 3 terminal Regulators

	1+	10+	25+		1+	25+		1+	25+
709C + data 8 pin DIL	38	36	34	7400	14	12	4000	18	17
723C + data 14 pin DIL	70	68	64	7402	14	12	4001	18	17
741C + data 8 pin DIL	23	22	22	7403	14	12	4002	18	17
NE555 + data 8 pin DIL	45	44	43	7404	16	13	4006	102	95
CA3046 14 pin DIL	84	81	77	7405	16	13	4007	18	17
TDA1405 5v 650mA	80	76	74	7410	14	12	4008	102	95
TDA1412 12v 500mA	80	76	74	7413	29	24	4009	50	46
TDA1415 15v 450mA	80	76	74	7420	14	12	4010	50	46
8C107, 108, 109	11	10.5	10	7430	14	12	4011	18	17
8C182, 184	12	11.5	11	7442	64	54	4012	18	17
8C212, 214	13	12.5	12	7447	90	80	4013	50	46
H-P 0.2" LED red	19	18	17	7473	30	25	4014	90	82
H-P 0.125" LED red	18	17	16	7474	32	26	4015	90	82
DIL Low profile 8	11	10	9	7476	32	26	4016	50	46
Sockets 14	12	11	10	7486	32	26	4017	90	82
Sockets 16	13	12	11	7490	48	39	4020	97	88
				7492	55	50	4023	18	17
				7493	48	39	4024	68	62
				74121	34	28	4025	18	17
							4027	50	45
							4028	78	71
							4030	50	43
							4040	93	84
							4042	74	67
							4046	117	107
							4049	50	45
							4050	50	45
							4068	18	17
							4071	18	17
							4078	18	17
							4081	18	17
							4507	50	45
							4511	138	126
							4518	109	99
							4520	109	99
							4527	138	126
AY-5-1224 16 pin DIL clock IC + data + circuit									4.00
Clock kit IC + 4 digits									11.00
Clock kit IC + 4 digits, transistors & transformer									13.00
T8A10AS 7W Audio Amp + circuit + data									1.15
TCA940 10W Audio Amp + circuit + data									2.20
TA0100 Radio IC + IF filter + data									1.70
Carbon film resistors 1/4W 5% E12, 1.2 ea. 10 11p, 100 95p.									

By return service P&P 10p (UK) SAE enquiries, lists, Schools, Colleges supplied

SILICON SEMICONDUCTOR SERVICES
41 Dunstable Road, Caddington, Luton LU1 4AL

TEST EQUIPMENT — UHF Sig. Gen, MI TF2012, Automatic Mod. Meter, 500 MHz Counter, Dual Beam Scope, all less than 1 year old. Tel. Sutton (Cambs) 756.

COMPUTER APPRECIATION CHRISTMAS SALE! HONEYWELL G-115 processor incl. p.s.u. and console, £70. HONEYWELL 7-track magtape units, £25. Travelling Wave Tube Amp. & TWT, £19. GE International High Speed Tape Reader, £38. Letter writing FLEXOWRITER, £150. Phone Godstone (088 384) 3106.

SURPLUS TEST EQUIPMENT AND RADIO AMATEUR GEAR. Bench power suppliers 200/400 v. Precision millivolt meters, chart recorders, Vanguard, Cambridges, etc., etc., precision standards room equipment. B&H COMPONENT LTD., Dept. WW, Leighton Electronics Centre, 59 North Street, Leighton Buzzard, Beds, LU7 7EG. (05253 2316). (49)

EX-GOV'T MONO to multi-track tape recorders. "E.M.I." Ferragraph-rich Leavers, etc. S.A.E. details A. Wright, 10 Church Street, Dowlais, Glamorgan. 4991.

MULLARD FERRITE CORES LA3 100 to 500 kHz 54p LA5 30 to 100kHz 81p. LA7 10kHz 81p. LA13 for W.W. Oscilloscope £1.50. SPECIAL OFFER IN 4148 switching Diodes 10 for 30p. 50 for £1.25, 100 for £1.50, 1,000 for £10. Transistors ALL BRANDED BC147 — BC149 — BC157 — BC158 — BC159 — BF194 — BF195 — BF196 — BF197 — 8p each or 100 for £6.50. All prices include UK postage and appropriate VAT at 8 or 25 per cent. Mail order only. — Xerox Radio, 1 East Street, Bishops Tawton, Devon. (5066)

COMPUTERS BURROUGHS E2100 series business machines. Programmed for stock control. TWO AVAILABLE reasonable offers invited. B. & H. Components Ltd., Dept WW Leighton Electronics Centre, 59 North Street, Leighton Buzzard, Beds, LU7 7EG (05253 2316). Surplus Test Equipment stocked. (49)

ARTICLES FOR SALE

SCOPE TUBES D14-121-GH 50 MHZ. 4.2 v/cm 'Y' sensitivity, with bases and mumetal shields. Also suitable unassembled cases, £30 the package. Suitable mains transformers, regulator P.C.B.s (no components) inverter transformers, multipliers, deflection amps attenuator switches, time base, switches etc. available to tube purchasers at virtually scrap prices. Everything brand new. Phone 01-202 6282. (5072)

LINSLEY-HOOD 75 watt amplifier spares, sescosom BDY56 £1.75, Motorola BD529, 530 65p each, 2N5459 45p, BF259 45p Tantalum bead 100/3V 15p. Filter switch click and mains/rf interference suppression kit, with full fitting instructions, £1.35. All components brand new and guaranteed. Prices are tax inclusive, 59 Powey Avenue, Torquay, S. Devon. (5064)

ARTICLES WANTED

- ★ **MINICOMPUTERS**
- ★ **PERIPHERALS**
- ★ **INSTRUMENTATION**

For fastest, best CASH offer, phone

COMPUTER APPRECIATION
Godstone (088 384) 3106 (5058)

WANTED, all types of communications receivers and test equipment. Details to R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley 4986. (63)

B-D ELECTRONICS offer prompt settlement for your surplus components. Our main field of interest is consumer electronics. Please telephone our Miss Hughes, Sandy (0767) 81616. (22)

AVO VCM 163 Valve tester. TF 1041c Valve voltmeter digital multimeter TDMS. 70. Fletcher, 62 Moorbridge Lane, Stapleford, Nottingham, 0602 397446. (4985)

WANTED AVO VCM 163 Valve tester "off air" frequency standard. Toms 70. Telegquipment D43 "Plug ins." Modern Marconi test equipment. Nottingham 0602 397446. (5053)

ARTICLES WANTED. We purchase large quantities of Transistors I.C.'s Diodes, etc, etc. Please telephone 01-359 4224. (5067)

SURPLUS COMPONENTS. Equipment and Computer panels wanted for cash. Ring Southampton 722501. (5061)

PLEASE HELP. Wanted Wireless World August 1975 to save several years' collection. Any reasonable price paid. Mr Romer, 15 Kenilworth Rd, Bognor Regis, PO21 5NE.

WIRELESS WORLD COLLECTOR requires January, March, April, June July, August 1966. February, March, April, May, June, July, August 1967. February 1968. February, March, April, May, July, October, November, December 1969. July 1970. April 1972. December 1973. — Box No. 5065.

NEW GRAM AND SOUND EQUIPMENT

GLASGOW. Hi Fi, Cassette Decks, Tape Recorders, Video Equipment, always available we buy, sell and exchange for Hi Fi sets and photographic equipment. **VICTOR MORRIS** Audio Visual Ltd, 340 Argyle Street, Glasgow, G1, 8/10 Glassford Street, Glasgow, G2, 31 Sauchiehall Street, Tele: 041-221 8958. (11)


COURSES

RADIO and Radar M.P.T. and C.G.L.I Courses. Write: Principal, Nautical College, Fleetwood, FY7 8JZ. (25)

VALVES WANTED

WE BUY new valves, transistors and clean new components, large or small quantities, all details, quotation by return — Walton's, 55 Worcester St., Wolverhampton. (62)

SERVICES

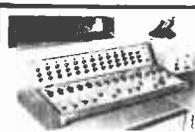

FOR SOUND SENSE

MIX WITH

PARTRIDGE ELECTRONICS

MANUFACTURERS OF AUDIO MIXERS, BIG AND SMALL, FOR ALL PURPOSES

21-25 Hart Road, Benfleet, Essex

Phone: (03745) 3256

BUDGET KITS

OR CUSTOM BUILT



QUALITY

GRAPHIC ELECTRONICS LTD.
PROFESSIONAL PRINTED CIRCUITS

Small - Medium - Large Batch Runs
Prototypes - Same Day Service

Marsh Road

Tel. 036-32-3530

Lords Meadow Industrial Estate, Crediton EX17 1EU

PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' hardware, Aluminium sheet and sections. Printed circuit board, top quality for individual or published designs.

Prompt service

Send 15p for catalogue

RAMAR CONSTRUCTOR SERVICES

Masons Road, Stratford-on-Avon
Warwicks. Tel. 4879 (38)

STRIPPER FOR HIRE

Your Free issue wire cut and stripped for 75p per 1000 leads. Supply of equipment cable available printed circuits assembled Cable looms and complete equipment manufactured to order. Wire supplied and cut, a quotation will cost you nothing from

HAMER & EMMINS LTD.
Desaronto Wharf, St. Mary's Road
Langley, Bucks
Tel. Slough 46760 or 46769

SERVICE AND REPAIRS

AUDIOMASTER BACKGROUND MUSIC . . . service, sales. Tape programmes. P. J. Equipments, 3 Onslow Street, Guildford 4801. (12)

THOR-HOLE CONVENTIONAL P.C.B.'s gold plating, roller tinning, prototypes, silk screening, drilling. All or part service. — **ELECTRO-CIRCUITS (P.C.) LTD.**, Delamare Road, Chesnut, Herts. Tel. Waltham Cross 38600 or 20344. (84)

TUBE POLISHING, mono, £5.63, colour £5.94. C.W.O. Return carriage and VAT paid. Phone: N.S. 300, Retube Limited, North Somercotes, Lough, Lincs. (27)

HAVE YOU DIFFICULTY in obtaining Electronic Components at the right price and when you require them. We are interested in purchasing components on behalf of manufacturers, overseas buyers, etc. Give our service a try and get the benefit of over 20 years experience, we make promises and not excuses. Contact Tom Powell, Elekon Enterprises, 224A St. Paul's Road, Highbury Corner, London, N1. Tel. 01-359 4224. (5068)

BOOKS WANTED

BOOKS WANTED "Electronic Transformers & Circuits" by R. Lee, "Transformers" by F. C. Connelly. Box No. 5054.



Instruments well worth servicing are worth servicing well

And now it's even easier because you can bring or send your AVO, MEGGER or SULLIVAN instruments for service or repair direct to the manufacturers' joint service and spares centre. In-house BCS certification facility.

London Instrument Repair Centre,
Repairs Enquiries
Cunnington Street, Archcliffe Road,
Acton Lane Works, DOVER,
Chiswick, Kent CT17 9EN,
London W4 5HJ. Tel: 0304 202620.
Tel: 01-995 9212. Telex: 96283.
Telex: 22583.

AVO-MEGGER-SULLIVAN



FOR CLASSIFIED ADVERTISING

RING OWEN BAILEY

ON
01-261 8508
OR
01-261-8423

LIGHT SWITCH



Automatically switches on lights at dusk and off at dawn. Can also be used where light and dark is a convenient way to stop and start an operation. Requires only a pair of wires to the normal switch. In bakelite box, normal switch-plate size. 1 amp model £3.75.

VAT and Postage 50p

8-SWITCH DISCO LAMP CONTROLLER

Mains motor driving a drum with adjustable trips operating 8 changeover 10 amp switches, so a total of 40K watts of lighting can be controlled enabling an unlimited variety of effects to be achieved and changed with the minimum of effort. This is a real snip at £7.50+£1.15 post and VAT.



RELAY BARGAIN

Type 600 relay, 2 changeover one open and one closed contact. Twin 500 ohm coils make this suitable or closing off DC 6v, DC 12v, DC 24v or AC mains using resistor and rectifier. 40p each. Resistor and rectifier 20p extra. Post and VAT 20p.



NUMICATOR TUBES

For digital instruments, counters, timers, clocks, etc. Hi-Vac XN.3. Price 99p each, 10 for £9.

MULLARD THYRISTOR TRIGGER MODULE

This produces pulses for phase control triggering, it has two isolated outputs, so one thyristor or two thyristors (in separate arms of bridge) can be controlled by one module. The timing circuit is synchronised to the mains frequency and control is by an external variable resistor or from a voltage or current source. Provision is made for feed-back where automatic control is required. Price £5.95.



MULTI-SPEED MOTOR

Six speeds are available 500, 850, and 1,100 r.p.m. and 8,000, 12,000 and 15,500 r.p.m. Shaft is 1/4 in. diameter and approximately 1 in. long. 230/240v. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor, size approx. 2 in. dia. x 5 in. long. Price £1.40 x 45p post & VAT.



SLIDE SWITCHES

Slide Switch, 2 pole changeover panel mounting by two 6BA screws. Size approx. 1in. x 1/4in rated 250V lamp. 15p + 7p post & VAT. Sub Miniature Slide Switch, DPDT 19mm (4in. approx.) between fixing centres 28p each + 9p post & VAT or 10 for £1.90. SP change over spring return 250v 1 amp. 25p + 8p post & VAT.



TANGENTIAL HEATER UNIT

This heater unit is most efficient and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. Comprises motor, impeller, 2kW element, and 1kW element allowing switching 1, 2 and 3 kW and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only needs control switch. £5.82 plus post & VAT £1.2kW Model as above except 2kW £4.25 plus VAT & post 75p. Don't miss this Control Switch 44p. P.&P. 40p.



CENTRIFUGAL BLOWER

Miniature mains driven blower centrifugal type blower unit by Woods Powerful but specially built for quick running—driven by cushioned induction motor with specially built low noise bearings. Overall size 4 1/2" x 4 1/2" x 4". When mounted by flange, air is blown into the equipment but to suck air out, mount from centre using clamp. Ideal for cooling electrical equipment or fitting into a cooker hood, film drying cabinet or for removing flux smoke when soldering, etc. A real bargain at £3.30 + 60p post & VAT.

DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 6 feet of flex cable. Wired up ready to work. £2.75. VAT & postage 65p.




AUDIO AMPLIFIER

Part of the famous Rediune background music system, secondhand but believed in good order. However, no guarantee, we are selling for spares value only. These are 6 valve amplifiers, the output valves are 2 x Et. 84 in push pull, complete with mains transformer, rectifier and ample smoothing equipment. The mains transformer alone, today would cost at least £4. Size is 9 1/2" x 5 1/2" x 4 1/2". Price only £2.00 + postage & VAT £1.50.



15A ELECTRICAL PROGRAMMER

Learn in your sleep. Have radio playing and kettle boiling as you awake — switch on lights to ward off intruders — have a warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price £2.95. VAT & Postage 60p or with glass front chrome bezel £1.50 extra.

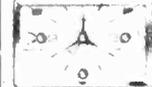

SMITHS CENTRAL HEATING CONTROLLER

Push button gives 10 variations as follows: (1) continuous hot water and continuous central heating (2) continuous hot water but central heating off at night (3) continuous hot water but central heating on only for 2 periods during the day (4) hot water and central heating both on but day time only (5) hot water all day but central heating only for 2 periods during the day (6) hot water and central heating on for 2 periods during the day time only — then for summer time use with central heating off (7) hot water continuous (8) hot water day time only (9) hot water twice daily (10) everything off. A handsome looking unit with 24 hour movement and the switches and other parts necessary to select the desired programme of heating. Supplied complete with wiring diagram. Originally sold, we believe at over £15 — we offer these, while stocks last at £6.95 each. VAT & Postage 85p each.



TERMS Where order is under £5 please add 30p surcharge to offset packing expenses

J. BULL (ELECTRICAL) LTD.
(Dept. W.W.), 103 TAMWORTH ROAD
CROYDON CRO IXX

YOU MAY BE IN TIME

For a valve volt-meter at £7.50 — a signal generator at £8.50, an oscilloscope at £12.50 — a frequency standard at £19.50 as these and many other good buys were offered in our December Advanced Advertising News. Send S.A.E. for a copy today.

Of course as subscribers received this list at least a month ago chances are best buys will have been snapped up so whilst writing why not send £1.25 and receive the next issue in advance.

BUY YOURSELF SOMETHING

Good buys available at these prices only during Jan. Prices include VAT.

	PRICE	Postage
	£ p	£ p
Mullard Unilex with speakers.	15.50	—
Full-FI stereo amplifier, in teak look case	9.95	1.00
7 watt stereo amplifier (American G.E.C.)	7.00	40
AM/FM tuner (less dial and drive) for above amplifier	6.50	50
Headphone stereo amplifier	4.50	25
Remitone 7 transistor pocket radio	2.00	20
Fluorescent kitchen light 20 watt with tube	2.95	1.00
Atlas car battery charger 6v and 12v with meter	2.25	75
Battery charger kit	1.95	50
Motorised car aerial 12v with controls	7.50	80
Jumpers leads for emergency starting	1.50	50
Solder gun with work light	3.25	50
Antex soldering iron 15 watts with 2 bits.	2.95	25
Mini immersion heater (quick cuppa)	2.00	20
Jug heater	3.00	30
Luxistor amplifier in case with speaker	6.50	50
Celestion 8" speaker 12 1/2 watts 8-10 ohms	4.00	75
6 1/2 v very high power motor	3.50	40
12v Smiths motor for blower, etc.	2.16	40
Light dimmer, 1250 watts, disco model	4.25	40
2000 watt motor driven disco light flasher	4.00	20
15 switch motor driven disco light controller	9.50	50
8 switch motor driven disco light controller	8.50	50
Black (UV) light amp for disco—175 watt	7.00	50
Randall central heating controller	7.00	30
Horstmann central heating controller	6.00	30
Crystal set kit	2.00	25
5 computer boards (at least 250 transistors, ICs and other components)	1.00	50
Batteries (10.7v), pack of 25	1.00	40
12v mains unit for driving models	2.50	30
Drill speed controller kit	2.95	40
Drill speed controller, but made up	3.95	40
Multirange test meter 1000 ohm fully switched	4.95	30
EP10K test meter	13.90	50
Sound to light unit	8.50	25
Automatic night light switch 240v	4.00	25
Automatic night light switch 12v	1.50	25
Immersion heater, 2kW, standard tank fitting	2.00	60
Soil heating kit (transformer, etc.)	3.00	75
Use this list as an order form and please note if your total order for these items exceeds £20 we will pay the postage.		
SOUND TO LIGHT UNIT		
Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450w). Unit in Box all ready to work. £7.95 plus 95 VAT and postage.		



ADVERTISEMENT

The Plessey Company Limited and L.S.I. (Electronic Systems) Limited announce, following settlement of a dispute between themselves and General Instrument Corporation of America and General Instrument Microelectronics Limited, that the following metal oxide semiconductor circuits have been withdrawn from the market:

- MP9100 Push button telephone dialler
- MP9200 Repertory telephone store
- MP1013A Universal asynchronous receiver/transmitter

The equivalent circuits AY-5-9100, AY-5-9200 and AY-5-1013/1013A can be obtained from General Instrument Microelectronics Limited.



PLESSEY Semiconductors

Now! The day-by-day yearbook.

Day-by-day usefulness throughout 1976—that's the keynote of our new, completely revised Yearbook. New features include a week-at-a-glance desk diary, and a fact-packed Serviceman's Section. Plus the industry's most comprehensive buyers' guide, big legal and technical sections, and pages of valuable trade names and addresses. Order your copy now!

To: General Sales Dept., IPC Electrical & Electronic Press Ltd., Room 11, Dorset House, Stamford St., London SE1 9LU
Please send me copies of Electrical & Electronic Trader Year Book and Diary 1976 @ £5.50 each, inclusive of postage and packaging. I enclose cheque p.o. for

Name
Address

* Cheques should be made payable to IPC Business Press Ltd

Trader

Company registered in England Registered No 677128
Registered address Dorset House, Stamford St SE1 9LU

Wilmslow Audio

THE firm for speakers!



- Baker Group 25, 3, 8, or 15 ohm **£8.64**
- Baker Group 35, 3, 8 or 15 ohm **£10.25**
- Baker Deluxe, 8 or 15 ohm **£13.75**
- Baker Major, 3, 8 or 15 ohm **£11.87**
- Baker Regent, 8 or 15 ohm **£10.00**
- Baker Superb, 8 or 15 ohm **£18.12**
- Celestion HF1300 8 or 15 ohm **£7.75**
- Celestion MH 1000 horn, 8 or 15 ohm **£13.50**
- Decca London and X over **£42.25**
- Decca DK30 and X over **£24.06**
- EMI 13 x 8, 150 d/c, 3, 8 or 15 ohm **£2.94**
- EMI 13 x 8, Type 350 **£9.56**
- EMI 13 x 8, 25 watt bass **£9.00**
- EMI 8 x 5, 10 watt, d/c, roll/s 8 ohm **£3.95**
- EMI 14" x 9" Base 80 **£13.25**
- Elac 59RM 109 15 ohm, 59RM 1148 ohm **£3.44**
- Elac 6 1/2" d/c roll/s 8 ohm **£4.06**
- Fane Pop 15 watt 12" **£5.25**
- Fane Pop 25T 30 watt 12" **£7.50**
- Fane Pop 50 watt, 12" **£12.00**
- Fane Pop 55, 12" 60 watt **£13.95**
- Fane Pop 60 watt, 15" **£17.25**
- Fane Pop 70 watt 15" **£18.75**
- Fane Pop 100 watt, 18" **£29.95**
- Fane Crescendo 12A or B, 8 or 15 ohm **£34.50**
- Fane Crescendo 15, 8 or 15 ohm **£47.50**
- Fane Crescendo 18, 8 or 15 ohm **£62.95**
- Fane 807T 8" d/c, roll/s, 8 or 15 ohm **£5.75**
- Fane 801T 8" d/c roll/s 8 ohm **£9.95**
- Goodmans 8P 8 or 15 ohm **£5.50**
- Goodmans 10P 8 or 15 ohm **£5.80**
- Goodmans 12P 8 or 15 ohm **£13.95**
- Goodmans 12P-D 8 or 15 ohms **£16.95**
- Goodmans 12P-G 8 or 15 ohms **£15.95**
- Goodmans Audiom 100 15-ohm **£13.90**
- Goodmans Audiom 200 8 ohm **£13.90**
- Goodmans Axent 100 8 ohm **£8.44**
- Goodmans Axion 402 8 or 15 ohm **£20.00**
- Goodmans Twinaxiom 8" 8 or 15 ohm **£10.14**
- Goodmans Twinaxiom 10" 8 or 15 ohm **£10.75**
- Kef T27 **£6.06**
- Kef T15 **£6.94**
- Kef B110 **£8.37**
- Kef B200 **£9.50**
- Kef B139 **£16.95**
- Kef DN8 **£2.31**
- Kef DN12 **£5.99**
- Kef DN13 **£4.50**
- Richard Allan HP88 8" 45 watt **£13.25**
- Richard Allan CG8T 8" d/c roll/s **£7.50**
- STC 400 1 G super tweeter **£6.56**
- Baker Major Module, each **£13.44**
- Goodmans Mezzo Twinkit, pair **£47.19**
- Goodmans DIN 20, 4 ohm, each **£14.75**
- Helme XLK35, pair **£24.00**
- Helme XLK40, pair **£35.00**
- Helme XLK30, pair **£19.00**
- Helme XLK50, pair **£56.00**
- Kefkit I, pair **£53.00**
- Kefkit III, each **£48.00**
- Richard Allan Twinkit, each **£10.95**
- Richard Allan Triple 8, each **£16.50**
- Richard Allan Triple, each **£23.95**
- Richard Allan Super Triple, each **£28.75**
- Richard Allan RA8 kit, pair **£42.00**
- Richard Allan RA82 kit, pair **£63.00**
- Wharfedale Linton 2 kit (pair) **£23.12**
- Wharfedale Glendale 3 kit, pair **£40.62**
- Wharfedale Dovedale 3 kit, pair **£63.12**

All Radford, Gauss, Castle, Jordan Watts, Eagle, Lowther, Peerless Lannoy units in stock
 Prices correct at 29.10.75
INCLUDING VAT AT 25% ON HI-FI 8% ON PRO AND PA
 Cabinets for PA AND HiFi, wadding, Vynair, etc.
 Send stamp for free booklet "Choosing a Speaker"
FREE with all orders over £7 — HiFi
Loudspeaker Enclosures Book
All units are guaranteed new and perfect
 Prompt despatch
 Carriage, Speakers 50p each, 12" and up 75p each, tweeters and cross-overs 30p each, kits 80p each (£1.60 pair)

WILMSLOW AUDIO

Dept. WW
Loudspeakers & Export Dept: Swan Works, Bank Square, Wilmslow, Cheshire SK9 1HF.
Discount HiFi, PA etc: 10 Swan Street, Wilmslow. Radio, HiFi, TV, Radio: Swift of Wilmslow, 5 Swan Street, Wilmslow. Tel. (Loudspeakers) Wilmslow 29599, (HiFi, etc.) Wilmslow 26213

WW—022 FOR FURTHER DETAILS

POLYESTER CAPACITORS I.T.W.

Radial Lead 10% Tolerance 100V D.C. 001mfd 03p, 015mfd 035p, 1mfd 06p, 0022mfd 03p, 022mfd 035p, 15mfd 07p, 0047mfd 03p, 033mfd 04p, 22mfd 08p, 0068mfd 03p, 047mfd 04p, 47mfd 15p 01mfd 03p, 068mfd 05p

Axial Lead 10% Tolerance 200V D.C. 01mfd 185p, 022mfd 185p, 047mfd 20p, 1mfd 25p

Dipped Tantalum Capacitors (Bead Type). Values available 1, 15, 22, 33, 1mfd, 1.5, 2.2, 3.3, 4.7, 75p, 47, 6, 8, 10mfd, 25v, 15, 22, 33, 47mfd, 16v Prices 10p each - 10 for 95p

Electrolytic Capacitors (Axial). 1000-40V 25p, 470-16V 15p 220-25V 12p 100-25V 6p, 47-25V 5p, 47-10V 5p, 22-40V 5p, 10-25V 5p, 4.7-63V 5p, 2.2-63V 5p, 1mfd 63V 5p **Radial.** 2200 (Tag) 40V 45p each, 1000 16V 25p, 470-25V 19p, 220-25V 12p, 100-25V 6p, 47-16V 5p 33-16V 5p 22-16V 5p, 10-16V 4p, 5mfd-16V 4p 4.7-16V 4p

Carbon Film Resistors. 1/2Watt RD1/3 5% (70 c) 01p each 90p per 100 1R-1Meg (1M2-10M 10%) Special Pack 20 popular values quarter W — 5 of each 90p 1/2Watt AEL 5% 4.7R-2M2 015p each; 75p per 100 1Watt AEL 4.7-2M2 2p each, 1.74 per 100. Special Pack 100 Resistors mixed 40p

Polyethylene Capacitors (pf) 63V & 160V 5%. 10, 15, 18, 22, 33, 56, 68, 100, 120, 150, 180, 270, 330, 390, 560, 680, 820, 03p each 1000, 1500, 2200, 3300, 035p each 470, 680, 820, 4p each 10,000pf 03p each

Semiconductors. BC107/8/9 09p, BC147/8/9 10p, BC157 8 9 9p, BCY70/1/2 17p 8FY51 19p SCR C106D 2P4M-400V 50p each

Integrated Circuits. 741 8 Pin DIL 27p, 723(TO99) 57p, LM309K(TO3) 1.48 1/C Sockets. (Gold) B/14/16 15p, (Tin) 8 14 16 14p

Zener Diodes. 400MW 9p 1Watt 17p (Standard voltages)

Diodes. IN4148 05p, BAX16 05p

Rectifiers. 1A IN4001 5p IN4002 06p, IN4003 07p, IN4004 08p, 3Amp 3A05(50v) 10p 3A10(100V) 11p

TERMS. CASH WITH ORDER **V.A.T.** PLEASE ADD 25% POST AND PACKING ADD 35p ON ALL ORDERS UNDER £5 **PROMPT SERVICE ALL COMPONENTS GUARANTEED**

Greenway Electronic Components
 (EAST GRINSTEAD) LTD
 62 MAYPOLE ROAD, ASHURST WOOD, EAST GRINSTEAD, SUSSEX RH19 3BB
 TEL: FOREST ROW 3782
 (STD 084 282) 3713

INVERTERS

To operate mains equipment from 12v or 24v DC on automatic stand-by



Sine wave Square wave Self-driven or Frequency controlled Suitable for maintaining mains supply during power failure, running equipment where the mains is not available, or insulation from the mains **Controlled battery charging incorporated.**

MAINS-STORE
 Send for information to
Interport Mains-Store Ltd.
 30 Old Bond Street, London, W1
 Tel. 01-727 7042 or 0225 3916

EURO CIRCUITS
 Printed Circuit Boards - Master layouts -
 Photography - Legend printing - Roller Tinning -
 Gold plating - Flexible films - Conventional
 fibre glass - No order too large or too small -
 Fast turnaround on prototypes.
 All or part service available NOW.....

EURO CIRCUITS LTD
 Highfield House
 West Kingsdown
 Nr. Sevenoaks, Kent. WK 2344

"SAVE IT" BARGAIN
500 WATT DIMMER SWITCH
 (not suitable for fluorescent lights)
 Basic Module with 1" Knob **£2.00**
 Complete on MK switch plate **£2.50**
 Larger 2" knob (BULGIN) 25p extra. P&P 25p
 Please add 8% VAT to all orders inc. P&P.

FRASER-MANNING LTD.
 40 TUDDENHAM ROAD, IPSWICH, IP4 2SL

SOWTER TYPE 3678
MULTITAP MICROPHONE TRANSFORMER
 Primary windings for 600 ohm 200 ohm and 60 ohm with Secondary loadings from 2K ohm to 10 K ohm. Frequency response plus minus 1/2dB 20 Hz to 25 KHz. Contained in well finished Muralist box. 33mm diameter by 22mm high with colour coded end leads. low distortion DELIVERY (small quantities) EX STOCK HIGHLY COMPETITIVE PRICE FULL DETAILS ON REQUEST
E. A. SOWTER LTD., Dedham Place, Ipswich
 IP4 1JP. Telephone 0473 52794

EXCLUSIVE OFFERS

WORLD-WIDE RANGE NEVER BEFORE OFFERED
COMPLETE TRANSPORTABLE H.F. COMMUNICATIONS CENTRE housed in Air Conditioned TRAILER fitted two COLLINS KWT-5 500W S.S.B. Transmitter-Receiver and one COLLINS Receiver all fully tuneable 2 to 30 mcs digital readout, synthesised frequency control, with line amplifiers and Inputs, operating position and remote control facilities and ancillary equipment. Power input 115V or 230V A.C. Full details on application.

PHILCO HC-15D POINT-TO-POINT STRIP RADIO HF RECEIVERS 2500 n.c.s. Ten fully tuneable channels to 0-6 mcs with synthesisers, single and diversity reception on ISB, DSB, SSB with 4 sub-bands to each channel. Full details and prices on application.

HIGHEST QUALITY 19" RACK MOUNTING CABINETS & RACKS

Our Height Ref. in inches	Width in inches	Depth in inches	Rack Panel Space in inches	Price	
CR	30	60	36	42	£12.50
CR	69	30	20	20	£24.00
DM	70	20	26	138	£21.00
FA	85	22	36	160	£22.00
FC	52	25	22	47	£17.00
FG	11	19	18	10	£11.00
FH	15	21	17	11	£12.00
FJ	15	21	15	12	£12.00
FN	70	24	20	68	£17.00
LI6	11	21	17	9	£15.00
LI7	16	20	12	14	£15.00
LI8	10	20	10	9	£15.00
LI9	17	21	17	14	£15.00
LI10	32	21	18	46	£15.00
MM	75	22	26	68	£22.00

Also Consoles, twin and multi-way Cabinets.

OPEN RACKS

Our Height Ref. in inches	Width in inches	Depth in inches	Base	Price	
RF	85	3	79	15	£11.00
RG	57	2	51	14	£9.00

Full details of all above on request.
 We have a large quantity of "bits and pieces" we cannot list—please send us your requirements we can probably help—all enquiries answered.

- * Collins KWT-5 SSB Transceivers P U R
- * Rhode and Schwarz HUZ Field Strength Measurer £45.00
- * Intertechnique SA40 Spectrum Analysers P U R
- * Teletype W 33 d/b Oscilloscopes £40.00
- * Inside Cabinet Shelf Sliders £3.00
- * DG-732 C.R.T.'s £3.00
- * Remscope Storage Scope with tracer £115.00
- * Textronic 519 Scope 1GHZ £450.00
- * Teletype SA40 Oscilloscopes C. Amp £47.00
- * M.V.R. Action Replay 20 sec. Videocine Unit P U R
- * Gresham quality enclosed chokes, 5H 200 m/a £2.00
- * Dow Keu Co-ax. Relays SPST 12 to 110v A C £6.00
- * Racial IKW S.S.B. Linear amplifiers 1.5/30 m/cs P U R
- * Advance HI Signal Generators, 15/50Kcs £18.00
- * Varian VA175-A Backward Wave Oscillators P U R
- * Kintel Standard Voltmeter 001/600 Vx 001v £40.00
- * Tally 5/8 Track Tape Readers 80 cps £48.00
- * Tally 5/8 Track Tape Readers 120 cps £65.00
- * 2 KVA Auto-Transformers £22.00
- * Coutant 40v 30A Powe Supplies £30.00
- * 15 foot 15 inch Lattice Steel Mast Sections £25.00
- * Cintel 2 KV Powe Supplies £29.00
- * Valradio 400 watt Inverters 24v to 230 VAC £22.00
- * Cawtell FL 4 Band Pass Filter Testers £60.00

We have a quantity of Power Transformers 250 watts to 15KVA at voltages up to 40KV. Best quality at low prices. List available.

- * Racial RA-63 SSB Adaptors, new £70.00
- * Racial RA-237 4-W Converters, new £70.00
- * 19" Blank Rack Panels 84in high £1.00
- * Apex Electrostat Photo Copier Electrostatic £40.00
- * Apoco Dial a Copy Photo Copier Electrostatic £60.00
- * Hewlett Packard 524C Digital Counter P U R
- * Armeec 702 Sig. Generators 30 cyc/30 Kcps £23.00
- * Tuning Roller 4 testers £3.50
- * Portable Mains Battery Floodlights £24.00
- * 400 channel Pulse Height Spectrum Analysers P U R
- * Solatron 5.25000 cyc. Oscillators £24.00
- * Addo 5/8 track Tape Punches £48.00

We have a varied assortment of industrial and professional Cathode Ray Tubes available. List on request.

INSTRUMENTATION-TAPE RECORDER-REPRODUCERS

- * Ampex TM-217 4 speeds 7 tracks
 - * Ampex 501 4 6 speeds, 2 tracks
 - * Ampex FR600 1", 4 speeds, 7 tracks
 - * Ampex FR600 1", 4 speeds, 14 tracks
 - * D R I RM-17, 4 speeds, 4 tracks
 - * LMI BTR-17, 1 speed, 1 track
 - * LMI R301G, 2 speeds, 2 tracks
 - * Mincom CMP-190, 1/2, 1" 6 speeds, 7 tracks
 - * Nak 1 5000 1/2 speed 7 tracks
 - * Leavers Kien DA-2P, 1/2, 2 speeds 2 tracks
- Prices of above £70 to £400

COMPUTER HARDWARE

- ★ **PRINTER**, High speed 1000 lines p.m.
- ★ **TAPE READER**, High speed 5/8 track 800 c.p.m.

Prices on Application
 PLEASE ADD V.A.T. AT APPROPRIATE RATE TO ABOVE
P. HARRIS
ORGANFORD-DORSET
 BH16 6BR
 BOURNEMOUTH-765051

WW—030 FOR FURTHER DETAILS

When you need to hire Video-
it pays to contact the most experienced
video company in the business

REW

R.E.W. HOUSE
10, 12 HIGH STREET
COLLIERS WOOD
LONDON SW19 2BE
PHONE: 01-540 9684

Also at **CENTRE POINT**
20/21 ST. GILES HIGH STREET
LONDON, WC2
PHONE: 01-240 3066

DIOTESTOR IN-CIRCUIT
TRANSISTOR TESTER



The DIOTESTOR detects faulty diodes and transistors when still in circuit without need for unsoldering.

BRITEC LIMITED

17 Devonshire Road, London SE23 3EN
Tel: 01-699 8844 Telex: 896161

WW-012 FOR FURTHER DETAILS

WE PURCHASE ALL FORMS OF ELECTRONIC EQUIPMENT AND COMPONENTS, ETC. SPOT CASH

CHILTMead LTD.

7, 9, 11 Arthur Road, Reading, Berks.
Tel: 582 605

J. LINSLEY HOOD

HIGH QUALITY AMPLIFIERS AND TEST EQUIPMENT available from

Examples: **TELERADIO HI FI**

75 Watt Amplifier, PA Module	£12.00 (Kit)	£15.95 (Made)
Pre-amp Module	£10.25 (Kit)	£14.50 (Made)
P.S.U. from	£18.50 (Kit)	£21.00 (Made)
F.M. Tuner, basic kit	£32.00 (p.p. 70p)	
de luxe p.b. version	£37.50 (p.p. 70p)	
Stereo Decoder	£4.85 (Kit)	£5.85 (Made)
Millivoltmeter Kit	£15.25 (Kit) (Tax 8%)	
Low Distortion Audio Osc.	£9.50 (Kit) (Tax 8%)	
Third Harmonic Analyser	£20.25 (Kit) (Tax 8%)	
Reg. P.S.V. 0/60v 1A	£17.50 (Kit), Tax 8%	

Tax extra 25% where unmarked. P/P extra (min. 25p)

FOR DETAILED AND ILLUSTRATED LISTS SEND S.A.E.

FM Tuner



Hi Q Amp 75 watt

Millivoltmeter



325 Fore St, Edmonton, London, N.9
01-807 3719 Closed Thursdays

BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, N. Finchley
London, N12 8JG
Telephone: 01-445 0749 01-445 2713 01-958 7624

MAY WE ASSIST YOU TO DISPOSE OF YOUR SURPLUS AND REDUNDANT STOCKS.

We will call anywhere in the British Isles, and pay SPOT CASH for Electronic Components and Equipment.

BRIDGE ELECTRONICS COMPONENTS

AC 126 13	BF 180 25	2N2904 .18
AC 127 13	BF 181 25	2N2905 .18
AC 128 11	BF 200 25	2N2906 .18
AC 151 18	BF 194 .09	2N2907 .18
AC 152 25	BF 195 .09	2N2926G .09
AC 153 27	BF 198 .12	2N3053 .20
AC 176 14	BF 199 .12	2N3054 .40
AC 187K 27	BF 257 24	2N3055 .45
AC 188K 27	BF 258 24	2N3393 .12
AD 161 35	BF 259 24	2N3441 .56
AD 162 36	BFX 23 22	2N3442 .96
BA 102 10	BFX 30 22	2N3638 .10
BAK 15 03	BFX 84 20	2N3638A .10
BAK 16 04	BFX 95 27	2N3702 .10
BC 107 09	BFX 98 20	2N3703 .10
BC 108 09	BFY 50 19	2N3704 .10
BC 109 09	BFY 51 19	2N3705 .10
BC 107 09	BFY 52 19	2N3706 .10
BC 148 08	BY126 11	2N3708 .10
BC 149 08	BY127 11	2N3771 1.25
BC 167 10	CA87 06	2N3772 1.35
BC 168 10	CA90 04	2N3773 2.00
BC 169 10	CA91 04	2N3904 11
BC 187 09	CA200 05	2N3906 12
BC 188 09	CA202 06	2N5294 35
BC 184 09	IN914 04	2N5296 35
BC 212 095	IN4004 05	2N5298 35
BC 213 095	IN4007 06	2N3794 .20
BC 214 095	IN4148 03	2N3819 .30
BC 237 08	IS920 05	2N3820 .55
BC 238 08	IS921 05	2N4036 .55
BC 239 08	IS923 05	2N4037 .40
BC 307 09	2N697 15	2N4286 .20
BC 308 09	2N698 14	2N4921 80
BC 309 09	2N706 10	2N5060 25
BC 327 12	2N708 10	2N4289 25
BC 328 12	2N710 10	2N5447 12
BC 329 12	2N916 23	2N5447 12
BC 330 13	2N1305 25	2N5449 12
BC 331 13	2N1307 25	2N5457 30
BC 332 12	2N1308 25	2N5458 27
BC 333 30	2N1613 15	2N6027 40
BC 334 25	2N1711 15	40361 45
BD 135 25	2N2218 175	40362 40
BD 136 26	2N2218A 18	40408 42
BD 137 27	2N2219 175	40409 42
BD 138 28	2N2219A 18	40410 42
BD 139 29	2N2221 175	40602 55
BD 140 32	2N2221A 18	40636 1.00
BD 56 1.00	2N2222 175	40673 80
BF 115 20	2N2646 30	

FULLY GUARANTEED

Mail order only VAT extra p&p 20p
Bridge Electronics
PO Box No. 10 Fishponds Bristol BS162LX

QUARTZ CRYSTAL UNITS from

- 1.0-50.0 MHZ
- FAST DELIVERY
- HIGH STABILITY
- TO DEF 5271-A

WRITE FOR LEAFLET AT 1
McKNIGHT CRYSTAL Co. Ltd.
HARDLEY INDUSTRIAL ESTATE, HYTHE, SOUTHAMPTON SO4 6ZY
TEL HYTHE 848961 STD CODE 0703

SOWTER TRANSFORMERS

FOR SOUND RECORDING AND REPRODUCING EQUIPMENT
We are suppliers to many well-known companies, studios and broadcasting authorities and were established in 1941.
Early deliveries. Competitive prices. Large or small quantities. Let us quote.
E. A. SOWTER LTD.
Transformer Manufacturers and Designers
12 Dadhan Place, Waterworks Street Ipswich IP4 1JF. Telephone 0473 52794
WW-030 FOR FURTHER DETAILS

PRECISION POLYCARBONATE CAPACITORS

440V All High Stability - Extremely Low Leakage

RANGE VALUE (F)	DIMENSIONS (mm) L	D	PRICE EACH	63V Range	±1%	±2%	±5%
0.1µF	27	12.7	51p	0.47µF	67p	50p	45p
0.22µF	33	16	64p	1.0µF	52p	62p	52p
0.25µF	33	16	67p	2.2µF	50p	62p	61p
0.47µF	33	15	80p	4.7µF	£1.62	£1.13	£1.13
0.5µF	33	19	87p	6.8µF	£1.96	£1.38	£1.38
0.68µF	50.8	19	93p	10µF	£2.40	£1.95	£1.64
1.0µF	50.8	19	£1.03	15µF	£3.22	£2.79	£2.24
2.0µF	50.8	25.4	£1.44	22µF	£4.28	£3.68	£3.08

*TANTALUM BEAD CAPACITORS - Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.8, 6µF at 15V/25V or 35V, 10µF at 16V/20V or 25V, 22µF at 6V or 16V, 33µF at 6V or 10V, 47µF at 3V or 6V, 100µF at 3V ALL at 10p each, 10 for 95p, 50 for £4.

TRANSISTORS & T.C.'s

AC128 14p	BC268A/384 10p	OC71 12p
AC176 18p	BC547/558A 12p	2N2926G 12p
AD149 40p	BCY72 12p	2N2926D 11p
AF178 30p	BD131/132 30p	2N2926Y 11p
AF239 38p	BF115/167 22p	2N3054 55p
BC107/8/9 9p	BF173 24p	2N3055 50p
BC114 12p	BF178 26p	2N3702/ 3704 11p
BC147/8/9 10p	BF184 22p	TIP30A 52p
BC153/154 12p	BF194/195 12p	TIP31A 55p
BC157/8/9 12p	BF196/197 12p	TIP32A 64p
BC177 18p	BF200 27p	TIP305S 55p
BC182/183L 11p	BF252/263 60p	MPU131 49p
BC183/183L 11p	BFY50/51 52 20p	NE555 61p
BC184/184L 12p	BFX64/86/88 20p	741C 32p
BC212/212L 14p	BFX85 26p	2N414 41p
BC213/213L 11p	BR101 41p	SN76013ND £1.50
BC214/214L 11p	GET872 25p	
BC267 12p	OC44/OC45 14p	

POPULAR DIODES - IN914 9p, 8 for 45p, 18 for 80p; IN918 8p, 6 for 45p, 14 for 80p; IS44 24 for 50p, 24 for £1.00; IN4148 5p, 6 for 27p, 12 for 48p; IN4001 5p; 002 6p; 003 6p; 004 7p; 006 8p; 007 8p.

LOW PRICE ZENER DIODES - 400MW Tol ±5% at 5mA. Values available: 3V, 3.3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13V, 13.5V, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V, All at 7p each, 5 for 33p; 10 for 65p. SPECIAL OFFER: 100 Zeners for £6.00.

*RESISTORS - High stability, low noise carbon film 5%, 1/2W at 40°C, 1/4W at 70°C E12 series only - from 2.2 to 2.2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value. SPECIAL PACK 10 of each value 2.2 to 2.2MΩ (730 resistors) 85.

SILICON PLASTIC RECTIFIERS - 1.5 amp brand new wire ended DO27: 100 P.I.V. 7p (4 for 26p), 400 P.I.V. 8p (4 for 30p). BRIDGE RECTIFIERS - 2 amp, 200V, 350V, 450V, 600V 55p. *SUBMINIATURE VERTICAL PRESETS - 0.1W only. ALL at 5p each, 50p, 100p, 220p, 470p, 680p, 1k, 1.2k, 1.4k, 1.7k, 2.2k, 2.7k, 3.3k, 3.9k, 4.7k, 5.6k, 6.8k, 8.2k, 10k, 15k, 22k, 27k, 33k, 39k, 47k, 56k, 68k, 82k, 100k, 150k, 220k, 270k, 330k, 390k, 470k, 560k, 680k, 820k, 1M, 1.5M, 2M, 2.5M, 3M.


PLEASE ADD 15p POST AND PACKING ON ALL ORDERS BELOW £5. ALL EXPORT ORDERS ADD COST OF SEA/AIR MAIL. PLEASE ADD 8% VAT to all items except those marked with * which are 25%.

Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona fide companies.

MARCO TRADING
(Dept. D1)
The Old School, Edstaston, Nr. Wem Shropshire
Tel. Whixall (Shropshire) (STD 094872) 464/5
(Proprs: Mimcost Trading Ltd.)

STABILIZER

With two years experience of frequency shifters the new Stabilizer includes all the features which have shown themselves to be desirable in a unit for how reduction. It provides shifts between 1 and 10 Hertz either upwards or downwards and has a front panel gain control, signal overload LED and SHIFTER BYPASS switch as well as a mains switch and neon. This unit has a considerably lower noise level than any previous shifter and hum pickup within the small case is avoided by the mains transformer and input transformer in the balanced version being in metametal screening cans. The input amplifier is protected from high voltage spikes on the signal line, whether from the valve equipment or occurring through static or earth leakage voltages while a system is being plugged up. The output line driving amplifier is preceded by a 24Hz high pass filter which not only provides further rejection of the shifting oscillator but is general good practice before feeding into a power amplifier. Available as a boxed unit with either balanced or unbalanced signal lines. Rack mounting version also available offering studio quality slider. SHIFTER control duplicated jack and XLR connectors and a smart anodised finish with an engraved front panel.

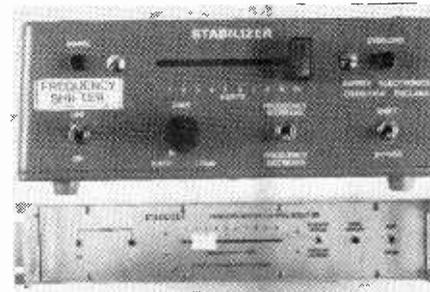

Shifters are proving effective in the following situations:
Sound reinforcement for television studio audiences
Feedback monitoring on stage
Live microphone telephone conference systems with a 5Hz shift each way giving 10Hz round the loop which is effective in the small non-reverberant rooms involved.
Group hearing aid systems for teaching deaf children
Microphones or radio microphones for discussion groups or floor questioners who are within the intended coverage of the PA loudspeakers as well as for straightforward sound reinforcement and public address.

+5Hz FIXED SHIFTER CIRCUIT BOARDS for WW July 1973 article
Small enough to be built inside the cabinets of many amplifiers. Complete kit and board £24. Including psu and mains transformer. DESIGNER APPROVED

Write or ring for leaflet giving full specifications for this or any other item - STEREO DISC AMPLIFIER, 10 OUTLET DISTRIBUTION AMPLIFIER, MICROPHONE PREAMPLIFIER, PPM DRIVE CIRCUITS and Ernest Turner PPM MOVEMENTS 642, 643 and TWIN, all meeting IBA requirements.

SPECTRUM SHIFTER:
Variable shifts 0.1 - 1000Hz for weird special effects on speech or music
SURREY ELECTRONICS
The Forge, Lucks Green, Cranleigh
Surrey GU6 7BG (STD 04866) 5997
CASH WITH ORDER less 5% UK post free add VAT at 8%

IBM GOLFBALL COMPUTER INPUT/OUTPUT TYPEWRITERS

STANDARD EBCDIC CODING

Will accept normal or sprocketed paper. Supplied in working order with data sheets, circuit diagram and application notes. Each machine serviced and tested

£100 + 8% VAT

As above but modified to take office range of Golf Balls. £110 + 8% VAT.

PAPST (or similar) **FANS** 4½ x 4½ x 2" 100 c.f.m. 50/60 c/s £4 (40p).

PAPST FANS Type 7576, new, 6" dia x 2¾" deep £5 (45p).

LIGHT DIMMERS 250w £2.70 (16p).
BC107/8/9, BC147/8/9, BC157/8/9 all 9p ea. (11p).

ELECTROLYTICS
10,000µ 63v £1 (25p) 2800µ 100v 80p (25p) 2240µ 100v 75p (25p). 1000µ 63v £1 (25p) 4500µ 35v 60p (15p). 2000µ 50v 35p (11p) 4000µ 70v 80p (20p) 4700µ 63v 80p (15p) 2500µ 60v 50p (12p)

EX-COMPUTER PC PANELS. 2 x 4" 50 boards for £2.40 (62p).

OPCOA SCA7 7mm 7-seg. led display £1 (12p)
QH bulbs 12v 55µ 60p (10p)
250 mixed resistors 60p (18p)
250 mixed capacitors 80p (18p)
Si recs 60A 100piv 4 for £1 (15p)
2N3055 equiv 4 for £1 (15p)

EXTRUDED HEAT SINK for 2 x TO3 50p (15p)

SMALL ELECTROLYTICS
2.2µ 10v, 10µ 35v, 50µ 40v, 100µ 40v, 100µ 6v, 150µ 10v, 64µ 10v, 300µ 10v, 200µ 10v 12 for 45p (12p)

PIHER PRESETS 100mW
220, 470 1k, 4k7, 10k, 47k, 100k, 220k, 12 for 50p (12p)

6v 0.5A Transformer 75p (18p)

ALMA REED RELAY CPRI/A 18.30v 50p (10p)

REED RELAYS 6v coil h/d contacts 5 for £1 (15p)

REED INSERTS h/d contacts 10 for £1 (12p)

WATER-COOLED HEATSINKS ex. eqpt. £1.20 (40p)

CHROMED HANDLES
5" mtg. centres per pair £1 (20p)
8" mtg. centres per pair £1.50 (25p)

P&P shown in brackets

ADD 25% VAT to TOTAL

8% VAT on PSUs, FANS, DIMMERS, BOARDS

KEYTRONICS

Shop open Monday-Saturday, 9-2

332 LEY STREET, ILFORD, ESSEX

01-553 1863 till 2 p.m.

01-478 8499 after 2 p.m.

Guide to Broadcasting Stations

17th Edition

A title which has sold more than 250,000 copies. The bulk of the book is devoted to lists of stations broadcasting in the long, medium, short and v.h.f. bands in both frequency and geographical and alphabetical order. The book also contains useful information on radio receivers, aerials and earth, propagation, signal identification and reception reports.

1973 206 pp., illustrated
0 592 00081 £1.00

Illustrations in Applied Network Theory

F. E. Rogers

A hundred numerical and algebraic illustrations designed to exemplify practical circuit problems and introduce, in analysis, principles consistent with studies of synthesis that may be pursued later.

1973 240 pp., illustrated
0 408 70425 X cased £5.75
0 408 70426 8 limp £2.65
Obtainable through any book-seller

Newnes- Butterworths

BOROUGH GREEN
SEVENOAKS
KENT TN15 8PH

TEL.
BOROUGH GREEN 884567

DIRECT COMMUNICATIONS

Division of Direct Electronics Ltd.

INTERCOMMS & TELEPHONES

● Simple 2-way wall/desk with 100ft cable. 6v batt or power supplv. £16 (£1 p&p)

● Similar but 2- to 7-way instrument only. Installation diagram. £8.50 each (50p)

● Superior 2- to 6-way Siemens & Halske. Wall-desk conversion kit, term. block and cord per instrument £10. (50p).

● AUTOMATIC INSTRUMENTS. Strowger compatible or PX working. New/refurbished/2nd hand. 232 332 706 746 722 (Trimfone), etc. Special and foreign types.

● ULTRA MODERN TYPES. "Gondola" International Touch-button dial; Charleston (candlestick); etc.: from £32.85

● Plan & Key Phones for home and export

● Jacks; Plugs; Cords; Term. Blocks. Cables (up to 25-way and 50 pair), etc.

● Entrance Phones and Electric Latches, with or without intercomm. facility.

● Telephone Amplifier (1-way), £6.95 (35p); hands-free tele. amp. (two-way conversation), £9.50 (50p)

★ TRANSISTORISED UNITS. Simple 2-way batt. intercomm. £7.75 (50p); Batt. Baby Alarm £5.25 (50p); Intercomm. with roving master £9.50 (50p)

● Wireless Intercomm. (just plug into mains); 2-way £20 (£1); batt. op. 3-way (master + 2 subs) £23.95 (£1); 4-way (master + 3 subs) £28.50 (£1)
★ mains adaptor 6v/7.5v/9v dc £3.75 (35p).

Add VAT ● = 8%; ★ = 25% on post paid price

TRADE ENQUIRIES WELCOMED

MANY SURPLUS ELECTRONIC BARGAINS FROM OLD STOCK STILL LEFT — COME AND DO A DEAL!

34 LISLE STREET, LONDON,
WC2H 7BD
Tel: 01-437 2524

SEMICONDUCTOR CIRCUIT ELEMENTS

Towers, T.D. Price: £6.00
ELECTRONIC CIRCUIT DESIGN
HANDBOOK by EEE Magazine
PRICE: £5.10

RADIO VALVE & SEMICONDUCTOR
DATA by A. M. Ball PRICE: £2.50

ELECTRONIC CIRCUITS & SYS-
TEMS by R. King PRICE: £5.45

HOW TO BUILD ELECTRONIC KITS
by V. Capel PRICE: £1.95

ELECTRONIC TEST EQUIPMENT by
H. T. Kitchen PRICE: £4.90

HI-FI LOUDSPEAKERS & ENCLO-
SURES by A. B. Cohen PRICE: £6.30

DESIGNING CIRCUITS WITH IC
OPERATIONAL AMPLIFIERS by R. G.
Seippel PRICE: £3.45

VIDEOTAPE RECORDING by J. F.
Robinson PRICE: £6.25

FOUNDATION OF WIRELESS &
ELECTRONICS by M. G. Scroggie
PRICE: £4.25

HI-FI YEAR BOOK 1976 by K. Ellmore
PRICE: £2.60

★ PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.

SPECIALISTS IN SCIENTIFIC
& TECHNICAL BOOKS

19-21 PRAED STREET
LONDON W2 1NP

Phone 723 4185
Closed Sat 1 p.m.



Quartz Crystal Units
ACCURATE
RELIABLE

Private enquiries, send 10p in stamps for brochure

THE QUARTZ CRYSTAL CO. LTD.
Q.C.C. WORKS, WELLINGTON CRESCENT,
NEW MALDEN, SURREY. 01-942-0334 & 2988



**QUARTZ
CRYSTALS**

- Quality Units 2 — 105 MHz
- Competitive Prices
- Industrial and Mobile Radio Crystals a speciality
- Prompt Delivery (Appx. 3 weeks)

For full details write or telephone.

C&C electronics
10 West Park, London SE9 4RQ
Telephone 01-852 9397

WW — 019 FOR FURTHER DETAILS

**ANY MAKE-UP OR
COPY QUERIES
CONTACT
JOHN GIBBON
01-261 8353**

LOW FREQUENCY ANALYSER

50Hz-50kHz
ASSEMBLY AND INSTRUCTION
INFORMATION S.A.E.

PRICE £27 p&p 75p

Board, modules and all
components (excluding
P.U.)

12" CRT

Magnetic Deflection. Blue Trace
Yellow Afterglow (P7). Informa-
tion and recommended circuits
with all purchases. Brand new,
boxed, **£4 each**. Carriage £2.

V.A.T. at 8%

CHILTMEAD LTD

7-9 ARTHUR ROAD, READING, BERKS. (rear Tech. College). Tel. Reading 582605

X-Y RECORDERS


Advance, Moseley
Hewlett Packard

Price from:
£80 each


INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 123-131

	PAGE		
Acoustical Mfg. Co. Ltd.	67	Gardners Transformers	9
Aero Electronics Ltd.	13, 18, 22	Grampian Reproducers Ltd.	6
Ambientacoustics	92	Greenway Elec. Comps. (E. Grinstead) Ltd.	133
Ambit International Ltd.	15, 24	Greenwood Electronics Ltd.	13
A.S.P. Ltd.	88	Hall Electronics Ltd.	7
Audix Ltd.	17	Harmsworth Townley & Co. Ltd.	Readers Card
B. Bamber Electronics	130	Harris Electronics (London) Ltd.	8, 15
Barrie Electronics Ltd.	91	Harris P.	133
Bayliss, A. D. & Sons Ltd.	25	Hart Electronics	86
Bentley Acoustic Corp. Ltd.	104	Henry's Radio Ltd.	86, 104
Beyer Dynamic (G.B.) Ltd.	16	Hi-Fi Yearbook	19
B.H. Component Factors Ltd.	112	Hi-Fidelity Designs	113
Bi-Pak Semiconductors Ltd.	17, 106, 107	Hoymitz Electronics Ltd.	25
Bi-Pre Pak Ltd.	119	I.L.P. (Electronics) Ltd.	89
Brenell Eng.	6	Icelectrics Ltd.	25
Bridge Electronics	134	Icon Design	14
Britec Ltd.	134	Industrial Tape Applications Ltd.	21
Broadfields & Mayco Disposals	134	Integrex Ltd.	99
Bull, J., Electrical Ltd.	132	Interport Mains Store Ltd.	133
Cambridge Learning	5	Jackson Bros. (Ldn.) Ltd.	96
Catronics	94	J.H. Associates Ltd.	12
C & C Electronics	135	Keytronics Ltd.	135
Chiltmead Ltd.	122, 134, 136	Kinnie Components Ltd.	88
Chromasonic Electronics	93	Klark Teknik Ltd.	17
City Audio	95	Ledon Instruments Ltd.	12
C.J.L. Ltd.	22	Levell Electronics Ltd.	1
Colomor (Electronics) Ltd.	98	Lexor Electronics Ltd.	11
Combined Precision Components Ltd.	94	Light Soldering Developments Ltd.	8
Computer Appreciation	95, 116	Lynx (Electronics) London Ltd.	110
Crofton Electronics Ltd.	95	Macinnes Labs. Ltd.	12
Cryslon Electronics Ltd.	24	Magnetic Tapes Ltd.	20
C.T. Electronics Ltd.	101	Maplin Electronic Supplies	90
Deimos Ltd.	16	Marco Trading Co.	134
Dema Electronics International	91	McKnight Crystal Co.	134
Direct Electronics Ltd.	135	McLennan Eng. Ltd.	16
Dolby Noise Unit	115	Marconi Instruments Ltd.	Cover ii
Doram Electronics Ltd.	22	Marshall, A., & Sons (London) Ltd.	102
Dymar Electronics Ltd.	83	Meteronic Ltd.	16
East Cornwall Components	110	Mills, W.	100
Edicron Ltd.	15	Modern Book Co.	135
Electrical & E/T/Y/Book	132	Multicore Solders Ltd.	Cover iv
Electronic Brokers Ltd.	113	Naim Audio	20
Electrovalue Ltd.	94	Nombrex Ltd.	23
English Electric Valve Co. Ltd.	10, 28	Olson Electronics Ltd.	96
Environmental Equipment Ltd.	23	OMB Electronics	15
ERG Industrial Corporation Ltd.	118	Physical & Electronic Labs. Ltd.	18
E/R/T Colour Faults Guide	118	Plessey Semiconductors	132
Euro-Circuits	133	Powertran Electronics	85, 87
European Electronics Suppliers Guide	114	Precision Petite Ltd.	18
Evershed & Vignoles Ltd.	3	Pulse Electronics Ltd.	14
Farnell Instruments Ltd.	20, 25	Purnell Books	Loose insert
Fashionable Leatherwear	117	Quality Electronics Ltd.	11
Ferrograph, The Co. Ltd.	19	Quartz Crystal Co. Ltd.	135
Fi-Comp Electronics	95	Radford Audio Ltd.	4
Flight Link Control Ltd.	114	Radford Laboratories Ltd.	11
Fraser-Manning Ltd.	133	Ralfe, P.	92
Future Film Developments Ltd.	118	Rank Film Equipment	9
		Rastra Electronics Ltd.	111
		R.C.S. Electronics	13
		Replecomps Ltd.	84
		R.E.W. Audio Visual Co.	134
		R.I. Audio	22
		Rola Celestion Ltd.	97
		R.S.T. Valves Ltd.	116
		Samsons (Electronics) Ltd.	112
		Scopex Ltd.	23
		S.C.S. Components	109
		Semicon Indexes Ltd.	102
		Servo & Electronics Sales Ltd.	8, 103
		Shure Electronics Ltd.	Cover iii
		Sinclair Radionics Ltd.	68, 69
		Sintel	24
		Sowler, E. A., Ltd.	133, 134
		Southern Aviation	18
		Special Products Ltd.	9
		Strumech Eng. Ltd.	20
		Sugden, J. E. & Co. Ltd.	22
		Sullivan Ltd.	10
		Surrey Electronics	134
		Swanley Electronics Ltd.	86
		Swift of Wilmslow	92
		Technomatic Ltd.	109
		Teleprinter Equipment Ltd.	102
		Tequipment Products (Tektronix U.K.) Ltd.	26
		Teleradio Special Products	134
		Telford Products Ltd.	11
		Thomson CSF/CTC	70
		T.O. Supplies (Teonex)	2
		Trampus Electronics	100
		Valradio Ltd.	6
		Wayne, Kerr, The, Co. Ltd.	21
		West London Direct Supplies	118
		Wilmslow Audio	133
		Wireless World Annual	105
		Wireless World Circards	108
		Wireless World Circuit Designs	120
		Wye Electronics Ltd.	14
		Z. & I. Aero Services Ltd.	4, 84
		Zettler (U.K.) Division	10

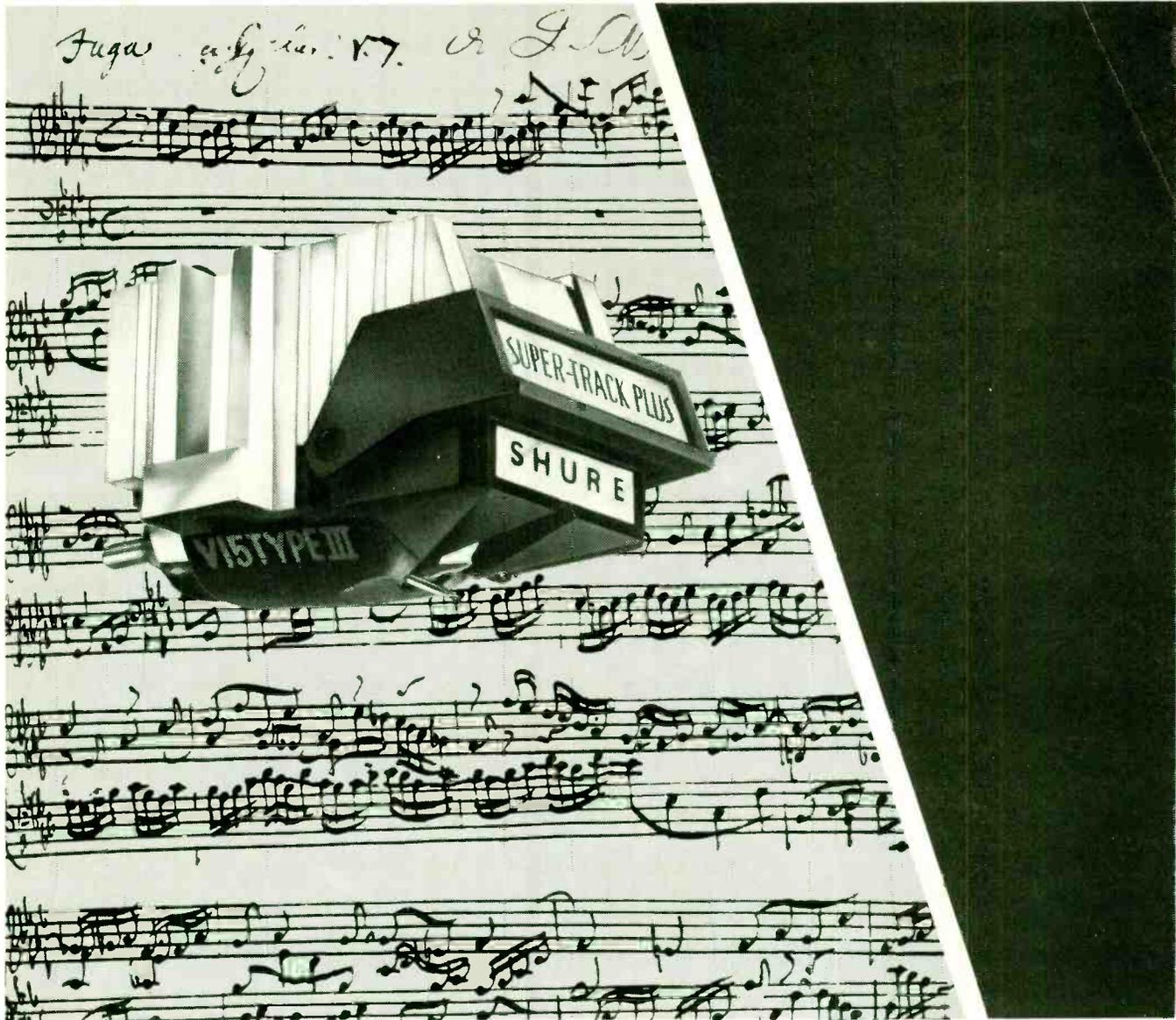

The Test of Time

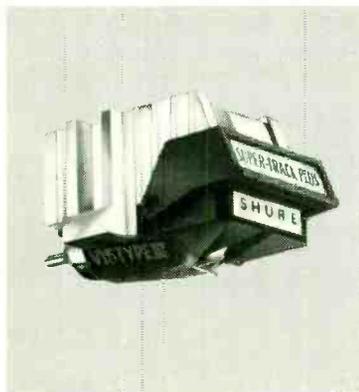

Critics were most generous in their praise when the Shure V-15 Type III pickup cartridge was introduced. The ultimate test, however, has been time. The original engineering innovations, the uniquely uniform quality and consistent performance reliability of the V-15 Type III have made it THE classic choice as the source of sound for the finest music systems, both here and abroad.

Consider making the relatively modest investment of a new cartridge to upgrade the performance of your entire hi-fi system. Why not ask Shure Electronics Limited for their recommendation?

Shure Electronics Limited
 Eccleston Road, Maidstone ME15 6AU
 Telephone: Maidstone (0622) 59881

The original manuscript by J. S. Bach shown is reproduced by kind permission of the Trustees of The British Museum.

I am at present using

Arm or Unit

Cartridge

Amplifier

Name

Address


Please recommend the best Shure cartridge to upgrade my system.





Before Concorde first took to the air...

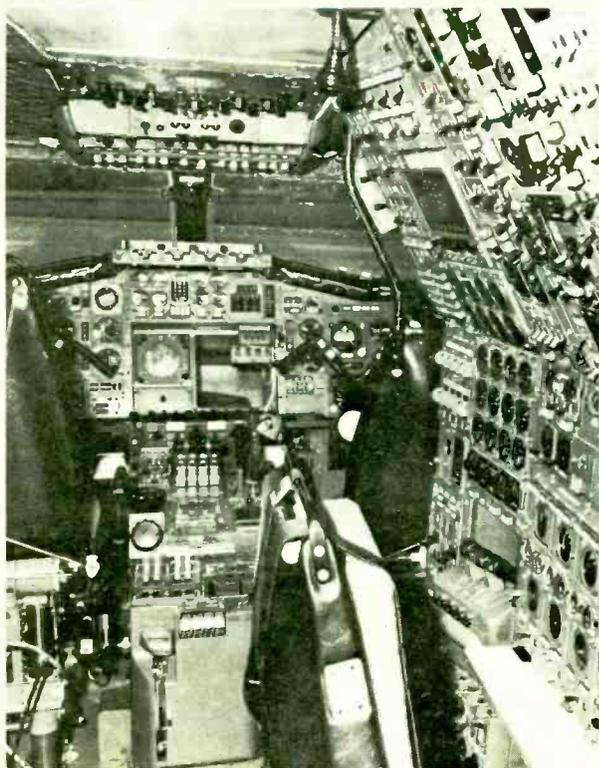**we made a
lot of contacts
on the
flight deck.**



Ersin Multicore 5-core solder was used for thousands of electrical connections on the British assembled Concorde. High-class connections! And Ersin Multicore quality will ensure that they stay connected. Before selection, Ersin Multicore Solders were subjected to rigorous testing against an extremely demanding international specification. They passed with (dare we say it?) flying colours. Ersin Multicore is always coming out best by test. The World's leading manufacturers of electronic equipment use Ersin Multicore Solder to ensure the utmost in reliability, efficiency and economy of soldered joints, whether they are making equipment for use in the sea, on land, in the air or in outer space. Write, on your Company's headed note paper, for technical information about Ersin Multicore Solder, Solder Chemicals and high purity EXTRUSOL for soldering machines and baths to:



**Multicore Solders
Limited**, Maylands Avenue
Hemel Hempstead, Herts. HP2 7EP
Tel: H. Hempstead 3636
Telex 82363

Steve Lane