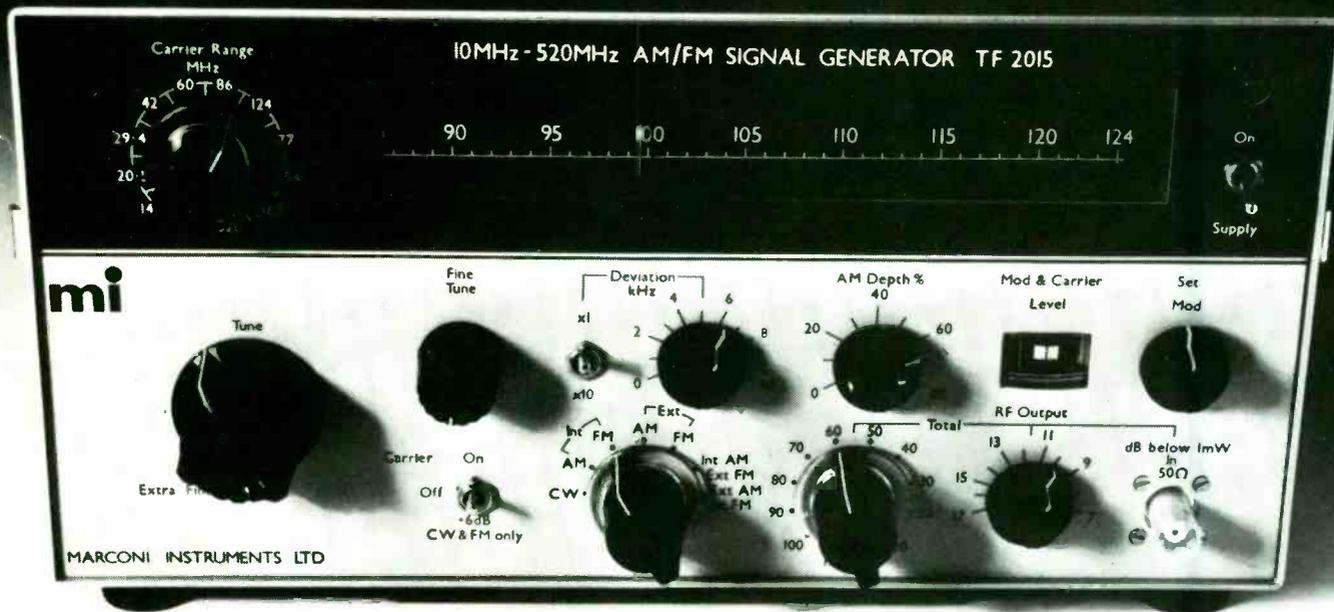


wireless world

FEBRUARY 1976 35p

Radio-code clock
New waveguide

Australia \$A1.20
Belgium Fr. 61.50
Canada \$1.50
Denmark Kr. 11.00
Finland Fmk. 6.20
Germany Dm. 4.50
Greece Dr. 45.00
Holland Dfl. 4.50
Italy L. 900
Malaysia M\$3.26
New Zealand \$NS1.20
Norway Kr. 10.00 incl. poms
Portugal Esc. 40.00
S. Africa R. 1.10
Spain Ptas 80.00
Sweden Kr. 6.90 incl. poms
U.S.A. \$1.50



mi's TF 2015 a wider view of signal generation...

The TF 2015 is a versatile 10-520 MHz signal generator with calibrated a.m. and f.m. and an accuracy of output level setting normally found only in instruments costing three times as much. A special system gives very fast tuning across the bands yet provides smooth control within the narrowest of passbands. Leakage radiation is carefully screened out to enable accurate measurements to be made even at levels below $1\mu\text{V}$.

Matched Synchronizer

The clip-on Synchronizer TF 2171 transforms the performance of TF 2015 into the equivalent of a synthesizer at less than half the comparable cost. The frequency is locked to crystal stability and can be dialled in 100 Hz. steps. Tuning is quick and easy - set the decade dials, switch to "lock" and tune the generator to the approximate

frequency and the synchronizer will finish the job for you. Now you can change the frequency by up to 2% using the decade dials **without touching the generator** - and all to an accuracy of 2 parts in 10^7 . It stays locked all day and doesn't degrade any aspect of the generator performance.

I.F. Probes

These are an invaluable aid to the testing of receivers with squelch or battery economiser circuits. These circuits are inactivated when the crystal-controlled signal from the probes is brought into the proximity of the receiver's i.f. strip. This makes it easy to tune the generator to a receiver when its channel frequency is unknown. The probes can also be used to check exact tuning by adjusting for zero beat.



mi: THE SIGNAL GENERATORS

MARCONI INSTRUMENTS LIMITED

Longacres, St. Albans, Hertfordshire, England, AL4 0JN · Telephone: St. Albans 59292. Telex: 23350.
A GEC-Marconi Electronics company.

WW-001 FOR FURTHER DETAILS

www.americanradiohistory.com

LEVELL

PORTABLE INSTRUMENTS

New for 1976

JANUARY

S	M	T	W	T	F	S
				1	2	3
4	5	6	7	8	9	10
11	12	13	14	15	16	17
18	19	20	21	22	23	24
25	26	27	28	29	30	31

FEBRUARY

S	M	T	W	T	F	S
1	2	3	4	5	6	7
8	9	10	11	12	13	14
15	16	17	18	19	20	21
22	23	24	25	26	27	28
29						

MARCH

S	M	T	W	T	F	S
	1	2	3	4	5	6
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30	31			

APRIL

S	M	T	W	T	F	S
				1	2	3
4	5	6	7	8	9	10
11	12	13	14	15	16	17
18	19	20	21	22	23	24
25	26	27	28	29	30	

MULTITESTER TYPE TM11

With over 100 basic ranges.



MAY

S	M	T	W	T	F	S
						1
2	3	4	5	6	7	8
9	10	11	12	13	14	15
16	17	18	19	20	21	22
23	24	25	26	27	28	29
30	31					

JUNE

S	M	T	W	T	F	S
		1	2	3	4	5
6	7	8	9	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30			

JULY

S	M	T	W	T	F	S
				1	2	3
4	5	6	7	8	9	10
11	12	13	14	15	16	17
18	19	20	21	22	23	24
25	26	27	28	29	30	31

AUGUST

S	M	T	W	T	F	S
	1	2	3	4	5	6
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30	31			

SEPTEMBER

S	M	T	W	T	F	S
			1	2	3	4
5	6	7	8	9	10	11
12	13	14	15	16	17	18
19	20	21	22	23	24	25
26	27	28	29	30		

OCTOBER

S	M	T	W	T	F	S
					1	2
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30
31						

NOVEMBER

S	M	T	W	T	F	S
	1	2	3	4	5	6
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30				

DECEMBER


S	M	T	W	T	F	S
			1	2	3	4
5	6	7	8	9	10	11
12	13	14	15	16	17	18
19	20	21	22	23	24	25
26	27	28	29	30	31	

- 50µV to 500V fsd. AC. } 3Hz to 200kHz
- 50pA to 500mA fsd. } above 500µV & 500nA.
- 90/+50dB mid scale. } Input R=100MΩ on V.
- 150µV to 500V fsd. DC. } Input R=100MΩ.
- 150pA to 500mA fsd. DC.
- 0.2Ω to 10GΩ Resistance at <0.7µW.
- D.C. Lin/Log ranges for nulling.

Send for literature covering our full range of portable instruments.

LEVELL ELECTRONICS LTD. Moxon Street, High Barnet, Herts. EN5 5SD
Tel: 01-449 5028/440 8686

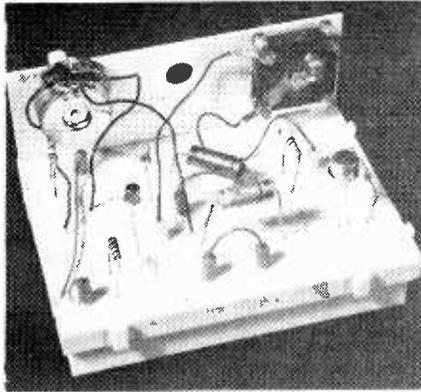S-DEC Solderless Breadboard 50p off + free solder board.



Designing circuits? It's easy with S-DEC! NO SOLDERING — just plug your components in. So they can be re-used indefinitely. As used by the Schools Project Technology Courses.

FREE with this offer — booklet giving a range of quick-assembly circuits for the S-DEC, including radio receiver; VHF radio microphone; 3-stage amplifier, and many others. Also, FREE control panel for mounting switches, lamps etc.


This offer also applies to the T-DEC, U-DEC, and the T- and U- super solder boards. Simply take this page to your local dealer, or send it direct to us.

S-DEC BREADBOARD + FREE SUPER SOLDER BOARD. £1.48 (send £1.80 to cover postage, packing and V.A.T.).

T-DEC + SUPER SOLDER BOARD £3.87	} covers postage, packing and V.A.T.
U-DEC A + SUPER SOLDER BOARD £4.31	
U-DEC B + SUPER SOLDER BOARD £7.71	

To use ICs with T and U-DEC A, 16 DIL adaptor with socket, £1.92; 10 to 5 adaptor with socket, £1.80.

NEW Low cost PB DEC Super Solder Boards.

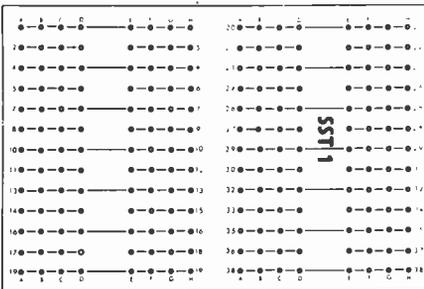

When your circuit is proved working on your DEC, simply plug the components into a Super Solder Board — a fibre-glass, drilled, roller-tinned finished circuit board using the same layout as the DEC breadboard. Once the components are plugged in, in the same positions as on the DEC, solder! (No cutting or drilling of contact rails.) The result — a perfect, finished, printed circuit board.

Super-solder boards are available in packs of 1 or 3 off.

SUPER SOLDER BOARD SSS-1 for use with S DEC circuits, only: 1 off £0.39; 3 off £1.00.


SUPER SOLDER BOARD SST-1 for discrete circuits: 1 off £0.59; 3 off £1.60.

SUPER SOLDER BOARD SSU-1 for discrete and DIL circuits: 1 off £0.59; 3 off £1.60.

SUPER SOLDER BOARD SSN-1 for discrete and DIL sockets. Up to 40-lead 0.6 in. DIL, and for the direct insertion of TO5 packages or 0.1 in. lead-out sockets: 1-off £0.69; 3-off, £2.00

When ordering, please also send £0.40 for post, packing and V.A.T.

Expo Reliant Drills and Kits.

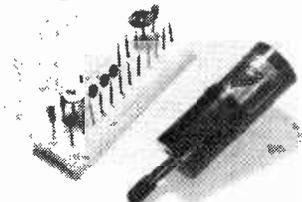


Powerful, miniature, low-voltage drills capable of sawing, grinding, burring, brushing and polishing — as well as drilling holes up to 3 mm. diameter through virtually any material.

The Expo drill operates from a power supply of 12V d.c. or, using the Titan transformer/rectifier unit (0220), from a.c. mains supplies at 200-250V a.c., 50Hz.

The Expo Reliant Mini Kit, consists of the Reliant Standard Drill (0150) and a set of 20 assorted tools (0305), providing a powerful, versatile kit for use both by the professional and the hobbyist. Prices: £9.40 including postage and packing, and V.A.T.

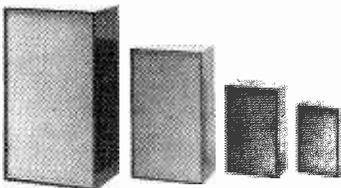Zippy Cabinets. Ideal For All Assembly Cabinets.



Robust ABS plastic assembly boxes, front panel designed to be cut and drilled, slots inside for mounting circuit boards attractive colouring and styling.

TP1 80 x 50 x 30mm £0.72 1 OFF TP3 155 x 90 x 50mm £1.62 1 OFF

TP2 115 x 65 x 40mm £1.27 1 OFF TP4 210 x 125 x 70mm £2.27 1 OFF

Discount for quantity prices include Post & VAT

Resist Coated Circuit Board Lowest price in U.K.
12" x 12" Glass Fibre 1/16 coated with resist £1.50 each.

Circuit Board Manufacture, Fast delivery, Low Price, any circuit board made in days.

NIGHT GUARD.

Dimmer with a difference, Guards your home from theft. SET, darkness comes, lights come on, dawn, lights go off. Dims room lights up to 500 watts. £5.95 + £1.05 VAT & POST

S DEC — T DEC — U DEC Accessories.

- 16 DIL ADAPTOR £0.99
- 16 DIL with socket £1.92
- Single ended leads (packs of ten) . . . £0.90
- Double ended leads (packs of ten) . . £0.90
- EXPERIMENT GUIDES used by all to teach electronics with DEC breadboards.
- GUIDE A 8 Projects £1.50
- GUIDE B 10 Projects £1.77
- GUIDE C 3 ADVANCED £0.90
- GUIDE D 10 Projects £2.40
- GUIDE E 23 Projects £4.20



P.B. ELECTRONICS LTD.

SCOTLAND

ELECTRONIC — SCIENTIFIC — INSTRUMENTS

Sales Office: 57 High Street, Saffron Walden, Essex. Tel: Saffron Walden (0799) 22876

Factory: 62 Largo Road, St. Andrews, Fife, Scotland. Tel: St. Andrews 2641.

WW-086 FOR FURTHER DETAILS

MEET OUR SCIENTISTS

Q1 1420 — SENIOR




1420

- Automatic selection of correct notation for result display (scientific or floating point)
- Dome keyboard for excellent response and preventing double entry input
- Algebraic mode operation
- Chain operations
- Change sign operation
- Three memories
- Display and memory exchangeable
- Trigonometric functions (sin, cos, tan)
- Inverse trigonometric functions (\sin^{-1} , \cos^{-1} , \tan^{-1})
- Radian or degree selectable
- π constant
- Logarithms (ln, log)
- Anti logarithms (e^x , 10^x)
- Combinatorial functions ($n!$, $\binom{n}{r}$, $(n)_r$)
- Normal distribution function ($Pr(x)$)
- Gamma function ($\Gamma(x)$)
- Group operations (Σz , \bar{O} , \bar{X} , $|x|$)
- Group controls ($K!$, $K!$, $\Sigma!$, $\Sigma!$ CLGRP)
- Power function (y^x)
- Reciprocal ($1/x$)
- Square root (\sqrt{x})
- Square (x^2)
- Sum of squares (Σx^2)
- Summation (ΣX)
- Item count (n)
- Mean value (\bar{X})
- Mixed chain operations with parentheses approach (up to two levels)

- 14-digit LED display
- 10-digit mantissa with sign and 2 digit exponent with sign for data entry or results ($10^{99} \sim 10^{-99}$)

PRICE: £61.55 (Excluding VAT)

Q1 1421 — PROGRAMMABLE

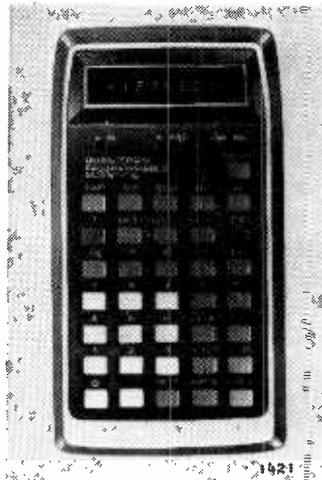

1421

- Reverse polish notation
- Display and Y-register exchangeable
- One accumulating memory (Memory store, Memory recall, $M + X$, $M - X$ and $M + X^2$)
- Trigonometric functions (sin, cos, tan)
- Inverse-trigonometric functions (\sin^{-1} , \cos^{-1} , \tan^{-1})
- Radians and degrees exchangeable
- π constant
- Logarithms (ln, log)
- Anti-logarithms (e^x)
- Power function (y^x)
- Reciprocal ($1/x$)
- Square root (\sqrt{x})
- Square (X^2)

IT CAN LOAD ANY 102 STEPS PROGRAM TO HELP YOU SOLVE THE REPEATED, ENORMOUS, COMPLEX PROBLEMS:

The Qualitron Programmable Calculator can be used to memorize any combination of key entries while in the LOAD mode, then automatically plays back the programmed sequences as often as desired in the RUN mode.

Up to 102 steps can be stored in multiprogram sequence blocks. Each block, or program can be executed individually or you can make the decision to branch to specific program, run each in series or perform intermediate calculations from the keyboard.

BESIDES HAVING THE CAPABILITY OF A SCIENTIFIC CALCULATOR:

- 9-digit LED display
- 8 digits capacity for data entry or results ($10^{99} \sim 10^9$)
- Full floating point
- Automatic display blanking
- Three-register operational stack
- Change sign operation

PRICE: £45.97 (Excluding VAT)

Q1 1439—FINANCIAL



1439

SPECIFICATION

- 9 digit green tube display
 - 8 digits capacity for data entry or results ($10^9 \sim 10^2$)
 - Fixed point (0.1, 2, 7 places), or full floating point selectable
 - Dome keyboard for excellent response and preventing double entry input
- BASIC FUNCTION (+, -, x, %) AND MEMORY**
- Algebraic mode operation
 - Constant operations
 - Repeat operations

- Chain operations
 - Percentage with automatic add-on and discount
 - Change sign operation
 - Four memories
- SPECIAL FUNCTION**
- Financial operations
 - Cost sell margin operators
 - Trend line operations
 - Delta percentage operations
 - Item count (n)
 - Mean value (\bar{X})
 - Square root (\sqrt{x})
 - Summation (ΣX)
 - Sum of squares (ΣX^2)

PRICE: £24.63 (Excluding VAT)

Q1 1419 — ADVANCED



1419

SPECIFICATION

- 14 digit LED display
 - 10 digit mantissa with sign and 2 digit exponent with sign for data entry or results ($10^{99} \sim 10^{-99}$)
 - Automatic selection of correct notation for result display (scientific or floating point)
 - Dome keyboard for excellent response and preventing double entry input
- BASIC FUNCTION (+, -, x, %) AND MEMORY**
- Algebraic mode operation
 - Constant operations
 - Repeat operations
 - Chain operations
 - Change sign operation

- Display and Y register exchangeable
 - One accumulating memory
 - Display and memory exchangeable
- SPECIAL FUNCTION**
- Trigonometric functions (sin, cos, tan)
 - Inverse trigonometric functions (\sin^{-1} , \cos^{-1} , \tan^{-1})
 - Hyperbolic functions (sinh, cosh, tanh)
 - Inverse hyperbolic functions (\sinh^{-1} , \cosh^{-1} , \tanh^{-1})
 - Radian or degree selectable
 - π constant
 - Logarithms (ln, log)
 - Anti-logarithms (e^x , 10^x)
 - Power function (y^x)
 - Reciprocal ($1/x$)
 - Square root (\sqrt{x})

PRICE: £31.25 (Excluding VAT)

Q1 1444 — SLIDE RULE



1444

SPECIFICATION

- 9 digit green tube display
- 8 digits capacity for data entry or results ($10^9 \sim 10^2$)
- Full floating point
- Floating negative sign
- Dome keyboard for excellent response and preventing double-entry input
- Automatic display blanking


BASIC FUNCTION (+, -, x, %) AND MEMORY

- Algebraic mode operation
- Constant operations
- Repeat operations
- Chain operations
- Percentage with automatic add-on and discount
- Change sign operation
- Display and Y-register exchangeable
- One accumulating memory

SPECIAL FUNCTION

- Reciprocal ($1/x$)
- Square root (\sqrt{x})
- Square (x^2)

PRICE: £18.62 (Excluding VAT)

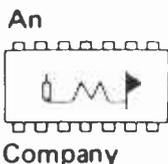

Company

IMTECH PRODUCTS LTD


IMP HOUSE, ASHFORD ROAD, ASHFORD, MIDDX. Tel: Ashford 44211. Telex: 936291

Audio Laboratory Instruments

To expand the distribution of Audio Laboratory Instruments RADFORD are looking for new dealer/agents outside the United Kingdom. If you are a supplier of laboratory instruments to professional and industrial end users it could be to your advantage to learn more about RADFORD audio measuring equipment.

Write today for leaflets and details of franchised dealership.

Radford Laboratory Instruments Ltd
Ashton Vale Road
Bristol BS3 2HZ England

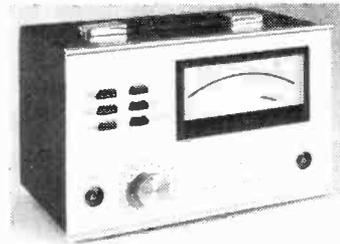

LDO3. Low Distortion Oscillator

Frequency range: 10Hz – 100kHz.
Distortion: Distortion less than 0.002% over audio band.
Size: 17" x 7" x 8 $\frac{3}{4}$ ". £275.00

LDO3B. Low Distortion Oscillator

As LDO3 but additionally fitted with output amplifier and transformer providing a 600 ohm floating balanced output.
Unbalance: –80dB. 1kHz. –60dB 10kHz. £375.00

DMS3. Distortion Measuring Set

Frequency range: 5Hz – 50kHz.
Measurement down to 0.001%.
Size: 17" x 7" x 8 $\frac{3}{4}$ ". £225.00

HSV1. High Sensitivity Voltmeter

Average reading: 10 μ V to 300V f.s.d. £125.00

HSV2. High Sensitivity Voltmeter

True r.m.s. reading. 10 μ V to 300V f.s.d. £175.00

ANM1. Audio Noise Meter and High Sensitivity Voltmeter

Average reading: 10 μ V to 300V f.s.d.
Includes Wide band, Audio band, IEC curve 'A' and CCIR weighting networks. Illustrated above. £150.00

ANM2. Audio Noise Meter and High Sensitivity Voltmeter

As ANM1 but true r.m.s. reading. £200.00

WW—022 FOR FURTHER DETAILS

“Where can I get an RF Generator nowadays that's easy to use, reliable, robust but not too expensive?”



“Here”—AVO's new HF 135—a really useful professional RF generator ideal for repair bench or test lab.

Wide frequency range—eight bands from 100kHz to 240MHz. Calibration accuracy conservatively rated at $\pm 1\%$ right across the range. Output level from 1 μ V to 100mV (± 6 dB). AF Signal source facility (1kHz). Input for external modulation. All wrapped up in a tough metal cabinet with ergonomically designed front panel and complete with connectors, crocodile clips and the AVO guarantee of reliability, serviceability, and accuracy at a sensible price.

For descriptive leaflet and name of your nearest stockist, phone or write:




Avo Limited, Archcliffe Road,
Dover, Kent. CT17 9EN.
Tel: 0304 202620 Telex: 96283.

Thorn Measurement Control and Automation Division

WW—089 FOR FURTHER DETAILS

FAST RESPONSE STRIP CHART RECORDERS


Made in USSR

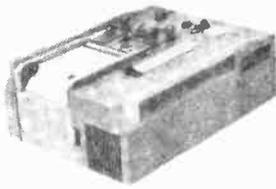

Type H3020-1
Single pen

Specification

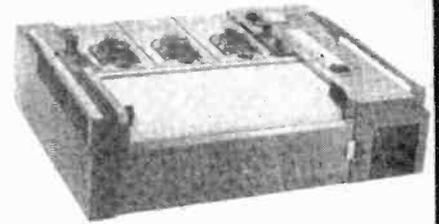- Basic error 2.5%
- Sensitivity 8mA F.S.D.
- Response 0.2 sec.
- Width of each channel 80mm
- Chart speeds, selected by push buttons 0.1-0.2-0.5-1-2.5-5-12.5-25mm/sec.
- Chart drive 200-250v 50Hz



Type H3020-3
Three-pen

- Recording:** Syphon pen directly attached to moving coil frame, curvilinear co-ordinates
- Equipment:** Marker pen, Timerpen, Paper footage indicator, 10 rolls of paper, connectors, etc.
- Dimensions:** H320-1: 285x384x16.5mm
H320-3: 475x384x16.5mm
- PRICE:** H320-1 £108.00
H320-3 £160.00
Exclusive of VAT

Available for immediate delivery

Z & I AERO SERVICES LTD.

44A WESTBOURNE GROVE, LONDON W2 5SF

Tel. 01-727 5641

Telex: 261306


WW-050 FOR FURTHER DETAILS

“Where can I get a Universal Bridge that’s good enough for the labs, simple to use and tough enough for the shop floor and doesn’t cost a fortune?”

“Here”—AVO’s Universal Bridge B150 Mk. 3 gives you measurement of resistance, capacitance, inductance accurate to 1%, can be used anywhere, it’s battery powered. And anyone can use it, connections are simple and readings easy to take—with no calculations thanks to the mechanical in-line digital display and interlocking units selector.

The B150 Mk. 3—for use in production, quality control, development labs—even at goods inwards. Tough metal cabinet, and the AVO guarantee of reliability, serviceability and accuracy, all at a price that’s a pleasant surprise. From good distributors everywhere.

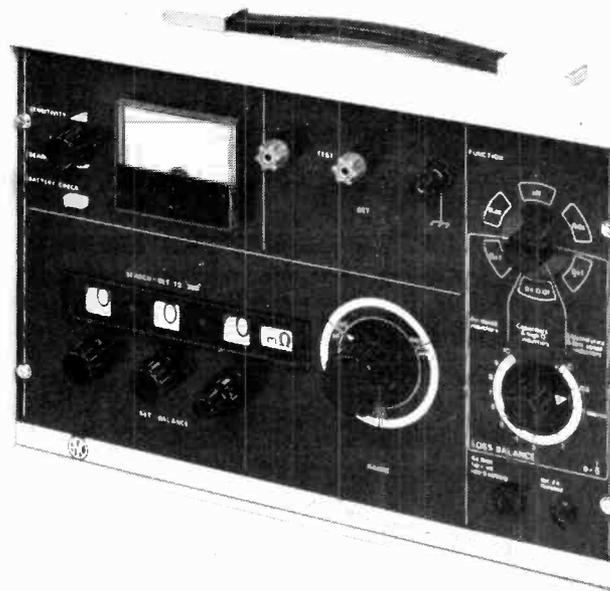Ring us for the name of your nearest stockist or for fuller details of AVO’s Universal Bridge B150 Mk. 3.




Avo Limited, Archcliffe Road,
Dover, Kent. CT17 9EN.
Tel: 0304 202620 Telex: 96283.

Thorn Measurement Control and Automation Division

WW-090 FOR FURTHER DETAILS

brandenburg's Olympian view.

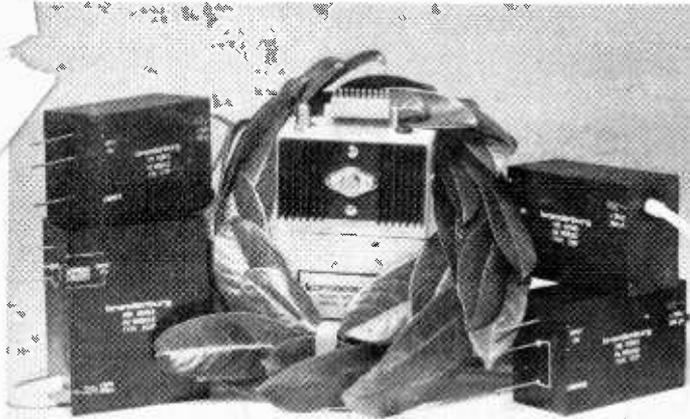

Our 200 Series and 479 HV supply modules.

Brandenburg's range of HV power supplies and associated equipment is unequalled by any other British manufacturer.

Take our 200 Series for instance. Totally resin encapsulated to provide high voltages for C.R.T. displays, storage tubes, projection systems and many other applications where a compact and reliable HV source is required.

Offering all the advantages of miniaturisation and standardisation of design, the 200 Series units come either regulated or unregulated within the output range 4kV to 20kV.

Or our 479 Photomultiplier supply module. Incorporating a low drift reference voltage source, this module is designed to provide stable, low ripple high voltages for a wide range of photomultipliers. The 479 provides a positive output which is adjustable over the range 500V to 3kV, and a maximum current of 2.5mA.


We at Brandenburg believe Britain does not do enough at or for the Olympic Games. So, as we are British through and through, we thought we would get our industry involved.

Please use our enquiry number and, apart from receiving full information on our 200 Series and 479 module, it could be the first step in your winning a free trip to the Montreal Olympics. We'll send you an entry form for our Olympian Competition which is, we are sure you'll agree, great fun. Get in training; use your pen now.

brandenburg


Due to our continued expansion, we have vacancies for sales engineers, development engineers and production personnel.

NT 3302 · fet fm tunerhead + AM gang

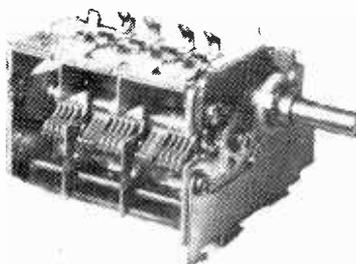

- * FET input stage
- * 3 stage tuning
- * 3:1 gearing
- * 335pF AM gangs
- * AFC facility

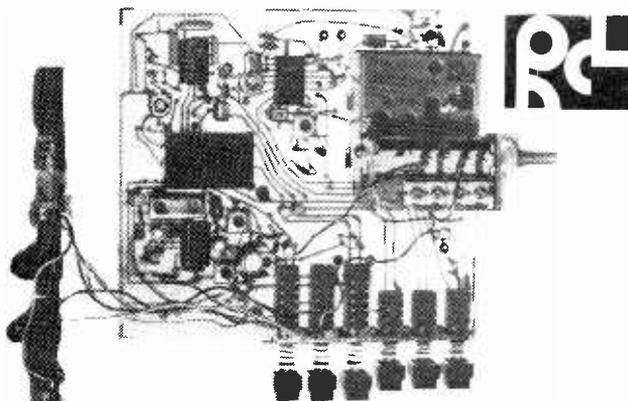TOKO's latest FM tunerhead is available for immediate evaluation with the Broadcasting 9000 tuner chassis- an AM (LW/MW) and mpx FM chassis, with switches inc.



*distributed by Ambit international, 37 High St
Brentwood, Essex. tel:216029, tlx:848095.*

ALL 9000 chassis enquiries to Ambit please.

OEM enquiries to TOKO UK, Ward Royal Parade,
Alma Road, Windsor, Berkshire. tel:54057, tlx:848095.

WW-063 FOR FURTHER DETAILS

QUARTZ CRYSTALS -FAST!



AEL GATWICK HOUSE, HORLEY, SURREY, ENGLAND

Tel. Horley (02934) 5353

Telex 87116 (Aerocon Horley) · Cables: Aerocon Telex Horley


WW-033 FOR FURTHER DETAILS

Brandenburg Limited,
939 London Road,
Thornton Heath,
Surrey CR4 6JE, England.
Telephone: 01-689 0441
Telex: 946149



WW-062 FOR FURTHER DETAILS

METER PROBLEMS?

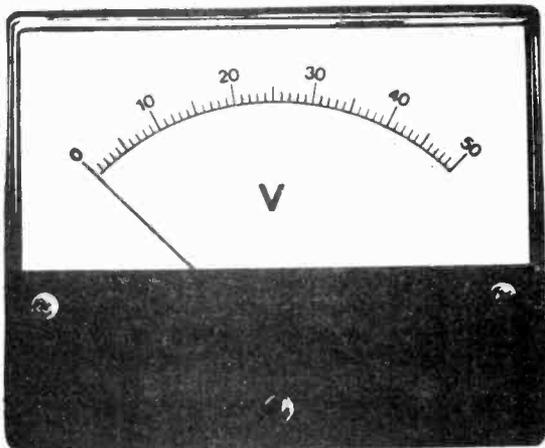

137 Standard Ranges in a variety of sizes and stylings available for 10-14 days delivery. Other Ranges and special scales can be made to order.

Full Information from:

HARRIS ELECTRONICS (London)

138 GRAYS INN ROAD, W.C.1 Phone: 01/837/7937

WW-016 FOR FURTHER DETAILS

nombrex



MODEL 40
WIDE RANGE AUDIO GENERATOR
£42.49 + VAT

- ★ 4 RANGES, 10Hz-100 KHz.
- ★ SINE AND SQUARE WAVE OUTPUT.
- ★ DUAL CALIBRATED ATTENUATOR.
- ★ STABILIZED OUTPUT LEVEL 1 V.

*Trade and Export enquiries welcome.
Send for full technical leaflets
Post and packing £1.00 extra*

**NOMBREX LTD., POUND PLACE, WOLBOROUGH STREET
NEWTON ABBOT, DEVON TQ12 1NE
Tel. Newton Abbot 68297**



WW-054 FOR FURTHER DETAILS

LABORATORY INSTRUMENTS

G5

WIDE BAND AUDIO SIGNAL GENERATOR

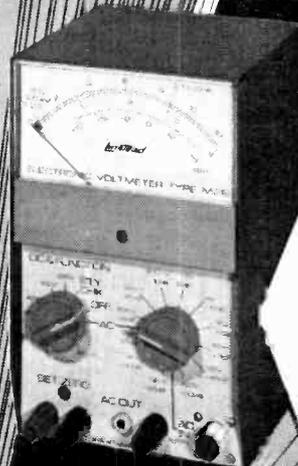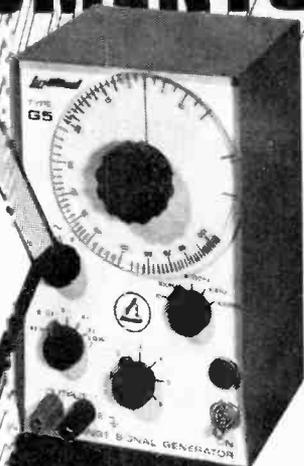a high accuracy solid state sine/square wave generator with 600 ohm attenuator output or low impedance output delivering 3 watts into a 5 ohm load



H2B

HIGH IMPEDANCE AC/DC MILLIVOLT-METER

(The Modern equivalent of the Valve Voltmeter) an AC/DC wide range meter with 20 scales covering 1.2 mV to 400 volts FSD incorporating a power scale in decibels.

LINSTEAD

MANUFACTURING CO. LTD.


ROSLYN ROAD LONDON N15 5JB

01 - 802 5144

IRELAND: LENNOX LTD P.O. BOX 212A DUBLIN 2. **DENMARK:** SCANFYSIK AB 13/15 HJORRINGGADE DK-2100 COPENHAGEN. **SWEDEN:** EMI SVENSKA AB TRITONVAGEN 17 FACK S-171 19 SOLNA 1. **NORWAY:** EMI NORSK AS POSTBOKS 42 KORSVOLL OSLO 8. **MALAYSIA:** LEC Sdn Bhd P.O. BOX 60 BATU-PAHAT. **SOUTH AFRICA:** PROTEA (PTY) 38 FARADAY STREET, JOHANNESBURG.

WW-057 FOR MORE DETAILS

Alice Broadcasting STM6

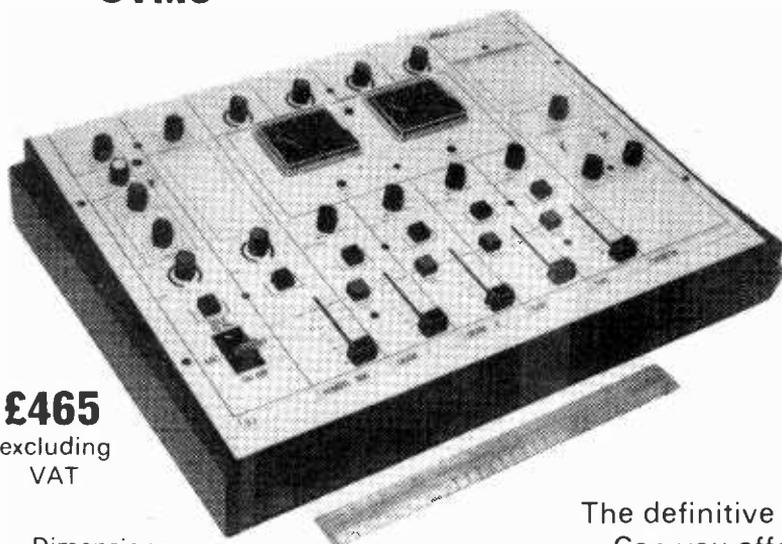

£465
excluding
VAT

Dimensions
20" x 15" x 4½"

Six Channel Stereo Transmission Mixer (ALICE'S BABY)

INPUTS

Microphones
Lines/Tape/Carts
Pick-ups
Off Air

OUTPUTS

Lines
P.A.
Headphones
Recording

The definitive DJ/OB/Production Mixer
Can you afford to use anything use?


Contact Chris Walden on Windsor 51056/7

ALICE (STANCOIL LTD.), 38 ALEXANDRA ROAD, WINDSOR, BERKS, ENGLAND

Also available from Roger Squires, London and Manchester

WW-071 FOR FURTHER DETAILS

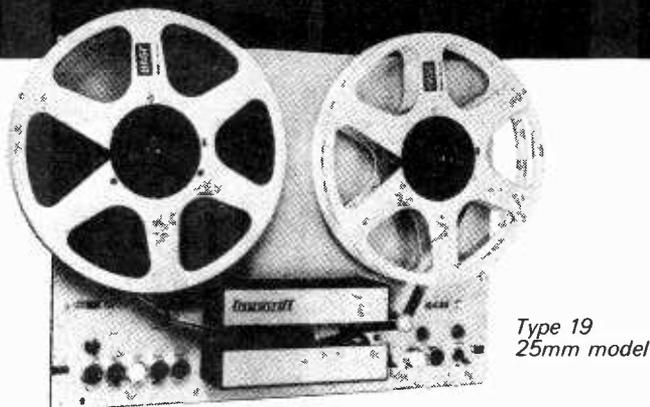brenell PROFESSIONAL TAPE TRANSPORTS and multi-channel electronics for studio and industrial use



- * Tapewidths up to 25mm
- * Speeds: 3mm/s minimum up to 152cm/s max
2 and 4 speed models
- * Reel Capacity up to 29cm
- * Remote Control Facility
- * Tape Tension Control
- * Automatic Interlock against misuse
- * Special models to customer requirements

**Finance
available**


BRENNELL ENGINEERING CO LTD

231-5 Liverpool Road, London N1 1LY. Tel: 01-607-8271

Switching problems? Rely on Zettler.

Producing 30 basic types of relay and 15,000 variants with regard to contact stacks, terminals, energizing current and contact material, Zettler is among the largest manufacturers of electro-mechanical components.

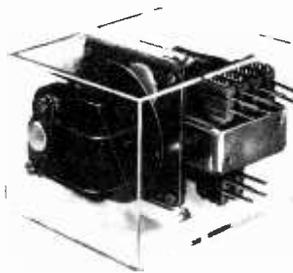Our product range comprises:
Low profile (platform) · Timing · Miniature · Low contact capacity · Hermetically sealed · Stepping · Mains switching · Latching · Contact stacks · Solenoids



AZ 103 Repetition Relay
Motor and gear system cam relay, intended as a programming unit for controlling recurring processes. Supplied in many varieties to suit special circumstances.
Spec.: MIL-R-5757.
Constant, low contact resistance. Independent of ambient conditions in temperature range -55 °C to +75 °C.
Long life,
10⁷ "dry-circuit" operations.

We resolve your switching problems rapidly and expertly. Please contact us for further details.



ZETTLER Zettler
UK Division
Brember Road
Harrow, Middx. HA2 8AS. Tel. (01) 4220061

A member of the worldwide ZETTLER electrical engineering group, est. 1877

WW-009 FOR FURTHER DETAILS

40 years

DANAVOX

INTERNATIONAL

DANAVOX (GT. BRITAIN) LTD.

"BROADLANDS" BAGSHOT ROAD,
SUNNINGHILL, ASCOT, BERKS.

TEL: 0990 23732/6; TELEX: 84584

of research... "on components and accessories for dictating machines, tele-communications, hearing aids and electroacoustic equipment etc."



STETOCCLIP JUNIOR 60 HEADSET




STETOCCLIP LIGHTWEIGHT HEADSET



SENIOR STETOCCLIP HEADSET



STETOMIKE BOOM MICROPHONE HEADSET

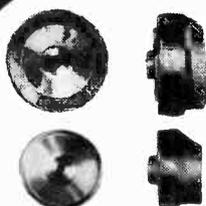


STANDARD & SUB-MINOR EARPHONES




PLASTIC EARHANGERS



DANAMIC FIDELITY EARSET

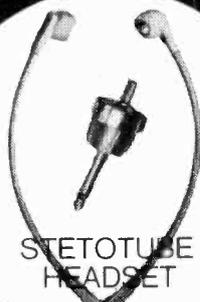

STETOTUBE HEADSET

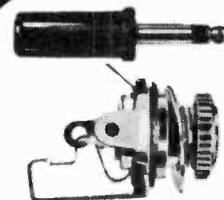


2.5 mm and 3.5 mm JACK PLUGS & SOCKETS



DANASOUND HEADSET



DANASONIC INDUCTION AUDIO LOOP RECEIVER

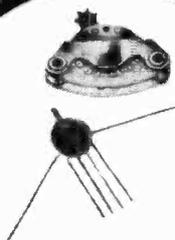

SUBMINIATURE SWITCHES

WW-053 FOR FURTHER DETAILS

Eddystone Model 990R

professional VHF receiver

Designed for fixed or mobile point-to-point service or for broadcast monitoring, this solid-state single-conversion VHF receiver is finding increasing use in other professional applications such as the meteorological service, radio astronomy, aerial investigations, civil aviation and in radio laboratories.

Continuous coverage is provided from 27 MHz to 240 MHz for CW, AM and FM reception, with exceptional stability and sensitivity. A crystal filter to suit 12.5 kHz, 25 kHz or 50 kHz channel spacing can be supplied to suit customer requirements; and output is available for panoramic display.



DCA NO. 10D/CA/5967

Eddystone Radio Limited

Member of Marconi Communication Systems Limited

Alvechurch Road, Birmingham B31 3PP, England
Telephone: 021-475 2231. Telex: 337081

A GEC-Marconi Electronics Company



WW-072 FOR FURTHER DETAILS

NEW FROM
STRUMECH

Electric powered
winch (110 volt, 5 amp)
Bolts directly onto
existing towers without
modification. Send for leaflet.
Price £115 ex works.

VERSATOWER

Strumech Engineering Limited
Coppice Side, Brownhills, Walsall, West Midlands
Telephone: Brownhills 4321

WW-068 FOR FURTHER DETAILS

A NEW DIMENSION IN SOLDERING

Iso-Tip Cordless Soldering Iron

Ideal for factory, field servicing, laboratory or home, the Iso-Tip Cordless offers a great advance in soldering. It is completely portable, heats in 5 seconds and recharges automatically in its own stand.

The Iso-Tip is powered by long-life nickel cadmium batteries giving tip performance up to 50 watts with a temperature of 370°C. Tips are available in five different sizes ranging from Micro to Heavy Duty to meet all soldering requirements.

Greenwood Electronics

Portman Rd, Reading RG3 1NE, England.
Telephone: Reading (0734) 595844.
Telex: 848659.



WW-040 FOR FURTHER DETAILS

Join the Digital Revolution

Teach yourself the latest techniques of digital electronics

Computers and calculators are only the beginning of the digital revolution in electronics. Telephones, wristwatches, TV, automobile instrumentation — these will be just some of the application areas in the next few years

Are you prepared to cope with these developments?

This four volume course — each volume measuring 11 $\frac{3}{4}$ " x 8 $\frac{1}{4}$ " and containing 48 pages — guides you step-by-step with hundreds of diagrams and questions through number systems, Boolean algebra, truth tables, de Morgan's theorem, flipflops, registers, counters and adders. All from first principles. The only initial ability assumed is simple arithmetic

At the end of the course you will have broadened your horizons, career prospects and your fundamental understanding of the changing world around you

Digital Computer Logic and Electronics

A Self-instructional Course

C. P. Gore MA (Camb.)
A. W. Linnell BA (Camb.)

Book 1 Basic computer logic

Book 2 Logical circuit elements

Book 3 Designing circuits to carry out logical functions

Book 4 Flipflops and registers



Design of Digital Systems
Book 1 Computer Arithmetic

Also available — a more advanced course in 6 volumes:

1. Computer Arithmetic
2. Boolean Logic
3. Arithmetic Circuits
4. Memories & Counters
5. Calculator Design
6. Computer Architecture

Offer. Order this together with Digital Computer Logic & Electronics for the bargain price of £9.25, plus 50p p&p.

£5.95 plus 50p p&p

Design of Digital Systems contains over twice as much information in each volume as the simpler course Digital Computer Logic and Electronics. All the information in the simpler course is covered as part of the first volumes of Design of Digital Systems which, as you can see from its contents, also covers many more advanced topics

**Designer
Manager
Enthusiast
Scientist
Engineer
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

Guarantee — no risk to you

If you are not entirely satisfied with Digital Computer Logic and Electronics or Design of Digital Systems, you may return them to us and your money will be refunded in full, no questions asked.



£3.95

plus 50p packing and surface mail anywhere in the world.

Quantity discounts available on request.

Payment may be made in foreign currencies.

VAT zero rated.

To: Cambridge Learning Enterprises,
FREEPOST, St. Ives, Huntingdon, Cambs.
PE17 4BR

*Please send me set(s) of Digital Computer Logic and Electronics at £4.45 each, p&p included

*or set(s) of Design of Digital Systems at £6.45 each, p&p included

*or combined set(s) at £9.75 each, p&p included

Name

Address

.

*delete as applicable
No need to use a stamp — just print FREEPOST on the envelope.

ww2



transformers

mains, audio, microphone, ferrite core and other wound components

A wide range of transformers manufactured in production quantities to customers individual requirements

Prompt Prototype Service available

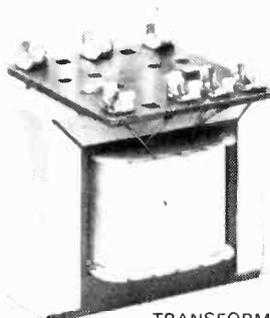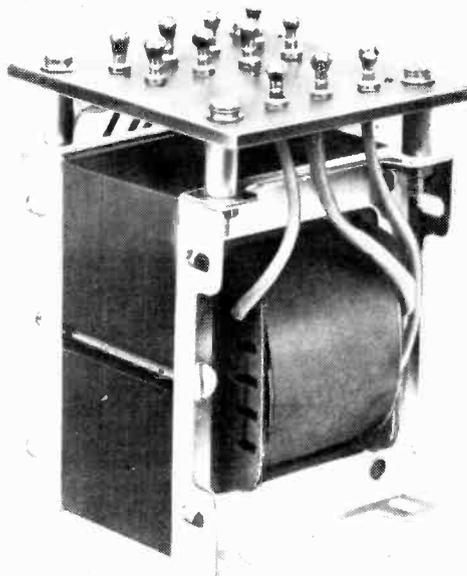TRANSFORMER WITH UNIVERSAL END FRAMES AND TURRET LUG CONNECTIONS



MICROPHONE TRANSFORMER IN MUMETAL CAN

TRANSFORMER WITH TWO HOLE CLAMP AND SOLDER TAG CONNECTIONS

Drake Transformers Limited

Telephone: Billericay 51155

Kennel Lane, Billericay, Essex.


WW-043 FOR FURTHER DETAILS



SHEET METAL PUNCHES

for quick, clean holes

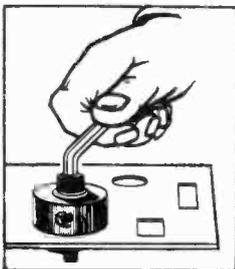- Easiest and quickest way of punching holes in sheet metal (up to 1.625mm)
- Simple operation • 100% British
- Burr-free holes—no jagged edges
- 57 Metric and Linear sizes (Lists on application)




Used by all Government Services and most industries
Wholesale and Export enquiries to:

"Q-MAX" (ELECTRONICS) LTD
44 PENTON STREET LONDON N19 0AA Tel: 01278 2500

WW-005 FOR FURTHER DETAILS

J E S AUDIO INSTRUMENTATION

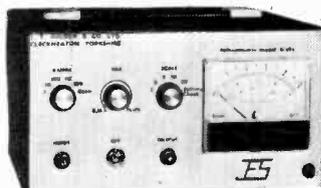

Illustrated the Si 451 Millivoltmeter — pk-pk or RMS calibration with variable control for relative measurements. 50 calibrated ranges **£50.00**

Si 452 **£40.00**

Si 453 **£50.00**

Distortion Measuring Unit.

Low distortion Oscillator.

15 Hz — 20 KHz — .01%

Sine — Square — RIAA

PRICES plus VAT

J. E. SUGDEN & CO. LTD. Tel. Cleckheaton (0274) 872501
GARR STREET CLECKHEATON, W. YORKS BD19 5LA

WW-010 FOR FURTHER DETAILS

Telford Oscilloscope cameras

Type A modular system with widest range of film backs, lenses, viewing systems and adaptors to meet virtually all requirements.

Plus Inexpensive Type P (prices from £50) utilizing coaterless Polaroid® film and Robot with economical 35mm film for continuous feed.

More complete details available on request from:

Telford PRODUCTS LTD.

WADSWORTH ROAD PERIVALE GREENFORD MIDD. ENGLAND Telephone: 01-998 1011 Telex: 935524

DAVALE A MEMBER COMPANY OF BENTIMA INDUSTRIES LIMITED

® Reg. Trade Mark.

WW-031 FOR FURTHER DETAILS

Complete the coupon and we'll send you our complete, new catalogue.



The new Heathkit catalogue is now out. Full as ever with exciting, new models. To make building a Heathkit even more interesting and satisfying.

And, naturally, being Heathkit, every kit is absolutely complete. Right down to the last nut and bolt. So you won't find yourself embarrassingly short of a vital component on a Saturday evening - when the shops are shut.

You'll also get a very easy to understand instruction manual that takes you step by step through the assembly.

Clip the coupon now and we'll send you your copy to browse through.

With the world's largest range of electronic kits to choose from, there really is something for everyone.

Including our full range of test equipment, amateur radio gear, hi-fi equipment and many general interest kits.


So, when you receive your catalogue you should have hours of pleasant reading.

And, if you happen to be in London or Gloucester, call in and see us. The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory in Bristol Road.


At either one you'll be able to see for yourself the one thing the catalogue can't show you.

Namely, how well a completed Heathkit performs. Heath (Gloucester) Limited, Dept. WW-26, Bristol Road, Gloucester, GL2 6EE. Tel: Gloucester (0452) 29451.


30 MHz Frequency counter

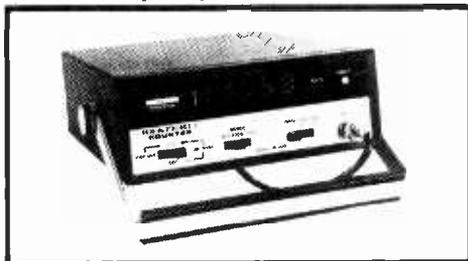

SSB Transceiver

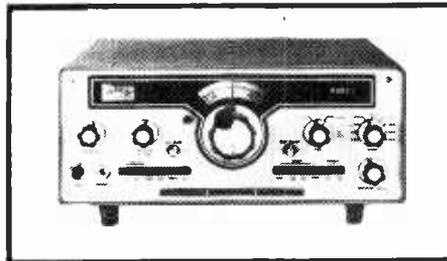

Digital electronic stop watch

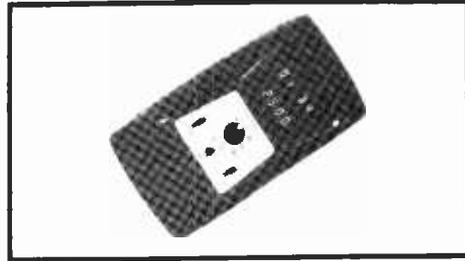

The new Heathkit catalogue. Out now. FREE.

To: Heath (Gloucester) Limited, Dept. WW-26, Gloucester, GL2 6EE.
Please send me my Heathkit catalogue.




Name _____ Address _____
Postcode _____

SPECIALISTS IN COIL AND TRANSFORMER WINDING:

Torroidal: c core: high speed high turn bobbin winding: chokes and wave winding any quantity, any rating.

Send for new catalogue.

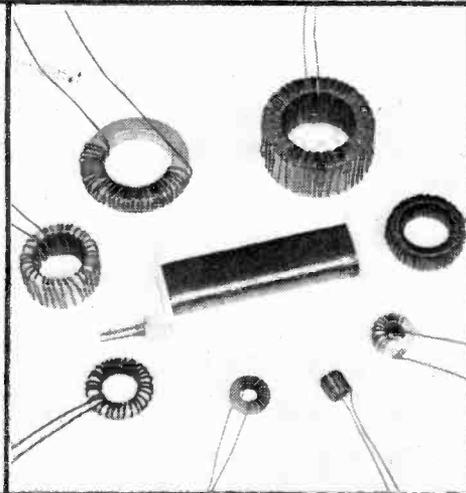

WYK

Electronics Limited

**27 STATION ROAD
BRIMINGTON
CHESTERFIELD
DERBYSHIRE, ENGLAND**
TEL: 0246 70297/8/9
TELEX 54284

WW-011 FOR FURTHER DETAILS

Bridge in a thousand



One part in one thousand is the accuracy of Universal Bridge B224 from 10 ohms to 1 gigohm, 0.1pF to 10 microfarads and 1 nanomho to 100 millimhos. Monitor its 1592Hz source frequency and also get 0.1% from 1mH to 10kH. With reducing accuracy, coverage extends above and below the ranges quoted, on R, C, G and L. Resistive and reactive terms read simultaneously. Sockets for 200Hz - 50kHz operation. Internal rechargeable battery. Many other valuable features detailed in Data Sheet B224.

WAYNE KERR

A member of the Wilmot Breedon group

For more information phone Bognor (02433) 25811, or write to Wayne Kerr, Durban Rd., Bognor Regis, Sussex PO22 9RL


WW - 064 FOR FURTHER DETAILS

PETITE PRECISION!

A 12V DC POWER TOOL FOR THE DESIGN AND RESEARCH ENGINEER
AVAILABLE IN KIT FORM OR SEPARATES

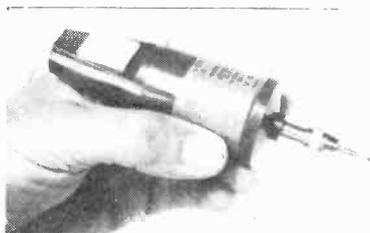EXAMPLE OF FRENCH PRECISION ENGINEERING

Diameter 33mm
Weight 160g
Length 125mm
Torque 105cmg
RPM
approx. 5000/6000
at 12V DC
Power 9/14V DC
Batteries
or AC/DC
transformer



Drill. £7.00 P&P 35p



Flexible drive.
£5.00
P&P 25p

Now in use by the following:
GPO, BBC, Atomic Energy
Authority, British Nuclear
Fuels, Weekend TV, Ministry
of Defence, Hospitals,
Opticians, etc.



Stand £3.76
P&P 35p

UK DISTRIBUTOR

PRECISION PETITE LTD
119A HIGH STREET
TEDDINGTON, MIDDX. UK
TEL. 01-977 0878

SAE for leaflets, price list and order form

WW-038 FOR FURTHER DETAILS



ALSO AVAILABLE AT LEADING BOOKSTALLS

The big four from Wireless World

Wireless World Annual 1976

1 The world of electronics, television, radio/audio is on parade in the second great Wireless World annual. Constructional articles include making a photographic timer. Surveys cover video, magnetic tape compatibility, electronic ignition and radio astronomy in schools.

Hi-Fi Year Book 1976

2 This is the book that tells you everything you need to know about the hi-fi equipment on the market. Separate illustrated sections cover every major category, together giving prices and specifications of over 2,000 products.

High Fidelity Designs

3 In response to demand for reprints of Wireless World constructional projects, we have collected fifteen of the most popular designs in one book.

Circuit Designs (1)

4 A compilation of the first ten sets of Wireless World Circards and including additional circuits. Each set in this hard back book is preceded by an explanatory introduction.

Order coupon

To General Sales Dept. Room 11,
Dorset House, Stamford St., SE1 9LU

Please send me books as indicated below (state number of copies of each)

Wireless World Annual 1976 @ £1.35 incl _____

Hi-Fi Yearbook 1976 @ £2.35 incl _____

High Fidelity Designs @ £1.35 incl _____

Circuit Designs (1) @ £10.40 incl _____

I enclose remittance value £ _____
(cheques payable to IPC Business Press Ltd)

Name _____

Address _____

Regd. in England - No. 677128 Regd. Office: Dorset House, Stamford St.
SE1 9LU



ULTRA MINIATURE LOW FREQUENCY QUARTZ CRYSTALS

Models SX & WX

FEATURES

- * Rugged tuning fork designs, semiconductor manufacturing techniques for low cost, high volume production
- * Frequency range from 10 kHz to 250 kHz
- * Hermetically sealed in TO-5 can
- * Calibration accuracies of 100 ppm for SX-1, 10 ppm for WX
- * Twenty most prevalent crystal frequencies available from stock
- * Low cost — unit price from £1.15 for production quantities
- * Shock 1000g, vibration 11g

Distributed in the United Kingdom by

INTERFACE QUARTZ DEVICES LIMITED


29 Market Street, Crewkerne, Somerset

Telephone: (046031) 2578 Telex: 46283

World-wide exporters and importers of all types of quartz crystals, crystal oscillators, filters, timers, counters and accessories

WW-004 FOR FURTHER DETAILS

TAKE A CLOSE LOOK

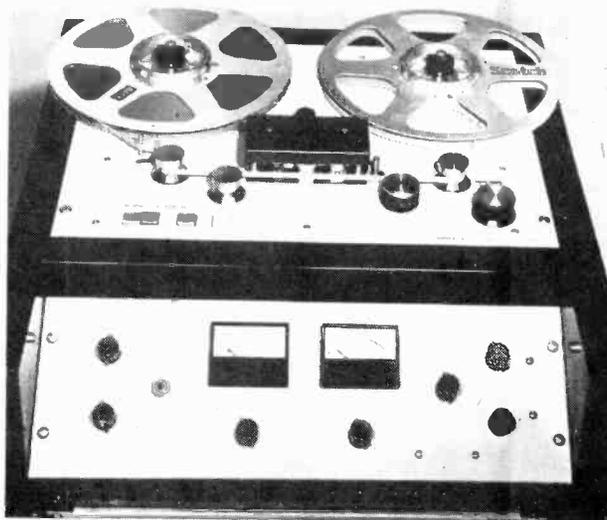

at a professional recorder that offers high performance, excellent reliability and is very easy to maintain. Ask yourself why so many commercial radio stations and recording studios are doing their best to wear them out, and not having much success. Decide if you need mono or stereo, console transportable or rack mounting versions and then inquire about prices. We are sure you will be very pleasantly surprised.

LEEVERS-RICH EQUIPMENT LTD. INC. BIAS ELECTRONICS

319 TRINITY RD., LONDON, SW18 3SL

01-974 9054

WW-045 FOR FURTHER DETAILS



SPEEDSERVICE

Hard-to-find tubes and semiconductors are normally included in our quotations. We try to give a complete answer.

AEL GATWICK HOUSE HORLEY SURREY RH6 9SU
Telex 87116 Cables Aerocon Telex Horley Telephone Horley 5353

WW-034 FOR FURTHER DETAILS

ES CHRONOMETERS and TIMERS


All models feature digital L.E.D. time display
Three grades of precision are available. **8% VAT**

Model	Oscillator employed	Features in Brief
401	Quartz, temperature-compensated	Very low power consumption. Accuracy one second per month at 20°C. Price range £44-£98.
402	3.276800 MHz AT-cut	
403		
501	Quartz, low-power controlled temperature oven. Low aging, 5MHz	Accuracy one second per month 5°C-45°C. Prices range from £180.
601	Rubidium atomic absorption with phase-locked crystal oscillator.	Very high accuracy, with leap-second adjustment facility. Price subject to quotation.

Kits also available (401 chronometer models only); everything needed is supplied, including wire, screws and case. Please send for full details to:

ELECTRO SYSTEMS & TIMING CO.
48 Robinson Road, Loudwater, High Wycombe, Bucks.
HP13 7BJ, England Tel: Penn (049481) 4661

WW-082 FOR FURTHER DETAILS

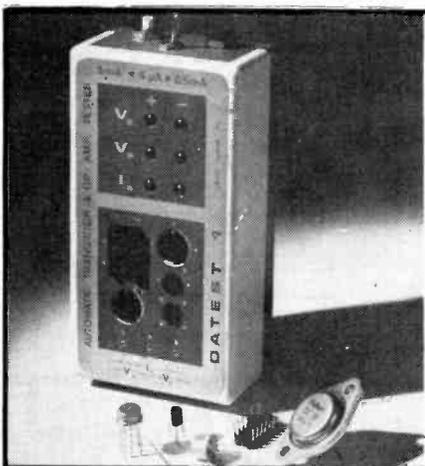

DATEST 1: THE NEW TIME SAVER

Automatic device tester and identifier

DATEST 1 saves valuable repair time by automatically testing diodes, transistors, and all types of FETs, both in and out-of-circuit, plus common op. amp. i.c.s out-of-circuit.

To carry out a test simply connect the device and switch on. If the display flashes its "No Go". If you get a steady pattern it's "Go". No prior knowledge is required of device polarity or whether it is bipolar or FET. On the contrary, the clear six-LED display tells you at a glance the polarity of the device (NPN, PNP, N-channel, P-channel) and for out-of-circuit tests whether it is bipolar, depletion FET, or enhancement FET. If you then flick the test current switch you can instantly place limits on current gain, leakage current, and FET parameters. Finally if you need to you can even plug in a multimeter and actually measure some of them. DATEST 1 with its advanced four i.c. and six transistor circuit (pat. appl. for) rapidly pays for itself in skilled man hours saved and in expensive mistakes avoided. For complete user confidence DATEST 1 even stops working abruptly and gives a special display when battery voltage has dropped to too low a value. DATEST 1 is available now and comes complete with battery, easy-to-use probes for in-circuit tests, and detailed handbook. Write for full details or send now for your own "time saver". Price £49 plus 8% VAT, cash with order.

DATONG ELECTRONICS LIMITED

11 Moor Park Avenue, Leeds LS6 4BT
Telephone: 0532 755579

WW-059 FOR MORE DETAILS

click

WW6

Light on the scene.

Local lighting just where you want it with Click's elegant, adjustable Spotlight or snake-arm Reading Lamp.

Tidy wires.


With Click you can hide all your leads and wires inside the uprights, with a neat, snap-in cover strip.

Keeping it steady.

With shelves fixed firmly to the wall, you eliminate floor vibration problems.

Finding a level.

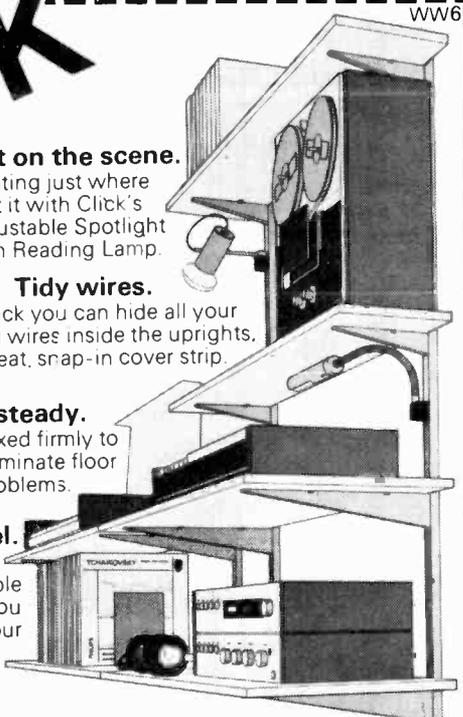Click brackets are infinitely adjustable for height so you can always get your shelves level.




**Shelving for hi-fi.
We've solved the problems.**

FREE Post this ad. with your name and address for a 10-page leaflet to **Click Shelving Ltd.**
Lowmoor Rd, Kirkby in Ashfield, Notts, NG17 7LH

WW-058 FOR FURTHER DETAILS

New Achievements from Xcelite

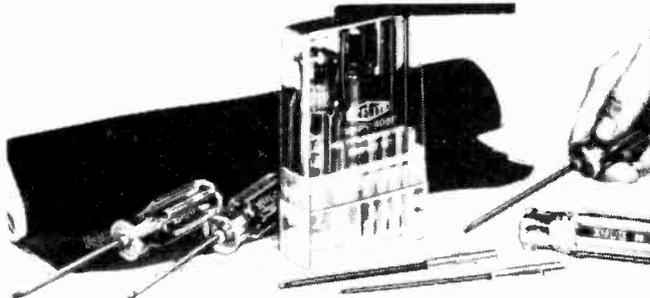

Xcelite technology has created some new additions to the famous 99 SERIES of Interchangeable Tools. The first of these is the Compact Set of Ball-End Hex drivers which, as illustrated, can drive from any angle.

Also now available in the same series are the POSIDRIV blades Nos. 1, 2 and 3.

Send for the complete Xcelite precision tools catalogue from:

Special Products Distributors Limited


81 Piccadilly, London W1V 0HL

Telephone: 01-629 9556

XCELITE PROFESSIONAL HAND TOOLS

WW - 008 FOR FURTHER DETAILS

Spot the Difference

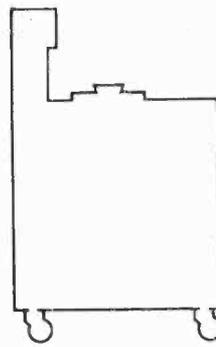

TYPICAL STEREO MASTER RECORDER
at around **£3,000.00**

Wow & Flutter
less than .05%

Start Time
less than .5 sec

Frequency Response
40 - 18KHz ± 2.0cB

Erasure
75dB

Full Servo Tension Noise
60dB below 320 nWb/m

Servo Controlled Capstans

Electronic Tape Timer



TEKNIK SM2 STEREO MASTER RECORDER
at ***£1,750.00 complete**

Wow & Flutter
less than .05%
(Typically .02% at 15 ips)

Start Time
less than .3 sec

Frequency Response
40 - 20KHz ± 2.0dB

Erasure
75dB

Full Servo Tension Noise
60dB below 320 nV/b/m at all speeds

Servo Controlled Capstans
with panel operated or remoteable varispeed

Electronic Tape Timer

Switchable NAB/DIN equalization
V.U. metering plus L.E.D. peak level indicators

* J.K. Trade Price



Klark-Teknik Ltd

Summerfield Kidderminster
Worcestershire DY11 7RE
Tel Kidderminster 64027

WW-023 FOR FURTHER DETAILS

NEW!...the decon-dalo 33 PC Quick -Dri etch -resist marker




A unique drafting aid for the electronics engineer enabling him to prepare in minutes a perfect PCB

A fine-tipped marking pen charged with free-flowing etch-resist ink — new formulation QUICK-DRI ink is ready for etching in just two minutes!

Simply draw the desired circuit onto copper laminated board — etch — clean.

The circuit is ready to use

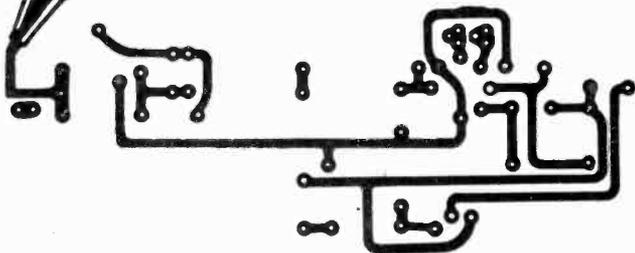

NO MESS — NO MASKING

A perfect circuit every time!

Still only £1.08 for one-off, £4.42 for six, £8.80 for twelve, post and VAT paid! Available now in every country in Europe. **AND FROM YOUR LOCAL COMPONENT SUPPLY SHOP!**

Decon Laboratories Ltd., Ellen Street, Portslade, Brighton BN4 1EQ Phone: 0273 414371

Please send me further details on the 33 PC Quick-Dri


Name

Address

Post to: **DECON LABORATORIES LTD.**
FREEPOST
PORTSLADE, BRIGHTON, ENGLAND
(No Stamp Needed) Phone 0273 414371

WW-007 FOR FURTHER DETAILS

ELECTRONIC INDUSTRIAL THERMOMETER

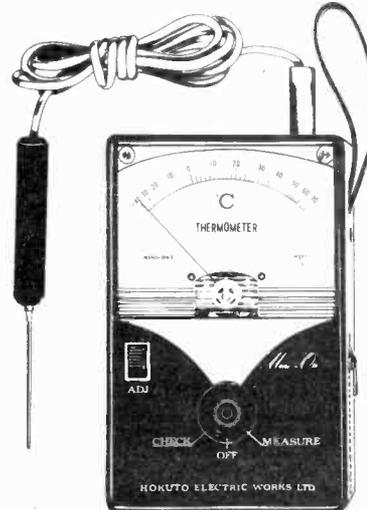

THE MODERN WAY TO MEASURE TEMPERATURE

A Thermometer designed to operate as an Electronic Test Meter. Will measure temperature of Air, Metals, Liquids, Machinery, etc., etc. Just plug-in the Probe, and read the temperature on the large open scale meter. Supplied in zippered vinyl case with transparent front and carrying loop. Probe, and internal 1½ volt standard size battery.

Model "Mini-On 1" measures from - 40°C to + 70°C, price £17.50

Model "Mini-On Hi" measures from + 100°C to + 500°C, price £20.00 (V.A.T. EXTRA)

Write for further details to


HARRIS ELECTRONICS (LONDON),
138 GRAY'S INN ROAD, LONDON. WC1X 8AX
(*Phone 01-837 7937)

WW-017 FOR FURTHER DETAILS



Red & Green LED applied Logic Level Indicator **MODEL 320 LOGIC PROBE**

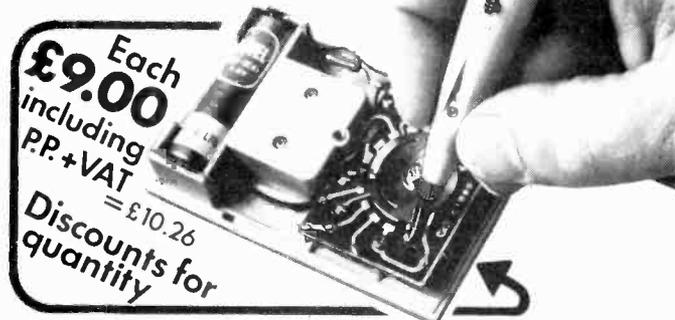- * Wrong polarity and overload protectors provided
- * Detection of the peak value of input waveform
- * Open circuit or faulty IC can be detected
- * All logic levels are visible at a glance
- * Powered from circuit under test
- * Built-in storage circuit
- * Up to 12 MHz



Each
£9.00
including
P.P. + VAT
= £10.26
Discounts for
quantity

JH Associates Ltd Sales Office: 52 Silver Street, Stansted, Essex. (0279) 814929

WW-048 FOR FURTHER DETAILS

RACAL COMMUNICATION EQUIPMENT

34	RA 117E High Stability H.F. Receiver Frequency Range 1 to 30 MHz	E400 00 + E5 00 p.p
34a	New condition	E350 00 + E5 00 p.p
34b	Good clean condition	E350 00 + E5 00 p.p
31	RA 17 Frequency range 500KHz to 30MHz	E315 00 + E5 00 p.p
31	In good clean condition	E315 00 + E5 00 p.p
38	RA 9B Single side band with A.F.C.	E85 00 + E2 00 p.p
40	RA 21B Single side band time tune unit for RA 117	E43 00 + E2 00 p.p
41	RA 63 Single side band time tune	E100 00 + E2 00 p.p
30	SECOND V.F.O.s with H.M. scale for RA 17s No guarantee	E15 00 + E1 50 p.p
44A	RACAL Test Rig Type MA 91 for RA 17s	E30 00 + E1 50 p.p

FULL SPEC. UPON REQUEST

TELECOMMUNICATION EQUIPMENT

27a	PYE Mobile Radio Telephones High/low band available V.H.F. Under-dash mounting Microphone on coil lead. Built-in speaker.	E25 00 ea. or E40 00 pair + p.p E1 50 ea
27b	PYE Mobile Radio Telephones Boot mounting C/W Control Box, wiring loom, built-in speaker, microphone on coil lead High power E30 00 ea or E50 00 pair + p.p E2 00 ea	E260 00 + E10 00 p.p E100 00 + E5 00 p.p
27c	MURPHY High Band Base Station 240v	E95 00 + E5 00 p.p
27d	MURPHY High Band Case Station. 240v + 10 High Band PYE Mobile Units (as in 27a above)	E260 00 + E10 00 p.p E100 00 + E5 00 p.p
27e	PYE High Band Base Station. 240v	E15 00 + E1 50 p.p
27f	PYE High Band Base Station. 240v + PYE High Band Mobile Units (as in 27a above)	E285 00 + E10 00 p.p

MOUNTING TRAYS/AERIALS ALSO AVAILABLE

ITEM

28a	Walkie Talkie Type 88 (Transceiver) £25.00 pair + £2.00 p.p.
28b	Walkie Talkie Type 18 (Transceiver) 6-10 MHz tunable, built-in check meter £10.00 each + £2.00 p.p.
28c	Walkie Talkie Type 38 (Transceiver), Tunable £15.00 each + £2.00 p.p.
29	Power & Modulator Unit Type 440 LRV 3B, Rotary covertor 24v, DC in 3HT out. (Ex-Airline.) £4.00 + £1.50 p.p.
50a	Cord 75 W.M. 4 £25.00 + £3.00 p.p.
50b	Telegraph (Terminal Unit) Tape Transmitter £25.00 + £2.00 p.p.
52a	Sperry Gyro Compass Mk. 4 £14.00 + £1.00 p.p.
52b	Navigator Indicator Units for above £12.00 + £1.00 p.p.
53	Inverter Type 100B 22-28v, DC working in 115v., 3 Phase 400 cycle/ out. 150 VA P.F. 8 for Sperry Gyro Equipment £15.00 + £1.50 p.p.
54	Dial Telephones, working order, clean appearance, B.P. type £10.00 for 10 + £3.00 p.p.
55	Klaxon Horns, 24v. or 240v £8.00 + £1.00 p.p.
56	Geared Motors, These motors have a 600-1 slipring gearbox built onto the end, high torque 6rpm. Electronic brake. Ideal for aerial, door, etc., rough externally. £2.00 + £2.00 p.p.
57	Electric Hot Air Hand Dryers, very effective £4.00 + £1.00 p.p.
58	FERROGRAPHS Series 6 Tape Recorder, 100-240V AC, 1/2 track, built in a strong durable case. Built-in speaker and amplifier £70.00 + £3.00 p.p.
59	FERROGRAPHS Series 3 Tape Recorder, As above, but smaller £25.00 + £2.50 p.p.
61	Tape Cartridge Player, built-in 10w amp. built driven, 240v, 50 cycles £5.00 + £1.50 p.p.
84	15 Watt Amplifier, in strong polished wood ash case, 2 input, Base/Treble controls, (Switched output 3 ohm/15 ohm/70v.) 240v, 50-60 cycles. Manufactured by Clarke & Smith £5.00 + £1.50 p.p.
85	QUAD 2 power amps, rough appearance, minus valves, Sold with circuit £9.00 + £1.50 p.p.
87	Close circuit fully transistorised video TV cameras, £40.00 + £1.50 p.p.
88	QUARTZ digital Watches, Day, date, hours, mins., secs. Remarkable accuracy. Complete with bracelet and power coil £65.00 + £1.50 p.p.

ITEM

89	B 41 Communication Receiver, IF version, rough condition	E150.00 + £2.00 p.p.
90	B 62 Communication Receiver, Rough condition	E200.00 + £2.50 p.p.
62	Aircraft Radar (no indicator)	E45.00 + £3.00 p.p.
64	DECCA 404 Marine Radar, Very clean condition, Cassal display, 220v, DC	E350.00 + £10.00 p.p.
64	DECCA Marine Navigator Mk. 5, Complete 110v., 240v, 50-60 cycles	E100.00 + £10.00 p.p.
132	SSB 4 Channel Transceiver, Crystal controlled, built in check meter, Marconi Type MSR 21, Less power supply	E80 + £3.50 p.p.
133	Ferrograph Tape recorder with built in Voltexon Amplifier, Deck mounted optical, built in speaker, 3 speed, complete in fabric covered cabinet	E85 + £2.50
134	Rank Aids Tutor 2 projector, 250 watt (J.J.) 240V. As new condition	E400 + £1.50

TEST EQUIPMENT

2	VHF Sweep Generator, 450-900 mcs (Teleonic)	E50.00 + £1.50 p.p.
3	Noise Generator, CT 410.15kcs-160 mcs in 3 bands	E30.00 + £2.00 p.p.
4	Pulse Generator Type 60 100S (Solastron)	E30.00 + £2.00 p.p.
5	Signal Generator 300kcs-30mcs in 7 bands, (Airmac)	E45.00 + £3.00 p.p.
7	Signal Generator CT 202 6-75 mcs	E25.00 + £2.00 p.p.
6	Microsecond Chronometer (Citel), 12v. DC or 240v, AC	E25.00 + £2.00 p.p.
8	Frequency Calibrator Type 221, 125-20,000 kc, AC power supply	E30.00 + £1.50 p.p.
9	High resistance measuring set, Type 0625	E20.00 + £2.50 p.p.
10	Calibrator Type TC 99 100-205 mcs	E20.00 + £2.00 p.p.
11	Frequency period counter (Beckman), Type 7360 JH, Table model, AC power 110-240v	E15.00 + £2.00 p.p.
12	VHF Frequency Standard (Wayne Kerr)	E100.00 + £1.50 p.p.

ITEM

13	TV Line selector Type L 190 (Mullard)	E25.00 + £2.00 p.p.
15	Klystron power supply Model 2016B (Eimac)	E35.00 + £2.00 p.p.
16	Voltage Regulator (Lung & Thompson), 1000w 220/240v	E30.00 + £4.00 p.p.
17	Wide range oscillator Type 400 C (Dove)	E15.00 + £2.00 p.p.
18	Video oscillator (Marconi), TF885, Rough external	E30.00 + £2.00 p.p.
20	Adjustable Phase Corrector (Rank Cintel)	E10.00 + £1.50 p.p.
22	Valve Voltmeter TF 428B	E10.00 + £1.50 p.p.
23	RF X Band Test Set Type CT 118	E35.00 + £2.00 p.p.
24	Storage Scope Type S01 (Hemscope)	E35.00 + £3.00 p.p.
25	Sweep Generator by ADVANCE, .005-100 cycles, square sine and saw tooth, Type SG 88, Very good condition	E250.00 + £5.00 p.p.
93	A.F. Analyser, 75 cycles in 7.5 kc, Type 1401 C	E10.00 + £1.50 p.p.
97	Feet Analyser Type 13171, 'United Control Corporation'	E60.00 + £3.00 p.p.
98	Regulated power supply, Model 503, Model, 'All Power Transformers Ltd.' Pos. 0-500v, controllable, Neg. 0-250v, Built-in check meter, 6.3v. @ 10 amps, Table model	E25.00 + £3.00 p.p.
99	Constant Voltage Transformer, 190-250v, 50 cycles in output, 240rms 75 watts p.l.1	E10.00 + £1.50 p.p.
100	Pan Recorder, 'Record' make, Type MC DC, Oscilloscope 3BA/CTA, New condition, 240v	E50.00 + £1.50 p.p.
102	Hand Magnets, Mounted on rubber feet	E2.50 + 50p p.p.
103	Reflection co-efficient meter, 2-30 Mc/s	E100.00 + £2.50 p.p.
105	Signal Generator Type CT345, 4.5 KHz-150KHz in 8 switch bands, Built-in calibrator	E15.00 + £3.00 p.p.
106	Solartron Component Indicator (Resolved), Model YF 253.2, 0.5 c/s to 1Kc	E100.00 + £3.00 p.p.
107	Low Frequency Decade Oscillator (Solartron), Model OS 103.2A	E75.00 + £3.00 p.p.
108	TFA Carrier Converter, Solartron, Type JX 941 A	E75.00 + £2.00 p.p.
109	Solartron Feedback Voltmeter, Type YF 252 E25.00 + £2.50 p.p.	
110	Transistor Test Set, Type CT 537 (AVO), New condition	E50.00 + £1.50 p.p.

ITEM


111	Transceiver, 6 channel (Ex-Airline), Plessey, Type PRA 100F	E30.00 + £1.50 p.p.
112	P.E. Quartz Spectrophotometer No. 13056, by Unicam Instruments	E160.00 + £10.00 p.p.
113	Foster Transformo Tester Unit, 0-10 Kv, with test cabinet P.O.A.	E260 00 + E10 00 p.p
114	Oscillator Test Set CT 373, 17c/s - 170Kc, Model, by A.L.L. P.D.A.	E100 00 + E5 00 p.p
115	Airmac Power Unit, Type 690B	E50.00 + £4.00 p.p.
116	Test Set, Decca Radar Type MW 58 S/R M12	E185.00 + £10.00 p.p.
117	Time Interval Meter, Type 771 Airmac	E50.00 + £2.00 p.p.
118	L.P. Filter, Type GF 001/01 Mullard	E15.00 + £1.50 p.p.
119	H.P. Filter, Type GF 001/02	E15.00 + £1.50 p.p.
120	Attenuator Type 0 560A, variable Muirhead	E15.00 + £1.50 p.p.
121	Broad Band Amplifier, 2-8MHz with graph, 240v working, Model, G.E.C.	E18.00 + £2.50 p.p.
122	Selective Amplifier Detector, Type D 669 A, 30c/s - 95c/s X 1, X 10, X 100, Switched attenuator built in 20 mv-e/v meter, 240v working Muirhead	E35.00 + £2.50 p.p.
123	Adjustable Inductance Standard, Constant resistance type, Model, Sullivan-Griffiths of London	E40.00 + £2.00 p.p.
124	Noise Generator, Type NW 45A/X, 8600-9700 mcs, Decca Radar Limited complete	E75.00 + £2.00 p.p.
125	Wide Band Amplifier, Type AWS 51A Freq. response 15KHz-350KHz, Calibrated switched attenuators, 0v voltmeter, A.C. mains working, Solartron	E55.00 + £4.00 p.p.
126	100v reference supply, Type AS7582 Solartron	E40.00 + £3.00 p.p.
127	High Power Oscillator Amplifier, Type 254 (Airmac), 30-300KHz X 1, X 10, X 100 Deal output	E160.00 + £5.00 p.p.
128	Display Oscilloscope Type 249 (Airmac) 14" Display in polished wooden cabinet	E150.00 + £10.00 p.p.
129	Standard Signal Generator, Type TF 527A, Marconi-Echo, 9.5 KHz - 50MHz, 8 switched bands, Adjustable modulation, Attenuated output	E80.00 + £4.00 p.p.
130	Wave Meter Type 695, with calibration chart, 0-500MHz approx.	E30.00 + £3.50 p.p.
131	R.F. Unit, Type 24, S. Band oscillator, built in adjustable micrometer	E50.00 + £2.00 p.p.

Mail Order only please to: **SOUTHERN AVIATION**

Station Approach, Epsom, Surrey. Telephone: Epsom (03727) 20691

TEST AND SURPLUS EQUIPMENT PURCHASED. CATALOGUES NOW AVAILABLE 50p

WW-087 FOR FURTHER DETAILS

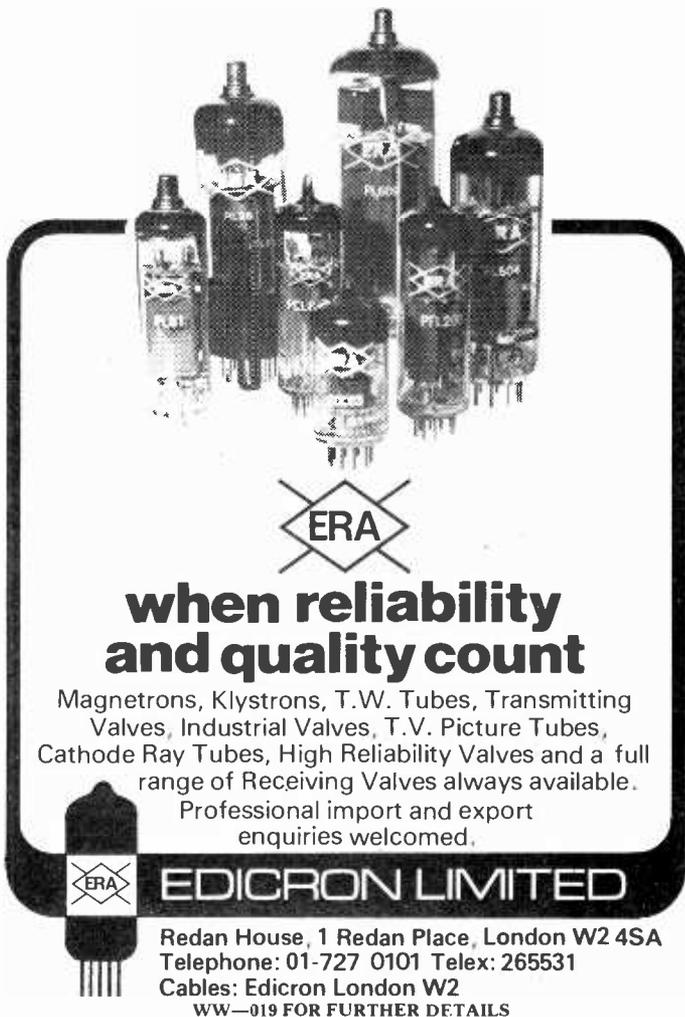

ERA

when reliability and quality count

Magnetrons, Klystrons, T.W. Tubes, Transmitting Valves, Industrial Valves, T.V. Picture Tubes, Cathode Ray Tubes, High Reliability Valves and a full range of Receiving Valves always available.

Professional import and export enquiries welcomed.

EDICRON LIMITED

Redan House, 1 Redan Place, London W2 4SA
 Telephone: 01-727 0101 Telex: 265531
 Cables: Edicron London W2
 WW-019 FOR FURTHER DETAILS

servos synchronous steppers dc motors



gearboxes and control systems

Stockists for **IMPEX Motors** **McLennan**

McLENNAN ENGINEERING LIMITED
 Kings Road Crowthorne Berks Telephone: Crowthorne 5757/8

WW-037 FOR FURTHER DETAILS


EXCLUSIVE — WORLDBEATING**DIGITAL ALARM
CLOCK KIT*****NON-ALARM £14 INC. VAT, ETC.****£16**INCL.
VAT &
DEL.

* Or Ready Built & Tested £22.50



- Built-in Alarm
- Photo cell controlled brightness
- AM/PM Indicator
- Giant 0.63" LED Display
- 12/24 hr. mode
- Mains failure ind.
- Tilt Snooze Sw.
- Separate alarm Control Sw.
- 9 min. Snooze
- No knowledge of electronics to build kit

**CWO, PULSE ELECTRONICS, DEPT. WW10, 202 SHEFFORD RD., CLIFTON,
SHEFFORD, BEDS.
PHONE: HITCHIN 0462 814477**

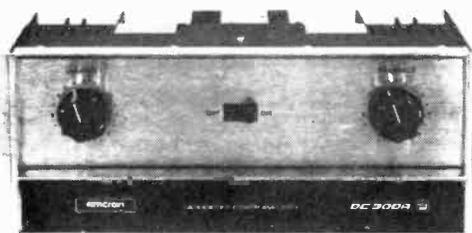HIGH POWER DC-COUPLED AMPLIFIER

- ★ UP TO 500 WATTS RMS FROM ONE CHANNEL
- ★ DC-COUPLED THROUGHOUT
- ★ OPERATES INTO LOADS AS LOW AS 1 OHM
- ★ FULLY PROTECTED AGAINST SHORT CCT, MISMATCH, ETC.
- ★ 3 YEAR WARRANTY ON PARTS AND LABOUR

The DC300A Power Amplifier is the successor to the world famous DC300 which is so widely used in Industrial, and Research applications in this country. It is DC-coupled throughout so providing a power bandwidth from DC to over 20.000Hz. The ability of the DC300A to operate without fuss into totally reactive loads while delivering its full power, and maintaining its faithful reproduction of Pulse or complex waveforms has established the DC300A as the world's leading power amplifier. Each of the two channels will operate into loads as low as 1 ohm, and the amplifier can be rapidly connected as a single ended amplifier providing over 650 watts RMS into a 4 ohms load, and still providing a bandwidth down to DC. Below is a brief specification of the DC300A, but if you require a data sheet, or a demonstration of this fine equipment please let us know.

Power Bandwidth	DC-20kHz @ 150 watts + 1db. - 0db.	Slewing Rate	8 volts per microsecond
Power at clip point (1 chan)	500 watts rms into 2.5 ohms	Load impedance	1 ohm to infinity
Phase Response	+0, -15° DC to 20kHz. 1 watt 8Ω	Input sensitivity	1.75 V for 150 watts into 8Ω
Harmonic Distortion	Below 0.05% DC to 20kHz	Input Impedance	10K ohms to 100K ohms
Intermod. Distortion	Below 0.05% 0.01 watt to 150 watts	Protection	Short, mismatch & open cct. protection
Damping Factor	Greater than 200 DC to 1kHz at 8Ω	Power supply	120-256V. 50-400Hz
Hum & Noise (20-20kHz)	At least 110db below 150 watts	Dimensions	19" Rackmount, 7" High, 9 3/4" Deep
Other models in the range: D60 — 60 watts per channel		D150 — 150 watts perchannel	

**MACINNES LABORATORIES LTD**

**MACINNES HOUSE, CARLTON PARK INDUSTRIAL ESTATE,
SAXMUNDHAM, SUFFOLK IP17 2NL
TEL: (0728) 2262 2615**

WW-052 FOR FURTHER DETAILS

HIGH VOLTAGE PROBE/METER

**Priced at
only £22.50**

This rugged self-contained direct reading 0 to 40 KV probe has a reading accuracy of 2% at 25KV. Plus a 1.75" probe tip for reaching under the corona cap. This probe is ideal for the Television Engineer.

For further information
contact: **01-639 0155/7**

Precision Instrument Laboratories
Instrument House, 212 Ilderton Road, London SE15 1NT

PIL

WW-067 FOR FURTHER DETAILS

HIGH FIDELITY STEREO RECEPTION by *Icon Design*

There is little doubt that live stereo radio broadcasts provide the highest fidelity reproduction available from any source. If you do not agree with this statement, it is probably because your tuner performance is not equal to the very high standard maintained by the BBC, and is restricting the quality of sound available.

It could be that you have not invested in an F.M. receiver, and are unaware of the wealth of listening pleasure going to waste over your rooftop, and could be yours to enjoy without the cost of a licence!

In either case you are in for a pleasant surprise when you install the ICON DESIGN tuner. Gone is the confusion of finding the right station from the multiplicity of transmitters now operating. Gone is the uncertainty of tuning for the best sound. Gone are the noises and distortions, the instabilities and warbles, common to most tuners. With the ICON DESIGN tuner you get only what you want: good clean sounds at the touch of a button or the turn of a knob. Tuning is unambiguous and clear, weak and out-of-tune stations are not heard, and the quality of reproduction will rival your best records.



BUILT & TESTED

This tuner is available ready to plug in and use, on a two week money back guarantee for your inspection and test, followed by a FIVE year performance guarantee against failure in normal use.

Available also are a number of ready built and tested sub-assemblies for inclusion in your own cabinet, and prices of these will be sent with full details upon request.

Main Receiver Board	£27.00
Stereo Decoder Board	£9.00
Complete Tuner	£102.00
Securicor (Mainland)	£4.00

KITS

A large number of kits are available to suit all needs, in addition to many individual items including P.C.B.s. All kits are guaranteed to work if correctly built, or we will repair them without charge. Compare this service with other sources! then build with confidence from our kits.

K1-4 Main receiver board	£25.65
K5-7 Stereo decoder board	£7.05
K8a/12 Pre-select unit & frequency meter	£24.75
K10 Power supply	£5.59
LP1186 Mullard front end module	£5.95
SFG10.7MA Filter Unit	£2.95
SBA750B I.F. amplifier I.C.	£2.95

Other parts available

DETAILS

For full details of all our products, prices and order form, send s.a.e. to

Icon Design

**33 Restrop View
Purton, WILTS
SN5 9DG**

All prices are exclusive of VAT at 25%




naim audio
the power amplifier

BE FAIR TO YOUR MUSIC

Reproduction of sound and its acceptability is dependent on a combination of physical parameters not yet fully explored. We believe that only a compatible combination of specifications will enable a system to

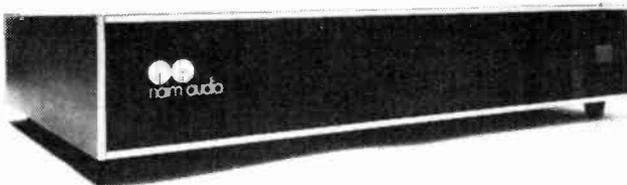reproduce music. We have taken care that the NAC 12 and NAP 160 pre and power amplifier will do so faithfully, while accepting the output of any pickup cartridge and driving any loudspeaker.



Naim Audio Ltd. 11 Salt Lane, Salisbury, Wilts. Tel: (0722) 3746

WW-039 FOR FURTHER DETAILS

OUR NEW XL35

our monitor, special



- Nominal 3½ digit display with 50% overrange to 2999.
 - Accuracy 0.05%.
 - Autozero.
 - Versions offering fully optically isolated bcd are available.
 - Mains or 5V dc power requirement.
 - Cost competitive.
- Send now for full details.



exel electronics limited
wollerton road, branksome
poole BH12 1LR

the panel meter people
telephone: bourne-mouth (0202) 766166. tx: 417143

WW 079 FOR FURTHER DETAILS



sound equipment by **Grampian**

GRAMPIAN REPRODUCERS LTD. HANWORTH TRADING ESTATE FELTHAM, MIDDLESEX TELEPHONE 01-894 9141

WW-041 FOR FURTHER DETAILS

**INDUSTRIAL PRICES FOR THE HOBBYIST
ALL 'BIG NAME' BRANDED GOODS
SAME DAY SERVICE
MONEY BACK GUARANTEE**

I/C's	£	£	£
CA3028A	0.64	CD4015AE	0.70
CA3035	1.10	CD4016AE	0.37
CA3046	0.57	CD4017AE	0.70
CA3048	1.40	CD4018AE	0.70
CA3052	1.00	CD4019AE	0.37
CA3089E	1.60	CD4020AE	0.74
CA3090Q	1.50	CD4021AE	0.70
CD4000AE	0.14	CD4022AE	0.65
CD4001AE	0.14	CD4023AE	0.14
CD4006AE	0.80	CD4024AE	0.50
CD4009AE	0.37	CD4025AE	0.14
CD4010AE	0.37	CD4026AE	1.14
CD4011AE	0.14	CD4027AE	0.37
CD4012AE	0.14	CD4028AE	0.60
CD4013AE	0.37	CD4029AE	0.75
CD4014AE	0.70	CD4030AE	0.37
		CD4037AE	0.63
		CD4041AE	0.56
		CD4043AE	0.69
		CD4044AE	0.62
		CD4045AE	0.93
		CD4046AE	0.88
		CD4047AE	0.60
		CD4048AE	0.37
		CD4049AE	0.37
		CD4050AE	0.37
		L005T1	1.17
		L036T1	1.17
		LM3091C	1.25
		TAA621	1.76
		TAA661B	1.14
		TBA651	1.03
		TBA800	0.89
		TBA810	1.00
		TBA820	0.60
		741c(Minidip)	0.18
TRANSISTORS			
	£	£	£
2N696	0.15	2N4036	0.43
2N706	0.10	2N4037	0.35
2N1711	0.18	2N5296	0.30
2N2102	0.56	3N128	0.61
2N2369	0.10	3N140	0.76
2N2905	0.27	3N141	0.68
2N3053	0.14	40360	0.33
2N3054	0.30	40361	0.31
2N3055	0.35	40362	0.33
2N3440	0.24	40406	0.31
2N3442	1.32	40407	0.28
2N3702	0.12	40408	0.41
2N3703	0.12	40409	0.43
2N3704	0.15	40410	0.43
2N3706	0.14	40411	1.82
2N3708	0.12	40594	0.59
		40595	0.69
		40636	0.91
		40673	0.46
		BC107	0.06
		BC108	0.06
		BC109	0.06
		BC237	0.05
		BCY70	0.09
		BCY71	0.18
		BCY72	0.09
		BFX29	0.26
		BFX30	0.29
		BFX84	0.21
		BFX85	0.26
		BFX88	0.22
		BFY50	0.18
		BFY51	0.17
		BFY52	0.18
		OC35	0.35
DIODES/ZENERS			
	£	£	£
IN/4001/2/3/4	0.03	IN4005/6/7	0.04
		IN4148	0.15
		BZY88 400mW.	
		All voltages	0.06
		OA47	0.05


Terms: C.W.O. Add 10p P/P 8% VAT Cos/Mos
25% VAT OTHER
Send SAE for comprehensive Cos/Mos List.

ROWNSGEM LTD.

Rosebank Parade, Plough Road, Yateley, Camberley, Surrey.
Phone No. 0252 871388

THE PROFESSIONAL ORGANISATION FOR THE 'HOBBYIST'

WW-014 FOR FURTHER DETAILS

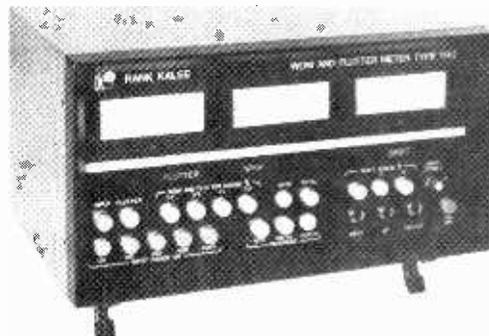

**The
new
Rank**

**WOW & FLUTTER Meter
Type 1742**
Fully transistorised
for high reliability

Versatile

Meets in every respect all current specifications
for measurement of Wow, Flutter and Rift
on Optical and Magnetic sound recording/reproduction
equipment using film, tape or disc

High accuracy

with crystal controlled oscillator

Simple to use

accepts wide range of input signals with
no manual tuning or adjustment

Two models available:

Type 1742 'A' BS4847: 1972 DIN 45507
CCIR 409-2 Specifications
Type 1742 'B' BS 1988: 1953 Rank Kalee
Specifications


For further information please address your enquiry to
Mrs B. Nodwell

Rank Film Equipment, PO Box 70
Great West Road, Brentford
Middlesex TW8 9HR

Tel: 01-568 9222 Telex 24408 Cables Rankaudio Brentford



**RANK FILM
EQUIPMENT**

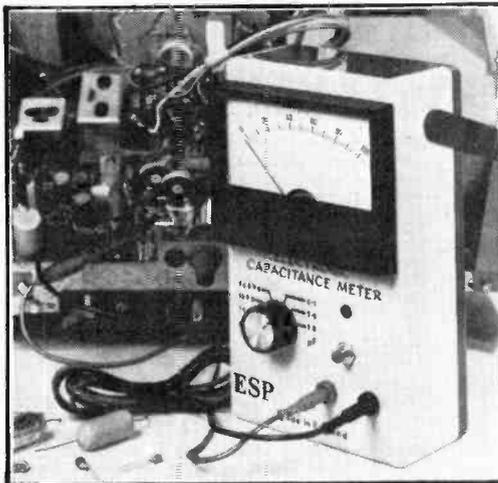

ELECTRONIC CAPACITANCE METER

NOW CAPACITORS ARE EASIER TO MEASURE THAN RESISTORS



PRICE
£38.50
+VAT
Ex-Stock

APPLICATIONS OF C-METERS

- ★ Filter Design
- ★ Decoupling and Coupling
- ★ Precision Timing Circuits
- ★ Tuned Circuits
- ★ C-R Networks
- ★ Fault-Finding. Quality Control

- ★ Less than a second to measure a capacitor.
- ★ Six ranges 1pF to 10µF.
- ★ Accuracy ±2%.
- ★ Robust construction. Long battery life.

OPTIONAL: MAINS/BATTERY + £5.00

SUPPLIERS TO: Ministry of Defence, G.P.O., B.B.C., Government Depts. and Electronic Laboratories world-wide

ESP

Electronic Services & Products Ltd.
Braunston, Daventry, Northants NN11 7HH
Telephone: Rugby 890672

WW—056 FOR FURTHER DETAILS


A message for dealers in exclusive high quality audio equipment — everywhere.

It is now proposed to expand the distribution of RADFORD products by supplying from the factory in BRISTOL direct to franchised dealers outside the United Kingdom.

If you have a discriminating clientele looking for the finest audio equipment and loudspeaker components available, you could profit from a direct RADFORD franchise.

Write today for details and leaflets.

Radford Audio Ltd
Ashton Vale Road
Bristol BS3 2HZ England

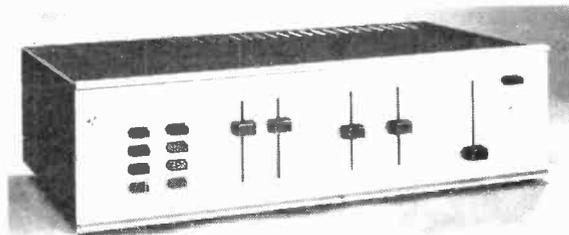

ZD22

Stereo Pre-amplifier Control Unit

A stereo pre-amplifier of virtually zero distortion. Inputs for disc, tuner, and two tape machines. Size 17" x 4 3/4" x 10" deep.

£145.00

HD250 Stereo Integrated amplifier

Incorporates ZD22 pre-amplifier with low distortion power amplifier of 50 watts per channel into 4-8 ohms load. Headphone output. Illustrated above. Size 17" x 4 3/4" x 11".

£195.00

ZD100 Power amplifier

Power output 120 watts in 4 ohms and 75 watts into 8 ohms. Distortion less than 0.004% up to clip level. Size 17" x 4 3/4" x 13".

£175.00

ZD200 Power amplifier

Power output 250 watts into 4 ohms and 150 watts into 8 ohms. Distortion less than 0.004% up to clip level. Size 17" x 7" x 13".

£295.00

WW—024 FOR FURTHER DETAILS

- P.A. SYSTEMS FOR AIRPORT, HOTEL, FACTORY.
- THEATRE AND LECTURE THEATRE AUDIO SYSTEMS
- AUDIO MIXING EQUIPMENT
- SIMULTANEOUS TRANSLATION SYSTEMS
- RADIO AND T.V. BROADCAST SOUND CONTROL EQUIPMENT
- MARINE INTERCOMMUNICATION AND ENTERTAINMENT EQUIPMENT
- *System design, manufacture and installation.*




audix

AUDIX LIMITED
Wenden, Saffron Walden, Essex CB11 4L9
TEL. Saffron Walden (0799) 40888; TELEX: 817444

tecknowledgery in consumer ICs - and their applications.

SGS Audio ICs

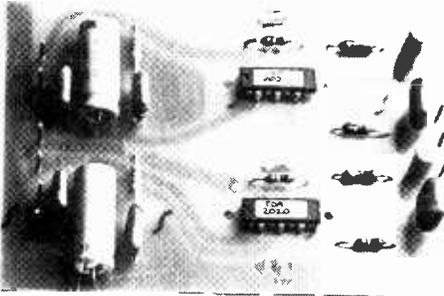

The much heralded TDA2020 is here. And just to make sure that you don't go wrong, so is the SGS application test circuit PCB for a stereo 15 + 15 (RMS) Hi Fi amplifier.

Prices :	IC	AUDIO	DISCRETES
TBA810AS	+HS 1.09	ZTX107/8/9	14p
TCA940E	+HS 1.80	ZTX413(LN)	17p
TDA2020	2.99	ZTX212/3/4	16p
FM LINEAR	ICS	BD 535 npn	7A/60v 52p
MC1350	0.70	BD536 pnp	53p
CA3089	+QC 1.94	BD377 npn	3A/50v 29p
TBA120	+QC 1.00	BD378 pnp	32p
MPX LINEAR	ICS	BD515 npn	2A/45v 27p
MC1310P	+LED 2.20	BD516 pnp	30p
CA3090AQ	+LED 3.75	BD609 npn	10A/90v 70p
		BD610 pnp	102p

We've moved

To accomodate expanded R & D facilities, AMBIT has moved sales and administration to 25 High St. Brentwood. The existing 37 High Street premises are retained for the engineering activities.

One of the first products of this move has been the development of a TV sound tuner, from an "off air" system, using its own varicap UHF TV tuner, with ICIF amplifiers and block filters by TOKO. And then one of our best ever circuits - an electronic touch tuner, with scanning mode, and facilities for 6 preset stations. The unit is suitable for use with FM, and now AM of course, and offers a complete tuner system without any moving parts. Selection is by means of touch tuning in all cases, with manual scan and preset switching automatically interlocked.

Our R&D facilities are available for general consultancy to OEMs: further details on application. Standard project estimation fee, including project evaluation comment data is £15.00 payable in advance.

Modules & Kits

New modules:

8011	Totally touch tuned varicap controller built	£14.99.
8005	Larsholt tunerset accessory unit, with pilot tone filter and audio stages, rectifier, IC stabilizer, meter driver circuits.	£4.99 (kit)
8001	55kHz low pass filter (mpx birdy filter)	£2.35 built £1.75 (kit)
2001	Stereo scratch and rumble filter, with continuously variable operating frequencies.	£5.80 (built) £4.60 (kit)
3000	Stereo control preamp - a wide dynamic range, low distortion AF preamp, with vol, bal, bass and treble controls.	kit £5.78
2020k	The TDA2020 stereo amp kit photographed on the left.	£7.85
7700	TV off air UHF sound tuner - built	£26.00 (4 preset stations)
9000 kit	AM/FM mpx tuner chassis, with mech. tuner	£17.50
7004 kit	MW/LW varicap tuner module, inc. ferrite rod	£9.95
7252	HiFi MOSFET FM tuner module by Larsholt	£24.00
7253	HiFi FET FM tuner module inc decoder	£11.25
5600	Hi Q MOSFET varicap tunerhead by TOKO	£5.00
EC3302	FET tunerhead from TOKO	

Complete FM Tuner kits, inc case, for use with the above modules: details SAE please. Prices range from £40 - £60.

Amongst our various accessories for entertainment electronics is a range of FM tuning, frequency and sig. strength meters with 12v, 50mA bulb. £2.50 ea.



ambit international
Trade Mark
25 high street, brentwood,
essex. cm14 4rh.
tel: (0277) 216029
tlx: 995194


Free price list with an SAE, catalogue of modules and parts 40p., including postage and VAT.

General Terms: CWO please, official bodies and companies please note min. invoice £7.50. PP for CWO orders 22p per order. (UK and Eire). Overseas customers please include sufficient for postage. VAT is not included, and must be added at 25%. In stock orders despatched within 48 hours.

WW 081—FOR FURTHER DETAILS

FYLDE

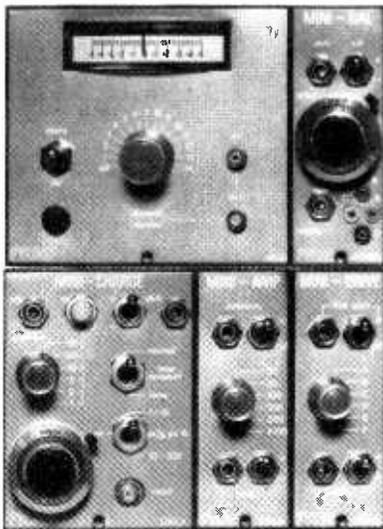TRANSDUCER and RECORDER
AMPLIFIERS and SYSTEMS




reliable high performance & practical controls. individually powered modules—mains or dc option single cases and up to 17 modules in standard 19" crates small size—low weight—realistic prices.

FYLDE

Fylde Electronic Laboratories Limited.

49/51 Fylde Road Preston
PR1 2XQ
Telephone 0772 57560

WW—084 FOR FURTHER DETAILS

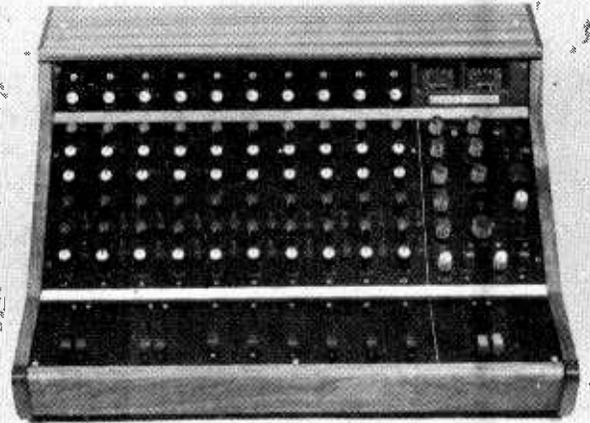

IS CHILTON'S MIXER THE BEST FOR YOUR USE?


Magnetic Tapes Ltd make the 10/2 above as well as a 16/2 and a 12/4 with all the inherent flexibility and quality customarily found in big studio mixers. Most of our mixers are constructed to meet the varying demands of the customer, perhaps we can do one for you. Prices start at £365 for the basic 10/2 + VAT @ 8%.

MAGNETIC TAPES LTD.

Chilton Works, Garden Road, Richmond
Surrey TW9 4NS - 01-876 7957

—TURNER—

STEREO POWER AMPLIFIERS

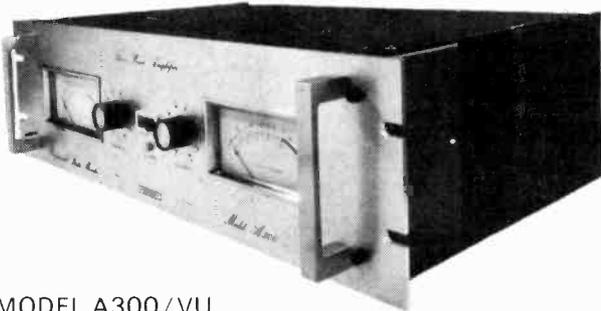

MODEL A300/VU

A range of professional stereo power amplifiers designed and manufactured to a very high standard.

The A Series (Professional Studio Monitor) amplifiers feature dual power supplies to maintain full RMS power on both channels.

The B Series (Professional) amplifiers feature single power supplies suitable for most music applications.

		STANDARD	WITH VU's
MODEL A500	250+250 watts RMS, 4 ohms	£380.00	£440.00
MODEL A300	150+150 watts RMS, 4 ohms	£262.50	£322.00
MODEL B300	150 watts RMS per channel	£210.00	£250.00
MODEL B200	100 watts RMS per channel	£170.00	£210.00

The above prices are list and exclusive of VAT.

Overseas Import Agents are invited to make their final applications for allocation of areas for 1976 exports.

TURNER ELECTRONIC INDUSTRIES LTD.
 175 Uxbridge Road, London W7 3TH
 Tel. 01-567 8472

WW—047 FOR FURTHER DETAILS

Test Equipment



Multimeters

The Eagle range of multimeters covers every possible need of the electrical or electronic engineer. They cost from about £6 to £58 (inc V.A.T.). There's at least one which suits your job precisely.

We have a lot of other test equipment too. Send the coupon and we'll send you our complete catalogue.

Please send me details of all your test equipment

NAME

ADDRESS



Eagle International Ltd., Precision Centre, Heather Park Drive, Wembley HA0 1SU
 Tel(01)-902 8832



WW—070 FOR FURTHER DETAILS

AEL 3030

The AEL 3030 is a compact, fully solid-state 150 watt PEP output Transmitter-Receiver covering 2.16 MHz on 4 or 6 channels.

Rugged construction for today's tough environments. Easily accessible for simple maintenance.

Ten plug-in modules give maximum insurance against loss of service.

The advanced technology used in the AEL 3030 provides unmatched efficiency in point to point or mobile communication, minimises size and cost and maximises reliability!

DESIGNED FOR RELIABILITY



For further information and colour brochure write to:

AEL GATWICK HOUSE
 HORLEY, SURREY, ENGLAND
 TELEPHONE: HORLEY (02934) 5353

Telex: 87116 (Aerocon Horley)
 Cables: Aerocon. Telex: Horlev

WW069—FOR FURTHER DETAILS



Telequipment's new battery/mains Miniature scope

Diminutive in size and weight—and in cost—Telequipment's new S22 miniature oscilloscope is packed with features usually seen only in instruments twice the size.

For its remarkable specification it is probably the smallest and least expensive scope in the world. Size 3in. x 8in. x 10in, weight less than 10lb.

The S22 is a single trace 5MHz scope with an additional high sensitivity (1mV) facility, and offers automatic selection of TV line or frame displays. It is battery or mains operated. The internal batteries are rechargeable.

For engineers on the move—or wherever accessibility is limited or working conditions are restricted—Telequipment's new S22 miniature scope is ideal. It is robust and easy to operate.

Telequipment gives you more scope for your budget

Write or telephone for full specification and a demonstration



Tektronix UK Ltd.
Beaverton House, PO Box 69, Harpenden, Herts.
Telephone: Harpenden 63141 Telex: 25559



WW-012 FOR FURTHER DETAILS

TO22

wireless world

Electronics, Television, Radio, Audio

FEBRUARY 1976 Vol 82 No 1482

Contents

- 29 **Deliver us from data**
- 30 **Time-code receiver clock** by A. F. Cross
- 35 **Literature received. Sixty years ago**
- 36 **News of the month**
 - Dublin, Sheffield receive Indian TV
 - Audio Fair under new management
 - Colour TV sent by p.c.m.
- 38 **New forms of waveguides** by H. M. Barlow and M. Nouri
- 40 **Microcomputer development system**
- 41 **Letters to the editor**
 - Audio amplifier load specification
 - Microprocessors
 - The consultants
- 45 **Electronic systems—2** by P. R. Darrington
- 47 **Wireless World Teletext decoder — 4** by J. F. Daniels
- 51 **February meetings**
- 52 **Space news**
- 57 **Thermistor and thermocouple action** by C. Budd
- 61 **Gunn effect and avalanche oscillators** by F. A. Myers
- 66 **H.F. predictions**
- 71 **Electronic circuit calculations simplified — 7** by S. W. Amos
- 76 **Circuit ideas**
 - Single gang pan-pot
 - C.r.o. input isolating probe
 - Automatic switch-off power supply
- 79 **World of amateur radio**
- 80 **New products**
- 83 **Circards 28: linear c.m.o.s. circuits** by J. Carruthers, J. H. Evans, J. Kinsler and P. Williams
- 84 **Real and imaginary** by "Vector"
- 122 APPOINTMENTS VACANT
- 136 INDEX TO ADVERTISERS

Price 35p (Back numbers 50p, from Room 11, Dorset House, Stamford Street, London SE1 9LU.)
Editorial & Advertising offices: Dorset House, Stamford Street, London SE1 9LU.
Telephones: Editorial 01-261 8620; Advertising 01-261 8339.
Telegrams/Telex. Wiworld Bisespres 25137 London. Cables. "Ethaworld, London SE1."
Subscription rates: 1 year: £7.00 UK and overseas (\$18.20 USA and Canada). Student rate: 1 year, £3.50 UK and overseas (\$9.10 USA and Canada).
Distribution: 40 Bowling Green Lane, London EC1R 0NE. Telephone 01-837 3636.
Subscriptions: Oakfield House, Perrymount Rd, Haywards Heath, Sussex RH16 3DH. Telephone 0444 53281. Subscribers are requested to notify a change of address.

© IPC Business Press Ltd, 1976



Cover shows trace of laser beam responding to sound waves, made by using mirrors attached to loudspeakers. Photograph, provided by Standard Elektrik Lorenz AG, was taken by Manfred Kage of the Institut für wissenschaftliche Fotografie.

IN OUR NEXT ISSUE


Push-button f.m. tuner design in two versions. Simple version for easy construction and adjustment. Advanced version for higher performance. Extra circuit facilities can be added.

Radar targets — aircraft, motor cars, birds and other things. How various objects appear to "eyes" which respond only to electromagnetic radiation.

Frequency modulation illustrated. Oscillograms obtained with the aid of a Fourier synthesizer show the significance of sidebands in an f.m. signal.

SIXTY-SIXTH YEAR
OF PUBLICATION

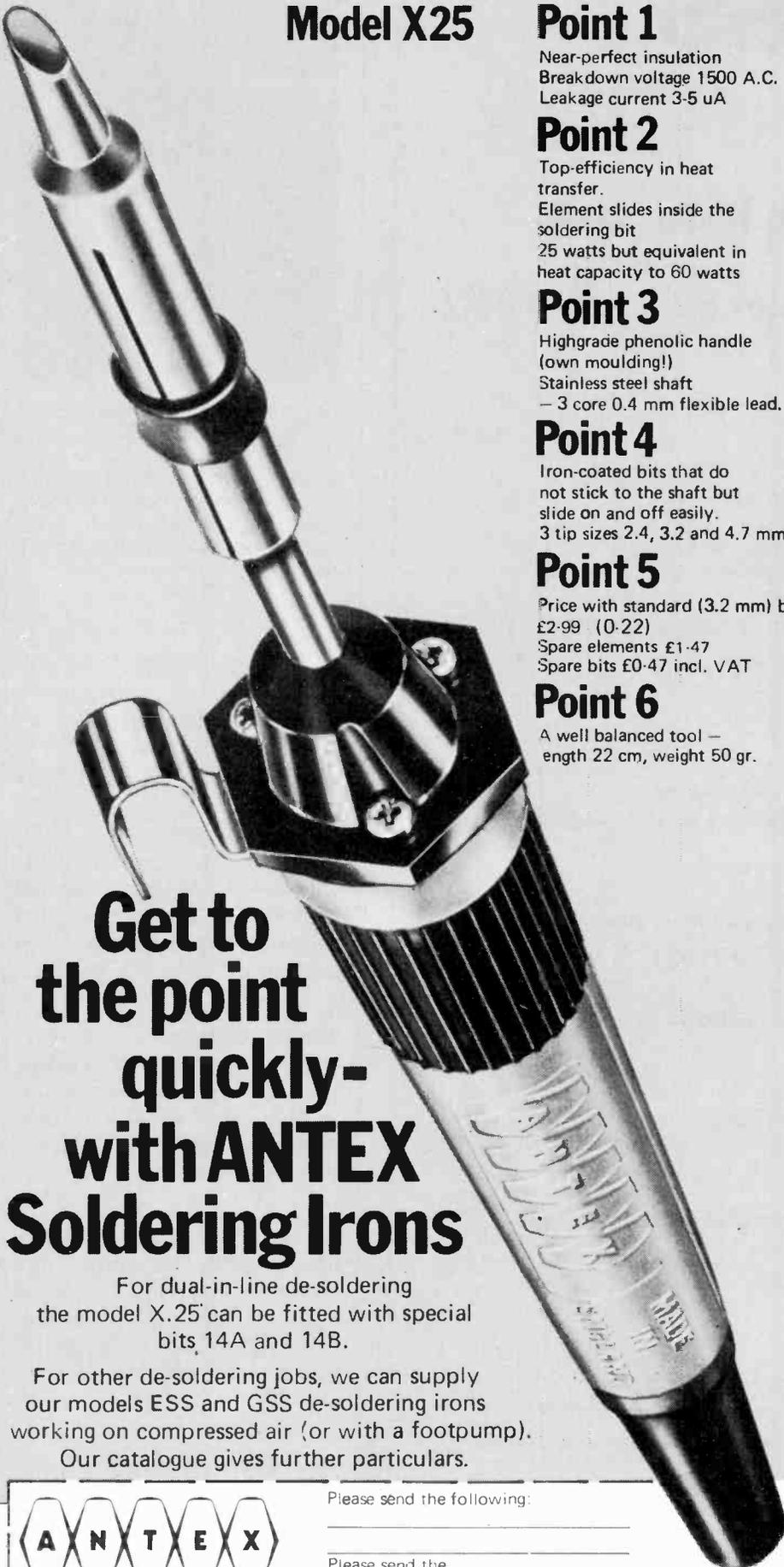ibpa
International Business
Press Associates



Model X25

Point 1

Near-perfect insulation
Breakdown voltage 1500 A.C.
Leakage current 3-5 uA

Point 2

Top-efficiency in heat transfer.
Element slides inside the soldering bit
25 watts but equivalent in heat capacity to 60 watts

Point 3

Highgrade phenolic handle (own moulding!)
Stainless steel shaft
- 3 core 0.4 mm flexible lead.

Point 4

Iron-coated bits that do not stick to the shaft but slide on and off easily.
3 tip sizes 2.4, 3.2 and 4.7 mm.

Point 5

Price with standard (3.2 mm) bit £2-99 (0-22)
Spare elements £1-47
Spare bits £0-47 incl. VAT

Point 6

A well balanced tool - length 22 cm, weight 50 gr.

Get to the point quickly - with ANTEX Soldering Irons

For dual-in-line de-soldering the model X.25 can be fitted with special bits 14A and 14B.

For other de-soldering jobs, we can supply our models ESS and GSS de-soldering irons working on compressed air (or with a footpump).

Our catalogue gives further particulars.

The Antex Range

All prices include VAT. P&P in brackets

MODEL C - 15 watt miniature soldering iron
Bits slide on and off stainless steel shaft. Elements fitted inside steel shaft for efficient heat transfer. Length 16 cm. Complete iron with 2.3 mm. iron-coated bit £2-99 (0-22) Spare elements £1-20 Spare bits £0-35 (nickel) £0-45 (iron-coated).

MODEL G - 18 watt miniature soldering iron
Looks exactly like model C, but because of the extra 3 watts should be kept going all day on repairs or production. Stainless steel shaft - fitted with standard iron-coated bit 2.3 mm. £3-21 (0-22) Spare elements £1-69 Spare bits 2.3, 3 or 4.7 mm. £0-45.

MODEL CCN - 15 watt miniature soldering iron
Unique - ceramic shaft - no measurable leakage - capacitance 30 pf. Tested at 2000 volts A.C. Length 16 cm. Complete with standard iron-coated bit 2.3 mm. £3-21 (0-22). 4 other slide-on and-off bits available from £0-45 Spare elements £1-69. Suitable for the most delicate soldering job imaginable.

MODEL X.50 T.C. - 50 watt temperature controlled soldering iron
Leakage current negligible - Temperature controlled to 2°C either way. Ceramic shaft inside stainless steel shaft. Tested at 2000 volts A.C. Complete with 3 mm. iron-coated bit £10-55 (0-27) Normally set at 370°C Length 20 cm. Weight 50 gr.

MODEL SK.1 - SOLDERING KIT
Fitted with model C miniature iron (see above), 2 spare bits 2.3 and 4 mm., heat sink, reel of solder. Plastic base serves as stand. Booklet "How to Solder" gives useful tips for beginners. Price £4-62 (0-42)

MODEL MLX - 12 volt - 25 watt Soldering iron with 4½ mtrs. lead and crocodile clips
Useful for repairs on motor cars, boats, model trains, etc. Can be worked off car-type battery. Complete with 3.2 mm. bit £3-53 (0-30) Two other bits available 2.4 and 4.7 mm. £0-47 each. Packed in a plastic wallet with guide "How to Solder".

STAND S.T.3
High grade insulation material, chromium plated steel spring. Suitable for all our models. Replaceable sponges, space for spare bits. Complete £1-21 (0-24)



Please send the following:

Please send the ANTEX colour catalogue.

From radio or electrical dealers, car accessory shops or in case of difficulty direct from: ANTEX LTD. FREEPOST, PLYMOUTH PL1 1BR (no stamp required) Tel. 0752 67377.

I enclose cheque/P.O./Cash (Giro No. 258 1000)

NAME _____

ADDRESS _____

wireless world

Deliver us from data

Editor:
TOM IVALL, M.I.E.R.E.

Deputy Editor:
PHILIP DARRINGTON
Phone 01-261 8435

Technical Editor:
GEOFFREY SHORTER, B.Sc.
Phone 01-261 8443

Assistant Editors:
BILL ANDERTON, B.Sc.
Phone 01-261 8620
MIKE SAGIN
Phone 01-261 8429

Production:
D. R. BRAY

Advertisements:
G. BENTON ROWELL (*Manager*)

KEVIN BURNAL
Phone 01-261 8515

O. BAILEY (*Classified Advertisements*)
Phone 01-261 8508 or 01-261 8423

JOHN GIBBON (*Make-up and copy*)
Phone 01-261 8353

IPC Electrical-Electronic Press Ltd
Publisher: Gordon Henderson

The Government's proposals for safeguarding the privacy of personal information held in electronic computers and data banks are welcome but not before time. In a recent White Paper* they announce their intention to set up a permanent watchdog organization, a Data Protection Authority, to oversee the use of computers and "ensure that they are operated with proper regard for privacy and with the necessary safeguards for the personal information which they contain." One wonders why it has taken so long for the UK to get as far as a mere statement of intent when other countries have already taken the necessary steps to protect their citizens by laws. Sweden introduced a Data Act in 1973, the USA a Privacy Act in 1975, a part of West Germany (Hesse) had a Data Protection Law as early as 1970, and legislation is on the way, in the form of Bills or draft laws, in at least ten other countries.

At least our tardiness in the UK may give us time to consider a wider danger, of which the threat to privacy in data banks is only a part: the extent to which we are in thrall to information. Two ways of getting power over people are to hold information about them and to control the information that is supplied to them. Electronics has enormously increased the capacity to do both these things. For the holding of information (as in data banks) electronics makes possible extensive, cheap storage, quick access and transfer between systems, and easy combination of data from different sources to form "identikit" pictures of individuals. And the information is held in codes which are not intelligible to the individuals themselves. For the controlling of information supplied to people, broadcasting is becoming increasingly powerful. It cannot control what people think but, like other media, it does control by its selection of material what they think about. Whenever there is a revolution or military coup the first thing to be taken over, usually by force, is the radio and television services. But broadcasting is not the end of the matter. Britain, in common with other industrialized nations, is considering the introduction of information services wired to people's homes (e.g. by existing domestic telephone lines or perhaps wideband optical fibres in the future). Already the British Post Office has started trials with its Viewdata system. And, as a correspondent pointed out in the January issue, if people are selecting information via a permanent wired system from an electronic data store held by some organization, it is possible to monitor their choice of information, discover what they are interested in and exploit this knowledge.

In a benign democratic society one may not think there is much to fear. Unfortunately, improved information technology helps benign democracy to become paternalistic bureaucracy. From there to repressive totalitarianism is but a short step.

*"Computers and Privacy" Cmnd. 6353, HMSO, 28p, with a supplement "Computers: safeguards for privacy" Cmnd. 6354, HMSO, 55p.

Time-code receiver clock — 1

An accurate and automatic digital time-piece

by A. F. Cross, B.Sc.

Thames Television Ltd

Last year time code transmissions started from Rugby on 60kHz, offering a new approach to accurate time-keeping in the UK. This article describes a 24-hour digital clock of flexible design, based on the Rugby signal.

Many designs for digital clocks have been published, but generally they have had two drawbacks; they require an accurate internal frequency source and manual setting. While the first problem may be solved, at a price, the second usually involves the GPO speaking-clock. This design was aimed at producing a relatively inexpensive time-piece capable of keeping correct time without regular checking. The usual mains-derived reference, whilst having a low long term frequency error, exhibits a high short term variation, with the result that a clock can be in error by several seconds at any time. On the other hand, a local crystal reference will exhibit an accumulating long term error.

The clock to be described uses a crystal oscillator and divider chain. Checking and setting of the clock is provided automatically by a received time code.

transmitter at Rugby. In 1974 a data code was added to the signal to give the exact time of day. The carrier is on-off modulated, as shown in Fig. 1. The one-second intervals are indicated by the start of a 100ms break in carrier, and the minute by a 500ms break. The data has been added to the 500ms break. The 20ms control pulse indicates that data is to follow, which comprises a leading 1 followed by thirteen data bits for hours and minutes. The data is followed by a parity bit which checks that the data has been correctly received.

The carrier, and hence the pulse timing, is based on a rubidium reference at Rugby, which is compared with a caesium reference at the NPL Teddington; the deviation is usually in the order of 1 in 10^{11} . The clock uses the timing of the code to resynchronize the reference divider, and the data to check and correct the displayed time. Several checks are carried out on the time code


before it is allowed to influence either internal timing or displayed time. The transmission is normally maintained twenty four hours a day, except for five or six hours on the first Tuesday of each month to allow for maintenance. The clock will free-run during this period and the accumulated error (a fraction of a second) will be eliminated when the code is again received.

Initially, consideration was given to using the one-second received pulses to clock the seconds display. This method has problems because interference can cause multiple clocking, and other information, which is transmitted during the minute, must be discriminated against. It was decided for overall simplicity to derive the 1Hz signal from the reference divider. Although the transmitted code is always GMT, or more precisely UTC (Universal Co-ordinated Time), the facility for switching the display to BST manually has been provided. A further feature of the clock is that it will follow the internationally agreed time-scale corrections, often referred to as the leap-second. This is a one-second correction which is made to all standard clocks to maintain tracking between the precise atomic standard and the astronomical time scale. The correction is made every 12 or 18 months as required (*Wireless World*, June 1971, p.276). A free-running clock, no matter how accurate, cannot carry out this adjustment automatically.

Transmission

The National Physical Laboratory has been controlling the transmission of 1s pulses radiated on 60kHz from the GPO

Fig. 1. On-off modulation of the 60kHz carrier — one-second intervals are indicated by the start of a 100ms break, and the minute by the 500ms break.

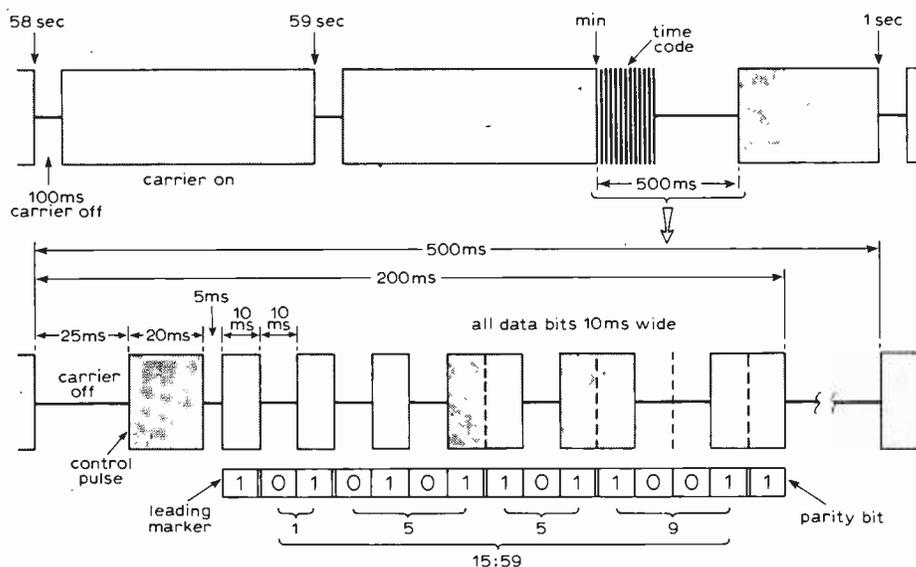

System operation

The block diagram in Fig. 2 shows the interconnexion between the circuit functions, each of which may be constructed independently. The circuit may be considered in two sections; a free-running clock, and a receiver plus control logic. The clock comprises the hours, minutes and seconds dividers and displays, the crystal oscillator, and the 5-decade reference divider. These sections together will operate as a normal digital clock, except that no manual setting facility is provided.

The receiver amplifies and demodulates the 60kHz signal which is then passed to the time code register section. When a control pulse has been detected a 100kHz clock loads the serial data into the shift register. When the register is full, clocking ceases and, if parity is correct, a data strobe pulse is generated. The data in the register is applied to the 13-bit comparator, which also receives data from the hours and minutes display-dividers. An output from the comparator to the control logic indicates whether the display-dividers agree with the received data. Upon receiving the data-strobe signal from the time-code register, and a comparison error signal from the comparator, the control logic initially assumes that the error is in the received code. If, however, two consecutive received data words both give an error signal, the control logic acts to correct the display-dividers. This is achieved in less than 15ms by fast-clocking the hours and minutes-dividers at 100kHz until the comparator gives the no-error signal. In normal operation the received code agrees with the contents of the hours and minutes display-dividers. The control logic then resets the seconds-divider, which should be reading zero, and resynchronizes the 5-decade divider, which is normally a correction of less than 1ms. The outputs of the hours-divider pass through the GMT/BST converter before driving the display logic. With the converter set to GMT there is no effect on the hours data; when set to BST, a one hour correction is made to the display.

Clock options

It is possible to simplify the clock by omitting certain functions. The simplest circuit would comprise the

receiver, the time-code register and the four-digit display logic. Such a clock would display GMT hours and minutes. A 1kHz signal is required to control the clock generator, but its accuracy need only be about $\pm 1\%$ and a 555 timer would be suitable. Retaining three decades of the divider chain, and improving the accuracy of the 1kHz clock to about $\pm 0.1\%$ would produce a 1Hz signal for clocking a seconds-divider. The 3-decade divider would be resynchronized with the data-strobe signal, which would also reset the seconds count. In the absence of a carrier these simplified clocks would cease to function correctly because there is no display counter. This also means that there is little protection against incorrect data; once a control pulse has been detected the display will show the contents of the shift register, even if it is wrong. The parity signal can, however, light a warning indicator. Also, if a control pulse is not recognised, the display will not update, but continue to show the previous time code. Even with these limitations, a simplified version of the clock can still find useful applications where an occasional time check is required and a continuous reliable readout is not necessary. The GMT/BST converter may be included or omitted as required.

Circuit operation

The units of seconds, minutes and hours each use a 7490 decade counter, and the tens-of-seconds and minutes use a


7492 divide-by-12 as shown in Fig. 3. With the most significant bit ignored, (output D) the device divides by 6 in binary sequence. The tens-of-hours divider is provided by a 7473 dual JK flip-flop, and the 24-hour reset is provided by a D-type flip-flop.

When a count of 24 exists in the hour-dividers a logic 0 is applied to the flip-flop via NAND gate IC_{5b} which is connected to the appropriate divider outputs. Because the D-type is clocked at 100kHz, the 0 on the D input will be clocked within 10 μ s, which sets the Q output to 0 and the \bar{Q} output to 1. The Q output provides a low reset to the JK flip-flops for tens-of-hours; the logic 1 on the \bar{Q} output provides the required high reset on the hours-units-divider. The D input now changes back to a 1, but the D-type does not change until the next clock pulse. Thus a 10 μ s reset pulse to the hours-divider is ensured.

The NAND gates IC_{4d} and IC_{5a} between the seconds and minutes-dividers provide the facility for injecting fast clocking pulses into the minutes and hours-dividers for time setting. In normal operation these gates have no effect, and the output pulses from the tens-seconds divider pass to the clock input of the units-minutes divider. When the fast-set condition is operating, the inhibit-seconds output signal goes low, thereby forcing the output of gate IC_{4d} to logic 1. Pulses at 100kHz appear on the set-time input of gate IC_{5a} which are then inverted. Thus the hours and minutes count is advanced at 100,000 steps per second. The maximum setting time is determined from the time taken to clock the dividers through 24 hours i.e. 14.4ms.

The 5-decade divider is shown in Fig. 4 and comprises five 7490 i.cs. Besides

Fig. 2. Block diagram which may be considered as two sections – a free running clock, and a receiver plus control logic.

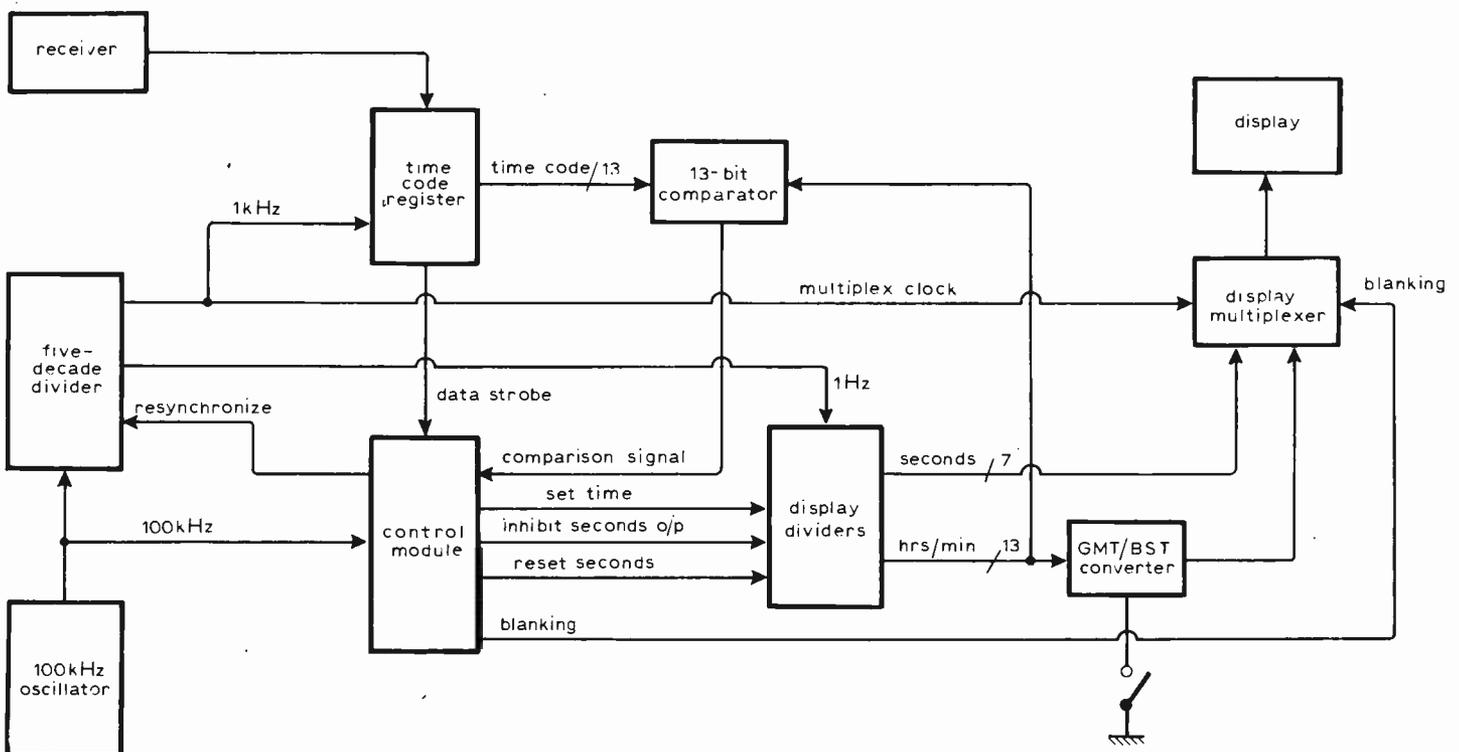

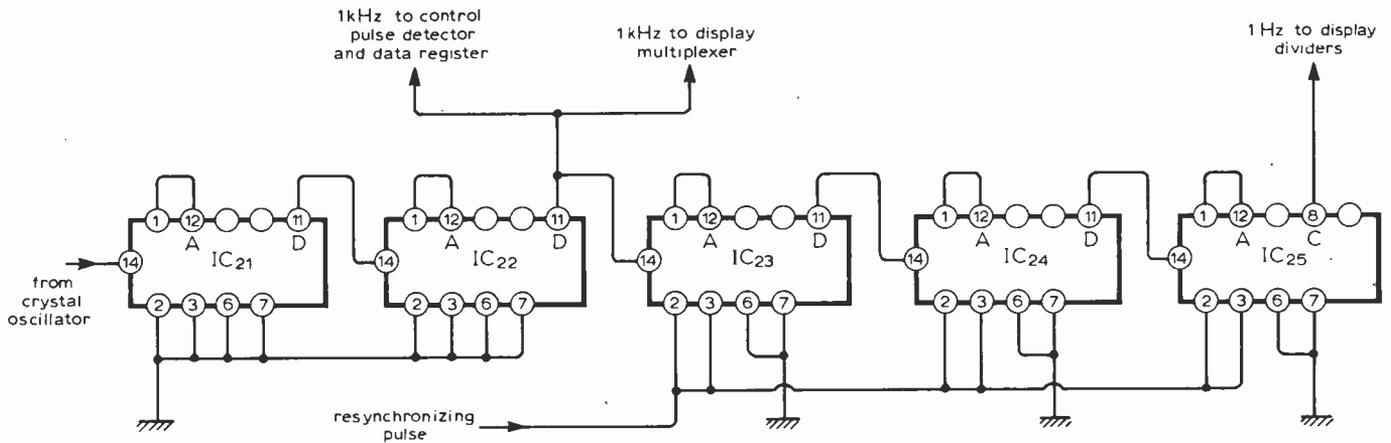
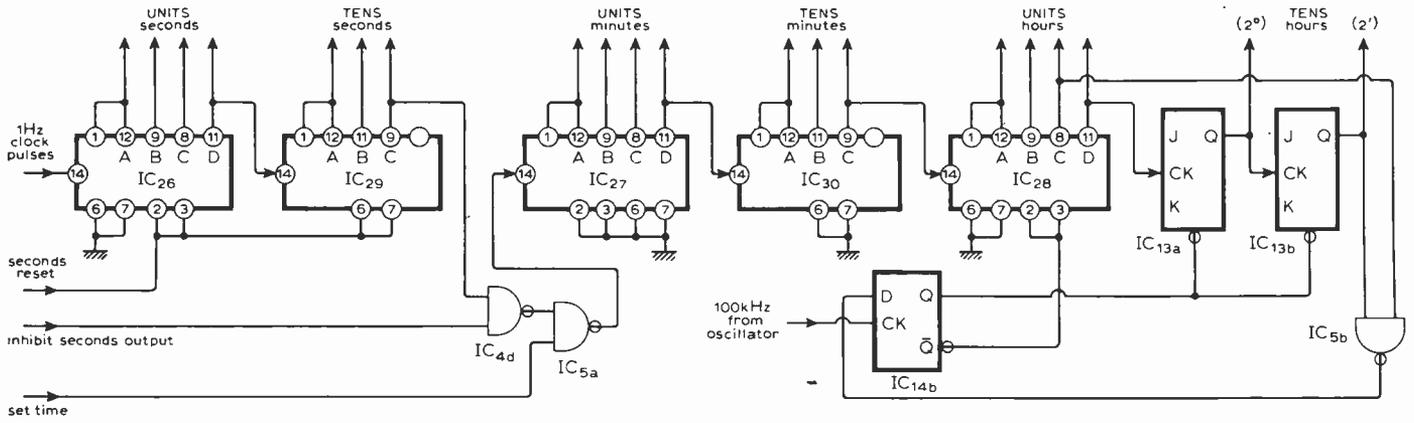


Fig. 3. (top) Display dividers – seconds, minutes and hours each use decade counters and the tens of seconds and minutes use divide-by-12s.

Fig. 4. (above) Five-decade divider. Besides providing the 1Hz output for clocking the display dividers, it also provides 1kHz for the time-code register.

Fig. 5. (right) Oscillator circuit incorporating a two transistor buffer to produce a t.t.l. compatible output at 100kHz.


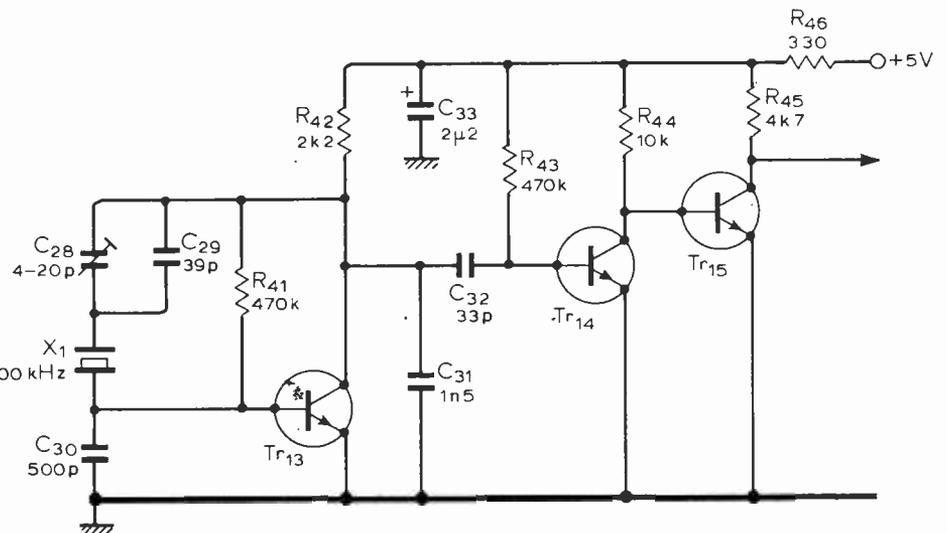


Fig. 6. (below) Receiver and demodulator circuit. A.g.c. is applied over the second and third stages.

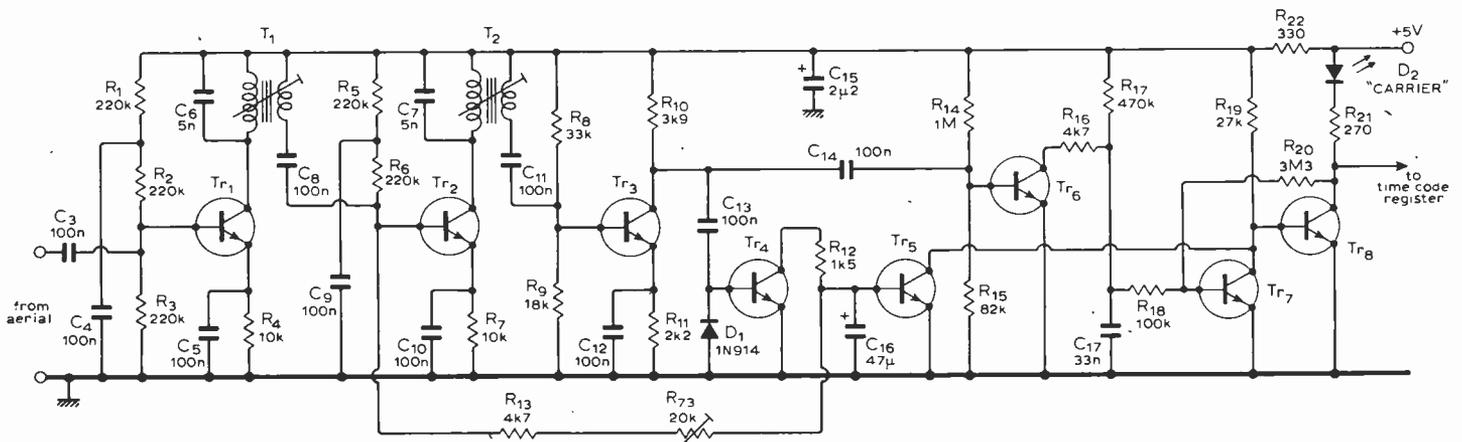

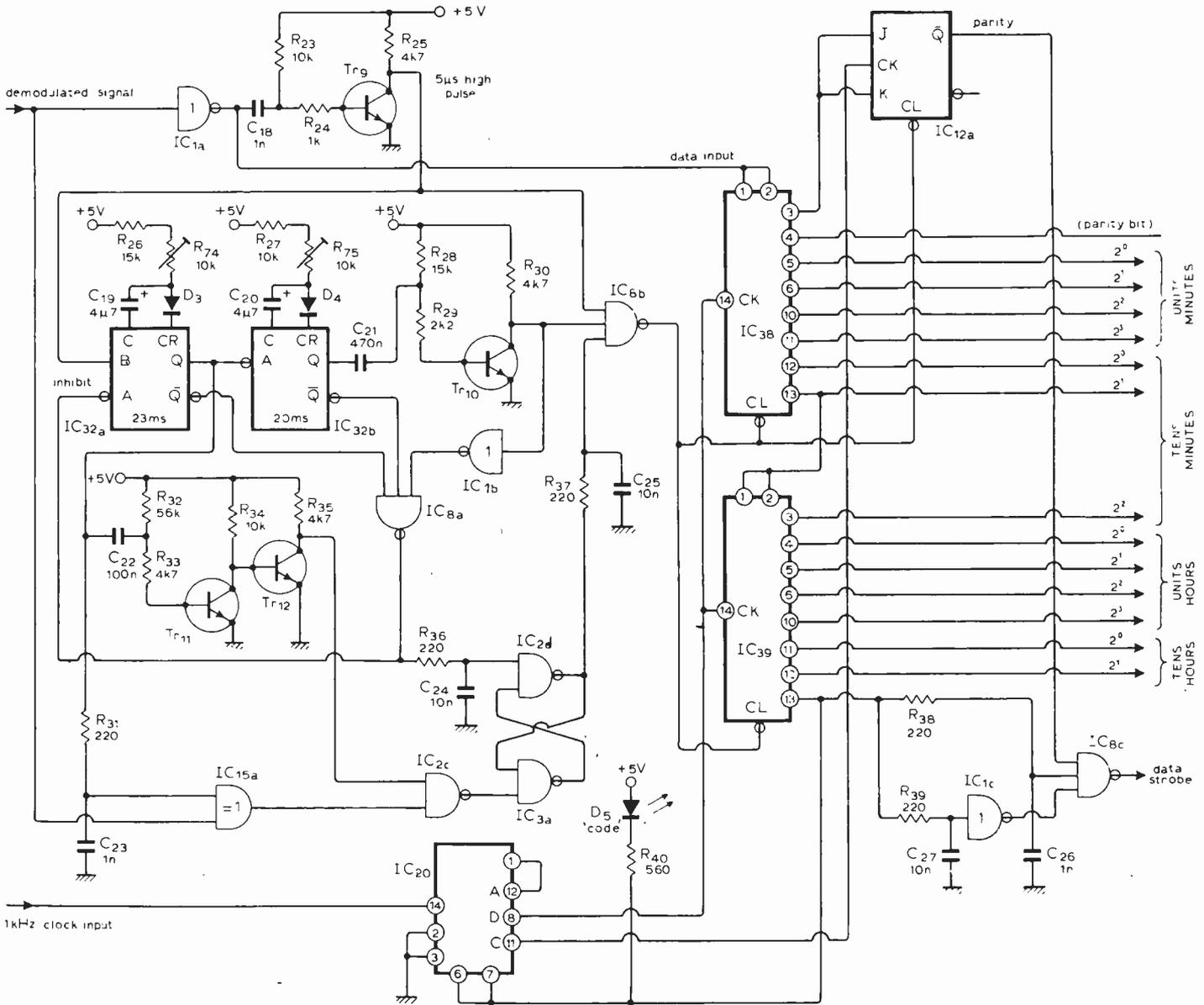


Fig. 7. Time-code register – takes in the demodulated signal, detects the control pulse and stores the incoming time code.

Truth table for decade counter

	D	C	B	A
Reset at 0.2s	0	0	0	0
State at 0.3s	0	0	0	1
State at 0.4s	0	0	1	0
State at 0.5s	0	0	1	1
State at 0.6s	0	1	0	0
State at 0.7s	0	1	0	1
State at 0.8s	0	1	1	0
State at 0.9s	0	1	1	1
State at 1.0s	1	0	0	0
State at 1.1s	1	0	0	1
State at 1.2s	0	0	0	0

Box: 1-0 transition provides clocking output at end of second.

providing the 1Hz output for clocking the display-dividers, it also provides 1kHz for the time-code register, which in turn derives the 100Hz data clocking pulses. The 5-decade divider is resynchronized by resetting the last three dividers. The resetting pulse from the control logic appears at the end of the received data word, which is about 200ms after the beginning of a second as shown in Fig. 1. Conventional setting to zero would therefore result in the clock being permanently 0.2s slow. However, Truth Table 1 for the decade divider reveals that, although the D output goes

low one second after the zeros reset, the C output does so after 0.8s. If, therefore, the C output is used to clock the seconds-display dividers, the indicated time will be correct to within about 5ms.

The oscillator circuit in Fig. 5 is quite conventional. A two transistor buffer is added to produce a t.t.l. compatible output which operates at 100kHz. When the Rugby transmitter is switched off for maintenance, the crystal oscillator is required to hold the correct time to an accuracy of about 5 parts per million. This can be achieved by a simple oscillator, over a restricted temperature range but, if greater accuracy is required, a temperature-compensated oscillator should be considered.

The receiver, see Fig. 6, uses a ferrite rod aerial, followed by three stages at r.f., the first two being tuned. Automatic

gain control is applied over the second and third stages and a simple transistor demodulator is employed followed by d.c. amplification to provide a t.t.l. compatible output. At low signal levels a muting circuit inhibits the demodulator output. The r.f. stages are conventional and require little explanation. The tuned transformers are not critical and the originals were hand-wound. Transistor Tr₄ is the level detector for the a.g.c. circuit. Signal peaks exceeding the base-emitter threshold voltage will result in Tr₄ discharging the a.g.c. reservoir capacitor C₁₆. This reduces the base bias voltage to Tr₂ which reduces the gain of the second stage. With a.g.c. operating, the signal at the collector of Tr₃ is between 600mV and 800mV peak-to-peak. The a.g.c. voltage is detected by Tr₅ and no-signal or a weak signal will result in an increase in a.g.c. voltage. When this voltage turns Tr₅ on the output of the demodulator is inhibited. To allow for differing transfer characteristics and variations in signal strength, a potentiometer (R₇₃) in the a.g.c. feedback line may be used to vary the level of signal at

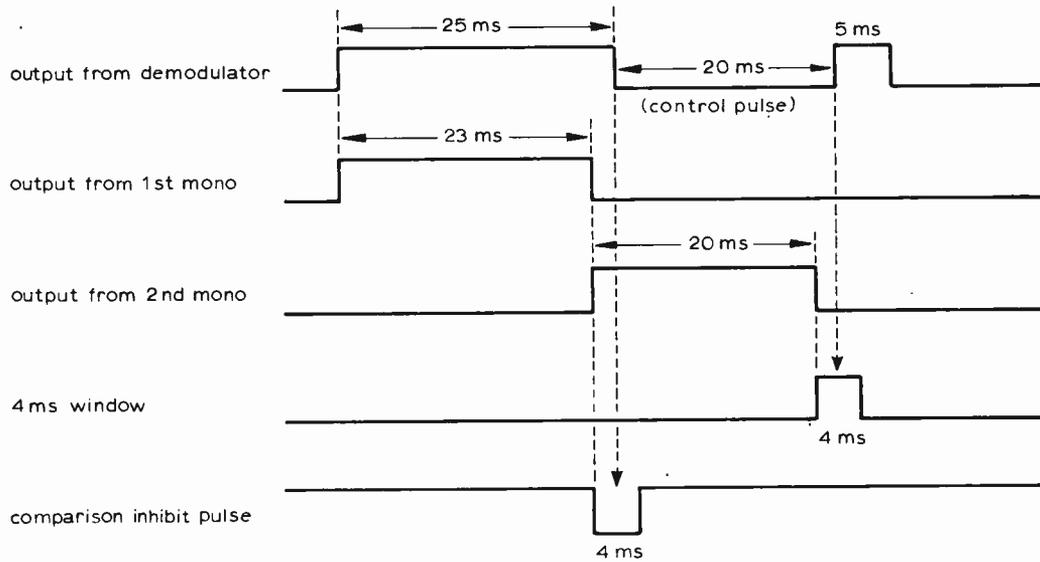



Fig. 8. Timing diagram for control pulse detection.

which the muting circuit operates. In areas of high signal strength, the muting circuit can operate at a higher signal level, thereby improving the interference rejection when the carrier is not present. With a weaker signal, the muting circuit must be set to operate at a lower level. Transistor Tr_6 is the demodulator and, with no signal present, is biased off. With a carrier signal, the positive peaks turn Tr_6 on which discharges C_{17} . The potential on C_{17} is detected by Tr_7 which, with Tr_8 , produces a 5V demodulated signal. Resistor R_{20} provides a small measure of positive feedback to assist clean switching. The output from Tr_8 is fed to the time-code-register logic, and also drives a l.e.d. indicator (carrier).

The time-code-register, Fig. 7, takes in the demodulated signal, detects the control pulse and stores the incoming time code. It also checks the parity of the detached signal and generates a data-strobe pulse when the register is full. Transistor Tr_9 produces a $5\mu s$ pulse for every carrier-off transition. This pulse is used to trigger monostable IC_{32a} (23ms), whose trailing edge triggers monostable IC_{32b} (20ms). The differentiated trailing edge of the second monostable pulses the transistor Tr_{10} which delivers an output of about 4ms. The output of gate IC_{8a} inhibits retriggering of the monostable chain during its active period, i.e. for 47ms. Gate IC_{8a} also applies a reset level to the cross-coupled NAND-gate bistable IC_{2b}/IC_{3a} , which is removed for the 47ms period. The timing of the internally generated pulses in relation to the demodulator output is shown in Fig. 8. The action of the detector is best explained if monostable IC_{32a} is imagined to have a period of 25ms, and monostable IC_{32b} a period of 18ms; the reason for modifying these periods will be explained later.

The detector attempts to mimic the expected incoming waveform of the control pulse. The Q output of the first monostable, once it has been triggered,

Fig. 9. Comparator circuit which compares 13 inputs from the time-code register with the hours and minute-divider output.

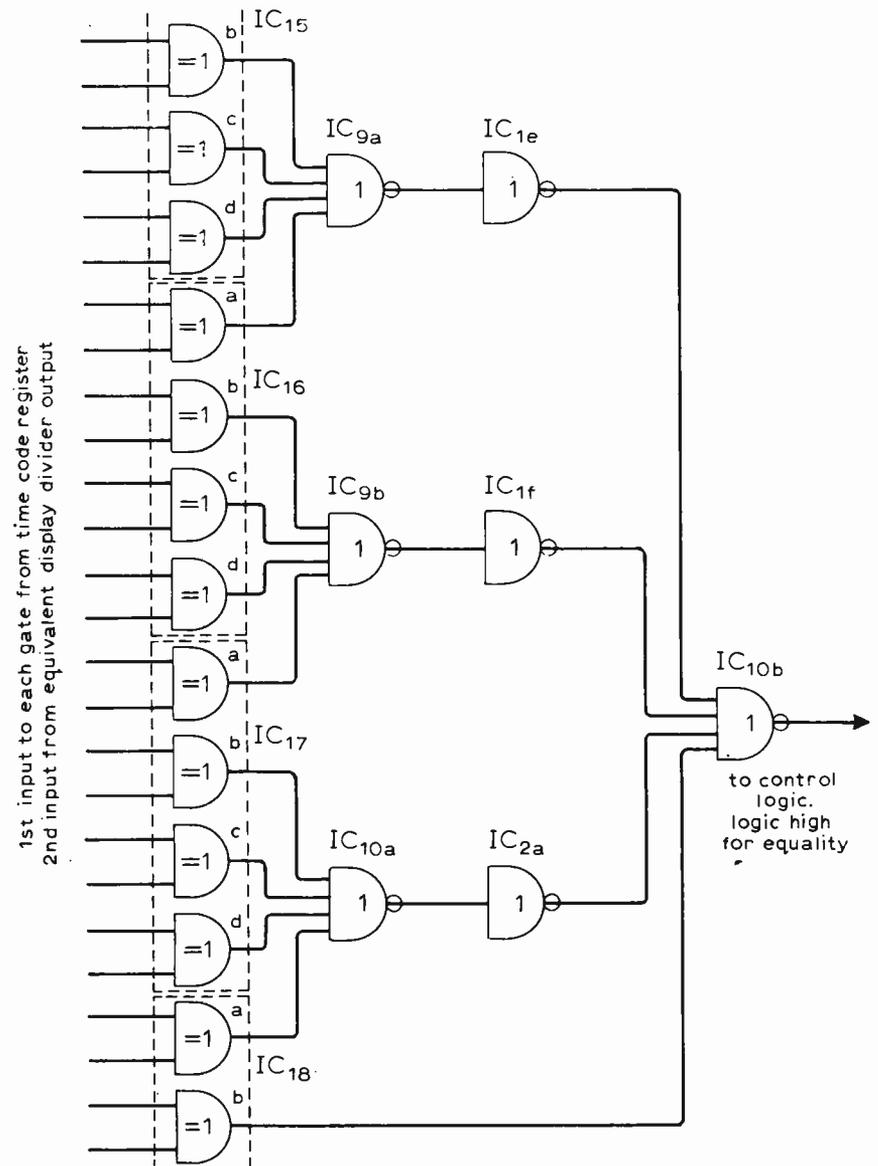

goes high for 25ms, and then low. This is exactly the signal out of the demodulator when a control pulse is received. The two signals are compared and any difference results in the output of exclusive-OR gate IC_{15a} going high, and the cross-coupled NAND-gate bistable becoming set (output of IC_{2d} low). Because it is impossible to mimic exactly the 25ms off-period, a degree of tolerance is allowed by shortening the monostable period to 23ms and producing at the end of the period, a 4ms inhibit pulse (Tr₁₁, Tr₁₂) which prevents the setting of the bistable around the time of the carrier-on transition. The timing allows a total error of up to 2ms either way. The 4ms pulse from Tr₁₀ generates a gating window for the period 43ms to 47ms after the initial triggering of the 23ms monostable. Its output is applied to the 3-input NAND gate (IC_{8b}). For a low pulse on the output of the gate, three input conditions must apply; the 4ms window must be open, the bistable must not have been set, and an off-transition pulse must appear on the collector of Tr₉. The low output pulse represents the end of the control pulse.

To summarise; after receipt of an off-transition, a continuous high for 23ms is sought, followed by a continuous low from 27ms to 43ms, again followed by an off-transition between 43ms and 47ms. The signal will be ignored if there is any deviation from these conditions. This detection technique has been found to give extremely good immunity against false triggering due to noise. The low pulse generated on the output of IC_{8b} resets the two 8-bit serial-in shift registers (IC₃₈ & 39). All outputs go low. When pin 13 of the second register goes low it removes the reset-to-nine signal from the clock generator IC₂₀ which is a divide-by-10, clocked by a continuous 1kHz signal from the 5-decade divider chain. Upon removal of the reset, it starts to generate a 100Hz signal on its D output, the first positive transition occurring between 8ms and 9ms after the removal of the reset, and thereafter at 10ms intervals. This signal is applied to the clock input of the shift registers, thereby clocking in the time code applied to the input of the first register.

The first data bit in the time code is always a 1; after 16 clock pulses this 1 will have reached the last bistable in the second shift register (pin 13). This output restores the reset to the clock generator which stops the clock pulses. The register now contains the complete time code, including leading marker bit and parity bit. The parity is checked by using a JK flip-flop (IC_{12a}) to count the number of 1's appearing at the first shift register output as the data is clocked through. For every 1 clocked into the register, the J and K inputs become logic 1; when clocked, the JK flip-flop inverts its previous state. For a 0 on the J and K inputs, the output state does not change when the flip-flop is clocked.

Thus the final state of the JK flip-flop is determined by whether an even or odd number of 1's have been clocked into the register. The flip-flop starts in the reset state, Q = 0; if received parity is correct the final state is Q = 1. Gate IC_{8c} generates the data-strobe pulse of 2μs about 200ns after the full signal is received from the shift register, and in the presence of correct parity. The data-strobe pulse is passed to the control logic. The data-clock enabling signal is used to drive the code indicator D₅, which will light for about 150ms upon recognition of a control pulse.

Thirteen inputs from the time-code register are compared with the hours and minutes divider outputs — Fig. 9. Thirteen exclusive-OR gates (IC_{15, 16 & 17}) each compare one bit, giving a logic 0 output for input identity and a 1 for disparity. The first twelve outputs are OR-ed via inverted NOR gates, and these outputs are again OR-ed, along with the thirteenth bit comparison, by NOR gate IC_{10b}, producing a logic high for no comparison error.

(To be continued)

Sixty Years Ago

The principle of redundancy, or the "belt and braces" approach to the achievement of reliability, is common enough, but for those who imagined it to be a modern, money-no-object attitude, the following piece from our issue of February, 1915, is some indication to the contrary. It rather reminds one of the writers who advocate the use of electronic ignition devices, but recommend the use of a changeover switch for instant reversion to the mechanical system.

"Every means of long-distance communication has been used in this war, and although the carrier pigeons' loft in the South of England, long utilised by the British Admiralty, was dismantled a few years ago on account of the introduction of wireless telegraphy, we know that pigeons are still being used by the British for war purposes. Only quite recently the War Office authorities issued instructions to the effect that it was hoped that British sportsmen who were not able to distinguish between ordinary wood pigeons and carrier pigeons would abstain from pigeon shooting altogether. The reason for this appears to have been that some of our own sportsmen were destroying British flying dispatch bearers. The fact of the matter with regard to all these things is that the latest method may for all ordinary purposes supersede its predecessors; but in times of strain and stress it is wise to have as many strings to one's bow as possible."

Literature Received

Magnifiers for desk use, quality control and inspection, including the illuminated variety, spectacle types and eye magnifiers are described in an illustrated brochure from Combined Optical Industries Ltd, 200 Bath Road, Slough, SL1 4DW
..... WW407

A seven-volume collection of data on Motorola semiconductor devices is now available. Devices from other manufacturers are covered in broad outline. Four of the books, the index and three volumes of discrete devices, are available at £10.50, while those concerned with emitter-coupled logic, complementary m.o.s. and linear i.c.s are priced at £6. The complete set costs £15. Motorola Ltd, Semiconductor Division, York House, Empire Way, Wembley, Middlesex HA9 0PR.

Plessey have produced an illustrated brochure on its range of resistors of various kinds, including faders, cermet power resistors, potentiometers and trimmers. R.f. chokes are included. Plessey Resistors, Cheney Manor, Swindon, Wilts SN2 2PZ
..... WW408

A complete catalogue of the prolific Foulsham range of books on hobbies and technical subjects, including electronics, is obtainable from Foulsham-Tab Ltd, Yeovil Road, Slough SL1 4JH
..... WW409

A comprehensive listing of all known professional resistors in Western Europe has been compiled by the European Space Agency as an introductory volume in a series covering all components. The lists will be published annually. The Resistance Reference Book is obtainable free from ESRIN/SDS, Electronic Components Databank, Casella Postale 64, I-00044 Frascati (Roma) WW410

Aerialite have sent us the first two leaflets in their new series, which describe and illustrate u.h.f. aerials and a range of coax, plugs and sockets, diplexers and a masthead amplifier. Aerialite Aerials Ltd, Whitegate, Broadway, Chadderton, Oldham, Lancs OL9 9QG
..... WW411

A shortform catalogue is obtainable from AMI Microsystems, which lists current and future projects in the field of microprocessors, memories, communication modules, watch and clock circuits, calculator chips and displays. AMI Microsystems Ltd, 108A Commercial Road, Swindon, Wilts
..... WW412

We have received a data sheet from ITT, which gives constructional and application details on their transformers and coils. It can be obtained from ITT Components Group Europe, Electrical Products Division, Edinburgh Way, Harlow, Essex
..... WW413

British Standard BS 1597 "Radio interference suppression on marine installations" is now revised. Copies are available at £3.50 from BSI Sales Department, 101 Pentonville Road, London N19ND.

A brochure is available on the ELLM earth line and leakage monitor which prevents the connexion of a piece of equipment to the mains via a circuit breaker if a leakage of over 30mA exists or if a sufficiently good earth is not provided. Commercial and Industrial Electrical Services Ltd, 73-75 Shawhill Road, Birmingham B8 3LJ
..... WW414

Correction


In the November issue we stated that Custom Transformers offered only the mechanical components for transformers. This was wrong — a winding service is provided. We apologize for the error. The catalogue is obtainable from Custom Transformers Ltd, Bristol Road, Malmesbury, Wilts SN16 0DU, and covers units from 5 to 1500VA
..... WW415

News of the Month

Dublin, Sheffield receive Indian TV

Broadcasts from the ATS-6 satellite now transmitting educational television programmes over the sub-continent of India (see "A star for India", p.549 December 1975 issue) have been received successfully by workers at University College, Dublin and by Steve Birkill of Sheffield. Special receivers have been built for the frequency modulated 625-line transmissions. The accompanying photograph was taken from the receiver at Dublin and *Wireless World* will be publishing further details of this installation in the next issue. The Sheffield installation consists of a 5ft aluminium mesh paraboloid (pictures were noisier than those received in Dublin where a 20ft diameter parabolic dish was used) with dipole disc feed and transistor head

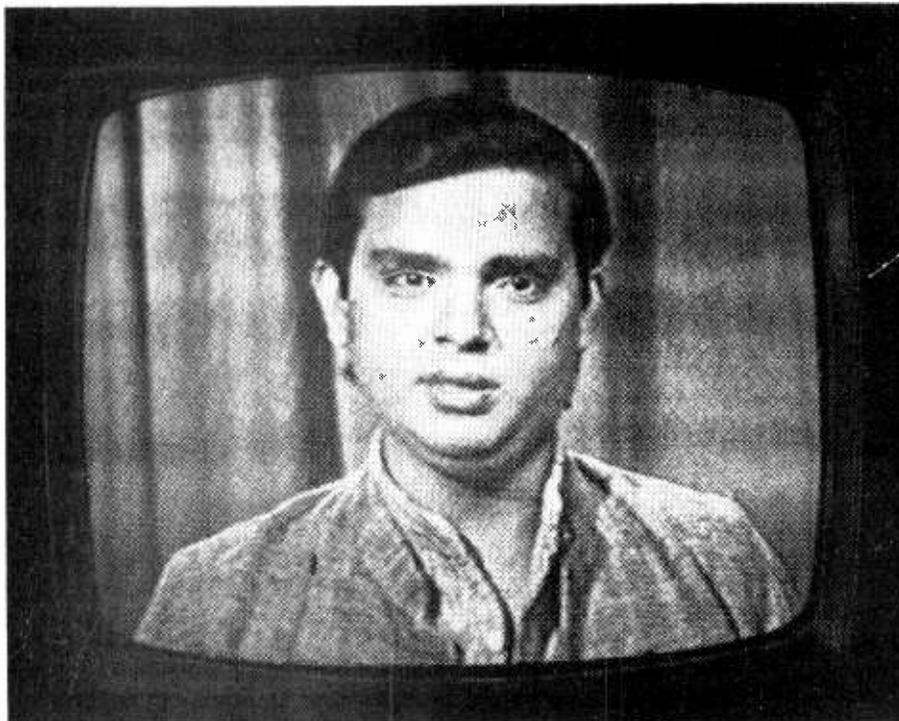Received from the ATS-6 satellite broadcasting educational TV programmes over India, this 625-line picture was photographed in Dublin (see news item).



amplifier, a 5MHz bandpass filter centred on 860MHz, and a standard u.h.f. TV tuner feeding an NE561B integrated phase-lock demodulator at an i.f. of 35MHz. From Britain the geostationary satellite over East Africa appears at about 20° elevation, bearing 135°. Signal strength is reported to be fairly constant with little or no variation from day to day. Polarization appears to be in a vertical plane and constant. It is estimated that from the direction of Sheffield the e.r.p. is approximately 30dB below that of the main lobe.

Audio Fair under new management

A new management team recruited by the Audio Fair's owners, Iliffe Promotions Ltd, will be responsible for the 1976 show, replacing the previous organizers Industrial and Trade Fairs Ltd. The 21st International Audio Festival and Fair will be held at London's Olympia from September 13 to 19, 1976. Improved facilities for trade visitors will include a day and a half reserved for trade only, and the organizers claim that there will be major innovations designed to make the event the best in its history. Backing for the Fair has been confirmed by the IPC Business Press journals *Wireless World*, *Melody Maker*, *Electrical & Radio Trading*, *Black Music* and *Electrical and Electronic Trader*. The new management team includes Cyril Rex-Hassan, Don Quillen and Geoffrey Tomkins, all well known in the running of audio events.

Jersey 'phones computerized

The States of Jersey Telecommunications Board has opened its first computer controlled telephone exchange system at Jersey Central. Initially the equipment will serve 2,500 lines in the island's capital, St. Helier, but to cope with growth in the tourist trade an extension to provide a further 2,500 lines is already in production.

By the use of stored programme control techniques (see July 1974 issue, p.241) the Board will be able to introduce new facilities in the future as and when required, often by quite simple changes in the computer programme and without the need for additional equipment. The system already provides for such facilities as automatic print-out of data for subscribers' accounts and print-out of the calling subscriber's identity on emergency 999 calls. In addition, by dialling a special digit recipients of malicious calls can cause a print-out of the telephone number of the originating caller, and the time and date, to be recorded on a teleprinter located at the exchange. Subscriber controlled call transfer will also be introduced on a limited basis to enable the Board to gauge the demand for such a facility. Subscribers who use this service will be able to have their calls automatically re-routed when they are away from their normal line. A second, similar installation designed by Pye TMC in association with Philips Telecommunicatie Industrie BV is to be brought into service early in the New Year at Jersey West Exchange.

Colour television sent by p.c.m.

After pilot field trials in April 1975, the BBC and Post Office have carried out a successful major field trial at Portsmouth of equipment for digitally multiplexing two colour television and twelve high quality sound signals to form a 120Mbit/s p.c.m. signal. This was transmitted over a new Post Office coaxial cable system (see "High capacity p.c.m. system", February 1975, p.92). Each video channel employed sub-Nyquist sampling at a rate equal to twice the colour subcarrier frequency of the PAL signal (i.e. about 8.9MHz). After quantizing with eight bits per sample, the bit rate was reduced to optionally five or six bits per sample, using a form of differential pulse code modulation. The resultant bit-rate was 53.2Mbit/s.

The multiplex 120Mbit/s input signal was generated in experimental equipment built in the BBC Research Department. It was formed by interleaving two similar 60Mbit/s "pack-

'ages', each consisting of a combination of one digital PAL colour video signal with a nominal bit rate of optionally 44.3 or 53.2Mbit/s and one 2048kbit/s signal for sound channels. The four signals in the 120Mbit/s multiplex were not synchronized, i.e. their precise bit-rates were independent of each other and also of the resultant 120Mbit/s bit-rate. Engineers of the Independent Broadcasting Authority's Experimental Development Department have also completed field trials of digitally encoded 120Mbit/s colour TV over the same route. The IBA's terminal equipment samples the TV waveform at three times the colour sub-carrier frequency, a rate just over 13.3MHz.

No noise is good noise

An agreement signed recently in Montebello, California between DBX Inc and the Teac Corporation will provide for the inclusion in certain Teac tape recorders of the DBX noise reduction system.

DBX will continue to produce their current range of tape noise reduction products for professional and semi-professional accessory use while Teac will incorporate the system within selected models of their tape recorder range and offer it as an optional extra for other models. The Tascam series 80-8 compact 1/2in eight track recorder will be the first to incorporate the system. Teac will shortly offer cassette machines equipped with the DBX type II system recently developed specifically for this format. The inclusion within tape recorders of the 2:1 double ended compression/expansion noise reduction system brings a number of claimed operating improvements, signal-to-noise ratio being increased by approximately 30dB and dynamic range headroom being improved by 10-12dB.

Orkneys in colour

The Independent Broadcasting Authority's new high-power u.h.f. television station on Keelylang Hill, Orkney, the first ITV station built in The Orkneys, began transmissions on December 12. It will provide Grampian Television programmes from Aberdeen on channel 43. The station, about four miles west of Kirkwall, will provide 625-line colour and black-and-white pictures for about 15,000 people in most of the group of islands from Papa Westray and North Ronaldsay in the north to Hoy and South Ronaldsay in the south. There will be a few places in The Orkneys screened by local hills where reception is unlikely to be satisfactory. To receive Keelylang Hill, viewers should use Group B aerials with the aerial rods horizontal, carefully positioned and directed towards



Multicurrency electronic bidding system shown in operation at Goff's new Bloodstock Sales Complex at Kill, near Dublin. The system was designed by CTH Electronics.

the transmitter. These aerials should prove equally suitable for the reception of BBC transmissions from this station.

Expansion in electronics forecast

The major European electronics markets are expected to expand in 1976 after two years of low growth, although 1973 output levels are unlikely to be repeated before 1977, according to the Mackintosh Electronics Yearbook 1975/76. In its analysis of the west European electronics industry, the yearbook forecasts a 50% growth from 1975 to 1979. General growth rates forecast are: Spain 5-6%; Norway 5.5%; France 4.5%; Belgium 3-4%; Austria and West Germany 4%. At the bottom of the scale are Switzerland and the UK at 1%; Sweden 1.3% and Finland 2%. In the UK a gradual recovery is expected from the 25% fall in the consumer sector during 1975. Telecommunications output has been reduced but the industrial and communications areas could benefit from North Sea oil investment and higher overseas demand in 1976, which in turn should lead to an upturn in the components market.

Microwave c.a.t.v. begins

A cable television network receiving signals by microwave from a Swiss mountain is bringing clear pictures of foreign TV programmes to 35,000 Swiss families for the first time. The Weissenstein c.a.t.v. network, named after the 4,000ft Swiss mountain on which the station is built, is the forerunner of similar systems being developed

throughout Europe. In Belgium, a system at Kontrijk will serve a wide area of West Flanders. Special interest is also being shown in Sweden, Denmark, Finland, Austria and the Netherlands, which have the same type of problem as Switzerland.

The microwave system has been introduced into Switzerland by Theta-Com, a subsidiary of the Hughes Aircraft Company. The advantage of using microwaves is that relatively long distances can be covered and natural barriers overcome without laying cables.

BBC equipment designs

New equipment designs by the BBC are being offered for commercial exploitation. Latest developments include a u.h.f. amplifier design for use as a low-power transposer or for transmitter driving (type AM14/550) with intermodulation products at -60dB; an a.m. crystal-controlled monitor receiver, RC3/10, for medium- and long-wave bands incorporating a d.s.b. synchronous demodulator (i.f. and image rejection < 80dB); an m.f./v.h.f. diplexer; and a directional aerial covering medium- and long-wave bands.

WW noise reducer

As a result of the success of the *Wireless World* Dolby B noise reducer project, our suppliers have successfully applied for a Dolby licence. Components and kits are now available directly from Integrex Ltd (see advertisement) and not from our General Sales Department.

New forms of waveguide

Novel structures for guiding waves offer a three-times improvement over conventional guides, measured on an attenuation x sectional area basis

by H. M. Barlow, Ph.D., D.Sc., Fel.I.E.E.E., F.I.Mech.E., F.I.E.R.E., F.I.E.E., F.R.S. and M. Nouri, Ph.D., both of University College, London

For many years electrical engineers have dealt with transmission lines and cables in terms of transverse electro-magnetic (t.e.m.) wave propagation. The approach has developed logically and consistently from low-frequency circuit concepts, starting with lumped resistance, inductance and capacitance elements, progressively translated to distributed parameters of the same kind as frequency rises. In the process consideration has been given to the need for components of electric field in the direction of propagation, but we have continued to describe the wave concerned as t.e.m. although in truth it cannot strictly maintain that configuration. The fact is that in practical arrangements using good conductors to carry the longitudinal current at frequencies up to the v.h.f. part of the spectrum, any departure from a pure t.e.m. field has always been minimal and represented, at most, a perturbation easily provided for within the treatment.

Closer examination of the situation, however, identifies a form of surface-wave, sometimes of only slight significance, associated with each surface acting as a field boundary. Thus the familiar t.e.m. wave so-called in a

coaxial cable can be depicted, perhaps with some exaggeration of axial electric field, as shown in Fig. 1 (b) and it can conveniently be described as embracing a dual surface-wave of circularly symmetrical variety. Metal surfaces coated with a thin layer of dielectric of higher permittivity than the surrounding medium exhibit enhanced reactance at high frequency and this accentuates the axial component of electric field, leading to a larger content of surface-wave within the total field.

One can also think of a coaxial line in which the outer surface has been removed to an infinite radius, operating in effect as a single-wire transmission line with a circularly symmetrical surface-wave of the Goubau type on the outside, progressively decaying in amplitude with distance from the surface. Fig. 1 (a). When the coaxial metal outer is brought to a finite radius to form a cable, a counterpart field is set up on its inside, satisfying the boundary conditions and forming the dual surface-wave configuration, Fig. 1 (b).

It should be borne in mind that surface-waves propagate freely at any frequency; they are slow-waves not subject to cut-off. This is always a feature of waves that are evanescent in

the transverse plane. Cut-off behaviour only arises when waves are reflected backwards and forwards across the guide, as part of the mechanism of forward travel.

Dipole-mode propagation

It happens that in a coaxial line, too small to accept waveguide modes susceptible to frequency cut-off, the usual circularly symmetrical field is not the only one possible. A field of dipole configuration can also exist when the surface impedances are anisotropic, that is to say when they are resistive and inductive to axial current while being resistive and capacitive to circumferential current. This dipole-mode is also a surface-wave and it is best known in its simplest form when propagating along the outside of an isolated dielectric rod, Fig. 2 (a). Such a guide presents to the field concerned an anisotropic surface-impedance of the kind described, but since there is only one surface at finite radius the field extends outside it to infinity, but decaying quite rapidly.

As in the case of the circularly symmetrical wave, a second surface placed coaxially can be made to satisfy the boundary conditions. An anisotro-

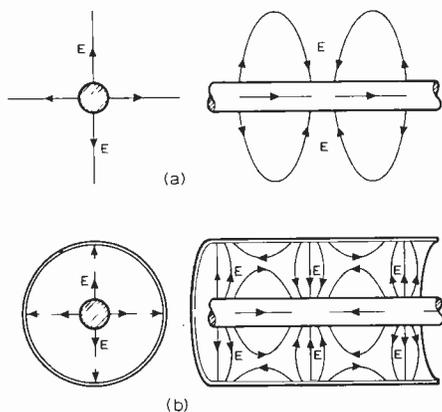


Fig. 1 Circularly symmetrical E_0 waves (a) E_0 surface-wave supported by a single conductor isolated in space. This is a slow-wave. (b) E_0 wave between coaxial metal surfaces. This is also a slow-wave and can be regarded as a form of dual surface-wave.

Comparison between performance of different waveguides operating at 3GHz.

Type of waveguide	Cross-section shown in relative sizes	Electrical features	Relative areas of cross-section	Relative Attenuation	Attenuation multiplied by cross-section
Rectangular half-dipole-mode waveguide		Wide-band Slow wave	1.0	1.0	1.0
Rectangular S-band waveguide Dominant H_{01} mode		Narrow band. Fast wave	24.5	0.14	3.42
Rigid coaxial line. Circularly symmetrical mode		Wide-band Slow wave	3.2	1.0	3.2



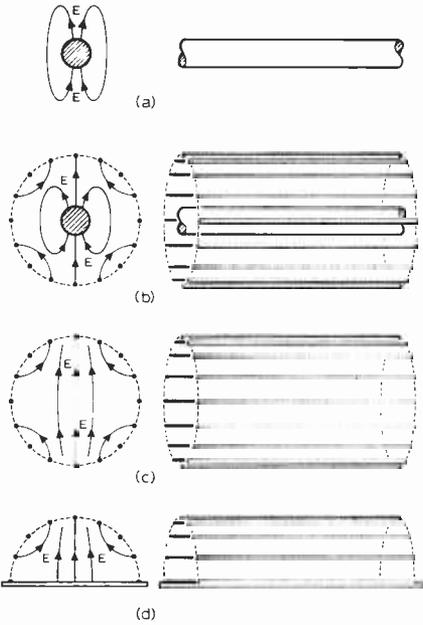
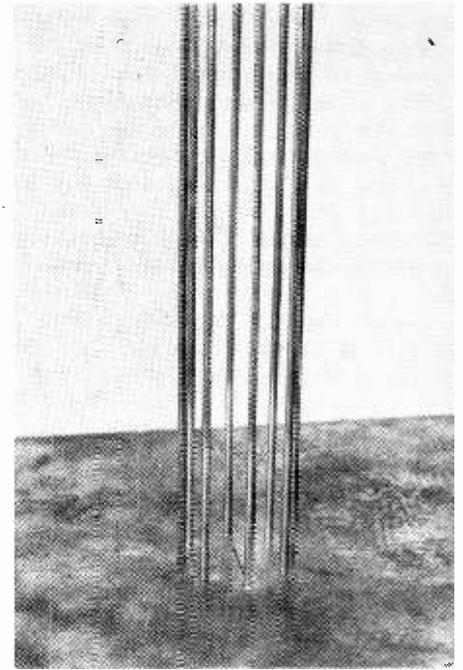



Fig. 2. Cylindrical forms of dipole-mode transmission line (a) Dipole-mode supported by a dielectric rod isolated in space. This is a surface-wave and the dielectric rod exhibits an anisotropic surface impedance. (b) Dual dipole-mode between coaxial surfaces, the inner comprising a dielectric rod and the outer a wire grid of cylindrical form. (c) Dipole-mode within an empty circular-section guide comprising a wire grid. (d) Half dipole-mode in hollow semi-cylindrical guide comprising a wire grid.

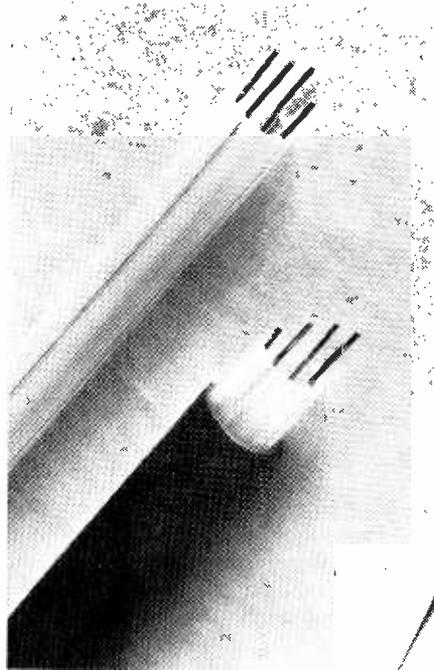

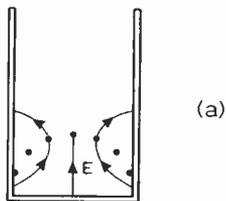
Dipole-mode multiwire waveguide of the circular kind (top) and of the rectangular kind (bottom).





(a)

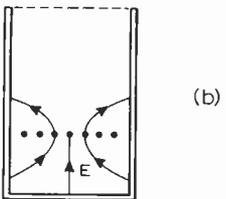

(b)

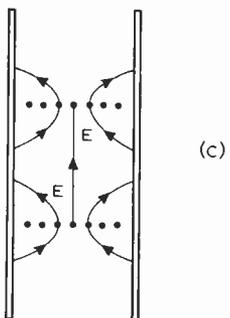

(c)

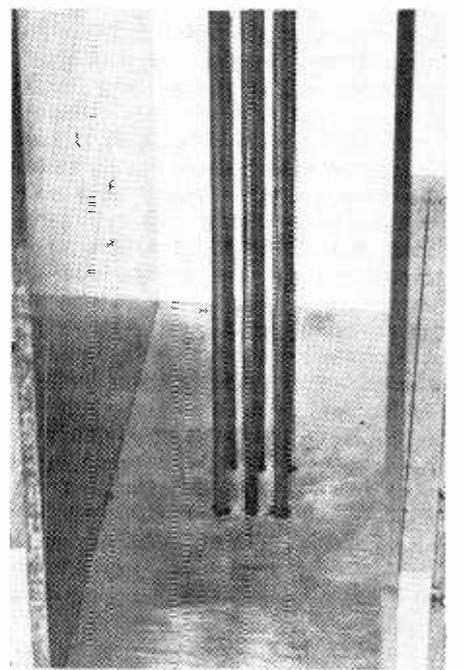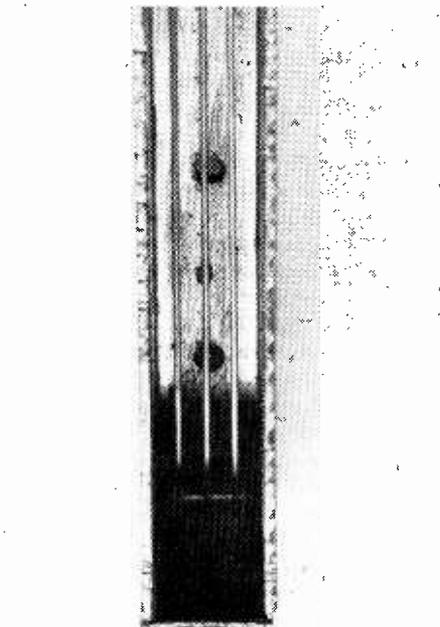

pic surface-impedance, similar to that of the dielectric rod, is required and this can be conveniently provided by a cylindrical grid of wires running parallel along the length, Fig. 2(b). A counter-

part dipole field is then established on the inside of the outer surface to form a dual dipole wave.

Having provided for such a wave in this structure, it is apparent that the inner dielectric rod may be removed to leave a hollow cylindrical guide of wire-grid formation supporting a dipole-type field on its inside, Fig. 2 (c). Incidentally, the inner of a coaxial line supporting a circularly symmetrical surface-wave cannot be removed without destroying the whole wave mode.

In the illustrations the field distributions for the dipole-mode are shown pictorially; no attempt is made to include axial components of field which also exist.

The hollow cylindrical structure

Fig. 3. Half and full-dipole waves in rectangular guide. (a) Half dipole-mode within a rectangular metal channel closed by a semi-circular wire-grid surface. Here parallel metal walls are added to the guide shown in Fig. 2 (d). (b) Half dipole-mode within a rectangular metal channel closed by a plane wire-grid surface. (c) Full dipole-mode in rectangular guide with two plane wire-grid surfaces.

supports a dipole field symmetrical about a diameter at right-angles to the direction of polarisation and consequently the image-line technique can be used, comprising the introduction of a metal plate normal to the electric field so as to give a half dipole-mode, Fig. 2 (d).

The evanescence of the field can then be accentuated by placing two parallel metal plates one on each side of the semi-cylindrical surface and perpendicular to the ground plane, Fig. 3 (a). A simple adjustment is to make the wire grid flat and thus provide for the half dipole-mode in a rectangular guide, Fig. 3 (b). The open side of the guide can be closed in most cases by a metal surface, because the field outside the grid is very highly evanescent and has no significant value at the opening.

The corresponding full dipole-mode in rectangular guide requires two grids, as shown in Fig. 3 (c).

Practical applications

A number of different waveguide structures capable of supporting variants of the dipole-mode of propagation have been constructed and measurements are in progress on their attenuation and phase-change characteristics. There are many variables in the design of these waveguides and efforts are being made to optimize performance in a practical structure, hopefully leading to significantly reduced losses and smaller dispersion when compared with conventional transmission lines.

Valuable features of dipole-mode propagation are that the wave is not subject to frequency cut-off and there is a distinct prospect of making better use of the cross-sectional area of the guide by achieving a more uniform energy-density over it. Preliminary results at 3GHz taking as a basis of comparison the product (*attenuation*) (*sectional area*) are most encouraging and the table shows that dipole-mode rectangular guide is, on this basis, about three times better than both the corresponding conventional rectangular guide and coaxial line.

Apart from the application of dipole-mode lines to a wide range of transmission circuits, there could be development as a leaky-waveguide for communications in tunnels or for coupling to moving vehicles on a railway track.

It is still early days in the development of this novel form of wave transmission but sufficient work has been done to establish firm belief in its future.

It seems that so-called t.e.m. propagation applied at high frequencies without too much regard for the precise nature of the field associated with a given practical structure, has very definite limitations and the time has come to apply more finesse in the approach to some of our problems. By this means new avenues of engineering development are likely to appear on the horizon.

Microcomputer development system

Programme proving and fault finding

The design and development of microprocessor-based equipment usually follows a fairly standard pattern. Once a microprocessor has been chosen, and the proposed system has been planned in some detail, hardware and software development will proceed separately. The programmer will employ what is called a development system, such as the Intellec from Intel or the Exorciser from Motorola, to develop, correct and run his programmes.

Development systems such as these provide the programmer with a good deal of assistance in that they contain "firmware"* designed to speed the operation. For example, they allow the programmer to insert a software "break-point". This means the microprocessor will stop programme execution when the break-point is reached so that the programmer can examine and analyse the state of the various registers within the system at the break-point. This is the equivalent to dividing a complex circuit into smaller units for fault diagnosis by isolating all but the section of interest.

At some stage in the proceedings the user's hardware and software will be combined and comprehensive system tests will be carried out. Fault finding can be difficult, as either the hardware or the software may be responsible for malfunctions.

To alleviate this problem, Intel have introduced a microprocessor development system which they call MDS. This is used in conjunction with a unit called ICE (in-circuit emulator) to provide a flexible microprocessor development and fault finding tool.

In its basic form, MDS comprises a complete 8080 eight-bit microprocessor system with 16kbytes of random-access memory (r.a.m.), 2kbytes of read-only memory (r.o.m.) which holds various programmes for system control and monitoring, 256 bytes of erasable, programmable, read-only memory (e.p.r.o.m.) and interface circuits for a teletype, video display unit, line printer, high-speed tape reader, high-speed tape punch and a universal e.p.r.o.m. programmer.

With an MDS and ICE combination, the hardware and software engineers are able to come together earlier in the

development cycle. The c.p.u. chip is unplugged from the user's prototype microprocessor system and the ICE unit, which is connected to the MDS, is plugged in in its place. This configuration allows components and software in the MDS unit to be substituted for components and software in the user's system.

For example, if the system being developed is a machine tool, the user's circuit card is coupled, through its interfaces, to the machine tool and the MDS and ICE units are connected as described above. Initially, the machine tool control programme will be loaded in the MDS and the microprocessor within the MDS will control the machine tool via the interfaces in the user's system. If there is a programme fault, the full facilities of the MDS are available to "de-bug" the programme in real time. Hardware break-points can be set. If, for example, the machine tool performs a faulty operation, a signal from the tool can be picked up and can be used to halt programme execution when the fault occurs. The programmer can then instruct the MDS to print out all the changes which occurred during the 44 steps which were executed just before the fault occurred, so that the sequence of events that led up to the faulty action can be studied.

Stage-by-stage control of the machine tool can be passed from the MDS to the user's system and, section by section, the correct operation of the user's system can be verified.

At the end of this process, the MDS and ICE units will only be performing the task of the c.p.u. chip in the user's system. The ICE unit is then unplugged, the c.p.u. is replaced and the user's system is ready to go into production. At this stage the MDS/ICE combination takes on a different role. It can be taken to the end of the production line and used for final system testing and trouble shooting.

Most of the peripheral units for the MDS mentioned earlier are supplied by Intel. The basic MDS can be expanded by plugging in extra cards to provide extra input/output ports and up to 64kbytes of memory.

*Firmware. A programme that is permanently stored in a read-only memory.

Letters to the Editor

AUDIO AMPLIFIER LOAD SPECIFICATION

Like Mr Stuart, I go along with the principle of Mr Walker's proposal in the December issue but would like to reconsider the load values. Consider a simple case — that of a single-unit loudspeaker. This will have a rated impedance, R , stated by the manufacturer and subject to a manufacturing tolerance. Part of this will be due to variations in voice-coil resistance and part due to motional impedance effects which show up as a shallow minimum in the impedance curve, usually at around 400Hz. At low and high frequencies the reactive component will dominate and the impedance will be much higher than the rated value, falling to the d.c. resistance as zero frequency is approached.

The worst-case condition from the point of view in question, that of spurious operation of protection circuits, will be around that minimum of the impedance curve. Here Mr Stuart's $jXR / (R + jX)$ is a somewhat severe but fairly reasonable value.

The famous DIN 45500 gives a lower limit for the magnitude of the impedance of a domestic hi-fi loudspeaker of 0.8 times the rated value (although it is delightfully coy about the phase angle), and this applies to multi-way systems with dividing networks as well as to single units. It seems reasonable that monitor loudspeakers should be able to meet this standard (in the form $1.13 jXR / (R + jX)$, that is) as well. After all, the BBC designs show very little impedance variation over the whole frequency range.

On examining typical loudspeaker impedance curves there seems to be little justification, however, for $R/2$, still less for Mr Stuart's $jXR / (R + jX)$ for values of X between 0 and R , and the demands made on heat sinks and power supply are considerably increased. An amplifier designed to drive the former load will, in fact, be capable of delivering twice its rated output power, which appears ultra-conservative. (For the latter case, no overload protection

would seem possible.) Be sure that foreign competitors will not de-rate their products in that way — and it is likely to be economically better to improve the loudspeaker impedance curve anyway.

As to Mr Stuart's final query, the process is already under way. This subject is on the agenda to be discussed by Working Group 10 of IEC SC29B at Gaithersburg, USA, in March 1976. Opinions expressed through the columns of *WW* will be available to the members of WG10 by that time (or before, if they subscribe!). Furthermore, members of the Audio Engineering Society, British Section, will soon be advised of a new venture by which proposals like that of Mr Walker can reach, more quickly, a wide audience of informed opinion and progress to adoption as effective standards quite quickly.

J. M. Woodgate,
Hastings,
Sussex.

Peter Walker raises a very valid point in his reference to the reactive loading of amplifiers (December issue). We have tried to subject our amplifiers to such loads but have found difficulty in defining a "standard load". Our first attempt was to use an R50 crossover network (four section circuit) loaded by resistors. This load did not seem to be difficult enough. We then tried a Spendor BC3, perhaps the most difficult load currently on sale. The Spendor couldn't handle steady tones without (quite naturally) burning out. We were faced with designing an equivalent circuit of the BC3. We have not to date been successful.

To illustrate the problem we compared a P40 amplifier (well respected in its day) with a Classic Two amplifier. The amplifiers were alternatively loaded with an 8 ohm non-inductive load and an R50 loudspeaker. With the gains set for 10 watts into 8 ohms the results were:

	P40	
	8 ohms	R50
400Hz	0.035%	0.13%
1kHz	0.016%	0.062%
10kHz	0.022%	0.084%
20kHz	0.047%	0.15%
	Classic Two	
400Hz	0.0018%	0.0034%
1kHz	0.0027%	0.0073%
10kHz	0.0051%	0.015%
20kHz	0.018%	0.017%

The figures were measured on a Sound Technology 1700A analyser. The results achieved using the R50 as a load are as expected from its impedance curve. Equally with the Classic Two there was no disturbance on a 10kHz square wave of 12 volt peak-to-peak amplitude. Thus any measurable effects of the loading are probably only apparent at much

higher levels, by which time the colourations of the speaker mask any amplifier colourations. Yet my ears tell me differently!

Stan Curtis,
Cambridge Audio,
Huntingdon.

I would like to add my voice to that of Mr Walker (December issue) in saying that a power amplifier must have a reasonable capability to drive reactive loads, if it is to truly called a high-fidelity amplifier.

His criteria seem reasonable to me (i.e. $R = \pm jX$), and indeed coincide with the often quoted load of $2\mu F // 8$ ohms at 10 kHz. All too often one sees an oscillogram published in an amplifier review, of the square wave response of an amplifier at 10kHz, which shows very severe slew rate limitation with an $80\text{ohm}/2\mu F$ load, but not without the capacitor.

I have recently been doing a good deal of work on class B amplifiers, and the requirement to deal with reactive loads has been well to the fore in my mind. The result of the work so far bears out Mr Walker's assertion that his criteria are no hardship to the designer.

I am frequently surprised at the relatively complex overload protection applied to amplifiers today, and especially that they often make no attempt to look at the mean rather than the instantaneous current. In my present class B design a simple fast-acting fuse is all that is used and this provides quite adequate protection from overload. I would add that the use of just a fuse means the use of transistors with a good safe operating area, and also the use of adequate heat sinks. To me, however, these two requirements are normal good design practice, which should be followed in any case.

Although the use of fast output transistors would seem to give a better output stage on paper, I have been able to get the necessary high performance I sought using 2N3055 (n-p-n) and 2N2955 (p-n-p) devices in the higher power versions of the amplifier, and owing to the use of a simple fuse the amplifier easily meets Mr Walker's requirements.

L. Nelson-Jones,
Bournemouth.

MICROPROCESSORS

Mr Waddington's article on microprocessors in the December issue stated that writing machine code by hand is not recommended for more than about 20 commands. Being an Open University student who used OPUS, a demonstration 8-bit computer with 128 by 8-bit bytes of memory, I feel that this figure is a little low. I was one of a number of students who wrote programmes for this of 70-80 instructions — limited only

by the memory size and the input/output facilities. I feel confident of being able to write and code programmes up to maybe a few hundred commands. However, one needs a machine on which to try out one's programmes and if this includes an assembler this will save a lot of time. Manufacturers' development systems cost from £2000 with necessary peripherals. The computer I am building will cost around £100. However, I am not denying that to write a complex programme involving many thousands of instructions the only reasonable way is to use a high level language like PL/M. This reduces the number of lines of programme that the programmer has to think about by a factor of ten, Intel claim. However, one has to buy time on a large computer to convert from PL/M to machine code and this will probably be beyond the pockets of amateurs like myself.

J. O. Owen, GW8JZB,
Pendine,
Dyfed.

I cannot agree with D. E. O'N. Waddington ("Microprocessors", December issue) that interpreters are only suitable for very large computers. Interpreters are easy to implement, and may save memory space if the interpreter's code can be designed so that it represents the problem more compactly than the host machine's instruction set. They are useful on computers of all sizes.

At Strathclyde we have an interpreter for a high-level language running in about 1k bytes of memory on an Intel 8080 microprocessor, providing immediate portability of programmes from several other ranges of computers. A student is now implementing a similar interpreter for the Motorola M6800 series of computers — hardly very large machines.

Eric C. Sprigg,
Department of Computer Science,
University of Strathclyde,
Glasgow.

Mr Waddington replies:

While I concede that it is quite feasible to write machine code programmes for more than 20 commands (I have done so myself) I do not recommend it as normal practice. The longer the programme, the more likelihood of error and, as Mr Owen says, it is desirable to have some means of trying out programmes before committing them to r.o.m. or p.r.o.m. Computer simulation provides a very powerful method if you can afford it.

Some figures on the cost of using a Time Sharing computer to assemble and simulate programmes, although very approximate, may be of interest.

The initial cost of obtaining a user account number is £5. The average user would spend at the rate of about £14 per hour although the actual cost would, of course, depend on the skill of the

programmer. The more skilful will spend at a faster rate but for a shorter time so that it would cost less. If you have no access to a teletypewriter, two courses are open: hire one by the month, only worthwhile if there is a lot of programming to be done, or use one at a computer bureau — Time Sharing charge about £5 a day. However, before embarking on such a course it is as well to realise that mistakes are expensive, particularly when simulating programmes. It is very difficult to estimate how much it will cost to debug a programme. My experience so far suggests that one can easily be out by a factor of two or three times!

With regard to interpreters, obviously Mr Sprigg is better qualified to discuss this subject than I, and I bow to his superior knowledge.

"THE CONSULTANTS"

I must congratulate Mr Dwyer on his review of the activities of consultants (November issue), though Raymond Cooke gave us all a devastating introductory blow. He must have met one of the many people who become acoustical consultants by buying a cheap sound level meter and a text book, having spent their previous twenty years repairing air compressors. There are a lot of these around.

Consultants are a private enterprise and they can only continue in practice as long as they are found to be worth their fees. We are clearly successful in this for we currently have over fifty active commissions ranging from the laboratory measurement of the impact insulation of a sample floor covering, through the design of a loudspeaker system to reproduce the level and spatial characteristics of truck noise, to the acoustic design of a quiet steam power station costing around £300 million. Business has never been so active.

The consultant provides the specialist expertise that is required when people meet a problem well outside their own experience. KEF do not need any advice on how to design loudspeakers but I am sure that if Raymond Cooke needed a spectrographic analysis of a loudspeaker magnet material he would find a consultant with the necessary equipment and specialist expertise in that field. He would never consider the alternative solution, spending £35,000 on the equipment and hiring a man to operate it at a salary of £4,000 a year, and then use the equipment and expertise two or three times a year.

Our clients include one of the big four car manufacturers, several other consulting engineers, some government departments and a large number of very well known architectural practices. They continue to bring their electro-acoustical problems to us, many of them having been with us for fifteen years, so

I can safely assume that we are giving good value for the fees we have to charge. KEF experience cannot be typical.

James Moir
James Moir & Associates,
Chipperfield,
Herts.

We found John Dwyer's report on consultants in the November issue to be very fair and objective and were surprised at the response of Mr Faulkner in December Letters.

Unfortunately the rate of progress is such that £10,000 does not buy much equipment. To equip just one of our test benches with: Sound Technology analyzer; Crown IMA analyzer; H-P function generator; H-P a.c. millivoltmeter; H-P oscilloscope; 1% precision loads; and a couple of AVOs sets us back around £4,500. When you start to add up the equipment needed in an R&D lab the figure really starts to climb. And that's just for amplifiers, before we consider f.m. tuners where the real money is.

We have come across consultants who do have their role in evaluating equipment for those (importers?) who do not possess laboratory facilities, but we do not feel they have proved themselves in the field of original product design. We employ a team of development engineers and production engineers in very close contact with our production staff, and despite this we have made mistakes in putting a product into production. Many competent engineers can design a good amplifier, but can they guarantee an outstanding performance on every unit when:

1. Batches of components come from a variety of suppliers with characteristics across the full band of their tolerances.
2. Equipment is made up by different girls with varying degrees of ability.
3. Equipment has to be tested by test engineers lacking the skills and abilities of their R&D counterparts?

When things do go wrong at the production stage it is prohibitively expensive to have a consultant virtually living on site to solve the daily problems.

Consultants do have a role to fulfil as long as they don't get carried away and set themselves up as demigods.

Stan Curtis,
Cambridge Audio,
Huntingdon.

VANISHING COMPONENTS SHOPS

I read with interest Mr Pethers's letter in the November issue. Perhaps it would be fair to show the other side of the counter.

As a small electronic component stockist, I do not wonder that the "big boys" have elected to sell higher value

items such as hi-fi rather than components. The time taken to sell one or two resistors at say £0.10 could well result in 10^3 times this small amount for the same staff serving time.

It is not that I decry small value sales: it is just that no-one can exist with the vanished profit on small components. London rents, rates, insurances, and all the other multiplicity of outgoings which come under the generic term "overheads", have escalated enormously. In reference to staff, perhaps Mr Pethers has not experienced the peculiar situation where, although there are N number unemployed, it is very difficult to find reliable people at non-ransom salary levels.

In many sales areas customers pay a minimum order charge. To make the component area viable it is getting to the stage where one cannot afford the trained staff to offer advice to a customer without making a service charge. But would the man in the street accept this? I suspect not. But without some bolstering I fear that London electronic component shops will become even more rare. In the last analysis the customer suffers, because competition provides optimum availability and realistic prices.

Perhaps the tycoons checked returns versus outlay and effort. Perhaps they decided that profits determine the type of goods to be sold. Surely the customer must acknowledge that people work for reward.

The shop assistant quite rightly expects to be paid for his labour. The more successful a business is, the more profit available. This results in more money to pay staff well, to stock in depth, to expand ranges, to explore other areas of activity, and thus to offer a better service to the customer.

Try using the smaller shops which cannot afford High Street positions. Telephone enquiries will elucidate "gen" on components. A cheque in the post will provide by-return-service. If a component is not what is expected, a refund follows the return of the goods. Or, possibly, a visit to the edge of the City might prove helpful.

Ron Barrie,
Barrie Electronics Ltd,
London, EC3.

Having had similar experiences I sympathise and am completely in agreement with your correspondent B. W. B. Pethers (November Letters).

Since the age of twelve, when the BBC was but one year old, I have been buying components for home construction. I, too, shopped in the recognised "component areas" of London for some fifty years, which enabled me to enjoy the creative work in making many receivers and transmitters, but today this is no longer possible. Briefly, two recent experiences: I needed a 500pF twin variable capacitor and tried Lisle Street: "Blimey, you're a bit behind aren't you, we haven't stocked anything

like that for more than five years." More recently I needed a few 2.7-ohm 1-watt carbon resistors, but more than a dozen shops in London were unable to supply. I did, however, as your reader mentioned, obtain them from the north — Durham.

Now in all fairness to these shopkeepers — who only seem to be interested in hi-fi, record and cassette players — I do think the fashion has changed and there are not nearly so many of us who like making things. Perhaps radio has become too complex to be as popular as it was originally?

Henry Hatch G2CBB,
South Croydon,
Surrey.

TRANSMITTER POWER AMPLIFIER DESIGN

I read with interest Mr O'Reilly's opening article in his series on Transmitter Power Amplifier Design in the September issue. There is one point in it where I feel the record needs setting straight. In the final paragraph he talks about the various methods of combining low power transistors to form higher power amplifiers, and whilst I do not quarrel with his technical arguments, I do disagree with his assertion that "Little success has been obtained by simply paralleling devices . . ."

I disagree with this statement on three counts. Firstly, Redifon Telecommunications Ltd, one of the leading companies currently manufacturing linear h.f. power amplifiers, make a range of medium to high power amplifiers from 100W to 1kW using the paralleling technique, which have designed-in protection against the failure modes mentioned in Mr O'Reilly's article. These amplifiers have been sold to a wide variety of professional users throughout the world as well as in the UK, and I think that amplifiers using this technique can justly claim a good share of the present market.

Secondly, in the early years of solid state amplifier design, devices available to the designer were of considerably lower power than those of today. Hybrid combining of such devices into power amplifiers would have involved multistage hybrid combiners which would not only have been more expensive but would also increase power losses due to the large number of hybrids and their dummy loads. Power amplifiers were therefore produced using the direct paralleling technique and proved commercially successful. It is this success, I believe, that gave added impetus to the device manufacturers to undertake the costly development of the higher power devices available today.

Thirdly, the chip construction of these high power transistors in most

cases uses the overlay or interdigitated technique, which in effect consists of a very large number of lower power transistors connected in parallel, usually with some form of emitter ballasting to overcome the major problem of paralleling, namely gain equalisation.

The technical arguments for and against paralleling and hybrids combining of power transistors will continue, but I think the record shows that there has indeed been some considerable success achieved by using the direct paralleling technique for combining power transistors in h.f. linear power amplifiers.

C. R. Mitchell,
Redifon Telecommunications Ltd,
London, SW18.

Mr O'Reilly replies:

While not wishing to challenge the historic data Mr Mitchell provides, I would point out that my assertion that parallel connection is rarely the optimum method of combining relates to the present time (as was stated in my sentence preceding the one in question).

Early designs of 1kW amplifier contained many dozens of power transistors in the output stage and so the cost of hybrid combining would have been prohibitive. Direct parallel connection was achieved with some safety only by suitably de-rating the "average" device to ensure safe operation of the highest gain ones. There are obvious problems of cost and perhaps spares provisioning. Transistor gain selection can help load sharing in such circuits.

The major difference between many individual low power transistors and a modern r.f. power transistor is that in the latter the individual devices are manufactured simultaneously and have nearly identical characteristics. Thus with minimal internal ballasting very good power sharing is achieved.

Nowadays 1kW can be obtained from just four push-pull modules and the advantages of hybrid combining are obtainable at little expense. In choosing a circuit configuration the designer must weigh the cost of additional protection circuitry and additional output devices, to permit greater average de-rating, against the cost of a combiner. The cost of failure should also be borne in mind.

RAILWAY FAIL-SAFE

I would like to reply to Mr Cockerell's letter in the December issue on the fail-safe timing circuit shown in Mr Anderton's article on railway electronics (August 1975 issue).

The safety of a system employing such a circuit depends on the time delay remaining longer than a given value. If, as Mr Cockerell suggests, the square wave generator were to fail, there

would never be an output from the circuit, and while this represents a failure, it is a safe failure.

The physical design of such a circuit employs screening techniques for the timing components, whereby all leakage currents would be to the 0V rail, giving rise to an increase in delay time. Should these screens become disconnected, no output will result.

The purpose of publishing this circuit was to illustrate the basic principle of the fail-safe design, which is the sequential charging of the timing capacitor, wherein the capacitor is used to perform two functions, i.e., timing and transferring the signal to the output stage.

E. Mooney,
M. L. Engineering (Plymouth) Ltd,
Plymouth.

PHASE EFFECTS IN LOUDSPEAKERS

It is easier to destroy than to create and I feel it must be a matter of regret that such a respected organisation as the BBC should have lent its name to the article which appeared in the January 1976 issue of your journal ("Audibility of phase effects in loudspeakers", pp 30-32) expressing, as it did, contempt and indifference for the research efforts of manufacturers who have designed and are producing linear phase loudspeaker systems.

I am managing director and head a research team at B & W Loudspeakers, who in October 1975 released a new three-unit dynamic loudspeaker system — DM6 — which has a transient performance comparable with the best full range electrostatic design and a substantially linear phase response. The design programme, spread over a period of two and a half years, involved enormous personal effort from our five design engineers, has resulted in the development of new measuring techniques, the use of new materials and the production of the first British linear phase loudspeaker system.

A complete argument for phase linearity in loudspeaker design is too lengthy a subject to be dealt with by correspondence and is one on which we hope to publish a paper later this year. However, in view of the implication of gimmickry* on the part of manufacturers, I feel some immediate comment is called for.

The article dismisses phase as being quite unimportant, after a simple experiment employing an all-pass phase shift network and the opinion of an unspecified listening panel. It must be presumed that this experiment was carried out on a non linear phase loudspeaker and that the recordings used were made on an analogue tape recorder. If this was the case a little thought would have led the writer to realise that for the experiment to be

even partially meaningful it would have been necessary to employ a linear phase loudspeaker system with digitally recorded material.

To those of us who have spent the major part of their working life on loudspeaker design it became apparent from the early days that the exact physical relationship between the drive units forming a multiway loudspeaker system was of importance. Indeed, if identical components are used both the spherical polar configuration and the sound impression will be changed by different placement of identical units on the baffle configuration. Linear amplitude measurements may be obtained by positioning the microphone to suit the configuration, but the phase characteristic of the system is changed and, being the only variable in the experiment, must account for the differing listening experience.

Both my company and one other British loudspeaker manufacturer have invested considerable sums of money in exploring loudspeaker transient behaviour. Not, as the article appears to suggest, as a gimmick but to advance the frontiers of knowledge and produce a better product. When one is involved in transient evaluation, phase linearisation, quite apart from its inherent advantages, is a basic step forward in good engineering practice, as it will be obvious to your readers that the transfer function of any network may be completely defined by reference to both its amplitude and phase characteristic.

Whilst the mechanism of hearing is a little understood subject it is relatively easy to prove that direct, as opposed to reflected, signals considerably influence the listening experience — hence, apart from other considerations, the importance of maintaining a linear free-field amplitude characteristic. I believe this is a theory to which Mr Harwood subscribes. It is therefore both logical and reasonable to suggest that unless we are to regard music as a steady state phenomenon the leading edge of a transient waveform would be clearly audible as a first arrival signal, the structure of which is determined both by the amplitude and the phase characteristic of the network — in this case the loudspeaker. In any event the subject is well documented and among others Hansen and Madsen, in a paper "Threshold of phase detection by hearing", presented proof that phase changes as small as 10° could be heard and that higher order changes were clearly detectable in normal semi-reverberant listening environments.

May I conclude by briefly commenting on two aspects of the article? First, gimmickry. Over the last two and a half years the research programme necessary to produce the B&W DM6 linear phase loudspeaker has cost, including capital investment in the necessary measuring equipment, some £75,000. Had we been looking for a

gimmick I can assure you that there are plenty to be had at a much lower cost. Lastly, the thought that the BBC Research Department as represented by Mr Harwood will "remain agog with indifference" to the efforts of manufacturers will not, I feel, dismay them unduly. Speaking personally, my own company, which incidentally received the Queen's Award to Industry in 1973 for export achievement, is currently exporting some 80% of its entire output and selling these products in direct competition with all contenders throughout the world. During this current financial year our exports will approach £1M, and I venture to suggest that this success is of more significance than the apparent satisfaction which Mr Harwood derives from his "captive audience" not complaining.

John Bowers,
B&W Loudspeakers,
Worthing, Sussex

* Editor's note: The subtitle "Are 'linear phase' loudspeakers a gimmick?" was an editorial addition.

ELECTRODYNAMICALLY INDUCED E.M.F.

As you have not yet declared this correspondence closed, may I comment on John Gray's further contribution to it in the December 1975 issue? It seems to me a good thing that Faraday, when he performed his classical experiments — in 1831 wasn't it? — was unaware that "relative motion between a conductor and the system within which the conductor e.m.f. is to be detected was a basic requirement for electrodynamic induction of e.m.f. in the conductor" or he might not have tried what he did. Nor could present-day power-station generators be expected to work.

As "electrodynamic" is not defined in the relevant British Standard, 4727, I'm not sure exactly what it means, but presumably it must be relevant to the matter under discussion. Which is more than can be said of Einstein's axiom, cited by Mr Gray. That refers to the impossibility of measuring absolute velocity in a closed system (or at all); but what we have been discussing all this time is the measurement of *relative* velocity with reference to a field in *another* system. It is true that a passenger in a soundproofed lift moving at constant velocity relative to the earth would be unable to tell whether he was moving, up, down, or neither — unless, for example, he had apparatus for comparing the air pressure on a small area of the floor with that on a similar area of the ceiling, thereby establishing an observational link with the system "earth".

Incidentally, on the assumptions made by C. S. Evans in the October issue, I think the e.m.f. should be 200 times smaller than his 26V. "Cathode Ray."

Electronic systems — 2

Background to a communications course

by P. R. Darrington



Communication between people, between machines and between machines and people is at the core of our society. Without communication, life would not be possible; indeed, without the communicating link of the DNA molecule, there would be no life.

In the somewhat more confined area of an electronic systems course, our concern is more specific and the two main subjects of interest are audio and visual communication. Both have arisen because the needs of people far outstrip their capabilities. People need to communicate with each other at a distance, or by "delayed action": information must sometimes be recorded for later use or the communicator requires that his message be modified in some way, perhaps to make it more entertaining.

The language that this kind of discussion is conducted in sometimes obscures the fact that these requirements can give rise to familiar objects. A "recorded, delayed visual communication" is better known as a photograph and "an electromagnetically-transmitted, melodic/visual stimulus" is not easily recognized as Top of the Pops. Such descriptions could be called breakdowns in communication and are fatuous, but can often be seen in print. We will try to avoid them.

Communication between people is at the centre of the subject and can be effected by the use of newspapers, town criers, posters, films, radio, records, tape and television. Our concern is with the last four, as the intention is to use electronics to illustrate systems in action in society, electronics being a prolific user of systems of all kinds.

Aural communication

The easiest way to communicate aurally is to open one's mouth and bellow. However deep-chested the bellow, this method has a limited range and electronics, in the form of radio, is employed to enable the message to travel almost any distance from a few yards to millions of miles. The original sound is carried by the wave-motion of the air — a short-range mechanism. By impressing the low-frequency sound waves via a mechanical-to-electrical transducer onto a high-frequency radio wave, which does not suffer the rapid

attenuation of an airborne wave, the message travels further. At the receiving end of the communication channel, the low-frequency sound is recovered and made audible by another transducer, this time electrical-to-mechanical — the loudspeaker or headphone.


Notice that the radio wave itself was not the message. Each cycle of the original radio wave is identical to any other and, as the probability of one being like the last is maximum and the recipient is aware of this, no information is carried. To reduce this probabili-

ty, the sound wave changes, or modulates, the cycles of the radio wave. The message is then in the differences between cycles. This matter of modulation is crucial.

As in any aspect of communication, control or measurement, the transducers mentioned above are also crucial. They are the boundary between the familiar acts of talking, listening or seeing and the world of electronic activity which cannot be tested by any of our senses. If they are inefficient, as loudspeakers are, we spend too much on driving them and if they distort we lose some of the message.

Stored aural communication (oh, really!) is the domain of the disc or the tape, although one does sometimes wonder if a recording of, say, Vera Lynn singing a World War II song is really communication. If one has heard the record played a hundred times, the

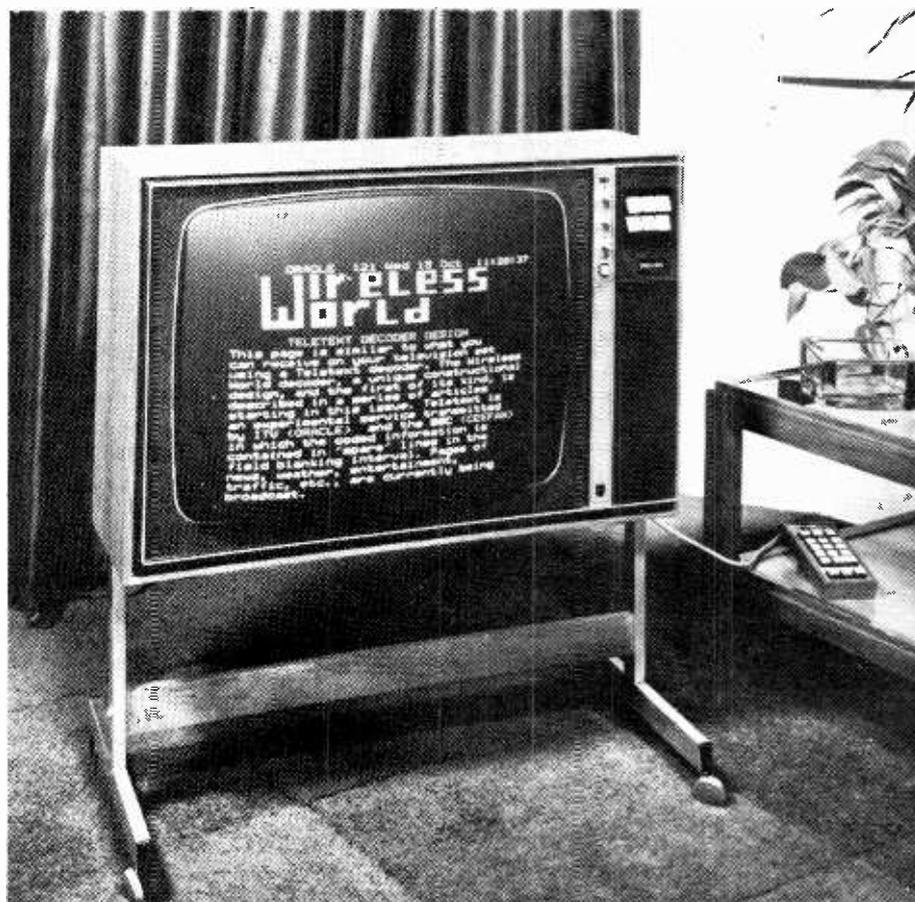A Philips television receiver, adapted to receive and display Teletext information. The system is capable of displaying several hundred "pages" of news and data. Photograph taken by the Independent Broadcasting Authority at their research centre.



probability that, on the 101st playing, it will be different is fairly low. Where, then, is the message? Storage, however, is the aim of the high-fidelity class of equipment. Discs and tape have their pro's and con's, concerned with ease of handling, vulnerability to damage and wear, and physical size. There is also the matter of access time — not, perhaps, as important domestically as in a computer service bureau, but a factor to note, nevertheless. When one is at the wrong end of a C-120 cassette, discs can take on a new appeal.

The problem of noise (defined here as unwanted sound) is a thorny one, particularly with tape. Recording materials, both for discs and tape, are responsible for background noise which is reproduced as though it were part of the original sound. It constitutes an error which, in most cases, is not serious but merely irritating. When information is transmitted digitally, each small piece of information frequently being denoted by the presence or absence of a signal, a noise signal can fake the presence of a legitimate signal and cause a lot of trouble. All information-carrying channels suffer from noise to a greater or lesser degree, but in the domestic, music-playing environment, the tape-recording process is more vulnerable than disc. Hence the appearance of the name of the inventor of a noise-reducing process on many cassettes and cassette recorders — Dolby.

Distortion in the waveshape of a signal is, again, always present, and can be considered a form of noise, because it often consists of added harmonics — unwanted sound. In a telephone system, distortion is not considered very important (unless one is in the habit of dialling a disc) but in a high-quality audio system, a very small amount indeed is unacceptable. Some of this is no doubt due to the peculiar genius of advertising copy-writers (one can listen to a heavily-distorting car radio without suffering) but it seems to be a fact that amounts of distortion which are imperceptible visually on an oscilloscope are easily discerned when listened to.

For many years, the audio amplifier has been subjected to intense examination by circuit designers, with the intention of reducing the amount of distortion contributed by this link in the chain. It is now down to around 0.005% in the top-class units. And yet the other elements in the audio system can contribute much larger amounts — a tape deck up to 2%; a loudspeaker about the same. It is as though a rare wine in a golden goblet were decanted through an old sock and drunk through a mouthful of black pudding.

The virtually distortionless and noiseless reproduction of music from one loudspeaker is not, of course, considered good enough now. In the last two or three decades, stereophonic reproduction has been adopted as standard and surround-sound is almost

upon us (assuming that the manufacturers ever decide which kind to make). Hearing mechanisms and the psychology of hearing are relevant subjects for study in this business of multichannel sound. Surround-sound reproduction is not always intended to give the listener the impression of being in a concert hall, listening to music from the platform. If the music is recorded in a studio and is mainly synthetic, the listener is quite likely to be among the players. The surround-sound effect is being used not to convey the literal truth, but the truth in a modified form.

Visual communication

Electronics come into their own here for remote viewing and storage. Perhaps the most spectacular televisual communication is that between a space capsule and Houston, Texas — communication in a very real sense. In its more mundane sphere, the science is perhaps not quite so communicative; the predictability of a weekly American detective film reduces the information content to a low level.

In industrial applications, a television channel will become part of a feedback loop. It can be used to observe the effect of a control and to display it to the controller, who is thereby protected from a possibly hazardous working area.

The amount of information required to reproduce an acceptable picture is large (between 300000 and 800000 elements). This immediately rules out any idea of transmitting a picture by means of a "one-to-one" photocell/lamp connexion for each element. Such a channel in cable form would be grotesquely expensive in copper and very bulky. This "parallel" method of transmission is therefore abandoned and a "sequential" approach adopted, wherein one channel is modulated with the brightness of each element in turn, by scanning the scene. At the receiver, a similar scan is "in step" with that at the transmitter. The scanning of a picture is used in television at high speeds for real-time viewing or at much lower speeds for facsimile and amateur use (slow-scan television — s.s.t.v.).

Recently, the exploitation of transmitted television signals has been increased by the Teletext experiment, which may become a permanent service. The previously unused sections of a television wave, blanked lines between scans, are now used to carry coded information. The code can be used by a domestic receiver to instruct a local "character generator" to display letters, numbers and graphic characters, forming a page of information on entertainment, news, weather forecasts, news flashes, financial reports and the like.

In the next article, the use of modulation techniques for signal transmission will be discussed.

Announcements

The third residential vacation school on the subject "RF Electrical Measurements" is being organized by the Institution of Electrical Engineers (IEE) and will take place at the University of Lancaster 11-23 July 1976. The school will be of interest to those working in calibration and standards laboratories as well as to research workers who require familiarity with modern measurement methods. The subject will be dealt with at a level appropriate to recent graduates or senior technicians. Further information can be obtained from the IEE, Savoy Place, London WC2P 0BL.

"Electronics for electrical equipment" and "How computers work" are two part-time courses to be held at South London College, Main Building, Knights Hill, London SE27 0TX. The first is an eight-week course held each Tuesday evening from January 26 and the latter is a nine-week course held each Thursday evening from January 29. Further details can be obtained from the Senior Administrative Officer.

Regent Acoustics, Carrington House, 130 Regent Street, London W1R 6BR, has announced that it is now appointed as sole UK distributor for the American direct cut Sheffield records. These records are recorded from the studio directly to the master disc.

Quarndon Electronics, Slack Lane, Derby, best known for their stock holding and distribution of semiconductors from leading manufacturers, have announced the opening of a microprocessor laboratory at their premises in Derby.

Nitron has appointed Peter Gray Electronics Ltd, 21-23 Station Road, Henley on Thames, Oxfordshire as their sole agent to cover customers in the UK and Ireland. Nitron, a division of the McDonnell Douglas Aircraft Corporation, manufacture a range of p- and n-channel m.o.s. microcircuits, including non-volatile memories, calculator chips, data communication circuits and static r.o.m.s.

Marshall's, 42 Cricklewood Broadway, London NW2 3ET, have announced their appointment as a specialist distributor for Mullard Ltd. This distributorship covers the full range of semiconductors, passive components and valves, specifically with reference to the radio, TV and hi-fi areas.

"Linear phase" loudspeakers

It has been brought to our attention that certain phrases in the article "Audibility of phase effects in loudspeakers" by H. D. Harwood in the January 1976 issue may be taken as criticisms of the quality of loudspeakers with "linear phase" characteristics now on the market. We would like to assure readers that in publishing this article we intended no such criticism. The high quality of sound reproduction of these products is not in question. The issue, as we see it, is the extent to which a "linear phase" characteristic contributes to this high quality, and Mr Harwood's article is presented as one viewpoint in the debate on this subject. We shall be glad to consider for publication any responsible articles or letters giving contrary results and conclusions to those of Mr Harwood.

Thanks to Brandenburg's superb products...



We're taking a couple to the Montreal Olympics.

You've heard, perhaps, that nowadays Brandenburg are taking an Olympian view?

We're doing so for two important reasons. Our products. And to support the Olympiad ideal.

First, our products. (Then we'll tell you how to get – all expenses paid – to Montreal).

The Olympic Games began by Mount Olympus – the home of the Gods, and the highest place known to the ancient Greeks. Which is why the word 'Olympian' means superior, magnificent and all manner of other fine things.

Which appeals to us at Brandenburg no end.

For over 21 years the Brandenburg name has been associated with HV power supply technology, and we are now established as Europe's leading manufacturer in this field.

We have an unequalled line-up of products, from our high technology Ensign range to HV modules and meters. All designed to satisfy the most demanding applications. We've just recently released our resin encapsulated 200 Series modules, and there's our second generation Alpha II units reflecting the very latest in high voltage state-of-the-art.

In parallel to our increasing range of power supplies, we've a unique selection of NIM modules and MCAs for nucleonic research from our Nuclear Engineering Division.

These are just some of our winners. In the months and years to come, there'll be more. For Brandenburg, in the truest Olympian tradition, is always reaching to better even today's finest achievements in HV and nucleonic engineering.

From these Olympian heights, we turn to others.

Two competitors will be Brandenburg's guests at a finals day – July 30th – at the 1976 Olympics. But to get there they'll have to work on it. We think the competition we've devised is fun, but it needs thought on your part – which is just as it should be.


So do look overleaf at the details.

Why are Brandenburg so keen on the Olympics? Well, we're British through and through – and we don't think Britain does enough at or for this extraordinarily prestigious event. In our own small way we're going to get our industry just a little more involved.



This is how you can win your tickets, your travel and your expenses to the Montreal Olympics next July. You'll try won't you?

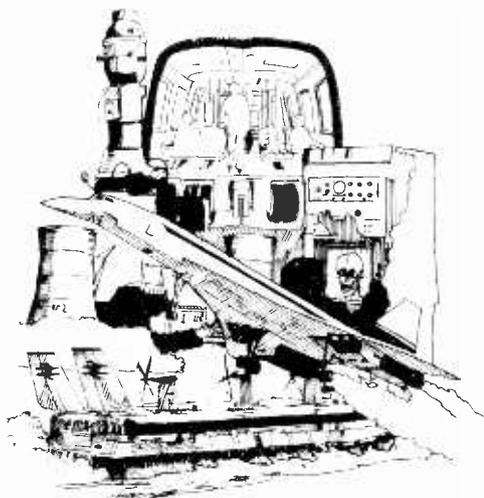Seven modern wonders of Brandenburg's world



First, we want you to list in order of importance these seven major British technological achievements. They are:

- Concorde
- The Hovercraft
- The scanning electron microscope
- The brain and body scanner
- Linear induction motors
- Fast breeder reactors
- Man-made fibres

Using, as they say, your skill and judgement – and, we hope, having discussed the list with your friends and colleagues – put them in order of technological importance. It's as easy as that – or as hard. But at least mathematically, you stand a two in five thousand and forty chance of a first prize.

Our judges will themselves work out what they believe to be the answer. And whoever agrees with their selection is in with a splendid chance.

Our judges are:
Mr. Kim Bachmann of New Electronics; Mr. Rex Grimoldby of Brandenburg; Mr. Brian Jennings of Electronic Engineering; Mr. Stan Mash of Electronic Equipment News; Mr. Stephen Broadbent of Flight International and Mr. Dave Whiffen of Laboratory Weekly.

The opinion of the judges is, of course, final.

2 Look into a crystal ball

Obviously more than two entrants will get the first part of the competition correct. So, to get around this problem, we've got another question for you to answer (in 25 words or less). What technological achievement would you like to see next – and why? Again the judges will decide. And remember, we are taking two winners – so try hard, won't you, as you peer into the crystal ball.




3 In the year of the 21st Olympiad—and our 21st anniversary—21 prizes for “runners-up”

Brandenburg has been in HV engineering for 21 years. So, to celebrate our 'coming of age', we're awarding 21 prizes for 'runners-up'.

They're record books of the Olympiad – which we can't show you because they're not printed until after the Games. But they're magnificent volumes and we know you'll treasure your copy for ever.

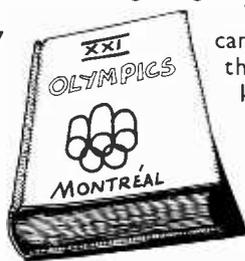Incidentally, all winners and runners-up will be informed by 7th May, 1976 and their names published in the afore-mentioned magazines.



4 How can I enter?

Just use our enquiry number – its 151 – and we'll send you an entry form. It's the only way we'll accept entries.

Brandenburg Limited, 939 London Road, Thornton Heath, Surrey, England. Tel: 01 689 0441 Telex: 946149.

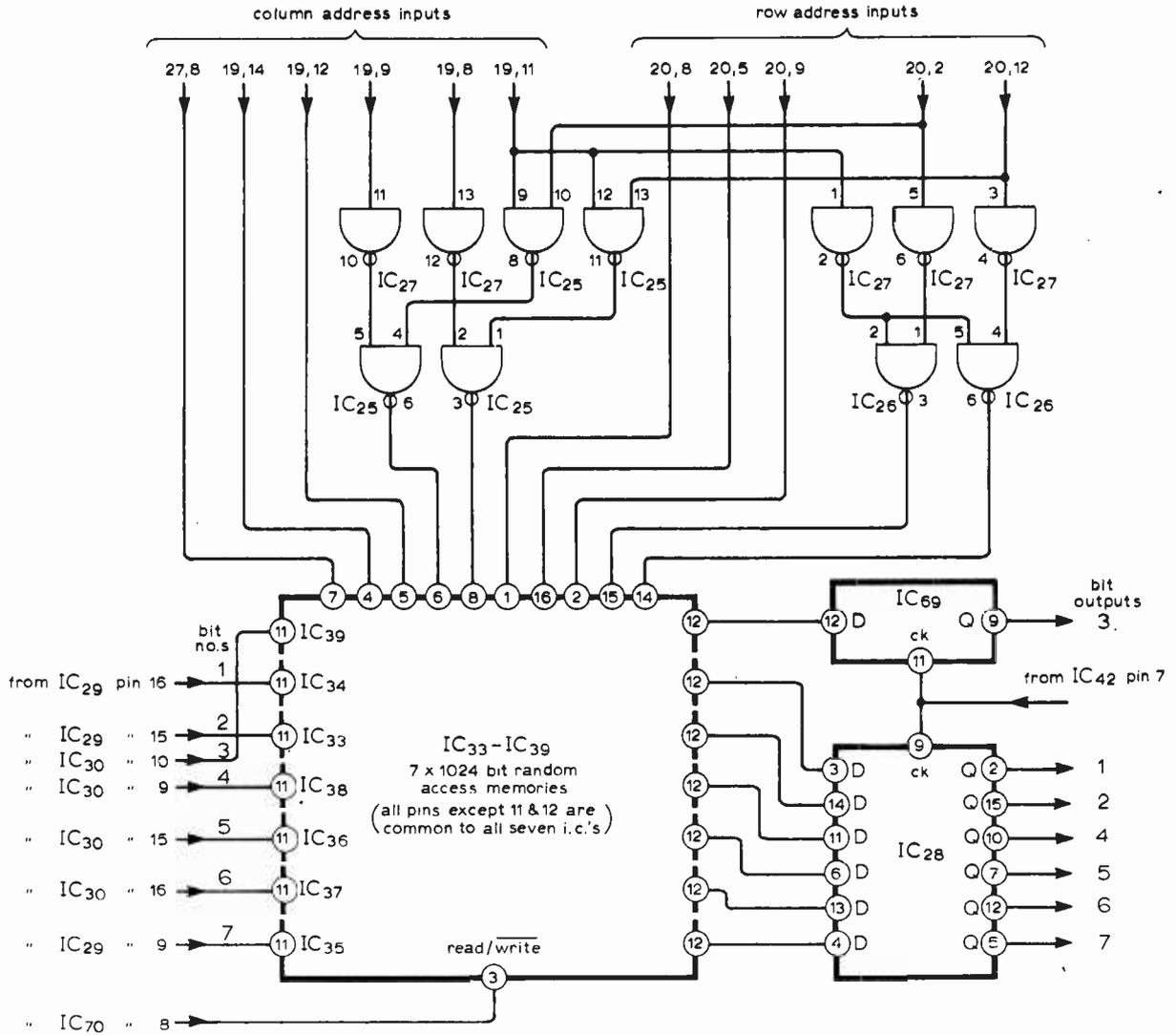


Fig. 4. Circuit diagram of the code converter and data store. IC_{25,26} are 7400, IC₂₇ is 7404, IC₂₈ is a 74174, IC₆₉ is a 7474 and the r.a.m.s are 2602B or 2102B.

detections during separated picture information are avoided. However, lines 16 and 329 carry another form of data, and lines 19, 332 and 20, 333 carry insertion test signals. Despite the precautions already taken it is still possible under some circumstances to detect a framing code at the correct time on one of these lines. It is this type of false detection that can cause lines of complete rubbish to be written into the display, and it is this type of error that is most objectionable. The simplest way of overcoming it in this design is to not look for framing codes on lines 16, 329, 19 & 20, 332 and 333 and this can be easily accomplished by inhibiting the entry of data into the 74164 shift register on these lines. This is achieved by feeding the QB output of IC₅ into the second data input of the shift register (shown dotted in Fig. 1). This solution to the problem has the disadvantage that if the allocation of lines in the vertical interval is changed in the future, a modification to the circuit may be required. For this reason the connexion is not included on the p.c.bs, but may be added by means of a wire link if it is found to be necessary.

A second type of error, which is also quite disturbing but which is due to an

entirely different cause, is apparent in rows which begin correctly with intelligible data, but turn to rubbish at some point across the line. For this to happen, the framing code must have been correctly detected, but somewhere across the line the divide-by-eight counter generating the latch strobe pulses gets out of step with the data bytes, and this causes the information to turn to rubbish. The most likely causes of this are that the clock oscillator is slightly off frequency, or that some particularly severe noise in the data line causes the clock generator to mistrigger.

The third type of error is the row which appears in the wrong position in the display. This probably has the secondary effect that the position it should have occupied in the display will be left blank, thus effectively making two rows of the display incorrect. This type of error is fairly uncommon in

decoders employing Hamming correction, as single errors in the row address will be corrected automatically. Even if an even number of errors are present (2, 4, or 6), the row will still not be written into the wrong position, as even errors can be detected, and in this design they cause the Data Allow waveform to return to "0", preventing any data being written into the store on that row. This means that only errors totalling 3, 5 or 7 bits in the row address group will cause rows to appear in the wrong position on the screen, and this is rather unlikely, except in cases of severe interference (car ignition interference, etc).

The types of error dealt with so far are all very undesirable for the simple reason that they may occur in the display at any time, even if the page is read out correctly the first time, and it is for this reason that the extensive precautions described above are taken to prevent their occurrence. The remaining types of error to be described are less annoying because they are self correcting, i.e., a page may be read out which has errors such as rows or letters missing, but these will be corrected when the selected page is next transmitted in 15-20 seconds time. This is another good reason for having a short

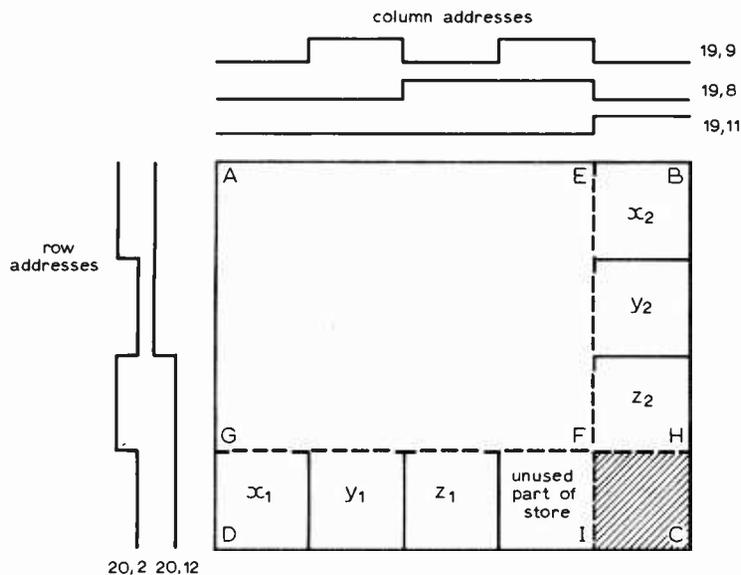


Fig. 5. Diagram showing the operation of the code converter circuit (see text for explanation).

page-access time, since corrections will be made faster.

A blank row in the display may be caused either by an even error detected in the row address group, or by a missed framing code. In either case this type of error cannot cause an already correct page to be made incorrect, and correct information will almost certainly be taken the next time the page is transmitted.

Nothing has yet been said about the parity bit contained in each of the display character groups. This is used in the following way: a parity check is made on each 8-bit data byte before it is written into the store, and if the check is satisfactory the seven bits of the character code are written in the normal manner. If, however, the check shows the parity to be incorrect, nothing is written into the store during that byte. (Anything already in the store at that address location will therefore be unaffected, as only the action of writing removes already-stored information.) This has the effect that when a page is first read out onto the screen, any parity errors will cause characters to be missing from the display. These letters will then be filled in 15 seconds or so later, when the page is next written into the store. Incorrect characters will only be read into the display if more than one error is present in the data word in such a way that the byte-parity is still correct.

This, then, is a brief resumé of the more common types of error that can be encountered in the teletext display, and we will now continue the circuit description by looking at the operation of the Hamming corrector circuit.

Hamming correction

It has already been explained that the Hamming-coded bytes contain four message bits and four parity bits. The use of four parity bits enables four separate parity checks to be carried out

over the byte and in this way it is possible to determine which one, if any, of the bits is incorrect. If one of the message bits is found to be incorrect, then it is simply inverted, and hence corrected. The table in Fig. 2 shows the parity checks that are carried out and the action taken if one or more of the checks fails. The actual circuit, shown in Fig. 3 does not need to be quite as complicated as the table suggests because there is nothing to be gained by correcting the odd numbered bits (parity bits) and in fact only the message bits are corrected.

Gates (32, 6), (24, 11) and (24, 8) indicate parity checks A, B and C respectively as shown in the table, and the results of these checks are fed into the four three-input NAND gates, (16, 12), (16, 8), (8, 12) and (8, 6). The output condition of these gates determines whether or not the bits from the \bar{Q} outputs of the 7475 latches will be inverted or passed through the exclusive-OR gates unchanged. (Normally the \bar{Q} outputs are inverted by these gates, but if an error is detected, the errant bit is passed through unchanged).

The 74180 eight-bit parity checking i.c. performs a dual function in this circuit. Firstly it is used simply as a parity checker for the ISO-7 coded characters, to determine whether they should be written into the store. Secondly, it is used in conjunction with gate (16, 6) to detect even-order errors during the Hamming-coded bytes. The input to gate (8, 8) from IC₇, pin 10 restricts the detection of even-order errors to the row address group only. As explained earlier an even-order error detected at the output of gate (8, 8)

returns the Data Allow waveform to "0", thus preventing the writing of information into the store on that row.

Data store and code converter

The data store consists of seven 1024-bit static random-access memories (r.a.m.s). These are m.o.s. devices, but are extremely easy to use, as they have fully t.t.l.-compatible inputs and outputs and require no external pull-up resistors. The printed-circuit boards are designed in such a way that holders may be used for these i.c.s to reduce the possibility of damage by "leaky" soldering irons etc. The outputs of these i.c.s are only capable of driving one t.t.l. load and must therefore be suitably buffered to obtain the normal t.t.l. fan-out of 10. They also have a somewhat variable access time, which depends on device type, temperature, and the particular 'location' in the store which is being addressed. Although the specification states that the access time will always be less than 1 μ s, it is important in this circuit that the bits are all time coincident at the output of the store, and this is achieved by using t.t.l. D-type latches on the outputs of the r.a.m.s. These D-type latches perform the dual function of providing bit outputs that are time-coincident and with a full fan-out of 10 t.t.l. loads.

The read/write input of the store is normally at the "1" level during the display of data on the screen. When new information is written into the store,

To help readers to buy components, we print here a list of i.c.s used in the decoder. The full parts list will follow later. IC_{85,90} are required for a two-r.o.m. character generator, also described later.

1 7493	31 7486	61 7412
2 7408	32 7486	62 7410
3 74121	33 2602B	63 7404
4 7428	34 2602B	64 7474
5 7490	35 2602B	65 -
6 7404	36 2602B	66 7404
7 7404	37 2602B	67 7404
8 7410	38 2602B	68 -
9 74H10	39 2602B	69 7474
10 7493	40 74180	70 7410
11 7474	41 7402	71 7400
12 7427	42 7442	72 7474
13 7400	43 7402	73 2513 (u.c.)
14 7493	44 7410	74 7403
15 7400	45 7420	75 7403
16 7410	46 7402	76 -
17 74121	47 7442	77 -
18 7400	48 7442	78 7474
19 7493	49 7400	79 7474
20 74177	50 7400	80 7474
21 74177	51 7474	81 75107
22 74H04	52 7474	82 7403
23 7430	53 7474	83 7400
24 7486	54 7402	84 7410
25 7400	55 7474	85 2513 (l.c.)
26 7400	56 7474	86 7483
27 7404	57 7400	87 7421
28 74174	58 7410	88 7400
29 7475	59 7404	89 7402
30 7475	60 7412	90 7403

this input is pulsed to the "0" level for each newly stored character code.

The address inputs to the r.a.ms are obtained from the column and row address dividers. As there are six column-address and five row-address outputs, and only ten address inputs to the r.a.ms, a code-converter circuit is needed to reduce the address word from eleven to ten bits. The method of doing this was briefly described in an earlier article, but with the help of Fig. 5, both the necessity for having a code converter and the method of achieving the conversion should become apparent. For simplicity the diagram only shows the addresses actually involved in the code conversion circuit, and not all the row and column addresses.

The area enclosed by ABHG is the area covered by the teletext display, i.e., 40 characters by 24 rows, and the area AEID is the 32 by 32 matrix of the random-access memory store. It can be seen fairly easily from this that if no code converter were used it would only be possible to obtain a teletext display of 32 by 24 characters (enclosed by AEFG). However, it is also fairly obvious that the extra space available in the r.a.ms enclosed by GFID is more than enough to store the extra eight character codes for each of the 24 rows. This is indicated in the diagram where the characters displayed in square x_2 are in fact stored in position x_1 in the r.a.ms and similarly y_2 in y_1 and z_2 in z_1 .

The method of achieving this in terms of gates is shown in Fig. 4 and the i.cs used are actually numbers 25, 26 and 27. It would take too long and serve little purpose to describe in detail this part of the circuit operation. Briefly, the circuit detects characters 32-40 on each row and changes the store row address to one of the unused rows between 24 and 31.

There are many ways in which the above code conversion can be performed, but it was considered that the method used was probably the cheapest in terms of i.c. types and it was adopted for this reason.

This completes the description of all the circuitry contained on digital board one, and next month the description will be continued by looking at the majority of board two which includes page and time detection, control logic, graphics and character generation.

Correction

In Fig. 1 of the January issue, IC₁₄ was specified as a 7490. It should be 7493.

Standards

We are informed by the BBC that, from February 2, 1976, the character code shown in our January issue will be broadcast on BBC1. BBC2 will revert to the old standard.

Meetings

FEBRUARY

LONDON

2nd. BKSTS — "Psychoacoustics: microphone techniques and the criteria of hearing" by Michael Gerzon at 19.00 at Thames Television, Studio 7, Euston Road, NW1.

3rd. IEE — "Automatic handwriting and speech recognition systems" by R. Watson and B. Paye at 17.30 at Savoy Pl., WC2.

3rd. IEE — Faraday lecture on "The entertaining electron" by F. H. Steele in the evening at The New London Theatre.

4th. IEE — Faraday lecture on "The entertaining electron" by F. H. Steele, morning, afternoon and evening at The New London Theatre.

4th. I. Phys. — One-day meeting on "Absorption of sound and vibration" at Imperial College, SW7.

4th. IEE — Colloquium on "Antenna systems for frequency re-use" at 14.30 at Savoy Pl., WC2.

4th. BKSTS/RTS/IEE — Symposium on "Large screen television displays" at 16.00 at Studio 1, London Weekend Television, South Bank Television Centre, Upper Ground, SE1.

5th. IEE — Colloquium on "H.F. communication systems" at 10.00 at Savoy Pl., WC2.

5th. IEE — Faraday lecture on "The entertaining electron" by F. H. Steele, morning and evening at The New London Theatre.

6th. IEE — Faraday lecture on "The entertaining electron" by F. H. Steele, morning and afternoon at The New London Theatre.

9th. IEE — "Safety regulations arising from the low-voltage safety document" by J. B. Lievens at 17.30 at Savoy Pl., WC2.

9th. BKSTS — "Studio recording principles" by John Andrews at 19.00 at Thames Television, Studio 7, Euston Road, NW1.

10th. IEE/IEETE — Discussion on "Black boxes and their role in the teaching of semiconductors" at 17.30 at Savoy Pl., WC2.

10th. AES — "Low levels to line" by David Rees at 19.15 at the IEE, Savoy Pl., WC2.

11th. I. Phys./IEE — One-day meeting on "Metallisation systems for semiconductor devices" at Imperial College, SW7.

11th. IEE — Colloquium on "Stroke rehabilitation as a problem in control" at 10.30 at Savoy Pl., WC2.

12th. IEE — "MF broadcasting" by T. Kilvington at 17.30 at Savoy Pl., WC2.

16th. IEE — Colloquium on "Electronics against pollution" at Savoy Pl., WC2.

16th. BKSTS — "Studio techniques" by John Andrews at 19.00 at Thames Television, Studio 7, Euston Road, NW1.

17th. IEE — Colloquium on "Field effect transistor circuits" at 10.30 at Savoy Pl., WC2.

18th. I. Phys. — One-day meeting on "Adhesion of thin films" at 10.30 at Imperial College, SW7.

18th. IEE — Fourteenth annual lecture of the Electronics Division by Prof. C. Cherry at 17.30 at Savoy Pl., WC2.

18th. IEE — "Liquid crystal materials" by Dr G. W. Grey at 17.30 at Savoy Pl., WC2.

23rd. IEE — Discussion on "Reduction of electro-magnetically excited vibration and noise" at 17.30 at Savoy Pl., WC2.

23rd. BKSTS — "Monitoring sound in studio and home" by Spencer Hughes at 19.00 at Thames Television, Studio 7, Euston Road, NW1.

25th. IEE — "Marketing engineering products in 1976" by L. A. Williams at 17.30 at Savoy Pl., WC2.

26th. IEE — Discussion on "Towards a real professionalism" at 14.00 at Savoy Pl., WC2.

BIRMINGHAM

18th. RTS — "Politics and broadcasting" by Peter Hardiman Scott at 19.00 at the BBC, Broadcasting Centre, Pebble Mill Road.

BLANDFORD

18th. IEETE — "Ultrasonics in TV" by J. C. Goodwin at 18.30 at Princess Mary Hall, School of Signals, Blandford Camp.

BOURNEMOUTH

10th. IEETE — "The work of the Independent Broadcasting Authority" by B. T. Hadley at 19.30 at Cotford Hall Hotel, Knyveton Road.

BRIGHTON

19th. IEETE — "Stabilise your a.c. supplies" by Max E. Symes at 19.30 at the Royal Albion Hotel, Old Steine.

CARMARTHEN

11th. IEETE — "Protective multiple earthing" by R. Hubbard at 19.30 at Carmarthen Technical and Agricultural College.

EXETER

5th. IEETE — "Fuel economy — control systems" at 19.30 at the Imperial Hotel, St Davids Hill.

GLASGOW

25th. IEE — Colloquium on "Electronics in the service of medicine" at the University of Strathclyde.

IPSWICH

5th. IEETE — "Hi-fi" by H. J. Dix at 19.30 at Room 1, Ipswich Town Hall.

MORDEN

24th. IEE — "Electronics on Saturday" by K. J. Dean at 18.30 at Merton Technical College, Morden Park, London Road.

REDHILL

5th. IEETE — "Automatic vehicle control — driverless buses and vehicles for the disabled" by J. Feaver and Dr G. Reynolds at 19.30 at Redhill Technical College, Gatton Point.

Tickets are required for some meetings: readers are advised therefore to contact the society concerned.



First Intelsat IV-A launched


The first in the series of Intelsat IV-A commercial communication satellites, capable of carrying 6,000 telephone calls and two television channels at once, was launched from Cape Canaveral, Florida on September 25, 1975. The satellite's capacity is almost twice that of each of the present communications satellites now in service. It is the first of six to be launched over the next few years.

The satellite carries 20 transponders, compared with 12 on each Intelsat IV, and a new antenna system that can concentrate several signal beams on to high traffic areas on each side of the Atlantic. Eighty-five per cent of all Intelsat use is for telephone transmission.

Using a technique of frequency re-use, the satellite will cast separate transmitting and receiving beams that will take in most of the Americas and Canada as well as Europe and Africa from its operating position in synchronous earth orbit 22,300 miles above the equator. The satellite is provided by Intelsat, the International Telecommunications Satellite Organisation, which was set up in 1964 to exploit satellites for commercial communications on a global scale. Britain is the second largest shareholder in the venture after the USA.

ESA's bird's eye

The European Space Agency plans to send up a high orbiting weather satellite as part of a world-wide effort to obtain even faster and more detailed information about the earth's weather and climate. The "Meteosat" satellite is due to start operating in mid 1977, and the data from its continuous observation should help to produce more reliable weather forecasts. Siemens, as the main contractor, is at present constructing the antenna for the main ground station for this project near Michelstadt in the Odenwald region. The purpose of the Meteosat weather satellite is to photograph cloud movements and

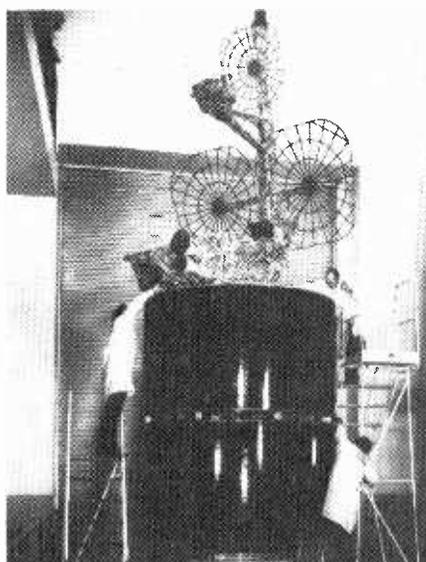

Intelsat IV-A communication satellite (see news item). British Aircraft Corporation Electronic & Space Systems Group at Bristol under contract to Hughes Aircraft Company manufactured major sections of the satellite including the spun structure, booster adapter, despun components, cable harness and solar arrays.



Main-station antenna near Michelstadt in the Odenwald region of Federal Germany for ESA's Meteosat weather satellite (see news item).

general atmospheric phenomena. From its orbiting position 36,000km above the equator at the Greenwich meridian, the satellite will be able to survey an area extending from northern Europe to the South Atlantic and from mid Atlantic to the Indian Ocean. One ordinary and one infra-red picture will be transmitted in digital form at half-hourly intervals to the ground station, where a computing centre will compare the newly received pictures with the previous ones. The functions performed by the satellite's transmission system include: transmitting the pictures taken by the satellite in the visible and infra-red range to the main station; transferring the processed meteorological pictures from the main station to the user stations; transmitting data from the unattended stations to the main station. The S band (2.1GHz or 1.7GHz) is used for traffic with the main station and the user station and the u.h.f. range (400 or 470MHz) is used for traffic with the unattended frequencies.

Satcom service for Alaska

Satellite Satcom I, designed specifically for Alaska communication services, was launched in mid December from the Kennedy Space Center at Cape Canaveral, USA. The satellite is urgently required for increased capacity voice, record and video services. These include critical operations for Alaskan pipeline communications, for telephone and public health services with the first 20 new small village earth stations under construction and also with 80 other small earth stations to follow in Alaska. Satcom I is the first of three that RCA will operate as part of its domestic satellite communications service available across the United States. The critical weight requirements of a high-capacity, 24-transponder communications satellite dictated the use of a three-axis stabilized spacecraft in place of the more familiar spinner type vehicle. Weight savings were achieved by the use of graphite-fibre epoxy composite materials instead of conventional substances for the communications input and output multiplexers, antenna horns, waveguide and support towers, which cut the weight of those subsystems in half. Satcom I has 24 independent 34MHz communication channels in the 500MHz bandwidth authorized for satellite communications. Information will be transmitted using alternate horizontal and vertical polarization. To prevent interference between these signals, wire grids are embedded in the four antenna reflectors. These are designed so that two reflectors will receive only horizontally polarized signals while the other two receive only the vertical.



For faster delivery try these sources

Our Appointed Distributors have been ordering instruments on your behalf for over a year now. This means they can deliver your order quicker than any other source. They can help you choose the right instrument, too. Here's where to contact them:

LONDON AREA

London

Edmundson Electric Ltd.

Tel: 01-891 1331

ERD(South East) Ltd.

Tel: 01-928 5620

Lugton & Co. Ltd. Tel: 01-348 8247

RT & I Electronics Ltd.

Tel: 01-539 4986

ITT Distributors Ltd.

Tel: 01-803 6522

Harlow

ITT Instrument Services

Tel: 0279 29522

Welwyn Garden City

Ellistons (Welwyn) Ltd.

Tel: 07073 26344

MIDLANDS

Coventry

Mercia Electronics Ltd.

Tel: 0203 24091

Birmingham

ITT Distributors Ltd.

Tel: 021-236 5030

ERD(Midlands) Ltd. Tel: 021-236 5060

Northampton

E.M.F.(Electrical) Ltd. Tel: 0604 21711

Norwich

Newey & Eyre Ltd. Tel: 0603 49341

Nottingham

Newey & Eyre Ltd. Tel: 0602 866531

NORTHERN IRELAND

Belfast

Eirco Ltd. Tel: 0232 42911

NORTHEAST

Hull

Edmundson Electric Ltd.

Tel: 0482 20691

Leeds

Farnell Electronic Components Ltd.

Tel: 0532 636311

Wetherby

Farnell Instruments Ltd.

Tel: 0937 3541

Newcastle upon Tyne

J. Gledson & Co. Ltd. Tel: 0632 860955

NORTH WEST AND N. WALES

Salford

Hirst Ibbetson & Taylor Ltd.

Tel: 061-832 9711

J. Walton (Electrical) Ltd.

Tel: 061-872 4224

SCOTLAND

Glasgow

ERD(Scotland) Ltd. Tel: 041-647 7141

Elesco-Fraser Ltd. Tel: 041-221 9301

SOUTH WEST AND S. WALES

Bristol

Black Arrow (Electronics) Ltd.

Tel: 0454 315824

Cardiff

Newey & Eyre Ltd. Tel: 0222 45831

Bath

ERD(South West) Ltd. Tel: 0225 63281

You will still be able to buy our instruments through your usual wholesaler, although he may not be an Appointed Distributor.



THORN

Thorn Measurement Control and Automation Division, Archcliffe Road, Dover, Kent. Telephone: Dover (0304) 202620

Avo Limited
Evershed & Vignoles Limited MEGGER Instruments Division
H. W. Sullivan Limited
Taylor Electrical Instruments Limited

WW-085 FOR FURTHER DETAILS
www.americanradiohistory.com

Now...the most exciting Sinclair kit ever


The Black Watch kit

At £17.95, it's

★ **practical** – easily built by anyone in an evening's straightforward assembly.

★ **complete** – right down to strap and batteries.

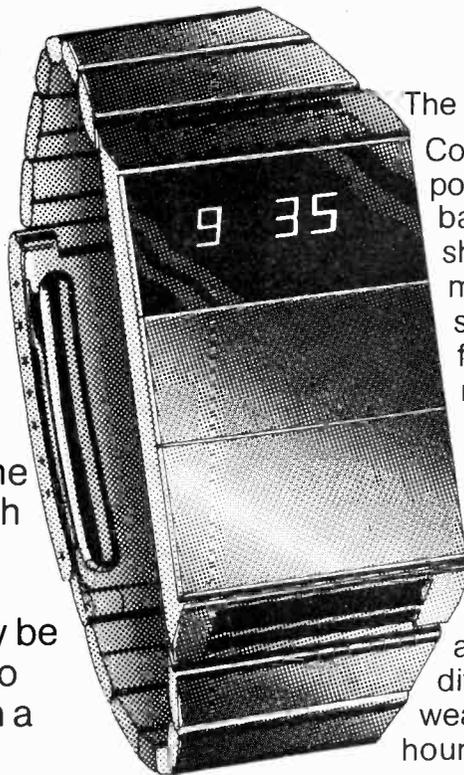★ **guaranteed.** A correctly-assembled watch is guaranteed for a year. It works as soon as you put the batteries in. On a built watch we guarantee an accuracy within a second a day – but building it yourself you may be able to adjust the trimmer to achieve an accuracy within a second a week.



The Black Watch by Sinclair is unique. Controlled by a quartz crystal... powered by two hearing aid batteries... using bright red LEDs to show hours and minutes and minutes and seconds... it's also styled in the cool prestige Sinclair fashion: no knobs, no buttons, no flash.

The Black Watch kit is unique, too. It's rational – Sinclair have reduced the separate components to just four.

It's simple – anybody who can use a soldering iron can assemble a Black Watch without difficulty. From opening the kit to wearing the watch is a couple of hours' work.




The special features of The Black Watch

Smooth, chunky, matt-black case, with black strap. (Black stainless-steel bracelet available as extra – see order form.)

Large, bright, red display – easily read at night.

Touch-and-see case – no unprofessional buttons.

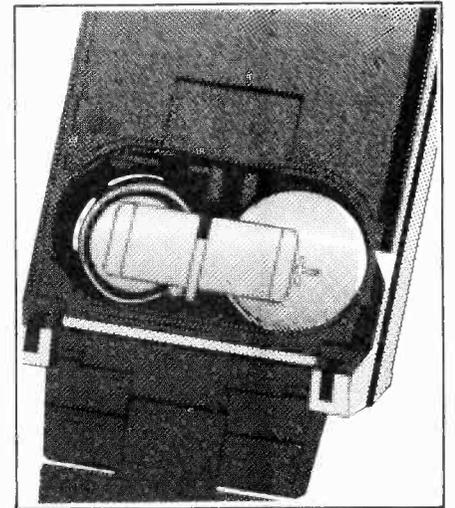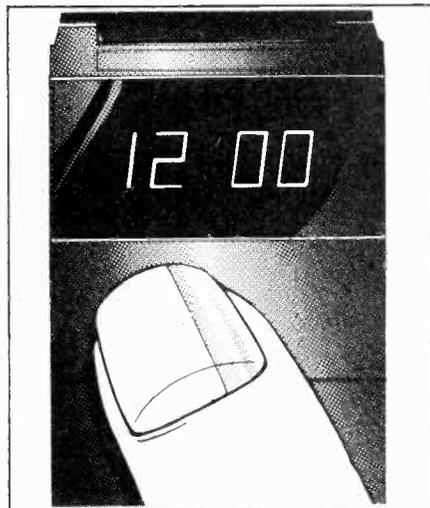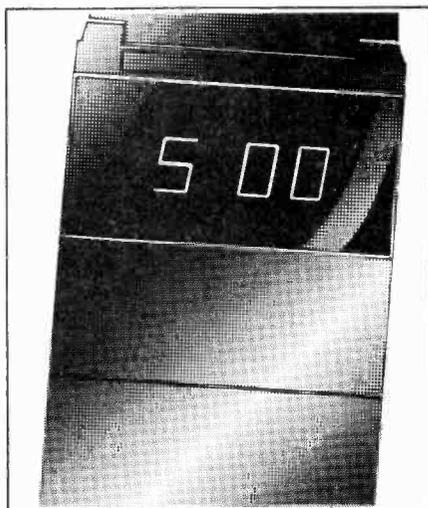Runs on two hearing-aid batteries (supplied). Change your batteries yourself – no expensive jeweller's service.



The Black Watch – using the unique Sinclair-designed state-of-the-art IC.

The chip...

The heart of the Black Watch is a unique IC designed by Sinclair and custom-built for them using state-of-the-art technology – integrated injection logic.

This chip of silicon measures only 3 mm x 3 mm and contains over 2000 transistors. The circuit includes

- a) reference oscillator
- b) divider chain
- c) decoder circuits
- d) display inhibit circuits
- e) display driving circuits.

The chip is totally designed and manufactured in the UK, and is the first design to incorporate all circuitry for a digital watch on a single chip.

...and how it works


A crystal-controlled reference is used to drive a chain of 15 binary dividers which reduce the frequency from 32,768 Hz to 1 Hz. This accurate signal is then counted into units of seconds, minutes, and hours, and on request the stored information is processed by the decoders and display drivers to feed the four 7-segment LED displays. When the display is not in operation, special power-saving circuits on the chip reduce current consumption to only a few microamps.

Complete kit £17.95!

The kit contains

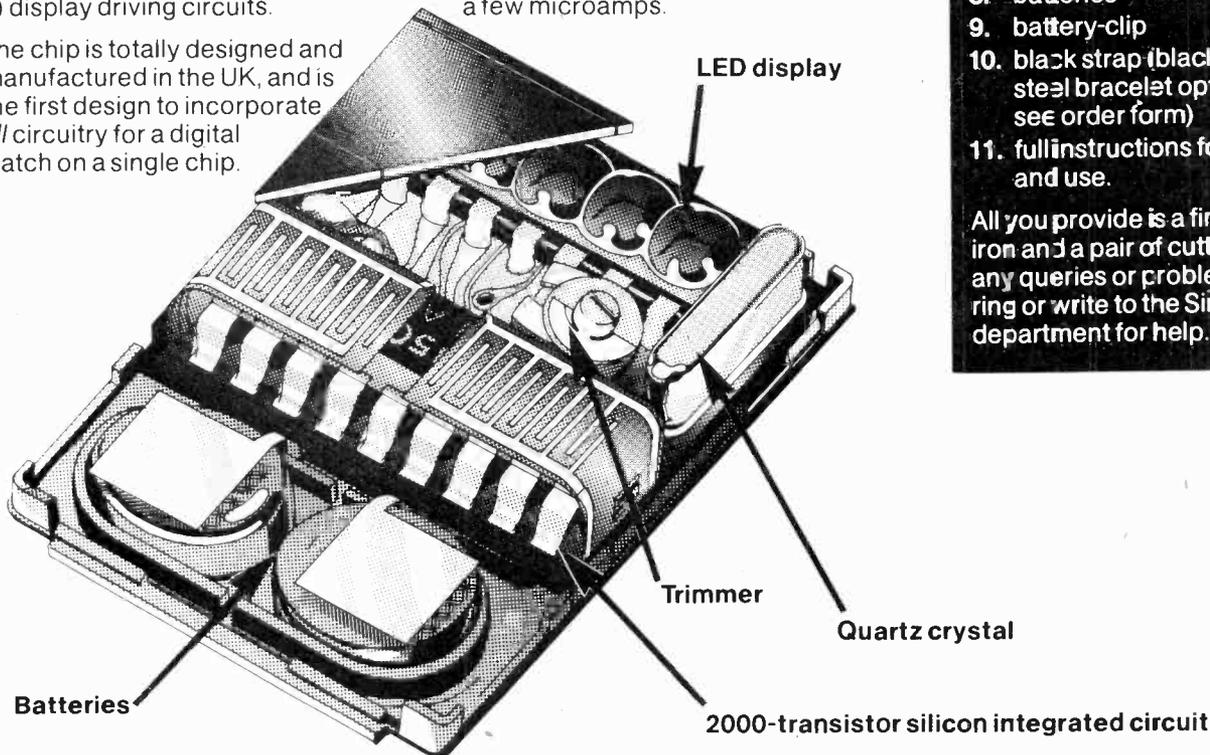1. printed circuit board
2. unique Sinclair-designed IC
3. encapsulated quartz crystal
4. trimmer
5. capacitor
6. LED display
7. 2-part case with window in position
8. batteries
9. battery-clip
10. black strap (black stainless-steel bracelet optional extra – see order form)
11. full instructions for building and use.

All you provide is a fine soldering iron and a pair of cutters. If you've any queries or problems in building, ring or write to the Sinclair service department for help.



Take advantage of this no-risks, money-back offer today!

The Sinclair Black Watch is fully guaranteed. Return your kit within 10 days and we'll refund your money without question. All parts are tested and checked before despatch – and correctly-assembled watches are guaranteed for one year. Simply fill in the FREEPOST order form and post it – today!

Price in kit form: £17.95 (inc. black strap, VAT, p&p).

sinclair

**Sinclair Radionics Ltd,
London Road, St Ives,
Huntingdon, Cambs., PE17 4HJ.
Tel: St Ives (0480) 64646.**

Reg. no: 699483 England. VAT Reg. no: 213 8170 88.

To: Sinclair Radionics Ltd, FREEPOST, St Ives, Huntingdon, Cambs., PE17 4BR.

Please send me

Total £

..... (qty) Sinclair Black Watch kit(s) at £17.95 (inc. black strap, VAT, p&p)

..... (qty) black stainless-steel bracelet(s) at £2.00 (inc. VAT, p&p)

* I enclose cheque for £..... made out to Sinclair Radionics Ltd and crossed.

* Please debit my *Barclaycard/Access/ American Express account number

Name _____

Address _____

ww2

Please print. FREEPOST – no stamp required.

*Delete as required

Now the Alpha costs less than the A*** will the 1567 engineers who are still without one please identify themselves ?




It was two years ago that Alpha one was launched by Advance.

As a brand new concept in low cost digital multimeters.

Now, many thousands of instruments later, Alpha I and II are everywhere.

You, too, should claim your Alpha. And to help you, we're listing the advantages engineers of competing firms enjoy :

- ★ Low, low prices. Alpha I now costs only **£49** and Alpha II is now only **£57** including a mains power supply but excluding VAT.
- ★ Extraordinary battery longevity. One PP9 lasts up to a year in an Alpha I.
- ★ No backache. Alphas are small, light, but in a tough as blazes carrying case.
- ★ No problems – reliability is superb with long periods between recalibration.
- ★ No squinting. Our LEDs give bright, clear, unambiguous readouts.

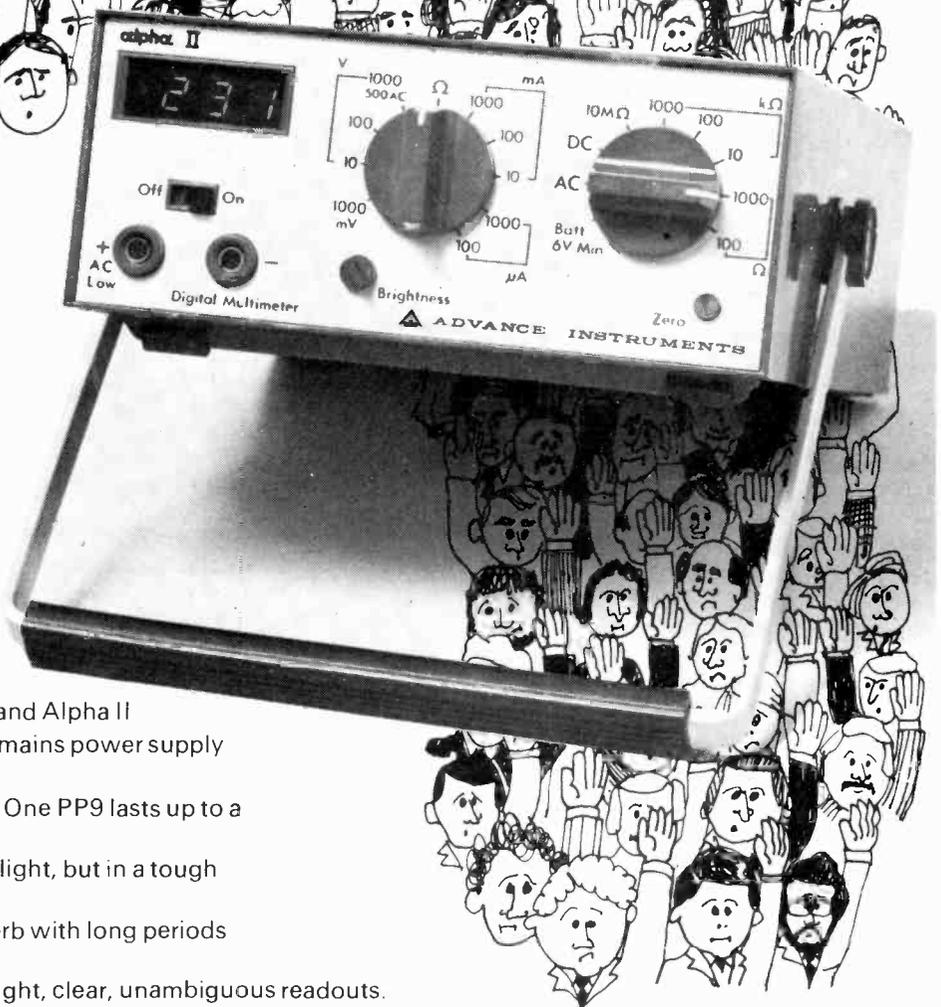

Do get the Gould Advance data on Alpha. You see, it's so much better.

Gould Advance Limited
Roebuck Road, Hainault, Essex, England.
Telephone: 01-500 1000 Telex: 263785

GOULD ADVANCE

WW 078—FOR FURTHER DETAILS

Thermistor and thermocouple action

Methods of measuring temperature

by C. Budd

With the widespread use of the thermistor, the thermocouple seems to have been neglected. This article reviews the characteristics and principles of operation of the two devices and discusses their relative merits in practical applications

Thermistor action is based on the rapid variations of resistivity with temperature found in semiconductor materials. This component is a black sheep in the family of low-frequency semiconductor devices because it contains no junctions — just a piece of semiconductor material with two ohmic non-rectifying contacts. There are two basic types of thermistor, negative-coefficient types (n.t.c.) and positive-coefficient types (p.t.c.)

P.t.c. thermistors

In a metal, the forbidden energy band between the valence and conduction bands (see Fig. 1) has zero width and electrons can pass freely from one band to the other at any temperature other than absolute zero. The number of electrons available for conduction is practically independent of temperature. Theory shows that, approximately;

$$\rho = 2mv/ne^2l \quad (1)$$

where m is the mass of each charge carrier (each electron in this case), v is the velocity of each charge carrier, n is the number of charge carriers available for conduction per unit volume, l is the average distance travelled by each charge carrier between collisions with the atoms of the material, e is the charge of each charge carrier (-1.602×10^{-19} coulombs for electrons), and ρ is the resistivity of the material. Because m , n , e , and l are constants and v increases with temperature the resistivity must increase with temperature. This effect, known as lattice scattering, is responsible for the small positive temperature-coefficient of resistivity in most metals.

Lattice scattering is only apparent in semiconductors when the thermal energy is small enough, or the temperature is high enough to make the number of charge carriers available per unit volume a constant. This occurs in

extrinsic (doped) silicon at about room temperature because ample thermal energy is available to excite electrons from the donor level to the conduction band in n-type silicons, or from the valence band to the acceptor level in p-type. A much greater temperature must be reached, however, before electrons can gain enough energy to pass from valence to conduction band and allow intrinsic conductivity. Therefore the number of charge carriers, either electrons or holes, available per unit volume is virtually independent of temperature, and the resistivity of the semiconductor will obey equation (1). The approximate relationship between resistivity and temperature is shown in Fig. 2. If the semiconductor sample is encapsulated, a resistor with a fairly


large positive temperature coefficient of resistance is formed. The approximate relationship between temperature and resistance for this device is;

$$R = R_0 \cdot T^S \quad (2)$$

where R_0 is a constant with the dimension of resistance which varies from device to device, R is the resistance of the device, T is the absolute temperature, S is a constant, about 2.7 for p-type silicon and 2.5 for n-type. Rearrangement and differentiation of equation (2) shows that the temperature coefficient of resistivity of the thermistor is equal to S/T . Therefore, at a room temperature of 300°K and assuming that the silicon is p-type, the temperature coefficient of resistance should have a value of about 0.9%/K. In practice a figure of about 0.72%/K can be achieved.

Extrinsic silicon is not the only material that may be used in p.t.c. thermistors. Barium-titanate is commonly used and is capable of far greater changes in resistivity. The relationship between temperature and resistivity for barium-titanate is shown in Fig. 3. The

Fig. 1. Orbital electron energy bands in insulators, semiconductors and metals. At absolute zero temperature, only the valency bands are occupied but electrons may cross the energy gap, at higher temperatures, to become available as charge carriers.

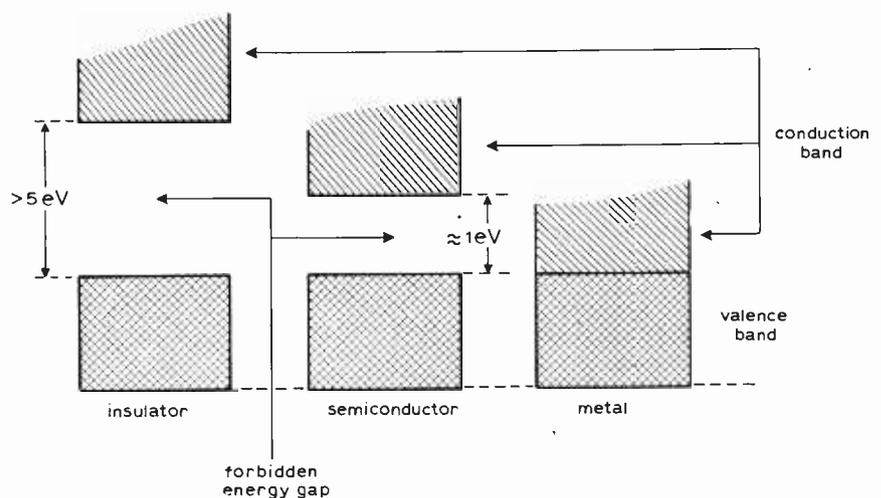

resistivity drops slowly and uniformly as the temperature is increased until a critical point (the Curie temperature) is reached and the resistivity sharply increases by a factor of between 10,000 and 100,000. For the sample of BaTiO₃ represented in Fig. 3, the Curie temperature would be about 393°K and the transition from low to high resistance would occur over a range of a few deg Kelvin. This type of device is known as a switching thermistor and finds application in protection circuits. By adding other titanates, the switching temperature may be varied between about 170 and 490°K and the rate of change of resistance may be reduced to almost any desired level. Both silicon and barium-titanate based thermistors have non-linear temperature-resistance functions and are not generally suitable for thermometric use.

N.t.c. thermistors

If the resistivity of intrinsic (pure) semiconductor material is plotted about temperature, a graph such as Fig. 4 is obtained. Because the sample is pure, conduction is by means of electrons thermally excited into the conduction band and by the holes created in the valence band. The resistivity of the material, therefore, decreases with rising temperature. An approximate relationship between temperature and resistance for such a device is;

$$R = A \exp(B/T) \quad (3)$$

where R is the resistance at temperature T , T is the absolute temperature, A is a constant for the device having the dimension of resistance. B is another constant for the particular device having the dimension of temperature. Rearrangement and differentiation shows that the temperature coefficient of resistance must be equal to $-B/T$ and this will usually lie between -2 and $-7\%/K$. Because the n.t.c. thermistor relies on intrinsic conduction, the semiconductor materials used must have fairly small forbidden-energy gaps to be useful at moderate temperatures. The energy gaps of germanium and silicon are too wide, so oxide semiconductors are almost exclusively used. In fact, the explanation of the resistance-temperature dependence given above is an over-simplification. Conduction in oxide semiconductors is less well understood than in elemental types.

The relationship between temperature and resistance is very non-linear, which makes the n.t.c. thermistor useless for accurate thermometric work. However, some n.t.c. thermistors may be regarded as having approximately linear characteristics over very limited temperature ranges and fairly simple correction can be applied to produce a cheap thermometer which is accurate over a limited range of temperatures. In this connection, thermistors encapsulated in glass beads do have

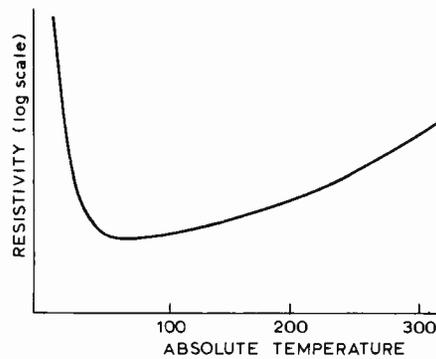


Fig. 2. Resistivity versus temperature graph for extrinsic silicon.

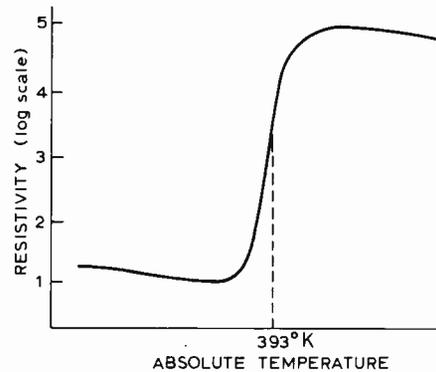


Fig. 3. Resistivity versus temperature graph for barium titanate.

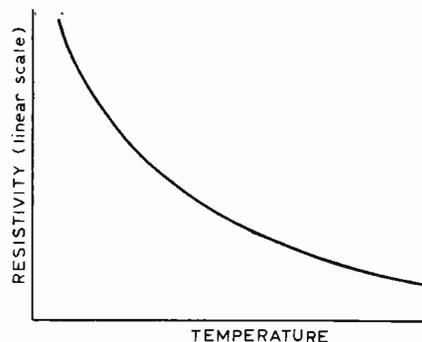


Fig. 4. Resistivity versus temperature for an intrinsic semiconductor material showing an approximate inverse-exponential curve.

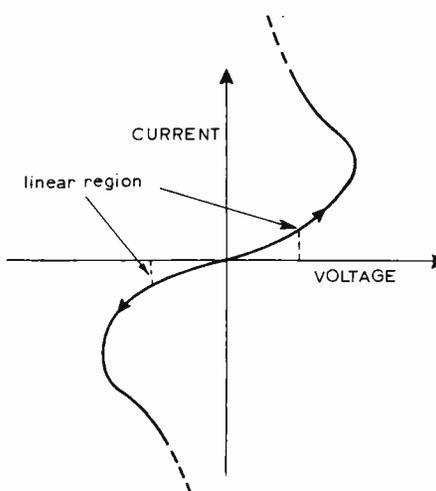


Fig. 5. Approximate current versus voltage characteristic for an n.t.c. thermistor heated by its own power dissipation.

the advantage of a very small heat capacity.

Applications of n.t.c. thermistors include temperature compensation in transistor circuits and certain situations requiring non-linear resistance elements in which the thermistor is heated by its own power dissipation. The voltage-current characteristic for an n.t.c. device is shown in Fig. 5.

Thermocouples

If two different metals are joined together a voltage will appear between them known as the contact potential. This voltage will be very small and arises as follows. The free electrons available for conduction in a metal may be regarded as forming a gas which possesses a pressure, and permeates the metal's crystal lattice. Two different metals will have different gas pressures and when they are joined the difference in pressure will cause a net flow of electrons from one metal to the other. This momentary flow will cease when the effective force on each electron due to the pressure gradient is countered by an equal but opposite electrostatic force due to the resulting contact potential. The generated voltage will increase with temperature at a rate between zero and 60 microvolts per degree Kelvin and will be independent of the area of contact. A single metal to metal junction as described is called a thermocouple and several such junctions joined in series is called a thermopile.

The actual contact potential of a thermocouple is rarely specified because the difference between a particular thermocouple's voltage at a particular temperature and the voltage developed by an exactly similar one at some reference temperature (usually zero degrees Celsius) is of more practical importance. On this basis, Fig 6(a), (b) show the difference-voltages developed by several common types of thermocouples for two different temperature ranges. The exact mathematical relationship between temperature and voltage for a thermocouple is rather involved, but a good approximation is given by the quadratic function;

$$V = A.T + B.T^2 \quad (4)$$

where T is the difference in temperature between the variable and fixed thermocouples, V is the difference voltage developed between the variable and fixed-temperature couples, and A and B are constants for the particular thermocouple type and the particular reference temperature. Shown in Fig. 7 is a general graph, deduced from equation (4), of temperature against voltage for any thermocouple. The temperatures H and I are known respectively as the neutral and inversion temperatures of the thermocouple. This graph is, in fact, mainly of academic interest because many thermocouples (copper/iron being a notable exception)

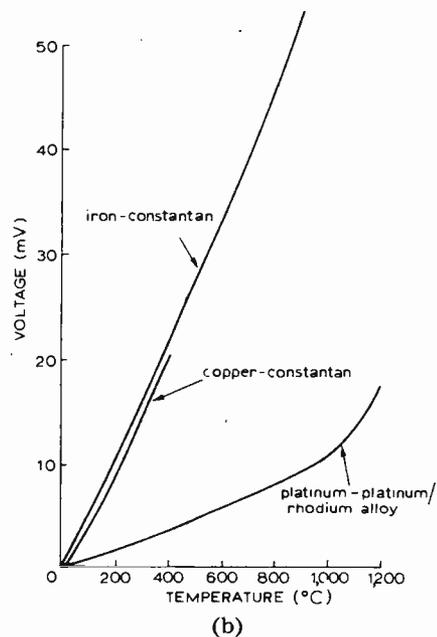
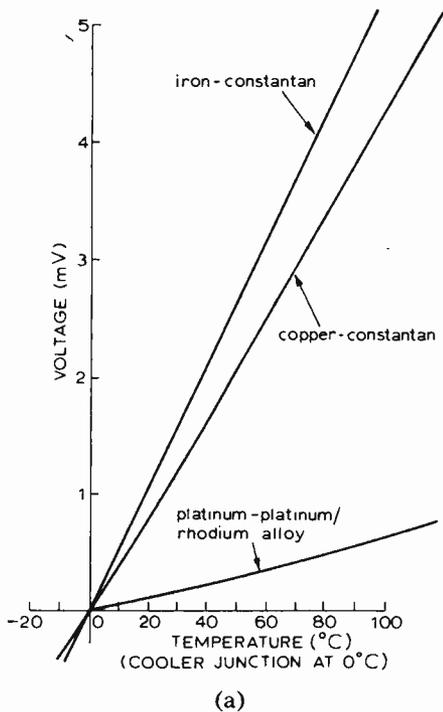


Fig. 6(a)(b). Difference-voltages developed by several common types of thermocouples for two different temperature ranges.

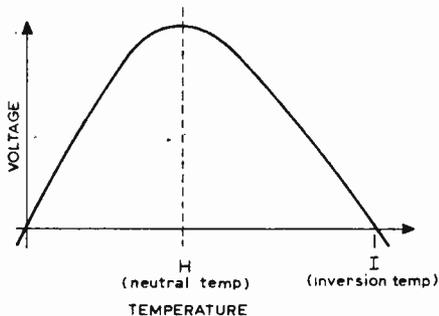


Fig. 7. General temperature versus voltage graph for a thermocouple.

either melt or undergo some chemical change before reaching the neutral temperature. Because B in equation (4) is often small enough, in a practical thermocouple, the temperature-voltage relationship can be regarded as linear over its useful range. Metal pairs used in common thermocouples are, iron/constantan – useable below 1030°K, sensitive and substantially linear. Copper/constantan – useable below 670°K, rather less linear and almost as sensitive as iron/constantan. Copper/iron – substantially non-linear, neutral temperature about 510°K. Platinum/platinum-rhodium alloy – much less sensitive than iron or copper with constantan, stable and linear at low temperatures and useable up to about 1370°K. The international temperature scale is defined between 903.16°K and 1336.16°K in terms of a platinum/platinum-rhodium alloy thermocouple pair; one couple being maintained at 0°C, the ratio of the concentrations of platinum and rhodium in the alloy being 9:1.

It is found that if several thermocouple-type junctions are connected in series and all held at the same temperature – see Fig. 8, the total voltage developed around the loop is zero. Using this principle, an arrangement such as Fig. 9(a) should act as a thermometer, giving a zero reading when the meter and the thermocouple are at the same temperature, and a steadily greater reading as the thermocouple temperature is raised above that of the meter. Such an arrangement is frequently used to measure the high temperatures of furnaces. This system has the disadvantage that the temperature corresponding to zero meter reading is the temperature of the meter itself and therefore varies with ambient temperature, slightly shifting the entire temperature scale as it does so. A circuit which overcomes these drawbacks is shown in Fig. 9(b), where two junctions between the connecting wires and the meter (or d.c. amplifier) are identical so the voltages they develop will be equal and opposite. The temperature of the sensing thermocouple (junction X) corresponding to zero meter reading will now be the reference temperature. The need for a reference temperature in the circuit of Fig 9(b) could be a considerable drawback if a simple thermometer is needed. In a remote temperature measuring application it will be necessary to station the meter or recorder and associated circuitry some distance from the thermocouple.

To prevent unwanted varying voltages it would be ideal to make the whole run, from each thermocouple to the instruments, in wire of the same metals as the thermocouple. This could be expensive, especially if the thermocouples are of the platinum/platinum-rhodium type, so an arrangement as shown in Fig. 10 may be used. This makes it possible for the whole run from each thermocouple to be made in

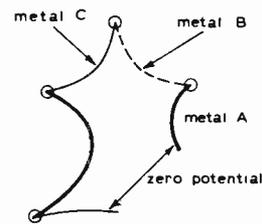


Fig. 8. Total voltage developed around a ring of thermocouples, all at the same temperature, is zero.

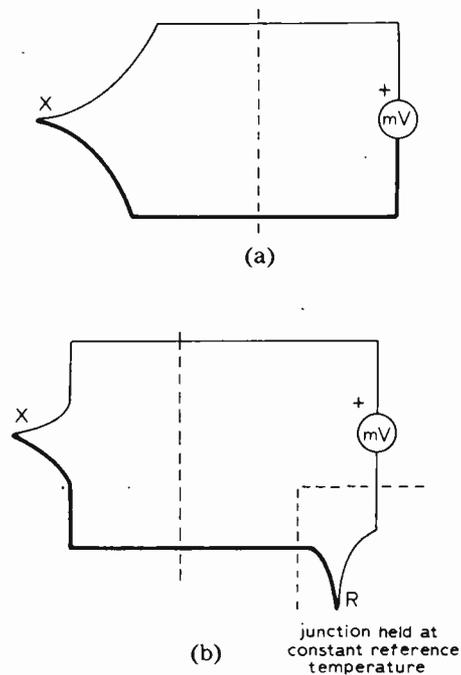


Fig. 9 (a). Simple thermocouple thermometer and a superior arrangement (b) where a second thermocouple is held at a constant reference temperature.

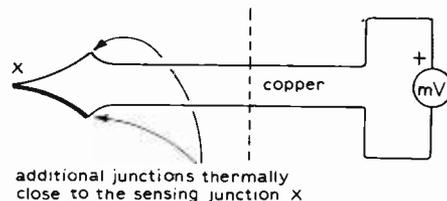


Fig. 10. Remote temperature-sensing arrangement which permits the use of copper wire for connecting the sensing thermocouple to the measuring instruments.

copper wire and obviates the need for an extra thermocouple at a reference temperature because the two connections between each pair of leads and the instruments are identical. The only additional requirement is that the two junctions created at each sensing point should be close enough to the main junction to be at the same temperature. A practical design for a thermocouple thermometer capable of remote mea-

surement at seven different points is given in reference 1.

Pyrometers

The temperatures of bodies may be measured without physical contact by using an instrument called a total radiation pyrometer in which the heat and light radiation from an object is focused by a mirror onto a blackened thermocouple. The voltage developed by this thermocouple is compared with the voltage from an identical one at

ambient temperature. The temperature of the object is determined from the difference voltage. The amount of radiation emitted by a body depends upon its emissive properties as well as the temperature and if it is not a black-body (i.e. a perfect radiator and absorber) the temperature measured by the total radiation pyrometer will be lower than the true temperature. Correction tables are available for the emissive properties of an object, but the error may still be considerable. Total

radiation pyrometers also have a disadvantage compared with direct contact thermometers because they can only be used with fairly large objects.

Practical thermocouple circuits

The output from a thermocouple is in the order of $40 \mu\text{V}/^\circ\text{K}$ for a copper/constantan couple. This makes a d.c. amplifier generally impracticable because the variations in thermocouple voltage would be swamped by the thermal drift of voltages within the amplifier. For this reason a d.c. chopper or synchronous amplifier is often used. The outline of such an amplifier is shown in Fig. 11 Ch.1 is a fast switch which alternately connects point Q to the input voltage and ground for equal times. Thus, a square waveform such as that shown in Fig. 12(a) is produced at Q. This is a.c. coupled to amplifier A to produce a square-wave at S which is symmetrical about ground—Fig. 12(b). Ch2 is another chopper which alternately connects T to S' and ground. By synchronizing Ch.1 with Ch.2 T is connected to S' during positive half-cycles of the waveform at S', producing a waveform as shown in Fig. 12(c) at T. Resistor R and capacitor C act as a smoothing network to produce a d.c. output at U proportional to the input voltage at P. The actual amplification is performed on an a.c. signal to avoid thermal drift.

A m.o.s.f.e.t. switching circuit is shown in Fig. 13. Transistor Tr_1 and Tr_2 are enhancement-mode m.o.s.f.e.t.s being switched by the square-wave voltage. An operational amplifier is a.c. coupled to the choppers. The chopping frequency is not important and an arrangement similar to that shown uses a frequency of 300Hz.

Correction for non-linearity

As shown in equation (4) and Fig. 7, all thermocouples have non-linear voltage temperature relationships, but for many applications the value of B in equation (4) is small enough, for them to be regarded as linear (B is about -0.02 for copper/iron and 0.04 for copper/constantan at 0°C). However, in an accurate thermocouple thermometer which operates over a wide portion of its useful range, some form of non-linear correction will be needed. There are many circuits capable of giving an adjustable non-linear response but they all depend on non-linear negative feedback to a d.c. amplifier. This technique is well described in reference 2.

References

1. "International Thermocouple Meter", *Electronics Today International*, December 1973.
2. "Experiments with Operational Amplifiers - 6", *Wireless World*, November 1972.

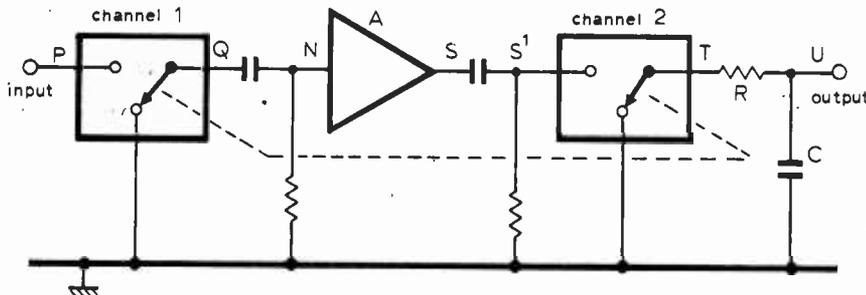


Fig. 11 (above). Outline of a d.c. chopper amplifier where channel 1 and 2 are fast switches which produce a square wave.


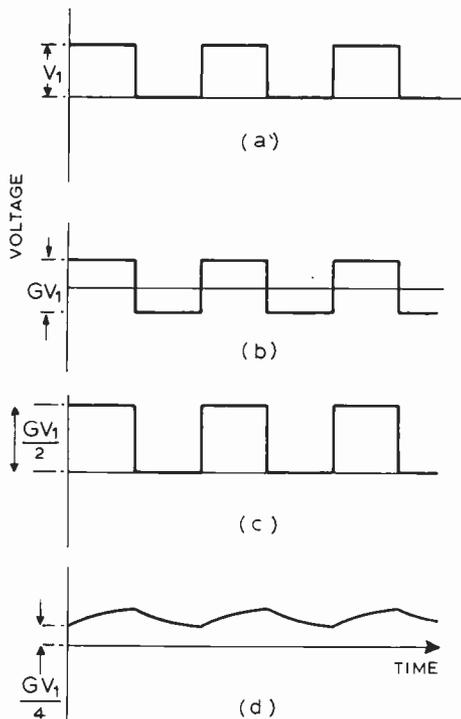


Fig. 12(a)(b)(c)(d). Waveforms at points Q, S, S' and U respectively in Fig. 11 where V_1 is the input voltage and G is the gain of amplifier A.

Fig. 13 (below). Outline of a d.c. chopper amplifier for use in a thermocouple amplifier. Transistors Tr_1 and Tr_2 are enhancement-mode m.o.s.f.e.t.s which are switched by the square wave input.

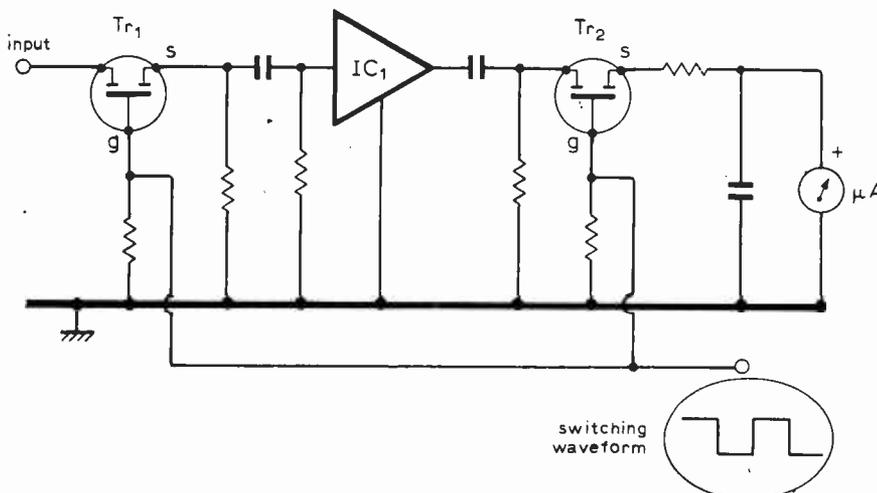

Gunn effect and avalanche oscillators

The generation of microwaves using solid-state diodes

by F. A. Myers, B.Sc., Ph.D.

Allen Clark Research Centre, The Plessey Company Ltd

Microwave solid-state oscillators have become well established in a new generation of electronic equipment. This article briefly discusses the operating principles of these oscillators and emphasizes the operational parameters that determine the choice of a device for a particular application.

Microwave solid-state oscillators have become well established in new generation electronic equipment, such as intruder alarms, man-pack radars, radar altimeters, distance measuring equipment etc. Gunn effect and avalanche diodes have played a major part in the development of these new systems and are replacing some of the older solid-state devices, such as multipliers, in many applications.

Gunn effect devices

It was established that when high electric fields are applied to a piece of gallium arsenide with ohmic contacts, a bulk negative resistance is produced which leads to the formation of a so-called high field domain. The domain propagates through the material at approximately the electron's velocity ($\approx 10^7$ cms/sec) and gives rise to an oscillatory current through the device. If the device is placed in a suitable resonant circuit, microwave power can be extracted. Due to the high velocity of the electron, the active material lengths must be short in order to obtain useful power: the basic frequency is given by $f = \text{electron velocity length}$. Practical limits vary from about 20 microns for a C-band (4GHz) diode to 1.5 microns for a Q-band (40GHz) device. The high frequency limit is around 100GHz and is caused by an inherent time delay which sets up the electron distribution required for negative resistance. Difficulties in material growth also set the limit at around 100GHz.

The active layers involved (2-20 microns) are far too thin to be handled practically in the form of bulk crystals, i.e. by lapping down thicker crystals. This means that some form of epitaxial growth must be used on a highly conducting and almost metallic substrate which will form one contact and also provide the required mechanical

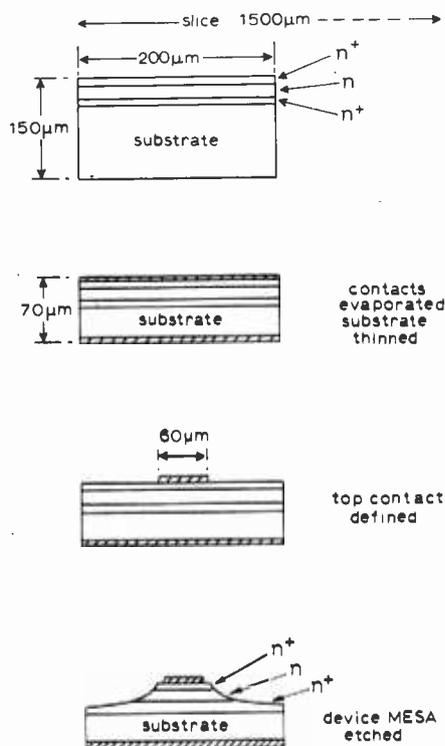


Fig. 1a

Fig. 1(a). Fabrication of a typical low power 20mW c.w. device. Scanning electron microscope photograph of such a device is shown at (b).

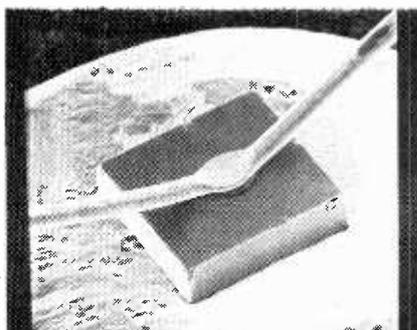


Fig. 1b

strength. The process invented and used by Plessey, and now many others, is the arsenic trichloride vapour epitaxy process which allows good control of the material for carrier concentrations of $1 \times 10^{15}/\text{cc}$ and above. Briefly, a substrate ($n+$) slice is very carefully lapped and polished to the required thickness and then a few microns of $n+$ gallium arsenide are grown epitaxially on this to mask remaining surface defects. The dopant in the gas stream is then reduced, in a continuous growth process, and the active layer of gallium arsenide is grown on to the so-called $n+$ buffer layer. The growth continues until the required thickness for the final device is obtained. At this stage the fabrication techniques used by various manufacturers diverge. The older technique requires that the growth ceases at this point and the slice is taken out of the reactor for contact metallization. This technique, although it produces usable devices, is rather difficult to control and produces devices with more variable characteristics such as device life and noise output. The more modern technique involves a further epitaxial growth of a thin $n+$ contact layer on to the active layer. The slice is then taken from the reactor and metallized. Contacting to highly-doped gallium arsenide is a far easier and more controlled process and produces a high yield of devices with virtually identical characteristics.

Semiconductor photoresist and etching techniques are used to define individual devices on the slice, after which they are diamond scribed and cleaved from the crystal. Individual devices are then bonded into packages suitable for mounting in a microwave environment. A brief pictorial summary of the fabrication of a typical low power ($\approx 20\text{mW}$) diode is shown in Fig. 1, together with a scanning electron microscope photograph of such a

device. Low power devices are alloy-bonded thermally with the substrate against the package heat sink, and are limited to a few tens of milliwatts of power output. Higher output powers can be obtained by a technique known as flip chip ultrasonic bonding but both of these methods are now being phased out of production in favour of the much more reliable and efficient integral-heat-sink (i.h.s.) devices. This technique is virtually identical to that used for avalanche diodes and is described in that section.

If the formation of a domain in a Gunn effect device is suppressed by some means, usually by careful control of the material characteristics and the circuit, one is left with a classic two-terminal negative resistance device which will oscillate in the i.s.a. mode when placed in the correct circuit. Very high power levels and efficiencies are possible with this type of device. Unfortunately, because the device is very thick and heat sinking is difficult, practical devices will usually only oscillate in a pulsed mode with low duty cycles around 0.1%. Very high power levels, up to 1kW peak, have been generated at X-band and this device is the nearest competitor to the microwave tubes. It is, however, proving a very difficult beast to tame and is not yet in large scale systems use due to both material difficulties in making the device and the circuit difficulties in using it. But it still remains one of the most promising of the solid state pulsed generators for high power and high efficiency.

Avalanche diodes

The avalanche diode differs from the Gunn device in that the basic mechanism arises from a junction effect. Because of this it is possible to make devices from virtually any semiconductor although silicon and gallium arsenide are the more commonly used.

In the device the junction (either p-n or Schottky) is reverse biased into the breakdown region and the combination of the build up time of the resulting avalanche current and the drift of carriers across the depletion region gives rise to a phase delay between the current and voltage. This can result in negative resistance and hence oscillation in a suitable circuit. The maximum frequency limit of the avalanche device is determined by electron tunnelling. When the voltage breakdown is around 2V, the carriers cannot gain sufficient energy for ionisation and no negative resistance occurs which sets an upper frequency limit in excess of 300GHz. This mode of operation is commonly given the name IMPATT (impact avalanche transit time), or, more simply, the avalanche mode.

The main requirement of any technique for constructing avalanche diode generators is that it provides a structure from which heat can be efficiently

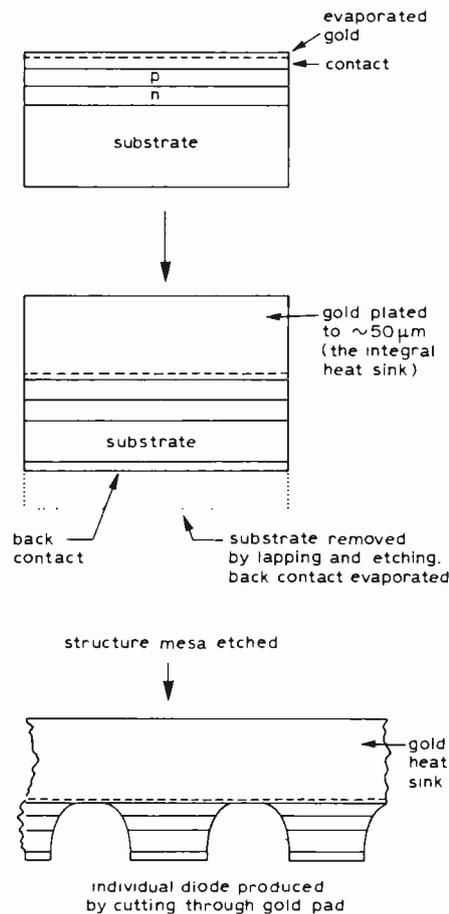


Fig. 2. Integral heat sink fabrication for an IMPATT diode. The active region of the device is adjacent to the metal heat sink for good thermal conductivity.

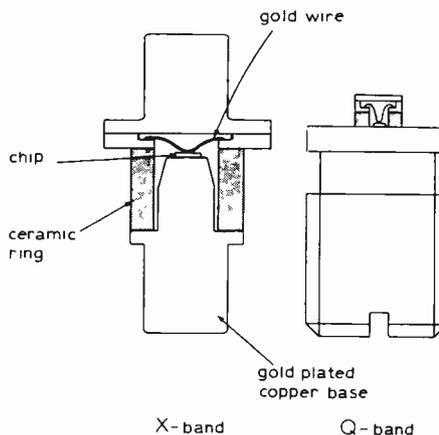


Fig. 3. Final packages for an IMPATT diode. These packages are similar for Gunn devices.

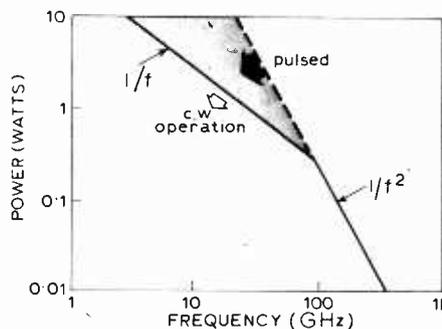


Fig. 4. Idealized plot of power output versus output frequency. The position of the $1/f^2$ line is controlled by the material properties of the semiconductor used.

removed. A process frequently used, known as the integral heat sink process, involves the deposition of a thick metal heat sink layer directly on the surface of the semiconductor slice. The junction is either a very shallow diffused p-n junction or a Schottky barrier. In either case the active region is adjacent to the metal heat sink which has a high thermal conductivity such as gold, copper or silver. Subsequent steps in the process include thinning the semiconductor slice from the back surface by mechanical or chemical polishing followed by photoengraving and chemical etching to define and isolate individual mesa diodes. The process and final diode structure is illustrated in Fig. 2. The integral heat sink is finally cut into square dice each supporting one diode chip. The dice are then bonded individually into conventional copper based microwave packages. The quality of the bond is important for high power operation and techniques such as thermocompression, and alloy or ultrasonic bonding have all been successfully applied. The final packaged diode configuration is shown in Fig. 3. These packages are similar for Gunn devices.

TRAPATT device

In 1967 a second mode of oscillation was discovered. This new mode remained unexplained for some time and was initially referred to as the anomalous mode. The principal characteristic features of this mode were a very high conversion efficiency of up to 60%, and low frequency of operation. The mechanism giving rise to this mode was later identified by computer simulation techniques and showed that a new transient breakdown phenomenon was involved. This breakdown occurs when the voltage is applied very rapidly to the diode. Because there is an inherent delay in the build up of an avalanche current, it is possible to overdrive the field, if applied sufficiently rapidly, and create a dense hole-electron plasma. The space charge of the carriers reduces the electric field to almost zero in the plasma region and the velocity of the carriers drops accordingly. This state, in which the diode is filled with plasma and the voltage has collapsed to a low value, is referred to as a trapped plasma state. The diode then recovers gradually as the holes and electrons drift slowly out of the active region thereby restoring the field and voltage to their initial level. This has been called the TRAPATT (trapped plasma avalanche triggered transit) mode.

Comparison of applications

At the highest frequencies the modes of oscillation in Gunn effect and avalanche devices are transit-time limited and are subject to a general power-frequency limitation in which the relative output power decreases as $1/f^2$. The absolute level of output power is controlled by the conversion efficiency and the minimum impedance level

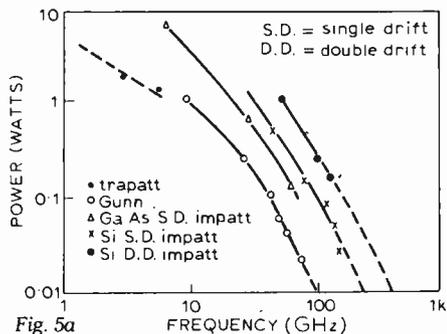


Fig. 5a

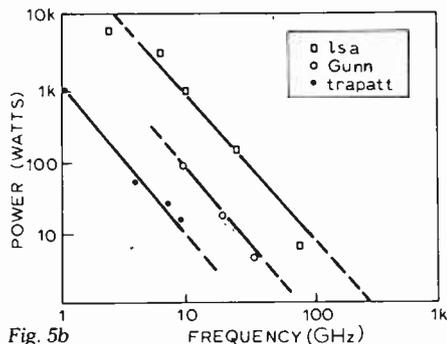


Fig. 5b

Fig. 5. Limiting plots of power versus frequency for (a) c.w. and (b) pulsed generation using current techniques and devices.

attainable in a microwave circuit. At lower frequencies, the devices are thermal-dissipation limited and become subject to a $1/f$ law relating relative output power to frequency. Shown in Fig. 4 is an idealised plot of power output versus frequency. The full line represents the output power limit for

continuous wave operation, and the shaded area represents a region in which devices can be operated for very short duty ratios under pulsed operation. Whilst the position of the $1/f^2$ line is controlled by the material properties of the semiconductor used, the position of the $1/f$ line is set by the device's thermal resistance. Fig. 5(a) and (b) shows how actual results are aligned with these simple theoretical laws. In practice, the efficiency is about 10% for Si IMPATTs and 15% for GaAs IMPATTs. The corresponding figure for Gunn devices varies between 3% and 12% depending on whether the results are "state of the art" or readily reproducible. The TRAPATT efficiency is much higher, up to 60% at low frequencies (around 1GHz) and dropping to 25% at 10 GHz (X-band). Because the carriers spend a considerable fraction of each TRAPATT cycle travelling at their low field drift velocities, one would expect an upper frequency limit well below the IMPATT frequency limit. In practice, difficulties in the control of necessary circuit harmonics will restrict the TRAPATT oscillator to frequencies around X-band for the near future.

It can be seen from the power levels in Fig. 5. that these diodes cannot compete with existing vacuum devices, such as klystrons and magnetrons, which can generate power outputs from milliwatts up to megawatts. Solid-state devices have therefore tended to generate completely new applications which previously could not be satisfied by

existing tubes because of size, reliability and power supply limitations. An attempt has been made to summarize the spectrum of applications in the microwave region from 1 to 100GHz in Fig. 6. The majority of systems lying within the region of solid-state devices are completely new. The possibility of some of these was appreciated before the advent of solid-state devices, but they were considered impracticable.

The decision on which class of solid-state source to use in a given application is usually based on the first-order considerations of output power required for the frequency of the system. Second-order factors may be considered with respect to conversion efficiency, noise and drive requirements.

The table over summarizes present views on preferred devices in a range of applications.

In addition, these devices can all be used as amplifiers but discussion on these is beyond the scope of this article.

The TRAPATT oscillator is best suited to high power pulsed applications such as radar transmitters. In this type of application it is in competition, up to X-band, with the high power pulsed modes of the Gunn and l.s.a. oscillator which can provide higher peak powers at a lower duty cycle. The specific advantage of the TRAPATT diode is its efficiency which becomes increasingly significant when very high power sources are required. Combinations of

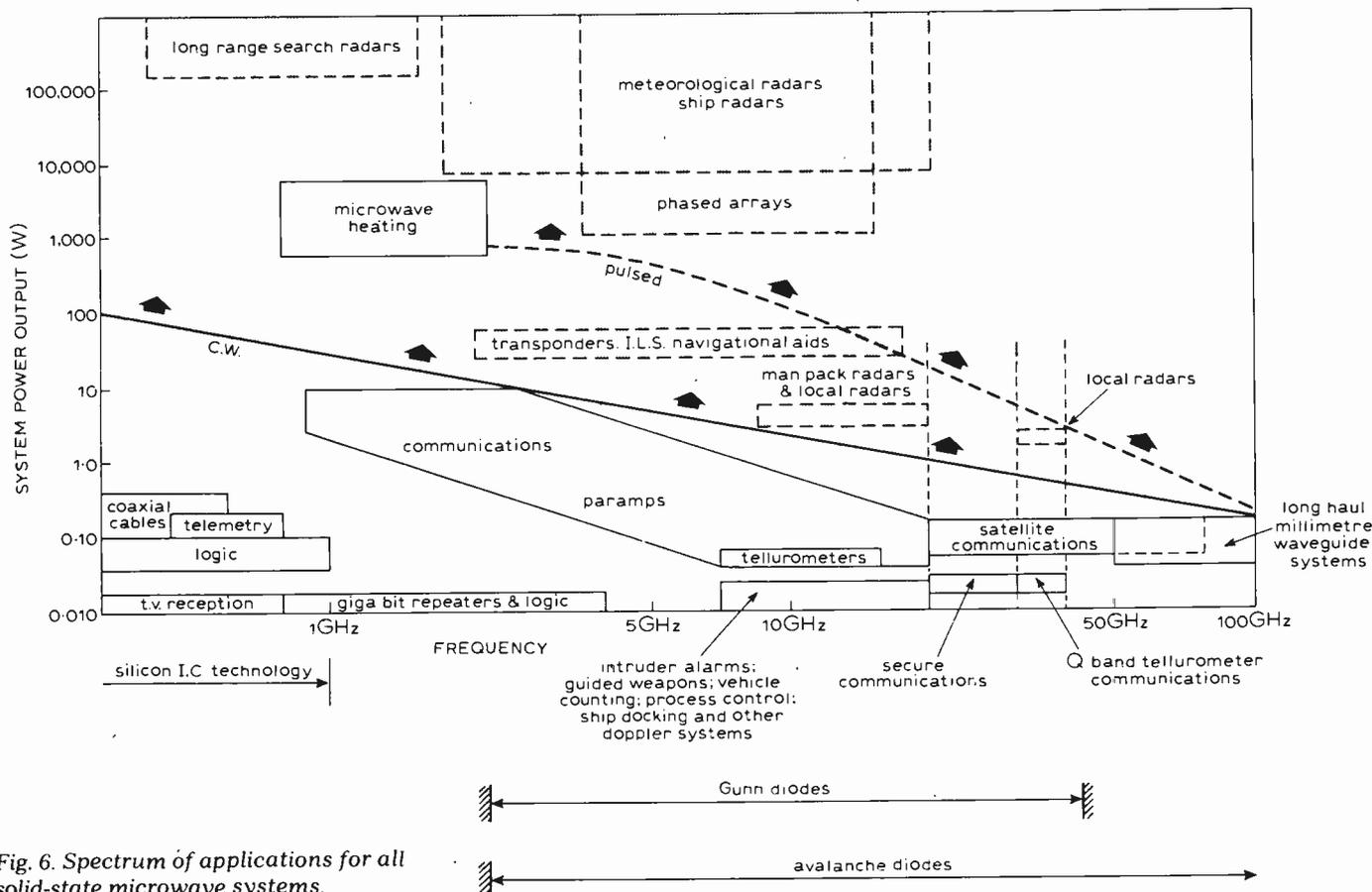


Fig. 6. Spectrum of applications for all solid-state microwave systems.

Application	Preferred device (advantages)
High pulsed power e.g. radar (primary & secondary)	Pulsed Gunn, I.s.a. (high peak power) TRAPATT (high efficiency)
Low power c.w. (<100mW) e.g. local oscillators intruder alarms	Either IMPATT or Gunn diode in many cases. Gunn diode has the advantage of lower noise and lower operating voltage
Medium power c.w. e.g. communication links (≈1W)	Either IMPATT or Gunn diode. IMPATT preferred for higher power and high efficiency, Gunn device for lower noise
High frequency applications (>40GHz) e.g. communication links, parametric amplifier pumps, etc.	IMPATT for high power and high frequency. Gunn diode when the noise performance is more important than high power for frequencies up to 60 GHz

these sources can be used where high powers are required, and the diode is well suited to phased array combinations because it can be operated in an amplifier mode. In this configuration the radar beam can be steered electronically by varying the phase of each element in the array.

The pulsed Gunn-effect device is particularly suited to applications requiring very short pulses, down to 1ns duration, and operates up to much higher frequencies than the TRAPATT. It is undergoing increasing exploitation in the field of miniature radars for both military and civil applications where its simplicity of use is a great advantage.

The IMPATT oscillator is generally preferred to the Gunn diode in c.w. applications requiring high power and/or high efficiency. Examples of these are free-space microwave communication links and trunk waveguide communications at millimetre wave frequencies. At frequencies above about 70GHz the IMPATT diode is the only solid state microwave source available and is finding applications as pump sources in parametric amplifiers, high frequency communication systems and high definition radar and imaging systems.

The principal disadvantages of the IMPATT in comparison with the Gunn diode are the noise performance and the high bias voltage. The IMPATT and TRAPATT diodes are fundamentally noisier than the Gunn diode and this precludes their use for certain applications. The noise originates in the avalanche multiplication process which produces a jitter in the current pulse from cycle to cycle under large signal conditions. Cavity control is not sufficient to completely overcome this problem. At a given frequency, the bias voltage on the c.w. Gunn diode is considerably less than the bias required on an IMPATT oscillator and this favours the Gunn diode in airborne or other similar applications where power supply voltages are limited. The table below lists some of the current applications for solid state devices. In principle, any of the devices (both

pulsed and c.w.) can be used for these systems but the Gunn effect device has found the widest use. Of these systems, the intruder alarm has made by far the biggest impact to date and is discussed below.

Military (also civil variants)	Industrial	Domestic and commercial
	Small movement detection	Intruder alarms
Electronic counter measures	Dimensional measurements	Satellite broadcasting
Missile guidance systems	Beam braking system	Small boat radars
Missile fuses	Proximity detection	Collision avoidance radars
Instrument landing systems	Velocity, flow, rotational measurement	Anti shop-lifting systems
Transponders Navigation beacons Altimeters	Vehicle and baggage identification	Distance measurement (tellurometry) Telemetry
Secure communications Ship docking radars Perimeter defence Man-pack radars Range measurement		Educational equipment

Intruder alarms

If an object moves in a microwave beam, a small amount of Doppler shifted radiation will be reflected from it. This Doppler shift can be detected, amplified and used to trigger an alarm. Several requirements dictate the features of the final system. To obtain a high Doppler signal the carrier frequency should be as high as possible, consistent with allocated frequencies. Two of the bands in use in Britain are at 10.687GHz ± 12.5 MHz and 13.7 GHz ± 300MHz. Overseas, other frequencies around the X-band region are in use. For an X-band system,

Doppler frequencies of interest, generated by an intruder, usually lie in the region of 10 to 100 Hz. For instance, a man moving at 3 m.p.h. will generate a Doppler frequency of about 90Hz, as given by the formula $f = 2 \times \text{velocity of the target} \times \text{frequency of radiation} / \text{velocity of light}$. Some of the requirements on the transmitter for such a system are therefore:

1. The device must operate in the X- or J-band region generating perhaps 10-20mW – usually adequate for most applications with ranges up to about 100m.
2. The noise output must be as low as possible because this determines the safety factor in the system and hence the false alarm rate – a very important parameter as these systems are often linked by telephone to a police station or central monitoring point.
3. The devices must be long-lived.
4. The devices must be stable with regard to environmental changes such as temperature.
5. The device must be as low cost as possible consistent with the above and capable of giving reproducible performance for large quantities of devices.

A Gunn device mounted in a well-designed waveguide cavity satisfies all of these requirements. Other types of resonant circuit may be used e.g. two potentially attractive systems are Gunn devices mounted in either microstrip circuits or lumped circuits. These are extremely competitive with regard to size and perhaps cost but cannot compare with a waveguide cavity with respect to noise output and stability. This is a direct result of the low Q-factor of these systems compared with waveguides. A typical waveguide cavity could be expected to have a loaded Q-factor of around 500 whereas the corresponding figure for a microstrip circuit would be around 20. These systems would thus seem suitable for very short range intruder alarms or some other system not requiring particularly good electrical performance.

Some means must be used to detect the reflected microwave signal. The most sensitive method is to use a separate detector diode mounted in a separate cavity. A small amount of non-shifted signal is fed into the detector and this is mixed with the reflected signal to produce the Doppler signal. An amplifier of modest gain (10,000) is then used to give reasonable signal levels after which some form of signal processing circuit is used to reduce false alarm rates by making the system less susceptible to triggering from spurious objects such as flapping curtains, falling leaves, etc. A diagram of such a system is shown in Fig. 7.

A system with somewhat reduced performance, but which is simpler and cheaper, utilises the Gunn device itself as the detector element. This is done by inserting a reasonably large resistor between the Gunn diode and the

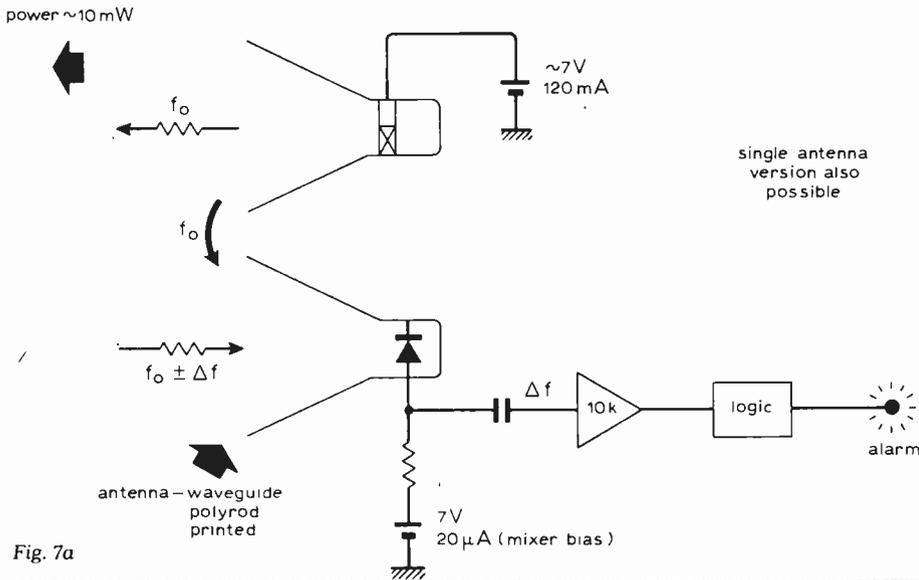


Fig. 7a

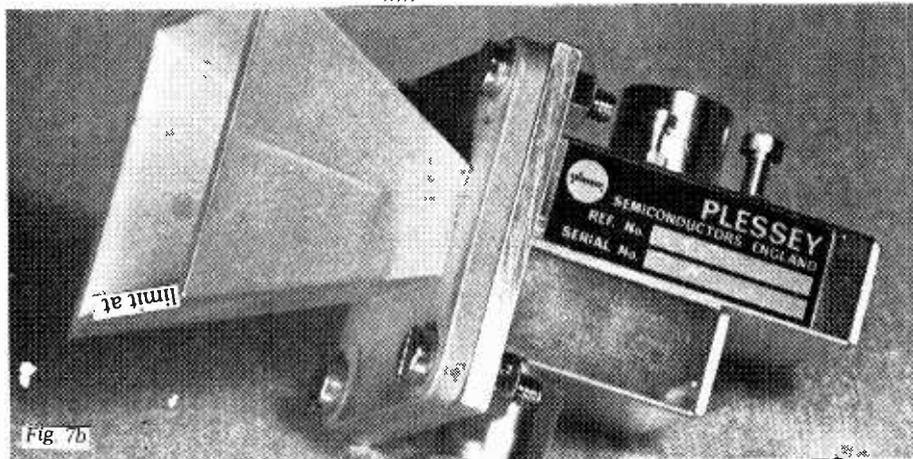


Fig. 7(b) Typical transmit/receive module— normally used for ranges from 10 to 100m.

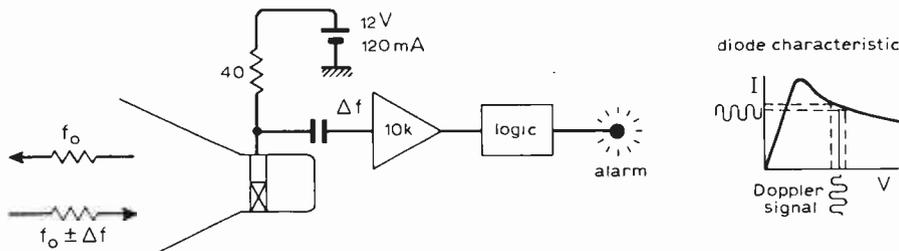


Fig. 8. Self-oscillating mixer alarm system. Due to a higher noise level and small signal from a moving object the circuit is only suitable for up to 10m.

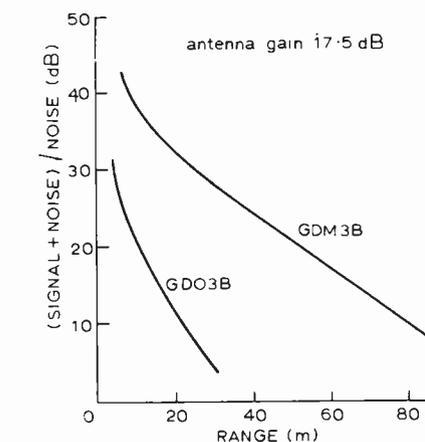
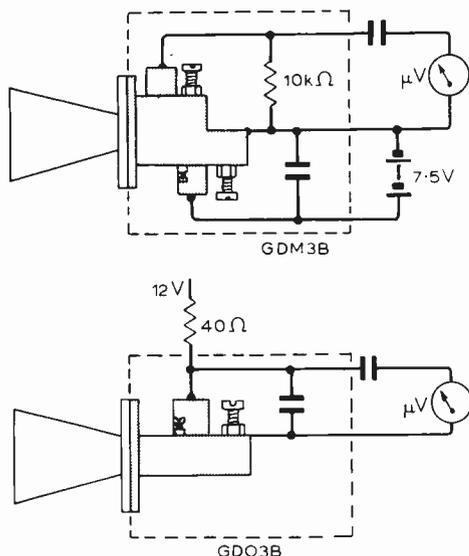


Fig. 9. (Signal + noise) / noise versus range of a self-oscillating mixer system and a separate-detector type using a man as the target, and the circuits used to obtain the range data.

constant voltage power supply. Any reflected signals modify the r.f. fields in the cavity and modulate the current through the diode at the Doppler frequency. Because of the series resistor this is detected as a voltage fluctuation at the diode terminals. There are several requirements for such a self-mixing system:

1. The cavity Q-factor must be high to produce a large r.f. field across the diode from the reflected signals, and therefore modulate the current.
2. The Gunn device must have a large differential negative current voltage characteristic as this parameter determines the output.
3. The system noise is now determined by current fluctuations through the diode which must be minimised.

A waveguide cavity satisfies the first point and the n+ contact Gunn diode scores over the metal contact diode for the second and third points. A diagram of such a self-oscillating mixer system is shown in Fig. 8. The electronic circuitry is virtually identical to the first system, but has a somewhat higher noise level and produces a smaller signal from a given object. It is therefore, usable only for fairly short range systems of up to 10m, depending upon the antenna used. Shown in Fig. 9. is the (signal + noise)/noise output from the two types of system described as a function of range, using a man (radar cross section $\approx 0.5m^2$) as the target. The signal processing circuit can be as complex as the system allows. The circuit will usually include a notch filter to overcome problems of interference from fluorescent lights, and some form of pulse counting circuit so that several cycles of Doppler signal must be detected before an alarm is generated. This will reduce false alarms caused by spuriously generated signals of short duration. More sophisticated alarms use pattern recognition techniques so that they only respond to the characteristic return signal from a man. Intruder alarms using the microwave principles detailed above have been produced commercially in the U.K. since about 1968 and have now reached a very high level of manufacture. In Europe and the U.S.A. the commercial exploitation is roughly equivalent to that in the U.K. about two years ago.

Small radars utilising Gunn devices

The situation with pulsed Gunn devices is similar to that of c.w. devices — new applications rather than replacing existing devices — as the power levels are limited to a few tens of watts peak. Powers of around 100W peak can be obtained by combining several devices. A typical pulsed Gunn application is in the field of small radars, either for battlefield surveillance and patrol duties, or for small marine radars. Typical ranges are usually around 2-5km. A diagram of one type of microwave system in use in such a

radar is shown in Fig. 10. The pulsed Gunn device is usually mounted in a waveguide cavity, the local oscillator device usually in a coaxial cavity incorporating a varactor diode which enables the frequency to be controlled electronically. This is used to maintain a constant i.f. over all operating conditions which reduces the bandwidth limitation on the i.f. amplifier. A complete radar system can be made small enough to be held and used in one hand. The information obtained by the radar may be given in the form of an audio tone, supplemented by a visual range indication. A photograph of a unit developed by the Royal Radar Establishment is shown in Fig. 11. In the case of marine radar the information may be displayed on a conventional cathode ray tube.

To date, the pulse devices are not in as common use as c.w. devices and most systems using them are of military origin. The potential market is immense, for instance, if a radar with the advantages of simplicity, small size and reliability could be made for a reasonable cost, the market could be in excess of 100,000 units. To a large extent the pulsed devices are analogues to the laser — a solution in search of a problem.

Acknowledgement

The author would like to thank Mr G. Gibbons, of the Allen Clark Research Centre, for his invaluable help in preparing this manuscript, and the directors of the Plessey Company Limited for permission to publish the article.

Further reading

1. *Transferred Electron Devices* by P. J. Bulman, G. S. Hobson and B. C. Taylor. Academic Press 1972.
2. M. W. Hosking. Realm of microwaves 7— Solid state oscillators, *Wireless World* February 1973.



Fig. 11. Small portable radar torch (SPRAT) in use. Photograph by courtesy of the Royal Radar Establishment who developed the unit.

3. *Avalanche Diode Microwave Oscillators* by G. Gibbons. Clarendon Press 1973.
4. R. L. Johnston, B. C. DeLoach and G. B. Cohen A silicon diode microwave oscillator. *Bell Syst. Tech. J.*, vol. 44, February 1965, pp. 369-372.
5. W. T. Read. A proposed high frequency negative resistance diode. *Bell Syst. Tech. J.*, vol. 37, March 1958, pp. 401-446.
6. H. J. Prager, K. K. N. Chang and S. Weisbrod. High-power high efficiency silicon avalanche diodes at ultra high frequencies. *Proc. IEEE (Lett)* vol. 55, April 1967, pp. 586-587.
7. R. L. Johnston, D. L. Scharfetter and D. J. Bartelink. High-efficiency oscillations in germanium avalanche diodes below the transit time frequency. *Proc. IEEE (Lett)* vol. 56 September 1968, pp. 1611-1613.


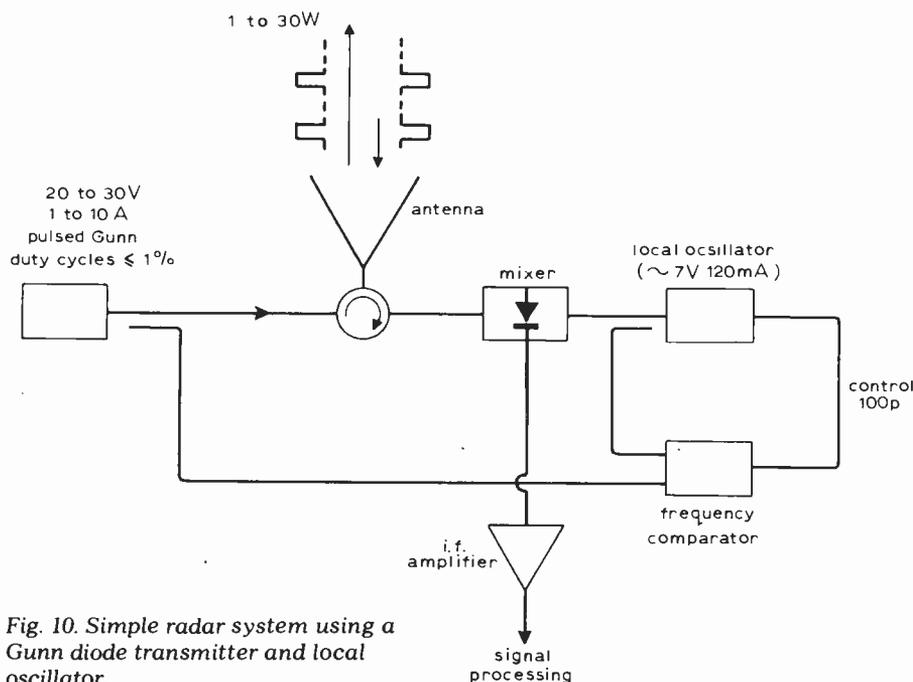
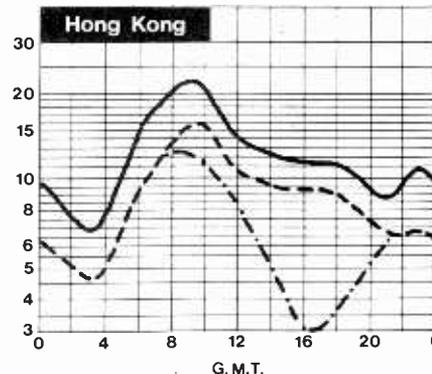
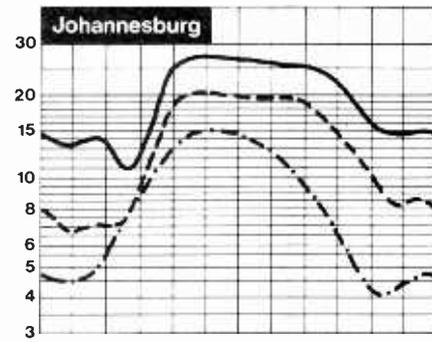
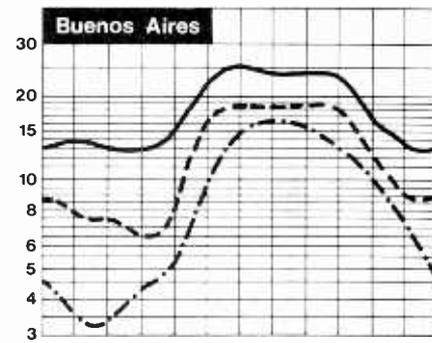



Fig. 10. Simple radar system using a Gunn diode transmitter and local oscillator.

HF predictions

The pattern of magnetic activity is now rather erratic and it is no longer possible to predict disturbed periods one or two months ahead with any confidence. From February 1974 until April 1975 there were two groups of days which were disturbed every solar rotation (27 days). That pattern continued until November 1975 but with the number of disturbed days in each group becoming fewer and fewer. Since August 1975 a new group has built up and its recurrence dates are around January 23 and February 19. Comparison with previous sunspot minimum periods suggests however that this new group will not persist and more notably that the next two years will have a minimum of magnetic and ionospheric disturbances.

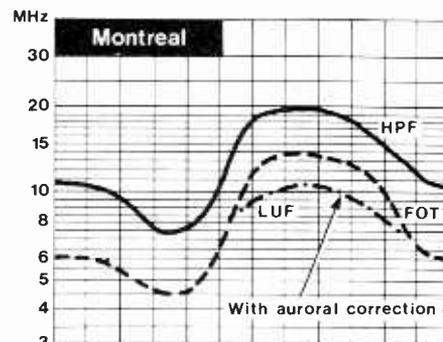

'Phone-in Programme

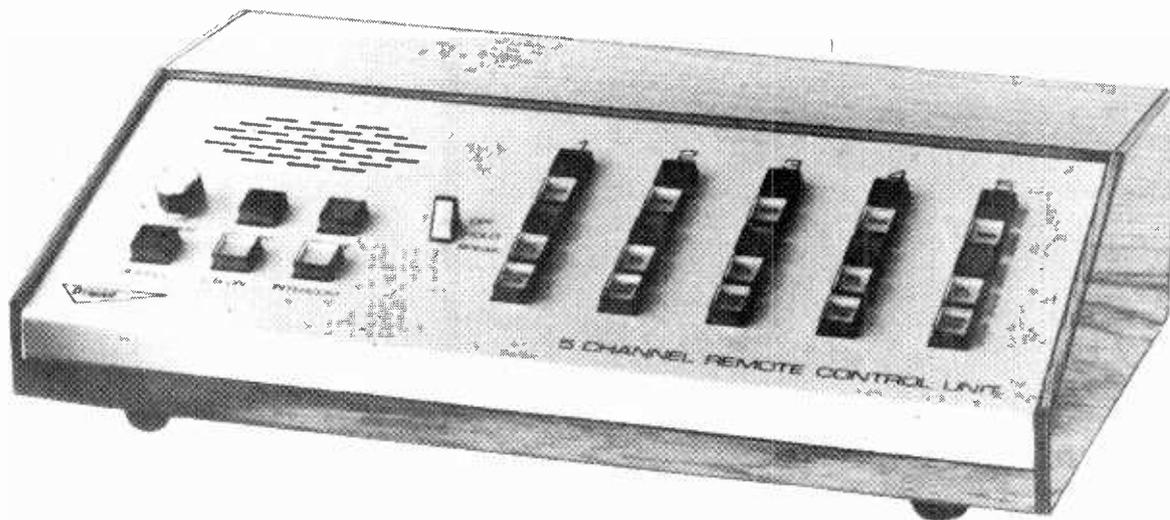

**When you can reach them. And they can reach you.
Any time. You've got a Dymar system.**

Computer controlled VHF radiotelephone network. Sounds great. The coming thing. At Dymar it's come! And that's the Dymar difference

Dymar designs systems that take all the local conditions into account. Terrain. Geographical distribution of the labour and the customers available to the user. Emergency situation control. Channel congestion. The lot.

Dymar does it with common frequency coverage using quasi-synchronous transmitters. With a CCIR compatible selective calling system. With automatic signal level selection. With computer control of signal routing.

Tomorrow's systems today. It's what you'd expect from a company 100% devoted to the radiotelephone business... and nothing else.

Discover the Dymar difference. Make contacting Dymar part of today's programme

DYMAR

the name in radiotelephone systems

Dymar Electronics Limited, Colonial Way, Radlett Road, Watford,
Herts WD2 4LA. Tel: Watford 37321. Telex: 923035
Cables: Dymar Watford

WW-013 FOR FURTHER DETAILS

The Sinclair DM2 Multimeter.

Comprehensive. Accurate. Portable.

And really rugged.

Yet only £59. (PLUS VAT)



State-of-the-art circuit design, incorporating high-quality components, has resulted in a professional, $3\frac{1}{2}$ digit instrument of outstanding performance and reliability at a realistic price.

A custom-designed MOS LSI digital processing IC controls the auto-polarity dual-slope-integration A to D converter. The circuit built around this IC uses a MOSFET op-amp input buffer with 0.1% metal-film resistors. The result is excellent accuracy and stability with a very high basic input impedance.

The instrument reads to ± 1999 and has a basic accuracy on the 1 V DC range of $0.3\% \pm 1$ digit. Four 8 mm LED displays provide excellent legibility and angle of view. Battery operation allows complete independence of mains supply.

The Sinclair DM2 has all the capability you need. Just take a look at its features and compare them with higher-priced multimeters. You'll find the DM2 is their equal in virtually everything – except price!

Features of the Sinclair DM2

5 functions giving 22 ranges

DC volts – 1 mV to 1000 V
AC volts – 1 mV to 500 V
DC current – 0.1 μ A to 1 A
AC current – 1 μ A to 1 A
Resistance – 1 Ω to 20 M Ω

Easy to use

Automatic polarity, bush-button selection for all ranges and modes from a single input terminal pair.

Easy to read

Big, bright 8 mm LED display gives a quick, clear reading.

$3\frac{1}{2}$ digit display

Display reads from 000 to 1999.

Overload indicator.

Protected

Separate fuses for current and resistance circuits.

Accurate

Dual slope integration. High stability.

Rugged construction

Tough metal casing takes the roughest treatment – try standing on it!

Two power sources

Supplied with a 9 V battery, giving 60-hour typical life. Mains adaptor also available.


Portable

Weighs only 3.5 lb approx, including battery. Measures only 2 in x 9 in x 6 in approx.


Optional extras

Mains adaptor – £3.19 inc VAT. Carrying case – £5.40 inc VAT.


12-month no-quibble guarantee

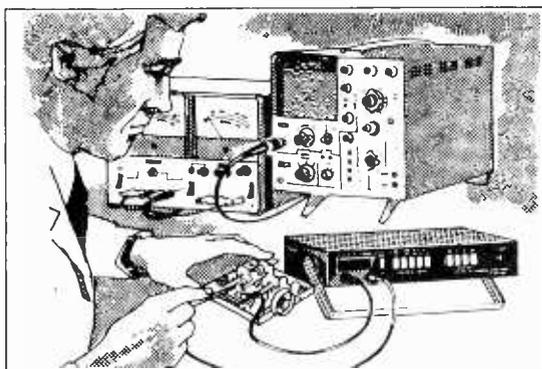

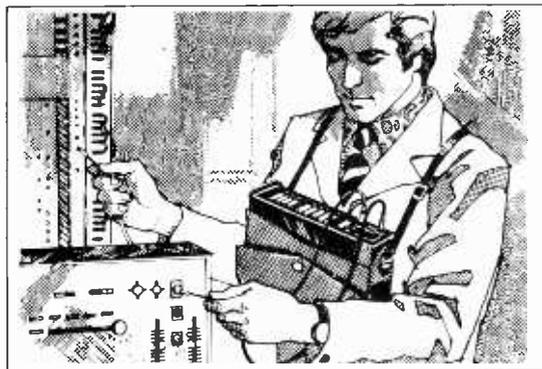Use it in your laboratory. The DM2 sits rigidly on its combined carrying handle/stand.



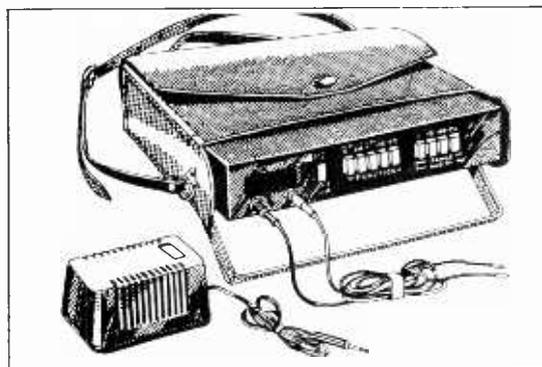Use it on the move. Keep the DM2 in its carrying case - it's always ready for use.



All you need to use the DM2... anywhere. Mains adaptor... carrying case... multimeter... you're ready for quick, efficient metering - whatever the situation.

Take advantage of this money-back, no-risk offer today

Test the Sinclair DM2 for yourself. Simply send us a cheque, your Access/Barclaycard number, or an official company order, with the coupon below. And in the unlikely event you find it's not what you need, return it to us within 10 days and we'll refund your money in full.

Interested in a quantity discount? Use the coupon to get details of prices on 5 or more instruments.

**Sinclair Radionics Ltd,
London Road, St Ives, Huntingdon,
Cambs., PE17 4HJ.**

Tel: St Ives (0480) 64646.
VAT Registration No: 213 8170 88.



The Sinclair DM2 Multimeter: full technical story

DC Volts Range	Accuracy	Input Impedance	Resolution
1 V	0.3% ± 1 Digit	> 100 MΩ	1 mV
10 V	0.5% ± 1 "	10 MΩ	10 mV
100 V	0.5% ± 1 "	10 MΩ	100 mV
1000 V	0.5% ± 1 "	10 MΩ	1 V

*Maximum overload - 350 V on 1 V range
1000 V on all other ranges.*

AC Volts Range	Accuracy	Input Impedance	Frequency Range
1 V	1.0% ± 2 Digits	10 MΩ/40 pF	20 Hz-3 KHz
10 V	1.0% ± 2 "	10 MΩ/40 pF	20 Hz-1 KHz
100 V	2.0% ± 2 "	10 MΩ/40 pF	20 Hz-200 Hz
1000 V	2.0% ± 2 "	10 MΩ/40 pF	20 Hz-200 Hz

*Maximum overload - 300 V on 1 V range
500 V on all other ranges.*

DC Current Range	Accuracy	Input Impedance	Resolution
100 μA	2.0% ± 1 Digit	10 KΩ	100 nA
1 mA	0.8% ± 1 "	1 KΩ	1 μA
10 mA	0.8% ± 1 "	100 Ω	10 μA
100 mA	0.8% ± 1 "	10 Ω	100 μA
1000 mA	2.0% ± 1 "	1 Ω	1 mA

Maximum overload - 1 A (fused).

AC Current Range	Accuracy	Frequency Range
1 mA	1.5% ± 2 Digits	20 Hz-3 KHz
10 mA	1.5% ± 2 "	20 Hz-1 KHz
100 mA	1.5% ± 2 "	20 Hz-1 KHz
1000 mA	2.0% ± 2 "	20 Hz-500 Hz

Maximum overload - 1 A (fused).

Resistance Range	Accuracy	Measuring Current
1 KΩ	1.0% ± 1 Digit	1 mA
10 KΩ	1.0% ± 1 "	100 μA
100 KΩ	1.0% ± 1 "	10 μA
1000 KΩ	1.0% ± 1 "	1 μA
10 MΩ	2.0% ± 1 "	100 nA

Overload protection - 50 mA (fused).

Readers outside the UK, please write for details of your local distributor to:

**Sinclair Equipment International Ltd,
33 Beauchamp Place, London SW1 1NU.**

To: Sinclair Radionics Ltd, FREEPOST, St Ives, Huntingdon, Cambs., PE17 4BR.

Please send me:

..... Multimeters @ £63.72 inc VAT. *I enclose a cheque for £

..... Mains adaptors @ £3.19 inc VAT. *My Access/Barclaycard number:

..... Carrying cases @ £5.40 inc VAT.

I am interested in 5 or more multimeters. *I enclose an official company order - signed and dated.

..... Please send details of quantity discounts. *Please complete or delete as applicable.

Name _____

Address _____

Please print

FREEPOST - no stamp needed with address above. **WW 276**

DM6

How B&W pioneered the measurement of phase/impulse response

These measurements and oscillograms are, as far as we know, the first to be published anywhere in the world. They relate to two vital aspects of loudspeaker performance that have not been previously assessed: phase response and impulse response.


This breakthrough is a result of a major investment by B&W in entirely new measuring techniques and instruments in an area where accurate quantifications were previously thought to be prohibitively complex.

It is well known that 'square' or impulse waves are made up of a fundamental sine wave plus a harmonic series. Equally well-known is the fact that the amplitude of these harmonics must not only be correct but must also arrive in the correct phase or time if the desired wave shape is to be reproduced. It is this correction for phase or time in the design of the units, the crossover network and the physical placement of the units which enables the DM6 dramatically to improve the square or impulse waveform performance as set out below.

The 'third octave' room measurement is yet another meaningful method in assessing how well the balance of the DM6 conforms to the idealized curve shown.

Response to \sin^2 pulse of 0.33 ms half-amplitude duration.

DM6

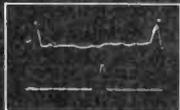


Full range electrostatic




Normal 3-way dynamic system.



Impulse response of DM6.

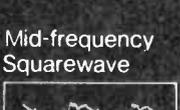


Mid-frequency Squarewave

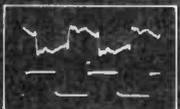


50 μ s pulse at 5 ms interval.




50 μ s pulse at 10 ms interval.

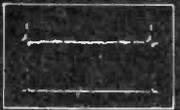

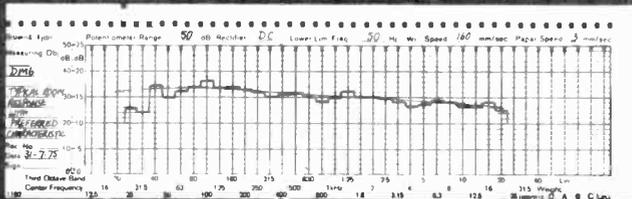
1/3rd Octave room response of system and optimum characteristic (from recommendation of "Relevant Hi-Fi Test at Home," Henning Møller, B&K Application Note 14 - 114).




Phase Response on-axis at 3 metres.

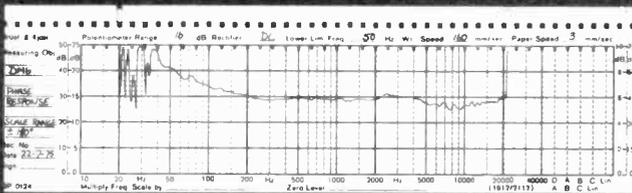

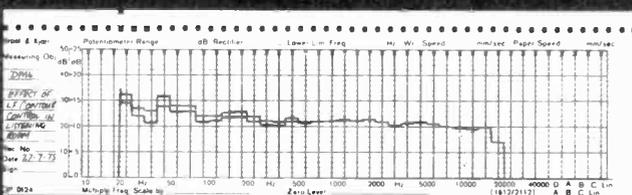
L. F. Contour Control Operating in listening environment.



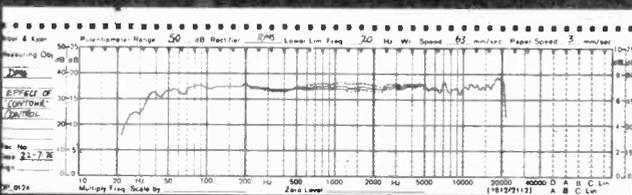
Contour Control operating between 500 Hz and 5 kHz.



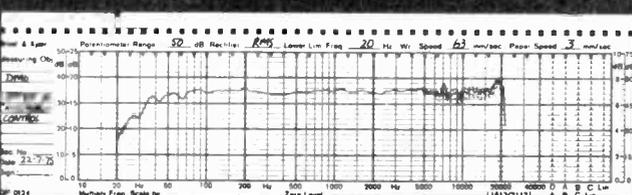H.F. Energy Control operating at frequencies above 5 kHz



New B&W DM6

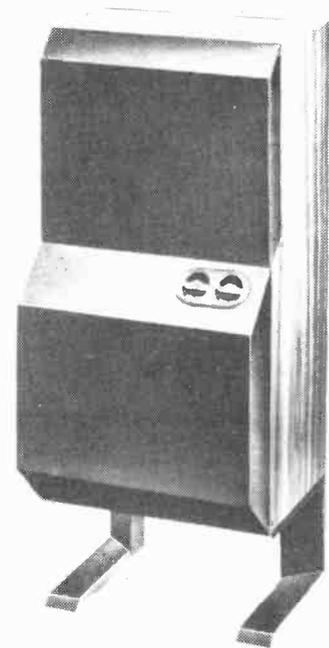

Now it can be told

It took a three year development programme and a major breakthrough to produce Britain's first linear phase dynamic speaker system.

B&W DM6 is the result - a system reproducing sound with transient accuracy usually achieved by only the best electrostatic designs.

DM6 incorporates three entirely new drive units developed at the B&W factory.

The bass unit achieves a level of performance that would normally be associated with a cabinet of much larger capacity than DM6's 51 litres.

The midrange unit employs totally new technology and materials. The cone assembly consists of a matrix of aromatic polyamide fibres formed and impregnated with critical quantities of PVA (patents applied for) and shows significant improvements in transient and conventional measurements.

A new high frequency transducer also shows improvements equivalent to those achieved in the midrange unit and linearly extends frequency response to 40 kHz.

All three units are integrated into a linear phase system by mounting in a stepped arrangement, after skilful shaping of the front baffle to allow for the different arrival times of the various components. And when a series of linear impedance first order filter configurations are introduced, new levels of linear phase and amplitude characteristics are achieved.

The cabinet is constructed to similar exacting standards and the complete system visually matched by one of this country's leading industrial designers. All DM6 loudspeaker systems carry a five year guarantee.

If you want to see and hear the new DM6, contact your B&W authorised dealer. Or drop a line to us and we'll send you detailed literature.

B&W Loudspeakers Ltd. (Room 6) Meadow Road
Worthing West Sussex BN11 2RX Tel. (0903) 205611

B&W DM is the registered trade mark of B&W Loudspeakers Ltd

WW-083 FOR FURTHER DETAILS



B&W Loudspeakers

Electronic circuit calculations simplified

7 — Active devices

by S. W. Amos, B.Sc., M.I.E.E.

Previous articles in this series have been devoted chiefly to calculations on inductors, capacitors and resistors and on combinations of these. Transistors and valves have been mentioned but the emphasis has been on methods of calculating the values of L , C and R necessary to give the required circuit performance. This article is devoted to calculations on the performance of the active devices themselves.

There are three main types of active device: the thermionic valve, the bipolar transistor and the field-effect transistor. Many of the properties of the f.e.t. are similar to those of the valve and it is possible to regard the f.e.t. as a valve without a filament or heater. Indeed f.e.t.s are now being manufactured with characteristics very similar to those of certain valves so that these f.e.t.s can be used as direct replacements for valves in old equipments: such f.e.t.s are termed fetrons. Thus we are concerned only with two types of active device: the bipolar transistor and the f.e.t. We will deal with them in that order.

Basic common-emitter amplifier.

Consider the simple common-emitter amplifier shown in Fig 1. The calculation of values of R_c suitable for a current output and a voltage output were given in Part 1: if the supply voltage is 9 and the mean collector current 1mA, R_c can be 8 kilohms for a current output and 4 kilohms for a voltage output. The problem is to calculate a suitable value for R_b . If β is the common-emitter current amplification factor (h_{fe}), then the mean value of the base current I_b is I_c/β . If β is 100 then I_b is 10 μ A. If the transistor is a silicon type there is a drop of 0.7V across the base-emitter junction and the voltage across R_b is therefore 8.3. Thus from Ohm's law:

$$R_b = \frac{8.3}{10 \times 10^{-6}} = 830 \text{ kilohms}$$

The calculation of a suitable value for C_b is dealt with in Part 5.

Bipolar transistors are inherently current-operated devices i.e. the curve relating collector current with base current is almost linear. Thus the amplifier of Fig. 1 would give a satis-

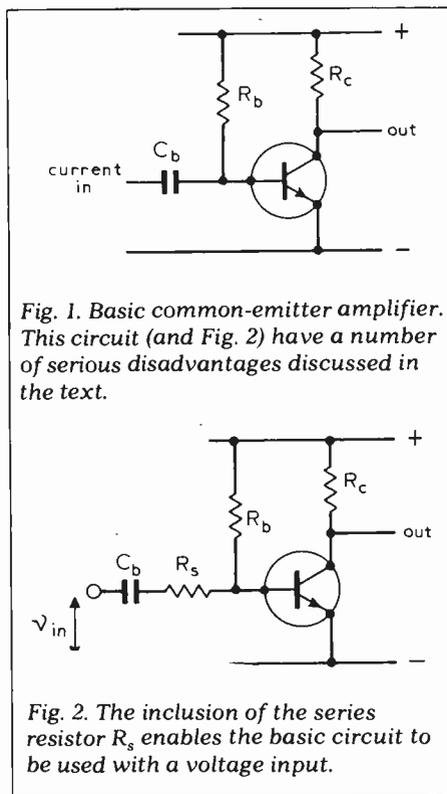


Fig. 1. Basic common-emitter amplifier. This circuit (and Fig. 2) have a number of serious disadvantages discussed in the text.

Fig. 2. The inclusion of the series resistor R_s enables the basic circuit to be used with a voltage input.

factory performance for a current input. Provided R_c is large compared with the external load most of the signal-frequency collector current enters the external load and the current gain of the amplifier is only slightly less than β .

If, however, the performance of the circuit of Fig. 1 is measured with respect to the voltage applied between base and emitter, it is far from satisfactory: in fact the input-output characteristic is exponential in shape. The voltage gain is given by

$$\frac{v_{out}}{v_{in}} = g_m R_c \tag{1}$$

The mutual conductance, g_m , of a bipolar transistor is generally much greater than that of a valve or f.e.t. and therefore permits very high values of voltage gain. For a bipolar transistor g_m is approximately 40mA/V for every milliampère of collector current. Thus if the mean collector current is 1mA, g_m is 40mA/V and if R_c is 5

kilohms, the voltage gain is given by

$$\frac{v_{out}}{v_{in}} = 40 \times 10^{-3} \times 5 \times 10^3 = 200$$

This high gain is, however, accompanied by such poor linearity that the amplifier is unlikely to be used in practice except for signals of very small amplitude. The non-linearity is due to the variations in input resistance with input-signal amplitude and can be reduced by using a series resistor R_s (Fig. 2) large compared with the average value of input resistance so that input-resistance variations are swamped. For 1mA mean collector current an average value of input resistance is 2 kilohms so that a suitable value for R_s is 20 kilohms. The input current is now given approximately by v_{in}/R_s and is magnified β times in the transistor, giving an output current of $\beta v_{in}/R_s$ and an output voltage of $\beta v_{in} R_c/R_s$. Thus the voltage gain for the circuit of Fig. 2 is given by

$$\frac{v_{out}}{v_{in}} = \frac{\beta R_c}{R_s} \tag{2}$$

For the typical practical values $\beta = 100$, $R_c = 5$ kilohms and $R_s = 20$ kilohms

$$\frac{v_{out}}{v_{in}} = \frac{100 \times 5}{20} = 25$$

a more modest gain but, of course, with a reasonable degree of linearity. It is significant that this gain and current gain of the circuit of Fig. 1 are both directly proportional to β .

Disadvantages of the basic amplifier. In practical versions of the circuits of Figs. 1 and 2 it is generally necessary to use a preset resistor for R_b and to adjust it empirically to give the required mean value of collector current. This is because the precise value of β is unlikely to be known. There is normally a tolerance of $\pm 50\%$ on the average value quoted by the manufacturer and therefore, for a nominal β of 100, values as low as 50 and as high as 150 are possible. This is a ratio of 3 : 1 and thus the value of R_b can also lie within a resistance range of 3 : 1. β also measures the gain of the circuit and this, too, can have any

value within a range of 3 : 1. A third disadvantage of this basic circuit is that it has no means of stabilising the mean collector current. Thus the current could increase (for example as a result of a rise in temperature) and, for a germanium transistor, the increase could be sufficient to prevent normal operation of the circuit. Although it is possible to obtain a satisfactory performance from individual examples of the circuits of Figs. 1 and 2, these circuits are quite unsuitable where a number of amplifiers with similar performance are required. For mass production it is essential to have a circuit which will give a desired value of mean collector current, within a small tolerance, in spite of variations in β due to manufacturing spreads or due to temperature variations: this is known as d.c. stabilisation of the operating point. It is equally essential, of course, that all circuits should give the same signal-frequency performance in spite of manufacturing spreads and temperature variations. These two requirements are achieved by the use of negative feedback: a d.c. negative feedback circuit ensures that the mean collector current is determined by the values of passive components within the feedback loop and is thus independent of the transistor parameters. An a.c. negative feedback circuit similarly ensures that the gain and other aspects of the signal-frequency performance are also determined by passive components within a such a loop. Negative feedback has other advantages: for example it reduces distortion, so linearising the input-output characteristic and it makes possible desired values of input or output resistance. We shall now examine the negative feedback circuits commonly used and will show how d.c. stability and signal-frequency performance are related to the constants of the feedback loop.

D.c. stability. D.c. stability is ensured by using a negative feedback circuit in which any change in mean collector current produces a correcting change in base current. The collector current is passed through a resistor and the voltage generated across this is used as the source of base bias. Two commonly-used circuits are shown in Fig. 3. In (a) I_c flows through R_c and the voltage across R_c is used to drive current, through R_b , to the base. This is another way of saying that I_c splits at the junction of R_c and R_b ; the current so fed back to the base is given by $I_c R_c / (R_c + R_b)$.

Let us attribute unwanted variations in I_c to a fictitious external input to the base of the transistor. This is a useful assumption because from it we can deduce that the factor by which negative feedback reduces unwanted variations in I_c is also the factor by which the d.c. gain of the transistor is reduced. This factor can easily be assessed as follows.

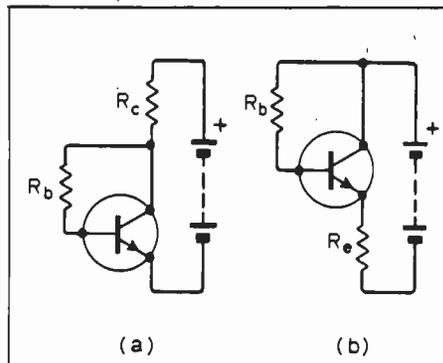


Fig. 3. Two fundamental methods of applying negative feedback to a bipolar transistor.

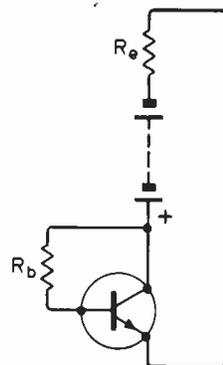


Fig. 4. Fig. 3 (b) redrawn to show its similarity to Fig. 3 (a).

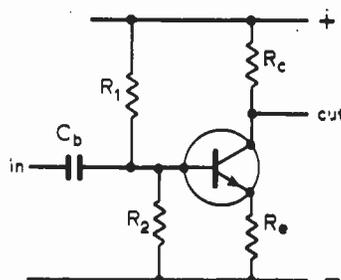


Fig. 5. Method of d.c. stabilising a transistor by a potential divider and emitter resistor.

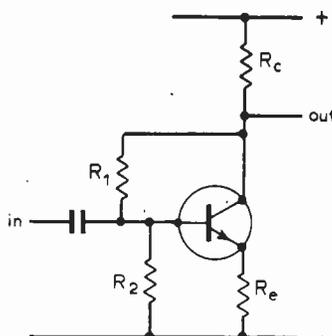


Fig. 6. Stabilising circuit based on a combination of the circuits of Figs. 3 (a) and (b).

In the absence of feedback a base current I_b gives rise to a collector current βI_b . The feedback current, as just shown, is a fraction of this and is given by $\beta I_b R_c / (R_c + R_b)$. As a result of this feedback the input current now required to give the same output current as before feedback was applied is given by

$$I_b + \beta I_b R_c / (R_c + R_b)$$

Formerly the input current was simply I_b . Thus the factor by which the d.c. gain of the transistor is reduced by feedback is

$$\frac{1}{1 + \beta R_c / (R_c + R_b)}$$

and this is a direct measure of the factor by which variations in mean collector current are reduced by feedback. We can call this fraction the stability factor. Thus

$$\text{stability factor} = \frac{1}{1 + \beta R_c / (R_c + R_b)}$$

Often R_b is large compared with R_c and we can say

$$\text{stability factor} = \frac{1}{1 + \beta R_c / R_b}$$

The smaller the value of this fraction, the better is the d.c. stability of the circuit. For good stability $\beta R_c / R_b$ must be large compared with unity and the stability factor is then given approximately by the simple expression

$$\text{stability factor} = \frac{R_b}{\beta R_c} \tag{4}$$

At first sight the circuit of Fig. 3 (b) appears quite different from that of Fig. 3 (a). But if we redraw Fig. 3 (b) as in Fig. 4 we can see that the only way in which it differs from Fig. 3 (a) is in the position of the battery and as the battery is assumed to have negligible d.c. resistance this can have no effect on the behaviour of the circuit. Thus for the same values of R_b and provided R_e equals R_c , the two circuits of Fig. 3 have identical stability factors.

Practical circuits are usually based on Fig. 3 (b). There is usually little freedom in choosing a value for R_e because this is limited by the need to ensure a reasonable value of emitter current. Thus to achieve good stability R_b must be kept small. In practice the base of the transistor is often connected to a potential divider $R_1 R_2$ as shown in Fig. 5 and R_b is then equal to the resistance of R_1 and R_2 in parallel. R_1 and R_2 are thus made as small as possible consistent with a reasonable drain current from the supply. The calculation of suitable values for R_1 and R_2 is given in Part 1 where one of the numerical examples has the following values:

- $R_1 = 82$ kilohms;
- $R_2 = 30$ kilohms;
- $R_e = 2.3$ kilohms.

For this example the parallel resistance of R_1 and R_2 is 22 kilohms and substitution of this and $\beta = 100$ in expression (4) gives

$$\text{stability factor} = \frac{R_b}{\beta R_c} = \frac{22}{100 \times 2.3} = \frac{1}{10} \text{ approximately}$$

showing that variations in mean collector current are reduced to 1/10th of their unstabilised value e.g. a 50% increase in mean current is held, by this circuit, to 5%, a worthwhile improvement in stability.

Better d.c. stability can be achieved by combining the circuits of Figs. 3 (a) and (b). An example of such a combined circuit is given in Fig. 6 in which the base resistors are replaced by a potential divider R_1, R_2 fed from the collector (not from the supply rail as in Fig. 5). High stability is possible from this circuit because both R_c and R_e contribute towards the stabilising process and the stability factor is therefore given by

$$\text{stability factor} = \frac{R_b'}{\beta R_c'} \quad (5)$$

where

R_b' is the parallel resistance of R_1 and R_2
 R_c' is the sum of R_c and R_e .

The value of R_c' is fixed by the need to have an adequate value of collector current and a typical practical value is 5 kilohms. Let β be 100. From expression (5) the stability factor is now determined by R_b' which should be as small as possible to ensure high stability. In the circuit in the basic form shown in Fig. 6 it is unlikely that R_b' could be reduced below 20 kilohms: even this value of R_b' gives a stability factor of 1/25. There is, however, a two-transistor version of Fig. 6 which permits values of R_b' as low as 5 kilohms: this gives a stability factor of 0.01, an impressively low figure. This highly effective circuit is described later.

Signal-frequency performance. The two negative feedback circuits of Fig. 3 give d.c. feedback and, to be effective in stabilising mean collector current, reduce the d.c. gain of the transistor to a very low value. The negative feedback circuit, being purely resistive, also reduces the signal-frequency gain of the transistor to this same low figure. This reduction is, in general, undesirable and in Fig. 3 (a) can be eliminated by decoupling the mid-point of R_b to emitter but a simpler solution is to use the circuit of Fig. 3 (b) and to decouple R_e by a low-reactance capacitor. This leaves the d.c. stability unchanged and enables signal-frequency feedback to be applied by an independent negative feedback circuit.

It was shown that at d.c. Figs. 3 (a) and (b) are effectively the same circuit. This is not true at signal frequencies: this is shown in Fig. 7 which is a repeat

Fig. 7. A repeat of Fig. 3 but including input and output terminals to show that the circuits behave differently at signal frequencies.


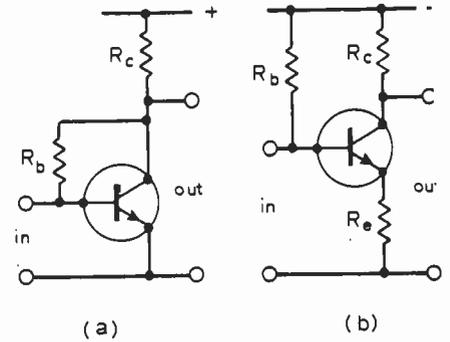


Fig. 8. A video amplifier based on the circuit of Fig. 7 (b).

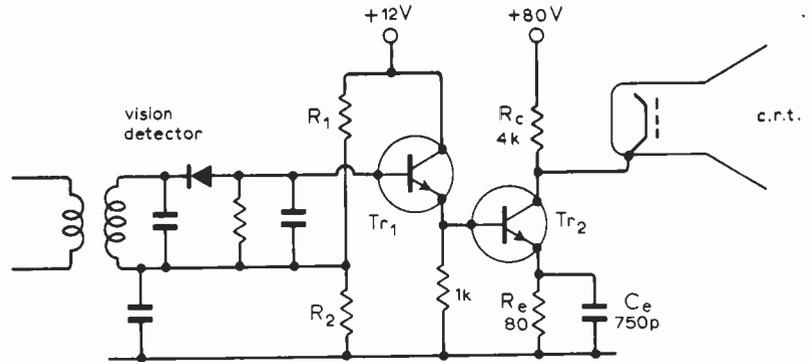

of Fig. 3 but includes input and output terminals. At (a) R_b returns to the base a feedback current proportional to the output voltage. Such feedback reduces both input resistance and output resistance, so making the circuit suitable for use with a current input and a voltage output. The ratio of these two quantities is, in fact, equal to R_b and is thus independent of the transistor parameters. Thus, for the circuit of Fig. 7 (a):

$$\frac{V_{out}}{i_{in}} = R_b \quad (6)$$

In Fig. 7 (b) R_e returns to the base-emitter circuit a voltage proportional to the emitter (and hence the collector) current. Such negative feedback increases both input resistance and output resistance, making this circuit suitable for use with a voltage input and a current output. The ratio of these two quantities is equal to $1/R_e$ and is thus independent of the transistor parameters. Thus, for the circuit of Fig. 7 (b):

$$\frac{i_{out}}{v_{in}} = \frac{1}{R_e} \quad (7)$$

Video amplifier for television receiver. As a numerical example suppose the amplifier of Fig. 7 (b) is used to drive the cathode of a picture tube in a television receiver. Suppose that the tube requires a video input of 70V peak-to-peak value. The value of R_c to use is determined by the total capacitance shunting R_c , say 15pF, and the upper frequency limit of the video band, say 5MHz. The reactance of 15pF at 5MHz is approximately 2 kilohms and, as explained in Part 5, if

R_c is also made 2 kilohms, the response will be 3dB down at 5MHz. If we make R_c 4 kilohms, the gain is doubled at low and middle video frequencies but the high-frequency loss is now 3dB at 2.5MHz and 7dB at 5MHz. This loss can, however, be offset by use of frequency-discriminating negative feedback and a value of 4 kilohms is suitable for R_c . If a video signal of 1.5V peak-to-peak is available from the vision detector to drive the amplifier then the amplifier requires a voltage gain of 70/1.5 i.e. approximately 50. The voltage gain of the amplifier is given by

$$\frac{v_{out}}{v_{in}} = \frac{R_c}{R_e}$$

which can readily be deduced from expression (7) by putting $i_{out} = v_{out}/R_c$. Thus

$$R_e = \frac{R_c}{50} = 80 \text{ ohms}$$

A common technique for maintaining the response at the upper end of the band is to shunt R_e by a capacitor which removes the negative feedback at high video frequencies. A simple way of determining the value of this capacitor is to equate the time constants in the collector and emitter circuits thus:

$$R_c C_c = R_e C_e$$

This gives

$$C_e = \frac{R_c}{R_e} C_c = 50 \times 16\text{pF} = 750\text{pF}$$

In a practical version of this amplifier provision must be made for ensuring d.c. stability and the obvious method is to use the 80-ohm emitter resistor in a

circuit of the type shown in Fig. 5 but the low value of R_c introduces difficulties. From expression (5) it is clear that if R_e is 80 ohms then R_b' must not be very great compared with this to achieve good stability. In fact if $R_b' = R_e$ the stability factor is $1/\beta$ which represents excellent stability. R_b' is the parallel resistance of the two arms of the potential divider and it would be impractical to make R_b' much less than 1 kilohm. A solution to this problem commonly adopted in television receivers is to interpose an emitter follower between the potential divider R_1R_2 and the base of the video amplifier as shown in Fig. 8, direct coupling being used throughout. The value of R_b' is now effectively the output resistance of the emitter follower: this depends on the resistance in the base circuit of the emitter follower but in this example is probably of the order of 80 ohms, so permitting excellent d.c. stability in the video amplifier.

The emitter follower is also of value at signal frequencies because its high input resistance minimises shunting of the diode load. Because of the direct coupling between the detector and the video amplifier it is possible to arrange the standing voltages so that the amplifier is biased to cut off by black-level signals. This has the advantage that the amplifier can be operated from a supply only slightly greater than the required video output: in this example an 80-V supply is adequate. The emitter follower and potential divider can be fed from a lower supply voltage e.g. 12V.

The values of R_1 and R_2 can be calculated in the following way. The output from the detector is almost zero for white-level signals. For such signals 70V must be developed across R_c and therefore 1.5V across R_e . If both transistors are silicon there is an offset voltage of 0.7 between each base and corresponding emitter. Thus the voltage across R_2 must be $(1.5 + 2 \times 0.7)$ i.e. 2.9V. If we assume a bleed current of 0.5mA in the potential divider then Ohm's law gives R_2 as 5.8 kilohms. If the potential divider supply is 12V then R_1 must be 18.2 kilohms. It would be an advantage to make R_1 or R_2 preset so that it can be adjusted to secure correct operating conditions in the video amplifier.

Two-stage voltage amplifier. The basic circuits of Fig. 7 can be combined to form a two-stage amplifier in two ways. If the first stage is of type (a) and the second stage of type (b), the resulting amplifier has a low input resistance and a high output resistance, making it suitable for current amplification. If, however, the first stage is of type (b) and the second stage of type (a), the resulting amplifier has a high input resistance and a low output resistance, making it suitable for voltage amplification. We will consider the design of such a voltage amplifier.

The basic form of the amplifier is

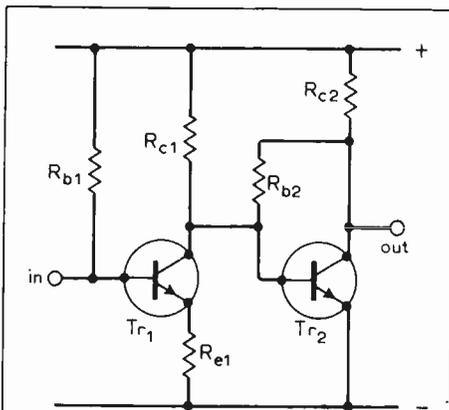


Fig. 9. Basic form of two-stage direct-coupled voltage amplifier.

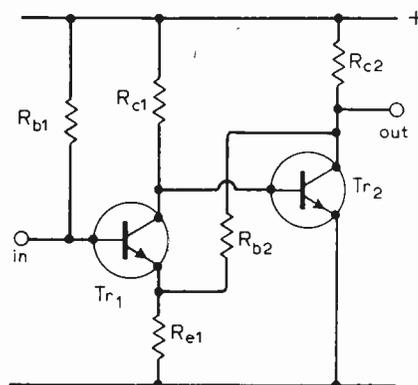


Fig. 10. This alteration to the position of R_{b2} makes little effect on the performance of the circuit.

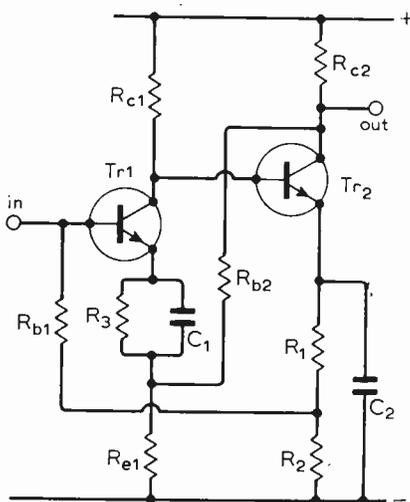


Fig. 11. Final form of the circuit of the two-stage voltage amplifier.

shown in Fig. 9 in which direct coupling is employed between the stages. The output current of Tr_1 is the input current of Tr_2 and by eliminating the terms in i between expressions (6) and (7) we have

$$\frac{v_{out}}{v_{in}} = \frac{R_{b2}}{R_{e1}} \dots \dots \dots (8)$$

It is more usual to connect R_{b2} to the emitter of Tr_1 than to the base of Tr_2 and

the circuit then has the form shown in Fig. 10. This change makes no fundamental difference to the performance of the amplifier because the feedback current injected into Tr_1 emitter by R_{b2} emerges from the collector and enters Tr_2 base with little loss. But it is clear from Fig. 10 that R_{b2} and R_{e1} constitute a potential divider across the amplifier output and so determine the voltage gain of the amplifier as mentioned in Part 1 and as indicated in expression (8). Signal-frequency feedback is thus provided by R_{b2} and R_{e1} . We now have to provide d.c. negative feedback to stabilise the mean collector currents of the two transistors.

It was mentioned earlier in this article that a most effective method of d.c. stabilisation is possible using a potential divider connected to the collector of the transistor, the base being fed from the tapping point. This method can readily be applied to the circuit of Fig. 10: all that is necessary is to put the potential divider R_1R_2 in the emitter circuit of Tr_2 and to return R_{b1} to the tapping point as shown in Fig. 11. D.c. stability then depends on the resistance in Tr_1 collector and emitter circuits and can be increased by the addition of R_3 in the emitter circuit. Decoupling capacitors C_1 and C_2 are required to eliminate the signal-frequency feedback which would otherwise result from R_1 , R_2 and R_3 . We will now calculate the values of the resistors required in a typical application of this circuit.

Before the calculations can be performed certain characteristics of the amplifier must be known or decided. For example suppose that the supply voltage is 15, that a voltage gain of 100 is required, that the amplifier must be capable of supplying an output signal of 3V amplitude and that the input resistance must be at least 50 kilohms. We must now decide the mean collector currents of the transistors. Here we may choose values giving maximum values of β or minimum noise. Let the current for Tr_1 be 0.3mA and for Tr_2 1mA. One more decision is necessary before calculation can begin and a convenient choice to make is that of Tr_2 emitter potential. Let us make this 6V. Ohm's law immediately gives the total emitter resistance for Tr_2 as 6 kilohms so that R_1 and R_2 can be 3 kilohms. To enable Tr_2 to deliver the required output voltage we can make R_{c2} 4 kilohms so that positive and negative collector voltage swings of 4V amplitude are possible. If Tr_2 is a silicon transistor its base potential is 6.7V, i.e. 0.7V above emitter potential. This is also Tr_1 collector potential. The voltage across R_{c1} is thus $(15 - 6.7)$, i.e. 8.3 and because the mean current is 0.3mA, Ohm's law gives the value of R_{c1} as 28 kilohms. If the voltage drop across R_{b1} due to base current is neglected, Tr_1 base potential is 3V. If Tr_1 is a silicon transistor its emitter potential is thus 2.3 V, giving the total emitter resistance as 8 kilohms. We can thus make R_3 7 kilohms and R_{e1} 1 kilohm. To

give the required voltage gain R_{b2} must be $100R_{e1}$ and is hence 100 kilohms.

The input resistance of the amplifier is made up of R_{b1} paralleled by the input resistance of Tr_1 which, by virtue of the feedback due to R_{b2} and R_{e1} , is very high. Thus the amplifier input resistance is effectively equal to R_{b1} which can be made 50 kilohms as required.

R_{e1} and R_{b2} determine the gain of the amplifier and should be narrow-tolerance components but this is not necessary for the other resistors provided that one of them (R_3 is suitable) is made preset so that it can be adjusted to secure correct operating conditions in the amplifier.

The stability factor for the amplifier is given by expression (5) in which R_c' is the sum of R_{c1} , R_{e1} , R_3 and R_{b1} . Substitution of these values and $\beta = 100$ gives the stability factor as 1/72 representing a very high degree of stability.

Field-effect transistors. Fig. 12 illustrates the simplest form of single-stage f.e.t. amplifier. The value of the load resistor R_d depends on whether an output current or voltage is required and can be calculated as described in Part 1. Bias is applied from a source of suitable voltage V_g via R_g and because an f.e.t. requires no gate current R_g can be made any value up to say 100 megohms without effect on the performance of the circuit. The ratio of output current to input voltage is the mutual conductance g_m of the transistor, one of the parameters quoted by the manufacturer: a typical value is 2mA/V, the same order as for a valve.

The voltage gain of the simple amplifier is given by

$$\frac{V_{out}}{V_{in}} = g_m R_d$$

and, as for the current output, is proportional to the value of g_m for the particular transistor used. The mean value of drain current also depends on the particular transistor used and can easily be so far from the desired value that the required performance cannot be obtained. Satisfactory results can be obtained from individual circuits of the type shown in Fig. 12 but to obtain them it is usually necessary to adjust the bias voltage. This difficulty stems from the fundamental property of the simple biasing circuit that it fixes the gate voltage and not the mean drain current or the mutual conductance.

Thus as for bipolar transistors practical f.e.t. circuits require a biasing circuit to give a desired value of mean drain current and d.c. negative feedback to maintain this current in spite of variations in transistor parameters. Signal-frequency feedback is also necessary to give the required signal-frequency performance and to maintain this in spite of variations in parameters.

As for bipolar transistors, enhancement-type f.e.t.s require a gate

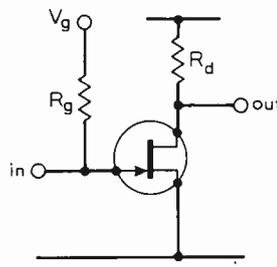


Fig. 12. Simplest type of f.e.t. amplifier which has a number of disadvantages.

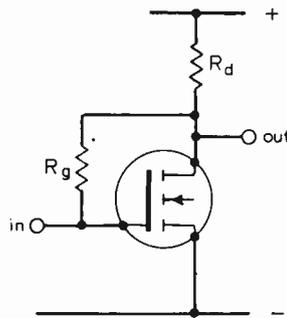


Fig. 13. Basic circuit for d.c. stabilisation of an enhancement type f.e.t.

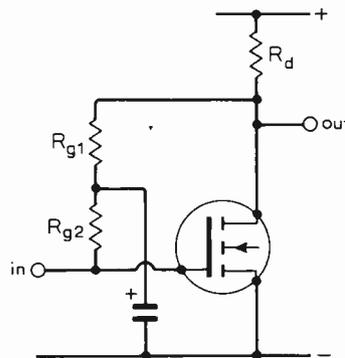


Fig. 14. Method of eliminating signal-frequency feedback in the circuit of Fig. 13.

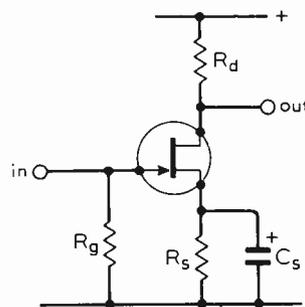


Fig. 15. Method of biasing and d.c. stabilising a depletion-type f.e.t.

bias voltage between that of the drain and that of the source: it is thus possible to use the d.c. biasing and stabilising circuits described earlier in this article. For example we can use the circuit of Fig. 3 (a): Fig. 13 shows an n-channel i.g.f.e.t. so stabilised. The stability factor is given by

$$\text{stability factor} = \frac{1}{1 + g_m R_d} \quad (9)$$

and is independent of the value of R_g which can thus be made very high. If $g_m = 2\text{mA/V}$ and $R_d = 5$ kilohms, both typical practical values, the stability factor is 1/11.

In the basic form of Fig. 13 the circuit has the disadvantage that R_g gives signal-frequency feedback but this can be eliminated by constructing R_g of two resistors in series and by decoupling their junction to source as shown in Fig. 14. R_{g1} and R_{g2} can be made equal and each may be several megohms, so retaining the chief feature of the f.e.t., its high input resistance.

For depletion-type f.e.t.s the gate bias voltage lies outside the range of the drain and source voltage: this is also true of valves, of course, and the biasing circuit used for valves can also be used for depletion-type f.e.t.s as illustrated in Fig. 15. The method of calculating the value of the bias resistor was described in Part 1. The stability factor is given by expression (9) by substituting R_s for R_d . Typical practical values are $g_m = 2\text{mA/V}$ and $R_s = 1$ kilohm for which the stability factor is 1/5. Better stability can be obtained by using the potential divider circuit (Fig. 5) which enables higher values for R_s to be employed. The potential divider circuit can also be used with enhancement-type f.e.t.s.

Corrections

“Crossover networks and phase response”, Nov. 1975 issue, p.531. The figures over the captions Fig. 5 and Fig. 6 should be interchanged. The filter proposed by Small is a modified fifth order filter, with final slopes corresponding to a third order filter.

“What’s in a name?”, Jan. 1976 issue, p.47. In the first column, the sentence beginning 23 lines from the bottom should read: “So it could hardly be more wrong to choose this word to mean a progressive voltage change in an unchanging direction...”

Schottky clock oscillator integrated circuit, type CO-238, mentioned in New Products, Nov. 1975 issue, p.548, will operate up to 100MHz, not 1,000MHz as stated.

Circuit Ideas

Simple c.r.o. input isolating probe

In many c.r.o. applications it is desirable to connect the Y deflection input to a p.d. that is floating with respect to the c.r.o. frame or earth. In some cases it is possible to float the c.r.o., but this is usually considered bad practice and may be potentially dangerous. Alternatively, it may be possible to float the circuit under test. However, neither of these expedients will solve the problem when one wishes to display simultaneously, with correct polarity on a double beam c.r.o., two p.d.s, one of which may be referenced to earth whilst the other is floating.

The circuit shown overcomes such problems by the use of optical coupling between the floating test p.d. V_i and the c.r.o. input V_y .


Two separate 9V batteries are used to power the input and output sides of the circuit, either or both of which may be earthed at any point to suit the test requirements. An inexpensive Texas i.c. opto-coupler is used and, in this circuit, has a bandwidth of about 30 kHz. A four-way switch gives three ranges and an off position.

Range 1 gives 1:1 transmission with

Diode curve tracer for oscilloscope

This circuit is designed to show the I/V characteristics of two-terminal devices on any oscilloscope which has an external X input. The sweep input can be any low voltage signal source, such as a 20V Variac. Current is monitored across the 100Ω series resistor, at a sensitivity of 10mA/V. This resistor also helps to limit the current. The floating device-voltage is monitored with a differential circuit and inverted with IC_2 . When a device is reverse biased the current flowing through the monitor is

approximately that through R_1 and R_2 plus the op-amp (741) bias current. If the oscilloscope X input has no amplifier, voltage sensitivity may be varied with R_3 . Three terminal devices such as unijunction transistors may be traced if an external bias is provided. Maximum voltage across the device, which is the op-amp saturation voltage, may be increased by reducing the gain of IC_1 .
S. Cahill,
Ulster College, Northern Ireland Polytechnic.

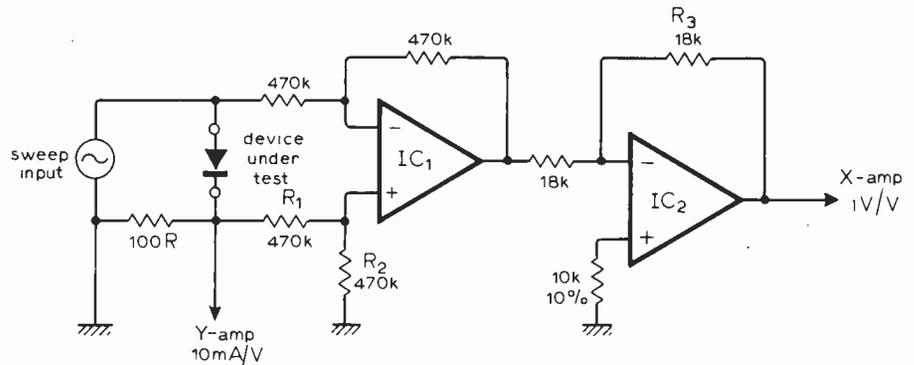


an input resistance of 10kΩ and up to 2V peak-to-peak input.

Range 2 gives 10:1 attenuation, an input resistance of 100kΩ and up to 20V peak-to-peak input.

Range 3 gives 100:1 attenuation, an input resistance of 1MΩ and up to 200V peak-to-peak input. Two 4.3V zener diodes provide input protection. Initial setting up is as follows: Set RV_1 and RV_2 to give unity V_y/V_i on range 1. RV_2 should have a final value such that the output circuit phototransistor is biased

to the centre of its linear range – about 4.5V between pins 4 and 5 of the i.c. RV_3 can be set to give zero d.c. output when the input terminals are shorted. This component is not essential and can be omitted if zeroing of output level is not needed. Assembly and layout are not critical but care must be exercised to preserve isolation between input and output sides of the circuit.

A. F. Sargent
Carshalton
Surrey


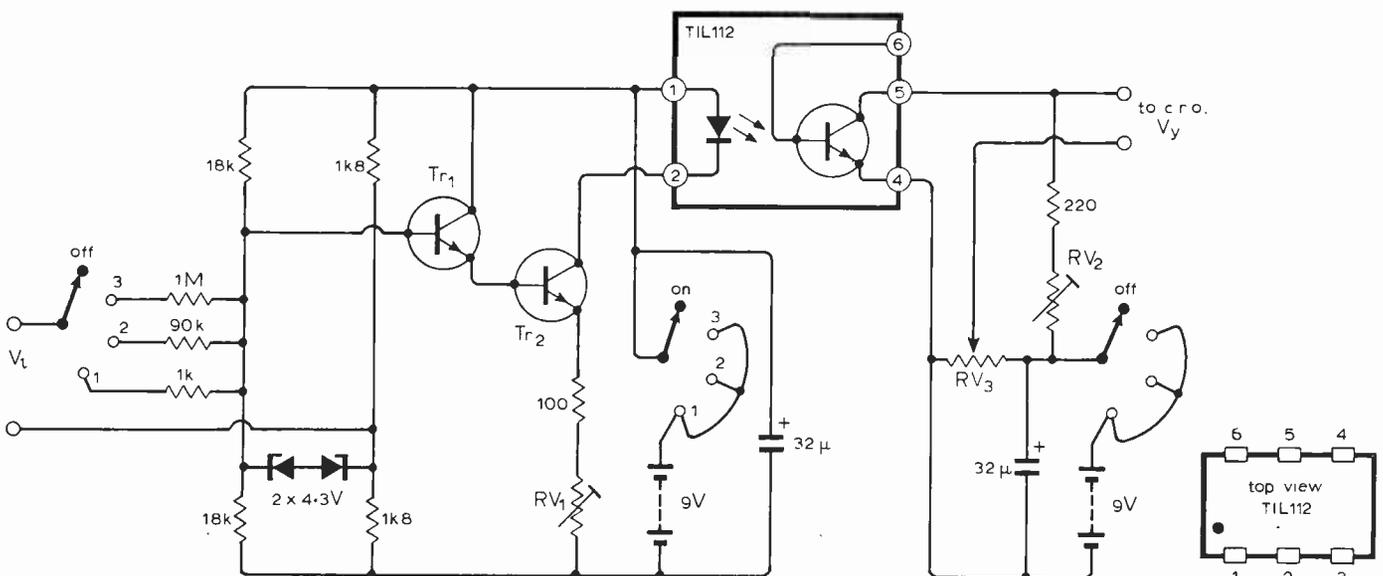


Alarm system with position indication

This application takes advantage of the p-n-p-n structure in the CA3083 transistor array i.c. which contains five n-p-n devices with separate substrate connection. The p type substrate and n-p-n structures of the transistors are utilised as p-n-p-n switches with common connection for anode (substrate). Thus, the transistor array is converted into a silicon controlled switch array. A relay forms the anode load and will be actuated if any of the s.c.s is triggered. By using five lamps in the circuit as shown, visual indication of the actuated channel is provided. Triggering sensitivity of the circuit is high and human touch will actuate the s.c.s. Alarm and visual indication will remain unless the circuit is reset.

Advantages of this circuit are miniaturization and low power consumption. In normal operating conditions, the s.c.s. will act as an open circuit. Use of dry battery cells makes the device small and portable. The number of channels can be increased by using two or more transistor arrays.

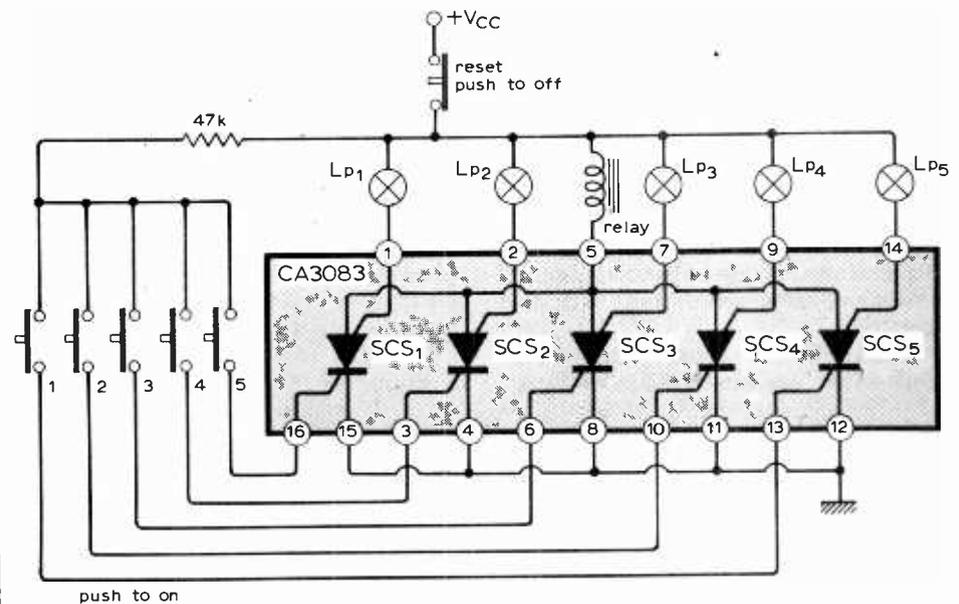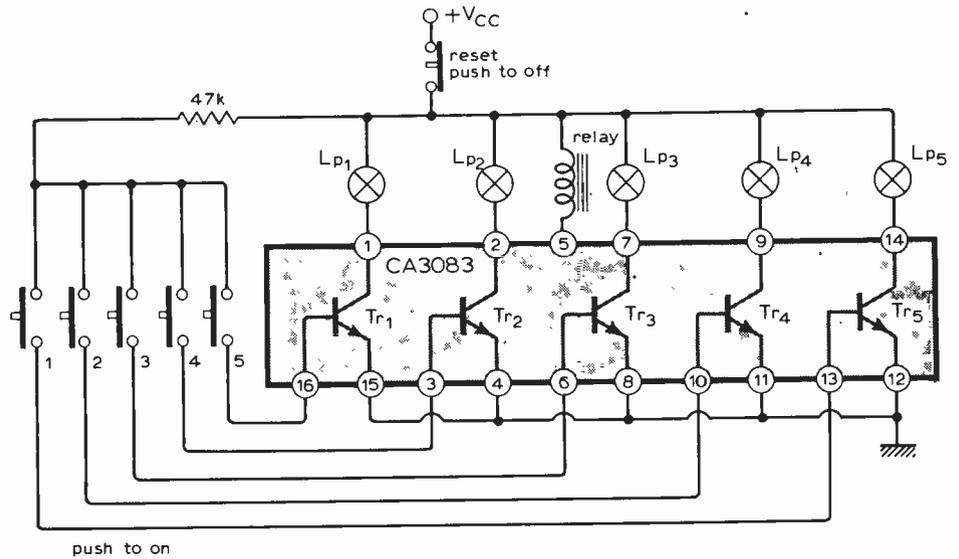H. S. Kothari,
Central Electronics
Engineering Research Institute,
India.




Automatic switch-off power supply

This power supply was designed to operate a digital exposure timer constructed from t.t.l. circuits. Because the logic is required only when the enlarger lamp is on, it was decided to automatically switch off the power supply when on standby. The supply to the t.t.l. circuits is turned on by closing the switch at the same time as the timing cycle is activated, which sets the timer output to 5V and turns on the lamp. Diode D_2 is also connected to this logic point and the power supply remains on when the switch is released. When the timer output goes low and the lamp is extinguished, gate current to Tr_4 is cut off which switches off Tr_1 and removes the current through the zener diode. The supply voltage therefore drops to zero.

This circuit is applicable to all uses where the logic is required for only part of the time, which allows a smaller transformer to be used to reduce weight and cost.

E. R. Rumbo,
Acton,
Australia

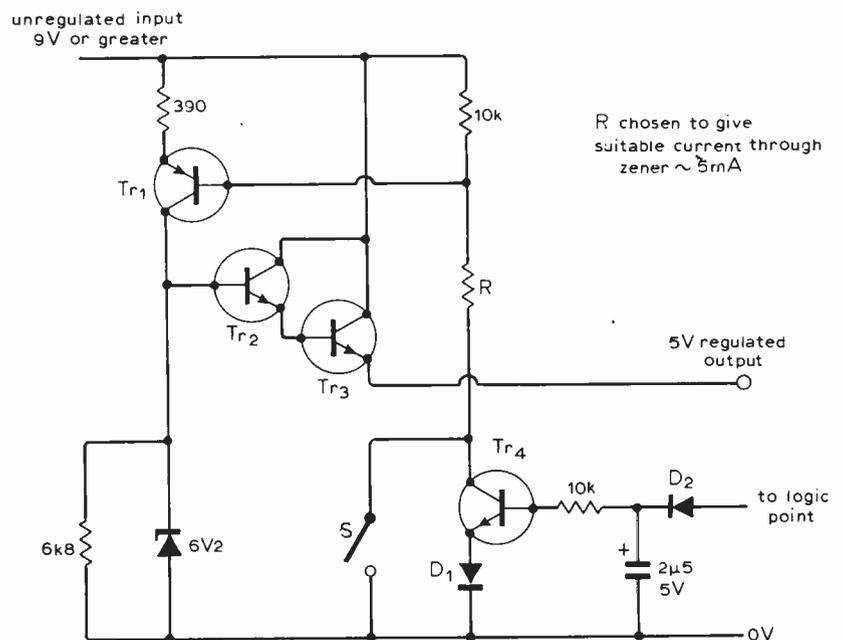


Single gang pan-pot

The use of a single-gang linear potentiometer as a balance control is well known. Shown here is a simple pan-pot for stereo audio mixers using the same technique. The circuit was designed to give the best approach to a sine law so that $A^2 = B^2$ is a constant, whatever the position of the wiper. The output was normalized at 90° (potentiometer at maximum) so:

$$\text{error } E = 20 \log \frac{A/A_{max}}{\sin(90 \times R/R_{max})}$$

is 0dB at $R = R_{max}$

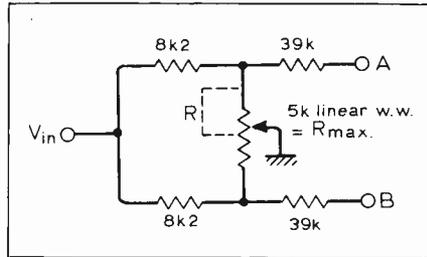

The calculated error for the circuit is less than 1dB over the full range of the potentiometer. The input impedance, about $5k\Omega$, is constant within 10% over the same range $A_{max} = 0.35V_{in}$.

If zero error at 45° (signal panned to centre) is required and some deviation from the sine law can be tolerated, the $5k\Omega$ should be changed to $10k\Omega$ which gives $A_{max} = 0.49V_{in}$. Clearly for higher input impedances all the values may be multiplied by a constant. Outputs A and B are virtual earth summing points and the potentiometer should be wire-wound for minimum cross-talk. In practice there is no audible change of level as the image is panned.

J. Dawson,
K.J.E. Northover,
D. C. Threlfall,
Cambridge University Tape Recording Society.

Pulse generator

This pulse generator was designed to provide clock pulses of variable width and p.r.f. for t.t.l. circuits at a relatively low cost. It uses a versatile 74123 dual monostable i.c. which can be triggered from a positive or negative going edge and can be cleared or re-triggered if desired. The pulse width is determined by an external CR combination, the recommended maximum and minimum resistance being $50k\Omega$ and $5k\Omega$ respectively.

With the switch set to "internal," the monostables are connected in an astable configuration with each monostable being on for its own time period and off for that of the other monostable. The output is taken from an emitter-follower for low output impedance. The on time of each monostable is determined by its variable external resistor and one of a bank of six capacitors, giving on or off times between 100ms and 100ns.

Therefore, it is not possible, as with some pulse generators, to set the pulse width greater than $1/p.r.f.$ — which gives no output.


With the switch in the "external" position the on-time monostable is

driven by three transistors arranged as a Schmitt trigger. This gives a pulse of the same frequency as the input waveform, the pulse width being determined by the on-time variables. Potentiometer VR_1 determines the trigger level.

The circuit of a suitable power supply is shown.

Performance is above expectations, but wire lengths must be kept to a minimum if good pulse shapes are to be obtained at the highest frequency.

J. Garrett
Dublin
Eire

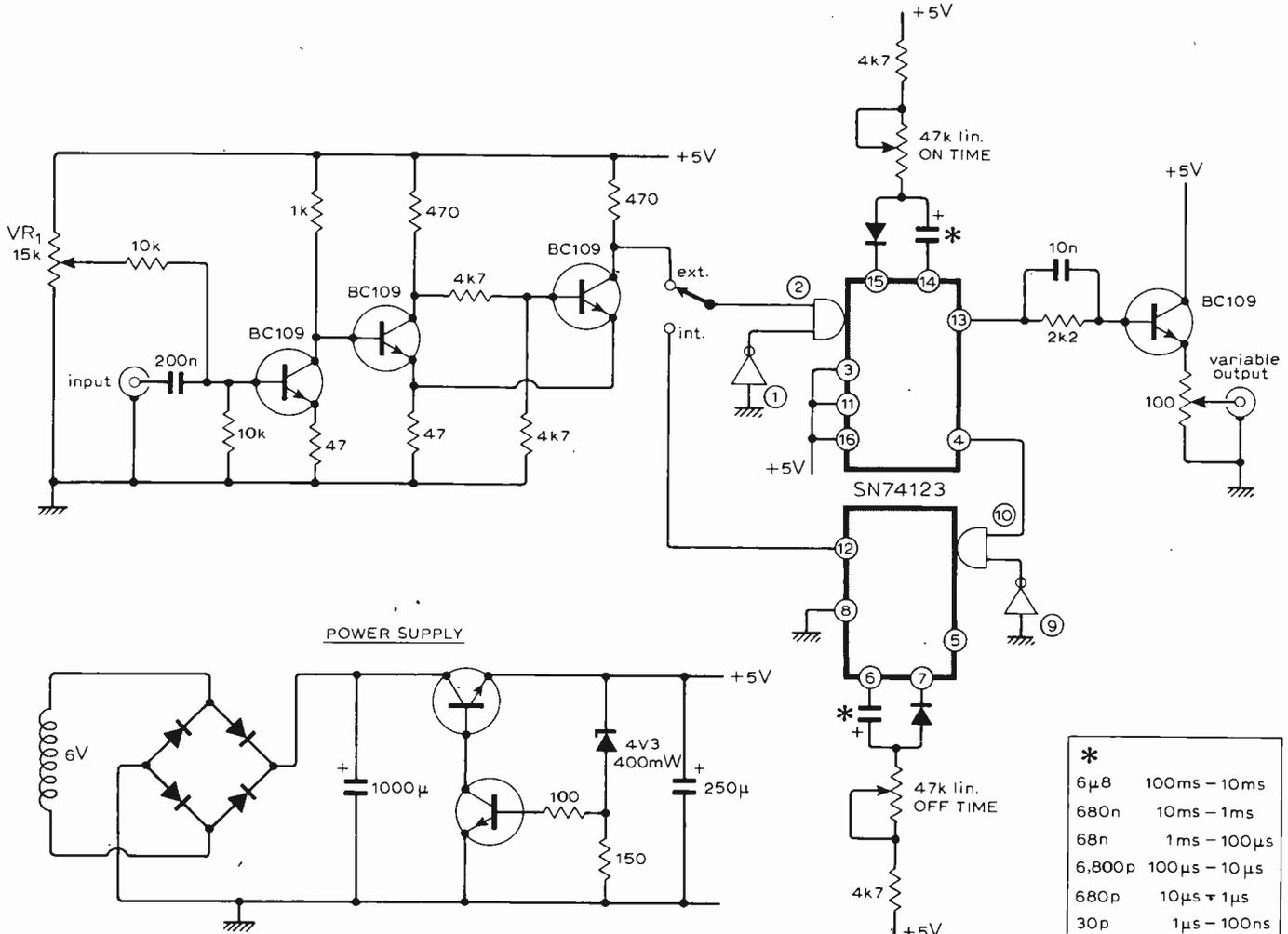

World of Amateur Radio

Long-delay echoes

Despite the many apparently authentic reports of long-delayed echoes being received on h.f. in the period 1928-1938, a project carried out at the Cavendish Laboratory in 1973 by Peter Duffett-Smith, G3XJE, completely failed to detect any such echoes in the course of more than half-a-million automatic transmissions on 7, 9 and 20 MHz. But now new evidence — and a possible explanation — is put forward in a 245-page report, "Long delayed radio echoes" by D. M. Sears of Stanford University, who in a five-year period has obtained tape recordings that, although none reproduces exactly the transmitted signal, exhibit features which the author states "seem unlikely to have been generated except by an l.d.e. mechanism".

Sears and Crawford at an URSI symposium in Peru last August suggested that these curious echoes are due to very low group velocity (1 km/s) propagation effects near the peak of the F-layer. It is proposed that very weak fluxes of kilovolt energy electrons could cause delays of several seconds.

But this remains a Loch Ness monster of h.f. radio — the early records of "sightings" were clear and specific, yet intensive investigations since 1969 have failed to come up with a single incontrovertible recording!

National societies

In an era where many amateur radio societies are facing acute financial problems there has been surprisingly little questioning of the fundamental issues. As became clear at the recent annual general meeting of the RSGB — where members voted overwhelmingly in favour of giving the Society's council full power in determining subscription rates — most amateurs accept the need for professionally administered societies providing a full range of services to members.

But Pierce Healy, VK2APQ, writing in *Electronics Australia*, raises basic issues in questioning "what future is there for amateur radio societies?" He points out that the societies were formed and

flourished as the result, almost entirely, of voluntary efforts on the part of the members: the "Wireless Institute of Australia", the oldest-established amateur radio society, being no exception. But during the past few years WIA has come to depend on executive staff, computerised membership records and a professionally produced journal. One result has been that rising subscriptions have reduced the percentage of Australian amateurs who belong to WIA from 54 to 50 per cent, and this process may be accelerated by a projected major increase in subscription rates.

Pierce Healy suggests that increasingly the amateur societies will be faced with only two possibilities: a membership willing to pay for high-cost tasks carried out on their behalf; or reversion to "the tried and proven voluntary effort system". The latter course, which he clearly favours, would be more economical but requires dedicated volunteers.

With thoughts increasingly turning to the next frequency conference in 1979 there is clearly a vital need for strong and effective societies, but he considers that unless high-cost amateur societies are willing to see themselves representing only a minority of amateurs in their own countries, they must depend for much of their effort on volunteers.

Notes and news

The Home Office has stated that it intends to undertake a review of the British amateur licence "when staffing time permits".

Colin Thomas, G3PSM, (73 Mexborough Avenue, Leeds LS7 3ED) who organises the "intruder watch" has asked for help from r.t.t.y. enthusiasts (whether amateur transmitters or listeners) in systematically checking and identifying non-amateur radio-teleprinter transmissions in exclusive amateur bands. The proposed "GB2ATG" weekly r.t.t.y. news bulletin transmission is still awaiting final Home Office approval and licensing.

A 432.91 MHz amateur beacon station, GB3EM, has been installed in the country's highest room — the enclosed room near the top of the IBA's concrete television aerial support tower at Emley Moor, near Huddersfield, Yorkshire. A modified all-semiconductor Pye transmitter provides 10 watts output to a J Beam "8 over 8" aerial beaming 170° ETN (i.e., a direction slightly east of London). The aerial is mounted on the roof of the room almost 900 ft above ground and over 1700 ft above sea level, keeping transmission line losses to a minimum. The automatic keyer has been built by A. Robinson, G3TQA, on behalf of the Bradford University amateur society. Beacon keeper is H. P. Bottom, G8DHD, a member of IBA staff at Emley Moor.

Dr J. A. Saxton, director of The Appleton Laboratory, has accepted an

invitation by the RSGB Council to become an Honorary Member. Dr Saxton was President of the society in 1970 and again in 1973.

The RSGB are proposing three n.b.f.m. simplex channels in the 70 MHz band, 70.5 MHz as calling channel and 70.475 MHz and 70.525 MHz as working channels.

In conjunction with representatives of a number of local societies concerned with repeater stations, the RSGB has formed a "repeater working group" and the Home Office has confirmed that the Society should provide an overall plan for the installation and operation of v.h.f. and u.h.f. repeaters in the U.K. and to be responsible for monitoring their operation.

An echo of the thirties

One of the oldest-established brand names in amateur radio — at one time the "world's largest builders of amateur communications receivers" — has recently changed hands: Hallicrafters amateur and citizen-band equipment will in future stem from Breaker Corporation of Arlington, Texas. The original Hallicrafters company of Chicago launched the "Super Skyrider" receiver in January 1935 and within a few years were producing a whole series of "Sky . . ." receivers. Many British amateurs used the Sky Buddy (selling in the U.K. for about £9) or the higher performance Sky Champion, which boasted an r.f. stage, in the years immediately before World War II.

A recent note from the Rev. Arthur Trewin, ZS5AX, of Durban, South Africa, mentions that although now 91 years old he is still active on the amateur bands. Formerly VQ5NTB, G2AT and ZS2AT, he recalls his first Uganda-to-U.K. contact in 1931 using a single P625 valve in the old "TNT" (tuned anode non-tuned grid) power oscillator transmitter and two-valve (0-v-1) receiver.

In brief

Brian Bower, G3COJ, appears to have pushed the U.K. record for the 432 MHz band to over 900 miles with a contact (July 1975) with the Swedish station SM5DSN . . . The Swiss national society USKA reports an increase during the year of 208 members to bring total membership to 2312 . . . Northern Radio Societies Association holds their annual convention at Belle Vue, Manchester on April 25 . . . The RSGB National VHF/UHF Conference is to be held for the first time at Brunel University, Uxbridge, Middlesex on May 8-9 . . . The British Amateur Radio Teleprinter Group's annual convention is at Meopham on May 22 . . . As an alternative to a national mobile rally, the RSGB is planning to hold an amateur radio exhibition at Alexandra Palace on July 30, 31 and August 1.

PAT HAWKER, G3VA


New Products

Digital i.c. test system

Teradyne has announced a digital i.c. test system for use in production and incoming inspection. The J325 computer-controlled test system is optimized for testing a wide spectrum of digital i.c.s, including t.t.l., d.t.l., e.c.l., c.m.o.s. and static m.o.s. The different test demands of these technologies are satisfied by the availability of two basic test stations. One is optimized for testing c.m.o.s., static m.o.s. and h.t.l., the other for e.c.l. and t.t.l. A two-station J325 is priced at around £70,000. Teradyne Ltd, Clive House, Queens Road, Weybridge, Surrey KT13 9XB.
WW 301 for further details.

Miniature rotary switches

Two ranges of miniature rotary switches are the 5920 and 5922ER series. Designed for mounting directly on to a p.c.b., the 5920 series has angled terminals on a pitch of 2.45mm (0.1in) and a total height of 10mm when mounted. They have gold-plated silver contacts rated at 0.2V at 150V a.c. and can be supplied in a variety of single and

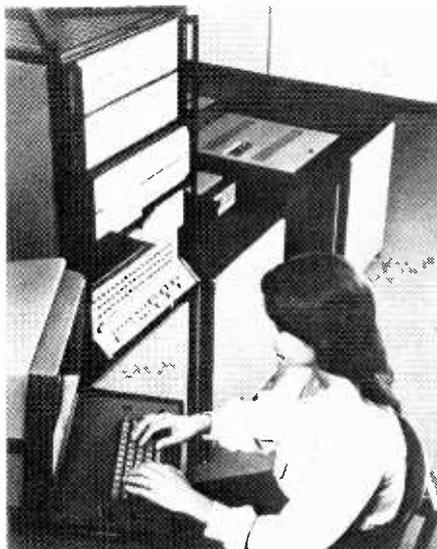

WW 301

multiple pole, multiple way switching configurations. The 5922ER series has been designed for panel-mounted applications, requiring an aperture of 10.2mm. They measure 20mm in diameter overall and can be supplied in various switching configurations. Contacts are silver, rated up to 0.3A at 220V a.c. Roxburgh Electronics Ltd, 22 Winchelsea Road, Rye, Sussex.
WW 302 for further details.

Noise cancelling mic


An efficient, moving coil, low impedance instrument designed to withstand demanding environments in industrial use has been introduced by Selsound. The microphones are available as inserts, type 2500, but can be provided with housings to suit specific customer requirements. Impedance is 25Ω and sensitivity 500μV at close proximity and normal speech level. The directional response gives -12dB at 1kHz at 90° and 270° off axis. Selsound Ltd, Victory Close, Industrial Estate, Chandlers Ford, Eastleigh, Hants.
WW 303 for further details.

Proximity switch

A heavy-duty, solid-state proximity switch, model 8-260, is a self contained barrel mounted switch designed for operation in severe environments. Manufactured by the Eldec Corporation and marketed in this country by Elliott Relays, the 8-260 is sealed by moulded epoxy in a one-piece construction for maximum protection against contamination. A load current rating of 1A permits lamp and relay operation — as well as a range of control circuitry requiring high input currents. Normally open or normally closed output switch versions are available. Sensing distance is 0.1in for ferrous metal targets and



WW 303

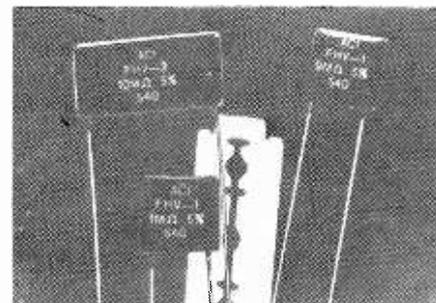

WW 305

0.05in for non ferrous metals. Elliott Relays, 70 Dudden Hill Lane, London NW10 1DJ.

WW 304 for further details.


High-voltage high-stability resistors

Up to 7.5kV can be handled by new resistors from Erg Components. Rated at 2.5 watts at 70°C, they have a temperature coefficient of ±200 parts per million per deg. C. High value-stability is achieved (2% after 2000 hours at full load) by using a noble-metal resistive glaze on an alumina substrate. Erg Industrial Corporation Ltd, Luton Road, Dunstable, Beds LU5 4LJ.
WW 305 for further details.

Multichannel analogue recorder

The Gould Brush 2400 direct-writing chart recorder has channel amplitudes of 100mm and 50mm and uses a servo-controlled pen motor to give frequency responses of 30Hz at 100mm, 50Hz at 50mm and up to 100Hz at lower amplitudes. The recorder is available in 12 configurations and can be used in two-, three- or four-channel form, with or without interchangeable plug-in preamplifiers. Portable or rack-mounted versions are available. The pen motor incorporates a non-contact servo feedback system known as Metrisite which gives a stiffness of 100g/mm and a linearity of 99.65% over the channel width. Rise time is less than 8ms for 100mm amplitude and 5ms for 50mm amplitude. Overshoot is less than 1% on square waves. Twelve chart speeds between 0.05mm/s and 200mm/s are provided. Gould Advance Ltd, Data Products Division, Raynham Road, Bishop's Stortford, Herts.

WW 306 for further details.

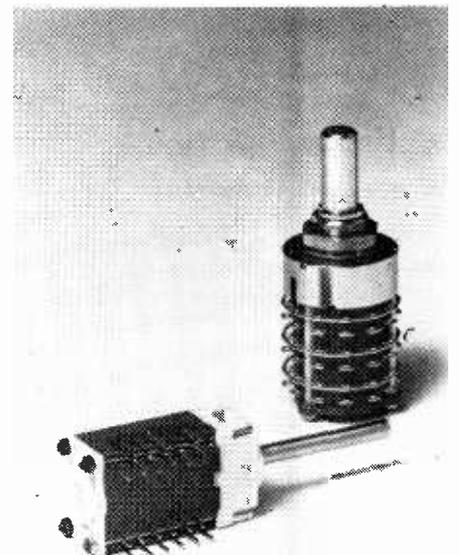


WW 302

SSB transceiver for h.f.

A single-sideband transceiver for the h.f. bands has been added to the AEL range of communications equipment. Covering 2 to 16MHz in four or six crystal-controlled channels, the transceiver – type AEL3030 – is designed for 12-volt mobile use. A version for fixed-station use has an internal 115/230V a.c. power pack. Output from the wideband p.a. is 150 watts p.e.p. with typical harmonic suppression of 50dB. Receiver sensitivity is $0.5\mu\text{V}$ for 20dB s+n/n. Above $5\mu\text{V}$, a.g.c. action gives a 3dB increase in output for a 100dB increase in input level. Ten of the eleven p.c. boards are plug-in modules. Acro Electronics (AEL) Ltd, Gatwick House, Horley, Surrey.

WW 307 for further details.

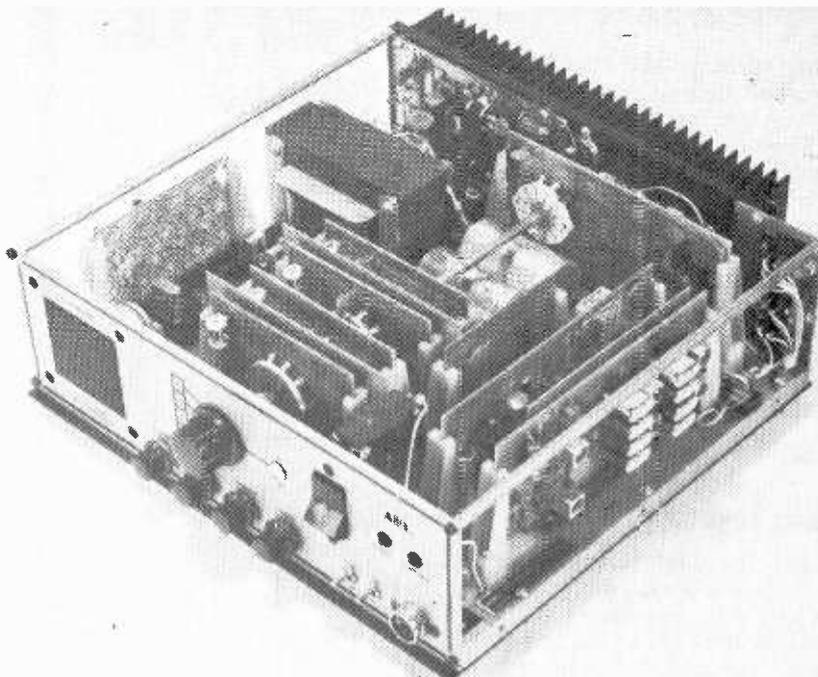


WW 307

Mini battery-mains scope

The B1010 miniature battery-mains scope (137mmW × 195mmD × 64mmH) is a development of the Lawtronic A1010 with additional facilities. It is a 10MHz bandwidth scope, the y-amplifier sensitivity ranging from 10mV/div to 50V/div and timebase speeds from 1ms to 1s/div. The scope has a choice of free running or triggered timebase as a standard facility. A decibel scale on the graticule gives direct reading of amplitude response and modulation depths in communication applications. Rechargeable nickel cadmium cells give up to three hours operating time while operation and recharging can be from 240V, 110V a.c. and 12V d.c. The z-modulation display facility is retained and an internal y-amplifier calibrator has been added. Complete with carrying case, the B1010 costs £198.00. Lawtronics Ltd, 139 High Street, Edenbridge, Kent TN8 5AX.

WW 308 for further details.

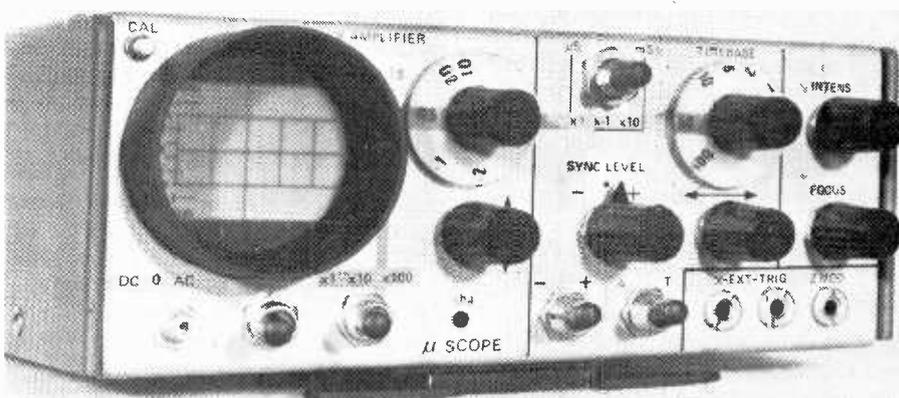

WW 308

Broadband test oscillator

A general-purpose broadband test oscillator providing sine waves from 10Hz to 10MHz, with additional square wave outputs from 10Hz to 1MHz, has been introduced by Farnell. The LFM3 has a t.t.l. output at 5V up to 10MHz and a sync output of 6V pk-pk sine. The output of 1mV to 20V into open circuit is levelled in seven attenuator steps of 10dB per step from +10dB to -50dB with an uncalibrated fine level control providing a further nominal adjustment. Main output sockets for 600Ω and 50Ω are provided. The LFM3 is intended for general calibration and instrument test work and is particularly suitable for video amplifier and a.c. bridge measurements. Farnell Instruments Ltd, Sandbeck Way, Wetherby LS22 4DH, Yorkshire.

WW 309 for further details.



WW 309

Rapid heat irons

A range of 30, 60 and 100W soldering irons which heat up within seconds of switch-on are being marketed by Kelgray Products. For ease of working in confined spaces, the 60W and 100W Engel irons have built-in lights to illuminate the working area. A range of blades is available for use with the 100W unit which extends the application of this model to include thermo-cutting of man-made fibres and ropes. Kelgray Products Ltd, Bywell House, South Godstone, Surrey.

WW 310 for further details.

Audio test set

Facilities offered by the Amber 4400 test set include function, sweep, noise, audio comb and burst generators, autoranging digital level meter and frequency counter, wave and spectrum analyzers and a dual digital memory. Dimensions are 133mmH x 210mmW x 279mmD. Additional features include a balanced or unbalanced output capability of +30dBm, a 10dB per step output attenuator ranging from +30dBm to -70dBm, programmable operation for most functions and an internal crystal timebase for accurate frequency reference. The unit should be available at the end of January and will cost approximately £950. Scenic Sounds Equipment Ltd, 27-31 Bryanston St, London W1H 7AB.

WW 311 for further details.

Electronic multimeter

Use of an i.c. amplifier in a Philips multimeter enables a robust meter movement to be used but with a "sensitivity" of 500kΩ/V. The multimeter, type SMT111, has 35 ranges, including f.s.ds for direct voltages of 30mV to 300V, direct currents of 3μA to 300mA (40 to 60mV voltage drop), alternating voltages of 300mV to 600V, and alternating currents of 30μA to 3A (400 to 600mV drop). In addition, the meter has five resistance ranges, a battery-check switch position and a frequency response that extends up to 10kHz on the 60V range and 40kHz on the 300mV range. Overload protection of the i.c. and movement is provided. Accuracy is ±3 or 4%, depending on range. Price is £30 (excluding v.a.t. at 8%). Combined Electronics Services Ltd, 604 Purley Way, Waddon, Croydon CR9 4DR.

WW 312 for further details.

Solid State Devices

Names of suppliers of devices in this section are given in abbreviation after each entry and in full at the end of the section.

Analogue delay line

A charge-coupled device made by Fairchild, type CCD311, can delay analogue signals from 20μs to 25ms by varying the rate of externally supplied clock pulses. The device is a "spin-off" from the Fairchild 256-element c.c.d. image sensor and is thought to have potential as a time base corrector in video tape recording systems. The device could also be used for a wide variety of other applications, including phase equalization and convergence correction in video systems, delay equalization in speech transmissions and scrambling systems, and construction of complex analogue filters. A signal-to-noise ratio of 50dB or more and a bandwidth of 4MHz are claimed. The device, housed in an 18-pin dual-in-line package, is available from Fairchild in the U.S.A. and can be ordered in the U.K. from their Aylesbury, Bucks address.

Fairchild

Linear optical sensor

An array of 1872 photodiodes at 15 micron centres forms the Reticon RL 1872F linear sensor. The device possesses its own low-dissipation commutating shift register, with a maximum data output rate of 20MHz. A ceramic dual-in-line package is used, a ground and polished quartz window covering the diodes. Clock generator, driver amplifier and integrator sample and hold

boards are available for use in high-speed facsimile equipment. P.c. cards containing all required drive circuitry for the device are available.

Rapid Recall

Low-cost micro processor

An 8-bit, p.m.o.s. microprocessor from National, the SC/MP, is capable of a 2μs cycle time and is powered by a single 10-14V supply; timing is on the chip. At £7.50 in quantities, the device is intended for use in toys, domestic appliances, car electronics and similar mass produced equipment which does not benefit from very high speeds or computing power. Multiple units can be bussed, each chip having "queueing" circuitry to organize the flow of information on the bus.

National

Fast 1-kbit r.a.m.

With an access time of 22ns, the MCM10146 is claimed by Motorola to be the fastest 1024-bit random-access memory yet available. The 1024 1-bit words are stored in a 32x32 array and selected by 5-bit x and y co-ordinates. The "write enable" input controls operation; when low, data at the inputs is stored and, when high, the data is output, without inversion. Outputs can be wire-ORed. Power consumption is around 510mW and the device is in a 16-pin d.i.p.

Motorola

Suppliers


Fairchild Semiconductors Ltd, Kingmaker House, Station Road, New Barnet, Herts.

National Semiconductor UK Ltd, 19 Goldington Road, Bedford.

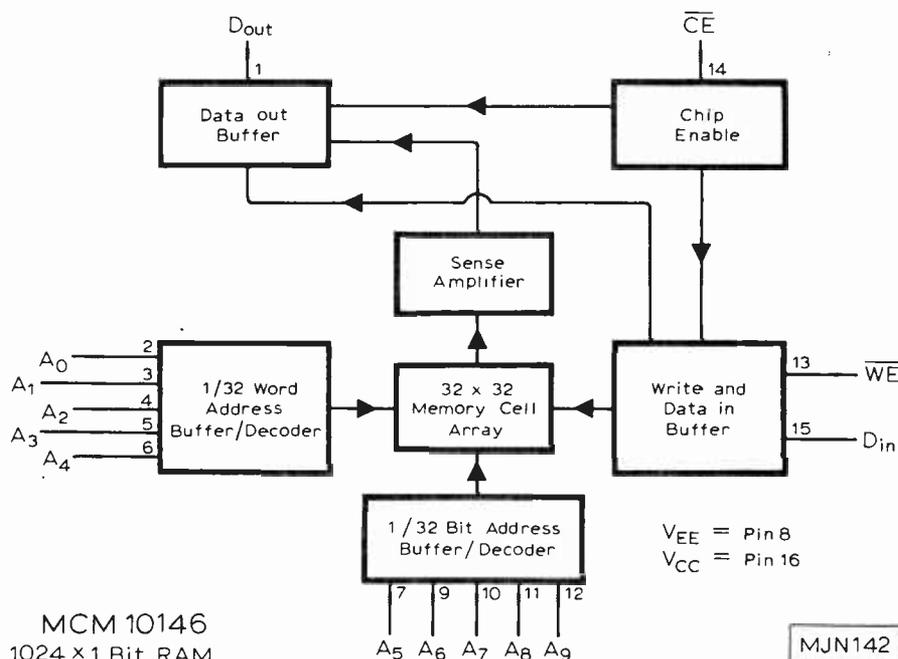A. Marshall (London) Ltd, 42 Cricklewood Broadway, London NW2 3ET.

Motorola Ltd, Semiconductor Division, York House, Empire Way, Wembley, Middlesex, HA9 0PR.

Rapid Recall Ltd, 9 Betterton Street, London WC2H 9BS.



Linear c.m.o.s. circuits

A further selection of tested circuits is published in Circards, set 28

by J. Carruthers, J. H. Evans, J. Kinsler & P. Williams

Paisley College of Technology

If logic circuits could be adapted only for amplifying functions, the exercise would still be worthwhile — it would avoid having to add separate operational amplifiers on those occasions when only simple signal processing is needed. In fact most other electronic circuits can be designed if care is taken to work with the characteristics of c.m.o.s. rather against them. A restriction is that only inverting stages can be used with negative feedback, there being no equivalent to the series-applied feedback circuits (e.g. voltage followers) common in operational amplifier designs. Non-inverting buffers or cascaded inverters lend themselves to positive feedback functions such as Schmitt trigger circuits. Variety can be introduced by using individual devices from certain c.m.o.s. i.cs in combination with inverters and gates.

As a general rule it is simpler to adapt those familiar circuits that use inverting amplifiers, unless the function required cannot be performed in this way.

Circuits that can be designed using inverting amplifiers include active filters such as the two-integrator loop, three-stage phase-shift oscillators, and the like. There is no need to restrict ourselves to simple buffers and inverters; other i.cs can be readily applied in analogue circuits of various kinds. For the more complex i.cs, the degree of internal interconnection reduces flexibility and it is less easy to see ways in which non-logic functions can be performed.

One form of flip-flop, the D-type, has a pair of outputs Q and \bar{Q} . When fed with a positive-going pulse on the clock input C, the output Q is forced to take up the logic state on the data input D at the instant of clocking. This state at the output is retained regardless of any variation at D until the next clock pulse. Such a flip-flop finds application in the processing of analogue signals, as in some forms of analogue to digital converters and phase-locked loops. In a particular application, the delta-sigma modulator, the integrator receives a current from the input voltage, which

causes its output to change until the comparator output swings through zero. On the succeeding clock pulse the Q-output must change, since the D value has changed, and this changes the f.e.t. between its conducting and non-conducting states. The polarity of input and reference voltage must be opposite so that the fed-back reference can reverse the direction of integration. Combining the clock pulse with Q (or \bar{Q}) in a suitable logic gate gives a pulse train in which the average number of pulses is proportional to input voltage.

The above appears to be a complex system, but two properties of c.m.o.s. allow efficient use of the flip-flop. The sharpness of the transfer-function means that the region of doubt at the D input is very small i.e. that even voltages close to $V_s/2$ are clearly distinguished as either logic 0 or logic 1. Hence the comparator can be dispensed with, the flip-flop acting as its own comparator. Similarly the output of the flip-flop is well-defined, and for a stable supply voltage the f.e.t. and separate voltage reference can also be eliminated reducing the system to one op-amp and a flip-flop.

Similar considerations lead to economical circuits for Schmitt trigger, astable and monostable circuits, by making use of the S and R or set and reset inputs, also available in D-type flip-flops. It must be remembered that such circuits may depend on properties which may not be covered directly by manufacturer's data, although the experimental evidence for their satisfactory behaviour is clear.

A semi-digital mode of operation is where inverters are used to drive power transistors. Output stages for class-D power amplifiers are examples where this technique is of use, the c.m.o.s. drivers also helping to switch the transistors off rapidly, though delays may be needed at the inverter inputs to avoid the possibility of simultaneous conduction of both transistors.

There is one family of c.m.o.s. circuits designed specifically for use in linear and non-linear analogue circuits viz the analogue gate/bilateral switch. By driv-

ing a parallel complementary pair of m.o.s. transistors with anti-phase logic level signals their conduction can be linearized so that the transfer of voltage is near unity when lightly loaded. This extends over the whole supply range and these gates can be used to switch components in and out of circuit as well as for direct gating of signals. Applications include d. to a. conversion, waveform synthesis and switched filters.

The technology developed for logic applications in c.m.o.s. has proved to have many characteristics that can be pressed into the service of linear circuit designers. The very low cost of these i.cs must commend them, and with care their limitations can be overcome or side-stepped in a wide variety of applications.

Topics in Circards set 28 (linear c.m.o.s. - 2) are:

- Transistor outputs.
- Current differencing amplifier.
- Frequency-to-voltage converter.
- Two integrator oscillator.
- D-type analogue circuits - 1.
- D-type analogue circuits - 2.
- Bandpass/notch filters.
- Low-pass/high-pass filters.
- D.C. feedback pair.

Circards are a unique way of collating and presenting data about circuits in a compact and easily retrievable way. The sets of 203 × 127mm (8 × 5in) doublesided cards are designed for easy filing in standard boxes and for easy access at the desk or at the bench, where transparent plastic wallets keep the cards in good condition.

Each card normally describes operation of a selected circuit, gives measured performance data and graphs, component values and ranges, circuit limitations and modifications to alter performance. Suggestions for further reading are included together with cross references to related circuits. The Circard concept was outlined more fully in the October 1972 issue of *Wireless World*, pp. 469/70.

Real and Imaginary

by "Vector"

DON'T PUT YOUR OFFSPRING IN THE CAGE, MR WORTHINGTON

For the past 20 years the American electronics engineer has had it made. The exigencies of defence and the space race made him the blue-eyed boy. The universities couldn't turn him out fast enough and extra supplies were lured from Europe and the rest of the world with the bait of the almighty dollar. The beauty of it was — or so it seemed at the time — that you didn't need any overall experience. If, for instance, you knew your way around in gating circuits, that was sufficient. The golden age of the blinkered specialist had arrived. With the resources of Fort Knox behind it, the American electronics industry could virtually write its own cheques.

Then came the writing on the wall — and a rude bit of graffiti it turned out to be. The space programme went into mothballs and defence projects suffered the fiscal chopper. The electronics manufacturers, faced with cancelled contracts, suddenly became much more discriminating in their hiring and far more profligate in their firing, particularly in the specialist bracket. There are now a lot of electronics engineers in the States who are either looking for jobs or fearing that each payday may be their last. And it's on the middle-aged that the chopper is mainly falling, to a degree that the situation has been christened "The Mid-Career Crisis".

Why the middle-aged? For two main reasons. One is that statistics indicate that, as a generalisation, engineers are at their most inventive in their 20s and 30s, while at 40 they're going over the top — and Americans are great believers in statistics. The other factor is the sheer pace of the development in electronics technology, hare-like in its speed and its bewildering twists and turns. And, beyond doubt, in the struggle to keep abreast of developments, the older engineer is handicapped.

For instance, any engineer who graduated circa 1949 did so in terms of valve technology. His sole excursions into solid state would have been a

cursorious glance at a quaint museum piece called the crystal detector, plus something on the silicon diode and metal rectifiers. True, there were one or two papers appearing in the literature concerning a weird little device called the point-contact transistor which allegedly could be used to amplify weak signals, but nobody at university knew much about it. The serious business lay with the omnipotent thermionic valve and so our friend, having mastered various aspects of this device and a groundwork of electrical engineering, took his degree. After a year or so in the laboratory and/or industry he could legitimately regard himself as a fully-fledged electronics engineer, with WELCOME on the mat at the portals of the learned society of his choice. God, it seemed, was in His heaven and all was right with the world. Or was it?

For, by this time the trickle of information on transistors was becoming an avalanche and in due course the point-contact transistor was elbowed out by all sorts of outlandish varieties of which he knew nothing.

He was now faced with a choice of action. He could retreat up the power scale where valve technology was still supreme or he could try to latch on to the theory of these new-fangled solid-state, current-operated devices. Being still young and enthusiastic he chose the second course, but it wasn't easy to throw his valve indoctrination overboard and go it alone with a textbook that never seemed to answer the questions he wanted to ask.

Then, scarcely had he mastered transistors when two further innovations blew up in his face, namely the computer and the integrated circuit. As a guessing-stick man he had a built-in mistrust of computers and all his training rebelled against the minuscule size and seeming fragility of the i.c. package; give him ¼-watt resistors and solid connecting wire every time in preference to these minute chips of semiconductor which had been mucked around by photographic and etching processes of which he knew nothing. And there was more to it than that. Up to this point in time, his position as a designer of discrete circuits had been unchallenged but now the advent of whole subsystems on a semiconductor chip, plus the onset of computer-aided design, had kicked the ladder from under him. As a circuit designer he was rapidly moving into the dodo category; despite all his hard-won experience he was back to square one, competing against wet-behind-the-ears graduates with uncluttered minds, all avid to use the new technologies.

So, all honour to those who survived; whose minds were flexible enough to cope and triumph over adversity. But it seems that in the United States at least there are many that weren't able to do so — hence the so-called Mid-Career Crisis. The man who is over 40 finds it

very difficult to change jobs and, if he's lucky enough to hold down his present one there is often an unpleasant climate in which the up-and-coming young Substrates leap-frog him to senior posts while he finds himself assigned to the humdrum routine chores.


So what's the answer? One approach over there is to arrange for group therapy, where engineers who are in this particular boat get together and discuss their problems among themselves. The philosophy behind this is "togetherness"; it is piously believed that when the over-40 engineer realises that he is not alone and that his anxieties are shared by others, then he won't worry nearly so much. A touch of Disneyland here, I fancy.

In considering the problem it's tempting to cast the top management as the heavy villain callously tying his victim to the railroad tracks of economic retrenchment. But it isn't as simple as that. In the American socio-economic structure (and equally in our own) any company has a rigid set of commandments to observe. The first of these is "Thou shalt keep thy shareholders happy" which, being interpreted, means providing them with an adequate return on their investment. Clearly this can't be done if, because of cancelled contracts, half the engineering staff is filling in its football pools in the firm's time. Equally clearly, expensive redundancies are to be avoided and sackings can involve unions and tribunals, while if either occur in quantity the news makes bad publicity in the media and causes the shares to sag. So the general philosophy is to give a leaden handshake to one higher-salaried engineer rather than to three lowly ones, particularly if he's shown signs of dragging his feet. Or, better still, make his life so frustrated that he opts out on his own.

So that's the way it's going in the States, it appears. We aren't nearly so defence-orientated over here, but cancelled Government contracts are causing headaches and the American electronics industry's ups and downs are often a foretaste of what's likely to happen here. As far as I know, no parallel situation exists with us but it wouldn't get publicity unless it reached epidemic proportions.

Nevertheless, if I were young Substrate I'd think seriously about getting out of engineering and into business management, for this is the area on which our industry's faith appears to be pinned. As Mr J. R. Thompson, chairman of the Science Education and Management Division of the IEE has pointed out, last year's starting salaries for engineers were in the £1,800-£2,000 bracket, while business graduates were offered from £3,250 to £4,800. And in management you're not over the top at 40. An industry with all cowboys and no Indians should be an interesting spectacle.

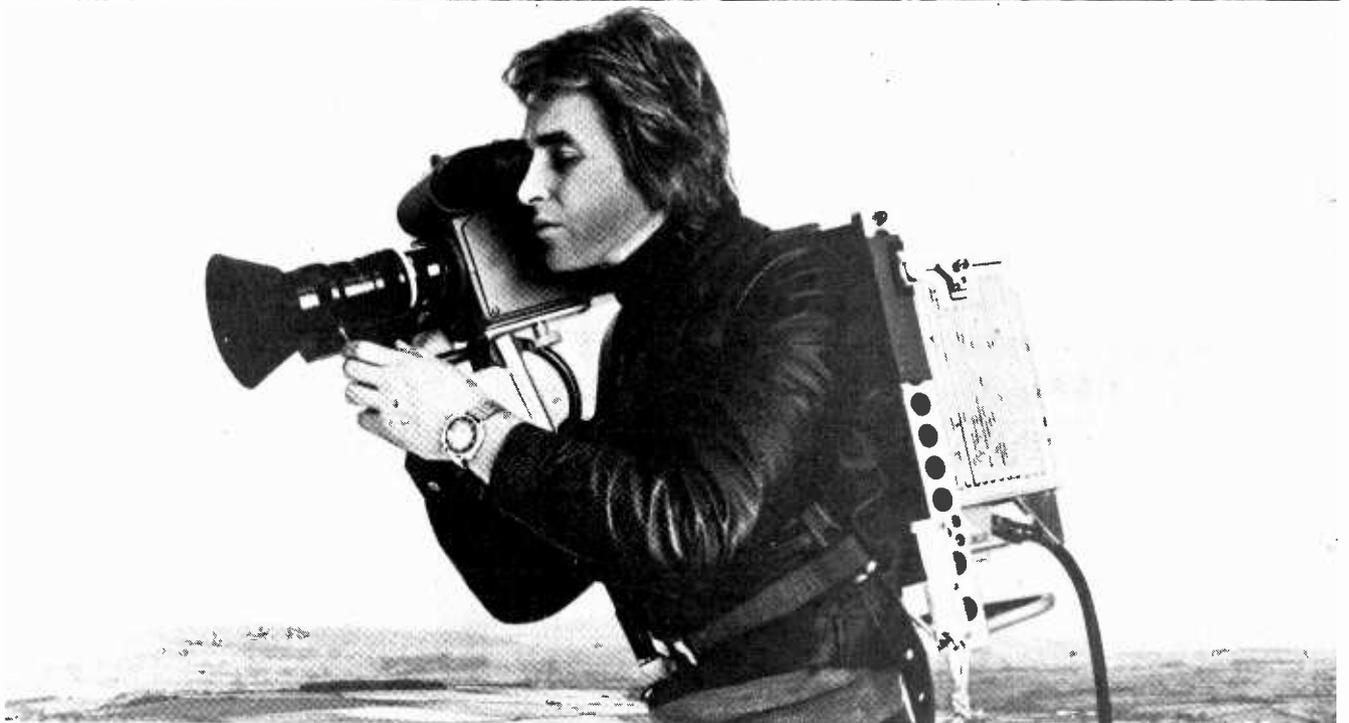The remarkable HL33. Only the camera is more action-packed than the programmes it makes.



For superb performance in a hand-held portable colour camera, programmers all over the world choose the HL33.

Truly, this is one of the world's great ENG cameras.

Even in the most difficult situations, the HL33 is easy to use. Easy to manoeuvre, thanks to its compact size and light weight. Easy to set up. And easy to manipulate; using a digital command technique, a single coaxial cable up to 1500 metres long interconnects the back-pack unit and base station, carrying video, auto white balance, program audio, intercom audio, colour lock signals, HV slip, iris controls

signals, HV centering control and return video, etc.

Extremely rugged, with excellent stability, the HL33 is literally packed with remarkable features.

It has a unique optical system. Light bias. Base station genlock. Horizontal and vertical detail corrector. And a battery running time of up to 4 hours. There's a whole range of back-up accessory equipment to extend its application.

The man to contact is Chris Quarton.

Dixons Technical Ltd
3 Soho Square London W1
Tel: 01-437 8811

Dixons
Technical Ltd
OF SOHO SQUARE




WW-074 FOR FURTHER DETAILS

CRYSLON

AUDIO EQUIPMENT

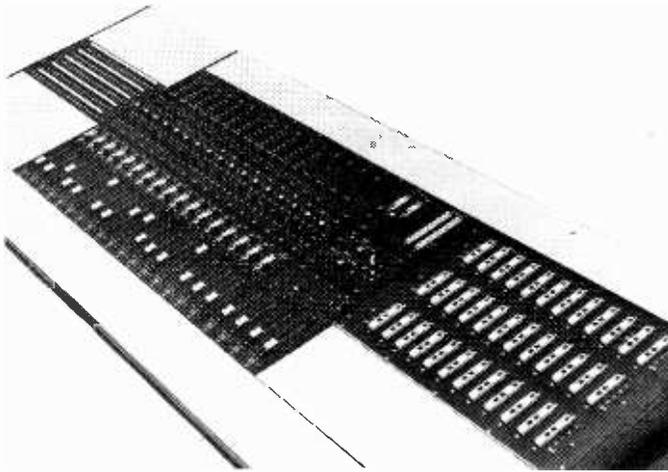SOUND AND COMMUNICATION EQUIPMENT TO SUIT ALL TYPES OF INSTALLATION



SOUND MIXERS
POWER AMPLIFIERS
TALKBACK UNITS
CUE SYSTEMS
STAGE MANAGER SYSTEMS

Write or Telephone for
Details or Quotation

CRYSLON ELECTRONICS LTD.
Berrington Road
Leamington Spa, Warks.

Tel.:
Leamington Spa (0206) 37628/9

WW-088 FOR FURTHER DETAILS

TAUT SUSPENSION MULTIMETERS Made in USSR



U4312: 41 ranges 0.3mA — 6A
D.C., 1.5mA — 6A A.C., 0.3-900v
A.C./D.C., 0.2-50k Ω ; Mirror scale.
Sensitivity 667 Ω /v; Accuracy 1%
D.C., 1.5% A.C. £11.50.

U4313: 40 ranges 0.06mA — 1.5A
D.C.; 0.6-1.5A A.C.; 1.5-600v
A.C./D.C., 0.06-60k Ω ; Mirror scale.
Sensitivity 20k Ω /v D.C.; 2k Ω /v
A.C. Accuracy 1.5% D.C., 2.5% A.C.
£14.90.

U4315: 43 ranges 0.05mA-2.5A
D.C., 0.5mA-2.5A A.C.; 1-1000v
D.C./A.C.; 0.3-500k Ω ; Sensitivity
20k Ω /v D.C., 2k Ω /v A.C. Accuracy
2.5% D.C., 4% A.C. £11.25

U4324: 33 ranges 0.06mA — 3A
D.C., 0.3mA — 3A A.C., 0.6-1200v
D.C., 3-900v A.C., 0.5-500k Ω ;
Sensitivity 20,000 Ω /v D.C.,
4000 Ω /v A.C. Accuracy 2.5% D.C.,
4% A.C. Re-chargeable cadmium cell
operation. £10.85.

LINEAR I.C. AMPLIFIERS

TAA263 — 3 stage low level amplifier
bandwidth DC to 600kHz. Supply
voltage 5-8V Output power 10mW To
72 4-lead £0.65

TAA293 — Med freq amplifier up to
600kHz Supply voltage 6V Output
10mW into 150 Ω TO 74 10-lead case
£0.65

TAA320 — Most stage followed by a
bi-polar transistor Gate-to-source voltage
9-14V Power dissipation 200mW Drain
current 1mA. TO 18 3-lead £0.60.


DIGITAL 7400 SERIES I.C.

Made in USSR

7400	£0.14	7440	£0.14
7401	£0.14	7450	£0.14
7410	£0.14	7453	£0.14
7420	£0.14	7455	£0.14
7422	£0.20	7460	£0.14
7430	£0.14	7472	£0.30
		7474	£0.25

A minimum of 10 assorted I.C. must be
ordered. Discount of 10% for any mix, up
to 25 and 20% for larger quantities

OSCILLOSCOPE CI-5 Made in USSR

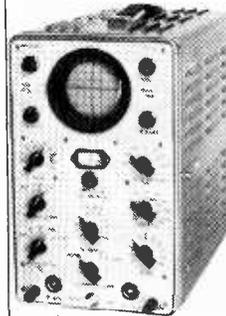

Extremely simple and easy to use single beam
oscilloscope. Well proved design based on standard
octal valves makes servicing and maintenance
straightforward and inexpensive. Because of its
bandwidth of 10 MHz the instrument is suitable for
general electronic applications and educational
purposes where a sophisticated instrument would be
both too expensive and delicate. 3-in. tube giving a 50
x 50mm clear display. Amplitude and time base
calibrations. Sensitivity 30mm/v max. Triggered and
free-running time base, suitable for displaying pulses
from 0.1 μ sec. to 3 m sec. A.C. mains operation.

Price £55.00 ex. works
Packing and carriage (U.K. only £2.50)

EDUCATIONAL METERS Made in USSR



A range of small portable free-standing meters suitable
for experiments and demonstration work. Moving coil
movements with centre-pole pieces. 69mm long open
scale. Basic calibration accuracy 4%. The following
ranges are available. 1, 2, 5, 10 Amps D.C.; 6, 15, 30
Volts D.C. Overall dimensions: 80 x 100 x 48mm

Price £1.90 ex. works
Packing and postage £0.20 per meter

SPECIAL TELEVISION BARGAINS

FIRST GRADE TRANSISTORS

R2008B	£0.95
R2010B	£1.65
BU126	£1.55
BU133	£1.55
BU208	£2.00

Have you already got our illustrated 1975 catalogue/price
list of valves, semiconductors, test equipment and passive
components? If not, please send £0.20 for your copy now

Prices are exclusive of VAT and unless stated otherwise,
packing and postage. When remitting cash with order
please add £0.80 per multimeter, or £0.20 in £ for other
items, as well as VAT (25% for valves, semiconductors and
linear I.C.s and 8% for other equipment)

Z & I AERO SERVICES LTD.


Head Office: 44A WESTBOURNE GROVE, LONDON W2 5SF
Tel.: 727 5641 Telex: 261306

Retail Branch:
85 Tottenham Court Road
London W1. Tel: 580 8403

WW-051 FOR FURTHER DETAILS

100 WATTS !

HY200

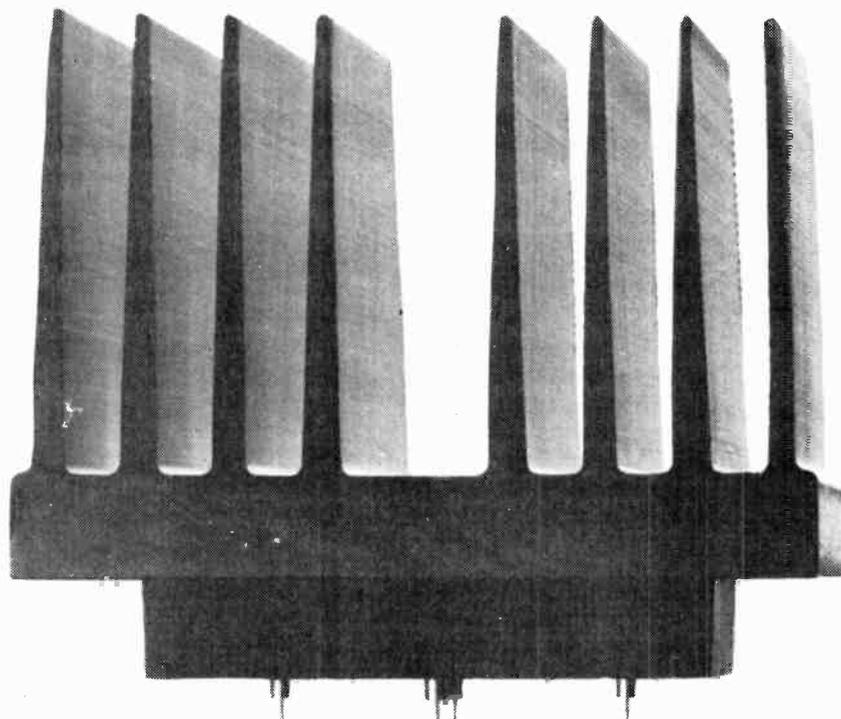

The HY200 is the latest hybrid amplifier from I.L.P. It has been designed to be virtually indestructible lending itself to domestic and industrial applications. Latest design techniques including thermal shutdown make the HY200 the most advanced amplifier of its kind in the World. Only five connections are required, input, output, power lines and earth.

Features:

Short Circuit Protection
No External Heatsinking
Thermal Shutdown
Only Five Connections
Low Distortion

Price £21.20 +VAT £5.30
P&P free

Specifications:

Output Power 100 watts R.M.S. into 8Ω
Input Impedance $100K\Omega$
Input Sensitivity 500mV R.M.S.
Distortion 0.05% Typical
Signal: Noise 96dB
Power Band Width 10Hz - 45KHz $\pm 3dB$
Power Supply 45-0-45v D.C. at 2 Amps
Weight 1 Kilo (2.2lb)
Power Supply PSV90 suitable for one HY200
Price £10.56 + VAT £2.64
P&P free

TWO YEARS GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd,
Crossland House,
Nackington, Canterbury,
Kent CT4 7AD
Tel (0227) 63218

Please Supply _____
Total Purchase Price _____
I Enclose Cheque Postal Orders Money Order
Please debit my Access account Barclay card account
Account number _____
Name & Address _____
Signature _____

CHROMASONIC electronics

Dept. 5, 56, Fortis Green Road,
Muswell Hill, London, N10 3HN.
telephone: 01-883 3705

C - MOS

	1-24	25-99	100up
CD4000AE	19p*	17p*	14p*
CD4001AE	19p*	17p*	14p*
CD4002AE	19p*	17p*	14p*
CD4006AE	19p*	17p*	14p*
CD4007AE	23p*	19p*	15p*
CD4008AE	19p*	17p*	14p*
CD4009AE	Use	CD4049*	15p*
CD4010AE	Use	CD4050*	15p*
CD4011AE	19p*	17p*	14p*
CD4012AE	19p*	17p*	14p*
CD4013AE	59p*	50p*	46p*
CD4014AE	19p*	17p*	14p*
CD4015AE	19p*	17p*	14p*
CD4016AE	55p*	48p*	44p*
CD4017AE	19p*	17p*	14p*
CD4018AE	19p*	17p*	14p*
CD4019AE	80p*	60p*	53p*
CD4020AE	19p*	17p*	14p*
CD4021AE	19p*	17p*	14p*
CD4022AE	19p*	17p*	14p*
CD4100AE	19p*	17p*	14p*

I.C. SOCKETS

Pin Sockets, pins in strips of 100. Just snip off what you need. 65p per strip

Dual in line

8 pin 13p 24 pin 26p IO5

14 pin 15p 28 pin 30p 8 pin 31p

16 pin 15p 36 pin 39p 10 pin 35p

FREE CIRCUITS

Our 8 Page A4 Audio I.C. Booklet is supplied FREE with purchases of Linear I.C.'s worth £1. or more (35p. if sold alone) Contains circuits and pin connections

15 Amplifiers 250 mW to 20 watts

5 Audio Pre-Amplifiers

1 Tape Pre-Amplifier

1 Power Driver

1 Instrument Amplifier (Bifet)

1 General Purpose Mini Amplifier

1 D.C. Controlled Gain Control

1 Micro-mini radio (2 I.C.'s)

PHOTO-DARLINGTON

V_{cc} 25v 2N5777 e

V_{cb} 25v c

V_{eb} 8v b

J1 250 mA

Pd 200 mW

Hfe 2500

35p

LINE-O-LIGHT

NEW LED Linear Cursors each device contains 10 light emitting diodes in a 20 pin dual in-line package. Ideal for solid state analogue meters or dials

Type 101 RED £2.26 * Complete with leaflet.

74 TTL

	1-24	25-99	100+
7400	14p*	12p*	10p*
7401	14p*	12p*	10p*
7402	14p*	12p*	10p*
7403	15p*	12p*	10p*
7404	16p*	13p*	11p*
7408	16p*	13p*	11p*
7409	16p*	13p*	11p*
7410	16p*	13p*	11p*
7413	20p*	24p*	20p*
7417	27p*	22p*	20p*
7420	16p*	13p*	11p*
7427	27p*	22p*	18p*
7430	16p*	13p*	11p*
7432	27p*	22p*	18p*
7437	27p*	22p*	18p*
7441	75p*	62p*	50p*
7442	65p*	55p*	43p*
7445	85p*	71p*	57p*
7447	81p*	75p*	65p*
7448	75p*	62p*	50p*
7447A	95p*	83p*	67p*
7470	30p*	25p*	20p*
7472	25p*	21p*	17p*
7473	30p*	25p*	20p*
7474	32p*	26p*	21p*
7475	47p*	39p*	31p*
7476	32p*	26p*	21p*
7482	75p*	62p*	50p*
7485	£1.30	£1.09	87p*
7486	32p*	26p*	21p*
7489	£2.92	£2.80	£2.10
7490	49p*	40p*	32p*
7491	65p*	55p*	45p*
7492	57p*	46p*	36p*
7493	45p*	40p*	32p*
7495	67p*	55p*	45p*
74100	£1.08	89p*	72p*
74107	35p*	28p*	23p*
74121	34p*	28p*	23p*
74122	47p*	39p*	31p*
74141	78p*	63p*	53p*
74145	68p*	58p*	48p*
74154	£1.62	£1.48	86p*
74174	£1.00	83p*	67p*
74180	£1.06	88p*	71p*
74181	£3.20	£2.50	£1.90
74192	£1.35	£1.14	90p*
74193	£1.35	£1.14	90p*
74196	£1.64	£1.34	99p*

LINEAR I.C.'s

555 (8 pin dip) V	55p*
555 (TO-99) T	81p*
556 (14 pin dip)	£1.29*
703 (RF/IF Amp)	68p
709 (8 pin dip)	38p
709 (14 pin dip)	39p
710 (8 pin dip)	39p
710 (TO-99)	45p
711 (TO-99)	51p
711 (14 pin dip)	44p
720 (A.M. Radio)	£1.76
723 (14 pin dip)	55p
741 (TO-99)	43p
741 (14 pin dip)	36p
747 (14 pin dip)	£1.04
748 (8 pin dip)	42p
748 (TO-99)	46p
748 (14 pin dip)	49p
753 (F.M. Int. I.F.)	£1.08
75491	88p*
75492	£1.10*
Regulator 100 mA	
78L05WC (TO-92)	60p*
78L12WC (TO-92)	60p*
78L15WC (TO-92)	60p*
Regulator 100mA	
78L05WC (TBA625A)	90p*
78L12WC (TBA625B)	90p*
78L15WC (TBA625C)	90p*
Regulator 500mA	
78M05HC	£1.35*
78M12HC	£1.35*
78M15HC	£1.35*
78M18HC	£1.35*
78M24HC	£1.35*
Regulator 1A	
7805KC (TO-3)	£2.09*
7812KC (TO-3)	£2.09*
7815KC (TO-3)	£2.09*
7818KC (TO-3)	£2.09*
7824KC (TO-3)	£2.09*
Regulator 1A	
7805UC (TO-220)	£1.72*
7812UC (TO-220)	£1.72*
7815UC (TO-220)	£1.72*
7818UC (TO-220)	£1.72*
7824UC (TO-220)	£1.72*
ICL8030	£3.52*
LM2111	£1.12
LM3900	69p
LM3909	60p*
MC1303L	£1.94
MC1306P	85p
MC1310P	£2.10
MC1312P	£2.52
MC1314P	£4.34
MC1315P	£4.85
MC1327P	£1.48
MC1330P	89p
MC3401P	81p
MC1339P	£1.80
MC1350	69p
MC1351	92p
MC1352	92p
MC1357	£1.80
MC1358(CA3065)	£1.23
MC1375	£1.56
MC1455 (555T)	65p*
MC1456CP	£1.77
MC1458CP	89p
MC1468G	£2.30
MC1495L	£4.48
MC1496G	£1.01
MC3302P	£1.65
MC3401P	81p
MFC4000B	87p
MFC4060A	85p*
MFC6030A	85p*
MFC6040	£1.01
MM5314	£4.80
MM5316	£9.99
MVRSV (TO-3)	£1.45
MVRI2V (TO-3)	£1.45
MVRI5V (TO-3)	£1.45
NE540L	£1.25
NE546A	£1.16
NE555V	69p*
NE556	£1.29
NE560B	£5.06
NE561B	£5.06
NE562B	£5.06
NE563	£2.96
NE565N	£2.63
NE566V	£1.87
NE567V	£2.63
SD6000	£1.22
SL414A	£2.09
SL415A	£2.75
SL437D	£7.50
SL440	£2.84
SN75491N	88p*
SN75492N	£1.10*
SN76001N (TAA611)	£1.82
SN76003N	£3.30
SN76013N	£1.98
SN76023N	£1.98
SN76227N(MC1327)	£1.89
SN76532N	£1.86
SN76544N	£1.81
SN76552-2	81p
SN76550-2(TAA550)	89p
SN76660N(TBA120)	75p
SN76666N(CA3065)	£1.12
TAA263	£1.50
TAA300	£2.16
TAA310A	£1.87
TAA320	£1.44
TAA350	£2.43
TAA370	£3.45
TAA550	75
TAA570	£2.75
TAA700	£5.03
TBA120S	£1.25
TBA231	£1.02
TBA281 (723)	£2.59
TBA500Q	£3.16
TBA520Q	£3.85
TBA530Q	£3.27
TBA540Q	£3.72
TBA550Q	£5.29
TBA560CQ	£5.29
TBA625A	£1.03
TBA625B	£1.03
TBA625C	£1.03
TBA651	£1.87
TBA720Q	£2.79
TBA750Q	£2.79
TBA800	£1.11
TBA810S	£1.24
TBA810AS	£1.24
TBA820	80p
TBA920Q	£4.71
TBA990Q	£4.71
TCA270Q	£5.24
TCA760	£2.16
TCA800Q	£7.24
TCA830S	£1.04
TCA940	£2.25
TDA1054	£1.50
TDA1200	£2.43
TDA1405	80p*
TDA1412	80p*
TDA1415	80p*
TDA2010	T.B.A.
TDA2020	T.B.A.
ULN2111A	£1.52
ZN414	£1.26

3 1/2 DECADE DVM I.C.

This state-of-the-art MOS LSI chip contains all the logic necessary for a 3 1/2 decade, dual slope integrating, automatic polarity detecting DVM. Supplied with free data and circuit booklet. AY-5-3507

OUR PRICE ONLY £6.59.*

(Data and Circuit Booklets alone 20p.)

The AY-5-1224 tick-tock

Another marvel from G.I. A 16 pin 12-24 hr. Clock I.C. with 25 pin capability and low external parts count. Supplied with manufacturers detailed leaflet £3.95p*(inc. VAT) (Leaflet alone 20p.) Full Kit (excluding case) available towards end of 1975. Phone Clive for details.

MULLARD MODULES

Still make the simplest, highly reliable F.M. tuner

LP1186 Varactor front end £8.60

LP1185 I.F. Strip £6.95

LP1400 Multiplex decoder £9.02

LED DISPLAYS

Litronix Double Digit Displays

0.5" Common Anode, 2 R/H Decimal Points

DL721 1.9

DL727 0.0 to 9.9

Suitable for Clocks, Meters, Instruments, Channel Indicators

Our price £4.75 * each

Litronix DL 707 Series

0.33" Monsanto MAN 50/70/80/3600

0.33" Xcitron XAN 70 Series

0.43" Monsanto MAN 4000 Series

0.63" Litronix DL747 'Jumbo' Series

15p*

NOTE: MAN 4000 Series pin outs are 14 pin dit! the same as MAN 50, 70 and 80 series.

LIGHT EMITTING DIODES

Free snap-on plastic retainer

0.125" dia. lens (LIT 209)	0.16" dia. lens	0.2" dia. lens (MLED 650)
1" 10" 100"	1" 10" 100"	1" 10" 100"
Red	14p 15p 13p	27p 24p 22p
Green	27p 24p 22p	33p 30p 27p
Orange	27p 24p 22p	33p 30p 27p
Yellow	34p 31p 29p	35p 32p 29p

18p 16p 14p*

30p 27p 25p*

30p 27p 25p*

35p 33p 30p*

MAINS TRANSFORMERS


Pack	Price
1 Fibreglass printed circuit board for front end, I.F. strip, demodulator, AFC and mute circuits	£2.15
2 Set of metal oxide resistors, thermistor, capacitors, cermet preset for mounting on pack 1	£4.80
3 Set of transistors, diodes, LED, integrated circuits for mounting on pack 1	£6.25
4 Pre-aligned front end module, coil assembly, three-section ceramic filter	£8.80
5 Fibreglass printed circuit board for stereo decoder	£1.10
6 Set of metal oxide resistors, capacitors, cermet preset for decoder	£2.60
7 Set of transistors LED, integrated circuit for decoder	£3.45
8 Set of components for channel selector switch module including fibreglass printed circuit board, push-button switches, knobs, LEDs preset adjusters, etc.	£8.30

Pack	Price
9 Function switch, 10 turn tuning potentiometer, knobs	£5.30
10 Frequency meter, meter drive components, fibreglass printed circuit board	£8.60
11 Toroidal transformer with electrostatic screen, Primary: 0-117V-234V	£4.45
12 Set of capacitors, rectifiers, voltage regulator for power supply	£2.95
13 Set of miscellaneous parts, including sockets, fuse holder, fuses, inter-connecting wire, etc.	£1.50
14 Set of metal work parts including silk screen printed fascia panel, acrylic silk screen printed tuning indicator panel insert, internal screen, fixing parts, etc.	£6.50
15 Construction notes (free with complete kit)	£0.25
16 Teak cabinet	£9.85
One each of packs 1-16 inclusive are required for complete stereo FM tuner.	
Total cost of individually purchased packs	£76.85

STEREO FM TUNER KIT

In the April and May issues of *Wireless World* there was published a novel design for an f.m. tuner which combines consistent high performance with the elimination of the critical setting-up procedure required by too many earlier tuners. This original circuit has been developed further and is used as the basis for our new slimline unit. The front end is a ready built pre-aligned module which then feeds an amplifier driven screened three section ceramic filter leading to an integrated circuit five-stage limiting amplifier providing excellent a.m. rejection. This is followed by a single coil integrated balanced demodulator from which the audio output may be taken. Temperature compensated varicap tuning allows stations to be selected either by a ten-turn tuning potentiometer or by a choice of six preset push-button controls. Each of the preset controls can be adjusted on the front panel with the settings being indicated by six LED lamps behind an acrylic silk screen printed fascia panel insert. Additional circuitry includes temperature compensated AFC restricted to less than station spacing, inter-station muting, a single-lamp LED tuning indicator and a linear scale frequency meter. The stereo decoder, built on a separate board, is based on a well-proven integrated circuit phase-locked-loop to which has been added active filters to remove sub-carrier harmonics and 'birdies'. The power supply, to ensure station holding stability, uses an integrated circuit voltage regulator which is powered via a low-hum field specially designed TOROIDAL TRANSFORMER.

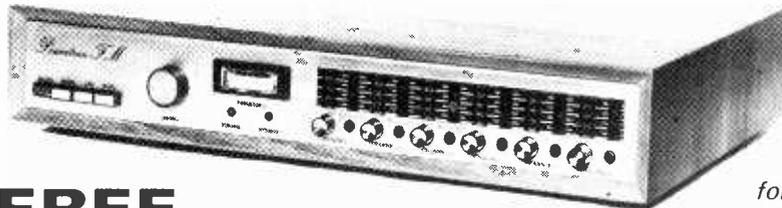STYLED TO COMPLEMENT THE WORLD-WIDE ACCLAIMED LINSLEY-HOOD 75W AMPLIFIER



FREE TEAK CASE WITH FULL KITS
 KIT PRICE only **£66.75** carriage free (U.K.)

for further information please write for FREE LIST

MORE KITS ON NEXT PAGE!

Typical P. & P. charges at November 1st (E & OE)

	L.H. 75 Watt		F.M. Tuner		T20+20	
	Air	Sea	Air	Sea	Air	Sea
Australia	£42.60	£11.40	£26.05	£7.25	£17.05	£4.65
Canada	£23.50	£8.00	£14.40	£5.05	£9.60	£3.45
Denmark	£10.50	£7.40	£6.00	£4.65	£4.75	£3.25
Germany	£10.50	£7.65	£6.00	£4.80	£4.75	£3.35
New Zealand	£41.60	£10.75	£25.25	£6.85	£16.85	£4.40
Norway	£11.40	£7.30	£6.70	£4.50	£5.20	£3.30
Rep. S. Africa	£25.00	£7.80	£15.15	£4.85	£10.35	£3.45
Sweden	£10.90	£7.25	£6.45	£4.50	£4.95	£3.25
Switzerland	£8.90	£6.85	£5.30	£4.25	£4.10	£3.10
U S A	£23.20	£9.85	£14.25	£6.30	£9.45	£4.05

EXPORT NO PROBLEM


£'s NOW HEAP CHEAP!

By special arrangement the U.K. government has continued its policy of industrial sabotage and stimulation of inflation ensuring the rapid decline in value of sterling, making it even easier for overseas readers to purchase the Powertran range of high-quality audio kits (£ down 12% against U.S. \$ in last 6 months!) Write now for postage quote

75W AMPLIFIER KIT

In Hi-Fi News there was published by Mr Linsley-Hood a series of four articles (November 1972-February 1973) and a subsequent follow-up article (April 1974) on a design for an amplifier of exceptional performance which has as its principal feature an ability to supply from a direct coupled fully protected output stage, power in excess of 75 watts whilst maintaining distortion at less than 0.01% even at very low power levels. The power amplifier is complemented by a pre-amplifier based on a discrete component operational amplifier referred to as the Linciac which is employed in the two most critical points of the system, namely the equalization stage and tone control stage, positions where most conventional designs run out of gain at the extremes of the frequency spectrum. Unusual features of the design are the variable transition frequencies of the tone controls and the variable slope of the scratch filter. There is a choice of four inputs, two equalized and two linear, each having independently adjustable signal level. The attractive slimline unit pictured has been made practical by highly compact PCBs and a specially designed Toroidal transformer.

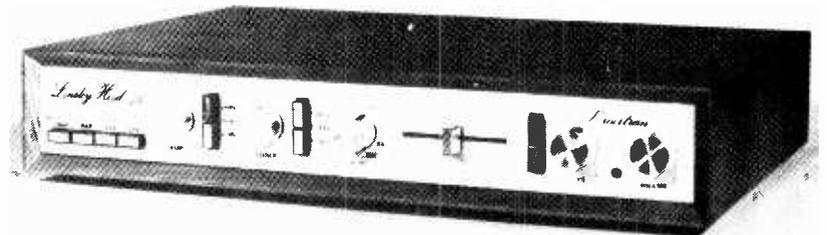Hi-Fi News Linsley-Hood 75W/Channel Amplifier Mk III Version (modifications as per Hi-Fi News April 1974)



Full circuit description in handbook (pack 15—price 30p)

FREE TEAK CASE WITH FULL KITS
 KIT PRICE only **£62.40** carriage free (U.K.)

V A T Please add 25%* to all U.K. orders

(*or at current rate if changed)
 U.K. ORDERS — Carriage free (MAIL ORDER ONLY).
 SECURICOR DELIVERY: For Securicor delivery to mainland—add £2 + VAT per kit.
 OVERSEAS—Postage at cost + 50p special packing, handling (remittance in sterling please)
Dept. WW2
POWERTRAN ELECTRONICS
 PORTWAY INDUSTRIAL ESTATE
 ANDOVER, HANTS SP10 3NN

Pack	Price
1 Fibreglass printed-circuit board for power amp	£0.85
2 Set of resistors, capacitors, pre-sets for power amp.	£1.70
3 Set of semiconductors for power amp. (now using BDY56, BD529, BD530)	£6.50
4 Pair of 2 drilled, finned heat sinks	£0.80
5 Fibreglass printed-circuit board for pre-amp.	£1.30
6 Set of low noise resistors, capacitors, pre-sets for pre-amp.	£2.70
7 Set of low noise high gain semiconductors for pre-amp	£2.40
8 Set of potentiometers (including mains switch)	£2.05
9 Set of 4 push-button switches, rotary mode switch	£3.70
10 Toroidal transformer complete with magnetic screen/housing primary: 0-117-234 V, secondaries: 33-0-33 V, 25-0-25 V.	£9.15

Pack	Price
11 Fibreglass printed-circuit board for power supply	£0.65
12 Set of resistors, capacitors secondary fuses, semiconductors for power supply	£3.50
13 Set of miscellaneous parts including DIN skts, mains input skt, fuse holder, inter connecting cable, control knobs	£4.25
14 Set of metalwork parts including silk screen printed fascia panel and all brackets, fixing parts, etc.	£6.30
15 Handbook	£0.30
16 Teak cabinet	£9.85
2 each of packs 1-7 inclusive are required for complete stereo system	
Total cost of individually purchased packs	£72.25

WW-025 FOR FURTHER DETAILS

QUALITY AMPLIFIER KITS by POWERTRAN

ELECTRONICS

20 WATTS / CHANNEL

Pack		Price
1	Set of all low noise resistors	£0.95
2	Set of all small capacitors	£1.50
3	Set of 4 power supply capacitors	£1.40
4	Set of miscellaneous parts including DIN sockets, fuses, fuse holders, control knobs, etc.	£1.90
5	Set of slide and push-button switches	£1.20
6	Set of potentiometers and selector switch	£2.00
7	Set of all semiconductors	£7.25
8	Special Toroidal Transformer	£4.95
9	Fibreglass PC Panel	£2.50
10	Complete chassis work, hardware and brackets	£4.20
11	Preformed cable/leads	£0.40
12	Handbook	£0.25
13	Teak Cabinet	£4.50

TOROIDAL T20 + 20

Developed from the famous Practical Wireless Texan

Designed by Texas engineers and published in a series of articles in **Practical Wireless**. The TEXAN was a remarkable breakthrough in delivering true Hi-Fi performance at exceptionally low cost. Now further developed to include a true Toroidal transformer, this slimline integrated circuit design, based upon a single F/Glass PCB, features all the normal facilities found on quality amplifiers, including scratch and rumble filters, adaptable input selector and headphones socket.



KIT PRICE
STILL ONLY **£28.25**
post free (U.K.)

FREE TEAK CASE and HANDBOOK with full kits

AND NOW OUR NEW T30 + 30 30 WATT VERSION!

The T20+20, already a development from the very successful Texan, has been developed still further to include all the improvements suggested in the P W July 1975 follow-up article and our new model offers RF interference filters, tape monitor facility and an additional 10 watts/channel of power

Pack		Price
1	Set of all low noise resistors	£1.05
2	Set of all small capacitors	£2.10
3	Set of 4 power supply capacitors	£2.05
4	Set of miscellaneous parts including DIN sockets, fuses, fuse holders, control knobs, etc.	£1.90
5	Set of slide and push button switches	£1.20
6	Set of potentiometers and selector switch	£2.00
7	Set of all semiconductors	£7.75
8	Special Toroidal Transformer	£6.80
9	Fibreglass PC Panel	£2.90
10	Complete chassis work, hardware and brackets	£4.80
11	Preformed cable leads	£0.40
12	Handbook (free with complete kit)	£0.25
13	Teak Cabinet	£4.50

FULL KIT (WITH FREE TEAK CASE) ONLY £32.95

WIRELESS WORLD AMPLIFIER DESIGNS

Component packs for a choice of three outstanding amplifiers are stocked together with packs for a regulated power supply suitable for use with a pair of any of them. Also stocked are packs for a very well-established pre-amplifier—the Bailey-Burrows design which features six inputs, a scratch and rumble filter and wide range tone controls which may be either rotary or slider operating.

30W BAILEY

Pk. 1 F/Glass PCB	£1.00
Pk. 2 Resistors, capacitors, pots	£2.35
Pk. 3 Semiconductor set	£4.70

20W LINSLEY-HOOD

Pk. 1 F/Glass PCB	£1.05
Pk. 2 Resistors, capacitors, pots	£3.20
Pk. 3 Semiconductor set	£3.35

60V REGULATED POWER SUPPLY

Pk. 1 F/Glass PCB	£0.95
Pk. 2 Resistors, capacitors, pots	£1.95
Pk. 3 Semiconductor set	£3.10

BAILEY-BURROWS PRE-AMP

Pk. 1 F/Glass PCB	£2.35
Pk. 2 Resistors, capacitors, pre-sets, transistors	£6.10

Pk. 3R Rotary potentiometer set	£2.00
Pk. 35 Slider potentiometer set (with knobs)	£2.70

STUART TAPE RECORDER

A set of three printed-circuit boards has been prepared for the stereo integrated circuit version of this high-performance *Wireless World* published design.

TRRP Pk. 1 Replay amplifier F/Glass PCB	£1.10
TRRC Pk. 1 Record amp./meter drive cct. F/Glass PCB	£1.60
TROS Pk. 1 Bias/erase/stabilizer cct. F/Glass PCB	£1.20

For details of component packs for this design please write for free list.

ACTIVE FILTER CROSSOVER

An essential and critical component in a high-quality speaker system is the crossover unit conventionally comprising of a series of passive networks which unfortunately, though introducing reactive impedances between the amplifier and the speakers, result in the loss of the advantage of high amplifier damping factor and renders the speakers prone to overshoots and resonances. An elegant solution to this problem, described by D. C. Read in **Wireless World**, involves the use of a series of active filters splitting the output of the pre-amplifier into three channels, of closely defined bandwidth, each of which is fed to the appropriate speaker by its own power amplifier. A design for a suitable 20-watt amplifier, based on a proven Texas circuit, was also described by Mr Read. The printed-circuit board for this has been designed such that three amplifiers may be stacked and mounted together on a common heat sink to achieve a conveniently compact module.

ACTIVE FILTER

Pack		
1	Fibreglass PCB (accommodates all filters for one channel)	£1.05
2	Set of pre-sets, solid tantalum capacitors, 2% metal oxide resistors, 2% polystyrene capacitors	£4.20
3	Set of semiconductors	£2.65
2 off each pack required for stereo system		

READ/TEXAS 20w amp.

Pack		£0.70
1	Fibreglass PCB	
2	Set of resistors, capacitors pre-sets (not including O/P coupling capacitors)	£1.10
3	Sets of semiconductors	£2.40
6 off each pack required for stereo system		
4	Special heat sink assembly for set of 3 amplifiers	£0.85
5	Set of 3 O/P coupling capacitors	£1.00
2 off packs 4, 5 required for stereo system		

POWER SUPPLY

FOR 20W/CHANNEL STEREO SYSTEM		
Pack		£0.50
1	Fibreglass PCB	
2	Set of rectifiers, zener diode, capacitors, fuses, fuse holders	£2.60
3	Toroidal transformer	£4.95

SUITABLE ALSO FOR FEEDING ANY OF OUR HIGH-POWER DESIGNS

MORE KITS ON PAGE 89

SEMICONDUCTORS

as used in our range of quality amplifiers

2N699	£0.25	BFY51	£0.20
2N1613	£0.20	BFY52	£0.20
2N1711	£0.25	CA3046	£0.70
2N2926G	£0.10	LP1186	£5.50
2N3055	£0.45	MC1310	£2.90
2N3442	£1.20	MC1351	£1.05
2N3711	£0.09	MFC4010	£0.95
2N3904	£0.17	MJ481	£1.20
2N3906	£0.20	MJ491	£1.30
2N4062	£0.11	MJE521	£0.60
2N4302	£0.60	MPSA05	£0.25
2N5087	£0.42	MPSA12	£0.55
2N5210	£0.54	MPSA14	£0.35
2N5457	£0.45	MPSA55	£0.25
2N5459	£0.45	MPSA65	£0.35
2N5461	£0.50	MPSA66	£0.40
2N5830	£0.30	MPSU05	£0.60
40361	£0.40	MPSU55	£0.70
40362	£0.45	SB8750A	£2.50
BC107	£0.10	SL301	£1.30
BC108	£0.10	SL3045	£1.60
BC109	£0.10	SN72741P	£0.40
BC109C	£0.12	SN72748P	£0.40
BC125	£0.15	TL209	£0.30
BC125	£0.15	TIP29A	£0.50
BC182	£0.10	TIP29C	£0.71
BC212	£0.12	TIP30A	£0.60
BC182K	£0.10	TIP30C	£0.78
BC212K	£0.12	TIP41A	£0.74
BC182L	£0.10	TIP42A	£0.90
BC184L	£0.11	TP 41B	£0.82
BC212L	£0.12	TIP 42B	£0.98
BC214L	£0.14	1N514	£0.07
BCY72	£0.13	1N916	£0.07
BD529	£0.85	1S920	£0.10
BD530	£0.85	5805	£1.20
BDY56	£1.60	FILTERS	
BF257	£0.40	FM4	£0.80
BF259	£0.47	SFG10.7MA	£2.80
BF839	£0.25		
BF879	£0.25		

V.A.T. Please add 25%* to all U.K. orders

(*or at current rate if changed)

U.K. ORDERS—Post free (mail order only)

SECURICOR DELIVERY—for this optional service (Mainland only) add £2.00 + VAT per kit

OVERSEAS—Postage at cost + 50p special packing, handling (remittance in sterling please)

Dept. WW2

POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE ANDOVER, HANTS SP10 3NN

Look AT THESE PRICES AND BUY QUALITY

VALVES

Type	Price (p)
DY87	30 0
DY802	30 0
ECC82	28 0
EF80	29 5
EF183	34 5
EF184	34 5
EH90	35 5
PC900	24 5
PCC89	40 0
PCC189	41 0
PCF80	31 5
PCF86	39 0
PCF801	42 0
PCF802	40 0
PCL82	39 0
PCL84	39 0
PCL85	44 5
PCL86	41 0
PFL200	59 5
PL36	55 5
PL84	25 0
PL504	64 5
PL508	67 0
PL519	£1 20
PY88	35 5
PY800	33 0
PY500A	85 0

SEMI CONDUCTORS

Type	Price Each (p)
AC127	17
AC128	13
AC141K	25
AC142K	25
AC151	20
AC154	18
AC155	18
AC156	20
AC176	22
AC187	19
AC187K	24
AC188	17
AC188K	26
AD142	45
AD149	40
AD161	38
AD162	38
AF114	24
AF115	21
AF116	22
AF117	19
AF118	50
AF139	35
AF178	45
AF180	45
AF181	45
AF239	40
AF240	60
BC107	11
BC108	10
BC109	14
BC109C	14
BC113	13
BC116A	19
BC117	14

Price Each (p)

Type	Price Each (p)
BC125B	15
BC132	25
BC135	15
BC137	19
BC138	26
BC142	23
BC143	25
BC147	11
BC147A	11
BC148	10
BC149	10
BC153	15
BC154	15
BC157	14
BC158	10
BC159	11
BC173	18
BC178B	20
BC182L	12
BC183L	12
BC187	25
BC214L	15
BC328	28
BC337	19
BD124	75
BD131	45
BD132	39
BD160	£1 39
BD235	49
BD237	52
BDX32	£2 40
BF115	20
BF160	15
BF167	20
BF173	20
BF178	35
BF179	40
BF180	31
BF181	32
BF184	25
BF185	25
BF194	9
BF195	8
BF196	10
BF197	12
BF198	23
BF200	25
BF218	30
BF224	23
BF258	34
BF336	28
BF337	35
BF355	54
BFX86	28
BFY50	19
BFY52	20
BSY52	35
BT106	£1 20
BU105/02	£1 95
BU108	£2 10
BU208	£2 95
E1222	30
MJE340	45
OC71	15
OC72	16

Price Each (p)

Type	Price Each (p)
R2008B	£2 00
R2010B	£2 00
RCA16334	80
RCA16335	80
TIP31A	57
TIP32A	67
TIP41A	67
TIP42A	80
2N3055	55

DIODES

Type	Price Each (p)
BA115	7
BA145	14
BA148	19
BA154/201	11
BY126	11
BY127	12
BY199	27
BY206	21
BY238	25
OA90	6
OA202	7 5
IN60/OA91	5
IN914	6
IN4002	5

INTEGRATED CIRCUITS

Type	Price Each (p)
ETTR6016	£2 00
MC1351P	70
SN76003N	£2 35
SN76013N	£1 50
SN76013ND	£1 50
SN76023N	£1 50
SN76023ND	£1 45
SN76033N	£2 35
SN76227N	£1 45
SN76532N	£1 45
SN76660N	58
SN76666N	87
TAA550	49
TAA700	£2 95
TBA120AS	£1 00
TBA120SQ	£1 00
TBA480Q	£1 40
TBA520Q	£2 35
TBA530Q	£1 75
TBA540Q	£1 75
TBA550Q	£2 90
TBA560CQ	£2 40
TBA800	£1 50
TBA920Q	£2 90
TBA99CQ	£2 90
TCA270Q	£2 90

EHT MULTIPLIERS MONOCHROME (BRC) Price Each

2HD 950MK1	960
	£1 70
2TQ 950MK2	1400
	£1 85
2DAK 1500 (17" & 19")	£1 85
2TAK 1500 (23" & 24")	£2 00

EHT MULTIPLIERS COLOUR

Type	Price Each
11TAQ ITT CVC 1, 2 & 3	£4 50
11TN GEC Sobell	£4 50
11TAZ GEC 2110	£4 85
11TAM Philips G8	£4 50
11TBD Philips 550	£4 50
3TCW Pye 691/693	£3 50
11TH Decca 30 Series	£4 50
11TAQ Decca Bradford	£4 50
3TCU Thorn 3000/3500	£5 00
11HAA Thorn 8000	£1 90
11HAB Thorn 8500	£4 25

New TOSHIBA TUBES

with 12 months in service guarantee

19" A49-191X equivalents	
A49-192 and A49-120X	£48 95
20" 510DJB22 equivalent	
A51-110X	£50 75
22" A56/120X	£54 25

PRICES SUBJECT TO 25% V.A.T.

All goods subject to settlement discount of 5% 7 days and 2% monthly. No postage charges or minimum order values. Write or phone for full details now.



PRICE QUALITY SERVICE




COMBINED PRECISION COMPONENTS (PRESTON) LTD

Department W, 194-200 North Rd, Preston PR1 1YP, Tel: 55034, Telex: 677122.

HART ELECTRONICS

Audio Kit Specialists since 1961

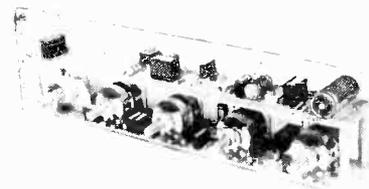

BAILEY/BURROWS/QUILTER PRE AMP This is the tone control section of the best pre-amp kit currently available. Consider the advantages:—*First quality fibreglass printed circuits with roller tinned finish and all component locations printed on reverse. *Low noise carbon film and metal film resistors throughout. *Finest quality low-noise ganged controls with matched tracks and shafts cut to length. *Well engineered layout for total stability. *Special decoupling and earthing arrangements to eliminate hum loops. *Controls, switches and input sockets mount directly on the boards to TOTALLY ELIMINATE wiring to these components. (We know of one pre-amp kit which claims its controls mount directly on the board—and so they do, by their shaft bushes! You still have to wire them up!!)

*We incorporate the Quilter modification which is most important as it reduces distortion and increases the bass and treble control range.

As can be seen from the photograph the tone control unit is very slim (only 1 1/2" from front to back) and may therefore be used in many other applications than our Bailey metalwork which it is designed to fit.

F.M. TUNER. Several useful modifications have been made to our compact tuner. The mechanical layout with all its advantages is retained and four important electrical extras are now offered. 1. Multi-turn preset pots for easier tuning. 2. MPX filter for trouble free taping. 3. Extra thermal stabilisation for tuning line to eliminate drift. 4. Provision for remote control tuning of as many stations as you require.

STUART TAPE CIRCUITS Our printed circuits and components offer the easy way to convert any suitable quality deck into a very high quality Stereo Tape unit. Input and output levels suit Bailey pre-amp. Total cost varies but around £35 is all you need. We can offer tape heads as well if you want new ones. All above kits have fibreglass PCB's. Prices exclude VAT but P&P is included.

FURTHER INFORMATION ON ALL KITS FREE if you send us a 9 in. x 4 in. S.A.E.

REPRINTS Post free, no VAT.

Bailey 30W 18p.

STUART TAPE RECORDER All 3 articles under one cover 30p.

BAILEY/BURROWS/QUILTER Preamp circuits, layouts and assembly notes 15p.

All prices exclude VAT.

Penylan Mill, Oswestry, Salop

Personal callers are always welcome but please note we are closed all day Saturday

ADVANCED CLOCK KIT

Complete kit including attractive slim case for 6 digit alarm clock with beep alarm, snooze and automatic intensity control, high brightness display driving with optional touch switch controls and crystal control/battery-back-up (both extra) using MK50253 and LED displays. Kit also includes PCBs, active and passive components, IC socket, miniature coil transformer, switches, flat cable, loudspeaker, mains plug and lead, perspex panel, and full instructions. With 0.5" JUMBO FND500 Displays **£27.31**

SEND LARGE S.A.E. FOR DETAILS AND PRICES OF THIS MONTH'S P.E. CAR/BOAT CLOCK/JOURNEY TIMER OR PHONE FOR IMMEDIATE DESPATCH.
SEND LARGE S.A.E. FOR DETAILS OF OUR MODULAR STOPWATCH SYSTEM USING CMOS.
SEND LARGE S.A.E. FOR DETAILS OF ATTRACTIVE SIMPLE 4 DIGIT GREEN CLOCK 50Hz CRYSTAL TIMEBASE KIT FOR CLOCKS INCL. ADVANCED KIT ABOVE **£6.28**

CMOS ICs	CD4031	1.82	CD4062	7.33	CD4518	1.03	DISPLAY INT.		
RCA MOT. ONLY	CD4032	0.88	CD4063	0.90	CD4520	1.03	SN75491	0.81	
CD4000	0.17	CD4033	1.14	CD4066	0.58	CD4527	1.30	SN75492	1.02
CD4001	0.17	CD4034	1.59	CD4067	2.95	CD4532	1.16	7444	1.05
CD4002	0.17	CD4035	0.97	CD4068	0.18	CD4555	0.74	7448	0.85
CD4006	0.97	CD4036	1.82	CD4069	0.18	CD4556	0.74		
CD4007	0.17	CD4037	0.78	CD4070	0.18	MC14508	2.37	FLAT CABLE	
CD4008	0.79	CD4038	0.88	CD4071	0.18	MC14528	0.86	20WAY 1M	1.00
CD4009	0.46	CD4039	2.86	CD4072	0.18	MC14534	6.04	10M for	8.50
CD4010	0.46	CD4040	0.88	CD4073	0.18	MC14553	4.07	10WAY 1M	0.60
CD4011	0.17	CD4041	0.69	CD4075	0.18	MC14566	1.21	10M FOR	4.80
CD4012	0.17	CD4042	0.69	CD4076	1.27	MCM14552	8.05		
CD4013	0.46	CD4043	0.83	CD4077	0.18			IC SOCKET PINS	
CD4014	0.83	CD4044	0.77	CD4078	0.18			100	0.50
CD4015	0.83	CD4045	1.15	CD4081	0.18	CLOCK CHIPS		1000	4.00
CD4016	0.46	CD4046	1.10	CD4082	0.18	MK50253	5.60	3000	10.50
CD4017	0.83	CD4047	0.74	CD4085	0.59	MM5314	4.44		
CD4018	0.83	CD4048	0.46	CD4086	0.59	AY51224	3.66	LSI SOCKETS	
CD4019	0.46	CD4049	0.46	CD4089	1.27	AY51202	4.76	PINS + SUP.	
CD4020	0.92	CD4050	0.46	CD4093	0.66			24 PIN	0.30
CD4021	0.83	CD4051	0.77	CD4094	1.53	CMOS BOOKS		28 PIN	0.30
CD4022	0.79	CD4052	0.77	CD4095	0.86	No VAT or P&P		40 PIN	0.30
CD4023	0.17	CD4053	0.77	CD4096	0.86	RCA11975	2.67		
CD4024	0.64	CD4054	0.95	CD4099	1.50	MCMOS	2.77	VEROCASES	
CD4025	0.17	CD4055	1.08	CD4502	0.98			751410J	2.64
CD4026	1.42	CD4056	1.08	CD4510	1.12			751411D	3.04
CD4027	0.46	CD4057	20.35	CD4511	1.28	DISPLAYS		751412K	4.00
CD4028	0.74	CD4059	10.64	CD4514	2.56	SLT 01	5.80		
CD4029	0.94	CD4060	0.92	CD4515	2.56	DL70AE	0.85		
CD4030	0.46	CD4061	16.43	CD4516	1.12	FND500	1.50		

ADD VAT at 8% (Higher rate does not apply to any of above). 15p P&P on orders under £3 — Despatch is by 1st Class post. Price list and data sent FREE with an order, or on request (an SAE helps). Official orders welcomed (written or phoned) — Univs. Polys. Govt. Cos. etc. Export orders. No VAT. Add 35p (Europe) £1 (Overseas) for Airmail P&P.

SINTEL 53C ASTON STREET, OXFORD
TEL. 0865 43203

WWW-015 FOR FURTHER DETAILS

KINNIE COMPONENTS

10 NEMES WAY,
HORNCHURCH, ESSEX RM11 2QZ
HORNCHURCH 45167

COPPER LAMINATE P.C. BOARD
8.4 x 7.7 inch, 3 for **75p.** P.P. 25p
9.45 x 8.15 inch, 3 for **90p.** P.P. 30p
10.10 x 7.90 inch, 3 for **£1.** P.P. 30p
13.1 x 9.4 inch, 3 for **£1.20.** P.P. 30p
17 x 9.5 inch, 2 for **£1.20.** P.P. 30p

MONSTER PACK
10 PIECES 10 1/2 in x 7.90 in PLUS FREE BOTTLE OF
CIRCUIT ETCHANT **£2.50.** P.P. 50p

TELEPHONE DIALS (new) **£1.** P.P. 15p
EXTENSION TELEPHONES (Type 706) Various colours **£3.95.** P.P. 75p
RATCHET RELAYS (310 ohm) Various types **£1.20.** P.P. 20p
UNISELECTORS (New) 25 way, 12 Bank (Non bridging). 68 ohms **£6.50.** P.P. 50p
MINIATURE UNISELECTOR
(Ex. Equip.) 6 Bank (5 non bridging, 1 bridging 100 ohms 24-30 V D.C.) **£1.50.** P.P. 50p



OVERLOAD CUT-OUTS. Panel mounting (1 3/4 x 1 1/4 x 1/2 in). 800 M/A/1 8 amp -10 amp **45p.** P.P. 5p

ADVANCE TRANSFORMERS "VOLSTAT". Input 240v A.C.
C.V.50. 38v at 1 amp, 25v. at 100 m/a, 75v at 200 m/a **£3.** P.P. 65p
C.V.75. 25v at 2 1/2 amp, **£3.25.** P.P. 75p
C.V.100. 50v at 2 amp, 50v. at 100 m/a, **£4.** P.P. 75p
C.V.250. 25v at 8 amp; 75v at 1/2 amp, **£6.50.** P.P. £1 50
C.V.500. 45v at 3 amp; 35v at 2 amp, **£12.** P.P. £1 75
H.T. TRANSFORMER. Prim 110/240v Sec 400v 100 m/a **£3.** P.P. 65p
L.T. TRANSFORMER "TOROIDAL". Prim 240v Sec 30v at 1/2 amp. Size 3 in. dia., 1" thick **£1.65.** P.P. 20p
L.T. TRANSFORMER. Prim 240v Sec 27-0-27 at 800 m/a 7.5 amp, **£2.25.** P.P. 50p
L.T. TRANSFORMER. Prim. 110/240v Sec 50v. at 10 amp **£10.** P.P. £1 50
L.T. TRANSFORMER. Prim 240v Sec 18v at 15 amp & 12v @ 1 amp, **£2.25.** P.P. 50p
L.T. TRANSFORMER. Prim 240v. Sec 18v 1 amp, **£1.** P.P. 20p
L.T. TRANSFORMER. Prim 240v Sec 12v at 1 amp **70p.** P.P. 25p

ALL PRICES INCLUDE V.A.T. EXCEPT WHERE SURCHARGE IS INDICATED.

QUADROPHONIC DECODER MODULE. C.B.S./S.Q. Type, using I.C. MC 1312P. With slight modification direct substitute for P.E. "RONDO" Board. Complete with Data. **£4** each

15% V.A.T. Surcharge

S.T.C. CRYSTAL FILTERS (10.7 Mhz). 445-LQU-901A (50 Khz spacing). **£3.** P.P. 20p 445-LQU-901B (25 Khz spacing). **£4.** P.P. 20p 10.7 M.H.Z Canned I.Fs. Size 1 x 1/2 x 1/2 in (with data) **65p.** P.P. 10p.

3 GANG TUNING CAPACITOR 8.5 PF to 320 PF **80p.** P.P. 20p.

V.H.F./U.H.F. POWER TRANSISTORS (type BLY38) 3 watt output at 100-500 Mhz. **£2.25.** P.P. 10p.

MINIATURE METERS 500 Micro amp. (level/stereo beacon etc.) scaled half black/half red. Size 1 x 1 inch **65p.** P.P. 15p.

HIGH CAPACITY ELECTROLYTICS
2,200 uF/100v (4 x 1 1/4 in.) **90p.** P.P. 20p 2,500 uF/100v (4 x 2 in) **90p.** P.P. 20p. 4,700 uF/25v (2 x 1 1/4 in.) **65p.** P.P. 15p. 10,000 uF/25v (4 1/2 x 1 1/2 in) **75p.** P.P. 25p 25,000 uF/40v (4 1/2 x 2 1/2 in) **£1.25.** P.P. 25p 47,000 uF/40v Powerlytic (5 1/2 x 3 in) **£2.** P.P. 50p 100,000 uF/10v Powerlytic (4 1/2 x 3 in) **£1.50.** P.P. 30p 160,000 uF/10v Powerlytic (6 x 3 in) **£2.** P.P. 50p

MULTICORE CABLE. 6-core (6 colours) 14/0076 Screened P.V.C. **22p** per yard; 100 yards at **£16.50.** P.P. 2p a yard. 7-core (7 colours) 7/22mm. Screened P.V.C. **22p** per yard; 100 yards **£16.50.** P.P. 2p per yard. 30-core (15 colours) **25p** per yard; 100 yards **£20.** P.P. 2p per yard

RIBBON CABLE (B colours) 10m: **£1.65.** P.P. 20p 100m: B-core 7/ mm Bonded side by side **£11.50.** P.P. £1

TRANSFORMERS

L.T. TRANSFORMER. Prim. 110/240v Sec 23/24/25v at 10 amps. **£7.** P.P. £1.
L.T. TRANSFORMER. Prim 110/240v Sec 20/21/22v at 8 amp. **£6.** P.P. £1.
L.T. TRANSFORMER. Prim. 110/240v Sec 0/24/40v at 1 1/2 amp (Shrouded) **£1.95.** P.P. 50p.
L.T. TRANSFORMER. Prim. 200/250v Sec 20/40/60v at 2 amp. (Shrouded) **£3.** P.P. 50p
L.T. TRANSFORMER. (H.D.) Prim 200/250v Sec. 18v at 27 amp. 40v at 9.8 amp.; 40v at 3.6 amp.; 52v at 1 amp. 25v at 3.7 amp. **£17.50.** P.P. £2.50

WE REGRET THAT ALL ORDERS VALUE UNDER £5 MUST BE ACCOMPANIED BY THE REMITTANCE.

HIGH - SPEED MAGNETIC COUNTERS. 4 digit (non reset) 24v or 48v (state which), 4 x 1 x 1 in **85p.** P.P. 15p
5 digit (non reset) 24v. **£1.50.** P.P. 15p
3 digit 12v (Rotary Reset) 2 1/4 x 1 1/4 x 1 1/4 in **£1.30.** P.P. 15p; 6 digit (Reset) 240v A.C. **£3.50.** P.P. 25p



H.D. ALARM BELLS. 6 in. Dome, 6/8v. d.c. Heavy cast housing for exterior/interior use **£3.75.** P.P. £1. Connecting wire (twin/twisted) 220v. reel **£3.** p.p. 75p.

MINIATURE REED RELAYS (3/6v). 1 make (30 x 8mm) **20p;** 2 make (32 x 12mm) **30p.** P.P. 5p. 12v. 2 c/o 5 amp. H.D. RELAY **65p.** P.P. 15p. 240v A.C. RELAY (PLUG-IN TYPE) 3 c/o. 10 amp contact with base **85p.** P.P. 25p

GARRARD PLINTH & COVER. For "Zero-100" etc. beautifully finished in brushed aluminium add black with hinged smoke/grey perspex lid. **£0.75** P.P. £1.

24v. A.C. RELAY (PLUG-IN). 3 pole c/o **75p.** P.P. 15p. 2-pole change over **55p.** P.P. 15p

BULK COMPONENTS OFFER. Resistors/Capacitors. 600 new components. **£2.50.** P.P. 35p. Trial order 100pcs. **60p.** P.P. 20p **15% V.A.T.**

D.C. SUPPLY. Input 240v a.c. giving 17 1/2v d.c. @ 1 1/2 amp. (unsmoothed) 2 1/2 x 2 1/2 x 2 1/2 in **£2.25p.** p.p. 45p.

MINIATURE "ELAPSED TIME" INDICATORS. (0-5000 hours) 45 x 8mm **75p.**

L.T. TRANSFORMER prim 240v Sec 20v @ 2.5 amp. **£2.** P.P. 50p
L.T. TRANSFORMER ("C" CORE) 200/240v. Secs. 1-3-8-9v All at 1.5 amp 50v at 1 amp. **£250.** P.P. 50p.
L.T. TRANSFORMER ("C" CORE). 200/240v Secs. 1-3-9-27v All at 4 amp. **£4.** P.P. 50p
L.T. TRANSFORMER ("C" CORE) 200/240v Secs. 1-3-9-27v All at 10 amp **£7.50.** P.P. £1.50.
L.T. TRANSFORMER ("C" CORE). 200/240v Secs. 1-3-9-20v All at 4 amp. **£5.50.** P.P. 75p
L.T. TRANSFORMER ("C" CORE) 120/120v. Secs. 1-3-9-9v. All at 10 amp. **£6.50.** P.P. £1.50.
L.T. TRANSFORMER ("C" CORE). 110/240v. Secs. 1-3-9v. 10 amp 35v. 1 amp.; 50v. 750 M/A **£6.50.** P.P. £1.50.

MAIL ORDER ONLY. PERSONAL CALLERS BY APPOINTMENT.

RADFORD HD250

High Definition Stereo Amplifier

A new standard for sound reproduction in the home! We believe that no other amplifier in the world can match the overall specification of the HD250.

Rated power output: 50 watts av. continuous per channel into any impedance from 4 to 8 ohms, both channels driven.

Maximum power output: 90 watts av. per channel into 5 ohms.

Distortion, preamplifier: Virtually zero (cannot be identified or measured as it is below inherent circuit noise.)

Distortion, power amplifier: Typically 0.006% at 25 watts, less than 0.02% at rated output (Typically 0.01% at 1 KHz)

Hum and noise: Disc. -83dBV measured flat with noise band width 23 KHz (ref 5mV); -88dBV "A" weighted (ref. 5mv)

Line -85 dBV measured flat (ref 100v)
-88dBV "A" weighted (ref 100v)

Hear the HD250 at
SWIFT OF WILMSLOW
Dept. www
5 Swan Street, Wilmslow, Cheshire (Tel. 26213)
Mail Order and Personal Export enquiries: Wilmslow Audio, Swan Works, Bank Square, Wilmslow (Tel. 29599)
In stock: All Radford speaker drive units and crossovers, ZD22 preamp, Low Distortion oscillator LD03 and Distortion Measuring set DMS3.

WW-027 FOR FURTHER DETAILS

SINCLAIR CALCULATORS

Cambridge **£8.95.** Scientific **£13.95.** Oxford 100 **£8.95.** Oxford 200 **£13.95.** Oxford 300 **£22.95.**
Programmable Scientific P.O.A. Oxford mains adaptor **£3.19.** Mains adaptor for Cambridge, Cambridge Memoery and Scientific **£3.15.**

S-DECS AND T-DECS

S-DeC **£2.24**
T-DeC **£4.05**
µDeC **£4.45**
µDeC **£7.85**
IC carriers:
16 dll: plain **£1.18**
With socket **£2.21**
10TDS: plain **£1.09.** With socket **£2.08.** SST1 3 for **£2.** SST1 3 for **£2.40.** 25p off any order accompanied by PB Electronics Coupon.

BATTERY ELIMINATORS

6-WAY SPECIAL
Switched output of 3, 4, 6, 7, 9, 12V at 500mA with unique 4-way multi jack connector and free matching socket. **£4.95.**

3-WAY MODEL
Switched output of 6, 7, 9V at 250mA with unique 4-way multi-jack connector and free matching socket. **£2.95.**

RADIO MODELS
50mA with poppet battery terminals for radios, etc. 6V **£2.95.** 9V **£2.95.** Double 4 1/2 + 4 1/2V **£3.95.** 6+6V **£3.95.** 9+9V **£3.95.**

CASSETTE MAINS UNITS
7 1/2V output. Complete with 5 pin DIN plug to run cassette tape recorders from the AC mains. **£3.45.**

CBM CALCULATORS

*776MD 7 digits/%/memory **£7.18.**
*887D 8 digit/%/memory/constant; **£9.95.** 385R 8 digit/%/const/rechargeable **£10.85.** *GL976MD **£9.50.** GL976MR **£13.60.** *GL997D **£11.95.** GL997R **£15.30.** SR7919D 8 digit/power/roots/memory/scientific notation/Q/trig/log **£14.55.** SR14148R **£42.95.** Mains unit for machines **£2.95.** Others include mains units.

SINCLAIR IC20 AMPLIFIER

IC20 10W+10W stereo amp kit with free booklet and printed circuit. **£8.58.**
PZ20 power supply kit for above. **£5.91.**
VP20 volume, tone control and preamp kit with printed circuits. **£7.95.**
SP20 10W 4-loudspeaker... **£2.95.**
SEND SAE FOR FREE LEAFLET

SINCLAIR PROJECT 80

AFU **£7.55.** FM tuner **£13.25.** Decoder **£8.55.** Z40 **£5.75.** Z60 **£7.10.** PZ8 **£8.20.** Trans for PZ8 **£5.40.** Stereo 80 **£9.95.** PZ5 **£3.95.** Project 805 **£28.95.** PZ6 **£8.70.**

JC12 AMPLIFIER

6W TC audio amp with free data and printed circuit **£2.80.** Special offer only **£2.45** if bought with deluxe kit.

DELUXE KIT FOR JC12

Includes all parts for the pcb and vol. bass and treble controls for mono version **£2.29.** Stereo version with balance control **£4.95.**

JC12 POWER KIT

Supplies 28V at 0.5 Amps **£2.95.**

JC12 PREAMP KITS

Type 1 for magnetic pickups, mics and tuners. Mono model **£1.95.** Stereo **£3.45.** Type 2 for ceramic or crystal pickups. Mono **95p.** Stereo **£1.90.**
SEND SAE FOR FREE DATA

Prices include post and VAT. Overseas customers please deduct VAT (8% on calculators and S-DeCs and T-DeCs, otherwise 25%). Official orders from schools, etc. welcome

SWANLEY ELECTRONICS

DEPT. WW, PO BOX 68, SWANLEY, KENT, BR8 8TQ



TRAMPUS ELECTRONICS LTD. WINDSOR

58-60 GROVE RD. WINDSOR, BERKS. SL4 1HS. ADD 8% VAT TO PRICES MARKED * ADD 3% VAT TO ALL OTHER PRICES SEND C.W.O. (EXCEPT GOVT DEPTS) POST & PACKING 20P FOR THE UK

NEW FAST SERVICE. LOW PRICES. MONEY BACK IF NOT SATISFIED. ALL BRAND NEW TOP GRADE FULL SPEC DEVICES. CALLERS WELCOME NEW CATALOGUE LIST FREE SAE. BARCLAYCARD & ACCESS BY POST. SORRY NO SALES TELEPHONE.

FAST SERVICE



DL707 COM. ANODE & DL704 COM. CATH. 0.3" 0-9dp 85p*ea. 747 JUMBO 0.8" CA LED DISPLAY £1.89* 3015P 0-9dp £1.20* DL33 MINI 3 DIGIT & MAGNIFIER £1.25* STROBE TUBE £5*

LEDS red 12P.

209 STYLE OR 0.2" NO CLIP 12p* TIL209 or 0.2" RED & CLIP 14p* GREEN LARGE/SMALL & CLIP 19p* ORANGE LARGE/SMALL & CLIP 19p* ORP12 57m* 2N5777 33p* TEC12 50p* DIGITAL CLOCKS MM5316 £5* MM5314 £3.39* MM5311 £5* AY51224 £3.49* PCB £1*

CAPACITORS

CERAMIC 22pf-0.1uf 50v 5p. ELECTROLYTIC: 10/50/100 uf in 25V 7p. 50V 9p. 2uf/10V 6p. 1000uf 25V 18p. 200/500uf 9p. POTENTIOMETERS LIN/LOG 14p. PRESETS 6p. RESISTORS 14p ea

HEATSINKS: T05 & T016 5p* TV4 15p* TV3/T03 14p* EXTRUDED 4" 4Y1 29p*

SWITCHES: SPST 18p. DPDT 25p. DIN PLUGS ALL 12p. SOCKETS ALL 9p

ALI CASES AB5/AB7 50p. AB13 65p* TRANSFORMERS 1/1A 6 or 12V £1.50*

TRAMPUS FULL SPEC PAKS ALL £1 ea

PAK A 10 RED LEDS our choice £1* PAK B 5 741C OP V1P 8 PIN £1* PAK C 1 2N3055 1.5" D 12 BC1061* PAK E 10 BC182 £1.10 11 2N3704 £1 PAK G 8 BFY51 £1.10 9 2N3819ec £1 PAK J 9 2N3053 £1.10 4 40 1N914 £1 NEW PAK M 4 PLASTIC 3055 90W £1*

IC'S LOW PRICES

703 RF/IF	26p	MC1303	£1.50
709 T099	22p*	MC1310	£2.20
709 DIL 14	28p*	MC1312 SQ	£2.50
710 DIL 14	31p*	MC1318	£2.50
723 Regular	45p*	MC1330	75p
741 DIL 8	21p*	MC1339	£1.40
741 DIL 14	31p*	MC1350/1/2	75p
741 T099	31p*	MC1466 /9	£3
747 2x741	67p*	MFC4000 1W	49p
748 DIL 8	27p*	NE536 FETOPA	£2*
7805 5V	£1.25*	NE540	£1.10*
7812 12V	£1.25*	NE550 2vr	£1*
7815 15V	£1.25*	NE555 TIMER	42p*
7900 Series	£2*	NE556 2x	88p*
76013 6W AF	75p	NE560 PILL	£4.00
CA3046	54p	NE561 PILL	£4.00
CA3048	£2	NE562 PILL	£4.00
CA3054	£1.50	NE563	£2.25
ICL8038 SGEN	£3*	NE565	£2.50
LM300	£1.50*	NE566	£1.55
LM301 OPA	41p*	NE567	£2.20
LM304 0-40V	£3*	SN72741	741 21p*
LM308 HI Bo	95p*	SN76660 IF	75p
LM309K 5V	£1.75*	SN76611 IF	£1
LM372 IF	£2.00	TAD100 8IP	£2*
LM377 2x2W	£3	TBA800	89p
LM380 60748	89p	TBA810 7VAF	99p
LM381	£1.50	TBA820	75p
LM3900 40PA	63p*	ZN414 RX	99p



7400 TTL

7400	11p*	7474	29p*
7401	13p*	7476	29p*
7402	13p*	7490	39p*
7403	13p*	7491	73p*
7404	15p*	7492	43p*
7410	13p*	7493	39p*
7412	29p*	7494	46p*
7420	13p*	7496	74p*
7430	13p*	74100	£1*
7410	13p*	74121	27p*
7411	31p*	74122	65p*
7417	69p*	74141	61p*
7420	69p*	74172	£2*
7422	94p*	74174	£1*
7423	99p*	74175	85p*

TRANSISTORS ALL FULL SPEC

PRICE EACH:-	20p*
AC127 & 128	11p*
AC176	9p*
AC187 & 188	11p*
AD149	45p*
AD161 & 162	33p*
BC107	8p*
BC107B	12p*
BC108	8p*
BC108B	12p*
BC109	9p*
BC109C	12p*
BC117/8/9	2p
BC117/8/9	12p
BC177/8/9	18p
BC182/3/4/44/10p	8p*
BC212/3/4/44/12p	12p*
BCV70/1/2	16p*
BD131 & 132	39p*
BF888 250V	35p
BFY50	14p*
BFY51	14p*
BFY52 & 53	14p*
BS119/20/21	16p*
MJ2955 T03	75p*
MJ12955	99p*
MJE3055	67p*
MPU131 PWT	49p

DIODES

0A81 & 0A91 GERMANIUM	5p.
1N4001 1A50V & 1N4002 5p*	
1N4004 6p*	1N4007 9p*
1N4118 & 1N914 SILICON	4p.
ZENERS RZY88 400mw	9p.
ZENERS 1W 17P Z1J noise	£1*
BRIDGE RECTIFIER 1A50 18p	
1A400V 25p.	4A100V 45p

SCR'S TRIACS

SCR'S TAG1/400 1A400V	50p*
1A50V 38p*	1A 600V 70p*
C106D 1A400V SCR ONLY	17p*
TRIAC SC1460 10A100V	£1*
TRIAC DISCO 16A400V	£1.75*
DIAC	ST2 20p. BR100 25p

VERO

36PINS 28p* FACE CUTTER 49p* COPPERCLAD 0.1 PITCH VERO 23"x5" 32p* 21"x31" 29p* 31"x5" 37p* 31"x31" 32p* 31"x17" £1.70* 31"x17" PLAIN 0.1" £1.00* DIL BREADBOARD 6x4" £2*

DALO pen 69P

DALO ETCH RESIST PEN 69p* FEC ETCH PAK 500gm 89p* 6x4" COPPER BOARD 50p* PCB KIT 3 ITEMS £2* CASSETTE MECHANISM £9 & ASC12 TGS GAS DETECTORS 308retet2*

OIL sockets

TOP QUALITY NYLON SOCKETS SPIN 12p* 14PIN 130P 14PIN 14p* SOLDIERCON PINS: 100 65p* 1000 £3.50*



WW-021 FOR FURTHER DETAILS

Don't miss your copy of

HENRY'S CATALOGUE

only 50p Plus 20p P&P



- ★ OVER 5,000 ITEMS - largest UK range of electronic components for home constructors.
- ★ 200 PAGES - every aspect of electronics and components for amateurs and hobbyists - kits, projects, test gear.
- ★ DOZENS of new lines and new ranges.
- ★ MANY price reductions throughout the new Catalogue.
- ★ A Discount Voucher with every copy, worth 50p.

FREE TO EDUCATIONAL ESTABLISHMENTS when ordered on official notepaper.

Write for your copy, enclosing 70p remittance

ELECTRONIC FOOTBALL & TENNIS WITH THE FABULOUS

VIDEO SPORT ON YOUR OWN TV

Play three exciting electronic ball games FOOTBALL TENNIS HOLE IN THE WALL on your own TV just plug Video Sport into the aerial socket of your TV and away you go. Completely safe for you, your children and your TV. Mains operated.

OUR INCREDIBLE PRICE £29.50 inc. VAT

Post and Packing £2.50 DEMONSTRATIONS NOW IN ALL CENTRES

AM/FM MODULES

LP1179 LP1171

Combined AM/FM tuner modules, together with a small number of R.C.s Ferrite Aerials, make up a sensitive FM/MW/LW tuner. 6 Volt supply, supplied with data and circuit sheets

LP1171 combined IF strip £4.60. LP1179 FM front end and AM gang £4.60. £8.62 the pair. Suitable Ferrite aerial 87p

UHF TV TUNERS

625-line receiver UHF transistorised tuners UK operation. Brand new (Post/packing 25p each). TYPE B 4-button push button (adjustable) £4.60. TYPE C variable tuning £2.90. TYPE D 6 button UHF tuner £5.20

BUILD THE TEXAN + FM TUNER TEXAN 20 + 20W STEREO AMP.

Features glass fibre PC board. Gardners low field transformer. 6 IC's. 10-transistors plus diodes etc. Designed by Texas instruments engineers for Henry's and P.W. 1972. Overall size 15 1/2" x 2 1/4" x 6 1/2" mains operated. Free teak sleeve with every kit.

£35.00 (CARRIAGE 50p) (also built and tested £45.00)

Stereo FM Tuner


Features capacity diode tuning. LED and tuning meter indicators, mains operated. High performance and sensitivity. Overall size in teak sleeve 8" x 2 1/4" x 6 3/4" Complete kit with teak sleeve

£26.25 (CARRIAGE 50p.) (also built and tested £31.20)

JOIN THE LARGE BAND OF CONSTRUCTORS!

AM/FM AND DECODER BOARD

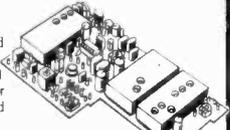Containing Mullard Modules LP1185 LP1186 and LP1181 with MC1310 decoder IC on compact printed circuit board.



Ready aligned, requires only Ferrite Aerial Tuning Gang and AM Oscillator Coil. Tuning Pot and Zener 15V supply, output 300mV. 75 ohms ariel input. Input circuit and instructions supplied

£16.50 inc. VAT & Postage

NEW FROM HENRY'S RADIO - HENELEC RADIO CONTROL SYSTEM - cosmos logic to minimise power consumption and extend battery life. Buy the components you want. Simple transmitter £11.75; PC Board for above 75p; Case for transmitter £1.25; 7-channel add-on kit £9.95; Basic receiver £6.95; Single-ch add-on for receiver £2.95; 7-channel decoder for receiver £4.25; Proportionally Controlled Switch £3.50.

ALL HENRY'S PRICES INCLUSIVE OF VAT

HENRY'S RADIO


LONDON. EDGWARE ROAD LONDON W2. 40-46 Electronics Centre & Supermarket -01 402 8381. 303 Balgoin Centre. 309 Electronics Supermarket. TOTTENHAM COURT ROAD W1. 231 Electronics Centre & Supermarket -01 580 1449

YOUR NEAREST STORE OUT OF TOWN NOTTINGHAM. 94-9 Elm Trees, Castle Nottingham 42668. ALL MAIL ORDERS TO 303 EDGWARE ROAD W2. Prices correct at time of preparation. Subject to change without notice. £ 0 0 P



Barclaycard & Access welcome ALL PRICES INCLUDE VAT

TELETEXT DECODER

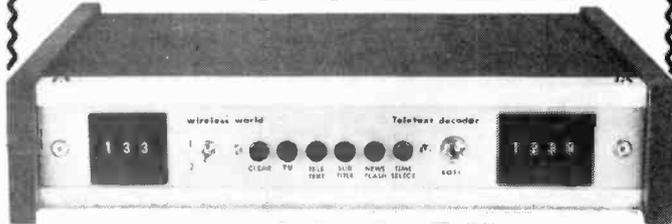

The design of this decoder is being described in a series of articles being published by 'Wireless World' (from November 1975 issue). However, it is available NOW — exclusively from Catronics Ltd.

Our kit contains all the printed circuit boards and components necessary to build the complete decoder. Signal input required is a minimum of 0.5V detected video. The output is approximately 4V of R, G and B drive suitable for driving most types of colour Television sets.

The power supply and video switching circuitry are normally installed within the television cabinet and the main decoding control and memory circuitry in a separate cabinet positioned on top of the television.

PRICES ARE AS FOLLOWS:

For upper case characters (CAPITALS only) version (as published)
 Set of 3 P.C.B.s only: £12.00 + V.A.T. (£3.00)
 Component Kit (inc. P.C.B.s): £87.00 + V.A.T. (£9.25)
 Cabinet and Front Panel: £11.60 + V.A.T. (£2.95)

For upper and lower case characters version

To be announced (Approx. £110.00 incl. V.A.T.)

Post & Packing: P.C.B.s are post free — but add £1 for component kit and/or cabinet




CATRONICS LTD. (Dept. 620)

39 Pound Street
 Carshalton, Surrey
 Tel: 01-669 6700

WW-620 FOR FURTHER DETAILS

Servodata Limited

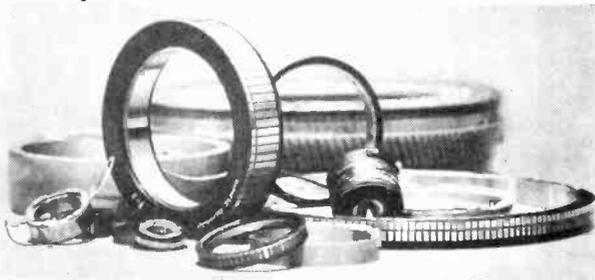Advanced Technology
 in Servo Control Components



DC Torque Motors and Tachometers

- ★ High performance, brush and brushless versions and complementary tachometers.
- ★ 840 Standard Models ranging from 15 oz-in to 120 lb-ft
- ★ Military, Industrial or Space Qualified models are already used by most European Nations.

Servodata

Is able to offer a technical design service utilising these devices in control systems as well as supplying amplifiers, solid state synchro/resolver to digital converters, readouts and other servo control transducers.

Servodata Limited

Highclere, Newbury
 Berkshire RG15 9PU
 Telephone: Highclere (STD 0635) 253579
 Telex: 847054

WW-046 FOR FURTHER DETAILS

TRANSFORMERS

ALL EX-STOCK — SAME DAY DESPATCH

MAINS ISOLATING VAT 8% **12 and/or 24-VOLT**
 PRI 120/240V SEC 120/240V PRIMARY 220-240 VOLTS
 CENTRE TAPPED AND SCREENED

Ref. No.	VA (Watts)	£	P&P	Ref. No.	AMPS 12v 24v	£	P&P
07*	20	3.77	58	111	0.5 0.25	1.54	28
149	60	4.69	72	213	1.0 0.5	1.86	58
150	100	5.33	85	71	2 1	2.41	58
151	200	8.54	112	18	4 2	2.97	72
152	250	10.32	141	70	6 3	4.43	72
153	350	12.47	141	108	8 4	5.09	85
154	500	14.33	161	72	10 5	5.50	85
155	750	21.94	BRS	116	12 6	5.80	97
156	1000	30.51	BRS	17	16 8	7.48	97
157	1500	34.89	BRS	115	20 10	10.91	161
158	2000	38.92	BRS	187	30 15	14.20	141
159	3000	61.48	BRS	226	60 30	17.67	BRS

*115 or 240 sec only

50 VOLT RANGE

SECONDARY TAPS
 01-19-25-33-40-50V

Ref. No.	Amps.	£	P&P
102	0.5	2.71	58
103	1.0	3.55	72
104	2.0	4.95	85
105	3.0	6.10	97
106	4.0	7.98	112
107	6.0	12.71	125
118	8.0	13.63	161
119	10.0	17.75	BRS

30 VOLT RANGE

SECONDARY TAPS
 0-12-15-20-25-30V

Ref. No.	Amps.	£	P&P
112	0.5	1.90	58
79	1.0	2.52	72
3	2.0	3.77	72
20	3.0	4.70	85
21	4.0	5.56	85
51	5.0	6.73	97
117	6.0	7.52	112
88	8.0	10.20	125
89	10.0	10.36	141

60 VOLT RANGE

SECONDARY TAPS
 0-24-30-40-48-60V

Ref. No.	Amps.	£	P&P
124	0.5	2.48	72
126	1.0	3.68	72
127	2.0	5.33	85
125	3.0	7.90	97
123	4.0	9.19	141
40	5.0	10.24	125
120	6.0	12.07	141
121	8.0	15.75	BRS
122	10.0	19.40	BRS
189	12.0	20.25	BRS

AUTO TRANSFORMERS

Ref. No.	VA (Watts)	AUTO TAPS	P&P
113	20	0-115-210-240	1.75 51
64	75	0-115-210-240	3.05 72
4	150	0-115-210-220-240	4.33 72
66	300	...	6.11 85
67	500	...	9.36 125
84	1000	...	14.36 161
93	1500	...	19.02 BRS
95	2000	...	25.41 BRS
73	3000	...	36.84 BRS

SCREENED MINIATURES

Ref.	mA	Volts	£	P&P
238	200	0-0-3	1.62	397
212	1A1A	0-6-0-6	1.93	46
13	100	9-0-9	1.56	25
235	330 330	0-9-0-9	1.64	25
207	500 500	0-8-9-0-8-9	2.02	51
208	1A 1A	0-8-9-0-8-9	3.07	58
236	200 200	0-15-0-15	1.56	25
214	300 300	0-20-0-20	2.03	58
221	700 (DC)	20-12-0-12-20	2.38	58
206	1A 1A	0-15-20-0-15-20	3.63	72
203	500 500	0-15-27-0-15-27	3.15	72
204	1A 1A	0-15-27-0-15-27	4.14	72
5112	500	12-15-20-24-30	1.97	58

HIGH VOLTAGE

MAINS ISOLATING
 PRI 200/220 OR 400/440
 SEC 100/120 OR 200/240

VA	Ref.	£	P&P
60	243	4.37	97
350	247	10.93	141
1000	250	26.31	BRS
2000	252	44.12	BRS

SPECIAL OFFER

Cased Isolator & Transformer
 1KVA, PRI 240v, sec 115V
 Few only £33.50 BRS

PLUS

BRIDGE RECTIFIERS

50v	2A	35p
100v	2A	40p
200v	1A	45p
400v	4A	65p
600v	2A	50p

£2.35
 P&P 15p VAT 25%

METERS

AV08 Mk 5	£55.88
AV072	£21.72
U4313*	£13.85
U4315*	£11.80

(USSR), inc. steel carrying case
 P&P £1.10 VAT 8%

MAGNETIC TO CERAMIC CARTRIDGE CONVERTER
 Operating Voltage 20/45v
 ONLY £2.65 P&P 18p
 VAT 25%

BSR MINI-DECK
 4-speed autochanger £6.00.
 P&P 51p VAT 25%

CASED AUTO. TRANSFORMERS

240v mains lead input and USA 2-pin outlets
 20VA £3.29, P&P 72p Ref. 113W
 150VA £6.37, P&P 85p Ref. 4W
 500VA £10.97, P&P £1.25p Ref. 67W
 100CVA £18.39 BRS Ref. 84W

HIGH QUALITY MODULES

3 watt RMS Amplifier	£2.30
5 watt RMS Amplifier	£2.65
10 watt RMS Amplifier	£2.95
25 watt RMS Amplifier	£3.95
Pre-Amp for 3-5-10w	£4.08
Pre-Amp for 25w	£13.20
Power Supplies for 3-5-10w	88p
Power Supplies for 25w	£3.00
Transformer for 3w	£1.48
Transformer for 5-10w	£2.13
Transformer for 25w	£2.60
P&P Amps/Pre-Amps/Power Supplies	18p
P&P Transformers	37p

VAT 25%

POWER UNITS

CC12-05. Output switched
 3-4-5-6-7 5-9-12v at 500mA
 £4.08. P&P 40p VAT 25%

ANTEX SOLDERING IRONS
 15W £2.68. 13W £2.45. 25W £2.26.
 Soldering iron kit £3.61
 Stand for above £1.13. P&P 25p VAT 8%

PLEASE ADD VAT AFTER P&P
 ELECTRODS. AND SEMICONDUCTOR
 STOCKISTS — CALLERS WELCOME (MON.-FRI.)
 OR SEND STAMP FOR LISTS

Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/8

NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.

WW-042 FOR FURTHER DETAILS

DEMA ELECTRONICS INTERNATIONAL

ELECTRONIC COMPONENTS DISTRIBUTOR FOR INDUSTRY AND HOBBYIST

MONTHLY SPECIALS from DEMA ELECTRONICS

CT 5001 12 Digit 4-Funct	£ 99	558 Timer	£ 0.40
CT5002 Battery Oper. 5001	1.19	556 Dual Timer	0.70
CT5005 12 Digit 4 Funct w/Mem	1.49	1C18038 Funct Gen Volt Contr	
MM6314 24 Pin 6 Digit Mux	2.75	Oscillator Sine Sq	1.95
CT7001 4 or 8 Digit Alarm	1.05	9-Digit LED Display Comm Cath Comp	
1103 256 Bit Ram Mos	1.95	w/8 Digit Clk Chips 12 Char	1.95
1103 1024 Bit Ram Mos	1.95	7446	65
5251 1024 Bit Ram L/Power	1.95	7448	45
1702A 2KE-Prom U/Violet	9.95	7475	27
5203 2048 Bit U/Violet PROMS	9.95	7490	30
2102 1024 Bit Status Ram	2.95	7403	33
		74123	39

TTL 7400 SERIES

7400	£ 0.11	7440	£ 0.11	7485	£ 0.85	74155	£ 0.69
7401	0.11	7441	0.60	7486	0.24	74156	0.69
7402	0.11	7442	0.55	7488	2.50	74157	0.69
7403	0.11	7443	0.55	7489	1.50	74158	0.89
7404	0.13	7444	0.60	7490	0.40	74160	0.89
7405	0.13	7445	0.75	7491	0.55	74162	0.89
7406	0.22	7446	0.85	7492	0.43	74163	0.89
7407	0.22	7447	0.75	7493	0.43	74164	1.05
7408	0.14	7448	0.65	7494	0.49	74165	1.05
7409	0.14	7450	0.12	7495	0.45	74166	1.05
7410	0.11	7451	0.13	7496	0.55	74170	1.05
7411	0.16	7453	0.13	74100	0.89	74175	0.90
7413	0.26	7454	0.14	74107	0.27	74180	0.80
7416	0.22	7460	0.11	74121	0.27	74181	2.50
7417	0.22	7470	0.24	74122	0.37	74182	0.80
7420	0.11	7472	0.21	74123	0.49	74192	0.30
7426	0.23	7473	0.25	74145	0.57	74193	0.85
7430	0.12	7474	0.25	74150	0.59	74194	0.85
7432	0.22	7475	0.37	74151	0.59	74195	0.80
7437	0.25	7476	0.26	74153	0.89	74198	1.70
7438	0.25	7483	0.69	74154	1.05	74199	1.70

HIGH SPEED 74H00

74H00	£ 0.16	74H20	£ 0.16	74H52	£ 0.16	74H71	£ 0.21
74H01	0.16	74H21	0.16	74H53	0.16	74H72	0.26
74H04	0.16	74H22	0.16	74H54	0.21	74H74	0.28
74H05	0.21	74H30	0.16	74H55	0.16	74H76	0.28
74H08	0.16	74H40	0.16	74H60	0.16		
74H10	0.16	74H50	0.16	74H61	0.16		
74H11	0.16	74H51	0.21	74H62	0.16		

CMOS 4000 SERIES

4000A	£ 0.19	4014	£ 1.10	4028	£ 0.95	4071	£ 0.23
4001	0.19	4015	1.10	4030	0.50	4072	0.25
4002	0.19	4016	0.55	4032	0.95	4073	0.25
4006	0.90	4019	0.67	4043	1.20	4075	0.25
4007	0.19	4020	1.10	4044	1.20	4078	0.25
4008	1.30	4021	1.10	4049	0.48	4081	0.25
4009	0.49	4023	0.19	4050	0.48	4082	0.29
4010	0.49	4024	0.85	4066	0.75	4528	0.85
4011	0.19	4025	0.19	4068	0.23	4585	1.25
4013	0.39	4027	0.75	4069	0.23		

DTL

930	£ 0.10	936	£ 0.10	944	£ 0.10	962	£ 0.10
932	0.10	937	0.10	946	0.10	963	0.10

LINEARS

LM300	T099	£ 0.45	340U	T092	£ 1.25	739	A DIP	£ 0.65
301	V DIP	0.29	380	A DIP	80	741	V DIP	0.22
302	T099	0.45	381	A DIP	1.05	747	A DIP	0.44
304	TO100	0.50	546	V DIP	0.51	748	V DIP	0.27
305	T099	0.60	550	A DIP	0.55	5556 (1456)	V DIP	0.65
307	V DIP	0.38	555	V DIP	0.45	5558 (1458)	V DIP	0.65
	T099	0.45	560	B DIP	2.55	ULN 2111	A DIP	0.95
308	A DIP	0.59	561	B DIP	2.55	LM3900	A DIP	0.35
	T099	0.79	561	B DIP	2.55	75450	V DIP	0.45
309K	TO3	1.45	562	B DIP	2.55	75451	V DIP	0.45
310	T pkg	0.55	565	A DIP	1.25	75452	V DIP	0.45
311	V OIP	0.90	566	V DIP	1.20	75453	V DIP	0.45
320K	TO3 NEG	5.2, 12, 15	709	A DIP	0.22	75454	V DIP	0.45
		1.25	709	A DIP	0.25	75491	A pkg	0.65
324	A DIP	1.07	710	A DIP	0.25	75492	A pkg	0.75
339	A DIP	1.49	711	A DIP	0.30	8038	B pkg	1.95
340K	TO3	2.10	723	A DIP	0.38	8864	22 Pin pkg	1.45

V = Mini Dip A = 14L Oip B = 16L DIP T099 = 8-Pin Header TO100 10-Pin Header
Data sheets supplied on request. Add 20 ea. excepted as noted.

CALCULATORS & CLOCKS w/DATA

MEMORIES w/DATA							
1101 256 Bit Ram Mos	£ 1.79	5001	Cal Chip	£ 0.99			
1103 1024 Bit Ram Mos	2.25	5002	Cal Chip	1.19			
7489 (8225) 64 Bit Ram TTL	1.50	5005	Cal Chip	1.49			
8223 Programmable ROM	2.50	5311	Clock Chip	2.95			
5260 1024 Bit Ram Low Power	1.95	5312	Clock Chip	2.95			
		5313	Clock Chip	2.95			
		5314	Clock Chip	3.45			
		5316	Clock Chip	3.95			
				0.50			

TRANSISTORS

2N 2219A	TO5	£ 0.37	2N 4124	TO92	0.10
2N 2222	TO18	0.15	2N 4126	TO92	0.10
2N 2369	TO18	0.10	2N 4401	TO92	0.10
2N 2905A	TO5	0.38	2N 5225	TO92	0.10
2N 3227	TO18	0.32	2N 5226	TO92	0.10

DISCOUNTS:	MIN ORDER	All Items New Branded
10% on orders over £ 10	£ 2.5	Guaranteed By DEMA ELECTRONICS
15% on orders over £ 25		

TERMS: PRICES LISTED ARE BRITISH POUNDS & PENCE. SEND CHEQUE WITH ORDER. MASTERCHARGE, BANKAMERICARD, BARCLAY CARD ACCEPTED. TERMS OFFERED TO SCHOOLS & INSTITUTIONS.

POSTAL AND HANDLING CHARGES SHIPMENT VIA AIR MAIL under 4.99 add 0.35 £ 10 and over 5.00-9.99 add 0.25 No Charge


DEMA ELECTRONICS INTERNATIONAL
P.O. Box 407 San Ramon, Ca. 94583 USA
Cable DEMAELINTL

CONTIL SAMOS miniature cases

In easy-to-work blue and white PVC/steel. Assemble in the lower half complete before springing cover into place—four Pordrivels, two to hinge lid, two to fasten it. Carries four P.C. boards horizontally, or two vertically; four required for each case (for one vertical board, two each case) Prices correct Dec. 1975

S1	100 x 50 x 50mm	£ 1.11
S2	100 x 100 x 50mm	£ 1.28
S3	100 x 150 x 50mm	£ 1.41
S4	125 x 80 x 75mm	£ 1.88
S5	125 x 100 x 75mm	£ 1.81
S6	125 x 150 x 75mm	£ 2.12
S7	125 x 200 x 75mm	£ 2.36

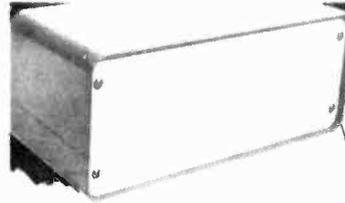much less for quantity. Prices include P & P, 8% VAT, four feet and four plated screws. Special feet to carry Printed Circuit Boards sold separately. Price incl. 8% VAT, 25p for four PC feet.




CONTIL MOD-3

Mod 301	£ 5.13	Width	7"	Height	3"	Depth	5 1/4"
Mod 302	£ 5.50		7"		4 1/2"		5 1/4"
Mod 303	£ 7.02		7"		6"		5 1/4"
Mod 304	£ 8.32		11"		3"		5 1/4"
Mod 305	£ 7.46		11"		4 1/2"		5 1/4"
Mod 306	£ 8.91		11"		6"		5 1/4"

Contil Mod-3 cases are in six sizes and offer the manufacturer of small instruments an attractive low cost case available ex-stock. Made in blue PVC-coated steel and complete with front and rear panels and chassis, they are light, strong and rigid. PCB and PSU mounting systems available.

Less for quantities Prices correct Dec. 1975.

BOPAL Die-cast aluminium enclosures

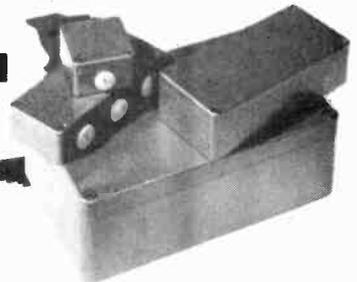


Made to standard IP65, these grey hammer die-cast aluminium boxes in 14 sizes are used widely for housing instruments and control gear. Standard tappings available on 4 sizes. Easy to machine, stable mechanically, excellent H.F. screening. S.s. screws are retained in the lid.

Prices, e.g.	Size	1 off
	A101	£ 2.38
	A110	£ 4.54
	A140	£ 22.14

Prices include VAT and P&P Less for quantities

Pads provided internally for mounting terminal strips. Lid seal recessed to protect them against mechanical damage. Mounting screws outside gasket area.

SWIFT Instrument cases

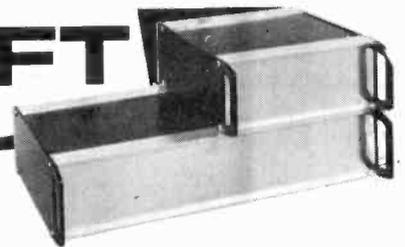

Heat Sink and Case in One

The front and back heavy extrusions contain slots for mounting power transistors or transformers. Access is by means of the removable side plates which allow the black PVC top and bottom panels to be slid out so providing good access to the interior. With 3/16" thick side removed, the case is still mechanically stiff.

Full width rack 3 1/2" high	1 off incl. P&P and VAT	£ 14.69	Size 17" x 10 1/2"
Half width rack 3 1/2" high		£ 11.99	8 1/2" x 10 1/2"

The good-looking Swift case is made of aluminium side plates black anodised, the front and rear extrusions satin anodised. Only B parts and B screws. The feet lock into the case below for stacking.

SWIFT Rack Brackets 86p per pair incl. VAT No extra charge for Lockures — Add L to order. Prices correct Dec. 1975. WEST HYDE NOW HAVE OVER 250 SIZES AND TYPES OF CASES, PLASTIC AND METAL.

WH-MK spacemiser storage system

Cabinets have stove enamelled steel frames in three heights all of equal width and depth. The frames are strong and rigid, fitted with top and bottom locating pegs and rear slots making stacking, wall or frame mounting positive and simple.

121	122	123	1 off	4 off
251	252	253	£ 6.49	£ 4.89
501	502	503	£ 8.95	£ 7.16
254	257	258	£ 14.35	£ 12.29
504			£ 8.65	£ 6.89
			£ 13.75	£ 11.97

Less for quantities. All prices include P & P, and 8% VAT.

Prices correct September 1974

WEST HYDE

Open Mon to Fri, 9 a.m. to 5.30 p.m. Cases less 10% collected, unpacked

WEST HYDE DEVELOPMENTS Ltd, Ryefield Cres., Northwood Hills, Northwood, Middx HA6 1NN. Tel: Northwood 24941/26732

Write or phone for new free catalogue

WW-065 FOR FURTHER DETAILS

Introducing the small speaker with 'big' ideas Celestion UL6

Compact Shape

How small? 11½ x 16 x 8¾ in. to be precise; these measurements are the only 'small' thing about UL6.

Expansive Sound

UL gives expansive, open, natural sound; only Celestion have truly conquered the technical problems which have previously been held to be insurmountable.

An intensive three year development programme has crystallized a life times know-how of speaker design and given birth to UL.

Superior Performance

Inside the beautiful exterior are the new 'acoustic motor units' which make these designs possible. New soft dome 'tweeters' of impeccable design to give smooth sweet treble sounds; bass units built on to diecast chassis, with small ultra-low distortion bextrene diaphragm, extra large voice coil (1½ in.) and magnet for high accuracy and ability to handle wide dynamic range and high peak music levels when required.


The third diaphragm is Celestions auxiliary bass radiator 'ABR' which comes into its own on the extreme low notes of instruments

such as organ and double bass.

UL means ultra linear. UL also represents unlimited quality of sound; Celestion experience makes possible a prestige product at an ordinary cost.

The UL6 speaker has precise and beautiful balance both aurally and visually.

Celestion

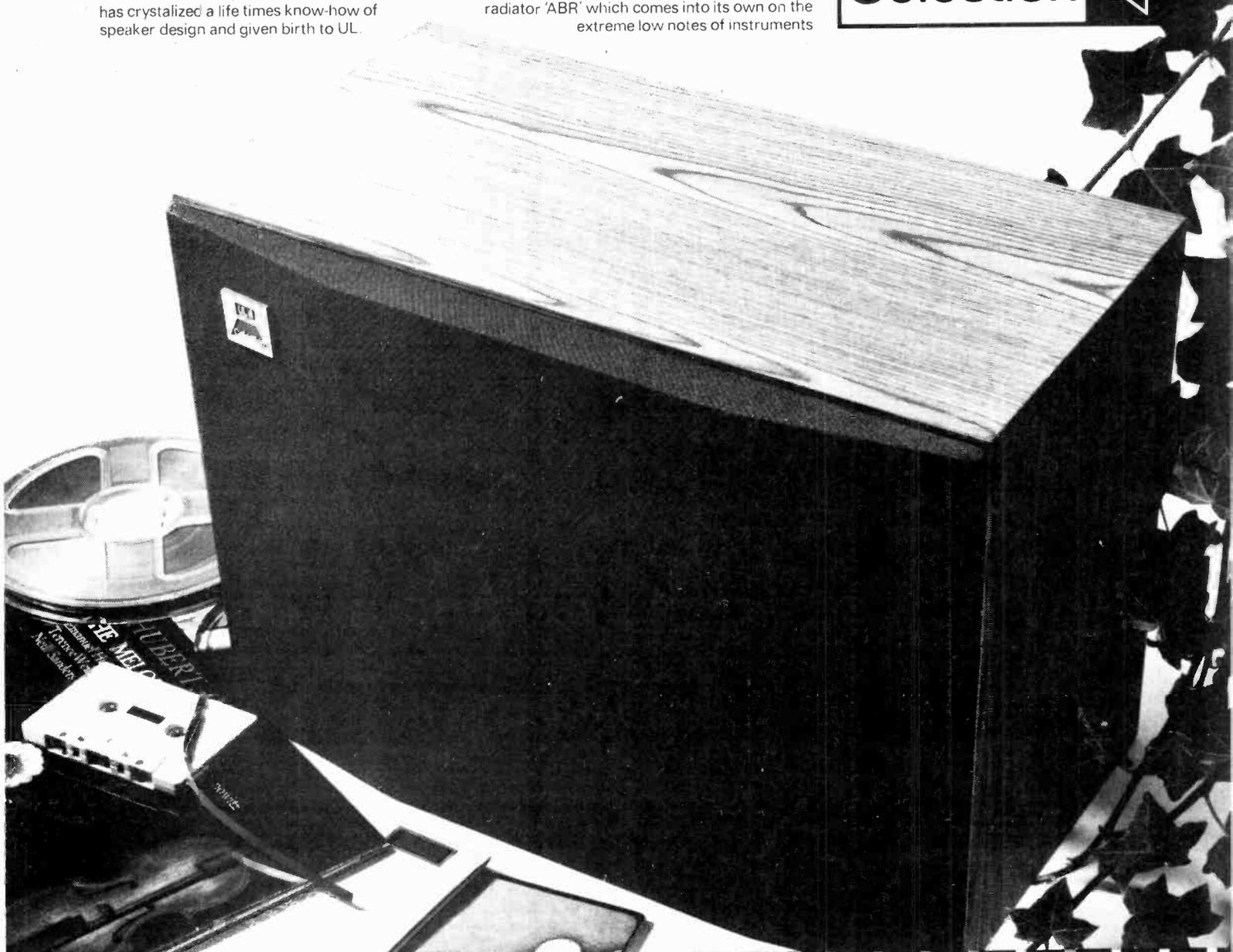


Hear the full range speak for itself:

Please send me full details of
UL6 UL8 UL10 and inform me of my
nearest franchised demonstration centre.

Name _____

Address _____

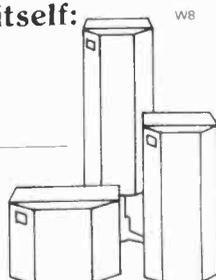

Rota Celestion Limited, Ditton Works, Foxhall Road, Ipswich, Suffolk IP3 8JP
Telephone Ipswich (0473) 73131 Cables: Voicecoil Ipswich Telex 98365

More than just a catalogue!


PROJECTS FOR YOU TO BUILD

4-digit clock, 6-digit clock, 10W high quality power amp., High quality stereo pre-amp., Stereo Tuner, F.M. Stereo decoder, etc., etc.

CIRCUITS . . . Frequency Doublers, Oscillators, Timers, Voltmeters, Power Supplies, Amplifiers, Capacitance Multiplier, etc., etc. . . .

Full details and pictures of our wide range of components, e.g. capacitors, cases, knobs, veroboards, edge connectors, plugs and sockets, lamps and lampholders, audio leads, adaptor plugs, rotary and slide potentiometers, presets, relays, resistors (even 1% types!), switches, interlocking pushbutton switches, pot cores, transformers, cable and wire, panel meters, nuts and bolts, tools, organ components, keyboards, L.E.D.'s, 7-segment displays, heatsinks, transistors, diodes, integrated circuits, etc., etc., etc. . . .


Really good value for money at just 40p.

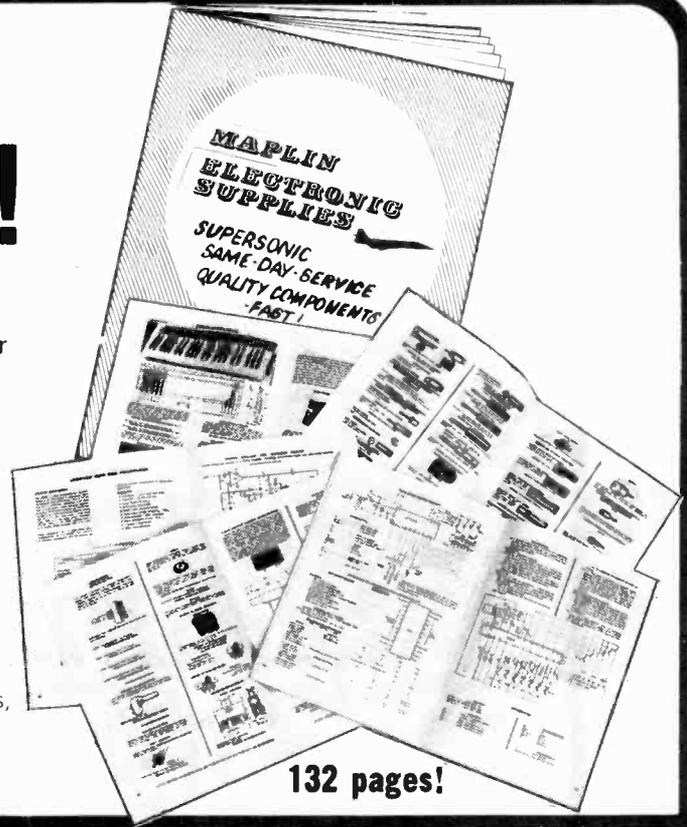

132 pages!

The 3600 SYNTHESISER

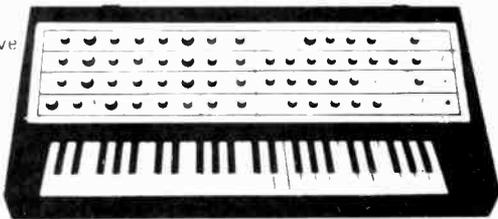
The 3600 synthesiser includes the most popular features of the 4600 model, but is simpler. Faster to operate, it has a switch patching system rather than the matrix patchboard of the larger unit and is particularly suitable for live performance and portable use.



S.A.E. please for price list


The 4600 SYNTHESISER

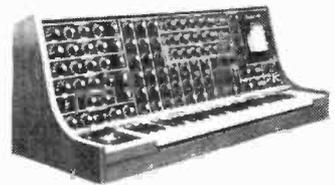We stock all the parts for this brilliantly designed synthesiser, including all the PCBs, metalwork and a drilled and printed front panel, giving a superb professional finish.



Opinions of authority agree the ETI International Synthesiser is technically superior to most of today's models. Complete construction details available now in our booklet price £1.50, or S.A.E. please for specification

GRAPHIC EQUALIZER

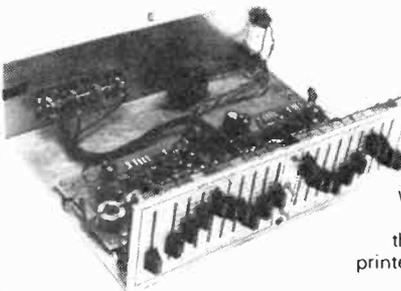

A really superior high quality stereo graphic equaliser as described in Jan. 1975 issue of ETI. We stock all parts (except woodwork) including all the metal work drilled and printed as required to suit our components and PCBs. Complete reprint of article — price 15p.

ELECTRONIC ORGAN

Build yourself an exciting Electronic Organ. Our leaflet MES51, price 15p, deals with the basic theory of electronic organs and describes the construction of a simple 49-note instrument with a single keyboard and a limited number of stops. Leaflet MES52, price 15p, describes the extension of the organ to two keyboards each with five voices and the extension by an octave of the organ's range.



Solid-state switching and new footages along with a pedal board and a further extension of the organ's range are shown in leaflet MES53, price 35p. (Pre-publication price 15p).

NO MORE DOUBTS ABOUT PRICES

Now our prices are GUARANTEED (changes in VAT excluded) for two month periods. We'll tell you about price changes in advance for just 30p a year (refunded on purchases). If you already have our catalogue send us an s.a.e. and we'll send you our latest list of GUARANTEED prices. Send us 30p and we'll put you on our mailing list — you'll receive immediately our latest price list then every two months from the starting date shown on that list you'll receive details of our prices for the next GUARANTEED period before the prices are implemented! — plus details of any new lines, special offers, interesting projects — and coupons to spend on components to repay your 30p

NOTE: The price list is based on the Order Codes shown in our catalogue so an investment in our super catalogue is an essential first step

Call in at our shop, 284 London Road, Westcliff on Sea, Essex. Please address all mail to

MAPLIN ELECTRONIC SUPPLIES
P.O. Box 3 Rayleigh Essex SS6 8LR

I enclose Cheque/P.O. value _____ ww
 For _____ copy/copies of your Catalogue
 Name _____
 Address _____

MAPLIN ELECTRONIC SUPPLIES P.O. Box 3 Rayleigh Essex SS6 8LR

TRANSFORMERS

CASED TRANSFORMERS

Housed in smart resin coated steel cases with 3 core power cable and outlet socket. Used primary winding. Isolation types are fitted with 3-pin outlet sockets and are available with 110 volt or 240 volt output (Please state). Auto types are fitted with 2-pin flat style sockets up to 500 VA. 3-pin sockets from 750 to 3000 VA. See Auto and Isolation sections for prices. Plugs extra.



SAFETY ISOLATING

Prim. 120/240V Sec. 120/240V Centre Tap with screen

VA (WATTS)	REF No.	PRICE Cased	Plugs 2 Pin + 1 Earth	PRICE Open	Post
20	148	5.25	0.98	3.75	0.72
60	149	9.03	0.98	4.70	0.72
100	150	9.87	0.98	5.35	0.85
200	151	12.29	0.98	8.61	0.97
250	152	13.81	0.98	10.31	1.18
350	153	16.54	0.98	12.50	1.29
500	154	18.38	0.98	14.31	1.44
750	155	28.72	1.25	22.12	0.85
1000	156	37.44	1.25	30.57	0.85
1500	157	44.37	1.25	34.98	0.85
2000	158	52.45	2.95	38.91	0.85
3000	159	77.18	2.95	61.51	0.85

MINIATURE & EQUIPMENT

PRIMARY 240V WITH SCREEN VOLTS		MILLIAMPS		REF No.	PRICE	Post
Sec. 1	Sec. 2	Sec. 1	Sec. 2			
3.0-3	0.6	500	500	228	1.95	0.34
0.6	0.6	1000	1000	224	1.56	0.34
0.6	0.6	1000	1000	212	2.12	0.46
9.0-9	0.9	100	—	13	1.60	0.34
0.9	0.9	330	330	235	1.62	0.34
0.8-9	0.8-9	500	500	207	1.69	0.46
0.8-9	0.8-9	1000	1000	208	2.79	0.46
15.0-15	1.5	40	—	240	1.55	0.34
0.15	0.15	200	200	236	1.56	0.34
0.20-20	0.2	30	—	241	1.55	0.34
0.20	0.20	150	150	237	1.56	0.34
0.15-20	0.15-20	500	500	205	2.88	0.58
0.20	0.20	300	300	214	2.03	0.61
0.20	0.20	3500	No Screen	211	11.16	0.97
20-120	—	700	—	221	2.50	0.61
12-20	—	(0.C.)	—	—	—	—
0.15-20	0.15-20	1000	1000	206	2.85	0.72
0.15-27	0.15-27	500	500	203	3.16	0.58
0.15-27	0.15-27	1000	1000	204	4.55	0.72

12 and 24 VOLTS PRIMARY 200-240 Volts

AMPS	VA (Watts)	REF No.	PRICE Cased	Plugs 2 & 3 Pin	PRICE Open	Post
12V	24V					
0.3	0.15	242	1.66	0.34		
0.5	0.25	111	1.60	0.46		
1	0.5	213	1.90	0.61		
2	1	71	2.47	0.61		
4	2	18	3.07	0.62		
6	3	70	4.50	0.72		
10	5	108	5.11	0.85		
12	6	72	5.63	0.85		
16	8	116	5.80	0.85		
20	10	17	7.26	0.97		
20	10	115	10.96	1.18		
30	15	187	14.06	1.36		
40	20	232	15.63	0.85		
60	30	226	17.70	0.85		

30 VOLTS

AMPS	Ref. No.	PRICE	Post
0.5	112	2.04	0.61
1	79	2.57	0.66
2	3	3.91	0.72
3	20	4.80	0.85
4	21	5.58	0.85
5	51	6.75	0.95
6	117	7.52	0.97
8	88	8.83	1.18
10	89	10.27	1.18

50 VOLTS

AMPS	Ref. No.	PRICE	Post
0.5	102	2.71	0.61
1	103	3.58	0.76
2	104	5.30	0.85
3	105	6.10	0.85
4	106	7.97	1.08
6	107	12.93	1.18
8	118	13.75	1.44
10	119	17.79	1.86

AMPS	Ref. No.	PRICE	Post
0.5	124	2.51	0.72
1	126	3.75	0.72
2	127	5.36	0.85
3	125	7.91	0.97
4	123	9.20	1.18
5	40	10.22	1.18
6	120	12.10	1.36
8	121	15.74	0.85
10	122	20.10	0.85
12	189	18.87	0.85

AUTO TRANSFORMERS

VA (Watts)	Ref. No.	PRICE Cased	Plugs 2 & 3 Pin	PRICE Open	Post
Tapped at 115, 220, 240 Volts					
20	113	4.31	0.25	1.88	0.61
Tapped at 115, 200, 220, 240 Volts					
150	4	6.99	0.25	4.28	0.72
200	65	7.67	0.25	5.21	0.78
300	66	8.67	0.25	6.11	0.85
500	67	11.82	0.25	9.48	1.18
750	83	14.81	0.95	11.30	1.28
1000	84	18.38	0.95	14.35	1.44
1500	93	23.26	0.95	19.22	0.85
2000	95	35.07	1.80	25.49	0.85
3000	73	50.61	2.35	34.87	0.85

BRIDGE RECTIFIERS

ONE AMP	Price	FOUR AMP	Price
50 P.I.V.	0.25	100 P.I.V.	0.55
100 P.I.V.	0.25	200 P.I.V.	0.59
200 P.I.V.	0.28	400 P.I.V.	0.85
600 P.I.V.	0.30	800 P.I.V.	0.75

SPECIAL OFFER!

2 KVA ISOLATORS
Fully impregnated & screened
2 primary windings 110V each
2 secondary windings 115V each
(2 matching transformers)
£29.50 plus carr. & VAT.

TWO AMP	Price	SIX AMP	Price
50 P.I.V.	0.35	50 P.I.V.	0.65
100 P.I.V.	0.40	100 P.I.V.	0.70
200 P.I.V.	0.45	200 P.I.V.	0.80
400 P.I.V.	0.50	400 P.I.V.	0.90

POWER UNIT TYPE CR12-05 British Made



SAVES BATTERIES SAVES MONEY
Housed in smart steel case, finished in hard epoxy coating. Screened for safety.

Output switched 3, 4.5, 6, 7.5, 9 and 12 Volts at 500 mA D.C. Operates from 240 V mains, suitable for Radios, Tape Recorders, Record Players, etc. Size 7.5 x 5.0 x 14.0 cm. Price £4.15. Post 3p. Plus 8% VAT.

NEW! 2" AND 4" PANEL METERS

2"		4"	
SIZE: 60mm Wide x 45mm High x 40mm Deep.	Movement	SIZE: 110mm Wide x 82mm High x 43mm Deep.	Movement
0.50 micro A	1550	0.50 micro A	1480
0.100 micro A	980	0.100 micro A	730
0.500 micro A	170	0.500 micro A	200
0.1 mA	170	0.1 mA	200
0.5 mA	170	0.5 mA	200
0.10 mA	6	0.10 mA	6
0.500 mA	6	0.500 mA	6
0.100 mA	0.5	0.100 mA	0.5
0.500 mA	0.5	0.500 mA	0.5
0.1 AMP	0.5	0.1 AMP	0.5
0.2 AMP	0.5	0.2 AMP	0.5
0.25 Volt	15K	0.25 Volt	15K
0.50 Volt	10K	0.50 Volt	30K
0.300 Volt	300K	0.300 Volt	300K
VU Meter	170	VU Meter	200
VU Meter	9250	VU Meter	5250

VU Meters are complete with detectors. Modern wide view. Price 2" £3.20 Post 10p. Price 4" £4.00 Post 10. Lamps 60p per set. Plus 8% VAT

C1000 MULTI-METER

Compact General Purpose Mini Multimeter
Input Resistance 1000 ohms per volt
Ranges: AC Volts 0-15 50 250 1000 Volts
DC Volts 0-10 50 250 1000 Volts
DC Current 0.1 mA 0.100 mA
Resistance 0.150K ohms
Size 60 x 24 x 90 mm
Complete with Batteries. Test Prods. Instructions



Special price **£3.35** Post 30p Plus 8% VAT

1/4-WATT CARBON FILM RESISTORS

also available 1/4 watt at 70 CE 12 range 100-1MΩ 5% tol. above 470KΩ 10% tol. at 95p per 100. Plus 25% VAT

MINIATURE NEONS

6mm dia. 12mm length leads length approx 20mm Recommended ballast resistor 150K ohms for 240 Volt operation Price Packet of 10 for 60p. Postage 15p Plus 8% VAT

PLEASE ADD 8% VAT ON ALL TRANSFORMERS


Send 25p for Catalogue

A.S.P. LTD.

DEPT. WW1, SIMMONS ROAD, WINCHEAP, CANTERBURY, KENT. Tel: (0227) 52436

FREQUENCY COUNTERS

HIGH PERFORMANCE REASONABLY PRICED ELECTRONIC INSTRUMENTS

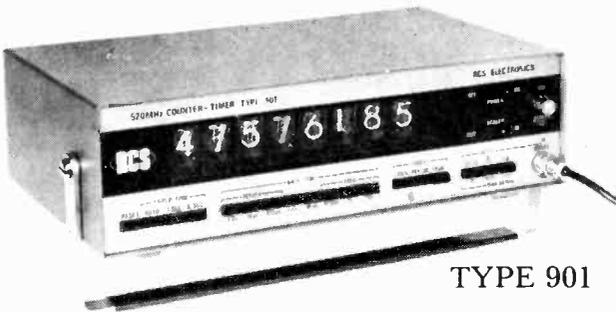

TYPE 901

CRYSTAL OVEN

TWO TONE BLUE CASE

£375 **520 MHz**

Sensitivity 10mV. Stability 5 parts 10¹⁰

301M	32MHz 5 Digit	£78	401	32MHz 6 Digit	£121
501	32MHz 8 Digit	£178	701A	80MHz 8 Digit	£195
801A/M	300MHz 8 Digit	£305	901M	520MHz 8 Digit	£375
801B/M	250MHz 8 Digit	£262	Memory versions available if not suffixed M £25 extra		

Start/Stop versions plus £12

Type 101 1MHz 100KHz 10KHz Crystal Standard £85

Type 103 Off/Air Standard £85

SUPPLIERS TO: Ministry of Defence, G.P.O., B.B.C., Government Depts., Crystal Manufacturers and Electronic Laboratories world-wide



R. C. S. ELECTRONICS

NATIONAL WORKS, BATH ROAD
HOUNSLOW, MIDDX. TW4 7EE
Telephone: 01-572 0933/4

WW-091 FOR FURTHER DETAILS

THE RADIO SHOP

16 CHERRY LANE
BRISTOL BS1 3NG

TELEPHONE
0272-421196



TRIACS

1.6AMP PLASTIC	6AMP ISOLATED TAB	10AMP ISOLATED TAB
NAS061W 100V .28	NAS061W 100V .65	NAS1001W 100V .72
NAS061X 100V .28	NAS0651W 100V .61	NAS1001X 100V .72
NAS0162W 200V .30	NAS0652W 200V .61	NAS1002W 200V .78
NAS0162X 200V .29	NAS0652X 200V .61	NAS1002X 200V .76
NAS0164W 400V .40	NAS0654W 400V .72	NAS1004W 400V 1.09
NAS0164X 400V .38	NAS0654X 400V .70	NAS1004X 400V 1.04
NAS0166W 600V .50	NAS0656W 600V .88	NAS1006W 600V 1.36
NAS0166X 600V .48	NAS0656X 600V .76	NAS1006X 600V 1.36
3.5AMP CLIPPED TAB	8.5AMP ISOLATED TAB	15 AMP ISOLATED TAB
NAS0351W 100V .52	NAS0851W 100V .38	NAS1501W 100V 1.05
NAS0351X 100V .52	NAS0851X 100V .38	NAS1501X 100V .95
NAS0352W 200V .56	NAS0852W 200V .76	NAS1502W 200V 1.02
NAS0352X 200V .56	NAS0852X 200V .76	NAS1502X 200V 1.02
NAS0354W 400V .68	NAS0854W 400V .38	NAS1504W 400V 1.51
NAS0354X 400V .67	NAS0854X 400V .35	NAS1504X 400V 1.48
NAS0356W 600V .85	NAS0856W 600V 1.10	NAS1506W 600V 1.89
NAS0356X 600V .84	NAS0856X 600V 1.06	NAS1506X 600V 1.84

Devices with Internal Trigger have "W" suffix. "X" denotes Standard Triac.

THYRISTORS

1.6AMP TOS	4AMP ISOLATED TAB	6AMP ISOLATED TAB
NAS006P 50P.V. .25	NAS106P 50P.V. .26	NAS206P 50P.V. .37
NAS006Q 100P.V. .28	NAS106Q 100P.V. .30	NAS206Q 100P.V. .42
NAS006R 200P.V. .31	NAS106R 200P.V. .37	NAS206R 200P.V. .50
NAS006S 400P.V. .40	NAS106S 400P.V. .56	NAS206S 400P.V. .77
NAS006T 600P.V. .52	NAS106T 600P.V. .90	
8AMP ISOLATED TAB	16AMP ISOLATED TAB	
NAS306P 50P.V. .41	NAS806P .50	
NAS306Q 100P.V. .47	NAS806Q .58	
NAS306R 200P.V. .59	NAS306R .73	
NAS306S 400P.V. .85	NAS806S 1.15	

Quantity Prices on Application. SAE
THYRISTORS C106 SERIES 4AMP
50V .32; 100V .37; 200V .46; 400V .56; 600V .70

INTEGRATED CIRCUITS

TAA550	TO18	54	78A600	.78	709	14 Pin	.27
TAA263	TO18	62	78A10A5	1.08	741	8 Pin	.35
555	8-pin	.40	78A14TO18	.75	748	14 Pin	.50

BI-PRE-PAK

Bargains in Semi-Conductors, components, modules & equipment.

B-P-P Packs

Originated in 1959 by the Company's managing director, his were the first semi-conductor and component packs to be marketed in this country, and indeed, the company's name grew out of "British Industrial Pre-Pack Components". Today, Bi-Pre-Pak continues to occupy a position of pre-eminence in the supply of packs as well as a vastly extended range of products detailed in our latest 24-page A.4 size free catalogue. Send 10p stamped large addressed envelope for your copy by return.

IT'S ALL IN OUR FREE CATALOGUE

Component Packs

- CP1 150 Capacitors, mixed bag of paper, silver mica, electrolytics, etc. Approx. quantity, counted by weight (post and packing) **60p**
- CP2 200 Resistors, mixed bag of different types, values, wattages, etc. Approx. quantity, counted by weight **60p**
- CP3 40 Wirewound resistors, mixed types, values and wattages **60p**
- CP4 12 Potentiometers, pre-sets, w/wound, carbon, etc. Mixed types and values **60p**
- CP5 5 Earphones, single low impedance for transistor radios, cassettes, etc. Less plugs for suitable plugs see PAKs CP9 and CP10 **60p**
- CP6 50 TO-5 mounting pads, fits between transistor and board, for that pro finish **60p**
- CP8 500 Cable clips for G.P.O. 1/4" dia. cable, Nylon with hardened steel pin (probably tungsten) per sealed box of 500 **60p**
- CP9 5 3.5mm plugs, miniature jack, to fit earphones in PAK CP5 **60p**
- CP10 5 2.5mm sub miniature jack plugs, to fit earphones in PAK CP5 **60p**
- CP11 6 Screwdrivers, 1 x mains neon tester, 5 x grub screwdrivers **60p**
- CP12 10 Reed relay inserts, 1" long 1/4" dia. These will operate from an external magnet or coil. For magnets see PAK CP13 **60p**
- CP13 10 Magnets of various sizes for operating reed switches on PAK CP12, ideal for burglar alarms on doors and windows, etc. **60p**
- CP14 40 Potentiometers, presets, wirewounds, carbons, dual gangs, with and without switches etc. Mixed values and wattages **£1.20**
- CP15 12 Standard crocodile clips, screw fixing, good quality **60p**
- CP16 5 P.C. boards each containing a BF150 UHF amplifier transistor. A good basis for building a T.V. aerial pre-amp as various parts etc. **60p**
- CP17 25 Electrolytic Capacitors, various values and voltages, many useful types, from T.V. to transistor radio and Hi-Fi (post and packing 23p) **60p**
- CP18 1 Light activated SCR 50 volts 1.6 amps type L9F Ready mounted on P.C. board with gate resistor and leads fitted. Full data and circuit diagrams for 14 projects, includes slave photo flash unit, burglar alarm, etc. **60p**
- CP19 3 Micro switches 1 pole change over standard model 1 1/2" x 1/2" **60p**
- CP20 10 Relays assorted types, Ex-G.P.O. and others, mixed voltages **£1.20**
- CP21 200 Square inches of copper laminate P.C. board, in approx. 8 pieces **60p**
- CP22 3 Fibreglass plain printed circuit boards, approx. 2 1/2" x 14" **60p**
- CP23 4 Switches, miniature push to make, single pole **60p**

YOUR SUPPLIERS FOR:

Semi-conductors — all popular types. Opto-electronic devices inc. Nixie Tubes, Solder Tools, Terminals, Switches, Knobs, Ex-G.P.O. items, Aluminium Boxes, Triacs, Thyristors, Zener Diodes and much more in our catalogue and shop.



Semi-Conductors

TESTED AND GUARANTEED PACKS

TP4 3 SN7490 integrated circuits, 14 pin dual in line TTL type. Decade counter. Get one FREE, these are 60p each in singles **£1.20p**

ALL THE FOLLOWING ARE AT 60p EACH PACK

- TP9 5 SN7400 integrated circuits, 14 pin dual in line TTL type. Quad 2-input NAND gate. Get one FREE, these are 15p each
- TP10 2 Light dependant resistors, 400 ohms light, 1 megohm dark, 1/4" dia
- TP11 10 Transistors XB102 and XB112 equivalent to AC126, AC156, OC81/2, OC72 etc
- TP12 4 BY127 Silicon rectifiers 1000 piv 1 amp. Plastic T.V. rectifier
- TP13 5 OCP71 Light sensitive transistors
- TP14 20 OC71 germanium PNP audio pre amp transistor, black glass type
- TP15 20 OC81 Germanium PNP audio output transistor, white glass type
- TP16 20 OC200/1/2/3 transistors, PNP silicon TO-5 unmarked
- TP17 20 1 watt zener diodes, mixed voltages 6.8 to 43 volts
- TP18 20 2N3707/B/8/9/10 transistors NPN silicon plastic, unmarked
- TP19 100 Diodes, mixture of germanium, gold bonded, silicon, etc., a useful selection of many types, marked and unmarked
- TP20 10 Mullard OC45 transistors, J.F. amp PNP germanium
- TP23 20 BFY50/1/2 2N696/7, 2N1613, etc. NPN silicon TO-5 unmarked. COMPLEMENTARY TO PAK TP24
- TP24 20 BFY64, 2N2904/5, etc. PNP silicon TO-5 unmarked. COMPLEMENTARY TO PAK TP23
- TP30 20 NPN silicon planar transistors, TO-18 similar to BC108, etc. unmarked
- TP31 20 PNP silicon planar transistors, TO-18 similar to BC178, etc. unmarked
- TP32 20 2N2926 silicon plastic transistors, unmarked and ungraded for colours

UNTESTED PACKS — 60p each Specially for keen bargain hunters

- UT1 50 PNP germanium transistors, AF and RF. Very good yield
- UT2 150 Germanium diodes, miniature glass type
- UT5 40 Zener diodes, 250 mW OAZ240 range, average 50% good
- UT6 25 Zener diodes, 1-1 1/2 watt top hat type, mixed voltages
- UT9 40 NPN silicon planar transistors, of the 2N3707-11 range, low noise amp
- UT10 15 Power transistors, PNP germanium and NPN silicon, mostly TO-3 but some plastic and some marked
- UT13 15 Integrated circuits, experimenters pak, dual in line, TO-5, TTL, OTL, marked and unmarked, some definitely good but old types

FOR FULL RANGES — SEE CATALOGUE

• Singles

BRIDGE RECTIFIERS Plastic encapsulated

P.I.V	50v	100v	400v
1 amp	25p	35p	45p
2 amp	35p	45p	55p
4 amp	45p	50p	80p
6 amp	50p	60p	90p

BY164 equiv. SK82/02 400v 1.5 amp 45p

FETs	18p	UNI-JUNCTION TRANSISTORS	65p
2N3919	20p	2N150	48p
2N4416		2N2646	31p
MOS F.E.T.s		TIS43	
3N141/MEM616	50p		

PUTs	50p	LEDs	18p
2N28027		TIL209—Red	33p
		TIL211—Green	

Also Power Diodes, Thyristors, Triacs, Diacs-Zener Diodes, Opto-Electronics, etc.

X-44 POCKET SIZE R.F. CROSS HATCH GENERATOR

Improved version of our famous Mk 2 model of which thousands are in regular use. Size 150 x 75 x 50mm, strong plastic case with handle/stand, 4 push button operation, 4 patterns. Self-contained line and frame generator and synchro pulse. Pre-set adjust for R.F. output and line/frame synch. Uses 4 alkaline type 1600 batts. Blank raster facility. **FOR COLOUR AND MONO.** (P/P add 35p)

£25 in kit form **£27.50** Built & tested

LOOK OUT NEXT MONTH FOR THE NEW STERLING SOUND MODULES

POWER TRANSISTORS

	Vce	Watts	1cAmps	Price
40P1	15	20	3	20p
40N2	40	40	4	30p
40P2	40	40	4	30p
90N1	15	45	4	25p
90P1	15	45	4	25p
90N2	40	90	8	35p
90P2	40	90	8	35p

Many other types available from 3 to 115 watts

INTEGRATED CIRCUITS

MM5314 Dual in line clock chip **£3**
LMS380/SLED745 Dual in line 2w. audio amp. with data, etc. **75p**
Dual in line I.C. sockets 8 pin **14p**; 14 pin **15p**; 16 pin **16p**.

Sundry

SIGNAL GENERATOR

For MW and IF Covers 550 KHz to 1.6 MHz for MW and 400 to 550KHz for IF. Fully portable. Invaluable in AM repair and alignment jobs (p/p 40p) **£4.25**

POCKET SIGNAL INJECTOR

Fountain-pen type. Invaluable for fault tracing in radio sets, amplifiers, TV's tape recorders, etc. Takes one HP7 battery. **£2.00**

EX-G.P.O. 5in SIDECUTTERS

Not new but in perfect order, per pair **50p**

EX-G.P.O. 6" LONG NOSE PLIERS

Not new, but in perfect order, per pair **60p**

MAINS TRANSFORMERS

MT6	6v 0.6v 100mA	£1.22
MT12	12v 0.12v 50mA	£1.22
SS19/1	9v 1amp	£1.67
SS11/2/1	12v 1amp	£2.05
SS18/1	18v 1amp	£2.50
SS25/2	25v 2amp	£3.00
SS230/2	30v 2amp	£4.25
SS235/4	35v 4amp	£5.50

(P/P 50p any one)

PC EDGE CONNECTORS

Type	Sizes	Pitch	
SSEC 6-way	1 1/4"	156"	32p
SSEC 10	1 3/4"	156"	50p
SSEC 12	2"	156"	60p
SSEC 16	2 1/2"	156"	75p
SSEC 18	3"	156"	85p
SSEC 22	3 1/2"	156"	1.00

UHF TUNER UNITS

Brand new, by famous manufacturer, 625 lines, Channels 21-65, ideal for use as TV sound receiver. With data **£2.50**

BOOKS

All free of VAT. We carry very large stocks of technical books by Babani & Bernard Publishers, by Newnes and Butterworth as well as reference books from the Common Market in English/German/Italian. All detailed in our catalogue.

MONEY SAVER FOR CAR OWNERS

The "Super Spark" Capacity Discharge Ignition Unit, developed out of our original ETI model (of which we have sold well over 9,000) enables you to enjoy this system at a truly economic price. Facilities include simple adaption to pos. or neg. earth, immediate switch back to conventional ignition, anti-burglar immobilisation with all parts in totally enclosed strong metal case. Very easy to fit and install. With full instructions. (P/P add 50p)

KIT £7.95 + READY-BUILT £10.50

• B-P-P SECURITY CHECK POINT

- Write your own name and address clearly in block capital letters.
- Check that your order is correct for description, quantity and price.
- Don't forget VAT at 25% of total value of order unless otherwise stated.
- MAKE SURE YOU GET OUR NAME AND ADDRESS RIGHT WHEN ORDERING.
- Cash (cheque, money or postal order) with your order, please.
- Mention this journal when ordering if you don't want to cut out the coupon.

TERMS OF BUSINESS:

VAT at 25% must be added to total value of order, except for items marked * or (8%) when VAT is to be added at 8%. No VAT on overseas orders. **POST & PACKING** Add 30p for UK orders except where shown otherwise. Minimum mail order acceptable — £1. Overseas orders add £1 for postage. And difference will be credited or charged. **PRICES** Subject to alteration without notice. **AVAILABILITY** All items available at time of going to press when every effort is made to ensure correctness of information.

To: BI-PRE-PAK, 220/222 WEST RD. WESTCLIFF-ON-SEA, ESSEX SSO 9DF

Please send inc. VAT
for which I enclose
NAME
ADDRESS

WW2A

BI-PRE-PAK LTD

Co. Reg. No. 820919

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.

TELEPHONE: SOUTHEND (0702) 46344.

• FIRST IN U.K. WITH PACKS FOR ELECTRONICS USERS

AIRMEC FREQUENCY METER TYPE 265: 0-6000 rpm and 0-100Kc/s £35. Carr. £2.
RACAL L.F. CONVERTER UNIT RA-37B: £35. Carr. £1.
RACAL I.S.B. ADAPTER RA-95A: £65. Carr. £2.
MUIRHEAD ATTENUATORS: 75 ohms 0-8 Mc/s 3V MAK 3 ranges 0-5, 0-25, 0-50 DB £3.00 + 75p post.
CREED MODEL 54 TELEPRINTER: £37.50 each. Carr. £4.
CREED MODEL 75 TELEPRINTER: Receiver only £30.00. Carr. £3.
CREED MODEL 75 TELEPRINTER: Receiver, Transmitter and perforator — £50. Carr. £4.
MULLARD VALVE VOLTMETER: E/7555/3 A.C./D.C. 2 ranges 0-5 and 0-500v. £35. Carr. £2.
EDDYSTONE TELEPRINTER ADAPTOR TYPE 937: £45. Carr. £1.
WAVEMETER CLASS 'D' NO. 2: 1.2 to 20Mc/s 12 volts d.c. input or 240v a.c. £12.50. Carr. £3.
WILD BARFIELD ELECTRIC FURNACE MODEL CCL22X: With ether indicating temperature controllers Model 990°-1400°C. £250. Carr. £5.
A.E.I. MASS SPECTROMETER TYPE MS.10: £300. Carr. £6.
METROVAC IONIZATION GAUGE MODEL V.C.3: £55. Carr. £3.
MUIRHEAD PAMETRADA WAVE ANALYSER D-489-EM: Primarily used for the analysis of complex vibration waveforms but will measure audio and power frequency waveforms from 19Hz-21KHz. Complete with power supply unit 230V 50Hz. Secondhand, very good condition, £110. Carr. £3.
REDIFON TELEPRINTER RELAY UNIT No. 12: ZA-41196 and power supply 200-250V a.c. Polarised relay type 3SEITR. 80-0V 25mA. Two stabilised valves CV 286. Centre Zero Meter 10-0-10. Size 8in. x 8in. x 8in. New condition. £10. Carr. 75p.
SOLARTRON PULSE GENERATOR TYPE G1101-2: £75.00 each. Carr. £2.00.
TELEPRINTER TYPE 7B: Pageprinter 24V d.c. power supply, speed 50 bauds per min, second hand cond. (excellent order) no parts broken. £20 each. Carriage £3.
INSULATION TEST SET: 0-10 kV negative, earth with amplifier provision for checking ionisation. 110/230v a.c. input. S/hand, good cond. £35 + £1 carr.
BRIDGE MEGGER: 250V. (Evershed Vignoles) series 2. £30 each. Carr. £1.
BRIDGE MEGGER: 2,500V., series 1. £30 each. Carr. £1.
CRYSTAL TEST SET TYPE 193: used for checking crystals in freq. range 3000-10,000KHz. Mains 230V 50Hz. Measures crystal current under oscillatory conditions and the equivalent resistance. Crystal freq. can be tested in conjunction with a freq. meter. £25. Carr. £1.50.
SOLARTRON VARIABLE POWER UNIT S.R.S. 1535: 0-500 volts at 100 mA and 6.3 volts C.T. 3 amps d.c. 110/250 volts a.c. input. £18.50. Carr. £1.50.
ALL CARRIAGE QUOTES GIVEN ARE FOR 50-MILE RADIUS OF LONDON ONLY.

NOISE FIGURE METER TYPE 113A (Magnetic AB, Sweden): Complete with Noise Source 121 and 122. £125. Carr. £1.
PRECISION PHASE DETECTOR TYPE 205: Freq. 0.1-15MHz in 5 ranges. Variable time delay microseconds 0-0.1c, 115V input. £55 each. Carr. £1.
MUIRHEAD PHASEMETER D-729: A.M. £85. Carr. £3.
RACAL RAI7 Front Panels: £5. £1 post.
RACAL RECEIVER TYPE 1218: £400.00.
CT.343 VALVE VOLTMETER: in ruggedised steel case. Range 1.2mV to 400V. 6 ranges indicated on 3" meter. 230v a.c. input. £25. Carr. £2.
UHF MICROWAVE MILLIWATTMETER TYPE 14: Direct reading, can be used to measure power from 100MHz upwards. F.S.D. on 4in. scale meter 2.5mW. £40 each. Carr. £1.
S-BAND RADAR TEST SET MW69S (Decca) Oscilloscope and Spectrum Analyser. Further details on request. £200.
Q METER: 30MHz-200MHz. £55. Carr. £1.
AVO TRANSISTOR ANALYSER CT.446: £35. carr. £1.50.
CT.420 SIGNAL GENERATOR: 200-8000c/s Variable tuning. Two fixed frequencies 9000 and 10,000. Internal calibrator 100 & 500 c/s. £75 each carr. £2.
NOISE GENERATOR TF-1106: Frequency 1 to 200 Mc/s Direct noise factor calibration. Output impedance 70 ohms £65 each. Carr. £1.50.
COUNTER EXTENSION UNIT TF-1434/2: Complete with plug-in units £75 carr. £1.50.
MW-59 UNIVERSAL KLYSTRON POWER SUPPLY: £85. Carr. £3.
TF-1278/1 TRAVELLING TUBE WAVE AMPLIFIER: £125. Carr. £2.
BPL A.C. MILLIVOLTMETER TYPE VM.348-D Mk. 3: 2 millivolts-2 volts, 6 ranges. £30. Carr. £1.
CAWKELL REMSCOPE TYPE 741: Memory scope, 'as new' cond. £150.00.
MANSON SYNTHESIZER Q115-URC: 2-30 mc/s. £175.00.
H.V. TRANSFORMER: 8000/8000. Output 300mA. rms. Size: 12in. x 12in. x 36in. 230V input. £40. Carr. £4.
FIREPROOF TELEPHONES: £25.00 each, carr. £1.50.
POWER UNIT: 110/230 volts a.c. input. 28 volts d.c. at 40 amps output. £30.00 each, carr. £3.00.
SMOOTHING UNIT (for the above): £10.00 each. carr. £2.00.
X-BAND MODULATOR CALIBRATOR TYPE MC-4420-X: Mnfr. James Scott. £125 each. Carr. £1.
BACKWARD WAVE OSCILLATOR TYPE SE-125: 6.3 heater, 105V Anode, 7.9mA. Mnfr. Watkins & Johnson. £85 each. Carr. £1.
TEKTRONIX TIME MARK GENERATOR TYPE 180-SI: 5, 10, 50 MHz. £65. Carr. £2.
ROTARY INVERTERS: TYPE PE.218E — input 24-28V d.c., 80 Amps, 4,800 rpm. Output 115V a.c. 13 Amp 400 c/s. 1Ph. P.F.9. £20.00 each. Carr. £2.50.
FREQUENCY METER BC-221: 125-20,000 Kc/s complete with original calibration charts. Checked out. working order £20 — £1.50 carr.

ALL U.K. ORDERS SUBJECT TO VALUE ADDED TAX.

If wishing to call at stores, please telephone for appointment

W. MILLS

3 & 3a BALDOCK STREET, WARE, HERTS. SG12 9DT
 WARE 66312 (STD 0920)
 and at ELSTOW STORAGE DEPOT. Phone: Bedford 740605 (STD 0234)

TRANSISTORS + DIODES

Type	Price excluding VAT	Price including VAT	Type	Price excluding VAT	Price including VAT
BC 107	0.090	0.113	2N 930	0.200	0.250
BC 107A	0.130	0.163	2N 1132	0.240	0.300
BC 107B	0.140	0.175	2N 2129	0.240	0.300
BC 108	0.090	0.113	2N 2218A	0.220	0.275
BC 108A	0.130	0.163	2N 2219	0.220	0.275
BC 108B	0.130	0.163	2N 2219A	0.220	0.275
BC 108C	0.140	0.175	2N 2221	0.180	0.225
BC 109	0.090	0.113	2N 2221A	0.210	0.263
BC 109B	0.140	0.175	2N 2222	0.200	0.250
BC 109C	0.140	0.175	2N 2222A	0.250	0.313
BC 184(K)	0.120	0.150	2N 2904	0.190	0.238
BC 212A(K)	0.110	0.138	2N 2905A	0.230	0.288
BC 212B(K)	0.110	0.138	2N 2906	0.170	0.213
BC 213C(K)	0.110	0.138	2N 2906A	0.170	0.213
BC 214B(K)	0.110	0.138	2N 2907	0.220	0.275
BCY 71	0.220	0.275	2N 2907A	0.240	0.300
BFY 50	0.200	0.250	2N 3053	0.180	0.225
BFY 51	0.200	0.250	2N 4037	0.250	0.313
BD 131A	0.360	0.450	1N 4001	0.050	0.054
BD 135	0.360	0.450	1N 4002	0.065	0.070
BD 136	0.396	0.495	1N 4003	0.070	0.076
BD 137	0.432	0.540	1N 4004	0.075	0.081
BD 138	0.450	0.563	1N 4005	0.080	0.086
BD 139	0.495	0.619	1N 4006	0.085	0.092
2N 929	0.230	0.288	1N 4007	0.090	0.097
			1N 4148	0.040	0.050

REPLECOMPS Ltd. Telephone: Hastings 427914
 123 Bohemia Road, ST. LEONARDS-ON-SEA, Sussex TN376RL

quality

Manufactured strictly to stringent specifications. 12 months guarantee.

service

Orders actioned in 24 hours. Over one million transistors in stock.

special discounts

For large quantities ordered by retailers, educational establishments and hobby clubs.

terms

Cash with order, please. Post and Packing 20p. Minimum order 50p.

Marshall's

A. Marshall (London) Ltd Dept: WW
 42 Cricklewood Broadway London NW2 3ET Tel: 01-452 0161/2
 Telex: 21492
 & 85 West Regent St Glasgow G2 2QD Tel: 041-332 4133
 & 1 Straits Parade Fishponds Bristol BS16 2LX
 Tel: 0272 654201/2
 & 27 Rue Danton Issy Les Moulineaux Paris 92 Tel: 644 2356
Catalogue price 25p Trade and export enquiries welcome

OUR RANGE COVERS OVER 7,000 ITEMS THE LARGEST SELECTION IN BRITAIN TOP 200 IC'S TTL, CMOS & LINEARS

CA3020A	1.80	CD3130	0.88	NE561	4.48	SN7448	0.90	SN74160	1.10
CA3028A	0.74	CD4510	1.25	NE565	4.48	SN7450	0.16	SN74161	1.10
CA3035	1.37	CD4511	1.25	SL604	1.80	SN7451	0.16	SN74162	1.10
CA3046	0.70	CD4516	1.25	SL610C	1.70	SN7453	0.16	SN74163	1.10
CA3048	2.11	CD4518	1.87	SL611C	1.70	SN7454	0.16	SN74164	2.01
CA3052	1.62	CD4520	1.87	SL612C	1.70	SN7460	0.16	SN74165	2.01
CA3089E	1.96	LM301A	0.48	SL620C	2.60	SN7470	0.33	SN74167	4.10
CA3090Q	4.23	LM308	2.50	SL621C	2.60	SN7472	0.26	SN74174	1.25
CD4300	0.36	LM051L	1.50	SL623C	4.59	SN7473	0.36	SN74175	0.90
CD4001	0.36	LM380	1.10	SN7400	3.10	SN7474	0.36	SN74176	1.44
CD4002	0.36	LM381	2.20	SN7401	0.16	SN7475	0.50	SN74180	1.40
CD4006	1.58	LM702C	0.75	SN7401AN	0.16	SN7476	0.36	SN74181	1.95
CD4007	0.36	LM709	0.25	SN7402	0.38	SN7480	0.50	SN74190	2.30
CD4008	1.63	T099	0.38	SN7403	0.16	SN7481	1.25	SN74191	2.30
CD4009	1.18	RDIL	0.45	SN7403	0.16	SN7482	0.75	SN74192	1.15
CD4010	1.18	14DIL	0.38	SN7404	0.19	SN7483	0.95	SN74193	1.15
CD4011	0.36	LM710	0.47	SN7405	0.19	SN7484	0.95	SN74196	1.60
CD4012	0.36	LM723C	0.90	SN7406	0.45	SN7485	1.25	SN74197	1.58
CD4013	0.66	LM741C	0.90	SN7407	0.45	SN7486	0.32	SN74198	2.25
CD4014	1.72	T099	0.40	SN7408	0.19	SN7490	0.45	SN74199	2.25
CD4015	1.72	RDIL	0.40	SN7409	0.22	SN7491	0.85	SN76003N	2.92
CD4016	0.66	14DIL	0.38	SN7410	0.16	SN7492	0.45	SN76013N	1.95
CD4017	1.72	LM747	1.05	SN7411	0.25	SN7493	0.45	SN76023N	1.60
CD4018	2.55	LM748	0.47	SN7412	0.28	SN7494	0.82	SN76033N	2.92
CD4019	0.86	BDIL	0.60	SN7413	0.35	SN7495	0.72	TAA263	1.10
CD4020	1.91	14DIL	0.73	SN7416	0.35	SN7496	0.75	TAA300	1.80
CD4021	1.72	LM3900	0.70	SN7417	0.35	SN74100	1.25	TAA350A	2.10
CD4022	1.66	LM7805	2.00	SN7420	0.16	SN74107	0.36	TAA550	0.60
CD4023	0.36	LM787	2.50	SN7423	0.29	SN74118	1.00	TAA61C	2.18
CD4024	1.24	LM7815	2.50	SN7425	0.29	SN74119	1.92	TAA621	2.03
CD4025	0.32	LM7824	2.50	SN7427	0.29	SN74121	0.37	TAA661B	1.32
CD4027	0.43	MC1303L	1.50	SN7430	0.16	SN74122	0.50	TBA641B	2.25
CD4028	1.50	MC1310P	2.50	SN7432	0.28	SN74123	0.60	TBA651	1.69
CD4029	3.50	MC1320P	0.90	SN7437	0.35	SN74141	0.85	TBA800	1.40
CD4030	0.87	MC1350P	0.84	SN7438	0.35	SN74145	0.90	TBA810	1.40
CD4031	5.19	MC1466L	3.50	SN7440	0.16	SN74150	1.50	TBA820	1.15
CD4037	1.93	MC1469R	2.75	SN7441AN	0.85	SN74151	0.85	TBA920	4.00
CD4041	1.86	MC14553	4.07	SN7442	0.65	SN74153	0.85	14DILSKT	0.12
CD4042	1.38	NE555V	0.70	SN7445	0.90	SN74154	1.50	16DILSKT	0.13
CD4049	0.81	NE556	1.30	SN7446	0.95	SN74155	1.50		
CD4050	0.66	NE560	4.48	SN7447	0.95	SN74157	0.95		

LONDON, GLASGOW, PARIS — AND NOW BRISTOL IT'S OUR SERVICE THAT MAKES US GROW

POPULAR SEMICONDUCTORS

2N696	0.22	2N3906	0.27	AFJ39	0.65	BD139	0.71	MPSA56	0.31
2N697	0.16	2N4037	0.42	AF239	0.65	BD140	0.87	OC2R	0.765
2N698	0.82	2N4036	0.67	AF240	0.90	BF115	0.36	OC35	0.60
2N699	0.59	2N4058	0.18	AF279	0.70	BF117	0.55	OC42	0.50
2N706	0.14	2N4062	0.15	AF280	0.79	BF154	0.20	OC45	0.32
2N708	0.28	2N4289	0.34	AL102	1.00	BF153	0.27	TIP29A	0.69
2N916	0.28	2N4920	1.10	BC107	0.16	BF180	0.35	TIP29C	0.58
2N918	0.32	2N4921	0.83	BC108	0.14	BF1R1	0.36	TIP31A	0.62
2N1302	0.185	2N4923	1.00	BC109	0.14	BF1R4	0.30	TIP32A	0.74
2N1304	0.26	2N5245	0.47	BC147B	0.14	BF194	0.12	TIP33A	1.01
2N1306	0.31	2N5294	0.48	BC148B	0.15	BF195	0.12	TIP34A	1.51
2N1308	0.37	2N5296	0.48	BC149B	0.15	BF196	0.13	TIP35A	2.90
2N1711	0.45	2N5457	0.49	BC157A	0.16	BF197	0.15	TIP36A	2.70
2N2102	0.60	2N5458	0.49	BC158A	0.16	BF198	0.18	TIP41A	0.79
2N2147	0.78	2N5459	0.46	BC167B	0.15	BF244	0.21	TIP42A	0.90
2N2148	0.94	2N6027	0.45	BC168B	0.15	BF257	0.47	TIP2955	0.98
2N2218A	0.22	3N128	0.73	BC169B	0.15	BF258	0.53	TIP3055	0.50
2N2219A	0.26	3N140	1.00	BC182	0.12	BF259	0.55	TIS43	0.28
2N2220	0.25	3N141	0.81	BC182L	0.12	BF561	0.27	ZTX300	0.13
2N2221	0.18	3N200	2.49	BC183	0.12	BF59R	0.25	ZTX301	0.13
2N2222	0.20	40361	0.40	BC183L	0.13	BFR39	0.24	ZTX500	0.15
2N2369	0.20	40362	0.45	BC184	0.13	BFR79	0.24	ZTX501	0.13
2N2646	0.55	40406	0.44	BC184L	0.13	BFX29	0.30	ZTX502	0.18
2N2904	0.22	40407	0.35	BC212A	0.16	BFX30	0.27	1N914	0.07
2N2905	0.25	40408	0.50	BC212LA	0.16	BFX84	0.24	1N3754	0.15
2N2906	0.19	40409	0.52	BC213LA	0.15	BFX85	0.30	1N4007	0.10
2N2907	0.22	40410	0.52	BC214B	0.18	BFX88	0.25	1N4148	0.07
2N2924	0.20	40411	2.00	BC237B	0.16	BFY50	0.225	1N4504	0.22
2N2926B	0.12	40594	0.74	BC238C	0.15	BFY51	0.23	1N5408	0.30
2N3053	0.25	40595	0.84	BC239C	0.15	BFY52	0.205	AI129	0.08
2N3054	0.60	40636	1.10	BC257A	0.16	BRY39	0.48	BA102	0.25
2N3055	0.75	40673	0.73	BC258B	0.16	ME0402	0.20	BA145	0.18
2N3391	0.28	AC126	0.20	BC259B	0.17	ME0412	0.18	BA154	0.12
2N3392	0.15	AC127	0.20	BC301	0.34	ME4102	0.11	BA155	0.12
2N3393	0.15	AC12R	0.20	BC307B	0.17	NJ480	0.95	BB103B	0.23
2N3440	0.59	AC151	0.24	BC308A	0.15	NJ48	1.20	BB104B	0.45
2N3442	1.40	AC152	0.49	BC309C	0.20	NJ490	1.05	BY126	0.12
2N3638	0.15	AC153	0.35	BC327	0.23	MJ491	1.45	BY127	0.15
2N3702	0.12	AC176	0.30	BC328	0.22	MJ2955	1.00	BY211	0.51
2N3703	0.13	AC187K	0.35	BCY70	0.17	MJE340	0.48	BY212	0.51
2N3704	0.15	AC188K	0.40	BCY71	0.22	MJE370	0.65	OA47	0.06
2N3706	0.15	AD143	0.68	BCY72	0.15	MJE371	0.75	OA81	0.18
2N3708	0.14	AD161	0.50	BD121	1.00	MJF520	0.60	OA90	0.06
2N3714	1.38	AD162	0.50	BD123	0.82	MJE521	0.70	OA91	0.06
2N3716	1.80	AF106	0.40	BD124	0.67	MJE2955	1.20	OA200	0.08
2N3771	2.20	AF109	0.40	BD131	0.40	MJE3055	0.75	BY164	0.57
2N3773	2.65	AF115	0.35	BD132	0.50	MPB113	0.47	ST2 diac	0.20
2N3789	0.37	AF116	0.35	BD135	0.43	MPF102	0.39	40669	1.00
2N3819	0.37	AF117	0.35	BD136	0.47	MPSA05	0.25	TC44	0.29
2N3820	0.64	AF118	0.35	BD137	0.53	MPSA06	0.31	CI06D	0.65
2N3904	0.27	AF124	0.30	BD138	0.63	MPSA55	0.31	OPR12	0.60

Prices correct at January, 1976, but all exclusive of V.A.T. Post & Packing 25p



the audio amateur ?

What a trip old Richard's Rhine journey could have become had he built his own mixers, 900 watt amps, octave equalizers, 24 inch woofers, electronic crossovers, and home brew electrostatics. Zounds what sounds!

Ask our Rhine maidens for details.


the Audio Amateur
 Yellow Oak Cottage
 Tillington nr. Hereford
 HR48LQ

Send now for a free prospectus.

Craig Stark of STEREO REVIEW says: "Top quality, only U.S. publication devoted to the serious audiophile constructor."

Name _____
 Address _____

ELECTROVALUE

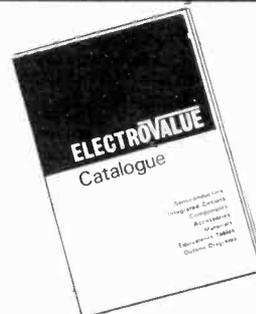

READY NOW CATALOGUE 8

- 144 pages
- New lines
- UP-DATED PRODUCT & PRICE INFORMATION
- 40P REFUND VOUCHER

We have made it just about as comprehensive and up-to-the-minute as possible. Thousands of items from vast ranges of semi-conductors including I.C.s to components, tools, accessories, technical information and diagrams are included as well as a refund voucher worth 40p for spending on orders list value £5 or more. SEND NOW FOR YOUR COPY BY RETURN. It's an investment in practical money-saving and reliability!

40p post paid

+ E.V. PRICE STABILIZATION POLICY FOR 1976
 This is one of reviewing prices every 3 months rather than trying to keep up with day by day changes as they occur. We have in fact held prices better than we anticipated in 1975. Next review period starts April 1st 1976.

+ E.V. DISCOUNT PLAN
 Applies to all items except the few where prices are shown NETT. 5% on orders from £5 to £14.99. 10% on orders value £15 or more.

+ FREE POST & PACKING
 In UK for pre-paid mail orders over £2. If under there is an additional handling charge of 15p.

+ QUALITY GUARANTEE
 All goods are sold on the understanding that they conform to makers' specifications. No rejects, seconds or sub-standard merchandise.

ELECTROVALUE LTD

All communications to Dept 4/2
 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
 Telephone Egham 3603. Telex 264475. Shop hours 9-5.30 daily, 9-1 p.m. Sats.
 NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester M19 1NA
 Telephone (061) 432 4945. Shop hours Daily 9-5.30 p.m., 9-1 p.m. Sats.
 In U.S.A. you are invited to contact ELECTROVALUE AMERICA, P.O. Box 337 Peterborough NH03458

REED SWITCH INSERTS



Overall length 1.85in (Body length 1.1in) Diameter 0.14in to switch up to 500mA or 250VDC Gold clad contacts 74p per doz **£4.15** per 100 **£29.85** per 1,000 All carriage paid U.K.
Operating Magnets 95p per doz **£6.95** per 100 **£67** per 1,000 All carriage paid U.K.
Operating Coils for 12v supply to accept up to four standard reeds **£2.50** per doz **£12.60** per 100 All carriage paid U.K.
Heavy duty type (Body length 2in) Diameter 0.22in to switch up to 1A at up to 250VAC Gold clad contacts **£1.45** per doz **£6.95** per 100. **£52.00** per 1,000 **Changeover Heavy Duty type £2.80** per doz All carriage paid U.K.
Magnets for HD reeds **£1.50** per doz A few coils available for HD reeds POA.

C-SCOPE METAL DETECTORS

Represent today's BEST VALUE in metal detection equipment:
 BF050 integral speaker **£26.24**
 BF060 integral speaker and meter **£33.59**
 IB100 with headphones **£52.59**
 IB300 with headphones and meter **£68.24**
 TR200 with headphones **£59.90**
 TR400 with headphones and meter **£78.43**

Full information on receipt of 10p stamp
HUNT THAT TREASURE!

INDUCTION GENERATOR

Requires a supply voltage of 50V 50Hz and provides an output of 7V per 1,000 r.p.m. directly proportional to speed. This instrument has a wide variety of applications, e.g. anemometers, measuring shaft speed etc. In brand new condition **£5.60** post paid

ITT OFFICE INTERCOM

20 way modern manual SWB and facilities. Lightweight desk sets. Brand new in cartons **£100** inc. P & P. VAT Spare dettaphones **£7.50** ea

TELEPRINTER PAPER

Standard rolls 1 ply **£5.00** per doz 2 ply **£5.00** per doz 3 ply **£5.40** per doz 4 ply **£5.70** per doz All P Pd U.K. Telex your order now

TAPE STORAGE CANS

Brand new finished steel cans originally intended for 16mm film but ideal for storing 7mm reels of tape. Our last supply of these items was quickly exhausted at 30p each but as a result of a massive new purchase we can now offer a case of 55 at **£6.80** inc. P & P. and VAT

SOLAR CELLS

Ferranti silicon MS118E, active area 390 sq. mm. Open CCT voltage 550mV at 3000 lumens/sq ft. Sh. Cct Current 60mA. Maximum load 9 ohms Dia 34mm. Thickness 6mm. Ex. made up panel **£1.35** (inc. P & P and VAT)

CONTINENTAL CUSTOMERS

— we have a direct link by air from Lydd to Beauvais (also Channel Islands) and are 35.45 minutes drive from Dover-Folkestone with direct hovercraft and sea links with France and Belgium

SPECIALIST STOCKISTS OF SERVOMOTORS, SYNCHROS, TEST EQUIPMENT, METERS AND CONNECTORS

Servo and Electronic Sales Ltd
 24 HIGH ST., LYDD, KENT TN29 9AJ. Tel. Lydd 20522 (STD 0679) VAT No. 201-1296-23. TELEX 965265

PLESSEY GROUND BASED

U.H.F. GROUND/AIR TX/RX FOR EXPORT ONLY OR SALE TO LICENSED USERS

Single Channel Receiver 5820-99-932-5694
 Single Channel Transmitter 5820-99-932-5698
 Single Channel Amplifier 5820-99-932-5701
 Power Unit for Amplifier 5820-99-932-5700
 Cooler Unit 5820-99-932-3995
 These assemble into free standing rack unit providing UHF communications over 225.0 to 399.9MHz. The TX Amplifier unit giving 100 Watts R.F. output into 50 Ohms. Spare sub-units available. All are guaranteed new and unused. Full details on request

HEWLETT PACKARD

SAMPLING SCOPE HP185A

£324 inc. carr. and VAT **HP185B £357.**

STAINLESS STEEL VACUUM CONTAINERS

FOR LIQUIDS. Capacity 2 U.S. GALLS. FITTED WITH DELIVERY TAPS. Brand new in cartons—**£25** (C Pd U.K.)

PANEL DISPLAY RECORDING CAMERA

Manufactured A.G.I. Specially for the recording of complex instrument displays on 2 1/4in x 2 1/4in sheets. Fitted 80mm F3.5 lens. Shutter speeds 1/100, 1/50, 1/25 sec. and time exp. Focusing at 1.75 to 50ft. in 18 steps. Aperture stgts. F3.5 to F22. Prismatic viewfinder and facility for viewing direct on ground glass screen. Rotating filter attachment. Cord film advance and shutter cock with septe. Button control and electrical release facility (24V DC). Spool holds 40 exposures. Camera may be wall mounted on bracket supplied. Tripod mounting socket provided. In wooden case. Two grades available as new. Grade A **£35.50** (inc. P and VAT). Somewhat used but serviceable Grade B **£28.40** (inc. P & P and VAT).

COMPUTERS AND PERIPHERALS

ICL 1904 CPU (complete) — documentation will be available — with 32K 2U5 Plessey core store **£1000**. ICL 7070/2 UNIFLEXER (complete) **£150**. BRPE 110 ch/sec 8-chan paper tape punches — some silence covers **£120**. Plessey 68/1339 32K (13 bits) 1uS corestores **£35**. Mullard AW 3331 16K (25 bit) 2uS corestores **£40**. Mullard AW 3795 corestores **£30**. IBM 729 1/4 M T U — documentation available **£200**. ICL mainframe PSUs 6V 25A **£25** and 28V 20A **£40**. ICL peripheral PSUs — 10V and — 20V **£20**. Ampex & D.R.I. digital tape heads (7 & 9 track) P.O.A. ICL 1971 & 1973 servo motors & vacuum blowers P.O.A. CDC/ICL 2802 (EDS) disc drives — mechanical spares P.O.A. RCA/ICL 1500 series electronic & mechanical spares P.O.A. Belling-Lee R.F.I. suppressors — 230v/20A (50Hz) **£30**. STC Sentryral fire (smoke) detectors — data available **£15**. Vactric Shaft position encoders type 11DP101 (10 bit) **£15**. Tolana B-channel F.M. instrumentation recorder (complete) **£350**.
 We can also design and construct non-standard interfaces between computers, instrumentation and control equipment etc. — and we have a large number of one off pieces of test equipment. If you have any problems in this field do not hesitate to get in touch with us. Contact D.P. Manager. Chris Seton (Ext. 3)

GE OPTICAL TAPE READERS

5, 7 and 8 track 300 ch/sec built-in amps and cont. ccts. Excellent condn. Tested **£70** inc. P&P and VAT

LEMANIA AIRCREW CHRONOGRAPHS
 Stainless steel case with screw back luminous hands and markings. One-fifth sec sweep hand controlled independently of main movement by press to start stop and return to zero button. 15 jewel movement. Many of these watches are as new but all have been completely overhauled and checked for accuracy. Fitted strap. White face **£18.80**. Black face **£19.75** inc. P & P

GS WATCHES
 All with brushed stainless steel case with screw back and black faces. Manufactured by TIMOR, ETERNA, LEMANIA, VERTEX, RECORD, CYMA, etc. to standard specification. Completely overhauled. Fitted strap **£9.05** (inc. P & P). We also have limited quantities of these watches by OMEGA, BUREN, HAMILTON and IWC at **£15.30** inc. P & P. SMITHS GS watch with sweep second hand **£9.25** inc. P & P. VAT. All watches: **Inspection against remittance**

ANALYTICAL EQUIPMENT GAS CHROMATOGRAPHY RESEARCH OVEN

PV4051/4056 (other GC items in stock)
 A large capacity oven or low thermal mass for use between 35 and 400°C. Provides a forced air circulating system yielding 1000 changes of air per min. The oven has forced air cooled outer surfaces when the internal temperature is high 210-240V 50Hz 2.6KW **£31.50** (C Pd England and Wales)

IONISATION AMPLIFIER PV4075
 A modern high grade low noise solid state amplifier to feed a potentiometer recorder. 18 input ranges from 10⁻¹ to 5 x 10⁻⁴. A with 5 outputs of 1mV to 100mV. Linearity 0.1% fs. Noise less than 0.5% fs at max sensitivity. Back off facility. Dimensions 28 x 10 x 43 cm deep. With operating information **£28.50** (C Pd U.K.).
 Details of these three and other gas chromatography items price 25p (C.W.O. only). Handbooks (complete) available

AIRCRAFT INSTRUMENTS

For industrial and educational use. Released items available for flight use.
400HZ ROTARY CONVERTERS
 Both DC & AC input available. e.g. 415v 50Hz 115v 400Hz 1 ph 50w AJ **£27.50**.

MULTIWAY CABLES

In stock up to 50 way or up to 750 amp. Also PTFE insulated types

MARCONI SPECTRUM ANALYSERS OA1094A/S

Listed at £2,700 our price **£565**.

ACTUATORS, RELAYS, FLOOD-LAMPS, POWER UNITS, TRIMPOTS, FANS, MICROWAVE EQUIPMENT

All ex stock

SOLARTRON OSCILLOSCOPES

In stock CD1183, CD1212, CD1220, CD1400, P O A and INSTRUMENTS SR151, 152, VP253, OS103, C0546, JX641, JX641A, VF252, JX746, LM1420, TD960, JX603, JM1600, etc P O A

REACH FOR THE PEAKS OF MEASURING INSTRUMENT ENGINEERING!

TYPE TAD

Dims	48	66	85	118	150
in	x	x	x	x	x
mm	42	50	70	106	110
50 uA	£3.73	£3.91	£4.10	£5.00	£5.55
500 uA	£3.44	£3.61	£3.82	£4.72	£5.42
1mA	£3.37	£3.54	£3.74	£4.60	£5.33
15vDC	£3.40	£3.59	£3.77	£4.67	£5.36
300vAC	£3.57	£3.76	£3.94	£4.83	£5.40

TYPE SA

Dims	43	51	61	82
in	x	x	x	x
mm	43	51	61	78
50 uA	£3.62	£3.69	£3.97	£4.22
500 uA	£3.31	£3.38	£3.63	£3.86
1mA	£3.21	£3.28	£3.53	£3.82
15vDC	£3.25	£3.32	£3.60	£3.86
300vAC	£3.49	£3.56	£3.77	£4.02

FOR YOUR PRODUCTION REQUIREMENTS USE ALPS PANEL METERS
FULL RANGE PRICE LIST—SAE PLEASE!
 Substantial quantity discounts to manufacturers
 Remember! We are the sole importers!

TYPE SR

Dims	73	78	92
in	x	x	x
mm	56	63	72
50 uA	£4.03	£4.28	£4.52
500 uA	£3.68	£3.93	£4.18
1mA	£3.58	£3.83	£4.08
15vDC	£3.70	£3.94	£4.19
300vAC	£3.83	£3.97	£4.32

LABORATORY TYPE SA65E

Metric size 82 x 78mm

50 uA	£6.69
500 uA	£6.44
1mA	£6.24
1A	£6.34
15vDC	£6.34
300vAC	£6.34

ALL ABOVE PRICES INCLUDE P. & P. and VAT

NEW ADDITIONS to our range of PANEL METERS available at present only in MANUFACTURING QUANTITIES

SE45	64 x 52 mm
SE52	80 x 60 mm
SE65	100 x 80 mm
SE85	120 x 100 mm

SU45	69 x 53 mm
SU55	87 x 63 mm
SU65	105 x 77 mm

Above meter forms are for moving coil movements only and may house S-meter and VU-meter instruments.

VU METERS

SF100	72 x 68 mm
SF104	63 x 60 mm
SF106	63 x 60 mm

With A or B Scales. Linear Movements or to B S T J spec. Also available in most standard cases.
 All meters can be supplied with special or personalised scales, internal illumination, coloured front lenses, mirror scales, special pointer forms, etc.

Full details and prices on request

AUTOMOBILE TEST EQUIPMENT SERVO AUTOTESTER No. 1


0.3 2 & 0.15v. 0.80 ADC & 0.20K Ohms. dwell angle and speed for 4, 6 & 8 cvc engines and EHT SEC VOLTS. A substitute capacitor is incorporated. Size 26.5 x 14 x 16.5cm. W6 3.25kg. With handbook **£30.37** inc. P & P & VAT

SERVO AUTOTESTER No. 2
 0.16v. 0.80A dwell angle. Speed for 4, 6 & 8 cvc engines. Size 16 x 9.5 x 6.5 cm. Wt 0.45kg. With instrns. **£11.15** inc. P & P & VAT

SERVO AUTOTESTER No. 3
 Simultaneously on separate meters 0.16v & 0.80A. Size 17 x 10 x 7 cm. Wt 0.45kg. Price **£9.78** inc. P & P & VAT

SERVO AUTOTESTER No. 4
 Dwell angle and engine speed. Hand held instnt. Size 14 x 8 x 5 cm. Wt 0.26kg. Price **£6.35** inc. P & P & VAT

MIL SYNCHROS AND SERVOMOTORS EX STOCK

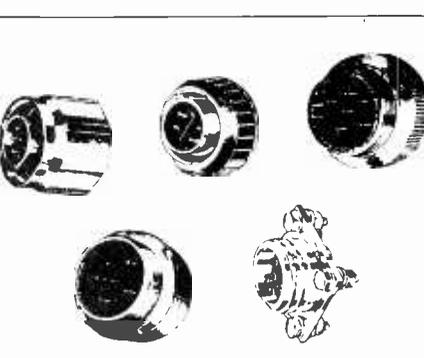

OVER 300,000 RF AND MULTIWAY CONNECTORS IN STOCK. TELEX YOUR REQUIREMENTS NOW!

Fully guaranteed Individually packed VALVES

A1055	£ 1.25	ECL82	£ 0.35	GZ37	£ 1.00	PY33	£ 0.80
ARB	0.55	ECL83	0.70	KT88	2.50	PY80	0.40
ATP4	0.50	ECL86	0.50	KT88	3.85	PY81	0.40
B12H	3.00	EF36	0.65	MM4	0.75	PY82	0.40
CY31	0.50	EF37A	1.20	ML6	0.65	PY83	0.40
DAF96	0.55	EF40	0.75	OA2	0.45	PY88	0.40
DF96	0.55	EF41	0.85	OB2	0.45	PY500	1.00
DK96	0.70	EF80	0.30	PC80B	0.40	PY800	0.45
DL92	0.40	EF83	0.35	PC97	0.50	PY801	0.50
DL96	0.60	EF85	0.30	PC900	0.50	QQV03-10	
DY86/87	0.40	EF86	0.35	PCC84	0.40		1.40
DY802	0.45	EF89	0.30	PCC85	0.40	QQV06-40A	
EB8CC/01120	0.90	EF92	0.50	PCC89	0.50		8.00
E180CC	0.70	EF95	0.40	PCC189	0.60	R19	0.75
E182CC	1.25	EF183	0.35	PCF80	0.40	SC1/400	3.00
EA50	0.40	EF184	0.35	PCF82	0.40	SC1/600	5.00
EABC80	0.40	EF1200	0.75	PCF84	0.60	SP61	0.75
EAF42	0.75	EL34	0.70	PCF86	0.60	T21	5.00
EB91	0.30	EL36	0.60	PCF200	0.75	U25	0.85
EB33	1.00	EL37	1.80	PCF201	0.75	U26	0.75
EB41	0.75	EL41	0.80	PCF80	0.55	U27	0.85
EBF80	0.40	EL81	0.60	PCF802	0.50	U191	0.75
EBF83	0.50	EL82	0.55	PCF805	0.90	UBD1	0.75
EBF89	0.40	EL84	0.30	PCF806	0.75	UABC80	0.40
EC52	0.35	EL85	0.60	PCF808	0.90	UAF42	0.85
EC881	0.80	EL86	0.45	PCH200	0.80	UBC41	0.80
EC82	0.35	EL90	0.45	PCL81	0.55	UBF80	0.40
EC83	0.35	EL504	0.60	PCL82	0.40	UBF89	0.40
EC84	0.35	EM31	0.60	PCL83	0.85	UBL1	1.00
EC85	0.40	EM80	0.55	PCL84	0.45	UBL21	0.75
EC86	0.90	EM84	0.40	PCL86	0.50	UCC85	0.45
EC88	0.50	EM87	1.00	PCL805	0.80	UCF80	0.75
EC8189	0.70	EY51	0.45	PFL200	0.70	UCH42	0.75
ECF80	0.40	EY81	0.40	PL35	0.60	UCH91	0.45
ECF82	0.40	EY86	0.40	PL81	0.50	UCL82	0.65
ECF801	0.75	EY88	0.50	PL82	0.45	UCL83	0.65
ECH35	1.40	EZ40	0.70	PL83	0.45	UF41	0.70
ECH42	0.80	EZ41	0.75	PL84	0.45	UF80	0.35
ECH81	0.35	EZ80	0.30	PL504	0.80	UF85	0.45
ECH83	0.45	EZ81	0.30	PL508	1.00	UF89	0.50
ECH84	0.45	GY501	0.75	PL509	1.35	UL41	0.70
ECL80	0.55	GZ34	0.70	PL802	1.75		

A lot of these valves are imported and prices vary for each delivery, so we reserve the right to change prices for new stock when unavoidable.

UL84	£ 0.40	3A4	£ 0.60	6AL5	£ 0.30	6AX5GT	£ 1.00	6C6	£ 0.50	6J7G	£ 0.40
UY41	0.50	5B1	7.00	6AL5W	0.55	6B7	0.70	6C6B	0.50	6K6GT	0.80
VR105/300	0.45	306	0.40	6AN6	0.80	6BA6	0.35	6C6B	1.45	6K7	0.55
VR150/300	0.45	354	0.40	6AN8	0.45	6BE6	0.40	6CL6	0.75	6K7G	0.30
X61M	1.40	3V4	0.85					6D6	0.55	6K8GT	0.50
X66	0.65	5B254M	4.50					6E8	0.85	6K25	1.00
Z800U	2.70	5B255M	4.50					6F7	1.10	6L6	1.90
Z801U	1.20	5R4GY	1.10					6FR6	0.75	6L6G	0.60
Z900T	2.70	SU4	0.50					6F23	0.90	6L7G	0.40
		5V4G	0.55					6F32	0.75	6SA7	0.50
		5Y3GT	0.60					6F33	3.50	6SA7GT	0.40
		5Z3	0.80	6A05	0.45	6BG6G	0.80	6H6	0.40	6SC7GT	0.40
		5Z4GT	0.55	6A05W	0.70	6B36	0.85	6J4WA	1.25	6SG7	0.50
		6A87	0.60	6A56	0.80	6B07A	0.60	6J5	0.85	6SJ7	0.55
		6A76	0.80	6A67	0.80	6B7	1.20	6J5GT	0.50	6SJ7GT	0.35
		6A6H	0.70	6A6V	0.40	6B9W6	1.00	6K6	0.30	6SK7	0.55
		6A6K5	0.40	6A6V6	0.45	6B9W7	1.00	6L7	0.60	6SL7GT	0.50
		6A6K8	0.40	6AX4GT	0.75	6C4	0.40				

VAT
Please add 25% to all orders

TRANSISTORS, DIODES etc.

AC113	AF178	BSY38	OAZ200	OC206	2N3054
AC126	AF186	BSY95A	OC22	SX754	2N3055
AC127	AF239	BZY16	OC25	ZR11	2N339
AC128	AF212	CRS1/10	OC26	ZR21	2N3638A
AC176	ASV26	CRS1/20	OC28	1N23A	2N3730
ACY18	ASV27	CRS1/30	OC29	1N25	2N3819
ACY19	ASV28	CRS1/40	OC35	1N32A	2N403R
ACY20	BC108	CRS3/10	OC36	1N38A	2N405R
ACY39	BC118	CRS3/20	OC42	1N43	2N4061
ACY40	BC119	CRS3/30	OC44	1N70	2N4785
AD149	BC136	CRS3/40	OC45	1N277	2N5295
AD161	BC137	CRS25/C25	OC70	1N415C	3N12R
AD162	BC148A	GET115	OC73	1N4148	3N154
AD211	BC172	GET116	OC78	2N456A	3N159
AD212	BC172A	GET117	OC78	2N708	2S303
AF114	BC212A	GEX66	OC81	2N518	20R2
AF115	BCY31	OA5	OC82	2N1304	40250
AF116	BCY33	OA47	OC82D	2N1305	40251
AF117	BCY72	OA70	OC82M	2N1307	40310
AF118	8F115	OA71	OC83	2N1309	40668
AF124	8F167	OA73	OC139	2N2082	
AF125	8F185	OA79	OC140	2N2147	
AF126	8F551	OA91	OC170	2N2411	
AF127	8F52	OA200	OC172	2N2989	
AF139	BSY27	OA202	OC200	2N3053	

MINIMUM POSTAL ORDER £1. PERSONAL CALLERS WELCOME.
MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves
U.K. Postage £1-£2 20p, £2-£3 30p, £3-£5 40p, over £5 free



COLOMOR
ALL valves guaranteed

6S87GT	£ 0.50	30C17	£ 1.00	6064	£ 0.80
6S07	0.55	30C18	0.90	6085	1.00
6V6GT	0.55	30F5	1.00	6087	0.70
6X4	0.40	39F11	1.00	6080	2.30
6X5G	0.40	30FL12	1.10	6146	3.35
6X5GT	0.50	30FL14	0.90	6146B	3.85
6V6G	0.90	30L15	0.95	8020	5.00
6Z4	0.65	30L17	0.95	9001	5.00
6Z0L2	0.90	30P12	1.00	9002	0.50
7B7	0.80	30P19	1.00	9003	0.70
7Y4	0.80	30P11	0.95	9004	0.35
9D6	0.40	30PL13	1.10	9006	0.35
11E2	6.00	30PL14	1.10		
12A6	0.55	35L6GT	0.75		
12A16	0.45	35W4	0.50		
12A17	0.40	35Z6GT	0.70		
12A7U	0.35	50C5	0.60		
12A6V	0.50	50CD6G	1.10		
12A7X	0.35	75	1.00		
12BA6	0.45	75C1	0.75		
12BE6	0.50	76	0.75		
12BH7	0.50	78	0.70		
12C8	0.55	80	0.75		
12E1	3.50	85A2	0.75		
12K5	1.10	723A/b	9.00		
12K7GT	0.50	803	6.00		
12K8GT	0.70	805	14.00		
12Q7GT	0.70	807	0.65		
12SA7GT	0.70	813	6.50		
12S67	0.55	866A	1.20		
12S7U	0.55	931A	6.00		
12Y4	0.40	954	0.50		
14S7	1.00	955	0.50		
18A05	0.65	956	0.50		
19G3	8.00	957	0.50		
19G6	6.80	1305	0.70		
19H5	14.00	1629	0.70		
20P3	0.60	2051	1.00		
20P4	1.10	5933	3.00		
25L6GT	0.70	6057	0.75		
30C15	1.00	6060	0.70		

C. R. TUBES


OG7-5	12.00
DG132	18.00
MCR33535	8.00
VCR139A	8.00
3BP1	4.50
8B1	8.00
8BL	9.00

SPECIAL VALVES

Cv239	45.00
M503-2J42	6.00
K301	7.00
KRN2A	6.00
OY4-250	6.00
TY-500	19.00
725A	30.00
2/192	23.00
140.00	

VALVES AND TRANSISTORS

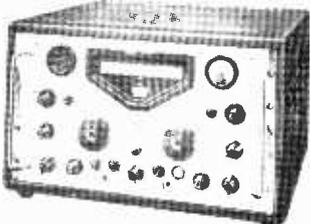Telephone enquiries for valves, transistors, etc retail 749 3934, trade and export 743 0899



RACAL RECEIVERS
Models RA17, RA17 Mk II, RA 17L, RA17W, RA17TE, in condition from working "as seen" to brand new in cabinets. Prices on application
DIVERSITY SWITCH TYPE MA168B solid state. £45.00.
RA98A SSB ADAPTOR P.O.A.

KAHN SSB ADAPTOR MODEL RSSB 62 1B Designed for receivers with 455-500kHz I.F. (eg Collins 51J AR8BD etc) at 100mV. (max) input. Features Electronic A.F.C. carrier frequency diversity to combat fading, 20 sec R.C. memory to maintain tuning during severe fading individual carrier meters; nuvistors; low distortion production demodulator. Full spec & P.O.A

TEKTRONIX OSCILLOSCOPES
545-33 MHz. Separate time bases with delay. Price on application.
PLUG-IN UNITS
G-20 MHz differential 50MV-20V.
D-High gain differential 1MV-50V.


CT 480 SIGNAL GENERATOR 70KMc/s to 12KMc/s £160
DIGITAL VOLTMETER DM 2003 1kv peak input. 2v to 1kv £75.

TECHNICAL MATERIAL CORP: EXCITER/TRANSMITTING MODE SELECTOR Freq 2-32MHz M.O and 10 crystal positions. Vernier tuning U.S.B. L.S.B. varicoupler section etc. £200.
F.S.K. EXCITER. Freq 1-6.5MHz 0-100Hz continuous frequency shift. Up to 600Hz switched frequency correction. Modes F A X F S S M S C C W. £50.

BOONTON FM/AM SIGNAL GENERATOR TYPES 202E & 202M. 54-216 MHz in two ranges, complete with separate power supply unit £275.
EHV POWER SUPPLY 115V input 100KV at 5mA output £150.

SOLARTRON CD 1400 Oscilloscope. Few left, only £110.

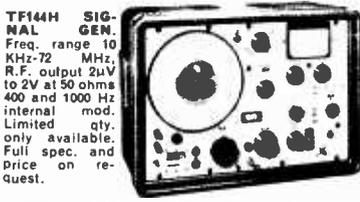Open 9-12.30, 1.30-5.30 p.m. except Thursday 9-1 p.m.



TF144H SIGNAL GENERATOR
Freq. range 10 KHz-72 MHz. R.F. output 2uV to 2V at 50 ohms 400 and 1000 Hz internal mod. Limited only available. Full spec. and Price on request.

TF 1220B, TF1225A, TF 577A. WHITE NOISE TEST SET £185.00. Full spec. on request.

TF 1400S DOUBLE PULSE GENERATOR WITH TM 6600S SECONDARY PULSE UNIT. For testing radar, nucleonics, scopes, counters, filters etc. SPEC. TF 1400S. Rep. freq. 10Hz to 100kHz, pulse width 0.1 to 100u sec., delay -1.5 to +3000u sec., rise time 30N sec. SPEC. TM 6600S. As for TF1400S except pulse width 0.5 to 25u sec., delay 0 to +300u sec. £175.

TF 893 AUDIO OUTPUT METERS £55.

NOISE GENERATOR TF1053 (CT207). Range 100-600MHz. Noise factor up to 150 (21.7db) at 75 ohms. Audio power up to 500MW. £95.
MARCONI TF893 AUDIO OUTPUT METERS Price on application

MARCONI HR23 TRIPLE DIVERSITY IS RECEIVERS. Freq 3-27.5 MHz. VFO or 6xtal positions. Reception of independent, single or double-side band transmissions. Full specification and price on application

HEWLETT-PACKARD 175A OSCILLOSCOPE with 1750A dual trace vert plug-in and 1781B delay time base plug-in. 50MHz minimum bandwidth at 50mV/cm. 17B modes: main, main single, mixed, main delayed, delaying. Full Spec & P.O.A.
540B TRANSFER OSCILLATOR. Measures frequency up to 12 GHz. May be used on its own or with freq counter. P.O.A.
200AB AUDIO OSCILLATOR 19kHz, 600ohm balanced or unbalanced small size. £25.
300A HARMONIC WAVE ANALYSER Freq 0-16kHz. Full spec & P.O.A.

MULLARD PRECISION VARIABLE CAPACITOR TYPE F.2. 15pF to 336pF. Supplied with individual calibration certificate. Brand new in original packing £12. Carriage £1.

MS 111D DANISH PRODUCTION SIGNAL GENERATOR 10Kc - 110Mc £150.

BEST PRICES PAID FOR TEST AND COMMUNICATION EQUIPMENT. Single items or quantities. Private or Industrial.



TF 801D1/5 SIGNAL GENERATOR. Range 10-485 MHz in five ranges. R.F. output 0.1 uV-1V source s.m.f. Dial calibrated in volts, decibels and power relative to thermal noise. Piston type attenuator. 50u output impedance. Internal modulation at 1 kHz at up to 90% depth, also external sine and pulse modulation. Built-in 5MHz crystal calibrator. Separate R.F. and mod. meters. P.O.A.

TF801B/2. Spec as for TF801D but minor circuit differences. Working order £95.

TF 1370 R.C. OSCILLATOR sine/square wave 10Hz to 10MHz £140.

TF995 A/1 or A/2 or A/2M SIGNAL GENERATORS. AM / FM freq 1.5-220MHz. Prices on application

TF 934 DEVIATION METER 250MHz/FM £55.

TM 8517 VIDEO AMPLIFIER £60.

ALL MAIL ORDER BY RETURN. C.O.D. SERVICE WELCOME

C. T. ELECTRONICS

Tel: 01-994 6275

All mail order and enquiries to 270 Acton Lane, Chiswick, London W4 5DG

VAT
Unless otherwise stated all prices are exclusive of VAT. Please check whether the goods you are ordering are 25% or 8% Carriage orders under £5 please add 33p. Order over £10 post free in U.K. only. This is to be at our discretion.

SEMICONDUCTORS

AAZ12	25p	BC214	14p	IS100	15p
AC107	35p	BC214L	15p	IS103	15p
AC125	25p	BC238	15p	MJ340	50p
AC126	25p	BC239	15p	MJ481	95p
AC127	25p	BC300	30p	MJ481	95p
AC128	25p	BC301	30p	MJ2801	£1.25
AC176	25p	BC302	30p	MJ2901	£1.95
AC187	27p	BC303	35p	MJ340	50p
AC188	27p	BCY31	35p	MJ370	75p
ACY17	25p	BCY32	95p	MJ371	90p
ACY18	25p	BCY33	60p	MJ520	65p
ACY19	25p	BCY34	30p	MJ2955	£1.20
ACY20	25p	BCY38	65p	MJ3055	75p
ACY21	25p	BCY39	95p	MM1613	45p
AD140	60p	BCY55	£1.50	MM1712	60p
AD142	60p	BCY70	20p	MPF102	45p
AD161	45p	BCY71	20p	MPF103	45p
AD162	45p	BCY72	20p	MPF104	35p
AF114	25p	BD121	75p	MPF104	35p
AF115	25p	BD123	85p	(2N5458)	35p
AF116	25p	BD124	70p	MPF105	40p
AF117	25p	BD131	40p	(2N5459)	40p
AF118	50p	BD132	50p	OA47	10p
AF124	30p	BD135	50p	OA70	10p
AF239	60p	BD139	50p	OA79	10p
BA102	30p	BD139	75p	OA81	10p
BA112	50p	BD140	87p	OA90	10p
BA114	16p	BD153	80p	OA91	10p
BA155	16p	BD156	80p	OA200	10p
BA156	15p	BDY17	£1.50	OA202	10p
BC107	15p	BDY18	£1.75	OA210	10p
BC108	12p	BDY19	£1.90	OA211	35p
BC109	14p	BDY20	£1.20	OC16	90p
BC109c	16p	BF152	20p	OC19	85p
BC113	13p	BF166	30p	OC22	55p
BC114	13p	BF178	35p	OC26	65p
BC115	15p	BF180	35p	OC28	60p
BC116	15p	BF194	16p	OC35	60p
BC117	20p	BF195	16p	OC36	65p
BC118	15p	BF196	16p	OC42	40p
BC119	30p	BF197	16p	OC44	20p
BC143	25p	BF200	35p	OC45	25p
BC147	12p	BF224	18p	OC70	15p
BC148	12p	BF243	18p	OC71	12p
BC149	12p	BF245	45p	OC72	20p
BC149c	14p	BF259	55p	OC75	25p
BC157	14p	BFX29	30p	OC76	25p
BC158	14p	BFX34	30p	OC77	40p
BC159	15p	BFX35	30p	OC78	25p
BC167	14p	BFX36	30p	OC83	25p
BC168	14p	BFX38	30p	OC84	25p
BC169	14p	BFY10	35p	OC139	30p
BC179c	15p	BFY44	50p	OC170	25p
BC192	13p	BFY50	25p	OC171	30p
BC192	12p	BFY51	25p	OC200	60p
BC192L	12p	BFY52	25p	OC201	60p
BC183	12p	BFY53	25p	OC202	75p
BC183L	12p	BFY90	65p	TIP29A	45p
BC184	12p	BSV68	70p	TIP30	55p
BC184L	12p	BSW63	65p	TIP31A	57p
BC185	35p	BSW68	80p	TIP32A	69p
BC186	27p	BSX19	15p	TIP33A	£1.00
BC192	12p	BSX20	15p	TIP34A	£1.40
BC212L	14p	BSX21	25p	TIP35A	£3.20
BC213	12p	BY127	20p	TIP36A	£3.50
BC213L	12p	BY164	65p	TIP41A	70p

QTY DISCOUNTS 12+10%, 25+15%, 100+20%

TTL (full stocks available)

SN7400	18p	SN7411	23p	SN7430	20p
SN7401	18p	SN7412	22p	SN7432	42p
SN7402	20p	SN7413	40p	SN7433	70p
SN7403	20p	SN7414	30p	SN7434	50p
SN7404	20p	SN7417	30p	SN7438	50p
SN7405	20p	SN7420	20p	SN7440	20p
SN7406	30p	SN7422	38p	SN7441AN	75p
SN7407	30p	SN7423	38p	SN7442	75p
SN7408	20p	SN7425	38p	SN7443	£1.00
SN7409	40p	SN7427	42p	SN7445	£1.70
SN7410	18p	SN7428	50p	SN7446	£2.00

TIP42A	85p	2N2306	70p
TIP29B	54p	2N2369A	50p
TIP30B	60p	2N2477	30p
TIP31B	65p	2N2646	50p
TIP32B	77p	2N2846	£1.50
TIP35B	£1.06	2N4904	25p
TIP36B	£3.50	2N2905	30p
TIP41B	70p	2N2906	25p
TIP42B	95p	2N2907	25p
TIP29C	68p	2N2926	13p
TIP30C	72p	2N3053	25p
TIP31C	80p	2N3055	50p
TIP32C	£1.00	2N3232	£1.35
TIP33C	£1.20	2N3553	£1.40
TIP34C	£1.80	2N3643	30p
TIP35C	£3.00	2N3702	12p
TIP36C	£3.74	2N3703	12p
TIP37C	£4.00	2N3705	12p
TIP38C	£4.00	2N3707	12p
TIP39C	£4.00	2N3708	14p
TIP40C	£4.00	2N3709	14p
TIP41C	£4.00	2N3711	£1.50
TIP42C	£1.00	2N3772	£1.60
TIP43C	£1.00	2N3792	£1.80
TIP44C	£1.00	2N3794	30p
TIP45C	£1.00	2N3819	35p
TIP46C	£1.00	2N3820	55p
TIP47C	£1.00	2N3823	70p
TIP48C	£1.00	2N3866	85p
TIP49C	£1.00	2N3904	22p
TIP50C	£1.00	2N3905	25p
TIP51C	£1.00	2N3906	25p
TIP52C	£1.00	2N4014	80p
TIP53C	£1.00	2N4035	62p
TIP54C	£1.00	2N4037	42p
TIP55C	£1.00	2N4058	14p
TIP56C	£1.00	2N4059	14p
TIP57C	£1.00	2N4060	12p
TIP58C	£1.00	2N4061	12p
TIP59C	£1.00	2N4062	12p
TIP60C	£1.00	2N4126	18p
TIP61C	£1.00	2N4286	25p
TIP62C	£1.00	2N4287	25p
TIP63C	£1.00	2N4288	27p
TIP64C	£1.00	2N4289	30p
TIP65C	£1.00	2N4290	25p
TIP66C	£1.00	2N4291	32p
TIP67C	£1.00	2N4302	45p
TIP68C	£1.00	2N4444	£1.90
TIP69C	£1.00	2N4871	35p
TIP70C	£1.00	2N4903	£1.30
TIP71C	£1.00	2N4919	90p
TIP72C	£1.00	2N5069	£1.30
TIP73C	£1.00	2N5191	96p
TIP74C	£1.00	2N5192	£1.20
TIP75C	£1.00	2N5194	£1.10
TIP76C	£1.00	2N5195	£1.40
TIP77C	£1.00	2N5245	45p
TIP78C	£1.00	2N5296	55p
TIP79C	£1.00	2N5298	50p
TIP80C	£1.00	2N5457	35p
TIP81C	£1.00	2N5458	35p
TIP82C	£1.00	2N5459	40p
TIP83C	£1.00	2N5485	55p
TIP84C	£1.00	2N5490	55p
TIP85C	£1.00	2N5555	65p
TIP86C	£1.00	2N5777	40p

S.C.R.s

CRS1/05	40p
CRS1/10	56p
CRS1/20	60p
CRS1/40	65p
CRS1/60	90p
CRS3/10	62p
CRS3/20	62p
CRS3/40	90p
CRS7/400	£1.00
CRS16/100	85p
CRS16/200	90p
CRS16/600	£1.60
C106B	45p
C106D	70p
40569	90p
TIC44	35p
2N4444	£1.90
BT10/500A	90p

BRIDGE RECTIFIERS

W02 1A 200V	38p
BY164 1.4A 200V	57p
MDA952/2 6A 100V	80p

ZENER DIODES

BZ98 Series	400mW
3.3V 33% 5%	11p
1.5W range	25p
10W range	45p

L.E.D.

TIL 209	38p
HP5082	28p
MA2082R	20p

L.D.R.

ORP12	60p
NE555 Timer	80p

TRIACS

TLX2288 400V	85p
SC400	£1.40
SC40E	£1.65
SC45D	£1.70
SC45E	£2.10
SC50D	£2.42
SC50E	£2.70
DIAC	25p

LINEAR I.C.s

LM304 Neg Voltage Reg	£2.10
LM309K 5V 1A Voltage Reg	£2.10
LM723C 2.37V 150mA Voltage Reg	75p
MFC4000 250mW Audio	75p
TBA800 5 Watt Audio	99p
709C Op Amp	15p
D.I.L./1099	8/14
741C Op Amp	35p
D.I.L./1099 Op Amp	£1.20
748C Op Amp	75p
D.I.L.	75p
ZN414 Radio I.C.	£1.25

TAD100 Radio I.C. inc Filter

CA3010	£1.90
CA3018	£1.00
CA3029	£1.20
CA3036	£1.00
CA3046	95p
CA3048	£2.35
CA3075	£1.60
CA3089E	£1.90
CA3090U	£4.85
MC1303L	£2.20
MC1310P	£2.80
SN7660EO	£2.80
TBA120	65p

TO3 VOLTAGE REGULATORS

L005 5V 650mA	£1.60 ea.
L036 12V 600mA	
L037 15V 450mA	

VEROBOARD

17 x 2 1/2"	0.1	0.15
17 x 3"	£1.18	89p
17 x 5"	£1.66	£1.30
72p	£2.10	
PIN INS TOOL	72p	72p
SP. F. CUTTER	65p	65p
100 PINS SS	40p	40p
100 PINS DS	40p	40p
2 1/2 x 3 1/4"	32p	32p
2 1/2 x 5"	35p	35p
3 1/4 x 5"	40p	41p
PIN INS TOOL	72p	72p
500 PINS SS	£1.55	£1.55
500 PINS DS	£1.55	£1.55

POTENTIOMETERS

Linear or Log	Single	Double
Rotary Pos	17p	45p
Rotary Switched	25p	—

METAL BOXES

ALUMINIUM BOXES IDEAL FOR VEROBOARD WITH BASE & P.K. SCREWS

AB7	2 3/4" Long	5 1/4" Wide	1 1/2" High	55p
AB8	4"	4"	1 1/2"	55p
AB9	4"	2 3/4"	1 1/2"	55p
AB10	4"	5 1/4"	1 1/2"	55p
AB11	4"	2"	2"	65p
AB12	3"	2"	1"	50p
AB13	6"	4"	2"	77p
AB14	7"	5"	2 1/2"	90p
AB15	8"	6"	3"	£1.16
AB16	10"	7"	3"	£1.32
AB17	10"	4 1/2"	3"	£1.10
AB18	12"	5"	3"	£1.32
AB19	12"	8"	3"	£1.80

ALUMINIUM BOXES WITH SLOPING TOP PANEL — IDEAL FOR PRE-AMPS, ETC., USING SLIDER CONTROLS

AB20	8" Long 9" Wide 3 1/2" High at back 2" High at front 6" Slope to front	£2.20
AB21	As above but 10" long	£2.20
AB22	As above but 12" long	£2.60

HIGH PERFORMANCE MODERN SCOPE TUBES

By Telefunken Limited, qty only 5" rectangular display Type No D14/131 Price £25.00 each + VAT 8%. All extras provided free whilst remaining in stock. Postage £1.00. All brand new

REXINE COVERED ALUMINIUM CASES WITH SCREWS & FEET

RBI 6" x 4" x 1 3/4"	£1.05
RB2 8" x 5" x 2"	£1.20
RB3 9" x 5" x 2 1/2"	£1.35
RB4 11"	

P. F. RALFE

10 CHAPEL ST. LONDON NW1.

Phone 01-723 8753

SIGNAL GENERATORS

MARCONI TF801D/1S. 10-480 mHz P.O.A.
MARCONI TF801B/2S. 10-480 mHz £225.
HGN MS3/U. 9.7-11.9 and 77-109 mHz. AM/FM.
ADVANCE SG63D. AM/FM 7.5-230mHz £125.
RACAL/AIRMEC 201A. 30kHz-30mHz. As new. P.O.A.
ADVANCE SG21 VHF Square-wave generator 9kHz-100mHz. £25.



OSCILLOSCOPES

SOLARTRON CD1400 DC-15mHz.
COSSOR CDU110. DC-80mHz.
TEKTRONIX 545A with CA unit. DC-30mHz. Price only £295.00
TEKTRONIX 531 DC-15mHz with L type plug-in
TEKTRONIX 535 DC-15mHz with L type plug-in
TEKTRONIX 545B DC-30mHz with 'CA' plug-in.
TEKTRONIX 585A. DC-80mHz with type 82 plug-in.
TEKTRONIX 654B. Storage oscilloscope.
TEKTRONIX 502. 200uV Sens. X-Y.
TEKTRONIX C27 Polaroid Camera. Series 125 with 560 series adapter.



MANY TYPES of RF plugs and sockets in stock:—

BNC plugs 50Ω. 30p. BNC sockets 50Ω. 25p. N. Type plugs 50Ω. 20p. Burndept plugs. 40p. Burndept sockets. 40p. Miniature PYE. 20p. Miniature sockets. 20p.

All connectors are brand new. Immediate delivery. Please add appropriate postage.

'MUFFIN' INSTRUMENT FANS.

Manufactured in Holland by Rotron Dims 4.5x4.5x1.5 ins This is a precision cooling fan, very quiet running specially designed for the cooling of electronic equipment, amplifiers, etc 115V 50Hz operation, drawing only 11 Watts The list price from Rotrons is over £10 each. Our price, brand new, only £4.50 each

MINIATURE DEAC NI-CADMIUM batteries, type 70DK 3 cells in package making 3.7 Volts. 25x17x15mm only 75p post paid

E.M.I. oscilloscopes type RMO15 Response to 40mHz 5 inch CRT 10KV E H T We can offer these quality oscilloscopes at the exceptional price of only £35 each to callers only

ADVANCE type 63A AM/FM R.F. Signal generators 7.5-230mHz Deviation 0-2.2 5 and 0-75 kHz X-sweep output. Crystal calibrator, scope output. £75.00.

MISCELLANEOUS TEST EQUIPMENT

MARCONI TF1400S double pulse generator with TM6600/S secondary pulse unit. £105.
MARCONI TF791D deviation meter, 4-1024mHz. 0-100kHz deviation
MARCONI 455E Wave Analyser £120.
MARCONI TF2600 Valve Voltmeter 1mV-300V Excellent £75.
ROHDE & SCHWARZ USVD calibrated receiver 280-940mHz (4600mHz)
LEVELL TG200 DM. RC Oscillator, c/w case. £65.
ROHDE & SCHWARZ URV milli-voltmeter BN10913 (late type) 1mV-10V. With 'T' type insertion unit, free probe and attenuator heads. 1kHz-1,600mHz £175.
COSSOR 1453 True RMS milli-voltmeter. Excellent. £75.
AIRMEC TYPE 210 modulation meter. Excellent condition.
ROHDE & SCHWARZ 'SCR' V.H.F. Signal Generator 1000-1900 mHz.
MARCONI type TF936 Impedance Bridge. £85.00.
GERTCH Phase Angle V. Meters. Range 1mV-300V. in 12 ranges.
SOLARTRON oscillator type CO 546. 25Hz-500kHz. £30.00.
GAMBRELL Precision 4 Decade Resistance Box. 1-11, 110 ohms £24.50.

PLEASE ADD 8% V.A.T. TO THE TOTAL AMOUNT WHEN ORDERING. INCORRECT AMOUNTS WILL CAUSE DELAY IN DESPATCH. THANK YOU.

MARCONI TF995A2/M AM/FM R.F. SIGNAL GENERATORS. 1.5-220mHz. 0-100kHz Deviation. 1μV—100mV output. Sold in excellent condition. P.O.A.

METRIX 210 WOBBLATORS. 0-25mHz Sweep width 0.5 - 20mHz Output 100mV attenuable in steps of 10 to 10uV Last few of these left at only £15.00 each to callers only

E.M.I. oscilloscopes model WM16 with type 7/1 W.B.A. plug-in unit Supplied in perfect condition complete with trolley £125.00.

20-way BPO Jack strips to accept 316 type Jack plugs. Also quantity of 316 plugs available. All good condition.

Centrifugal blowers by WOODS 8 inch snail type Outlet 2 1/4 x 2 in. 24V DC 2.8A 2400 r.p.m. Grey stove finish All brand new Price is £10.50 + carriage.

GENTS/FRIEDLAND fire alarm bells Operating voltages 12v dc/24v dc All in as new condition and tested before despatch Sizes 6/8/12 inch Prices £4.80, £5.20 and £6.50 resp

COMPUTER PERIPHERALS. Tape punches, 8 hole by Westec and other well known manufacturers Tape readers by Elliot All virtually brand new Prices are better than one half the maker's. Write or phone for quotation

An exceptional buy enables us to offer stabilised and regulated power supplies by APT at a very cheap price 16-24v dc @ 10 Amps, and 8-10v dc @ A Both supplies are extremely stable with low ripple voltage Price each £18.50 + carriage

SQ IS A TRADEMARK OF CBS INC.

NEW
LOW
PRICES!

SQ QUADRAPHONIC DECODERS

SQ the leading quadraphonic system designed by CBS engineers, offers not only 4 channel ambiphony from the fast expanding range of SQ encoded discs but also immensely increased depth and fullness of sound from standard stereo recordings too.
 Feed 2 channels (200-1000mV as obtainable from most pre amplifiers) into your choice of any of our 3 decoders and take 4 channels out with no overall signal level reduction. On the logic enhanced decoders Volume Front Back LF-RF LB-RB and Dimension controls can all be implemented by simple single gang potentiometers - no need for exotic 4 gang units!
 These state of the art circuits used under licence from CBS are offered in kit form comprising first grade components only—fibre glass circuit boards of professional quality designed for edge connector insertion all resistors 2% metal oxide all polystyrene and polycarbonate capacitors 5% or better and in decoder L2 ultra low noise (MPS A18 0.5dB typ) transistors used in each amplifying stage.
 M1 Basic matrix decoder with fixed 10 40 blend 10 Resistors 14 Capacitors 1 Integrated Circuit Printed Circuit Board £5.90.
 L1 Full logic controlled decoder with wave matching and front back logic for enhanced channel separation using three specially designed Integrated Circuits 24 Resistors 42 Capacitors 3 Integrated Circuits Printed Circuit Board £17.20.
 L2 More advanced full logic decoder with variable blend extended frequency response increased front back separation 43 Resistors 44 Capacitors 3 Integrated Circuits 9 Transistors 6 Diodes Printed Circuit Board £24.60.
 All kits include IC sockets and construction notes. Prices include CBS licence fee.
 Please write for further details in FREE LIST.
 United Kingdom Post Free Please add 25% VAT Overseas No VAT Please add (per kit) £2 00 p & p AIR MAIL or £1 00 p & p SURFACE MAIL

AMBIENTACOUSTICS

PO BOX 3000
ANDOVER, HANTS SP10 3LQ

WW—032 FOR FURTHER DETAILS

SOUND INSTALLATIONS

Design, installation and commissioning of recording and broadcast studios, sound reinforcement equipment, theatre communication and other systems

SOUND EQUIPMENT

Supply and, where required, manufacture of equipment to customers specifications

We also specialise in television lighting and other systems

PHILIP DRAKE ELECTRONICS LTD.

165 LANCASTER ROAD, NEW BARNET, HERTS.

Telephone: 01-445 1144

WW—060 FOR FURTHER DETAILS

FREE Brochure on New KITS

Whether professional, student, teacher or amateur, the field of electronics can open up a new world for you.

CROFTON don't just sell kits, we offer you a technical back up service to ensure your success

The following is a selection of some of the more popular kits -

- ★ Mullard CCTV Camera
- ★ PE CCTV Camera
- ★ PE Rovin Quadraphonic Four Channel Sound (Designer Approved)
- ★ Wireless amplifier
- ★ Sound Operated Flash
- ★ P.W. Tele Tennis Game
- ★ UHF Modulation
- ★ Bench Power Supply
- ★ Wireless
- ★ All E.T. Top Projects
- ★ Many of the E.ektor Projects

NOTE: PCBs for most published projects available to order

CROFTON ELECTRONICS LTD

Dept.D, 124, Colne Road, Twickenham, Middx. 01-898 1569

WW—035 FOR FURTHER DETAILS

BENTLEY ACOUSTIC CORPORATION LTD.

7A GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX. Tel. 6743
ALL PRICES SHOWN INCLUDE V.A.T.

0B2 0.45	68C8 0.90	6L12 0.47	12BA6 0.53	30P4 0.88	AZ31 0.60	EC53 1.00	EL84 0.36	PC95 0.70	PY88 0.47	U18/20 1.17	2N404 0.23	AF186 0.71	GD11 0.26	OC45 0.14
A24 0.55	68E6 0.41	6L18 0.64	12BE8 0.50	30P16 0.43	AZ41 0.50	EC54 1.00	EL96 0.60	PC97 0.42	PY301 0.59	U19 4.00	2N1966 0.88	AF277 0.55	GD12 0.26	OC46 0.20
IA3 0.65	68G6 1.23	6L19 2.00	12BH7 0.59	30P18 0.50	BL63 2.34	EC58 0.90	EL90 0.53	PC90 0.30	PY500A 1.11	U25 0.70	2N1217 1.10	AY28 0.42	GD14 0.64	OC65 1.45
IA5GT 0.59	68H6 0.75	6L22 0.45	12BY7 0.85	30P11 1.00	CL33 1.85	EC82 0.90	EL95 0.70	PC94 0.50	PY800 0.45	U26 0.65	2N2927 0.28	AS29 0.64	GD16 0.26	OC71 0.14
IA7GT 0.80	68J6 0.64	6L20 0.88	12C17 0.50	30P12 0.45	CV6 0.82	EC88 0.55	EL98 0.50	PC98 0.50	PY801 0.45	U31 1.75	2N3613 0.50	BA115 0.23	GD18 0.26	OC72 0.14
IB3GT 0.58	68K7 0.85	6N7GT 0.70	12J5GT 0.39	30P13 1.20	CV83 1.00	EC33 2.00	EL99 0.50	PC99 0.50	PY230 0.50	U33 1.75	2N2953 0.42	BA116 0.23	GD19 0.26	OC73 0.29
IC2 1.15	68Q5 0.36	6L42 0.45	12J7GT 0.70	30P14 1.20	CV86 0.28	EC32 2.00	EL99 0.50	PC99 0.50	PY211 1.10	U35 1.75	2N3613 0.42	BA117 0.23	GD20 0.26	OC74 0.29
IG6 1.17	68Q7A 0.64	6P15 0.36	12K5 1.17	30P15 0.90	CY1C 1.00	EC35 2.00	EL99 0.50	PC99 0.50	PY212 1.10	U37 2.80	2N3703 0.25	BA130 0.23	GD21 0.26	OC75 0.14
IHSGT 0.80	68R7 1.20	6Q7G 0.56	12K7GT 0.50	35A3 0.76	CY31 0.70	EC39 1.00	EL99 0.50	PC99 0.50	PY213 1.10	U40 0.65	2N3866 1.29	BCY10 0.59	GD22 0.26	OC76 0.20
IL4 0.25	68R8 1.24	6Q7GT 0.60	12K8 0.85	35C5 0.59	D1 0.50	EC39 1.00	EL99 0.50	PC99 0.50	PY214 1.10	U41 0.65	2N3866 1.29	BCY11 0.59	GD23 0.26	OC77 0.20
ILD5 0.70	68S7 1.64	6Q7M 0.64	12K9GT 0.50	35D5 0.90	D63 0.30	EC40 1.20	EL99 0.50	PC99 0.50	PY215 1.10	U42 0.65	2N3866 1.29	BCY12 0.64	GD24 0.26	OC78 0.20
ILN5 0.70	68W6 1.00	6R7G 0.70	12S2AGT 0.50	35L6GT 0.88	DAC32 0.90	EC40 1.20	EL99 0.50	PC99 0.50	PY216 1.10	U43 0.65	2N3866 1.29	BCY13 0.64	GD25 0.26	OC79 0.20
INSGT 0.76	68W7 0.85	6R7M 0.88	12S2AGT 0.50	35W4 0.60	DAF91 0.40	EC40 1.20	EL99 0.50	PC99 0.50	PY217 1.10	U44 0.65	2N3866 1.29	BCY14 0.64	GD26 0.26	OC80 0.20
IR5 0.50	68X6 0.30	6SA7 0.55	12S2GT 0.70	35Z3 0.88	DAF96 0.60	EC40 1.20	EL99 0.50	PC99 0.50	PY218 1.10	U45 0.65	2N3866 1.29	BCY15 0.64	GD27 0.26	OC81 0.20
IS4 0.39	68Y7 0.40	6S7GT 0.50	12S2GT 0.70	35Z4GT 0.82	OC90 0.70	EC40 1.20	EL99 0.50	PC99 0.50	PY219 1.10	U46 0.65	2N3866 1.29	BCY16 0.64	GD28 0.26	OC82 0.20
IS5 0.40	68Z6 0.57	6S7 0.52	12S2GT 0.70	35Z5GT 0.90	DD4 0.80	EC40 1.20	EL99 0.50	PC99 0.50	PY220 1.10	U47 0.65	2N3866 1.29	BCY17 0.64	GD29 0.26	OC83 0.20
IU4 0.30	6C4 0.47	6S7 0.52	12S2GT 0.70	42 1.00	DF3 0.76	EC40 1.20	EL99 0.50	PC99 0.50	PY221 1.10	U48 0.65	2N3866 1.29	BCY18 0.64	GD30 0.26	OC84 0.20
IUS 0.88	6C5 0.47	6S7 0.52	12S2GT 0.70	50B5 1.00	DF3 0.30	EC40 1.20	EL99 0.50	PC99 0.50	PY222 1.10	U49 0.65	2N3866 1.29	BCY19 0.64	GD31 0.26	OC85 0.20
2D21 0.80	6C9 2.00	6S7GT 0.50	12S2GT 0.70	50C5 0.70	DF36 0.65	EC40 1.20	EL99 0.50	PC99 0.50	PY223 1.10	U50 0.65	2N3866 1.29	BCY20 0.64	GD32 0.26	OC86 0.20
2DK5 0.75	6C10 0.60	6U4GT 0.82	12S2GT 0.70	50C5D6G 1.46	DH63 0.50	EC40 1.20	EL99 0.50	PC99 0.50	PY224 1.10	U51 0.65	2N3866 1.29	BCY21 0.64	GD33 0.26	OC87 0.20
2X2 0.70	6C86A 0.47	6U7G 0.55	12S2GT 0.70	50E1H5 0.88	DH77 0.53	EC40 1.20	EL99 0.50	PC99 0.50	PY225 1.10	U52 0.65	2N3866 1.29	BCY22 0.64	GD34 0.26	OC88 0.20
3A4 0.60	6C12 0.40	6V6G 0.30	12S2GT 0.70	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY226 1.10	U53 0.65	2N3866 1.29	BCY23 0.64	GD35 0.26	OC89 0.20
3B7 0.53	6C17 2.34	6V6GT 0.53	12S2GT 0.70	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY227 1.10	U54 0.65	2N3866 1.29	BCY24 0.64	GD36 0.26	OC90 0.20
3DE 0.47	6C24 1.17	7B7 0.82	12S2GT 0.70	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY228 1.10	U55 0.65	2N3866 1.29	BCY25 0.64	GD37 0.26	OC91 0.20
3Q4 0.85	6C88A 0.88	6X5GT 0.50	1447 1.10	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY229 1.10	U56 0.65	2N3866 1.29	BCY26 0.64	GD38 0.26	OC92 0.20
3Q5GT 0.70	6C16 0.76	6Y6G 0.94	18 1.17	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY230 1.10	U57 0.65	2N3866 1.29	BCY27 0.64	GD39 0.26	OC93 0.20
3S4 0.47	6C18A 0.94	7A7G 1.17	19A05 0.85	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY231 1.10	U58 0.65	2N3866 1.29	BCY28 0.64	GD40 0.26	OC94 0.20
3V4 0.82	6C7M 0.88	7A7 1.00	19B9G 1.17	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY232 1.10	U59 0.65	2N3866 1.29	BCY29 0.64	GD41 0.26	OC95 0.20
4C86 0.75	6C05 0.88	7B6 0.38	19G6 7.00	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY233 1.10	U60 0.65	2N3866 1.29	BCY30 0.64	GD42 0.26	OC96 0.20
5C98 0.75	6C94 1.17	7B7 0.82	19H1 4.00	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY234 1.10	U61 0.65	2N3866 1.29	BCY31 0.64	GD43 0.26	OC97 0.20
5R4CY 0.84	6D3 0.75	7D6 2.00	20D1 4.00	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY235 1.10	U62 0.65	2N3866 1.29	BCY32 0.64	GD44 0.26	OC98 0.20
5T4 0.47	6E7 0.88	7F8 1.00	20D4 2.34	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY236 1.10	U63 0.65	2N3866 1.29	BCY33 0.64	GD45 0.26	OC99 0.20
5U4G 0.50	6D78A 0.88	7H7 0.88	20F2 3.00	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY237 1.10	U64 0.65	2N3866 1.29	BCY34 0.64	GD46 0.26	OC100 0.20
5V4G 0.50	6E6 0.88	7H7 2.00	20P1 1.29	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY238 1.10	U65 0.65	2N3866 1.29	BCY35 0.64	GD47 0.26	OC101 0.20
5Y3GT 0.55	6E5 1.17	7T7 1.76	20P1 1.00	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY239 1.10	U66 0.65	2N3866 1.29	BCY36 0.64	GD48 0.26	OC102 0.20
5Z3 0.88	6F1 0.80	7Y4 1.90	20P1 1.00	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY240 1.10	U67 0.65	2N3866 1.29	BCY37 0.64	GD49 0.26	OC103 0.20
5Z4G 0.55	6F6G 0.60	7Z4 0.90	20P4 1.17	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY241 1.10	U68 0.65	2N3866 1.29	BCY38 0.64	GD50 0.26	OC104 0.20
5Z4GT 0.55	6F12 0.50	9D7W6 0.88	20P5 1.50	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY242 1.10	U69 0.65	2N3866 1.29	BCY39 0.64	GD51 0.26	OC105 0.20
6/30L2 0.80	6F13 0.90	9D7 0.70	25A6G 0.70	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY243 1.10	U70 0.65	2N3866 1.29	BCY40 0.64	GD52 0.26	OC106 0.20
6A8G 1.46	6F14 0.88	10D2 0.82	25L6G 0.70	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY244 1.10	U71 0.65	2N3866 1.29	BCY41 0.64	GD53 0.26	OC107 0.20
6AC7 0.60	6F15 0.76	10D1 0.82	25V5 0.80	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY245 1.10	U72 0.65	2N3866 1.29	BCY42 0.64	GD54 0.26	OC108 0.20
6AG5 0.35	6F18 0.84	10E1 0.85	25Y5G 0.80	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY246 1.10	U73 0.65	2N3866 1.29	BCY43 0.64	GD55 0.26	OC109 0.20
6AH8 0.80	6F20 0.80	10F1 0.85	25Y5G 0.80	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY247 1.10	U74 0.65	2N3866 1.29	BCY44 0.64	GD56 0.26	OC110 0.20
6AJ5 0.76	6F24 1.00	10F3 1.17	25Z5 0.75	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY248 1.10	U75 0.65	2N3866 1.29	BCY45 0.64	GD57 0.26	OC111 0.20
6AJ8 0.40	6F25 1.17	10F9 0.78	25Z6G 0.80	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY249 1.10	U76 0.65	2N3866 1.29	BCY46 0.64	GD58 0.26	OC112 0.20
6AK5 0.47	6F26 0.40	10F8 0.60	28D7 2.00	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY250 1.10	U77 0.65	2N3866 1.29	BCY47 0.64	GD59 0.26	OC113 0.20
6AK6 0.70	6F28 0.78	10L14 0.53	30A1 0.47	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY251 1.10	U78 0.65	2N3866 1.29	BCY48 0.64	GD60 0.26	OC114 0.20
6AK8 0.45	6F32 0.70	10L11 0.53	30C5 0.47	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY252 1.10	U79 0.65	2N3866 1.29	BCY49 0.64	GD61 0.26	OC115 0.20
6AL5 0.23	6G6G 0.60	10P12 0.45	30C15 0.80	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY253 1.10	U80 0.65	2N3866 1.29	BCY50 0.64	GD62 0.26	OC116 0.20
6AM8A 0.80	6G8 0.88	10P13 0.88	30C17 0.85	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY254 1.10	U81 0.65	2N3866 1.29	BCY51 0.64	GD63 0.26	OC117 0.20
6AN8 0.82	6GK5 0.76	10P14 2.34	30C18 0.85	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY255 1.10	U82 0.65	2N3866 1.29	BCY52 0.64	GD64 0.26	OC118 0.20
6AQ5 0.53	6G07 0.88	10P18 0.49	30F5 0.75	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY256 1.10	U83 0.65	2N3866 1.29	BCY53 0.64	GD65 0.26	OC119 0.20
6AQ8 0.47	6H6GT 0.29	12A6 0.75	30FL1 1.10	50L6GT 1.00	DH81 0.77	EC40 1.20	EL99 0.50	PC99 0.50	PY257 1.10	U84 0.65	2N3866 1.29	BCY54 0.64	GD66 0.26	OC120 0.20
6AR5 0.80	6J5GT 0.53	12AC6 0.90	30FL2 1.10	50L6GT 1.00	DH81 0.77	EC40 1.20</								

TTLs by TEXAS 7400 13p 7482 70p 7401 14p 7483 80p 7402 14p 7484 95p 7403 16p 7485 120p 7404 16p 7486 30p 7405 16p 7489 270p 7406 38p 7490 40p 7407 38p 7491 75p 7408 16p 7492 45p 7409 20p 7493 40p 7410 13p 7494 75p 7411 22p 7495 65p 7412 23p 7496 78p 7413 32p 74100 108p 7414 60p 74107 30p 7416 33p 74121 30p 7417 30p 74122 46p 7420 14p 74123 68p 7422 18p 74141 65p 7423 34p 74145 70p 7425 30p 74150 125p 7427 37p 74151 72p 7430 14p 74153 85p 7432 25p 74154 150p 7437 25p 74155 76p 7440 14p 74156 76p 7441 65p 74160 99p 7442 60p 74161 99p 7443 120p 74162 99p 7444 120p 74163 99p 7445 120p 74164 120p 7446 120p 74166 126p 7447 75p 74174 120p 7448 70p 74175 85p 7450 15p 74180 100p 7451 16p 74181 298p 7453 16p 74182 82p 7454 16p 74185 135p 7460 15p 74190 144p 7470 27p 74191 144p 7472 25p 74192 120p 7473 30p 74193 120p 7474 30p 74194 108p 7475 45p 74195 75p 7476 30p 74196 100p 7480 50p 74197 100p 7481 95p 74198 198p 74199 180p		C-MOS LOGIC I.C.s NEW LOW PRICES CD4000AE 19p CD4001AE 19p CD4002AE 19p CD4007AE 19p CD4009AE 67p CD4011AE 19p CD4012AE 19p CD4013AE 55p CD4016AE 50p CD4017AE 120p CD4018AE 175p CD4020AE 250p CD4022AE 170p CD4023AE 19p CD4024AE 120p CD4025AE 19p CD4026AE 196p CD4027AE 75p CD4028AE 140p CD4029AE 175p CD4030AE 55p CD4042AE 137p CD4043AE 202p CD4046AE 140p CD4047AE 154p CD4049AE 63p CD4054AE 196p CD4055AE 135p CD4060AE 229p CD4069AE 37p CD4071AE 27p CD4072AE 27p CD4081AE 19p CD4082AE 27p CD4510AE 130p CD4511AE 200p CD4518AE 100p CD4528AE 120p		OP. AMPS 1458 Dual Op. Amp. Int. Comp. 8 pin DIL 70p 301A Ext. Comp. 8 pin DIL 36p 3130 COSMOS/Bi-Polar MosFet 8 pin DIL 100p 3900 Quad. Op. Amp. 14 pin DIL 70p 536T FET Op. Amp. TO-99 275p 709 Ext. Comp. 8/14 pin DIL 30p 741 Int. Comp. 8/14 pin DIL 22p 747 Dual 741 14 pin DIL 70p 748 Ext. Comp. 8/14 pin DIL 36p 776 Programmable Op. Amp. TO-5 140p		TRANSISTORS *BU105 140p BU108 250p *MJE340 45p MJE2955 99p MJE3055 65p *MPSA06 30p *MPSA12 50p *MPSA56 32p *MPSU06 62p *MPSU56 78p OC28 65p OC35 55p OC36 60p *OC41/2 15p *OC45 15p *OC71 20p *TIP29A 40p *TIP30A 48p TIP31A 52p TIP32A 58p *TIP33A 90p TIP34A 115p TIP35A 225p TIP36A 270p TIP41A 65p TIP42A 70p TIP2955 70p *TX108 10p *TX300 13p *TX500 15p *TX502 18p 2N697 13p 2N698 30p 2N706 12p 2N708 18p 2N918 40p 2N928 20p 2N930 18p 2N1131 18p 2N1132 18p 2N1304 21p 2N1305 21p 2N1306 28p 2N1307 28p 2N1308 28p 2N1309 28p 2N1613 20p 2N1711 20p 2N1893 30p 2N2218 21p 2N2219 20p 2N2220 19p 2N2221 20p 2N2222 20p 2N2369 14p 2N2484 30p 2N2904 20p 2N2905 20p 2N2906 20p *2N2926B 7p *2N2926B 7p *2N2926B 8p *2N2926Y 9p *2N2926G 9p 2N3053 18p 2N3054 45p 2N3055 50p 2N3439 67p 2N3442 140p *2N3702 11p *2N3703 11p *2N3704 11p *2N3705 11p *2N3706 10p *2N3707 11p *2N3708 9p *2N3709 9p 2N3773 220p 2N3866 90p *2N3903 18p *2N3904 20p *2N3905 18p *2N3906 20p *2N4058 15p *2N4059 10p *2N4060 13p		ZENER 3.3V to 33V* *400mW 9p *1W 18p TUNNEL AEY11 70p VARICAP *B8105 25p NOISE *Z5J 110p BRIDGE RECTIFIERS *25A100V20p *1A 50V 22p *1A 100V 22p *1A 400V 27p *1A 600V 30p *2A 50V 30p *2A 100V 35p *2A 400V 45p *4A 100V 60p 6A 50V 60p 6A 100V 65p TRIACS Amp Volts 3 400 120p 6 400 150p 6 500 180p 10 400 185p 10 500 195p 15 400 210p 15 500 250p 40A30 99p 40A86 99p 40A81 8p 40A85 10p 40A90 7p 40A91 7p 40A95 7p 40A200 8p 40A202 10p IN914 4p IN916 4p IN4148 9p SPECIAL OFFERS FOR JAN. & FEB. 555 £34 741 £18 (8 pin DIL MFC) } 4000B } £50 2N2926 } £4 (Red & Brown)									
PERIPHERAL DRIVERS by TEXAS (2 TTL Gates & 2 High Current Output Transistors on one chip) 75450 Positive-AND 14 pin DIL 120p 75451 Positive-AND 8 pin DIL 72p 75452 Positive-NAND 8 pin DIL 72p 75453 Positive-OR 8 pin DIL 72p 75454 Positive-NOR 8 pin DIL 72p Applications: Lamp, Relay, MOS, Line, Core, and Power Drivers -- and Logic buffers.		LINEAR I.C.s *CA3028 Diff. Cascade Amp TO5 90p *CA3046 5 Transistor Array 14 pin DIL 50p *CA3048 Quad Low Noise Amp 16 pin DIL 200p *CA3089E FM IF System 16 pin DIL 200p *CA3090E FM Stereo Multi. Dec. 16 pin DIL 150p *ICL8038CC VCO Fun. Gen. 14 pin DIL 275p *LM380 2W Audio Amp 14 pin DIL 90p *LM381 Stereo Preamp 14 pin DIL 160p *M252 Rhythm Generator 16 pin DIL 900p *MC1310P FM Stereo Dec. 14 pin DIL 175p *MC1312 SQ Quad Dec. 14 pin DIL 950p *MC1314 Bal. Mod/Demod. 16 pin DIL 100p *MC1315 1/4W Audio Amp PCB 70p *MFC4000B Electronic Attenuator PCB 90p MFC6040 Timer 8 pin DIL 40p NE555 Dual 555 14 pin DIL 100p NE561 PLL with AM Demod. 16 pin DIL 325p NE562 PLL with VCO 16 pin DIL 325p NE565 PLL 14 pin DIL 200p NE566 PLL Fun. Gen. 8 pin DIL 150p NE567 PLL Tone Dec. 8 pin DIL 200p 2567 Dual 567 14 pin DIL 120p *SN7273Z Pwr Aud Amp with int HS 14 pin DIL 370p *SN76013N Pwr Aud Amp with int HS 14 pin DIL 370p *SN76023 Pwr Aud Amp with int HS 14 pin DIL 370p *TBA6418 Audio Amp 14 pin DIL 250p *TBA800 5W Audio Amp QIL 90p *TBA810 7W Audio Amp QIL 100p *TBA820 2W Audio Amp QIL 80p KR2240 Prog. Timer/Counter 16 pin DIL 370p *ZN414 TRF Radio Receiver TO-18 110p		OPTO-ELECTRONICS Phototransistors L D Rs 40p OCP70 30p ORP12 50p OCP71 120p ORP60 75p 2N5777 40p ORP61 75p LEDS TIL209 Red 14p TIL211 Green 30p Infrared Emitter TIL 32 75p.		SEVEN SEGMENT DISPLAYS 3015F Minitorn 0.3 in. 120p DL704 Com. Cathode 0.3 in. 150p DL707 Com. Anode 0.3 in. 150p DL747 Com. Anode 0.6 in. 222p		OPTO-ISOLATORS Phototransistor: TIL 112 (IL 12) 6 pin DIL 140p Photodarlington: ILC A-55 6 pin DIL 250p		DRIVERS 75491 Quad Segment Driver 14 pin DIL 72p 75492 Hex Digit Driver 14 pin DL 90p		SCR-THYRISTORS BT106 1A/700V Stud 140p C106D 1A/700V Plastic 55p 1A 50V TO5 40p 4A/400V Plastic 55p 1A100V TO5 42p MCR101 55p 1A400V TO5 52p 0.5A/15V TO-92 25p 1A600V TO5 70p 2N3525 25p 3A100V Stud 49p 5A/400V TO-66 90p 3A400V Stud 75p 2N4444 90p 7A100V TO5+HS 84p 8A/600V Plastic 185p 7A400V TO5+HS 90p *2N5060 185p 8A 50V Plastic 130p 0.8A/30V TO-92 34p 12A400V Plastic 160p *2N5062 34p 16A100V Plastic 160p 0.8A/100V TO-92 37p 16A400V Plastic 180p *2N5064 37p 16A600V Plastic 220p 0.8A/200V TO-92 40p		DIODES BF115 22p 2N2220 19p BF167 23p 2N2221 20p BF170 23p 2N2222 20p BF173 25p 2N2369 14p BF177 26p 2N2484 30p BF178 28p 2N2904 20p BF179 33p 2N2905 20p BF180 33p 2N2906 20p BF181 33p *2N2926B 7p BF182 33p *2N2926B 7p BF184 22p *2N2926B 8p BF185 22p *2N2926Y 9p *BF194 10p *2N2926G 9p *BF195 9p 2N3053 18p *BF196 14p 2N3054 45p *BF197 15p 2N3055 50p BF200 32p 2N3439 67p BF257 32p 2N3442 140p BF258 36p *2N3702 11p *BFR39 30p *2N3703 11p *BFR40 30p *2N3704 11p *BFR79 30p *2N3705 11p *BFR80 30p *2N3706 10p *BFR88 30p *2N3707 11p BFX30 30p *2N3708 9p BFX84 26p *2N3709 9p BFX85 25p 2N3773 220p BFX86 25p 2N3866 90p BFX87 20p *2N3903 18p BFX88 24p *2N3904 20p BFX50 16p *2N3905 18p BFX51 15p *2N3906 20p BFX52 16p *2N4058 15p BRY39 34p *2N4059 10p 8SX19 16p *2N4060 13p BSX20 18p		VAT RATES ALL ITEMS AT 8% EX-CEPT where marked * which are rated at 25%.	

Fully branded devices by Texas, RCA, Motorola, National, Mullard, etc. Minimum Order £2 P&P 20p. Please add VAT to total. Mail Order Only Govt. Colleges, etc. orders accepted. **TECHNOMATIC LTD.** 84 SANDHURST ROAD, LONDON, NW9 Tel: 01-204 4333

Illustrations in Applied Network Theory

F. E. Rogers

A hundred numerical and algebraic illustrations designed to exemplify practical circuit problems and introduce, in analysis, principles consistent with studies of synthesis that may be pursued later.

1973 240 pp., illustrated
 0 408 70425 X cased £5.75
 0 408 70426 8 limp £2.65

Obtainable through any bookseller

Newnes-Butterworths
 BOROUGH GREEN, SEVENOAKS
 KENT TN15 8PH
 Tel: BOROUGHS GREEN 884567

Audio Connectors

Broadcast pattern jackfields, jackcords, plugs and jacks.


Quick disconnect microphone connectors
 Amphenol (Tuchel) miniature connectors with coupling nut

Hirschmann Banana plugs and test probes
 XLR compatible in-line attenuators and reversers.

Low cost slider faders by Ruf

Future Film Developments Ltd.
 90 Wardour Street
 London W1V 3LE
 01-437 1892/3

WW-061 FOR FURTHER DETAILS

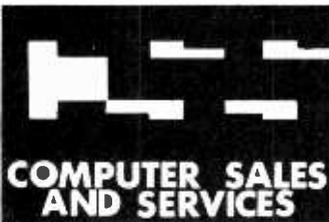

The SECOND-USER Computer Specialists

Peripherals and Systems for Data Processing
Systems, Equipment and Components

Mini-Computer Exchange

JUST ARRIVED — SUPERB PDP8M

- 16K Processor
- TU56 Dual DECTape
- SUN60 Dual DEC Cassette
- SINTRON Dual Floppy Disc
- LA30 DECWriter
- ASR33 Teletype
- RT02 Display

Less than a year old — a bargain at £7,500. On display now in our London showroom — callers welcome.

Just received — DEC DF32 Disk Drive with power supply and control for PDP8E. DEC maintained, first-class condition. Rack cabinet available if required.

Also available PDP11/15 4K Processor, PDP8L BK Processor, PCB1 Reader Punch and Control, RK05 Disk Drives

Ring now for prices. Other models becoming available all the time — let us know your requirements.

TERMINALS — SPECIAL CLEARANCE OFFER: COSBOR DIDS 402.2 VISUAL DISPLAY UNITS. Full 64-character ASCII Keyboard Display area 8" x 4 1/2" (13 lines of 40 ch.). Data Transfer rate 120 cps. PRICE: £100.00

Add 8% VAT to all prices shown. Carriage extra — details on request.

Callers welcome — Monday to Friday 9 a.m. to 5 p.m.

COMPUTER SALES & SERVICES (EQUIPMENT) LIMITED
49/53 Pancras Road, London NW1 2QB. Tel. 01-278 5571

PAPER TAPE PUNCHES & READERS




TELETYPE BRPE 110 cps Synchronous Punch 5/7/8 channel. Self-contained, mains-operated unit consisting of punch unit, base, motor and tape supply spool. Price £145.00. Sound-reducing cabinet available at £25.00.

DATA DYNAMICS 1114 Rack-Mounted 110 cps Punch, as new. Mounted in sound-reducing rack cabinet and complete with control and interface electronics and power supply unit with short circuit and overload protection. Asynchronous operation up to 110 cps. Our special price £550.

DIGITAL PRINTING MECHANISM TYPE EP101

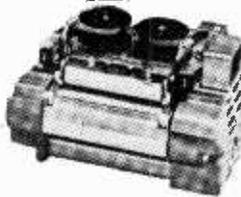Capacity 21 columns, 16 print positions (0-9 + — 5) Parallel data entry. Column spacing 3.5mm. Line spacing 5.1mm. Character Dimensions 1.8mm wide x 2.9mm high. Power requirements 15V DC Current 150mA non maximum printing load. Very compact unit measuring 6" x 5" x 4". **OUR BARGAIN PRICE £49.00 (P&P £1)**



MAGNETIC COMPUTER TAPE
1/4" x 2400' £3.00 per reel
1/2" x 2400' £4.00 per reel
5/8" x 1200' £2.50 per reel
Film for Eliott Film Handler £5.00 per reel

JUST ARRIVED — SPECIAL PURCHASE OF DISK STORAGE DRIVES BY CDC. WILL ACCEPT 6-SPEED DISK-PACKS AVAILABLE EITHER 2 OR 4 MEG CAPACITY. NEVER OFFERED BEFORE. PRICES FROM £450.00

Keyboards

NEW REED-SWITCH KEYBOARDS BY CLARE-PENDAR WITH READ ONLY MEMORY ASCII-CODED OUTPUT

Ideal for communications equipment, VDUs, prototype designs, etc. 68-key versions plus 11 instruction keys. Positive logic. Input voltage -12V DC+5V.

OUR INCREDIBLE PRICE £29.50 (DUE TO SPECIAL PURCHASE) + £1.00 P&P

NEW STOCK JUST RECEIVED:

16-Key Japanese Keyboard, BRAND NEW SURPLUS! Magnetically operated relay rotary switches mounted on PCB 9 white keys, 4 black, 2 yellow, 1 red. Dimensions 3 1/4" x 3 1/4". Price £3.50 (P&P 30p).

4 BANK HONEYWELL ALPHANUMERIC KEYBOARD — BRAND NEW Mounted on printed circuit board (non-coded). 53 character keys + 10 instruction keys and 2 space bars. Layout can be re-arranged as required. Ideal for prototypes and special applications. Hall-effect switches. Power requirement +5V 420 mA. Price £20.00 (P&P £1)

REED-SWITCH 4-BANK ALPHA-NUMERIC KEYBOARD mounted on printed circuit board with ASCII coded output. 43 character keys + 2 shift keys and 12 instructional keys. Ideal for data displays, computer programming, etc. (a) Ex-equipment, housed in metal case £30.00 + £3.00 P&P. (b) Brand new, mounted on PCB board only £30.00 + £1.00 P&P

TERMINALS

Hazeltone 2000 VDU with 24" slave monitor. First-class condition. £900.00.

ASR35 Heavy-duty console-mounted version of ASR33. Designed for continuous running with minimum maintenance. £950.00

KSR33 Input/Output Console (hard copy only) £375.00.

COSBOR DIDS SERIES 402.2 and 402.2A Visual Display Units. Provide high-speed visual access from computer or other information sources. Data transfer rate 120 cps. The model 402.2 displays 13 lines of 40 characters with a viewing surface of 8" x 4 1/2", while the 402.2A displays 13 lines of 80 characters with a viewing surface of 8" x 6" 64 character alphanumeric keyboard. Prices from £325.00.

HAZELTONE 1000 Video Display Terminal. 64 character ASCII-coded alphanumeric keyboard. Display area 12 lines of 80 characters. Data transmission rate 110/300. Price £475.00.

IBM Selectric "Golfball" Input/Output Typewriters. Various models available from £275.00.

WW—094 FOR FURTHER DETAILS

LYNX ELECTRONICS (LONDON) LTD.

AC126 0.15	BC301 0.32	BY206 0.15	1N4003 0.08*
AC127 0.16	BC323 0.60	BY207 0.20	1N4004 0.07*
AC128 0.13	BC327 0.18*	BYX36-300 0.12*	1N4005 0.08*
AC128K 0.25	BC328 0.16*	BYX36-600 0.15*	1N4006 0.09*
AC141 0.18	BC337 0.17*	BYX36-900 0.18*	1N4007 0.10*
AC141K 0.28	BC338 0.17*	BYX36-12000.21*	2N696 0.14
AC142 0.18	BCY70 0.12	BYX38-300 0.50	2N697 0.12
AC142K 0.28	BCY71 0.18	BYX38-600 0.55	2N706 0.10
AC176 0.16	BCY72 0.12	BYX38-900 0.80	2N709 0.14
AC176K 0.25	BD115 0.55	BYX38-12000.65	2N930 0.14
AC187 0.18	BD131 0.36	BZX61 Series	2N1131 0.15
AC187K 0.25	BD132 0.40	Zeners	2N1132 0.16
AC188 0.18	BD135 0.36	BZX83 or BZX88	2N1304 0.20
AC188K 0.25	BD136 0.39	Series	2N1305 0.20
AD140 0.50	BD137 0.40	Zeners	2N1711 0.18
AD142 0.50	BD138 0.48	C106A 0.40	2N2102 0.44
AD143 0.46	BD139	C106B 0.45	2N2369 0.14
AD149 0.45	BD181 0.86	C106D 0.50	2N2369A 0.14
AD161 0.35	BD182 0.92	C106F 0.35	2N2484 0.16
AD162 0.35	BD183 0.97	CRS1.05 0.25	2N2546 0.50
AL102 0.95	BD232 0.80*	CRS1.10 0.25	2N2905 0.18
AL103 0.93	BD233 0.48*	CRS1.20 0.35	2N2905A 0.22
AF114 0.20	BD237 0.55*	CRS1.40 0.40	2N2926R 0.10*
AF115 0.20	BD238 0.60*	CRS1.60 0.65	2N2926Q 0.09*
AF116 0.20	BD184 1.20	CRS3-05 0.34	2N2926T 0.09*
AF117 0.20	BDY20 0.80	CRS3-10 0.45	2N2926G 0.10*
AF118 0.50	BDY38 0.60	CRS3-20 0.50	2N3053 0.15
AF139 0.33	BDY60 0.60	CRS3-40 0.60	2N3054 0.40
AF239 0.37	BDY61 0.65	CRS3-60 0.85	2N3055 0.50
BC107 0.14	BFV62 0.55	MJ480 0.80	2N3440 0.56
BC107B 0.16	BF178 0.28	MJ481 1.05	2N3442 1.20
BC108 0.13	BF179 0.30	MJ490 0.90	2N3525 0.75
BC109 0.14	BF194 0.10*	MJ491 1.15	2N3570 0.80
BC109C 0.16	BF195 0.10*	MJE340 0.40*	2N3702 0.10*
BC117 0.19*	BF196 0.12*	MJE371 0.60	2N3703 0.10*
BC125 0.18*	BF197 0.12*	MJE520 0.45	2N3704 0.10*
BC126 0.20*	BF224J 0.18*	MJE521 0.55	2N3705 0.10*
BC140 0.28	BF244 0.17*	OAS 0.50*	2N3706 0.10*
BC142 0.23	BF257 0.30*	OA90 0.08	2N3707 0.10*
BC143 0.23	BF258 0.35	OA91 0.08	2N3714 1.05
BC144 0.30	BF337 0.32	OC41 0.15	2N3715 1.15
BC147 0.09*	BFW60 0.17*	OC42 0.15	2N3716 1.25
BC148 0.09*	BFX29 0.26	OC44 0.12	2N3771 1.80
BC149 0.09*	BFX30 0.30	OC45 0.10	2N3772 1.60
BC152 0.25*	BFX84 0.23	OC70 0.10	2N3773 2.10
BC153 0.18*	BFX85 0.25	OC71 0.10	2N3819 0.28*
BC157 0.09*	BFX88 0.20	OC72 0.22	2N3904 0.16*
BC158 0.09*	BFY50 0.20	OC84 0.14	2N3906 0.16*
BC159 0.09*	BFY51 0.18	SC40A 0.73	2N4124 0.14*
BC160 0.32	BFY52 0.19	SC40B 0.81	2N4290 0.12*
BC161 0.38	BFY64 0.35	SC40D 0.98	2N4348 1.20
BC168B 0.09	BFY69 0.65	SC40F 0.65	2N4870 0.35
BC182 0.11*	BR100 0.20	SC41A 0.65	2N4871 0.35
BC182L 0.11*	BRV39 0.40	SC41B 0.70	2N4919 0.70*
BC183 0.10*	BSX19 0.16	SC41D 0.85	2N4920 0.50*
BC183L 0.10*	BSX20 0.18	SC41F 0.80	2N4922 0.58*
BC184 0.11*	BSX21 0.20	ST2 0.20	2N4923 0.64*
BC184L 0.11*	BSY95A 0.12	TIP29A 0.44	2N5060 0.20*
BC207B 0.12*	BT106 1.00	TIP30A 0.52	2N5061 0.25*
BC212 0.11*	BT107 1.60	TIP31A 0.54	2N5062 0.27*
BC212L 0.11*	BT108 1.60	TIP32A 0.84	2N5064 0.30*
BC213 0.12	BT109 1.00	TIP34 1.05	2N5496 0.65
BC213L 0.12*	BT116 1.00	TIP41A 0.68	
BC214 0.14*	BU105 1.80*	TIP42A 0.72	
BC214L 0.14*	BU105/5	1N2069 0.14	
BC237 0.16*	02 1.90*	1N2070 0.16	
BC238 0.16*	BU126 1.60*	1N4001 0.04*	
BC300 0.34		1N4002 0.05*	

DIGITAL DISPLAYS & LED'S

DL704 99p	DL747 £1.75	2 RED LED ONLY 13p
DL707 99p	DL750 £1.75	GREEN CLEAR 15p

THYRISTORS

	8A (T092)	1A (T05)	3A (C100 type)	6A (T0220)	9A (T0220)	10A
50	20	25	35	41	42	47
100	25	35	40	47	48	54
200	27	35	45	58	60	68
400	30	40	50	87	88	98
600	32	65	70	1.09	1.19	1.28

TRIACS (PLASTIC TO-220 PKGE. ISOLATED TAB)

	4A	6.5A	8.5A	10A	15A
	(a) (b)				
100V	0.60 0.60	0.70 0.70	0.78 0.78	0.83 0.83	1.01 1.01
200V	0.84 0.64	0.75 0.75	0.87 0.87	0.87 0.87	1.17 1.17
400V	0.77 0.78	0.80 0.83	0.97 1.01	1.13 1.19	1.70 1.74
600V	0.96 0.99	0.87 1.01	1.21 1.26	1.42 1.50	2.11 2.17

N.B. Triacs without internal trigger diac are priced under column (a). Triacs with internal trigger diac are priced under column (b). When ordering please indicate clearly the type required.

74 TTL mixed prices

7400 1.24	25-99 100+	7445 1.24	25-99 100+	7493 1.24	25-99 100+
7401 14p	12p 10p	7446 85p	71p 57p	7494 45p	40p 32p
7402 14p	12p 10p	7447 81p	75p 65p	7495 67p	55p 45p
7403 15p	12 1/2p 10p	7448 75p	62p 50p	74100 £1.08	89p 72p
7404 16p	13p 11p	7449 95p	83p 67p	74107 35p	28p 22p
7405 16p	13p 11p	7470 30p	25p 20p	74121 34p	28p 23p
7406 16p	13p 11p	7472 25p	21p 17p	74122 47p	39p 31p
7409 16p	13p 11p	7473 30p	26p 20p	74141 78p	63p 53p
7410 16p	13p 11p	7474 32p	26p 21p	74145 68p	58p 48p
7413 25p	24p 20p	7475 47p	39p 31p	74154 £1.62	£1.48 86p
7417 27p	22 1/2p 20p	7476 32p	26p 21p	74174 £1.00	83p 67p
7420 16p	13p 11p	7482 75p	62p 50p	74180 £1.06	88p 71p
7427 27p	22 1/2p 18p	7485 £1.30	£1.09 87p	74181 £3.20	£2.50 £1.90
7430 16p	13p 11p	7486 32p	28p 21p	74192 £1.35	£1.14 90p
7432 27p	22 1/2p 18p	7489 £2.92	£2.80 £2.10	74193 £1.35	£1.14 90p
7437 27p	22 1/2p 18p	7490 48p	40p 32p	74195 £1.64	£1.34 99p
7441 75p	62p 50p	7491 65p	65p 45p		
7442 65p	55p 43p	7492 57p	46p 36p		

LINEAR IC'S

301A 8 pin DIL 35p*	3900 74 pin DIL 70p*	565 14 pin DIL £2.00*
307 85p*	709 8, 14 pin DIL 35p*	566 8 pin DIL £1.50*
309K £1.60	741 8 pin DIL 28p*	567 8 pin DIL £2.00*
380 14 pin DIL .90p	741 14 pin DIL 35p*	CA3046 14 pin DIL 50p*
381 14 pin DIL £1.60*	748 8 pin DIL 38p*	CA3045 85p*
	555 8 pin DIL 45p	

HIGHAM MEED, CHESHAM, BUCKS. Tel. (02405) 75151

VAT — Please add 8% except items marked * which are 25%

TELETYPE 28 — NEW SPECIAL PRICE

TELETYPE 28 without keyboard. Good condition (can be used as receive only) **£32.50** ea.

TELETYPE 28 with housing, keyboard and Power supply **£45** ea.

Limited quantities — information in process of being obtained — this may not be available when orders are dispatched but we guarantee to forward comprehensive information at the earliest possible time.

POLARAD SPECTRUM ANALYZER

Type TSA covering 10MHZ-1 GHZ. 25KHZ resolution. **£325.**

Can be extended to 44GHZ with additional plug-in units at nominal cost.

MARCONI Signal Generator. TF801B 12 - 470MHZ **£120** ea.

MARCONI Valve Voltmeter type TF1041B **£45.**

MARCONI TF934/2 FM Deviation Meter **£35.**

MARCONI TF1020A RF Power Meter 150 and 300 Watts. As New. **£60** ea.

MARCONI TF1020A RF Power Meter 50 and 100 Watts. As New. **£45** ea.

MARCONI TF1094A/S HF Spectrum Analyser. Late model. Must go. **£160.**

MARCONI TF1434/2 Counter Range extension unit 10-100MHZ **£25** ea.

KELVIN & HUGHES Single Channel Recorders with spare paper **£18** ea.

FURZEHILL Valve Voltmeter V200. 10mv full scale. **£18** ea. Nice condition.

LOCKHEED ELECTRONICS simultaneous 4 CHANNEL DATA RECORDERS. 18 volt operation. Portable-compact **£120** each.

SOLARTRON OSCILLOSCOPE
TYPE CT316 DC-6mc/s. Size 8½" x 11" x 20". Very fine condition, in Ministry transit cases. Complete with copy of manual **£45** each

RHODE & SCHWARZ Admittance Meter VLUK-BN3511. As new, **£110.**

BRUEL & KJOER Voltmeter type 2409 2 cs to 200k/cs. **£85** ea.

DUAL TRACE PLUG-IN units for CD1212 Scopes DC-24MHZ **£35** ea.

TELEVIC Sweep Generator SM2000/1. Main frame with 0-20kHz plug-in **£300.**

TEKTRONIX Oscilloscope type 516 **£240.**

AIRMEC Printer, type 316. Fine condition. **£35** ea.

MARCONI TF 867 Signal Generator 15KHZ to 30MHZ. **£50** ea.

MARCONI TF 885 Video Oscillator. **£30** ea.

MARCONI TF 791D Deviation Meter. **£90.**

MARCONI TF 791C Deviation Meter. **£60**

MARCONI TF1370 R.C. Oscillator. **£80.**

MARCONI TF1060 UHF Signal Generator. **£175**

MARCONI TF995 AM/FM Signal Generator. **£150**

IBM Data Unit Type 901. **£85** ea

ROHDE & SCHWARZ Receiver ESM180 BN 15073/2. **£425.**

ROHDE & SCHWARZ Generator 300-1000 MHZ. Type SDR BN 41022. **£300.**

FLANN Signal Generator type 501 0.8-3 GC/S **£90** ea.

DATAPULSE Generator 101 by Systron-Donner Corporation. **£90** ea.

★ AB POTENTIOMETERS
100K + 100K LIN DUAL GANG
25p ea.
Discount for quantities. P. & P extra

EX-MINISTRY CT436 Double Beam Oscilloscope DC-6 meg. Max Sensitivity 10mv/cm. Small compact. Size 10 x 10 x 16 in. Suitable for Colour TV servicing. Price **£85** each including copy of manual.

FHACHI RAMP MODULE FX21 24 Volt DC input for 18 volt saw tooth output. Requires only external capacitor and 100K ohm potentiometer to control frequency range up to 100KHZ (eg 50 mfd electrolytic gives sweep of approx. 1 cm per second). In or out sync capability. Price **£5.75**. P. & P. 20p.

★ TELEPHONES
MODERN STYLE 706 BLACK OR TWO-TONE GREY **£3.75** ea. P. & P. 45p. **STYLE 7006** TWO-TONE GREEN OR GREY **£3.75** ea. P. & P. 45p. **HANDSETS**—complete with 2 insets and lead **£1.25** ea. P. & P. 37p. **DIALS ONLY**. 50p ea. P. & P. 30p. **STILL AVAILABLE** MODERN STANDARD TELEPHONES IN GREY OR GREEN WITH A PLACE TO PUT YOUR FINGERS LIKE THE 746. **£3.00** ea. P. & P. 45p.

***CAPACITOR PACK** 50 Brand new components only **50p**. P. & P. 27p
***P.C. MOUNT SKELETON PRE-SETS.** Screwdriver adjust 10 5 and 2.5M a **2p** ea 1M 500, 250 and 25K a **4p** ea Finger ad just 10, 5 and 2.5M a **3p** ea. 1M 500, 250 and 25K a **5p** ea Min. P. & P. 15p

25p the LOT. P. & P. 15p
***PHOTOCELL** equivalent OCP71. **13p** ea.
GRATICULES. 12 cm by 14 cm in High Quality plastic. **15p** each. P. & P. 8p.

VENNER Hour Meters—5 digit. wall mount —sealed case Standard mains. **£3.75** ea. P. & P. 55p

RESETTABLE COUNTERS—4 digit by Stonebridge Sodoco. 1 000 ohm coil. **£2** ea. P & P 35p

***Beehive Trimmer 3/30 pf.** Brand new Qty 1-9 **13p** ea P. & P. 15p. 10-99 **10p** ea P. & P. 25p. 100-999 **7p** ea. P. & P. free

***Vast quantity of good quality components** —NO PASSING TRADE—so we offer **3 LB. OF ELECTRONIC GOODIES** for £1 70 post paid

TRANSFORMERS. All standard inputs. Gard/Parm/Part. 450-400-0-400-450. 180 MA 2 x 6.3v. **£3** ea

E.H.T. CAPACITORS
1 mfd 7.5KV working 2 mfd 5KV working. 8 mfd 2.5KV working. 0.5 mfd 10KV working **£2** each

RAPID DISCHARGE
1 mfd 5.6KV **£2.50** ea. 0.9 mfd 15KV **£3.50** ea. 0 15 mfd 120KV **£7** ea Carriage extra

DELIVERED TO YOUR DOOR 1 cwt. of Electronic Scrap chassis boards etc. No Rubbish FOR ONLY **£4.50**. N Ireland £2 extra
P.C.B. PACK S & D Quantity 2 sq ft —no tiny pieces. **50p** plus P & P 25p

HF Crystal Drive Unit. 19 in rack mount. Standard 240V input with superb crystal oven by Labgear (no crystals) **£5** ea. Carr **£2**

FANTASTIC VALUE
Miniature Transformer Standard 240V input .3V 1 amp output Brand New **65p** ea P & P 20p. Discount for quantity

FHACHI VCC MODULE FX11—10HZ-100KHZ

Size 2 x 1½ x ¾". Input 12V to 24V DC (not centre tapped) 18V input giving 10V constant amplitude output Requires only a 1 meg ohm potentiometer to tune entire range — or can be swept with a saw tooth input Price **£5.75**. P & P 20p

***TRIMMER PACK.** 2 Twin 50/200 pf ceramic. 2 Twin 10/60 pf ceramic. 2 min strips with 4 preset 5/20 pf on each. 3 air spaced preset 30/100 pf on ceramic base ALL BRAND NEW

BOURNS TRIMPOT POTENTIOMETERS. 20, 50, 100, 200, 500 ohms, 1, 2, 2.5, 5, 10; 25K at **35p** ea ALL BRAND NEW

FIBREGLASS PRINTED CIRCUIT BOARD. Brand New Single or Double sided Any size **1½p** per sq. in Postage 20p per order

DON'T FORGET YOUR MANUALS S.A.E. WITH REQUIREMENTS

RELIANCE P.C.B. mounting 270 470, 500 ohms; 10K at **35p** ea ALL BRAND NEW
TEN TURN POTS. Ex equ As new. Micropot Model 205 Two point nine ohms 0 1% @ £1 50 ea. P&P 20p
Bourns Model 3507S-3-101 100 ohms £1 25 ea. P&P 15p

***HIGH VALUE PRINTED BOARD PACK.** no two boards the same—no short leaded computer boards. **£1.75** post paid

***METER PACKS**—3 different meters for **£2**. P & P 55p

LOW FREQUENCY WOBBULATOR

For alignment of Receivers, Filters, etc. 250KHz to 5MHz. effective to 30MHz on harmonics. Three controls—RF level, sweep width and frequency. Order LX63. Price **£8.50** P. & P. 35p. As above but can have extended cover range down to 20KHz by addition of external capacitors. Order LX63E. Price **£11.50** P. & P. 35p. Both models can be used with any general-purpose oscilloscope. Requires 6.3V AC input. Supplied connected for automatic 50Hz sweeping. An external sweep voltage can be used instead. These units are encapsulated for additional reliability. with the exception of the controls (not cased, not calibrated).

20HZ to 200KHZ

SINE AND SQUARE WAVE GENERATOR

In four ranges. Wien bridge oscillator thermistor stabilised. Separate independent sine and square wave amplitude controls. 3V max sine 6V max square outputs. Completely assembled P.C. Board, ready to use. 9 to 12V supply required. **£8.85** each. P. & P. **35p**. Sine Wave only. **£6.85** each. P. & P. **35p**.

WIDE RANGE WOBBULATOR

5 MHZ to 150 MHZ (Useful harmonics up to 1.5 GHZ) up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10-7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6-3V AC and use within minutes of receiving. All this for only **£6.75**. P. & P. **35p**. (Not cased..not calibrated.)

TRANSISTOR INVERTORS

TYPE A
Input: 12V DC
Output: 1.3kV AC 1.5MA
Price **£3.45**

TYPE B
Input: 12V DC
Output: 1.3kV DC 1.5MA
Price **£4.70**

TYPE C
Input: 12V to 24V DC
Output: 1.5kV to 4kV AC 0.5MA
Price **£6.35**
Postage & Packing **36p**

TYPE D
Input: 12V to 24V DC
Output: 14kV DC 100 micro amps at 24V. Progressively reducing for lower input voltages
Price **£11**

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2 HZ to 8 MHZ. Hook up a 9 volt battery and connect to your scope and have two traces for ONLY **£6.25**. P. & P. 25p. **STILL AVAILABLE** our 20 MHZ version at **£9.75**. P. & P. 25p.

Unless stated — please add £2.50 carriage to all units

VALUE ADDED TAX not included in prices—Goods marked with ★ 25% VAT, otherwise 8%

Official Orders Welcomed, Gov./Educational Depts., Authorities, etc., otherwise Cash with Order

Open 9 a.m. to 5.30 p.m. Mon. to Sat.



CHILTMHEAD LTD



7/9 ARTHUR ROAD, READING, BERKS. (rear Tech. College, Kings Road)

Tel.: Reading 582605


RETURN OF POST MAIL ORDER SERVICE

BSR HI-FI AUTOCHANGER STEREO AND MONO
Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. A.C. 200/250V. Size 13½ x 11¼ in. Above motor board 3¼ in. Below motor board 2½ in. with STEREO and MONO CARTRIDGE **£10.95** Post 75p



PORTABLE PLAYER CABINET
Modern design. Rexine covered. Vynair front grille. Chrome fittings. Size 17 x 15 x 8 in approx. Motor board cut for BSR or Garrard deck **£5.25** Post 75p

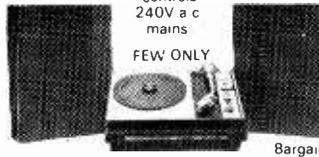COMPLETE STEREO HI-FI SYSTEM
Two full size loudspeakers 13¼ x 10 x 3¼ in. Player unit clips to loudspeakers making it extremely compact, overall size only 13¼ x 10 x 8½ in. 3 watts per channel, plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls 240V a.c. mains **£25** Post 30p



Attractive Teak finish **£25** Post 30p
Bargain Price **£1** carriage

SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH 0-60 MINUTES £2.50 Post 35p
Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on/off at full or intermediate settings. Brand new and fully guaranteed.



TEAKWOOD LOUDSPEAKER GRILLES will easily fit to baffle board. Size 18¼ x 10½ in—**75p**. 10½ x 7½ in—**45p**.

WEYRAD P50 — TRANSISTOR COILS

RA2W Ferrite Aerial 85p	Driver Trans. LFD4T 65p
I.F. P50/2CC 470 kc/s 40p	Printed Circuit, PCA1 65p
3rd I.F. P50/3CC 40p	J.B. Tuning Gang £1.20
Spares Core 3p	Weyrad Booklet 10p
P50/1AC 60p	OPT1 65p

Mullard Ferrite Rod 8 x ¾ in. **20p**. 6 x 5/16 in. **20p**. 3 x ¾ in. **10p**

VOLUME CONTROLS
5kΩ to 2MΩ. LOG or LIN. L/S **25p**. D.P. **40p**. STEREO L/S **55p**. D.P. **75p**. Edge 5K S.P. Transistor **30p**.

80 Ohm Coax 8p yd.
BRITISH AERIALITE AERIAL-AIR SPACED 40 yd **£2**; 60 yd. **£3** 15p
FRINGE LOW LOSS
Ideal 625 and colour yd.

8 in. or 10 x 6 in. ELAC HI-FI SPEAKER
Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 c/s. Bass resonance 55 c/s. 8 ohm impedance. 10 watts. music power **£4.35** Post 35p



E.M.I. 13½ x 8 in. SPEAKER SALE!
With tweeter and crossover 10 watt. State 3 or 8 ohm. As illustrated **£5.25** Post 35p **£6.60**

13 in x 8 in Bass Woofer 20 watts

With flared tweeter cone and ceramic magnet 10 watt. Bass res. 45-60 c/s. Flux 10,000 gauss. 8 ohm 40 to 11,000 c/s **£3.45** Post 35p

Bookshelf Cabinet Teak finish 16 x 10 x 9 in **£6.95** Post 75p

THE "INSTANT" BULK TAPE ERASER AND HEAD DEMAGNETISER. Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S.A.E. **£4.35** Post 30p



BLANK ALUMINIUM CHASSIS. 6 x 4—**70p**; 8 x 6—**80p**; 10 x 7—**£1.15**; 12 x 8—**£1.35**; 14 x 9—**£1.50**; 16 x 6—**£1.45**; 16 x 10—**£1.70**.
ALUMINIUM PANELS. 6 x 4—**17p**; 8 x 6—**24p**; 14 x 3—**25p**; 10 x 7—**35p**; 12 x 8—**43p**; 12 x 5—**30p**; 16 x 6—**43p**; 14 x 9—**52p**; 12 x 12—**68p**; 16 x 10—**75p**.

ELAC 9 x 5 in HI-FI SPEAKER TYPE 59RM
This famous unit now available. 10 watts. 8 ohm **£3.45** Post 35p

QUALITY LOUDSPEAKER ENCLOSURE
Teak veneered ¾ in. thick wood cabinet. Size 18½ in. x 18½ in. x 8½ in. Weight 23lb. This cabinet features a wide mesh Silver Grill covering a separate compartment for mounting Tweeters or Mid-Range Horn. The fully sealed bass compartment is cut out for 6½ inch Woofer **£7.50**. Carr 85p. Rosewood Version **£8.50**. Carr 85p. Baffle could be cut to take larger speaker.



RCS POWER PACK KIT **£3.35** Post 30p
12 VOLT 750mA. Complete with printed circuit board and assembly instructions. 12 VOLT 300mA KIT, **£3.15**. 9 VOLT 1 AMP KIT, **£3.35**.

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER — BRITISH MADE
Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12V or H.T. line 200-300V d.c. operation. Size 1¼ x 1¼ x ¾ in. Response 25 c/s to 25 kc/s. 26 dB gain. For use with valve or transistor equipment. Full instructions supplied. Details S.A.E. **£1.45** Post 30p

ELECTRO MAGNETIC PENDULUM MECHANISM
1.5V d.c. operation over 300 hours continuous on SP2 battery, fully adjustable swing and speed. Ideal displays. teaching electro magnetism or for metronome, strob. etc **95p** Post 30p

R.C.S. "MINOR" 10 watt AMPLIFIER KIT
This kit is suitable for record players, guitars, tape playback, electronic instruments or small P.A. systems. Two versions available. Mono, **£12.50**; Stereo, **£20**. Post 45p. Specification 10W per channel; input 100mV, size 9½ x 3 x 2 in approx. S.A.E. details. Full instructions supplied.

MAINS TRANSFORMERS ALL POST

250-0-250V 70mA. 6.5V. 2A	Large 75p
250-0-250 80mA. 6.3V 3.5A. 6.3V 1A or 5V 2A	£2.90
350-0-350 80mA. 6.3V 3.5A. 6.3V 1A or 5V 2A	£5.80
300-0-300V 120mA. 6.3V 4A C.T. 6.3V 2A	£7.00
MIDGET 220V 45mA. 6.3V 2A	£1.25
HEATED TRANSFORMER 6.3V ½ amp 95p; 3 amp £1.40	

GENERAL PURPOSE LOW VOLTAGE Tapped outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V **£4.60**
1 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£4.60**
2 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£8.70**
5 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£11.25**
6.06V 500mA **£1**, 9V 1 amp **£1**, 12V 300mA **£1.15**, 12V 500mA **£1**, 12V 750mA **£1**, 10V, 30V, 40V, 2 amp. **£2.75**, 20V, 3 amp. **£2.45**, 40V, 2 amp. **£2.95**, 22-0-22V, 4 amp d.c. **£3.45**, 16V, ½ amp. **95p**, 16V, 2 amp. **£2.20**, 0, 5, 8, 10, 16V, ½ amp. **£1.95**, 20V ½ amp. **£1.75**, 20V, 1 amp. **£2.20**.
AUTO TRANSFORMERS. 115V to 230V or 230V to 115V **150p**; 250V **£6**; 400V **£7**; 500V **£8**.
FULL WAVE BRIDGE CHARGER RECTIFIERS 6 or 12V outputs. 1½ amp **40p**; 2 amp **55p**; 4 amp **85p**.
CHARGER TRANSFORMERS 1½ amp **£2.75**; 4 amp **£4.60**.

GOODMANS 6½ in. HI-FI SPEAKER
4 ohm or 8 ohm, 10W Large ceramic magnet. Special Cambric cone surround. Twin cone. Frequency response 30-15,000 c/s. Hi-Fi Enclosure Systems, etc **£4.60**



NEW ELECTROLYTIC CONDENSERS

2/350V 20p	250/25V 20p	50+50/350V 50p
4/350V 20p	500/25V 25p	900/350V 95p
8/350V 28p	100+100/275V 65p	32+32 250V 20p
16/350V 35p	150+200/275V 70p	32+32/450V 80p
32/350V 60p	8+8/350V 50p	350+50/325V 85p
25/25V 15p	8+16 350V 50p	100+50+50/350V 85p
50/50V 15p	16+16 350V 60p	32+32+32/350V 65p
100/25V 15p	32+32 350V 60p	4700 63V 95p

LOW VOLTAGE ELECTROLYTICS
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.
500mF 12V 15p; 25V 35p; 50V 47p; 100V 70p.
1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p.
2000mF 6V 25p; 25V 42p; 50V 57p.
2500mF 50V 62p; 3000mF 25V 47p; 50V 65p.
5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 95p.

TRIMMERS 10pF, 30pF, 50pF, 5p, 100pF, 150pF, 15p. **CERAMIC**, 1pF to 0.01mF, 5p. Silver Mica 2 to 5000pF, 5p. **PAPER** 350V-0 1 7p; 0.5 13p; 1mF 150V 15p; 2mF 150V 15p; 500V-0 0.01 to 0.05 5p; 0 1 10p; 0 25 13p; 0.47 25p. **MICRO SWITCH SPCD 20p**. **SUB-MIN MICRO SWITCH**, 25p. Single pole change over. **TWIN GANG**, "0-0" 208pF + 176pF **£1.20**; 500pF standard **75p**; 365 + 365 + 25 + 25pF. Slow motion drive **50p**. **120pF TWIN GANG**, **50p**; **365pF TWIN GANG**, **50p**. **NEON PANEL INDICATORS 250V AC/D.C.** Amber **30p**. **RESISTORS.** ¼W, ½W, 1W, 20% 2p; 2W, 10p; 10Ω to 10M. **HIGH STABILITY.** ½W 2% 10 ohms to 6 meg., 12p. Ditto 5%. Preferred values 10 ohms to 10 meg., 5p. **WIRE-WOUND RESISTORS** 5 watt, 10 watt, 15 watt, 10 ohms to 100K 12p each. **TAPE OSCILLATOR COIL** Valve type, 35p.

NEW MODEL "BAKER LOUDSPEAKER", 12 in. 60 WATT. GROUP 50/12, 8 OR 15 OHM HIGH POWER. FULL RANGE PROFESSIONAL QUALITY **£14.50** Post 80p

BAKER MAJOR 12" £11.50
30-14,500 c/s. 12 in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 25W. NOTE 3 or 8 or 15 ohms must be stated.
Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions **£14.50** Post 60p each
Please state 3 or 8 or 15 ohms.



BAKER "BIG-SOUND" SPEAKERS. Post 50p each.

'Group 25'	'Group 35'	'Group 50/15'
12 in 30W £8.95	12 in 40W £10.50	15 in 75W £19.50
3 or 8 or 15 ohm	3 or 8 or 15 ohm	8 or 15 ohm

TEAK VENEERED HI-FI SPEAKERS AND CABINETS
For 12 in or 10 in dia speaker 20x13x12 in **£12.50** Post 95p
De Luxe Horn Tweeters 2-18kc/s. 15W 15 ohm **£4.50**
For 8x5 in speaker 16x8x6 in **£5.80** Post 50p
LOUDSPEAKER CABINET WADDING 18 in. wide, 20p ft

R.C.S. 100 watt VALVE AMPLIFIER
Four inputs. Four way mixing, master volume, treble and bass controls. Suits all speakers. This professional quality amplifier chassis is suitable for all groups, disco, P.A., where high quality power is required. 5 speaker outputs. A/C mains operated. Slave output. Produced by demand for a quality valve amplifier. Send for leaflet. Price **£85** carr. **£2** 50



SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 2-16kc/s. 10W 8 ohm or 15 ohm **£3**. De Luxe Horn Tweeters 2-18kc/s. 15W 15 ohm **£4.50**. **CROSSOVERS. TWO-WAY** 3000 c/s 3 or 8 or 15 ohm **£1.90**. **LOUDSPEAKERS P.M. 3 OHMS.** 7x4 in **£1.50**; 6½ in. **£1.80**; 8x5 in. **£1.90**; 8 in. **£2.20**. **SPECIAL OFFER:** 80 ohm 2½ in., 2½ in., 35 ohm, 2 in., 3 in., 25 ohm, 2½ in. dia, 3 in. dia, 5 in. dia, 8 ohm, 2½ in., 3 in., 3½ in., 15 ohm, 3¼ in. dia, 6x4 in., 7x4 in., 8x5 in., 3 ohm, 2½ in., 2½ in., 3½ in., 5 in. dia **£1.25 each**. **RICHARD ALLAN TWIN CONE LOUDSPEAKERS** 8 in. diameter **£W 42.50**, 10 in. diameter **5W £2.95**; 12 in. diameter **6W £3.50**, 3/8/15 ohms, please state. **VALVE OUTPUT TRANS. 40p**; **MIKE TRANS. 50 1 40p**. Mike trans mu metal 100 1 **£1.25**.

Loudspeaker Volume Control 15 ohms 10W with one inch long threaded bush for wood panel mounting. ¼ in. spindle. **65p** each. Post 15p

BAKER 100 WATT ALL PURPOSE AMPLIFIER
All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm a.c. Mains. Separate treble and bass controls. Guaranteed. Details S.A.E. **NEW MODEL MAJOR—50 watt, 4 input, 2 vol** Treble and bass. Ideal disco amplifier **£49.95**
100 WATT DISCO AMPLIFIER
Chassis volume, treble, bass controls 500 mu input **£55**
Four L/S O.P. 4 to 16 ohm



BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER
Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9V. **£5.20**
TWO STEREO CHANNEL VERSION **£6.85**
BARGAIN 3 WATT AMPLIFIER, 4 Transistor Push-Pull Ready Built, with volume, Treble and bass controls. 18 volt d.c. Mains Power Pack **£3.45**

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p. OUTLET BOXES, SURFACE 40p. FLUSH 60p. TWIN 85p. BALANCED TWIN RIBBON FEEDER 300 ohms. 7p yd. JACK SOCKET Std. open-circuit 18p, closed circuit 23p; Chrome Lead-Socket 45p. Phono Plugs 8p. Phono Socket 8p. JACK PLUGS Std. Chrome 30p; 3.5mm Chrome 15p. DIN SOCKETS Chassis 3-pin 10p, 5-pin 10p. DIN SOCKETS lead 3-pin 25p, 5-pin 25p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS, 10p; CERAMIC 10p; CANS 10p.

R.C.S. SOUND TO LIGHT KIT
Kit of parts to build a 3 channel sound to light unit 1,000 watts per channel. **£12.50**. Post 35p. Easy to build. Full instructions supplied. As featured in December Practical Wireless.

E.M.I. TAPE MOTOR **£2**
E.M.I. TAPE MOTORS. 240V a.c. 1,200 r.p.m. 4 pole 135mA. Spindle 0.187x0.75 in. Size 3¼x2½x2¼ in (illustrated). Post 40p. 120V Model. **£1**



RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON

Open 9-6. Wed. 9-1. Sat. 9-5 (Closed for lunch 1.15-2.30)
Buses 50, 68, 159. Rail Selhurst. Tel. 01-684 1665

SERVICE TRADING CO

RELAYS

SIEMENS PLESSEY, etc. MINIATURE RELAYS			
1	2	3	4
52	4-8	2 c/o	75p
58	5-9	6 c/o	85p
185	8-12	6 M	85p
230	9-18	2 c/oHD	75p
430	15-24	4 c/o	85p
700	12-24	4 c/o	65p

(1) Coil ohms; (2) Working d.c. volts; (3) Contacts; (4) Price HD=Heavy Duty. All Post Paid. (*Including Base)

OPEN TYPE RELAYS

6 VOLT D.C. 1 make relay 35p Post 15p

9 VOLT D.C. RELAY 3 c/o 5 amp contacts. 70 ohm coil 75p Post 15p

12 VOLT D.C. RELAY 3 c/o 5 amp contacts. 120 ohm coil 75p Post 15p

24 VOLT D.C. 2 HD c/o 700 ohm coil 75p Post 15p

4 c/o 300 ohm coil 85p Post 15p

100 VOLT a.c. 2 c/o 65p. 3 c/o 75p. Post 15p

ENCLOSED TYPE RELAYS

24V D.C. 3 c/o 75p. Post 20p. Base 15p

24 VOLT A.C. Mtg. ITT 3 h.d. c/o contacts 55p. Post 20p. Base 15p extra

55 VOLT A.C. 3 heavy duty c/o contacts. Price 55p. Post 20p. Base 15p

230 VOLT A.C. RELAY 240V. A.C. heavy duty 3 c/o contacts

Price 75p. Post 20p. Octal base 15p extra

220/240 VOLT AC RELAY 3 c/o 5 amp cont. Sealed Mtg. ISKRA £1.25. Post 20p. Base 15p extra

ARROW 230/240V AC 2 c/o 15 amp contacts. Air connectors £1.00. Post 20p

110 VOLT A.C. 2 c/o. 20 amp. £1.25 Post 15p

CLARE-ELLIOT Type RP 7641 G8 Miniature relay. 675 ohm coil. 24 volt D.C. 2 c/o. P.P.P

MANY OTHERS FROM STOCK, PHONE FOR DETAILS

VARIABLE VOLTAGE TRANSFORMERS

Carriage extra
INPUT 230 v. A.C. 50/60
OUTPUT VARIABLE 0/260 v. A.C.
BRAND NEW. All types.
200W (1 Amp) £10.00
0.5 KVA (Max. 2 1/2 Amp) £11.50
1 KVA (Max. 5 Amp) £16.50
2 KVA (Max. 10 Amp) £30.00
3 KVA (Max. 15 Amp) £33.00
4 KVA (Max. 20 Amp) £60.00
(max. 37.5 Amp) £102.50

LT TRANSFORMERS

0 6 12 volt a 10 amp £5.60 Post 70p
 0 10 17 18 volt a 10 amp £7.90 Post £1.00
 0 6 12 volt a 20 amp £9.00 Post £1.00
 0 12 24 volt a 10 amp £9.00 Post £1.00
 0 4 6 24 32 volt a 12 amp £9.90 Post £1.00
 0 6 12 17 18 20 volt a 20 amp £10.40 Post £1.00
 Other types to order at short notice - Phone your enquiries

AUTO TRANSFORMERS

Step up step down 0 115 200 220 240 volts
 At 75 watt £2.64 Post 40p. 150 watt £3.50 Post 50p. 300 watt £6.20 Post 60p. 500 watt £9.20 Post 75p. 1000 watt £12.00 Post 90p

STROBE! STROBE! STROBE!

★ **FOUR EASY TO BUILD KITS USING XENON WHITE LIGHT FLASH TUBES, SOLID STATE TIMING & TRIGGERING CIRCUITS. PROVISION FOR EXTERNAL TRIGGERING. 230-250V. A.C. OPERATION.** ★

★ **HY-LITE STROBE Mk IV** Designed for use in large rooms, halls and utilizes a silica tube. printed circuit. Speed adjustable 1.20 f.p.s. Light output greater than many (so called 4 Joule) strobes. Price £15.40. Post 75p

★ **RANGE OF THREE OTHER STROBE KITS FROM STOCK. FROM £6.30 to £22.00 S.A.E. (Footscap) for details.** ★

★ **BIG BLACK LIGHT** 400 Watt. Mercury vapour ultra violet lamp. ★

★ **Extremely compact and powerful source of u.v.** ★

★ **Innumerable industrial applications also ideal for stage display, discos etc. P.F. ballast is essential with these bulbs. Price of matched ballast and bulb £21.00. Post £1.50. Spare bulb £8.00. Post 65p** ★

★ **BLACK LIGHT FLUORESCENT U.V. TUBES** ★

★ **4ft. 40 watt £5.50 (callers only). 2ft. 20 watt £4.25. Post 60p** ★

★ **(For use in stan. b-pin fittings) MINI 12in. 8 watt £1.60. Post 25p. 9in. 6 watt £1.30. Post 25p. Complete ballast unit and holders for either 9" or 12" tube. £1.70. Post 30p (9" x 12" measures approx.)** ★

★ **U.D.I. SINGLE CHANNEL. 750 watt MANUAL/AUTO DIMMER** ★

★ **750W Solid State Fader, with three functions. Manual fade. Auto fade-up. Auto fade-down. Automatic cycling up and down. Functions selected with three position rocker switch. Two ranges of cycling for 'Flashing' or 'Slow blending'. Ready built module 6" x 3" glass fibre board incorporating 10 amp TRIAC. Two or more modules for top quality colour blending and flashing effects. PRICE £15.00. Post 65p.** ★

★ **SQUAD LIGHT** ★

★ **A new conception in light control. Four channels each capable of handling 750 watts of spotlights, floodlights or dozens of small mains lamps. Seven programs all speed controlled plus flash modulation, effectively giving 14 different displays. Makes sound-to-light obsolete. Completely electrically and mechanically noise free. Can be used on same circuit as radio makes or sensitive amplifiers. A whole new range of lighting effects possible with astounding results. Already in use in London's foremost theatres, night clubs and discos. Conforms to all R.F.I. tests, including Common Market regulations. Supplied in tough well designed case with embossed front panel. Price only £60.00. Post 75p. S.A.E. (Footscap) for further details.** ★

★ **WHY PAY MORE?!** ★

★ **MULTI RANGE METER. A.C. volts 2.5-500 O.C. volts 2.5-500 (Sensitivity 2000Ω/V O.C. & A.C.). DC current 0/1/10/100 mA. Ohms range. Sturdy compact moving coil instrument with 21 ranges, dimensions 120x80x44mm. Weight 0.32 kg. SERVICE TRADING CO. Price £5.00. Incl. leads and battery. Post 50p. (Total price inc. VAT & Post £5.94).** ★

★ **METERS NEW** ★

★ **90mm Diameter. Type 05C5 2A DC M/C. 5A DC M/C. 10A DC M/C. 20A DC M/C** ★

★ **Type 6272 1A A.C. M/I. 20A A.C. M/I. 300V A.C. M/I. ALL ABOVE £2.50. Post 30p** ★

★ **Type 6515 300V A.C. R/M/C. £2.75. Post 30p** ★

★ **VAT AT 8% MUST BE ADDED TO ALL ORDERS** ★

★ **FOR THE TOTAL VALUE OF GOODS INCLUDING POSTAGE UNLESS OTHERWISE STATED** ★

GEARED MOTOR

Type SD48 15 r.p.m. 80 lb. ins. Input 100/120 volt A.C. Length incl. gearbox 270mm. Height 135mm. Width 150mm. Shaft drive 16mm. Weight 8.5 kilos. BRAND NEW Price £10.00, carr. £1.00. Suitable transformer for use on 220/240 volt A.C. £3.85. Post 50p

REVERSIBLE MOTOR

General Electric. 230V. A.C. 1.600 r.p.m. 0.25 amp. Complete with anti-vibration mounting bracket and capacitor. O/A size 110mm x 95mm. Spindle 5/16" dia 20mm long. Ex-equipment tested £3.00. Post 50p

20 r.p.m. GEARED MOTOR

230/240 volt-20 r.p.m. motor. £1.00. Post 20p

BODINE TYPE N.C.I. GEARED MOTOR

(Type 1) 71 r.p.m. torque 10 lb. in. Reversible 1/70th h.p. cycle-38 amp. (Type 2) 28 r.p.m. torque 20 lb. in. Reversible 1/80th h.p. 50 cycle-28 amp. The above two precision made U.S.A. motors are offered in 'as new' condition. Input voltage of motor 115V A.C. Supplied complete with transformer for 230/240V A.C. input. Price: either type £6.25. Post 75p or less transformer £3.75. Post 65p. These motors are ideal for rotating aerials, drawing curtains, display stands, vending machines, etc. etc.

BENDIX MAGNETIC CLUTCH

A superb example of Electro-mechanics! The main body is in two sections. The coil section is fixed and has a 1/2in. sleeve. The drive section rotating on the outer perimeters. The uniting plate has 1/4in. ID bearing concentric with main section and 18-tooth cog wheel. When energized transmission is extremely powerful. 24V d.c. at 240 MA OUR PRICE JUST £2.50. Post 45p

ROTARY VACUUM AIR COMPRESSOR AND PUMP

Carbon vane, oil-less 100/115V A.C. 1/12 h.p. motor. 50/60 cycle. 2875/3450 r.p.m. 20" vacuum. 1.25 c.i.m. 10 p.s.i. (approx. figures) New unused surplus stock with elect. connection data. Fraction of maker's price £12.00. Post £1.00. Suitable transformer £3.50. Post 50p

UNISELECTOR SWITCHES - NEW

4 BANK 25 WAY FULL WIPER 25 ohm coil, 24v. D.C. operation £6.90. Post 50p

6 BANK 25 WAY FULL WIPER 25 ohm coil, 24 v. D.C. £7.90. Post 50p

8 BANK 25 WAY FULL WIPER 24 v. D.C. operation £9.50. Post 65p.

TIME SWITCH

Hostmann Type V Mk II Time Switch. 200/250 volt A.C. Two on/off every 24 hours. At any manually pre-set time. 30 amp contacts. 36-hour spring reserve in case of power failure. Day omitting device. Fitted in heavy high impact case, with glass observation window. Built to highest Electricity Board spec. Individually tested. Price £7.75. Post 50p. (Total inc. VAT £8.91)

A.C. MAINS TIMER UNIT

Based on an electric clock, with 25 amp single-pole switch, which can be preset for any period up to 12 hrs. ahead to any manually on for any length of time, from 10 mins. to 6 hrs. then switch off. An additional 60 min. audible timer is also incorporated. Ideal for Tape Recorders, Lights, Electric Blankets etc. Attractive satin copper finish. Size 135 mm x 130 mm x 60 mm. Price £2.25. Post 40p. (Total inc. VAT & Post £2.87.)

PROGRAMME TIMERS

230/240 Volt A.C. 15 RPM Motors. Each cam operates a c/o motor switch. Ideal for lighting effects, animated displays etc. Ex equipment tested similar to illustration. 2 cam model 15 r.p.m. £2.00 post 35p. 4 cam model 15 r.p.m. £2.50 post 40p. 8 cam model 20 r.p.m. £4.75 post 60p. 8 cam model each cam fully adjustable. 6 r.p.m. Mfg by Magnetic Devices. £7.50. Post 60p

POWER RHEOSTATS

New ceramic construction, vitreous, enamel embedded winding, heavy duty brush assembly, continuously rated. 25 WATT 10 25 100 150 250 500 1k 1.5k ohm £1.70. Post 20p. 50 WATT 1.5 10 25 50 100 500 1k ohm £2.10. Post 25p. 100 WATT 10/10/25/50/100/250/500/1k/1.5k/2.5k/5k ohm. £3.30. Post 35p. Black Silver Skirted knob calibrated in Nos. 1-9. 1 1/2 in. dia. brass bush. Ideal for above Rheostats, 22p ea.

'GENTS' 6" ALARM BELL

200/250 volt AC DC Brand New. Price: £5.00. Post 75p (illus.) VAT 25%.

'STC' 6" RED ALARM BELL

Brand New. Price £4.00. Post 50p. 24/48V DC. VAT 25%

INSULATION TESTERS (NEW)

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L. 8 in. W. 4 in. H. 6 in. weight 6 lb. 500 VOLTS 500 megohms £30.00 Post 80p. 1000 VOLTS 1000 megohms £36.00. Post 80p.

ALL MAIL ORDERS, ALSO CALLERS AT:

57 BRIDGMAN ROAD, CHISWICK, LONDON, W4 5BB. Phone: 01-995 1560. Closed Saturdays.

SERVICE TRADING CO.

SHOWROOMS NOW OPEN
 AMPLE PARKING

PERSONAL CALLERS ONLY

9 LITTLE NEWPORT STREET, LONDON, WC2H 7JJ. Tel.: 01-437 0576

TEAC

TEAC A3340(S)
4-CHANNEL
RECORDER



Industrial version upgraded to studio requirements with increased signal to noise performance and improved reliability. Four totally independent channels each with sel. sync. input mixing, switchable VU's and all the facilities for easy multitracking. This industrial model is in more studios than any other version.

Available only from ITA
(Semi-pro version also available)
IMMEDIATE DELIVERY

REVOX

REVOX A-700 SERIES



The new big Revox — ideal for all studio requirements. Highly sophisticated design features include servo tape tension, full deck logic, crystal controlled servo electronics, 3 speeds, tape footage counter.

£595 IMMEDIATE DELIVERY

The famous A77 has been consistently improved over the past 8 years and is now available in the latest Mk. 4 version. The wide choice of specifications includes versions for duplicating and logging applications. Backed by UK's latest fastest service.


A-77 SERIES Mk 4



Hire service
Check our prices from £275
IMMEDIATE DELIVERY

ITA

ITA 10-4
MODULAR MIXER

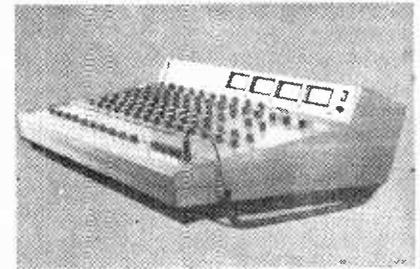

Ten balanced inputs, four output groups, 4 limiters, bass, mid and treble EQ, modular construction, headphone monitoring. Extremely high quality construction only matched by mixers costing around £1000.

10-4 £647

20-4 £990

EIGHT OUTPUT £1260

IMMEDIATE DELIVERY

Also available for hire

PRICES EXCLUSIVE OF V.A.T.

Industrial Tape Applications



5 Pratt Street, London NW1 0AE
Telephone: 01-485 6162. Telex: 21879

WW-092 FOR FURTHER DETAILS


																<p align="center">Stereo Tape Recorders</p> <p align="center">Stereo Cassette Recorders Stereo Car Cassette Players</p> <p align="center">SPECIAL AUDIO & VIDEO TAPES SUPPLIED. PRICES ON REQUEST</p>											
<p>EMIL FUJI MAXELL</p>		<p>*** LEADING BRANDS OF CASSETTES - REPLACEMENT GUARANTEE ***</p>																									
PLASTIC SNAP PACK		BASF LH		BASF Super S/M		BASF CROZ		Memorex MRX		Memorex CROZ		REEL TO REEL		BASF Low Noise in Plastic Box		BASF LH Super in Plastic Box		Scotch Hi-Fi Boxed		Agfa Low Noise in Plastic Box		Agfa PFM in Plastic Box					
	One	10	One	10	One	10	One	10	One	10	One	10	One	10	One	10	One	10	One	10	One	10	One	10			
C60	42p	£4.15	60p	£5.90	90p	£8.89	57p	£5.63	77p	£7.68	LONG PLAY		One	10	One	10	One	10	One	10	One	10	One	10			
C90	62p	£6.07	76p	£7.20	112p	£10.50	76p	£7.53	98p	£9.75	5 1/4" x 900'	£1.75	£17.00	£1.97	£19.00	—	—	—	—	£1.27	£12.65	£1.95	£19.10				
C120	82p	£8.14	1.09	£10.80	1.54	£15.40	1.08	£10.70	—	—	5 1/4" x 1200'	£2.20	£20.00	£2.25	£20.50	—	—	—	—	£1.60	£15.90	—	—				
											7" x 1800'	£2.75	£26.50	£3.10	£29.00	£3.20	£31.10	—	—	£2.19	£11.85	£2.90	£28.60				
											10 1/2" x 3600' NAB	—	—	—	—	—	—	—	—	£5.95	£59.00	—	—				
											10 1/2" x 4200' NAB	—	—	—	—	—	—	—	—	£5.20	£51.95	—	—				
											10 1/2" x 2400' 9NE	—	—	—	—	—	—	—	—	—	—	—	—				
PLASTIC SNAP PACK		TDK DYNAMIC		TDK Superb Dynamic		TDK Extra Dynamic		TDK CROZ		Agfa LH		DOUBLE PLAY		One		10		One		10		One		10			
C60	54p	£5.30	75p	£7.35	95p	£9.30	£1.20	£11.80	33p	£3.25	5" x 1200'	£2.20	£20.00	£2.35	£22.50	£1.95	£18.50	£1.49	£14.50	—	—	—	—				
C90	75p	£7.35	95p	£9.20	1.60	£15.70	1.60	£15.70	53p	£5.14	5 1/4" x 1800'	£2.85	£28.00	£3.50	£33.00	£2.50	£23.50	£2.19	£21.10	—	—	—	—				
C120	99p	£9.70	1.38	£13.50	—	—	—	—	73p	£7.20	7" x 2400'	£3.50	£34.00	£4.35	£41.00	£2.75	£26.50	£2.89	£28.85	£3.95	£35.60	—	—				
PLASTIC SNAP PACK		Agfa Super		Agfa CROZ		EMI Soundhog		EMI High Dynamic		EMI X1000 UD		TRIPLE PLAY		One		10		One		10		One		10			
C60	55p	£5.45	66p	£6.55	30p	£2.75	40p	£3.90	48p	£4.75	5 1/4" x 1800'	£2.95	£28.00	—	—	£2.50	£24.50	£2.46	£23.80	—	—	—	—				
C90	68p	£6.75	85p	£8.45	44p	£4.35	54p	£5.35	67p	£6.65	5 1/4" x 2400'	£3.50	£34.00	—	—	£3.10	£29.50	£2.96	£28.80	—	—	—	—				
C120	93p	£9.25	1.24	£12.35	—	—	66p	£6.55	—	—	7" x 3610'	£4.30	£42.00	—	—	£3.50	£32.50	£3.76	£35.50	—	—	—	—				
PLASTIC SNAP PACK		Philips LH		Scotch High Energy		Scotch CROZ		Scotch Classic		Maxell Super		REEL TO REEL		Memorex LH in Plastic Box		EMI-HMV High Output		TDK Audia LH Boxed		SPECIAL OFFER							
C60	41p	£4.05	—	—	—	—	£1.24	£12.00	55p	£5.45	5" x 900'	£1.30	£12.90	£1.40	£13.50	—	—	—	—	<p>FREE Cassette Head Cleaner with every C.A. cassette order over £15.</p>							
C90	57p	£5.65	85p	£8.45	98p	£9.75	£1.68	£16.75	69p	£6.30	5 1/4" x 1200'	£1.70	£17.00	£1.75	£17.00	—	—	—	—								
C120	78p	£7.75	—	—	—	—	—	—	94p	£8.50	7" x 1800'	£2.10	£20.95	£2.25	£22.00	£3.20	£30.50	£3.20	£30.50								
PLASTIC SNAP PACK		Maxell Ultra Dynamic		Fuji Super LN		Fuji Extra Dynamic		Pyral Hi-Fi LN		C-A De Luxe		DOUBLE PLAY		One		10		One		10		<p>MUSIC Cassettes and Cartridges</p> <p>Send large (9" x 4") SAE to R/C Dept. for catalogue</p>					
C60	78p	£7.20	43p	£4.20	40/63p	£6.28	35p	£3.45	47p	£4.60	5" x 1200'	£1.55	£14.90	£1.50	£14.95	—	—	—	—	<p>Prices shown include VAT at 8%, but are subject to change without notice. Mail Order Only - Cash with orders. For postage and packing, add 10p every 10 cassettes, 10p every reel-to-reel tape. Minimum 20p. Maximum 70p. Offers apply to U.K. Mainland only.</p> <p>CITY AUDIO, STRAND HOUSE GREAT WEST ROAD, BRENTFORD MIDDLESEX (Tel. 01-560 4191)</p>							
C90	1.00	£9.35	59p	£5.60	91p	£9.05	49p	£4.85	52p	£5.00	5 1/4" x 1800'	—	—	£1.90	£13.50	—	—	—	—								
C120	1.32	£11.20	80p	£7.95	—	—	64p	£6.38	71p	£7.00	7" x 2400'	£2.59	£25.00	£2.50	£24.95	—	—	—	—								
8-TRACK CARTRIDGES		BASF		Memorex		TDK		EMI		Scotch																	
40/45 mins.	£1.12	£10.70	£1.10	£10.70	40/£1.25	£11.60	89p	£8.60	£1.12	£10.60	<p>If you wish to use Barclaycard or Access, simply quote name, address and card number when ordering.</p>																
60/64 mins.	£1.25	£11.60	£1.25	£11.60	—	—	93p	£9.20	—	—																	
90/100 mins.	£1.42	£13.50	£1.42	£13.50	50/£1.65	£15.10	£1.95	£10.80	£1.35	£12.70																	

BI-PAK P.O. BOX 6 WARE, HERTS. SEMICONDUCTORS

POSTAGE & PACKING
Please add 25p. Overseas add extra for airmail. Minimum order 75p.

GREAT WINTER SALE!

SUCH REDUCED PRICES — IT'S CRIMINAL

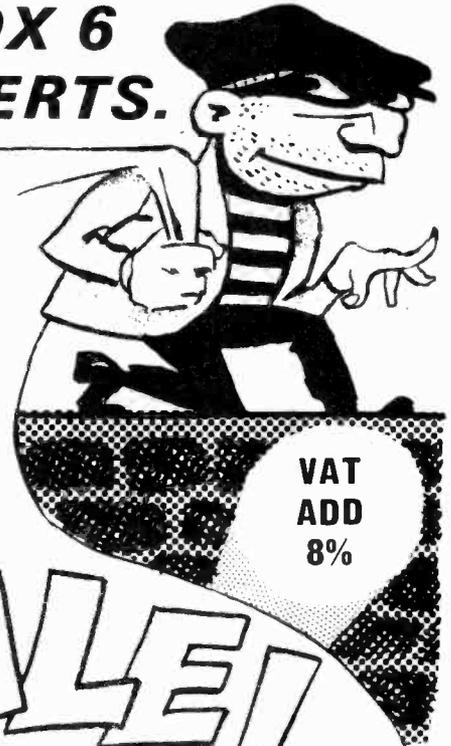

74 SERIES TTLIC's

TYPE	QUANTITY		TYPE	QUANTITY		TYPE	QUANTITY	
	1	100		1	100		1	100
	£ p.	£ p.		£ p.	£ p.		£ p.	£ p.
7400	0 08	0 07	7448	0 70	0 68	74122	0 42	0 40
7401	0 12	0 09	7450	0 12	0 10	74123	0 58	0 50
7402	0 10	0 09	7451	0 12	0 10	74141	0 62	0 60
7403	0 12	0 09	7453	0 12	0 10	74145	0 70	0 65
7404	0 10	0 09	7454	0 12	0 10	74150	1 30	1 25
7405	0 10	0 09	7460	0 12	0 10	74151	0 65	0 60
7406	0 28	0 25	7470	0 26	0 24	74153	0 65	0 60
7407	0 28	0 25	7472	0 22	0 20	74154	1 30	1 25
7408	0 14	0 10	7473	0 26	0 22	74155	0 65	0 60
7409	0 14	0 10	7474	0 27	0 23	74156	0 65	0 60
7410	0 08	0 07	7475	0 44	0 40	74157	0 90	0 80
7411	0 20	0 18	7476	0 28	0 25	74160	0 95	0 85
7412	0 20	0 18	7480	0 40	0 35	74161	0 95	0 85
7413	0 26	0 25	7481	0 95	0 90	74162	0 95	0 85
7416	0 28	0 25	7482	0 72	0 62	74163	0 95	0 85
7417	0 27	0 24	7483	0 80	0 68	74164	1 20	1 10
7420	0 10	0 09	7484	0 85	0 80	74165	1 20	1 10
7422	0 25	0 23	7485	1 20	0 95	74166	1 20	1 10
7423	0 26	0 24	7486	0 30	0 25	74174	1 00	0 90
7425	0 26	0 24	7489	2 70	2 50	74175	0 95	0 85
7426	0 26	0 24	7490	0 38	0 32	74176	1 00	0 95
7427	0 26	0 24	7491	0 60	0 50	74177	1 00	0 95
7428	0 36	0 34	7492	0 43	0 35	74180	1 00	0 95
7430	0 12	0 10	7493	0 38	0 35	74181	2 00	1 80
7432	0 25	0 22	7494	0 45	0 40	74182	1 00	0 90
7433	0 35	0 32	7495	0 58	0 50	74184	1 50	1 40
7437	0 25	0 22	7496	0 68	0 63	74190	1 40	1 30
7438	0 25	0 22	74100	1 00	0 90	74191	1 40	1 30
7440	0 12	0 10	74101	0 30	0 25	74192	1 10	1 00
7441	0 64	0 58	74105	0 30	0 25	74193	1 10	1 00
7442	0 60	0 52	74107	0 30	0 25	74194	1 00	0 95
7443	0 95	0 90	74110	0 50	0 45	74195	0 75	0 70
7444	0 95	0 90	74111	0 80	0 75	74196	1 00	0 95
7445	0 75	0 55	74118	0 90	0 82	74197	1 00	0 95
7446	0 95	0 85	74119	1 30	1 20	74198	1 90	1 80
7447	0 68	0 65	74121	0 26	0 25	74199	1 80	1 70

Devices may be mixed to qualify for quantity price. (TTL 74 series only) data is available for the above series of I.C.'s in booklet form. Price 35p.

SOCKETS

BPS8 9p BPS14 10p BPS16 11p

LINEAR IC

741P 8PIN 20p

TIMERS

NE555 42p DUAL NE556 85p

TRANSISTORS

TYPE	PRICE	TYPE	PRICE
AC128	10p	2N2217	15p
AC153K	18p	2N2218	14c
AC176K	20p	2N2218A	15p
AC153/176K		2N2219	14p
MP	38p	2N2219A	15p
AC187K	20p	2N2221	14p
AC188K	18p	2N2221A	15p
AC187K/188K		2N2222	14p
MP	38p	2N2222A	15p
OC71	9p	2N2369	12p
BC107	6p	2N2369A	12p
BC108	6p	2N2904	12p
BC109	6p	2N2904A	13p
BC118	8p	2N2905	13p
BC154	20p	2N2905A	10p
BC147	8p	2N2906	10p
BC148	8p	2N2906A	12p
BC149	10p	2N2907	11p
BC157	12p	2N2907A	13p
BC158	10p	2N2926G	9p
BC159	10p	2N2926Y	8p
BC169C	7p	2N3053	15p
BC170	5p	2N3055	40p
BC171	5p	2N3702	8p
BC172	5p	2N3703	8p
BC182 L&K	10p	2N3704	9p
BC183	10p	2N3705	8p
BC184	12p	2N3706	8p
BC212 L&K	10p	2N3707	7p
BC213	10p	2N3708	7p
BC214	12p	2N3709	7p
BC251	6p	2N3710	7p
BC327	12p	2N3711	7p
BC328	12p		
BC337	11p		
BC338	11p		
BF115	10p		
BF167	10p		
BF173	10p		
BF198	12p		
BF199	12p	2N3819	12p
BF194	9p	2N3903	8p
BF195	9p	2N3904	8p
BF196	11p	2N3905	9p
BF197	11p	2N3906	9p
BF257	22p	2N4058	8p
BF258	26p	2N4059	8p
BF259	30p	2N4060	9p
BFX29	18p	2N4061	9p
BFX84	15p	2N4062	9p
BFX85	20p	2N5172	9p
BFX86	16p		
BFY50	15p		
BFY51	15p		
BFY52	15p		
BFY53	14p		
2N696	10p		
2N697	11p		
2N706	6p		
2N706A	6p		
2N708	7p		
2N1613	15p		
2N1711	15p		
2N1893	18p		

DIODES

TYPE	PRICE
OA10	15p
OA47	5p
OA85-OA81	5p
OA91	5p
OA200/BAX13	5p
IN914	4p
IN4148	4p
IN4001	3p
IN4002	4p
IN4003	4p
IN4004	5p
IN4005	5p
IN4006	6p
IN4007	7p

S.C.R.'s

1A/50V TO5	15p
1A/400V TO5	25p
5A/50V TO66	25p
5A/400V TO66	40p

VOLTAGE REGS.

L129 (UA7805)	85p
L130 (UA7812)	85p
L131 (UA7815)	85p

L.E.D.

TIL209/FLV117	
RED	5 for 50p

F.E.T.

2N3819	12p
2N3903	8p
2N3904	8p
2N3905	9p
2N3906	9p
2N4058	8p
2N4059	8p
2N4060	9p
2N4061	9p
2N4062	9p
2N5172	9p


UNIUNCTION

UT46 = T1543	20p
ZTX300	5p
ZTX500	8p
ZTX107	5p
ZTX108	5p
ZTX109	5p



BI-PAK

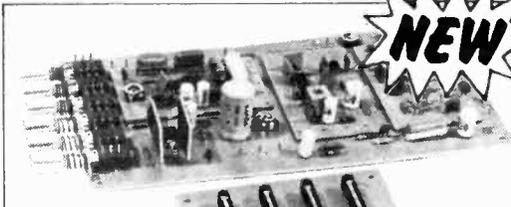High quality modules for stereo, mono and other audio equipment.



NEW

PUSH-BUTTON STEREO FM TUNER

Fitted with Phase Lock-loop


OUR PRICE ONLY
£19.95

The 450 Tuner provides instant program selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, by simply changing the settings of the pre-set controls. Used with your existing audio equipment or with the BI-KITS STEREO 30 or the MK60 Kit etc. Alternatively the PS12 can be used if no suitable supply is available, together with the Transformer T461. The S450 is supplied fully built, tested and aligned. The unit is easily installed using the simple instructions supplied.

- ★ FET Input Stage
- ★ VARI-CAP diode tuning
- ★ Switched AFC
- ★ Multi turn pre-sets
- ★ LED Stereo Indicator

Typical Specification:
Sensitivity 3µ volts
Stereo separation 30db
Supply required 20-30v at 90 Ma max.

MPA 30

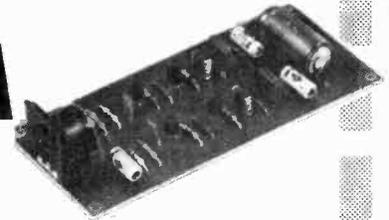

Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the new M.P.A. 30, a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only. It is provided with a standard DIN input socket for ease of connection. Full instructions supplied.

£2.65

STEREO PRE-AMPLIFIER




PA 100
OUR PRICE
£13.50

A top quality stereo pre-amplifier and tone control unit. The six push-button selector switch provides a choice of inputs together with two really effective filters for high and low frequencies, plus tape output.

MK. 60 AUDIO KIT: Comprising 2 x SPM80 1 x BTM80 1 x PA100 1 front panel and knobs. 1 Kit of parts to include on/off switch, neon indicator, stereo headphone sockets plus instruction booklet. **COMPLETE PRICE £27.55.**

TEAK 60 AUDIO KIT: plus 62p postage. Comprising Teak veneered cabinet size 16 3/4" x 11 1/2" x 3 3/4", other parts include aluminium chassis, heatsink and front panel bracket plus back panel and appropriate sockets etc. **KIT PRICE £9.20** plus 62p postage.

Frequency Response + 1dB 20Hz - 20KHz Sensitivity of inputs
1. Tape Input 100mV into 100K ohms
2. Radio Tuner 100mV into 100K ohms
3. Magnetic P.U. 3mV into 50K ohms
P.U. Input equalises to R1AA curve with 1dB from 20Hz to 20KHz
Supply - 20-35V at 20mA.
Dimensions - 299mm x 89mm x 35mm.

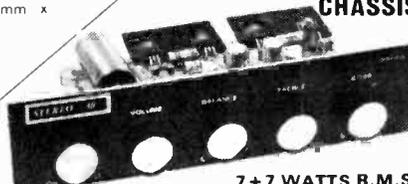

STEREO 30
COMPLETE AUDIO CHASSIS

7 + 7 WATTS R.M.S.

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This, with only the addition of a transformer or overwind will produce a high quality audio unit suitable for use with a wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo tape deck etc. Simple to install, capable of producing really first class results, this unit is supplied with full instructions, black front panel knobs, mains switch, fuse and fuse holder and universal mounting brackets enabling it to be installed in a record plinth, cabinets of your own construction or the cabinet available. Ideal for the beginner or the advanced constructor who requires Hi-Fi performance with a minimum of installation difficulty (can be installed in 30 mins).
TRANSFORMER £2.45 plus 62p p & p
TEAK CASE £3.65 plus 62p p & p.

£15.75

VAT ADD 25%

POSTAGE & PACKING
Postage & Packing add 25p unless otherwise shown. Add extra for airmail. Min. £1.00

AL10-20-30 AUDIO AMPLIFIER MODULES

Ideal for record players, recorders, stereo amplifiers, etc.

Harmonic Distortion $P_o = 3$ watts $f = 1$ KHz 02.5%

Load Impedance 8-16ohm
Frequency response ± 3 dB $P_o = 2$ watts 50Hz-25KHz

Sensitivity for Rated O/P - $V_s = 25$ v. $R_L = 8$ ohm $f = 1$ KHz 75mV. RMS

Size: 75mm x 63mm x 25mm

AL10 3w R.M.S. **£2.30**
AL20 5w R.M.S. **£2.65**
AL30 10w R.M.S. **£2.95**



AL 60 25 Watts (RMS)

★ Max Heat Sink temp 90C. ★ Frequency response 20Hz to 100KHz ★ Distortion better than 0.1 at 1KHz ★ Supply voltage 15-50v ★ Thermal Feedback ★ Latest Design Improvements ★ Load - 3,4,5, or 16 ohms ★ Signal to noise ratio 80db ★ Overall size 63mm. 105mm. 13mm.

Especially designed to a strict specification. Only the finest components have been used and the latest solid-state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast

£3.95

NEW

PA12

NEW PA12 Stereo Pre-Amplifier completely redesigned for use with AL10/20/30 Amplifier Modules. Features include on/off volume, Balance, Bass and Treble controls. Complete with tape output.

Frequency Response 20Hz-20KHz (-3dB). Bass and Treble range 12dB. Input Impedance 1 meg ohm. Input Sensitivity 300mV. Supply requirements 24V. 5mA. Size 152mm x 84mm x 33mm.

£6.50

PS12

Power supply for AL10/20/30, PA12, SA450 etc.

Input voltage 15-20v A.C. Output voltage 22-30v D.C. Output current 800 mA Max. Size 60mm x 43mm x 26mm.

OUR PRICE **£1.20**
Transformer T538 **£2.30**

Stabilised Power Supply Type SPM80


SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watts (R.M.S.) per channel simultaneously. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5A at 35V. Size 63mm. 105mm. 30mm. Incorporating short circuit protection.

Transformer BMT80 **£2.60 + 62p postage**

£3.00

BI-PAK

P.O. BOX 6, WARE, HERTS.

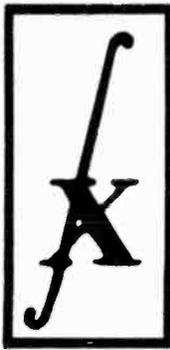

Wireless World Dolby™ noise reducer

Trademark of Dolby Laboratories Inc.

We are proud to announce the latest addition to our range of matching high fidelity units.

Featuring:

- switching for both encoding (low-level h.f. compression) and decoding
- a switchable f.m. stereo multiplex and bias filter
- provision for decoding Dolby f.m. radio transmissions (as in USA)
- no equipment needed for alignment
- suitability for both open-reel and cassette tape machines
- check tape switch for encoded monitoring in three-head machines

The kit includes:

- complete set of components for stereo processor
- regulated power supply components
- board-mounted DIN sockets and push-button switches
- fibreglass board designed for minimum wiring
- solid mahogany cabinet, chassis, twin meters, front panel, knobs, mounting screws and nuts

Typical performance

Noise reduction: better than 9dB weighted

Clipping level: 16.5dB above Dolby level (measure of 1% third harmonic content)

Harmonic distortion 0.1% at Dolby level typically over most of band, rising to a maximum of 0.12%.

Signal-to-noise ratio: 66dB (20Hz to 20kHz, signal at Dolby level)

30mV sensitivity.

PRICE: £34.40 + VAT

Calibration tapes are available for open-reel use and for cassette (specify which) **Price £1.80 + VAT***

Single channel plug-in Dolby™ PROCESSOR BOARDS (92 x 87mm) with gold plated contacts are available with all components **Price £6.50 + VAT**

Single channel board with selected fet. **Price £2.00 + VAT**

Gold plated edge connector **Price £1.27 + VAT***

Selected FET's **54p** each + VAT, **96p** + VAT for two, **£1.76** + VAT for four

Please add VAT at 25% unless marked thus*, when 8% applies
We guarantee full after sales technical and servicing facilities on all our kits



INTEGREX LTD.


Please send SAE for complete lists and specifications
**Portwood Industrial Estate, Church Gresley,
Burton-on-Trent, Staffs DE11 9PT
Tel. Swadlincote (0283 87) 5432. Telex 377106**

INTEGREX

S-2020TA STEREO TUNER / AMPLIFIER KIT

SOLID MAHOGANY CABINET

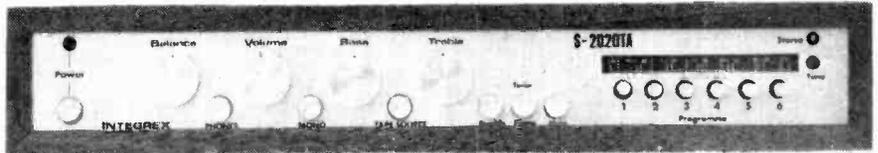A high-quality push-button FM Varicap Stereo Tuner combined with a 20W r.m.s. per channel Stereo Amplifier.



Brief Spec. Amplifier: Low field Toroidal transformer, Mag. input, Tape In / Out facility (for noise reduction unit, etc), THD less than 0.1% at 20W into 8 ohms. All sockets, fuses, etc., are PC mounted for ease of assembly. Tuner section: uses Mullard LP1186 module requiring no RF alignment, ceramic IF, INTERSTATION MUTE, and phase-locked IC stereo decoder. LED tuning and stereo indicators. Tuning range 88—104MHz. 30dB mono S/N @ 1.8µV. THD typ. 0.4%

PRICE: £48.95 + VAT

NELSON-JONES STEREO FM TUNER KIT

A very high performance tuner with dual gate MOSFET RF and Mixer front end, triple gang varicap tuning, and dual ceramic filter / dual IC IF amp.




Brief Spec. Tuning range 88—104MHz. 20dB mono quieting @ 0.75µV. Image rejection — 70dB. IF rejection—85dB. THD typically 0.4% IC stabilized PSU and LED tuning indicators. Push-button tuning and AFC unit. Choice of either mono or stereo with a choice of stereo decoders.

Compare this spec. with tuners costing twice the price

Mono £26.31 + VAT

With ICPL Decoder £30.58 + VAT

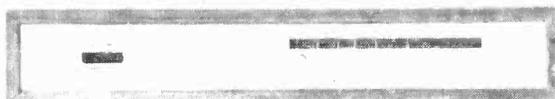**With Portus-Haywood Decoder
£32.81 + VAT**



Sens. 30dB S/N mono @ 1.8µV
THD typically 0.4%
Tuning range 88—104MHz
LED sig. strength and stereo indicator

STEREO MODULE TUNER KIT

A low-cost Stereo Tuner based on the Mullard LP1186 RF module requiring no alignment. The IF comprises a ceramic filter and high-performance IC Variable INTERSTATION MUTE. PLL stereo decoder IC

PRICE: Mono £25.55 + VAT

Stereo £28.65 + VAT

S-202A AMPLIFIER KIT

Developed in our laboratories from the highly successful "TEXAN" design. PC mounting potentiometers, switches, sockets and fuses are used for ease of assembly and to minimize wiring



Typ. Spec. 20+20W r.m.s. into 8-ohm load at less than 0.1% THD. Mag. PU input S/N 60dB. Radio input S/N 72dB. Headphone output. Tape In / Out facility (for noise reduction unit, etc.). Toroidal mains transformer.

PRICE: £30.94 + VAT

ALL THE ABOVE KITS ARE SUPPLIED COMPLETE WITH ALL METALWORK, SOCKETS, FUSES, NUTS AND BOLTS, KNOBS, FRONT PANELS, SOLID MAHOGANY CABINETS AND COMPREHENSIVE INSTRUCTIONS

BASIC NELSON-JONES TUNER KIT . . . £13.13 + VAT
BASIC MODULE TUNER KIT (Mono) . . . £13.25 + VAT
BASIC MODULE TUNER KIT (stereo) . . . £15.25 + VAT

PHASE-LOCKED IC DECODER KIT . . . £4.47 + VAT
PUSH-BUTTON UNIT . . . £3.50 + VAT

PORTUS-HAYWOOD PHASE-LOCKED STEREO DECODER KIT . . . £7.93 + VAT

WW—077 FOR FURTHER DETAILS

ELECTRONIC BROKERS

Electronic Brokers Ltd. are one of the leading electronic instrumentation companies in the UK, providing a full range of services to Universities, Industry, Colleges and Governments both at home and overseas.

We have the largest stocks of secondhand test equipment in Europe as well



as a selected range of new products. These are on display at our London showrooms where customers can examine the equipment of their choice and see it working.



Electronic Brokers Ltd. have fully equipped workshops on the premises to test and report on the majority of equipment we sell.



TELEPHONE TEST EQUIPMENT

WANDEL & GOLTERMAN
Level Transmitter TFPS 42 10KHz-14MHz £375
Level Meter TFFM 43 10KHz-14MHz £376

Wandel & Golterman VZM 2 Distortion measuring set for phase and amplitude mod. For multichannel FM Radio Systems up to 12MHz base bands £350

SIEMENS
Level Meter 3D 332 D.3-1200KHz £250
Level Meter 3D 335 10KHz-17MHz £300
Level Oscillator 3W29 0.3-1200KHz £250
Level Oscillator 3W518 £300

PULSE GENERATORS

ADVANCE
Double Pulse Generator PG 56 Pulse Amplitude 0.1V-10V Sq wave 0-10V Rise Time 10nsec (typical) £87.50 P.O.A.
Pulse Generator PG 55 £90 P.O.A.
Modular Pulse Generator Advance Type PG 52 System of 5 Signal Generating & Processing Units. Repetition freqs. up to 20MHz & Output Pulses to 20V (50ohms) Rise & Fall times 5nsec. Its versatility enables the production of complex pulse & ramp waveforms not obtainable from pulse generators £250

SIGNAL SOURCES

MARCONI INSTRS.
F.M./A.M. Signal Generator TF 995A/3S. Ministry type No. CT402 1.5MHz-220MHz R.F. o/p 2µV-200mV Internal & External Mod. Facilities. V. good condition. F.M./A.M. Signal Generator TF 995A/5 1.5-220MHz in 5 bands 0.1µV-200mV F.M. up to ±120KHz from 50Hz-15KHz. A.M. up to 50% from 100Hz-10KHz o/p (1) 2µV-200mV (2) with terminating unit 1µV-100mV Int. mod. freqs. 400Hz, 1KHz & 1.5KHz. Distortion (1) on internal F.M. ±25Hz (2) on internal A.M. 6% at 30% mod. £300 to £350
A.M. Signal Generator TFB01D/1 Freq. range 10-470MHz R.F. output 0.1µV-1V. Piston attenuator 50ohms impedance. Modulation Int. A.M. 1KHz Ext. A.M. 30 Hz-20KHz. Low spurious F.M. & drift. V.S.W.R. 1.2 or less £400-£800
A.M. Signal Generator TFB01D/1S Military Version 10.485MHz £450-£800
R.C. Oscillator TE1101 Superb Condition 20Hz-200KHz 60dB Attenuator. Output continuously variable up to 20V £220
R.C. Oscillator TF1370A 10Hz-10MHz Square Wave up to 100KHz High Outputs up to 31.6V £285
R.C. Oscillator TF1370 £90
Phase/A.M. Signal Generator TF 2003 0.4-12MHz £150

HEWLETT PACKARD
F.M./A.M. Signal Generator 202H F.M. A.M. CW & pulse coverage 54 to 216 MHz R.F. o/p 0.1µV-0.2V 50ohms Impedance £450
Univert 207H for use with above £100
U.H.F. Signal Generator 612A 450-1200MHz £495
V.H.F. Signal Generator 608E 10-480MHz (5 band) Accuracy ±0.5% o/p 0.1µV-1V (variable) 50ohms. Int. A.M. 400 & 1000Hz Ext. A.M. 20Hz-20KHz Superb condition £895

OSCILLOSCOPES

ADVANCE
OS 2000 Scope c/w OS 2002Y & OS 2003X Plug ins £215

MARCONI
Portable Scope TF 2203 DC-15MHz 50mV/cm £115
T.V. Scope TF 2200A/1 c/w TV Diff Plug in TM 6457A OC-30MHz £190

PHILIPS
Oscilloscope PM 3250/02 DC-50MHz £395

SOLARTRON
Portable Scope DC-6MHz Double Beam £90
Solarscope CD 1016 NS 10 DC-5MHz Double Beam Suitable for TV Servicing £90
Portable Scope CD 1400 DC-15MHz Plug ins available CX 1441, 1443, 1444 £175

HEATHKIT
10-12µ Scope Single Beam 50mV/cm DC-45MHz 5" Tube Assembled Refurbished Our price £49.50

ROBAND
25MHz Scope R 050 c/w 5C Plug in £200
25MHz Scope R 050A c/w 5C Plug in £225

VOLTMETERS

SIGN ELECTRONICS
A.F. Voltmeter AM324 £60
HF Millivoltmeter Philips Type GM 8014 Ranges 1mV-300mV in 6 Ranges. Facility also for 100mV-30V. Meter equipped with dB scale. Accuracy at 30KHz less than 3% F.S.D. Amplitude characteristic flat within ±5% £55

HEWLETT PACKARD
DC Vacuum Tube Voltmeter 412A 1mV-1000V 1% Accuracy. Can also be used as Ohmmeter & Ammeter £75
VTVM 4000 1mV to 300V FSD 12 ranges 10Hz to 4MHz 2% accuracy. Input Impedance 10Mohms £85
VTVM 400L Logarithmic version of 4000 Reads RMS value of sine wave. Log. voltage scale 0.3 to 1 & 0.8 to 3. Linear dB scale. Input Impedance 10Mohms £90

MARCONI
Sensitive Valve Voltmeter TF 1100 100µV-300V AC Freq. coverage 10Hz-10MHz. Meter has dB scale facility £85

ADVANCE
778 AC Millivoltmeter 50Hz-4.5MHz 0.001V to 300V FSD Input Impedance 10Mohms £42
Voltmeter VM 90 AC Volts 0-500V (ranges 6) DC Volts 0-1.5KV 7 ranges Resistance 0-1000Mohms £45

FLUKE
A.C./D.C. Differential Voltmeter 803 0-500V Null Ranges 10 1 0.1 & 0.01V £125
Differential Voltmeter 821A For calibration, testing, stability measurements of regulated power supplies. DC Voltmeter calibration ±0.01% absolute accuracy infinite input resistance at null over entire 0-500V range standard cell reference. Polarity switch. In-line readout with automatic lighted decimal. No zero controls. Usable as conventional V.T.V.M. (3% FSD) £165

MISCELLANEOUS

BECKMAN
Transfer Oscillator 7580H DC-15GHz with counter. 7.5MHz-15GHz without counter. Sensitivity 100mV (R.M.S.) £350

AIRMEC
Modulation Meter 210 £75 to £100

BELL
Gaussmeter Type 120, complete with Probes P.O.A.

GENERAL RADIO
Immittance Bridge 1607A Immaculate Condition in Wooden Transit Case £1000

HEWLETT PACKARD
Distortion Analyser 331A £210
Digital Recorder 560A £110
Digital Recorder 561B £140

MARCONI INSTRS.
Attenuator TF 1073A 25 £85
Distortion Factor Meter TF 2331 Brand New Condition £300
Blank & Sync. Mixer TF 2908 £90
Quantization Distortion Tester TF 2343 P.O.A.
R.F. Power Meter TF 1152/1 £75

RADIOMETER
Stereo Signal Generator SMG 1 P.O.A.
RHODE & SCHWARTZ
Stereo Coder MSCBN 4192/2 P.O.A.
TELEVIC
Sweep Generator SM 2000 c/w Plug Ins E-3M, S-6 & S-4M P.O.A.
SIGN ELECTRONICS
Distortion Factor Meter DM 344A £160
ADVANCE
Digital Multimeter DMU 3 c/w Battery Pacil £110

COMPONENTS

Numeric Tube B 5853 0-9 Digit 1.4" height Brand new £1
Also Alpha Numeric Nixie Tube B 7971 Displays alphabet & 9-0 numerals 99p

SELF-SCAN

Panel Display Model SSD 1000-0030 Direct Visual Presentation of Alpha-Numeric Data

Each panel is a self-contained package, providing 16 to 18 display positions, each of which may be instructed by a 6-bit coded signal to display one of 64 pre-programmed characters as a 5 x 7 dot-matrix formed by special gas discharge units. Each character is 0.4 inches high providing a bright image, visible over a wide viewing angle.


Full applications data is available, giving all necessary information.

Abridged Specification
Size: 8 1/2" x 2 1/4" x 1 1/2" approx.
Input signals: 6 bit data, clock, reset etc.
Power Supplies: +5v, -12V & +250v.

Auxiliary data input available to permit generation of additional symbols etc.

Internal repertoire: A to Z, 1 to D, @, #, /, % = - etc.

Brand New £60
Secondhand £50
P&P £2

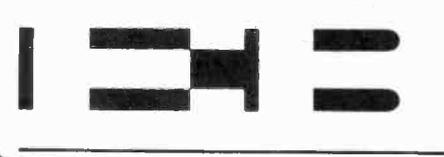

ELECTRONIC

A member of the EB group

ADD 8% VAT TO ALL PRICES

the test equipment people



On these pages you will find just the briefest selection from the vast range which we hold in stock at any one time.


If you are seeking a specific item and it is not listed, it will pay you to ring us first — we believe we offer the best prices and the best service. **WORLD WIDE EXPORT.**

Enquiries and tenders welcome from any part of the world.

HOW TO REACH US

We are easy to reach, no matter where you live. Minutes away from Kings Cross or St. Pancras main-line stations, and a bus ride from Euston; only just over half an hour from Heathrow Airport. Parking is easy too.

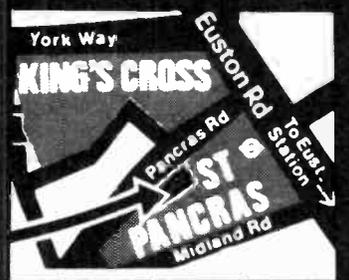49-53 Pancras Road, London NW1 2QB
Tel: 01-837 7781



MULTIMETERS

SUPER TESTER 680R ICE
 20,000 Ghm per Volt Sensitivity. Fully screened against external magnetic fields. Scale width and small case dimensions (128 x 95 x 32 mm). Accuracy and stability (1% in D.C., 2% in A.C.) of indicated reading. Simplicity and ease of use and readability. Full ranges of accessories. 1000 times overload. Printed circuit board is removable without de-soldering. More ranges than any other meter. Ask for free catalogue. **£18.50**

Dimensions: 13 x 13 x 120 mm (including 15 mm prod tip)
 Weight: 20 gm approx



Technical Description
 The I.C.E. Signal Injector Model 63 is a compact, self-powered unit which has been designed to assist the electronics and radio-technician in fault-finding in both vacuum-tube and transistorised equipment. It is particularly valuable in the location of failures in radio receivers amplifiers etc.

A small, hand-held, moulded plastic body contains the transistorised oscillator circuit its 1.5v cell, and is fitted with a conductive prod-tip for application to the circuit under test. A thumb-operated spring-loaded button permits application of power to the oscillator, at will, thus conserving battery life.

The circuit of the Signal Injector Model 63 incorporates two transistors and two inductors in a blocking-oscillator configuration which produces two basic frequencies namely 500 and 1 kHz, of nominally rectangular waveform of fast rise-time, so containing high-order harmonics covering a wide frequency spectrum.

£5.95. P&P 40p.

FANTASTIC NEW MICROTEST 80

MEASURES ONLY
 90 x 70 x 18mm
 Electronic zero Ω



Amazing Value at £11.95
 3 fields of measurement and 40 ranges

PRINTED CIRCUIT BOARD IS REMOVABLE WITHOUT SOLDERING


Volts d.c. 6 ranges: 100mV, 2V, 10V, 50V, 200V, 1,000V (20k Ω/V) 2% precision on d.c. and a.c.
Volts a.c. 5 ranges: 1.5, 10V, 50V, 250V, 1,000V (4k Ω/V)
Amp. d.c. 6 ranges: 50 μ A, 500 μ A, 5mA, 50mA, 500mA, 5A
Amp. a.c. 5 ranges: 250 μ A, 2.5mA, 25mA, 250mA, 2.5A
Ohms 4 ranges: Low Ω x 1 Ω x 10, Ω x 100 (from 1 Ω to 5M Ω)
V Output 5 ranges: 1.5V, 10V, 50V, 250V, 1,000V
Decibels 5 ranges: +6dB, -22dB, +36dB, +50dB, +62dB
Capacity 4 ranges: 25 μ F, 250 μ F, 2,500 μ F, 25,000 μ F

Accessories (extra) available to convert Microtest 80 & Super tester 680R into following: **SIGNAL INJECTOR, GAUSS METER, ELECTRONIC VOLTMETER, AMPER-CLAMP, TRANSISTOR TESTER, TEMPERATURE PROBE, PHASE SEQUENCE INDICATOR** — Send for details

I.C.E. Signal Injector, Model 63
 Data Summary
 Basic Output
 Frequencies: 500 kHz & 1 kHz
 Power Supply: Internal 1.5v cell VARTA 245 1ECR1 (for equivalent)

MORE RANGES FOR LESS MONEY!

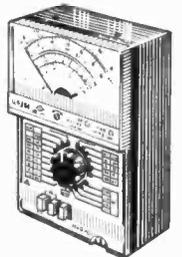
AC/DC Multimeter type UA324
 A DC 0.05-3A — 6 Ranges
 A-AC 0.3A — 5 Ranges
 V-DC 0.6-1200V — 9 Ranges
 V-AC 3-900V — 8 Ranges
 Free: in the range of 45 to 20kHz. Resistance 500 ohm to 5 Mohm — 5 Ranges
 Decibel — 10 to +12dB Accuracy $\pm 2.5\%$



All above Multimeters are brand new

DC $\pm 4\%$ AC
 Dimensions 167 x 98 x 63mm
 Only **£9.75.**
 POST & PACKING 60p

Shown on these pages are just a few samples of our huge stock. If the item you require is not shown please give us a ring.

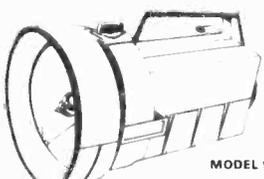

MODEL 964

STROBETTE STROBOSCOPE TACHOMETER

Two Units in One
SOME SPECIFIC APPLICATIONS
 ● To check and analyze motion while designing data processing units
 ● To check register in printing presses
 ● To check balance in balancing machines
 ● To check speed of motors, gear reducers, etc.
 ● To check speed of pulleys, gears, fans, shafts or anything that rotates over 200 RPM
 ● To observe motion of packages, bottles, cans, envelopes, etc., while they are being manufactured
 ● To observe belt slippage
 ● To demonstrate strobe action to students

SPECIFICATIONS
STROBOSCOPIC FLASH RATE — 200 to 6,000 flashes per minute
TACHOMETER SPEED RATE — 200 to 6,000 RPM
ACCURACY — 3% better
CALIBRATION — At 3,600 F.P.M. against any known synchronous speed — 7200, 3600, 1800, 1200, 900 RPM, etc.
CIRCUITRY — 100% solid state
FLASH DURATION — Approximately 10 to 25 microseconds
FLASHLIGHT COLOR — Xenon white 6,500 K
FLASH ENERGY — 40 Watts second (Joules)
DUTY CYCLE — Below 1,000 F.P.M. = 30 minutes
 1,000 to 3,600 F.P.M. = 1/2 duty cycle
 3,600 F.P.M. and above = 1/4 duty cycle
BEAM ANGLE — 80°
PHYSICAL — High impact case. Plastic lens. Mirror type reflector.
SIZE — 3" x 3" x 7" with 4" diameter reflector
WEIGHT — 27oz (76 Kg) Shipping weight 4 lb (1.8 Kg)
TRIPOD MOUNTING — Built-in 1/4-20 thread tripod socket.
POWER — 220 VOLTS 50/60 Hz 22 watts

FANTASTIC VALUE £49.50



NEW!

Only **£89.50**

"TOUCHLESS" RETRO-REFLECTIVE TACHOMETER

FEATURES
 ● Reads RPM from as far as 24" away!
 ● Four ranges 0-1,000, 3,000, 10,000, 30,000 RPM
 ● Instant field calibration
 ● Reads low or high speed on any type of machinery
 ● Battery powered — Built-in voltage checker
 ● Touchless — (no torque loss) measurements
 ● Direct reading mirror type scale
 ● Hand portable (only 32 oz) (0.9 Kg)
 ● Accuracy 1 1/2% of full scale
 ● Aluminium case — baked enamel finish
 ● Reads on marked shafts as small as 1/16" diameter
 ● Marking tape provided
 ● Complete solid-state circuitry
 ● Push-button reading
 ● Hidden probe cable extends to 24" (60cm)

SPECIFICATIONS
Photocell: Photo transistor **Lamp:** GE No. 222X
Batteries: One 5.4 V type TR-134R Except Model B 912 **Accuracy:** 1 1/2% of full scale **Meter:** Shock-proof movement, large clear-face dial
Calibration: From any fluorescent light 50 to 60 cycles **Dimensions:** 5 1/2" (130.0 mm) wide 7 1/2" (190.0 mm) high, 2 1/2" (63.5 mm) deep

Carrying case **£12.50**

BROKERS LTD

Carriage and packing charge extra on all items unless otherwise stated.

Please note: All instruments offered are secondhand and tested and guaranteed 12 months unless otherwise stated.

HIGH POWER BATTERY MOTOR

6v/12v operated. Strong enough to power a motor mower, go-cart or similar. Speed easily variable. Series wound, so virtually impossible to stop, very hard duty. Snp at **£3.50**. VAT and postage 85p.
Less powerful 12 volt motor suitable for fan or heater. **£2.00**. Post and VAT 65p.

MAINS TRANSISTOR PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v, 9v, 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries PP1, PP3, PP4, PP6, PP7, PP9 and others. Kit comprises main transformer, rectifier, smoothing and load resistor, condensers and instructions. Real snip at only **£1.50**. VAT and Postage 60p.

MULTI-SPEED MOTOR

Six speeds are available 500, 850, and 1 100 r.p.m. and 8 000 12 000 and 15 500 r.p.m. Shaft is 1/4in diameter and approximately 1 in long. 230/240v. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor size approx 2 in dia x 5 in long. Price **£1.40** + 45p post & VAT.

DC HIGH CURRENT PANEL METERS

3 1/2" wound wide angle 240 movement meters flush mounting fitted with external shunts made by Crompton Parkinson brand new still in makers cartons. These are a real bargain at **15 50** each. Reasonable quantities available in the following ranges 0-10 amps, 0-20 amps, 0-30 amps, 0-40 amps, 0-50 amps. Post and VAT 80p each.

TAPE DECK

In metal case with carrying handle heavy fly wheel and capstan drive. Tape speed 3 1/4. Mains operated on metal platform with tape head and guide. Not new but guaranteed good working order. Price **£1.50** plus VAT and Postage 1 50.

SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1 2 or 3 lamps (maximum 450w). Unit in Box all ready to work. **£7.95** plus 95p VAT and postage.

OVEN THERMOSTAT

Made by the famous Diamond H Company this has a sensor joined by a capillary to a variable control and when fitted with a knob is ideal for many ovens or processes. 50p each + post and VAT 15p.

HONEYWELL PROGRAMMER

This is a drum timing device, the drum being calibrated to equal divisions for switch-setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips, thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting, animated and signs, Signalling, etc. Price from makers probably over £20 each. Special snip price **£9.95**. £1 00 Post and VAT. Don't miss this terrific bargain.

BREAK-DOWN UNIT

Contains hundreds of useful parts some of which are as follows — 66 silicon diodes equivalent OA 91 68 resistors mostly 1/2 watt 5%, covering a wide range of values 4 x 1 mfd 400v mfd condensers 15 x 01 mfd 100v condensers 2 RF chokes 8 x B9 valve holders 1 x 4H choke 1 x 115v transformer 1 boxed unit containing 4 delay lines also tag panels trimmer condensers suppressors etc. on a useful chassis sized approx 9" x 5" x 7". Only 75p (the 66 diodes would cost at least 10 times this amount). This is a snip not to be missed. Post and VAT 75p.

THIS MONTH'S SNIP

MULLARD UNILEX

A mains operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost any one. In easy-to-assemble modular form and complete with a pair of Goodmans speakers this should sell at about £30 — but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only **£15.50** including VAT and postage.

GPO PUSH BUTTON DIALLING UNIT

Will take the place of the normal rotating dial. Has 10 numbered keys so suitable for other digital systems. A desk mounting unit with rubber feet. This is a very intricate and expensive piece of apparatus. New and unused — our price only **19** each + £1 36 post and VAT.

TWIN OUTPUT POWER PACKS

These have two separately R.C. smoothed outputs so can operate two battery radios on a stereo amp without cross modulation (they will of course operate one radio/tape/cassette/calculator, in fact any battery appliance, and will save their cost in a few months). Specs: Full wave rectification double insulated mains transformer — total enclosed in a hard P.V.C. case — three core mains lead-terminal output — when ordering please state output voltage 4 1/2v, 6v, 7 1/2v, 9v, 12v or 24v. Price **£3.95**, Post and VAT included.

TERMS Where order is under £5 please add 30p surcharge to offset packing expenses.

J. BULL (ELECTRICAL) LTD.

(Dept. W.W.), 103 TAMWORTH ROAD, CROYDON CRO IXX

YOU MAY BE IN TIME

For a valve volt-meter at **£7.50** — a signal generator at **£8.50**, an oscilloscope at **£12.50** — a frequency standard at **£18.50** as these and many other good buys were offered in our December Advanced Advertising News. Send S.A.E. for a copy today. Subscribers received this list at least a month ago, chances are best buys will have been snapped up, so whilst writing why not send a few stamped envelopes and receive these newsletters directly they are printed.

MAINS TRANSFORMERS

All standard 230-250 volt primaries

1v	1 amp (special)	1.75
2 4	5 amp	.85
6 3v	2 amp	1.25
9v	3 amp	1.75
12v	1 amp	.95
9v	3 1/2 amp	2.50
12v	1 1/2 amp	1.50
12v	1 amp	1.00
6 5v-0 6 5v	1 amp	1.50
18v	1 amp	1.50
24v	2 amp	2.25
24v	3 amp	3.50
12 0 12v	50mA	1.20
6 0 6v	50mA	1.20
8 0 8v	1 1/2 amp	1.50
18 0 18v	2 amps	3.50
25v	1 1/2 amp	1.95
50v 2 amp & 6 3v	1 amp	4.50
60v 5 amp & 5v	1 amp	7.50
27v	8 amp	4.50
30v	3 1/2 amp	22.00
80v tapped 75v & 70v	4 amp	5.50
230v 60mA & 6 3v	1 1/2 amp	1.75
275 0 275v at 30mA & 60v	3 amps	2.25
EHT Transformer 5000v 23mA (intermittent)		5.50
Charger Transformers		
6v and 12v	2 amps	1.50
6v and 12v	3 amps	2.25
6v and 12v	5 amps	3.50

Add 30p per l. to cover postage and VAT 25%.
And 25% except for industrial types.

ONLY £1.50 FOR SEVEN ELECTRIC MOTORS

7 powerful batt. motors as used in racing cars and power models. Output and types vary for use in hundreds of projects. Tools toys models etc. All brand new reversible and for 1 1/2 12v batts. Wiring diag. inc. VAT & Post 40p. FREE plan for min power station.

1 R.P.M. MOTOR & GEAR BOX

Made by the famous Chamberlain & Hookham Ltd. These could be made to drive clock or similar. Really robust reliable unit. Price **£1.50** + 30p post & VAT.


BLACK LIGHT

As used in discotheques and for stage effects etc. Virtually no white light appears until the rays impinge on luminous paint or white shirts etc. We offer 9" 6w tubes complete with starter, choke, lamp-holders and starter holder. Price **£2.75** + 30p post. Tubes only **£2**. Post & VAT 50p.
230 volt/175 watt model **£6.50**. Post & VAT 92p.

Relays

Co-ax Relays for Aerial Switching

951 Magnetic Devices Relay

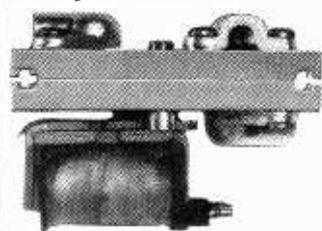

SPECIAL OFFER

£5 each

Inc. P & P and VAT

When ordering specify operating voltage required

Cash with order

- Available with 12V or 24V DC coil
- Single Change-over contact
- For use with UR43 co-ax cable
- Characteristic impedance 50 ohms
- Nominal frequency 450 MHz
- VSWR approx. 1.1 : 1
- Cross-talk 39dB
- Contact rated at 1 amp or 50W max

REL Equipment & Components Ltd.

Components Division
Croft House, Bancroft, Hitchin, Hertfordshire, SG5 1BU, England
Telephone: (0462) 50551/2/3 · 52202 · 52776/7/8/9 Telex: 82431

WW — 049 FOR FURTHER DETAILS

The

'MISTRAL' Digital Clock

* A Complete Kit *
or fully built



Kit **£12.50** (incl)

Built **£18.00**.

- Pleasant green display
- 24 Hour readout
- Silent Synchronous Accuracy
- Fully electronic
- Pulsating colon
- Push button setting
- Building time 1Hr
- Attractive acrylic case
- Easy to follow instructions
- Size 10.5 x 5.7 x 8 cm
- Ready drilled PCB to accept components

Even in the kit — this unique transformerless design at a substantial saving on retail price. The kit is complete — less mains lead — all you require is a soldering iron, solder, and screw driver to assemble your own digital clock.



EXETRON Time Ltd
Regal House,
Penhill Road,
LANCING, Sussex.

Payment: CWO, Cheque, Access, Barclaycard. (quote Number)

NEW PRODUCTS

PROTO BOARDS

Build & test circuits as fast as you think!

PB100	10 IC cap breadboard kit, 4.5 x 6.0 x 1.3"	£17.45
PB101	10 14-DIP cap, 5-way post, 940 solderless tie points, 5.8 x 4.5"	£26.15
PB102	12 14-DIP cap, like PB101 with 1,240 tie points, 7.0 x 4.5"	£34.90
PB103	24 14-DIP cap, 4 5-way posts, 2,250 tie points, 6.0 x 9.0"	£52.35
PB104	32 14-DIP cap, 3 060 solderless tie points, 8.0 x 9.76"	£69.80

LOGIC MONITOR
Simultaneously displays static and dynamic logic states of DTL, TTL, HTL or CMOS DIP ICs. Pocket size. **£59.95**

PROTO-CLIP
For power on/hands off signal tracing. Bring IC leads up from PC board surface for fast trouble shooting.
PC14 14-pin **£3.25**
PC16 16-pin **£3.40**

SOCKETS & BUS STRIPS

Plug-in, wire, test, modify or expand without patch cords or solder. Snap together to form breadboard needed.

PN/Description	Hole-to-Hole	Term's	Price
QT59S Socket	6.5"	6.2" 118	£10.90
QT59B Bus	6.5"	6.2" 20	£2.20
QT14S Socket	5.3"	5.0" 94	£8.75
QT47B Bus	5.3"	5.0" 16	£2.00
QT15S Socket	4.1"	3.8" 70	£7.45
QT35B Bus	4.1"	3.8" 12	£1.75
QT19S Socket	2.4"	2.1" 36	£4.15
QT11S Socket	1.8"	1.5" 24	£3.30
QT8S Socket	1.4"	1.1" 16	£2.85
QT7S Socket	1.3"	1.0" 14	£2.65

7400 Series TTL

SN7400	1	25	100+	SN7494	0.48	0.45	0.40
SN7401	0.14	0.13	0.12	SN7495	0.60	0.56	0.50
SN7402	0.14	0.13	0.12	SN7496	0.70	0.67	0.60
SN7403	0.14	0.13	0.12	SN7497	0.70	0.69	0.68
SN7404	0.15	0.14	0.13	SN74100	1.35	1.30	1.25
SN7405	0.15	0.14	0.13	SN74104	0.31	0.29	0.26
SN7406	0.30	0.29	0.28	SN74105	0.31	0.29	0.26
SN7407	0.30	0.29	0.28	SN74107	1.00	0.97	0.95
SN7408	0.15	0.13	0.12	SN74110	0.52	0.50	0.45
SN7409	0.15	0.13	0.12	SN74111	0.81	0.80	0.76
SN7410	0.14	0.13	0.12	SN74114	1.00	0.97	0.95
SN7411	0.23	0.22	0.21	SN74115	1.00	0.97	0.95
SN7412	0.19	0.18	0.17	SN74118	1.00	0.95	0.90
SN7413	0.30	0.29	0.28	SN74121	0.31	0.29	0.25
SN7414	0.71	0.70	0.69	SN74122	0.44	0.41	0.37
SN7415	0.30	0.29	0.27	SN74123	0.62	0.58	0.50
SN7416	0.28	0.27	0.26	SN74125	0.70	0.65	0.60
SN7417	0.28	0.27	0.26	SN74126	0.75	0.70	0.65
SN7420	0.14	0.13	0.12	SN74128	1.40	1.35	1.30
SN7421	0.95	0.94	0.93	SN74132	2.10	2.05	2.00
SN7422	0.25	0.24	0.23	SN74136	0.95	0.90	0.85
SN7423	0.25	0.25	0.22	SN74140	2.50	2.45	2.40
SN7425	0.26	0.25	0.22	SN74141	0.75	0.70	0.62
SN7426	0.26	0.25	0.22	SN74145	1.15	1.10	1.05
SN7427	0.26	0.25	0.22	SN74147	2.95	2.90	2.85
SN7428	0.39	0.38	0.37	SN74148	2.30	2.25	2.20
SN7430	0.14	0.13	0.12	SN74150	1.35	1.30	1.25
SN7432	0.25	0.24	0.22	SN74151	0.60	0.52	0.55
SN7433	0.36	0.35	0.34	SN74152	1.55	1.50	1.45
SN7437	0.27	0.26	0.22	SN74153	0.68	0.62	0.55
SN7438	0.27	0.26	0.22	SN74154	1.55	1.50	1.45
SN7439	1.10	1.08	1.06	SN74155	0.68	0.62	0.55
SN7440	0.14	0.13	0.12	SN74156	0.68	0.62	0.55
SN7441	0.70	0.69	0.66	SN74157	0.90	0.85	0.80
SN7442	0.63	0.60	0.53	SN74158	1.50	1.45	1.40
SN7443	1.00	0.99	0.90	SN74160	0.95	0.90	0.80
SN7444	1.08	1.07	1.05	SN74161	0.95	0.90	0.80
SN7445	0.85	0.83	0.70	SN74162	0.95	0.90	0.80
SN7446	1.03	1.00	0.85	SN74163	0.95	0.90	0.80
SN7447	1.03	1.00	0.85	SN74164	1.60	1.55	1.50
SN7448	0.85	0.83	0.70	SN74165	1.60	1.55	1.50
SN7450	0.14	0.13	0.12	SN74166	1.40	1.30	1.15
SN7451	0.14	0.13	0.12	SN74170	2.40	2.30	2.20
SN7453	0.14	0.13	0.12	SN74173	1.65	1.60	1.55
SN7454	0.14	0.13	0.12	SN74174	1.15	1.10	1.00
SN7455	0.40	0.39	0.38	SN74175	0.97	0.90	0.80
SN7460	0.14	0.13	0.12	SN74176	1.10	1.05	1.00
SN7462	0.45	0.44	0.42	SN74177	1.10	1.05	1.00
SN7464	0.45	0.44	0.42	SN74180	1.10	1.05	1.00
SN7465	0.45	0.44	0.42	SN74181	3.50	3.45	3.35
SN7470	0.30	0.27	0.25	SN74182	1.10	1.05	1.00
SN7471	0.60	0.59	0.58	SN74184	1.60	1.55	1.50
SN7472	0.25	0.24	0.21	SN74185	2.30	2.25	2.20
SN7473	0.30	0.27	0.26	SN74188	4.90	4.85	4.80
SN7474	0.31	0.29	0.26	SN74190	1.75	1.70	1.65
SN7475	0.40	0.39	0.38	SN74191	1.70	1.65	1.60
SN7476	0.31	0.29	0.26	SN74192	1.25	1.05	1.00
SN7478	0.65	0.63	0.61	SN74193	1.25	1.05	1.00
SN7480	0.43	0.41	0.36	SN74194	1.10	1.05	1.00
SN7481	1.00	0.95	0.90	SN74195	0.90	0.85	0.80
SN7482	0.75	0.70	0.62	SN74196	1.05	1.00	0.95
SN7483	0.81	0.80	0.68	SN74197	1.05	1.00	0.95
SN7484	0.90	0.86	0.85	SN74198	2.05	2.00	1.70
SN7485	1.25	1.15	1.00	SN74199	2.05	2.00	1.70
SN7486	0.31	0.28	0.25	SN74200	6.00	5.95	5.80
SN7488	3.50	3.20	3.00	SN74221	1.80	1.75	1.70
SN7490	0.45	0.42	0.35	SN74225	1.80	1.75	1.70
SN7491	1.00	0.95	0.90	SN74278	3.00	2.90	2.80
SN7492	0.45	0.42	0.35	SN74279	1.20	1.15	1.10
SN7493	0.45	0.42	0.35	SN74293	0.90	0.85	0.80
				SN74298	2.60	2.55	2.60

'LS' and 'S' Series TTL also available

HIGH-SPEED TTL

SN74H00	0.34	0.33	0.30	SN74H51	0.36	0.35	0.33
SN74H01	0.34	0.33	0.30	SN74H52	0.36	0.35	0.33
SN74H04	0.38	0.37	0.34	SN74H53	0.36	0.35	0.33
SN74H05	0.37	0.36	0.33	SN74H54	0.36	0.35	0.33
SN74H08	0.40	0.39	0.37	SN74H55	0.36	0.35	0.33
SN74H10	0.36	0.35	0.33	SN74H60	0.36	0.35	0.33
SN74H20	0.36	0.35	0.33	SN74H61	0.36	0.35	0.33
SN74H21	0.36	0.35	0.33	SN74H62	0.36	0.35	0.33
SN74H30	0.36	0.35	0.33	SN74H71	0.80	0.78	0.75
SN74H40	0.36	0.35	0.33	SN74H72	0.74	0.73	0.70
SN74H50	0.36	0.35	0.33	SN74H73	0.90	0.88	0.85
				SN74H74	0.87	0.85	0.81
				SN74H76	0.90	0.88	0.85
				SN74H101	0.80	0.78	0.75
				SN74H102	0.80	0.78	0.75
				SN74H103	1.10	1.09	1.05
				SN74H106	0.95	0.93	0.90

LOW-POWER TTL

SN74L00	0.34	0.33	0.30	SN93L01	1.60	1.55	1.50
SN74L02	0.34	0.33	0.30	SN93L08	3.20	3.10	2.90
SN74L03	0.39	0.37	0.34	SN93L09	1.80	1.75	1.70
SN74L04	0.39	0.37	0.34	SN93L10	2.80	2.75	2.65
SN74L10	0.34	0.33	0.30	SN93L11	4.20	4.10	3.90
SN74L20	0.39	0.37	0.34	SN93L12	1.80	1.75	1.70
SN74L42	1.62	1.58	1.50	SN93L14	1.70	1.65	1.60
SN74L51	0.34	0.33	0.30	SN93L16	3.20	3.10	2.95
SN74L73	0.74	0.71	0.68	SN93L21	1.50	1.46	1.42
SN74L74	0.89	0.87	0.80	SN93L22	1.80	1.76	1.70
SN74L90	1.62	1.58	1.50	SN93L24	2.80	2.72	2.63
SN74L93	1.74	1.71	1.65	SN93L28	3.70	3.60	3.42
SN74L95	1.62	1.58	1.50	SN93L34	4.00	3.70	3.50
SN93L00	1.50	1.45	1.40	SN93L38	4.20	4.10	3.90
				SN93L40	6.50	6.30	5.90
				SN93L41	6.50	6.30	5.90
				SN93L60	3.00	2.90	2.70
				SN93L66	2.70	2.65	2.55

WAVEFORM GENERATOR KITS

Here's a highly versatile instrument at a fraction of the cost of conventional unit. Kit includes two XR205 IC's, data & applications, PC board (etched & drilled, ready for assembly) and detailed instructions.

XR-205K **£12.30**

The Function Generator Kit features sine, triangle and square wave. THD 0.5% typ. AM/FM capability.

XR-2206KA FUNCTION GENERATOR KIT

Includes monolithic function generator IC, PC board, and assembly instruction manual. **£11.50**

XR-2206KB FUNCTION GENERATOR KIT

Same as XR-2206KA above and includes components for PC board. **£16.00**

PICO-PAC

THE SMALLEST REGULATED AC/DC POWER SUPPLY EVER!
Only 1.70" x 1.00"
x 0.85" output pre-set ±5% 9 models.
£15.00 each


PREMIUM QUALITY COMPONENTS

We've been buying and selling top quality components for nearly ten years. We handle only original parts, from the world's leading manufacturers and our customers include some of the largest and most quality-conscious companies. Now you can take advantage of our component buying skills and power and select from a broad range of advanced circuits.



NEW

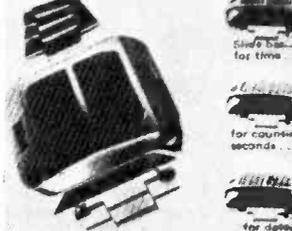Solar Powered Watch with 100-YEAR CALENDAR




Solar cells draw power from the sun (10 to 15 minutes per day) or from ambient light (slightly longer) to keep batteries fully charged. Batteries operate up to 10 years. LSI circuitry is programmed to provide a calendar to the year 2100, automatically adjusting for 30 and 31 day months, even leap years. Automatic brightness control adjusts LED for perfect viewing even in outdoors. Shows minutes and hours, counts out seconds or shows the date. Easily adjusts to reset hour or date without affecting calendar. Shock and water resistant. Accurate to 5 seconds per month. Price: **£298.50 each.**

Appointments

Advertisements accepted up to 12 noon Monday, February 2, for the March issue subject to space being available.

DISPLAYED APPOINTMENTS VACANT: £6.99 per single col. centimetre (min. 3cm).
LINE advertisements (run on): 99p per line (approx. 7 words), minimum three lines.
BOX NUMBERS: 40p extra. (Replies should be addressed to the Box numbers in the advertisement, c/o Wireless World, Dorset House, Stamford Street, London SE1 9LU).
PHONE: Allan Petters on 01-261 8508 or 01-261 8423.

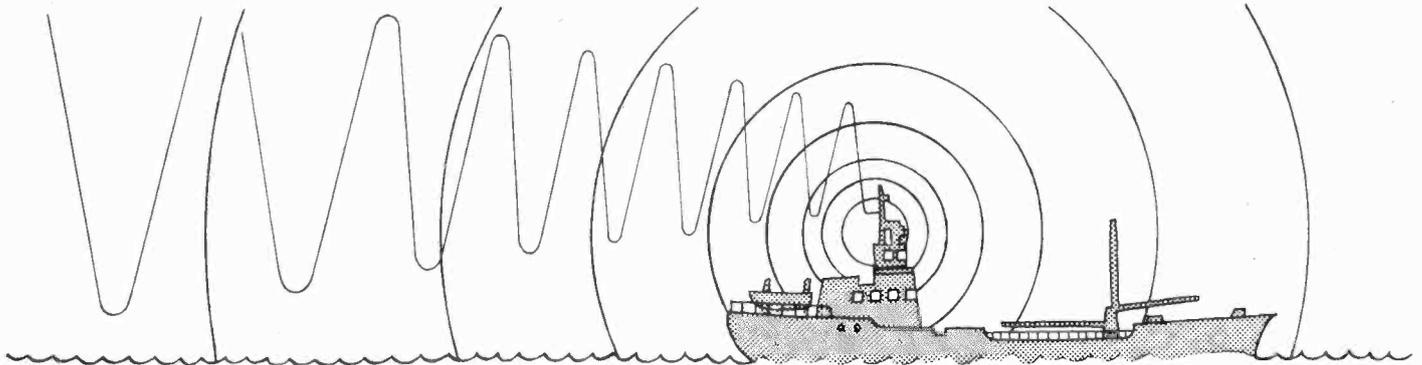Classified Advertisement Rates are currently zero rated for the purpose of V.A.T.



Radio Officers—now you can enjoy the comforts of home.

Working for the Post Office Maritime Services really makes sense. You still do the work that interests you, but with all the advantages of a shore-based job: more time to enjoy home life, job security and good money. To qualify, you need a United Kingdom Maritime Radiocommunication Operator's General Certificate or First Class Certificate of competence in Radiotelegraphy, or an equivalent certificate issued by a Commonwealth Administration or the Irish Republic.

Starting salaries, at 25 or over, are £2905 rising to £3704 after three years service. Between 19 and 24, the starting salary varies from £2234 to £2627

according to age. You'll also receive an allowance for shift duties which at the maximum of the scale averages £900 a year and there are opportunities to earn overtime. There's a good pension scheme, sick pay benefits and prospects of promotion to senior management.

Right now we have vacancies at some of our coastal radio stations, so if you're 19 or over, write to: ETE Maritime Radio Services Division (R/B/1), ET 17.1.1.2., Room 643, Union House, St. Martins-le-Grand, London EC1A 1AR.

Post Office Telecommunications

93

A Career With BRITISH RELAY TV


TV Communal Aerial Systems Video and Audio Communications

A vacancy has arisen for a Manager based in Edinburgh to control the Company's activities in the above fields for the whole of Scotland. Applications are invited from suitably qualified and experienced persons. Preferably with management or supervisory background and sound practical experience in the following aspects.

Systems Design
Planning and Estimating

Project Control
Installation Supervision

Test and Commissioning

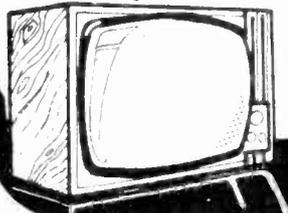

The salary is negotiable and a Company Car is provided. Enquiries and applications for interview will be treated in strict confidence and should be made in writing to:

The General Operations Manager
British Relay Limited
55 Melville Street
EDINBURGH EH3 7HN

(5085)

BRITISH RELAY TV



Opportunities in the ELECTRONICS FIELD

People with analogue or digital qualifications / experience seeking higher paid posts in: TEST - SERVICE - DESIGN - SALES.

Phone: Mike Gernat, Ref. W.W.

NEWMAN APPOINTMENTS
360 Oxford Street, W.1,
01-629 0501

(94)

How many professional new T.V. broadcasting systems have you pioneered lately?

Zanzibar, Nigeria, Korea, Oman and, most recently, Indonesia?

Over the past few years, Pye TVT have been breaking technological barriers in the broadcasting industry. Installing complete T.V. Broadcasting systems in countries, which have never before seen television and in places where existing systems are converting monochrome to colour.

Because each new system is a one-off, custom built job with unique technical innovations and maybe installed in widely differing conditions both in climate and terrain, we offer an unlimited challenge and interest to really creative engineers who have imaginative yet practical ideas, whilst being sufficiently resilient to thrive in our high technology business.

Senior Systems Engineers (Transmitters)

Who are self motivated and capable of aligning complete T.V. transmitter systems to customer specifications using modern test equipment. Applicants should be able to locate and rectify complex faults involving the whole system or individual items of equipment and work with customers' engineers of many nationalities. Experience in U.H.F., Klystrons and/or high power transmitters is essential.


Senior Installation Engineers

Working either independently or as a head of a small team which may involve taking charge of local labour, you'll be installing and commissioning V.H.F. and U.H.F. transmitters practically anywhere in the world. Your experience could have been gained with a U.K. or overseas broadcaster, but whatever your background, you should be a very competent T.V. transmitter engineer. Projects vary in length and in certain cases your family may be able to join you. Overseas allowances will be paid in addition to basic salary and subsistence.

All appointments will be based in Cambridge and besides excellent salaries, will receive many worthwhile benefits, including relocation expenses in certain cases.

It is only to be expected that an organisation involved for so long in pioneering broadcasting would have been responsible for many firsts throughout the industry. With your help, we hope to produce many more.

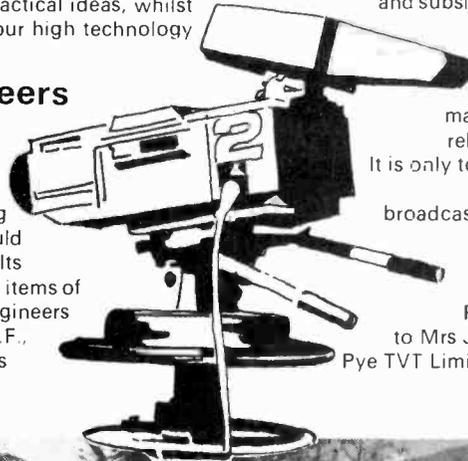Please write with full career details to Mrs J. A. Macnab, Personnel Manager, Pye TVT Limited, P.O. Box 41, Coldhams Lane, Cambridge, CB1 3JU.



A member of the Pye of Cambridge Group

Pye TVT Limited

PO Box 41 Coldhams Lane Cambridge England CB1 3JU
Tel: Cambridge (0223) 45115 Telex: 81103PYE TVT CAMBGE

Instrumentation and Control Systems

The Electronics and Applied Physics Division has a vital role as a centre for advanced electronic knowledge and as a source of specialised equipment for the multi-disciplinary laboratory at Harwell, for the whole UK Atomic Energy Authority and for industrial projects. Our responsibilities cover a broad range including measurement system design, transducers, semiconductor technology, and signal processing and communication in both analogue and digital forms, often requiring knowledge of both hardware and software.

Our work ranges from initiating applied research aimed at anticipating future needs, to tackling immediate problems in close collaboration with workers in other disciplines. We participate in the nuclear power programme, and we have research and development programmes in the environmental, marine and medical fields.

Applicants should have a clear interest in some of the above areas and should possess a good Honours Degree in Electrical/Electronic Engineering or in Physics with a bias towards Engineering; preference will be given to those with postgraduate experience in an appropriate area and who have scientific or technical management potential.

Appointments will be either to the permanent staff or to Fellowships with a salary or stipend in the range £3500-£5000 depending upon experience and ability.

Further enquiries and requests for application forms should be sent to:
Appointments Section 'A', AERE, Harwell, Oxon. OX11 0RA

HARWELL

ELECTRONIC ENGINEERS AND AN INSTRUCTOR

Vacancies exist for Electronic Engineers and an instructor to join the technical back-up team of an expanding department, involved in electronic calculators and business equipment systems.

Electronic Engineers should have a good basic electronic background, preferably with some experience of pulse and counting circuitry.

The Instructor should have a similar technical background in addition to proven teaching ability.

Please telephone or write for more details and application forms to:

Mr. D. D. Davies
Sumlock Anita Ltd.
1 Frogmore Road, Apsley
Hemel Hempstead, Herts.
Tel. Hemel Hempstead 61771



Sumlock Anita Ltd.
Rockwell International

M.Sc. COURSE IN ELECTRICAL ENGINEERING

with specialisation in any one of the following:
**Electrical Machines
Communication**

**Systems
Electronic
Instrumentation
Control Engineering
and**

**Digital Electronic
Systems**

**Design of Pulse and
Digital Circuits and
Systems**

The Course, which commences in October 1976, may be taken on a Full Time, Part Time, Sandwich or Block Release basis, and is open to applicants who will have graduated in Science or Engineering, or who will hold equivalent qualifications, by that date. The Science Research Council has accepted the Course as suitable for the tenure of its Advanced Course Studentships.

A Diploma Course, in some of the above topics or in Power Systems, is also open to applicants with the above, or slightly lower qualifications.

Research in

Electrical Engineering

Applications are also invited from similarly qualified persons who wish to pursue a course of research leading to the Degree of M.Phil. or Ph.D. in any of the above topics.

Application forms and further particulars from the Head of the Department of Electrical Engineering (Ref. M.Sc. 4), The University of Aston in Birmingham, Birmingham B4 7PB.

(5100)



THE UNIVERSITY
OF ASTON
IN BIRMINGHAM

UNIVERSITY OF DURHAM INSTITUTE OF EDUCATION

Colleges of Education Television Recording Unit

ENGINEER

An Engineer is needed to assist in the maintenance and operation of a Monochrome Television Recording Unit serving Colleges of Education in the Durham area, based at Neville's Cross College.

The Unit provides videotapes on a wide range of subjects for use in the training of student teachers. High quality recordings are made on locations throughout the county, using a well equipped Mobile Television Control Vehicle. The successful applicant will join a team of six and will be expected to undertake not only engineering duties but also will have the opportunity to participate fully in a wide variety of production tasks.

Essential qualifications are a general knowledge of television techniques and equipment and a current driving licence. Salary: Local Authority Scale T3. £2,922-£3,282.

Applications, including the names of two referees, should be sent to the **Secretary, University of Durham, Institute of Education, 48 Old Elvet, Durham**, not later than Friday, 6th February, 1976.

5113

MEDICAL PHYSICS TECHNICIAN

GRADE IV

Area Medical Physics Department

Required for duties in the INTENSIVE CARE UNIT and in the wards primarily at Leicester General Hospital.

The work involves close contact with patients. It will include care, use and maintenance of intensive care equipment and sophisticated monitoring systems both in the Unit and throughout the hospital.

A technician qualified ONC/HNC (Electronics) will be required. Experience whilst desirable is not essential, as training in this aspect of work will be provided.

Salary: Technician IV, £2346-£3267. New entrants would normally start at minimum.

Applications stating age, qualifications and previous experience together with the names of two referees, to the **Sector Administrator, Leicester General Hospital, Gwendolen Road, Leicester LE5 4PW.**

Closing date: 31st January 1976

(5109)



Leicestershire Health Service

LEICESTERSHIRE AREA HEALTH AUTHORITY (TEACHING)



YAMAHA

require an

AUDIO ENGINEER

We require an Engineer to service Yamaha Hi Fi products. Applicants must be used to working on current sophisticated audio products and should be able to repair these without assistance to the highest standards.

Please apply in writing to:

(5114)

Natural Sound Systems
Ltd.
Strathcona Road, North Wembley, Middlesex HA9 8QL

*Looking
for
a
new
job?*

Perhaps we can help!

We have regular contact with hundreds of electronics and electrical companies needing qualified electronics engineers and technicians and TV service engineers.

We can, therefore, help you to find an interesting and well paid job. All you need to do is to return the coupon below or give us a ring. Our service is confidential and costs you nothing.

**TJB Technical Services Bureau,
3A South Bar,
Banbury, Oxfordshire.
Banbury (0295) 53529**



Technical Services Bureau is a division of Technical & Executive Personnel Ltd and is solely concerned with job placement in the Electronics and Electrical Industries

Please note that this service is available only for engineers who are (or will be) available in the U.K. for interview.

Please send me an "Application for Registration" form

NAME

ADDRESS

.....

..... (90)

Depot Engineers

Due to continually increasing commitments we need to expand our shore based engineering staff at our service depots at Cardiff and Tilbury.

The work is concerned with installation and service of our world famous communication equipment on board commercial vessels of all types.

In some instances opportunities may exist for overseas travel.

The ideal candidate will probably have served as a Radio or Electronics Officer at sea and will have three or more years sea service.

A company vehicle is provided for business and personal use.

If you are interested and would like to know more please write or telephone (reverse charges) to:

*Jonathan Smith,
International Marine Radio Co. Ltd.,
Peall Road, Croydon, CR9 3AX
Telephone 01-684 9771*



(5093)

Inner London
Education Authority

South Thames College

Audio- Visual Technician

Grade 6

responsible for

College CCTV System and All Audio-Visual Aids

(including first line maintenance and operation).

Applicants must have an appropriate advanced CGLI or equivalent or higher qualification and six years' experience (including training period).

Salary: Grade 6 £3156-£3762, with, additionally, £411 London Allowance added.

Application forms and further particulars from Vice-Principal, South Thames College, Wandsworth High Street, London SW18 2PP, to whom they should be returned within two weeks of the date of this advertisement.

THE UNIVERSITY OF LEEDS

Department of
Physical Chemistry

ELECTRONICS: DESIGN AND DEVELOPMENT

Applications are invited for a post to assist research groups within the department in the design and development of electronic equipment. Applicants should have a degree or its equivalent and a working knowledge of modern electronics including computers, digital techniques and radio-frequency circuitry.

The appointment will be at the Experimental Officer Grade with starting salary in the range £2370-£3594 (under review).

Applications (three copies) stating age, experience and qualifications and naming three referees should be sent as soon as possible to the Registrar, The University, Leeds LS2 9JT.

(5091)

AREA SALES MANAGER H.F. & U.H.F.

Our client is in the business of HF & UHF transmitters and receivers and radio antenna. We are seeking a person experienced in this field, who will be fluent in French. Based at Weybridge. Sales territory: French speaking African countries. Salary C. £4,500.

Write or phone V. Green

S&W SERVICES**26a HIGH STREET, HOUNSLOW, MIDDX.****01-572 7363**

(5105)

PRODUCTION MANAGER RELAY/ELECTRONICS

A leading installer of burglar alarms systems, now expanding to produce its own range of Control and Electronic Equipment, seeks person with relevant design and management expertise to develop from scratch the manufacturing division in EC1. Salary negotiable A.A.E.

For details please contact:

I.C.S. APPTS. 01-278 9551

(5119)

CCTV ENGINEER

The successful applicant will:

- Be experienced in the servicing of all types of CCTV equipment including Video Tape Recorders.
- Be preferably with some experience of Colour Cameras and VTR's
- Be capable of working to a large degree on own initiative with a minimum of supervision.
- Be resident in (or willing to move to) the Edinburgh area.

**P.T.S. (Electronics) Ltd.
St. Alkmunds Way
Derby**

5112

Teach TELEPHONY to Post Office Students at ACTON TECHNICAL COLLEGE

Do you have a real interest in teaching, a sound knowledge of Post Office equipment and a Telecommunications Technician Certificate? Then join a **team** of teachers who would welcome your expertise.

In return we offer you a rewarding and interesting career as a Lecturer II with good prospects.

Starting salary in the range £3,279-£5,493 plus £351 London Weighting.

For further details and application form write or telephone NOW:

**Registrar & Clerk to the Governing Body
Acton Technical College
High Street
LONDON W3 6RD
Telephone: 01-993 2344 ext. 2371**

5108

SERVICE ENGINEER

F. W. O. BAUCH LIMITED

A vacancy exists for a service engineer seeking varied and interesting work in the professional audio field, the successful applicant should have a sound knowledge of electronics and some mechanical aptitude. Previous experience of professional broadcasting or recording studios would be an advantage.

The post involves repairing and servicing high quality audio equipment both in our own laboratory and in the field, salary negotiable.

Apply in writing directly to:

**49 Theobald Street
Borehamwood
HERTS. WD6 4RZ**

(5124)

TECHNICAL SALES ASSISTANT

Required by Importers of the famous AMCRON range of Laboratory Power Amplifiers to handle telephone sales, and service queries, and assist the Sales Manager in all aspects of sales, and marketing at the Company's Head Office in East Anglia.

The successful applicant will be 20-25 years of age with a sound knowledge of modern transistor circuit techniques. Some practicable experience in Research or Industry would be an advantage, but a pleasant personality and smart appearance is of prime importance.

Write in the first instance to the
Managing Director
Macinnes Laboratories Ltd.
Macinnes House
Carlton Park Industrial Estate
Saxmundham, Suffolk, IP17 2NL

(5136)

TANN SYNCHRONOME

Field Support Engineer

Opportunity for a technically qualified young Engineer.

In a rapidly expanding Division of a National Company should have some experience in the following ANALOGUE/DIGITAL, FAULT DIAGNOSTICS, small batch prototype assembly and wiring. Full staff status, 4 weeks' holiday with pay for 1976. Plus all statutory holidays. Excellent subsidised canteen, service increments after 1 and 2 years' service. Salary over £3,000 per annum. Write or telephone Mr. R. Fossey, Personnel Manager, John Tann Security Ltd., Sterling Corner, Borehamwood, Herts. Tel 01-953 2021.

REPAIR TECHNICIAN

for Audio equipment and photographic electronic instrument servicing

Good knowledge of solid state circuitry and mechanical expertise essential.

Salary in region of £3,000 p.a.

AXCO INSTRUMENTS LTD.
228 Regents Park Road, Finchley N3 3HP
(Tel. Mr. Brody - 01-346 8302)

(5092)

AIRFIELD NAVAIDS

Training course starting April 26

IAL is a world leader in communications and aviation services and we will be running a series of UK training courses this year to meet our expanding overseas commitments. Successful completion will lead to interesting, highly-paid postings abroad and opportunities to expand with the company.

To qualify for a place on the course, you should have several years' experience in the maintenance and operation of ILS, VOR and DME, together with a knowledge of associated ground-to-

air communications systems

We offer attractive tax-free salaries overseas and additional benefits include: free furnished accommodation; an excellent pension scheme; opportunities for accompanied postings; education/child allowance.

The next course starts April 26th, 1976. Secure your place by contacting the Senior Recruitment Engineer, International Aeradio Limited, Aeradio House, Hayes Road,

Southall,
Middlesex.
Telephone:
01-571 1808 or
01-571 0678.



PAE PARK AIR ELECTRONICS

RF DESIGN ENGINEER

Our planned Company expansion has created an opportunity to join our team engaged on the design of VHF Transmitters and Receivers for use in the Airports of the World.

The person we are looking for must be keen to work as a member of this specialist team and be prepared to take the responsibility of working on the project as a whole. The successful applicant will be formally qualified and will have had really relevant experience in our field. Reporting to the Development Manager and will be keen to progress a career in the expansion phase the Company is entering at the moment.

Salary will be in line with the job responsibility. There is an excellent contributory pension scheme, World Wide Air Fare rebates for holiday travel, and relocation assistance will be given.

If you would like to work for a small company which offers career prospects and big company benefits in this pleasant rural area, please contact Clive Picking at:

PAE PARK AIR ELECTRONICS LIMITED

Ryhall Road, Stamford, Lincolnshire, England
Telephone: Stamford 2187
Member of the International Aeradio Group



(5153)

LONDON BOROUGH OF BARKING BARKING COLLEGE OF TECHNOLOGY

LECTURER GRADE I/II IN TELECOMMUNICATIONS AND ELECTRONICS

required, principally for full-time courses in Marine Radio and for City and Guilds of London Institute Telecommunications Certificate. Applicants should have appropriate qualifications and experience. Appointment on the Grade II scale will depend upon the extent of such experience and qualifications obtained.

Burnham Scales (I) £2,649 to £4,377 (II) £3,279 to £5,493 both plus £351 London Weighting. Application forms and further details from the Registrar, Barking College of Technology, Dagenham Road, Romford, Essex RM7 0XU. Completed forms to be returned to him within 14 days of this notice.

5017



**CAPITAL
APPOINTMENTS LTD**

Recession? Don't you believe it!

We have more jobs for good Electronic Design Development and Test Engineers than ever before. All areas UK, all applications. Salaries to £5,000. (5128)

34 Percy Street, London, W.1
01-636 9659 (day) or
550 0836 (evg.)

CLARENDON LABORATORY, University of Oxford, offers 3 year appointment to holder of Grad. Inst. P., with considerable experience in cryogenics and related applied physics techniques to join Nuclear Orientation research group having helium dilution refrigerator. Salary according to age, experience and qualifications within the range £3,378 to £5,010 p.a. Transit accommodation available. Apply in writing giving full particulars of education, training and experience to Dr. A. J. Croft. (5142)

UNIVERSITY OF EXETER

ELECTRONICS TECHNICIAN

A vacancy has arisen in the Department of Biological Sciences for a Technician in the Electronic Workshops, within the Grade range 3 to 5. The appointed technician will be required to provide a repair and maintenance service for electrical and electronic equipment for use in research and teaching.

Salary: £2,325 to £3,207 p.a.

Applications are invited from qualified persons, and/or persons interested in attending ONC or HNC courses. These should be sent, together with the names and addresses of two referees, to the Administrative Officer (staffing), University of Exeter, Northcote House, The Queen's Drive, Exeter EX4 4QJ, by 29th January, 1976. Please quote reference no. 1/79/5058. (5104)

RCS ELECTRONICS have the following vacancies: Electronic Engineer with general electronic experience for work on 74 Series Logic R.F. and Digital Circuits. Design & Development Engineer with wide experience in R.F. and Digital Equipment. Apply: R.C.S. Electronics, National Works, Bath Road, Hounslow, Middx. Phone: 01-572 0933. (5140)

EXPERIENCED CLOSED CIRCUIT TELEVISION SECURITY SYSTEM Design and Project Engineer capable of taking full responsibility for major projects. Must be thorough, self-motivating and imaginative. Also required experienced CCTV Technicians. Excellent salary and benefits to right people with world-wide travel prospects. Please ring Brian Kent, Windsor 51966. (5123)

AGENTS WANTED

DANISH COMPANY seeks contact with British manufacturer of magnetic tapes (Compact Cassette and Open Reels) for possible agency in Scandinavia or Denmark. Please write to: Per Meistrup, Aksel Moellers Have 12, DK2000 Copenhagen F, Denmark. (5134)

CHELSEA COLLEGE University of London

TELEVISION TECHNICIAN

A Television Technician (Grade 5) is required to operate and maintain a wide range of audio and video equipment. The successful candidate will be expected to work closely with academic staff and students, and assist in the interpretation of their requirements in television terms. The television service at the college is expanding and the installation and commissioning of new equipment will present additional responsibilities. Salary Scale: £3161-£3617 per annum (inclusive).

Application forms from: **Personnel Officer, Chelsea College, Manresa Road, London SW3 6LX.**

LEICESTER POLYTECHNIC ELECTRONICS TECHNICIAN

required in the School of Chemistry, to be responsible for (a) the design, development and construction of prototype electronic equipment for chemical applications; (b) the maintenance of existing equipment.

Successful applicant must have a knowledge of analogue and digital electronics and will probably have at least two years' experience subsequent to taking a Full Technological Certificate in Electronics, a HND in Electronics or a Degree in Electronics.

Salary: £2277 - £2529 p.a.

Apply in writing, giving full details, to: **Staffing Officer, Leicester Polytechnic, P.O. Box 143, Leicester, LE1 9BH.**

(5094)

SERVICE MANAGER CAR RADIO STEREO TAPE PLAYERS

The sole national distributors for Pioneer Automotive Equipment require a Service Manager, fully conversant with all aspects of Service/Repair, fitting, suppression, technical advisory service and current technology. Modern well equipped workshop (one assistant). Salary negotiable according to experience and qualifications. Non-contributory pension scheme.

Applications in writing with full details to:

**AUTOCAR ELECTRICAL
EQUIPMENT CO. LTD.**
Chantry Road Industrial Estate
Kempston, Beds.

(5121)

ARTICLES FOR SALE

B. BAMBER ELECTRONICS

(DEPT. WW), 5 STATION ROAD, LITTLEPORT, CAMBS, CB6 1QE
TEL: ELY (0353) 860185 (TUESDAY-SATURDAY)

TERMS OF BUSINESS: CASH WITH ORDER
ALL PRICES INCLUDE POST AND PACKING (UK ONLY)
EXPORT ENQUIRIES WELCOME. CALLERS WELCOME TUES.-SAT.
PLEASE ADD VAT. MINIMUM ORDER £1
PLEASE ENCLOSE STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES (5030)

ALL BELOW — ADD 8% VAT
MARCONI TF867 SIGNAL GENERATOR (up to 30MHz), good condition. £52.00.

A LARGE SELECTION of Test Equipment. Surplus Equipment, Components, etc. Bulk Loads for dealers. Ring for appointment.

ISEP RACKING, 19" wide, 15" deep to take 7" panels (with some PCB slides and sockets) brand new. £8.00

PAL DECODER PANELS (from Philips Colour Monitors), type EL8618/00, new, complete, but untested. £20.00.

AS ABOVE, but NTSC. £10.00.

PF1 POCKETPHONES, UHF, untested, but complete, less batteries. 1 TX + 1 RX. £32.50.

PYE CAMBRIDGE BOOT MOUNT AM10B sets only, no control gear. 25KHz channel spacing. £20.00. (High or Low Band available, state which required.)

MULLARD TUBULAR CERAMIC TRIMMERS, 1-18pf. 6 for 50p.

(as featured in Rad. Comm. Jan p.25)

ICs, some coded, 14DIL type, untested, mixed. 20 for 25p.

2-6PF., 10MM CIRCULAR; CERAMIC TRIMMERS (for VHF/UHF work), 3 pin mounting, 5 for 50p.

CERAMIC HIGH VOLTAGE PILLARS (metal ends, tapped 4BA), approx 1in. long, 10 for 60p.

MAINS TRANSFORMERS
All 240V input, voltages quoted approx RMS

(Please quote Type No. only when ordering)
TYPE 10/2 10.0-10V at 2A. £1.50.

TYPE 72703 400V at 10mA, 200V at 5mA, 6.3V at 400mA, £1.25.

TYPE 28/4 28V at 4A, 125V at 500mA, £4.00.

TYPE 125BS, approx 125V at 30mA, 65p.

COLOUR MONITOR DECODER PANELS. By leading British manufacturer. Designed to B.B.C standards. Units consist of chrominance module, PAL filter and delay module, luminance module and encoded video input module. All units brand new and complete including edge connectors and service manual. £30.00. Manual supplied separately. £1.00 each.

ALL BELOW — ADD 8% VAT
BFY51 TRANSISTORS 4 for 60p.

BSX20 TRANSISTORS 3 for 50p.
BC108 (metal can) 4 for 50p.

PBC108 (plastic BC108) 5 for 50p.
BSY95A TRANSISTORS, 6 for 50p.

BCY72 TRANSISTORS, 4 for 50p.
MINIATURE 2 PIN PLUGS & SOCKETS

(Fit into 1/4" hole, pins enclosed, with covers for chassis mounting, or can be used for in-line connectors) Bargain pack of 3 plugs + 3 sockets + covers 50p.

PROGRAMMERS (Magnetic Devices) Contain 9 microswitches (suitable for mains operation) with 9 rotating cams, all individually adjustable, ideal for switching disco lights, displays etc. or industrial machine programming. (Need slow motion motor to drive cams, not supplied) 9 switch version £1.50, or 15 switch version £2.00.

10 WAY PUSH-BUTTON UNITS, 1/2" square buttons, marked 0-9, cancelling type, mounted on one PCB for easy fixing, ex-equip 50p.

HEAVY DUTY HEATSINK BLOCKS, undrilled base area 2 1/4" x 2 1/4", with 6 fins, total height 2 1/4", 50p each.

9V RELAYS, Continental type, 2 pole change over 35p.

RUBBER MAGNETS 1/2" square, with mounting hole, 20 for 30p.

PYE CAMBRIDGE PC BOARDS (Removed from high band AM10)

RF and MIXER BOARD £7.00
10.7 MHz IF BOARD £1.50

10.7 MHz OSCILLATOR/MIXER BOARD (with 11 155 Xtal) £1.25.

455 KHz IF BOARD £2.00
AM AUDIO BOARD £1.20

AM SQUELCH BOARD 50p
6 CHANNEL LEDEX SWITCHES, 12V, complete with all trimmers and coils (removed from high band AM10) £4.00.

PYE WESTMINSTER W30 AM MAN-UALS (shop soiled) £1.20 (Zero rated VAT).

T03 TRANSISTOR INSULATOR SETS, 10 for 50p.

SPECIAL OFFER. Miniature 50 ohm coax, high quality, PTFE insulation and blue PTFE cover, solid silver-plated inner, and silver-plated braid, approx 3mm overall diameter. (ideal for unit wiring of RF stages up to 23cms etc.) 4 metres for 50p.

ALL BELOW — ADD 8% VAT
24V MIN. REED RELAYS, encapsulated single-pole make, 2 for 50p.

WE NOW STOCK SPIRALUX TOOLS for the electronics enthusiast. Screwdrivers, nut spinners, BA and Metric sizes, pop rivet guns, etc. SAE for list.

PLUGS AND SOCKETS

25-WAY ISEP PLUGS AND SOCKETS, 40p set (1 plug + 1 skt). Plugs and sockets sold separately at 25p each.

ANDREWS 44AN FREE SKTS. (N-type) for FH4/50B or FHJ4/50B cable, £1.00 each.

BULGIN ROUND FREE SKTS. 3 pin, for mains input on test equipment, etc., 25p each.

SO239 BACK TO BACK SOCKETS, £1.25 each.

PL259 PLUGS (PTFE). Brand new. Packed with reducers 65p each, or 5 for £3.00.

SO239 SOCKETS (PTFE). Brand new (4 hole fixing type), 50p each, or 5 for £2.25.

N-TYPE SKTS. (4 hole chassis mounting, 50ohms, small coax lead type), 50p each.

N-TYPE PLUGS 50ohm, 60p each.

GREENPAR (GE35012) CHASSIS LEAD TERMINATIONS (These are the units which bolt on to the chassis, the lead is secured by screw cap, and the inner of the coax passes through the chassis), 30p each, 4 for £1.00.

BULGIN FLAT 2 pin FLEX CONNECTORS. Non-reversible 40p each.

PYE RADIO-TELEPHONE EQUIPMENT

Cambridge, Westminster, Motofone, Europa series. Ser'd s.a.e. for full details.

WELLER STOCKIST. All irons and spares available. S.A.E. for list.

VALVES

QV03/20A (ex-equipment) £3.00.
QV03/10 (ex-equipment) 75p or 2 for £1.20.

2C39A (ex. equipment), £1.00 each.
QV02/6 (ex. equipment), £1.00 each.

4X250B (ex. equipment), £1.50 each.
DET22 (ex. equipment), 2 for £1.00.

APPOINTMENTS

**DEVELOPMENT LABORATORY ASSISTANT/
JUNIOR ENGINEER**

To work with Design team on monochrome and Colour television monitors, switching and mixing modules and systems. These positions offer interesting work, with good prospects in a fast growing company. Preferred qualifications are ONC/HNC or equivalent (or studying for).

Write or telephone: **Griff Chanot** (Chief Engineer) for appointment

MELFORD ELECTRONICS LTD.

High Wycombe, Leigh Court, Leigh St., High Wycombe, Bucks HP11 2QU
Tel: High Wycombe 25696/7/8 (5101)

THOMSON FOUNDATION TELEVISION COLLEGE

This college which is involved in training engineering and production staff from overseas in advanced broadcast techniques requires an

ENGINEERING ASSISTANT

to assist the lecturing staff in the preparation and maintenance of a wide range of colour and monochrome broadcast equipment.

Starting salary in the range £2000 - £2500 p.a. (contributory pension scheme).

Experience in maintenance of broadcast or C.C.T.V. equipment desirable.

Application forms from: The Principal,

THOMSON FOUNDATION TELEVISION COLLEGE

Kirkhill House, Broom Road East
Newton Mearns, Glasgow G77 5RH (5102)

ARTICLES FOR SALE

100,000 C280 CAPACITORS, good mixed selection from .01uf to 2.2uf-250v/w & 400v/w price 100/£1.25, 1,000/£10. AC128 transistors marked un-used but require testing, price per 50/£1.50. Prices include VAT, P&P 25p. Electronic Mail-order Ltd., Ramsbottom, Bury Lanes. (5024)

"MOTIVATOR" Curtain Cord Controllers. Mains battery models and kits for use with corded domestic curtains. From £18-20. Aid-Us Products, Dept. WW10, 8 Hillview Road, Pinner HA5 4PA, Middlesex. 4988

DIGITAL CLOCK CHIP, AY-5-1224, with data and circuit diagram, £3.66 plus VAT, + Jumbo LED digits (16mm high) type economy DL/747 only £2.04 each plus VAT, post free. Greenbank Electronics, 94 New Chester Road, Wirral Merseyside L62 5AG. (83)

C.R.T. REGUNNING PLANT. New and second-hand reconditioned training, demonstration, colour or B/W. Barretts, Mayo Road, Croydon, Surrey, CR0 2QP. (36)

16MM B & H 631 Sound projectors c/w speaker and transformers £135. — Hilton Cine, 9 West Hill, Dartford -T. 20009. (15)

fibre optic suppliers

MARE'S TAIL 22" dia 7,000 + Fibres £10.00. Glass fibres — requires cover.

FIBROFLEX SIZE 1 440 Strand Flexible Glass Light Conduit, 1 1/4mm Active Dia. Black Sheath, 10m £3.00; 100m £21.00

FIBROFLEX SIZE 4 1760 strand £1.50.

CROFFON 1610 Flexible 64 Strand Plastic Light Conduit. Active Dia. 1.8mm, O.D. 3.3mm £1.20 per M., 10m £9.00

PLASTIC OPTICAL MONOFIBRE Flexible Light Guide Dia. 10, 20, 40, 60 thou. FP10 100m £4.00, FP20 (D.5mm) 100m £8.00, FP40 10m £4.00; 100m £32.00, FP60 10m £8.00; 100m £65.00

OPTIKIT 103 2m CROFFON 1610 + 3m each FP20, FP40, FP60 + Polishing Compound, ideal laboratory pack £5.50

OPTIKIT LB 6 Convex Glass Lenses Dia. 7-14, 21/26/47/51mm £3.00. (Lenses also available separately.)

OPTIKITS RR5 Five Retro-Reflectors for Optical/beam systems. Dia. 22/36/44/83mm + 150mm Strip. £2.50.

ULTRASONIC TRANSDUCERS SE05B-40T/R Sensitive 40kHz Tx/Rx pair (Suitable for Doppler/Remote Control) £3.50

ULTRASONIC TRANSDUCERS SE04B-25T/R 25 kHz Tx/Rx Pair. (Better Sensitivity Lower Bandwidth than SE05B-40) £3.50

CIRCULAR POLARISERS Reduce glare on all types of instrument. RED AMBER or NEUTRAL. 50mm sq, 70p; 75mm sq, £1.40; 150mm sq, £4.50. Linear Polarizers also available.

OPTOELECTRONICS LIGHT SOURCES & DETECTORS
MVS4 2mm Red LED 20p. MLE500 1092 Red LED 20p.
XC209-Red (3mm) 20p. XC209-Y, XC209-G (Amber, Green) 30p.
MLE92 Infra Red Emitter 30p. MLS203 Photo-Thyristor £1.20.
2N5777 High Sensitivity Photo-Darlington 25V 50p.
MRO 150 2mm High Speed Photo-Transistor (4 us) 40V 70p.
Please add 8% VAT to prices. S.A.E. please for short form data.

FIBRE OPTIC SUPPLIERS (WW): 6 CHIPPENHAM MEWS, LONDON W9. (5029)

APPOINTMENTS

R & D MEDICAL ELECTRONICS

Cardiac Recorders have a vacancy for an Electronics Engineer to work on the design and development of Electro-medical equipment.

The successful applicant will have a degree or HND in Electronics, preferably with at least two years' experience and proven ability in circuit design.

The work demands considerable responsibility, with a commensurate salary.

Apply in writing with full details to: **R. Colson, Cardiac Recorders Ltd., 34 Scarborough Road, London N4 4LU.**

ARTICLES FOR SALE

Electrotime


FOR CLOCKS
WATCHES
CALCULATORS



Add to the sophistication of your life with one of our digital clocks, all solid state design in an attractive, white plastic case.

- Features—4 digit display
Flashing colon for seconds
p.m. indicator
Brightness control
Snooze alarm

£14.50
inc. VAT

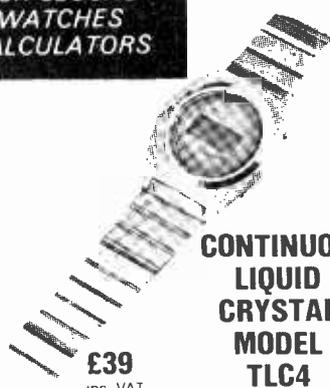


**CONTINUOUS
LIQUID
CRYSTAL
MODEL
TLC4**

£39
inc. VAT

Gold or rhodium
plated bracelet

Features—

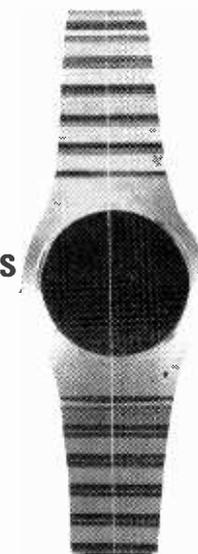- ★ Hours
- ★ Minutes
- ★ Seconds
- ★ Date



**THE
ULTIMATE
MODEL
TLE5**

Gold or rhodium
plated bracelet

Features—

- ★ Hours
- ★ Minutes
- ★ Seconds
- ★ Date
- ★ Alpha day

£45 inc. VAT

One-year guarantee with all models



GENERAL CALCULATOR MODEL 1437
Features—8 digit capability
Full floating point
Basic functions (+ - × ÷ %)
Automatic power-on clear
Leading zero suppression
£13.80
inc. VAT

**PROGRAMMABLE SCIENTIFIC
CALCULATOR MODEL 1421**
Features—
8 digit capability
Full floating point
Three register stack
Memory
Trig functions
Plus—capability of being
loaded with up to a 102
step program for complex
or tedious calculations
Radians—Degrees
— constant
Logs (in log)
Power functions
Reciprocals
Square/square root
£50
inc. VAT



**Electrotime, 111 Storforth Lane Trading Estate
Chesterfield, Derbyshire. Tel: 35804**

Please supply:

Name

Address

COLOUR UHF and TV SPARES. Lists available on request "Wireless World" TV tuner project, by D. C. Read, Kits of parts available. New cross hatch kit, Aerial input type. No other connections. Battery operated, portable. Incl. Sync & UHF Modulator units. £11.00 P/P 45p. CRT Reactivator kit for colour and mono £17.48 p/p 70p. Signal strength meter kit £18.00 p/p 60p. 625 TV I.F. Unit, suitable for Hi-Fi amp on tape recording £6.80 p/p 60p. Bush CTV 25 new convergence panels + yoke and blue lateral £3.60 p/p 65p. New Philips single standard convergence panels complete, incl. 16 controls, coils, P.B. switches, leads £3.75 p/p 65p. New colour scan coils, Mullard or Plessey, plus convergence yoke and blue lateral £9.20 p/p 70p. Mullard at 1023/05 convergence yoke £2.50 p/p 50p. Mullard or Plessey Blue laterals 75p p/p 25p. BRC 3000 type scan coils £2.00 p/p 60p. Bush CTV25 scan coils, new. £2.50 p/p 60p. Delay lines DL20 £3.50, DL40 £1.50, DL1E, DL1 £1.00 p/p 35p. Lum Delay Lines 50p p/p 20p. EHT colour quadrupler for Bush/Murphy CTV25 3/174 Series £8.50 p/p 60p. Special offer, colour triplers: ITT TH25/ITH £2.00 p/p 40p. GEC 2040 tripler £1.75 p/p 40p. Philips G8 panels, part complete, surplus/salvaged: decoder £2.50, IF, incl. 5 modules £2.25, T-Base £1.00 p/p 50p, CRT base 75p p/p 20p. G.E.C. 2040 panels for spares. Decoder £3.50, Timebase £1.00 p/p 55p. VARICAP TUNERS. UHF ELC 1043, new £4.20, ELC 1043/05, £5.00, VHF ELC 1042, new £5.00. Salvaged VHF and UHF Varicap tuners £1.50 p/p 25p. SPECIAL OFFER: RBM 6psn. Varicap control units £1.00 p/p 25p. UHF tuners, new, transistorised, incl. slow motion drive, £3.80, 4-position and 6-position push-button transistorised, £4.20 p/p 60p. Philips, Bush, Decca integrated UHF/VHF transd. tuners £4.50 p/p 65p. Thorn 850 dual standard time base panel 50p p/p 50p. Philips 626 I.F. amp incl. cct. 50p p/p 50p. VHF turret tuners at 7650 incl. Valves for K.B. Featherlight, Philips 19TG170, GEC 2010 ETC. £2.50. Pye miniature incremental for 110 to 830, Pam and INVICTA £1.00. New Fireball tuners, Ferguson, HMV, Marconi. £1.00 p/p all tuners 50p. Mullard 1100 Mono scan coils, new, suitable all standard Philips, Stella, Pye, Ekco, Ferranti, Invicta £2.00 p/p 55p. Large selection. LOPTS. FOPTS available for most popular makes. 200 + 200 = 100 MFD 350V Electrolytic £1.00 p/p 30p. MANOR SUPPLIES. 172 West End Lane, London, N.W.6. Shop Premises. Callers welcome. (No. 28, 159, 59 buses or W. Hampstead-Bakerloo and Brit. Rail). Mail Order: 64 Golders Manor Drive, London NW11. Tel: 01-794 8751. VAT. Please ADD 25% TO ALL PRICES (EXCEPT KITS. VAT 8%).

RTTY AUDIO FREQUENCY SHIFT CONVERTOR CV-89A/URA-8A. This must be the first quantity release of this most sought after Ritty Convertor. Brief description uses 15 BG9 & BG7 Valves, with a 2" C.R. Tuning Tube Housed in a Grey Alloy Case size 17" x 5" x 15" deep Input supply fully filtered for interference. Requires 105 - 125 Volts A C A two position Selectivity or Filter Switch that enables to set up for any Narrow Shift from 10-200 Cycles or any Wide Shift from 200-1000 Cycles. The Mean or Centre Freq for the Narrow Shift is 1000 Cycles, for the Wide Shift is 2550 Cycles Normal Audio Input from Receiver is 600 OHMS The Convertor will operate with an input of 60 Microwatts to 60 Milliwatts or about -14 to plus 18 DBM Has Internal Tone OSC Freq 595-1785 CPS Mark Space Switch Normal or Reverse. Supplied in good used condition, checked complete, but not tested Electronically £22 50 Carr £2 50 onwards.

We also have a few COMPARATORS CM-22A/URA-8A same colour and size, using 13 BG7 and BG9 Valves Made for use with above for Dual Diversity. Reception. 105-125 V.A.C. Supply fully filtered for interference. Used Good condition, checked complete but not tested Electronically £10 00 Carr. as above
We have in stock a Clip on Fan Blower Cooler complete with Filter & Heat Switch that only switches on when Units get to a preselected heat. Normally if Units are used up to 24 hours a day Housed in Alloy case £2 50 Post or carr. 50p

TELEPRINTER CREED 7B. New or rebuilt as new by Gov. in original Gov. Transit Case Power 100 - 250V D.C. Few only at £22.50 ea. Carr. £3.50 or at cost.

SUPPLY UNIT 7. Input Voltage 12V d.c. or 100-250 A.C. Output 70-100 Volts 30M/A twice 30-45V A.C. 40 M/A. 11 5-14V d.c. 2-4 amps. In small box. These are mainly for supplying Relay Voltage for the Teleprinters. Brand New at £3.50. Carr or post £1.00

If possible collect ex Warehouse by appointment, and save carr. cost also delivery time.
Terms cash with order. VAT at 8%.
Phone Morley Code 0532-531179

JOHNS RADIO
424 BRADFORD ROAD, BATLEY, YORKS.
(5045)

THE SCIENTIFIC WIRE CO.

Copper — Nickel — Chrome — Eureka —
Ltz — Manganin Wires.
Enamelled — Silk — Cotton — Tinned
Coverings.

- ★ No minimum charges or quantities.
- ★ Trade and export enquiries welcome.
- ★ S.A.E. brings List.

P.O. BOX 30, LONDON E4 9BW

OSCILLOSCOPE, Solartron CD711S.2. Any reasonable offer. St. Leonards House, Ashtree Close, Worlingham, Suffolk. Tel: Beccles 713786 (5032)

E.C.L. LOGIC I.C.s. Mc10101L, Mc101002L; Mc10105L all first grade, guaranteed, 50p per gate, post free. Discounts: £4.20 for 10 pieces; £38 for 100. Tunnel diodes TD253 at £1.50 each post free. Capacitor clearance: 0.1 micro-farad 250v polyester films tape C280 at £1.80 per thousand. (These are physically perfect but are surplus untested). Tested C280s: 0.47 at £1.20 per 100; 0.33 at £1.00 per 100; 0.22 at 90p per 100; 0.033 at 70p per 100. N. O'Brien, 189 West Hendon, Broadway, London, NW9. (5042)

OSCILLOSCOPE TUBES Mullard type D14-121-GH complete with shield, and base. Suitable case. C Core mains transformer and multi-rail regulator P.C.B. Inverter transformer and E.H.T. multiplier. Twin plug-in deflection amplifiers. All at £35 per package. All brand new. Circuits supplied phone 01-202 6282, very limited stock. (5043)

SUPERB INSTRUMENT CASES by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range, competitive prices start at a low 75p. Over 400 models to choose from. Prompt despatch. Free literature (stamp would be appreciated). Bazelli, Dept No 22, St Wilfrid's, Foundry Lane, Halton, Lancaster, LA2 6LT. (5052)

TAPE SPOOLS, 5in & 5 1/2in diameter, in crystal polystyrene with quick load slots. Available ex-stock. Plasro Plastics Ltd., 38 Wates Way, Mitcham, Surrey. 01-640 0145. (5129)

500 DUAL STANDARD COLOUR TV's. In stock from £30. Contact: S.H.C. Television, Norlett Building, Dormer Road, Thame, Oxon. Thame 4331. (20)

VACUUM is our speciality, new and second-hand rotary pumps, diffusion outfits, accessories, coaters, etc. Silicone rubber or varnish outgassing equipment from £40. V. N. Barrett (Sales) Ltd., 1 Mayo Road, Croydon. 01-684 9917. (24)

ARTICLES FOR SALE

CRYSTALS

Fast delivery of prototype and production quantities to your specification. EG

100 KHz	0.005%	HC13/U	£2.50 each: £1,900 per 1,000
1 MHz	0.005%	HC6/U	£2.50 each: £1,600 per 1,000
2.097152 MHz	0.0025%	HC6/U	£3.05 each: £1,550 per 1,000
3.2768 MHz	0.0025%	HC6/U	£2.70 each: £1,500 per 1,000
10 MHz	0.002%	HC18/U	£2.00 each: £1,100 per 1,000

Also. Statek LF. crystals in TU-5 package. many stock frequencies in the range 10-240 KHz. e.g., 10, 12.8, 16.384, 32.768 & 100 KHz. prices from £2.55 each: £1,400 per 1,000.

Please send for further details.
INTERFACE QUARTZ DEVICES LTD., 29 Market Street, Crewkerne, Somerset. Telephone: (046031) 2578 Telex: 46283.

ENAMELLED COPPER WIRE

S.W.G.	1 lb. reel	1/2 lb. reel
10 to 19	2.40	1.35
20 to 29	2.45	1.40
30 to 34	2.60	1.50
35 to 40	2.85	1.60

All the above prices are inclusive of postage and packing in U.K.

COPPER SUPPLIES

102 Parrswood Road, Withington, Manchester 20
 Telephone 061-445 8753

NEAL CASSETTE RECORDERS

Opportunity to own a famous machine at a fabulous saving. Demonstration, Display and Review units — all models Thoroughly rechecked to full specification by Manufacturer and reboxed. FULL GUARANTEE

Example Model 102 Mk 1 at only £120 + VAT — £150 incl.

Post enquiries only please. **dB Associates, 75 Marlow Road, London SE20 or phone 08926 3150** 5110

60 KHz MSF RUGBY RECEIVERS. BCD TIME-OF-DAY OUTPUT. High performance, phase locked loop radio receiver. 5V operation with LED indication. Kit complete £9.50; assembled and tested unit £11.12 (prices include postage and V.A.T.) Also available low power receiver with signal and audio outputs. Send for details. **Toolex, Sherborne (4359) Dorset. (21)**

TIDY PACK with 6 different sizes of neat shrink sleeving each 1M in length 100 self-locking cable ties and a roll of black PVC tape. All for only £2 inc. VAT & PP. **B.D.O. Products Ltd. Retail Division, 13A Heath Road, St Albans, Herts. (5090)**

SOLARTRON CD 7115. 2 Double beam Oscilloscope. 9MHz amplifiers, Xtal calibrator, variable trigger delay, with manual: £40. — Telephone **Dr Bell, 01-789 6611. (5098)**

WE INVITE ENQUIRIES from anywhere in the World. We have in stock several million carbon resistors 1/4, 1/2, 1, and 1 watt. 1/2 million wire wound resistors 5 and 10 watt — 1 million capacitors — 1 million electrolytic condensers — 1/2 million transistors and diodes, thousands of potentiometers, and hosts of other components. Write, phone or call at our warehouse — **Broadfields & Mayco Disposals Ltd., 21 Lodge Lane, N. Finchley, London, N.12. 01-445 0749, 445 2713. (5097)**

QUERSA RT 45U. Chasing machine. 220/240V. Used one dwelling only, 90. VGC. — 79 Ashley Road, New Milton, Hants. Tel: New Milton 615912. (5103)

LINSLEY-HOOD 75 watt amplifier spares by return. Sescosem BDY56 £1.75, Motorola BD529, BD530 65p each. 2N5457, 2N5459 45p each. BF258 35p, BFR 39 35p, BFR 79 35p. Tantalum bead 100/3V 15p. Headphone socket kit, with full fitting instructions, £1.45. Filter switch click and mains/RF interference suppression Kit, with instructions, £1.35. All components brand new and guaranteed. Inclusive prices. P&P 10p. List SAE. **I. G. Bowman, 59 Fowey Avenue, Torquay, S. Devon. (5106)**

TEXTRONIX 564B Storage oscilloscope with a 4-channel amplifier and time base £350. Fluke 8000A digital multi meter £70. 051-709 1898. (5138)

MULLARD LP1400 high performance stereo decoder modules. Limited quantity to clear, only £6 including p & p. **Mr. Cook, 39 Barrett Road, London, E.17. Mail order only.**

DISCO CONSOLE consisting of two 100 watt DJ Power Amplifiers with SDL mixer Mk 11, 2 Garrard SP25 MKIII Turntables with Shure. Magnetic cartridges, housed in compact mobile unit. 4 speaker units; 2 containing four 12" 50 watt Goodman speakers. 2 containing 18" EMI speakers, 100 watt Pluto light projector, microphone (including stand and boom) Speaker leads, Bank lights. All perfect and ready for use. £800. 01-805 3898.

ARTICLES WANTED

FRENCH RADIO — ELECTRONICS WHOLESALE

Wishes to buy in Great Britain, in co-operation with British Wholesaler:

1. Radio.
2. Tape Recorders.
3. Hi-Fi Record Players (Philips-Garrard).
4. Koss Stereo head phones.
5. Philips/Mullard. Radio tubes.

S. A. CERUTTI & CIE

201/203 Bd. V. Hugo, BP 3512 - 59020 LILLE CEDEX

Telex: 120082

CERUTTI — LILLE

WE PURCHASE

bulk quantity of fall-out or scrap grade

TRANSISTORS, DIODES

such as To-92, To-18, To-106, To-5, Do-35, Do-7 (Germanium), Do-41 . . . etc.

If available, PLS, Sample to:

W.K. ELECTRONICS CO.

57 Kam Ping St. D7 13/F

Tung Fat Building

North Point, Hong Kong (5122)

★ **MINICOMPUTERS**
 ★ **PERIPHERALS**
 ★ **INSTRUMENTATION**

For fastest, best CASH offer, phone

COMPUTER APPRECIATION

Godstone (088 384) 3106 (41)

WANTED, all types of communications receivers and test equipment. Details to **R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley 4986. (63)**

B-D ELECTRONICS offer prompt settlement for your surplus components. Our main field of interest is consumer electronics. Please telephone our Miss Hughes, Sandy (0767) 81616. (22)

WIRELESS WORLD COLLECTOR requires January, March, April, June, July, August 1966. February, March, April, May, June, July, August 1967. February 1968. February, March, April, May, July, October, November, December 1969. July 1970. April 1972. December 1973. — Box No. 5065.

WANTED, Valve Tester/Characteristic meter. Cowley. 40 Langbank Ave., Ernsford Grange, Coventry (0203) 453676. (5111)

WILLIAMSON AMPLIFIER output transformers, one pair of identical impedance, Partridge or Savage. Alternative, are Partridge type VDN 436B or CFB/0 of 0.95 ohm impedance. — Reply: **D. Fairbairn, Whitmore Farm, Windlesham, Surrey. (5096)**

VALVES RADIO TV TRANSMITTING INDUSTRIAL 1936 to 1975, many obsolete types, list 20p s.a.e. for quotation. Postal export service. We wish to buy all types of valves new and boxed. Wholesalers, Dealers, etc., stocks purchased. **Cox Radio (Sussex) Ltd., The Parade, East Wittering, Sussex, West Wittering 2023. (5141)**

WANTED!

all types of scrap and **REDUNDANT ELECTRONIC & COMPUTER MATERIALS** with precious metal content

TRANSISTORS & PRINTED CIRCUIT BOARDS to COMPLETE COMPUTERS

The COMMERCIAL SMELTING and REFINING Co. Ltd.

171 FARRINGDON ROAD, LONDON EC1R 3AL

Tel. 01-837 1475. Cables: COMSMELT, EC1

Works: FLECKNEY, near LEICESTER (5116)

SURPLUS COMPONENTS, Equipment and Computer panels wanted for cash. Ring Southampton 772501. (16)

TAPE RECORDING ETC.

RECORDS MADE TO ORDER

DEMO DISCS MASTERS FOR RECORD COMPANIES	VINYLITE PRESSINGS
---	-----------------------

Single disc: 1.20, Mono or Stereo, delivery 4 days from your tapes. Quantity runs 25 to 1,000 records **PRESSED IN VINYLITE IN OUR OWN PLANT.** Delivery 3-4 weeks. Sleeves/Labels. Finest quality **NEUMANN STEREO/Mono Lathes** We cut for many studios **UK/OVERSEAS. SAE list**

DEROY RECORDS

PO Box 3, Hawk Street, Camforth, Lancs. Tel. 2273 (82)

EX-GOV'T MONO to multi-track tape recorders, "E.M.I." Ferrograph-rich Leavers, etc. **S.A.E.** details **A. Wright, 10 Church Street, Dowlais Glamorgan. 4991**

RECEIVERS AND AMPLIFIERS —

HRO Rx5s, etc., AR88, CR100, BRT400, G209, S640, etc., etc., in stock. **R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E11 Ley 4986. (65)**

SIGNAL Generators, Oscilloscopes, Output Meters, Wave Voltmeters, Frequency Meters, Multi-range Meters, etc., etc., in stock. **R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley 4986. (64)**

CAPACITY AVAILABLE

STRIPPER FOR HIRE

Your Free issue wire cut and stripped for 75p per 1000 leads Supply of equipment cable available, printed circuits assembled Cable looms and complete equipment manufactured to order. Wire supplied and cut, a quotation will cost you nothing from:

HAMER & EMMINS LTD
Deseronto Wharf, St. Mary's Road
Langley, Bucks
Tel. Slough 46760 or 46769

When you need to hire Video-

it pays to contact the most experienced video company in the business

REW

R.E.W. HOUSE
10, 12 HIGH STREET
COLLIERS WOOD
LONDON SW19 2BE
PHONE: 01-540 9684

Also at **CENTRE POINT**
20/21 ST. GILES HIGH STREET
LONDON, WC2
PHONE: 01-240 3066

ARTICLES FOR SALE CONT.

Economise on Semiconductors

All prices include VAT — by return service

- ★ Lower price CMOS
- ★ Lower price 741C

- ★ Low price DIL sockets
- ★ Low price NE555

			TTL Mixed		prices		CMOS Mixed prices	
	1+	10+	1+	25+	1+	25+	1+	25+
723C + data 14 pin DIL	70	68	7400	13	12	4000	17	16
741C + data 8 pin DIL	23	22	7402	13	12	4001	16	15
748C + data 8 pin DIL	36	34	7403	13	12	4002	16	15
LM308 + data 8 pin DIL	110	99	7404	15	13	4006	104	95
NE555 + data 8 pin DIL	44	42	7405	15	13	4007	17	16
CA3046 14 pin DIL	84	81	7410	13	12	4008	95	88
TDA1405 5V 650mA	80	76	7413	28	24	4009	50	46
TDA1412 12V 500mA	80	76	7420	13	12	4010	50	46
TDA1415 15V 450mA	75	72	7430	13	12	4011	16	15
BC107, 108, 109, 109C	11	10.5	7442	60	54	4012	16	15
BC182, 184	12	11.5	7447	85	80	4013	45	40
BC212, 214	13	12.5	7473	28	24	4014	90	82
H-P 0.2" LED red + clip	19	18	7474	30	26	4015	85	80
H-P 1/4" LED red	18	17	7476	30	26	4016	48	44
DIL low profile sockets	8 pin 11	10	7486	28	24	4017	85	80
	14 pin 12	11	7490	45	38	4020	99	93
	16 pin 13	12	7492	55	50	4023	16	15
H-P 5082-7740 cc digit	180		7495	45	38	4024	68	62
MT242CS Transformer	150		74121	33	28	4025	16	15
						4027	48	44
						4028	78	71
						4030	48	44
						4040	93	85
						4046	117	107
						4049	48	44
						4050	48	44
						4068	17	16
						4071	16	15
						4078	17	16
						4081	16	15
						4507	50	45
						4511	138	126
						4518	110	101
						4520	112	103
						4527	138	126

BC177	21	2N3702	12	1N4001	4
BC179	22	2N3708	10	1N4002	4.5
BF244B	30	2N3055	49	1N4003	5
BFY51	15	1N914	4	1N4004	6
BZY88C-3V3-15	11			1N4006	7
				1N4148	4

AY-5-1224 16 pin DIL clock IC + data + circuit 4.00
 Clock IC + 4 H-P 0.3" red digits 11.00
 Clock IC + 4 digits + transformer + transistors 13.00
 TBAB10AS 7W Audio Amp + circuit + data 1.15
 TCA940 10W Audio Amp + circuits + data 2.00
 TAD100 radio IC + IF filter + circuit + data 1.70
 Carbon Film high stab. resistor, 1/4W 5% E12 values 10ohm - 2M2, 1.1p ea. 10 for 10p, 100 90p. Same value.


All prices include VAT. P&P (UK) 12p. Overseas at cost. SAE enquiries. All goods new. Full spec. devices from Motorola, Mullard, TI, SGS, etc. Schools, colleges, etc., supplied. By return service.

SILICON SEMICONDUCTOR SERVICES

41 Dunstable Road, Caddington, Luton LU1 4AL (40)

QUARTZ CRYSTAL UNITS from

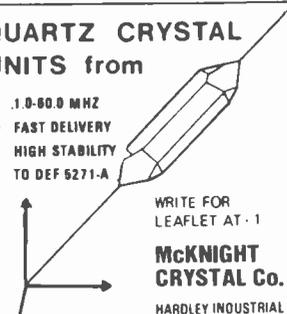- 1.0-60.0 MHZ
- FAST DELIVERY
- HIGH STABILITY
- TO DEF 6271-A



WRITE FOR LEAFLET AT 1

McKNIGHT CRYSTAL Co. Ltd.
HARDLEY INDUSTRIAL ESTATE, HYTHE, SOUTHAMPTON SO4 6ZY

TEL. HYTHE 848961
STD CODE 0703

SOWTER TYPE 3678 MULTITAP MICROPHONE TRANSFORMER

Primary windings for 600 ohm, 200 ohm and 60 ohm with Secondary loadings from 2K ohm to 10 K ohm. Frequency response plus/minus 1/2dB 20 Hz to 25 KHz. Contained in well finished Mumetal box, 33mm diameter by 22mm high, with colour coded end leads, low distortion. DELIVERY (small quantities) EX STOCK. HIGHLY COMPETITIVE PRICE. FULL DETAILS ON REQUEST.

E. A. SOWTER LTD., Dedham Place, Ipswich IP4 1JP. Telephone 0473 52794

POLYESTER CAPACITORS I.T.W.

Radial Lead 10% Tolerance 100V D.C. 001 3p, 0022 3p, 0047 3p, 0068 3p, 01 3p, 015 035p, 022 035p, 033 04p, 047 04p, 068 05p, 1 055p, 15 06p, 22 065p, 33 075p, 47 095p

Axial Lead 10% Tolerance 200V D.C. 01mfd 185p, 022mfd 185p, 047mfd 20p, 1mfd 25p

Dipped Tantalum Capacitors (Bead Type). Values available 1 15, 22, 33 1mfd, 15, 22, 33, 47, 35V, 47 6.8, 10mfd, 25V, 15, 22, 33, 47mfd, 16V. Prices 10p each - 10 for 95p

Electrolytic Capacitors (Axial). 1000-40V 25p, 470-16V 15p, 220-25V 12p, 100-25V 6p, 47-25V 5p, 47-10V 5p, 22-40V 5p, 10-25V 5p, 4 7-63V 5p, 2 2-63V 5p, 1mfd-63V 5p **Radial.** 2200 (Tag) 40V 45p each, 1000-16V 25p, 470-25V 19p, 220-25V 12p, 100-25V 6p, 47-16V 5p, 33-16V 5p, 22-16V 5p, 10-16V 4p, 5mfd-16V 4p, 4 7-16V 4p

Carbon Film Resistors. 1/2Watt RD1/3 5% (70 c) 01p each, 90p per 100 1R-1Meg (1M2-10M 10%) Special Pack 20 popular values quarter W — 5 of each 90p 1/2Watt AEL 5% 4 7R-2M2 015p each, 75p per 100 1Watt AEL 4 7-2M2 2p each, 1 74 per 100 Special Pack 100 Resistors mixed 40p

Polystyrene Capacitors (pf) 63V & 160V 5%. 10, 15 18 22 33 56 68, 100, 120, 150 180, 270, 330, 390 560 680 820 03p each 1000, 1500 2200, 3300 035p each 4700, 6800 8200, 4p each 10,000pf 05p each

Semiconductors. BC107/8 9 09p, 8C147/8/9 10p, 8C157 8 9 9p, 8CY70/1/2 17p, 8FY51 19p SCR C106D-2P4M-400V 50p each

Integrated Circuits. 741 8 Pin DIL 27p, 723(TO99) 57p LM309K(TO3) 1 48 1/C Sockets. (Gold) B/14 16 15p (Tin) 8/14/16 14p Minitron £1 20 each

Zener Diodes. 400MW 9p, 1Watt 17p (Standard voltages)

Diodes. 1N4148 05p 8AX16 05p

Rectifiers. 1A 1N4001 5p, 1N4002 06p, 1N4003 07p, 1N4004 08p, 3Amp 3A05(50v) 10p, 3A10(100v) 11p

TERMS. CASH WITH ORDER. V.A.T. PLEASE ADD 25%. POST AND PACKING ADD 35p ON ALL ORDERS UNDER £5. PROMPT SERVICE. ALL COMPONENTS GUARANTEED

TENDERS

BOROUGH OF CHARNWOOD TECHNICAL DEPARTMENT

Tenders for Surplus Radio Telephone Equipment

Tenders are invited for eleven low band Pye Westminster radiotelephones together with base station. This equipment can be inspected at the Council's Depot, Limehurst Avenue, Loughborough, and has become available due to the merging of two existing systems in which low band frequencies have been relinquished.

E. T. Anderson, CEng, FIMunE, Chief Technical Officer
Macaulay House, 5 Cattle Market, LOUGHBOROUGH



Greenway Electronic Components
(EAST GRINSTEAD) LTD
62 MAYPOLE ROAD, ASHURST WOOD, EAST GRINSTEAD, SUSSEX RH13 9BB
TEL: F0RECAST ROW 3782
(STD 054 282) 3713

Wilmslow Audio

THE firm for speakers!



Baker Group 25, 3, 8, or 15 ohm	£8.64
Baker Group 35, 3' 8 or 15 ohm	£10.25
Baker Deluxe, 8 or 15 ohm	£13.75
Baker Major, 3, 8 or 15 ohm	£11.87
Baker Regent, 8 or 15 ohm	£10.00
Baker Superb, 8 or 15 ohm	£18.12
Celestion HF1300 8 or 15 ohm	£7.75
Celestion MH 1000 horn, 8 or 15 ohm	£13.50
Decca London and X over	£42.25
Decca DK30 and X over	£24.06
EMI 13 x 8, 150 d/c, 3, 8 or 15 ohm	£2.94
EMI 13 x 8, Type 350	£9.56
EMI 13 x 8, 25 watt bass	£9.00
EMI 8 x 5, 10 watt, d/c, roll/s 8 ohm	£3.95
EMI 14" x 9" Base 80	£13.25
Elac 59RM 109 15 ohm, 59RM 1148 ohm	£3.44
Elac 6 1/2" d/c roll/s 8 ohm	£4.06
Fane Pop 15 watt 12"	£5.25
Fane Pop 25T 30 watt 12"	£7.50
Fane Pop 50 watt, 12"	£12.00
Fane Pop 55, 12" 60 watt	£13.95
Fane Pop 60 watt, 15"	£17.25
Fane Pop 70 watt 15"	£18.75
Fane Pop 100 watt, 18"	£29.95
Fane Crescendo 12A or B, 8 or 15 ohm	£34.50
Fane Crescendo 15, 8 or 15 ohm	£47.50
Fane Crescendo 18, 8 or 15 ohm	£62.95
Fane 807T 8" d/c, roll/s, 8 or 15 ohm	£5.75
Fane 801T 8" d/c roll/s 8 ohm	£9.95
Goodmans 8P 8 or 15 ohm	£5.50
Goodmans 10P 8 or 15 ohm	£5.80
Goodmans 12P 8 or 15 ohm	£13.95
Goodmans 12P-D 8 or 15 ohms	£16.95
Goodmans 12P-G 8 or 15 ohms	£15.95
Goodmans Audiom 100 15-ohm	£13.90
Goodmans Audiom 200 8 ohm	£13.90
Goodmans Axiom 100 8 ohm	£8.44
Goodmans Axiom 402 8 or 15 ohm	£20.00
Goodmans Twinaxiom 8" 8 or 15 ohm	£10.14
Goodmans Twinaxiom 10" 8 or 15 ohm	£10.75
Kef T27	£6.06
Kef T15	£6.94
Kef B110	£8.37
Kef B200	£9.50
Kef B139	£16.95
Kef DN8	£2.31
Kef DN12	£5.99
Kef DN13	£4.50
Richard Allan HPBB 8" 45 watt	£13.25
Richard Allan CGBT 8" d/c roll/s	£7.50
STC 400 1 G super tweeter	£6.56
Baker Major Module, each	£13.44
Goodmans Mezzo Twinkit, pair	£47.19
Goodmans DIN 20, 4 ohm, each	£14.75
Helme XLK35, pair	£24.00
Helme XLK40, pair	£35.00
Helme XLK30, pair	£19.00
Helme XLK50, pair	£56.00
Kefkit 1, pair	£53.00
Kefkit III, each	£48.00
Richard Allan Twinkit, each	£10.95
Richard Allan Triple 8, each	£16.50
Richard Allan Triple, each	£23.95
Richard Allan Super Triple, each	£28.75
Richard Allan RA8 kit, pair	£42.00
Richard Allan RA82 kit, pair	£63.00
Wharfedale Linton 2 kit (pair)	£23.12
Wharfedale Glendale 3 kit, pair	£40.62
Wharfedale Dovedale 3 kit, pair	£63.12

All Radford, Gauss, Castle, Jordan Watts, Eagle, Lowther, Peerless Tannoy units in stock
Prices correct at 29 10 75
**INCLUDING VAT AT 25% ON HI-FI
8% ON PRO AND PA**

Cabinets for PA AND HiFi, wadding, Vynair, etc
Send stamp for free booklet "Choosing a Speaker"
FREE with all orders over £7 — HiFi

Loudspeaker Enclosures Book
All units are guaranteed new and perfect
Prompt despatch

Carriage Speakers 50p each, 12" and up 75p each,
tweeters and cross-overs 30p each, kits 80p each
(£1.60 pair)

WILMSLOW AUDIO

Dept. WW

Loudspeakers & Export Dept: Swan Works,
Bank Square, Wilmslow, Cheshire SK9 1HF.
Discount HiFi, PA etc; 10 Swan Street,
Wilmslow. Radio, HiFi, TV, Radio: Swift of
Wilmslow, 5 Swan Street, Wilmslow. Tel.
(Loudspeakers) Wilmslow 29599, (HiFi, etc.)
Wilmslow 26213

WW—020 FOR FURTHER DETAILS

GIRO NO. 331 7056. Access and
Barclaycard accepted. C.W.O. only
Terms of business as in our catalogue
Export Order enquiries welcome (£5 min.)
Official Orders accepted from
Educational & Government Departments
E. & O. E. ALL PRICES INCLUDE VAT & P. & P.
Shop hours: 9-12.30, 1.30-5 p.m. 6 days

66 PAGES — 3000 ITEMS
FULLY ILLUSTRATED
★ 20p CREDIT VOUCHERS
★ ALL NEW STOCK
★ SATISFACTION
GUARANTEE
★ DISCOUNTS
★ NEW PRICE LIST — S.A.E.

20p plus 10p postage

TRANSFORMERS
SEMICONDUCTORS
MODULES — AUDIO
HEATSINKS — S-DEC
AUDIO ACCESSORIES
TOOLS — TEST METERS
CALCULATORS — AUDIO
LEADS—BATTERIES—KITS
RESISTORS — CAPACITORS
CASES — COILS — BOOKS
CONNECTORS — VEROBOARD
PC MATERIALS — HARDWARE
BOXES — SCREWS — KNOBS
POTS—STORAGE UNITS.. ETC.. ETC

SPECIAL RESISTOR KITS (CARBON FILM 5%)
(Prices include post & packing)
10E12 1/4W or 1/4W KIT 10 of each E12 value
220ohms — 1M, a total of 570 **£5.29** net
25E12 1/4W or 1/4W KIT 25 of each E12 value 22
ohms 1M a total of 1425 **£12.64** net

SPECIAL CAPACITOR KITS
C280 Kit—PC Mounting polyester 250V 5 of each value 0.01, 0.022
0.047, 0.1, 220pF, 2 of 0.47, 1pF **£1.98** net
C296 Kit—Tubular polyester 400V 5 of each value 0.01, 0.022, 0.047, 0.1
0.22pF, 2 of 0.47pF **£2.67** net
Ceramic Kit—square plaque 50V 5 of each value 22, 33, 47, 100, 220, 330,
470, 1000pF, 2200, 4700pF, 0.01pF **£1.66** net
250V Paper Kit—Tubular metal case, 3 of each value 0.05, 0.1, 0.25
0.5 1pF **£1.41** net
500V Paper Kit—Tubular metal case, 3 of each value 0.025, 0.05, 0.1
0.025, 0.5pF **£1.41** net
1000V Paper Kit—Tubular metal case, 3 of each value 0.01, 0.025, 0.05,
0.1pF **£1.63** net

B.H. COMPONENT FACTORS LTD.

MULTIMETER U4341
27 Ranges plus Transistor Tester
16 7000! Volt
Vdc — 0 3 — 900V in 8 ranges
Vac — 1 5 — 750V in 6 ranges
Idc — 0 06 — 600mA in 5 ranges
Iac — 0 3 — 300mA in 4 ranges
Resistance — 2K Ω — 2M Ω in 4 ranges
Accuracy — dc — 2 1/2%
ac — 4% of F S D
nfe — 10 — 350 in 2 ranges
Size — 115 x 215 x 90mm
Complete with steel carrying case, test
leads and battery. PRICE **£11.88** net P & P
75p



U4341

MULTIMETER U4313
33 ranges. Knife edge with mirror scale
20 0000! Volt. High accuracy mVdc — 25mV
Vdc — 1 5 — 600V in 9 ranges
Vac — 1 5 — 600V in 9 ranges
Idc — 60 — 120 microamps in 2
Idc — 0 6 — 1500mA in 6 ranges
Iac — 0 6 — 1500mA in 6 ranges
Resistance — 1K Ω — 1M Ω in 4 ranges
db scale 10 to + 12db
Accuracy — dc — 1 1/2%, ac — 2 1/2%
Size — 115 x 215 x 90mm
Complete with steel carrying case test
leads and battery
PRICE **£14.90** net P & P 75p



U4313

MULTIMETER U4323
23 Ranges plus AF IF Oscillator
20 0000! Volt
Vdc — 0 5 — 1000V in 7 ranges
Vac — 2 5 — 1000V in 6 ranges
Idc — 0 05 — 500mA in 5
ranges
Resistance — 5 Ω — 1M Ω in 4 ranges
Accuracy — 5% of F S D
OSCILLATOR — 1 KHz and 465 KHz (A M) at approx 1
volt. Size — 160 x 97 x 40mm
Supplied complete with carrying case test leads and
battery
PRICE **£8.64** net P & P 75p



U4323

MULTIMETER U4324
34 Ranges High sensitivity
20 0000! Volt
Vdc — 0 6 — 1200V in 9 ranges
Vac — 3 — 900V in 8 ranges
Idc — 0 06 — 3A in 6 ranges
Iac — 0 3 — 3A in 5 ranges
Resistance — 25 Ω — 5M Ω in 5 ranges
Accuracy — dc and R — 2 1/2% of F S D
ac and db 4% of F S D
Size — 167 x 98 x 63mm
Supplied complete with storage case, test
leads, spare diode and battery
PRICE **£10.64** net P & P 75p



U4324

(W.W.), LEIGHTON ELECTRONICS CENTRE, 59
NORTH STREET, LEIGHTON BUZZARD, LU7 7EG
Tel Leighton Buzzard 2316 (Std code 05253)

EXCLUSIVE OFFERS

WORLD-WIDE RANGE NEVER BEFORE OFFERED
COMPLETE TRANSPORTABLE H.F. COMMUNICATIONS CENTRE housed in Air Conditioned TRAILER fitted two COLLINS KW10 600W S.S.B. Transmitter-Receiver and one COLLINS Receiver all fully tuneable 2 to 30 mcs digital readout synthesised frequency control, with line amplifiers and inputs, operating position and remote control facilities and ancillary equipment. Power input 115V or 230V A.C. Full details on application.
PHILCO RC-150 POINT-TO-POINT STRIP RADIO HF RECEIVERS 2/30 mcs. Ten fully tuneable channels to 0-5 kes with synthesizers. Single and diversity reception on ISB, DSB, SSB with 4 sub-bands to each channel. Full details and prices on application.

HIGHEST QUALITY 19" RACK MOUNTING CABINETS & RACKS

U.P. ref	Height in inches	Width in inches	Depth in inches	Rack Panel Space in ins	Price
CR	69	30	20	—	£24.00
FA	85	22	36	160	£22.00
FC	52	25	22	47	£17.00
FH	15	21	17	11	£12.00
FJ	15	21	15	12	£12.00
LL6	11	21	17	9	£15.00
LL7	16	20	12	14	£15.00
LL8	10	20	10	9	£15.00
LL9	17	21	17	14	£15.00
LL10	52	21	18	46	£15.00
MM	75	22	26	68	£22.00

Also Consoles, twin and multi-way Cabinets
OPEN RACKS

U.P. ref	Height in inches	Chassis Depth	Rack Panel Space	Base	Price
K1	66	2	51	14	£9.00
RG	66	2	51	14	£9.00

Full details of all above on request

We have a large quantity of "bits and pieces" we cannot list—please send us your requirements we can probably help—all enquiries answered.

- * 1600ft 16 m/m Film Spools ally (unused) 10 for £4.00
- * Quality electric Weather Vanes 8 contacts £10.00
- * Hel Facsimile Machines £45.00
- * Large Aerial Rotators for Coaxial £18.00
- * Collins 500 watt Telephone Transmitters 2/12 mcs £300.00
- * B.N.C. Connectors 200 for £17.00
- * Video Cross Hatch TV Generators £42.00
- * Rascal MA-175 I.S.B. Modulators (new) £45.00
- * Collins KWT 6 SSB Transceivers 500 watts 2/30 mcs P.U.R. £17.00
- * Intertechique SA40 Spectrum Analysers P.U.R. £80.00
- * Tequipment D53 d/b Oscilloscopes £17.00
- * Imslie Cabinet Shelf Sliders £3.00
- * DG-7.32 C.R.T.'s £3.00
- * Remscope Storage Scope with tracer £115.00
- * Textronic 519 Scope 1GHZ £450.00
- * M.V.R. Action Replay 20 sec. Videodisc Unit P.U.R. £17.00
- * Rascal 1KW S.S.B. Linear amplifiers 1.5/30 m/cs P.U.R. £18.00
- * Advance H1 Signal Generators, 15/50Kcs P.U.R. £17.00
- * Yanan VA175S Backward Wave Oscillators P.U.R. £48.00
- * Tally 5/8 Track Tape Readers 80 cps £60.00
- * Tally 5/8 Track Tape Readers 120 cps £60.00
- * 2 KVA Auto-Transformers £22.00
- * Coutant 40v 30A Power Supplies £30.00
- * 15 foot 15 inch Lattice-Steel Mast Sections £29.00
- * Cintel 2 KV Power Supplies £35.00
- * Cavkell FU 4 Band Pass Filter Testers £60.00

We have a quantity of Power Transformers 250 watts to 15KVA at voltages up to 40KV Best quality at low prices
List available

- * 500w Westinghouse Transmitters 2/1200 Kcs less P/S & Valves, new £50.00
- * Simon Airport Recorders 8 hour £50.00
- * AN/TRC1 Aerials VHF £8.00
- * 40" 1" co-axial, high quality £2.00
- * American all chrome Police sirens 6v, new £20.00
- * Rascal RA-63 SSB Adaptors, new £70.00
- * Rascal RA 237 L.W. Converters, new £70.00
- * 19" Blank Rack Panels 85cm High £1.00
- * Apco Dial a Copy Photo Copier Electrostatic £60.00
- * Hewlett Packard 524C Digital Counter P.U.R. £23.00
- * Airmec 702 Sig. Generator 30 cyc/30 k/c/s £23.00
- * Tuning Roller Coasters £3.50
- * Portable Mains Battery Floodlights £24.00
- * 400 channel Pulse Height Spectrum Analysers £600.00
- * Addo 5/8 track Tape Punchers £48.00

We have a varied assortment of industrial and professional Cathode Ray Tubes available. List on request.

INSTRUMENTATION-TAPE RECORDER-REPRODUCERS

- * Ampex TM 2 1/2", 4 speeds, 7 tracks
 - * Ampex FR-1100 1/2", 6 speeds, 2 tracks
 - * Ampex FR600 1/2", 4 speeds, 7 tracks
 - * Ampex FR600 1/2", 4 speeds, 14 tracks
 - * D.R.I. RM-1 1/2", 4 speeds, 4 tracks
 - * EMI BTR-1 1/2", 1 speed, 1 track
 - * EMI R301G 1/2", 2 speeds, 2 tracks
 - * Mincom CMP-100 1/2", 1, 6 speeds, 7 tracks
 - * Rascal T-5000 1/2", speed, 7 tracks
 - * Levers Rich DA-2P 1/2", 2 speeds, 2 tracks
- Prices of above £70 to £400

Also Transport Decks only available

COMPUTER HARDWARE

- * PRINTER, High speed 1000 lines p.m.
- * TAPE READER, High speed 5/8 track 800 c.p.m.
- * CARD READER 80 col. 600 c.p.m.

Prices on Application
PLEASE ADD V.A.T. AT APPROPRIATE RATE TO ABOVE

P. HARRIS
ORGANFORD-DORSET
BH16 6BR
BOURNEMOUTH-766051 (0202)

DIRECT COMMUNICATIONS

Division of Direct Electronics Ltd.

INTERCOMMS & TELEPHONES

- Simple 2-way wall/desk with 100ft cable. 6v batt or power supply. £16 (£1 p&p)
- Similar but 2- to 7-way instrument only. Installation diagram. £8.50 each (50p)
- Superior 2- to 6-way Siemens & Halske. Wall-desk conversion kit, term. block and cord per instrument £10. (50p).
- AUTOMATIC INSTRUMENTS. Strouwer compatible or PX working. New/refurbished/2nd hand. 232 332 706 746 722 (Trimfone), etc. Special and foreign types.
- ULTRA MODERN TYPES. "Gondola" International: Touch-button dial; Charleston (candlestick); etc.: from £32.85
- Plan & Key Phones for home and export
- Jacks; Plugs; Cords; Term. Blocks; Cables (up to 25-way and 50 pair), etc.
- Entrance Phones and Electric Latches, with or without intercomm. facility.
- Telephone Amplifier (1-way), £6.95 (35p); hands-free tele. amp. (two-way conversation), £9.50 (50p)
- ★ TRANSISTORISED UNITS. Simple 2-way batt. intercomm. £7.75 (50p); Batt. Baby Alarm £5.25 (50p); Intercomm. with roving master £9.50 (50p)
- Wireless Intercomm. (just plug into mains): 2-way £20 (£1); batt. op. 3-way (master + 2 subs) £23.95 (£1); 4-way (master + 3 subs) £28.50 (£1)
- ★ mains adaptor 6v/7.5v/9v dc £3.75 (35p).

Add VAT ● = 8%; ★ = 25% on post paid price

TRADE ENQUIRIES WELCOMED

MANY SURPLUS ELECTRONIC BARGAINS FROM OLD STOCK STILL LEFT — COME AND DO A DEAL!

34 LISLE STREET, LONDON, WC2H 7BD
Tel: 01-437 2524

CLOCK CHIPS AND DISPLAYS

LITRONIX CLASS II LEDs

1-24	25-99	100+	
DL707E, 704E, 701E 0.3"	0.70	0.48	0.36
DL727E, 728E, 721E 0.5"	1.80	1.15	0.86
DL747E, 746E, 750E 0.6"	1.50	1.00	0.80

NATIONAL CLOCK CHIPS

1-9	10-24	25-99	
*MM5309 7 seg. + BCD with reset to zero	5.69	4.84	4.35
*MM5311 7 seg. + BCD	5.69	4.84	4.35
*MM5314 7 segment	4.88	4.15	3.75
*MM5318 7 seg. + BCD (external digit select)	3.36	3.36	3.36
*MM5378 Car clock, crystal controlled LED	6.73	5.72	5.15

MOSTEK CLOCK CHIPS

*MK50250 Alarm (12Hr + 60Hz/24Hr + 50Hz)	5.60	4.90	4.26
*MK50253 Alarm (12Hr + 50Hz/24Hr + 60Hz)	5.60	4.98	4.33
*MK50204 Stopwatch Calculator	11.19	11.19	9.73
*MK50395 Up/Down Counter, 6 Decade	14.50	14.50	11.50
*MK50396 Up/Down Counter HMMSS	14.50	14.50	11.50
*MK50397 Up/Down Counter MMSS.99	14.50	14.50	11.50

*Available in our MHI kit systems. All these kits interface directly with common anode LEDs — 0.3", 0.5", 0.6", details in our catalogue.

DISPLAYS

1-9	10-24	25-99	
DL707, 704, 701 0.3"	1.48	1.48	1.28
DL727, 728, 721 0.5"			
2 digit package	3.75	3.75	3.12
DL747, 746, 750 0.6"	2.45	2.05	1.80
5LT01, 4 digital phosphor diode	5.80	4.80	3.90
3017 Minitron (filamentary)	2.00	2.00	1.70

MHI CASE. Dimensions, 8 x 5.5 x 3 inches. £2.95 (Please include 25p post & packing)

Terms C.W.O., Access, Barclaycard (simply quote your number and sign).

Credit facilities to Accredited Account Holders

All prices on this advert exclude VAT at 8%

BYWOOD ELECTRONICS
68 Ebbens Road
Hemel Hempstead
Herts, HP3 9QRF

WW-076 FOR FURTHER DETAILS

MICROPHONE PREAMPLIFIER

Small pc board (70x90mm) accepting two 30-600 ohm microphones (balanced inputs and feeding) loads down to 5Kohm. Board plugs into 12-way gold edge connector (supplied) and has presets for gain: 1 5dB noise figure. Supply + 24V. Board built and tested. £37 Kit £29

STEREO DISC AMP

FOR BROADCASTING AND DISC MONITORING
Magnetic cartridge to balanced lines with HF and LF filtering. Excellent distortion and overload performance. MEETS IBA SPECIFICATION.

10-OUTLET DISTRIBUTION AMP

One balanced input — 10 isolated balanced outputs
GENERAL STUDIO WORK • FEEDING MULTIPLE SLAVE PA AMPLIFIERS • DRIVING FOLDBACK HEADPHONES
Meets IBA signal path specification. Complete and boxed unit £100
Set of parts excluding case and all XLR connectors £62

PEAK PROGRAM METERS TO BS4297

also 200KHz version for high speed copying
Drive circuit, 35 x 80mm for 1mA L.H. zero meter to BBC ED1498. Gold 8-way edge con supplied.
Complete kit £13 Built and aligned £19.00
ERNEST TURNER PPM meters, scalings 1/7 OR-22 + 4 Types 642, 71 x 56mm £14; 643, 102 x 79mm £16.70; Twin movement, scale 86 x 54mm £42.00.

STABILIZER

FOR HOWL REDUCTION, BALANCED AND UNBALANCED VERSIONS BOXED OR RACK MOUNTING
PUBLIC ADDRESS : SOUND REINFORCEMENT



+ 5Hz FIXED SHEET CIRCUIT BOARDS FOR WW July 1973 article

Small enough to be built inside the cabinets of many amplifiers. Complete kit and board £24. Board built and aligned £31. DESIGNER APPROVED

SPECTRUM SHIFTER

Variable shifts 0.1 — 1000Hz for weird special effects on speech or music

SURREY ELECTRONICS

The Forge, Lucks Green, Cranleigh
Surrey GU6 7BG (STD 04866) 5997
CASH WITH ORDER less 5% UK POST FREE ADD VAT at 8%

SOFTER TRANSFORMERS

FOR SOUND RECORDING AND REPRODUCING EQUIPMENT

We are suppliers to many well-known companies, studios and broadcasting authorities and were established in 1941. Early deliveries. Competitive prices. Large or small quantities. Let us quote.

E. A. SOWTER LTD.
Transformer Manufacturers and Designers
12 Dodingham Place, Waterworks Street
Ipswich IP4 1JF. Telephone 0473 52794
WW-030 FOR FURTHER DETAILS

EURO CIRCUITS

Printed Circuit Boards — Master layouts —
Photography — Legend printing — Roller tinning —
Gold plating — Flexible films — Conventional fibre glass — No order too large or too small —
Fast turnaround on prototypes.
All or part service available NOW.....

EURO CIRCUITS LTD
Highfield House
West Kingsdown
Nr. Sevenoaks, Kent. WK 2344

Quartz Crystal Units
ACCURATE RELIABLE
Private enquiries, send 13p in stamps for brochure
THE QUARTZ CRYSTAL CO. LTD.
Q.C.C. WORKS, WELLINGTON CRESCENT,
NEW MALDEN, SURREY. 01 942 0334 & 2988

PRECISION POLYCARBONATE CAPACITORS

440V All High Stability — Extremely Low Leakage

RANGE VALUE	DIMENSIONS (mm)	PRICE EACH	± 1%	± 2%	± 5%	
0.1µF	27 12.7	51p	0.47µF	67p	50p	43p
0.22µF	33 16	64p	1.0µF	82p	62p	52p
0.25µF	33 16	67p	2.2µF	96p	75p	61p
0.47µF	33 19	80p	4.7µF	£1.62	£1.13	94p
0.5µF	33 19	87p	10.8µF	£1.96	£1.38	£1.13
0.65µF	50.8 19	93p	10µF	£2.40	£1.95	£1.64
1.0µF	50.8 19	£1.03	15µF	£3.22	£2.79	£2.24
2.0µF	50.8 25.4	£1.44	22µF	£4.28	£3.68	£3.08

*TANTALUM BEAD CAPACITORS — Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.8, 6.8µF at 15V/25V or 35V; 10µF at 16V/20V or 25V; 22µF at 6V or 16V; 33µF at 6V or 10V; 47.0µF at 3V or 6V; 100µF at 3V. ALL at 10p each. 10 for 95p, 50 for £4.

TRANSISTORS & I.C.'S

AC128 14p	BC268A/384* 10p	OC71 12p
AC176 16p	*BC547/588A 12p	*2N2926G 12p
AD149 40p	BCY72 12p	*2N2980 11p
AF178 30p	BD131/132 30p	*2N2985Y 11p
AF239 38p	BF115/167 22p	2N3054 65p
BC107/8/9 9p	BF173 22p	2N3055 50p
*BC114 12p	BF176 26p	2N3702/ 3704 11p
*BC147/8/9 10p	BF184 24p	TIP30A 52p
*BC153/154 12p	*BF194/195* 12p	TIP31A 55p
*BC157/8/9 12p	*BF196/197* 12p	TIP32A 64p
BC177 18p	BF200 27p	TIP3055 55p
*BC182/183L 11p	*BF262/263* 60p	*MPU131 49p
*BC183/183L 11p	BFY50/51/52 20p	NE555 61p
*BC184/184L 12p	BFX84/86/88 20p	741C 32p
*BC212/212L 14p	BFX85 26p	ZN414 £1.15
*BC213/213L 11p	BR101 41p	SN76013ND £1.50
*BC214/214L 11p	GET872 25p	
BC287 12p	OC44/OC45 14p	

POPULAR DIODES — 1N914 6p, 8 for 45p, 18 for 90p; 1N916 6p, 6 for 45p, 14 for 90p; 1S44 5p, 11 for 50p, 24 for £1.00; 1N4148 5p, 6 for 27p, 12 for 48p; 1N4001 54p; 002 6p; 003 6p; 004 7p; 006 8p; 007 8p.

LOW PRICE ZENER DIODES — 400MW. Tol. ± 5% at 5mA. Values available: 3V, 3.3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13V, 13.5V, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V. All at 7p each; 5 for 33p; 10 for 65p. SPECIAL OFFER: 100 Zeners for £6.00.

*RESISTORS — High stability, low noise carbon film 5%, 1/4W at 40°C, 1/4W at 70°C. E12 series only — from 2.2Ω to 2.2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (730 resistors) 65.

SILICON PLASTIC RECTIFIERS — 1.5 amp. brand new wire ended D027; 100 P.I.V. 7p (4 for 26p), 400 P.I.V. 8p (4 for 30p). BRIDGE RECTIFIERS — 2½ amp. 200V 40p, 350V 45p, 600V 55p. *SUBMINIATURE VERTICAL PRESETS — 0.1W only. ALL at 5p each; 50: 1.00Ω, 2.20Ω, 4.70Ω, 6.80Ω, 1kΩ, 2.2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 68kΩ, 100kΩ, 250kΩ, 680kΩ, 1MΩ, 2.5MΩ, 5MΩ.

PLEASE ADD 15p POST AND PACKING ON ALL ORDERS BELOW 65. ALL EXPORT ORDERS ADD COST OF SEA/AIR MAIL. PLEASE ADD 8% VAT to all items except those marked with * which are 25%.

Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona fide companies.

MARCO TRADING
(Dept. D2)

The Old School, Edstaston, Nr. Wem, Shropshire
Tel. Whixall (Shropshire) (STD 094872) 464/5.
(Proprs: Minicost Trading Ltd.)

Mail order protection scheme

Members of the Periodical Publishers Association have given to the Director General of Fair Trading and undertaking to refund the monies sent by readers in response to mail order advertisements (except for classified advertisements) placed by mail order traders who fail to supply goods or refund monies owing to liquidation or bankruptcy. This arrangement does not apply to any failure to supply goods advertised in a catalogue or in a direct mail solicitation. Publishers in membership of the Periodical Publishers Association are making these refunds voluntarily and readers' claims can only be entertained in cases where the mail order advertiser is the subject of liquidation or bankruptcy, **where proof of payment can be established** and if lodged within three months of the date on which the advertisement appeared. Any claims received after the three month period will be considered at the discretion of the publisher.

BROADFIELDS & MAYCO DISPOSALS LTD.
21 Lodge Lane, N. Finchley
London N12 8JG
Telephone: 01-445 0749 01-445 2713 01-958 7624

URGENTLY REQUIRED FOR CASH
Large quantities of radio, TV and electronic components or equipment which may be redundant or surplus to your requirements.
Will call and inspect anywhere in the U.K.

"SAVE IT" BARGAIN
500 WATT DIMMER SWITCH
(not suitable for fluorescent lights)
Basic Module with 1" Knob £2.00
Complete on MK switch plate £2.50
Larger 2" knob (BULGIN) 25p extra, P&P 25p.
Please add 8% VAT to all orders inc. P&P.
FRASER-MANNING LTD.
40 TUDDENHAM ROAD, IPSWICH, IP4 2SL

WE PURCHASE ALL FORMS OF ELECTRONIC EQUIPMENT AND COMPONENTS, ETC.
SPOT CASH
CHILTMead LTD.
7, 9, 11 Arthur Road, Reading, Berks.
Tel: 582 605

IBM GOLFBALL
COMPUTER INPUT/OUTPUT
TYPEWRITERS
STANDARD EBCDIC CODING

Will accept normal or sprocketed paper. Supplied in working order with data sheets, circuit diagram and application notes. Each machine serviced and tested
£100 + 8% VAT

As above but modified to take office range of Golf Balls.
£110 + 8% VAT.

RELAYS
Varley 2p c/o 185Ω **65p** (12p)
Varley 2p c/o 280Ω **65p** (12p)
P&B 2p c/o 1500Ω **40p** (12p)

PAPST (or similar) **FANS** 4 1/2 x 4 1/2 x 2 1/2" 100 c.f.m. 50/60 c/s **£4** (40p).

LIGHT DIMMERS 250w **£2.70** (16p)
BC107/8/9, BC147/8/9, BC157/8/9 all **9p** ea. (11p).

ELECTROLYTICS
10,000 μ 63v **£1** (25p) 2800 μ 100v **80p** (25p). 2240μ 100v **75p** (25p). 1000μ 63v **£1** (25p) 4500μ 35v **60p** (15p). 2000μ 50v **35p** (11p). 4000μ 70v **80p** (20p). 4700μ 63v **80p** (15p). 2500μ 60v **50p** (12p) 2000μ 30v **30p** (14p) 10,000μ 16v **50p** (15p)

EX-COMPUTER PC PANELS. 2 x 4" 50 boards for **£2.40** (62p).

OPCOA SCA7 7mm 7-seg led display. **£1** (12p)
QH bulbs 12v 55μ **60p** (10p)
250 mixed resistors. **60p** (18p)
250 mixed capacitors **60p** (18p)
Si recs 60A 100piv. 4 for **£1.50** (15p)
2N3055 equiv 4 for **£1** (15p)

EXTRUDED HEAT SINK for 2 x TO3 **50p** (15p)

SMALL ELECTROLYTICS
2.2μ 10v, 10μ 35v, 50μ 40v, 100μ 40v, 100μ 6v, 150μ 10v, 64μ 10v, 300μ 10v, 200μ 10v 12 for **45p** (12p).
12 for **45p** (12p)

PIHER PRESETS 100mW
220, 470 1k, 4k7, 10k, 47k, 100k, 220k, 12 for **50p** (12p)
6v 0.5A Transformer **75p** (18p)

REED RELAYS 6v coil h/d contacts 5 for **£1** (15p)

REED INSERTS h/d contacts 10 for **£1** (12p)

WATER-COOLED HEATSINKS ex. eqpt. **£1.20** (40p)

CHROMED HANDLES
5" mtg. centres per pair **£1** (20p)
8" mtg. centres per pair **£1.50** (25p)

P&P shown in brackets
ADD 25% VAT to TOTAL
8% VAT on PSUs, FANS, DIMMERS, BOARDS

KEYTRONICS
Shop open Monday-Saturday, 9-2
332 LEY STREET, ILFORD, ESSEX
01-553 1863 till 2 p.m.
01-478 8499 after 2 p.m.

TRANSISTOR ELECTRONIC ORGANS FOR THE AMATEUR

by A. Douglas Price: **£4.70**

SOLID STATE DEVICES MANUAL by R.C.A. Price: **£1.70**

UNDERSTANDING SOLID-STATE ELECTRONICS by Texas Instruments-Price **£1.40**

COLOUR TELEVISION WITH PARTICULAR REFERENCE TO THE PAL SYSTEM by G. N. Patchett Price **£5.30**

RADIO COMMUNICATION by J. H. Reyner Price **£5.50**

FOUNDATIONS OF WIRELESS & ELECTRONICS by M. G. Scroggie Price: **£4.25**

SEMICONDUCTOR CIRCUIT ELEMENTS by T. D. Towers Price: **£5.90**
PRINCIPLES OF TRANSISTOR CIRCUITS by S. W. Amos Price **£3.60**

LOGICAL DESIGN OF SWITCHING CIRCUITS by D. Lewin Price: **£5.45**

RADIO VALVE & SEMI-CONDUCTOR DATA by A. M. Ball Price: **£2.50**
GUIDEBOOK OF ELECTRONIC CIRCUITS by J. Markus Price **£15.00**

★ PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.

SPECIALISTS IN SCIENTIFIC & TECHNICAL BOOKS

19-21 PRAED STREET LONDON W2 1NP

Phone 723 4185
Closed Sat 1 p.m

BRIDGE ELECTRONICS COMPONENTS

AC 128 .13	BF 180 .25	2N2904 .18
AC 127 .13	BF 181 .25	2N2905 .18
AC 128 .11	BF 200 .25	2N2906 .18
AC 151 .18	BF 194 .09	2N2907 .18
AC 152 .25	BF 195 .09	2N2926G .09
AC 153 .27	BF 198 .12	2N3053 .20
AC 176 .14	BF 199 .12	2N3054 .40
AC 187K .27	BF 257 .38	2N4055 .48
AC 188K .27	BF 258 .24	2N3393 .12
AD 161 .35	BF 259 .24	2N4441 .56
AD 162 .35	BFX 29 .22	2N4442 .96
BA 102 .10	BFX 30 .22	2N3638 .10
BAX 13 .03	BFX 84 .20	2N3070A .10
BAX 16 .04	BFX 85 .27	2N3070 .10
BC 107 .09	BFX 88 .20	2N3073 .10
BC 108 .09	BFY 50 .19	2N3704 .10
BC 109 .09	BFY 51 .19	2N3705 .10
BC 107 .09	BFY 52 .19	2N3706 .10
BC 148 .09	BY126 .11	2N3708 .10
BC 149 .09	BY127 .11	2N3711 1.25
BC 167 .10	OA47 .06	2N3772 1.25
BC 168 .10	OA90 .04	2N3773 2.00
BC 169 .10	OA91 .04	2N3704 .11
BC 182 .09	OA200 .05	2N3906 .12
BC 183 .09	OA202 .06	2N4294 .35
BC 184 .09	IN914 .04	2N4296 .35
BC 212 .095	IN4004 .05	2N5298 .35
BC 213 .095	IN4007 .06	2N3794 .20
BC 214 .095	IN4148 .03	2N3819 .30
BC 237 .08	15920 .05	2N3820 .55
BC 238 .08	15921 .05	2N4036 .55
BC 239 .08	15923 .05	2N4037 .40
BC 308 .09	2N697 .15	2N4285 .20
BC 309 .09	2N698 .14	2N4921 .80
BC 309 .09	2N706 .10	2N5060 .25
BC 317 .12	2N708 .10	2N4289 .25
BC 318 .12	2N916 .23	2N4447 .12
BCY 10 .13	2N1305 .25	2N4449 .12
BCY 11 .13	2N1307 .25	2N4457 .30
BCY 12 .12	2N1308 .25	2N4458 .27
BD 131 .30	2N1613 .15	2N4027 .40
BD 132 .30	2N1711 .15	40361 .45
BD 135 .25	2N218 .175	40362 .40
BD 136 .26	2N218A .18	40448 .42
BD 137 .27	2N2219 .175	40409 .42
BD 138 .28	2N2219A .18	40410 .42
BD 139 .29	2N2221 .175	40602 .55
BD 140 .32	2N2221A .18	40636 1.00
BDY 56 1.00	2N2222 .175	40673 .60
BF 115 .20	2N2646 .30	

FULLY GUARANTEED

Mail order only VAT extra p&p 20p
Bridge Electronics
PO Box No. 10 Fishponds Bristol BS162LX

SERVICE AND REPAIRS

Two British ELECTRONICS ENGINEERS

resident in South Korea

offer service to importers of all types Electrical/Electronic goods manufactured to UK standards.

Prices very competitive. write: **G. and I Services, C.P.O. Box 626, Busan, Korea.**

(5115)

AUDIOMASTER BACKGROUND MUSIC . . . service. sales. Tape programmes. P. J. Equipments, 3 Onslow Street, Guildford 4801. (12)

TUBE POLISHING, mono, £5.63, colour £5.94. C.W.O. Return carriage and VAT paid. Phone: N.S. 300, Retube Limited, North Somercotes, Lough, Lincs. (27)

PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' hardware, Aluminium sheet and sections. Printed circuit board, top quality for individual or published designs.

Prompt service
Send 15p for catalogue

RAMAR CONSTRUCTOR SERVICES
Masons Road, Stratford-on-Avon
Warwicks. Tel. 4879 (38)

THOR-HOLE CONVENTIONAL P.C.B.'s gold plating, roller tinning, prototypes, silk screening, drilling. All or part service. — **ELECTRO-CIRCUITS (P.C.) LTD.**, Delamare Road, Chesnut, Herts. Tel. Waltham Cross 38600 or 20344. (84)

NEW GRAM AND SOUND EQUIPMENT

GLASGOW. Hi Fi, Cassette Decks, Tape Recorders, Video Equipment, always available we buy, sell and exchange for Hi Fi sets and photographic equipment. **VICTOR MORRIS** Audio Visual Ltd, 340 Argyle Street, Glasgow, G1, 8/10 Glassford Street, Glasgow, G2, 31 Sauchiehall Street, Tele: 041-221 8958. (11)

VALVES WANTED

WE BUY new valves, transistors and clean new components, large or small quantities, all details, quotation by return — Walton's, 55 Worcester St., Wolverhampton. (62)

COURSES

RADIO and Radar M.P.T. and C.G.L.I. Courses. Write: Principal, Nautical College, Fleetwood, FY7 8JZ. (25)

COURSES

UWIST

Department of Applied Physics and Electronics

M.Sc. / DIPLOMA COURSE IN ELECTRONICS

Applications are invited for places in the full-time one year M.Sc./Diploma Course in Electronics, commencing 29th September, 1976

Further details may be obtained from the Academic Registrar, UWIST, Cardiff CF1 3NU.

Application forms should be completed and returned to the College as soon as possible (5083)

TEACHING MACHINE
For EDP; Computers Data Input. Operators. French Manufacturing Company is seeking for a British Distributor.

DATALOGOS
124 Gambetta Ave., 94120
Fontenay — Bois, France (5120)

BOOKS WANTED

WIRELESS WORLD 1961-1975, 3 missing — offers please. **ELECTRONIC COMPONENTS.** Instruments clearance: — valves styli ferrite, transformers, switches, etc. Large SAE or 8 1/2" stamp for lists. Write Box WW 5089. (5089)

LOW FREQUENCY ANALYSER

50Hz-50kHz
ASSEMBLY AND INSTRUCTION
INFORMATION S.A.E.

PRICE £27 p&p 75p

Board, modules and all components (excluding P.U.).

12" CRT

Magnetic Deflection. Blue Trace Yellow Afterglow (P7). Information and recommended circuits with all purchases. Brand new, boxed, **£4 each**. Carriage £2.

V.A.T. at 8%

X-Y RECORDERS

Advance, Moseley
Hewlett Packard

Price from:
£80 each

CHILTMEAD LTD

7-9 ARTHUR ROAD, READING, BERKS. (rear Tech. College). Tel. Reading 582605

INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 122-132

	PAGE		PAGE		PAGE
Aero Electronics Ltd.	6, 16, 25	Electronic Brokers Ltd.	118, 119	Naim Audio	21
Alice Broadcasting (Stancoil Ltd)	8	Electrosystems & Timing Co.	16	Nombrex Ltd.	7
Ambientacoustics	106	Electronic Services & Products Ltd.	23		
Ambit International Ltd.	6, 24	Electrovalve Ltd	102	PB Electronics (Scotland) Ltd.	2
Antex Ltd	28	Euro-Circuits	134	Powertran Electronics	89, 91
A.S.P. Ltd.	99	Evershed & Vignoles Ltd.	53	Precision Petite Ltd.	14
Audix Ltd.	23	Exel Electronics Ltd.	21	Precision Instrument Laboratories	20
Avo Ltd	4, 5	Exetron Time Ltd.	120	Pulse Electronics Ltd.	20
Audio Amateur	102				
		Fi-Comp Electronics	90	Q-Max Electronics Ltd.	12
B. Bamber Electronics	129	Fraser-Manning Ltd.	134	Quartz Crystal Co. Ltd.	134
Barrie Electronics Ltd.	95	Future Film Developments Ltd.	108		
Bentley Acoustic Corp. Ltd.	107	Fylde Electronic Laboratories Ltd.	24	Radford Audio Ltd.	23
B.H. Component Factors Ltd	133			Radford Laboratories Ltd.	4
Bi-Pak Semiconductors Ltd.	114, 115	Gould Advance Ltd.	56	Radio Component Specialists	111
Bi-Pre Pak Ltd.	100	Gramplan Reproducers Ltd.	22	The Radio Shop	99
Brandenburg Ltd.	6, bound-in insert	Greenway Elec. Comps. (E. Grinstead) Ltd.	132	Ralfe, P.	106
Brenell Eng.	8	Greenwood Electronics Ltd.	10	Rank Film Equipment	22
Bridge Electronics	135			Rastronics Ltd.	121
Broadfields & Mayco Disposals	134	Harmsworth Townley & Co. Ltd.	Readers Card	R.C.S. Electronics	99
Bull, J., Electrical Ltd.	120	Harris Electronics (London) Ltd.	7, 18	Replecomps Ltd.	101
B&W Loudspeakers Ltd.	70	Harris P.	133	R.E.L. Equipment & Components Ltd.	120
Bywood Electronics	134	Hart Electronics	92	R.E.W. Audio Visual Co.	132
		Heath (Gloucester) Ltd.	13	Rola Celestion Ltd.	97
		Henry's Radio Ltd.	94	Rowngem Ltd.	22
				R.S.T. Valves Ltd.	90
Cambridge Learning	11	I.L.P. (Electronics) Ltd.	87		
Catronics	95	Icon Design	21	Service Trading Co.	112
CDI Electronics Systems Ltd	90	Imtech Products Ltd.	3	Servo Data Ltd.	95
Chiltmead Ltd.	110, 134, 136	Industrial Tape Applications Ltd	113	Servo & Electronics Sales Ltd.	103
Chromasonic Electronics	88	Integrex Ltd.	116, 117	Shure Electronics Ltd.	Cover iii
City Audio	113	Interpace Quartz Devices Ltd.	16	Sinclair Radionics Ltd.	54, 55, 68, 69
Click Shelving Ltd.	17			Sintel	92
Colomor (Electronics) Ltd.	104	J.H. Associates Ltd.	18	Sowter, E. A., Ltd.	132, 134
Combined Precision Components Ltd.	92			Southern Aviation	19
Computer Sales & Services (Equipment) Ltd	109	Keytronics Ltd.	135	Special Products Ltd.	17
Consumer Association	Loose insert	Kinnie Components Ltd.	93	Strumech Eng. Ltd.	10
Crofton Electronics Ltd.	106	Klark Teknik Ltd.	17	Sugden, J. E. & Co. Ltd.	12
Cryslon Electronics Ltd.	86			Surrey Electronics	134
C.T. Electronics Ltd.	105	Leevers-Rich Equipment Ltd.	16	Swanley Electronics Ltd.	93
		Levell Electronics Ltd.	1	Swift of Wilmslow	93
Danavox (G.B.) Ltd.	9	Linstead Electronics	7		
Datong Electronics Ltd.	16	Lynx (Electronics) London Ltd.	109	Technomatic Ltd.	108
Decon Laboratories Ltd.	18			Tequipment Products (Tektronix U.K.) Ltd.	26
Dema Electronics International	96	MacInnes Labs Limited	20	Telford Products Ltd.	12
Direct Electronics Ltd.	134	Magnetic Tapes Ltd.	24	Trampus Electronics	94
Dixons Technical Ltd.	85	Mail Order Protection Scheme	134	Turner Electronics	25
Dolby Noise Unit	116, 117	Maplin Electronic Supplies	98		
Drake Transformers Ltd.	12	Marco Trading Co.	134	Wayne, Kerr, The, Co. Ltd.	14
Drake, Philip, Electronic Ltd.	106	McKnight Crystal Co.	132	West Hyde Developments Ltd.	96
Dymar Electronics Ltd.	67	McLennan Eng. Ltd.	19	Wilmslow Audio	133
		Marconi Instruments Ltd.	Cover ii	Wireless World (The Big Four)	15
Eagle International Ltd.	25	Marshall, A., & Sons (London) Ltd.	102	Wye Electronics Ltd.	14
East Cornwall Components	107	Mills, W.	101		
Eddystone Radio Ltd.	10	Modern Book Co.	135	Z. & I. Aero Services Ltd.	5, 86
Edicron Ltd.	19	Multicore Solders Ltd.	Cover iv	Zettler (U.K.) Division	8



Microphones matter most.



Never have so few words said so much about sound system installations. The truth is that a carefully chosen, top-quality microphone makes a measurable difference in sound system quality—regardless of the other components in the system. It is false economy at its worst to be a microphone miser. Install *Shure Unidyne* or *Unisphere* microphones—for installations with a marked superiority in voice intelligibility (and fewer service calls due to microphone problems). For the name of your local sound specialist, write:

Shure Electronics Limited
Eccleston Road, Maidstone ME15 6AU
Telephone: Maidstone (0622) 59881



WW-002 FOR FURTHER DETAILS

Steve Lane

What's new in Soldering Chemicals?

Multicore's R & D Laboratories are still making news—three important new chemicals for electronics manufacturers.

MULTICORE PC 26 ROSIN FOAM FLUX

A completely new general purpose liquid soldering flux particularly suitable for the automated soldering of all types of printed circuits. PC 26 provides a unique combination of desirable properties.

- Complies with U.K. Ministry Flux Specification D.T.D. 599A.
- Eliminates "icicles" and "bridging".
- 0.5% max. halide content and yet gives better soldering than non-approved fluxes with high halide contents.
- Leaves negligible flux residues so p.c. boards are dry after soldering, can be handled and inspected easily and have better sales appeal.

MULTICORE PC 81 SOLVENT CLEANER & FLUX REMOVER

A unique blend of polar and non-polar solvents formulated for degreasing electronic hardware prior to soldering as well as for removing rosin flux residues including ionizable activators after soldering. Its intermediate boiling range of 71 to 80°C and selective solvency make it ideal for vapour degreasing.

The boiling range of PC. 81 is higher than fluorinated solvents (approx 46°C) and lower than either trichloroethylene (87°C) or perchloroethylene (121°C). Also its solvency properties for rosin flux removal are superior to fluorinated solvents without in any way affecting most electronic hardware. As a result, PC. 81 solvent will perform its vapour cleaning function longer and more effectively than fluorinated solvents whose vapour condensation ceases at 46°C with a consequent end to flux removal.

Solvent evaporation rate is substantially lower than that of the fluorinated solvents, making it more economical to use in open tanks and vapour degreasers.



Multicore PC. 81 is a highly stabilized solvent blend, extremely resistant to thermal or chemical breakdown during prolonged heating or as a result of the introduction of activators from the solution of rosin during its working life. Its relatively narrow boiling range and high stability make it readily useable again without property changes after distillation.

PC. 81 can also be used for cold cleaning and to reinforce ultrasonic cleaning. Even though its toxicity is relatively low, well ventilated areas are required.

PC. 81 is expected to be particularly welcome as it is non-flammable and non-combustible under the new British "Highly Inflammable Liquid" Regulations.

Supplied in one gallon metal cans and 45 gallon steel drums.

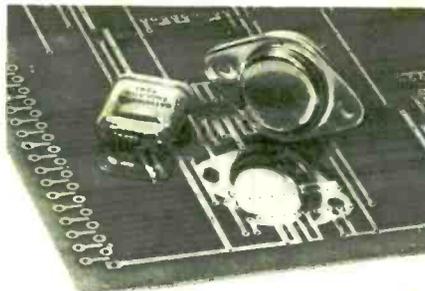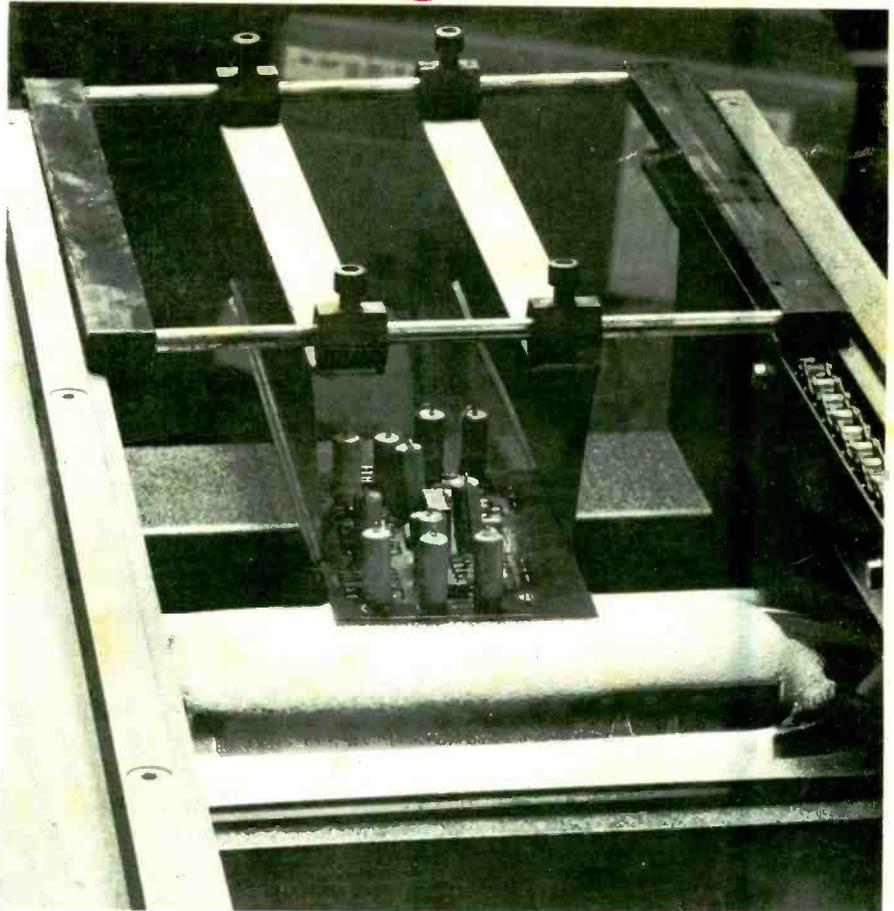Specific Gravity (20°C) — 1.256
Boiling Range — 71–80°C
Toxicity (TLV) — 340 ppm
Residue on Evaporation — less than 10 ppm



MULTICORE PC 54 CONFORMAL COATING

Fully meets the requirements of the new U.K. Defence Standard 59-47/issue 2 and U.S. Spec. MIL-I-46058C, which are becoming mandatory for the protection of many electronics assemblies against adverse environment, contamination and attack by chemicals.

PC. 54 is a two-part epoxy resin system which is conveniently mixed in equal parts by volume. It may be applied by dip, spray or brush to either one or both sides of p.c. boards and components where it forms a thin tough coating after curing. PC. 54 will dry in 1 hour under normal ambient conditions and develop its full properties after several days at room temperature or it may be cured in 2 to 4 hours at 65°C. A glass fibre brush can be used to remove the coating locally to enable rework and repair.

Other Multicore Soldering Chemicals include a complete range of liquid fluxes and the following special chemicals.

PC 2 Multicore Tarnish Remover

Cleans tarnish from metal surfaces prior to soldering.

PC 10A Activated Surface Preservative

Applied after pre-cleaning, preserves solderability and need not be removed.

PC 10D

A special version of PC 10A for application by roller coating machines.

PC 90 Peeloff Solder Resist and PC 91 Thinners

A temporary solder resist for edge-connector contact areas etc. Replaces masking tape.

PC 41 and PC 43

Solder Bath dross inhibitors.

PC 52 Protective Coating

One-part conformal coating. Can be soldered through.

PC 70 Thinners

Compatible Solvent blend for use with all rosin fluxes, PC 10A and PC 52.

Please write for Technical Bulletins on your Company's letterhead for products which interest you to:



MULTICORE SOLDERS LIMITED

Hemel Hempstead, Herts. HP2 7EP

Tel: Hemel Hempstead 3636 Telex 82363