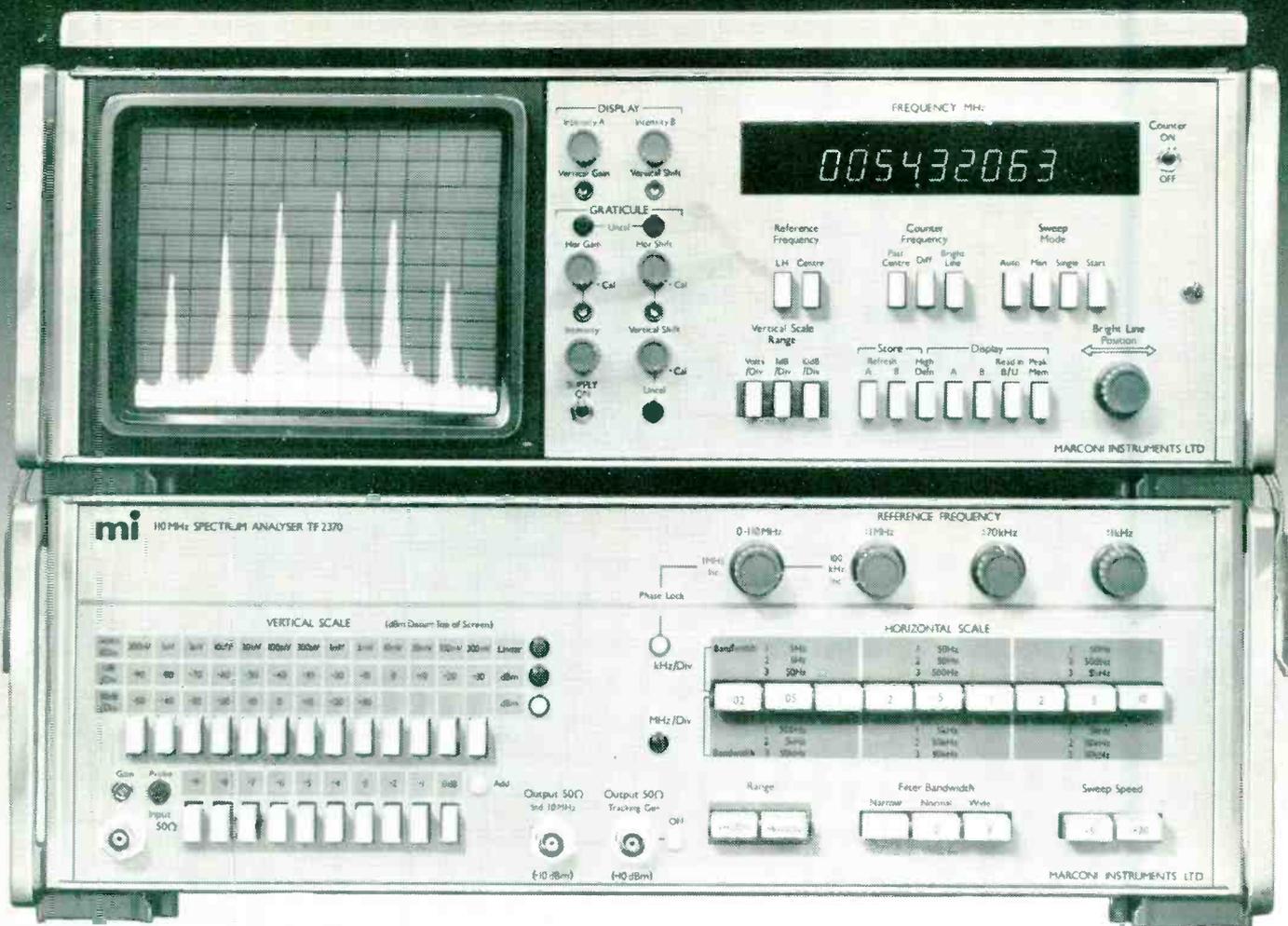


wireless world

JULY 1976 35p

Video discs
Wide-band compander

Australia \$A1.20
Canada \$1.50
Denmark Kr. 11.30
Finland Fmk. 6.20
Germany Dm. 4.50
Greece Dr. 45.00
Holland Dfl. 4.50
Italy L. 900
Malaysia M\$3.25
New Zealand \$NZ1.20
Norway Kr. 10.00 incl. postage
Portugal Esc. 40.00
South Africa R. 1.10
Spain Ptas 80.00
Sweden Kr. 6.90 incl. postage
U.S.A. \$1.50



The Most Advanced Spectrum Analyser

You've never seen a faster, more accurate way
of measuring frequency response from 30Hz to 110MHz

The TF 2370 Spectrum Analyser employs advanced technology to provide a complete system for measuring response, level, frequency, signal purity, modulation and much more, with a speed and degree of accuracy previously unobtainable. A digital memory permits the use of a standard monitor tube and internal logic selects gain ratios and sweep speeds for optimum performance. The specification speaks for itself:

- * Flicker-free 100 dB display of frequency response from 30 Hz to 110 MHz on a high brightness c.r.t.
- * Electronic graticule, with a $\pm 15\%$ variation of horizontal divisions for pin-point positioning against waveform display.
- * Three amplitude scales: one linear and two logarithmic with expansion to 1 dB/div. with an accuracy of ± 0.1 dB/dB.
- * 9-digit electronic counter automatically gives centre frequency, reads any other frequency corresponding to manually-adjusted 'bright line' position on display, or the difference frequency between the two, at the press of a

button. All to an accuracy of $\pm 2\text{Hz} \pm$ reference frequency accuracy on high resolution and manual. Internal reference frequency provided with setting accuracy of 1 in 10^7 .

- * Internal generator supplies synchronous signal source for measuring such items as networks and filters.
- * For comparative measurements, unique memory storage system will retain one display indefinitely as required, for simultaneous display with response produced by items under test.
- * Automatic adjustment of amplifier gains to give optimum lowest-noise performance with full protection against input overloading.
- * Automatic selection of optimum sweep speed.
- * With the 5 Hz filter, signals 100 Hz from a response at 0 dB can be measured to -70 dB.

Please send for full information or ask for a demonstration – seeing is believing!

mi: THE INNOVATORS

MARCONI INSTRUMENTS LIMITED,

Longacres, St. Albans, Hertfordshire, England, AL4 0JN. Telephone: St. Albans 59292 Telex: 23350.

A GEC-Marconi Electronics Company





WW-001 FOR FURTHER DETAILS

LOW COST VOLTMETERS

from the
range
of

LEVELL
PORTABLE INSTRUMENTS

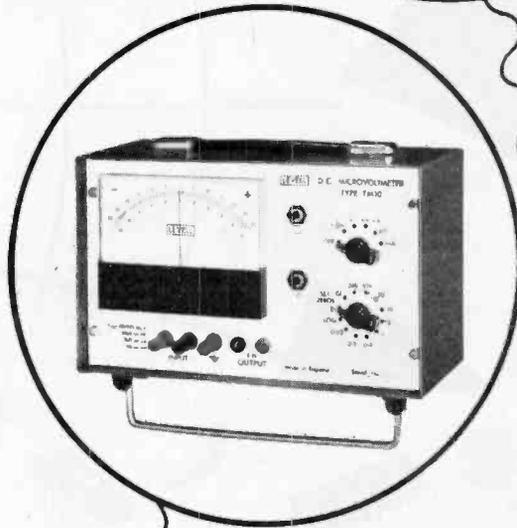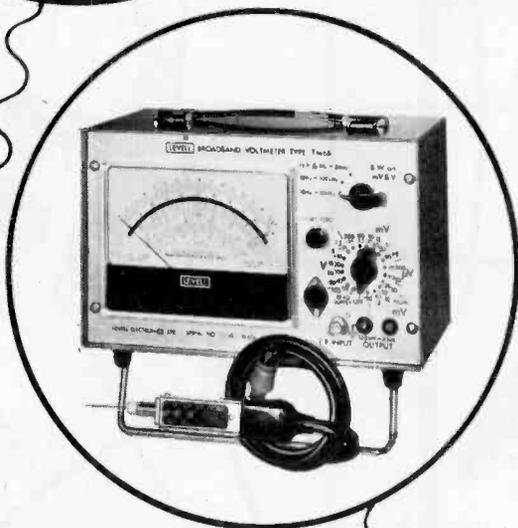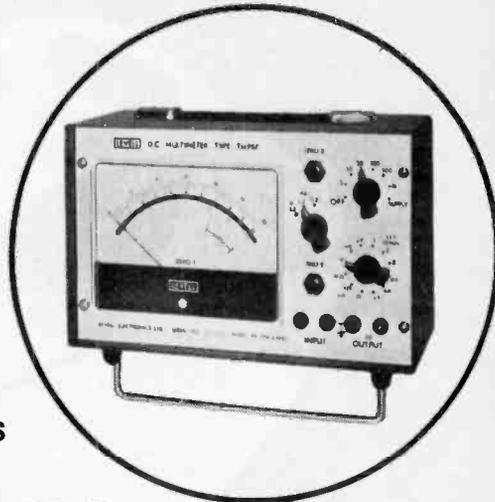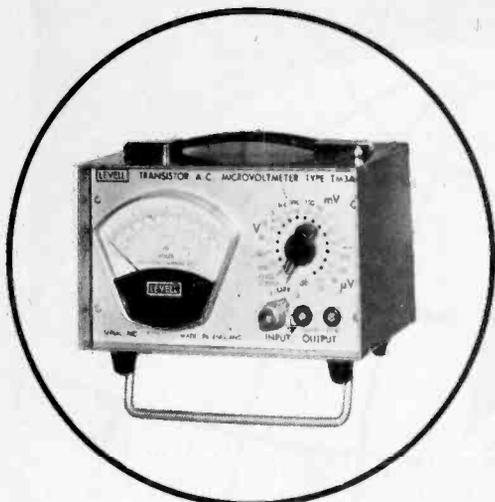SEE US AT THE LEEDS ELECTRONICS
EXHIBITION 29/30th June, 1st July



A.C. MICROVOLTMETERS
VOLTAGE & dB RANGES: 15µV, 50µV, 150µV ... 500V.
 Acc. ± 1% ± 1% f.s.d. ± 1µV at 1kHz — 100, — 90 ... +50dB
 Scale — 20dB/ + 6dB rel. to 1mW/600Ω.
RESPONSE: ± 3dB from 1 Hz to 3MHz. ± 0.3dB from 4Hz to 1MHz above 500µV. Type TM3B can be set to a restricted B.W. of 10Hz to 10kHz or 100 kHz.
INPUT IMPEDANCE: Above 50mV > 4 3MΩ < 20pf. On 50µV to 50mV : > 5MΩ < 50pf.
AMPLIFIER OUTPUT: 150mV at f.s.d.
 type **TM3A £77** type **TM3B £88**

D.C. MULTIMETERS
VOLTAGE RANGES: 3µV, 10µV, 30µV ... 1kV.
 Acc. ± 1% ± 1% f.s.d. ± 0.1µV. LZ & CZ scales.
CURRENT RANGES: 3pA, 10pA, 30pA ... 1mA (1A for TM9BP).
 Acc. ± 2% ± 1% f.s.d. ± 0.3pA. LZ & CZ scales.
RESISTANCE RANGES: 3Ω, 10Ω, 30Ω ... 1 GΩ linear Acc. ± 1% ± 1% f.s.d. up to 100MΩ.
RECORDER OUTPUT: 1V at f.s.d. into > 1kΩ on LZ ranges.
 type **TM9A £110** type **TM9BP £125**

BROADBAND VOLTMETERS
H.F. VOLTAGE & dB RANGES: 1mV, 3mV, 10mV ... 3V.
 Acc. ± 4% ± 1% f.s.d. at 30MHz. — 50dB, — 40dB, — 30dB to + 20dB. Scale — 10dB/ + 3dB rel. to 1mW/50Ω ± 0.7dB from 1MHz to 50MHz. ± 3dB from 300kHz to 400MHz.
L.F. RANGES: As TM3 except for the omission of 15µV and 150µV.
AMPLIFIER OUTPUT: Square wave at 20Hz on H.F. with amplitude proportional to square of input. As TM3 on L.F.
 type **TM6A £125** type **TM6B £135**


D.C. MICROVOLTMETERS
VOLTAGE RANGES: 30µV, 100µV, 300µV ... 300V.
 Acc. ± 1%, ± 2% f.s.d. ± 1µV. CZ scale.
CURRENT RANGES: 30pA, 100pA, 300pA ... 300mA.
 Acc. ± 2%, ± 2% f.s.d. ± 2pA. CZ scale.
LOGARITHMIC RANGE: ± 5µV at ± 10% f.s.d., ± 5mV at ± 50% f.s.d., ± 500mV at f.s.d.
RECORDER OUTPUT: ± 1V at f.s.d. into > 1kΩ.
 type **TM10 £73**

These highly accurate instruments incorporate many useful features, including long battery life. All A type models have 83mm scale meters, and case sizes 185x110x130mm. B types have 127mm mirror scale meters and case sizes 260x125x180mm.

LEVELL ELECTRONICS LTD.
 Moxon Street, High Barnet, Herts. EN5 5SD
 Tel: 01-449 5028/440 8686

Prices include batteries and U.K. DELIVERY. VAT extra. Optional extras are leather cases and mains power units. send for data covering our range of portable instruments.

WW-057 FOR FURTHER DETAILS

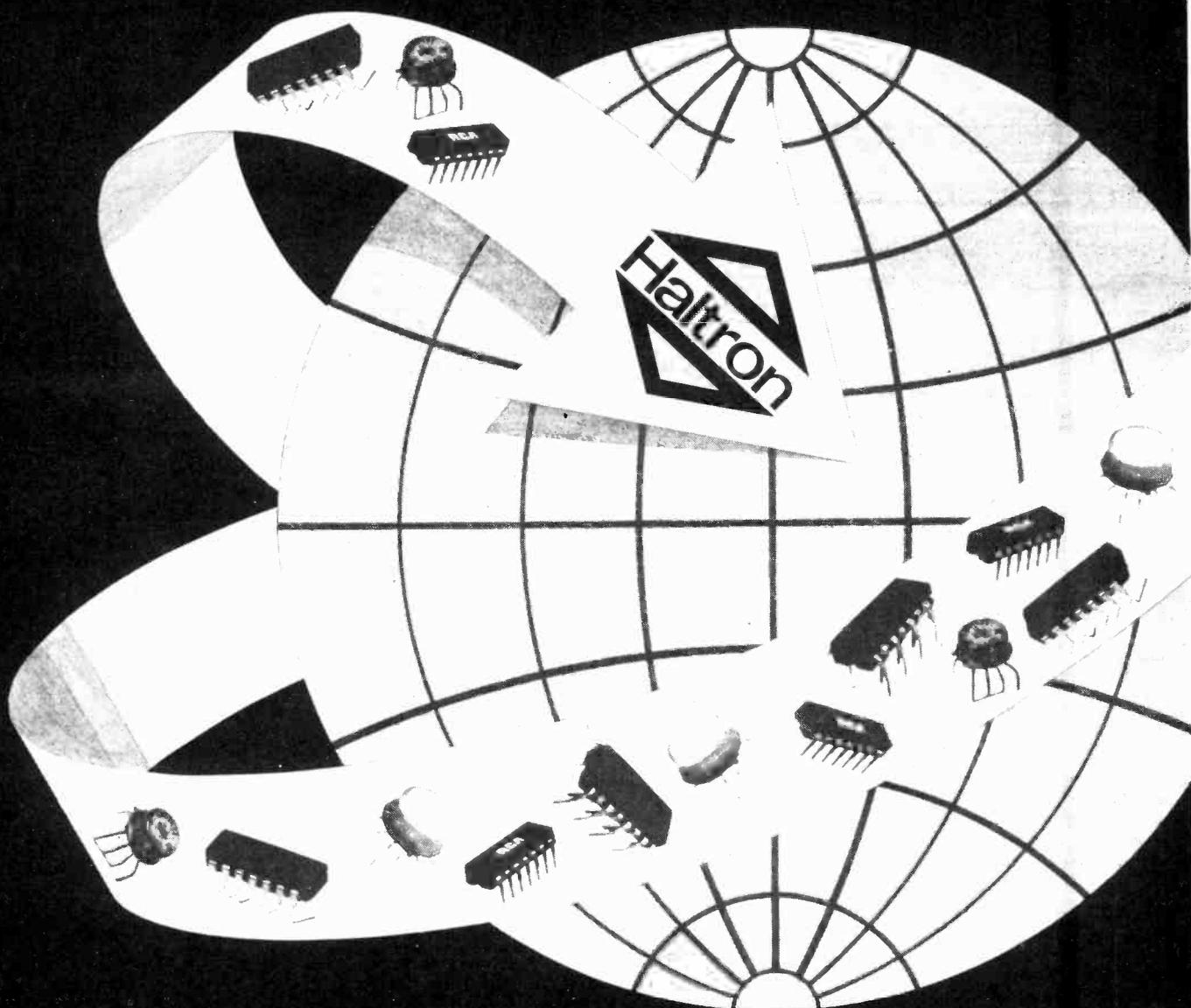

**The world over-
You get the
best service
from Haltron**

For high quality electronic valves, semiconductors and integrated circuits – and the speediest service – specify Haltron. It's the first choice of Governments and many other users throughout the world. Haltron product quality and reliability are clearly confirmed. The product range is very, very wide. And Haltron export expertise will surely meet your requirements. Wherever you are, get the best service. From Haltron.



Hall Electric Limited,
Electron House,
Cray Avenue, St. Mary Cray,
Orpington, Kent BR5 3QJ.
Telephone: Orpington 27099
Telex: 896141

WW-040 FOR FURTHER DETAILS

Not a win on the pools, a trip to a Pacific paradise, or a reduction in income tax, but distortionless "current dumping".

Z's 1 to 4 are the four passive components which interconnect the current dumpers, (the output transistors which supply the power), to the small high quality amplifier which provides the error signal, so that when the above condition is met the current in the load, the loud-speaker, is independent of the current in the dumpers and hence distortion is solely dependent on the quality of the error amplifier, which because it is small can be very good.

Wonderful indeed.

For further details on current dumping and other Quad products write to Dept. WW
The Acoustical Manufacturing Co.
Ltd., Huntingdon, Cambs.,
PE18 7DB Telephone (0480) 52561

**"Something wonderful *
happens when $Z_1Z_3=Z_2Z_4$ "**




* Elektor Electronics
Magazine No. 8. Dec. 1975

QUAD

**for the closest approach to the original sound
for twenty-five years**

QUAD is a Registered Trade Mark
WW-074 FOR FURTHER DETAILS
www.americanradiohistory.com

The British Plot!

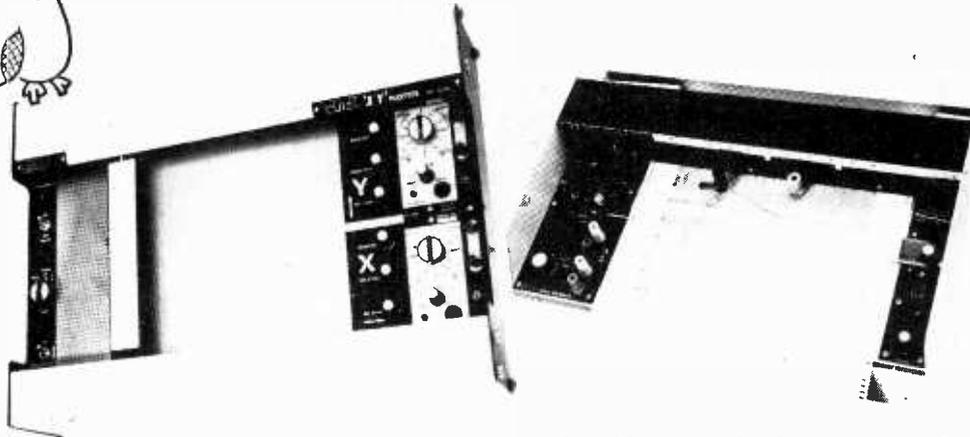

Offers exceptional value; e.g. the 2 channel CR552 Yt Recorder has a comprehensive specification (5 sensitivities, 9 chart speeds, electric pen lift, event marker, etc.) at an inclusive ex works price of £396 (excluding V.A.T.)

Improved PL100 XY/t Plotter now with increased Y axis writing speed.

New PL200 XY/t Plotter plus electric pen lift and vertical or horizontal mounting.

For industry, research and education, JJ offer rapid delivery of electrical reference, measuring and recording equipment in a wide range of prices and specifications.

Resistance Bridges; Galvanometers; Potentiometers; Decade Boxes; Dynamometers; Machine Sets; Tensile Testers; Pen Recorders.



Send for our illustrated catalogues.

J.J. LLOYD INSTRUMENTS LIMITED


Brook Avenue, Warsash, Southampton SO3 6HP, England.

Tel: Locks Heath 4221 (STD 048 95)

Telex: 477042 - JAY JAY - SOTON. Cables: Eddymes, Southampton.

WW — 059 FOR FURTHER DETAILS

Wayne Kerr's top-selling bridge

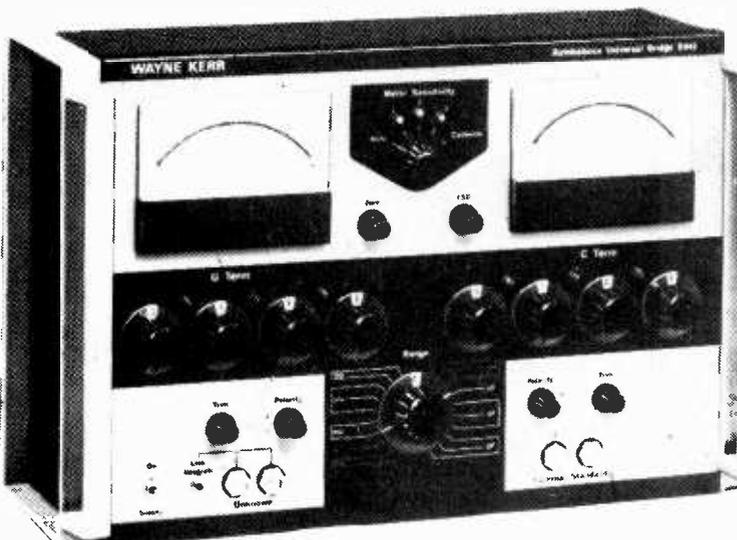

Meets modern requirements. Is accurate to 0.1%.

Is self-balancing. Has 2.3 and 4-terminal connections. Continuous readout of real and quadrature terms. Overall range 10 micro-ohms to 100 gigohms, 0.001pF to 10 farads, 1 nanohenry to 10 megahenrys and 10 picomhos to 100 kilomhos. Built-in source/detector (1592Hz).

Connectors for 200Hz — 20kHz manual operation.

Comparator facilities. Analog outputs.

Adjustable sensitivity. Ask for B642

Data Sheet.



Wilmot Breedon Electronics Limited*

Durban Road, South Bersted, Bognor Regis, West Sussex, PO22 9RL


Telephone: Bognor Regis (02433) 25811 Telex: 86120

*Incorporating FERROGRAPH · RENDAR · WAYNE KERR

WW — 043 FOR FURTHER DETAILS

3009+SL120

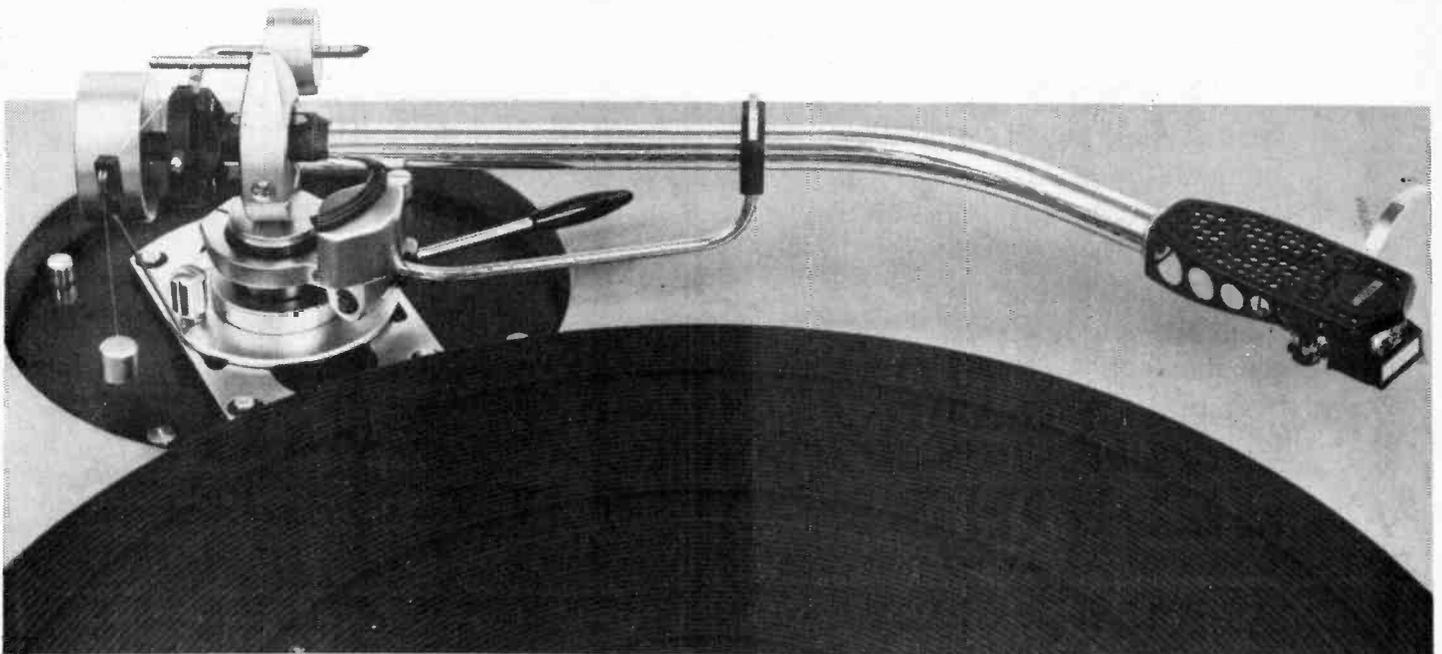This turntable offers the mechanical excellence of the SL110 in a more compact form. Ideally suited to our precision pick-up arms, its use is detailed in information sheet No. 15, a copy of which will be sent to you on request.




Write to Dept 0638 · SME Limited · Steyning · Sussex · England

SME


The best pick-up arm in the world
WW-064 FOR FURTHER DETAILS

www.americanradiohistory.com

Now over to the Test Match

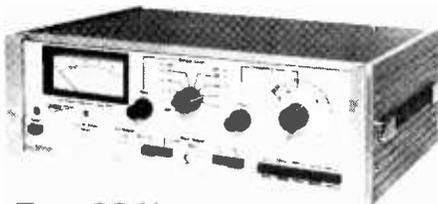

Type 2041

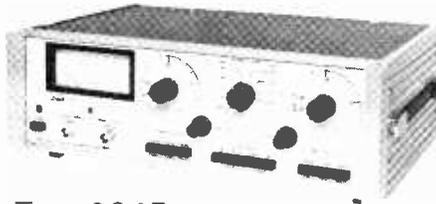

Type 2045



Type 2065

Three new additions to the Dymar communications instruments team make a perfect match. They are:
Type 2041 AF signal generator. Frequency range 3Hz to 300kHz. Maximum output 3W into 3 ohms. A combination to cover the field from audio applications to vibration analysis. Calibrated and stepped 600 ohms attenuator gives adjustable output levels from 1mV to 3V (fsd). Auxiliary output from oscillator for frequency monitoring.
Type 2045 AF two-tone signal generator.

Full audio range, 30Hz to 30kHz, with two simultaneous but independently adjustable AF tones of high stability and purity. For intermodulation testing, or for evaluating communications circuits.

Constant source impedance of 600 ohms and output levels adjustable from 1mV fsd to 1V emf (3V for a single tone).

Type 2065 AF distortion factor meter. Accurate measurement of noise and harmonic distortion of AF waveforms in the frequency range 6.4Hz to 64kHz. Handles distortion measurements down to 0.03% and can be used as a tuneable bandstop filter. Sensitivity: 300mV to 10V. Naturally, all three operate on mains or optional internal rechargeable batteries—for classic home or away performance. Ask Dymar for details or use the Reader Reply Service.

DYMAR

instruments for communications

Dymar Electronics Limited, Colonial Way,
 Radlett Road, Watford, Herts. WD2 4LA, England.
 Telephone: Watford 37321. Telex: 923035.
 Cables: Dymar Watford.

Gardners

The Best of British

Where performance is paramount, professionals prefer Gardners...

We, at Gardners, have been in the communications business for many more years than we care to remember — so have our Audio Transformers. Used throughout the world by leading broadcasting and recording companies or wherever only the highest technical standards and levels of reliability are good enough our products are still preferred by professionals who know...

From microphone to tape (or film), speakers or headphones, studio consoles, manpacks, amplifiers, modems, we at Gardners have tried to anticipate your needs. Miniaturisation (yes!) plus good performance (yes!) through to exceptional performance (of course!). Impedance changing, coupling, isolation, bridging, low and high power, with or without D.C. Choose from our standard range of 95 models! Every one an example of sheer professionalism.

All have low loss, low distortion, low phase-shift, low pick-up, BUT wide frequency range.

Cat. No.	Impedance Input	Impedance Output (OHMS)	Turns Ratio Sec/Pri	Operating Level dBm at 50Hz	Frequency Response
MU 7501	0.3/15	100k	83/188 1	B	± 1 dB 50Hz—10kHz
MU 7503	0.200/600	100k	13/23 1		
MU 7514	600	600/2.4k	1 1/1 1		
MU 7518	10k CT	10k	1 1 CT		
MU 7521	3.75/15	600 CT	6.32/12.64 1	16.5	± 0.5 dB 30Hz—20kHz (* ± 1dB at 20kHz)
MU 7522	3.75/15	100k*	82/164 1		
MU 7524	150/600	600 CT	1/2 1		
MU 7525	600 CT	300/1.2k	1 1/1 1.41 CT		
MU 7530	10k CT	10k	1 1 CT	20	± 0.5dB 10Hz—100kHz
MU 7534	50/200	100k*	22.4/44.8 1		
MU 7566	600 CT	10k/2.5k	4.08/2.04 1		
MU 7567	600/150	50k	9.13/18.26 1		
MU 7582	200/50	600 CT	1.73/3.46 1	4.75	± 1dB 30Hz—22kHz
VM 7461	15/3.75	600	6.35/12.7 1		
VM 7464	600/150	600	1/2 1		
VM 7466	600	10k/2.5k	4.14/2.07 1		
VM 7468	50/12.5	50k	32/64 1		± 1dB 30Hz—12kHz

We would emphasise that the above is a representative selection only. Send for Brochure GT5 for complete listings. All units described are normally AVAILABLE FROM STOCK.

SPECIAL DESIGN SERVICE. If your requirements cannot be met by our standard range, then we will gladly design for your production needs.



Gardners

Gardners Transformers Ltd.
Christchurch Dorset BH23 3PN
Telephone 02015-2284
Telex 41276 Gardners XCH
Approved manufacturers of
electronic transformers, modular power supplies, inverters and
converters to Defence Standard 05-21

WW — 044 FOR FURTHER DETAILS



With our New
**ORYX
SUPER 30**
soldering iron
we have a slight
problem
at £2.95* how
do we convince
you that it is a
precision tool.

Our reputation for professional soldering equipment has been built on our precision products, so we have taken extreme care to see that our new ORYX Super 30 iron at, dare we repeat it, only £2.95, is going to be the best at its price.

* plus VAT at 8%

Here are some of the features you get as standard:

- A neon Safety Light,
 - A long life element,
 - Iron coated screw-on tip,
 - Stainless steel shaft,
 - Styled handle,
 - A two-minute element change, and a Stainless steel clip-on hook.
- You can have further technical information, or by ordering one now you will see why we call it the Super 30.

Illustration actual size.

Greenwood Electronics

Greenwood Electronics, Portman Road, Reading, RG3 1NE
Telephone: 0734-595844. Telex 848659

WW — 027 FOR FURTHER DETAILS

Grampian slot easily into this modular age...



GRAMPIAN REPRODUCERS LTD.
HANWORTH TRADING ESTATE, FELTHAM, MIDDLESEX,
ENGLAND. TEL: 01-894 9141

Grampian introduced the modular plug-in concept for building multi facility sound installations, together with solid state audio switching over three years ago. Since then many hundreds of complex installations have been supplied and have set a standard for reliability under the most stringent conditions. All equipments are built to a necessary engineering standard and not down to a price with its ultimate high cost of ownership. All amplifying equipments supported by an extensive range of manufactured microphones, loudspeakers and all items required for sound installations by the firm of forty years standing in the sound business.

X222

WW067 FOR FURTHER DETAILS

Problem.

Where to obtain devices for push-pull audio power amplifiers which give good linearity and don't blow up on the slightest overload.

Solution.

M-OV audio beam tetrodes. A pair of KT66s will give up to 50W and a pair of KT88s will give up to 100W. And M-OV audio triodes, too: a pair of DA42s gives up to 200W and a pair of DA 100s gives up to 300W.




LAP81

**EEV and M-OV
know how.**

THE M-O VALVE CO LTD, Hammersmith, London, England W6 7PE
Tel: 01-603 3431. Telex: 23435 Grams. Thermionic London **SBC** 
WW — 054 FOR FURTHER DETAILS

ELECTRONIC INDUSTRIAL THERMOMETER

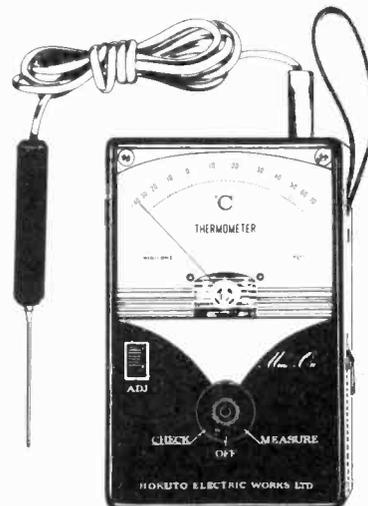

THE MODERN WAY TO MEASURE TEMPERATURE

A Thermometer designed to operate as an Electronic Test Meter. Will measure temperature of Air, Metals, Liquids, Machinery, etc., etc. Just plug-in the Probe, and read the temperature on the large open scale meter. Supplied with carrying case, Probe and internal 1 1/2 volt standard size battery

Model "Mini-Z 1" measures from -40° C to + 70° C

Model "Mini-Z 2" measures from -5° C to + 105° C

Model "Mini-on Hi" measures from + 100° C to + 500° C

PRICE £20.00 each (VAT 8% EXTRA)

Write for further details to

HARRIS ELECTRONICS (LONDON),
138 GRAY'S INN ROAD, LONDON. WC1X 8AX
(Phone 01-837 7937)

WW — 021 FOR FURTHER DETAILS

- P.A. SYSTEMS FOR AIRPORT, HOTEL, FACTORY.
- THEATRE AND LECTURE THEATRE AUDIO SYSTEMS
- AUDIO MIXING EQUIPMENT
- SIMULTANEOUS TRANSLATION SYSTEMS
- RADIO AND T.V. BROADCAST SOUND CONTROL EQUIPMENT
- MARINE INTERCOMMUNICATION AND ENTERTAINMENT EQUIPMENT
- *System design, manufacture and installation.*



audix

AUDIX LIMITED
 Wenden, Saffron Walden, Essex CB11 4L9
 TEL. Saffron Walden (0799) 40888: TELEX: 817444




INLAND MOTOR amplifiers and motors

NEW!

DC SERVO AMPLIFIER

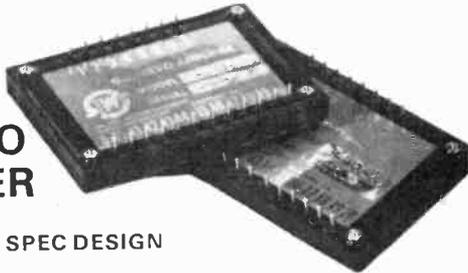EM-1800 SERIES
 25-300 WATT MIL SPEC DESIGN



Features:

- Small size for package flexibility
- Wide band-width for fast servo response
- Voltage or current feedback to provide low or high impedance output.
- Adjustable gain for maximum flexibility.
- Current limiting to prevent demagnetization of a DC torque motor and for short circuit protection.

Applications:

- DC Torque Motors
- Other DC Servo Motors
- Deflection Coils
- Servo Valves
- Low Inertia Motors.

DIRECT DRIVE TORQUE MOTORS
TACHOGENERATORS
BRUSHLESS MOTORS
SERVO MOTORS
 for
Aerospace/Military applications.

Inland products are available from plants in USA or Europe. Motors for tapedrives, capstan drives and instruments are also available.



hightech
 COMPONENTS LTD.

Inland UK Representatives
 219 Kings Road, Reading RG1 4LS Berkshire
 Telephone: Reading (0734) 68980/65929 Telex: 847032

WW-066 FOR FURTHER DETAILS

DIGITAL CLOCKS
NEW PRICES



"DELTA"
 12 hour from
 4 RED 0.5" LEDs

£9.00

	STD	ALARM
Module Kit (excl. case)	9.00	11.50
Module: Assembled (excl. case)	9.50	12.00
Complete Clock Kit Perspex Case	12.00	15.00
Complete Clock Kit Teak Case	12.70	15.70
Ready built Clock Perspex Case	17.00	21.00
Ready built Clock Teak Case	17.70	21.70

Perspex Case Colours: Black, White, Red, Blue, Green, Orange. Available separately £4.40

Built Alpha Units: State 12 or 24 hour
2-YEAR GUARANTEE ON READY BUILT CLOCKS

MODULES

KITS CALCULATORS
NEW MODELS

ALARMS: Built-in alarm: Tilt operated snooze
 AM/PM indicator: Power failure indicator


"ALPHA"
 4 GREEN 0.5" DIGITS
 12/24 hour

£10.00

	STD	ALARM
Module Kit (excl. case)	10.00	13.00
Module Assembled (excl. case)	11.00	14.00
Complete Clock Kit Perspex Case	12.50	15.50
Ready-built Clock Perspex case	17.50	21.50

NOVUS CALCULATORS
 650 £5.40
 850 £6.75


Send S.A.E. for complete range

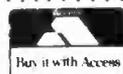

CWO. PULSE ELECTRONICS LTD (E.1), 202 SHEFFORD ROAD, CLIFTON, SHEFFORD, BEDS. Tel. Hitchin (0462) 814477

FAST RESPONSE STRIP CHART RECORDERS


Made in USSR

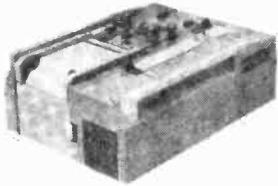

Type H3020-1
Single pen

Specification

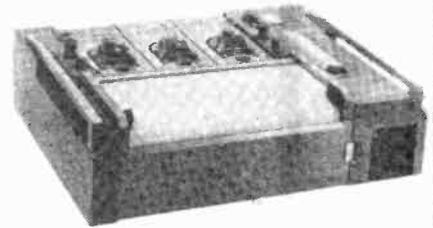Basic error.....2.5%
Sensitivity.....8mA F.S.D.
Response.....0.2 sec.
Width of each channel.....80mm
Chart speeds, selected by
push buttons.....0.1-0.2-0.5-1-2.5-
-5-12.5-25mm/sec.
Chart drive.....200-250v 50Hz



Type H3020-3
Three-pen

Recording:

Syphon pen directly attached to moving coil frame, curvilinear co-ordinates

Equipment:

Marker pen, Timerpen, Paper footage indicator, 10 rolls of paper, connectors, etc.

Dimensions:

H320-1: 285x384x16.5mm
H320-3: 475x384x16.5mm

PRICE: H320-1 £108.00
H320-3 £160.00
Exclusive of VAT

Available for immediate delivery

Z & I AERO SERVICES LTD.

44A WESTBOURNE GROVE, LONDON W2 5SF

Tel. 01-727 5641

Telex: 261306

WW — 046 FOR FURTHER DETAILS

Autocrat

The absolute leader in its class

Farnell offer the only
DIGITAL MULTIMETER
with all these features

- ★ AUTORANGING (with hold) ★ AUTOPOLARITY
- ★ AUTOZERO ★ SIX RESISTANCE RANGES
- ★ LARGE DISPLAYS ★ A.C. & D.C. VOLTS & CURRENTS
- ★ TEMPERATURE MEASUREMENT

DM 131
(mains powered)

£147

DM 131/B
(mains/battery)

£173



Details from: Farnell Instruments Limited · Wetherby · W. Yorks LS22 4DH
Telephone · 0937 3541 or 01 864 7433

WW — 053 FOR FURTHER DETAILS

Keep your tools handy in case...



With JENSEN
special quality industrial
tool kits and cases


Send now for details of the superb Jensen range of tools, meters and accessory equipment, all in the most handy and robust cases — also available separately. Jensen products are specifically designed for industrial use, perfect for all engineers, technicians, electricians, instrument repairmen etc. Choice of more than twenty kits and cases.

Write for free Jensen catalogue to:

SPECIAL PRODUCTS DISTRIBUTORS LTD,
81 Piccadilly, London W1V 0HL. Tel: 01-629 9556. Cables: Specipro London W1.

WW — 071 FOR FURTHER DETAILS

LOW-COST INSTRUMENTS

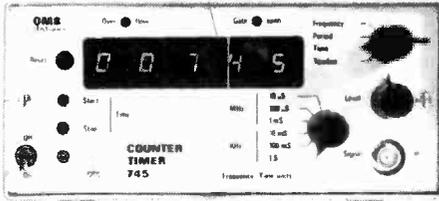

VALUE!

£82
+ £2.00 p.p.
+ VAT

745 COUNTER TIMER

Measures frequency, period, time and totalises
32 MHz frequency range (DC coupled)
5-digit .3" LED display
6 Gate times/Time units, 10µs to 1 S in decades
Sensitive, protected FET input WW 048



744 COUNTER TIMER
£79 + £2.00 p.&p. + VAT

Measures frequency, period and time
30MHz frequency range (DC coupled)
5-digit, long-life incandescent display
Sensitive, protected FET input
WW 049




643 FUNCTION GENERATOR
£86 + £2.00 p.&p. + VAT

Accurate, digital frequency setting
.01Hz-1MHz
Wide range external control of frequency
Triangle, Squarewave and Low Distortion
Sinewave outputs
50Ω + simultaneous outputs
DC offset WW 050

*Delivery is normally ex-stock—telephone for confirmation
Prices correct at time of going to press, subject to change without notice*

OMB ELECTRONICS
Riverside, Eynsford, Kent DA4 0AE
Tel. Farningham (0322) 863567

FREQUENCY COUNTERS
HIGHER PERFORMANCE INSTRUMENTS FROM
1/10 Hz to 1.2 GHz. MEASURING FREQUENCY,
PERIOD, TIME, FREQ./RATIO AND CALIBRATED
OUTPUT FACILITY. FAST DELIVERY.

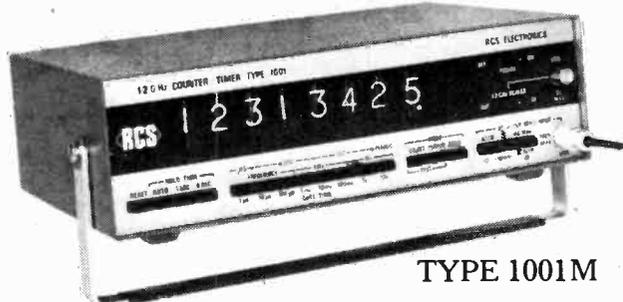

TYPE 1001M

CRYSTAL OVEN
OPERATING MANUAL
TWO TONE BLUE CASE **£670 1.2 GHz**

Sensitivity 10mV. Stability 5 parts 10.¹⁰

301M	32MHz 5 Digit £82	401	32MHz 6 Digit £121
501	32MHz 8 Digit £178	701A	80MHz 8 Digit £195
801A/M	300MHz 8 Digit £305	901M	520MHz 8 Digit £375
801B/M	250MHz 8 Digit £262	1001M	1.2GHz 8 Digit £670

Start/Stop versions plus **£12** Memory versions available if not
suffixed M **£25 extra**

Type 101 1MHz 100KHz 10 KHz Crystal Standard **£85**
Type 103 Off/Air Standard **£85**

SUPPLIERS TO: Ministry of Defence, G.P.O., B.B.C., Government Dept., Crystal
Manufacturers and Electronic Laboratories world-wide



R.C.S. ELECTRONICS
6 WOLSEY ROAD, ASHFORD
MIDDX. TW15 2RB
Telephone: Ashford (Code 69) 53661/2

WW — 014 FOR FURTHER DETAILS

**Now nothing
can touch our
new standard
range of
encapsulated
toroids!...**

**WITH 5 POWER RATINGS
now available
"OFF-THE-SHELF"**



Our standard range of toroidal transformers are
now encapsulated to give full protection and
present a more attractive component.
Power ratings from 15VA to 130VA
Comprehensive range of secondary voltages to
suit most power supply requirements.



Full details from
Avel Lindberg Ltd., South Ockendon, Essex RM15 5TD.
Telephone: South Ockendon 3444. Telex 897106

WW—077 FOR FURTHER DETAILS

NEAL STEREO
NEAL 3 CHANNEL AUDIO VISUAL
NEAL 4 CHANNEL RECORDERS



140 Series
4 Channel

CASSETTE
RECORDERS
FOR THE
PROFESSIONAL
USER

Special models
to order

NEAL Range includes: 102AV, 103AV STEREO AV DOLBY
 102, 103 STEREO DOLBY 140SERIES 4 CHANNEL
 110 MONO AV DOLBY 104 HEAVY DUTY REPLAY

NEAL

TRANSCRIPTION CASSETTE RECORDERS
 NORTH EAST AUDIO LIMITED


5 Charlotte Square, Newcastle upon Tyne NE1 4XE. Telephone (0632) 26660

WW-056 FOR FURTHER DETAILS

**Switching problems?
 Rely on Zettler.**

Producing 30 basic types of relay and 15,000 variants with regard to contact stacks, terminals, energizing current and contact material, Zettler is among the largest manufacturers of electro-mechanical components.

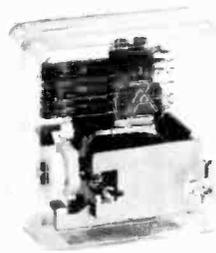Our product range comprises:
 Low profile (flatform) · Timing · Miniature · Low contact capacity · Hermetically sealed · Stepping · Mains switching · Latching Contact stacks · Solenoids



Stepping Relay AZ 170

Contacts are mechanically latched and thus unaffected by supply interruption. Regular contact configurations from 1 make up to 3 changeovers. Heavy duty version with 1 make or 1 changeover. Switching capability: 3 A at 125 V AC. Coil voltages: 6 to 110 V DC.

We resolve your switching problems rapidly and expertly. Please contact us for further details.



ZETTLER Zettler UK Division
 Brember Road, Harrow, Middx. HA2 8AS. Tel. (01) 422 0061

Please look us up at
Leetronex, Leeds, 29 June-1 July, 1976

A member of the worldwide ZETTLER electrical engineering group, est. 1877

WW-008 FOR FURTHER DETAILS

Valradio TRANSVERTORS
 TRANSISTORISED INVERTERS



VALRADIO TRANSVERTORS ARE BEING USED ALL OVER THE WORLD FOR MANY APPLICATIONS, INCLUDING: VIDEO TAPE RECORDERS, SOUND TAPE RECORDERS, ALARMS, LABORATORY EQUIPMENT, TELEVISIONS AND MANY OTHER TYPES OF EQUIPMENT.


SOME TYPICAL TYPES ARE:

- D24/500S 24v DC input 500 watts sine wave output 230v AC **£217.20**
- D12/150T 12v DC input 150 watts square wave 230v output **£47.55**
- D24/60S 24v DC input 60 watts sine wave 230v output **£66.95**

We also manufacture Frequency Changers, Power Supplies and Standby Systems, and we are always happy to quote for your special requirements. All prices plus VAT

Please send for full details to
VALRADIO LIMITED, BROWELLS LANE, FELTHAM, MIDDLESEX, TW13 7EN
 Tel. 01-890 4242/4837

WW-036 FOR FURTHER DETAILS

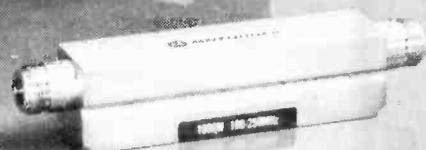

**MOTOROLA
 IN-LINE WATTMETER**

Measures power output from transmitter and reverse power from antenna.

Compact and light weight (approx. 1 lb)


Frequency range 2MHz to 19Hz.

Measures RF power from 1W to 1KW.

System includes a series of wide range RF elements which can be left permanently in-line in the transmission cable — measurements can then be taken without disconnecting the antenna.

MOTOROLA ELECTRONICS LTD.,
 444 BATH ROAD, SLOUGH, BERKS.
 TELEPHONE: BURNHAM 62427 TELEX: 847121.

WW-018 FOR FURTHER DETAILS

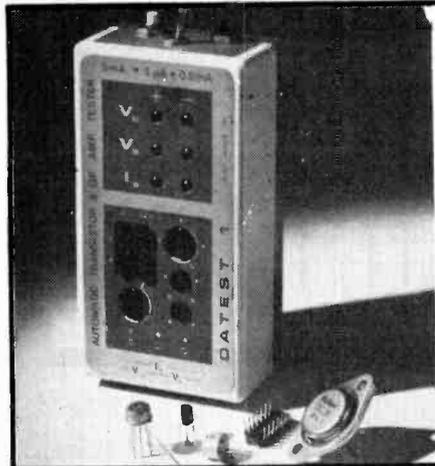

DATEST 1: THE NEW TIME SAVER

Automatic device tester and identifier

DATEST 1 saves valuable repair time by *automatically* testing diodes, transistors, and all types of FETs, both in and out-of-circuit, plus common op. amp. i.c.s out-of-circuit.

To carry out a test simply connect the device and switch on. If the display flashes its "No Go". If you get a steady pattern it's "Go". No prior knowledge is required of device polarity or whether it is bipolar or FET. On the contrary, the clear six-LED display tells you at a glance the polarity of the device (NPN, PNP, N-channel, P-channel) and for out-of-circuit tests whether it is bipolar, depletion FET, or enhancement FET. If you then flick the test current switch you can instantly place limits on current gain, leakage current, and FET parameters. Finally if you need to you can even plug in a multimeter and actually measure some of them. DATEST 1 with its advanced four i.c. and six transistor circuit (pat. appl. for) rapidly pays for itself in skilled man hours saved and in expensive mistakes avoided. For complete user confidence DATEST 1 even stops working abruptly and gives a special display when battery voltage has dropped to too low a value. DATEST 1 is available now and comes complete with battery, easy-to-use probes for in-circuit tests, and detailed handbook. Write for full details or send now for your own "time saver". Price £49 plus 8% VAT, cash with order.


DATONG ELECTRONICS LIMITED

11 Moor Park Avenue, Leeds LS6 4BT
Telephone: 0532 755579

WW-035 FOR FURTHER DETAILS

THIS IS IT!

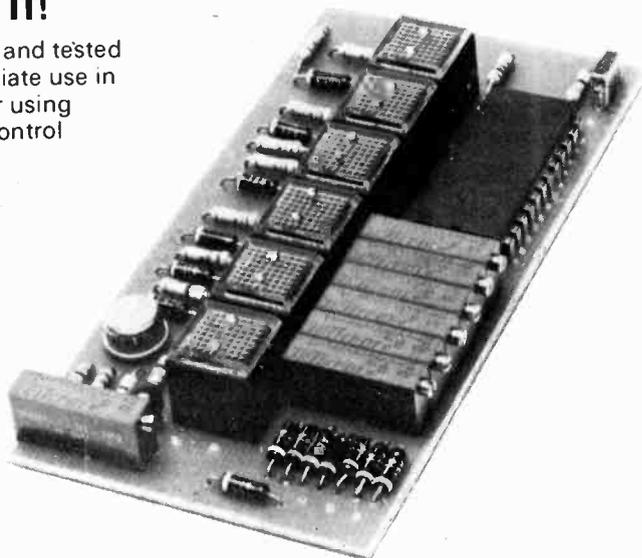Fully built and tested for immediate use in ANY tuner using Vari-cap control



TOUCH TUNE PRE-SELECT UNIT

Shown here with meter drive components from Kit K12 mounted on same P.C.B.



Our Tuner is now fully updated and improved. If you intend to build, you must buy our new booklet fully describing our updated tuner. (50p post free, refundable on orders over £10)



NOW IS THE TIME TO BUY!

Our prices were **reduced** in April. Now VAT has been halved. Will things ever be quite this good again? Make use of your credit card and buy now with confidence. We give full after-sales service and guarantee with all parts and kits.

- 6 channels plus manual.
- Illuminated touch buttons.
- 20 volts supply.
- Full instructions for use.
- Fully built and tested.
- Available now, post free.
- Introductory price £16.71 inc. V.A.T.
- See May's advertisement for full lists and prices, or write to:

Icon Design

33 Restrop View
Purton, WILTS.
SN5 9DG


JES AUDIO INSTRUMENTATION

Illustrated the Si453 Audio Oscillator SPECIAL FEATURES:

- ★ very low distortion content—less than 0.03%
- ★ an output conforming to RIAA recording characteristic
- ★ battery operation for no ripple or hum loop
- ★ square wave output of fast rise time

£50.00

also available

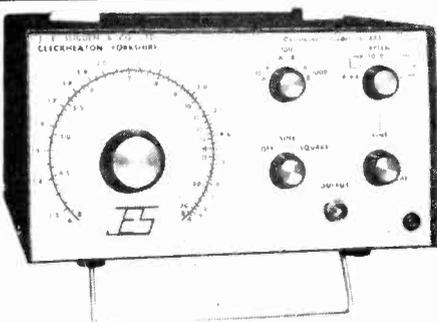

Si451 Millivoltmeter

- ★ 20 ranges also with variable control permitting easy reading of relative frequency response

£50.00

Si452 Distortion Measuring Unit

- ★ low cost distortion measurement down to 0.01% with comprehensive facilities including L.F. cut switch, etc.



£40.00

ALL PRICES PLUS VAT

J. E. SUGDEN & CO. LTD., CARR STREET, CLECKHEATON, W. YORKS. BD19 5LA.

Tel. 0274-872501

WW-079 FOR FURTHER DETAILS

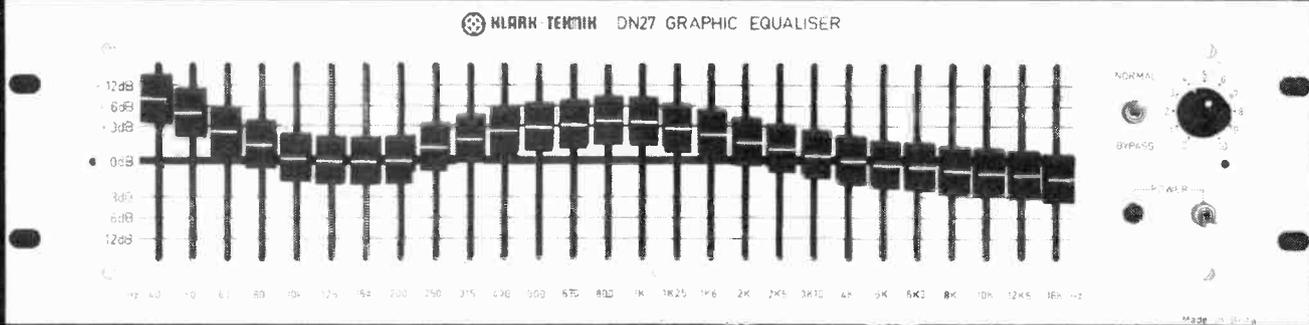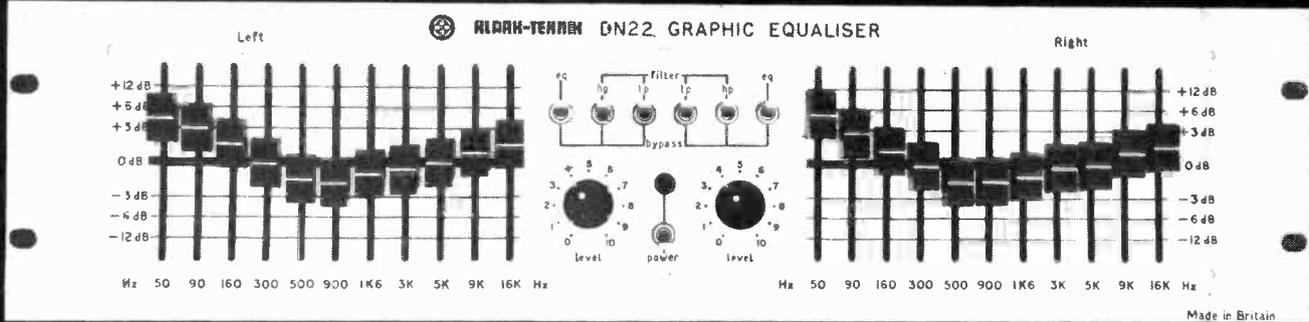

Better Performance than any Graphic Equaliser on the market

BUY BRITISH  **BUY KLARK-TEKNIK RESEARCH LIMITED**
 Summerfield Kidderminster DY11 7RE
 Tel Kidderminster 64027

WW — 045 FOR FURTHER DETAILS

NEW FROM STRUMECH

Electric powered winch (1:10 vch/5 amp).
 Bolts directly onto existing towers without modification. Send for leaflet.
 Price £115 ex works.

VERSATOWER
 Strumech Engineering Limited
 Coppice Side, Brownhills, Walsall, West Midlands
 Telephone: Brownhills 4321

WW — 011 FOR FUTURE DETAILS


DATA AND COMMUNICATIONS TERMINALS

Teletype 28, 32, 33, 35, 40
 TermiNet 30, 300 & 1200 (30 and 120 cps)
 Teleterm 1030 & 1132 (portable 30 cps with integral coupler and RS 232C)
 Other page printers (by Siemens, ITT Creed, etc.)
 TermiNet 120 line printer

- ★ Spares, repairs, overhauls and maintenance
- ★ Other types and models available
 - ★ Refurbished units also available
 - ★ Short and long period rentals
 - ★ Minicomputer interfaces
 - ★ Quantity discounts
 - ★ Immediate delivery

TELEPRINTER EQUIPMENT LTD.
 70-80 AKEMAN STREET,
 TRING, HERTS., U.K.

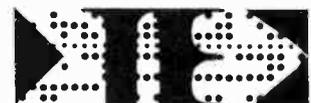Telephone 0442-82-4011
 Cables RAHNO Tring
 Telex 82362
 A/B Batelcom Tring



WW—010 FOR FURTHER DETAILS


AMCRON POWER AMPLIFIERS

The AMCRON range of DC-coupled power amplifiers are used by Government, and University Research Departments as well as by Industry for a variety of applications ranging from Shaker, and Vibrator driving, to driving both AC and DC Motors, providing variable frequency power supply, or high voltage material testing. All models are DC-coupled throughout, with Intermodulation, and Harmonic Distortion below 0.05%, damping factor of at least 400 from DC to 1 kHz, and the ability to operate into load impedances from 1 ohm to infinity even into highly reactive loads.



M600

RMS power out 750 watts into 8 ohms
1,350 watts into 4 ohms
Power bandwidth DC to 20 kHz + 1 db - 0 db
Phase response + 0' - 15' DC - 20 kHz
Slew rate 16 V/μsecond
Hum & noise 120 db below 600 Watts
Dimensions 19" std rack, 8¾" H, 16½" Deep

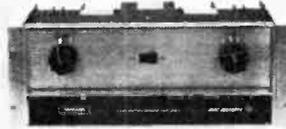

DC 300A

500 watts rms into 2.5 ohms (1 chan)
DC-20kHz + 1 db - 0 db
+0, - 15' DC to 20kHz
8 volts per microsecond
At least 110db below 150 watts
19" Rackmount, 7" High, 9¾" Deep



D150A

200 watts into 2.5 ohms (1 chan)
DC-20 kHz + 1 db, - 0 db
+ 0', - 15' DC to 20 kHz
6 volts per microsecond
At least 115 db below 90 watts
19" Rackmount, 5¼" H, 8¾" D. Deep



MACINNES LABORATORIES LTD.

MacInnes House, Carlton Park Industrial Estate
Saxmundham, Suffolk IP17 2NL. Tel: (0728) 2262 2615


MACINNES FRANCE

45 Rue Fessart
Paris 75019, France
Tel: 203-30-01

WW-006 FOR FURTHER DETAILS

itam

ITAM 805 (8TRACK) MASTER RECORDER

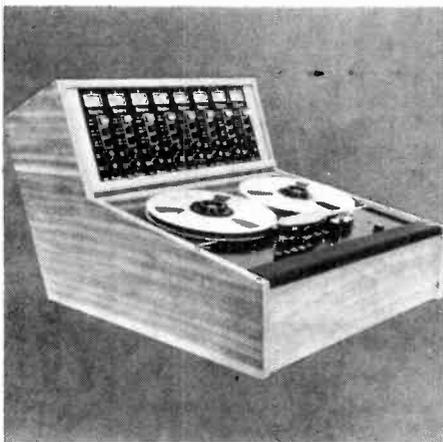

Fully modular electronics using plug-in PCB's throughout. Separate sync and replay amps give identical levels. Switchable VU's with slow decay. Individual oscillator for each channel. Dolby A switching facility. Comprehensive facilities include sync on all channels, servo controlled capstan, modular electronics, variable speed (optional), relay-solenoid operation. Compact presentation for easy portability.

£1790 + VAT Full console optional extra.

Compatible 8-output Mixer available
£1260 + VAT

OTARI

OTARI DP-4050 CASSETTE COPIER



Ideal for one copy or ten thousand. Eight times copy speed, foolproof operation for non-skilled personnel, modular construction, servo-controlled direct capstan drive.

Immediate delivery.

THESE ITEMS ARE INDUSTRIAL PRODUCTS AND SUBJECT TO 8% VAT

Industrial Tape Applications



5 Pratt Street, London NW1 0AE
Telephone: 01-485 6162. Telex: 21879


WW - 069 FOR FURTHER DETAILS

Alice Broadcasting

USA: CCA ELECTRONICS CORPORATION
NEW JERSEY
TELEX 84-5200

CANADA: CALDWELL AV. EQUIPMENT CO. LTD.
TORONTO
TELEX 06-963645

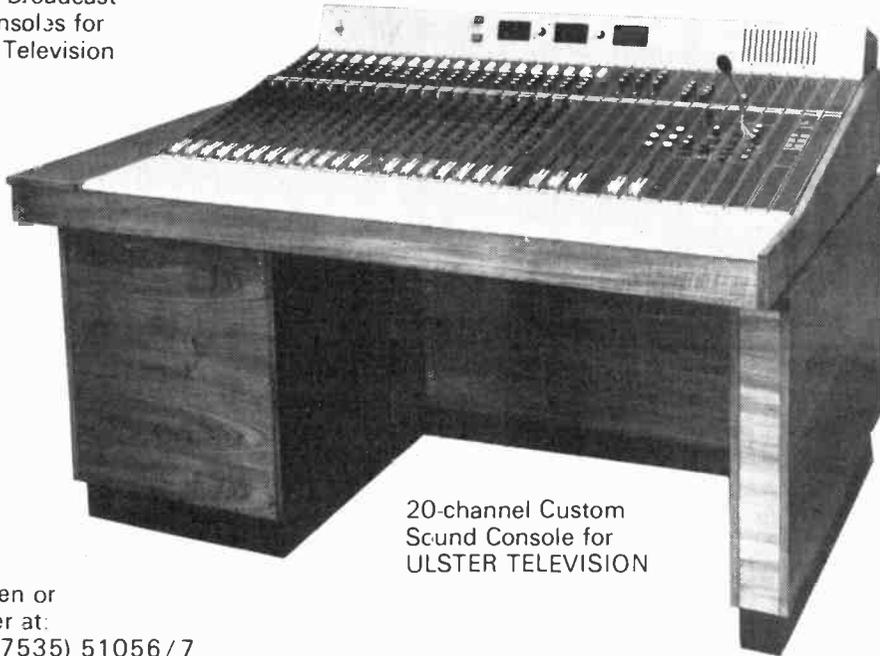AM Series Broadcast
Mixing Consoles for
Radio and Television



JAPAN: TAITO BOEKI LTD.
TOKYO 106
TELEX J2-2498

20-channel Custom
Sound Console for
ULSTER TELEVISION


Contact:
Chris Walden or
Ted Fletcher at:
Windsor (07535) 51056/7

Alice

(Stancoil Ltd.), Alexandra Road, Windsor, Berks. Telex 849323 AEGIS G

TPA SERIES - D

integrated circuit
power amplifier

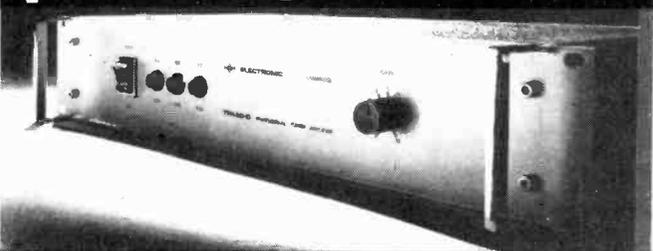

TPA 50 - D Specification

Power Output	100 watts rms into 4 ohms 65 watts rms into 15 ohms
Freq Response	± 0.1 dB 20Hz to 20KHz into 15 ohms. -1dB at 150KHz
Total harmonic distortion	Less than 0.04% at all levels up to 50 watts rms into 15 ohms
Input sensitivity	0dBm
Noise	-100dB
Rise time	2 μ seconds
Price	£77 plus V.A.T.

100V Line (C.T.) and balanced inputs available.

For full technical information contact:

H/E ELECTRONIC

CAMBRIDGE ROAD, MILTON, CAMBS
TELEPHONE CAMBRIDGE 65945/6/7

WW - 023 FOR FURTHER DETAILS

Test Equipment



Multimeters

The Eagle range of multimeters covers every possible need of the electrical or electronic engineer. They cost from about £6 to £58 (inc V.A.T.). There's at least one which suits your job precisely.

We have a lot of other test equipment too. Send the coupon and we'll send you our complete catalogue.

Please send me details of all your test equipment

NAME

ADDRESS



Eagle International Ltd., Precision Centre, Heather Park Drive, Wembley HA0 1SU
Tel(01)-902 8832

Eagle

WW - 030 FOR FURTHER DETAILS

THE 'MISTRAL' 1 DIGITAL CLOCK

★ COMPLETE KIT ★



- Pleasant green display · 12/24 Hour readout
- Silent Synchronous Accuracy · Fully electronic
- Pulsating colon · Push-button setting
- Building time 1 Hr. · Attractive acrylic case
- Easy to follow instructions · Size 10.5x5.7x8 cm
- Ready drilled PCB to accept components

KIT PRICE £10.25

+ 82p VAT P&P inc.

THE 'MISTRAL' 2 DIGITAL ALARM CLOCK

★ Fully Built, Tested and Guaranteed ★
WITH SLEEP-OVER FEATURE




- Soft Green Display
- 24 Hour Alarm
- 10 Minute Repetition
- Alarm Set Indicator
- Accurate Silent Timekeeping
- British Designed and Built

**COMPLETE CLOCK
£12.99**

+ £1.04 VAT P&P inc.



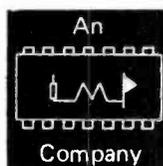Available direct or from: Henrys, Electro-value, Electotime, Metac, Bywood, Crofton, Swanley, Orchard Radio Shop, Progressive, Radio, etc.



IMTECH PRODUCTS LTD

IMP HOUSE, ASHFORD ROAD
ASHFORD, MIDDX. TW15 1XB W
telephone ASHFORD 44211 (4 lines)
telex 936291 WESSIMP ASHFORD

Cash, Cheque or Postal Order or if you wish to use Barclaycard or Access, simply quote name, address and card number when ordering.

SUMMER SALE DEDUCT 10% FROM THE PRICES SHOWN HERE. OFFER CLOSES JULY 31st 1976

min. CWO £1.

LINEAR ICs

CA3089E	1.94	7805KC	1.75*
KB4402	1.94	7805UC	1.55*
TDA1200	1.94	78L12	0.45*
HA1137W	2.20	78M12	1.20*
CA3090AQ	3.75	TDA1412	0.95*
MC1310P	2.20	7812	1.55*
KB4400	2.20	7815	1.55*
CA3053	0.40	78M20	1.20*
CA3088E	1.50	78M24	1.20*
LM1496	1.02	uA723	0.80*
		NE550	0.80*
MC1350P	0.70	LS8038	3.10*
SN7666ON	0.75	NE555	0.70*
TBA120AS	1.00	NE560	2.50
TBA651	1.81	NE561	2.50
uA720PC	1.40	NE562	2.50
uA753	0.99	NE565	2.50
TDA440	1.75	NE566	2.55*
		NE567	2.50*
LM380	1.00	MVAM2	1.05
LM381N	1.81	BA102	0.30
LM3900	0.68*	BA121	0.30
MC3401	0.68*	MV104	0.45
uA741	0.40*	MEM615	0.38
TBA810AS	1.09	MEM616	0.50
TCA940E	1.80	11C90	14.00*
TDA2020	2.99		

DISCRETE

ZTX107n	0.14
ZTX108n	0.14
ZTX109n	0.14
ZTX212p	0.16
ZTX213p	0.16
ZTX214p	0.16
ZTX413n	0.18
ZTX551p	0.18
ZTX451n	0.18
BF224n	0.22
BD515n	0.27
BD516p	0.30
BD165n	0.50
BD166p	0.54
BD535n	0.52
BD536p	0.53
BD609n	0.70
BD610p	1.20
BD377n	0.29
BD378p	0.32
1N4001	0.06
1N4004	0.10
1N4148	0.07
OA91	0.08
DL704	0.95*
SLA1	1.25*

Modules, tuners

5600	Varicap Mosfet with 4 tuned RF ccts.	11.00
EC3302	Varicap FET/Bipolar min. tunerhead.	5.50
9001	Frequency meter, scale 88 - 108.	2.50
9002	Strength meter, scale 0 - 10.	2.50
9007	Tuning meter, scale 3 - 0 - 3	2.50
7700	'Off-air' UHF TV sound receiver Varicap tuned, with interstation muting, and sound detection at 38 MHz (Built). inc. P.S.U.	26.00
8011	6 station electronic station selector for any positively tuned varicap tuner system, incorporating a muting output, AFC lock and scan tuning. Built.	14.99
7252	Top quality tuner VHF to audio Varicap tuned with 3 meter outputs.	24.00
7253	Tuner with built-in stereo decoder. Varicap tuned.	24.00
8319	Dual Mosfet tunerhead as used in 7252.	12.00
2020k	TDA2020 stereo amplifier kit.	7.85
202CHS	Heatsink for one TDA2020 (only with IC).	0.75
8001k	55kHz low pass filter (birdy filter) for stereo radio (between detector and decoder).	1.75

Suffix 'k' indicates kit, otherwise supplied built and tested.

NEW MODULES (EDGE TERMINATED)

5619	6 stage, dual mosfet UHF tunerhead.	£12.50
7020k	10uV FM IF system with muting, agc, main tuning voltage AFC system.	£4.50
92310k	Comprehensive 1310 decoder, with notch filters and 5x gain.	£5.35

ambit INTERNATIONAL

General Terms: CWO please, official bodies and companies please note min. invoice £7.50. PP for CWO orders 22p per order. (UK and Eire). Overseas customers please include sufficient for postage. VAT is not included, and must be added at 12½%, but where items are marked * only add 8%. In stock orders despatched within 48 hours.
25 High Street, Brentwood, Essex. Tel: (0277) 216029, Telex: 995194.

D.M.W.

D.M.W. ASSOCIATES (ELECTRONICS) LIMITED

Time code generators' translators, tape search systems with manual or computer control

A comprehensive range of airborne and ground based Time Code Generators, Translators, and Tape Search Units. The equipment is used in conjunction with instrumentation and other types of magnetic Tape Recorders, for efficient data acquisition and analysis. Manually operated equipment and fully computer controlled systems are available. The computer controlled systems include installation, commissioning and checkout software. A design service for special time code applications is also available.

High-power wideband linear amplifiers




A comprehensive range of wideband linear amplifier systems covering the frequency range 500 kHz-60 MHz is available. A wide range of power output is available by combination of basic modules. Hybrid couplers for power splitting and combining, sub-octave high power switched filters, and automatic aerial matching units are also available. The company also offers a design and development service for special systems.

HIGH SPEED VIDEO ANALOGUE TO DIGITAL AND DIGITAL TO ANALOGUE CONVERTERS AND SYSTEMS.

VIDEO INSERTION UNITS

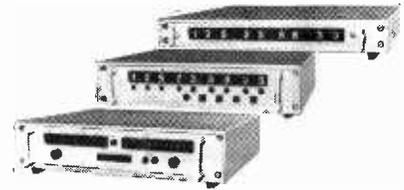SYSTEMS
STUDY—DESIGN
ENGINEERING
AND
INSTALLATION



RESEARCH AND DEVELOPMENT FACILITIES COVERING A WIDE RANGE OF TECHNOLOGY

DMW Associates (Electronics) Ltd
6-8 Morris Road
Royal Oak Industrial Estate
Daventry, Northamptonshire
Great Britain, NN11 5PD
Telephone: Daventry (032 72) 71472

BIMBOARD

Stop Ruining Your I.C.'s And Wasting Time Soldering
Plug Into The Revolutionary New

BIMBOARD


The Only Professional Quality Breadboard That
Accepts All DIL Packages With 6 To 40 Pins

Incorporates Bus Strips For Vcc And Ground

Includes A Component Support Bracket

Has Over 500 Individual Sockets

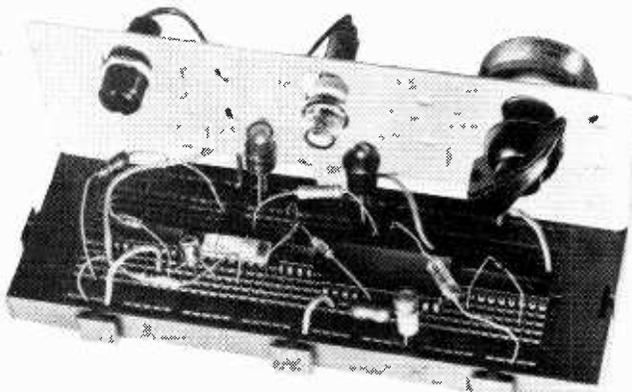And Allows You To Use And Re-Use
IC's, Transistors, LED's, 7 Segment Displays,
Diodes, Resistors, Capacitors




Only £9.72 (cheque with order) Including VAT and P.P.
Special Quantity Discounts Available For
Radio Clubs, Retail Outlets, Distributors

BOSS INDUSTRIAL MOULDINGS LTD

Higgs Industrial Estate, 2 Herne Hill Road, London, SE24 0AU, England
Telephone 01-737 2383 Telex 919693

Why resist?

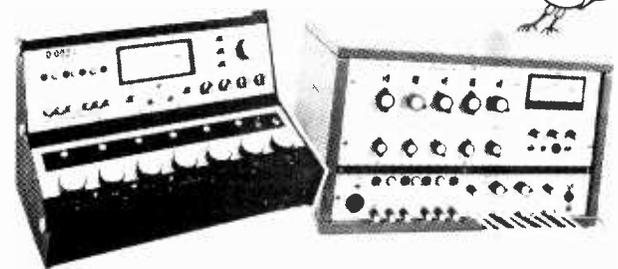

With a calibration accuracy of
5 ppm and a resolution better than 0.1 ppm, the
JJ BR150/10 a.c. bridge is particularly suited to precision
resistance thermometry.

The BR100 d.c. bridge will calibrate an eight decade
resistance box on every setting of every decade
to within 2 ppm in less than 5 minutes.

For industry, research and education, JJ offer rapid delivery of
electrical reference, measuring and recording equipment in a
wide range of prices and specifications.

**Resistance Bridges; Galvanometers; Potentiometers; Decade Boxes;
Dynamometers; Machine Sets; Tensile Testers; Pen Recorders.**

Send for our illustrated catalogues:

JJ
INSTRUMENTS

J.J. LLOYD INSTRUMENTS LTD.

Brook Avenue, Warsash, Southampton
SO3 6HP, England.

Tel: Locks Heath 4221 (STD 048 95)

Telex: 477042 - JAY JAY - SOTON.

Cables: Eddymes, Southampton.

WW-058 FOR FURTHER DETAILS

Contractors to H.M. Govt. P.O.

REPAIRS

OF ELECTRICAL MEASURING INSTRUMENTS
7-14 DAYS SERVICE

◀ MODEL 8 MK.V




STOCKISTS
ALSO SUPPLIERS OF GEC
RISSO AND OTHER
MULTI-RANGE TEST SETS

WE SPECIALISE IN ASSEMBLIES, AND IN THE
REPAIR, CALIBRATION AND CONVERSION
OF ALL TYPES OF INSTRUMENTS, INDUSTRIAL
AND PRECISION GRADE

LEDON INSTRUMENTS LTD.

GLADSTONE WORKS, GLADSTONE RD,
FOLKESTONE, KENT.
TEL: (STD) 0303 57555

WW — 031 FOR FURTHER DETAILS

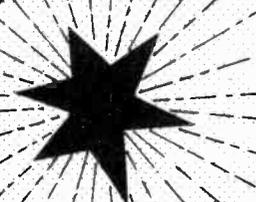

a star is born..

ROTEX

Emmen Holland

ask for our catalogue!



FREQ. COUNTERS
RFC 30
RFC 250



LIGHTORGANS
3X500 AND
3X1000 WATT



2MTR. RECEIVER



STEREO MIXERS 6 MODELS



POWER SUPPLIES
PS.2
0.30V
2 A



LIGHTDIMMERS

and a large variety
of electronic
modules

sales only via wholesale dealers
RADIO ROTOR EMMEN HOLLAND
P.O. BOX 260, TELEF. 01031-5910-16810, TELEX 53910

WW — 012 FOR FURTHER DETAILS

servos synchronous steppers dc motors



gearboxes and control systems



Stockists for **IMPEX Motors** **McLennan**

McLENNAN ENGINEERING LIMITED
Kings Road Crowthorne Berks Telephone: Crowthorne 5757/8

WW — 005 FOR FURTHER DETAILS

PRECISION PETITE LTD.

119A HIGH STREET, TEDDINGTON, MIDDX.
TEL. 01-977 0878

Now with the:


• NEW MK. II DRILL •


10,000 r.p.m., 120
cmg.

“MORE POWER — MORE TORQUE”

12v. - 14v. DC
DRILL ONLY £8.00
(P.P. 35p)
STAND £3.76
(P.P. 35p)
Incl. VAT

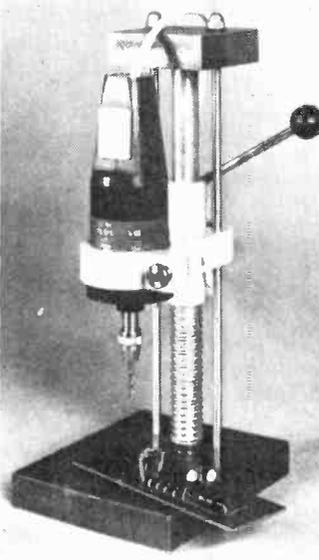(Together 50p P.P.)
SAE for illustrated
leaflet and order form



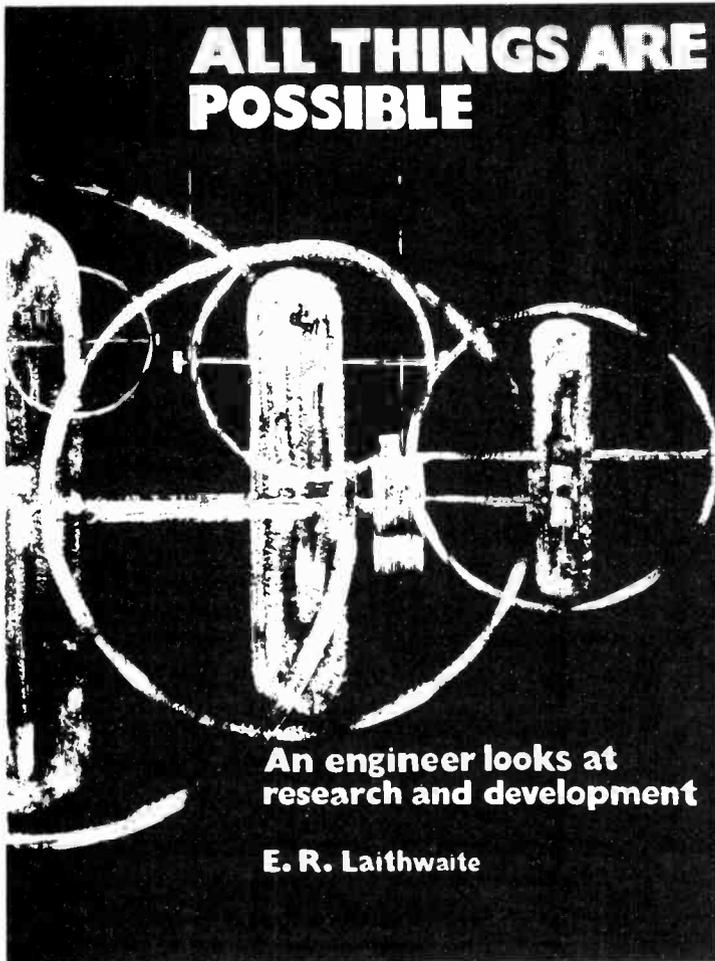

ALL THINGS ARE POSSIBLE

An engineer looks at research and development

E. R. Laithwaite

All Things are Possible

In this, Professor Laithwaite's seventh book, he again offers us a rich mixture of controversial and always thought provoking articles. In the manner that we have learned to expect, he conveys through his writings and experiments the excitement of engineering and invention, and the ways in which man in his laboured progress has so often merely mimicked nature's own engineering achievements.

The author, famous in the academic world and for numerous television appearances, presents us with two series of articles, 44 in all, which will appeal to the engineer, scientist and all interested readers equally. The price of the book is £2.85.

From leading newsagents and bookshops, or can be ordered direct by using the coupon below.

Order Form

To General Sales Dept., Room 11, Dorset House, Stamford St., London SE1 9LU.
 Please send me..... copy/copies of "All Things are Possible" at
 £2.85 each post free.
 I enclose remittance value £.....
 IPC Business Press Ltd.)

Name (Please Print).....
 Address.....

(Cheques made payable to
 Company regd. in England No. 677128
 Regd. office: Dorset House, Stamford St., London SE1 9LU

COIL WINDING



Manufacturers of all wound components including transformers, chokes, stators and armatures. Prototype and design service available.

Electric Windings' factories are equipped to handle large or small volume production. Vacuum impregnation plants provide varnish impregnation for all temperature requirements.

ELECTRIC WINDINGS (LONDON) LTD.
(Dept. WW) Avenue Works, Gallows Corner
Romford, ESSEX RM3 0AJ

Ingrebourne 46677

A NEW DIMENSION IN SOLDERING

Iso-Tip Cordless Soldering Iron

Ideal for factory, field servicing, laboratory or home, the Iso-Tip Cordless offers a great advance in soldering. It is completely portable, heats in 5 seconds and recharges automatically in its own stand.


The Iso-Tip is powered by long-life nickel cadmium batteries giving tip performance up to 50 watts with a temperature of 370°C. Tips are available in five different sizes ranging from Micro to Heavy Duty to meet all soldering requirements.



Greenwood Electronics
Portman Rd, Reading RG3 1NE, England.
Telephone: Reading (0734) 595844.
Telex: 848659.

WW — 026 FOR FURTHER DETAILS

METER PROBLEMS?

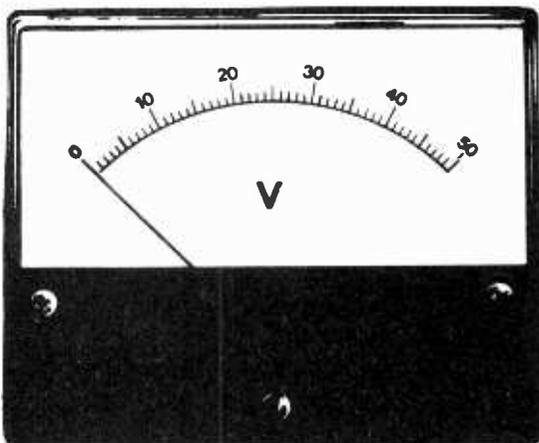

137 Standard Ranges in a variety of sizes and stylings available for 10-14 days delivery. Other Ranges and special scales can be made to order.

Full Information from:

HARRIS ELECTRONICS (London)
138 GRAYS INN ROAD, W.C.1 Phone: 01/637/7937

WW — 022 FOR FURTHER DETAILS

ELECTRONORGTECHNICA

carbon film

RESISTORS

1/8 and 1/4w 70°C 5% tol. E.12
EX-STOCK

£4.50 PER 1,000 PLUS
OF ONE VALUE V.A.T.

Contact John Gingell

Z & I

AERO SERVICES LTD.

44A Westbourne Grove
London W2 5SF
TEL: 01-727 5641 TELEX 261306

WW-080 FOR FURTHER DETAILS


**QUARTZ
CRYSTALS
-FAST!**



AEL GATWICK HOUSE, HORLEY, SURREY, ENGLAND
Tel: Horley (02934) 5353
Telex: 87116 (Aerocon Horley) Cables: Aerocon Telex Horley

WW-039 FOR FURTHER DETAILS

PRINTED CIRCUIT BOARD TRANSFER SYSTEMS

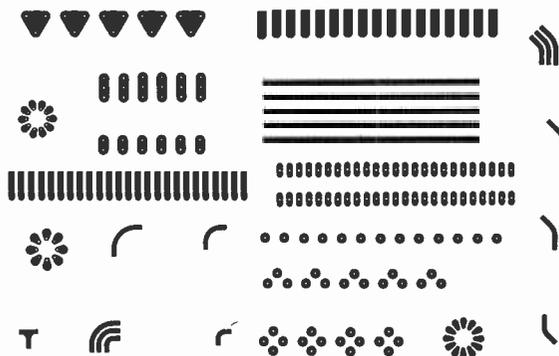

Acid resistant transfers for direct application to P.C. Board. This is a new approach to printed circuit board manufacture, giving a professional finish with all details that an electronics engineer would require, including all drilling positions automatically marked.

Ideal for single unit boards or small quantities. All at a very low cost—for example an average 6" x 4" layout would cost less than 30p, and the time taken under one hour, including etching to complete.

The system is simple, briefly it consists of 10 sheets of self adhesive acid resistant transfers made in required shapes — i.e. edge connectors, lines, pads, dual in line I.C.s, 8-10-12. T.O.5 Cans, 3-4 lead transistors, etc., etc., which only require pressing into the required positions on the printed circuit board before etching.

The printed circuit transfer system is a genuine offer to the public and industry, A full money back guarantee is sent with each order, trade prices on application.

List of Prices


Complete system including post and VAT	£2.95
Individual sheets	30p
Sample sheet	30p
Ex. U.K. Post Extra	£1.00

Printed circuit board PCB transfer systems patent applied for

E. R. NICHOLLS, 46 LOWFIELD ROAD, STOCKPORT, CHESHIRE
TELEPHONE NUMBER 061-480 2179

GROOVAC

vacuum record cleaner

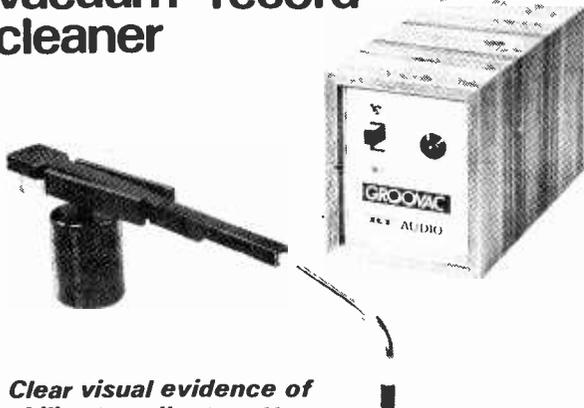

Clear visual evidence of ability to collect matter

Hi Fi News, May '76

Silent and most effective

Hi Fi Answers, Aug '75

Can you hear the difference? Definitely yes

Gramophone, Dec '75

Exhaust silencer virtually eliminates noise

Gramophone, Dec '75

Price £15.95 inc VAT, p & p 75p

Leaflets and Reviews available


- ★ BIAS FOR PERFECT TRACKING
- ★ NEW SILENCER
- ★ STRONGER SUCTION

Supplied with — both magnetic and self adhesive mounting nozzle cleaning brush spare filter adjustable height

RI AUDIO

Kernick Road, Penryn Cornwall TR10 9DQ, England Telephone: Penryn 72753

WW — 051 FOR FURTHER DETAILS

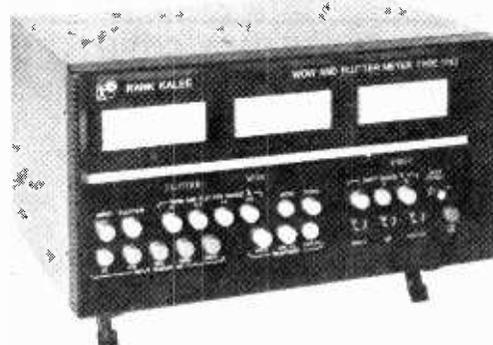

The new Rank

WOW & FLUTTER Meter Type 1742

Fully transistorised for high reliability

Versatile

Meets in every respect all current specifications for measurement of Wow, Flutter and Drift on Optical and Magnetic sound recording/reproduction equipment using film, tape or disc

High accuracy

with crystal controlled oscillator

Simple to use

accepts wide range of input signals with no manual tuning or adjustment

Two models available:

- Type 1742 'A' BS.4847: 1972 DIN 45507 CCR 409-2 Specifications
- Type 1742 'B' BS 1988: 1953 Rank Kaler Specifications

For further information please address your enquiry to

Mrs B. Nodwell

Rank Film Equipment, PO Box 70

Great West Road, Brentford


Middlesex TW8 9HR

Tel: 01-568 9222 Telex 24408 Cables Rankaudio Brentford



RANK FILM EQUIPMENT

WW — 013 FOR FURTHER DETAILS

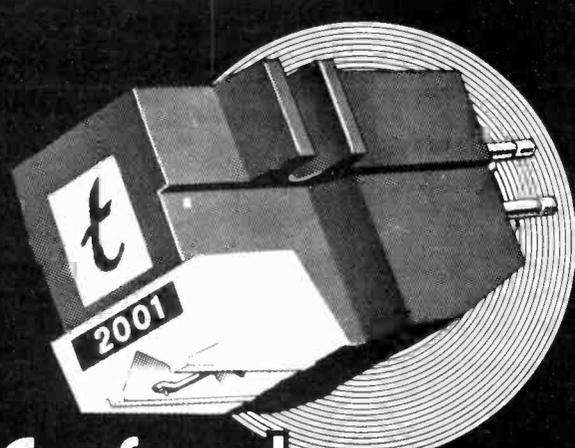

Confused about cartridges?

Looking for a new cartridge or replacing your old one? ... then undoubtedly Tenorel can help you. See your local Hi-Fi Dealer for further details or fill in our coupon below:-

Prices start from as low as £5.45 up to £17.50 ex VAT.

tenorel Distributed by:-
Condor Electronics Ltd., 100 Coombe Lane,
London SW20 0AY. Tel: 01-946 0033.

to Condor Electronics Ltd., 100 Coombe Lane, London SW20 0AY.


Please send me details on the New Tenorel Range of cartridges and local stockists.

Name _____

Address _____

WW7

nombrex

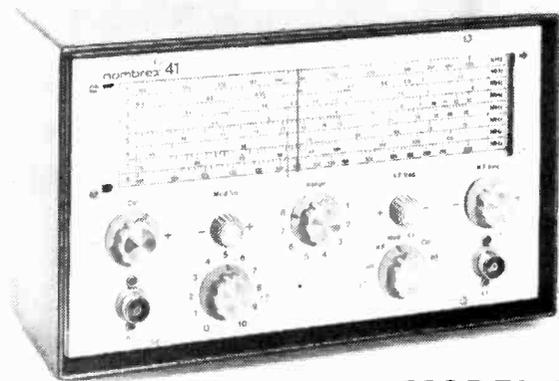

**MODEL 41
R.F. SIGNAL GENERATOR
Price £54.85
PLUS V.A.T.**

- ★ 150 KHz — 220 MHz on fundamentals.
- ★ 8 clear scales — Total length 130mm.
- ★ Spin-Wheel Slow Motion Drive 11 — 1 ratio.
- ★ Overall Accuracy — 2½%.
- ★ Modulation, Variable depth and frequency.
- ★ Internal Crystal Oscillator providing calibration checks throughout all ranges.
- ★ Mechanical scale adjustment for accurate alignment against internal 1MHz crystal oscillator.
- ★ Powered by 9V Battery.

*Trade and Export enquiries welcome.
Send for full technical leaflets.
Post and Packing £1.00 extra*

**NOMBREX LTD., POUND PLACE, WOLBOROUGH STREET,
NEWTON ABBOT, DEVON, TQ12 1NE
Tel. Newton Abbot 68297**

WW — 016 FOR FURTHER DETAILS

PROFESSIONAL - FREQUENCY COUNTERS BY HOYMITZ

Up-to-the-minute design. All five of our range of frequency-period-ratio counters are **directly gated**. For best resolution — FAST.

Stability. Electronic controlled crystal oven 3 parts 10⁴

Bright. .63" character height display. (All Nine)

CHOICE. Filament or LED with Polaroid Filter.

All counters have suppressed leading zeros and auto decimal point positioning for easy positive readings. The memory is also standard.


Suffix F— Filament	Suffix L— LED
Type DG100L Type DG100F Sensitivity 10mV Frequency 100 Mhz PRICE £199.00	Type DG400L Type DG400F PRICE £349.00 Sensitivity AMP 1.DC-150 Mhz. 10mV Sensitivity AMP 2.40 Mhz-400 Mhz. 10mV
Type DG32L Type DG32F (8 digit only) Sensitivity 10mV Frequency 32 Mhz PRICE £169.00	Type DG500L Type DG500F PRICE £475.00 Sensitivity AMP 1.DC-150 Mhz. 10mV Sensitivity AMP 2.40 Mhz-500 Mhz. 10mV
Type DG700L Type DG700F Sensitivity AMP 1.DC-200 Mhz. 10mV. PRICE £569.00 Sensitivity AMP 2.40-700 Mhz. 10mV	<p style="text-align: center;">SPECIALS TO ORDER</p> Telephone Today 0642-43124 Telex No. 587238

Hoymitz Electronics Ltd.
7-9 Albert Terrace, Middlesbrough
Cleveland, TS1 3PA, England

Prices exclusive of VAT

WW—033 FOR FURTHER INFORMATION

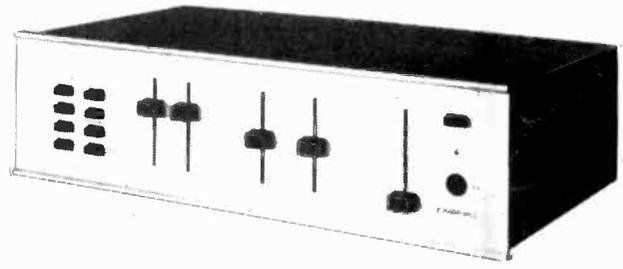RADFORD HD250 High Definition Stereo Amplifier



A new standard for sound reproduction in the home! We believe that no other amplifier in the world can match the overall specification of the HD250.

Rated power output: 50 watts av. continuous per channel into any impedance from 4 to 8 ohms, both channels driven.

Maximum power output: 90 watts av. per channel into 5 ohms.

Distortion, preamplifier: Virtually zero (cannot be identified or measured as it is below inherent circuit noise.)

Distortion, power amplifier: Typically 0.006% at 25 watts, less than 0.02% at rated output (Typically 0.01% at 1 KHz)

Hum and noise: Disc.—83dBV measured flat with noise band width 23 KHz (ref 5mV); —88dBV "A" weighted (ref. 5mv)

Line —85 dBV measured flat (ref 100v)
—88dBV "A" weighted (ref 100v)

Hear the **HD250** at

SWIFT OF WILMSLOW

Dept. WW

5 Swan Street, Wilmslow, Cheshire (Tel. 26213)

Mail Order and Personal Export enquiries: Wilmslow Audio, Swan Works, Bank Square, Wilmslow (Tel. 29599)

Also in stock: All Radford speaker drive units and crossovers, ZD22 preamp, Low Distortion oscillator LD03 and Distortion Measuring set DMS3.

WW — 061 FOR FURTHER DETAILS

SGS-ATES power linears or it's lonely at the top

Our loneliness and our leadership go back a long, long time; they began with power linears.

In fact, right from the start we've done it all ourselves; paving the way for the others. So that now, when you talk about power linears you automatically talk about SGS-ATES. And in all senses - from experience to technological progress, from the fullness of range to production know-how.

In 1968 we put the first audio amplifier on the market - the 2 W TAA 611 - and since then we've gone on being first at every new step along the way. In 1970 we were the first to achieve 5 W with the TBA 641 and TBA 800; in 1972 the first circuit with thermal protection - the 7 W TDA 810S.

In 1973 the first amplifier to achieve 10 W with full protection - the TCA 940.

In 1974 the first real Hi-Fi, the TDA 2020 - 20 W with 1% distortion.

The development of these technologies has also made it possible to make the first complete sound-channel for TV; the first monolithic vertical deflection system; the first complementary Darlington integrated pair.

And now?

The TDA 2002: the most robust and compact audio amplifier. The very best of our design experience has gone into producing the TDA 2002: in the chip and the package. It comes in Pentawatt® and it's highly protected against thermal overloads; against short-circuits; against supply overvoltages including spikes.


With a 14.4 V supply it gives 8 W on 2 Ω. It is ideal for car radios and saves 50% on external components and even more on space.



And that's why



SGS-ATES (UNITED KINGDOM) LTD.

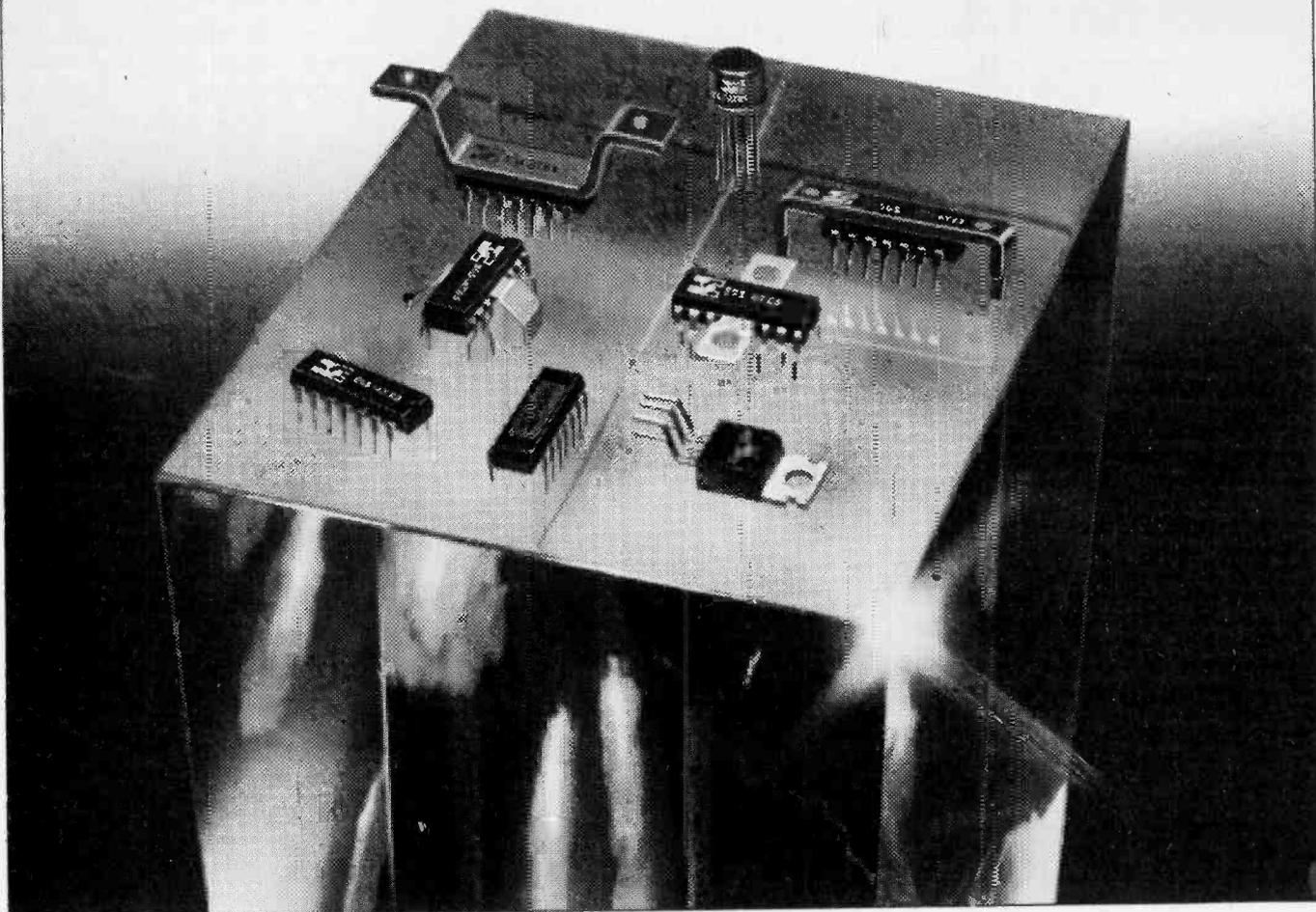

WW-083 FOR FURTHER DETAILS

EEV marine magnetrons?

+ + + EEV MAGNETRONS FOR MARINE RADAR STOP.

EXPANSION COMPLETE STOP ALL TYPES NOW

AVAILABLE STOP FOR EX STOCK DELIVERIES


ORDER NOW. ENELECTICO

Yes.

To meet increasing world-wide demand, we've stepped up production of EEV marine magnetrons.

Now you can order all EEV types and be sure of getting them from stock.

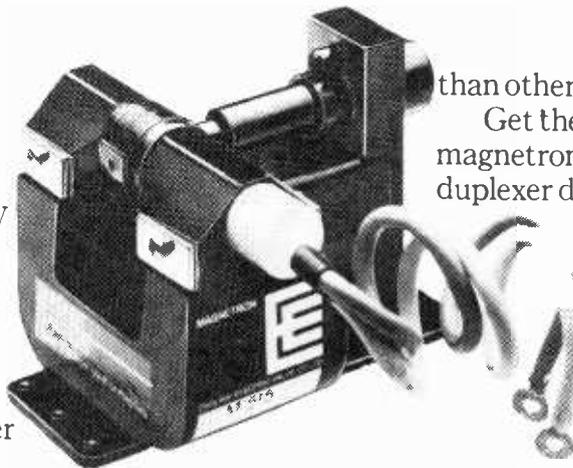You'll be sure, too, of getting the world's best tubes. EEV's unique metal/ceramic magnetrons can last 60% longer



than other makers' glass types.

Get the best. Fast. EEV/M-OV magnetrons, modulator tubes, duplexer devices, CRTs - in fact, all the tubes you need for marine radar.

From EEV/M-OV international stockists everywhere. Or if you'd like our equivalents list, contact Chelmsford.

EEV and M-OV know how.

THE M-O VALVE CO LTD, Hammersmith, London, England W6 7PE. Tel: 01-603 3431. Telex: 23435. Grams: Thermionic London.
ENGLISH ELECTRIC VALVE CO LTD, Chelmsford, Essex, England CM1 2QU. Tel: 0245 61777. Telex: 99103. Grams: Enelectico Chelmsford.

SBC 

WW-075 FOR FURTHER DETAILS


wireless world

Electronics, Television, Radio, Audio

JULY 1976 Vol 82 No 1487

Contents

- 29 Alien audio
- 30 Video discs?
- 32 Schmitt trigger design with op-amps by R. D. Tuthill
- 34 Circuit ideas
 - P.c.b. ammeter
 - Electrostatic headphone amplifier
 - Thermostat
- 37 IRCAM
- 38 F.m. adaptor for a.p.t. tape recording by T. B. Tuke
- 40 Wireless across space — 2 by Tong B. Tang
- 42 H.F. predictions. Literature received
- 43 Unfamiliar forms of temperature compensated voltage reference by K. C. Johnson
- 45 Wideband compander design by John Vanderkooy
- 50 News of the month
 - Video-plus-data recording
 - Brake regulator eliminates locking
 - Tributes to Arthur C. Clarke
- 52 World of amateur radio
- 53 Analogue-to-digital meter by G. Kalanit
- 57 F.m. tuner designs by D. C. Read
- 58 Receiving weak TV signals by W. H. Jarvis
- 59 Space news
- 60 Letters to the editor
 - Traffic broadcasting
 - Current-dumping amplifier
 - TV tuner design
- 64 Circards 31: digital multipliers and dividers by J. Carruthers, J. H. Evans, K. Kinsler and P. Williams
- 65 Surround sound decoders — 2 by David Heller
- 68 Announcements
- 71 Binary Counting by C. Jones
- 76 Doppler shifts analyse Chinese ceramics
- 77 Electronic systems — 4 by W. E. Anderton
- 79 IEA products
- 81 New products
- 123 APPOINTMENTS VACANT
- 136 INDEX TO ADVERTISERS.

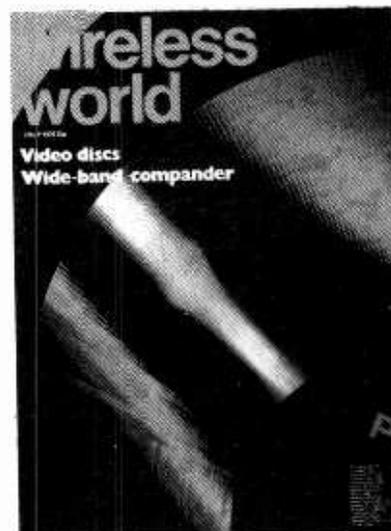

Photographer Paul Brierley

Front cover introduces the article on video discs in this issue and shows colour patterns produced by light interference effects on the surface of a Philips VLP video disc.

IN OUR NEXT ISSUE

The inventors. An examination of the difficulties of inventors in the electronics field in getting their ideas accepted by the Establishment — some revealing interviews.

Accurate digital clock. First part of a design for a self-setting clock controlled by radio using the time-of-day code transmitted by MSF, Rugby.


Linear characteristics. First article of a tutorial series on linear and non-linear characteristics and load lines in electronic circuits.

Price 35p (Back numbers 50p, from Room 11, Dorset House, Stamford Street, London SE1 9LU.)
Editorial & Advertising offices: Dorset House, Stamford Street, London SE1 9LU.
Telephones: Editorial 01-261 8620; Advertising 01-261 8339.
Telegrams/Telex, Wiworld Bisnespres 25137 London, Cables, "Ethaworld, London SE1."
Subscription rates: 1 year: £7.00 UK and overseas (\$18.20 USA and Canada). Student rate: 1 year, £3.50 UK and overseas (\$9.10 USA and Canada).
Distribution: 40 Bowling Green Lane, London EC1R 0NE. Telephone 01-837 3636.
Subscriptions: Oakfield House, Perrymount Rd, Haywards Heath, Sussex RH16 3DH. Telephone 0444 59188. Subscribers are requested to notify a change of address.


© IPC Business Press Ltd, 1976

SIXTY-SIXTH YEAR
OF PUBLICATION



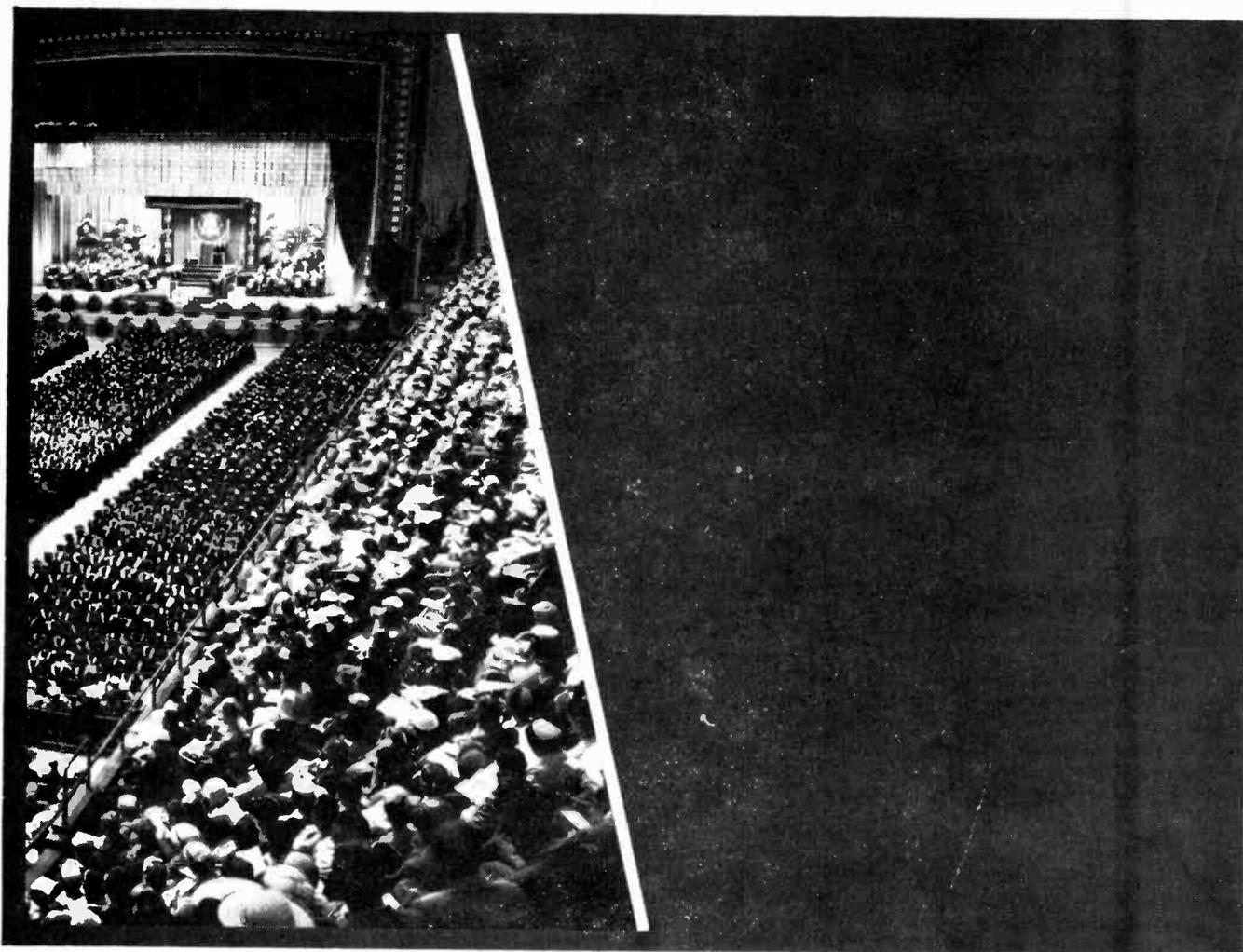

Vocal Master of Ceremonies

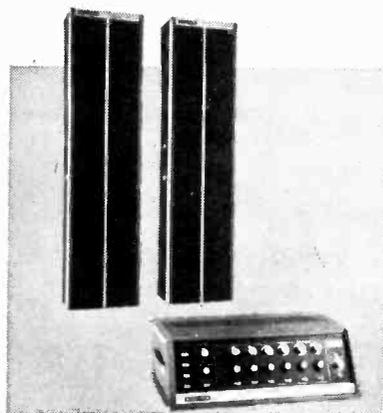

There are precious few ceremonies, functions, meetings or entertainment events that *Shure Vocal Master Sound Systems* can't cover — regardless of room size or apparent acoustic difficulties. The Vocal Master is designed to project the voice with intelligibility and authority to the rear of large areas without overwhelming the listeners up front. It's versatile, easy to operate, and totally reliable. It's the system that earned its reputation for superb sound amplification by meeting the standards of professional entertainers — and is now used in hotels, churches, schools, executive meeting rooms and entertainment facilities from Land's End to John O'Groats in preference to built-in "custom" systems costing *many* times more.

Shure Electronics Limited
Eccleston Road, Maidstone ME15 6AU
Telephone: Maidstone (0622) 59881



WW—062 FOR FURTHER DETAILS

wireless world

Alien audio

Editor:
TOM IVALL, M.I.E.R.E.

Deputy Editor:
PHILIP DARRINGTON
Phone 01-261 8435

Technical Editor:
GEOFFREY SHORTER, B.Sc.
Phone 01-261 8443

Assistant Editors:
BILL ANDERTON, B.Sc.
Phone 01-261 8620
MIKE SAGIN
Phone 01-261 8429

Production:
D. R. BRAY

Advertisements:
G. BENTON ROWELL (*Manager*)

KEVIN BURNAL
Phone 01-261 8515

NIGEL LITTERICK
Phone 01-261 8037

O. BAILEY (*Classified Advertisements*)
Phone 01-261 8508 or 01-261 8423

JOHN GIBBON (*Make-up and copy*)
Phone 01-261 8353

IPC Electrical-Electronic Press Ltd
Publisher: Gordon Henderson

We were recently talking to a man who takes published designs for audio equipment (among other things), collects the components together and, after attending to the mechanical design of the instrument, sells kits of parts. The finished appearance of the equipment was mentioned and he was of the opinion that an extra few decibels of s/n ratio or another order of magnitude less on the t.h.d. figure were as nought compared with a multitude of "facilities" and a satin-finished front panel. Not that his kits reflect this point of view — they are extremely well done — but he is beginning to think in terms of a spurious "technical" appearance, quite apart from high quality, to sell his products. The conversation made us think about the imbalance in the hi-fi shops in favour of foreign equipment and why it exists.

There are at least two main reasons for this imbalance. The first is advertising: in a recent check in one of the high-fidelity magazines we counted 30 pages (full-page, single-name ads) for foreign, mainly Japanese equipment, against 12 similar pages for British products. And that didn't include the discount companies who handle a very high proportion of foreign equipment. It is also evident that the use of English-sounding names for many of these foreign products is widespread. Secondly, the appearance of most foreign equipment is designed to project a "scientific" look, often with superfluous controls and indicators. The performance of these products is good, but is not better than that of home-grown equipment, whose appearance is less deliberately contrived. However, if the "mission-control" category of product is what the average person likes and therefore buys, why not let him have it? It could pay British designers to take more notice of the preferences of their customers. Or perhaps a foreign name might help!

British sound reproduction equipment has always been in the lead for sheer high quality and it seems stupid to let foreign companies take over the market by means of high-pressure saturation advertising through their distributors. Loudspeakers and electronics made in Britain have no peers anywhere, except perhaps in presentation, and that shouldn't present too much of a problem to a competent industrial designer who is prepared to cater for the demonstrated taste of the equipment-buying public.

Video discs?

“Without doubt the video disc is not the end of the story”

The quotation is how we ended our June 1975 view of the video disc scene. That view made the point that everyone seems to have taken for granted the use of the domestic television receiver for display of video records. It is of course the existence of a huge number of tv sets that prompts industrial and commercial concerns to think in terms of selling a home video unit to set owners. The return on investment could no doubt be enormous if things turn out right for them. But it does bring into focus the question of whether the currently-promoted video disc systems are the best way to achieve this end; not to mention the more fundamental question of priority about whose needs are to be met in the first place.

If an attraction for the electronics giants is the sheer volume of production, can it be achieved with the precision mechanisms, by domestic standards, that so far appear to be needed? Video players are not like other domestic products of the electronics industry, many of which can almost be thrown together and sold in millions at rock-bottom prices. Not yet anyway. They are precision machines, made from close-tolerance and hence costly components, and clearly fall into a different category from the low production-cost things we see around the home. Cost reduction by quantity production has its limits for such instruments and unless price can be reduced to amounts within the pocket of the ordinary citizen where is the one-video-player-per-family market? Teldec are not finding it easy to sell TeD players at DM1500.

It is doubtful that the tv-type display will be optimum for many applications. All manner of new display devices are currently being dreamed up, and it seems unlikely that the television line-by-line scanning system would be optimum to these. (If scanning is at all appropriate, a variable scanning rate, depending on changes in information density, may offer advantages.) Together with developments in the newer kinds of storage methods – for example photochromic, photoplastic and thermoplastic materials, possibly linked with holography – and possibilities for spatial information processing, it would seem unwise to limit the options now.

So we hope engineers will take a broad view of the possibilities for video records. The commercial pressures will be there, but let's continue to question our priorities and ask whether we need video disc players in our homes so soon. The present situation could easily produce a “bandwagon” effect – a tendency for the pace to quicken for fear of either being left behind in the market place or of writing off large R & D investments. Let's take our time and get it right, for everybody's sake.

If we had rushed into a standardized format at the outset for surround-sound records, for instance, we might conceivably, commercial interests aside, have got the best of the available systems at the time. As it became clear only a short time later, the initial attempts at providing surround-sound codings fell short of what was optimum – that is, of making the best use of channel capacity to portray sound direction.

THERE ARE SIGNS of consolidation among those who were first in the (optical) field. Following the collaboration of Philips and MCA it now seems that if Zenith opt for an optical system it will be based on the same broad specifications i.e. 1800 rev/min (NTSC) to give one tv frame per disc revolution and allowing “stop action”, spiral track with direct NTSC coding by frequency modulation, two sound channels with subcarriers at 2.3 and 2.8MHz, and 8 or 12in reflective discs, either 1mm rigid or 0.2mm flexible. (See WW 1973, pages 541-3 for details of European version.)

Thomson-CSF, who with Zenith have developed aerodynamic stabilization of discs, have put in some effort to reduce player cost. This stabilization means that a focusing servo mechanism can be eliminated. In addition, the method used to correct radial tracking error doesn't require a separate motorized mirror; the error signal is derived instead from the photodetector array.

Bosch have developed a system along similar lines to these optical systems (WW August 1975, pages 364-5); with its higher resolution – the disc spins at 3000 rev/min – application is in the professional television and archival areas. RCA too have a synchronous optical disc for picture storage though this, like the Ampex magnetic ESS


(electronic still store) and the Sony magnetic card, is for broadcast use.

By adopting a mechanical guidance method for the pickup, RCA avoid the need for servo tracking in their Selecta-vision system. But more significant in terms of cost saving is the use of a capacitance pickup from a metallic electrode deposited on the stylus. RCA claim the stylus is easy and inexpensive to fabricate compared to other pickups, and that it is capable of resolving signal elements smaller than the wavelength of visible light, permitting high density recording with an electron beam.

A further point of difference is the choice of speed, 450 rev/min. According to RCA, effects of vibration due to unbalance of rotating parts are reduced compared to a rotational speed of 1500 or 1800 rev/min. Errors in signal timing that result from warp or eccentricities of the disc occur at a lower frequency, making it easier for the synchronizing circuits of the television receiver to follow. More important, a simple and inexpensive transducer can be used to reduce time-base errors, permitting playback into receivers with relatively slow horizontal sync circuits without requiring circuit modification. This consists of a small moving coil element which drives the stylus arm back and forth along its long dimension, parallel to the record groove. If the record runs too slowly, the stylus is pulled toward the transducer to increase the relative speed, and if the record runs too fast, the stylus is pushed away from the transducer to reduce the relative speed. Error signals are derived from the colour burst frequency as the record is played.

Luminance, chrominance and audio signals are encoded on carriers and recorded on the disc as variations in the width or spacing of slots in the bottom of the grooves on a master disc. Colour information is encoded to give spectrum peaks at odd multiples of half line frequency to conserve bandwidth.

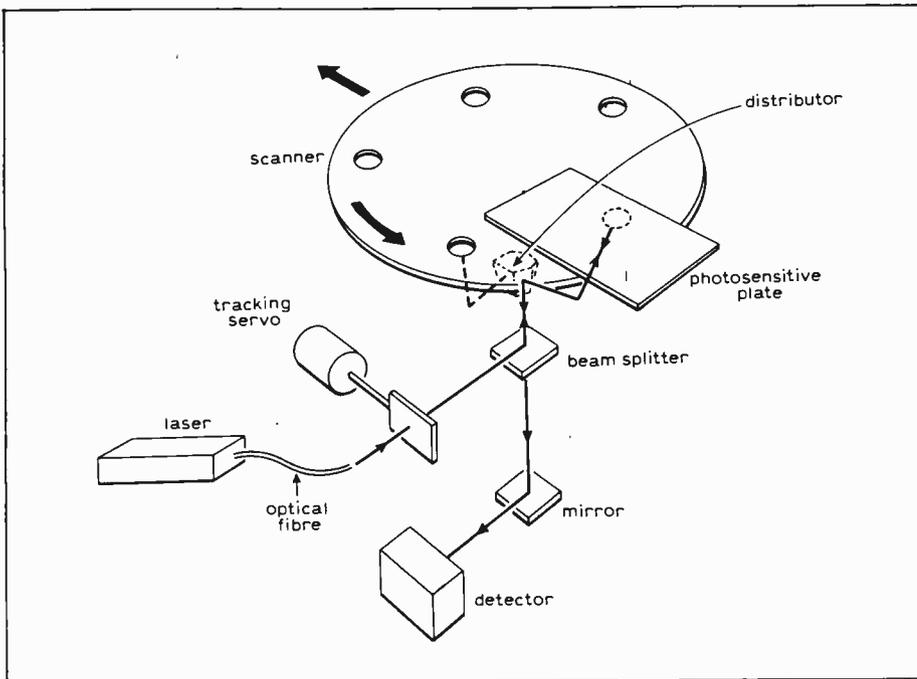The master recording is made with an electron beam to record the signal slots in a material similar to photo-resist, but optimized for sensitivity to electron beam exposure. Replication is similar to conventional processes. After discs are pressed, they are coated with three 40nm layers. First, a conductive metallic



In the digital video record system, the 5×7in record is stationary and the scanner moves. A distributing prism acts to switch the beam from the end of one track to the start of the next.

coating is applied which serves as one electrode of a capacitor. Then an insulating coating is applied to act as the dielectric, and finally a thin layer of oil is added as a lubricant to prolong the life of the disc and stylus. The tip of the sapphire stylus is triangular in shape, and a metal electrode is deposited on the back surface. Signals are recovered by detecting the variations in electrical capacitance between the tip of the electrode on the stylus and the metal coating on the disc as the stylus passes over the slots in the bottom of the groove. Apart from the stylus, RCA say the components are conventional and have been used for years in consumer products.

Whilst this electrostatic system may be able to provide low-cost players, the film-based systems claim the advantage of potentially low-cost duplication. The I/O Metrics system is f.m. and based on synchronous disc speeds, whereas the DRC system, see below, is digital with non-circular records. Full details of the French SEPO technique aren't available, but in 1974 they quoted a disc production cost of one franc!

Perhaps replication cost of the MDR magnetic disc is being quietly forgotten, as the system lends itself to home recording. MDR say they will market this year at DM2000. It started with the aim of low-speed recording and replay to allow the use of ordinary turntables, but a speed of 156 rev/min has had to be accepted. We do not know how much of a problem disc-head contact is going to be.

High-density optical system is digital

It is perhaps surprising that of all the video disc systems announced not one has been truly digital. Most are analogue systems relying on frequency modulation of a carrier. Recently, we learned of a video record system that uses, in effect, photographic plates digitally encoded. Developed originally by a division of the Battelle Memorial Institute, work on the system is now sponsored by the Digital Recording Corporation of Scarborough, New York, whose president recently told *Wireless World* of the system.

Applications for the digital technique are seen in wide variety of situations. In information storage and retrieval, costs are expected to be lower than any other storage technique and much lower than any other system with automatic access. In this application, four possible information handling schemes can be adopted depending on the nature of the material to be stored. For continuous tones the material would be scanned with an 800-line resolution system to digitize the image. The digitized data can then be stored by differential binary coding, giving a linear reduction of 150 times. A two-level (black or white) image e.g. line drawings or text can be stored with a linear reduction of 270 times or, by storing changes only, 460 times. Computer coding could allow a reduction of 1700 times. On this basis, a reduction of storage area can be about three million times, compared with 400 times for conventional microfilm or microfiche techniques. In an archival system, a storage unit of 1000 plastic 4×5in records is envisaged with an access time of five seconds or so (milliseconds on

the same record). Between 5 and 600 million frames could be stored in the space of a four-drawer file, depending on storage mode. Storage size could be increased by a factor of ten if speed can be sacrificed.

As a device for playback on home TV receivers, a unit could cost \$150 to produce. It could make use of 5×7in records loaded singly or automatically from a stack. The storage medium could equally well be a film cassette, automatically wound-on. And according to the company a playback unit can be modified to provide a home recording unit, the optics and mechanics being the same. Replication cost is said to be low and a production cost of "much less than 25 cents" has been mentioned.

As with other video storage techniques, it would lend itself to audio records. Use of a digital technique allows a greater dynamic range, elimination of various distortions, an unwearable and more compact record. An audio player, possibly small enough to fit into a car, could store 30 to 60 minutes of surround sound on a 3×3in record. There could also be applications in the professional or studio television area, especially for advertising spots. Variable delay can be provided for monitoring and editing, and loss-free stop and start, stop-action, frame indexing and computer-controlled editing are a few of the more obvious facilities. Freedom of jitter and of errors in colour, together with high signal-to-noise ratio come with the digital format.

Although the patents held by DRC cover a wide compass of configurations, one type is described to illustrate the approach. Information on the records is in the form of spots and spaces distributed along a curved path on a photosensitive glass plate. In recording such a plate, the data are scanned in serial order on to the plate by a rotating scanning head with several scanning apertures around its perimeter (see diagram). An optical distributing prism placed on-axis switches the light beam so that when a scanning aperture reaches the end of a track, the light beam is cut off and reinstated at the start of the next track. Thus the track pattern is a series of arcs, rather than the popularly used spiral. To produce sequential tracks, the scanning components are translated in the direction of the arrow. The fixed-plate approach is claimed to result in a simpler and less expensive mechanism.

In playback, the light beam is reflected from the dark '1' spots, but not from the clear '0' bits. Because the same machine would not generally be used for both recording and playback a tracking servo (not operative on recording) is provided to deflect the beam slightly as required. This feature,

● Continued on page 36

Schmitt trigger design with op-amps

Graphical technique eases design procedure

by R. D. Tuthill

The common form of a Schmitt trigger design using discrete components as shown in Fig. 1 has several disadvantages. If V_{in} is 0V, transistor Tr_1 is switched off and Tr_2 will therefore be switched on. It can be seen that V_{out} has a minimum voltage level, set by the ratio of R_5 and R_6 values, which is the first disadvantage. If the potential of V_{in} is raised, Tr_1 will start to conduct and the potential at the collector will fall. This starts to switch off Tr_2 which causes the voltages across R_6 to fall and Tr_1 to switch on. Although the change of state is now complete, there is now a current flowing into the base of Tr_1 which changes the input impedance of the circuit. This is also a disadvantage. The basic Schmitt trigger in Fig. 1 is a non-inverting type, and this can also be a disadvantage.

Using integrated circuit op-amps these disadvantages can easily be overcome. From Fig. 2(a) and (b) the only apparent difference between inverting and non-inverting configurations is the reversal of functions at the two inputs. However, for the same specified input and output conditions, different values of R_i , R_f and reference potential are required. Note that when using op-amps, switching always occurs when there is virtually no potential difference between the two inputs. Secondly, because the input impedance of an op-amp is high, virtually all of the current in the feedback resistor also flows through the input resistor. Therefore, the potential at the amplifier input can be calculated by knowing the voltage applied to R_i , the output voltage, the values of R_i and R_f or just their ratio.

The design procedure relies on the last-mentioned point. In the non-inverting configuration V_{IH} is the upper input voltage limit, V_{IL} the lower limit, V_{OH} the positive output voltage, V_{OL} the negative output and V_R the reference voltage. When the voltage ranges have been selected, a suitable voltage scale as shown in Fig. 3, can be chosen. A vertical line is drawn through Q and using the same scale as that on the left-hand side, V_{OH} and V_{OL} are marked. For the example shown V_{OH} is + 10V,


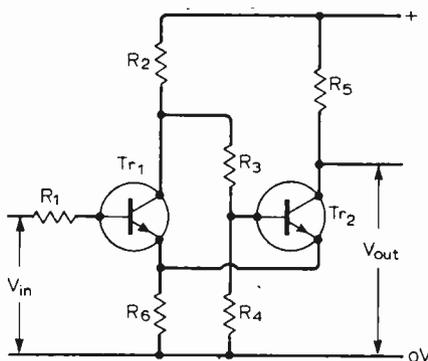


Fig. 1. Common form of non-inverting Schmitt trigger.

$V_{OL} = -10V$, $V_{IH} = 8V$, and $V_{IL} = -1V$. This gives hysteresis of $V_{IH} - V_{IL}$ which is $8 - (-1) = 9V$. At the left-hand end of the 0V line, point P is chosen and a vertical line through P is marked with V_{IH} and V_{IL} , again using the same voltage scale. Referring now to Fig.

Fig. 2. (a) Non-inverting and (b) inverting Schmitt trigger both using a single op-amp.

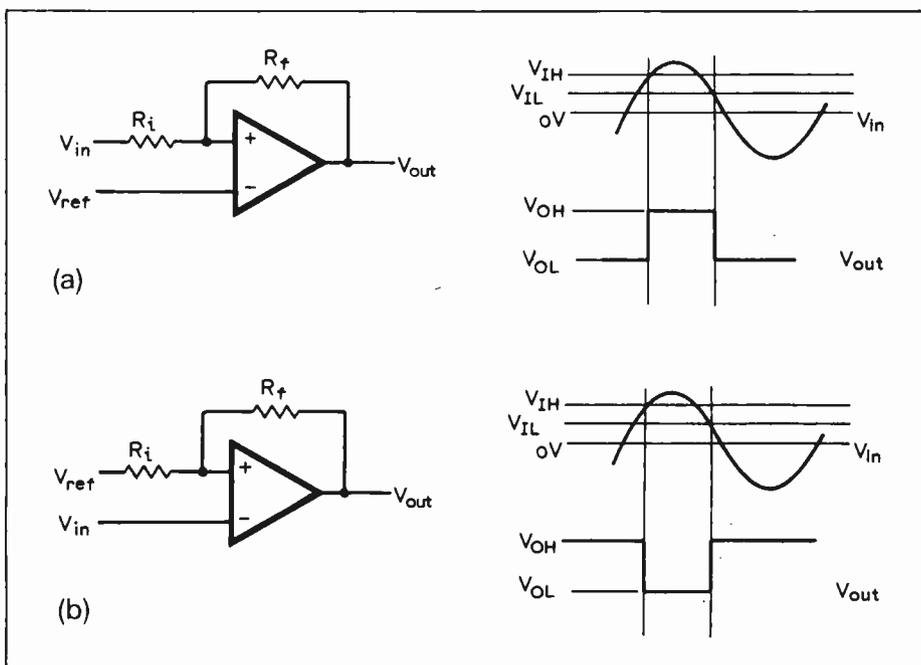

2(a), the inverting input of the op-amp is connected to the reference voltage. Note that the non-inverting input must also be at potential V_R for switching to occur. This potential is not yet known but a line from V_H to V_{OL} , the conditions which exist just prior to switching, can be drawn. If the length of this line represents the impedance $R_i + R_f$, then, by knowing their ratios or values, the value of R_f can be found. Unfortunately neither of these are known but a second set of conditions is, and this may have the same reasoning applied to it, i.e. just prior to the output switching from V_{OH} to V_{OL} the voltage at the non-inverting input is also V_R . Therefore, a line from V_{OH} to V_{IL} can be drawn. The intersection of the two lines gives the value of V_R when scaled vertically from the 0V line.

The ratio R_f/R_i can be found as well as the value of R_i if a suitable value for R_f already exists. Using the scale of resistance, R_f is marked on the horizontal axis, in this case 100k Ω , and a line is constructed from this point through R to intersect the vertical line at point X. Using X as a starting point a second line is constructed through W to finish at Z.

Circuit Ideas


the 741 which was chosen for the merit of low cost.

The l.e.d. shown in the circuit has a twofold use. Firstly, when there is an offset voltage at the input, on shorting all four wires of the probe on a dead conductor, it will light or, alternatively, the ammeter will show a reading. Secondly, when the probe input is reversed the l.e.d. will again light. Diodes $D_{1,2}$ and $D_{3,6}$ provide protection to the circuit which may be floated from voltage to voltage when in use. Finally, the d.c. converter enables the circuit to use a single battery.

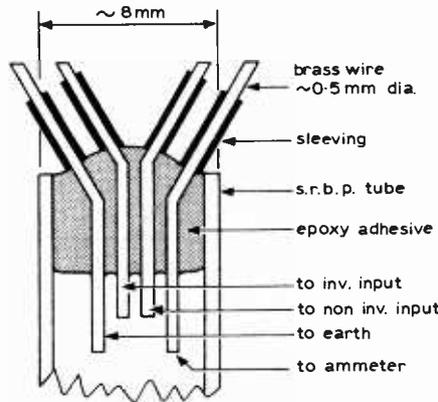F. Andrews,
Southampton College of Technology.

P.c.b. ammeter



This circuit allows measurement of current in a single printed circuit conductor, without the necessity of breaking the track. The device uses a probe of four wires and when all the wires are in contact with a conductor a p.d. appears at the input of a differential amplifier. The two outer wires carry a current of opposite polarity via an ammeter. Because there is a negative feedback loop in the conductor, the differential amplifier input voltage will return to zero when the outgoing current is equal to that of the unknown current, the former being read from the ammeter. The differential amplifier offset voltage must be maintained to as near zero as the twenty-turn preset potentiometer will permit. An advantage would be to use a 725C instead of



Simple sine-wave oscillator

This circuit provides a simple a.f. sine-wave oscillator by using a unijunction transistor as a negative resistance in a RLC circuit. The potential divider R_2 sets the peak point of the emitter and should be adjusted for maximum output consistent with a good sine wave. The output is about 200mV and the circuit operates from 1kHz to 50kHz by using suitable values of L and C.

R. P. Hart,
Hadlow,
Kent.

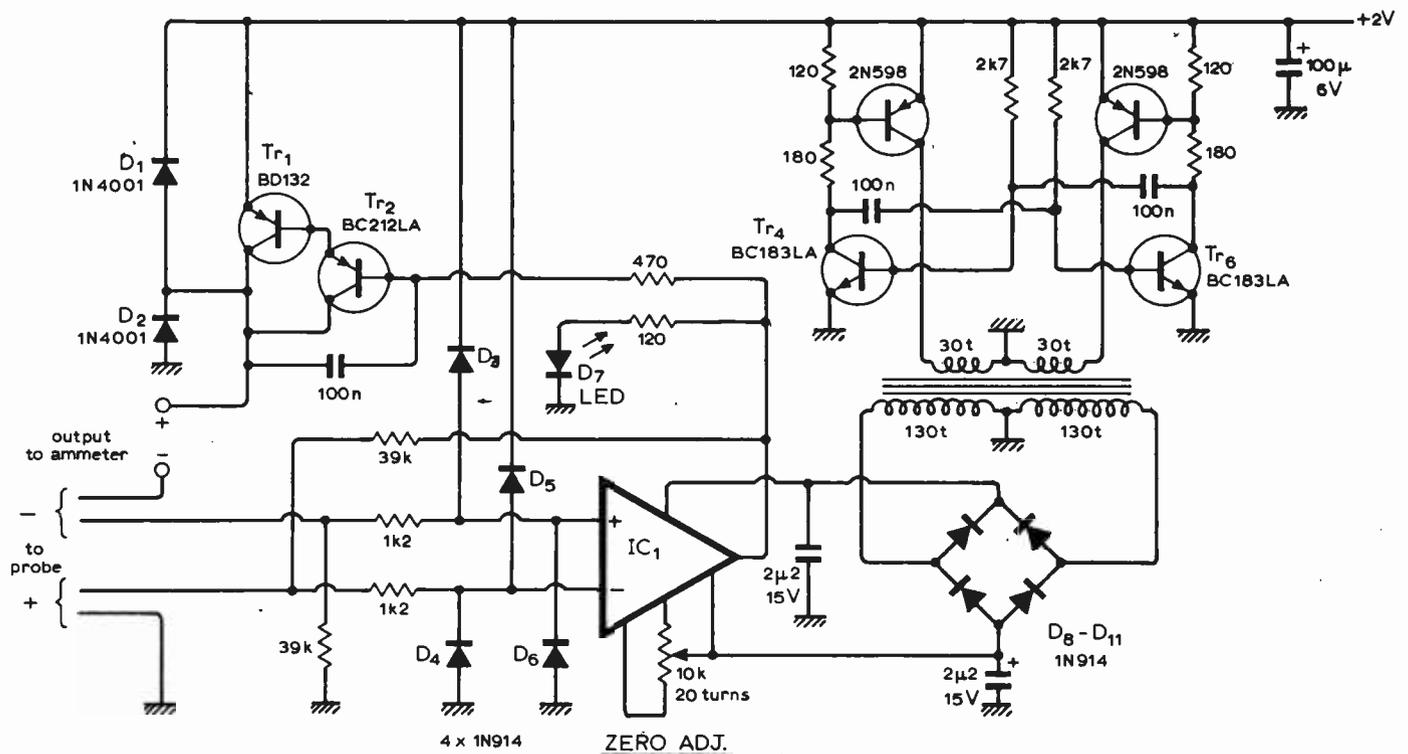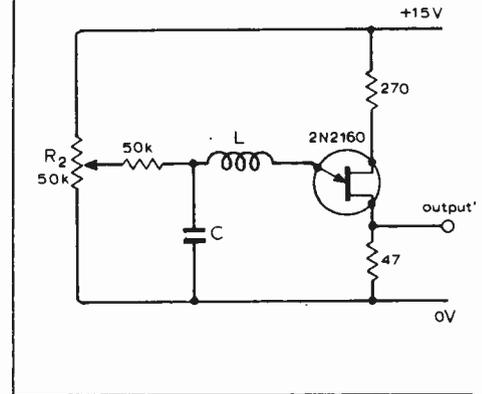




Electrostatic headphone amplifier

This circuit has been used successfully with a pair of headphones based on the W.W. design Dec. 1968. The amplifier can be driven from the headphone output of most power amplifiers. Potentiometers R_5 and R_6 are used to set V_1 and V_2 at half the supply voltage.

Resistor R_1 is required to compensate for the small signal resistance of a diode in the non-inverting input of IC_{1b} . If headphones of greater capacitance than 150pF are used it is necessary to reduce R_2 and R_3 to maintain the power bandwidth. It may then be necessary to heat sink the power transistors. The +15V bias supply for IC_{1a} and IC_{1b} must be well filtered. The amplifier has a

small signal frequency response of (-3dB) 10Hz to 40kHz, a power bandwidth of 10Hz to 15kHz, and a total harmonic distortion at 1kHz (almost entirely second harmonic) of 0.1% at 50V pk-pk and 1.0% at 300V pk-pk output.

N. Pollock,
Sandringham,
Australia.

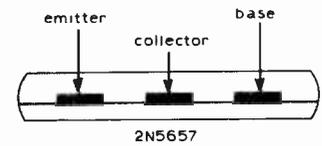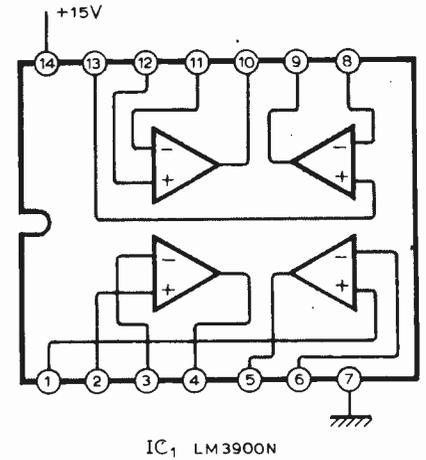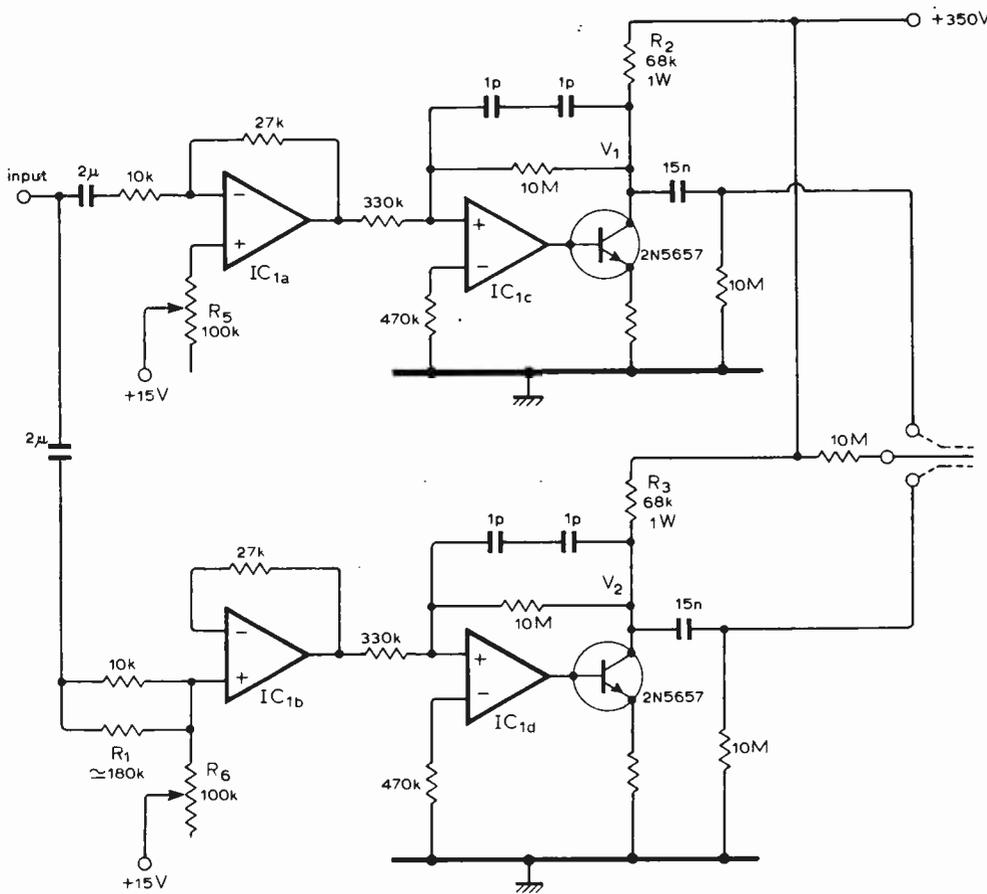


Short-circuit protector

The short-circuit protector shown is fast and cheap. The transistor is biased to saturation and the collector-emitter voltage is therefore less than a volt. If a short-circuit occurs, the collector is pulled along the constant current line of its output characteristic corresponding to the base bias current I_B . The short-circuit current is therefore restricted to some value say I_{max} . Suppose that a maximum load current of I_{max} is to be made available from a supply of V_s , and the transistor has a current gain of h_{FE} , then the base resistor is calculated as follows. As $I_B = I_{max}/h_{FE}$, and because V_{BF} is small, $R_B \approx V_s/I_B$. Therefore $R_B \approx V_s h_{FE}/I_{max}$. If the precise current gain of the transistor is not known, or if a variable I_{max} is necessary, R_B may

be made partly variable and adjusted on test. For a +15V supply from which at least 100mA may be drawn, suitable components for the short circuit protector would be a silicon p-n-p transistor with h_{FE} 100 (e.g. BC327) and a base resistor of 12kΩ. The output voltage will then be 14.5V and the value which I_{max} reaches will exceed 100mA.

Under normal operation very little power is dissipated in the protection transistor. Under a short-circuited load condition the power developed is $V_s I_{max}$ watts. For negative supplies a n-p-n transistor may be used in the same configuration.

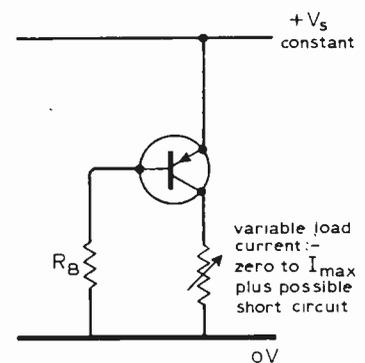
M. C. Hatley,
Robert Gordon's Institute of
Technology,
Aberdeen.



Thermistor controlled thermostat

Essentially the circuit is a bridge formed by the thermistor, R_1 , R_4 , R_5 and R_6 with an amplifier for sensing the unbalance. The circuit switches a relay on when the temperature is below a chosen level, and by altering R_1 the operating temperature can be changed. If the opposite function is required the positions of the thermistor and R_1 are reversed. The sensing circuit uses a CA3046 which supplies two matched pairs of transistors in addition to the output transistor. Tr_1 and Tr_2 act as a voltage comparator; the tail current being provided by the current mirror Tr_3 and Tr_4 . The base voltage of Tr_2 can be adjusted using R_5 which allows the switching temperature to be set precisely. Positive feedback via R_7 prevents chatter when the switching point is reached. If the thermistor is separate from the amplifier, a $0.1\mu\text{F}$ capacitor should be connected across R_1 to minimize pick-up effects.

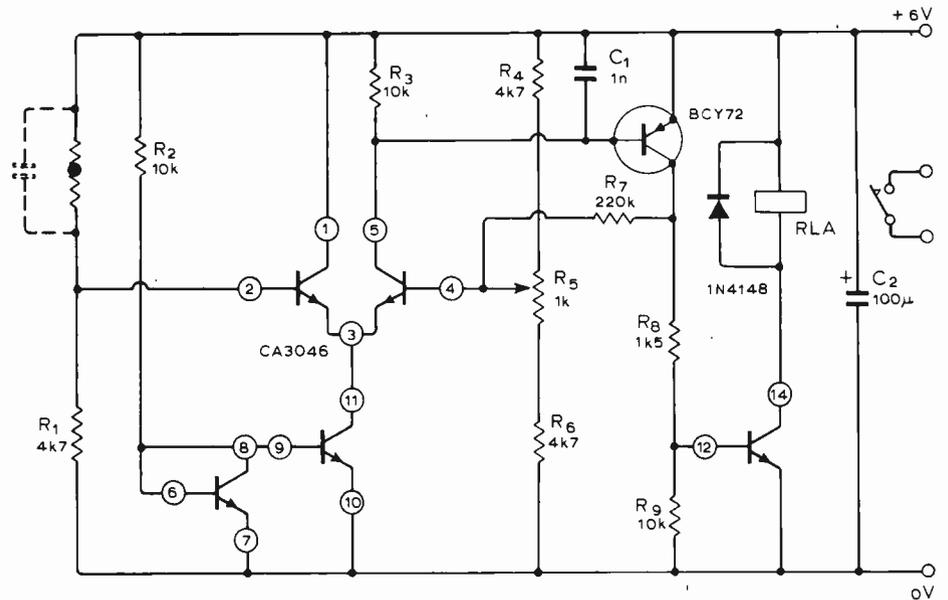D. E. O'N. Waddington,
St. Albans,
Herts.




Square-wave generator with single frequency-adjustment resistor

When the circuit shown is switched on C is uncharged and Tr_1 is non-conducting. Transistor Tr_2 is therefore fully on and its emitter is at a potential near V_{cc} . Capacitor C therefore charges until Tr_1 begins to conduct which causes Tr_2 to rapidly cut-off, by regenerative action. The emitter of Tr_2 falls to a level determined by the ratio of R_1 to R_3 , and C discharges through R_4 until Tr_1 cuts-off and the cycle repeats.

The transition times of the circuit are rapid and it will work with small-signal silicon transistors up to at least 0.5MHz, and down to a frequency determined by CR . The output is almost an equal mark-to-space ratio over a wide frequency range, though this can be trimmed if required by the ratio of R_2 to R_3 , or by a small resistor in Tr_1 base.

J. L. Linsley Hood,
Taunton.

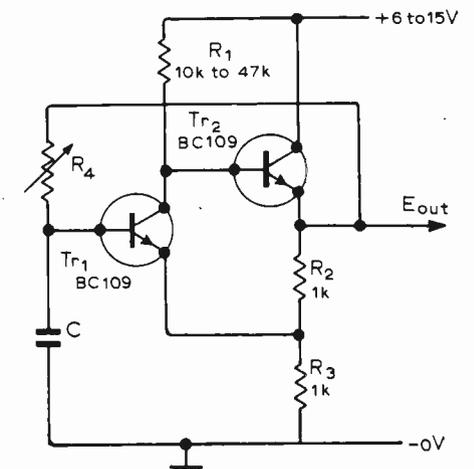

Video discs (continued from page 31)

common to most analogue optical disc systems, allows some tolerance on record positioning and on hole alignment in the scanning disc.

An interesting point concerns the limiting spot size. According to classical diffraction theory the focused spot produced by a lens passing monochromatic light shows an intensity distribution in which the bright central area contains 84% of incident energy. The diameter of the first dark ring surrounding this area determines, at first sight, the maximum achievable bit density. But in practice, the spot size on a photographic emulsion will be smaller due to the gamma effect of the emulsion. (Gamma is the maximum slope of the log of exposure versus density.) The intensity distribution of the diffraction pattern is not "mirrored" by the photographic density distribution, and the slope of the central peak in the diffraction pattern is sharpened on the emulsion - in effect a sharpening of the spot size, allowing greater spot density. Spot sizes of $1\mu\text{m}$ are produced on silver halide emulsions at 633nm wavelength and a focal length-to-aperture ratio of two, allowing a bit density of 10^8 bit/cm.

Because of possible variations in emulsion depth and position depth of focus must be adequate. A technique that avoids the expense of servo-controlled focusing is to blank off the central portion of the lens, in playback if

not in recording. This has the effect of increasing the depth of focus, but at the expense of more energy appearing in the secondary rings of the diffraction pattern. This is not very important in playback because of the way the detector electronics respond to sharp modulation represented by the central spot. Depth can be increased from 20 to $40\mu\text{m}$ by occulting three-quarters of the lens. (Actually, DRC say $10\mu\text{m}$ is adequate for rigid records in commercial form.)

For flexible records an holographic lens - made by replacing the lens by a transmission hologram after exposure by sending monochromatic light backwards through the system which can compensate for errors in the optical system - could yield up to $120\mu\text{m}$ depth.

An advantage of a digital method is that emulsion noise is much less noticeable than in an analogue method - only extreme fluctuations of grain density and size would show. In certain applications, error-correcting codes could be built into the system.

In demonstration apparatus, differential encoding has been used to remove some of the redundancy in normal tv pictures. Each picture element is recorded as a four-bit word, three bits for luminance and one bit for colour. Instruction codes are recorded instead of the usual blanking signals so that audio signals can be digitized and time multiplexed into the horizontal blanking periods.

IRCAM

Electronics at the Paris Institute for Research and Coordination in Acoustics and Music

Under construction, just off the boulevard de Sebastopol in the heart of Paris is the new Centre Beaubourg research institute which is to form part of a major contemporary art centre. The Centre Georges Pompidou will house a museum of modern art, a centre for industrial design and an extensive public library in which space will be reserved for displays on current events and for the operation of audiovisual facilities. The centre, to be officially opened in April 1977, will also include a fourth department, IRCAM – Institut de Recherche et Coordination Acoustique/Musique, built underground next to the Centre Beaubourg.

IRCAM is to provide research facilities for developing future aspects of music. To do this the aid of digital electronics has been enlisted as an important tool in the processing of real time electronic sound reproduction. At the heart of the technical facilities will be a Computer Automation PDP10 with its associated 24k bit core store and a peripheral number of interlinked visual display units and input/output keyboards. Nothing out of the ordinary to those already involved in the use of computer facilities, but the application is unique and likely to cause initial scepticism. Computers for making music? What then will happen to the composer and instrumentalist and the essence of *human* expression? In the words of Pierre Boulez, Director of the research programme "The musician must assimilate a certain scientific knowledge, making it an integral part of his creative imagination. As to the scientist, we are of course not asking him to compose, but to conceive with precision what the composer, or instrumentalist, expects of him, to understand the direction contemporary music has taken, and to orient his imagination along these lines. At educational meetings, scientists and musicians will become familiar with one another's point of view and approach. In this way we hope to forge a kind of common language that scarcely exists at present, while training a staff who will be basically oriented towards musical creation."

Computer aided design

It has become clear that with the appearance of synthesized sound, tra-

ditional instruments no longer determine the limits of perception and comprehension of music. The aim of the research at IRCAM is to determine in which direction these limits should be pushed in widening the available scope for composition and performance. A computer programme, Musik V, has been developed over the last few years to assist these aims. Its initial application is in the examination of the waveforms produced by musical instruments in order to determine the parameters relevant to their accepted perception. This is not as simple as it sounds. For instance, a waveform of say a trumpet can be reproduced easily enough, but it was found that the result still did not sound like a trumpet. Further investigation showed the reason to be that the decay of harmonics was dependent on their frequency. In other words harmonics of high frequency decayed at a different rate to those of lower frequency.

Using computer facilities to analyse results such as this should be applicable to the development of new instruments. For instance a composer could stipulate the range and timbre of the sound he requires by simulating them on the computer, analyzing their component parts and developing an individual instrument that can produce them. Another application is in 'bending' the sound of a standard instrument so that its range of timbre can be increased or completely altered. It was demonstrated at the centre how the waveform from a violin could be fed to a computer which gradually reshaped the signal to that produced by a trumpet, the startling result being a sound emanating from the same instrument which gradually changed from one type of known instrument timbre to that of another.

Such flexibility provided by the computer can be coupled in the IRCAM centre with its 'Espace de Projection'. This area of the underground building will be used for transmitting any sound produced in the studios, for acoustic measurements and also for direct participation of concert audiences in sound experiments. The acoustics of the Espace de Projection will be mechanically variable so that reverberation time will depend on the position of moveable absorption elements in the walls and ceiling. Also it will be possible to lower

and raise the ceiling and a system of curtains across the area will provide even more flexibility of the acoustic environment. Other facilities in the building will include two acoustically isolated studios with 'ideal' reverberant conditions and a department for the study of psychoacoustic effects. Finally, it will be the job of the 'Diagonal department' (le departement Diagonal) to coordinate the different branches of research and instigate the transplanting of techniques from one department to another. It will also undertake research work on the transmission, projection and perception of sound as well as on pure acoustics, music theory and their relationships with other disciplines.

Common effort

Two aspects of the centre which it was surprising to find were not being considered in depth were the use of video in composition and the use of a computerised system for multichannel sound recording. Lack of video applications was surprising as there is a lot of interest in its use by many contemporary artists in both the fields of music and the visual arts. More importantly however it was felt that recording techniques are as complex in their execution as the basic research of the institute already mentioned. If results of the work produced from IRCAM in years to come are to be communicated to as wide a public as possible then it would be a pity if the subtleties of compositions using new acoustic effects were lost because recording equipment was not developed to an equivalent degree of flexibility. . . . "Contemporary music has at the moment less need of individual souls and their vagaries than of common effort to explore its own innermost nature, to explore sound itself, both with instruments and artificially, in order to unlock new sonorous possibilities for composition, to explore musical perception, in order to understand why some tools function better than others, to explore relationships between music, performance and listeners. This adventure will take place in many ways: through the severity of scientific analysis, through experimental testing of hypotheses, through all manner of public presentation, and through composition itself" – Gerald Bennett. WEA

F.m. adaptor for a.p.t. tape recording

P.I.I. design overcomes replay amplitude variations

by J. B. Tuke

Many earth stations receiving automatic picture transmissions from satellites use a tape recorder as an intermediate link between the radio receiver and picture printing equipment. This system has advantages because some picture printers need to be operated in complete or semi-darkness, and many aerial systems are manually tracked which requires the operator's full attention during satellite transit.

The 2400Hz amplitude-modulated signal which carries the picture information can be recorded and reproduced on a domestic type of tape recorder, preferably running at 7½ in/s. However, the picture produced on replay shows dark horizontal streaks, caused by fluctuations in the replayed signal level. These variations of about a decibel are in the most critical part of the picture level, where minute changes of intensity produce appreciable changes in the shades of grey. If infra-red data is being displayed using the intensification process, deterioration can become severe.

To overcome the amplitude variations a frequency modulated signal can

Fig. 1. (a) Block diagram of phase locked loop, (b) signal path for the modulating mode, (c) connections for the demodulating mode.

be used. This technique is well known and the Signetics NE565 phase-locked loop i.c. is used, as shown in Fig. 1(a). The v.c.o. frequency-determining components are chosen to produce the required carrier frequency, and the modulation is applied to pin 7. The v.c.o. output on pin 4 is then passed to the recorder as shown in Fig. 1(b). On replay, the f.m. signal from the tape recorder is fed to pin 2 of the i.c., which is connected in the conventional p.i.i. demodulator mode and the demodulated output appears on pin 7, see Fig. 1(c).

Choice of v.c.o. frequency is important. The upper frequency limit of the v.c.o. is set by the tape recorder and experiments have shown that a carrier frequency of 11kHz is quite satisfactory. Remember that the f.m. sidebands on both sides of the carrier must be reproduced. For this type of recording, using limited deviation and where fidelity of the replayed signal is not of primary importance, it is adequate to consider the required bandwidth as being twice the modulating frequency either side of the carrier. With an 11kHz carrier and 2.4kHz modulation, the tape recorder should be able to deal with a frequency band between about 6 and 16kHz.


As replay is only concerned with an f.m. signal, this band does not have to be

replayed at the same level as long as there is sufficient signal from the tape recorder to lock the p.l.l. A carrier frequency which is an exact multiple of 2400Hz should be avoided to prevent patterning on the finished picture.

Measurements of input amplitude against output signal have shown an almost linear relationship within the dynamic range of the system. The signal to be recorded may have a value up to -3dBm. Higher values than this cause excessive carrier deviation and loss of lock on replay. If the weakest signal (full black) is recorded at -30dBm, the worst signal-to-noise ratio is 15dB and the dynamic range is nearly 30dB which is ample for a.p.t. signals.

When setting the record level remember that in NOAA spacecraft signals, peak-white occurs at the edges of the picture and not in the picture itself. Due to the global position of the U.K., picture content rarely exceeds 80% of the peak value. Consequently the input must be adjusted so that signal peaks do not exceed -3 dBm otherwise the circuit will momentarily drop out of lock. Although this may not be part of the line scan carrying picture data, lock takes a few milliseconds to recover and causes a large black streak.

If the 2.4kHz signal were first rectified to produce the video (f_{max} is 1.8kHz) and

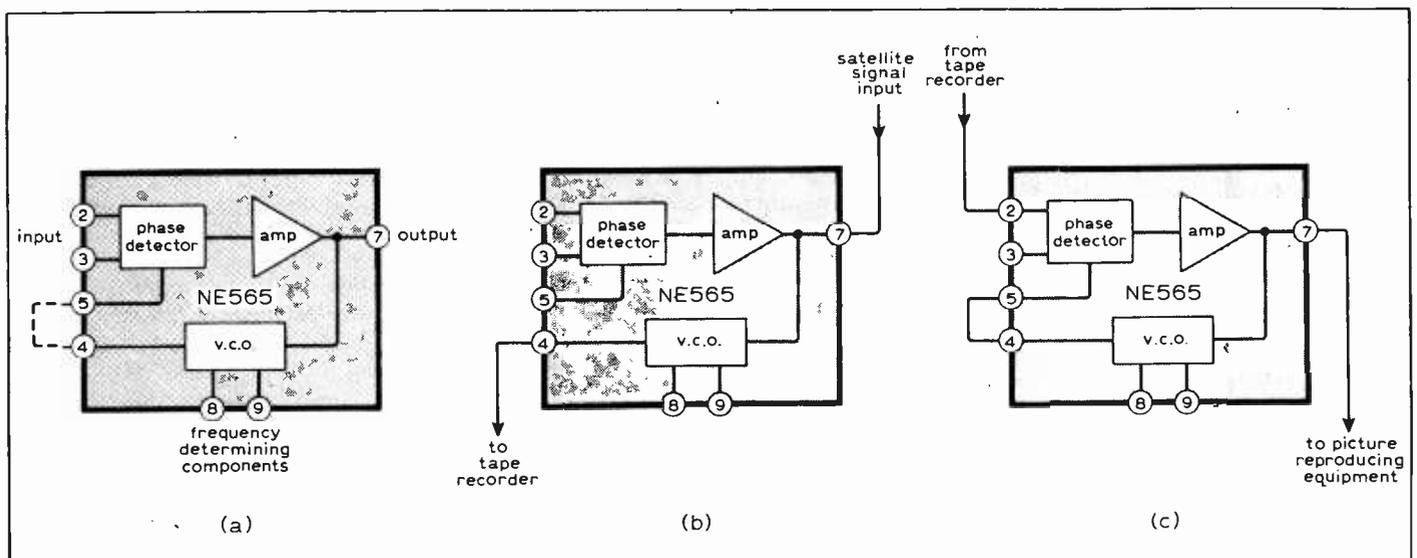

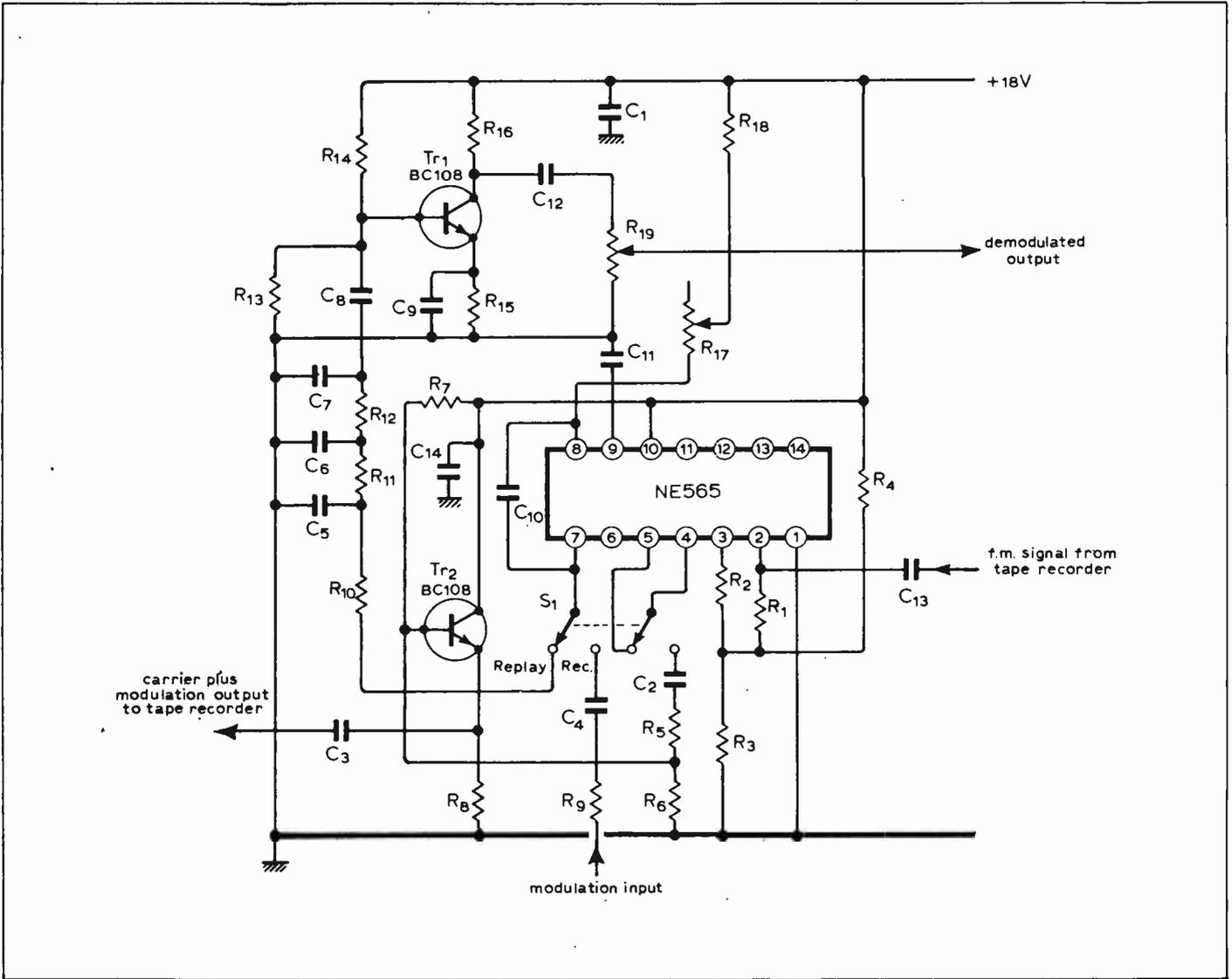


Fig. 2. Practical circuit for modulator / demodulator using one p.l.l. and a d.p.d.t. switch. Tr₁ provides an overall gain of 0dB in the replay mode, and Tr₂ isolates the v.c.o. output in the record mode.

then applied to the NE565, the resultant f.m. signal would be of a simpler nature and a lower carrier frequency could be used. This system presents no problems in the record mode but when amplification is required on replay, the d.c. component would have to be preserved right through to the picture printing device. Infra-red NOAA pictures indicate temperature by the relative intensity of black and white. A typical read-out from near the north pole to

north Africa shows a steady darkening of the picture from north to south as the surface temperature increases. This may be referred to calibration charts for exact temperatures and therefore the d.c. levels must be maintained. This complication is removed by retaining the 2.4kHz portion of the signal.

A practical circuit as in Fig. 2 consists of the NE565 together with two simple transistor amplifiers. In the record mode the v.c.o. output is isolated from the tape recorder by an emitter follower. In the replay mode a transistor amplifier is used to produce an overall gain of 0dB. A d.p.d.t. switch enables one i.c. to be used in both modes, although two devices can be used.

The unit may be built on Vero-board and powered by an 18V regulated supply. Using this adapter, which can be built for around £10, pictures can be recorded which are almost indistinguishable from the original.

Correction

The following apply to 'Weather satellites ground station - 3' by G. R. Kennedy, January 1975: capacitors C₇₇₋₇₉ and C₈₅₋₈₇ should be 1,800pF and R₃₄ is a 5kΩ ten-turn pot; in Fig.23, IC₇ output is from pin 12, IC₆ should have pin 10 grounded; Tr₂₇ should be 2N4061, 2N3702 or similar; S₄ is labelled in reverse; on page 25 for S and S read S₅ and S₆ and in the appendix for R₃₃ read R₅₇ for C₆₇ read C₆₈; in the parts list add R₁₀₅ - 390Ω, for REL65 read REC65 and C₉₃ should be 1.5μF.

Component list

C1	100μF 25V	R1,2	7.5k
2,3	100n	3,16	4.7k
4,8	470n	4	10k
5,6,7	47n	5	22k
9	25μF 6V	6	3.3k
10	1n	7	33k
11	10n	8,9,10,	
12	50μF 25V	11,12,	1k
13	200n	15	1k
14	100n	13	6.8k
		14	68k
		17	20k
		18	2.2k
		19	10k

Wireless across space

2 — Proximity of communicating civilizations in the Milky Way

by Tong B. Tang, M.Tech

St John's College Cambridge

That communication with extraterrestrial intelligence (sometimes abbreviated to CETI) is possible with today's radio technology was postulated in Part 1. As further support of the thesis, we will now consider an order-of-magnitude calculation of the most probable distance separating a civilisation from its nearest neighbour, using today's knowledge and opinions.

There are at least 10^{10} galaxies, some containing more and some less stars than the Milky Way, in the part of the universe so far observed. But for our present purpose we need only to consider our own galaxy, the Milky Way (Fig. 5); which from statistical star counts has some 10^{11} stars. (On the scale of galaxy diameters intergalactic distances are two orders of magnitude higher.) After Drake⁵, the number of civilisations which have the capacity for interstellar communication can be analysed as

$$N^* = R f_p n f_1 f_h f_c T$$

Here R is the average rate of star formation. The age of the Milky Way is about 1.5×10^{10} years, and thus the overall R will be seven stars per year. However, the actual R in earlier times must have been larger, and in later times smaller, while those stars formed in the earlier periods are likely to be lacking in heavy chemical elements and should be excluded because in their absence advanced civilisations or perhaps even life itself cannot arise. In view of this, a reasonable value of R will be one star per year.

f_p is the fraction of stars possessing planets. For a long time it has been observed that stars whose temperatures are similar to or less than that of our sun — and nine out of ten stars belong to this category — are usually rotating much less rapidly than the remaining stars; the observation is deduced from the much smaller amounts of the Doppler broadening in their spectral lines. The interpretation is that they have planets to which most of their rotational energies have been transferred. Furthermore, in particular, the motions of some nearby stars, "Bernard's Star" for instance, have been seen to "wobble," and this almost certainly shows that they have dark companions (planets) in

orbit around them.²⁶ The mechanism of planet formation is not yet well-established theoretically²⁷ but in all possibilities it is consistent with that of star formation, viz. the self-gravitational collapse of a nebula of gas and "dust" into a state where it is hot and dense enough for the start of nuclear reactions and the birth of the star. We shall be conservative by taking f_p as 0.5.

n is the mean number of planets in each planetary system which have environments suitable for life; or, in astrobiologists' jargon, which lie within the ecosphere of the local sun. The most important factor here is whether the planet in question acquires by outgassing its crust an atmosphere which initially contains hydrogen but not oxygen (where complex molecules when formed will not be at once oxidised) and a hydrosphere of water. In our solar system Earth and Mars satisfy the conditions, and we shall use 2 as the value of n , by the "assumption of mediocrity"¹¹ (that what is true for us cannot be unique and is likely to be the average for the whole galaxy).

f_1 is the percentage of these planets in which life does develop. It looks to us that the abiogenic (spontaneous) synthesis of probionts (self-replicating molecular assemblies) is, given the boundary conditions of a primitive hydrosphere containing hydrogen, methane and ammonia, forced by the laws of physics and chemistry and therefore a certainty. Given, in addition, sufficient time and an environment which is not entirely static, self-reproducing organisms are bound to appear later. (Incidentally, I mention the speculation that the properties of matter or even the physical laws change, until they are such that the appearance of life in the universe becomes inevitable. We should therefore not be surprised that everything seems to just fit in, so that in particular we exist on earth, because when it is not so we do not exist to know. We are here, hence the world is being such that life can exist — the "anthropic principle"; and hence there is life "out there" as well — the assumption of mediocrity.) It follows that f_1 is very nearly 1 and as a

close estimation is taken as 1.

f_h is the fraction of inhabited planets in the biospheres of which life advances to a high level, during the lifetime of the local sun. A high-level life form means one which will not become an evolution cul-de-sac. It is, I think, one which can form an internal analytical model of the external environment, and which relies mainly on this ability for the survival of its species (or, more exactly, its genes). On earth this occurred when the first truly erect walking species, *Sinanthropus pekinensis*, appeared; that was 1.5 million years ago, according to the very recent fossil dating by R. E. F. Leakey. Ample artefacts have been uncovered to show that they were tool-using and relied more on manipulative skill than on structural adaptations of the body for species survival. We have, or at least think that we have, reasons to suppose that, given certain broad and fairly general initial conditions, the appearance of such species in due course is again a certainty. Of course, there are many hurdles to jump before its superiority over other species, many of which are splendidly adapted to specific environments so long as they do not change, becomes established (as is so for us, *Homo sapiens*). Some species (e.g., the *Neanderthal man*) failed and went extinct. However, eventually one species would succeed. This is not so only if, for example, the planet is covered entirely by water, so that there is no land for life to invade from the sea and to develop stronger interactions with the environment. From these considerations a guess of f_h will be 0.5.

f_c is the fraction of planets populated by higher forms of life, on which civilisations develop to the stage of participating in interstellar communication. That is, they change from "planetary" civilisations (civilisations whose activities and modes of thinking are restricted in their scopes to their own planets) to extra-planetary civilisations. This is precisely the threshold over which we are about to step, and it is difficult to imagine that we will somehow regress. My considered belief is that similar laws of technological and social evolution apply in different

planets, except where the natural conditions differ fundamentally. Lower life forms can be very unlike on different planets or even on different regions of a planet, because of the multiplicity of planetary initial conditions and of evolutionary accidents. However, as they evolve further, the influences of these boundary conditions decrease in proportion to those dictated by the universal laws of nature. Accordingly, the "psychologies" of different intelligent races should in general converge. With the conservative assumption that the development of a technological civilisation requires that things like low melting-point alloys and easily accessible fossil fuels are naturally existing, we take f_c as 0.2.

Finally, T is the lifetime of the communicative stage of these civilisations. In our view the *continued* development and progress of a technologically advanced civilisation depend on its social system, which is a matter of experimenting and choice, so that they are not only possible but probable because presumably they are its intentions. We then judge that, say, one out of ten civilisations lasts as long as the local sun remains "healthy." The averaged value of T will be 10^9 years.

With these values, N^* comes to be $(1 \text{ year}^{-1}) \times 0.5 \times 2 \times 1 \times 0.5 \times 0.2 \times (10^9 \text{ years}) = 10^6$. In other words, on average one out of a thousand stars will possess on average one planet where there is a civilisation in the interstellar communicative stage. The main uncertainties in this estimation of N^* lie with the last three factors, namely f_p , f_c and T .

Using the mean density of stars in the Milky Way, which is 1 star per 200 cubic light-years, the mean minimum separation of communicating civilisations (i.e., the most probable distance between the nearest neighbours) will be the radius of the sphere of volume 2×10^5 light-years, or roughly 40 light-years. In general, the distance is $2 \times 10^4 \sqrt[3]{N^*}$ light years.

If direct radio contact is considered, the civilisations have to exist in the same epoch. A slightly more complicated procedure gets $23 \sqrt[3]{T_G/T}$ light-years as the likely minimum separation between 'contemporary' civilisations,²⁸ in which T_G is the galaxy time-scale, i.e. 10^{10} years. In our estimation therefore it will be about 50 light-years. This is not much greater than the previous estimation of 40 light-years, because we have taken T to be not much smaller than T_G . A more exact assessment will have to take into account the length of time required in biological evolution²⁹ but being much less than 10^9 years it can be taken as zero.

The chance that a randomly selected star is sending interstellar signals is 0.001. If and when the synchronisation problem referred to previously has been solved, we can be sure that, when we look at it, its signals are beamed towards us. In this case, the probability of achieving at least one contact after

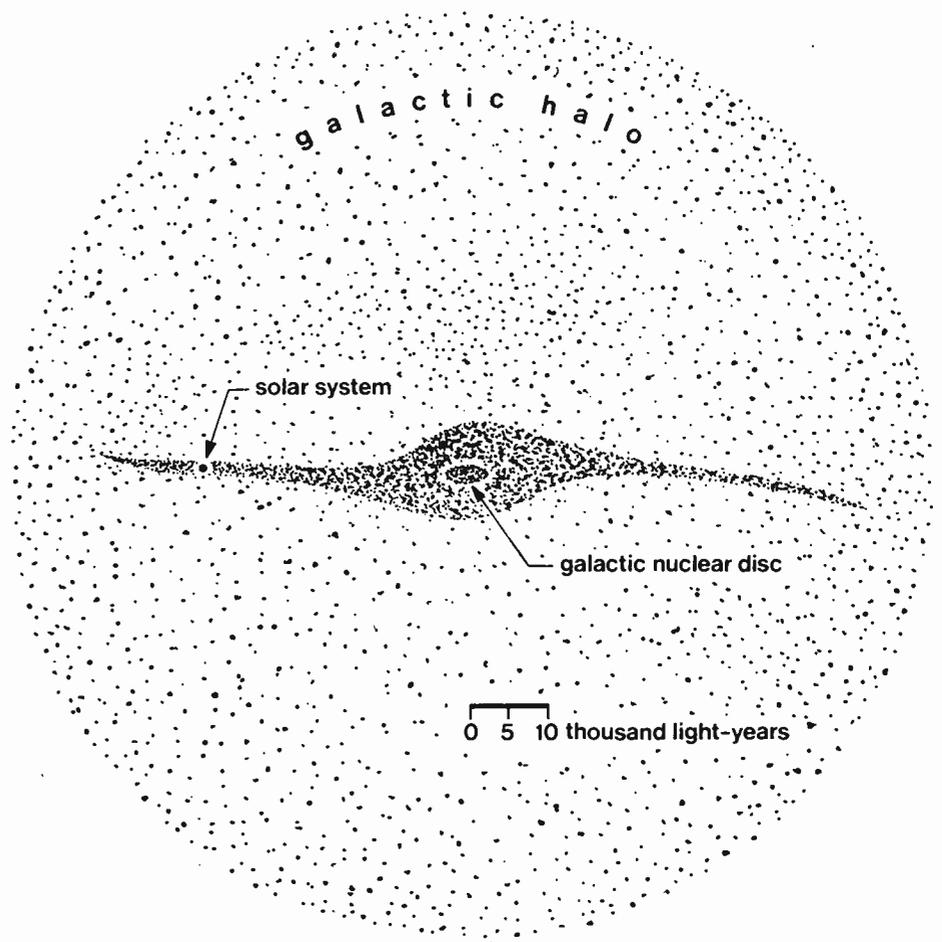


Fig. 5. Schematic picture of the galaxy, showing its shape and size and the relative position of our solar system.

searching N stars is $1 - (1 - 0.001)^N$ or approximately $1 - \exp(-0.001N)$. A search of a thousand stars will, assuming perfect synchronisation, give us a 63% success.

Inevitability of participation in interstellar communication

The feasibility of intentionally achieving communication by radio contact with extra-terrestrial civilisations has been shown. By way of conclusion I would point out one more consideration. We have been using u.h.f. radio communication for some fifteen years. Also, there must be now a few thousand television stations on our planet which transmit in channels 14 to 83 at a power of something like 20kW on average, and a lot of u.h.f. transmitters such as maritime radio beacons and satellites' telemetry and tracking. Earth is then radiating nearly a tenth of a watt per hertz into space at centimetre wavelengths. By the equation for L , we see that these radiations can be detected, over a distance of 50 light-years, by a radio telescope of effective area 40km^2 and listening to a bandwidth of one hertz. If there is such a telescope on a planet within this distance, the discovery of our presence in due course, whether we intend it or not, is highly probably.

To build this telescope does not necessitate fantastic technological sophistication. In fact, as investigated in the Project Cyclops³⁰, the construction by us of a phased antenna array of ten thousand parabolic reflectors, each 30m in diameter, is feasible (it would cost six to ten thousand million dollars but this is less than half the cost of the Apollo space programme.) Such an antenna system would have an effective area of 20km^2 , and there appears to be no technological limitation to its expansion, to a size of 100km^2 or more. If we do build this colossal telescope, we will be able to eavesdrop on our neighbours. (A further feasibility study after Project Cyclops is being undertaken, and should be completed by summer 1976.) The Cyclops concept is already the basis of a very-large-array telescope now under construction in the plain west of Socorro in New Mexico. When completed, it will have 27 parabolic dishes, each 30m in diameter, and an estimated sum of seventy-six million dollars will have been spent. Scheduled for general radio-astronomical observations at 1.3, 2, 6 and 18-21cm wavelengths, it will be partially operating by the winter of 1977.

I have not discussed the rationality or even necessity of communicating with extra-terrestrial civilisations. Everyone will form his or her own opinion, and it seems out of place to argue here. However, it does appear obvious to me that it is wiser to devote our labours and

resources to seeking out life outside Earth, than to building things which potentially destroy life on Earth and which are no less expensive.

The table³¹ published last month listed projects to detect radio signals from extra-terrestrial intelligence which are still in progress. The complete projected programme in the USSR has been published³²; it is perhaps at present the country where (mainly for political reasons) such work is taken on most seriously.

References

- 26. Argyle, E., "On the observability of extrasolar planetary systems", *Icarus*, vol. 21, pp.199-201 (1974).
- 27. Huang, S.-S., "Extrasolar planetary system". *Icarus*, vol. 18, pp.339-376 (1973).
- 28. Shkovskii, I. S., "Multiplicity of inhabited worlds and the problem of interstellar communication", in *ibid* Ref. 9, p.80.
- 29. Freeman, J., and Lampton, M., "Interstellar archaeology and the prevalence of intelligence", *Icarus*, vol. 25, pp.368-9 (1975).
- 30. Oliver, B.M. et al, "Project Cyclops, a design study of a system for detecting extraterrestrial intelligent life", NASA Document CR-114445, 1972.
- 31. Sagan, C., and Drake, F. D., "The search for extraterrestrial intelligence", Scientific American, May 1975, pp.80-89.
- 32. U.S.S.R. Academy of Sciences, "The Soviet CETI Program", *Soviet Astron.-AJ*, vol. 18, pp.669-675 (1975).

Some readers interested in CETI and related subjects may like to read, among other magazines and journals, *Spaceflight* and the Red Cover issues of *J.B.I.S.*, both published by the British Interplanetary Society.

Sixty Years Ago

The following piece was printed, without much comment, in our issue of July, 1916. It was in the section "Digest or wireless literature", which contains a couple of fairly imaginative accounts of inventions and development, including a description of a wireless-controlled boat of 30 tons, which carried a torpedo at 50 mph and would turn upon and destroy any jamming transmitter!

Radium and aerials

"The following abstract of an article by E. Leimer in the *Elektrotechnische Zeitschrift*, printed recently by the *Electrician*, will be of special interest to our readers as it contains a report of some experiments on new lines.

On the results of Szilard with radium-coated lightning conductors becoming known to the author he was led to consider the possibility that radium might exert some effect upon the reception of radio-telegraphic signals.

The first experiments were made with an indoor antenna consisting of a wood rod closely wound throughout its length with wire, the rod being directed towards a sending station, FL, about 300 km distant from it. This antenna was suspended in a room. The receiving set used comprised a galena detector, 4,000 ohm telephones, and a tuning coil 50mm in diameter, and having 800 turns of enamelled wire. No signals were audible from FL at any position on the tuning coil. Signals were, however, at once distinctly audible as soon as a sealed glass tube containing radium bromide of 50,000 units. (and thus very weak) was brought near.

Literature Received

Television sound, off-air, is provided by the *Ambit 7700* tuner, which contains a u.h.f. tuning head and therefore requires no pickup coil. The tuner is compatible with 6MHz, 5.5MHz and 4.5MHz intercarrier frequencies at aerial input levels of 10µV or more and is provided with a four-channel selector and indicator. A leaflet is obtainable from *Ambit International*, 25 High St, Brentwood, Essex WW401

Multiway circular connectors, type 602GB, are described by *Amphenol* in a new catalogue. The connectors are intended for military and civil aerospace use and are resistant to most solvents and fluids likely to be encountered, including salt spray. They also meet the requirements of BS 2G 100 P2 C11. *Amphenol Ltd*, Thanet Way, Whitstable, Kent WW402

Rare-earth cobalt alloys in powder form, for the making of permanent magnets, are made in a new process by *T. H. Goldschmidt Ltd*, which is discussed in issue 4/75 No.35 of *Goldschmidt Informiert*, available from the company at York House, 353a Station Road, Harrow, Middx WW403

Aerials for domestic radio and television are dealt with in a publication from the *British Aerial Standards Council*. The booklet describes methods of measurement, together with the relevant electrical and mechanical requirements. Available from the council at 27 Ingorsby Lane, Houghton on the Hill, Leicestershire, the booklet costs £1.

Heathkit's new catalogue supplements, containing the latest exotica, are now available. Introductions are a pre-amplifier (£94), an equalizer (£88), a 200W power amplifier at up to £340, a 10MHz oscilloscope at £270 and a digital i.c. tester at £49. But the real mind-boggler is, we are informed, a *Digital AM/FM Stereo/Quadraphonic Tuner/Preamplifier* at £550. The only thing we couldn't spot on the front panel was a handle to wind it up. The supplements can be obtained from *Heath (Gloucester) Ltd*, Bristol Road, Gloucester WW404


Precision metal pressing by *Latham Manufacturing Co Ltd* is briefly described and illustrated in a brochure, now available from *Latham* at Croxstalls Road, Bloxwich, Walsall, Staffs WW405

Audio accessories are listed by *Ross Electronics* in their enlarged catalogue, which includes tape, headphones, microphones, test meters and connecting leads. The catalogue can be obtained from *Ross Electronics*, 32 Rathbone Place, London W1P 1AD (Trade only.)

An X-Y recorder, the *HR2000*, is the subject of a brochure from *Gould Advance*. The instrument takes the form of a mainframe with inputs and pen controls, with a range of input modules to provide a choice of sensitivity and speed. The brochure is obtainable from *Gould Advance Ltd*, Roebuck Road, Hainault, Essex WW406

HF predictions

HPF (highest probable frequency) is the frequency above which the probability of ionospheric reflection is less than 10% and FOT (from the French optimum working frequency) is the frequency below which reflection probability is greater than 90%. Thus the skywave probability of any given frequency can be found from the charts. Although a skywave path may exist signals can be below noise level and LUF (lowest usable frequency) is the 90% probability contour of signal level exceeding noise level by a certain amount. Best operating frequencies for consistent day to day working will lie between FOT and LUF and this applies when LUF is higher or lower than FOT. The latter condition implies that the certain amount referred to above cannot be realised.

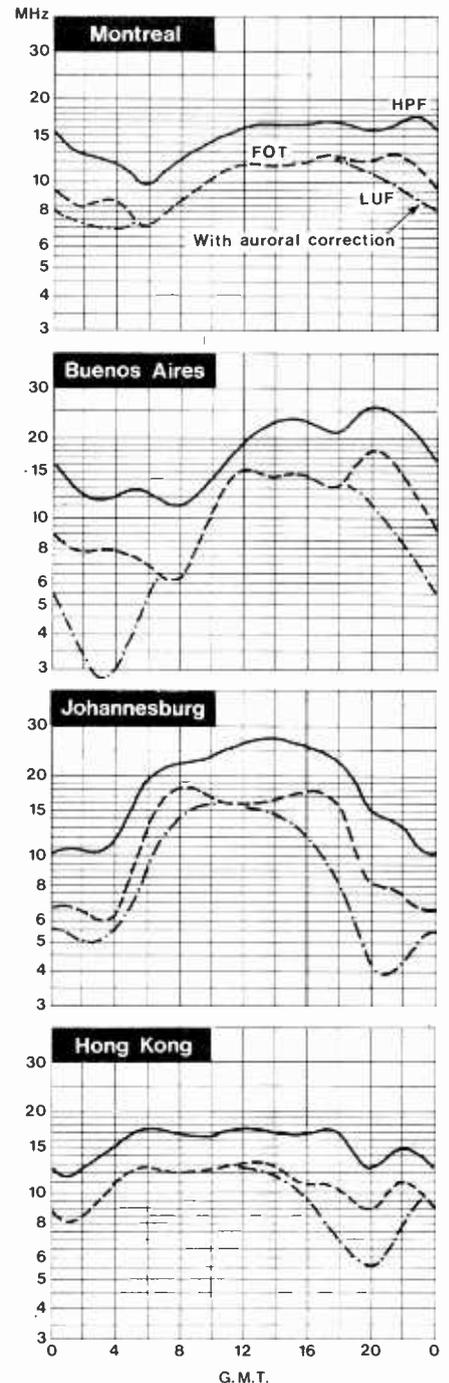

Unfamiliar forms of temperature compensated voltage reference

The Widlar diode and others

by K. C. Johnson, M.A.

It is almost universal, at the present time, to use zener diodes whenever a constant voltage is required in an electronic circuit. These devices depend on the breakdown of a reverse-biased junction between two semiconductors and the characteristic voltage can be varied over a wide range by controlling the abruptness of the junction (width of the depletion layer) during manufacture. If a very abrupt junction is made, breakdown occurs at a low voltage, while less abrupt junctions give higher voltages. In low-voltage devices the temperature coefficient is negative, since the breakdown is predominantly by the true zener action, while in higher-voltage devices, where breakdown is due to avalanche action, the coefficient is positive. In silicon, the two effects compensate at about 5.6V; consequently a silicon diode with this breakdown value has an almost zero variation with temperature. At 3.3V the variation matches that of an ordinary forward-biased junction such as the base-emitter of a transistor. Both of these types of diode, together with others where compensation is obtained by connecting junctions in series, are in very wide use and will be familiar to readers.

There are, however, two other ways in which temperature-compensated reference voltages can be obtained, using only the forward conduction characteristics of semiconductor junctions. These arrangements are very much less known, but offer advantages in that they work at lower voltages and do not require such precise control of the abruptness of the junctions. In order to understand their action one must first consider the effect of temperature on conduction under forward bias.

Forward-biased junctions

The usual Schottky formula for the current flow i at an applied voltage V is

$$I = I_0 [\exp(qV/kT) - 1]$$

where I_0 is the leakage current, q the electronic charge, k Boltzmann's constant, T the absolute temperature.

From its appearance, this formula should also predict the changes of

current with temperature, as it clearly contains T , but in fact any results it gives will be wildly wrong. The trouble is that I_0 is not constant but changes rapidly with temperature.

To improve matters we must alter the formula into the form

$$I = I_G \left[\exp(q(V - V_G)/kT) - \exp(qV_G/kT) \right]$$

and choose a value for V_G so that I_G really is essentially constant irrespective of temperature changes within the working region. When this is done it turns out that V_G is approximately equal to the energy gap of the semiconductor material (1.2V for silicon) while

I_G has a value far larger than any real working current.

Suppose now that such a diode is made to carry a constant current while its temperature is allowed to change. The second exponential term in the formula represents the insignificant leakage current only and so the first term must remain virtually constant. It can only remain constant if $(V - V_G)$ changes in direct proportion to T , and this is what happens in practice.


If, for example, a particular type of silicon diode requires 0.65V to carry 1mA at 25°C, the formula predicts a temperature variation of

$$\frac{0.65 - 1.2}{25 + 273} = -0.00185 \text{ V/}^\circ\text{C}$$

which clearly agrees well enough with the normally accepted figure of $-1.8\text{mV/}^\circ\text{C}$.

This behaviour can be represented graphically as in Fig. 1. A diode behaves as if cooling to absolute zero temperature would make it insulate at all

Fig. 1. Zener diode characteristics indicating how the difference between the voltage (V) across a diode at any given current and the energy gap (V_G) of the semiconductor expands in direct proportion to the absolute temp. (T).

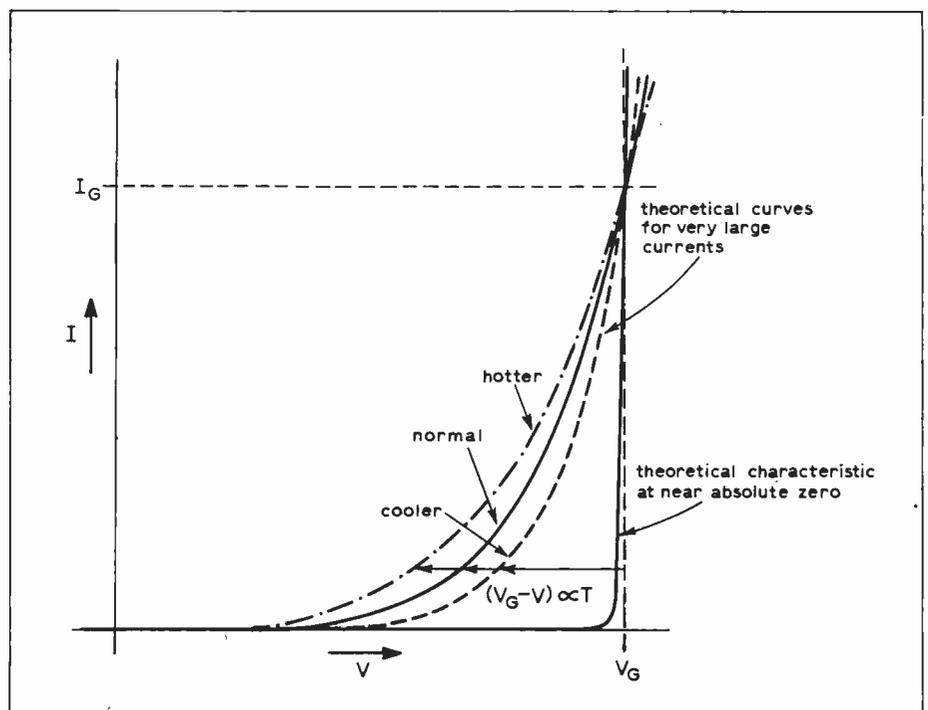

voltages below V_G and then turn on unlimited forward current, with an almost superconducting slope resistance, at that voltage. As the temperature is increased, the familiar exponential characteristic appears and expands linearly away from the V_G ordinate.

The Widlar diode

The Widlar diode is really an assembly of three transistors and three resistors, as shown in Fig 2. All the junctions are of the same semiconductor material and are essentially at the same temperature, but the circuit behaves as a compensated voltage reference as seen at the two terminals. Temperature compensation is obtained by exploiting the fact that a forward-biased junction, carrying less current in the same area, has a working voltage further away from V_G and hence has a greater temperature coefficient. In silicon, the effect is roughly a 10% increase for every reduction by a factor of 10 in the current. This can be verified from the formula given.

The three resistors in the circuit are selected so that Tr_1 and Tr_3 each carry 1mA, while Tr_2 carries 0.1mA (all three transistors being of the same type) when the voltage applied is at some value near 1.2 volts. Typically, the values might be 540 Ω , 575 Ω and 5.4k Ω respectively for R_1 , R_2 , and R_3 . Therefore the whole assembly carries 2.1mA at 1.2 volts.

If the applied voltage is increased slightly, the current in Tr_1 will, of course, increase. The stabilizing effect of R_2 , however, makes the corresponding increase at Tr_2 very much less, even as a proportion. The voltage across R_3 therefore remains almost constant and a large part of the original voltage increase is passed to the base of Tr_3 , which is consequently turned on. The overall effect is that the slope resistance at the terminals is in the region of 30 Ω while the intercept resistance is nearly twenty times this value. The circuit clearly gives a constant voltage action.

Suppose now that the temperature rises slightly. The voltage at the base of Tr_1 will fall, since the junction conducts

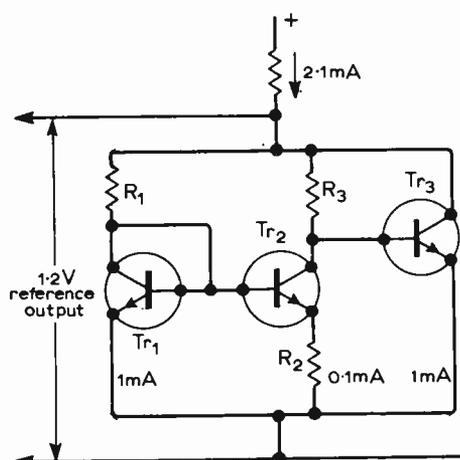


Fig. 2. The Widlar diode circuit.

more easily, and the base of Tr_2 will fall with it. The emitter junction of Tr_2 , however, was carrying less current and so has a greater temperature coefficient. The voltage across R_2 therefore rises and increased current flows in Tr_2 and Tr_3 . If R_3 is large enough the resulting fall of voltage at the base of Tr_3 can be sufficient to cut the current in that transistor by an amount greater than the combined increase in Tr_1 and Tr_2 , despite the warming of the emitter junction.

The magnitude of R_3 depends directly on the value selected for the voltage when the resistor values were determined. Selection of a large voltage would therefore have given over-compensation, while a small voltage would have under-compensated. The value for an exact balance depends on the precise properties of the components used, but is in the region of the figure of 1.2V already quoted.

The fact that this arrangement uses only standard transistors operating in the normal way makes it much more attractive than a zener for use in integrated circuits. The lower voltage is also more convenient if the incoming power is from batteries or a standard 5V supply. Many integrated circuits rely on Widlar diodes for their voltage references, but the three transistors are often hidden in a complex circuit diagram without any clear explanation of their function.

The l.e.d. as a reference

Another, simpler, form of temperature-compensated voltage reference can be obtained using the forward conduction characteristic only. If two junctions of different semiconductor materials both obey the theoretical formula reasonably well then it is possible to select the devices and adjust their current levels so that the values of $(V - V_G)$ match to give equal variations with temperature, while the actual values of forward voltage are appreciably different. If the two voltages are arranged to subtract in a circuit the required effect can be obtained.

Silicon and germanium could obviously be used in this way but the resulting difference in voltage would be rather small and might not be very stable. A more attractive alternative, which has only recently become possible, is silicon and gallium phosphide or arsenide phosphide. Diodes made from these new materials are now in large scale production for use as l.e.d.s and are already no more expensive than zener diodes. In spite of the fact that they are designed primarily for making visible light these devices have a surprisingly low series resistance and obey the Schottky formula well at currents in the milliampere region.

A great many different types of device are being made and the values of $(V - V_G)$ can be expected to vary accordingly, but some measurements of a few

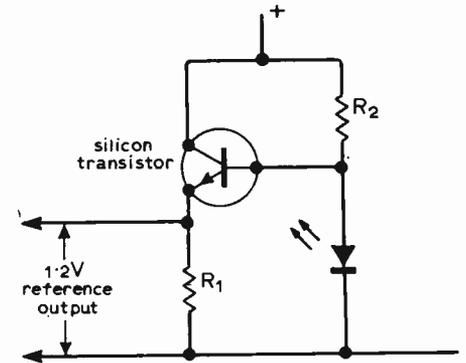


Fig. 3. A reference voltage using a gallium phosphide l.e.d.

commercial l.e.d.s of various colours were made by Mr S. G. Hale and all showed values of temperature variation within 10% of that of a typical silicon transistor. There would appear to be little difficulty in selecting devices to match more accurately than this. The value of V_G for this material is about 2.4V, so the compensated reference output will again be in the region of 1.2V.

The kind of circuit shown in Fig. 3 can be used to obtain the necessary subtraction. The resistors R_1 and R_2 fix the levels of current in the two junctions and can be adjusted to give a fine control of the compensation, since a larger current gives a reduced variation. If a really stable output is required the l.e.d. should be shielded to avoid any photo-cell action, but for most practical applications this refinement is unlikely to be needed and the device might even do double duty as an indicator lamp.

If a constant current rather than a voltage is required, then this can be obtained from the collector of the transistor in Fig. 3. Once the basic principle is understood, there is no great difficulty in arranging circuits for multiplication of the voltage or any other of a vast range of requirements. This second system may well prove the more useful to readers on account of its simplicity, but it is unlikely to find application in integrated circuits due to the mixing of semiconductors.

Gravitational radiation — a fruitless search

Another disappointment in the search for gravitational radiation: the Glasgow University team working on the subject report a negative result from further test runs. This latest work was designed to test the possibility that a series of short pulses of gravitational radiation might produce a cumulative response in a detector, big enough to account for reported detections elsewhere. This now seems likely.

Wideband compander design

Simple square-law circuit gives 100dB dynamic range

by John Vanderkooy

University of Waterloo, Ontario

The wideband compander described can preserve the dynamic range of virtually any input signal when recorded by a normal tape recorder. Operational amplifiers and matched photocells allow accurate compansion with no necessity for calibration or care in recording levels. The unit can be used in compression mode for recording or playback in noisy environments, and for speech signals.

The dynamic range of tape recorders has never been adequate for high quality reproduction. If a high input level is used in an attempt to decrease the effects of tape noise, distortion results on loud passages and transients are severely distorted. Reducing the level to allow even moderate transients to be captured with little distortion means that small signals will be lost in noise. A good quality half-track reel-to-reel machine can expect a signal-to-noise ratio of about 60dB and because normal audio signals vary more than this, most recording is caught in the compromise between noise and signal distortion.

Several commercial devices are available to solve these noise problems. Dolby A systems are compressor-expanders that work in a number of frequency bands in the audio spectrum. They are very virtuous but are beyond the stage where home construction can be contemplated. The Burwen compressor-expander¹ is a device that works over the whole audio spectrum, using cube-root compression and cubic expansion, along with some equalization. Circuits for this compander were not available to the author, but the appeal of the basic system was such that a design suitable for home construction was sought and finally achieved. A recent advertisement from DBX indicates their companders may be similar to the one described here. Recently, Self² has detailed a circuit for compression only. Stuart³ has described several other active systems but not the power law compander so its basic merits will be given below.

If a compressor is designed to take an input audio signal I of large dynamic range and compress it to an output θ in accordance with the law

$$\theta = k_1 I^n$$

where k_1 is a constant and n is a positive integer (it could be fractional, but the electronics is more complicated), then the dynamic range of θ can be such that a tape recorder can faithfully record this signal. We assume that the playback signal P is equal to θ for a unity gain recorder. (There will be some error and its effect will be discussed later). Then if an expander is made which gives a final output signal S given by

$$\begin{aligned} S &= k_2 P^n \\ \text{then } S &= k_2 \theta^n = k_2 (k_1 I^n)^n \\ &= k_2 k_1^n I \end{aligned}$$

and hence except for the constants, which will vary if level controls are altered, the signal S is a scaled version of the original input I . For domestic use it is argued that $n=2$ is a good choice. An input signal of 100dB variation will be compressed to 50dB at the tape, thereby achieving a good performance with modest recorders. The $n=3$ system used by Burwen¹ shows deficiencies when used with domestic recorders having considerable variations in response with frequency. If the recorder has a response error of X dB then the final expanded signal will have an error of nX dB. A wide spectrum signal such as normal audio will relieve these difficulties, but if a 6dB variation in response exists, the cubic system is impractical.

Recent articles by Shorter⁴ on the Wireless World Dolby B noise reducer give much useful information on compansion in general and prompt a comparison between wideband compansion and Dolby B. I have always preferred the transmission of programme material by simple 2:1 logarithmic compression, rather than Dolby B methods, because the frequency response is then not altered by receivers not equipped with standard decoders. I fear the extra top will become so enticing to people that the Dolby decoders will hardly find use. In essence it boils down to a preference for distortion in level as opposed to distortion in frequency response. An interesting view of Dolby methods from the BBC recently appeared in a letter to the editor⁵.

A real advantage of the Dolby B approach is that only high frequencies are altered, and gain changes can be made so quickly that no noticeable noise modulation and breathing exist. Present-day wideband companders can partially solve these problems as well. Firstly, the attack time can be very short, so that extra pre-emphasis can be used with a consequent reduction in noise. This however, creates more incompatibility with existing components and pre-emphasis is not used in the present design. Secondly, by using special filters to eliminate self-modulation distortion, but still retaining a rapid decay-time, the effects of noise modulation and breathing are subjectively reduced. This concept is used in this design. A definite advantage of wideband compansion is the much greater degree of noise reduction for low-level signals, as will be evident later. Professional

assessments of companders and Dolby systems are given in recent reviews⁶. For the moment it is to be appreciated that wideband compansion prevents overloading the recorder, reduces the effects of noise at low signal levels, and virtually makes recording level controls unnecessary. In addition an accurate power law device will reproduce faithfully irrespective of the settings of the level controls. No reference levels are necessary as in Dolby systems or other non-linear companders.

Requirements

The heart of a compander is a gain-controlled amplifier which can divide or multiply the gain by means of a control voltage. It must be capable of 50 or 60dB gain variation with an accurate characteristic. A good audio bandwidth must be maintained over the whole variation, and the distortion should not exceed 1%. The gain variation must be rapidly programmable as well. A servo system driving a potentiometer would be accurate but too slow. A good figure to shoot for in response time is several milliseconds. This allows even transients to be respectably dealt with.

A well-built transconductance multiplier will satisfy the above characteristics, but it has too much wideband noise. This is due to the necessity of small signal levels at the bases of the multiplying transistors to prevent distortion.

As well as an accurate multiplier-divider, the circuits which caliper the audio level and produce a smooth rectified signal proportional to the amplitude must be accurate and have an attack time less than a few milliseconds. The release time should be rapid to prevent pumping but not rapid enough to cause distortion by "self modulation" of a low-frequency signal.

Experiments

Early experimental attempts at making the multiplier-divider centred on f.e.t.s and their source-drain characteristics near the origin. Distortion is high if the f.e.t. is used in a straightforward way. It can be greatly reduced if the gate is driven not only as a control voltage but as an alternating voltage which is midway between that of the source and the drain as in Fig. 1(a). This gives the device a drain characteristic of odd symmetry. Thus all even harmonics are entirely

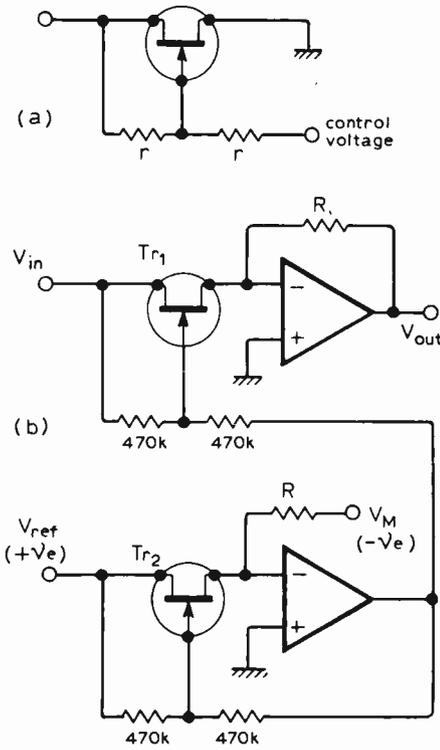


Fig. 1 (a) The distortion of the f.e.t. as a voltage-controlled attenuator can be reduced by driving the gate with an alternating voltage midway between the source and drain voltages. (b) by using a second matched f.e.t. the variation of the gain can be made proportional to V_m/V_{ref} .

removed by this "push-pull" technique, and only odd harmonics, mainly third, occur at higher signal levels. The problem still remains that a large gain variation of greater than 30dB is difficult to achieve, and the gain is not a simple function of the control voltage. The last-mentioned problem can be alleviated by using one of a matched pair of f.e.t.s (a dual) to generate a specific resistance using an operational amplifier.

In Fig. 1(b), Tr₂ has a resistance which is determined by setting the input current of the op-amp equal to zero with due respect for the virtual earth, i.e. $V_{ref}/R_{f.e.t.} = V_m/R$. Transistor Tr₁ will have the same resistance and the upper circuit, which handles both polarities for audio, will obey a law $V_{out}/R = V_{in}/R_{f.e.t.} = V_m V_{in}/V_{ref} R$. Thus $V_{out} = V_{in} V_m/V_{ref}$. Division and multiplication have both been accomplished! This circuit technique must be remembered for the multiplier to be described later. It is not suitable in the present form since not enough gain variation is available.

Another method attempted was to make a transconductance multiplier using f.e.t.s as the input active elements. They would not be as linear as transistors on a relative basis but since the voltage scale on which they turn on is about a volt as opposed to the 25mV for a transistor, much less attenuation of the input signal is necessary and this together with lower f.e.t. noise would reduce the noise to small values. Disadvantages of the design are the difficulty of obtaining division and the requirement of four well-matched f.e.t.s.

Photoconductive cells were also considered as possible gain control elements for

the multiplier-divider. Initial experiments indicated that when a light-emitting diode was suddenly turned on the coupled photocell would respond with approximately two time constants, one a fast but rather small relative behaviour, the other a slower rise of about 10ms to a final conductance level. This is not suitable for a fast-acting gain control circuit. Also the final conductance value was not properly proportional to the i.e.d. current. Fig. 2 shows the characteristic of resistance versus current for a CL904N photocell coupled to an i.e.d. A straight line of slope -1 would represent ideal behaviour.

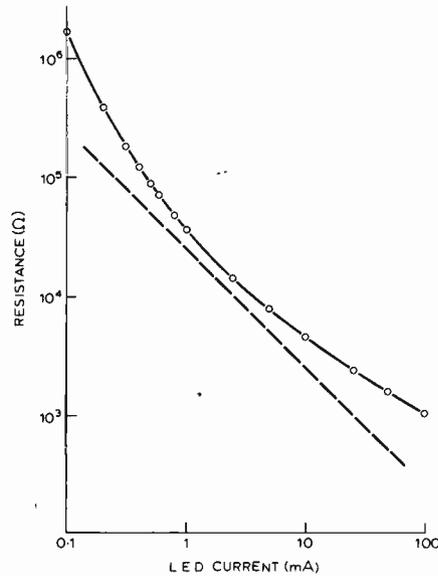


Fig. 2 Curve of photocell resistance versus i.e.d. current for a Clairex CL904N photocell when illuminated by a red i.e.d. The unbroken line is drawn through the experimental points. The dashed line represents ideal behaviour.

It was decided to employ op-amps to linearize the cells using the technique mentioned earlier. Fig. 3 shows the basic idea for a multiplier. A divider can be constructed by interchanging the resistor and the photocell as gain-determining elements for the amplifier A₁. The i.e.d. shines equally onto both photocells. Tracking of the photocells is essential for an accurate power law comparison, but an error does not significantly affect the overall characteristic, see later. From five photocells at least two would track well over factors of 100 change in the resistance.

Experiments with this multiplier-divider

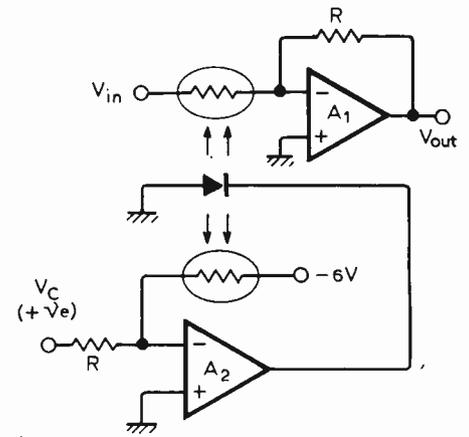


Fig. 3 Photocells and a controlling i.e.d. are used here as a multiplier using a concept similar to that shown in Fig. 1 (b). For this circuit $V_{out} = V_c V_{in}/6$.

showed that a 60dB range was possible and the attack time for a large step increase in the control voltage was about one millisecond. The feedback has thus considerably reduced the sluggishness of the cell. At low light levels the cell seems to have a longer time constant and a nonlinear network placed in series with the i.e.d. maintains good control stability over all voltage levels.

Fig. 4 shows the rectifier circuit that was adopted to produce a direct control voltage for the multiplier-divider. Amplifier A₂ has circuitry which creates an absolute value circuit with a gain of 2/3. Diode D₂ is used to create a virtual earth at the inverting input for positive input signals so that the upper 5k and 10k resistors can form a simple attenuator. This diode also prevents op-amp saturation and hence allows accurate response up to the highest audio frequencies, a feature which many precision rectifier circuits do not have.

Amplifier A₃ is a peak detector in which D₄ prevents saturation of the op-amp when the input voltage from the absolute value rectifier is lower than the voltage on C₁. Another advantage of this diode is more subtle. If a rectified sine wave of constant amplitude is fed into the peak detector, the

Fig. 4 Schematic of the circuit used to obtain an absolute value of the audio signal and produce a control voltage proportional to the peak of the waveform.

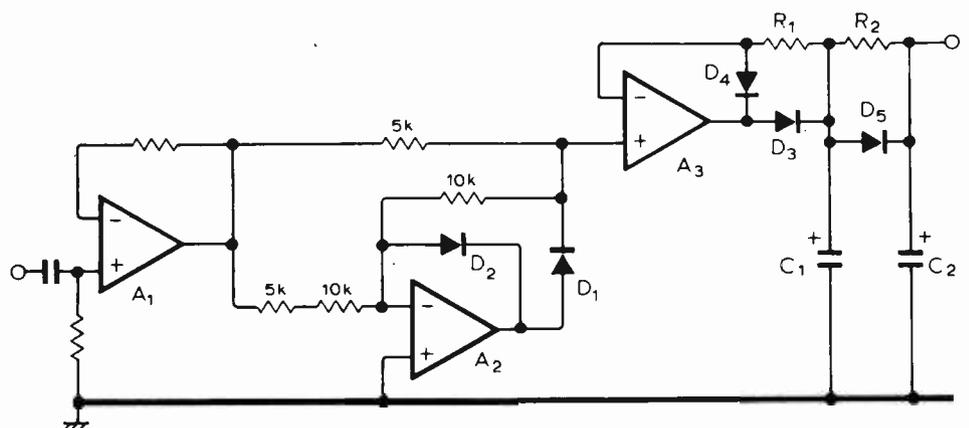


Fig. 5 Complete schematic of the compander. Op-amps are assumed to have $\pm 15V$ power supplies. For best performance amplifier A_1 should have separately decoupled supplies. The $10k\Omega$ resistor in the compensation should be referred to the negative supply.

droop at C_1 is much less than in a circuit in which R_1 is returned to ground rather than the inverting input terminal. This is so because the negative input terminal follows faithfully the input signal on the non-inverting input terminal. However, if the audio signal disappears, then R_1 is effectively returned to ground and the decay time constant is short. For audio frequencies $> 1/2\pi R_1 C_1$, the droop is only $1 - (2/\pi) \approx 0.36$ as large in this circuit as when R_1 is returned to ground. Components R_2 and C_2 provide extra filtering and D_3 allows the control voltage to rise quickly in the presence of audio transients. The input follower A_1 is necessary because the input impedance of the absolute value circuit changes with signal polarity.

Circuit description


The complete compander circuit diagram is shown in Fig. 5. Switching allows the circuit to be used as a compressor during recording, and as an expander during playback. In the compression mode, the control voltage acts to decrease the audio gain as a divider. Hence the output θ will be related to the input by the relations $\theta \propto I/V_c$ or $\theta \propto \sqrt{I}$, a square-root compressor. When in the expansion mode, the audio gain is precisely proportional to the control voltage. Hence the final output signal S is related to the playback signal by the relation $S \propto PV_c$ but V_c is derived now from the audio signal P , hence $V_c \propto P$. Thus $S \propto P^2$ and a square-law expander results.

If the photocells do not track well, the division or multiplication factor must still be the same function of control voltage, say $f(V_c)$, because of the way the photocell is switched in the compress and expand modes. Hence $\theta = I/f(V_c)$, and if we assume again that $P = \theta$ (for a good recorder) then

$$S = Pf(V_c) = \theta f(V_c) = I.$$

Thus a perfectly complementary system still results. Careful analysis shows that this is true only if the recorder has unity gain, because otherwise the playback signal would produce a different control voltage than that used during recording. Only a power-law behaviour of the function $f(V_c)$ will preserve the relative level differences. In the present circuit $f(x) = x$, a simple function indeed.

The major circuit blocks in Fig. 5 can easily be recognised from the earlier discussion, but several features warrant special consideration. The operational amplifier A_1 used in the multiplier is used in a circuit in which the gain is varied by up to 60dB. At unity inverting gain, a compensation capacitor of about 15pF between pins 1 and 8 (half of that for a voltage follower) is necessary for stability. But this is detrimental to the frequency response when the gain is high (a small amount of feedback), as for example during small signal levels in compression. Pin 8 comes from the output circuit of the op-amp. Pin 1 is a high impedance point which has a signal referred to the negative supply line. The difficulty occurs when the

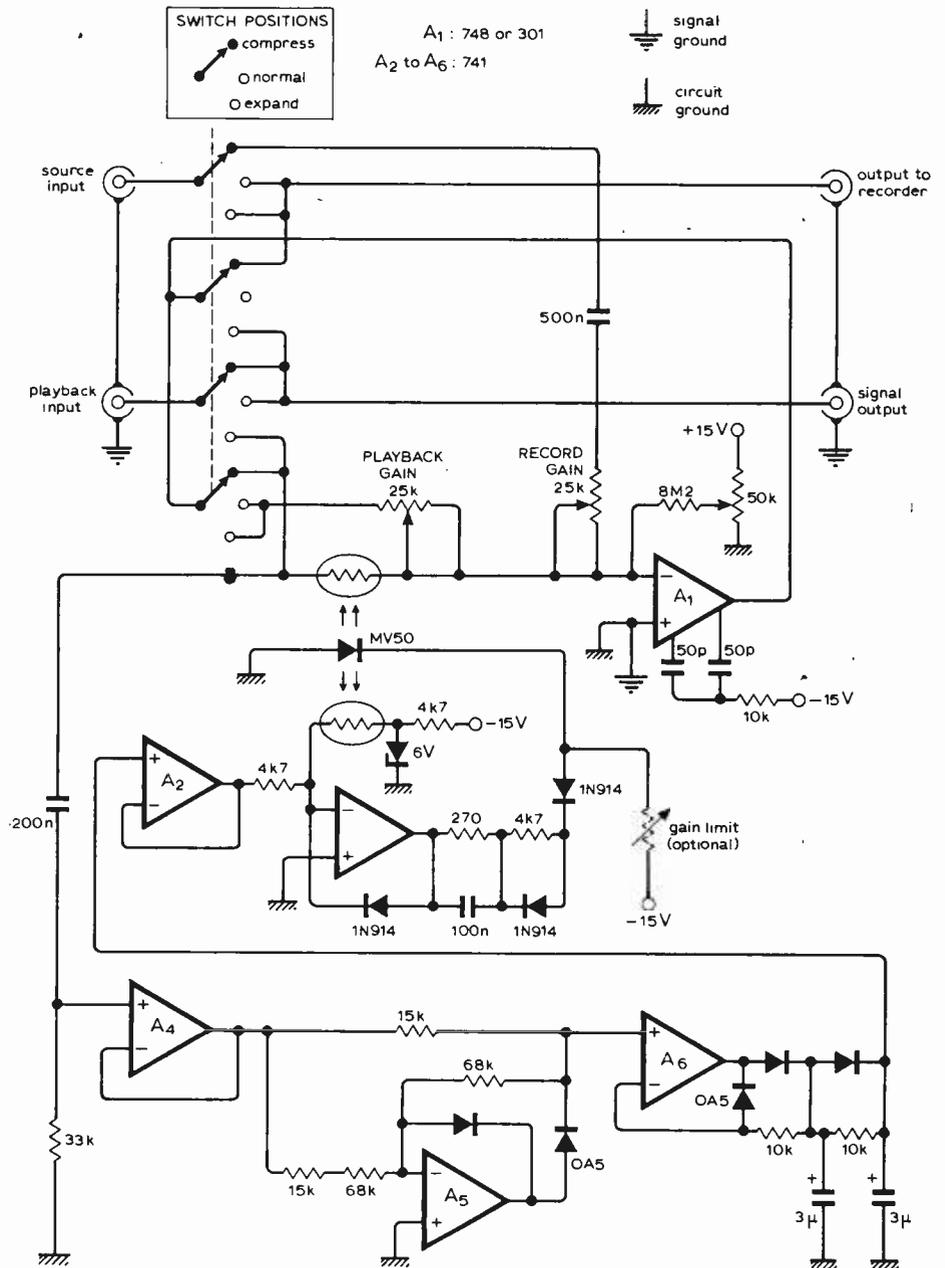


high level signal from pin 8 is injected into pin 1 through the normal compensation capacitor. The gain is drastically reduced at high audio frequencies. But there is no problem with op-amp stability at these frequencies; instability only occurs near 1MHz. The $10k\Omega$ resistor between the two $50pF$ capacitors shunts the gain reducing signal to the negative supply line thus restoring the gain at audio frequencies while not materially affecting stability considerations at megahertz frequencies.

An important point is the selection of photoconductive cells. Impedances of $1k\Omega$ are ideal for op-amp gain determining resistors. Lower values might tend to cause current limiting at high signal levels. It is therefore recommended that the photocells have resistances of not much less than $1k\Omega$ when illuminated by an l.e.d. carrying a current of 10mA. The l.e.d. can be glued to the two matched photocells (or dual photocell) with clear epoxy.

In a stereo system one has a choice of building a compander for each channel (the best solution) or of combining functions together. In a combined system it will be necessary to control three photocells with one l.e.d. If matched l.e.ds are available then

two double units can be used. But they are not easily matched. Some require a threshold current before they start to emit light. In any event the right and left channels should be summed before peak detection. The voltage follower in the rectifier circuit can easily be rewired to act as an inverting summer. Of course two separate op-amps will be necessary with compensation as described earlier.

Due to the switching in the rectifier and peak detecting circuits, it is recommended that separate decoupling be used for the supply lines to the signal op-amp. All input and output connectors should have their signal ground connected to the non-inverting input of A_1 . You may wonder why a low-noise audio op-amp such as the Fairchild 739 was not used in the signal circuits. This is because these do not have adequate reserve gain for the multiplier - divider action necessary here. They also draw more input current, causing greater offsets when the gain is high. It is wise to include the input offset current adjustments for the signal op-amps as shown in Fig. 5. The offset is adjusted to provide zero direct output voltage with a very low signal input in the compress mode. If this is not done a low frequency thump will occur when the gain

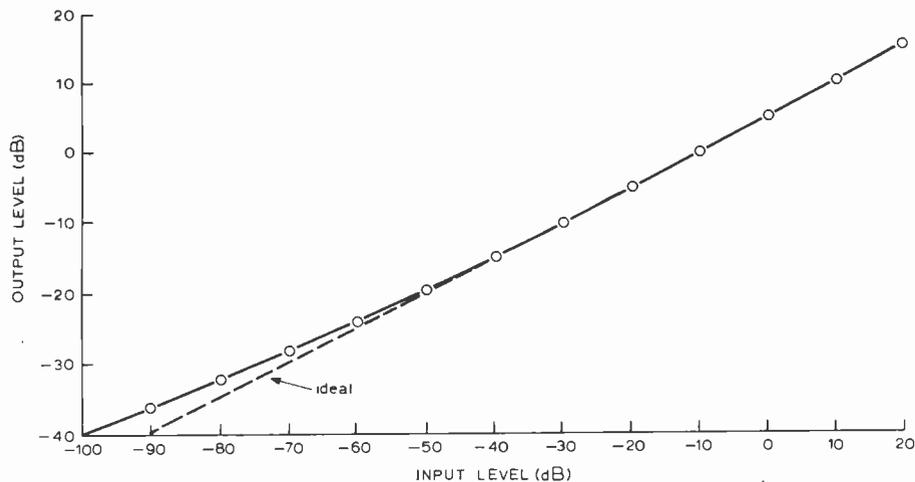

changes quickly.

Another point is that for no signal level in the compress mode, the gain is very large and is limited mainly by the rectified output noise. This is not usually a problem since most sources for recording in the home such as discs and microphone arrangements have enough background noise. An easy way to eliminate such problems is the inclusion of a resistor shown dotted in Fig. 5 which limits the maximum gain, by preventing the i.e.d. current from becoming zero.

As shown, the compander responds to very low frequency signals and has low phase shift. Sometimes a turntable can have a large low frequency rumble which can modulate the compressor gain. In such cases a filter should be used to remove such low frequencies. A simple solution is to decrease the value of the $0.5\mu\text{F}$ record input coupling capacitor to give an appropriate cut off frequency. If a recorder with restricted bandwidth is used, it is wise to restrict the input to the compander to the same extent. This ensures that the rectifier circuits will see similar signals on compression and expansion.

The power supplies should be well regulated for optimum performance, but unregulated supplies with good ripple filtering are acceptable. The transformer should supply 11V a.c. on open circuit and allow 70mA of current drain.

All diodes can be silicon signal diodes, such as 1N914, 1N4148, 1S44; only D_3 in Fig. 4 should be a germanium signal diode as this will help reduce overshoots in compression.

Input impedances are simply given by the values of the record and playback preset potentiometers. The outputs are low impedance, and perhaps 560Ω resistors should be added in series with these outputs to prevent damage if high signal levels are inadvertently applied to these outputs.

Performance

The most important characteristics are the compression and the accuracy of the whole process. Fig. 6 shows the graph of output level versus input level in the compression mode of operation. The deviation of the curve at very low input levels is due mainly to photocell tracking error, and partially from the amplified noise of the 748 op-amp. The input voltage is not measured at these low levels; it is inferred from the settings of an accurate low impedance attenuator. Deviation from a square root behaviour is never more than 1dB for well over 80dB of dynamic range. All levels are in dBm ($0\text{dBm} = 0.775\text{V r.m.s.}$).

Fig. 6 Curve indicates output level versus input level when the compander is in the compression mode. Note that a 60dB input variation is compressed to 30dB of output variation to be recorded on the tape.

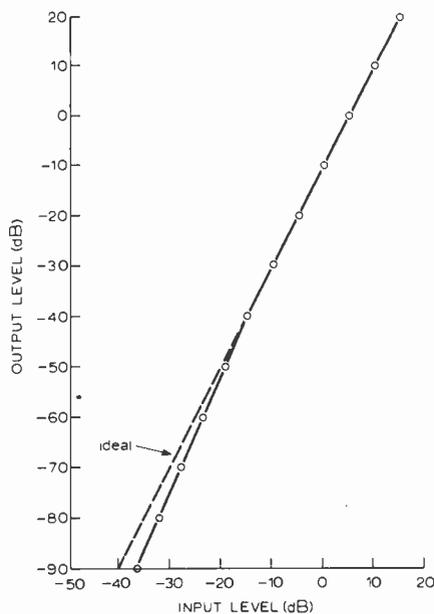


Fig. 7 Output level versus input level in decibels for the expansion mode. A 30dB input variation from the recorder on playback would be expanded to an output of 60dB to be fed to a power amplifier.

Fig. 7 shows the output level versus input level in the expansion mode. The curve again shows almost no discernable deviation from a square law. Output levels are difficult to measure with standard a.c. voltmeters below about -90dB . The complete characteristic from recording input to final signal output is linear to much better than 1dB because of the exact complementarity discussed earlier.

Even the dynamic characteristics are precisely complementary, because the audio signal used to produce the control voltage is derived from the output in compression

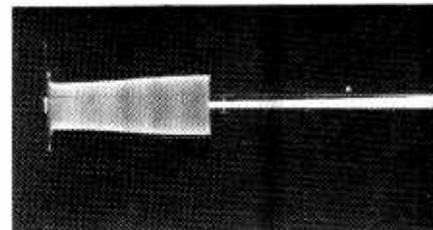


Fig. 8 Oscillograph of the compressor output when the 1kHz input signal is suddenly increased by about 30dB by a mercury wetted relay. (20ms/div horizontally, 2V/div vertically.)

mode, and from the playback input signal in expansion mode. These two signals should be the same for a good tape recorder. An overshoot in the compression mode, which is very difficult to suppress completely because of the time constants of the photocells and the peak rectifier, will not be exactly undone in the expansion mode. Only the leading edge of a transient sound will perhaps not be faithfully recorded, but the ear will forgive severe distortion for periods of several milliseconds. Fig. 8 shows the output signal to the recorder in compression mode when the input signal is suddenly increased by about 20dB. The signal frequency is 1kHz. Notice that there is a slight overshoot in the compression that lasts about 10ms. The transient edge dies away with a time constant of about a millisecond. There is some dependence in Fig. 8 on the phase of the input signal at the moment of switching in the higher level. One would expect this in fast-acting circuits. A real audio transient is likely to be less severe than the instantaneous switching used here as a test signal.

The release time constant is less than a tenth of a second, giving a fast enough action that even on a rapid reduction in signal level, no noise is noticeable on replay. The rapid release time is also advantageous if the compressor is used on the output of an automobile radio. The normally large variations in signal level will be reduced so that low levels are not masked by the ambient noise. (I have often wanted something akin to an engine-speed dependent volume adjustment on my automobile radio.)

For high fidelity purposes the compander must have low distortion. Fig. 9 shows the measured second and third harmonic distortion versus frequency in compression mode for an input level of +10dB. The rise at low frequencies is due to the ripple from the peak rectifier. The wideband distortion is due to the photocell characteristic and is mainly third harmonic.

Fig. 10 shows the second and third harmonic distortion versus the output signal level (the voltage across the photocell) at a frequency of 1kHz. Except at high output level, the distortion quickly falls near the noise limit of the wave analyser. There is approximately 0.05% of residual third harmonic distortion in the oscillator which may slightly raise or lower the measured third harmonic, depending on phase relationships. Distortion level is low enough because it does not represent a crossover distortion, only a gently curving transfer characteristic. However, it would be unwise to be too defensive

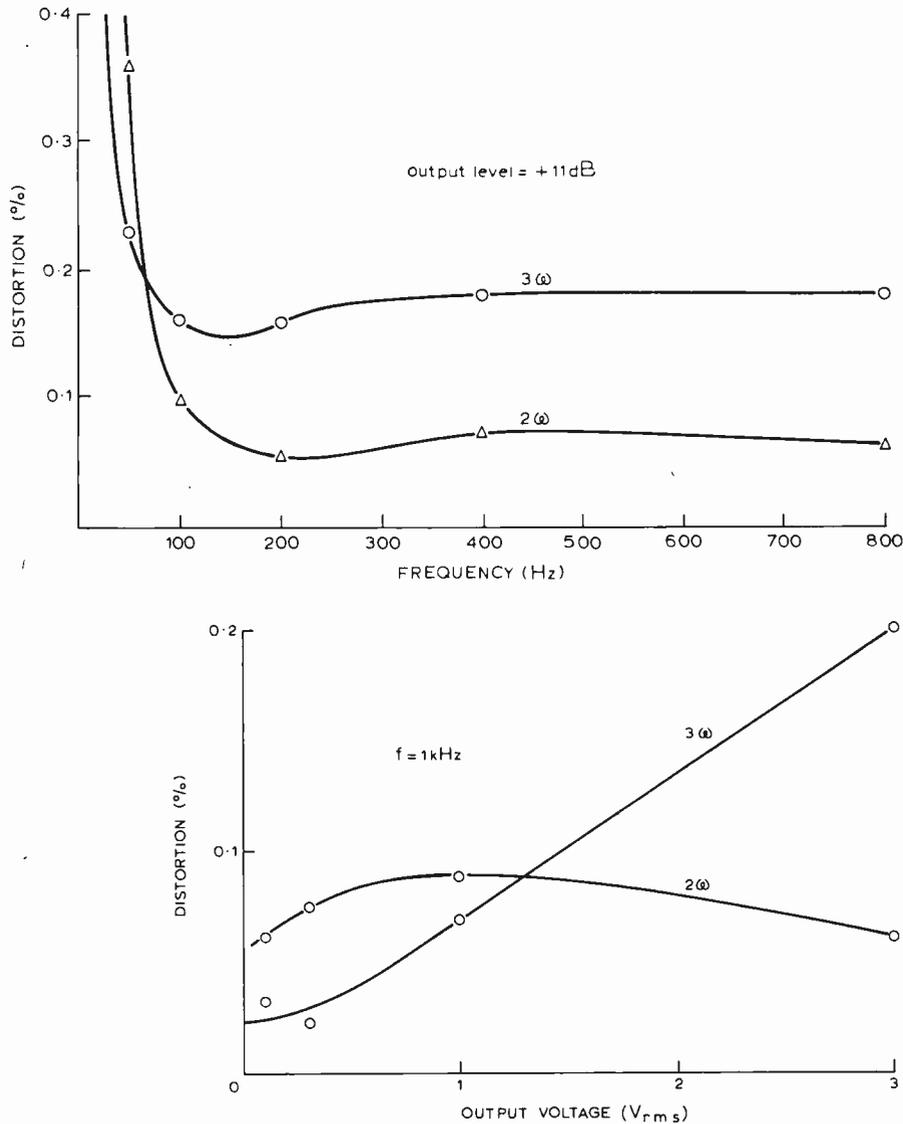


Fig. 9 Distortion of the compressor versus frequency for an input level of +10dB. Curves are substantially constant beyond 800Hz with a small increase beginning beyond 10kHz.

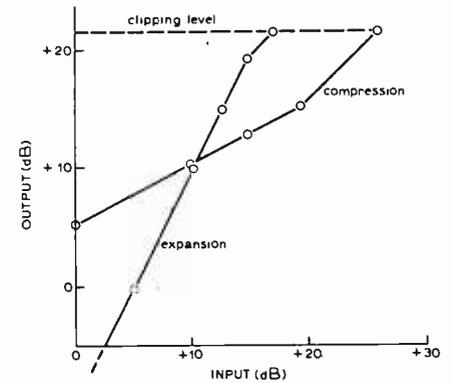


Fig. 11 Characteristics of the compander for high level signals. Clipping level in the compression or the expansion mode is determined by the supply voltage of the operational amplifiers. Deviation from square-root compression and square-law expansion results from the current limiting of the amplifier A₃ driving the l.e.d. These levels were obtained by setting the record and playback present potentiometers to 10kΩ. Altering these values will alter the point at which the behaviour saturates.

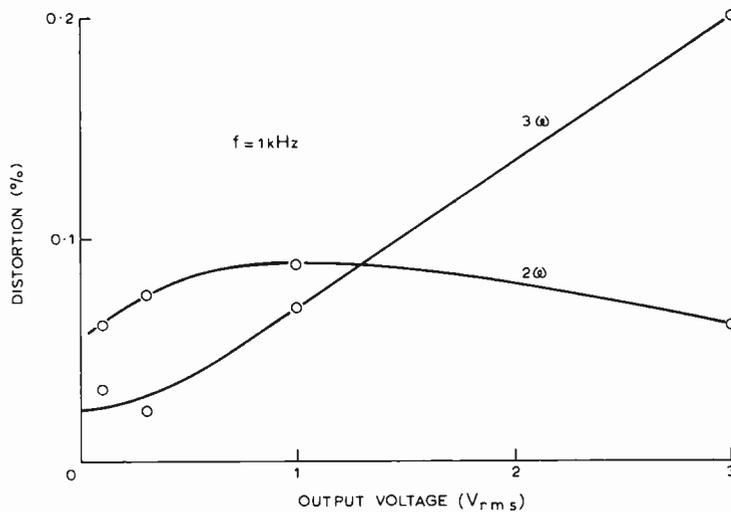


Fig. 10 Distortion of the compressor versus output voltage level at a signal frequency of 1kHz. There is a residual distortion of about 0.05% third harmonic in the oscillator which may alter the third harmonic results somewhat at low levels.

about distortion levels in photocell circuits. Some cells have much larger distortion than others. A number of different types were tried. I admit I could not hear the difference, but measured distortions of up to 2% at high level were occurring for some cells. The circuit whose measured low distortion is shown in Fig. 9 and 10 uses quite inexpensive cells, type VT-833, manufactured by Vactec Incorporated.*

Any reasonably fast CdSe photocell could be used with resistance characteristics as described earlier. A quick check on distortion can be made by applying 10V r.m.s. at 1kHz to a divider made up of 10kΩ resistor and the cell, illuminated to a resistance of about 10kΩ. If no appreciable curvature exists on an X-Y oscilloscope display or cell voltage versus oscillator voltage, the cell has suitable characteristics.

In Fig. 11 the clipping characteristics of the compander are shown in compression and expansion modes. The break point is due to current limiting of the amplifier A₃ in Fig. 5 which drives the l.e.d.

The final test of performance of an audio circuit must be the human ear. In microphone arrangements using the compander there is dead quiet at no signal level. This is far from true without the compander. Replay sounds natural and the settings of the level controls on either recording or playback are

unimportant as long as overload is prevented. Using good discs as a source there is no noticeable difference in the dynamics even on piano music when the compander is used. This is impressive performance for such a simple circuit.

How can the audio enthusiast use the compander? If his tape recorder has a signal-to-noise ratio not much worse than the sources at his disposal, then it is hardly worthwhile using it to preserve dynamic range. However, modern stereo cassette recorders have signal-to-noise ratios of around 50dB, whereas a live f.m. broadcast can have 70dB. Then 20dB of increased dynamic range will result. In a live microphone setup with a low noise preamplifier the increase in dynamic range is greater than 40dB, and here the compander allows almost complete disregard of the level controls.

If master tapes and discs were made with a square root compressor and radio stations would broadcast these directly, then an expander in the receiver could bring back the full dynamic range of the original signal. Another use for the compander occurs whenever there is a high background noise

level, such as in an automobile, workshop, or a home with children. The unit can be used to process a signal using compress mode, so that the dynamic range of the signal stays sensibly above the noise level. It is wise to include the dotted resistor of Fig. 5 in such setups to reduce the noise output when the signal level is very low.

References

- 1 Burwen R. S. Design of a noise eliminator system *Audio Eng. Soc.* Vol 19 December 1971.
- 2 Self, R. G. High-quality compressor printer, *Wireless World*, Dec. 1975 p.587-90.
- 3 Stuart, J. R. Tape noise reduction, *Wireless World* March 1972.
- 4 Shorter, G. *Wireless World* Dolby noise reducer, *Wireless World*, May 1975, p.200
- 5 Dolby f.m. broadcasting (letter), *Wireless World*, Sept 1974, p.344.
- 6 See, for example, *Studio Sound*, March 1974.

Printed circuit boards

Wireless World has arranged a supply of glass fibre p.c.bs. The board is a stereo version but using a common control circuit. (Two boards are needed for a two-channel version with separate control circuits.) Provision has been made for board-mounted l.e.ds and photocells, and connections are brought to one edge. One-off price is £3.50 inclusive from M. R. Sagin, 11 Villiers Road, London NW2.

*U.K. agents Teknis Ltd, Teknis House, Meadrow, Godalming, Surrey GU7 3HQ. The cells cost around £1.

News of the Month

Video-plus-data recording

The Japanese are using a teletext type of method to record simultaneously on video tape pictures and measurement data from industrial or other processes. The idea is that in investigating certain processes it is useful to be able to correlate pictures of events with measurements of the variables (e.g. temperature, pressure) that are significant in these events. At the 7th IMEKO congress held in London in May, H. Soga and co-authors described a system for multiplexing television pictures and data that has been applied to blast furnace operation and human body movement patterns. It uses an ordinary closed-circuit television camera and magnetic-tape video data coder.

The c.c.t.v. camera signals are sent by coaxial cable to the video data coder, and at the same time measurement signals from transducers on the process are fed in via an analogue-to-digital converter. The a-d converter produces the measurements as 10-bit digital signals, and after storage in a register the successive pulses of these data signals are fed out sequentially from the register and combined with the camera's video signal. Each data pulse is accommodated in an extended blanking period, following the line sync pulse and colour burst and before the video signal proper. Addressing is done by means of an additional identifying pulse, called a "group bit pulse", inserted at intervals also into the blanking period. Finally the composite video-and-data signal is recorded by the video recorder. On playback the data pulses are picked out of the composite signal by gating, converted back to analogue signals by a d-a converter and passed to pen recorders or other display instruments.

This process monitoring technique is said to be particularly useful when an experiment cannot be artificially repeated, or is expensive, time consuming or dangerous, or when a fully explanatory record is required for educational purposes.

Brake regulator eliminates locking

A new brake regulator system which allows car drivers to brake hard at high speed without risk of the wheels locking has been developed in Sweden. Many accidents are caused by cars going out of control because the wheels have become locked as a result of abrupt brake application at high speed, especially on icy or wet roads. The new system has a toothed rim mounted inside each wheel hub. The rim's rate of rotation is continuously monitored by a photocell which feeds data on every change in speed to an electronic control unit. When the brakes are applied and a wheel is about to lock, the electronic unit actuates a valve mechanism which causes the brakes to be released for a short time and then to be applied again. This process can be repeated up to 15 times per second and the brakes retain full effectiveness without locking the wheels. The inventors, two Linköping technicians, believe that, if the new system can be manufactured on a sufficiently large scale, it could be supplied at "reasonable cost" either as a spare part or as a component for installation during manufacture.

Microwaves for Ireland

The Republic of Ireland is to be provided with a new microwave communication system that will replace the country's existing television distribution network and provide additional TV coverage to new areas. The system will utilise 22 repeater stations over approximately a 750-mile route and will provide two main television channels which will

each have an 1800-channel capacity. Originating from Dublin, the system will provide high-quality television broadcasting to Ireland's most populated areas which include Cork and the south coast, Galway and the west coast, Donegal, Athlone and Dundalk.


The 3.5m dollar contract to provide and install microwave equipment was awarded to GTE Telecomunicazioni S.p.A., Milan, GTE International's Italian subsidiary, by Ireland's Department of Post and Telegraphs. The system is expected to become operational in early 1977.

Tributes to Arthur C. Clarke

Arthur C. Clarke may not have received the first L. M. Ericsson prize for his significant contribution to telecommunications (see "Who thought up the synchronous satellite?", April issue, p.68) but he did get an appropriate material tribute for his work from the Indian Space Research Organisation. A party of their engineers arrived at his home in Colombo, Sri Lanka, one day and fitted up a complete installation for receiving the Indian television programmes now being broadcast from the ATS-6 satellite (March issue, p.68). The 15ft antenna, mounted on a balcony, is shown in the picture. The 22-inch monochrome set was made in India.

Also, Dr Harold Rosen of Hughes Aircraft, on receiving the Ericsson prize

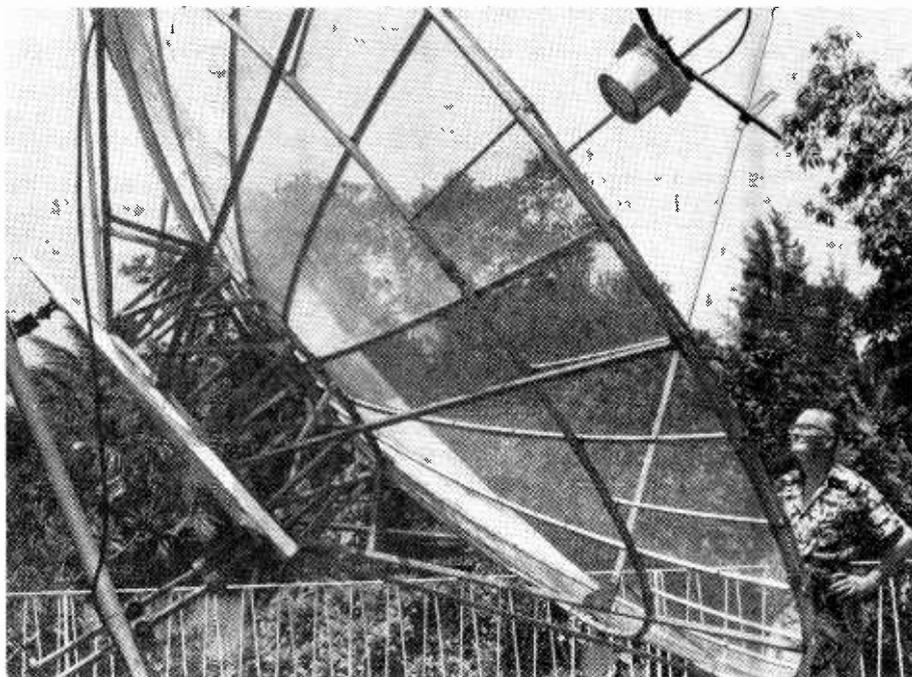Arthur C. Clarke and the 15ft paraboloid of the ATS-6 television satellite receiving station presented to him by the Indian Space Research Organization. The feed unit contains an 860MHz three-stage low-noise pre-amplifier (see news item).



in Stockholm in May, made a graceful reference to Arthur Clarke in an address on the history of geo-stationary communications satellites. Earlier this year Mr Clarke was awarded an Honorary Fellowship of the American Institution of Aeronautics and Astronautics in New York. In fact he made history by being promoted from Member to Fellow and then to Honorary Fellow all in the same year.

Radio relay above 13GHz

A radio relay system has been developed to operate in the frequency range above 13GHz and to transmit information by means of digital phase modulation. Modern radio relay systems using frequencies up to 13GHz fulfil their functions in analogue long-range communication networks. Nevertheless, factors such as the increasing digitization of communications traffic, future transmission capacity requirements and economic considerations have made the new relay system necessary.

The PSK 120-240/15000, developed by Siemens, operates with differential four-phase shift keying of the carrier, information being contained in the phase shifts at 0°, 90°, 180° and 270°. This type of modulation permits a good compromise between immunity to interference, bandwidth requirements and technical complexity. On the basis of rainfall figures for Germany, radio path lengths of 22 to 28km were found advisable, so that the system is suitable for dense radio relay networks whose nodes have several links radiating from them and which have relatively short transmission paths of between 25 and 50km. Such network structures and corresponding transmission capacities can be found for instance at the short-haul level of the Federal German communication networks. This is where the PSK radio relay system (see photo) will probably be used first when it becomes necessary to transmit large numbers of digital signals such as p.c.m. speech bands or coded videotelephone signals.

Open University's telecommunication course

An understanding of technical advances and their practical application for the present and future, form the basis of a one-year course 'Telecommunication Systems' being offered by the Open University. With over 55,000 students spread throughout the UK,



Clean room at Mullard Hazel Grove, a Philips Industries semiconductor components factory. Instead of having large open areas serviced with cleaned and filtered air, the working stations are fitted into modules that can be put together to form an open-ended tunnel.

improved communication systems have a special interest for the University. A part of the course which is therefore of particular interest is a case study of the use of tutorials by telephone and an examination of current developments in the transmission of graphical information over telephone lines with visual displays at remote terminals.

The course which is part of the University's 'Post-experience' programme for 1977, deals mainly with the way in which various elements of telecommunication systems are selected and combined, the functions they serve, the way they interact and the effects which inherent imperfections have on the overall system performance. Application and further information on the course can be obtained from the Post-experience Student Office, the Open University, PO Box 76, Milton Keynes, MK7 6AA.

TV deliveries down

Deliveries to UK distributors of UK made and imported colour television receivers reached 109,000 in March, a fall of 22 per cent on March 1975 (139,000), according to the latest statistics compiled by the British Radio Equipment Manufacturers' Association. This brought the total for the year to 309,000, a fall of 35 per cent compared with the same period in 1975 (475,000). Total monochrome TV deliveries for March were 96,000, an increase of 55 per cent compared with March 1975

(62,000), bringing the year's total to 244,000 compared with 212,000 last year. These figures include deliveries to rental and relay companies.

IBA's 300th transmitter opened

The opening of a local television relay station at Beacroft Hill near Leeds, which came into full service on April 30, 1976, brings the number of IBA television and radio transmitting stations to 300. Of these, 200 have been opened in the four years since April 28, 1972, when a television relay at Brighton, Sussex, brought the IBA's total to 100. There are now 213 u.h.f. 625-line television transmitting stations, including 46 high-power 'main' stations, serving just over 96 per cent of the population of England, Scotland, Wales and Northern Ireland; 39 v.h.f. and medium-wave sound transmitting stations for the 19 independent local radio companies; and 47 v.h.f. television transmitting stations which continue to provide television services for viewers with older 405-line receivers or who are not yet in range of the u.h.f. services.

The introduction by the IBA of unattended transmitters at all power ratings has meant that the 300 existing transmitting installations are operated and maintained by approximately the same number of field engineering staff as were needed before 1969 for the original ITV v.h.f. television network of under 50 transmitting stations.

World of Amateur Radio

More u.h.f. repeaters

During April the Home Office licensed 20 u.h.f. "talk through" repeaters in England, Scotland and Wales and within a week or two the installations at Corby, Manchester, North Wales and some near London were operating. The introduction of these repeaters between 433 and 435 MHz has, however, caused some consternation in amateur television circles and it is to be hoped that arrangements will be worked out to enable both services to operate without mutual interference. Many other amateurs are perturbed at the deliberate interference to and abuse of the 144 MHz repeaters (particularly the GB3LO repeater in London) and the whole subject of repeaters is still creating a highly charged atmosphere.

Some 40 u.h.f. repeaters are planned, conforming to a 33km square grid covering the UK. There are now some 2,000 amateur repeaters in the United States and the FCC has recently authorised repeaters in the 28 MHz band, between 29.5 and 29.7 MHz with a suggested 100 kHz separation of input and output frequencies.

Experimental retransmission of 625-line amateur television vision and sound signals through a u.h.f. repeater has been reported from Adelaide, South Australia, with 441 MHz input and 579 MHz output. Pictures from the 1.5W repeater transmitter can be received on standard u.h.f. domestic TV sets.

Interference suppression

Both amateurs and broadcast listeners have learned how difficult it can be to cope with two intractable sources of electrical interference: car ignition systems and domestic TV.

A team at Stanford Research Institute have come up with a suggestion that could do much to reduce ignition problems: a modified form of sparking plug that by increasing capacitance between the centre electrode and the resistive lead to about 10 pF provides, in effect, a built-in low-bass filter. In *IEEE Transactions on Vehicular Technology* (February 1976) the team — R. A. Shepherd, J. C. Gaddie and D. L. Nielson

— report that such plugs, if a manufacturer would produce them, could result in 13 to 20 dB additional suppression, compared with conventional techniques, over the range 30 to 500 MHz. Earlier research by the same team drew attention to the wide variation in ignition noise radiated by different vehicles and even between different firings of the plugs. Some "super-noisy" vehicles were found to radiate 40 dB more interference than others.

Interference radiated by television sets (sometimes called reverse-tvi or "ivt") seems to have risen with the increasing use of switched-mode power supplies and greater deflection power in colour receivers, often ruining broadcast reception below about 800 kHz and producing whiskery signals at line-frequency separation throughout the h.f. spectrum. While various "braid-breaker" high-pass filters in the aerial leads of the TV sets can sometimes reduce radiation from individual sets, urban areas appear to be increasingly heavily polluted during popular TV viewing hours.

ARRL and Citizens' Band

Although one still finds among American amateurs a deep dislike of many aspects of the CB scene, a notable attempt to heal the breach has been made by Richard Baldwin, W1RU, general manager of ARRL and secretary of IARU. He admits, in a QST editorial, the widespread interference caused by CB to television but also pays tribute to "some fine public work" by CB operators. He believes that the big expansion has now brought into existence "a new breed of CBers interested in CB because it is a way of talking to someone — not because it is radio — to relieve the boredom of long trips and to keep posted on traffic conditions". No longer, he suggests, is the bulk of CB operation from frustrated would-be radio amateurs who wanted to be on the air because of a hobby interest in radio but who did not want to learn the Morse code or pass examinations. He feels, however, that there are still some CB enthusiasts who become interested in radio communication as radio and who should be encouraged.

This distinction between amateur radio and CB communication is something not always appreciated in the UK. The Council of the RSGB has stated that the Society will give no support to a 27 MHz communications band, partly because the press does not differentiate between licensed radio amateurs and the 27 MHz users.

In the United States CB has reached the stage where the radio stores carry large stocks of mobile and hand-held 27 MHz transceivers and the bookshops carry more CB publications (including dictionaries of CB slang) than books on amateur radio. It has become very big business but clearly both CB and amateurs would gain from keeping the

two types of activities entirely distinct. FCC are to attempt to move very low power CB hand-held operation to frequencies around 50 MHz.

In brief

One little known fact about that supreme recluse — the late Howard Hughes: at one time he held the amateur callsign W5CY . . . The revival of an RSGB Radio Communications Exhibition this year in the London area has already been promised considerable trade support: it is to be held at Alexandra Palace from 10 a.m. to 8 p.m. on July 30 and 31, and 10 a.m. to 4 p.m. on August 1 . . . For the first time in its 63-year history, the membership of RSGB has exceeded 20,000 . . . The 1976 convention of the British Amateur Television Club will be held on Saturday, September 18, at Parkinson Court, Leeds University . . . ARRL are appealing for 100,000 new US amateurs by 1979, now that those who graduate from training courses held by affiliated clubs and societies will be able to obtain licences without the usual issuing delays . . . Combined operational life of the Oscar 6 and Oscar 7 satellites now exceeds five years with Oscar 6 clocking up 3½ years in service in April and Oscar 7 1½ years in May . . . Total of UK amateur licences had reached 22,789 (class A 15,819; class B 5,843; class F (mobile only), 21; and television, 306) by the beginning of March . . . Novice and Technician licences first came into force in the United States 25 years ago on July 1, 1951. A current proposal for novice licences in Canada would provide c.w. only between 3700 to 3725, 7100 to 7150, 21,100 to 21,200, 28,100 to 28,200 kHz with 150-watts input. Licences would be issued for two years only and require 5 w.p.m. morse, knowledge of regulations, adjustment, operation and care of radio apparatus; tests would be administered by Advanced Class amateurs not related to the applicant. . . A German international "hamfest" is being held this year in a new location at Friedrichshafen on Lake Constance between June 25 and 27 (details DARC, PO Box 1155, D-3507, Baunatal, Federal Republic of Germany) . . . The "National Wireless Museum" has opened, under the auspices of the Wireless Preservation Society at Arreton Manor, near Newport, Isle of Wight, with early radio and television receivers, crystal sets, early loudspeakers, etc (10 a.m. to 6 p.m. on weekdays, Sunday afternoons) . . . In the USA a new electronic-communications museum at East Bloomfield, New York, contains over 25,000 pieces of equipment, including 7,000 valves (with an original 1905 Fleming diode given by The Marconi Company) and including a number of replicas of early amateur stations (including a 1923 station, W2AN, which operates on 1.8 MHz); early ship and coast stations are also reproduced. It is run by the Antique Wireless Association.

PAT HAWKER, G3VAV

Analogue to digital meter

Circuit using I.e.ds or 1 1/2-digit display

by G. Kalanit, B.Sc., M.I.E.E.

Rediffusion Engineering Ltd

In level measurements such as signal strength in communication, an accuracy of about $\pm 10\%$ and a resolution of about 5% may be sufficient. For such a requirement an I.e.d. array may replace a conventional meter. The level is displayed as a moving bright dot, calibrated with an appropriate scale. The advantage of such a circuit is its clarity and its instantaneous display of varying levels. Mechanically it is robust. Its main characteristics are a resolution of half a digit, and a minimal consumption of supply power. The current drain is almost constant and used mostly (about 80%) to illuminate the array I.e.ds. For applications where a digital display or level warning is also required, an output from the meter is described.

Initially when the d.c. input level is low, Fig 1(a), transistors Tr_1 , Tr_2 and Tr_3 are cut off and transistors Tr_{01} , Tr_{02} and Tr_{03} are in a saturated state. Hence the I.e.d. for 0 is illuminated. Because of the

voltage drop across Tr_{01} base-emitter junction, there is not enough voltage drop across I.e.d. 1, and therefore it is not switched on. By the same reasoning I.e.d. 2 is also off. When the input direct voltage is raised sufficiently to switch transistor Tr_1 on, Fig. 1(b), transistor Tr_{01} cuts off and I.e.d. 0 is switched off. This results in I.e.d. 1 being on. With a further increase of input voltage, Fig. 1(c), transistor Tr_2 comes into saturation and cuts off transistor Tr_{02} and I.e.d. 1. This results in I.e.d. 2 being switched on. Hence, in the final state transistors Tr_1 , Tr_2 and Tr_6 are switched on, and only I.e.d. 2 is illuminated. The circuit may be described as a column of transistor pairs.

The switching from one I.e.d. to another is not a snap action, and illumination from 0 to 1 to 2 is continuous. This means that halfway between 0 and 1, both I.e.d. 0 and I.e.d. 1 are lit together. Similarly halfway

between 1 and 2, I.e.d. 1 and 2 are lit together. Because of the constant-current feed, the level of the illumination is halved for each I.e.d; however, the total level remains constant and the visual effect is to give a resolution of half a digit.

A complete meter circuit is given in Fig. 2 for an eleven-I.e.d. array. A constant-current source of 20mA gives a fairly bright display. Fig. 3 gives a calibration curve of the circuit in Fig. 2. The curve slope is the meter sensitivity which may be defined as the increase in input voltage required to change one digit, i.e. $i \times R_n + V_{ce(sat)}(Tr_n)$, where i is the constant current through R_n , and $V_{ce(sat)}(Tr_n)$ is the saturation voltage drop across transistor Tr_n . In the circuit, Fig. 2, for n values 1 to 10, sensitivity is

$$20\text{mA} \times 15\Omega + 0.15\text{V} = 0.45\text{V}$$

The fact that the sensitivity of each

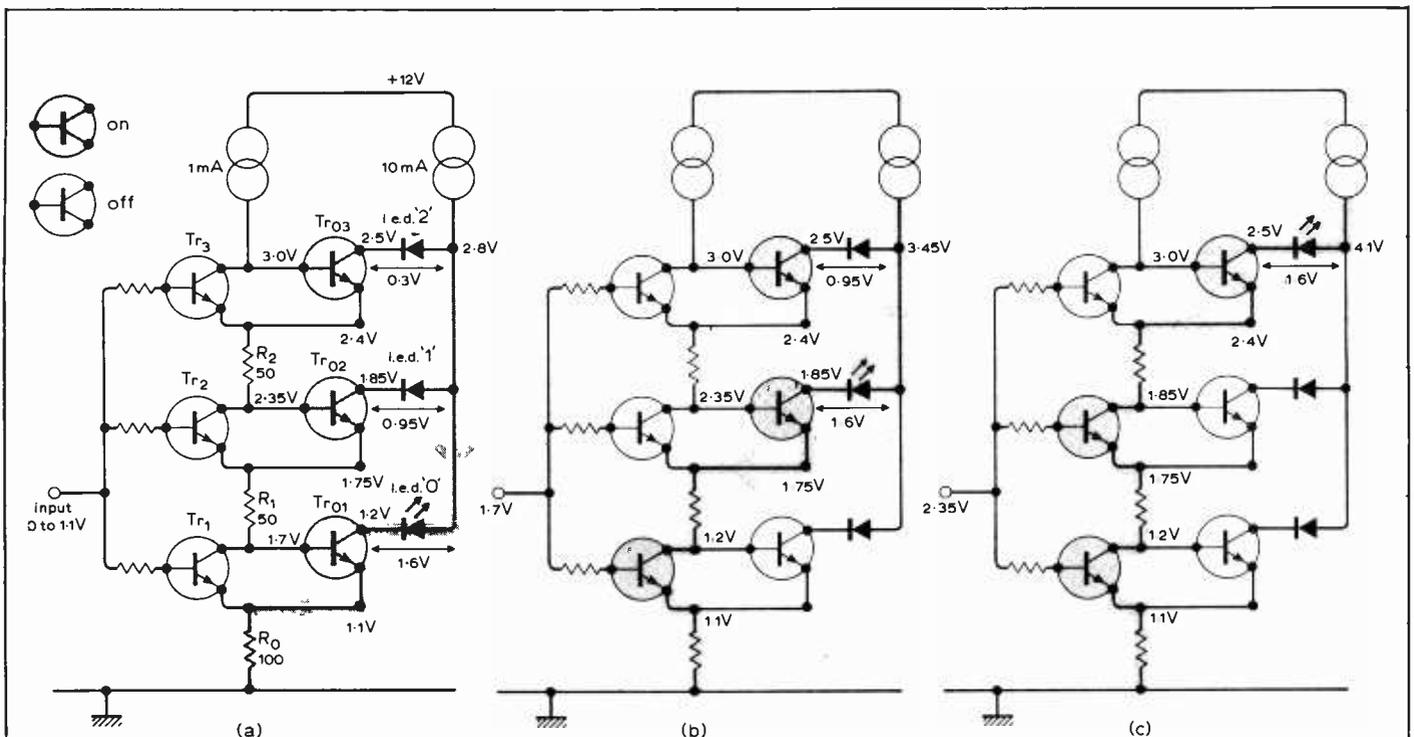


Fig. 1 Circuit for an I.e.d. array display for use as an output level meter, e.g. signal strength meter, showing how the I.e.ds switch on in sequence as the input voltage is increased. Voltage conditions assume V_{be} of 0.6V and V_{ce} of 0.1V.

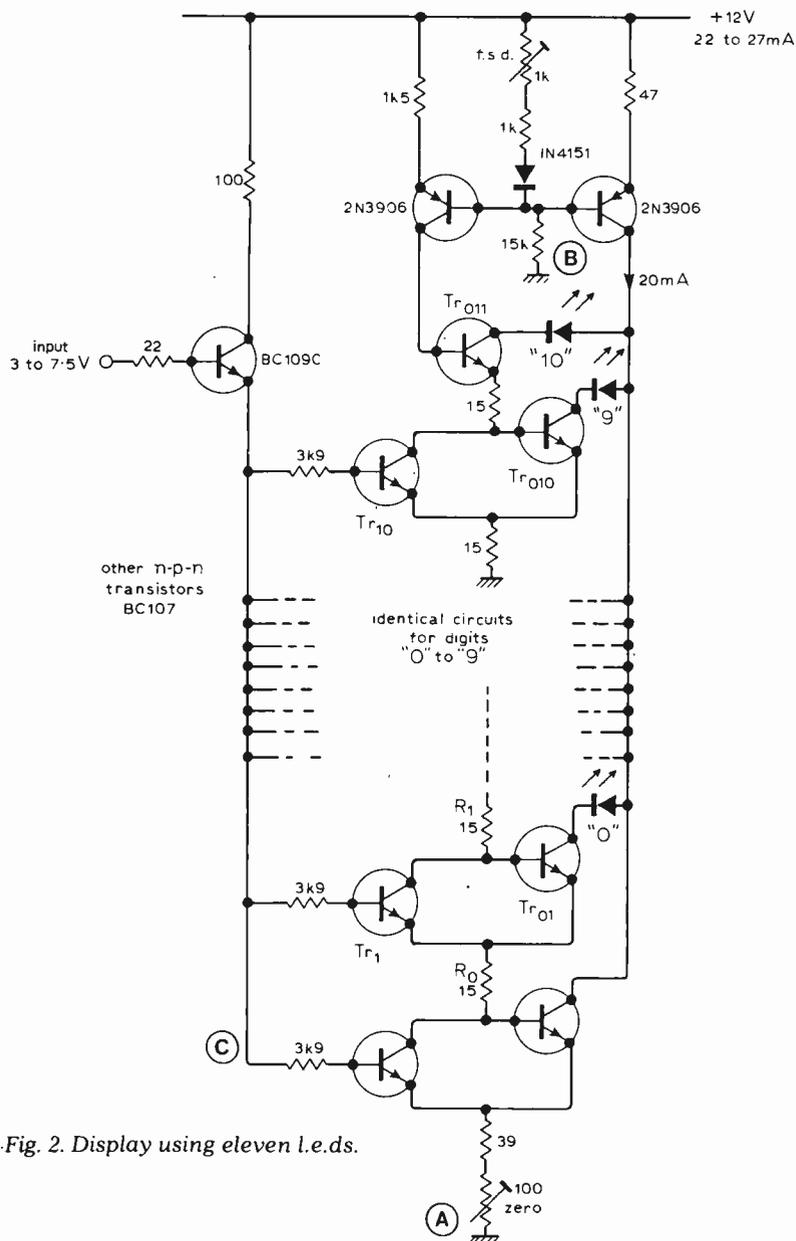


Fig. 2. Display using eleven l.e.ds.

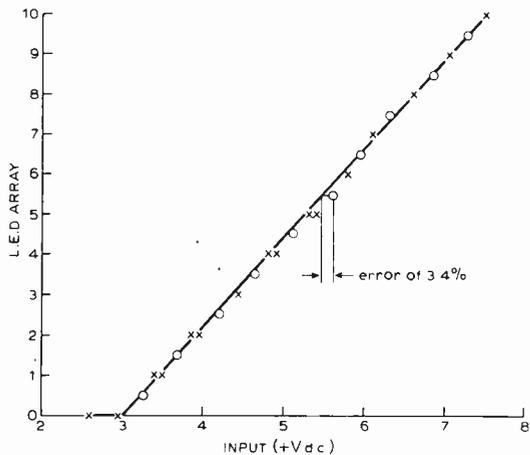


Fig. 3. Calibration curve for the display in Fig. 2 showing the input voltages required to light l.e.ds numbers 0 to 10. Points X represent a single l.e.d. when lit, points O represent two adjacent l.e.ds when equally bright; e.g. at an input of 5.6V both l.e.ds 5 and 6 are equally on and the error is about 0.12V. Full scale is 3.5V d.c. therefore error at full scale is $0.12 \times 100/3.5 = 3.4\%$

digit can be controlled with the value of the corresponding resistor, means that the meter may be easily employed in non-linear requirements. It was adapted to a newly developed r.f. calibrated level receiver. Response of the receiver detector output was plotted against a decibel varied input, shown in Fig. 4. The slope of Fig. 2 circuit was then adjusted with a new set of R_0 to R_{10} resistors, values of which are given in the table (see Fig. 4). Fig. 5 shows the total response of the receiver input r.f. level against the l.e.d. meter display. Hence the meter reads decibels with a resolution of $\frac{1}{2}$ dB. The l.e.d. display array is shown in Fig. 6. Adjacent to the 10dB scale are the voltage level scales.

Each display l.e.d. requires two n-p-n transistors. The circuit of Fig. 2 requires a total of 24 n-p-n transistors. Arrays of n-p-n transistors are the obvious solution for a reduction in number and cost of active elements in the circuit. RCA type CA3086 is a suitable example, containing 5 n-p-n transistors. Because one of the transistors in the array has to be wired to the earth rail, only four out

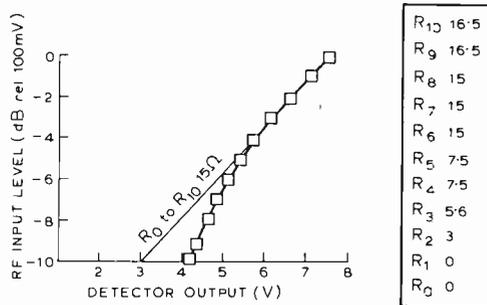


Fig. 4. Graph showing how the selection of the resistors R_0 to R_{10} allows the circuit in Fig. 2 to be used for a non-linear application; in this case an r.f. calibrated receiver.

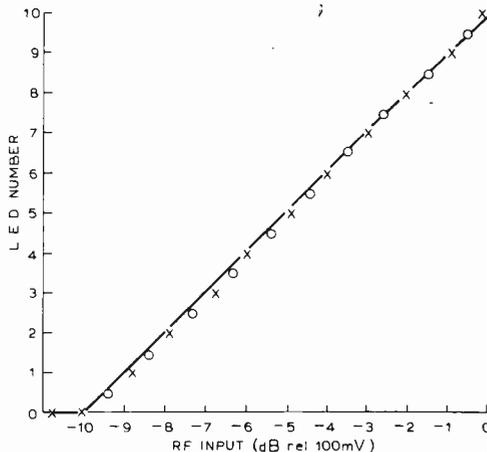


Fig. 5. Graph showing the response of the receiver input r.f. level against the l.e.d. display when using the parameters described in Fig. 4.

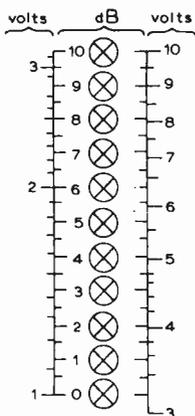


Fig. 6. Typical display array for l.e.ds showing 0 to 10dB and equivalent voltage levels.

Fig. 7. Modifications to Fig. 2 to provide digital outputs. $D_n = 0$ when l.e.d. "n" is on.


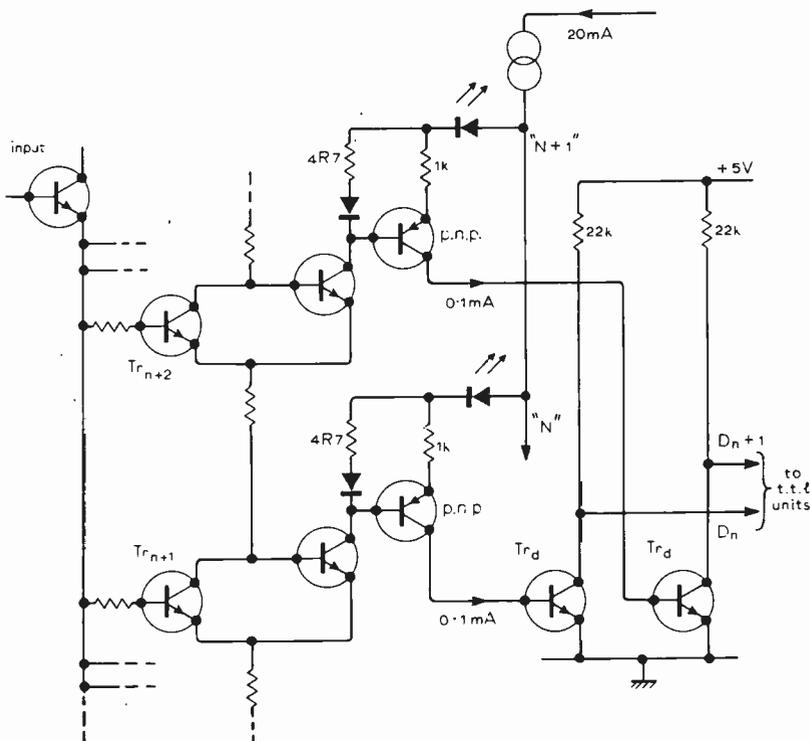


Fig. 8. Typical modification to Fig. 2 providing digital outputs arranged to drive a digital display of 1½ digits.

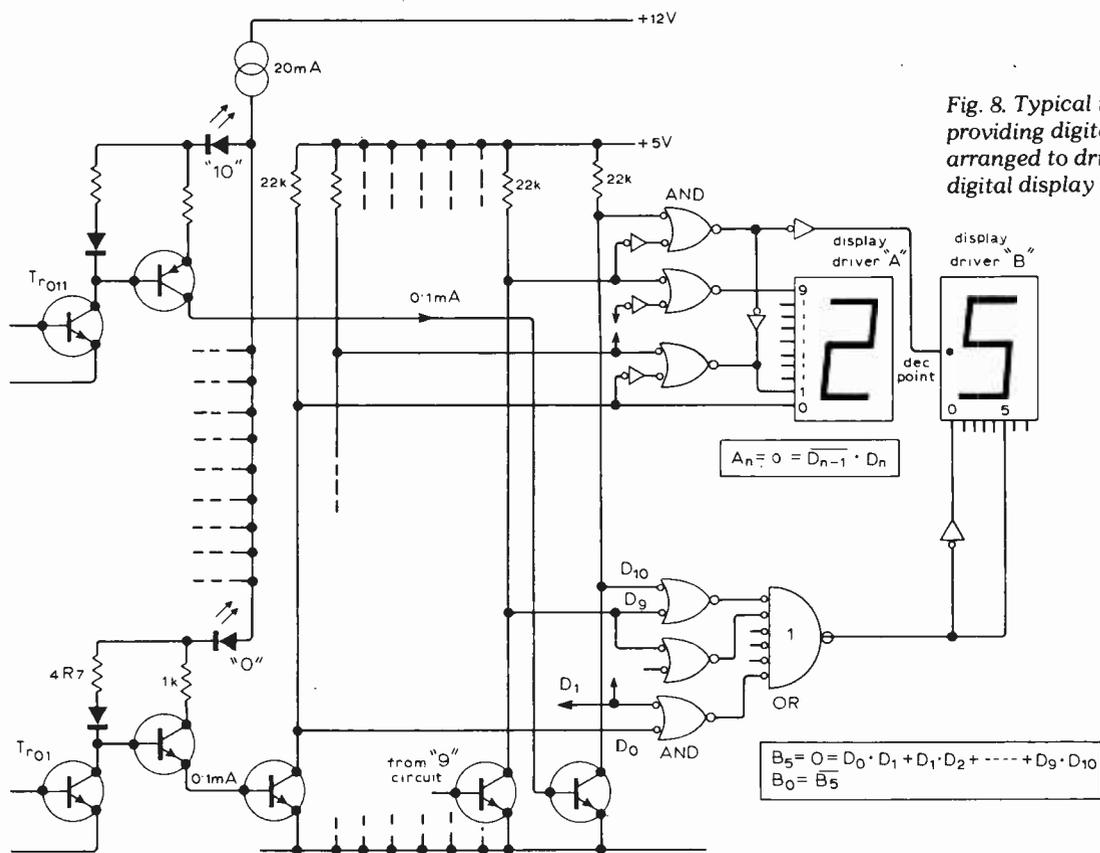

of the five transistors can be used. Hence, six units of CA3086 must be employed, making a worthwhile reduction in number and cost.

The meter can be arranged to have digital outlets for systems which require level limits warnings. The basic circuit is given in Fig. 7. The 4.7-ohm resistor in series with the diode, together, sense the l.e.d. current, and develop a voltage which switches on the p-n-p transistor.

The 1k Ω resistor in series with the p-n-p transistor emitter limits the transistor current to 0.1mA, and therefore does not load the 20mA current source and disturb the l.e.d. chain switching action which depends on constant current, i.e. only 0.5% (0.1mA/20mA) of the constant current is drained away by the p-n-p transistor. In the circuit, the p-n-p collector current switches on a t.t.l. drive transistor (T_{r_d}).

Fig. 8 demonstrates the use of the outlets to drive a display of 1½ digits. A drive transistor is on when the corresponding l.e.d. number n is on, hence output $D_n = 0$ for l.e.ds being on. As the digit display units may also require a zero voltage to drive them on, it is convenient to use negative logic for the Boolean expressions of logic requirements, as follows: The 0.5 digit B is on only when two adjacent l.e.ds are on

together, otherwise 0.0 is displayed. Hence for zero input into B_5

$$B_5 = 0 = D_1 + D_1 \cdot D_2 + \dots + D_9 \cdot D_{10}$$

also $B_0 = \bar{B}_5$. For the A digit, the requirement is that, number A_n is on only when $A_{(n-1)}$ is switched off. Hence $A_n = 0 = \bar{D}_{(n-1)} \cdot D_n$. For the 10 display, A_{10} is fed via a buffer to A_1 input i.e. digits 1 and 0 are on, and the decimal point is switched off.

Automatic brightness control

The light emitting diodes, in the meter example of Fig. 2, are driven with a constant current of 20mA to give a bright display suitable for outdoor use. Indoors, however, it would be desirable, to reduce the i.e.ds' current consumption to improve their life span. Also, the power of the battery source, in the case of portable equipment, may be saved.

Truth table (negative logic)

input	L.E.D. 'D'					input driver A				decimal point	input driver B		display
	0	1	2	9	10	A_0	A_1	A_2	A_9		B_0	B_5	
<0	1	1	1	1	1	1	1	1	1	0	0	1	.0
0.0	0	1	1	1	1	0	1	1	1	0	0	1	0.0
0.5	0	0	1	1	1	0	1	1	1	0	1	0	0.5
1.0	1	0	1	1	1	1	0	1	1	0	0	1	1.0
1.5	1	0	0	1	1	1	0	1	1	0	1	0	1.5
2.0	1	1	0	1	1	1	1	0	1	0	0	1	2.0
9.0	1	1	1	0	1	1	1	1	0	0	0	1	9.0
9.5	1	1	1	0	0	1	1	1	0	0	1	0	9.5
10.0	1	1	1	1	0	1	0	1	1	1	0	1	10

The earth rail of the meter circuit (Fig. 2) is lifted and re-connected to earth via a saturated transistor Tr_6 (Figs. 9 & 10) which acts as an on/off switch. Transistor Tr_6 is switched on/off by astable multivibrator $Tr_3, Tr_4,$

at a rate of 66Hz to 630Hz. The on time is fixed to 1.5ms duration (see waveforms in Fig. 9). The off time is variable and is inversely in proportion to ambient light. Thus, we have a pulse-width-modulated multivibrator controlled by ambient

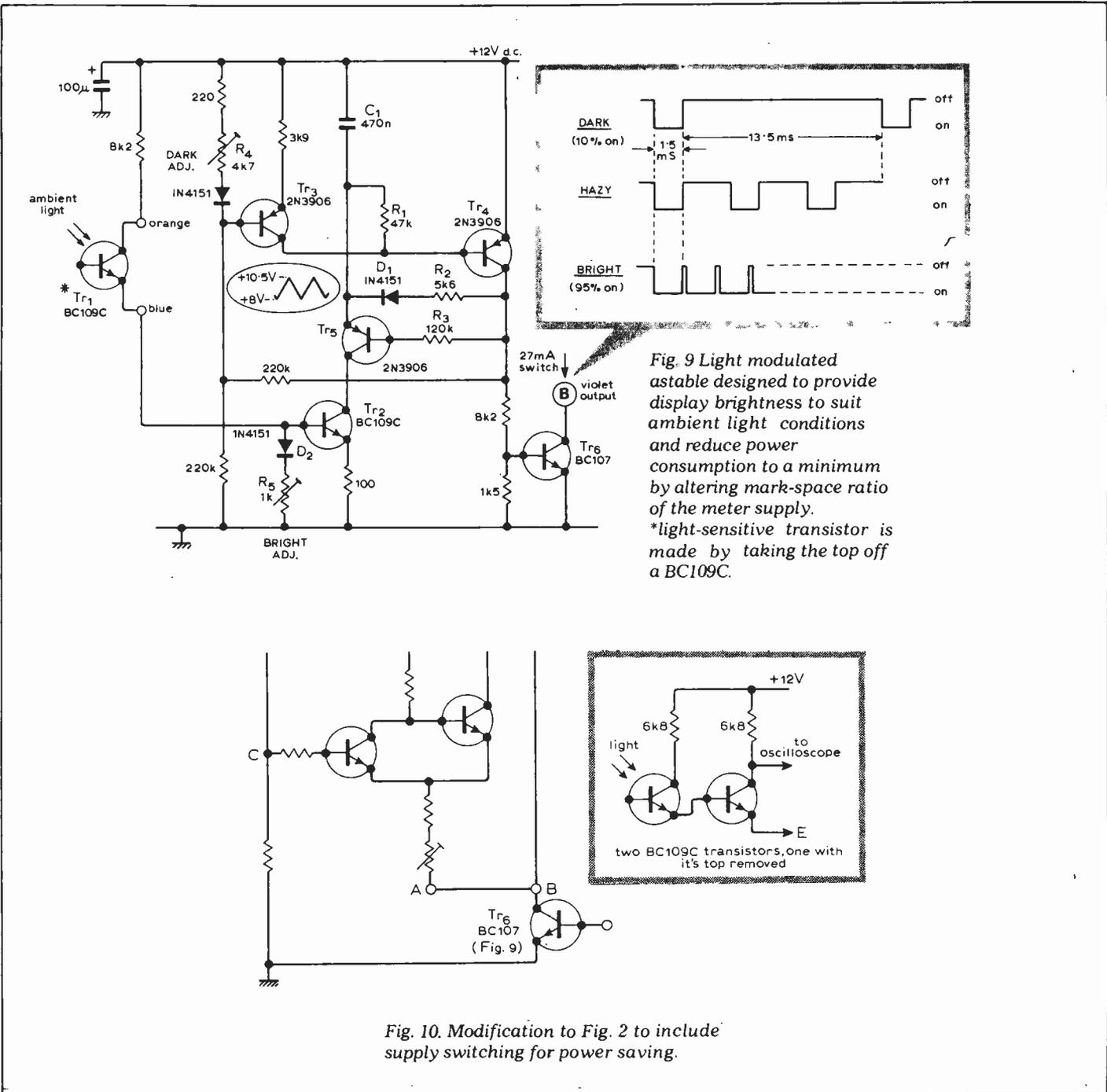


Fig. 10. Modification to Fig. 2 to include supply switching for power saving.

light with a variable mark to space ratio from about 5% to 98%. In practice it was found that a ratio range of 10% to 95% was adequate.

Transistors Tr_3 , Tr_4 are connected d.c. wise as a Schmitt trigger with input at junction C_1 , R_1 . The off/on switching voltages at C_1 , R_1 are approximately +8V and +10.5V. The timing of the sawtooth which occurs at C_1 , R_1 is controlled by C_1 and the independent mark and space charging and discharging circuits. The mark time is determined by the discharge resistor R_2 only, and lasts 1.5ms. The space time is controlled by the charging current through Tr_3 and Tr_2 . The current amplitude depends on the ambient light affecting the light sensitive transistor Tr_1 . The brighter the light, the larger the charging current and the shorter is the space time. The space 'dark' charging current is determined by R_3 to be 13.5ms (Tr_2 is cut off).

During the mark time, when Tr_4 is on, D_1 is on and Tr_5 is off. During the space time, when Tr_4 is off, D_1 is off and Tr_5 is on, giving complete independence of mark and space time control. Potentiometer R_4 controls the direct voltages at which the on/off occur; this it controls the 'dark' mark-to-space ratio. Potentiometer R_5 controls the d.c. gain of transistor Tr_2 ; thus it controls the 'bright' mark-to-space ratio.

The astable current consumption is 0.4mA indoors at 10% duty cycle and 2mA outdoors at 95% duty cycle. The total meter circuit consumes only 2.6 to 3.3mA indoors at 10% duty cycle, and 23 to 27mA outdoors at 95% duty cycle.

The lowest frequency of the astable was chosen to be 66Hz to avoid flicker effect. The cycle length is 15ms, therefore the maximum mark time of 10% duty cycle is 1.5ms.

To see how well the l.e.d.s follow the input waveform, a photosensitive probe (see inset in Fig. 10) was placed in front of an illuminated l.e.d. in the meter array. The waveform was then displayed on a double-beam 'scope together with Tr_6 collector waveform. The waveform from the probe was delayed by about 0.1ms with a rise and fall time of about 0.1ms.

Acknowledgment. The astable circuit was suggested by Messrs. H. L. Baker and J. W. Sinclair of Rediffusion Engineering Ltd., who used an op-amp type LM3900. The above design follows the basic circuitry of the LM3900 but consumes less current. A similar circuit employing an op-amp is also shown by A. Cantori in *Electronics Letters* vol. 9 1973 no. 7, p.158.

FM tuner designs

Further details of construction and alignment

by D. C. Read, B.Sc.

As the result of experience gained in building what might be termed production models of the f.m. tuners described recently in *Wireless World* (March and April), the following information on construction and alignment is given, together with suggestions for possible modifications and component alternatives, and some corrections to details already published.

As a board layout was arranged to take specific capacitor types, further details are:

C_1, C_6, C_{15} - polystyrene 2 per cent types were used originally but disc ceramic capacitors are also suitable;

C_{20}, C_{21a}, C_{21b} - polystyrene;

C_{24}, C_{25}, C_{26} - polystyrene (these low-pass filter components need to be as accurate in value as possible);

C_4, C_{32}, C_{33} - 10 per cent polyester, e.g. Mullard type 334.

On the p.c. board supplied for the tuner there are two positions marked for each of C_{32} and C_{33} . This provides for additional components to be installed so that the theoretical 75 μ s de-emphasis time-constant can be obtained very accurately if necessary. Unless otherwise specified, the remaining capacitors are either disc ceramic or tantalum types, the last-mentioned being marked with polarity on the circuit diagrams.

Push-button assemblies

Push-button switch assemblies may be used, but remember that as these are generally equipped with high-value adjustment resistors (100k Ω per section), the reservoir capacitors, C_{42} to C_{48} in Fig. 1, would not then be suitable because tantalum capacitors are subject to considerable variation of leakage current with change in temperature. They are unsuitable for use in a high-resistance circuit within an a.f.c. loop; given a modest change in temperature, the resulting frequency bias created by the consequent change in the tantalum characteristics could so offset the a.f.c. system as to prevent it giving satisfactory overall control.

As a compromise, disc ceramic capacitors of, say, 220nF could be used in these positions to provide a small but useful reservoir effect. Note, however, that without the decoupling action of

the 22 μ F components, the tuning-voltage feed to the LP1186 module is more liable to pick up hum and noise interference and hence allow spurious modulation of the received signal. Thus, if a push-button unit remote from the tuner is installed, it is good practice to screen this feed and/or ensure that it is kept well away from possible sources of interference, e.g. mains wiring. When loaded with the high-resistance selection circuit, the tuning voltage regulator diode, D_4 , may be fed with much more current than is needed to carry out its control function. In this event, R_{44} could be increased, say to 100 Ω .

AFC circuit

In Fig. 5 (April issue) a 3.3 μ F capacitor was specified for C_6 in the a.f.c. line from pin 7 of the CA3089E demodulator. This is an unnecessarily large value because the feed only carries an appreciable audio component under off-tune conditions. A smaller, and hence cheaper, component, say a 470nF disc ceramic or polyester capacitor, would suffice.

Too large an a.f.c. range can be a disadvantage because of station-jumping. If four diodes, arranged as two series pairs connected back-to-back in parallel, are placed across points 1 and 2 in the a.f.c. circuit, the positive and negative voltage excursions are limited each to about 1.2 volts so that the maximum possible tuning frequency change under a.f.c. action is always less than the minimum channel separation.

The other modification concerns extension of the a.f.c. sensitivity control as a front panel facility. This can be done by making R_9 a variable component, still connected between points 1 and 2, but with R_8 taken to the slider. Such an arrangement then enables reduction in sensitivity to be carried out manually whenever necessary but does not prevent the voltage changes appearing across R_9 from being used to operate the l.e.d. indicator circuit detailed in Fig. 4 of the March issue.

Muting circuit

In at least one of the advanced tuners so far built and aligned, the CA3089E muting output from pin 12 took the form of amplitude-clipped noise instead

Filter type	3dB bandwidth	$\pm 300\text{kHz}$ rejection	stopband loss
Vernitron FM4	235kHz	30dB	40dB
Toko CFSA	300kHz	20dB	30dB

of varying d.c. The interconnecting circuit feeding the muting input on pin 5 then produced an average of this output which was not sufficient to operate the mute when required. As the i.c. gave a satisfactory performance in all other respects, it was worthwhile making a suitable circuit change to correct for the abnormality. The circuit published in the April issue was therefore modified to give an increased output by disconnecting the existing circuit between pins 12 and 5 and connecting a 1N914 and 50k Ω potentiometer in series between pins 12 and 5 (anode to pin 12). Connect C₂₁ between pin 5 and the zero-volt line.

Aerial coil

The aerial coil, L₁, used to feed incoming signal to the tuned r.f. stage in the advanced version is constructed as shown below. Note that the total number of turns on this coil is 7, not 8 $\frac{1}{4}$ as stated on page 50 of the April issue.


Cut Neosid 6mm former to about 14mm.

Wind on 7 turns 22 s.w.g. tinned copper wire, equally spaced out to 11mm.

Remove former, tap at 1 $\frac{1}{4}$ turn from start, open turns adjacent to tap to avoid shorting.

Re-insert former and centralise. Screw in core together with p.t.f.e. tape. Coat with Denfix or nail varnish.

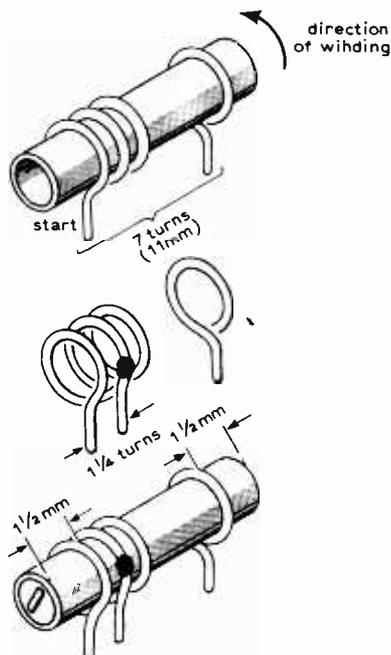In some examples of the advanced version, C₁ may not be required because stray capacitance and the input capacitance of Tr₁ added together are sufficient.



Ceramic filters

Difficulty has recently been found in obtaining the Vernitron filters specified for F₁ and F₂ in both versions. Fortunately, ceramic filters from the Toko type CFSA 10.7 range are readily available. These replacement components offer a performance which is not quite as good as that of the Vernitron FM4, but it is generally adequate for the tuners described. The Toko units are also cheaper — about half the cost.

If these alternative filters are used, a small change in Fig. 1 circuit values would be required because the amount of overall phase response correction given by C₂₈ and R₂₇ in the Tr₂/Tr₃ amplifier is no longer suitable. The values should be changed to 3.3nF and 2.4k Ω . Resistor R₂₇ can be adjusted on test to obtain up to 38dB channel separation from 1 to 5kHz.

Adjustment of L₃

The quadrature-phase signal derived for both demodulators, TAA661B in the simple version and CA3089E in the advanced version, could optionally be produced by means of a double-tuned coil at L₃. When setting the two cores of L₃ so as to take the best possible advantage of the linearizing effect of current in the dummy coil, it is essential that the cores be kept as far apart as possible in the former, thus minimising changes in coupling between the coils when adjustment is made. The lower core is used to tune the mail L₃ coil; it should initially be screwed in just enough to give as symmetrical an S-curve as possible. When this has been set satisfactorily, the upper core is added and screwed in enough to straighten the bend in the transfer slope as in the left hand trace of Fig. 2. More precise adjustment would require the use of a wave analyser or distortion meter.

Corrections

In Fig. 1 of the March article, R₂ should be 1k not 100k Ω and R₆₅ should be 10k, not 12k Ω . The switch shown in broken line at pin 14 of IC₃ is an optional component which operates as a cancel-stereo shorting contact when closed. Note also that the common-circuit line mainly joining Tr₂, Tr₃ and IC₃ should be labelled '0V' — it is not a continuation of the +4.5V line in the tuning selector circuit. In Fig. 5 of the April article R₃₇ should be 47 Ω not 470 Ω . In the p.c. board/layout diagram, R₁₈ (top, centre) should be shown as R₁₃ and the unmarked component immediately to the left of R₄₃ (centre, toward r.h.s.) should be marked D₄.

Receiving weak TV signals

by W. H. Jarvis,

Rannoch School, Perthshire

With the aid of a grant from the Royal Society, we have been studying for years various approaches to the problem of weak TV reception in a remote, mountainous area of Scotland.

Some years ago, two licensed amateurs (one pupil and one teacher) set up a 10W f.m. transmitter operating on 145MHz at a local beauty spot known as Queen's View, and showed that it gave good signal levels to about 800 potential listeners or viewers who at present have little or no signal.

In tackling the problem of using the existing very weak signals, we have until recently been without a calibrated signal strength meter, so we modified a 12V portable dual-standard TV receiver to give a meter indication of relative strengths (*Physics Education*, vol. 16 No 2, p86). We bought a 44-element J-Beam for channels 10 and 11, and, whilst we failed to get an "enjoyable" IBA signal from either Kirk O'Shotts or Angus (Dundee), we did get consistent enough results to show that in highly wooded areas, the average signal falls in spring when foliage begins to appear, and rises in autumn when the leaves fall. In a separate experiment on amateur v.h.f. bands, we showed that horizontally polarised signals travel better through woods than do vertically polarised signals, and we attribute this to a greater average conductivity in the vertical direction when one is surrounded by damp trees.

Intermittent work on trying to improve reception for local residents led to the installation of 3-channel colour through a piped system using 7 in-line amplifiers; unfortunately only one householder benefited, and no-one connected with the school could be served.

In establishing a v.h.f. TV relay at the school (*School Science Review*, Sep '71), we found that even high-grade low-loss coax deteriorates rapidly as damp diffuses through the coating and dielectric.

We are now experimenting with a Signetics NE561 p.l.l. i.c., hoping to find a demodulating circuit which will give a higher signal-to-noise ratio with existing signals (about 15 μ V).

In addition to thanking the Royal Society and Professor Lamb of the University of Glasgow, we would gratefully acknowledge the help of the BBC and the Post Office, and the loan of a signal strength meter from the local firm of K. Atter and Partners.



Earthquakes examined


A satellite which looks like a giant golf ball has been launched by NASA into a 5,900-km high orbit to obtain information on the Earth's polar motion and crustal movements. The Laser Geodynamic Satellite (Lageos) will use laser satellite tracking techniques to make extremely accurate measurements which include minute movements of large land masses, called tectonic plates.

Lageos carries an array of 426 prisms called cube-corner retroreflectors, giving it the dimpled appearance of a golf ball. Retroreflectors are three dimensional prisms that reflect light (in this case a laser beam) back to its source, regardless of the angle of incidence. A laser pulse beamed from a ground tracking-receiving station to Lageos initiates a timing signal at the ground station that continues until the pulse is bounced back from the satellite and received at the station. By measuring this length of

time, the distance between the station and the satellite can be calculated and in this way movements detected of the Earth's surface.

New ESA ground stations network

The European Space Agency ground stations network, controlled by the European Space Operations Centre is now composed of two types of station; the v.h.f. stations (Redu and Fairbanks) and the "specialized" stations (Odenwald, Fucino and Villafranca del Castillo). The Redu (Belgium) and Fairbanks (Alaska) stations form part of the network set up by ESRO in 1966 in relation to the orbits of the first European satellites which were mainly low and polar. The stations at Ny Alesund (Spitsbergen) and Port Stanley (Falkland Islands) which also formed part of this network, are now closed.

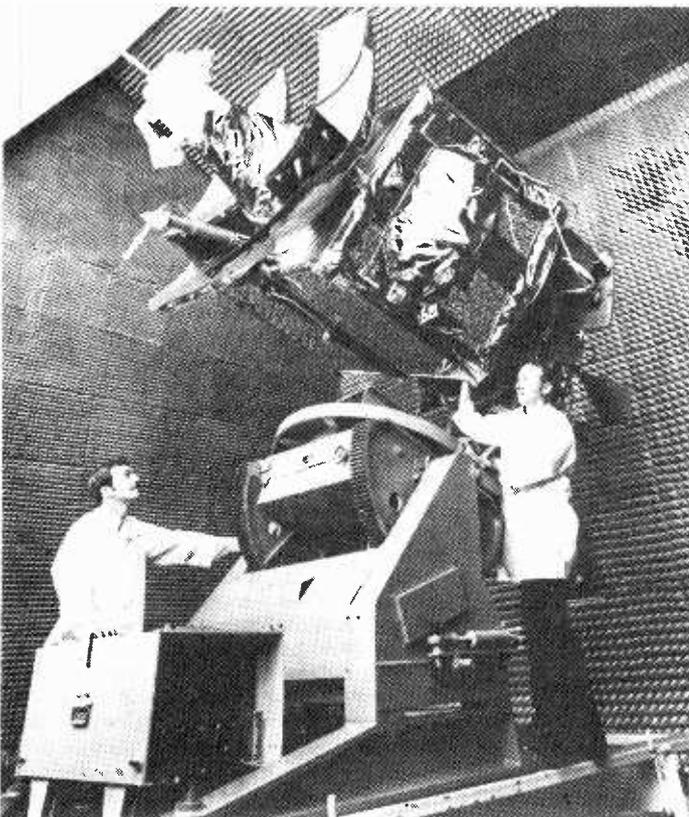

Satcom II during tests of the antenna system at RCA's Astro-Electronics Division, Princeton, New Jersey. The domestic communications satellite has recently joined Satcom I in orbit. It is capable of providing a communications service to 50 North American states.

At present Redu is performing tracking, telemetry and v.h.f. telecommand operations for COS-B, launched in 1975, and ANS, a Dutch satellite also launched in 1975. This will be the main v.h.f. station for GEOS tracking and telecommand (due for launch in 1977) and back-up v.h.f. for Meteosat (1977), OTS (1977) and Marots (1978). Fairbanks is also participating in support operations for COS-B.

The Odenwald station (Michelstadt, Germany) will acquire S-band data from GEOS. It will also collect, process and disseminate raw meteorological data from Meteosat.

The Villafranca del Castillo station near Madrid will perform the acquisition, scientific processing and control as well as the main support of the in-orbit operations of the maritime satellite, Marots (1978) and the aeronautical satellite, Aerosat (1979). The Fucino station near Rome, which is to perform the control of the operations of the telecommunications satellite OTS (1977), is already equipped with its main antenna and will be operational in 1977.

First Comstar in orbit

The first Comstar 1 communication satellite that will relay telephone and television traffic within the United States, Alaska, Hawaii and Puerto Rico was launched from Cape Kennedy at the beginning of May. Each Comstar 1 will be able to handle approximately 14,400 telephone conversations or about twice the capacity of the satellites presently operating. This has been achieved by a cross polarization technique which allows re-use of the same frequency bands and therefore more efficient use of the r.f. spectrum. The British Aircraft Corporation has manufactured a large part of the structure, solar arrays, cable harnesses and battery packs for these massive satellites which stand 20ft tall. Cylindrical solar panels, covered with nearly 17,000 solar cells, provide the satellite with primary power of 570W.

International magnetospheric study underway

An international magnetospheric study is now underway which is to last several years and is expected to help scientists understand more about the magnetic field surrounding the Earth. Geos, the first geostationary research satellite of the European Space Agency is due to be launched this autumn and will contribute information to the study. The antenna of the Earth station for this project was erected near Michelstadt, Odenwald by Siemens and was recently handed over ready for service to ESA.

Letters to the Editor

TRAFFIC BROADCASTING

I have read your very interesting article in News of the Month (*Wireless World* May 1976) concerning the BBC traffic service proposal. I should like to amplify a statement made in the final sentence, which deals with international aspects.

The European Broadcasting Union, through both its Technical and Programme Committees, has been studying the use of broadcasting in helping the motorist for some time. The requirements vary considerably from country to country, and lack of precise knowledge on this aspect has so far precluded a firm recommendation for any particular system. However, their technical sub-group (of which I am a member) regards the West German v.h.f. system as suitable in the short term. They have also said that in the longer term where a dedicated service is required, the t.d.m. (BBC) system might be feasible. The BBC has now demonstrated that, technically, this solution is feasible. It also represents a cheaper and more efficient approach for the United Kingdom, although the full technical implications of international operation have not yet been examined.

The proposal has clear advantages, but obviously to be successful it depends upon the organizations which obtain and process traffic information. This aspect and the interface with the broadcasting network are now being examined by the authorities concerned. This will, one hopes, lead to a public experiment.

R. S. Sandell,
BBC Research Dept.,
Kingwood Warren,
Surrey.

OUR DAILY BREAD

The pay and status of engineers has been an issue – amongst engineers – for some time, but no amount of criticism of employers, or of railing at an unjust world, can alter the fact that we are paid what we are worth, at least in the eyes of the world. The unpalatable truth is that the supply of engineers balances the demand at the prevailing rates of pay: we are not, in general, seen as demonstrating any particular sense of responsibility, and we must face the fact that the standard of education necessary to function to a satisfactory level is not particularly high, in spite of pious attempts

by our own establishment to make people believe so. If the pay demanded by a chartered engineer is too high, then his job can, and will, be done by someone else, with very few exceptions.

I believe we have not accepted sufficient responsibility for the end uses to which our products are put, we tend to be too short sighted, too involved in the immediate problems of how to make something work, to worry about implications for the future. The engineering profession is very inward looking; we seem to split into two camps which seldom meet. The one camp concentrates on the job in hand, meeting the employer's specification, cost and delivery, but never worrying about the use of the end product; and the other camp sits on committees, in institutions, universities and colleges, considering the engineering profession; its status, training and qualifications, occasionally handing down a sermon: "the engineer must be broadly educated", which is done by the addition of a class on "the engineer in society" or some such pretence: or perhaps "the engineer should join a trade union", the latest edict!

I suggest that we shall gain nothing from joining a trade union since we shall still be over-ruled by the giant manual unions, the power of which will continue to grow. They will not allow themselves to become the dog, wagged by the professional engineers' "tail".

The true answers, I submit, are two-fold. Firstly, we shall raise our status by demonstrating our responsibility and concern at the purpose and uses of those things which *would not exist* were it not for engineers; and secondly, we shall raise our pay, relative to the unskilled, only if we enter the political arena and join the battle to reduce the power of the unions, to get us out of the terrifyingly unstable situation we are now in. After all, if the pay of manual workers continues to increase at the expense of the professional engineer, we shall reach the stage where we simply refuse to become professional engineers and all become manual workers, and our civilisation cannot exist in those conditions.

J. C. Taylor, M.I.E.R.E.
Heywood,
Lancs.

CURRENT DUMPING AUDIO AMPLIFIER

I have had many enjoyable discussions with P. J. Walker, M. P. Albinson, P. Blomley and R. C. Bowes in the quest for the ideal audio amplifier which would be totally free from audible distortion, have no adjustments of any kind, and be economical and straightforward to manufacture. Numerous fascinating schemes have been considered, and assessing their overall relative virtues has been quite difficult – and indeed, at times, very perplexing.

When the Quad 303 circuit was first evolved, it was evident that the very good linearity of the individual triples, resulting from their internal feedback, was, in a sense, being partially wasted, because the existence of some residual crossover distortion in the transfer of current from one triple to the other necessitated a large amount of overall feedback in addition. A superb performance is, of course, thus obtained, but one was left feeling that if only a circuit could be devised that would sense when both triples were on

together and apply extra negative feedback to prevent the gain from increasing, then a more economical design, preferably free from preset adjustments, might be possible. Countless hours were spent scratching around trying to solve this and related problems, and there were moments of elation when it was thought that an answer had been found. But then it turned out that the proposed solution, to work ideally, involved the concept of infinite loop gain – camouflaged, maybe, as a requirement for a zero source impedance at some internal point in the circuit. In other words it turned out merely to be an example of Mr Halliday's "familiar assertion that the distortion can be made negligible by huge amounts of feedback".

Then Peter Blomley's fundamental and excellent new idea came along! – a class B amplifier in which both halves of the output stage retained their full mutual conductance throughout the whole audio cycle. This seemed to me at first to be the total answer to the problem of an adjustment-free amplifier with first-class performance, and I did a good deal of very encouraging experimental work leading to simplified circuit designs. It became evident, however, that though the technique is basically absolutely sound, the major practical problem is to ensure that, in the absence of any kind of adjustments or selection of transistors, the quiescent current will fall within reasonable practical limits, albeit quite uncritical ones, without wasting too much output power in highish-valued output-stage emitter resistors, or requiring, somewhere in the circuit, transistors having closely-matched V_{be} values at a given current. Circuits using dual transistors, or i.c.s, in the quiescent-current-determining circuitry, were inclined to become undesirably complex, though excellent results were obtainable.

I tried to persuade Peter Walker, at an early stage, that Quad would do well to develop an amplifier based on the Blomley idea, but he and Michael Albinson, with remarkable intuitive wisdom, sensed that the economics of such an approach might well be less than ideal, and they continued to investigate other techniques. The current-dumping scheme as conceived and developed by them seems to me to have an impressive elegance and economic "rightness" about it. Much of the practical success of the 405 design is due to the master-stroke of making the class A amplifier into an integrator, with an inductor elsewhere in the circuit, but there is also the ingenious economy of making the integrator output transistor (Tr_7 in Fig. 4, page 562, December 1975 issue) function in addition as the driver for one of the dumper transistors. (For practical reasons the dumpers-off regime is displaced to one side of the zero-load-current state.)

For the record, it may be mentioned that R. C. Bowes independently put forward a proposal for a current-dumping amplifier circuit, in which the current fed by the dumpers to the load was monitored not by a resistor directly in series with the load, but by small resistors in the collector leads of the dumpers. A negative-feedback voltage was derived from the sum of the voltage drops across these resistors, and values were so chosen that the gain of the system was independent of whether or not the dumpers were in action. So far as I can recollect, however, nothing comparable with the integrator-and-inductor scheme was envisaged.

Having just completed a chapter on amplifiers for the forthcoming Butterworths

publication "Radio, TV and Audio Technical Reference Book", I thought some *Wireless World* readers might be interested in the simple explanation there given of the Quad current-dumping technique. It seems to me that this rather different approach has the virtues (a) that it is more directly related to very familiar ideas and (b) that it provides a simple and convincing physical argument that the scheme must work, without recourse to any algebra. I believe that it is always very much worthwhile to seek the simplest possible, sound, non-mathematical explanation of any circuit, to supplement the algebraic analysis which may already have been done.

Consider first diagram (a). In the absence of overall feedback via R_1 , and assuming for convenience a resistive load, the transfer characteristic will be as at (b), giving gross distortion. With overall feedback, the transfer characteristic is much better, as shown at (c); but however much feedback is applied, it can never be quite perfect. Clearly what is wanted is to apply a little more negative feedback in the AB and A'B' regimes than in the AA' regime, thus equalizing the slopes in the three regimes. This is achieved with the (d) arrangement, in which R_1 receives a small extra voltage component (the voltage drop in R_4) only when the dumpers are in action. If R_4 is made too large, there will evidently be too much extra feedback, and the gain will then be less in the AB and A'B' regimes than in the AA' regime. The correct value of R_4 will thus give exactly

equal slopes, and there is clearly no need for infinite gain to exist anywhere in the circuit for this result to be obtained.

If R_2 is made very large, the system will have a large forward gain and there will then be a lot of overall feedback. Consequently, even with $R_4=0$, the characteristic shown at (c) will have nearly equal slope everywhere, so that a very small value of R_4 is all that is then required for perfect slope equalization. Thus, if R_2 is replaced by a capacitor, giving high forward gain at low frequencies only, the impedance element replacing R_4 needs to have an impedance which is very small at low frequencies but which increases in proportion to frequency to offset the effect of the falling forward gain introduced by C. An inductor is therefore required, as shown in (e).

When the circuit shown at (e) is handling a high-level sine-wave signal, the voltage waveform at 'P' is, of course, very non-sinusoidal, and it is therefore necessary for the class A integrating amplifier to have a clean performance up to much higher frequencies than the upper limit of the audio band. A very simple circuit is capable, however, of giving the required performance.





One way to arrive at the correct choice of values for distortionless results with circuit (e), assuming a perfect integrator, is as follows. Consider first the ideal limiting case that the dumper stage is not only on, but that it has infinite mutual conductance. Then the incremental output impedance of the complete circuit is clearly that of R_3 and L in

parallel, for at the left-hand side of both of these elements we see the zero output impedance of an ideal feedback circuit. Now consider the other limiting case, where the dumpers are completely off, and work out the output impedance (or, more conveniently, admittance) of the circuit which then applies. It will be found that if L is made equal to $R_3 R_4 C$, this output impedance is equal to that of L and R_3 in parallel, as before. Now any system with a distortionless no-load output voltage, and an output impedance independent of loading, must be distortionless.

P. J. Baxandall,
Malvern,
Worcs.

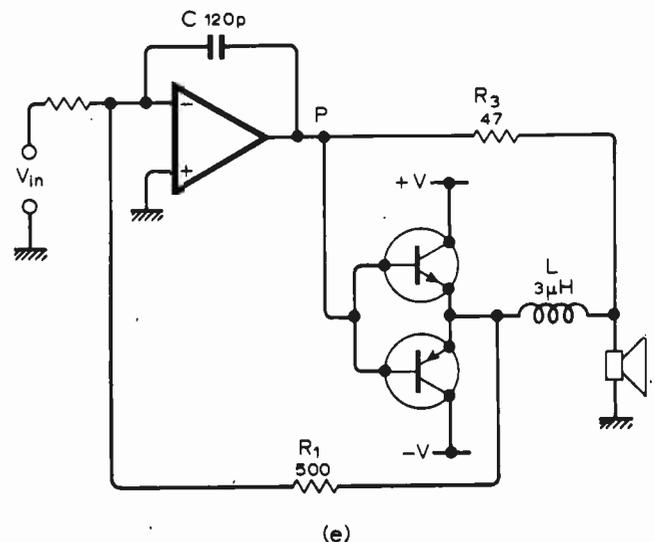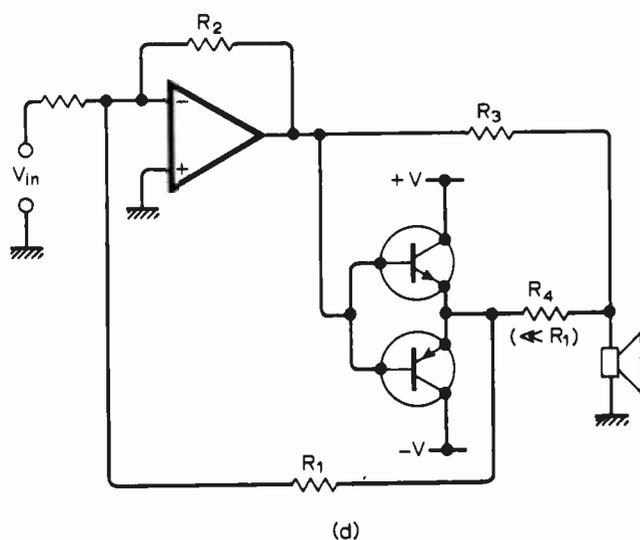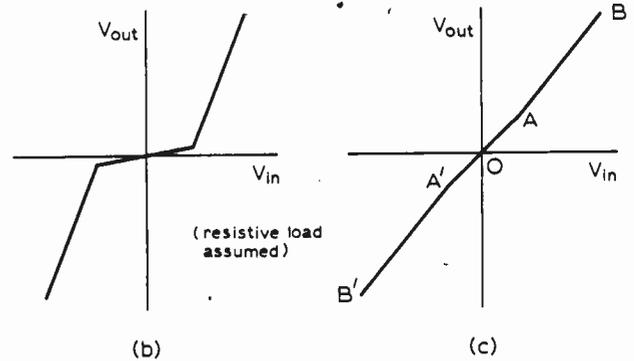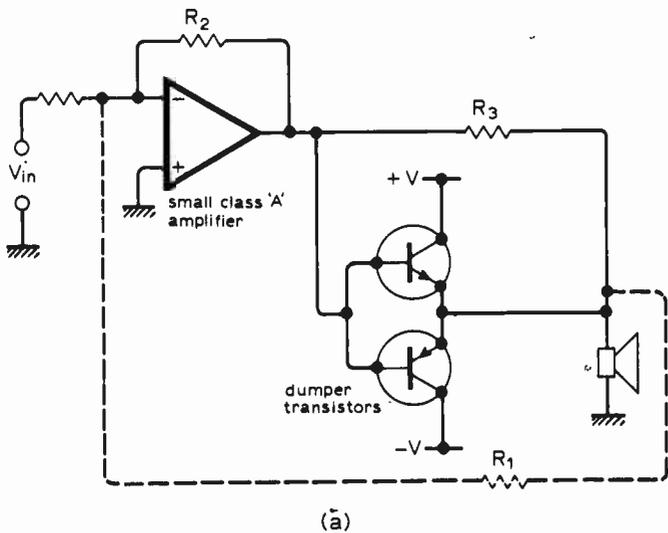1. Blomley, P., "New Approach to Class B Amplifier Design", *Wireless World*, Feb. 1971, pp. 57-61 and March 1971, pp. 127-131. (Also in *Wireless World* "High-Fidelity Designs" book.)

In the April issue of *Wireless World*, Mr P. G. Walker tries to prove that the feed-forward is linear, referred to the input. It would then be possible for the A gain (or G_{m1}) to be arbitrarily low and the current dumping to be linear at the same time. This is not the case. The error in the top figure on p. 55 is that it does not show the interaction between G_{m1} and G_{m2} . If G_{m2} is nonlinear it is impossible for G_{m1} (or A) to have a linear voltage and current gain consistent with linear load current. During the cross-over instant, when the power-section is cut-off, the total gain is only $A \cdot R_L / (Z_3 + R)$. During the remainder of the cycle the gain is A, because the power-section has approximately unity voltage gain. This causes some cross-over distortion if the gain of A is not infinite. No



more proof is needed to show that the feed-forward is not linear, referred to the input terminals.

One may look a little closer at the non-linear feed-forward, or shall we say, non-linear *gain*, assuming the existence of one of the following extremes of A and the power-section. Independent of how the amplifier A is fed back, it may have one of the extremes of voltage or current feedback or no feedback at all. Amplifier A may thus, by design, have a constant-voltage or constant-current output.

Constant-voltage output in series with Z_3 gives a constant G_{m1} – as long as Tr_1 and Tr_2 take no input current. But when they draw a base current comparable to the current in Z_3 the G_{m1} is no longer constant. Constant current generated by A has the same error. The conditions for constant G_{m1} do not exist as long as Z_3 is connected in parallel to the variable input impedance of Tr_1 and Tr_2 . In other words there is no way to make A linear, which was required to make term I_1 disappear from the equations. Since there is no linear relationship between the output voltage and the output from amplifier A , the "rigidity of interconnection" is missing, as pointed out by Mr A. Sandman.

The current dumping method acquires a linear *feedback* current, i.e., it is proportional to the total output current, but this goal can with the same merit by arranged by common voltage feedback (assuming constant load) as shown by Mr J. G. Bennett. The feedback from each output path is made proportional to the output current in that path. This holds both statically (feedback resistors only) and dynamically (feedback resistors, capacitors and inductors are used) because of the design rules suggested by P. J. Walker:

$$\frac{\text{feedback current}}{\text{output current}} = \frac{Z_3}{Z_2} = \frac{Z_4}{Z_1} = k.$$

That is: 1 mA of output current (or 1 mA/ μ s) causes $k \cdot 1$ mA feedback current, whether the current is sensed by Z_3 or Z_4 . In addition, there is only one summing point. The audio amplifier can not sense from where the feedback signal originates – all the output current branches being equally weighted by the rule of design. The *forward* linearity will not be changed by the divided feedback loops, since the same input voltage-differential V is needed to drive the current I_1 , and the base current of Tr_1 and Tr_2 , *irrespective* of how the feedback is taken.

The current dumping method would be unique if the feedback network could separate the different output paths. But it cannot, and the mode of operation is not different from one feedback resistor sensing the output current or output voltage or parts of both. The use of reactances, as in Fig. 2 in Walker's first paper, causes the feedback to increase with the frequency in the same way as if the single feedback resistor is shunted by a small capacitor. There is one implicit feature – that of current continuity, accomplished by Z_1 . If Z_1 has a low impedance, any non-linear amplifier would be less non-linear. The existence of Z_1 causes an improvement, but not a change of nature of the amplifier.

One arrives inevitably at the conclusion that the current-dumping scheme has the same forward nonlinearity and identical feedback collection of output current information, as an ordinary amplifier with zero bias current and with the same amount of feedback. In fact there is no difference at all. Bengt G. Olsson, Xelax AB, Stockholm.

THE WALLTENNA

Any reader who is offended by unsightly roof-top TV antennae should consider another alternative before starting to strip the wallpaper (The "Walltenna", WW May 1976 pp 57-59) – the screened loop. This gives me excellent colour TV reception in conditions where a commercial wide-band Yagi array (folded dipole, reflector, and 21 directors) gave excessive ghosting, and gross deterioration of the picture in bad weather. My house is about 50 km east of Crystal Palace, on high ground but surrounded by tall trees, which clearly provided most of the multiple-path interference. A two-turn screened loop mounted horizontally in the loft below the ridge-beam of the roof solved all my problems, and was very easy to make. The last two metres of the coaxial cable to the receiver were coiled to form two turns, and lashed with adhesive tape. A short length of the outer insulating sheath adjoining the loop was removed to expose the braided screen, and a copper-foil clip clamped round it: the free end of the cable was stripped and the screen cut back, the centre conductor being connected to the clip. The result is a loop antenna, having two turns fully electrostatically screened from each other and from interfering sources. The improvement in picture quality was sensational, and my chimney stack is now unadorned. The feeder to the receiver was dropped inside a cavity wall to a flush socket in the living-room, so the installation could not be neater. It is baffling that screened-loop antennae are not more widely used: in areas reasonably close to a transmitter they offer a far tidier roofscape, and less chance of ghosting from mutual interference.

David T. Broadbent,
Chatham,
Kent.

PHASE AND SOUND QUALITY

I hesitate to proliferate the correspondence on phase distortion, but there were letters published in the April issue worthy of comment.

Analogies between eye and ear can be interesting, although I am not sure that they are always constructive; specifically, the suggestion that parallels may be drawn between colour perception and the analysis of chords (even "broadly speaking") is quite wrong. I assume that when Mr Gamble refers to the presentation of a harmonic interval, such as a major third, he means that the tones are to be played simultaneously, otherwise the analogy will bear even less resemblance to the mixing of primary colours. If two notes, reasonably separated in frequency, are played simultaneously, the ordinary observer can pick out the two components making up the chord. If he cannot do this he will most easily hear the upper note, but there is certainly no perception of some kind of average frequency, half way between the two. In vision the situation is entirely different. With suitable choice of intensities a mixture of red and green light, of wavelengths around 600 nm and 540 nm respectively, will look indistinguishable from a pure yellow of

intermediate wavelength and the spectral components will be invisible.)

A far better analogy is to be drawn between the way in which we hear auditory frequencies and see spatial frequencies, such as a region covered by stripes. There is strong evidence (e.g. Campbell and Robson, *Journal of Physiology*, 1968) that the visual system analyses such stimuli in a manner equivalent to Fourier Analysis and it has been shown that a visual square wave (i.e. alternating dark/light stripes of equal width and with no merging through grey) invokes sensations at the third harmonic, as if there are stripes present three times as close. If stripes of high spatial frequency, with brightness varying sinusoidally, are displayed on a c.r.t. the contrast can be amplitude modulated at a lower frequency. This is exactly equivalent to amplitude modulating a high pitched tone with a lower frequency. In both cases, although the fundamental is not physically present, the low frequency, whether visual or auditory, is perceived.

In the same issue Mr Hodgkinson points out the many other sources of phase distortion that modify the wave form of a signal, apart from the loudspeaker. One that he does not mention is the outer ear flap or pinna. The little folds of the pinnae produce delays and echoes in the sound, particularly at higher frequencies, where the wavelength is comparable to the fold size. Far from being a nuisance to the auditory system the distortion of the waveform is a valuable direction-finding cue, since the effect varies with source/head angle. To extract a clear signal, when it is followed by multiple reflections, we use both ears. If readers care to listen to sounds in a fairly reverberent room and then cover one ear they will observe an increase in "boomyness." However, they will still be able to judge source direction fairly well. If those keen enough now fill in the folds of their exposed ears with plasticine they will find a marked decrease in localising ability! Some listeners to dummy-head recordings do not at first find them particularly convincing, but with continued listening the reality grows. This occurs as the listener learns to hear with a new set of pinnae. Of course, surroundings will modify the spectrum of a sound too, but the distortion remains constant for a given frequency and source direction and the auditory system seems very quickly to cope with this, learning to treat it as a constant. As long as the phase distortions introduced by loudspeakers do not fluctuate arbitrarily over short time intervals, then there is no reason to suppose that we cannot listen comfortably to the results, which is not to say that, given the opportunity to make fairly quick alternate comparisons, we cannot hear a difference between two loudspeakers of differing phase linearity.

Peter Naish,
University of Reading,
Berks.

Being a hi-fi enthusiast myself I have followed the arguments for and against the audibility of phase distortion in audio program material with much interest. To some extent I was hoping that this illusive but controversial effect may explain the differences in sound from systems which are not borne out by differences in specifications. The case for phase linearity in loudspeakers is obviously dubious by virtue of the preceding stages in the process from recording to the output terminals of the

amplifier, none of which (with possible exception of the amplifier) are performed with phase linearity as a subject of cause.

However it has intrigued me as to whether, given phase linear material applied directly to a loudspeaker, any phase difference gave rise to a difference in overall sound experience of the listener. In the absence of any phase linear material it is possible to obtain a signal source from two sine wave generators and feed these directly into a loudspeaker via a mixer network whilst monitoring the waveform on a c.r.t. It must be realized that this configuration obviates any of the negative arguments put forward by linear phase optimists that the effects are masked by the use of phase distorted program in subjective tests. It must be accepted that the sine waves from both generators, however pure or impure, are constant and phase distortion in a loudspeaker cannot exist (relative to constant listening position) when it is fed by a single sine wave without any fixed reference.

If the levels of both generators are the same and they are set at 1kHz adjustment of generator B will cause enhancement and cancellation effects at a critical point on the scale. If generator B is then increased to 2KHz and is offset sufficiently to allow it to drift gently in and out of phase with respect to generator A, the tone remains constant and apparently absent of aberrations due to the constant drift of phase between signals! I have carried out this experiment at all harmonic multiples and at various levels and ratios of level with various loudspeakers and have so far failed to hear any relationship between the relative phase of the generators and the actual sound of the resultant waveform.



However, if the resultant signal is seriously distorted by introducing a diode across the loudspeaker terminals, regular changes in sound, at the rate of changes in phase, can be heard at a few apparently arbitrary harmonics of the fixed generator A. It seems, therefore, that phase relationships of signals is only audible when the resultant composite signal is wildly distorted! This leads me to believe that, since all musical waveforms are made up of a complex combination of a wide range of sine waves, phase linearity cannot be heard or appreciated unless the output stages of the amplifier are clipping or half waving. And that the sound is then produced by the effect of the waveform meeting an insufficient threshold and is consequently incomplete?

Paul A. Furindle,
Norwich.

Television tuner design

Just a few points about the coil winding for D. C. Read's TV tuner. With regard to the pile wound centre-tapped coils, I presume it is best to wind them with a double strand of wire and make the centre tap the start.

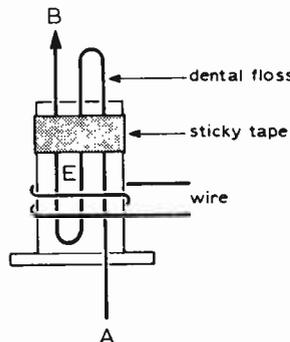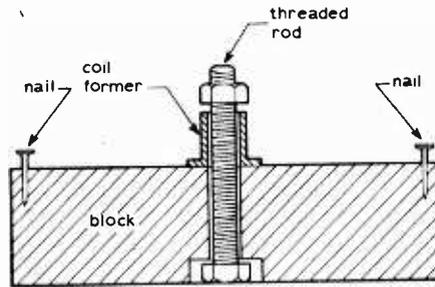Secondly, I would like to mention ways of making a single layer unframed coil very firm. Of course one winds on a simple jig, as in Fig. 1. To give the coils extra firmness either double-sided sticky tape folded back over the coil or a double looped technique using dental floss can be used. Wire is started through loop E and wound over the 3 strands of floss and to finish passed through loop F.



Then pulling end A will tighten the finish of the coil and pulling end B will tighten the start. It may help to attach the dental floss to the end with double sided sticky tape to start the coil. This makes a very firm coil.

J. Rankin,
Harpenden,
Herts.

Mr Read replies:

I thank Mr Rankin for his helpful coil-construction hints, particularly the one given for making secure winding ends. The double-loop, draw-through process will be well known and perhaps fondly remembered by any ex-Scout (or ex-Guide, for that matter) as the means to produce tidy 'whipping'; the extension of this technique to coil-winding, especially with dental floss as the draw string, is a very useful idea.

I must, however, correct Mr Rankin's wrong supposition regarding the winding of centre-tapped coils. As the tuner circuit diagram (Fig. 2 Part 1) shows, the sense of winding in each instance is 'series-aiding', and for such an arrangement it is necessary to have the centre tap at a finish/start point (assuming the coiling sense to be the same on both sides of the tap). It would be possible to use bifilar winding on these coils such as Mr Rankin suggests, but the double start could not be used as a centre tap because the two halves would then be in series opposition. In fact, with the coils parallel wound like this, the centre tap must be formed by cutting the double start and joining one of the resulting free ends to a winding finish.

But as most of the centre-tapped coils are used in the group-delay equalizer and this circuit is operating at an unusually high impedance of 750 ohms, this is not a satisfactory winding method because it results in excessive self-capacitance, with the danger of in-band self-resonant coils.


As explained in the follow-up article (Wireless World, April, page 83), pile winding is the best way to reduce coil capacitance and can be used for tapped as well as single coils. The diagram shows how the winding order is modified to enable the tap to be brought out.

The tuned circuits L_{10} (110 μ H) - C_{13} and L_{11} (14 μ H) - C_{31} should resonate at 3MHz and L_{12} (39 μ H) - C_{32} and L_{13} (12 μ H) - C_{33} should resonate at 5.5MHz. Wind L_{13} with 23 turns, and not 31 as given in the parts list. The correct tuning for these inductors should obtain when the cores are turned back between 1 and 4 turns from the fully-in position. In case of difficulty in resonating L_{10} , L_{13} , the shunt capacitors can be reduced.

The group delay network, L_{10} - L_{13} , may add a small amount of stray shunt capacitance and cause a slight droop of the video characteristic - between 1 and 2dB - which can be compensated by adjustment of the optional equalizer circuit in parallel with R_{25} (see broken lines at Tr_5 in Fig. 2, October issue page 450).

A pack containing all the parts required for the tuner inductors is available from Manor Supplies (excepting the rubber cushion shown on page 83. Cut this from rubber 1.2mm thick to a size of 13mm square).

Finally, a small but important aspect of reception inadvertently not covered in the earlier articles should be mentioned. It concerns the high-order vision and sound carrier harmonics generated by carrier clipping diodes in the MC1330 demodulator and the discriminator circuit. Some of these harmonics, specifically from the 12th to the 20th, fall in bands IV & V, and, if picked up on the aerial input, could cause considerable interference. Obviously, it is good practice to have efficient screens at all low-level circuit points, especially at the ELC1043 aerial input connection. For this particular purpose, a Mullard accessory - called an immunity shield (part number 4313 132 01910) - is available. A satisfactory home-made alternative can be constructed, however, by suitably stretching the screening braid of the incoming aerial co-ax so as to form a hood over the connection. As illustrated in the diagram below, this is most easily done by

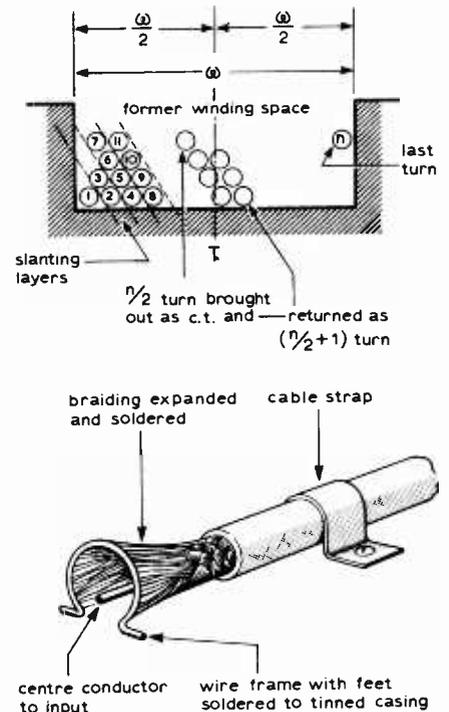

bending a small piece of wire (about 20 s.w.g.) into an omega-shape and soldering this to the tinned cover. The braid end is then pulled over and round the frame as shown and then soldered, allowing small amounts of solder to run over the braid to strengthen the hood.

Digital multipliers and dividers

Summary of circuits in set 31 of Circards

by J. Carruthers, J. H. Evans, J. Kinsler & P. Williams

Paisley College of Technology

Many transducers used in the measurement, or as a monitoring function, of physical processes deliver digital signals in the form of a pulse-rate. This sort of information is usefully processed by rate-multipliers which are available as m.s.i. circuits, both in t.t.l. and c.m.o.s. Their range of application is wide, covering numerical control, digital filtering and frequency synthesis, to name a few. When combined with up-down counters, rate-multipliers may perform arithmetic functions such as multiplication, division, square-rooting and integration.

Basically, a rate-multiplier generates an output pulse-rate or frequency which is proportional to the product of two inputs, one of which is a clock frequency f_c , and the other, an n -bit binary or binary-coded-decimal integer. M is the programmed number, with $N=2^n-1$, and the output pulse rate is $f_c \cdot M/N$ where $N > M$, so that the output rate is always less than the input pulse rate. Usually the rate-multiplier produces a train of unevenly-spaced pulses, but this is not too critical when the output rate is time-averaged to the correct fractional rate of the input pulse train.

This type of multiplier is useful under conditions where variable input pulse rates are to be multiplied or divided on-line. For example, an unknown input frequency can be compared against a rate-multiplier output and on the result of the comparison, a counter can be made to count up or down until a stable result is acquired, which will relate to the unknown quantity. This is usually a counter/multiplier closed loop which allows fairly straightforward implementation. Discrete and m.s.i. forms with applications are covered in three of the cards of this set.

Card 8 considers a simpler frequency ratio ratemeter to provide an analogue output signal proportional to the ratio N_1/N_2 , where N_1 and N_2 are the average rates of two input pulse trains, but this requires additional constraints on the ratio that can be recognized. Normal frequency division with m.s.i. counters provides output pulse trains which are

not symmetrical, whereby with fairly simple external gating, card 7 summarises techniques for obtaining a range of dividers which always produce symmetrical outputs.

Stochastic multiplication is reviewed in card 4, with a novel delta-sigma modulation technique using probabilistic principles being discussed on card 6. The specific application arranges for squared and cubic outputs proportional to an analogue input, but demanding a synchronous clock-drive. Another m.s.i. package for implementing cellular-array structures provides for 2 bit by 2 bit multiplication, and is shown to be extendable to increased bit manipulation by straightforward interconnection of the i.c. packages. To conclude this short summary of Set 31, a digital/analogue monolithic 8-bit d-a converter is shown to provide a fairly simple technique for multiplying two-binary numbers and giving an analogue output voltage or current proportional to the result.

Titles of cards in this set are:

- 1 monolithic d/a multiplier
- 2 2 x 2 bit binary multiplier
- 3 binary rate multiplier
- 4 stochastic multiplication
- 5 dual-slope a/d multiplier
- 6 $\Delta\Sigma$ modulator probability multiplier
- 7 symmetrical programmable divider
- 8 pulse ratio measurement
- 9 applications of rate multipliers/dividers - I
- 10 applications of rate multipliers/dividers - II

How to get Circards

Order a subscription by sending £18 for a series of ten sets to:

Circards
IPC Electrical-Electronic Press Ltd
General Sales Department, Room 11
Dorset House
Stamford Street
London SE1 9LU

Specify which set your order should start with, if not the current one. One set costs £2.00, postage included (all

countries). Make cheques payable to IPC Business Press Ltd.

Circard sets available

- 1 active filters
- 2 switching circuits (comparator and Schmitt circuits)
- 3 waveform generators
- 4 a.c. measurement
- 5 audio circuits (equalizers, etc.)
- 6 constant-current circuits
- 7 power amplifiers (classes A, B, C, D)
- 8 astable multivibrator circuits
- 9 optoelectronics: devices and uses
- 10 micropower circuits
- 11 basic logic gates
- 12 wideband amplifiers
- 13 alarm circuits
- 14 digital counters
- 15 pulse modulators
- 16 current-differencing amplifiers — signal processing
- 17 c.d.as — signal generation
- 18 c.d.as — measurement and detection
- 19 monostable circuits
- 20 transistor pairs
- 21 voltage to frequency converters
- 22 amplitude modulators
- 23 reference circuits
- 24 voltage regulators
- 25 RC oscillators-1
- 26 RC oscillators-2
- 27 linear c.m.o.s.-1
- 28 linear c.m.o.s.-2
- 29 analogue multipliers
- 30 non-linear circuits
- 31 digital multipliers and dividers

Surround sound decoders — 2

Assembly, setting-up CD-4 unit, cartridge notes

David Heller, B.Sc.(Eng.)

This article includes performance details of a CD-4 decoder using the QSI i.c., which includes preamplifier, phase-locked loop demodulator, a.n.r.s. expander and muting circuits. Spectrum analyser traces show performance of record-cartridge-decoder system for various extended-response cartridges. Subsequent articles by the same author will give circuits for QS and SQ surround sound decoders.

The construction of the demodulator is straightforward, but note the following points. Solder the link wires whose positions have been silk-screened on top of the board after soldering resistors into position, but before soldering the remaining components. Do not apply too much heat to the polystyrene capacitors; these 30 volt devices are closely wound and excessive heat will short the layers together.

The 12mH, 15mH and 18mH inductors are variable inductors which have been preset. They are either marked with their values or colour coded with paint (red — 12mH, green — 15mH and grey — 18mH). On no account should the pot cores be adjusted and each coil should only be handled by its case so as not to disturb the core.

Use insulated wire to connect remaining links (marked A to A, B to B, C to C, D to D, E to E, F to F, G to G and H to H on the board). These connections are best made on the copper side of the board.

In connecting the signal input to the board (points h and i on the switches to points h and i on the board), use screened cable but only earth one side of the lead. To stop possible r.f. breakthrough, loop small ferrite beads with three to four turns of wire and solder one end of this wire to the points on the board (marked h and i) with the other end going to the audio lead.

Connect the points on the switch positions to the similarly marked points on the board using insulated wire. Again it is preferable to make the connections on the underside of the board. (The positions to be connected are b to b, o to o, c to c, x to x, d to d, m to m, e to e, l to l. Points f, k, a and p are left unconnected.) The signal input leads to the selector switches are: tuner input to v (left) and w (right); auxiliary input to s (left) and t (right); tape input

to g (left) and r (right), and disc input to g (left) and j (right).

Care must be taken not to create an earth loop; in particular the input socket earth must not touch the chassis. A separate earth line should be run from the mains socket earth to the earth of the power supply. And the board should only be earthed in one position i.e. an earth wire is run from the earth point on the board to the power supply earth. A 100nF capacitor should be soldered between the input socket earth and chassis. Run an earth wire from the chassis to the power supply earth terminal.

Connections for switches S_1 are best "hard-wired", depending on whether a magnetic or semi-conductor cartridge is used. (Note that on the p.c. board, the marking "S1E" correspond to S_{1b} in the circuit diagram. S_4 on the board corresponds to S_2 in the circuit.)

When wiring is completed (do not forget the l.e.d. — anode to supply rail) mount the board in its box and connect up a regulated 13 to 14 volt supply line to the supply rail, but do not turn on. (A power supply is included in the kit available from Compcor; a circuit will be given with the next part and is suitable for the CD-4, QS and SQ decoders.)

Setting-up procedure

Connect the record player fitted with extended-response cartridge to the input jacks of the demodulator using low-capacity TV cable of approximately 50pF/metre. Limit the cable length to maintain a total capacitance of 100pF or less. Run a separate earth wire from the chassis of the demodulator to a screw or chassis of the turntable.

Switch on the equipment and place the pickup on band 2 of side 2 of the test record. If the demodulator is functioning and either of the two phase locked

loops are in-lock, the l.e.d. should glow. Adjust the 4.7k Ω v.c.o. potentiometers so that the l.e.d. glows brightest. By turning the v.c.o.-adjust potentiometer ($R_{57,157}$) to either of the extreme positions, the l.e.d. will either go off or vary in intensity depending whether the other v.c.o. is in lock or out of lock.

Turn the test record to side 1, band 3. This gives the same music played sequentially out of each speaker. Turn down the front volume controls of your amplifier. Adjust the 1k Ω separation potentiometer ($R_{9,109}$) of the preamplifier for minimum loudness out of the respective rear channels when the announcer states the front channel sound. The announcer will state "left front channel" and music will follow. Adjust the left separation adjust to get minimum loudness from the left rear channel. Disregard the announcement of the rear channel music. Repeat the process for the right front channel announcement, this time tuning for minimum right rear channel loudness.

Alternatively, the white noise source on band 2 can be used. This is fully explained on the test record. Return to side 2 of the test record and place the cartridge anywhere from band 2 onward. Turn the balance control first to the left side and adjust the left hand side v.c.o. control for minimum distortion. Repeat the process with the balance control set for the right hand side.

Extended-response cartridges

The following nine cartridges were tested: Tenorel 2001SD, Audio Technica 12S, Nagaoka JT322, JVC 4MD20X, B & O MMC5000, B & O MMC6000, JVCX1, Pickering UV152400 and Pickering XUV4500. Each cartridge was tested in an SME arm with detachable headshell. Tracking weights between 1gm and 3gm were chosen depending on the

various manufacturers' recommendations. Using side 1, band 3 of the test record, the separation control was adjusted for minimum level out of each of the rear speakers.

Side 1, band 2 of the test record contains CD-4 encoded white noise. With the aid of an audio spectrum analyser, kindly loaned by Hewlett-Packard, the spectrum level of the front channel was measured and stored on the display. The analyser was then connected to the rear channels and the same passage of white noise was replayed and the spectrum level recorded on the lower trace.

The accompanying photographs, Fig. 11, show the relative levels between front and back for the left hand channels only, the top trace being the front channel and the lower trace being the rear channel. The difference in level is thus the separation obtained from the disc encoded material through the cartridge and demodulator.

Performance

Input level	0.7 to 14mV
Input impedance	
magnetic	100kΩ
semiconductor	2.2kΩ
Output level	300mV
Output impedance	less than 200Ω
Amplitude response	
baseband system	30Hz to 15kHz, -3dB
carrier system	30Hz to 12kHz, -3dB
Harmonic distortion	
baseband	less than 0.2%, at 150mV output (typically 0.05%)
carrier channel	less than 1%, at 150mV output, 1-10kHz
Power supply	12 to 15V, 130mA max

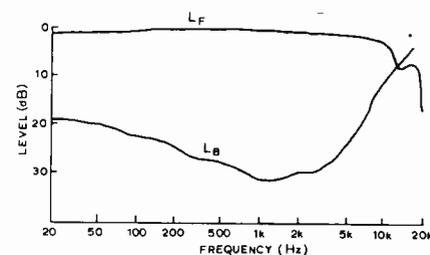


Fig. 13. Front-back separation measured using test bench generator. Sum signal delayed by 45μs with reference to the carrier signal.

Separation front-back	>30dB at 1kHz. See Fig. 13 for system separation
left-right	60dB at 1kHz
S/n ratio*	>60dB

*Measured using a virgin test record, containing an unmodulated and modulated (1kHz) carrier together with 1kHz baseband signal.

Components

Resistors All 1/4W 5% carbon film

R ₁ , 101	47k
R ₂ , 102	100k
R ₃ , 103	10k
R ₄ , 104	150k
R ₅ , 105	15k
R ₆ , 106	15k
R ₇ , 107	15k
R ₈ , 108	2.2k
R ₉ , 109	1k pot
R ₁₀ , 110	20
R ₁₁ , 111	2.2k
R ₁₂ , 112	20
R ₁₃ , 113	330
R ₁₄ , 114	3.3k
R ₁₅ , 115	150k
R ₁₆	100k
R ₁₇ , 117	6.8k
R ₁₈ , 118	8.2k
R ₁₉ , 119	7.5k
R ₂₀ , 120	15k
R ₂₁ , 121	4.7k
R ₂₂ , 122	4.7k
R ₂₃ , 123	4.7k
R ₂₄ , 124	8.2k
R ₂₅ , 125	4.7k
R ₂₆ , 126	1k
R ₂₇ , 127	27k
R ₂₈ , 128	4.7k
R ₂₉ , 129	15k
R ₃₀ , 130	220k
R ₃₁ , 131	15k
R ₃₂ , 132	4.7k
R ₃₃ , 133	10k
R ₃₄ , 134	220k
R ₃₅ , 135	3.3k
R ₃₆ , 136	4.7k
R ₃₇ , 137	4.7k
R ₃₈ , 138	4.7k
R ₃₉ , 139	4.7k
R ₄₀ , 140	470k
R ₄₁ , 141	1.8k
R ₄₂ , 142	4.7k
R ₄₃ , 143	4.7k
R ₄₄ , 144	4.7k
R ₄₅ , 145	47k

R ₄₆ , 146	4.7k
R ₄₇ , 147	4.7k
R ₄₈ , 148	4.7k
R ₄₉ , 149	47k
R ₅₀	1.8k
R ₅₁ , 151	560k
R ₅₂	330
R ₅₃ , 153	2.7k
R ₅₄ , 154	1k
R ₅₅ , 155	330
R ₅₆ , 156	56k
R ₅₇ , 157	4.7k
	preset
R ₅₈ , 158	10k
R ₅₉ , 159	10k
R ₆₀ , 160	10k
	optional
R ₆₁ , 161	10k

Capacitors

Types E are electrolytic. PC Siemens B32540 polycarbonate, PE polyester, PS 30V polystyrene, and DC disc ceramic.

C ₁ , 101	3.3μ	16V	E
C ₂ , 102	200μ	10V	E
C ₃ , 103	4.7n	PS	
C ₄ , 104	22n	PC	
C ₅ , 105	0.47μ	E	
C ₆ , 106	33n	PS	
C ₇ , 107	2.2n	PC	
C ₈ , 108	2.2n	PC	
C ₉ , 109	8n	PE	
C ₁₀ , 110	450p	PS	
C ₁₁ , 111	1.4n	PS	
C ₁₂ , 112	1.6n	PS	
C ₁₃ , 113	10n	DC	
C ₁₄ , 114	3.3μ	16V	E
C ₁₅ , 115	2.7n	PS	
C ₁₆ , 116	2.1n	PS	
C ₁₇ , 117	960p	PS	
C ₁₈ , 118	3.9n	PS	
C ₁₉ , 119	6.8n	PS	
C ₂₀ , 120	3.3μ	16V	E
C ₂₁ , 121	7.2n	PS	
C ₂₂ , 122	10n	DC	
C ₂₃ , 123	3.3μ	16V	E
C ₂₄ , 124	100p	PS	
C ₂₅ , 125	100p	PS	

C ₂₆ , 126	0.47μ	16V	E
C ₂₇ , 127	2.2n	PC	
C ₂₈ , 128	0.68	PC	
C ₂₉ , 129	4.7μ	16V	E
C ₃₀ , 130	960p	PS	
C ₃₁ , 131	3.9n	PS	
C ₃₂ , 132	3.1n	PS	
C ₃₃ , 133	3.3μ	16V	E
C ₃₄ , 134	3.3μ	16V	E
C ₁₃₅	100μ	10V	E
C ₃₆ , 136	10n	DC	
C ₃₇ , 137	6.2n	PS	
C ₃₈ , 138	800p	PS	
C ₃₉ , 139	3.3μ	16V	E
C ₄₀ , 140	68p	DC	
C ₄₁ , 141	10n	DC	
C ₄₂ , 142	6.2n	PS	
C ₄₃ , 143	800p	PS	
C ₄₄ , 144	3.3μ	16V	E
C ₄₅ , 145	68p	DC	
C ₄₆ , 146	10n	DC	
C ₁₄₇	100μ	10V	E
C ₄₈ , 148	100μ	16V	E
C ₄₉ , 149	33μ	10V	E
C ₅₀ , 150	6.8n	PS	
C ₅₁ , 151	10μ	16V	E
C ₅₂ , 152	100n	DC	
C ₅₃ , 153	68p	DC	
C ₅₄ , 154	10n	DC	
C ₅₅ , 155	10n	DC	
C ₅₆ , 156	68p	DC	

Semiconductor devices

IC₁, IC₁₀₁ Signetics QS5022
 Tr₁ - Tr₄, Tr₁₀₁ - Tr₁₀₄ BC208A
 D₁, D₁₀₁, D₂, D₁₀₂ 1N4148
 light-emitting diode TIL209, MLED650, or similar

Inductors

L ₁ , 101	15mH	Toko	80016
L ₂ , 102	18mH	Toko	80016
L ₃ , 103	12mH	Toko	80016
L ₄ , 104	15mH	Toko	80016
L ₅ , 105	100mH	TDK	104J

A 10kHz bandwidth is displayed because, in all but one case, the separation fell below 5dB after 10kHz. The only exception was the B & O MMC5000 where 10dB of separation extended to 13kHz Fig. 12.

In addition listening tests were carried out using difficult CD-4 records. The following is a brief assessment of each cartridge.

Tenorel 2001SD. Separation of 18dB was attained at about 2kHz, but disappeared totally at 9kHz and reversed at 9.25 kHz. In the listening tests, carrier dropout occurred frequently with annoying results. Playing weights of close on 3gm were required with the result that the cartridge base nearly touched the record.

Audio Technica 12S. Peak separation of 18dB occurred at about 2kHz, decreasing to 5dB at about 8kHz and remained at such to 13kHz, where the low-pass filter in the demodulator started to take effect. A tracking weight of 1.8gm gave good results with little carrier dropout. This cartridge is available at discount stores for about £17 (including v.a.t.) and is the low cost cartridge I would recommend for the system.

Nagaoka JT322. This cartridge displayed 15dB separation at 2kHz, but this disappeared at about 9kHz. Its output at 2gm tracking weight was on the low side and it did not track difficult passages as well as the AT12S. This cartridge is available from its distributor in The Netherlands at a cost of about £22. The AT12S is a better bet.

JVC 4MD20X. This cartridge gave essentially similar results to the AT12S, but is about twice its cost. I would go for the AT12S in preference as I found little to choose between the two in performance.

B & O MMC6000. The MMC6000 has a recommended tracking weight of 1gm. I tried three of these cartridges and none functioned satisfactorily. The devices suffered from carrier loss particularly in the left channel. The latest sample I tried was found to be defective when played through B & O's own demodulator. I believe the cartridge should only be used in the tangential player for which it was designed; the SME arm has too much mass for such a delicate cartridge.

B & O MMC5000. The MMC5000 gave excellent separation results, as the extended separation trace of Fig. 12 shows. However, the maximum practicable tracking weight was 1.5gm and this was inadequate for an SME or similar type arm. The cartridge is ideally suited for the B & O 3400 unit which has a low-mass arm and can thus track at a lower weight more effectively. A pity, because this cartridge showed signs of excellence, but carrier breakup was too frequent for comfort. On consulting B & O they agreed that a low-mass arm would be needed to ensure effective tracking.

JVC X1. This cartridge gave 20dB


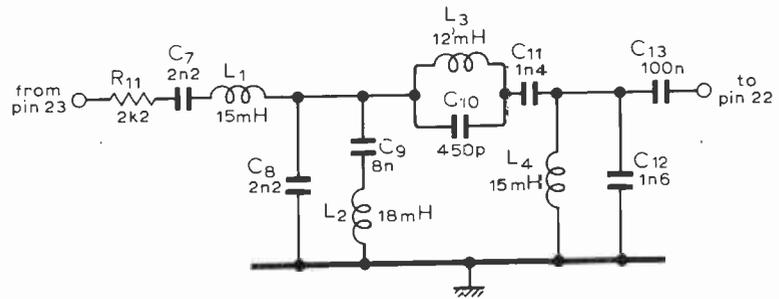


Fig. 10. Linear phase filter with delay of 32µs, 19-45kHz. Two of these filters are used in the circuit of Fig. 9.

Fig. 11. Spectra of the left front and left back demodulated signals from a white noise CD-4 encoded disc through selected cartridges and the demodulator.

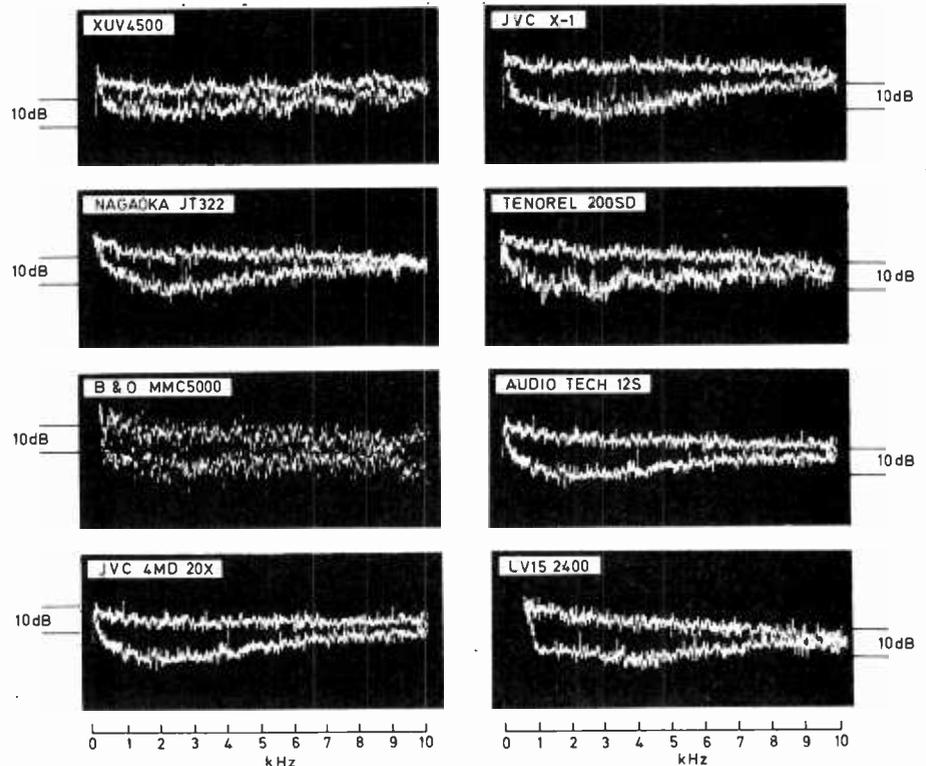

separation between 2 and 5kHz, settling to about 5dB at 9kHz. Its tracking of CD-4 records at 1.8gm was excellent and its clarity was unequalled by any other cartridge except Pickering's XUV4500. This is indeed an excellent CD-4 cartridge and is available at some discount stores at about £50. For those who have the money, this represents very good value.

Pickering UV152400 and XUV4500. Both of these cartridges are very expensive. The UV152400 displayed similar separation characteristics as the AT12S but was clearly superior in tonal quality. However, it is more expensive than the JVC X1.

The XUV4500 was an excellent cartridge. Admittedly the separation exhibited in the photograph looks poor (about 10dB over the bandwidth displayed), but it is likely that this is


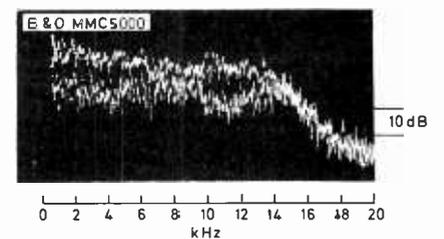


Fig. 12. Separation of 10dB or more extends to 13kHz in the case of the B&O mmc5000 cartridge.

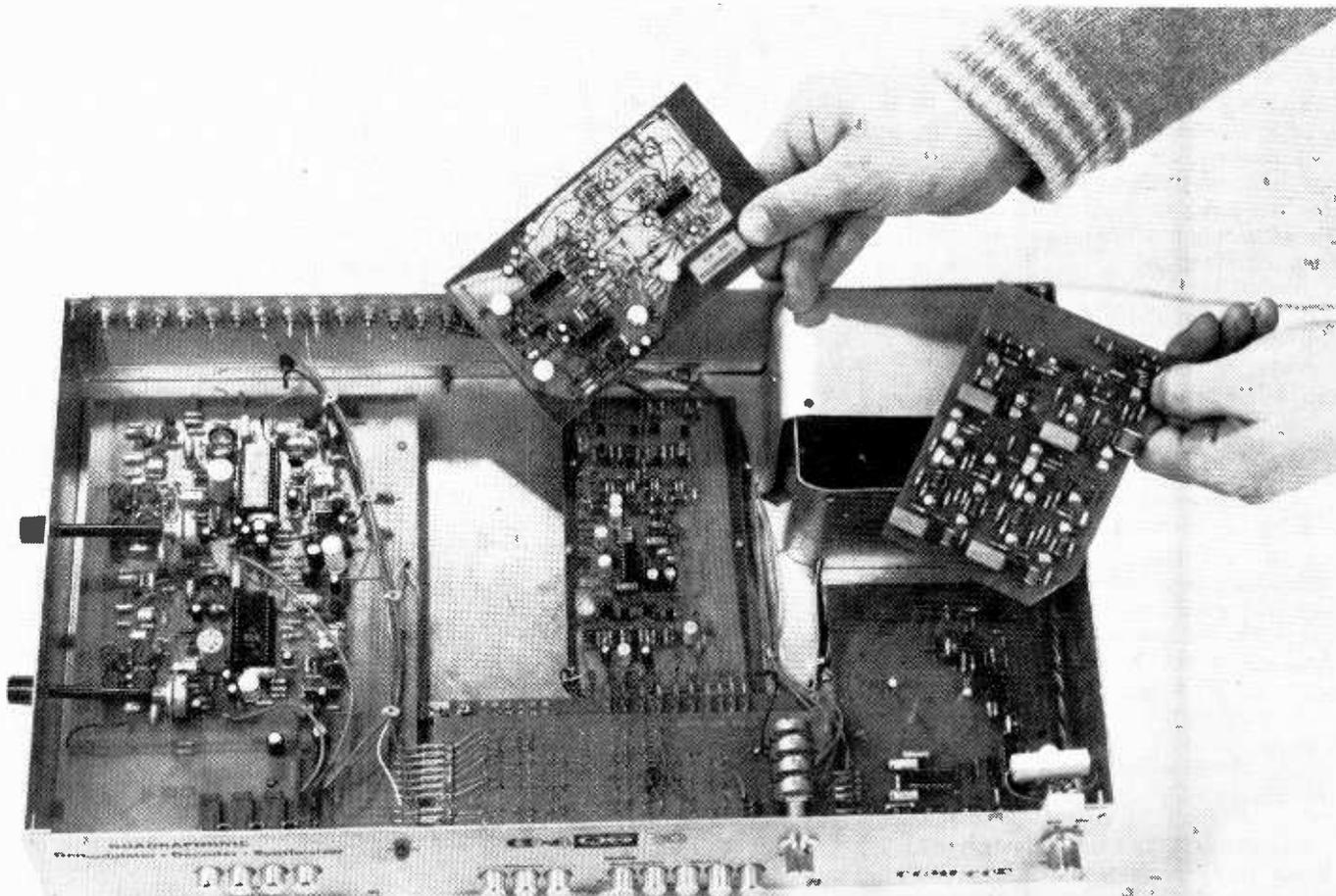because the delay time of this cartridge is shorter than that of the other cartridges tested (12µs for the XUV4500 against 25µs for the majority of the others). The demodulator is designed for a 25µs delay through the cartridge and any deviation from this will reduce separation. In listening tests I was not



able to perceive any less separation through this cartridge when compared to the JVC X1. It performed equally as well as the X1 and proved superior on stereo discs to the X1. Both cartridges were tested using the difficult band of the Hi-Fi Sound 75 test record. The XUV4500 tracked this band perfectly, while the JVC X1 displayed some slight mistracking.

After carrying out extensive tests on the cartridges named, I would recommend the AT12S for budget systems and the JVC X1 for those who can afford it. In both cases a tracking weight of between 1.8 and 2.0gm proved optimal.

Correction. On page 45 of the June

One format of the surround-sound decoder incorporating CD-4 unit (left). A two-board SQ decoder is shown right, and a two-board QS decoder middle. There is space for a rear-channel, preamplifier and tone control, above the switchboard.

issue, the reference to C₃₈ should be to C₃₃.

Acknowledgement. I should like to thank Lou Dorren of Quadracast Systems Inc. for the valuable help and guidance given in the preparation of this CD-4 project. Thanks too to Hewlett Packard for the loan of the audio spectrum analyser.

A kit of parts (except metalwork) may be obtained from Compcor Electronics Ltd, 9 Dell Way, London W13 8JH for £37 inclusive of v.a.t., packing, postage and insurance. The same price applies to overseas readers, and covers the cost of airmail postage. A test record produced by Quadracast Systems Inc is available for £4.20 inclusive from the same supplier.

A specially constructed case is available from Bazelli Instrument Cases, St. Wilfred's, Foundry Lane, Halton, Lancaster LA2 6LT for £10 (including v.a.t. and carriage) with fully punched panels or £8 unpunched. This case will house CD-4, QS and SQ decoders and power supply. A suitable case for the CD-4 module only is type B304, available from the same company for about £5 (unpunched) inclusive of delivery and v.a.t.

Announcements

Panduit Ltd of Sittingbourne, Kent, manufacturer of cable ties and DIN connectors, has announced the appointment of Vero Electronics Ltd, Chandler's Ford, Eastleigh, Hants, as the UK stockist and distributor for the Panduit range of DIN 41612 and 41613 one-piece and two-piece connectors.

Gould Advance Ltd has appointed J. Sinclair Ltd, 8 Dixon Place, College Milton North, E. Kilbride, Glasgow, G74 5JF, as the Scottish agent for Gould Advance power supplies and Gould Brush oscillographic recorders.

Ferroglyph, Ferroglyph Professional, Rendar and Wayne Kerr, formerly operating as separate companies within the Wilmot Breeden (Holdings) Ltd, are to trade collectively as **Wilmot Breeden Electronics Ltd**. Manufacturing facilities for the various product groups will remain at South Shields, Burgess Hill and Bognor Regis.

Laskys, one of Europe's leading hi-fi retailers, has announced a new service. All of Laskys' 35 branches will offer a **repair service** for any hi-fi equipment, provided that spare parts are available. You do not need to have purchased the equipment from Laskys.

Boosey & Hawkes Ltd has formulated a new subsidiary **Boosey & Hawkes (Electrosonics) Limited**. This follows the acquisition earlier this month of 50 per cent of Hammond Organ UK Ltd. Hammond will continue to be run by its existing management team who will also manage Boosey & Hawkes (Electrosonics). Boosey & Hawkes (Electrosonics) will market a range of electronic musical products both in the UK and overseas. It will be exclusive distributor of Leslie Speakers in the UK and will operate from new premises at St Albans, Herts.

Steatite Insulations Ltd, Hagley House, Hagley Road, Birmingham, B16 8QW, have announced their entry into the field of semiconductor devices in co-operation with **Toshiba (UK) Ltd**. The aim of the agreement is to broaden the UK penetration of Toshiba's semiconductors and to enable this by forming a semiconductor marketing department at the Steatite Group's headquarters in Birmingham.

In keeping with their involvement with the military electronics industry, **Sealelectro Ltd**, Walton Road, Farlington, Portsmouth, PO6 1TB, manufacturers of precision coaxial connectors, insulated terminals and programming devices, have received approval by the Ministry of Defence to the recently introduced standard 05-21.

The UK agency for **Fuki Film magnetic tape**, has been given to Belmont A/V Ltd, a member of the Pyser Group, at Fircroft Way, Edenbridge, Kent, TN8 6HA. The range of Fuki Film cassette and open reel tapes is available to the public from mid-May, 1976.

Uber Werke Munchen have announced that with effect from April 1st, 1976, a wholly owned subsidiary company, namely Uher Ltd, 24 Market Place, Falloden Way, London, N.W.11, will transact all business in the UK and Channel Islands under a distribution agreement.

Jermyn Industries, Vestry estate, Sevenoaks, Kent, will programme all National p.r.o.ms free of charge, providing the memories are purchased from them. They will also consider programming memories of other manufacture free of charge dependent on type of memory, application and complexity.

IF THE NAKAMICHI CAN CAPTURE HIM, THINK WHAT IT'LL DO FOR BEE THOVEN.

Most portable cassette decks are quite happy recording the odd pop song.

But give them something truly challenging, and you soon realize their shortcomings. Fine, if you're content to be unambitious. But at Nakamichi we think you should be able to record any sound you want. Which is the reason why we produced the Nakamichi 550.

From a mouse squeak to the triumphant sounds of Beethoven, you can record it all on a Nakamichi 550.

Its peak level meters have a range of 45dB. Its signal-to-noise ratio is more than 60dB. Its microphone inputs have a dynamic range of 125dB.

Wider ranges than any other portable cassette deck in the world.

And that's not all. The 550 is also the only portable cassette deck with 3 microphone inputs. And a tape end alarm with pre-set timer.

The only one too, with a button that shows how much of your cassette you've used.

And Nakamichi's exclusive record/playback head. And it's the only one with a battery life that can give you up to 15 hours continuous playing.

When you try the Nakamichi 550, you'll know why it costs £274.50 including VAT at 12½%. Suddenly, other portable cassette decks look like toys.



NAKAMICHI

THE WORLD'S MOST VERSATILE PORTABLE CASSETTE DECK

Natural Sound Systems Limited,
Strathcona Road, North Wembley, Middx. HA9 8QL. 01-904 0141.

WW-065 FOR FURTHER DETAILS

www.americanradiohistory.com

PLESSEY

You know the name
but did you know that we
supply electronic
components from stock?

**24 hour
turn round.**

**No minimum
order charge.**

**No post or
packing charges
in the UK.**

For priced stock catalogue
and terms of business,
contact:



**PLESSEY
DISTRIBUTORS**

Vicarage Lane Ilford Essex IG1 4AQ
Telephone: (01) 478 3040 Extn 3391
Telex: 23766

WW — 072 FOR FURTHER DETAILS

621 P007A


Reliable Signal Rerouting with Hatfield Coaxial Switches

The new 2320 series
Microwave Coaxial Switches
provide efficient and accurate signal rerouting
for Television, Radio and
telegraphic communications
in the 2 — 4 GHz
range. They have
low VSWR,
low crosstalk,
single-pole
2 to 6-way
switching.



Low priced 2700 series Coaxial Relays

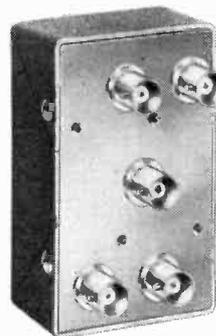provide single pole switches of 2, 4 or 6 ways.
Exceptionally low insertion loss with high isolation.
Versions available for 12 or 24 volt operation.
Contact rating (non switching) 100 watts C.W.
50 or 75Ω terminations.



Hatfield 6 and 11 Coaxial Switches

are designed for selective
switching of R.F. signals
without mismatch.
Specifications extend to
500 MHz. Alternative versions
incorporate automatic
terminations of unused ways
in to 50 or 75Ω.

For more complex
applications,
ask for details
of Hatfield,
26 way TTL
Compatible Reed
Relay Switch.



HATFIELD
forward thinking in electronics

HATFIELD INSTRUMENTS LIMITED,
Burrington Way, Plymouth PL5 3LZ, Devon.
Telephone: Plymouth (0752) 727773.
Telex: 45592. Grams: Sigjen, Plymouth.

WW—087 FOR FURTHER DETAILS

Binary counting

Explanations of terms used in today's techniques

by C. Jones

As digital techniques continue to spread to increasingly diverse applications so the ranks of those obliged to keep abreast of developments in logic design are swelling accordingly. It is lamentable that this area of most rapid change is also surrounded by the heaviest element of mystique, perpetuated to a large degree by excessive and often cynical use of jargon in much of the associated literature.

While it is true that current trends in logic design are quickly reflected in additions to the integrated circuit lists, there is a tendency for the various manufacturers to favour differing terminology when referring to what are, in fact, identical circuit types and functions. This is particularly marked in the case of the binary counter which, as the most versatile of the digital building blocks, has spawned so many variations.

Counters now attract such terms as "programmable", "variable-modulo", "parallel access", and "carry lookahead" while clocking arrangements are described as synchronous, asynchronous or even semisynchronous.

The implications of these and many other circuit descriptions are certainly of more than just academic interest and are considered in this review of current binary counting techniques.

Basic counting and the JK flip-flop. The basic counter arrangement Fig.1, which is included for the sake of completeness, consists of a chain of four JK edge-triggered bistables with the count pulse, or "clock", applied to the first stage only. Each successive stage accepts the (Q) output of the preceding one as a clock

pulse input and will change stage each time this preceding stage is reset.

Note that the leading (least significant) stage does not change state until the trailing edge of the clock pulse — this is a feature of the JK class of flip-flop which is the bistable most favoured in integrated logic design. The adoption of the JK flip-flop as the preferred micrologic bistable is based on the versatility obtained by combining the best features of alternative configurations to form one multipurpose design suitable for all applications.

Functional differences between the more familiar RS (set/reset) flip-flop and the JK type are illustrated by comparison of the truth tables (Tables 1 and 2). The troublesome indeterminate condition resulting from a "1" level being presented to both R and S inputs simultaneously is overcome in the JK arrangement by "back-priming" connections (Fig. 2) which force a straightforward change of state for the double "1" input condition. However, as the changeover will normally take place well within the width of the clock pulse the effect of simple back-priming connections will be to allow the circuit to tumble between one state and the other until the clock pulse ends. This problem is overcome by adopting the slightly more complex arrangement (Fig. 3) in which two RS flip-flops are connected in cascade with clock pulse inversion and gating in such a way that the second flip-flop (slave) is prevented from following the first (master) until the trailing edge of the clock pulse. In

effect, a delay has been introduced on the back-priming lines to prevent unstable operation.

It is this characteristic two-stage transfer action that has added the term "master/slave" to the JK flip-flop description in which J and K have been

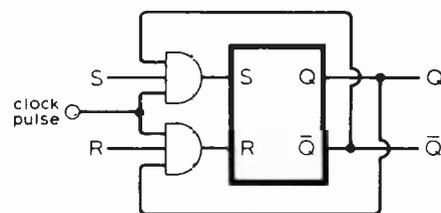


Fig. 2. Simple back-priming of RS flip-flop.

R	S	\bar{Q}' Q'	\bar{Q} Q
0	1	\bar{Q}' Q'	0 1
1	0	"	1 0
0	0	"	\bar{Q}' Q'
1	1	"	* *

Table 1. RS flip-flop.

K	J	\bar{Q}' Q'	\bar{Q} Q
0	1	\bar{Q}' Q'	0 1
1	0	"	1 0
0	0	"	\bar{Q}' Q'
1	1	"	Q' \bar{Q}'

* indeterminate
 \bar{Q}' Q' outputs before clock
 \bar{Q} Q outputs after clock

Table 2. JK flip-flop.

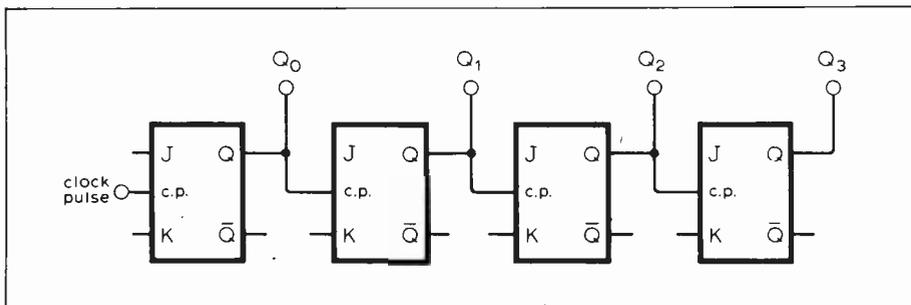


Fig. 1. Basic JK count chain.

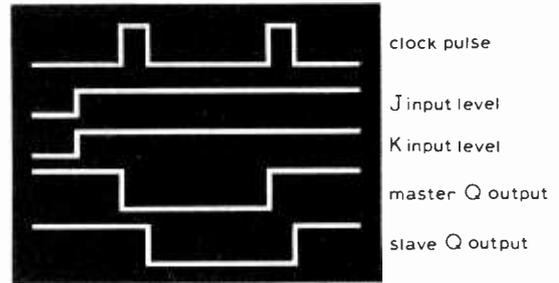
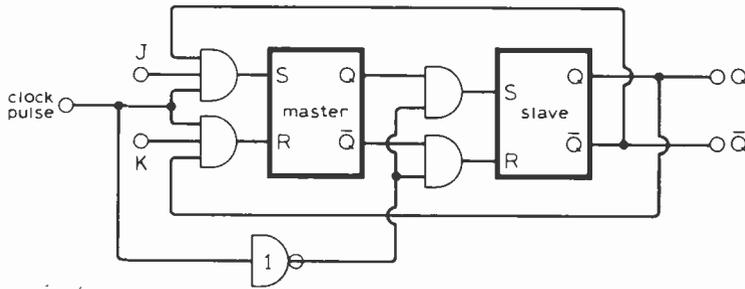


Fig. 3. JK (master/slave) flip-flop.

taken to correspond to S (set) and R (reset) respectively. In the binary counting application the J and K inputs of each stage are internally tied to the logic "1" level so that the required binary sequence is followed.

Reduced counts. When the internal organisation of the various counter types is studied it becomes evident that certain basic configurations have been generally preferred, mainly to ensure that each device meets the widest possible field of applications.

To this end it will be found that standard four-bit counters have no internal connection between the first and second stages and separate access is provided to the clock input of the second stage (Fig. 4).

By splitting the count chain into two distinct parts, three count modes are made available with an external connection required for the full division by sixteen. When operating in the split-count mode, the first and final three stages are able to function quite independently of each other in the divide-by-two and divide-by-eight modes, even when working at widely differing clock rates. However, as the reset-to-zero facility has not been similarly split the dual count mode is restricted to those applications which either do not use a reset or those that can tolerate common resetting.

The split-count method of providing for shortened counts is purely organisational and cannot be regarded as a true reduced count in the same way, as, for example, the decade counter which involves a premature reset-to-zero. Retaining the split-count format will now result in separate divide-by-two and divide-by-five modes or a full count which is held-down to ten.

The divide-by-twelve counter, although apparently similar to the decade format, has important functional differences which show clearly when the count patterns are compared. The

output lines of the decade counter are allowed to follow a true binary coded decimal (b.c.d.) progression from 0 to 9. By comparison, the method used to produce the divide-by-twelve count is a combination of premature resetting and count knock-on logic which, in effect, causes two count states to be skipped.

This forcing-on technique inevitably results in count patterns appearing at the output pins which do not accurately relate to the true count. The sequence diagram (Fig. 5) shows that this occurs during the second half of the count cycle with counts 6 and 7 being skipped and the reset being forced at the appearance of 14. The divide-by-twelve counter is therefore unsuitable for the direct driving of count displays any further than the 50% duty cycle point.

Synchronous working. The counting scheme so far outlined (Fig. 1 and 4) in which the clocking pulse is applied to the first stage only is generally known as ripple or asynchronous counting and is only acceptable provided that speed of operation is not of primary importance. If, however, the total count length has been greatly extended by a stringing together process, then the time taken for a resetting edge to "ripple" through the entire counter length could well prove to be prohibitive. This would apply particularly to uses in which various processing steps are initiated or otherwise controlled by the count sequence, and would therefore need to be inhibited for a period at least equal to the worst-case settling time following each clock pulse.

The time penalty involved in avoiding the effect of spurious counts during settling is largely overcome by the technique of synchronous counting, in

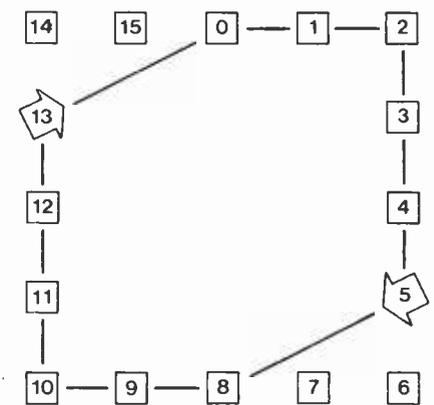


Fig. 5. Divide-by-twelve sequence diagram.

which all stages are clocked simultaneously but via interstage gating (Fig. 6). The steering gates ensure that the clock pulse only reaches those stages having a full count in the preceding (less significant) positions. By this method all change-of-state switching is synchronised with the trailing edge of the clock pulse with no false count patterns appearing between one condition and the next.

Semisynchronous format. The split-count configuration in which the first and second stages are not internally coupled cannot be combined with fully synchronous working but results in a hybrid action classed as semi-synchronous (Fig. 7). With the external link in place the second, third and fourth stages do not receive the clock pulse direct but are simultaneously clocked by the output of stage A. The only difference, therefore, between full and semi-synchronous working is the switching time of the first stage.

Group carries in synchronous counting. Providing for synchronous operation over a four-bit counter is perhaps deceptively simple due to the functionally straightforward nature of the clock steering logic. In fact, a problem still exists in providing a system arrangement which will allow something approaching true synchronous operation when a number of packages are cascaded to form an extended chain. Although functionally straightforward, the clock gating commitment for synchronous working rapidly becomes unwieldy as the number of stages

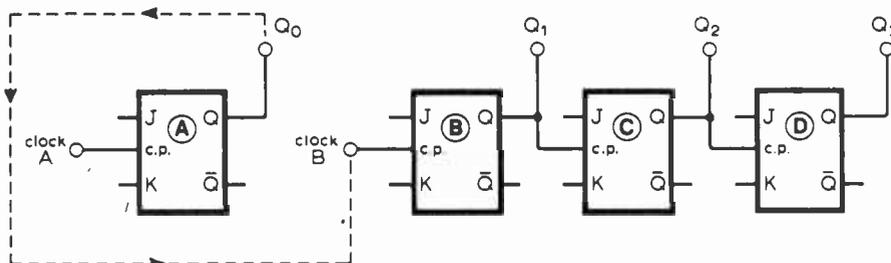


Fig. 4. Split count chain.

increases so that even the improved package count lengths of l.s.i. do not provide an altogether effective answer.

Advancing the count state from one package to the next is referred to as a "group carry" and the design requirements of the synchronous counter will always include additional gating to generate the group carry signal for use by the following counter group(s). The group carry output will be typically labelled by different manufacturers as "terminal count", "ripple clock" or simply "carry", but in each case will be the product of a full (terminal) count condition plus the group carry level from the preceding counter.

The resulting scheme (Fig. 8) provides a reasonable compromise in counting speed but one which still imposes a heavy restriction on the maximum count rate possible. The restricting factor hinges on the series enabling line only being held active for the time that the first (least significant) counter is actually holding a full count. This allows only one clock period for the group carry to propagate (trickle) through to the final group(s) as the total count reaches the full reset point. Any carry operation not completed before the arrival of the next clock pulse will, of course, result in a false count.

Greater group carry speed is possible using a modified version of the trickle method (Fig. 9) but one that requires each counter to include an additional enable input which controls only the clock pulse and not both clock and carry output. The least significant counter is now only permitted to control the clock enabling of the remaining counters via this additional input, which is usually labelled "parallel enable" as distinct from the trickle (series) enable. It is now the full count of the second package that has the longest trickle path forward but with the complete count cycle of the least significant counter effectively acting as a time buffer.

To remove the remaining restriction on count rate would require external "look ahead" logic, probably in the form of carry look-ahead packages which are actually intended for the generation of fast carries in parallel adding schemes and can operate in a similar manner across blocks of four counter packages.

Reversed counting and parallel access.

As the counting down process is invariably concerned with the reduction of a preset count level to zero rather than with a repetitive count cycle, it would be most unusual for the reverse count feature to be incorporated into the design of a counter without a parallel loading facility also being included. The resulting combination offers the convenience of being able to force the count to any desired state independently of the clock style (asynchronously) and for the count to then continue up or down from this point.

A reducing count sequence will be obtained if the "reset" output of each flip-flop is used as the clocking line (ripple), or clock controlling influence (synchronous) in place of the "set" outputs. The reversible, or up/down counter, must therefore include both types of interstage connection with either one or the other enabled to decide the direction of count.

Two types of direction control logic are used: the dual clock method in which separate clock inputs control the count direction, or the single clock scheme with direction being selected by a separate up/down control line (Fig.

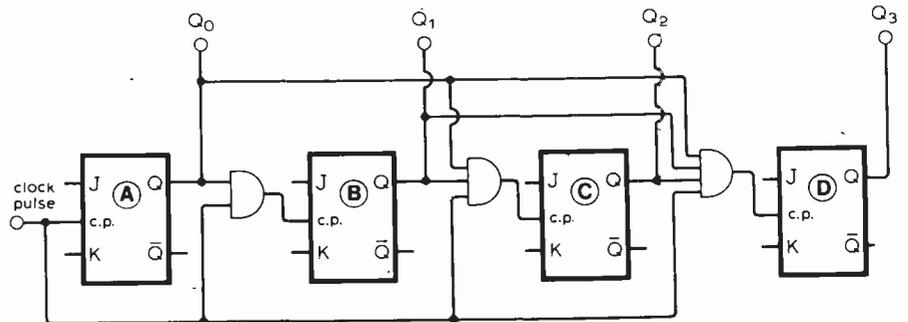


Fig. 6. Four stage synchronous clocking.

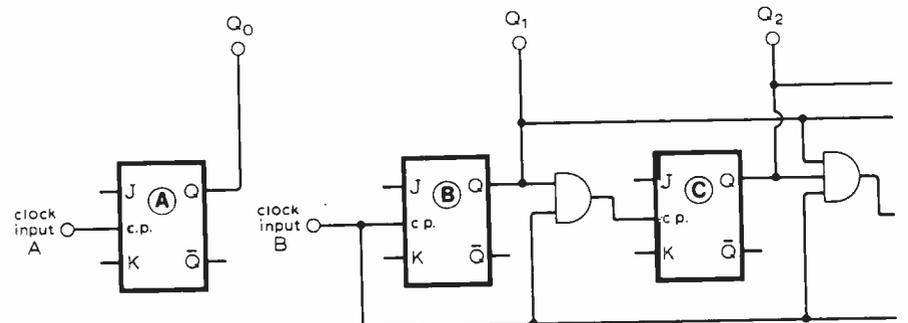


Fig. 7. Semi-synchronous format.

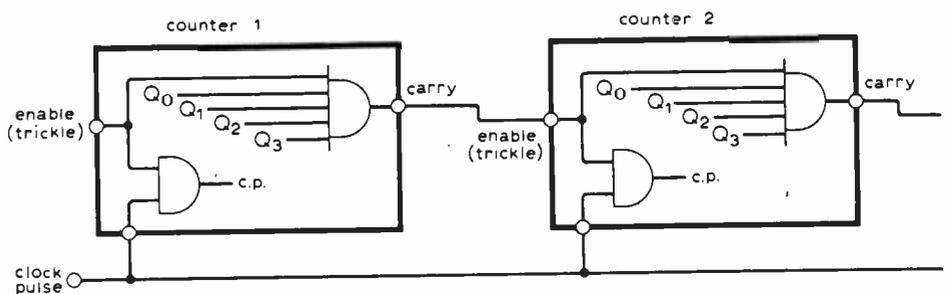


Fig. 8. Trickle group carry scheme —skeleton logic.

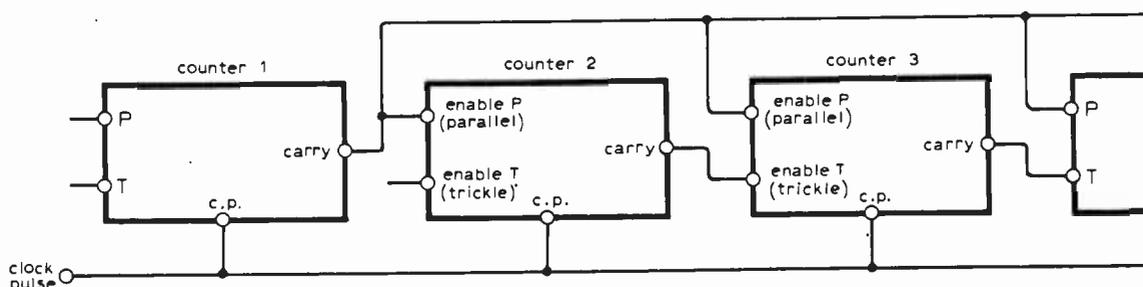


Fig. 9. Group carry scheme —fast.

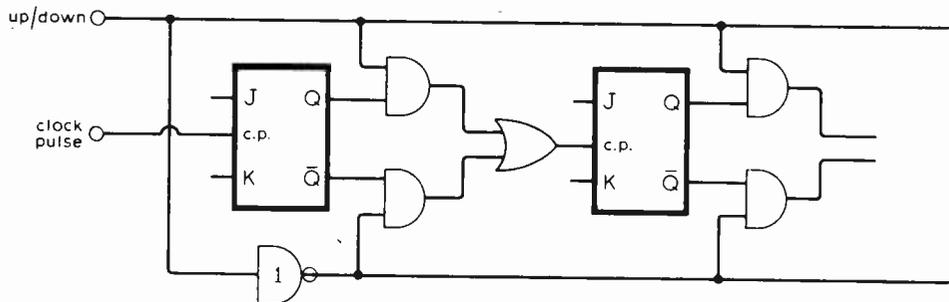


Fig. 10. Reversible count logic—single clock.

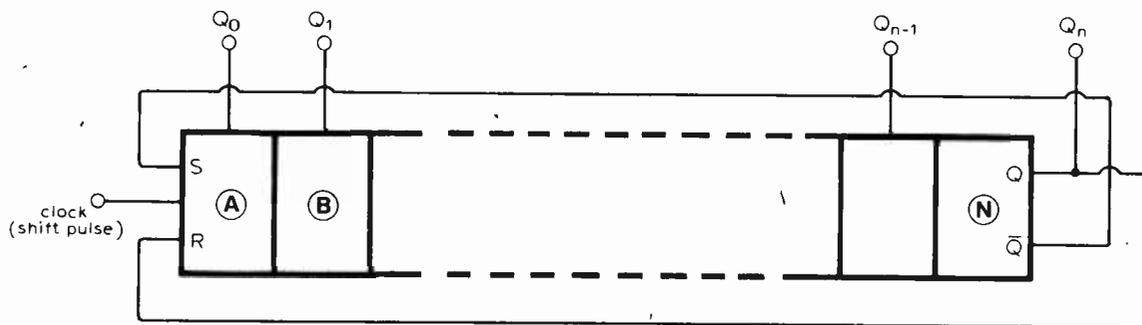


Fig. 11. Basic Johnson counting.

TABLE 3

count	stage outputs				two input octal decode
	Q ₀	Q ₁	Q ₂	Q ₃	
0	0	0	0	0	$\bar{Q}_0 \cdot \bar{Q}_3$
1	1	0	0	0	$Q_0 \cdot \bar{Q}_1$
2	1	1	0	0	$Q_1 \cdot \bar{Q}_2$
3	1	1	1	0	$Q_2 \cdot \bar{Q}_3$
4	1	1	1	1	$Q_0 \cdot Q_3$
5	0	1	1	1	$\bar{Q}_1 \cdot Q_2$
6	0	0	1	1	$\bar{Q}_0 \cdot Q_1$
7	0	0	0	1	$\bar{Q}_2 \cdot Q_3$

Table 3. Four-bit Johnson count sequence.

10). Both methods are straightforward in operation but result in slightly different cascading arrangements.

The cascading requirement for a reducing count is virtually identical to that of the forward count but the group carry function now becomes a "group borrow" and must reflect zero count states rather than the full counts of a carry line. Use of the dual clock method of direction control dictates separate carry and borrow lines which are controlled by the appropriate up or down clock input. Alternatively, the single clock system allows both carry and borrow functions to share a common "max/min" output which is quite independent of the clock line and which signals the full or zero condition as selected by the count direction (up/down) input.

In addition to the max/min output it is common to have a "ripple clock" output which allows the equivalent of the trickle group carry scheme, while fast operation is possible by using the max/min output in conjunction with external look-ahead logic.

From the crop of exotic-sounding circuit descriptions used to refer to the parallel loading facility, those most likely to be encountered are the terms "parallel entry", "parallel access", "side-loading", "programmable" or "presettable". All are used to describe the arrangement in which a set of inputs, under the control of a "data load" line, may over-ride an existing bit pattern by forcing each count stage to follow its appropriate parallel data input. This load function can be referenced to the clock cycle for synchronous working or be left to operate in the more flexible asynchronous mode.

Variable modulo. The terminal (full) count output of the synchronous counter is especially useful in serving as the data load input when forming a variable count length without the need

for external sensing logic. The count length of the resulting variable-modulo configuration is equal to the normal full count, minus the bit pattern set up on the parallel data lines and to which the counter resets. In this manner, a continuously variable count length is possible by manipulation of the data input lines.


Purpose designed variable-modulo counters use various methods of modulo selection and often no individual stage outputs are provided, particularly when the maximum count length is extremely long. In these instances output information is limited to a single divide-by-N pin which flags the terminal count condition.

Johnson counters. Octal and decade counter/dividers in which a four or five stage Johnson format is used as a basis for obtaining a set of linear spike-free outputs are now quite common. Basically a ring counter, the Johnson sequence follows the bit pattern of a back-primed shift register with the clock input acting as the shift pulse (Fig. 11). Decoding each count state of the Johnson sequence (Table 3) to produce a linear one-of-eight or one-of-ten output is particularly straightforward and involves a simple two input gating function for each linear output line (Fig. 12).

The advantages of this type of counter are the high speed operation resulting from not having to follow true binary 1,2, 4, 8 code and the spike-free outputs taken via decoding gates.

Unlike standard binary counters, the Johnson counter must be guarded against unwanted codes which, once established, lock "holes" into the

Fig. 12. Johnson-based counter/divider (octal).

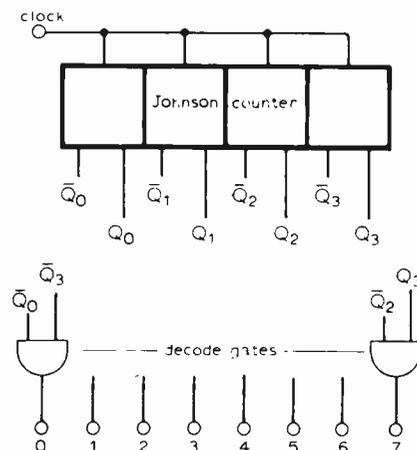

sequence with the inevitable output errors. It is also possible for certain types of Johnson logic to lock up completely in some circumstances and anti-lock logic is necessary to ensure that only valid codes can exist.

Tomorrow's counters. As fuller use is made of the high density logic families so the present building-block approach to digital system design will take on a more concealing blackbox character. For the counter, this trend will not be restricted to extending package count lengths but will result in much decoding and look-ahead logic being included as part of the counter packaging. A current forerunner to this level of inclusive counter logic is the full four decade counter with a single time-shared b.c.d. output, and the variable modulo concept has now been taken to the stage where the maximum divide-by-N factor equals 16,000.

As the existing logic families expand and new lists appear so the task of technical monitoring becomes more unmanageable but at the same time even more vital. Hopefully, keeping tabs on state-of-the-art counting techniques will at least go some way in maintaining a foot in the door of the digital skyscraper.

Commercially available i.c. counters grouped under general function headings

BASIC ASYNCHRONOUS COUNTERS (RIPPLE CLOCK)

	TEXAS	MULLARD
4 bit binary	SN7493	FJJ211
decade	SN7490	FJJ141
divide by 12	SN7492	FJJ251

SYNCHRONOUS COUNTERS (PRESETTABLE)

	TEXAS	MULLARD
4 bit binary	SN74161	FJB9316
	SN74163	
decade	SN74160	FJB9310
	SN74162	

REVERSIBLE COUNTERS (SYNCHRONOUS)

	TEXAS	MULLARD
4 bit binary	SN74191	FJB9366
	SN74193	
decade	SN74190	FJB9360
	SN74192	

ASYNCHRONOUS PRESETTABLE COUNTERS

	TEXAS	MULLARD
4 bit binary	SN74177	FJB93177
decade	SN74176	FJB93176

VARIABLE MODULO COUNTERS

	RCA	MULLARD
4 bit binary	---	FJB9305
four decade	CD4059 (cmos)	---

JOHNSON-BASED COUNTER/DIVIDERS (CMOS)

	MOTOROLA	NATIONAL
octal	MC 14022	MM 4622A
decade	---	MM 4617A

Semiconductor developments

Power f.e.t. and improved bi-polar transistor

Audio power f.e.t.s were first reported in *Wireless World* in June 1974. These devices were developed by Yamaha under a commission by Japan Technology Development Foundation. At the same time, Sony started a separate line of development concerned with power f.e.t.s and as a result produced versions which differed in detail from the Yamaha device. Interestingly, Yamaha produced only one polarity of f.e.t., the n-type f.e.t., whereas Sony developed complementary pairs. The structure of the Sony f.e.t. is shown in Fig. 1 and consists of a drain of n⁺ doped silicon mounted on a substrate, a grid of p⁺ gates diffused into n⁻ drain area and a source also selectively diffused through the inner silicon oxide layer between the grid of the gate. The structure is completed by a metal connecting bridge to the gate and the source. The complete chip of the power f.e.t. is 3mm square and has approximately 1500 rectangular source areas. The complementary version of this f.e.t. is produced by reversing the polarity of the impurities used in each layer.

The difference between this device and the Yamaha device reported earlier appears to be largely one of detail design, and also of power dissipation. The Sony devices are rated at considerably lower powers than the Yamaha versions, the former having a total dissipation of 63 watts for both types.


Fig. 2 shows the output characteristics of two power f.e.t.s, showing a strong resemblance to the characteristics of a triode valve. These devices are known as vertical f.e.t.s (v-f.e.t.) because current flows from the substrate area through the thickness of the chip to the metal connections at the top. The advantages to be obtained

through this form of construction are a greater current density, coupled with a high input and low output impedance characteristic. Other advantages claimed for the v-f.e.t. are a fast pulse response originating from the low capacitance due to the thick insulating layer separating the source from the drain, and a voltage rather than a current controlled response.

In a paper presented to the AES at the recent 50th Convention, a speaker reported on the characteristics of two devices developed and used by Sony, the 2SK60 and the SJ18. These are complementary power devices with a voltage amplification factor $\mu = 4-5$, a mutual conductance, $g_m = 250\text{mS}$, and an output resistance $R_D = 16\Omega$. Unlike its bi-polar counterpart, the v-f.e.t. has no area of second breakdown and this, coupled with its extremely fast switching response, indicated to the equipment designers that it was particularly suitable for a Class B or similar power output stage.

Several power amplifiers have been designed by Sony using these v-f.e.t.s. However, only two have appeared here in the UK, these being mentioned above. The version described in the AES paper mentioned is not available yet in the UK, though it is believed that the design techniques described are similar to the models now available. The model described is the TAN-8550 power amplifier which utilises three n-channel and three p-channel devices in parallel, complementary arrangement to produce a 100 watt per channel output into an 8 Ω load at any frequency in the audio

Fig. 1. A cross-section of the Sony v-f.e.t.

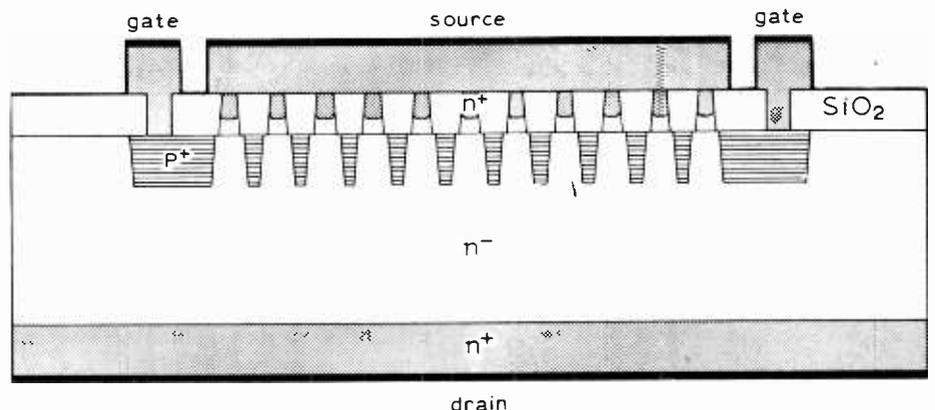

spectrum. The output stage is driven from a Class A stage consisting of three direct coupled differential amplifiers. The total open loop gain of this circuit is approximately 82dB with a distortion that has been held to below 1% over the audio spectrum, before negative feedback is applied.

In designing the v-f.e.t. power stage, two alternatives offered themselves, the first of which was a source follower, the second being a drain follower. The source follower suffers from a gain loss by the amount of the offset bias potential; the drain follower circuit provides a gain proportional to the amount of the actual amplification factor μ_R . The main disadvantage of the drain follower is that the power supply voltage needs to be rather higher than that for source follower. A simplification of the bias circuit is obtained by using the source follower design and this in fact is a version used in the Sony TAN-8550 amplifier. The open-loop frequency response extends to a roll-off point of about 35kHz before negative feedback is applied. This initial wide frequency response is said to bring an improved transient intermodulation performance, an improved stability and a reduced high order harmonic distortion, compared with a similar bi-polar output stage.

There appeared to be some disadvantages to the use of v-f.e.t., these being principally associated with the values of voltage required from the power supplies. In the case of the Sony

amplifiers at least three supply rails are provided, and, in addition, the idling current in the output stage produces a high order of power dissipation in the static, no-signal condition. In one amplifier designed by Sony, the static dissipation is in the order of 65 watts for a 100 watt amplifier.

A further disadvantage of the type of design approach utilising the parallel arrangement of output devices is that should one break down and require replacement, the complete six need replacement since the six v-f.e.t.s are matched in characteristics.

Sony have also produced a lower powered version of the v-f.e.t. which is used elsewhere in voltage amplification stages in at least one of their v-f.e.t. amplifiers.

A second semiconductor device developed by Sony and used in some of their v-f.e.t. integrated amplifiers is known as the l.e.c. bi-polar transistor. The abbreviation l.e.c. stands for low emitter impurity concentration, which describes in elementary form the structure of the emitter area of what is otherwise a conventional bi-polar transistor. In a recent paper the Sony engineers described the general design of the l.e.c. device, which appears to have arisen from a study designed to investigate the noise characteristics of small signal transistors.

Conventional transistors, in order to obtain a high emitter efficiency have a higher emitter impurity concentration than that of the base region. The reason for this is to keep the value of the injected minority carrier current from the base into the emitter as low as possible. Any attempt at reducing the emitter impurity concentration below that in the base results in a reduced emitter efficiency because there is an increase in the ineffective minority carrier current being injected into the emitter which is inversely proportional to the emitter concentration.

The l.e.c. transistor does not suffer from this disadvantage because the emitter region is double diffused to produce a secondary junction. This junction divides an area of high emitter impurity concentration from an area of low emitter impurity concentration and thus is an n+n or a p+p junction. The purposes of this barrier is to reflect unwanted minority carriers injected into the emitter and thus retain higher emitter efficiency.

The n+n junction is not the only type of barrier which is capable of reflecting injected minority carriers. Other barriers listed in the original paper are as follows; surface barrier, m.i.s. (sic) barrier, p-n junction barrier, hetero-junction barrier and the Schottky barrier. An example of one application of the m.i.s. barrier application is where a metal gate device with such a structure, is designed to control the surface recombination velocity and thus the gate so formed can change the

amplification factor by changes in its bias.

However, the l.e.c. transistor described has the singular advantage of having high current gain with very low noise and in particular the flicker noise and burst noise is reduced below that normally found in conventional bi-polar devices.



Doppler shifts analyse Chinese ceramics

The aesthetic appeal of ancient Chinese ceramics is enhanced by their coloured glazes which are found in a variety of forms with names such as Tea Dust, Coral Red, and Mirror Black. It would be of interest to know how the potter produced these effects — without destroying the specimens in the course of finding out.

A step in this direction has been made at the Research Laboratory for Archaeology and the History of Art at Oxford. R. E. M. Hedges reports some preliminary work on measurements based on Mössbauer spectroscopy. This applies an effect, discovered by Mössbauer in 1957, concerned with the way in which very short electromagnetic waves (gamma rays) are emitted and absorbed by crystalline substances. The processes of emission and absorption are tremendously frequency-dependent, and each element has characteristic frequencies. For iron, the selectivity of the effect corresponds to a Q-factor of about 3 million million. The frequency of emission is slightly different from the frequency of absorption, and because of the high Q the emission frequency falls outside the absorption passband. The emission and absorption frequencies can however be made to coincide by moving the emitter relative to the absorber, so that the emission frequency is Doppler shifted by the right amount. This is the basis of Mössbauer spectroscopy. If a specimen is believed to contain a certain element, its absorption of the gamma rays from a moving emitter is measured. By changing the velocity of the emitter different absorption peaks can be tuned in. The interest to the physical chemist lies in the fact that the shape of the frequency response is modified by the way in which the element is chemically bound in a crystal. This enables the structure to be deduced and, in the case of the Chinese glazes, makes possible intelligent guesses about the original production processes.

The work done at Oxford so far used iron-containing glaze ground off the surface of pieces of broken china (sherds) but an improved instrument, now under construction, based on reflection rather than absorption should enable non-destructive measurements to be made, and with luck reveal the secrets of the potters' techniques.

Fig. 2. Output characteristics of two complementary v-f.e.t. devices.

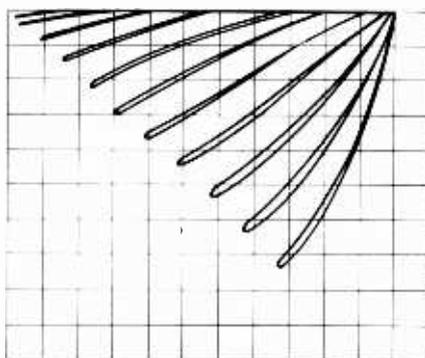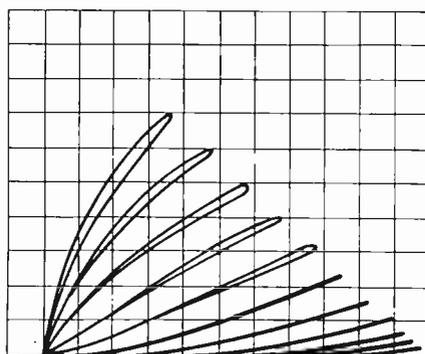

$I_D = 0.5 \text{ A/div}$ (vertical scale)
 $V_{DS} = 5 \text{ V/div}$ (horizontal scale)

Electronic systems — 4

More about modulation and transmitting signals

by W. E. Anderton *Assistant Editor, Wireless World*



Further considerations in an amplitude modulation system include the depth of modulation. We must not over modulate the carrier as this would be like asking for more than full output or less than no output and the effect would be to distort the transmitted and thus the received signal. Fig.1 illustrates this principle with examples of the waveforms expected for 0%, 50%, 100% and more than 100% modulation.

Figure 1 also shows the quantities which must be measured in order to calculate the depth of modulation. The amplitude labelled *b* represents the mean carrier level, i.e. the unmodulated carrier amplitude. The quantity labelled *a* is the peak modulation amplitude on the resultant modulated carrier. Depth of modulation is given by the relationship $\text{depth of modulation} = (a/b) \times 100\%$.

If we examine the case where $a = b$ then we can see that the carrier will be 100% modulated.

Spectrum of an a.m. signal

The transmitted signal involves multiplication of the carrier and modulating signals. The multiplication process produces a complex output signal which contains the sum and difference frequencies of the two input signals. If we are to transmit the baseband speech signal previously described, the sum and difference components will form two bands of frequencies on either side of the carrier frequency. These bands of frequencies are known as "sidebands", each of them having a bandwidth equal to the bandwidth of the modulation signal.

If our a.m. system is to transmit baseband signals up to 4kHz, then each sideband will have a bandwidth of 4kHz. The total bandwidth of the transmitted signal (accounting for both the upper and lower sidebands) will be 8kHz. The spectrum of such a system is shown in Fig.2.

Channel allocation

The long-wave and medium-wave amplitude-modulated broadcast bands have all been split into 9kHz channels.

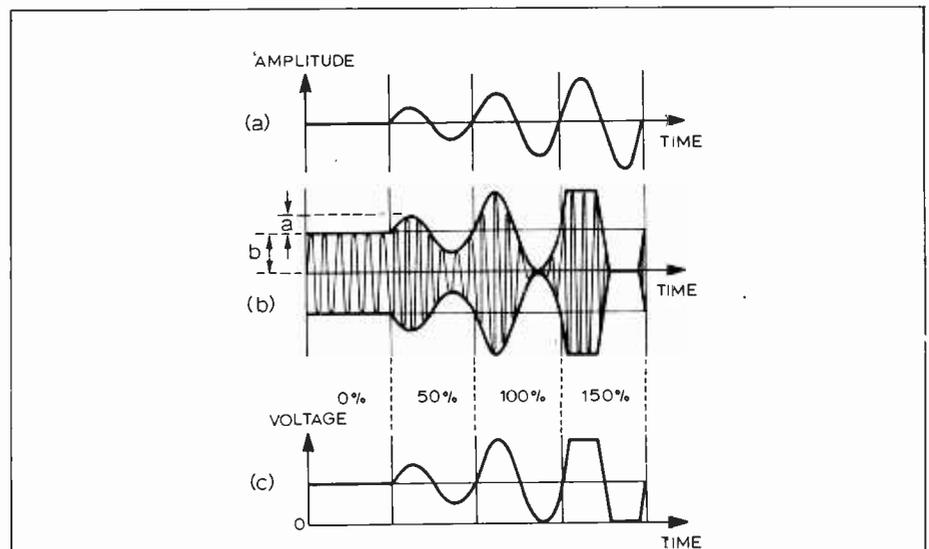


Fig. 1. Illustrating the meaning of modulation depth in an amplitude modulated system with examples of the waveforms expected for 0%, 50%, 100% and more than 100% modulation.

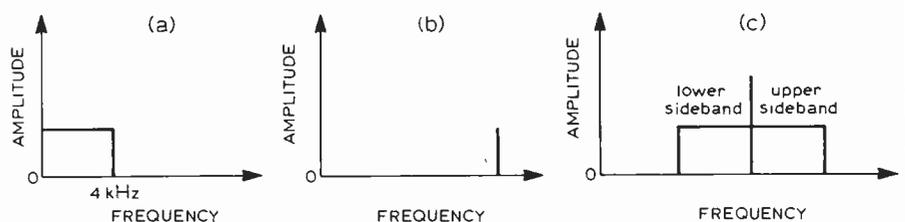


Fig. 2. Spectrum of an a.m. system which is to transmit baseband signals up to 4kHz.

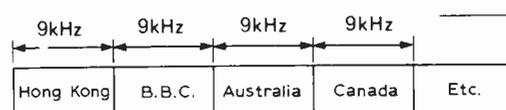


Fig. 3. Type of allocation of channels one might expect over a small portion of the medium wave band.

Each radio station is allocated a channel in which it is allowed to transmit so that each of these stations is located at an allocated frequency in each band. Now, because the channel bandwidth is only 9kHz, each station can only transmit baseband signals up to the maximum of 4.5kHz. If a station were to transmit outside its allocated channel, the people receiving adjacent channels would experience interchannel interference. In an attempt to alleviate this problem, adjacent channels are allocated to stations as far removed geographically, from one another as possible. Figure 3 indicates the type of allocation of channels one could expect over a small portion of the medium wave band.

Advantages and disadvantages of am.

One of the main advantages of an a.m. transmission system is that it is simple both in design and implementation at both the transmitter and the receiver, making the system relatively cheap to operate and maintain.

The disadvantages of the a.m. systems are all concerned with quality of reception. We started this section by describing how early experiments were conducted using spark transmitters (now illegal, incidentally). All sparks cause propagation through space on a wide range of frequencies and hence amplitude-modulated systems are subject to impulsive, wideband noise. Impulsive noise can be generated by arc ignition systems, electric motors, arcing switch contacts, etc. The received impulsive noise is so intrusive in some locations as to make concentration on the received programme extremely difficult.

The second disadvantage is again concerned with quality; this time it is the low bandwidth which is considered an impairment. Two sidebands are accommodated within a narrow channel and transmitted bandwidth is necessarily limited.

Frequency modulation

Frequency modulation (f.m.) was developed in an attempt to overcome the limitations of an a.m. system. The transmitter again supplies a sinusoidal voltage to an aerial, but this time the frequency of the sinewave varies in sympathy with the modulation signal, the amplitude of the transmitted signal being kept constant (see Fig.4, part 3, April issue). The receiver is designed in such a way that the demodulated output is insensitive to impulsive amplitude changes of the carrier wave.

When there is no modulation signal, the carrier wave is at a fixed frequency. The modulation signal causes a frequency deviation of the carrier and this deviation is proportional to the instantaneous amplitude of the modulation signal.

The spectrum produced by this f.m. signal is extremely complex. Mathema-

This series of articles is based on a proposed Advanced Level course for schools and is prepared in consultation with Professor G. B. B. Chaplin, University of Essex. The next article will deal with reception and demodulation.

tical analysis shows that there exists an infinite number of sidebands, each one of less amplitude than the previous one. To achieve full modulation in the receiver one can argue that you would require to transmit and receive a signal of infinite bandwidth, but in practice, it is found that the bandwidth required is given by $2(f_d + f_m)$ where f_d is the maximum deviation frequency and f_m is the maximum modulation frequency. If we remember that lack of baseband available bandwidth was one of the criticisms of an a.m. system, then our f.m. system must attempt to improve this situation. Very high frequency f.m. transmissions can be modulated at up to at least 15kHz and achieve a quality comparable to hi fi record reproduction.

The bandwidth required to transmit a broadcast f.m. signal is greater than 100kHz; consequently f.m. stations are only found on the v.h.f. band where these large bandwidths can be accommodated. (The v.h.f. f.m. band, known as Band II, is from 87 to 10MHz). The v.h.f. transmissions have a disadvantage in that the transmitters and receivers are complex and thus relatively expensive. Coupled with this disadvantage is also the fact that v.h.f. transmitters have a limited range, often no more than about 50 miles. Thus more transmitters are required to provide national coverage than would be the case with an a.m. system.

Contrast of a.m. and f.m.

In a.m. the amplitude of the carrier is varied, whereas in f.m. the carrier frequency is varied. Frequency modulation gives a much better signal-to-noise ratio than a.m. under similar operating conditions. Frequency-modulated systems are usually more sophisticated and expensive than a.m. systems.

Appendix 1

Derivation of a.m. sidebands. Let the modulation signal be represented by

$$V_{mod} = \cos A$$

and the carrier be represented by

$$V_c = \cos B$$

Modulation will be the product of the two input signals plus a function representing the carrier itself. Thus the output (the transmitted signal) is

$$V_{out} = \cos B + k \cos B \cos A$$

where k is a constant chosen to ensure that the expression $1 + k \cos A$ never becomes negative. Alternatively,

$$V_{out} = \cos B + (k/2)(\cos(A-B) + \cos(A+B)).$$

Appendix 2

Representing the f.m. carrier wave. To obtain an expression for an f.m. wave, let the instantaneous carrier wave be represented by

$$v_c = V_c \sin \omega_i t = V_c \sin 2\pi f_i t$$

where f_i is the instantaneous frequency. For a positive increase in frequency we have

$$f_i = f_c + \Delta f_c \sin \omega_m t$$

where f_c is the carrier frequency and Δf_c is the frequency deviation of the carrier wave due to the modulating signal of frequency f_m .

If the instantaneous carrier phase is Φ_i , then

$$\frac{1}{2\pi} \frac{d\Phi_i}{dt} = f_i = f_c + \Delta f_c \sin \omega_m t$$

$$\text{or } \frac{d\Phi_i}{dt} = 2\pi f_i = \omega_c + 2\pi \Delta f_c \sin \omega_m t.$$

By integration and a correct choice of the phase angle, we obtain

$$\Phi_i = \omega_c t - \frac{\Delta f_c}{f_m} \cos \omega_m t$$

or

$$\Phi_i = \omega_c t - m_f \cos \omega_m t$$

where $m_f = \Delta f_c / f_m$ is called the modulation index. Since $v_c = V_c \sin \Phi_i$ we obtain

$$v_c = V_c \sin \omega_c t - m_f \cos \omega_m t$$

which represents an f.m. carrier wave.

This article was prepared in consultation with Professor G.B.B. Chaplin, University of Essex.

Further reading

Obtainable from Mr. R. A. Smith, Department of Electrical Engineering Science, University of Essex, Wivenhoe Park, Colchester CO4 3SQ, Essex, are the teaching texts for the electronic systems pilot A-level course, price £4.50; communication systems section only, £2.00; computer systems section only, £2.00; feedback systems section only, £2.00; basic electronics section only, £1.50.

Teletext at Birmingham

Our demonstration of teletext at the IEA/Electrex exhibition during May was not an undiluted success and for this we apologize to those people who went to the exhibition for the express purpose of seeing the decoder. We were rendered *hors de combat* by an obscure fault in the television receiver and were unable to either rectify it or obtain another, modified receiver in time to go on with the demonstration, in spite of rapid assistance from the set makers.

Correction

In the article "Some factors in loudspeaker quality" by H. D. Harwood, May 1976, reference & should be accredited to D. E. L. Shorter and A. Gee.

New Products

IEA New Products

Seen at the IEA/
Electrex exhibition,
Birmingham 1976

Digital counter

A range of low-cost digital frequency meters was one of the highlights of the Marconi Instruments stand. The meters, designated TF2430, TF2431 and TF2432, cover the ranges 10Hz to 80MHz, 10Hz to 200MHz, and 10Hz to 560MHz respectively. Large-scale-integration component design and automatic production methods have enabled the instruments to be manufactured for reliability, and at low cost. Frequency measurements are made directly, requiring no prescaling, and switching allows a maximum resolution of 0.1Hz. A feature of this range of meters is the simplicity of design. Each instrument has as few controls as possible and incorporates automatic gain control on the input channel, which will accept from 10mV to mains voltage, to cut out the need for a sensitivity control. The readout, which is in the form of a l.e.d. display, is operated from a memory so

IEA

that only the last measured value is displayed and the blur of the digits during counting is avoided. This facility, together with an in-built leading-zero suppression, ensures that the meter is easy to read. Attention has been paid, during design, to the construction and layout of the meters to give good servicing accessibility. Marconi Instruments Ltd, Longacres, St Albans, Herts AL4 0JN.

WW 301 for further details

Programmable power supply

Two digitally programmable power supplies, types GXP25/25 and GXP10/50, were among the major items displayed by Gresham Lion Ltd. These power supplies provide outputs which may be controlled by a binary-coded-decimal logic input. Type GXP25/25 has a range up to 24.975V and 2.475A, and minimum settings of 25mV and 25mA. The GXP10/50 covers a range up to 9.99V providing up to 4.95A. Minimum settings for the GXP10/50 are 10mV and 10mA. The input, which can accept up to 50V without damage, is by standard p.c.b. connector. Gresham Lion Ltd, Twickenham Road, Feltham, Middlesex TW13 6HA.

WW 302 for further details

Low cost oscilloscope

The model 4S6-LS oscilloscope has a vertical amplifier sensitivity of 10mV/cm with a 6MHz bandwidth and an accuracy of $\pm 5\%$. A major difference between the 4S6-LS and previous models is in the timebase sweep range which has been extended to 1s/cm at $\pm 5\%$ accuracy. To ensure that the oscilloscope produces a good display with the low-speed sweep a P7 long-persistence cathode ray tube is fitted as a standard. As an optional extra the c.r.t. graticules may be treated with Glarecheq, a non-reflective acrylic


IEA

coating which helps to reduce the amount of reflection from the screen. At the time of release the oscilloscope, treated with Glarecheq, was priced at £106. Scopex Instruments Ltd, Pixmore Industrial Estate, Pixmore Avenue, Letchworth, Herts SG6 1JU.


WW 303 for further details

Programming aids

A collection of programming aids for microprocessor systems design were exhibited by Osprey Electronics Ltd. The aids, produced by Stag Electronic Designs Ltd, offer a system which, it is claimed, avoids the problems of time consumption and inconvenience resulting from the large number of changes and trial runs inevitable in software development. Each system may consist of a range of r.o.m. and p.r.o.m. simulators, a simulator programmer, a p.r.o.m. eraser, and a p.r.o.m. programmer. Pin-compatible simulators are available for the 1702, 2704 and 2708 series of ultra-violet erasable p.r.o.ms.

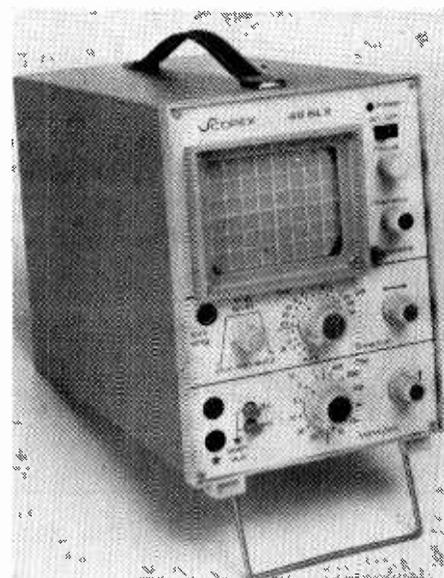

WW 303 for further details

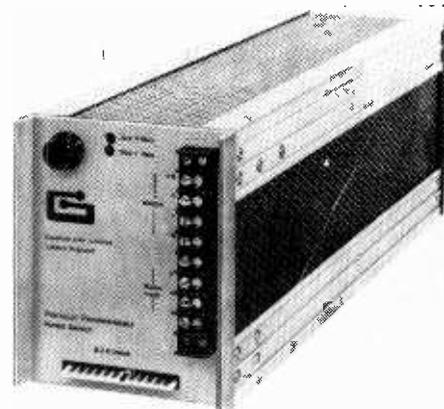

WW 302 for further details



WW 301 for further details


IEA

as well as an equivalent of the Motorola MCM6830L mask programmed r.o.m. The SP2 simulator programmer is a manually operated data entry device capable of programming any of the Stag range of p.r.o.m. or r.o.m. simulators. This programmer can be used to modify individual locations or load complete programmes – by keyboard for data entry and by thumbwheel switches for address selection. Two p.r.o.m. erasers suitable for electronically programmable r.o.ms are available, the SE4 which will take four p.r.o.ms and the SE15 with a capacity for 15 p.r.o.ms. The p.r.o.ms are placed in a tray, within the eraser, and are then exposed to high intensity ultra violet light for a prescribed time, preset on a timer dial. Two p.r.o.m. programmers exist, the PP2 for the 1702 series and the PP8 for the 2704 and 2708 series. These programmers are suitable for electrically programmable r.o.ms and are capable of transferring master p.r.o.m. or simulator data directly into a p.r.o.m. Stag Electronic Designs Ltd, Northaw House, Potters Bar, Herts EN6 4PS.

WW 304 for further details



WW 304 for further details

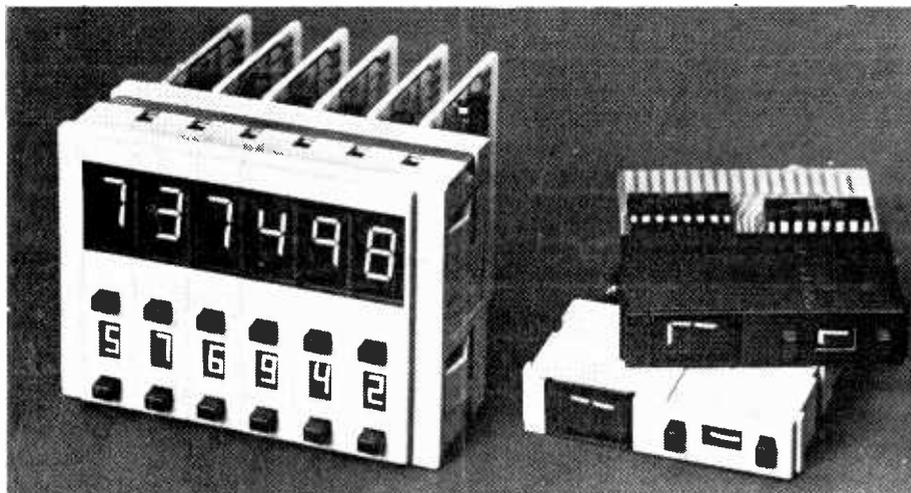

WW 309 for further details

IEA

Multimeters

The **Dolomiti** has 39 ranges and measures current, voltage, resistance, capacitance and decibels. This meter has a sensitivity of 20k Ω /volt, with an accuracy of $\pm 2.0\%$ on d.c. ranges and $\pm 2.5\%$ on a.c. and resistance ranges. Operating frequencies on the a.c. ranges are from 20Hz to 20kHz. The meter, which measures 130 x 125 x 40mm, requires two 1.5V batteries and one 22.5V battery and incorporates diodes, a cutout and a fuse for automatic overload protection. Optional extras include a 30kV probe and a signal injector. Carlo Gravazzi (U.K.) Ltd, North Crawley Road, Newport Pagnell, Bucks, MK16 9HF.

WW 305 for further details

Avometer model 73 is a pocket sized multimeter measuring up to 750V and up to 3A on both a.c. and d.c. ranges. On resistance ranges the meter will measure up to 20M Ω using internal batteries. This meter has a sensitivity of 20k Ω /volt d.c. and 1k Ω /volt a.c. and an accuracy of $\pm 2.5\%$ on direct voltage

IEA

and current ranges. On a.c. ranges the **model 73** will operate on frequencies up to 75kHz. Fuse protection allows the application of up to 250V r.m.s. for 10 seconds on any range. Avo Ltd, Archcliffe Road, Dover, Kent CT17 9EN.

WW 306 for further details

Sanwa N-501 has a 2 μ A movement, enabling resolutions of 0.05mA or 1mV, and measures current, voltage, resistance and decibels. This meter has current ranges up to 12A a.c./d.c. and voltage ranges up to 1.2kV a.c./d.c. with an accuracy of $\pm 2.0\%$ on the d.c. ranges and $\pm 2.5\%$ on the a.c. ranges. Operating frequencies on the a.c. ranges are from 20Hz to 50kHz. The **N-501**, which measures 252 x 191 x 107mm, is protected by diodes and a fuse. Quality Electronics Ltd, 24 High Street, Lydd, Kent TN29 9AJ.

WW 307 for further details

Miseco Tester 20 is a 20k Ω /volt, 40 range meter measuring current, voltage, resistance and decibels. This general-purpose unit can measure d.c. current up to 10A, has an accuracy of 2.0% on the d.c. and resistance ranges and 3.0% on the a.c. ranges. Operating frequencies on the a.c. ranges are from 20Hz to 20kHz. The **Tester 20** measures 105 x 130 x 35mm and requires two 1.5V batteries. Optional extras include a 15kV/30kV d.c. probe. Alcon Instruments Ltd, 19 Mulberry Walk, London SW3 6DZ.

WW 308 for further details

Display modules

Compact 7-segment l.e.d. display modules, with integral push-button decade switches for preset counting, were featured by Contraves Industrial Products Ltd. The displays, called Multicount modules, may be assembled into multi-decade display and switching banks, for instrument and control panel mounting. Each module occupies 10mm x 50mm of panel space, and end brackets, for push-in front-of-panel mounting, add a further 10mm to the width. A variety of functions are available in the Multicount range; these include a built-in-memory, an up or down counter, a comparator and a sign display. Dummy modules can be supplied for incorporating additional functions such as push-buttons, key-switches or electronic circuits. The bidirectional decade switches have binary-coded decimal outputs which can either function independently from the digital display, or may be connected to the display logic. Contraves Industrial Products Ltd, Times House, Station Approach, Ruislip, Middlesex, HA4 8LH.

WW 309 for further details

Base stations for f.m. systems

Burndept Electronics have introduced two f.m. base station transceivers, the BE454 for u.h.f. and the BE458 for v.h.f. The u.h.f. station operates within the range 420 to 470MHz, with channel spacings of 25kHz, and has a transmitter output of 5 watts with a spurious output of less than $2.5\mu\text{W}$. The v.h.f. station operates in the bands 68 to 108MHz and 132 to 174MHz with channel spacings of 12.5 or 25kHz. Receiver sensitivity for both transceivers is $0.35\mu\text{V}$ for 20dB quieting. Crystal stability is ± 5 parts in a million over the temperature range -10 to $+60^\circ\text{C}$. The transceivers, which can also be used for repeater operation, are designed to be operated either locally or remotely in a communications network. Remote control is achieved by tone or d.c. signalling over two or four wire systems. A range of quick-change modules are available allowing both versatility and ease of maintenance. Both transceivers can be used in single or two frequency simplex, or duplex modes and are available in single or multichannel versions. Optional extras include tone squelch and selective calling controls. Burndept Electronics (E.R.) Ltd, St Fidelis Road, Erith, Kent DA8 1AU.

WW 310 for further details

Cam switch

Adjustable cam switches, suitable for up to 700 rev/min, have been introduced by Barden Corporation. These miniature switches, in the PA1 and PA2 series, give infinitely adjustable shaft and dwell angles between 3° and 357° . The units, which can be adjusted while the shaft is fixed or rotating, can be mounted in series to provide from 1 to 10 independently adjustable switches. Features include precision ball bearings and low inertia and operating torque for fast and accurate switch operation at minimum power. Operating characteristics are: 115/230V a.c. for 5A inductive and resistive load, 30V d.c. for 5A resistive load or a 3A inductive load with an inrush capacity of up to 24A. The Bardon Corporation (UK) Ltd, Western Road, Bracknell, Berks, RG12 1QU.

WW 311 for further details

Digital cassette recorder

A digital cassette recorder, known as the Raycorder, is claimed by its makers, Raymond Engineering Inc., to be a highly reliable instrument suitable for minicomputer, telecommunications, and research applications. The recorder is designed primarily for use in data terminals and data logging systems, but may also serve as a digital interface. A

number of versions are available, including single or dual-channel machines with either read-write or read-while-write options. The reels and capstans are driven directly by four motors, eliminating clutches, belts and flywheels to give maximum reliability and performance. Mean time before failure has been rated at 5000h. The motors have low-mass ironless armatures and are controlled by a servo-system which enables the tape to be accelerated uniformly and accurately. Preferred tape speeds are factory set between 3in/s and 30in/s with variations not exceeding $\pm 2\%$. Typical acceleration and deceleration times are 20ms at 3in/s and 60ms at 15in/s. Trend Telecommunications Ltd, St. John's Estate, Tyllers Green, High Wycombe, Buckinghamshire, HP10 8HW.

WW 312 for further details

Microprocessor kit


The SC/MP Introkit includes a SC/MP central processing unit — the ISP-8A/500D, a 512×8 r.o.m. (MM5214), a 256×8 r.a.m. (MM2112-1), a 1MHz crystal, interface circuits and discrete components. It is claimed that these components can be assembled on to the 100×160 mm Introkit printed circuit board in one hour, providing a practical method of familiarising users with microcomputer characteristics. Small programmes can be developed and entered into the r.a.m. using a teletype keyboard or a compatible terminal. These programmes can then be run and their performance monitored by the Kitbug programme which is stored in the r.o.m. Applications for this kit could include automatic control systems, domestic appliance programmes, traffic light sequencing and machine tool control. The kit, which includes a data sheet and technical manuals, was priced at £54.50 at the time of release. DTV Group Ltd, 126 Hamilton Road, London SE27 9SG.

WW 313 for further details


Recorder-calculator

The SX4500 cassette recorder, introduced by Hadley Sales Services, has a built-in calculator. The two-track recorder, which can be operated from either the mains supply or internal batteries, will take C30, C60 and C90 cassettes, has an audio output of 300mW, and uses a built-in condenser microphone. Calculator functions include addition, subtraction, multiplication, division, constant multiplication or division, power calculation, a memory and a percentage calculation. Calculations may be made to seven decimal places. The overall size of the instrument is $4 \times 1\frac{1}{4} \times 8$ in. Hadley Sales Services, 112 Gilbert Road, Smethwick, Warley, Birmingham B66 4PZ.


WW 314 for further details

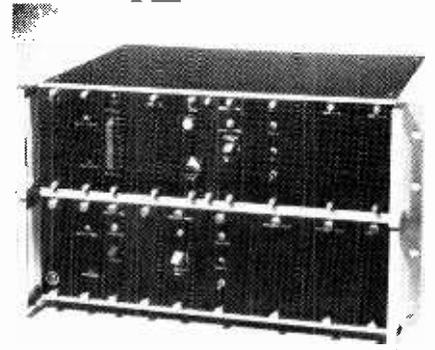

WW 310 for further details

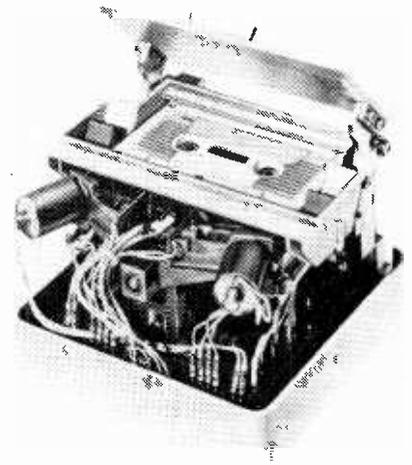

WW 312 for further details

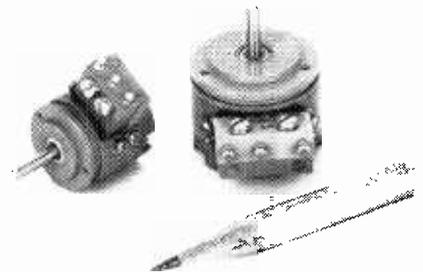

WW 311 for further details

Audio switching system

A system of modules for audio mixing and switching have been introduced by Prowest Electronics Ltd. The system consists of a five channel input buffer, a ten by one switching unit, a twin output amplifier and a d.c. controlled fading amplifier. Four field effect transistors in a series shunt configuration are used as the switching elements and a further series switch on each board reduces system crosstalk to approximately 90dB at 20kHz. Maximum level through the system is $+26\text{dBm}$ and distortion is less than 0.03% at all levels up to $+20\text{dB}$. The modules are all based on 7in printed circuit boards, are built into standard Imhoff 19in racks, and use a common $\pm 18\text{V}$ power supply. The switching can

be controlled directly or by a binary-coded-decimal address. Prowest Electronics Ltd, Alma Road, Windsor, Berks. **WW 315** for further details

Resistance standards

A range of 4-terminal resistance standards have been manufactured by Croydon Precision Instrument Company for values from 0.0001Ω to $100k\Omega$. The standards, type RS3, offer accuracies between $\pm 0.005\%$ and $\pm 0.02\%$ depending upon the resistance values. Each standard is designed to have the maximum permanence of calibration combined with a good load coefficient, and is suitable for use in air or in a temperature controlled oil bath. Croydon Precision Instrument Company, Hampton Road, Croydon, CR9 2RU.

WW 316 for further details

Tantalum capacitors

Thomson-CSF have introduced a range of solid-tantalum electrolytic resin-dipped capacitors. The capacitors have values ranging from $0.1\mu F/35V$ to $100\mu F/3V$ with tolerances of $\pm 20\%$. Case dimensions vary from $6.5 \times 4mm$ to $10 \times 7mm$. The leads are $0.6mm$ diameter and are spaced $5.08mm$ apart. Thomson-CSF (UK) Ltd, Ringway House, Bell Road, Daneshill, Basingstoke, Hants RG24 0QG.

WW 317 for further details

Dual-in-line switches

A series of subminiature switches for printed circuit applications has been introduced by Secme. Three basic types of switch are available within the range; one to eight single-pole on/off, one to four double-pole on/off, and one to four single-pole change-over. Other functions may be combined in the same body if required. The switches, which are

rated for $0.5A$ at $12V$, have a contact resistance of less than $30m\Omega$, and can be stacked end to end in any number on standard $0.1in$ pitches. The bases are sealed to prevent the ingress of moisture. Souriau (UK) Ltd, Shirley Avenue-Vale Road, Windsor, Berkshire.

WW 318 for further details

All purpose stroboscope

A compact portable stroboscope has been made available by ESI Nuclear for use in industry, research, education and medicine. The 202, as it is called, has three ranges covering from one to 250 flashes per second with an accuracy of $\pm 2\%$. A feature of the 202 is its flexibility; two or more units may be coupled to flash simultaneously while controlled by one dial, external sockets may be used to drive an external frequency meter, and there is also a provision for external triggering. At $\pounds 64$, the 202 is claimed to be amongst the most inexpensive instruments of its kind. ESI Nuclear, 6A Holmesdale Road, Reigate, Surrey RH2 0BQ.

WW319 for further details

Line impairment simulator

A new release at the "All Electronics Show" was the model 770 line impairment simulator from Axel. The simulator is claimed to be cheaper and more compact than previous models, and capable of simulating most of the line conditions common in data transmission systems. These conditions include those in voice-transmission-type telephone lines which, when used for data transmission, degrade the digital data – especially at speeds above 2400 bits per second – switch-selection enabling simulation of the worst cases of Bell C1, C2, C4 and 3002 lines. A user

may also add to the simulation certain steady-state disturbances such as various random noises, phase jitter, frequency shifts, and harmonic distortion. Transient disturbances such as impulse noise and sudden amplitude changes can also be added. The disturbances may be selected individually or simultaneously, as required. A built-in random noise generator with a calibrated attenuator allows selection of the desired signal-to-noise ratio, having output levels from $-16dBm$ to $-88dBm$ in $1dBm$ steps. At the time of going to press the model 770, which weighs 16 lb and is suitable for bench or rack applications, could be obtained for $\pounds 2,650$. A portable version, the model 771, is also available. JVN Components, 204-206 High Street, Bromley, Kent BR1 1PW.

WW 320 for further details

High Q bandpass filter


Pulse Engineering has introduced a high Q bandpass filter, PE 86 030, that can be tuned to any frequency from 67Hz to 3kHz. Each tone frequency is actively trimmed to better than $\pm 0.15\%$ and Q factor is typically 150. Deviation from the specified centre frequency over a temperature range 0 to $50^\circ C$ is less than $\pm 0.25\%$. These filters can replace tuning forks in paging applications and two-way transceivers for the detection of specific tone frequencies and are claimed to eliminate reliability problems and shock sensitivity. Aurisma Ltd, Components Division, 442 Bath Road, Slough, Berks.

WW 321 for further details


Digital thermometer

A pocket-size thermometer, introduced by Kane-May Ltd, is claimed to give a rapid digital reading, to a resolution of $0.1^\circ C$, over a temperature range from $-30^\circ C$ to $199.9^\circ C$. The device, called the Digitherm "Universal" electronic thermometer, is also available for a wider range from $-50^\circ C$ to $1100^\circ C$, to a resolution of $1^\circ C$. Built-in circuitry compensates for ambient temperature and also for loss of battery voltage, which can be checked as required, the accuracy being maintained until the battery potential drops away sharply. The thermometer is intended for food processors, plastics manufacturers and in other industries where fast transient temperature changes must be measured. Kane-May Ltd, Burrowfield, Welwyn Garden City, Herts.

WW 322 for further details

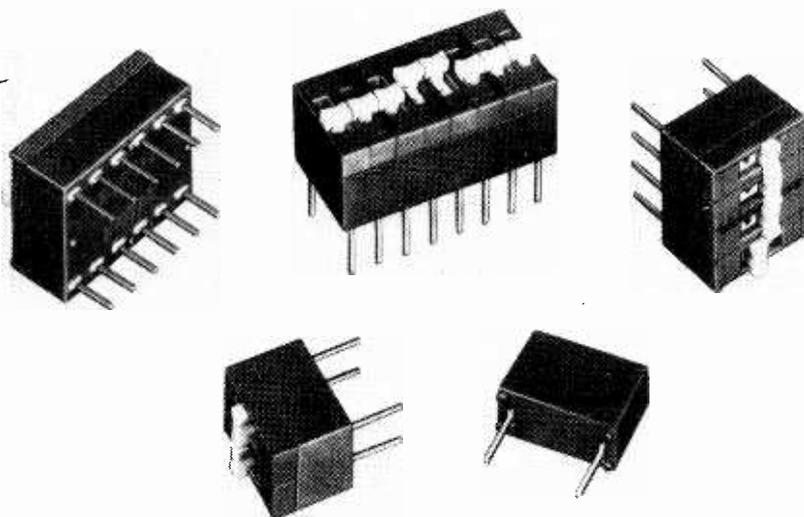

WW 318 for further details

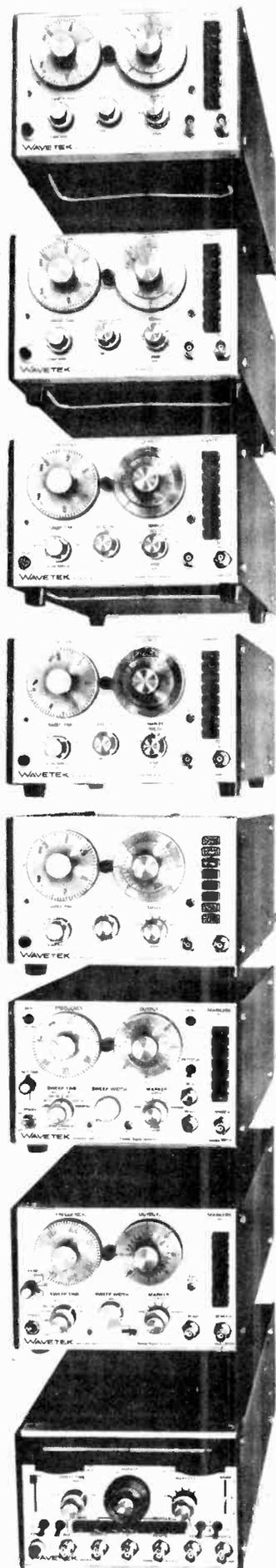

SWEeper MODELS*

1001A	0.5MHz to 300MHz	£830
1002	1MHz to 500MHz	£830
1004-1	450MHz to 950MHz	£830
1004	500MHz to 1GHz	£830
1005	700MHz to 1.4GHz	£830
1801A	1MHz to 950MHz	£1145
2000	1MHz to 1.4GHz	£1120
2001	1MHz to 1.4GHz	£1330


*We also offer a complete line of attenuators and detectors covering the same frequency ranges.

**One thousand one...
 one thousand two...
 one thousand four-one...
 one thousand four...
 one thousand five...
 one thousand eight
 hundred one...
 two thousand...
 two thousand one...
 that's how you count
 to 1.4 GHz in sweepers.**

It's also how to tell the story of the most complete line of sweepers in the business. Our latest additions include the 1801A for CATV equipment testing and the 2000—a less expensive version of the spectacular 2001. All of our sweepers have rugged, solid-state designs and are suited for laboratory, production and systems use. They are available with both 50-ohm and 75-ohm calibrated RF outputs and feature pin-diode leveling, crystal-controlled markers and excellent display linearity characteristics. All include remote programming of frequency and sweep width, and can be AM or FM modulated. If you'd like more information, use the reader service card or get in touch with us directly. You can count on an immediate response.

WAVETEK®

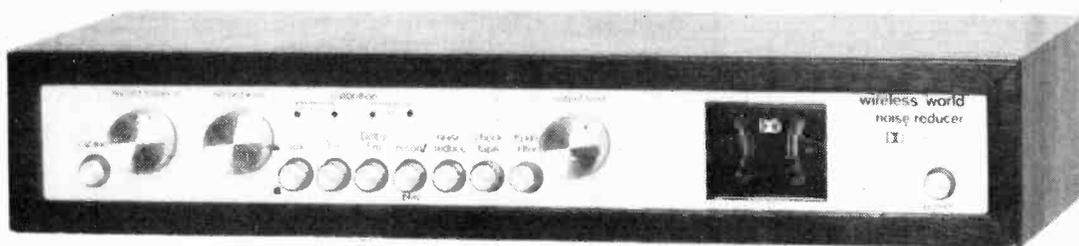Wavetek Electronics Limited,
 109, Crockhamwell Road,
 Woodley, Reading, Berks RG5 3JP
 Tel: Reading (0734) 694944. Telex: 849301



Wireless World DolbyTM noise reducer

Trademark of Dolby Laboratories Inc.

We are proud to announce the latest addition to our range of matching high fidelity units.

Featuring:

- switching for both encoding (low-level h.f. compression) and decoding
- a switchable f.m. stereo multiplex and bias filter
- provision for decoding Dolby f.m. radio transmissions (as in USA)
- no equipment needed for alignment
- suitability for both open-reel and cassette tape machines
- check tape switch for encoded monitoring in three-head machines

The kit includes:

- complete set of components for stereo processor
- regulated power supply components
- board-mounted DIN sockets and push-button switches
- fibreglass board designed for minimum wiring
- solid mahogany cabinet, chassis, twin meters, front panel, knobs, mounting screws and nuts

Typical performance

Noise reduction: better than 9dB weighted

Clipping level: 16.5dB above Dolby level (measured at 1% third harmonic content)

Harmonic distortion 0.1% at Dolby level typically 0.05% over most of band, rising to a maximum of 0.12%.

Signal-to-noise ratio: 75dB (20Hz to 20kHz, signal at Dolby level) at Monitor output.

Dynamic Range > 90dB

30mV sensitivity.

PRICE: £34.40 + VAT

Calibration tapes are available for open-reel use and for cassette (specify which) **Price £1.80 + VAT***

Single channel plug-in DolbyTM PROCESSOR BOARDS (92 x 87mm) with gold plated contacts are available with all components **Price £6.50 + VAT**

Single channel board with selected fet. **Price £2.00 + VAT**

Gold plated edge connector **Price £1.27 + VAT***

Selected FET's **54p** each + VAT, **96p** + VAT for two, **£1.76** + VAT for four

Please add VAT at 12½% unless marked thus*, when 8% applies
We guarantee full after-sales technical and servicing facilities on all our kits



INTEGREX LTD.

Please send SAE for complete lists and specifications
**Portwood Industrial Estate, Church Gresley,
Burton-on-Trent, Staffs DE11 9PT
Burton-on-Trent (0283) 215432 Telex 377106**


INTEGREX

S-2020TA STEREO TUNER / AMPLIFIER KIT

SOLID MAHOGANY CABINET

A high-quality push-button FM Varicap Stereo Tuner combined with a 20W r.m.s. per channel Stereo Amplifier.

Brief Spec. Amplifier: Low field Toroidal transformer, Mag. input, Tape In/Out facility (for noise reduction unit, etc), THD less than 0.1% at 20W into 8 ohms. All sockets, fuses, etc., are PC mounted for ease of assembly. Tuner section: uses Mullard LP1186 module requiring no RF alignment, ceramic IF, INTERSTATION MUTE, and phase-locked IC stereo decoder. LED tuning and stereo indicators. Tuning range 88—104MHz. 30dB mono S/N @ 1.8µV. THD typ. 0.4%

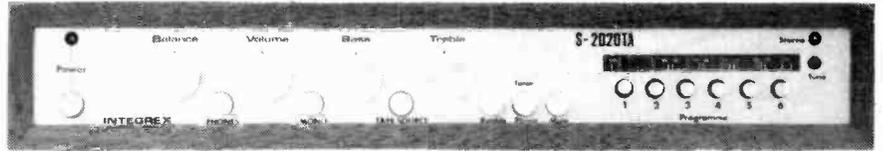

PRICE: £48.95 + VAT

NELSON-JONES STEREO FM TUNER KIT

A very high performance tuner with dual gate MOSFET RF and Mixer front end, triple gang varicap tuning, and dual ceramic filter / dual IC IF amp.



Brief Spec. Tuning range 88—104MHz. 20dB mono quieting @ 0.75µV. Image rejection — 70dB. IF rejection—85dB. THD typically 0.4% IC stabilized PSU and LED tuning indicators. Push-button tuning and AFC unit. Choice of either mono or stereo with a choice of stereo decoders.

Compare this spec. with tuners costing twice the price

Mono £26.31 + VAT

With ICPL Decoder £30.58 + VAT

**With Portus-Haywood Decoder
£32.81 + VAT**



Sens. 30dB S/N mono @ 1.8µV
THD typically 0.4%
Tuning range 88—104MHz
LED sig. strength and stereo indicator

STEREO MODULE TUNER KIT


A low-cost Stereo Tuner based on the Mullard LP1186 RF module requiring no alignment. The IF comprises a ceramic filter and high-performance IC Variable INTERSTATION MUTE. PLL stereo decoder IC

PRICE: Mono £25.55 + VAT

Stereo £28.65 + VAT

S-2020A AMPLIFIER KIT

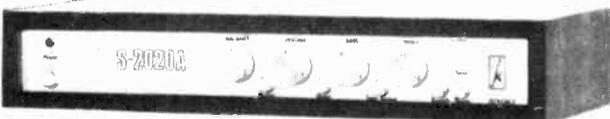Developed in our laboratories from the highly successful "TEXAN" design. PC mounting potentiometers, switches, sockets and fuses are used for ease of assembly and to minimize wiring



Typ. Spec. 20+20W r.m.s. into 8-ohm load at less than 0.1% THD. Mag. PU input S/N 60dB. Radio input S/N 72dB. Headphone output. Tape In/Out facility (for noise reduction unit, etc.). Toroidal mains transformer.

PRICE: £30.94 + VAT

ALL THE ABOVE KITS ARE SUPPLIED COMPLETE WITH ALL METALWORK, SOCKETS, FUSES, NUTS AND BOLTS, KNOBS, FRONT PANELS, SOLID MAHOGANY CABINETS AND COMPREHENSIVE INSTRUCTIONS

BASIC NELSON-JONES TUNER KIT £13.13 + VAT
BASIC MODULE TUNER KIT (Mono) £13.25 + VAT
BASIC MODULE TUNER KIT (stereo) £15.25 + VAT

PHASE-LOCKED IC DECODER KIT £4.47 + VAT
PUSH-BUTTON UNIT £3.50 + VAT

PORTUS-HAYWOOD PHASE-LOCKED STEREO DECODER KIT £7.93 + VAT



DESIGNED BY TEXAS

Texan Amplifier as featured by PRACTICAL WIRELESS
SOLE U.K. DISTRIBUTORS — HENRY'S

Build it yourself for only

£32 KIT PRICE INC. VAT + £1.00 p&p
 Built and tested £42.00 inc. VAT + £1.00 p&p.

Build the Texan stereo amplifier, then you can be doubly proud! For a start, you'll own a superb home entertainment unit. And have had all the pleasure of doing it yourself, with the Henry's kit.
Look at the Texan specification
 Incorporating fully integrated stereo preamp and power amp, with 6 IC's, 10 transistors, 6 rectifiers and zener diodes. Plus stabilised, protected circuitry, glass fib pcb. Gardeners low-field low-line mains transformer, all facilities and controls. Slim design, chassis 14 1/2" x 6" x 2" overall. 20 watts per channel RMS, less than 0.1% distortion at 1 kHz.

- ★ Can be built Stage by stage
- ★ Ask for leaflets 5.
- ★ Everything necessary supplied.
- ★ Full after sales service and guarantees.

TEXAN FM TUNER KIT **£23.50**
 inc. VAT + 50p p&p

Built and tested £28.50 inc. VAT + 50p p&p
 Build the matching Texan stereo tuner! Features advanced varicap tuning. Phase lock loop decoder. Professionally designed circuit. Everything you need is in the kit. From the glass fibre pcb to the cabinet itself. Excellent spec. 2.5 uV aerial sensitivity. 500 mV output (adjustable). Tuning range 87-102 MHz. Mains powered.

THE NATURAL FOLLOW-ON

Henry's latest ELECTRONICS CATALOGUE

- * over 5000 items - many new
- * free 50p voucher inside every copy
- * virtually everything needed by amateurs and professionals
- * over 200 pages
- * easy-to-use, complete alphabetical index
- * section index
- * everything at competitive prices

FREE to Educational Establishments when ordered on official headed notepaper + 20p call/pack

VIDEO SPORT



An up-to-the-minute game. Plugs into your own TV aerial socket. Switch on. And you're away! Choose your game - football, tennis or hole-in-the-wall. Absolutely safe. For you. Your children. And your TV. Mains powered. List Price £42.50

HENRY'S PRICE £25.00
 inc. VAT + 50p p&p

★ OVER 10,000 ALREADY SOLD
 ★ IDEAL GIFT

For this latest edition, we have made hundreds of changes and additions. Features now include:



HENRY'S RADIO

All mail to: Henry's Radio
 303 Edgware Rd. London W2

- LONDON W2: 404/6 Edgware Road. Tel: 01-402 8381
- LONDON W1: 231 Tottenham Ct Rd. (lower sales floor) Tel: 01-636 6681
- * NOTTINGHAM: 94/96 Upper Parliament St. Tel: (0602) 40403
- * READING, BERKS: 130/131 Friar Street. Tel: (0734) 583230
- * HARROW: 190/4 Station Road. Tel: 01-863 7788
- * CROYDON: 110 North End. Tel: 01-681 3310

NEW STORES
 Please Note: Mail Order Customers HENRY'S WILL CREDIT ANY VAT OVERPAYMENTS

WW — 041 FOR FURTHER DETAILS

ELECTROVALUE

Wise buyer's first choice

CATALOGUE 8
ISSUE No. 2



- 144 pages
- UP-DATED PRODUCT & PRICE INFORMATION
- 40p POST PAID + 40p REFUND VOUCHER

We have made it just about as comprehensive and up-to-the-minute as possible. Thousands of items from vast ranges of semi-conductors including I.C.s to components, tools, accessories, technical information and diagrams are included as well as a refund voucher worth 40p for spending on orders list value £5 or more. SEND NOW FOR YOUR COPY OF CATALOGUE 8, ISSUE No. 2 BY RETURN. It's an investment in practical money saving and reliability!

+ E.V. PRICE STABILIZATION POLICY
 This is one of reviewing prices every 3 months rather than trying to keep up with day by day changes as they occur. We have on the whole held prices better than anticipated in following this plan. Next review period starts July 1st

+ E.V. DISCOUNT PLAN
 Applies to all items except the few where prices are shown NETT 5% on orders from £5 to £14.99 10% on orders value £15 or more.

+ FREE POST & PACKING
 In UK for pre-paid mail orders over £2. If under there is an additional handling charge of 15p

+ QUALITY GUARANTEE
 All goods are sold on the understanding that they conform to makers' specifications. No rejects, seconds or sub-standard merchandise.

ELECTROVALUE LTD

All communications to Dept. 4/6
 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
 Telephone Egham 3603 Telex 264475. Shop hours 9-5.30 daily, 9-1 p.m. Sats
 NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester M19 1NA
 Telephone (061) 432 4945. Shop hours Daily 9-5.30 p.m., 9-1 p.m. Sats.
 In U.S.A. you are invited to contact ELECTROVALUE AMERICA, P.O. 337 Peterborough NH03458

HART ELECTRONICS

Audio Kit Specialists since 1961

J. L. Linsley-Hood High Quality Cassette Recorder

Full kits of parts for this outstanding design, including metalwork, cabinet, low humfield mains transformer and all other parts. Please send SAE for full data.

Cassette Mechanism only complete with Erase and Record/Playback head, £19.10 + 12 1/2% VAT.

FURTHER INFORMATION ON ALL KITS FREE if you send us a 9 in x 4 in. S.A.E.

REPRINTS Post free, no VAT

BAILEY 30W 18p.

STUART TAPE RECORDER. All 3 articles under one cover 30p.

BAILEY/BURROWS/QUILTER Preamp circuits, layouts and assembly notes 15p.

All prices exclude VAT @ 12 1/2 per cent except for reprints which are exempt.

Penylan Mill, Oswestry, Salop

Personal callers are always welcome, but please note we are closed all day Saturday

LOW PRICED Top Quality Components



VALVES

Qty	Type	Price (p)	Qty	Type	Price (p)
	DY87	37.0		PCF802	48.0
	DY802	37.0		PCL82	54.0
	ECC82	37.0		PCL84	46.0
	EF80	34.0		PCL85	52.0
	EF183	39.0		PCL86	50.0
	EF184	39.0		PFL200	65.0
	EH90	40.0		PL36	63.0
	PC86	58.0		PL84	30.0
	PC88	58.0		PL504	75.0
	PCC89	46.0		PL508	78.0
	PCC189	47.0		PL509	£1.35
	PCF80	38.0		PY88	43.0
	PCF86	44.0		PY500A	£1.00
	PCF801	46.0		PY800	42.0

SEMI CONDUCTORS

Qty	Type	Price (p)	Qty	Type	Price (p)
	AC127	20		BC135	15
	AC128	15		BC137	20
	AC141K	25		BC138	30
	AC142K	25		BC142	20
	AC151	20		BC143	25
	AC154	18		BC147	8
	AC155	18		BC147A	11
	AC156	20		BC148	9
	AC176	22		BC149	10
	AC187	20		BC153	20
	AC187K	30		BC154	20
	AC188	18		BC157	11
	AC188K	30		BC158	10
	AD142	62		BC159	11
	AD149	45		BC173	15
	AD161	38		BC178B	20
	AD162	38		BC182L	12
	AF114	25		BC183L	12
	AF115	22		BC187	25
	AF116	22		BC214L	15
	AF117	20		BC328	28
	AF118	45		BC337	19
	AF139	35		BD124	75
	AF178	45		BD131	35
	AF180	40		BD132	39
	AF181	40		BD160	£1.65
	AF239	45		BD235	50
	AF240	20		BD237	60
	BC107	10		BDX32	£2.40
	BC108	10		BF115	24
	BC109	12		BF160	35
	BC109C	14		BF167	24
	BC113	15		BF173	25
	BC116A	25		BF178	33
	BC117	14		BF179	38
	BC125B	18		BF180	31
	BC132	15		BF181	37

BF184	29	BT106	£1.20
BF185	30	BU105/02	£1.60
BF194	8	BU108	£1.80
BF195	8	BU208	£2.20
BF196	10	E1222	38
BF197	11	MJE340	45
BF198	23	OC71	18
BF200	25	OC72	18
BF218	40	R2008B	£1.90
BF224	20	R2010B	£1.90
BF258	26	RCA16334	80
BF336	27	RCA16335	80
BF337	35	TIP31A	52
BF355	50	TIP32A	62
BFX86	28	TIP41A	60
BFY50	19	TIP42A	75
BFY52	20	2N3055	55
BSY52	30		

DIODES

Qty	Type	Each Price (p)	Qty	Type	Each Price (p)
	BA115	7		BY206	17
	BA145	16		BY238	25
	BA148	16		OA90	6
	BA154/201	12		OA202	8
	BY126	11		IN60/OA91	7
	BY127	10		IN914	6
	BY199	25		IN4002	5

INTEGRATED CIRCUITS

Qty	Type	Each Price (p)	Qty	Type	Each Price (p)
	ETTR6016	£2.00		TBA120AS	60
	MC1351P	70		TBA120SQ	£1.00
	SN76003N	£2.35		TBA480Q	£1.40
	SN76013N	£1.43		TBA520Q	£2.40
	SN76013ND	£1.25		TBA530Q	£1.75
	SN76023N	£1.43		TBA540Q	£1.25
	SN76023ND	£1.20		TBA550Q	£2.30
	SN76033N	£2.15		TBA560CQ	£2.40
	SN76227N	£1.45		TBA800	£1.10
	SN76532N	£1.45		TBA920Q	£2.90
	SN76660N	60		TBA990Q	£2.50
	SN76666N	90		TCA270Q	£2.90
	TAA550	32			
	TAA700	£3.80			

EHT MULTIPLIERS MONOCHROME B.R.C.

Qty	Type	Price (p)
	2TQ 950MK2 1400	£2.05
	2DAK 1500 (17" x 19")	£1.85
	2TAK 1500 (23" x 24")	£2.05

EHT MULTIPLIERS COLOUR

Qty	Type	Price each
	11 TAQ ITT CVC 1, 2 & 3	£5.10
	ITN GEC Sobell	£4.50
	IITAZ GEC 2110	£4.50
	IITAM Philips G8	£4.50
	IITBD Philips 550	£4.65
	3TCW Pye 691/693	£3.49
	ITH Decca 30 Series	£4.60
	3TCU Thorn 3000/3500	£5.00
	11HAA Thorn 8000	£1.99
	11HAB Thorn 8500	£4.31
	IITCP Bush 823	£5.50

New BLACK & WHITE TUBES with Full Year's Guarantee

Qty	Type	Price each
	20" CME 2013	£13.90
	24" CME 2413	£15.95

New TOSHIBA TUBES with 12 months in service guarantee

Qty	Type	Price each
	19" A49-191X equivalents	
	A49-192 and A49-120X	£52.00
	20" 510DJB22 equivalent	
	A51-110X	£54.30
	22" A56/120X	£55.40

* All goods subject to settlement discount of 5% 7 days and 2% monthly.

* Prices subject to 12 1/2% VAT w.e.f. April 12th 76

* No Postal Charges

* C.P.C. - Price · Quality · Service

* No Minimum Orders

C.P.C.

COMBINED PRECISION COMPONENTS LTD.
Good People to Deal With

Around the World Export Service



C.P.C. supply many large Multiple Organisations in the U.K. Contact our Export Division for special prices NOW. Or send your order with this page.

I enclose cheque/PO to the value £.....p for the goods as specified above.

Name _____ Position _____

Company _____

Address _____

Tel. No. _____

Send this coupon NOW to:
C.P.C., Dept.W, 194-200 NORTH ROAD, PRESTON, LANCASHIRE, ENGLAND.
Phone: Preston (STD 0772) 55034. Telex 677122
New price list 1.4.76

Get a great deal from Marshall's

A Marshall (London) Ltd Dept WW
 40/42 Cricklewood Broadway, London NW2 3ET. Tel: 01-452 0161/2
 & 85 West Regent St Glasgow G2 2QD Tel 041-332 4133 Telex: 21492
 & 1 Straits Parade Fishponds Bristol BS16 2LX Tel 0272-654201/2
 & 27 Rue Danton Issy Les Moulineaux Paris 92
 Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat
 Trade and export enquiries welcome. **Catalogue price 35p (30p to callers)**

OUR RANGE COVERS OVER 7,000 ITEMS THE LARGEST SELECTION IN BRITAIN TOP 200 IC'S, TTL, CMOS & LINEARS

CA3020A 1.80	CO4030 0.52	LM7815P 1.60	LN7413 0.28	SN7486 0.29	SN74190 1.86
CA3028A 0.79	CD4031 1.98	LM7824P 1.60	SN7416 0.28	SN7490 0.42	SN74191 1.86
CA3035 1.37	CD4037 0.88	MC1303L 1.50	SN7417 0.28	SN7491 0.75	SN74192 1.15
CA3046 0.70	CD4041 0.70	MC1310P 2.50	SN7420 0.16	SN7492 0.45	SN74193 1.15
CA3048 2.11	CD4042 0.83	MC1330P 0.90	SN7423 0.23	SN7493 0.45	SN74196 1.80
CA3052 1.62	CD4049 0.45	MC1351P 0.80	SN7425 0.23	SN7494 0.75	SN74197 1.58
CA3089E 1.26	CD4050 0.45	MC1466 3.50	SN7427 0.23	SN7495 0.68	SN74198 1.80
CA3090Q 4.33	CD4510 1.25	MC1469 2.75	SN7430 0.15	SN7496 0.68	SN74199 1.80
CA3130 0.88	CD4511 1.94	MC14553 4.07	SN7432 0.22	SN74100 1.10	SN76003N2.92
CA3130 0.88	CD4516 1.25	NE555V 0.48	SN7437 0.28	SN74107 0.30	SN76013N1.95
CA3130 0.88	CD4518 1.87	NE566 1.30	SN7438 0.28	SN74118 0.85	SN76023N1.60
CA3130 0.88	CD4520 1.87	NE560 4.48	SN7440 0.16	SN74119 0.75	SN76033N2.82
CA3130 0.88	LM301A 0.48	NE561 4.48	SN7441 0.68	SN74121 0.32	TA2263 1.20
CA3130 0.88	LM308 1.17	NE565 4.48	SN7442 0.65	SN74122 0.42	TAA300 1.84
CA3130 0.88	LM309K 1.88	SL41L 2.35	SN7445 0.78	SN74123 0.65	TAA350A 1.86
CA3130 0.88	LM380 0.98	SL610C 2.35	SN7446 0.84	SN74141 0.75	TAAS50 0.32
CA3130 0.88	LM381 2.07	SL611C 2.35	SN7447 0.80	SN74145 0.72	TA611C 2.18
CA3130 0.88	LM702C 0.75	SL612C 2.35	SN7448 0.90	SN74150 1.20	TA621 2.03
CA3130 0.88	LM709 0.87	SL620C 3.50	SN7449 0.16	SN74151 0.88	TAA661B 1.03
CA3130 0.88	TO99 0.38	SL621C 3.50	SN7451 0.16	SN74153 0.88	TBA618 1.32
CA3130 0.88	8DIL 0.45	SL630C 5.75	SN7453 0.16	SN74154 1.20	TBA651 1.89
CA3130 0.88	14DIL 0.38	SL640C 4.00	SN7454 0.16	SN74155 0.78	TBA800 0.98
CA3130 0.88	LM710 0.47	SN7400 0.16	SN7460 0.16	SN74157 0.76	TBA810 0.98
CA3130 0.88	LM723C 0.66	SN7401 0.16	SN7470 0.29	SN74180 0.88	TBA820 0.80
CA3130 0.88	LM741C 0.16	SN7402 0.16	SN7472 0.21	SN74181 0.88	TBA920 1.79
CA3130 0.88	TO99 0.40	SN7403 0.16	SN7473 0.31	SN74182 0.88	BDLSKT 0.12
CA3130 0.88	80IL 0.40	SN7404 0.19	SN7474 0.31	SN74163 0.88	14DILSKT 0.14
CA3130 0.88	14DIL 0.38	SN7405 0.19	SN7475 0.45	SN74164 1.60	16DILSKT 0.14
CA3130 0.88	LM747 1.05	SN7406 0.36	SN7476 0.30	SN74165 1.60	DINPLUGS18p
CA3130 0.88	LM748 0.48	SN7407 0.36	SN7480 0.42	SN74167 3.30	DIN CHASSIS
CA3130 0.88	8DIL 0.44	SN7408 0.19	SN7481 1.00	SN74174 0.99	SOCKETS 11p
CA3130 0.88	14DIL 0.41	SN7409 0.18	SN7482 0.65	SN74175 0.70	3-way, 4-way
CA3130 0.88	LM3900 0.61	SN7410 0.16	SN7483 0.82	SN74176 1.14	5-way 180°
CA3130 0.88	LM7805P 1.60	SN7411 0.20	SN7484 0.95	SN74180 1.10	5-way 240° and
CA3130 0.88	LM7812P 1.60	SN7412 0.22	SN7415 1.00	SN74181 1.95	6-way spkr

LONDON, GLASGOW, PARIS — AND NOW BRISTOL
 IT'S OUR SERVICE THAT MAKES US GROW

POPULAR SEMICONDUCTORS

2N696 0.22	2N3716 1.80	AC153 0.35	BC157A 0.16	BFX84 0.30	TIP36A 3.70
2N697 0.16	2N3771 2.20	AC176 0.41	BC159B 0.17	BFX85 0.30	TIP41A 0.79
2N699 0.59	2N3773 2.65	AC187K 0.35	BC101 0.34	BFX88 0.30	TIP42A 0.80
2N706 0.14	2N3789 2.06	AC188K 0.40	BC107B 0.17	BFY50 0.30	TIP2955 0.98
2N708 0.17	2N3819 0.37	AO161 0.69	BC108A 0.15	BFY51 0.28	TIP3055 0.50
2N916 0.28	2N3820 0.29	AD162 0.69	BC109C 0.20	BFY52 0.30	TIS43 0.28
2N918 0.32	2N3904 0.19	AF106 0.40	BC127 0.23	BRV39 0.48	ZTX300 0.13
2N1302 0.185	2N3906 0.19	AF109 0.40	BC128 0.22	ME0402 0.20	ZTX301 0.13
2N1306 0.31	2N4058 0.18	AF114 0.35	BC130 0.17	ME0412 0.18	ZTX500 0.15
2N1308 0.47	2N4062 0.15	AF116 0.35	BC131 0.22	ME4102 0.11	ZTX501 0.13
2N1711 0.27	2N4921 0.83	AF117 0.35	BC132 0.18	MJ480 0.95	ZTX502 0.18
2N2102 0.60	2N4923 1.00	AF118 0.35	BC133 0.18	MJ481 1.20	IN914 0.07
2N2148 0.94	2N5245 0.29	AF124 0.30	BC134 0.82	MJ490 1.05	IN3754 0.36
2N2218A 0.47	2N5294 0.48	AF139 0.65	BD124 1.20	MJ491 1.45	IN4007 0.10
2N2219A 0.52	2N5296 0.48	AF239 0.65	BC135 0.50	MJ2955 1.00	IN4148 0.07
2N2220 0.25	2N5458 0.26	AF279 0.70	BC136 0.21	MJ340 0.65	IN4504 0.22
2N2221 0.18	2N5459 0.29	AF280 0.79	BC137 0.21	MJ370 0.88	IN4508 0.30
2N2222 0.20	2N6027 0.45	AL102 1.00	BC138 0.22	MJ371 0.75	AA119 0.08
2N2369 0.20	3N128 0.73	BC107 0.14	BC139 0.24	MJ481 1.20	BA102 0.25
2N2646 0.55	3N140 1.00	BC109 0.15	BC140 0.26	MJ521 0.70	BA145 0.18
2N2905 0.47	3N141 0.81	BC149B 0.10	BC141 0.26	MJE2955 1.20	BA154 0.12
2N2906 0.33	3N200 2.49	BC149C 0.11	BC142 0.26	MJE3055 0.78	BA155 0.12
2N2907 0.22	40361 0.40	BC157A 0.16	BC143 0.26	MP8113 0.47	BB103B 0.23
2N2926G 0.12	40362 0.45	BC158A 0.16	BC144 0.26	MPF102 0.39	BB104B 0.45
2N3053 0.25	40406 0.44	BC167B 0.15	BC145 0.26	MPSA05 0.25	BY126 0.27
2N3054 0.60	40407 0.35	BC168B 0.15	BC146 0.26	MPSA06 0.31	BY127 0.29
2N3055 0.65	40408 0.50	BC169B 0.15	BC147 0.26	MPSA07 0.31	BY211 0.51
2N3056 0.65	40409 0.52	BC169C 0.15	BC148 0.26	MPSA15 0.21	BY212 0.51
2N3392 0.15	40410 0.52	BC182L 0.12	BC149 0.26	MPSA16 0.31	CA47 0.06
2N3393 0.15	40411 2.00	BC183 0.12	BC150 0.26	OC7B 1.48	DAE* 0.18
2N3440 0.59	40594 0.74	BC183L 0.13	BC151 0.26	OC7C 0.50	OAE 0.06
2N3442 1.40	40595 0.88	BC184 0.13	BC152 0.26	OC7D 0.32	DA91 0.06
2N3638 0.15	40636 1.10	BC184L 0.13	BC153 0.26	TH29A 0.49	OA200 0.08
2N3691 0.28	40637 0.73	BC189 0.12	BC154 0.26	TH21C 0.40	BY164 0.57
2N3703 0.13	AC126 0.20	BC121L 0.16	BC155 0.26	TH31A 0.82	ST2 diac 0.20
2N3704 0.15	AC127 0.40	BC121 0.15	BC156 0.26	TH31A 0.74	40669 1.00
2N3706 0.15	AC128 0.35	BC121AL 0.18	BC157 0.26	TH31A 1.01	TIC47 0.38
2N3708 0.14	AC151 0.27	BC237B 0.16	BC158 0.26	TH31A 1.51	C106D 0.65
2N3714 1.38	AC152 0.49	BC239C 0.15	BC159 0.26	TIP35A 2.90	OPR12 0.60

Prices correct as June 1976, but all exclusive of V.A.T. Post & Packing 30p



MARCONI TF 867 SIGNAL GENERATOR
 Range, 15KHz to 30MHz Output 0.4V to 4V at 13 or 75 ohms Impedance with termination (supplied) Built in crystal check facility with handbook £138 including carriage

HEWLETT-PACKARD AUDIO GENERATOR MODEL 206-A. Freq 20c to 20,000c, matching impedance 50 150 600 ohms. Price £85.00 carriage £4.00
OSCILLOSCOPES 175A with 1750A dual trace vertically plug-in and 1781B delay time base plug-in, 50MHz mini-meter band switch at 50 Mv/CM Modes of operation Single muxed, delaying Full spec and price on application

DIVERSITY SWITCH TYPE MA168B. Solid state £45.00
REDIFON SSB TRANSMITTER/RECEIVER TYPE GR410. Full particulars and price on request
SOLOTRON REGULATED PSU MODEL SR5 152. 0.170v DC to 200mA 160-340v 330-500v and AC 6 3v 5 amp £205.00. Carriage £5.00

RACAL RECEIVERS MODELS. RA17 in fully working and tuned condition Prices on application RA98A ADAPTOR £85.00.
RACAL FREQUENCY COUNTER SA 550. Measures freq up to 100MHz also period and time £135.00 carriage £4.00
524B FREQUENCY COUNTER. Measures basically to 10MHz Display on neon lamp 8 decibels PDA

PHILIPS AUDIO GENERATOR TYPE GM 2308. 0.16kcs Attenuator 0.0001 0.0003 0.001 to 1 with output asym. & sum and matching impedance 5 250, 600 & 1000 ohms Price £120.00 carriage £4.00
FERRANTI SWEEP GENERATOR LF Mk 2. 0.2 to 20 cps Band sweep 1.5 to 15MHz Carrier freq 10-220MHz £55.00 carriage £5.00

BOONTON AM/FM SIGNAL GENERATOR. TYPE 202E & 202H. 54-216MHz in 2 ranges £275.00.
SIGNAL GENERATOR TS. 497/URS 2.5Mz, 13MHz, 30MHz, 78MHz, 180MHz, 400MHz. 0.1v-1.0v £150 carriage £3.00.

Open Monday to Friday
 9-12.30, 1.30-5.30 p.m.

BRUEL & KJOER RANDOM NOISE GENERATOR TYPE 1402. Freq resp 20 200 000 c/s time constant 0.5 1.5 5 15 sec Matching impedance 6 60 600 6000 ohms and attenuator 0.04 0.1 0.4 1 2 4 4.000 output level 1 to 10. Price £155.00 carriage £3.00
TRIGGERED VACUUM SPARK GAP TYPE ZR 7512. Capable of switching 15 000 joules at 45KV £50.00 carriage £2.00
LOW RESISTANCE HEADPHONES TYPE CLR £2.50. 400 postage VAT 25%

CINTEL TYPE 1873 SQUARE WAVE & PULSE GENERATOR. Freq 5c/s to 250KHz Pulse 0.5 usec 0.3-3.3 Output to 50v for 1000Ω & to 5v for 100Ω P.O.A.
RADIOMETER TYPE MS111 SIGNAL GENERATOR. High quality Danish production 10KHz 110MHz £200 carriage £5.00
CT480 SIGNAL GENERATOR 7 KMC/S to 12 KMC/S mod CW F.M. Pulse £160 carriage £5.00
AVO NOISE GENERATOR CT 410 £30 carriage £2.00
BRIDGE IMPEDANCE NO. 5 0.1 10MΩ 1pF 1.0v
EDSWAN STABILIZED PULSE UNIT. 1 to 100 50MA Type R1280 to 300v 150MA and 300v 75mA
TEKTRONIX OSCILLOSCOPES 535, 545 & 545A. With plug in units CA (33MHz double beam) G(20MHz differential 50mV 20v) and D (high gain differential 1MW-50v)
 Price on application


TECHNICAL MATERIAL CORP EXCITER/TRANSMITTER MODE SELECTOR. Freq 2 32MHz M.O. and 10 crystal positions. Vernier tuning USB LSB var carrier insertion etc £200 carriage £10.00
FSK EXCITER. Freq 1.6 5MHz 0 100Hz continued frequency shift up to 600Hz switched CW/FSK Modes FAX FS MSC CW £50.00 carriage £5.00
AMPLIFIER UNIT TYPE 1430. Dynatron Production Pulse amplifier with control 0.08uS to 8-uS Attenuation to 20dB P.O.A.
PULSE ANALYZER. Made by Dynatron with discriminator all meter reads channel width threshold level P.O.A.

RHOIDE & SCHWARZ. Zg OIAGRAPH TYPE ZDU 30 420MHz 50Ω Directly measures mutual network phase shift phase angle with complimentary POWER SIGNAL GENERATOR TYPE SMLM high freq resolution internal external mod up to 3v out £750.
FREQUENCY SYNTHESIZER TYPE XUA. 30Hz-30MHz with FREQUENCY INDICATOR TYPE FKM 15 30MHz 30 100MHz £1,000
SIGNAL GENERATOR NO 16. 8cm 11cm £85 carriage 4.00
SIGNAL GENERATOR NO 13. 20MHz 80MHz AM 1.4 CW 1-1.1v £65 carriage 10.00
KAHN SSB ADAPTOR TYPE RSSB - £2 - 18. Designed for receivers with 455 500KHz IF at 100Mv (max) input Features electronic AFC carrier freq diversity to combat fading 20 sec R.C memory to maintain tuning during severe fading Individual carrier meters nullifiers IOW distortion production demodulator £65 carriage £5.00 carriage £5.00
TF 801B/2. Spec. as for 801D but minor circuit differences. Few only left £120 carriage £5.00

BEST PRICES PAID FOR TEST AND MEASUREMENT EQUIPMENT. Single items or quantities. Private or Industrial.



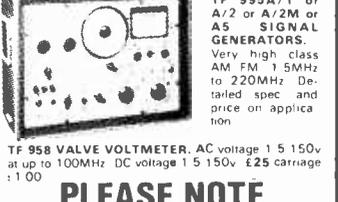EMF 1066 SIGNAL GENERATOR. Freq. 10 470MHz with attenuator EMF from 50Ω square -6dB Price on application



TF 995A/1 or A/2 or A/2M or A/5 SIGNAL GENERATORS. Very high class AM FM 1.5MHz to 220MHz Detailed spec and price on application
TF 958 VALVE VOLTMETER. AC voltage 1.5 150v at up to 100MHz DC voltage 1.5 150v. £25 carriage £1.00

TF 801D/1/S SIGNAL GENERATOR. Range 10 485MHz in 5 ranges RF output 0.1V 1V Source C.M. Dial calibrated in volts, decibels and power relative to thermal noise. Piston type attenuator 50Ω output impedance. Internal modulation at 1KHz at up to 90% depth also external sine and pulse modulation Built in 5MHz crystal calibrator Separate RF and mod meters P.O.A.
TF 1066 SIGNAL GENERATOR. Freq. 10 470MHz with attenuator EMF from 50Ω square -6dB Price on application
TF 1060 SIGNAL GENERATOR. 450MHz to 1200MHz with attenuator. Output for 0.1V to 4V CW Int. A.M. & Ext. Pulse £200.00 carriage £5.00
TF 1041 B VALVE MULTIMETER. General purpose measuring DC voltage from 300mV to 1000V AC voltage from 300mV to 300V at up to 1000MHz and resistance up to 500ohms Price £85 carriage £3.00
TF 1370 R.C. OSCILLATOR FOR SQUARE & SINE WAVE. Freq. -31.6V rms. 10Hz 1MHz square wave 0.73 2pp 10Hz 100KHz Attenuator range -50db to +10db impedance 75 100 600Ω £145 carriage £5.00
EMF OSCILLOSCOPE WMB AC/DC to 15 mc/s. Time base 0.15Msec 15Msec £44 carriage £5.00
HR 23 TRIPLE DIVERSITY SSB RECEIVERS. Freq 3.275MHz V.F.O. at 6 dial positions Reception of independent single or double side band transceivers Full spec on application £350 carriage £35.00
TF 885A/1 VIDEO OSCILLATOR. 0.30KHz 5MHz 1Mv 31.6V £85 carriage £4.00
TF 934 DIVERSITY METER. 250MHz £55 carriage £3.00
TF 1400S DOUBLE PULSE GENERATOR WITH TM 6600 SECONDARY PULSE UNIT for testing radon nucleonics scopes counters filters etc £175 carriage £5.00

PLEASE NOTE
 Unless offered as "as seen"
ALL EQUIPMENT
 ordered from us is completely overhauled mechanically and electrically in our own laboratories

SOLOTRON CD 1220 OSCILLOSCOPE
 With plug in units up to 40MHz single beam or 20MHz double beam £175.00 plus £6.00 carriage
SOLOTRON DIGITAL VOLTMETERS
 LM 14202 2.2 5v ± 1000v in 6 ranges Accuracy 0.05% of range i.e. ± 1 digit sensitivity 2.5 5v per digit £320.
 LM 1426 25mV 1000V in 6 ranges Acc range 1 in 0.02% £170.
 Also available
 CD 1420 £170.
 CD 1440-2 £220.

500/250 MEDIUM WAVE BROADCAST TRANSMITTERS. Export only Price and details on application
VAT FOR TEST EQUIPMENT 8% PLEASE ADD 8%
PLEASE SEND STAMP WITH ENQUIRIES
COLOMOR 170 Goldhawk Rd., London, W.12. (ELECTRONICS LTD.)

ARR8 D & LF SPARES. We hold the largest stock in UK write for list
RF METERS. 0.8 amp 2 1/4" (USA) brand new £1.50 P&P 25p
TELEPHONE TYPE "J" tropicalised 10 LINE MAGNETO SWITCHBOARDS 50 LINE AUTOMATIC PRIVATE TELEPHONE SWITCHBOARDS CABLE LAYING APPARATUS No 11. New Production P.O.A.
FOR EXPORT ONLY RCA ET 4336 TRANSMITTERS
 Also modified version of increased output to 700W
 COLLINS TYPE 2310 4 SKW TRANSMITTER 10 channel Autotune and manual tuning
 C13 TRANSmitters 38 62 TRANSCEIVERS NO 53 TRANSMITTERS REDIFON 100W SSB TRANSCEIVERS MULLARD C11 HIGH POWER INSTALLATION (1 000W)

KINNIE COMPONENTS

10, NELMES WAY, HORNCHURCH
ESSEX RM11 2OZ
HORNCHURCH 45167

CIRCUIT BOARD

P.C.B. 1/16. 1 oz. COPPER

FORMICA

Dim. 8.4 x 7.7 in 3 pcs., **80p**
Dim. 9.4 x 8.1 in 3 pcs., **90p**
Dim. 10.1 x 7.9 in 3 pcs., **£1.00** } p.p. 35p
Dim. 13.1 x 9.4 in 3 pcs., **£1.20**
Dim. 17.0 x 9.0 in 2 pcs., **£1.20**

BARGAIN PACK

10 pcs. 10.1 x 7.9 in. Plus free 1/2lb etching
Xtals **£3.10** P.P. 65p.

FIBRE GLASS P.C.B.

Dim. 6 x 6 in. **50p** each
Dim. 12 x 6 in. **75p** each
Dim. 12 x 12 in. **£1.30** each } P.P. 15p
Equals less than **1p** sq. in.

FIBRE GLASS P.C.B. DOUBLE SIDED

Dim. 6 x 6 in **40p** each
Dim. 12 x 6 in. **65p** each
Dim. 12 x 12 in. **£1.30** each } P.P. 15p

ETCH RESIST PENS

Pens **55p**, P.P. 5p

RESIST COATED P.C.B. FORMICA

10.1 x 7.9 in. **65p** ea.
13.1 x 9.4 in **75p** ea.

RESIST COATED P.C.B. FIBRE GLASS

6 x 6 in. **65p** ea.
12 x 6 in. **£1.35** ea.
12 x 12 in. **£2.00** ea.

BLUE P.C.B. INK

Etch resist use with any pen. Much cheaper
than ready loaded pens.
50 c.c. **55p**. P.P. 10p.

FERRIC CHLORIDE ETCHING XTALS

1 lb - 1 litre pack, **70p** P.P. 35p.
5 lb - 5 litre pack, **£2.20** P.P. 65p.

PRINTED CIRCUIT KIT

The no frills all value kit. Containing 4 pcs 8 x
7 Formica laminate. 1 pce 6 x 6 Fibre glass
laminate, 1 lb Etching Crystals, 50 c.c.
Resist ink, with instructions.
£2.40 P.P. 65p.

BARGAIN PACK FIBRE GLASS P.C.B.

200 sq. in. all usable pieces **£1.25** P.P. 25p.

EDGE CONNECTORS. 54 WAY

.1 Vero size etc. Can be cut to any length.
55p P.P. 10p. Side Guides to suit above **15p**
each.

TELEPHONE DIALS

(New) **£1** P.P. 25p.

EXTENSION TELEPHONES

(Type 706). Various colours.
£3.95 P.P. 75p.

12V MINIATURE

UNISELECTOR

11 ways. 4 bank (3 non bridging, 1 homing),
£2.50 P.P. 35p.



UNISELECTORS

(New) 25 way. 12 Bank (Non bridging). 68
ohms. **£6.50** P.P. 50p.

MINIATURE UNISELECTOR

(Ex. Equip.) 6 Bank (5 non bridging. 1
bridging) 100 ohms 24-30 V.D.C. **£1.50**
P.P. 50p.

1,000 TYPE KEY SWITCHES

Single 2 x 2 c/o Locking. **50p**. P.P. 10p
Bank of 4-2 x 4 c/o each switch (one biased),
£1.20 P.P. 25p.

MULTICORE CABLE

6-core (6 colours) 14/0076 Screened P.V.C.
30p per yard; 100 yards at **£16.50** P.P. 2p
a yard, 7-core (7 colours) 7/22 mm.
Screened P.V.C. **30p** per yard; 100 yards
£16.50 P.P. 4p per yard.

P.T.F.E. CONNECTING WIRE

1/20 Black or White 100 m. Drum **£2.50**
P.P. 30p.

OVERLOAD CUT OUTS

Panel mounting 800 M/A 1.8 amp. 10
amp. **55p** ea.

H.D. ALARM BELLS

6in. Dome. 6/8v. d.c. Heavy cast housing
for exterior/interior use. **£3.75** P.P. £1.
Connecting wire (twin/twisted) 220yd. reel
£3 P.P. 75p.

HIGH CAPACITY ELECTROLYTICS

250mfd/63 volt, **20p** P.P. 8p.
1,000mfd/100 volt, **70p** P.P. 25p.
2,200mfd/100 volt, **90p**. P.P. 25p.
4,700mfd/25 volt, **65p**. P.P. 20p.
6,800mfd/16 volt, **50p**. P.P. 15p.
10,000mfd/25 volt, **75p**. P.P. 25p.
25,000mfd/40 volt, **£1.25**. P.P. 30p.
47,000mfd/40 volt, **£2.00**. P.P. 50p.
100,000mfd/10 volt, **£1.50**. P.P. 50p.
160,000mfd/10 volt, **£2.00**. P.P. 50p.

BULK COMPONENTS OFFER

Resistors/capacitors 600 new components
£2.75. P.P. 36p.
Trial order 100 pcs **75p**. P.P. 20p.

SMITHS GEARED MOTORS 240V AC

3 rev. per min. **£1.50**. P.P. 25p.
4 rev. per min. **£1.50**. P.P. 25p.
6 rev. per min. **£1.50**. P.P. 25p.
2 rev. per hour. **£1.50**. P.P. 25p.
6 rev. per hour. **£1.50**. P.P. 25p.

HIGH-SPEED MAGNETIC COUNTERS

4 digit (non reset) 24v or 48v
(state which)
4 x 1 x 1 in. **£1**. P.P. 20p.
5 digit (non reset) 24v **£1.50**. P.P. 20p.
3 digit 12v (Rotary Reset) 2 1/4 x 1 3/4 x 1 1/4
£1.40. P.P. 15p.
6 digit (Reset) 220v. a.c. **£3.50**. P.P. 25p.



RESET COUNTER (BRAND NEW)

6 digit 24v. 25 I.P.S. **£5** P.P. 25p.

TRANSFORMERS

H.T. TRANSFORMERS. Prim. 110/240v.
Sec. 400v. 100 M/A **£3**. P.P. 65p.
L.T. TRANSFORMER. Prim. 240v. Sec.
27-0-27 at 800 M/A. **£2.35**. P.P. 50p.
L.T. TRANSFORMER. Prim. 110/240v.
Sec. 50v. at 10 amp. **£10**. P.P. £1.50.
L.T. TRANSFORMER. Prim. 240v. Sec. 18v.
at 1.5 amp. & 12v. at 1 amp. **£2.25**. P.P.
65p.
L.T. TRANSFORMER. Prim. 240v. Sec. 18v.
1 amp. **£1.10** P.P. 35p.
L.T. TRANSFORMER. Prim. 240v. Sec. 12v
at 1 amp. **£1** P.P. 25p.
L.T. TRANSFORMER. Prim. 110/240v.
Sec. 23/24/25v. at 10 amps **£7**. P.P. £1.
L.T. TRANSFORMER. Prim. 110/240v.
Sec. 20/21/22v. at 8 amp. **£6**. P.P. £1.

L.T. TRANSFORMER. Prim. 110/240v.
Sec. 0/24/40v. at 1 1/2 amp. (Shrouded).
£1.95. P.P. 50p.
L.T. TRANSFORMER. Prim. 200/250v.
Sec. 20/40/60v. at 2 amp. (Shrouded) **£3**.
P.P. 70p.
L.T. TRANSFORMER. (H.D.) Prim.
200/250v. Sec. 18v. at 27 amp; 40v. at
9.8 amp; 40v. at 3.6 amp; 52v. at 1 amp;
25v. at 3.7 amp. **£17.50**. P.P. £2.50.
L.T. TRANSFORMER. Prim 240v. Sec. 20v.
at 2.5 amp. **£2**. P.P. 65p.
L.T. TRANSFORMER ("" CORE)
200/240v. Secs. 1-3-8-9c. All at 1.5 amp.
50v. at 1 amp. **£2.50**. P.P. 50p

SIEMENS MINIATURE RELAYS

6v. 4 c/o **65p**. 24v. 2 c/o **50p**.

MINIATURE RELAYS

(1 3/8 x 1 1/4 x 1/2) 24 v. 4 c/o **35p**. P.P. 5p.

MAINS RELAY 240V.a.c.

3 c/o 10 amp. contacts **80p**. with base P.P.
20p

24v a.c. RELAY (PLUG IN)

3 pole c/o **75p**. P.P. 15p.
2-pole c/o **55p**. P.P. 15p.

MINIATURE REED RELAY

(1 x 1/4) 12v. 1 c/o **50p**. P.P. 10p.


S-DECS AND T-DECS

S-DEC **£1.90**.

U-DEC A **£4.20**.

T-DEC **£3.60**.

U-DEC B **£6.90**.

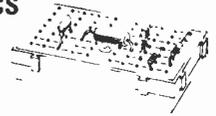

S.T.C. CRYSTAL FILTERS

(10.7Mhz) 445-LQU-901A (50 Khz spac-
ing). **£3**. P.P. 20p.

445-LQU-901B (25 Khz spacing). **£4**. P.P.
20p. 10.7 Mhz Canned I.F.s. Size 1 x 1/2 x 1/2
in. (with data) **65p**. P.P. 10p.

3 GANG TUNING CAPACITOR

8.5 PF. to 320 P.F. **80p**. P.P. 20p.

V.H.F./U.H.F. POWER TRANSISTORS

(type BLY 38). 3 watt output at 100-500
Mhz. **£2.25**. P.P. 10p.

AM/FM TUNING METER

125-0-125 μ A Edgewise 1 1/2 x 1/2. **£1.10**

SIGNAL STRENGTH METER

250 μ A (illum.) Edgewise 1 1/2 x 1/2. **£1.10**

OUTPUT METER CLEAR PLASTIC


500 μ A 1 1/2 x 1 1/2. **£1.30**

MINIATURE METERS

500 micro-amp (level stereo beacon, etc)
scaled half back/half red. Size 1 x 1 in. **65p**.
P.P. 15p.

PANEL METERS

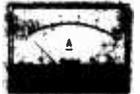2 3/8 in. x 1 1/8 T8 500mA
T1 50 μ A T9 1Amp
T2 100 μ A T10 50v.a.c.
T3 500 μ A T11 300v.a.c.
T4 1mA T12 50/0/50 μ A
T5 10mA T13 100/0/100 μ A
T6 50mA T14 500/0/500 μ A
T7 100mA All at **£3.75**. P.P. 15p.



PANEL METERS

4 1/2 ins. x 3 1/4 D3 200 μ A
D1 50 μ A D4 500 μ A
D2 100 μ A All at **£4.60**. P.P. 15p.

S.C.R. - THYRISTORS

1 amp. 400 P.I.V. **35p**
5 amp. 400 P.I.V. **40p**

MINIATURE "ELAPSED TIME" INDICATORS

(0.5000 hours) 45 x 8mm **75p**. P.P. 15p.

L.T. TRANSFORMER ("" CORE) Prim.
120v/120v SECS. 1-3-9-20v. 10 amps
£7.50. P.P. £1.25.
L.T. TRANSFORMER ("" CORE)
200/240v. Secs. 1-3-9-27v. All at 10 amp.
£7.50. P.P. £1.50
L.T. TRANSFORMER ("" CORE)
200/240v. Secs. 1-3-9-20v. All at 4 amp.
£5.50. P.P. 75p.
L.T. TRANSFORMER ("" CORE)
120/120v. Secs. 1-3-9-9v. All at 10 amp.
£6.50. P.P. £1.50.
L.T. TRANSFORMER ("" CORE)
110/240v. Secs. 1-3-9v. 10 amp. 35v. 1
amp; 50v. 750 M/A. **£6.50**. P.P. £1.50.

MAIL ORDER ONLY. PERSONAL CALLERS BY APPOINTMENT

TRAMPUS ELECTRONICS LTD. WINDSOR

58-60 GROVE RD. WINDSOR, BERKS. SL4 1HS.
 ADD 8% VAT TO PRICES MARKED *
 ADD 12% VAT TO ALL OTHER PRICES
 SEND CWO (EXCEPT GOVT. DEPTS.)
 POST & PACKING 20p FOR THE UK

NEW FAST SERVICE. LOW PRICES. MONEY BACK IF NOT SATISFIED. ALL BRAND NEW TOP GRADE FULL SPEC DEVICES. CALLERS WELCOME. NEW CATALOGUE LIST FREE SAE. BARCLAYCARD & ACCESS BY POST OR TELEPHONE ON £5 MINIMUM

FAST SERVICE



LEDS red 12P.

209 STYLE OR 0.2" NO CLIP 11p*
 TIL209 or 0.2" RED & CLIP 13p*
 GREEN LARGE/SWALL & CLIP 22p*
 ORANGE LARGE/SWALL & CLIP 22p*
 ORP12 57p* 2N5777 33p* TEC12 50p*
 DIGITAL CLOCKS MM5316 £5*
 MM5314 £3.39* MM5311 £5*
 A751224 £3.49* PCB £1*
 CAPACITORS
 CERAMIC 22pF-0.1uF 50V 5p.
 ELECTROLYTIC: 10/50/100 uF 10 or 25V 7p. 50V 9p. 2uF/10V 6p.
 1000uF 25V 18p. 200/500uF 22p.
 POTENTIOMETERS LIN/LOG 16p ea
 PRESETS 6p. RESISTORS 1 P ea

HEATSINKS T05/18 7p. T03 15p.
 SWITCHES: SPST 19p. DPDT 24p.
 DIN PLUGS ALL 12p. SOCKETS 9p.
 ALI CASES: A35/A37 50p. AB13 65p.
 TRANSFORMERS .100mA 89p ea.
 1/2A/1A 6/12 or 12/24 £2 each.
 NEW AUDIBLE WARNING BLEEPER £1
 TRAMPUS FULL SPEC PAKS ALL £1 ea
 PAK A 10 RED LEDS our choice £1*
 PAK B 1 741C OP AMP 8 PIN £1*
 PAK C 4 2N3055 £1*. D 12 BC109C £1*
 PAK E 10 BC182 £1. F 11 2N3704 £1
 PAK G 8 BFY51 £1*. H 9 2N3819 £1
 PAK J 9 2N3053 £1*. K 40 1N914 £1
 NEW PAK M 4 PLASTIC 3055 90W £1*

IC's LOW PRICES

703 RF/IF	36p	MC1303	£1.47
709 TO99	22p	MC1310	£2.09
709 DIL 14	28p	MC1312 SQ	£1.50
DL704 COM. CATHODE	710	MC1318	£2.50
0.3" 0-9DP 89p. ea	723 Regul'r	MC1330	75p
747 JUMBO 0.6" CA	741 DIL 8	MC1339	£1.40
LED DISPLAY £1.75*	741 DIL 14	MC1350/1/2	75p
3015F 0-9DP £1.25*	741 TO99	MC1466 /9	£1
DISCO etc STROBE	747 2x741	MFC4000 1W	59p
ZENON TUBE £5 ea	748 DIL 8	NE536 FETOPA £2*	
	7805 5V	NE540	£1.10*
	7812 12V	NE550 2vr	£1*
	7815 15V	NE555 TIMER 41p*	
	7900 Series	NE556 2x	81p*
	76013 6W AF	NE560 PLL	£4.00
	CA3048	NI 561 PLL	£4.00
	CA3048	NE562 PLL	£4.65
	CA3054	NE563	£2.25
	ICL8038	NE565	£2.50
	LM300	NE566	£2.20
	LM301 OPA	NE567	£2.20
	LM304 0-40V	SN72741 741	20p*
	LM308 HI Bo	SN76660 IF	7p
	LM309K 5V	NE56611 IF	£1
	LM372 IF	TAD100 & IF	£2
	LM377 2x2W	TBA800	89p
	LM380 60745	TBA810 7WAF	80p
	LM381	THA820	£1.10
	LM3900 40PA	ZN414 RX	89p

749 TTL FULL SPEC. 5% off 100MIX

7400	8p*	7474	17p*
7401	10p*	7476	27p*
7402/3	11p*	7490	37p*
7404	13p*	7491	60p*
7405/6/7	25p*	7492/93	43p*
7408/9/10	9p*	7494	43p*
7413	26p*	7496	68p*
7420/30	13p*	74100	1p
7414	13p*	74121	20p*
7411	41p*	74123	8p*
7412	47p*	74141	81p*
7470	22p*	74171	£1*
7471	22p*	74175	35p*
7473	30p*	74190	£1*

TRANSISTORS

PRICE EACH -	MATCHING	30p*	
AC127 & 128	10p*	INS. BUSH SET	8p*
AC176	15p*	TIP29 & 30	43p*
AC187 & 188	18p*	T1131 & 32	54p*
AD149	45p*	TIP41	63p*
AD161 & 162	33p*	TIP42	67p*
AD107	8p*	TIP2955	67p*
AD107B	12p*	TIP3055	67p*
AD108	7p*	11543 UJCT	25p*
AD108B	12p*	ZTX107/18/9	11p
BC109	8p*	ZTX300 4304	20p*
BC109C	10p*	ZTX500 4304	42p*
BC147/8/9	12p*	2N706 & 708	11p*
BC157/8/9	12p*	2N264C UJT	38p*
BC167/8/9	12p*	2N2401 & 2	9p*
BC177/8/9	12p*	2N2926/100V	15p*
BC182/3/4/44/120	12p*	2N3053	15p*
BC212/3/4/44/120	12p*	2N3054	42p*
BC700/1/2	16p*	2N3055 115W	37p*
BD131 & 132	39p*	2N3055 RCA	60p*
BFRR8 250V	35p*	2N3702/3/4/5	8p*
BFY50	14p*	2N3706/7/8/9	9p*
BFY51	12p*	2N3710 & 11	19p*
BFY52 & 53	14p*	2N3819E FET	19p*
BSX19/20/21	16p*	2N3820 FET	40p*
MJ2955 T03	75p*	2N3823L FET	16p*
MJ12955	45p*	2N3901/5/6	13p*
MJ3055	61p*	2N4289 m.f.f.	31p*
PU131 PNT	49p*	2N4357 FET	10p*

CMOS LOGIC

NEW MOTOROLA	CD14533	£2.35*	
CD4000	15p*	CD4008	43p*
CD1001	18p*	CD4014	£1*
CD4002	18p*	CD4017	71p*
CD4009	45p*	CD4049	41p*
CD4011	17p*	CD4054	49p*
CD4013	45p*	CD4055	£1*
CD4015	45p*	CD4060	9p*
CD4017	82p*	CD4061	17p*
CD4018	82p*	CD4062	17p*
CD4022	77p*	CD4071	£1.10*
CD4027	16p*	CD4071	£1.10*
CD1091	65p*	CD1528	£1.10*
CD401	45p*	CD4558	£2.35*

TELEPHONE 54525

DIODES
 OA81 & OA91 GERMANIUM 5p.
 1N4001 1A50V & 1N4002 5p*
 1N4004 6p* 1N4007 9p*
 1N4148 & 1N914 SILICON 1p.
 ZENERS 8ZY88 400mW 9p.
 ZENERS 1½W 17P. 21½noise £1
 BRIDGE RECTIFIER 1A50 18p
 1A400V 25p. 4A100V 45p

SCR's TRIACS
 SCR's TAG1/400 1A400V 50p*
 1A50V 38p* 1A 600V 70p*
 C106D 4A400V SCR ONLY 47p*
 TRIAC SC146D 10A400V £1*
 TRIAC DISCO 16A400V £1.75*
 DIACS: ST2 20p. BR100 25p

vero
 36PINS 28p*FACE CUTTER 49p*
 COPPERCLAD 0.1 PITCH VERO
 2½"x3½" 32p 2½"x3½" 29p*
 3½"x5" 37p 3½"x3½" 32p*
 3½"x17" £1.70*
 3½"x17" PLAIN 0.1" £1.06*
 DIL BREADBOARD 6x4" £2*

DALO 69P

DALO ETCH RESIST PEN 69p*
 FEC ETCH PAK 500gm 89p*
 6x4" COPPER BOARD 59p*
 PCB KIT 3 ITEMS £9*
 CASSETTE MECHANISM C9 & ASC12
 TGS GAS DETECTORS 308ctc£2*

DIL sockets
 TOP QUALITY NYLON
 SOCKETS 8PIN 12p*
 14PIN 12p* 16PIN 12p*
 SOLDERCON PINS
 100 65p* 1000 £3.50*

WWW - 052 FOR FURTHER DETAILS

MURHEAD D-658 18" MUFAX CHART TRANSMITTERS (Model GA). Further details on request. For 110/250v a.c. operation £325.00
MEGGER (Record): 500 volts £20.00 £1.00 post
MEGGER (Evershed Vignoles): 250 volts £17.50 £1.00 post
R216 Receiver MANUAL (photostat copy): £1.50 inc. post
RACAL I.S.B. ADAPTOR RA-95A: £65. Carr. £2.
MURHEAD ATTENUATORS: 75 ohms 0-8 Mc/s 3V MAK 3 ranges 0-5, 0-25, 0-50 DB £3.00 + 75p post.
CREED MODEL 54 TELEPRINTER: £37.50 each. Carr. £4.
CREED MODEL 75 TELEPRINTER: Receiver only £30.00. Carr. £3.
EDDYSTONE TELEPRINTER ADAPTOR TYPE 937: £45. Carr. £1.
WILD BARFIELD ELECTRIC FURNACE MODEL CCI.22X: With ether indicating temperature controllers Model 990. 0-1400° C. £250. Carr. £5.
METROVAC IONIZATION GAUGE MODEL V.C.3: £55. Carr. £3.
AVO VALVE TESTER CT.160: (Portable) similar to Avo Mk. 3 Characteristic meter. Good condition. £45.00. Carr. £2.00.
REDIFON TELEPRINTER RELAY UNIT No. 12: ZA-41196 and power supply. 200-250V a.c. Polarised relay type 3SEITR. 80-0V. 25mA. Two stabilised valves CV 286. Centre Zero Meter 10-0-10. Size 8in. x 8in. x 8in. New condition. £10. Carr. 75p.
SOLARTRON PULSE GENERATOR TYPE G1101-2: £75.00 each. Carr. £2.00.
TELEPRINTER TYPE 7B: Pageprinter 24V d.c. power supply, speed 50 bauds per min. second hand cond. (excellent order) no parts broken. £20 each. Carriage £3.
AUTO TRANSFORMER: 230V 50c/s, 1000 watts. Mounted in strong steel case 5" x 6½" x 7". Bitumen impregnated. £12.00. Carr. £1.50.
CRYSTAL TEST SET TYPE 193: used for checking crystals in freq. range 3000-10,000KHz. Mains 230V 50Hz. Measures crystal current under oscillatory conditions and the equivalent resistance. Crystal freq. can be tested in conjunction with a freq. meter. £25. Carr. £1.50.
SOLARTRON VARIABLE POWER UNIT S.R.S. 1535: 0-500 volts at 100 mA and 6.3 volts C.T. 3 amps d.c. 110/250V volts a.c. input. £18.50. Carr. £1.50.
ADVANCE A.F. SIGNAL GENERATOR H1E: Sinesoidal or square wave output. 15-50KHz. Adjustable level between 200uv and 20v. Overall distortion less than 1%. Output adjustable 1.4mV to 140V. Waveform ratio 50:50 up to 25kHz. Standard A.C. mains input. As new condition £40.00. Carr. £2.00.
ADVANCE A.F. SIGNAL GENERATOR H.I.: Same frequency and characteristics as above. Earlier model. Secondhand condition. £25.00. Carr. £2.00.
ANTENNA MAST: 40ft. aluminium 1¼" dia. in 5ft. sections complete with guys. etc. £25.00. Carr. £3.00.
PULSE GENERATOR PG21: Pulse width variable 15nS to 200msec in 7 ranges. Delay variable 40nS to 200msec with respect to sync pulse output in 7 ranges. Jitter less than .1%. Repetition rate 1Hz to 10MHz in 7 decade ranges. 20MHz available in double pulse mode. Pulse mode: normal, square wave and double pulse. 240v a.c. As new condition. £125.00. Carr. £2.00.

CLASS 'D' WAVEMETER NO. 1: Crystal controlled heterodyne frequency meter covering 2-8 MHz. Power supply 6V d.c. Good secondhand condition. £8.50. Carr. £1.50.
PRECISION PHASE DETECTOR TYPE 205: Freq. 0.1-15MHz in 5 ranges. Variable time delay microseconds 0-0.1c. 115V input. £55 each. Carr. £1.
RING TOROIDAL DUST CORES: Size 2½" outside 1¼" inside 5/16" thick. Box of two £1.00. Post 30p.
MURHEAD PHASEMETER TYPE D729: A.M. £95.00. Carr. £3.00.
CT.420 SIGNAL GENERATOR: 200-8000c/s Variable tuning. Two fixed frequencies 9000 and 10,000. Internal calibrator 100 & 500 c/s. £75 each carr. £2.
NOISE GENERATOR TF-1106: Frequency 1 to 200 Mc/s Direct noise factor calibration. Output impedance 70 ohms £65 each. Carr. £1.50.
MW-59 UNIVERSAL KLYSTRON POWER SUPPLY: £85. Carr. £3.
TF-1278/I TRAVELLING TUBE WAVE AMPLIFIER: £125. Carr. £2.
BPL A.C. MILLIVOLTMETER TYPE VM.348-D Mk. 3: 2 millivolts-2 volts, 6 ranges. £30. Carr. £1.
CAWKELL REMSCOPE TYPE 741: Memory scope. 'as new' cond. £150.00.
MARCONI SYNTHESISER Q115-URC: 2-30 mc/s. £175.00.
FIREPROOF TELEPHONES: £25.00 each, carr. £1.50.
POWER UNIT: 110/230 volts a.c. input. 28 volts d.c. at 40 amps output. £30.00 each, carr. £3.00.
SMOOTHING UNIT (for the above): £10.00 each, carr. £2.00.
X-BAND MODULATOR CALIBRATOR TYPE MC-4420-X: Mnfr. James Scott. £125 each. Carr. £1.
BACKWARD WAVE OSCILLATOR TYPE SE-125: 6.3 heater, 105V Anode, 7.9mA. Mnfr. Watkins & Johnson. £85 each. Carr. £1.
TEKTRONIX TIME MARK GENERATOR TYPE 180-S1: 5, 10, 50 MHz. £65. Carr. £2.
ROTARY INVERTERS: TYPE PE.218E — input 24-28V d.c., 80 Amps. 4.800 rpm. Output 115V a.c. 13 Amp 400 c/s. 1Ph. P.F.9. £20.00 each. Carr. £2.50.
FREQUENCY METER BC-221: 125-20,000 Kc/s complete with original calibration charts. Checked out, working order £20 + £1.50 carr.
SORENSEN VOLTAGE REGULATOR: Input 190/260 volts a.c. Output 220/240 volts a.c. 1000 watts. £40.00, carr. £3.00.
EVERSHED SAFETY OHM. METER: Max 10Ma. Test pressure 30v. Complete in leather case. £25.00 each, post £1.00.
FYLDAM AMPLIFIERS TYPE 154 BDM: Rack mounted 3v d.c. and power supply FE.500.TP. £65.00, carr. £2.00.
AUTOMATIC VOLTAGE STABILIZERS: Input 207-242v a.c. Output 230v a.c. at 2.80 amps. £17.50, carriage £1.50.

ALL U.K. ORDERS SUBJECT TO VALUE ADDED TAX.

If wishing to call at stores, please telephone for appointment

W. MILLS

3 & 3a BALDOCK STREET, WARE, HERTS. SG12 9DT
 WARE 66312 (STD 0920)
 and at ELSTOW STORAGE DEPOT. Phone: Bedford 740605 (STD 0234)

RETURN OF POST MAIL ORDER SERVICE

BSR HI-FI AUTOCHANGER STEREO AND MONO

'Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. A.C. 200/250V. Size 13½-11¼in., 3 speeds. Above motor board 3¼in. Below motor board 2½in with STEREO and MONO CARTRIDGE



£10.25 Post 75p

B S R SINGLE PLAYER P128 Same as MP60 with stereo cartridge cueing device. **£17.50.**

PORTABLE PLAYER CABINET

Modern design. Rexine covered. Vynair front grille. Chrome fittings. Size 17 x 15 x 8in. approx. Motor board cut for BSR or Garrard deck

£4.50 Post 50p

HEAVY METAL PLINTHS

With P.V.C. Cover Cut out for most B S R or Garrard decks Silver grey finish Model "A" Size 12½ x 14¼ x 7½in. **£5.50** Model "B" Size 16" x 13¼" x 7in **£5.85.** Post 75p

COMPLETE STEREO SYSTEM

Two full size loudspeakers 13¼ x 10 x 3¼in. Player unit clips to loudspeakers making it extremely compact. overall size only 13¼ x 10 x 8½in., 3 watts per channel. plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls. Attractive Teak finish. **£22.50** 240V a.c. mains **£1** carriage



SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH

0-60 MINUTES **£2.95** Post 35p Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings Brand new and fully guaranteed



TEAKWOOD LOUDSPEAKER GRILLES will easily fit to baffle board Size 10½ x 7½in-**45p.**

WEYRAD P50 TYPE TRANSISTOR COILS

RA2W Ferrite Aerial **85p** Driver Trans LFDT4 **65p** I F P50/2CC 470 kc/s **40p** Printed Circuit, PCA1 **65p** 3rd I F P50/3CC **40p** J B Tuning Gang **£2.00** P50/1AC **60p** OPT1 **65p** Ferrite Rod 8 x ¾in., **20p.** 6 x 5/16in., **20p.** 3 x ¾in. **10p**

VOLUME CONTROLS

5KΩ to 2MΩ LOG or LIN. L/S **25p.** D.P. **40p.** STEREO L/S **55p.** D.P. **75p.** Edge 5K. S.P. Transistor **30p.** STANDARD TYPE VHF **15p** FRINGE LOW LOSS Ideal 625 and colour **yd.**

ELAC HI-FI SPEAKER 8in. or 10 x 6in.

Dual cone plasticised roll surround. Large ceramic magnet 50-16,000 c/s. Bass resonance 55 c/s 8 ohm impedance, 10 watts. music power. **£3.95** Post 35p



É.M.I. 13½ x 8in. SPEAKER SALE!

With tweeter and crossover, 10 watt State 3 or 8 ohm As illustrated **£6.60** Post 45p

£5.25 Post 35p

With tweeter and crossover, **£8.95** 20 watt. Bass res 25 c/s Flux = 11,000 gauss Post 45p 8 or 15 ohm 20 to 20,000 c/s

Bookshelf Cabinet

Teak finish 16 x 10 x 9in **£6.95** Post 75p

THE "INSTANT" BULK TAPE ERASER AND HEAD DEMAGNETISER.

Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V Leaflet S.A.E. Will also demagnetise small tools **£4.35** Post 30p



BLANK ALUMINIUM CHASSIS. 6 x 4-70p; 8 x 6-90p; 10 x 7-£1.15; 12 x 8-£1.35; 14 x 9-£1.50; 16 x 6-£1.45; 16 x 10-£1.70. **ALUMINIUM PANELS.** 6 x 4-17p; 8 x 6-24p; 14 x 3-25p; 10 x 7-35p; 12 x 8-43p; 12 x 5-30p; 16 x 6-43p; 14 x 9-52p; 12 x 12-68p; 16 x 10-75p.

ELAC 9 x 5in HI-FI SPEAKER TYPE 59RM

This famous unit now available. 10 watts. 8 ohm. **£3.45** Post 35p

RCS LOW VOLTAGE STABILISED POWER PACK KITS

All parts and instructions with Zener diode, printed circuit rectifiers and double wound mains transformer. Input 200/240V a.c. Output voltages available, 6 or 7.5 or 9 or 12V d.c., up to 100mA or less. Size 3 x 2½ x 1½ in. Please state voltage required. **£2.95** Post 45p

RCS POWER PACK KIT

12 VOLT, 750mA. Complete with printed circuit board and assembly instructions. 12 VOLT 300mA KIT, **£3.15.** 9 VOLT 1 AMP KIT, **£3.35.**

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER - BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12V or H.T. line 200-300V d.c. operation. Size: 1¾ x 1¼ x ¾in. Response 25 c/s to 25 kc/s. 26 dB gain. For use with valve or transistor equipment. Full instructions supplied. Details S.A.E. **£1.45** Post 30p

ELECTRO MAGNETIC PENDULUM MECHANISM

1.5V d.c. operation over 300 hours continuous on SP2 battery, fully adjustable swing and speed. Ideal displays, teaching electro magnetism or for metronome, strobe, etc. **95p** Post 30p

R.C.S. "MINOR" 10 watt AMPLIFIER KIT

This kit is suitable for record players, guitars, tape playback, electronic instruments or small P.A. systems. Two versions available Mono **£11.25;** Stereo, **£18.** Post 45p Specification 10W per channel; input 100mV; size 9½ x 3 x 2in. approx S.A.E. details. Full instructions supplied. AC mains powered.

MAINS TRANSFORMERS

ALL POST 50p
250-0-250V 70mA, 6 SV, 2A **£3.45**
250-0-250 80mA, 6 3V 3 5A, 6 3V 1A or 5V 2A **£4.80**
350-0-350 80mA, 6 3V 3 5A, 6 3V 1A or 5V 2A **£5.80**
300-0-300V 120mA, 6 3V 4A C.T., 6 3V 2A **£7.00**
MIDGET 220V 45mA, 6 3V 2A **£1.40**
HEATED TRANS. 6.3V ½ amp **£1;** 3 amp **£1.40**
GENERAL PURPOSE LOW VOLTAGE Tapped outputs at 2 amp, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V **£4.80.** 1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£7.00.** 3 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£7.00.** 5 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£11.25.** 6 06V 500mA **£1,** 9V 1 amp, **£1,** 12V 300mA, **£1,** 12V 500mA, **£1,** 12V 750mA, **£1,** 10V, 30V, 40V, 2 amp, **£2.75,** 20V, 3 amp, **£2.45,** 40V, 2 amp, **£2.95,** 22-0-22V, 4 amp, d.c., **£3.45,** 16V, ½ amp, **£1,** 16V, 2 amp, **£2.20,** 0, 5, 8, 10, 16V, ½ amp, **£1.95,** 20V ½ amp, **£1.75,** 20V, 1 amp, **£2.20.** AUTO TRANSFORMERS, 115V to 230V or 230V to 115V 150W **£5;** 250W **£6;** 400W **£7;** 500W **£8.** FULL WAVE BRIDGE CHARGER RECTIFIERS 6 or 12V outputs, 1½ amp **40p;** 2 amp **55p;** 4 amp **85p.** CHARGER TRANSFORMERS 1½ amp **£2.75;** 4 amp **£4.80.** 12V, 1½A HALF WAVE Selenium Rectifier, **25p.**

GOODMANS 8-inch HI-FI BASS WOOFER

8 ohm, 10W Large ceramic magnet Special Rubber cone surround Frequency response, 30-8000 c/s. Ideal Hi-Fi Enclosure Systems. **£6.75**



NEW ELECTROLYTIC CONDENSERS

2/350V	20p	250/25V	20p	50+50/300V	50p
4/350V	20p	500/25V	25p	30,000/25V	95p
8/350V	25p	100+100/275V	65p	32+32/250V	20p
16/350V	38p	150+200/275V	70p	32+32/450V	80p
32/500V	60p	8+8/350V	50p	350+50/325V	85p
25/25V	15p	8+16/350V	50p	100+50+50/350V	85p
50/50V	15p	16+16/350V	60p	32+32+32/350V	65p
100/25V	15p	32+32/350V	60p	4700/63V	95p

LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V **10p.** 500mF 12V **15p;** 25V **20p;** 50V **30p.** 1000mF 12V **17p;** 25V **35p;** 50V **47p;** 100V **70p.** 2000mF 6V **25p;** 25V **42p;** 50V **57p.** 2500mF 50V **62p;** 3000mF 25V **47p;** 50V **65p.** 5000mF 6V **25p;** 12V **42p;** 25V **75p;** 35V **85p;** 50V **95p.**

HORT WAVE 100pF air spaced ganoable tuner, **95p.** TRIMMERS 10pF, 30pF, 50pF, 5p, 100pF, 150pF, 15p. CERAMIC, 1pF to 0.01mF, 5p. Silver Mica 2 to 5000pF, 5p. PAPER 350V-0 1 7p; 0.5 13p; 1mF 150V 15p; 2mF 150V 15p; 500V-0 001 to 0.05 5p; 0.1 10p; 0.25 13p; 0.47 25p. MICRO SWITCH SINGLE POLE CHANGEOVER 20p. SUB-MIN MICRO SWITCH, 25p. Single pole change over TWIN GANG, "0-0" 208pF + 176pF **£2.00;** 500pF standard **75p;** 365 + 365 + 25 + 25pF. Slow-motion drive **50p.** 120pF TWIN GANG, **50p;** 365pF TWIN GANG, **50p.** NEON PANEL INDICATORS 250V AC/DC. Amber or red, **30p.** RESISTORS: ¼W, ½W, 1W, 20% 2p; 2W, 10p; 10p to 10M HIGH STABILITY. ½W 2% 10 ohms to 6 meg., **12p.** Ditto 5% Preferred values 10 ohms to 10 meg., **5p.** WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K **12p** each

TAPE OSCILLATOR COIL Valve type, **35p.** BRIDGE RECTIFIER 200V PIV ½ amp **50p.** TOGGLE SWITCHES. SP 20p, DP ST 25p, DP DT 30p

BAKER MAJOR 12" £10.35



30-14,500 c/s. 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 25W. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit. 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£13** Post 60p each Please state 3 or 8 or 15 ohms.

BAKER "BIG-SOUND" SPEAKERS. Post 50p each.

'Group 25'		'Group 35'		'Group 50/15'	
12in	30W	12in	40W	15in	75W
3 or 8 or 15 ohm	£8.95	3 or 8 or 15 ohm	£10.50	8 or 15 ohm	£19.50

NEW MODEL BAKER LOUDSPEAKER, 12-inch 60 WATT. GROUP 50/12, 8 OR 15 OHM HIGH POWER. FULL RANGE PROFESSIONAL QUALITY. 30-16,000 CPS MASSIVE CERAMIC MAGNET. ALUMINIUM PRESENCE CENTRE DOME. **£14.50** Post 80p

TEAK VENEERED HI-FI SPEAKERS AND CABINETS For 12in or 10in, speaker 20x13x12in. **£12.50** Post 95p For 13x8in, or 8in, speaker 16x10x7in. **£8.95** Post 75p. For 8x5in, speaker 12x8x6in. **£4.95** Post 50p LOUDSPEAKER CABINET WADDING 18in. wide, 20p ft.

R.C.S. 100 watt VALVE AMPLIFIER CHASSIS



Four inputs Four way mixing, master volume, treble and bass controls. Suits all speakers This professional quality amplifier chassis is suitable for all groups, disco, P.A., where high quality power is required. 5 speaker outputs A/C mains operated. Slave output. Produced by demand for a quality valve amplifier. Send for leaflet. Price **£85** carr. **£2.50**

SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 2-16kc/s, 10W 8 ohm or 15 ohm **£3.60** De Luxe Horn Tweeters 3-18 kc/s, 30W 8 ohm **£7.50.** CROSSOVERS. TWO-WAY 3000 c/s 3 or 8 or 15 ohm **£1.90.** 3-way 950 cps/3000 cps. **£2.20.**

LOUDSPEAKERS P.M. 3 OHMS. 7x4in **£1.50;** 6½in, **£1.80;** 8x5in, **£1.90;** 8in, **£1.95.**

SPECIAL OFFER: 80 ohm, 2½in., 2½in., 35 ohm, 2in., 3in., 25 ohm, 2½in, dia, 3in, dia, 5x3in, 8 ohm, 2½in., 3in., 3½in., 5in., 15 ohm, 3½in, dia, 6x4in 7x4in 5x3in 3 ohm, 2½in, 2½in., 3½in., 5in, dia **£1.25** each.

PHILIPS LOUDSPEAKER, 8in., 4 ohms, 4 watts, ceramic magnet **£1.95**

RICHARD ALLAN TWIN CONE LOUDSPEAKERS Bin. diameter 4W **£2.50.** 10in. diameter 5W **£2.95;** 12in. diameter 6W **£3.50.** 3/8/15 ohms, please state

VALVE OUTPUT TRANS. 40p; MIKE TRANS. 50 1, 40p. Mike trans. mu metal 100 1 **£1.25.**

Loudspeaker Volume Control 15 ohms 10W with one inch long threaded bush for wood panel mounting. ¼in. spindle. **65p**

BAKER 100 WATT ALL PURPOSE AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm. a.c. Mains Separate treble and bass controls. Guaranteed. Details S.A.E. **£65** Carr. **£1.00** each



NEW MODEL MAJOR-50 watt, 4 input, 2 vol. Treble and bass. Ideal disc amplifier. **£49.95**

100 WATT DISCO AMPLIFIER CHASSIS volume, treble, bass controls, 500 M.V. input. Four loudspeaker outputs 4 to 16 phm **£52**

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9V. **£5.20**

TWO STEREO CHANNEL VERSION **£6.85**

BARGAIN 3 WATT AMPLIFIER, 4 Transistor Push-Pull Ready Built, with volume, Treble and bass controls. 18 volt d.c. Mains Power Pack **£3.45**

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p. OUTLET BOXES, SURFACE 40p. FLUSH 60p. TWIN 85p. BALANCED TWIN RIBBON FEEDER 300 ohms. 7p yd. JACK SOCKET Std. open-circuit 20p, closed circuit 25p; Chrome Lead-Socket 45p. Mono or Stereo. Phono Plugs 6p. Phono Socket 8p.

JACK PLUGS Std. Chrome 30p. Plastic 25p. 3.5mm 15p. DIN SOCKETS Chassis 3-pin 10p, 5-pin 10p. DIN SOCKETS FREE 3-pin 25p; 5-pin 25p. DIN PLUGS 3-pin 25p; 5-pin 25p. VALVE HOLDERS, 10p; CANS, 10p.


R.C.S. SOUND TO LIGHT KIT

Kit of parts to build a 3 channel sound to light unit. 1,000 watts per channel. **£12.50.** Post 35p. Easy to build. Full instructions supplied, cabinet. **£3.** As featured in December Practical Wireless.

E.M.I. TAPE MOTORS. 240V a.c. 1,200 r.p.m. 4 pole 185mA. Spindle 0.187x0.75in. Size 3¼ x 2¼ x 2¼in. **£2.** Post 40p 120V Model, **£1**



MULTIMETER F4313 *(Made in USSR)*

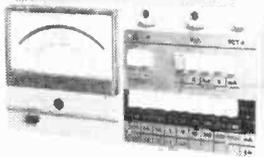

SENSITIVITY
 1200V DC range: 10,000 Ω/V
 Other DC ranges: 20,000 Ω/V
 1200 AC range: 6,000 Ω/V
 600V AC range: 15,000 Ω/V
 300V AC range: 15,000 Ω/V
 Other AC ranges: 20,000 Ω/V


AC/DC current ranges: 60-120-600μA-3-12-300mA-1 2-6A
 AC/DC voltage ranges: 60-300mV-1 2-6-30-120-300-600-1200V
 Resistance ranges: 300Ω-10-100-1000K
 Accuracy: 1.5% DC; 2.5% AC (of full scale deflection)

Mirror scale and knife edge pointer. Taut suspension of movement. Transistor amplifier is used for all AC ranges thus achieving a common linear scale for both AC and DC ranges.

Meter is fully protected for a transistorised cut-out relay circuit. Range selection is achieved by clearly marked piano keys. Power source: 5 1.5V dry cells. Dimensions: 95 x 225 x 120mm.

Price £37.50 plus VAT
 Packaging and postage £1.10

OSCILLOSCOPE CI-5 *Made in USSR*

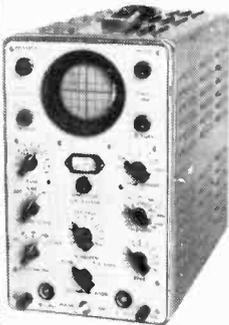

Extremely simple and easy to use single beam oscilloscope. Well proved design based on standard octal valves makes servicing and maintenance straightforward and inexpensive. Because of its bandwidth of 10 MHz the instrument is suitable for general electronic applications and educational purposes where a sophisticated instrument would be both too expensive and delicate. 3-in. tube giving a 50 x 50mm clear display. Amplitude and time base calibrations. Sensitivity 30mm/v max. Triggered and free-running time base, suitable for displaying pulses from 0.1 μ sec. to 3 m sec. A.C. mains operation.

Price £55.00 ex. works
 Packing and carriage (U.K. only £2.50)

FULLY GUARANTEED



0A2	0.45	6SN7GT	0.55	ECC83	0.38	EF86	0.40	KT66	3.40	PL508	0.90
0A3	0.55	12AT7	0.45	ECC84	0.35	EF183	0.35	KT88	3.65	PL509	1.30
0B2	0.45	12AU7	0.38	ECC85	0.45	EF184	0.40	PC86	0.65	PL802	1.40
0C3	0.45	12AX7	0.38	ECC86	1.25	EF200	0.75	PC88	0.65	PY31	0.50
0D3	0.45	12BA4	0.80	ECC88	0.60	EL34	0.70	PC900	0.55	PY33	0.63
5R4GY	1.00	12BA6	0.60	ECC89	0.60	EL36	0.60	PCC84	0.45	PY81	0.45
5U4G	0.55	12BE6	0.60	ECC189	0.80	EL41	0.80	PCC85	0.45	PY82	0.45
5Z4C	0.55	12BH7	0.60	ECC180	0.45	EL81	0.60	PCC88	0.65	PY88	0.50
5Y3GT	0.65	12X4	0.50	ECC181	0.45	EL82	0.60	PCC89	0.55	PSY00A	1.10
6AR4	0.50	19A05	0.75	ECC182	0.45	EL83	0.60	PCF189	0.65	PF800	0.50
6AU6	0.65	30A5	0.70	ECC183	0.50	EL84	0.60	PCF80	0.40	TT21	5.90
6AU5	0.45	35A3	0.70	ECC184	0.50	EM80	0.55	PCF82	0.40	TT22	5.90
6AL5	0.30	35A5	0.80	ECC185	0.50	EM81	0.60	PCF86	0.65	WABC80	0.50
6AQ5	0.50	35B5	0.70	ECC186	0.55	EZ40	0.60	PCF200	0.80	UAF42	0.70
6AT6	0.60	35C5	0.70	ECC187	0.75	EZ41	0.75	PCF201	0.85	UBC41	0.50
6AV6	0.50	35A5	0.80	ECC188	0.40	EZ42	0.85	PCF801	0.55	UBC81	0.50
6AW8A	0.75	35WA	0.60	ECC189	0.80	EL81	0.60	PCF802	0.55	UBF80	0.50
6AU6	0.40	50A5	1.00	ECC180	0.40	EM84	0.40	PCH200	0.75	UBF89	0.50
68A6	0.38	50B5	0.85	ECC181	0.45	EL82	0.60	PCL81	0.55	UCC84	0.75
68E6	0.45	50C5	0.70	ECC182	0.75	EL83	0.60	PCL82	0.40	UCC85	0.50
68H6	0.75	57G3	1.50	ECC183	0.50	EL84	0.35	PCL83	0.70	UCF80	0.75
68J6	0.75	EABC80	0.40	ECC184	0.75	EL90	0.50	PCL84	0.50	UCH42	0.80
68N6	0.80	EAC91	0.55	ECC185	0.42	EY51	0.45	PCL85	0.60	UCH81	0.50
68N8	0.65	EAF42	0.70	ECC186	0.50	EL500	0.80	PCL86	0.60	UCL82	0.40
68Z6	0.55	EAF801	0.65	ECC187	0.60	EM80	0.55	PCL200	0.75	UCL83	0.70
68Z7	0.70	EBC41	0.75	ECC188	0.50	EM81	0.60	P0500	1.70	UF41	0.75
6CA	0.40	EBC81	0.75	ECC189	0.40	EM84	0.40	PFL200	0.70	UF42	0.75
6CB6	0.50	EBF80	0.50	ECL81	0.75	EY51	0.45	PL35	0.40	UF80	0.40
6EAB	0.75	EBF83	0.50	ECL82	0.42	EY51	0.45	PL36	0.60	UF85	0.50
6GK5	0.70	EBF89	0.40	ECL83	0.75	EY87	0.50	PL38	0.65	UF89	0.50
6GK6	0.65	EC86	0.75	ECL84	0.60	EY88	0.50	PL81	0.55	UL41	0.70
6J4	0.75	EC88	0.75	ECL85	0.65	EZ40	0.60	PL82	0.50	UL84	0.50
6J5GT	0.55	EC91	2.60	ECL86	0.55	EZ41	0.75	PL83	0.50	UY41	0.55
6J6	0.35	ECC40	0.80	ECL800	4.50	EZ80	0.30	PL84	0.50	UY42	0.55
6L6GT	0.60	ECC81	0.45	EF80	0.35	EZ81	0.35	PL95	0.70	UY82	0.60
6SL7GT	0.55	ECC82	0.38	EF85	0.45	GZ34	0.75	PL504	0.90	UY85	0.50

HIGH GAIN DARLINGTON PAIRS

Plastic 3-Lead Case Darlington Pairs. Typical current gain 30,000. Max. collector voltage V_{CB0} 40V. Max. collector current 400mA. IC80-10nA. BC516 PNP £0.80 BC517 NPN £0.80

TRANSISTORS FOR T.V.

R20008B	0.95
R2010B	1.65
BU126	1.55
BU133	1.55
BU208	2.00

Z & I AERO SERVICES LTD.

Head Office: 44A WESTBOURNE GROVE, LONDON W2 5SF
 Tel.: 727 5641 Telex: 261306


Retail Branch:
 75 Tottenham Court Road
 London W1. Tel: 580 8403

WW — 047 FOR FURTHER DETAILS

Displays from major manufacturers backed by our no-quibble guarantee

CMOS from the leading manufacturers only

DISPLAYS

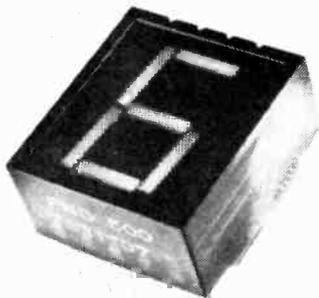

FND500
 Outstanding Value:
 Only **£1.02** each for
 this high quality
 display.

Part No	Manufacturer	Colour	Type	Size	Price
FND500	Fairchild	Red	Common Cathode LED	0.5"	£1.02
TIL322	Texas Instr	Red	Common Cathode LED	13mm	£1.20
TIL321	Texas Instr	Red	Common Anode LED	13mm	£1.30
XAN654	Xciton	Green	Common Cathode LED	0.6"	£1.75
XAN652	Xciton	Green	Common Anode LED	0.6"	£1.75
MAN3M	Monsanto	Red	Common Cathode LED	0.13"	48p
5LT01	Futaba	Green	4 dig Phos Diode	0.5"	£5.80

Note: TIL322 is the Texas Instrument pin-for-pin equivalent of the FND500, may be supplied instead of FND500 - please state if you would not want this substitution, e.g. if you want FND500's to match a previous purchase.

DISPLAY PCB's (wired for multiplexed output - each PCB fits neatly into Veracase J)
 For FND500 or TIL322 or TIL321 D500-6 (6 digit clock) **£1.35**; D500-4 (4 digit clock) **90p**;
 D500-8 (up to 8 digits, counter etc) **£1.35**.
 For DL704 D704-6K (6 digit clock) **£1.35**; D704-8C (up to 8 digit counter) **£1.35**.

ADD VAT at standard rate (now 8%) - 25p p&p on all orders. Price List sent with orders, or on request. Data available on request. Export no VAT 50p (Europe), £1 (Overseas) for Air Mail p&p (no Export outside Europe for databooks and transformers).

SINTEL 53c ASTON STREET, OXFORD
 TEL. 0865 49791

CD4000	0.18	CD4028	0.78	CD4053	0.81	CD4086	0.62	CLOCK CHIPS	
CD4001	0.18	CD4029	0.99	CD4054	1.01	CD4089	1.34	Mk50250	5.00
CD4002	0.18	CD4030	0.48	CD4055	1.14	CD4093	0.69	MK50253	5.60
CD4006	1.02	CD4031	1.92	CD4056	1.14	CD4094	1.62	MK5030M	
CD4007	0.18	CD4032	0.92	CD4057	21.56	CD4095	0.91		12.50
CD4008	0.83	CD4033	1.21	CD4059	4.77	CD4096	0.91	AY1202	2.89
CD4009	0.48	CD4034	1.65	CD4060	0.97	CD4097	3.12	AY51224	3.50
CD4010	0.48	CD4035	1.02	CD4061	18.92	CD4099	1.59		
CD4011	0.18	CD4036	2.23	CD4062	7.77	CD4502	1.07		
CD4012	0.18	CD4037	0.83	CD4063	0.95	CD4510	1.18	FLAT CABLE	
CD4013	0.48	CD4038	0.93	CD4066	0.61	CD4511	1.36	20 WAY 1m	
CD4014	0.87	CD4039	2.23	CD4067	3.12	CD4514	2.72	10 metres	1.00
CD4015	0.87	CD4040	0.92	CD4068	0.20	CD4515	2.72	10 metres	8.50
CD4016	0.48	CD4041	0.73	CD4069	0.20	CD4516	1.18	1D WAY 1m	
CD4017	0.87	CD4042	0.73	CD4070	0.48	CD4518	1.08		0.60
CD4018	0.87	CD4043	0.87	CD4071	0.20	CD4520	1.08	10 metres	4.80
CD4019	0.48	CD4044	0.81	CD4072	0.20	CD4527	1.37		
CD4020	0.97	CD4045	1.22	CD4073	0.20	CD4532	1.25		
CD4021	0.87	CD4046	1.16	CD4075	0.20	CD4555	0.78		
CD4022	6.83	CD4047	0.78	CD4076	1.34	CD4556	0.78		
CD4023	0.18	CD4048	0.48	CD4077	0.48	MC14528	1.01		
CD4024	0.67	CD4049	0.48	CD4078	0.20	MC14534	6.04		
CD4025	0.18	CD4050	0.48	CD4081	0.20	MC14553	4.07		
CD4026	1.50	CD4051	0.81	CD4082	0.20	MC14566	1.21		
CD4027	0.48	CD4052	0.81	CD4085	0.62	MCM14552	8.05	CA3130	0.88

Motorola MCMOS Databook (Vol. 5 Series A) £2.77 (No VAT)
IC SOCKET PINS. Lowest Cost Sockets for CMOS TTL IC's. Displays Strip of 100 pins for **50p**. 400 for £2. 1000 for £4. 3000 for **£10.50**.

Verocases: White ABS Cases with PCB guides etc. front and rear aluminium panels. 75-1410J 205 x 140 x 40mm. **£2.64**. 75-1411D 205 x 140 x 75mm. **£2.94**.

8-way BOSS Switch (for programming, BCD etc.) 8 ultra-min toggle switches in 16 pin DIL **£2.60**

DL704E 0.3" Common Cathode Red LED Now only **75p**

ADVANCED CLOCK KIT. Complete kit including attractive slim case for 6 digit alarm clock with beep alarm, snooze and automatic intensity control high brightness display driving - with optional touch switch controls and crystal control battery back-up (both extra) using MK50253 and Jumbo 0.5" LED displays. Kit also includes PCB's active and passive components, IC socket miniature cool transformer, switches, flat cable, loudspeaker, perspex panel and full instructions. **£26.80**

CRYSTAL TIMEBASE KIT. All components including PCB (47 x 59mm) to provide 50 cps for clock IC's, giving time accurate to a few seconds a month. Kit includes PCB, 32.768 kHz miniature watch crystal, trimmer, 3 CMOS IC's and sockets, C's, R's **£6.28**

Advanced Clock Kit + Crystal Timebase Kit + Battery Back-up Kit **£39.50**

The clock will keep correct time if mains power is disconnected.

32.768 kHz. Min. Watch Quartz Crystal £3.60. 5.12 MHz Quartz Crystal £3.60.

PE CAR CLOCK with Journey Timer. 6 digit clock for use in any car with 12V battery with an independent 6 digit, 24-hour, journey timer incorporated. Jumbo LED display comes on with ignition - automatic intensity control. Complete kit of all parts needed including case, PCB and all components **£39.50**

Easy to Build **EE DIGITAL CLOCK** (Jan '76) Kit of all components including case, PCB, min transformer, etc. to build this attractive 4 digit clock with 0.5" green display **£15.70**

SINTEL

Official Orders Welcomed. Terms 30 days for written or phoned orders from Companies, Govt. Dept's, Nat. Industries, Univs., Polys, etc. **Fast delivery for R&D.**

plus BISPLAYS

BI-PRE-PAK

Bargains in Semi-Conductors, components, modules & equipment.

B-P-P Packs



Originated in 1959 by the Company's managing director, his were the first semi-conductor and component packs to be marketed in this country, and indeed, the company's name grew out of "British Industrial Pre-Pack Components". Today, Bi-Pre-Pak continues to occupy a position of pre-eminence in the supply of packs as well as a vastly extended range of products detailed in our latest 24-page A.4 size free catalogue. Send 10p stamped large addressed envelope for your copy by return.

IT'S ALL IN OUR FREE CATALOGUE

Component Packs

- CP1 150 Capacitors mixed bag of paper, silver mica, electrolytics etc. Approx. quantity counted by weight **60p**
- CP2 200 Resistors mixed bag of different types, values, wattages etc. Approx. quantity counted by weight **60p**
- CP3 40 Wirewound resistors mixed types values and wattages **60p**
- CP4 12 Potentiometers, pre-sets, w/wound carbon etc. Mixed types and values **60p**
- CP5 5 Earphones, single low impedance for transistor radios, cassettes, etc. Less plugs for suitable plugs see PAKs CP9 and CP10 **60p**
- CP6 50 TO-5 mounting pads, fits between transistor and board, for that pro finish **60p**
- CP8 500 Cable clips for G.P.O. 1/4" dia. cable. Nylon with hardened steel pin (probably tungsten) per sealed box of 500 **60p**
- CP9 5 3.5mm plugs, miniature jack, to fit earphones in PAK CP5 **60p**
- CP10 5 2.5mm sub miniature jack plugs, to fit earphones in PAK CP5 **60p**
- CP11 6 Screwdrivers, 1 mains neon tester, 5 x grub screwdrivers **60p**
- CP12 10 Reed relay inserts, 1" long 1/4" dia. These will operate from an external magnet or coil. For magnets see PAK CP13 **60p**
- CP13 10 Magnets of various sizes for operating reed switches on PAK CP12. Ideal for burglar alarms on doors and windows etc. **60p**
- CP14 40 Potentiometers, pre-sets, wirewounds, carbons, dual gangs with and without switches etc. Mixed values and wattages **£1.20**
- CP15 12 Standard crocodile clips, screw fixing, good quality **60p**
- CP16 5 P.C. boards each containing a BF180 UHF amplifier transistor. A good basis for building a T.V. aerial pre-amp as various parts inc. **60p**
- CP17 25 Electrolytic Capacitors, various values and voltages, many useful types, from T.V. to transistor-radio and Hi-Fi **60p**
- CP18 1 Light activated SCR 50 volts 1.6 amps type 19F. Ready mounted on P.C. board with gate resistor and leads fitted. Full data and circuit diagrams for 14 projects, includes slave photo flash unit, burglar alarm, etc. **60p**
- CP19 3 Micro switches 1 pole change over, standard model 1 1/4" x 1/2" **60p**
- CP20 10 Relays, assorted types, Ex-G.P.O. and others, mixed voltages **£1.20**
- CP21 200 Square inches of copper laminate P.C. board, in approx. 8 pieces **60p**
- CP22 3 Fibreglass plain printed circuit boards, approx. 2 1/2" x 14" **60p**
- CP23 4 Switches, miniature push to make, single pole **60p**

YOUR SUPPLIERS FOR:

Semi-conductors — all popular types. Opto-electronic devices inc. Nixie Tubes, Solder Tools, Terminals, Switches, Knobs, Ex-G.P.O. items, Aluminium Boxes, Triacs, Thyristors, Zener Diodes and much more in our catalogue and shop.

Semi-Conductors

TESTED AND GUARANTEED PACKS

- TP4 3 SN7490 integrated circuits, 14 pin dual in line TTL type. Decade counter. Get one FREE these are 60p each in singles **£1.20p**
- TP9 5 SN7400 integrated circuits, 14 pin dual in line TTL type. Quad 2-input NAND gate. Get one FREE these are 15p each
- TP10 2 Light dependant resistors, 400 ohms light 1 megohm dark 1/4" dia
- TP11 10 Transistors XB102 and XB112 equivalent to AC126 AC156 OC81/2 OC72 etc.
- TP12 4 BY127 Silicon rectifiers 1000 p.w. 1 amp. Plastic T.V. rectifier
- TP13 5 OC711 Light sensitive transistors
- TP14 20 OC71 Germanium PNP audio pre amp transistor, black glass type
- TP15 20 OC81 Germanium PNP audio output transistor, white glass type
- TP16 20 OC200 1/2/3 transistors, PNP silicon TO-5 unmarked
- TP17 20 1 watt zener diodes, mixed voltages, 6.8 to 43 volts
- TP18 20 2N3707, 8/9/10 transistors, NPN silicon plastic unmarked
- TP19 100 Diodes, mixture of germanium, gold bonded silicon etc. a useful selection of many types, marked and unmarked
- TP20 10 Mullard OC45 transistors 1F amp. PNP germanium
- TP23 20 BFY50/1/2 2N596/7 2N1613 etc. NPN silicon TO-5 unmarked. COMPLEMENTARY TO PAK TP24
- TP24 20 BFY64 2N2904 5 etc. PNP silicon TO-5 unmarked. COMPLEMENTARY TO PAK TP23
- TP30 20 NPN silicon planar transistors, TO-18 similar to BC108 etc. unmarked
- TP31 20 PNP silicon planar transistors, TO-18 similar to BC178 etc. unmarked
- TP32 20 2N2926 silicon plastic transistors, unmarked and ungraded for colours

UNTESTED PACKS — 60p each Specially for keen bargain hunters

- UT1 50 PNP germanium transistors, AF and RF. Very good yield
- UT2 150 Germanium diodes, miniature glass type
- UT5 40 Zener diodes, 250 mV DAZ240 range, average 50% good
- UT6 25 Zener diodes, 1 1/2 watt top hat type, mixed voltages
- UT9 40 NPN silicon planar transistors, of the 2N3707 11 range, low noise amp.
- UT10 15 Power transistors, PNP germanium and NPN silicon, mostly TO-3 but some plastic and some marked
- UT13 15 Integrated circuits, experiments pak, dual in line, TO-5 TTL, DTL, marked and unmarked, some definitely good but old types

FOR FULL RANGES — SEE CATALOGUE

POWER TRANSISTORS

	Vce	Watts	1cAmps	Price
40P1	15	20	3	30p
40N2	40	40	4	30p
40P2	40	40	4	30p
90N1	15	45	4	25p
90P1	15	45	4	25p
90N2	40	90	8	35p
90P2	40	90	8	35p

Many other types available from 3 to 115 watts

INTEGRATED CIRCUITS

- MM5314 Dual in line clock chip **£3**
- LMS380/SI60745 Dual in line 2w audio amp with data etc **75p**
- Dual in line IC sockets 8 pin 14p; 14 pin 15p; 16 pin 16p

FETs

- 2N3919 18p
- 2N4416 20p
- MOS F.E.T.s 3N141/MEM616 50p

UNI-JUNCTION TRANSISTORS

- 2N2160 65p
- 2N2646 48p
- T1S43 31p

PUTs

- 2N26027 50p

LEDs

- TIL209—Red 18p
- TIL211—Green 33p

Also Power Diodes, Thyristors, Triacs, Diacs-Zener Diodes, Opto-Electronics, etc.

WHEN ORDERING

- Write your own name and address clearly in block capital letters.
- Check that your order is correct for description, quantity and price.
- Don't forget VAT at 12 1/2% of total value of order unless otherwise marked * or 18%.
- MAKE SURE YOU GET OUR NAME AND ADDRESS RIGHT WHEN ORDERING.
- Mention this journal when ordering if you don't want to cut out the coupon.

TERMS OF BUSINESS:

VAT at 12 1/2% must be added to total value of order, except for items marked * or (8%), when VAT is to be added at 8%. No VAT on overseas orders. POST & PACKING add 30p for UK orders except where shown otherwise. Minimum mail order acceptable—£1. Overseas orders add £1 for postage. And difference will be credited or charged. PRICES Subject to alteration without notice. AVAILABILITY All items are available at time of going to press when every effort is made to ensure correctness of information. Cash with order please. Cheques or money orders should be crossed and made payable to Bi-Pre-Pak Ltd.

Singles

BRIDGE RECTIFIERS Plastic encapsulated

P.I.V	50v	100v	400v
1 amp	25p	35p	45p
2 amp	35p	45p	55p
4 amp	45p	50p	80p
6 amp	50p	60p	90p

BY164 equiv. SKB2/02 400v 1.5 amp 45p

Sundry

SIGNAL GENERATOR

For MW and IF. Covers 550 KHz to 1.6 MHz for MW and 400 to 550KHz for IF. Fully portable. Invaluable in AM repair and alignment jobs. (p/p 40p) **£4.25**

POCKET SIGNAL INJECTOR

Fountain pen type. Invaluable for fault tracing in radio sets, amplifiers, TVs, tape recorders etc. Takes one HP7 battery **£2.00**

EX-G.P.O. 5" SIDECUTTERS

Not new but in perfect order. per pair **50p**

EX-G.P.O. 6" LONG NOSE PLIERS

Not new, but in perfect order. per pair **60p**

MAINS TRANSFORMERS

MT6	6v 0.6v 100mA	£1.22
MT12	12v 0.12v 50mA	£1.22
SST9/1	9v 1amp	£1.67
SST12/1	12v 1amp	£2.05
SST18/1	18v 1amp	£2.50
SST25/2	25v 2amp	£3.00
SST30/2	30v 2amp	£4.25
SST35/4	35v 4amp	£5.50

(P/P 50p any one)

PC EDGE CONNECTORS

Type	Sizes	Pitch	
SSEC 6way	1 1/2"	156"	32p
SSEC 10	1 1/4"	156"	50p
SSEC 12	2"	156"	60p
SSEC 16	2 1/2"	156"	75p
SSEC 18	3"	156"	85p
SSEC 22	3 1/2"	156"	1.00

UHF TUNER UNITS

Brand new by famous manufacturer. 625 lines. Channels 21-65. Ideal for use as TV sound receiver. With data **£2.50**

BOOKS

All free of VAT. We carry very large stocks of technical books by Babani & Bernard Publishers, by Newnes and Butterworth as well as reference books from the Common Market in English/German/Italian. All detailed in our catalogue.

MONEY SAVER FOR CAR OWNERS

The Super Spark Mk 5 Capacity Discharge Ignition Unit developed out of our original ETI model (of which we have sold well over 9,000) enables you to enjoy this system at a truly economic price. Facilities include simple adaptation to pos. or neg. earth, immediate switch back to conventional ignition, anti-burglar immobilisation with all parts in totally enclosed strong metal case. Very easy to fit and install. With full instructions (P/P add 50p). "A very good investment indeed" (Practical Wireless, May '76).

KIT £7.95 + READY-BUILT £10.50*

X-44 R.F. POCKET SIZE

CROSS HATCH GENERATOR

Improved version of our famous Mk 2 model of which thousands are in regular use. Size 150x75x50mm, strong plastic case with handle, stand, 4 push button operation, 4 patterns. Self-contained line conventional ignition, anti-burglar immobilisation with all parts in totally enclosed strong metal case. Very easy to fit and install. With full instructions (P/P add 50p). "A very good investment indeed" (Practical Wireless, May '76).

£27.50 *Built & tested

SOME SPECIAL OFFERS

FM STEREO DECODERS

IC unit for negat we earth, with data **£1.95**

Transistorised version for positive earth **£1.75**

RADIO SET CHASSIS

On P.C.B.s, unsorted useful for experimenting etc. Various kinds (cannot be exchanged) AM/FM **£1.00**

AM types each **75p**

BI-PRE-PAK LTD

Co. Reg. No. B201919

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.

TELEPHONE: SOUTHEND (0702) 46344.

● FIRST IN U.K. WITH PACKS FOR ELECTRONIC USERS

To: BI-PRE-PAK, 220/222 WEST RD.
WESTCLIFF-ON-SEA, ESSEX SSO 9DF

Please send me the following items, which I enclose inc. VAT

NAME

ADDRESS

WW7A


Bahrain Singapore Thailand Iceland Brazil Sweden Germany Iran Jamaica St. Kitts Tunisia
 Yugoslavia
 Zambia
 Ghana
 Turkey
 West Africa
 South Africa
 South West Africa
 South
 Guernsey
 Oman
 Norway
 United States
 Hungary
 Muscat
 & Oman
 Cyprus
 Eire
 Hungary
 Switzerland
 Portugal
 Mozambique
 Belgium
 Sumatra

POWERTRAN ELECTRONICS

INCORPORATING

AMBIENTACOUSTICS

HI-FI NEWS 75W/CHANNEL AMPLIFIER

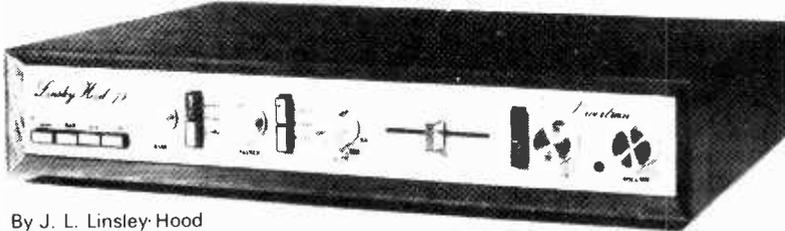

By J. L. Linsley Hood

- | | | | |
|--|--------------|--|--------------|
| Pack | Price | Pack | Price |
| 1. Fibreglass printed-circuit board for power amp | £0.85 | 11. Fibreglass printed-circuit board for power supply | £0.65 |
| 2. Set of resistors, capacitors, pre-sets for power amp | £1.70 | 12. Set of resistors, capacitors, secondary fuses, semi-conductors for power supply | £3.50 |
| 3. Set of semiconductors for power amp | £6.50 | 13. Set of miscellaneous parts including DIN skts, mains input skt, fuse holder, inter-connecting cable, control knobs | £4.25 |
| 4. Pair of 2 drilled, finned heat sinks | £0.80 | 14. Set of metalwork parts including silk screen printed fascia panel and all brackets, fixing parts, etc. | £6.30 |
| 5. Fibreglass printed-circuit board for pre-amp | £1.30 | 15. Handbook | £0.30 |
| 6. Set of low noise resistors, capacitors, pre-sets for pre-amp | £2.70 | 16. Teak cabinet 18.3" x 12.7" x 3.1" | £9.85 |
| 7. Set of low noise, high gain semiconductors for pre-amp | £2.40 | | |
| 8. Set of potentiometers (including mains switch) | £2.05 | | |
| 9. Set of 4 push-button switches, rotary mode switch | £3.70 | | |
| 10. Toroidal transformer complete with magnetic screen/housing primary: 0 117-234 V; secondaries: 33-0-33 V, 25-0-25 V | £9.15 | | |
- 2 each of packs 1-7 inclusive are required for complete stereo system. Total cost of individually purchased packs £72.25

Designed in response to demand for a tuner to complement the world-wide acclaimed Linsley Hood 75W Amplifier, this kit provides the perfect match. The Wireless World published original circuit has been developed further for inclusion into this outstanding slimline unit and features a pre-aligned front end module, excellent a.m. rejection and temperature compensated varicap tuning, which may be controlled either continuously or by push button pre-selection. Frequencies are indicated by a frequency meter and sliding LED indicators, attached to each channel selector pre-set. The PLL stereo decoder incorporates active filters for "birdy" suppression and power is supplied via a toroidal transformer and integrated regulator. For long term stability metal oxide resistors are used throughout.

STOP PRESS !

LINSLEY-HOOD CASSETTE DECK

- | | |
|---|--------|
| Goldring-Lenco mechanism, as specified | £19.10 |
| Stereo P.C.B. (accommodates 2 rec. amps, 2 rec. amps, 2 meter amps, bias/erase osc, relay), 7.3" x 3 7/8" | £3.35 |
| Stereo set of capacitors, M.O. resistors, potentiometers for above | £9.80 |
| Stereo set of semiconductors for above | £8.90 |

FURTHER DETAILS in our FREE LIST

Wireless World Amplifier Designs

Full kits are not available for these projects but component packs and PCBs are stocked for the highly regarded Bailey and 20W class AB Linsley Hood designs, together with an efficient regulated power supply of our own design. Suitable for driving these amplifiers is the Bailey Burrows pre-amplifier and our circuit board, for the stereo version of it features 6 inputs, scratch and rumble filters and wide range tone controls which may be either rotary or slider operating. For those intending to get the best out of their speakers, we also offer an active filter system described by D C Read, which splits the output of each channel from the pre-amplifier into three channels each of which is fed to the appropriate speaker by its own power amplifier. The Read/Texas 20W, or any of our other kits are suitable for these. For tape systems a set of three PCBs have been prepared for the integrated circuit based, high performance stereo Stuart design. Details of component packs are in our free list.

- | | |
|---|-------|
| 30W Bailey Amplifier | £1.00 |
| BAIL Pk 1 F/Glass PCB | £2.35 |
| BAIL Pk 2 Resistors, Capacitors, Potentiometer set | £4.70 |
| BAIL Pk 3 Semiconductor set | |
| 20W Linsley Hood Class AB | £1.05 |
| LHAB Pk 1 F/Glass PCB | £3.20 |
| LHAB Pk 2 Resistor, Capacitor, Potentiometer set | £3.35 |
| LHAB Pk 3 Semiconductor set | |
| Regulated Power Supply | £0.85 |
| 60VS Pk 1 F/Glass PCB | £1.95 |
| 60VS Pk 2 Resistor, Capacitor set | £3.10 |
| 60VS Pk 3 Semiconductor set | £7.95 |
| 60VS Pk 6A Toroidal transformer (for use with Bailey) | £7.25 |
| 60VS Pk 6B Toroidal transformer (for use with 20W LH) | |
| Bailey Burrows Stereo Pre-Amp | £2.35 |
| BBPA Pk 1 F/Glass PCB | £6.10 |
| BBPA Pk 2 Resistor, capacitor semiconductor set | £2.40 |
| BBPA Pk 3R Rotary Potentiometer set | £2.70 |
| BBPA Pk 3S Slider Potentiometer set with knobs | |

Further details of above and additional packs given in our FREE LIST

In Hi-Fi News there was published by Mr Linsley-Hood a series of four articles (November, 1972-February, 1973) and a subsequent follow-up article (April, 1974) on a design for an amplifier of exceptional performance which has as its principal feature an ability to supply from a direct coupled fully protected output stage, power in excess of 75 watts whilst maintaining distortion at less than 0.01% even at very low power levels. The power amplifier is complemented by a pre-amplifier based on a discrete component operational amplifier referred to as the Liniac which is employed in the two most critical points of the system, namely the equalization stage and tone control stage, positions where most conventional designs run out of gain at the extremes of the frequency spectrum. Unusual features of the design are the variable transition frequencies of the tone controls and the variable slope of the scratch filter. There is a choice of four inputs, two equalized and two linear, each having independently adjustable signal level. The attractive slimline unit pictured has been made practical by highly compact PCBs and a specially designed Toroidal transformer.

FREE TEAK CASE WITH FULL KITS
£62.40
 KIT PRICE ONLY

WIRELESS WORLD FM TUNER



- | | | | |
|--|--------------|--|--------------|
| Pack | Price | Pack | Price |
| 1. Fibreglass printed board for front end IF strip, demodulator, AFC and mute circuits | £2.15 | 9. Function switch, 10 turn tuning potentiometer, knobs | £5.30 |
| 2. Set of metal oxide resistors, thermistor, capacitors, ceramic preset for mounting on pack 1 | £4.80 | 10. Frequency meter, meter drive components, fibreglass printed circuit board | £8.60 |
| 3. Set of transistors, diodes, LED, integrated circuits for mounting on pack 1 | £6.25 | 11. Toroidal transformer with electrostatic screen, Primary: 0-117V-234V | £4.45 |
| 4. Pre-aligned front end module, coil assembly, three section ceramic filter | £8.80 | 12. Set of capacitors, rectifiers, voltage regulator for power supply | £2.95 |
| 5. Fibreglass printed circuit board for stereo decoder | £1.10 | 13. Set of miscellaneous parts, including sockets, fuse holder, fuses, inter-connecting wire, etc. | £1.50 |
| 6. Set of metal oxide resistors, capacitors, ceramic preset for decoder | £2.60 | 14. Set of metal work parts including silk screen printed fascia panel, acrylic silk screen printed tuning indicator panel insert, internal screen, fixing parts, etc. | £6.50 |
| 7. Set of transistors LED, integrated circuit for decoder | £3.45 | 15. Construction notes (free with complete kit) | £0.25 |
| 8. Set of components for channel selector switch, module including fibreglass printed circuit board, push-button switches, knobs, LEDs, preset adjusters, etc. | £8.30 | 16. Teak cabinet 18.3" x 12.7" x 3.1" | £9.85 |

One each of packs 1-16 inclusive are required for complete stereo FM tuner. Total cost of individually purchased packs £76.85

FREE TEAK CASE WITH FULL KITS
£66.75
 KIT PRICE ONLY

PRICE STABILITY!

Order with confidence! Irrespective of any price changes we will honour all prices in this advertisement for two months from issue date provided that this advertisement is quoted with your order. E&OE VAT rate changes excluded. All components are brand new first grade full specification devices. All resistors (except where stated) are low noise carbon film types. All printed circuit boards are fibre-glass, drilled, roller tinned and supplied with circuit diagrams and construction layouts. U.K. Orders. Subject to 12½% Surcharge for VAT. Carriage free MAIL ORDER ONLY (or at current rate if changed). Securicor Delivery. For this optional service (Mainland only) add £2.50 VAT inc. per kit. Overseas Orders. No VAT. Postage charged at actual cost plus 50p packing and handling.

DEPT. WW07


POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE
 ANDOVER, HANTS SP10 3NN

Hong Kong Jersey Australia St. Lucia India Barbados Antigua Jordan Spain Israel Mauritius St. Vincent Uganda Ascension Island Malta Sierra Leone Somalia New Guinea Italy Kuwait Netherlands Canada Trinidad Malaya Austria

AUDIO KIT SUPPLIERS TO THE WORLD

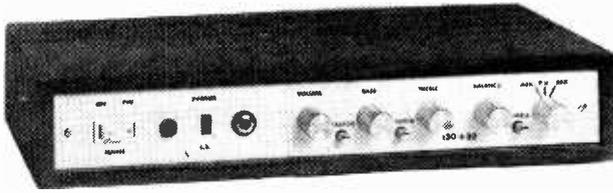T20 + 20 and our new T30 + 30 20W, 30W AMPLIFIERS



Designed by Texas engineers and described in Practical Wireless the Texan was an immediate success. Now developed further in our laboratories to include a Toroidal transformer and additional improvements, the slimline T20 + 20 delivers 20W per channel of true Hi-Fi at exceptionally low cost. The design is based on a single F/Glass PCB and features all the normal facilities found on quality amplifiers, including scratch and rumble filters, adaptable input selector and head phones socket. In a follow up article in Practical Wireless further modifications were suggested and these have been incorporated into the T30 + 30. These include RF interference filters and a tape monitor facility. Power output of this new model is 30W per channel.

Pack	T20	T30	Pack	T20	T30
1. Set of low noise resistors	0.95	1.05	8. Toroidal transformer - 240V prim. a.s. screen	4.95	6.80
2. Set of small capacitors	1.50	2.10	9. Fibreglass PCB	2.50	2.90
3. Set of power supply capacitors	1.40	2.05	10. Set of metalwork, fixing parts	4.20	4.80
4. Set of miscellaneous parts	1.90	1.90	11. Set of cables, mains lead	0.40	0.40
5. Set of slide, mains, P.B. switches	1.20	1.20	12. Handbook (free with complete kit)	0.25	0.25
6. Set of pots, selector switch	2.00	2.00	13. Teak cabinet 15.4" x 6.7" x 2.8"	4.50	4.50
7. Set of semiconductors, ICs, skts.	7.25	7.75			

FREE TEAK CASE WITH FULL KITS

T20 + 20
KIT PRICE only **£28.25**


T30 + 30
KIT PRICE only **£32.95**

2 NEW TUNERS!

WW SFMT II

Following the success of our Wireless World FM Tuner kit we are now pleased to introduce our new cost reduced model, designed to complement the T20 and T30 amplifiers. The frequency meter of the more advanced model has been omitted and the mechanics simplified, however the circuitry is identical and this new kit offers most exceptional value for money. Facilities included are switchable afc, adjustable, switchable muting, channel selection by slider or readily adjustable pre-set push-button controls and LED tuning indication. Individual pack prices in our free list.


KIT PRICE
£47.40

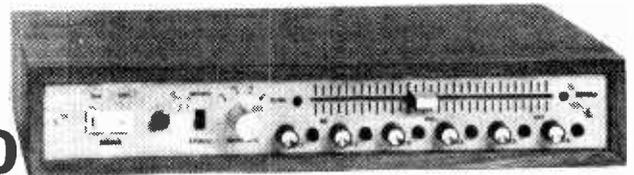

POWERTRAN SFMT

This easy to construct tuner using our own circuit design includes a pre-aligned front end module, PLL stereo decoder, adjustable, switchable muting, switchable afc and push-button channel selection. As with all our full kits, all components down to the last nut and bolt are supplied together with full constructional details.

KIT PRICE
£32.60

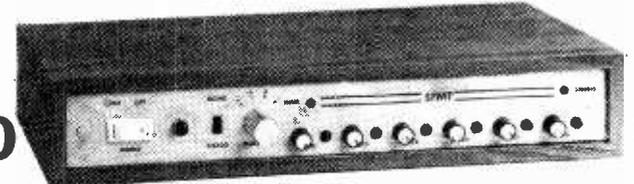

CONVERT NOW TO QUADRAPHONICS!



SQM1 - 30
KIT PRICE **£37.15**

With 100s of titles now available no longer is there any problem over suitable software. No problems with hardware either. Our new unit the SQM1-30 simply plugs into the tape monitor socket of your existing amplifier and drives two additional speakers at 30W per channel. A full complement of controls including volume, bass, treble and balance are provided as are comprehensive switching facilities enabling the unit to be used for either front or rear channels, by-passing the decoder for stereo-only use and exchanging left and right channels. The SQ matrix decoder is based upon a single integrated circuit and was designed by CBS whilst the power and tone control sections are identical to those used in our T30 + 30 amplifier which the SQM1-30 matches perfectly. Kit price includes CBS licence fee. **Special offer to T20 + 20 and Texan owners!** Owners of T20 + 20 and Texan amplifiers, which have no tape monitor outlet, purchasing an SQM1-30 will be supplied, on request, a free conversion kit to fit a tape monitoring facility to the existing amplifier. This makes simple the connection to the highly adaptable SQM1-30 quadraphonic decoder/rear channel amplifier.





SEMICONDUCTORS

as used in our range of quality audio equipment.

2N699	£0.20	BC212K	£0.12	MPSA65	£0.35
2N1613	£0.20	BC182L	£0.10	MPSA66	£0.40
2N1711	£0.25	BC184L	£0.14	MPSU05	£0.60
2N2926G	£0.10	BC212L	£0.12	MPSU55	£0.70
2N3055	£0.45	BC214L	£0.14	SBA750A	£2.50
2N3442	£1.20	BCY72	£0.13	SL301	£1.30
2N3711	£0.09	BD529	£0.83	SL3045	£1.60
2N3904	£0.17	BD530	£0.85	SN72741P	£0.40
2N3906	£0.20	BDY56	£1.60	SN72748P	£0.40
2N4062	£0.11	BF257	£0.40	TIL209	£0.30
2N4302	£0.60	BF259	£0.47	TIP29A	£0.50
2N5087	£0.42	BFR39	£0.25	TIP30A	£0.60
2N5210	£0.54	BFR79	£0.25	TIP29C	£0.71
2N5457	£0.45	BFY51	£0.20	TIP30C	£0.78
2N5459	£0.45	BFY52	£0.20	TIP41A	£0.74
2N5461	£0.50	CA3046	£0.70	TIP42A	£0.90
2N5830	£0.35	LP1186	£5.50	TIP41B	£0.82
40361	£0.40	MC1310	£2.90	TIP42B	£0.98
40362	£0.45	MC1351	£1.05	1N914	£0.07
BC107	£0.10	MYC4010	£0.95	1N916	£0.07
BC108	£0.10	MJ481	£1.20	1S320	£0.10
BC109	£0.10	MJ491	£1.30	5B65	£1.20
BC109C	£0.12	MJE521	£0.60		
BC125	£0.15	MPSA05	£0.25	FILTERS	
BC126	£0.15	MPSA12	£0.55	FM4	£0.80
BC182	£0.10	MPSA14	£0.35	SFG10 7MA	£2.80
BC212	£0.12	MPSA55	£0.25		
BC182K	£0.10				

SQ QUADRAPHONIC DECODERS

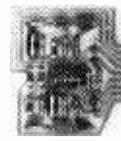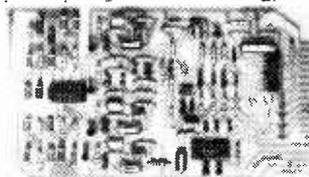

Feed 2 channels (200-1000mV as obtainable from most pre-amplifiers or amplifier tape monitor outlets) into any one of our 3 decoders and take 4 channels out with no overall signal level reduction. On the logic enhanced decoders Volume, Front-Back, LF-RF balance, LB-RB balance and Dimension controls can all be implemented by simple single gang potentiometers. These state-of-the-art circuits used under licence from CBS are offered in kits of superior quality with close tolerance capacitors, metal oxide resistors and fibre-glass PCBs designed for edge connector insertion. All kit prices include CBS licence fee.


M1 Basic matrix decoder with fixed 10:40 blend. All components, PCB **£5.90**
 L1 Full logic controlled decoder with "wave matching" and "front back logic" for enhanced channel separation. All components PCB **£17.20**
 L2A More advanced full logic decoder with "variable blend", extended frequency response, increased front back separation. All components, PCB **£24.60**

EXPORT NO PROBLEM

Our Export Department will be pleased to advise on postal costs to any country in the world. Some of the countries to which we sent kits in 1975 are shown surrounding this advertisement.

Kenya France St. Martin, Java New Zealand Borneo South Africa Denmark Nigeria Anguilla Finland

Ten into one will go.

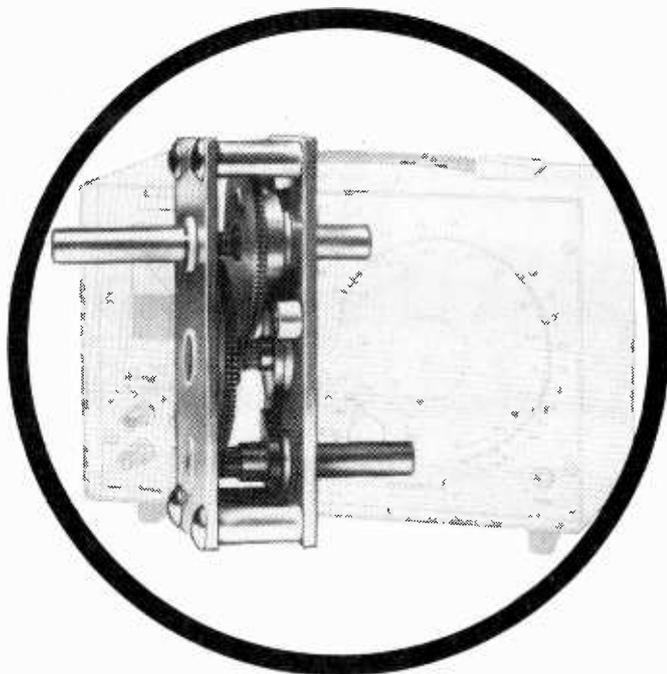

With the precision of the Jackson G10 Gearbox, you get ten turns of input equalling one effective turn of output. This makes the G10 ideal for decimal presentation for analog control. The Gear Box itself is packaged within 70mm by 35mm by 19mm. The output shaft drive torque is greater than 700 gm cms. Input shaft diameters are 6mm. All the gears are fully anti-backlash loaded. The Jackson G10, the compact, versatile gearbox.

All Jackson Products are backed by 50 years' experience in the communications field. Highly skilled men, and Jackson Brothers' good name.



Write for further information to:
**JACKSON BROTHERS
(LONDON) LIMITED**

Kingsway, Waddon, Croydon CR9 4DG
Tel: 01-681 2754/7 Telex 946849
U.S. Office: Swedgal Electronics Inc.,
258 Broadway, New York, N.Y. 10007
B.S. 9000 Approved. DEF STAN 05-21.

WW — 007 FOR FURTHER DETAILS

Join the Digital Revolution

Understand the latest developments in calculators, computers, watches, telephones, television, automotive instrumentation . . .

Each of the 6 volumes of this self-instruction course measures 11 3/4" x 8 1/4" and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers.

Design of Digital Systems.



£6.20

plus 80p packing and surface post anywhere in the world.

Payments may be made in foreign currencies.

Quantity discounts available on request.

VAT zero rated.

Also available — a more elementary course assuming no prior knowledge except simple arithmetic.

Digital Computer Logic and Electronics.

In 4 volumes:

1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flipflops and Registers

£4.20

plus 80p P. & P.

Offer Order both courses for the bargain price £9.70, plus 80p P. & P.

**Designer
Manager
Enthusiast
Scientist
Engineer
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

Guarantee—no risk to you

If you are not entirely satisfied with Design of Digital Systems or Digital Computer Logic and Electronics, you may return them to us and your money will be refunded in full, no questions asked.

To: Cambridge Learning Enterprises, Dept COM
FREEPOST, St. Ives, Huntingdon, Cambs. PE17 4BR
*Please send me . . . set(s) of Design of Digital Systems at £7.00 each, p & p included

*or . . . set(s) of Digital Computer Logic and Electronics at £5.00 each, p & p included

*or . . . combined set(s) at £10.50 each, p & p included

Name

Address

*delete as applicable

No need to use a stamp — just print FREEPOST on the envelope.

WW7

Make it with MAPLIN!


ELECTRONIC COMPONENTS
WIDE RANGE • HIGH QUALITY • FAST SERVICE

The 4600 SYNTHESISER



We stock all the parts for this brilliantly designed synthesiser, including all the PCB's, metalwork and a drilled and printed front panel, giving a superb professional finish. Opinions of authority agree the ETI International Synthesiser is technically superior to most of today's models. Complete construction details in our booklet now available price £1.50, or send SAE for specification.

ELECTRONIC ORGAN

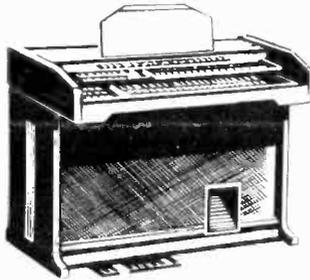


BUILD IT YOURSELF . . . IN STAGES

Get started with a 49 note instrument — features tremulant and reverberation. Ideal to learn on. Leaflet MES 51. Price 15p gives full details to build this complete instrument. Extend the range of MES 51 by adding another keyboard and several new tone colours. Leaflet MES 52. Price 15p also shows how to use 61 note keyboards.

Fully controllable attack and delay controls (normally found only on the most expensive organs), up to seven footages on each keyboard, up to 70 controls including drawbars, and a 13 note pedalboard, make up the additions described in the step-by-step 32 page instruction leaflet MES 53. Price 35p.


GRAPHIC EQUALIZER

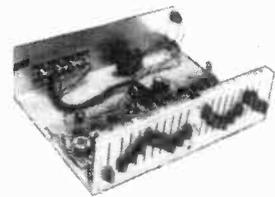

A really superior high quality stereo graphic equalizer featuring 9 octaves per channel. We stock all the parts (except woodwork) including the metalwork drilled and printed. 15p brings you a reprint of the article.

DIGITAL CLOCK KITS

ONLY **£8.60** INC. VAT
E/P/P

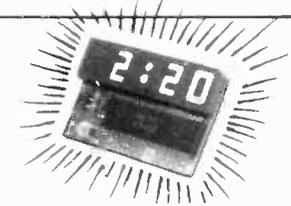

This is a fully constructed and tested electronic clock module as illustrated. Data sheet supplied. Simple to connect to alarm and your battery/mains radio. Smart case available shortly. Data sheet available separately. Please send SAE.

- ★ Bright 4 Digit 0.5" Display
- ★ Flashing Colon (1Hz)
- ★ Switch for Display Seconds
- ★ Alarm Set Indicator
- ★ P.M. Indicator
- ★ Power Failure Indicator
- ★ Sleep Timer
- ★ Snooze Timer
- ★ Time can be set accurately to within one second
- ★ Leading Zero Blanking

SIMPLE ALARM KIT — £9.38 ALARM CLOCK KIT — £10.99
ALARM CLOCK & RADIO CONTROLLER KIT — £11.51
SMART PLASTIC CASE with fully punched chassis — £2.49
Please send SAE for our Clock data sheet



100 W PER CHANNEL STEREO DISCO

- ★ Automatic voice operated fader
- ★ Belt drive turntables
- ★ Monitor facilities (Headphones and VU meter)
- ★ Sound operated light show — plus many other advantages

Send for our leaflet MES 41, giving full details for construction. Price 20p. Soon you'll be the Deejay everyone wants at their party!

Get our FABULOUS NEW 1977/78 CATALOGUE

PUBLICATION DATE OCT. 28, 1976 ON APPROVAL

All new ● Completely re-written ● Hundreds of new lines
Lots of exciting new projects to build — PRICE 50p
SEND NO MONEY NOW. Overseas send 8 International reply coupons.

JOIN OUR MAILING LIST NOW!

Published every two months our Newsletter gives full details of our latest guaranteed prices.

- ★ SAVE ££'s ON SPECIAL OFFERS!
- ★ DETAILS OF NEW PROJECTS AND NEW LINES

Send just 30p towards cost of postage and we'll send you the next six issues as they are published. (A 5p voucher is sent with each newsletter which may be used on purchases.)

Please rush me a copy of your brand new 1977/78 catalogue the instant it is printed (Oct. 28th, 1976). Only if I am completely satisfied that it is worth every penny will I send 50p within 14 days of receipt. If I am not satisfied I may return the catalogue to you within 14 days without obligation. I understand that I need not purchase anything from your catalogue should I choose to keep it.

NAME _____
ADDRESS _____



MAPLIN ELECTRONIC SUPPLIES
All mail to: P O Box 3, Rayleigh, Essex SS6 8LR
Shop 284 London Road, Westcliff-on-Sea, Essex
(Closed on Monday). Tel Southend (0702) 44101

If you do not wish to cut magazine, write your request for catalogue on separate sheet
1975/76 GREEN COVER CATALOGUE STILL AVAILABLE PRICE 40p

15 — 240 Watts!

HY5 Preamplifier


The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc) are catered for internally. The desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: Complete pre-amplifier in single pack — Multi function equalization — Low noise — Low distortion — High overload — Two simply combined for stereo

APPLICATIONS: Hi-Fi — Mixers — Disco — Guitar and Organ — Public address

SPECIFICATIONS:

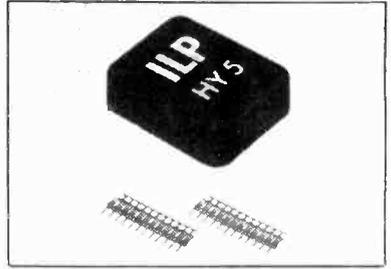INPUTS: Magnetic Pick-up 3mV, Ceramic Pick-up 30mV, Tuner 100mV, Microphone 10mV, Auxiliary 3-100mV, input impedance 47k Ω at 1kHz
OUTPUTS: Tape 100mV, Main output 500mV R.M.S.
ACTIVE TONE CONTROLS: Treble +12dB at 10kHz, Bass - at 100Hz
DISTORTION: 0.1% at 1kHz, Signal Noise Ratio 68dB
OVERLOAD: 38dB on Magnetic Pick-up, SUPPLY VOLTAGE: 16-50V
Price £4.75 + 59p VAT P&P free.



HY30 15 Watts into 8 Ω

The HY30 is an exciting New kit from I.L.P. it features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

FEATURES: Complete Kit — Low Distortion — Short, Open and Thermal Protection — Easy to Build
APPLICATIONS: Updating audio equipment — Guitar practice amplifier — Test amplifier — audio oscillator

SPECIFICATIONS:

OUTPUT POWER: 15W R.M.S. into 8 Ω ! **DISTORTION:** 0.1% at 15W
INPUT SENSITIVITY: 500mV **FREQUENCY RESPONSE:** 10Hz-16kHz — 3dB
SUPPLY VOLTAGE: 18V
Price £4.75 + 59p VAT P&P free.

Available
June '76

HY50 25 Watts into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: Low Distortion — Integral Heatsink — Only five connections — 7 Amp output transistors — No external components

APPLICATIONS: Medium Power Hi-Fi systems — Low power disco — Guitar amplifier

SPECIFICATIONS: INPUT SENSITIVITY 500mV

OUTPUT POWER: 25W RMS into 8 Ω ! **LOAD IMPEDANCE:** 4-16 Ω ! **DISTORTION:** 0.04% at 25W at 1kHz
SIGNAL NOISE RATIO: 75dB **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB
SUPPLY VOLTAGE: 25V **SIZE:** 105 50 25mm
Price £6.20 + 77p VAT P&P free.



HY120 60 Watts into 8 Ω


The HY120 is the baby of I.L.P.'s new high power range designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: Very low distortion — Integral heatsink — Load line protection — Thermal protection — Five connections — No external components

APPLICATIONS: Hi-Fi — High quality disco — Public address — Monitor amplifier — Guitar and organ

SPECIFICATIONS:

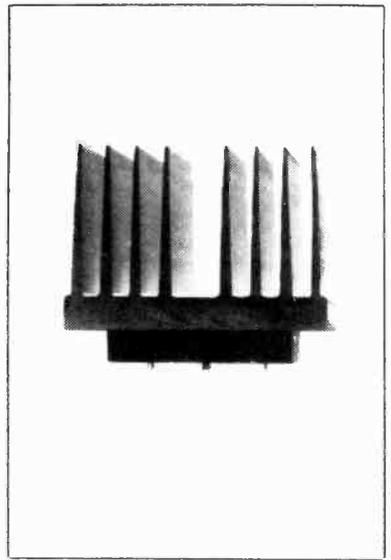INPUT SENSITIVITY: 500mV
OUTPUT POWER: 60W RMS into 8 Ω ! **LOAD IMPEDANCE:** 4-16 Ω ! **DISTORTION:** 0.04% at 60W at 1kHz
SIGNAL NOISE RATIO: 90dB **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB **SUPPLY VOLTAGE:** 35V
SIZE: 114 50 85mm
Price £14.40 + £1.16 VAT P&P free.



HY200 120 Watts into 8 Ω

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

FEATURES: Thermal shutdown — Very low distortion — Load line protection — Integral heatsink — No external components

APPLICATIONS: Hi-Fi — Disco — Monitor — Power slave — Industrial — Public Address

SPECIFICATIONS:

INPUT SENSITIVITY: 500mV
OUTPUT POWER: 120W RMS into 8 Ω ! **LOAD IMPEDANCE:** 4-16 Ω ! **DISTORTION:** 0.05% at 100W at 1kHz
SIGNAL NOISE RATIO: 96 dB **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB **SUPPLY VOLTAGE:** 45V
SIZE: 114 100 85mm
Price £21.20 + £1.70 VAT P&P free.

HY400 240 Watts into 4 Ω


The HY400 is I.L.P.'s 'Big Daddy' of the range producing 240W into 4 Ω ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: Thermal shutdown — Very low distortion — Load line protection — No external components

APPLICATIONS: Public address — Disco — Power slave — Industrial

SPECIFICATIONS:

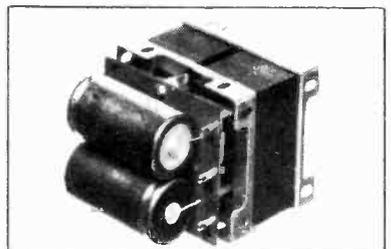OUTPUT POWER: 240W RMS into 4 Ω ! **LOAD IMPEDANCE:** 4-16 Ω ! **DISTORTION:** 0.1% at 240W at 1kHz
SIGNAL NOISE RATIO: 94dB **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB **SUPPLY VOLTAGE:** 45V
INPUT SENSITIVITY: 500mV **SIZE:** 114x100x85mm
Price £29.25 + £2.34 VAT P&P free.



POWER SUPPLIES

PSU36 suitable for two HY30's £4.75 plus 59p VAT P.P. free
 PSU50 suitable for two HY50's £6.20 plus 77p VAT P.P. free
 PSU70 suitable for two HY120's £12.50 plus 1.00 VAT P.P. free
 PSU90 suitable for one HY200 £11.50 plus 1.00 VAT P.P. free
 PSU180 suitable for two HY200's or one HY400 £21.00 plus 1.68 VAT P.P. free

TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS

I.L.P. Electronics Ltd
 Crossland House
 Nackington, Canterbury
 Kent CT4 7AD
 Tel (0227) 63218

Please Supply _____
 Total Purchase Price _____
 I Enclose Cheque Postal Orders Money Order
 Please debit my Access account Barclaycard account
 Account number _____
 Name & Address _____
 Signature _____

WW — 019 FOR FURTHER DETAILS

P. F. RALFE

10 CHAPEL ST. LONDON NW1.
Phone 01-723 8753

SIGNAL GENERATORS

MARCONI TF801D/1S. 10-480 mHz P.O.A.
MARCONI TF801B/2S. 10-480 mHz £225.
HGN MS3/U. 9.7-11.9 and 77-109 mHz. AM/FM.
ADVANCE SG63D. AM/FM 7.5-230mHz £125.
RACAL/AIRMEC 201A. 30kHz-30mHz. As new. P.O.A.
ADVANCE SG21 VHF Square-wave generator 9kHz-100mHz. £25.



OSCILLOSCOPES

SOLARTRON CD1400 DC-15mHz.
COSSOR CDU110. DC-80mHz.
TEKTRONIX 545A with CA unit. DC-30mHz. Price only £295.00
TEKTRONIX 531 DC-15mHz with L type plug-in
TEKTRONIX 535 DC-15mHz with L type plug-in
TEKTRONIX 545B DC-30mHz with 'CA' plug-in.
TEKTRONIX 585A. DC-80mHz with type 82 plug-in.
TEKTRONIX 654B. Storage oscilloscope.
TEKTRONIX 502. 200uV. Sens. X-Y.
TEKTRONIX C27 Polaroid Camera. Series 125 with 560 series adapter.



CO-AXIAL CHANGE OVER RELAYS. Terminated in 'N'-type sockets (3 off). Suitable for frequencies up to 1GHz. 48V.D.C. coil. Plugs available at 50p each. Relay only £5.50 each.

PRINTED CIRCUIT MOTORS. Manufactured in U.S. by Photocircuits Corp. 24 V.D.C. 2,000 rpm. 14 cms diameter. These are quality made, high precision motors offered at a fraction of list price. Only £8.50 each

"WEE MEGGERS". 250V Insulation Testers. Good working condition £8.50.

'MUFFIN' INSTRUMENT FANS. Manufactured in Holland by Rotron. Dims. 4.5x4.5x1.5 ins. This is a precision cooling fan, very quiet running specially designed for the cooling of electronic equipment, amplifiers, etc. 115V.50Hz operation, drawing only 11 Watts. The list price from Rotrons is over £10 each. Our price, brand new, only £4.50 each

MINIATURE DEAC NI-CADMIUM batteries, type 70DK. 3 cells in package making 3.7 Volts 25x17x15mm only 75p post paid.

DAWE Stroboscope type 1202C. Excellent condition £85.00
MARCONI TF2700 Universal Bridge LC&R £100
PYE Electrostatic Voltmeter reads up to 40KV RMS £120.00
TEKTRONIX type 575 Transistor curve tracer excellent condition

ADVANCE type 63A AM/FM R.F. Signal generators. 7.5-230mHz. Deviation 0-22.5 and 0-75 kHz. X-sweep output. Crystal calibrator. scope output £75.00.

MARCONI TF995A2/M AM/FM R.F. SIGNAL GENERATORS. 1.5-220mHz. 0-100kHz Deviation. 1µV-100mV output. Sold in excellent condition. P.O.A.

METRIX 210 WOBBLATORS. 0.25mHz. Sweep width 0.5-20mHz. Output 100mV attenuable in steps of 10 to 10uV. Last few of these left at only £15.00 each to callers only.

E. M. I. oscilloscopes model WM16 with type 7/1 W.B.A. plug-in unit. Supplied in perfect condition complete with trolley. £125.00.

20-way BPO Jack strips to accept 316 type Jack plugs. Also quantity of 316 plugs available. All good condition.

Centrifugal blowers by WOODS. 8 inch snail type Outlet 2 1/2 x 2in 24V DC 2 BA 2400 r.p.m. Grey stove finish. All brand new. Price is £10.50 + carriage.

GENTS/FRIEDLAND fire alarm bells. Operating voltages 12v dc/24v dc. All in as new condition and tested before despatch. Sizes 6/8/12 inch. Prices £4.80, £5.20 and £6.50 resp.

COMPUTER PERIPHERALS. Tape punches, 8 hole by Westrex and other well known manufacturers. Tape readers by Elliot. All virtually brand new. Prices are better than one half the maker's. Write or phone for quotation

An exceptional buy enables us to offer stabilised and regulated power supplies by APT at a very cheap price. 16-24v dc @ 10 Amps, and 8-10v dc @ A. Both supplies are extremely stable with low ripple voltage. Price each £18.50 + carriage.

MISCELLANEOUS TEST EQUIPMENT

MARCONI TF1400S double pulse generator with TM6600/S secondary pulse unit. £105.
MARCONI TF791D deviation meter, 4-1024mHz. 0-100kHz deviation.
MARCONI 455E Wave Analyser £120.
MARCONI TF2600 Valve Voltmeter 1mV-300V. Excellent. £75.
ROHDE & SCHWARZ USVD calibrated receiver 280-940mHz (4600mHz)
LEVELL TG200 DM. RC Oscillator, c/w case. £65.
ROHDE & SCHWARZ URV milli-voltmeter BN10913 (late type) 1mV-10V. With 'T' type insertion unit, free probe and attenuator heads. 1kHz-1.600mHz. £175.
COSSOR 1453 True RMS milli-voltmeter. Excellent. £75.
AIRMEC TYPE 210 modulation meter. Excellent condition.
ROHDE & SCHWARZ "SCR" V.H.F. Signal Generator 1000-1900 mHz.
MAKONIX type TF936 Impedance Bridge. £85.00.
GERTCH Phase Angle V. Meters. Range 1mV-300V, in 12 ranges.
SOLARTRON oscillator type CO 546. 25Hz-500kHz £30.00.
GAMBRELL Precision 4 Decade Resistance Box. 1-11, 110 ohms. £24.50.
MARCONI TF329G Q-Meter £95.

PLEASE ADD 8% V.A.T. TO THE TOTAL AMOUNT WHEN ORDERING. INCORRECT AMOUNTS WILL CAUSE DELAY IN DESPATCH. THANK YOU.

TRANSFORMERS

ALL EX-STOCK — SAME-DAY DESPATCH

MAINS ISOLATING VAT 8% 12 and/or 24-VOLT

Ref.	VA (Watts)		£	P&P	Ref.	AMPS		£	P&P
	12v	24v				12v	24v		
07*	20		£3.10	58	111	0.5	0.25	1.54	28
149	60		4.69	72	213	1.0	0.5	1.86	58
150	100		5.33	85	71	2	1	2.41	58
151	200		8.54	112	18	4	2	2.97	72
152	250		10.32	141	70	6	3	4.43	72
153	350		12.47	141	108	8	4	5.09	85
154	500		14.33	161	72	10	5	5.50	85
155	750		21.94	BRS	118	12	6	5.80	97
156	1000		30.51	BRS	17	16	8	7.48	97
157	1500		34.89	BRS	15	20	10	10.91	161
158	2000		38.92	BRS	18*	30	15	14.20	141
159	3000		61.48	BRS	22*	60	30	17.67	BRS

50 VOLT RANGE

SEC TAPS 0-19-25 33-40-50V

Ref.	Amps	£	P&P
102	0.5	2.71	58
103	1.0	3.55	72
104	2.0	4.95	85
105	3.0	6.10	87
106	4.0	7.98	112
107	6.0	12.71	125
118	8.0	13.63	161
119	10.0	17.75	BRS

30 VOLT RANGE

SEC TAPS 0-12-15-20-25-30V

Ref.	Amps	£	P&P
112	0.5	1.90	58
75	1.0	2.52	72
3	2.0	3.77	72
20	3.0	4.70	85
21	4.0	5.56	85
51	5.0	6.73	97
117	6.0	7.52	112
88	8.0	10.20	125
89	10.0	10.36	141

60 VOLT RANGE

SEC TAPS 0-24-30-40-48-60V

Ref.	Amps	£	P&P
124	0.5	2.48	72
126	1.0	3.68	72
127	2.0	5.33	85
125	3.0	7.90	87
123	4.0	9.19	141
40	5.0	10.24	125
120	6.0	12.07	141
121	8.0	15.75	BRS
122	10.0	19.40	BRS
189	12.0	20.25	BRS

AUTO TRANSFORMERS

Ref.	VA (Watts)	AUTO TAPS	£	P&P
113	20	0-115-210-240V	1.75	51
64	75	0-115-210-240V	3.05	72
4	150	0-115-210-240V	4.33	72
66	300		6.11	85
67	500		9.36	125
84	1000		14.36	161
93	1500		19.02	BRS
95	2000		25.41	BRS
73	3000		36.84	BRS

SCREENED MINIATURES

Ref.	mA	Volts	£	P&P
238	200	3-0-3	1.62	39
212	1A, 1A	0-6-0-6	1.93	49
13	330, 330	9-0-9	1.56	29
235	500, 500	0-9-0-9	1.64	25
207	1A, 1A	0-8-9, 0-8-9	2.02	51
208	200, 200	0-8-9, 0-8-9	3.07	48
236	300, 300	0-15-0-15	1.56	25
214	1A, 1A	0-20-0-20	2.03	58
221	500, 500	20-12-0-12-20	2.38	58
206	1A, 1A	0-15-20, 0-15-20	3.63	72
203	500, 500	0-15-27, 0-15-27	3.15	72
204	1A, 1A	0-15-27, 0-15-27	4.14	72
S112	500	12, 15, 20, 24, 30	1.97	58

ON-SITE TOOL ISOLATORS

240v to 110v (To BS3535)

Ref.	VA	£
277	500	29.96
278	750	34.47
279	1000	37.63
280	1500	41.55

P&P BRS Send for details

BRIDGE RECTIFIERS

Ref.	VA	£
50v	2A	35p
100v	2A	40p
100v	6A	70p
200v	1A	35p
200v	2A	45p
400v	2A	50p
400v	4A	55p
600v	2A	55p
500v	10A	PM7A6 £2.35

P&P 15p VAT 12 1/2%

METERS

AVOB	£61.09
AVO72	£24.07
AVOMM5	£20.94

P&P £1.10 VAT 8%
Alps Panel Meters
Sanwa Multi-Meters
Full range now in stock

STEREO F.M. TUNER

4 Pre-selected stations
Switched AFC
Supply 20-35v 90Ma Max
£19.95. P&P 25p VAT 12 1/2%

MAGNETIC TO CERAMIC CARTRIDGE CONVERTER

Operating Voltage 20/45v
ONLY £2.65 P&P 18p
Vat 12 1/2%

BSR MINI-DECK

4-speed autochanger £6.00.
Garrard SP25 Mk. IV (Chassis) £17.20
P&P 72p VAT 12 1/2%

CASED AUTO. TRANSFORMERS

240v mains lead input and USA 2 pin outlets
20VA £3.29, P&P 72p Ref: 113W
150VA £6.37, P&P 85p Ref: 44W
500VA £10.97, P&P £1.25p Ref: 81W
1000VA £18.39 BRS Ref: 84W
2000VA £28.71 BRS Ref: 95W

HIGH QUALITY MODULES

3 watt RMS Amplifier £2.30
5 watt RMS Amplifier £2.65
10 watt RMS Amplifier £2.95
25 watt RMS Amplifier £3.95
Pre-Amp for 3-5-10w (new) £6.50
Pre-Amp for 25w £13.87
Power Supplies for 3-5-10w £1.20
Power Supplies for 25w £3.00
Transformer for 3w £1.90
Transformer for 5-10w £2.30
Transformer for 25w £2.60
P&P Amps/Pre-Amps/Power Supplies 18p
P&P Transformers 37p
VAT 12 1/2%

NEW STEREO 30

Complete chassis, inc 7+7w rms amps, pre-amp, power supply, front panel, knobs (needs mains trans) £15.75. Mains trans £2.45. Teak veneered cab. £3.65. P&P 88p. VAT 12 1/2%

POWER UNITS

CC12-05. Output switched
3 4 5v 6v 7.5v 9v 12v at 500mA
£4.08. P&P 40p VAT 12 1/2%

ANTEX SOLDERING IRONS

15W £2.90. 8W £2.75. 25W £2.45
Soldering iron kit £3.90
Stand for above £1.13. P&P 25p VAT 8%

PLEASE ADD VAT AFTER P&P
ELECTROSIL AND SEMICONDUCTOR
STOCK STS AUDIO ACCESSORIES & BARGAIN
PAKS CALLERS WELCOME (MON-FRI) OR
SEND STAMP FOR LISTS

Barrie Electronics Ltd.
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/8
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.

CHROMASONIC electronics

Dept. 5.

56, FORTIS GREEN ROAD, LONDON, N10 3HN, ENGLAND.

Telephone 01-883 3705

Electronic Component suppliers to H.M. Government, Armed Services, Universities, Colleges, Broadcasting Authorities, Fire and Government Institutions, Industries and Educational Establishments.

74 TTL

	1-24	25-99	100
7400	14p	12p	10p
7401	14p	12p	10p
7402	14p	13p	10p
7403	15p	12p	10p
7404	16p	13p	11p
7408	16p	13p	11p
7409	16p	13p	11p
7410	16p	13p	11p
7413	29p	24p	20p
7417	27p	22p	20p
7420	16p	13p	11p
7427	27p	22p	18p
7430	16p	13p	11p
7432	27p	22p	18p
7437	27p	22p	18p
7441	75p	62p	50p
7442	65p	55p	43p
7445	85p	71p	57p
7447	81p	75p	65p
7448	75p	62p	50p
7447A	95p	83p	67p
7470	30p	25p	20p
7472	25p	21p	17p
7473	30p	25p	20p
7474	32p	26p	21p
7475	47p	39p	31p
7476	37p	26p	21p
7482	75p	62p	50p
7485	£1.30	£1.09	87p
7486	32p	26p	21p
7489	£2.92	£2.80	£2.10
7490	49p	40p	32p
7491	65p	55p	43p
7492	57p	46p	36p
7493	45p	40p	32p
7495	67p	55p	43p
74100	£1.08	89p	72p
74107	35p	28p	22p
74121	34p	28p	22p
74122	47p	39p	31p
74141	78p	63p	53p
74145	68p	58p	48p
74154	£1.62	£1.48	86p
74174	£1.00	83p	67p
74180	£1.06	88p	71p
74181	£3.20	£2.50	£1.90
74192	£1.35	£1.14	90p
74193	£1.35	£1.14	90p
74196	£1.64	£1.34	99p

LIGHT EMITTING DIODES

New Prices	0.125" dia. lens (TTL 209)			0.16" dia. lens			0.2" dia. lens (MLED 650)		
	10	100	1000	10	100	1000	10	100	1000
Red	10p	15p	13p	20p	18p	16p	17p	16p	15p
Green	26p	24p	22p	26p	24p	22p	26p	24p	22p
Amber	26p	24p	22p	26p	24p	22p	26p	24p	22p
Yellow	26p	24p	22p	26p	24p	22p	26p	24p	22p

I.C. SOCKETS

Pin Sockets, pins in strips of 100. Just strip off what you need. 65p per strip.

Dual in line

8 pin 13p	24 pin 26p	105
14 pin 15p	28 pin 30p	8 pin 31p
16 pin 15p	36 pin 39p	10 pin 35p

The AY-5-1224 tick-tock

Another marvel from G.I. A 16 pin 12-24 hr. Clock I.C. with 25 pin capability and low external parts count. Supplied with manufacturers detailed leaflet £3.95p (inc. VAT) (Leaflet alone 20p.) Full Kit (excluding case) available towards end of 1975. Phone Clive for details.

MULLARD MODULES

Still make the simplest, highly reliable F.M. tuner

LP186 Varactor front end £7.74
 LP185 I.F. Strip £6.26
 LP1400 Multiplex decoder £8.12

LINE-O-LIGHT

NEW LED Linear Cursors each device contains 10 light emitting diodes in a 20 pin dual in-line package. Ideal for solid state analogue meters or dials. Red and Green £3.19 each on Yellow, same in stock now.

DISPLAYS

Can./H Dec. pin
 Can./L/H Dec. pin
 Can./R/H Dec. pin
 C.C. R/H Dec. pin

PHOTO-DARLINGTON

V_{cc} 25v 2N5777
 V_{cb} 25v
 V_{eb} 8v
 I₁ 250 mA
 P_d 200 mW
 H_f 2500

0.33

Litronix DL 707 Series
 Monsanto MAN 50/70/80/3600
 Xciton XAN 70 Series
 Monsanto MAN 4000 Series
 Litronix DL747 'Jumbo' Series

all £1.82

each (Red only)
 Red £1.73 others £3.06 except C A R HL3 38
 all £1.64 Each
 Red £2.38 others £3.38
 all £2.66 Each (Red only) C/C as C A
 0.6" Xciton Red £1.97 Green and Yellow £2.66

NOTE: MAN 4000 Series pin outs are 14 pin dit. the same as MAN 50, 70 and 80 series

Our Bulk Buying Power enables a repeat of our Special Offer.
0.33" (LIT 707) £1.39
 Performance guaranteed

Short Form Catalogue

for your free copy send a S.A.E.

OPTO-ISOLATORS

ILI 4N25 or TIL116
 6 pin industry standard package
 2.5KV isolation £1.21

C. Mos	Linear	Zener	Regulators	Resistors	Switches
Audio I.C.'s	Memories	Rectifiers	Triacs	Pots	Boxes
TV I.C.'s	Diodes	Heat Sinks	SCR's, SCS's	Vero	Tuning Cons.
Radio I.C.'s	Transistors	Capacitors	Bridges	Coils	Connectors

MAINS TRANSFORMERS

Secondaries	Transformers	1A	2A	4A
6.0-6	100 mA	99p		
9.0-9	100 mA	99p		
12.0-12	100 mA	99p		
20.0-20	1 A	£3.45		
24.0-24	0.5 A	£2.95		
28.0-28	1 A	£3.95		

Transformers	1A	2A	4A
0-9-17 V		£2.49	£3.57
0-12-15-20-24-30V		£3.47	£4.65
0-24-30-40-48-60V		£5.18	£7.02
0-19-25-33-40-50V	£3.47	£4.65	£7.24

P&P on transformers 20% of price min. 25p

VAT INC

Items followed by * inc. VAT at 8% all others include 12 1/2%
 Overseas customers deduct 4/27 from * items - 1/9 from others
 Postage and Packing 20p. Orders for over £6. post free. Except transformers

3 1/2 DECADE DVM I.C.

This state-of-the-art MOS LSI chip contains all the logic necessary for a 3 1/2 decade, dual slope integrating, automatic polarity detecting DVM. Supplied with free data and circuit booklet.

OUR PRICE ONLY £6.59*

Data Sheet and photocopy service available at 10p per page. CALLERS ARE WELCOME

APRIL 1976

Samson's

(ELECTRONICS) LTD.

9 & 10 CHAPEL ST., LONDON, N.W.1
 01-723 7851 01-262 5125

ADJACENT TO EDGWARE ROAD MET. LINE STATION
 PLEASE ADD 8% TO ALL ORDERS INC. CARR.

CURRENT RANGE OF NEW L.T. TRANSFORMERS OPEN TYPE TAG CONNECTIONS ALL PRIMARIES 220-240V

Type	Sec. Taps	Amps	Price	Carr
1	24.30-40-48-60V	12	£20.25	£2.00
2	21.30-40-48-60V	10	£19.40	£2.00
3	24.30-40-48-60V	8	£15.75	£1.50
4	24.30-40-48-60V	5	£10.24	£1.00
5	24.30-40-48-60V	3	£7.90	75p
6	24.30-40-48-60V	2	£5.63	75p

6.8-10-12-16-18-20-24-36-40-48-60V CAN BE OBTAINED FROM THE ABOVE RANGE

7	19.25-33-40-50V	10	£17.75	£2.00
8	19.25-33-40-50V	6	£12.00	£1.25
9	19.25-33-40-50V	3	£6.00	75p
10	19.25-33-40-50V	2	£4.95	75p

5-7-8-10-13-15-17-20-25-30-40-50V OR 25.0-25V or 20.0-20V CAN BE OBTAINED FROM THE ABOVE RANGE

11	12.15-20-25-30V	10	£10.35	£1.25
12	12.15-20-25-30V	5	£6.70	£1.00
13	12.15-20-25-30V	2	£3.75	75p

3-4-5-6-8-9-10-12-15-18-20-24-30V or 12.0-12V or 15.0-15V CAN BE OBTAINED FROM THE ABOVE RANGE

14	12-24V	12V 60A 24V 30A	£17.50	£2.00
15	12-24V	12V 30A 24V 15A	£14.25	£1.50
16	12-24V	12V 20A 24V 10A	£10.75	£1.25
17	12-24V	12V 10A 24V 5A	£5.50	75p
18	12-24V	12V 4A 24V 2A	£2.95	60p

FULLY SHROUDED TYPE TERMINAL CONNECTIONS

19	4-16-24-32V	4	£6.95	75p
20	4-16-24-32V	2	£4.65	65p
21	12-20-24V	10	£9.50	£1.00
22	12-20-24V	5	£6.50	75p
23	24-30-36V	10	£12.00	£1.25
24	24-30-36V	5	£9.50	£1.00
25	24-30-36V	2	£4.50	65p

CENTRE TAPPED L.T. TRANSFORMERS

Fully shrouded terminal block connections Pri 220-240V Scr sec tapped 30 25 0 25 30V 2 amps £5.95, p.p. 75p 36 25 0 25 36 5 amps £11.95, p.p. 11 Open frame type tag connections Pri 240V Scr 18.0-18V 12 5A Core tablet type connections £10.00, carr £2

WODEN AUTO TRANSFORMERS

3000 watts tapped 105-115-125-135-200 215-230-245 260V open type terminal block connections £19.50, carr £2.00 in metal case with twin American 2/3 pin flush mounted sockets 3 core 240V mains lead. Carrying handle £32.50, carr £3

AUTO TRANSFORMERS FOR AMERICAN EQUIPMENT

240/110V 80-3000 watts. fitted with 2 3 pin sockets, and 3 core mains lead. Send sale for price list. We have England's largest selection of American electrical accessories 2-3 pin plugs, recessed and surface type 2-3 sockets, multi-way adaptors 2-3 pin grounding adaptors Cable type sockets. Extension cords 240V Edison screw type light bulbs. Industrial plugs and sockets. Let us know your requirements.

HT TRANSFORMERS BY FAMOUS MAKER. ALL PRIMARIES 240V OPEN TYPE TAG CONNECTIONS

Sec 350-0-350V 120 mA 6.3V CT 1A 5V 2A £3.75, p.p. 85p 300-0-300V 150 mA 6.3CT 4A 5V 6.3V 2A £3.75, p.p. 85p 300-0-300V 100 mA 6.3V 3.5A 5V 2A £3.00, p.p. 85p 250-0-250V 120 mA 6.3V 3 1/2A 5V 2A £3.00, p.p. 85p C core type 250-0-250V 50 mA 6.3V 1A 6.3V 0.7A 6.3V 0.8A £2.00, p.p. 75p Shrouded types 500-0-500 200 mA £4.50, carr £1.25 20V mA 6.3V 1A £1.1, p.p. 40p

GRESHAM L.T. TRANSFORMERS

All primaries tapped 10-0-200-220-240V open type tropicalised terminal block connections fraction of maker's price. No 2 4.7-11-31-32-33-34-35V 10A £8.50, No 3 4.7-11-32-33-34-35V 10A £6.50, No 4 6.1-3-20-54-56-58-59 5A £6.50, Carr on all type 11 C core types all primaries 200-220-240V, No 1 4 separate secs 1V 3V 9V 27V All at 15A £12.00, No 2, 3 separate secs 29.30-33V 15A 23-24-26V 5A 14-15-17 5A £12.00, carr £2

POIRED H.T. TRANSFORMERS BY FAMOUS MAKERS

No 1 Pri 110-220-240V Scr Sec tapped 408-200-0-200-408V High taps 165M/A Low taps 500M/A £5.50, carr £1 No 2 Pri 115-220-240V Scr Sec 400-0-400V 400M/A £5.75, carr £1 No 3 Pri 115-220-240V Scr Sec 350-0-350V 200M/A 6.3V 6A, 5V 3A £4.50, carr £1 No 4 Pri 115-220-240V Scr Sec 330-0-330V 200M/A 6.3V 6A 5V 3A £4.00, carr £1 No 5 Pri 220-240V Scr Sec 250-0-250V 320M/A 5V 3V 10A £4.50, carr £1 No 6 Pri 110-220-240V Scr Sec 187.5V 60M/A and 500V 31M/A £5.00, carr £1 No 7 Pri 110-220-240V Scr Sec 230V 200M/A 6.3V 7A £3.00, carr 75p No 8 Pri 220-240V Scr Sec 250-0-250V 75M/A 6.3V 2A 6.3V 1A £3.00, carr 75p No 9 Pri 220-240V Scr Sec 100-0-100V 170V 180-190 200 210-220-230-240V 175M/A 6.3V 3A 6.3V 2A £3.75, carr 75p No 10 Pri 220-240V Scr Sec 250-0-250V 100M/A 6.3V 3A 5V 2A £3.00, carr 75p

L.T. TRANSFORMERS BY FAMOUS MAKERS. ALL PRIMARIES 240V

Sec 91-2V 20 amps open type tablet type connections £8.50, carr £2 20V 20 amps £10, carr £2 12V 30 amps twice £17.50, carr £3

3 PHASE ISOLATION TRANSFORMERS BY FAMOUS MAKER

Input tapped 380 400 415-430 volts RMS NOM Line to line 3 phase 4 wire 50Hz output 415 volts 3 phase 4 wire at 2.15kVA Regulation 2% secondary fully screened open type construction Terminal block connections size 16x1/2x7/8ins Weight 90lbs Brand new. Fraction of maker's price £27.50 plus VAT carriage charges at cost.

RELAYS

Keyswitch Kmk3 230V AC 3 CO 75p. Kmk3 12V AC 3 CO 75p. Kmk1 230V AC 1 CO 60p. Omron Mk 2P 12V DC 2 CO plug in type 75p. bases 10p. Mk 2 24V AC 12V DC 2 CO 60p. pp all types 15p Siemens miniature types 230V 4 CO 75p. 185V 4 CO 75p. 2500V 4 CO 60p. pp all types 15p American miniature type 6V DC 1 CO 35p. pp 15p Siemens open type AC 230V 1 make 40p. pp 15p Cutler and Hammer 230V AC contactors One NO or NC 16 amp 600V AC contacts in metal cast £1.50, pp 35p

OIL FILLED BLOCK CAPACITORS BY FAMOUS MAKERS

4-4 1/4 + 2 1/2 mfd 600V DC Wkg £1.50, pp 50p 8mfd 2500V DC Wkg £3.75, pp £1.25 8mfd 400V DC Wkg 65p, pp 25p 8mfd 350V DC Wkg 60p, pp 25p 8mfd 300V DC Wkg 50p, pp 25p 6mfd 1000V DC Wkg 75p, pp 25p 6mfd 600V DC Wkg 65p, pp 25p 4mfd 1250V DC Wkg £1.00, pp 25p 4mfd 1000V DC Wkg 75p, pp 25p 4mfd 350V DC Wkg 40p, pp 25p 2mfd 2000V DC Wkg 65p, pp 25p 2mfd 500V DC Wkg 30p, pp 15p 1mfd 2000V DC Wkg 50p, pp 25p 1mfd 600V DC Wkg 25p, pp 15p 0.25mfd 7500V DC Wkg £1.00, pp 25p 0.1mfd 3000V DC Wkg 30p, pp 15p 0.001mfd Mica 6000V DC Wkg 75p, pp 25p Electrolytics 100 000 mfd (-10+50%) 35p, pp 15p TCC dry electrolytics block type 2000mfd -20% +50% 50V DC Wkg 75p, pp 25p

HIGH VOLTAGE INSULATION TRANSFORMER

Pri 200-220-240V SEC tapped 4-5-6-3V 12 amps and 2 5V 35 amps One only £20.00, carr £3

AC WKG BLOCK CAPACITORS BY FAMOUS MAKERS

Outlier 15mfd 330V AC Wkg £1.25, P.P 25p 10mfd 350V AC Wkg £1.00, P.P 25p 5mfd 300V AC Wkg 75p, P.P 25p 4mfd 650V AC Wkg £1.00, P.P 25p 4mfd 500V AC Wkg 75p, P.P 25p T.C.C 4mfd 250V AC Wkg 50p, P.P 20p 2 5mfd 300 AC Wkg 50p, P.P 20p 1 5mfd 400V AC Wkg 75p, P.P 20p 0.4mfd 440V AC Wkg 50p, P.P 20p Bosch 1mfd 800V AC £1.00, P.P 20p


H.T. SMOOTHING CHOKES BY FAMOUS MAKERS

Parmeko pots types 10H 180 M/A £2.00, P.P 50p 10H 75 M/A £1.00, P.P 35p 50H 25 M/A £1.00, P.P 35p 15H 75 M/A £1.00, P.P 35p Swinging type 10 0.04A 4H 0.25A £1.25, P.P 50p Gardners 100H 20 M/A £1.75, P.P 35p 20H 80 M/A £1.00, P.P 35p C core type 10H 350 M/A £3.50, P.P £1.00

L.T. TRANSFORMERS BY FAMOUS MAKERS

Open types No 1 Pri 240V Sec 26V 10A and 12V 0 1A £5.50, No 2 Pri 220-240V Sec Tapped 51-61 65-67-69 10A £10.00, carr £1.50 No 3 Pri 220-240V Sec Tapped 58-63 69-74 3A £4.75, carr £1 No 4 Pri 115-230V Sec 6.3V 5.7A twice and 26V 600 M/A C core £3.75, P.P 75p No 5 Pri 115-230V Sec 33V 6A and 18.0-18V 1A £3.00, P.P 75p No 6 Pri 110 200 220-240V Sec 14V 5A 14V 2.5A 12V 10A 8V 10A 24V 750 M/A 200V 500 M/A Separate windings £10.00, carr £1.50 No 7 Pri 200-220-240V Sec 4V 6A 4V 3A £3.50, P.P 75p No 8 Pri 110 220 235V Sec 12V 2 2A and 12V 1A and 200V 35 M/A £2.50, P.P 75p No 9 Pri 200-220-240V Sec 37V 5.5A and 37V 2A and 21V 11A £8.50, carr £1.50 No 10 Pri 200-220-240V Sec 31V 7A 26V 5A 16V 4A 25V 2A Separate windings £8.50, carr £2.00 No 11 C core type No 12 Pri 220-240V Sec 18.0-18V 21A £10.00, No 12 Pri 230V Sec 1.25-0.11 25V 10A £2.00, P.P 50p No 13 Potted types Pri 110-220-240V Sec 70V 1A and 30V 1A £3.50, carr £1 No 14 Pri 115-220-240V Sec 43V 0.75A and 43V 0.5A and 6.3V 1A £3.50, P.P £1 No 15 Pri 110-220-240V Sec 29.7V 5A 23V 1/2A 78V 60 M/A 181V 100 M/A Separate windings £6.00, carr £1.50 No 16 Pri 200-240V Sec 12V 6A and 15

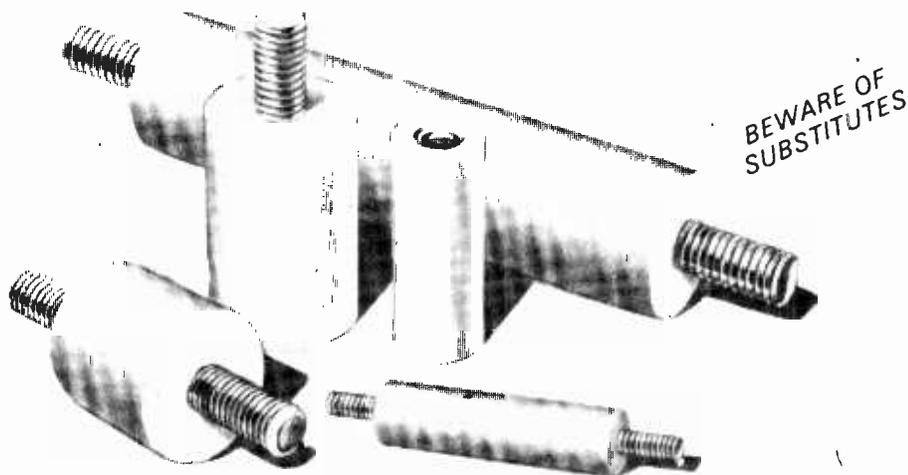INSULATE THAT CHASSIS, OR COMPONENT,
THE EASY WAY BY MOUNTING WITH
TRANSIPILLARS
FOR
STRENGTH



INJECTION MOULDED NYLON PILLARS WITH
INSERTS MOULDED IN FOR SUPER STRENGTH

TRANSIPILLARS

ARE
STRONGER THAN ANY SIMILAR DEVICES
HAVING MECHANICALLY ASSEMBLED INSERTS

SIZES FROM 6BA 1/2" LONG TO OBA 2 3/4" LONG

METRIC EQUIVALENTS ALSO AVAILABLE

MIXED TERMINATIONS

(E.G. 2BA ONE END, 4BA AT OTHER END)
AND LENGTHS MADE TO USERS' REQUIREMENTS

DETAILS, PRICES AND SAMPLES FROM



WK ELECTRONICS

Scientific Instruments & Electronic Components

40a NAPIER ROAD, BROMLEY KENT BR2 9JA

Telephone: 01-460 9861 Telex 896071

LYNX ELECTRONICS (LONDON) LTD.

AC126 0.15	BC301 0.32	BY206 0.15	1N4003 0.06
AC127 0.16	BC323 0.60	BY207 0.20	1N4004 0.07
AC128 0.13	BC327 0.18	BYX36-300 0.12	1N4005 0.08
AC128K 0.25	BC328 0.18	BYX36-600 0.15	1N4006 0.09
AC141 0.18	BC337 0.17	BYX36-900 0.18	1N4007 0.10
AC141K 0.28	BC338 0.17	BYX36-12000.21	2N696 0.14
AC142 0.18	BCY70 0.12	BYX38-300 0.50	2N697 0.12
AC142K 0.28	BCY71 0.18	BYX38-600 0.55	2N706 0.10
AC176 0.16	BCY72 0.12	BYX38-900 0.60	2N929 0.14
AC176K 0.25	BD115 0.55	BYX38-12000.65	2N930 0.14
AC187 0.18	BD131 0.36	BZX61 Series	2N1131 0.15
AC187K 0.25	BD132 0.40	Zeners 0.20	2N1132 0.16
AC188 0.18	BD135 0.36	BZX83 or BZX88	2N1304 0.20
AC188K 0.25	BD136 0.39	Series	2N1305 0.20
AD140 0.50	BD137 0.40	Zeners 0.11	2N1711 0.18
AD142 0.50	BD138 0.48	C106A 0.40	2N2102 0.44
AD143 0.46	BD139 0.58	C106B 0.45	2N2369 0.14
AD149 0.45	BD181 0.86	C106D 0.50	2N2369A 0.14
AD161 0.35	BD182 0.92	C106F 0.35	2N2484 0.16
AD162 0.35	BD183 0.97	CR51/05 0.25	2N2646 0.50
AL102 0.95	BD232 0.60	CR51/10 0.25	2N2905 0.18
AL103 0.93	BD233 0.48	CR51/20 0.35	2N2905A 0.22
AF114 0.20	BD237 0.55	CR51/40 0.40	2N2926R 0.10
AF115 0.20	BD238 0.60	CR51/60 0.65	2N2926G 0.09
AF116 0.20	BD184 1.20	CR53/05 0.34	2N2926T 0.09
AF117 0.20	BDY20 0.80	CR53/10 0.45	2N2926G 0.10
AF118 0.50	BDY38 0.60	CR53/20 0.50	2N3053 0.15
AF139 0.33	BDY60 0.60	CR53/40 0.60	2N3054 0.40
AF239 0.37	BDY61 0.65	CR53/60 0.85	2N3055 0.50
BC107 0.14	BDY62 0.65	MJ480 0.80	2N3440 0.56
BC107B 0.16	BF178 0.28	MJ481 1.05	2N3442 1.20
BC108 0.13	BF179 0.30	MJ490 0.90	2N3525 0.75
BC109 0.14	BF194 0.10	MJ491 1.15	2N3570 0.80
BC109C 0.16	BF195 0.10	MJE340 0.10	2N3702 0.10
BC117 0.19	BF196 0.12	MJE371 0.60	2N3703 0.10
BC125 0.18	BF197 0.12	MJE520 0.45	2N3704 0.10
BC126 0.20	BF224J 0.18	MJE521 0.55	2N3705 0.10
BC141 0.28	BF244 0.17	OA5 0.50	2N3706 0.10
BC142 0.23	BF257 0.30	OA90 0.08	2N3707 0.10
BC143 0.23	BF258 0.35	OA91 0.08	2N3714 1.05
BC144 0.30	BF337 0.32	OC41 0.15	2N3715 1.15
BC147 0.09	BFV60 0.17	OC42 0.15	2N3716 1.25
BC148 0.09	BFX29 0.26	OC44 0.12	2N3771 1.60
BC149 0.09	BFX30 0.30	OC45 0.10	2N3772 1.60
BC152 0.25	BFX84 0.23	OC70 0.10	2N3773 2.10
BC153 0.18	BFX85 0.25	OC71 0.10	2N3819 0.28
BC157 0.09	BFX88 0.20	OC72 0.22	2N3904 0.16
BC158 0.09	BFY50 0.20	OC84 0.14	2N3906 0.16
BC159 0.09	BFY51 0.18	SC40A 0.73	2N4124 0.14
BC160 0.32	BFY52 0.19	SC40B 0.81	2N4290 0.12
BC161 0.38	BFY64 0.35	SC40D 0.98	2N4348 1.20
BC168B 0.09	BFY90 0.65	SC40F 0.65	2N4870 0.35
BC182 0.11	BR100 0.20	SC41A 0.65	2N4871 0.35
BC182L 0.11	BRV39 0.40	SC41B 0.70	2N4919 0.70
BC183 0.10	BSX19 0.16	SC41D 0.85	2N4920 0.50
BC183L 0.10	BSX20 0.18	SC41F 0.60	2N4922 0.58
BC184 0.11	BSX21 0.20	ST2 0.23	2N4923 0.64
BC184L 0.11	BSY95A 0.12	TIP29A 0.44	2N5060 0.20
BC207B 0.12	BT106 1.00	TIP30A 0.52	2N5061 0.25
BC212 0.11	BT107 1.60	TIP31A 0.54	2N5062 0.27
BC212L 0.11	BT108 1.60	TIP32A 0.84	2N5064 0.30
BC213 0.12	BT109 1.00	TIP34 1.05	2N5496 0.65
BC214 0.14	BU105 1.80	TIP41A 1.68	
BC214L 0.14	BU105 1.80	TIP42A 0.72	
BC237 0.16	BU126 1.90	IN2069 0.14	
BC238 0.16	BU126 1.90	IN2070 0.16	
BC300 0.34		IN4001 0.04	
		IN4002 0.05	

DIGITAL DISPLAYS & LED'S

DL704 99p	DL747 £1.75	2 RED LED ONLY	13p
DL707 99p	DL750 £1.75	GREEN CLEAR	15p

THYRISTORS

	8A (TO92)	1A (TO5)	3A (C106 type)	6A (TO220)	8A (TO220)	10A
50	20	25	35	41	42	47
100	25	25	40	47	48	54
200	27	35	45	58	60	68
400	30	40	50	67	68	98
600	30	65	70	1.09	1.19	1.26

TRIACS (PLASTIC TO-220 PKGE. ISOLATED TAB)

	4A		6.5A		8.5A		10A		15A	
	(a)	(b)								
100V	0.60	0.60	0.70	0.70	0.78	0.78	0.83	0.83	1.01	1.01
200V	0.64	0.64	0.75	0.75	0.87	0.87	0.87	0.87	1.17	1.17
400V	0.77	0.78	0.80	0.83	0.97	1.01	1.13	1.19	1.70	1.74
600V	0.96	0.99	0.87	1.01	1.21	1.26	1.42	1.50	2.11	2.17

N.B. Triacs without internal trigger diac are priced under column (a). Triacs with internal trigger diac are priced under column (b). When ordering please indicate clearly the type required.

74 TTL mixed prices

7400	1.24	25.99	100+	7445	85p	71p	57p	7493	45p	40p	32p
7401	14p	12p	10p	7447	81p	75p	65p	7495	67p	55p	45p
7402	14p	12p	10p	7448	75p	62p	50p	7400	£1.08	89p	72p
7403	15p	12 1/2p	10p	7447A	95p	83p	67p	74107	35p	28p	22p
7404	16p	13p	11p	7470	30p	25p	20p	74121	34p	28p	23p
7408	16p	13p	11p	7472	25p	21p	17p	74122	47p	39p	31p
7409	16p	13p	11p	7473	30p	25p	20p	74141	78p	63p	53p
7410	16p	13p	11p	7474	32p	26p	21p	74145	68p	58p	48p
7413	29p	24p	20p	7474	42p	36p	31p	74154	£1.62	£1.48	86p
7417	27p	22 1/2p	20p	7476	32p	26p	21p	74174	£1.00	83p	67p
7420	16p	13p	11p	7482	75p	62p	50p	74180	£1.06	88p	71p
7427	27p	22 1/2p	18p		£1.30	£1.09	87p	74181	£3.20	£2.50	£1.90
7430	16p	13p	11p	7486	32p	26p	21p	74192	£1.35	£1.14	90p
7432	27p	22 1/2p	18p	7489	£2.92	£2.80	£2.10	74193	£1.35	£1.14	90p
7437	27p	22 1/2p	18p	7490	49p	40p	32p	74196	£1.64	£1.34	99p
7441	75p	62p	50p	7491	65p	55p	45p				
7442	65p	55p	43p	7497	57p	48p	36p				

LINEAR IC'S

301A 8 pin DIL	35p	3900 14 pin DIL	70p	565 14 pin DIL	£2.00
307	35p	709 8 14 pin DIL	35p	566 8 pin DIL	£1.50
309K	£1.60	741 8 pin DIL	28p	567 8 pin DIL	£2.00
380 14 pin DIL	90p	741 14 pin DIL		CA3046 14 pin DIL	50p
381 14 pin DIL	£1.60	748 8 pin DIL	36p	CA3045	85p
		555 8 pin DIL	45p		

HIGHAM MEED, CHESHAM, BUCKS. TEL. (02405) 75154

VAT - Please add 8% except items marked * which are 12 1/2 %

P & P 20p. Overseas 80p

BOOKS

Diodes Transistors, etc., over 3500 Pages	£10.50
CMOS over 400 Pages	£1.50
Linear I.C. over 800 Pages	£2.00
Motrola M6800 Programming Manual	£3.50
Motrola M6800 Applications Manual	£7.00
From Minicomputers to Microprocessors	£1.00

SIGNETICS

Data/Applications book, over 1600 Pages	£4.00
DMOS; 74LS; Consumer, shift registers, RAM's, PROM's	20p each

FERRANTI

E-Line Applications	50p
Complete range of data and applications notes available	

NO VAT THIS SECTION

LINEAR IC's

LM301AV Ext. comp. operational amplifier	36p
LM307V Int. comp. operational amplifier	45p
MC1458V Dual comp. operational amplifier	80p
NE510A Video amplifier	£1.58
NE540L Audio power driver	£7.00
NE555V Timer	44p
NE556A Dual 555 14 pin	99p
NE515B Phase locked loop with A.M. demode	£2.70
NE562B Phase locked loop with V.C.O.	£2.70
NE566V Phase locked loop function gen	£1.50
PA239A Dual low noise stereo pre-amp	95p
AA741CV Op. amp	42p
AA747CA Dual op. amp	90p
MC1303L Dual Stereo pre-amp	£1.47
MC1306P 1/2W audio amp	64p
MC1304P F.M. multiplex stereo demodulator	£1.12
MC1301P Stereo demodulator	£1.92
MC1312P	£1.94
MC1314P Quadrophonic decoder kit	£3.31
MC1315P	£3.59
MC1330P Low level video detector	61p
MC1496G Double Balanced mixer	

MOS I.C.s

AY-5-1224 12/24 24 hour digital clock circuit	14.25
AY-5-3510 3 1/2 digit DVM circuit	16.10
AY-1-0212 Master tone generator	15.55
AY-1-5015 4 stage divider	11.20
AY-1-6731 5 1/2 stage divider	11.30
AY-1-6731 6 1/2 stage divider	11.45
AY-1-0000 7 stage divider	11.75
C500 8 digit calculator chip	16.50
C500 8 digit calculator chip	13.25
Z1028 MOS 1024 bit static RAM	13.00

FERRANTI I.C.s

ZN1040C Universal counter/display CCT	£12.00
ZN1034C Precision timer CCT	9.99
ZN41A A.M. radio circuit	£1.00
Data and Circuits on ZN414	5p

SPECIAL OFFERS

IN4148 Diodes	12 for 50p
	30 for £1.00
0127" Display (MAN3M)	1000 for £25.00
	35p
5% Discount orders over £5.00	
10% Discount orders over £10.00	
Discount not applicable to kit or special offers	

I.C. SOCKETS

14 pin	12p	28 pin	27p
16 pin	15p	40 pin	30p
24 pin	25p		

CAPACITORS

Electrolytic; paper; Non polar Tant	
Pack of 25 Mixed	our choice 50p

Metal Tant 5v	1; 3.3; 4.7; 56; 68; 180
10v	150;
15v	4.7
20v	0.1 1 39; 68
35v	0.47; 0.56; 0.68; 0.82; 1.2
1.8; 2.7; 3.3; 4.7; 10; 15; 33	
50v	3.3; 3.9; 10; 15; 22; 27; 50
Plastic Tant 6v	4.7

Tubular 20v	15
35v	2.2; 3.3; 4.7; 6.8

RESISTORS

All values microfarads			
Your choice 10p each			

BI-PAK SEMICONDUCTORS

TRANSISTORS

BRAND NEW, FULLY GUARANTEED			
TYPE	PRICE	TYPE	PRICE
AC117K	+0.30	BC170	0.09
AC122	+0.12	BC171	0.09
AC125	+0.18	BC172	0.09
AC126	+0.14	BC173	0.09
AC127	+0.11	BC174	0.15
AC128	+0.11	BC175	+0.22
AC132	+0.15	BC177	+0.16
AC134	+0.15	BC178	+0.16
AC137	+0.15	BC179	+0.16
AC141	+0.19	BC180	+0.25
AC141K	+0.80	BC181	0.25
AC142	+0.19	BC182	0.09
AC142K	+0.26	BC183	0.09
AC151	+0.16	BC183L	0.09
AC153K	+0.24	BC184	0.09
AC154	+0.20	BC184	0.09
AC155	+0.20	BC184L	0.09
AC156	+0.20	BC185	+0.29
AC157	+0.23	BC187	0.11
AC165	+0.20	BC207	0.11
AC166	+0.20	BC208	0.11
AC167	+0.20	BC209	0.12
AC168	+0.23	BC212	0.10
AC169	+0.13	BC212L	0.10
AC176	+0.11	BC213	0.10
AC176K	+0.26	BC213L	0.10
AC177	+0.25	BC214	0.10
AC178	+0.29	BC214L	0.10
AC179	+0.29	BC225	0.26
AC180	+0.20	BC226	0.36
AC180K	+0.30	BC251	0.10
AC181	+0.20	BC301	0.28
AC181K	+0.30	BC302	+0.25
AC187	+0.22	BC303	+0.31
AC187K	+0.23	BC304	+0.37
AC188	+0.19	BC327	0.12
AC188K	+0.23	BC328	0.12
AC17	+0.26	BC337	0.12
AC18	+0.20	BC338	0.12
AC19	+0.20	BC440	+0.31
AC20	+0.20	BC460	+0.37
AC21	+0.20	BC460	+0.37
AC22	+0.17	BCY31	+0.27
AC23	+0.19	BCY32	+0.31
AC278	+0.19	BCY33	+0.31
AC29	+0.36	BCY34	+0.26
AC290	+0.29	BCY70	+0.15
AC291	+0.29	BCY71	+0.20
AC292	+0.29	BCY72	+0.15
AC293	+0.29	BCY73	+0.21
AC294	+0.29	BCY74	+0.26
AC295	+0.29	BCY75	+0.26
AC296	+0.29	BCY76	+0.26
AC297	+0.29	BCY77	+0.26
AC298	+0.29	BCY78	+0.26
AC299	+0.29	BCY79	+0.26
AD130	+0.39	BD121	+0.61
AD140	+0.49	BD122	+0.67
AD142	+0.53	BD123	+0.71
AD143	+0.49	BD131	+0.38
AD149	+0.43	BD132	+0.40
AD161	+0.36	BD133	+0.67
AD162	+0.38	BD135	0.41
AD162(MP)	+0.69	BD136	0.41
AD174	+0.22	BD140	0.61
AF115	+0.22	BD155	+0.81
AF116	+0.22	BD177	+0.61
AF117	+0.22	BD178	+0.61
AF118	+0.32	BD177	+0.67
AF124	+0.28	BD178	+0.67
AF125	+0.28	BD179	+0.71
AF126	+0.28	BD180	+0.71
AF127	+0.28	BD185	+0.67
AF130	+0.31	BD187	+0.71
AF178	+0.51	BD188	+0.71
AF180	+0.51	BD189	+0.77
AF181	+0.51	BD190	+0.77
AF186	+0.51	BD195	+0.87
AF239	+0.38	BD196	+0.87
AL102	+0.75	BD197	+0.92
AL103	+0.75	BD198	+0.92
AS226	+0.26	BD199	+0.98
AS227	+0.31	BD200	+0.98
AS228	+0.26	BD205	+0.81
AS229	+0.26	BD207	+0.98
AS230	+0.26	BD208	+0.98
AS231	+0.26	BD209	+0.98
AS439	+0.26	BD417	+0.98
AS440			

BI-PAK

High quality modules for stereo, mono and other audio equipment.

NEW



PUSH-BUTTON STEREO FM TUNER

OUR PRICE ONLY **£19.95** Fitted with Phase Lock-loop Decoder

The 450 Tuner provides instant program selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, by simply changing the settings of the pre-set controls. Used with your existing audio equipment or with the BI-KITS STEREO 30 or the MK60 Kit etc. Alternatively the PS12 can be used if no suitable supply is available, together with the Transformer T461. The S450 is supplied fully built, tested and aligned. The unit is easily installed using the simple instructions supplied.


- ★ FET Input Stage
- ★ VARI-CAP diode tuning
- ★ Switched AFC
- ★ Multi turn pre-sets
- ★ LED Stereo Indicator

Typical Specification:
Sensitivity 3µ volts
Stereo separation 30db
Supply required 20-30v at 90 Ma max.

MPA 30

Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the new M.P.A. 30, a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only. It is provided with a standard DIN input socket for ease of connection. Full instructions supplied.

£2.65

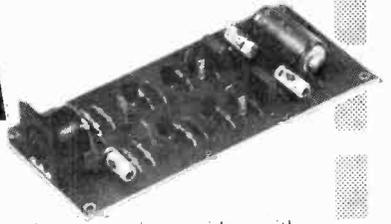

STEREO PRE-AMPLIFIER



PA 100
OUR PRICE **£13.50**


A top quality stereo pre-amplifier and tone control unit. The six push-button selector switch provides a choice of inputs together with two really effective filters for high and low frequencies, plus tape output.

- Frequency Response + 1dB 20Hz - 20KHz Sensitivity of inputs
- 1 Tape Input 100mV into 100K ohms
 - 2 Radio Tuner 100mV into 100K ohms
 - 3 Magnetic P U 3mV into 50K ohms
- P U Input equalises to R1AA curve with 1dB from 20Hz to 20KHz
Supply - 20-35V at 20mA

Dimensions
299mm x 89mm x 35mm

MK. 60 AUDIO KIT: Comprising 2 x AL60's 1 x SPM80 1 x BTM80. 1 x PA100 1 front panel and knobs. 1 Kit of parts to include on/off switch, neon indicator, stereo headphone sockets plus instruction booklet. **COMPLETE PRICE £27.55.**

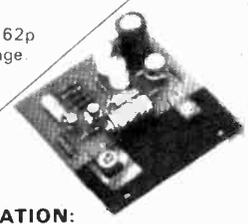TEAK 60 AUDIO KIT: plus 62p postage.
Comprising Teak veneered cabinet size 16 3/4" x 11 1/2" x 3 3/4" other parts include aluminium chassis, heatsink and front panel bracket plus back panel and appropriate sockets etc **KIT PRICE £9.20** plus 62p postage.



AUDIO AMPLIFIER MODULES

The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S. The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the home.

SPECIFICATION:

- Harmonic Distortion Po=3 watts f=1KHz 02.5%
- Load Impedance 8-16ohm
- Frequency response ± 3dB Po=2 watts 50Hz-25KHz
- Sensitivity for Rated O/P - Vs=25v. RL=8ohm f=1KHz 75mV. RMS

AL10 3w R.M.S. **£2.30** AL20 5w R.M.S. **£2.65** AL30 10w R.M.S. **£2.95**

VAT ADD 12 1/2%

POSTAGE & PACKING

Postage & Packing add 25p unless otherwise shown. Add extra for airmail. Min. £1.00

STEREO 30

COMPLETE AUDIO CHASSIS

7+7 WATTS R.M.S.



£15.75

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This, with only the addition of a transformer or overwind will produce a high quality audio unit suitable for use with a wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo tape deck etc. Simple to install, capable of producing really first class results, this unit is supplied with full instructions, black front panel knobs, main switch, fuse and fuse holder and universal mounting brackets enabling it to be installed in a record plinth, cabinets of your own construction or the cabinet available ideal for the beginner or the advanced constructor who requires Hi-Fi performance with a minimum of installation difficulty (can be installed in 30 mins)

TRANSFORMER £2.45 plus 62p p & p
TEAK CASE £3.65 plus 62p p & p



AL 60 25 Watts (RMS)

- ★ Max Heat Sink temp 90C.
- ★ Frequency response 20Hz to 100KHz
- ★ Distortion better than 0.1 at 1KHz
- ★ Supply voltage 15-50v
- ★ Thermal Feedback
- ★ Latest Design Improvements
- ★ Load - 3,4,8, or 16 ohms
- ★ Signal to noise ratio 80db
- ★ Overall size 63mm. 105mm. 13mm.

Especially designed to a strict specification. Only the finest components have been used and the latest solid-state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

£3.95

NEW

PA12

NEW PA12 Stereo Pre-Amplifier completely redesigned for use with AL10/20/30 Amplifier

Modules. Features include on/off volume, Balance, Bass and Treble controls. Complete with tape output.

Frequency Response 20Hz-20KHz (-3dB). Bass and Treble range 12dB. Input Impedance 1 meg ohm. Input Sensitivity 300mV. Supply requirements 24V. 5mA. Size 152mm x 84mm x 33mm.

£6.50

PS12

Power supply for AL10/20/30, PA12, SA450 etc

Input voltage 15-20v A.C. Output voltage 22-30v D.C.
Output current 800 mA Max. Size 60mm x 43mm x 26mm.

Transformer T529 £2.30

OUR PRICE **£1.20**

Stabilised Power Supply Type SPM80

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watts (R.M.S.) per channel simultaneously. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5A at 35V. Size 63mm. 105mm. 30mm. Incorporating short circuit protection.

Transformer BMT80 **£2.60 + 62p postage**

£3.00

BI-PAK

P.O. BOX 6, WARE, HERTS.

DRILL CONTROLLER
Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. **£2.95** including post & VAT. Made up model **£1.00** Extra.



NUMICATOR TUBES
For digital instruments, counters, timers, clocks, etc. Hi-vac XNII. Price **£1.25** each inc. Post and VAT.



RADIO STETHOSCOPE
Easiest way to fault find traces signal from aerial to speaker, when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything. Complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. **£2.95** twin stetho-set instead of earpiece inc. VAT & Postage.

MAINS TRANSISTOR PACK
Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9 and others. Kit comprises: main transformer, rectifier, smoothing and load resistor, condensers and instructions. Real snip at only **£1.75** including Post & VAT.


MOTORISED DISCO SWITCH
With six 10 amp changeover switches, adjustable over 360° switches are rated at 10 amp each so a total of 2000w's can be controlled and this would provide a magnificent display. The motors are 50v., but are of such a low wattage only 2 watts that they can be driven by a resistor or condenser voltage dropper. **PRICE £2.25**. DITTO BUT 12 SWITCH **£3.65** POST & VAT PAID.

CAR TESTING OSCILLOSCOPE
Enables the electrical performance of the entire ignition circuit to be observed whilst the engine is running. It takes into account working conditions including compression and temperature, both of which directly affect the sparking plug firing voltage. Intermittent and four definite faults are clearly shown by changes in the image display. Made by E.E., these are self-contained with carrying handle in a crackle finish metal case. **PRICE £12.50**. Carriage £2 + 8p. Complete with operating instructions less leads. **PLUS 15p** POST & VAT.

WINDSCREEN WIPER CONTROL
Vary speed of your wiper to suit conditions. All parts and instructions to make **£3.25** plus post and VAT.



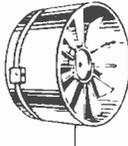EXTRACTOR FAN
Cleans the air at the rate of 10,000 cubic feet per hour. Suitable for kitchens, bathrooms, factories, changing rooms, etc. It's so quiet it can hardly be heard. Compact, 5 1/2" casing comprises motor, fan blades, sheet-steel casing, pull switch, mains connector and fixing brackets. **£4.74** including post & VAT. Monthly list available free, send long stamped envelope.



28 R.P.M. GEARED MAINS MOTOR
This is a substantial motor (1 1/2" stack induction type) quite powerful, definitely large enough to drive a rotating display or a tumbler for polishing stones etc. Approximate overall size 4" x 3 3/4" x 2 1/4". These are ex-used equipment, carrying our normal ex-equipment guarantees. **PRICE £2.95** POST & VAT PAID.

GLAMORISE YOUR ROCKS
The way to make rock samples, stamps etc. really show themselves off is to light them by means of our miniature UV tube. This is only 0w's so the electricity costs are negligible. Complete kit comprises UV tube and its 2 mounting holders, control choke and starter. **Total price £3.75** POST & VAT PAID.

TELESCOPIC AERIALS
for portable, car radio or transmitter. Chrome plated—six sections, extends from 7 1/2 to 47in. **50p** + 15p Post & VAT. **KNUCKLED MODEL FOR F.M.** **80p** + 17p Post & VAT.



SPEED CONTROLLED 9 V MOTOR
This is a motor with a governor 9v operation intended for record players and tape recorders. These are reversible and electro magnetically and acoustically screened. Size approx 1 1/2" diameter by 1" deep with good length spindle. Japanese made, portable replacement in a good many popular cassette and record players. **PRICE 95p** inc. POST & VAT.

NEED A SPECIAL SWITCH
Double Leaf Contact. Very slight pressure closes both contacts 12p each. Plastic pushrod suitable for operating **10p** each 10 for **68p**.



LIGHT OPERATED SWITCH FOR 12-24V BATTERY OPERATION
This is completely encapsulated and so make weather-proof against all the elements. It can, therefore, be put to many useful applications. To name a few: 1) Automatic switch for a mast head light on a boat. 2) Automatic switch on for battery operated lights or alarms in remote places. 3) Auto parking light for a vehicle, no doubt other applications would be found by our readers and we would be glad to hear about them. Encapsulate unit measures approx 1 6/8" x 9/8" x 1 5/8" deep. This can be conveniently mounted through the front panel of a conduit box or similar. **PRICE £1.95** POST & VAT PAID.

SPECIAL PRICES THIS MONTH

MULLARD UNILEX
A mains operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost any one. In easy-to-assemble modular form and complete with a pair of Godmans speakers this should sell at about £30 — but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only **£14.00** including VAT and postage.



GPO PUSH-BUTTON DIALLING UNIT
Will take the place of the normal rotating dial, has 10 numbered keys, so suitable for other digital systems. A desk mounting unit with rubber feet, this is a very intricate and expensive piece of apparatus. New and unused — our price only **£9** each including post and VAT.



TWIN OUTPUT POWER PACKS
These have two separately R.C. smoothed outputs so can operate two battery radios on a stereo amp without cross modulation (they will of course operate one radio/tape/cassette/calculator, in fact any battery appliance and will save their cost in a few months). Specs. Full wave rectification, double insulated mains transformer — total enclosed in a hard P.V.C. case — three core mains lead-terminal output — when ordering please state output voltage 4 1/2v., 6v., 7 1/2v., 9v., 12v or 24v. **Price £3.95**. Post and VAT included.



MULLARD THYRISTOR TRIGGER MODULE
This produces pulses for phase control triggering, it has two isolated outputs, so one thyristor or two thyristor (in separate arms of bridge) can be controlled by one module. The timing circuit is synchronised to the mains frequency and control is by an external variable resistor or from a voltage or current source. Provision is made for feedback where automatic control is required. **Price £5.95**.



THIS MONTH'S SNIP

250 watt Transformer is a very versatile transformer which can be used for many purposes. Rated at 250 watts it is very well built with frames for upright mounting and is varnish impregnated. Its primary is for 230/240 volts 50 cycles, it has four secondaries each 10v very high current windings. Just a few of the circuits it can power are 10-0-10v at up to 12 amps, 20-0-20v at up to 6 amps, single 10v at 25 amps, single 20v at 12 1/2 amps, single 30v at 9 amps; single 40v at 6.5 amps. The transformer can be used for power circuits (charging, etc.) or for amplifiers, there being an earth screen between primary and secondaries. A transformer like this today would cost at least £15 from the makers however, we are making a special offer at **£3.60** + 28p, post £1 + 8p each. Grab some while you can, our stock may not last long.

INFRA RED BINOCULARS
Made for military purposes during and immediately after the last war to enable snipers, vehicle drivers, etc. to see in the dark. The binoculars have to be fed from a high voltage source (5kV approx.) and providing the objects are in the rays of an infra red beam then the binoculars will enable these objects to be seen. Each binocular eye tube contains a complete optical lens system as well as the infra red cell, technical data on which is available. The binoculars are unused, believed to be in good order. In fact they were never issued and are still in original cases. **PRICE £16.50** per set.



SMITHS CENTRAL HEATING CONTROLLER
Push-button gives 10 variations as follows: (1) continuous hot water and continuous central heating (2) continuous hot water but central off at night (3) continuous hot water but central heating on for 2 periods during the day (4) hot water and central hot on but day time only (5) hot water all day but central heating only for 2 periods during the day (6) hot water and central heating on for 2 periods during the day time only — then for summer time use with central heating off (7) hot water continuous (8) hot water day time only (9) hot water twice daily (10) everything off.



SHORTWAVE CRYSTAL SET
Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19, 25, 31, 29 metre bands — Kit contains chassis front panel and all the parts. **£1.50** — crystal earphones 55p including VAT & Postage.



ONLY £1.50 FOR SEVEN ELECTRIC MOTORS
7 powerful batt. motors as used in racing cars and power models. Output and types vary for use in hundreds of projects — Tools, toys, models, etc. All brand new reversible and for 1 1/2-12v batts. Wiring diag. inc. VAT & POST PAID.



LIGHT PIPE
A mains operated travelling light array 24ft long is uses 130 miniature bulbs which flash in sequence to make bands of light move along the tube — The tube can be draped around a particular item or set and cannot fail to attract attention — complete kit consists of — 24ft of translucent tubing — 140 min. lamps — 8 yds multicore cable — motorised switch — taps for quick connections and full wiring instructions. **£15.00** FOR COMPLETE KIT. POST & VAT PAID.



INSTANT START FLUORESCENT LIGHTING BARGAINS
Starterless control gear, complete with tube ends and tube clips for window lighting, signs fascias, etc. 4ft 40w **£1.90**; 5ft 65w **£2.00**; 5ft 80w **£2.20**; 6ft 80w **£2.45**; and for parts as follows — twin 2ft 20w **£2.85**; twin 3ft 30w **£3.55**; twin 4ft 40w **£3.25**; twin 5ft 65w **£3.25**; twin 5ft 80w **£3.95**; twin 8ft 125w **£6.75**. These are about one half of maker's current prices and can be repeated once stocks are cleared. Please add 30p per piece to cover postage or carriage and 8% VAT.

Terms: When order under £5 please add 40p to offset handling and packing charges. Cash with order except institutions and Public Companies.

LIST FREE SEND SAE

SWITCH TRIGGER MATS
So thin is undetectable under carpet but will switch on with slight pressure. For burglar alarms, shop doors, etc. 24in x 18in **£1.90**, post & VAT 30p 13in x 10in **£1.50**, post & VAT 25p.



MAINS TRANSFORMERS

All standard 230-250 volt primaries		£ P
1v	1 amp (special)	1.78
2 1/2v	5 amp	.85
6 3v	2 amp	1.25
6 3v	3 amp	1.75
9v	1 amp	.95
9v	3 1/2 amp	2.50
12v	1 1/2 amp	1.60
12v	1 amp	1.00
6 5v-0 6 5v	1 amp	1.50
18v	1 amp	1.50
24v	2 amp	2.25
24v	3 amp	3.80
12 0-12v	50mA	1.20
6 0-6v	50mA	1.20
8 0-8v	1/2 amp	1.50
250 0-25v	2 amps	3.50
25v	1 1/2 amps	1.95
50v	2 amp & 6 3v	4.50
60v	5 amp & 5v	7.50
27v	8 amp	4.50
30v	37 amp	22.00
80v tapped 75v & 70v	4 amp	5.50
250v-60mA & 6 3v	1 1/2 amps	1.75
275 0-275v at 90mA & 6 4v	3 amps	2.25
EHT Transformer 5000v 23mA (intermittent)		5.50
Charger Transformers		
6v and 12v	2 amps	1.50
6v and 12v	3 amps	2.25
6v and 12v	5 amps	3.50

Add 30p per £1 to cover postage and VAT

MULTI-SPEED MOTOR
Six speeds are available 500, 850 and 1,100 r.p.m. and 8,000, 12,000 and 15,500 r.p.m. Shaft is 1/4in diameter and approximately 1in long 230/240v its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor, size approx 2in dia x 5in long. **Price £1.50** including post & VAT. **SPEED CONTROL SWITCH 50p** + 4.



SPIT MOTOR WITH CARTER GEAR-BOX
Probably one of the best spit motors made. Originally intended to be used in very high priced cookers however, this can be put to plenty of other uses, for instance your garden barbecue or to drive a colour disc for a dance or display or to drive a tumbler for stone polishing, in fact, there is no end to its uses. Normal mains operation. Special price during May and June **£2.75** including post & VAT.

SOUND TO LIGHT UNIT
Another new kit this month is single Channel Sound to Light Unit, complete kit including plastic container, main components include 5 amp thyristor, plus transformer, variable pot with on/off switch and theoretical circuit diagram. **PRICE £1.95** POST & VAT PAID.



SMITHS 24-HR. TIMER HEART
Really the Autoset without its plastic case. This is a 24 hr twin on twice off, clock switch which will repeat until re-programmed. Switches rated at 15 amps. Limited supplies—**£3.95** including VAT & post.

PRESSURE SWITCH
Containing a 15 amp change over switch operated by a diaphragm which in turn is operated by air pressure through a small metal tube. The operating pressure is adjustable but is set to operate in approx 10in of water. These are quite low pressure devices and can in fact be operated simply by blowing into the inlet tube. Original use was for washing machine to turn off water when tube had reached correct level but no doubt has many other applications. **£1.95** including post & VAT.



DC HIGH CURRENT PANEL METERS
3 1/2" wound wide angle 240° movement meters flush mounting fitted with external shunts made by Crompton Parkinson, brand new, still in maker's cartons. These are a real bargain at **£5.50** each including post & VAT. Reasonable quantities available in the following ranges: 0-10 amps, 0-20 amps, 0-30 amps, 0-40 amps, 0-50 amps.



PP3/PP9 BATTERY ELIMINATOR
Made in Japan for Bush Radio. This is very neat little transformer driven full wave unit totally enclosed with input mains and output leads. This power supply unit which was originally marketed by Bush at over £6 is offered as this month's snip. **PRICE £2.00** INCLUDING POST & VAT.

MULLARD AUDIO AMPLIFIERS
All in module form, each ready built complete with heat sinks and connection tags, data supplied.

Model 1153 500mW power output	£1.10 including post & VAT
Model 1172 1w power output	£1.35 including post & VAT
Model EP900 4 watt power, output	£2.40 including post & VAT
EP9001 twin channel or stereo pre-amp.	£2.50 including post & VAT



J. BULL (ELECTRICAL) LTD.
(Dept. W.W.), 103 TAMWORTH ROAD CROYDON CRO IX

BENTLEY ACOUSTIC CORPORATION LTD.

7A GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX. Tel. 6743

ALL PRICES SHOWN INCLUDE V.A.T. AT 12 1/2 %

0B2 0.40	6B8G 0.35	6L6GC 0.70	12AV6 0.60	30P4 0.90	AZ1 0.50	EBC90 0.50	EL35 3.00	PABC80 0.45	PY83 0.44	U18/20 1.90	Transistors 0.20	AF125 0.20	G05 0.32	OC44 0.12
0Z4 0.55	6BA6 0.40	6L7(M) 0.60	12AX7 0.34	30P16 0.37	AZ21 0.60	EBC91 0.50	EL37 3.00	PCY8 0.62	U19 0.90	0.00 and Diodes 0.00	AF129 0.21	G06 0.32	OC45 0.13	OC46 0.18
1A3 0.60	6BC8 0.40	6L7 0.39	12AY7 1.00	30P18 0.50	B3E 0.75	EBC92 0.50	EL41 0.65	PC86 0.70	U22 0.85	IN124A 0.81	AF139 0.76	G08 0.23	OC46 0.18	OC46 0.18
1ASGT 0.55	6BE6 0.40	6L8 0.60	12BA6 0.50	30P21 1.00	B3E 0.75	EBC93 0.50	EL81 0.65	PC95 0.70	U25 0.71	IN4744 0.58	AF178 0.79	G09 0.23	OC46 0.18	OC46 0.18
1A7GT 0.60	6BG6 1.20	6L9 2.00	12BE6 0.50	30P22 1.00	B719 0.39	EBC94 0.50	EL83 0.70	PC97 0.39	U26 0.60	IN4952 0.58	AF180 0.56	G11 0.23	OC46 0.18	OC46 0.18
1B5GT 0.55	6BH6 0.70	6LD12 0.40	12BH7 0.55	30P23 1.00	B729 0.79	EBC95 0.50	EL86 0.60	PC98 0.49	U31 0.50	2N404 0.21	AF186 0.64	G12 0.23	OC46 0.18	OC46 0.18
1C2 1.00	6BJ6 0.65	6LD20 0.60	12BY7 0.85	30P24 1.29	B739 0.79	EBC96 0.50	EL90 0.47	PC99 0.49	U33 1.75	2N986 0.61	AF239 0.44	G14 0.26	OC46 0.18	OC46 0.18
1D5 0.75	6BK7A 0.85	6N7GT 0.70	12E1 3.50	30P25 1.00	B749 0.79	EBC97 0.50	EL95 0.67	PC98 0.61	U37 2.00	2N1756 0.56	ASV27 0.39	G15 0.47	OC46 0.18	OC46 0.18
1G6 1.00	6BQ5 0.34	6PL12 0.40	12J5GT 0.40	35A3 0.75	B759 0.79	EBC98 0.50	EL96 0.67	PC98 0.61	U45 1.20	2N2369 0.16	ASV28 0.39	G16 0.47	OC46 0.18	OC46 0.18
1HG7 0.90	6BQ7A 0.60	6P15 0.34	12J7GT 0.70	35C5 0.80	B769 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U47 0.71	2N2996 1.16	ASV29 0.39	G17 0.47	OC46 0.18	OC46 0.18
1LA 0.25	6BR7 1.00	6Q7 0.50	12K5 1.50	35D5 0.90	B779 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U49 0.60	2N2996 1.16	ASV29 0.39	G18 0.47	OC46 0.18	OC46 0.18
1LD5 0.70	6BR8 1.25	6Q7GT 0.50	12K7GT 0.50	35L6GT 0.80	B789 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U50 0.55	2N3063 2.30	BA116 0.21	G19 0.47	OC46 0.18	OC46 0.18
1LN5 0.70	6BS7 1.70	6Q7M 0.65	12K8 0.75	35W4 0.55	B799 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U52 0.60	2N3121 2.90	BA129 0.14	G20 0.47	OC46 0.18	OC46 0.18
1NSGT 0.75	6BW6 1.00	6R7G 0.70	12Q7GT 0.50	35Z3 0.80	B809 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U56 0.70	2N3703 0.23	BA130 0.12	G21 0.47	OC46 0.18	OC46 0.18
1R5 0.50	6BW7 0.85	6R7(M) 0.70	12Q8GT 0.50	35Z4GT 0.80	B819 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U57 0.45	2N3709 0.23	BA153 0.18	G22 0.47	OC46 0.18	OC46 0.18
1S4 0.40	6BX6 0.29	6SA7 0.55	12S7 0.55	42 1.50	B829 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U58 0.60	2N3988 0.58	BCV12 0.58	G23 0.47	OC46 0.18	OC46 0.18
1SS 0.55	6BY7 0.36	6SC7GT 0.75	12S7GT 0.55	42 1.50	B839 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U59 1.00	2N3988 0.58	BCV12 0.58	G24 0.47	OC46 0.18	OC46 0.18
1T05 0.30	6BZ8 0.80	6S7 0.55	12SH7 0.50	50B5 0.95	B849 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U61 0.80	2N3988 0.58	BCV12 0.58	G25 0.47	OC46 0.18	OC46 0.18
1U4 0.70	6C4 0.40	6SH7 0.55	12SI7 0.60	50C5 0.70	B859 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U62 0.80	2N3988 0.58	BCV12 0.58	G26 0.47	OC46 0.18	OC46 0.18
1U5 0.85	6CSG 0.60	6S7 0.55	12SK7 0.60	50C6 1.20	B869 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U63 2.00	2N3988 0.58	BCV12 0.58	G27 0.47	OC46 0.18	OC46 0.18
2D21 0.55	6C6 0.45	6SK7GT 0.55	12SN7GT 0.75	50E45 0.85	B879 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U64 1.00	2N3988 0.58	BCV12 0.58	G28 0.47	OC46 0.18	OC46 0.18
2GK5 0.75	6C9 2.00	6S7 0.55	12SQ7 0.60	50L6GT 1.00	B889 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U65 1.00	2N3988 0.58	BCV12 0.58	G29 0.47	OC46 0.18	OC46 0.18
2X2 0.70	6C10 0.71	6U4GT 0.90	12SQ7GT 0.80	72 0.70	B899 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U66 1.00	2N3988 0.58	BCV12 0.58	G30 0.47	OC46 0.18	OC46 0.18
3A4 0.55	6C10A 0.60	6U4GT 0.90	12SQ7GT 0.80	72 0.70	B909 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U67 1.00	2N3988 0.58	BCV12 0.58	G31 0.47	OC46 0.18	OC46 0.18
3B7 0.55	6C12 0.35	6V6GT 0.30	12S7GT 0.55	72 0.70	B919 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U68 1.00	2N3988 0.58	BCV12 0.58	G32 0.47	OC46 0.18	OC46 0.18
3D6 0.40	6C16 0.60	6V6GT 0.55	14S7 1.00	85A3 0.75	B929 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U69 1.00	2N3988 0.58	BCV12 0.58	G33 0.47	OC46 0.18	OC46 0.18
3Q4 0.90	6C18A 0.90	6X4 0.45	18 1.25	90A3 0.75	B939 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U70 1.00	2N3988 0.58	BCV12 0.58	G34 0.47	OC46 0.18	OC46 0.18
3Q5GT 0.70	6C16 0.75	6X5GT 0.45	19A05 0.65	90C3 2.90	B949 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U71 1.00	2N3988 0.58	BCV12 0.58	G35 0.47	OC46 0.18	OC46 0.18
3S4 0.45	6C18A 0.95	6V6G 0.95	19B06G 1.00	90CV 2.90	B959 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U72 1.00	2N3988 0.58	BCV12 0.58	G36 0.47	OC46 0.18	OC46 0.18
3V4 0.90	6C18 0.50	6U7G 1.25	19C3 0.50	90C1 0.85	B969 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U73 1.00	2N3988 0.58	BCV12 0.58	G37 0.47	OC46 0.18	OC46 0.18
4C36 0.75	6C28 0.75	6S7 0.55	14H7 0.75	85A2 0.75	B979 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U74 1.00	2N3988 0.58	BCV12 0.58	G38 0.47	OC46 0.18	OC46 0.18
3Q4 0.90	6C28A 0.90	6X4 0.45	18 1.25	90A3 0.75	B989 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U75 1.00	2N3988 0.58	BCV12 0.58	G39 0.47	OC46 0.18	OC46 0.18
3Q5GT 0.70	6C16 0.75	6X5GT 0.45	19A05 0.65	90C3 2.90	B999 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U76 1.00	2N3988 0.58	BCV12 0.58	G40 0.47	OC46 0.18	OC46 0.18
3S4 0.45	6C18A 0.95	6V6G 0.95	19B06G 1.00	90CV 2.90	B999 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U77 1.00	2N3988 0.58	BCV12 0.58	G41 0.47	OC46 0.18	OC46 0.18
3V4 0.90	6C18 0.50	6U7G 1.25	19C3 0.50	90C1 0.85	B999 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U78 1.00	2N3988 0.58	BCV12 0.58	G42 0.47	OC46 0.18	OC46 0.18
4C36 0.75	6C28 0.75	6S7 0.55	14H7 0.75	85A2 0.75	B999 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U79 1.00	2N3988 0.58	BCV12 0.58	G43 0.47	OC46 0.18	OC46 0.18
3Q4 0.90	6C28A 0.90	6X4 0.45	18 1.25	90A3 0.75	B999 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U80 1.00	2N3988 0.58	BCV12 0.58	G44 0.47	OC46 0.18	OC46 0.18
3Q5GT 0.70	6C16 0.75	6X5GT 0.45	19A05 0.65	90C3 2.90	B999 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U81 1.00	2N3988 0.58	BCV12 0.58	G45 0.47	OC46 0.18	OC46 0.18
3S4 0.45	6C18A 0.95	6V6G 0.95	19B06G 1.00	90CV 2.90	B999 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U82 1.00	2N3988 0.58	BCV12 0.58	G46 0.47	OC46 0.18	OC46 0.18
3V4 0.90	6C18 0.50	6U7G 1.25	19C3 0.50	90C1 0.85	B999 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U83 1.00	2N3988 0.58	BCV12 0.58	G47 0.47	OC46 0.18	OC46 0.18
4C36 0.75	6C28 0.75	6S7 0.55	14H7 0.75	85A2 0.75	B999 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U84 1.00	2N3988 0.58	BCV12 0.58	G48 0.47	OC46 0.18	OC46 0.18
3Q4 0.90	6C28A 0.90	6X4 0.45	18 1.25	90A3 0.75	B999 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U85 1.00	2N3988 0.58	BCV12 0.58	G49 0.47	OC46 0.18	OC46 0.18
3Q5GT 0.70	6C16 0.75	6X5GT 0.45	19A05 0.65	90C3 2.90	B999 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U86 1.00	2N3988 0.58	BCV12 0.58	G50 0.47	OC46 0.18	OC46 0.18
3S4 0.45	6C18A 0.95	6V6G 0.95	19B06G 1.00	90CV 2.90	B999 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U87 1.00	2N3988 0.58	BCV12 0.58	G51 0.47	OC46 0.18	OC46 0.18
3V4 0.90	6C18 0.50	6U7G 1.25	19C3 0.50	90C1 0.85	B999 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U88 1.00	2N3988 0.58	BCV12 0.58	G52 0.47	OC46 0.18	OC46 0.18
4C36 0.75	6C28 0.75	6S7 0.55	14H7 0.75	85A2 0.75	B999 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U89 1.00	2N3988 0.58	BCV12 0.58	G53 0.47	OC46 0.18	OC46 0.18
3Q4 0.90	6C28A 0.90	6X4 0.45	18 1.25	90A3 0.75	B999 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U90 1.00	2N3988 0.58	BCV12 0.58	G54 0.47	OC46 0.18	OC46 0.18
3Q5GT 0.70	6C16 0.75	6X5GT 0.45	19A05 0.65	90C3 2.90	B999 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U91 1.00	2N3988 0.58	BCV12 0.58	G55 0.47	OC46 0.18	OC46 0.18
3S4 0.45	6C18A 0.95	6V6G 0.95	19B06G 1.00	90CV 2.90	B999 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U92 1.00	2N3988 0.58	BCV12 0.58	G56 0.47	OC46 0.18	OC46 0.18
3V4 0.90	6C18 0.50	6U7G 1.25	19C3 0.50	90C1 0.85	B999 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U93 1.00	2N3988 0.58	BCV12 0.58	G57 0.47	OC46 0.18	OC46 0.18
4C36 0.75	6C28 0.75	6S7 0.55	14H7 0.75	85A2 0.75	B999 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U94 1.00	2N3988 0.58	BCV12 0.58	G58 0.47	OC46 0.18	OC46 0.18
3Q4 0.90	6C28A 0.90	6X4 0.45	18 1.25	90A3 0.75	B999 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U95 1.00	2N3988 0.58	BCV12 0.58	G59 0.47	OC46 0.18	OC46 0.18
3Q5GT 0.70	6C16 0.75	6X5GT 0.45	19A05 0.65	90C3 2.90	B999 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U96 1.00	2N3988 0.58	BCV12 0.58	G60 0.47	OC46 0.18	OC46 0.18
3S4 0.45	6C18A 0.95	6V6G 0.95	19B06G 1.00	90CV 2.90	B999 0.79	EBC99 0.50	EL96 0.67	PC98 0.61	U97 1.00	2N3988 0.58	BCV12 0.58	G61 0.47	OC46 0.18	OC46 0.18
3V4														

New to the UK from PRONTO

**Battery operated LCD read out
CALENDAR CLOCK KIT - crystal accuracy -
Bold Digits - runs on two Penlight Cells.**




Now is the time for the hobbyist to move into Advanced Technology with Pronto!
PRONTO MODEL 301 - The first completely portable liquid crystal display, digital CALENDAR CLOCK KIT offered in the United Kingdom.

- * Battery operation - two small alkaline cells give a minimum life of 12 months.
- * Superb accuracy through crystal control - of 3 minutes a year
- * Wide angle display with 1/2" digits
- * Push Buttons give choice of 3 display modes - hours minutes on 12 hour display with flashing colon, or seconds, or date.
- * PRONTO 301 comes complete with easy to follow

instructions AT **£29-50** including V.A.T. You save Pounds off the recommended retail price of a comparable made up clock.

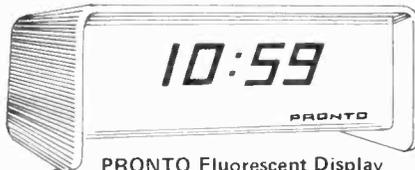TERMS: Cash with order - make cheque and/or postal order payable to PRONTO ELECTRONIC SYSTEMS LIMITED. (P & P - U.K. £0.45 Overseas £1.50)



PRONTO Fluorescent Display Alarm Clock KIT

Wake up to the electronic age with the new PRONTO 304 Alarm Clock

- * Large Bright Green Display
- * Alarm with 10 minute 'snooze' feature
- * AM/PM indication and simple setting
- * Automatic brightness control on digits governed by room lighting

- * Ingenious gravity alarm - time setting mode switch
- * Full assembly instructions

AT **£15-50** including V.A.T. With all PRONTO products - enquiries from the Trade, as well as the Hobbyist, are welcome, and you can also buy individual components!

PRONTO CONSTRUCTOR'S CLUB
When you buy your first Pronto kit you're automatically a Member of the PRONTO CONSTRUCTOR'S CLUB. It will not only keep you in the picture on new ideas and kits... but gives you **FREE a £2 Voucher** against the purchase of your next kit!
Isn't it time you joined the Club?

Please send me -

- PRONTO 301 KIT/S AT £29.50 EACH (Plus P & P)
- PRONTO 304 KIT/S AT £15.50 EACH (Plus P & P)

My cheque/P.O. for _____ is enclosed

NAME _____
ADDRESS _____

Pronto Electronic Systems Ltd.
645/647 High Rd., Seven Kings,
Essex IG3 8RA. 01-599 3041



The SECOND-USER Computer Specialists

COMPUTER SALES AND SERVICES

Peripherals and Systems for Data Processing Systems, Equipment and Components

Mini-Computer Exchange

- PDP 8K** Processor with Teletype & Reader Punch Control Modules.
- PDP 81 8K & 16K** Processors with Teletype Control Module
- PDP11/20 20K** Processor with Dual DECIape & Control. 64K Disc Drive & Control. Programmable Real Time Clock 64 ch. Line Printer
- NOVA 840 24K** Processor with 128K Nova Disc. Visual Display Unit. Real Time Clock. Paper Tape Reader. ASR 33 Teletype
- HONEYWELL 1250 64K** Processor with 2 x 64Kc/s 7-track Tape Units. 950 lpm 120pp Line Printer. Card Reader. 2 x 18.4meg. Disk Drives
- PERIPHERALS:** DEC DF32 Disk Drive & Control. DEC TU60 Dual Cassette Drive & Control. DEC RT02 Single Line Alphanumeric Display and Control. ASR33, ASR35 & KSR33 Teletypes

MAGNETIC TAPES.
Manufacturer's surplus stocks just received. Brand new in original sealed packs. 1/2" x 2,400 ft. **£4** per reel, 3/4" x 2,400 ft. **£4.50** per reel. P&P extra.

Add 8% VAT to all prices shown. Carriage extra - details on request.

Paper Tape Punches and Readers



TELETYPE BRPE 110 cps. Synchronous Punch 5 7/8 channel. Self-contained, mains-operated unit consisting of punch unit, base motor and tape supply spool. Price **£150.00**. Sound reducing cabinet available at **£25.00**.

FACIT 4060 rack mounting heavy-duty punch. 5.8 channel. maximum operating speed 150 cps. Complete with supply and take-up spools, tape low out sensor and large built-in chad box. **£595.00**. Control unit also available.

- TALLY P.120** panel-mounted perforator. Asynchronous operation up to 120 cps. Integral tape supply and take-up spools. Price **£200.00**.
- TALLY 420** Rack-mounting perforator. Asynchronous operation up to 60 cps. Integral supply and take-up spools. Complete with Model 5088 transistorised drive package. **£495.00**
- WELMEC LOW-SPEED PUNCH.** Magnetically driven up to 17 cps. Ideal for data logging. Large chad box. **£45.00**
- FACIT 4001** Rack-mounting high-speed reader. A very high quality unit with dielectric reading and capstan drive. Reading speed up to 500 cps (or 1000 cps using separate spooler). Can be stopped between two consecutive characters. **£650.00**.
- TALLY R150A READER.** 150 rps. Fast rewind. Suitable for rack mounting. Complete with supply and take-up spools. **£200.00**
- TALLY 424** rack-mounting star-wheel reader. Bidirectional operation up to 600 cps. Complete with supply and take-up spools. Price **£125.00**.
- WELMEC R82** solenoid-operated mechanical reader. Low-cost low-speed reader for speeds up to 17 cps. Compact free-standing unit. **£45.00**
- DATA DYNAMICS** Punched Card-to-Paper Tape Converter. Paper tape hand editing units. **£12.50** (P&P 50p). Paper tape hand splicers **£18.50** (P&P 50p)
- IBM 1130 SYSTEM BK** Processor, Paper tape reader and punch. Card read punch. Automatic typewriter console
- IBM I/O WRITERS** Model 73 Golfball Input/Output typewriters. BCD Coded. **£295.00**
- IBM 7330 TAPE DECKS.** 'Stripped-down units' (i.e. no electronics) consisting of complete deck with 7-track read/write head, drive and vacuum motors and control panel. Read/write speed 36"/sec. 556 bp. low and high speed rewind.
- MDS KEY-TO-TAPE ENCODERS.** 9-track encoders. IBM coded. Price **£450.00**.

New Economy 80 Column Hand Punch

Completely redesigned with many important new features - send for brochure from **£69.50**



Keyboards

- 16-Key Japanese Keyboard.** BRAND NEW SURPLUS! Magnetically operated reed relay switches mounted on PCB. 9 white keys, 4 black, 2 yellow, 1 red. Dimensions 3 1/2" x 3 1/2" x 1 1/2". Price **£3.50** (P&P 30p).
- 4 BANK HONEYWELL ALPHANUMERIC KEYBOARD - BRAND NEW** Mounted on printed circuit board (non-coded) 53 character keys + 10 instruction keys and 2 space bars. Layout can be re-arranged as required. Ideal for prototypes and special applications. 'Hall-effect' switches. Power requirement +5V 420 mA. Price **£20.00** (P&P £1)
- REED SWITCH 4-BANK ALPHANUMERIC KEYBOARD** mounted on printed circuit board with ASCII coded output, 43 character keys + 2 shift keys and 12 instructional keys. Ideal for data displays, computer programming, etc. (a) Ex-equipment, housed in metal case. **£30.00** + £3.00 P&P. (b) Brand new, mounted on PCB board only. **£30.00** + £1.00 P&P
- MINIATURE MATRIX PROGRAMME BOARDS.** X.Y matrix board with 3mm grating. BRAND NEW by Ghelmetti of Switzerland. 20x30 positions (4 1/2" x 3 1/2"). **£15.00**; 12x10 (2 3/4" x 2 1/4") **£8.00**; 3x10 (1 3/4" x 1 1/2") **£4.00**. P&P 40p. Diode pins available to special order from 40p each
- SANDERS 720 DATA DISPLAY SYSTEM.** 6 ASCII-coded visible display units linked via control unit to communications buffer. Suitable for use with IBM 360/370 and many other processors.

COMPUTER SALES & SERVICES (EQUIPMENT) LIMITED
49/53 Pancras Road, London NW1 2QB. Tel. 01-278 5571

Callers welcome Monday to Friday 9 a.m. to 5 p.m.

WW-090 FOR FURTHER DETAILS

RST VALVE MAIL ORDER CO.

159 Fallsbrook Rd, Streatham, London, SW16 6ED

Tel: 01-677 2424 Telex: 946 708.

VALVES	ECH35	1.50	EZ80	0.30	PEN45DD	UCL83	0.70	6DC8G	1.50	30C15	1.00
AZ31	1.00	ECH81	0.35	EZ80	0.31	UF41	0.75	6CH6	2.20	30C17	1.00
AZ41	0.70	ECH83	0.50	GY501	0.60	UF89	0.50	6E5GT	1.50	30C18	0.90
CB131	1.40	ECH84	0.50	GZ30	0.65	UL41	0.85	6F23	0.90	30F5	1.00
CL33	1.50	ECL80	0.60	GZ32	0.65	UL84	0.50	6J5GT	0.55	30F11	1.00
CY31	1.00	ECL82	0.42	GZ34	0.75	UY41	0.55	6J5GT	0.55	30F14	1.00
DAF91	0.46	ECL86	0.55	H63	0.30	UY85	0.45	6J7GT	0.45	30F15	0.95
DAF96	0.60	ECL800	0.55	HL84	0.50	V448	1.25	6K6GT	0.80	30F17	0.95
DCX90	1.35			LD141DD		VR75/30	0.55	6K7GT	0.35	30P12	1.00
DF91	0.40	EF37A	1.50	HN309	1.50	VR105/30	0.40	6K9GT	0.50	30P19	0.95
DF96	0.60	EF39	1.25	KT81	3.40	VR150/30	0.40	6L25	3.00	30PL1	0.95
DK91	0.50	EF41	0.75	KT96	3.40			6M25	3.00	30PL13	1.10
DK92	1.00	EF55	1.50	KT81 (7C5)	1.50			6M25	3.00	30PL14	1.10
DK96	0.75	EF80	0.35	PL801	1.00			6M25	3.00	30PL15	1.10
DL32	0.50	EF86	0.45	PL802	2.00	YR3	0.45	6S7GT	0.30	3516GT	0.90
DL34	0.44	EF86	0.50	PT88	1.65	YR5	1.25	6S7GT	0.55	35W4	0.80
DL36	0.55	EF89	0.35	PT22	0.63	YR5	1.25	6S7GT	0.55	35Z3	0.80
DM70	0.70	EF91	0.40	PT33	0.63	YR5	1.25	6S7GT	0.55	35Z4GT	0.70
DY78.7	0.45	EF92	0.50	PT81/800	1.50	YR5	1.25	6S7GT	0.55	50C5	1.50
DY802	0.47	EF93	0.80	YR5	1.25	YR5	1.25	6S7GT	0.55	50C6G	1.20
EAB90	0.38	EF93	0.80	YR5	1.25	YR5	1.25	6S7GT	0.55	60C4	0.45
EA42	0.70	EF94	0.60	YR5	1.25	YR5	1.25	6S7GT	0.55	60C4	0.45
EA47801	0.75	EL33	0.30	YR5	1.25	YR5	1.25	6S7GT	0.55	60C4	0.45
EB33	1.00	EL34	0.70	YR5	1.25	YR5	1.25	6S7GT	0.55	60C4	0.45
EBC41	0.75	EL41	0.90	YR5	1.25	YR5	1.25	6S7GT	0.55	60C4	0.45
EB81	0.40	EL42	1.55	YR5	1.25	YR5	1.25	6S7GT	0.55	60C4	0.45
EB90	0.40	EL43	2.35	YR5	1.25	YR5	1.25	6S7GT	0.55	60C4	0.45
EBF83	0.40	EL81	2.00	YR5	1.25	YR5	1.25	6S7GT	0.55	60C4	0.45
EBF89	0.32	EL95	0.60	YR5	1.25	YR5	1.25	6S7GT	0.55	60C4	0.45
ECL360	1.75	EL96	0.60	YR5	1.25	YR5	1.25	6S7GT	0.55	60C4	0.45
ECC40	1.00	EM180	0.55	YR5	1.25	YR5	1.25	6S7GT	0.55	60C4	0.45
ECC81	0.45	EM81	0.60	YR5	1.25	YR5	1.25	6S7GT	0.55	60C4	0.45
ECC82	0.38	EM81	0.60	YR5	1.25	YR5	1.25	6S7GT	0.55	60C4	0.45
ECC83	0.38	EM81	0.60	YR5	1.25	YR5	1.25	6S7GT	0.55	60C4	0.45
ECC85	0.45	EM81	0.60	YR5	1.25	YR5	1.25	6S7GT	0.55	60C4	0.45
ECC88	0.50	EM81	0.60	YR5	1.25	YR5	1.25	6S7GT	0.55	60C4	0.45
ECC90	0.45	EM81	0.60	YR5	1.25	YR5	1.25	6S7GT	0.55	60C4	0.45
ECC92	0.45	EM81	0.60	YR5	1.25	YR5	1.25	6S7GT	0.55	60C4	0.45

INDUSTRIAL VALVES	5R/255M	705A	6060	CV131	CV3986	EF54	OD3
1B3GT	5R/256M	715A	6061	CV132	CV3988	EF55	OG3
1B24	5R/257M	715B	6062	CV133	CV3991	EF804	OZ4
1B35A	5C22	723A/B	6063	CV135	CV3998	EFP60	OZ4A
1B63A	5D21	725A	6064	CV136	CV4001	EL91	PT15
1N21B	5R4GY		6065	CV137	CV4002	EN30	QA2400
1N23B	5U4GB		6072	CV140	CV4004	EN31	QA2403
1N23CR	801		6073	CV144	CV4005	EN91	QA2404
1X2A	5Z3		6074	CV160	CV4006	ESU74	QA2406
607GT	5Z4G		6080	CV173	CV4007	ESU76	QA2407
6097B	6AF4A		6097C	CV187	CV4008	FX219	QB3 300
2A3	6AK5		6130	CV188	CV4009	FX225	QB3 5 750
2AS15	6AM5		6189	CV190	CV4010	FX225	QB4 1100
2C26A	6AM6		6197	CV210	CV4011	FX225	QB4 1100
2C34	6AN5		6201	CV213	CV4012	FX225	QB4 1100
2C39A	6AN8		6202	CV284	CV4013	FX225	QB4 1100
2C43	6AR5		6203	CV286	CV4014	FX225	QB4 1100
2D21	6AS6		6205	CV287	CV4015	FX225	QB4 1100
2D21W	6AX5GT		6205	CV287	CV4016	FX225	QB4 1100
2E24	6AUGTA		6242	CV315	CV4017	FX225	QB4 1100
2I31	6AU6		6463	CV332	CV4018	FX225	QB4 1100
2I50	6AV5GTA		6530	CV347	CV4019	FX225	QB4 1100
2I56A	6AW8A		6807	CV345	CV4020	FX225	QB4 1100
2I56B	6AX5GT		6807	CV345	CV4022	FX225	QB4 1100
2K25	6BJG		6923	CV354	CV4023	FX225	QB4 1100
2K26	6BK4		6939	CV359	CV4024	FX225	QB4 1100
2K28	6BK7A			CV360	CV4025	FX225	QB4 1100
2K45	6BL7GTA			CV361	CV4028	FX225	QB4 1100
2X2A	6BN6			CV372	CV4033	FX225	QB4 1100
3A/107A	6BR7			CV378	CV4035	FX225	QB4 1100
3A/108A	6BS7			CV391	CV4038	FX225	QB4 1100
3A/108B	6BX7GT			CV397	CV4043	FX225	QB4 1100
3A/109B	6BZ6			CV428	CV4045	FX225	QB4 1100
3A/110A	6C86			CV434	CV4056	FX225	QB4 1100
3A/110B	6CH6			CV447	CV4059	FX225	QB4 1100
3A/146J	6CL6			CV449	CV4062	FX225	QB4 1100
3A/167M	6CW4			CV466	CV4063	FX225	QB4 1100
3A5	6DK6			CV469	CV4064	FX225	QB4 1100
3B/240M	6DQ6B			CV488	CV4079	FX225	QB4 1100
3B241M	6E8A			CV491	CV4501	FX225	QB4 1100
3B28	6E8B			CV492	CV4502	FX225	QB4 1100
3B29	6F16(metal)			CV493	CV4503	FX225	QB4 1100
3C22	6K7GT			CV497	CV4504	FX225	QB4 1100
3C23	6L8A			CV507	CV4507	FX225	QB4 1100
3C24	6M25			CV1072	CV4508	FX225	QB4 1100
3C24/24G	6V6GT			CV1076	CV4509	FX225	QB4 1100
3C45				CV1092	CV4510	FX225	QB4 1100
3CX100A5				CV1219	CV4511	FX225	QB4 1100
3E29				CV1475	CV4512	FX225	QB4 1100
3J121E				CV1476	CV4513	FX225	QB4 1100
3J160E				CV1477	CV4514	FX225	QB4 1100
3J170E				CV1478	CV4515	FX225	QB4 1100
3O150E				CV1794	CV4516	FX225	QB4 1100
3Q195E				CV1890	CV4517	FX225	QB4 1100
3R1				CV1891	CV4518	FX225	QB4 1100
3V340B				CV1892	CV4519	FX225	QB4 1100
3V340A				CV1893	CV4520	FX225	QB4 1100
3V340B				CV1894	CV4521	FX225	QB4 1100
4125A				CV1895	CV4522	FX225	QB4 1100
4250A				CV1896	CV4523	FX225	QB4 1100
4400A				CV1897	CV4524	FX225	QB4 1100
4B32				CV1898	CV4525	FX225	QB4 1100
4C35				CV1899	CV4526	FX225	QB4 1100
4CX250B				CV1900	CV4527	FX225	QB4 1100
4E27				CV1901	CV4528	FX225	QB4 1100
4J50				CV1902	CV4529	FX225	QB4 1100
4K52				CV1903	CV4530	FX225	QB4 1100
4L52A				CV1904	CV4531	FX225	QB4 1100
4M53				CV1905	CV4532	FX225	QB4 1100
4X150A				CV1906	CV4533	FX225	QB4 1100
4X150D				CV1907	CV4534	FX225	QB4 1100
4X250B				CV1908	CV4535	FX225	QB4 1100
5B/251M				CV1909	CV4536	FX225	QB4 1100
5B/252M				CV1910	CV4537	FX225	QB4 1100
5B/254M				CV1911	CV4538	FX225	QB4 1100

TRANSISTORS & ICs	2N696	0.15	2N4289	0.30	SN7476	0.65	
AA119	0.07	BF179	0.33	3N141	0.81	SN7480	0.48
AA215	0.12	BF180	0.36	40360	0.40	SN7482	0.81
AC107	0.51	BF194	0.10	40361	0.45	SN7483	0.81
AC126	0.25	BF195	0.13	40362	0.40	SN7484	1.00
AC127	0.25	BF197	0.15	40363	0.40	SN7486	0.47
AC128	0.15	BF200	0.32	40364	0.40	SN7488	0.55
AC176	0.25	BF561	0.25	40365	0.40	SN7491A	1.00
AC187	0.45	BF598	0.25	40366	0.40	SN7492	0.70
AC188	0.20	BF510	0.61	40367	0.40	SN7493	0.80
AC191	0.35	BF529	0.28	40368	0.40	SN7494	0.80
AC192	0.15	BF588	0.24	40369	0.40	SN7495	0.80
AD140	0.50	BF590	0.21	40370	0.40	SN7496	0.95
AD149	0.75	BF591	0.21	40371	0.40	SN7497	0.85
AD161	0.44	BF592	0.20	40372	0.40	SN7498	0.85
AD162	0.44	BR100	0.40	40373	0.40	SN7499	0.85
AF115	0.25	BY100	0.27	40374	0.40	SN7500	0.85
AF116	0.25	BY126	0.14	40375	0.40	SN7501	0.85
AF117	0.24	BY127	0.12	40376	0.40	SN7502	0.85
AF186	0.48	BZ761 series		40377	0.40	SN7503	0.85
AF239	0.44	ORP12	0.20	40378	0.40	SN7504	0.85
ASV27	0.40	BZ768 series		40379	0.40	SN7505	0.85
ASV28	0.25			40380	0.40	SN7506	0.85
BA102	0.25	CRS1-05	0.45	40381	0.40	SN7507	0.85
BA115	0.10	CRS1-40	0.65	40382	0.40	SN7508	0.85
BC107	0.14	CRS1-05	0.45	40383	0.40	SN7509	0.85
BA108	0.13	CRS1-40	0.65	40384	0.40	SN7510	0.85
BC109	0.14	MJE340	0.47	40385	0.40	SN7511	0.85
BC113	0.15	MJE370	0.60	40386	0.40	SN7512	0.85
BC117	0.21	MJE520	0.63	40387	0.40	SN7513	0.85
BC143	0.30	MJE2855	1.27	40388	0.40	SN7514	0.85
BC147	0.10	MJE3055	0.77				

Collect wireless world Circards. And build a valuable dossier on circuit design.


Circards is a unique and comprehensive system, launched by Wireless World, to provide professional engineers and enthusiasts with valuable and up-to-the-minute data on circuit design — data not available from any other single source.

Each Circard is 8" x 5" and usually shows a specific tested circuit, a description of the circuit operation; component values and ranges; circuit limitations and modifications; performance data and graphs.

The double-sided format enables the Circard to be filed in standard boxes for easy reference. And the plastic wallet provided keeps the cards well protected.

Circard sets (10 cards) come in wallets and cost £2.00. A subscription for 10 consecutive sets costs £18.

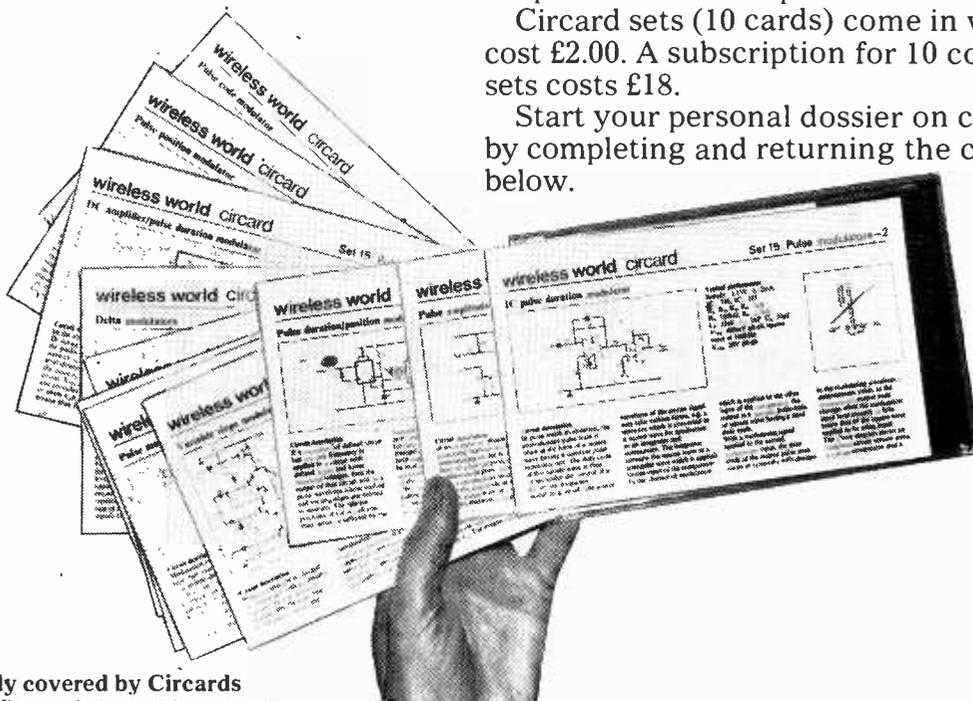Start your personal dossier on circuit design by completing and returning the coupon below.



Subjects already covered by Circards

1. Basic active filters. 2. Switching circuits comparators and schmitts.
3. Waveform generators. 4. AC measurements.
5. Audio circuits: preamplifiers, mixers, filters and tone controls.
6. Constant current circuits. 7. Power amplifiers.
8. Astables. 9. Opto-electronics.
10. Micropower circuits. 11. Basic logic gates.
12. Wideband amplifiers. 13. Alarm circuits.
14. Digital counters. 15. Pulse modulators.
16. Current differencing amplifiers — signal processing.
17. Current differencing amplifiers — generation.
18. Current differencing amplifiers — measurement and detection.
19. Monostable circuits. 20. Transistor pairs.
21. Voltage to frequency converters.
22. Amplitude modulators. 23. Reference circuits.
24. Voltage regulators
25. RC oscillators — I. 26. RC oscillators — II.
27. Linear C.M.O.S.—I.
28. Linear C.M.O.S.—II.
29. Analogue multipliers
30. Non-linear functions

To: General Sales Dept., IPC Business Press Ltd., Room 11 Dorset House, Stamford Street, London SE1 9LU

Please send me set no(s) @ £2.00 each *
 @ £18.00 *


I wish to subscribe, starting with no

I enclose cheque/money order for £
*Tick as required/Cheques to be made payable to IPC Business Press Ltd.


Name

Address

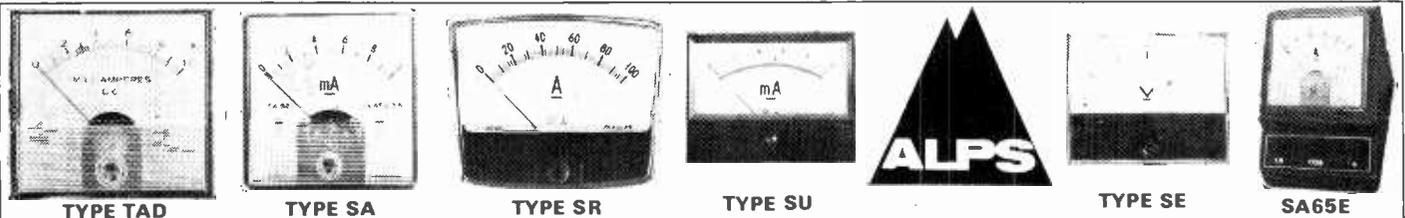Company registered in England. Registered address, Dorset House Stamford Street, SE1 9LU, England. Registered Number 677128



ALPS INSTRUMENT CO. PANEL METERS are available in production quantities at extremely competitive prices. The meters are of high quality and attractive appearance. **FOR YOUR NEW INSTRUMENTS SPECIFY ALPS METERS, PROTOTYPES AT SHORT NOTICE**. Our range includes 240° in instruments and TRUE VU METERS. Personalised Scales and Special movements manufactured to customers' requirements. For one off prices see the May WW

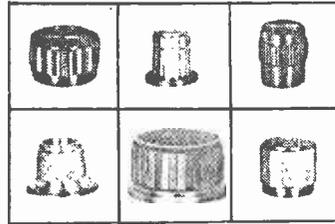


High quality competitively priced Knobs in production quantities only. Min. order 1000 Pcs of any one of 266 types.

NDI MOTORS

We can now offer a range of Mini and Micro Motors with or without gear heads for AC and DC operation.

MOTORIZED ZOOM LENSES-FOR TV & CCTV USE

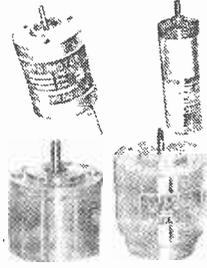DC pulse driven Turntable Units of especially high performance.



ENVIRONMENTAL TEST EQUIPMENT
A Standard Range offering the following facilities:

- High temperatures to 500° C
- Low temperatures to -75° C
- Humidity Cycling
- Thermal Shock
- Vibration
- Pressure Cycling
- Sand and Dust exposure
- Corrosive Gas exposure
- Explosion Test



UNIVERSAL AVOMETERS. Ranges DC Volts 2.5 10 50 100 500 1000 (10K Ω /V) DC current 1mA 2.5mA 10mA 50mA 100mA 500mA 1A AC Volts 10 100 1000 (1K Ω /V) Resistance 100K Ω (mid scale 1K) 1M (m s 10K), 10M (m s 100K) Fitted as usual with AVO reverse movement button and cut-out. £29.50 (inc P&P & VAT) (Good condition with test certificate all normal ranges)

METAL OXIDE RESISTORS. TR4 or MR4 tol as available £3.70 per 100 TR5 or MR5 tol as available £2.50 per 100. Most standard vols in stock. TR6 & TR8 also in stock.

COWL GILL MOTORS. Used but good condition £19.50 ea (inc P&P & VAT)

DESSYN SYSTEMS. 24v Transmitters and receivers in aircraft type instruments in stock £6.50 per pair (inc P&P & VAT)



LEMANIA AIRCREW CHRONOGRAPHS

Stainless steel case with screw back luminous hands and markings. One-fifth sec. sweep hand by press to start stop and return to zero button. 15-jewel movement. Many of these watches are as new but all have been completely overhauled and checked for accuracy. Fitted strap. White face £18.80. Black face £19.75 inc P&P

GS WATCHES


All with brushed stainless steel case with screw back and black faces. Manufactured by TIMOR ETERNA, LEMANIA, VERTEX RECORD, CYMA etc. to a standard specification. Completely overhauled. Fitted strap £9.05 (inc P&P) We also have limited quantities of these watches by BUREN, HAMILTON and IWC at £15.30 inc P&P. SMITH'S GS watch with sweep second hand £9.25 inc P&P & VAT. All watches available for inspection against remittance.



LEMANIA STOPWATCHES

Fitted with one red and one black sweep hands independently controlled enabling elapsed periods forming part of the main period to be measured separately without stopping the measurement of the main time period. Many as new. Cleaned and checked. £15 inc P&P & VAT. 1/10 SEC. STOPWATCHES. Overhauled £6.50. 1/100 SEC. STOPWATCHES. 0.6 sec £8.50 (inc P&P & VAT)

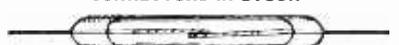OVER 300,000 RF AND MULTIWAY CONNECTORS IN STOCK



REED SWITCH INSERTS

Overall length 1.85in (Body length 1.1in) Diameter 0.14in. to switch up to 500mA or 250VDC. Gold clad contacts 74p per doz. £4.15 per 100 £29.65 per 1,000. All carriage paid U.K. Operating Coils for 12v supply to accept up to four standard reeds £2.50 per doz. £12.60 per 100. All carriage paid U.K. Heavy duty type. (Body length 2in) Diameter 0.22in. to switch up to 1A at up to 250VAC. Gold clad contacts £1.45 per doz. £6.95 per 100 £52.00 per 1,000. Changeover Heavy Duty type £2.80 per doz. All carriage paid U.K. Magnets for HD reeds £1.50 per doz. A few coils available for HD reeds

SPECIALIST STOCKISTS OF SERVOMOTORS, SYNCHROS, TEST EQUIPMENT, METERS AND CONNECTORS
Servo and Electronic Sales Ltd
Established 1953
24 HIGH ST., LYDD, KENT TN29 9AJ. Tel. Lydd 20252 (STD 0679) VAT No. 201-1296-23. TELEX 965265

RE-EQUIPPING?

When replacing your obsolete or BER multimeters, whether for

- RESEARCH LABORATORY
- UNIVERSITY
- SCHOOL OR COLLEGE
- SERVICE FACILITY
- HOSPITAL OR
- HAM SHACK

YX-360TR

Comparable with high grade meters in performance. Universally accepted as a most versatile standard tester and used extensively by electrical and radio engineers. Accurately checks transistor circuits on the low DC voltage ranges for their high internal resistance. Apart from its function as a wide range circuit tester, the SANWA model YX-360TR also serves as a simplified semi-conductor checker. Provided with LI and LV scales, the meter tests the characteristics of practically all types by semi-conductors diodes, thermistors, etc.



Measurement ranges available:
DCV 100mV 0.5 2.5 10 50 250 1KV (20KV Ω /V) (25KV with HV Probe)
ACV 10 50 250 1KV (8K Ω /V)
OCA 50 μ A 2.5mA 25mA 0.25A (250mV 100mV for 50 μ A)
 Ω Range x1, x10, x1K, x10K Maximum 2K, 20K, 20M, 20M Mid-scale 20 200 20K, 200K
dB -10 ~ +22 (for 10V AC)
hFE 0 - 1000
ICEO 0 - 150 μ A (x1K Ω) 0 - 15mA (x10 Ω) 0 - 150mA (x1 Ω)
Accuracy:
-3% f.s.d. for DC ranges +4% f.s.d. for AC ranges +3% of scale length for Ω ranges +3% of scale length for hFE +5% of scale length for ICEO
Meter £18.07. Meter with case £24.36
Size and weight: 100 x 150 x 57mm and 420g

K.30. THD

The Model K.30 THD has thermal scales provided which directly read temperature. Along with a thermometer probe attached, the meter checks temperature of from -50 C up to 200 C. 1 The midget bead thermistor is used as its thermal element accelerates temperatures response, and time lag is minimized compared with conventional thermometers. 2 By simply replacing the probe with usual test leads, the meter performs as a circuit tester. 3 As a circuit tester, the 18-position rotary system range selector switch and individual jacks cover practically all measurement requirements. 4 The collapsible stand angles the meter to facilitate use of the meter.



Technical Data
DC volts 0.25 - 1000V in 6 ranges (10K Ω /V)
AC volts 10 - 100V in 5 ranges (5K Ω /V)
DC milliamperes 0.25 - 250mA in 4 ranges
DC ohms R x 1 - R x 1000 in 4 ranges (min 2 Ω & max 10mg Ω)
Decibels -20 ~ +62 db
Temperature -50 C - 100 C & 0 - 200 C - 50 - 200 F & 30 - 400 F
Accuracy: DC \pm 3% AC \pm 4%
Size: 144 x 96 x 45mm Weight: 590g
Meter £25.17. Meter available with case £31.48.

FOLLOW THE COURSE MANY THOUSANDS IN BRITAIN HAVE ALREADY TAKEN AND ORDER

SUPER QUALITY **sanwa** MULTITESTERS
FROM QUALITY ELECTRONICS LTD.

Full catalogue and prices on request

sanwa
electronic test instruments

are manufactured by one of the oldest and most respected companies in Japan and supplied in the United Kingdom and Eire by Quality Electronics Ltd.

FULL SERVICING AND SPARES SERVICE NOW IN OPERATION AT LYDD, KENT

Published prices include P&P & VAT

QUANTITY DISCOUNTS AVAILABLE TO TRADE, PROFESSIONAL AND OEM USERS! For details contact: Ann Reynolds
QUALITY ELECTRONICS LTD.
Established 1956

24 High Street, Lydd, Kent TN29 9AJ. Tel. Lydd (0679) 20252 (opposite the Guildhall) Telex 965265 (A/B Servolydd)



N-401
The N-401 MULTITESTER has two outstanding advantages. Firstly a taut band meter movement of 5 μ A is introduced in sensitivity it is close to that of a galvanometer. Secondly an original automatic cut-out device provides exceptional protection against overload.

SPECIFICATIONS:
Range Available
DCV (1) 0.16 0.4 1.6 4 8 16 40 160 400 800 1.6kV Input impedance 200k Ω /V for 40V & below 160k Ω /V for 160V 40M Ω /V for 1.6kV 20M Ω /V for 400V & 800V
DCA (1) 8 μ A 40 μ A 400 μ A 1.6mA 4mA 16mA 40mA 160mA 1.6A 16A Voltage drop 400mV (500mV for 160mA)
ACV 4V 8V 16V 40V 160V 400V 1.6kV Input impedance 5k Ω /V for 16V & above at 50Hz
ACA 1.6A 16A Voltage drop 400mV
 Ω Range x1 x10 x100 x1k x10k Maximum 5k Ω 50k Ω 500k Ω 5 50m Ω
Accuracy: Within \pm 2% f.s.d. for DC ranges
Within \pm 3% f.s.d. for AC ranges
Within \pm 2% of scale length for Ω ranges
Frequency error: Within \pm 1db - 50Hz ~ 250kHz (4V & 8V AC) 50Hz ~ 5kHz (other ranges)
Size and Weight: 252 x 191 x 107mm & 1.95 Kg
Meter £42.97. (C)

SP-10D


A small pocket instrument of robust construction with meter movement protection rugged shockproof plastic rear case low ohms range minimum 0.2 Ω 20 Ω midscale



SPECIFICATIONS:
Measurement ranges:
DCV 0.25 10 50 250 500 1000 (4k Ω /V)
DCmA 0.25 25 500 (750mV drop)
ACV 10 50 250 500 1000 (4k Ω /V)
 Ω Range x1, x10, x1K, x10K
Mid-scale - 20 200 10k
Maximum - 500 5k 1M
Battery - 1.5V x 1
dB -20 - +22 +20 - +36
hFE 0 1 - 50
f 0.0001 - 0.02 0.01 - 0.3
Using external power

Accuracy:
Within \pm 2.5% f.s.d. for DCV & DCmA
Within \pm 3% f.s.d. for ACV & dB
Within \pm 3% of arc for Ω
Size and Weight: 140H x 95W x 44D mm 310g
Meter £16.15 (A)
Meter with case £21.87

TTLs by TEXAS 7400 13p 7485 120p 7400 20p 7486 30p 7401 14p 7489 270p 7402 14p 7490 40p 7403 16p 7491 75p 7404 16p 7492 45p 74H04 22p 7493 40p 7405 16p 7494 75p 7406 38p 7495 65p 7407 36p 7496 78p 7408 16p 7497 270p 7409 20p 74100 108p 7410 13p 74104 45p 7411 20p 74105 45p 7411 22p 74107 30p 7412 23p 74110 40p 7413 32p 74118 84p 7414 60p 74121 30p 7416 33p 74122 46p 7417 30p 74123 68p 7420 14p 74126 70p 7421 40p 74132 70p 7422 18p 74136 75p 7423 34p 74141 65p 7425 30p 74145 70p 7427 37p 74148 160p 7428 36p 74150 125p 7430 14p 74151 72p 7432 25p 74153 85p 7437 25p 74154 150p 7438 27p 74155 76p 7440 14p 74156 76p 7441 65p 74160 99p 7442 60p 74161 99p 7443 140p 74162 99p 7444 140p 74163 99p 7445 90p 74164 120p 7446 90p 74166 126p 7447 75p 74174 120p 7448 70p 74175 85p 7450 15p 74176 120p 7451 16p 74177 100p 7453 16p 74180 100p 7454 16p 74181 298p 7460 15p 74182 82p 7470 27p 74185 135p 7472 25p 74190 144p 7473 30p 74191 144p 7474 30p 74192 120p 7475 45p 74193 120p 7476 30p 74194 108p 7480 50p 74195 75p 7481 95p 74196 100p 7482 70p 74197 100p 7483 80p 74198 198p 7484 95p 74199 180p		C-MOS I.C.s CD4000AE 16p CD4001AE 16p CD4002AE 16p CD4006AE 104p CD4007AE 16p CD4009AE 67p CD4011AE 16p CD4012AE 16p CD4013AE 55p CD4015AE 90p CD4016AE 50p CD4017AE 120p CD4018AE 175p CD4019AE 52p CD4020AE 250p CD4022AE 170p CD4023AE 19p CD4024AE 120p CD4025AE 19p CD4026AE 196p CD4027AE 75p CD4028AE 140p CD4029AE 175p CD4030AE 55p CD4042AE 137p CD4043AE 202p CD4046AE 140p CD4047AE 154p CD4049AE 63p CD4050AE 52p CD4054AE 196p CD4055AE 196p CD4056AE 135p CD4060AE 229p CD4069AE 37p CD4071AE 27p CD4072AE 27p CD4081AE 19p CD4082AE 27p CD4510AE 130p CD4511AE 200p CD4516AE 112p CD4518AE 100p CD4528AE 120p		OP. AMPS 1458 Dual Op. Amp Int. Comp 8 pin DIL 70p 301A Ext. Comp 8 pin DIL 36p 3130 COSMOS/Bi-Polar MosFet 8 pin DIL 100p 3900 Quad. Op. Amp 14 pin DIL 70p 536T Fet Op. Amp. TO-99 275p 709 Ext. Comp 8/14 pin DIL 30p 741 Int. Comp 8/14 pin DIL 22p 747 Dual 741 14 pin DIL 70p 748 Ext. Comp 8/14 pin DIL 36p 776 Programmable Op. Amp TO-5 140p		TRANSISTORS AC125 16p AC126 14p AC127 14p AC128 12p AC141 18p AC142 18p AC176 11p AC187 15p AC187K 25p AC188 14p AC188K 25p AD149 49p AD161 36p AD162 36p AF114 18p AF115 18p AF116 18p AF117 18p AF139 43p AF239 48p BC107 9p BC108 9p BC109 10p BC109C 12p BC117 22p BC147 7p BC148 7p BC149C 8p BC157 11p BC158 10p BC159 11p BC169C 12p BC177 18p BC178 17p BC179 18p BC182 10p BC183 10p BC184 11p BC187 30p BC212 11p BC213 10p BC214 14p BC278 30p BC307 18p BC371 22p BD124 90p BD131 36p BD132 40p BD136 43p BD139 43p BN930 18p BD1131 18p BN1132 18p BN1304 36p BN1306 36p BN1307 26p BN1308 28p BN1309 33p BN1310 33p BN1311 22p BN1312 10p BN1313 10p BN1314 10p BN1315 10p BN1500 10p		DIODES SIGNAL* OA47 7p OA7 15p OA81 9p OA85 15p OA90 7p OA91 7p OA95 7p OA200 8p OA202 10p IN914 4p IN916 9p IN4148 9p RECTIFIER BY100 25p BY126 12p BY127 15p IN4001 5p IN4002 5p IN4004 6p IN4005 6p IN4007 7p ZENER 2.7V to 33V* 8p 400mW 18p 1W 9p TUNNEL AEY11 70p VARICAP BB105 25p NOISE Z5J 110p BRIDGE RECTIFIERS 25A100V 20p 1A 50V 20p 1A 100V 22p 1A 200V 24p 1A 400V 25p 1A 600V 30p 2A 50V 30p 2A 100V 35p 2A 200V 40p 2A 400V 45p 4A 100V 55p 6A 200V 78p 6A 400V 84p TRIACS Amp Vols 3 400 120p 6 400 150p 6 500 180p 10 400 185p 10 500 195p 15 400 215p 15 500 250p 40430 99p 40486 99p 40669 99p DIAC BR100 30p							
MEMORIES 2602B 1024 bit RAM £2.50 2513(UC) Character Generator £8.50 2513(LC) Character Generator £8.50		OPTO-ELECTRONICS Phototransistors L.D.Rs. OCP70 30p ORP12 60p OCP71 120p ORP60 75p 2N5777 40p ORP61 75p		LEDs TIL209 Red 14p Red 16p TIL211 Green 30p Green 28p TIL32 Infrared 75p Yellow 30p		SEVEN SEGMENT DISPLAYS 3015F Minitoron 0.3 160p DL704 Com. Cathode 0.3 in 140p DL707 Com. Anode 0.3 in 140p DL747 Com. Anode 0.6 in 225p		OPTO-ISOLATORS Phototransistor: TIL 112 (IL 12) 6 pin DIL 140p Photodiator: ILCA-55 6 pin DIL 250p		DRIVERS 75491 Quad Segment Driver 14 pin DIL 78p 75492 Hex Digit Driver 14 pin DIL 90p		TELETEXT DECODER Complete Semiconductor kit for the above "WW" Project available (includes all I.C.s, Ts, etc for U.C., L.C. and P.S. unit) £61.00 inc V.A.T. and P&P Please send S.A.E. for details.			
LOW PROFILE DIL SOCKETS BY TEXAS 8 pin 13p, 14 pin 14p, 16 pin 15p, 24 pin 50p. 40 pin 75p, 28 pin 60p		VOLTA GE REGULATORS - FIXED - PLASTIC 1 Amp Positive 1 Amp Negative 5V 7805 140p 5V 7905 200p 12V 7812 140p 12V 7912 200p 15V 7815 140p 15V 7915 200p 18V 7818 140p 18V 7918 200p 24V 7824 140p 24V 7924 200p LM309K 1 Amp 5V TO3 140p		DUAL VOLTAGE REGULATOR 1468 ±15V 100mA 16 pin DIL 300p. (Adjustable by resistors from ±8V min. to ±20V max.)		VARIABLE VOLTAGE REGULATOR 723 2V to 37V 150mA 14 pin DIL 45p LM305H 4.5V to 30V 20mA TO5 120p Basic Data Sheets on Vol. Regs. at 10p each + SAE		SCR-THYRISTORS - BT106 1A/700V Stud 140p C106D 1A 50V TO5 40p 4A/400V Plastic 59p 1A100V TO5 42p *MCR101 1A400V TO5 45p 0.5A/15V TO-92 25p 1A600V TO5 70p 2N3525 3A100V Stud 49p 5A/400V TO-66 95p 3A400V Stud 75p 2N4444 7A100V TO5+HS 84p 8A/600V Plastic 185p 7A400V TO5+HS 90p *2N5060 8A 50V Plastic 130p 0.8A/30V TO-92 34p 12A400V Plastic 160p *2N5062 16A100V Plastic 160p 0.8A/100V TO-92 37p 16A400V Plastic 180p *2N5064 16A600V Plastic 220p 0.8A/200V TO-92 40p		MOSEFETS 3N128 85p 3N140 85p 3N141 85p 3N187 180p 3N202 120p 40603 58p 40673 58p		UJTs *TIS43 34p 2N2160 95p 2N2646 45p *2N4871 34p		PUJT *2N6027 48p	

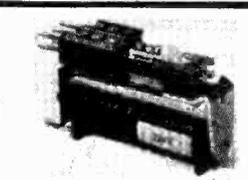

Wilkinson RELAYS

POST OFFICE TYPE 3000 AND 600 BUILT TO YOUR OWN SPECIFICATIONS AND REQUIREMENTS. THE BEST KNOWN OF ALL RELAYS WITH A LARGE VARIETY OF CONTACT ARRANGEMENTS. KNOWN THROUGHOUT THE WORLD. COMPLETE BANKS OF CONTACTS. MADE TO ORDER AND COMPONENT PARTS SUPPLIED. HIGHEST QUALITY AT COMPETITIVE PRICES WITH A QUICK DELIVERY SERVICE. QUOTATIONS BY RETURN HOME AND OVERSEAS. WE ARE SPECIALISTS IN EXPORT ORDERS.

JACK - IN AND STRIP MOUNTINGS to house BPO type 3000 Relays and associated components used in BPO 2000 and 4000 type telephone exchange equipments and industrial control systems. The mountings are drilled to accept BPO type 3000 Relays or any other type of equipment using similar drawings, supplied complete with test jacks. Prices on request.


Single and Double pole High Speed Relays available, various resistances. Uniselectors, Line Transformers, Multi-point plugs, P.O. type Bobbin resistors and complete Relay Selector Units also available at competitive prices.

HIGH SPEED COUNTERS £1.75 each
 3 1/2" x 1" 10 counts per second with 4 figures. The following D.C. voltages are available: 5 v, 12 v, 24 v, 50 v, or 110 v. Auxiliary contacts normally open. 40p extra. Five Digit Counters BPO type 150A 500 ohms 35mA operating current. £3 each.

BRIDGE MEGGERS 1,000 volts range 0-100 megohms-infinity with resistance box. £55 each.
TUNING FORKS 125 Hz for 45/50 band teleprinter speeds. £2.50 each.
MINIATURE DIGITAL INDICATOR 1/2 inch digits, illuminated by 28 volt magnet flanged lamps, weight 3 ozs reading 0 to 9 with decimal points. £2.50 each.

L. WILKINSON (CROYDON) LTD., LONGLEY HOUSE
 LONGLEY ROAD, CROYDON, CR0 3LH - Phone 01-884 0236 - Grams: WILCO CROYDON
 All prices shown are carriage paid U.K. only but subject to VAT at the standard rate.

WW-086 FOR FURTHER DETAILS

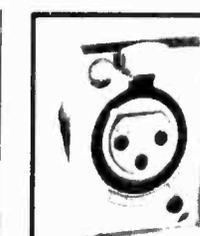

Audio Connectors

Broadcast pattern jackfields, jackcords, plugs and jacks.

Quick disconnect microphone connectors
 Amphenol (Tuchel) miniature connectors with coupling nut.

Hirschmann Banana plugs and test probes
 XLR compatible in-line attenuators and reversers.

Low cost slider faders by Ruf.


Future Film Developments Ltd.
 90 Wardour Street
 London W1V 3LE
 01-437 1892/3

WW-028 FOR FURTHER DETAILS

A.S.P.

(Dept. WW4), SIMMONDS ROAD
 WINCHEAP, CANTERBURY, KENT
 Tel: (0227) 52436

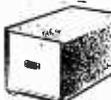CASED TRANSFORMERS
 Housed in smart resin coated steel cases with 3 core power cable and outlet socket fused primary winding. Isolation types are fitted with 3-pin outlet sockets and are available with 110 volt or 240 volt output (Please state) Auto types are fitted with 2-pin flat style sockets up to 500 VA 3-pin sockets from 750 to 3000 VA See Auto and isolation sections for prices Plugs extra



TRANSFORMERS

30 VOLTS See catalogue for full range
 PRIMARY 200/240V
 SECONDARY 12, 15, 20, 24, 30V

AMPS	Ref. No.	Price £	Post £
0.5	112	2.17	0.61

SAFETY ISOLATING See catalogue for full range
 Prim 120/240V Sec 120/240V Centre Tap with screen

VA (WATTS)	REF No	PRICE £	Plugs Cased Earth	PRICE £	Plugs Open Earth	Post £
60	149	9.46	0.98	5.02	0.72	
200	151	12.87	0.98	9.07	0.97	
250	152	14.47	0.98	10.81	1.18	

50 VOLTS See catalogue for full range
 PRIMARY 200/240V
 SECONDARY 19, 25, 33, 40, 50V

AMPS	Ref. No.	Price £	Post £
1	103	3.67	0.76
2	104	5.57	0.85

AUTO TRANSFORMERS See catalogue for full range

VA (Watts)	Ref No	PRICE £	Plugs Cased 2 & 3 pin	PRICE £	Open	Post
1500	93..	£24.37	0.95	20.13	0A	

60 VOLTS See catalogue for full range
 PRIMARY 200/240V
 SECONDARY 24, 30, 40, 48, 60V

AMPS	Ref. No.	Price £	Post £
0.5	124	2.72	0.72
1	126	4.08	0.72
2	127	5.63	0.85

MINIATURE & EQUIPMENT See catalogue for full range
 Primary 240V with Screen

VOLTS	Sec 1	Sec 2	MILLIAMPS	REF No	PRICE £	Post £
3-0-3	-	-	-	207	1.75	0.34
0-6	0-6	-	500	500	2.36	0.34
0-6	0-6	-	1000	1000	2.12	0.42
0-9-9	-	-	100	100	1.75	0.34
0-9	0-9	-	330	330	2.35	0.34

BRIDGE RECTIFIERS

ONEAMP	Price	FOURAMP	Price
50 P.I.V.	0.25	100 P.I.V.	0.60
100 P.I.V.	0.30	200 P.I.V.	0.85
200 P.I.V.	0.35	400 P.I.V.	0.80
800 P.I.V.	0.40	800 P.I.V.	1.10

TWO AMP	Price	SIX AMP	Price
50 P.I.V.	0.40	50 P.I.V.	0.70
100 P.I.V.	0.45	100 P.I.V.	0.75
200 P.I.V.	0.50	200 P.I.V.	0.80
400 P.I.V.	0.55	400 P.I.V.	0.95

Add 25% VAT on all prices

12 and 24 VOLTS PRIMARY 200-240 Volts See catalogue for full range

AMPS	24V	REF No	PRICE £	Post £
12V				
0.3	0.5	242	1.86	0.34
0.5	0.25	111	1.60	0.46
1	1.5	219	1.90	0.61
2	1	71	2.64	0.61
4	2	18	3.12	0.62
8	3	76	4.82	0.72
11	4		5.65	0.86

SPECIAL OFFER!

2 KVA ISOLATORS

Fully impregnated & screened
 2 primary windings 110V each
 2 secondary windings 115V each
 (2 matching transformers)
£29.50 plus carr. & VAT.

★ PLEASE ADD 8% VAT ON ALL TRANSFORMERS & METERS

2" AND 4" PANEL METERS

See catalogue for full range

2" SIZE: 60mm Wide x 45mm High x 40mm Deep

4" SIZE: 110mm Wide x 82mm High x 43mm Deep

VU Meters are complete with detectors. Modern wide view 25% VAT. Price £3.30
 Post 10p. Price 4" £4.10. Post 10p. Lamps 60p per set. Plus 8% VAT

NEW CATALOGUE 25p

Catronics

Remarkable Value!
WW

TELETEXT DECODER

Our kit contains all the printed circuit boards and components necessary to build the complete decoder. The power supply and video switching circuitry are normally installed within the television cabinet and the main decoding control and memory circuitry in a separate cabinet positioned on top of the television

PRICES ARE AS FOLLOWS

Set of 5 PCBs (incl. PSU & Video Switching)	£16.00+VAT = £18.00
Component Kit (incl. PCBs)	£96.02+VAT = £104.10
Add-on Unit for Lower Case: PCB only	£2.00+VAT = £2.25
Component Kit (incl. PCB)	£12.65+VAT = £13.75
Cabinet	£12.00+VAT = £13.50
READY BUILT AND TESTED	£148.00+VAT = £162.55
for Lower Case add --	£15.00+VAT = £16.40

Post & Packing PCBs are post free but add £1 for component kit and 50p for cabinet
COMPONENTS ALSO AVAILABLE SEPARATELY e.g 2513, £8.50; 2602-B, £2.50; + 8% + 20p P & P - SAE for full price list

VHF DIGITAL FREQUENCY METER

New 200MHz, 7 digit, D.F.M. for direct readings up to the mobile radio VHF 'High Band'. Will operate on mains or 12V supply, making it ideal for use with mobile equipment.

Price only £121 + £1 carriage + VAT (currently 8%).

Write for illustrated leaflet

Catronics

CATRONICS LTD. (Dept. 627)
 39 Pound Street,
 Carshalton, Surrey
 Tel: 01-669 6700

WW-627 FOR FURTHER DETAILS

ELECTROTIME

SPECIALISTS IN ELECTRONIC TIMEKEEPING

ELECTRONIC DIGITAL ALARM CLOCK MODEL EC3



- ★ LARGE 4 DIGIT DISPLAY
- ★ AM/PM INDICATOR
- ★ FLASHING SECONDS INDICATOR
- ★ 5 MINUTE REPEATING SNOOZE ALARM

- ★ 24 HOUR ALARM
- ★ BRIGHTNESS CONTROL
- ★ ATTRACTIVE WHITE CASE

COMPLETE BUILT CLOCK PRICE **£14** inc VAT

THE "MISTRAL" I DIGITAL CLOCK



- ★ PLEASANT GREEN DISPLAY
- ★ 12/24 HOUR READOUT
- ★ FULLY ELECTRONIC

- ★ PULSATING COLON
- ★ PUSH BUTTON SETTING
- ★ BUILDING TIME 1 HOUR

COMPLETE KIT PRICE **£11.07** inc VAT
 BUILT CLOCK PRICE **£14.95**

LCD MODEL TLC4

CONTINUOUS READOUT UTILISING LIQUID CRYSTAL DISPLAY

WITH BACKLIGHT FOR NIGHT READING

FEATURES—

- ★ HOURS
- ★ MINUTES
- ★ SECONDS
- ★ DATE



£39.95

GOLD **£41.50** inc VAT

LED MODEL TLE5

FEATURES

- ★ HOURS
- ★ MINUTES
- ★ SECONDS
- ★ DATE
- ★ DAY OF WEEK

£29.50

inc VAT

GOLD OR RHODIUM PLATED



We are proud to announce the opening of our new showroom in which you will find one of the Largest Ranges of Digital Electronic Clocks and Watches available in the UK so why not call in and see us?

ELECTROTIME, DEPT. 3/7, 11 SHEPLEY'S YARD
 CHESTERFIELD, DERBYSHIRE. TEL. (0246) 35804


PLEASE SUPPLY
 I ENCLOSE CHEQUE/POSTAL ORDER

NAME _____

ADDRESS _____

www.americanradiohistory.com

It's the cat's whiskers!

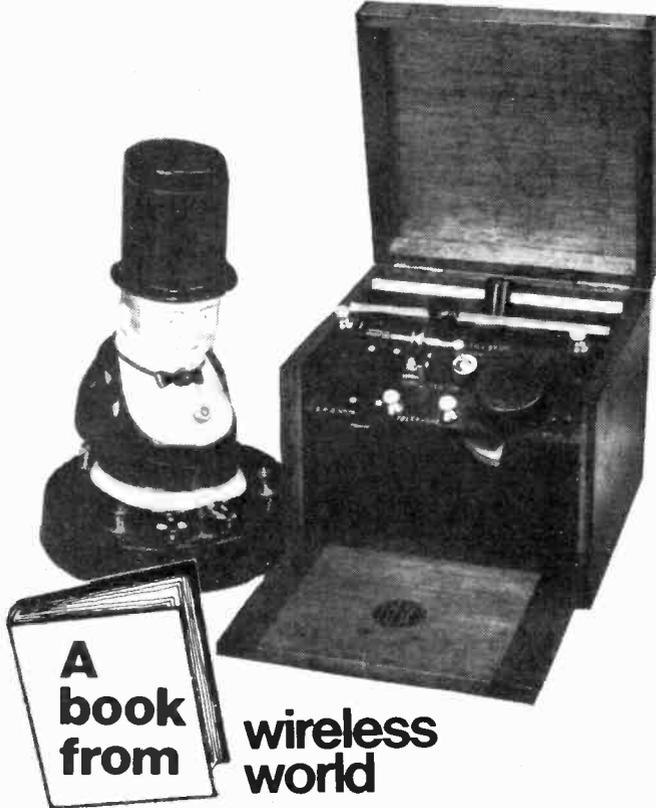

A fascinating excursion into the past. The author has unearthed some 400 trade names from the crystal set days, along with nearly 200 manufacturers—giving the name of the set, technical description and original price. He also reviews the first days of broadcasting and looks at the difficulties experienced by crystal set users. Concise information and over 40 illustrations make this book a valuable work of reference as well as a rare piece of nostalgia for collectors.

VINTAGE CRYSTAL SETS 1922~1927

£2.50 from bookshops or £2.80 inclusive direct from Wireless World, Room 11, General Sales Dept., IPC Business Press Ltd., Dorset House, Stamford Street, London SE1 9LU.

LEEDS ELECTRONICS EXHIBITION

**29, 30 June
and 1 July
1976**

Catalogues and Tickets for Seminars
available from:

University of Leeds Department of
Electrical and Electronic Engineering

STEREO IC DECODER

HIGH PERFORMANCE PHASE LOCKED LOOP
(as in 'W.W.' July '72)

**MOTOROLA MC1310P EX STOCK
DELIVERY SPECIFICATION**

Separation: 40dB 50Hz-15kHz
I/P level: 560mV rms
Input impedance: 50kΩ
Distortion: 0.3%
O/P level: 485mV rms per channel
Power requirements: 8-14V at 16mA
Will drive up to 75mA stereo 'on' lamp or LED.

KIT COMPRISES FIBREGLASS PCB
(Roller tinned), Resistors, I.C., Capacitors,
Preset Potm & Comprehensive Instructions

LIGHT EMITTING DIODE
Suitable as stereo 'on' indicator for above

**ONLY
£3.98
RED
GREEN** **WHY PAY
MORE?
post free
29p
59p**

MC1310P only £2.15 plus p.p. 10p

NOTE


As the supplier of the first MC1310P decoder kit, of which we have sold literally thousands, our customers can benefit from our wide experience.

V.A.T.

Please add V.A.T. to all prices

FI-COMP ELECTRONICS
PORTWOOD INDUSTRIAL ESTATE, CHURCH GRESLEY
BURTON-ON-TRENT, STAFFS. DE11 9PT

N.A.B'C' CARTRIDGE TAPE TRANSPORTS

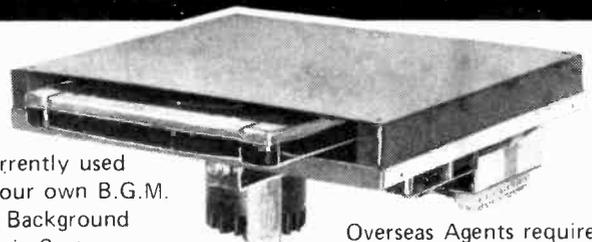

Currently used
in our own B.G.M.
50 Background
Music System

Overseas Agents required

For further information write or telephone:

FITCH TAPE MECHANISMS

7a Balham Grove London SW12 01-673 1362

WW — 085 FOR FURTHER DETAILS

SERVICE TRADING CO

RELAYS

SIEMENS PLESSEY, etc. MINIATURE RELAYS			
1	2	3	4
52	4-8	2 c/o	75p
58	5-9	6 c/o	85p
185	8-12	6 M	75p
230	9-18	2 c/o HD	75p
430	9-24	2 c/o	75p
430	15-24	4 c/o	75p
600	10-20	6M	85p
1	700	12-24	2 c/o r/p
700	16-24	4 c/o	85p
1250	18-36	2 c/o	75p
2500	36-45	6 M	75p
2500	31-43	2 c/o HD	75p
15k	85-110	6 M	75p
5800	33-72	2 c/o	75p

(1) Coil ohms; (2) Working d.c. volts; (3) Contacts; (4) Price HD=Heavy Duty. All Post Paid. (*Including Base)

OPEN TYPE RELAYS
6 VOLT D.C. 1 make con 45p. Post 15p
9 VOLT D.C. RELAY
 3 c/o 5 amp contacts 70 ohm coil 85p. Post 15p
9/12 VOLT D.C. RELAY
 3 c/o 5 amp contacts 120 ohm available as single hole fixing or P.C. fixing. state type required 85p. Post 15p

24 VOLT D.C.
 2 HD c/o 700 ohm coil 85p. Post 15p
 4 c/o 300 ohm coil 95p. Post 15p
100 VOLT AC 2 c/o 75p 3 c/o 85p. Post 15p

ENCLOSED TYPE RELAYS
6 VOLT DC 3 c/o 85p. Post 15p
24V DC 3 c/o 85p. Post 20p Base 15p
24 VOLT A.C. Mfg IIT 3hd c/o contacts 65p. Post 20p Base 15p extra
55 VOLT A.C.
 3 heavy duty c/o contacts Price 65p. Post 20p Base 15p

230 VOLT A.C. RELAY
 240V A.C. heavy duty 3 c/o contacts
 Price 85p. Post 20p. Uctal base 15p extra
220/240 VOLT AC RELAY
 3 c/o 5 amp cont Sealed Mfg ISKRA £1.35. Post 20p. Base 15p extra

ARROW 230/240V AC 2 c/o 15 amp contacts
 Amp connectors £1.10. Post 20p
CLARE-ELLIOT Type RP 7641 G8
 Miniature relay 675 ohm coil 24 volt D.C. 2 c/o 80p P.P

MANY OTHERS FROM STOCK, PHONE FOR DETAILS

LATCHING RELAY
 Twin latching relay flip-flop 2c/o each relay
 Mains contacts 115 volts A.C. or 50 volt D.C.
 operation or 740 volts A.C. with 2.5K resistor. 85p.
 Post 20p

PRECISION CENTRIGUAL BLOWERS
 Mfg by Simms Industries Miniature model Series
 SF 200 Size 95mm x 82mm x 82mm Aperture
 38mm x 31mm 12 c/f m. £2.75. Post 50p
 Mfg by Airflow Developments Ltd
 Precision made continuously rated smooth running 230 240v A.C.
 motor 80c f.m. As illustrated but with round aperture. £6.50. Post 75p

Mfg by Woods
 Extremely powerful 220 250v A.C. 0.3 amp 2 700 r.p.m. continuously
 rated Capacitor start Cast construction Aperture 66mm x 50mm O.A.
 200mm £12.00. Post 1.00
 Mfg by Parvalux Type SD38B 220v A.C. 50 Hz 0.55 amp Continuously
 rated 2800rpm 120c/m Brand new Fraction of makers price £10.00.
 Post 1.00

230 VOLT FAN ASSEMBLY
 Continuously rated, removable aluminium
 blades Price £1.25. Post 50p
VAT 12 1/2 %

C/O MICRO SWITCH
 VERY SPECIAL OFFER Mfg by CEM 3 amp
 250 volt 10 amp 125 volt 50 for £3. Post 36
 100 for £5. Post 50p 1 000 for £45. Post paid
 DOUBLE POLE C/O or 2 make, 2 break micro switch 10 amp 250 v A.C.
 With detachable roller assembly 10 for £2.50. Post 50p. (Min. order 10)

MINIATURE ROLLER
 M. switch OMRON type V15 F12 1C 10 for £2.00 post
 50p (Min. order 10)

230-250 VOLT A.C. SOLENOID
 Similar in appearance to illustration
 Approximately 1 1/2 lb. pull. Size of feet 1 1/2"
 1 1/4" Price £1.00. Post 25p

SOLENOID HEAVY DUTY MODEL
 230 250v A.C. Apprx 10lb pull 4" long x 2 1/2" wide x 3"
 high £2.50. Post 50p

24 VOLT DC SOLENOIDS
 UNIT containing 1 heavy duty solenoid approx 25 lb. pull
 at 1 in. travel. 2 solenoids of approx. 1 lb. pull at 1 in. travel
 6 solenoids of approx. 4 oz. pull at 1 in. travel. Plus 1 24V D.C.
 heavy duty 1 make relay Price £2.50. Post 1.00
ABSOLUTE BARGAIN.

240 V.A.C. SOLENOID OPERATED FLUID VALVE
 Rated 1 p.s.i. will handle up to 7 p.s.i. Fitted
 brass body stainless steel cone and spring in
 d.s.p. metal cabinet. Precision made British mfg.
 PRICE £2.25 Post 50p. N/W original packing

600 WATT DIMMER SWITCH
 Easily fitted Fully guaranteed by makers Will
 control up to 600 watts of all lighting except floor
 escents at mains voltage. Complete with simple
 instructions £3.15. Post 25p
 1000 watt model £4.50 Post 25p
 2000 watt model 9.00 Post 40p

VARIABLE VOLTAGE TRANSFORMERS

Carriage extra INPUT 230 v. A.C. 50/60
 OUTPUT VARIABLE 0/260v. A.C.
BRAND NEW. All types.
 200W (1 Amp) £10.00
 0.5 KVA (Max. 2 1/2 Amp) £11.50
 1 KVA (Max. 5 Amp) £16.50
 2 KVA (Max. 10 Amp) £30.00
 3 KVA (Max. 15 Amp) £33.00
 4 KVA (Max. 20 Amp) £60.00
 (max. 37.5 Amp) £102.50

LT TRANSFORMERS
 0.6 12 volt @ 10 amp £6.15 Post 70p
 0.10 17 18 volt @ 10 amp. £8.70 Post 1.00
 0.6 12 volt @ 20 amp £9.90 Post 1.00
 0.12 24 volt @ 10 amp £9.90 Post 1.00
 0.4 6 24 32 volt @ 12 amp £10.30 Post 1.00
 0.6 12 17 18 20 volt @ 20 amp £11.80 Post 1.00
 Other types to order at short notice. Phone your enquiries

AUTO TRANSFORMERS
 Step up step down 0.115 200 220 240 volts
 At 75 watt £3.00 Post 40p 150 watt £4.30 Post 50p 300
 watt £6.20. Post 60p 500 watt £9.20 Post 75p 1000 watt
 £13.50 Post 90p

RING TRANSFORMERS
 Functional Versatile Educational
 These multi-purpose Auto Transformers with large Centre
 aperture can be used as a Double wound current
 Transformer Auto Transformer HT or LT Transformer
 by simply hand winding the required number of turns
 through the Centre opening
 E.g. Using the RT 100V A Model the output could be wound to give 8V
 @ 12 1/2 Amp 4V @ 25 Amp or 2V @ 50 Amp etc Price
 RT 100VA 3 1/8 turns per volt £5.00. Post 75p
 RT 2KVA 1 1/5 turns per volt £21.00. Post 1.50
 RT 3KVA 1 1/5 turns per volt £28.00. Post 1.50

STROBE! STROBE! STROBE!

*** HY-LIGHT STROBE Mk. IV ***
 Latest type Xenon white light tube. Solid state timing and triggering
 circuit. 230/240 volt A.C. operation. Speed adjustable 1-20 f.p.s.
 Designed for large rooms, halls, etc. Light output greater than many
 (so called 4 Joule) strobes. Price £15.40. Post 75p
 * Specially designed case and reflector for Hy Light £8.25. Post 1.00
*** XENON FLASH GUN TUBES ***
 Range of Xenon tubes available from
 stock S.A.E. for full details
*** ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES ***
 4ft. 40 watt £6.00 (callers only), 2ft. 20 watt £4.60. Post 60p
 (5p. per inch over 4ft. lengths) MINI 12in. 8 watt £1.75. Post 25p
 75p. 9in. 6 watt £1.40. Post 25p. Complete ballast unit and
 holders for either 9" or 12" tube £1.70. Post 30p (9" x 12"
 measures approx.)
*** * * * ***

SQUAD LIGHT

A new conception in light control. Four channels each
 capable of handling 750 watts of spotlights floodlights or
 dozens of small mains lamps. Seven programs all speed controlled
 plus flash modulation, effectively giving 14 different displays.
 Makes sound-to-light obsolete. Completely electrically and
 mechanically noise free. Price only £58.00
 Post 75p S.A.E. (Footscap) for further details

WHY PAY MORE?!

MULTI RANGE METER A.C. volts 2.5-500 0 C
 volts 2.5-500 (Sensitivity 20000! VDC & AC) DC
 current 0.1 10 100 mA Ohms range Sturdy
 compact moving coil instrument with 21 ranges
 dimensions 120x80x44mm. Weight 0.32 kg
 SERVICE TRADING CO Price £5.00. Incl leads
 and battery. Post 50p (Total price incl VAT &
 Post £5.94)

TRIAC
 Raytheon Tag symmetrical Triac. Type TAG 250 500v 10 amp 500
 p.w. Glass passivated plastic triac. Swiss precision product for long term
 reliability £1.00. Post 10p (inclusive of Date and application sheet)
 Suitable Duct 18p.

INSULATED TERMINALS
 Incorporating 4mm socket
 Available in black red white yellow blue
 and green 18p each Post Paid

INSULATION TESTERS (NEW)
 Test to I.E.E. Spec. Rugged metal con-
 struction, suitable for bench or field
 work constant speed clutch. Size L. 8 in.
 W. 4 in. H. 6 in. weight 6 lb.
 500 VOLTS 500 megohms £40.00
 Post 80p
 1000 VOLTS 1000 megohms £46.00
 Post 80p

VAT VAT AT 8%
 MUST BE ADDED
 TO ALL ORDERS
 FOR THE TOTAL VALUE OF GOODS INCLUDING
 POSTAGE UNLESS OTHERWISE STATED

GEARED MOTORS

100 R.P.M. 115 lbs. ins.!!
 115 lb ins 110 volt 50Hz 2.8 amp single phase split
 capacitor motor Immense power. Continuously rated
 Totally enclosed Fan cooled In-line gearbox Length
 250mm Dia 135mm Spindle Dia 15.5mm Length
 145mm ex-equipment tested £12.00. Post 1.50
 Suitable transformer 230/240 volt £8.00. Post 75p

15 R.P.M.
 Type SD48 15 r.p.m. 80 lb ins Input 100 120 volt A.C. Length incl
 gearbox 270mm Height 135mm Width 150mm Shaft drive 16mm
 Weight 8.5 Kilos BRAND NEW Price £10.00. carr £1.00
 Suitable transformer for use on 220/240 volt A.C. £3.85. Post 50p

60 R.P.M. REVERSIBLE
 220/240 volt A.C. Small powerful continuously rated motor Mfg
 BERGER (Germany) Size 80mm x 65mm x 65mm Spindle dia
 6mm Length 155mm Weight 725 grams £6.50. Post 50p

BODINE TYPE N.C.I. GEARED MOTOR
 (Type 1) 71 r.p.m. torque 10 lb in
 Reversible 1 70th h.p. cycle 38 amp
 (Type 2) 28 r.p.m. torque 20 lb in
 Reversible 1 80th h.p. cycle 28 amp. The above two
 precision made U.S.A. motors are offered in as new
 condition. Input voltage of motor 115v A.C. Supplied com-
 plete with transformer for 230/240v A.C. input.
 Price either type £6.25. Post 75p or less transformer £3.75. Post
 65p

(Type 3) 71 r.p.m. 230 Volt A.C.
 Continuously rated. Non reversible £6.50 Post 75p

6/9 VOLT D.C. GOVERNED
 40mm x 40mm Spindle 10mm Dia 2 mm £1.00 Post Paid Two for
 £1.65 Post Paid

24 R.P.M.
 230 volt A.C. Continuously rated Mfg Mylex Ex-equip. Fully tested
 £3.85 Post 75p

1 R.P.M. 230/240 VOLT A.C. SYNCHRONOUS!!
 Ex-equipment. Thoroughly tested and guaranteed. ONLY £1.50 Post
 20p

20 r.p.m. GEARED MOTOR
 230/240 volt 20 r.p.m. motor £1.00. Post 20p

REVERSIBLE MOTOR 230V A.C.
 General Electric 230v A.C. 1600 r.p.m. 0.25 amp. Complete with
 anti-vibration mounting bracket and capacitor. O. A size 110mm x 95mm
 Spindle 5 16" dia 20mm long. Ex-equipment tested £3.00. Post 50p

METERS NEW 90mm Diameter
 Type: 65CS DC M/C 2.5 10 20 50 amp £2.75. Post 20p 100
 amp £3.25. Post 20p
 Type: 6272 A.C. M/I 1 20 50 amp £2.50 Post 20p 0.300 Volt
 A.C. M/I £2.75 and 300 Volt A.C. R/M/C £3.00 Post 30p

ROTARY VACUUM AIR COMPRESSOR AND PUMP
 Carbon vane oilless 100 115V A.C. 1 1/2
 h.p. motor 50 60 cycle 2875 3450 r.p.m.
 20" vacuum 1.25 c.f.m. 10 p.s.i. (approx
 figures) New unused surplus stock with elect
 connection data. Fraction of maker's price
 £12.00. Post 1.00 Suitable transformer
 £3.50. Post 50p

TIME SWITCH
 Horstmann Type V Mk II Time Switch 200/250 volt
 A.C. Two on two off every 24 hours. at any manually
 preset time. 30 amp contacts. 36-hour spring reserve
 in case of power failure. Day omitting device. Fitted in
 heavy high impact case with glass observation
 window. Built to highest Electrically Board spec
 individually tested Price £7.75. Post 50p (Total inc
 VAT £8.91)

A.C. MAINS TIMER UNIT
 Based on an electric clock with 25 amp
 single pole switch which can be preset for
 any period up to 12 hrs. ahead to switch
 on for any length of time from 10 mins to 6
 hrs. then switch off. An additional 60 min. audible timer is also
 incorporated. Ideal for Tape Recorders. Lights. Electric Blankets.
 etc. Attractive satin copper finish. Size 135 mm x 130 mm x
 60 mm. Price £2.25. Post 30p. (Total inc. VAT & Post £2.87.)

POWER RHEOSTATS
 New ceramic construction, vitreous
 enamel embedded winding, heavy duty
 brush assembly, continuously rated.
 25 WATT 10 25 100 150 250 500 1k 1.5k ohms
 £1.70. Post 20p 50 WATT 1 5 10 25 50 100 500 1k ohm
 £2.10. Post 25p 250 25p
 1 10 25 50/100/250/500/1k/1.5k/2.5k/5k ohm. £3.30.
 Post 35p
 Black Silver Skirted knob calibrated in Nos. 1-9. 1 1/2
 in dia brass bush. Ideal for above Rheostats, 22p ea.

PROGRAMME TIMERS
 230 Volt A.C. Operation. 15 or 20 r.p.m.
 Each cam operates a C.O. micro switch. Ideal
 for lighting effects displays etc. Ex equip
 tested. Similar to illustration
 6 CAM made 15.00
 11 CAM made 6.50
 11 CAM made 7.50
 Post 50p. Also available for 50 volt AC operation. Prices available

ALL MAIL ORDERS, ALSO CALLERS AT: **SERVICE TRADING CO.** PERSONAL CALLERS ONLY

57 BRIDGMAN ROAD, CHISWICK,
 LONDON, W4 5BB. Phone: 01-995 1560
 Closed Saturdays.

SHOWROOMS NOW OPEN
 AMPLE PARKING


9 LITTLE NEWPORT STREET,
 LONDON, WC2H 7JJ.
 Tel.: 01-437 0576

ELECTRONIC BROKERS

Electronic Brokers Ltd. are one of the leading electronic instrumentation companies in the UK, providing a full range of services to Universities, Industry, Colleges and Governments both at home and overseas.

We have the largest stocks of secondhand test equipment in Europe as well

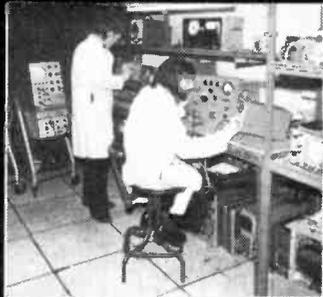as a selected range of new products. These are on display at our London showrooms where customers can examine the equipment of their choice and see it working.



Electronic Brokers Ltd. have fully equipped workshops on the premises to test and report on the majority of equipment we sell.

TELEPHONE TEST EQUIPMENT

- SIEMENS**
 Level Meter 3D 332 0.3-1200KHz £250
 Level Meter 3D 335 10KHz-17MHz £300
 Level Oscillator 3W29 0.3-1200KHz £250
 Level Oscillator 3W513 £300
 Carrier Frequency Sweep measuring set up, Type Rel 32 M710 (to 15MHz) Comprising Level Oscillator Rel 3W 513 Level Meter Rel 3D 335 Sweep Attachment Rel 3W 933 Tracing Receiver Rel 3D 346 Used for measurement on carrier telephone equipment for coaxial systems (e.g. V960, V1200 & V2700) and wideband radio relay systems (e.g. FM600, FM900 FM1800). P.O.A.
- WANDEL & GÖLTERMAN**
 Level Transmitter TFP5 42 10KHz-14MHz £375
 Level Meter TFM 43 10KHz-14MHz £375
 Wandel & Gölterman Y2M 2 Distortion measuring set for phase and amplitude mod. For multichannel FM Radio Systems up to 12MHz base bands £350

SWEEP GENERATORS

- HEWLETT PACKARD**
 Sweep Oscillator 692D 2.4GHz Sweeps from start to stop freq. SPECIAL OFFER £300
 Sweep Oscillator 693D 4-8GHz. SPECIAL OFFER £325
 Sweep Oscillator 693D 4-8GHz £325
- JERROLD**
 Sweep Signal Generator 900B Central Freqs 500KHz-1200MHz Sweep widths narrow as 10KHz to 400MHz wide 50ohms o/p impedance £400
 M.E.S.L.
 Swept Signal Source MH883 7-12 5GHz £480.00

FUTURE ADDITIONS

The following equipment is becoming available to us in the near future, should you require prices etc., please contact us and then we will reserve your specific requirements.

- HEWLETT PACKARD**
 334A Distortion Analyser
 52461 Electronic Counter
 826A Signal Generator
 8552B Spectrum Analyser - IF Section
 8618A Signal Generator
 141T Spect. Anal. Display
 211A Crystal Monitored Sig. Gen.
 355D Attenuator
 6820B Meter Calibrator
 6328B Univ. Timer/Counter/D.V.M.
 435A Power Meter
 1707B
- MARCONI INSTR.**
 TF 106B5/6 FM Signal Generator
- FLUKE**
 8100A Digital Multimeter
 8300A Digital Voltmeter
 332B Voltage Calibrator
 341A O.V.M. Calibrator
- TEKTRONIX**
 434
 485 100MHz D.T. Scope
 485/05/07 TV Scope
 475 200MHz D.T. Scope
 422 15MHz D.T. Scope
 549 Storage Scope
 1140 Spectrum Analyser Plug in.

SIGNAL SOURCES

- ADVANCE**
 V.H.F. Square Wave Generator SG21
 10 KHz-100MHz Max. o/p 2V £35.00

- GENERAL RADIO**
 Unit Oscillator 1209C Freq. 250-920MHz Accuracy 1% Drift 0.2% 0/p in to 50ohms = 150mW supplied with Power Supply Type 1201-CQ1B as illustrated £215.00
 Unit Oscillator 1218A 900-2000MHz Power output of 200mW across band £140.00
- HEWLETT PACKARD**
 F.M. A.M. Signal Generator 202H F.M. A.M. CW & pulse coverage 54 to 216 MHz R.F. o/p 0.1µV-2V 50ohms Impedance £450
 V.H.F. Signal Generator 608E 10-480MHz (5 band) Accuracy ±0.5% o/p 0.1µV-1V (variable) 50ohms int. A.M. 400 & 1000Hz Ext. A.M. 20Hz-20KHz Superb condition £895
 S.H.F. Signal Generator 618C 2.8-7.6GHz ±1% 50ohms £550.00
 U.H.F. Signal Generator 616A 1.8-4.2GHz £475.00

- MARCONI INSTR.**
 F.M. A.M. Signal Generator TF 995A/3S Ministry type No CT402 1.5MHz-220MHz R.F. o/p 2µV-200mV Internal & External Mod Facilities V. good condition £385
 F.M. A.M. Signal Generator TF 995A/5 1.5-220MHz in 5 bands 0.1µV-200mV F.M. up to ±120KHz from 50Hz-15KHz A.M. up to 50% from 100Hz-10KHz o/p (1) 2µV-200mV (2) with terminating unit 1µV-100mV Int. mod. freqs. 400Hz, 1KHz & 1.5KHz Distortion (1) on internal F.M. ±25Hz (2) on internal A.M. 6% at 30% mod. £300 to £450.00
 A.M. Signal Generator TF801D/1 Freq. range 10-470MHz R.F. output 0.1µV-1V Piston attenuator 50ohms Impedance Modulation Int. A.M. 1KHz Ext. A.M. 30 Hz-20KHz Low spurious F.M. & drift V.S.W.R. 1.2 or less £400-£800
 A.M. Signal Generator TF801D/1S Military Version 10-485MHz £450-£800
 R.C. Oscillator TF1370A 10Hz-10MHz Square Wave up to 100KHz High Outputs up to 31 V £285
 Phase A.M. Signal Generator TF 2003 0.4-12MHz £150
 A.M. Signal Generator TF 801B/3S 12 485MHz 0.1µV-1V £195.00
 R.C. Oscillator TF1101 Frequency range 20Hz-200KHz Output Direct into 600Ω:20V variable Attenuator 0.6dB in 10dB steps Impedance 600Ω Distortion Via 1KHz Filter less than 1% Direct or via Attenuator. Less than 0.5% 50Hz-20KHz Less than 1% 20Hz-200KHz Superb condition £175
 U.H.F. & S.H.F. Signal Generator TF1055E 1600-4000MHz 0.1µV-445mV 50ohms Impedance £295.00
 FM/AM signal Generator TF937 1 CT320 35KHz-18.3MHz As seen condition £80.00
 Portable Receiver Tester TF888 3 Freq. 70KHz-70MHz Xtal check 500KHz & 5MHz Output Phase A.M. Signal Generator TF2003 0.4-12MHz £150.00
 V.H.F. Mobile Radio Test Set TF1064B 5M £300
 Signal Generator TF144H 4 Late models in superb condition £500 to £650
 AM FM Generator TF995B 5 (Brand new unused) £750
- MURHEAD**
 L.F. Decade Oscillator D880A 2 phase 0.01Hz-11.2KHz £295.00
 Decade Oscillator D890A 1Hz-11.2KHz £335.00
- RADIOMETER**
 Stereo signal generator SMG1C Full spec. on request Superb condition £400



- AM FM Generator Type MS27G £315
WAYNE KERR
 Video Oscillator 0 222 7KHz-8MHz in 6 ranges £75.00
 Video Oscillator 0 22D 10 KHz-10MHz £150.00


OSCILLOSCOPES

- COSSOR**
 Type 3100 DC to 35 MHz £410
 C.D.U. 150 P.O.A.
- HEWLETT PACKARD**
 Oscilloscope 140A c/w 1415A time domain reflectometer for testing of cables connectors strip-lines & transmission lines £750
 Sampling Scope 185B DC-3.5 GHz £395.00
 Oscilloscope 175A DC-50MHz Main Frame £150.00
 Plug-ins available from £25-£55.00
 50MHz single channel 1751A Time Mark Gen 1783 Aux Plug-in 1780A Display Scanner 1782A Sweep Delay Gen 1781B Dual Trace Vern. Amp 1750A Delay Gen 1781A


HAMEG

- Transistorised compact single beam portable scope bandwidth of 8MHz. Compensated Y-attenuator 12 ranges 50mV/cm to 30V/cm. Timebase sweep range of 10Hz to 500KHz and can be triggered from +Ve or -Ve externally or internally. Y input can be AC or DC coupled. Display area 6cm x 4cm. Rise time 44ns. Dimensions 203mm x 160mm x 240mm Wt. 5kg
BRAND NEW. Type No. HM207. £85.00
- MARCONI**
 TV Scope TF 2200A 1 c/w TV Diff. plug in TM 6457A DC-30MHz £190
 Portable Scope TF2203 15MHz Bandwidth DC coupled 50mV/cm sensitivity £125.00
- SOLARTRON**
 Portable Scope DC 6MHz Double Beam CT436 £95
 CD 1014 3 DC-5MHz £90
 Portable Scope CD 1400 DC-15MHz Plug ins available CX 1441, 1443, 1444, 1448 £180
 Wide Band General Purpose Scope CD-1212 (Min. spec. CT484) Plug ins CX1251 & CX1252 (collection only) £149.50
 Portable transistorised CD 1642 Dual trace DC - 15MHz 10mV/cm. Sensitivity triggering to 25MHz Screen 10 x 6cm £195
- HEATHKIT**
 10-12 µ Scope Single Beam 50mV/cm AC coupled B/W 4.5MHz 5" Tube Assembled Refurbished 90 Day Warranty Our price £49.50
- ROBAND**
 25MHz Scope R 050 c/w 5C Plug in £200
 25MHz Scope R 050A c/w 5C Plug in £225
- TEKTRONIX**
 Sampling Scope 661 c/w plug ins £450
 453 DC-50MHz Solid state & portable TV Wave Form Monitor Type 5z5 £175
 545 c/w C.A. Plug-in £275

DISPLAYS

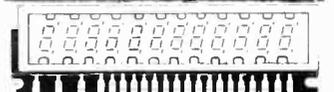

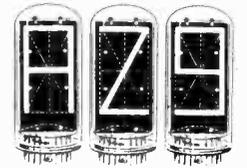Segmented Multiple Cold Cathode Gas-filled Indicator Tube Type ZM1500/12 made by Mullard - unused 12 Decades Character height 7.6mm Striking voltage 160 Ideal for Display Applications requiring a large No. of digits to be displayed. e.g. Desk Top Calculators. Overall width 86.2mm Overall height 26mm. £3.75 + P&P 30p + VAT 8%.



Numeric Tube B 5853 0-9 Digit 1.4" height. Brand New £1.00. Also Alpha Numeric Nixie Tube B 7971 Displays alphabet & 0-9 numerals 99p

PANEL SCAN
 Panel Display Model SSD 1000-0030 Direct Visual Presentation of Alpha-Numeric Data. Each panel is a self-contained package, providing 16 to 18 display positions, each of which may be instructed by a 6-bit coded signal to display one of 64 pre-programmed characters as a 5 x 7 dot-matrix, formed by special gas-discharge units. Each character is 0.4 inches high providing a bright image, visible over a wide viewing angle. Full applications data is available giving any necessary information. Price £60

POWER SUPPLIES

- I.B.M. Ex Computers**, highly stabilised transistorised incl. overload protection (220V input). On INPUT & OUTPUT Load regulation of 1% or better. Low ripple. Fast response time.
- 6V-6A £14
 3V-8A £17
 3V-4A £9.50
 3V-16A £25
 Regulated only
 48V-2.7A -7.25V 4.8A £9.50
- N.C.R.**
 Ex Computer (108-132V Input) Type 007-6004501 Mod 0 240V-20A £35
 Type 315-0516424 B 32-36V-4.8A £20



ELECTRONIC

A member of the EB group

ADD 8% VAT TO ALL PRICES

the test equipment people



On these pages you will find just the briefest selection from the vast range which we hold in stock at any one time.

If you are seeking a specific item and it is not listed, it will pay you to ring us first — we believe we offer the best prices and the best service.

WORLD WIDE EXPORT.

Enquiries and tenders welcome from any part of the world.

HOW TO REACH US

We are easy to reach, no matter where you live. Minutes away from Kings Cross or St. Pancras main-line stations, and a bus ride from Euston, only just over half an hour from Heathrow Airport. Parking is easy too.

49-53 Pancras Road, London NW1 2QB
Tel: 01-837 7781



AC/DC Breakdown & Ionisation Tester RM215-L/A

AIRMEC/RACAL
Wave Analyser 248A 5-300MHz **£195-£300**
Wave Analyser 853 30KHz-30MHz Sensitivity 1µV to 1V up to 20 MHz. 4µV to 4V up to 30MHz **£95.00**
Wave Analyser 248 Freq Range 5MHz-300MHz **£110**

AIRMEC
Modulation Meter 210 **£75 to £100**

AMPEX
F.M./Direct Recorder/Reproducer SP 300 4 Channels Speed 1 1/2, 3 1/2, 7 1/2, 15 ips Freq. response. Instrumentation: 50Hz-40Hz at 1.5 ips. Audio: 50Hz-18KHz at 15 ips **Special offer £880**

BECKMAN
Transfer Oscillator 7580H DC-15GHz with counter. 7.5MHz-15GHz without counter. Sensitivity 100mV (R.M.S.) **SPECIAL OFFER £250**

BELL
Gaussmeter Type 120, complete with Probes **P.O.A.**

B. & K.
Deviation Bridge 1505 **P.O.A.**

B.P.L.
Component Comparator CZ457/5 **P.O.A.**

BURNDIPT
Battery Charger BE370 **£30.00**

COSSOR
Battery Charger CC 99 **£15.00**

DECCA
Power Supply for Noise Source. MW 61 **P.O.A.**

EDDYSTONE
Receiver Type 7705 Freq. 500-100MHz **P.O.A.**

TELEONIC
Band Pass Filter. TBA 140-60-5CC1 5 Section. TNC to TNC connectors. 1/4" tubular 60MHz bandwidth 140MHz centre freq. Brand new **£20**

TEKTRONIX
Probe type P6006 (with UHF plug fitted) **£12.50**

PYE
Thermocouple test set 7556 **£95**

GENERAL RADIO
Immittance Bridge 1607A Immaculate Condition in Wooden Transit Case **£1000**

Unit Null Detector 1212A 20Hz-5MHz Log Response with 120dB scale **P.O.A.**

HEWLETT PACKARD
Distortion Analyser 331A **£210**

Digital Recorder 560A **£110**

Digital Recorder 561B **£140**

HEWLETT PACKARD
Directional detector 787D 1.9-4.1GHz **£90**

Directional detector 788C 3.7-8.3GHz **£95**

MARCONI INSTR.
Attenuator TF 1073A/25 **£85**

Out of Limits Indicator TF 2404/2M1 Checks readings from electronic counters and other digital insts. Local and remote visual and electrical indication suitable for use by unskilled personnel and with A.T.E. **P.O.A.**

Blank & Sync. Mixer TF 290B **£90**

Quantization Distortion Tester TF 2343 **P.O.A.**

R.F. Power Meter TF 1152/1 **£75**

'Q' Meter TF 329G **£200**

MARCONI
Probe kit TMB120/1 X1 for use with valve voltmeter TF2600. Brand new **£20**

RHODE & SCHWARTZ
Stereo Coder MSCBN 4192/2 **P.O.A.**

Polyscop Swob II **£1450**

Attenuator type DPR Z=60 ohms BN 18042 **P.O.A.**

U.H.F. Millivoltmeter Type URV **£175**

Frequency Indicator FKM-BN 47051 **P.O.A.**


SIGN ELECTRONICS
D.F.M. type DM344A **£115**

TELEONIC
Sweep Generator SM 2000 c/w Plug Ins E-3M, S-6 & S-4M **P.O.A.**

WAYNE KERR
Current Ratio Transformer T102C **P.O.A.**

Add 50p Post & Packing, plus VAT (8%) to all above prices

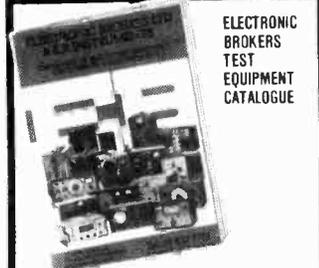Type 315-0502654D 12V-15A **£32**
Type 315-0505928G 12V-25A **£40**



ELECTRONIC BROKERS TEST EQUIPMENT CATALOGUE

The most comprehensive catalogue of its kind ever compiled in the UK. Send 50p towards printing, postage, etc. (Overseas customers £1) and a catalogue will be sent by return. Electronic Brokers Ltd. will then keep the catalogue updated by forwarding revision sheets free of charge.

MULTIMETERS

AVO
Avometer Test Set No. 1 (Panclimatic Version of Model 9) **£44**
Avometer Model 8X (same spec. as Model 8) **£40**
Avometer Model 7 **£29**
All above refurbished, calibrated and guaranteed test leads. NEW for above Models **£4**
Ever Ready cases **£6.50**
Multimeter Mk. 4 c/w carrying case & leads **£17.50**
EVERSHED & VIGNOLES
250V Megger **£18**

RUSSIA
AC Clamp Volt-ammeter U.91 Brand New **£13.75**
Spec Current 10 2 1/2-100-250-500 Amps. Voltage 300, 600V Accuracy 4% Used for measurements of AC Voltages and currents without breaking the circuits. Ranges are selected by means of a Rotary Selector Switch **£37**
Megohmmeter Type M4100/3 Brand New **£37**
Nominal o/p Voltage (open ckt.) 500V High measurements Range (at 500V) 500MΩ (Mid Scale

5MΩ) Low measurements Range 1000KΩ. Portable (7lbs) and Hand operated c/w carrying case. **SEE ALSO INSIDE BACK PAGE.**

VOLTMETERS

ADVANCE
Differential Voltmeter M500 c/w AC/DC Converter M501 **P.O.A.**
A.C. Millivoltmeter 77B **£40**
HEWLETT PACKARD
DC Vacuum Tube Voltmeter 412A 1mV-1000V 1% Accuracy Can also be used as Ohmmeter & Ammeter **£75**
VTVM 400D 1mV to 300V F.S. 12 ranges 10Hz to 4MHz 2% accuracy. Input Impedance 10Mohms **£85**
VTVM 400L Logarithmic version of 400D Reads RMS value of sine wave Log. voltage scale 0.3 to 1 & 0.8 to 3. Linear dB scale. Input Impedance 10Mohms **£90**
Vacuum Tube Voltmeter 410B Freq. Range 20Hz-700MHz AC1-600V (6 ranges) DC 1V-1KV ohmmeter 0.2 ohms to 500Mohms (7 ranges) Accuracy ± 3% **£65.00**
Vacuum Tube Voltmeter 400H Freq. Range 10Hz-4MHz Volts 1.0mV-300V F.S. (12 ranges) Accuracy ± 1% (50Hz-500KHz) ± 2% (20Hz-1MHz) **P.O.A.**
AV Voltmeter 400E Solid state AC volts 1mV-300V FS (12 ranges) Freq 10Hz-10MHz Accuracy 1% **P.O.A.**
R.M.S. Voltmeter 3400A **£285**
AC Voltmeter 400F **P.O.A.**

MARCONI
Sensitive Valve Voltmeter TF 1100 100V-300V AC. Freq. coverage 10Hz-10MHz. Meter has dB scale facility **£85**
Valve Voltmeter TF 1041B General Spec. 0-300V AC 0-1KV DC Resistance up to 500Mohms **£60/£95**
Voltmeter No. 3 CT 20B TF 95B AC 100mV-150V multiplier extends AC range to 1.5KV DC 50mV-100V Freq. Range 20Hz-100MHz **£55.00**
Valve Voltmeter TF2600 AC 25mV-300V (7 ranges) DC 10mV-1000V (8 ranges) Ohms 0.2 to 59M (7 ranges) 20Hz to 1500MHz. Brand new condition **£175**

PHILIPS
L.F. Millivoltmeter GM 6012 12 ranges 1mV-300V dB scale on meter. Accuracy 2Hz 5% 5Hz-100KHz 2.5% 100KHz-1MHz 0.5% Amplification available 50/70 **£65.00**
H.F. Millivoltmeter GM 6014 Measuring Ranges 1mV-300mV in 6 ranges Accuracy at 30KHz 3% of FSD - Amplitude Char. 1KHz-30KHz flat within ± 5% **£55.00**
DC Microvoltmeter GM6020 10µV-1kV Current 10µA-10mA Accuracy 5% (FSD) 0-100µV 3% (FSD) All other ranges Recorder o/p facility **£65.00**

SIGN ELECTRONICS **£60**
A.F. Voltmeter AM324

SOLARTRON **£235.00**
D.C. Digital Voltmeter LM1420.2 2.5-V-1Kv in 6 ranges 0-0.5% DC accuracy

D.V.M. Type LM1420 2Ba DC. true R.M.S. & mean AC sensing. Accurate measurement irrespective of harmonic distortion accuracy ± 0.25% Freq. 40Hz-20KHz **£350**

AC Converter LM1219 30mV-300V mean reading Freq. range 10Hz-10KHz **P.O.A.**

FLUKE
Differential Voltmeter 821A. For calibration, testing stability measurements of regulated power supplies. DC Voltmeter calibration ± 0.01% absolute accuracy. infinite input resistance at null over entire 0-500V range standard cell reference. Polarity switch. In-line readout with automatic lighted decimal. No zero controls. Usable as conventional V.T.V.M. (3% FSD) **£165**

Differential Voltmeter 821A. For calibration, testing stability measurements of regulated power supplies. DC Voltmeter calibration ± 0.01% absolute accuracy. infinite input resistance at null over entire 0-500V range standard cell reference. Polarity switch. In-line readout with automatic lighted decimal. No zero controls. Usable as conventional V.T.V.M. (3% FSD) **£165**

Differential Voltmeter 821A. For calibration, testing stability measurements of regulated power supplies. DC Voltmeter calibration ± 0.01% absolute accuracy. infinite input resistance at null over entire 0-500V range standard cell reference. Polarity switch. In-line readout with automatic lighted decimal. No zero controls. Usable as conventional V.T.V.M. (3% FSD) **£165**

Differential Voltmeter 821A. For calibration, testing stability measurements of regulated power supplies. DC Voltmeter calibration ± 0.01% absolute accuracy. infinite input resistance at null over entire 0-500V range standard cell reference. Polarity switch. In-line readout with automatic lighted decimal. No zero controls. Usable as conventional V.T.V.M. (3% FSD) **£165**

BROKERS LTD

Carriage and packing charge extra on all items unless otherwise stated.

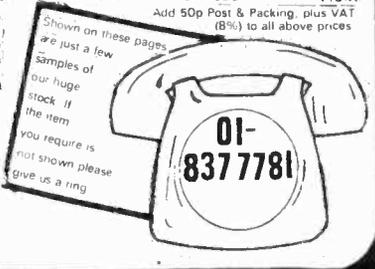Please note: All instruments offered are secondhand and tested and guaranteed 12 months unless otherwise stated.



SPECIAL LOW PRICE ARRANGEMENTS FOR VISITING OVERSEAS TRADE FAIRS

wireless
world



IPC Electrical-Electronic Press Ltd., the world's largest publishers of computer, electrical and electronic journals, have made special arrangements for readers wishing to visit important overseas trade fairs. The cost, in most cases, is little more than the normal air fare but includes – travel by scheduled airline from Heathrow and Manchester * first-class hotel accommodation * arrival and departure transfers * admission to the trade fair * services of an experienced tour manager. The current programme comprises the following tours.

To obtain a brochure and booking form, tick the box against the tours in which you are interested, complete the coupon and post to the exclusively appointed travel agent, Commercial Trade Travel Ltd., Carlisle House, 8 Southampton Row, London WC1. Telephone 01-405-8666 or 01-405-5469.

International Radio and Television Exhibition – FIRATO – Amsterdam, August 27-29 1976. Two nights at the first-class American Hotel. Fully inclusive price £89.00

Western Electronic Show and Convention – WESCON – Los Angeles – September 14-17, 1976. 10 nights at the de luxe Downtown Hilton Hotel. Fully inclusive price – £399.00.

International Exhibition of Data Processing, Communication and Office Organisation – SICOB Paris, September 23 – October 1 1976. Two nights at the de luxe Meridien Hotel. Fully inclusive price £86.50, extra nights as required.

Hifi International Exhibition and Festival – Dusseldorf – September 24-29, 1976. 2 nights at the first class Quality Inn Hotel. – Ratingen (8 km from the Fair Ground). Fully inclusive price – £99.90.

International Industrial Electronics Trade Fair – FAIREX – Amsterdam, October 18-20 1976. Two nights at the first-class American Hotel. Fully inclusive price £89.00

International Trade Fair for Production in the Electronics Industry – ELECTRONICA – Munich, November 25-December 1, 1976. Two nights at the first class Hotel Der Konigshof. Fully inclusive price £118.00, extra nights as required.

Please send details of the tours indicated above.

NAME

COMPANY

ADDRESS

Telephone

TRANSIPACK®

NO BREAK POWER SUPPLIES


NEW 2000 SERIES — FOURTH GENERATION

1KVA TO 200KVA


24 HOURS WORLDWIDE SERVICE 2 YEARS' GUARANTEE AVAILABLE

BRITISH MADE

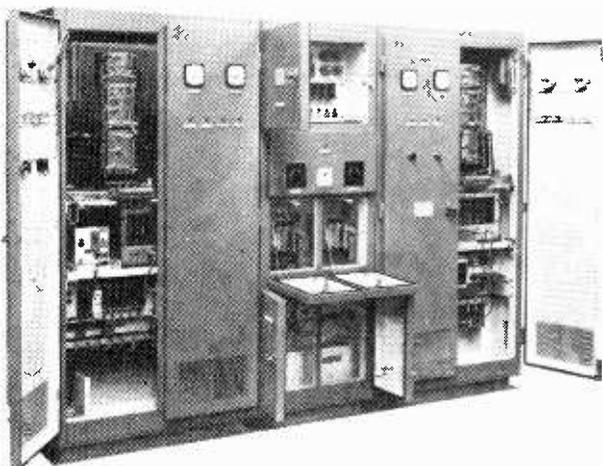VISIT US AT HASTINGS AND SEE OUR
STATIC INVERTER CENTRE



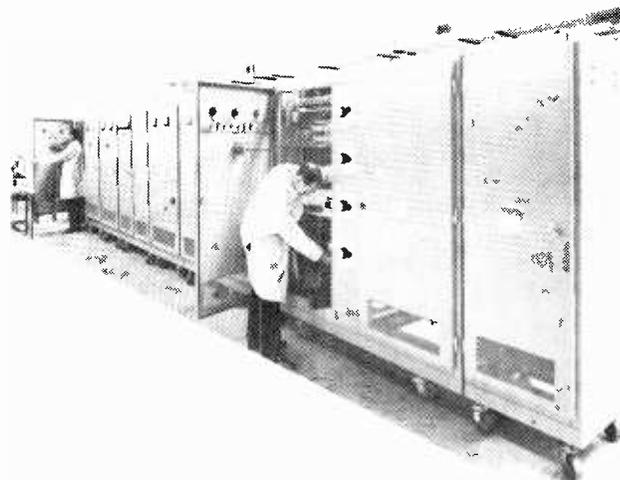TYPICAL TRANSIPACK
NO-BREAK POWER SUPPLY
AS DELIVERED TO C.E.G.B.



TYPICAL
TRANSIPACK U.P.S.
FOR COMPUTER
APPLICATIONS



NI-CD
BATTERIES
FROM
STOCK

**INDUSTRIAL
INSTRUMENTS
LIMITED**
TRANSIPACK®

Sales and Laboratories
STANLEY ROAD
BROMLEY BR2 9JF
KENT, ENGLAND
Telephone: 01-460 9861/5
Telegrams: TRANSIPACK, BROMLEY
Telex: 896071
Factory
THEAKLEN DRIVE
PONSWOOD INDUSTRIAL ESTATE
HASTINGS, SUSSEX, ENGLAND
Telephone: Hastings 427344

TELETYPE 35RO ASC11 CODE

HEAVY DUTY CONTINUOUS OPERATION with 240Volt Power Supply and Paper Feed. Circuits, Diagrams, Information supplied with all purchases.

A MUST AT £50 each

To all purchasers of the Teletype 35RO we offer a Re-Buildable Electronic Keyboard. In addition to the conventional keyboard layout there are 21 separate push-button function switches. Circuits of the internal logic and core system are provided. Power requirements obtainable from P.U. supplied with 35RO. Price £10 ONLY

MARCONI TF1094 SPECTRUM ANALYSER

Late Model, 3 MHz to 30 MHz. Resolution down to 6 Hz. Nice condition with copy of manual. Cost new in excess of £2,000. Our Price £75. Carr. £2.50. SPECIAL OFFER TO FIRST TEN PURCHASERS a FREE L.F. Adaptor extending the range down to 100Hz.

- POLARAD Receiver Model FIM-82 Complete 1-10GHz £750
- 12 CHANNEL CHART RECORDER FSD 5V 20MA per channel £29
- MARCONI ADAPTOR TM6113 for TF2700, TF1313, TF8688 £45
- AIRMEC 4-trace scope type 279. Large screen £150
- TELEVIC SWEEPER 2000-1 with LA-1M 20HZ-20KHZ £140
- MARCONI TF1101 Oscillator 20HZ-20KHZ £95
- SOLARTRON VF252 AC Millivoltmeter 1.5mv 150V full scale in 10 ranges 6" meter +/- 1% These have recently been refurbished by Solartron extra £35

COME AND LOOK ON OUR SHELVES — HUNDREDS OF OTHER ITEMS TO INTEREST YOU. TOO FAR AWAY? THEN SEND FOR LISTS

Ex-Min SCOPES CT436 DB 6 meg £95 ea. SOLARTRON CD1212 SB 40meg £95. DB 24meg twice £120. Many other types available

ONLY £10 EACH STABILISED POWER SUPPLY. 240V 50HZ input. Outputs — 15V @ 10A + 15V @ 4A — 4.5V @ 12A — 21.5V @ 1.5A. Size 16 x 20 x 9". Auto overload trips on each voltage rail with push-button resets. Many OTHER POWER SUPPLIES — call and see

TELEPHONES: Post Office style 746. Black or two-tone grey £6.50 ea. Modern style 706. Black or two-tone grey £4.50 ea. P&P 75p ea.

TELEPHONE EXCHANGES, eg 15-way automatic (exchange only) from £95.

MUFFIN FANS. 115V. Size 5 x 5 x 1 1/4". Superbly quiet and reliable. Ex-eq. but tested. £1.50 ea. P&P 75p. Also 230V @ £2.50 ea. P&P 75p

PHOTOMULTIPLIER type 931A £4 ea. P&P 75p. Other types available. also suitable Power Supplies

POTENTIOMETERS — All types. P&P extra. Metal bodied AB Linear. PCB Mount. Brand New 10K 100K ganged, 250K ganged. 100K ganged concentric shafts

BEEHIVE TRIMMERS 3/30pf. Brand New 10 off 40p. P&P 15p. 100 off £3.50 P&P 75p. 500 off £15. P&P £1.25. 1,000 off £25. P&P £1.50

LARGE RANGE ELECTROSTATIC VOLTMETERS. From 0-300V 2" £3 to 20KV Max. General guide 5KV 3 1/2" £5. Thereafter £1 per KV. P&P 75p

VARIACS 240V input 0-270V output 5A £18 ea. P&P £1. 20A £30 ea. Carr. £2.50

4.43MHz CB Crystal 25p ea. P&P 15p. 50KHZ Crystal B7/Octal base £3 ea. P&P 50p

E.H.T. TRANSFORMER 26KV AC 10MA. 240V 50HZ Single phase input £60 ea. Many other EHT Transformers and EHT Capacitors available

TRANSFORMERS — All 240V 50HZ inputs. Type A 17 0-17V 250MA. 7 5-0-7.5V 250MA. 0-20V 5A. 0-1-1.5V 5A. £2 ea. P&P £1.25. Type B 17-0-17V 250MA. 8-0-8V 250MA. 0-12.5-13.5V 5A. 0-1-5-2V 5A. £1.50 ea. P&P £1. Type C 19-0-19V 250MA. 8-0-8V 250MA. 0-7.5V 5A. 0-1-4V 5A. £1.25 ea. P&P £1.25. Type D 34V 4A. 15V 4A. 17V 4A. £3 ea. P&P £1.25. Type E 3V 1A 25p ea. P&P 50p. Type F 17V 1A 55p ea. P&P 50p. Type G 20-0-20V 200MA. 0-6V 100MA 75p ea. P&P 75p

ALL BRAND NEW (APT surplus types A B C & D. Honeywell surplus type E. Recordcall surplus type F. Parmeko Atlantic series type G)

TUBES. All Brand New Boxed. Electrostatic deflection. Type 40BA 1 1/2" dia 7 1/2" long Blue Trace £2.50 ea. P&P 75p. Type CV1526 (3EG1) 3" dia £4 ea. P&P £1. Type DG7/36 3" dia (Replacement for Telequipment 531) £15 ea. P&P £1.50. Magnetic Deflection 12DP7 12" round. Blue with yellow after glow. £1 ea. AND FOR THE VDU BUILDER. M38-111GH Rectangular 30x20cm. Green trace. Superb value. £12, or Economy type CME 1220 24 x 18cm. White Trace. £9 ea.

DON'T FORGET YOUR MANUALS. SAE with requirements

20HZ to 200KHZ SINE & SQUARE WAVE GENERATOR. In four ranges. When bridge oscillator thermostat stabilised. Separate independent sine and square wave amplitude controls. 3V max sine. 6V max square outputs. Completely assembled PCB board. ready for use. 9 to 12V supply required. £8.85 ea. P&P 35p. Sine wave only £6.85 ea.

Minimum Mail Order £2. Excess postage refunded

Unless stated — please add £2.50 carriage to all units.

VALUE ADDED TAX not included in prices — Goods marked with * 12 1/2% VAT, otherwise 8%. Official Orders Welcomed. Government/Educational Depts., Authorities, etc., otherwise Cash with Order.

Open 9 a.m. to 5.30 p.m. Mon to Sat

CHILTMead LTD

7/9 ARTHUR ROAD, READING, BERKS. (rear Tech. Collage, King's Road). Tel. Reading 582605

For those who appreciate Quality...
a complete electronic kit
The Forgestone 400
high quality
colour television receiver

A really up-to-the-minute kit, with all these Plus Features . . .

- 9 integrated circuits
- Thick film resistor units
- Ready-built and aligned IF module
- Glass epoxy printed circuit panels
- High quality components
- Fully isolated power supply
- Plugs and sockets for easy panel removal
- Each module kit available separately
- Full technical construction manual
- LT supply regulator

Buy as you build — all Forgestone Kitsets are for the constructor of today, each section of the kit is available separately. Please send stamp for further details of these quality products.

Forgestone Colour Developments Limited

Ketteringham, Wymondham, Norfolk, NR18 9RY, U.K.

Telephone: Norwich 810453 (STD 0603)

MAIL ORDER — Barclaycard & Access accepted



WW—089 FOR FURTHER DETAILS

Fantastic Big Name Instrument Scoop!!

★ Complete, undamaged units! ★ Fabulous bargains in all departments!

Just look at these low, low prices! Look around as much as you like — you won't beat these incredibly low prices for complete, undamaged instruments. But you must contact Carston Electronics, the big name in the used instrument business in the UK!

			£ Sale Price
FLUKE	873A	Differential Voltmeter 0-1100 V AC/DC. Infinite impedance at null	50 00
Solartron	LM1420 2BA	Digital Voltmeter. 0-1000 V DC. Mean or true RMS AC. 4 digits. 0.05% (DC)	180 00
Solartron	VP250 2	Resolved Component Indicator. Quadrant indicators. For synchro, etc., testing	60 00
B & K Laboratories	2203	Sound Level Meter. Precision standard. Complete with 1" microphone. Battery operated	290 00
Hewlett Packard	5252A	Frequency Counter Plug-in for 5200 series main frames. DC 350 MHz	41 00
Marconi	TF1417A	Frequency Counter/Timer. DC-15 MHz. 6 digits	100 00
Cossor	4100A	Oscilloscope. 75MHz. Dual Trace. Portable	390 00
Tektronix	C12R	Oscilloscope Camera. Takes Polaroid roll film. Adaptors available. Fits Tek 540 series	60 00
Uher	4000L	Audio Tape Recorder. Professional Class. Fully portable	90 00
Marconi	TF2005A	Twin Signal Generator. 20 Hz - 20 KHz	130 00
Schaevitz E - M	P700	Pressure Sensor. Gas and Liquid Pressures. Dynamic or static. Strain gauge operating principle. Ranges 5-5000 ps i	52 00
Bell	110	Gaussmeter. DC only. 1 Gauss - 30 K Gauss. Hall effect probes available at extra cost	80 00

These are just a few of the incredible bargains available from Carston. For the latest list of low-priced, used instruments, contact:



Carston Electronics Limited

Shirley House 27 Camden Road London NW1 Tel: 01-267 4257

BUY NOW!


WW—093 FOR FURTHER DETAILS

For all who want to know about electronic circuits

Here's a book of very special appeal to all concerned with designing, using or understanding electronic circuits. It comprises information previously included in the first ten sets of Wireless World's highly successful Circards – regularly published cards giving *selected* and *tested* circuits, descriptions of circuit operation, component values and ranges, circuit limitations, modifications, performance data and graphs. Each of the ten sets – including additional circuits – in this magazine size hard cover book has been updated where necessary, and is preceded by an explanatory introduction. Circuit designs (1) is the first collection of its kind.

Circuits covered are:

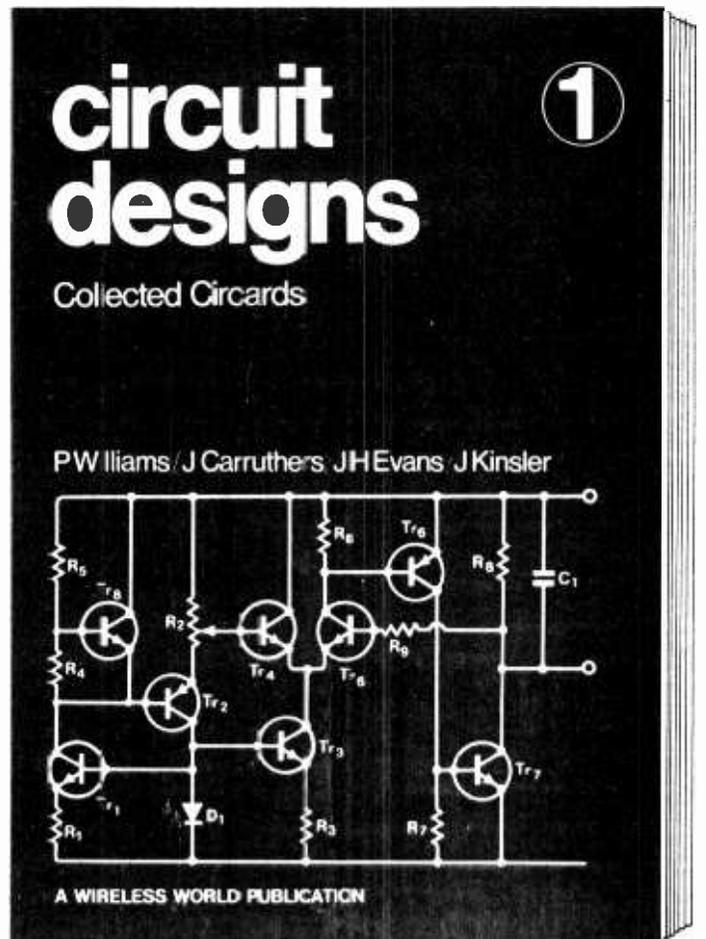- Basic active filters**
- Switching circuits**
- Waveform generators**
- AC measurements**
- Audio circuits**
- Constant-current circuits**
- Power amplifiers**
- Astable circuits**
- Optoelectronics**
- Micropower circuits**



A new book from Wireless World

ORDER FORM

To: General Sales Department,
IPC Business Press Limited,
Room 11, Dorset House,
Stamford Street, London SE1 9LU.

NAME (please print)

ADDRESS

Please send me copy/copies of
Circuit Designs – Number 1 at £10.40
each inclusive. I enclose remittance
value £. (cheques payable to
IPC Business Press Ltd.)

Company registered in England and a subsidiary of Reed
International Limited Registered No 677128 Regd. office
Dorset House, Stamford Street, London SE1 9LU.

Wilmslow Audio

THE firm for speakers!



Baker Group 25, 3, 8, or 15 ohm	£8.64
Baker Group 35, 3, 8 or 15 ohm	£10.25
Baker Deluxe, 8 or 15 ohm	£12.38
Baker Major, 3, 8 or 15 ohm	£10.69
Baker Regent, 8 or 15 ohm	£9.00
Baker Superb, 8 or 15 ohm	£16.31
Celestion HF1300 8 or 15 ohm	£6.98
Celestion MH 1000 horn, 8 or 15 ohm	£13.50
Decca London and X over	£36.25
Decca DK30 and X over	£24.00
EMI 5" Mid range	£3.15
EMI 6 1/2" d/cone roll surr. 8 ohm	£3.93
EMI 8 x 5, 10 watt. d/c. roll/s 8 ohm	£3.56
EMI 14" x 9" Bass 8 ohm	£11.92
Elac 59RM 109 15 ohm, 59RM 1148 ohm	£3.38
Elac 6 1/2" d/c roll/s 8 ohm	£3.83
Fane Pop 15 watt 12"	£5.25
Fane Pop 33T 33 watt 12"	£9.25
Fane Pop 50 watt, 12"	£12.50
Fane Pop 55, 12" 60 watt	£15.50
Fane Pop 60 watt, 15"	£17.95
Fane Pop 70 watt 15"	£18.75
Fane Pop 100 watt, 18"	£27.95
Fane Crescendo 12A or B, 8 or 15 ohm	£37.95
Fane Crescendo 15, 8 or 15 ohm	£49.95
Fane Crescendo 18, 8 or 15 ohm	£67.95
Fane 80T 8" d/c, rolls/s, 8 or 15 ohm	£5.18
Fane 80T 8" d/c roll/s 8 ohm	£8.96
Goodmans 8P 8 or 15 ohm	£5.95
Goodmans 10P 8 or 15 ohm	£6.25
Goodmans 12P 8 or 15 ohm	£14.95
Goodmans 12P-D 8 or 15 ohms	£16.95
Goodmans 12P-G 8 or 15 ohms	£16.50
Goodmans Audiom 200 8 ohm	£13.46
Goodmans Axent 100 8 ohm	£7.60
Goodmans Axiom 402 8 or 15 ohm	£19.80
Goodmans Twinaxiom 8" 8 or 15 ohm	£9.50
Goodmans Twinaxiom 10" 8 or 15 ohm	£9.86
Kef T27	£5.18
Kef T15	£6.25
Kef B110	£6.75
Kef B200	£7.85
Kef B139	£15.08
Kef DN8	£2.08
Kef DN12	£5.39
Kef DN13	£4.05
Richard Allan HP8B 8" 45 watt	£11.93
Richard Allan CG8T 8" d/c roll/s	£7.65
STC 400 1 G super tweeter	£5.90
STC 400 1 K super tweeter	£5.90
Baker Major Module, each	£13.28
Goodmans Mezzo Twinkit, pair	£46.50
Goodmans DIN 20, 4 ohm, each	£13.28
Heime XLK35, pair	£26.75
Heime XLK40, pair	£38.50
Heime XLK30, pair	£21.95
Heime XLK50, pair	£55.50
Kefkit 1, pair	£44.10
Kefkit III, each	£39.38
Richard Allan Twinkit, each	£13.46
Richard Allan Triple 8, each	£20.25
Richard Allan Triple, each	£25.18
Richard Allan Super Triple, each	£29.25
Richard Allan RA8 kit, pair	£37.80
Richard Allan RA82 kit, pair	£59.40
Wharfedale Linton 2 kit (pair)	£20.81
Wharfedale Glendale 3 XP kit, pair	£47.70
Wharfedale Dovedale 3 kit, pair	£59.40

Prices correct at 14/5/76

ALL PRICES INCLUDE VAT

Cabinets wadding, Vynair, Crossovers etc. Send stamp for free booklet "Choosing a Speaker"

FREE with all orders over £10 — HiFi

Loudspeaker Enclosures Book

All units are guaranteed new and perfect

Prompt despatch

Carriage: Speakers 50p each, 12" and up 75p each, tweeters and crossovers 30p each, kits 80p each (£1.60 pair)

WILMSLOW AUDIO

Dept. WW

Loudspeakers & Export Dept: Swan Works, Bank Square, Wilmslow, Cheshire SK9 1HF. Discount HiFi, PA etc: 10 Swan Street, Wilmslow. Radio, Hi-Fi, TV: Swift of Wilmslow, 5 Swan Street, Wilmslow. Tel. (Loudspeakers) Wilmslow 29599, (HiFi, etc.) Wilmslow 26213.

WW-009 FOR FURTHER DETAILS

GIRO NO. 331 7856. Access and Barclaycard accepted. C.W.O. only
 Terms of business as in our catalogue
 Export Order enquiries welcome (£5 min.)
 Official Orders accepted from Educational & Government Departments
ALL PRICES INCLUDE VAT & P. & P.
 E. & O. E. Shop hours: 9-12.30, 1.30-5 p.m. 5 days
 Except Wednesday

1976 ISSUE 66 PAGES — 3000 ITEMS FULLY ILLUSTRATED

- * 20p CREDIT VOUCHERS
- * ALL NEW STOCK
- * SATISFACTION GUARANTEE
- * DISCOUNTS
- * NEW PRICE LIST — S.A.E. FOR CAT. 4a

20p plus 10p postage

TRANSFORMERS SEMICONDUCTORS MODULES — AUDIO HEATSINKS — S-DEC AUDIO ACCESSORIES TOOLS — TEST METERS CALCULATORS — AUDIO LEADS — BATTERIES — KITS RESISTORS — CAPACITORS CASES — COILS — BOOKS CONNECTORS — VERBOARD PC MATERIALS — HARDWARE BOXES — SCREWS — KNOBS POTS — STORAGE UNITS, ETC., ETC.

SPECIAL RESISTOR KITS (CARBON FILM 5%)

(Prices include post & packing)
 10E12 1/4W or 1/4W KIT 10 of each E12 value.
 22ohms — 1M, a total of 570 **£5.29** net
 25E12 1/4W or 1/4W KIT 25 of each E12 value. 22 ohms — 1M, a total of 1425 **£12.64** net

SPECIAL CAPACITOR KITS

C280 Kit—PC Mounting polyester 250V 5 of each value 0.01 0.022, 0.047, 0.1, 22µF, 2 of 0.47, 1µF **£1.98** net.
 C296 Kit—Tubular polyester 400V 5 of each value 0.01 0.022, 0.047, 0.1, 0.22µF, 2 of 0.47µF **£2.67** net.
 Ceramic Kit—square plaque 50V 5 of each value 22, 33, 47, 100, 220, 330, 470, 1000µF, 2200, 4700µF, 0.01µF **£1.66** net.
 250V Paper Kit—Tubular-metal case, 3 of each value 0.05, 0.1, 0.25, 0.5 1µF **£1.41** net.
 500V Paper Kit—Tubular metal case, 3 of each value 0.025, 0.05, 0.1, 0.25, 0.5µF **£1.41** net.
 1000V Paper Kit—Tubular metal case, 3 of each value 0.01, 0.025, 0.05, 0.1µF **£1.63** net.

B.H. COMPONENT FACTORS LTD.

MULTIMETER U4341


27 Ranges plus Transistor Tester
 16 700Ω Volt
 Vdc—0-3—900V in 8 ranges
 Vac—1.5—750V in 6 ranges
 Idc—0.06—600mA in 5 ranges
 Iac—0.3—300mA in 4 ranges
 Resistance—2KΩ—2MΩ in 4 ranges
 Accuracy—dc—2 1/2%
 ac—4% of F.S.D.
 hfe—10—350 in 2 ranges
 Size—115 x 215 x 90mm
 Complete with steel carrying case, test leads and battery **PRICE £12.10** net P&P 75p



U4341

MULTIMETER U4313

33 ranges Knife edge with mirror scale
 20 000Ω Volt High accuracy mVdc—25mV
 Vdc—1.5—600V in 9 ranges
 Vac—1.5—600V in 9 ranges
 Idc—60—120 microamps in 2
 Idc—0.6—1500mA in 6 ranges
 Iac—0.6—1500mA in 6 ranges
 Resistance—1KΩ—1MΩ in 4 ranges
 db scale—10 to +12db
 Accuracy—dc—1 1/2%, ac—2 1/2%
 Size—115 x 215 x 90mm
 Complete with steel carrying case, test leads and battery
PRICE £16.09 net P&P 75p

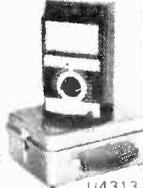

U4313

MULTIMETER U4323

22 Ranges plus AF 1F Oscillator
 20 000Ω Volt
 Vdc—0.5—1000V in 7 ranges
 Vac—2.5—1000V in 6 ranges
 Idc—0.05—500mA in 5 ranges
 Resistance—5Ω—1MΩ in 4 ranges
 Accuracy—5% of F.S.D.
 OSCILLATOR—1 KHz and 465 KHz (A.M.) at approx. 1 Volt
 Size—160 x 97 x 40mm
 Supplied complete with carrying case, test leads and battery
PRICE £9.95 net P&P 75p



U4323

MULTIMETER U4324


34 Ranges High sensitivity
 20 000Ω Volt
 Vdc—0.6—1200V in 9 ranges
 Vac—3—900V in 8 ranges
 Idc—0.06—3A in 6 ranges
 Iac—0.3—3A in 5 ranges
 Resistance—25Ω—5MΩ in 5 ranges
 Accuracy—dc and R—2 1/2% of F.S.D.
 ac and db 4% of F.S.D.
 Size—167 x 98 x 63mm
 Supplied complete with storage case, test leads, spare diode and battery
PRICE £11.72 net P&P 75p



U4324

(WWW), LEIGHTON ELECTRONICS CENTRE, 59 NORTH STREET, LEIGHTON BUZZARD, LU7 7EG.
 Tel. Leighton Buzzard 2316 (Std code 05253)

NEW! BK PRECISION Test Instruments

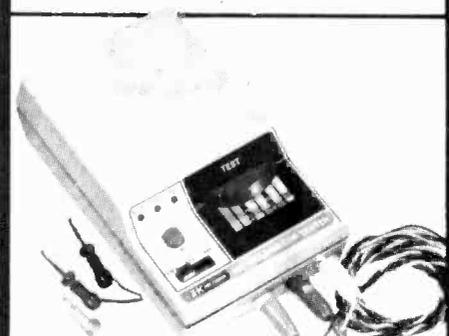

MODEL 510 Exclusive Dynapeak™ With Selectable Hi-Lo Drive For Accurate In-Circuit And Out-of-Circuit Transistor Testing.

- Fast GO/NO-GO in-circuit transistor testing
- Fast and thorough GOOD/BAD out-of-circuit testing
- Test FET's and SCR's in-circuit or out-of-circuit



MODEL 280 3-Digit Portable Multimeter.

- Low price • Easy to read
- Reliable—fully overload protected
- Large LED readout
- Completely portable—use it anywhere!



MODEL 283 3 1/2 Digit Multimeter.

- High intensity, high reliability 3 1/2 digit LED display for maximum readability
- Selectable HI/LO ohms function allows in-circuit resistance
- Universal AC power supply

For complete specifications and prices write:

EMPIRE EXPORTERS Inc.

270 Newtown Rd., Plainview, N.Y. 11803

Cable Address: EMPEXINC PLAINVIEW, N.Y. STATE


Telex No. 96-7880 MORHAN EX PLVV

WW-063 FOR FURTHER DETAILS

Appointments

Advertisements accepted up to 12 noon Monday, June 28, for the August issue, subject to space being available.

DISPLAYED APPOINTMENTS VACANT: £6.50 per single col. centimetre (min. 3cm).
LINE advertisements (run on): £1 per line, minimum three lines.
BOX NUMBERS: 45p extra. (Replies should be addressed to the Box Number in the advertisement, c/o Wireless World, Dorset House, Stamford Street, London SE1 9LU.)
PHONE: Owen Bailey on 01-261 8508 or 01-261 8423.
Classified Advertisement Rates are currently zero rated for the purpose of V.A.T.

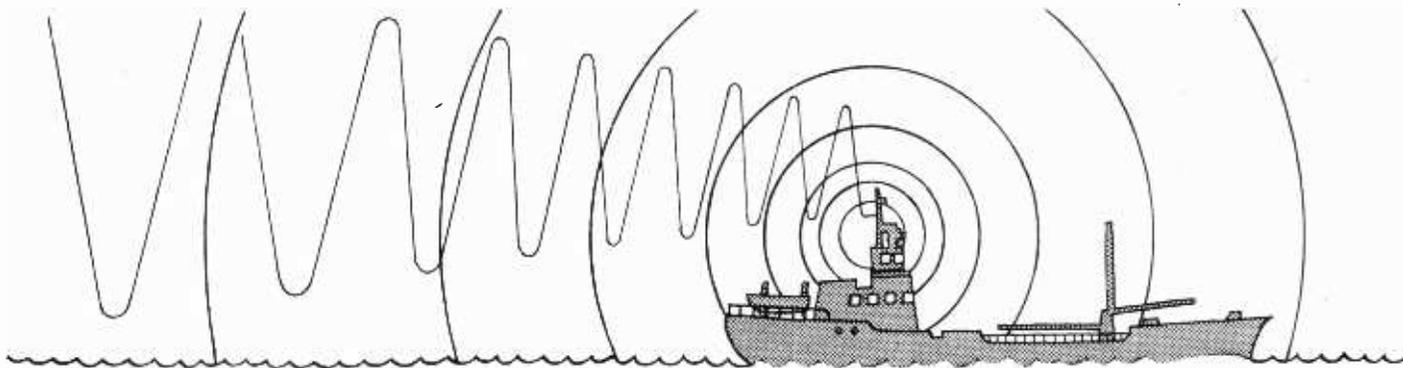

Radio Officers—now you can enjoy the comforts of home.

Working for the Post Office Maritime Services really makes sense. You still do the work that interests you, but with all the advantages of a shore-based job: more time to enjoy home life, job security and good money. To qualify, you need a United Kingdom Maritime Radiocommunication Operator's General Certificate or First Class Certificate of competence in Radiotelegraphy, or an equivalent certificate issued by a Commonwealth Administration or the Irish Republic.

Starting salaries, at 25 or over, are £2905 rising to £3704 after three years service. Between 19 and 24, the starting salary varies from £2234 to £2627

according to age. You'll also receive an allowance for shift duties which at the maximum of the scale averages £900 a year and there are opportunities to earn overtime. There's a good pension scheme, sick pay benefits and prospects of promotion to senior management.

Right now we have vacancies at some of our coastal radio stations, so if you're 19 or over, write to: ETE Maritime Radio Services Division (L687), ET 17.1.1.2., Room 643, Union House, St. Martins-le-Grand, London EC1A 1AR.

Post Office Telecommunications

IMPERIAL COLLEGE OF SCIENCE AND TECHNOLOGY

Department of Electrical Engineering

DEPARTMENTAL SUPERINTENDENT

Applications are invited from candidates with suitable experience for the post of Departmental Superintendent, Electrical Engineering Department.

Duties will include supervising the operation of departmental technical services and departmental records/finance office. The superintendent will have regular contact with over 100 departmental academic and technical staff, and with a wide range of college administrative staff. Proven administrative, supervisory and technical ability is essential. Salary in the administrative grade II scale £5214-£6446 per annum plus £450 London allowance.

Further particulars may be obtained from the Head of Department, Electrical Engineering Department, Imperial College SW7 2BT, to whom applications should be sent by 30th June, 1976.

(5884)

audio development engineers

Grampian, a member of the Telephone Rentals group, manufacture a wide range of electronic and electro-acoustic audio and internal telephone equipment. We have vacancies for development engineers to work on all aspects of communications processing and audio distribution systems. We are seeking people with experience of analogue development work, preferably in the audio field, and possessing a high degree of motivation. In return for initiative we offer competitive salaries and generous Pension and Life Assurance schemes.

For application form or further details please contact Mr. G. N. Turner

Grampian

GRAMPIAN REPRODUCERS LIMITED
 The Hanworth Trading Estate
 Feltham, Middlesex TW13 6EJ
 01-894 9141

(5272)

UNIVERSITY OF LIVERPOOL ELECTRONICS TECHNICIAN/ ENGINEER

Required for the Electronics Workshop of the Department of Electrical Engineering and Electronics. This post would be suitable for a person holding either HNC or C & G Final Certificate for telecommunications technicians, together with practical experience of the lay-out of printed circuit boards and the use of linear and digital integrated circuits. The successful applicant will assist in the development and production of a wide range of instruments used in the teaching and research laboratories.

Initial salary within a range up to £3207 per annum, according to qualifications and experience.

Application forms may be obtained from the Registrar, The University, P.O. Box 147, Liverpool L69 3BX. Quote ref. RV/791/WW.

(5593)

TEST AND LIAISON ENGINEERS

Ferranti in Edinburgh have a number of Ministry of Defence contracts involving the design and development of advanced avionic equipment for military aircraft in an international market.

We have vacancies for test and liaison engineers who will probably be qualified to HND level in electronic engineering with some years' experience in design, test or support of modern avionic equipment. A knowledge of digital and analogue techniques is essential.

Close liaison with design/development teams currently engaged on inertial navigation and display systems will be necessary and the work will entail factory acceptance testing, fault diagnosis and system commissioning on a variety of sophisticated equipment.

There will be opportunities for some of these engineers after a period of in-house training to be selected for technical liaison duties at locations in the U.K., Europe, Middle and Far East.

The Company offers an attractive employment package which includes 22 days holiday and membership of a life assurance and pension scheme. Incoming personnel will qualify for housing under the Scottish Special Housing Association scheme and realistic assistance will be given with relocation expenses where applicable.

Apply in writing giving details of age, experience and qualifications to:

THE STAFF APPOINTMENTS OFFICER

FERRANTI LIMITED
FERRY ROAD
EDINBURGH EH52XS

FERRANTI

Engineer Technicians

EMI have all kinds of future for you at Hayes

With several different EMI industries concentrated at Hayes, Middlesex, the Company offers you work on a wide variety of equipments - plus opportunities to win promotions in one direction or another without ever having to move out of the Hayes area.

And, since the entire EMI Group is constantly expanding - and, indeed, looks likely to continue to expand for years to come - these opportunities may be expected to come up frequently.

Recent practical electronics experience associated with maintenance, commissioning, fault finding, testing or calibration, either in industry or with HM forces is essential.

Ideally, it will have involved work on advanced and complex electronic devices.

Certainly you'll need a good technical background with knowledge equivalent to ONC.

Given these minimum conditions, Engineer Technicians of all levels are required - and you're starting salary will faithfully reflect the experience you have accumulated to date.

Terms and conditions of employment at EMI are everything you would expect of a major international organisation, and assistance towards relocation expenses will be considered where necessary.

To apply, please write to Bill Clark, Personnel Department EMI Limited, 135 Blyth Road, Hayes, Middlesex.



Or telephone him on 01-573 3888 extension 639 or Record-a-call anytime on 01-573 5524.

The international music, electronics and leisure Group.

(5381)

Opportunities in the ELECTRONICS FIELD

Persons with analogue or digital qualifications/exp. seeking higher paid posts in TEST, SERVICE, DESIGN, SALES, COMMUNICATIONS, phone Gary Bukay or Richard Swain 01-637 0781.

ATA SELECTION (5591)

UNIVERSITY OF STRATHCLYDE

ELECTRONICS TECHNICIAN

(Grade 5)

Applications are invited for the above post in the Department of Psychology. The post involves the use, maintenance and construction of a wide range of electronic equipment for teaching and research. This includes audio and video tape recorders, projectors and other display devices, tape readers and solid state logical circuiting, as well as the usual range of electronic test equipment.

The successful candidate will be expected to be able to take some responsibility for servicing and setting up equipment with minimal supervision, and should hold an ONC or equivalent qualification and have 7-9 years' relevant experience.

Salary Scale £2751-£2307 per annum, with placing dependent on experience and qualifications.

Applications in writing, QUOTING REFERENCE P.33, giving details of age, experience and qualifications, should be made to The Personnel Officer, University of Strathclyde, Royal College Building, 204 George Street, Glasgow G1 1XW.

(5556)

ZAMBIA

A superb location

— particularly for broadening professional and management skills with a 3-year contract. This land-locked central African state, larger than France, Belgium, The Netherlands and Switzerland combined, has a congenial, equable climate and a wealth of fascinating scenery. Although mainly a broad plateau, Zambia also has spectacular mountains, dense forest, penetrating rivers and vast lakes as well as huge wildlife reserves. Large cities and towns containing all the usual modern facilities are linked by excellent road and rail services. Extensive natural resources, copper particularly, have provided the firm economic base for dramatic post-independence progress. Wide-ranging, expanding industries and substantial agriculture, which includes both crops and dairy farming, ensure the long-term continuation of Zambia's prosperity.

Chief Engineer

Qualifications:

A relevant degree or status as a Chartered Engineer. Wide practical experience of sound and television broadcasting systems and knowledge of modern transmitter design and installation.

Duties:

The planning of general broadcasting developments, overall supervision, planning and development of all technical and administrative matters in the Engineering Division. Guiding and training of Zambian Engineers.

Salary Scale:

K7200 x 204 – K7608 p.a. (£5414 – £5720)

Supplement £4128 (Married) £2724 (Single)

Maintenance Engineer

(Radio transmission, Short and Medium wave)

Qualifications:

Final City and Guilds Certificate in Telecommunications or equivalent plus at least 8 years' experience with a Broadcasting Organisation with particular experience in the installation and maintenance of transmitters

Duties:

The installation of medium and short wave transmitters and antennas ranging in power from 10Kw to 500Kw. He will also be responsible for maintenance of transmitters and will be expected to train local staff.

Salary Scale:

K4416 – K5136 p.a. (£3397 – £3862). Entry point will depend on previous relevant experience.

Supplement £3060 – £3540 (Married) £1710 – £2136 (Single)

Maintenance Engineer

(TV Transmitters)

Qualifications:

As in above post.

Duties:

The operation and maintenance of TV transmitters operating in Band I and Band III. He should have wide experience to be able to train local staff.

Salary Scale:

K4416 – K5136 p.a. (£3397 – £3862). Entry point will depend on previous relevant experience.

Supplement £3060 – £3540 (Married) £1710 – £2136 (Single)

Strong financial attractions

— salaries plus TAX-FREE supplements, TAX-FREE terminal gratuities, low-cost accommodation, low taxation and free passages together add up to exceptional real earnings. Starting salaries relate to qualifications/experience (the maximum of each scale is shown), while gratuities total 25% of basic salary. Salary-related supplements are paid by the British Government to designated British nationals, (annual maximum is shown), while appointment grants, educational allowances, car loans, medical aid assistance and free holiday visits for children educated in Britain are also provided for those receiving supplements. N.B. Sterling equivalents given are approximations only, due to constant exchange rate fluctuations

For further information please send full personal/professional details (without obligation), to: Recruiting Officer, Zambia High Commission, 7-11 Cavendish Place, London, W.1.



(5574)

*Looking
for
a
new
job?*


Perhaps we can help!

We have regular contact with hundreds of electronics and electrical companies needing qualified electronics engineers and technicians and TV service engineers.

We can, therefore, help you to find an interesting and well paid job. All you need to do is to return the coupon below or give us a ring. Our service is confidential and costs you nothing.

**TJB Electrotechnical
Personnel Services
12 Mount Ephraim
Tunbridge Wells, Kent**

Tunbridge Wells (0892) 39388

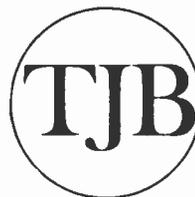

TJB Electrotechnical Personnel Services is a division of Technical & Executive Personnel Ltd. and is solely concerned with job placement in the Electronics and Electrical Industries

Please note that this service is available only for engineers who are (or will be) available in the U.K. for interview.

Please send me an "Application for Registration" form

NAME

ADDRESS

.....
..... (90)

Professionally frustrated? We can find you a new job.

You know you're good but your present employers are apparently ignorant of the fact. Enough to make you look for a new job. Put your name on the Lansdowne Appointments Register and make it easy on yourself. Hundreds of employers use our register to fill their key jobs. And remember the best jobs are not always advertised.

It costs nothing to take advantage of our help so you've nothing to lose and everything to gain. And our service is conducted in strictest confidence.

So make sure you're 'in the know' by phoning 01-579 6585 or writing to Stuart Tait, Lansdowne Appointments Register, Design House, The Mall, London W5 5LS.

Name _____

Address _____

WW 14/6

lansdowne
appointments Register

5603

TELEVISION IN SOUTH AFRICA

TELEVISION & ELECTRICAL DISTRIBUTORS LIMITED the MAJOR manufacturers of television receivers in South Africa, manufacturing and marketing the world-famous range of SONY and BLAUPUNKT colour and monochrome receivers, require more FIELD, BENCH and SENIOR TELEVISION SERVICE TECHNICIANS to join their already successful team comprising mainly of personnel from the United Kingdom.

Ability, thoroughness, tact and willingness to get involved are essential requirements for these posts at locations throughout the Republic.

This is a challenging opportunity for qualified and experienced RECEIVER SERVICE TECHNICIANS wishing to join a highly successful public company working on the latest television receivers employing advanced electronic techniques.

Salaries range from R6000 (£3429) p.a. to R9000 (£5143) p.a. dependent upon qualifications and experience.

Financial assistance with immigration can be arranged for suitable applicants and the Company pays a settling-in allowance on arrival. A medical aid and pension scheme is in operation. Company vehicles are provided.

Application and Immigration forms can be obtained by writing to Miss M. L. Fretwell, J. A. Ewing & Co. (London) Ltd., Ewing House, 108/126 Kings Road, Brentwood, Essex CM14 4EA.

(5543)

RF ENGINEERS

Vacancies exist for engineers and physicists to work on problems of electromagnetic interference — investigating generation of noise, modes of coupling and methods of control. The Electromagnetic Interference Laboratory is engaged in rf investigations for a wide range of sponsors covering problems arising in complex industrial systems as well as in ships, military vehicles and aircraft. The investigations are not confined to the laboratory and opportunities for travel could well exist in the future. There are several vacancies for which the qualifications range from HNC to Degree standard and although experience in radio frequency techniques is desirable, consideration will certainly be given to suitable applicants without experience.

ERA is an independent engineering organisation specialising in the application of electrotechnology in industry, commerce and the public services. Located in pleasant surroundings and amenities include full canteen facilities and an active Sports and Social Club.

Please write or telephone for an application form to: The Personnel Office, ERA Ltd., Cleave Road, Leatherhead, Surrey KT22 7SA, Leatherhead 74151.

ERA

(5544)

UNIVERSITY OF READING
 Department of Linguistic Science
EXPERIMENTAL OFFICER

required to be responsible for the technical services provided by the Phonetics Laboratory. Equipment in use includes PDP8E computer and a wide range of peripherals for spectrum analysis at audio frequencies. Applicants should be able to design peripheral and suitable interfaces and be familiar with audio recording up to professional standard. Equipment for CCTV, high speed photography and electromyography will be acquired shortly. Maintenance of all equipment is carried out within the laboratory.

Salary within the range £2766-£5418 per annum according to qualifications and experience.

Apply with full particulars and names of two referees, quoting Ref. TWV23A, to Assistant Bursar (Personnel), University of Reading, Whiteknights, Reading, Berks. RG6 2AH.

(5594)

IMPERIAL WAR MUSEUM. Department of Sound Records. Applicants are invited for a post which involves a variety of both technical and library-type duties. The Department of Sound Records has a wide range of professional equipment and facilities and the post would suit a young person interested in working in the audio field. Full training will be provided by an experienced Audio Technician. Candidates must have a strong technical aptitude and be capable of careful and systematic work. The post is graded Library Assistant 2 and the starting salary is from £28.15 at age 16 to £45.21 at age 23 and over rising to £50.91. A Pay Supplement ranging from £4 pw at age 16 to £6 pw at age 18 and over is payable in addition. Leave is 3 weeks 3 days per year, rising to 4 weeks after 7 years' Service. There are prospects of permanent and pensionable employment. Please apply in writing to the Establishment Officer, Imperial War Museum, Lambeth Road, London SE1 6HZ. (5578)



A Great opportunity for
TV Engineers
 in South Africa £4800 +

With the introduction of Television into South Africa, OK Bazaars are busy capturing the major share of the market. As the largest retail organisation in southern Africa we're building up a comprehensive and professional TV service operation and with our extensive involvement in this exciting new development, we are able to offer outstanding prospects to experienced personnel. Many British Technicians who started with us less than 12 months ago are already in management and senior technical positions and we now need to enlarge our already substantial staff by appointing additional Technicians in various centres throughout the Country.

defects in apparatus. Essential requirements are a recognised apprenticeship or training course on radio and TV servicing and at least three years' experience in colour TV. Applicants should also possess a City & Guilds Final Certificate in radio and TV with RTEB colour endorsement or an equivalent qualification.

Salary will be at least £4800 per annum with an extensive range of fringe benefits including Company assisted pension and medical aid schemes, full air passages, initial hotel accommodation and relocation allowances.

Initially, the work will entail carrying out repairs in the field and in the workshops, keeping records of time and materials involved and feeding back information to management on recurrent faults and

Interviews will be held in the UK, so write now with details of age, qualifications and experience to OK Bazaars, 20, Soho Square, London W1A 1DS, including a telephone number where you can be contacted.

Live and work in the sun

5541



TEST ENGINEERS
 S. LONDON
 UP TO £2,800 p.a.

Dolby Laboratories is a young, go-ahead company with a world-wide reputation for their audio noise reduction system.

Test Engineers with a good understanding of basic circuits are required to test and troubleshoot professional audio P.C.B.s and equipment. This is interesting and well paid work. We give over four weeks' holiday per annum.

Write or phone: Mr. C. Keys
 Dolby Laboratories Inc.
 346 Clapham Road
 London, SW9
 Tel. 01-720 1111

(5588)

TEST/SERVICE ENGINEER

Able to work on own initiative with digital circuitry.

Please telephone or write:

MORFAX LIMITED
 Willow Lane
 Mitcham
 Surrey CR4 4TD
 01-648 7040

(5599)

CA CAPITAL APPOINTMENTS LTD.

FIELD SERVICE ENGINEERS (ELECTRONICS)

If you're not earning over £3,500 p.a. plus a car — then you had better contact us!

(5540)

34 Percy Street, London, W.1
 01-636 9859 (day) or
 550 0836 (evening)

E.M.A.

Opportunities in the ELECTRONICS FIELD

We have selected from many vacancies those which offer exceptional career prospects and job interest. If you have experience in design, test, sales or service and wish to progress your career, please telephone Mike Gernat B.Sc. who is advising on these opportunities

E.M.A. Management Personnel Ltd.
 Burne House, 88/89 High Holborn
 London WC1V 6LR
 01-242 7773

ENERGETIC YOUNG DOGSBODY

with some electronics training (or better, experience!) required as assistant in maintenance department in enterprising recording studio. An exacting position with good prospects for an intelligent and conscientious person. CONTACT ROB HAGGAS, 01-586 1271.

(5589)

THE OPEN UNIVERSITY

FACULTY OF TECHNOLOGY

Research Post in Telecommunications

The research topic is in the field of telecommunications and the vacancy is for a suitably qualified graduate based at Walton Hall. The successful applicant will be concerned with the development of a low-cost acoustic modem for use with remote teaching terminals that are presently under development at the Open University. It is envisaged that the project will involve considerable use of computing and microprocessor technology. The salary is on the scale £2766-£3990 per annum plus U.S.S. benefits. Application forms and further particulars are obtainable, by postcard requests only please, stating sender's name and address, from the Personnel Manager (RT3), The Open University, P.O. Box 75, Walton Hall, Milton Keynes MK7 6AL. Telephone Milton Keynes 63868/9. Closing date Monday, 28th June, 1976.

ZAMBIA

A superb location

— particularly for broadening professional and management skills with a 3-year contract. This land-locked central African state, larger than France, Belgium, The Netherlands and Switzerland combined, has a congenial, equable climate and a wealth of fascinating scenery. Although mainly a broad plateau, Zambia also has spectacular mountains, dense forest, penetrating rivers and vast lakes as well as huge wildlife reserves. Large cities and towns containing all the usual modern facilities are linked by excellent road and rail services. Extensive natural resources, copper particularly, have provided the firm economic base for dramatic post-independence progress. Wide-ranging, expanding industries and substantial agriculture, which includes both crops and dairy farming, ensure the long-term continuation of Zambia's prosperity.

Radio Engineer - Aviation

Up to K4416 (c£2870)
Supplement £2898 (married), £1596 (single).

Requirements:

either 5-year apprenticeship, service trade certificate, ICAO certificate or equivalent; knowledge of medium-powered HF transmitters, frequency key shifting, SSB and equipment, medium-frequency non-directional radio beacons plus low and high-powered VHF AM equipment; and knowledge of either (a) VHF, omni-range, automatic VHF, direction finders, distance measuring equipment, (b) instrument landing systems, (c) radar X-band terminal and PPI talkdown equipment, (d) audio and remote control equipment, public address equipment, airport magnetic type equipment, inter-office communications, underground control cables, impulse and DC switching systems or (e) teleprinter telegraphy (torn tape) and associated page printers, tape recorders (auto heads), printing reperforators, semi-automatic message switching systems.

Responsibilities:

installation/maintenance/overhaul of ground terminal radio communication equipment and navigational aids.

Senior Radar Technician

Up to K5136 (c£3862).
Supplement £3156 (married), £1806 (single).

Requirements:

G & GC Level with specialisation in radar or Electronic Engineering Diploma.

Responsibilities:

Controlling a small team operating the Meteorological Department's electronic equipment; training, manual drafting, involvement in obtaining new equipment and establishing an instruments laboratory and workshop.

Strong financial attractions

— salaries plus TAX FREE supplements, TAX FREE terminal gratuities; low-cost accommodation, low taxation and free passages together add up to exceptional real earnings. Starting salaries relate to qualifications/experience (the maximum of each scale is shown), while gratuities total 25% of basic salary. Salary-related supplements are paid by the British Government to designated British nationals, (annual maximum is shown), while appointment grants, educational allowances, car loans, medical aid assistance and free holiday visits for children educated in Britain are also provided for those receiving supplements. N.B. Sterling equivalents given are approximations only, due to constant exchange rate fluctuations.

For further information please send full personal/professional details (without obligation), to: Recruiting Officer, Zambia High Commission, 7-11 Cavendish Place, London, W.1.



5573

INTERNATIONAL FIELD SERVICE ENGINEER

Required for our International Mass Spectrometer Service Division based in the U.K. A sound knowledge of modern electronics is essential and a working knowledge of high vacuum systems would be an advantage, although training will be given. Applicants should possess City and Guilds or equivalent qualifications. Due to the extensive travel involved, the position is probably more suitable for a single person aged between 20 and 30 years.

The Company is internationally renowned for the quality of its products and offers excellent working conditions, including company car, pension scheme, superannuation and profit sharing bonus scheme.

Write or telephone for an application form.

Service Manager
G Division
LKB Instruments Limited
232 Addington Road
Selsdon, South Croydon, Surrey CR2 8YD

01-657 8822

(5587)

G.R. International Electronics Ltd

is seeking an

ELECTRONICS ENGINEER

Experienced in the design of consumer audio equipment with particular emphasis on current tape-recording and/or radio receiving techniques.

The position offered is membership of a small but busy design team. The successful applicant will be able to work with a minimum of supervision under the direction of the Chief Engineer. Qualifications are of secondary importance to the ability and willingness to get the job done. The company is situated in a very pleasant part of Central Scotland, with many and varied sporting and social facilities, including an active sports and social club on the company premises.

Removal expenses will be reimbursed, and where applicable, assistance in re-housing will be given.

Please write in the first instance, giving details of age, experience, marital status, qualification and current salary, to

Mr. J. Bandeen
G.R. INTERNATIONAL ELECTRONICS LTD
Almondbank, Perthshire, Scotland, PH1 3NQ

(5555)

Broadcasting & Television Project Staff

As consulting engineers we are compiling a register of professionally qualified broadcasting and television engineers who would be willing to undertake assignments in the UK and overseas on contract terms for short periods of from 3 to 12 months in connection with preliminary planning, feasibility studies, systems designs, project management, supervision of installation and acceptance testing of broadcasting and television studio and transmitter projects.

Applicants should have experience of the planning and installation of such projects, preferably gained overseas. Experience limited to operations and maintenance will not be acceptable.

Interested applicants should send brief details of relevant technical qualifications and experience to

Crown Agents

Engineering Services Division, 4 Millbank, London SW1P 3JD
quoting reference Q1011/4/2/WF

LEICESTER POLYTECHNIC

**School of Chemistry
ELECTRONICS
TECHNICIAN**

To be responsible for (a) the design, development and construction of prototype electronic equipment for chemical applications; (b) the maintenance of existing equipment.

Successful applicant must have a knowledge of analogue and digital electronics and will probably have at least two years' experience subsequent to taking a Full Technological Certificate, HND, or a degree in Electronics.

Salary: £2,922-£3,702 per annum, plus additions for certain qualifications.

Apply in writing, giving full details, to Staffing Officer, Leicester Polytechnic, P.O. Box 143, Leicester LE1 9BH. (5565)

Kingston Polytechnic CCTV Unit

**ASSISTANT
ENGINEER/PRODUCER**

for the maintenance and operation of TV cameras and recording equipment. The ability is required to help staff and students in preparation and making of short TV programmes. HND electronics or applied physics or equivalent necessary plus keen interest in photographic presentation problems of TV work.

Salary grade AP3/4 £2922-£3702 + £261 London allowance.

Application form from Assistant Registrar, Kingston Polytechnic, Penrhyn Road, Kingston upon Thames KT1 2EE. 01-549 1366. (5580)

AGENTS REQUIRED to sell quality electric soldering instruments and ancillary equipment to industry. Commission only basis. Suit persons selling allied products who require additional income. Good potential. Box No. WW 5600.

Electronics Development Engineers

Mechanical X-ray power sources for EMI-Scanner systems—
A challenge to your electronic ingenuity.

Pantak (EMI) of Windsor are world-leaders in production of X-ray equipment, and supply the sophisticated high voltage power source units for the internationally acclaimed EMI-Scanner.

Continuous development plans include refinement of the power sources to permit a degree of operational accuracy approaching nil tolerance. To achieve this, the Company's development engineering staff, housed in a new production block, is to be increased by several electronics engineers.

Although this is a highly specialised work it requires broadly based, *non-specialist* experience in electronics development and the ability to fulfil a wide variety of functions, such as production liaison and design and development of own test equipment. Engineers selected will be expected to work on their own initiative with very little supervision.

Senior Engineers should have HNC or degree-level qualification and a minimum of 5 years' *electronics* development experience. Junior Engineers require at least ONC and 2 years' *electronics* development experience.

Salaries will take full account of experience, ability and qualification. Successful candidates will enjoy EMI Group benefits – including future opportunities for advancement, not only with Pantak, but also with other companies in the Group. Relocation expenses will be paid where appropriate.

Pantak is easily accessible from the M4 (Junction 6), A4, A332 and A355, and parking space is ample.

Applicants of either sex will be considered.

To apply, please telephone or write to Geoff Smith, Pantak (EMI) Limited, Vale Road, Windsor, Berks SL4 5JP. Telephone Windsor (95) 55611 or 55028. (5577)



A member of the EMI Group of companies.

The international music, electronics and leisure Group.

Pantak

**A leading Radio Manufacturer in
JOHANNESBURG, SOUTH AFRICA**

requires an experienced

DEVELOPMENT ENGINEER

Responsible to the Chief Engineer, but able to work on his own initiative, on radio development work.

Applicants should be qualified to at least HNC/HND, and are unlikely to have less than five years' production experience in the domestic radio field, including a close association with design and manufacturing activities.

The requirement above else is for a practical engineer with both the ability and experience to make a genuine contribution to the engineering team.

Salary: £6000 with additional benefits including pension and sickness scheme together with full assistance with relocation.

Apply now with full details of your qualifications and experience to Mr. T. Willis

P.O. Box 43121
INDUSTRIA
2042
S.A.

(5592)

**CIRCUIT DESIGN ENGINEERS
SYSTEMS TEST ENGINEERS
SALES AND CONTRACTS
ENGINEERS**



**MALLA
TECHNICAL STAFF**
334 Euston Road
London NW1 3BG
01-387 1043 (5243)

**ELECTRONICS
TECHNICIAN**

**AREA MEDICAL PHYSICS
DEPARTMENT** located at the Nottingham General and University Hospitals and Medical School requires a technician for a key position in the Electronics and Instrumentation Section which is involved in research and development projects, equipment evaluation and servicing.

Applicants should have qualifications of ONC or HNC or equivalent and relevant experience though not necessarily in medical electronics.

Salary £2931-£3834 + £312 supplement to earnings.

Further details from Area Chief Technician Tel (0602) 46161, Ext. 641

Application form from Sector Administrator General Hospital, Park Row, Nottingham

(5596)

Training Officer (Audio)

RETAIL SALES STAFF

The range of audio merchandise being sold in our retail branches is becoming increasingly complex and sophisticated, extending from simple transistor radios to expensive music centres. This situation is making greater demands on the sales staff concerned, both in the form of basic product knowledge and in answering queries from increasingly knowledgeable customers.

We wish to appoint an Audio Trainer, who will be responsible to the Training and Development Manager for the training of retail branch staff. The successful applicant will probably be aged under 40 and could come from one of a variety of backgrounds, but the ability to communicate technical ideas in a simple language, a knowledge of electronics and enthusiasm for the subject is essential. Evidence of a successful record in education and/or training will be expected. The appointment is based at our Nottingham Head Office, but a limited amount of travel and some evening work will be involved. It is open to male and female candidates.

Conditions of employment are first class and include a Profit Sharing Bonus Scheme.

Please apply in writing to: John Hobbs, Employment Services Manager.



The Boots Company Ltd.,
Station Street,
Nottingham NG2 3AA.

5579

Staffordshire Area Health Authority
Mid-Staffordshire Health District
STAFFORDSHIRE GENERAL
INFIRMARY

ELECTRONICS TECHNICIAN

Salary £2931-£3834
in 7 Annual Increments

This is an interesting new post established to provide a maintenance service to the District for a wide range of medical and engineering electronic equipment.

Applicants shall be qualified to O.N.C. preferably H.N.C. (Electronics) standard and have had considerable experience in the maintenance of electronic equipment as found in the Health Service.

Applications Forms and Job Description from Mr C B Denne, District Works Officer, Mid Staffs Health District, Coton Hill Hospital, Weston Road, Stafford Tel Stafford 57238

(5564)

RADAR/RADIO ENGINEER

REQUIRED

Duties will include the maintenance of Airport ground radars, navigational aids and communications equipment. Technical qualifications are desirable and it is essential that applicants should have considerable experience and be capable of working without close supervision.

Salary scale £2529-£3282 plus shift allowance. Salary claim pending — additional £312 p.a. anticipated from 1st July.

Written applications, giving age, experience and qualifications, to the Airport Commandant, Municipal Airport, Southend-on-Sea, Essex.

(5563)

ELECTRONICS DESIGNER. We are a small company situated in S.W. London. We require a designer to join our young electronics team working on professional equipment. He/she will design new circuitry and update present equipment in the digital, analogue and audio fields. Some experience in similar areas is essential. The Company operates a profit sharing scheme. Telephone Mr Hamill on 01-542 1171 for an application form. (5585)

LEICESTER POLYTECHNIC School of Chemistry ELECTRONICS TECHNICIAN

To be responsible for (a) the design, development and construction of prototype electronic equipment for chemical applications; (b) the maintenance of existing equipment. Successful applicant must have a knowledge of analogue and digital electronics and will probably have at least two years' experience subsequent to taking a Full Technological Certificate, HND, or a degree in Electronics.

Salary: £2,922-£3,702 p.a. plus additions for certain qualifications.

Apply in writing, giving full details, to Staffing Officer, Leicester Polytechnic P.O. Box 143, Leicester, LE1 9BH. (5565)

MANCHESTER POLYTECHNIC, Educational Services Unit. Television Engineer. Applications are invited from candidates having technical qualifications such as HNC or appropriate City and Guilds certificates with experience in the servicing of closed circuit television equipment of all types. Television studio experience preferred but not essential. Salary scale: Technician 4 £3,366-£3,702. For further particulars and application form (returnable by 31 July 1976) please send a self-addressed envelope marked "T/304" to the Secretary, Manchester Polytechnic, Lower Ormond Street, Manchester M15 6BX. (5597)

ASSISTANT EXPORT AREA MANAGER

Pye TVT, already one of the world's largest suppliers of radio and television broadcast equipment, is further expanding its already very substantial export business. To assist with this expansion, it is now seeking a young broadcast engineer as Assistant Area Sales Manager for Africa.

The engineer will give substantial back-up to the two Area Managers for Africa by handling technical/commercial correspondence and discussions with customers and agents visiting the Company.

Occasionally the engineer will be required to travel to the area for further discussions.

An HNC or equivalent in electronic engineering is desirable with some experience of broadcast operations and a working knowledge of French and/or Arabic would be an advantage.

The position offers career prospects with a progressive salary and benefits including pension scheme with life assurance. Assistance with removal expenses will be given in approved cases.

Please telephone or write for an application form to Mrs. J. A. Macnab, Personnel Manager, Pye TVT Limited, PO Box 41, Coldhams Lane, Cambridge CB1 3JU. Telephone Cambridge 45115. (5545)



Pye TVT Limited

PO Box 41 Coldhams Lane Cambridge England CB1 3JU
Tel Cambridge (0223) 45115 Telex 81103 PYE TVT CAMB

THOMSON FOUNDATION TELEVISION COLLEGE

require

ENGINEERING LECTURER

To join a team in the training of senior engineering staff from overseas television stations, in studio and transmission equipment, maintenance and operations. The post will be based in Glasgow with occasional overseas visits.

Minimum Qualifications: H.N.C. City & Guilds Full Telecommunications Certificate or equivalent: 3 years' professional broadcasting experience.

Salary: £4,266-£5,256 incremental. Contributory pension scheme.

Application forms from: The Principal, Thomson Foundation Television College, Kirkhall House, Newton Mearns, Glasgow G77 5RH. (5569)

MEDICAL PHYSICS TECHNICIAN GRADE II for Guy's Hospital

Department of Clinical Physics & Bioengineering. He/She will be a member of a team of Physicists and Technicians engaged in a variety of clerical instrumentation projects. ONC/HNC or higher qualification required, plus 2 years electronics experience in NHS Technicians Grade III. Salary scale £3,558-£4,581 plus £312 London Weighting plus £6 per week. Apply to Personnel Department, Guy's Hospital, St. Thomas Street, London SE1 9RT. Tel. 01-407 7600, Ext. 3462. (5578)

TRAINEE ENGINEER required by broadcast television production company. Applicants should have electronic engineering background, preferably associated with television and a keen interest in production. Ring John Beedie 01-734 9151. (5571)

ARTICLES FOR SALE

PRECISION POLYCARBONATE CAPACITORS

All High Stability - Extremely Low Leakage

Table with columns: RANGE, DIMENSIONS, PRICE, etc. for various capacitor types.

TANTALUM BEAD CAPACITORS - Values available 0.1 to 2.2 uF at 15V, 20V or 25V.

TRANSISTORS & ICs

Table listing various transistors and ICs with their specifications and prices.

LOW PRICE ZENER DIODES - 400MW TOL - 5% at 5mA.

RELIABLE HIGH STABILITY LOW NOISE CARBON FILM RESISTORS - 1/4W at 40°C.

SILICON PLANAR RECTIFIERS - 1.5 amp brand new wire ended.

BRIDGE RECTIFIERS - 2.5 amp, 200V, 350V, 450V, 600V.

SUBMINIATURE VERTICAL PRESETS - 0.1V only, ALL at 5p each.

Send S.A.E. for list of additional test stock items.

MARCO TRADING

(Dept. D1) The Old School, Edstaston, Nr. Wem Shropshire. Tel. Whixall (Shropshire) (STD) 094872) 464/5

ORCHARD ELECTRONICS

I.C.s, TTL, C.Mos. Linear, Capacitors, Resistors, Diodes, LED, Thyristors, Zeners, Voltage Reg. DIL Sockets, Bridge Rectifiers, Potentiometers, Presets, Tracs, Diac, Plugs, Sockets, Cable, Vero. Carefully selected range. Excellent despatch service, same-day turn round.

S.A.E. List Orchard Electronics, Flint House, High Street, Wallingford, Oxon. Tel: 0491 35529.

LICENCE OFFERED

ACoustically ADJUSTABLE Loudspeakers. We wish to appoint licensees to manufacture the world's first Monitor Loudspeaker with acoustic adjustability.

IBM GOLFBALL 735 I/O TYPEWRITERS

Coding similar to EBDCIC. Will accept normal or sprocketed paper. Supplied in working order with photo copy of IBM interface manual.

As above but modified to take office range of golfballs £118 + 8% VAT (including new golfball) UK delivery by Securicor + packing £7.50 Overseas air freight or surface at cost.

RELAYS: Varley 2p c/o 185U: 65p (12p). Varley 2p c/o 280U: 65p (12p). PXB 2p c/o 1500U: 40p (12p).

PAPST (or similar) Fans 4 1/2 x 4 1/2 x 2 in 100 cfm 50/60 £3.50 (65p) c/s.

ELECTROLYTICS: 10 000 63V £1 (30p) 2 800 u 100V 70p (25p) 2240 u 100V 70p (25p) 4 000 u 35V 50p (20p) 2 000 u 50V 35p (11p) 4 000 u 70V 80p (25p) 10 000 u 16V 50p (20p)

EX COMPUTER PC PANELS 2 x 4" 50 boards £2.40 (62p). GH bulbs 12v 55w 60p (10p).

PIHER PRESETS 100mw. 220, 470, 1K, 4.7K, 10K, 47K, 100K, 220K, 12 for 50p (12p).

REED RELAYS 6v coil h/d contacts 5 for £1 (20p). Reed inserts h/d contacts 10 for £1 (12p).

TRANSFORMER 6v 500mA 75p (18p). TRANSFORMER 31v 330mA 60p (30p).

KEYTRONICS. Shop open Monday to Saturday 9.30 am - 2 p.m. 332 Ley Street, Ilford, Essex. 01-553 1863

THE SCIENTIFIC WIRE CO

Copper - Nickel - Chrome - Eureka - Litz - Manganin Wires. Enamelled - Silk - Cotton - Tinned Coverings. No minimum charges or quantities. Trade and export enquiries welcome. S.A.E. brings list. P.O. BOX 30, LONDON E4 9BW

CRYSTALS

Fast delivery of prototype and production quantities to your specification. EG. 100 KHz 0.005", HC13/0 £2.50 each £1.900 per 1,000.

VALVES WANTED

VALVES. Good prices. Types CV2797 CV2798, CV2792, CV2130, CV345, CV450. Phone 021-373 4357

EXCLUSIVE OFFER

WORLD-WIDE RANGE NEVER BEFORE OFFERED PHILCO HC-150 POINT-TO-POINT STRIP RADIO HF RECEIVERS 2/30 m/cs.

HIGHEST QUALITY 19" RACK MOUNTING CABINETS & RACKS

Table with columns: Our Ref, Height in ins, Width in ins, Depth in ins, Rack Panel Space in ins, Price.

OPEN RACKS

Table with columns: Our Ref, Height in ins, Channel Depth in ins, Panel Base in ins, Price.

We have a large quantity of 'bits and pieces' we cannot list - please send us your requirements, we can probably help - all enquiries answered.

- Belling Lee 75ft. Sky Tower, self supporting £475.00. Rhode & Schwarz 5BR sig gen. 1.6/2.4 gmc. £70.00. Airmec 702 sig gen 30 cyc/30 kcs. £26.00. Murrehad D669 Analysers. £70.00. S.E. 4000 System Units. P.U.R. Large Aerial Turning Units. P.U.R. Murrehad Hydraulic Relays. P.U.R. Layoue OS-62 Oscilloscopes 115V 15 m/cs. £65.00. S.T.C. Rxs 5 Receivers 0.5/25 0v m/cs Dual. £90.00. 45 feet Uniradio 4 Co-ax 50 ohms. £20.00. Stelma RTT Scopes. £20.00. Baluns Professional Exterior 600/75 ohms. £6.00. Telegraph Distortion Test Sets. £30.00. 25ft Telescopic Aerial Masts. £24.00. Advance LI Signal Generator 300/1000 m/cs. £70.00. Addo 5/8 Track Tape Punches. £48.00. Digital Cassette Recorders 1/2" 1000 bps. £250.00. OS-8 Oscilloscopes 115V. £30.00. 1600ft 16 m/m Film Spools ally (unused). £4.00. Quality electric Weather Vanes 8 contacts (unused). £15.00. Large Aerial Rotators for Coaxial. £18.00. B.N.C. Connectors 200 for. £42.00. Video Cross Hatch TV Generators. £17.00. Racal MA-175 I.S.B. Modulators (new). £45.00. Collins KWT-6 SSB Transceivers 500 watts 2/30 m/cs. P.U.R.

- Inside Cabinet Shelf Sliders. £3.00. DG7/32 and DG7/3 C.R.T. £3.00. Remscope Storage Scope with tracer. £15.00. M.V.R. Action Replay 20 sec. Videodisc Unit. P.U.R. Advance HI Signal Generators, 15/50Kcs. £18.00. Varian VA175EA Backward Wave Oscillators. P.U.R. Tally 5/8 Track Tape Readers 60 cps. £48.00. Tally 5/8 Track Tape Readers 120 cps. £65.00. 2 KVA Auto-Transformers. £22.00. 15 foot 12 inch Lattice Steel Mast Sections. £29.00. Cintel 2 KV Power Supplies. £35.00. Cawkill FU 4 Band Pass Filter Testers. £60.00. Avo Geiger Counters (new). £7.50.

We have a quantity of Power Transformers 250 watts to 15KVA at voltages up to 40KV. Best quality at low prices. Lists available.

- Racal RA-63 SSB Adaptors, new. £70.00. Racal RA-237 L.W. Converters, new. £70.00. 19" Blank Rack Panels 8 1/2 inch high, new. £1.00. Apoco Dial a Copy Photo Copier Electrostatic. £60.00. Hewlett Packard 524C Digital Counter. P.U.R. Portable Mains Battery Floodlights. £24.00. 400 channel Pulse Height Spectrum Analysers. £600.00.

We have a varied assortment of industrial and professional Cathode Ray Tubes available. List on request.

AUDIO AND INSTRUMENTATION-TAPE RECORDER-REPRODUCERS

- Plessey ID33 Digital Units, 7 track. Plessey M5500 Digital Unit, 7 tracks. Ampex FR-1100, 6 speeds, stereo 1/2". Ampex FR600, 4 speeds, 7 tracks 1/2". Ampex FR600, 4 speeds, 14 tracks 1/2". D.R.I. RM1, 4 speeds, 4 tracks 1/2". EMI TR90, 2 speeds, 1 track 1/2". EMI BTR1, 1 speed, 1 track 1/2". EMI R301G, 2 speeds, 2 tracks 1/2". Minicom CMP-100, 6 speeds, 7 tracks 1/2", 1/4". Leavers Rich DA-2P, 2 speeds, 2 tracks 1/2".

COMPUTER HARDWARE

- LINE PRINTER, High speed 1000 lines c.p.m. TAPE READER, High-speed 5/8 track 800 c.p.m. CARD READER 80 col. 600 c.p.m. Prices on Application. PLEASE ADD CARRIAGE AND V.A.T. AT APPROPRIATE RATE TO ABOVE.

P. HARRIS ORGANFORD - DORSET BH16 6BR BOURNEMOUTH, (0202) 765051 (5547)

GREENBANK ELECTRONICS (ESTABLISHED 1970). DIGITAL CLOCK MODULES, KITS. PHOSPHOR DISPLAYS. OP-AMPS. CLOCK CHIPS. IC SOCKET PINS. CMOS WITH DISCOUNTS. (Any mix disc 10 - 25 - 25% 100+)

ARTICLES FOR SALE

DIRECT COMMUNICATIONS

Division of Direct Electronics Ltd

INTERCOMMS & TELEPHONES

- New Italian Designed 2-Way Telephone Intercomm Wall/Desk with 30 metres cable. £19 95 (£1) Operates on 6 to 9v batt or power supply
- As above, 2- to 6-way Wall Model. £10 65 Desk model inc term block. £12 65 per inst 2- to 11-way wall model. £11 50 Desk inc term block £13 45 per inst (50p) Colours, ivory and grey blue
- Superior 2- to 6-way Siemens & Halske Wall Intercomm with desk conversion kit, term block and cord Per instrument £10 (packing and carriage 50p)
- Push-button Intercomms from 2- to 21-way with multi-channel and conference facilities New 6-way £24, 11-way £27, 16-way £30 21-way £35 Refurbished at half the above prices (£1 each unit)
- Entrance Phones Single unit + Internal Phone + Electric lock release + Twin Power Supply. £39 95 (£3) Add £7 for each additional button and Internal Phone up to 20-way (+ 50p per way)
- Transistorised 2-way Intercomm with 6v Power Supply and 50ft cable. £11 75 (£1)
- Transistorised batt-op 3-way Intercomm (Master - 2 subs) £23 95 (£1) 4-way (Master - 3 subs). £28 50 (£1)
- Wireless Intercomm (just plug 2 or more into mains - no wires required) £20 pair (£1). Ideal for baby alarm
- Automatic Instruments Strowger-compatible or PAX working New P O Types 706 and 746. £15 722 (Trumpphone). £41 65 Refurbished from £5 00 (£1) Also Special and Foreign types
- Ultra Modern Types Gondola (dial in hand set) £39 95 Charleston (Candlestick) moulded black £34 75. Leather covered red green or brown. £50 95 Electronic-button styles from £88 100 other superb Reproduction and Modern styles available in wood acrylic leather, onyx, etc. Come and see
- Plan and Key phones for Home and Export New or refurbished
- Telephone amplifier (1-way) £5.95 (35p) Hands-Free Tele Amp (two-way conversation) £9 50 (50p) With recording facility £12 50 (50p)
- Telephone terminal blocks 3-way 45p, 4-way 75p, 6-way £1 25, 24-way £2 75, 48-way £3 75 (20p)
- 95a Jack Sockets £1 50 (20p), 420 plugs £1 50 (20p) Less 10% per dozen
- Telephone cords 4-way to 9-way, 6ft 75p, 10ft £1 15 16ft £1 65 (15p)
- Telephone cable Per metre, 4-way 18p, 6-way 20p, 10-way 50p 13-way 56p (Add 10%) Paired cable also available up to 50 pair
- Intruder Alarm Microwave space protector Power Supply £25 (£1)
- ★ Mains Adaptors 6/7 5/9vdc, switched, £3 75 (50p) 3/4 5/6/7 5/9/12v, £5 (50p) Suit Transistor Radios, Cassette Recorders, Intercomms, etc
- Auto Exchange 10 extension + 1 circuit Power supply incorporated £175 (carr free)
- New Transformers Extensive range in stock or quick delivery Auto Isolating, H.V. Charger, Equipment, Output, etc 1 2 va to 6000 va (6Kva) from £1 70 Please enquire
- Ball point stretch pens, self-adhesive, attach to anything, anywhere, 95p (20p)
- Telephone locks with 2 keys, 95p (20)

Add VAT ● = 8% ★ = 25% on post paid price
TRADE ENQUIRIES WELCOMED

Many surplus bargains still available at exceptionally low prices All must be cleared
34 LISLE STREET, LONDON, WC2H 7BD - Tel: 01-437 2524

(5583)

Economise on Semiconductors

All prices include VAT - by return service

★ Lower price 741C

★ Lower price CMOS

		1+	10+	25+	TTL Mixed prices		CMOS Prices			
					1+	25+	1+	25+		
723C + data 14 pin DIL		70	68	64	7400	11	10	4000	16	15
741C + data 8 pin DIL		21	21	20	7402	12	11	4001	15	14
748C + data 8 pin DIL		34	33	31	7403	12	11	4002	15	14
LM308 + data 8 pin DIL		95	89	85	7404	13	12	4006	100	90
CA3046 14 pin DIL		80			7405	13	12	4007	16	15
TDA 1415 15V 450mA		70	68	65	7410	12	11	4008	95	88
BC107, 108, 109, 109C		10	10	9	7413	28	24	4009	45	42
BC182, 184		12	11.5	11	7430	11	10	4010	45	42
BC212, 214		13	12.5	12	7442	60	54	4011	15	14
HP 0.2" LED red + chip		20	19	18	7447	80	75	4012	15	14
HP 1/4" LED red		19	18	17	7473	28	24	4013	42	39
DIL low profile	8 pin	12	11	10	7474	30	26	4014	90	82
Sockets	14 pin	13	12	11	7475	30	26	4015	80	75
	16 pin	14	13	12	7486	28	24	4016	48	44
HP 5082-7740 red cc digit		170			7490	45	38	4017	83	78
MT 242CS 12-0-12 Transformer		130			7492	55	50	4023	15	14
					7493	42	39	4024	65	60
					74121	32	27	4025	15	14
								4027	45	42
								4028	78	71
								4030	45	42
								4040	90	84
								4046	110	102
								4049	45	42
								4050	45	42
								4068	16	15
								4071	15	14
								4078	16	15
								4081	15	14
								4507	90	85
								4511	130	120
								4520	112	103

BC177	21	2N3702	11	1N4002	4.5
BC179	22	2N3704	12	1N4004	6
BF244B	30	2N3708	8	1N4006	7
BPY51	15	2N3055	49	1N4148	4
BZY88C-3V3-15	11	1N914	4	1N4148(10off)	33
		1N4001	4		

AY-5-1224 16 pin digital clock IC + data + circuit	4.00
Clock IC + 4 HP 0.3" digits	10.00
Clock IC + 4 digits + transformer + transistors	11.50
TCA940 10W audio amp + data + circuit	1.90
TA0100 radio IC + IF filter + circuit	1.65
Carbon film high stab resistor 1/4W 5% E12 values 10ohm - 2M2, 1.1p ea., 10 for 10p, 100 90p same value	

All prices include VAT. P&P (UK) 15p, Overseas at cost. All goods new. Full spec. devices from Motorola, Mullard, TI, SGS, etc. Schools, colleges supplied on credit. By return service.

SILICON SEMICONDUCTOR SERVICES

41 Dunstable Road, Caddington, Luton LU1 4AL

(40)

DIOTESTOR IN-CIRCUIT TRANSISTOR TESTER



The DIOTESTOR detects faulty diodes and transistors when still in circuit without need for unsoldering.

BRITEC LIMITED

17 Devonshire Road, London SE23 3EN
Tel. 01-699 8844 Telex: 896161

5322

LINSLEY-HOOD 75 watt amplifier spares by return. BDY56 £1.65, BD529 55p, BD530 55p, 2N5457 35p, 2N5450 45p, BF528 35p, MP5A 40p, BFR39 25p, BFR79 25p, BC109C 12p, BC182L 10p, BC184L 11p, BC212L 12p, BC214L 13p, 1S920 5p, MC1310P £2.30. Interference suppression kit (also reduces preamp noise), with full instructions £1.35. Inclusive prices. P & P 10p. All components brand new and guaranteed. SAE for list. I. G. Bowman (Dept WW), 59 Fowey Avenue, Torquay S. Devon. (5586)


STEREO CASSETTE MECHANISMS. Similar to those used in low-noise cassette deck WW May. Choice of side or top loading. Complete with heads and full technical data. Send S.A.E. Box No. 5497.

CREED 54/N4 TELEPRINTERS in good condition, enquiries to:—D. M. Hogan, 7 Valley View, Landkey, Barnstable, Devon. Tel. Swinbridge 489. (5553)

VALVE OUTPUT transformers sectionalised silcor laminations, Kw 15 watts (Two) 4Kk 20 watts (Two), 15 OHM Secondaries. Offers. (5558)

MINUTEMAN

DIGITAL ELECTRONIC CLOCK

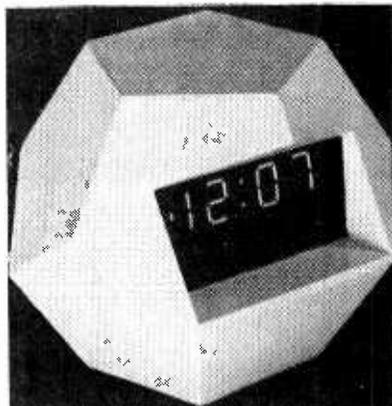

For the fastidious

A superior product featuring

- ★ UNIQUE DESIGN
- ★ LARGE LED DISPLAY
- ★ BRIGHTNESS CONTROL
- ★ PM INDICATOR
- ★ ALARM WITH SNOOZE FACILITY
- ★ PULSATING COLON

£16.50 plus VAT

Please send CWO to:



HEP ELECTRONICS
128 Greenstead Road, Colchester, Essex
Telephone: 0206 47188

(5595)

FOR SOUND SENSE BUDGET KITS

MIX WITH OR CUSTOM BUILT


PARTRIDGE ELECTRONICS

MANUFACTURERS OF AUDIO MIXERS, BIG AND SMALL, FOR ALL PURPOSES

21-25 Hart Road, Benfleet, Essex
Phone: (03745) 3256

QUARTZ CRYSTAL UNITS from

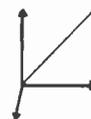- 1.0-96.0 MHz
- FAST DELIVERY
- HIGH STABILITY
- TO DEF 5271-A



WRITE FOR LEAFLET AT 1

MCKNIGHT CRYSTAL Co. Ltd.

HARDLEY INDUSTRIAL ESTATE, MYTHE, SOUTHAMPTON SO4 6ZY

TEL. HYTHE 848961
STD CODE 0703

FREQUENCY SYNTHESISER. Fluke model 6160A/DX 4-30 MHz in 1Hz steps brand new, boxed full spec. and price send s.a.e. Antenna tuning systems model A.T.S.-2 technical material corp. 2-30 MHz 1Kw continuous at 100% mod. Forward and reverse power. Measurement brand new boxed £100. Branson, 111 Park Road, Peterborough. (5598)

RECHARGEABLE NICAD BATTERIES. Pencil 'AA', 94p; sub 'C', £1.16; 'C', £1.92; 'D', £2.59; PP3, £4.48; Chargers for 'AA', sub 'C', £4.48; 'C' & 'D', £4.98; 'PP3', £3.98. Others. All prices includes VAT. Add 10% Post and package. S.A.E. for price list plus 25p for information booklet. Sandwell Plant Ltd., 1 Denholm Road, Sutton Coldfield, West Midlands 021-354 9764. (5566)

30 FERRUTTOR TAPE RECORDERS for sale. New 1968, 19 are in good order, 11 in need of some repair but all have been reasonably maintained. Make well-known for durability. Available South London from end of June. Offers and inquiries to Box WW 5568.

ARTICLES FOR SALE

OPPORTUNITY
SECOND HAND EDP HARDWARE
COMPUTERS (sold as peripherals or complete systems)
NCR 315 SYSTEM (with full software support) £9500 315-100 processor, 316-902/903 CORE MEMORY (10K/5K WORDS) 340-601 Buffered Line printer (1000 LPM), Three 353-3 CRAM-units, TP Communication adapter (TELEX) and 100 CRAM-DECK's
NCR 500 SYSTEM £1900 517-2 Processor/memory, 590-4 console, 551-1 printer card reader controller, 541-1 Line printer, 563-2 paper tape reader, 572-1 paper tape punch, 586-1 magn. ledger card reader
NCR 446 Billing machine system £1000. **FRIDEN 5010** £100 and **5015** £150 computer systems. **BURROUGHS E-1000** system £500
PERIPHERALS MDS 1320 £1000 NCR 541-1 £500 Line printers (as new) **ELLIOT 803** magn. film hand- lers £300, **NCR 361-1/561-1** paper tape readers £150, **NCR 362-1** paper tape reader £75, **NCR 586-1** magn. ledger and card reader £50, **MISC.** paper tape readers (Elliott D4/34) £25-100, **MISC.** paper tape punches 20-110 CPS £50-100.
DATA CAPTURING EQUIP- MENT MDS 1118 (NCR 735-801) magn. tape encoder (w. IBM GOLF BOLL Type Writer) £950, **NCR 171** add-machine +411 check digit verifier +461 paper tape punch £90, **NCR 16** add-machine +411 check digit verifier +461 paper tape punch £175, **NCR 468-1/468-3** card punch couplers £10/£15, **NCR 434** alpha couplers £10, **FACIT/OLLIVETTI** bookopp. mach. w paper tape punch £125.
AC CONVERTERS 50 to 60 cyc- les up to 50 KVA.
 Two complete **ELLIOT 803** COMPU- TERS are available in parts.
 Skandinavisk
DATA-AUTOMATION AB
 S: Mickelsgatan 79
 S-126 54 Hägersten Sweden (5581)

ULTRASONIC REMOTE CONTROL SWITCH
 £13 below list price
 By pointing the transmitter at the receiver, mains appliances (TVs, radios, lights, etc.) can be switched on/off. 600 watt max. Range up to 40ft.
ONLY £12.95 + 65p P&P
C.3025 TRANSISTOR CHECKER
 - miniature, neat, compact checker for germanium and silicon transistors - PNP/NPN flick switch selection rotary settings for β and I_{CO} factors.
 Panel meter. 9v internal battery. Quick check socket.
 Metal case. List price £9.55 - Our price £3.95 plus 35p P&P.
 (Dept WW), Box 60
J.E.C. Crawley SUSSEX RH11 7UF

SOWTER TRANSFORMERS
 FOR SOUND RECORDING AND REPRODUCING EQUIPMENT
 We are suppliers to many well-known categories, studios and broadcasting authorities and were established in 1941. Early deliveries. Competitive prices. Large of small quantities. List on quote.
 A recent release
SOWTER TYPE 3670 MULTITAP MICROPHONE TRANSFORMER
 Primary windings for 400 ohm, 200 ohm and 60 ohm with Secondary loadings from 24 ohm to 10 K ohm. Frequency response plus/minus ± 0.25 db to 25 KHz. Encased in well finished Munsell box. 20mm diameter by 22mm high, with colour coded red leads. Low distortion. DELIVERY (small quantities) EX STOCK. HEAVY COMPETITIVE PRICE. FULL DETAILS ON REQUEST.
E. A. SOWTER LTD.
 Transformer Manufacturers and Designers.
 7 Daulham Place, Fove Street
 Ipswich IP4 1JP. Tel. 0473 62794 (5216)

Quartz Crystal Units
 ACCURATE RELIABLE
 Private enquiries, send 1 Op in stamps for brochure
THE QUARTZ CRYSTAL CO. LTD.
 QCC WORKS, WELLINGTON CRESCENT
 NEW MALDEN, SURREY TW20 0JZ 0314 & 2988

VACUUM is our speciality, new and secondhand rotary pumps, diffusion outfits, accessories, coaters, etc. Silicone rubber or varnish out-gassing equipment from £40. V. N. Barrett (Sales) Ltd., 1 Mayo Road, Croydon. 01-684 9917. (24)

C.R.T. REGUNNING PLANT. New and secondhand reconditioned training, demonstration, colour or B/W Barretts, Mayo Road, Croydon, Surrey, CRO 2QP. (36)


QUANTITY OF MARCONI SIGNAL GENERATORS, type TF144G. £25 each. Cash with order. Carriage forward. - Contact Neil Broady, Ascot (Berks) 23422. Office hours. (5369)

16MM B & H 631 Sound projectors c/w speaker and transformers £135. - Hilton Cine, 9 West Hill, Dartford -T. 20009. (15)

FOR SALE-24 Pye "Ranger" and 19 Pye "Vanguard". Mobile Radio Sets with associated equipment consisting of 38 Control Units (17 with speakers), 16 separate speakers and 40 microphones. Equipment does not comply with current Government specifications and is scrap. Offers to The Chief Constable, Police H.Q., Dumfries, by 31st May, 1976. (5570)

NEW PEAK PROGRAMME METER
 A PPM drive circuit with standard performance. Manufactured under licence from the British Broadcasting Corporation it is based on the ME12/9 but with the addition of our electronic floating input circuitry which will withstand mains or static voltages on the signal line.
 Intended for use in the most critical monitoring applications it possesses excellent temperature and long term stability. Meeting BS4297 the proposed revision of BS4297 and the proposed new IEC Type 2 meter specifications it also fulfills the requirements of the IBA EBU and BPO.
 The circuit board is designed to mount on the rear of the meter movement and it accepts balanced or unbalanced signal inputs at line level. The sensitivity may be increased by 20dB and the supply requirement is 24V at 30mA either polarity or earth free.
ERNEST TURNER 642 and **643** meter movements stocked with 1/7 and -2/7 & 4 scalings
 Ring or write for leaflet with specifications and photographs

COLOUR, UHF AND TV SPARES. Lists on request. "Wireless World" TV Tuner and FM Tuner Projects by D. C. Read. Kits of parts available. **JAPANESE SOLID STATE COLOUR CHASSIS** for the experimenter. Includes IF, Decoder, CDA, Timebases, Output stages, etc. Incl. circuit. Brand new. £20 p/p £1.50. New Cross Hatch kit, Aerial Input type. No other connections. Battery operated, portable. Incl. Sync & UHF Modulator units £11* Add-on Grey Scale kit, £2.90* p/p 45p. CRT Reactivator kit for colour and mono. £17.48* p/p 80p. Signal Strength Meter kit £18*. p/p 70p. 625 TV IF Unit, for Hi-Fi amps or tape recording £6.80 p/p 65p. Decca Colour TV Thyristor Power Supply Unit, incl. H.T., L.T., etc. Incl. circuits £3.80 p/p 95p. Bush CTV 25 Power Supply Unit, incl. H.T., L.T., etc. £3.20 p/p £1.20. Bush CTV 25 Convergence panel plus yoke, blue lateral £3.60 p/p 80p. Philips single stand convergence units complete, incl 16 controls, £3.75 p/p 75p. Colour Scan Coils, Mullard or Plessey £6 p/p 80p. Mullard AT1023/05 or Plessey Converg. Yoke £2.50 p/p 55p. Mullard or Plessey Blue Laterals 75p p/p 30p. BRC 3000 type scan coils £2 p/p 80p. Bush CTV 25 Scan Coils £2.50 p/p 80p. Delay Lines: DL20 £3.50 DL40 £1.50 DL1E, DL1 85p p/p 40p. Lum. delay lines 50p p/p 30p. Bush/Murphy CTV 25 3/174 EHT quadrupler £8.50 p/p 75p. Special offer colour triplers, ITT TH25 1TH £2 GEC 2040 £1.75 p/p 50p. Philips G8 Panels, part complete, surplus/salvaged: Decoder £2.50, IF incl. 5 modules £2.25, T. Base £1 p/p 70p. CRT Base 75p p/p 30p. GEC 2040 Decoder panel for spares £3.50 p/p 70p. VARICAP TUNERS. UHF: ELC 1043 £4.20. ELC 1043/05 £5. VHF: ELC 1042 £5.50. Philips VHF £3.80. Salvaged UHF & VHF Vari- caps £1.50 p/p 35p. SPECIAL OFFER: RBM 6 psn. Varicap control unit £1 p/p 35p. UHF Tuners transd. incl. slow motion drive £3.80. 4 Psn. and 6 Psn. push button transd. £4.20 p/p 70p. Philips. Bush. Decca integrated UHF/VHF transd. tuners £4.50 p/p 80p. Thorn 850 dual stand, time base panels 50p. Philips 625 IF panel incl. cct. 50p. p/p 65p. VHF Turret tuners AT 7650 for KB Featherlight. Philips 19TG170, GEC 2010, etc. £2.50. Pye miniature incremental tuners £1. Fireball tuners, Ferguson, HMV, Marconi 80p p/p all tuners 70p. Mullard Mono scan coils for Philips, Stella, Pye. Ekco. Ferranti, Invicta £2 p/p 70p. Large selection LOPTS, FOPTS available for most popular makes MANOR SUPPLIES, 172 West End Lane, London, N.W.6. Shop premises. Callers welcome. (Nos. 28, 159 buses or West Hampstead-Bakerloo Line and British Rail). Mail Order: 64 Golders Manor Drive, London, N.W.11. Tel: 01-794 8751. V.A.T. Please Add 12% TO ALL PRICES (EXCEPT WHERE MARKED * VAT 8%). (60)

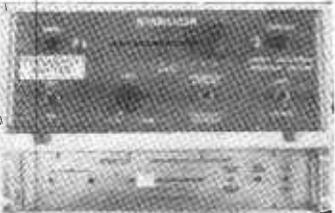STABILIZER
 FOR HOWL REDUCTION, BALANCED AND UNBALANCED VERSIONS BOXED OR RACK MOUNTING
PUBLIC ADDRESS : SOUND REINFORCEMENT

+ 5Hz Fixed Shift Circuit Boards for WW July 1973 article.
 Small enough to be built inside the cabinets of many amplifiers
 Complete kit and board £24 including PSU & designer DESIGNER Board built and aligned £31 mains transformer approved APPROVED
SPECTRUM SHIFTER
 Variable shifts 0.1 - 1000Hz for weird special effects on speech or music
SURREY ELECTRONICS
 The Forge, Luck's Green, Cranleigh
 Surrey GU6 7BG (STD 04866) 5997
 CASH WITH ORDER less 5%
 UK POST FREE ADD VAT at 8%

VHF-UHF MANUAL
 by D. S. Evans. Price £5.60
ELECTRONICS POCKET BOOK by P J McGoldrick PRICE £4.00
SERVICING WITH THE OSCILLOSCOPE by G J King PRICE £4.80
99 WAYS TO KNOW & USE YOUR ELECTRONIC CALCULATOR by L E Frenzel PRICE £4.00
MINICOMPUTERS & MICRO-PROCESSORS by M Healey PRICE £6.65
LINEAR INTEGRATED CIRCUIT APPLICATIONS by G B Clayton PRICE £4.80
SOLID-STATE DEVICES MANUAL by RCA PRICE £3.50
PRINCIPLES OF TRANSISTOR CIRCUITS by S W Amos PRICE £4.25
FOUNDATIONS OF WIRELESS & ELECTRONICS by M G Scroggie PRICE £4.35
HANDBOOK OF DATA COMMUNICATIONS by N C C PRICE £9.00
THE ELECTRONIC MUSICAL INSTRUMENT MANUAL by A Douglas PRICE £8.00
 * ALL PRICES INCLUDE POSTAGE * (44)

THE MODERN BOOK CO
 SPECIALISTS IN SCIENTIFIC & TECHNICAL BOOKS
 19-21 PRAED STREET
 LONDON W2 1NP
 Phone 723 4185
 Closed Sat. 1 p.m.

SAVE IT BARGAIN
500 WATT DIMMER SWITCH
 (not suitable for fluorescent lights)
 Basic Module with 1" Knob £2 00
 Complete on MK switch plate £2 50
 Large 2" knob (BULGIN) 25p extra. P&P 25p
 Please add 8% VAT to all orders inc P&P
FRASER-MANNING LTD.
 40 TUDDENHAM ROAD, IPSWICH IP4 2SL (35)

WE INVITE ENQUIRIES from anywhere in the World. We have in stock several million carbon resistors 1/4, 1/2, and 1 watt. 1/2 million wire wound resistors 5 and 10 watt - 1 million capacitors - 1 million electrolytic condensers - 1/2 million transistors and diodes, thousands of potentiometers, and hosts of other components. Write, phone or call at our warehouse - Broadfields & Mayco Disposals Ltd., 21 Lodge Lane, N. Finchley, London, N.12. 01-445 0749, 445 2713. (5097)

PRINTED CIRCUIT BOARDS. High quality, fast deliveries. - Photo-techniques, 11 Old Witney Road, Eynsham, Oxford. Tel. Oxford (0865) 880845. (5525)

60 KHz MSF RUGBY RECEIVERS. BCD TIME-OF-DAY OUTPUT. High performance, phase locked loop radio receiver. 5V operation with LED indication. Kit complete £9.50; assembled and tested unit £11.12 (prices include postage and V.A.T.) Also available low power receiver with signal and audio outputs. Send for details Toolex, Sherborne (4359) Dorset. (21)

DIGITAL CLOCK CHIP, AY-5-1224, with data and circuit diagram. £3.66 plus VAT. 'Jumbo' LED digits (16mm high) type economy DL/747 only £2.04 each plus VAT, post free. Greenbank Electronics, 94 New Chester Road, Wirral, Merseyside L62 5AG. (83)

ARTICLES FOR SALE

MARCONI TF 885A/1 VIDEO OSCILLATOR 50 c/s to 12 Mc/s 31.6 Volt Max O/P, £85; **Marconi TF B45/1** 10 Mc/s Digital Counter with TM 5953 Plug In, £40; **Solartron AT 203 DC** to 300 Kc/s Calibrating Unit, £10; **Advance Millivoltmeter Type 77** 15 cps to 4.5 mc/s, £32; **Dawe Transistor Phase Meter Type 830A** Battery/Mains, £30; **Marconi Wave Analyser TF455E** 0.16 kc/s 4 cps Bandwidth, £90; **Marconi Universal Mridge Type TF868/1**, £60; **Solartron Oscilloscope CD523 S**, £45; **Advance "Q" Meter Type TT1** 100 Kc/s to 100 Mc/s Q Range 10 to 400, £85; **Dawe Audio Oscillator type 440A** 20 c/s to 200 Kc/s 600 or 15 ohms output, £35; **Health-kit Variable Power Supply Stabilized** 100 to 350v 150 MA max £30; **Solartron Digital Voltmeter LM902.2** 0.1 volt to 1000v 4 digits, £35; **Advance Transistor Tester TTI/s** tests diodes and NPN PNP transistors, £15; **Advance B4B5 A.M. Signal Generator**, £35; **Nagard 5002 Double Pulse Generator** + or - 0.50 volt max single shot 0.1 c/s 1 mc/s, £40; **Dawe True R.C.S. Voltmeter Type 612A** 0.4 mv to 300 volt P.S.D., £30; **Tektronix Type G** and **Type L Plug-ins**, £29 **Muirhead Facsimile Xmitter MD901 AM/MH**, £50; **Muirhead Tunable Filter, D925A**, £20; **Muirhead Phasemeter D729AM**, £50; **Muirhead Phasemeter D729BM**, £30; **B.P.L. electrolytic bridge CB154/D3**, £30; **S and H power oscillator Type 48**, £20; **S and H rejector V.V. Type 64**, £20; **Solartron Phasemeter VP 250**, £45; **Brandenburg H.V. P.S.U. S0530/8**, £60; **U.H.F. Siggen 370-560 Mhz**, £20; **Pulse Generator, AN/UPM15**, £35; **Vibron electro-mechanical 33B/2**, £25; **Cossor CDU 110 Oscilloscope**, £220; **Dawe ULF Oscillator 0.01Hz 1KHz 90 degrees** and **Ref phase O/P terminals**, £30; **Lapmaster monochromatic light unit**, £25; **Gertsch complex ratio bridge CRB B1 mint**, 6 decades phase 4 real, £300 **Wayne Kerr Mod/Demod nit SA400**, £35; **Wayne Kerr transfer function computer**, £200; **Airmec 853 wave analyser** 30 Khz to 30 Mhz, £65; **Cossor Motor driven oscilloscope camera unit**, £60; **Marconi D.F.M. T.F. 142E**, £25; **Solartron Synchro test unit JM 355.2**, £40; **B.P.L. Megometer RM175-LZ MK2**, £30; **Teletype 33C Amp plug-in unit**, £20; **Polaroid oscilloscope camera unit**, £60; **P.S.U. A.P.T. fully stabilised 20V at 10 Amps**, £14. **Terms C.W.O., V.A.T. at 8 per cent and postage.** "Q" Services Electronic (Camberley) Ltd., 29 Lawford Crescent, Yateley Camberley, Surrey (0252) 871048. (5557)

PHOTO ETCH LIMITED

9 LOWER QUEEN STREET
PENZANCE, CORNWALL
TR18 4DF

Prototype or long run — we will supply your printed circuit requirements
Also facilities for Design, Assembly and Test
Prompt and efficient service assured

Contact David Webster
PENZANCE (0738) 4472

EQUIPMENT WANTED

**BROADFIELDS AND
MAYCO DISPOSALS**

21 Lodge Lane, N. Finchley
London, N12 8JG
Telephone:
01-445 0749 01-958 7624

MAY WE ASSIST YOU TO DISPOSE OF YOUR SURPLUS AND REDUNDANT STOCKS?

We will call anywhere in the British Isles, and pay SPOT CASH for Electronic Components and Equipment. (5330)

ARTICLES WANTED

WANTED IN LARGE QUANTITIES

Electronic components: resistors, capacitors, potentiometers, chassis loudspeakers, semi-conductors, diodes, TV tubes, especially colours, etc., etc., etc.
Finished or incomplete products record players, amplifiers, radios, tuners, tape recorders, enclosures, etc., etc., etc.
We will buy complete factories and pay cash.

TEL. 01-491 4636
E.C.E. AVON HOUSE
360/366 OXFORD STREET
LONDON, W.1 (5552)

WANTED, all types of communication receivers and test equipment. Details to R. T. & I. Electronics Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley 4986. (63)

CASH AVAILABLE for purchase of surplus R.F. Power transistors and components of VHF/UHF interest. Convert your surpluses to cash. (5567)

SURPLUS COMPONENTS, Equipment and Computer panels wanted for cash. Ring Southampton 772501. (16)

WANTED, Agent to purchase Mono and Colour T.V.'s transistor radios; vacuum cleaners, washing machines, cookers, etc. New and second-hand. Box No. 5328.

LISTS OF SURPLUS electronic components from business selling same. Write Malloy W.G.M. Electronics, 66 Woodvale Avenue, Belfast. BT13 3EX, N. Ireland. (5601)

COURSES

The Polytechnic of North London

Why not a Career in Electronics?

The electronics industry is the fastest growing industry in the country. Expansion averages 20% per year, and to help this expansion qualified technicians and engineers are needed.

* With two "A" levels, ONC, or equivalent, you could become a

Chartered Electronic and Radio Engineer

Write for details of our three-year full-time CNAA degree course in Electronic and Communications Engineering. * With three "O" levels, City and Guilds Part I, or equivalent, you could become a

Professional Technician Engineer (CEI)

Write for details of our two-year full-time course in Electronics.

Department of Electronic and Communications Engineering, Polytechnic of North London, Holloway N7 8DB. Tel. 01-607 6767. (5542)

RADIO and Radar M.P.T. and C.G.L.I. Courses. Write: Principal, Nautical College, Fleetwood, FY7 8JZ. (25)

★ MINICOMPUTERS ★ PERIPHERALS ★ INSTRUMENTATION

For fastest, best CASH offer, phone

COMPUTER APPRECIATION
Godstone (088 384) 3106

WE BUY new valves, transistors and clean new components, large or small quantities, all details, quotations by return. — Walton's, 55 Worcester St., Wolverhampton, (62)

REQUIRED from Ministry of Defence and other sources Plessey models P.T.R. 371, also 691, 692 and 693. Please post fullest details to John F. Learney, 16 Pine Walk, Carshalton Beeches, Surrey. (5226)

B-D ELECTRONICS offer prompt settlement for your surplus components. Our main field of interest is consumer electronics. Please telephone our Miss Hughes, Sandy (0767) 81616. (22)

NEW GRAM AND SOUND EQUIPMENT

GLASGOW, Hi Fi, Cassette Decks, Tape Recorders, Video Equipment, always available we buy, sell and exchange for Hi Fi sets and photographic equipment. **VICTOR MORRIS Audio Visual Ltd.**, 340 Argyle Street, Glasgow, G1, 8/10 Glassford Street, Glasgow, G1, 8/10 Sauchiehall Street. Tel: 041-221 8958. (11)

TAPE RECEIVERS

RECORDS MADE TO ORDER

DEMO DISCS MASTERS FOR RECORD COMPANIES	VINYLLITE PRESSINGS
---	------------------------

Single disc, 1 20. Mono or Stereo, delivery 4 days from your tapes. Quantity runs 25 to 1,000 records PRESSED IN VINYLITE IN OUR OWN PLANT. Delivery 3-4 weeks. Sleeves/Labels. Finest quality NEUMANN STEREO/Mono Lathes. We cut for many studios UK/OVERSEAS SAE list

DEROY RECORDS

Eastwood Cove, Dunbartonshire
Scotland

HRO Rx5s, etc., **AR88**, **CR100**, **BRT400** **G209**, **S640**, etc., etc., in stock. R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E11. Ley 4986. (65)

SIGNAL Generators, Oscilloscopes, Output Meters, Wave Voltmeters, Frequency Meters, Multi-range Meters etc., etc. in stock. R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley 4986. (64)

SERVICES

AUDIOMASTER BACKGROUND MUSIC service, sales. Tape programmes. P. J. Equipments, 3 Onslow Street, Guildford 4801. (12)

THOR-HOLE CONVENTIONAL P.C.B.'s gold plating, roller tinning, prototypes, silk screening, drilling. All or part service. — **ELECTRO-CIRCUITS (P.C.) LTD.**, Delamare Road, Cheshunt, Herts. Tel. Waltham Cross 38600 or 20344. (84)

LABELS, NAMEPLATES, FASCIAs on aluminium or plastic. Speedy delivery G.S.M. Graphic Arts Ltd., 1-5 Rectory Lane, Guisborough (02873-4443), Yorks, U.K. (5305)

TUBE POLISHING, scratched faces on your tubes can be repaired for £8.88 total cost. V.A.T. and return carriage included. — **Retube Ltd.**, North Somercotes, Louth, Lincs. — Phone N/S 300 (Std. 050785).

CAPACITY AVAILABLE

A.A.A. SERVICE

Small batch production wiring, assembly to sample or drawings. Specialists in printed circuit assembly Cableforms to order. Rock Electronics, 42 Bishopfield, Harlow, Essex. Tel. Harlow (0279) 33108. (19)

STOVE ENAMELLING, Single items or production runs. Gloss, hammer or acrylic finish. We also manufacture complete units of electronic equipment. Wiring, p.c. boards, cases. **Olson Electronics Ltd.**, 5 Long Street, London E2. 739-2343. (5394)

FINE SPOT WELDING, coil winding, soldering, mechanical and electrical assembly, light sheet metal and presswork. Contact — **Webson (Manchester) Ltd.**, Shentonfield Road, Sharston, Industrial Estate, Manchester 22. (5376)

A.A.A. SERVICE, Small batch production wiring, assembly to sample or drawings. Specialists in printed circuit assembly. Cableforms to order. **Rock Electronics Ltd.**, 42 Bishopfield Harlow, Essex, Tel. Harlow (0279) 33018. (19)

AIRTRONICS LTD., for Coil Winding — large or small production runs. Also PC Boards Assemblies. Suppliers to P.O., M.O.D., etc. Export enquiries welcomed, 3a Waterland Road, London SE13 7PE. Tel: 01-852 1706. (61)

DESIGN, development, repair, test and small production of electronic equipment. Specialist in production of printed circuit assemblies. **YOUNG ELECTRONICS LTD.**, 184 Royal College Street, London NW1 9NN. 01-267 0201. (20)

BATCH Production Wiring and Assembly to sample or drawings. **Deane Electricals**, 19B Station Parade, Ealing Common, London, W.5. Tel: 01-992 8976. (23)

CAPACITY available to the Electronic Industry. Precision turned parts, engraving, milling and grinding both in metals and plastics. Limited capacity available on Mathey SP33 jig borer. Write for lists of full plant capacity to C.B. Industrial Engineering Ltd., 1 Mackintosh Lane, E9 6AB. Tel: 01-985 7057. (14)

PRINTED CIRCUIT BOARDS — Quick deliveries, competitive prices, quotations on request, roller tinning, drilling, etc., speciality small batches, larger quantities available **Jamiesons Automatics Ltd.**, 1-5 Westgate, Bridlington, N. Humberside, for the attention of Mr. J. Harrison. Tel: (0262) 4738/77877. (18)

SERVICES

PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors hardware Aluminium sheet and sections Printed circuit board, top quality for individual or published designs

Prompt service
Send 15p for catalogue


RAMAR CONSTRUCTOR SERVICES

Masons Road, Stratford-on-Avon
Warwicks. Tel: 4879

EURO CIRCUITS

Printed Circuit Boards — Master layouts — Photography — Legend printing — Roller tinning — Gold plating — Flexible films — Conventional fibre glass — No order too large or too small — Fast turnaround on prototypes All or part service available NOW

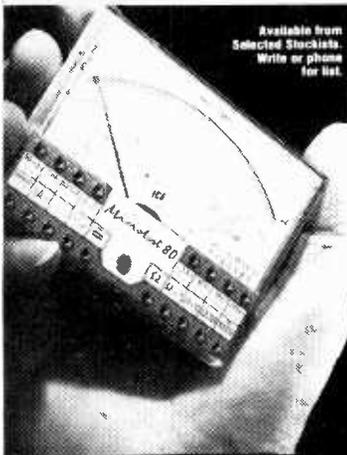EURO CIRCUITS TD.
Highfield House
West Kingsdown
Nr. Sevenoaks, Kent. WK2344



Available from Selected Stockists. Write or phone for list.

INCREDIBLE VALUE IN PRECISION TEST METERS

MICROTEST 80 — I.C.E.

20,000 OHMS/VOLT 40 RANGES
 20 000 ohms/Volt 4 000 ohms/Volt (AC) 2% accuracy
 V DC 100mV to 1KV (6 Ranges) 1 DC 50-A to 5A (6 Ranges)
 V AC 1.5V to 1KV (5 Ranges) 1 AC 250-A to 2.5A (5 Ranges)
 Ohms Low ohms ohms x 1 ohms x 10 ohms x 100
 Power Output Measurements 1.5V to 1000V (5 Ranges)
 + 6dB to 62dB (5 Ranges)
 Capacitance 25-F to 25 000 -F (4 Ranges)
 1000 times overload protection (on Ohm ranges)
 Meter movement diode protection
 Size (without case) 90 x 70 x 18 mm
 Electronic zero non-parallax mirror scale Unbreakable carrying case and probes supplied
 Full After Sales Service available
 Price **£14.50**, Post & Packing 50p VAT @ 8% £1 20 SEND TOTAL £16 20

SUPERTESTER 680R — I.C.E.

20,000 OHMS/VOLT 80 RANGES
 20 000 ohms Vch 1 1/2 DC 2 A C V DC 100mV to 2KV (13 Ranges) V AC 2 to 2KV (11 Ranges) 1 DC 50-A to 10A (12 Ranges) 1 AC 250-A to 5A (10 Ranges) R x1 x100 x1000 x10 000 and Low ohms Detector Reactance 0.10 M ohms Freq. Measurement 0-5000 Hz (2 Ranges) Power Output 10 2000V (9 Ranges) Decibels -24 + 70 dB (10 Ranges) Capacitance 0-500 000 pF (2 Ranges using mains supply) 0-20 000 -F (4 Ranges using internal 3 Volt battery) 1000 times overload protection on ohms ranges, and meter movement diode protection 10 Fields of Measurement and 80 ranges Size 128 x 95 x 32 mm Non parallax mirror scale Unbreakable carrying case supplied which contains probes mains lead crocodile clips and shorting link



Price **£22.50**
 Post & Packing 75p
 VAT @ 8% £1 86
 SEND TOTAL £26 11

ACCESSORIES FOR 680R AND MICROTEST 80 (EXTRA) (if orders from not visible on Microtest 80)
 AMPERELAMP A.G. 7.5A to 500A (6 Ranges) 3% £13.50 H.V. PROBE MOD. 18: 25KV (MAX I.P.Z. = 500 M ohms (Nom) £5.99 LIGHT METER PROBE MOD. 24: 2 — 20 000 Lux £13.50 RESISTANCE MULTIPLIER MOD. 25: Multiplying Factor x 100 000 R. Range (with 680R) 0 — 100M £5.95 GAUSSMETER PROBE MOD. 27: 0-15 Kilogauss £12.50 PHASE SEQUENCE INDICATOR MOD. 28: 100-400V (A.C.) 50-60 Hz £5.95 D.C. CURRENT SHUNTS MOD. 32 SERIES: 10A 25A 50A and 100A £5.50 each TEMPERATURE PROBE MOD. 36: -50° C to + 200° C £12.50 SIGNAL INJECTOR MOD. 63: Basic O/P Frags 500KHz and 1KHz £5.95 CURRENT TRANSFORMER MOD. 616: 250mA to 100A £2.50 TRANSISTOR TESTER 662 I.C.E. hfe 5 000 000 Measures Icbo, Iebo, Icco, Ices, Vce sat, Vbe, hfe, VF and IR £12.50 ELECTRONIC VOLTMETER 660: Full spec request £39.50 AMPEREST 660: £39.50 Add 50p Post & Packing, plus VAT (8%) to all above prices.

Sole Importers and Distributors

ELECTRONIC BROKERS LTD.

49-53 Pancras Road, London NW1 2QB
 Tel: 01-837 7781

WW — 070 FOR FURTHER DETAILS

INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 123-135

Acoustical Mfg. Co. Ltd.	PAGE 3	Gardners Transformers Ltd.	PAGE 7	Quality Electronics Ltd.	PAGE 111
Aero Electronics Ltd.	22	Grampian Reproducers Ltd.	8	Radford Laboratories Ltd.	19
Alice (Stancoil) Ltd.	16	Greenwood Electronics Ltd.	7, 22	Radio Component Specialists	91
All Things Are Possible	21	Hall Electric Ltd.	2	Ralfe, P.	99
Ambit International	17	Harmsworth Townley & Co. Ltd.	Readers Card	Rank Film Equipment	23
A.S.P.	113	Harris Electronics (London) Ltd.	8, 22	R.C.S. Electronics	11
Audio Amateur	103	Harris, P.	131	R.I. Audio	23
Audix Ltd.	9	Hart Electronics	86	Rotex	20
Avel-Lindberg	11	Hatfield Instruments Ltd.	70	R.S.T. Valves Ltd.	109
Barrie Electronics Ltd.	99	Henry's Radio Ltd.	86	Samsons (Electronics) Ltd.	100
Bentley Acoustic Corp. Ltd.	107	H/H Electronic	16	S.C.S. Components	102
B.H. Component Factors Ltd	122	Hightech Components	9	Semiconductor Supplies Ltd.	Loose insert
Bi-Pak Semiconductors Ltd.	104, 105	Hoymitz Electronics Ltd.	24	Semicon Indexes Ltd.	19
Bi-Pre Pak Ltd.	93	Icon Designs.	13	Service Trading Co.	115
Boss Industrial Mouldings Ltd.	18	Intech Products Ltd.	17	Servo & Electronic Sales Ltd.	111
Bradley, G. & E. Ltd	Cover iii	Industrial Instruments	119	S.G.S.-Ates (U.K.) Ltd.	25
Brenell Eng.	19	Industrial Tape Applications Ltd.	15	Shure Electronics Ltd.	28
Bull, J., Electrical, Ltd.	106	Integrex Ltd.	84, 85	Sintel	92
Cambridge Learning	96	I.P.L. Electronics Ltd.	98	S.M.E. Ltd.	5
Carston Electronics	120	Jackson Bros. (Ldn.) Ltd.	96	Special Products Ltd.	10
Catronics.	113	Kinnie Components Ltd.	89	Strumech Eng. Ltd.	14
Chiltmead Ltd	120	Klark Teknik Ltd.	14	Sugden, J. E. & Co. Ltd.	13
Chromasonic Electronics	100	Leads Instruments Ltd.	20	Surrey Electronics Ltd.	133
Colomor (Electronics) Ltd.	88	Leeds University	114	Swanley Electronics Ltd.	103
Combined Precision Components Ltd.	87	Levell Electronics Ltd.	1	Swift of Wilmslow	24
Computer Sales & Service	108	Lloyd J. J. Instruments Ltd.	4, 18	Technomatic Ltd.	112
Condor Electronics Ltd.	24	Lynx (Electronics) London Ltd.	102	Teleprinter Equipment Ltd.	14
Datong Electronics Ltd.	13	MacInnes Laboratories Ltd.	15	Teleradio Hi-Fi.	109
Dema Electronics International	103	McLennan Eng. Ltd.	20	Trampus Electronics	90
Direct Electronics Ltd.	132	Maplin Electronic Supplies	97	Valradio Ltd.	12
D.M.W. Associates (Electronics) Ltd.	18	Marconi Instruments Ltd.	Cover ii	Wavetek Electronics Ltd.	83
Dolby Noise Unit	84, 85	Marshall, A., & Sons (London) Ltd.	88	West Hyde Developments Ltd.	107
Dymar Electronics Ltd.	6	Mills, W.	90	Wilkinson, L. (Croydon) Ltd.	112
Eagle International Ltd.	16	Modern Book Company	133	Wilmot Breeden Electronics Ltd.	4
Electronic Brokers Ltd.	116, 117, 136	Motorola Electronics Ltd.	12	Wilmslow Audio	122
Electronic Windings (Ldn) Ltd.	22	Multicore Solders Ltd.	Cover iv	Wireless World Circards	110
Electromite Ltd.	113	Natural Sound Systems Ltd.	69	Wireless World Circuit Designs	121
Electrovalue Ltd.	86	Nicholls, E. R.	23	W.K. Electronics	101
Empire Exporters Inc.	122	Nombrex Ltd.	24	Z. & I. Aero Services Ltd.	10, 22, 92
English Electric Valve Co. Ltd.	8, 26	North East Audio Ltd.	12	Zettler (U.K.) Division	12
Farnell Instruments Ltd.	10	OMB Electronics	11		
Fi-Comp Electronics	114	Physical & Elec. Labs. Ltd.	109		
Fitch Tape Mechanisms	114	Plessey Distributors	70		
Forgestone Colour Developments Ltd.	120	Powertran Electronics	94, 95		
Future Film Developments Ltd.	112	Precision Petite Ltd.	20		
		Pronto Electronics Systems Ltd.	108		
		Pulse Electronics Ltd.	9		

A hand is holding a white tag with various brand logos. The tag is positioned in front of a piece of electronic equipment, possibly a test meter, which has a large circular dial and several buttons. The background is a light-colored surface.

We're experts on all of these



For the Great Names a Great Service

Bradley Electronics are well known as manufacturers of precision electronic instrumentation. But there's another important aspect of our business – we're also experts on other people's products.

For 21 years our Services Division has been providing a first-class repair and recalibration service for all types and makes of electronic test and measuring equipment – from simple meters to complicated systems. *Any* manufacturer's instrument in the frequency range DC to 18 GHz – and to

36 GHz in some cases – collected and delivered back to your door ready to plug-in.

The Services Division has its own 35,000 sq ft factory, expert staff, comprehensive spares, and a Standards Laboratory approved by the British Calibration Service. It will supply calibration certificates for AC, DC and RF measurements. And, of course, our standards are directly traceable to NPL and NBS.

So – when your calibrator won't calibrate anymore, your generator

refuses to generate, or your counter stops counting – you know who to contact.

G & E BRADLEY LIMITED
Electal House, Neasden Lane,
London NW10 1RR
Telephone: 01-450 7811
Telex: 225583

A Lucas Company

BRADLEY
electronics

8 MILL Lane

Multicore Solder Creams are oxide free!

Multicore's newest solder creams are designed specifically for hybrid microcircuits P.C.B's and critical component joints. Unlike ordinary creams - which suffer from the problem of oxide around each atomised solder powder particle - they're completely oxide-free. The advantage is faster soldering with clear flux residues and no solder globules.

The new range can be made in any quantity and with a very wide variety of soft solder alloys, fluxes, particle sizes and viscosities. They're suitable for screen printing, stencilling or application by automatic precision dispensers. Add to that the speed, simplicity, reliability and low application cost of solder creams in many operations and you have a product that takes the art of soldering one step further.

Multicore's solder cream can often be used instead of solder preforms. No tool costs are involved and inventories of individual shapes are avoided. The cream can often be applied more quickly and has more uniform flux content than preforms. But for those assemblies where preforms are preferred...

...don't forget Multicore preforms

These precision-made solder preforms come in virtually any size and shape. Rings, washers, discs, pellets and lengths of solder tape in most soft-solder alloys, with or without flux cores, are easily placed between the parts to be soldered.



Whether cream or preforms are used, just raise the temperature of the metal surfaces to around 50°C above the melting temperature of the solder. The solder cream or preform does the rest. Heating techniques can include gas flame, hot plate, oven conveyor, induction coils, resistance/electrode soldering, hot gas and infra-red.

Multicore Solders Ltd are Ministry of Defence Registered Contractors and on Qualified Products List QQ-S-571E of U.S. Defense Supply Agency for solder creams and preforms.



Multicore Solders Limited,

Maylands Avenue, Hemel Hempstead, Herts. HP2 7EP
Telephone: Hemel Hempstead 3636. Telex: 82363