

# wireless world


MAY 1977 40p

**Electrolytic capacitor tester**  
**Radio in the '80s**

**New isotope  
scanning  
technique**

Australia \$A1.20  
Canada \$1.50  
Denmark Kr. 1.00  
Finland Fmk. 6.50  
Germany DM. 4.50  
Greece Dr. 45.00  
Holland Dfl. 4.50  
Italy L. 900  
Malaysia M\$3.25  
New Zealand \$NS1.40  
Norway Kr. 10.00 incl. moms  
Portugal Esc. 40.00  
South Africa R. 1.10  
Spain Ptas. 80.00  
Sweden Kr. 6.90 incl. moms  
U.S.A. \$1.50

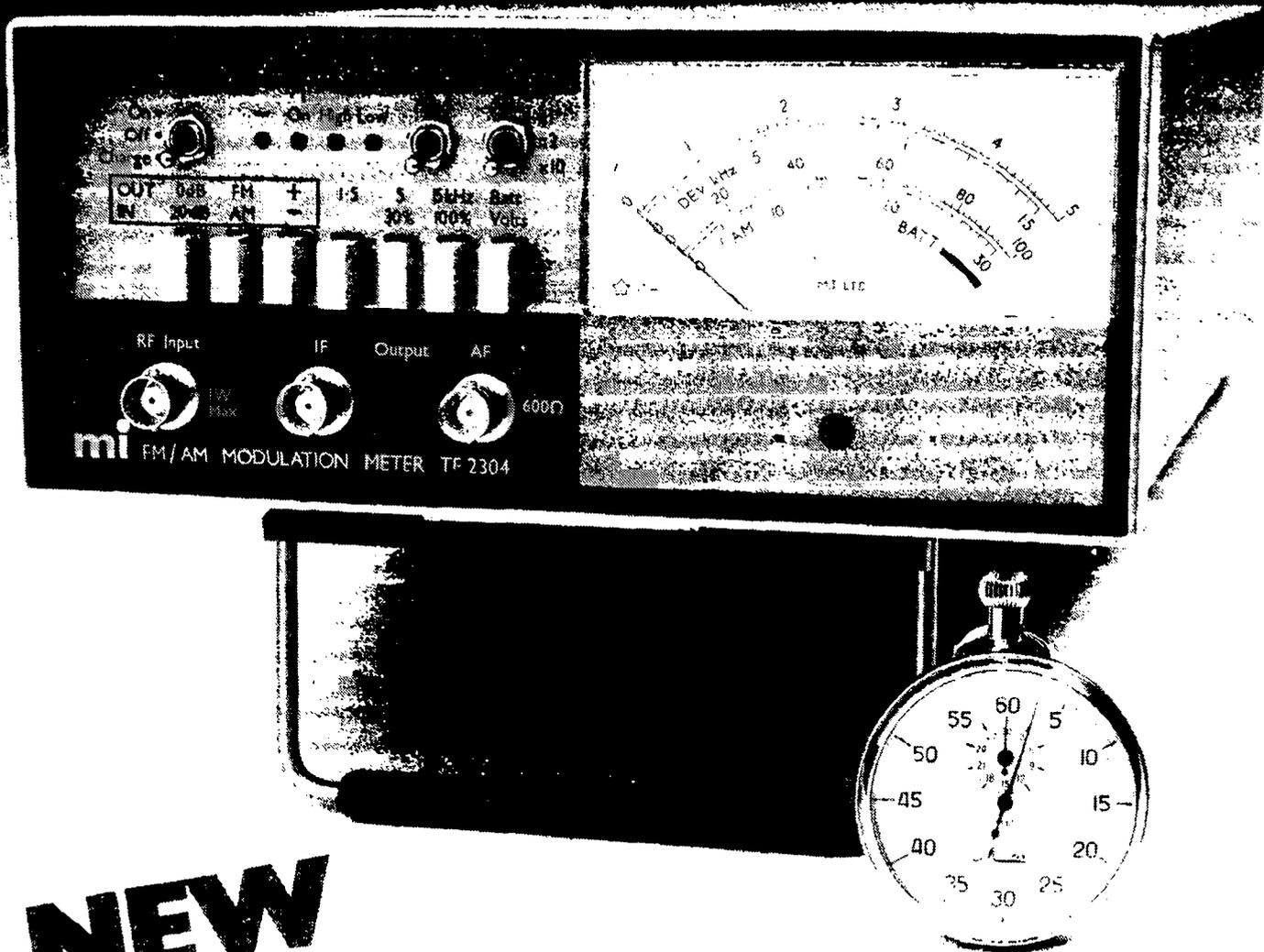BBC EXCLUSIVE  
Quad Decoding Part 1  
Variomatrix Adapter



**NEW**

# Automatic fm/am Modulation Meter

How long does it take for you to make a series of modulation tests with the meter you are using? The M.I. TF 2304 Automatic Modulation Meter eliminates at least five manual operations for each test and even more per test when a series of measurements is to be made. That can save you hours in a production day.

When connected to a transmitter, the TF 2304 automatically tunes to the carrier frequency and automatically sets the level, all within a few seconds. Exceptionally efficient screening and a very low distortion mixer ensure locking to the wanted signal. It is only necessary to select the required mode and range and the meter will read either deviation or % depth. L.E.D. lamps indicate if the signal level is too high or low and a push-button inserts a 20 dB attenuator to extend the maximum input level to 1 watt.

The basic frequency range is 25-1000 MHz and there are 8 peak deviation ranges covering 1.5 kHz f.s.d. to 150 kHz f.s.d. and a.m. depth ranges of 30% and 100% f.s.d. all with a modulation frequency range of 50 Hz to 9 kHz. Modulation symmetry can be checked by push-button selection of positive or negative deviation and peak or trough amplitude.

The accuracy of modulation measurement is  $\pm 3\%$  of full scale so transmitter deviation can now be set close to the permitted maximum with a consequent increase in efficiency.

The TF 2304 can be operated either from mains or internal rechargeable battery. It's small and light and there's a comprehensive range of accessories including a carrying case.

The price will pleasantly surprise you. Ask for full details.

**mi: THE AUTOMATIC CHOICE**

MARCONI INSTRUMENTS LIMITED,

Longacres, St. Albans, Hertfordshire, AL4 0JN. England. Telephone: St. Albans 59292. Telex: 23350.

A GEC-Marconi Electronics Company.  
WW-001 FOR FURTHER DETAILS

# wireless world

Electronics, Television, Radio, Audio

MAY 1977

Vol 83

No 1497

## Contents

- 35 **Surround sound — time to consolidate**  
36 **Radio in the '80s** by *Duncan MacEwan*  
41 **BBC Matrix H** by *P. A. Ratcliffe and D. J. Meares*  
46 **World of amateur radio**  
47 **Automatic electrolytic tester** by *A. Drummond-Murray*  
50 **Variomatrix adapter for System 45J and Matrix H**  
by *Michael A Gerzon*  
51 **H.F. predictions**  
52 **Logic design — 4** by *B. Holdsworth and D. Zissos*  
55 **Viewdata — 4** by *S. Fedida*  
60 **Letters to the editor**  
Mobile radio planning  
Do-it-yourself biofeedback  
Audibility of phase effects  
63 **News of the month**  
Annan and technology  
ITU Conference results  
British Rail high-speed track measurements  
67 **Two-stage linear amplifier** by *Helge Gronberg*  
71 **Power semiconductors — 2** by *Mike Sagin*  
79 **Circuit ideas**  
Linear voltage/frequency converter  
Pulse-counting frequency comparator  
Op-amp power output stage  
82 **New tomography machine** by *John Dwyer*  
85 **New products**  
**APPOINTMENTS VACANT**  
**INDEX TO ADVERTISERS**

Current issue price 40p, back issues (if available) 50p, at Retail and Trade Counter, Paris Garden, London SE1. By post, current issue 55p, back issues (if available) 50p, order and payment to Room 11, Dorset House, London SE1 9LU.

Editorial & Advertising offices: Dorset House, Stamford Street, London SE1 9LU.

Telephones: Editorial 01-261 8620; Advertising 01-261 8339.


Telegrams/Telex, Wiworld Bisnespres 25137 BISPRS G. Cables: "Ethaworld, London SE1.

Subscription rates: 1 year: £7.00 UK and overseas (\$18.20 USA and Canada). Student rate: 1 year, £3.50 UK and overseas (\$9.10 USA and Canada).

Distribution: 40 Bowling Green Lane, London EC1R 0NE. Telephone 01-837 3636.

Subscriptions: Oakfield House, Perrymount Rd, Haywards Heath, Sussex RH16 3DH. Telephone 0444 59188. Subscribers are requested to notify a change of address. © I.P.C. Business Press Ltd, 1977

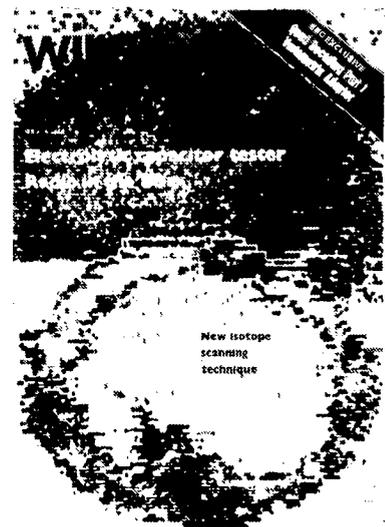"USA mailing agents: Expeditors of the Printed Word Ltd., 527 Madison Avenue, Suite 1217, New York, NY 10022. 2nd-class postage paid at New York.



Front cover is a print produced by the Tomoscanner, described by John Dwyer on page 82 of this issue. Print supplied by J. & P. Engineering (Reading) Ltd.

## IN OUR NEXT ISSUE

**Loudspeakers and rooms.** A discussion by James Moir of the interaction between the output of a loudspeaker and the acoustic performance of the listening room.

**Matrix H decoding.** Circuit details of a matrix H variable matrix decoder, a development of Sansui's Variomatrix, for use with experimental surround-sound programmes.

**Using a microprocessor.** The start of a series of articles on the design of a typical processor-based control system, starting with no assumptions of prior knowledge on the reader's part.

ISSN 0043 6062

**ibpa**  
International Business  
Press Associates

**ABC**  
ASSOCIATION OF THE BEST  
MAGAZINE OF CALCULATION

# QUAD-Quarter of a century of amplifier development



The Acoustical Manufacturing Co. Ltd. have been designing and producing amplifiers since 1936 but it was not until 1951 that the Q.U.A.D. 1 was introduced, the forerunner of the Quad series of Amplifiers which have earned an unrivalled reputation for originality of design, excellence of performance and reliability in the ensuing twenty-five years.


The introduction of the Quad 405 current dumping amplifier represents yet another contribution to the science of sound reproduction.

Current dumping successfully overcomes many of the problems associated with high power amplifiers, crossover, thermal tracking and matching of components, added to which the complete absence of adjustments or alignment requirements, ensures that performance will be consistently maintained.

For further details on current dumping and other Quad products write to Dept. WW

The Acoustical Manufacturing Co. Ltd.  
Huntingdon, Cambs., PE18 7DB  
Telephone: (0480) 52561

**Design Council  
Award 1976**

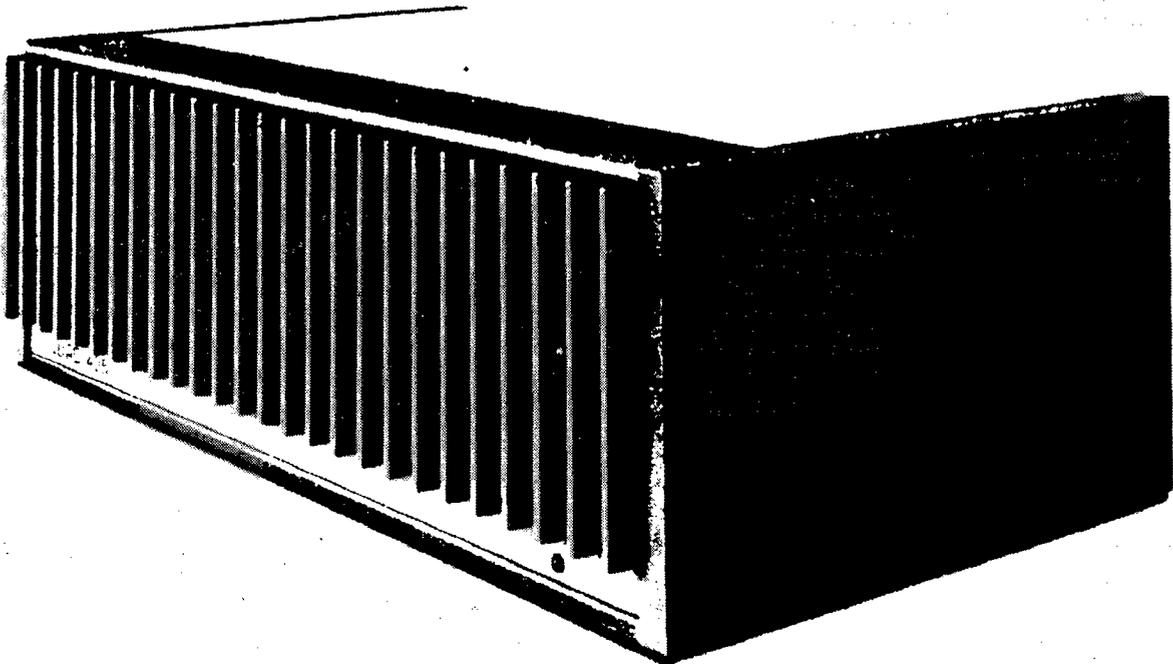

## QUAD





**for the closest approach to the original sound  
for twenty-five years.**

*QUAD is a Registered Trade Mark*  
WW-064 FOR FURTHER DETAILS

# LOW COST VOLTMETERS

from the  
range  
of

**LEVELL**  
PORTABLE INSTRUMENTS

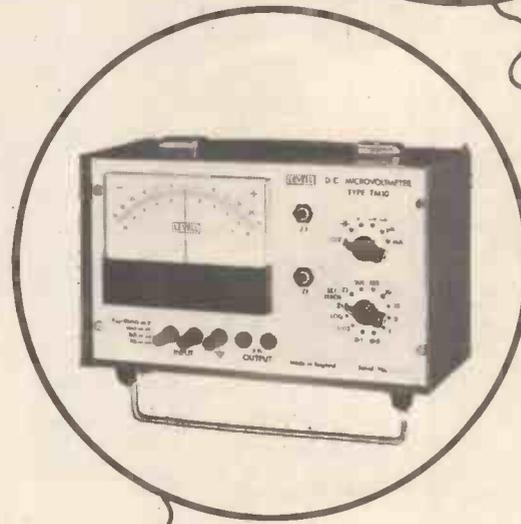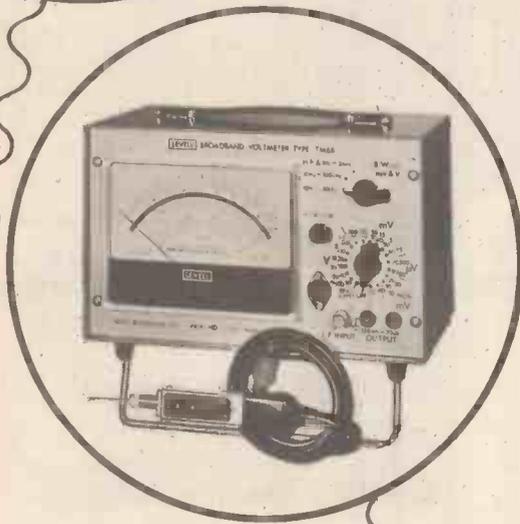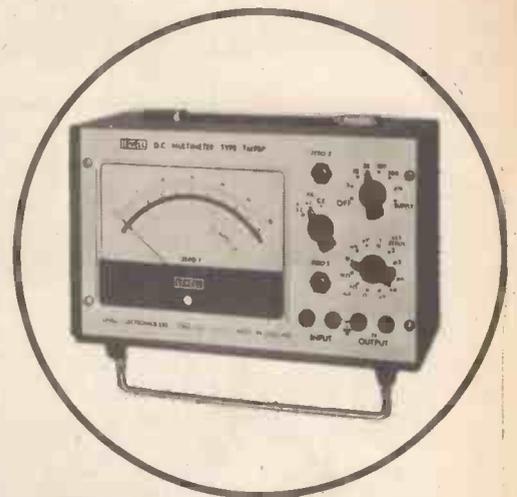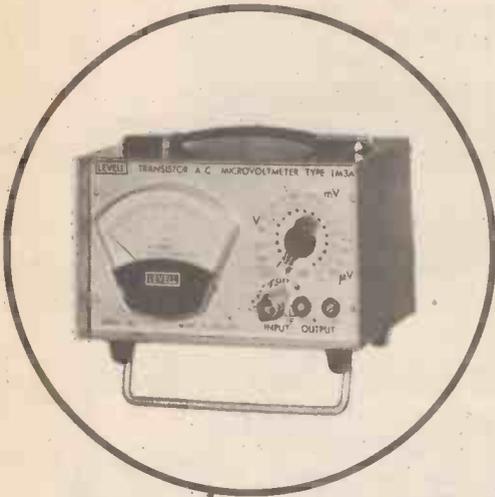

### A.C. MICROVOLTMETERS

**VOLTAGE & dB RANGES:** 15 $\mu$ V, 50 $\mu$ V, 150 $\mu$ V ... 500V.  
Acc.  $\pm 1\%$   $\pm 1\%$  f.s.d.  $\pm 1\mu$ V at 1kHz - 100, - 90°  
+50dB  
Scale - 20dB/ + 6dB rel. to 1mW/600 $\Omega$ .  
**RESPONSE:**  $\pm 3$ dB from 1 Hz to 3MHz,  $\pm 0.3$ dB from  
4Hz to 1MHz above 500 $\mu$ V. Type TM3B can be  
set to a restricted B.W. of 10Hz to 10kHz or 100 kHz.  
**INPUT IMPEDANCE:** Above 50mV > 4 3M $\Omega$  < 20pf.  
On 50 $\mu$ V to 50mV: > 5M $\Omega$  < 50pf.  
**AMPLIFIER OUTPUT:** 150mV at f.s.d.

type **£85** type **£95**  
TM3A TM3B

### D.C. MULTIMETERS

**VOLTAGE RANGES:** 3 $\mu$ V, 10 $\mu$ V, 30 $\mu$ V ... 1kV.  
Acc.  $\pm 1\%$   $\pm 1\%$  f.s.d.  $\pm 0.1\mu$ V. LZ & CZ scales.  
**CURRENT RANGES:** 3pA, 10pA, 30pA ... 1mA (IA for  
TM9BP).  
Acc.  $\pm 2\%$   $\pm 1\%$  f.s.d.  $\pm 0.3$ pA. LZ & CZ scales  
**RESISTANCE RANGES:** 3 $\Omega$ , 10 $\Omega$ , 30 $\Omega$  ... 1 G $\Omega$  linear Acc.  
 $\pm 1\%$   $\pm 1\%$  f.s.d. up to 100M $\Omega$ .  
**RECORDER OUTPUT:** 1V at f.s.d. into > 1k $\Omega$  on LZ ranges.

type **£125** type **£135**  
TM9A TM9BP

### BROADBAND VOLTMETERS

**H.F. VOLTAGE & dB RANGES:** 1mV, 3mV, 10mV ... 3V.  
Acc.  $\pm 4\%$   $\pm 1\%$  f.s.d. at 30MHz. - 50dB, - 40dB,  
- 30dB to + 20dB. Scale - 10dB/ + 3dB rel. to 1mW/50 $\Omega$   
 $\pm 0.7$ dB from 1MHz to 50MHz,  $\pm 3$ dB from 300kHz to  
400MHz.  
**L.F. RANGES:** As TM3 except for the omission of 15 $\mu$ V and  
150 $\mu$ V.  
**AMPLIFIER OUTPUT:** Square wave at 20Hz on H.F. with  
amplitude proportional to square of input. As TM3 on L.F.

type **£135** type **£145**  
TM6A TM6B

### D.C. MICROVOLTMETERS


**VOLTAGE RANGES:** 30 $\mu$ V, 100 $\mu$ V, 300 $\mu$ V ... 300V.  
Acc.  $\pm 1\%$ ,  $\pm 2\%$  f.s.d.,  $\pm 1\mu$ V. CZ scale.  
**CURRENT RANGES:** 30pA, 100pA, 300pA ... 300mA.  
Acc.  $\pm 2\%$ ,  $\pm 2\%$  f.s.d.,  $\pm 2$ pA. CZ scale.  
**LOGARITHMIC RANGE:**  
 $\pm 5\mu$ V at  $\pm 10\%$  f.s.d.,  $\pm 5$ mV at  $\pm 50\%$  f.s.d.,  $\pm 500$ mV at  
f.s.d.  
**RECORDER OUTPUT:**  $\pm 1$ V at f.s.d. into > 1k $\Omega$ .

type **£77**  
TM10

These highly accurate instruments incorporate many useful features, including long battery life. All A type models have 83mm scale meters, and case sizes 185x110x130mm. B types have 127mm mirror scale meters and case sizes 260x125x180mm.

**LEVELL ELECTRONICS LTD.**  
Moxon Street, High Barnet, Herts. EN5 5SD  
Tel: 01-449 5028/440 8686

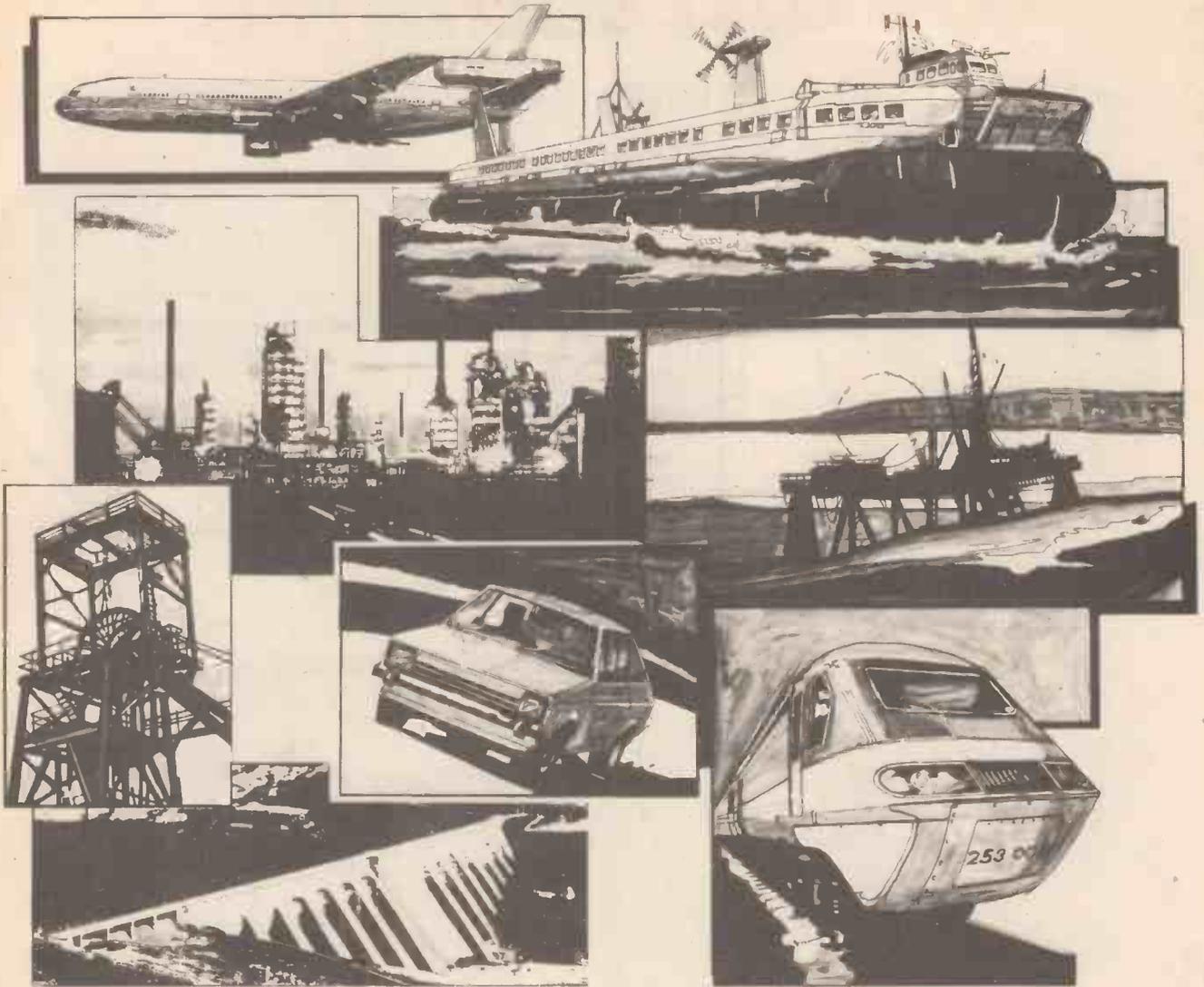Prices are ex works with batteries. Carriage and packing extra. VAT extra in U.K. Optional extras are leather cases and mains power units. Send for data covering our range of portable instruments.



## On site instrumentation recording. From the world's leading Datatape<sup>®</sup> manufacturer

The Bell & Howell CR3000 battery operated cassette recorder enables engineers to collect data at source.

Forget the problems of threading tape out of doors. Just load the cassette and the four channel CR3000 is ready to make recordings of instrumentation quality. Specifically developed for portability, the CR3000 is compact and lightweight, you no longer have to strain with heavy equipment to achieve high quality recordings. Plug-in self-contained preamplifier provides for input levels down to one millivolt, so no more signal conditioning to recorder problems either.

The built-in noise canceller means high quality reproduction, even when recordings are made in rugged environments. Use of standard cassettes reduces costs, saves storage space and ensures a local supply of tape.

CR3000 is available in three I.R.I.G. speed versions with FM and direct electronics selected at the press of a button, providing frequency coverage



For further information please contact C. Southee.

**ELECTRONICS & INSTRUMENTS DIVISION**

**BELL & HOWELL**

Lennox Road, Basingstoke, Hampshire  
RG22 4AW Basingstoke (0256) 20244


WW — 074 FOR FURTHER DETAILS

of d.c. to 24kHz dependent on speed and electronics used.

The CR3000 is competitively priced and includes built-in metering, voice and battery charger as standard.

*Measurement and control systems available from Bell & Howell:*

- Pressure Transducers
- Level Measurement
- Physiological Instruments
- Marine Pressure Measurement Instruments
- Transmitters—Gauge & DP
- Intrinsically Safe Pressure Transmitters
- Flameproof Pressure Transducers
- Pressure Standards
- Liquid Density Transmitters
- Vibration Monitoring Systems
- Accelerometers
- Instrumentation Magnetic Tape Recorders
- Direct Writing Oscillograph Recording Systems
- Microcomputer Instrumentation Systems

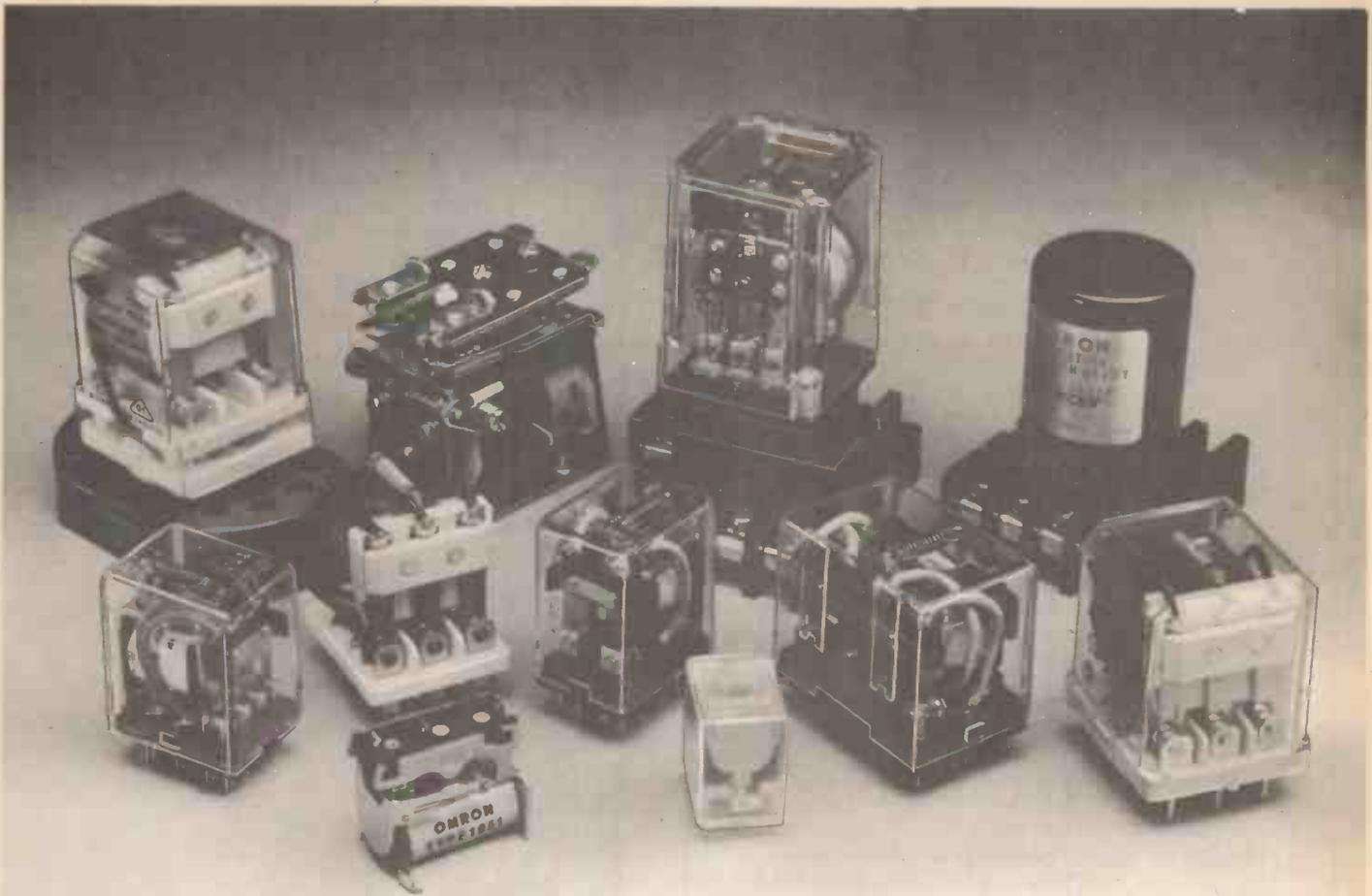

## Why are we bothering to become sole distributors of Omron relays when our own are so good?

The IMO Series 60 are a fine range of relays, but only by the inclusion of the wide Omron range are we able to offer relays for every conceivable relay application.

Omron covers the whole spectrum of the relay industry. From switching dry circuits with electronic and reed relays to heavy duty control circuits with miniature relay contactors. IMO with Omron will meet every specification.

This puts the whole Omron component range conveniently under the same roof. And that means the same consistent, reliable and helpful IMO service.

IMO and Omron; a combined range that covers just about every application and every price bracket.

Isn't that something worth bothering about?

To: IMO Precision Controls Ltd.,  
349 Edgware Road, London W2 1BS. Tel: 01-723 2231.

WW 5/77

Please send me full details on IMO and Omron relays.

Name \_\_\_\_\_

Position \_\_\_\_\_


Company \_\_\_\_\_

Address \_\_\_\_\_

Tel: \_\_\_\_\_

**IMO. Now most people know**

## ELECTRONIC INDUSTRIAL THERMOMETER

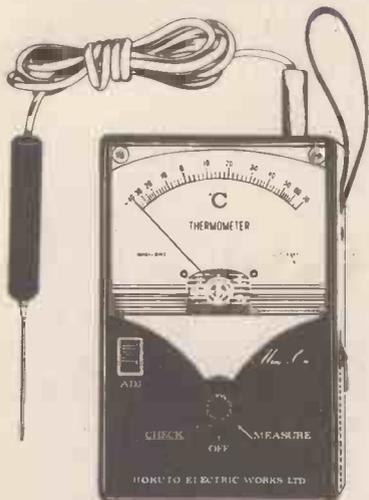

### THE MODERN WAY TO MEASURE TEMPERATURE

A Thermometer designed to operate as an Electronic Test Meter. Will measure temperature of Air, Metals, Liquids, Machinery, etc., etc. Just plug-in the Probe, and read the temperature on the large open scale meter. Supplied with carrying case, Probe and internal 1½ volt standard size battery.

Model "Mini-Z 1" measures from -40° C to + 70° C Price £25.00  
 Model "Mini-Z 2" measures from -5° C to + 105° C Price £25.00  
 Model "Mini-on HI" measures from + 100° C to + 500° C £20.00  
 (VAT 8% EXTRA)

Write for further details to

**HARRIS ELECTRONICS (LONDON)**  
 138 GRAY'S INN ROAD, LONDON. WC1X 8AX  
 ('Phone 01-837 7937)

WW-028 FOR FURTHER DETAILS

### BIMBOARD

Stop Ruining Your I.C.'s And Wasting Time Soldering  
 Plug Into The Revolutionary New

### BIMBOARD


The Only Professional Quality Breadboard That  
 Accepts All DIL Packages With 6 To 40 Pins

Incorporates Bus Strips For Vcc And Ground

Includes A Component Support Bracket

Has Over 500 Individual Sockets

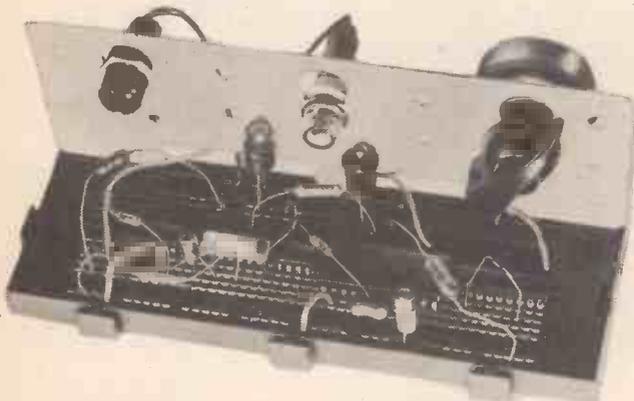And Allows You To Use And Re-Use  
 IC's, Transistors, LED's, 7 Segment Displays,  
 Diodes, Resistors, Capacitors



Only £9.72 (cheque with order) Including VAT and P.P.  
 Special Quantity Discounts Available For  
 Radio Clubs, Retail Outlets, Distributors

### BOSS INDUSTRIAL MOULDINGS LTD

Higgs Industrial Estate, 2 Herne Hill Road, London, SE24 0AU, England  
 Telephone 01-737 2383 Telex 919693

Transient  
 Peaks  
 Our Unit Conquers

### The Allen and Heath Broadcast Feed Forward Delay Limiter.

The only limiter that makes it **IMPOSSIBLE** for a transient peak to pass through the unit, without the use of clipping devices. Included in its design is a revolutionary bucket brigade integrated circuit. This delays the main signal path by approximately one thousandth of a second. Thus gain reduction is fed forward before there is any increase in the programme level. The unit can be used with high powered equipment such as broadcast units and P.A. systems. Use it too in studios with effects units.

Try and test one at our demo. studio. Pembroke House, Campsbourne Road, Hornsey, London N8.  
 Or, for more information, call Andrew Stirling at 01-340 3291.


**AH** Allen and Heath Limited.

WW-070 FOR FURTHER DETAILS

Looks like a display.  
Works like a newscaster.


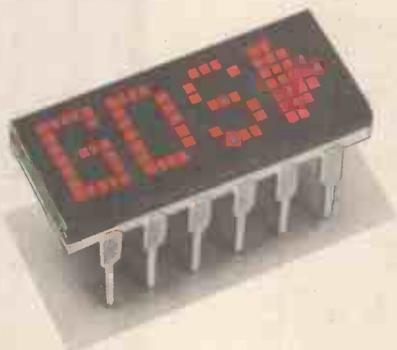
## The new Hewlett-Packard Alphanumeric Display from GDS.



This important development from Hewlett-Packard is a significant advance in the design and manufacture of Alphanumeric displays.

The HP HDSP-2000 is a 3.8mm. 5x7 LED array, available in 4 character clusters and packaged in a 12 pin DIL ceramic glass pack. A serial-in-parallel-out, 7 bit shift register associated with each digit controls constant current

LED drivers. Full character display is achieved by external column strobing.

Applications include interactive I/O terminals, point of sale equipment, portable telecommunications gear plus a good many more that you can now consider.

For full data and highly informative answers to your questions, write or telephone:



A Crellon Company

GDS Sales Ltd.  
380 Bath Road, Slough, Berks SL1 6JE.  
Tel: Burnham (06286) 63611





An 'off-the-shelf'  
solution to all your  
filtering problems

## Barr & Stroud Active Filter Modules

In so many electronic projects there is a need to incorporate an element of filtering. Quickly, easily and—above all—for a minimum cost.

The most rapid solution is to select one of the Barr & Stroud 'ready to use' compact filter units. They are inexpensive and readily available. They come 'one-off' or in 'thousands' to match your requirements.

Each containing a basic filter function, adjustable for cut-off or centre frequency and response type. Adjustment is simple. No filter knowledge is required. The modules are available in low-pass, high-pass, universal and notch designs with a pass band capability from d.c. to 1 MHz. Complete details are in freely available literature, yours on request.

**BARR & STROUD LIMITED**

London Office:  
1 Pall Mall East,  
London SW1Y 5AU  
Tel: 01-930 1541  
Telex: 261877



WW—023 FOR FURTHER DETAILS

"He's asking  
for a  
**reed relay  
assembly  
with a 30kV  
isolated coil**"



People often bring their need to us. They know the Whiteley speciality. Being helpful! And the item that started life as a customer request, joins the Whiteley product list, ready to help other designers over a problem. You, perhaps? Consider a neat relay assembly — one or two dry reed switches with a rating of 25W, housed in a mounting tube, with either 'normally open' or 'change-over' contacts. Around them, a coil operating from 8, 12, 24 or 50V supply, 30kV isolated from the contacts. The whole unit mounting on a 0.25" insulating plate with a couple of 3 way tag strips. If you're interested, ask for a data sheet. But more, keep Whiteley in mind as the people who make useful things.



...manufacturing  
your electrical  
and electronic  
requirements.

# Whiteley

Whiteley Electrical Radio Co. Ltd.


Mansfield, Notts NG18 5RW, England. Tel: 0623 24762.

WW—058 FOR FURTHER DETAILS
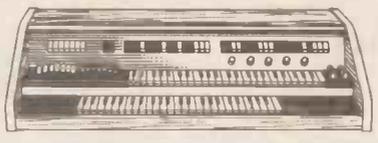
# MAPLIN



The only organ you can build in stages and tailor to your requirements as you go along — and at each stage you'll have a fully working instrument! We haven't got the gimmicks (yet — they're coming soon), but we have got the most beautiful sounds — you won't find them on any organ less than twice our price. So get our MES50 series leaflets now! 65p buys the three available so far.



We stock a wide range of switches including a really low-priced high quality interlocking push-button switch system, which is extremely versatile. We've got toggle switches, slide switches, push switches, rotary switches — there are dozens to choose from, but it's only a tiny part of our fantastic range.

A completely self-contained pedal unit. 13-note, 2-octave-range, 4 organ stops. It can be added to any organ! A really unusual extra is the bass guitar stop which uses four envelope shapers to give a real bass guitar sound. A must for the solo guitarist. Full construction details in our catalogue — post the coupon below now!

Play fascinating games NOW on your own t.v. in your own living room. The kids will think it's magic when the scores pop up on the screen. Lay your bets — anyone could win — with Maplin's prices everyone can win. Get the May edition of Electronics Today International now — then get all the parts from us at a remarkably low price (I.C. alone £11.99). All prices include VAT and P&P.

This high-quality Graphic Equaliser will enhance even the most sophisticated system at a fraction of the cost of a ready-made equaliser of equal quality. You can get all the parts from us (except woodwork) including drilled and printed metalwork. Construction details in our leaflet: 15p.



## IT'S A FANTASTIC BESTSELLER!

216 big (11" x 8") pages! Over a thousand illustrations!  
 Over 30 pages of complete projects to build!  
 Thousands and thousands of useful components described and illustrated! No wonder it's a bestseller!  
**DON'T MISS OUT! SEND 50p NOW!**

**POST THIS COUPON NOW FOR YOUR COPY OF OUR CATALOGUE PRICE 50p**


Please rush me a copy of your 216 page catalogue by return of post. I enclose 50p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 50p refunded immediately.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

\_\_\_\_\_

WW 5

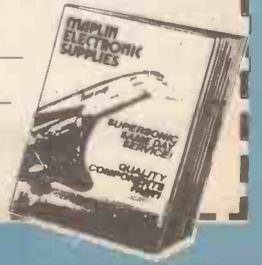

Our bi-monthly newsletter keeps you up to date with latest guaranteed prices — our latest special offers (they save you loads) — details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).

**MAPLIN ELECTRONIC SUPPLIES**  
 P.O. BOX 3 RAYLEIGH ESSEX SS6 8LR

Telephone: Southend (0702) 715155  
 Shop: 284, London Road, Westcliff-on-Sea, Essex  
 (Closed on Monday) Telephone: Southend (0702) 47379

WW — 016 FOR FURTHER DETAILS

# specify CINCH

BARRIER TERMINAL BLOCKS & ACCESSORIES  
J-SERIES MULTIWAY PLUGS & SOCKETS  
PRINTED CIRCUIT BOARD EDGE CONNECTORS  
D-SUBMINIATURES

# and be certain

**United-Carr Supplies carries the widest range of CINCH parts available in the UK, and will accept for quick delivery mixed or small quantity orders. So make United-Carr Supplies your Single CINCH Source. Send for free catalogue illustrating the full range of components available.**




**United-Carr Supplies Limited**

*The largest CINCH, DOT and FT stockist*

112 Station Road, Ilkeston, Derbyshire DE7 5LF  
Tel: 0602 328711 Telex 377117

# JAMES SCOTT TRAFFIC RADAR SYSTEMS

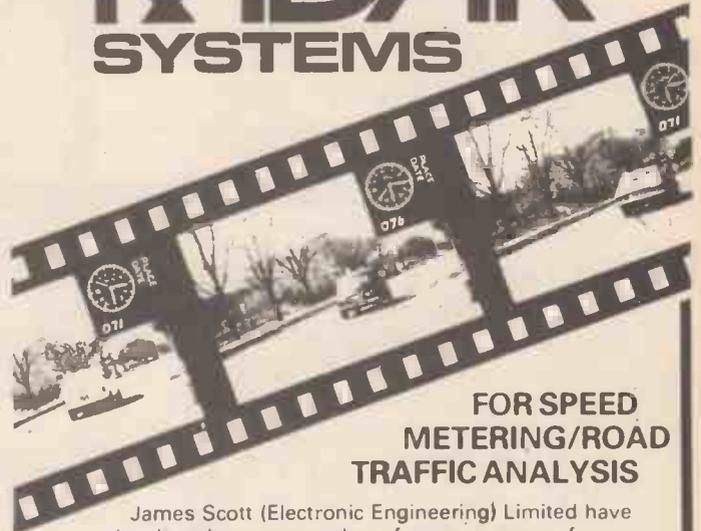

**FOR SPEED  
METERING/ROAD  
TRAFFIC ANALYSIS**

James Scott (Electronic Engineering) Limited have developed, over a number of years, a range of miniature traffic radar systems of advanced design for law enforcement and traffic analysis applications.

- Digital speed presentation • Suitable for LH/RH traffic systems • Alarm speed selectable in the range 21 to 99 mph or kph in unit steps • Can be used tripod mounted or from inside a parked vehicle
- Compact, lightweight design with solid state circuitry except for digital display tubes • Facility to operate camera/flash unit (available as optional extra) • Test oscillator incorporated • BCD output available for data-logging.


These are some of the reasons why the James Scott Gatso Mini Radars are rapidly gaining acceptance with Police Forces and Traffic Engineers throughout the world (U.K., West Germany, Holland, Belgium, Greece, Singapore, Malaysia, Australia.) If you want more please write or telephone.



AS SUPPLIED TO  
THE HOME OFFICE,  
LONDON.



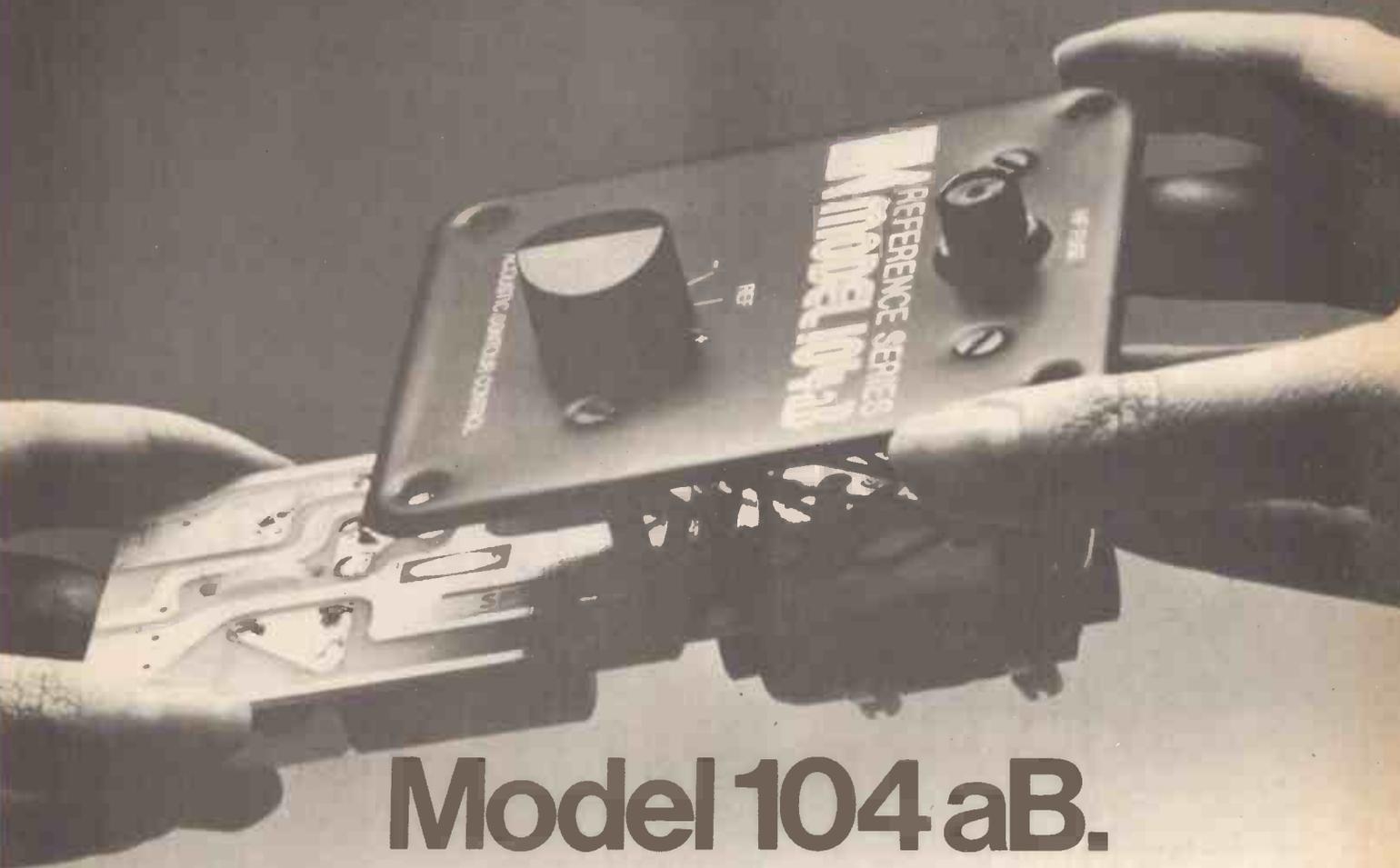**JAMES  
SCOTT**  
**(Electronic Engineering) Ltd**  
CARNTYNE INDUSTRIAL ESTATE  
GLASGOW G32 6AB Tel: 041-778 4206 Telex 778286



## Model 104 aB.

# One step nearer the reference.

Computer-based analysis has led KEF engineers to a significant advance in speaker performance – the acoustic Butterworth (aB) filter network. Now, replacing conventional filter circuitry in the renowned Model 104, it transforms performance with reduced colouration, increased stereo depth and imaging. A difference you can hear. An advance radical enough to justify making the new network available for replacement in existing Model 104's – see your dealer about this. Power rating is higher too – 100 watts programme – with fuse protection for the tweeter. So KEF engineers have seemingly done the impossible – taken the superb 3 speaker system that reviewers already praised for its clean, uncoloured 'reference' sound – **and improved it.**


Model 104aB – one step nearer the reference – live sound.

Tell me more  
about Reference  
Series Model  
104aB

Stamps for return postage  
appreciated.

Name

Address

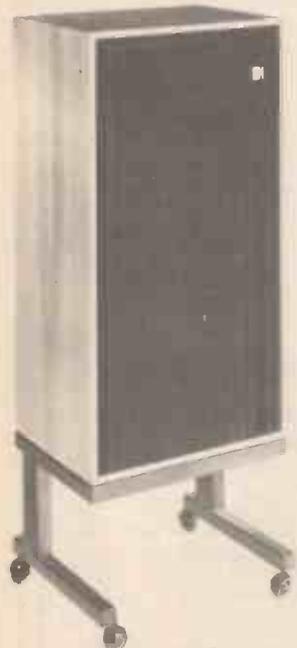

KEF

the speaker  
engineers



KEF Electronics Limited  
Tovil Maidstone ME15 6QP Kent  
Telephone 0622 672261 Telex 96140

WW 5/77

The world's most famous company in communication, the Nippon Electric Company Ltd., Tokyo, has developed the famous NED CQ radio amateur gears, being with regard to design, quality, reliability and price real pace-setters for today's communicators.

First in history of amateur radio, such a big and famous company with more than 80 years of experience in construction of communication facilities, made its experience available to radio amateurs around the world.

The NEC, which has declared microwave space communication to its speciality, knows perfectly which attributes equipments must have for becoming bestsellers.

Today we present:

## NEC CQ 110 E DIGITAL



allband, HF, 300 watt transceiver, 160 / 80 / 40 / 20 / 15 / 11 / 10A / 10B / 10C / 10D / WWV, modes FSK, USB, LSB, CW, AM, with separate 8 pole X-tal lattice filters for each mode fitted.

Further features: Side tone at CW, VOX (automatic transmit-receive by talking into microphone), 11 meter CB band, all channels easily selectable through digital counter, excellent receiver sensitivity at extreme crossmodulation security by application for the 7360 low noise beam, deflection mixer tube.

This feature alone makes of the NEC CQ 110 E a top rider. Fixed channel communication on 22 channels is possible. A 60 page manual and a high quality dynamic microphone are supplied with the transceiver. Speaker, AC 100-235 volts and DC 13.5 volts power supplies are built in of course.

## NEC CQ 301



allband HF, 3KW, linear amplifier, 160/80/40/20/15/11/10 meter, for modern amateur communication. Two EIMAC 3-500 Z triodes, in zero bias grounded grid application guarantee long trouble free communication. The NEC CQ 301 can be driven by our CQ 110E or other excitors capable of about 50-100 watts of drive. AC power supply 100-235 volts is built in of course.

RETAILERS: Do not hesitate to accept our offer. Join us in selling these bestsellers!

Sole distributor in Europe:

**CEC** Corp., Via Valdani 1 -- CH 6830 CHIASSO--SWITZERLAND  
Phone: (091) 44 26 51. Telex: 79959 CH

WW-019 FOR FURTHER DETAILS

# Join the Digital Revolution

Understand the latest developments in calculators, computers, watches, telephones, television, automotive instrumentation . . .

Each of the 6 volumes of this self-instruction course measures 11 3/4" x 8 1/4" and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers.

Design of Digital Systems.



## £6.20

plus 80p packing and surface post anywhere in the world.

Payments may be made in foreign currencies.

Quantity discounts available on request.

VAT zero rated

Also available -- a more elementary course assuming no prior knowledge except simple arithmetic.

Digital Computer Logic and Electronics.

In 4 volumes:

1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flipflops and Registers

## £4.20

plus 80p P. & P

Offer Order both courses for the bargain price £9.70, plus 80p P. & P.

**Designer  
Manager  
Enthusiast  
Scientist  
Engineer  
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

### Guarantee--no risk to you

If you are not entirely satisfied with Design of Digital Systems or Digital Computer Logic and Electronics, you may return them to us and your money will be refunded in full, no questions asked.

To Cambridge Learning Enterprises, Dept. COM, FREEPOST Rivermill House, St. Ives, Huntingdon, Cambs. PE17 4RR

\*Please send me . . . set(s) of Design of Digital Systems at £7.00 each p & p included

\*or . . . set(s) of Digital Computer Logic and Electronics at £5.00 each, p & p included

or . . . combined set(s) at £10.50 each, p & p included

Name .....

Address .....

\*delete as applicable

No need to use a stamp -- just print FREEPOST on the envelope.

WW5

# We measure up to your standards


**B900**  
Automatic Digital Bridge 1kHz 0.1%



**B224**  
Wide-range Audio Bridge 1592Hz  
(200Hz-20kHz external)



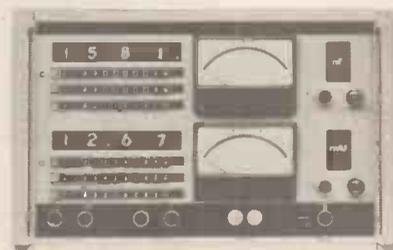**B331**  
Self-balancing 0.01% Precision Bridge



**B642**  
Autobalance Universal Bridge 0.1%



**B421**  
Direct-reading Component Meter 0.25%



Whether you check components at Goods Inwards, during production or on Final Test, Wayne Kerr has the bridge you need. For fast measurements of resistance, capacitance and inductance, or for continuous monitoring of changing values, you can select the ideal instrument from our comprehensive range.

All models—AF, RF and VHF—have a wide measurement range and are easy to use. Many have automatic readout and automatic lead compensation; most will measure components *in situ*.

Only part of our range is illustrated. Send in the coupon for further information.



**Wilmot Breeden Electronics**  
Ferrograph    Rendar    Wayne Kerr

Wilmot Breeden Electronics Limited,  
442 Bath Road, Slough,  
SL1 6BB, England.  
Telephone: Burnham (06286) 62511  
Telex: 847297

Please send me the Wayne Kerr short form catalogue.

Name \_\_\_\_\_

Position \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

Telephone \_\_\_\_\_

(WW 5/77)



Wilmot Breeden Electronics Limited,  
442 Bath Road,  
Slough, SL1 6BB,  
England.

## WAYNE KERR BRIDGES

WW-027 FOR FURTHER DETAILS

# This is an echo chamber?




Yes, and much more! It is the first N-channel Bucket Brigade Device designed with the audio engineer in mind. The SAD-1024 Serial Analog Delay will provide reverberation, echo, tremolo, vibrato and chorus effects in electronic organs and musical instruments. It will equalise speaker systems in an auditorium, or can be used in speech compression or voice scrambling systems. The SAD-1024, which contains two independent sections of 512 analog storage elements will accomplish all of these with a signal-to-noise ratio in excess of 75dB. The two sections may be used independently or they may be connected in sequence to provide 1024 clock periods of delay. The delay provided by the device can be continuously varied by the clock rate from less than one milli-second to more than one second.

Other performance characteristics include: signal bandwidth from 0 to 200 KHz, less than 1% total harmonic distortion, 0dB insertion loss, and less than 5mW power requirements from a single 15V power supply.

You get all these features for less than 1p per storage element in OEM quantities.

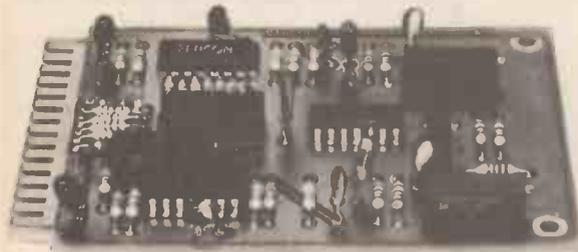We also offer an optional complete circuit card to help you evaluate this exciting new device. Other devices for applications such as time base correction in the video bandwidth are also available.



## RETICON®

The SAD-1024 and circuit card is available immediately from Reticon's sole UK distributors, Herbert Controls and Instruments Limited, Spring Road, Letchworth, Herts SG6 4AJ. Telephone: 04626-3841. Telex: 825535.

WW — 060 FOR FURTHER DETAILS

## POWER UNITS

### Valradio

PRODUCTION TESTING ★ DEVELOPMENT  
SERVICING



**TYPE 250VRU/30/25**

Input 200-250v 50Hz or 100-120v 60Hz to order. Output 1: 0-30v 25A DC. Output 2: 0-70v 10A AC. Output 3: 0-250v 4A AC.

PRICE: £233.60 excluding VAT

Regulated and unregulated outputs with output voltages of 12, 24, 50, 110 or 220v DC are also available at very competitive prices.

Send for further details of these versatile units to:-

### Valradio

BROWELLS LANE, FELTHAM, MIDDX.

TW13 7EN


PHONE: 01-890 4242 or 4837

WW—043 FOR FURTHER DETAILS
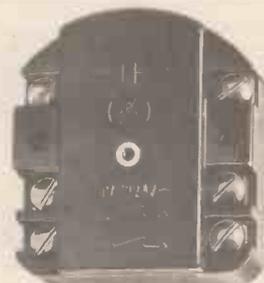
## Switching problems? Rely on Zettler.

Producing 30 basic types of relay and 15,000 variants with regard to contact stacks, terminals, energizing current and contact material, Zettler is among the largest manufacturers of electro-mechanical components.

Our product range comprises:  
Low profile (platform)  
Timing · Miniature · Low contact capacity · Hermetically sealed · Stepping  
Mains switching · Latching  
Contact stacks · Solenoids



**Impulse Latching Relay  
AZ 340**

Make contacts:  
Resistive load: 10 A/240 V AC.  
Lamp load: 8 A/240 V AC.  
Compensated fluorescent tubes:  
3.7 A/240 V AC.  
Break contacts:  
Resistive load: 8 A/240 V AC.  
Lamp load: 5 A/240 V AC.  
Compensated fluorescent tubes:  
3.7 A/240 V AC.

We resolve your switching problems rapidly and expertly. Please contact us for further details.



**ZETTLER** Zettler  
UK Division

Brember Road, Harrow, Middx.  
HA2 8AS. Tel. (01) 422 0061

Please look us up at

IFSSEC 77, Olympia, London, 25th-29th April. Stand No. 27  
All-Electronics Show, Grosvenor House, Park Lane, London  
19th-21st April, Stand No. 141, Great Room

A member of the worldwide ZETTLER electrical engineering group, est. 1877

WW — 017 FOR FURTHER DETAILS



## Four and a half digits for every budget

The new Philips range of 4½ digit multimeters is designed to meet modern technology's demand for ever higher measuring accuracy and resolution – and to meet individual application requirements and budgets. They are all high quality instruments, fully tested to IEC standards, and offer numerous attractive features to make your measurements easier, safer and more efficient.

The one manual ranging multimeter in the family, PM2522A, features a display-hold facility which can be remotely controlled at the measuring probe, while the other models incorporate intelligent auto ranging circuits providing ultra-fast stable displays.

True r.m.s. measurement is possible with the PM2526 and PM2527 and these models can also be fitted with an optional IEC bus interface. In addition the PM2527 features

sophisticated guarding, very sensitive current and wide resistance ranges, making it ideal for measurements on advanced low-power circuitry.

All models permit measurement of surface temperature with an extremely fast-acting probe, over a range of -60 to +200°C.

Numerous options and accessories allow you to further tailor the specifications to your requirements and keep the cost within your budget. Study the basic specifications below.

Please write, telephone or use the reader enquiry service for further information.



### Pye Unicam Ltd.

Philips Electronic Instruments Dept  
York Street Cambridge England CB1 2PX  
Tel Cambridge (0223) 58866

A member of the Pye of Cambridge Group

|   | PM 2522 A  | PM 2524  | PM 2526  | PM 2527  |
|---|--|--|--|--|
| Parameters                                    | V <sub>DC</sub> , V <sub>AC</sub> , I <sub>DC</sub> , I <sub>AC</sub> , R, Temperature | V <sub>DC</sub> , V <sub>AC</sub> , I <sub>DC</sub> , I <sub>AC</sub> , R, Temperature | V <sub>DC</sub> , V <sub>AC</sub> , R, V <sub>HF</sub> , Temperature | V <sub>DC</sub> , V <sub>AC</sub> , I <sub>DC</sub> , I <sub>AC</sub> , R, V <sub>HF</sub> , Temperature |
| Ranging                                       | Manual   | Auto and Manual  | Auto and Manual  | Auto and Manual  |
| VDC Accuracy                                  | ± 0.03 % rdng  | ± 0.02 % rdng  | ± 0.02 % rdng  | ± 0.02 % rdng  |
| VDC Resolution in Lowest Range                | 100 µV   | 10 µV  | 10 µV  | 10 µV  |
| Max. Ω / Ω-Resolution in value / Lowest Range | 20 MΩ / 0.1 Ω  | 20 MΩ / 0.1 Ω  | 20 MΩ / 0.01 Ω   | 2000 MΩ / 0.01 Ω   |
| Max. I / Current Resolution in Lowest Range   | 2000 mA / 10 µA  | 2000 mA / 100 µA   | —  | 2000 mA / 100 pA   |
| VAC Frequency Range                           | 35 Hz - 30 kHz   | 40 Hz - 30 kHz   | 30 Hz - 100 kHz  | 30 Hz - 100 kHz  |
| AC-DC Conversion                              | Averaging  | Averaging  | True RMS (VAC + VDC)   | True RMS VAC, IAC  |
| Type of Input/Power Supply                    | Floating/Mains and Battery   | Floating/Mains and Battery   | Floating/Mains   | Guarded/Mains  |

The **RANGE** of experience

# PHILIPS




Test & Measuring Instruments

# Edicron

## For Quality and Reliability

Edicron Limited  
Redan House 1 Redan Place  
London W2 4SA  
Tel: 01-727 0101  
Telex: 265531  
Cables: Edicron London W2


Electronic  
Valves/Tubes

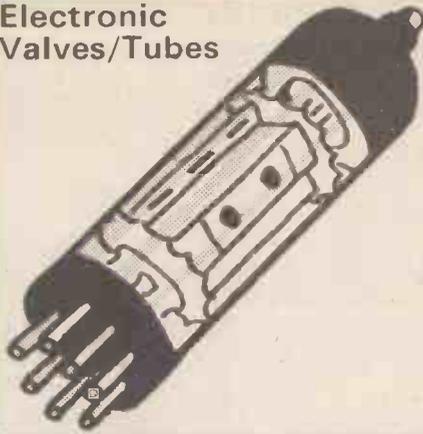


Resistors and  
Capacitors



TV Picture  
Tubes

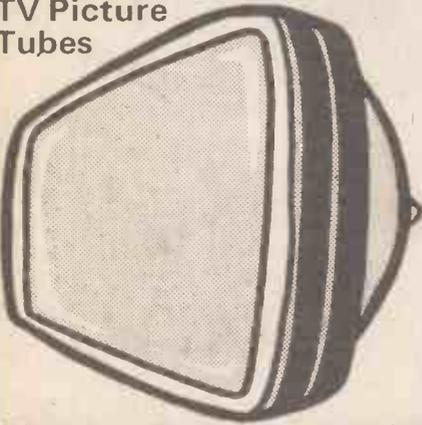

Transistors

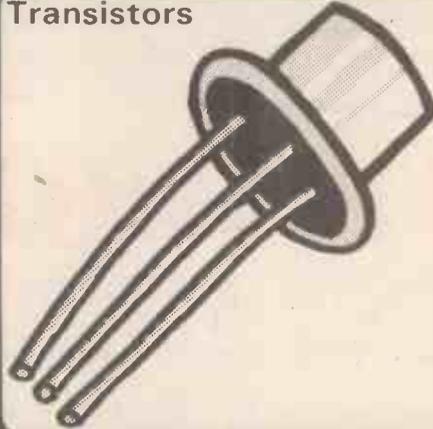

CR Gun  
Assemblies




# EXPORT — INDUSTRY — WHOLESALE

WW—032 FOR FURTHER DETAILS
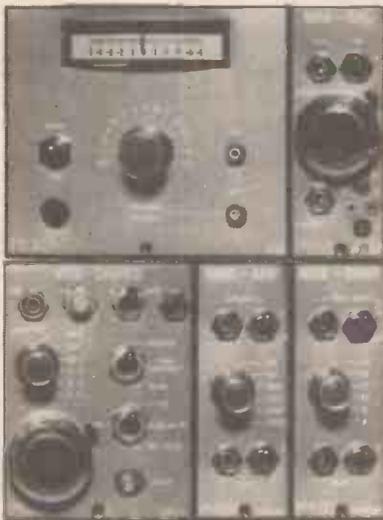
## FYLDE

TRANSDUCER and RECORDER  
AMPLIFIERS and SYSTEMS



reliable high performance & practical controls. individually powered modules—mains or dc option single cases and up to 17 modules in standard 19" crates small size—low weight—realistic prices.

## FYLDE

Fylde  
Electronic  
Laboratories  
Limited.

49/51 Fylde Road Preston  
PR1 2XQ  
Telephone 0772 57560

WW—044 FOR FURTHER DETAILS

Contractors to H. M. Govt. P. O.

# REPAIRS

OF ELECTRICAL MEASURING INSTRUMENTS  
**7-14 DAYS SERVICE**

◀ MODEL 8 MK.V



**STOCKISTS**  
ALSO SUPPLIERS OF GEC  
RISSE AND OTHER  
MULTI-RANGE TEST SETS

WE SPECIALISE IN ASSEMBLIES, AND IN THE  
REPAIR, CALIBRATION AND CONVERSION  
OF ALL TYPES OF INSTRUMENTS, INDUSTRIAL  
AND PRECISION GRADE

## LEDON INSTRUMENTS LTD.

GLADSTONE WORKS, GLADSTONE RD,  
FOLKESTONE, KENT.  
TEL: (STD) 0303 57555

WW—042 FOR FURTHER DETAILS

Safe, tough, efficient and versatile – that's our new miniature CX iron.

**Safe** because it is virtually leak-free (leakage current less than  $1\mu\text{A}$ ). Earth it if you like – three core lead. It is made to conform with B.S. 3456 and has a breakdown voltage of more than 4000V.

**Tough** because the handle is almost unbreakable and the ceramic shaft is covered by a stainless steel shaft.

**Efficient** because the element is situated right inside the soldering bit and the heat generated by its 17 watts is not wasted.

**Versatile** because the iron can be used for a wide variety of soldering jobs; with six easily interchangeable, slide-on bits, ranging from  $\frac{1}{4}$ " right down to  $\frac{3}{32}$ " (1mm). It's suitable for small, miniature and micro miniature joints.

Available for 220-250 volts or 100-120 volts. Weight –  $1\frac{1}{2}$  oz (40 gram). Length  $7\frac{1}{2}$ " (19cm). Price – £3.40 fitted with standard bit  $\frac{3}{32}$ " (2.3mm). Spare bits £0.46; £0.72; £0.84 exclusive of VAT.

Stocked by most of the well-known wholesalers and many retailers. Or direct from us if you are desperate.

Send for colour catalogue from:  
Antex Freepost, Plymouth PL1 1BR

Model X.25 is a general purpose soldering iron, also with two shafts for toughness and perfect insulation. Available for 220-250 volts or 100-120 volts at 25 watts and priced at £3.40 exclusive of VAT.




Stand model S.T.3 has a chromium plated steel spring, two sponges for cleaning the bits and is priced at £1.40 exclusive of VAT.



Mayflower House, Plymouth.  
Telephone (0752) 67377/8 Telex 45296  
Giro 2581000

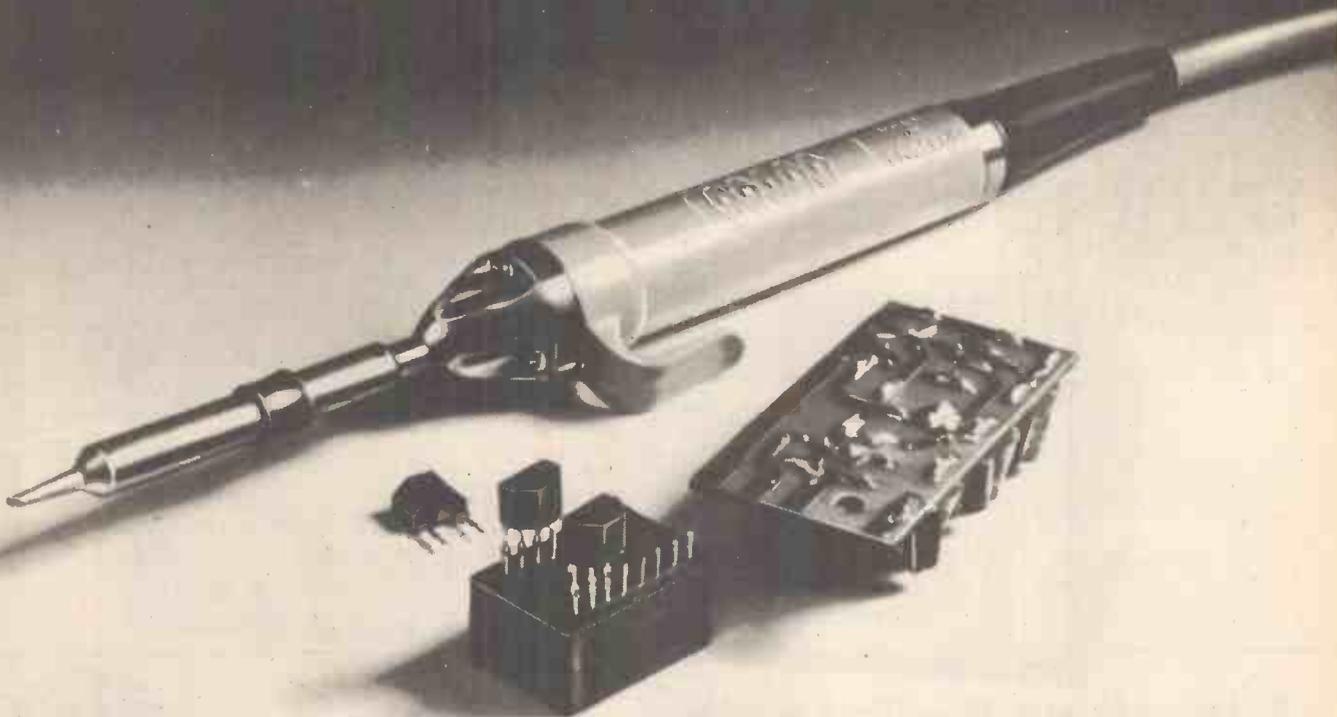Forget all you've ever read about  
miniaturised soldering irons.  
This is the NEW ANTEX CX.



# HIGH POWER DC-COUPLED AMPLIFIER



- ★ UP TO 500 WATTS RMS FROM ONE CHANNEL
- ★ DC-COUPLED THROUGHOUT
- ★ OPERATES INTO LOADS AS LOW AS 1 OHM
- ★ FULLY PROTECTED AGAINST SHORT CCT, MISMATCH, ETC.
- ★ 3 YEAR WARRANTY ON PARTS AND LABOUR

The DC300A Power Amplifier is the successor to the world famous DC300 which is so widely used in Industrial, and Research applications in this country. It is DC-coupled throughout so providing a power bandwidth from DC to over 20,000Hz. The ability of the DC300A to operate without fuss into totally reactive loads while delivering its full power, and maintaining its faithful reproduction of Pulse or complex waveforms has established the DC300A as the world's leading power amplifier. Each of the two channels will operate into loads as low as 1 ohm, and the amplifier can be rapidly connected as a single ended amplifier providing over 650 watts RMS into a 4 ohms load, and still providing a bandwidth down to DC. Below is a brief specification of the DC300A, but if you require a data sheet, or a demonstration of this fine equipment please let us know.

|   |                                    |                               |  |
|---|------------------------------------|-------------------------------|--|
| Power Bandwidth                                       | DC-20kHz @ 150 watts + 1db. - 0db. | Slewing Rate                  | 8 volts per microsecond                |
| Power at clip point (1 chan)                          | 500 watts rms into 2.5 ohms        | Load impedance                | 1 ohm to infinity                      |
| Phase Response  | +0. - 15° DC to 20kHz, 1 watt @Ω   | Input sensitivity             | 1.75 V for 150 watts into 8Ω           |
| Harmonic Distortion                                   | Below 0.05% DC to 20kHz            | Input impedance               | 10K ohms to 100K ohms                  |
| Intermod. Distortion                                  | Below 0.05% 0.01 watt to 150 watts | Protection                    | Short, mismatch & open cct. protection |
| Damping Factor  | Greater than 200 DC to 1kHz at 8Ω  | Power supply                  | 120-256V, 50-400Hz                     |
| Hum & Noise (20-20kHz)                                | At least 110db below 150 watts     | Dimensions                    | 19" Rackmount, 7" High, 9½" Deep       |
| Other models in the range: D60 — 60 watts per channel |                                    | D150A — 150 watts per channel |  |

Other models available from 100 watts to 3000 watts



## MACINNES LABORATORIES LTD.

MacInnes House, Carlton Park Industrial Estate  
Saxmundham, Suffolk IP17 2NL. Tel: (0728) 2262 2615

## MACINNES FRANCE

18 Rue Botzaris  
Paris 75019, France  
Tel: 206-60-80 or 206-83-61

WW-025 FOR FURTHER DETAILS

# Do you really need a synthesiser?

The Eddystone 1830 series of general purpose HF/MF communication receivers is widely used in marine, military, police, broadcasting and other professional applications. Using the optional crystal control facility, high stability performance is obtained at minimal cost.

Economy, simplicity and reliability are characteristics of the 1830 series. Continuous coverage is provided from 120 kHz to 30 MHz in 9 ranges, with reception facilities for CW, MCW, AM and SSB signals. Variants are available with modified coverage, and 50-channel crystal capability.

DCA NO: 10D/CA 10696




## Eddystone Radio Limited


Member of Marconi Communication Systems Limited

Alvechurch Road, Birmingham B31 3PP, England  
Telephone: 021-475 2231 Telex: 337081

A GEC-Marconi Electronics Company

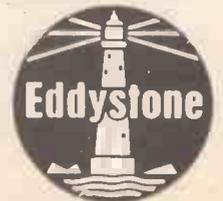

WW-059 FOR FURTHER DETAILS

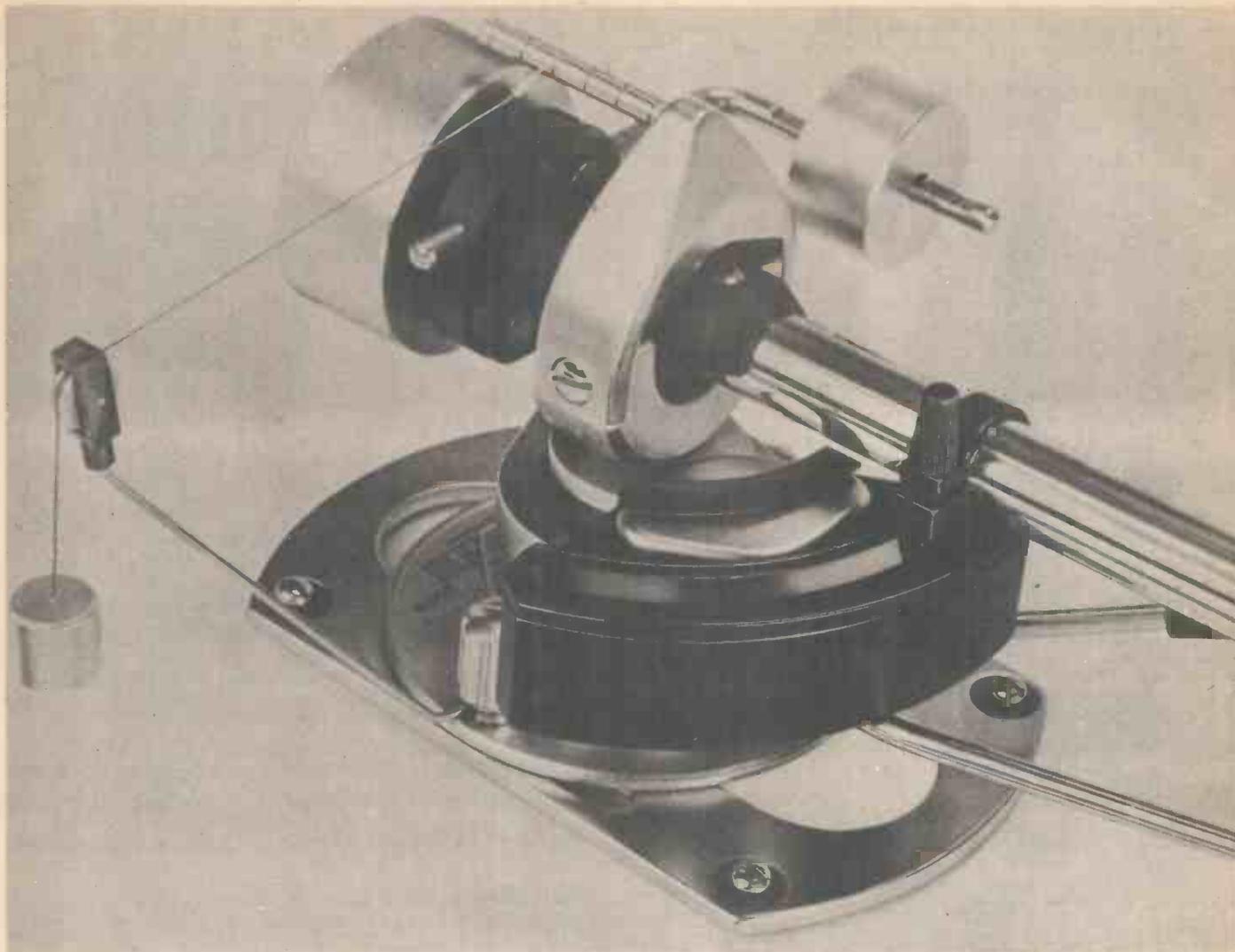


## 3009+FD200

The FD200 is a new accessory from SME: a fluid damping device which can be fitted, easily and quickly, to any Series II or Series II Improved arm. The benefits

of fluid damping have long been known: audibly improved bass and the reduction of spurious low frequencies; but these are not fully realised when the damping is applied at the bearings. For this reason the FD200 is designed to be fitted at a point along the length of the arm.

The FD200 design overcomes the usual problems of leakage and low efficiency. It offers a choice of two damping rates, to suit a wide range of cartridge compliances. The attractively presented kit includes ready-filled tank and full instructions.

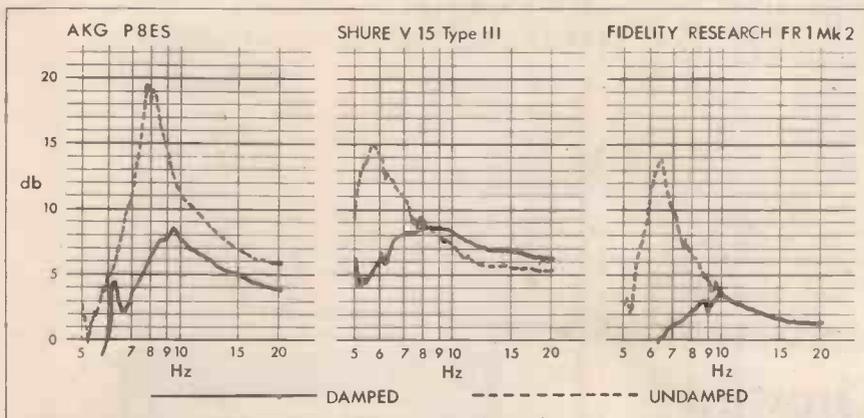Write to Dept 0643 · SME Limited  
Steyning · Sussex · England



The illustrations show typical extreme low frequency response characteristics of three cartridges in the Series II Improved arm. Note the substantial reduction in the Q of the low frequency resonance. Although

these frequencies are themselves outside the range of human hearing they give rise to undesirable side-effects which are audible.

# SME

The best pick-up arm in the world



\* Illustration actual size

## ORYX SUPER 30

The feature packed general purpose iron built to professional standards for only £2.95 + (8%vat)

When we introduced the Super 30 last year it was the best general purpose soldering iron at its price in Britain—it still is, at only £2.95p. (plus 8% VAT)

The ORYX Super 30 offers you all these features as standard: Neon safety light, Long life element, Iron coated screw-on tip, Stainless steel shaft, Styled handle, Two minute element change and a stainless steel clip-on hook.

Industrial Distributors include:  
Electroplan Ltd., Orchard Road,  
Royston, Herts SG8 5HH  
GDS (Sales) Ltd., 380 Bath Road,  
Slough, Berks SL1 6JE  
ITT Electronic Services, Edinburgh  
Way, Harlow, Essex CM20 2DF

### Greenwood Electronics

Greenwood Electronics, Portman Road, Reading, RG3 1NE  
Telephone: 0734-595844, Telex 848659

# Our forte



40,000 L series bench power supplies sold and 50% of the U.K. market is certainly a strong point in favour of buying Farnell.

The latest version provides either constant voltage or constant current, features large recessed meters, overload and short-circuit protection, coarse and fine adjustment controls, a separate output switch and LED indicators for mains on and current limit.

#### Models available

|                          |                 |
|--------------------------|-----------------|
| L50-05                   | 0-50V, 0.5A     |
| L30-1                    | 0-30V, 1A       |
| L10-3C*                  | 0-10V, 3A       |
| L30-2                    | 0-30V, 2A       |
| L30-5                    | 0-30V, 5A       |
| L12-10C*                 | 0-10V, 10A      |
| LT50-05 twin output unit | 2 x 0-50V, 0.5A |
| LT30-1 twin output unit  | 2 x 0-30V, 1A   |
| LT30-2 twin output unit  | 2 x 0-30V, 2A   |

\*with adjustable overvoltage protection

For full specification and prices contact:



FARNELL INSTRUMENTS LIMITED · SANDBECK WAY · WETHERBY · WEST YORKS  
LS22 4DH · TELEPHONE 0937-3541 · TELEX 557294 · LONDON TEL. 01-864 7433

WW — 081 FOR FURTHER DETAILS

WW — 076 FOR FURTHER DETAILS

# News of the Decade



**RESISTANCE  
CAPACITANCE  
INDUCTANCE**  
over 60 different models  
available, many from stock

CONTACT US IF YOU NEED MORE INFORMATION OR DEMONSTRATION

## DECADE BOXES

### "Junior" Series—Resistance—1%

| Model | Decades | Ohms Range    | Ohms Resolution | £     |
|-------|---------|---------------|-----------------|-------|
| J1    | 5       | 0— 1,111,100  | 10              | 33.20 |
| J2    | 5       | 0— 111,110    | 1               | 32.80 |
| J3    | 4       | 0— 111,100    | 10              | 27.00 |
| J4    | 4       | 0— 11,110     | 1               | 26.70 |
| J5    | 3       | 0— 11,100     | 10              | 22.20 |
| J6    | 3       | 0— 1,110      | 1               | 22.00 |
| J60   | 6       | 0— 1,111,110  | 1               | 40.00 |
| J70   | 7       | 0— 11,111,110 | 1               | 47.00 |

### "Junior" Series—Capacitance—1%

| Model | Decades | pF Range     | pF Resolution | £     |
|-------|---------|--------------|---------------|-------|
| JC1   | 3       | 100— 111,000 | 100           | 23.90 |
| JC2   | 2 + var | 30— 11,140   | "Infinite"    | 25.00 |

### "Point One" Series—Resistance—0.1%

| Model | Decades | Ohms Range     | Ohms Resolution | £      |
|-------|---------|----------------|-----------------|--------|
| R3    | 4       | 0— 1,111       | 0.1             | 53.40  |
| R4    | 4       | 0— 11,110      | 1               | 53.10  |
| R5    | 4       | 0— 111,110     | 10              | 52.20  |
| R7    | 5       | 0— 1,111,100   | 10              | 64.80  |
| R9    | 5       | 0— 111,110     | 1               | 65.50  |
| R10   | 5       | 0— 11,110      | 0.1             | 66.00  |
| R11   | 5       | 0— 11,111,000  | 100             | 75.40  |
| R20   | 6       | 0— 1,111,110   | 1               | 78.50  |
| R21   | 6       | 0— 111,111     | 0.1             | 79.50  |
| R22   | 6       | 0— 11,111.1    | 0.01            | 86.40  |
| R30   | 7       | 0— 11,111,110  | 1               | 99.10  |
| R31   | 7       | 0— 1,111,111   | 0.1             | 92.10  |
| R32   | 7       | 0— 111,111.1   | 0.01            | 92.80  |
| R41   | 8       | 0— 11,111,111  | 0.1             | 112.50 |
| R42   | 8       | 0— 1,111,111.1 | 0.01            | 108.00 |

### "Hundred" Series—Resistance—0.03%

| Model | Decades | Ohms Range    | Ohms Resolution | £      |
|-------|---------|---------------|-----------------|--------|
| R400  | 4       | 0— 111,100    | 10              | 96.00  |
| R401  | 4       | 0— 11,110     | 1               | 100.50 |
| R402  | 4       | 0— 1,111      | 0.1             | 101.60 |
| R403  | 4       | 0— 111.1      | 0.1             | 108.60 |
| R600  | 6       | 0— 11,111,100 | 10              | 130.60 |
| R601  | 6       | 0— 1,111,110  | 1               | 132.90 |
| R602  | 6       | 0— 111,111    | 0.1             | 135.20 |
| R603  | 6       | 0— 11,111.1   | 0.01            | 141.60 |
| R701  | 7       | 0— 11,111,110 | 1               | 154.80 |
| R702  | 7       | 0— 1,111,111  | 0.1             | 157.10 |
| R703  | 7       | 0— 111,111.1  | 0.01            | 162.90 |
| R802  | 8       | 0— 11,111,111 | 0.1             | 176.20 |

## DECADE BOXES continued

| Model                                   | Decades | Ohms Range     | Ohms Resolution | £      |
|---|---------|----------------|-----------------|--------|
| R803                                    | 8       | 0— 1,111,111.1 | 0.01            | 179.10 |
| <b>High Dissipation—Resistance—1%</b>   |         |                |                 |        |
| HD1                                     | 5       | 0— 1,111,100   | 10              | 110.00 |
| HD1/L                                   | 5       | 0— 111,110     | 0.2 Approx.     | 115.80 |
| <b>"Point One" Series—Inductance—5%</b> |         |                |                 |        |
| L1                                      | 3       | 0— 1,110       | mH Resolution   | £      |
| L2                                      | 2       | 0— 110         | 1               | 100.40 |
| L3                                      | 2       | 0— 1,100       | 10              | 70.50  |
| <b>"Hundred" Series—Inductance—0.3%</b> |         |                |                 |        |
| L300                                    | 3       | 0— 1,110       | mH Resolution   | £      |
| L400                                    | 4       | 0— 11,110      | 1               | 290.90 |
|   |         |                |                 | 378.00 |

## CAPACITANCE BOXES

| Model                                | Decades | pF Range       | pF Resolution | Accuracy | £       |
|--------------------------------------|---------|----------------|---------------|----------|---------|
| C3                                   | 3       | 100— 111,000   | 100           | 1%       | 51.90   |
| PC3                                  | 3       | 100— 111,000   | 100           | 0.5%     | 71.70   |
| C4                                   | 4       | 100— 1,111,000 | 100           | 1%       | 79.10   |
| PC4                                  | 4       | 100— 1,111,000 | 100           | 0.5%     | 111.60  |
| <b>Decade plus Variables</b>         |         |                |               |          |         |
| VC4                                  | 3       | 50— 111,150    | INFINITE      | 1%       | 65.60   |
| VC5                                  | 4       | 50— 1,111,150  | ..            | 1%       | 92.80   |
| PVC5                                 | 4       | 50— 1,111,150  | ..            | 0.5%     | 138.50  |
| SVC5                                 | 4       | 50— 1,111,150  | ..            | 0.05%    | 679.00  |
| C500                                 | 4       | 50— 1,111,150  | ..            | 0.2%     | 256.40† |
| SVC5 special. Details on application |         |                |               |          |         |
| <b>Variables</b>                     |         |                |               |          |         |
| PVC1 Mk. 2                           |         | 5— 200         |               | 0.5%     | 131.70  |
| PVC2 Mk. 2                           |         | 20— 1,120      |               | 0.5%     | 118.70  |
| VC2                                  |         | 20— 1,130      |               | 1%       | 45.80   |
| PVC4                                 |         | 0— 10          |               | 1%       | 83.00   |
| PVC1/S                               |         | 20— 120        |               | 0.5%     | 79.40   |
| <b>Switched</b>                      |         |                |               |          |         |
| C140                                 |         | 0— 140         | 1.0           | 5%       | 167.70† |
| C100                                 |         | 0— 100         | 1.0           | 5%       | 141.90† |
| C60                                  |         | 0— 61          | 0.1           | 5%       | 126.40† |
| C60P                                 |         | 0— 61          | 0.1           | 1%       | 256.90† |

† Packing and Handling extra. Prices do not include VAT



**J.J. Lloyd  
Instruments Ltd**

Brook Avenue, Warsash, Southampton SO3 6HP  
Tel: Locks Heath 4221

WW—067 FOR FURTHER DETAILS

# FAST RESPONSE STRIP CHART RECORDERS

Made in USSR

## Series H3020



Basic error: 2.5%  
Sensitivity: 8mA F.S.D.  
Response: 0.2 sec.  
Width of each channel:  
Single and three-pen  
recorders: 80mm  
Five-pen recorders: 50mm

Chart speeds, selected by push buttons: 0.1-0.2-0.5-1.0-2.5-5.0-12.5-25 mm/sec.

Chart drive: 200-250V 50Hz

Recording: Syphon pen directly attached to moving coil frames.  
Curvilinear co-ordinates.

Equipment: Marker pen, timer pen, paper footage indicator, 10 rolls of paper, connectors, etc.

**H3020-1 (Single pen):** 285mm wide x 384mm deep x 165mm high  
PRICE £108.00

**H3020-3 (Three pen):** 475mm wide x 384mm deep x 165mm high  
PRICE £160.00

**H3020-5 (Five pen):** 475mm wide x 384mm deep x 185mm high  
PRICE £295.00

## Series H327



Polarized moving iron movements with syphon pens directly attached. Built-in solid state amplifier (one per channel) provides 8 calibrated sensitivity steps. Two marker pens are provided.  
Basic error 4%. Frequency response from DC to 100Hz 2dB.

Sensitivity: 0.02 - 0.05 - 0.1 - 0.2 - 0.5 - 1 - 2 - 5 volts/cm

Width of each recording channel: 40mm

Chart drive: 220-250V 50Hz

Chart speeds: 1-2-5-10-50-125-250mm/sec.

**Type H3271-1. Single pen:** Dimensions: 259 x 384 x 165mm  
Weight 15 kilos PRICE £265.00

**Type H327-3. Three pen:** Dimensions 335 x 384 x 165mm  
Weight 20 kilos PRICE £520.00

**Type H327-5. Five pen.** Dimensions: 425 x 385 x 165mm.  
Weight 25 kilos PRICE £770.00.

Note: Prices are exclusive of VAT

Available for immediate delivery

# Z & I AERO SERVICES LTD.

44A WESTBOURNE GROVE, LONDON W2 5SF

Tel. 01-727 5641


Telex: 261306

WW — 053 FOR FURTHER DETAILS

## The Quickest, Simplest Way of Punching Holes in Sheet Metal

Q-Max punches make clean, accurate holes every time. In no time. With no filing, no jagged edges, virtually no burrs—with no hard work. And no holes are barred. Round or square. Q-Max punches are available in sizes down to 10mm up to 75mm for use on sheet metal up to 16 gauge. No wonder they're used by all government services (Atomic, Military, Naval, Air, GPO, Ministry of Works) and all over the world by radio, motor and industrial manufacturers, plumbing and sheet metal trades and garages.

57  
metric  
and linear  
sizes

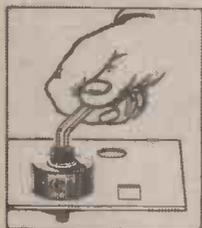

# Q-MAX

SHEET METAL PUNCHES

Wholesale and Export enquiries welcomed. Further details from,

**"Q-MAX" (ELECTRONICS) LTD**

44 PENTON STREET · LONDON N1 9QA Tel: 01-278 2500

WW—101 FOR FURTHER DETAILS

# Test Equipment

## Multimeters



The Eagle range of multimeters covers every possible need of the electrical or electronic engineer. They cost from about £6 to £58 (inc V.A.T.). There's at least one which suits your job precisely.

We have a lot of other test equipment too. Send the coupon and we'll send you our complete catalogue.



Please send me details of all your test equipment.

NAME

ADDRESS

Eagle International, Precision Centre, Heather Park Drive,  
Wembley HA0 1SU Tel: (01)-902 8832

# Eagle

WW/4



**If you  
can hand clean  
a board  
for 12p**

**...keep up the  
hard work.**

## **An 'Arklone' cleaning plant costs £410**

There has never been a stronger case for solvent cleaning with Arklone 'K'. Combining efficiency, simplicity, speed, safety and surprising economy in use, Arklone 'K' has rapidly become the firm-favourite solvent choice of Britain's leading electronics companies for cleaning p.c. boards. And in times when labour is increasingly expensive, old-fashioned hand-wiping could be making a sizeable hole in your profits.

Installation of a solvent cleaning plant is unlikely to break your bank—when for less than £500 you could be set up in business, and the improvements you'll get in results

are really quite dramatic. Arklone 'K' not only searches out flux and contamination from even the most inaccessible places, but also dries perfectly cleanly—leaving no problems of residue or stain. And, of course, as your throughput goes up, your labour bill and unit cleaning costs go down. So you recover your capital outlay in next to no time. You won't need much space either—because the plants made specially by ICI to suit the solvent are neat and compact.

You'll find solvent cleaning with Arklone 'K' makes a very good deal of sense. So clip out the coupon and do yourself a good deal.

 **'Arklone'K**  
for effective low-cost cleaning

**To: ICI Mond Division, P.O. Box 13,  
The Heath, Runcorn, Cheshire  
WA7 4QF**

Please send me more details of  
electronics cleaning with Arklone 'K'

Name


Position

Company

Address

ICI Mond Division, P.O. Box 13, The Heath, Runcorn, Cheshire WA7 4QF England

# FOR THICK FILM PRODUCTS

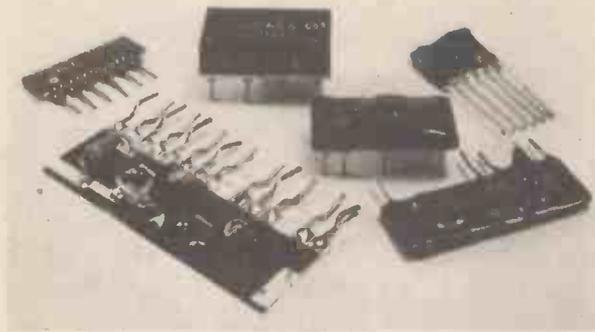

**SAY**



As the leading Thick Film manufacturer in the U.K., Erie are the obvious choice for these cost saving, highly reliable products, with over twelve years experience in the design and production of Passive and Hybrid Thick Film circuits.

Erie offer a comprehensive range of units including:-

Dual In Line Custom designed and Standard Resistor Networks in Ceramic Sandwich and Plastic Transfer Moulded formats.

Single In Line Custom designed and Standard Resistor Networks.

Power Resistors with Pluggable terminations, and High Value High Voltage wire ended Resistors.

Our experience, engineering and production facilities enable us to offer hybrid circuits in a variety of formats including Dual and Single In Line conformally coated and transfer moulded packages for a wide range of applications.

For more information about Thick Film contact:-

**ERIE ELECTRONICS LIMITED**

Resistor Division


South Denes, Great Yarmouth, Norfolk.

Tel: 0493 56122 Telex: 97421

Components **ITT**

WW-094 FOR FURTHER DETAILS

## METER PROBLEMS?

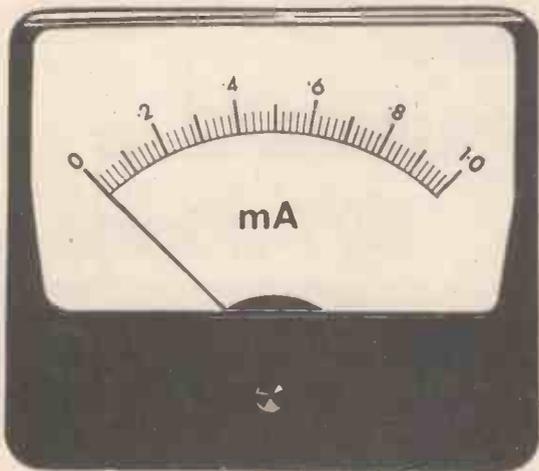

137 Standard Ranges in a variety of sizes and stylings available for 10-14 days delivery. Other Ranges and special scales can be made to order.

Full Information from:

**HARRIS ELECTRONICS (London)**

138 GRAYS INN ROAD, W.C.1 Phone: 01/837/7937

WW - 039 FOR FURTHER DETAILS

**NEAL** STEREO

**NEAL** 3 CHANNEL AUDIO VISUAL

**NEAL** 4 CHANNEL RECORDERS



CASSETTE  
RECORDERS  
FOR THE  
PROFESSIONAL  
USER

Special models  
to order

NEAL Range includes:  
102, 103 STEREO DOLBY  
110 MONO AV DOLBY

102AV, 103AV STEREO AV DOLBY  
140SERIES 4 CHANNEL  
104 HEAVY DUTY REPLAY

**NEAL**

**TRANSCRIPTION CASSETTE RECORDERS**

NORTH EAST AUDIO LIMITED


5 Charlotte Square, Newcastle upon Tyne NE1 4XE. Telephone (0632) 26660

WW-041 FOR FURTHER DETAILS

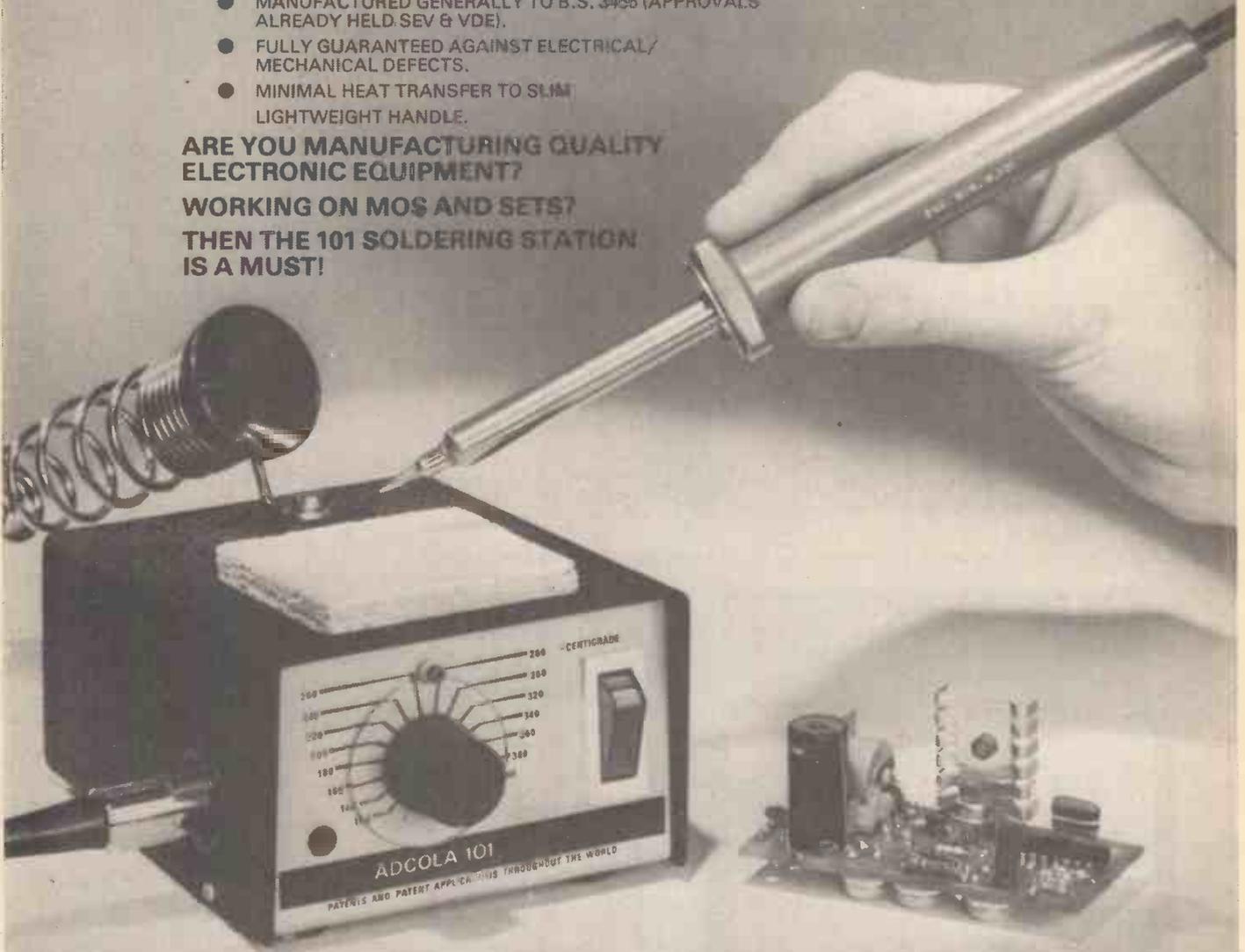
# SOPHISTICATION IN SOLDERING

- TEMPERATURE ACCURACY  $\pm 2\%$  OF INDICATED DIAL TEMPERATURE
- ELECTRONIC CONTROL (NO MOVING PARTS).
- FULLY EARTHED SYSTEM.
- RADIO SUPPRESSED WITH NO MAINS "SPIKING".
- LOW VOLTAGE ON ACTUAL SOLDERING INSTRUMENT.
- A SELECTION OF ELEVEN "ADIRON" BIT PROFILES.
- MANUFACTURED GENERALLY TO B.S. 3456 (APPROVALS ALREADY HELD SEV & VDE).
- FULLY GUARANTEED AGAINST ELECTRICAL/MECHANICAL DEFECTS.
- MINIMAL HEAT TRANSFER TO SLIM LIGHTWEIGHT HANDLE.

**ARE YOU MANUFACTURING QUALITY  
ELECTRONIC EQUIPMENT?  
WORKING ON MOS AND SETS?  
THEN THE 101 SOLDERING STATION  
IS A MUST!**



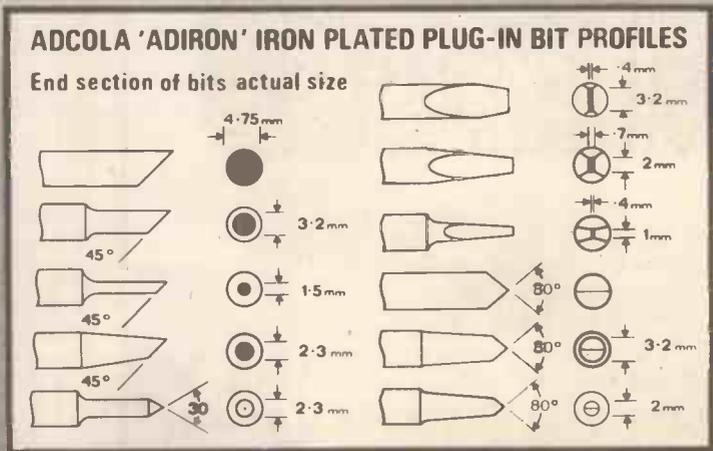THIS UNIT WILL BE ON SHOW AT THE  
**INTERNATIONAL LONDON ELECTRONIC  
COMPONENTS SHOW  
OLYMPIA MAY 17-20 1977**  
FULL TECHNICAL INFORMATION  
CAN BE OBTAINED FROM  
**ADCOLA PRODUCTS LIMITED  
ADCOLA HOUSE LONDON SW4 6LH**  
TELEPHONE 01-622 0291/3  
TELEX 21851 ADCOLA



# The measure of our success.

**MAJOR Multimeter**  
£34.30



41 Ranges  
40 Kohm/V DC & AC  
1200V AC & DC. 3 Amps  
dB - Frequency - Capacitance Ranges.

**Signal Injector**  
£7.50



Useful for both valve and transistorised equipment.  
Frequencies up to 500MHz VHF & UHF  
Pen type style.

**Transistor Tester**  
£24.65



In Circuit Tester  
NPN & PNP Signal  
& Power Devices. Clear Colour Zone Scale.

**CITO Multimeter**  
£14.00



30 Ranges  
10 Kohm/V DC  
1.5KV AC. 1 Amp DC.  
Resistance & dB Ranges.

**Capacitance Meter** £27.50



Range 50pF to 0.5pF  
5 Ranges. Clear Scale.

Precision Instrument Laboratories have rapidly become the most comprehensive instrument stockist in the U.K. Shown above are just 5 of the instruments that we have available for the Radio and Television engineer.

Our full range includes Oscilloscopes, DVM's, Field Strength Meters, Valve Testers, Logic Probes and Colour Bar Generators.

Instruments Electrical Co. Ltd., the repair associate company of P.I.L., offer a complete repair service on all these and many other types of instrumentation.

## PIL IEC


Precision Instrument Laboratories  
Instruments Electrical Co. Ltd  
Instrument Hse., 212 Ilderton Road  
London SE15 1NT. Tel: 01-639 0155  
or North London. Tel: 01-965 2352

Items illustrated may be purchased by enclosing a cheque for amount shown + 8% VAT. Wholesale Enquiries Welcome.

## FREQUENCY COUNTERS

1/10 Hz to 1.2GHz

High performance instruments measuring frequency, period, time, freq./ratio and calibrated output facility. Fast delivery. Specials by arrangement.

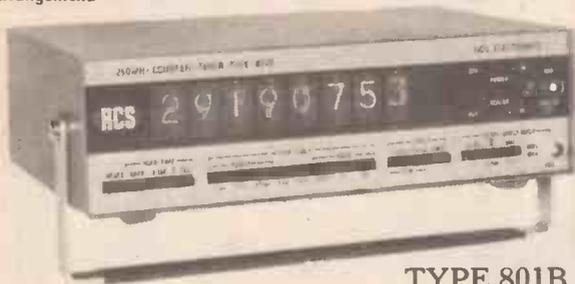

TYPE 801B

CRYSTAL OVEN  
OPERATING MANUAL  
TWO TONE BLUE CASE

£274 250 MHz

Sensitivity 10mV. Stability 5 parts 10.<sup>10</sup>

Resolution ± 1 Count

|        |                     |       |                     |
|--------|---------------------|-------|---------------------|
| 301M   | 32MHz 5 Digit £95   | 401A  | 32MHz 6 Digit £132  |
| 501    | 32MHz 8 Digit £188  | 701A  | 80MHz 8 Digit £205  |
| 8018/M | 250MHz 8 Digit £274 | 901M  | 520MHz 8 Digit £375 |
|        |                     | 1001M | 1.2GHz 8 Digit £670 |

Start/Stop versions plus £15 Memory versions available if not suffixed M £25 extra

Type 101 1MHz 100KHz 10 KHz Crystal Standard £95  
Type 103 Off/Air Standard £95

SUPPLIERS TO: Ministry of Defence, G.P.O., B.B.C., Government Depts., Crystal Manufacturers and Electronic Laboratories world-wide



**R.C.S. ELECTRONICS**  
6 WOLSEY ROAD, ASHFORD  
MIDD. TW15 2RB  
Telephone: Ashford (Code 69)  
53661/2

WW-56 FOR FURTHER DETAILS

## 745 COUNTER TIMER

DC-32 MHz

FREQUENCY, PERIOD, TIME & TOTALISE

± 5ppm STABILITY @ 25°C



745 COUNTER TIMER £94 + £2.50 p&p WW009

Other products include:


|                         |      |        |
|-------------------------|------|--------|
| 744 Counter Timer       | £85  | WW 010 |
| 643 Function Generator  | £98  | WW 011 |
| 643A Function Generator | £85  | WW 012 |
| 631 Filter Oscillator   | £108 | WW 013 |

Delivery is normally ex-stock — telephone for confirmation  
Prices correct at time of going to press, subject to change without notice

**OMB electronics, Riverside, Eynsford, Kent. Tel: 0322 863567**

TICK THE APPROPRIATE REPLY NO. FOR DETAILS

## TELFORD COMMUNICATIONS

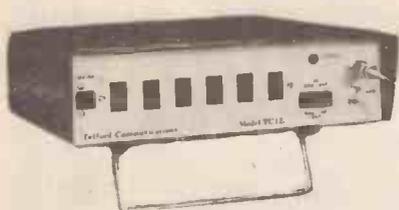

TC12 Freq. Counter  
10Hz to 200MHz



TC15 Inductance Bridge  
1uH to 20H



TC14 Cap. Meter  
1pf to 1uf.

Measure rapid and accurately with Telford Digital Test Equipment. Suppliers to Industry and Educational Establishments World Wide.

78B HIGH STREET, BRIDGNORTH WV16 4DS, SALOP, ENGLAND. TEL. 074-62 4082

WW-071 FOR FURTHER DETAILS

ELECTRONORGTECHNICA

## carbon film RESISTORS

1/8 and 1/4w 70°C 5% tol. E.12

EX-STOCK

**£4.90 PER 1,000** PLUS & POSTAGE  
OF ONE VALUE V.A.T.

Minimum export order £100

Contact John Gingell




**AERO SERVICES LTD.**

44A Westbourne Grove  
London W2 5SF  
TEL: 01-727 5641 TELEX 261306

WW — 055 FOR FURTHER DETAILS

## JES AUDIO INSTRUMENTATION

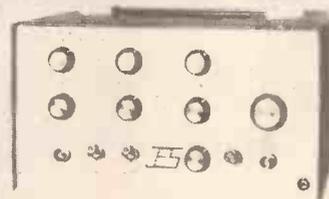

Illustrated the Si452  
Distortion Measuring  
Unit—low cost distortion  
measurement down  
to .01% £48.00

|                              |           |                           |        |
|------------------------------|-----------|---------------------------|--------|
| Si451                        | £60.00    | Si453                     | £60.00 |
| Comprehensive Millivoltmeter |           | Low distortion Oscillator |        |
| 350µ Volts                   | 20 ranges | sine — square — RIAA      |        |

prices plus VAT

**J. E. SUGDEN & CO. LTD.** Tel. Cleckheaton (0274) 872501  
CARR STREET, CLECKHEATON, W. YORKSHIRE B19 5LA

WW-048 FOR FURTHER DETAILS

# ESP Capacitance measuring




ESP 100 A  
1 pF to 10  $\mu$ F

Portable  
£49.00 + V.A.T.

ESP 200 A  
0.1 pF to 50  $\mu$ F

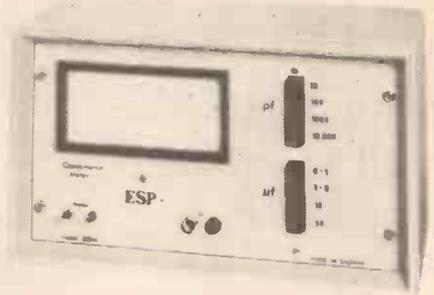Wide scale  
laboratory model  
£120.00 + V.A.T.



ESP 300 A  
1 pF to 2,000  $\mu$ F

Autorange  
capacitance bridge  
£235.00 + V.A.T.

See all  
our products  
on display at  
THE METAC  
ELECTRONICS CENTRE  
NEW ARCADE  
HIGH ST.  
UXBRIDGE

**ESP**

MIDDLE MARCH  
LONG MARCH INDUSTRIAL ESTATE  
DAVENTRY  
NORTHANTS NN11 4PQ  
Telephone: (03272) 76720

STAND 554C  
LECS OLYMPIA  
17-20 MAY 1977


A complete range of British-made instruments designed to simplify capacitance measuring.

- Accurate and sensitive
- Requires no manual balancing
- Takes less than a second to measure a capacitor
- Updates changes in capacitance automatically
- Wide range of applications

Send for technical literature and free booklet: "Modern methods of capacitance measuring"

Suppliers to: Ministry of Defence, Post Office, B.B.C., Government departments and Electronic Laboratories world-wide.

WW — 091 FOR FURTHER DETAILS

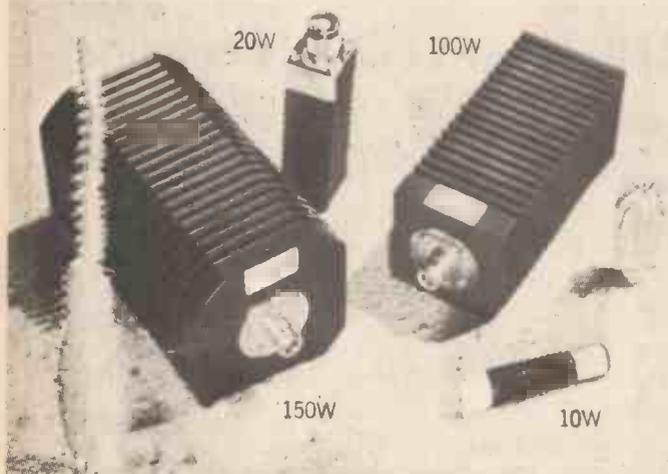

## PAY LESS FOR LOADS?

With nearly 3 decades of experience built into every TERMALINE® Coaxial Load Resistor, buying BIRD will often cost no more or save you money. BIRD QC Quick-Change Connectors on many models offer a choice of any common RF connector, eliminating the need for performance-degrading adapters.

Twenty aircooled dry Loads (2W to 225W), thirteen aircooled liquid Loads (20W to 5kW) and nineteen watercooled TERMALINE® models (1kW to 50kW) are listed in our 1977 Catalog. Ask for it.

EXCLUSIVE U.K. REPRESENTATIVE FOR BIRD ELECTRONICS


**aspen**

**electronics limited**

2 KILDARE CLOSE, EASTCOTE, MIDDX. HA4 9UW.

Tel: 01-868 1188. Telex: 8812727

WW — 014 FOR FURTHER DETAILS

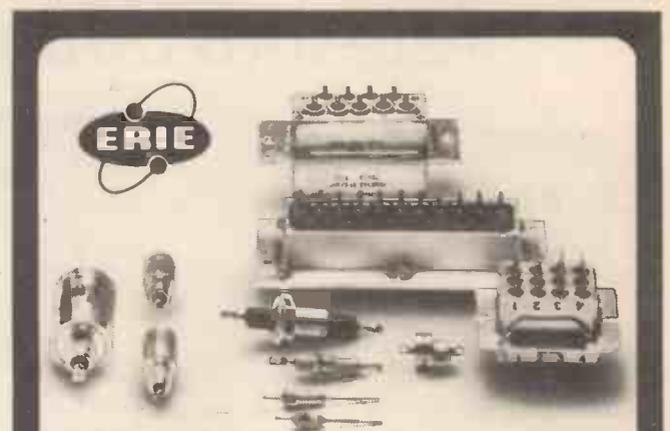

## FOR R.F.I. SAY ERIE.

When your problem is elimination of R.F.I., space and weight are at a premium and reliable performance is essential, specify ERIE Filters.


Erie Technological Products of Canada are the worlds largest volume producer of R.F.I. low pass suppression filters and filter assemblies for aerospace and defence systems. Their position as world leader in the field of miniature R.F.I. filters is a matter of record, for no other company has comparable capability in-house.

For the latest information on "state of the art" miniature R.F.I. filters contact:-

**ERIE ELECTRONICS LIMITED**  
Resistor Division  
South Denes, Great Yarmouth, Norfolk.  
Tel: 0493 56122 Telex: 97421

Components **ITT**

WW—095 FOR FURTHER DETAILS

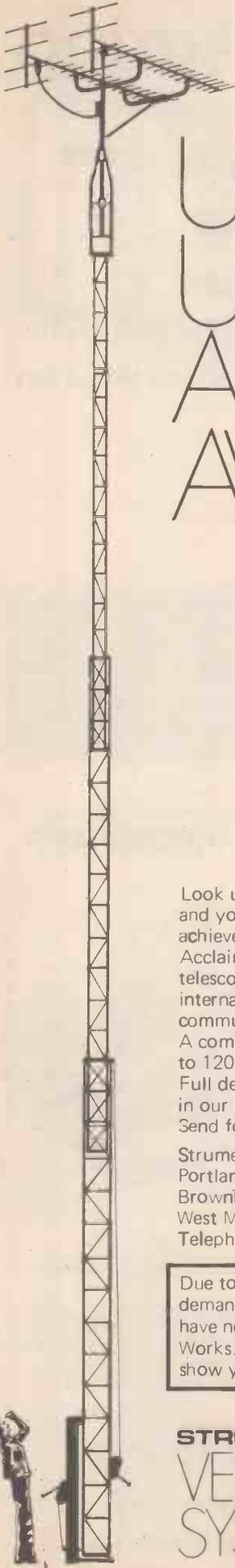

UP  
UP  
AND  
AWAY!

Look up to a Versatower installation and your radio communications will achieve new heights! Acclaimed as the World's leading telescopic tilt-over tower in the international field of radio communication.

A complete range of models: from 20 to 120 feet, static and mobile. Full details and specifications are in our brochure. Send for it today!

Strumech Engineering Limited,  
Portland House, Coppice Side,  
Brownhills, Walsall,  
West Midlands WS8 7EX.  
Telephone: Brownhills 4321

Due to the enormously increased demand for Versatower systems we have now opened our new West Works. Phone us — we'll be glad to show you around.

**STRUMECH**  
VERSATOWER  
SYSTEM



WW — 068 FOR FURTHER DETAILS

If it's  
good enough  
for us...



... the Digitron 175 could solve YOUR temperature measurement problem

We evaluated most of the digital thermometers on the market and the Digitron 175 came out the best buy on almost every count. The unique auto-ranging facility gives the user the advantage of a wide temperature span without having to select individual ranges.

Automatic cold junction compensation and automatic zeroing gives a high degree of accuracy and reliability. All readings taken throughout the range  $-50$  to  $+1200^{\circ}\text{C}$  are shown on a clear bright LED seven-segment display. A range of interchangeable Type K thermocouple probes are available. The instrument is supplied in an attractive carrying case which can accommodate several alternative probes and the unit is available powered from dry batteries or with an optional rechargeable battery pack and charger.

Contact Electroplan today and put us to the test.

Electroplan Ltd., P.O. Box 19,  
Orchard Road, Royston, Herts, SG8 5HH.  
Tel: Royston (0763) 41171 Telex: 81337

**electroplan**  
a service to measurement

An Electrocomponents Group Company.

WW—090 FOR FURTHER DETAILS

Rechargeable power sources, calibration and potentiometric measurement, d.c. power supplies, tools and accessories, frequency counter-timers, digital multimeters, digital panel meters.

temperature measurement, laboratory instruments, hard copy recording, oscilloscopes and accessories, analogue multimeters, signal sources, logic test equipment, computer peripherals

# Priced too low for comfort?

No need to worry: it's an Exact Model 121 swept-frequency waveform generator, with all of the quality assurance that superb breeding brings. You may wonder what corners have been cut to get the price down to £225.00  
Relax, the answer is 'None'



Dana/Exact Model 121

- Sine, square, triangle, pulse & ramp waveforms over 0.02 Hz to 2.2 MHz
- Most compact, but rugged: 18.7 cm wide by 21.6 cm deep by 7.3 cm high
- 10 V peak-to-peak signal into a 50-ohm load (20 V open circuit)
- Internal sweep generator to sweep the main generator with a 3-decade sweep width
- Sweep rate adjustable from 1 ms to 10 s
- 60 dB attenuation on low output, using the 30 dB variable amplitude control

# DANA

Others measure by us.

Makers of High-quality Instruments: Frequency Counters

Digital Voltmeters

Dana Electronics Ltd.,

Collingdon Street,

Luton, Beds. Telex: 82430

Telephone: 0582 24236

Waveform Generators


Communications Test Equipment

Microwave Counters

Frequency Synthesizers

WW — 092 FOR FURTHER DETAILS

## BULK ERASURE PROBLEMS?

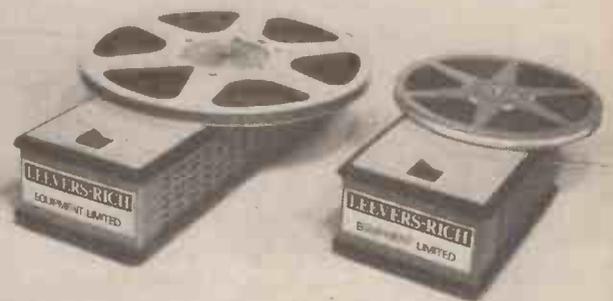

**LR71**

MAX REEL SIZE 11 1/2"

**LR70**

MAX REEL SIZE 8 1/4"

If it's personal we can only advise a diet or joining weightwatchers. If it's to do with tape, then why not consider the LR70/71 bulk tape erasers. They are simple to operate and will erase cassettes, cartridges and reels of tape up to a maximum reel size of 11 1/2" and tape width of 1", quickly and efficiently within the time it takes to read this advertisement.

The LR70/71 bulk erasers are currently used in Broadcast Companies, Recording Studios, Government Departments, Educational Establishments and the Computer Industry.

Moderately priced and available from:

**LEAVERS-RICH EQUIPMENT LIMITED**

INCORP. BIAS ELECTRONICS

319 Trinity Road, Wandsworth, London SW18 3SL

Telephone 01-874 9054

Cables: Leemag London SW18. Telex 923455 Wembley

WW—085 FOR FURTHER DETAILS

# OUTSIDE UK?

ELECTRONICS EXPORT

List requirements for return quotation. Or send for details of a purchasing service.

integrated circuits  
capacitors  
resistors  
heatsinks  
diodes  
cases  
switches  
transistors  
tools  
transformers  
c-mos t.t.l.  
l.s.i. linear  
etc.

TRIANGLE DIGITAL SERVICES  
BCM 8477  
LONDON WC1V 6XX



WW — 073 FOR FURTHER DETAILS

IRAN U.A.E. AUSTRALIA INDIA NIGERIA ITALY YUGOSLAVIA SINGAPORE ISRAEL TUNISIA PORTUGAL SPAIN DENMARK GERMANY BRAZIL GREECE PAKISTAN BAHREIN TURKEY NETHERLANDS

**Gardners**

# The Best of British

Where performance is paramount, professionals prefer Gardners...

We, at Gardners, have been in the communications business for many more years than we care to remember — so have our Audio Transformers. Used throughout the world by leading broadcasting and recording companies or wherever only the highest technical standards and levels of reliability are good enough our products are still preferred by professionals who know...

From microphone to tape (or film), speakers or headphones, studio consoles, manpacks, amplifiers, modems, we at Gardners have tried to anticipate your needs. Miniaturisation (yes!) plus good performance (yes!) through to exceptional performance (of course!). Impedance changing, coupling, isolation, bridging, low and high power, with or without D.C. Choose from our standard range of 95 models! Every one an example of sheer professionalism.

All have low loss, low distortion, low phase-shift, low pick-up, BUT wide frequency range.

| Cat. No. | Impedance Input | Impedance Output (OHMS) | Turns Ratio Sec/Pri | Operating Level dBm at 50Hz | Frequency Response                          |
|----------|-----------------|-------------------------|---------------------|-----------------------------|---|
| MU 7501  | 0.3/15          | 100k                    | 83/188:1            | 8                           | ± 1 dB<br>50Hz-10kHz                        |
| MU 7503  | 0.200/600       | 100k                    | 13/23:1             |                             |   |
| MU 7514  | 600             | 600/2.4k                | 1 + 1:1             |                             |   |
| MU 7518  | 10k CT          | 10k                     | 1:1 CT              |                             |   |
| MU 7521  | 3.75/15         | 600 CT                  | 6.32/12.64:1        | 16.5                        | ± 0.8 dB<br>30Hz-20kHz<br>(± 1 dB at 20kHz) |
| MU 7522  | 3.75/15         | 100k*                   | 82/164:1            |                             |   |
| MU 7524  | 180/600         | 600 CT                  | 1/2:1               |                             |   |
| MU 7525  | 600 CT          | 300/1.2k                | 1 + 1:1.41 CT       |                             |   |
| MU 7530  | 10k CT          | 10k                     | 1:1 CT              | 12                          | ± 0.5dB 10Hz-100kHz                         |
| MU 7534  | 50/200          | 100k*                   | 22.4/44.8:1         |                             |   |
| MU 7556  | 600 CT          | 10k/2.5k                | 4.08/2.04:1         |                             |   |
| MU 7567  | 600/150         | 50k                     | 9.13/18.26:1        |                             |   |
| MU 7582  | 200/50          | 600 CT                  | 1.73/3.46:1         | 20                          | ± 1dB 30Hz-22kHz                            |
| VM 7461  | 15/3.75         | 600                     | 6.35/12.7:1         |                             |   |
| VM 7464  | 600/150         | 600                     | 1/2:1               |                             |   |
| VM 7466  | 600             | 10k/2.5k                | 4.14/2.07:1         |                             |   |
| VM 7468  | 50/12.5         | 50k                     | 32/64:1             | 4.75                        | ± 1dB 30Hz-12kHz                            |

We would emphasise that the above is a representative selection only. Send for Brochure GT5 for complete listings. All units described are normally AVAILABLE FROM STOCK.

**SPECIAL DESIGN SERVICE.** If your requirements cannot be met by our standard range, then we will gladly design for your production needs.



**Gardners**


Gardners Transformers Ltd.  
Christchurch Dorset BH23 3PN  
Telephone 02015-2284  
Telex 41276 Gardners XCH  
Approved manufacturers of  
electronic transformers, modular power supplies, inverters and  
converters to Defence Standard 05-21

WW 5/77

WW-086 FOR FURTHER DETAILS

# Cut costs by 50% with the same high performance.
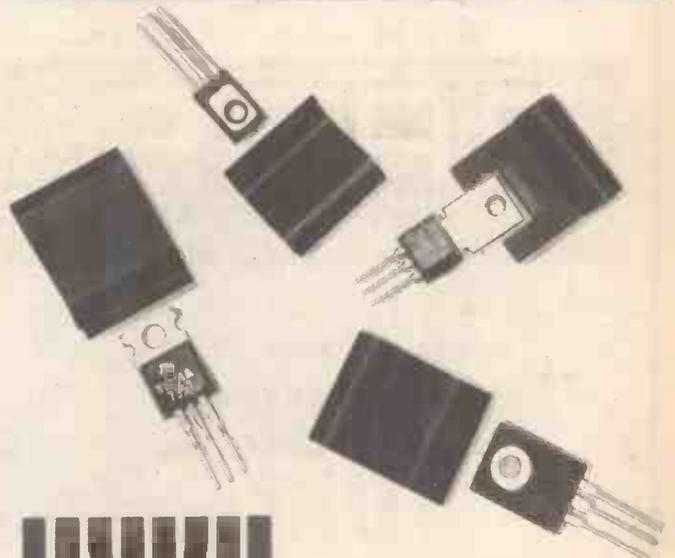
## Isn't that what new ideas are all about?



Light in weight and low in cost, new Thermalloy heat sinks are designed specifically for plastic or metal case power devices.

They are remarkably simple to use, no extra mounting hardware is required — and they can be attached to the device after board assembly.

The slip on types have positive retention and can be supplied with locking tabs.

For full details of the range, simply return the coupon — cutting costs without cutting performance is a good idea you ought to know about.



**Thermalloy**

MCP Electronics Ltd. Alpertons, Wembley, Middlesex  
Tel: 01-902 5941.



Please send me full details on Thermalloy heat sinks.

Name \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

Tel: \_\_\_\_\_


WW 5/77

# F.M. MODULES, KITS & TUNERS by

# Icon Design
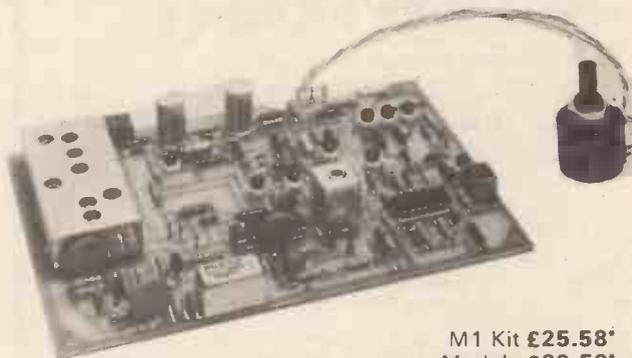
## MAIN RECEIVER MODULE M1


We have claimed before that this F.M. system is the most advanced on the market, and after nearly three years we repeat our claim. Some have borrowed ideas, some have not, but no other tuner gives you all the features of this unit. How many tuners mute the spurious tuning effects found at either side of a correctly tuned station? How many tuners fade the sound out as you tune too far off station for good quality sound? How many tuners kill the tuning indicator so that it does not indicate when there is no station there? How many offer you drift free tuning? We could go on. If you want a tuner that has been well thought out and engineered, start with this module.



M1 Kit £25.58\*  
Module £28.50\*
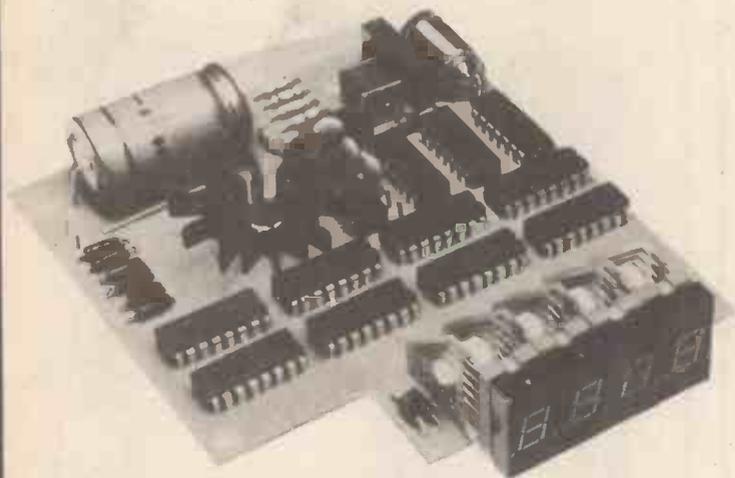
## DIGITAL FREQUENCY METER M6


We are very proud of this one. We don't have to say it's the best, as far as we know it's the only one! On a board less than 4" square is all the electronics of a stable counter with i.f. offset (added) and a stabilized power supply! With the aid of a small daughter board (not shown) which fits neatly into the above module (M1), the exact station frequency is displayed to the nearest 0.1MHz. It's a tuning scale 20" long with accurate calibrations every 0.1"! You get the transformer, daughter board (ready wired in), polarized filter, and a list of station frequencies. What more do you want?



M6  
Module only £44.40\*
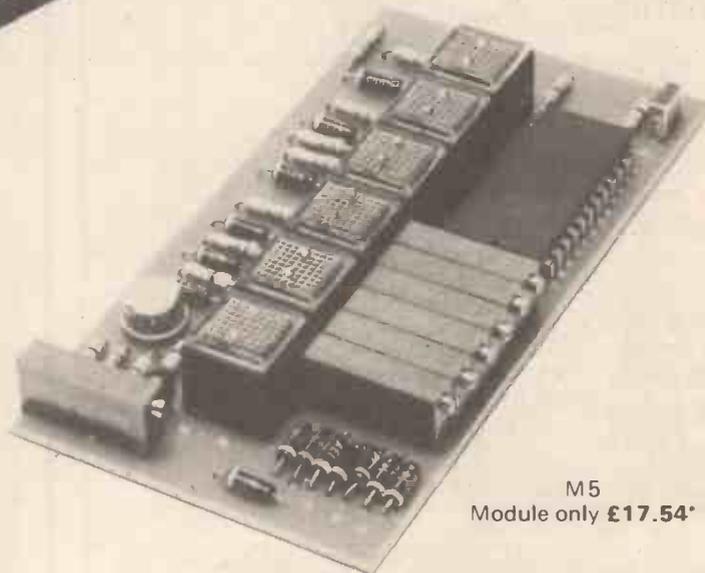
## TOUCH TUNE MODULE M5

This module must put the finishing touches to an outstanding combination. Six pre-set stations at the touch of a button. No moving parts to go wrong, or contacts to get dirty. Internal illumination shows you which button has been touched, while the tuning adjustment is made using high reliability multi-turn cermet pots for repeatable selection of the most used stations, yet retaining the use of separate manual tuning. This module interfaces directly with the M1 above, being wired between the board and the normal manual tuning control. A touch of sheer genius!



M5  
Module only £17.54\*

FULL DETAILS FROM

# Icon Design

33 Restrop View  
Purton, WILTS  
SN5 9DG



\*All prices subject to VAT  
(12.5% at the time of printing)



Fully descriptive booklet (issue 2) with circuits and assembly instructions  
U.K. 50p. Export £1 post free

# PLASTIC FASTENERS FOR ELECTRONICS



**SELF-ADHESIVE CABLE CLIPS** are a quick and simple means of securing cables, cords and small looms to flat surfaces. No drilling or fixing screws necessary. The peel-off backing is removed immediately before placing the clip. The coating adheres to most clean, flat surfaces and withstands a wide range of humidity and temperature. Cable clips are moulded in natural nylon and have rounded edges to prevent damage to the cables.



**CABLE STRAPS** are semi-permanent fasteners for strapping wires and cables into tight, compact looms. The ratchet fastener is adjustable and can be released by pinching-in the sides of the fastener head. Cable straps are made from black nylon.



**WIRE TIES** are a flexible means of fastening wires and small cables into orderly, compact looms. They are quick and easy to fit and can be re-used, greatly reducing re-loomng times. Wire ties are made from nylon and are available in various sizes each determined by a different colour.

The **P.C. BOARD GUIDE** is a self-retaining edge support for printed circuit boards. It has good panel retention and grips p.c. boards firmly and securely. The guide is available in two types of material - yellow acetal or grey Noryl, for high temperature and voltage applications.



**P.C. BOARD SPACERS** are simple to fit, one-piece mouldings for use with p.c. boards. They have a self retaining shank for fastening into panels and a T-shaped anchor for securing p.c. boards of 0.062" thickness. They have good resistance to vibration and are suitable for board-to-board or board-to-chassis use.

**P.C. BOARD STAND-OFFS** are quickly assembled, self-retaining panel supports for p.c. boards. Made from natural (off white) nylon and have good resistance to vibration. Suitable for panels up to 0.079" thickness. Stand-Offs accept a No. 4 self-tapping screw.



**PLASTIC RIVETS** fasten panels, fittings and name plates to metal plastic and wood. Resilient enough to fix into brittle materials like fibreglass, hardboard and glass. Shank, head and pin are one piece. Fixing is by driving the pin through the head into the space between the legs, gripping the work.

**DRIVE FASTENERS** hold two or more panels together. Easily fixed, normally by thumb pressure. No special tools required. Boat-shaped **DRIVE** Fasteners are for panels of thin and medium thickness and are removable. Ribbed **DRIVE** Fasteners are used in blind holes where hole length exceeds length of shank.



**PLASTIC HOLE PLUGS** are quick, inexpensive means of plugging unwanted holes. Hole Plugs keep out dust, dirt and moisture. Attractively shaped heads give a neat finish. The snap action grip of the Hole Plug makes a vibration resistant seal. Hole Plugs are made from nylon and are non-corrosive.

**LOKUT ANCHORS** are used to strengthen holes by providing additional screw thread engagement in materials where self-tapping screws would be unsatisfactory. Made from high strength nylon and used in insulation, and electrical chassis work. Easily fitted by hand.



**1000's OF OTHER TYPES OF PLASTIC AND METAL FASTENERS**  
LEAFLETS ON REQUEST

## HARMSWORTH

HARMSWORTH, TOWNLEY & CO. LTD.  
HAREHILL TODMORDEN LANCS OL14 5JY  
Phone TODMORDEN 2601 (STD 070-681 2601)

8 FOR FURTHER DETAILS

# Belling-Lee

DEF-approved STAN 05-21

**BEAB accepted**  
**SEMKO approved**  
**20 mm x 5 mm fuse links**



- Conforming to IEC 127
- Range of fuseholders meeting European safety requirements.
- Fast acting (F) L 1427B 32 mA to 6.3 A.  
Time lag (T) L 2080A 50 mA to 5 A.

Available from stock and through countrywide network of Belling-Lee distributors.

## Ⓟ Belling-Lee

**better  
by  
design**



Belling and Lee Limited, Electronic Components Group,  
Gt. Cambridge Road, Enfield, Middlesex, England, EN1 3RY.  
Telephone: 01-363 5393 Telex: 263265.

KWPS/BL176

WW-104 FOR FURTHER DETAILS



# When failure spells disaster

## that's the testing time

Advanced electronic technology now forms a major part of systems designed to support man's activities in increasingly demanding and even hostile environments. In such systems, an equipment malfunction may take on a new and more serious significance.


When so much depends on maintaining the performance of such vital equipment, the provision of the right test instrument can be of paramount importance.

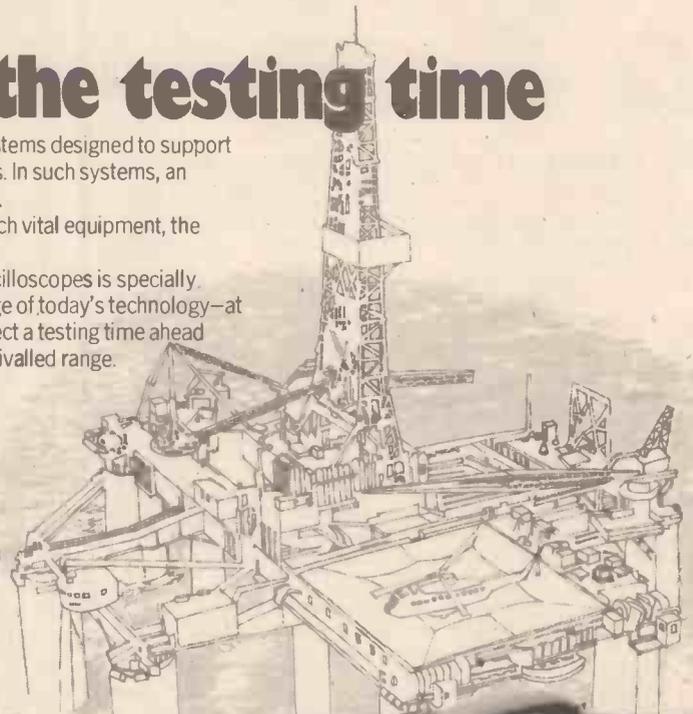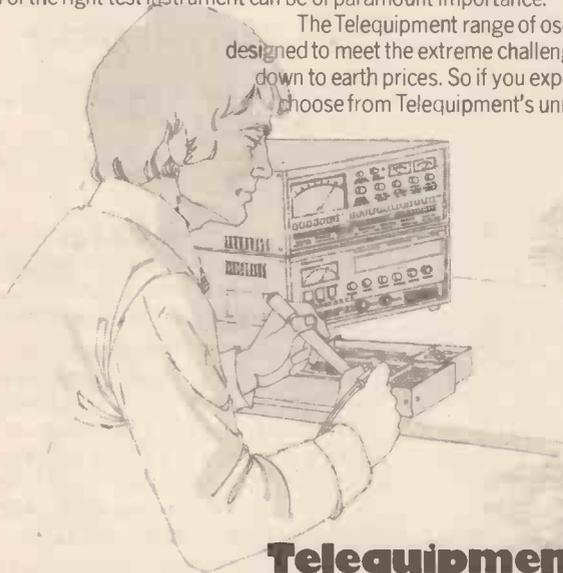The Telequipment range of oscilloscopes is specially designed to meet the extreme challenge of today's technology—at down to earth prices. So if you expect a testing time ahead choose from Telequipment's unrivalled range.


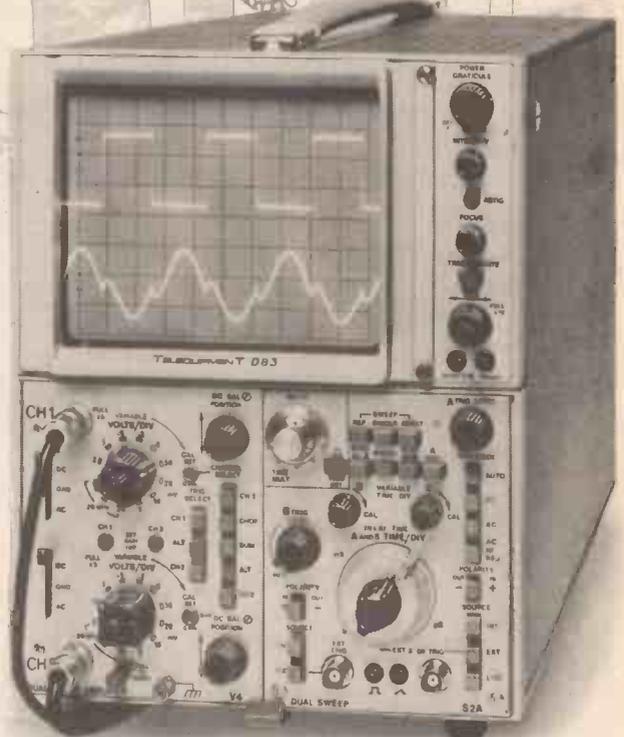
### Telequipment D83


The Telequipment D83 is a dual trace 50MHz oscilloscope offering exceptional performance at modest cost. A large size CRT operated at 15kV provides a bright sharp display and a wide range of plug-in amplifiers offers a choice between 5mV/div sensitivity at maximum bandwidth and 50 $\mu$ V/div differential sensitivity with high common-mode rejection. A dual time base option provides comprehensive sweep intensifying, sweep delaying and single shot facilities while a simple single time base plug-in offers additional X-Y capabilities. Measurements on 625 line TV waveforms are made simple with a special TV amplifier plug-in.



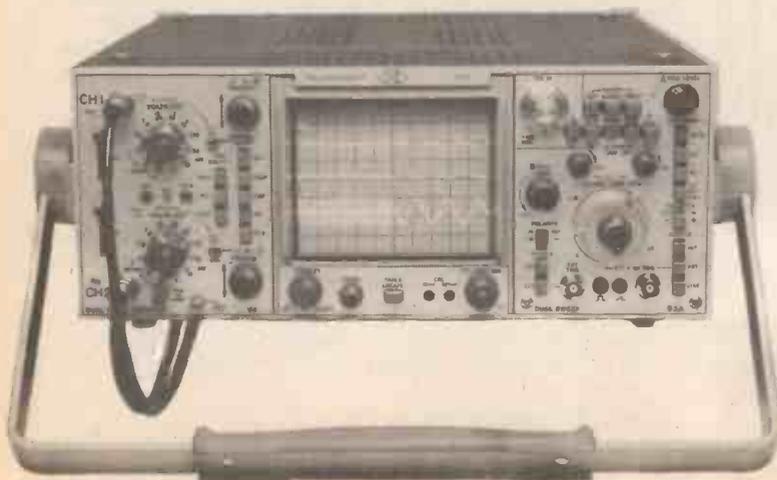**TELEQUIPMENT**



Tektronix U.K. Limited  
P.O. Box 69, Beaverton House, Harpenden, Herts.  
Tel: Harpenden 63141 Telex: 25559.



### Telequipment D75

This is a lightweight portable version of the dual trace 50MHz D83 model. It brings the same laboratory standards of measurement and performance in a rugged monolithic form ideal for mains-driven field use. The 8 x 10cm CRT operated at 15kV provides a bright sharp display under all normal conditions, while a choice of factory fitted options from the well proven D83 series plug-ins make it suitable for a wide variety of measurement applications. When fitted with the S2A dual time base, for instance, the D75 offers comprehensive features such as mixed sweep, sweep intensifying and delaying modes. As with the D83 measuring accuracy is  $\pm 3\%$ .

# wireless world

**Editor:**  
TOM IVALL, M.I.E.R.E.

**Deputy Editor:**  
PHILIP DARRINGTON  
Phone 01-261 8435

**Technical Editor:**  
GEOFFREY SHORTER, B.Sc.  
Phone 01-261 8443

**Assistant Editors:**  
MIKE SAGIN  
Phone 01-261 8429  
RAY ASHMORE, B.Sc., G8KYY  
Phone 01-261 8043  
JOHN DWYER  
Phone 01-261 8620

**Production:**  
D. R. BRAY

**Advertisement Controller:**  
G. BENTON ROWELL

**Advertisements:**  
PHILIP NOSSEL (Manager)  
Phone 01-261 8622

LEO KEMBERY  
Phone 01-261 8515

CHRIS PRIER  
Phone 01-261 8037

**Classified Manager**  
BRIAN DURRANT  
Phone 01-261 8508 or 01-261 8423

EDDIE FARRELL (Classified Advertisements)  
Phone 01-261 8508

JOHN GIBBON (Make-up and copy)  
Phone 01-261 8353

**Publishing Director:**  
GORDON HENDERSON

## Surround sound — time to consolidate

It may seem strange that when surround-sound equipment sales are at a low level, the systems confrontation is still unsettled, and people apparently are disillusioned by the whole thing, interest in surround sound seems as high as ever among broadcasters, particularly in Europe. This apparent paradox is the consequence of having forced quadraphonics on the public, discovering what went wrong (*Wireless World*, December 1974) and trying to put it right second time round. *Wireless World* is in the midst of publishing details of what may be the most significant contributions to the art, reflecting an escape from the blind alley into which quadraphonics, as conceived at the turn of the decade, appears to have led.

One of the effects of these early attempts at coding two channels for surround use was to send people away thinking of other ways of doing it. One such avenue, followed independently by Duane Cooper and Peter Fellgett, in 1971, led to the omni-phaser idea. This phase-encoding of direction could, by simple sum and difference matrixing, produce a reasonably compatible stereo pair of signals. The snag was a 90° phase difference between the pair.

A derivative of this was therefore studied by the BBC Research Department in 1973. Dubbed Matrix H, it was last in a list of eight arrangements tested. The front part of its pan-locus was bent toward the in-phase mono point on the energy sphere, which gave a front centre sound a reduced phase difference of 48° and appeared to give commendable overall compatibility.

Then in 1975 an effort was made to achieve a compromise, between the limit of RM on the one hand and BMX on the other, that would suit both broadcasters and the record industry. But the move failed (see *News* page 65) and messrs Fellgett and Gerzon were left to put forward their idea for a provisional

industry standard in *Electronics Letters* later that year.

Now that patents have been granted, fuller details of this NRDC-sponsored work are available. They show that a range of options exists for pairwise mixed material to enable a variety of needs to be met; indeed the H matrix could almost be one of the options.

For a surround encoding to be universally adopted, allowance must be made for the addition of a third channel where feasible (a fourth would allow three-dimensional sound reproduction but that seems very much in the future), the resulting system not then needing "rescue" by non-linear circuitry.

The record industry seems well able to produce band-limited carrier-channel discs, but the transmission of quadrature sidebands along with the in-phase difference-signal sidebands can have undesirable effects in some stereo receivers. To prevent this one could transmit the quadrature information at a level chosen to reduce these effects to agreed proportions, hopefully negligible. And to avoid signal-to-noise ratio problems it follows that the bandwidth of this third channel would need to be restricted. Design procedures are now available that allow computation of third signal coefficients so that reduction of its level does not upset localization.

What we now have is the opportunity to standardize on a rational, unified surround sound technology, which will meet the needs of broadcasters and the record industry, now and for the foreseeable future, with an assurance that the system is not likely to be bettered. As these two British proposals — BBC H and NRDC J — have much in common, it would be most unfortunate if this opportunity were to be wasted. We urge the two parties to get together: there is so much to be lost by fighting and so much to be gained by pulling together.

# Radio in the '80s

## Broadcasting and the ideal sound receiver of the future

by Duncan MacEwan, *Chief Engineer, Radio Broadcasting, BBC*

A number of policy changes and trends in broadcasting over the last two decades have a very definite bearing on reception difficulties and the adequacy or otherwise of present day receivers:

- There has been a move away from mixed programming on networks towards channels and stations which can be clearly identified with one particular kind of output, e.g. news, orchestral music, light middle-of-the-road music, rock, country and western, "pop", etc. This "generic broadcasting" concept applies to a greater or lesser extent in many countries of the world today. The BBC itself has for its own national networks such a format (as indicated in Fig. 1).

- Within these basic frameworks, however, most countries run networks which also offer strands or segments of specialised programming, e.g. education, ethnic languages, sport, motoring information, immigrants' programmes, etc. Fig. 2 shows something of BBC Radio's special programme services within its four networks, which it can be seen offer seven different programme outlets. Such widening of choice to the listener must be matched by his ability to take advantage of this by means of a receiver with adequate facilities.

- Programme scheduling on networks has become much more closely geared to the realities of life in the '70s. For example, television competition, not only from outside but also from within the same organisation, is recognised by radio programme planners. Peak listening times — breakfast, middle of the day and early evening — are established and programme patterns developed against such a background. In the process, some of radio's inherent advantages — speed, range of outlets, fulfilling needs which television cannot — can be capitalised on. As a second example, different programming is scheduled during clearly identifiable leisure times, which are the weekends and weekday evenings for most. Furthermore, listening habits have changed dramatically. The television set now occupies the place in the room previously held by the mains radio of the '40s and early '50s, and by far the largest amount of listening is

now done on portables, but with a growing element in cars.

- The introduction of more radio services, many of which have found their outlets on f.m. However, in some parts of the world, for a variety of reasons, countries have grown to rely heavily not just on a.m. in the medium wave-

band but also on long waves. This gives rise to the need for a three-waveband set, even before any short-wave requirement is taken into account for those who either actually need such a facility in order to receive their own national services, or simply wish it in order to extend the range of choice by being able

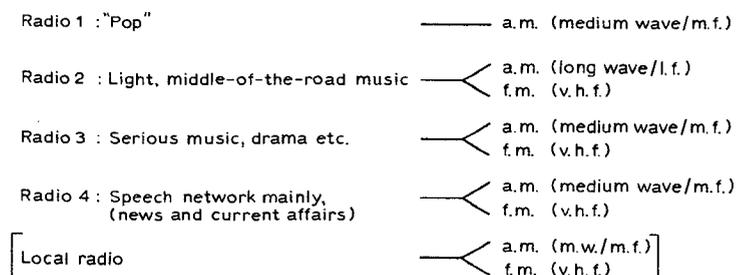


Fig. 1. The basic "generic network" concept used by BBC Radio. Note that there is a total of nine outlets.

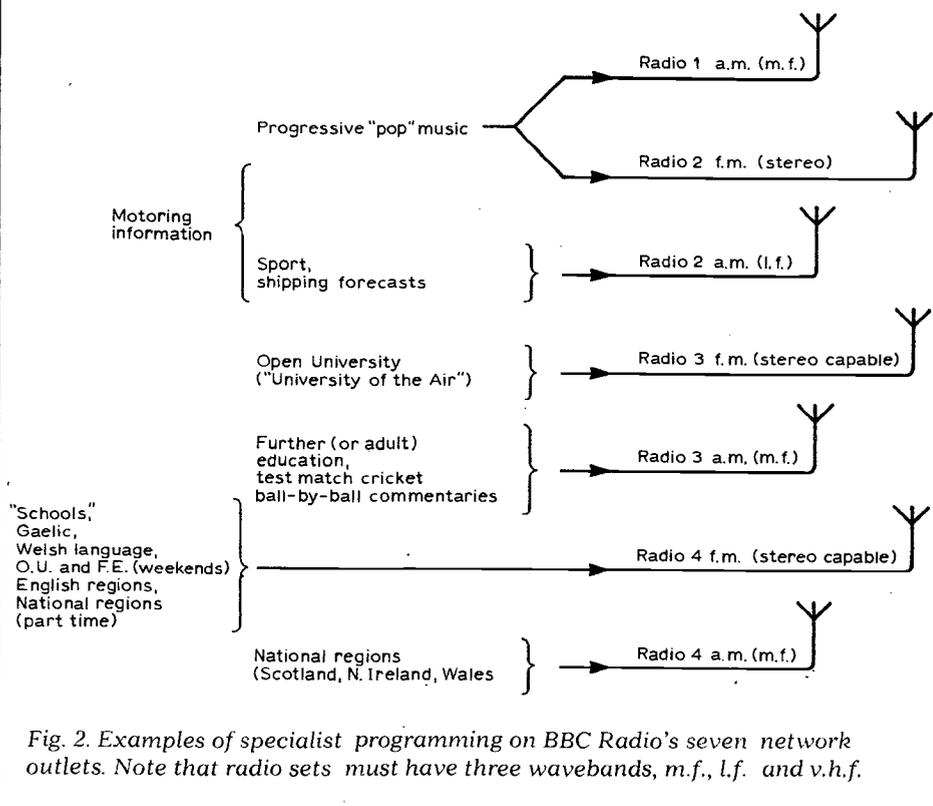


Fig. 2. Examples of specialist programming on BBC Radio's seven network outlets. Note that radio sets must have three wavebands, m.f., l.f. and v.h.f.

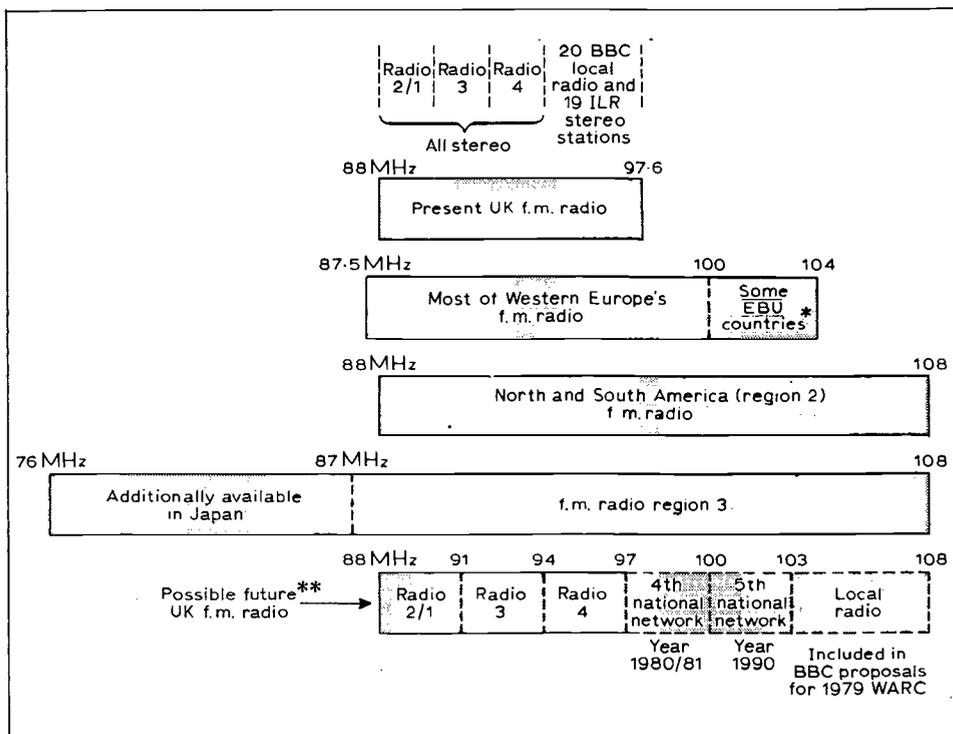


Fig. 3. Band II (v.h.f.) allocation for broadcasting. Notes: \* applies to Austria, Belgium, Denmark, Israel, Italy, Netherlands, Spain, Switzerland, W. Germany and Yugoslavia. \*\* All frequency spacings suitable for stereo transmissions.

to listen to broadcasts from distant countries. Whereas in a modern television set channel selection is normally effected by simple switches or buttons, the counterpart of these in the radio set is usually required to band change, leaving station selections to be subsequently achieved by a second process, manual tuning; this in itself is not always found easy, nor can stations invariably be located and identified positively. The problem for the listener in the UK may be highlighted by brief reference to the situation now obtaining in certain cities. In both London and Birmingham, for example, a total of 13 radio broadcasting outlets is available, viz. the BBC's nine plus the a.m./f.m. pairs of two independent commercial local radio stations.

Many broadcasting organisations' programme journals usually have to give pride of place to television programmes and indeed are encouraged to do so in light of the lucrative advertisements they attract. This often results in too little space being left for a proper, easily readable display of radio's multifarious choices. The would-be listeners find difficulty in spotting programmes of their taste and perhaps miss many they might otherwise have enjoyed.

**Technical factors**

The demand for the increased number and range of services has given rise to severe congestion in the a.m. medium and long wave bands. The Geneva fre-

quency conference of 1974-75 authorised transmission for some 10,000 stations in Regions 1 and 3, within spectrum space which allows for a total of only 135 channels (120 medium wave and 15 long wave). This represents an increase of 2½ times the present number of assignments with a total carrier power of 540 megawatts — a greater than four-fold increase. Services after dark will inevitably suffer badly and greater reliance must therefore be placed on f.m. in the future. Broadcasting organisations may well find themselves having to work out a strategy for weaning listeners off a.m. where such outlets are merely carrying in duplication the same programmes. "On air" and written publicity would be key factors in any campaign of this kind.

Because of the different propagation characteristics prevailing during the hours of darkness, which give rise to the all too familiar night-time interference, population coverage figures are lower at these times. For example, in the BBC's own case:

|         | Daylight | Night-time |
|---------|----------|------------|
| Radio 1 | 87%      | 37%        |
| Radio 2 | 98%      | 83%        |
| Radio 3 | 94%      | 72%        |
| Radio 4 | 98%      | 74%        |

In the face of these night-time figures alone, a case can be made for duplication on f.m.

Many of the world's a.m. services were planned on the basis of much lower signal strengths than are now found necessary in city centres, with their high rise, steel framed buildings. In an earlier era the BBC considered 3 to 5 millivolts per metre to be adequate, whereas now it recognises the need for about 10 millivolts. In certain other countries signal levels as high as 25 millivolts are considered essential. This

is also a function of which end of the a.m. medium wave band the station lies. At the high frequency end, due allowance has to be made for the increased attenuation which is experienced as the signal traverses a city.

While the position in respect of f.m. (Band II v.h.f.) is a good deal easier, the packing density of stations is getting dangerously high in some countries. Stereo channels, which are on the increase, call for more spectrum space than monophonic services. In Band II, frequency allocation is fast becoming very difficult and pressure is being put on other users — taxi, fire authorities, police and ambulance services — to move out of it. In the UK the degree of privation (Fig. 3) is such as to have inhibited the development of further national networks, while extension in the number of local services is in jeopardy. The same is true in certain other countries including those which are restricted by their geographical proximity to the densely populated areas of their neighbours. It is hardly surprising, therefore, that most European countries seek an enlargement of that part of Band II allocated to them as broadcasters. The Americas and the countries in the Far East are in a privileged position with at least 20MHz of band space within which frequencies may be allocated, whereas in the UK it is only 9.6MHz at present.

Many f.m. services were planned in the early '50s in an era when practically all receivers were mains operated and used in fixed positions. Coverage areas were predicted on the basis of roof top (or loft) aerials at a height of 10 metres. The advent of the battery operated transistor set changed all this, and small portables with a built-in aerial and often with only one a.m. band became the norm; many are still in use. Those sets capable of receiving the f.m. services were provided additionally with an extendable rod aerial and used at a height rarely exceeding one metre above ground level. For satisfactory reception at this level, the signal strength required at roof level would have to be four times the strength normally needed for a roof-top aerial. To give point to this, the BBC has quoted for some years, and quite correctly so, its f.m. monophonic service national coverage figure as 99.3% of the population for all three v.h.f. networks, the figure applicable to the roof-top aerial situation. More recently it has estimated, however, that reception on transistor portables of all types is nominally unsatisfactory possibly for as much as 10% of the population. Even with a roof-top aerial good stereo reception calls typically for about twice the signal strength adequate for the same standard of mono, but in difficult reception conditions much more may be needed. Put another way, this means that stereo service areas are always smaller than the monophonic ones.

A recent BBC Engineering/Audience

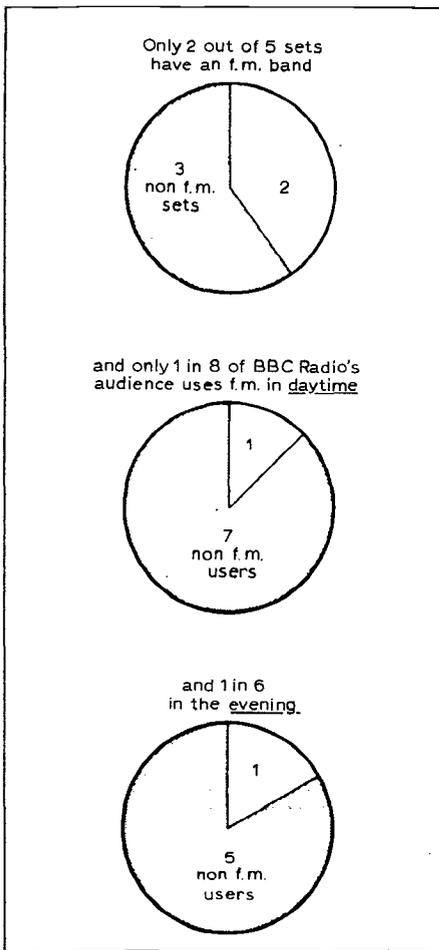


Fig. 4. Radio set statistics in the UK.

Research survey in some depth has demonstrated the continuing importance to BBC radio of its a.m. services. Over 86% of all listening is done on the medium and long wavebands and 58% on portable receivers. This latter figure indicates very clearly that there are almost equal markets for both the good quality fixed-position mains receiver and the portable. Listening in cars (6.5%) was established as of growing importance.

The survey has also shown that even now, 20 years after the BBC's first v.h.f./f.m. transmitter went on the air, only 40% of the sets in the hands of the British public have facilities for receiving such transmissions. F.m. receivers, in spite of affording vastly improved quality, remain in many cases more difficult to tune, and the portables are equipped with awkward rod aerials, consume more battery power and have to be carefully placed within the room for optimum results. Since they also invariably cost more, customer and listener resistance is generated. Furthermore many v.h.f. portables have too small loudspeakers to take much advantage of the higher quality offered by the transmitted signals. Under these circumstances it is more difficult to convince the public that the f.m. service is so very much better than the a.m. one. In addition, good f.m. car radios tend to be very costly, and suppression of ignition, wiper and other local electrical interferences proves difficult. Since this

varies from model to model and is often a function of the car manufacturing process, no one solution can be universally applied, which means that installation costs tend to be high. Too few good economically priced f.m./a.m. car radios are available; even fewer have built-in suppression and cover all three wavebands.

In other parts of the world the position may well be different.


Most broadcasting organisations, when establishing their f.m. services some time ago, did so with a horizontal plane of polarisation. How well does this serve the listener to a portable set with its vertical rod aerial in and out of doors, and those in cars? A recent EBU Working Party K study showed under what circumstances horizontal, vertical or mixed polarisation gave optimum results. For this particular type of potential audience it concluded that in other than rugged terrain served by an existing horizontally polarised transmitter it would be advantageous to change to or establish from the outset either mixed or vertical polarisation. (Many transmitting stations in the USA have been modified in this way during the last decade.) The cost of such a programme of work for a national broadcasting organisation is, however, prodigious. Of the BBC's own 20 local radio stations built during the 1970-72 period, seven are slant polarised as a result of the same kind of considerations, coupled with the need to keep faith with those f.m. listeners who had equipped themselves in earlier years with horizontal roof-top aerials for the three national network services and for

whom a move to vertical polarisation would have meant too severe a drop in signal strength.

In the duplicated service situation, considerable problems can arise in those parts of a country where the a.m. and f.m. transmitter coverages differ, leaving a proportion of the listeners solely dependent on one or other outlet. In the UK this difficulty is prevalent in mountainous regions of Wales and in parts of the north and north west of Scotland. For two principal reasons — finance and frequency allocation — such situations can present nearly insoluble problems, and are most acute for a public service broadcasting organisation which has as its objective 100% national coverage.

The language of both the broadcasting engineer and set manufacturer often act against the public's interest and certainly its understanding of wavebands and frequencies — there is much talk of a.m. and f.m., medium wave, long wave and v.h.f., m.f. and l.f., of metres, kilohertz and megahertz. On the European continent many countries adopt the simple expedient of quoting channel numbers only, where the f.m. band is concerned, while some manufacturers continue to put station names on their

Fig. 5. Features of the ideal set of the future. In addition to those listed it should have an internal aerial, built-in recorder, rechargeable batteries and an integral charger, interference protection, and a sealed rigid and waterproof cabinet with improved acoustics.

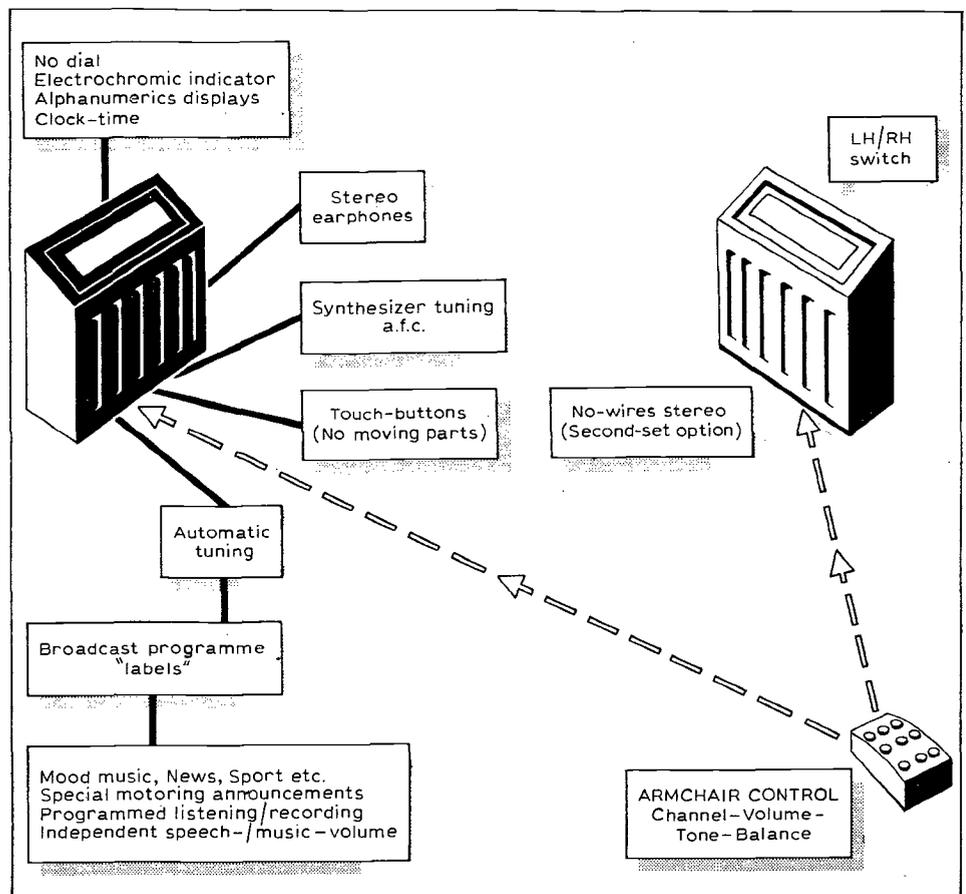

set dials — a restriction for the broadcaster in the face of any impending reallocation of frequencies and a potential source of frustration to the listener.

### Requirements for sets

The conclusions which might be drawn from all this are that if in the future the broadcaster is not to be restricted and the listener suffer deprivation:

- every set sold in the country must be capable of receiving at least all the indigenous services available in that country. This must be made to apply to both home produced and imported sets, and legislation will be required to ensure the inclusion of all the necessary wavebands
- f.m. portables must be made easier to tune and be rid of the rod aerial
- an adequate number of pre-set push buttons should be provided for making network or station selection and switching as simple as it already is on television sets
- channel identification must be simplified
- programme journals need designing with the problems outlined earlier very much in mind
- the frequency with which stations are identified "on the air" needs to be increased in subtle ways
- signal strengths will in some cases have to be increased to take greater account of the indoor listener using his portable in one room or another, and often within a steel framed building
- changes need to be made in the plane of polarisation of many f.m. transmitters
- f.m. portables could with advantage be made more sensitive to help the "fringe area" listener.

The immediate problem is one of ensuring that the right programmes can be easily found and listened to around the home in a variety of domestic situations, in the car or out of doors. Potential audiences will be lost and programmes missed unless these can be easily and positively located. The complex programming of a multiplicity of transmission outlets can only be really successful if programme people as well as engineers understand the technical parameters of the problem and jointly engage with the receiver industry in seeking a solution.

### The ideal set of the future?

Looking forward into the 1980s, the ideal radio set might well have the following features:

No dial but either an alphanumeric

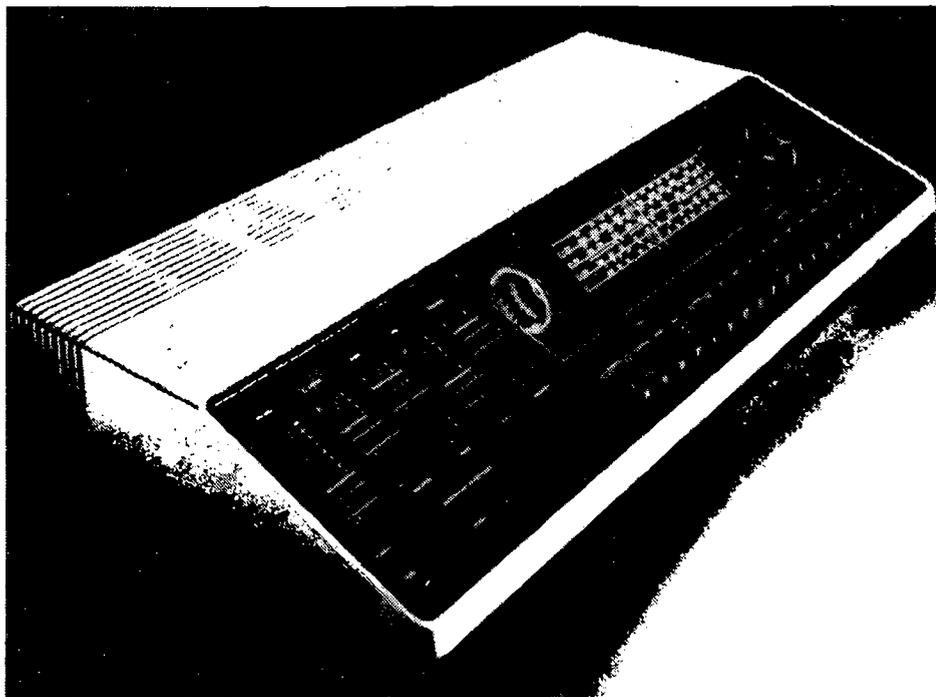


Fig. 6. Receiver with "electronic search tuning" operating on the f.m. band (Philips type RH752).

display or an electrochromic indicator. The frequency or channel identification could simply appear as a number in a "window". Some of the more sophisticated tuner-amplifier combinations at the expensive end of the market already use an alphanumeric display of which Toshiba, Revox and Telefunken are examples. Electrochromic cells which might well prove suitable for this purpose have been developed by ICI.

**No manual tuning control** as such, the set using pre-tuned button selection, or this combined with "memorised selection". A new Swiss Revox tuner has a programmable memory — 16 pre-sets with a storage time of 6 months before any re-establishing of the choices originally made becomes necessary. Philips are marketing a receiver with "electronic search tuning" — by pressing a button the tuner will search up or down the band, stopping for 2 seconds on any f.m. signal of sufficient strength before moving on to the next one. When the listener is satisfied with what he hears he simply releases the button. This particular tuner also includes a "fast run-on" or "back" facility (Fig. 6). Blaupunkt have had a car radio on the market for some years with "search" mode.

**Plug-in pre-set frequency cards** for the channels applicable to the area in which the set is to be used; these could be issued with the local area's edition of the programme journal and would ensure that the receiver was tuned to the correct station. (A decision at the Geneva l.f./m.f. conference that the a.m. m.f. broadcast carrier frequencies be multiples of 9kHz greatly assists concepts like those above.)

**Electronic programme "labelling"** by the broadcaster, using unobtrusive data

signals travelling with the broadcast signal signifying, for example, a particular channel or type of programme. Various technical possibilities suggest themselves using a sub-carrier in or out of band. Frequency modulation of the a.m. carrier is another avenue of approach. Many applications for such labels are possible:

- Programmes could be selected by type or channel and a receiver designed to "search" the frequency band for a programme carrying a particular label; generic broadcasting makes such a concept more meaningful for the listener. Since searching may take time, it is possible to envisage a second, auxiliary receiver contained within the same box that would search and log behind the scenes, as it were, so that programmes or stations would be available for the listener without delay.
- A receiver could be pre-programmed for an evening's listening, making use of broadcast data labels to switch "on" and "off", channel select, etc, according to a pre-set plan.
- Coupled with a built-in recorder and using similar methods to that above, selected programmes (e.g. news bulletins, weather forecasts, educational programmes, etc) could be stored for later recall by the set owner.
- Such a receiver could incorporate a digital clock either driven from an internal quartz oscillator or "running free" but corrected at regular intervals by clock-time data signals transmitted by the broadcaster, thus absolving the listener from the need to take any action himself.
- Remote control by the broadcaster of

Fig. 7. Set which automatically watches for "programme-labelled" news broadcasts from Radio Luxembourg and becomes audible when one is being transmitted (ITT "Oceanic").

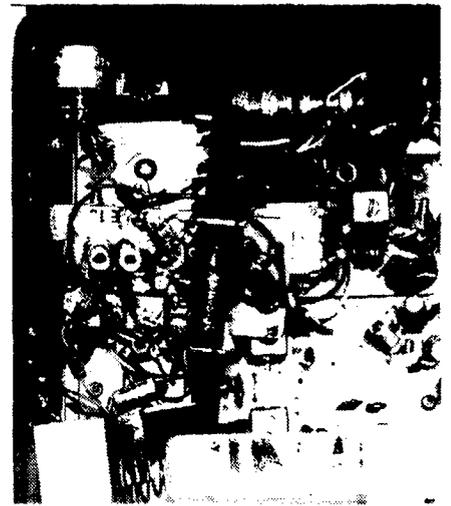
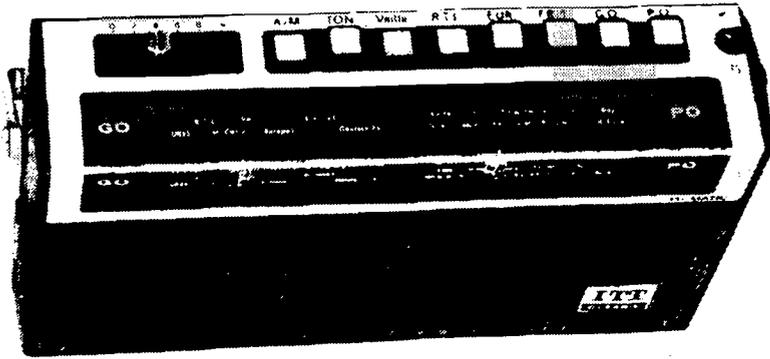


Fig. 8. Ferrite rod aerial for v.h.f./f.m. reception (the vertical one) in a portable set modified by the BBC Research Department.

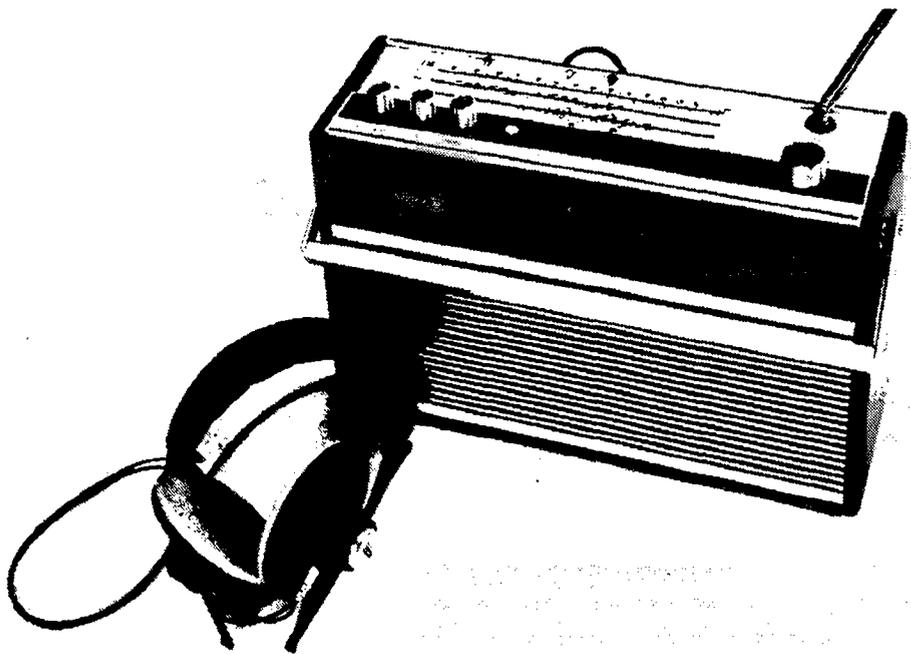


Fig. 9. Portable with stereo decoder for earphone listening (Hacker "Silver Knight").

the volume required for satisfactory speech and music levels by 'data-labelling', which would solve an age-old listeners' complaint.

Radio Luxembourg uses a simple form of programme-labelling by adding coded signals just before and after its news broadcasts. A frequency within the audio band (2325Hz) carries frequency modulation in the shape of a square wave; a deviation of 175Hz is used to open the receiver and 75Hz to close it. ITT market the "Oceanic" receiver (Fig. 7) with a fixed tuning button for RTL associated with which is another marked "VEILLE"; with both pressed the receiver "watches" for news broadcasts only, and bursts into audio life when one is being transmitted. The Dutch are also beginning to experiment with coded programme-labelling using a sub-carrier well out of the audio and stereo bands.

The American SCA (Subsidiary Communications Authorisation) or "store-casting" facility as it is commonly

called. This could be used for an additional low quality monophonic service of narrow bandwidth when the main transmission was also monophonic.

An f.m. as well as a.m. ferrite aerial contained within the body of the set. The BBC's Research Department has modified a portable in this way and has also produced two different versions for cars, all with encouraging results (Fig. 8).

**Armchair control** of channel, volume, tone and stereo balance using remote acoustic, infra-red, etc. control.

**Improved f.m. interference protection** drawing upon new techniques evolved for digital processes. At least one well-known European manufacturer of car radios has incorporated such a circuit with advantageous results.

**Frequency compensation** for listening level, since both the low and high audio frequencies require to be boosted for low volume control settings.

**Stereo decoder in portables** for earphones listening. BBC Designs Department produced such a thing about five years ago for our own use, since when Hacker have taken this idea up commercially with their "Silver Knight"

model (Fig. 9), as have ITT and others. (A new Hacker model takes the proposition a stage further with a loudspeaker facing out from either end.)

"No-wires" stereo becomes possible if two f.m. portables are equipped with these small, relatively inexpensive decoders, provided each is also fitted with a left-channel/right channel switch; paired up they could be arranged to provide good stereo listening on their loudspeakers.

A cabinet which is rigid, sealed, waterproof, rugged and with improved acoustics.

**Rechargeable batteries** with inbuilt-charger.

The technology clearly already exists to bring all of these facilities into being. Which do the world's broadcasters consider the most important for (a) fixed set listening; (b) portables, and (c) car radios, and what are likely to be the price restrictions on the degree of sophistication? For its part, the BBC has had discussions with the British Radio Equipment Manufacturers Association (BREMA) as part of its continuing dialogue with that body, and has been encouraged by its response. BREMA has agreed to co-operate in any experiment the BBC decides to mount.

In conclusion, the author believes that since technology is no longer holding back either the broadcaster or the manufacturer, major developments in receiver design are possible; the receivers of the future are, however, only going to match our needs if the broadcaster specifies these clearly and works closely with the set-making industry.

#### Acknowledgements

The author wishes to record his thanks to S. M. Edwardson of the BBC's Engineering Research Department for his help and advice in preparing this article, and to Howard Newby, Managing Director, BBC Radio, and James Redmond, Director of Engineering, for their permission to publish it.

# BBC Matrix H

## Compatible system for broadcasting

by P. A. Ratliff, B.Sc., Ph.D and D. J. Meares, B.Sc.(Hons) *BBC Research Department*

During the past few years the BBC has been involved in assessing the performance of "surround sound" systems to determine whether the provision of a surround sound broadcast service would be viable. Most system proposals may loosely be called "quadraphonic" and they use four loudspeakers for reproduction, arranged as a fore and aft stereo set-up. To carry four loudspeaker signals to the listener, multiplexing techniques have been devised for discs in which four nominally independent signals are recorded, and a decoder, not unlike two stereo broadcast decoders in concept, is required to extract them. In circumstances where only two channels are available (as for conventional stereo discs, cassettes/tapes, and broadcasting), many proposals for channel-reduction matrices have been made whereby four loudspeaker signals are derived in the listener's decoder from two signals as recorded or broadcast.

The broadcasting of four independent signals would require either two complete stereo networks for each quadraphonic programme (as for example the BBC experimental broadcasts on 6th July and 23rd December, 1974, which used Radio 3 and 4 v.h.f. transmitters) or alternatively the inclusion of the additional signals by quadrature modulation of the 38kHz subcarrier and/or the addition of a further subcarrier. There are not enough Band II v.h.f. broadcast channels to permit the first-mentioned possibility on a permanent basis, and although the last has been discussed at some length<sup>1</sup>, including the transmission of only three signals<sup>2</sup>, there are serious problems in practice<sup>2,3</sup>.

To overcome some of these problems three-channel systems have been proposed which transmit the third signal with a reduced bandwidth and/or modulation level. These could substantially reduce the problem of incompatibility with existing stereo receivers, but at the same time would reduce the service area.

Most attention has therefore been

paid to two-channel matrix systems for possible broadcast use, as these would not, in principle, require any changes in distribution, transmission, or receiving apparatus. It would also be possible to record them with conventional stereo equipment. However, some loss of information is inevitable in mixing surround-sound signals into only two independent channels, and re-creation of the surround sound-stage, by means of a suitable decoder to provide four loudspeaker signals, has enjoyed a varying degree of success. The lack of loudspeaker signal separation inherent with any linear decoding matrix<sup>4</sup> has led to considerable effort being devoted to the design of variable matrices, whose decoding parameters are dependent upon the programme content. Such systems can only work ideally for one source direction at a time, and thus compromises must be made to enable a complex sound distribution to be accommodated.

Of paramount importance, the two encoded matrix signals must be capable of sensible reproduction, both directly in stereo and when summed in mono. This compatibility requirement, which is desirable in the disc, cassette, and tape market to eliminate the need for double inventories (i.e. the same programme material being released in both stereo and "quad" editions), becomes essential in broadcasting because all but a small proportion of the public will use existing stereo and mono receivers for the same broadcasts. Indeed, there must be no penalty paid by the existing stereo and mono audiences, who are likely to be in the majority for many years to come, if not permanently, in order to satisfy a minority quadraphonic audience. This requirement is perhaps the most important of a matrix system for broadcasting, and is the one which the commercial systems have failed to satisfy completely so far.

### Psychoacoustics

Initial studies at BBC Research Department concentrated on investigating the subjective properties of the human hearing mechanism, to find out the extent to which quadraphonic signals are capable of producing a subjective enhancement of the sound sensation for

the listener. Ideally, by surrounding the listener with sound information, a system should create a greater sense of realism and involvement in the programme. It is important to realise, however, that the programme must satisfy the listener subjectively, and merely the re-creation of the actual sound field at a suitable position in the recording environment may not be sufficient. This feature is, of course, well known in stereo reproduction, but applies equally for surround sound, because the lack of other perceptions of the recording environment (e.g. visual) often requires that the aural presentation be artificially exaggerated.

From a large number of subjective experiments, it was found that at normal listening levels the listener is almost equally sensitive to the loudness of a sound at any azimuth around him, and although his assessment of the location of a sound exhibits a left/right expansion in the rear of the sound-stage, he can co-locate two separate sounds to an accuracy of better than  $\pm 3^\circ$  for all stage azimuths. This last-mentioned factor is clearly the more important for surround sound reproduction, as the listener will not be so concerned about the true positions of the various sound sources in a programme, but will be likely to be more critical of their relative positions.

Studies were then made of quadraphonic presentation of sounds; in particular, the effects of combinations of signals with various amplitude and phase relationships typical of those produced by proposed matrix systems. Using conventional stereophonic sound-panning techniques\* for positioning a sound-image, a discrete system (i.e. four independent audio signals) is capable of giving good sound-image localization in the front and rear of the sound stage, but is sensitive to the listener's head position for the sides unless the listener turns to face the sound, particularly in non-reverberant surroundings. Fortunately, the acoustics of typical home living

\* The minimum number of channels which intuitively can provide independent directional information in one plane, i.e. a horizontal sound-stage.

\* A sound-image is moved between the two stereo loudspeakers by electrically altering the ratio of the sound signal fed to each loudspeaker, keeping the total power constant. This technique is also known as pairwise panpot mixing.

rooms serve to mitigate the last mentioned effect. When groups of directional microphones or channel reduction matrices are employed, more complex output signal configurations occur which can give rise to most unnatural sound effects, changing the location, definition and quality of the sound. On the other hand, with suitable control of these parameters, it is possible to enhance the sound image considerably.

Furthermore, it was necessary to examine the compatibility requirements of a sound system for stereo and mono reproduction. All the two-channel matrix proposals use phase difference between the left and right stereo signals, in addition to their amplitude ratio, to convey left/right and front/back directional information. For normal stereo the phase difference between the two signals is maintained at a nominal zero degrees, and it is well known that completely antiphase signals give rise to quite unpleasant, even nauseating, effects when the amplitude difference between the signals is small. Nevertheless, a much more detailed knowledge was required with the advent of matrix systems, and a comprehensive investigation into the effects of phase on stereo image formation was undertaken. As a result, the compatibility of any two-channel system can be predicted from a knowledge of its encoding parameters.

A useful pictorial representation of the stereo signal is given by Scheiber's sphere<sup>5</sup>, which maps the amplitude ratio ( $L/R$ ) and the phase differences  $\beta$  of the two-channel signals onto the surface of a sphere. This is facilitated by expressing the amplitude ratio as an angle, by the relationship  $\alpha = 2 \tan^{-1} |L/R|$ . Thus  $\alpha = 0^\circ$  when the signal is totally in the right channel,  $90^\circ$  when it is split equally between the left and right channels, and  $180^\circ$  when the signal is totally in the left channel. The right-hand half of the sphere is represented in Fig. 1, where the phase difference  $\beta$  is plotted as the angle around the circle, and the amplitude ratio  $\alpha$  is plotted as the radius of the circle, so that  $\alpha = 0^\circ$  (signal all in the right channel) is at the centre of the circle, and  $\alpha = 90^\circ$  (signal equal in the left and right channels) is on the circumference. The left-hand half of the sphere can be regarded as mirrored the other side of the paper with  $\alpha = 180^\circ$  (signal all in the left channel) at the centre of the circle on that side. Usually left/right symmetry pertains in stereophonic transmission systems and it is sufficient to examine only the one half of the sphere.

From the work on the effects of phase it was possible to divide the sphere into areas of impairment of stereo image quality, and in Fig. 1 three nominal regions are defined, namely negligible, slight, and severe impairment zones, as shown by the appropriately shaded areas. Impairment zones can be defined

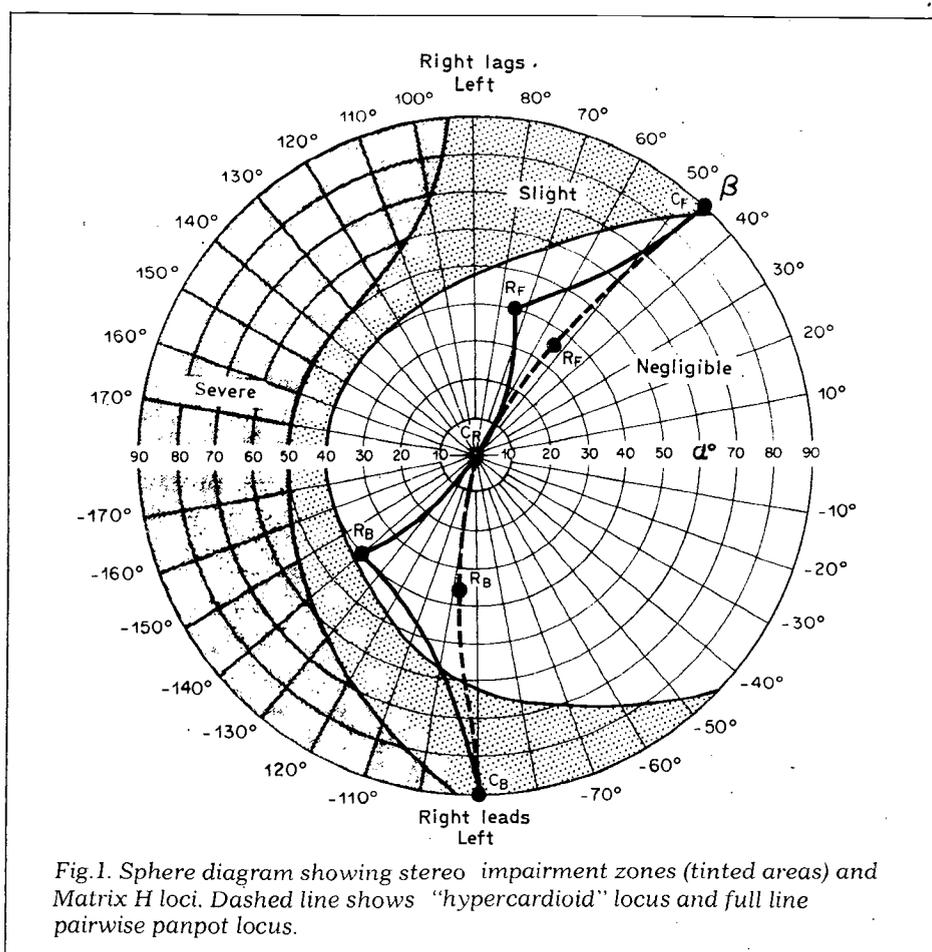


Fig. 1. Sphere diagram showing stereo impairment zones (tinted areas) and Matrix H loci. Dashed line shows "hypercardioid" locus and full line pairwise panpot locus.

for mono reproduction, but these are less severe, resulting only in a reduction of level for large values of the two-channel phase difference  $\beta$  thus affecting the balance in mono of sounds from different encoding azimuths.

The compatibility problems found with earlier matrix system proposals could now clearly be seen when the system loci were plotted on the sphere; they all transgressed into the slight and/or severe impairment zones to too great an extent. What was required was a system whose encoding locus lay principally within the negligible impairment zone, having a sensible image distribution in stereo reduction, and yet retaining the capability to be decoded in surround sound with both left/right and front/back sound-stage discrimination.

### Matrix H encoding

The requirement was met with the development of Matrix H<sup>6,7</sup> at the Research Department. The two-channel encoding matrix may be defined in terms of the position of the sound source in the surround sound stage to give left and right channel coded signals of<sup>8</sup>

$$\begin{bmatrix} L \\ R \end{bmatrix} = \begin{bmatrix} 0.63 \angle -7.5^\circ & 0.43 \angle +73^\circ & 0.63 \angle -7.5^\circ \\ 0.63 \angle +7.5^\circ & 0.43 \angle -73^\circ & 0.63 \angle +7.5^\circ \end{bmatrix} \begin{bmatrix} 1 \\ \cos \theta \\ \sin \theta \end{bmatrix}$$

where  $r \angle \phi$  represents a quantity of magnitude  $r$  and phase-shift  $\phi$  relative

to an arbitrary reference, and  $\theta$  is the azimuth angle of a unit amplitude sound source measured in a clockwise sense from the centre-front direction of the sound stage. The first component represents the mono, or omnidirectional response, the second the front/back directional response, and the third component represents the left/right directional response. The locus of this encoding equation on the sphere is shown by the dashed line in Fig. 1, with marks for the encoding positions of the eight cardinal sound-stage locations ( $C_F, R_F, C_R, R_B, C_B$  shown, and  $L_B, C_L, L_F$  are on the other side of the sphere to the corresponding right-hand positions). This locus also corresponds to that obtained using coincident group-microphone techniques for recording the natural sound-field at a single location.

It is common studio practice however, to position a sound-source electrically by panning a source signal between pairs of channels (pairwise panpot mixing). In quad mixing such panning is usually arranged to take place between the four corner channels  $L_F, R_F, L_B, R_B$ , and the equation for Matrix H given above has to be adapted to accommodate these inputs. It then takes on the form

$$\begin{bmatrix} L \\ R \end{bmatrix} = \begin{bmatrix} 0.94 \angle 10^\circ & 0.34 \angle 65^\circ & 0.94 \angle -25^\circ & 0.34 \angle -115^\circ \\ 0.34 \angle -65^\circ & 0.94 \angle -10^\circ & 0.34 \angle 115^\circ & 0.94 \angle 25^\circ \end{bmatrix} \begin{bmatrix} L_F \\ R_F \\ L_B \\ R_B \end{bmatrix}$$

The locus of this equation is shown by the solid line in Fig. 1 for pairwise panpot mixing, and is the form in which Matrix H is usually instrumented. This

<sup>8</sup>An explanation of matrix notation in relation to surround systems may be found in reference<sup>1</sup>.

configuration also provides ideal group-microphone encoding, following the dashed curve, for four coincident hypercardioid-response microphones arranged to point in the directions of the corresponding loudspeakers used in quadrasonic reproduction. In practice four cardioid-response microphone elements are used, and their signals are mixed to give the required hypercardioid-response signals, with a forward/backward response ratio of 5.83.

For maximum front/back discrimination the centre-front ( $C_F$ ) and centre-back ( $C_B$ ) encoding points should be diametrically opposite one another on the sphere, as are the centre-left ( $C_L$ ) and centre-right ( $C_R$ ) encoding points. However, this would involve using too much of the slight and severe impairment zones, thus seriously affecting compatibility, and so the Matrix H loci have been bent so that 80% of the locus lies in the negligible impairment zone. None of the locus enters the severe impairment zone and only the region near  $C_B$  significantly enters the slight impairment zone. This last-mentioned feature is used to advantage in that even the stereophonic listener gains an impression of the depth of the sound stage.

The distribution of encoding azimuths around the locus is arranged to give sensible localization in stereo as well as correct localization in quad. Fig.2 shows experimental results for the stereo image localization and image spread, or diffuseness, using Matrix H and, for comparison, using a direct stereo fold-down from a four-channel discrete system. (The corresponding front and back signals are simply summed to give what is known as discrete-blend stereo.) With discrete-blend stereo, full stage width is given to the front and back quadrants of the sound stage whilst the side quadrants are compressed to two points. This usually results in a very "ping-pong" stereo presentation of the programme. Also there is no differentiation between front and back quadrants, which can make the sound presentation dull or even confusing.

Matrix H, on the other hand, gives a more uniform distribution of the sound-stage whilst maintaining prime emphasis on the all-important front sector. The front quadrant spans most of the stereo stage with  $C_L$  and  $C_R$  actually at the loudspeakers, and the rear corner positions are arranged so that overwidth stereo may be obtained, particularly when using pairwise-panpot mixing. Thus, images may be localized outside the space enclosed by the loudspeakers and, without generating unpleasant phase effects, a "super stereo" can be produced when desired. Centre-back is reproduced somewhat spread compared with  $C_F$  and also displaced slightly to one side. This diffuseness of rear images is subjectively very good in a complex programme mix in that it gives a more distant

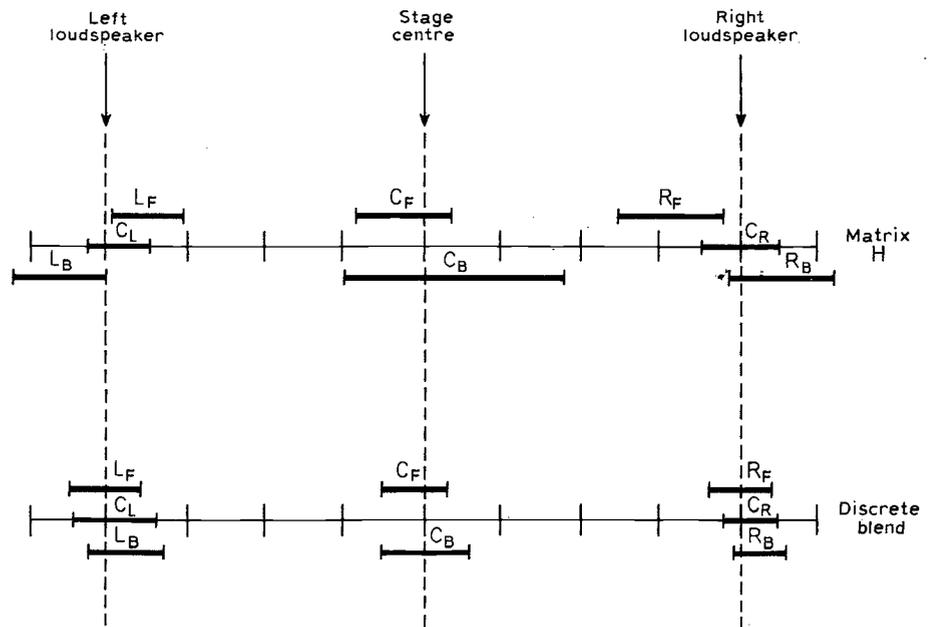


Fig.2. Stereo image localization and spread for Matrix H and "discrete blend".

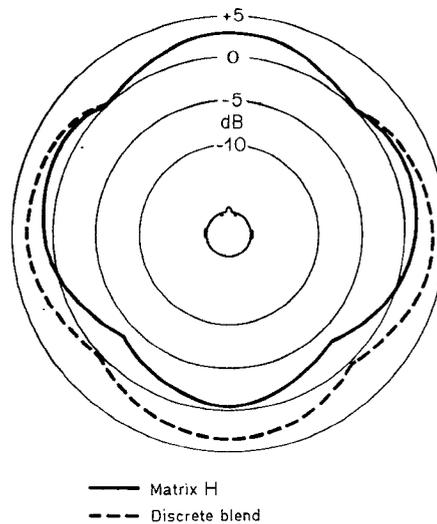


Fig.3. Variation of mono signal with sound-stage location.

perspective and hence creates depth to the stereophonic sound-picture, with the front sound stage appearing more prominent.

In monophonic reproduction, Fig.3, Matrix H gives a small bias towards the front of the sound-stage when compared with discrete-blend mono (obtained by summing the four-channels of a discrete system). With pairwise panpot mixing, a maximum level reduction of 3.6dB with respect to the front corner stage locations occurs at the rear corner positions. This is a highly desirable feature for stage/ambience (e.g. concert hall) recordings, where a reduction of ambience level is required in mono to retain a subjectively satisfactory sound balance with principal sources. In surround presentations, where such a level drop would not be desirable, the rear corner sounds

are simply panned inward slightly toward stage centre, equivalent to about -15dB cross-mix to the opposite front corner encoding point. This corresponds to moving the rear corner encoding point on the sphere towards that for coincident microphone recording. Thus "quad" presentation is not substantially altered, and the only penalty paid is that the overwidth effect in stereo is reduced slightly.

**Matrix H decoding**

To obtain surround sound, a suitable decoder is required to extract the directional information from the coded two-channel signal. A linear decoding matrix may be formed by taking the complex conjugates of the row elements of the encode matrix and writing them down as the column elements of the decode matrix

$$\begin{bmatrix} L'_F \\ R'_F \\ L'_B \\ R'_B \end{bmatrix} = \begin{bmatrix} 0.94 \angle -10^\circ & 0.34 \angle 65^\circ \\ 0.34 \angle -65^\circ & 0.94 \angle 10^\circ \\ 0.94 \angle 25^\circ & 0.34 \angle -115^\circ \\ 0.34 \angle 115^\circ & 0.94 \angle -25^\circ \end{bmatrix} \begin{bmatrix} L \\ R \end{bmatrix}$$

This results in an overall transfer function for the Matrix H system of

$$\begin{bmatrix} L'_F \\ R'_F \\ L'_B \\ R'_B \end{bmatrix} = \begin{bmatrix} 1.00 \angle 0^\circ & 0.64 \angle 55^\circ & 0.79 \angle -40^\circ & 0.19 \angle 163^\circ \\ 0.64 \angle -55^\circ & 1.00 \angle 0^\circ & 0.19 \angle -163^\circ & 0.79 \angle 40^\circ \\ 0.79 \angle 40^\circ & 0.19 \angle 163^\circ & 1.00 \angle 0^\circ & 0.64 \angle -90^\circ \\ 0.19 \angle -163^\circ & 0.79 \angle -40^\circ & 0.64 \angle 90^\circ & 1.00 \angle 0^\circ \end{bmatrix} \begin{bmatrix} L_F \\ R_F \\ L_B \\ R_B \end{bmatrix}$$

Low separation figures are obtained between adjacent outputs; this characteristic is typical of two-channel linear matrix systems, as only two outputs can be completely isolated. However, in the case of Matrix H decoding the signal separations obtained are not symmetrically disposed, and were optimized by taking account of psychoacoustic properties so that a centrally-seated, forward-facing listener obtains optimum results. In addition, the phase relationships between these signals were modified to further enhance the directionality of sound sources and substantially eliminate unpleasant

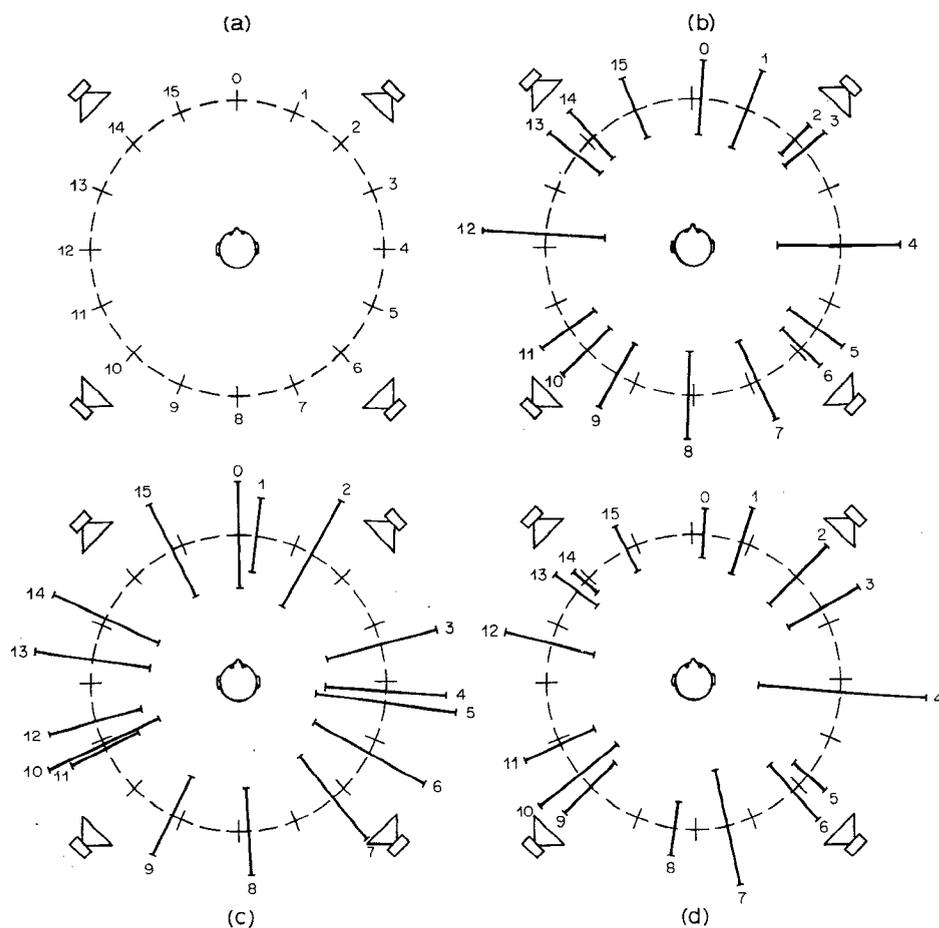


Fig. 4. "Quad" image localization and spread (length of radial bars). (a) Ideal test-image positions, (b) four-channel results, (c) two-channel Matrix H linear decoder, and (d) Matrix H with programme-dependent decoder.

phase effects which can occur with basic matrix decoding due to large phase differences between associated signals.

The performance of this decoder was initially assessed in single-source localization tests, in which the listener was asked to estimate the position and spread, or diffuseness, of the sound-image produced when a source-signal was encoded at any one of 16 azimuth positions. Fig. 4(a) shows the ideal locations of the test sound-images (numbered 0 to 15, position 0 corresponding to the  $C_F$  position) and Fig. 4(b) shows the corresponding mean assessed image positions together with their image spreads, for a discrete four-channel system.

A reasonable distribution of images is obtained, although the side quadrant positions are more diffuse and sensitive to positioning. In comparison, Fig. 4(c) shows results for the basic linear Matrix H system. Although there is more variation in absolute positional accuracy, a fairly uniform image distribution is maintained and hence relative sound localization is good. Image spreads are greater for Matrix H, notably in the

corner locations, but again remain fairly uniform around the whole sound stage.

These results were substantially better than for any other linear matrix system tested. However, a limitation of linear matrix decoding is that it is sensitive to listening position if the correct directionality of sounds is to be maintained. Also the sound stage is reproduced too close to the listener. Nevertheless, linear Matrix H creates a pleasing sound sensation, even when listening off-centre, possessing the warm and spacious characteristics of good surround sound reproduction.

For a larger effective usable listening area, signal separations greater than can be provided by linear matrix decoding are required. These can be achieved by a programme dependent technique in the decoding process. The decoder is still based upon the linear matrix of the system, but circuits are introduced which detect the principal (loudest) sound-source location and vary the decoding parameters to enhance its subjective localization.

In principle, an enhanced two-channel matrix decoder is capable of reproducing sources at any single location with the same fidelity as a four-channel discrete system. However, it is a fundamental limitation of such matrix systems that sources at different locations cannot all be reproduced faithfully at the same time. In fact, some of the early "enhanced" decoders caused quite unpleasant effects, such as severe image instability and/or level variations, but if the variable decoding mechanisms are

suitably controlled, e.g. the gain-laws and time-constants selected with care, these objectionable effects can be reduced almost to the point of inaudibility.

It has been found that a variable-matrix enhancement technique, first developed by Sansui<sup>8</sup> (see for example reference 9) is the most successful to date. The detailed mechanics of such decoding are complex and there are many possible variations, but details of such a technique for matrix H and a suitable decoder are to be published in a subsequent issue of *Wireless World*. With Matrix H, however, the advantages of a good linear decoding matrix are combined with those of variable matrix enhancement, so that a good decoding performance is obtained not only when there is a principal sound source to command the enhancement circuits, but also in an ambience-sound situation when there is no dominant sound source to cause the decoding matrix to vary from its quiescent linear condition. This obviously eases the compromises that have to be made in decoder design to make it perform well with both simple and complex sound-stage arrangements.

Subjectively, when enhancement is applied to a Matrix H decoder, the sensitivity to listener position is reduced, and the "closing in" characteristic of the linear matrix disappears. Fig. 4(d) shows image localization and spread results obtained for an experimental enhanced Matrix H decoder. Positional accuracy is close to that of a discrete four-channel system and image spreads are very similar. Assessments on pre-mixed programme material also show a surround-sound performance similar to that of a discrete system is obtained. The performance is better than that from the best commercial systems with programme-dependent decoding, but with the significant advantage that it combines with a highly compatible stereo and mono presentation from the same encoded signals.

### System assessment

Matrix H had proved to be highly compatible and effective in the laboratory, but it was then necessary to find out whether the system was readily useable in practice, under the normal processes of programme production in existing studio installations. Also it was important to set up an impartial experiment to find out whether any of the other system proposals had developed to the point where they might in practice be equally, or better suited to a surround-sound broadcast service. The BBC invited the proponents of all known practical systems to submit their equipment and supervise its installation. The following accepted: BMX, SQ, QS and Matrix H.

Programme production teams selected material recorded on 16-track master-tapes, some recorded using indivi-

dual spot microphones and some recorded using coincident groups of microphones, and were asked to make surround-sound programmes, suitable for compatible broadcasting, with each of five anonymous systems, one of which was a discrete four-channel system which served as a reference. They had to mix the programme independently through each system to try and attain their desired intention, making compromises where necessary to maintain good stereo and mono compatibility.

The resulting programme mixes were recorded and later played back for independent assessment of the quad, stereo, and mono performances, still as anonymous systems to the listeners. The listeners were told of the producers' broad intentions, in the form of an ideal stage layout chart for each programme item and were asked to score each system by placing a mark at the appropriate point on a linear scale running from "bad" to "good". Fig. 5 shows the averaged results for separate assessments of the quad, stereo, and mono performances together with an overall assessment. As the systems were presented in a randomized order in each set of tests, listeners were then told which of their results pertained to the same, but still anonymous, system so that they could give their overall assessment.


Listening in quadraphony Fig.5(a), the discrete four-channel system came out best, with Matrix H a close second; and the three other systems (labelled X, Y and Z) were significantly worse. In stereo, Fig.5(b) Matrix H was clearly preferred, and in mono the preference for Matrix H was slight. Note that the direct fold-down of the discrete four-channel system (discrete blend) was not particularly well liked for its stereo and mono performances, as was predicted. Finally, Fig.5(d) shows the average of listeners overall assessments and confirms that as a broadcast system Matrix H is the best viable choice.

**Broadcast developments**


Matrix H encoded programmes have been made by the BBC and other European broadcasters; some of the Promenade Concerts broadcast during the 1976 season were encoded by Matrix H. Recordings of the latter were made off-air, using a conventional v.h.f. stereo receiver, and later compared with recordings made on site at the recording environment. Such comparisons provided confirmation that the BBC's normal stereo broadcast network can handle Matrix H transmissions without problem.

The advantage of the two-channel compatible system is that surround-sound broadcasting can take place over existing stereo networks and transmitters, and all existing stereo facilities can continue to be used. Most importantly, this includes the listener's equipment, and not only his v.h.f. stereo receiver, but also his disc and tape apparatus.


**(a) QUADRAPHONIC PERFORMANCE**

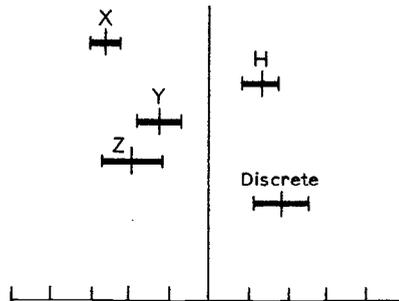

**(b) STEREO PERFORMANCE**

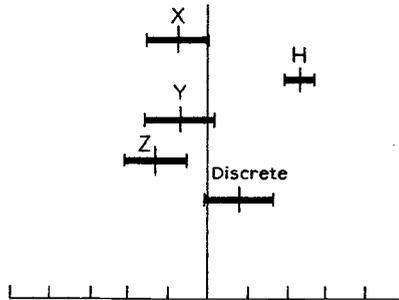

**(c) MONO PERFORMANCE**

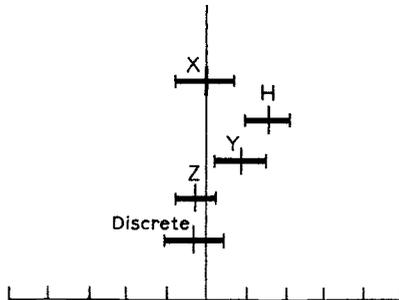

**(d) OVERALL PERFORMANCE**

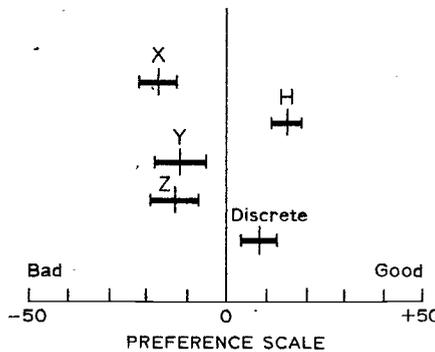


Fig.5. System comparison tests showing listener's preference for "serious" music (horizontal bars show standard deviations).

Nothing is rendered redundant, but it is of course necessary to provide a decoder, loudspeakers, and amplifier, to gain the extra sound dimension.

Systems using a third or fourth signal could not be handled by existing receivers or recording apparatus, and the additional cost to both listener and broadcaster of adding extra signals would be large. The question would be whether any achieved improvement in performance over that of two-channel Matrix H could be considered worth-

while. In the unlikely event of it becoming possible to devise a new broadcasting system, with the necessary extra bandwidth and improved s/n Matrix H could, of course, readily be expanded to provide three or even four transmission signals. Even so, as it would retain its present excellent stereo and mono compatibility and the present high standard of quadraphony for existing listeners, one wonders how many listeners would consider the additional expense of three- or four-channel receiving apparatus justifiable.

The BBC intends to broadcast a number of experimental programmes using Matrix H throughout the remainder of 1977, and the early part of 1978 at least. Details of these will be published in *Radio Times*. Listeners who wish to decode these broadcasts to give the full surround-sound effect will be interested in the forthcoming *Wireless World* article describing a suitable decoder. Existing decoders designed for use with other systems will not normally provide a satisfactory performance without modification\*† and naturally optimum performance can only be expected from a purpose-built decoder.

**Acknowledgements.** The authors wish to thank the Director of Engineering of the BBC for permission to publish this article and are also grateful to the many people who have helped during the development of Matrix H, in particular Messrs Crompton, Gaskell, Harrison, and Wright.

**References**

- Carey, M. J. and Sager, J. C. Quadrasonic broadcasting — current proposals and the way ahead. *Wireless World* Vol.80 November 1974, pp.422-5.
- Meares, D. J. Quadrasonic broadcasting — an alternative view *Wireless World* Vol.81, February 1975, pp.65/6.
- Netzband, R. Multiplex systems for v.h.f./f.m. sound broadcasting. *E.B.U. Review*, (Technical,) October 1974, pp.225-9.
- Shorter, G. Four-channel stereo. *Wireless World*, Vol.78 January 1972 pp.2-5 and February 1972, pp.54-7.
- Scheiber, P. Analysing phase-amplitude matrix. *Journal of the Audio Engineering Society*, vol.19 November 1971, pp.835-9.
- British Patent Application no. 34839/74.
- Meares, D. J. and Ratliff, P. A. Development of a compatible 4-2-4 quadrasonic matrix system, Matrix 'H'. *E.B.U. Review* (Technical), October 1976, pp.208-17.
- British Patent No. 1,402,320.
- Heller, D. Surround-sound decoders. Parts 3 and 4 (QS Variomatrix). *Wireless World*, Vol.82 August 1976 pp.57-9 and September 1976 pp.53-6.

\* However the latest NRDC proposals (system 45J, see last issue) are close to Matrix H encoding specification; this should enable a suitably designed decoder to give a satisfactory performance with either system.

† See elsewhere in this issue for Variomatrix modification details.—Ed.

# World of Amateur Radio

## Changes in amateur examination

Since its introduction in 1946 the Radio Amateurs' Examination of the City and Guilds of London Institute — the examination which must be passed to obtain either a Class A or Class B licence in the United Kingdom — has been conducted as a three-hour written paper, divided into two parts: Part 1 with two compulsory questions; Part 2 with eight questions of which six should be attempted.

But from 1979, City and Guilds are expected to introduce a new format to the examination based on objective tests containing multiple-choice questions, i.e. four possible answers are provided and the candidate indicates which he thinks is the right one. This technique, if pitched at the right level, can provide a revealing assessment of the knowledge of a candidate without reference to his "literary" abilities and can result in more consistent marking. Such an approach would seem very suitable for an examination taken by candidates who range from about 14 to over 70 years of age.

In preparation for these changes the City and Guilds is inviting readers in the London area to take part in pre-tests of the new form of exam on May 3, as follows:

"The RAE from 1979 will be in the form of Objective Tests containing multiple-choice questions. If you are preparing for your amateur licence on your own and live in the London area, you may be able to assist. It is the Institute's policy to pre-test objective questions, trying them out on candidates who have reached examination standard. Pre-tests are intended to test the performance of individual questions and syllabus coverage. Information is obtained which assists the Institute's reviewing panels in judging whether each individual question should be included in the question bank for use in future exams . . . pre-tests must be administered to a sample of students representative of those who will take the exam. Many would-be radio amateurs prepare for exams without fol-

lowing a college course and the Institute invites such candidates who live in the London area to assist.

"The pre-tests are to be held at the Institute, 76 Portland Place, W1, on Tuesday, May 3, from 10.15 a.m. As well as helping us the tests may help would-be examinees to revise their work and gain some exam experience. If you are willing to assist please telephone Miss Jackie Clifford (01-278 2468, ext. 491). Invitation will be issued to eligible candidates."

## Promoting RTTY

The British Amateur Radio Teleprinter Group seems to have stepped up its efforts to encourage more use of r.t.t.y. by British amateurs. Apart from publishing information on the principles and practice of r.t.t.y., BARTG has recently established a team of lecturers prepared to talk on r.t.t.y. to amateur radio clubs. Requests should be made to J. P. G. Jones, GW31GG, Hon. Sec. BARTG, 40 Lower Quay Road, Hook, Haverfordwest, Dyfed SA62 4LR.

BARTG is holding its annual convention on Saturday, May 21, at the Village Hall, Meopham, Kent, where there will be lectures, trade stands, bring-and-buy stall and a "tape factory". Trains arriving at Meopham station before 1315 hours will be met by transport.

An American amateur who first demonstrated a radio teleprinter system as long ago as 1921 has recently been honoured by the Radio Club of America. The club's 1976 Sarnoff Medal has been awarded to Captain W. G. H. Finch, first licensed in 1912 as 8MK and 8IE. His early r.t.t.y. was based on his invention of a highly sensitive relay.

## Silver Jubilee prefix

To mark the Queen's Silver Jubilee the Home Office is authorizing all British Class A and B amateurs to use the special commemorative prefix "GE" instead of the usual G, GM etc. in all parts of the UK from 0001 hours on Saturday, June 4 to 2359 hours on Sunday, June 12. This is the first time a special prefix has been made generally available to UK amateurs to mark a national event and the Home Office state that it will not set a precedent.

## Scanning the bands

Sunspot activity seems to be rising again (at last!) with h.f. conditions in December, January and February benefiting from the small but noticeable improvement. Particularly fortunate was the ARRL DX contest (c.w. section) on February 10-20 with many of the new "N" two-letter calls pounding in on 7, 14 and 21 MHz. Maritime activity on 21MHz also seems to be on the increase: recent contacts have been with JF3HAN/mm near Hong Kong;

JA4GY/mm in the Arabian Sea; and YU3EO/mm a freighter in mid-Atlantic.

It is reported that during the American bicentennial year (1976) Dick Spencerley, KV4AA — operating as AJ3AA — made some 35,000 contacts, an average of nearly 100 a day, from the Virgin Islands — surely a record!

Microwave Associates are producing a 20mW Gunn-diode 10GHz transceiver specifically for the amateur. It is supplied with (or without) a 17dB gain horn antenna, Schottky diode mixer and circulator. It can put an amateur on the 10GHz band at costs very favourable in comparison with those for factory equipment at lower frequencies. Details are in "Bulletin 7624" issued by the firm.

"World Radio Club" — the BBC World Service programme for DX enthusiasts and amateurs — celebrated its 500th weekly edition with one of the few audience participation broadcasts ever produced at Bush House. Over 32,000 listeners have joined the club since it began in July 1967.

"Employers in the communications industry have reason to be grateful to the RSGB for the enthusiasm and expertise implanted in many of their young apprentices through membership of local radio clubs and the society itself. I hope more firms will take a closer and more practical interest in the RSGB in the future" — Lord Wallace of Coslany at his installation as 1977 president of the RSGB held at the Palace of Westminster.

## In brief

The new honorary secretary of the Radio Amateur Invalid and Bedfast Club is Mr H. R. Boutle, G2CLP, 14 Queen's Drive, Bedford MK41 9QB . . . A feature of the RSGB International Radio Communication Exhibition and Convention at Alexandra Palace, London on May 6-8 will be a "Members' Mart" on May 8 in the west corridor . . . Northern Radio Societies' Association annual convention and exhibition — sponsored by a number of radio societies in the north of England, is at Belle Vue, Manchester, on Sunday, April 24. A record number of trade exhibitors and club standards are expected . . . The 3rd European Conference for Radio Amateurs under the aegis of the German society DARC takes place May 27-30 at Wolfsburg. Earlier conferences were held in 1968 and 1972 . . . Harold Woodhead, G2NX, who died recently was one of the first, if not the first, amateur to use single-sideband in the UK . . . A busy time for mobile rallies: May 1 Spalding Tulip-Time Rally (Gleed Boys School, Spalding); May 22 Welsh Mobile Rally (Barry Rugby Football Ground) and Northern Mobile Rally (Victoria Park Hall, Keighley); May 29 Suffolk Wireless Revival (Ipswich), Southend (Fitzwimarc School, Rayleigh) and a Hull rally.

PAT HAWKER, G3VA


# Electrolytic capacitor tester

Automatic instrument offers a reform facility and meter display

by A. Drummond-Murray

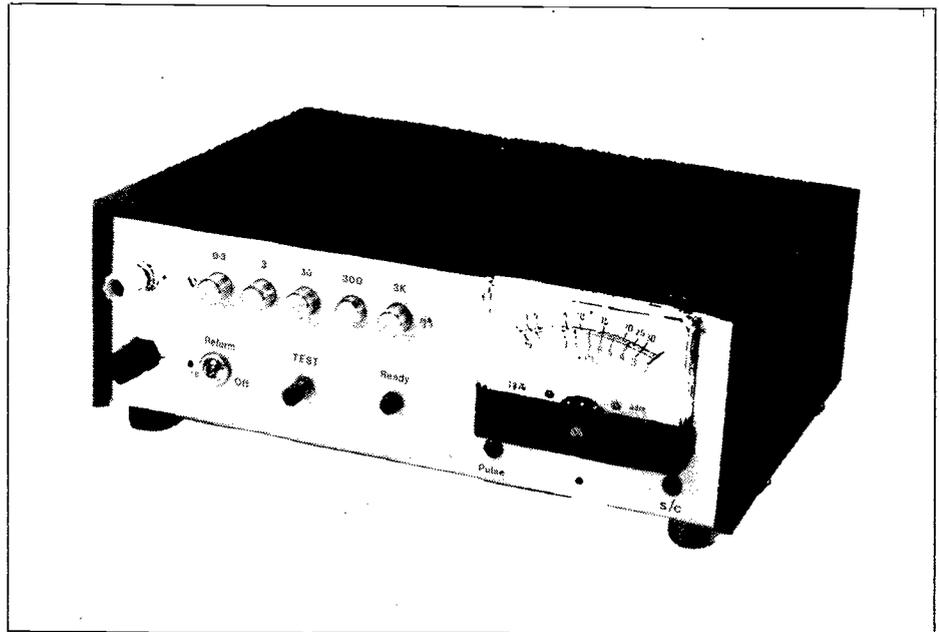**This instrument uses a charge injection technique to develop a voltage across the capacitor under test. The voltage is measured on a calibrated meter and no balancing or adjusting is required except for range selection. A reform facility allows an old or unused capacitor to have a voltage applied for about 15s which re-polarizes the dielectric before a measurement is made. An indication of leakage is also provided by the meter movement which is buffered by a f.e.t.-input amplifier.**

Electrolytic capacitors depend on a dielectric formed on a aluminium or tantalum electrode by a thin layer of oxide. This dielectric requires polarizing to maintain its insulating properties and long periods of rest can result in de-polarization, a high leakage current and even total breakdown. Fortunately, the dielectric layer can be restored by applying a polarizing potential to the capacitor for at least five minutes via a current limiting resistor. This process is known as reforming. If a capacitor is to be tested and has started to de-polarize, a reforming period is necessary before any meaningful results can be obtained. The tester is provided with a reform facility which charges the capacitor to +12V via a 1200 $\Omega$  resistor for about 15 seconds prior to the capacitance measurement. Although this period is too short for complete reforming, it is sufficient for most capacitors to recover enough for testing. The main property to suffer from incomplete reforming is leakage current. If, on test, a capacitor exhibits a high leakage current, a second reform period will often suffice. If no such improvement is apparent, the capacitor is faulty and unlikely to benefit from a prolonged reform. A short tone from the instrument indicates that the reform period is complete. Three l.e.d.s indicate the state of the circuit during the test process. A green l.e.d. indicates that the reform process is ready to start and a red type indicates that an excessive current is flowing during the polarizing period. This facility is useful for detecting short circuit capacitors.



During the measuring cycle, a further l.e.d. flashes when the test capacitor is being charged.

An equivalent circuit is shown in Fig. 1. The charge period on any range is the same for any unknown capacitance, and the voltage developed across the capacitor is proportional to its capacitance. If this voltage is measured from 0V instead of 12V, the capacitance increase is indicated as an increased voltage. This voltage rises exponentially. Fig. 2 shows the sequence of events following a start pulse. After a polarizing potential is applied, the capacitor is completely discharged through a circuit which limits the peak current to 100mA. A finite charge is then injected into the capacitor and the voltage is measured on a calibrated meter. The rate of decay is taken as a measure of internal

leakage. A complete circuit of the tester is shown in Fig. 3.

Input impedance of the measuring circuit is important because of the shunting effect which occurs. Fortunately, modern operational amplifiers are ideally suited for producing high input


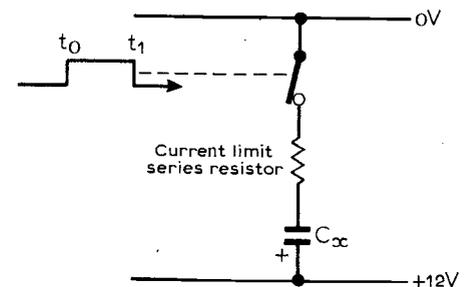


Fig.1. Simplified circuit of the tester

Fig.2. Block diagram of circuit operation.

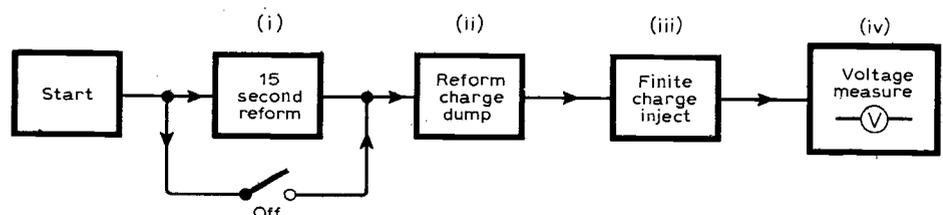

impedances. Simple devices like the 741 can be made to have a high input impedance, but the bias current taken by the input transistors can still cause the capacitor voltage to vary. F.e.t.-input op-amps do not suffer from this problem, and the input resistance is greater than 1000MΩ. Using a f.e.t.-input amplifier the meter reading obtained with a 1μF polyester capacitor had no change after 20 minutes. Leakage current through any conventional electrolytic capacitor is certain to be many times higher than this, so the meter-drive loading may be disregarded.

In general the range of the instrument is altered by varying the charge current period. Because each range is ten times larger than the previous one, the charge injected increases by the same proportion, so the scale calibration is correct for all ranges. Calibration of the instrument is achieved by using known values of capacitance and marking the scale accordingly. Mullard 10% 100V polyester types with values 0.33μF, 0.47μF and 1.0μF ×3, were used and checked on a capacitance bridge and found to be within ±5%. These are quite adequate for calibration in view of the wide tolerance of electrolytic types (up to +100% -50%). On the 3000μF range a ten-fold increase in charge current is used to avoid a 47μF non-electrolytic capacitor, which is both large and expensive. The charging current is determined by the series resistance in the circuit and by the exponential rise in voltage across the capacitor. On the 3000μF range the

initial current is a little under 100mA, so a well regulated supply is required to prevent a momentary fall in voltage as the 100mA demand is met.

The timing sequences are controlled by three monostable multivibrators. The initial forming period is determined by the 1000μF electrolytic capacitor on IC<sub>1a</sub> and will vary with the component used. If it is not desired to reform a capacitor before testing, the 1000μF capacitor is switched out of circuit, and the period reduces to a few nanoseconds. At the completion of this period the test capacitor is fully discharged. The duration of the discharge cycle is 0.25s on all except the 3000μF range which is increased to 2s. Capacitor C<sub>5</sub> is switched in parallel with the existing timing capacitor, C<sub>4</sub> for this purpose.

As discussed earlier, the accuracy of the instrument depends on each range having a ten-fold change in the amount of charge injected during the test period. Stable capacitors are therefore required on the timing multivibrator, IC<sub>3</sub>. Polycarbonate and polystyrene capacitors are particularly suitable but mylar, paper or ceramic devices are not recommended.


On all but the 3000μF range, the test capacitors are charged through a series 1.2kΩ resistor and consequently the accuracy with which the periods change directly affects the meter calibration from range to range. On the

3000μF range the test capacitor is charged through 120Ω, formed by the addition of 135Ω in parallel with R<sub>12</sub>. Two extra resistors are used to prevent aging due to the relatively high peak current of 100mA.

A monostable is used to drive the precision charge circuit because this device is recommended by the manufacturer for stability and repeatability.

Operation of the circuit is indicated by the pulsing of LED<sub>2</sub>. During the reform period, current passing through R<sub>12</sub> is monitored by Tr<sub>4</sub>. If the V<sub>be</sub> exceeds 0.7V then Tr<sub>4</sub> turns on LED<sub>3</sub>. Resistor R<sub>14</sub> limits the base current and prevents Tr<sub>4</sub> from shunting R<sub>12</sub>. The l.e.d. is illuminated fully when the capacitor current exceeds about 5mA. During the discharge sequence, Tr<sub>2</sub> is turned on by Tr<sub>3</sub> and Tr<sub>1</sub> remains cut off. When Tr<sub>2</sub> turns on, the discharge path is completed via R<sub>12</sub> and R<sub>13</sub> in series. Because R<sub>12</sub> is in parallel with a diode which will be forward biased, the maximum potential across R<sub>12</sub> is limited to 0.7V so the remainder of the voltage drop will be across R<sub>13</sub> which is a low resistance. Diode D<sub>3</sub> removes R<sub>12</sub> from the discharge path during the initial current flow, and until the capacitor voltage falls below 0.7V. Schmitt trigger IC<sub>4a</sub> is connected as a simple oscillator producing a continuous rectangular waveform. The second Schmitt trigger IC<sub>4b</sub> isolates the oscillator from the loudspeaker. The trailing edge of the reform cycle pulse at Pin 13 of IC<sub>1a</sub> has a positive-going edge which is differentiated by C<sub>2</sub>, R<sub>5</sub> and used to switch the oscillator output to the loudspeaker. It

Fig.3. Complete circuit of the capacitor tester. Switches 3<sub>a</sub> and 3<sub>b</sub> only close on range M of switch 3<sub>c</sub>.

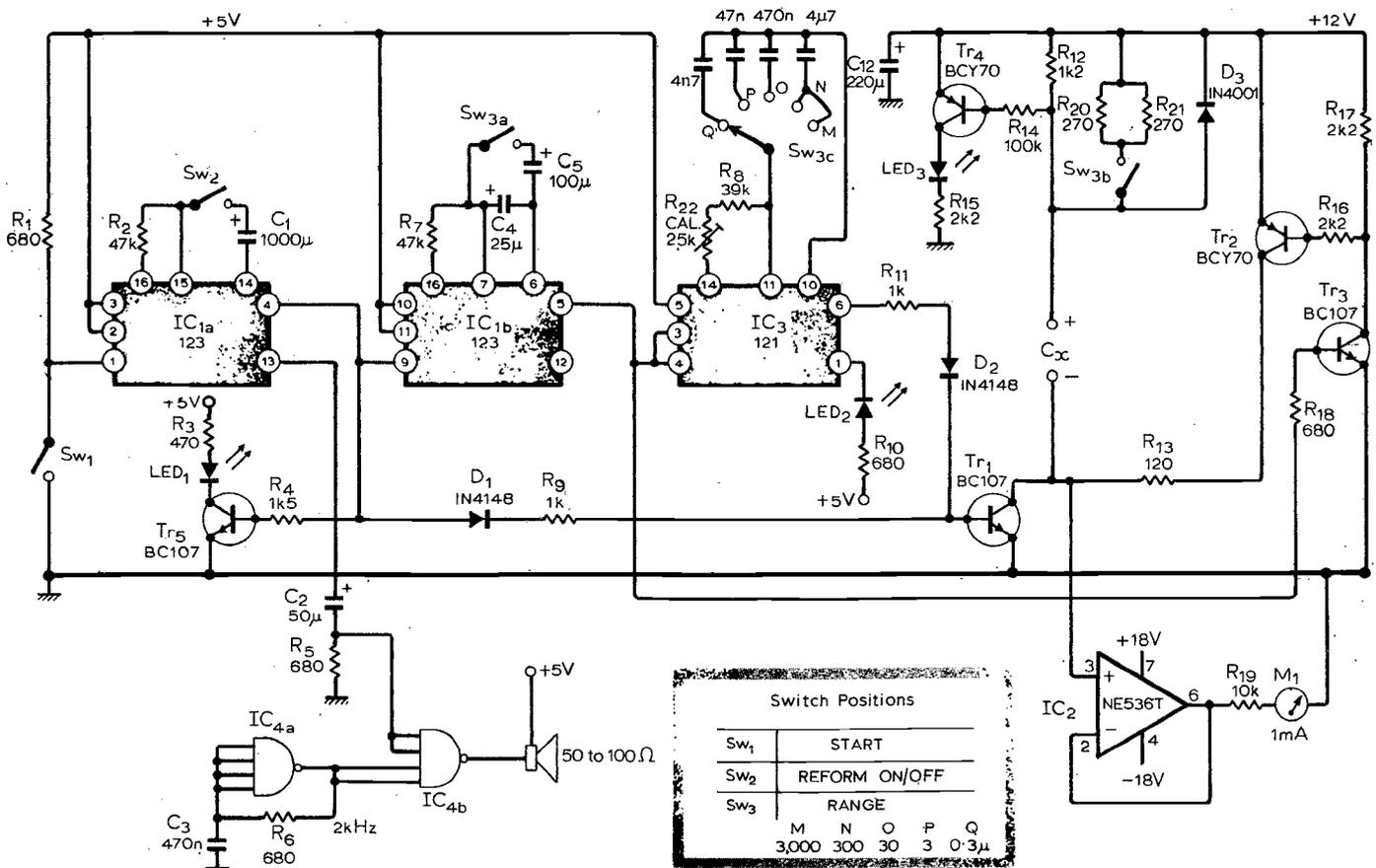

**Components list**

|                       |                                     |
|-----------------------|-------------------------------------|
| R <sub>1</sub>        | 680Ω                                |
| R <sub>2</sub>        | 47k                                 |
| R <sub>3</sub>        | 470Ω                                |
| R <sub>4</sub>        | 1.5k                                |
| R <sub>5</sub>        | 680Ω                                |
| R <sub>6</sub>        | 680Ω                                |
| R <sub>7</sub>        | 47k                                 |
| R <sub>8</sub>        | 39k                                 |
| R <sub>9</sub>        | 1k                                  |
| R <sub>10</sub>       | 680Ω                                |
| R <sub>11</sub>       | 1k                                  |
| R <sub>12</sub>       | 1.2k                                |
| R <sub>13</sub>       | 120Ω ¼W                             |
| R <sub>14</sub>       | 100k                                |
| R <sub>15,16,17</sub> | 2.2k                                |
| R <sub>18</sub>       | 680Ω                                |
| R <sub>19</sub>       | 10k                                 |
| R <sub>20,21</sub>    | 270Ω                                |
| R <sub>22</sub>       | 25k preset                          |
| C <sub>1</sub>        | 1000µF 10V                          |
| C <sub>2</sub>        | 50µF 10V                            |
| C <sub>3</sub>        | 0.47µF 10V                          |
| C <sub>4</sub>        | 25µF 10V                            |
| C <sub>5</sub>        | 100µF 10V                           |
| C <sub>6</sub>        | 4700pF polystyrene                  |
| C <sub>7</sub>        | 47nF                                |
| C <sub>8</sub>        | 0.47µF polycarbonate                |
| C <sub>9</sub>        | 4.7µF polycarbonate                 |
| C <sub>10</sub>       | 2000µF 25V                          |
| C <sub>11</sub>       | 100µF 25V                           |
| C <sub>12</sub>       | 220µF 25V                           |
| C <sub>13,14</sub>    | 0.1µF disc ceramic                  |
| D <sub>1,2</sub>      | 1N4148                              |
| D <sub>3</sub>        | 1N4001                              |
| Tr <sub>1,3,5</sub>   | BC107                               |
| Tr <sub>2,4</sub>     | BCY70                               |
| LED <sub>1</sub>      | Green                               |
| LED <sub>2,3</sub>    | Red                                 |
| IC <sub>1</sub>       | SN74123N                            |
| IC <sub>2</sub>       | NE536 (or RS Components 'FET MOPA') |
| IC <sub>3</sub>       | SN74121N                            |
| IC <sub>4</sub>       | SN7413N                             |
| IC <sub>5</sub>       | MC7812CP                            |
| IC <sub>6</sub>       | MC7805CP                            |
| Bridge rectifier      | 100V p.i.v., 1A                     |
| <b>Miscellaneous</b>  |                                     |
| Loudspeaker           | 50-100Ω min                         |
| Panel meter           | 1mA                                 |
| Transformer           | 240/15.0.15 1A                      |
| Sw <sub>1</sub>       | SPSM                                |
| Sw <sub>2</sub>       | SPSM                                |
| Sw <sub>3</sub>       | 3P5W                                |
| Fuse                  | 250mA                               |

**Prototype scale calibration**

|  |                         |
|--|-------------------------|
| <i>Capacitance / terminal voltage meter scaled 0-1</i> |                         |
| 0µF  | 0                       |
| 0.33µF   | 0.08                    |
| 0.5µF  | 0.12                    |
| 0.8µF  | 0.34                    |
| 1.0µF  | 0.44                    |
| 1.5µF  | 0.59                    |
| 2.0µF  | 0.75                    |
| 3.0µF  | 0.90                    |
| 12V  | 0                       |
| 10V  | 0.2                     |
| 8V   | 0.4                     |
| 6V   | 0.6                     |
| 4V   | 0.8                     |
| 2V   | 1.0                     |
| 0V   | 20% greater than f.s.d. |

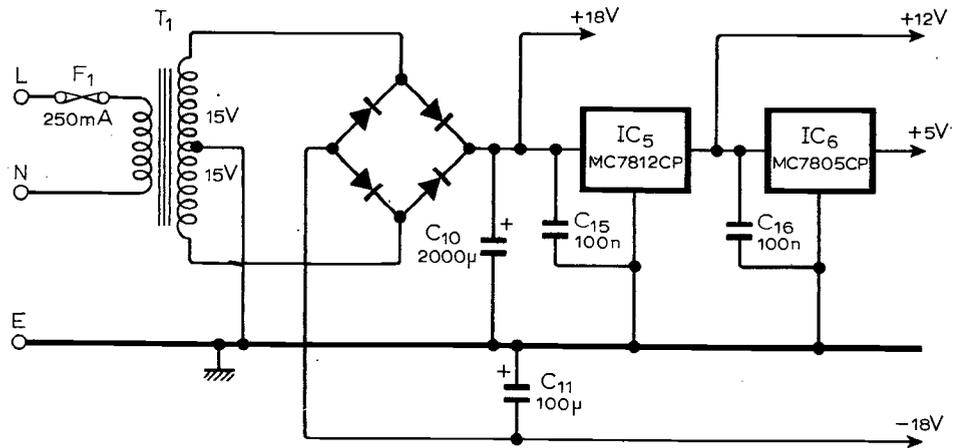


Fig.4. Power supply.

is important that this spike is applied only to a Schmitt trigger input to prevent oscillation when the input voltage lies between logic 1 and 0. The operational amplifier requires positive and negative supplies in order to operate on inputs that are very close to 0 or +12V. Current consumption of the amplifier is low, and the inherent ripple rejection is high so a simple power supply as shown in Fig. 4 is adequate.

**Construction & calibration**

Leads should be kept short and wherever possible separate. This is particularly important in the relatively high impedance wiring associated with the timing circuits of IC<sub>1</sub> and IC<sub>3</sub>. An efficient ground plane should be provided on the circuit board to keep the earth impedance as low as possible. Disc ceramic capacitors should be used to decouple the circuits at h.f. If the power supply leads are more than 25cm long sufficient l.f. decoupling must also be provided. The best solution is to mount the power supply regulators on the circuit board. If monolithic voltage regulators are used, it is advisable to decouple the input lead with a disc ceramic capacitor to ensure stability.

Calibration of the meter movement is achieved by adjusting the preset potentiometer on IC<sub>3</sub> with a capacitor of known value on test. Calibration for other values and ranges should then be correct. Resistor R<sub>19</sub> is used for scaling the voltmeter circuit. The prototype uses a 1mA meter movement and consequently a 10kΩ resistor is required to provide a 10V f.s.d. range. The tester is not really suitable for capacitors with voltage ratings of less than 10V. Lower voltage components may be tested provided that no attempt is made to reform them from the internal 12V current-limited supply, and the range selected for testing ensures that the terminal voltage is less than the capacitor peak voltage rating. The meter scale

can be marked with the capacitor terminal voltage corresponding to the capacitance value of this purpose. The table shows the prototype meter calibration figures.

Electrolytic capacitors vary in value according to the applied voltage, and when a capacitor is severely under-rated, the nominal capacitance is reduced. This must be borne in mind when relatively high voltage capacitors are tested. Because the tester measures voltage from 0V, the capacitor voltage will decay upwards. Some capacitors, always faulty, exhibit a fall of meter reading. This effect is similar to a c.r.t. regaining the e.h.t. potential, after switch-off, due to the physical properties of the glass dielectric.

**P.C.B.s**

A glass fibre printed circuit board which accommodates board mounted switches will be available for £3.50 inclusive from M. R. Sagin at 23 Keyes Road, London NW2.

We understand that Circuit Services, 36 Hallows Crescent, S. Oxhey, Herts, will be offering a set of components for this design.

**Correction**

In the article "Metal detector," published in the April issue, the values of R<sub>3</sub> and R<sub>7</sub> were printed incorrectly in the parts list. The correct values are 4.7kΩ as shown in the circuit diagram.

*Readers of the April issue may have been fooled by Part 2 of the article entitled Power Semiconductors — so were we; it should have read Part 1.*

## Surround sound decoders — 5

# Variomatrix adaptor for System 45J and Matrix H

## Phase shift circuit allows Variomatrix to decode Matrix H and System 45J

by Michael A. Gerzon, M.A., *Mathematical Institute, Oxford.*

Many hi-fi enthusiasts have Sansui Variomatrix decoders, and the present article describes an adaptor suitable for converting the Variomatrix for decoding signals encoded via the NRDC System 45J or BBC Matrix H systems. While such a decoder cannot by psycho-acoustically optimal, it does permit existing owners to extend the usefulness of their equipment.

The adaptor essentially does the job of converting the 45J or Matrix H signals into a form which the Variomatrix is designed to handle, i.e. into signals which are good approximations of Regular Matrix signals. The optimum method of conversion is slightly different for these two systems, but fortunately involves in both cases the use of a  $58^\circ$  phase-shift network, so that the circuit is kept fairly simple despite its two-fold function.

Essentially, the Matrix H adaptor consists of a  $58^\circ$  phase lead put into the right-channel signal relative to the left channel. The System 45J adaptor adds to this a  $-15\text{dB}$  blend circuit at the outputs of the phase shifters. The six pole phase shifter described gives a  $58^\circ$

shift with  $\pm 4^\circ$  error over the frequency range 44Hz to 17kHz if precision components are used, and so is suitable for use even with a studio-quality Variomatrix. In practice for domestic applications, 5% tolerance components may be used, although the use of 2% resistors will give better results.

The input circuit of the adaptor is shown in Fig. 1. Depending on the quality desired, the operational amplifiers may be 741 types or special audio types. The circuit is designed to offer a fairly high and resistive input impedance (18k or 14k depending on switch position), and gives approximately unity overall gain in all modes. The mode switch offers three positions: normal (i.e. conventional use for stereo and Regular Matrix), Matrix H, and System 45J.

An odd feature of the way the adaptor is connected is that (except in normal

mode) all left input signals are fed to the inputs labelled right on the Variomatrix, and vice-versa as shown in Fig. 1. Similarly, all outputs labelled left on the Variomatrix are connected to the corresponding right quadraphonic inputs on the preamplifier, and vice-versa. The reason for the switching shown is to ensure that the left/right interchanging of the Variomatrix inputs and outputs does not occur in the normal switch position, and for this reason, the mode switch is six-pole three-way. Also shown in Fig. 2 is a  $+2\text{dB}$  gain for the back channel outputs in the System 45J mode only; such a  $+2\text{dB}$  gain is necessary for best results. However, constructors may omit these gains from the circuit provided that the front/rear balance control of their system is adjusted to give this  $+2\text{dB}$  rear gain when decoding System 45J.

Owners of Sansui equipment in which the Variomatrix is integrated with the preamplifier and amplifier may not always find it convenient to use the output switching circuitry of Fig. 2, since this would involve breaking into the equipment. For such users, we

Fig. 1. Circuit of pre-Variomatrix adaptor. For best results, components should be 2% tolerance, though 5% should be acceptable.

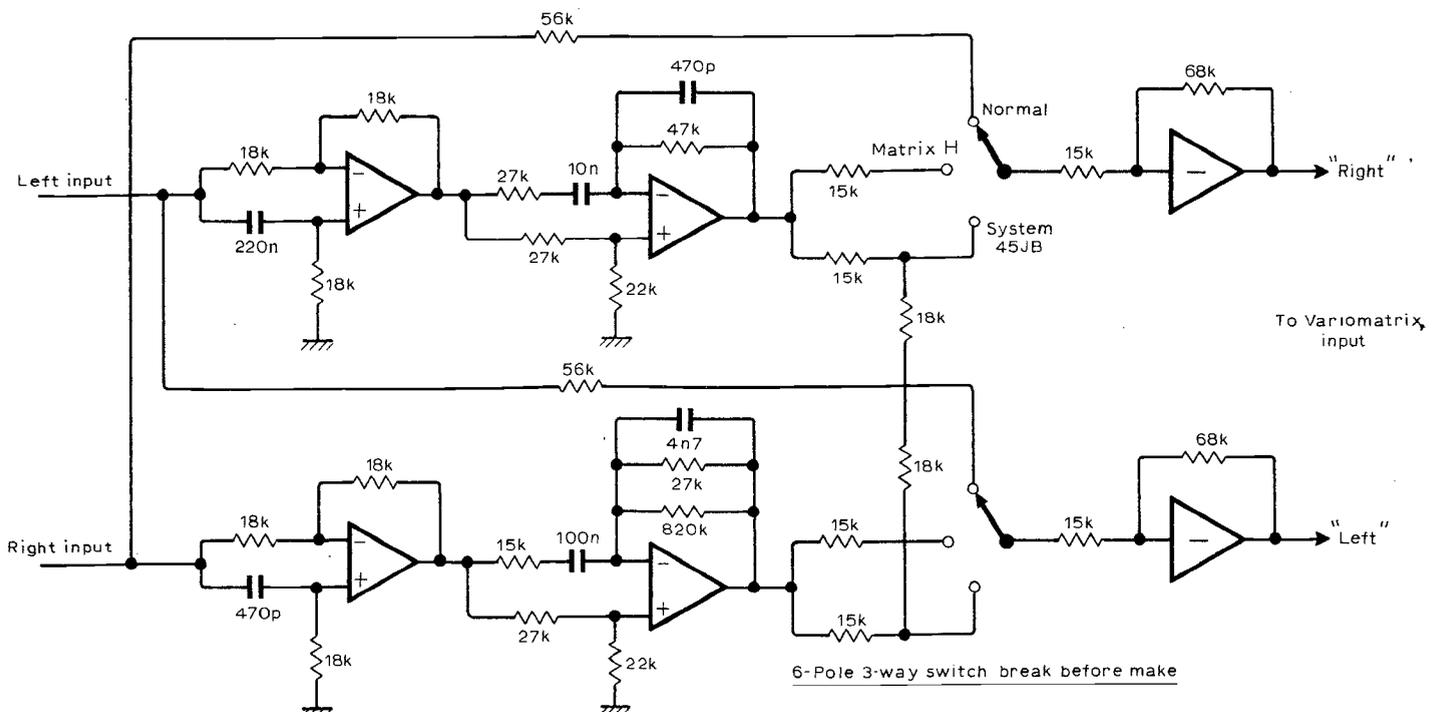


Fig. 2. Post-Variomatrix circuit, includes rear channel switched gain compensation. Resisting 5 or 10% tolerance.

suggest that they use the circuit of Fig. 1, for example in the tape monitoring circuit, but with the following modifications.


Connect the top output of Fig. 1 to the left Variomatrix input (and not the right), and the bottom output of Fig. 1 to the right Variomatrix input (and not the left), and

Feed the two 56kΩ resistors connected to the normal switch position from the left input for the top switch of Fig. 1, and the right input for the bottom switch of Fig. 1.

When used in this way, no left/right interchanging is used, and the switch need only be two-pole three-way. This method of use does not handle "interior encoded" sounds quite so well, but still generally works. For best results with System 45J with this simplified method of use, the front/rear balance control should be set to give +2dB gain to the rear speakers.

The Matrix H switch position will decode existing BMX discs (e.g. the UD-4 discs of Nippon Columbia) with reasonably accurate results, so that in practice the circuit allows decoding of Regular Matrix, Matrix H, System 45J and BMX.

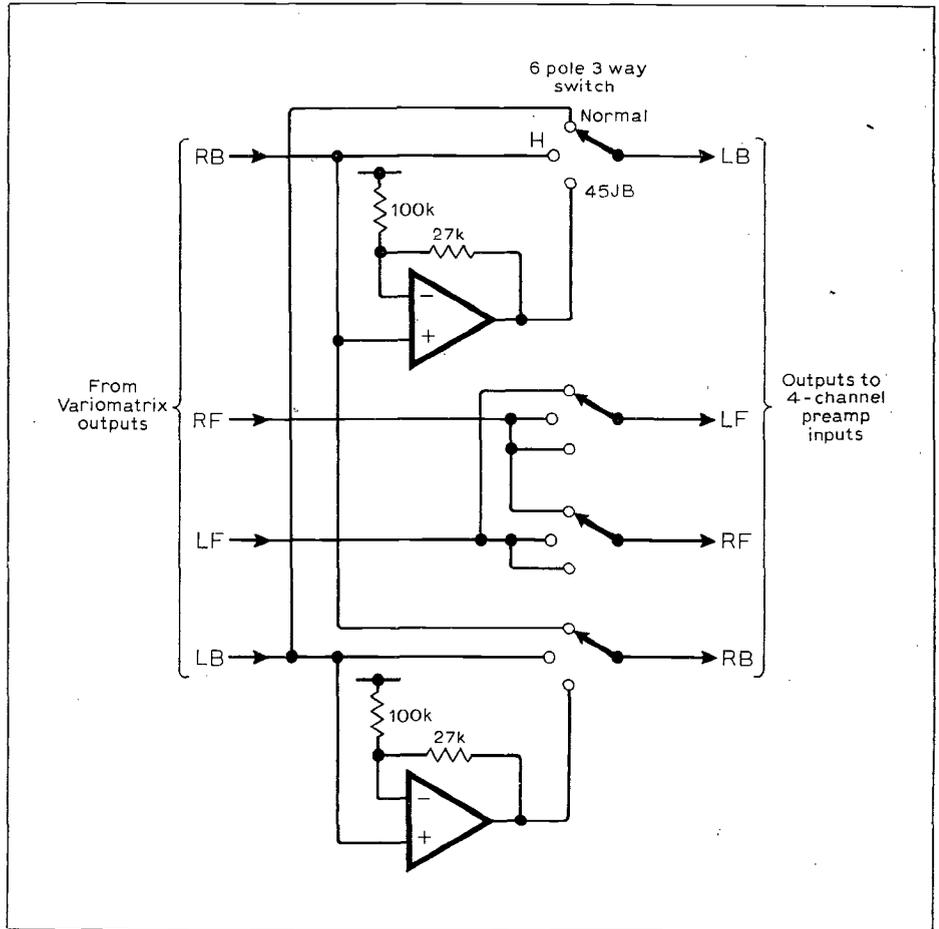As the author is connected with the NRDC Ambisonic project, in order to avoid possible misunderstandings it is pointed out that the use of a Variomatrix with the adaptor described will not give proper NRDC Ambisonic decoding



with optimal psychoacoustic results, but is merely a means of enabling Variomatrix owners to use their existing equipment with some of the newer systems.

Also, the method of using the Variomatrix described is solely the author's responsibility, and neither Sansui Elec-

tric Company Ltd nor the BBC would necessarily regard such use as being according to their own recommendations.





The BBC have applied for a patent (34839/74) on the use of a Variomatrix decoder with a prior phase shifting circuit of about 60°. — Ed.

# HF predictions

Ionospheric conditions this month are about the same as they were in 1974 except that solar activity then was decreasing and now is increasing.

Magnetic disturbance is likely to occur over the whole of the second half of the month.

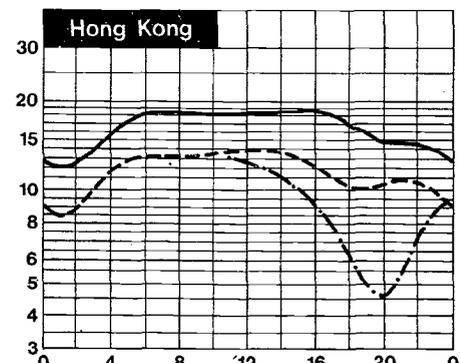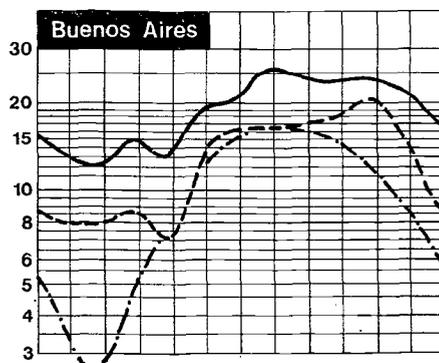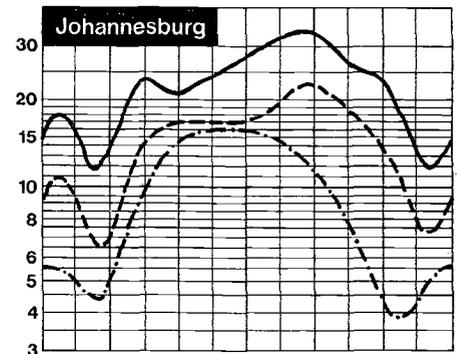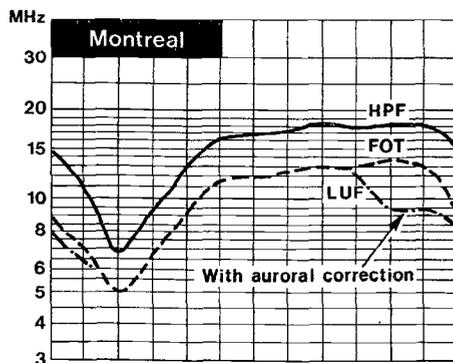Sporadic E propagation is forecast on at least 20% of the days and should modify the FOT curves as follows: Hong Kong peaking to 21MHz at 10 GMT; Johannesburg rising to 22MHz at 09 GMT and remaining so until 15GMT; Montreal maintaining 10MHz from 23 through 08 GMT; Buenos Aires dip between 06 and 10 GMT smoothed out.



Time scale on right is 2-hour divisions GMT, midnight to midnight.

# Logic design — 4

## Causes of malfunction in event-driven circuits

by B. Holdsworth\* and D. Zissost†

\*Chelsea College, University of London †Department of Computing Science, University of Calgary, Canada.

In the last article, the procedure needed for the design of event-driven logic circuits was discussed. This second half of that article goes on to describe the causes of misoperation in such circuits and concludes with some examples of design. It is unfortunate that some of the diagrams concerned with this half of the article appeared in the first half — for this, we apologise.

**Races between primary signals.** The circuit shown in Fig. 11 is required to operate three lamps  $L_1$ ,  $L_2$ , and  $L_3$ , according to the following specifications.

(1) Lamp  $L_1$  is to turn-on when both X and Y are operated, but only if switch X is operated before switch Y.

(2) Lamp  $L_2$  is to turn-on when both input switches are operated simultaneously.

(3) Lamp  $L_3$  is to turn-on when both X and Y are operated, but only if switch Y is operated first.

In practice, a logic circuit responds with different speeds to changes in the input signals. Hence the response time of the circuit to a change in the input signal X must be assumed to be different from the response time to a change in Y. As a consequence the circuit, instead of assuming state  $S_3$  on leaving state  $S_0$ , either assumes state  $S_2$ , if the circuit responds to the change in X first, or alternatively it enters state  $S_5$ , if the circuit responds to a change in Y first. In both cases the circuit operation is not according to specification.

Since there is no remedy to this problem the circuit constraint applied is that only one input signal is allowed to change at a time.

**Races between secondary signals.** In the internal state diagram shown in Fig. 12(a), the coding of the internal states is such that circuit transitions  $S_0$  to  $S_1$  and  $S_2$  to  $S_3$  involve the change of more than one secondary signal. In practice because of variations in the response times of the two secondary signals to a change in the input signal X from 0 to 1, either A or B will change first.

Assuming that A changes first the circuit, when it leaves  $S_0$ , first enters  $S_2$ ,

From state  $S_2$ , because  $X=1$ , the circuit assumes state  $S_3$  instead of  $S_1$ , and this a stable state for  $X=1$ . This is clearly incorrect operation of the circuit. Obviously a similar analysis of the circuit operation can be performed for the case when B changes faster than A.

The solution to this problem is to ensure that each circuit transition involves the change of one secondary signal only and a race-free assignment of the state variables should be used as described earlier in this article and as shown in Fig. 12(b).

**Races between primary and secondary signals.** A circuit implementation of Fig. 12(b) is shown in block schematic form in Fig. 13. The letters a and b are

assigned to the two sections of the circuit which generate the secondary signals A and B.

Consider the transition from  $S_0$  to  $S_1$  in Fig. 12(b). This transition will take place in the time  $t_s$ , which it takes to turn-on the secondary signal B. It will also be assumed that the time taken to invert the primary signal X is  $t_p$ . If  $t_p > t_s$  the following sequence of events will take place.

(1) At time  $t_s$ , B changes to 1 and the circuit assumes state  $S_1$ .

(2) Since  $t_p > t_s$ ,  $\bar{X}=1$ , and the condition for turning A on exists.

(3) A turns on causing the circuit to move to state  $S_2$ .

(4) On assuming state  $S_2$ , the circuit

Fig. 11. Three-lamp circuit and its state diagram.

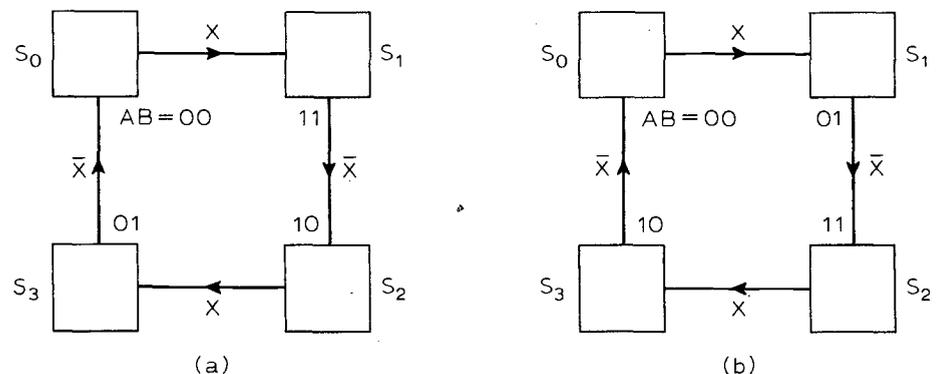
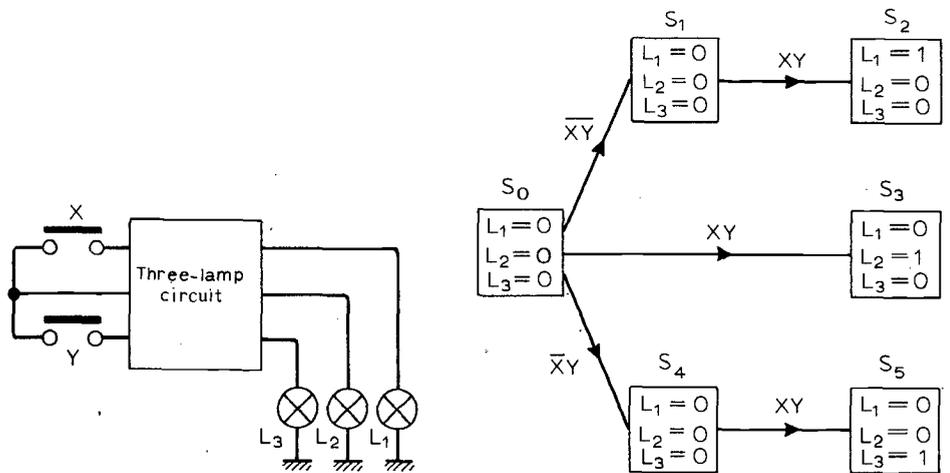


Fig. 12. Elimination of races between secondary signals.

moves to state  $S_3$ , since  $X=1$ .

If  $t_p < t_s$  on assuming state  $S_1$  the input signal to section a has already changed, i.e.  $\bar{X}=0$ , and the circuit remains in state  $S_1$ .

Unlike the previous two cases, elimination of races between primary and secondary signals cannot be achieved, since a change in a primary signal initiates a change in a secondary signal. Therefore to avoid circuit misoperation it is necessary to ensure that  $t_p \leq t_s$ . It follows that incorrect circuit behaviour will not occur if the maximum delay associated with a primary signal  $t_{pmax}$ , is less than the minimum delay associated with a secondary signal  $t_{smin}$ . Hence

$$\frac{t_{pmax}}{t_{smin}} \leq 1$$

**The 33 1/3% property**

The sequential circuits designed with the aid of the sequential equations are hazard-free when implemented with gates whose maximum speed tolerance is  $\pm 33\frac{1}{3}\%$ . The justification for this statement is as follows.

The maximum delay by which a primary signal in primitive sequential circuits can be delayed is one gate delay,  $t_g$ , when it has to be inverted. Allowing

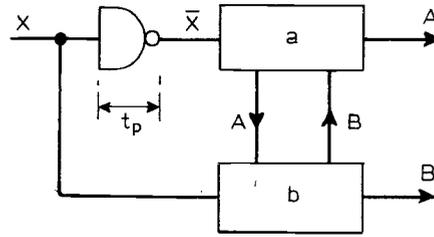


Fig. 13. Races between primary and secondary signals.

$x\%$  variation due to production spread, loading etc.  $t_{pmax} = t_g(1+x)$ .

The minimum delay associated with a secondary signal is  $2t_g$ , since at least two levels of switching are involved, as an examination of the NAND sequential equation  $Q = S + \bar{R}Q$  will show. Allowing  $x\%$  variation,  $t_{smin} = 2t_g(1-x)$ .

Substituting these values in the equation developed in the last section gives  $t_g(1+x)/2t_g(1-x) \leq 1$  for correct circuit behaviour. The reader should observe that this property is valid for

Fig. 14. Function to be realized in (a) and its state diagram is at (b), while the state table is shown in (c) and in merged form at (d). Initial state diagram based on (d) is shown at (e), and realization of the circuit is (f). Output of r.h. circuit is a.

circuits in which the sequential equations are implemented in their primitive form. Algebraic manipulation of the sequential equations will lead to a modification of the relative delays of the primary and secondary signals and therefore invalidate the 33 1/3% property. Hence, processing of the sequential equations is not advised.



**Design steps**

**Step 1.** Draw a block diagram showing the available input signals and the required output signals.

**Step 2.** Draw a state diagram describing the internal performance of the circuit.

**Step 3.** This step is optional and can be omitted. Its purpose is to provide the designer with a means of reducing the number of internal states obtained in Step 2, if such a reduction is possible or desirable.

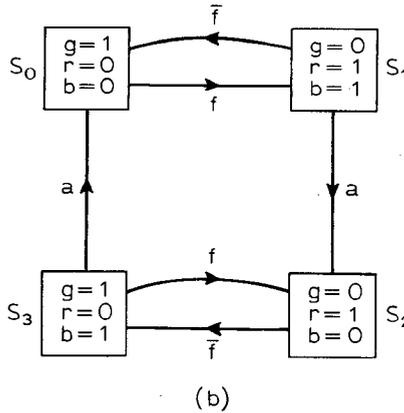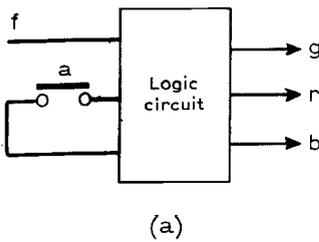**Step 4.** With the aid of a race-free diagram if necessary, each internal state is given a unique code. From the coded state diagram the turn-on and turn-off sets for the secondary signals are obtained and these are used to derive the primitive sequential equations. Expressions are also obtained for the output signals. The implementation of these equations is the required circuit.




|                |  |                                      |                                      |                          |
|----------------|--|--------------------------------------|--------------------------------------|--------------------------|
|                | 00   | 01                                   | 11                                   | 10                       |
| S <sub>0</sub> | (S <sub>0</sub> )<br>g=1 r=0<br>b=0<br>100 | (S <sub>0</sub> )<br>100             | ∅ <sub>1</sub> S <sub>2</sub><br>010 | S <sub>1</sub><br>011    |
| S <sub>1</sub> | S <sub>0</sub><br>100                      | S <sub>0</sub><br>100                | S <sub>2</sub><br>010                | (S <sub>1</sub> )<br>011 |
| S <sub>2</sub> | S <sub>3</sub><br>101                      | ∅ <sub>3</sub> S <sub>0</sub><br>100 | (S <sub>2</sub> )<br>010             | (S <sub>2</sub> )<br>010 |
| S <sub>3</sub> | (S <sub>3</sub> )<br>101                   | S <sub>0</sub><br>100                | S <sub>2</sub><br>010                | S <sub>2</sub><br>010    |



(c)

|                 |   |                           |                           |                           |
|-----------------|---|---------------------------|---------------------------|---------------------------|
|                 | 00  | 01                        | 11                        | 10                        |
| S <sub>01</sub> | (S <sub>01</sub> )<br>g=1 r=0<br>b=0<br>100 | (S <sub>01</sub> )<br>100 | S <sub>23</sub><br>010    | (S <sub>01</sub> )<br>011 |
| S <sub>23</sub> | (S <sub>23</sub> )<br>101                   | S <sub>01</sub><br>100    | (S <sub>23</sub> )<br>010 | (S <sub>23</sub> )<br>010 |


(d)

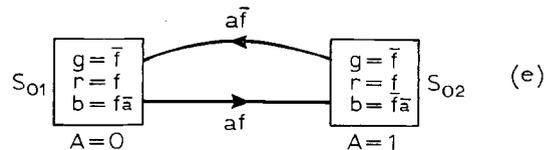


(e)

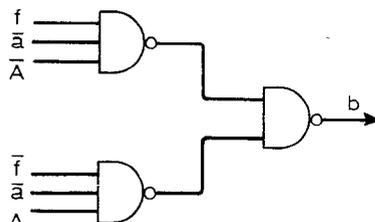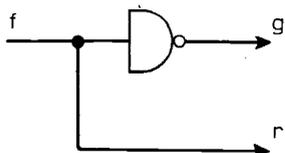

(f)

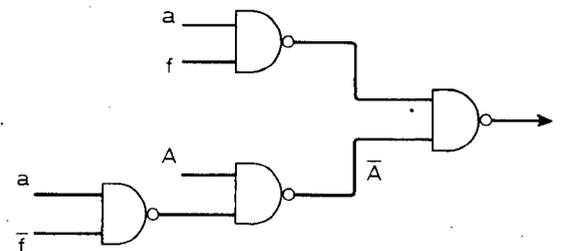

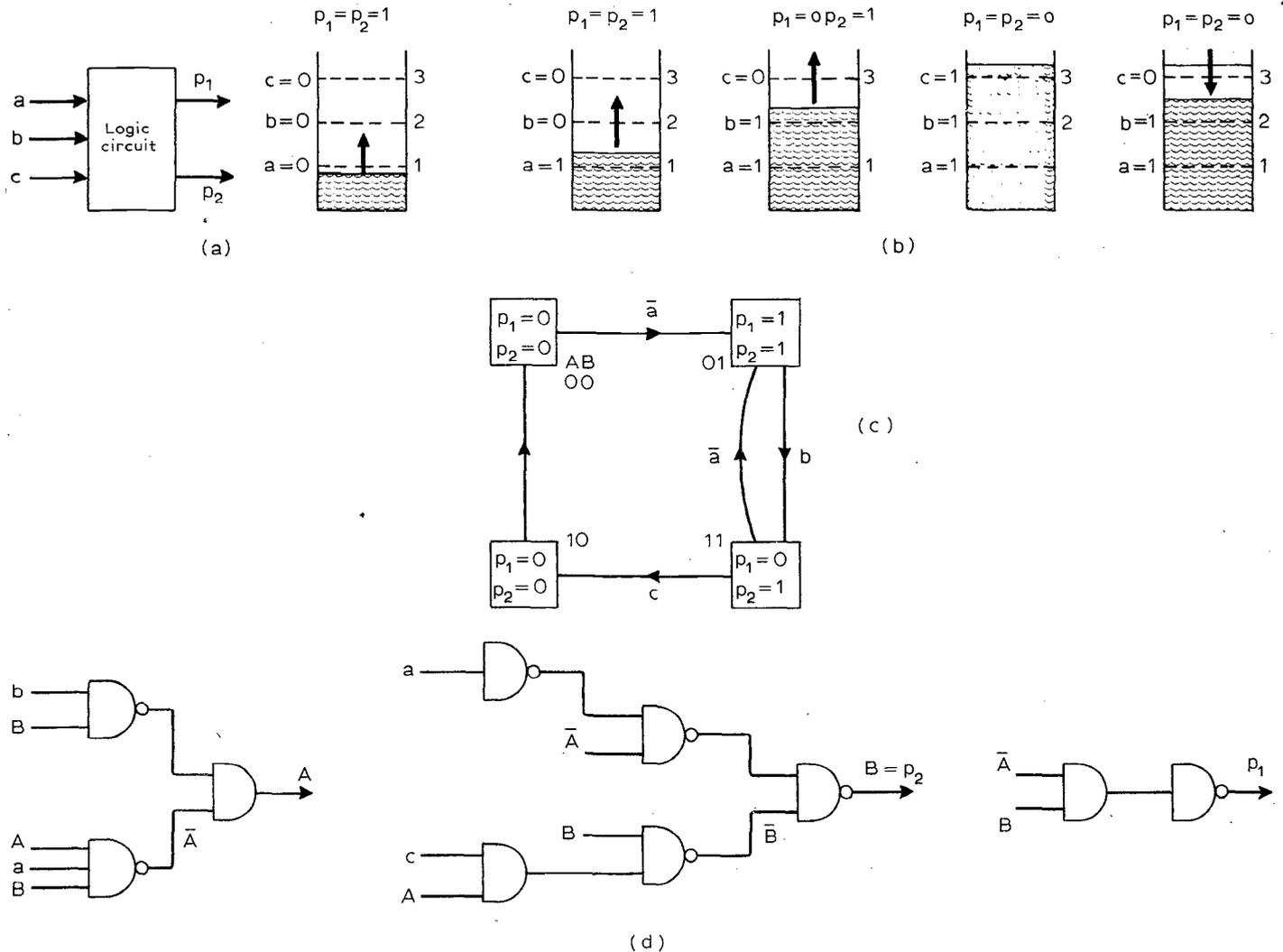

The design procedure will now be applied to the solution of two problems.

**Example 1**

Design a fault detector with the following terminal characteristics. The appearance of a fault signal *f* activates an alarm bell, turns a green light off and a red light on. The operator turns off the bell by pressing an acknowledge button *a*. When the fault is cleared, the red light turns off, the green light turns on and the bell is reactivated to attract the operator's attention. The bell is turned off when the operator presses the acknowledge button. Should the fault clear before the operator has responded, the circuit is to reset. Also if a fault reappears before the operator has responded the green light turns off, the red light turns on and the bell turns off.

**Step 1.** See Figs. 15(a) and (b)

**Step 2.** A suitable state diagram is shown in Fig. 15(c).

**Step 3.** The state table corresponding to Fig. 14(b) is shown in Fig. 14(c). Applying Caldwell's merging rules to the state table in Fig. 14(c), states *S*<sub>0</sub> and *S*<sub>1</sub> can be merged to form state *S*<sub>01</sub> and states *S*<sub>2</sub> and *S*<sub>3</sub> can be merged to form state *S*<sub>23</sub>. The reduced state table is shown in Fig. 14(d).

The internal state diagram based on the reduced state table is shown in Fig. 14(e).

**Step 4.** By direct reference to Fig. 14(e)

Fig. 15. Function required by Example 2 is seen in (a) and (b). State diagram in (c) provides turn-on and turn-off sets for use in NAND realization. Circuit is shown in (d).

the turn-on and turn-off sets are: Turn-on set of *A* = *a**f*. Turn-off set of *A* = *a* $\bar{f}$ . Therefore the NAND circuit equation for *A* is

$$A = af + Aa\bar{f}$$

$$A = af + A(\bar{a} + f)$$

$$g = \bar{f}$$

$$r = f$$

$$b = f\bar{A}\bar{a} + \bar{f}A\bar{a}$$

The corresponding circuit is shown in Fig. 14(f).

**Example 2**

Water is pumped into a water tower by two pumps *p*<sub>1</sub> and *p*<sub>2</sub>, where *p*<sub>1</sub> is an auxiliary pump used for boosting purposes. Both pumps are to turn on when the water goes below level 1 and are to remain on until the water reaches level 2, when pump *p*<sub>1</sub> turns off and remains off until the water is below level 1 again. Pump *p*<sub>2</sub> remains on until level 3 is reached when it also turns off and remains off until the water falls below level 1 again.

Level sensors are used to provide level detection signals as follows: Signal *a* = 1 when the water is at or

above level 1, otherwise *a* = 0. Signal *b* = 1 when the water is at or above level 2, otherwise *b* = 0. Signal *c* = 1 when the water is at or above level 3, otherwise *c* = 0.

Develop a sequential logic circuit to control the pumps *p*<sub>1</sub> and *p*<sub>2</sub> according to the specification given above.

**Step 1.** See Figs. 15(a) and (b)

**Step 2.** A suitable state diagram is shown in Fig. 15(c).

**Step 3.** It is left as an exercise for the reader to draw the state table and examine the possibility of state reduction.

**Step 4.** By direct reference to Fig. 15(c) the turn-on and turn-off sets are:

$$\text{Turn-on set of } A = bB$$

$$\text{Turn-off set of } A = \bar{B} + \bar{a}$$

$$= \bar{B} + \bar{a}$$

$$\text{Turn-on set of } B = \bar{a}\bar{A}$$

$$\text{Turn-off set of } B = cA$$

Therefore the NAND circuit equations are:

$$A = bB + A(\bar{B} + \bar{a})$$

$$= bB + A\bar{a}\bar{B}$$

$$B = \bar{a}\bar{A} + (c + \bar{A})B$$

$$p_1 = \bar{A}B$$

$$p_2 = \bar{A}B + AB$$

$$= B$$

The corresponding circuit is shown in Fig. 15(d).

Article 5 of the series will be a discussion of clock-driven circuits.

# Viewdata

## 4 — The Viewdata terminal in more detail

by S. Fedida, B.Sc.(Eng.), M.Sc., F.I.E.E., A.C.G.I., *Post Office Research Centre*

A Viewdata decoder may be considered as being made up of six parts, as shown from left to right in Fig 1(a): a line isolation unit; a modem; a keypad; an input processor; a store (possibly r.a.m.); and an output processor. Indeed the breakdown of facilities is very similar to that of teletext, shown in Fig. 1(b). This diagram also indicates that, apart from additional minor interconnections, parts common to Viewdata and teletext are the store and output processor. These are substantial components and therefore combined Viewdata/teletext receivers show important savings over two separate decoders for the two services. This is a slightly over-simplified picture but the situation will be clarified later.

Note however, an important difference. The input circuits in Viewdata, up to and including the store are bi-directional, thus highlighting the interactive nature of the system. On teletext the input circuits are one way only.

### Line transmission

The transmission code used over the telephone line between the Viewdata terminal and the computer is at present 8-bit, 10-unit asynchronous (or start stop), as shown in Fig. 2. Each character

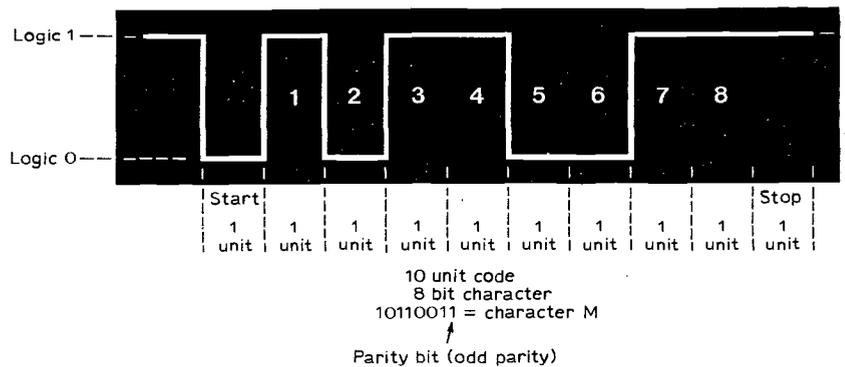



Fig. 2. Transmission code used between a Viewdata terminal and the computer is an 8-bit, 10-unit asynchronous code.

consists of an 8-bit code, the first 7 bits containing the information while the 8th bit is a parity bit. Preceding each character is a start bit, with a stop bit terminating the character. The character illustrated in Fig. 2 is M, with odd parity. A 10-unit asynchronous system

was chosen for simplicity. It is clearly not as efficient as a synchronous transmission mode, in which characters follow each other without the intervention of start and stop bits, but it is simpler to implement and is currently used by many time-sharing computer systems.

In order to transmit this code over a telephone line, a modem (modulator-demodulator) is required. Essentially this device modulates the code on to a voice frequency carrier, within the speech band, thus obviating the problems encountered with very low frequency transmission over the telephone network. The modem also enables the go and return transmission to take place

Fig. 1. Comparing the main sections of (a) a Viewdata decoder with (b) those of a teletext decoder

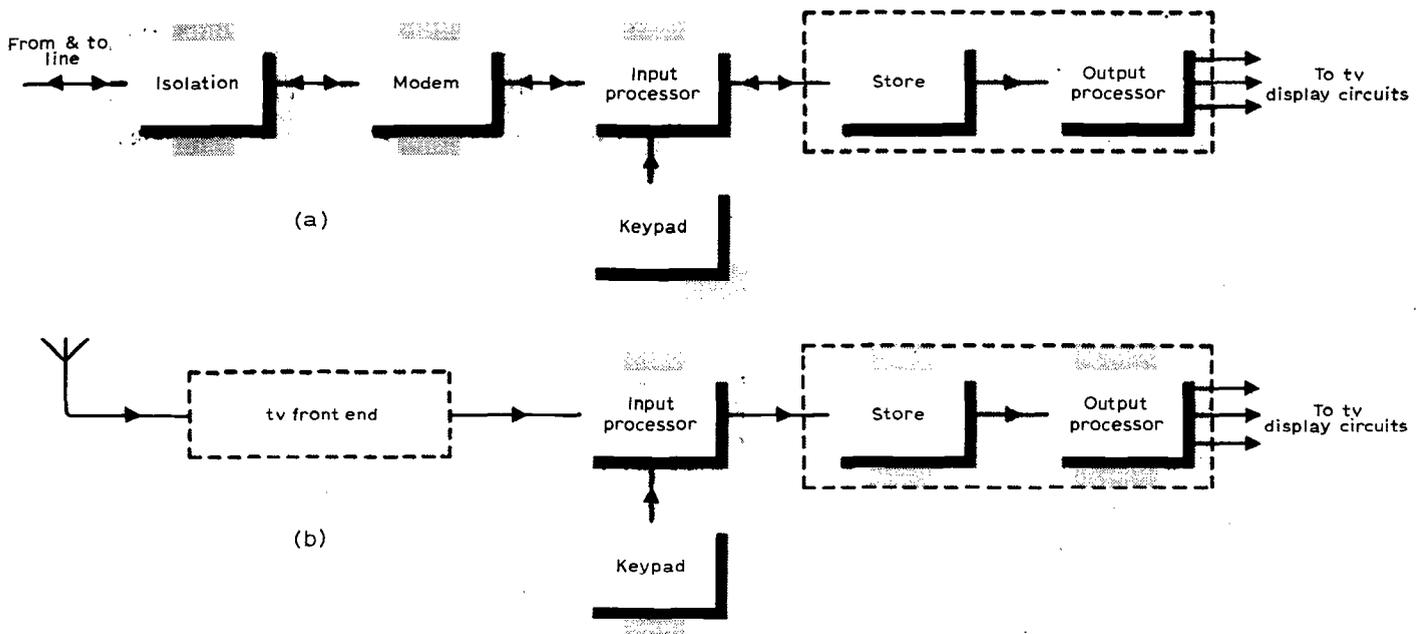

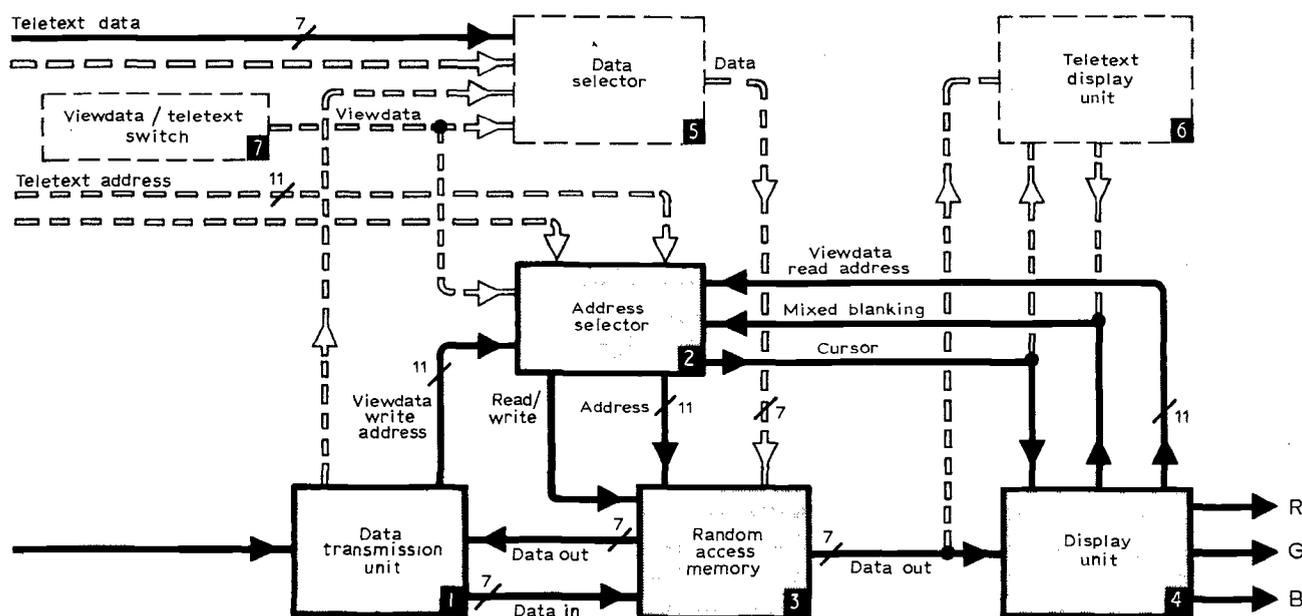


Fig. 3. Simplified block diagram of a Viewdata terminal, with adaptation to teletext shown in broken lines. The number and bar on certain connecting lines indicate that the line is carrying parallel information on that number of wires.

simultaneously over the two-wire telephone line.

Transmission rates selected for Viewdata during the present experimental phase are 1200 bits per second from computer to terminal and 75 bits per second in the reverse direction.

In the computer-to-terminal direction as high a transmission rate as possible is desirable in order to achieve a fast picture build-up. 1200 bits per second was chosen to fit in with a well tried and readily available modem. For the majority of Viewdata displays, consisting for example of mainly alphanumeric characters, the picture build-up is much faster than can be read by the user, and hence quite adequate from this point of view. Where, however, large uniform areas of graphics are displayed, the build-up may appear rather slow (the display shows repetitive information), and improvements to the build-up in this case may be obtained by using special means. But in general the additional complexity is not really worthwhile.

In the direction from terminal to computer the bit rate of 75 bits per second (7.5 characters per second) is quite adequate for hand keying.

The frequencies used in line transmission are as follows:

Forward channel: binary 1 = 390 Hz  
(from terminal to computer) binary 0 = 450 Hz

Return channel: binary 1 = 1300 Hz  
(from computer to terminal) binary 0 = 2100 Hz

When no data transmission is taking place on the line the terminal is transmitting continuously at 390Hz and the computer at 1300Hz. These tones are used in the modems at either end of the line to provide an indication of continuity, which as we shall see below is of some importance in the operation of the whole system.

When data is being transmitted the

carrier is frequency modulated (frequency shift keying), between the binary 1 and binary 0 frequencies, the change being smoothed out to give a gradual transition between the frequencies.

The transmission arrangement used at present is duplex, with "echoing" facilities provided from the computer to the terminal. In a duplex system transmission may take place in both directions at once over the telephone with no mutual interference (hence, of course, the choice of frequencies). Characters keyed at the terminal are first transmitted by the modem to the computer and displayed only when they are "echoed" back. This arrangement gives some important advantages. First, it provides a measure of error detection, the user being aware of any corruption in transmission, errors in the computer or mis-keying errors. Secondly, duplex working also increases the user's confidence in the working of the system, as "echoed" characters provide a continuous indication that the whole system is in satisfactory order.

"Echoing" from the terminal to the computer is not necessary. A parity check is sufficient to provide for the detection of the majority of errors, the computer usually responding in these cases by requesting a repetition of the instruction. The computer also monitors continuously the terminal carrier, thus ensuring that a line break is noted as soon as it occurs. This avoids the possibility of the user being incorrectly charged for using the system after the occurrence of a line interruption.

### Experimental Viewdata terminal

The experimental Viewdata terminal at present in use is best introduced in two parts: (a) the data transmission unit, which deals with the Viewdata signal between the telephone line and the internal store, and (2) the display unit, which deals with the Viewdata signal between the store and display device (the c.r.t. of a television set). As explained earlier, much of the display part is common with teletext.

A typical arrangement of a Viewdata terminal is shown in Fig. 3. There are four major units as follows: the data transmission unit (1); the address selector (2); the random access memory (3); and the display unit (4).

The address selector (2) is the only unit which interconnects the input and output processors, essentially for the purpose of preventing mutual interference. Unlike the situation in teletext data is received at random times from the telephone line, completely unsynchronized with the operation of the display. It is therefore necessary to organise the access to the memory for reading out and display on the one hand, and writing-in incoming characters on the other hand, without cross-interference. This function is carried out by the address selector. The write address generated in the data transmission unit (1) and the read address generated in the display unit (4) are both available at the address selector.

A mixed blanking waveform, also generated in the display unit, indicates the times at which characters are required to be extracted from the memory for display purposes essentially during 40 microseconds of every line period, excluding blank lines at the top and bottom margins of the display. During these times incoming characters are made to dwell a little longer in an input character buffer in the data transmission unit and the address supplied to the memory is the read address. At other times the write address is



signal is fed out to the transmission control unit at a level of  $-6V$  for a frequency of 1300Hz (binary 1) and  $+6V$  for a frequency of 2100Hz (binary 0).

**The transmission control unit.** The transmission control unit accepts data in serial form and, using a sampling technique controlled by the clock generator, recognises the start and stop bits of each 10-bit character sequence, and stores each character in a temporary buffer. This completed, it signals the event to the timing unit, and control codes decoder, i.e. that a character has been received and is available for transfer at the input data highway in a 7-bit parallel form.

The transmission control unit also checks character parity and feeds out IPE (input parity error) to the control codes decoder if parity is found in error.

**The timing unit** provides a number of waveforms which control the storage of characters in the memory. On receipt of a "data available" signal from the transmission control unit, it transfers the intended location of the received character from memory address to memory, enables memory to accept the character, clocks memory address to the next character position and resets the transmission control unit to indicate that the character received has been accepted.

**The control codes decoder** accepts incoming characters from the input data highway, decodes the special control codes and initiates the appropriate actions as follows. The unit is "transparent" to all characters other than control codes, the former being applied direct to the memory to be stored therein.

The control codes decoder performs the following functions. On receipt of:

- (a) Non storing characters such as NUL, CR, LF, BS, FF, etc. it inhibits their storage in memory. (Write disable to timing unit.)

- (b) BS, it causes memory address to count down one character

- (c) VT, it causes memory address to count down one row.

- (d) CR, it causes memory address to be reset to character address of zero, leaving row address unchanged.

- (e) LF it causes memory address to count up one row.

- (f) FF it causes memory address to be reset to character address of zero and row address of zero. It also causes the complete content of memory to be erased by setting the code on the input data highway to "space" and entering this in the whole memory.

- (g) ESC it causes bit 7 of the received character to be changed from 1 to 0, before storage.

- (h) DC1 to DC4, it sets latches to control internal devices.

The control codes decoder, when receiving input parity error, substitutes

character 7/15 for the character received in error before it is entered in the memory. The implementation of memory and memory address may be either in the form of a random access memory or a series of shift registers. A r.a.m. appears to lend itself to a rather simpler logic circuit than a shift register memory and because of this has been assumed in the description of the terminal.

The memory address consists of characters and row counters which are controlled by the control codes decoder to indicate the address at which the next character is to be stored in the memory.

### Transmission of Viewdata signals

The transmission of Viewdata signals originates either from the keypad unit or the page transmission unit.

The keypad unit controls a keyboard connected in a cross-matrix of 5 columns and 9 rows, with a shift button, which together with the 45 keys, provide a maximum of 90 codes. The basic keypad with which most of the Viewdata facilities may be used provides only 12 codes, (0 to 9), \* and #, with additional optional codes for automatic calling.

In both cases the output of the keyboard matrix is applied to an encoder which generates codes appropriate to the keys selected, serializes the bit pattern thus obtained, adds parity, start and stop bits and applies the resulting data stream directly to the modulator, under the control of an internal timing unit which generates the appropriate clock signals. Characters fed out are not displayed on the screen until they have been "echoed" back by the computer.

The page transmission unit operates jointly with the transmission control unit and timing unit, and its operation is initiated manually by a push-button on the terminal. This causes the page transmission unit to reset memory address zero and enables transmission buffer empty (TBE) signal from the transmission control unit to start the timing unit (using the page transmission enables signal). It also inhibits the writing into memory, via write disable to timing unit.

On receipt of TBE, the timing unit generates a load signal to the transmission control unit which causes the latter to accept a character from memory, and to clock it out in serial form at 75 bits/second, complete with start, stop and parity bits, to the modulator. The timing unit also increases the memory address count by one. When a character has been discharged from the transmission control unit, the next transmission buffer empty signal recommences the above cycle on the next character. When 960 characters have been sent out, the page transmission unit notes the fact and resets the terminal to the quiescent state.

At the beginning of a Viewdata session the computer interrogates the

built-in terminal identifier. The control codes decoder initiates the operation of this unit, which sends out an identification code to the transmission control unit. This code is transmitted to the modulator, complete with start, stop and parity bits. The operation is similar to that of the page transmission unit except that the identification code is stored in the terminal identifier.

### Display unit

The display unit is shown in more detail in Fig 5. The function of the display unit is to generate line and frame synchronising signal for the television raster, to decode the special display control characters for colour and graphics and to generate alphanumeric and graphic symbols for display.

As mentioned earlier, the display unit is nearly identical to the corresponding part in the teletext decoder. The major differences are in the line and frame synchronising generators and in the provision for the cursor, which is not required in teletext. With respect to the line and frame synchronising pulses, these are essential in a Viewdata-only receiver since it is required that the Viewdata service should be available at all times and not just during tv broadcasting hours; thus it is not always possible to rely on the presence of tv line and frame sync to maintain the raster. The provision of line and frame sync pulses is also very useful in a combined Viewdata/teletext decoder, as indeed in a teletext-only decoder, since it is provided in teletext that viewers should be able to store a page of information transmitted during tv broadcasting hours and to view it later at their convenience, possible outside broadcasting hours.

The display unit consists of a sync generator and memory scanner (1), a display control codes decoder (2), an alphanumeric character generator (3), a graphics generator (4), a character rounding unit (5), and an output unit (6).

The sync generator and memory scanner generates line and frame synchronising pulses which are applied to the tv timebase generators, and row and character addresses which are applied to the r.a.m. via the address selector. The unit derives these waveforms from an 8MHz crystal controlled master oscillator followed by a chain of dividers. The extraction of characters from the memory and their display on the screen occurs at a rate of 1MHz, which is derived directly from the 8MHz clock by a divide-by-8 circuit, a further division by 64 providing the line synchronizing pulses. There is a certain amount of flexibility in the choice of master oscillator frequency; a lower frequency, say 7MHz or 6MHz, giving a wider character on the display, while not being quite so demanding on the width of the video passband. The width of individual characters may also be altered by adjusting the blank margins

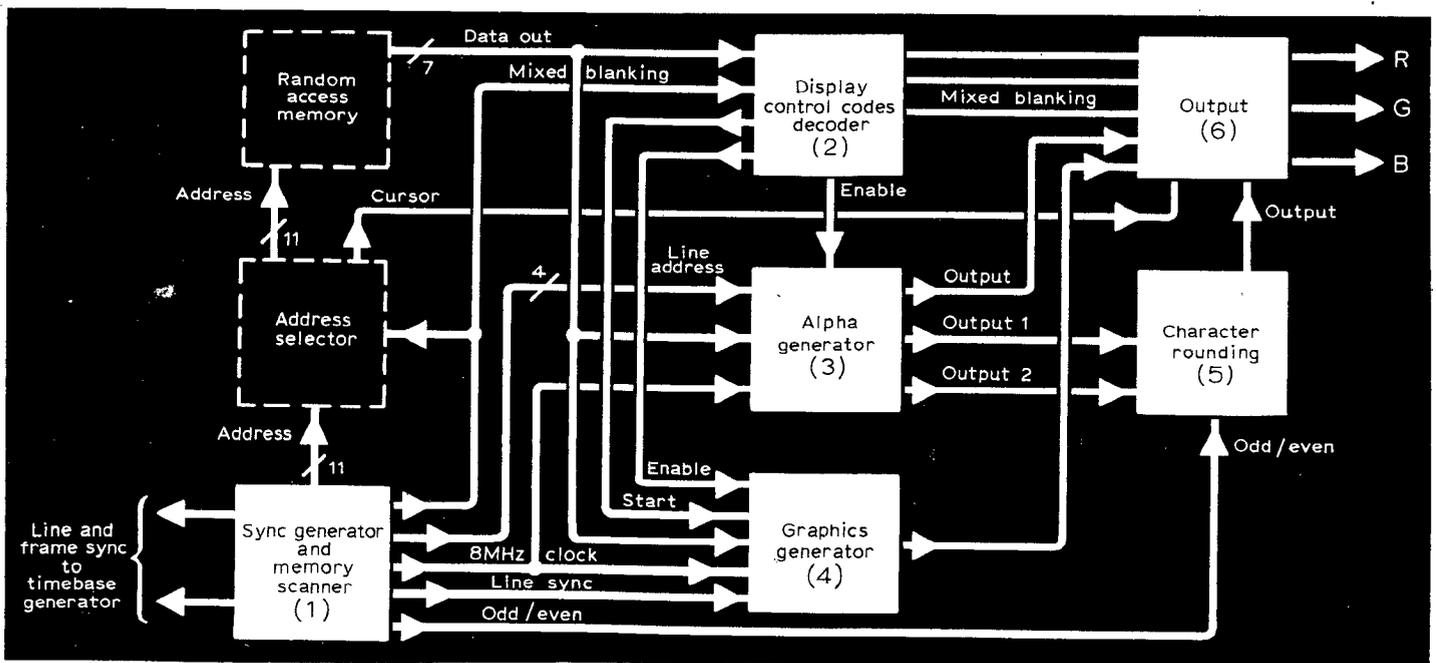


Fig. 5. Display unit at Viewdata terminal. The number and bar on certain connecting lines indicate that the line is carrying parallel information on that number of wires. Some commercial Viewdata tv receivers may have clock frequencies other than 8 MHz.

to the left and right of the page on display. The choice of 8MHz here is mainly of convenience to simplify the subsequent dividing circuits. The sync generator and memory scanner must also generate the mixed blanking waveform which provides the margins around the display area. Thus every  $1\mu\text{s}$  a read signal is applied to the r.a.m. which then feeds out the character stored at the location indicated by the row and character addresses generated by the unit.

The timing of the whole display unit must take into account delays occurring in the r.a.m. and in the alphanumeric character generators. These delays may be each of the order of 200 to 600 nanoseconds, depending on cost, the faster unit obviously being more expensive. Thus in order to take up these tolerances and allow the cheaper units to be used, a  $2\mu\text{s}$  delay is allowed for from the instant a character is requested from memory to the time it is displayed.

As in teletext, a row of characters consists of 10 television lines in each frame (20 lines counting the interlace), made up of 7 display lines and 3 spacing lines, each character space in the horizontal direction consisting of 8 dots, 5 display dots and 3 space dots, the dots occurring at the 8MHz rate.

As each character is fed out from the memory it is transferred to the display control codes decoder which is programmed to recognise the characters in columns 0 and 1 of Fig 7 in the April issue, i.e. the special colour, graphics and other display control characters; provide blanking for the duration of these characters (since these are non-display characters); and inhibit the character generator or graphics generators as appropriate.

At the beginning of every row of characters all the latches are set to white, alphanumeric, steady according to the teletext convention. The output

of the decoder is applied to the output unit which provides R, G, B signals to the guns of the cathode-ray tube.

Non-control codes are applied to the alphanumeric character generator which generates the required character pattern. This generator also receives a 4-bit line address from the sync generator, which indicates which line out of the ten lines required for character display has been selected at any one time. When a line of dots is fed out from the character generator it is entered in 5-bit parallel form in a 5-stage shift register and clocked out in the next  $1\mu\text{s}$  period at the 8MHz rate, under the control of the 8MHz clock.

If a graphics control character is displayed, a latch is set in the display control codes decoder to indicate that all subsequent characters are graphics. The inhibition is lifted, however, in the case of the "blast-through" characters in columns 4 and 5 of Fig. 6 in the April issue.

Generation of graphic symbols is carried out under the control of vertical and horizontal bright-up waveforms, generated in the graphics generator. The horizontal bright-up waveform picks up left, right or both columns of the graphics symbol while the vertical bright-up waveform picks up one or more of the top, middle or bottom pair of squares in the graphics symbols. The 7-bit graphic character is decoded with the aid of these two waveforms and control signals applied to the output unit.

The display of the Viewdata cursor is initiated by the address selector, which notes the coincidence of input and output memory addresses and enables an exclusive-OR gate in the output unit. This causes normal display of characters when the cursor is off, but inverted display (i.e. black on white) when the cursor is on. Thus characters on display may be read through the cursor.

Character rounding is provided in the character rounding unit when this feature is required, i.e. mostly with large screen displays. Character rounding is initiated by the odd/even signal generated together with the line interlace pulse in the sync generator unit. A second alphanumeric character generator unit similar to unit (3) may be required, both units operating simultaneously out of step by one line of the  $7 \times 5$  character matrix. The two outputs, one delayed with respect to the other, are compared in the character rounding unit and additional dot pulses generated half way in the 8MHz dot interval and transmitted to the output unit to give the required result.

The use of character rounding is not necessary in the case of the small-size Viewdataphone display for use in the office, and this results in a useful simplification.

(To be continued)

A limited number of commercial television sets containing Viewdata/teletext decoders are now being manufactured for marketing trials of Viewdata due to start in March 1978. In a later issue we hope to publish an article outlining the main features of a typical commercial set of this kind.

# Letters to the Editor

---



---

## MOBILE RADIO PLANNING

---



---

Recent editorials in your journal have complained about the secrecy surrounding the planning of mobile radio in the UK and have also referred to a document on the subject, which has been given a limited circulation by the Pye company. Unfortunately, the Pye document, which is issued in two versions, is not available to the generality of your readers so it does not contribute greatly to the ventilation of the subject which you rightly judge to be desirable. I am one of the small number of people who have been privileged to see both the government and commercial documents and my views may therefore be of interest. I trust I am not giving away state secrets when I say I find the overall picture confused.

You have expressed concern about the issues involved, particularly in relation to the forthcoming World Administrative Radio Conference to be held in Geneva in 1979. This conference may however be of less importance in the matter than you anticipate, for two reasons. First, the ability of the UK delegation to influence the international decisions affecting mobile radio must be necessarily limited. Second, many of the important decisions which have to be taken about mobile radio (like shall we have a Citizens' Band) are national ones and can be taken now before the WARC or after it. I trust that the *Wireless World's* interest in the subject is a lasting one and not tied to the WARC, which may possibly turn out to be something of a non-event as far as mobile radio is concerned.

As an example of a national decision, one of the most rewarding steps that can be taken to make more channels available for mobile radio is to split the u.h.f. channels from 25 kHz to 12.5 kHz. This would provide hundreds of additional channels and it is a step which can be initiated immediately. The Pye report in its full version agrees that this can be done and suggests a date for its introduction (1978), yet surprisingly this proposal is omitted from the later and shortened version. Splitting the u.h.f. channels was shown to be eminently practical no less than seven years ago by I.T.T. and one wonders why, if channels are really short, this proposal has been kept so long on the back-burner. In the meantime, the more 25 kHz u.h.f. equipment which continues to go into the field, the longer it will be before the channel splitting dividend can be reaped.

A puzzling feature which emerges from the current reviews is that mobile radio in the UK seems to make very poor utilisation of the spectrum available to it. A total of approximately 1,000 channels accommodates some 200,000 equipments, an average of only 200 mobiles per channel spread over the entire country. There are some 20 populous centres in the UK where each frequency can be repeated and this suggests an average of 10 mobiles per centre, ignoring all rural development which in itself cannot be negligible. The populous south east of England only accounts for about one fifth of the vehicle population so it is difficult to see that average channel loading can be very heavy even there. I am told that if you listen on many of the channels, which you are not supposed to do (more secrecy), message traffic is surprisingly light even in the London area.

A further point of concern is that other countries, notably the USA, Germany, Sweden and Denmark, seem to have been able to equip a much higher percentage of their vehicles within their existing frequency allocations. I believe a main factor in this has been better channel sharing arrangements and I have been long of the opinion that the UK channel sharing arrangements are unsatisfactory, discourage investment and are badly in need of review.

I have no doubt that mobile radio in the UK should be allocated more frequency space but it must be remembered that any such additional space must be taken from other important spectrum users. These users will certainly resist badly made claims. The present situation in which the long established mobile radio consultative machinery has failed to produce a unanimous report and a leading manufacturer is disputing the ministry viewpoint is a disturbing one and cannot strengthen any claims being made for more mobile radio frequency space. The frequency spectrum is one of our greatest national assets and claims for revised shares in it should be well made and be seen to be well made.

You have rightly sensed a serious failure and your journal's continuing interest in the matter can, I believe, only be beneficial.

J. R. Brinkley,  
Redifon Ltd,  
London, SW18.

---



---

## DO-IT-YOURSELF BIOFEEDBACK

---



---

A number of articles published in the technical press in recent years give popular accounts of biofeedback, together with details of the instrumentation required to "do it yourself". I write to draw attention to two aspects of this which are disquieting to the professional biomedical scientist.

The first is the impression of technological simplicity that is often conveyed. Probably the simplest demonstration of biofeedback is to convert the electrical activity of the muscles - the electromyogram - into sound using an audio amplifier, or a visual display via an oscilloscope, and hear or see what happens when a muscle is tensed or relaxed. The arm muscles are convenient and all that is required is to (a) clean and abrade the skin overlying a muscle in two places, (b) fix small metal plates to these areas with surgical plaster and a conducting interface, e.g. cotton wool soaked in salt solution, and (c) connect these "electrodes" to the display

system via a differential amplifier. The overall gain of the system should be sufficient to cope with millivolt signals. This procedure would not meet the professional standards of the clinical neurophysiologist, but would certainly demonstrate biofeedback and help one to learn to relax muscles.

Other physiological variables are not so easy to use in the feedback situation, however. Most publicity has probably been given to the electrical activity of the brain, the electroencephalogram, or e.e.g. and particularly that part of it in the 8 to 14 Hz frequency band, the alpha rhythm. Here the technological requirements are much more stringent and it is exceedingly difficult for even the professional electroencephalographer to record his own e.e.g. There are two reasons for this. One is that the signals are very much smaller in amplitude, of the order of tens of microvolts, and so require higher gain amplifiers and more careful attention to common mode rejection. The second reason is that the electrodes will detect other signals as well as the e.e.g. These will be physiological from the muscles, skin and other tissues around the head, and also physical from electrodes, interference fields, and mechanical displacement of electrode relative to skin surface. All of these artefacts can quite easily be larger in amplitude than the e.e.g., and will certainly have components in the same frequency range. In the biofeedback situation it is usual to filter the e.e.g. with a bandpass filter to reject all but the alpha rhythm, or other frequencies of interest. It is therefore impossible to tell whether the output signal is in fact e.e.g. or artefact without considerable experience of e.e.g. recording.

The professional e.e.g. technician spends several years learning to record these signals, to differentiate true e.e.g. signals from artefacts, and to improve technique to reduce these artefacts to a minimum.<sup>1</sup> Appropriate application of electrodes to one's own scalp is very difficult indeed.

The second area of disquiet concerns the interpretations of the subjective effects of biofeedback, particularly the so called "alpha experience". It is generally assumed in popular articles that learning to enhance alpha activity via biofeedback invariably results in a state of mind associated with tranquility, relaxation, meditation states, and generally pleasant feelings. Experiments which have attempted to control for the effect of feedback on these factors have not always confirmed these claims however. Thus Sacks et al<sup>2</sup> used well established methods for measuring subjects' feeling and mental states and found no difference when subjects enhanced their alpha to maintain a light on or inhibited it to maintain the light off. In a study of 140 subjects by Travis et al<sup>3</sup>, "under both eyes-open and eyes-closed conditions, approximately 50 per cent of the subjects reported that alpha enhancement was 'pleasant' and 50 per cent 'unpleasant/neutral'". Plotkin and Cohen<sup>4</sup> concluded from their experiments that "... undirected, free-flowing thought or thoughtlessness, and pleasant emotional states, are in no way intrinsically associated with enhanced occipital alpha strength ...".

These are just a small selection from many research studies urging caution in the interpretation of alpha feedback results, and of course, one could quote an equal number putting a more optimistic point of view. The popular interpretation of the "alpha experience" is by no means established however.

There is no doubt that biofeedback is an exciting and valuable research tool. Whether it will be clinically useful is still to be proved<sup>5</sup>.

The laboratory situation of "do it yourself" enthusiasm which accompanies it may indeed result in subjective feelings of relaxation or other pleasant sensations. It does not necessarily follow that these are directly due to subjective control over brain mechanisms. After all, as Lynch and Paskewitz have pointed out<sup>6</sup> "Simple physical manoeuvres like closing or opening the eyes have not been related to mood changes of the sort reported in feedback situations and yet such eye manoeuvres markedly affect alpha density."

J. C. Shaw,  
MRC Clinical Psychiatry Unit,  
Graylingwell Hospital,  
Chichester, Sussex.

**References**

1. Cooper, R., Osselton, J.W. and Shaw, J.C. "EEG Technology", second edition, Butterworth, London, 1974.
2. Sacks, B., Fenwick, P. B. C., Marks, I., Fenton, G. W., and Hebden, A. An investigation of the phenomenon of autocontrol of the alpha rhythm and possible associated feeling states using visual feedback. *Electroencephalography and Clinical Neurophysiology*, 32, 461, 1972.
3. Travis, T. A., Kondo, C. Y. and Knott, J. R. Subjective aspects of alpha enhancement. *British Journal of Psychiatry*, 127, 122-6, 1975.
4. Plotkin, W. W., and Cohen, R. Occipital alpha and the attributes of the "alpha experience". *Psychophysiology*, 13, 16-21, 1976.
5. Blanchard, E. B. and Young, L. D. Self-control of cardiac functioning: a promise as yet unfulfilled. *Psychological Bulletin*, 79, 145-163, 1973.
6. Lynch, J. J. and Paskewitz, D. A. On the mechanisms of the feedback control of human brain wave activity. *The Journal of Nervous and Mental Disease*, 153, 205-217, 1971.

## DIGITAL FILTERS USING MICROPROCESSORS

I am very grateful to Mr V. J. Rees for giving the extra bit of explanation I needed to understand digital filter principles (October 1976 issue). And in spite of the possible shortcoming of the article, I think that the criticisms of M. J. Brazier (December 1976 letters) are unjustified.

Firstly, even if it is obviously impossible to "operate the filter in real time" on a calculator, it is very instructive to do so for a student and very informative for a designer.

Secondly, I did not have any problem in realizing from the example that the coefficients were constant unless the filter characteristics were time varying.


Thirdly, there is an improved form of the digital filter which requires only one multiplication and two subtractions. These can be performed within the suggested 100 microseconds on a Motorola 6800 in single precision (see appendix).

Finally, digital signal processing is more likely to be used in process control or similar applications where the frequencies involved are much lower. Present "slow" microprocessors will certainly be used in that area, if they are not already.

Gérald Garon,  
Otterburn Park,  
Quebec, Canada.

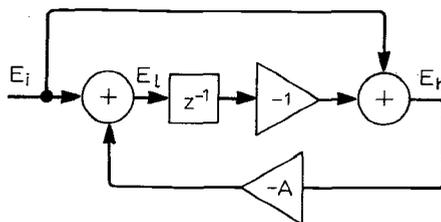**Appendix**

The improved form of digital filter is shown in the figure, and the 6800 programme to implement it is given below. The coefficient is inserted in the programme by putting NOP in the bit positions where the coefficient has



$$E_h = E_i - E_l z^{-1}$$

$$E_l = E_i - A E_h$$

- E<sub>i</sub> input signal
- E<sub>l</sub> low pass output
- E<sub>h</sub> high pass output
- A coefficient e<sup>-aT</sup>
- z<sup>-1</sup> delay T

zeros and ABA where it has ones. In the example, the coefficient is 11101100<sub>2</sub> (0.921875). The execution time of this programme is independent of the coefficient value. For any given coefficient value, it is possible to speed up the program by either omitting the NOPs or using Booth's algorithm.

**Programme**

| INSTR | CLA B              | Clear B on initial start |
|-------|--------------------|--------------------------|
| 4     | NWSMP LDA A SAMPLE | Get new sample           |
| 4     | STA A SVSMPL       | Save it                  |
| 2     | SBA                | EH = EI - EL(PREV)       |
| 5     | STA A HPOUT        | Output High Pass         |
| 2     | TAB                | Get Ready For Multiply   |
| 2     | CLA                |                          |
|       |                    | Multiply 0.15B           |
| 2     | NOP                |                          |
| 2     | ASR A              |                          |
| 2     | NOP                | 0                        |
| 2     | ASR A              |                          |
| 2     | ABA                | 1                        |
| 2     | ASR A              |                          |
| 2     | ABA                | 1                        |
| 2     | ASR A              |                          |
| 2     | NOP                | 0                        |
| 2     | ASR A              |                          |
| 2     | ABA                | 1                        |
| 2     | ASR A              |                          |
| 2     | ABA                | 1                        |
| 2     | ASR A              |                          |
| 2     | ABA                | 1                        |
| 2     | ASR A              |                          |
| 2     | NEG A              | Make Result Negative     |
| 3     | ADD A SVSMPL       | EH = EI - A. EH          |
| 5     | STA A LPOUT        | Output Low Pass          |
| 2     | TAB                | Save In B                |
| 4     | BRA NWSMP          | Go Get Next Sample       |

67 microseconds

**References and further reading**

- Gold B. & Rader C. M., "Digital Processing of Signals," McGraw-Hill, 1969.
- Mick J. R. (ed), "Digital Signal Processing Handbook," Advanced Micro Devices, 1976.

## BROADCASTS MODULATE PAGING SYSTEM

Over a period of more than a year I have heard on 27.26MHz a weak carrier which is amplitude modulated with material corresponding to that of the Radio 3 transmission on 647kHz including, prior to 0700 local time, material from the BBC World Service.

At intervals this carrier disappears for about ten seconds and it was later noticed that these interruptions coincided with

periods of calling signal and short speech announcement from a hospital paging system on 27.23MHz. A band of noise embraces this latter frequency and this too is interrupted during operation of the paging system.

During evening hours of darkness the noise band can be resolved as a large number of separate carriers, some of which are modulated with programme material which matches certain transmissions in the m.f. band around 600 kHz.

By now some of your readers will have suspected, as I do, that the receivers of the paging system are of the superregenerative type and this is borne out by quenching of the noise when the calling carrier is switched on.

What is not so clear, however, is the mechanism by which the sidebands are modulated by transmissions in the medium frequency band and it is this peculiarity that your readers may be able to suggest a reason for.

I should explain that my receiver is a double superhet with i.fs of 4.034MHz and 455kHz, but spurious operation can, I believe, be ruled out and tuned aerial traps have confirmed that the signal I receive is borne on 27MHz. It is moreover occasionally subject to aircraft flutter.

My receiver location is about 2½ miles from the hospital concerned and the signal is a weak one but in an area within a few hundred yards of the grounds it provides an almost usable relay of Radio 3.

All this may be only a minor instance of spectrum pollution but I am reminded that frequencies of the order of 27MHz are allotted to model aircraft control.

I do not think, however, that there is any likelihood of these aircraft being affected by a new-style Bermuda triangle!

Gwilym Dann,  
Chipstead,  
Surrey.

## RIAA EQUALIZATION IN PRE-AMPLIFIERS

Having just read Graham Nalty's and D. Self's arguments on disc RIAA equalization in your March issue, I would like to add a few words.

While I was living in Japan I designed an expensive pre-amplifier for a well known company which has earned good reviews everywhere. Anyway, the RIAA circuit was conventional in that the time constants were in the feedback loop. However, the problem is that at high frequencies the amplifier ultimately becomes a unity gain circuit above about 60kHz so compensation becomes a real problem; therefore in its open loop form the amplifier starts to roll off at a low of 30Hz and t.i.m. never is perfect, although in my case it was lower than that of any of its competitors.

I have for myself designed a totally passive RIAA amplifier with accurate equalization from below 10Hz up to beyond 200kHz. I had succeeded in getting as good an input over load value from 20Hz to 20kHz to compare with feedback methods.

As to listening and also square wave tests, the purely passive circuit always performed better (I always use polystyrene and polycarbonate capacitors as they are more musical!). This went through many hours of listening, with many types of cartridges, power amplifiers and loudspeakers.

I sacrifice 3dB of signal-to-noise since impedances are not perfectly optimum and distortion at 2dB below clip is only 0.03% over 20-20kHz.

But this is the way thoughts are going in Japan.

Tim de Paravicini,  
London NW6.

---

## ADVANCED PRE-AMPLIFIER DESIGN

---

In reply to Mr Williamson (Letters, April), I think there are mainly two points to be made. One, that any pre-amplifier should have adequate signal handling capacity in excess of the performance of any pickup cartridge both dynamically and in pure consideration of the amplitude of signals. Second, that as far as I am concerned the two pickup cartridges which are capable of giving peaks in excess of 200mV are the Ortofon SL15 with appropriate transformer and the Decca London cartridge.

The reference to signal peaks of 80 cm/s observed on gramophone records came from the book "Hi-Fi Systems" by G. King where there is a graph illustrating the velocities measured on gramophone records at various frequencies.

I nominate my favourite charity as the Musicians Union!

A. J. Watts.  
SGS-ATES (United Kingdom) Ltd,  
Aylesbury,  
Bucks.

---

## LONG WAVES FOR AMATEURS?

---

I am normally in favour of amateur radio but a statement in your March 1977 issue (p. 78) that the USA may request a frequency allocation in the l.f. band for amateurs fills me with anger. How can anyone be so wickedly irresponsible or unappreciative of the value of long wave channels!

Just in case the unique feature of long wave transmission has slipped anyone's mind I would point out that the long wave channels are the only ones capable of giving reliable, fade-free global communication without resorting to the use of satellites.

In my opinion it shows a serious lack of appreciation of the potentialities of these frequencies to allow anyone to use them just for low power local broadcasting, and hence it is quite wrong to allow more than one transmitter on each channel unless the carriers are synchronised and they are radiating the same programme.

H. G. May,  
Barton-on-Sea,  
Hants.

---

## AUDIBILITY OF PHASE EFFECTS

---

In view of the continuing controversy in these columns over the audibility (and hence undesirability) of non-linear-phase shifts in an audio signal — i.e., phase shifts which leave the harmonic structure unaltered but distort the signal waveform — the following

recent observations of mine may be of interest to your readers. In particular, they may enable readers who have built the *Wireless World* Dolby B noise reducer to verify some of these effects for themselves.

Having completed the noise reducer kit from Integrex Ltd., I was somewhat surprised to find that, listening to the built-in calibration signal at the monitor output (with the input selector in the auxiliary position), I could hear a subtle but distinct difference between the apparent purity of the (approximately 456Hz) tone with the record/play button in and the sound with the button out. Reference to the circuit diagram shows that the only change introduced by this switch is the insertion of a unity-gain polarity inverting stage into the output circuit. Further investigation showed that the gain of this stage was indeed unity (within 0.02dB) and its harmonic distortion very low (of the order of 0.02% t.h.d.). So it clearly was not the culprit. It was at this point that I measured the calibration oscillator t.h.d. and found that this was 2.66%, comprised of 2.57% second harmonic, 0.62% third harmonic, 0.25% fourth harmonic and approximately 0.16% higher-order harmonic distortion. The pronounced second harmonic distortion, like all even-order harmonic distortions, rendered the waveform asymmetrical; this asymmetry was sufficient to be just barely visible on an oscilloscope.

Here, then, was the explanation of the change in sound quality observed before. It is known from recent work<sup>1,2,3</sup> that the inner ear does not respond symmetrically to compression and rarefaction, and at lowish frequencies (below say 1kHz) where the rate of neuron firings can be modulated by the audio waveform, the ear performs to a certain extent at least like an asymmetrical waveform detector, responding more to one signal polarity than to the other. In this connection reference should be made to the publications cited in references<sup>1,2</sup> and<sup>3</sup>, and in particular to the work of J. H. Craig and L. A. Jeffress. By switching from "record" to "playback", and hence inverting the slightly asymmetrical calibration waveform, the fact that the ear treats compressions and rarefactions unequally resulted in an audible difference in the tonal quality. Of course, this polarity reversal of the asymmetrical signal is equivalent to a phase shift of the harmonics relative to the fundamental, and so this result has direct relevance to the current discussions on the audibility of phase distortion. The letter by M. A. Gerzon<sup>4</sup> should also be consulted for corroborative evidence.

The above explanation has subsequently been confirmed by introducing polarity reversals at other points in the reproduction chain, with the same effect. The audible effect of the polarity reversal in the Dolby noise reducer could be exactly counter-balanced by another polarity reversal later in the chain. In this way, it was possible to rule out transducer asymmetry as a contributory cause. The audibility of the polarity reversal has also been confirmed by friends on whom I have repeated the experiment.

The audibility of the polarity reversal depends to a great extent on having the volume level just right — neither too loud nor too soft. This also agreed with the earlier experiments cited. The change is audible on both headphones and loudspeakers, but for convenience the former were used primarily in my tests.

I would like to invite readers who have constructed the *Wireless World* Dolby B circuit to try this experiment themselves. Of course, I cannot vouch that the distortion of

their calibration oscillators will be the same as mine and so produce the desired asymmetry! It should be emphasized that the change is *subtle*, and some perseverance may be required in order to hear the tonal difference. (Experiment also with the volume level.) The noise reduction should be switched "off." (Switching it "on" exaggerates the difference in the right-hand channel, by pre-emphasizing the higher harmonics when in the "record" mode and de-emphasizing them when in the "playback" mode. The left-hand Dolby side-processor loop is not performing its normal function when the calibration oscillator is on, and so the left-hand channel does not display this further effect. Thus it may be found helpful initially to monitor the right-hand channel output with the noise reduction switched "on," to serve as an aid in learning what to listen for. The change under these circumstances is, however, *not* a simple polarity reversal.)

At first sight, all the above would seem to bear only on the audibility of polarity reversals of non-sinusoidal waveforms. As such, it strongly suggests that an effort should be made to standardize the polarities of the whole recording/reproduction chain from microphone, through record or tape, to loudspeaker. This suggestion has been made before, for example by D. S. Stodolsky<sup>1</sup>. It also serves as a warning to those who conduct A/B comparison tests on audio components without taking into account the possible relative polarity reversals which such components can introduce. For example, some power amplifiers are inverting from input to output, whereas others are non-inverting. Some of the alleged differences between components compared A/B may be due to such oversights.

Our observation does, however, indeed bear directly on the vexed question of the audibility of non-linear-phase shifts for the following reasons. Non-linear-phase distortion results in waveform distortion, and hence can change the symmetries of the signal waveform. As shown above, such symmetry changes can be detected by the ear, and so such phase distortion must be classed as undesirable, whatever the component is which introduces it. So, to conclude, it is my belief that phase distortion is audible under suitable circumstances, that more effort should be devoted to obtaining bounds on the allowable phase distortion on programme material (by means of properly conducted experiments with source signals which have not been phase-distorted by the audio chain), and that in principle the goal of phase-linearity (at least over the bulk of the audio band) is a desirable one which is worth pursuing, especially in transducers.

Stanley P. Lipshitz,  
University of Waterloo,  
Ontario, Canada.

### References

1. Stodolsky, D. S. "The standardization of monaural phase", *I.E.E.E. Transactions on Audio and Electroacoustics*, vol. AU-18 (1970), 288-299.
2. Hansen, V., Madsen, E. R. "On aural phase detection, Parts I and II", *J. Audio Eng. Soc.*, vol. 22 (1974), 10-14 and 783-788.
3. Schroeder, M. R. "Models of hearing," *Proc. I.E.E.E.*, vol. 63 (1975), 1332-1350.
4. Gerzon, M. A. Letter to the Editor. *Wireless World*, vol. 82, March 1976, 60-61.

Further letters on the audibility of phase effects, and also letters on transient intermodulation distortion in amplifiers, will be published in a later issue.

# News of the Month

---



---

## Annans and technology

---



---

Mobile radio should get some of the frequencies freed from 405 line tv transmissions in 1982, Professor Geoffrey Sims said at a press conference marking the publication of the Report of the Committee of enquiry into broadcasting of which he was a member. Asked what would happen to the 405 line channels and whether they would be used for citizens' band radio Professor Sims said: "I think there are certain problems about these frequencies. They are not well suited to colour television. Certain of them, band three for example, could be reserved for a colour television channel, but not all of these frequencies will be used for television services. For example they could be used for mobile radio services."

Pressed further to say why a report over 500 pages long which had been awaited eagerly as a sign of the way new techniques would affect broadcasting in the future contained only 20 pages on technology Mr Sims pointed out that there were in fact 35 pages, or two chapters on technology. "We are all aware" he said, "that we are surrounded by new forms of technology which can be deployed in broadcasting." The difficulty was that there was a shortage of money to develop these techniques, and a shortage of good material to broadcast by them. All sorts of techniques, from fibre optics to satellite transmission were available, "but the way it's done is neither here nor there provided you can afford to do it some way. Either new technology is not developed to the point where it would be sensible to create these new large networks, or there is a lack of programme material. It's all right to talk about a fourth or fifth channel but when you come to the 24th or 25th, which is what these things could provide, the whole question becomes a different matter." Citizens' band was outside the scope of the committee's remit, but "It must be introduced at frequencies which do not interfere with public broadcasting."

Professor Sims's final point on the

adoption of new technology was that the u.h.f. investment programme was still going forward. "By the early 1980s some u.h.f. transmitters will be going out of service, and some people who now get programmes won't get them unless these are replaced." Mr Phillip Whitehead, MP, a member of the committee, added that citizens' band was mentioned at the end of chapter 24. "We can't take that in this country." The kind of service that existed in the United States, on 27MHz, would cause "grave interference with services which are much more important."

The report makes scathing criticisms of the British television manufacturers, and presses for tighter control on the illegal use of c.b. equipment, including banning its sale as well as its manufacture and importation. The committee also recommends the setting up, as suggested in evidence by the National Electronics Council (see *Wireless World*, October 1975, p.447) of a telecommunications advisory committee to advise the government on the prospects for and implications of technical developments for all telecommunications, including broadcasting.

The committee over-ruled suggestions by the Newspaper Publishers Association and the Newspaper Society that teletext development should be held back for five years "to enable newspapers to adjust to the new competition." Neither need they be consulted about these developments. "We recommend that the BBC and IBA should be authorised to provide CEEFAX and ORACLE as an extension of their existing services." There should however be an enquiry by the new Public Enquiry board.

*Wireless World* will publish a full account of the less publicised aspects of the report in our next issue.

---



---

## Battery car charges while braking

---



---

The Department of Industry is funding the development of a braking system for electrically powered vehicles which will feed the energy normally lost during braking back into the battery. Although the technique adopted, using the traction motor as a dynamo during braking, is fairly well established, up to the present time, the Department say, "regenerative braking systems have required a considerable number of additional components in the control circuit and hence have been costly, have necessitated critical adjustments to provide the requisite safety margin against miscommutation (which would effectively short circuit the battery and blow the traction fuses) and were not capable of operation at low road speeds."

The solution, developed after joint funding by the DoI and Cableform Ltd,

is to use a Cableform Pulsomatic Mk 10 controller, developed for control of the acceleration of the vehicle, to control braking as well. Mr P. F. Hodges, field sales manager of Cableform, told *Wireless World*, "We started looking at this two years ago and, like everyone else, we ended up with about 250 discrete electronic components in the circuit. Then we noticed that the acceleration characteristics had so much in common with the braking characteristics that we could use the same controller for each function with only 120 components, and of course, as always happens when you reduce the number of components, the reliability shot up."

The detailed operation of the device is complicated, but in essence it overcomes the difficulty of absorbing the large amounts of energy that are generated by motors in a short time during braking. On the one hand there is a large current surge which may destroy the battery, and on the other a large voltage surge which is hostile to the semiconductor sections of the thyristor control circuit. Cableform have managed to mitigate the effects of both by feeding the energy back in smaller, more manageable quantities over a longer period. They have also overcome the reduced braking rate at lower speeds. The Department of Industry appear delighted with the device, and full of praise for Cableform.

The money, £16,500 to match Cableform's contribution, was channelled through the transport section of the Research Requirements Board. The Department of Industry sees it as its duty to put help under one of several publicised schemes into any company or organisation which comes forward with a proposal which the Department of Industry judges to be viable. That means the proposal must produce sales, and a project which represents solid judgement and good engineering will be preferred to one which, as one spokesman put it, "is a technological marvel that collects dust on someone's shelf."

One of the tasks with which the Department was charged was to look at the technical options offered by electric vehicles and the amount of energy that could be saved in using them. They came across "an ingenious way of simplifying a regenerative control". In particular, Cableform's design, described in three versions in the patent specification, eliminates the need for any tricky adjustments, according to the DoI.

---



---


## ITU conference results

---



---

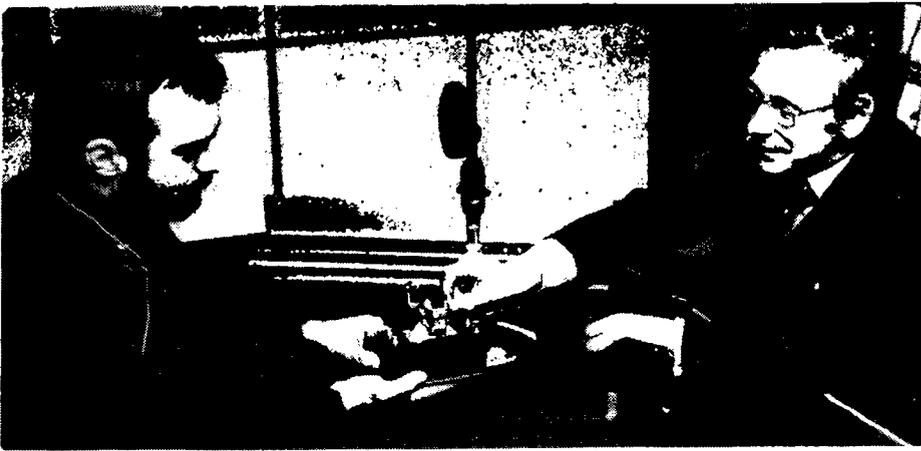The sense of accord at the ITU Broadcasting Satellite Conference, which ended in Geneva on February 13,



Johnny Longden, chief engineer of BBC Radio London (right) examines a forerunner of the audio amplifier with David Clifton, until recently presenter and producer of the station's Sounds Good programme. The valveless amplifier was originally used to drive loudspeakers from crystal circuits normally able only to power headphones. According to Longden the device, made by S. G. Brown, may have been intended for morse code rather than audio, since there was a peak of 12dB at around 1.5kHz.

Sounds Good has been running on Radio London almost since the station opened in October 1970. If the Annan Committee gets its way the BBC will lose all its local radio stations (full report next month).

was such, according to one report, that no votes were taken even on matters about which the 660 delegates from 111 countries disagreed. The amount of work done was therefore prodigious. A plan was adopted which gave every country present, with the exception of those in region 2, the Americas, frequencies and orbital positions for satellite broadcasting which will come into force on January 1, 1979. Region 1 (Europe and Africa) was given 40 channels and Region 3 (Asia and Australasia) 24. Region 3 has the frequency band from 11.7GHz to 12.2GHz, and region 1 up to 12.5GHz. The allocations are in the form of a 42-page table worked out by computer in channel order from 1 to 40. The plan is valid for 15 years. The final document produced by the conference, some 150 pages, contained 16 articles, including the plan, 11 annexes, a final protocol, nine resolutions and eight recommendations, as well as a small section relating to the rearrangement of the radio regulations, some additional regulations and a recommendation that they be published this September in good time for the 1979 WARC in Geneva, when the regulations agreed last month will form the basis for proposals to that conference.

Region 2, dominated by the United States, decided to wait for its final orbital station and frequency allocation until they hold their own regional administrative conference in 1982. Contingency plans have been made establishing a claim to orbital space, and each country in region 2 will get at least four channels at the 1982 conference.

The technical details of the plan, we believe, include the following: the

broadcast signal will be either f.m, which will predominate, or another type of modulation which has at least the same interference standards; circular polarisation; at the edge of the coverage area in regions 1 and 3 the power flux density will be  $-103\text{dBW}$ , needing a receiver with a figure of merit (defined as the aerial gain divided by the system noise temperature in degrees Kelvin) of 6dB/K and a 90cm aerial. This is the equivalent of an effective isotropic radiated power of 67 dBW at the satellite; and a nominal spacing has been set for the satellites in regions 1 & 3 of  $6^\circ \pm 0.1^\circ$  at the equatorial orbit. Narrower spacings are allowed at lower powers provided interference does not result.

The American countries are adopting slightly different standards, it is understood. Their power will be 2dBW lower at  $-105\text{dBW}$  at the edge of the coverage area, or a radiation from the satellite of 63dBW e.i.r.p, needing a 1m aerial. As a comparison, the Canadian communications satellite (see WW, March, p40) has an e.i.r.p. of 59dBW.

## IBA host EBU surround sound demonstrations

Working Party S of the European Broadcasting Union will be meeting at IBA Engineering HQ, Crawley Court, June 14-17 to investigate surround-sound broadcasting systems. The IBA will be giving demonstrations of five systems: BBC Matrix H, CBS SQ, NRDC 45J, Nippon Columbia UMX and Sansui QS. The aim is eventually to arrive at a single agreed system for the whole of Europe.

The IBA is currently exploring several surround systems, but still at a relatively early stage of its investigations and is anxious to complete them before making any formal statement of its views. "The choice of a preferred system involves questions not only of subjective performance" the IBA say "but also of the degree to which it would affect listeners relying on monophonic or two-channel stereophonic reception; whether it would significantly affect the coverage of the transmitting stations; whether it would cause, or be vulnerable to, interference to or from stations using adjacent channels and so complicate frequency planning; and of course the costs to broadcasters and listeners.

"It is also recognised that it would be highly desirable that the same system should be adopted nationally and internationally. In Europe the adoption of a particular system is primarily a question of achieving general agreement among the members of the European Broadcasting Union and ultimately the CCIR. Thus while the IBA and other members of EBU are currently investigating and making individual contributions in this field it is hoped that it will prove possible to agree on the system best suited to European broadcasting. The work in this area is being shared through Working Party S of the EBU."

During the meeting of the Working Party the IBA expects, with the co-operation of the BBC and the other broadcasters concerned, to stage a comprehensive series of demonstrations and experiments based on a number of different proposals, using different types of programme material.

"It must be stressed however that these experimental demonstrations to Working Party S cannot be expected to lead to an immediate recommendation by the EBU. It is only after consideration in detail of the technical and economic factors involved that European broadcasters are likely to be satisfied that a wise and prudent choice has been made from among the proposed systems, all of which appear to have useful features but also some ambiguities. It is interesting to note that despite the intensive work in this area since 1972 in the United States of America no final recommendation has yet been made by the Federal Communication Commission."

## High speed track measurement

As the speed of passenger rail transport increases it becomes more necessary than ever to make sure that track is fault-free. The High Speed Track Recording Coach, which has already gone into service with British Rail, uses gyroscopes, accelerometers and mini-

computers to take track measurements at speeds up to 125 m.p.h. These measurements enable two types of fault to be located; those related to passenger comfort and those related to safety. Parameters measured include vertical (top) and horizontal (alignment) rail-profiles, cross-level (cant), curvature, gauge and slope. An Interdata model 70 digital computer samples the analogue measurements and allows other parameters such as twist, to be derived. The track assessments employ calculations based on the statistical standard-deviation principle.

Data from the gyroscopes and accelerometers is processed using a Membrain digital/analogue computer, acting as an integrator, to provide a measure of the dynamic motion of the coach. This enables the main computer to distinguish between cants and curvatures due to natural slopes and corners and those due to faults.

Vertical measurements are made to within 1mm using potentiometric displacement transducers mounted above the centre of running wheels. Lateral sensing, however, is by a non-contacting optical system. Light projectors are mounted on the bogies and arranged so that a small area of each railhead is illuminated. The reflected illumination from the railheads is converted into a video waveform by linescan cameras so that the gauge face, where the illumination intensity changes rapidly, can be sensed, to an accuracy of about 2mm, by using a threshold detector. While an ultra-violet recorder monitors the real-time analogue data, a 14-channel f.m. magnetic recorder stores this information for later playback at The Railway Technical Centre in Derby, where detailed studies can be made. In addition, there is a magnetic tape recorder which is used to store the digital data and act as a transfer medium for the main computer. A character printer also provides printed pages of data indicating track statistics at 200m intervals.

This coach, a result of work by British Rail's Research and Development Division, will run over 80,000 miles each year checking most of Britain's 21,000 miles of track. The existing system of track recording has been in use for over 20 years and is often limited to a speed of 20 m.p.h.

Other countries also have track geometry coaches but this, the first to use a computer, is believed to be the most accurate and reliable.

British Rail are also collaborating with Harwell in the development of a new system for their Ultrasonic Test Train. At present, data from the train, which looks for defects such as cracks in rails by recording the reflections of ultrasonic pulses, are recorded on film before subsequent interpretation by a computer system at Paddington. The new system will be fully automated and will save about one mile of film for every

100 miles of track inspected. Ultimately, it is hoped that the complete evaluation will be made on board the vehicle by using mini-computers. This real-time system, which could increase the inspection speed from 20 m.p.h. to 40 m.p.h., is expected to be installed by the summer of 1978.

British Rail is confident that the Recording Coach and the Ultrasonic Test Train are likely to be of considerable interest to railways throughout the world and, together with its consultancy company, Transmark, and Harwell Laboratories, it is taking steps to sell them in Germany and Eastern Europe. According to Transmark, the coaches, which are custom-built units, will be taking a stand at the American Railway Supplies Exhibition in Chicago.

---

## Rise in components industry morale

---

The destinations of the £20 million of government funding for the electronic components industry (WW March p39) became a little clearer at a press conference to mark the merging of the Electronic Components Board with the larger Radio & Electronic Components Industry Federation, held on March 11. Mr M. St. A. Eley, of Plessey, said, "We won't have the final say in how or where the money goes, but I think it will be going towards projects that are convincing enough to the Department [of Industry], whether from a small, large or medium sized company."

Former director of the ECB Sir Ronald Melville, now an additional director of the new Electronic Components Industry Federation, said, "A lot of thought will be given to what use the technology is to be put." As well as being used for R & D the accent would be on the creation of new jobs and the building of factories. Eley added that the Department of Industry would sift potential projects very carefully. The announcement of the first successful applications is expected within a maximum of two months. The Secretary of State for Industry, Mr Varley is said to be already impatient to have the money available.

The formation of the ECIF, which first met on February 23 under the chairmanship of Jack Akerman of Mullard, coupled with the prospect of Government money, appear to mark a heightening of morale in the industry. Also contributing to this is what the ECIF calls the "five star treatment" that the industry will get as one of the five special industry sectors in the Government's industrial strategy, worked out with the National Economic Development Council and the trade unions. It appears that it is still no clearer what this "five star treatment" means and, asked by *Wireless World* to put a little

more flesh on the skeleton the ECIF council were clearly at a loss. Akerman seemed satisfied with the Government's attitude, however: "It means that the Secretary of State will take a personal interest in the industry. In effect, we have got an open door to go straight to the government, up to cabinet level if necessary, to put forward our views."

Also indicative of a more positive approach on the part of the industry is the reduction of emphasis on import controls. "What we are pressing for," said Jack Akerman, long the leading campaigner for controls, "is effective import surveillance." This meant that they would expect to be able to retaliate against the importation of colour sets made by our European trading partners using tubes made in the Far East. "We want fair trading, and effective import surveillance so that we know what is going on. For example the declaration of current domestic value on the import documentation."

Commenting on the £20 million funds he said, he regarded it as merely the first instalment, although "We don't want to give the impression that this industry exists solely on the basis of taking its cap to the government. We must be careful that we don't come over as a lame duck."

ECIF members seem to feel that large research and development expenditures may have to be forgone in favour of less glamorous activities: "We do know that the government wants the money put into the sharp end rather than the blunt end. It's tempting to put the money into R & D but we should put the money into marketing and making our product acceptable abroad."

---

## Digital course

---

Chelsea college will hold a one week course in Digital system design beginning May 16. The course, says the Department of Electronics, "is designed to give practising engineers and scientists a formal approach to the logical design of digital systems and should also prove useful to those engineers and scientists working in the field of digital electronics who have had no previous training in the methods of logic design." Professor J. E. Houldin, department of electronics, Chelsea College, Pulton Place, London SW6 5PR. 01-736 1244.

Owing to a communication error, the date of the course for teachers of the new A level course in electronic systems was published as June 18 to 20 instead of the correct date, July 18 to 20.

---

## "UD-45"?

---

In case you're wondering why articles on the NRDC system 45J decoding are appearing without there being any encoded material available, a clue to the

probable answer appeared in our last issue. No prizes, but if you want to do a bit of detective work stop reading here and read "NRDC surround sound system."

Concurrent with the gradual emergence of System 45J, moves were made to bring about a compromise settlement with surround-sound system codes. What seemed to be needed was a circle locus on the energy sphere that lay between two extremes. On the one hand was the BMX or "bimodal" matrix coding of Duane Cooper, used in the Nippon Columbia UD-4 basebands, and of Peter Fellgett's patent (with its one day priority over Bauer's similar "New Orleans" patent!) and on the other, was the amplitude coding of the Japanese Regular Matrix, to which Sansui's QS System approximated. The BMX vertical circle gave good mono performance but had a 90° phase difference between stereo channels, and the RM locus gave disastrous mono performance.

Now the best compromise is not necessarily the half way mark between these two extremes. The best plan may well have been to allow for a range of loci over which the balance may be tipped, in favour of reduced phasiness in the front section or else in favour of improved performance in mono, to suit the application. (Actually, the 45J system allows for such a range, but in its pairwise mixed options, rather than in its kernel form.) The BBC chose their locus to be about half way for the front part of the sound stage, and to be more like BMX for the rear part. Nippon Columbia tended to record front sounds with a reduced phase angle anyway when soloists appeared at centre front. The trend of the NRDC-sponsored project was departing from the originally patented scheme to a titled locus (but still a circle in its kernel form). It all looked very hopeful.

But this opportunity of producing a joint standard didn't appear to be grasped. Nippon Columbia went quiet; Sansui would have preferred to tilt their locus in the opposite direction; the BBC

seemed happy with what they had. Result: apparent stalemate. Yet looking at that article it is clear that *someone* is about to produce a 45J decoder. "... in the near future a decoder will be publicly demonstrated reproducing sounds via an arbitrary rectangle speaker layout..." We subsequently learnt from the UK section of the AES that Dr T. Takagi, who is general manager of Nippon Columbia's research laboratory, may also be taking part in a lecture that will include discussion of the 45J system... Perhaps this is the year to consolidate on the part of broadcasters and the record industry (page 35), lest this new enthusiasm should go off at half cock.

## Spacelab experiments

The first Spacelab mission towards the end of 1980 will carry 61 European, 15 American and one Japanese experiments. The mission, jointly planned between the National Aeronautics and Space Administration of the United States and the European Space Agency, will involve 222 experimenters from 16 countries. The experiments were chosen from 2,000 replies to invitations to participate. Eighty-one of the investigators come from Japan, 135 from Europe and the rest from Canada, India and Japan.

Spacelab will be launched aboard the NASA space shuttle, remaining attached to its three-man orbiter. The first mission carrying two instrument operators will last a week, but the re-usable Spacelab may stay in orbit for up to a month on subsequent occasions, carrying four operators, or "payload specialists", as they are called. The laboratory is expected to fly 50 missions during its ten-year life. The two operators will work shifts with the orbiter crew to ensure the laboratory, which is expected to complete 100 man hours experiments, is used round the clock.

The two payload specialist posts have now been advertised and they are expected to be filled in the summer of next year.

Of the nine experiments selected in the life sciences Britain has managed to capture three, compared with one each for France, Germany, Italy, Sweden, Switzerland and the United States. The three are:

Canal otolith interactions and adaptation in man (A. J. Benson of the RAF Institute of Aviation Medicine); Mass discrimination during weightlessness (Dr Helen Ross, Stirling University Department of Psychology); Personal miniature electrophysiological tape recorder (Mr Heinz Wolff, Clinical Research Committee).

Of the three Astronomy experiments Britain has one, France, Germany and Italy sharing the other two. It is a Mullard Space Science Laboratory

experiment on X-ray astronomy spectroscopy using a gas scintillation proportional counter. The four participants are Professor Boyd, Dr Brownlie, Dr Culhame and Dr Sanford.

Dr H. M. Rosenburg of Oxford University has one of the 39 material science experiments, Processing of composite materials in Spacelab. From the School of Chemistry, Bristol, Dr J. M. Haynes has two experiments: Kinetics of the spreading of liquids on solids, and a model study of interspatial instability and capillary hysteresis. Almost half a dozen materials science experiments put forward by the Department of Industry are being considered for funding, of which two or three will be successful. As we go to press the decisions had not been made.


## No decision yet on microwave landing system

A working party of the International Civil Aviation Organisation, meeting at the ICAO's headquarters in Montreal, has failed to reach agreement on the choice of a worldwide microwave landing system (m.l.s.). For two weeks beginning February 28 the All Weather Operations Panel of ICAO tried, in the final session of discussions that have lasted over a year, to decide among three rival systems: the British Doppler system; the American Federal Aviation Authority-sponsored scanning beam system; and a German ground-based system.

The search for a microwave replacement for the current instrument landing system (i.l.s.) began in the late 1950s when it became clear that, in view of the growth in air traffic, the current v.h.f./u.h.f. equipment was inadequate. However, the ICAO has endorsed the view that i.l.s. will be standard for another 25 years. First used in 1946, and adopted by the ICAO in 1949, it provides, essentially, three sets of information for the pilot: azimuth, or bearing, elevation and "distance to go." Three marker beacons five miles, one mile and 300 feet from the end of the runway provide distance. A "glide path" transmitter provides two overlapping beams modulated at 90 and 150Hz which are equal in received amplitude only when the angle of approach, normally 3°, is correct; above or below that angle one or other tone will predominate. A similar localizer beam operates down the centre of the runway, and another provides lateral information.

In a typical large airport installation meeting ICAO's "Category 3" standards (full instrument guidance from 25 nautical miles to the safe end of the runway with various subcategories for visibility) some 87 signals have to be

● continued on page 76

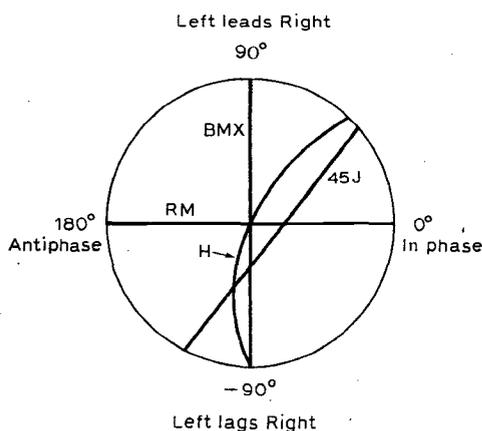

Side view of amplitude-phase energy sphere model shows how H and 45J "kernel" loci relate to the BMX code of UD-4 and the Regular Matrix of EIAJ

# Two-stage h.f. linear amplifier

by Helge O. Granberg

Motorola Semiconductor Products, Phoenix, Arizona

This article discusses the design of 50W and 300W linear amplifiers for the 1.6 to 30MHz frequency band, both of which employ push-pull design for low, even-harmonic distortion. This harmonic distortion and the 50Vd.c. supply voltage make the output impedance matching easier for  $50\Omega$  interface, and permit the use of efficient 1:1 and 4:1 broadband transformers. The four 300W modules are combined to provide a 1 to 1.2kW p.e.p. or c.w. output capability. The driver amplifier increases the total power gain of the system to approximately 34dB.

## Bias voltage

The bias voltage source shown in Fig.1 is employed with each of the 300W modules and the preamplifier. Its basic components are the integrated-circuit voltage regulator MC1723C, the current boost transistor  $Tr_3$ , the temperature sensing diode  $D_1$  and the voltage adjustment element  $R_{10}$ . Advantages of this type of bias source are:


- line voltage regulation, which is important if the amplifier is to be operated from various supply voltages,
- adjustable current limit,
- very low stand-by current drain.

The supply voltage is reduced by  $D_2$  and  $R_{12}$  to a level below 40V, which is the maximum input voltage of the regulator. The base-emitter junction of a 2N5190, in a Case 77 plastic package, forms the diode  $D_1$  of which the temperature compensation has a slight negative coefficient. Current limiting resistor  $R_5$  sets the limit to approximately 0.65A, which is sufficient for devices with a minimum  $h_{FE}$  of 17, ( $I_B = I_C/h_{FE}$ ) when the maximum average  $I_C$  is 10.9A. Typically, the MRF428  $h_{FE}$  is 30-40.

Measured output voltage variations of the bias source (0 — 600mA) are  $\pm 5$  to 7mV, which implies a source impedance of approximately 20 milliohms.
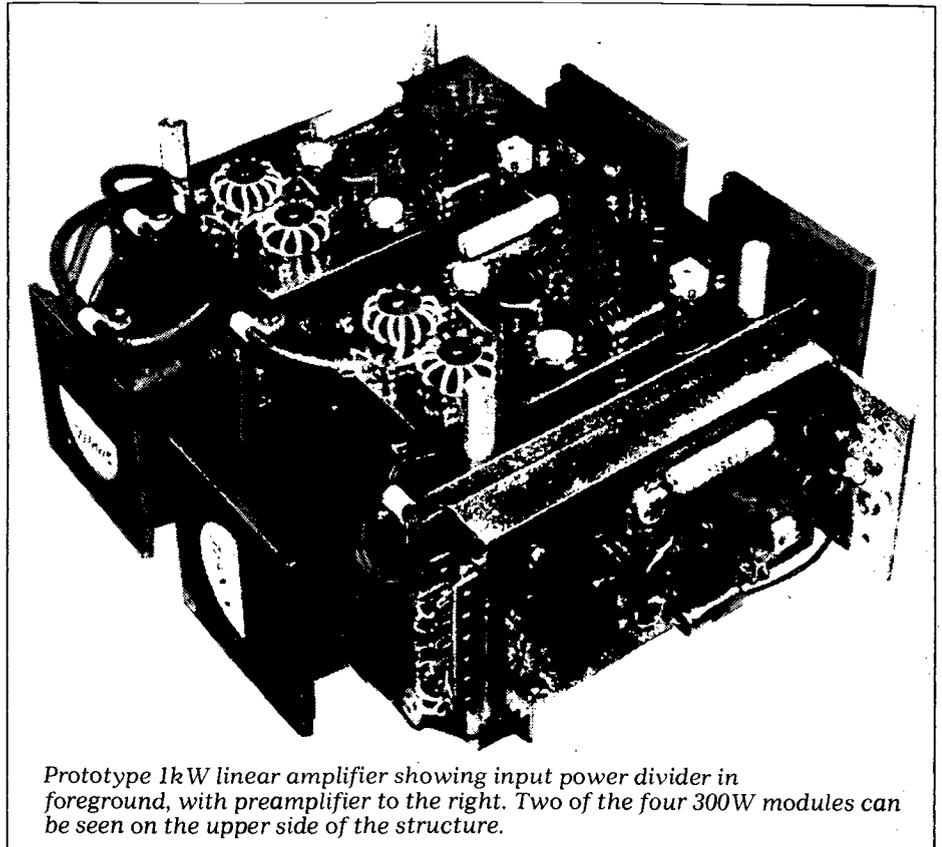
## 300W amplifier

Due to the large emitter periphery of the MRF428, the series base impedance is as low as  $0.88 - j0.80\Omega$  at 30 MHz. In a



Prototype 1kW linear amplifier showing input power divider in foreground, with preamplifier to the right. Two of the four 300W modules can be seen on the upper side of the structure.

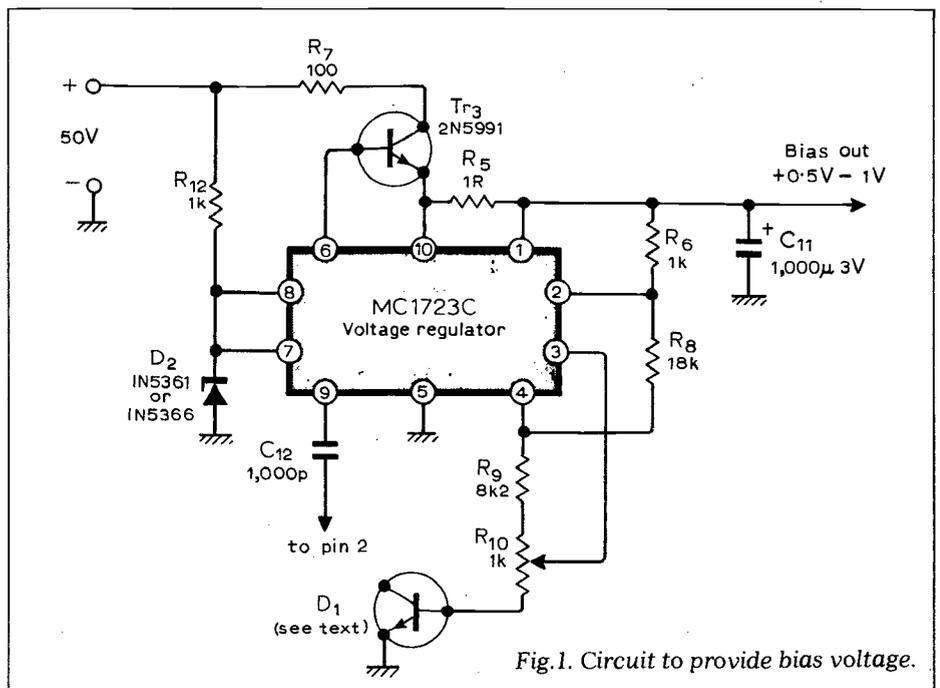


Fig.1. Circuit to provide bias voltage.

push-pull circuit a 16:1 input transformer would provide the best impedance match from a 50Ω source but would result in a high v.s.w.r. at 2 MHz, and would make it difficult to implement the gain-correction network design. For this reason a 9:1 transformer, which is more ideal at the lower frequencies, was chosen. This represents a 5.55Ω base-to-base source impedance.

A centre tap, common in push-pull circuits, is not necessary in the input transformer secondary, if the transistors are balanced. ( $C_{ib}$ ,  $h_{FE}$ ,  $V_{BEf}$ ) The base current return path of the momentarily amplifying transistor is through the base-emitter junction of the momentarily non-amplifying transistor, which acts as a clamping diode, and the power gain is somewhat dependent upon the bias current. The equivalent input circuit of Fig. 2 represents one half of the push-pull circuit, and for calculations  $R_S$  equals the total source impedance ( $R_S'$ ) divided by two.

Since a junction transistor is a current amplifier, it should ideally be driven from a current source which, in r.f. applications, would result in excessive loss of power gain. However, input networks can be designed with frequency slopes having some of the current source characteristics at low frequencies, where excess gain is available.

The complex base input characteristics of a transistor would require a very complicated input compensation network for optimum overall performance. The design goal here was to maintain an input v.s.w.r. of 2:1 or less and a maximum gain variation of  $\pm 1.5$ dB from 2 to 30MHz. Initial calculations indicated that these requirements could be met with a simple RC

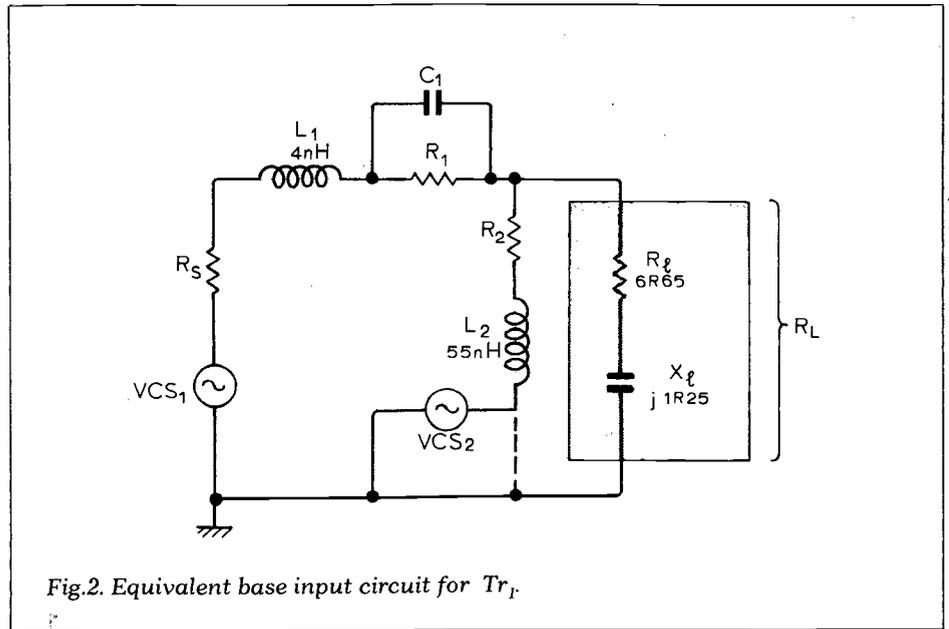


Fig. 2. Equivalent base input circuit for  $Tr_1$ .

network in conjunction with negative collector-to-base feedback. Fig. 2 shows this network for one device, where  $L_1$  and  $L_2$  represent lead lengths, their values being fixed. The feedback is provided through  $R_2$  and  $L_2$ . Because the calculations were done without the feedback, this branch is grounded to simulate the operating conditions.

Calculated values of  $R_1$  and  $R_2$  along with other known values and the device input data at four frequencies were used to simulate the network in a computer programme. An estimated arbitrary value of 4000 pF for  $C_1$  was chosen, and  $V_{CS2}$  represents the negative-feedback voltage (Fig. 2). The optimization was done in two separate programmes for  $R_1$ ,  $R_2$ ,  $C_1$  and  $V_{CS2}$  and in several steps. The goals were (a)  $V_{CS}$  and  $R_2$  for a transducer loss of 13 dB at 2 MHz and a

minimum loss at 30 MHz. b)  $R_1$  and  $C_1$  for input v.s.w.r. of <1.1:1 and <2:1 respectively. The optimized values obtained were  $C_1 - 5850$  pF,  $R_2 - 1.3\Omega$ ,  $R_1 - 2.1\Omega$  and  $V_{CS2} - 15V$ . The minimum obtainable transducer loss at 30MHz was 2.3dB, which is partly caused by the highest reflected power at this frequency, and can be reduced by "over-compensation" of the input transformer. This indicates that at the higher frequencies, the source impedance ( $R_S$ ) is effectively decreased, which leaves the input v.s.w.r. highest at 15 MHz.

In the practical circuit the value of  $C_1$  (and  $C_2$ ) was rounded to the nearest standard, or 5600 pF. For each half cycle of operation  $R_2$  and  $R_4$  are in series and the value of each should be  $1.3\Omega/2$  for a  $V_{CS2}$  of 1.5V. Since the voltage across ac

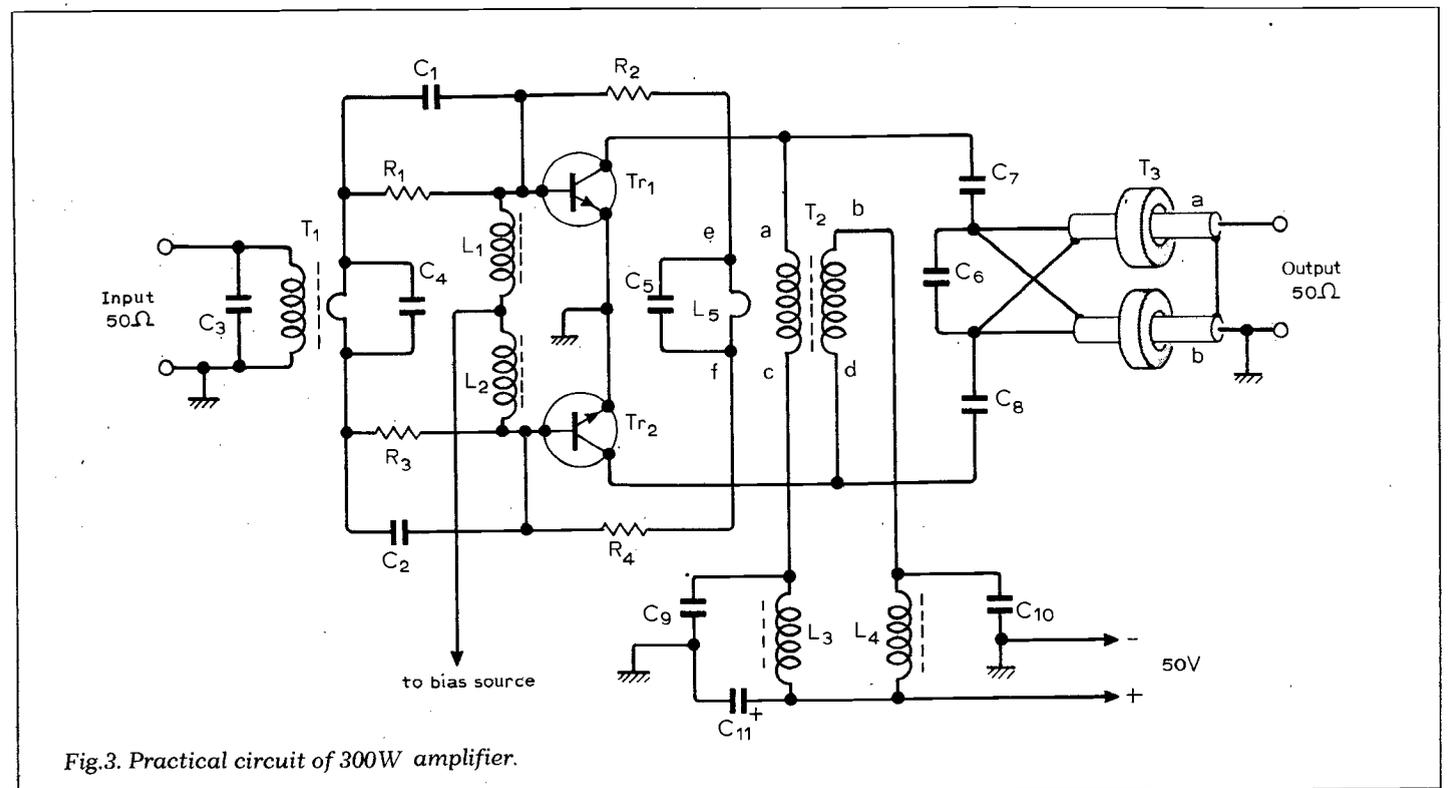


Fig. 3. Practical circuit of 300W amplifier.

and  $bd = V_{CE}$ , a turns ratio of 32:1 would be required. It appears that if the feedback voltage on the bases remains unchanged, the ratio of the voltage across  $L_5$  ( $V_{CS2}$ ) and  $R_2R_4$  can be varied with only a small effect to the overall input v.s.w.r. To minimize the resistive losses in the bifilar winding of  $T_2$  in Fig. 3, the highest practical turns ratio should not be much higher than that required for the minimum inductance, which is

$$\frac{4R}{2\pi} = \frac{50}{12.5} = 4.0\mu\text{H},$$

where  $R$  is the collector-to-collector impedance of  $12.5\ \Omega$  and  $f = 2\text{MHz}$ . The inductance of  $ac$  or  $bd$  will then be  $1.0\ \mu\text{H}$ , which amounts to 5 turns. A margin of 25% over this represents a 7:1 ratio, setting  $V_{CS2}$  to 6.9V.

The currents for each half cycle are in opposite phase in  $ac$  and  $bd$  and, depending on the coupling factor between the windings, the even harmonic components will see a much lower impedance than the fundamental. The optimum line impedance for  $ac$ ,  $bd$  would equal the collector-to-collector impedance, but experiments have shown that increasing this number by a factor of 2 to 3 affects the second and fourth harmonic amplitudes by only 1 to 2 dB.

Since the minimum gain loss obtainable at 30 MHz with the network in Fig. 2, and the modified  $V_{CS2}$  source was about  $-3.8\ \text{dB}$  at 30 MHz,  $C_5$  was added to form, with  $L_5$ , a parallel resonant circuit with a  $Q$  of approximately 1.5. Its purpose is to increase the shunting impedance across the bases, and to disturb the  $180^\circ$  phase difference between the input signal and the feedback voltage at the higher frequencies. This reduces the gain loss of 3.8 dB, of which 1.4 dB is caused by the feedback at 30 MHz. The amount depends upon the resonant frequency of  $C_5L_5$ , which should be above the highest operating frequency to avoid possible instabilities.

The input transformer is a 9:1 type, and uses a television aerial balun type ferrite core, made of high permeability material. The low-impedance winding consists of one turn of 1/8in copper braid. The sections which pass through the openings in the ferrite core are rounded to resemble two pieces of tubing electrically. The primary consists of 23 s.w.g. p.t.f.e insulated wire, threaded through the rounded sections of braid, with the primary and secondary leads in opposite ends of the core<sup>1,2</sup>. The saturation flux density is about 60 gauss, which is well below the limits for this type of core.

Several types of output transformer configuration were considered. The  $12.5\ \Omega$  collector-to-collector impedance estimated earlier requires a 4:1 transformer for a  $50\ \Omega$  output. A coaxial cable version was adapted for this design, since the transmission line type transformers are theoretically ideal for r.f.

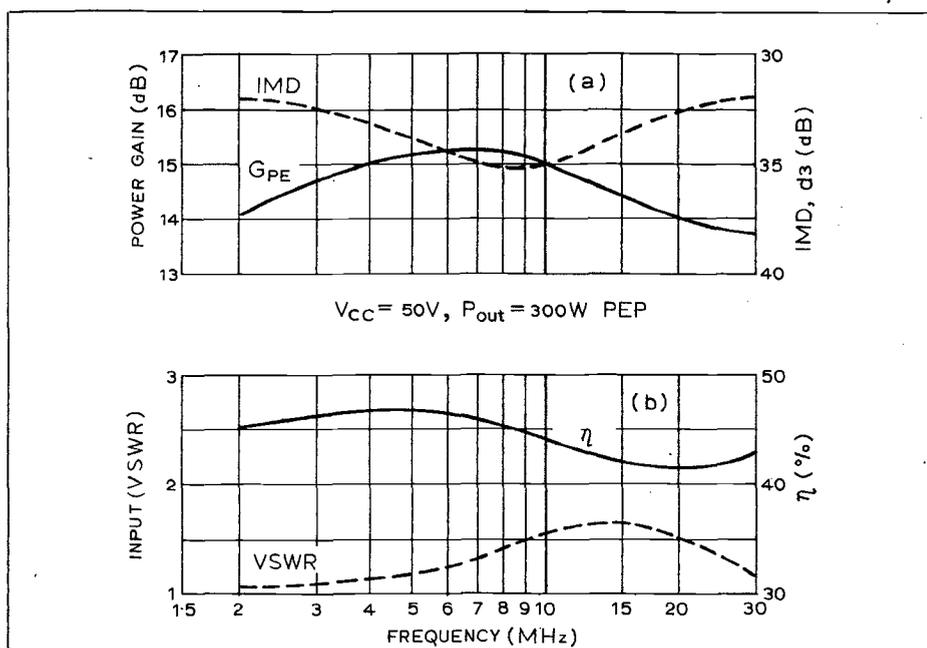


Fig. 4. Intermodulation distortion (3rd) and power gain are shown at (a), while (b) gives input voltage standing-wave ratio and efficiency ( $\eta$ ) against frequency.

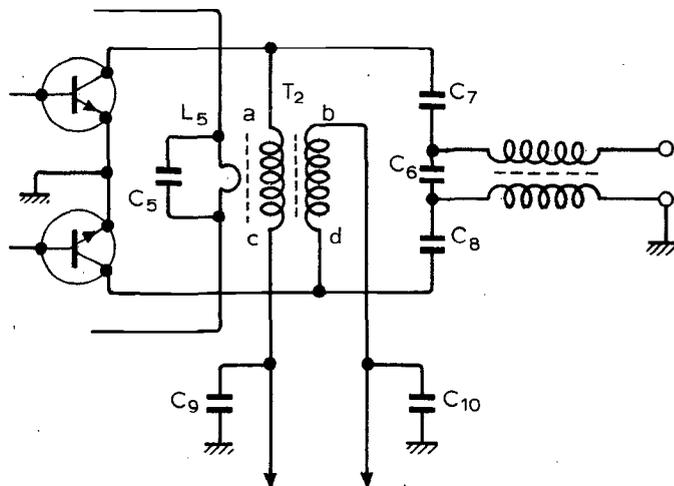


Fig. 5. Driver amplifier for 50W output.

applications, especially in the 1:4 impedance ratio. A balanced-to-unbalanced function would normally require three separate transmission lines including a balun<sup>2,3</sup>, but the third line can be omitted, if lines  $a$  and  $b$  in Fig. 3 are wound on separate magnetic cores, and the physical length of the lines is sufficient to provide the necessary isolation between the collectors and the load. Measurements showed the core losses to be negligible compared to the line losses at 2 MHz and 30MHz. However, the losses increase as the square of  $B_{max}$  at low frequencies.

With the amount of h.f. compensation dependent upon circuit layout and the exact transformer construction, no calculations were made on this aspect for the input (or output) transformers. The values of  $C_3$ ,  $C_4$ , and  $C_6$  were selected by employing adjustable capacitors on a prototype whose values

were then measured. The performance data of the 300W module is shown in Fig. 4.

### Driver amplifier

The driver shown in Fig. 5, uses a pair of MRF 427 devices, and the same circuit board layout as the power amplifier, with the exception of the type of the output transformer.

The input transformer is similar to that used with the power amplifier, but has a 4:1 impedance ratio. The required minimum inductance ( $4\ \mu\text{H}$ ) in the one turn secondary (Fig. 3) being considerably higher in this case, the  $A_L$  product of the core is barely sufficient. The measured inductances between a number of cores range 3.8 –  $4.1\ \mu\text{H}$ .

This formula also applies to the output transformer, which is a 1:1 balun. The required minimum inductance at 2MHz is  $16\ \mu\text{H}$ , amounting to 11

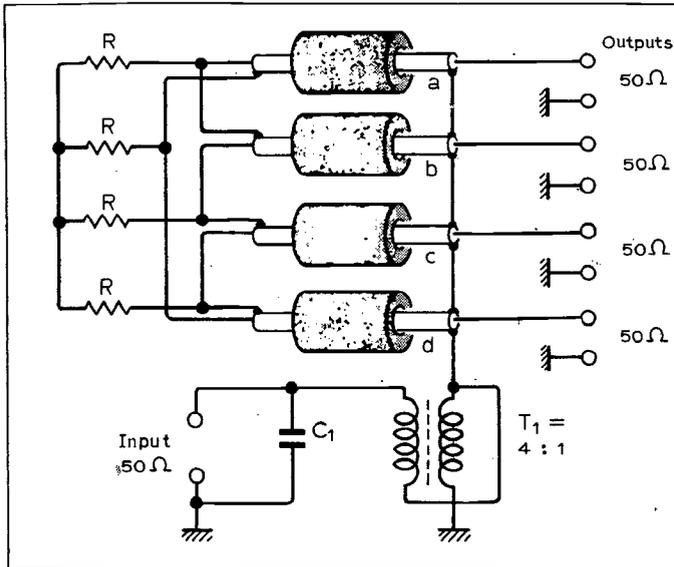


Fig. 6. Four-port input power divider.

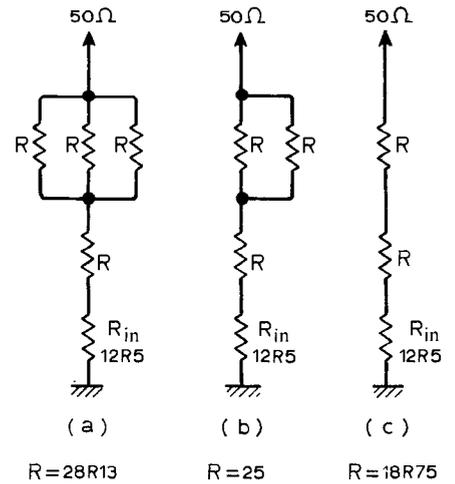


Fig. 7. Balancing resistors R in Fig. 6 when one or more loads open-circuit.

turns on a Ferroxcube 2616P-A100-4C4 pot core.

**Input power divider**

The purpose of the power divider is to divide the input power into four equal sources, providing an amount of isolation between each. The outputs are designed for 50Ω impedance, which sets the common input at 12.5Ω. This requires an additional 4:1 step down transformer to provide a 50Ω load for the driver amplifier. Another requirement is a 0° phase shift between the input and the 50Ω outputs, which can be accomplished with 1:1 balun transformers (a,b,c and d in Fig. 6). For improved low frequency isolation characteristics the line impedance must be increased for the parallel currents. This can be done, without affecting the physical length of the line, by loading the line with magnetic material. In this type of transformer, the currents cancel, making it possible to employ high-permeability ferrite and a relatively short physical length for the transmission lines.

The purpose of the balancing resistors R is to dissipate any excess power if the v.s.w.r. increases. Their optimum values, which are equal, are determined by the number of 50Ω sources assumed unbalanced at one time, and the resistor values are calculated accordingly.

Examining the currents with one load open, it can be seen that the excess power is dissipated in one resistor in series with three parallel resistors, whose total value is  $50 - 12.5 = 37.5\Omega$ . Similarly, if two loads are open, the current flows through one resistor in series with two parallel resistors, totalling 37.5Ω again. This situation is illustrated in Fig. 7.

**Output combiner**

The operation of the output combiner shown in Fig. 8, is the reverse of that of the input power divider. In this application we have four 50Ω inputs and one 12.5Ω output, which is transformed to 50Ω by a 1:4 impedance transformer.

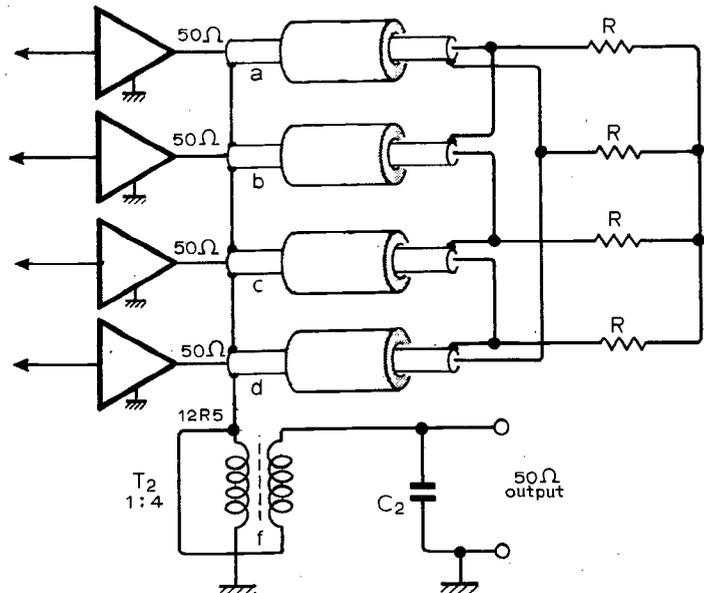


Fig. 8. Circuit of four-port power combiner – the reverse of circuit of Fig. 6.

An arrangement similar to the input power divider is employed in the combiner. The baluns consist of straight pieces of coaxial cable loaded by a sleeve of magnetic material (ferrite). The line length is determined by the physical dimensions of the ferrite sleeves. Straight-line baluns such as these have the advantage over multi-turn toroidal types in introducing a smaller possibility for phase errors, due to the smaller length of the line. The largest possible phase errors occur in the input and output connecting cables, whose lengths are 18in and 10in respectively. All four input and output cables must be of equal length within approximately 1/4in, and the excess in some, caused by the asymmetrical system layout, can be coiled or formed into loops.

The output connecting cables between the power amplifier outputs and the combiner are made of low loss RG-142B/U coaxial cable, that can adequately handle the 300W power with the average current of 2.45A.

The purpose of the step-up trans-

former T<sub>2</sub> is to transform the 12.5Ω impedance from the combiner up to 50Ω. It is a standard 1:4 unbalanced-to-unbalanced transmission line type transformer 3,4,5 in which the line is made of two RG-188 coaxial cables connected in parallel. As in the input transformer, the h.f. compensation (C<sub>2</sub>) was not required.

**References**

1. Granberg, H.: Get 300 Watts PEP Linear Across 2 to 30 MHz From this Push-Pull Amplifier, EB-27, Motorola Semiconductor Products Inc.
2. Granberg, H.: Broadband Transformers and Power Combining Techniques for RF, AN-749, Motorola Semiconductor Products Inc.
3. Hilbers: Design of H.F. Wideband Power Transformer Techniques, Philips Application Information 530.
4. Pizalis-Couse: Broadband Transformer Design for RF Transistor Amplifiers, ECOM-2989, U.S. Army Electronics Command, Fort Monmouth, New Jersey, July 1968.
5. Philips Telecommunication Review, Volume 30, No. 4, pp.137-146, November 1972.

# Power semiconductors — 2

## A survey of devices, technologies and applications

by Mike Sagin *Assistant editor, Wireless World*

Last month's article discussed the group of switching power semiconductor devices known as thyristors. This concluding article looks at power devices which can be used in the linear or switching mode.

### Power transistors

Bipolar junction transistors have been in use since 1948 and, although the early types used germanium, almost all of today's devices are silicon. A power transistor is a current amplifying device whose parameters are dependent upon the structure and geometry. There are four important parameters, voltage breakdown, current gain, speed, and power dissipation, all of which are mutually dependent. This places constraints on the design of a power transistor, and in general the most important parameter is given priority and the others are a compromise.

At low current density, the peak current-gain is determined by the emitter efficiency, base lifetime, and sometimes surface recombination. At high current density, the geometry and base-width are the most important factors. Voltage breakdown is generally proportional to the resistivity or impurity doping concentration on both sides of the junction. Most of the voltage drop occurs on the side of the junction with the lower impurity doping. Power dissipation is restricted by thermal and electrical limitations. Thermal limitation is controlled by the pellet size, thermal capacitance and resistance of the device. Electrical limitation is controlled by the secondary breakdown characteristic. Speed, or transient response, is determined by the capacitance and resistance of the transistor. Junction area and periphery control the capacitance, while doping and thickness of the active regions control the resistivity.

Because of the various trade-offs that exist in power transistors, several different structures have been developed.

**Single diffused**, sometimes called hometaxial-base, transistors — Fig. 20 start with a wafer of moderately high

resistivity silicon which then has several thin layers of impurities deposited and diffused deeply into both sides. Early in this diffusion process the top of the wafer is etched to produce a plateau which becomes the emitter area. This raised area is called a mesa. The process is completed when the deeply-diffused junctions are separated by a base region of about 25 micro-metres.

The single diffused process produces a very rugged device which has a high safe operating area (s.o.a.). The wide

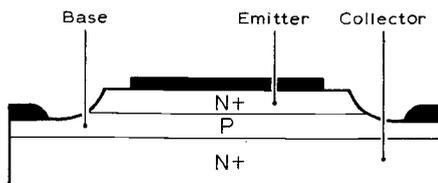


Fig.20. Single-diffused structure.

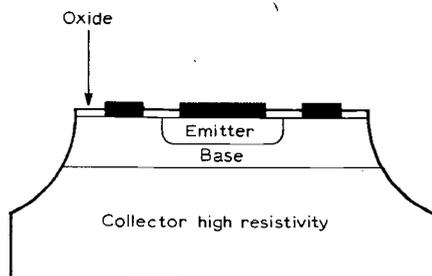


Fig.21. Double-diffused mesa structure.

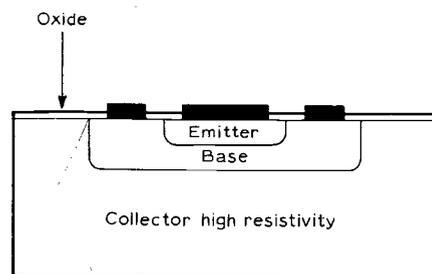


Fig.22. Double-diffused planar structure. Because the collector base junction terminates at the surface of the wafer it can be protected by an oxide layer.

undiffused base region, called homogeneous, allows injected charge carriers to spread out and reduce the charge carrier density at the collector junction where most of the heating takes place. The wide base region does, however, restrict the maximum  $f_T$  to around 2MHz. Large batch processing allows these devices to be manufactured cheaply although only n-p-n varieties can be produced. Maximum ratings for single diffused transistors are  $V_{CEO}$  of around 200V and continuous  $I_C$  of about 30A.

**Double diffused mesa transistors** — Fig. 21 start with a moderately high resistivity silicon wafer which has a dopant impurity deposited and then diffused to a shallow depth. Silicon dioxide is selectively etched to define regions where the emitter impurity is to be deposited and diffused. The oxide forms a mask which causes the emitter to diffuse more rapidly than the base. This action provides a narrow base region. Double diffused structures have the high-resistivity side of the collector-base junction on the collector side. As a result, the collector voltage can be designed almost independently of the base width.

The narrow nonhomogenous base provides an  $f_T$  up to around 20MHz but the base is also more fragile which reduces the s.o.a. The thick high-resistivity collector region also produces a high saturation resistance.

**Double diffused planar transistors** — Fig. 22 are very similar to the mesa type except for the collector-base junction. An additional selective mask is used for the base impurities which terminates the collector-base junction at the surface of the wafer instead of on the side. This junction is therefore passivated by a protective oxide layer as is the base-emitter junction in the mesa structure.

The planar transistor offers a greatly-reduced collector leakage current and more predictable device characteristics. Disadvantages are similar to those of the mesa type but the planar structure also has a collector voltage capability

which is up to 20% lower than a comparable mesa type. Again, only n-p-n devices are available.

**Triple-diffused transistors** — Fig. 23 are similar to double-diffused devices except for a third diffusion on the opposite side of the silicon wafer. This eliminates the high saturation resis-

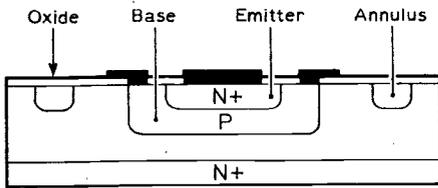


Fig. 23. Triple-diffused planar structure.



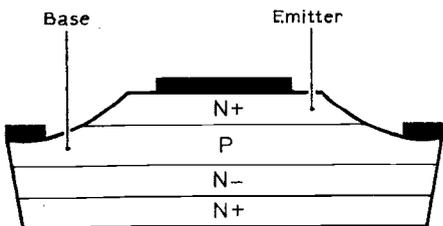


Fig. 24. Triple-diffused etch cut. This is a variation of the standard triple diffused device which offers a much higher  $V_{CEO}$  rating.

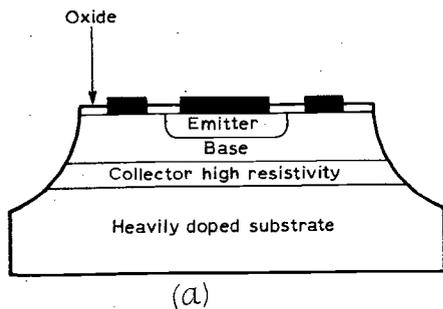

(a)

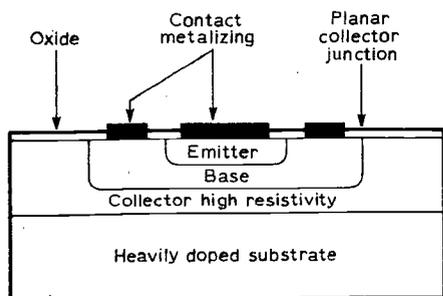

(b)

Fig. 25. (a) Double-diffused epitaxial mesa structure, (b) planar structure.

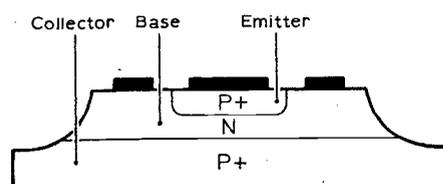


Fig. 26. Epitaxial-base mesa structure.

tance. The structure shown in Fig. 23 is the planar version and, like the double diffused, a mesa structure is also available. Devices with  $f_T$  ratings up to 30MHz,  $V_{CEO}$  ratings around 400V and continuous  $I_C$  ratings up to 15A are possible. Because the high-resistivity collector region is narrowed by a third diffusion, and the bulk of the collector is heavily doped and highly conductive, the junction is very fragile which greatly reduces the s.o.a. As with previous diffused devices, only n-p-n types are available.

A variation of this structure is the triple-diffused etch-cut device from Motorola — Fig. 24. This produces transistors with  $V_{CEO}$  ratings of up to 1000V, and continuous  $I_C$  ratings up to 15A. The  $h_{fe}$  rating is normally reduced together with the  $f_T$ , up to 10MHz, but the s.o.a. is slightly increased. Only n-p-n devices are available.

**Double-diffused epitaxial transistors** — Fig. 25 (a) and (b) are similar in appearance to the triple-diffused types, except that the diffused collector region is replaced by a heavily doped homogeneous layer referred to as the epitaxial substrate. A difference in doping produces improvements in the  $f_T$  up to 100MHz, and saturation resistance. However, the s.o.a. is very low and this type of device is unsuitable for driving capacitive or inductive loads. Both mesa and planar structures are available with  $V_{CEO}$  ratings up to around 300V and continuous  $I_C$  ratings up to 50A. Unlike the normal diffused transistors, both n-p-n and p-n-p types are available.

**Epitaxial-base mesa transistors** — Fig. 26 use epitaxial layers in the actual formation of the base-collector junction. A layer of impurity is epitaxially grown, rather than diffused, on to an opposite polarity and highly doped substrate. Oxide masking and emitter diffusion into this epitaxial layer completes the construction. The main

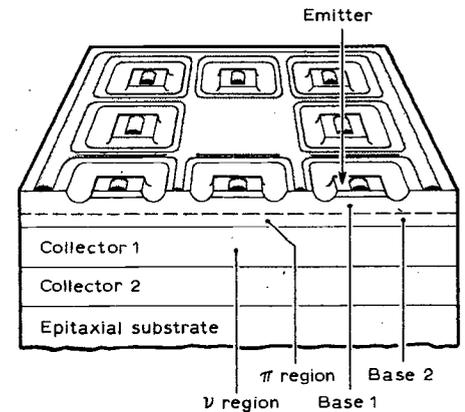


Fig. 27. Multiple epitaxial base mesa structure.

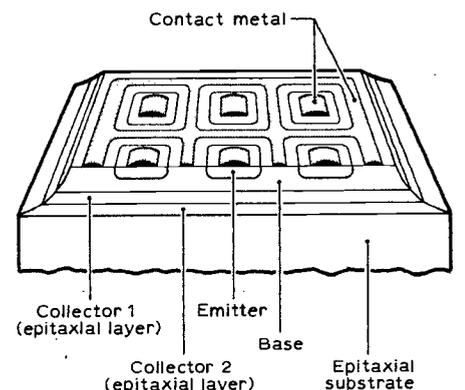


Fig. 28. Multiple-epitaxial double-diffused mesa structure.

advantage of the epitaxial-base structure is its ruggedness and s.o.a.

The epitaxial-base mesa transistor also has a higher frequency response, up to 10MHz, and the ability to carry higher currents for an equivalent emitter area. Maximum  $V_{CEO}$  ratings are around 160V with continuous  $I_C$  ratings up to 50A. The disadvantage of this design is the low voltage limitation which is due to the abrupt base-collector junction formed between the heavily doped collector substrate and the

Table 3. Silicon power transistor structures and trade-offs

| Structure                               | Advantages  | Disadvantages                   |
|---|---|---------------------------------|
| Single diffused (hometaxial-base)       | Rugged, low cost  | Low speed                       |
| Double-diffused mesa                    | High speed  | High saturation resistance      |
| Double-diffused planar                  | High speed, low leakage   | High saturation resistance      |
| Triple-diffused                         | High Speed, low saturation resistance                           | Moderate cost, moderate leakage |
| Triple-diffused etch cut                | High voltage  | Moderate speed                  |
| Double-diffused epitaxial mesa          | High speed, low saturation resistance                           | Moderate cost, moderate leakage |
| Double-diffused epitaxial planar        | High speed, low leakage, low saturation resistance              | less rugged                     |
| Epitaxial-base mesa                     | Moderate speed, low saturation resistance, moderately rugged    | Higher cost, less rugged        |
| Multiple epitaxial base mesa            | Moderate speed, low saturation resistance, rugged, high voltage | Low voltage, moderate leakage   |
| Double-diffused multiple-epitaxial mesa | High speed, rugged, low saturation resistance                   | Moderate cost                   |
|   |   | Moderate cost, moderate leakage |

epitaxially deposited base layer. A second disadvantage is the moderate collector leakage-current resulting from the mesa construction. Both n-p-n and p-n-p devices are available.

**Multiple-epitaxial base transistors** —

Fig. 27 are similar to the epitaxial base devices except for an added high-resistivity epitaxial layer for the active collector region. The transistor is constructed from a heavily doped silicon wafer on which alternate layers of p-n or n-p high resistivity silicon are epitaxially grown to create a  $\pi$ -v or v- $\pi$  base-collector junction. An emitter area is then diffused into the structure.

The main advantages of this construction are high voltage ratings and good current carrying abilities together with an improved s.o.a. The higher voltage ratings are due to the base and collector regions which both support the applied collector voltage. Good current ratings are due to the lower collector resistivity. The moderately wide base region and partial homogeneous base doping, which spreads the charge carrier density, provides good secondary breakdown characteristics. The main disadvantage of this construction is the relatively high manufacturing cost.

**Multiple-epitaxial double-diffused mesa transistors** —

Fig. 28 are similar to the double-diffused epitaxial types except that multiple epitaxial layers are used in the collector region. The top collector is a thin highly resistive layer followed by one or more thin heavily doped layers. These layers are grown sequentially onto a thick and heavily doped silicon substrate wafer. Advantages of this process are high speed, low saturation resistance, higher collector-junction voltage ratings and an increased s.o.a. Disadvantages are high cost and moderate leakage in the structure.

The types of structures already discussed are summarized in Table 3 with advantages and disadvantages. Performance curves for five popular types of device are shown in Fig. 29.

The geometry of a transistor can be considered as its topography. This together with the structure defines most of the fundamental properties. Most geometry designs in power transistors are aimed at increasing the current handling per unit area of device. The diagrams in Fig. 30 show various configurations from the inefficient ring-dot format to a present day overlay system. The recent interdigitated and overlay-geometries greatly increase the emitter periphery which in turn reduces high current density. This reduction in current crowding effectively increases the current gain of the device.

Two general methods exist for connecting the ohmic portion of the emitter and base contacts to the external leads of the package. Either wire bonds or soldered contact clips are used and Table 4 shows a range of connections.

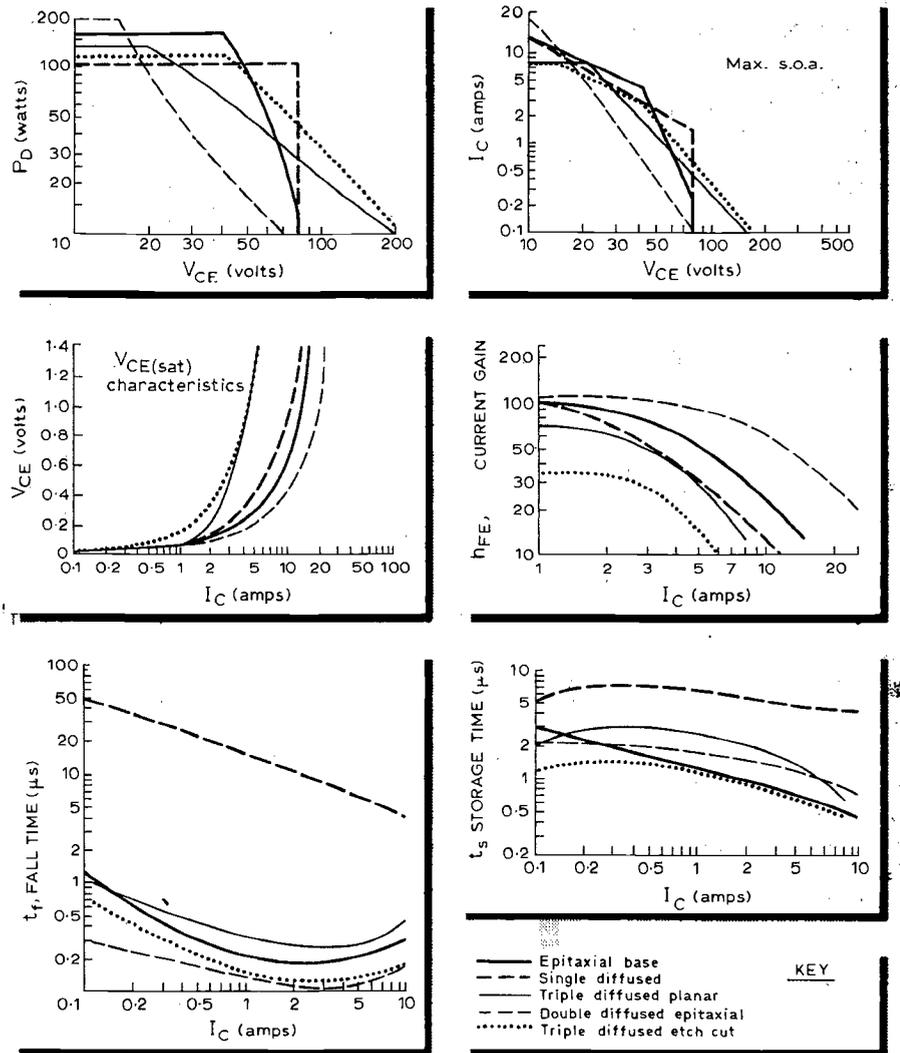


Fig. 29. Performance curves for five different transistor structures.

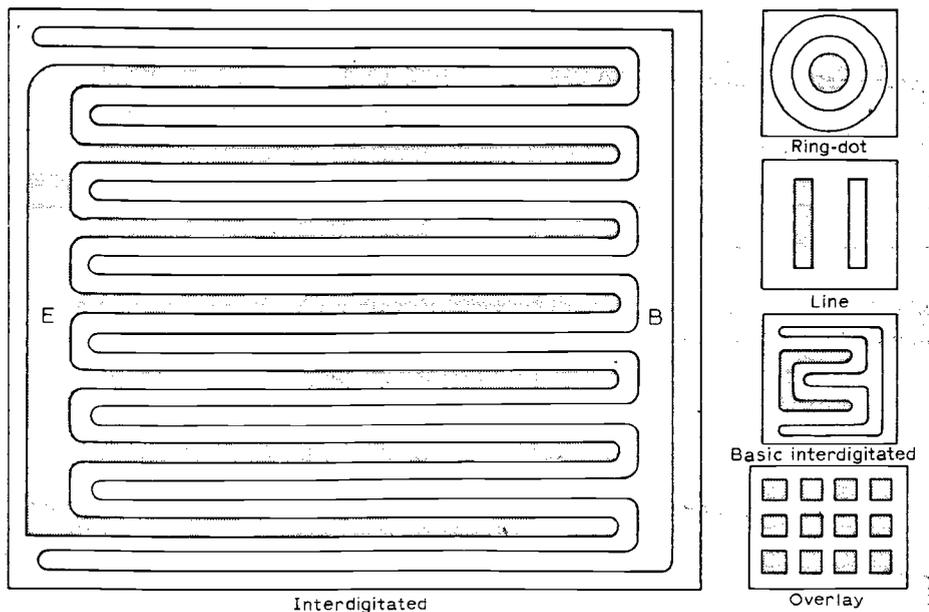


Fig. 30. Various transistor geometries.

**Table 4. Methods of lead attachment**

|                    |                               |                           |  |                              |
|--------------------|-------------------------------|---------------------------|--|------------------------------|
| Thermo-compression | High temperature and pressure | Gold-wire ribbon          | Very small areas                                   | Costly in large devices      |
| Nailhead bond      | High temperature and pressure | Gold wire with end balled | Stronger than thermo-compression bond, less costly | Larger contact area required |
| Ultrasonic bond    | Ultrasonic weld               | Aluminium or gold wire    | Avoids gold-alum problems                          | Costly in large devices      |
| Wire solder        | Insert wire in molten solder  | Suitable solderable wires | Moderate cost                                      | Large contact area required  |
| Clip solder        | Pre-set into clips; solder    | Phosphor-bronze or nickel | Low cost   | Large contact areas required |

**Darlington transistors**

The Darlington pair is a well-known current-gain configuration which uses two transistors and one or two passive components. A relatively new device is the monolithic power Darlington which combines these components on one chip. The structure and equivalent circuit of such a device is shown in Fig. 31. This particular structure uses a double-epitaxial, single-diffused process where the collector consists of an n<sup>+</sup> substrate plus an epitaxially grown n-type layer. The p-type base is epitaxially grown on top of the substrate, and the n-type emitter impurities are diffused into the base. For p-n-p versions the structure is similar. Construction of such a power Darlington is essentially the same as an epitaxial single-diffused transistor. The geometry, however, is very different. The driver transistor in the structure of Fig. 31 is in the centre of the pellet and is surrounded by the output transistor. The base emitter connection of the two devices is formed by metallization on the surface of the pellet.

Although monolithic Darlington have not been in existence for many years, some awesome devices are currently being produced. Toshiba have introduced a range of switching devices, one of which can handle a current of 400A at 300V and dissipate a staggering 3000W while offering a  $h_{fe}$  of 100 and a turn on time of 1μs. This sort of device is intended to replace thyristors in the control of d.c. motors.

Most Darlington structures have an integral diode connected across the output collector and emitter. The diode forward voltage drop is designed to be

less than the rated  $V_{EBO}$  and can be useful as an emitter clamp. A new device from Texas, the BU180/A, also has an integral speed-up diode connected between the base and emitter of


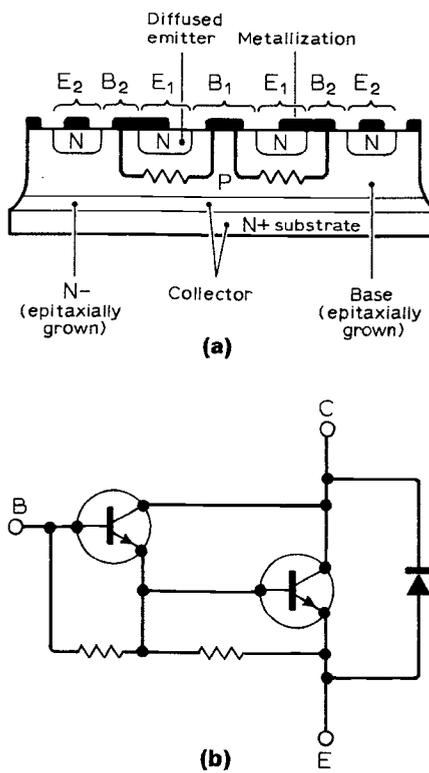


Fig.31. (a) Monolithic power Darlington structure, (b) equivalent circuit.

Fig. 32. Power Darlington bridge used to replace conventional thyristor motor-drive circuit. Each transistor has a high speed rectifier and surge suppressor across the collector/emitter.

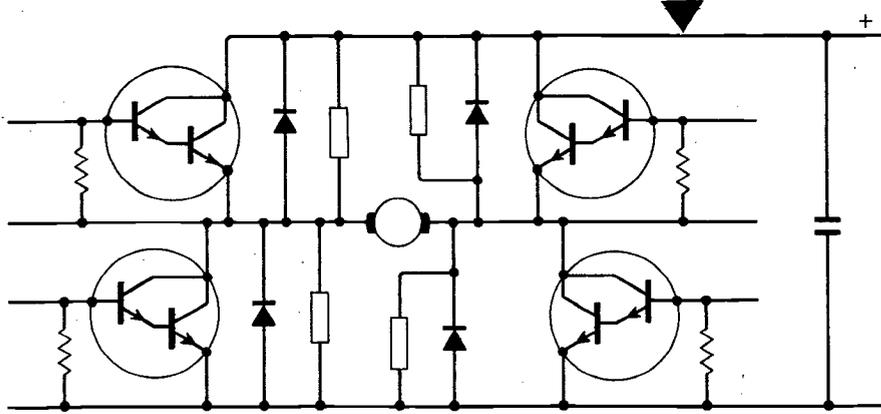

the driver transistor. This type of device has been designed to compete with medium and high power thyristors in d.c. applications. Faster devices are also being developed to compete with conventional low-gain power switching transistors.

**Power f.e.t.s**

Over the last three years f.e.t.s have challenged conventional bipolar power devices. Advantages of these f.e.t.s include high input impedance, greater linearity, majority carriers as opposed to minority carriers in bipolar devices, fast switching, and a negative temperature coefficient for the drain current. The last mentioned prevents secondary breakdown and provides an inherently short-circuit proof device when used in the output of an amplifier.

Although there are only two main types of power field-effect transistor available at the moment, much confusion has arisen from the use of loose terminology. The current "buzz" word is "V" f.e.t.s which has been used to describe either the vertical current flow within the device, the physical V shaped groove in the device, or both. The most publicised f.e.t.s at present are the Japanese devices, first reported in *Wireless World* July 74 and July 76. These are vertical-junction depletion-mode (normally on) f.e.t.s and are currently being used in audio equipment. Six devices from the three manufacturers are shown in table 5, and Fig. 33(a) shows a simplified construction. Current flows vertically from the substrate through the chip, which measures about 3×3mm, and allows a greater current density for high power applications. This type of construction permits the production of complementary pairs. Output characteristics of these devices are very similar to a triode valve. One disadvantage of this construction is the relatively high capacitance ( $C_{ISS}$ ), around 700pF for the NEC type and 3000pF for the Yamaha, which limits the upper frequency response. Also, when used in linear amplifiers, several different supply voltages are necessary. Because the devices are

**Table 5 Power ratings of commercial vertical junction f.e.t.s**

| Nippon Electric | Sony        | Yamaha      |
|-----------------|-------------|-------------|
| 2SK70 2SJ20     | 2SK60 2SJ18 | 2SK75 2SK77 |
| n channel       | n channel   | n channel   |
| 100W at 25°C    | 63W at 25°C | 20W 200W    |
| --              | 170V        | 200V 200V   |
| --              | 5A          | 0.5A 20A    |

normally on, a gate bias has to be applied before power is supplied to the output stage. Conversely, power has to be removed from the output stage before the gate bias.

Up to date these devices have only been commercially used in linear hi-fi equipment but in a recent paper presented at the 55th AES Convention, Mr T. Suzuki of the Sony Corporation outlined the design of a pulse-width modulation audio power amplifier using vertical junction f.e.t.s.

Although these f.e.t.s are better suited to low frequency application, future devices will offer lower saturation resistances by using larger chip sizes, and higher amplification factors.

Power m.o.s.f.e.t.s, commonly called v.m.o.s, are the second group of devices and several companies are developing this technology. At present most of the devices are lower power than junction f.e.t.s, but offer faster switching speeds. American Microsystems and Electronic Arrays are developing v.m.o.s structures — see Fig. 33(b) for use in r.o.ms, r.a.ms and possibly microprocessors. Westinghouse Research Centre have experimented with "shadow mask" gate metallization in the structure shown in Fig. 33(c). The overhanging oxide layer forms an aperture through which the gate metallization is sputtered over the channel. This process has been used to produce microwave devices which exhibit an  $F_T$  of 4.8GHz, but there are no commercial products available yet.

Harris Semiconductor have developed a 12W device using the structure shown in Fig. 33(d). This offers depletion mode performance and is called v.m.o.s. because of the groove and not the current path. Hitachi have produced a v.m.o.s. device without the groove, see Fig. 33(e). Current flow is again vertical but a polysilicon gate is used and this allows a high packing density but limits the high frequency performance to 1MHz. By using a large geometry size of 5x5mm, the device has an 80V 20A capability and is aimed at the high fidelity market as an alternative to the vertical-junction f.e.t.s. Siliconix have commercially available a range of v.m.o.s. devices under the trade mark MOSPOWER. These f.e.t.s are based on the structure in Fig. 33(f). The n+ substrate becomes the drain and an n- epilayer increases the drain-source breakdown voltage by absorbing the depletion region from the drain p-body junction which is normally reversed biased. Because the gate overlaps n- instead of n+ material, the feedback capacitance is reduced by the epilayer. A p- body and n+ source are then diffused into the epilayer, similar to the base and emitter diffusions in a bipolar transistor. A V groove is then etched through the source body and into the n- epilayer. Oxide is grown, followed by the deposition of an aluminium gate. The completed chip is then passivated. In operation the gate is taken positive with respect to the source. The resulting

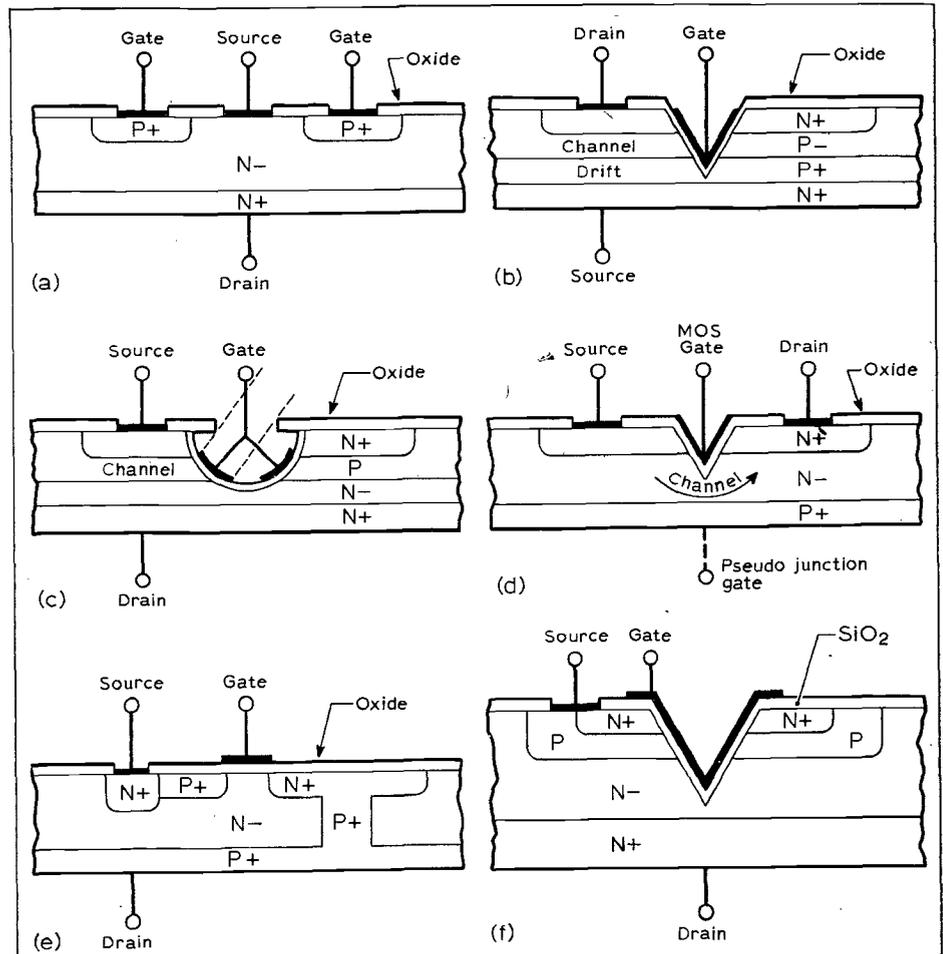


Fig. 33 Various-power f.e.t. structures under development and in production.

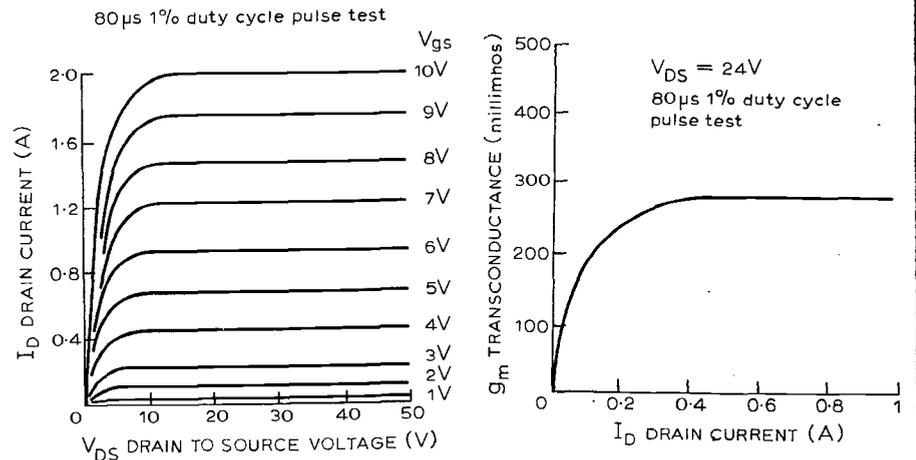


Fig. 34 Output characteristics of a typical v.m.o.s. field effect transistor.


electric field induces an n-type channel on both surfaces of the body facing the gate. Electrons can then flow directly from the source through the n-type channel and epilayer into the drain.

The V groove structure offers several advantages over conventional m.o.s. devices. The length of the channel is determined by diffusion depths which are much more controllable than the mask spacings used to define the channel length in standard low power devices. The substrate forms the drain contact, so drain metal runs are not required on top of the chip. This reduces chip area and keeps the saturation

resistance low. Because the groove creates two channels the current density is doubled, which also keeps the chip capacitance low.

Output characteristics of a typical device are shown in Fig. 34. Because of the extremely fast switching time, 1 amp in 4ns, and typical on resistance of around 3Ω, these f.e.t.s can be used in converter, r.f., and switching regulator circuits. Although the maximum dissipation is around 25W at 25°C several devices can be used in parallel operation as shown in Fig. 35. This practical audio amplifier circuit will deliver around 40W continuous into 8Ω. As the f.e.t.s

Fig. 35. Practical audio amplifier using six v.m.o.s. f.e.t.s in the output stage. The circuit has a bandwidth of 800kHz and a typical distortion content at 1kHz 40W, of 0.04%. Resistors  $R_{16}$  to  $R_{18}$  and  $R_{21}$  to  $R_{23}$  should be connected to within one inch of

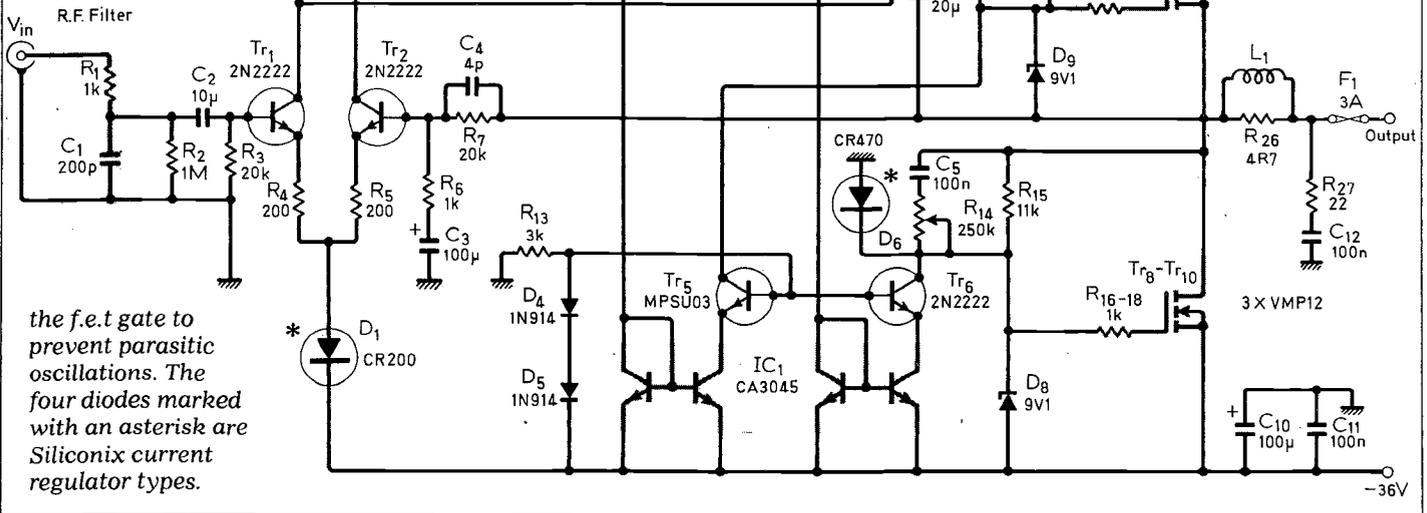

the f.e.t. gate to prevent parasitic oscillations. The four diodes marked with an asterisk are Siliconix current regulator types.

are enhancement mode (normally off) only one split power supply is needed. The circuit has a bandwidth from 1Hz to 800kHz, a typical distortion figure of

0.04% at 1kHz 40W, and the output is short circuit proof due to the negative temperature coefficient.

The future of v.m.o.s. devices seems

well assured especially as Siliconix are talking about transistors with 10A, 200V capabilities, and on-resistances of below one ohm.

#### ● continued from page 66

communicated not counting voice channels.

I.l.s. has a limited number of channels, and some airports do not have suitable ground sites for the equipment. It is also susceptible to severe multipath interference, scattering and diffractions from buildings, geographical features and moving aircraft. Aircraft must land one at a time.

The ideal ICAO-approved m.l.s. system will have left-right guidance up to 30 miles away, two elevation aeriels providing "coarse" and "fine" height information, and a back azimuth beam to guide aircraft that overshoot. The information will be available over a much wider area than can currently be provided by the thin i.l.s. beam, and thus it will be within the range of more than one aircraft at a time.

In addition, the ICAO wants to move towards making it possible to use the landing system when visibility is zero. At the moment the category 3(a) standard applying to most major airports provides for landing with an external visual reference of 200m. Category 3(b) is defined with a visual range of 50m. The zero range is category 3(c).


Following the setting up of a committee in 1967, when about 50 microwave landing systems were competing, the decision to base future systems on microwaves was taken about five years ago. Broadly, the choice is between two, the American and the British, though both sides have changed their proposals frequently in a way reminiscent of the surround-sound matrix battle in audio systems. The British system was devised by Charles Earp of Standard Telephone Laboratories, Harlow, in 1968. He thought that if a fixed frequency r.f. signal were moved back and forth perpendicular to ideal path down the centre of the runway, a plane approaching at a wrong angle would observe a change in its frequency, a Doppler shift, proportional to the sine of the angle the plane's path made with the correct approach. Any Doppler shift caused by the movement of the plane could be compensated by an additional stationary reference beam at the same frequency.

A horizontal Doppler beam would provide the azimuth, and a vertical one the approach angle. In a practical system the moving source could be replaced with a switched series of

stationary sources. The British proposal is now being put forward by Plessey, for whom STL are now subcontractors.

The American system, the time-reference scanning beam (t.r.s.b.) devised by Bendix, works by sending out two fan-shaped beams which scan through predetermined angles. One beam provides azimuth and the other elevation information. During each scan, the aircraft receives two pulses, one each during the to and fro scans. The position angle of the aircraft is determined by the time differences between these pulses; since the aircraft will only receive them at equal intervals if it is directly on course. A third "flare" transmitter provides the low-angle guidance needed in the last half mile before touchdown.

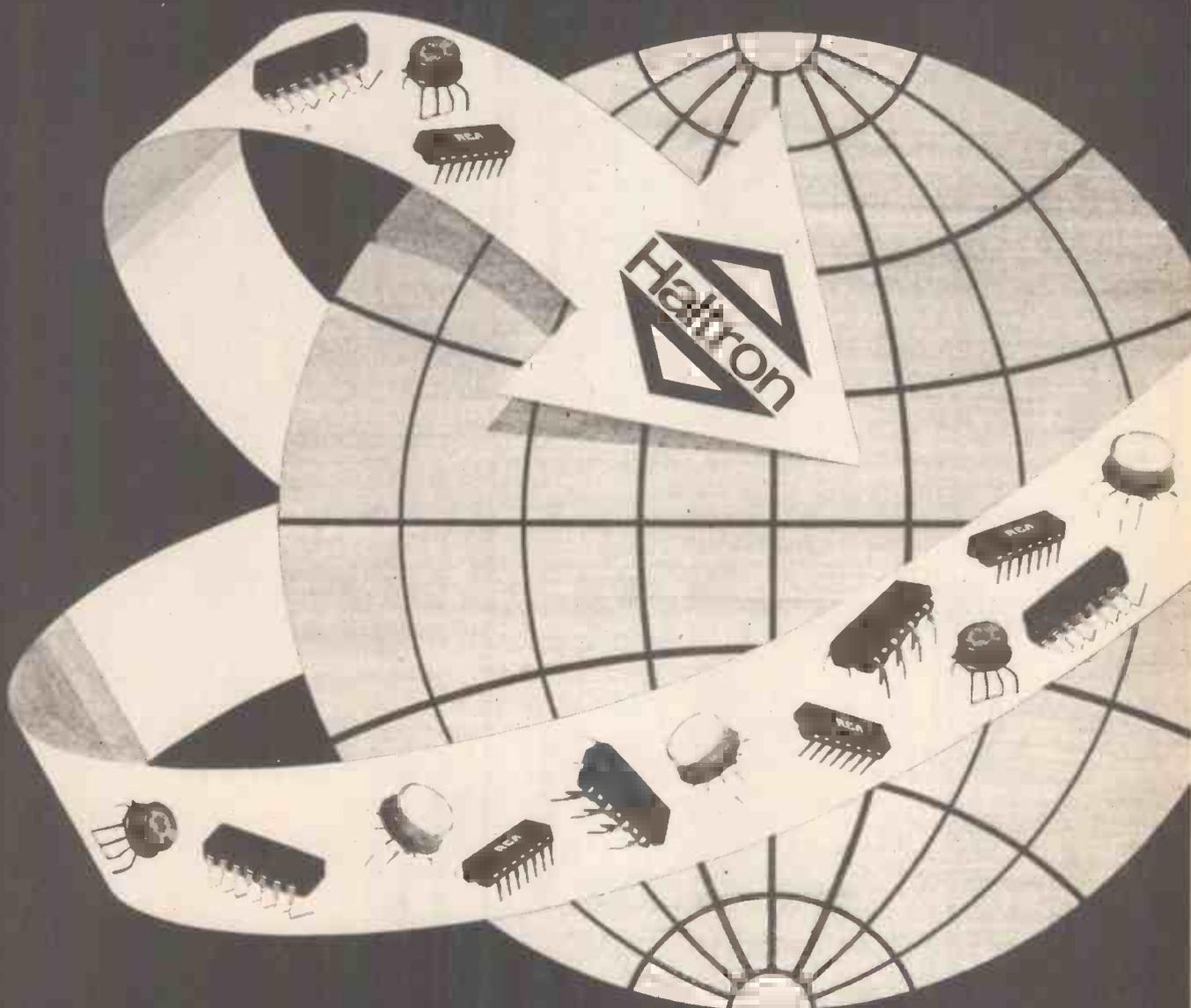In the voting in Montreal Britain was supported by Dutch and Canadian delegates and the representatives of the International Federation of Airline Pilots' Associations. The US system was supported by a formidable alliance of Russia, Australia and the International Air Transport Association, for the airlines. The ICAO navigation committee is expected to meet in the autumn.



**The world over-  
You get the  
best service  
from Haltron**

For high quality electronic valves, semiconductors and integrated circuits – and the speediest service – specify Haltron. It's the first choice of Governments and many other users throughout the world. Haltron product quality and reliability are clearly confirmed. The product range is very, very wide. And Haltron export expertise will surely meet your requirements. Wherever you are, get the best service. From Haltron.



Hall Electric Limited,  
Electron House,  
Cray Avenue, St. Mary Cray,  
Orpington, Kent BR5 3QJ.  
Telephone: Orpington 27099  
Telex: 896141

# Way out in front!

A great new line of RF-heating products from THOMSON-CSF:

- Output power from 100 to 800 kW
- Superior PYROBLOC<sup>®</sup> grids and HYPERVAPOTRON<sup>®</sup> anode cooling - the latest word in power-grid tube technology.

Specially designed for industrial thermal treatment and built using rugged metal/ceramic technology.


Get the latest advance in the power-grid tube state of the art from the RF-heating leader: THOMSON-CSF!

Contact us today.



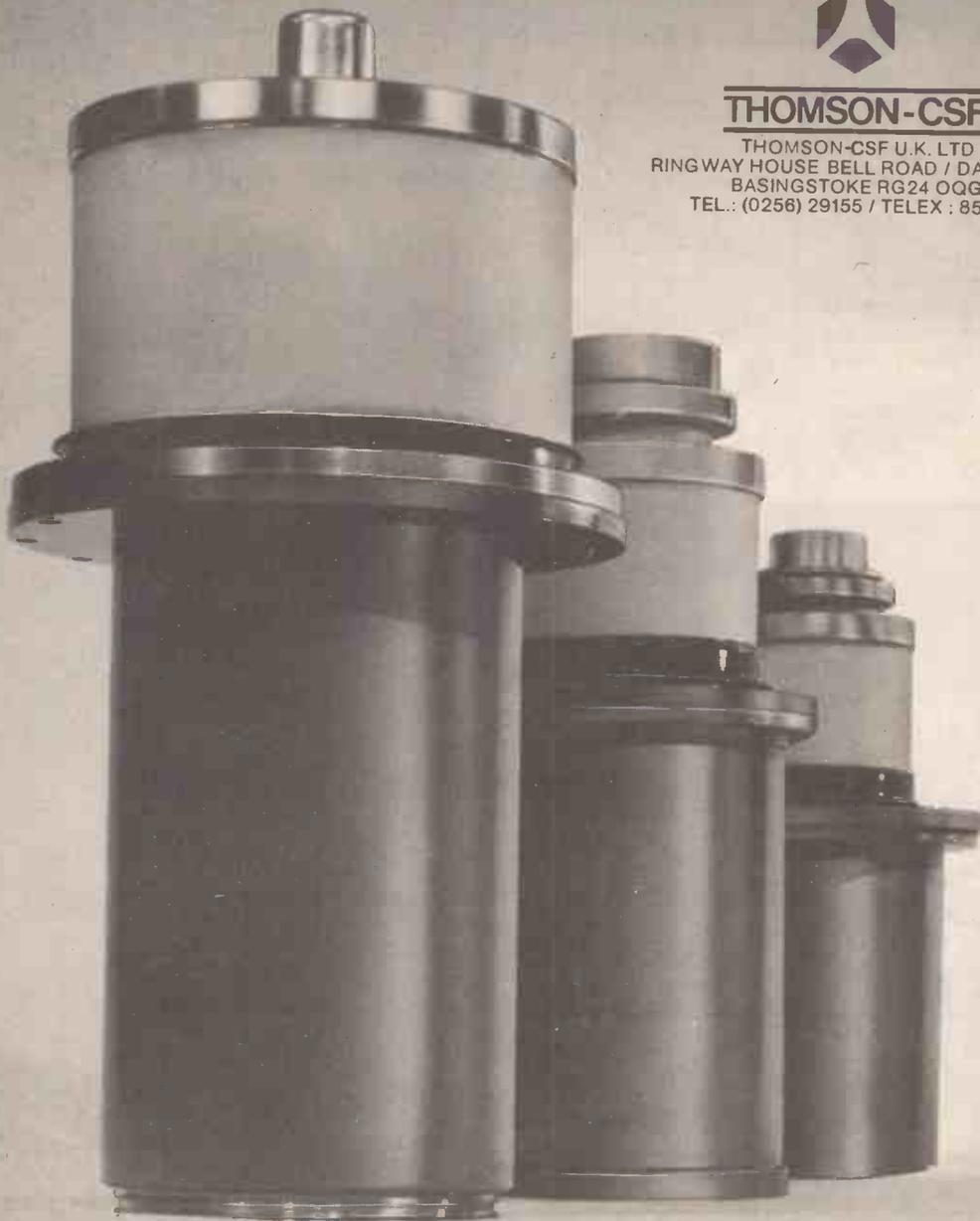**THOMSON-CSF**

THOMSON-CSF U.K. LTD  
RINGWAY HOUSE BELL ROAD / DANESHILL  
BASINGSTOKE RG24 0QG  
TEL.: (0256) 29155 / TELEX : 858865



# Circuit Ideas

## Op-amp power output stage

This circuit overcomes the difficulty in setting quiescent current by using  $R_2$  for adjustment and  $R_3$ , within the feedback loop of the op-amp, for stabilization.

Positive signals are handled by  $Tr_1$  with base current flowing down  $L_1$ . Negative signals are handled by  $Tr_2$  with base current initially via  $R_1$ . For large negative signals  $D_1$  becomes forward biased and base current for  $Tr_2$  is then drawn through the load and  $D_1$ . Resistor  $R_1$  must be large enough to forward bias  $D_1$  for negative excursions in order to prevent  $Tr_1$  from being turned on. It is possible to omit  $R_1$ ,  $C_4$  and  $R_3$ , but the crossovers are then less smooth. The op-amp may be used in the virtual earth mode if desired.

D. Rawson-Harris,  
Ferranti Ltd,  
Manchester.

## Zero crossing detection with exponentially decaying hysteresis

It is well known that a zero detector may be constructed as shown in Fig. 1. Assuming that the output  $V_0$  of the operational amplifier is at its positive limit  $V_+$ , then the voltage  $V_+$  on the non-inverting input is  $V_1 R_2 / (R_1 + R_2)$ , and the amplifier output will not change

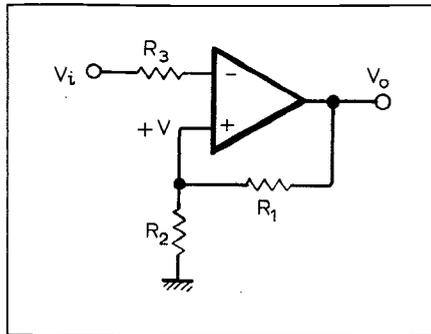


Fig 1

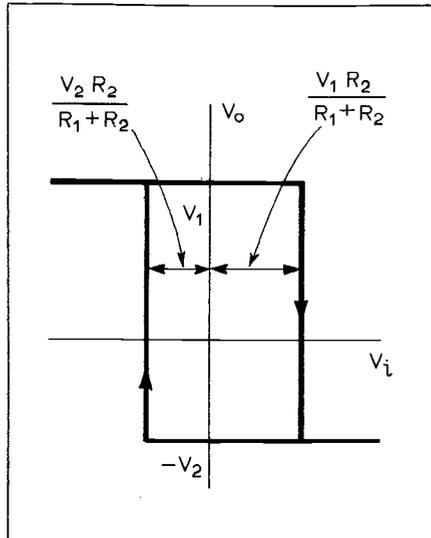


Fig 2

unless  $V_i > V_+$ . Once  $V_0$  starts to fall,  $V_+$  decreases and the switching process is accelerated due to positive feedback through  $R_1$ . The penalty for this sharp switching is that when  $V_0$  is at its negative limit  $-V_2$ , the amplifier will not start to switch unless  $V_i < -V_2 R_2 / (R_1 + R_2)$  and thus exhibits a hysteresis band of width  $(V_1 + V_2) R_2 / (R_1 + R_2)$  as shown in Fig. 2. This hysteresis is often valuable because it avoids multiple switching of the detector when the input consists of a low frequency signal corrupted with high frequency noise. It does, however, reduce detector sensitivity for small inputs.

The modified circuit shown in Fig. 3 gives improved zero detection. When the circuit changes state,  $V_0$  changes by an amount  $(V_1 + V_2)$  and thus  $V_+$  immediately changes by  $(V_1 + V_2) R_2 / (R_1 + R_2)$ , because the charge on the capacitor cannot change instantaneously. Subsequently,  $V_+$  decays exponentially to zero with time constant  $(R_1 + R_2)C$ . Since  $V_0$  only


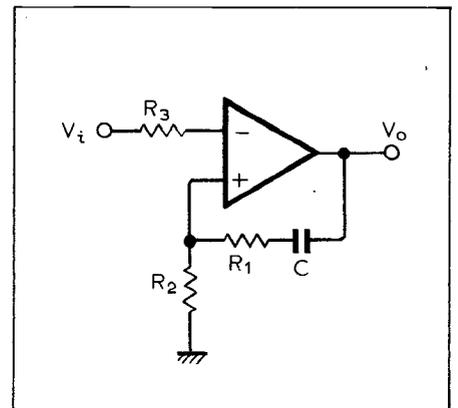


Fig 3

changes when  $V_i = V_+$  the hysteresis in the detector is large just after a change of state has occurred, but later decays to zero. Therefore, there is sharp switching between the limits and when noise is present multiple switching is avoided. If the time constant is significantly shorter than the average time separation of the zero crossings the zero detection is very accurate.

To avoid error with the input bias currents of the amplifier,  $R_3 = R_1 R_2 / (R_1 + R_2)$  in Fig. 1 and  $R_3 = R_2$  in Fig. 3. Also in Fig. 3  $R_1 > R_2$  so that the input-voltage limits of the operational amplifier are not exceeded.

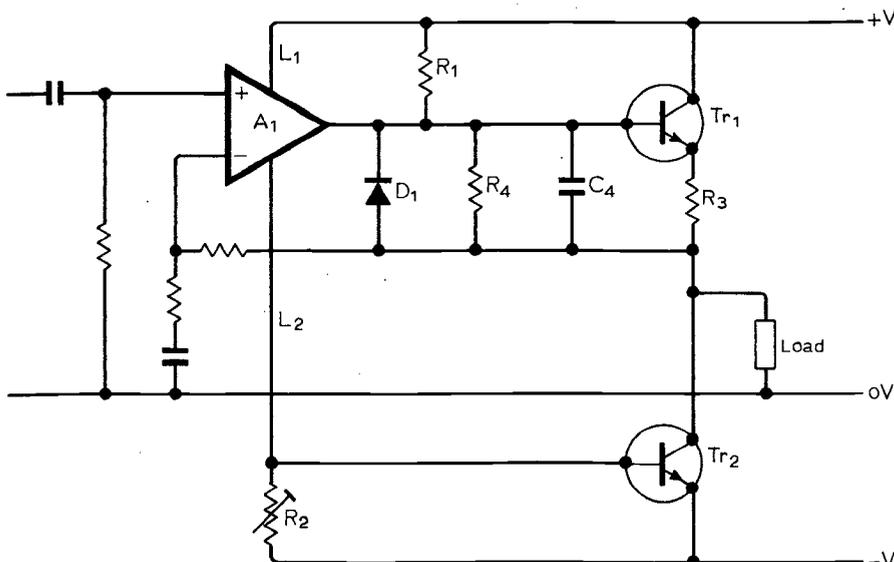M. L. Bransby,  
University of Sheffield.





Contributors to Circuit Ideas are urged to say what is new or improved about their circuit early in the item, preferably in the first sentence.
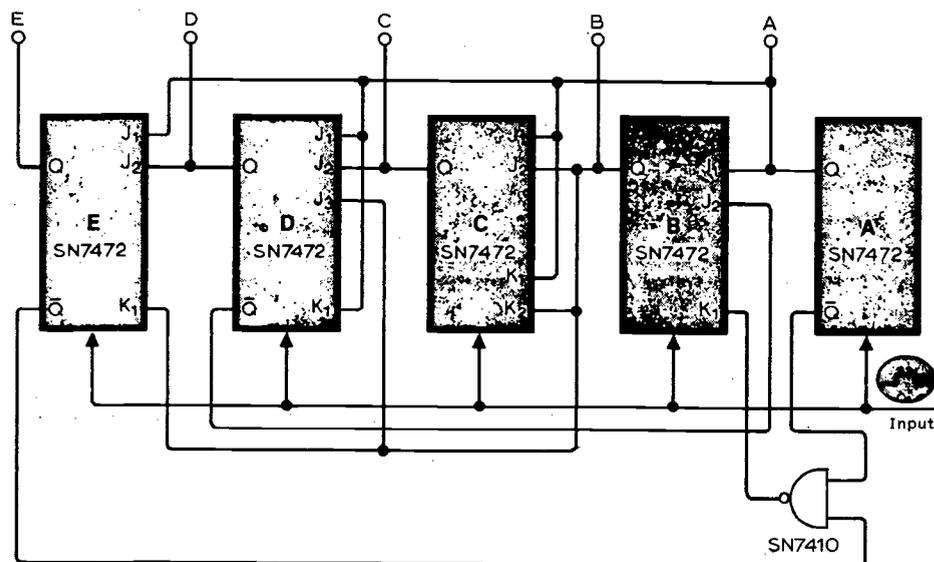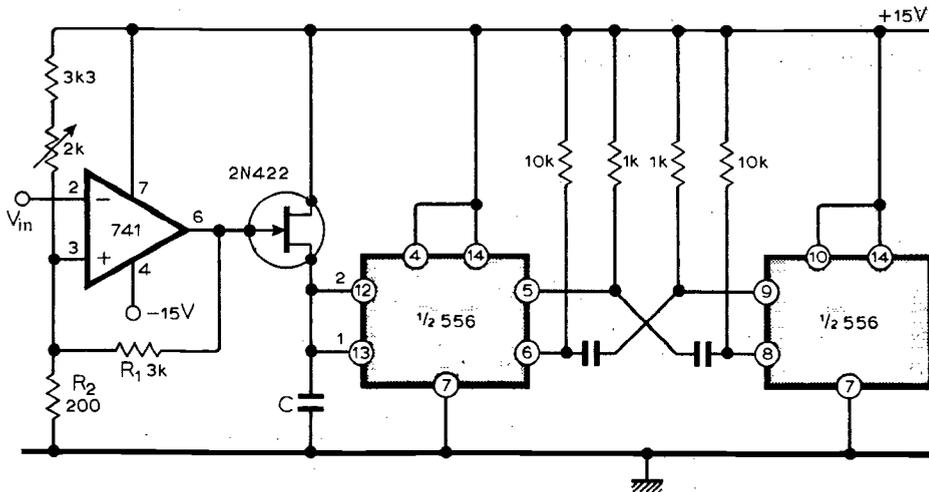
### Linear v-f converter

In this circuit a NE556 timer is used in a dual mode. Frequency of operation is  $0.91/2RC$  where R is the resistance of the f.e.t. Because the resistance R is indirectly proportional to the input voltage, the circuit is very linear. Frequency range is from 0.1Hz to 100kHz and the linearity is within 0.005%.

Kamil Kraus,  
Rokycany,  
Czechoslovakia.



### True count-by-twelve circuit

An ordinary divide-by-twelve circuit gives a logical sequence of output states that go from zero to eleven, whereas a true count-by-twelve circuit will do so from the count 1 through 12 and will come back to 1 with no zero. One application of such a circuit is in a 12-hour digital clock. The design is fairly straightforward and relies on the truth table of the J-K flip-flop. On resetting, all the outputs go to logical zero but, on clocking, the zero state does not recur.


Ijazur Rehman,  
University of Islamabad,  
Pakistan.

### Speech compressor/limiter

This simple compressor/limiter, which was developed for p.a. applications, uses the voltage-controlled attenuator designed by D. Self, *Wireless World*, December 1975. Resistor R<sub>1</sub> sets the threshold voltage and the compression law. The output signal from the attenuator is made as large as possible by the inverting CA3130 before being applied to the rectifier and low-pass filter. This minimizes the effects of diode non-linearities and capacitor leakage. The low-pass filter is necessary to obtain a fast attack time of around 500µs and long decay time of about 1 min.

The circuit was used successfully with a microphone in a p.a. system with no noticeable distortion. Bandwidth of the circuit is 15Hz to 25kHz.

M. B. Taylor,  
Kingston-upon-Hull.

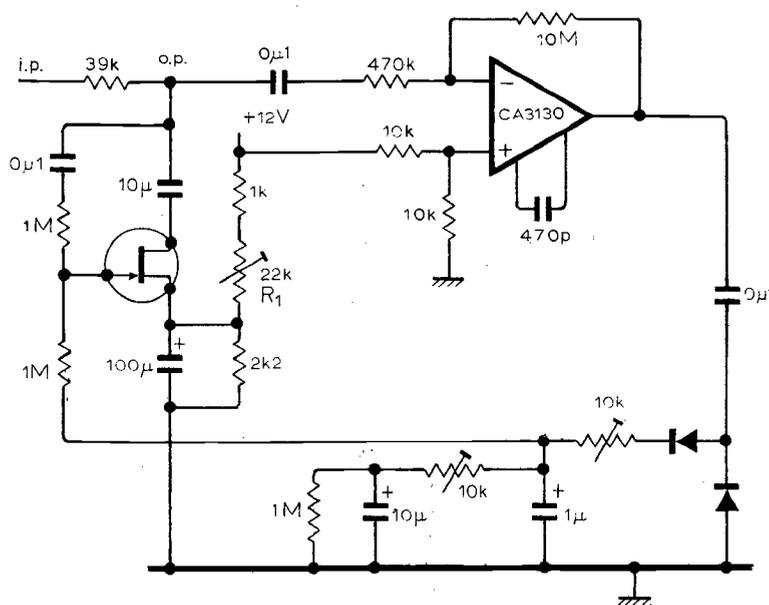


## Pulse-counting frequency comparator

With two periodic signals of nearly equal frequency, it is easy to generate their beat frequency and make it drive a pulse-counting discriminator. This produces an output voltage linearly proportional to the modulus of the difference frequency. The circuit shown works on the same principle but the output is positive or negative according to which input is at the higher frequency.

The Schmitt triggers and dividers convert the inputs to square waves of unity mark-space ratio. These i.c.s may be omitted if the inputs are already suitable, in which case divider (a) must be replaced by an inverting gate. Unity mark-space ratios are desirable if operation over the maximum range of beat frequency is required.


Dividers (c) and (d) produce two square waves in quadrature at frequency  $f_1/4$ . The interconnection of (c) and (d) ensures that the quadrature wave is always lagging. These waveforms together with  $f_2/4$  drive two D-type flip-flops as shown. The outputs at points X and Y define four possible states. Monostables (s) and (t) feed positive and negative-going pulses respectively, of constant area into a summing and integrating network to produce the desired output.

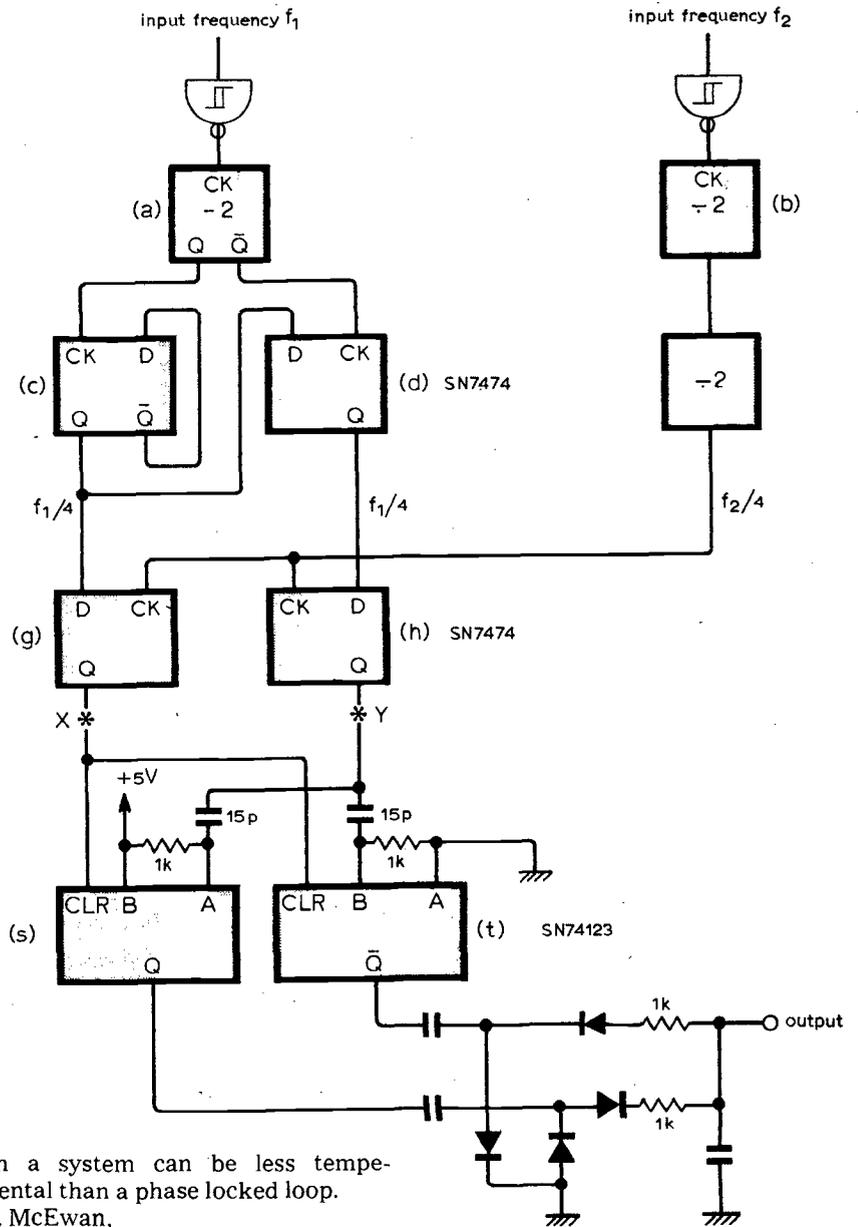The output is proportional to the frequency if  $f_2$  lies between  $4/5 f_1$  and  $4/3 f_1$ . There is negligible offset on the output voltage because when the inputs are phase locked, neither monostable is triggering. The circuit can be used in frequency servo-systems where a signal has to be locked in frequency, though not in phase, to a reference frequency.




Such a system can be less temperamental than a phase locked loop.  
N. J. McEwan,  
University of Bradford.

## B.c.d. converter

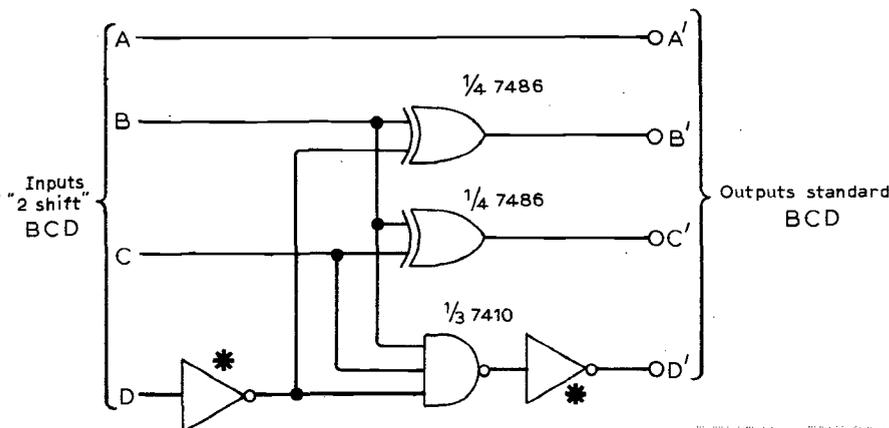


Conversion of "2 shift" b.c.d. to standard b.c.d. can be achieved with the circuit shown. Circuits which drive "Nixie" tubes or similar decimal displays may be economically converted for driving other displays such as seven segment i.e.d. types via a decoder driver i.c.

P. M. Weston,  
Birkenhead, Merseyside.

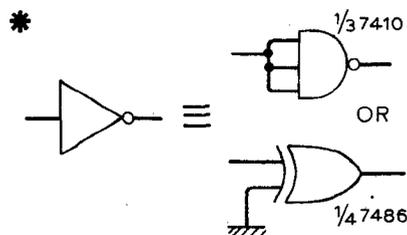
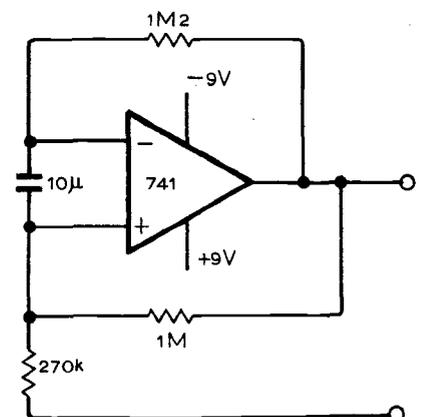
## Unusual sinewave generator

With the values shown the frequency is about 3.8kHz.  
Jorge S. Lucas,  
Brazil.



# A new tomography machine

Machines still appearing despite slowdown in the medical equipment scramble.

by John Dwyer

A company with less than 100 employees has launched what they say is "a diagnostic instrument complementary to the much publicised EMI scanner, but costing only a quarter of the price." Mr Anthony Bernard, managing director of J&P Engineering (Reading) Ltd, said in a statement: "We will be competing for sales with the EMI scanner, but in an ideal world the two pieces of equipment would be used together to provide an entirely new dimension to diagnosis." The price is £65,000.

The Tomoscanner uses a different technique from that exploited by EMI. Instead of measuring the degree to which certain tissues absorb external X-rays, the Tomoscanner measures the concentrations of injected chemicals within the body. This is known as an "invasive" technique. In a process called 'labelling,' radioisotopes are bonded to the molecules of the pharmaceutical used and radioactivity in a series of points in the organ under study is measured. Gamma ray photography has been used since the early '60s, but the resolution of the plots achieved with it has been notably less than seems possible with the Tomoscanner method, and it is only the use of a computer that enables the construction of a section through the patient. The radioactive dose the patient has to take is "comparable with a normal chest X-ray," according to technical director John Eppstein.

## Dual detectors

The patient lies on a padded plywood couch between two sensors placed at either side of the couch so that they can either rotate through a circle with the patient at the centre, or, for rectilinear scans used to build up a conventional profile, move in two parallel planes with the patient between them. The whole apparatus can be moved down the couch to take scans of any part of the body, though most of the clinical experience with the Tomoscanner, some 1,000 case histories over the last 18 months according to J & P, has been gained with brain scanning.

The detectors are sodium iodide, and the field of view is 40cm by 40cm. Using



*J & P Engineering's Tomoscanner. The two detectors are shown tilted at about 45°. They are each capable of detecting two different activity-level isotopes. The movements of the detectors, either around the patient, along her body or in two parallel planes at either side, can be controlled by a small hand-held device connected to the scanner.*

the moving couch for bone scans the field of view can be extended to 40cm x 160cm. The scanning speed is adjustable from 0 to 5cm with line spacings of 1.7, 2.5 or 3.4mm. Each detector can differentiate between two types of isotope, so that in the case of organs such as the liver and spleen, which may need to be viewed together but which absorb different pharmaceuticals, addition and subtraction can be used to differentiate between the two and to view them together.

In normal use, a rectilinear scan is first taken of, say, the upper half of the head. Each detector will provide a profile of one side of the head, or a view of the front or back. Once any abnormal features are seen on any of these scans, the Tomoscanner can take 30 angled views around the head in any plane through it. The information from each

of these scans is processed by a computer which assembles a printout showing a section about 12mm thick through the head in that plane. "The section image is computed as an 80 x 80 cell matrix, and is subsequently interpolated and played back as a 160 x 160 cell picture for display purposes." The printout is the same size as the patient's head. J & P say a typical scan lasts seven minutes, with another three for computing and plotting time. The printout can be in a scale of nine colours or a corresponding gray scale on X-ray plates.

J & P say the advantage of the method is that it shows only the organs under investigation, unlike the X-ray method, which shows up a lot of extraneous detail. "Experience . . . shows that the section view confirms lesions which are equivocal in other scans, and helps to distinguish between cerebral infarcts, subdural and extradural haematoma."

## Rivalry

J&P stress they have no wish to suggest that their machine in any way supercedes the X ray scanner, but EMI have taken exception to the ambiguity of a phrase in the J&P press statement saying: "the complementary isotope mission technique can yield more valuable clinical data of the physiological and biochemical processes for the same view." Neither do they see how it can give more physiological data than the X ray method. Linked with that, EMI say they see little point in trumpeting the selective nature of the Tomoscanner. If EMI want to show a particular organ, they say, they just use the appropriate part of the X ray scan, which can be altered in size to concentrate on chosen areas.

At a somewhat higher level of argument, one source involved in similar research described the Tomoscanner as "a backward step." Asked why, he said that it went against the general tendency to lower the radioactive doses administered to patients, with the eventual aim of using totally non-invasive techniques which can carry out all the clinical procedures needed without any danger or discomfort to the patient

at all, however slight. If isotopes of very low radiation were used absorption and scattering in the tissues between radiating organ and detector caused loss of resolution.

### Scan times

In the case of the Tomoscanner there is also the problem of long scan times. American machines, admittedly a very great deal more costly than either that or the EMI machine, can scan the patient in under 5s, well within the time that most patients can hold their breath. But in seven minutes, the Tomoscanner scan time, the body will make involuntary movements which produce a blurred image. That is one reason why early machines, such as the original EMI machine of early 1972, could only scan the head, which can be held still. The current EMI machine can scan in 20s, a considerable reduction on the original 4½ minutes.

Shorter scan times can be obtained by greatly increasing the number of detectors and, if an X-ray technique is being used, rotating the source to scan the detectors through the patient. This adds considerably to the cost, however, since the detectors may be the most expensive part of the device. A General Electric machine developed in the US used 320 Xenon detectors and cost \$615,000. The EMI system uses 30 detectors where once there were two.

Another difficulty of whole body scanning is that the range of tissue densities to be handled is so much greater. Yet typically the spread of densities is still very small. Whole blood has a specific gravity of 1.034, fat of 0.93, the liver 1.05, heart muscle 1.04 and breast tissue 0.97.

*Wireless World* asked Dr David Everett of the Medical Research Council's National Institute for Medical Research what he thought of the merits

of the two methods: "The present objectives in diagnostic medicine are towards the investigation of body functions. This is the strongest potential advantage of a radioisotope system over X-rays or ultrasonics, which can only reproduce the structure in the region of interest. The function of organs can be investigated by labelling gases for lung function, iodine for thyroid investigation etc. These are slow processes which can be partially followed with conventional gamma cameras and to some extent by X-ray and ultrasonic techniques, but the study of blood flow in the heart, for instance, poses a problem which we feel could be handled by our 'Compton' camera system. The medical implications of such imaging techniques are immense."

### Compton effect


The X-ray scanners currently in use have beam energies of around 70 keV and, like the gamma ray cameras,

operate mostly in the photoelectric region, the detector measuring simply the number of photons arriving at it normal to the detector.

At higher energies, between about 400keV and 2MeV for sodium iodide, the Compton effect takes over. In 1927 American physicist Arthur Compton was awarded the Nobel Prize for discovering that the trajectory of a photon incident on the electron of an atom in a low atomic weight absorber, in this case body tissue, can be calculated from the change in wavelength of the incident and scattered photons and their change in angle. Because the collision reduces the energy of the incident photon, there is a slight reduction in frequency, the scattered radiation containing both the original and modified wavelengths. This means there is a linear relationship between tissue density and the alterations in energy and direction of the X-ray photon.



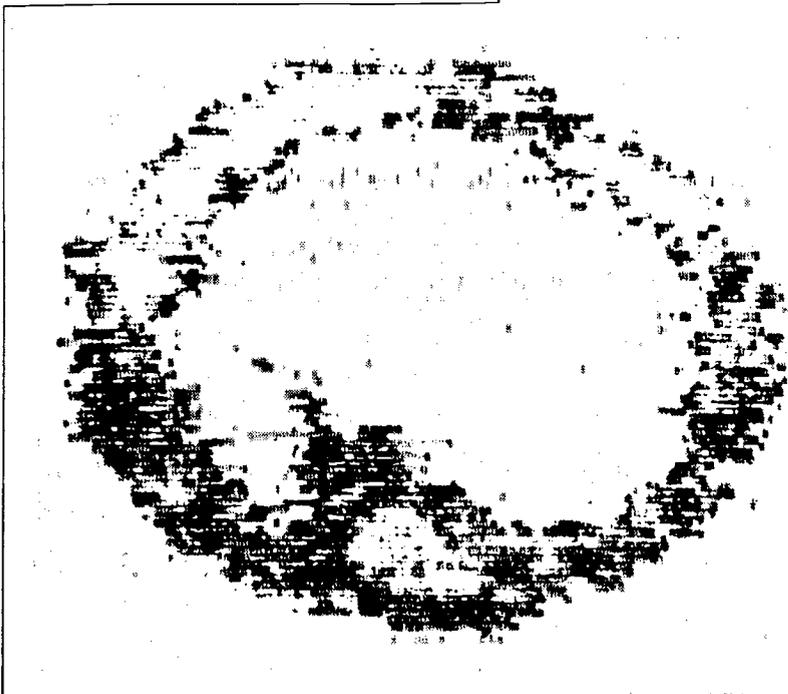A scan of the left side of a patient's head. The lighter areas show high isotope activity, meaning that there has been increased blood flow to these regions where there should be none.



Having obtained the side view, the Tomoscanner is adjusted to take a section through the patient's head at the level of the light spot on the side view. This shows the result, which tells doctors the extent and shape of the abnormality. "Further investigation indicated presence of a parietal cyst associated with a mural tumour," say J & P. The large light area to the right of the left side scan proved to be a scalp lesion due to a plexiform neuroma.

The detectors in present scanners are highly collimated to reduce scatter photons. EMI estimate that only about a thousandth of the particles reaching the detectors are used in building up the final picture. The Compton camera, which should be able to produce three-dimensional pictures, is an attempt to use all the particles, including the scatter, and, by measuring their incident angles, build up a picture of their trajectories before they reached the detector. This means using two arrays and observing the displacement the particle undergoes in travelling from one array to the next.

### Schottky arrays

In the Compton camera the detector is analogous to the lens in an optical system, and each photon incident on the detector defines an ellipse on the image plane. The source could be on any point on the circumference of that ellipse. Successive interactions produce a series of ellipses which intersect on the image plane to define a point. This point can be found by direct summation of all the ellipses generated. "It is possible to project images on to a multitude of planes using the same set of measurements, and even to superimpose them to obtain three dimensional images."


The Compton camera detector is based on a lattice of Schottky barrier orthogonal arrays of 0.4mm cubic elements. The elements are Schottky barrier junctions on n-type high resistivity silicon slices. There are 50 slices of silicon each 5cm in diameter and each having an associated energy amplifier, or photomultiplier. The imaging time is about a second. Resolution is about 2.5mm, compared with 8mm on conventional gamma cameras.

This technique is certainly attractive, particularly because of the number of photons being used, each one providing information and contributing to the final picture. But it has drawbacks. EMI say they have already thought about the technique a great deal. The chief scientist at EMI's central research Laboratories, Dr R. J. Froggatt, told *Wireless World* EMI had "done the sums and we are very, very dubious."

He identified two main difficulties: the particles may already have been through two or more collisions before they reach the Compton detector lens so "you're never sure where they're coming from"; and each time you looked at the incident photon, which you had to do twice, you tended to deflect it - it could not be incident on each of the two matrices without something happening to it. Dr Froggatt added, however, that "We're waiting to see whether they can bring it off."
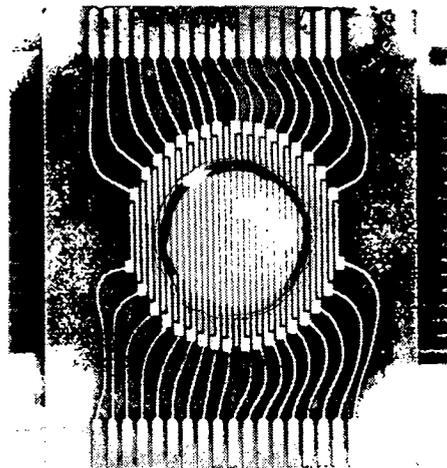
### Scanner business fall

The US congress reported last August that there were about 300 scanners in use in the country and several hundred more on order. A year ago EMI's



*One of the prototype silicon detector elements in the NRDC-funded National Institute for Medical Research Compton camera. Fifty such elements determine the trajectory of a gamma ray from a labelled pharmaceutical by measuring wavelength and path changes in photons. Southampton University teaching hospital and the National Centre for Alternative Technology were also involved.*

excellent financial record for the year to the end of the previous June was largely attributable to the success of their brain scanner, even before the body scanner had gone into production.

EMI's brain scanner was the first. In October 1973 the American National Biomedical Research Foundation announced a colour, whole body scanner with better resolution, they claimed, than that from a normal X-ray. EMI's body scanner arrived in July 1975, and by September press reports in American journals were reflecting the growing size of the scanner bandwagon.

Digital Information Sciences Corporation began to make the scanner developed by NBRF, and it was marketed in the US by Pfizer medical systems. Ohio-Nuclear made another scanner which Siemens marketed in Europe as well as their own Siretom scanner. Ohio-Nuclear told the American journal *Electronics* in September 1975 that they expected to sell \$50 million worth to Siemens alone. The world wide market at this time was estimated at around 10,000 units a year, with an average price of perhaps \$0.5 million each. General Electric jumped in with their 5s scanner and, in a single week in December that year, half a dozen new makers of scanning equipment announced their products.

### Medical instrument legislation

There has been growing concern in America about the proliferation of scanners, and it has been suggested that patients are not benefiting as greatly from that proliferation as they might. The same congressional report said that each machine scanned 12 patients a day

at a charge of at least \$200 per scan. So Americans now appear to be spending at least \$200 million a year on scanning although, the report says, many more scans are being made than can be accounted for by substitution for previously available techniques. The implication is clear: that some patients are paying for scans they don't need.

Linked with this is the enactment of the 1976 Medical Device Amendments to the Food, Drug and Cosmetic Act. The amendments followed agitation by the Association for the Advancement of Medical Instrumentation as far back as 1969, and the setting up by the department of Health, Education and Welfare of a study group under the chairmanship of the director of the National Heart and Lung Institute, National Institutes of Health, Theodore Cooper. The Cooper report advocating legislation to improve safety was published in September 1970, and various bills were introduced in congress over the following years, as well as bills sponsored by the administration, but because of delays caused by Watergate, among other things, it was not until May last year that the legislation was signed, by President Ford.

### Devices "too exotic"

The Amendments will oblige manufacturers to establish the safety and effectiveness of their products to the satisfaction of the food and drugs administration before they are marketed. The journal *IEEE Spectrum* reported in January that "compliance with this new law may result in increases in the costs of medical devices. And ... real questions have arisen as to the cost benefit and cost effectiveness of such expensive equipment."

Throughout the seventies doctors have been criticising the standards of medical instruments. In 1973 the *Electronics* interviewed 12 doctors, most of whom said that "the electronics industry has a tendency to place too much emphasis on exotic devices with little or no legitimate applicability, while insufficient stress is placed on a variety of urgent problems, some of which appear to be mundane." There was concern that in the welter of instrumentation the patient might be forgotten.

Dr Froggatt of EMI says he thinks it would be difficult to prove that there was any racketeering in X-ray scanning, but he felt the British public were well protected in any case because there were very many fewer patients paying for their own treatment. In addition, he thought that scanning had provided a useful amount of clinical information.

Whatever doubts may be being expressed elsewhere, J & P are gearing up for a boom. Managing director Anthony Bernard said in a statement: "If the Tomoscanner generates the global attention we expect, then a large and rapid expansion is in prospect."


# New Products

## Terminal covers

A range of insulating terminal covers, from Highvol Connectors Ltd, have been developed to comply with international safety regulations. The covers are preformed and require no heating or chemical agent for attachment to their terminals. The range includes many different covers to suit wire and cable terminals of most shapes and sizes. Highvol Connectors Limited, Uddens Trading Estate, Wimborne, Dorset BH21 7NL.  
**WW301**

## Digital multimeter

In addition to a 3½-digit, 11mm l.e.d. display, the 460-3 multimeter has a calibrated analogue meter, intended for nulling and scanning peaks and variations. The meter has 32 overload-protected, push-button ranges giving five direct voltage ranges up to 1000V, five alternating voltage ranges up to 600V, six a.c. and six d.c. ranges, both up to 10A, and five resistance ranges up to 2MΩ. There are also five low-power

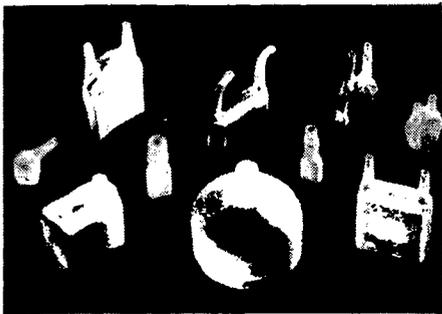

WW301



WW 302

resistance ranges up to 2MΩ. Accuracy on all direct voltage ranges is ±0.1% of reading plus one digit. The instrument, available in either mains/rechargeable battery or mains only, is priced at about £200. Bach-Simpson (UK) Limited, Trentant Industrial Estate, Wadebridge, Cornwall PL27 6HD.  
**WW302**

## Crystal frequency sources

Small plastic encapsulated crystals, in the SPXO range from Cathodeon Crystals Ltd, provide a stability of ±0.002% over the range 4 to 10MHz, operating in the temperature range -20 to +70°C. Pin positions are on a standard 0.1in grid but a variety of mounting arrangements are also available. Cathodeon Crystals Limited, Linton, Cambridge CB1 6JU.  
**WW303**

## Inductance bridge

The model B324, from Wayne Kerr, is a low-inductance bridge suitable for measuring audio-frequency coils, as used in amplifiers, filters and telecommunication circuits. The unit provides a choice of three switch-selected measurement frequencies, 400Hz, 1kHz and 10kHz, and an adjustable test signal level. An aperiodic high-gain amplifier is used as the detector and provision is made for the connection of an external tuned detector for specialized tests. On its most sensitive range, the discrimination available from the B324 is 1nH and 100μΩ. Top values measurable are 1.111H and 11.11kΩ. The bridge is subject to a maximum error of 0.25% up to 10mH and 1kΩ, increasing to 0.5% for measurements of higher values. Wilmot

Breeden Electronics Limited, 442 Bath Road, Slough SL1 6BB.  
**WW304**

## Power supplies

A series of chassis-mounting power supplies, from Datel Systems, comprises two single-output models, types UCM5/1000 and UCM5/2000, and three dual-output models, types BCM15/100, BCM15/200 and BCM15/300. The UCM models are designed for digital applications and have outputs of +5V d.c. at 1 and 2A respectively, with line regulations of 0.05% max, load regulations of 0.1% max. and output ripples of 1mV r.m.s. max. The BCM models are designed for linear applications and these have outputs of ±15V at 100, 200 and 300mA respectively, with line regulations of 0.02% max., load regulations of 0.05% max. and output ripples of 2mV r.m.s. max. Units are encapsulated in a phenolic case measuring 3.5in long by 2.5in wide and up to 1.56in high. Datel Systems Incorporated, 1020 Turnpike Street, Canton, Mass. 02021 U.S.A.  
**WW305**

## Mains capacitors

A range of paper and foil Duralit capacitors, from Wima, is approved to VDE0560-7 for use between line and neutral (Class X), for 630V ratings, and for use between line and earth (Class Y), for 1000V ratings. The capacitors, which are available in values from 470 to 4700pF, have axial leads and are epoxy resin impregnated for a high ionization inception level. These capacitors can also be supplied for 400 and 1250V. Waycom Limited, Wokingham Road, Bracknell, Berks.  
**WW306**




WW304

## Television aeriels

Three television aeriels, having extra large screen grid reflectors, have been added to the range available from Jaybeam Ltd. Type MSG-8 has eight-by-four directors, type MSG-15 has 15-by-four directors and type MSG-21 has 21-by-four directors. In addition to the above, each aerial has two launch directors. These aeriels, which are available for television channel groups A (21 to 24), B (39 to 53) and C (48 to 68), give improved directivity and signal rejection characteristics compared to previous models. Maximum gain figures, referred to a half-wave dipole and measured in accordance with IEE 138A/63 and BASC recommendations, are 14, 16 and 18dB respectively. Jaybeam Limited, Moulton Park Industrial Estate, Northampton NN3 WW307

## Ceramic interference filters

Filters in the 1000 and 2000 series are 100% tested and are suitable for use up to 240V and 400Hz. Type 2000 has a relatively stable dielectric and is for use in military and aerospace applications requiring high reliability and a capacitance change of less than  $\pm 20\%$  over the range  $-55$  to  $+125^\circ\text{C}$ , together with a guaranteed insertion loss over this range. Type 1000 uses a slightly less stable and cheaper dielectric and is suitable for commercial and industrial applications. These filters meet the requirements of MIL-SPEC-202 and MIL-F-15733. Uncased ceramic disc filters, giving up to 10 times as much capacitance per unit volume, are also available. G. E. Electronics (London) Limited, Eardley House, 182/4 Campden Hill Road, Kensington London W8 7AS. WW308

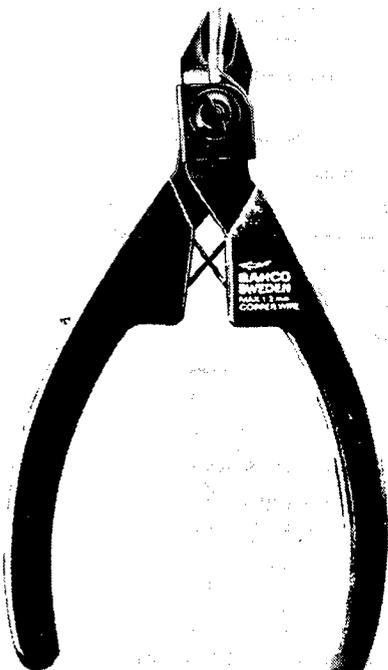

WW 310

## Low profile keyboards

The KL series of low profile keyboards are now available with encoding facilities for dual tone multi-frequency switching, for communications applications, and row and column formats for microprocessor systems. These keyboards, called Minikeys, have precious metal contacts with ratings of 50mA at 28V d.c. resistive. The top of each key on the Minikey extends only 1.78mm from the face of the keyboard and has a travel of 1.27mm. Total keyboard depth is less than 3.12mm. Tactile "feedback" is by a mechanism which ensures fast positive closure of the contact. Prices for a one-off are from £5.20. Digitran Endevco UK Division, Melbourn, Royston, Herts SG8 6AQ. WW309

## Wire cutters

Two low-cost side cutters, types 2131 and 2132 from Bahco Tools Ltd of Sweden, are produced by blanking instead of forging, depending on grinding and heat treatment for the cutting edges. Bahco claim that the useful life of the cutters, which cut copper wire from 0.3 to 1.2mm dia., is comparable to that of more expensive forged patterns. Type 2131 has a bevel on the outer face of the jaws, while type 2132 has no bevel and may be used for flush cutting. The pliers have polypropylene grips for comfort, and include a detachable clip which holds the wire off-cut after each operation. Prices are £6.38 each. Bahco Tools Ltd, Bahco House, Beaumont Road, Banbury, Oxon. WW310

## Low-loss soft ferrites

Ceramag 24B is a ceramic ferrite material which, it is claimed, offers a reduction in losses of 30% at

16kHz and 25% at 60kHz, with no changes in permeability or saturation. In addition, losses are lowest in the range 85 to 95°C. A wide range of these cores is available, including E-cores with heights of 0.937in and lengths up to 4.062in, and toroids up to 5.938in outside diameter. Walmore Electronics Limited, 11-15 Betterton Street, Drury Lane, London WC2H 9BS. WW311

## 10MHz oscilloscope


The VP-5100A is a general-purpose 10MHz oscilloscope having nine calibrated ranges from 10mV/div. to 5V/div. A variable control allows continuous variation between steps up to 12.5V/div. In addition to seven calibrated sweep rates, from 0.1 $\mu\text{s}$ /div. to 0.1s/div., the timebase provides a mode for viewing composite TV signals. Telonic Altair UK, 2 Castle Hill Terrace, Maidenhead, Berkshire SL6 4JR. WW312

## Strain gauge indicator

The Doric 420 Digital Indicator displays the output of strain gauge devices in engineering units. This instrument can be used to measure pressure, torque, thrust and force, etc., with a resolution of one part in 10,000. The sensitivity is adjustable from 1 to 12 $\mu\text{V}$  per increment. Five 0.63in l.e.d.s provide the display. Lee Engineering, Napier House, Bridge Street, Walton-on-Thames, Surrey KT12 1AP. WW313

## Miniature slide switch

A single-pole, double-throw slide switch, type 1101, is said to be capable of breaking 6A at an alternating voltage of 120V or a direct voltage of 28V. The

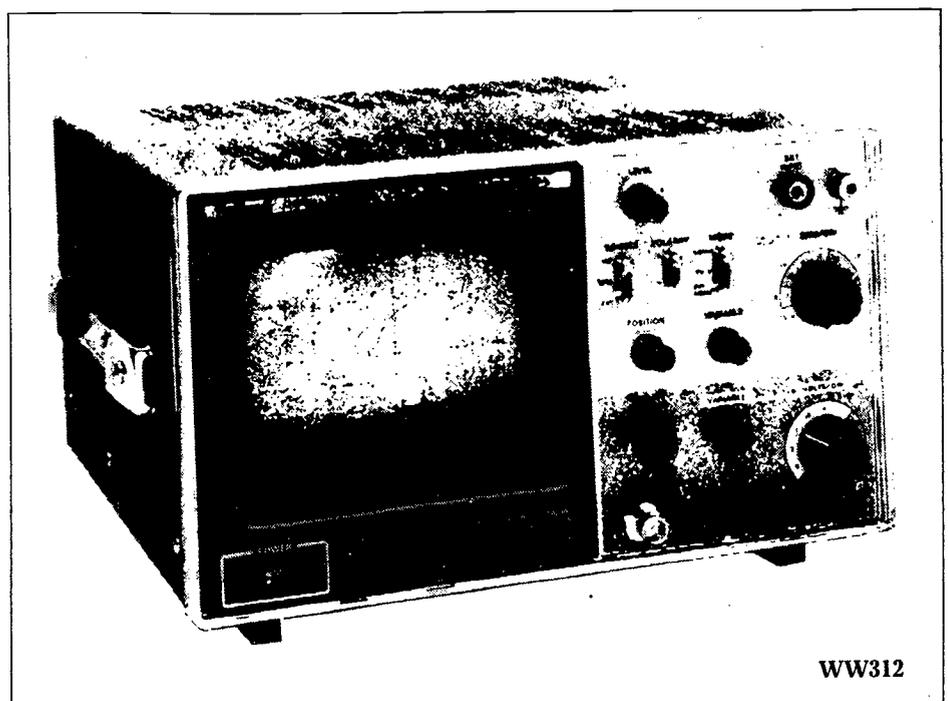

WW312

switch, which incorporates the C & K toggle mechanism, measures  $0.5 \times 0.26 \times 0.25$ in and may be mounted directly on to a p.c.b. Typical characteristics include a maximum contact resistance of  $10m\Omega$ , minimum insulation resistance of  $100G\Omega$  and dielectric strength of  $1kV$  r.m.s. Roxburgh Electronics Limited, 22 Winchelsea Road, Rye, Sussex.

**WW314**

### Microwave absorber

A flexible microwave absorber called Eccosorb RMP is intended for frequencies of 2.4GHz and above. The absorber, available in silicone rubber (RMP-S-75) or vinyl rubber (RMP-V-75), is a mould of pyramids each having a height of about 2.5cm and a base of about 2.54cm square. The silicon product is fabric reinforced and is preferred for high temperature, high power and airborne applications. The vinyl absorber is more rugged and is intended for outdoor use. Both products have nominal reflectivities of 17 to 20dB down, over the useful frequency range, and are supplied in 30.5cm square sheets. Both absorbers conform to curvature, can be bonded in place and cut with a knife. Neither product will support combustion. Emerson & Cuming (UK) Limited, Colville Road, Acton, London W3.

**WW315**

### Programmable pulse generator

A programmable pulse generator, designated as model EH1501A/129, is specifically designed for e.c.l. and other high speed applications. The programmable output stage can deliver positive or negative pulses of up to 2V amplitude and  $\pm 1V$  offset with rise and fall times of less than 500ps at full amplitude. This generator has a programmable fre-

quency of up to 50MHz. A variety of programming interfaces are also available and include the IEC 488 and facilities such as memory read-out or optical isolation. Elex-Electronics, 22-24 Bell Street, Henley, -on-Thames, Oxfordshire RG9 2BG.

**WW316**

### Piezo-electric sounder


A long-life, low-power piezo-electric sounder, the U3-50R, generates a single tone in excess of 85dB at a rated current of 8mA and rated voltage of 24V. The sounder, which is 60mm square and 10mm deep, has no moving parts and is claimed to have a life of 1000h, compared with about 50h for a conventional electro-mechanical bell. ITT Components Group Europe, Standard Telephones and Cables Limited, Edinburgh Way, Harlow, Essex.

**WW317**

### Spectrum analyser

A spectrum analyser, from Court Acoustics, uses a 28 by 11 i.e.d. matrix, measuring  $14 \times 4$ in, to provide an easy-to-read real-time display of audio frequencies from 28Hz to 20kHz with standard ISO centre frequencies from 31.5Kz to 16kHz. An extra i.e.d. display reads the full programme level, in dBm on line settings and in s.p.l. on microphone settings. Facilities are included for a 2.5ms attack and decay, a 2s decay, peak accumulation readings and display storage. The unit has a digital pseudo-random noise generator with a word length of 16Mbits which can provide pink or white noise to an isolated socket. On pink noise an output of 20Hz to 20kHz  $\pm 0.5$ dB is available with a peak-to-mean ratio of 4:1. Court Acoustics, 50 Dennington Park Road, West Hampstead, London N.W.6.

**WW318**

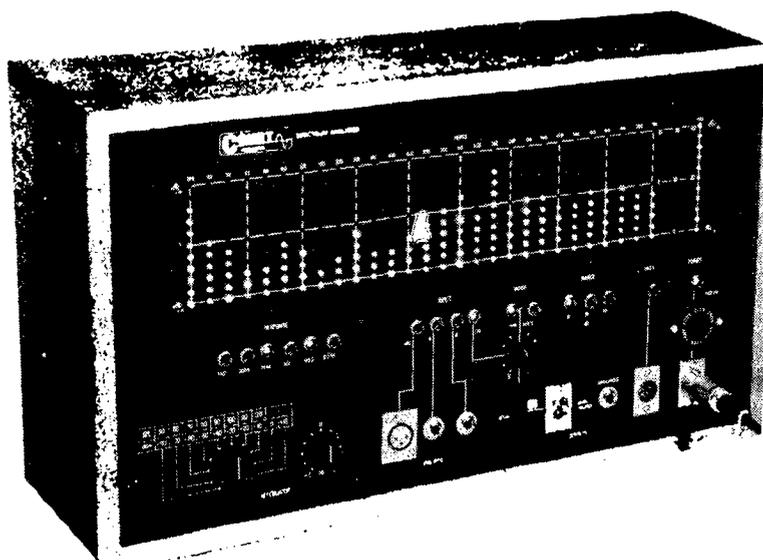

**WW318**

### Low-cost logic wiring system

The Wire Distribution System, from Zartronix, uses solderable synthetic enamel wire (36 s.w.g.) for producing prototype logic circuit boards. The point-to-point wiring is retained by moulded distribution strips which may be used for any desired i.c. packing density. Two types of strip are available: a general purpose moulding which can be used on all types of circuit board (when used with a quick-set adhesive), and another, designed specifically to press fit into any board with 1mm dia. holes on a 2.54mm pitch matrix. The versatility of the strips ensures that there is no restriction on size or type of prototype breadboard used. An introductory kit is available and consists of wire distribution strips and pencil, a spare spool, i.c. leg deformer, circuit board and a comprehensive instruction leaflet. Zartronix, 115 Lion Lane, Haslemere, Surrey.

**WW319**


### Wire-wrapping tool

A battery-operated wire-wrapping tool from Vero Systems Ltd, is designed for 0.63mm square terminals using 0.25mm wire. The tool, priced at £32.50, is fitted with a bit and sleeve so that  $1\frac{1}{2}$  turns of insulation are wound around the terminal before the bare-wire wrap is made. A built-in device prevents overwrapping and the unit is self-indexing to simplify use and provide a constant wire turn consistency. The tools are moulded from impact resistant material, weigh 11 oz and can be supplied with rechargeable nickel-cadmium batteries and a charger. Vero Systems (Electronic) Limited, 362a Spring Road, Sholing, Southampton.

**WW320**



**WW319**

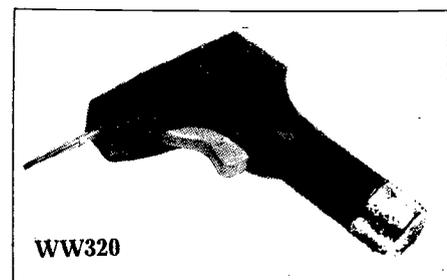

**WW320**

## Breakdown voltage tester


An instrument, available from Stoneleigh Electronics Ltd, has been designed for determining the voltage breakdown characteristics of transistors, diodes, neon lamps and other semiconductor devices. The device to be tested is placed across the test terminals of the instrument and then a constant current source, which can be set within the range of 1 to 15mA, is applied to it. This source has an output potential of up to 300V. The breakdown voltage is then displayed on a voltmeter which has switched ranges of 10, 30, 100 and 300V f.s.d. The instrument, which can also be used to check voltage ratings of semiconductor devices, has a polarity switch allowing forward and reverse characteristics to be checked quickly. Stoneleigh Electronics Limited, Mawney Road, Romford, Essex RM7 7SE.

WW321

## Infrared pyroelectric vidicon

The P8092 is a lin vidicon which is sensitive to infrared radiation from 1.8 to 1000 $\mu$ m, with optimized performance in the 8 to 14 $\mu$ m band. When used with a high-performance lens, this tube can resolve increments in scene temperature of less than 0.2°C. The tube has a spatial resolution capability of 300 TV lines, and deuterated triglycine-sulphate target having a useful diameter of 18mm. The P8092 requires no gas coolant or mechanical scanning system and it has a fully compatible TV output signal. English Electric Valve Co. Limited, Chelmsford, Essex CM1 2QU.

WW322

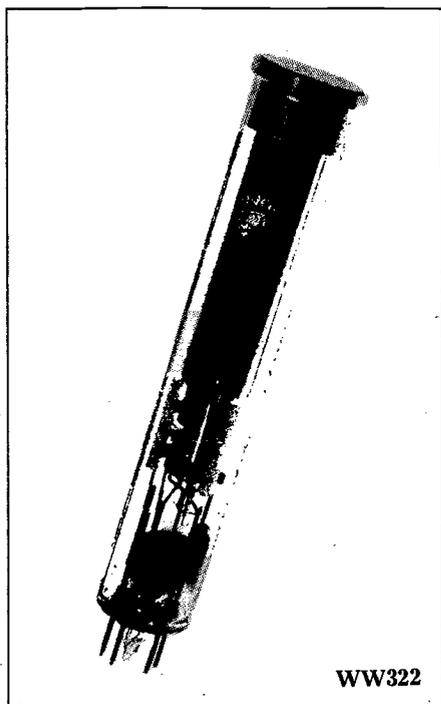

WW322

# Solid State Devices

## High-power switching transistors

Four transistors, designated as RCA-2N6338, 2N6339, 2N6340 and 2N6341, have maximum rise and fall times of 0.3 and 0.25 ns respectively at a collector current of 10A d.c. Voltage ratings are high, for example  $V_{CB}$  (max) for the 2N6341 is 180V. For an  $I_C$  of 10A,  $V_{BE}$  (sat) is only 1.8V and with an  $I_C$  of 25A a high gain is maintained and a minimum forward-current transfer of 12 is obtained. The devices are in hermetic steel TO-3 packages. RCA Solid State-Europe, Sunbury-on-Thames, Middlesex TW16 7HW.

WW323

## Fast-recovery rectifiers

A range of fast switching rectifiers, designated as the RGP series, has devices rated at 1, 1.5, 2 and 3A with peak-inverse voltages between 50 and 1000V. The rectifiers, which are claimed to meet all international requirements, have recovery times varying from 150ns for 50V types to 500ns for 1000V types. Typical reverse leakage currents are less than 1  $\mu$ A. In all cases the peak forward surge currents are at least 30 times the rated value. The devices comply with UL flammability classification 94V-0 and generally exceed the environmental MIL-Std-19500/228. General Instruments UK Limited, Cock Lane, High Wycombe, Bucks.

WW324

## Field programmable logic array

Two military-range versions of industrial programmable logic arrays (f.p.l.a.s.) are now available from Mullard. Type S82S100 has a three-state output and type S82S101 is an open-collector version. The Schottky-t.t.l. devices employ nichrome fuse technology and have typical power dissipations of 600mW and maximum access times of 80ns. Signetics IC Marketing Group, Mullard Limited, Mullard House, Torrington Place, London WC1E 7HD.

WW325

## V.h.f. m.o.s.f.e.t.

The BF327 is a protected-gate depletion mode m.o.s.f.e.t. suitable for use in v.h.f. amplifier and mixer circuits. It has a low feedback capacitance of 0.03pF, a low noise figure, typically 2.3dB, and offers high gain. The plastic encapsulation reduces manufacturing costs without

impairing performance and conforms to the outline requirements popularly adopted as the European standard for these v.h.f. and u.h.f. devices. Mullard Limited, Mullard House, Torrington Place, London WC1E 7HD.

WW326

## R.f. transistor

The BFT96 transistor has been added to the range of silicon p-n-p devices available from SGS-ATES. This transistor is a driver or medium power amplifier giving linear outputs up to 0.5V across 75 $\Omega$  at 1GHz. By using the BFT96 with the BFT95 (see New Products August 1976) as the first stage in a wideband amplifier, typical noise figures of 2dB can be obtained between 40 and 1000MHz. The two devices may also be used for medium-power complementary applications for centralized antennae systems. SGS-ATES (UK) Limited, Walton Street, Aylesbury, Bucks.

WW327

## Planar transistor

The BFW92, from SGS-ATES, is an n-p-n silicon planar transistor designed for use in broadband amplifiers. It offers low noise (4dB at 500MHz) and low cross-modulation with a high  $f_T$  (1.6GHz). The package is in a common-emitter configuration and offers reduced parasitics for u.h.f. applications. SGS-ATES (UK) Limited, Walton Street, Aylesbury, Bucks HP21 7QN.

WW328

## Avalanche diodes

Two silicon planar epitaxial controlled-avalanche diodes, types BAW21A and BAW21B, are fast switching devices intended for use in general applications where transients occur, or where a very steep forward characteristic is required. Avalanche breakdown voltages are 90 to 150V for type A and 120 to 175V for type B, at an  $I_r$  of 100 $\mu$ A. The diodes, in a DO-35 package, have maximum rectified forward currents of 0.4mA when averaged over a 20ms period. Mullard Limited, Mullard House, Torrington Place, London WC1E 7HD.

WW329

## Impatt diodes

Two Read-profile Impatt diodes, types MS927A and MS927B, are intended for operation from 12 to 14GHz. The MS927A offers a power output of 2.5W minimum at 20% minimum efficiency and the MS927B is for 1.5W minimum at 15% minimum efficiency.

Walmore Electronics Limited, Microwave Division, 11-15 Betterton Street, Drury Lane, London WC2H 9BS.

WW330

SEW analogue panel meters are now available ex-stock (compared with 6-8 week delivery date from competitive manufacturers). And that's not the only advantage to buyers now ITT Instrument Services are sole UK stockists and distributors.

You also enjoy big choice of types, in-depth stocks, smooth streamlined progressing of your order and of course, a friendly personal service.

- Broad range of sensitivities and sizes.
- Low individual cost\* with attractive quantity discounts.

■ Special scales to meet individual customer requirements on quantity orders.

■ Precision construction with high quality pivot and jewel movement.

■ Choice of moving coil, rectified moving coil and moving iron movements to suit applications.

Edinburgh Way, Harlow, Essex.


Tel: Harlow (0279) 29522 Telex: 81525

**ITT instrument services**

THE ONLY WAY TO BUY.

# Analogue Panel Meters. Only SEW and ITT give you all this.

\*From £4 one off to £2.66 for 1000+

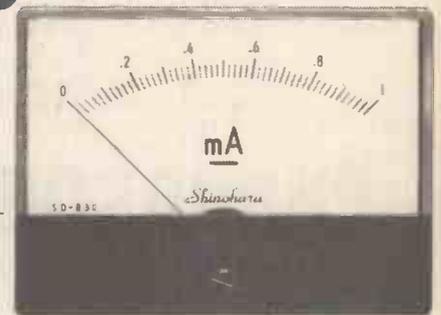

WW-045 FOR FURTHER DETAILS

## Put new life into your equalising ....



## With the Trident Parametric.

THE TRIDENT MODEL CB9066 PARAMETRIC EQUALISER/FILTER is a comprehensive equaliser offering the user a degree of flexibility in tone correction hitherto unavailable. The five sections of the Equaliser can be used simultaneously. Silent switch operation enables the facility to be used during critical applications such as Disc Mastering, Re-Mixing, etc.

### FEATURES:

- Low, Mid and High range, continuously variable control of Frequency, Amplitude and Q.
- ★ Separate High-Pass and Low-Pass Filters with continuously variable control of Cut-off frequency and slope.
- ★ Silent IN/OUT switching of ranges and system.
- ★ Automatic compensation for sharp and broad Q settings adjusts for apparent loss of loudness in sharp Q modes.
- ★ Compact 19in. x 1 1/4in. x 8in. rack mountable.
- ★ Built-in Power Supply.

Send for details to:  
**Trident Audio Developments Ltd.**  
 Sales Office: 36-44 Brewer Street  
 London, W.1  
 Tel. 01-439 4177. Telex 27782 Tridisc.



### United States Agents:

**East Coast:**  
**Audiotechniques Inc.**  
 142 Hamilton Avenue, Stamford, Conn. 06902  
 Tel. (203) 359 2312  
 Contact: Adam Howell.

### West Coast:

**Studio Maintenance Service**  
 2444 Wilshire Blvd., Suite 214, Santa Monica  
 Ca. 90403  
 Tel. (213) 990 5855  
 Contact: David Michaels

# The Finest —

The "S.K.A." Plastic Keyboard was developed by Kimber Allen Ltd in co-operation with a Swedish company and the manufacturers state that in their opinion it is the finest moulded plastic keyboard made and is not to be confused with cheaper keyboards available.

The keys are moulded in Acrylic plastic, a material chosen for its hard wearing properties and ideal feel to the touch. They are moulded in two parts, the key face, which has to be perfect in appearance and finish; and the action, which has to be strong and carry the mechanism. The strong section of aluminium extrusion upon which they are mounted is specially designed to take all the pressures of playing. Springs, felts, and contact actuators are supplied ready-fitted.

The contact assemblies are constructed of laminated bakelite, thus giving smooth slot walls and completely free movement of the gold-clad contact wires. Types available as follows (Contact pairs normally open):

GJ-SPCO: 24p each GE-4 pairs : 45p each  
 GB-2 pairs: 27p each GH-5 pairs : 57p each  
 GC-3 pairs: 36p each 4PS-SPCO & 3prs: 53p ea

Palladium Wire Bus Bars — 1 octave lengths : 50p each

We also stock kits and PCBs for the P.E. Synthesiser, P.E. Joanna (electronic piano), P.E. Minisonic, and other sound synthesising and modifying projects published in Practical Electronics. Send SAE for full list (Overseas send 40p).


## PHONOSONICS

DEPT. WW75, 22 HIGH STREET  
 SIDCUP, KENT DA14 6EH

# KEYBOARDS



## & CONTACTS

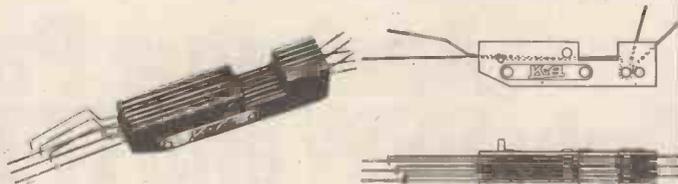

U.K. POST & HANDLING:  
 Keyboards: £1.50 each  
 Contacts:

Orders under £15.00: 25p  
 Orders over £15.00: 50p

37 Note C-C Keyboard :  
 £25.50

49 Note C-C Keyboard :  
 £32.25

61 Note C-C Keyboard :  
 £39.75

VAT: Add 12 1/2 % to final total on all U.K. orders

EXPORT ORDERS ARE WELCOME but please see our price list for Export Postage Rates. N.B. EIRE, CHANNEL ISLES & B.F.P.O. classify as Export.

MAIL ORDER AND C.W.O. ONLY — SORRY BUT NO CALLERS PLEASE  
 Prices are correct at time of Press, E. & D.E. Delivery subject to availability

WW — 006 FOR FURTHER DETAILS

## — TURNER —

STEREO POWER AMPLIFIERS  
 (from 100 watts to 500 watts)



Professional Stereo Power Amplifiers designed and manufactured to the very highest standard.


TURNER POWER is setting a new standard in the studios for ultra-clean monitoring, and with bands on the road for ruggedness and reliability.

Customers include: Air Studios, Wessex Studios, Gooseberry Studios, Lansdowne Studios, Decibel Studios, Queen and leading hire companies.

TURNER ELECTRONIC INDUSTRIES LTD.  
 175 Uxbridge Road, London W7 3TH  
 Tel. 01-567 8472

WW — 040 FOR FURTHER DETAILS

# RELAYS

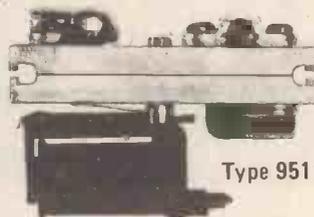

Type 951

**SPECIAL  
 OFFER**

## CO-AX RELAYS For Aerial Switching

- Available with 12V or 24V DC coil
- Single change-over contact
- For use with UR43 co-ax cable
- Characteristic impedance: 50 ohms
- Nominal frequency: 450 MHz
- VSWR approx: 1.1 : 1
- Cross-talk: 39dB
- Contact rated at 1 amp or 50W max.

**£5** EACH  
 Inc. P & P  
 and V.A.T.


When ordering  
 specify operating  
 voltage required.

Offer applies to  
 Gt. Britain and  
 N. Ireland only.  
 Cash with order.

### REL Equipment & Components Ltd.

Croft House, Bancroft, Hitchin, Hertfordshire, SG5 1BU, England  
 Telephone: Hitchin(0462)57181(10lines) Telex: 82431

WW—051 FOR FURTHER DETAILS

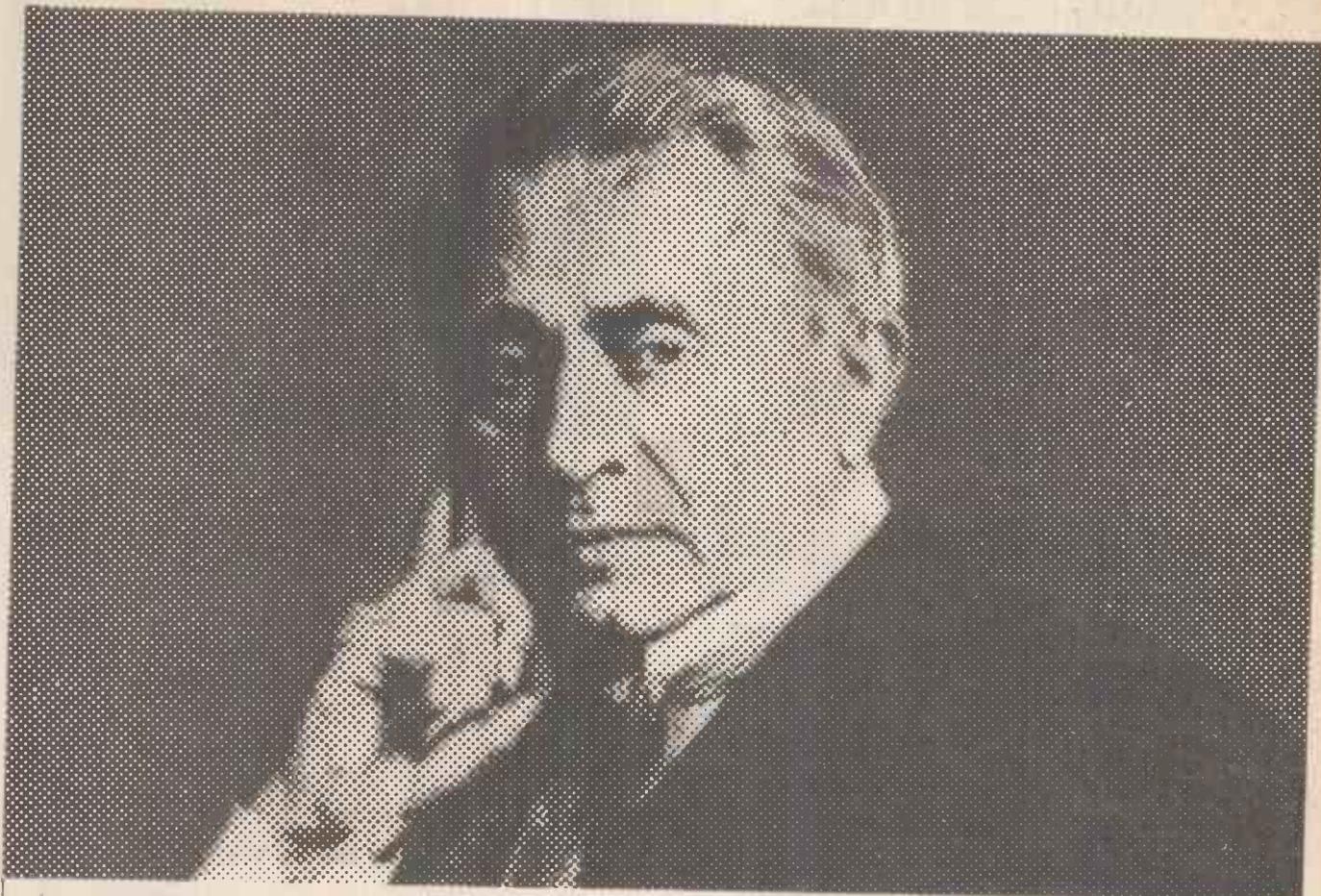

JOSEPH HENRY

# ...The leaders through creativity

## GR 1657 DigiBridge

Automatically measures R, L, C, D and Q. Ranging from  $0.001\Omega$  to  $99.999\text{ M}\Omega$ ,  $0.0001\text{ mH}$  to  $9999.9\text{ H}$ ,  $0.0001\text{ nF}$  to  $99999\mu\text{ F}$ . D from 0001 to 9.999 and Q from 00.01 to 999.9. Basic accuracy 0.2%. Five digit display for R, L and C, four digit display for D and Q.

Microprocessor — directed ranging. Selectable test frequencies of 1 KHz and 100 Hz (120Hz).

Series or parallel measurement selection. Built-in Kelvin test fixture tests radial and axial lead components. Other bridges from our range include:

|               |               |               |                    |                   |
|---------------|---------------|---------------|--------------------|-------------------|
| <b>GR1650</b> | <b>GR1656</b> | <b>GR1608</b> | <b>GR1683</b>      | <b>GR1685</b>     |
| RLC Bridge    | RLC Bridge    | RLC Bridge    | Digital RLC Bridge | Digital RLC Meter |
| Precision 1%  | 0.1%          | 0.05%         | Automatic, 0.1%    | Automatic, 0.1%   |

It is easy to test components with GenRad. Write or call for descriptive literature to GenRad Ltd. Bourne End, Bucks SL8 5AT.  
(06285) 26611



# GenRad

WW-004 FOR FURTHER DETAILS

## SURROUND SOUND KITS

**Demodulator TDM29**  
A new JVC design with improved muting.

**Type A Variomatrix Decoder Synthesizer**  
(with or without SQ Option).

**Decoder**  
Type 3A  
Type 5A

PRICE LIST (VAT in brackets; overseas customers neglect)

|            |                              |         |         |
|------------|------------------------------|---------|---------|
| <b>CD4</b> | Complete kit                 | £35.00+ | (£4.38) |
|            | PCB ICS and coils only       | £18.00+ | (£2.25) |
| <b>QS</b>  | Variomatrix Decoder Kit      | £32.00+ | (£4.00) |
|            | *As above but with SQ option | £36.00+ | (£4.50) |
| <b>SQ</b>  | Type L3A Kit                 | £26.50+ | (£3.31) |
|            | Type L5A Kit                 | £31.50+ | (£3.94) |
|            | PCBs (for both types)        | £6.90+  | (£0.86) |
|            | Master Switch Kit            | £9.50+  | (£1.19) |
|            | 4 Gang Potentiometer         | £2.00+  | (£0.25) |

(Overseas Airmail £4 per kit)

For details send SAE to

**COMPCOR ELECTRONICS LIMITED**  
9 DELL WAY, LONDON W13 8JH. Telephone 01-998 8221

WW-087 FOR FURTHER DETAILS

**CROFTON FOR USED VIDEO EQUIPMENT**

Used Video Equipment bought and sold daily. If we do not have what you want, we enter your requirements on our register and advise you when it is available.

U.H.F. Modulators supplied for connecting a camera directly to a domestic TV or Philips V.C.R. Camera Kits for the enthusiast also in stock.

Fujinon lens available.

Repairs of all types of Video equipment undertaken.

WHATEVER YOUR VIDEO REQUIREMENTS FIRST CONTACT CROFTON

**CROFTON ELECTRONICS LTD.**  
35 Grosvenor Road,  
Twickenham  
Middx. TW1 4AA 01-891 1923

WW-020 FOR FURTHER DETAILS

## Keep holes neat or stop them up.



**HEYCO NYLON SNAP BUSHINGS** convert sharp edges to smooth, insulated holes, quickly and easily. Snap lock into panels. 56 sizes to fit holes from  $\frac{3}{16}$ " to 3" diameter.

**HEYCO NYLON HOLE PLUGS** seal unwanted holes neatly, quickly and easily. Low cost. Rattle-free fit. 25 sizes to fit holes from  $\frac{3}{16}$ " to 2" diameter.

**FREE SAMPLES**

and catalogue showing our full range of bushings on request.



**Heyco Manufacturing Co. Ltd.**

Uddens Trading Estate,

Nr. Wimborne, Dorset BH21 7NL

Tel: Ferndown (STD: 0202) 871411/2/3

Ⓢ Telegrams: HEYCOMAN Wimborne. Telex: 41408

WW-038 FOR FURTHER DETAILS

## TIME + FUEL + EFFORT = MONEY

You can effectively reduce costs by the installation of a STORNO mobile radio system.

To investigate further, write, telephone or telex to

# Storno

RADIO COMMUNICATION SYSTEMS

Storno Limited, Frimley Road, Camberley, Surrey.  
Telephone: Camberley (0276) 29131 Telex: 858154


WW-035 FOR FURTHER DETAILS

## ELECTRONIC DIGITAL CLOCK

**SAME DAY DISPATCH**

ORDERS RECEIVED BEFORE 2 p.m. are posted on the same day.

From this . . . **KIT** — to this

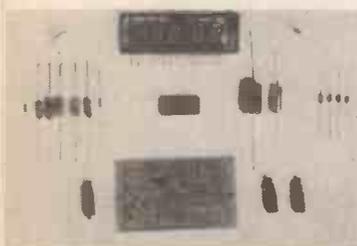

★ **CHRONOMETER ACCURACY WITH SOLID STATE RELIABILITY**

Size 10.5 x 5.7 x 8 cms

**Electronic Digital Timepiece**

in LESS THAN ONE HOUR

A professional product for the home constructor. It has been designed by engineers using the most modern techniques and components. It will appeal both to the confirmed hobbyist and to the man who simply wants to 'have a go'. The kit contains everything except a mains lead. The only tools required are a small soldering iron, solder, screwdriver and wire cutters.

- ★ LARGE BRIGHT GREEN DISPLAY
- ★ ATTRACTIVE ACRYLIC CASE
- ★ 12/24-HOUR READOUT

**£9.60**  
+ 76 Pence VAT

SEND YOUR ORDER TO

**DAVENTRY**

**UXBRIDGE**

**METAC ELECTRONICS & TIME CENTRE**

67 HIGH STREET  
DAVENTRY  
NORTHANTS  
TEL: (032-72) 76545


3 THE NEW ARCADE  
HIGH ST., UXBRIDGE  
MIDDLESEX  
TEL. UXBRIDGE  
(0895) 56961

Cash, Cheque or Postal Order or if you wish to use Barclaycard or Access, simply quote name, address and card number when ordering.

**SHOWROOMS OPEN 9 - 5.30 DAILY**

# The New ETC/2B 'CALPLUG' Electronic Soldering System

From **Litesold**

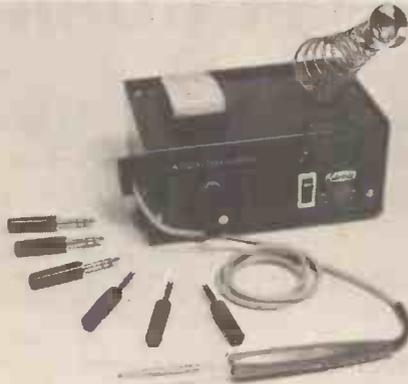

The Litesold ETC/2B provides simple, tamper-proof, electronic temperature control.

- CLOSELY temperature controlled
- INSTANTLY adjustable, yet tamper-proof
- ENTIRELY static and transient free
- LOW voltage DC operated
- INEXPENSIVE and simple to maintain

**LIGHT SOLDERING DEVELOPMENTS LIMITED**  
 97-99 Gloucester Road, Croydon, Surrey.  
 Tel: 01 889 0574 Telex: 8811945

WW — 082 FOR FURTHER DETAILS

# DEMA ELECTRONICS INTERNATIONAL

ELECTRONIC COMPONENTS DISTRIBUTOR FOR INDUSTRY AND HOBBYIST

| SPECIAL SALE PRICED ITEMS   |  |   |  | "SPECIAL PURCHASE WHILE THEY LAST" |  |                                       |  |
|---|--|---|--|------------------------------------|--|---------------------------------------|--|
| <b>LEDS</b>   |  | Panel Indicator Lamp .10 or 3/25        |  | <b>MEMORIES</b>                    |  | 1702 2048 Bit Prom 3.95               |  |
| MV 5020 Jumbo Red or Clear .12 or 3/30                              |  | Red 7 Seg 270" 85 or 3/2.00             |  | 2102 1024 Bit Stat Ram 1.69        |  |                                       |  |
| <b>LINEARS</b>  |  | LM 301K 20 or 3/55 741 .18 or 3/50      |  | <b>CLOCK CHIPS</b>                 |  | 5314 6 Digit MUX 12-24 HR 24 Pin 2.95 |  |
| LM 555 .20 or 3/90 1458 .35 or 3/85                                 |  | LM 556 .69 or 3/1.80 LM 3900 20 or 3/55 |  | 5316 4 Digit 12-24 HR 24 Pin 2.95  |  | 7001 4 or 6 Digit Alarm 3.50          |  |
| <b>CALCULATOR CHIPS</b>   |  | CT 5002 Batt Opp 5001 .59 or 3/1.25     |  | <b>TTL</b>                         |  | 7437 .20 or 3/50 7454 .10 or 3/25     |  |
| CT 5005 12 Digit 4 Func w/Mem .89 or 3/1.45                         |  | 5725 18 Pin 6 Digit MUX 1.75 or 3/5.00  |  | 7444 50 or 3/1.40 7470 .19 or 3/55 |  | 7450 .10 or 3/25 7485 .20 or 3/55     |  |
| 5738 8 Digit 5 Func Mem/Const Floating Dec Batt Oper 1.10 or 3/2.95 |  |   |  | 7451 .10 or 3/25 74123 .35 or 3/75 |  | 7453 .10 or 3/25 74141 .49 or 3/1.25  |  |

| TTL 7400 SERIES |             | NEW LOW PRICES |              |
|-----------------|-------------|----------------|--------------|
| 7400 £ 0.08     | 7440 £ 0.11 | 7485 £ 0.85    | 74155 £ 0.69 |
| 7401 0.09       | 7441 0.58   | 7486 0.25      | 74156 0.69   |
| 7402 0.10       | 7442 0.48   | 7489 1.45      | 74157 0.69   |
| 7403 0.10       | 7443 0.48   | 7490 0.32      | 74158 0.69   |
| 7404 0.13       | 7444 0.60   | 7491 0.55      | 74160 0.89   |
| 7405 0.13       | 7445 0.70   | 7492 0.36      | 74162 0.89   |
| 7406 0.22       | 7446 0.50   | 7493 0.35      | 74163 0.89   |
| 7407 0.22       | 7447 0.65   | 7494 0.40      | 74164 1.05   |
| 7408 0.13       | 7448 0.60   | 7495 0.45      | 74165 1.05   |
| 7409 0.13       | 7450 0.12   | 7496 0.55      | 74166 1.05   |
| 7410 0.09       | 7451 0.12   | 74100 0.89     | 74170 1.65   |
| 7411 0.16       | 7453 0.12   | 74107 0.23     | 74175 0.85   |
| 7413 0.25       | 7454 0.12   | 74121 0.23     | 74180 0.80   |
| 7416 0.22       | 7460 0.11   | 74122 0.37     | 74181 2.00   |
| 7417 0.22       | 7470 0.24   | 74123 0.45     | 74182 0.80   |
| 7420 0.11       | 7472 0.21   | 74145 0.57     | 74192 0.95   |
| 7426 0.23       | 7473 0.25   | 74150 0.75     | 74193 0.95   |
| 7430 0.11       | 7474 0.25   | 74151 0.59     | 74194 0.85   |
| 7432 0.22       | 7475 0.35   | 74153 0.69     | 74195 0.78   |
| 7437 0.25       | 7476 0.24   | 74154 1.05     | 74198 1.20   |
| 7438 0.19       | 7483 0.69   |                | 74199 1.70   |

| SCHOTTKY  |           |           |           |
|-----------|-----------|-----------|-----------|
| 74500 .24 | 74504 .29 | 74520 .29 | 74574 .29 |
| 74502 .29 | 74508 .35 | 74522 .29 |           |
| 74503 .24 | 74510 .29 | 74532 .39 |           |

| LOW POWER SCHOTTKY |             |              |              |
|--------------------|-------------|--------------|--------------|
| 74LS00 .23         | 74LS20 .23  | 74LS90 1.25  | 74LS193 1.75 |
| 74LS02 .23         | 74LS32 .27  | 74LS93 1.25  | 74LS197 1.65 |
| 74LS04 .25         | 74LS40 .33  | 74LS95 2.10  |              |
| 74LS08 .27         | 74LS42 1.30 | 74LS107 .99  |              |
| 74LS10 .23         | 74LS74 .39  | 74LS164 1.80 |              |

| CMOS 4000 SERIES |             |             |             |
|------------------|-------------|-------------|-------------|
| 4000A £ 0.14     | 4010 £ 0.36 | 4023 £ 0.65 | 4050 £ 0.35 |
| 4001 0.14        | 4011 0.14   | 4024 0.50   | 4066 0.46   |
| 4002 0.14        | 4012 0.14   | 4025 0.14   | 4069 0.15   |
| 4006 0.75        | 4013 0.36   | 4077 0.36   | 4071 0.15   |
| 4007 0.14        | 4014 0.65   | 4078 0.59   |             |
| 4008 0.65        | 4015 0.65   | 4030 0.36   |             |
| 4009 0.36        | 4016 0.38   | 4035 0.75   |             |
|                  | 4017 0.75   | 4042 0.55   |             |
|                  | 4018 0.65   | 4049 0.35   |             |
|                  | 4019 0.14   |             |             |

| LINEARS           |                  |   |  |
|-------------------|------------------|---|--|
| LM300 TO99 £ 0.45 | 340T TO92 £ 1.25 | 739 A DIP £ 0.65                                    |  |
| 301 V DIP 0.25    | 380 A DIP 0.80   | 741 V DIP 0.22                                      |  |
| 302 TO99 0.40     | 381 A DIP 0.90   | 747 A DIP 0.44                                      |  |
| 304 TO100 0.50    | 550 A DIP 0.55   | 748 V DIP 0.24                                      |  |
| 305 TO99 0.45     | 555 V DIP 0.35   | 5556 (11456) V DIP 0.95                             |  |
| 307 V DIP 0.38    | 556 B DIP 0.75   | 5558 (11458) V DIP 0.45                             |  |
| TO99 0.45         | 560 B DIP 2.45   | LM3900 A DIP 0.25                                   |  |
| 308 A DIP 0.59    | 562 B DIP 2.45   | 75450 V DIP 1.00                                    |  |
| TO99 0.65         | 565 A DIP 1.40   | 75451 V DIP 0.23                                    |  |
| 309K TO3 1.10     | 566 V DIP 1.40   | 75452 V DIP 0.23                                    |  |
| 310 T pkg 0.59    | 567 V DIP 1.55   | 75453 V DIP 0.23                                    |  |
| 311 V DIP 0.75    | 709 A DIP 0.20   | 75491 A pkg 0.60                                    |  |
| 320K TO3 NEG 7.10 | A DIP 0.25       | 75492 A pkg 0.65                                    |  |
| 5.2, 12, 15 1.00  | 711 A DIP 0.18   | ICL8038 Funct Gen 2.80                              |  |
| 324 A DIP 1.07    | 723 A DIP 0.38   | Volt Contr Oscillator, Sine Sq 8864 22 Pin pkg 1.45 |  |
| 339 A DIP 1.15    |                  |   |  |
| 340K TO3 1.50     |                  |   |  |

V. Mini Dip. A - 14L Dip B 16L DIP TO99 8-Pin Header TO100 10 Pin Header  
 Data sheets supplied on request Add 20 ea. excepted as noted

| MEMORIES w/DATA                  |                      | CALCULATORS & CLOCKS w/DATA |  |
|----------------------------------|----------------------|-----------------------------|--|
| 1101 256 Bit Ram Mos £ 1.30      | 5002 Cal Chip 0.79   | 5005 Cal Chip 0.79          |  |
| 1103 1024 Bit Ram Mos 1.25       | 5725 Cal Chip 1.75   | 5729 Cal Chip 1.75          |  |
| 7489 182251 64 Bit Ram TTL 1.45  | 5738 Cal Chip 1.20   | 5739 Cal Chip 1.20          |  |
| 82523 Programmable ROM 2.15      | 5311 Clock Chip 2.80 | 5312 Clock Chip 2.50        |  |
| 5260 1024 Bit Ram Low Power 1.45 | 5314 Clock Chip 3.45 | 5316 Clock Chip 3.95        |  |
| 5261 1024 Bit Ram L Power 1.56   | 5316 Clock Chip 3.95 | CT7001 Clock Chip 3.85      |  |
| 1702A 2048 Bit Prom 6.95         |                      |                             |  |
| 2102 1024 Bit Status Ram 2.75    |                      |                             |  |

| LEDS   |                            | TRANSISTORS         |                   |
|--|----------------------------|---------------------|-------------------|
| MV 5020 Jumbo Red or Clear £ 0.15                          | MAN 1 Red 7 Seg .270" 1.20 | 2N 2219A TO5 £ 0.42 | 2N 4124 TO92 0.11 |
| MAN 1 Red 7 Seg .127" 0.20                                 | MAN 3A Red Seg .127" 1.85  | 2N 2222 TO18 0.17   | 2N 4126 TO92 0.11 |
| MAN 5 Green 7 Seg .270" 2.60                               | MAN 6 6 Solid Seg 2.60     | 2N 2369 TO18 0.11   | 2N 4401 TO92 0.11 |
| 9 Digit Array Fairchild 37 with clear magnifying lens 2.80 | 2N 3227 TO18 0.37          | 2N 2905A TO5 0.43   | 2N 5225 TO92 0.17 |
|  |                            | 2N 3227 TO18 0.37   | 2N 5226 TO92 0.17 |

|                         |                  |                                |
|-------------------------|------------------|--------------------------------|
| <b>DISCOUNTS:</b>       | <b>MIN ORDER</b> | <b>All Items New/Branded</b>   |
| 10% on orders over £ 10 | £ 2.00           | Guaranteed By DEMA ELECTRONICS |
| 15% on orders over £ 25 |                  |                                |

**TERMS: PRICES LISTED ARE BRITISH POUNDS & PENCE. SEND CHEQUE WITH ORDER. ACCESS CARD, BANKAMERICARD, BARCLAY CARD ACCEPTED. (Card # and expiration date requested). TERMS OFFERED TO SCHOOLS & INSTITUTIONS.**


| POSTAL AND HANDLING CHARGES SHIPMENT VIA AIR MAIL |         |               |
|---|---------|---------------|
| under 4.99  | add .45 | £ 10 and over |
| 5.00-9.99   | add .35 | No Charge     |

**DEMA ELECTRONICS INTERNATIONAL**  
 P.O. Box 407 San Ramon, Ca. 94583 USA  
 Cable DEMAEINTL

SEND FOR FREE CATALOGUE

SEND FOR FREE CATALOGUE

# nombrex

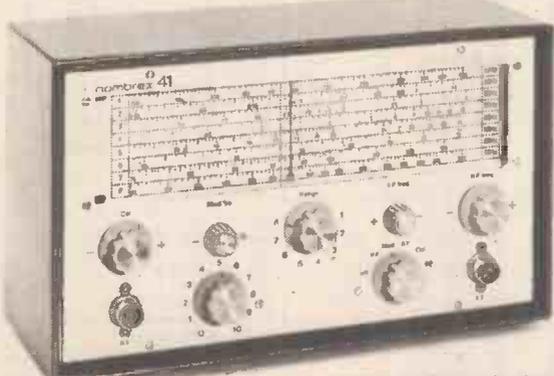

**MODEL 41**  
**R.F. SIGNAL GENERATOR**  
**Price £54.85**


- ★ 150 KHz — 220 MHz on fundamentals.
- ★ 8 clear scales — Total length 130mm.
- ★ Spin-Wheel Slow Motion Drive 11 — 1 ratio.
- ★ Overall Accuracy — 2 1/2%.
- ★ Modulation, Variable depth and frequency.
- ★ Internal Crystal Oscillator providing calibration checks throughout all ranges.
- ★ Mechanical scale adjustment for accurate alignment against internal 1MHz crystal oscillator.
- ★ Powered by 9V Battery.

Trade and Export enquiries welcome.  
 Send for full technical details.  
 Post and Packing £1.00 extra

**NOMBREX LTD., POUND PLACE, WOLBOROUGH STREET, NEWTON ABBOT, DEVON, TQ12 1NE**  
 Tel. Newton Abbot 68287

WW—036 FOR FURTHER DETAILS

# New Achievements from Xcelite

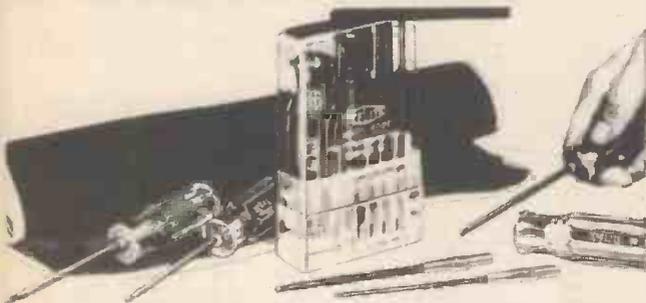

Xcelite technology has created some new additions to the famous 99 SERIES of Interchangeable Tools. The first of these is the Compact Set of Ball-End Hex drivers which, as illustrated, can drive from any angle.

Also now available in the same series are the POSIDRIV blades Nos. 1, 2 and 3.

Send for the complete Xcelite precision tools catalogue from:

**Special Products Distributors Limited**

81 Piccadilly, London W1V 0HL

Telephone: 01-629 9556

**XCELITE PROFESSIONAL HAND TOOLS**

WW — 066 FOR FURTHER DETAILS

## MORE POWER— MORE TORQUE

with the

### NEW MK. II DRILL

**SPEED**  
10,000 r.p.m.

**TORQUE**  
120 cmg

**VOLTAGE**  
9-14v d.c.

**DRILL ONLY £8.79**  
(p&p 35p)


**STAND £4.40**

(p&p 35p)

Inc. VAT

(Together 50p p&p)

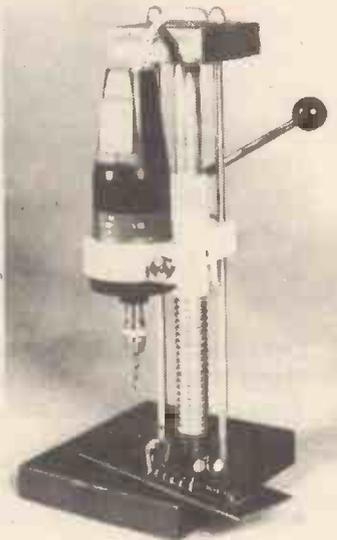Send a 9" x 4"  
SAE for illustrated  
leaflet and order form  
to:



## PRECISION PETITE LTD.

119A HIGH STREET, TEDDINGTON, MIDDX.

TEL. 01-977 0878

(24-hour answering service)

## VALVES

|              |              |              |
|--------------|--------------|--------------|
| A1065 1.25   | EF37A 1.50   | G234 0.80    |
| AR9 0.60     | EF39 1.00    | G237 2.00    |
| ATP3 0.60    | EF40 0.70    | KT66 3.50    |
| ATP4 0.50    | EF41 0.75    | KT88 4.50    |
| B12H 3.00    | EF80 0.35    | MM4 1.00     |
| DAF96 0.60   | EF83 1.50    | ML6 1.00     |
| DET22 1.85   | EF86 0.45    | OA2 0.45     |
| DF96 0.60    | EF86 0.45    | OB2 0.45     |
| DK96 0.80    | EF89 0.35    | PAB80 0.40   |
| DL92 0.50    | EF91 0.65    | PC86 0.65    |
| OL96 0.70    | EF92 0.75    | PC88 0.65    |
| DY86/87 0.45 | EF95 0.45    | PC92 0.65    |
| DY802 0.45   | EF183 0.40   | PC84 0.45    |
| EB8CC/01     | EF184 0.40   | PC85 0.50    |
| 1.30         | EF804 2.00   | PC89 0.55    |
| E180CC 1.30  | EFL200 0.75  | PCC1890 0.58 |
| E182CC 3.50  | EH30 0.60    | PCF80 0.40   |
| E810F 6.00   | EL32 0.60    | PCF82 0.40   |
| EA50 0.45    | EL34 0.70    | PCF84 0.65   |
| EABC80 0.40  | EL35 0.60    | PCF86 0.65   |
| EAF42 0.70   | EL37 3.00    | PCF200 0.90  |
| EB91 0.70    | EL41 0.80    | PCF201 0.80  |
| EC33 1.30    | EL81 1.80    | PCF801 0.55  |
| EC41 0.35    | EL82 0.60    | PCF802 0.55  |
| EF80 0.45    | EL84 0.35    | PCF805 1.10  |
| EF83 0.45    | EL86 0.50    | PCF806 0.80  |
| EF89 0.45    | EL90 0.50    | PCF808 1.00  |
| EC52 0.40    | EL91 1.80    | PCW200 0.80  |
| EC88 0.45    | EL95 0.70    | PCL81 0.60   |
| EC82 0.40    | EL504 0.80   | PCL82 0.45   |
| EC83 0.40    | EL821 3.00   | PCL83 0.70   |
| EC84 0.35    | EM31 0.75    | PCL84 0.60   |
| EC85 0.45    | EM80 0.55    | PCL86 0.60   |
| EC86 1.25    | EM81 0.60    | PCL805/85    |
| EC88 0.55    | EM84 0.40    | 0.80         |
| EC189 0.80   | EM87 1.00    | PFL200 0.70  |
| ECF80 0.45   | EY81 0.45    | PL36 0.60    |
| ECF82 0.45   | EY81 0.45    | PL81 0.55    |
| ECF801 0.75  | EY86/87 0.50 | PL82 0.50    |
| ECM42 0.85   | EY88 0.50    | PL83 0.50    |
| ECM81 0.45   | EZ40 0.60    | PL84 0.50    |
| ECM84 0.50   | EZ41 0.75    | PL504 0.85   |
| ECL80 0.60   | EZ80 0.30    | PL508 0.95   |
| ECL82 0.50   | EZ81 0.35    | PL509 1.35   |
| ECL83 1.20   | GT1C 7.00    | PC802 2.00   |
| ECL86 0.85   | GY501 0.75   | PY33 0.60    |
| EF36 0.75    | G732 0.65    |              |

## PLUMBICON TUBES TYPE XO 1071 Mullard

|             |             |            |              |            |             |
|-------------|-------------|------------|--------------|------------|-------------|
| PY80 0.60   | TT21 6.50   | UCL83 0.70 | 1A3 0.80     | 5R4GY 1.10 | 6AQ5W 0.85  |
| PY81/800    | U25 1.00    | UF41 0.75  | 1L4 0.30     | 5U4G 0.60  | 6AS6 0.80   |
| PY82 0.55   | U26 0.85    | UF80 0.40  | 1R5 0.55     | 5V4G 0.65  | 6AT6 0.65   |
| PY83 0.45   | U27 1.00    | UF85 0.60  | 1S4 0.40     | 5Y3GT 0.65 | 6AU6 0.40   |
| PY88 0.50   | U191 0.75   | UF89 0.50  | 1S5 0.40     | 5Z3 1.00   | 6AV6 0.50   |
| PY901 0.55  | U301 0.80   | UL41 0.75  | 1T4 0.40     | 5Z4G 0.70  | 6AX4GT 0.80 |
| QV03-10     | U48C80 0.80 | UL84 0.50  | 1X2B 0.80    | 6A87 0.60  | 6AX6GT 1.00 |
| 1.60        | UAF42 0.75  | UY41 0.85  | 2X2 0.80     | 6AC7 0.60  | 6B7 0.75    |
| QV06-40A    | UBC41 0.60  | UY85 0.50  | 2D21 0.55    | 6AC7 0.75  | 6BA6 0.40   |
| 14.00       | UF80 0.50   | VR105/30   | 2K25 0.90    | 6AH6 0.75  | 6BE6 0.45   |
| QV03-121.60 | UF89 0.50   | 0.50       | 3A4 0.60     | 6AK5 0.45  | 6BG6 1.00   |
| R19 0.80    | UL81 1.00   | VR150/30   | 3E29 0.50    | 6AK8 0.40  | 6BJ6 0.75   |
| S104/1K2.50 | UCC85 0.50  | 0.50       | 306 0.40     | 6AL5 0.30  | 6BQ7A 0.60  |
| SC1/4004.00 | UCF80 0.80  | X66 0.75   | 3S4 0.50     | 6AL5W 0.65 | 6BR7 2.30   |
| SC1/6004.00 | UCH42 0.80  | Z800U 3.00 | 3V4 0.85     | 6AM5 1.60  | 6BW6 1.30   |
| SP61 0.88   | UCL81 0.50  | Z801U 3.50 | 5B/254M 5.50 | 6AM6 0.65  | 6BW7 1.00   |
|             | UCL82 0.45  | Z900T 1.50 | 5B/255M 5.80 | 6AN8 0.85  | 6C4 0.40    |
|             |             |            | 6AQS 0.50    | 6AQS 0.50  | 6C6 0.55    |
|             |             |            |              |            | 6C8 0.80    |

## VIDECON TUBE TYPE P 863 B English Electric

£20.00

## TRANSISTORS 12 1/2 % Please add VAT 12 1/2 % for valves, etc.

|       |        |         |           |        |          |         |
|-------|--------|---------|-----------|--------|----------|---------|
| AAZ12 | AF125  | BC172A  | CRS3/30   | OC26   | OC200    | 2N3638A |
| AC113 | AF126  | BC212A  | CRS3/40   | OC28   | OC204    | 2N3730  |
| AC126 | AF127  | BCY31   | CRS25/025 | OC29   | OC206    | 2N3819  |
| AC127 | AF139  | BCY33   | GET115    | OC35   | RA5310AF | 2N4038  |
| AC128 | AF178  | BCY72   | GET116    | OC36   | ZR11     | 2N4058  |
| AC176 | AF186  | BF115   | GEX66     | OC42   | ZR21     | 2N4061  |
| ACV17 | AF239  | BF167   | NKT222    | OC44   | ZR22     | 2N4172  |
| ACV18 | AFZ12  | BF173   | PCL304    | OC45   | 2N456A   | 2N5295  |
| ACV19 | ASY26  | BF185   | NKT404    | OC70   | 2N696    | 3N141   |
| ACV20 | ASY27  | BFV51   | OA5       | OC73   | 2N708    | 3N154   |
| ACV39 | ASY28  | BFV52   | OA47      | OC75   | 2N916    | SK642   |
| ACV40 | BC107  | BFV25   | OA70      | OC78   | 2N1305   | SK754   |
| AD149 | BC108  | BSV27   | OA71      | OC78B  | 2N1307   | 25303   |
| AD161 | BC109  | BSY38   | OA73      | OC81   | 2N1309   | 1T2082  |
| AD211 | BC113  | BSY95A  | OA79      | OC82   | 2N2062   | 40235   |
| AD212 | BC116  | BY100   | OA91      | OC82DM | 2N2270   | 40250   |
| AF114 | BC118  | BY216   | OA200     | OC83   | 2N2904A  | 40251   |
| AF115 | BC136  | CRS1/20 | OC220     | OC89B  | 2N2989   | IN23A   |
| AF116 | BC137  | CRS1/30 | OC220     | OC139  | 2N3053   | IN38A   |
| AF117 | BC148A | CRS3/10 | OC27      | OC140  | 2N3054   | IN43    |
| AF124 | BC172  | CRS3/20 | OC25      | OC170  | 2N3055   | IN70    |
|       |        |         |           | OC172  | 2N3391   | IN72    |

## VALVES AND TRANSISTORS

Telephone enquiries for valves, transistors, etc., retail 749 3934, trade and export 743 0899.

**VAT FOR TEST EQUIPMENT**  
8% PLEASE ADD 8%

## E.H. RESEARCH LABORATORIES

**133A PULSE GENERATOR.** Features Ultra linear ramp, rise and fall independently variable 50v output into 50 ohms, either polarity. Automatic overload protection. Synchronous gating, all solid state. Full specification on request £275.00

## MODEL 122 GENERATOR

Features 122 pulses to 200MHz. Nanosecond Switching times, synchronous gating. Pulse-to-pulse inversion, plus offset, all solid state. Full specification on request. £295.00

OTHERS IN STOCK inc. integrated circuits, CRT & special valves. Min. Mail Order £1. UK POSTAGE £1-£2 20p. £2-£3 30p. £3-£5 40p. Over £5 free. Casual callers welcome.

A lot of these valves are imported and prices vary for each delivery, so we reserve the right to change prices for new stock when unavoidable.

## FOR EXPORT ONLY

RCA ET4338, 2 Mc/s-20Mc/s, 350W also modified version of increased output to 700W. Collins 231D 4/5 kW, 3 MHz-24 MHz 10 channel Auto. or manual tuning. 53 Transmitter 62 Transceivers Mullard C11, high power installation (1000W). Technical details and prices available on request.



THE VALVE WITH A GUARANTEE

|             |           |
|-------------|-----------|
| 12K7GT 0.60 | 954 0.80  |
| 12K8GT 0.70 | 955 0.80  |
| 12Q7GT 0.60 | 956 0.50  |
| 12SC7 0.55  | 957 0.90  |
| 12SG7 0.85  | 1629 0.70 |
| 12SJ7 0.55  | 2051 1.00 |
| 12Y4 0.40   | 5763 1.60 |
| 14S7 1.00   | 5933 3.00 |
| 19AQ5 0.75  | 8057 0.85 |
| 19G3 10.00  | 8060 0.85 |
| 12SG7 0.85  | 8064 0.85 |
| 19H5 17.00  | 8065 1.20 |
| 20P3 0.60   | 8067 1.50 |
| 20P4 1.10   | 8080 3.00 |
| 25L6GT 0.80 | 8146 3.80 |
| 30CL2 1.00  | 6146 4.20 |
| 30C17 1.10  | 6360 1.60 |
| 30C18 1.10  | 8020 6.80 |
| 30F5 1.00   | 9001 0.40 |
| 30FL2 1.00  | 9002 0.55 |
| 30FL12 1.20 | 9003 0.70 |
| 30FL14 1.00 | 9004 0.40 |
| 30L15 1.00  | 9006 0.40 |
| 30L16 1.00  |           |
| 30L17 1.00  |           |
| 30L18 1.00  |           |
| 30L99 1.00  |           |
| 30L100 1.00 |           |

C.R. TUBES  
DG7-5 15.00  
DG13-222.00  
HMW13-35 35.00

VCR139A 10.00  
3BP1 8.00  
5FP7 10.00  
8B1 9.00  
8BL 9.00  
CV1526 10.00

SPECIAL VALVES  
BR189 250.00  
M503-2J42

803 18.00  
K301 7.00  
KR2A 6.00  
6J5 25.00  
2J/52A 75.00  
CV2339 45.00  
CV522 17.50

We hold one of the largest stocks of valves in the UK

PLEASE SEND STAMP WITH ENQUIRIES

**COLOMOR**  
(ELECTRONICS LTD.)

170 Goldhawk Rd., London, W.12  
Tel. 01-743 0899

Open Monday to Friday  
9-12.30, 1.30-5.30 pm.

# Samson's

(ELECTRONICS) LTD.  
9 & 10 CHAPEL ST., LONDON, N.W.1  
01-723 7851 01-262 5125  
ADJACENT TO EDGWARE ROAD MET. LINE STATION  
PLEASE ADD 8% TO ALL ORDERS INC. CARR.

### CURRENT RANGE OF NEW L.T. TRANSFORMERS

| Type | Sec Taps        | Price  | Carr  |
|------|-----------------|--------|-------|
| 1    | 24-30-40-48-60v | £27.75 | £2.00 |
| 2    | 24-30-40-48-60v | £26.50 | £2.00 |
| 3    | 24-30-40-48-60v | £21.70 | £1.50 |
| 4    | 24-30-40-48-60v | £14.15 | £1.00 |
| 5    | 24-30-40-48-60v | £10.90 | 75p   |
| 6    | 24-30-40-48-60v | £7.34  | 75p   |

CAN BE OBTAINED FROM THE ABOVE RANGE

|    |                 |        |       |
|----|-----------------|--------|-------|
| 7  | 19-25-33-40-50v | £24.25 | £2.00 |
| 8  | 19-25-33-40-50v | £16.54 | £1.25 |
| 9  | 19-25-33-40-50v | £8.45  | 75p   |
| 10 | 19-25-33-40-50v | £6.83  | 75p   |

OR 25-0-25 OR 20-0-20v CAN BE OBTAINED FROM THE ABOVE RANGE

|    |                 |        |       |
|----|-----------------|--------|-------|
| 11 | 12-15-20-25-30v | £13.30 | £1.25 |
| 12 | 12-15-20-25-30v | £9.30  | £1.00 |
| 13 | 12-15-20-25-30v | £5.20  | 75p   |

3.4-5.6-8.9-10-12-15-18-20-24-30v OR 12-0-12v, OR 15-0-15v CAN BE OBTAINED FROM THE ABOVE RANGE

|    |        |         |         |        |       |
|----|--------|---------|---------|--------|-------|
| 14 | 12-24v | 12v 60A | 24v 30A | £24.38 | £2.00 |
| 15 | 12-24v | 12v 30A | 24v 15A | £19.80 | £1.50 |
| 16 | 12-24v | 12v 20A | 24v 10A | £14.07 | £1.25 |
| 17 | 12-24v | 12v 10A | 24v 5A  | £7.59  | 75p   |
| 18 | 12-24v | 12v 4A  | 24v 2A  | £4.10  | 60p   |

### FULLY SHROUDED TYPE TERMINAL CONNECTIONS

|    |           |    |        |       |
|----|-----------|----|--------|-------|
| 19 | 28-32v    | 4  | £8.95  | 75p   |
| 20 | 14-16v    | 2  | £5.35  | 65p   |
| 21 | 12-20-24v | 10 | £13.50 | £1.00 |
| 22 | 12-20-24v | 5  | £7.95  | 75p   |
| 23 | 24-30-36v | 10 | £13.95 | £1.25 |
| 24 | 24-30-36v | 5  | £10.98 | £1.00 |
| 25 | 6-12v     | 10 | £8.00  | 75p   |
| 26 | 8-0-8v    | 2  | £5.35  | 65p   |

### CENTRE TAPPED TRANSFORMERS

Fully shrouded terminal block connections. Screen. Pn. 220-240v, sec. tapped 36-25-0-25-36v 5A £13.50, pp. £1. 30-25-0-25-30v 2A £6.75, pp. £1. 18-0-18v 2A £5.25, pp. £1. Open frame types. Pn. 220-240v, sec. 60-0-60v 1A £5.95, pp. 75p. 50-0-50v 2A £8.85, pp. £1.

### HEAVY DUTY TYPES

Pn. 230-240v, sec. 12v 30A twice will give 12v 60A or 24v 30A £33.00, carr. £2. Sec. 6-12v 20A £10.95, carr. £1.75. Sec. 20v, 23A £12.00, carr. £1.75.

### PARMEKO ISOLATION TRANSFORMERS

Es. equipment in perfect condition. Metal shrouded open table top connections. Pn. 200-250v in 5v steps. Sec. 240v 10 amps £35, carr. £4. Pn. 200-250v in 10v steps. Sec. tapped 90-100-110-120v 7.5 amps £19.50, carr. £3. Pn. 200-250v in 5v steps. Sec. 115v 13.5A £39.50, carr. £4.

### GARDNERS ISOLATION TRANSFORMERS

New, fraction of maker's price. Open type table top connections. Pn. 220-240v. Sec. 240v 6 amps £22.50, carr. £3. Open type cable lead connections. Pn. 200-220-240v. Sec. 240v 700 watts £10, carr. £2.

### HEAVY DUTY AUTO TRANSFORMERS

For mains boosting etc. equipment. Input 200-260v in 10v steps, output 240v 6kva. Enclosed in metal case. £40, carr. £5. One only.

### 3 PHASE ISOLATION TRANSFORMERS BY FAMOUS MAKER

Input tapped 380-400-415-430 volts RMS NOM. Line to line 3 phase 4 wire 50Hz output 415 volts. NOM 3 phase 4 wire at 2.15kVA. Regulating 2% secondary fully screened open type construction. Terminal board connections, size 16x2x7/8ins. Weight 90lbs. Brand new. Fraction of maker's price. £29.50, carr. £4.

### WODEN 3000 WATT TRANSFORMERS

Es. equipment, perfect condition. Tapped 105-115-125-135-200-215-230-245-260v. Open type terminal block connections £22.50, carr. £2. Can be supplied in metal case with two American 2/3 pin flush mounting sockets. 3 core 240v mains lead. Carrying handle £37.50, carr. £3.

### AUTO TRANSFORMERS FOR AMERICAN EQUIPMENT

240/110v, 80-3000 Watts, fitted with 2-3 pin sockets and 3 core mains lead. Send see for price list. We have England's largest selection of American electrical accessories, 2-3 pin sockets, recessed and surface type, 2-3 sockets, multi-way adaptors, 2-3 pin grounding adaptors. Cable type sockets. Extension cords. 240v Edison screw type light bulbs. Industrial plugs and sockets. Let us know your requirements.

### DC POWER SUPPLIES

Es. computer types. AC input 240v, DC output 40v 2A, 28v 1/2A, 78v 1/2A, incorporating Advance Components c/v transformer. Construction. Open frame chassis. Size 26x13x19cm. £8.50, carr. £1.50.

### HOWELLS "C" CORE TRANSFORMERS

Pn. 220-240v screen. Sec. 70-0-70v, 10 amp table top connections, size 7x7.7 inches, £15.00, carr. £2.00. Pn. 220-240v. Sec. 18-0-18v 12.5 amps conservatively rated. Table top connections £10.00, carr. £2.00.

### L.T. TRANSFORMERS

By famous makers. Fraction of maker's price. All primaries 220-240v open type. No. 1: Sec. 26v 10A. Top panel connections £5.75, pp. £1. No. 2: Sec. 43v 3A. Wire end connections £3.75, pp. 75p. No. 3: 33v 5A and 18-0-18v 1A. Wire connections £5.75, pp. 75p. No. 4: 30v 5A and 12v 2.2A £5.50, pp. £1. No. 5: Sec. 14v 5A, 14v 2.5A, 12v 10A, 8v 10A, 24v 750m/A, separate windings £10, carr. £2. No. 6: 26v 5A, 16v 4A, 25v 2A, separate windings £8.50, pp. £1. Potted types, No. 7: Sec. tapped 24-30-32v 2A £3, pp. 75p. No. 8: Sec. 2-0-2v 24A, high voltage insulation £8.80, carr. £1. No. 9: Sec. 6.6v 6A, 6.6v 6A, 5v 6A, separate windings. The following outputs can be obtained: 6.6v 6A, 6v 6.6A, 5v 6A, 13v 6A and 5v 6A, 6.6v 12A and 5v 6A, 11-6v 6A and 6.6v 6A, 18-2v 6A £5.95, carr. £1. No. 10: 24-0-24v 470m/A and 4.5 1A and 150v 15m/A, separate windings £2.50, pp. 75p. No. 11: Sec. 4.2v 1A £1.25, pp. 50p. No. 12: Sec. 50v 1A and 140v 195m/A and 6.3v 1 25A £3.50, pp. £1. No. 13: Sec. 6v 1A twice £2, pp. 50p. No. 14: Sec. 24v 1A, 24v 750m/A £3, pp. 50p. No. 15: Sec. 9v 2A and 9v 1A, open type £2.50, pp. 50p. No. 1A, Sec. 35v 5A, 200v 100m/A, 30v 100m/A, separate windings £7.50, carr. £1.50.

### GECLT TRANSFORMERS ALL PRIMARIES 220-240V

G.P.O. spec. Sec. tapped 58-61-66-68-67-69v 10A £3, carr. £2. Sec. tapped 58-69-74v 3A £4.50, pp. 75p. Both types terminal block connections, open frame. Pn. 380-400-420-440v. Sec. 240v 40vA. Terminal block connections, open type £3.50, pp. £1.

### GRESHAM L.T. TRANSFORMERS

All primaries tapped 10-0-200-220-240v, open type tropicalised. Terminal block connections. Fraction of maker's price. No. 1: Sec. tapped 0-4-16-17-18-19-20v 20A £7.00, No. 2: 4-7-11-31-32-33-32v 20A £8.50, No. 3: 4-7-11-32-33-34-35v 10A, £6.50, No. 4: 6-13-20-54-56-58-59v 5A £6.50. Carr. on all types £1.

### "C" CORE TYPES ALL PRIMARIES 220-240V

No. 1: Sec. 18-0-18v 21A £10, carr. £2. No. 2: Sec. tapped 22-25-28v 5A and 16v 1A twice, 10v 1A twice, 28v 2.5A, 23v 1A, 6.3v 2A 145-0-145v 20m/A, separate windings £6, carr. £1. No. 3: Tapped 29-31-32v 15A and 23-24-26v 5A and 14-15-17v 5A £12, carr. £2. No. 4: Sec. tapped 27-28-30-39v 10A £12, carr. £2. No. 5: Sec. tapped 10-21v 5A and 1-3v 5A, the following outputs can be obtained 1-3-10-11-12-21-22-24v 5A £4, carr. £1. No. 6: Sec. tapped 1-3v, 1 1A and 10-30v 1.1A £2.50, pp. 75p. No. 7: Sec. tapped 20-22v 1.5A £2, pp. 75p. No. 8: Pn. 50v only, sec. 100v 2.5A twice £8.50, carr. £1.50.

### MINIATURE L.T. TRANSFORMERS

Pn. 240v. Sec. 24-0-24v 100m/A. Size 45 x 35 x 30mm £1, pp. 30p.

### DURAPLUG 3-PIN CONNECTORS

Rubber cast 3-pin in line cable connectors. 250v 5 amp. Colour yellow. Three for £2 inc. postage.

### AIR MINISTRY SWITCHES

2 pole push to make. Robustly built in black bakelite housing, size 1 1/2 in. dia. Panel mounting. Three for £1, including postage. Cutter 4 pole. Centre of all toggle switches 250v 5A each pole two for £1, postage paid.

### WHARFEDALE O.P. TRANSFORMERS

Type P. Four ratios, 30-45-60 and 90 to 1. Also 90-1 centre tapped for push pull Class B. 75p PP 25p.

### "C" CORE LT. CHOKES

10m/H 25 amps £8.75, carr. £1.25. Swinging types 7.5m/H 4A-75m/H 0.5A £3.95, carr. £1. 10m/H 6amps-100m/H 0.5 amps £3.50, carr. £1.

### HEAVY DUTY H.T. CHOKES

Parmeko potted type: 9H 500m/A 5kv wkg. £8.50, carr. £1.50. G.E.C. potted type 20H 200m/A £3.00, pp. £1. 12H 150m/A £2, carr. 75p. 20H 180m/A £2.75, pp. £1.

### HIGH VOLTAGE DC SUPPLY UNITS BY FAMOUS MAKER

AC input 220-240v DC output 3900-3100-0-3100-3900v 100m/A, incorporating c/v input transformer, Cap smoothed. Moused in metal case, size 15 x 10 x 8 ins. 8 amp safety cut out and input and output sockets on front panel £50, carr. £4.

### HEAVY DUTY HIGH VOLTAGE TRANSFORMERS

Pn. 230v, sec. tapped 4500-3500-2600v 500m/A 6000v wkg. Open type. Size 12 x 10 x 15 ins. £38, carr. £5.

### HEAVY DUTY BLOCK CAPACITORS

100mfd 400v DC wkg. £4.50, carr. £1.50. 0.215mfd 1250v rms £2.50, pp. £1. 10mfd 3kv discharge rating. 55 deg C £4, carr. £1. 8mfd 2500v DC 70 deg C £3.50, carr. £1. 2mfd 1500v DC 140 deg F £2.00, pp. 75p.

### PRESSURE SWITCHES

KDC range 0-500psi 250v 5 amp switch off or on. Enclosed in metal box, size 5 x 5 x 2 1/2 ins. Ward Brook 0-3000 psi 250v 5 amp switch off or on enclosed in metal case, size 7 x 6 x 3 ins. Either type £3.75, pp. 75p.

### HIGH VOLTAGE INSULATION TRANSFORMER

One only. Pn. 220-240v Tapped 4-5-6.3v 12 amps and 2.5v 35v 100v AC wkg. £20, carr. £3.

PLEASE ADD 8% VAT TO ALL ORDERS INC. CARR.

### H.T. TRANSFORMERS BY FAMOUS MAKERS

#### Fraction of original prices ALL PRIMARIES 220-240V

Potted types. No. 1: 408-200-0-200-408v. 408v taps 165m/A, 200v taps 500m/A. £5.50, carr. £1.50. No. 2: Sec. 330-0-330v 200m/A, 6.3v 6.6A, 5v 3A £4.75, carr. £1.25. No. 3: 350-0-350v 200m/A, 6.3v 6.6A, 5v 3A £4.95, carr. £1.25. No. 4: 300v 37m/A twice, 4v 1A, 4v 0.3A, 4kv DC wkg. £3, pp. 75p. No. 5: Sec. 630-0-630v 105m/A, 5v 4A, 5v 2A £4.95, carr. £1.25. No. 6: Sec. 400-0-400v 170m/A, 6.3v 6A, 6.3v 1.6A, 5v 3A £4.50, carr. £1. No. 7: 400-230-0-230-400v 120m/A, 6.3v 4A, 6.3v 3A, 5v 3A £4.50, carr. £1. No. 8: Sec. tapped 700-760v 100m/A, 6.3v 1.5A £3.50, pp. 75p. No. 9: Pn. 115v only, sec. 530-0-530v 330m/A, 6.5v 6A £7.50, carr. £1.50. No. 10: Sec. 65v 1A and 18-24v 0.5A £3.75, pp. £1. No. 11: 250-0-250v 60m/A, 2.8-0-2.8v 2A, 24v 3A, 6.3v 3A "C" core type £5.50, pp. £1. No. 12: Sec. tapped 370-490-410v 6m/A "C" core. £1.25, pp. 35p. No. 13: Sec. 250v 80m/A and 15v 1.2A and 6.3v 4.5A, open type £3.50, pp. 50p. No. 14: 500-0-500v 200m/A, fully shrouded £4.50, carr. £1. No. 15: 250v 20m/A, 6.3v 1A, shrouded £1.25, pp. 50p. No. 16: 220v 20m/A, 6.3v 1A £1.25, pp. 50p. Open type tag connections. Sec. 350-0-350v 120m/A, 6.3v ct 4A, 5v 2A £3.95, pp. 75p. Sec. 300-0-300v 150m/A, 6.3v ct 4A, 5-6-3v 2A £3.95, pp. 75p. Sec. 300-0-300v 100m/A, 6.3v 3.5A, 5v 2A £3.50, pp. 75p. Sec. 250-0-250v 80m/A, 6.3v 3.5A, 6.3v 1A, 5v £3.25, pp. Sec. 50-0-50v 2A £4.75, pp. £1.

### HIGH VOLTAGE TRANSFORMERS

Gresham. Pn. 240v sec. 2300v 10m/A, 6.3v 1.5A. Open type. Table top connections £3.80, pp. 50p. Woden. Pn. 230v sec. 890-710-0-710-890v 120m/A. Open type T.T. connections £3.75, pp. 75p. Parmeko potted type. Pn. 110-220-240v sec. 187v 60m/A, 6.4v 6A, 5v 3A £5.50, carr. £1. Parmeko potted type. Pn. 230-240v, sec. tapped 3100-3200v 200m/A £8.50, carr. £1.50.

### REPANCO INVERTER TRANSFORMERS

Type TT51 12v DC to 240v AC 15 watts £3, pp. 50p. Type TT24 10watt amp for PA or car radio £3, pp. 50p.

### OUTPUT TRANSFORMERS

Multi tapped type MRT3 7 watts max. DC 60m/A, single 1-3-1 to 100-1 P.P. 20-1 to 100-1 £1.95, pp. 50p. Type MRT2 2 watts max. DC 50m/A, single 7-7-1 to 80-1, P.P. 15-1 to 80-1 £1.25, pp. 50p. Elstone OT3 pin. load 5000 ohms, sec. 15 and 3.75 ohms £3, pp. 50p. Type OT26EL fully shrouded, 1.75k ohms £1.34x4, see to suit 3.75-7.5-15 ohms 100 watts £7.50, pp. 100p. All types with data sheet.

### A.E.R.E. HIGH VOLTAGE INSULATION "C" CORE TRANSFORMERS. EX EQUIP.

Pn. 200-220-240v sec. 2.5v 45amps 30kv DC wkg. £3.00, carr. £1.50. Sec. 5v 3A 30kv DC wkg. £3.00, carr. £1. Potted types. Woden "C" Core: Pn. 230v sec. 2.5v 10A, -2.5v 5A, 2.5v 5A, three separate windings £4.50, pp. £1.

### H.T. SMOOTHING CHOKES

Parmeko potted type, 5H 280 m/A, 5H 200m/A, 10H 180m/A £2, pp. 75p. 5H 25m/A, 15H 75m/A £1, pp. 50p. Gardners: 15H 180m/A £3, pp. £1. 10H 300m/A £4, pp. £1. 100H 20m/A £1, pp. 80p. "C" core types: 0-7H 250m/A £1, pp. 50p. 70H 10m/A £1, pp. 50p. 20H 75m/A £1.75, pp. 50p. Potted swinging type: 5H 40m/A-4H 250m/A £2, pp. 75p. L.T. Chokes: 4.8m/H 10A £4, pp. £1. 150m/H 3A £3, pp. £1. Potted type: 100m/H 2A £4, pp. £1. 13m/H 1.5A £1.50, pp. 50p. Open swinging type: 60m/H 2A-180m/H 0.2A. Parmeko open type, twin coil 2+2m/H 12A £6, pp. £1. 50m/H 2A, fully shrouded £3, pp. 75p.

### PAINTON SWITCHED ATTENUATORS

600Ω in 15 steps. Stud rotary switch type, fully screened. Size 2 1/2 ins. dia. 2 1/2 ins. dia. spindle £1, pp. 25p.

### AC WKG BLOCK CAPACITORS BY FAMOUS MANUFACTURERS

| MFD     | Volts   | Price |
|---------|---------|-------|
| 0.25    | 1500VAC | 50p   |
| 0.75    | 440VAC  | 50p   |
| 1       | 470VAC  | 60p   |
| 1.25    | 380VAC  | 65p   |
| 2       | 400VAC  | 75p   |
| 2.4     | 360VAC  | 75p   |
| 2.5     | 360VAC  | 75p   |
| 2.7+0.1 | 700VAC  | £1.25 |
| 3       | 440VAC  | £1.00 |
| 3.5     | 250VAC  | £1.00 |
| 4       | 360VAC  | £1.25 |
| 5       | 440VAC  | £1.50 |
| 7.2     | 440VAC  | £1.00 |
| 8.4     | 250VAC  | £1.00 |
| 15      | 250VAC  | £1.75 |

PP up to 2 5MFD 25p, 2 7 to 1 1/2MFD 50p + 8p, on total 10MFD 400VDC £1.50, PP 50p.

### MULTI-TAPPED "C" CORE LT TRANSFORMERS

PN 110-220-240v. Four separate secs 1v, 2v, 3v, 21v, all at 5A, 1.3-9-10-12-21-3v 24-30-30-31-33-34v 5A can be obtained, £5.50 PPE!

### OIL FILLED BLOCK CAPACITORS

TCC: 8mfd 800v DC wkg. £1, pp. 35p; 1mfd 2000v DC wkg. 75p, pp. 35p; 1mfd 1500v DC wkg. 60p, pp. 25p; 1mfd 1000v DC wkg. 55p, pp. 25p; 1mfd 500v DC wkg. 30p, pp. 15p. 2mfd 200v DC wkg. Three for 50p, pp. 35p. Dubiiler: 8mfd 350v DC wkg. 50p, pp. 35p. 4mfd 1250v DC wkg. £1, pp. 35p; 2mfd 750v DC wkg. 50p, pp. 25p; 2mfd 600v DC wkg. 40p, pp. 25p; 0.1mfd 10kv DC wkg. 3kv RMS £2, pp. 75p; 0.1mfd 3000v DC wkg. 75p, pp. 25p. Hunts: 2mfd 350v DC wkg. 2mfd 200v DC wkg., either type, three for 50p, pp. 25p. American types 4-4-4-4+2+1 mfd 600v DC wkg. £3, pp. 75p; 8+8+4-4mfd 650v DC wkg. £3, pp. 75p; 6+4+2mfd 40v DC wkg. £2, pp. 75p; 7mfd 600v DC wkg. 75p, pp. 35p; 6mfd 600v DC wkg. 60p, pp. 25p; 4mfd 600v DC wkg. 50p, pp. 25p. TMC Special Offer: 2mfd 100v DC wkg. Cartons of 12 £1, pp. 50p; 50mfd 50v DC wkg. £1, pp. 25p. AC Wkg Types 15mfd 330v AC £1.80; 6mfd 300v AC 75p; 4mfd 400v AC 75p; 4mfd tubular 250v AC 80p.

### HIGH CAPACITY ELECTROLYTICS

Sprague 3600mfd 150v DC 85 degs. C. £1, pp.



# Wireless World Dolby<sup>TM</sup> noise reducer

Trademark of Dolby Laboratories Inc.

We are proud to announce the latest addition to our range of matching high fidelity units.

## Featuring

- switching for both encoding (low-level h.f. compression) and decoding
- a switchable f.m. stereo multiplex and bias filter
- provision for decoding Dolby f.m. radio transmissions (as in USA)
- no equipment needed for alignment
- suitability for both open-reel and cassette tape machines
- check tape switch for encoded monitoring in three-head machines

## The kit includes

- complete set of components for stereo processor
- regulated power supply components
- board-mounted DIN sockets and push-button switches
- fibreglass board designed for minimum wiring
- solid mahogany cabinet, chassis, twin meters, front panel, knobs, mounting screws and nuts

## Typical performance

Noise reduction better than 9dB weighted

Clipping level 16.5dB above Dolby level (measured at 1% third harmonic content)

Harmonic distortion 0.1% at Dolby level typically 0.05% over most of band, rising to a maximum of 0.12%

Signal-to-noise ratio: 75dB (20Hz to 20kHz, signal at Dolby level) at Monitor output

Dynamic Range >90dB  
30mV sensitivity.

**PRICE: £39.90 + VAT**

Also available ready built and tested ..... **Price £54.00 + VAT**

Calibration tapes are available for open-reel use and for cassette (specify which) ..... **Price £2.20 + VAT \***

Single channel plug-in Dolby<sup>TM</sup> PROCESSOR BOARDS (92 x 87mm) with gold plated contacts are available with all components ..... **Price £8.20 + VAT**

Single channel board with selected fet ..... **Price £2.50 + VAT**

Gold Plated edge connector ..... **Price £1.50 + VAT \***

Selected FETs **60p** each + VAT, **100p** + VAT for two, **£1.90** + VAT for four

Please add VAT @ 12½% unless marked thus\*, when 8% applies (or current rates)

We guarantee full after-sales technical and servicing facilities on all our kits, have you checked that these services are available from other suppliers?



# INTEGREX LTD.

Please send SAE for complete lists and specifications  
Portwood Industrial Estate, Church Gresley,  
Burton-on-Trent, Staffs DE11 9PT  
Burton-on-Trent (0283) 215432 Telex 377106

# INTEGREX

## S-2020TA STEREO TUNER / AMPLIFIER KIT

**SOLID MAHOGANY CABINET**

*A high-quality push-button FM Varicap Stereo Tuner combined with a 24W r.m.s. per channel Stereo Amplifier.*




**Brief Spec.** Amplifier Low field Toroidal transformer, Mag. input, Tape In/Out facility (for noise reduction unit, etc.), THD less than 0.1% at 20W into 8 ohms. Power on/off FET transient protection. All sockets, fuses, etc., are PC mounted for ease of assembly. Tuner section uses 3302 FET module requiring no RF alignment, ceramic IF, INTERSTATION MUTE, and phase-locked IC stereo decoder. LED tuning and stereo indicators. Tuning range 88—104MHz. 30dB mono S/N @ 1.2µV. THD 0.3%. Pre-decoder 'birdy' filter.

**PRICE: £58.95 + VAT**
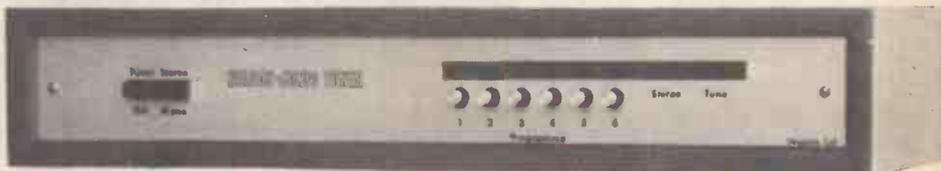
## NELSON-JONES STEREO FM TUNER KIT

*A very high performance tuner with dual gate MOSFET RF and Mixer front end, triple gang varicap tuning, and dual ceramic filter / dual IC IF amp.*



**Brief Spec.** Tuning range 88—104MHz. 20dB mono quieting @ 0.75µV. Image rejection — 70dB. IF rejection — 85dB. THD typically 0.4%. IC stabilized PSU and LED tuning indicators. Push-button tuning and AFC unit. Choice of either mono or stereo with a choice of stereo decoders.

*Compare this spec. with tuners costing twice the price.*

**Mono £32.40 + VAT**

**With ICPL Decoder £36.67 + VAT**

**With Portus-Haywood Decoder  
£39.20 + VAT**



Sens. 30dB S/N mono @ 1.2µV  
THD typically 0.3%  
Tuning range 88—104MHz  
LED sig. strength and stereo indicator

## STEREO MODULE TUNER KIT

*A low-cost Stereo Tuner based on the 3302 FET RF module requiring no alignment. The IF comprises a ceramic filter and high-performance IC Variable INTERSTATION MUTE. PLL stereo decoder IC. Pre-decoder 'birdy' filter*

**PRICE: Stereo £31.95 + VAT**



## S-2020A AMPLIFIER KIT

*Developed in our laboratories from the highly successful "TEXAN" design. PC mounting potentiometers, switches, sockets and fuses are used for ease of assembly and to minimize wiring*

*Power 'on/off' FET transient protection.*

**Typ Spec.** 24 + 24W r.m.s. into 8-ohm load at less than 0.1% THD. Mag. PU input S/N 60dB. Radio input S/N 72dB. Headphone output. Tape In/Out facility (for noise reduction unit, etc.). Toroidal mains transformer.

**PRICE: £33.95 + VAT**

**ALL THE ABOVE KITS ARE SUPPLIED COMPLETE WITH ALL METALWORK, SOCKETS, FUSES, NUTS AND BOLTS, KNOBS, FRONT PANELS, SOLID MAHOGANY CABINETS AND COMPREHENSIVE INSTRUCTIONS**

|   |                     |                                    |                    |
|---|---------------------|------------------------------------|--------------------|
| <b>BASIC NELSON-JONES TUNER KIT</b>                   | <b>£14.28 + VAT</b> | <b>PHASE-LOCKED IC DECODER KIT</b> | <b>£4.47 + VAT</b> |
| <b>BASIC MODULE TUNER KIT (stereo)</b>                | <b>£16.75 + VAT</b> | <b>PUSH-BUTTON UNIT</b>            | <b>£5.00 + VAT</b> |
| <b>PORTUS-HAYWOOD PHASE-LOCKED STEREO DECODER KIT</b> | <b>£8.00 + VAT</b>  |                                    |                    |

# Get a great deal from Marshall's

A. Marshall (London) Ltd Dept: WW  
 40-42 Cricklewood Broadway, London NW2 3ET  
 Tel: 01-452 0161/2 Telex: 21492  
 & 85 West Regent St Glasgow G2 2QD Tel: 041-332 4133  
 & 1 Straits Parade Fishponds Bristol BS16 2LX Tel: 0272 654201/2  
 Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat  
 Trade and export enquiries welcome. Please enquire for types not listed.  
**NEW 168 PAGE CATALOGUE WITH 500 NEW LINES 55p post paid (40p to callers)**

**Our range covers over 7,000 items. The largest selection in Britain. Top 200 ICs, TTL, CMOS & Linears**

|              |              |                |              |              |
|--------------|--------------|----------------|--------------|--------------|
| CA3020A 2.29 | LM382N 1.25  | NE556 1.05     | TAA560 1.60  | TCA280A 1.30 |
| CA3028A 1.01 | LM384N 1.45  | NE555 1.30     | TAA570 2.30  | TCA290A 3.13 |
| CA3028B 1.29 | LM386N 0.80  | NE556 1.65     | TAA611B 1.85 | TCA420A 1.84 |
| CA3030 1.24  | LM387N 1.05  | NE587 1.80     | TAA621 2.15  | TCA730 3.22  |
| CA3036 0.97  | LM388N 1.00  | SAS560         | TAA661B 1.32 | TCA740 2.76  |
| CA3045 1.40  | LM389N 1.00  | SAS570         | TAA700 3.91  | TCA750 2.30  |
| CA3046 0.89  | LM702C 0.75  | SO42P          | TAA930A 1.00 | TCA760 1.38  |
| CA3048 2.23  | LM709C 0.65  | 78001N 1.57    | TAA930B 1.05 | TCA800 3.13  |
| CA3049 1.66  | LM709N 0.45  | 78003N 2.55    | TAD100 1.85  | UAA170 2.00  |
| CA3052 1.82  | LM710C 0.80  | 78008K 2.50    | TBA120 0.65  | UAA180 2.00  |
| CA3053 0.60  | LM710N 0.60  | 78013N 1.70    | TBA400 1.50  | CD4000 0.20  |
| CA3080 0.68  | LM723C 0.86  | 78013ND 1.57   | TBA500 2.21  | CD4001 0.20  |
| CA3080A 1.88 | LM723N 0.75  | 78018K 2.50    | TBA500Q 2.30 | CD4002 0.20  |
| CA3086 0.51  | LM741C 0.85  | 78023N 1.70    | TBA510 2.21  | CD4006 1.10  |
| CA3088 1.59  | LM741N 0.50  | 78023ND 1.57   | TBA510Q 2.30 | CD4007 0.20  |
| CA3089 2.52  | LM741-B 0.40 | 78033N 2.55    | TBA520 2.21  | CD4008 0.97  |
| CA3090 3.80  | LM747N 0.90  | 78110N 1.46    | TBA520Q 2.30 | CD4009 0.57  |
| CA3130 0.94  | LM748-B 0.50 | 78115N 1.87    | TBA530 1.98  | CD4011 0.20  |
| LM301A 0.65  | LM748N 0.90  | 78116N 2.06    | TBA530Q 2.07 | CD4012 0.20  |
| LM301N 0.44  | LM1800 1.76  | 78131N 1.30    | TBA540 2.21  | CD4013 0.57  |
| LM304 2.45   | LM1808 1.92  | 78226N 1.94    | TBA540Q 2.30 | CD4014 1.01  |
| LM307N 0.65  | LM1828 1.75  | 78227N 1.51    | TBA550 3.13  | CD4014 0.57  |
| LM308N 1.17  | LM3301N 0.85 | 78228N 1.75    | TBA550Q 3.22 | CD4015 1.01  |
| LM309K 2.10  | LM3302N 1.40 | 78530N 0.91    | TBA560Q 3.22 | CD4016 0.56  |
| LM317K 3.00  | LM3401N 1.60 | 78532N 1.50    | TBA570 1.29  | CD4017 1.01  |
| LM318N 2.25  | LM3900 0.75  | 78533N 1.30    | TBA570Q 1.38 |              |
| LM323K 6.40  | LM3905 1.60  | 78544N 1.44    | TBA641Q 2.50 |              |
| LM339N 1.75  | LM3909 0.68  | 78545N 2.09    | TBA651 1.80  |              |
| LM348N 1.91  | MC1035 1.75  | 78546N 1.44    | TBA700 1.52  |              |
| LM360N 2.75  | MC1303 1.47  | 78550N 0.41    | TBA700Q 1.61 |              |
| LM370N 3.00  | MC1306 1.95  | 78552N 0.85    | TBA720Q 2.30 |              |
| LM371N 2.25  | MC1306 1.00  | 78570N 2.08    | TBA750 1.88  |              |
| LM372N 2.15  | MC1310 1.91  | 78620N 1.10    | TBA750Q 2.07 |              |
| LM373N 2.25  | MC1312 1.98  | 78650N 1.10    | TBA800 1.20  |              |
| LM374N 2.25  | MC1327 1.54  | 78660N 0.60    | TBA810 1.16  |              |
| LM377N 1.75  | MC1330 0.92  | 78668N 7/8 1/4 | TBA920 1.03  |              |
| LM378N 2.25  | MC1350 0.75  | TAA310A 1.50   | TBA920 1.79  |              |
| LM379S 3.95  | MC1351 1.20  | TAA320A 1.15   | TBA920Q 2.99 |              |
| LM380-B 0.90 | MC1352 0.97  | TAA350A 2.48   | TBA940 1.62  |              |
| LM380N 0.98  | MC1357 1.45  | TAA521 1.00    | TCA160C 1.85 |              |
| LM381A 2.45  | MC1458 0.91  | TAA522 1.90    | TCA160B 1.61 |              |
| LM381N 1.60  | NE555 0.53   | TAA550 0.60    | TCA270 2.25  |              |

**POPULAR SEMICONDUCTORS (A very small selection from our vast stocks, please enquire about devices not listed.)**

|             |              |              |              |             |             |
|-------------|--------------|--------------|--------------|-------------|-------------|
| AF139 0.89  | 2N698 0.62   | 2N2923 0.14  | 2N3638A 0.66 | 2N3905 0.22 | 2N5449 0.19 |
| AF239 0.74  | 2N706 0.24   | 2N2924 0.15  | 2N3662 0.23  | 2N3906 0.22 | 2N5457 0.32 |
| ASY28 1.20  | 2N718 0.27   | 2N2926G 0.13 | 2N3663 0.26  | 2N3962 0.85 | 2N5458 0.33 |
| ASY55 0.65  | 2N914 0.35   | 2N2926Y 0.13 | 2N3702 0.17  | 2N4058 0.20 | 2N5485 0.38 |
| BC118 0.16  | 2N929 0.26   | 2N3019 0.55  | 2N3703 0.15  | 2N4060 0.20 | 2N5703 3.85 |
| BC154 0.27  | 2N930 0.26   | 2N3053 0.30  | 2N3704 0.15  | 2N4122 0.25 | 2N5702 3.00 |
| BC167A 0.12 | 2N1132 0.60  | 2N3055 0.70  | 2N3705 0.15  | 2N4123 0.17 | 40232 0.50  |
| BC167B 0.12 | 2N1483 1.20  | 2N3108 0.50  | 2N3706 0.16  | 2N4125 0.17 | 40311 0.45  |
| BC169B 0.12 | 2N1613 0.35  | 2N3133 0.45  | 2N3707 0.18  | 2N4250 0.24 | 40363 1.20  |
| BC171B 0.15 | 2N1711 0.37  | 2N3392 0.16  | 2N3708 0.16  | 2N4266 0.20 | 40673 0.73  |
| BC182 0.11  | 2N1893 0.38  | 2N3393 0.15  | 2N3709 0.18  | 2N4264 0.35 | AC126 0.37  |
| BC182L 0.14 | 2N2080 5.00  | 2N3417 0.40  | 2N3710 0.16  | 2N4286 0.20 | AC127 0.44  |
| BC184L 0.14 | 2N2219 0.30  | 2N3439 0.88  | 2N3711 0.18  | 2N4288 0.20 | AC152 0.50  |
| BC212A 0.14 | 2N2221 0.22  | 2N3441 0.85  | 2N3771 1.85  | 2N4403 0.18 | AC153 0.49  |
| BC214L 0.16 | 2N2222 0.26  | 2N3553 1.05  | 2N3773 2.90  | 2N4822 0.75 | AC187K 0.55 |
| BD135 0.37  | 2N2222A 0.25 | 2N3565 0.15  | 2N3794 0.20  | 2N4916 0.20 | AC188K 0.55 |
| BF195 0.13  | 2N2368 0.25  | 2N3566 0.15  | 2N3819 0.36  | 2N5129 0.20 | ACV22 0.40  |
| BFX84 0.40  | 2N2369 0.25  | 2N3567 0.17  | 2N3854A 0.25 | 2N5192 0.75 | ACV30 0.80  |
| BFY51 0.38  | 2N2646 0.75  | 2N3571 3.70  | 2N3856A 0.25 | 2N5222 0.18 | AF108 0.55  |
| BSY65 0.40  | 2N2906 0.37  | 2N3572 3.00  | 2N3859A 0.21 | 2N5245 0.34 | AF109 0.75  |
| 2N697 0.30  | 2N2906 0.28  | 2N3638 0.16  |              | 2N5447 0.15 | AF115 0.65  |

If the type you require is not listed, please enquire. This is just a very small part of our range.

A selection from our range:

- GR Pocket TTY **£173.00**
- 1702 Prom Simulator **£270.00**
- S1702 Volatile Simulator **£70.00**
- S1702N Non Volatile Simulator **£97.00**
- SP2 (5V) Manual Programmer **£194.00**
- SP2 (main) **£226.00**
- SE15 Prom Eraser **£98.00**
- I SP-BA-5000 SC/MP Chip **£15.50**
- INS 808A Chip **£23.45**
- Vero CPU Board **£33.00**
- Vero Memory Board **£32.00**
- Vero Interphase Board **£33.00**
- SC/MP Data Pack **£1.50**
- LCDS low cost development system **£370.00**

**WRITE FOR OUR SPECIAL PRODUCTS LIST**

Prices correct as at 17 March, but please add VAT, p&p 30p

**SEE US AT THE ALL ELECTRONICS SHOW - GROSVENOR HOUSE, 19-21 APRIL**

## DATA AND COMMUNICATIONS TERMINALS

Teletype 28, 32, 33, 35, 40  
 TermiNet 30, 300 & 1200 (30 and 120 cps)  
 Teleterm 1132 and 1200 series (portable/fixed 30 cps)  
 with integral coupler and RS 232C)  
 Other page printers (by Siemens, ITT Creed, etc.)

- ★ Spares, repairs, overhauls and maintenance
- ★ Other types and models available
- ★ Refurbished units also available
- ★ Short and long period rentals
- ★ Minicomputer interfaces
- ★ Quantity discounts
- ★ Immediate delivery

**TELEPRINTER EQUIPMENT LTD.**  
 70-80 AKEMAN STREET  
 TRING, HERTS., U.K.

Telephone 0442-82-4011  
 Cables RAHNO Tring  
 Telex 82362  
 A/B Batelcom Tring

WW-034 FOR FURTHER DETAILS

## RADFORD HD250

### High Definition Stereo Amplifier

**A new standard for sound reproduction in the home! We believe that no other amplifier in the world can match the overall specification of the HD250.**

- Rated power output: 50 watts av. continuous per channel into any impedance from 4 to 8 ohms, both channels driven.
- Maximum power output: 90 watts av. per channel into 5 ohms.
- Distortion, preamplifier: Virtually zero (cannot be identified or measured as it is below inherent circuit noise.)
- Distortion, power amplifier: Typically 0.006% at 25 watts, less than 0.02% at rated output (Typically 0.01% at 1 KHz)
- Hum and noise: Disc.—83dBV measured flat with noise band width 23 KHz (ref. 5mV); —88dBV "A" weighted (ref. 5mV)
- Line —85 dBV measured flat (ref. 100V)  
 —88dBV "A" weighted (ref. 100V)

Hear the HD250 at  
**SWIFT OF WILMSLOW**  
 Dept. WW, 5 Swan Street, Wilmslow, Cheshire  
 (Tel: 26213)

Mail Order and Personal Export enquiries: Wilmslow Audio, Swan Works, Bank Square, Wilmslow (Tel. 29599)

**Now available ZD100 power amplifier and ZD22 pre-amplifier**

WW-063 FOR FURTHER DETAILS

RETURN OF POST MAIL ORDER SERVICE

**BSR HI-FI AUTOCHANGER**  
**STEREO AND MONO £11.95** Post 75p  
 Plays 12", 10" or 7" records, Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. A.C. 200/250V. Size 13½-11¼in. 3 speeds. Above motor board 3¼in. Below motor board 2½in. with STEREO and MONO CARTRIDGE B.S.R. SINGLE PLAYER similar to above with stereo cartridge and cueing device, large turntable £13.50 B.S.R. P128 with magnetic cartridge. Balanced arm cueing device £23.50. Post £1.  
**PORTABLE PLAYER CABINET**  
 Modern design. Rexine covered. Vynair front grille. Chrome fittings. Size 17 x 15 x 8in. approx. **£4.50** Post 75p  
 \*Motor board cut for BSR or Garrard deck

**HEAVY METAL PLINTHS**  
 With P.V.C. Cover. Cut out for most B.S.R. or Garrard decks. Silver grey finish. **£6.50** Post £1.50  
 Model "A" Size 12½ x 14¼ x 7½in.  
 Model "B" Size 16 x 13¼ x 7in. **£7.50**.  
 Extra large plinth & cover, teak wood base. Size 20" x 17½" x 9" **£19.50**. Callers only.

**COMPLETE STEREO SYSTEM**  
 Two full size loudspeakers 13¼ x 10 x 3¼in. Player unit clips to loudspeakers making it extremely compact, overall size only 13¼ x 10 x 8½in., 3 watts per channel, plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls Attractive Teak finish 240V a.c. mains **£22.50** £1 carriage



**SPECIAL OFFER!**  
**SMITH'S CLOCKWORK 15 AMP TIME SWITCH**  
**0-60 MINUTES £2.95** Post 35p  
 Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Brand new and fully guaranteed.  
 0-6 Hour version—**£3.30**  
 TEAKWOOD LOUDSPEAKER GRILLES will easily fit to baffle board. Size 10½ x 7½in—45p.

**R.C.S. "MINOR" 10 watt AMPLIFIER KIT**  
 This kit is suitable for record players, guitars, tape playback, electronic instruments or small P.A. systems. Two versions available Mono, **£11.25**; Stereo, **£18**. Post 45p. Specification 10W per channel, input 100mV, size 9½ x 3 x 2in. approx. S.A.E. details. Full instructions supplied. AC mains powered.

**VOLUME CONTROLS**  
 5kΩ to 2MΩ. LOG or LIN. L/S 35p. D.P. 60p. STEREO L/S 85p. D.P. £1. Edge 5K. S.P. Transistor 45p.  
**80 Ohm Coax 8p yd.**  
 STANDARD TYPE VHF. FRINGE LOW LOSS 15p yd. Ideal 625 and colour PLUGS 10p. SOCKETS 10p. LINE SOCKETS 18p. OUTLET BOXES 50p.

**ELAC HI-FI SPEAKER**  
**8in. TWIN CONE**  
 Dual cone plastisolized roll surround. Large ceramic magnet. 50-16,000 c/s. Bass resonance 55 c/s. 8 ohm impedance. 10 watts. music power. **£3.95** Post 35p

**E.M.I. 13½ x 8in. SPEAKER SALE!**  
 With tweeter and crossover. 10 watt. State 3 or 8 ohm. As illustrated.  
**£5.95** Post 45p  
 Ditto 15 watts. 8 or 15 ohm. **£8.50** Post 65p

**Bookshelf Cabinet**  
 Teak finish. For EMI 13 x 8 speakers. **£7.50** Post £1.00

**THE "INSTANT" BULK TAPE ERASER AND HEAD DEMAGNETISER.** Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S.A.E. Will also demagnetise small tools. **£4.50** Post 50p

**BLANK ALUMINIUM CHASSIS.** 6 x 4—70p; 8 x 6—90p; 10 x 7—£1.15; 12 x 8—£1.35; 14 x 9—£1.50; 16 x 6—£1.45; 16 x 10—£1.70. ANGLE ALLI. 6 x ¾ x ¾in—15p.  
**ALUMINIUM PANELS.** 6 x 4—17p; 8 x 6—24p; 14 x 3—25p; 10 x 7—35p; 12 x 8—43p; 12 x 5—30p; 16 x 6—43p; 14 x 9—52p; 12 x 12—68p; 16 x 10—75p.  
**MANY ALI BOXES IN STOCK. MANY SIZES**

**ELAC 9 x 5in HI-FI SPEAKER**  
**£3.45** Post 35p  
 This famous unit now available, 10 watts, 8 ohm.

**R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS**  
 All parts and instructions with Zener diode, printed circuit rectifiers and double wound mains transformer. Input 200/240V a.c. Output voltages available, 6 or 7.5 or 9 or 12V d.c. up to 100mA or less. Size 3 x 2½ x 1½in. Please state voltage required. **£2.95** Post 45p  
**R.C.S. POWER PACK KIT**  
 12 VOLT, 750mA. Complete with printed circuit board and assembly instructions. **£3.35** Post 30p  
 12 VOLT 300mA KIT, **£3.15**; 9 VOLT 1 AMP KIT, **£3.35**.

**R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER — BRITISH MADE**  
 Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with battery 9-12V or H.T. line 200-300V d.c. operation. Size: 1¼ x 1¼ x ¾in. Response 25 c/s to 25 kc/s. 26 dB gain. For use with valve or transistor equipment. **£1.45** Post 30p  
 Full instructions supplied. Details S.A.E.

**ELECTRO MAGNETIC PENDULUM MECHANISM**  
 1.5V d.c. operation over 300 hours continuous on SP2 battery, fully adjustable swing and speed. Ideal displays, teaching electron magnetism or for metronome, strobe, etc. **95p** Post 30p

**MAINS TRANSFORMERS** ALL POST 50p  
 250-0-250V 70mA, 6.5V, 2A **£3.45**  
 250-0-250 80mA, 6.3V 3.5A, 6.3V 1A or 5V 2A **£4.60**  
 350-0-350 80mA, 6.3V 3.5A, 6.3V 1A or 5V 2A **£5.80**  
 300-0-300V 120mA, 6.3V 4A C.T.; 6.3V 2A **£7.00**  
 MIDGET 220V 45mA, 6.3V 2A **£1.75**  
 HEATED TRANS. 6.3V ½ amp **£1**; 3 amp **£1.40**  
 GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V **£4.60**. 1 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£4.60**. 2 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£7.30**. 3 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£8.70**. 5 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£11.25**. 6.06V 500mA **£1**, 9V 1 amp, **£1**, 12V 300mA, **£1**, 12V 500mA, **£1**, 12V 750mA, **£1**, 10V, 30V, 40V, 2 amp, **£2.75**, 20V, 3 amp, **£2.45**, 40V, 2 amp, **£2.95**, 30V 5A and 34V 2ACT **£3.45**, 16V, 2 amp, **£2.20**, 0, 5, 8, 10, 16V, ½ amp, **£1.95**, 20V ½ amp, **£1.75**, 20V, 1 amp, **£2.20**, 20V 3 amp, **£2.50**, 20-0-20V 1 amp, **£2.95**, 30V 1½ amp, **£2.75**; 20V, 40V, 60V or 20-0-20V, 1 amp, **£3.50**.  
 AUTO TRANSFORMERS, 115V to 230V or 230V to 115V 150W **£5**; 250W **£6**; 400W **£7**; 500W **£8**.  
 FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs, 1½ amp **40p**; 2 amp **55p**; 4 amp **85p**.  
 CHARGER TRANSFORMERS: 1½ amp **£2.75**; 4 amp **£4.60**. 12V, 1½A HALF WAVE Selenium Rectifier, 25p.

**R.C.S. BOOKSHELF SPEAKERS**  
 Size 14½in. x 9½in. x 6in. 50 to 14,000 cps B watts rms. 8 or 4 ohms. **£16 pair** Post £1.30

**KUBA-KOPENHAGEN STEREO**  
**TUNER-AMPLIFIER CHASSIS AM-FM 5+5 WATT**  
 This Continental 4-band radiogram chassis uses first class quality components throughout. Features: Large fascia panel with 7 push buttons for medium, long, short, VHF-FM, AFC, phono, mains, on-off, 4-rotary controls, tuning, volume, tone, balance. Facia size 17 x 4½ inches. Chassis size 17 x 4½ x 5½ inches. DIN-connector sockets for tape record/playback, loudspeakers, phono pick-up, external FM-AM aerials. Automatic stereo beacon light. Built-in ferrite rod aerial for medium/longwave. A.C. 240V mains. Circuit supplied. **£33.50** Post £1.60  
 Above speakers are suitable

**LOW VOLTAGE ELECTROLYTICS**  
 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.  
 500mF 12V 15p; 25V 20p; 50V 30p.  
 1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p.  
 2000mF 6V 25p; 25V 42p; 50V 57p.  
 2500mF 50V 62p; 3000mF 25V 47p; 50V 65p.  
 3900mF 100V **£1.60**.  
 4700mF 63V **£1.20**.  
 5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p.  
**SHORT WAVE 100pF** air spaced gangable tuner, 95p.  
**TRIMMERS** 10pF, 30pF, 50pF, 50pF, 100pF, 150pF, 15p.  
**CERAMIC**, 1pF to 0.01mF, 5p. Silver Mica 2 to 5000pF, 5p.  
**PAPER** 350V-0.1 7p; 0.5 13p; 1mF 150V 15p; 2mF 150V 15p; 500V-0.001 to 0.05 5p; 0.1 10p; 0.25 13p; 0.47 25p.  
**MICRO SWITCH SINGLE POLE CHANGEOVER** 20p.  
**SUB-MIN MICRO SWITCH**, 25p. Single pole change over.  
**TWIN GANG**, 385 + 385pF 50p; 500pF standard 75p; 365 + 365 + 25 + 25pF, Slow motion drive 65p.  
**120pF TWIN GANG**, 50p; 365pF **TWIN GANG**, 50p.  
**NEON PANEL INDICATORS** 250V. Amber or red 30p.  
**RESISTORS**, ¼W, ½W, 1W, 200 2p; 2W, 10p; 10Ω to 10M.  
**HIGH STABILITY**, ½W 2% 10 ohms to 6 meg., 12p.  
 Dito 5%. Preferred values 10 ohms to 10 meg., 5p.  
**WIRE-WOUND RESISTORS** 5 watt, 10 watt, 15 watt, 10 ohms to 100K 12p each  
**TAG STRIP** 28-way 12p.  
**TAPE OSCILLATOR COIL**, Valve type, 35p.  
**BRIDGE RECTIFIER** 200V PIN ½ amp 50p.  
**TOGGLE SWITCHES** S.P. 20p, D.P.S.T. 25p, D.P.D.T. 30p.  
**MANY OTHER TOGGLES IN STOCK**  
**PICK-UP CARTRIDGES** ACOS GP91 **£1.50**, GP93 **£2.50**.  
**SONOTONE** stereo **£2.00**.

**BAKER MAJOR 12" £14.95** Post £1.00  
 30-14,500 c/s, 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 25W. NOTE: 4 or 8 or 16 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. Post **£1.60p** each. Please state 3 or 8 or 15 ohms. **£18.95**

**BAKER "BIG-SOUND" SPEAKERS** Post £1.00 each.  
 'Group 25' 12in. **£11.95**, 30W 4 or 8 or 16 ohm  
 'Group 35' 12in. **£13.95**, 40W 4 or 8 or 16 ohm  
 'Group 50/15' 15in. **£24.95**, 75W 8 or 16 ohm

**BAKER LOUDSPEAKER, 12 INCH. 60 WATT. GROUP 50/12, 8 OR 15 OHM HIGH POWER. FULL RANGE PROFESSIONAL QUALITY. RESPONSE 30-16,000 CPS. MASSIVE CERAMIC MAGNET WITH ALUMINIUM PRESENCE CENTRE DOME.** Post **£1.60**

**TEAK VENEERED HI-FI SPEAKERS AND CABINETS**  
 For 12in. or 10in. speaker 20x13x12in. **£14.50** Post £2  
 For 13x8in. or 8in. speaker **£7.50** Post £1  
 For 6½in. speaker and tweeter 12x8x6in. **£5.80** Post 75p  
 Many other cabinets in stock. Phone your requirements.

**R.C.S. 100 watt VALVE AMPLIFIER CHASSIS**  
 Four inputs. Four way mixing, master volume, treble and bass controls. Suits all speakers. This professional quality amplifier chassis is suitable for all groups, disco, P.A., where high quality power is required. 5 speaker outputs. A/C mains operated. Slave output socket. Produced by demand for a quality valve amplifier. 100V line output to order. Suitable carrying cab **£14**. Price **£85** carr. **£2.50**

**SPEAKER COVERING MATERIALS.** Samples Large S.A.E. **LOUDSPEAKER CABINET WADDING** 18in. wide 20p ft. Horn Tweeters 2-16kc/s, 10W 8 ohm or 15 ohm **£3.60**. De Luxe Horn Tweeters 3-18kc/s, 30W, 8 ohm, **£7.50**. **CROSSOVERS, TWO-WAY 3000 c/s** 3 or 8 or 15 ohm **£1.90**, 3-way 950 cps/3000 cps, **£2.20**. **LOUDSPEAKERS P.M. 3 OHM** 7x4in. **£1.50**; 6½in., **£1.80**; 8x5in., **£1.90**; 8in., **£1.95**. **SPECIAL OFFER:** 80 ohm, 2½in., 2½in., 35 ohm, 3in., 25 ohm, 2½in., 3in., 5x3in., 7x4in., 8 ohm, 2½in., 3in., 3½in., 5in., 15 ohm, 2in., 3½in., dia. 6x4in., 7x4in., 5x3in., 3 ohm, 2½in., 2½in., 3½in., 5in. dia. **£1.25** each.

**PHILIPS LOUDSPEAKER, 8in.**, 4 ohms, 4 watts, **£1.95**  
**RICHARD ALLAN TWIN CONE LOUDSPEAKERS** 8in. diameter 4W **£2.50**, 10in. diameter 5W **£2.95**; 12in. diameter 6W **£3.50**, 3/8/15 ohms, please state.  
**PIEZO ELECTRIC HORN TWEETER.** Handles up to 100 watts. No crossover required. **£10.95**.  
 Tweeter Volume Control 15 ohms 10W with one inch long threaded bush for wood panel mounting ¼in. spindle. **65p**.

**BAKER 150 WATT PROFESSIONAL MIXER AMPLIFIER**  
 All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 4 8/15 ohms. a.c. Mains. Separate treble and bass controls. Master volume control. Guaranteed. Details S.A.E. **£68** £1.50 carr.  
**NEW MODEL MAJOR—50 watt**, 4 input, 2 vol. Treble and bass. Ideal disco amplifier. **£49** Carr. **£1**

**100 WATT DISCO AMPLIFIER CHASSIS**  
 volume, treble, bass controls. 500 M.V. or 1 volt input. Four loudspeaker outputs 4 to 16 ohm. All transistor **£52**

**BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER**  
 Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9V. **£5.95**  
**TWO STEREO CHANNEL VERSION** **£7.50**  
**JARGAIN 3 WATT AMPLIFIER.** 4 Transistor Push-Pull Ready Built, with volume, Treble and bass controls. 18 volt d.c. Mains Power Pack **£3.45**

**ALUMINIUM HEAT SINKS.** Finned type. Sizes 6½" x 4½" x 2¼" 95p. 6½" x 2" x 2¼" 65p.  
**BALANCED TWIN RIBBON FEEDER** 300 ohms. 5p yd.  
**JACK SOCKET Std.** open-circuit 20p, closed circuit 25p;  
 Chrome Lead-Socket 45p. Mono or Stereo.  
 Phono Plugs 8p. Phono Socket 8p.  
**JACK PLUGS Std.** Chrome 30p; Plastic 25p; 3.5mm 15p.  
**STEREO JACK PLUG** 30p. **SOCKET** 25p.  
**DIN SOCKETS** Chassis 3-pin 10p, 5-pin 10p.  
**DIN SOCKETS FREE** 3-pin 25p; 5-pin 25p. **DIN PLUGS** 3-pin 25p; 5-pin 25p. **VALVE HOLDERS**, 10p; **CANS** 10p.

**R.C.S. SOUND TO LIGHT KIT**  
 Kit of parts to build a 3 channel sound to light unit. 1,000 watts per channel. **£14**. Post 35p. Easy to build. Full instructions supplied. Cabinet **£3**.

**PERIOD LOUDSPEAKER CABINETS.** Two styles available, Regency and Queen Anne. Size approximately 34 x 19 x 16in. These cabinets are slightly soiled and are priced from **£10** each. Callers only.

# PAKS - PARTS - AUDIO MODULES

## PANEL METERS

### 4" RANGE

|         |      |       |
|---------|------|-------|
| Value   | No.  | Price |
| 0-50UA  | 1302 | £4.50 |
| 0-100UA | 1303 | £4.50 |
| 0-500UA | 1304 | £4.50 |
| 0-1MA   | 1305 | £6.00 |
| 0-50V   | 1306 | £6.00 |

### 2" RANGE

|         |      |       |
|---------|------|-------|
| Value   | No.  | Price |
| 0-50UA  | 1307 | £3.50 |
| 0-100UA | 1308 | £3.50 |
| 0-500UA | 1309 | £3.50 |
| 0-1MA   | 1310 | £3.50 |
| 0-50V   | 1311 | £3.50 |

### MR2P TYPE

|        |      |       |
|--------|------|-------|
| Value  | No.  | Price |
| 0-50UA | 1313 | £4.80 |
| 0-1MA  | 1315 | £3.20 |

### EDGEWISE

|         |      |       |
|---------|------|-------|
| Value   | No.  | Price |
| 0-1MA   | 1316 | £4.05 |
| 0-500UA | 1317 | £4.05 |

### MINIATURE BALANCE/TUNING METER

|             |      |       |
|-------------|------|-------|
| Value       | No.  | Price |
| 100/0/100MA | 1318 | £1.95 |

### BALANCE/TUNING

|             |      |       |
|-------------|------|-------|
| Value       | No.  | Price |
| 100/0/100UA | 1319 | £2.00 |

### MIN. LEVEL METER

|       |      |       |
|-------|------|-------|
| Value | No.  | Price |
| 1320  | 1320 | £1.95 |

### Vu METER

|       |      |       |
|-------|------|-------|
| Value | No.  | Price |
| 1321  | 1321 | £2.00 |

### MINI-MULTI-METER

|       |      |       |
|-------|------|-------|
| Value | No.  | Price |
| 1322  | 1322 | £5.95 |

### HIGH SENSITIVITY TEST METER

|       |      |        |
|-------|------|--------|
| Value | No.  | Price  |
| 1324  | 1324 | £19.78 |

## TRANSISTORS

BRAND NEW - FULLY GUARANTEED

| Type    | Price | Type   | Price | Type    | Price | Type     | Price | Type    | Price | Type    | Price | Type | Price | Type | Price |
|---------|-------|--------|-------|---------|-------|----------|-------|---------|-------|---------|-------|------|-------|------|-------|
| AC126   | £0.16 | BC108C | £0.08 | BC550   | £0.14 | BFV52    | £0.14 | TIP2955 | £0.95 | 2N3706  | £0.07 |      |       |      |       |
| AC127   | £0.14 | BC147  | £0.09 | BC555   | £0.14 | BP19     | £0.38 | TIP3055 | £0.75 | 2N3708A | £0.07 |      |       |      |       |
| AC128   | £0.12 | BC148  | £0.09 | BC557   | £0.13 | BP20     | £0.38 | TIS43   | £0.22 | 2N3709  | £0.07 |      |       |      |       |
| AC128K  | £0.12 | BC149  | £0.09 | BC558   | £0.12 | BP19B    | £0.14 | TIS43B  | £0.22 | 2N3710  | £0.07 |      |       |      |       |
| AC132   | £0.15 | BC157  | £0.12 | BC559   | £0.14 | 20 MP    | £0.80 | UT46    | £0.20 | 2N3711  | £0.07 |      |       |      |       |
| AC134   | £0.15 | BC158  | £0.12 | BD115   | £0.50 | BR39     | £0.45 | ZTX107  | £0.10 | 2N3819  | £0.20 |      |       |      |       |
| AC137   | £0.15 | BC159  | £0.12 | BD116   | £0.80 | BU105    | £1.90 | ZTX108  | £0.10 | 2N3820  | £0.40 |      |       |      |       |
| AC141   | £0.18 | BC167  | £0.12 | BD121   | £0.65 | BU105/02 | £1.95 | ZTX109  | £0.10 | 2N3821  | £0.60 |      |       |      |       |
| AC141K  | £0.20 | BC168  | £0.12 | BD123   | £0.65 | BU204    | £1.70 | ZTX300  | £0.12 | 2N3823  | £0.40 |      |       |      |       |
| AC142   | £0.18 | BC169  | £0.12 | BD124   | £0.70 | BU205    | £1.70 | ZTX500  | £0.14 | 2N4058  | £0.12 |      |       |      |       |
| AC176   | £0.12 | BC189C | £0.12 | BD131   | £0.35 | BU208    | £2.40 | 2N1613  | £0.20 | 2N4059  | £0.14 |      |       |      |       |
| AC176K  | £0.26 | BC170  | £0.10 | BD132   | £0.38 | BU208/02 | £2.95 | 2N1711  | £0.20 | 2N4080  | £0.14 |      |       |      |       |
| AC178   | £0.25 | BC171  | £0.10 | BD131/1 | £1.22 |          |       | 2N1889  | £0.45 | 2N4061  | £0.12 |      |       |      |       |
| AC179   | £0.25 | BC172  | £0.10 | 132 MP  | £0.80 | MJE2955  | £0.88 | 2N1890  | £0.45 | 2N4062  | £0.12 |      |       |      |       |
| AF115K  | £0.20 | BC173  | £0.12 | BD133   | £0.65 | MJE3055  | £0.60 | 2N1893  | £0.30 | 2N4284  | £0.18 |      |       |      |       |
| AC180K  | £0.30 | BC177  | £0.16 | BD135   | £0.38 | MJE3440  | £0.45 | 2N2147  | £0.78 | 2N4285  | £0.18 |      |       |      |       |
| AC181   | £0.20 | BC178  | £0.16 | BD136   | £0.36 | MPB113   | £0.48 | 2N2148  | £0.70 | 2N4286  | £0.18 |      |       |      |       |
| AC181K  | £0.30 | BC179  | £0.16 | BD137   | £0.38 | MPF102   | £0.35 | 2N2160  | £0.80 | 2N4287  | £0.18 |      |       |      |       |
| AC187   | £0.16 | BC180  | £0.25 | BD138   | £0.45 | MPF104   | £0.39 | 2N2192  | £0.38 | 2N4288  | £0.18 |      |       |      |       |
| AC187K  | £0.26 | BC181  | £0.25 | BD139   | £0.54 | MPF105   | £0.39 | 2N2193  | £0.38 | 2N4289  | £0.18 |      |       |      |       |
| AC188   | £0.16 | BC182  | £0.11 | BD140   | £0.60 | MPSA05   | £0.20 | 2N2194  | £0.38 | 2N4290  | £0.18 |      |       |      |       |
| AC188K  | £0.26 | BC183  | £0.10 | BD139/1 | £0.20 | MPSA05   | £0.20 | 2N2217  | £0.22 | 2N4291  | £0.18 |      |       |      |       |
| AD140   | £0.60 | BC183K | £0.10 | 140 MP  | £1.20 | MPSA5    | £0.20 | 2N2218  | £0.22 | 2N4292  | £0.18 |      |       |      |       |
| AD142   | £0.85 | BC184  | £0.10 | BD155   | £0.80 | MPSA66   | £0.20 | 2N2218A | £0.20 | 2N4293  | £0.18 |      |       |      |       |
| AD143   | £0.75 | BC184K | £0.10 | BD175   | £0.60 | OC22     | £1.50 | 2N2219  | £0.20 | 2N4292  | £0.55 |      |       |      |       |
| AF114   | £0.20 | BC207  | £0.11 | BD176   | £0.60 | OC23     | £1.50 | 2N2319A | £0.24 | 2N4923  | £0.65 |      |       |      |       |
| AD161   | £0.38 | BC208  | £0.11 | BD177   | £0.60 | OC25     | £0.88 | 2N2319B | £0.24 | 2N4924  | £0.65 |      |       |      |       |
| AD162   | £0.38 | BC209  | £0.12 | BD178   | £0.88 | OC24     | £1.40 | 2N2904A | £0.21 | 2N5136  | £0.10 |      |       |      |       |
| AD161/1 | £0.75 | BC212  | £0.11 | BD179   | £0.75 | OC26     | £0.60 | 2N2905  | £0.18 | 2N5138  | £0.10 |      |       |      |       |
| 161 MP  | £0.75 | BC212L | £0.11 | BD201/1 | £1.70 | OC28     | £0.90 | 2N2905A | £0.21 | 2N5194  | £0.56 |      |       |      |       |
| AF114   | £0.20 | BC213  | £0.11 | 202 MP  | £0.80 | OC29     | £1.00 | 2N2906  | £0.16 | 2N5245  | £0.28 |      |       |      |       |
| AF115   | £0.20 | BC214  | £0.11 | BD202   | £0.80 | OC35     | £0.90 | 2N2906A | £0.19 | 2N5294  | £0.34 |      |       |      |       |
| AF116   | £0.20 | BC214  | £0.12 | BD204   | £0.80 | OC36     | £0.90 | 2N2907  | £0.18 | 2N5295  | £0.32 |      |       |      |       |
| AF117   | £0.20 | BC214L | £0.12 | BD203/3 | £0.70 | OC70     | £0.15 | 2N2907A | £0.22 | 2N5457  | £0.32 |      |       |      |       |
| AF118   | £0.40 | BC237  | £0.16 | 204 MP  | £1.70 | OC71     | £0.15 | 2N2926G | £0.09 | 2N5458  | £0.32 |      |       |      |       |
| AF124   | £0.30 | BC238  | £0.16 | BDY20   | £0.80 | TIC44    | £0.29 | 2N2926Y | £0.08 | 2N5459  | £0.38 |      |       |      |       |
| AF125   | £0.30 | BC251  | £0.15 | BDX77   | £0.90 | TIC45    | £0.29 | 2N29260 | £0.08 | 2N5551  | £0.30 |      |       |      |       |
| AF126   | £0.30 | BC251L | £0.15 | BDX78   | £0.90 | TIP29A   | £0.44 | 2N29268 | £0.08 | 2N6027  | £0.32 |      |       |      |       |
| AF127   | £0.32 | BC301  | £0.30 | BF458   | £0.37 | TIP29B   | £0.52 | 2N29268 | £0.08 | 2N6121  | £0.70 |      |       |      |       |
| AF139   | £0.58 | BC302  | £0.28 | BF459   | £0.38 | TIP29C   | £0.52 | 2N3053  | £0.16 | 2N6122  | £0.70 |      |       |      |       |
| AF180   | £0.58 | BC303  | £0.32 | BF594   | £0.38 | TIP30A   | £0.50 | 2N3054  | £0.40 | 40311   | £0.36 |      |       |      |       |
| AF181   | £0.58 | BC304  | £0.38 | BF596   | £0.37 | TIP30B   | £0.60 | 2N3055  | £0.40 | 40313   | £0.95 |      |       |      |       |
| AF186   | £0.58 | BC327  | £0.16 | BF939   | £0.25 | TIP30C   | £0.70 | 2N3414  | £0.16 | 40316   | £0.58 |      |       |      |       |
| AF239   | £0.38 | BC328  | £0.15 | BF945   | £0.25 | TIP31B   | £0.54 | 2N3415  | £0.16 | 40317   | £0.38 |      |       |      |       |
| AL102   | £0.95 | BC337  | £0.15 | BF979   | £0.28 | TIP31A   | £0.54 | 2N3416  | £0.29 | 40326   | £0.45 |      |       |      |       |
| AL103   | £0.95 | BC338  | £0.15 | BF980   | £0.28 | TIP31C   | £0.68 | 2N3417  | £0.29 | 40327   | £0.45 |      |       |      |       |
| AU104   | £1.00 | BC440  | £0.30 | BFX29   | £0.25 | TIP32A   | £0.64 | 2N3614  | £0.85 | 40346   | £0.42 |      |       |      |       |
| AU110   | £1.00 | BC441  | £0.30 | BFX30   | £0.30 | TIP32B   | £0.78 | 2N3615  | £0.90 | 40347   | £0.55 |      |       |      |       |
| AU113   | £1.00 | BC460  | £0.38 | BFX84   | £0.23 | TIP32C   | £0.80 | 2N3616  | £0.90 | 40348   | £0.70 |      |       |      |       |
| BC107A  | £0.08 | BC461  | £0.38 | BFX85   | £0.25 | TIP41A   | £0.68 | 2N3646  | £0.08 | 40360   | £0.38 |      |       |      |       |
| BC107B  | £0.08 | BC477  | £0.20 | BFX86   | £0.22 | TIP41B   | £0.70 | 2N3702  | £0.08 | 40361   | £0.38 |      |       |      |       |
| BC107C  | £0.08 | BC478  | £0.19 | BFX87   | £0.22 | TIP41C   | £0.70 | 2N3703  | £0.08 | 40362   | £0.38 |      |       |      |       |
| BC108A  | £0.08 | BC479  | £0.20 | BFX88   | £0.22 | TIP41C   | £0.80 | 2N3704  | £0.07 | 40406   | £0.40 |      |       |      |       |
| BC108B  | £0.08 | BC547  | £0.12 | BFX90   | £0.55 | TIP42A   | £0.72 | 2N3705  | £0.07 | 40407   | £0.28 |      |       |      |       |
| BC108C  | £0.08 | BC548  | £0.12 | BFY50   | £0.14 | TIP42B   | £0.78 | 2N3706  | £0.08 | 40408   | £0.48 |      |       |      |       |
| BC108B  | £0.08 | BC549  | £0.12 | BFY51   | £0.14 | TIP42C   | £0.95 | 2N3707  | £0.08 | 40409   | £0.52 |      |       |      |       |

## 74 SERIES TTL ICs

FULL SPECIFICATION GUARANTEED ALL FAMOUS MANUFACTURERS

| Type | Price | Type | Price | Type | Price | Type | Price | Type  | Price | Type  | Price | Type | Price | Type | Price |
|------|-------|------|-------|------|-------|------|-------|-------|-------|-------|-------|------|-------|------|-------|
| 7400 | £0.16 | 7409 | £0.15 | 7441 | £0.64 | 7492 | £0.42 | 74122 | £0.50 |       |       |      |       |      |       |
| 7401 | £0.14 | 7410 | £0.14 | 7442 | £0.64 | 7493 | £0.95 | 7494  | £0.88 | 74123 | £0.70 |      |       |      |       |
| 7402 | £0.15 | 7411 | £0.23 | 7445 | £0.90 | 7484 | £0.98 | 7495  | £0.75 | 74141 | £0.80 |      |       |      |       |
| 7403 | £0.15 | 7412 | £0.23 | 7446 | £0.90 | 7485 | £1.20 | 7496  | £0.80 | 74154 | £1.30 |      |       |      |       |
| 7404 | £0.15 | 7413 | £0.27 | 7447 | £0.78 | 7486 | £0.30 | 74100 | £1.00 | 74180 | £1.10 |      |       |      |       |
| 7405 | £0.15 | 7414 | £0.58 | 7448 | £0.80 | 7489 | £2.90 | 74110 | £0.50 | 74181 | £2.00 |      |       |      |       |
| 7406 | £0.15 | 7416 | £0.28 | 7449 | £0.78 | 7490 | £0.42 | 74111 | £0.50 | 74182 | £2.00 |      |       |      |       |
| 7407 | £0.30 | 7417 | £0.28 | 7480 | £0.60 | 7491 | £0.75 | 74119 | £1.85 | 74198 | £1.50 |      |       |      |       |
| 7408 | £0.15 | 7440 | £0.15 | 7481 | £0.98 | 7492 | £0.45 | 74121 | £0.30 | 74199 | £1.90 |      |       |      |       |

## CMOS ICs

| Type   | Price | Type | Price | Type | Price |
|--------|-------|--------|-------|--------|-------|--------|-------|--------|-------|--------|-------|------|-------|------|-------|
| CD4000 | £0.14 | CD4012 | £0.18 | CD4022 | £0.95 | CD4031 | £2.20 | CD4046 | £1.30 | CD4071 | £0.28 |      |       |      |       |
| CD4001 | £0.18 | CD4013 | £0.50 | CD4023 | £0.18 | CD4035 | £1.05 | CD4047 | £1.10 | CD4072 | £0.28 |      |       |      |       |
| CD4002 | £0.18 | CD4015 | £0.90 | CD4024 | £0.72 | CD4037 | £0.62 | CD4049 | £0.55 | CD4081 | £1.18 |      |       |      |       |
| CD4006 | £0.98 | CD4016 | £0.50 | CD4025 | £1.18 | CD4040 | £0.95 | CD4050 | £0.55 | CD4082 | £0.28 |      |       |      |       |
| CD4007 | £1.18 | CD4017 | £0.90 | CD4026 | £0.98 | CD4041 | £0.82 | CD4054 | £1.20 | CD4510 | £1.30 |      |       |      |       |
| CD4008 | £0.98 | CD4018 | £1.00 | CD4027 | £0.60 | CD4042 | £0.82 | CD4055 | £1.20 | CD4511 | £1.60 |      |       |      |       |

# BI-PAK

High quality modules for stereo, mono and other audio equipment.



**NEW**

## PUSH-BUTTON STEREO FM TUNER

OUR PRICE ONLY  
**£20.45**

Fitted with Phase Lock-loop Decoder

The 450 Tuner provides instant program selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, by simply changing the settings of the pre-set controls.

Used with your existing audio equipment or with the BI-KITS STEREO 30 or the MK60 Kit etc. Alternatively the PS12 can be used if no suitable supply is available, together with the Transformer T538.

The S450 is supplied fully built, tested and aligned. The unit is easily installed using the simple instructions supplied.

- ★ FET Input Stage
- ★ VARI-CAP diode tuning
- ★ Switched AFC
- ★ Multi turn pre-sets
- ★ LED Stereo Indicator

**Typical Specification:**  
Sensitivity 3µ volts  
Stereo separation 30db  
Supply required 20-30v at 30 Ma max.

## MPA 30



Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the new M.P.A. 30, a high quality pre-amplifier-enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only. It is provided with a standard DIN input socket for ease of connection. Full instructions supplied.

**£2.85**

**VAT  
ADD  
12½%**

**POSTAGE & PACKING**

Postage & Packing add 25p unless otherwise shown. Add extra for airmail. Min. £1.00

## STEREO PRE-AMPLIFIER



**PA 100**  
OUR PRICE  
**£13.75**

A top quality stereo pre-amplifier and tone control unit. The six push-button selector switch provides a choice of inputs together with two really effective filters for high and low frequencies, plus tape output.

**MK. 60 AUDIO KIT:** Comprising 2 x AL60's, 1 x SPM80, 1 x BTM80, 1 x PA100, 1 front panel and knobs, 1 Kit of parts to include on/off switch, neon indicator, stereo headphone sockets plus instruction booklet. **COMPLETE PRICE £29.55** plus 85p postage.

**TEAK 60 AUDIO KIT:** Comprising: Teak veneered cabinet size 16¾" x 11½" x 3¾", other parts include aluminium chassis, heatsink and front panel bracket plus back panel and appropriate sockets etc. **KIT PRICE £10.70** plus 85p postage.

Frequency Response + 1dB 20Hz - 20KHz. Sensitivity of inputs  
1. Tape Input 100mV into 100K ohms  
2. Radio Tuner 100mV into 100K ohms  
3. Magnetic P.U. 3mV into 50K ohms  
P.U. Input equalises to R1AA curve with 1dB from 20Hz to 20KHz.  
Supply - 20-35V at 20mA.

Dimensions -  
299mm x 89mm x 35mm.

## AL-30

**AUDIO AMPLIFIER  
MODULE**

The versatility of the design makes it ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the home.

**SPECIFICATION:**

- Harmonic Distortion Po=3 watts f=1KHz 02.5%
- Load Impedance 8-16ohm
- Frequency response ±3dB Po=2 watts 50Hz-25KHz
- Sensitivity for Rated O/P - Vs=25v. RL=8ohm f=1KHz 75mV.RMS

**AL30 10w R.M.S. £3.45**

## STEREO 30 COMPLETE AUDIO

7+7 WATTS  
R.M.S.



P & P 45p.

**£16.25**

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This, with only the addition of a transformer or overwind will produce a high quality audio unit suitable for use with a wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo tape deck etc. Simple to install, capable of producing really first class results, this unit is supplied with full instructions, black front panel knobs, main switch, fuse and fuse holder and universal mounting brackets enabling it to be installed in a record plinth, cabinets of your own construction or the cabinet available. Ideal for the beginner or the advanced constructor who requires Hi-Fi performance with a minimum of installation difficulty (can be installed in 30 mins).

**TRANSFORMER £2.45** plus 62p p & p  
**TEAK CASE £5.25** plus 62p p & p.

**NEW PA12**

**NEW PA12 Stereo Pre-Amplifier** completely redesigned for use with AL 30 Amplifier Modules. Features include on/off volume, Balance, Bass and Treble controls. Complete with tape output.

Frequency Response 20Hz-20KHz (-3dB). Bass and Treble range -12dB. Input Impedance 1 meg ohm. Input Sensitivity 300mV. Supply requirements 24V .5mA. Size 152mm x 84mm x 33mm.

**£6.70**

## PS12

Power supply for AL20/30, PA12, SA450 etc.

**OUR PRICE  
£1.30**

**£4.35**

# BI-PAK

P.O. BOX 6,  
WARE,  
HERTS.

SHOP AT 18 BALDOCK ST., WARE, HERTS  
OPEN 9 to 5.30 Mon./Sat.



## AL 60 25 Watts (RMS)

★ Max Heat Sink temp 90C. ★ Frequency response 20Hz to 100KHz ★ Distortion better than 0.1 at 1KHz ★ Supply voltage 15-50v ★ Thermal Feedback ★ Latest Design Improvements ★ Load - 3,4,8, or 16 ohms ★ Signal to noise ratio 80db ★ Overall size 63mm. 105mm. 13mm.

Especially designed to a strict specification. Only the finest components have been used and the latest solid-state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

## Stabilised Power Supply Type SPM80

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watts (R.M.S.) per channel simultaneously. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5A at 35V. Size: 63mm. 105mm. 30mm. Incorporating short circuit protection.

Transformer BMT80  
**£2.60 + 62p postage**

**£3.75**



# TRAMPUS ELECTRONICS LTD

58-60 GROVE RD.  
WINDSOR, BERKS.  
SL4 1HS.  
TEL. 54525

ADD 8% VAT TO PRICES MARKED \*  
ADD 12% TO ALL OTHER PRICES.  
OR AS CURRENT VAT LEGISLATION  
SEND C.W.O. (EXCEPT GOV'T DEPT)  
POST & PACKING 20P FOR THE U.K.  
BARCLAYCARD & ACCESS BY POST  
OR £5 MIN ON TELEPHONE ORDERS.  
NEW CATALOGUE LIST FREE S.A.E.  
MONEY BACK IF NOT SATISFIED.

## FAST SERVICE



NORMALLY 24 HOURS  
ON EX STOCK ITEMS



SEVEN SEGMENT LED DISPLAYS  
BRIGHT DL707 COM ANODE &  
DL704 COM CATH., 0.3" £1\*  
DL747 0.6" JUMBO CA £1.25\*

DIGITAL CLOCK IC 51224 £4\*  
ZENON STROBE TUBES £4 & £7\*

## RED LEDS 10P.

RED LEDS 209-STYLE 0.125"  
OR 0.2" DIA. NO CLIP 10p\*

TIL209 RED LED & CLIP 12p\*  
BIG 0.2" RED LED & " 14p\*  
GREEN OR ORANGE LEDS 29p\*  
ORP12 54p\* 2N5777/OCP71 34p\*

TRAMPUS  
THE GREAT  
BRITISH  
DISTRIBUTOR



INDUSTRIAL, EDUCATIONAL, TRADE  
& EXPORT SUPPLIED. SEND FOR  
OUR FREE CATALOGUE LIST SAE  
MANUFACTURERS EXCESS STOCKS  
PURCHASED. DISCOUNTS 10% OFF  
100 sp. 15% OFF 1000 up....

## TOP DISCOUNTS.

### INTEGRATED CIRCUITS

|                    |        |                    |       |
|--------------------|--------|--------------------|-------|
| 555 TIMER          | 34p*   | LM380(60745)       | £1    |
| 556 2 x 555        | 90p*   | LM381 Preamp       | £2    |
| 703 RF/IF AMP      | 29p    | LM3900 4xOPA       | 53p*  |
| 709 T099 or DIL26p | 35p*   | MC1303 2xPre       | £2    |
| 710 DIL14          | 35p*   | MC1310 stereo      | £2    |
| 723 Regulator      | 44p*   | MC1312P SQ         | £1.70 |
| 741 DIL 8pin       | 21p*   | MC1330             | 75p   |
| 741 DIL 14pin      | 31p*   | MC1339 Preamp      | £2    |
| 741 T099           | 33p*   | MFC4000B 1W        | 72p   |
| 747 DUAL 741       | 69p*   | MFC6030            | £1    |
| 748 DIL 8 pin      | 32p*   | NE536 FETOPA       | £2*   |
| 7805 5V1+reg       | £1.35* | NE540 or 550       | £2*   |
| 7812 & 7815ea      | £1.40* | NE555 TIMER        | 34p*  |
| 76013 6W AF        | £1.50  | NE556 2x555        | 90p*  |
| AY51224 CLOCK      | £4*    | NE560/1/2/5/6/7/£3 |       |
| CA3046             | 54p*   | SN72741 as 741     |       |
| ICL8038 Sigen      | £4*    | SN76660 IF         | 74p   |
| LM300H             | £1*    | SN76611 IF         | £1    |
| LM301A D11 8       | 33p*   | TBA800 5W AF       | 84p   |
| LM309K 5V reg      | £2*    | TBA810 7W AF       | 94p   |
| LM309H T05 can     | £1*    | ZN414 Radio        | £1.19 |
| LM318 70VusOPA     | £3*    | NEW 1466/69        | £4    |

## CMOS TTL

|      |        |         |      |         |        |
|------|--------|---------|------|---------|--------|
| 4000 | 14p*   | 7400    | 12p* | 7490    | 39p*   |
| 4001 | 15p*   | 7401    | 13p* | 7491    | 75p*   |
| 4002 | 16p*   | 7402    | 15p* | 7492/93 | 45p*   |
| 4007 | 16p*   | 7404    | 19p* | 7495/96 | 72p*   |
| 4009 | 50p*   | 7408/10 | 18p* | 74100   | £1.25* |
| 4011 | 16p*   | 7413    | 29p* | 74107   | 32p*   |
| 4012 | 17p*   | 7440    | 16p* | 74121   | 29p*   |
| 4049 | 50p*   | 7441    | 71p* | 74123   | 69p*   |
| 4069 | 20p*   | 7442    | 72p* | 74141   | 74p*   |
| 4501 | 26p*   | 7447    | 79p* | 74145   | 85p*   |
| 4511 | £1.65* | 7470/72 | 27p* | 74147   | £2.50* |
| 4528 | £1*    | 7473/74 | 31p* | 74151   | 75p*   |
| 4543 | £2*    | 7475/36 | 35p* | 74154   | £1.40* |
| 4553 | £5*    | 7486    | 35p* | 74196   | £1.50* |

DIL SOCKETS PROFESSIONAL QUALITY  
8pin, 14pin & 16pin ALL 12p ea \*  
SOLDERCONS 100 49p\* 1000 £3.95\*

## NEW LOW PRICES.

### TRANSISTORS AND DIODES

|                     |                 |        |
|---------------------|-----------------|--------|
| INS BUSH SET 5p ea* | TIP31/32        | 50p**  |
| MATCHING 20p Pr*    | TIP31c32c68p*   |        |
| AC127/8 176 15p*    | TIP41/42ea      | 66p*   |
| AD161/162 ea36p*    | TIP41c42c       | £1.50* |
| BC107               | TIP2955         | 69p*   |
| BC107B              | TIP3055         | 65p*   |
| BC108               | TIS43 UJT       | 26p    |
| BC108B or C 13p*    | IN914/4148      | 4p     |
| BC109               | IN4001/2        | 4p*    |
| BC109B or C 12p*    | IN4004          | 5p*    |
| BC147/8/9           | IN4007          | 7p*    |
| BC157/8/9           | 2N706/8         | 14p*   |
| BC167/8/9           | 2N2646 UJT      | 40p*   |
| BC177/8/9           | 2N2904/5pnp     | 29p*   |
| BC182/3/4a/110p     | 2N2926 ory      | 7p*    |
| BC212/3/4a/112p     | 2N3053          | 17p*   |
| BCY70/1/2           | 2N3055 90W      | 33p*   |
| BD131/132ea         | 2N3055 115w     | 45p*   |
| BFY50/51            | 2N3614 T03      | £1*    |
| BFY52/53            | 2N3702/3/4      | 10p    |
| BSX 19/20/21/19p*   | 2N3705/6/7      | 9p     |
| BZY88 ZENER         | 2N3708/9        | 9p     |
| C106D SCR           | 2N3710/11       | 15p    |
| MJ2955 T03          | 2N3819 & 23e17p |        |
| MJE2955             | 2N3820 PPET     | 40p    |
| MJE3055             | 2N3904/5/6      | 15p    |
| OAS1/91             | 2N5457 FET      | 32p    |
| TIP29 & 30          | BRIDGE1A50      | 20p*   |

### BARGAIN PAKS FULL SPEC 11ea,

PAK A: 11 RED LEDES full spec £1\*  
PAK B: 5 741C 8 PIN OP AMP £1\*  
PAK C: 4 2N3055 £1\* D 12 BC109 £1\*  
PAK E: 11 BC182 £1 F 11 2N3704 £1  
PAK G: 7 BFY51 £1\* H 8 2N3819 £1  
PAK J: 6 2N3053 £1\* K 40x1N914 £1  
PAK M: 3 T099 3055 £1\* N 25 OA91 £1  
PAK P: 20 PLASTIC BC109 TYPEnp£1

10-365PF TUNER. SINGLE GANG FOR  
MED/SHORT WAVE, XTAL SET etc £1\*  
SET3/IF CANS 455/470KHZ TOKO £1\*

## Full spec devices

# DALO pen 75p

PCB ETCH KIT 3 ITEMS £2\*  
ETCH RESIST PEN 2TIPS 75p\*  
FEC ETCH PAK TUB 600gm £1\*  
6x4" SRBP 45p\* NYLON F/G£1\*

SCR AND TRIACS BR100 25p\*  
TAG 1A400V 50p\* 1A600V 69p\*  
1A50V 37p\* C106D 4A400 60p\*  
TRIACS: SC146D 10A400V £1\*  
DISCO TRIAC 15A400V £2\*  
AUDIBLE WARNING BLEEPER  
12V35mA £1.20/10 off £1\*  
CAPACITORS 22pf - .01 5p  
ELECTROLYTIC IN 10 & 25V  
1/2/10/50/100 7p 50V 10p  
200/500 10p. 1000/25 20p

## vero

VERO 0.1" PITCH COPPERCLAD  
2 1/2"x5" 40p\* 3 1/2"x5" 45p\*  
2 1/2"x3 1/2" 36p\* 3 1/2"x3 1/2" 40p\*  
3 1/2"x17" £2 FACE CUTTER 65p\*  
DIL BREADBOARD 2"x4" £1 or  
6"x4" £2. VERO PINS 36 30p\*  
BLACK PLASTIC CASES 42mmx.  
80x60 50p\* 100x75 60p\* 99x  
120 70p. DESOLDER BRAID 50p

# QUARTZ CRYSTALS - FAST!



AEL CRYSTALS LIMITED  
Gatwick House, Horley, Surrey, England RH6 9SU  
Telephone: Horley (02934) 5353 Telex: 87118 (Aerocon Horley)  
Cables: Aerocon Telex Horley

WW-022 FOR FURTHER DETAILS

## INSTANT SINAD MEASUREMENTS

with the  
**sinadder**



The SINADDER is a specialized distortion meter for Sinad Measurements. Just connect it to the audio output and read SINAD directly. No adjustments to make. Automatic circuitry does the level setting for you.

£120 + p. & p. & VAT




## LYONS INSTRUMENTS

Hoddesdon Herts EN11 9DX Tel: 67161 Telex 22724

A Claude Lyons Company

WW-029 FOR FURTHER DETAILS

# PUT IT ON RECORD WITH WATANABE

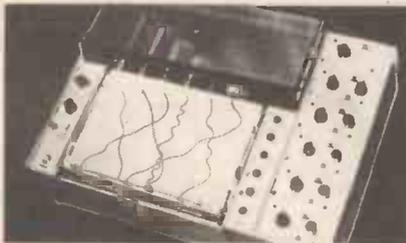


## MULTICORDER - SERVOCODER

- POTENTIOMETRIC
- 1-6 PENS ● 250mm CHARTWIDTH
- MULTI RANGE ● MULTISPEED



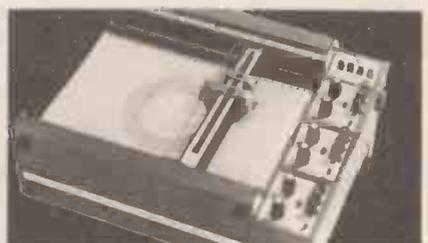
## LINEARCORDER - MINIWRITER

- FAST RESPONSE DC - 100 Hz
- 1-16 PENS ● 4 & 8 cm PER CHANNEL
- MULTI RANGE ● MULTISPEED


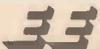
## X - Y RECORDERS

- HORIZONTAL & VERTICAL USE
- 1 & 2 PEN ● TIME BASE
- ROLL CHART OPTION



ENVIRONMENTAL EQUIPMENTS LTD. Eastheath Avenue, Wokingham, Berks, RG11 2PP. Tel: Wokingham 784922

WW-103 FOR FURTHER DETAILS

# SERVICE TRADING CO

## RELAYS

Wide range of AC and DC relays available from stock. Phone or write in your enquiries.

### WHY PAY MORE?!

**MULTI RANGE METER.** A.C. volts 2.5-500 D.C. volts 2.5-500 (Sensitivity 2000V/V D.C. & A.C.) D.C. current 0.1/110/100 mA. Ohms range. Sturdy compact moving coil instrument with 21 ranges, dimensions 120 x 80 x 44mm. Weight 0.32 kg. **SERVICE TRADING CO.** Price £5.50. Incl. leads and battery. Post 50p (Total price inc. VAT & Post £6.48.)



**TRIAC.** Raytheon tag symmetrical Triac. Type Tag 250/500v. 10 amp 500 piv. Glass passivated plastic triac. Swiss precision product for long term reliability £1.25. P&P 10p (inclusive of date and application sheet). Suitable Diac 20p.

**0 to 60 MINUTES CLOCKWORK TIMER.** Double pole 15 amp 230AC. Contacts (no dial). £1.50. P&P 30p.

**GALVANOMETER.** 50 micro mirror galvo. Calibrated 50-0-50 and 0-100. Mfg. by Griffin & George Ltd. Offered at fraction of maker's price. in original ministry packing £12.00. p&p 60p.



**CONTACTOR** Mfg. by Henryrey Relays. Type C2839 220/250 AC ops. Contact 4C/0 at 20 amp at 440 volts AC price £6.00. P&P 75p.

**CITENCO** FHP motor type C7333/15 220/240 volts AC. 19 rpm reversible motor, torque 14.5kg, gear ratio 144-1. Brand new incl. compassors, our price £14.25. P&P £1.25.

**230 VOLT FAN ASSEMBLY** Continuously rated removable aluminium blades. Price £1.25. Post 50p. VAT 12 1/2 %.



### 21-WAY SELECTOR SWITCH

The ingenious electro mechanical device can be switched up to 21 positions and can be reset from any position by energising the reset coil. 230/240V. A.C. operation. Unit is mounted on strong chassis. Complete with cover. Price £5.50. P&P 75p.



### PRECISION CENTRIFUGAL BLOWERS

(230/240V AC) Mfg. by Smiths Industries. Miniature model Series SF/200. Size 95mm x 82mm Aperture 38mm x 31mm. 12 c.f.m. £2.75. Post 50p. Other types available, phone for details.



### BLOWER UNIT

200/240V a.c. precision. German built. Dynamically balanced, quiet, con rated, reversible. Consumption 60mA. Size 120mm dia. x 60mm dep. Price £3.50. Post 50p.



### NI-CAD BATTERIES

40 AH 1.2v Plastic Coated £8.00, 35 AH Metal £6.50, 23 AH Plastic £4.00, 16 AH Metal £3.00. P&P 75p. Limited stock, buy now!

### UNISELECTOR SWITCH

4 bank, 25 way 75 ohm coil, 36-48v D.C. operation. Ex. new equipment. £4.25. P&P 75p. Total price inc. VAT. £5.40.



### MINIATURE UNISELECTOR

12v. 11 way 4 bank (3 non-bridging, 1 homing). £2.50. P&P 35p.


### MICRO SWITCHES

Omron roller micro switch Type V15 FL 22-1C. 10 for £2.00 post 50p (min. order 10). Sub-miniature Burgess type V 4T 1. 10 for £2.50, 50 for £10.00, post paid. Sub-miniature Honeywell roller M/S Type 3 115M 906T 10 for £2.50, post paid. **LEVER OPERATED** 20 amp c/o. Mfg. by Unimax USA 10 for £4.00 plus 50p P&P (min. order 10).


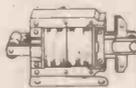
### NEW HEAVY DUTY SOLENOID

Mfg. by Magnetic Devices. 240v A.C. operation approx. 20lb. pull at 1.25". Price £7.00. P&P 75p. Similar to above approx. 10lb pull £3.50. P&P 60p.



### 230-250 VOLT A.C. SOLENOID

Similar in appearance to illustration. Approximately 1 1/2 lb. pull. Size of feet 1 1/4" x 1 3/16". Price £1.00. Post 25p.



### 24 VOLT D.C. SOLENOIDS

UNIT containing 1 heavy duty solenoid approx. 25 lb. pull at 1 in. travel. 2 solenoids of approx 1 lb. pull at 1/2 in. travel. 6 solenoids of approx. 4 oz. pull at 1/2 in. travel. Plus 1 24V D.C. **ABSOLUTE BARGAIN.**

### 240 A.C. SOLENOID OPERATED FLUID VALVE

Rated 1 p.s.i. will handle up to 7 p.s.i. Forged brass body, stainless steel core and spring 1/2 in. b.s.p. inlet outlet. Precision made. British mfg. PRICE £2.75. Post 50p. new original packing



## VARIABLE VOLTAGE TRANSFORMERS

Carriage extra

INPUT 230 v. A.C. 50/60

OUTPUT VARIABLE 0/260v. A.C.

**BRAND NEW. All types. 200W (1 Amp) fitted A/C volt meter**

|                          |        |
|--------------------------|--------|
| 0.5 KVA (Max. 2 1/2 Amp) | £14.00 |
| 1 KVA (Max. 5 Amp)       | £18.00 |
| 2 KVA (Max. 10 Amp)      | £30.00 |
| 3 KVA (Max. 15 Amp)      | £38.00 |
| 4 KVA (Max. 20 Amp)      | £60.00 |



## LT TRANSFORMERS

|   |                  |
|---|------------------|
| 0-12v/24v at 1 amp.                           | £2.50 p&p 50p    |
| 0-15v at 1 amp. + D-15v at 1 amp (30v J amp.) | £2.50 p&p 50p    |
| 25-0-25v at 2 1/2 amp.                        | £4.50 p&p 75p    |
| 0-12v/24v. 10 amp.                            | £12.35 p&p £1.50 |
| 0-4v/8v/24v/32v at 12 amp.                    | £13.00 p&p £1.50 |
| 0-12v at 20 amp. or 0-24v at 10 amp.          | £12.40 p&p £1.50 |
| 0-6v/12v/17v/18v/20v at 20 amp.               | £14.00 p&p £1.50 |
| 0-6v/12v at 20 amp.                           | £11.85 p&p £1.00 |

Other types in stock, phone in enquiries

## 300 V.A. ISOLATING TRANSFORMER

115/230 screened primary, two separate or 115v for 115 or 230v. Secondary two 115v at 150 V.A. each for 115 or 230v. output. Can be used in series or parallel connections. Fully tropicalised. Length 13.5cm., width 11cm., weight 15lbs. Special price £8.00. carr. £1.00.

## RODENE UNISET TYPE 71 TIMER

0-60 sec. 230v AC operation. Incorporating a lapsed time indicator and repeat facilities. A precision motorised timer ideal for process timing, photography, welding, mixing etc. Price £6.00 p&p 60p.



## STROBE! STROBE! STROBE!

**HY-LIGHT STROBE KIT Mk. IV**  
 Latest type Xenon white light tube. Solid state timing and triggering circuit. 230/240 volt A.C. operation. Speed adjustable 1-20 f.p.s. Designed for large rooms, halls, etc. Light output greater than many (so called 4 Joule) strobes. Price £18.00. Post 75p. Specially designed case and reflector for Hy-Light £8.25. Post £1.00.

**XENON FLASH GUN TUBES**  
 Range of Xenon tubes available from stock. S.A.E. for full details.

\*\*\*\*\*

**ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES**  
 4ft. 40 watt £7.00 (callers only). 2ft. 20 watt £5.00. Post 60p (For use in stan bi-pin fittings). MINI 12in. 8 watt £1.75. Post 25p. 9in. 6 watt £1.40. 6in. 4 watt £1.40. Post 25p. Complete ballast unit. Either 6", 9" or 12" tube 230V. A.C. op. £3.50 plus p&p 40p. Also available for 12V. D.C. op. £3.50 plus p&p 40p.

\*\*\*\*\*

### SQUAD LIGHT

A new conception in light control. Four channels each capable of handling 750 watts of spotlights, floodlights or dozens of small mains lamps. Seven programs all speed controlled plus flash modulation, effectively giving 14 different displays. Makes sound-to-light obsolete. Completely electrically and mechanically noise free. Price only £60.00. Post 75p. S.A.E. (foolscap) for further details.

## RELAYS

Wide range of AC and DC relays available from stock. Phone or write in your enquiries.

### FT3

High intensity multi turn, high voltage, neon glow, discharge flash tube. Design for ignition timing etc. £1.50 p&p 25p. 3 for £3.00 p&p 50p.

### RESET COUNTER

230 volts AC 3 digits mfg. Veeder Root type LL/1441 £1.75 p&p 25p.

### BIG INCH

Tiny precision built 3 rpm USA motor size only 1 X 1 100 volt AC op. supplied with resistor for 230 volt AC price £2.00 p&p 20p. 4 for £5.00 post paid.

### INSULATION TESTERS (NEW)

Test to I.E.E. spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L. 8 in., W. 4 in H. 6 in., weight 6 lb. **500 VOLTS** 500 megohms £40.00 Post 80p **1000 VOLTS** 1000 megohms £46.00 Post 80p SAE for leaflet



## VAT

AT CURRENT RATE  
MUST BE ADDED  
TO ALL ORDERS  
FOR THE TOTAL VALUE OF GOODS INCLUDING  
POSTAGE UNLESS OTHERWISE STATED

ACCOUNT CUSTOMERS MIN. ORDER £10.00

## GEARED MOTORS

100 R.P.M. 115 lbs. ins.!!

115 lb. ins., 110 volt, 50Hz, 2.8 amp, single phase, split capacitor motor. Immense power. Continuously rated. Totally enclosed. Fan cooled in-line gearbox. Length 250mm. Dia 135mm. Spindle Dia 15.5mm. Length 145mm. ex-equipment tested £12.00. Post £1.50. Suitable transformer 230/240 volt £8.00. Post 75p.



15 R.P.M.

Type SD48 15 r.p.m. 80 lb. ins. Input 100/120 volt A.C. Length incl. gearbox 270mm. Height 135mm. Width 150mm. Shaft drive 16mm. Weight 8.5 kilos. BRAND NEW. Price £10.00, carr. £1.00. Suitable transformer for use on 220/240 volt A.C. £6.00. Post 50p.

### DRAYTON MOTOR

Type RGR 230/250v 50c. Continuously rated 1 RPM. 90lb. in. Reversible motor. Twin spindle size 100mm by 140mm by 125mm. Shaft 50mm by 8mm. Weight 2 kilos. New Price £16.50. P&P £1.00.



### BODINE TYPE N.C.I. GEARED MOTOR

(Type 1) 71 r.p.m. torque 10 lb. in. Reversible 1/70th h.p. cycle 38 amp. This U.S.A. motor is offered in as new condition. Input voltage of motor 115v A.C. Supplied complete with transformer for 230/240v A.C. Input. Price type £6.25. Post 75p or less transformer £3.75. Post 65p. (Type 3) 71 r.p.m. 230 Volt A.C. Continuously rated. Non reversible. £6.50 Post 75p.



6/9 VOLT D.C. GOVERNED 40mm x 40mm. Spindle 10mm. Dia. 2 mm. £1.00 Post Paid. Two for £1.65 Post Paid.

24 R.P.M. 230 volt A.C. Continuously rated. Mfg. Mycalex Ex-equip. Fully tested £3.85 Post 75p.

1 R.P.M. 230/240 VOLT A.C. SYNCHRONOUS Ex-equipment. Thoroughly tested and guaranteed. ONLY £1.50. Post 20p.

20 R.P.M. GEARED MOTOR. 230/240 volt 20 r.p.m. motor £1.00. Post 20p.

### HALF REV. PER HOUR.

Sync. Motor. 230/240v. A.C. Mfg. by Smiths £1. P&P 20p.

### REVERSIBLE MOTOR 230V A.C.

General Electric 230V A.C., 1.600 r.p.m. 0.25 amp. Complete with anti-vibration mounting bracket and capacitor. O/A size 110mm x 95mm. Spindle 5/16" dia. 20mm long. Ex-equipment tested. £3.00. Post 50p.

### REVERSIBLE MOTOR

AEI 1/12 hp continuous rated, reversible motor. 100/120v. A.C. 50/60 cycle. 2850 r.p.m. Flange fixing dia 4". length 4 1/2". shaft 1" x 5/16". Price £3.25. P&P 75p.


### METERS NEW 90mm Diameter

Type: 65CS D.C. mc. 2.5, 10, 20, 50 amp £3.00, 100 amp £3.25. Type: 62T2 A.C. M/1, 1, 10, 50 amp £3.00, 0-150 Volt. A.C. M/1 £3.25 and 300 Volt A.C. R/M/C. £3.00 P&P 30p.


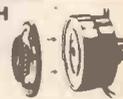
### BENDIX MAGNETIC CLUTCH

Superb example of electro-mechanics. Main body in two sections. Coil section is fixed and has 3/8" sleeve. The drive section rotating on the outer periphery. When engaged the transmitter shaft is extremely powerful. Diameter 1 1/4". Total width 1 1/4". 24V D.C. op. Price £3.50 plus p&p 45p.



### TIME SWITCH

Horstmann Type V Mk II Time Switch 200/250 vclt A.C. Two on/two off every 24 hours, at any manually pre-set time 30 amp contacts 36-hour spring reserve in case of power failure. Day omitting device. Fitted in heavy high impact case, with glass observation window. Built to highest Electricity Board spec. individually tested. Price £7.75. Post 50p. (Total inc. VAT £8.91).



### A.C. MAINS TIMER UNIT

Based on an electric clock, with 25 amp, single-pole switch, which can be preset for any period up to 12 hrs, ahead to switch on for any length of time, from 10 mins to 6 hrs then switch off. An additional 60 min. audible timer is also incorporated. Ideal for Tape Recorders, Lights, Electric Blankets, etc. Attractive satin-copper finish. Size 135 mm x 130 mm x 60 mm. Price £2.25. Post 40p. (Total inc. VAT & Post £2.87).



## POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.

|   |                  |
|---|------------------|
| 25 WATT 10, 25, 100, 150, 250, 500 1k 1.5k ohm                          | £1.90, Post 20p. |
| 50 WATT 25, 100, 500, 1k ohm  | £2.40, Post 25p. |
| WATT 1 / 5 / 10 / 25 / 50 / 100 / 250 / 500 / 1k / 1.5k / 2.5k / 5k ohm | £3.70, Post 35p. |

Black Silver Skirted knob calibrated in Nos. 1-9, 1 1/2 in. dia brass bush. Ideal for above Rheostats. 22p ea.

### PROGRAMME TIMERS

230 Volt AC Operation. 15 or 20 r.p.m. Each cam operates a c/o micro switch. Ideal for lighting effects, displays, etc. Ex equip tested. Similar to illustration.

|              |       |
|--------------|-------|
| 6 CAM model  | £5.00 |
| 9 CAM model  | £6.50 |
| 12 CAM model | £7.50 |

Post 60p. Also available for 50 volt A.C. operation. Prices as above.



# Z & I AERO SERVICES LTD.

Head Office: 44A WESTBOURNE GROVE, LONDON W2 5SF  
Tel.: 727 5641 Telex: 261306

Retail Branch:  
85 Tottenham Court Road  
London W1. Tel: 580 8403

## MULTIMETER F4313 (Made in USSR)



**SENSITIVITY:**  
1200V DC range: 10,000 Ω/V  
Other DC ranges: 20,000 Ω/V  
1200 AC range: 6,000 Ω/V  
600V AC range: 15,000 Ω/V  
300V AC range: 15,000 Ω/V  
Other AC ranges: 20,000 Ω/V

AC/DC current ranges: 60-120-600μA-3-12-300mA-1.2-6A  
AC/DC voltage ranges: 60-300mV-1.2-6-30-120-300-600-1200V  
Resistance ranges: 300Ω-10-100-1000Ω  
Accuracy: 1.5% DC; 2.5% AC (of full scale deflection)

Mirror scale and knife edge pointer. Taut suspension of movement. Transistor amplifier is used for all AC ranges thus achieving a common linear scale for both AC and DC ranges.

Meter is protected by a transistorised cut-out relay circuit. Range selection is achieved by clearly marked piano keys. Power source: 5 1.5V dry cells. Dimensions: 95 x 225 x 120mm.

PRICE £39.50 plus VAT  
Packaging and postage £1.10



## OSCILLOSCOPE CI-5 Made in USSR

Extremely simple and easy to use single beam oscilloscope. Well proved design based on standard octal valves makes servicing and maintenance straightforward and inexpensive. Because of its bandwidth of 10 MHz the instrument is suitable for general electronic applications and educational purposes where a sophisticated instrument would be both too expensive and delicate. 3in. tube giving a 50 x 50mm clear display. Amplitude and time base calibrations. Sensitivity 30mm/v max. Triggered and free-running time base, suitable for displaying pulses from 0.1 μsec. to 3 m sec. A.C. mains operation.

Price £55.00 ex. works, plus VAT  
Packing and carriage (U.K. only) £3.00

## A SELECTION FROM OUR LARGE STOCKS

### TRANSISTORS

|         |      |         |      |         |      |         |      |               |      |
|---------|------|---------|------|---------|------|---------|------|---------------|------|
| 2N696   | 0.15 | *2N3705 | 0.10 | AF239   | 0.36 | BF177   | 0.18 | *1N4004       | 0.05 |
| 2N697   | 0.15 | *2N3706 | 0.10 | ASY26   | 0.25 | BF178   | 0.32 | *1N4005       | 0.05 |
| 2N706   | 0.10 | *2N3707 | 0.10 | ASY27   | 0.30 | BF179   | 0.35 | *1N4006       | 0.06 |
| 2N706A  | 0.10 | *2N3708 | 0.10 | ASY28   | 0.30 | BF180   | 0.31 | *1N4007       | 0.06 |
| 2N753   | 0.23 | *2N3709 | 0.10 | BC107   | 0.10 | BF181   | 0.35 | *1N4148       | 0.04 |
| 2N929   | 0.14 | *2N3710 | 0.10 | BC107A  | 0.12 | BF184   | 0.29 | *1N5408       | 0.20 |
| 2N930   | 0.14 | *2N3711 | 0.10 | BC107B  | 0.12 | BF185   | 0.30 | *BY101        | 0.15 |
| 2N1131  | 0.25 | *2N3819 | 0.35 | BC108   | 0.10 | *BF194  | 0.08 | *BY105        | 0.15 |
| 2N1132  | 0.25 | *2N3904 | 0.20 | BC108A  | 0.12 | *BF195  | 0.08 | *BY126        | 0.10 |
| 2N1302  | 0.17 | *2N3905 | 0.25 | BC108B  | 0.12 | *BF196  | 0.10 | *BY127        | 0.13 |
| 2N1303  | 0.15 | *2N3906 | 0.25 | BC109   | 0.12 | *BF197  | 0.11 | *BY130        | 0.10 |
| 2N1304  | 0.20 | AC125   | 0.20 | BC109A  | 0.12 | BF200   | 0.28 | *BY164        | 0.50 |
| 2N1305  | 0.20 | AC126   | 0.20 | BC109B  | 0.12 | BFX88   | 0.20 | BZX61         | 0.20 |
| 2N1306  | 0.27 | AC127   | 0.17 | *BC147  | 0.12 | *BFY51  | 0.19 | series        | 0.20 |
| 2N1307  | 0.25 | AC132   | 0.25 | *BC149  | 0.08 | BFY52   | 0.20 | series        | 0.10 |
| 2N1308  | 0.25 | AC176   | 0.22 | *BC158  | 0.10 | *BU208  | 2.00 | *OA70         | 0.07 |
| 2N1309  | 0.25 | AC187   | 0.20 | *BC171  | 0.10 | OC36    | 0.65 | *OA79         | 0.07 |
| 2N1613  | 0.17 | AC188   | 0.18 | BC178   | 0.18 | OC41    | 0.25 | *OA81         | 0.07 |
| 2N1711  | 0.18 | AC211   | 0.20 | *BC182  | 0.11 | OC45    | 0.20 | *OA85         | 0.07 |
| 2N2221  | 0.20 | AC222   | 0.14 | *BC182A | 0.10 | OC70    | 0.15 | *OA90         | 0.07 |
| 2N2222A | 0.20 | AD161   | 0.38 | BC186   | 0.25 | OC71    | 0.15 | *OA91         | 0.07 |
| 2N2369A | 0.25 | AD162   | 0.38 | BC187   | 0.25 | OC72    | 0.18 | *OA95         | 0.07 |
| 2N2646  | 0.40 | AD211   | 1.25 | *BC212  | 0.11 | OC75    | 0.15 | *OA200        | 0.07 |
| 2N2906  | 0.25 | AD212   | 1.25 | *BC237  | 0.11 | OC76    | 0.18 | *OA202        | 0.08 |
| 2N2907  | 0.20 | AF106   | 0.25 | *BC238  | 0.11 | OC81    | 0.20 | RAS310AF      | 0.35 |
| 2N2907  | 0.20 | AF114   | 0.17 | BCY32   | 1.20 | OC83    | 0.30 | RAS508AF      | 0.40 |
| *2N2926 | 0.10 | AF115   | 0.17 | BCY70   | 0.15 | OC84    | 0.30 | TTL SERIES    |      |
| 2N3053  | 0.20 | AF116   | 0.17 | BCY71   | 0.20 | OC204   | 0.60 | Russian made  |      |
| 2N3054  | 0.65 | AF117   | 0.17 | BCY72   | 0.15 | OC206   | 0.70 | Special offer |      |
| 2N3055  | 0.55 | AF118   | 0.25 | BD115   | 0.39 | ORP12   | 0.80 | 7400          | 0.09 |
| 2N3391  | 0.17 | AF124   | 0.25 | BD116   | 0.59 | *TIP30A | 0.50 | 7401          | 0.09 |
| 2N3392  | 0.17 | AF125   | 0.25 | BD132   | 0.39 |         |      | 7410          | 0.09 |
| 2N3393  | 0.15 | AF126   | 0.25 | BD133   | 0.45 |         |      | 7420          | 0.11 |
| 2N3414  | 0.20 | AF127   | 0.25 | *BD137  | 0.30 |         |      | 7422          | 0.20 |
| 2N3415  | 0.15 | AF139   | 0.30 | BF115   | 0.28 | *1N914  | 0.05 | 7430          | 0.11 |
| *2N3702 | 0.10 | AF178   | 0.50 | *BF152  | 0.20 | *1N4001 | 0.04 | 7430          | 0.20 |
| *2N3703 | 0.10 | AF180   | 0.50 | BF167   | 0.25 | *1N4002 | 0.05 | 7440          | 0.11 |
| *2N3704 | 0.10 | AF181   | 0.50 | BF173   | 0.25 | *1N4003 | 0.05 | 7450          | 0.11 |

P&P 25p min. (U.K. only). Please add 8% VAT ★ 12.5%

MINIMUM EXPORT ORDER £100

FULLY GUARANTEED



1976/1977  
CATALOGUE  
AVAILABLE 30p

WW — 054 FOR FURTHER DETAILS

# Bargain Time!

TO INTRODUCE THE

# new 7<sup>TH</sup> edition of


THE  
SEMICON

INTERNATIONAL TRANSISTOR INDEX  
AND THE DIODE/SCR INDEX

WE HAVE

**A SPECIAL OFFER**  
FOR NEW AND EXISTING SUBSCRIBERS  
SEND FOR DETAILS • DON'T DELAY

● AVAILABLE FOR  
A LIMITED PERIOD ONLY.

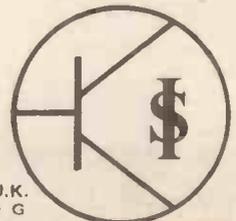

## SEMICON INDEXES LTD.

7, KING'S PARADE, KING'S ROAD, FLEET, HAMPSHIRE. GU13 9AB. U.K.  
TELEPHONE: FLEET (025 14) 28526 TELEX: 858855 Barmer G

WW—102 FOR FURTHER DETAILS

TF 1064 B/P 2.75 TF 1152 A/1 £2.50

£5.75 M.I. LTD  
S. DIV 105  
D. D. D. D. D.

### MARCONI TEST EQUIPMENT

TF329G circuit magnification meter.  
TF455E Wave analyser.  
TF801D RF signal generator.  
TF868 Universal bridge.  
TF995A/2 AM/FM generator.  
TF1041B V.T. Voltmeter.  
TF2200 Oscilloscope.  
TF1100 Sensitive v/voltmeter.  
TF1152A/1 RF power meter.  
TF1245 Q-meter.  
TF1417 200mHz frequency counter.  
TF1342 Low capacitance bridge.  
TF1370 Wide-range RC oscillator.  
TF2163 UHF attenuator DC-1GHz.  
TF2500 Af power meter.  
TF2600 Sensitive v/voltmeter.  
TF2604 Electronic voltmeter.  
TF2606 Differential DC voltmeter.  
TF2660 Digital voltmeter.

### MARCONI TF995B/2. AM/FM GENERATORS.

200kHz-220mHz in 5 bands.  
0.1 µV-200mV. Continuously variable  
FM in two ranges to 75kHz. Price and full spec upon request.

### EVER-READY NICKEL-CADMIUM BATTERIES.

Size 'D' (HPZ) 1.25V. 3.5 AH. Only small quantity available at £2 + 10p. post.

### AVO UNIVERSAL MEASURING BRIDGE.

Measures LC&R. Small portable instrument. As new £125.00.

### BECKMAN TURNS COUNTER DIALS

Miniature type (22mm diam.) Counting up to 15 turn 'Helipot'. Brand new with mounting instructions. Only £2.50 each


FRACMO Geared motors. 24V. AC 0.5RPM. 68A. Torque 40lb. in. Price including starting capacitor £10.50

CENTRIFUGAL TYPE Blowers. 12V DC. Outlet diam. 7 cms. Overall diam. 15 cms and 17 cms deep. Very powerful fans £9.50
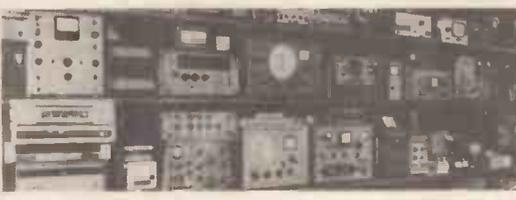
## P. F. RALFE ELECTRONICS

10 CHAPEL STREET, LONDON, NW1  
TEL: 01-723 8753

**NOTICE.** All the pre-owned equipment shown has been carefully tested in our workshop and reconditioned where necessary. It is sold in first class operational condition and most items carry our three months' guarantee. Calibration and certificates can be arranged at cost. Overseas enquiries welcome. Prices quoted are subject to an additional 8% VAT.



- HEWLETT PACKARD 432A. Power meter.  
ADVANCE TCD500 Frequency dividers to 500mHz £100  
AIRMEC 210A Modulation meter 3-300mHz.  
APTS04 Power supply. 0-500V at 250mA £35  
BPL Capacitance decade (5) CD133. 100pf-1uf £45  
BRANDENBURG High voltage generator type S.0530/10 0-20KV and MR50 type 0-50KV.  
FLUKE 891A DC Differential voltmeter.  
GERTSCH Frequency meter and deviation meter 20-1000mHz £250  
GR Standard sweep frequency generator. 400kHz-230mHz £485  
HEWLETT PACKARD. 612. Signal generator. 400-1000mHz.  
HEWLETT PACKARD. 208A. Battery powered oscillator. 5-500 KHz.  
HEWLETT PACKARD 693D sweep oscillator. £350  
MEDISTOR type A-75A Potentiometric microvoltmeter £115  
PYE EHT scalamp voltmeter 0-40KV. £125  
RACAL 1.2mHz counter timer. 6 Digits. SA535B £85  
RADIOMETER Wave analyser type FRA28. 0-16KHz £160  
SCHNEIDER type cf52. 100mHz frequency counter £235  
SCHOMANDL Frequency meter type FD1.  
SOLARTRON Pulse generator type G01101.2 £65  
TEKTRONIX type 575 Transistor curve tracer.  
TEKTRONIX 585A oscilloscope with '82' P.I. DC-80mHz.  
TEKTRONIX type 526. Vectorscope.  
TEKTRONIX type 180A. Time mark generator £110

### ROHDE & SCHWARZ EQUIPMENT

Midget crystal clock type XSZ. BN 15221.  
Selective UHF v/meter, bands 4&5. USVF.  
Selectomat. RF Voltmeter. USWV. BN 15221.  
Standard attenuator 0-100db 0-300mHz. DPR.  
UHF Receiver type ESM300.  
UHF Signal generator type SCR.  
UHF Test receiver type USDV.  
POLYSKOP. SWOB I.  
POLYSKOP. SWOB II.  
SBTF. T.V. Signal generator, vision-sound modulator and transmitter.

|                                    |         |
|------------------------------------|---------|
| ICL type 2640 Paper tape readers.  | 250cps. |
| New                                | £95     |
| Westrex 8-hole paper-tape punches. | £95     |
| Sound-proof case available         | £15     |

### MUFFIN INSTRUMENT COOLING FANS

Made by Rotron Holland. These are very high quality, quiet running fans, specially designed for the cooling of all types of electronic equipment. Measures 4.5x4.5x1.5". 115V.AC. 11 Watts. The list price of these is over £10 each. We have a quantity available brand new for only £4.50 each

### 500V TRANSISTORISED INSULATION TESTER

Lightweight, small size (13x7x4cms). Reads insulation from 0.2-100MΩ at 500V pressure. Runs from standard 9V.PP3. Brand new £16.50

### AVO MULTI-METERS

Type Multi-minor Mk 4. Light, small size instrument (14x9x3 1/2 cms). Measures volts AC/DC to 1KV. DC. 1 from 0.1mA-1A. Resistance ranges 10KΩ/V.DC. 1KΩ/V.AC. Tested, and in excellent condition £8.50

### MUIRHEAD DECADE OSCILLATORS type 890A.

1Hz-110kHz in four decade ranges. Scope monitored output for high accuracy of frequency. Excellent generator. £135.

# DETECKNOWLEDGEY

**DETECKNOWLEDGEY ?**

Not a spelling mistake, but a new publication from AMBIT that sets out to explain some of the basic theory that surrounds metal location techniques. It is an explanation, that builds up from first principles, why iron sometimes reacts like a non-ferrous metal, what determines detector range, what the shortcomings are, how to avoid them. In fact, it explains about BFO, IB, VCO and Pulse Induction techniques, as a result of research carried out to produce our range of locators, and why we chose the methods we used. As a general purpose reference work for designers, constructors, users etc., we think you will find it unique. £1.00 inc. postage.

### Bionic Ferret Metal Locators

As a result of our investigations, we offer you three metal locators now: The VCO 4000, the IB phase angle meter, and the 'Pulsedec' pulse induction metal locator. It is impossible to catalogue the relative virtues of each type here, so please send an SAE for details.

Components for Wireless: ICs, Coils, Ceramic & Mechanical Filters, trimmers etc

| Linear ICs           | Tuner modules/TOKO parts | Discrete devices                         |
|----------------------|--------------------------|--|
| CA3089E/KB4402 1.94  | ICL8038CC* 4.50          | EF5800 6 cct varicap head 14.00          |
| MC1310/KB4400 2.20   | NE555V* 0.70             | EF5600 5 cct varicap head 12.95          |
| TBA120/SN76660 0.75  | NE565/6/7* 2.50          | EC3302 3 cct varicap head 7.50           |
| uA753 1.80           | NE560B* 3.50             | 7030 linear phase FM if system 10.95     |
| HA1137W 2.20         |                          | 91196 high spec mpx decoder 12.99        |
| CA3090AQ 3.75        |                          | other types in catalogue                 |
| HA1196 4.20          | 40673/MEM616* 0.57       | 91197 varicap MW/LW tuner 11.35          |
| uA720/CA3123E 1.40   | MEM680* 0.75             | 7701 Mk2 double conversion TV            |
| HA1197 1.40          | MEM614* 0.38             | UHF off air sound tuner board 27.00      |
| TBA651 1.81          | BF256L/S 0.34            | Larsholt Signalmaster Mk 8 complete      |
| LM380N 1.00          | MVAM115 varicap 0.95     | FM tuner for all levels of experience    |
| LM381N 1.81          | MVAM125 0.90             | in electronics (kit) 85.00               |
| LM3900* 0.75         | MVAM2 1.35               | Larsholt Audiomaster 25+25W superb       |
| TDA2020 2.99         | BB104 0.45               | audio amplifier kit 79.00                |
| TC9A90 1.80          | BB105 0.32               | Ambit Int. Mk 2 series: all the pieces,  |
| TBA810AS 1.09        | BA102/BA121 0.30         | case/chassis/hardware/panel/PSU/presets  |
| MC1312 1.50          | ZTX/BC107/8/9 0.14       | etc. for you to present your FM tuner    |
| 7805UC* 1.55         | ZTX/BC212/4 0.17         | in a stylish unit. 33.00                 |
| 78M12* /TDA1412 1.20 | BC413 0.18               | NEW NEW NEW NEW NEW NEW NEW              |
| 78M20* 1.20          | ZX451/551 0.18           | Stiron soldering irons, made in UK to    |
| 78M24* 1.20          | BD609 0.70               | meet all known safety specs, thermally   |
| uA723CN* 0.80        | BD610 1.20               | regulated with stand, also pro tools for |
| TAA550B* 0.50        | more in price list.....  | PCB construction: SAE for leaflet pse    |

PLEASE NOTE: Vat is extra, at 12.5% except where marked \* (8%). PP 22p per order. An A5 size SAE for free current price lists, or 40p for the complete catalogue. Write to: 37a High Street, Brentwood, Essex, CM14 4RH. (tel. 0277-216029)

# ambit international

WW-100 FOR FURTHER DETAILS

0582 33866

## Crimson Elektrik

### AUDIBLY SUPERIOR POWER AMPLIFIER MODULES

A power amp. built with CE modules will be audibly comparable to the very best amps. commercially available, but at a much reduced cost. T.h.d. is typically -01% by the use of output triples & moderate feedback, while t.i.d. is no worry with a slew-rate limit of 16v/µs (only 9v/µs is required for the power bandwidth of CE 1008). Settling time < 15µs. ★S/N>110dB ★120x80x25mm ★Fully protected ★250mv/56kΩ ★12Hz-35kHz, -3dB ★14Trs, 4Di

**Power Supplies: Featuring high quality Toroidal transformers with 120-**

|                                      |        |                        |
|--------------------------------------|--------|------------------------|
| CPS 1 For 2xCE 608 or 1xCE 1004      | £12.55 | 240v primary & screen; |
| CPS 2 For 2xCE 1004 or 2 or 4xCE 608 | £14.55 | 2 large capacitors;    |
| CPS 3 For 2xCE 1008                  | £15.85 | rectifier; fixings.    |

**Power amp. modules:**  
CE608 60Wrms/4n, ±35v, £14.55  
CE1004 100Wrms/4n, ±35v, £17.55  
CE1008 100Wrms/8n, ±45v, £21.55

H/sinks: 50mm 85p; H/duty 100mm, £1.50

All prices inclusive CRIMSON ELEKTRIK  
S.A.E. for full details 74 STATION ROAD,  
tel: 019-530533-388211 RATBY; LEICESTER. CE 1008 + Domestic heat sink. (50mm.)

WW-078 FOR FURTHER DETAILS

## Audio Connectors

Broadcast pattern jackfields, jatkords, plugs and jacks.

Quick disconnect microphone connectors  
Amphenol (Tuchel) miniature connectors with coupling nut.

Hirschmann Banana plugs and test probes  
XLR compatible in-line attenuators and reversers.

Low cost slider faders by Ruf.

### Future Film Developments Ltd.

90 Wardour Street  
London W1V 3LE  
01-437 1892/3

WW-031 FOR FURTHER DETAILS

## THE ELECTRICAL REMOTELY CONTROLLED AERIAL AMPLIFIER RB 45

To acquire long-distance TV reception, an aerial amplifier is needed which combines high gain and low noise performance. These properties you will find in a narrow band or channel amplifier. To obtain more amplified channels (programmes) SCHRADER ELECTRONICA has developed an electronic remotely tunable amplifier, which can be tuned at any desired channel from 21 up to 65, in other words the whole UHF Band (IV/V). The ideal position is to mount the RB 45 as near as possible to a UHF wide band aerial, in order to obtain a good signal to noise ratio. The RB 45 should be applied in combination with the power supply and control unit VR 12/01.

### TECHNICAL DATA:

|  |               |
|--|---------------|
| Channel range                                | 21-65         |
| Gain   | 22-30 dB      |
| Noise ratio                                  | 3.5dB         |
| Impedance input                              | 60/240 75/300 |
| output                                       | 60/75         |
| Transistors                                  | 2 x S1        |
| Varicapacitors                               | 5             |
| Max output voltage at d <sub>sm</sub> -30 dB | 300 mV        |
| Power consumption                            | 8 mA/18 V.    |

Complete unit price £50 (RB 45 + VR 12/01)  
Long Distance Aerial £32.50. Channel 21-69 gain 13-18 dB

Prices mentioned are FOB Amsterdam. By sending an international Money Order we will send you these articles immediately.

**SCHRADER**  
ELECTRONICA BV  
Lippijnstraat 4 B AMSTERDAM HOLLAND  
Tel. 020-861543 Telex: TELAM + 18118

### buy, lease or rent:

- Teletype 33 and DD 390 (10cps) printer terminals
- DECWRITER LA36 and DD303 (30cps) printer terminals
- OKIDATA 110(66 lpm) and Teletype 40 (300 lpm) high-speed printers
- Lear Siegler ADM 1, 2 and 3A video keyboard display
- Teletype 40 (7200 baud) asynchronous and synchronous displays
- DD Paper tape punch range (up to 110 cps)



for prompt delivery  
telephone London (01) 848 9781  
Edinburgh (031) 226 6201  
Manchester (061) 224 3306  
telex 935429

WW-024 FOR FURTHER DETAILS

## ASTONISHING STEREO DISC AMPLIFIER 2

FOR BROADCASTING, DISC MONITORING AND TRANSFER WITH THE HIGHEST QUALITY. Stereo Disc Amplifier 2 is a self-contained mains powered unit which accepts cartridge inputs and produces balanced line level outputs. Permanent rumble filtering and switched scratch filtering is included.

**FURTHER SPECIFICATIONS:** (For THD, IMD, etc. see March advertisement, page 112)  
1KHz at 6mV set for 0dBV.7 output. Loaded 600 ohms

### Frequency Response RIAA Accuracy

30Hz-20KHz

Within 0.5dB

Clipping at 1 KHz

Output +24dBV.7

Clipping Point Complementary to RIAA Curve

30Hz-20KHz

Within 0.5dB

Clipping determined by onset of peaky distortion products or THD exceeding -80dB.

Crosstalk

1KHz -76dB; 30Hz-20KHz -60dB

Outputs - Electronically balanced

Source impedance 50 ohms

H.F. Filter

Front panel switch

10KHz, 18dB/octave

Change in response at 8KHz or below

Less than 0.5dB

Sensitivity @ 1KHz

2.8-13mV for 0dBV.7 output. Presets adjustable through holes

### SURREY ELECTRONICS

The Forge, Lucks Green, Cranleigh, Surrey GU6 7BG (STD 04866) 5997

PHILIPS



# YOU & PHILIPS HI-FI KITS

The top sellers for home assembly in Europe - now available in the U.K.

Now - read all about the Philips range of quality kits for home assembly - mixers, amplifiers, speakers, etc. Send today to S.S.T. Distributors (Electronic Components) Ltd., West Road, Tottenham, London N17 0RN

Please send me, quickly, the new colour catalogue. WW51

Name

Address

PHILIPS

Postcode



**free** SEND TODAY!


S.S.T. Distributors is a member of the Philips Group of Companies.

## You've got to hand it to the 3001 thermometer.

Weighing only 300 gms., and easily fitting into the palm of your hand, the 3001 digital thermometer's bright green 8.2mm display gives 0.5°C resolution over the range -50°C to +1000°C.

A front panel thumb switch makes for simple control, and the unit's dry batteries or rechargeable cells give up to 7 hours operational life.

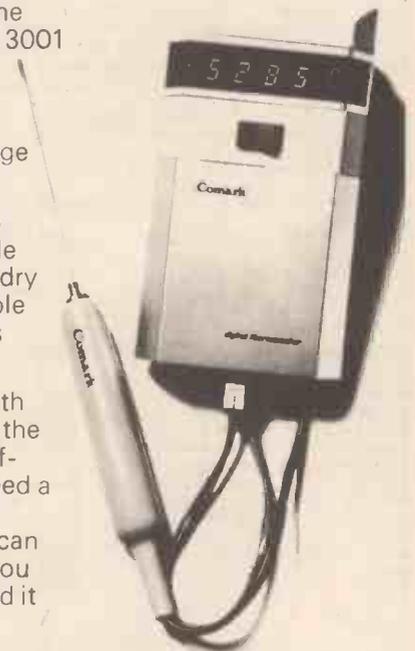Designed for use with thermocouple sensors the 3001 is completely self-contained, so if you need a reliable and durable thermometer that you can take anywhere; then you need a 3001. You'll find it really handy.



Comark Electronics Limited,  
Brookside Avenue, Rustington,  
West Sussex BN16 3LF, England.  
Tel: Rustington (090 62) 71911.  
Telex: 877317.

**Comark**

WW-065 FOR FURTHER DETAILS

# VALVE MAIL ORDER CO.

Climax House, 159 Fallsbrook Rd., Streatham  
London SW16 6ED

Tel: 01-677 2424 Telex: 946 708

| VALVES |      |             |      | INDUSTRIAL VALVES |      |        |      | TUBES  |      |        |      | TRANSISTORS & ICs |      |              |      |
|--------|------|-------------|------|-------------------|------|--------|------|--------|------|--------|------|-------------------|------|--------------|------|
| A231   | 1.00 | ECH81       | 0.35 | 6B5T              | 4.00 | 12A17  | 0.45 | 2N1303 | 0.45 | 2N7405 | 0.22 | AA119             | 0.17 | BF180        | 0.30 |
| A241   | 1.70 | ECH83       | 0.50 | 6BW6              | 3.00 | 12A16  | 0.50 | 2N1304 | 0.45 | 2N7406 | 0.42 | AA121             | 0.18 | BF181        | 0.30 |
| CB131  | 1.40 | ECH84       | 0.50 | 6BW7              | 1.12 | 12A17  | 0.38 | 2N1305 | 0.45 | 2N7407 | 0.42 | AA125             | 0.12 | BF194        | 0.10 |
| CL33   | 1.50 | ECL86       | 0.55 | 6C4               | 0.40 | 12A17  | 0.38 | 2N1306 | 0.45 | 2N7408 | 0.28 | AC107             | 0.75 | BF195        | 0.10 |
| CY31   | 1.00 | EF37A       | 3.00 | 6C4               | 0.40 | 12A17  | 0.38 | 2N1307 | 0.50 | 2N7409 | 0.28 | AC126             | 0.25 | BF197        | 0.12 |
| DAF91  | 0.60 | EF39        | 1.78 | 6C8C              | 1.60 | 12B6E  | 0.60 | 2N1308 | 0.50 | 2N7410 | 0.18 | AC127             | 0.25 | BF200        | 0.32 |
| DAF96  | 0.40 | EF41        | 0.75 | 6C8E              | 3.85 | 12B7H  | 0.60 | 2N1309 | 0.50 | 2N7411 | 0.25 | AC138             | 0.40 | BF201        | 0.40 |
| DCC90  | 1.35 | EF55        | 1.50 | 6E5T              | 1.50 | 30C15  | 1.00 | 2N1310 | 0.28 | 2N7412 | 0.30 | AC176             | 0.27 | BF598        | 0.25 |
| DF91   | 0.40 | EF60        | 0.35 | 6F23              | 0.90 | 30C17  | 1.00 | 2N1613 | 0.21 | 2N7413 | 0.36 | AC187             | 0.25 | BF599        | 0.25 |
| DF96   | 0.60 | EF85        | 0.45 | 6F28              | 0.96 | 30C18  | 1.28 | 2N1614 | 0.21 | 2N7414 | 0.36 | AC188             | 0.25 | BF599        | 0.25 |
| DK91   | 1.50 | EF86 (Jap)  |      | 6J5G              | 0.45 | 30F5   | 1.00 | 2N1615 | 0.21 | 2N7415 | 1.00 | AC189             | 0.25 | BF599        | 0.25 |
| DK92   | 1.00 | EF86 (USSR) |      | 6J6G              | 0.45 | 30F5   | 1.00 | 2N1616 | 0.21 | 2N7416 | 0.36 | AC193             | 0.38 | BF599        | 0.25 |
| DL92   | 0.75 | EF86 (USSR) |      | 6J7G              | 0.45 | 30F12  | 1.00 | 2N1617 | 0.21 | 2N7417 | 0.36 | AC194             | 0.38 | BF599        | 0.25 |
| DL96   | 0.55 | EF86 (USSR) |      | 6K6GT             | 0.80 | 30FL14 | 1.28 | 2N1618 | 0.21 | 2N7418 | 0.36 | AC195             | 0.38 | BF599        | 0.25 |
| DM70   | 0.70 | EF89        | 0.75 | 6K7GT             | 0.35 | 30L15  | 0.95 | 2N1619 | 0.21 | 2N7419 | 0.36 | AC196             | 0.38 | BF599        | 0.25 |
| DY86/7 | 0.45 | EF91        | 0.85 | 6K8GT             | 0.50 | 30L17  | 0.95 | 2N1620 | 0.21 | 2N7420 | 0.36 | AC197             | 0.38 | BF599        | 0.25 |
| DY87   | 0.47 | EF92        | 0.75 | 6L6GC             | 1.20 | 30P12  | 1.00 | 2N1621 | 0.21 | 2N7421 | 0.36 | AC198             | 0.38 | BF599        | 0.25 |
| EABCB0 | 0.38 | EF95 (USSR) |      | 6P25              | 1.25 | 30P18  | 0.95 | 2N1622 | 0.21 | 2N7422 | 0.36 | AC199             | 0.38 | BF599        | 0.25 |
| EAF42  | 0.70 | EF95 (USSR) |      | 6Q7GT             | 0.43 | 30PL1  | 1.44 | 2N1623 | 0.21 | 2N7423 | 0.36 | AD149             | 0.65 | BF599        | 0.25 |
| EAF901 | 0.75 | EF95 (UK)   |      | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1624 | 0.21 | 2N7424 | 0.36 | AD161             | 0.45 | BR100        | 0.40 |
| EBC33  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1625 | 0.21 | 2N7425 | 0.36 | AD162             | 0.45 | BY100        | 0.40 |
| EBC34  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1626 | 0.21 | 2N7426 | 0.36 | AF115             | 0.25 | BY126        | 0.12 |
| EBC35  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1627 | 0.21 | 2N7427 | 0.36 | AF116             | 0.25 | BY127        | 0.12 |
| EBC36  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1628 | 0.21 | 2N7428 | 0.36 | AF117             | 0.25 | BY127        | 0.12 |
| EBC37  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1629 | 0.21 | 2N7429 | 0.36 | AF118             | 0.25 | BY127        | 0.12 |
| EBC38  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1630 | 0.21 | 2N7430 | 0.36 | AF239             | 0.45 | BZ188 series |      |
| EBC39  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1631 | 0.21 | 2N7431 | 0.36 | AS27              | 0.25 |              |      |
| EBC40  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1632 | 0.21 | 2N7432 | 0.36 | AS28              | 0.25 |              |      |
| EBC41  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1633 | 0.21 | 2N7433 | 0.36 | BA102             | 0.25 |              |      |
| EBC42  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1634 | 0.21 | 2N7434 | 0.36 | BA115             | 0.15 |              |      |
| EBC43  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1635 | 0.21 | 2N7435 | 0.36 | BC107             | 0.14 |              |      |
| EBC44  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1636 | 0.21 | 2N7436 | 0.36 | BC108             | 0.14 |              |      |
| EBC45  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1637 | 0.21 | 2N7437 | 0.36 | BC109             | 0.15 |              |      |
| EBC46  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1638 | 0.21 | 2N7438 | 0.36 | BC113             | 0.15 |              |      |
| EBC47  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1639 | 0.21 | 2N7439 | 0.36 | BC117             | 0.27 |              |      |
| EBC48  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1640 | 0.21 | 2N7440 | 0.36 | BC143             | 0.30 |              |      |
| EBC49  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1641 | 0.21 | 2N7441 | 0.36 | BC147             | 0.10 |              |      |
| EBC50  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1642 | 0.21 | 2N7442 | 0.36 | BC148             | 0.08 |              |      |
| EBC51  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1643 | 0.21 | 2N7443 | 0.36 | BC189C            | 0.18 |              |      |
| EBC52  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1644 | 0.21 | 2N7444 | 0.36 | BC182             | 0.12 |              |      |
| EBC53  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1645 | 0.21 | 2N7445 | 0.36 | BC182L            | 0.12 |              |      |
| EBC54  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1646 | 0.21 | 2N7446 | 0.36 | BC184L            | 0.13 |              |      |
| EBC55  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1647 | 0.21 | 2N7447 | 0.36 | BCY32             | 1.00 |              |      |
| EBC56  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1648 | 0.21 | 2N7448 | 0.36 | BCY33             | 1.00 |              |      |
| EBC57  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1649 | 0.21 | 2N7449 | 0.36 | BCY34             | 0.75 |              |      |
| EBC58  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1650 | 0.21 | 2N7450 | 0.36 | BCY70             | 0.18 |              |      |
| EBC59  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1651 | 0.21 | 2N7451 | 0.36 | BCY71             | 0.22 |              |      |
| EBC60  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1652 | 0.21 | 2N7452 | 0.36 | BCY72             | 0.17 |              |      |
| EBC61  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1653 | 0.21 | 2N7453 | 0.36 | BCZ11             | 1.25 |              |      |
| EBC62  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1654 | 0.21 | 2N7454 | 0.36 | BD121             | 1.55 |              |      |
| EBC63  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1655 | 0.21 | 2N7455 | 0.36 | BD124             | 0.75 |              |      |
| EBC64  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1656 | 0.21 | 2N7456 | 0.36 | BD131             | 0.40 |              |      |
| EBC65  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1657 | 0.21 | 2N7457 | 0.36 | BD132             | 0.45 |              |      |
| EBC66  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1658 | 0.21 | 2N7458 | 0.36 | BF178             | 0.25 |              |      |
| EBC67  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1659 | 0.21 | 2N7459 | 0.36 | BF179             | 0.36 |              |      |
| EBC68  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1660 | 0.21 | 2N7460 | 0.36 |                   |      |              |      |
| EBC69  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1661 | 0.21 | 2N7461 | 0.36 |                   |      |              |      |
| EBC70  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1662 | 0.21 | 2N7462 | 0.36 |                   |      |              |      |
| EBC71  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1663 | 0.21 | 2N7463 | 0.36 |                   |      |              |      |
| EBC72  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1664 | 0.21 | 2N7464 | 0.36 |                   |      |              |      |
| EBC73  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1665 | 0.21 | 2N7465 | 0.36 |                   |      |              |      |
| EBC74  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1666 | 0.21 | 2N7466 | 0.36 |                   |      |              |      |
| EBC75  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1667 | 0.21 | 2N7467 | 0.36 |                   |      |              |      |
| EBC76  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1668 | 0.21 | 2N7468 | 0.36 |                   |      |              |      |
| EBC77  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1669 | 0.21 | 2N7469 | 0.36 |                   |      |              |      |
| EBC78  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1670 | 0.21 | 2N7470 | 0.36 |                   |      |              |      |
| EBC79  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1671 | 0.21 | 2N7471 | 0.36 |                   |      |              |      |
| EBC80  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1672 | 0.21 | 2N7472 | 0.36 |                   |      |              |      |
| EBC81  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1673 | 0.21 | 2N7473 | 0.36 |                   |      |              |      |
| EBC82  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1674 | 0.21 | 2N7474 | 0.36 |                   |      |              |      |
| EBC83  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1675 | 0.21 | 2N7475 | 0.36 |                   |      |              |      |
| EBC84  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1676 | 0.21 | 2N7476 | 0.36 |                   |      |              |      |
| EBC85  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1677 | 0.21 | 2N7477 | 0.36 |                   |      |              |      |
| EBC86  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1678 | 0.21 | 2N7478 | 0.36 |                   |      |              |      |
| EBC87  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1679 | 0.21 | 2N7479 | 0.36 |                   |      |              |      |
| EBC88  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1680 | 0.21 | 2N7480 | 0.36 |                   |      |              |      |
| EBC89  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1681 | 0.21 | 2N7481 | 0.36 |                   |      |              |      |
| EBC90  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1682 | 0.21 | 2N7482 | 0.36 |                   |      |              |      |
| EBC91  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1683 | 0.21 | 2N7483 | 0.36 |                   |      |              |      |
| EBC92  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1684 | 0.21 | 2N7484 | 0.36 |                   |      |              |      |
| EBC93  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1.44 | 2N1685 | 0.21 | 2N7485 | 0.36 |                   |      |              |      |
| EBC94  | 1.00 | EF98        | 0.80 | 6S7GT             | 0.50 | 30PL13 | 1    |        |      |        |      |                   |      |              |      |

Zambia Gibraltar Chile Spain United Arab Emirates Singapore New Guinea Israel

Falkland Islands Portugal Guyana India Greece Jordan America Yugoslavia Island Ascension Malaysia

# POWERTRAN ELECTRONICS

INCORPORATING

# AMBIENTACOUSTICS

## HI-FI NEWS 75W/CHANNEL AMPLIFIER



By J. L. Linsley Hood

In Hi-Fi News there was published by Mr. Linsley-Hood a series of four articles (November, 1972-February, 1973) and a subsequent follow-up article (April, 1974) on a design for an amplifier of exceptional performance which has as its principal feature an ability to supply from a direct coupled fully protected output stage, power in excess of 75 watts whilst maintaining distortion at less than 0.01% even at very low power levels. The power amplifier is complemented by a pre-amplifier based on a discrete component operational amplifier referred to as the Linciac which is employed in the two most critical points of the system, namely the equalization stage and tone control stage, positions where most conventional designs run out of gain at the extremes of the frequency spectrum. Unusual features of the design are the variable transition frequencies of the tone controls and the variable slope of the scratch filter. There is a choice of four inputs, two equalized and two linear, each having independently adjustable signal level. The attractive slimline unit pictured, has been made practical by highly compact PCBs and a specially designed Toroidal transformer.

- | Pack  | Price  |
|---|--------|
| 1. Fibreglass printed-circuit board for power amp   | £1.15  |
| 2. Set of resistors, capacitors, pre-sets for power amp   | £2.50  |
| 3. Set of semiconductors for power amp  | £5.50  |
| 4. Pair of 2 drilled, finned heat sinks   | £1.10  |
| 5. Fibreglass printed-circuit board for pre-amp   | £1.90  |
| 6. Set of low noise resistors, capacitors, pre-sets for pre-amp   | £4.10  |
| 7. Set of low noise, high gain semiconductors for pre-amp   | £2.40  |
| 8. Set of potentiometers (including mains switch)   | £3.50  |
| 9. Set of 4 push-button switches, rotary mode switch  | £5.40  |
| 10. Toroidal transformer complete with magnetic screen/insulating primary: 0 117-234 V; secondaries: 33-0-33 V, 25-0-25 V | £10.95 |

- | Pack  | Price  |
|---|--------|
| 11. Fibreglass printed-circuit board for power supply   | £0.85  |
| 12. Set of resistors, capacitors, secondary semiconductors for power supply   | £5.40  |
| 13. Set of miscellaneous parts including DIN sinks, mains input sht, fuse holder, inter-connecting cable, control knobs | £6.20  |
| 14. Set of metalwork parts including silk screen printed fascia panel and all brackets, fixing parts, etc               | £8.20  |
| 15. Handbook (free with complete kit)   | £0.30  |
| 16. Teak cabinet 18.3" x 12.7" x 3.1"   | £10.70 |
- 2 each of packs 1-7 inclusive are required for complete stereo system. Total cost of individually purchased packs ..... £90.80

Designed in response to demand for a tuner to complement the world-wide acclaimed Linsley Hood 75W Amplifier, this kit provides the perfect match. The Wireless World (Skingley and Thompson - April, May 1974) published original circuit has been developed further for inclusion into this outstanding slimline unit and features a pre-aligned front end module, excellent a.m. rejection and temperature compensated varicap tuning, which may be controlled either continuously or by push button pre-selection. Frequencies are indicated by a frequency meter and sliding LED indicators, attached to each channel selector pre-set. The PLL stereo decoder incorporates active filters for "birdy" suppression and power is supplied via a toroidal transformer and integrated regulator. For long term stability metal oxide resistors are used throughout.

- | Pack   | Price  |
|--|--------|
| 1. Fibreglass printed board for front end IF strip, demodulator, AFC and auto circuits   | £2.15  |
| 2. Set of metal oxide resistors, thermistor, capacitors, current preset for mounting on pack 1   | £4.80  |
| 3. Set of transistors, diodes, LED, integrated circuits for mounting on pack 1   | £5.25  |
| 4. Pre-aligned front end module, coil assembly, three section ceramic filter   | £8.50  |
| 5. Fibreglass printed circuit board for stereo decoder   | £1.10  |
| 6. Set of metal oxide resistors, capacitors, current preset for decoder  | £2.60  |
| 7. Set of transistors, LED, integrated circuit for decoder   | £2.90  |
| 8. Set of components for channel selector switch, module including fibreglass printed circuit board, push-button switches, knobs, LEDs, preset adjusters, etc. | £9.40  |
| 9. Function switch, 10 turn tuning potentiometer, knobs  | £5.80  |
| 10. Frequency meter, meter drive components, fibreglass printed circuit board  | £10.35 |

- | Pack   | Price  |
|--|--------|
| 11. Toroidal transformer with electrostatic screen, Primary: 0-117V 234V   | £4.90  |
| 12. Set of capacitors, rectifiers, voltage regulator for power supply  | £2.10  |
| 13. Set of miscellaneous parts, including sockets, fuse holder, fuses, inter-connecting wire, etc.   | £2.05  |
| 14. Set of metal work parts including silk screen printed fascia panel, acrylic silk screen printed tuning indicator panel insert, internal screen, fixing parts, etc. | £8.30  |
| 15. Construction notes (free with complete kit)  | £0.25  |
| 16. Teak cabinet 10.3" x 12.7" x 3.1"  | £10.70 |
- One each of packs 1-16 inclusive are required for complete stereo FM tuner. Total cost of individually purchased packs ..... £81.15

Published in Wireless World (May, June, August 1976) by Mr. Linsley-Hood, this design, although straightforward and relatively low cost nevertheless provides a very high standard of performance. To permit circuit optimization separate record and replay amplifiers are used, the latter using a discrete component front-end designed such that the noise level is below that of the tape background. Push button switches are used to provide a choice of equalization time constants, a choice of bias levels and also an option of using an additional pre-amplifier for microphone use. The mechanism used is the Goldring-Lenco CRV, a unit distinguished in its robustness and ease of operation. Speed control and automatic cassette ejection are both implemented by electronic circuitry. This unit which is powered by a toroidal transformer and uses metal oxide resistors throughout offers an excellent match for the Wireless World Tuner and the Linsley-Hood 75 Watt Amplifier.

### PRICE STABILITY

Order with confidence! Irrespective of any price changes we will honour all prices in this advertisement for two months from issue date provided that this advertisement is quoted with your order. E&OE VAT rate changes excluded. All components are brand new first grade full specification devices. All resistors (except where stated) are low noise carbon film types. All printed circuit boards are fibre-glass, drilled, roller tinned and supplied with circuit diagrams and construction layouts.

Value Added Tax not included in prices.

EXPORT ORDERS. No VAT charged. Postage charged at actual cost plus 50p, documentation and handling. Please make payment by Irrevocable Letter of Credit (£500 minimum), Bank Draft, Postal Order, International Money Order in Sterling. SECURICOR DELIVERY: For this optional service (U.K. Mainland only) add £2.50 (VAT INC.) per kit.

U.K. ORDERS: Subject to 12 1/2 % surcharge for VAT. Carriage free. MAIL ORDER ONLY. (Not at current rate if changed)

FREE TEAK CASE WITH FULL KITS  
KIT PRICE ONLY **£79.80**

## WIRELESS WORLD FM TUNER



FREE TEAK CASE WITH FULL KITS  
KIT PRICE ONLY **£70.20**

## LINSLEY-HOOD CASSETTE DECK



- | Pack   | Price  |
|--|--------|
| 1. Stereo PCB (accommodates 2 rec. amps, 2 rec. amps, 2 motor amps, bias/erase osc. relay) | £3.35  |
| 2. Stereo set of capitors, M.O. resistors, potentiometers for above                        | £9.80  |
| 3. Stereo set of semiconductors for above  | £8.50  |
| 4. Miniature relay with socket   | £2.90  |
| 5. PCB, all components for solenoid, speed control circuits                                | £3.80  |
| 6. Goldring Lenco mechanism as specified   | £21.95 |
| 7. Function switch, knobs  | £1.90  |
| 8. Dual VU meter with illuminating lamp  | £8.70  |
| 9. Toroidal transformer with E.S. screen prim, 0-117V, 234V, Sec. 15V                      | £4.90  |

- | Pack  | Price  |
|---|--------|
| 10. Set of capacitors, rectifiers, i.C. voltage regulator for power supply (Powertran design)     | £2.80  |
| 11. Set of miscellaneous parts, including sockets, fuse holder, fuses, interconnecting wire, etc. | £3.40  |
| 12. Set of metalwork including silk screened fascia panel, internal screen, fixing parts, etc.    | £7.10  |
| 13. Construction notes  | £0.25  |
| 14. Teak cabinet 18.3" x 12.7" x 3.1"   | £10.70 |
- One each of packs 1-14 inclusive are required for complete stereo cassette deck. Total cost of individually purchased packs ..... £90.05

SPECIAL PRICE FOR COMPLETE KITS **£85.90**

Further details of above given in our FREE CATALOGUE EXPORT CUSTOMERS. Please send five INTERNATIONAL REPLY COUPONS OR £0.50 for catalogue to be sent by airmail. DEPT. WW4

# POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE  
ANDOVER, HANTS SP10 3NN

Indonesia Brazil Switzerland Canada Saudi Arabia New Zealand Norway Iceland Sweden

Guernsey Cyprus Belgium Uganda Brunei Trinidad South West Africa Italy Java Grenada

# AUDIO KIT SUPPLIERS TO THE WORLD



## T20+20 and our new T30+30 20W, 30W AMPLIFIERS

Designed by Texas engineers and described in Practical Wireless the Texan was an immediate success. Now developed further in our laboratories to include a Toroidal transformer and additional improvements, the slimline T20+20 delivers 20W per channel of true Hi-Fi at an exceptionally low cost. The design is based on a single F/Glass PCB and features all the normal facilities found on quality amplifiers, including scratch and rumble filters, adaptable input selector and head phones socket. In a follow up article in Practical Wireless further modifications were suggested and these have been incorporated into the T30+30. These include RF interference filters and a tape monitor facility. Power output of this new model is 30W per channel.

| Pack                                  | T20  | T30  |
|---------------------------------------|------|------|
| 1. Set of low noise resistors         | 1.60 | 1.70 |
| 2. Set of small capacitors            | 2.60 | 3.40 |
| 3. Set of power supply capacitors     | 2.20 | 2.50 |
| 4. Set of miscellaneous parts         | 3.50 | 3.50 |
| 5. Set of slide, mains, P.B. switches | 1.50 | 1.50 |
| 6. Set of pots, selector switch       | 2.80 | 2.80 |
| 7. Set of semiconductors, ICs, skts.  | 7.25 | 7.25 |

| Pack   | T20  | T30  |
|--|------|------|
| 8. Toroidal transformer — 240V prim. e.s. screen | 5.60 | 7.20 |
| 9. Fibreglass PCB                                | 3.50 | 3.90 |
| 10. Set of metalwork, fixing parts               | 5.20 | 6.20 |
| 11. Set of cables, mains lead                    | 0.40 | 0.40 |
| 12. Handbook (free with complete kit)            | 0.25 | 0.25 |
| 13. Teak cabinet 15.4" x 6.7" x 2.8"             | 4.50 | 4.50 |

### SPECIAL PRICES

FOR COMPLETE KITS!

T20+20  
KIT PRICE only **£ 34.20**

T30+30  
KIT PRICE only **£ 39.50**

### 2 MATCHING TUNERS!

#### WW SFMT II

Following the success of our Wireless World FM Tuner kit we are now pleased to introduce our new cost reduced model, designed to complement the T20 and T30 amplifiers. The frequency meter of the more advanced model has been omitted and the mechanics simplified, however the circuitry is identical and this new kit offers most exceptional value for money. Facilities included are switchable afc, adjustable, switchable muting, channel selection by slider or readily adjustable pre-set push-button controls and LED tuning indication. Individual pack prices in our free list.


KIT PRICE  
**£47.70**



#### POWERTRAN SFMT

This easy to construct tuner using our own circuit design includes a pre-tuned front end module, PLL stereo decoder, adjustable, switchable muting, switchable afc and push-button channel selection. As with all our full kits, all components down to the last nut and bolt are supplied together with full constructional details.

KIT PRICE  
**£35.90**

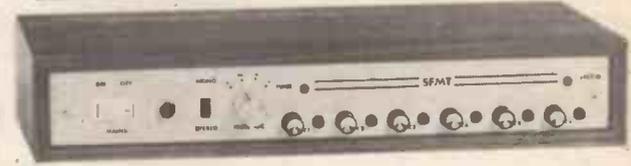

### CONVERT NOW TO QUADRAPHONICS!



**SQM1 - 30** KIT PRICE **£40.75**

Wireless World Amplifier Designs. Full kits are not available for these projects but component packs and PCBs are stocked for the highly regarded Bailey and 20W class AB Unley Hood designs, together with an efficient regulated power supply of our own design. Suitable for driving these amplifiers is the Bailey Burrows pre-amplifier and our circuit board, for the stereo version of it features 6 inputs, scratch and rumble filters and wide range tone controls which may be either rotary or slider operating. For those intending to get the best out of their speakers, we also offer an active filter system, described by D. C. Read, which splits the output of each channel from the pre-amplifier into three channels each of which is fed to the appropriate speaker by its own power amplifier. The Read/Texas 20W, or any of our other kits are suitable for these. For tape systems a set of three PCBs have been prepared for the integrated circuit based, high performance stereo Stuart design. Details of component packs are in our free catalogue.

With 100s of titles now available no longer is there any problem over suitable software. No problems with hardware either. Our new unit the SQM1-30 simply plugs into the tape monitor socket of your existing amplifier and drives two additional speakers at 30W per channel. A full complement of controls including: volume, bass, treble and balance are provided as are comprehensive switching facilities enabling the unit to be used, for either front or rear channels, by-passing the decoder for stereo-only use and exchanging left and right channels. The SQ matrix decoder is based upon a single integrated circuit and was designed by CBS whilst the power and tone control sections are identical to those used in our T30 + 30 amplifier which the SQM1-30 matches perfectly. Kit price includes CBS licence fee.



Special offer to T20 + 20 and Texan owners!  
Owners of T20 + 20 and Texan amplifiers, which have no tape monitor outlet, purchasing an SQM 1-30 will be supplied on request, a free conversion kit to fit a tape monitoring facility to the existing amplifier. This makes simple the connection to the highly adaptable SQM 1-30 quadraphonic decoder/rear channel amplifier.

### SQ QUADRAPHONIC DECODERS

Feed 2 channels (200-1000mV as obtainable from most pre-amplifiers or amplifier tape monitor outlets) into any one of our 3 decoders and take 4 channels out with no overall signal level reduction. On the logic enhanced decoders Volume, Front-Back, LF-RF balance, LB-RB balance and Dimension controls can all be implemented by simple single gang potentiometers.

These state-of-the-art circuits used under licence from CBS are offered in kits of superior quality with close tolerance capacitors, metal oxide resistors and fibre-glass PCBs designed for edge connector insertion. All kit prices include CBS licence fee.

- M1. Basic matrix decoder with fixed 10-40 blend. All components, PCB **£5.90**
  - L1. Full logic controlled decoder with "wave matching" and "front back logic" for enhanced channel separation. All components PCB **£17.20**
  - L2A. More advanced full logic decoder with "variable blend" for increased front back separation. All components, PCB **£22.60**
  - L3A. Decoder similar to L2A but with discreet component front end with high precision 6-pole phase shift networks for increased frequency response. All components (carbon film resistors), PCB **£25.90**
- Also available with M.O. resistors, cermet pre-set — add **£4.20**

### SEMICONDUCTORS as used in our range of quality audio equipment:

|           |       |        |       |          |       |          |       |        |       |
|-----------|-------|--------|-------|----------|-------|----------|-------|--------|-------|
| 2N695     | £0.20 | BC10B  | £0.10 | BF257    | £0.40 | MPSA05   | £0.25 | TIP20C | £0.55 |
| 2N1613    | £0.20 | BC109  | £0.10 | BF259    | £0.47 | MPSA12   | £0.35 | TIP30C | £0.60 |
| 2N3055    | £0.45 | BC109C | £0.12 | BFR39    | £0.30 | MPSA14   | £0.30 | TIP41A | £0.70 |
| 2N3442    | £1.20 | BC125  | £0.15 | BFR79    | £0.30 | MPSA55   | £0.25 | TIP42A | £0.80 |
| 2N3711    | £0.09 | BC126  | £0.15 | BFY51    | £0.20 | MPSA65   | £0.35 | TIP41B | £0.75 |
| 2N3904    | £0.17 | BC182  | £0.10 | BFY52    | £0.20 | MPSA66   | £0.40 | TIP42B | £0.90 |
| 2N3906    | £0.20 | BC212  | £0.12 | CA3046   | £0.70 | MPSU05   | £0.50 | 1N914  | £0.07 |
| 2N5087    | £0.25 | BC182L | £0.10 | LP1186   | £8.50 | SBA750A  | £1.90 | 1N916  | £0.07 |
| 2N5457    | £0.45 | BC184L | £0.11 | MC1310   | £2.20 | SL301    | £1.30 | 1S920  | £0.10 |
| 2N5459    | £0.45 | BC212L | £0.12 | MC1351   | £1.05 | SL3045   | £1.20 |        |       |
| 2N5461    | £0.50 | BC214L | £0.14 | MC1741CG | £0.65 | SN72741P | £0.40 |        |       |
| 2N5830    | £0.35 | BCY72  | £0.13 | MFC4010  | £0.95 | SN72748P | £0.40 |        |       |
| TRRP P1   | £0.30 | 40361  | £0.40 | BD529    | £0.65 | MJ481    | £1.20 | TIL209 | £0.20 |
| TRRC Pk 1 | £1.70 | 40362  | £0.45 | BD530    | £0.55 | MJ491    | £1.45 | TIP29A | £0.40 |
| TROS Pk 1 | £1.20 | BC107  | £0.10 | BDY56    | £1.60 | MJ521    | £0.60 | TIP30A | £0.45 |

FILTERS  
FMA £1.00  
SFJ10,7MA £1.50

### EXPORT NO PROBLEM

Our Export Department will be pleased to advise on postal costs to any country in the world. Some of the countries to which we sent kits in 1976 are shown surrounding this advertisement.

Tunisia Germany Nauru Hong Kong Australia Eire Gambia Denmark France Muscat & Oman

Sierra Leone Jamaica Holland Kenya Malta Windward Isles Austria Czechoslovakia South Africa Finland Nigeria Luxembourg

# 15 - 240 Watts!

## HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc.) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

**FEATURES:** Complete pre-amplifier in single pack — Multi-function equalization — Low noise — Low distortion — High overload — two simply combined for stereo.

**APPLICATIONS:** Hi-Fi — Mixers — Disco — Guitar and Organ — Public address.

**SPECIFICATIONS:**

**INPUTS:** Magnetic Pick-up 3mV; Ceramic Pick-up 30mV; Tuner: 100mV; Microphone: 10mV; Auxiliary 3-100mV; input impedance 47k $\Omega$  at 1kHz.

**OUTPUTS:** Tape 100mV; Main output 500mV R.M.S.


**ACTIVE TONE CONTROLS:** Treble  $\pm$  12dB at 10kHz; Bass  $\pm$  at 100Hz.

**DISTORTION:** 0.1% at 1kHz; Signal/Noise Ratio 68dB.

**OVERLOAD:** 38dB on Magnetic Pick-up; **SUPPLY VOLTAGE**  $\pm$  16.50V

**Price** £5.22 + 65p VAT P&P free

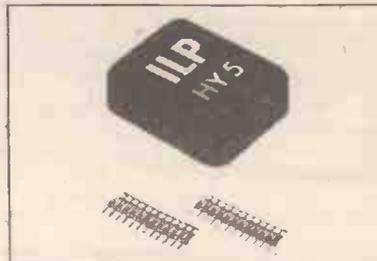HY5 mounting board B1 48p  $\downarrow$  6p VAT P&P free.



## HY30 15 Watts into 8 $\Omega$

The HY30 is an exciting New kit from I.L.P., it features a virtually Indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

**FEATURES:** Complete kit — Low Distortion — Short, Open and Thermal Protection — Easy to Build. **APPLICATIONS:** Updating audio equipment — Guitar practice amplifier — Test amplifier — Audio oscillator.

**SPECIFICATIONS:**

**OUTPUT POWER** 15W R.M.S. into 8 $\Omega$ . **DISTORTION** 0.1% at 15W.

**INPUT SENSITIVITY** 500mV. **FREQUENCY RESPONSE** 10Hz-16kHz — 3dB.

**SUPPLY VOLTAGE**  $\pm$  18V.

**Price** £5.22 + 65p VAT P&P free.



## HY50 25 Watts into 8 $\Omega$

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

**FEATURES:** Low Distortion — Integral Heatsink — Only five connections — 7 Amp output transistors — No external components.

**APPLICATIONS:** Medium Power Hi-Fi systems — Low power disco — Guitar amplifier.

**SPECIFICATIONS:** **INPUT SENSITIVITY** 500mV.

**OUTPUT POWER** 25W RMS in 8 $\Omega$  **LOAD IMPEDANCE** 4-16 $\Omega$ . **DISTORTION** 0.04% at 25W at 1kHz.

**SIGNAL/NOISE RATIO** 75dB. **FREQUENCY RESPONSE** 10Hz-45kHz — 3dB.

**SUPPLY VOLTAGE**  $\pm$  25V. **SIZE** 105.50.25mm.

**Price** £6.82 + 85p VAT P&P free



## HY120 60 Watts into 8 $\Omega$

The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection, this amplifier sets a new standard in modular design.

**FEATURES:** Very low distortion — Integral Heatsink — Load line protection — Thermal protection — Five connections — No external components.

**APPLICATIONS:** Hi-Fi — High quality disco — Public address — Monitor amplifier — Guitar and organ.

**SPECIFICATIONS:**


**INPUT SENSITIVITY** 500mV

**OUTPUT POWER** 60W RMS into 8 $\Omega$ . **LOAD IMPEDANCE** 4-16 $\Omega$ . **DISTORTION** 0.04% at 60W at 1kHz.

**SIGNAL/NOISE RATIO** 90dB. **FREQUENCY RESPONSE** 10Hz-45kHz — 3dB. **SUPPLY VOLTAGE**  $\pm$  35V.

**Size:** 114 x 50 x 85mm.

**Price** £15.84 + £1.27 VAT P&P free.

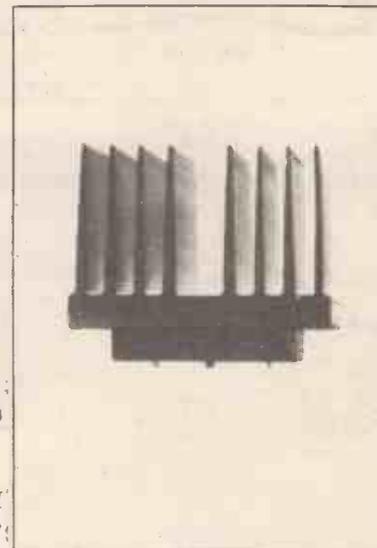

## HY200 120 Watts into 8 $\Omega$

The HY200, now improved to give an output of 120 Watts, has been designed to stand the most rugged conditions, such as disco or group while still retaining true Hi-Fi performance.

**FEATURES:** Thermal shutdown — Very low distortion — Loadline protection — Integral Heatsink — No external components.

**APPLICATIONS:** Hi-Fi — Disco — Monitor — Power Slave — Industrial — Public address.

**SPECIFICATIONS:**

**INPUT SENSITIVITY** 500mV.

**OUTPUT POWER** 120W RMS into 8 $\Omega$ . **LOAD IMPEDANCE** 4-16 $\Omega$ . **DISTORTION** 0.05% at 100W at 1kHz.

**SIGNAL/NOISE RATIO** 96dB. **FREQUENCY RESPONSE** 10Hz-45kHz — 3dB. **SUPPLY VOLTAGE**  $\pm$  45V.

**SIZE** 114 x 100 x 85mm.

**Price** £23.32 + £1.87 VAT P&P free.

## HY400 240 Watts into 4 $\Omega$

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 $\Omega$ ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

**FEATURES:** Thermal shutdown — Very low distortion — Load line protection — No external components.

**APPLICATIONS:** Public address — Disco — Power slave — Industrial.


**SPECIFICATIONS:**

**OUTPUT POWER** 240W RMS into 4 $\Omega$ . **LOAD IMPEDANCE** 4-16 $\Omega$ . **DISTORTION** 0.1% at 240W at 1kHz.

**SIGNAL/NOISE RATIO** 94dB. **FREQUENCY RESPONSE** 10Hz-45kHz — 3dB. **SUPPLY VOLTAGE**  $\pm$  45V.

**INPUT SENSITIVITY** 500mV. **SIZE** 114 x 100 x 85mm.

**Price** £32.17 + £2.57 VAT P&P free.

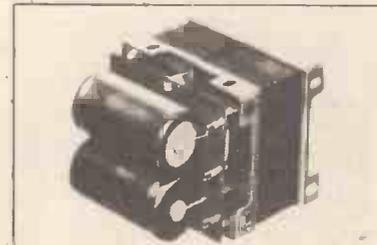

## POWER SUPPLIES

PSU36 suitable for two HY30's £5.22 plus 65p VAT P/P free.  
 PSU50 suitable for two HY50's £6.82 plus 85p VAT P/P free.  
 PSU70 suitable for 2 HY120's £13.75 plus £1.10 VAT P/P free.  
 PSU90 suitable for one HY200 £12.65 plus £1.01 VAT P/P free.  
 PSU180 suitable for two HY200's or one HY400 £23.10 plus £1.85 VAT P/P free.  
 $\downarrow$  48p plus 6p VAT

TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS

I.L.P. Electronics Ltd  
 Crossland House  
 Nackington, Canterbury  
 Kent CT4 7AD  
 Tel (0227) 63218

Please Supply \_\_\_\_\_  
 Total Purchase Price \_\_\_\_\_  
 I Enclose Cheque  Postal Orders  Money Order   
 Please debit my Access account  Barclaycard account   
 Account number \_\_\_\_\_  
 Name & Address \_\_\_\_\_  
 Signature \_\_\_\_\_

# CATRONICS WW TELETEXT DECODER



Our kit contains all the printed circuit boards and components necessary to build the complete decoder. The power supply and video switching circuitry are normally installed within the television cabinet and the main decoding control and memory circuitry in a separate cabinet positioned on top of the television.

**PRICES (INCLUDING VAT) ARE AS FOLLOWS:**

|                                | Standard version using 2513 | New version with Texas X887 | Post & Packing |
|--------------------------------|-----------------------------|-----------------------------|----------------|
| Set of 5 PCBs                  | £20.70                      | £20.65                      | 30p            |
| Component Kit (incl. PCBs)     | £120.95                     | £133.70                     | £1.50          |
| Add-on Unit for lower case PCB | £2.70                       | —                           | —              |
| Component Kit (incl. PCB)      | £13.75                      | —                           | —              |
| Cabinet                        | £14.85                      | £14.85                      | £1.00          |

PLATED-THROUGH hole PCBs are available for TEXAS version only at additional cost of £27.00.

A reprint of the series of articles is available at £1.50 + large 14p SAE (included free in complete kit).

**COMPONENTS ALSO AVAILABLE SEPARATELY — SAE for price list. READY BUILT & TESTED DECODERS also available at £241.87 + £5 Carr.**

## VHF DIGITAL FREQUENCY METER

200MHz, 7 digit, D.F.M.

for direct readings up to the mobile radio VHF 'High Band'. Will operate on mains or 12V supply, making it ideal for use with mobile equipment. Manufactured and guaranteed by Catronics. Price only £141.75 + £1.50 carriage (inc. VAT). Write for illustrated leaflet.



**CATRONICS LTD (Dept 725)**

Communications House, 20 Wallington Square, Wallington, Surrey Tel: 01-669 6700



WW — 725 FOR FURTHER DETAILS

## Signal chokes

Miniature low-cost precision inductors for radio, TV, calculators, filters etc.




7BA




7BA: 1uH to 1mH

8RB

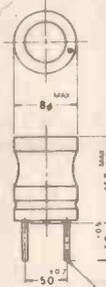


8RB: 0.1mH to 33mH

10RB

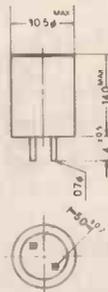

10RB: 1mH to 120mH

10RA

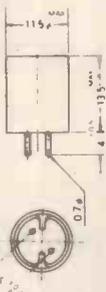

10RA: 1mH to 80mH

TOKO (UK) Ltd. Ward Royal Pde., Alma Rd., Windsor, Berkshire. (07535-54057)

Ambit International, 37a High St., Brentwood, Essex. (0277-227050) for ex-stock values.

WW—062 FOR FURTHER DETAILS

## TRANSFORMERS

ALL EX-STOCK — SAME-DAY DESPATCH

MAINS ISOLATING VAT 8% 12 and/or 24-VOLT

PRI 120/240V SEC 120/240V Centre Tapped and Screened

Separate 12v windings Primary 220-240 Volts

| Ref. | VA (Watts) | £     | Ref. | 12v Amps | 24v Amps | £    | P&P   |      |
|------|------------|-------|------|----------|----------|------|-------|------|
| 07*  | 20         | 3.57  | 86   | 111      | 0.5      | 0.25 | 1.77  | .36  |
| 149  | 60         | 5.39  | 80   | 213      | 1.0      | 0.5  | 2.14  | .65  |
| 150  | 100        | 6.13  | 95   | 71       | 2        | 1    | 2.77  | .80  |
| 151  | 200        | 9.82  | 1.25 | 18       | 4        | 2    | 3.42  | .80  |
| 152  | 250        | 11.87 | 1.53 | 70       | 6        | 3    | 5.09  | .80  |
| 153  | 350        | 14.34 | 1.53 | 108      | 8        | 4    | 5.85  | .95  |
| 154  | 500        | 16.48 | 1.79 | 72       | 10       | 5    | 6.33  | .95  |
| 155  | 750        | 25.23 | OA   | 116      | 12       | 6    | 6.67  | 1.10 |
| 156  | 1000       | 35.16 | OA   | 17       | 16       | 8    | 8.60  | 1.10 |
| 157  | 1500       | 40.12 | OA   | 115      | 20       | 10   | 12.55 | 1.73 |
| 158  | 2000       | 44.76 | OA   | 187      | 30       | 15   | 16.33 | 1.73 |
| 159  | 3000       | 70.70 | OA   | 226      | 60       | 30   | 20.32 | OA   |

\*15 or 240 sec only

### 50 VOLT RANGE

Primary 220-240V

SEC. TAPS 0-19-25-33-40-50V

| Ref. | Amps | £     | P&P  |
|------|------|-------|------|
| 102  | 0.5  | 3.12  | .65  |
| 103  | 1.0  | 4.08  | .80  |
| 104  | 2.0  | 5.69  | .95  |
| 105  | 3.0  | 7.02  | 1.10 |
| 106  | 4.0  | 9.18  | 1.25 |
| 107  | 6.0  | 14.62 | 1.37 |
| 118  | 8.0  | 15.56 | 1.73 |
| 119  | 10.0 | 20.41 | OA   |

### 30 VOLT RANGE

Primary 220-240V

SEC. TAPS 0-12-15-20-25-30V

| Ref. | Amps | £     | P&P    |
|------|------|-------|--------|
| 112  | 0.5  | 2.27  | .65    |
| 79   | 1.0  | 2.90  | .80    |
| 3    | 2.0  | 4.34  | .80    |
| 20   | 3.0  | 5.41  | .95    |
| 21   | 4.0  | 6.39  | .95    |
| 51   | 5.0  | 7.74  | £ 1.10 |
| 117  | 6.0  | 8.65  | 1.25   |
| 88   | 8.0  | 11.73 | 1.37   |
| 89   | 10.0 | 11.91 | 1.53   |

### 60 VOLT RANGE

Primary 220-240V

SEC TAPS 0-24-30-40-48-60V

| Ref. | Amps | £     | P&P  |
|------|------|-------|------|
| 124  | 0.5  | 2.85  | .80  |
| 126  | 1.0  | 4.23  | .80  |
| 127  | 2.0  | 6.13  | .95  |
| 125  | 3.0  | 9.09  | 1.10 |
| 123  | 4.0  | 10.57 | 1.53 |
| 40   | 5.0  | 11.78 | 1.37 |
| 120  | 6.0  | 13.88 | 1.53 |
| 121  | 8.0  | 18.11 | BRS  |
| 122  | 10.0 | 22.31 | BRS  |
| 189  | 12.0 | 23.30 | BRS  |

### AUTO TRANSFORMERS

| Ref. | VA (Watts) | TAPS               | £     | P&P  |
|------|------------|--------------------|-------|------|
| 113  | 20         | 0-115-210-240V     | 2.01  | .59  |
| 64   | 75         | 0-115-210-240V     | 3.51  | .80  |
| 4    | 150        | 0-115-210-220-240V | 4.98  | .80  |
| 66   | 300        | ..                 | 7.03  | .95  |
| 67   | 500        | ..                 | 10.76 | 1.37 |
| 84   | 1000       | ..                 | 16.51 | 1.73 |
| 93   | 1500       | ..                 | 21.87 | BRS  |
| 95   | 2000       | ..                 | 29.22 | BRS  |
| 73   | 3000       | ..                 | 42.37 | BRS  |

### SCREENED MINIATURES

| Ref. | mA       | Volts            | £    | P&P |
|------|----------|------------------|------|-----|
| 238  | 200      | 3-0-3            | .86  | .46 |
| 212  | 1A, 1A   | 0-6, 0-6         | 2.22 | .65 |
| 13   | 100      | 9-0-9            | 1.79 | .32 |
| 235  | 330, 330 | 0-9, 0-9         | 1.89 | .32 |
| 207  | 500, 500 | 0-8-9, 0-8-9     | 2.32 | .59 |
| 208  | 1A, 1A   | 0-8-9, 0-8-9     | 3.53 | .65 |
| 236  | 200, 200 | 0-15, 0-15       | 1.79 | .32 |
| 214  | 300, 300 | 0-20, 0-20       | 2.33 | .65 |
| 221  | 700 (DC) | *20-12-0-12-20   | 2.74 | .65 |
| 206  | 1A, 1A   | 0-15-20, 0-15-20 | 4.17 | .80 |
| 203  | 500, 500 | 0-15-27, 0-15-27 | 3.62 | .80 |
| 204  | 1A, 1A   | 0-15-27, 0-15-27 | 4.76 | .80 |
| S112 | 500      | 0-12-15-20-24-30 | 2.27 | .65 |

### CASED AUTO. TRANSFORMERS

| 240V cable input. USA 2-pin outlets | Ref.   | VA        | TAPS      | £ | P&P |
|-------------------------------------|--------|-----------|-----------|---|-----|
| 20VA                                | £3.78  | P&P 80p   | Ref. 113W |   |     |
| 75VA                                | £5.51  | P&P 95p   | Ref. 64W  |   |     |
| 150VA                               | £7.33  | P&P 95p   | Ref. 4W   |   |     |
| 300VA                               | £10.81 | P&P £1.15 | Ref. 66W  |   |     |
| 500VA                               | £12.62 | P&P £1.37 | Ref. 67W  |   |     |
| 750VA                               | £16.80 | P&P £1.53 | Ref. 83W  |   |     |
| 1000VA                              | £21.15 | OA        | Ref. 84W  |   |     |
| 2000VA                              | £33.02 | OA        | Ref. 95W  |   |     |

| HIGH QUALITY MODULES VAT 12 1/2%  | £      |
|-----------------------------------|--------|
| 5 watt RMS Amplifier              | £2.95  |
| 10 watt RMS Amplifier             | £3.25  |
| 25 watt RMS Amplifier             | £4.35  |
| Pre-Amp for 3.5-10w               | £6.70  |
| Pre-Amp for 25w                   | £13.75 |
| Power Supplies for 3.5-10w        | £1.30  |
| Power Supplies for 25w            | £3.75  |
| Transformer for 5.10w             | £2.30  |
| Transformer for 25w (tone module) | £2.90  |
| P&P Amps/Pre-Amps/Power Supplies  | 18p    |
| P&P Transformers                  | 58p    |

### BRIDGE RECTIFIERS

|      |      |       |
|------|------|-------|
| 200v | 2A   | 45p   |
| 400v | 2A   | 55p   |
| 200v | 4A   | 65p   |
| 400v | 4A   | 80p   |
| 400v | 6A   | £1.00 |
| 500v | 10A* | £2.35 |

P&P 15p. VAT 12 1/2% \*VAT 8%

### METERS

|            |        |
|------------|--------|
| AV08       | £61.09 |
| AV071      | £25.10 |
| AV0MM5     | £20.94 |
| WEE MEGGER | £51.05 |
| AVO TT169  | £26.00 |
| U4315      | £13.00 |

Includes steel carry case in-circuits transistor tester Avo Cases and Accessories P&P £1.25. VAT 8%

### TI MINI-MULTIMETER

DC-1000V. AC-1000V AC/DC-1000Q/V DC-100mA. Res — 150K Bargain at £5.30 VAT 8% P&P 45p

### STEREO F.M. TUNER

4 Pre-selected stations Switched AFC Supply 20-35v 90Ma Max. £20.45. P&P 25p. VAT 12 1/2%

### MAGNETIC TO CERAMIC CARTRIDGE CONVERTER

Operating Voltage 20/45v ONLY £2.85 P&P 18p VAT 12 1/2%

### STEREO 30

Complete chassis, inc. 7+7w r.m.s. amps, pre-amp, power supply, front panel, knobs (needs mains trans.). £16.25. Mains trans. £2.45. Teak veneered cab. £3.65. P&P 88p. VAT 12 1/2%.

### POWER UNITS

CC12-05. 3, 4.5, 7.5, 9, 12v 500mA: £4.08 STABILISED 3, 6, 7.5, 9v at 400mA: £5.95 3300. 6, 7.5, 9v at 300mA plugs direct into 13A socket: £2.85

P&P 48p. VAT 12 1/2%.

### ANTEX SOLDERING IRONS

15W £3.46, 18W £3.46, 25W £3.20 Soldering iron-kit £4.93 Stand for above £1.45. P&P 32p. VAT 8%.

PLEASE ADD VAT AFTER P&P ELECTROSIL AND SEMICONDUCTOR STOCKISTS, AUDIO ACCESSORIES & BARGAIN PAKS. CALLERS WELCOME (MON-FRI.) OR SEND STAMP FOR LISTS PRICES CORRECT AT 9/2/77

# Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ


TELEPHONE: 01-488 3316/8

NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.

WW—046 FOR FURTHER DETAILS
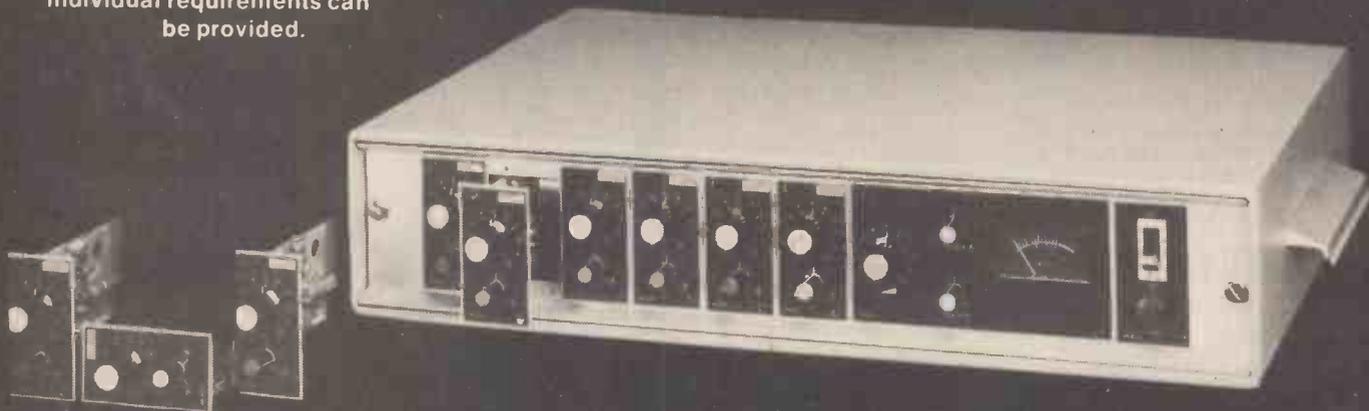
# 'Wenden' range modular amplifiers

A range of communications amplifiers having power ratings from 15 to 200 watts, plug-in input facilities ensure individual requirements can be provided.



Manufacturers of sound systems and electronics

Station Road, Wenden  
Saffron Walden  
Essex CB11 4LG  
Saffron Walden  
(0799) 40888



3% Measuring Accuracy  
Stabilised Power Supplies  
10 MHz Dual Trace  
10 mV Sensitivity

## SCOPEX 4D10A



Now YOU can afford the Best at

**£175**  
UK ex VAT




Scopex Instruments Limited, Pixmore Industrial Estate, Pixmore Avenue, Letchworth, Herts. SG6 1JJ Letchworth 72771 (STD 046 26)

## 30x30 WATT AMPLIFIER KIT

Specially designed by RT-VC for the experienced constructor, this kit comes complete in every detail. Same facilities as Viscount IV amplifier. Chassis is ready punched; drilled and formed Cabinet is finished in teak veneer. Black fascia and easy-to-handle aluminium knobs. **£29.00**  
Output 30+30 watts rms, 60+60 peak.

+ p & p £2.10

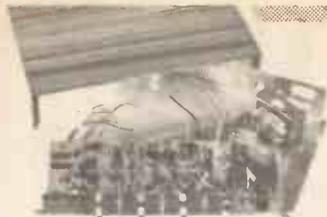


FANTASTIC SAVING
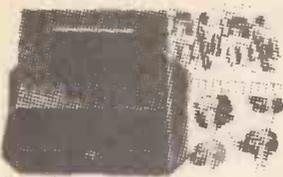
## NEW! sinclair I.C 20, 20 WATTS STEREO AMPLIFIER KIT WITH PZ 20 POWER UNIT

A build-it-yourself stereo power amplifier with latest integrated circuitry. 10W RMS per channel output, full short-circuit and overheat protection. **£5.95** OUR PRICE  
+ p & p £1

Complete with PZ20 Power Supply **LIST £14.50**



## 4x4 STEREO AMP KIT £14.50 P&P £2.00

For the experienced constructor who wants to design his own stereo, kit includes all necessary components including constructors manual. Plus pair of easy to build 4 watt speakers in kit form, with teak simulate finish cabinets 12"x9"x5" approx.

## DIY SPEAKER KITS

### EASY-TO-BUILD WITH ENCLOSURE

Specially designed by RT-VC for cost-conscious hi-fi enthusiasts, these kits incorporate two teak-simulate enclosures, two EMI 13"x8" (approx.) woofers, two tweeters and a pair of matching cross-overs. Easily constructed, using a few basic tools. Supplied complete with an easy-to-follow circuit diagram, and crossover components. Input 15 watts rms. 30 watts peak, each unit. **£25.50** PER PAIR  
Cabinet size 20"x11"x9 1/2" (approx.) + p & p £5.50



## 20x20 WATT STEREO AMPLIFIER

**£29.90**  
+ p & p £2.10



Superb Viscount IV unit in teak-finished cabinet. Silver fascia with aluminium rotary controls and pushbuttons, red mains indicator and stereo jack socket. Function switch for mic, magnetic and crystal pick-ups, tape, tuner, and auxiliary. Rear panel features two mains outlets, DIN speaker and input sockets, plus fuse. 20 + 20 watts rms, 40 + 40 watts peak.

## HOW YOU CAN SAVE

**SYSTEM 1B** For only £80, you get the 20+20 watt Viscount IV amplifier, a pair of our 12-watt-rms Duo Type IIb matched speakers; a BSR MP 60 type deck complete with magnetic cartridge, de luxe plinth **£80.00** and cover. + p & p £6.50

**SYSTEM 2** Comprising our 20+20 watt Viscount IV amplifier: a pair of our large Duo Type III matching speakers which handle 20watts rms each, and a BSR MP 60 type deck with magnetic cartridge, **£92.00** de luxe plinth and cover. + p & p £7.60

Carnage surcharge to Scotland: System 1B £2.50, System 2 £5.00

**SPEAKERS** Two models- Duo IIb, teak veneer, 12 watts rms, 24 watts peak, 18 1/2" x 13 1/2" x 7 1/4" approx. **£34** PER PAIR  
+ p & p £6.50

Duo III, 20 watts rms, 40 watts peak, 27" x 13" x 11 1/2" approx. **£52** PER PAIR  
+ p & p £7.50



**TURNTABLE** Popular BSR MP 60 type, complete with magnetic cartridge, diamond stylus, and de luxe plinth and cover. **£29.00**  
+ p & p £4.50



## 15-WATT KIT IN CHASSIS FORM

**£17.00** PER STEREO  
£3.40 P & P PAIR

When you are looking for a good speaker, why not build your own from this kit. It's the unit which we supply with the above enclosures. Size 13"x8" (approx.) woofer, (EMI) tweeter, and matching crossover. Power handling capacity 15 watts rms. 30 watts peak.

## 'COMPACT' FOR TOP VALUE

How about this for incredible bookshelf value from RT-VC! A pair of high efficiency units for only £7.50 - just what you need for low-power amplifiers. These infinite baffle enclosures come to you ready mitred and professionally finished. Each cabinet measures 12"x9"x5" (approx.) deep, and is in wood simulate. Complete with two 8" (approx.) speakers for max. **£7.50** per pair  
power handling of 7 watts. + p & p £1.70

## BSR TURN-TABLES

BSR MP60 TYPE  
Single play record player (Chassis form) less cartridge **£15.95**  
Cartridges to suit above P & P £2.00  
ACOS MAGNETIC STEREO... **£4.95**  
CERAMIC STEREO... **£1.95**  
BSR automatic record player deck (Chassis form) with cueing device and stereo ceramic head **£9.95**  
P & P £2.00



## CAR RADIO KIT



**MOTOR TOP 10 AWARD**

Complete with speaker, baffle and fixing strip. The Tourist IV for the experienced constructor only. The Tourist IV has five push buttons, four medium band and one for long wave band. The tuning scale is illuminated and attractive small aluminium control knobs are used for manual tuning and volume control. The modern style fascia has been designed to blend with most car interiors and the finished radio will slot into a standard car radio aperture. Size approx 7" x 2" x 4 1/4" Power Supply Nominal 12 volts positive or negative earth (altered internally) Power Output 4 watts into 4 ohms. **£12.50**  
+ p & p £1.50



## 35-WATT DISCO AMP

Here's the mono unit you need to start off with. Gives you a good solid 35 watts rms, 70 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble **£27.50**  
controls and master volume. + p & p £1.50



## PORTABLE DISCO CONSOLE with built-in pre-amplifiers

Here's the big-value portable disco console from RT-VC! It features a pair of BSR MP 60 type auto-return, single-play professional series record decks. Plus all the controls and features you need to give fabulous disco performances. Simply **£64.00**  
connects into your existing slave or external amplifier. + p & p £6.50



## 70 & 100 WATT DISCO AMPS

Brilliantly styled for easy disco performance! Sloping fascia, so that you can use the controls without fuss or bother. Brushed aluminium fascia and rotary controls. Five smooth-acting, vertically mounted slide controls - master volume, tape level, mic level, deck level. PLUS INTER-DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre-fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level 70 watts rms, 140 watts peak output. All the big features as on the 70-watt disco amplifier, but with a massive 100 watts rms, 200 watts peak output power.


**70 WATT £49.00**  
+ p & p £3.00  
**100 WATT £65.00**  
+ p & p £4



Special offer to personal shoppers only
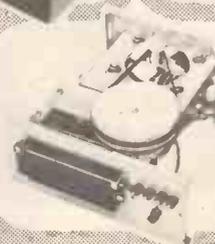
## PYE STEREO GRAM CHASSIS

Complete ready to install-Wave bands L, M, VHF STEREO, VHF MONO. Controls for tuning volume, balance, bass and treble. Power output 7 watts R.M.S. per channel 14 watts peak into 8 ohms. 2 x 8" approx chassis speakers and BSR C141 auto record player deck. **£35.00**



**BSR T145 8-TRACK CARTRIDGE PLAYER MECHANISM**  
Requires some attention. Complete with built in pre-amp, A.C. 240V **£6.95**  
+ p & p £1.50

**SPECIAL OFFER**

## ALL PRICES INC. VAT. AT 12 1/2%

GOODS NOT DESPATCHED OUTSIDE UK  
All items subject to availability. Price correct at 1.3.77 and subject to change without notice  
We are unable to show all our products, so please Send stamped addressed envelope for our fully descriptive catalogue and any further information.

**DO NOT SEND CARD**  
Just write your order giving your credit card number



**21E HIGH STREET, ACTON, LONDON W3 6NG**  
**323 EDGWARE ROAD, LONDON W2**  
Personal Shoppers EDGWARE ROAD 9.30am-5.30pm. Half day Thurs.  
ACTON: Mail Order only. No callers

# ELECTRO-TECH COMPONENTS LTD


315, 317, 364 EDGWARE ROAD, LONDON W2  
 TEL: 01-723 5667 & 01-402 5580

Shops and mail order dept (mail to 364) open 9 to 6 Mon. to Sat. inc.  
 Prices include VAT. Carr./p. & p. quoted U.K. only

ACCESS & BARCLAY accepted. Minimum order £5 otherwise C.W.O. For credit on approved accounts invoicing costs necessitate minimum order of £20

## FANS

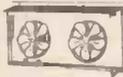**DUAL EXTRACTOR FAN.** 240v, 50 Hz. Two thick stack shaded pole motors make this a highly efficient unit producing a powerful airflow. Mounted in heavy steel frame each has five element 6 1/2" blades. Size 22 1/2" x 14" x 5 1/2" deep. **£10.95.** carr. **£2.75.**



**SINGLE FAN** with motor similar to above. Very useful in home and workshop. Remember last summer. Keep cool this year. **Only £3.95.** p&p. **85p.**

## PROGRAMME TIMERS

Magnetic Devices Ltd. Synchronous 230V 50Hz motor geared down to 1 rev. per 8 hours. Drives shaft mounting three cams, each of which actuates an on/off micro-switch with 10 amp contacts. Any switch can be set to remain on from 4 to 8 hrs. Push-on connections. Overall size 4 1/2" x 4 1/2" x 3 3/4" **£4.75** plus 85p p. & p. Ideal for switching on and off radios and lights as burglar deterrent in unoccupied premises.

Smiths 200/250V, synchronous motor geared down to 40 r.p.m. Size 2 1/2" x 1 1/2" x 1 1/2" **£2.25** each plus 25p p. & p. 4 or more **£1.50** each plus 70p p. & p. per pack of 4.

Midgley Harmer Ltd. 200/250V, synchronous motor geared to 1 rev. per 7 1/2 mins. All dimensions 2 1/4" x 1 1/2" x 1 1/2" **£1.50** each plus 25p p. & p. 4 or more **£1.00** each plus 48p p. & p. per pack of 4.

## ROTARY STUD SWITCH

PLESSEY. 30 way, 2 bank Single pole. Contacts 1 amp. 240V. AC/DC. .005" res. Break before make. Stop infinitely adjustable allowing for any desired arc of travel. Ideal for instrument and model switching. Size 2 1/2" dia. overall x 2 1/2" deep plus 1 1/2" x 1/2" dia. spindle. **£2.25.** p&p. 20p. 5 off **£11.95** each. p&p. **40p.**



## UNI-SELECTOR

240V. AC or OC operation. Split 30 way double bank contacts. Overall size approx. 2 1/2" dia. x 2 1/2" deep. Brand new. Bargain at **£4.50.** p&p. **65p.**



## TRANSFORMERS

**DAVENST AUTO.** 2KVA continuously rated. Tapped for any voltage from 5-260v. in steps of 5v. With an isolated winding of 0.5-10v. at 8 1/2 amps. This transformer is an extremely useful buy. Push-on connections. Size 8" x 5 1/2" x 6 1/2". A really robust job. Bargain at **£23.50.** Carr. **£3.00.** 750VA. continuously rated. Tapped as above with 0.5-10V. isolated winding of 5 amps. Same connections. Size 4 1/2" x 3 1/4" x 4 1/2". Also bargain at **£12.50.** Carr. **£2.00.**


**GRESHAM** Pri. 10-D-200-220-240v. Sec. tapped 0-3 1/2-7-11-32-33-34-35 at 10 amps. to give 24 useful voltages **£6.00** carr. **£1.00.**

**TORRIDAL** Pri. 15-0-210-240v. Sec. 140v. at 25 m/a., 31v. at 500 m/a.e.t., 10v. at 1.9 amps. Scr. Size 3 1/2" dia. x 1 1/2". **£3.95** p. & p. **30p.**

**MINIATURE** Pri. 240V. Sec. 6v. at 1/2 amp. Size 1 1/4" x 1 1/2" x 1 1/4". Ideal as power supply base for models, radios, cassettes, etc. **£1.50** ea. p. & p. 20p. 6 off **£10.00** ea. p. & p. 45p  
**GOODYEAR** 1KV $\frac{1}{2}$  automatic transformer. 0-110-115-120-200-220-240v. Fully shrouded. Terminal block connections. Size 5" x 4 1/4" x 5 1/2" plus block. cannot be bettered at **£13.95.** p. & p. **£1.50.**
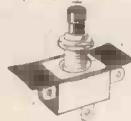
## ARROW SWITCH

Press on/off. Single hole fixing. SP/ST. Size 1 1/2" x 1 1/2". Stud extends 1/2". Rated 1 amp. at 240V. 2 1/2 amps. at 125V. Price for 5 (min. qty.) **£1.75** p. & p. 30p. 10 or more 30p each p. & p. **40p.**



## REED SWITCHES

Glass encaps N/O contacts. Glass length 1 1/2". dia. 1/8". overall length 1 1/2". 10 off **£1.00.** p. & p. 25p. 100 off **£8.00.** p. & p. free. 1000 off **£68.00.** p. & p. free.



**SYLVANIA SWITCH**  
 Complete with magnet contacts M/C. 3 amp vacuum sealed. 1 1/4" x 1 1/4" dia.  
 10 for **£2.50**  
 50 for **£11.00**  
 100 for **£18.00**  
 Plus 50p p. & p. any quantity

## MOTORS

**CITENCO F.H.P.** reversible geared motor. 220/240v. 50 Hz. 1 Ph. cap. start. cont. rating. 0.2 amps. Gearing 144/1. final drive 19 rms. Torque 14.5 Kg/cm. 5/16" dia. shaft. Size 6" x 3 1/2" dia. plus base. Brand new. Limited quantity. **£16.50.** p&p. **£1.50.**



**CRUYDON 1/10 HP.** reversible motor 230/240v. 50 Hz. 1 Ph. Cap. start. cont. rating. 1500 rpm. 1/2" dia. shaft. Size 8" x 4 1/4" dia. plus base. New **£17.50.** carr. **£3.00.**

**1/8 HP.** reversible geared motor. 220/240v. 50 Hz. 1 Ph. cap. start. cont. rating. Gearing 5:1. Final drive approx 280 rpm. 1/2" dia. shaft. Size 14" inc. gearbox x 5 1/2" dia. plus cap. and base. New. Robust. **£23.95.** carr. **£3.00.**



**ACADEX shaded pole motor.** Open frame 230v. 50 Hz. Double ended 5/32" dia. spindle, each 1 1/4" long. Ideal for fans, models, etc. Size 1 1/4" x 2 1/4" x 1 1/4" deep plus spindles. **£1.50** p&p. **45p.**

**CRUZET shaded pole motor.** Open frame 115/230v. 50 Hz. 1425 rpm. Size 2 1/2" x 2 1/4" x 1 1/2" deep plus 1/4" long x 5/32" dia. spindle **£3.60** p&p. **62p.**


**PAPST motors.** Noted for advanced design and superb construction. Rotating diecast outer body acts as flywheel and eliminates wobble and flutter. 50 Hz. capacitor start. MODEL HSK 32.80-6/12. 220v. Dual speed tape deck motor 500/1000 rpm. 12 mm. drive shaft gives tape speeds of 9.53/19.05 cm/sec. (3 1/2"/7 1/2" ins/sec.) respectively. Size approx. 5 1/2" dia. x 3 1/2" plus 1 1/2" spindle. **£16.80.** p&p. **£1.10.**



MODEL RO 32.65-4. Dual voltage 125/250v. Size 2 1/4" x 3 1/4". Spindle 5/16" dia. **£12.50.** p&p. **£1.10.**  
 MODEL HSK 20.25-2. Basically 42v. but can be operated from mains with additional capacitor. A magnificent small motor. Size 1 1/2" x 2 1/4". spindle 5/16" dia. **£5.95.** p&p. **45p.**
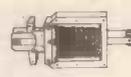
## SOLENOIDS 240V A.C.

**MAGNETIC DEVICES LTD.** (No. 1) has 20lb pull for 50% duty. 1 1/2" travel, push or pull. Shackle both ends. Size 1 1/2" wide x 3 1/2" high x 4" long plus 3" arm travel. **£6.75** plus p. & p. **£1.00.** (No. 2) has 2lb pull continuously rated 1/2" travel. Size 1 1/2" x 1 1/2" x 2 1/4" plus travel. **£1.80.** 30p p. & p.



**PYE ETHER LTD** Thrust operates through spring loaded hinged lever giving a 1lb. pull or push. Complete with mounting bracket and push on connections. Size overall inc. bracket 2 1/2" w x 3" h x 3 1/2" long. **£2.25** P&P **45p.**

## RELAYS

Octal base 2 C/O 6 amp contacts. Following voltages 12V a.c. 48V d.c. 110 d.c. 230 a.c., all **£1.25** each plus base 15p postage and packing 15p. 11-pin 3 C/O 6 amp contacts, following voltages 115 a.c. 48 d.c. 24 d.c. all at **£1.50** each, base 15p plus 15p p. & p.



## LOGIC OP/AMP POWER SUPPLIES

B. Davis Electronics Limited quantity only.

| Type No.       | SPS 40      | SPS 5       | SPS 7W         | SPS 9(1)       |
|----------------|-------------|-------------|----------------|----------------|
| Supply Form    | Card Form   | logic       | Fully enclosed | Fully enclosed |
| Op. volts      | 4.5/5.0 (3) | 4.5/5.0 (3) | 12/18          | 4.5/6.0 (3)    |
| Ampl. Max.     | 1.25        | 2.0         | 0.5 (2)        | 10.0           |
| Ripple (4)     | 0.5         | 0.5         | 0.15           | 0.1            |
| Regulation (5) | 0.02        | 0.02        | 0.005          | 0.02           |
| Price          | £14.00      | £26.00      | £28.00         | £51.00         |
| Carr/p. & p.   | 60p         | £1.20       | £1.20          | £1.20          |

Notes (1) Programmable. (2) Each rail. (3) Zero volts protection. (4) Pk-Pk M/V. All have stability of 10,000:1, current limiting re-entrant and output impedance of 0.25Ω at 100 KHz.

## MINIATURE LAMPS


| Type | Size (Dia.) | Volt/Curr. | Type | Size (Dia.) | Volt/Curr.  |
|------|-------------|------------|------|-------------|-------------|
| A    | 3MM         | 5-6V 60 MA | D    | 3MM         | 2.5V 360 MA |
| B    | 4MM         | 4V 250 MA  | E    | 4MM         | 5-6 60 MA   |
|      |             | 5V 50 MA   |      |             | 6V 200 MA   |
|      |             | 12V 40 MA  |      |             | 6-3 200 MA  |
|      |             | 12V 100 MA |      |             | 14V 40 MA   |
|      |             | 14V 75 MA  | F    | 4MM         | 2.7V 60 MA  |
|      |             | 28V 40 MA  |      |             | 12V 160 MA  |
| C    | 5MM         | 28V 40 MA  |      |             | 14V 80 MA   |
| G    |             |            |      |             |             |

Small telephone jack type 6 or 24V

Price Types A-F **£4.00** for 25, 50 and upwards **13p** each. Type G **45p** each. p. & p. **20p** per order.
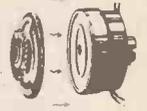
## BENDIX MAGNETIC CLUTCH

Superb example of electro-mechanics. Main body in two sections, coil section fixed with 3/16" sleeve; drive section rotating on outer perimeter. Uniting plate has 3/16" ID bearing concentric with main section and 18-tooth cog wheel. Extremely powerful transmission. 24V O/C 240 m/a. **£3.75** plus p. & p. **40p.**



## PCB EDGE CONNECTOR

CINCH. .15" pitch. 27 way but designed with adjustable finger endplates enabling connector to be cut and used in any length desired. 50p p. & p. 15p. 10 off **£4.00** p. & p. **30p.**

## MEM LIMIT SWITCH

Snap action 5 amps at 240/410 A.C. size base. 3 1/2" x 1 1/2" x 1 1/2" plus heavy duty roller plunger 1 1/2" ext. or 1" when compressed. Very robust for troubleless operation. weather proof. Price **£2.20** plus p. & p. **40p.**

## JABSCO (ITT) ROTARY PUMP

Self-priming. Works from electric drill or suitably powered motor for 1/4" drive shaft. 1/2" hose connections. Throughput 2/3 galls. per min. at 2400 rpm. Dozens of uses in home and workshop. Giveaway at **£2.75.** p&p. **20p.**



WW-088 FOR FURTHER DETAILS

# Strobes, Tachos, Meters, Generators and Telecommunications Test Equipment

E.B. import and distribute high-grade products from World-renowned British & Overseas Manufacturers.

## NEW FUNCTION GENERATORS!



G430 provides Sine-wave (0-10Vrms) and Square-wave (0-20V p-p) from 600Ω, continuously variable, via 4-position 0-60dB, push-button operated step attenuator. Frequency range 1Hz to 1MHz.

**£95** Send for details of our complete range



## NEW PULSE GENERATOR Model 70 (illustrated above)

Compact, low-cost pulse and square-wave generator, featuring:

- P.R.F. 4Hz to 400kHz, gated or free-running.
- O/P 10v peak from 50Ω, also synchron. O/P.
- Pulse width 1 μSec to 100mSec.
- Delay 1 μSec to 100mSec.
- Pulse mark / space inversion.
- TTL/CMOS HI LO gating facility.

**£94**

## NEW WIDE-RANGE MULTIMETER UM-11

Features 38-colour-coded ranges with high input impedance.



- d.c. Volts, 150mV to 1500V f.s.d.
- at 100kΩ/V a.c. Volts, 1.5V to 1500V f.s.d. at 31.6kΩ/V.
- d.c. Current, 10μA to 15A.
- a.c. Current 15A.

Other star features include mirror-scale, rugged taut band suspension, dB scale, diode and fuse protection.

Supplied complete with test-leads and leather carrying case.

**£39.50**



See inside back cover for details of ICE Super range of multi-meters!

Add 8% VAT to all prices shown. Carriage extra details on request



**ELECTRONIC BROKERS LIMITED (New Products Division)**  
 49-53 Pancras Road, London NW1 2QB. Tel: 01-837 7781

Callers welcome—Monday to Friday 9 a.m. to 5 p.m.

WW-106 FOR FURTHER DETAILS

# BENTLEY ACOUSTIC CORPORATION LTD.

7A GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX. Tel. 6743

ALL PRICES SHOWN INCLUDE V.A.T. AT 12 1/2 %

|       |      |       |      |        |      |         |      |           |      |        |      |        |      |
|-------|------|-------|------|--------|------|---------|------|-----------|------|--------|------|--------|------|
| 0A2   | 0.85 | 688G  | 0.35 | 6L6GC  | 0.70 | 12A7T   | 0.34 | 30PL12    | 0.40 | B719   | 0.39 | E8L21  | 2.00 |
| 0B2   | 0.40 | 68A6  | 0.40 | 6L7(M) | 0.60 | 12A06   | 0.50 | 30PL13    | 1.00 | B729   | 0.79 | E8C52  | 1.00 |
| 0C2   | 0.55 | 68C8  | 0.90 | 6L12   | 0.39 | 12A07   | 0.34 | 30PL14    | 1.29 | BL63   | 2.00 | E8C53  | 1.00 |
| 1A3   | 0.60 | 68E6  | 0.40 | 6L18   | 0.60 | 12A08   | 0.60 | 30PL15    | 1.00 | CL33   | 1.75 | E8C54  | 1.00 |
| 1A5GT | 0.55 | 68G6  | 1.00 | 6L19   | 2.00 | 12A0X   | 0.34 | 35A3      | 0.75 | CV6    | 0.60 | E8C86  | 0.84 |
| 1A7GT | 0.60 | 68H6  | 0.70 | 6L12   | 0.40 | 12A7    | 1.00 | 35C5      | 0.80 | CV63   | 1.00 | E8C91  | 0.60 |
| 1B3GT | 0.55 | 68J6  | 0.65 | 6L20   | 0.60 | 12A6    | 0.50 | 35D5      | 0.90 | CV988  | 0.25 | E8C92  | 0.55 |
| 1C2   | 1.00 | 68K7A | 0.85 | 6N7GT  | 0.70 | 12B6E   | 0.55 | 35L8GT    | 0.80 | CV1C   | 1.00 | E8C32  | 1.00 |
| 1D5   | 0.75 | 68Q5  | 0.34 | 6P12   | 0.40 | 12B7H   | 0.55 | 35W4      | 0.55 | CV31   | 0.70 | E8C33  | 2.00 |
| 1G6   | 1.00 | 68Q7A | 0.60 | 6P15   | 0.34 | 12B7Y   | 0.85 | 35Z3      | 0.80 | D1     | 0.50 | E8C35  | 2.00 |
| 1H5GT | 0.80 | 68R7  | 1.00 | 6Q7G   | 0.50 | 12E1    | 3.50 | 35Z4GT    | 0.70 | D63    | 0.30 | E8C40  | 0.90 |
| 1L4   | 0.25 | 68R8  | 1.25 | 6Q7GT  | 0.50 | 12J5GT  | 0.40 | 35Z5GT    | 0.80 | DAC32  | 0.80 | E8C81  | 0.34 |
| 1LD5  | 0.70 | 68S7  | 1.70 | 6R7M   | 0.65 | 12J7GT  | 0.70 | 42        | 1.50 | DAF91  | 0.35 | E8C82  | 0.34 |
| 1LN5  | 0.70 | 68W6  | 1.70 | 6R7G   | 0.70 | 12K5    | 1.50 | 50B5      | 0.95 | DAF96  | 0.60 | E8C83  | 0.34 |
| 1NSGT | 0.75 | 68W7  | 0.65 | 6R7(M) | 1.00 | 12K7GT  | 0.50 | 50C5      | 0.70 | DC90   | 0.70 | E8C84  | 0.35 |
| 1R5   | 0.50 | 68X2  | 0.20 | 6S47   | 0.35 | 12K8    | 0.75 | 50C8G     | 1.20 | D14    | 0.80 | E8C85  | 0.39 |
| 1S4   | 0.40 | 68Y7  | 0.38 | 6S7GT  | 0.75 | 12Q7GT  | 0.50 | 50EH5     | 0.85 | DF33   | 0.75 | E8C86  | 1.25 |
| 1S5   | 0.35 | 68Z6  | 0.60 | 6S7G   | 0.50 | 12S47GT | 0.75 | 50L8GT    | 1.00 | DF91   | 0.30 | E8C88  | 0.51 |
| 1T4   | 0.30 | 6C4   | 0.40 | 6SH7   | 0.55 | 12S7G   | 0.50 | 66K0      | 0.52 | DF92   | 0.60 | E8C91  | 0.35 |
| 1U4   | 0.70 | 6C5G  | 0.60 | 6S17   | 0.60 | 12SCT   | 0.55 | 72        | 0.70 | DH63   | 0.50 | E8C189 | 0.80 |
| 1U5   | 0.85 | 6C6   | 0.45 | 6S7GT  | 0.55 | 12SH7   | 0.50 | 77        | 0.45 | DH76   | 0.50 | E8C804 | 0.79 |
| 2D21  | 0.55 | 6C9   | 2.00 | 6S07   | 0.80 | 12S17   | 0.60 | 85A2      | 0.75 | DH77   | 0.80 | E8C85  | 0.39 |
| 2GK5  | 0.75 | 6C10  | 0.71 | 6U4GT  | 0.80 | 12S7GT  | 0.50 | 85A3      | 0.75 | DH81   | 0.80 | E8C80  | 0.50 |
| 2K2   | 0.70 | 6C8A  | 0.50 | 6U7G   | 0.55 | 12SN7GT | 0.75 | 90CV      | 2.80 | DK32   | 0.60 | E8C82  | 0.50 |
| 3A4   | 0.55 | 6C12  | 0.40 | 608    | 0.50 | 12S0CT  | 0.80 | 108C1     | 0.40 | DK40   | 0.70 | E8C86  | 0.80 |
| 3B7   | 0.55 | 6C8G  | 1.60 | 6V6G   | 0.30 | 12S0VGT | 0.80 | 108B2     | 1.00 | DK91   | 0.50 | E8C21  | 2.00 |
| 3D6   | 0.40 | 6C8A  | 0.90 | 6V6GT  | 1.00 | 12SR7   | 0.75 | 150C2     | 0.85 | DK92   | 1.00 | E8C35  | 1.60 |
| 3Q4   | 0.80 | 6C15  | 0.75 | 6K4    | 0.45 | 12I7    | 0.34 | 2155G     | 0.60 | DK96   | 0.70 | E8C92  | 0.70 |
| 3Q5GT | 0.70 | 6C8A  | 0.95 | 6XS7   | 0.45 | 1A57    | 1.00 | 302       | 1.20 | DL63   | 0.70 | E8C81  | 0.40 |
| 3A2   | 0.45 | 6C17  | 1.00 | 6Y6G   | 0.95 | 1L      | 1.25 | 303       | 1.20 | DL82   | 0.30 | E8C83  | 0.50 |
| 3V4   | 0.80 | 6C65  | 0.45 | 6Y7G   | 1.25 | 19A05   | 0.65 | 305       | 1.20 | DL92   | 0.45 | E8C84  | 0.50 |
| 4C86  | 0.75 | 6C5   | 0.90 | 7A7    | 1.00 | 19B6G   | 1.00 | 807       | 1.10 | DL94   | 0.80 | E8C80  | 0.45 |
| 5C8G  | 0.75 | 6D3   | 0.75 | 7B6    | 0.80 | 19G6    | 6.50 | 956       | 0.50 | DL96   | 0.80 | E8C82  | 0.50 |
| 5R4GY | 1.00 | 6D7   | 0.90 | 7B7    | 0.80 | 19H1    | 4.80 | 1025      | 2.50 | DM70   | 0.80 | E8C83  | 0.74 |
| 5T4   | 1.00 | 6D15A | 0.85 | 7D6    | 2.00 | 19Y3    | 4.40 | 1821      | 1.00 | DM71   | 1.75 | E8C84  | 0.65 |
| 5U4G  | 0.60 | 6E6   | 0.85 | 7F8    | 2.00 | 20D1    | 0.70 | 5702      | 1.20 | DW4300 | 1.15 | E8C85  | 1.75 |
| 5V4G  | 0.60 | 6E5   | 1.00 | 7H7    | 0.80 | 20D4    | 2.50 | 5763      | 1.65 | DY876  | 0.35 | E8C86  | 0.64 |
| 5Y3GT | 0.55 | 6F1   | 0.80 | 7R7    | 2.00 | 20F2    | 0.85 | 6057      | 1.00 | DY802  | 0.50 | E8C22  | 1.00 |
| 5Z3   | 0.60 | 6F8G  | 0.60 | 7V7    | 2.00 | 20L1    | 1.20 | 6960      | 1.00 | E800C  | 2.50 | E8C20  | 1.00 |
| 5Z4G  | 0.48 | 6F2   | 0.50 | 7Z0    | 1.00 | 20Y1    | 1.00 | 6967      | 1.00 | E80CF  | 1.00 | E8C21  | 1.00 |
| 5Z4GT | 0.55 | 6F13  | 0.90 | 7Z4    | 0.80 | 20P3    | 1.00 | 6146      | 3.50 | E80F   | 2.20 | E8C22  | 1.00 |
| 630L2 | 0.79 | 6F14  | 0.90 | 82D    | 0.50 | 20P4    | 0.84 | 6463      | 2.00 | E83F   | 1.60 | E8C23  | 1.00 |
| 6A8G  | 1.40 | 6F15  | 0.85 | 8D8    | 0.45 | 20P5    | 1.50 | 7025      | 1.50 | E88CC  | 1.20 | E8C20  | 1.00 |
| 6A8G  | 1.40 | 6F16  | 0.75 | 98W6   | 0.90 | 25A6G   | 0.70 | 7193      | 0.60 | E92CC  | 0.70 | E8C23  | 1.25 |
| 6A8G  | 0.35 | 6F18  | 0.60 | 9D7    | 0.70 | 25L6G   | 0.70 | 7475      | 1.20 | E180CC | 0.80 | E8C24  | 0.70 |
| 6A8G  | 0.60 | 6F23  | 0.65 | 9U8    | 0.45 | 25Y5    | 0.80 | 9002      | 0.55 | E180F  | 1.15 | E8C25  | 0.75 |
| 6A8G  | 0.70 | 6F24  | 0.80 | 10C2   | 0.70 | 25Z4G   | 0.50 | 9006      | 0.45 | E182CC | 3.00 | E8C26  | 0.75 |
| 6A1J  | 0.70 | 6F25  | 1.00 | 10C14  | 0.45 | 25Z5    | 0.75 | 9134      | 1.00 | E188CC | 2.50 | E8C27  | 0.90 |
| 6A8J  | 0.40 | 6F26  | 0.36 | 10D1   | 0.85 | 25Z6G   | 0.80 | A2134     | 3.00 | E280F  | 0.50 | E8C28  | 1.20 |
| 6A8J  | 0.45 | 6F28  | 0.74 | 10D7   | 0.80 | 28D7    | 2.00 | A3042     | 6.00 | E1148  | 0.80 | E8C29  | 0.40 |
| 6A8J  | 0.70 | 6F32  | 0.70 | 10F1   | 0.87 | 30A5    | 0.75 | AC2PEN    | 1.80 | E450   | 0.40 | E8C30  | 0.90 |
| 6A8J  | 0.40 | 6C6G  | 0.80 | 10F9   | 0.85 | 30C1    | 0.80 | AC2PENDD  | 1.80 | E476   | 3.00 | E8C31  | 0.90 |
| 6A8J  | 0.40 | 6C6H  | 0.80 | 10F18  | 0.85 | 30C15   | 0.77 | 1.00      | 1.00 | E48C30 | 0.40 | E8C32  | 0.90 |
| 6A8J  | 0.40 | 6C6K  | 0.75 | 10L14  | 0.45 | 30C17   | 0.77 | AC6/PEN   | 0.80 | E4C91  | 0.55 | E8C33  | 0.90 |
| 6A8J  | 0.40 | 6C6L  | 0.70 | 10L11  | 0.75 | 30F5    | 0.70 | AC/P4     | 1.50 | E4F42  | 0.70 | E8C34  | 0.40 |
| 6A8J  | 0.40 | 6C6M  | 0.70 | 10L12  | 0.45 | 30L1    | 0.39 | AC/PEN(T) | 1.80 | E4F801 | 0.75 | E8C35  | 0.40 |
| 6A8J  | 0.40 | 6C6N  | 0.70 | 10L13  | 0.45 | 30L15   | 0.75 | 1.00      | 1.00 | E4830  | 0.30 | E8C36  | 1.75 |
| 6A8J  | 0.40 | 6C6P  | 0.70 | 10L14  | 0.45 | 30L17   | 0.70 | AC/TH1    | 1.00 | E891   | 0.20 | E8C37  | 0.40 |
| 6A8J  | 0.40 | 6C6Q  | 0.70 | 10L15  | 0.45 | 30P4    | 0.90 | AL50      | 1.20 | E8C41  | 0.75 | E8C38  | 0.40 |
| 6A8J  | 0.40 | 6C6R  | 0.70 | 10L16  | 0.45 | 30P12   | 0.74 | ARP3      | 0.60 | E8C42  | 0.45 | E8C39  | 0.40 |
| 6A8J  | 0.40 | 6C6S  | 0.70 | 10L17  | 0.45 | 30P19   | 0.74 | ATP4      | 0.50 | E8C43  | 0.45 | E8C40  | 0.40 |
| 6A8J  | 0.40 | 6C6T  | 0.70 | 10L18  | 0.45 | 30P4    | 0.90 | AZ1       | 0.50 | E8C44  | 0.50 | E8C41  | 0.50 |
| 6A8J  | 0.40 | 6C6U  | 0.70 | 10L19  | 0.45 | 30P16   | 0.37 | AZ21      | 0.60 | E8C45  | 0.40 | E8C42  | 0.50 |
| 6A8J  | 0.40 | 6C6V  | 0.70 | 10L20  | 0.45 | 30P18   | 0.50 | AZ41      | 0.50 | E8C46  | 0.45 | E8C43  | 0.50 |
| 6A8J  | 0.40 | 6C6W  | 0.70 | 10L21  | 0.45 | 30P11   | 1.00 | B36       | 0.75 | E8C47  | 0.40 | E8C44  | 0.50 |

|        |      |        |      |          |      |        |      |        |      |       |      |        |      |       |      |
|--------|------|--------|------|----------|------|--------|------|--------|------|-------|------|--------|------|-------|------|
| EL83   | 0.70 | N709   | 0.34 | PY83     | 0.50 | U17    | 1.00 | X719   | 0.40 | AD162 | 0.53 | BYZ15  | 2.03 | OC41  | 0.58 |
| EL84   | 0.54 | PE1    | 0.60 | PY88     | 0.50 | U18/20 | 1.50 | Z145   | 0.67 | AF102 | 1.04 | CG12E  | 0.23 | OC42  | 0.73 |
| EL86   | 0.60 | PAB80  | 0.45 | PY301    | 0.50 | U19    | 4.00 | Z152   | 0.23 | AF106 | 0.58 | CG64H  | 0.23 | OC43  | 1.37 |
| EL90   | 0.68 | PC86   | 0.62 | PY500    | 1.20 | U22    | 0.85 | Z329   | 0.70 | AF114 | 0.30 | FSY11A | 0.26 | OC44  | 0.12 |
| EL95   | 0.67 | PC88   | 0.62 | PY500A   | 1.20 | U25    | 0.71 | Z719   | 0.29 | AF115 | 0.30 | GSY41A | 0.26 | OC45  | 0.13 |
| EL360  | 1.80 | PC92   | 0.55 | PY800    | 0.50 | U26    | 0.80 | Z729   | 0.45 | AF117 | 0.23 | FD4    | 0.38 | OC46  | 0.18 |
| EL506  | 1.20 | PC95   | 1.00 | PY801    | 0.50 | U31    | 0.50 | Z749   | 0.65 | AF121 | 0.35 | GD5    | 0.32 | OC65  | 1.31 |
| EL509  | 2.50 | PC97   | 0.75 | PZ30     | 1.50 | U33    | 1.75 | Z759   | 5.85 | AF123 | 0.35 | GF124  | 0.23 | OC70  | 0.14 |
| EM80   | 0.55 | PC90   | 0.40 | QP21     | 1.10 | U35    | 1.75 |        |      | AF125 | 0.50 | GD8    | 0.23 | OC71  | 0.13 |
| EM81   | 0.60 | PC84   | 0.39 | QQV03/10 | U37  | 2.00   |      |        |      | AF139 | 0.76 | GD9    | 0.23 | OC72  | 0.13 |
| EM83   | 0.60 | PC85   | 0.47 |          | U45  | 1.20   |      |        |      | AF178 | 0.79 | GD11   | 0.23 | OC74  | 0.26 |
| EM84   | 0.45 | PC88   | 0.61 | QS75/20  | 1.00 | U47    | 0.71 | IN124A | 0.61 | AF180 | 0.56 | GD12   | 0.23 | OC75  | 0.13 |
| EM85   | 1.20 | PC89   | 0.49 | QS85/10  | 1.00 | U49    | 0.60 | IN474A | 0.16 | AF186 | 0.64 | GD14   | 0.38 | OC76  | 0.18 |
| EM87   | 1.10 | PC89   | 0.52 | QS150/15 | 1.00 | U50    | 0.55 | IN4852 | 0.58 | AF239 | 0.44 | GD15   | 0.47 | OC77  | 0.32 |
| EM88   | 0.84 | PC88   | 0.85 | QV03/12  | 1.85 | U52    | 0.60 | 2N404  | 0.21 | AS27  | 0.50 | GD16   | 0.23 | OC78  | 0.18 |
| EM89   | 0.84 | PC86   | 0.70 | QV04/7   | 3.00 | U56    | 0.70 | 2N966  | 0.61 | AS28  | 0.38 | GET113 | 0.23 | OC78D | 0.18 |
| EM91   | 0.50 | PC87   | 0.45 | QV06/20  | 3.50 | U78    | 0.45 | 2N1756 | 0.58 | AS29  | 0.58 | GET118 | 0.23 | OC79  | 0.47 |
| EM93   | 0.60 | PC82   | 0.45 | R11      | 1.00 | U81    | 0.80 | 2N2147 | 0.99 | BA102 | 0.53 | GET119 | 0.30 | OC81  | 0.13 |
| EM94   | 0.45 | PC84   | 0.70 | R16      | 2.00 | U90    | 0.52 | 2N2297 | 0.26 | BA115 | 0.16 | GET133 | 0.44 | OC81D | 0.13 |
| EM95   | 0.70 | PC87   | 0.57 | R17      | 1.00 | U91    | 0.50 | 2N2369 | 0.16 | BA116 | 0.21 | GET137 | 0.50 | OC82  | 0.13 |
| EM96/7 | 0.37 | PC87   | 0.77 | R18      | 1.20 | U91    | 0.50 | 2N2613 | 0.45 | BA129 | 0.14 | GET172 | 1.11 | OC82D | 0.13 |
| EM98   | 0.40 | PCF20  | 1.20 | R19      | 0.75 | U92    | 0.40 | 2N3053 | 0.38 | BA130 | 0.12 | GET173 | 0.18 | OC83  | 0.23 |
| EM99   | 0.35 | PCF201 | 1.00 | R20      | 0.60 | U93    | 0.50 | 2N3121 | 2.90 | BA153 | 0.18 | GET182 | 0.58 | OC84  | 0.28 |
| EM100  | 0.35 | PCF800 | 0.77 | R52      | 0.48 | U94    | 0.50 | 2N3703 | 0.23 | BCY10 | 0.53 | GET187 | 0.26 | OC123 | 0.26 |
| EM101  | 0.35 | PCF801 | 0.49 | RK34     | 1.00 | U281   | 0.75 | 2N3709 | 0.64 | BCY12 | 0.58 | GET189 | 0.26 | OC139 | 0.50 |
| EM102  |      |        |      |          |      |        |      |        |      |       |      |        |      |       |      |

# Stirling Sound

**DO AWAY WITH YOUR V.A.T. AND POSTAGE PROBLEMS**


**and provide a speedier direct-from-the-factory delivery service**

Why worry about working out V.A.T. (12½% on £4.87 plus 8% on £3.39 plus 85p for p/p, or should it be 54p)? We do it for you. Just send your order with the advertised prices — we do the rest. If a number of items together cost us less to post, we credit you the difference. Buy at our shop in person and we deduct the postage charges automatically. This is not all. Now you send your orders direct to our factory (see below) and we send back your order directly from there — real time saving that! AND STIRLING SOUND PRICES REMAIN KEENLY COMPETITIVE ALL THE TIME maintaining the lead we took in 1959 by being first to sell bargain component packs. We've come a long way since then — with our exciting programme for the seventies we're going even further!

**YOU PAY THE PRICE YOU READ AND NOTHING MORE**

subject only to (very rarely) there being a printing error or really vicious price rise in production costs. You're SAFE when you buy from Stirling Sound — the business that has grown on really understanding customers' needs and interests.

**POWER AMPS FROM 4 TO 100 WATTS R.M.S.**

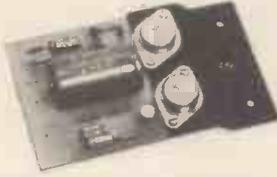

**SS.105**  
4 watts R.M.S. into 3 ohms using 12V supply. Ideal for use in in-car entertainment. Size — 89 x 51 x 19mm. **£3.49**

**S.110**  
Similar in size and design to SS.105, this QV module delivers 10 watts R.M.S. into 4 ohms using a 24V supply, e.g. SS.324. **£4.05**

**SS.120**  
Using a 34 volt supply, such as SS.334, this amplifier will deliver 20 watts into a 4 ohm load. Same dimensions as above. **£4.61**

**SS.140**  
Mk. 3 version. Delivers 40 watts R.M.S. into 4 ohms from a 45 volt supply such as the SS.345. Designed specially for long and heavy work. **£4.99**


**SS.1100**  
100 watts R.M.S. into 4Ω using 70 volt supply. Ideal P.A. or disco unit. With o/p capacitor and heatsink type mounting flange. **£10.43**  
Heat Sink for above **£1.39.**

**SS.1100 WITH SS.370**  
By buying the SS.1100 (£10.43), the heatsink (£1.39) and SS.370 (£14.63) (Total £26.45) **YOU PAY ONLY £24.20** — a genuine saving of £2.25 on a power amplifier assembly that is superb value by any standards. **ORDER NOW WHILE OFFER LASTS.**

**SAVE £2.25**

**STIRLING SOUND PRE-AMP/TONE CONTROL UNITS**

**UNIT ONE**  
Combined pre-amp with active tone control circuits. 200mV output for 50 mV in. Runs on 10 to 16V supply. Treble ±15 dB at 10KHz, Bass ±15 dB at 30Hz. Stereo Balance, vol., treble and bass controls. **£9.00**

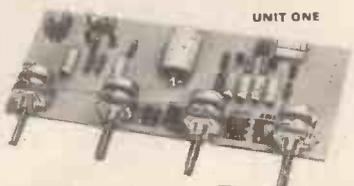

**SS.100**  
Active tone control, bass and treble. **£3.00**

**SS.101**  
Pre-amp for ceramic cartridges, etc., passive tone control circuit shown in data supplied. **£2.33**

**SS.102 STEREO PRE-AMP**  
R.L.A.A. corrected for mag., plus tape, radio, etc. **£4.04**

**UNIT TWO**  
Similar to UNIT ONE but for mag. inputs 1mV-5mV. Adaptable to ceramic. Excellent x-channel and S/N ratings. **£12.43**

**TODAY'S FINEST VALUES IN POWER SUPPLIES**

Of the eight models available in this wide ranging series, all except SS.312 have a low voltage (13-15V) outlet. The range is calculated to meet the majority of users' needs.

|               |        |              |                  |  |               |
|---------------|--------|--------------|------------------|--|---------------|
| <b>SS.312</b> | 12V/1A | <b>£6.35</b> | <b>SS.345</b>    | 45V/2A   | <b>£9.98</b>  |
| <b>SS.318</b> | 18V/1A | <b>£6.54</b> | <b>SS.350</b>    | 50V/2A   | <b>£10.36</b> |
| <b>SS.324</b> | 24V/1A | <b>£7.27</b> | <b>SS.370</b>    | 70/2A  | <b>£14.53</b> |
| <b>SS.334</b> | 34V/2A | <b>£8.31</b> | <b>SS.310/50</b> | Output variable from 10 to 50V/2A; built-in short circuit protection | <b>£16.69</b> |

**SS.300 POWER STABILISING UNIT** for adding to units. Adjustable from 10V/2A to 50V/8A. Anti-short protected. **£5.02**

**ORDERING COULD NOT BE SIMPLER**

The advertised price includes V.A.T. and postage charges, so pay the price you read and make cheques payable to Bi-Pre-Pak Ltd. Every effort is made to ensure correctness of information at time of going to press

# Stirling Sound

Send your order to: **STIRLING SOUND, Dept. WW.5**  
**37 VANGUARD WAY, SHOE BURNNESS, ESSEX**  
Telephone (0702-28) 5543

Shop customers as usual to:  
**220-224 West Rd., Westcliff-on-Sea, Essex, S50 9DF**

# BI-PRE-PAK COMPONENT BARGAIN SALE

**PRICES INCLUDE V.A.T., POSTAGE IN U.K. NO EXTRAS POSTAGE DEDUCTED FOR PERSONAL SHOPPERS**

**100 TRANSISTORS** mixed types, PNP germanium; PNP and NPN silicon. AF and RF types. Unmarked and untested. Good yield. **£1.35**

**100 I.C.s** mixed types, marked. Ideal for experimenters, etc. Limited supplies **£1.35**

**40 WIRE WOUND RESISTORS** mixed values and wattages **85p**

**40 POTENTIOMETERS** various values and types, some switched, pre-set, etc. **£1.35**

**100 DIODES** silicon, equal to 1N914, 1N4148, etc. unsorted, untested. **75p**

**100 DIODES**, germanium, glass and metal types, untested **75p**

**10 EHT RECTIFIER STICKS** for colour TV triplers. 12 KV working. Type CSD11 BXP **65p**

**100 ZENER DIODES** 400mW. Mixed voltages. Untested **75p**

**PCB** Printed circuit board, plain copper laminate, approx. 250 sq. ins. in about 7 pieces **£1.35**

**2 LIGHT ACTIVATED S.C.R.s** 50V/1.6A. Type LF9. With full data and 14 project details **£1.35**

**PUSH BUTTON TUNER ASSEMBLIES** for FM, TV, and Radio varicap tuners. Brand new by famous maker.  
4-button assemblies **£1.95**  
7-button assemblies **£2.80**

**EX-C.P.O. INSTRUMENT CASES**  
Heavy gauge stove enamelled grey aluminium. Internal racking and panels usable as heatsinks, etc. Ideal for P.A., power supplies, oscilloscopes, instruments, etc.  
**BRAND NEW, BOXED**  
SIZE 'A' — 14" x 15" x 6" deep **£8.00**  
SIZE 'B' — 17" x 16" x 12" deep **£10.00**

**50 ONLY SIGNAL GENERATORS** (Med. Wave & I.F.), pocket size. **£5.25**

**POCKET SIGNAL INJECTOR** to trace fault, in A.F., R.F., T.V., etc. **£2.75**

**WHEN ORDERING**

Make cheques, money orders payable to Bi-Pre-Pak Ltd. **THERE IS NOTHING EXTRA TO ADD FOR POSTAGE & V.A.T. IN U.K.** Any small variation in V.A.T. will be absorbed by us or credited to you accordingly. Above offers open for as long as stocks last

**BI-PRE-PAK LTD.** 220-224 WEST ROAD WESTCLIFF-ON-SEA, ESSEX S50 9DF  
Telephone Southend (0702) 46344  
Personal shoppers welcome



## Better instruments. Better service.

We have established a nationwide network of approved service organisations to deal with the repair and maintenance of our instruments. Every repair is backed by a full 12 month guarantee. Here's where to find them.

**ENGLAND** London Instrument Repair Centre, Acton Lane, Chiswick, London W4 5HJ. Trade Reception: Cunnington Street. Tel: 01-995 9212  
London Instrument Repair Centre, Archcliffe Road, Dover, Kent. Tel: Dover (0304) 202620  
Farnell International Instruments Ltd., Sandbeck Way, Wetherby, West Yorkshire LS22 4DH. Tel: Wetherby (0937) 3541  
T.E.R. Instrumentmnts Ltd., Peel Lane, Astley, Manchester M29 7JH. Tel: Atherton (05234) 2275 or 5611  
Midlands Instrument Repair Centre, Thorn Automation Ltd., Armitage Road, Rugeley, Staffs. Tel: Rugeley (08894) 5151

**SCOTLAND** Falcon Electronics, 92 High Street, Johnstone, Scotland. Tel: Johnstone (0505) 23377

**WALES** Electro Services, 25 Chepstow Road, Newport, Gwent NPT 8BX. Tel: Newport (0633) 211243



The manufacturers' joint service organisation.

WW-105 FOR FURTHER DETAILS

# SINTEL for MEMORIES — MPUs — PCBs

Components from  
Leading Manufacturers only

## A NEW RANGE OF SINTEL INDUSTRIAL MODULE KITS

Using only the highest quality components — Fibreglass roller-tinned PCBs — ICs and Displays direct from "Blue chip" Manufacturers.  
**KITS FOR TTL LATCHED COUNTER MODULES**  
Each kit includes a set of displays (0.5" Red LED type TIL321/FND507) and two PCBs, one each per digit of 7447, 7475, and 7490, plus brackets, resistors capacitors, a single in-line plug and socket, nuts, screws, washers, instructions, etc. Sockets are NOT included and we recommend that you order Soldercon Pins separately (112 for a 2 digit module, 224 for a 4 digit module and 336 for a 6 digit module).  
Each module consists of one vertical PCB holding the displays, fixed by two brackets to a horizontal PCB which holds the remaining components.  
Full Kit for 2 digit TTL Counter with Latch: Order as ..... **526-412 £12.50**  
Full Kit for 4 digit TTL Counter with Latch: Order as ..... **657-412 £22.50**  
Full Kit for 6 digit TTL Counter with Latch: Order as ..... **721-412 £32.50**



**KIT FOR SINGLE PCB CMOS COUNTER MODULE WITH LATCH**  
A complete kit for building a 2 digit single PCB CMOS Counter Module with Latch includes PCB 2 x TIL322 or FND500 2 x 4511 1 x 4518. Rs socket pins etc. Size h 67mm w 71mm d 18mm  
Order as **142-269. £8.60**

**SETS OF JUMBO DISPLAYS WITH DISPLAY HOLDING PCB**  
Each set consists of the appropriate number of 0.5" red LED displays (either common anode TIL321/FND507s or common cathode TIL322/FND500s) and a display holding PCB.  
OPTIONS: PCBs wired for multiplexing or non-multiplexing, clock format or counter format.

| TYPE<br>Non-Multiplexed | COMMON ANODE |        | COMMON CATHODE |        |
|-------------------------|--------------|--------|----------------|--------|
|                         | Part No.     | Price  | Part No.       | Price  |
| 2 digit Counter         | 574-822      | £3.37  | 446-822        | £2.97  |
| 4 digit Counter         | 777-822      | £6.63  | 128-322        | £5.83  |
| 6 digit Counter         | 684-822      | £9.89  | 271-822        | £8.69  |
| <b>Multiplexed</b>      |              |        |                |        |
| 4 digit Clock           | 301-822      | £6.86  | 262-822        | £5.86  |
| 6 digit Clock           | 417-822      | £10.15 | 452-822        | £8.95  |
| 8 digit Counter         | 119-822      | £13.09 | 515-822        | £11.49 |

## DATABOOKS

|   |        |
|---|--------|
| RCA CMOS and Linear IC Combined Databook                          | £6.70  |
| National Semiconductor 7400 series TTL Databook, c. 200 pages     | £3.45  |
| TTL Pin-Out Card Index  | £2.95  |
| Intel Memory Design Handbook, C.280 pages                         | £5.20  |
| Intel 8080 Microcomputer System Users Manual, c. 220 pages        | £5.25  |
| Motorola McMOS Databook (Vol. 5 Series B), c. 500 pages           | £3.50  |
| Motorola M6800 Micro Application Manual, c. 650 pages             | £12.95 |
| Motorola M6800 Programming Manual, c. 200 pages                   | £5.35  |
| Motorola Booklet introducing Microprocessors                      | £1.80  |
| National SC/MP IntroKit Users Manual                              | £0.75  |
| National SC/MP Technical Description                              | £1.95  |
| Zilog Z80-CPU Technical Manual (NEW)                              | £5.80  |
| Zilog Z80-CTC Product Specification (NEW)                         | £0.80  |
| Zilog Z80-P10 Technical Manual (NEW)                              | £3.30  |
| <b>DATASHEETS on Microprocessors, etc. (Usually Xerox Copies)</b> |        |
| Intel 8080 12 bit   | £0.75  |
| National SC/MP 8 bit  | £0.75  |
| Signetics 2650 8 bit, Low cost                                    | £0.75  |
| TMS 8080  | £0.75  |
| 9131 Memory   | £0.75  |
| RCA CDP 1802 8 bit CMOS   | £0.75  |
| Zilog Z80 (enhanced 8080)   | £0.75  |
| Motog MC 6800   | £0.75  |
| TMS 5501 for 8080   | £0.75  |

Our offices are at Link Property, 209 Cowley Road, Oxford, but please do not use this as a postal address.

**FAST SERVICE.** We guarantee that Telephone Orders for goods in stock, received by 4.15 p.m. (Mon.-Fri.) will be despatched on the same day by 1st Class Post (some heavy items by parcel post) and our stocking is good. Private customers should telephone and pay by giving their Access or Barclaycard number, with a minimum order value £5. Official orders, no minimum. All prices valid until 31st August, 1977.

**ORDERS:** C.W.O. add VAT @ 8% + 25p p&p. TELEPHONE and CREDIT (Invoice) Orders add VAT @ 8% + 50p p&p and please see "FAST SERVICE". EXPORT Orders welcome, no VAT but add 10% (Europe), 15% (Overseas) for Air Mail p&p. For Export postage rates on heavy items — contact us first.

SEND YOUR SINTEL  
ORDER TO PO BOX 75C, OXFORD  
Tel. 0865 49791



**LOW COST IC SOCKETS**  
Soldercon Pins are the ideal low cost method of providing sockets for TTL, CMOS, Displays and ICs. Simply cut off the lengths you need, solder into board and snap off the connecting carrier. A single purchase of Soldercon Pins gives you any socket you may need, and at low prices. 50p per strip of 100 pins, 1,000 for £4, 3,000 for £10.50.

## HIGH QUALITY KITS



**ACK  
£27.80**

**ATTRACTIVE SIX DIGIT ALARM CLOCK KIT**  
Six red 0.5" digits • White case • Touch switch snooze • Battery backup • Crystal timebase plus other features • Size h. 40mm, w. 205mm, d. 140mm • Complete less mains cable, plug and battery.  
Order as **ACK + BBK + XTK** ..... **£34.33**  
Available without crystal control and battery backup, which can be added later.  
Order as **ACK** ..... **£27.80**

**FOUR DIGIT MANTLEPIECE OR OFFICE CLOCK**  
Four bright green 0.5" digits • White Case • Battery backup • Crystal control • Size h. 40mm, w. 154mm, d. 85mm • Complete less mains cable, plug and battery.  
Order as **GCK + GBBK + XTK** ..... **£19.65**  
Available without crystal control and battery backup.  
Order as **GCK** ..... **£14.40**

**SIX DIGIT CAR CLOCK WITH INDEPENDENT JOURNEY-TIMER**  
Crystal controlled • Shows time or elapsed time in hrs. mins. secs • Runs off car 12v supply • Nine push buttons for Start-Stop-Reset, selecting display to show time or elapsed time • All controls functional irrespective of display mode • Size h. 40mm, w. 205mm, d. 140mm  
Order as **GCK** ..... **£42.00**

**FOUR DIGIT CAR CLOCK**  
Four red 0.5" digits • White case • Battery backup • Crystal control • Suitable for all 12v negative earth cars • Size h. 40mm, w. 154mm, d. 85mm • Complete less battery.  
Order as **AUT-CK** ..... **£17.85**


**50Hz CRYSTAL TIMEBASE KIT**  
Use to improve accuracy of your digital clock • As a 50Hz source in a clock with battery backup • Accurate to within a few seconds a month • Size h. 14mm, w. 64mm, d. 49mm.  
Order as **XTK** ..... **£6.28**
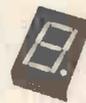
## DISPLAYS

These Jumbo LED displays take no more current than 0.3" types. All our common cathode (C.C.) digits can be used in place of any other C.C. display (DL704, D1750, MAN3640, etc.) since they are all electrically identical (but may have different pin-outs). Similarly our common anode digits may be used in place of any other C.A. types (DL707, DL747, RS/Qoram 586/699, etc.)



**FND500 C.C.**  
**£1.30**  
Red 0.5" by Fairchild



**TIL321 C.A.** £1.50  
**TIL322 C.C.** £1.49  
Red 0.5" by 11

**5LTD1 £5.80**

A very attractive four digit display with large 0.5" green digits, AM/PM and colon. Phosphor diode (vacuum fluorescent).



## COMPONENTS Send for Catalogue

| CLOCK CHIPS       | MPUs                | CMOS       |             |
|-------------------|---------------------|------------|-------------|
| AYS1202 3.10      | 6800 24.84          | Mainly RCA | CD4032 1.02 |
| AYS1224 3.50      | SC/MP CPU           |            | CD4033 1.44 |
| MK50253 5.60      | ISPB4/5000          |            | CD4034 1.97 |
|                   | Z80 14.50           |            | CD4035 1.22 |
| <b>FLAT CABLE</b> |                     |            | CD4036 3.29 |
| 20w 1m 1.00       |                     |            | CD4037 3.85 |
| 10m for 8.00      |                     |            | CD4038 1.10 |
|                   | <b>MPU KIT</b>      |            | CD4039 3.20 |
|                   | INTRO KIT           |            | CD4040 1.11 |
|                   | ISPBK/200E          |            | CD4041 0.86 |
|                   |                     |            | CD4042 0.86 |
| <b>VEROCASES</b>  |                     |            | CD4043 1.01 |
| 751410J 3.36      |                     |            | CD4044 0.96 |
| 751411D 4.10      |                     |            | CD4045 1.45 |
| 751237J 2.50      |                     |            | CD4046 1.37 |
| 751238D 3.00      |                     |            | CD4048 0.58 |
| 751239K 3.58      |                     |            | CD4049 0.98 |
|                   | <b>TRANSFORMERS</b> |            | CD4050 1.24 |
|                   | LEDTRF 1.95         |            | CD4051 0.94 |
|                   | SLTRF 1.95          |            | CD4052 0.94 |
|                   |                     |            | CD4053 1.36 |
|                   | <b>SWITCHES</b>     |            | CD4054 1.20 |
|                   | Slide switches      |            | CD4055 1.36 |
|                   | SL-PK (5) 0.65      |            | CD4056 1.36 |
|                   | Push Button         |            | CD4057 3.85 |
|                   | PB-PK (5) 0.75      |            | CD4058 4.93 |
|                   | DIL switch 2.10     |            | CD4059 1.15 |
|                   | (8way)              |            | CD4060 1.13 |
|                   |                     |            | CD4061 1.13 |
|                   |                     |            | CD4062 0.23 |
|                   |                     |            | CD4063 0.83 |
|                   |                     |            | CD4064 1.78 |
|                   |                     |            | CD4065 0.23 |
|                   |                     |            | CD4066 0.23 |
|                   |                     |            | CD4067 0.23 |
|                   |                     |            | CD4068 0.23 |
|                   |                     |            | CD4069 0.23 |
|                   |                     |            | CD4070 0.23 |
|                   |                     |            | CD4071 0.23 |
|                   |                     |            | CD4072 0.23 |
|                   |                     |            | CD4073 0.23 |
|                   |                     |            | CD4074 0.23 |
|                   |                     |            | CD4075 0.23 |
|                   |                     |            | CD4076 1.34 |
|                   |                     |            | CD4077 0.45 |
|                   |                     |            | CD4078 0.23 |
|                   |                     |            | CD4081 0.23 |
|                   |                     |            | CD4082 0.23 |
|                   |                     |            | CD4083 0.74 |
|                   |                     |            | CD4084 0.74 |
|                   |                     |            | CD4085 1.60 |
|                   |                     |            | CD4086 0.92 |
|                   |                     |            | CD4087 1.94 |
|                   |                     |            | CD4088 1.08 |
|                   |                     |            | CD4089 1.13 |
|                   |                     |            | CD4090 1.99 |
|                   |                     |            | CD4091 1.24 |
|                   |                     |            | CD4092 1.41 |
|                   |                     |            | CD4093 1.72 |
|                   |                     |            | CD4094 2.84 |
|                   |                     |            | CD4095 3.24 |
|                   |                     |            | CD4096 1.40 |
|                   |                     |            | CD4097 1.25 |
|                   |                     |            | CD4098 1.19 |
|                   |                     |            | CD4099 1.64 |
|                   |                     |            | CD4100 1.39 |
|                   |                     |            | CD4101 0.90 |
|                   |                     |            | CD4102 0.90 |
|                   |                     |            | CD4103 1.22 |
|                   |                     |            | CD4104 4.68 |
|                   |                     |            | CD4105 8.05 |
|                   |                     |            | CD4106 0.23 |
|                   |                     |            | CD4107 0.23 |
|                   |                     |            | CD4108 0.23 |
|                   |                     |            | CD4200 0.23 |

## INJECTION AND COMPRESSION MOULDING TO YOUR REQUIREMENTS ALSO INDELIBLE PRINTING OF G.R.P. ALUMINIUM AND COATED PANELS. GLASS FIBRE CASES. D.M.C. OR S.M.C. GREY, BUT OTHER COLOURS BY ARRANGEMENT.

| SIZES            | BOX ALONE | WITH ADDITION* |
|------------------|-----------|----------------|
| 8" x 5 1/2" x 5" | £1.94     | £2.71          |
| 9" x 4" x 3"     | £1.30     | £2.07          |
| 6" x 4" x 4"     | £1.10     | £1.96          |
| 5" x 3" x 1 1/2" | £0.51     |                |
| 4" x 4" x 1 1/2" | £0.54     |                |

Plus VAT and carriage

WITH FRONT PANEL, INSIDE PANEL (BOTH ALUMINIUM) AND 4 RUBBER FEET

TRADE PRICES ON REQUEST

Polythene Bags to your requirement, Dept. DP

**THOMAS MAUGHAN & ASSOCIATES**  
(DEPT. AW)

CLARENCE MILL, BOLLINGTON, NR. MACCLESFIELD, CHESHIRE  
Tel: BOLLINGTON 74294

WW-049 FOR FURTHER DETAILS

ANY MAKE-UP OR  
COPY QUERIES  
CONTACT  
JOHN GIBBON  
01-261 8353

**CARAVAN / CAR CONNECTOR**



The famous Clanc connectors heavy cast body enclosing the electrical socket and plug — screw together cannot be pulled out or come out with vibration. Socket screw on cover keeps out dirt when caravan is not connected. Socket £2.50. Plug £2.85 or Socket fixed to solid angle iron (ready for mounting) £3.50.

**SCORE CURLY LEAD**

Water and oil proof terminating each end with 3 pin clamp plug. Length extended approx 10ft. Price £6.00 + 75p

**12v AUTOMATIC SWITCH**

It can sometimes be a problem to find your car or caravan in a big car park or caravan site after dark, so why not fit a light that will come on automatically when it gets dark. We are offering a kit for this comprises light sensitive switch 12v bulb and bulb holder in tubular casing with coloured lens with wiring diagram. Price £3.00 + 37½p + 20p + 2p. Main operation switch available £3.95.



**TAPE HEADS ETC.**



2 track record/playback 75p.  
4 track record/playback £1.10.  
Erase head 2 track 50p, 4 track 90p.  
M. metal shells and holders 65p each.  
2 track 1/4" head and 2 track erase head, schedule and fixed on mounting plate ready for tape £1.85.

**INDUCTION MOTORS**

230v mains operated — precision made as used in fans — record players — tape recorders — heaters, etc., etc. ½" stack (as illustrated) £1.35. ¾" stack £1.76. 1" stack £2.25.



**MOTORISED DISCO SWITCHES**

With six 10 amp changeover switches. Multi adjustable switches are rated at 10 amp each so a total of 2000w's can be controlled and this would provide a magnificent display. For mains operating £4.25 post & VAT paid. Otto 9 switch £4.95 post & VAT paid. OTTO BUT 12 SWITCH £5.75 POST & VAT PAID.



**DELAY SWITCH**



Mains operated — delay can be accurately set with pointers knob for periods of up to 2½ hrs. 2 contacts suitable to switch 10 amps — second contact opens few minutes after 1st contact 95p.

**UNISELECTORS**

These are pulse operated switches as used in automatic telephone switchboards etc. A 24v pulse moves the switch through one switch way all we have are of the 25 switch full wiper type the following sizes are in stock



|         |             |
|---------|-------------|
| 3 bank  | £4.80 + 37p |
| 4 bank  | £5.94 +     |
| 8 bank  | £9.72 +     |
| 12 bank | £12.96 +    |

|                |        |
|----------------|--------|
| 3 bank & Homer | £5.40  |
| 5 bank         | £7.02  |
| 10 bank        | £10.80 |


**BLOWER / FAN**



Centrifugal type blower/fans with rectangular outlets designed to fit into trunking for heat blowing etc., will also function as extractors. Main voltage motors — three sizes available small (overall size approx. 4½" x 4" x 4") £4.50 — medium (overall size 9" x 8" x 3" approx) £6.50 — large (overall size 12" x 12" x 10" approx) £13.50.

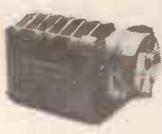**CENTRAL HEATING HEARTS**

Randal replacement in 3060 etc £8.75. HORTSMAN £6.30. SMITHS Controller 10/100 complete in wall mounting case £7.50.



**MAINS TRANSFORMER BARGAINS**

|             |        |       |                          |
|-------------|--------|-------|--------------------------|
| 20v         | ½ amp  | £1.25 | 10v 20v 30v 40v          |
| 18v         | 1 amp  | £1.55 | 250 watt loading £5.50   |
| 6.3v        | 2 amp  | £1.39 | 20 watt auto 115v £1.25  |
| 25v         | 1½ amp | £1.75 | 100 watt auto 115v £1.75 |
| 24v 2 amp   |        | £2.00 |                          |
| 50v 2 amp   |        | £4.50 |                          |
| 9v 1 amp    |        | £1.25 |                          |
| 8.5v-0.8 5v |        | £1.25 |                          |
| ½ amp       |        |       |                          |



**THERMOSTATS**

Refrigeration. As illustrated with 36" capillary £1.62. Limpet Stat. Must be mounted in close contact calibrated 90 - 180°F 15 amp contacts £1.62. Appliance Stat. Fix like a volume control — 15 amp contact 30" 80°F 85p. ditto but for high temps £1.25. Over Stat. With Serson and capillary 85p.

**THIS MONTH'S SNIP**

**HI-FI RECORD PLAYER**



Stereo 5 watts per channel. Russian made but guaranteed repairable. Travel damaged or test line rejects, in need of attention, consist of mains operated record desk — mounted in wooden plinth with super 10 watt amplifier. Controls are: "on/off", "Tape/phone", "mono/stereo", "Base", "Treb.", "Balance", "Volume".

We are offering these at price of record desk only so are a bargain not to be missed, only £8.75, post £2.00. Note cartridge and all spares are available at low prices

**WEE MEGGER**

A very Special Offer. Most famous testing instruments Made by Evershed & Vignol, a must for every electrical contractor and service man. In perfect going order having been thoroughly reconditioned for the G.P.O. Price £14.00 + £1.12 Post 80p 6p.



**LOW R.P.M. MOTORS**



Made by Crouzet — Smiths — SAIWA — Vennar and similar famous companies — all supplied ready for 230/240v 50Hz mains working, all £2.75 each. Following speeds in stock when preparing this advertisement.


|                  |                |                |
|------------------|----------------|----------------|
| 1 rev per day    | 6 revs per day | 1 rev per hour |
| 12 revs per hour | ½ rev per min  | 1 rev per min  |
| 2 rpm 1½ rpm     | 5 rpm 15 rpm   | 20 rpm 25 rpm  |
| 30 rpm           |                |                |

**REMEMBER 7.029**

We are still able to offer the electrical equivalent of this in 100 metre coils at a very special price of £10.26, carriage £2 50. Our remaining stock of this is 3 core and earth this is a little larger physically than twin and earth but if space limited then just remove the unwanted core before taking cable into small socket box. FREE Telephone line. If you are using the above cable for taking a supply to a shed or remote point then the third core can be used as a telephone line. For lighting we can offer 1.5mm Three core at £6.50, carriage £1 60.



**WAFER SWITCHES**

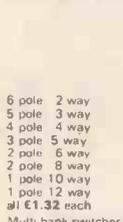

|                |                |                |
|----------------|----------------|----------------|
| 6 pole 2 way   | 12 pole 2 way  | 18 pole 2 way  |
| 5 pole 3 way   | 10 pole 3 way  | 15 pole 3 way  |
| 4 pole 4 way   | 8 pole 4 way   | 12 pole 4 way  |
| 3 pole 5 way   | 6 pole 5 way   | 9 pole 5 way   |
| 2 pole 6 way   | 4 pole 6 way   | 6 pole 6 way   |
| 2 pole 8 way   | 4 pole 8 way   | 6 pole 8 way   |
| 1 pole 10 way  | 4 pole 9 way   | 6 pole 9 way   |
| 1 pole 12 way  | 2 pole 10 way  | 3 pole 10 way  |
| all £1.32 each | all £2.41 each | all £3.12 each |

Multi bank switches up to 72 pole 2 way — to 12 pole 12 way, quickly made to special order.

**24-HOUR TIMERS**

VERMEN as illustrated with sun correction made for G.P.O. phone boxes uncut and perfect £2.25. 20 amp switching contacts. SMITHS timer heart similar to Autotest etc 2 13 amp on/off per 24 hrs. £4.15. TIMAC module, really miniature (approx. 2" cube) but with 2 15 amp on/off per 24 hrs. £4.50.

**MULLARD UNILEX**

A mains operated 4 + 4 stereo system. Railed one of the finest performers in the stereo field, this would make a wonderful gift for almost anyone, in easy-to-assemble modular form and complete with a pair of Goodmans speakers this should sell at about £30 — but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £14.00 including VAT and postage.



**TERMS**

Cash with order — delivery same day as order received. Prices includes VAT and carriage unless stated but orders under £6 must add 50p to off-set packing etc. BULK ENQUIRIES WELCOMED

**J. BULL (ELECTRICAL) LTD.**

(Dept. WW)  
103 TAMWORTH ROAD  
CROYDON CR9 1SG

**IT'S FREE!**

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived — often bargains which sell out before our advertisement can appear — it's an interesting list and it's free — just send S.A.E. Below are a few of the Bargains still available from previous issues.

Infra Red Receiver and transmitter. Again we believe to be a burglar alarm, these are two separate units each in a very neat metal box, size 6" x 3" x 3". One unit contains the projector the other contains the receiver. Both units have a lens system for focusing and receiving the infra red beam. These again have not been tampered with and appear to be new and unused so it is reasonable to expect them to be in working order but again we do not guarantee this. Price £12.50 + £1.00. Post £1.00 + 12½p

Bleepone. Capsule size 2" dia. for fitting into burglar alarms and similar applications — 3v operated. Price £1.25 + 10p. PP3/PP9 Replacement Mains Unit. Japanese made in plastic container with leads size 2" x 1½" x 1½", this is ideal to power a calculator or radio. It has a full wave rectified and smoothed output of 9 volts suitable for a loading of up to 100mA. Price £2.00 + 25p. Post 25p + 3p

Mullard Instrument Power Supplies. Fully smoothed and stabilised, we have two models, Ref. No. 88 9103 has an output of plus 12 volts and minus 12 volts, maximum loading 1 amp. 4 amp respectively. Input is for 50Hz and settings are adjustable in 5v steps from 105-120v and 210-240v, size approx 8½" x 5" x 3½", high, weight approx. 3½lbs, price £4.00 + 32p. Post £1.00 + 8p.

Ref. No. B 891006. This has an output of 6v positive and 6v negative with a current capacity of 600mA and 150mA respectively, input 50-60 cycles 220v or 235v plus or minus 10%. Size approx. 8½" x 5" x 2¾", high, weight approx. 3½lbs. Price £3.50 + 25p. Post £1.00 + 8p. Students Relay Parcel. 10 Multi contact 600 type relays all different coil values covering most experimenters needs. Total retail value approx £10 — yours for £3 plus 30p post.

BSR record auto-changer, current model of very high repute with a ceramic stereo cartridge £10.95 + £1 37 Post £1.00 + 12½p.

Fluorescent kit for 5ft. tubes. This is another exceptional bargain. It comprises polyester filled almost silent running 65w choke made by GEC, starter and holder, tube ends and very clips to hold the tube and wiring diagram etc. THIS MONTH'S SNIP at only £1.75 + 12p the lot + 50p + 4p post and packing. Just what sort of a bargain this is will be realised when you look at the new prices for chokes only the recommended list price of 65w is now over £3 50.

Car Plugs. These go in the cigar lighter socket. They have been out of stock for a long while but we are pleased to say they are once again in stock new price 40 + 4p

Self-adhesive paper discs ¼", ideal for making leads as you take them off or for providing quick insulation of soldered or twisted joints. Box of 5000 £1 + 8p + 20p + 2p.

Multi-core Cable, 7 cores each pvc insulated and colour coded, screened overall than with pvc outer covering. A miniature cable diameter approx ¼". Price 25p + 2p per metre, available in lengths up to 15 metres.

12v Mini immersion heater. Another must for your camping or picnic basket, this will make a cup of tea in a minute or two or warm the baby's food etc. Price £2.75 + 35p. Post 15p + 3p.

12v Motors made by Smiths as used in car heaters and similar purposes. Approx size 3" dia ½" long plus spindle approx. 1" x ¼" dia. If you want to make a heater or a cooling fan or even a 12v food mixer this may do the job — these are easily reversible and being series wound will work off AC through voltage dropper. Price £2.00 + 25p. Post 30p + 3p

Last time of these prices. In our January/February newsletter you will remember we offered a car starter kit that consisted of a heavy duty transformer and rectifiers to give 20 amp charging and starting current, which after a few minutes is enough to get most engines running even in very cold weather. We offered this at a special price of £8.50 and we repeat this offer but point out that the offer closes on April 30th after which the price will have to increase by 25%.

Instant Start Ballast for 8ft. tubes. Fortunately purchase this month enable us to offer this at a special price of £1.50 + 12p + 3p each (about half regular price). The ballast is made by a very famous company and is polyester filled so is quite quiet in operation. This is a heavy unit so unfortunately we cannot make any reduction of carriage charges to quantity buyers.

Instant Start Ballast for 5ft. tubes. Description is as for 8ft. ballast, price £1.50 + 12p + 3p. Coloured Tubes. We have quite a lot of these in stock at bargain prices. If you are needing any for the coming Jubilee celebrations then send for a list of types available.

Lamp Harnesses. With the jubilee celebrations not far off, many gardens will have to be lit with coloured lamps and to this end we are stocking waterproof lamp holder sets, 3 lengths, 12 lamp sets, 20 lamp sets and 40 lamp sets, prices at £8.00 + 72p, £12.75 + £1.08 and £22.50 + £1.60 respectively. Coloured bulbs for these are available, price 40p each. Alternatively if you want to make up your own harnesses then we have the lamp holders which screw on to the cable, the cable does not have to be prepared in any way. If you want to change the position of the lamp holder just unscrew and holes made by the points will reseat themselves. Price of the lamp holders, 10 for £2.50 + 20p + 40p + 4p.

Cable for lamp harnesses. Obviously you can't use any old cable for this, firstly the cores must be the right distance apart or the lamp holder spikes will not make contact and secondly often quite a high current is involved so a rubber based cable is used. We recommend 4mm twin for these harnesses and can supply them at a special bargain price £9 + 72p Post £1 60 + 12p. Spiked lamp holders 10 x £2.50 + 20p. Post 40p + 4p.

Telephone handsets. Ideal for this or other intercoms 50p + 4p. Post 40p + 3p. Circuit for bell ringing not requiring extra wires will be supplied if requested.

Extension Speaker Bargain. 8 ohm solidly made. Round cone which is a metric size but near enough equivalent to the popular 8" round — this speaker is a very fine performer and can truly be called hi-fi. Also it is housed in a well made teak veneered cabinet with back, price only £3.75 + 48p — actually you would have a job to buy or make the cabinet only for this price. So order early to avoid disappointment. If you cannot collect please add £1 + 12½p for post and packing. Plinth for B.S.R. Very nice looking wooden surround with hardboard base and motor board cut out for B.S.R. — one of our special bargains at 84p + 11p Post £1 + 12½p — plinths with covers also available at low prices but owing to breakage problem we cannot send these.

Posts with ¼" spindles min 1" long only 10p each. The following values in stock 5k, 10k, 50k, 100k, 250k, 500k, 1 meg. Min quantity 10 of a value. VAT 12%, post free.

Rechargeable Battery Units for Hand lamps. With ever increasing costs of dry batteries, hand lamps can be very expensive items. Many of the replacement dry batteries for instance cost over £1.00 each. We have a limited supply of Dac Nickel Cadmium rechargeable batteries to replace 12v or 6v dry batteries complete with chargers, all conveniently mounted on a panel. The panel will go into the battery compartment of most popular hand lamps with only a small modification if your hand lamp is 6v and all you have to do is to bring out a short lead terminated with a 2 pin plug for connecting to the mains for recharging. Price less than cost £3.50 + 44p. Post 30p + 3p.


Pressure Switch. Industrial type made by Satchwell. Their type PS, specification no. 421-2-209. Intended for high pressure lines and to be quickly adjustable mains voltage switches are 6A changeover between 32-75. The differential of this can also be adjusted between 15-80. An expensive unit but we are able to offer them at £4.50 each + 34p. Post 40p + 4p.

Pressure Switch made by J. Hubar of Switzerland, again 6A switch. £2.50 + 20p.

Microwave Receiver and Transmitter, side by side in aluminium case, size approx. 5" x 6" x 3", the aluminium case is mounted so that it can swivel by means of a wall mounting bracket which also contains the electrical connections and test points. We believe this to be a burglar alarm but have no information. It is obviously an expensive piece of equipment containing many transistors, thyristor, IC relay, microswitches etc. We have a few of these and they have not been tampered with so it is reasonable to assume that they could be in working order. Price £10.00 + 80p Post £1 50 + 12p.

# TEAC

TEAC A3340(S)  
4-CHANNEL  
RECORDER

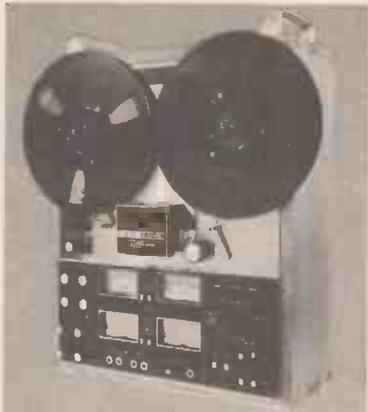


Industrial version upgraded to studio requirements, with increased signal to noise performance and improved reliability. Four totally independent channels each with sel sync, input mixing, switchable VU's and all the facilities for easy multitracking. This industrial model is in more studios than any other version.

Available only from ITA  
(Semi-pro version also available)  
IMMEDIATE DELIVERY

# REVOX

REVOX A-700 SERIES

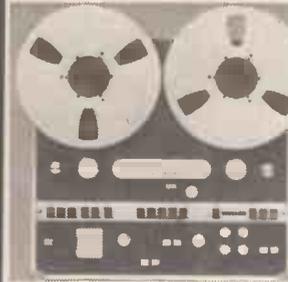

IMMEDIATE DELIVERY

The new big Revox — ideal for all studio requirements. Highly sophisticated design features include servo tape tension, full deck logic, crystal controlled servo electronics, 3 speeds, tape footage counter.

The famous A77 has been consistently improved over the past 8 years and is now available in the latest Mk. 4 version. The wide choice of specifications includes versions for duplicating and logging applications. Backed by UK's latest fastest service.

A-77 SERIES Mk 4




Hire service. Check our prices

IMMEDIATE DELIVERY

# ITA

ITA 10-4  
MODULAR MIXER

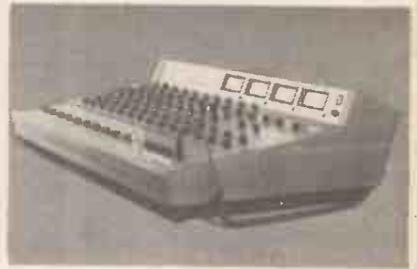

Ten balanced inputs; four output groups, 4 limiters; bass mid and treble EQ, modular construction, headphone monitoring. Extremely high quality construction only matched by mixers costing around £1,000.

10-4 £690

20-4 £1190

EIGHT OUTPUT £1360

IMMEDIATE DELIVERY

Also available for hire

PRICES EXCLUSIVE OF V.A.T.

## Industrial Tape Applications



1-7 Harewood Avenue, Marylebone Road, London NW1  
Telephone: 01-724 2497 Telex: 21879

WW-107 FOR FURTHER DETAILS

## LYNX ELECTRONICS (London) LTD.

92 Broad Street, Chesham, Bucks. Tel (02405) 75154

VAT 8% except \* which are 12 1/2 %

Return Post Service

P&P 30p. Overseas 90p. Matching 20p per pair \*New Price List 20p

Prices correct at 31st March. ACCESS WELCOME

### TRANSISTORS

|        |      |        |       |          |       |         |       |         |       |        |      |
|--------|------|--------|-------|----------|-------|---------|-------|---------|-------|--------|------|
| AC126  | 0.15 | BC182  | 0.11* | BDY60    | 1.70  | BU133   | 1.60* | 2N2926D | 0.09* | 4023BE | 0.20 |
| AC127  | 0.16 | BC182L | 0.12* | BDY81    | 1.65  | BU204   | 1.60* | 2N2926R | 0.10* | 4024BE | 0.86 |
| AC128  | 0.16 | BC183  | 0.10* | BDY62    | 1.15  | BU205   | 1.90* | 2N2926Y | 0.09* | 4025BE | 0.20 |
| AC128K | 0.25 | BC183L | 0.10* | BDY95    | 2.14  | BU206   | 2.40* | 2N2926G | 0.10* | 4026BE | 1.55 |
| AC141  | 0.22 | BC184  | 0.11* | BDY96    | 4.96  | BU208   | 2.60* | 2N3053  | 0.20  | 4027BE | 0.62 |
| AC141K | 0.34 | BC184L | 0.12* | BDY97    | 2.45  | MJ480   | 0.80  | 2N3055  | 0.50  | 4028BE | 0.91 |
| AC142  | 0.18 | BC186  | 0.20* | BF179    | 0.30  | MJ491   | 1.05  | 2N3704  | 0.10* | 4048BE | 1.10 |
| AC142K | 0.32 | BC187  | 0.24* | BF179    | 0.30  | MJ490   | 0.90  | 2N3440  | 0.56  | 4030BE | 0.55 |
| AC176  | 0.16 | BC207B | 0.12* | BF181    | 0.30  | MJ491   | 1.15  | 2N3442  | 1.20  | 4041BE | 0.80 |
| AC176K | 0.32 | BC212  | 0.11* | BF182    | 0.30  | MJE340  | 0.40* | 2N3570  | 3.60  | 4042BE | 0.83 |
| AC187  | 0.18 | BC212L | 0.12* | BF183    | 0.30  | MJE520  | 0.45  | 2N3702  | 0.10* | 4034BE | 1.00 |
| AC187K | 0.36 | BC213  | 0.12* | BF184    | 0.20  | MJE521  | 0.55  | 2N3703  | 0.10* | 4044BE | 0.94 |
| AC169  | 0.18 | BC213L | 0.14* | BF185    | 0.20  | OC43    | 0.95  | 2N3704  | 0.10* | 4046BE | 1.32 |
| AC188K | 0.32 | BC214  | 0.14* | BF184    | 0.30* | OC44    | 0.32  | 2N3705  | 0.10* | 4049BE | 0.54 |
| AD149  | 0.45 | BC214L | 0.15* | BF196    | 0.12* | OC45    | 0.32  | 2N3706  | 0.10* | 4050BE | 0.54 |
| AD161  | 0.35 | BC237  | 0.16* | BF197    | 0.12* | OC46    | 0.20  | 2N3707  | 0.10* | 4059BE | 0.30 |
| AD162  | 0.35 | BC238  | 0.16* | BF224J   | 0.18* | OC70    | 0.30  | 2N3708  | 0.09* | 4070BE | 0.50 |
| AF114  | 0.20 | BC300  | 0.34  | BF224    | 0.17* | OC71    | 0.35  | 2N3709  | 0.09* | 4071BE | 0.26 |
| AF115  | 0.20 | BC301  | 0.32  | BF257    | 0.30  | OC72    | 0.22  | 2N3710  | 0.10* | 4072BE | 0.26 |
| AF116  | 0.20 | BC302  | 0.40  | BF336    | 0.35* | OC84    | 0.40  | 2N3711  | 0.10* | 4081BE | 0.20 |
| AF117  | 0.20 | BC303  | 0.46  | BF337    | 0.32* | OC139   | 1.30  | 2N3715  | 1.70  | 4082BE | 0.26 |
| AF118  | 0.50 | BC303  | 0.55  | BF338    | 0.45* | OC140   | 1.40* | 2N3716  | 1.80  | 4510BE | 1.42 |
| AF124  | 0.25 | BC31   | 0.55  | BFW30    | 1.25  | OC170   | 0.23  | 2N3721  | 1.60  | 4511BE | 1.50 |
| AF125  | 0.25 | BC32   | 0.60  | BFW59    | 0.30  | TIP29A  | 0.44* | 2N3722  | 1.90  | 4516BE | 1.35 |
| AF126  | 0.25 | BC33   | 0.55  | BFW59    | 0.30  | TIP30A  | 0.52* | 2N3723  | 2.10  | 4518BE | 1.28 |
| AF139  | 0.35 | BC334  | 0.55  | BFY41    | 0.26  | TIP31A  | 0.54  | 2N3819  | 0.28* | 4520BE | 1.20 |
| AF239  | 0.37 | BC338  | 0.75  | BFX30    | 0.30  | TIP32A  | 0.64  | 2N4347  | 1.10  |        |      |
| AL102  | 1.45 | BC339  | 1.15  | BFX34    | 0.23  | TIP41A  | 0.66  | 2N4348  | 1.20  |        |      |
| AL103  | 1.30 | BC340  | 0.70  | BFX84    | 0.23  | TIP42A  | 0.72  | 2N4870  | 0.35* |        |      |
| AU107  | 3.30 | BC342  | 0.30  | BFX85    | 0.25  | 2N404   | 0.40  | 2N4871  | 0.35* |        |      |
| AU110  | 1.75 | BC354  | 1.60  | BFX86    | 0.25  | 2N404   | 0.40  | 2N4918  | 0.60* |        |      |
| AU113  | 1.60 | BC370  | 0.12  | BFX87    | 0.20  | 2N697   | 0.20  | 2N4919  | 0.70* |        |      |
| BC107  | 0.12 | BC371  | 0.18  | BFX89    | 0.90  | 2N706   | 0.15  | 2N4920  | 0.50* |        |      |
| BC107B | 0.12 | BC372  | 0.12  | BFY11    | 1.10  | 2N1137  | 0.15  | 2N4922  | 0.58* |        |      |
| BC108  | 0.12 | BD115  | 0.15  | BFY18    | 0.50  | 2N1132  | 0.16  | 2N4923  | 0.46* |        |      |
| BC108B | 0.12 | BD131  | 0.36  | BFY40    | 0.50  | 2N1302  | 0.40  |         |       |        |      |
| BC109  | 0.12 | BD132  | 0.40  | BFY41    | 0.50  | 2N1303  | 0.40  |         |       |        |      |
| BC109B | 0.12 | BD135  | 0.36* | BFY50    | 0.20  | 2N1304  | 0.45  |         |       |        |      |
| BC109C | 0.15 | BD136  | 0.39* | BFY51    | 0.18  | 2N1305  | 0.45  |         |       |        |      |
| BC117  | 0.19 | BD137  | 0.40* | BFY52    | 0.19  | 2N1307  | 0.50  |         |       |        |      |
| BC119  | 0.25 | BD138  | 0.48* | BFY53    | 0.25  | 2N1308  | 0.60  |         |       |        |      |
| BC125  | 0.18 | BD139  | 0.58* | BFY64    | 0.35  | 2N1309  | 0.60  |         |       |        |      |
| BC126  | 0.20 | BD144  | 2.20  | BFY90    | 0.90  | 2N2369  | 0.14  |         |       |        |      |
| BC140  | 0.32 | BD157  | 0.80  | BSX19    | 0.16  | 2N1711  | 0.24  |         |       |        |      |
| BC141  | 0.28 | BD181  | 0.86  | BSX20    | 0.18  | 2N2102  | 0.44  |         |       |        |      |
| BC142  | 0.23 | BD182  | 0.92  | BSX21    | 0.20  | 2N2171  | 0.30  |         |       |        |      |
| BC143  | 0.23 | BD183  | 0.92  | BSX22    | 0.20  | 2N2171  | 0.30  |         |       |        |      |
| BC147  | 0.09 | BD184  | 1.20  | BSY52    | 0.28  | 2N2369A | 0.14  |         |       |        |      |
| BC148  | 0.09 | BD232  | 0.60  | BSY53    | 0.39  | 2N2483  | 0.20  |         |       |        |      |
| BC149  | 0.09 | BD233  | 0.48  | BSY54    | 0.33  | 2N2484  | 0.16  |         |       |        |      |
| BC157  | 0.09 | BD237  | 0.55  | BSY55    | 0.34  | 2N2646  | 0.50  |         |       |        |      |
| BC158  | 0.09 | BD238  | 0.60  | BSY65    | 0.30  | 2N2711  | 0.20  |         |       |        |      |
| BC159  | 0.09 | BD410  | 0.60  | BSY95A   | 0.16  | 2N2712  | 0.15  |         |       |        |      |
| BC160  | 0.32 | BDX32  | 2.30  | BU105    | 1.80* | 2N2904A | 0.20  |         |       |        |      |
| BC161  | 0.38 | BDY10  | 1.50  | BU105/02 | 1.90* | 2N2905  | 0.18  |         |       |        |      |
| BC168  | 0.09 | BDY11  | 2.00  | BU108    | 3.00* | 2N2905A | 0.22  |         |       |        |      |
| BC169  | 0.12 | BDY20  | 0.80  | BU109    | 2.50* | 2N2906  | 0.18  |         |       |        |      |
| BC169C | 0.14 | BDY38  | 0.60  | BU126    | 1.60* | 2N2925  | 0.14* |         |       |        |      |

### CMOS-PLASTIC

|        |      |
|--------|------|
| 4000BE | 0.20 |
| 4001BE | 0.20 |
| 4002BE | 0.20 |
| 4006BE | 1.05 |
| 4007BE | 0.20 |
| 4008BE | 0.93 |
| 4009BE | 0.52 |
| 4010BE | 0.52 |
| 4011BE | 0.20 |
| 4012BE | 0.20 |
| 4013BE | 0.50 |
| 4014BE | 1.00 |
| 4015BE | 0.95 |
| 4016BE | 0.20 |
| 4017BE | 1.00 |
| 4018BE | 1.10 |
| 4019BE | 0.50 |
| 4020BE | 1.12 |
| 4021BE | 1.03 |
| 4022BE | 0.95 |

### Resistors

|             |      |
|-------------|------|
| E24 Series  | 1.5  |
| 10ohm-10meg | 2.0p |
| 1/4 watt    |      |
| 1/2 watt    |      |

### Capacitors

|                 |     |
|-----------------|-----|
| C20 Series      | 0.1 |
| 4p 22 6p        |     |
| 015 4p .22 9p   |     |
| .022 4p .47 10p |     |
| .033 4p 68 14p  |     |
| .047 4p 1.0 17p |     |
| .068 5p 1.5 25p |     |
| 1 5p 22 29p     |     |
| 15 6p           |     |

### REGULATORS

|          |      |
|----------|------|
| 723      | 0.45 |
| 7805     | 1.50 |
| 7812     | 1.50 |
| 7815     | 1.50 |
| 7818     | 1.50 |
| LM309K   | 0.95 |
| LM340-5  | 1.35 |
| LM340-12 | 1.35 |
| LM340-15 | 1.35 |
| LM340-18 | 1.35 |

### OPTO ELECTRONICS

|          |      |
|----------|------|
| DISPLAYS | 0.99 |
| 704      | 0.99 |
| 707      | 0.99 |
| 727      | 1.95 |
| 728      | 1.95 |
| 750      | 1.80 |
| L.E.D.   |      |
| .2 Red   | 0.13 |
| .2 Green | 0.20 |
| .2 Clear | 0.10 |
| TIL209   | 0.10 |

### TTL 7400 SERIES

|        |      |        |      |
|--------|------|--------|------|
| 7400   | 0.16 | 7480   | 0.55 |
| 7401   | 0.16 | 7482   | 0.75 |
| 7402   | 0.16 | 7486   | 0.32 |
| 7403   | 0.16 | 7489   | 2.02 |
| 7404   | 0.40 | 7490AN | 0.49 |
| 7405   | 0.18 | 7491AN | 0.65 |
| 7408   | 0.18 | 7492   | 0.57 |
| 7409   | 0.18 | 7493   | 0.45 |
| 7410   | 0.16 | 7494   | 0.85 |
| 7412   | 0.25 | 7495   | 0.67 |
| 7413   | 0.40 | 7496   | 0.82 |
| 7414   | 0.72 | 74100  | 1.07 |
| 7417   | 0.43 | 74107  | 0.35 |
| 7420   | 0.16 | 74121  | 0.34 |
| 7425   | 0.30 | 74122  | 0.47 |
| 7427   | 0.30 | 74123  | 0.65 |
| 7430   | 0.16 | 74141  | 0.78 |
| 7432   | 0.28 | 74145  | 0.68 |
| 7437   | 0.30 | 74154  | 1.30 |
| 7441AN | 0.76 | 74164  | 0.93 |
| 7442   | 0.65 | 74165  | 0.93 |
| 7445   | 0.90 | 74174  | 1.40 |
| 7447AN | 0.81 | 74175  | 0.94 |
| 7448   | 0.81 | 74180  | 1.06 |
| 7470   | 0.32 | 74181  | 2.70 |
| 7472   | 0.26 | 74191  | 1.33 |
| 7473   | 0.30 | 74192  | 1.20 |
| 7474   | 0.32 | 74193  | 1.35 |
| 7475   | 0.47 | 74194  | 1.20 |
| 7476   | 0.36 | 74196  | 1.64 |

### LINEAR I.C.s

|              |       |              |       |
|--------------|-------|--------------|-------|
| 301A         | 0.40* | MC1352P0.75  |       |
| 307          | 0.55* | MC1353P0.75  |       |
| 380          | 0.90* | MC1458P0.77  |       |
| 381          | 1.60* | MC1496L0.82  |       |
| 3900         | 0.70* | SA5560.225   |       |
| 709          | 0.27  | SA5570.225   |       |
| 741          | 0.28  | TA4300.161   |       |
| 748          | 0.35  | TA4310A.138  |       |
| NE555        | 0.45  | TA4550.045   |       |
| NE566        | 1.50* | TA611812     |       |
| NE567        | 2.00* | TA861.065    |       |
| CA3045       | 0.85* | TBA5300.185* |       |
| CA3046       | 0.85* | TBA5300.190* |       |
| CA3130       | 0.79  | TBA560.280*  |       |
| MC1304P1.60* |       | TBA570.098   |       |
| MC1307P0.85* |       | TC2705Q      | 1.95* |
| MC1310P1.18* |       |              |       |
| MC1351P0.75* |       |              |       |

### THYRISTORS

| PV  | 1A    | 3A    | 4A      | 6A      | 8A      | 10A     | 15A    |
|-----|-------|-------|---------|---------|---------|---------|--------|
|     | (10A) | (Shd) | (T0220) | (T0220) | (T0220) | (T0220) | (T048) |
| 200 | 0.35  | 0.50  | 0.45    | 0.40    | 0.58    | 0.60    | 0.68   |
| 400 | 0.40  | 0.60  | 0.50    | 0.45    | 0.88    | 0.88    | 0.98   |
| 600 | 0.65  | 0.85  |         |         |         |         |        |

# ORCHARD ELECTRONICS

NEW BIG CAT 50p - Refundable Vouchers

## SERVICE SECOND TO NONE TRY US AND SEE

SUPPLIERS TO D.O.E., A.E.R.E., U.K.A.E.A. Government Depts., Universities, Schools and equipment manufacturers.

All customers are important. Are you being served? Join the professionals and get the best service.

### TRANSISTORS

|         |       |        |       |        |       |        |       |         |       |        |       |          |       |
|---------|-------|--------|-------|--------|-------|--------|-------|---------|-------|--------|-------|----------|-------|
| AA119   | 0.08  | BC1778 | 0.18  | BF158  | 0.20* | OC44   | 0.45  | 2N3703  | 0.14* | 1/25   | 0.10* | 47/35    | 0.12* |
| AC125   | 0.26  | BC1788 | 0.18  | BF166  | 0.38  | OC45   | 0.45  | 2N3704  | 0.13* | 1/63   | 0.10* | 50/10    | 0.10* |
| AC126   | 0.26  | BC1798 | 0.19  | BF167  | 0.21  | OC71   | 0.35  | 2N3705  | 0.14* | 1/75   | 0.10* | 50/15    | 0.10* |
| AC127   | 0.28  | BC1828 | 0.12* | BF173  | 0.20  | OC72   | 0.45  | 2N3707  | 0.12* | 2/2/25 | 0.10* | 100/18   | 0.06* |
| AC128   | 0.20  | BC1821 | 0.11* | BF178  | 0.24  | OC74   | 0.45  | 2N3708  | 0.12* | 2/2/25 | 0.10* | 100/25   | 0.10* |
| AC151   | 0.35  | BC1838 | 0.10* | BF179  | 0.25  | OC81   | 0.60  | 2N3709  | 0.14* | 2/5/64 | 0.10* | 100/35   | 0.11* |
| AC153   | 0.35  | BC1831 | 0.10* | BF183  | 0.34  | OC82   | 0.70  | 2N3710  | 0.11* | 4/7/16 | 0.08* | 100/50   | 0.15* |
| AC176   | 0.22  | BC1848 | 0.12* | BF184  | 0.25  | ORP12  | 0.68  | 2N3711  | 0.11* | 4/7/63 | 0.10* | 150/35   | 0.15* |
| AC187   | 0.22  | BC1841 | 0.11* | BF185  | 0.28  | TRP29A | 0.47* | 2N3819E | 0.25* | 5/10   | 0.10* | 220/16   | 0.15* |
| AC188   | 0.20  | BC186  | 0.25  | BF194  | 0.10* | TRP30A | 0.56* | 2N3820  | 0.45* | 5/16   | 0.11* | 220/25   | 0.16* |
| AD149   | 0.68  | BC187  | 0.26  | BF195  | 0.10* | TRP31A | 0.57  | 2N3823E | 0.25* | 8/8/25 | 0.10* | 220/63   | 0.25* |
| AD161   | 0.52  | BC204A | 0.16* | BF196  | 0.12* | TRP32A | 0.87  | 2N4036  | 0.40  | 6/8/40 | 0.10* | 250/12   | 0.12* |
| AD162   | 0.52  | BC204B | 0.16* | BF197  | 0.12* | TRP33A | 0.94  | 2N4058  | 0.16* | 8/70   | 0.10* | 250/50   | 0.18* |
| MCM/PPR | 1.24  | BC209B | 0.13* | BF199  | 0.15* | TRP34A | 1.13  | 2N4059  | 0.10* | 10/16  | 0.09* | 250/64   | 0.20* |
| AF116   | 0.24  | BC212A | 0.13* | BF200  | 0.38  | TRP41A | 0.67  | 2N4061  | 0.12* | 10/25  | 0.09* | 330/16   | 0.15* |
| AF117   | 0.28  | BC212L | 0.15* | BF209  | 0.26  | TRP42A | 0.80  | 2N4124  | 0.20* | 10/35  | 0.10* | 470/6/3  | 0.10* |
| AF124   | 0.46  | BC2136 | 0.12* | BF230  | 0.25  | TS43   | 0.35  | 2N4126  | 0.30* | 10/64  | 0.10* | 470/10   | 0.12* |
| AF156   | 0.95  | BC213L | 0.14* | BF240  | 0.28  | ZTX109 | 0.14* | 2N4298  | 0.50  | 10/250 | 0.18* | 470/16   | 0.18* |
| AF239   | 0.30  | BC214  | 0.15* | BF284  | 0.22  | ZTX300 | 0.13* | 2N4547  | 0.50  | 15/40  | 0.10* | 470/25   | 0.20* |
| AU113   | 1.72* | BC214L | 0.17* | BF288  | 0.22  | ZTX301 | 0.13* | 2N4548  | 0.40* | 15/400 | 0.35* | 680/25   | 0.25* |
| CG101   | 0.11* | BC237A | 0.16* | BF290  | 0.25  | ZTX302 | 0.18* | 2N4549  | 0.40* | 16/10  | 0.10* | 1000/16  | 0.25* |
| CG107A  | 0.12  | BC238A | 0.15* | BF291  | 0.25  | ZTX500 | 0.15* | 2N40361 | 0.38* | 20/15  | 0.10* | 1000/25  | 0.30* |
| CG107B  | 0.13  | BC261A | 0.16  | BF292  | 0.25  | ZTX508 | 0.25* | 2N40363 | 0.50* | 20/70  | 0.10* | 1000/50  | 0.40* |
| CG108   | 0.10  | BC262A | 0.19  | BF300  | 0.23  | ZTX508 | 0.25* | 2N40613 | 0.95  | 22/6V3 | 0.10* | 1500/25  | 0.35* |
| CL108   | 0.06  | BC267A | 0.17  | BU108  | 2.50* | ZTX530 | 0.23* | 25C1172 | 3.00* | 22/16  | 0.10* | 2200/6V3 | 0.30* |
| CG108B  | 0.11  | BC268B | 0.17  | BU208  | 3.00* | 1N914  | 0.05  |         |       | 25/25  | 0.11* | 2200/40  | 0.60* |
| CG108C  | 0.12  | BC269  | 0.17  | BY126  | 0.16  | 1N4001 | 0.06  |         |       | 33/50  | 0.12* | 2500/15  | 0.45* |
| CG109   | 0.12  | BC269  | 0.28  | BY127  | 0.16  | 1N4002 | 0.05  |         |       | 47/6V3 | 0.10* | 3300/30  | 0.45* |
| CG109B  | 0.13  | BC280  | 0.25  | BY152  | 0.25  | 1N4003 | 0.07  |         |       | 17/10  | 0.10* | 500/12   | 0.45* |
| CG109C  | 0.13  | BC301  | 0.34  | BY154  | 0.40  | 1N4004 | 0.08  |         |       | 47/16  | 0.10* |          |       |
| CG117   | 0.18* | BC303  | 0.35  | ME401  | 0.18* | 1N4005 | 0.09  |         |       |        |       |          |       |
|         |       | BC327  | 0.20* | ME402  | 0.18* | 1N4006 | 0.10  |         |       |        |       |          |       |
| BC136   | 0.16* | BC328  | 0.18* | ME4011 | 0.18* | 1N4007 | 0.11  |         |       |        |       |          |       |
| BC142   | 0.24  | BC338  | 0.16* | ME412  | 0.19* | 1N4148 | 0.05  |         |       |        |       |          |       |
| BC143   | 0.24  | BC310  | 0.16* | ME413  | 0.15* | 1N4100 | 0.13  |         |       |        |       |          |       |
| BC147A  | 0.09* | BC340  | 0.15* | ME414  | 0.15* | 1N4101 | 0.13  |         |       |        |       |          |       |
| BC147B  | 0.10* | BC461  | 0.35  | ME461  | 0.21* | 1N4504 | 0.21  |         |       |        |       |          |       |
| BC148   | 0.09* | BC557  | 0.15* | ME462  | 0.21* | 2N708  | 0.20  |         |       |        |       |          |       |
| BC148B  | 0.10* | BC558  | 0.15* | ME463  | 0.14* | 2N1613 | 0.30  |         |       |        |       |          |       |
| BC149   | 0.10* | BC559  | 0.15* | ME4101 | 0.11* | 2N1711 | 0.30  |         |       |        |       |          |       |
| BC149B  | 0.11* | BC710  | 0.15* | ME3340 | 0.76* | 2N2102 | 0.50  |         |       |        |       |          |       |
| BC149C  | 0.11* | BC711  | 0.18  | MPF102 | 0.40* | 2N2219 | 0.30  |         |       |        |       |          |       |
| BC153   | 0.18* | BC712  | 0.14  | OAS    | 0.71  | 2N2222 | 0.20  |         |       |        |       |          |       |
| BC154   | 0.18* | BC713  | 0.20  | DA10   | 0.62  | 2N2646 | 0.55  |         |       |        |       |          |       |
| BC157   | 0.12* | BC714  | 0.20  | DA12   | 0.14  | 2N2926 | 0.13* |         |       |        |       |          |       |
| BC157B  | 0.14* | BC715  | 0.20  | DA81   | 0.30  | 2N2926 | 0.15* |         |       |        |       |          |       |
| BC158A  | 0.12* | BC716  | 0.20  | DA82   | 0.07  | 2N3653 | 0.25  |         |       |        |       |          |       |
| BC159A  | 0.12* | BC717  | 0.20  | DA91   | 0.08  | 2N3654 | 0.25  |         |       |        |       |          |       |
| BC172A  | 0.15* | BC718  | 0.20  | DA95   | 0.08  | 2N3655 | 0.60  |         |       |        |       |          |       |
| BC172B  | 0.15* | BC719  | 0.20  | DA99   | 0.10  | 2N3643 | 0.17* |         |       |        |       |          |       |
| BC173B  | 0.16* | BC720  | 0.20  | DA92   | 0.11  | 2N3646 | 0.17* |         |       |        |       |          |       |
| BC177   | 0.17* | BC721  | 0.22  | DC35   | 1.20  | 2N3702 | 0.11* |         |       |        |       |          |       |

### CAPACITORS ELEC. MFD/V

|        |       |          |       |
|--------|-------|----------|-------|
| 1/25   | 0.10* | 47/35    | 0.12* |
| 1/63   | 0.10* | 50/10    | 0.10* |
| 1/75   | 0.10* | 50/15    | 0.10* |
| 2/2/25 | 0.10* | 100/18   | 0.06* |
| 2/5/64 | 0.10* | 100/35   | 0.11* |
| 4/7/16 | 0.08* | 100/50   | 0.15* |
| 4/7/63 | 0.10* | 150/35   | 0.15* |
| 5/10   | 0.10* | 220/16   | 0.15* |
| 5/16   | 0.11* | 220/25   | 0.16* |
| 8/8/25 | 0.10* | 220/63   | 0.25* |
| 6/8/40 | 0.10* | 250/12   | 0.12* |
| 8/70   | 0.10* | 250/50   | 0.18* |
| 10/16  | 0.09* | 250/64   | 0.20* |
| 10/25  | 0.09* | 330/16   | 0.15* |
| 10/35  | 0.10* | 470/6/3  | 0.10* |
| 10/64  | 0.10* | 470/10   | 0.12* |
| 10/250 | 0.18* | 470/16   | 0.18* |
| 15/40  | 0.10* | 470/25   | 0.20* |
| 15/400 | 0.35* | 680/25   | 0.25* |
| 16/10  | 0.10* | 1000/16  | 0.25* |
| 20/15  | 0.10* | 1000/25  | 0.30* |
| 20/70  | 0.10* | 1000/50  | 0.40* |
| 22/6V3 | 0.10* | 1500/25  | 0.35* |
| 22/16  | 0.10* | 2200/6V3 | 0.30* |
| 25/25  | 0.11* | 2200/40  | 0.60* |
| 33/50  | 0.12* | 2500/15  | 0.45* |
| 47/6V3 | 0.10* | 3300/30  | 0.45* |
| 17/10  | 0.10* | 500/12   | 0.45* |
| 47/16  | 0.10* |          |       |

### CERAMICS 50V

|  |
|--|
| 2.2, 4.7, 6, 10, 22, 33, 39, 47, 100, 200, 470, 560, 1000, 1500, 2200, 3000, 4700, 10000, 47000p. 1MFD 10V. All at 6p* each. 1M963V 8p*. |
|--|

### 1/C LINEAR

|                |       |      |      |       |      |
|----------------|-------|------|------|-------|------|
| 709 (7099)     | 0.35  | 7407 | 0.40 | 7491  | 0.75 |
| 709 (8 PH OIL) | 0.40  | 7408 | 0.24 | 7492  | 0.55 |
| 741 (8 PH OIL) | 0.28  | 7409 | 0.23 | 7493  | 0.55 |
| CA3130         | 0.87* | 7410 | 0.18 | 7494  | 0.85 |
| LM301A         | 0.55  | 7411 | 0.24 | 7495  | 0.74 |
| LM309K         | 2.00  | 7412 | 0.25 | 7496  | 0.90 |
| LM324          | 2.05  | 7413 | 0.38 | 74107 | 0.30 |
| LM3801         | 1.29* | 7414 | 0.12 | 74121 | 0.38 |
| LM3801/5L60745 | 2.00* | 7416 | 0.36 | 74123 | 0.48 |
| LM723          | 0.58  | 7417 | 0.36 | 74141 | 0.80 |
| LM733          | 0.69  | 7420 | 0.18 | 74145 | 1.15 |
| MC1327         | 1.35* | 7421 | 0.36 | 74151 | 0.94 |
| MC1330P        | 0.75* | 7422 | 0.22 | 74174 | 1.20 |
| MC1350P        | 0.75* | 7423 | 0.34 | 74190 | 1.60 |
| MPF0040        | 1.50  | 7426 | 0.36 | 74191 | 2.10 |
| NE555          | 0.49  | 7427 | 0.32 | 74192 | 1.60 |
| NE566          | 1.90* | 7428 | 0.50 |       |      |
| NE567          | 2.70* | 7429 | 0.50 |       |      |
| SN7603N        | 2.80* | 7430 | 0.28 |       |      |
| SN76033N       | 1.60* | 7433 | 0.33 |       |      |
| SN76033N       | 1.75* | 7437 | 0.42 |       |      |
| SN76033N       | 1.75* | 7438 | 0.30 |       |      |
| SN76033N       | 1.60* | 7440 | 0.18 |       |      |
| SN76033N       | 2.75* | 7441 | 0.85 |       |      |
| TAAS50         | 0.60* | 7442 | 0.68 |       |      |
| TBA120AS0      | 1.30* | 7443 | 1.00 |       |      |
| TBA4800        | 1.25* | 7444 | 1.00 |       |      |
| SN76033N       | 1.70* | 7445 | 0.90 |       |      |
| TBA5000        | 1.90* | 7446 | 1.00 |       |      |
| TBA5400        | 1.90* | 7447 | 0.98 |       |      |
| TBA5500        | 3.40* | 7448 | 0.98 |       |      |
| TBA5600Q       | 2.30* | 7450 | 0.18 |       |      |
| TBA641         | 2.55* | 7451 | 0.18 |       |      |
| TBA750         | 1.90* | 7452 | 0.18 |       |      |
| TBA8000        | 1.35* | 7453 | 0.18 |       |      |
| TBA81050       | 1.49* | 7454 | 0.18 |       |      |
| TBA8200        | 1.20* | 7470 | 0.32 |       |      |
| TBA9200        | 2.80* | 7472 | 0.30 |       |      |
| TBA9900        | 2.50* | 7473 | 0.30 |       |      |
| TC4270         | 2.20* | 7474 | 0.35 |       |      |
| ZM414          | 1.40* | 7475 | 0.49 |       |      |
| Z513UC         | 8.50* | 7476 | 0.48 |       |      |
|                |       | 7480 | 0.48 |       |      |
|                |       | 7481 | 1.00 |       |      |
|                |       | 7482 | 1.00 |       |      |
|                |       | 7483 | 1.00 |       |      |
|                |       | 7484 | 1.20 |       |      |
|                |       | 7485 | 1.60 |       |      |
|                |       | 7486 | 0.43 |       |      |
|                |       | 7403 | 0.18 |       |      |
|                |       | 7404 | 0.23 |       |      |
|                |       | 7405 | 0.23 |       |      |
|                |       | 7406 | 0.40 |       |      |

### POTENTIOMETERS

|         |  |
|---------|--|
| Lin/Log | 5K, 10K, 25K, 50K, 100K, 250K, 500K 1M, 2M, 25p* each. |
|---------|--|

### PRESET

|               |   |
|---------------|---|
| MIN & SUB-MIN | 100ohm, 220ohm, 470ohm, 1K, 2K, 4K, 10K, 20K, 50K, 100K, 250K, 470K 1M, 2M, 2p* each. |
|---------------|---|

### THYRISTORS

|              |              |      |     |
|--------------|--------------|------|-----|
| 60V 1A 0.25  | 100V 1A 0.38 | TA61 | 100 |
| 200V 1A 0.60 | TA62         | 100  | 100 |
| 600V 1A 1.40 | BT 106       | 100  | 100 |
| 400V 4A 0.65 | CI06D1       | 100  | 100 |
| 500V 6A 1.85 | BT 109       | 100  | 100 |

### ZENERS (4000mV) BZX 83

|   |
|---|
| 3V, 3V3, 5V1, 5V6, 7V5, 9V1, 10V, 12V, 18V, 22V, 30V, All at 12p* each. |
|---|

### LED TR 209/70.125" 0.2"

|                 |     |     |
|-----------------|-----|-----|
| Red             | 20p | 20p |
| Green           | 29p | 29p |
| Clips for above |     | 3p  |

### TTL DIGITAL

|      |      |      |      |
|------|------|------|------|
| 7400 | 0.15 | 7480 | 0.48 |
| 7401 | 0.20 | 7481 | 1.00 |
| 7402 | 0.18 | 7482 | 1.00 |
| 7403 | 0.18 | 7483 | 1.20 |
| 7404 | 0.23 | 7484 |      |

**WH WEST HYDE**



Offer instrument manufacturers low-cost cases ex-stock. Blue PVC coated steel strength and rigidity. PVC aluminium grey front and rear panels are removable. PCB and PSU mounting system available. Also available in black, 301 price of 302, Bk 302 303, Bk 304 305.



A range of eyebrow cases in blue textured acrylic. Front panels normally white zincite or PVC/aluminium; also available unpainted up to 1277 size. Aluminium panels 20p extra up to 16127 only.

**Instrument cases**

All dimensions are WidthxHeightxDepth  
PRICES 1 off inc. P & P but not VAT.

|                               |                 |       |
|-------------------------------|-----------------|-------|
| MOD-3 (including chassis)     | C 4.5x10x 6.5"  | 9.44  |
| 301 7x3 x5.5"                 | D 9 x 3x 6.5"   | 9.44  |
| 302 7x4 1/2x5.5"              | E 9 x 7x 6.5"   | 10.45 |
| 303 7x5 x5.5"                 | F 9 x 10x 6.5"  | 12.32 |
| 304 11x3 x5.5"                | G 13 x 3x 6.5"  | 10.45 |
| 305 11x4 1/2x5.5"             | H 13 x 7x 6.5"  | 12.32 |
| 306 11x6 x5.5"                | I 13 x 10x 6.5" | 13.91 |
| CONTIL TEXTURED               | J 18 x 3x 6.5"  | 12.32 |
| 755 7x5x5"                    | K 18 x 7x 6.5"  | 16.97 |
| 867 8x7x6"                    | L 18 x 10x 6.5" | 20.96 |
| 975 9x5x7"                    | M 4.5x 3x13"    | 7.72  |
| 1277 12x7x7"                  | N 4.5x 7x13"    | 10.45 |
| 1277 unpainted                | O 4.5x10x13"    | 13.91 |
| 16127 16x7x12"                | P 9 x 3x13"     | 10.45 |
| 191010 19x10x10"              | Q 9 x 7x13"     | 13.91 |
| ELF CASES Grey (inc. chassis) | R 9 x 10x13"    | 16.97 |
| EIF 6x4x4"                    | S 13 x 3x13"    | 13.91 |
| Bare EIF (less ft. ch. pnl)   | T 13 x 7x13"    | 16.97 |
| Giant EIF 8x5 1/2x5"          | U 13 x 10x13"   | 20.96 |
| Long EIF 9x4x3"               | V 18 x 3x13"    | 16.97 |
| Jumbo EIF 10 1/4x5 1/2x5 1/2" | W 18 x 7x13"    | 20.96 |
|                               | X 18 x 10x13"   | 24.52 |

Mod 2 in Woodgrain or Black finish in sizes A-L & N.  
Prices as for one price up on Mod 2, e.g. Mod 2A Woodgrain or Black is 5 Mod 2B.

**WEST HYDE WH**



Mod-2 cases over 24 sizes. Front and back panels grey PVC. Aluminium chassis included. Packed flat. Outer casing blue PVC steel or up to size L also available in wood-grain and black. (Price as for next price higher i.e. A Black is B price).



These tough little cases add very little to the cost of a job. Front panel aluminium with protective coat. Elf cases are available in 4 sizes, all dough-moulded in grey glass polyester, all panels, feet and chassis included.

All West Hyde cases are available with substantial discounts for quantities. Most cases have discounts at 5 off and 25 off with discounts up to 25% at 100 off. Prices include P & P and are less 10% if collected, on first three price breaks on cases only.

**BUY A CASE FROM A SMALL RANGE, YOU GET A CASE—BUY A CASE FROM A BIG RANGE, YOU GET A SOLUTION**



A prestige anodised case, black PVC steel top and bottom which can be supplied louvered at no extra cost. Free standing or rack mounting, available in rack or half-width assembled in special polystyrene pack for safe postage.

**Instrument cases**

|                            |                  |       |
|----------------------------|------------------|-------|
| BRIGHTCASE MARK II         | SAMOS            |       |
| BC212 13 1/2" Full Rack    | S1 100x 50x50mm  | 1.36  |
| BC222 13 1/2" Half Rack    | S2 100x 100x50mm | 1.56  |
| BC312 15 1/2" Full Rack    | S3 100x 150x50mm | 1.73  |
| BC322 15 1/2" Half Rack    | S4 125x 50x75mm  | 1.95  |
| Rack Brackets available    | S5 125x 100x75mm | 2.24  |
| No extra for Louvers add L | S6 125x 150x75mm | 2.62  |
|                            | S7 125x 200x75mm | 2.91  |
| MINOS                      | HEAVY DUTY CASE  |       |
| M2 65x100x50mm             | M3 8x 8x5"       | 14.89 |
| M3 100x130x50mm            | M2 Bare          | 16.54 |
| M2 Bare                    | M3 Bare          | 20.95 |




Miniature instrument cases in blue and white PVC steel. Assemble in the lower half, clip-in feet, 2 screws allow the cover to hinge off cases, 2 more to fix. PC feet are available to hold up to 4 PC boards horizontally in cases.



Smart miniature ABS cases in tough rigid high gloss black. Front panels either aluminium or PVC steel. Built-in slots for PC cards, dividers etc. Chassis or PC boards can be supported on 'P' clips from internal pillars.

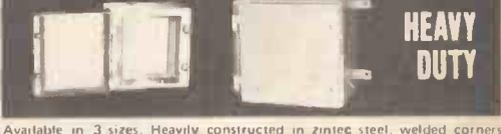OVER 400 DIFFERENT CASES IN STOCK—SIZE RANGE OVER 5000:1 IN VOLUME  
Prices correct 1st April 77



Available in 3 sizes. Heavily constructed in zinc steel, welded corners with heavy hinges. 2 screw fixings and foam around the door. In the base is a gland plate with gasket and a chassis with screws provided.

**THE INSTRUMENT**

Send for catalogue  
**WEST HYDE**  
DEVELOPMENTS LIMITED  
Rye Field Cres., Northwood Hills, Northwood, Middx., HA6 1NN  
Telephone: Northwood 24941/26732/27051  
Telex: 923231 West Hyde Nthwd.

**CASE SPECIALISTS**

**WH WEST HYDE**



Above: Red LED, R Threaded chrome LED, Q, S, PCG, PCE, PCH, PCI, PCF, PCC, PCB, PCA, PPA, PPB. LEDs in red, green on own or in threaded chromium housing, 6.5mm d. hole. S neon 5.5mm d. Q neon 7mm d. Neons in PC housings 9.5mm d., 3 cap. colours, dome, top-hat, square. PP 12.5mm d. 6" leads std., 30" extra cost; neon only, 110, 220 or 500 volts.

**COMPONENTS**

Neon prices include P & P.

|                       |     |     |     |     |     |      |
|-----------------------|-----|-----|-----|-----|-----|------|
| LEDs:                 | 1   | 10  | 50  | 100 | 500 | 1000 |
| Red (LED 32)          | 21p | 19p | 17p | 16p | 15p | 14p  |
| Green (LED 35)        | 30  | 27  | 24  | 22  | 21  | 20   |
| Red (Thread) (LED 12) | 55  | 49  | 44  | 41  | 38  | 37   |
| Green .. (LED 15)     | 65  | 58  | 52  | 49  | 45  | 43   |

|                      |    |    |     |     |      |       |
|----------------------|----|----|-----|-----|------|-------|
| NEONS, 110 or 230V   | 1  | 10 | 100 | 500 | 1000 | 10000 |
| PCA/I & PP. 6"       | 32 | 27 | 24  | 21  | 19   | 16    |
| PCA/I & PP. 30"      | 38 | 32 | 28  | 25  | 23   | 19    |
| Q                    | 62 | 53 | 46  | 41  | 37   | 31    |
| S                    | 40 | 34 | 30  | 27  | 24   | 20    |
| N per 10 (neon only) | 50 | 42 | 37  | 33  | 30   | 25    |

PRICES - 1 off inc. P & P but not VAT  
Discounts for quantities  
Minimum order: £2.00.

**WEST HYDE WH**



Hundreds of knobs, collet or screw fixing, plastic or aluminium, fluted, textured, smooth, wing, pointer, insulated, slow-motion, digital, crank-handle, heavy-duty, wing, contemporary, dual, & diamond turned. Shafts from 3mm to 10mm. Dia. from 8mm to 58mm.



On L., extruded PVC and anod. al. Centre: heavy duty carrying handles. On R. anod. & chromium. Wide range (47 different) in PVC, nylon, chromium, anodised, flush, extruded and carrying.

|                 |      |                         |       |
|-----------------|------|-------------------------|-------|
| HANDLES         |      | KNOBS                   |       |
| Chromium from   | .81  | See Catalogue for Price |       |
| Extruded from   | 1.99 | PANAVICE                |       |
| Nylon from      | .95  | (Photo L to R)          |       |
| PVC from        | .69  | 301, base plus vice     | 19.95 |
| Pivoting        | 1.90 | 306, 165mm opening      | 9.97  |
| Flush precision | 5.58 | 300, Screw base         | 11.95 |
| Very Heavy duty |      | 380, Vacuum base        | 17.63 |
| 150 Kg          |      | 315, PC holder          | 17.27 |
|                 |      | 311 Bench clamp         | 9.97  |
|                 |      | 303, Vertical vice      | 8.43  |

|                 |       |                |       |
|-----------------|-------|----------------|-------|
| TEST METERS     |       | ORYX SOLDERING |       |
| LT101           | 6.23  | Solder pot     | 10.50 |
| LT801           | 13.35 | Oryx Stand     | 3.20  |
| TS141           | 30.82 | Oryx 50        | 7.95  |
| 141/30A Shunt   | 5.86  | SR2 desolder   | 7.75  |
| 141/Lux         | 26.41 | SR3A desolder  | 5.60  |
| 141/Thermometer | 23.47 | SR3S desolder  | 4.95  |
| 141/25K V       | 11.00 | Soldersuck     | 1.60  |




A very good holding system. Four vices, 3 different bases, all interchangeable. Many vice jaws to hold PCs or available in steel, neoprene, nylon etc. Max. opening 6". Table mounting. Screw mount or Vacuum base.



Pop-up 20,000 ohms/v., LT801, 17 ranges. Pocket LT101 low-cost, 12 ranges, 1,000 ohms/v. TS141, 66 ranges, 20,000 ohms/v. incl. nylon case, 115mm scale, 5amps AC & DC, 2,500 v. AC, well damped, many accessories.



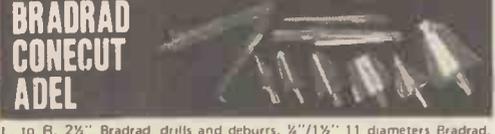Solder pots incl. neons, temp controlled irons Oryx Stand available, but not shown. Oryx 50 thermostat in handle. Desoldering tools, all with PTFE nozzle. On right, solder suck at minimum cost.



L. to R. 2 1/2" Bradrad, drills and deburrs, 1/2"/1 1/2" 11 diameters Bradrad, 4 Conecuts, 1/2"/12". Adel nibbling tool, square or round holes, 11mm d. entry. Underneath: 2 reamers, 1/2"/11". To make round holes with no vibration.

|                        |       |                       |            |
|------------------------|-------|-----------------------|------------|
| BRADRAD, CONECUT, ADEL |       | RESISTORS             |            |
| Bradrad 1 1/2" or 36mm | 17.34 | Price per pack of     |            |
| Bradrad 2 1/2" or 60mm | 44.02 | RCF 0.25W             | .25 100    |
| Conecut No 1           | 5.40  | RCF 125W              | .29 .75    |
| Conecut No 2           | 8.78  | RCF 5W                | .34 .91    |
| Conecut No 3           | 13.12 | RWW 25W               | .57 1.50   |
| Conecut No 4           | 16.04 | RWW 5W                | .88 1.64   |
| Set 1, 2, 3            | 24.70 | RWW 2 5W (over 1.1)   | 6.77 10.63 |
| Reamer, small          | 8.24  | RWW 6W (over 1.1)     | 6.77 10.63 |
| Reamer, large          | 9.63  | 2.5 or 6W (under 1.1) | 4.56 20.45 |
| Reamer, pair           | 16.07 |                       |            |

1 less for quantity



|          |         |         |          |         |         |
|----------|---------|---------|----------|---------|---------|
| Type (W) | Min (Ω) | Max (Ω) | Type (W) | Min (Ω) | Max (Ω) |
| RCF .12  | 10      | 1M      | RWW .5   | OR1     | 10      |
| RCF .25  | 4R/     | 2M2     | RWW 2.5  | OR5     | 5K      |
| RCF .5   | 1R/     | 2M2     | RWW 6.   | OR5     | 10K     |
| RWW .25  | OR1     | 10      |          |         |         |

Carbon film resistors (RCF) together with wirewound resistors (RWW) in low values and vitreous wirewound (RWW) available in packs of 25 100 1 000 10 000 only i.e. 125 off priced as 100 off plus 25 off

**THE INSTRUMENT**

OVER 400 DIFFERENT CASES IN STOCK—SIZE RANGE OVER 5000:1 IN VOLUME  
Prices correct 1st April 77

Send for catalogue  
**WEST HYDE**  
DEVELOPMENTS LIMITED  
Rye Field Cres., Northwood Hills, Northwood, Middx., HA6 1NN  
Telephone: Northwood 24941/26732/27051  
Telex: 923231 West Hyde Nthwd.

**CASE SPECIALISTS**

## SIGNAL SOURCES

**ADVANCE**  
V.H.F. Square wave Generator SG21 10 KHz-100MHz. Max. o/p 2V £35  
H1 Audio Signal Generator. 15Hz-50KHz Sine and Square £35.00  
E2 R.F. Signal Generator 10KHz-100MHz £76.00

**H1E Audio Signal Generator.**  
Sine & Square Wave  
15Hz-50KHz. 200V to 20V (Sine) Distortion 1% 1.4mV to 140V (square). Brand new condition £70.00

**GENERAL RADIO**  
Unit Oscillator 1209C. Freq. 250-920MHz. Accuracy 1% Drift. 0.2%. O/p into 50ohms = 150mW supplied with Power Supply Type 1201-CQ £145

**HEWLETT PACKARD**  
10515A Frequency Doubler. Extends the useable frequency range of signal generators. Operating on input frequencies 0.5MHz to 500MHz it provides a doubled output in the range of 1MHz to 1GHz. The frequency response of this 50 ohm device is very flat (< ±2dB typically) over the entire frequency range and undesired harmonics are well suppressed. Brand 211A Square Wave Generator 1Hz-1MHz £75.00  
F.M./A.M. Signal Generator 202H. F.M. A.M. C/W & pulse coverage 54 to 215 MHz R.F. o/p 0.1uV-0.2V 50ohms Impedance £450  
Audio Signal Generator 206A 20Hz-20KHz ±2% accuracy Distortion <1% £90  
612A-U.H.F. Signal Generator 450-1230MHz 0.1uV-0.5V (50 ohms) A.M. internal & external. Pulse mod. facilities. SUPERB CONDITION £1250.00

**MARCONI INSTRUMENTS**  
TF1060 U.H.F. Signal Generator 450-1250MHz. Sine wave and pulse a.m. £350.00  
TF867 Signal Generator 15KHz-30MHz O/p volts 0.4uV-4V £135.00  
TF2005R Two Tone Source. The instrument comprises two identical low-distortion a.f. oscillators and a monitored attenuator unit, to form a compact test set for the measurement of inter-modulation distortion using the methods recommended by S.M.P.T.E. and C.C.I.F. Frequency range 20Hz to 20KHz in six bands (each oscillator can be adjusted and used independently). Harmonic distortion Less than 0.05% between 63Hz and 6KHz when using unbalanced output. Generally less than 0.1% under other conditions. Intermodulation Band -80dB with respect to the wanted signal. Amplitude Reference Level Up to +10dBm from each oscillator. Output attenuator 11dB in 0.1dB steps. Output impedance 800Ω unbalanced, or 600Ω 150Ω or 75Ω balanced and centre-tapped £485.00  
S.F. Signal Generator 618C 2.8-7.6GHz ±1% 50 ohms £500  
F.M./A.M. Signal Generator TF 995A/3S Ministry type No CT402 15MHz-220MHz R.F. o/p 2.0-200mV Internal & External Mod Facilities V good condition £385  
F.M./A.M. Signal Generator TF995A/5 1.5-220MHz in 5 bands. 0.1uV-200mV F.M. up to ±120KHz from 50Hz-15KHz A.M. up to 50KHz from 100Hz-10KHz o/p (1) 2uV-200mV (2) with terminating unit 1uV-100mV Int. mod. freqs 400Hz, 1KHz & 1.5KHz Distortion (1) on internal F.M. ±25Hz (2) on internal A.M. 6% at 30% mod. £300 to £450  
A.M. Signal Generator TF801D/1 Freq. range 10-470MHz R.F. output 0.1uV-1V Piston attenuator. 50ohms Impedance. Modulation Int. A.M. 1KHz Ext. A.M. 30Hz-20KHz Low spurious F.M. & drift V.S.W.R. 1.2 or less £400-£800  
A.M. Signal Generator TF801D/1S Military version 10-485MHz £450-£800  
R.C. Oscillator TF1370A 10Hz-10MHz Square Wave up to 100KHz High Outputs up to 31 V £235  
Phase/A.M. Signal Generator TF 2003 0.4-12MHz £150  
A.M. Signal Generator TF 8018/3S. 12.485MHz 0.1uV-1V £195  
R.C. Oscillator TF1101 Frequency range 20Hz-200KHz Output Direct into 600Ω/20V variable Attenuator 0.6dB in 10dB steps Impedance 600Ω Distortion Via 1KHz Filter less than 0.1%. Direct or via Attenuator Less than 0.5% 50Hz-20KHz Less than 1% 20Hz-200KHz £120-£150  
F.M./A.M. Signal Generator TF937/1 CT320 35KHz-18.3MHz As seen condition. £80  
Signal Generator TF144M/4 Late models in super condition. £500 to £650  
TF995B/5 A.M./F.M. Signal Generator 200KHz-220MHz Narrow deviation model for mobile radio testing. 3 mod. trans. £675.00

**MARCONI-SANDERS**  
Microwave Sweep Generator type 6800A c/w 6619 in 1.7GHz-4.2GHz £2900.00  
**MURHEAD LF** Decade Oscillator D880A, 2-phase 0.01Hz-11.2KHz £295  
Decade Oscillator D890D 1Hz-11.2KHz £260

**NEUWIRTH (WEST GERMANY)**  
VHF Signal Generator M54/U Freq. Range 9.6MHz to 230MHz Turret Osc. for each band Accuracy 1.2% o/p 30mV-1uV Freq. Dev. 1KHz-100KHz Amp. Mod. 0-100% £175.00

**PHILIPS**  
PM 5167 Function Generator Sine, triangle square, positive pulse, negative pulse and ramp 9.0 and 1.9 0.001 Hz to 10MHz (sawtooth) and pulse up to max 1MHz Output 40V(P-P) Impedance 50 ohms Variable DC Offset External sweep Single shot set phase Hold function Overrange warning light Superb condition £615.00

Electronic Brokers Ltd. are one of the leading electronic instrumentation companies in the UK, providing a full range of services to Universities, Industry, Colleges and Governments both at home and overseas.

We have the largest stocks of secondhand test equipment in Europe as well as a selected range of new products. These are on display at our London showrooms where customers can examine the equipment of their choice and see it working.

Electronic Brokers Ltd. have fully equipped workshops on the premises to test and report on the majority of equipment we sell.



# WRITE NOW...

for a FREE copy of our latest Test Equipment Catalogue. Please apply on headed paper.

**PM5501** Colour bar generator. Extremely light and compact instrument for mobile maintenance. 5 different test patterns for colour and black/white TV installation and service. R.F. output signal switchable VHF, Band III and UHF Band IV. 1KHz tone for sound performance checks (sine wave) £165.00  
50MHz Pulse Generator PM5712 £435.00  
Pulse Generator PM5775 £800.00  
Pulse Generator PM5776 £900.00

**SANDERS**  
CT478 Microwave Signal Generator 1.5GHz-4.5GHz £285.00

**RHODE & SCHWARTZ**  
S.H.F. generator SMCB-8N 41042 1700-5000MHz P.O.A.

**WAYNE KERR**  
Video Oscillator O 222, 7KHz-8KHz in 6 ranges. £75

**WANDEL & GOLTERMAN**  
U.H.F. Power Oscillator LMS-68 c/w plug in Oscillators:  
Type LU-4 4.41MHz  
Type LO-40 40-108MHz  
Type LD-170 170-330MHz  
Type LD-610 610-960MHz

## MULTIMETERS

**AVO**  
Test Leads £4.00  
Multimeter Mk. 4 c/w carrying case & leads £13.50

## OSCILLOSCOPES

**DYNAMCO**  
Type 7200 15MHz Dual Channel Portable c/w Plug Ins 7201 & 7212. Solid State. 10mV/div to 5V/div. X10 on channel 1 permits 1mV/div to 12.5V/div Calibrated Sweep Delay c/w bait pack £310.00

**GREENPAR**  
Probe Kits GE81600/1 - New £25.00

**HEWLETT PACKARD**  
175A 50MHz Oscilloscope, c/w Plug-ins. 1750B Dual Trace Vert. Amp. 50mV/cm 1780A Auxiliary Plug-in £295.00  
185B 1000 MHz Oscilloscope Sampling c/w Plug-in 188A or Plug-in 187C £395.00

**PHILIPS**  
15MHz Portable double scope PM3226 £380.00

**SOLARTRON**  
Portable Scope DC-6MHz Double Beam CT436 £105  
Portable Scope CD 1400DC-15MHz Plug ins available CX1441, 1443, 1448 1571 £180

**TEKTRONIX**  
Sampling Scope 661 c/w plug ins £450  
Scope Camera C-12. Superb cond. & complete £190.00  
50MHz Model 546 c/w 1A1 plug-in £635.00  
50MHz Model 547 c/w 1A1 plug-in £695.00

TV Waveform Monitor S25 Freq. response Flat - within 1% between 60Hz & 5MHz. Low Pass - Passes stair steps, eliminates H.F. High Pass - Passes H.F. eliminates stair steps. IRE - meets IRE standards for level measurements. Sensitivity - Deflection factor of the vertical amplifier is 0.015V/cm Vert. Att. - 1x, 2x, 5x Keyed Clamp-type DC. Restorer Gain stability within 1% £125

Differential Unit 10A1 Used on 647 Series £300  
585 c/w Type 82 Plug-in Dual Trace 80MHz B width Sweep Delay. £750. Other plug-ins available 80 and 86

Transistor Curve Tracer 575. Displays curves of NPN & PNP transistors and dynamic characteristics of a wide range of semiconductor devices. P.O.A.

Dual Beam Scope 551. 2 vertical deflection systems. Accepts Amp. Spect. analyser. Sampling and special purpose Plug-ins DC-27MHz Price dependent on plug-ins required P.O.A.

531A DC-15MHz Oscilloscope c/w K Plug-in Single Trace 50mV/cm £195.00

531A 15MHz Oscilloscope c/w CA Plug-in Dual Trace 50mV/cm £210.00

544 DC-50MHz Oscilloscope c/w 1A4 Plug-in (4 trace) £600.00

544 DC-50MHz Oscilloscope c/w CA Plug-in, Dual Trace. 24MHz, 50mV/cm £375.00

549 Storage Oscilloscope (Mainframe) £610.00

**TELEQUIPMENT**  
D33R Oscilloscope min sensitivity 10mV div DC-6MHz £115.00  
D43 Oscilloscope £125.00

**WANDEL & GOLTERMANN**  
BLS 218 Storage Oscilloscope c/w Power Supply £325.00

**PRDBES (New)**  
X1 Part No 90 £6.50  
X10 Part No 91 £8.50  
X1 & X10 (switchable) Part No 95 £10.50

## MISCELLANEOUS

**ADVANCE**  
Frequency Counter TC16 £110.00  
Recorder Calibrator HC20 £15  
X-Y Plotter LR100 - Further details on request £325.00

Digital Panel Meter DPM302 (new) £45.00  
Digital Panel Meter DPM301 (new) £50.00

**AIRMEC**  
Time Interval Meter 369. Mains operated transistorised unit. Time Intervals 100nsecs to 30msecs Superb condition £95.00

**BECKMAN**  
Transfer Oscillator 7580H DC-15GHz with counter 7.5MHz-15GHz without counter. Sensitivity 100mV (R.M.S.) SPECIAL OFFER £250

**B & K**  
Deviation Bridge 1504 P.O.A.

**BIRD**  
Coaxial Resistor 8053 10W RF coaxial load resistor £20.00

Wattmeter Terminal 6835 3 ranges 0-120/0-600/0-1200W 30-500MHz £425.00

Wattmeter Terminal 67 3 ranges 0-25/0-100/0-500W 30-500MHz £265.00

**B.P.L.**  
Component Comparator C2457 5 P.O.A.

**BRUEL & KJAER**  
Automatic Vibration Exciter Control 1018 £395.00

**DECCA**  
Power Supply for Noise Source MW 61 P.O.A.

the test

**FLUKE**  
Industrial Counter/Totaliser 1941A Freq. Measurement 5Hz-40MHz 40mV sensitivity Totalise measurements to 999999 units Presettable display RPM measurement £150.00

**HEWLETT PACKARD**  
Digital Recorder 560A £110  
Digital Recorder 561B £140  
Directional detector 787D 1.9-4.1GHz £90  
Directional detector 788C 3.7-8.3GHz £95  
UHF Attenuator 355C £90

**HOUSTON**  
XY Omnidirectional Recorder type 6520 P.O.A.  
XY & YXY Omnidirectional Recorder type 6462 P.O.A.

**MARCONI INSTR.**  
Attenuator TF 1073A/2S £85  
Quantization Distortion Tester TF2343 P.O.A.

Probe Kit TM8120/1x1 for use with valve voltmeter TF2600 Brand new £20

A.F. Power Meter TF893A 20Hz-20KHz 1mW to 10 Watts F.S. Z = 25 ohms to 20Kohms in 48 Steps £150.00

Out of Limits Indicator TF 2404/2M1 Checks readings from electronic counters and other digital insts. Local and remote visual and electrical indication suitable for use by unskilled personnel and with A.T.E. P.O.A.

Blank & Sync Mixer TF 2908 £90

**RHODE & SCHWARTZ**  
Polyscop Swob II £1000  
Selektomat USWW £835.00  
Frequency Indicator FKN-BN 47051 £475

**TEKTRONIX**  
Programmer 262 P.O.A.

Sq. Wave Gen 105 Risetme - 13m secs Freq

# ELECTRONIC

49-53 Pancras Road  
London NW11 2QB  
Tel: 01-837 7781

ADD 8% VAT TO ALL PRICES

# BROKERS LTD

equipment people

On these pages you will find just the briefest selection from the vast range which we hold in stock at any one time.

If you are seeking a specific item and it is not listed, it will pay you to ring us first — we believe we offer the best prices and the best service.

**WORLD WIDE EXPORT**

Enquiries and tenders welcome from any part of the world.  
**HOW TO REACH US . . .**

We are easy to reach, no matter where you live. Minutes away from Kings Cross or St. Pancras main-line stations, and a bus ride from Euston; only just over half an hour from Heathrow Airport.

49-53  
Pancras Rd  
London  
NW1 2QB  
Telephone:  
01-837 7781



3590A Wave Analyser. Freq. range 20Hz to 620KHz **£650.00**  
**MARCONI INSTS.**  
Distortion Factor Meter TF 142F. Fundamental Freq. Range 100Hz-8KHz Dist. measuring ranges 0.5% 0.50% Measures all spurious components up to 30KHz **£80.00-£80.00**

## TELEPHONE TEST EQUIPMENT

**SIEMENS**  
Level Meter 3D 332 0.3-1200KHz **£250**  
Level Meter 3D 335 10KHz-17MHz **£300**  
Level Oscillator 3W29 0.3-1200KHz **£250**  
Level Oscillator 3W518 **£300**

## BRIDGES

**MARCONI INST.**  
TF936 Impedance Bridge **£125.00**  
Universal Bridge TF1313A **£525**  
LCR Bridge TF 868B **£115.00**  
TF1245 C.T Magn. Meter c/w Oscillator **£685.00**  
TF1246 **£685.00**

**WAYNE KERR**  
Radio Freq. Bridge B601 **£95**  
R.F. Admittance Bridge B701 **£85**

**COMPONENT BRIDGE B521 (CT 375)**  
Self-contained portable mains operated equipment designed to provide accurate measurements over an extremely wide range of resistance, capacitance, inductance and impedance values. Resistance 10 ranges from 1m ohm to 1000 M ohm. Capacitance 10 ranges from 50kaf to 500pF Inductance 10 ranges from 1µF to 500 KH Capable of measuring components in situ. **£105.00**

**A.F. TRANSMISSION MEASURING SET, Model TF2332** Frequency Range 20Hz to 20KHz Accuracy, ±1% 0.2Hz **£105.00**

**RADIOMETER**  
Wave Analyser FRA 2 T3 Special version of FRA 2 with facilities for intermodulation measurements and selective measurements of frequency responses. Freq. range 30Hz to 16KHz Incremental freq. 0Hz to ±60Hz Selectivity 3 curves with following 1dB points ±1.25Hz ±12.5Hz ±63Hz and 60dB points ±40Hz ±130 Hz ±350 Hz ±150 Hz ±450 Hz

Voltage range 100µV - 1KV Auxiliary Oscillator 0/p level 0.5mV - 2.5VFSO Lowest adjustable 50µV (EMF) continuously variable. Impedance 1 Kohms 16µF **£375.00**

**WANDEL & GOLTERMAN**  
Level Transmitter TFPS.42, 10 KHz-14MHz Generator 0/p level 0.5mV - 2.5VFSO Lowest adjustable 50µV. Synchronous tuning of generator and level meter possible. Output impedance 150, 75, 70, 60, 50 and ohms ±25KHz. Fine Tuning range **£250.00**  
Level Meter TFSM - 43, 10KHz-14MHz, 3dB Bandwidth (600Hz and 4KHz) Selective measuring range 8V to 40µV (lowest readable 2µV). Switchable

**VIVM.4000** fmv to 300V FSD 12 ranges 10Hz to 4MHz. 2% accuracy. Input Impedance 10Mohms **£85**  
**VIVM. 400L** Logarithmic version of 400D Reads RMS value of sine wave. Log. voltage scale 0.3 to 1 & 0.8 to 3. Linear dB scale. Input Impedance 10Mohms **£90**  
**Vacuum Tube Voltmeter 400H** Freq. Range 10Hz-4MHz Volts: 1.0mV-300V F.S. (12 ranges) Accuracy ±1% (50Hz-500KHz) **£155**  
**AC Voltmeter 400F & 400E** **£155**  
**Broad Band Sampling Voltmeter 3406A** **£495.00**  
**MARCONI**  
Sensitive Valve Voltmeter TF 1100. 100µV-300V AC. Freq. coverage 10Hz-10MHz. Meter has dB scale facility **£88**  
Valve Voltmeter TF.1041B General Spec. 0-300V AC. 0-1KV DC Resistance up to 500Mohms. **£80/£95**  
Electronic Voltmeter TF2604 **£225.00**  
Voltmeter No 3 CT.208 TF 95B. AC 100mV-150V. multiplier extends AC range to 15KV. DC 50mV-100V Freq. Range 20Hz-100MHz **£55**  
Valve Voltmeter TF2600 **£175**

**PHILIPS**  
H.F. Millivoltmeter GM 6014 Measuring Ranges 1mV-300mV in 6 ranges. Accuracy at 30KHz at 3% of FSD = Amplitude Char. 1KHz-30KHz flat within ±5%. **£55**  
DC Microvoltmeter GM6020. 10µV-1KV current 10pA-10µA Accuracy 5% (FSD) 0-100µV 3% (FSD) AU other ranges Recorder o/p facility **£65**

## TRANSMISSION TEST EQUIPMENT

**AIRMEC/RACAL**  
Wave Analyser 24BA. 5-300MHz. **£250 to £300**  
Wave Analyser 24B Freq. range 5MHz-300MHz **£145.00**  
Modulation Meter 409 **P.O.A.**  
Type 210 Modulation Meter (earlier version of 210A) **£85-£100**  
Type 210A Modulation Meter 2.5-300 MHz. A.M. Range D-100%. F.M. Range 0 to ±100 KHz in 4 ranges **£185-£245**

**HEWLETT PACKARD**  
Sweeping Local Oscillator 3595A Plug-in for use with

bandwidth ±15KHz fine tuning. High sensitivity. Full specification for the above on request **£250.00**  
Distortion Meter VZM.83. 62/304/556 KHz. This unit, comprises a generator and receive portion and operates according to the intermodulation method. This distortion measuring set is mainly used to measure transmission distortions occurring on FM radio link systems **£190.00**  
VZM2 Distortion measuring set for phase and amplitude mod. For multichannel FM Radio Systems up to 12MHz base bands **£350**

## DIGITAL VOLTMETERS AND MULTIMETERS

**DYNAMCO**  
D.V.M. DM 2022S 10µV-2KV Max reading 39999 Accuracy 0.02% Resolution 1 in 40,000 Input impedance 25KMohms **£265.00**  
Digital Voltmeter DM 2023. C/w DC Ranging unit C1 Scale 99999. 0.001%. F.S.O. DC Accuracy 10µV-1Kv DC **£450.00**  
D.V.M. DM 2004 **P.O.A.**  
**J. FLUKE**  
Digital Multimeter 8120A. Measures AC and DC volts to 1200 volts. AC and DC current to 1.2A. Resistance to 12Kohm, 4 digit plus 20% overrange. Compact and lightweight **£235.00**

**HEWLETT PACKARD**  
DVM type 3430A. 3 digit. 5 ranges 100mV to 100V F.S. Input resistance 10Mohms. Overload protection **£145.00**

Digital Multimeter 34702A with Display 34740A. 4 digit display. 4 ranges both AC & DC plus 6 ranges of ohms. AC function covers 45Hz to 100KHz. Ohms ranges are 100ohms to 10Mohms F.S. LED display. New condition. A much sought after device still in current production **£400**

**PHILIPS**  
D.M.M. TYPE PM2423 3 1/2 digit, DC Volts 2V-1 KV AC VOLTS 2V-350V. R=200 ohms - 200 M.ohms. Accuracy 0.1% of reading. Automatic range switching for all functions. Automatic polarity indicator **£140.00**  
D.M.M. TYPE PM2522, 3 1/2 digit, DC Volts 0.2-1KV, AC Volts 0.2-600V. AC/DC Current 0.2mA-2A, R = 200 ohms - 20 M.ohms Accuracy 0.1% ± 0.1% of range DC Volts. Full circuit protection. LED display **£150.00**

**SIGN/ROGERS**  
A.F. Voltmeter AM324 **£50.00**  
**SOLARTRON**  
A.C. Converter LM1219. 30mV-300V mean reading. Freq. range 10Hz-10KHz **P.O.A.**  
D.C. Digital Voltmeter LM1420.2, 2.5µV-1Kv in 6 ranges. 0.05% DC accuracy **£235.00**  
O.V.M. Type LM1420.2Ba DC, true R.M.S. and mean A.C. sensing. Accurate measurement irrespective of harmonic distortion accuracy ±0.25%. Freq. 10Hz-20KHz **£325**  
DVM Type LM 1440.2. 10µV-2Kv DC in 5 ranges. Oven controlled zenerdiode. Accuracy ±0.033% FSD ±0.005% reading **P.O.A.**  
D.V.M. LM 1460.3. Autorangeing version of LM 1440.3. Max reading 39999. 5µV-2Kv DC. Full spec on request **P.O.A.**  
O.V.M LM 1604. DC only 1µV sensitivity. 0.01% accuracy Max. reading 1µV-1KV. Remote and Autorangeing. 110dB series mode reject on No common Mode error **P.O.A.**  
D.M.M. 7050 (autorangeing) **£245.00**

**VIDAR**  
Integrating D.V.M. 520. 6 ranges 10mV-1KV. Guarded can be floated to ±500V High measurement speed with ultimate C.M.R. No filters. Up to X6 faster than most integrating D.V.M.'s. Built-in calibrator. Manual, automatic and remote operation Wideband freq. and period measurements are standard. 10mV F.S. range built-in, eliminates ext. pre-amp., no loss of C.M.R. Freq. range 10Hz-2MHz **£525.00**

## REMEMBER We also buy

We are interested in providing quotations for the purchase of good quality used and unused Test Equipment.

Shown on these pages are just a few samples of our huge stock. If the item you require is not shown please give us a ring.

# BROKERS LTD

Carriage and packing charge extra on all items unless otherwise stated

Please note: All instruments offered are secondhand and tested and guaranteed 12 months unless otherwise stated

# AMATEUR COMPONENTS

## ORCHARD WORKS, CHURCH LANE, WALLINGTON, SURREY SM6 7NF

MAIL ORDER DIVISION OF SEMICONDUCTOR SUPPLIES (CROYDON) LTD.

### For Semiconductors Capacitors Resistors 1/C Sockets L.E.D.'s and

|        |     |        |    |        |    |        |    |        |    |       |    |       |      |        |     |         |      |         |     |         |    |
|--------|-----|--------|----|--------|----|--------|----|--------|----|-------|----|-------|------|--------|-----|---------|------|---------|-----|---------|----|
| AC125  | 20  | BC108B | 12 | BC173  | 15 | BC212L | 15 | BC307A | 16 | BCY58 | 22 | BU133 | 1.95 | TIP31A | 57  | 2N1671  | 1.50 | 2N3638A | 16  | 2N4304  | 44 |
| AC126  | 20  | BC108C | 13 | BC173A | 16 | BC212L | 15 | BC307B | 16 | BCY70 | 17 | BU205 | 2.00 | TIP31B | 64  | 2N1671A | 1.80 | 2N3641  | 17  | 2N4410  | 50 |
| AC127  | 20  | BC109  | 13 | BC173B | 16 | BC212L | 15 | BC307C | 16 | BCY71 | 18 | BU208 | 2.45 | TIP31C | 79  | 2N1671B | 1.90 | 2N3642  | 17  | 2N4416  | 70 |
| AC127K | 30  | BC109B | 13 | BC173C | 16 | BC212L | 15 | BC308  | 12 | BCY72 | 14 | BU273 | 3.00 | TIP32  | 60  | 2N1711  | 3.00 | 2N3643  | 17  | 2N4416E | 40 |
| AC128  | 18  | BC109C | 14 | BC174  | 16 | BC212L | 15 | BC308  | 12 | BCY73 | 15 | BU274 | 3.00 | TIP32A | 67  | 2N1889  | 34   | 2N3644  | 18  | 2N4871  | 50 |
| AC128K | 26  | BC113  | 12 | BC177  | 17 | BC212L | 15 | BC308  | 12 | BCY74 | 14 | BU274 | 3.4  | TIP32B | 76  | 2N1890  | 34   | 2N3645  | 18  | 2N5126  | 18 |
| AC132  | 35  | BC114  | 15 | BC177A | 17 | BC212L | 15 | BC308A | 14 | BD115 | 60 | BF336 | 3.2  | TIP32C | 94  | 2N1893  | 28   | 2N3646  | 17  | 2N5127  | 19 |
| AC141  | 20  | BC115  | 15 | BC177B | 18 | BC212L | 15 | BC308B | 14 | BD121 | 90 | BF337 | 3.3  | TIP33  | 84  | 2N1990  | 58   | 2N3681  | 16  | 2N5128  | 16 |
| AC141K | 20  | BC115B | 15 | BC177C | 19 | BC212L | 15 | BC308C | 14 | BD122 | 90 | BF338 | 3.4  | TIP33A | 94  | 2N1990  | 58   | 2N3682  | 17  | 2N5129  | 17 |
| AC142  | 25  | BC116A | 15 | BC178A | 18 | BC212L | 15 | BC308C | 15 | BD123 | 90 | BF339 | 3.4  | TIP33B | 105 | 2N2102  | 90   | 2N3693  | 17  | 2N5131  | 17 |
| AC142K | 25  | BC117  | 18 | BC178B | 18 | BC212L | 15 | BC309  | 16 | BD131 | 42 | BF340 | 3.6  | TIP33C | 131 | 2N2192  | 40   | 2N3694  | 17  | 2N5132  | 17 |
| AC151  | 24  | BC118  | 10 | BC178C | 18 | BC212L | 15 | BC309B | 16 | BD132 | 42 | BF341 | 3.6  | TIP33D | 131 | 2N2192A | 40   | 2N3702  | 11  | 2N5133  | 17 |
| AC151K | 34  | BC119  | 28 | BC179  | 19 | BC212L | 15 | BC309C | 16 | BD133 | 65 | BF342 | 3.6  | TIP34  | 100 | 2N2193  | 35   | 2N3703  | 14  | 2N5135  | 18 |
| AC153  | 27  | BC125  | 16 | BC179B | 19 | BC212L | 15 | BC310  | 16 | BD134 | 65 | BF343 | 3.6  | TIP34A | 113 | 2N2194  | 35   | 2N3704  | 14  | 2N5136  | 18 |
| AC153K | 37  | BC126  | 20 | BC179C | 19 | BC212L | 15 | BC311  | 16 | BD135 | 65 | BF344 | 3.6  | TIP34B | 126 | 2N2195  | 35   | 2N3705  | 14  | 2N5137  | 18 |
| AC176  | 22  | BC128  | 25 | BC182  | 11 | BC212L | 15 | BC312  | 16 | BD136 | 65 | BF345 | 3.6  | TIP34C | 159 | 2N2196  | 35   | 2N3706  | 14  | 2N5139  | 17 |
| AC176K | 26  | BC132  | 14 | BC182A | 12 | BC212L | 15 | BC313  | 16 | BD137 | 65 | BF346 | 3.6  | TIP34D | 159 | 2N2197  | 35   | 2N3707  | 14  | 2N5141  | 16 |
| AC187  | 22  | BC134  | 14 | BC182B | 12 | BC212L | 15 | BC314  | 16 | BD138 | 65 | BF347 | 3.6  | TIP35  | 237 | 2N2198  | 35   | 2N3708  | 11  | 2N5143  | 16 |
| AC187K | 27  | BC135  | 14 | BC182C | 12 | BC212L | 15 | BC315  | 16 | BD139 | 65 | BF348 | 3.6  | TIP35A | 261 | 2N2199  | 35   | 2N3709  | 15  | 2N5183  | 34 |
| AC188  | 20  | BC136  | 16 | BC182D | 12 | BC212L | 15 | BC316  | 16 | BD140 | 65 | BF349 | 3.6  | TIP35B | 280 | 2N2200  | 35   | 2N3710  | 11  | 2N5172  | 16 |
| AC188K | 27  | BC137  | 16 | BC182E | 12 | BC212L | 15 | BC317  | 16 | BD141 | 65 | BF350 | 3.6  | TIP35C | 320 | 2N2201  | 35   | 2N3711  | 11  | 2N5294  | 50 |
| AD149  | 70  | BC139  | 35 | BC183  | 10 | BC212L | 15 | BC318  | 16 | BD142 | 65 | BF351 | 3.6  | TIP35D | 320 | 2N2202  | 35   | 2N3712  | 210 | 2N5298  | 50 |
| AD162  | 92  | BC140  | 30 | BC183A | 10 | BC212L | 15 | BC319  | 16 | BD143 | 65 | BF352 | 3.6  | TIP35E | 320 | 2N2203  | 35   | 2N3713  | 210 | 2N5299  | 50 |
| AF114  | 24  | BC141  | 32 | BC183B | 10 | BC212L | 15 | BC320  | 16 | BD144 | 65 | BF353 | 3.6  | TIP35F | 320 | 2N2204  | 35   | 2N3714  | 210 | 2N5400  | 52 |
| AF115  | 24  | BC142  | 22 | BC183C | 10 | BC212L | 15 | BC321  | 16 | BD145 | 65 | BF354 | 3.6  | TIP35G | 320 | 2N2205  | 35   | 2N3715  | 210 | 2N5401  | 52 |
| AF116  | 24  | BC143  | 28 | BC183D | 10 | BC212L | 15 | BC322  | 16 | BD146 | 65 | BF355 | 3.6  | TIP35H | 320 | 2N2206  | 35   | 2N3716  | 210 | 2N5402  | 52 |
| AF117  | 24  | BC147  | 10 | BC183E | 10 | BC212L | 15 | BC323  | 16 | BD147 | 65 | BF356 | 3.6  | TIP35I | 320 | 2N2207  | 35   | 2N3717  | 210 | 2N5403  | 52 |
| AF118  | 70  | BC147A | 11 | BC183F | 10 | BC212L | 15 | BC324  | 16 | BD148 | 65 | BF357 | 3.6  | TIP35J | 320 | 2N2208  | 35   | 2N3718  | 210 | 2N5404  | 52 |
| AF124  | 30  | BC147B | 11 | BC184  | 11 | BC212L | 15 | BC325  | 16 | BD149 | 65 | BF358 | 3.6  | TIP35K | 320 | 2N2209  | 35   | 2N3719  | 210 | 2N5405  | 52 |
| AF125  | 30  | BC148  | 08 | BC184B | 12 | BC212L | 15 | BC326  | 16 | BD150 | 65 | BF359 | 3.6  | TIP35L | 320 | 2N2210  | 35   | 2N3720  | 210 | 2N5406  | 52 |
| AF126  | 28  | BC148A | 08 | BC184C | 12 | BC212L | 15 | BC327  | 16 | BD151 | 65 | BF360 | 3.6  | TIP35M | 320 | 2N2211  | 35   | 2N3721  | 210 | 2N5407  | 52 |
| AF127  | 28  | BC148B | 08 | BC184D | 12 | BC212L | 15 | BC328  | 16 | BD152 | 65 | BF361 | 3.6  | TIP35N | 320 | 2N2212  | 35   | 2N3722  | 210 | 2N5408  | 52 |
| AF139  | 34  | BC148C | 09 | BC184E | 12 | BC212L | 15 | BC329  | 16 | BD153 | 65 | BF362 | 3.6  | TIP35O | 320 | 2N2213  | 35   | 2N3723  | 210 | 2N5409  | 52 |
| AF178  | 120 | BC149  | 10 | BC184F | 12 | BC212L | 15 | BC330  | 16 | BD154 | 65 | BF363 | 3.6  | TIP35P | 320 | 2N2214  | 35   | 2N3724  | 210 | 2N5410  | 52 |
| AF179  | 120 | BC149B | 12 | BC186  | 25 | BC212L | 15 | BC331  | 16 | BD155 | 65 | BF364 | 3.6  | TIP35Q | 320 | 2N2215  | 35   | 2N3725  | 210 | 2N5411  | 52 |
| AF180  | 120 | BC149C | 12 | BC187  | 26 | BC212L | 15 | BC332  | 16 | BD156 | 65 | BF365 | 3.6  | TIP35R | 320 | 2N2216  | 35   | 2N3726  | 210 | 2N5412  | 52 |
| AF181  | 120 | BC153  | 18 | BC204  | 15 | BC212L | 15 | BC333  | 16 | BD157 | 65 | BF366 | 3.6  | TIP35S | 320 | 2N2217  | 35   | 2N3727  | 210 | 2N5413  | 52 |
| AF186  | 120 | BC154  | 18 | BC204A | 16 | BC212L | 15 | BC334  | 16 | BD158 | 65 | BF367 | 3.6  | TIP35T | 320 | 2N2218  | 35   | 2N3728  | 210 | 2N5414  | 52 |
| AF239  | 37  | BC157  | 11 | BC204B | 16 | BC212L | 15 | BC335  | 16 | BD159 | 65 | BF368 | 3.6  | TIP35U | 320 | 2N2219  | 35   | 2N3729  | 210 | 2N5415  | 52 |
| ASY26  | 40  | BC157A | 12 | BC205  | 15 | BC212L | 15 | BC336  | 16 | BD160 | 65 | BF369 | 3.6  | TIP35V | 320 | 2N2220  | 35   | 2N3730  | 210 | 2N5416  | 52 |
| ASY27  | 45  | BC157B | 12 | BC205A | 15 | BC212L | 15 | BC337  | 16 | BD161 | 65 | BF370 | 3.6  | TIP35W | 320 | 2N2221  | 35   | 2N3731  | 210 | 2N5417  | 52 |
| ASY28  | 40  | BC158  | 10 | BC205B | 15 | BC212L | 15 | BC338  | 16 | BD162 | 65 | BF371 | 3.6  | TIP35X | 320 | 2N2222  | 35   | 2N3732  | 210 | 2N5418  | 52 |
| ASY29  | 45  | BC158A | 11 | BC205C | 15 | BC212L | 15 | BC339  | 16 | BD163 | 65 | BF372 | 3.6  | TIP35Y | 320 | 2N2223  | 35   | 2N3733  | 210 | 2N5419  | 52 |
| ASY67  | 140 | BC158B | 11 | BC205D | 15 | BC212L | 15 | BC340  | 16 | BD164 | 65 | BF373 | 3.6  | TIP35Z | 320 | 2N2224  | 35   | 2N3734  | 210 | 2N5420  | 52 |
| ASZ21  | 200 | BC159  | 12 | BC206  | 16 | BC212L | 15 | BC341  | 16 | BD165 | 65 | BF374 | 3.6  | TIP36  | 320 | 2N2225  | 35   | 2N3735  | 210 | 2N5421  | 52 |
| BA145  | 15  | BC159B | 13 | BC207  | 16 | BC212L | 15 | BC342  | 16 | BD166 | 65 | BF375 | 3.6  | TIP36A | 320 | 2N2226  | 35   | 2N3736  | 210 | 2N5422  | 52 |
| BA148  | 15  | BC159C | 13 | BC207A | 16 | BC212L | 15 | BC343  | 16 | BD167 | 65 | BF376 | 3.6  | TIP36B | 320 | 2N2227  | 35   | 2N3737  | 210 | 2N5423  | 52 |
| BA154  | 10  | BC167  | 13 | BC207B | 16 | BC212L | 15 | BC344  | 16 | BD168 | 65 | BF377 | 3.6  | TIP36C | 320 | 2N2228  | 35   | 2N3738  | 210 | 2N5424  | 52 |
| BA155  | 12  | BC168  | 12 | BC208  | 16 | BC212L | 15 | BC345  | 16 | BD169 | 65 | BF378 | 3.6  | TIP36D | 320 | 2N2229  | 35   | 2N3739  | 210 | 2N5425  | 52 |
| BA156  | 13  | BC169  | 14 | BC208A | 16 | BC212L | 15 | BC346  | 16 | BD170 | 65 | BF379 | 3.6  | TIP36E | 320 | 2N2230  | 35   | 2N3740  | 210 | 2N5426  | 52 |
| BA157  | 11  | BC170  | 11 | BC208B | 16 | BC212L | 15 | BC347  | 16 | BD171 | 65 | BF380 | 3.6  | TIP36F | 320 | 2N2231  | 35   | 2N3741  | 210 | 2N5427  | 52 |
| BAK13  | 07  | BC171  | 14 | BC208C | 11 | BC212L | 15 | BC348  | 16 | BD172 | 65 | BF381 | 3.6  | TIP36G | 320 | 2N2232  | 35   | 2N3742  | 210 | 2N5428  | 52 |
| BAK16  | 07  | BC171A | 14 | BC209  | 12 | BC212L | 15 | BC349  | 16 | BD173 | 65 | BF382 | 3.6  | TIP36H | 320 | 2N2233  | 35   | 2N3743  | 210 | 2N5429  | 52 |
| BC107  | 12  | BC171B | 15 | BC209B | 13 | BC212L | 15 | BC350  | 16 | BD174 | 65 | BF383 | 3.6  | TIP36I | 320 | 2N2234  | 35   | 2N3744  | 210 | 2N5430  | 52 |
| BC107A | 12  | BC172  | 14 | BC209C | 13 | BC212L | 15 | BC351  | 16 | BD175 | 65 | BF384 | 3.6  | TIP36J | 320 | 2N2235  | 35   | 2N3745  | 210 | 2N5431  | 52 |
| BC107B | 15  | BC172A | 14 | BC209D | 13 | BC212L | 15 | BC352  | 16 | BD176 | 65 | BF385 | 3.6  | TIP36K | 320 | 2N2236  | 35   | 2N3746  | 210 | 2N5432  | 52 |
| BC108  | 11  | BC172B | 15 | BC210  | 13 | BC212L | 15 | BC353  | 16 | BD177 | 65 | BF386 | 3.6  | TIP36L | 320 | 2N2237  | 35   | 2N3747  | 210 | 2N5433  | 52 |
| BC108A | 11  | BC172C | 15 | BC210B | 13 | BC212L | 15 | BC354  | 16 | BD178 | 65 | BF387 | 3.6  | TIP36M | 320 | 2N2238  | 35   | 2N3748  | 210 | 2N5434  | 52 |
| BC108B | 11  | BC172D | 15 | BC210C | 13 | BC212L | 15 | BC355  | 16 | BD179 | 65 | BF388 | 3.6  | TIP36N | 320 | 2N2239  | 35   | 2N3749  | 210 | 2N5435  | 52 |
| BC108C | 11  | BC172E | 15 | BC210D | 13 | BC212L | 15 | BC356  | 16 | BD180 | 65 | BF389 | 3.6  | TIP36O | 320 | 2N2240  | 35   | 2N3750  | 210 | 2N5436  | 52 |
| BC108D | 11  | BC172F | 15 | BC210E | 13 | BC212L | 15 | BC357  | 16 | BD181 | 65 | BF390 | 3.6  | TIP36P | 320 | 2N2241  | 35   | 2N3751  | 210 | 2N5437  | 52 |
| BC108E | 11  | BC172G | 15 | BC210F | 13 | BC212L | 15 | BC358  | 16 | BD182 | 65 | BF391 | 3.6  | TIP36Q | 320 | 2N2242  |      |         |     |         |    |

|  |  |  |   |
|--|--|--|---|
| <p><b>MARCONI TF675F WIDE RANGE PULSE GENERATOR</b><br/>+/- variable outputs up to 50V. Optional delay. Small compact unit <b>£18 ea.</b></p>  | <p><b>ROYAL INVERTORS</b> manufactured USA. 28V. DC Input. Output 115V AC 400HZ up to 2KVA. Brand new. Crated <b>£12.50 ea.</b></p>                      | <p><b>MARCONI NOISE GENERATOR TF987/1.</b><br/>4 Ranges 0-5; 0-10; 0-15; 0-30. Due to large purchases now priced at <b>£15 ea.</b></p> | <p><b>AVO TRANSISTOR ANALYSER CT446</b><br/>Suitcase style<br/><b>NOW £27.50 each</b></p>   |
| <p><b>FOR THE VDU BUILDER.</b> New stock of Large Rectangular Screen 30 x 20cm tube. Type M38 at the ridiculous price of <b>£4 each.</b> And also still available the CME1220, 24 x 15cm at <b>£9 ea.</b> Base connections for both tubes supplied.</p>  | <p><b>WE ARE BREAKING COMPUTERS</b><br/>UNIVAC/HONEYWELL/ICL 1900 etc.<br/>Boards, Power Supplies, Core Stores are available<br/><b>CALL AND SEE</b></p> |  | <p><b>EDWARDS HIGH VACUUM PUMPS</b><br/>Type 1SC30 @ <b>£55 each.</b> Type ES35 @ <b>£45 each</b><br/>Carriage <b>£2.50</b></p>   |
| <p><b>HONEYWELL MAGNETIC TAPE UNITS</b><br/>Self-contained, complete with heads, magnetic tape, leads, etc.<br/>Tested. Carriage paid <b>£57.50</b></p>  | <p><b>SPOOLS OF 1/2" MAG TAPE</b><br/><b>APPROX. 2000ft</b><br/><b>50p ea. P&amp;P £1 ea.</b></p>  |  | <p><b>COMPRESSOR/VACUUM PUMP</b><br/>Twin Cylinder opposed with Integral 1/2 H.P. 50HZ Single Phase Motor Tested &amp; Checked.<br/>110 Volts models only <b>£15 ea.</b><br/>1/2 H.P. Motor 110V <b>£10 ea.</b></p> |
| <p><b>R&amp;S DIAGRAPH &amp; GENERATOR 3-300MHZ.</b> Very nice condition <b>£440.</b><br/><b>RHODE &amp; SCHWARZ ADMITTANCE METER BN3511.</b> As new <b>£65.</b><br/><b>POLARAD RECEIVER</b> Model FIM-B2. Complete 1-10GHZ <b>£395.</b><br/><b>MARCONI OSCILLATOR</b> TF1101 20HZ-20KHZ. Nice condition. Special price <b>£50.</b><br/><b>MARCONI Wide Range Oscillator</b> TF1370. Freq. range 10HZ to 10MHZ. Sine Wave: 10HZ to 100KHZ. Square Wave. High outputs up to 31.6V. Fantastic value at <b>£90 ea.</b><br/><b>MARCONI ADAPTOR</b> TM6113 for TF2700; TF1313; TF8668B <b>£20 ea.</b><br/><b>AIRMEC 4 trace scope</b> Type 279. Large screen <b>£95.</b><br/><b>MARCONI TF142F DISTORTION FACTOR METER</b> giving percentage distortion on a directly calibrated dial and includes all spurious components up to 30KHZ <b>£32.50 ea.</b><br/><b>MARCONI PORTABLE FREQUENCY METER</b> TF1026/11. 100 to 160MHZ. Very fine condition <b>£25.</b><br/><b>DECCA NAVIGATOR DISPLAY UNIT.</b> Very impressive. <b>£12.50 ea.</b><br/><b>COURTENAY MAJOR Mk.2.</b> 250 joules, 5 outputs. Can be combined — 1250 joules. No heads. <b>£30.</b><br/><b>MARCONI SIGNAL GENERATORS.</b> TF801B from <b>£140;</b> TF801D from <b>£190.</b> Usually available ex stock.<br/><b>MARCONI DEVIATION METER.</b> TF791D <b>£75 ea.</b><br/><b>RHODE &amp; SCHWARZ POWER METER.</b> BNRD-BN2412/50 <b>£50.</b><br/><b>MARCONI RF POWER METER.</b> TF1020A/1 50 ohm <b>£65.</b><br/><b>HEWLETT PICKARD 11 Channel Numerical Printer</b> <b>£30.I.C. TESTER</b> by SCHLUMBERGER. Model TCL232 — tests 741; 709 etc. Dual In lines; flat packs or TO's <b>£65 each.</b><br/><b>AIRMEC MODULATION METER 210</b> <b>£95.</b><br/><b>HILGER &amp; WATTS SPECTROMETER H1170</b> <b>£275.</b><br/><b>RHODE &amp; SCHWARZ Tunable Indicating Amplifier UBM</b> <b>£75.</b><br/><b>TEKTRONIX 180A Time Marker Generator</b> <b>£55.</b><br/><b>S.E. Labs Oscilloscope</b> type 102 <b>£220.</b><br/><b>TEKTRONIX 181 Time Marker Generator</b> <b>£40.</b><br/><b>HEWLETT PICKARD Oscilloscope</b> type 175 DC-50MHZ Double Beam <b>£180</b> with delay amplifier <b>£220.</b><br/><b>GENERAL RADIO PULSE SWEEP &amp; Time Delay Generator</b> type 1391B <b>£120.</b></p> <p><b>SPECTRUM ANALYSER</b> by NELSON ROSS. Plug-in for TEKTRONIX Oscilloscopes 561/506 etc. Freq 0-500KHZ <b>£225.</b></p> <p><b>SOLARTRON</b> CD1212 SB 40 meg <b>£85.</b> DB24meg twice <b>£120.</b> Many other types available.<br/><b>Ex-Ministry OSCILLOSCOPE.</b> CT436 Double beam DC.6MHZ <b>£95 each.</b><br/><b>*TELEPHONES.</b> Post Office style 746. Black or two-tone grey <b>£6.50 ea.</b> Modern style 706. Black or two-tone grey <b>£4.50 ea.</b> P&amp;P <b>75p ea.</b> Old black style <b>£1.50 ea.</b> P&amp;P <b>75p.</b><br/><b>TELEPHONE EXCHANGES.</b> eg 15-way automatic (exchange only) from <b>£95.</b><br/><b>MODERN FANS.</b> 4 1/4 x 4 1/4 x 1 1/2". 240 volts. Superbly quiet. 6 Blades <b>£4.50 ea.</b> P&amp;P <b>75p.</b><br/><b>PAPSTOM</b> model 240V available at <b>£7.50 ea.</b> P&amp;P <b>75p.</b><br/><b>PHOTOMULTIPLIER</b> Type 931A <b>£4 ea.</b> P&amp;P <b>75p.</b> Other types available.<br/><b>*POTENTIOMETERS</b> — All 5p ea. P&amp;P extra. Metal bodied AB Linear. PCB Mount. Brand New. 10K; 100K ganged; 250K ganged; 100K ganged, concentric shafts.<br/><b>*BEEHIVE TRIMMERS</b> 3/30pf. Brand New 10 off <b>40p</b> P&amp;P <b>15p;</b> 100 off <b>£3.50</b> P&amp;P <b>75p.</b> 500off <b>£15</b> P&amp;P <b>£1.25;</b> 1,000 off <b>£25</b> P&amp;P <b>£1.50.</b><br/><b>LARGE RANGE OF ELECTROSTATIC VOLTMEERS.</b> From 0-300V 2" <b>£3,</b> to 20KV Max. General guide 5KV 3 1/2" <b>£5.</b> Thereafter <b>£1 per KV.</b> P&amp;P <b>75p.</b><br/><b>VARIACS</b> 240V input 0-240V output 8A <b>£18 ea.;</b> 20A <b>£30 ea.</b> Carr. <b>£2.50.</b><br/><b>E.H.T. TRANSFORMERS</b> 20KV 2KVA <b>£70 ea.</b> Many other EHT transformers and EHT Capacitors available.<br/><b>DON'T FORGET YOUR MANUALS.</b> S.A.E. with requirements.<br/><b>TUBE</b> type DB7/36 — Replacement for Telecomputings S31 <b>£11 ea.</b> P&amp;P <b>£1.50.</b><br/><b>SEMICONDUCTORS</b> — All at 5p ea.* P&amp;P extra. Guaranteed all full spec. devices. Manufacturer's markings.<br/>BC147; BF197; BC327; 2N4403; BC172B; BC261B; BC251B; BC348B; BC171A/B; 2N3055RCA 40p ea. P&amp;P <b>8p.</b><br/>2N5879 with 2N5881 Motorola 150 Watt Comp. pair <b>£2 pr.</b> P&amp;P <b>15p.</b><br/>*Linear Amp 709 <b>25p ea.</b> P&amp;P <b>8p.</b></p> |  |  |   |

# PICK-A-PACK — 50 PENCE A POUND

FROM OUR "PICK-A-PACK" AREA WEIGH UP YOUR OWN COMPONENTS  
NO RESTRICTIONS ON WHAT YOU TAKE

|  |   |   |
|--|---|---|
| <p><b>SUPERB PROFESSIONAL VDU CASES,</b> size 23" x 16" x 27" on stands. Hammer grey. BRAND NEW<br/>SCHLUMBERGER Surplus <b>£35 each.</b> Carriage <b>£2.50</b></p>  | <p><b>EX-DYNAMCO Oscilloscopes INVERTORS</b><br/>30V Input 6KV Output. Size 2" x 4 1/2" x 1 1/2"<br/>Complete with circuit <b>£10 each.</b> P&amp;P <b>£1</b></p>   |   |
| <p><b>LINE PRINTERS — VARIOUS MODELS</b><br/><b>£100 each.</b> Carriage <b>£15</b><br/>Size approx. 4' 4" x 3' x 4' high</p>   | <p><b>C.D.C. DISK DRIVES</b> complete with electronics, power supply, etc. Fine condition with Disk Pack.<br/><b>£100 each.</b> Carriage <b>£15</b><br/>Size approx 2' x 2' 10" x 3' 5" high</p>  | <p><b>Quantity of CABINETS</b> — Approximately 5ft. 6in. and smaller. Computer types — very smart.<br/>Prices from <b>£4 to £20</b> dependent on size. Carr. <b>£2.50</b></p> |
| <p><b>MINIATURE — OXLEY PATCH PANELS — BRAND NEW</b><br/><b>EX-DYNAMCO</b><br/>10 x 10 complete with pins. <b>£8 each.</b> P&amp;P <b>50p</b></p>  | <div style="display: flex; justify-content: space-between;"> <div data-bbox="529 1395 991 1771"> <p><b>DATA LOGGER</b><br/>by DYNAMCO</p> <p>These are BRAND NEW — not finished — DATA LOGGERS BY DYNAMCO</p> <p>They are completed but for the plug-in boards. The case with hinged lid is quite superb and extremely adaptable. It contains as well as the mother board an equally superb Power Supply with the following voltages +28V; +15V; +5V (2.5A) — this supply is crowbar protected; -5V; -14V; -20V; -24V; -48V and other supplies including auto 110V. This unit supplied in its original cardboard box complete with original manual and must be of serious interest to the professional constructor and anyone considering the construction of a micro processor system. Unit size 7 1/2" high x 19" wide x 23" deep.<br/>Price <b>£45 each.</b> Carriage <b>£2.50</b></p> </div> <div data-bbox="991 1395 1461 1771">  </div> </div> |   |
| <p><b>SURPLUS — BRAND NEW — REPLACEMENT TUBES FOR DYNAMCO 7100 SERIES OSCILLOSCOPES TYPE BRIMAR D13-51GH</b></p> <p>Mesh P.D.A. Transistor Scan Wide Bandwidth 60MHZ + Rectangular 6 x 10cm — 1KV EHT X Sensitivity 15V/CM. Y Sensitivity 6V/CM. Standard heaters. Length 13 1/4".<br/>THIS IS A MUST AS A SPARE FOR THE DYNAMCO 7100 SCOPE OR IDEAL FOR THE HIGH QUALITY TRANSISTOR SCOPE BUILDER<br/>At <b>£65 each.</b> Carriage <b>£2.50</b></p> <p>To Tube purchasers only. Numetal Shields at <b>£2.50</b><br/>ALSO AVAILABLE TUBE TYPE BRIMAR D10-210GH/32 Rectangular 7 x 5cm. Mesh P.D.A. Short 9 1/4". 30MHZ + Sensitivity x 14V/CM. Y 10V/CM. BRAND NEW at <b>£70 each.</b> Carriage <b>£2.50</b></p> | <p><b>APOLLO SCRIBEMASTER</b><br/>PRINTED CIRCUIT BOARD MAKER<br/><b>£425</b></p> <p><b>FRY'S ELECTROVERT WAVESOLDERING MACHINE</b><br/>Type WASL 12 — Complete with Ultrasonic cleaner, Fluxwave applicator, jet blower, etc.<br/><b>£950</b></p>  |   |

Minimum Mail Order **£2.** Excess postage refunded. Unless stated — please add **£2.50** carriage to all units  
**VALUE ADDED TAX** not included in prices — Goods marked with \* **12 1/2 % VAT,** otherwise **8 %**  
Official Orders Welcomed. Gov./Educational Depts., Authorities, etc., otherwise Cash with Order  
Open 9 a.m. to 5.30 p.m. Mon. to Sat.



# CHILTMHEAD LTD



7/9 ARTHUR ROAD, READING, BERKS (rear Tech. College, King's Road). Tel. Reading 582605

# Unique full-function 8-digit wrist calculator... available only as a kit.

A wrist calculator is the ultimate in common-sense portable calculating power. Even a pocket calculator goes where your pocket goes – take your jacket off, and you're lost!

But a wrist-calculator is only worth having if it offers a genuinely comprehensive range of functions, with a full-size 8-digit display.

This one does. What's more, because it *is* a kit, supplied *direct* from the manufacturer, it costs only a very reasonable £9.95 (plus 8% VAT, P&P). And for that, you get not only a high-calibre calculator, but the fascination of building it yourself.

### How to make 10 keys do the work of 27

The Sinclair Instrument wrist calculator offers the full range of arithmetic functions. It uses normal algebraic logic ('enter it as you write it'). But in addition, it offers a % key; plus the convenience functions  $\sqrt{x}$ ,  $1/x$ ,  $x^2$ ; plus a full 5-function memory.

All this, from just 10 keys! The secret? An ingenious, simple three-position switch. It works like this.



1. The switch in its normal, central position. With the switch centred, numbers – which make up the vast majority of key-strokes – are tapped in the normal way

2. Hold the switch to the left to use the functions to the left above the keys...

3. and hold it to the right to use the functions to the right above the keys.



The display uses 8 full-size red LED digits, and the calculator runs on readily-available hearing-aid batteries to give weeks of normal use.



Dimensions:  
1 13/16 (46 mm) wide,  
1 1/8 (37 mm) deep.  
Weight:  
less than 1oz (28g).

**KIT  
ONLY  
£9.95  
PLUS VAT,  
P&P**

Sinclair Instrument Ltd,  
6 Kings Parade, Cambridge,  
Cambs., CB2 1SN.  
Tel: Cambridge (0223) 311488.

### Assembling the Sinclair Instrument wrist calculator

The wrist calculator kit comes to you complete and ready for assembly. All you need is a reasonable degree of skill with a fine-point soldering iron. It takes about three hours to assemble. If anything goes wrong, Sinclair Instrument will replace any damaged components *free*: we want you to enjoy assembling the kit, and to end up with a valuable and useful calculator.

**Contents**  
Case and display window.  
Strap.  
Printed circuit board.  
Switches.  
Special direct-drive chip (no interface chip needed).  
Display.  
Batteries.

Everything is packaged in a neat plastic box, and is accompanied by full instructions.

The only thing you need is a fine-point soldering iron.

All components are fully guaranteed, and any which are damaged during assembly will be replaced free.

The wrist-calculator kit is available only direct from Sinclair Instrument. Take advantage of this 10-day money-back undertaking.

Send the coupon today.

To: Sinclair Instrument Ltd,  
6 Kings Parade, Cambridge, Cambs., CB2 1SN.

\* Please send me ... (qty) Sinclair Instrument wrist-calculator kits at £9.95 plus 80p VAT plus 25p P&P (Total £11).

\* I enclose cheque/PO/money order for £.....

\* Complete as applicable.

Name \_\_\_\_\_

Address \_\_\_\_\_

(Please print)

I understand that you will refund my money in full if I return the kit undamaged within 10 days of receipt.

WW/5



# The greatest public show of home entertainment -at Olympia in September

That's the Audio Fair this year. It's moved with the market – as the emphasis changes, so does the Fair.

More people buy systems. More people look to home electronics for entertainment, as outside attractions become priced out of the market. More people want the package deal. So . . . not only audio and hi-fi, but also the whole spectrum of

**RADIO...TELEVISION...MUSIC...TV GAMES  
...RECORDS...TAPES...HOME RECORDING  
and MUSIC-MAKING**

More young people are among the buyers. More older people are getting into the new scene of sound. That's why the Audio Fair is a big family occasion, with the big family attractions.

Already the exhibitors include Agfa-Gevaert, Amstrad, Hitachi, National Panasonic, Natural Sound Systems, Rank, Sanyo – to name a few that indicate the width of appeal.

***There's a whole world of Home Entertainment  
at the Audio Festival and Fair this year.  
You ought to be there! It's Sound Sense!***

● **LONDON'S OLYMPIA** – the industry's favoured location, where the people and the money are . . . and the only venue with the size, scope and facilities for this great trade and public festival.

● **SEPTEMBER 12 to 18, 1977** – the preferred pre-Christmas selling-time period . . . and opening with a day and a half for the trade only.

● **BACKED** by major IPC specialist, trade and consumer publications, commanding a combined readership of 1,750,000.

● **ORGANISED** by the IPC Business Press specialist exhibition company, with a remarkable record and reputation for handling specialist fairs.

## THE COMPLETE HOME ENTERTAINMENT SHOW

To: Audio Fair,  
Iliffe Promotions Limited,  
Dorset House,  
Stamford Street,  
London SE1 9LU



YES, I MUST find out more about the 1977 International Audio Festival and Fair. Please send me an exhibitor's brochure right away.

Name .....

Position in firm .....

Address .....

Products we want to exhibit .....

**RELAYS—UNISELECTORS—SWITCHES**

**MINIATURE PLUG-IN RELAYS** (Siemens/Varley) with perspex dust cover and base.  
6-12-24-48v D.C. in Stock  
2 c/o 50p: 6 make 60p  
4 c/o 75p: P & P 10p

**S.T.C. MINIATURE (P.C. Mounting)** with dust cover  
2 c/o (18/24v) 45p P.P. 10p  
4 c/o (24/36v) 50p P.P. 10p  
6 c/o (36/48v) 75p P.P. 10p

**I.T.T. 240v A.C. Plug-In RELAYS** (with perspex cover) 10 amp contacts  
3 c/o 75p P.P. 10p

**H.D. TIME SWITCHES** (100 amp contacts) 1 on/off in 24 hrs. Excellent condition. 240v-50 Hz £6.50 P.P. £1.00

**UNISELECTORS 25 WAY**

5 Bank Full Wipe 75 ohm £5.50 P.P. 50p  
6 Bank Full Wipe 75 ohm £6.25 P.P. 50p  
8 Bank Full Wipe 75 ohm £7.50 P.P. 50p  
12 Bank Half Wipe 68 ohm £8.50 P.P. 60p

**SMALL 12V UNISELECTORS** 4 Bank 11 way £2.50 P.P. 50p

**D.C. SOLENOIDS** 24v (Cont. Rated)  
10lb Pull .20 mm Stroke. Size 50 x 48 x 42 mm  
75p P.P. 15p

**H.D. HONEYWELL MICRO SWITCH** (contacts 2 N.O./2 N.C. 20 amp) ¼ turn action complete with roller actuator.  
£2 P.P. 35p

**DECADE INDICATOR SWITCHES** with plus & minus Push Buttons. 6 mm digits 75p each P.P. 10p  
Also in B.C.D.

**KEY SWITCHES '1000' TYPE**

4 c/o each way locking 60p P.P. 10p  
6 make each way locking 60p P.P. 10p  
Bank of 4. 4 c/o each way. 1 biased £1.25 P.P. 15p

**MAGNETIC COUNTERS**

**MICROFLEX COUNTERS** (HZ40B6) 240v 50Hz Switches off or automatically resets after pre-determined number of input pulses. Contact rating 15 amp. £10.00 P.P. £1.00

**3 DIGIT RESET COUNTERS** (12v D.C.) £1.50 (Ex. Equip.) P.P. 20p

**3 DIGIT RESET COUNTERS** (240v 50 Hz) £1.75 (new) P.P. 25p

**6 DIGIT RESET COUNTERS** (24v D.C.) £4 (new) P.P. 25p

**4 DIGIT NON-RESET** (24v D.C.) £1 (New) P.P. 20p

**5 DIGIT NON-RESET** (24v D.C.) £1 (Ex Equip.) P.P. 20p

**6 DIGIT NON-RESET** (48v D.C.) £1.50 (New) P.P. 20p

**MULTICORE CABLES**

**4 CORE RIBBON (RAINBOW) CABLE** 4 x 10 / 2m.m. forming ¼in. wide strip 10m—75p: 50m—£3: 100m—£6. P.P. 1p per metre

**8 CORE RIBBON (RAINBOW) CABLE** 8 x 14 / 76 Forming ½in wide strip  
10m—£1.50: 50m—£6.50: 100m—£12.00 P.P. 1p per metre

**5 CORE H.D. CABLE** 5 x 70 / 76 P.V.C.  
Black Outer P.V.C. O.D. ½ in  
10m—£2.50: 50m—£12: 100m—£22.50 P.P. 2p per metre

**6 CORE ARMOURED** 6 x 40 / 76 P.V.C. INS  
Outer Sheath-Flexible Galvanised Tubing. O.D. ½in.  
10m—£3: 50m—£14: 100m—£25. P.P. 2p per metre

**10 CORE CABLE** 10 x 7 / 76 (10 colours) P.V.C. O.D. 7m.m.  
10m—£2: 50m—£8.50: 100m—£16. P.P. 2p per metre

**16 PAIR RIBBON CABLE** 16 x 2 core P.V.C. double sheathed forming 55 m.m. wide strip. 10m—£3: 50m—£25: 100m—£40. P.P. 2p per metre

**EQUIPMENT COOLING FANS** (100 C.F.M.)

**PAPST-LUFER** 120x120x38 m.m. 115v 50Hz £5.75 (New) P.P. 50p

**PAPST** 112x112x55 m.m. 220v 50 Hz £3.50 (Ex. Equip.) P.P. 50p

**MUFFIN TYPE** 120x120x38 m.m. £3 (Ex. Equip.) P.P. 50p

**SMALL TRANSFORMERS** 240 / 115v 40p each

**WOODS EXTRACTOR** 130x130x80 m.m. 240v. 50 Hz £3.50 (Ex. Equip.) P.P. 75p

**PAPST (SQUIRREL CAGE)** 9 Blade. Less Mounting. £3.50 (new) 240v 50Hz P.P. 50p

**VARIOUS**

**E.H.T. MODULES.** Input 190-260v 50 HZ. Output 13.7kV, PK @ 0.50 m/a. (150 x 95 x 70mm) £12. P.P. £1.

**MYRIA MEGOHMMETER TYPE 35A.** 20-200K MEG/OHMS 500v test. Excellent condition. £45. carr. £2.50.

**SYNCHRONOUS GEARED MOTORS** (Smiths) 2 r.p.m. 3 r.p.m. 30 r.p.m. 20 r.p.m. 6 r.p.m. 2 r.p.m. h: all 240v £1.50 ea P.P. 25p

**P.C. EDGE CONNECTORS**

32 way (1 pitch) finished ends 45p P.P. 10p

56 way (1 pitch) cuttable 65p P.P. 10p

64 way (1 pitch) cuttable 75p P.P. 10p

Mounting Pillars for 56/64 way 15p pair

Gold Plated Contacts 15p extra

32 way (1.5 pitch) Double-Sided Gold Plate Contacts 50p P.P. 10p

40 way (1.5 pitch) Double-sided 50p P.P. 10p

**H.D. ALARM BELLS** (Ext./Int. use)

4 in Dome (Ext. Gong) 4½ / 6v D.C. £2.50 P.P. £1.00

6 in Dome (Ext. Gong) 6 / 8v D.C. £2.75 P.P. £1.25

6 in Dome (Internal Gong) 12v D.C. £3.75 P.P. £1.25

10 in. Dome (Int. Gong) 24 / 48v D.C. £5.00 P.P. £1.50

**D.C. POWER SUPPLIES** Input 240v A.C.

TYPE 1 20v D.C. at 1 amp. Fully regulated 155 x 155 x 75 mm totally enclosed £5 P.P. 75p

PLEASE ADD 8% V.A.T.

**J. B. PATTRICK**

191/193 LONDON ROAD

ROMFORD, ESSEX RM7 9DJ

ROMFORD 44473

# Wilmslow Audio



## THE firm for speakers!

|  |        |   |        |
|--|--------|---|--------|
| Baker Group 25. 3. 8 or 15 ohm . . . . .         | £13.00 | Goodmans 12P 8 or 15 ohm . . . . .          | £16.50 |
| Baker Group 35. 3. 8 or 15 ohm . . . . .         | £14.50 | Goodmans 12P-D 8 or 15 ohm . . . . .        | £18.75 |
| Baker Deluxe 8 or 15 ohm . . . . .               | £17.50 | Goodmans 12P-G 8 or 15 ohm . . . . .        | £17.75 |
| Baker Major. 3. 8 or 15 ohm . . . . .            | £15.00 | Goodmans Audiom 200 8 ohm . . . . .         | £14.95 |
| Baker Regent, 8 or 15 ohm . . . . .              | £12.50 | Goodmans Axent 100 8 ohm . . . . .          | £8.50  |
| Baker Superb. 8 or 15 ohm . . . . .              | £22.50 | Goodmans Axiom 402 8 or 15 ohm . . . . .    | £22.00 |
| Celestion HF1300 8 or 15 ohm . . . . .           | £7.50  | Goodmans Twinaxiom 8" 8 or 15 ohm . . . . . | £10.60 |
| Celestion MH. 1000 horn. 8 or 15 ohm . . . . .   | £13.50 | Kef T27 . . . . .                           | £8.50  |
| Coles 400 1 G super tweeter . . . . .            | £5.90  | Kef T15 . . . . .                           | £10.75 |
| Coles 400 1 K super tweeter . . . . .            | £5.90  | Kef B110 . . . . .                          | £10.95 |
| Decca London and X over . . . . .                | £38.45 | Kef B200 . . . . .                          | £11.95 |
| Decca DK30 and X over . . . . .                  | £25.25 | Kef B139 . . . . .                          | £24.95 |
| EMI 5" Mid range . . . . .                       | £3.50  | Kef DN8 . . . . .                           | £2.75  |
| EMI 6½" d/cone roll surr. 8 ohm . . . . .        | £3.95  | Kef DN12 . . . . .                          | £7.25  |
| EMI 8 x 5, 10 watt. d/c. roll/s 8 ohm £3.95      |        | Kef DN13 . . . . .                          | £4.95  |
| EMI 14" x 9" Bass 8 ohm . . . . .                | £12.50 | Richard Allan HP8B 8" 45 watt . . . . .     | £12.50 |
| Elac 59RM 109 15 ohm. 59RM 1148 ohm . . . . .    | £3.50  | Richard Allan CG8T 8" d/c roll/s . . . . .  | £7.95  |
| Elac 6½" d/c roll/s 8 ohm . . . . .              | £3.95  | Baker Major Module. each . . . . .          | £18.00 |
| Fane Pop 15 watt 12" . . . . .                   | £5.75  | Goodmans Mezzo Twinkit. pair . . . . .      | £51.95 |
| Fane Pop 33T 33 watt 12" . . . . .               | £9.95  | Goodmans DIN 20. 4 ohm. each . . . . .      | £15.75 |
| Fane Pop 50 watt, 12" . . . . .                  | £12.50 | Helme XLK35. pair . . . . .                 | £26.75 |
| Fane Pop 55. 12" 60 watt . . . . .               | £16.95 | Helme XLK40. pair . . . . .                 | £38.50 |
| Fane Pop 60 watt, 15" . . . . .                  | £19.95 | Helme XLK30. pair . . . . .                 | £21.95 |
| Fane Pop 70 watt 15" . . . . .                   | £21.75 | Kefkit 1. pair . . . . .                    | £59.50 |
| Fane Pop 100 watt. 18" . . . . .                 | £33.95 | Kefkit III. each . . . . .                  | £56.00 |
| Fane Crescendo 12A or B. 8 or 15 ohm . . . . .   | £42.95 | Richard Allan Twinkit. each . . . . .       | £13.95 |
| Fane Crescendo 15. 8 or 15 ohm . . . . .         | £54.95 | Richard Allan Triple 8. each . . . . .      | £20.75 |
| Fane Crescendo 18. 8 or 15 ohm . . . . .         | £75.95 | Richard Allan Triple 12. each . . . . .     | £25.95 |
| Fane 807T 8" d/c. rolls/s. 8 or 15 ohm . . . . . | £5.40  | Richard Allan Super Triple. each . . . . .  | £29.50 |
| Fane 801T 8" d/c roll/s 8 ohm . . . . .          | £9.50  | Richard Allan RA8 kit. pair . . . . .       | £37.80 |
| Goodmans 8PA 8 or 15 ohm . . . . .               | £3.50  | Richard Allan RA82 kit. pair . . . . .      | £59.40 |
| Goodmans 10P 8 or 15 ohm . . . . .               | £6.95  | Wharfedale Denton 2XP Kit. pair . . . . .   | £23.25 |
|  |        | Wharfedale Linton 3XP Kit. pair . . . . .   | £34.25 |
|  |        | Wharfedale Glendale 3XP kit. pair . . . . . | £49.50 |

All Radford, Gauss, Castle, Jordan Watts, Eagle, Lowther, Peerless Tannoy units in stock

Prices correct at 21/3/77

**ALL PRICES INCLUDE VAT**

**FREE with all orders over £10 —**

**Hi-Fi Loudspeaker Enclosures Book**

Send stamp for free 38-page booklet

"Choosing a Speaker"

Cabinets wadding, Vynair, Crossovers etc.

**All units are guaranteed new and perfect**

Prompt despatch

Carriage: Speakers up to 12" 60p; 12" £1; 15" £1.75; 18" £2.50

Kits £1 each (£2 per pair). Tweeters & Crossovers 33p each.

## WILMSLOW AUDIO

Dept. WW

Loudspeakers & Export Dept: Swan Works, Bank Square, Wilmslow, Cheshire SK9 1HF. Discount Hi-Fi, PA, etc.; 10 Swan Street, Wilmslow, Radio, Hi-Fi, TV; Swift of Wilmslow, 5 Swan Street, Wilmslow. Tel. (Loudspeakers), Wilmslow 29599 (Hi-Fi, etc.), Wilmslow 26213.


Access and Barclaycard orders accepted by phone

WW — 015 FOR FURTHER DETAILS
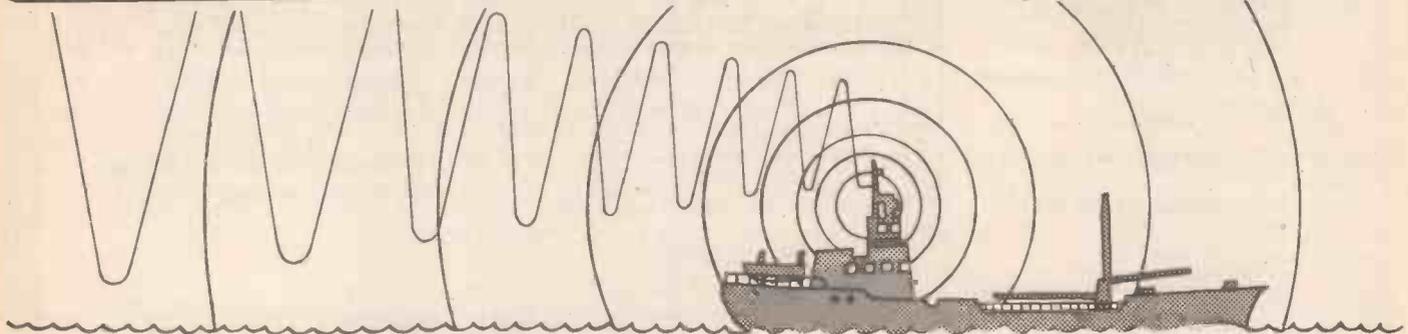
# Appointments

Advertisements accepted up to 12 noon Monday, May 2, for the June issue, subject to space being available.

**DISPLAYED APPOINTMENTS VACANT:** £7.50 per single col. centimetre (min. 3cm).  
**LINE advertisements (run on):** £1.10 per line, minimum three lines.  
**BOX NUMBERS:** 50p extra. (Replies should be addressed to the Box Number in the advertisement, c/o Wireless World, Dorset House, Stamford Street, London SE1 9LU.)  
**PHONE:** Eddie Farrell on 01-261 8508  
*Classified Advertisement Rates are currently zero rated for the purpose of V.A.T.*



## Radio Officers—now you can enjoy the comforts of home.

Working for the Post Office Maritime Services really makes sense. You still do the work that interests you, but with all the advantages of a shore-based job: more time to enjoy home life, job security and good money. To qualify, you need a United Kingdom Maritime Radiocommunication Operator's General Certificate or First Class Certificate of competence in Radiotelegraphy, or an equivalent certificate issued by a Commonwealth Administration or the Irish Republic.

Starting salaries, at 25 or over, are £2905 rising to £3704 after three years service. Between 19 and 24, the starting salary varies from £2234 to £2627 according to age. In addition, a supplement of £312

p.a. is payable. You'll also receive an allowance for shift duties which at the maximum of the scale averages £900 a year and there are opportunities to earn overtime. There's a good pension scheme, sick pay benefits and prospects of promotion to senior management.

Right now we have a few vacancies at some of our coastal radio stations, so if you're 19 or over, preferably with sea-going experience, write to: ETE Maritime Radio Services Division (L690), ET 17.1.1.2., Room 643, Union House, St. Martins-le-Grand, London EC1A 1AR.

Post Office Telecommunications

**CAPITAL APPTS.**

**FREE LISTS**  
 101 Design/Development and Test Jobs  
 Permanent and Contract  
 To £6,000

34, Percy St. London, W.1.  
 637 5551 day; 550 0836 eve.

**WH**

**SENIOR SALES ENGINEER/MANAGER**  
 Initially for internal Sales with management responsibility.  
 SALARY RANGE £4,000 TO £8,000 p.a.  
 A good background in electronic housings and a reasonable knowledge of electronics are necessary as is commercial experience. The applicant will report direct to the Sales Director. After a period the post will be one of considerable responsibility.  
 Please phone Mr. W. A. Wemyss, Man. Dir. on Gt. Missenden 2235 any time.

**WEST HYDE DEVELOPMENTS LTD.**  
 RYEFIELD CRES., NORTHWOOD, MIDDX.

## ELECTRONIC FIELD ENGINEER

to supervise commissioning and operation servicing of NC machine tools. The applicant should be qualified to at least HNC level or equivalent, having organising ability and preferably should have had practical experience of machine tools.

The position attracts a salary commensurate with the responsibility of the appointment, together with the total use of a company car.

Please apply in writing, giving details of experience, qualifications and age to:—Mr. A. Turner, Products Engineer,

**HEPWORTH IRON CO. (ENGINEERING) LIMITED**  
 Bridge Mills, Holmfirth  
 Huddersfield HD7 2TW

(7171)

### SOUTH COAST

Several of our clients require the following personnel urgently, offering excellent salaries and relocation expenses where necessary.

**PROJECT ENGINEERS**  
**ELECTRONIC ENGINEERS**  
**TEST ENGINEERS AND TECHNICIANS**  
**QUALITY ASSURANCE ENGINEERS**  
**TECHNICAL AUTHORS**  
**SYSTEMS PROGRAMMERS**  
**DRAUGHTSMEN/WOMEN, Electro-Mechanical and BUYERS**

Please write or ring: **CBS APPOINTMENTS**  
 224 Old Christchurch Rd., Bournemouth, Bournemouth  
 292155 or Wimbome 4891 after 7 p.m. (7142)

### DESIGN TEST FIELD SERVICE

Immediate vacancies exist in most areas for engineers qualified to BSc/HNC/C&G with analogue, digital or R.F. experience.

Phone or write

**APEX PERSONNEL**  
 800 FULHAM ROAD  
 LONDON S.W.6

**01-731 4353**

(7155)

## **ELECTRONIC DESIGN/ DEVELOPMENT ENGINEERS FERRANTI OFFERS YOU FREEDOM**

..... freedom to create. Over the years leading design and development engineers have been attracted to Ferranti by our reputation for truly innovative engineering and together they have formed specialised teams involved on a variety of sophisticated projects related to the Tornado, Sea Harrier, Jaguar, Nimrod 2 and other front line aircraft.

We now require additional engineers to join these teams engaged on the creative work of designing and developing airborne radar, laser and inertial navigation systems and their associated test equipment.

**Engineers are required in the following technical fields:-**  
**Digital and analogue electronic circuitry design.**  
**Design and application of small digital computers.**  
**Microwave and laser techniques.**  
**Advanced instrument design including gyroscopes of inertial quality.**  
**Design of small mechanical structures and analysis of stress.**

In addition to the above we have vacancies for production engineers with either electrical or mechanical backgrounds in these fields.

Applicants should have some design/development experience to offer in avionics and a desire to expand their experience to project leader level.

Edinburgh, with its outstanding facilities for education, housing, sport and entertainment, is one of the ideal cities in Europe in which to live, work and bring up a family. And to make moving here easier, we pay realistic relocation expenses. Salaries are negotiable and the Company operates a contributory pension and life assurance scheme.

Apply in writing, with full details of experience and qualifications to

**Staff Appointments Officer,  
Ferranti Limited,  
Ferry Road,  
EDINBURGH, EH5 2XS.**

Please quote Ref. WW/3

**FERRANTI**

# Radio Communications Engineering

Hampshire to £5,000

Plessey Avionics and Communications at West Leigh, Havant, is a leader in the design, manufacture and development of advanced radio communications equipment and systems. A number of opportunities exist, at various levels, for electronics engineers. The work is stimulating and rewarding, and there is considerable scope for career progress.

## HF/VHF Military Radio Design

Successful candidates will be involved in the design of new products using advanced miniaturisation techniques. Experience of digital systems and RF techniques at HF and VHF would be particularly valuable. These appointments will be of particular interest to designers willing to work against short time scale development plans on products mainly for the export market.

## UHF/SHF Radio Relay Design

Engineers to work on the design of transmitters and receivers at UHF and SHF, IF amplifiers, and base-band amplifiers for multi-channel radio relay equipment. It would be useful if experience included liaison with production.

## Radio Relay Systems Design

Engineers for the design of overall radio relay systems, the development of sub-equipments and systems evaluation. Previous experience in the design and/or commissioning of radio communications systems is desirable.

Candidates should be educated to degree level or equivalent and have at least two years experience. Situated in a semi-rural environment near Portsmouth, Chichester, the South Downs and several seaside resorts, we are well placed for housing, shops, school and recreational amenities. Relocation assistance will be given where appropriate and there is a comprehensive range of large company benefits. Attractive salaries will be negotiated in line with experience and qualifications. Please write with brief career details or telephone for an application form. L. Wise, Recruitment Manager, The Plessey Company Limited, Martin Road, West Leigh, Havant, Hants. Tel (07012) 6391. Applications are invited from either sex.



**PLESSEY**

(7116)

## DIGITAL RADIO COMMISSIONING

International Aeradio, world leaders in the overseas telecommunications field, require an Engineer with extensive experience of Digital Radio Links. Although UK based, the successful applicant will spend periods overseas.

Applicants must have HNC or an equivalent practical background, combined with field experience of digital radio, PCM testing and of associated proprietary test equipment.

The post offers attractive career opportunities in a rapidly expanding and progressive company, a pension scheme, generous leave and allowances, staff restaurant and social club facilities are available.

Please write now with brief résumé of career activities and quoting ref: 97, to: The Technical Recruitment Officer, International Aeradio Limited, Aeradio House, Hayes Road, Southall, Middlesex or telephone 01-571 1808 or 01-572 2892.

7159

## APPOINTMENTS IN ELECTRONICS

Take your pick of the permanent posts in:

- MISSILES — MEDICAL
- COMPUTERS — COMMS
- MICROWAVE — MARINE
- HARDWARE — SOFTWARE

For expert advice and immediate action on career improvement, phone, or write to, Mike Gernat BSC.

**Technomark**  
Engineering and Technical Recruitment

11 Westbourne Grove  
London W2. 01-229 9239.

7098

TELSEC INSTRUMENTS LTD. are manufacturers of one of the widest ranges of X-ray Spectrometers and due to an internal promotion we have the following vacancy

## ELECTRONICS ENGINEER


We need a person with at least HNC to join a team testing and setting up computerised spectrometers in the role of Senior Test Engineer. Experience in instrumentation or computers is desirable.

An excellent salary will be offered and there are prospects of promotion to the head of the Test Section.

Applications to:

**K. M. Field**  
Telsec Instruments Ltd.  
Sandy Lane West, Littlemore  
Tel: Oxford 770361

(7145)

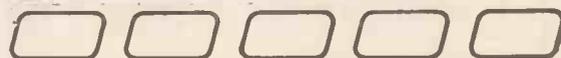

## SENIOR PROGRAMMER (COMPUTER GRAPHICS)

The BBC Television Service is examining ways of developing interactive computer aided graphics for programme makers.

We should like to hear from experienced programmers who are interested, and have experience, in the development of this type of application.

Programmers who have considerable real time programming experience plus either training in or a practical knowledge of the creative side of graphic arts are particularly invited to apply. Knowledge of D.E.C. equipment and the RSXII operating system would be desirable. This appointment will be on a contract basis for a period of up to two years, and based in West London.

Salary in the range of £4953-£5913 per annum, plus appropriate Pay Supplement.

Write or telephone immediately for application form (enclosing addressed foolscap envelope and quoting reference number 77.G.647WV) to Appointments Department, BBC, London W1A 1AA. Telephone 01-580 4468. Ext. 4619.

(Applicants may also telephone Terry Smith, 01-743 8000 extns. 4593/4., Head of Television Computer Projects, for further details of this post.

7189



**ELECTRONICS/ELECTRICAL ENGINEERS  
COMPUTER SCIENTISTS  
PHYSICISTS**

**If you want to develop the computers  
of the future...join ICL**

**£3500-£5500 Manchester or Kidsgrove**

We are offering you an opportunity to join one of the foremost computer development teams in the world. Its reputation has been built on the successful 2900 Series, the most powerful and sophisticated computer system currently built in Europe, which the team is evolving to meet the needs of the 1980s. The work, incorporating radically new technologies, is creative; it is also exciting and demanding.  
**You could be part of it. With the team's expansion,**

we have a large number of vacancies for men and women. We can offer generous relocation expenses where appropriate and planned career development in a variety of roles, such as:

- LOGIC SYSTEMS DESIGNER
- BIPOLAR/MOS LSI DESIGNER
- QA ENGINEER
- CIRCUIT DESIGNER

Have you a degree or equivalent in electronics, electrical engineering, physics or computer science

and post-graduate experience in digital electronics, semiconductor or process engineering?

If you want to put your knowledge and experience into practice, we'd like to see you. Contact John Davies, CDD Personnel, ICL, Wenlock Way, West Gorton, Manchester M12 5DR. Telephone 061-2231301 extension 2694 or 2797. (Reverse the charges.)

**International Computers**

think computers—think ICL

**ICL**

# Electronic Test Engineers

Pye Telecommunications of Cambridge has immediate vacancies for Production Test Engineers, of either sex.

The work entails checking to an exacting specification VHF/UHF radio-telephone equipment before customer delivery; applicants must therefore have experience of fault finding and testing electronic equipment, preferably communications equipment.

Formal qualifications while desirable, are not as important as practical proficiency. Armed service experience of such work would be perfectly acceptable.

Pye Telecommunications is a major exporter of radio-telephone equipment and is shortly moving into a new purpose built factory.

There are good opportunities for promotion within the Company.

Pye also encourages its staff to take higher technical and professional qualifications.

Write or telephone without delay for an application form to: Miss C. Barton

/187



**Pye Telecommunications Ltd**

Elizabeth Way, Cambridge CB4 1DW  
Tel. Cambridge (0223) 58985 Telex 81105

A member of the Pye of Cambridge Group

## Brunei Training Officers

a) In the field of cable jointing

b) Laying subscribers' apparatus installation and maintenance are required for on-job training of in-service staff who have minimal formal training and little or no knowledge of correct telecommunications methods and of new entrants to complement formal class training. They will be required to support the overall departmental training programme wherever necessary including the organisation of practical training classes.

Candidates must have 5 years' experience either in or working on behalf of a telecommunication operating organisation in a relevant field, preferably in a developing country.

Salary in a scale equivalent to £6,195-£7,150 tax-free including special allowance.

Appointment is for 2 or 3 years. Benefits include 25% gratuity, free passages, education allowances and subsidised housing.

For full details and application form write quoting MT/309/WD, to:

**Crown Agents** 

The Crown Agents for Oversea Governments and Administrations, Appointments Division,  
4 Millbank, London SW1P 3JD.

(7146)

## SERVICE AND TEST ENGINEERS

At Stanmore we are involved in the provision of spares and the repair, maintenance and overhaul of a wide range of British and American airborne electronics equipment.

It's skilled work calling for the highest standards of craftsmanship and with the continuing growth of our servicing programme we are now looking for additional personnel to join our teams of Service and Test Engineers working both in the aircraft and in our extensively equipped workshops.

You should have a good knowledge of radio and electronics theory, ranging from audio to microwave, and at least two years' experience in servicing and

maintaining complex electronic equipment, including fault diagnosis using sophisticated test gear. A recognised qualification would also be desirable

### FOR AIRBORNE ELECTRONICS EQUIPMENT

but sound practical experience is more important. A good salary will be offered together with an attractive range of benefits.

Working conditions are excellent and the establishment is conveniently situated in pleasant surroundings within easy reach of the A1 and M1.

Write with details of experience to Mrs. E. Wagg, Marconi-Elliott Avionic Systems Limited, 22-26 Dalston Gardens, Stanmore, Middlesex HA7 1BZ. Tel: 01-204 3322.

## MARCONI ELLIOTT AVIONICS

A GEC-Marconi Electronics Company

(7125)

**CA CAPITAL APPOINTMENTS LTD.**

**FREE JOBS LIST**  
for  
**FIELD SERVICE ENGINEERS**  
BASIC SALARIES TO  
**£5,000 + CAR**

(7151)

34 Percy Street, London. W1  
01-637 5551

### VIDEO SALES REPRESENTATIVES

Due to expansion, we require additional experienced salespersons with proven sales record, enthusiasm and self-motivation. Excellent salary and bonus, plus car and expenses, for the right applicants.

Please write, stating relevant details, to:  
**M. Murray, Managing Director**  
**REW Audio Visual Company**  
10/12 High Street, Colliers Wood  
SW19 2BE (7122)

### INTEROFFICE TELEPHONES LIMITED

An opportunity exists to join our Sound and Time Section to maintain in London/H. Counties various types of Radio/Amplifiers. Some knowledge of Impulse Clock Systems and direct speech installations would be an advantage.

Please telephone for an appointment:  
**01-274 3214/5; 01-274 5091(7131)**

### PIPCO (S & W SERVICES)

For Electronic Engineers, Technicians & TV Service Engineers.

26a High Street  
Hounslow, Middx.  
Tel: 01-572 7363

Telex PIPCO Hounslow 935413 (6552)

## Electronic Circuit Designer

We are one of the European leaders in the manufacture of thick film hybrid circuits.

We are looking for a young circuit designer to join an established team which deals with design, limitations and potential of thick film technology. You should have experience of analogue and digital circuit design, but not necessarily in thick film, and have an understanding of C.A.D. procedures and tolerancing for production. You should not be bound by currently accepted solutions to problems, but be prepared to explore unconventional methods within the manufacturing technology.

Salary is negotiable, there is an excellent range of fringe benefits and relocation expenses are available to this very pleasant location.

For further information and an application form, please contact:

**C. L. BORROW**

7117

**NKT** Newmarket Transistors Ltd  
Exning Road Newmarket Suffolk England CB8 0AU  
Tel: Newmarket 3381 Telex: 81358 SEMICON NEWMKT

A member of the Plur of Cambridge Group

## ELECTRONICS ENGINEER

An interesting and challenging opportunity exists within our international organisation which will appeal to the individualist electronics engineer.

Our range of highly sophisticated scientific instruments is of advanced design and involves all aspects of electronics from high-power RF to high-speed digital switching.

We require a first-class Electronics Engineer to carry out installation, commissioning and after-sales service at customers' premises.

The ideal applicant will be aged 25-35, have a minimum qualification of HNC (Electronics) and some industrial experience, preferably in a design/development environment, and be capable of working with a minimum of supervision.

Extensive travel in the United Kingdom is involved with occasional trips abroad.

Knowledge of the German language though not essential would be an advantage.

The job is both rewarding and demanding and requires a high degree of technical ability, as well as a keen sense of responsibility. In return we offer a good salary and excellent conditions, as well as a great deal of personal freedom.

If you want a job which will really give you something to think about, then apply in writing giving fullest possible details of age, qualifications, career to date, salary, etc., to:



**R. F. LADBURY**  
**BRUKER SPECTROSPIN LIMITED**

UNIT 3, 209 TORRINGTON AVENUE  
COVENTRY CV4 9HN

(7128)

## LONDON BOROUGH OF SUTTON

EDUCATION DEPARTMENT

### TECHNICIAN

Carshalton College of F.E.

Technical 2 £2529-£2853 plus £285  
London Weighting and £312  
supplement

required in the Department of Electrical Engineering to be responsible for, Electronic Laboratories and associated equipment. Applicants must be 20 years of age or over and hold City & Guilds Technician Final Certificate or equivalent and have at least three years' experience in this field.

Application forms and further details from Principal, Carshalton College of Further Education, Nightingale Road, Carshalton, Surrey on receipt of a stamped addressed envelope. Tel. No. 01-647 0021/7.

Closing date 2nd May, 1977.

(7168)

Britain's No. 1 Mobile Recording Unit producing only prestige material require an

### ENGINEERING ASSISTANT

(Technical) to take charge of audio equipment maintenance.

Applicant must be experienced with multi-track audio facilities, able to drive, and prepared to work on location. The unit is based at Henley-on-Thames and the successful applicant will be expected to reside locally.

Phone: Bob Auger 04912-5434 for an appointment.

7118

### AUDIO MAINTENANCE ENGINEER

A leading London based recording studio has a vacancy for a maintenance engineer with an excellent background in audio and digital electronics.

Duties will include assisting in the service and maintenance of some of the most up-to-date audio equipment currently available. For further details please apply to

R. Cameron  
ADVISION LTD.  
23 Gosfield Street, London W.1  
Tel: 01-580 5707

7123

# ENGINEERS

The Cable and Wireless Group is continuing its impressive growth record, and is now seeking additional Engineers and Assistant Engineers in the following disciplines, for its Head Office Engineering Department in Central London:

**International and National Telex and Telephony; MF, HF, VHF, Microwave and Satellite-Radio; Primary Power Plant and distribution; Data and Telegraph Transmission and Switching; Telemetry.**

The responsibilities could involve the complete range of project work, from assessment, through to commissioning and acceptance. Occasional overseas visits may be necessary. Applicants should have specialist knowledge and experience of one or more of the above disciplines together with a wide appreciation of telecommunications operations in general. Some experience of customer liaison would be an advantage.

Candidates for the Engineer posts would probably have a relevant degree or professional qualification, although this is not essential. At least five years related experience is required. **Salary will be up to £6,000.**

For the Assistant Engineer posts an HNC/C&G FTC is desirable and several years' related experience. **Salary will be up to £5,000.**

Benefits include a pension scheme, staff restaurant, sports and social club and generous overseas allowances.

*If you think that your qualifications and experience make you suitable for one of these opportunities, please send a summary of your career. Write to:*


Recruitment Manager, Cable & Wireless Ltd.,  
(A587/WW),  
Theobalds Road, London WC1X 8RX.  
Tel: 01-242 4433 Ext. 4008

7175,

# Cable & Wireless

Are You Interested In

## Radio Communications

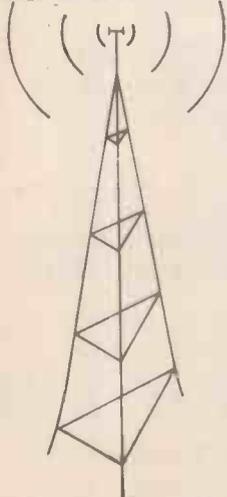

and do you have practical experience in this field

if you have City and Guilds Intermediate Certificate in Electronics or Telecommunications; ONC; or an equivalent qualification

then the Metropolitan Police may have a job for you as a Radio Technician.

**we offer**  
Good pay  
Excellent prospects  
Secure employment  
4 weeks holiday  
Day release

Phone our Engineer Mr. H. G. Fielding on 01-653 0881, during office hours, to arrange an informal interview, or write to Metropolitan Police, Room 1634, New Scotland Yard, Broadway, London SW1H 0BG.

(7140)

## TECHNICAL EDITOR TECHNICAL SUB-EDITOR

Britain's highest selling monthly electronic consumer publications, which include PRACTICAL WIRELESS, PRACTICAL ELECTRONICS, EVERYDAY ELECTRONICS, etc., wish to strengthen their editorial teams and expertise.

Applications are invited from men and women from the radio, audio and electronic fields with an ability to write in depth on electronics, in as easily understandable style. Technical experience is essential, together with an appreciation of the latest technological trends. Our publications appeal to the amateur constructor, and therefore candidates are required to assess projects for publication and be capable of designing and building projects and liaising with contributors.

Whilst journalistic experience is not essential, he or she is likely to have worked in an electronics company or their publicity department and will possess flair, and an enquiring mind.

We offer excellent salaries, four weeks' leave, subsidised luncheon facilities, plus the career advancement opportunities associated with a major company.

Please write giving full details, stating present salary, age and qualifications to:

Mr. R. Muggleton, Publisher  
Practical Group, Fleetway House  
Farringdon Street, London EC4 4AD

IPC Magazines Ltd. — A member of the Reed Group of Companies

7127

UNITED GLASS LTD.

## TECHNICAL OFFICER

A person is required to join a small team engaged in the development and use of electronic equipment for monitoring process variables in the glass container industry. This will initially concern time and temperature measuring equipment, but subsequently involvement in the use of a microprocessor system currently being developed will be necessary. The applicant should be familiar with digital and analogue circuitry. The starting salary is expected to be in the range £3,000-£3,500 per annum.

We offer excellent working conditions, including a subsidised staff restaurant, four weeks' paid holiday and Pension Scheme.



Apply to:  
**Group Research Manager**  
**UNITED GLASS LTD**  
 Research & Development Centre  
 Porters Wood  
 St. Albans  
 Herts. AL3 6NY

(7147)

## Service Engineers

££3400 + Car

Our Client, based 50 miles North of London are leading distributors of electronic organs, amplifiers, synthesisers and mixers.

They now require an Electronics Engineer to repair and service their equipment. You will be liaising with Retailers' Engineers and Professional Musicians' Engineers on technical matters. This position will involve trips to Hamburg or Japan for product training. A higher salary will be considered for an applicant who is fully conversant with this type of work.

Contact Sue Skidmore, PER, 56-62 Park Street Luton LU1 3JB. Telephone (0582) 417562

**PER** PROFESSIONAL and EXECUTIVE RECRUITMENT

This vacancy is open to male or female candidates.

Rolls-Royce Limited

## Data Acquisition Engineer

Within an extensive application of electro and electronic measuring systems used in the development of aero engines we have positions for engineers interested in the collection of data of an experimental nature.

The work encompasses measurement techniques applied to static and dynamic parameters, that is, stress, pressure, flow and temperature.

Ideally candidates (male or female) should possess an HND or HNC in Electrical or Electronic Engineering with experience in this type of work, but candidates with suitable alternative backgrounds who are prepared to undergo specialist training will be considered.

Salary will be paid according to age, qualifications and experience.

The Company operates a Staff Pension Scheme.

We should be pleased to discuss re-location expenses with candidates who are invited for interview.

Enquiries should be addressed to:



Mr J A J Clarke, Senior Personnel Officer  
 Rolls-Royce Limited  
 PO Box 31 Derby DE2 8BJ  
 Telephone: Derby 42424 Extension 109



YAMAHA



Nakamichi

## AUDIO ENGINEERS

We require experienced bench engineers to work to a high standard on the above products.

Applicants should have a keen interest in, and at least 3 years' experience of all aspects of Audio servicing with similar quality equipment.

For further details and application forms please contact the Service Manager, Terry Finn, at

Natural Sound Systems Ltd.

10 Byron Road  
 Wealdstone, Harrow, Middx.  
 Tel: 01-863 8622

Strathcona Road, North Wembley, Middlesex HA9 8QL

(7126)

**ALCAN LABORATORIES LIMITED**  
ATLANTIC REGION RESEARCH CENTRE



## INSTRUMENT TECHNICIAN

Alcan Laboratories Limited require an Instrument Technician at their Research Centre in Banbury, Oxfordshire. The work will be concerned mainly with the development of electronic measurement and control equipment which will be used in the Laboratory and in Alcan factories.

The Research Centre, which is one of Europe's leading metallurgical laboratories, carries out Research and Development work for associated Group companies in the U.K., Europe, Africa and South America; it is part of the Canadian-based Alcan Aluminium Limited Group, which is one of the world's major aluminium producers.

Candidates will be required to work largely on their own initiative; they should have an HNC in Electronic Engineering followed by two/three years' experience in the development of prototype electronic equipment.

The company offers excellent working conditions, progressive salary scales, flexible working hours and a contributory pension scheme. Assistance with the cost of moving house will be given where appropriate.

Application forms can be obtained from:

**Mrs. S. M. White**  
**ALCAN LABORATORIES LIMITED**  
Southam Road  
Banbury, Oxon OX16 7SP  
Tel: Banbury (0295) 2821

7170

**UNIVERSITY OF LEEDS.** Applications are invited for the post of electronics technician Grade 3 in the Department of Psychology, University of Leeds. Duties include maintenance of existing equipment and building of new equipment to interface with a mini-computer for monitoring on-line experiments. The successful candidate will be able to work without constant supervision, should hold ONC and/or City and Guilds Intermediate Qualifications and have at least three years relevant experience including some digital work. Salary on the scale £2455-£2788. Applications, giving full details of education and experience together with names and addresses of two referees, to: Mr D. Pritchatt, Department of Psychology. (7119)

**ELECTRONICS TECHNICIAN** for Educational Services Unit. Candidate should have interest in television as a teaching and research tool, sound background in electronics with ability to communicate with patients, students and staff at all levels. Major part of the post involves maintenance of small studio in Department of Psychiatry, preparation and replay of video-recordings. Salary scale £2,889-£3,367 p.a. Application forms from: Assistant Secretary, Personnel Office, University of Birmingham, P.O. Box 363, Birmingham B15 2TT. Ref. 496/C/57.

**MEDICAL Electronics Engineers** required for servicing, testing and fault finding must be fully experienced. Qualifications to HNC level. Salary being negotiable. — Contact Mr Cooper for interview telephone 272 9212. (7134)

**LANCHESTER POLYTECHNIC,** Coventry site. Technician, Centre for Media Studies. An Electronics Technician is required to constitute part of the work of a highly creative team involved in all aspects of the Media. The appointee will work in the areas of Electric Media (study of light, sound and motor), Video and Sound Recording. Duties will include constructing, fitting, maintenance and testing of experimental equipment and involvement in under-graduate projects. The successful candidate will be expected to have experience in one of these fields, be suitably qualified and be prepared to use his/her own initiative in coping with a diversity of demands. Salary scale: £2529-£3282 plus £312 supplement per annum with possible progression to £3702 per annum. For application form please apply in writing enclosing a foolscap stamped and addressed envelope to the Assistant Secretary (Personnel) Lanchester Polytechnic, Priory Street, Coventry, CV1 5FB, returnable within ten days of the appearance of this advertisement. (7121)

**TEST ENGINEER** with sound knowledge of logic circuitry for work on ou range of instruments. Phone or write R.C.S. Electronics, 6 Wolsey Road, Ashford, Middlesex. STD 69/53661. (7166)

**ELECTRONIC TECHNICIAN** Grade 5 required in the Chemical and biochemical Engineering Department for the electronic workshop. Good knowledge of fault-finding and servicing standard electronic instruments required, together with the ability to work on prototype circuits. Salary in range £3,377 to £3,856 including London weighting. Application form and further details from Personnel Officer (Technical Staff EB3/WW), University College London, Gower Street, WC1E 6BT. (7120)

# Marconi Instruments

## Professional Electronics In St Albans

### Development Engineers

Designing state of the art r.f. and digital circuitry as members of small project teams.

### Components Engineer

To specialise in the analysis of new components used in electronic equipment manufacture.

### ATE Field Service Engineers

Servicing Automatic Electrical Inspection Systems throughout the UK.

### Advanced Test Engineer

To develop test methods in particular programming systems in new generation instrumentation that utilize microprocessors and state of the art logic.

### Export Engineer

Based in St. Albans, travelling the world selling the Company's range of r.f. and digital test equipment.

### Technical Author

Compiling instruction manuals on communications test equipment and ATE.

### Test Technicians

Commissioning a wide-range of batch produced test equipment eg. Spectrum analyses, signal generators and modulation meters.

### Technician Engineer

Working within a Test Gear Maintenance Department repairing a very wide range of modern, commercial and special to type test equipment.

## In Luton

### Test Engineers

Servicing customer owned equipment in the largest communications test equipment maintenance organisation in W. Europe.

Further information may be obtained from John Prodger:

**Marconi Instruments Ltd.,**  
Longacres,  
St. Albans, Herts.  
Tel: St. Albans 59292.

A GEC-Marconi Electronics Company.

7153

## PROJECT ENGINEER

(LIGHTING CONTROL SYSTEMS)

We are a leading Company in the field of thyristor controlled lighting and associated equipment, including standby power sources, power distribution and industrial control. A high percentage of our production is exported.

Due to our continued expansion, we require a project engineer to assist in the design and planning of equipment to meet customer requirements, provide manufacturing information, and organise on-site commissioning. The ability to work with minimal supervision and to be self-motivated is essential.

Contact: **P. J. Harrison, Technical Director**



**Polaron Controls Limited**  
60/62 Greenhill Crescent  
Holywell Industrial Estate  
Watford, Herts WD1 8RL  
Tel. Watford (0923) 37144  
Telex 922980

An opportunity has arisen at our Warrington Factory for an electronics engineer, in our Technical Services Department, with proven ability in a wide range of fields connected with the manufacture of H.F. communications receivers and drive units.

## Senior Electronics Engineer



The person chosen for this demanding position will need considerable practical experience of dealing at first hand with engineering problems arising from the manufacture of communications equipment. Duties will also include the control and development of test schedules for computer controlled automatic test equipment as well as repair and calibration of proprietary test equipment.

The successful candidate will be qualified to degree level and have had several years experience in a similar or related field.

This position carries competitive rates of pay and a generous holiday entitlement and sick pay scheme together with a pension scheme with free Life Assurance.

If you are interested then

### Communicate with Racal

Please apply in writing to  
The Personnel Manager,  
Racal Communications Equipment Ltd.,  
Chesford Grange, Woolston,  
WARRINGTON, Cheshire WA1 4RH.

7176

**RACAL**  
The Electronics Group

## Botswana Telecomms Maintenance Engineer

To co-ordinate the planning, installation and maintenance of all telecomms equipment, co-ordinate responsibility between operating switching, and transmission services; control and estimate spending; plan maintenance schedules and maintain quality control; and inspect outstations and equipment.

You would have sole responsibility for the efficient functioning of telegraph, telex, telephone and broadcast transmission equipment, supervise Senior Assistant Engineers, and train staff.

You must be MIEE or MIERE and preferably possess a degree in telecomms, electronics or electrical engineering. You should have at least 5 years' experience in a senior position in a telecomms organisation with full responsibility for engineering and administrative activities.

Your experience should cover radio relay and multiplex systems, maintenance and operation of step by step and common control automatic telephone and telex exchanges and subscriber's equipment including PABX distribution networks and open wire routes.

Starting salary is equivalent to £6145 - £7680pa and includes a substantial and normally tax-free allowance paid under Britain's overseas aid programme. Basic salary attracts a 25% tax-free gratuity.

Benefits include free passages, generous paid leave, children's holiday visit passages and education allowances, subsidised housing, appointment grant and interest-free car loan.

For full details and application form write quoting M1X/1202/WD to

**Crown Agents**

The Crown Agents for Oversea Governments and Administrations, Appointments Division,  
4 Millbank, London SW1P 3JD. /150

### ARTICLES FOR SALE

**60KHz MSF Rugby Receiver.** BCD TIME OF DAY OUTPUT. High performance, phase locked loop radio receiver. 5V operation with 1 second LED indication. Kit complete with tuned ferrite rod aerial £14.08 (including postage and VAT). Assembled circuit and cased-up version also available. Send for details Toolex, Sherborne (4359), Dorset. (21)

**RECHARGEABLE NICAD BATTERIES.** 'AA' (HP7) £1.26. 'Sub C' £1.29. 'C' (HP11) £2.38. 'D' (HP2) £2.92. PP3 £4.98. Matching chargers respectively £4.48, £4.48, £5.24, £5.24, £3.99, all prices include VAT. Add 10% post & package. SAE for full list, plus if wanted 50p for 'Nickel Cadmium Power' booklet, Sandwell Plant Power Ltd., 1 Denholm Road, Sutton Coldfield, West Midlands. B73 6PP. Tel No. 021-354 9784. (6554)

**VALVES RADIO** — T.V.-Industrial-Transmitting. We dispatch valves to all parts of the world by return of post, air or sea mail, 2,700 types in stock, 1930 to 1976. Obsolete types a speciality. List 20p. Quotation S.A.E. Open to callers Monday to Saturday 9.30 to 5.00. Closed Wednesday 1.00. We wish to purchase all types of new and boxed valves. Cox Radio (Sussex) Ltd., Dept WW, The Parade, East Wittering, Sussex PO20 5BN. West Wittering 2023 (STD Code 024366). (5392)

**SPOTWELDERS** new from £85. Sameside from £220. — Ring 01-540 7337/8. Rentweld's, 14 Clarendon Road, London S.W.19. (6518)

**ELECTRONIC INSTRUMENTATION.** If you are interested in the buying or selling of good quality used Electronic Test Instruments, ring Reading 51074, Martin Associates and converse with our Sheila Hatch who will deal promptly with your enquiry. (6758)

### INVERTERS

To operate mains equipment from 12v to 24v DC on automatic stand-by



Sine wave. Square wave. Self driven or Frequency controlled. Suitable for maintaining mains supply during power failure, running equipment where the mains is not available, or insulation from the mains. **Controlled battery charging incorporated.**

#### MAINS-STORE

Send for information to  
Interport Mains-Store Ltd.  
30 Old Bond Street, London W1  
Tel: 01-727 7042 or 0225 310916 (7140)

### E.M.I. VIDEO EFFECTS GENERATOR AND CONTROL PANEL

Type 895/896

Provides a wide variety of wipes and keying effects together with several special effects including a flashing pointer whose position on the screen may be varied. The principal facilities are for wiping between two picture sources in 11 patterns, selected by push-button controls therefore giving a total of 22 patterns. Quadrant lacer control. Self or external keying of 2 sources. Many other facilities. Systems — 625 line CCIR/GIRT. 525 line IRE EIA. Due to special purchase we have a few units only available complete with all necessary connectors, full instruction manual/circuits. All units new in original manufacturer's packing. PRICE £500 + £40 VAT each.

LEKTROPACKS, 17 Turnham Green Terrace London, W4. Tel. 01-994 2784

### 100 Resistors 75p

1/4W 5% c/FILM 2.2Ω—2.2MΩ (E12) 10 each of any value

C60 CASSETTES 32p  
C90 CASSETTES 45p

All Cassettes in Plastic Case with Index and Screwed Assembly

All prices include VAT

Quantity Discounts  
10 Units 5%  
50 Units 7%  
100 Units 10%

Add Postage 10p in £1

SALOP ELECTRONICS  
23 WYLE COP  
SHREWSBURY  
Tel. 53206 (7133)

### ENAMELLED COPPER WIRE

| s.w.g.   | 1lb reel | 1/2lb reel |
|----------|----------|------------|
| 10 to 19 | £2.95    | £1.60      |
| 20 to 29 | £3.15    | £1.80      |
| 30 to 34 | £3.45    | £1.90      |
| 35 to 40 | £3.65    | £2.10      |

All the above prices are inclusive of postage and packing in UK

#### COPPER SUPPLIES

102 Parrswood Road, Withington, Manchester 20  
Telephone 061-445 8753

**SITUATIONS VACANT**

# Nigerian Radio Technician

A radio technician is required to provide an installation and maintenance service for the Company's private radio systems in Nigeria.

The systems utilise HF, VHF and UHF equipment and the technicians must, in addition to basic training to City and Guilds intermediate level, have relevant experience in all these categories.

The technician will be based in the Lagos area, but frequent visits to other parts of Nigeria will be needed.

Salary will be negotiable.

All applicants should be of Nigerian nationality and should address their enquiries to:

**Company Radio Engineer  
George Wimpey & Co. Limited  
Stockwood Road  
Brislington  
Bristol**



(7143)

**ARTICLES FOR SALE**

**EXCLUSIVE OFFER**

**WORLD-WIDE RANGE  
NEVER BEFORE OFFERED**

**PHILCO HC-150 POINT-TO-POINT RADIO HF RECEIVERS** 2/30 m/cs. Ten fully tuneable channels to 0.5 kcs with synthesisers. Single and diversity reception on ISB, DSB, SSB with 4 sub-bands to each channel. Full details and prices on application.

**HIGHEST QUALITY 19" RACK MOUNTING CABINETS & RACKS**

**ENQUIRIES INVITED FOR NEW STOCKS NOW AVAILABLE**

**AUDIO AND INSTRUMENTATION-TAPE RECORDER-REPRODUCERS**

- \* Plessey ID33 Digital Units, 7 track 1/2"
- \* Plessey M5500 Digital Unit, 7 tracks 1/2"
- \* Ampex FR-1100, 6 speeds, stereo 1/2"
- \* Ampex FR600, 4 speeds, 7 tracks 1/2"
- \* D.R.I. RM1, 4 speeds, 4 tracks 1/2"
- \* EMI TR90 2 speeds, 1 track 1/2"
- \* EMI BTR1, 1 speed, 1 track 1/2"
- \* EMI R301G, 2 speeds, 2 tracks 1/2"
- \* EMI RE321 1/2", 7 1/2" 1 track
- \* Ficord 1A 1/4", 1 1/2", 7 1/2", 1 track
- \* Mincom CMP-100, 6 speeds, 7 tracks 1/2, 1"
- \* Leavers Rich DA-2P, 2 speeds, 2 tracks 1 1/2"
- \* Leavers Rich Console 2 track 1/2", 2 speeds

**Prices of above £70 to £500**

Also Transport Decks only available

We have a large quantity of "bits and pieces" we cannot list - please send us your requirements, we can probably help - all enquiries answered.

**All our aerial equipment is professional MOD quality**

- \* Davian Logic Testers ..... £20.00
- \* General Radio Strobotacs ..... £30.00
- \* Data Efficiency Respooler, 240v ..... £28.00
- \* Belling Lee 100 Amp Interference Filters ..... £78.00
- \* Airmec 201 Sig. Gen. 30 KCS/30 MCS ..... £78.00
- \* Valradio Invertors 12V DC/240V AC 300W ..... £42.00
- \* Oscilloscopes Gen. purpose 3" ..... £35.00
- \* Solartron CD 711/52 D/U Oscilloscopes ..... £110.00
- \* Airmec 702 Sig Gen. 30/300KCS ..... £35.00
- \* R-216 Power Supply Units ..... £15.00
- \* 10ft Lightweight Mast sections, 6" sides ..... £14.00
- \* Oscilloscope Trays from Transmitters ..... £12.00
- \* I.B.M. Video Display Units 4 col ..... £48.00
- \* 3AZP/2 C.R.T.s ..... £18.00
- \* Venner 5336 Counters ..... £40.00
- \* Autophon VHF Receivers 20/120mcs ..... £140.00
- \* Solartron CD 524 Oscilloscopes ..... £90.00
- \* 100 amp Belling Lee Interference Filters ..... £75.00
- \* Marconi TF2331 Distortion Meters ..... £160.00
- \* AVO VT Voltmeters CT-471A ..... £75.00
- \* Solartron Digital Voltmeters LM 1420/2 ..... £120.00
- \* Rascal MA197 Pre-Selectors ..... £65.00
- \* Marconi TF-888 Receiver Testers ..... £60.00
- \* Collins 500 watt 2/18 mcs. Transmitters ..... £1000.00
- \* Collins KW7E SSB 500w Transceivers ..... £1250.00
- \* Collins KW7E 200 m/w AM Transceivers ..... £750.00
- \* STC Rx5 2/25 mcs Receivers Diversity ..... £140.00
- \* Rack Mounting Operator Tables ..... £10.00
- \* Gaumo Kalee 384 Flutter Meters ..... £75.00
- \* Hewlett Packard 6188 Sig. Gen. 3.8/7.2 GHz ..... £120.00
- \* Rohm 95ft masts lattice 12" sides ..... P.U.R.
- \* 30ft Lattice Masts, 14" sides ..... £55.00
- \* 15ft Lattice Mast sections, 12" sides ..... £35.00
- \* 120ft Lattice Masts, 15" sides ..... P.U.R.
- \* 75/90ft Sky Towers, self-supporting ..... £475.00
- \* Heavy Aerial Rotators ..... P.U.R.
- \* Rascal SA 304 Voltage converters ..... £25.00
- \* Elliot Recording M/A Meters ..... £75.00
- \* 75ft Aluminium Lattice Masts, 20ft sides ..... £400.00
- \* Plessey peak distortion meters ..... £35.00
- \* Polarad Microwave power meters ..... £55.00
- \* Rhode & Schwarz SBR sig gen, 1.6/2.4 gmc ..... £70.00
- \* Large Aerial Turning Units ..... P.U.R.
- \* 45 feet Uniradio 4 Coax 50 ohms ..... £2.00
- \* Baluns Professional Exterior 600/75 ohms ..... £6.00
- \* Addo 5/8 Track Tape Punches ..... £48.00
- \* Quality Weather Vanes 8 contacts (unused) ..... £25.00
- \* Rascal MA-175 I.S.B. Modulators (new) ..... £45.00
- \* Inslide Cabinet Shelf Sliders ..... £3.00
- \* DG-7/42 or DG7/5 C.A.T.s ..... £3.00
- \* Tally 5/8 Track Tape Readers 60 cps ..... £48.00
- \* Tally 5/8 Track Tape Readers Track Spooling ..... £65.00
- \* Cawkell FU 4 Band Pass Filter Testers ..... £60.00

We have a quantity of Power Transformers 250 watts to 15kVA at voltages up to 40KV. Best quality at low prices. Lists available.

- \* Rascal RA-63 SSB Adaptors, new ..... £70.00
- \* Rascal RA-237 L-V Converters, new ..... £70.00
- \* Portable Mains Battery Hospital Lights ..... £24.00
- \* 400 Channel Pulse Height Spectrum Analyzers ..... £600.00

We have a varied assortment of industrial and professional Cathode Ray Tubes available. List on request.

**PLEASE ADD CARRIAGE AND V.A.T.**

**P. HARRIS**  
ORGANFORD - DORSET  
BH16 6BR  
BOURNEMOUTH (0202) 765051

(33)

**ARTICLES FOR SALE**

**PHOTO ETCH LIMITED**  
9 LOWER QUEEN STREET  
PENZANCE, CORNWALL  
TR18 4DF

Prototype or long run - we will supply your printed circuit requirements.

Also facilities for Design, Assembly and Test

Prompt and efficient service assured

contact David Webster  
PENZANCE (07381) 4478 56

**TELEPHONE ANSWERING Machines for Sale.** New £120. Answers and Records. Plus 2-way Conversations and Dictation. Free Accessories and guaranteed 1 year. Callsaver. C.R.V. Electronics Ltd, 01-249 0416, 01-580 1800. 30 Goodge Street, London W1.

**CASSETTE HEADS AND MECHANISM.** Three-head cassette system; allows off-tape monitoring; Four-in-Line cassette record/play head; Ferrite record/play stereo head; top loading stereo cassette mechanism with piano key controls. For full technical data send A4 s.a.e. Box No. WW 7139. (7139)

**BRENELL MK 6** tape transport with Bogen heads and Hart Electronics, Stuart circuits. Cased, needs further attention. Offers - M. Mills, 144 Blackbrook Road, Fareham, Hants PO15 5BY. (7135)

**2 MOTOROLA Page Boy III** and 20 capacity encoder, almost new, £450 plus VAT. Would exchange Storno High/Band equipment. Also 25KC Storno Viscounts £25 each. - Thamesdon Communication, 0793 72401. (7136)

**ILIFFE BOUND** Wireless World 1940-1957 inclusive, complete used reference only, in excellent condition. Offers. - 16 Ennerdale Drive, Aughton, Ormskirk L39 5HF. (7137)

# Glaxo

## ELECTRONICS TECHNICIAN

We require an Electronics Technician, preferably under the age of 35, to assist in the maintenance and construction of electronic instruments in our Research Laboratories at Greenford and neighbouring sites.

The successful applicant will be a member of a small team responsible for the design and servicing of a wide range of electronic instruments used in our chemistry and biological laboratories.

A qualification equivalent to O.N.C. or H.N.C. would be an advantage. Consideration would be given to granting day-release for further training.

The appointment will be made in our Technical Officer grade. The minimum starting salary would not be less than £2,732 per annum (including supplement and London Allowance) but could be higher for those with experience. Present scale maximum rises to above £4,800 per annum.

There are pension and bonus schemes and four weeks' annual holiday entitlement.

Please write or telephone for an application form, quoting Ref ZH/155 to:



**Mr. R. E. Nolan, Personnel Officer  
GLAXO RESEARCH LIMITED  
Greenford, Middlesex. Tel. 01-422 3434**



## ARTICLES FOR SALE

### MAGNETIC MICROPHONE SPEAKERS

4T inserts, ideal for all sound speaking and listening applications. Very rugged. DC res. 20 ohms.  
Size: 1 1/2" dia. 3/4" deep.  
40p ea. + 10p P&P.  
6 for £2.20 + 20p P&P.  
12 for £4.50, P&P free.  
S.A.E. for list. Many other items. Trade enquiries welcome.

**B.B. SUPPLIES, 141 Shalford Street  
Nr. CANTERBURY, Kent CT4 7QZ**  
(6792)



### Best choice for used TV

• Largest stock and selection of colour and mono TV in Britain.  
• 1976 exports exceeded 250,000 sets.

Trade enquiries to:

**Midland TV Trade Services,  
Worcester Road, Kidderminster DY10 1HY,  
England. Tel. Kidderminster 61907 or 67390.  
Telex 337993** (7130)

## CAPACITY AVAILABLE

### ANY CAPACITY WIRING AND ASSEMBLY PCBs CABLE FORMS, etc.

Collection and delivery refs. available.

**LESLIE TROUT & CO. LTD.**  
01-699 2395 (7174)

**AIRTRONICS LTD.,** for Coil Winding — large or small production runs. Also PC Boards Assemblies. Suppliers to P.O., M.O.D., etc. Export enquiries welcomed, 3a Walerand Road, London SE13 7PE. Tel: 01-852 1706. (61)

**SMALL BATCH PRODUCTION** wiring, assembly to sample or drawings. Specialists in printed circuit assembly. Rock Electronics, 41 Silver Street, Stansted, Essex. Tel. Stansted (0279) 33018/814006. (19)

**PRINTED CIRCUIT BOARDS** — Quick deliveries, competitive prices, quotations on request, roller tinnings, drilling, etc., speciality small batches, larger quantities available Jamiesons' Automatics Ltd., 1-5 Westgate, Bridlington, N. Humberside, for the attention of Mr. J. Harrison. Tel: (0262) 4738/77877. (18)

**AIRTRONICS LTD.** for coil winding. Large or small production runs. Bobbin — Layer — Wave — Bifilar — Miniature — Toroidals. Airtronics Limited, Gardner Industrial Estate, Kent House Lane, Beckenham, Kent BR3 7UG. Tel. 01-659 1147. (7158)

**CAPACITY AVAILABLE** for small batch production wiring and assembly of cableforms, p.c.b.'s gun wire wrapping's mech. assembly and spot welding. Contact Citronics, 36 Coles Road, Milton, Cambridge. Tel Cambridge 861305. (7164)

## SERVICE AND REPAIRS

### EURO CIRCUITS

Printed Circuit Boards — Master layouts — Photography — Legend printing — Roller tinning — Gold plating — Flexible films — Conventional fibre glass — No order too large or too small — Fast turnaround on prototypes. All or part service available NOW

**EURO CIRCUITS TD.**  
Highfield House  
West Kingsdown  
Nr. Sevenoaks, Kent. **WK2344**

**LABELS, NAMEPLATES, FASCIA'S** on aluminium or plastic. Speedy delivery G.S.M. Graphic Arts Ltd., 1-5 Rectory Lane, Gulsborough (02873-4443), Yorks, U.K. (13)

**ARTWORK LAYOUTS** by experienced draughtsmen manufacturing facilities available to every requirement. For all enquiries please write to H.C.B. Artwork Designs, 3 Roden Street, Ilford, Essex. (7193)

## ARTICLES WANTED

### WANTED IN LARGE QUANTITIES

Electronic components, resistors, capacitors, potentiometers, chassis, loudspeakers, semi-conductors, diodes, TV tubes, especially colours, etc., etc. 1st and 2nd grades. Finished or incomplete products, record players, amplifiers, radios, tuners, tape recorders, enclosures, etc., etc., etc.  
We will buy complete factories and pay cash.

Telephone 01-491 4636  
E.C.E. Avon House  
360-366 Oxford Street  
London W1N 9HA

7167

### WE PURCHASE ALL FORMS OF ELECTRONIC EQUIPMENT AND COMPONENTS, ETC.

SPOT CASH  
**CHILTMead LTD.**  
7, 9, 11 Arthur Road  
Reading, Berks.  
Tel. (0734) 582 605

### ★ MINICOMPUTERS ★ PERIPHERALS ★ INSTRUMENTATION

For fastest, best CASH offer, phone

**COMPUTER APPRECIATION**  
Godstone (088 384) 3221

**WANTED, all types of communications receivers and test equipment.** Details to R. T. & I. Electronics Ltd., Ashville Old Hall, Ashville Rd., London, E.11, Ley 4986. (63)

**SURPLUS COMPONENTS, Equipment and Computer panels wanted for cash.** Ring Southampton 772501. (16)

**WE BUY** new valves, transistors and clean new components, large or small quantities, all details, quotations by return. — Walton's, 55 Worcester St., Wolverhampton. (62)

**WANTED . . . CRYSTALS, new or used, any frequency, any quantity.** HC6U/HC25U/HC18U only. W. H. Westlake, Clawton, Holsworthy, Devon. (7162)

**B-D ELECTRONICS** offer prompt settlement for your surplus components. Our main field of interest is consumer electronics. Please telephone our Miss Hughes, Peterborough (0733) 265219. (22)

## EQUIPMENT WANTED

### BROADFIELDS AND MAYCO DISPOSALS

21 Lodge Lane, N. Finchley  
London, N12 8JG  
Telephone:  
01-445 2713

01-445 0749 01-958 7624

**WE ARE INTERESTED IN PURCHASING ALL KINDS OF RADIO, T.V. AND ELECTRONIC COMPONENTS AND EQUIPMENT IN BULK QUANTITIES. WE PAY PROMPT CASH AND CLEAR MATERIAL BY RETURN.** (46)

### ★ MINICOMPUTERS ★ PERIPHERALS ★ INSTRUMENTATION

For fastest, best CASH offer, phone:

**CHILTMead LTD.**  
Reading (0734) 586419

### WANTED: TEST AND COMMUNICATION EQUIPMENT



single items or quantities, also RF plugs, sockets and connectors.

Call or phone.

170 Goldhawj Road, London, W.12  
01-743 0899 (7006)

### TOP CASH AVAILABLE for NEW SURPLUS-COMPONENTS

All details to:  
**SKYWAVE ELECTRONICS**  
01-568 1331

**RADFORD VALVED AMPLIFIERS, STA 100, STA60, STA25, STA 15, power amps. SC22 pre-amps. FM tuners. Good prices paid. — Details to 64A Walbrook Road, Derby.** (7138)

**WANTED: Test equipment, RF power transistors, and components of VHF/UHF type. Immediate cash available. Modular Electronics. Phone: 024-361 2916, Mr Craig.** (7183)

**BACK NUMBERS. W/W 1965 to date (7 missing). Electronics Eng. 1964 to June 72 (1 missing). Offers invited, Cooke, Court Dr., Shillingford, Oxon. Tel Warborough 8491.** (7160)

**WANTED: Modulation Monitor/Deviation Meter AM/FM Signal Generator Power Meter (R.F.), Mobile Radio Test Set (TF2950). Double Beam 'Scope and any test equipment suitable for mobile radio testing. Cash paid for clean goods. Tel: 03742 71724.** (7165)

**ALL SURPLUS or used equipment wanted. Radio telephones — complete systems purchased. Ships equipment and small boat radio's — components, partly assembled chassis etc, etc. Established 20 years. For prompt attention contact Mr Grout at Worthing 34897. GWM Radio Limited 40/42 Portland Road, Worthing, Sussex.** (6594)

**WILL BUY ANYTHING, any quantity if price is right ring Stan Willetts, West Bromwich, 021 553 0186.** (6815)

## RECEIVERS AND AMPLIFIERS

**HRO Rx5s, etc., AR88, CR100, BRT400, G209, S640, etc., etc., in stock. R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E11, Ley 4986.** (65)

**SIGNAL Generators, Oscilloscopes, Output Meters, Wave Voltmeters, Frequency Meters, Multi-range Meters etc., etc. in stock. R. T. & I. Electronics Ltd., Ashville Old Hall, Ashville Rd., London, E.11, Ley 4986.** (64)

## COURSES

### The Polytechnic of North London

### Department of Physics

#### B. Sc.(Hons.) THE PHYSICS AND TECHNOLOGY OF ELECTRONICS

A four-year sandwich course dealing with the theory, practice and applications of physics and electronics, including solid-state physics, integrated circuits, microwaves, lasers, nuclear physics, computers and computing.

#### B.Sc.(Hons.) and B.Sc. SCIENCE

These are three-year full-time or five-year part-time modular degree courses offering a wide choice of units, of which up to two-thirds may be in physics (including electronics) and the remainder in mathematical and computing subjects, if desired.

#### M.Sc. THE PHYSICAL BASIS OF ELECTRONICS

Available as a one-year full-time, two-year part-time and three-year evenings-only courses for graduates in Physics, Electrical Engineering and allied disciplines.

#### H.N.C. IN APPLIED PHYSICS

A two-year day-release course, including electronics, vacuum physics and spectroscopy. For technicians and others with suitable O.N.C. A-levels or equivalent.

#### RESEARCH DEGREES

There are active research groups in magnetic properties of thin films and data-storage techniques, particle counting and cosmic-ray physics, plasma physics and spectroscopy.

Further details may be obtained from:

The Secretary, Physics Department  
(Ref. WW1)  
**THE POLYTECHNIC OF NORTH LONDON**  
Holloway Road, London N7 8DB  
(Ref. 01-607 2789, Ext. 2180) 7129

**RADIO and Radar M.P.T. and C.G.L.I. Courses. Write: Principal, Nautical College, Fleetwood, FY7 8JZ.** (25)

## BOOKS

We are the U.K.'s leading stockists of

### TEXAS INSTRUMENTS TECHNICAL PUBLICATIONS

Data Books, Text Books, 9900 Software, etc.

Send S.A.E. for leaflet and Price List

### BEDFORD DISTRIBUTION CO

Dept W, St Johns Works, Bedford (71855)

**"VINTAGE CRYSTAL SETS, 1922-1927"**. Just published by Wireless World, contains 128 pages. Chapters on the first days of broadcasting. The Crystal Set, Vintage Wireless Trademarks. Also catalogue sections listing and describing crystal sets together with their original prices in £:s:d. A book for the collector or those interested in nostalgia. Available from main bookshops or direct from us. Please send £2.80 inclusive to IPC Business Press Ltd., Room 11 Dorset House, Stamford Street, London, SE1 9LJ. (6125)

## TAPE RECORDING ETC.

**YOUR TAPES TO DISC.** Mono or Stereo Cutting. Vinylite Pressings. Sleeves/Labels. Top professional quality. S.A.E. for photo leaflet. **HEROY Records, "Eastwood," Cove Dunbartonshire, Scotland.** (82)

# SPECIAL LOW PRICE ARRANGEMENTS FOR VISITING OVERSEAS TRADE FAIRS



IPC Electrical-Electronic Press Ltd., the world's largest publishers of computer, electrical and electronic journals, have made special arrangements for readers wishing to visit important overseas trade fairs. The cost, in most cases, is little more than the normal air fare but includes – travel by scheduled airline from Heathrow and Manchester \* first-class hotel accommodation \* arrival and departure transfers \* admission to the trade fair \* services of an experienced tour manager. The current programme comprises the following tours.

To obtain a brochure and booking form, tick the box against the tours in which you are interested, complete the coupon and post to the exclusively appointed travel agent, Commercial Trade Travel Ltd., Carlisle House, 8 Southampton Row, London WC1. Telephone 01-405-8666 or 01-405-5469.

- |   |          |                  |   |        |                     |
|---|----------|------------------|---|--------|---------------------|
| Hanover Fair <input type="checkbox"/>   | Hanover, | April 20-28 1977 | International Exhibition of Computers and Peripheral equipment – SYSTEMS <input type="checkbox"/> | Munich | October 17-21 1977  |
| International Electric Vehicle Exhibition and Conference <input type="checkbox"/>               | Chicago  | April 26-29 1977 | Internecon/Industrial Electronik <input type="checkbox"/>   | Vienna | November 9-12 1977  |
| Computer, Systems & Peripheral Exhibition & Conference – COMPEC EUROPE <input type="checkbox"/> | Brussels | May 10-12 1977   | International Exhibition for Electronic Production – PRODUCTRONICA <input type="checkbox"/>       | Munich | November 22-26 1977 |

Please send details of the tours indicated above.

NAME ..... COMPANY .....

ADDRESS ..... Telephone .....

# Two books from Wireless World

These books are of very special appeal to all concerned with designing, using and understanding electronic circuits. They comprise information previously included in Wireless World's highly successful


Circards – regularly published cards giving selected and tested circuits, descriptions of circuit operation, component values and ranges, circuit limitations, modifications, performance data and graphs. Each of these magazine-size hard cover books contains ten sets of Circards plus additional circuits and explanatory introduction.

## circuit designs

1

Collected Circards

PWilliams/J Carruthers/JHEvans/JKinsler

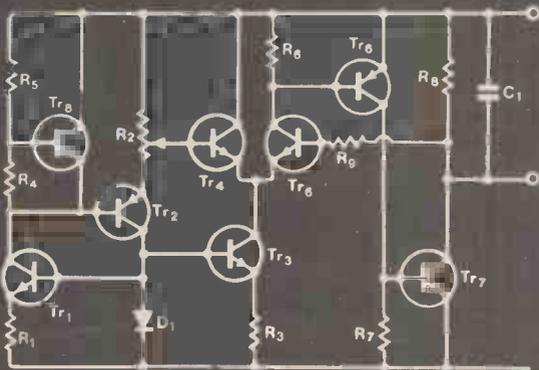

A WIRELESS WORLD PUBLICATION

### BOOK 1

Basic active filters  
Switching circuits  
Waveform generators  
AC measurements  
Audio circuits


Constant-current circuits  
Power amplifiers  
Astable circuits  
Optoelectronics  
Micropower circuits

## circuit designs

2

Collected Circards

PWilliams J Carruthers JHEvans JKinsler

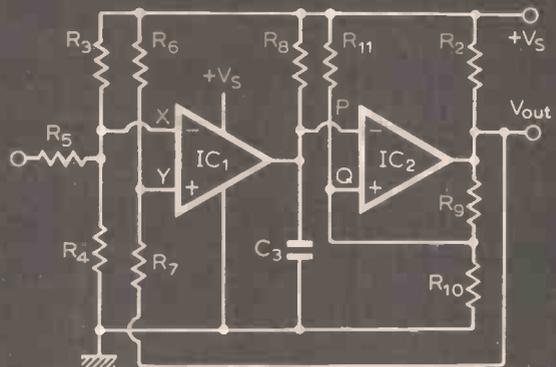

A WIRELESS WORLD PUBLICATION

### BOOK 2

Basic logic gates  
Wideband amplifiers  
Alarm circuits  
Digital counters  
Pulse modulators

C.d.as – signal processing  
C.d.as – signal generation  
C.d.as – measurement and detection  
Monostable circuits  
Transistor pairs

### ORDER FORM

To : General Sales Department,  
IPC Business Press Limited,  
Room 11, Dorset House,  
Stamford Street, London SE1 9LU.

Please send me.....copy/copies of  
Circuit Designs – Number 1 at £10.40   
Circuit Designs – Number 2 at £12.50   
each inclusive. I enclose remittance value £.....  
(cheques payable to IPC Business Press Ltd.)

Name (please print) .....

Address .....

Company registered in England and a subsidiary of Reed  
International Limited Registered No. 677128 Regd. office  
Dorset House, Stamford Street, London SE1 9LU.

# I.C.E. MULTIMETERS

## TWICE the information in HALF the size

The I.C.E. range of multimeters provides an unrivalled combination of maximum performance within minimum dimensions, at a truly low cost. Plus, a complete range of add-on accessories for more ranges, more functions.

All I.C.E. multimeters are supplied complete with unbreakable plastic carrying case, test leads, etc., and a 50-plus page, fully detailed and illustrated Operating and Maintenance Manual.

Now available from selected stockists. Write of phone for list, or for details of direct mail-order service.

### Supertester 680R (illustrated)


20kΩ/V. ±1% fsd on d.c.  
4kΩ/V. ±2% fsd on a.c.  
80 Ranges — 10 Functions  
140 x 105 x 55mm  
**£25.25 + VAT**

### Supertester 680G

20kΩ/V. ±2% fsd on d.c.  
4kΩ/V. ±2% fsd on a.c.  
48 Ranges — 10 Functions  
109 x 113 x 37mm  
**£19.95 + VAT**
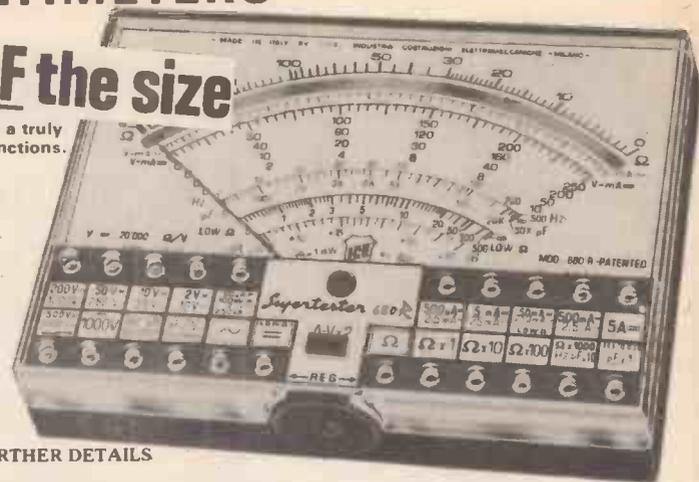
### Microtest 80

20kΩ/V. ±2% fsd on d.c.  
4kΩ/V. ±2% fsd on a.c.  
40 Ranges — 8 Functions  
Complete with case — only 93 x 95 x 23mm  
**£14.95 + VAT**



Electronic Brokers Ltd.  
49-53 Pancras Road, London NW1 2QB  
Tel. 01-837 7781

WW—111 FOR FURTHER DETAILS

## INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 130-141

|                                | PAGE                    |                                   | PAGE         |                                   | PAGE        |
|--------------------------------|-------------------------|-----------------------------------|--------------|-----------------------------------|-------------|
| Acoustical MFG Co. Ltd.        | 2                       | Hall Electric Ltd.                | 77           | Q. Max Electronics Ltd            | 22          |
| Adcola Products Ltd.           | 25                      | Harmsworth Townley & Co. Ltd.     | 33           | Radio Component Specialists       | 99          |
| AEL Crystals Ltd.              | 102                     | Harris Electronics (London) Ltd.  | 6, 24        | Ralfe, P. F.                      | 105         |
| Allen & Heath                  | 6                       | Harris P.                         | 139          | R.C.S. Electronics                | 27          |
| Amateur Components             | 124                     | Hart Electronics                  | 115          | REL Equipment & Components Ltd.   | 90          |
| Ambit International            | 105, 111                | Herbert Controls Ltd.             | 14           | R.S.T. Valves Ltd.                | 107         |
| Antex                          | 17                      | Heyco Mfg. Co. Ltd.               | 92           | RTVC                              | 113         |
| Aspen Electronics Ltd.         | 28                      | ICI Arklone                       | 23           | Samsons (Electronics) Ltd.        | 95          |
| Astra-Pak                      | 127                     | Icon Designs                      | 32           | Schrader Electronics              | 106         |
| Audio Fair                     | 128                     | ILP Electronics Ltd.              | 110          | Scopex Instruments Ltd.           | 112         |
| Audix Ltd.                     | 112                     | IMO Precision Controls Ltd.       | 5            | Scott, J. (Elec. Eng.) Ltd.       | 10          |
| Barr & Stroud Ltd              | 8                       | Industrial Tape Applications      | 119          | Semicon Indexes Ltd.              | 104         |
| Barrie Electronics Ltd.        | 111                     | Integrex Ltd.                     | 96, 97       | Service Trading Co.               | 103         |
| Bell & Howell                  | 4                       | Interport Mains Store Ltd.        | 138          | Shure Electronics Ltd.            | Cover iii   |
| Belling & Lee Ltd.             | 33                      | ITT Instrument Services           | 89           | Sinclair Instruments Ltd.         | 126         |
| Bentley Acoustic Corp. Ltd.    | 115                     | KEF Electronics Ltd.              | 11           | Sintel                            | 117         |
| Bi-Pak Semiconductors Ltd.     | 100, 101                | Ledon Instruments Ltd.            | 16           | SME Ltd.                          | 19          |
| Bi-Pre-Pak Ltd.                | 116                     | Leevers-Rich Equipment Ltd.       | 30           | Sowter, E.A.                      | 140         |
| Boss Industrial Mouldings Ltd. | 6                       | Levell Electronics Ltd.           | 3            | Special Products Ltd.             | 94          |
| Bull, J.                       | 118                     | Light Soldering Developments Ltd. | 93           | SST Distributors                  | 106         |
| Cambridge Learning             | 12                      | Lloyd J. J. Instruments Ltd.      | 21           | Stirling Sound (Bi-Pre-Pak Ltd.)  | 116         |
| Catronics                      | 111                     | London Instrument Repairs         | 116          | Storno Ltd.                       | 92          |
| CEC Corporation                | 12                      | Lyons Instruments                 | 102          | Strumeh Engineering Ltd.          | 29          |
| Chiltmead Ltd.                 | 125                     | Lynx (Electronics) London Ltd.    | 119          | Sugden, J. E. & Co. Ltd.          | 27          |
| Circuit Designs                | 143                     | McKnight Crystals                 | 140          | Surrey Electronics Ltd.           | 106         |
| Colomor (Electronics) Ltd.     | 94                      | MacInnes Laboratories Ltd.        | 18           | Swanley Electronics Ltd.          | 124         |
| Comark Electronics             | 106                     | Maplin Electronic Supplies        | 9            | Swift of Wilmslow                 | 98          |
| Commercial T/Travel            | 142                     | Marconi Instruments Ltd.          | Cover ii     | Technomatic Ltd.                  | 127         |
| Compcor Electronics            | 92                      | Marshall, A. & Sons (London) Ltd. | 98           | Tektronix (Teleguipment) Ltd.     | 34          |
| Crimson Elektrik               | 105                     | Maughan, Thos. & Associates Ltd.  | 117          | Teleprinter Equipment Ltd.        | 98          |
| Crofton Electronics Ltd.       | 92                      | MCP Electronics                   | 31           | Television                        | 107         |
| Dana Electronics Ltd.          | 30                      | Metac-Electronics & Time Centre   | 92           | Telford Communications            | 27          |
| Data Dynamics                  | 106                     | Modern Book, The                  | 140          | Thomson, C. S. F.                 | 78          |
| Dema Electronics International | 93                      | Multicore Solders Ltd.            | Cover iv     | Trampus Electronics               | 102         |
| Eagle International            | 22                      | Neal                              | 24           | Triangle Digital Services         | 30          |
| Eddystone Radio Ltd.           | 18                      | Nombrex (1969) Ltd.               | 93           | Trident Audio Developments Ltd.   | 89          |
| Edicron Ltd.                   | 16                      | OMB Electronics                   | 27           | Turner Electronic Industries Ltd. | 90          |
| Electronic Brokers Ltd.        | 114, 120, 122, 123, 144 | Orchard Electronics               | 120          | United-Carr Supplies Ltd.         | 10          |
| Electroplan Ltd.               | 29                      | Patrick, J. B.                    | 129          | Valradio Ltd.                     | 14          |
| Electro-Tech Components Ltd.   | 114                     | Phonosonic                        | 90           | West Hyde Developments Ltd.       | 121         |
| Environmental Equipments Ltd.  | 102                     | Powertran Electronics             | 108, 109     | Whiteley Electrical Co. Ltd.      | 8           |
| Erie Electronics Ltd.          | 24, 28                  | Precision Instruments Ltd.        | 26           | Wilmot Breeden Electronics Ltd.   | 13          |
| ES Electronics                 | 124                     | Precision Petite Ltd.             | 94           | Wilmslow Audio                    | 129         |
| E.S.P.                         | 28                      | Purnell                           | Loose insert | Z. & I. Aero Services Ltd.        | 22, 27, 104 |
| Farnell Instruments Ltd.       | Readers Card, 20        | Pye Unicam Ltd.                   | 15           | Zettler (UK) Division             | 14          |
| Future Film Developments       | 105                     |                                   |              |                                   |             |
| Fyld Electronic Comps. Ltd.    | 16                      |                                   |              |                                   |             |
| G.D.S.                         | 7                       |                                   |              |                                   |             |
| Gardners Transformers          | 31                      |                                   |              |                                   |             |
| Genrad Ltd.                    | 91                      |                                   |              |                                   |             |
| Greenwood Electronics Ltd.     | 20                      |                                   |              |                                   |             |

### OVERSEAS ADVERTISEMENT AGENTS:

France: M. D. Soubeyran, Compagnie Francaise D'Editions, Division Internationale, 40 Rue du Colisee, Paris 8e Telephone: 225-77-50 — Telex 280274.

Hungary: Mrs. Edit Bajusz, Hungexpo Advertising Agency, Budapest XIV, Varosliget Telephone: 225 008 — Telex: Budapest 22-4525 INTFOIRE.

Italy: Sig. C. Epis, Etas-Kompass, S.p.a. — Servizio Estero, Via Mantegna 6 20154 Milan Telephone 347051 — Telex 37342 Kompass

Japan: Mr. Inatsuki, Trade Media — IBPA (Japan), B212 Azabu Heights, 1-5-10 Roppongi, Minato-ku, Tokyo 106. Telephone: (03) 585-0581

United States of America: Ray Barnes, IPC Business Press, 205 East 42nd Street, New York, NY 10017 — Telephone: (212) 689 5961 — Telex 421710. Mr. Jack Farley Jr., The Farley Co., Suite 1584, 35 East Wacker Drive, Chicago, Illinois 60601 — Telephone: (312) 63074

Mr. Richard Sands Scott Marshall, Sands & Latta Inc. 5th Floor 85 Post Street, San Francisco, California 94104 — Telephone: (415) 421 7950 — Telegrams: Dascotico, San Francisco

Mr. William Marshall, Scott, Marshall, Sands & Latta Inc., 1830 West Eighth Street, Los Angeles, California 90057 — Telephone: (213) 382 6346 — Telegrams: Dascotico, Los Angeles

Mr. Jack Mentel, The Farley Co., Suite 650 Ranna Building, Cleveland, Ohio 44115 — Telephone: (216) 621 1919. Mr. Ray Rickles, Ray Rickles & Co., P.O. Box 2008, Miami Beach, Florida 33140 — Telephone: (305) 532 7301. Mr. Jim Parks, Ray Rickles & Co., 3116 Maple Drive N.E., Atlanta, Georgia 30305. Telephone: (404) 237 7432. Mike Loughlin, IPC Business Press, 15055 Memorial, Ste 119, Houston, Texas 77079 — Telephone: (713) 783 8673.

Canada: Mr. Colin H. MacCulloch, International Advertising Consultants Ltd., 915 Carlton Tower, 2 Carlton Street, Toronto 2 — Telephone: (416) 364 2269.

\*Also subscription agents



## Small wonder.

One of the world's smallest dynamic-element lavalier microphones is designed to be heard, not seen. Other mini-mics may be O.K. at first, but, as you know, there have been problems with sudden failures... sometimes on the air! The new Shure SM11 lavalier solves the problem with an unusually high quality dynamic element that delivers all the reliability of a desk microphone—yet it weighs less than a third of an ounce.

Rugged, all-around durability and a

field-serviceable design keeps this new breed of lavalier on the air when you need it most. Without batteries or unnecessary wiring. And without a big price tag either. The SM11 has everything: size, performance, durability, price. That's not just small talk!

Shure Electronics Limited  
Eccleston Road,  
Maidstone ME15 6AU  
Telephone: Maidstone (0622) 59881

### TECHNICORNER

Frequency Response: 50 to 15,000 Hz  
Polar Pattern: Omnidirectional  
Impedance: 150 ohms (200 ohms actual) for connection to microphone inputs rated at 25 to 200 ohms  
Hum Pickup: Less than 35.3 dB equivalent SPL in a 1 millioersted field  
Accessories Supplied: Specially designed lavalier assembly; clip-on clasp; tie-rack assembly; connector belt clip.



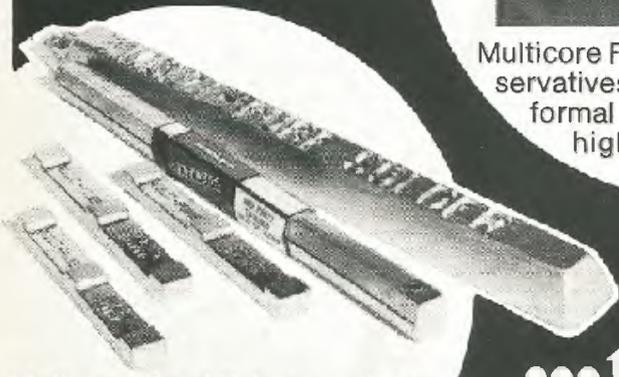
# “There’s a lot more to Multicore...”



Multicore Fluxes, Chemicals, Preservatives, Cleaners and Conformal Coatings. For highest quality soldering.




Multicore Oxide-free Solder Creams. For microcircuits and P.C.'s. Also a wide variety of pre-forms for repetitive soldering operations.



Multicore Solid Solders. In Bars, Ingots, Sticks, Wire or Pellets. For all dip and wave-soldering.

## ...than meets the iron!

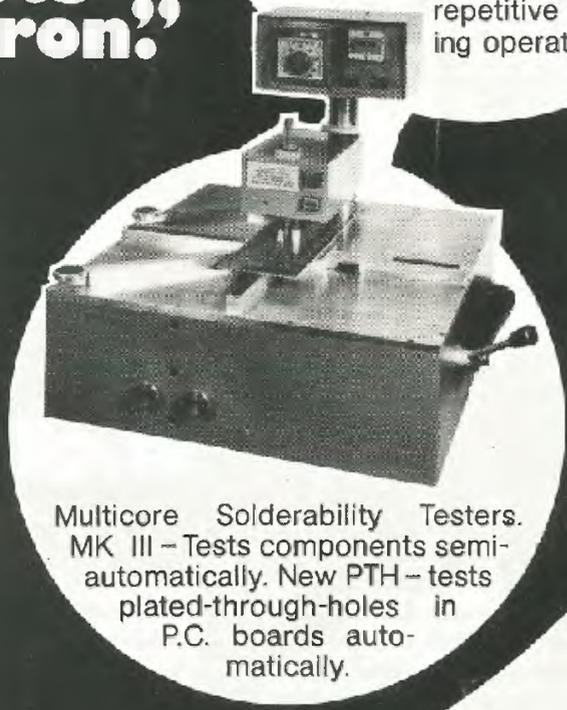

Multicore Solderability Testers. MK III - Tests components semi-automatically. New PTH - tests plated-through-holes in P.C. boards automatically.



Multicore now solders the 'impossible'. ALU-SOL 45D solders most types of aluminium and has a good corrosion resistance. Arax 96S for difficult stainless steels, being non-toxic and bright.



### “The name that stands for quality and quantity.”

Please write on your Company's letterhead for further details on your particular application.

**Multicore Solders Limited,**

Maylands Avenue, Hemel Hempstead, Herts HP2 7EP. Tel: Hemel Hempstead 3636. Telex: 82363.