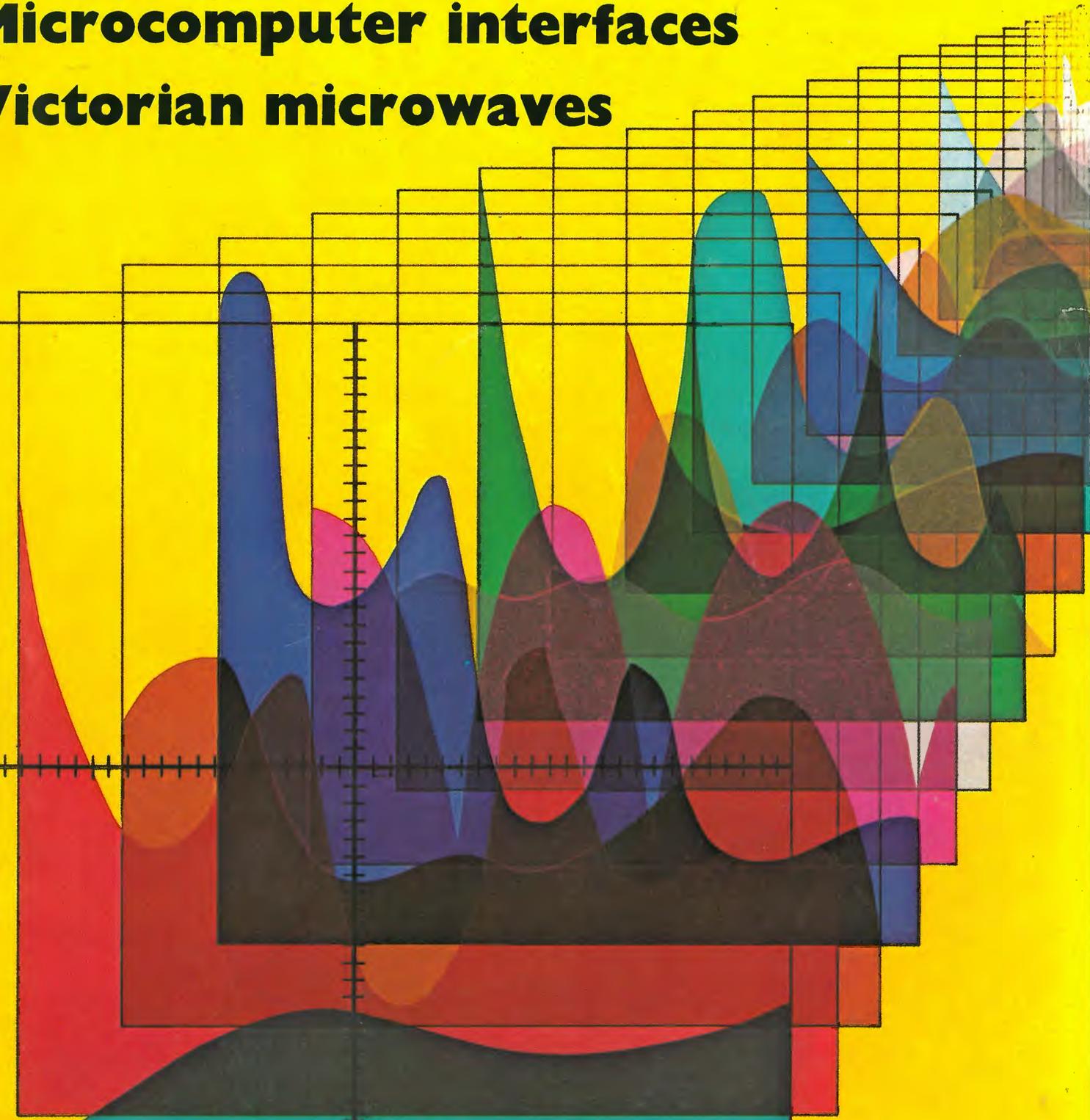


wireless world

SEPTEMBER 1979 50p

Microcomputer interfaces
Victorian microwaves



Log. sweep generator

Whether you need the flexibility made possible by two independent time bases as in the D67A, or the cost saving virtues of the D66A with its single time base, you will still get 25MHz bandwidth in dual trace mode. And both come complete with those unique Telequipment attributes, high performance, high reliability and sheer value for money. Find out more, ask for our 36 page catalogue. It's quite free.

TELEQUIPMENT

Tektronix UK Ltd., PO Box 69, Coldharbour Lane, Harpenden, Herts. AL5 4UP.
Tel: Harpenden 63141.

Dual trace 25MHz with a choice of timebases



Front cover is 'Waves-torm', an abstract design by Betty Palmer based on displays from Alan Ainslie's sweep generator, described in this issue.

Multimode two-metre transceiver. Advanced design will operate in s.s.b., f.m. and c.w. modes over the 144-146MHz amateur band.

Loudspeaker directivity and sound quality. How variation in speaker polar diagram with frequency affects quality — and methods of measurement.

How Michael Gerzon's soundfield microphone (News, August 1978) can in effect be adjusted after recording and protect recordings from obsolescence.

Current issue price 50p, back issue (if available) £1.00, at Retail and Trade Counter, Paris Garden, London SE1. Available on microfilm: please contact editor.

By post, current issue 65p, back issues (if available) £1.00, order and payments to Room CP34, Dorset House, London SE1 9LU.

Editorial & Advertising offices: Dorset House, Stamford Street, London SE1 9LU.

Telephones: Editorial 01-261 8620. Advertising 01-261 8339.

Telegrams/Telex: Wiworld Bispres 25137 BISPRS G. Cables Ethaworld, London SE1.

Subscription rates: 1 year £9.00 UK and \$31 outside UK.

Student rate: 1 year, £4.00 UK and \$15.50 outside UK.

Distribution: 40 Bowling Green Lane, London EC1R 0NE. Telephone 01-837 3636.

Subscriptions: Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. Telephone 0444 59188. Please notify a change of address.

USA mailing agents: Expeditors of the Printed Word Ltd, 527 Madison Avenue, Suite 1217, New York, NY 10022. 2nd-class postage paid at New York.

© IPC Business Press Ltd, 1979
ISSN 0043 6062

wireless world

ELECTRONICS/TELEVISION/RADIO/AUDIO

SEPTEMBER 1979 Vol 85 No 1525

41 Good, clean fun

42 Logarithmic audio sweep generator
by A. C. Ainslie

48 Novatexts
by P. Williams

50 World of amateur radio

51 Sidebands as phasors
by J. M. Osborne

55 Auditory cues in stereophony
by Philip Vanderlyn

61 A scientific computer — 6
by J. H. Adams

63 Sixty years ago

64 Selecting stabilizer thermistors for Wien-bridge oscillators
by M. Salem

67 Microcomputer interfaces — 1
by Ian H. Witten

70 Literature received

71 News of the month
Viewdata for America Post Office monopoly

75 Circuit ideas
L.e.d. flashers Differential rumble filter

79 Letters to the editor
Engineers victims of market Audio kits
T.h.d. measurement

83 Passive notch filters — 2
by G. Kalanit

87 Linear voltage-controlled oscillator
by J. H. Linsley Hood

91 Video disc battle looms

93 Victorian microwaves
by K. L. Smith

96 New products

98 Sidebands
byk Mixer

ibpa
International Business
Press Associates

ABC
BUREAU OF THE ADVERT
SPECIAL OF CIRCULATIONS

THINK OF A SHAPE



S 500D — dual channel
up to 500W/RMS per
channel DC-20 KHZ

Whatever it is, the **H||H** 'S' range of power amplifiers will handle it

The **H||H** 'S' range is designed to handle heavy industrial usage in the fields of vibrator driving, variable frequency power supplies and servo motor systems.

S 500D

Dual Channel
19" rack mount 3½" high
500w r.m.s. into 2.5 ohms per channel
900w r.m.s. in bridge mode
DC-20 KHZ at full power
0.005% harmonic distortion (typical) at
300w r.m.s. into 4 ohms at 1 KHZ
3KW dissipation from in-built force cooled
dissipators

S 250D

Single Channel
19" rack mount 3½" high
500w r.m.s. into 2.5 ohms
Retro-convertible to dual channel
DC-20 KHZ at full power
Full short and open circuit protection
Drives totally reactive loads with no
adverse effects

A complete range of matching transformers and peripheral equipment for closed loop, constant current and voltage use are available.

Alternative input and output termination to order. Rack case for bench use built to specifications. For complete data write or call.




Kirkham Electronics



MILL HALL, MILL LANE, PULHAM MARKET, DISS, NORFOLK IP21 4XL
DIVISION OF K.R.S. LIMITED
TELEPHONE (037 976) 639/594

FRANCHISED COMMERCIAL AND INDUSTRIAL AGENTS FOR **H||H** ELEC-

WW-031 FOR FURTHER DETAILS

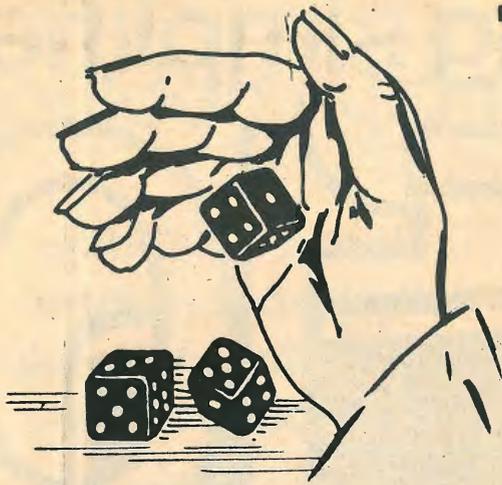

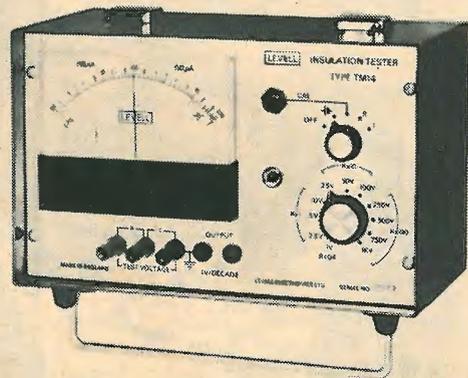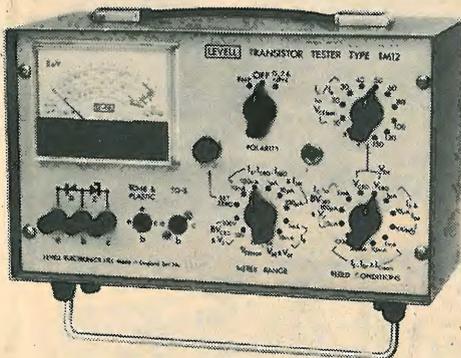DON'T GAMBLE WITH PERFORMANCE BUY LEVELL TESTERS



Tests bipolar transistors, diodes and zener diodes. Measures leakage down to 0.5 nA at 2V to 150V. Current gains are checked from 1µA to 100mA. Breakdown voltages up to 100V are measured at 10µA, 100µA and 1mA. Collector to emitter saturation voltage is measured at 1mA, 10mA, 30mA and 100mA for I_C/I_B ratios of 10, 20, 30. The instrument is powered by a 9V battery.

TRANSISTOR RANGES (PNP OR NPN)

I_{CBO} & I_{EBO} : 10nA, 100nA, 1µA, 10µA and 100µA f.s.d. acc. ±2% f.s.d. ±1% at voltages of 2V, 5V, 10V, 20V, 30V, 40V, 50V, 60V, 80V, 100V, 120V, and 150V acc. ±3% ±100mV up to 10µA with fall at 100µA < 5% +250mV.

BV_{CBO} : 10V or 100V f.s.d. acc. ±2% f.s.d. ±1% at currents of 10µA, 100µA and 1mA ±20%.

I_B : 10nA, 100nA, 1µA... 10mA f.s.d. acc. ±2% f.s.d. ±1% at fixed I_E of 1µA, 10µA, 100µA, 1mA, 10mA, 30mA, and 100mA acc. ±1%.

h_{FE} : 3 inverse scales of 2000 to 100, 400 to 30 and 100 to 10 convert I_B into h_{FE} readings.

V_{BE} : 1V f.s.d. acc. ±20mV measured at conditions on h_{FE} test.

$V_{CE(sat)}$: 1V f.s.d. acc. ±20mV at collector currents of 1mA, 10mA, 30mA and 100mA with I_C/I_B selected at 10, 20 or 30 acc. ±20%.

DIODE & ZENER DIODE RANGES

I_{DR} : As I_{EBO} transistor ranges.

V_Z : Breakdown ranges as BV_{CBO} for transistors.

V_{DF} : 1V f.s.d. acc. ±20mV at I_{DF} of 1µA, 10µA, 100µA, 1mA, 10mA, 30mA and 100mA.

type TM12 **£145**

A logarithmic scale covering 6 decades is used to display either insulation resistance or leakage current at a fixed stabilised test voltage. The current available is limited to a maximum value of 3mA for safety and capacitors are automatically discharged when the instrument is switched off or to the CAL condition. The instrument operates from a 9V internal battery.

RESISTANCE RANGES

10MΩ to 10TΩ (10^{13} Ω) at 250V, 500V, 750V and 1kV.

1MΩ to 1TΩ at 25V, 50V and 100V.

100kΩ to 100GΩ at 2.5V, 5V and 10V.

10kΩ to 10GΩ at 1V.

Accuracy ±15% +800Ω on 6 decade logarithmic scale.

Accuracy of test voltages ±3% ±50mV at scale centre.

Fall of test voltages < 2% at 10µA and < 20% at 100µA.

Short circuit current between 500µA and 3mA.

CURRENT RANGE

100pA to 100µA on 6 decade logarithmic scale.

Accuracy of current measurement ±15% of indicated value.

Input voltage drop is approximately 20mV at 100pA, 200µA at 100nA and 400mV at 100µA.

Maximum safe continuous overload is 50mA.

MEASUREMENT TIME

< 3s for resistance on all ranges relative to CAL position.

< 10s for resistance of 10GΩ across 1µF on 50V to 500V.

Discharge time to 1% is 0.1s per µF on CAL position.

RECORDER OUTPUT

1V per decade ±2% with zero output at scale centre.

Maximum output ±3V. Output resistance 1kΩ.

type TM14 **£155**

Optional extras are leather cases and mains power units. Prices are ex works, V.A.T. extra in U.K.

LEVELL ELECTRONICS LTD.

MOXON STREET, BARNET, HERTS., EN5 5SD.
TEL: 01-449 5028/440 8686

Telegraph testing simplified

TCT10



Lightweight, portable, Telegdata TCT10 makes light work of on-site circuits and machines.

This new Plessey instrument combines signal generator and analyser in a single briefcase-size unit enabling on-site testing of telegraph circuits and machines to be carried out speedily and with a high degree of accuracy.

Powered from the a.c. mains supply, the TCT10 gives a choice of output levels and test signals in CCITT No 2 and No 5 alphabets including the full 96 character 'fox' message, Q9S and any single character on demand.

Accurate readout (to 1%) is given unambiguously on an LED scale registering up to 40% distortion early/mark bias and late/space bias.

Full specification is available in a colour-illustrated brochure. See how your telegraph test operations can be improved — telex or write to: Telegdata Department, Plessey Controls Limited, Sopers Lane, Poole, Dorset, United Kingdom BH17 7ER. Telex: 41272.



PLESSEY
CONTROLS

moulded nylon **TRANSIPILLARS**[®]


probably the most versatile and rugged insulating mounting system ever developed

Transipillar insulating mounts hold heavy sub-assemblies totally secure. Because they're precision moulded from very tough Nylon.

Metric or Imperial versions are available, with insulator lengths from 1/2 in to 2 3/4 in, and a choice of metal screw or threaded insert end fittings from 0 to 6BA.

If one of the preferred sizes won't suit your application, the chances are we can make one that will.

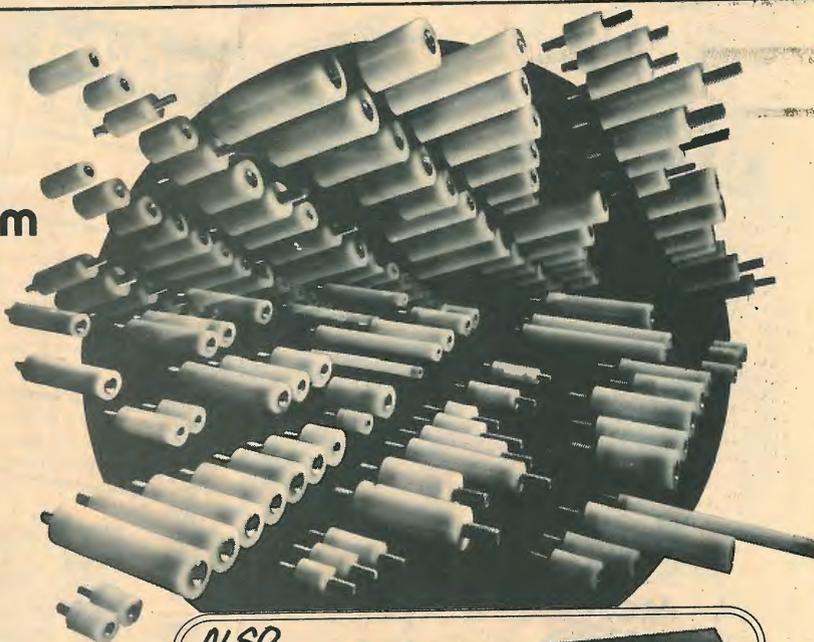Write today for samples, full technical details and prices of TRANSIPILLARS.



ALSO TRANSIBLOCK[®]

the patented insulating mount for 1/4 in thick heatsinks. Eliminates the need for power transistor mica washers.



WK ELECTRONICS LTD
 Napier Road Bromley Kent BR2 9JA
 Telephone: 01-460 9861/5 Telex: 896071


WW — 086 FOR FURTHER DETAILS

Britain's BIGGEST Computer Exhibition

COMPUTERS ...
 SMALL COMPUTERS ...
 SOFTWARE ... MINIS ... MICROS ...
 TERMINALS ... SOFTWARE
 PERIPHERALS ...
 SMALL BUSINESS SYSTEMS ...

OVER 350 EXHIBITORS AT
OLYMPIA, LONDON

COMPEC '79

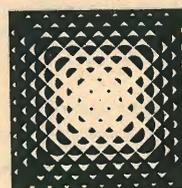

NOVEMBER 6, 7 & 8
 from 10 am each day

Admission is £2 if you register on arrival, but FREE pre-registration tickets are yours if this coupon reaches us by October 15.

COMPEC '79 tickets
 Room 821, Dorset House,
 Stamford Street, London, SE1 9LU
 England.

Please send me . . . FREE pre-registration tickets for Compec '79

USE BLOCK LETTERS. WRITE WITHIN SPACE

	Name
	Street & No.
	Town & Post or zip code
	Country

F

U.K. Two-way Radio Checklist				
	STORNO	MOTOROLA	GEC	PYE
Most EXPERIENCE				✓
Most DEPOTS				✓
Most SITES				✓
Most ENGINEERS				✓
Most SALES				✓

OK

But what does it all add up to?

Big is not always beautiful.

So when we boast more resources than all our competitors put together you might be inclined to think: so what?

We agree.

When *you* are making substantial investments in two-way radio we expect more than facts and figures to be taken into account.

Like the people you are dealing with, starting with the salesman and right up to the top. How good is your relationship with the man up front. Is he thinking long term or looking for a quick sale today?

And who is backing up his promises - a well resourced U.K. based manufacturing and supplying

company wholly dedicated to the future growth and development of two-way radio or a remote parent company looking for maximum advantage in whichever markets suit it best at the time? (If the latter, ensure he'll be around next time you have a replacement or extension problem).

We are not suggesting that you look to Pye Telecom for perfection. In this business staying the course for 35 years and making all the running for the future will always have its problems. But if ever those problems happen to be yours, you can count on our full commitment now and our resources whenever you need them.



Pye Telecommunications Ltd.,
St. Andrews Road, Cambridge, CB4 1DW.
Telephone: 0223 61222

WW-028 FOR FURTHER DETAILS

Cambridge Learning Enterprises

SELF-INSTRUCTION COURSES

UNDERSTANDING DIGITAL ELECTRONICS

In the years ahead the products of digital electronics technology will play an important part in your life. Calculators and digital watches are already commonplace. Tomorrow a digital display could show your vehicle speed and fuel consumption; you could be phoning people by entering their name into a telephone which would automatically look up their number and dial it for you.

These courses were written by experts in electronics and learning systems so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being faster and more thorough than classroom learning. You work at your own pace and must respond by answering questions on each new piece of information before proceeding.

After completing these courses you will have broadened your career prospects and increased your fundamental understanding of the rapidly changing technological world around you.



Digital Computer Logic and Electronics is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed, though the student should have an aptitude for logical thought. It consists of four volumes - each A4 size - and serves as an introduction to the subject of digital electronics. Everyone can learn from it - designer, executive, scientist, student, engineer.

Contents include: Binary, octal and decimal number systems; conversion between number systems, AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables; De Morgans Laws; design of logic circuits using NOR gates; R-S and J-K flip flops; binary counters, shift registers and half adders.

FLOW CHARTS & ALGORITHMS help you present: safety procedures, government legislation, office procedures, teaching materials and computer programs by means of YES and NO answers to questions.

The Algorithm Writer's Guide


explains how to: define the questions, put them in the best order and draw the flow chart, with numerous examples shown. All that students require is an aptitude for logical thought. Size: A5, 130 pages. This book is a **MUST** for those with things to say.

NEW from Cambridge Learning Enterprises

O - LEVEL ENGLISH LANGUAGE

More and more jobs require a C-GRADE PASS, and over 250,000 people fail to get this every year. Will one of them be in your family? This new course, written by experts in a style that's serious yet fun to read, shows you how to mark your own work and compare it with the work of other people in their exam year. Set your own pace and assess your results immediately with no postal delays: watch your speed and standards improve. In Book 1 learn how you will be marked on **COMPREHENSION**, Book 2 covers **SUMMARY**, **PUNCTUATION & SPELLING**, and Book 3 coaches you in the principles of **COMPOSITION**. Size: 3 A4 volumes totalling 250 pages.

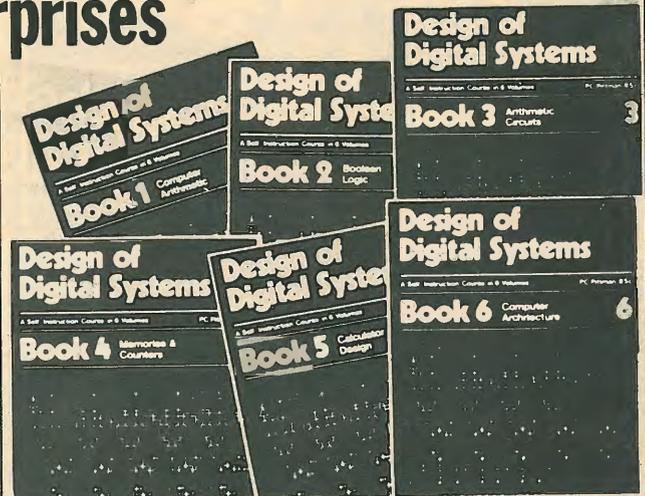CAMBRIDGE LEARNING ENTERPRISES, UNIT 32 RIVERMILL SITE, FREEPOST, ST. IVES, HUNTINGDON, CAMBS. PE17 4BR, ENGLAND
 TELEPHONE: ST. IVES (0480) 67446.
 PROPRIETORS: DAYRIDGE LTD. REG. OFFICE: RIVERMILL LODGE, ST. IVES REGD. IN ENGLAND No. 1328762



Design of Digital Systems is written for the engineer seeking to learn more about digital electronics. Its six volumes - each A4 size are packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters and simple arithmetic circuits, and finally to a complete understanding of the design and operation of calculators and computers. Contents include:

Book 1 Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.

Book 2 OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.

Book 3 Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.

Book 4 Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).

Book 5 Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control programme structure.

Book 6 Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.

Four volumes Digital Computer Logic & Electronics at £6.50 inc
 Six volumes Design of Digital Systems at £10.50 inc p & p
 Three volumes O-Level English Language at £6.50 inc p & p
 The Algorithm Writer's Guide at £3.40 inc p & p
 If your order exceeds £14 deduct £2 from your payment
 Price includes surface mail anywhere in the world, airmail extra
GUARANTEE If you are not entirely satisfied your money will be refunded
 Please allow 21 days for delivery

Cambridge Learning Enterprises, Unit 32, Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs. PE17 4BR, England.

Please send me the following books:
 sets Digital Computer Logic & Electronics at £6.50, p & p
 sets Design of Digital Systems at £10.50, p & p included
 O-Level English Language at £6.50 p & p included
 The Algorithm Writer's guide at £3.40, p & p included


Name
 Address

I enclose a *cheque/PO payable to Cambridge Learning Enterprises for £.....

Please charge my *Access/Barclaycard/Visa/Eurocard/Mastercharge/Interbank account number

Signature..... *delete as appropriate.
 Telephone orders from credit card holders accepted on 0480-67446 (Ansafone). Overseas customers should send a bank draft in sterling drawn on a London Bank, or quote credit card number.

Testing... Testing... Testing...

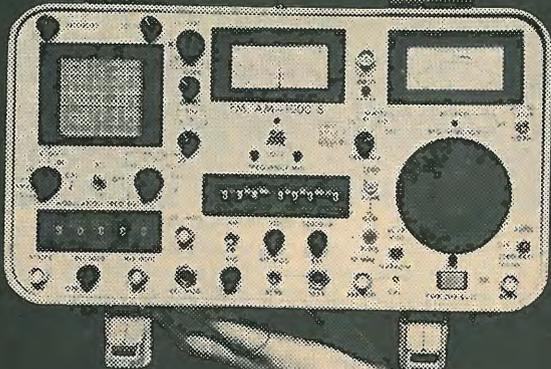

anywhere!

The FM/AM 1000s with Spectrum Analyser

A portable communications service monitor from IFR, light enough to carry anywhere and good enough for most two-way radio system tests. The FM/AM 1000s can do the work of a spectrum analyser, oscilloscope, tone generator, deviation meter, modulation meter, signal generator, wattmeter, voltmeter, frequency error meter - and up to five service engineers who could be doing something else!

For further information contact Mike Taylor



FieldTech

FieldTech Ltd
Heathrow Airport -
London Hounslow
TW6 3AF
Tel: 01-759 2811
Telex: 23734
FLDTEC G

IFR precision simulators

WW-036 FOR FURTHER DETAILS

THE JAMES SCOTT INDUSTRIAL microwave RANGE OF EQUIPMENT

The James Scott range of Microwave equipment offers industrial users a greater choice of alternative systems in robust, industrial, cast aluminium housings, for a wide variety of applications.

The range is made up of standard sub-assemblies which can be permuted to suit individual application requirements. Here are some suggested applications for these units.

- TRAIN CONTROL SYSTEMS
- SAFETY BARRIERS
- INTRUDER ALARMS
- ROAD VEHICLE SENSING SYSTEMS
- PROXIMITY ALARMS
- PROCESS CONTROL SYSTEMS
- INDUSTRIAL ALARM SYSTEMS
- SMALL OBJECT COUNTERS
- POSITIONING SYSTEMS
- VIBRATION SENSING SYSTEMS
- LEVEL CONTROLLERS
- DOOR OPENING SYSTEMS
- PRESENCE/DETECTORS


Please write or telephone for further information and technical literature to



JAMES
SCOTT
(Electronic Engineering) Ltd

CARNTYNE INDUSTRIAL ESTATE
GLASGOW G32 6AB Tel: 041 778 4206 Telex 778286

WW-025 FOR FURTHER DETAILS

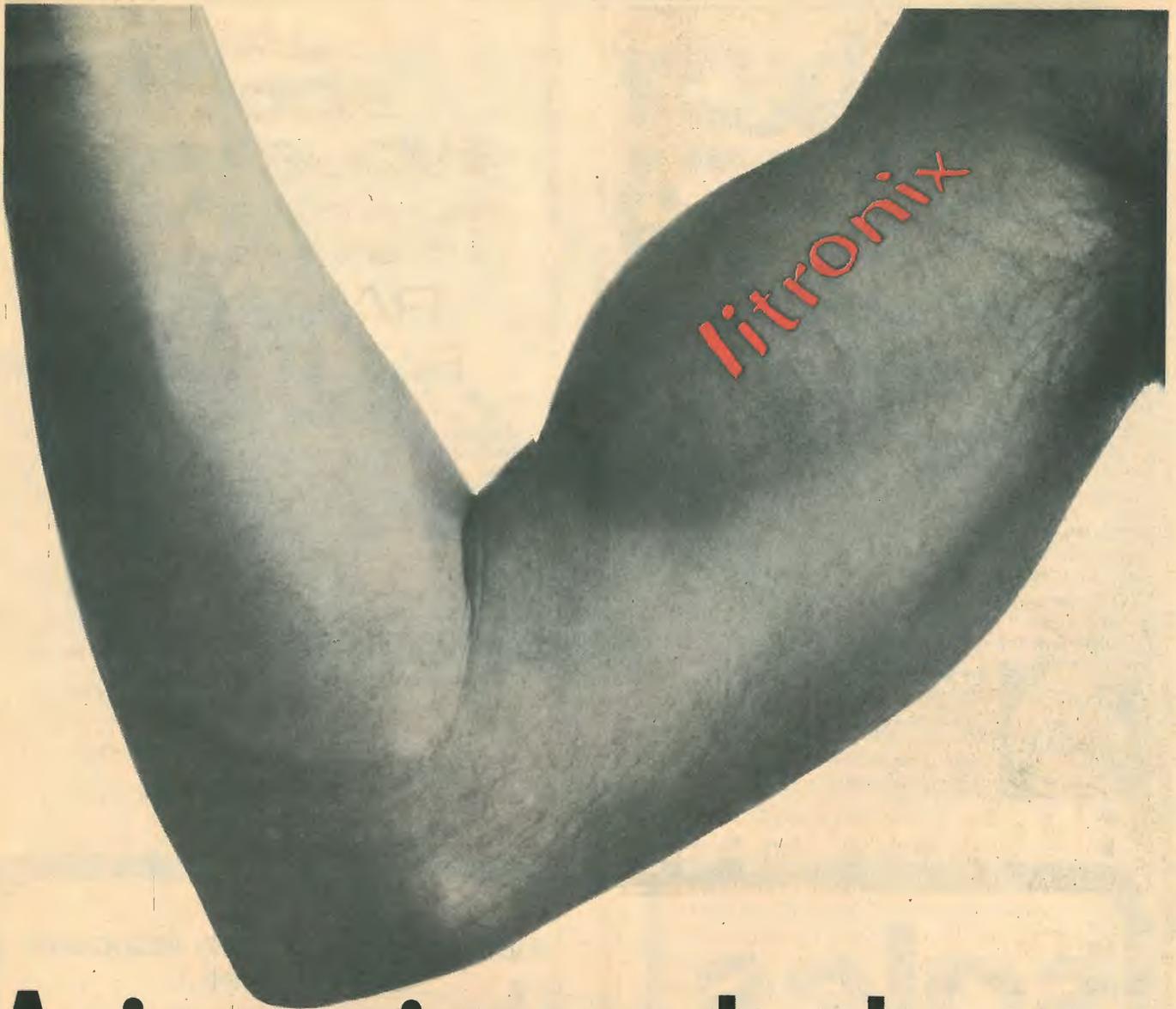

An impressive new development at Crellon.

Litronix is our most recent newcomer. This is very much in line with the Crellon policy of acting as distributor for only the finest principals.

The Litronix range is as impressive as its famous name and covers the following products:

LED's —
red, yellow, orange, green and infra-red Photo-transistors.


Opto isolators —
in a range that includes jedec types, high speed, duals and quads.

Displays —
including 7 segment and 16 segment alphanumeric.

Intelligent displays, too, alphanumeric with memory, decoder, driver and control circuitry, new smaller size package and much faster access time.

Add to all this the prompt, helpful and reliable Crellon service and you'll soon see why, when it comes to distribution, we've got plenty of muscle.

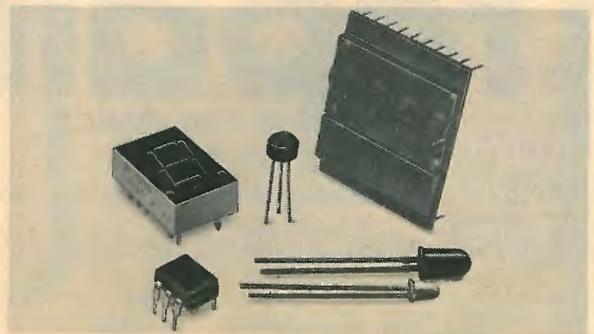There's a very informative data pack available — telephone or complete the reader reply card.



 **litronix**
Ideas with logic.


Crellon Electronics Ltd., 380 Bath Road, Slough, Bucks
Tel: Burnham (06286) 4434. Telex: 847571

The Polar capacity

Wingrove & Rogers have now expanded their operations to include four distinct divisions within the Company. Write or phone for further detailed information and samples.



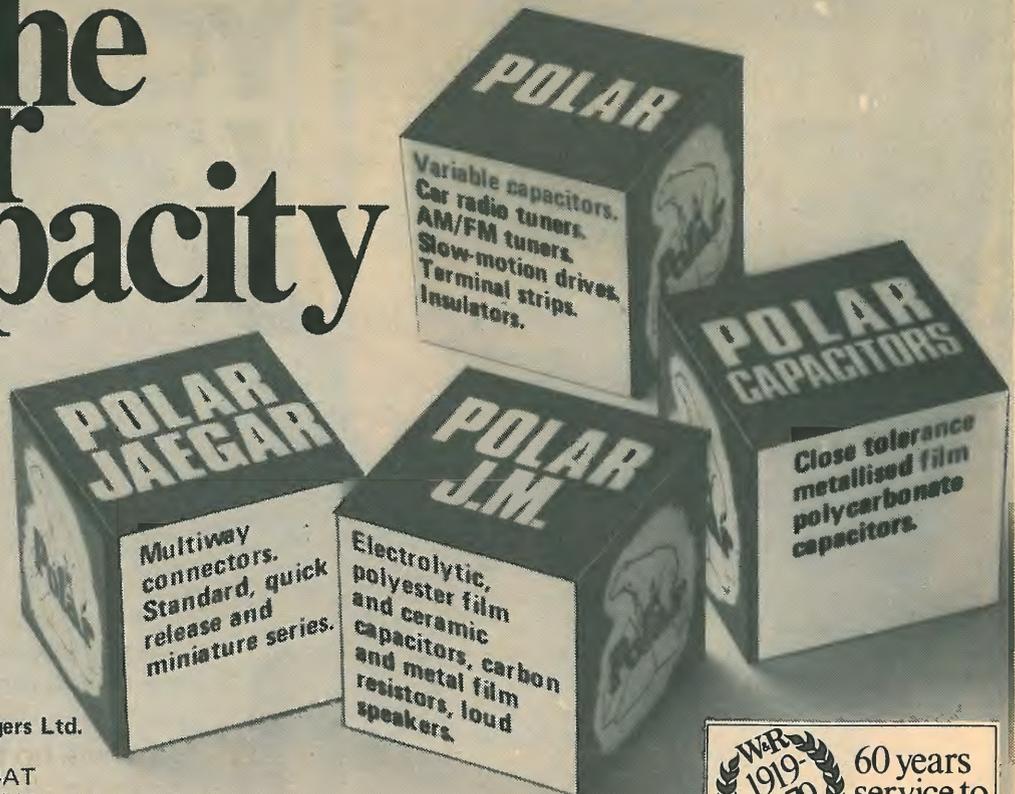Wingrove & Rogers Ltd.
Domville Road
Liverpool L13 4AT
Tel: 051-220 4641
Telex: Chacom Liverpool
627110 for Winrog



60 years
service to
industry

WW — 016 FOR FURTHER DETAILS

sales hire repair



**You'll do better at Martin Associates
we guarantee it!**

ANALYSERS

AIRMEC 248 5-300MHz £125.00
AIRMEC 853 30KHz-30MHz £85.00
MARCONI 2330 20Hz-78KHz £500.00
TEKTRONIX IL20 10MHz-4.2GHz Spectrum Analyser £1500.00

ATTENUATORS

ADVANCE A.64 0-70dB in 1dB step 600 ohms £30.00
MARCONI TF.1073A 0-100dB in 1dB steps 50 ohms £75.00

BRIDGES

B.P.L. CZ.457 Mk. II Component Comparator £70.00
GENERAL RADIO 1607 Transfer Function Immittance Bridge From: £450.00
WAYNE KERR B.221 0.1% Universal Bridge £200.00
WAYNE KERR 521 1.0% Universal Bridge £85.00

COUNTERS

MARCONI TF.1417 + 500MHz Divider 7 digit £225.00
RACAL 835 DC-15MHz 6 digit £130.00
SYSTRON DONNER 6035 20Hz-3GHz 7 digit £550.00

DIGITAL VOLTMETERS

DYNAMCO 2022S 0-2000V Scale 39999 10uV £250.00
ROBAND RDV.4. 0-1000V 4 digit £95.00

MARTIN ASSOCIATES



34 Crown Street
Reading
Berks. RG1 2SE
Tel. Reading (0734) 51074

METERS

JAC.331 Freq. Meter & Generator DC-3GHz £200.00
AVO Precision Meter £160.00
MARCONI TF.1245/46/47 Cct Magnification Meter + Oscillator £1000.00
MUIRHEAD D-729-BM Phase Meter £225.00
RADIOMETER BFK.6 Distortion Meter £250.00

OSCILLOSCOPES

TEKTRONIX 535A DC-15MHz c/w H Plug In Unit £250.00
TEKTRONIX 567 Sampling 1GHz Digital Readout £750.00
SCOPEX 4D-10B DC-10MHz 10mV Sens. NEW £188.00
SCOPEX 4D-25 DC-25MHz NEW £315.00
SCOPEX 4S-6 DC-6MHz NEW £138.00
HEWLETT-PACKARD 130C X-Y-T DC-500KHz 200uV Sens £275.00
TELFORD 'A' OSCILLOSCOPE CAMERA £250.00
VARIOUS PLUG INS & PROBES Information on Application

POWER SUPPLY UNITS

ADVANCE CV.500/A 240V r.m.s. 500 Watt £30.00
ROBAND T.172 0-30V 10A £140.00
ROBAND T.113 0-30V 20A £200.00

SIGNAL SOURCES

ADVANCE J1B 15Hz-50KHz 600ohms/50hms £60.00
GENERAL RADIO 1362 UHF Oscillator 220-920MHz £400.00
GENERAL RADIO 1209C UHF Oscillator 250-960MHz £100.00
GENERAL RADIO 1215C Oscillator Unit 50-250MHz £150.00
HEWLETT-PACKARD 608D 10-420MHz £350.00
HEWLETT-PACKARD 608F 10-455MHz 50ohms £500.00
MARCONI TF.995A/3/S 1.5MHz-220MHz FM/AM £500.00
MARCONI TF.1066B/6 10MHz-470MHz £600.00
MARCONI TF.1099 Sweep variable to 20MHz almost new £200.00
MARCONI TF.144H/4 10KHz-72MHz 50 ohms A.M. £470.00
MARCONI TF.1370 10Hz-10MHz £150.00
R & S SWF 5MHz-225MHz Sweep Generator £185.00
R & S SWH 50Hz-12MHz Sweep Generator £195.00

RECORDERS

LIGHT LAB 361D 0-100°C & -70° -0°C 9 Probes £65.00
SMITHS Miniscript 0-100uA £40.00

MISCELLANEOUS

GALLENKAMP FR.554 Muffle Furnace 1100°C £200.00
GRIFFIN Oven Amb. -100°C £60.00
ADMIRAL CORP 198A/B IFF/ATC Radar Test Set £800.00
WESTON ROTEK 146AG5 A.C. Voltage Standard £350.00
PERKIN ELMER F.11 Gas Chromatograph £1000.00

*Hundreds
more items
in stock!*

WW—029 FOR FURTHER DETAILS

IF IT'S TIME YOU HAD A NEW TIMER COUNTER, DC TO 35 MHz IS ENOUGH

Gould Advance have a *wide* range of timer counters.

And here are two which should meet most engineers' needs.

Both the TC320 and the TC321 have made extensive use of the latest low-power circuitry (CMOS, Schottky and thick film resistor networks, for example) and we have no hesitation in offering a (seldom-used) 2-year guarantee.

Check the functions— whilst remembering that both instruments are truly portable when internal rechargeable batteries are fitted as an option.

- * Frequency (Manual and Autoranging)
- * Single Period
- * Multiple Period
- * Multiple Period Average (Manual and Autoranging)
- * Time A-B
- * Automatic Pulse Width
- * Count
- * Totalise
- * Count A/B-B
- * Ratio.

Of the two instruments, the 321 has the more sophisticated 'spec'. But both are interesting.

Do ask for data. It'll be *enough* to impress you.



TC320



TC321



GOULD
An Electrical/Electronics Company

Gould Instruments Division,
Roebuck Road, Hainault, Essex IG6 3UE
Telex: 263785

TELEPHONE: 01-500 1000

WW — 073 FOR FURTHER DETAILS


GRADE: *Professional and Military*
 FREQUENCY RANGE: *100kHz to 31MHz*
 STABILITY: *High - with digital lock*
 COST: *Modest*
 MAKER: *Eddystone, of course!*
1837/1838 SERIES



- Covers most general-purpose applications in professional and military communication including marine use (speech, telegraphy or f.s.k. teleprinter signals)
 - Manual tuning plus accurate digital frequency lock
 - High reliability and environmental performance
 - Complies fully with MPT specifications 1201, 1216, 1217, 1204
- Please ask for details

Eddystone Radio Limited

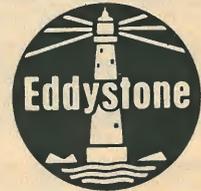Member of Marconi Communication Systems Limited
 Alvechurch Road, Birmingham B31 3PP, England
 Telephone: 021-475 2231 Telex: 337081
 A GEC-Marconi Electronics Company




WW — 017 FOR FURTHER DETAILS

TOTAL AMPLIFICATION FROM CRIMSON ELEKTRIK

WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS —

STEREO PRE-AMPLIFIER

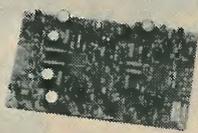

CPR 1 — THE ADVANCED PRE-AMPLIFIER. The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably the disc stage. The overload margin is a superb 40dB, this together with the high slewing rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV; distortion < .005% at 30dB overload 20kHz.

Following this stage is the flat gain/balance stage to bring tape, tuner, etc. up to power amp. signal levels. Signal to noise ratio 86dB; slew-rate 3V/μs; T.H.D. 20Hz—20kHz < 0.08% at any level.

F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 138x80x20mm. Supply to be ± 15 volts.

MC 1 — PRE-AMPLIFIER. Suitable for nearly all moving-coil cartridges. Sensitivity 70/170μV switchable on the p.c.b. This module brings signals from the now popular low output moving-coil cartridges up to 3.5mV (typical signal required by most pre-amp disc inputs). Can be powered from a 9V battery or from our REG 1 regulator board.

XO2:XO3 — ACTIVE CROSSOVERS. XO2 — two way, XO3 — three way. Slope 24dB/octave. Crossover points set to order within 10%.

REG 1 — POWER SUPPLY. The regulator module, REG 1 provides 15.0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

POWER AMPLIFIERS. It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc. who have been using CRIMSON amps satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types, they all have the same specification. T.H.D. typically 0.1% any power 1kHz 8 ohms. T.I.D. insignificant, slew rate limit 25V/μs; signal to noise ratio 110dB; frequency response 10Hz-35kHz. — 3dB; stability unconditional, protection drives any load safely; sensitivity 775mV (250mV or 100mV on request), size 120x80-25mm.

POWER SUPPLIES. We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120-240 primary and single bolt fixing (includes capacitors/bridge rectifier).


POWER AMPLIFIER MODULE



POWER AMPLIFIER KIT. The kit includes all metalwork, heatsinks and hardware to house any two of our power amp modules plus a power supply. It is contemporarily styled and its quality is consistent with that of our other products. Comprehensive instructions and full back-up services enable a novice to build it with confidence in a few hours.

PRE-AMP KIT

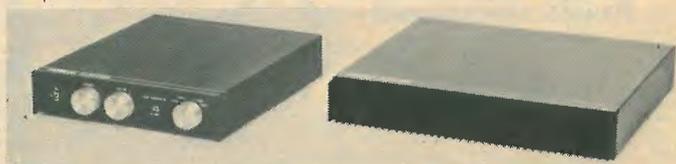This includes all metalwork, pots, knobs, etc., to make a complete pre-amp with the CPR1(S) module and the MC1(S) module if required.



POWER AMPLIFIER MODULES

CE 608 60W/8 ohms 35-0-35v	£19.52
CE 1004 100W/4 ohms 35-0-35v	£23.02
CE 1008 100W/8 ohms 45-0-45v	£25.96
CE 1704 170W/4 ohms 45-0-45v	£31.00
CE 1708 170W/8 ohms 60-0-60v	£33.97

TOROIDAL POWER SUPPLIES

CPS1 for 2xCE 608 or 1xCE 1004	£16.56
CPS2 for 2xCE 1004 or 2/4xCE 608	£18.80
CPS3 for 2xCE 1008 or 1xCE 1704	£19.75
CPS4 for 1xCE 1008	£17.12
CPS5 1 for 1xCE 1708	£24.15
CPS6 for 2xCE 1704 or 2xCE 1708	£25.53

HEATSINKS

Light duty, 50mm, 2 C/W	£1.44
Medium power, 100mm, 1-4 C/W	£2.35
Disc/group, 150mm, 1-1 C/W	£3.04
Fan, 80mm, state 120 or 240v	£19.70
Fan mounted on two drilled 100mm heatsinks 2x4 C/W, 65 max. with two 170W modules	£31.05

THERMAL CUT-OFF, 70°C £1.54

POWER AMP KIT £35.03

PRE-AMPS

These are available in two versions — one uses standard components, and the other (the S), uses MO resistors where necessary and tantalum capacitors.

CPR 1	£31.65
MC 1	£21.28
CPR 1S	£40.87
MC 1S	£33.17

ACTIVE CROSSOVERS

XO2	£15.16
XO3	£23.58

POWER SUPPLY

REG1	£6.90	TR6	£1.97
------	-------	-----	-------

PRE-AMP KIT

£38.07

BRIDGE DRIVER, BD1


Obtain up to 340W using 2x170W amps and this module. £5.75

CRIMSON ELEKTRIK

1A STAMFORD STREET, LEICESTER LE1 6NL. Tel. (0533) 553508
 U.K. — Please allow up to 21 days for delivery

All prices shown are UK only and include VAT and post. COD 90p extra 1100 limit. Export is no problem: please write for specific quote. Send large SAE or 3 International Reply Coupons for detailed information.
 Distributors: Minic Teleprodukt, Box 12035 S-750 12 Uppsala 12, Sweden. Badger Sound Services Ltd 46 Wood Street, Lytham St. Annes Lancashire, FY8 1QG

Series III S precision pick-up arm

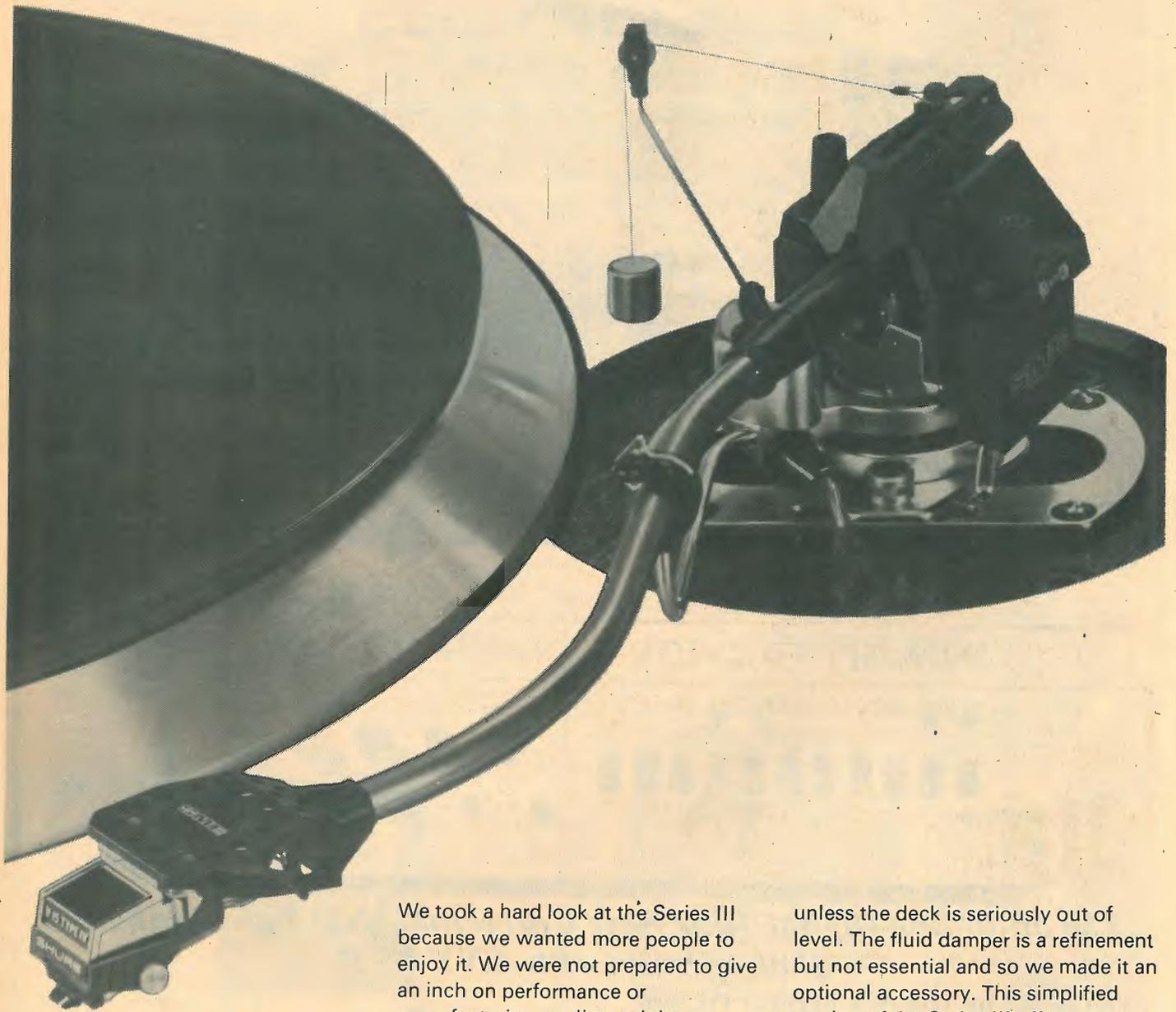

We took a hard look at the Series III because we wanted more people to enjoy it. We were not prepared to give an inch on performance or manufacturing quality and the nitrogen hardened titanium tone arm had to remain. However we found a number of ways in which economies could be effected and they have been incorporated in this new model.

Adjustments are made directly instead of through lead screws or rack and pinion, the absence of these things being a matter of operating convenience only. Lateral balance was also dispensed with as it is unimportant in this type of arm

unless the deck is seriously out of level. The fluid damper is a refinement but not essential and so we made it an optional accessory. This simplified version of the Series III offers an attractive saving in price and either is immediately available through your usual dealer. We shall be glad to send you details on request.

**Another accolade for SME: the Series III precision pick-up arm was one of the Design and Engineering Awards at the 1979 U.S Summer Consumer Electronics Show, the only pick-up arm to be acknowledged in this way.*

SME


The best pick-up arm in the world

Write to Dept 0656,
SME Limited, Steyning, Sussex,
BN4 3GY, England

This advertisement introduced the IVC 2001 Europe's most popular TBC



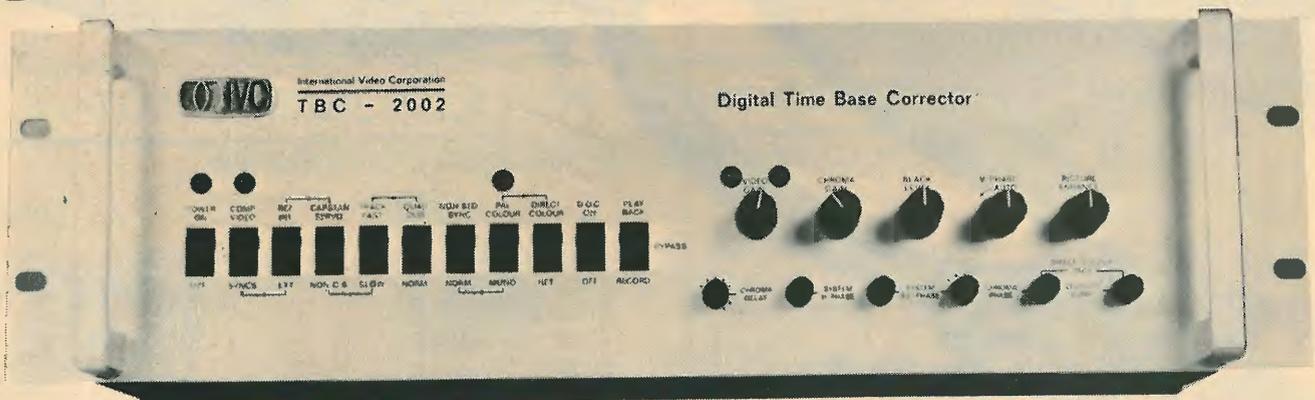So what extra has the second generation IVC 2002 got to offer?



The all-in-one Digital Time Base Corrector AND Video Enhancer that operates with ANY VTR.

FEATURES OF THE ALL BRITISH IVC 2002


- Fully "Floating Window" with Dynamic Steering
- Random Access Memory Store
- Built-in Picture Enhancer
- Built-in Processing Amplifier
- Built-in Noise Reducer
- Chrominance/Luminance Delay Correction
- Capstan or Non-Capstan Servo Operation
- Output Fully Locked and Phased to Studio Sync
- Single Wire Locking or 3 Wire Drive
- Self-contained SPG
- Full Colour Drop Out Compensator
- Full Front Panel Controls
- Colour Averaging Noise Reduction
- New High Performance ADC Unit
- Small Size, Cool and Silent
- Fully Automatic Edit Framing with No Line Hop
- Selectable Sync & Blanking Re-insertion
- Selectable Process Modes
- Direct or Heterodyned Colour Inputs
- 4 or 16 Line Store Option
- Quad-Dub Option for Remote Link or Non-Capstan Servo VTR

Please telephone or write for full details of our TBC's.



International Video Corporation
 10 Portman Road, Reading, Berkshire, RG3 1J
 Phone: (0734) 585421 Telex: 847579

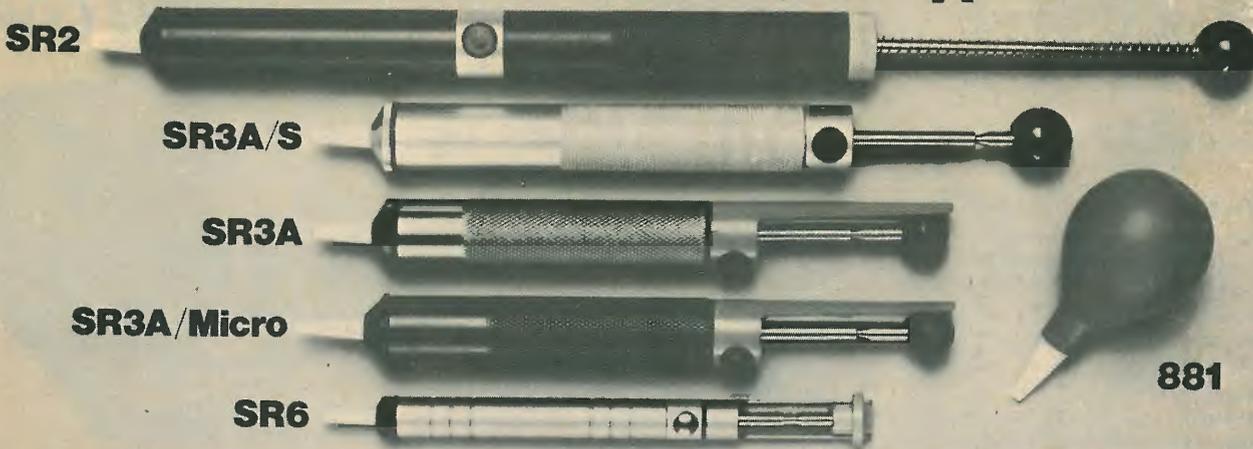Greenwood Electronics offer you six different de-solder tools for all applications



ORYX SR-2
High power de-solder tool with anti-recoil safety spring.

ORYX SR3A/S
Mini-silver de-solder tool. A more powerful version of the SR3A.

ORYX SR3A
Mini-orange. Our most popular model, the industry's standard tool.

The NEW ORYX SR3A/Micro
Identical to the SR3A but has a finer nozzle – only 1.5mm internal diameter.

The Micro-Mini SR6
Only 1/8" diameter. Weighs only 1 oz – the smallest, really effective de-solder tool available.


ORYX 881
Bulb Solder Sucker. Handy, lightweight and easy to use.

Greenwood Electronics

Portman Road, Reading, Berks. RG3 1NE Tel: (0734) 595844 Telex: 848659

WW — 009 FOR FURTHER DETAILS

ELECTRONIC INDUSTRIAL THERMOMETER

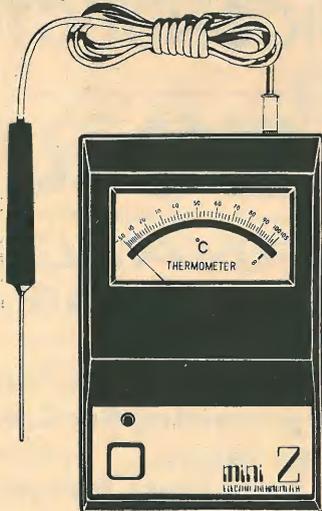

THE MODERN WAY TO MEASURE TEMPERATURE


A Thermometer designed to operate as an Electronic Test Meter. Will measure temperature of Air, Metals, Liquids, Machinery, etc., etc. Just plug-in the Probe, and read the temperature on the large open scale meter. Supplied with carrying case, Probe and internal 1 1/2 volt standard size battery.

Model "Mini-Z 1" measures from -40° C to + 70° C. Price £30.00
 Model "Mini-Z 2" measures from -5° C to + 105° C. Price £30.00
 Model "Mini-Z Hi" measures from + 100° C to 500° C. Price £33.00
 (VAT 15% EXTRA)

Write for further details to

HARRIS ELECTRONICS (LONDON)
138 GRAY'S INN ROAD, LONDON, WC1X 8AX
(Phone 01-837 7937)

WW—034 FOR FURTHER DETAILS

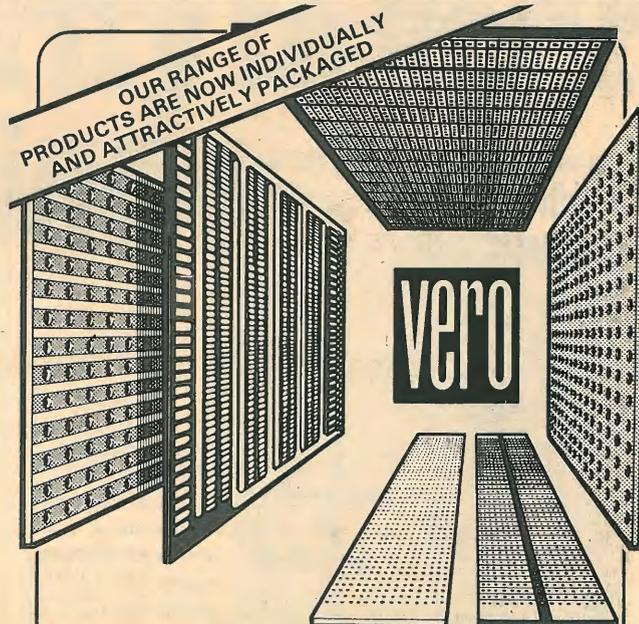

Our new catalogue lists circuit boards for all your projects, from good old Veroboard through to specialised boards for ICs. And we've got accessories, module systems, cases and boxes – everything you need to give your equipment the quality you demand. Send 25p to cover post and packing, and the catalogue's yours.

VERO ELECTRONICS LTD. RETAIL DEPT.
Industrial Estate, Chandlers Ford, Hants. SO5 3ZR
Telephone Chandlers Ford (04215) 2956

WW — 008 FOR FURTHER DETAILS

The DMM you've wanted: Quality and performance at a low, low cost

A surprisingly low £ 49.95. Surprising because you get the type of performance you've wanted but expected to pay much more for.

Quality, Performance and Accuracy

The 2010A offers you long-term accuracy with a laser-trimmed resistor network, a stable bandgap reference element, and single-chip LSI circuitry. With 31 ranges and 6 functions, you can measure AC or DC volts from 100 μ V to 1000 V; AC and DC current from 0.1 μ A all the way to 10 A; resistance from 0.1 Ω to 20 M Ω . Typical DCV and Ohms accuracy is 0.1% \pm 1 digit. Easy-to-read 3 1/2 digit LED's with 9 mm numerals and automatic decimal point.

Extra features for greater convenience and flexibility

- Unique X10 multiplier switch gives you convenient selection of the next higher decade. Hi-Low Power Ohms capability gives you three high-ohm ranges that supply enough voltage to turn on a semiconductor junction. You use the three low-ohm ranges for in-circuit resistance measurements.
- Wide Frequency Response: 40 Hz to 40 kHz bandwidth lets you measure audio through ultrasonic AC signals.
- Touch-and-Hold Capability (with optional probe) lets you hold readings as long as you



wish so you can make measurements in hard-to-reach places without taking your eyes off the probe tip.

• And More: automatic polarity and zeroing; overrange indication; overload protection on all ranges.

This compact unit is powered by 4 «C» cells (not included) so that you can take your lab-quality benchtop unit anywhere with you.

Kit or Factory-Assembled

Either is a tremendous value. Complete kit only £ 49.95; assemble it yourself with our easy-to-follow instructions. Or, for only £ 64.95. Sabtronics will ship your 2010A factory-assembled and calibrated.

Whether you're a professional or a hobbyist (or both!): When quality, accuracy, and price count, you should check out the 2010A DMM for yourself.

2010A Kit: £ 49.95

2010A Assembled: £ 64.95

(plus p.p. £ 3.50 and VAT at 8%)

THP-20 Touch and Hold Probe: £ 9.95.

Making Performance Affordable

sabtronics INTERNATIONAL INC.

Send your orders with your payment to:
TIMWOOD INDUSTRIES LTD,
Prospect Road, Cowes, Isle of Wight,
England, Telex 86892

WW — 022 FOR FURTHER DETAILS

FYLDE

TRANSDUCER and RECORDER
AMPLIFIERS and SYSTEMS



reliable high performance & practical controls. individually powered modules—mains or dc option single cases and up to 17 modules in standard 19" crates small size—low weight—realistic prices.

FYLDE

49/51 Fylde Road Preston
PR1 2XQ
Telephone 0772 57560

Fylde
Electronic
Laboratories
Limited.

WW — 047 FOR FURTHER DETAILS

FOR POWER SEMICONDUCTORS

IOR

INTERNATIONAL RECTIFIER


Diodes Thyristors
Fuses for protecting Semiconductors
Power Transistors Potted Bridges
Solid State Relays
Silicon Stacks Surge Suppressors

IN A HURRY!

070-681 4931

HARMSWORTH, TOWNLEY & CO. LTD.
HAREHILL TODMORDEN LANCS OL14 5JY

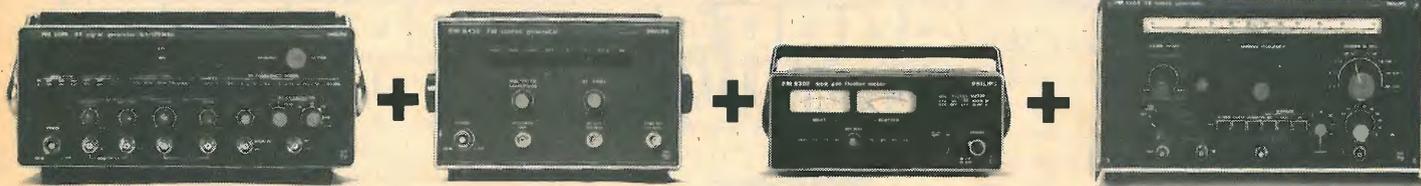Phone: 070 681 4931
Telex 635 091 Albion G
Attn: HARMSWORTH



Add superiority to your service

Philips superiority is the kind that comes with years of research and experience in virtually every aspect of electronic technology.

A range of instruments is available to give comprehensive back-up to your audio and video service. Five examples are shown here:

■ The new PM 5519 TV colour pattern generator - the professionals' choice with no fewer than 20 different colour and black and white test pattern combinations.

■ The PM 5326 RF signal generator,

service

ideal for fast and accurate receiver sensitivity and selectivity measurements.

■ The PM 6456 stereo generator transforms what used to be the complex procedure of checking and aligning FM tuners and receivers into a logical sequence of operations, using professional signals.

■ The PM 6307 wow and flutter meter

makes possible very accurate checks and alignments on audio and video tape recorders, record players and movie projectors.

■ The PM 5334 TV sweep generator, designed for the quick alignment and servicing of colour and black and white TV. Also suitable for checking wide-band amplifiers.

Full information about these and all the rest of Philips audio and video service products is contained in a new 16-page brochure, available now. Send for your copy today.

Pye Unicam Ltd
 Philips Electronic Instruments Dept
 York Street, Cambridge, England CB1 2PX
 Tel: Cambridge (0223) 58866 Telex: 817331



Test & Measuring Instruments

PHILIPS



MODEL 756 FULL ASCII KEYBOARD

LOW COST!
Fully Assembled

756 KEYBOARD

- * Intended for professional micro-processor applications.
 - * This one Keyboard will meet most present and future requirements.
 - * Full 128-character ASCII 8-bit code Tri-mode MOS encoding.
 - * Applications notes for auto repeat, numeric pad, serial output.
 - * Upper and lower case characters generated by keyboard with latching shift-lock.
 - * Selectable polarity.
 - * Size 305 X 140 X 32mm (12 1/4 X 5 1/2 X 1 1/4 in)
 - * MOS/DTL/TTL compatible outputs.
 - * New guaranteed OEM grade components.
 - * Needs +5 and -12V supply
- * Board has space for small low cost DC/DC converter so that entire unit operates off single 5V rail.

NUMERIC KEYPAD


£49.50 + VAT 15%

Also available:
 Numeric keypad — interfaces with 756 £7.50
 DC to DC converter to give — 12V £5.00
 (Mounts direct on 756 P.C.)
 Plastic enclosure type 701 £10.75
 Gold plated edge connector type 756/con £1.95

Generous Quantity Discounts Available
 U.K. orders add 8% VAT on order total.
 All U.K. enquiries to
CITADEL PRODUCTS LTD.
 50 High St., Edgware, Middx. HA8 7EP
 Tel.: 01-951 1848

- * Alpha lock.
 - * Extra loose keys available.
 - * Supplied complete with full technical data.
 - * Rugged mil. spec. G-10 PCB with plated through holes.
 - * 2-key roll-over
 - * DC level and pulse strobe signal for easy interface to any 8-bit input port microprocessor system, video display or terminal board.
 - * Strobe pulse width 1 ms.
- User selection of positive or negative logic data and strobe output.

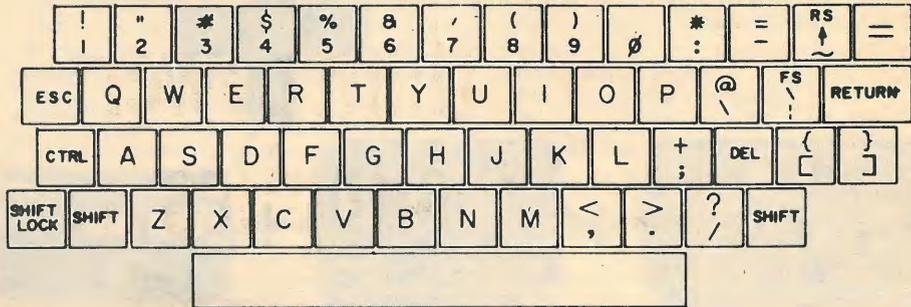Carter Associates
 P.O. Box 11262 VLAEBERG
 South Africa postal code 8018



WW — 054 FOR FURTHER DETAILS

LOWE ELECTRONICS LTD.

119 CAVENDISH ROAD, MATLOCK, DERBYSHIRE
 TEL. 0629 2430 OR 2817. TELEX 377482 LOWLEC G



**CS1577
130mm DUAL TRACE
TRIGGERED SWEEP
OSCILLOSCOPE**

£480 + VAT

PRICE INCLUDES TWO X10
 FULL BANDWIDTH PROBES

- * 130 mm mesh PDA
- * DC - 30 MHz
- * 2 mV sensitivity
- * Signal delay
- * Auto level triggering
- * Display modes CH1, CH2, DUAL, ADD, X-Y
- * Single shot with variable hold off

SPECIFICATION

Bandwidth: DC - 30 MHz (3 dB) 40 MHz (6 dB)

Sensitivity: 2 mV/cm - 10V/cm

Input R.C.: 1 M ohm 22 pF

Risetime: 11.7 nS

Overshoot: less than 3%

Sweep time: 100 nS/cm - 0.5S/cm better than 3%

Linearity: 1 KHz 100 mV square wave

Calibrator:

Trigger bandwidth: DC - 40 MHz

Trace rotation: Electrical


Phosphor: P31

Power: AC 100 / 120 / / 220/240V 50/60 Hz 40W

Dimensions: 260mm x 190mm x 375mm

Weight: 10 Kg

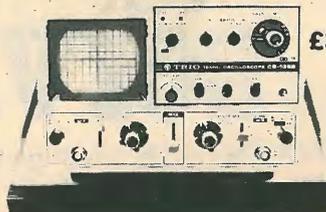**CS1352 DUAL TRACE 15
MHz/2mV PORTABLE**



£350 + VAT

The CS1352 oscilloscope offers you not only dual trace, 15MHz bandwidth operation at sensitivities down to 2mV/cm but also use from 100-240 Vac mains and portable operation using the optional rechargeable battery pack. Automatic charging is carried out when the CS1352 is plugged into a mains supply. Now you can have top performance both on the bench and out in the field — and at an affordable price.



CS1575 DUAL TRACE 4 FUNCTION

The CS1575 is a unique tool for the audio engineer. It features the normal facility of dual trace display with sensitivity to 1 mV/cm but not only can it display the input signals on two channels, it can **simultaneously** display the phase angle between them and measure the phase angle referenced to a zero phase calibration display. In addition to these unique features, you also have independent triggering from each channel to give stable displays even with widely differing input frequencies.

Absolutely indispensable to the professional audio engineer, the CS1575 is now in use all over the world. See it in action or send for complete details.




£278 + VAT

**TRIO
OSCILLOSCOPES**

The Trio range of oscilloscopes offer top quality at moderate cost. The brief specifications show the performance features which have made these oscilloscopes firm favourites in all parts of the world, with bandwidths to 30 MHz and sensitivities down to 1mV/cm on 130 mm screens. Prices are very realistic and we try to ensure that delivery is ex-stock at all times — quite a change these days.


FOR FULL DETAILS ON THESE AND OTHER MODELS, CONTACT THE SOLE AGENTS, LOWE ELECTRONICS

WW — 055 FOR FURTHER DETAILS

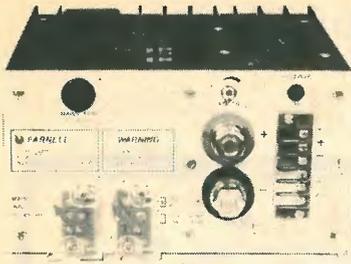

POWER SUPPLIES

- A.C. in/d.c. stabilised out. Sub-units
- D.C. in/d.c. stabilised out
- Series/linear regulator. Low cost O.E.M.
- Op. amp. powering. Encapsulated
- Miniature non-encapsulated
- High efficiency/small size switching
- Constant voltage. Constant current
- Outputs from 0 to 50V, 0 to 60A standards
- Sub-bench (variable unmetred)
- Low cost utility bench units
- High stability bench units
- Constant voltage/current with or without automatic crossover. H.T.
- Rack mounting
- S.C.R. chopped
- Fan cooled
- Outputs up to 100A from standard
- Battery standby systems (to order)
- Specials and custom design work

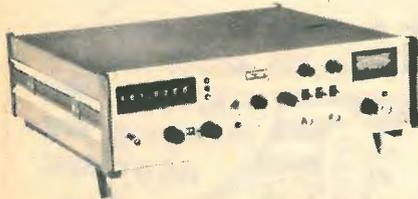

SIGNAL SOURCES

- Sine-square oscillators
- Function generators
- Pulse generators
- Digital signal generators
- R.F. signal generators
- Synthesized signal generators
- Sweep generators

ANALOGUE MEASURING INSTRUMENTS

- A.C./d.c. millivoltmeters
- R.F. millivoltmeter
- Phasemeter
- Automatic modulation meter

DIGITAL MEASURING INSTRUMENTS

- Digital multimeters. Digital thermometers
- Digital tachometers. Digital panel meters
- Digital frequency meters. Digital timers
- Modular high speed digital event counters




**There's more
to Farnell
than power
supplies...**




RECORDING INSTRUMENTS

- Potentiometric pen recorders
- Roll paper type
- Single or two pen models
- Input modules to suit measurement parameter — microvolts, millivolts, volts, a.c. or d.c., current, frequency, temperature
- X-Y recorders. Printers. A3 and A4 sizes
- With or without timebase
- Consumables for above — paper, pens, etc.
- Instrumentation tape recorders
- Data recorders (cartridge tape)
- Digital reel to reel

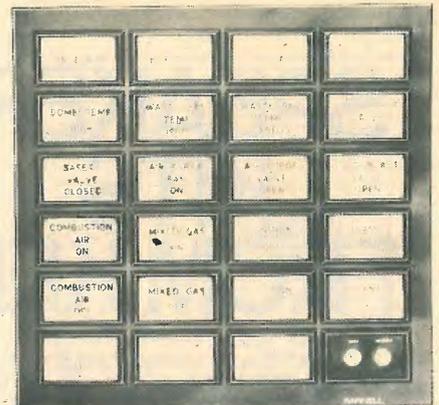

INDUSTRIAL CONTROL

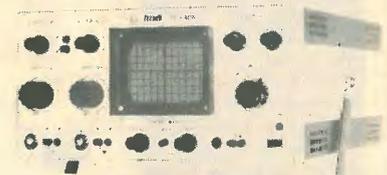- Alarm annunciator modules and systems
- Trip amplifiers. Control panels and systems
- Panel meters



OSCILLOSCOPES

- 12MHz bandwidth
- 30MHz bandwidth
- Dual trace
- Long persistence tube versions
- Rack mounting versions
- Probes
- Carrying cases/protector muffs

AGENCIES

through Farnell International Instruments Ltd.

AVO

- Avometer instruments and accessories
- Avo component testers and accessories

MEGGER

- 'Megger' testers. Insulation testers
- Earth testers, etc.

SULLIVAN

- Precision instruments
- Measurement standards

TANDBERG

- Computer peripherals. Formatters. Systems
- Digital tape transport. Video display terminals
- 4 Channel F.M. instrumentation tape recorder
- Cartridge data recorder

DATA PRECISION

- 3 1/2, 4 1/2, 5 1/2 digital multimeters
- Low cost models. Portables. Bench models
- Systems compatible models
- Counter/timers. Frequency meters




FARNELL INSTRUMENTS LIMITED

SANDBECK WAY · WETHERBY · WEST YORKSHIRE LS22 4DH

TEL. 0937-63541 or 01-864 7433 · TELEX 557294 FARIST G

SPEAKER KITS FROM KEF.

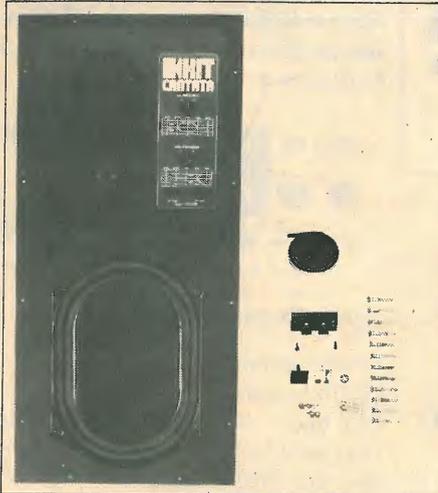Now you can build a three-way loudspeaker system which incorporates all the features developed for the superb KEF Cantata, and hear its quality at your KEF dealer before you buy and build the kit.



KEF KIT CANTATA

The kit contains two baffles (only one illustrated) each with the three drive units preassembled, pretested and fully wired through an Acoustic Butterworth filter network. The middle and high frequency units have acoustic balance controls and are fuse protected.

The Cantata was developed by KEF using their concept of "Total System Design" whereby drive units, filters and enclosure are matched together to produce an acoustic response as near to the ideal as possible.



To get the same results, build the recommended enclosures, connect a few wires, install the baffles and switch on.


Write now for more details, and the name of your nearest KEF dealer.

KEF Electronics Ltd.,
Tovil, Maidstone, Kent ME15 6QP.
Telephone: 0622-672261. Telex: 96140.



WW — 018 FOR FURTHER DETAILS

METER PROBLEMS?

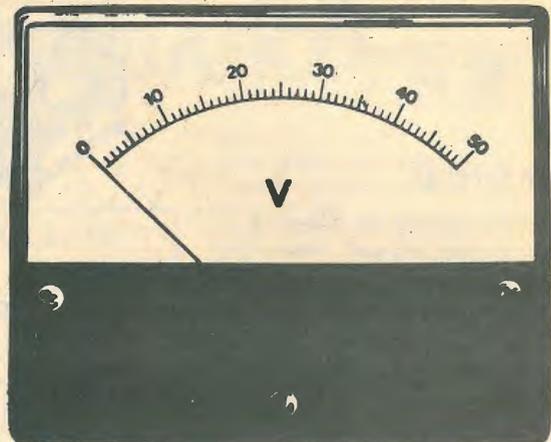


137 Standard Ranges in a variety of sizes and stylings available for 10-14 days delivery. Other Ranges and special scales can be made to order.

Full Information from:

HARRIS ELECTRONICS (London)

138 GRAYS INN ROAD, W.C.1 Phone: 01/837/7937

WW — 053 FOR FURTHER DETAILS

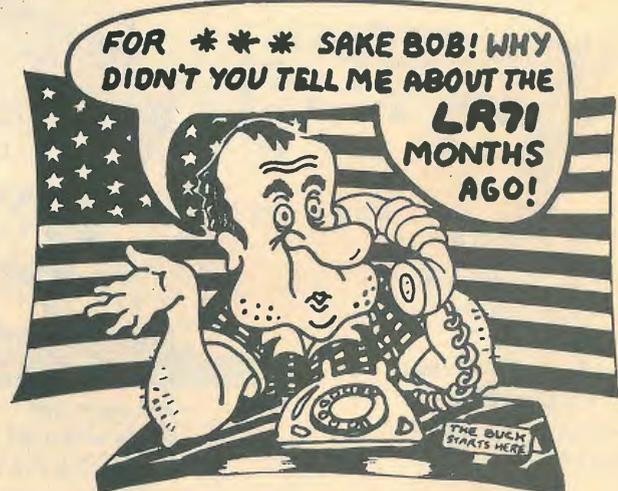

for all demagnetising problems

LEEVERS - RICH
have the answer

LR70 for tapes
up to 8¼ Dia and 1" wide


LR71 for tapes
up to 11½ Dia and 1" wide

LR72 Han-d-mag for
demagnetising heads and
tape path components



LEEVERS - RICH EQUIPMENT LTD 319 Trinity Road, Wandsworth, London SW18 3SL Tel: 01-874 9054 Telex: 92355

WW — 046 FOR FURTHER DETAILS

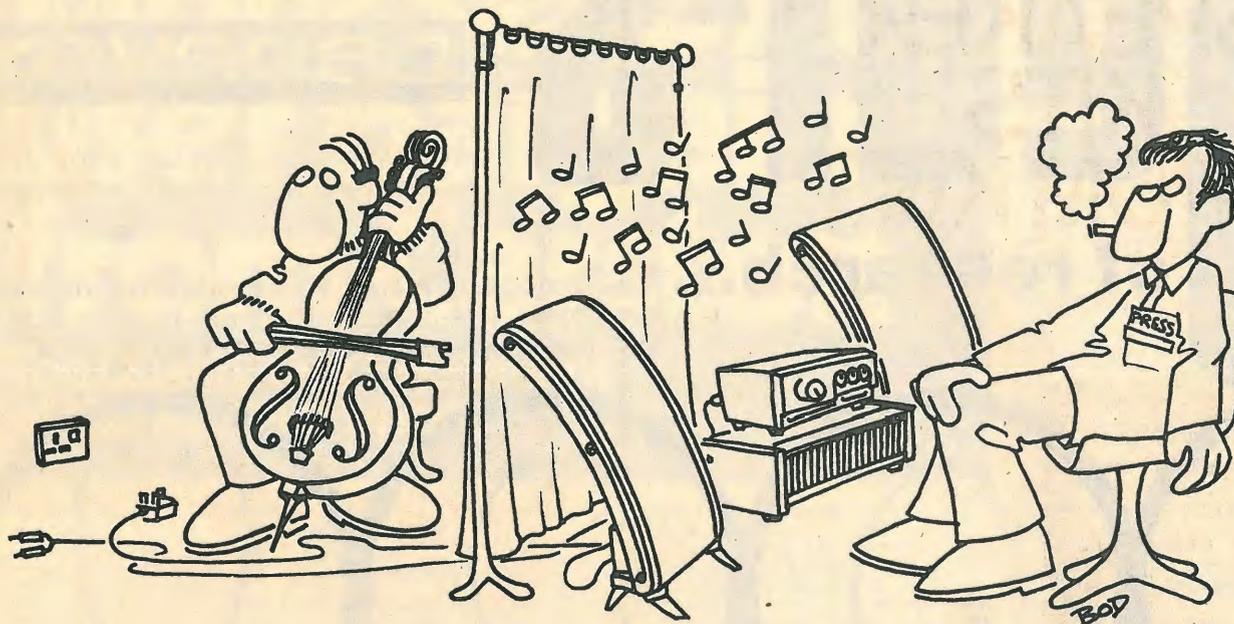

Artistic licence?

We at QUAD go to a very great deal of trouble to ensure that with a QUAD 33 in the Cancel position, the voltage delivered to your loudspeakers is a virtually exact RIAA transfer of the voltage the pickup will produce into a stated passive load. Nothing added – nothing taken away.

A visiting journalist recently suggested that we should not do this. Final adjustment should be done by ear, he said.

What an opportunity!

After all we know that if we add a little warmth with a subtle boost in the lower middle and balance this with an ever so gentle hump in the quack region (2-3kHz), we can make most programmes sound superficially more impressive. Come to that, why not change the 3180 μ S to 5000 μ S adding a little more 'heft' that most people will fall for. We could even make a special model for the boom and tizz brigade.

Been to any live concerts recently ?

For further details on the full range of QUAD products write to:
The Acoustical Manufacturing Co. Ltd.,
Huntingdon, Cambs. PE18 7DB
Telephone : (0480) 52561

QUAD



for the closest approach to the original sound


QUAD is a Registered Trade Mark

40 years of research...




DANAVOX (GT. BRITAIN) LTD.
"BROADLANDS" BAGSHOT ROAD,
SUNNINGHILL, ASCOT, BERKS.
TEL: 0990 23732/6; TELEX: 84584

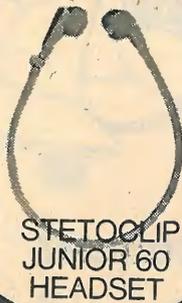"on components and accessories for dictating machines, tele-communications, hearing aids and electroacoustic equipment etc."



STETOCLIP JUNIOR 60 HEADSET

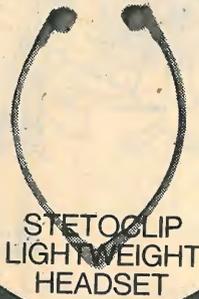


STETOCLIP LIGHTWEIGHT HEADSET




SENIOR STETOCLIP HEADSET



STETOMIKE BOOM MICROPHONE HEADSET

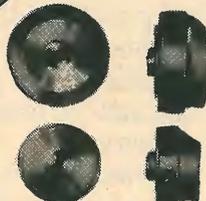


STANDARD & SUB-MINOR EARPHONES

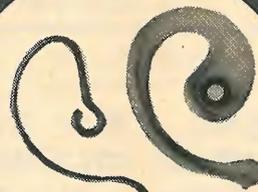


PLASTIC EARHANGERS



DANAMIC FIDELITY EARSET

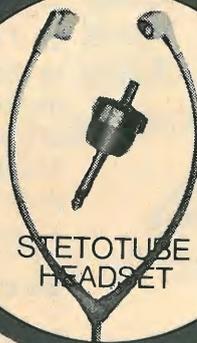

STETOTUBE HEADSET

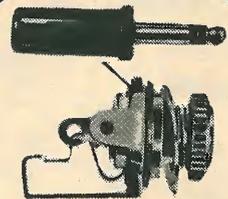


2,5 mm and 3,5 mm JACK PLUGS & SOCKETS



DANASOUND HEADSET



DANASONIC INDUCTION AUDIO LOOP RECEIVER

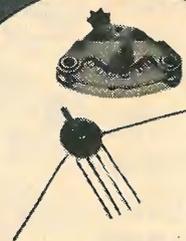

SUBMINIATURE SWITCHES

Prices from £

More second user bargains from Carston

Top Quality Test Equipment at the keenest prices

Acoustic	Prices from £	Oscilloscopes	Prices from £	Pulse Generators	Prices from £
BRUEL & KJAER		ADVANCE		E. H. RESEARCH	
2203 Precision sound level meter	400	OS1000A DC-20 MHz dual trace	310	G710 5 V/50 Ω 30 Hz-50 MHz RT 5 ns	100
2204 Precision sound level meter	475	COSSOR		132AL 50 V/50 Ω 5 Hz-3 MHz RT 12 ns	175
1613 Octave filter set couples directly to 2203 & 2204	250	110/111 DC-20 MHz dual trace	325	LYONS INSTRUMENTS	
4216 Artificial Mouth	25	110/112 DC-1 MHz differential	275	PG2E 10 V/50 Ω 1 Hz-16 MHz RT 10 ns	130
*2624 Charge Amplifier	65	HEWLETT PACKARD		PG23 10 V/50 Ω 1 Hz-10 MHz RT 5 ns	135
CEL		184A + 1801A + 1822A DC-50 MHz system, T.B. and amplifier included, storage facility (storage de-rated please ask for details)	650	SYSTRON DONNER	
112 LEQ meter-digital readout	450	1707B20 DC-75 MHz dual trace D.T.B.	700	101 10 V/50 Ω 10 Hz-10 MHz RT 5 ns	95
Bridges etc.		1710B DC-200 MHz dual trace	1250	Recorders & Signal Conditioning Equipment	
DAWE		TEKTRONIX		BRUNO WOELKE	
210B Decade Capacitance box		5103N/D15		ME102B Wow and flutter meter	75
0.1 μF-1 mF 0.1 μf step	20	Storage system 800 div/ms DC-2 MHz	350	ME102C Wow and flutter meter	90
MUIRHEAD		7A13 DC-100 MHz differential comparator	350	Recorders & Signal Conditioning Equipment	
D30A Wheatstone bridge test set	75	7B70 Dual time base with 7B71 delayed sweep (for 7000 series)	275	BRUEL & KJAER	
SULLIVAN		536 Mainframe 11 MHz X-Y	100	2305B Stylus Recorder includes 50 db pot	650
T1098 Decade resistance bridge	-90	519 1 GHz Real Time. Matching accessories included	860	HEWLETT PACKARD	
WAYNE KERR		535A/CA DC-15 MHz dual trace DTB	250	17502A Plug-in for 7100 series recorder temperature module	25
B601Z RF bridge to 5 MHz	275	545B/CA DC-24 MHz dual trace DTB	350	SE LABS	
SR268 Source for B601Z		585A/81 DC-80 MHz dual trace DTB	550	3006DLT 12 channels UV 6 inch chart	450
Cable Test Equipment		454 DC-150 MHz dual trace DTB	1350	A1000 Galvo 600 Hz 0.34 mA/cm	30
MARCONI		TELEQUIPMENT		MICROMOVEMENTS	
TF2091A/TF2092A White noise generator/receiver 300 channel system complete	350	D54 DC-10 MHz dual trace	240	M400 Galvo 300 Hz 50 μA/cm	25
*TF2333 Transmission Test Set	575	D75 DC-50 MHz dual trace D.T.B. (Portable)	550	M1000 Galvo 600 Hz 0.34 mA/cm	25
STC		D83 DC-50 MHz dual trace D.T.B. (Bench)	575	M1600 Galvo 1000 Hz 0.4 mA/cm	25
74226B Telephone cable test set	120	D53/CD/G DC-15 MHz Dual Trace with differential amplifier	225	M8000 Galvo 5 kHz 15.5 mA/cm	25
*74216A Noise Generator CCITT	240	Oscilloscope Probes - Current		SIEMENS	
*74261A Psophometer CCITT	475	TEKTRONIX		KOMP III 2 pen potentiometric roll chart	425
Circuit Magnification		P6021 AC current probe to 20 MHz	200	Signal Sources & Generators	
MARCONI		Oscilloscope Probes - Voltage		ADVANCE	
TF1245/46/47 'Q' Meter with Oscillators	525	HEWLETT PACKARD		H1 15 Hz-50 KHz	40
Counter Timers		1121 A 500 MHz	90	DAWE	
HEWLETT PACKARD		TEKTRONIX		410C 0.1 Hz-10 KHz	40
5263A Time interval plug-in	60	P6046 Differential probe DC-100 MHz	215	EH RESEARCH	
MARCONI		Oscilloscope Cameras		967 Attenuator 25W 0-40 db	30
TF2414A DC-40 MHz 7 digits	170	HEWLETT PACKARD		HEWLETT PACKARD	
TF2422 Frequency divider to 300 MHz	30	195A Pack film polaroid	190	200CD 5 Hz-600 kHz O/P 10 V RMS	75
RACAL		198A Pack film polaroid	120	8693/100 3.7-8.3 GHz 5 mW. sweeper plug-in	525
9024 10 Hz-600 MHz 7 + 1 digits	325	TEKTRONIX		* 608E 10-480 MHz AM	410
9059 DC-560 MHz with battery pack	300	P6046 Differential probe DC-100 MHz	215	* 618C 3-8-7.6 GHz FM	1600
9835 DC-15 MHz 6 digits	145	Oscilloscope Probes - Voltage		* 620B 7-11 GHz FM	1600
9837 DC-80 MHz 6 digits	190	HEWLETT PACKARD		MARCONI	
Function Generators		195A Pack film polaroid	190	TF791 FM Deviation Meter 4-1024 MHz	95
HEWLETT PACKARD		198A Pack film polaroid	120	TF801D1 10-470 MHz AM, PM	150
3300A 0.01 Hz-100 kHz sine, square triangular	100	TEKTRONIX		TF885 0-12 MHz Sine/Square	75
3301 Auxiliary plug-in		C30AR Roll film polaroid	130	TF995A/2 1.5-220 MHz AM, FM	350
Logic Analysers		Power Meters		TF995B/5 0.2-220 MHz AM, FM	475
HEWLETT PACKARD		HEWLETT PACKARD		TF1060 0-1.2 GHz AM, PM	150
1601L Logic state analyser 12 channel display	600	432A/478A 10 MHz-10 GHz wideband with bolometer	350	TF2005A Two tone 20 Hz-20 KHz	200
Mains Monitors		Power Supplies		ROHDE & SCHWARZ	
AMPROBE		HEWLETT PACKARD		SWOB I 0.5-400 MHz 75 Ω	225
LAV3X Mains voltage recorder	45	6265B DC stab. variable 40 V/3 A	195	SWOB II 0.5-1200 MHz 50 Ω with delay line and accessories	1250
GEC		ROBAND			
FB31A Surge monitor records mains spikes + filter	85	T101 50 V 1 A Variable	30		
RUSTRAK		SOLARTRON			
288 + CT Clamp-on AC recording ammeter	95	As 751 50 V 1 A Variable	25		
Modulation Meters		STARTRONIC			
AIRMEC		117 20 V 0.5 A Variable	25		
*210 1-300 MHz AM/FM	195	SYSTRON DONNER			
*409 3-1500 MHz AM/FM	325	LNG 16-10 16 V/10 A variable	75		
MARCONI		Pressure & Displacement Transducers			
*TF2300A 1-1000 MHz AM/FM	520	ELECTRO MECHANISMS			
		LVDT DC linear variable ±0.50 inches	25		

TEXSCAN
VS40 1-300 MHz sweeper 450

WAYNE KERR
S121 10 Hz-120 KHz 25
022B 10 Hz-10 MHz 75

Spectrum Analysers
HEWLETT PACKARD
141T Display unit storage 845
8552A I.F. Plug-in 1600
8553L 1 kHz-110 kHz Plug-in 1650
8554L 500 kHz-1250 MHz Plug-in 2100

T.V. Test Equipment
MARCONI
TF2909 Gray scale generator 250

Temperature & Humidity
COMARK
1604BLU Analogue thermometer 0-100 °C 40

LEE-DICKENS
HP5 Humidity probe 130
HUMIGUN Temp/humidity probe with meter 215

RAYTEK
T1000 Infra-red thermoprobe 200

Vibration
DAWE
1461 CV(M) Portable Vibration Analyser Kit 450

Voltmeters - Analogue
AIRMEC
264 Millivoltmeter 3 mV-1 V ranges 45

AVO
*8 Mk V AC/DC/OHMS 60

BOONTON
93A 20 Hz-20 MHz True RMS 260

BRADLEY
CT471C AC/DC/Ω/current multimeter and RF 165

DAWE
614C Millivoltmeter 0.3 mV-300 V ranges 25

HEWLETT PACKARD
427A AC/DC/Ω multimeter 275
3406A 10 kHz-1.2 GHz 395

KEITHLEY
610B Electrometer recorder O/P 330

LINSTEAD
M2B DC/AC 10 Hz-500 kHz 25

MARCONI
TF2603 AC voltmeter to 1.5 GHz 300

NORMA
U-Function Dual channel peak/RMS meter 325

PHILIPS
PM2454B AC voltmeter to 12 MHz 225

Voltmeters - Digital
ADVANCE
DMM3 1999 FSD AC/DC/Ω/current 85

DANA
5230 119999 FSD AC/DC 175

FLUKE
8300A 119999 FSD DC only 150

HEWLETT PACKARD
3474/2 9999 FSD AC/DC/Ω 185

SOLARTRON
A200 19999 FSD DC only 160
A205 19999 FSD AC/DC/Ω 300

*7045 19999 Auto AC/DC/OHMS 295
*7050 99999 Auto AC/DC/OHMS 395

Wave Analysers
GENERAL RADIO
1232A Tuned amplifier and null detector 20 Hz-20 KHz 75

HEWLETT PACKARD
302A 20 Hz-50 kHz 75 db range 375

WAYNE KERR
A321 20 Hz-20 KHz. Sens. -75 db 125

*Equipment added this month

Redundant Test Equipment
Why not turn your under-utilized test equipment into cash? Ring us and we'll make you an offer.

VAT charged at Standard Rate

Contact David Kennedy

01-267 5311/2

Carston Electronics Limited,
Shirley House, 27 Camden Road,
London NW1 9NR. Telex: 23920

note our new telephone number

WHY BUY A MICRO-COMPUTER FROM **PETALECT** ELECTRONIC SERVICING LTD.

BECAUSE

- 1) Established company trading since 1971
- 2) Electronic servicing is our speciality
- 3) We have in house programmers/ systems analysts
- 4) We have our own service engineers
- 5) We will demonstrate the PET at your premises
- 6) We can customise the PET to your requirements
- 7) We can arrange finance

- 8) We offer, after the three-month warranty, a service contract from £69.50
- 9) You benefit from our experience of having sold over 250 micro-computers to industrial, educational and business, personal users.
- 10) We specialise in programs and interfaces for weighing applications for average weight control and counting, etc.



8K £550.00 + VAT
16K £675.00 + VAT
32K £795.00 + VAT

New Large
Keyboard 'PETS'
Now in Stock

All 'PETS' sold with a Basic Tutorial Tape
In our showroom we sell
Books, Programs, etc.

Also available:

24K Memory Expansion Boards (disk-compatible), only £320 + VAT
PET-compatible dual floppy disk unit with advanced operating system, only £840 + VAT
Large Extension Keyboard for the PET £89.50 + VAT
Telephone for complete system prices : Wide Range of Printers Available

If you require any more information or demonstration regarding the PET 2001/8 or any associated equipment, programs, etc., please contact Mr. P. J. A. Watts or Mr. D. W. Randall at:

PETALECT ELECTRONIC SERVICES LTD
33/35 Portugal Road, Woking, Surrey
Tel. Woking 69032/68497

Shop at:
PETALECT
Chertsey Road, Woking, Surrey
Tel. Woking 20727/23637

WW — 061 FOR FURTHER DETAILS

<p>CMOS</p> <table style="width: 100%;"> <tr><td>4000</td><td>.15</td></tr> <tr><td>4001</td><td>.15</td></tr> <tr><td>4002</td><td>.15</td></tr> <tr><td>4007</td><td>.15</td></tr> <tr><td>4011</td><td>.15</td></tr> <tr><td>4012</td><td>.15</td></tr> <tr><td>4013</td><td>.26</td></tr> <tr><td>4015</td><td>.76</td></tr> <tr><td>4016</td><td>.28</td></tr> <tr><td>4017</td><td>.57</td></tr> <tr><td>4018</td><td>.65</td></tr> <tr><td>4020</td><td>.67</td></tr> <tr><td>4021</td><td>.67</td></tr> <tr><td>4022</td><td>.65</td></tr> <tr><td>4023</td><td>.15</td></tr> <tr><td>4024</td><td>.48</td></tr> <tr><td>4025</td><td>.15</td></tr> <tr><td>4027</td><td>.31</td></tr> <tr><td>4028</td><td>.54</td></tr> <tr><td>4029</td><td>.70</td></tr> <tr><td>4040</td><td>.65</td></tr> <tr><td>4042</td><td>.53</td></tr> <tr><td>4043</td><td>.57</td></tr> <tr><td>4044</td><td>.57</td></tr> <tr><td>4046</td><td>.82</td></tr> <tr><td>4047</td><td>.95</td></tr> <tr><td>4049</td><td>.28</td></tr> <tr><td>4050</td><td>.31</td></tr> <tr><td>4051</td><td>.51</td></tr> <tr><td>4052</td><td>.51</td></tr> <tr><td>4053</td><td>.51</td></tr> <tr><td>4060</td><td>.94</td></tr> </table>	4000	.15	4001	.15	4002	.15	4007	.15	4011	.15	4012	.15	4013	.26	4015	.76	4016	.28	4017	.57	4018	.65	4020	.67	4021	.67	4022	.65	4023	.15	4024	.48	4025	.15	4027	.31	4028	.54	4029	.70	4040	.65	4042	.53	4043	.57	4044	.57	4046	.82	4047	.95	4049	.28	4050	.31	4051	.51	4052	.51	4053	.51	4060	.94	<h2 style="margin: 0;">★★★ WE HAVE MEMORIES ★★★</h2> <table style="width: 100%; margin-top: 10px;"> <tr> <td style="width: 33%;">2104-2 4096 bit DRAM (200ns) 6.50</td> <td style="width: 33%;">75110 Interface .54</td> </tr> <tr> <td>4116-3 16kX1 DRAM (250ns) 9.00</td> <td>5325 Memory Driver .97</td> </tr> <tr> <td>4118 1k X 8 SRAM 19.50</td> <td>Z-80 CPU 4MHz 11.50</td> </tr> <tr> <td>74118AN 256 bit PROM 2.00</td> <td>Z-80 PIO 9.50</td> </tr> <tr> <td>2708 1k X 8 EPROM (450ns) 9.50</td> <td></td> </tr> </table> <h3 style="margin-top: 20px;">LET US GIVE YOU A TIP</h3> <table style="width: 100%; margin-top: 10px;"> <tr> <td style="width: 50%;">TIP 29A .31</td> <td style="width: 50%;">TIP 34C .76</td> </tr> <tr> <td>TIP 29C .36</td> <td>TIP 35A 1.25</td> </tr> <tr> <td>TIP 30A .32</td> <td>TIP 35C 1.50</td> </tr> <tr> <td>TIP 30C .36</td> <td>TIP 36A 1.36</td> </tr> <tr> <td>TIP 31A .33</td> <td>TIP 36C 1.63</td> </tr> <tr> <td>TIP 31C .36</td> <td>TIP 41A .47</td> </tr> <tr> <td>TIP 32 .33</td> <td>TIP 41C .53</td> </tr> <tr> <td>TIP 32C .36</td> <td>TIP 42A .49</td> </tr> <tr> <td>TIP 33A .57</td> <td>TIP 42C .53</td> </tr> <tr> <td>TIP 33C .68</td> <td>TIP 2955 .57</td> </tr> <tr> <td>TIP 34A .31</td> <td>TIP 3055 .57</td> </tr> </table> <p style="text-align: center; margin-top: 10px;">VAT Included P&P 30p</p> <p style="text-align: center;">Access Cards Welcome</p>	2104-2 4096 bit DRAM (200ns) 6.50	75110 Interface .54	4116-3 16kX1 DRAM (250ns) 9.00	5325 Memory Driver .97	4118 1k X 8 SRAM 19.50	Z-80 CPU 4MHz 11.50	74118AN 256 bit PROM 2.00	Z-80 PIO 9.50	2708 1k X 8 EPROM (450ns) 9.50		TIP 29A .31	TIP 34C .76	TIP 29C .36	TIP 35A 1.25	TIP 30A .32	TIP 35C 1.50	TIP 30C .36	TIP 36A 1.36	TIP 31A .33	TIP 36C 1.63	TIP 31C .36	TIP 41A .47	TIP 32 .33	TIP 41C .53	TIP 32C .36	TIP 42A .49	TIP 33A .57	TIP 42C .53	TIP 33C .68	TIP 2955 .57	TIP 34A .31	TIP 3055 .57	<table style="width: 100%;"> <tr><td>4066</td><td>.33</td></tr> <tr><td>4068</td><td>.15</td></tr> <tr><td>4069</td><td>.15</td></tr> <tr><td>4070</td><td>.15</td></tr> <tr><td>4071</td><td>.15</td></tr> <tr><td>4072</td><td>.15</td></tr> <tr><td>4073</td><td>.15</td></tr> <tr><td>4075</td><td>.15</td></tr> <tr><td>4076</td><td>.73</td></tr> <tr><td>4077</td><td>.15</td></tr> <tr><td>4078</td><td>.15</td></tr> <tr><td>4081</td><td>.15</td></tr> <tr><td>4082</td><td>.15</td></tr> <tr><td>4093</td><td>.39</td></tr> </table> <h3 style="margin-top: 20px;">DIL SOCKETS</h3> <table style="width: 100%;"> <tr><td>8 pin</td><td>.12</td></tr> <tr><td>14 pin</td><td>.13</td></tr> <tr><td>16 pin</td><td>.14</td></tr> <tr><td>18 pin</td><td>.20</td></tr> <tr><td>20 pin</td><td>.21</td></tr> <tr><td>22 pin</td><td>.23</td></tr> <tr><td>24 pin</td><td>.24</td></tr> <tr><td>28 pin</td><td>.31</td></tr> <tr><td>40 pin</td><td>.44</td></tr> </table> <div style="text-align: center; margin-top: 20px;"> We welcome Access </div>	4066	.33	4068	.15	4069	.15	4070	.15	4071	.15	4072	.15	4073	.15	4075	.15	4076	.73	4077	.15	4078	.15	4081	.15	4082	.15	4093	.39	8 pin	.12	14 pin	.13	16 pin	.14	18 pin	.20	20 pin	.21	22 pin	.23	24 pin	.24	28 pin	.31	40 pin	.44
4000	.15																																																																																																																																															
4001	.15																																																																																																																																															
4002	.15																																																																																																																																															
4007	.15																																																																																																																																															
4011	.15																																																																																																																																															
4012	.15																																																																																																																																															
4013	.26																																																																																																																																															
4015	.76																																																																																																																																															
4016	.28																																																																																																																																															
4017	.57																																																																																																																																															
4018	.65																																																																																																																																															
4020	.67																																																																																																																																															
4021	.67																																																																																																																																															
4022	.65																																																																																																																																															
4023	.15																																																																																																																																															
4024	.48																																																																																																																																															
4025	.15																																																																																																																																															
4027	.31																																																																																																																																															
4028	.54																																																																																																																																															
4029	.70																																																																																																																																															
4040	.65																																																																																																																																															
4042	.53																																																																																																																																															
4043	.57																																																																																																																																															
4044	.57																																																																																																																																															
4046	.82																																																																																																																																															
4047	.95																																																																																																																																															
4049	.28																																																																																																																																															
4050	.31																																																																																																																																															
4051	.51																																																																																																																																															
4052	.51																																																																																																																																															
4053	.51																																																																																																																																															
4060	.94																																																																																																																																															
2104-2 4096 bit DRAM (200ns) 6.50	75110 Interface .54																																																																																																																																															
4116-3 16kX1 DRAM (250ns) 9.00	5325 Memory Driver .97																																																																																																																																															
4118 1k X 8 SRAM 19.50	Z-80 CPU 4MHz 11.50																																																																																																																																															
74118AN 256 bit PROM 2.00	Z-80 PIO 9.50																																																																																																																																															
2708 1k X 8 EPROM (450ns) 9.50																																																																																																																																																
TIP 29A .31	TIP 34C .76																																																																																																																																															
TIP 29C .36	TIP 35A 1.25																																																																																																																																															
TIP 30A .32	TIP 35C 1.50																																																																																																																																															
TIP 30C .36	TIP 36A 1.36																																																																																																																																															
TIP 31A .33	TIP 36C 1.63																																																																																																																																															
TIP 31C .36	TIP 41A .47																																																																																																																																															
TIP 32 .33	TIP 41C .53																																																																																																																																															
TIP 32C .36	TIP 42A .49																																																																																																																																															
TIP 33A .57	TIP 42C .53																																																																																																																																															
TIP 33C .68	TIP 2955 .57																																																																																																																																															
TIP 34A .31	TIP 3055 .57																																																																																																																																															
4066	.33																																																																																																																																															
4068	.15																																																																																																																																															
4069	.15																																																																																																																																															
4070	.15																																																																																																																																															
4071	.15																																																																																																																																															
4072	.15																																																																																																																																															
4073	.15																																																																																																																																															
4075	.15																																																																																																																																															
4076	.73																																																																																																																																															
4077	.15																																																																																																																																															
4078	.15																																																																																																																																															
4081	.15																																																																																																																																															
4082	.15																																																																																																																																															
4093	.39																																																																																																																																															
8 pin	.12																																																																																																																																															
14 pin	.13																																																																																																																																															
16 pin	.14																																																																																																																																															
18 pin	.20																																																																																																																																															
20 pin	.21																																																																																																																																															
22 pin	.23																																																																																																																																															
24 pin	.24																																																																																																																																															
28 pin	.31																																																																																																																																															
40 pin	.44																																																																																																																																															
Resistors 1/4w 5% E12																																																																																																																																																
Same Value .80 per 100																																																																																																																																																

**STRUTT ELECTRICAL & MECHANICAL
ENGINEERING LTD.**
TELEX 45263

**3C BARLEY MARKET ST.
TAVISTOCK, DEVON PL19 05F
TEL. TAVISTOCK 0822 5439**

WW — 027 FOR FURTHER DETAILS



How...Why...When?

Distress calls are made every day—hundreds each year, and in every case questions are asked. Questions which require accurate, up-to-the-minute answers. Answers that can only come from reliable and immediately accessible communications recordings.

When police, ambulance, fire, local ATC and other services are called upon, either by radio or telephone, they often receive hasty, garbled messages—sometimes several at a time. In such instances a positive need for communications


recording arises—a need for a system with instant message trace and replay—at the touch of a button—and at any speed to assist intelligibility.

All these facilities, and more, are available in the Racal Recorders 'Callstore' cassette recorder/reproducer. Actuated either by incoming audio signals or by local or remote control, Callstore uses four cassette transports, each giving up to four separate channels, including a search control track which is cued at the beginning of each message.

For details write to:

Racal Recorders Limited
Hardley Industrial Estate
Hythe, Southampton,
Hampshire, SO4 6ZH
England.
Telephone: 0703 843265.
Telex: 47600.

RACAL

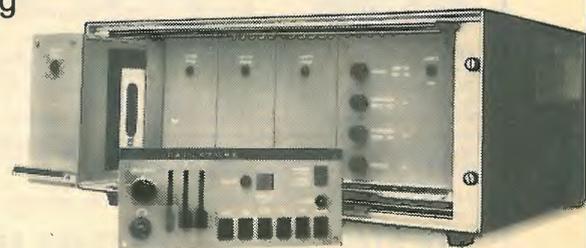

Callstore, from Racal Recorders, answers all the questions.

Quantum Electronics

THE LATEST AND BEST SOURCE OF SUPERFI AUDIO EQUIPMENT

Although we may be a new name to you, our products use refinements of circuitry which has been well proven over the past few years. By redesigning to what we consider the optimum cost/performance/appearance breakpoint we can now offer the best sound per pound that you will find anywhere. In addition to the items below we can supply ready built power amps, with active crossovers if required, in a variety of options including custom designed and finished metalwork in small (5+) or large quantities. If you do not see what you want please enquire.

'STATE OF THE ART' PRE-AMP



Undoubtedly the best pre-amp on the market, it is supplied ready built, **not a kit**, and caters for disc, aux and 2 or 3-head tape machine. The built-in supply regulators require only rough dc, available from all our power amps or the matching mains supply kit, CSI. The performance is almost perfect, with virtually zero thd (<.002%, 1kHz), zero common mode distortion, fast slewing, high overload (40dB) and low noise (70dB mag). It is attractively finished in black and is also available in a special version to cater for moving-coil cartridges.

CI (mag): £67.85 CSI (mains supply kit): £10.13
 CI mc (m-coil): £73.10 Module (trade and export only): £47.25, £51.60 (m-coil)

'DOMESTIC' POWER AMP KITS



P1. Mono 55W/8Ω £67.81
 P2. Stereo 2x45W/8Ω £79.35
 P3. Mono 130W/8Ω £83.32
 P4. Stereo 2x100W/8Ω £99.48
 Also available ready built EPOA

Styled and finished to match the CI, they are supplied with ready built and tested pcbs and require only simple assembly and point-to-point wiring of power transistors, supply, etc. In this way the possibility of errors and subsequent damage is drastically reduced. The performance, again, is second to none in this magazine, with ultra low thd (<.004%, 1k, 10W) and fast slewing contributing to their established exceptional subjective qualities.

'SLAVE TRAY' & RACK MOUNTING KITS



ASLAVE TRAY KITS:
 ST1. Mono 1x75W/4Ω, 55W/8Ω £49.45
 ST2. Stereo 2x60W/4Ω, 45W/8Ω £65.55
 ST3. Mono 1 x 130W/8Ω £83.84
 ST4. Stereo 2 x 110W/8Ω £93.61
 ST5. Mono 1 x 220W/4Ω 130W/8Ω £79.74
 ST6. Mono 1x250W/8Ω £96.25
 Plain lid: £4.23
 Black lid: £7.68
 Rack mounting kit. Slave tray + £15.41

These kits are designed to cope with sustained high level use, for which the domestic kits are not suitable. The same high performance circuitry is used with the power transistors mounted on substantial external heatsinks. The "slave tray" is the bare bones of a power amp and comprises a simple plain finished chassis, tested amp pcbs and transistors, heatsinks and power supply. No specific connectors are supplied to allow flexibility of application. A plain finish lid and black lid are available. The rack mounting kits use a heavy gauge black finish front and lid and are supplied without connectors, a range of which are stocked for your convenience. We can also supply ready-built amps with your choice of connectors. There is spare room inside the case to accommodate pre-amp circuitry if required. Low field toroidal transformers are used in all kits.

MODULES: UP TO 250W r.m.s.



These modules are available in a variety of powers and forms (including L bracket mounting) to trade and export customers only. They come ready built and tested and use the same proven circuitry as the other amps in our range and set an unsurpassed standard of performance and reliability. We also have power supplies for use with these. Please contact us for prices with competitive quantity discounts. The module illustrated is a medium duty 250W rms type using 4 of the latest Japanese "super" power transistors.

EXPORT: We can deal efficiently with orders to any country. Please write with your specific requirements for a quote by return. All power amps can be wired for 110v mains.
INFORMATION: Before ordering any of these or competitors' products, why not send for our detailed information? Large SAE or dollar bill please.

All prices shown are inclusive and all power ratings are real RMS watts, unlike the phoney ratings of many modules. Although we try to deal with orders promptly, please allow 28 days to avoid disappointment. Large orders please phone for delivery date.

DISTRIBUTORS: We are eager to establish distributors throughout the world and invite enquiries from interested parties.

SERVICING: We offer an after-sales service, with fixed maximum charges, for all our kits.

1A STAMFORD ST., LEICESTER LE1 6NL
Tel. 546198

WW — 078 FOR FURTHER DETAILS

KONTAKT 60

EUROPE'S LEADING CONTACT CLEANING SPRAY



Kontakt products 60-61 and WL provide an unsurpassed cleaning capability for contacts and switchgear.

KONTAKT 60

Safely dissolves oxides and sulphides and disposes of resinated contact greases and dirt, but does not attack plastics or any standard production materials.

Is silicone free.

Contains a light lubricant to avoid possible corrosion of contact paths — and obviates further oxydisation and "creep" currents.

Quality Industrial Sprays from Kontakt Chemie

K70 Protective Plastic Spray K72 Insulating Spray K75 Cold Spray

K80 Siliconised Polish K90 Video Spray K100 Antistatic Spray

K101 Dehydrating Spray and Pos. 20 POSITIVE PHOTO RESIST VARNISH.

Distributed by:

SPECIAL PRODUCTS DISTRIBUTORS LTD.

81 Piccadilly, London W1V 0HL

Tel. 01-629 9556. Cables: Specipro, London W1

Descriptive leaflets of the above products are freely available on request.

WW — 072 FOR FURTHER DETAILS

PRODUCTION TESTING

DEVELOPMENT

SERVICING

POWER UNITS

Now available with
3 OUTPUTS



Type 250VRU/30/25

OUTPUT 1: 0-30v, 25A DC

OUTPUT 2: 0-70v, 10A AC

OUTPUT 3: 0-250v, 4A AC

ALL
 Continuously
 Variable

Valradio


VALRADIO LIMITED, BROWELLS LANE, FELTHAM
 MIDDLESEX TW13 7EN
 Telephone: 01-890 4242/4837

WW — 059 FOR FURTHER DETAILS

sonimag 17

XVII INTERNATIONAL IMAGE, SOUND AND ELECTRONICS SHOW

TO SEE AND HEAR

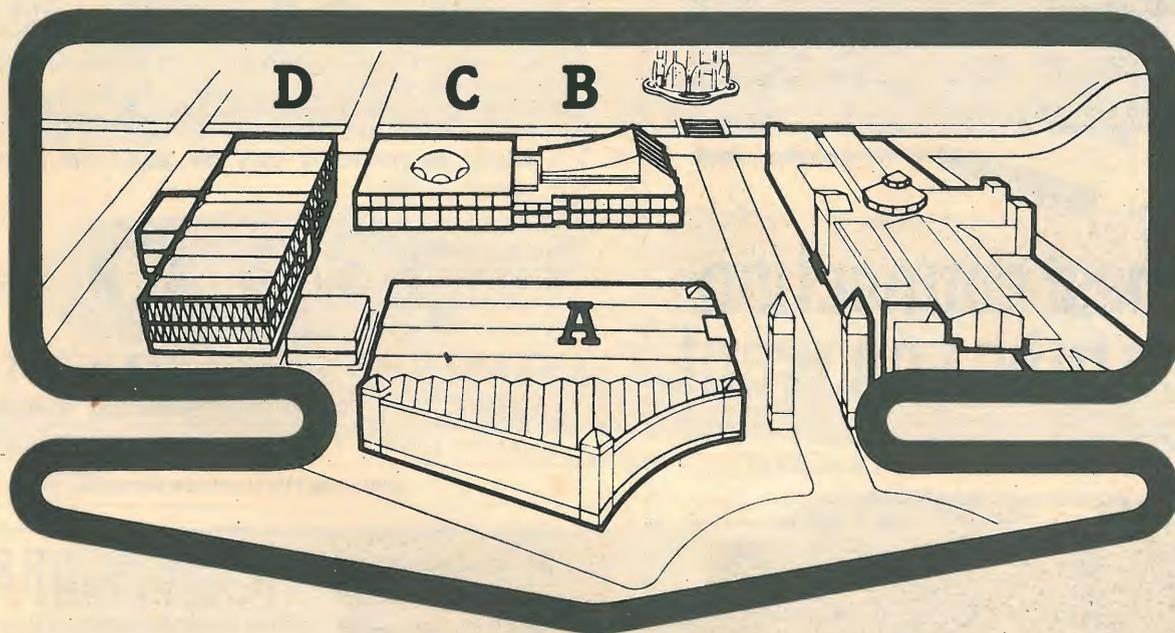

4 large exhibitions dealing with:

A



In the Palace No. 1 (A) there will be the manufacturers of radio and TV who will, moreover, give a sample of their most up-to-date know-how in the production of Hi-Fi systems, comprising amplifiers, modular sets, tuners and other accessories. The exhibition will be completed with the most modern Sound and Image recording and playback equipment.

C



The Fair Palace (C), specially set aside for Sound, is where the professional and the amateur will find everything relating to Hi-Fi, Public Address, Sound and Vision Recording and Playback, Musical Instruments and Show Illumination.

B



The Palace of Congresses (B) will house the largest Photography show in our country. Here the visitor will find from the simplest to the most sophisticated equipment, comprising complex professional developing and processing units. Moreover, supplementary to the Photographic Show, the whole wide, fascinating range of Audiovisual equipment.

D



Electronic components will be exhibited in the Fiftieth Anniversary Palace (D), together with production systems and materials for electronic design, measuring and control instruments, communications (both at the highest technical and professional level and for radio hams and Security Systems).

65,000 SQ. M. OF SHOW SPACE WITH 380 EXHIBITORS REPRESENTING 1200 FIRMS FROM 30 COUNTRIES.

FAIR GROUND (20-28 OCTOBER, 1979) BARCELONA-SPAIN.



The best connection for the tube you want.

Whatever industrial tubes you need, you can be sure you'll find them in this extensive collection of information-packed literature. There's everything from camera tubes to display tubes. Lasers to photomultipliers. Transmitting valves to receiving tubes. I.R. emitters to CCD Image Sensors.

Having this wealth of reference material on hand can save time, trouble and money. Apart from setting out data in the most clear and convenient way, you'll find that our booklets group products into types and outline major parameters.

These include selection, replacement, equivalents and characteristics tables that will help narrow your choice.

Just contact us for the best connection in tubes you'll ever make.

Crellon Electronics Ltd.,
380 Bath Road, Slough, Berks.
Tel: Burnham (06286) 4434. Telex: 847571.



RCA

WW — 075 FOR FURTHER DETAILS

IQXO-100 SERIES LOW PROFILE CRYSTAL CLOCK OSCILLATORS



- Hermetically sealed metal package
- DIL compatible
- 20.70L x 13.08W x 5.08H (mm)

The frequency range 600 Hz to 30 MHz is covered by both CMOS (600 Hz – 8 MHz) and TTL (150 KHz – 30 MHz) types having an overall tolerance of $\pm 0.01\%$ from 0 to $+70^\circ\text{C}$. For more stringent requirements, $\pm 0.01\%$ from -55 to $+125^\circ\text{C}$ is available.

Many frequencies can be supplied from stock.




INTERFACE QUARTZ DEVICES LTD

29 Market Street, Crewkerne, Somerset TA18 7JU
Crewkerne (0460) 74433 Telex 46283 inface g

WW — 063 FOR FURTHER DETAILS

carbon film RESISTORS

PRICES REDUCED. SEND FOR DETAILS NOW

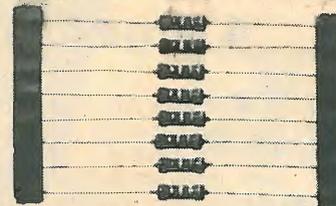

Z & I

AERO SERVICES LTD.

42-44A-46 Westbourne Grove
London W2 5SF
Tel. 01-727 5641 Telex 261306

WW—023 FOR FURTHER DETAILS

Ceramic Capacitors **£3.50** per 100
Cable Sleeves and Markers from **£1.00** per 1,000
Compression Terminals from **£7.29** per 1,000
Pcb self-fixing Guides from **£4.86** per 100
Elma Knobs and Accessories

Phone, write or call for catalogue

Carbon Film Resistors from **£4.00** per 1,000
Polystyrene Capacitors from **£1.50** per 100

Send for lists of values available


PBRA LTD. Hopfield
(073274) 345

Golden Green, Tonbridge, Kent, TN11 0LH

WW — 044 FOR FURTHER DETAILS

You can't beat The System.

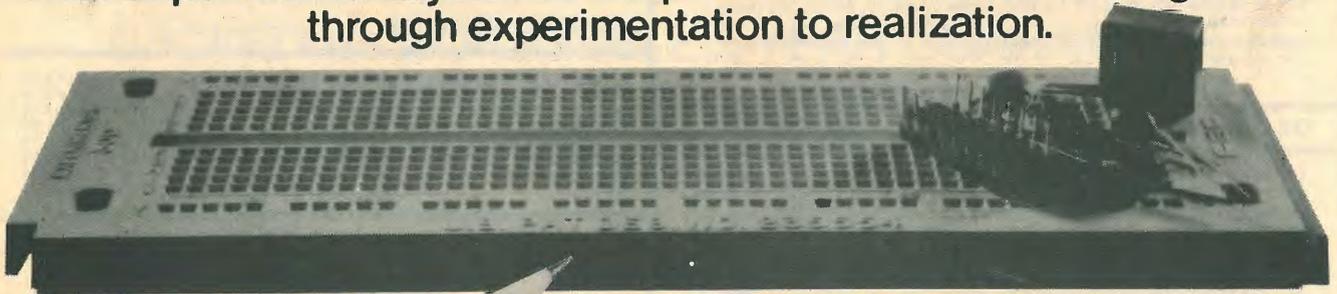The Experimentor System™ — a quicker transition from imagination through experimentation to realization.



Experimentor solderless breadboard.



Experimentor Scratchboard™ workpads.



Experimentor Matchboard™ pre-drilled PCBs.

When you have a circuit idea that you want to make happen, we have a system to make it happen quicker and easier than ever before: The Experimentor System.

You already know how big a help our Experimentor solderless breadboards can be. Now we've taken our good idea two steps further.

We've added Experimentor Scratchboard workpads, with our breadboard hole-and-connection pattern printed in light blue ink. To let you sketch up a layout you already have working so you can reproduce it later.

With Experimentor Matchboard you can go from breadboard to the finished product nonstop! We've matched our breadboard pattern again, this time on a printed circuit board, finished and ready to build on. All for about £1.32.

There's even a letter-and-number index for each hole, so you can move from breadboard (where they're moulded) to Scratchboard™ (where they're printed) to Matchboard™ (where they're silkscreened onto the component side) and always know where you are.

When you want to save time and energy, you can't beat The Experimentor System.

- 1 EXP-300PC, which includes one item: * A Matchboard pre-drilled PCB. **£1.32**
- 2 EXP-302, which includes three items: * Three 50-sheet Scratchboard workpads. **£1.68**
- 3 EXP-303, which includes three items: Two Matchboards and an EXP-300 solderless breadboard. **£8.60**
- 4 EXP-304, which includes four items: Two Matchboards, an EXP-300 breadboard and a Scratchboard workpad. **£9.30**

CONTINENTAL SPECIALTIES CORPORATION



EUROPE, AFRICA, MIDEAST: CSC UK LTD., DEPT. 7W
 Shire Hill Industrial Estate Units 1 and 2
 Saffron Walden, Essex CB11 3AQ
 Telephone: SAFFRON WALDEN (0799)
 21682. TLX 817477

CONTINENTAL SPECIALTIES CORPORATION. DEPT. 7W

Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex.

Name _____

Address _____

Inc P&P and 15% VAT

1. EXP 300PC	Qty. Reqd.	2. EXP 302	Qty. Reqd.
£2.38		£2.79	
3. EXP 303	Qty. Reqd.	4. EXP 304	Qty. Reqd.
£11.04		£11.85	

FREE Catalogue tick box

I enclose cheque/ PO for


£ _____

Phone your order with Access, Barclaycard or American Express

Card No. _____ Expiry date _____

Simply ahead!

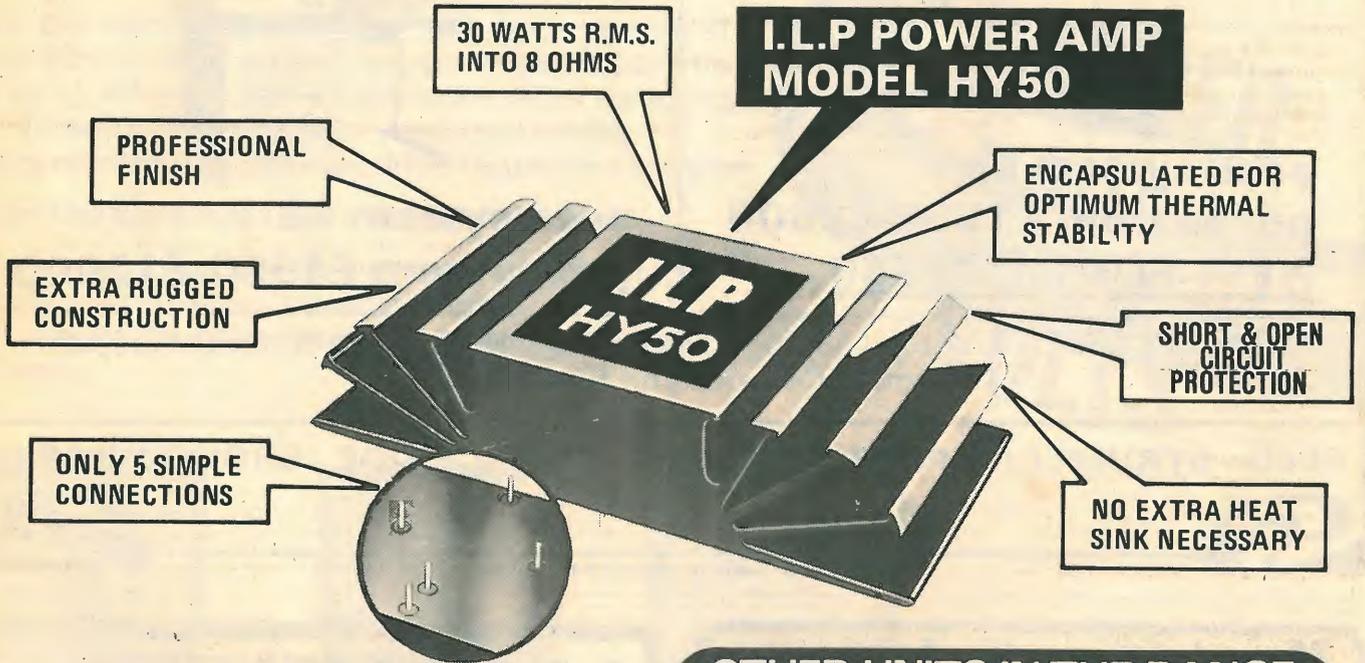**HIGH PERFORMANCE MODULAR UNITS
BACKED BY NO-QUIBBLE 5 YEAR GUARANTEE**



Of all the purpose-built power amplifier modules by I.L.P., the HY50 is understandably the most popular with those wanting to build or up-grade a hi-fi system, run a small high quality P.A. system, amplify a musical instrument (say for practise or small range use) or use it for lab work. Its useful 30 watts RMS output into 8 ohms, its rugged construction and freedom from heatsink worries make HY50 the ideal all-purpose quality power amp — and it is unconditionally guaranteed for five years! Tens of thousands are in regular use throughout the world.

... and a spec that just means what it says!

Encapsulated power amp with integral full-rated heatsink.
Input — 500mV.
Output 30 watts RMS/8Ω.
Load Impedance — 4 to 16Ω.
Distortion — 0.04% from 100mW to 25 watts at 1KHz/8Ω.
Supply Voltage ± 25V. Size 105 x 50 x 25mm.

£8.33

Inc. VAT and postage in U.K.

Nothing has been overlooked in the design and manufacture of I.L.P. Modular Units. Heavy duty heatsinks, encapsulated circuitry, no-compromise production standards and true professional finish ensure world leadership for I.L.P. Now we have **up-graded** output ratings and **down-graded** prices to bring I.L.P. within easier reach of all who want the best.

New production techniques have enabled us to reduce prices by an average of 20%, making I.L.P. a better buy than ever.

*** Guaranteed 7 days despatch on all products**

USE OUR FREE POST SERVICE


for sending your orders, requests for information sheets, etc. Simply address envelope. No stamps required.



FREEPOST 5, Graham Bell House, Roper Close, CANTERBURY, Kent CT2 7EP. Phone (0227) 54778.

OTHER UNITS IN THE RANGE

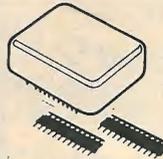
All prices inc. VAT at 15% and postage in the U.K.



HY5 PRE-AMPLIFIER

Compatible with all I.L.P. power amps and P.S.U.s. In a single pack, needs external pots and switches. Multi-function equalization, 5 inputs. High overload margin. Active tone controls, 500mV out. Distortion at 1 KHz-0.01%. Two connects easily for stereo.


£5.34

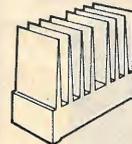

THE POWER AMPS

With heatsinks, full load line and thermal protection. Distortion typically 0.05% at 1 KHz.

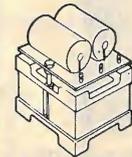HY120 60 Watts RMS/8Ω 114 x 50 x 85mm **£17.48**
HY200 120 Watts RMS/8Ω 114 x 50 x 85mm **£21.21**
HY400 240 Watts RMS/4Ω 114 x 100 x 85mm **£31.83**



THE POWER SUPPLY UNITS

(Split line outputs to suit I.L.P. power units and HY5).

PSU 50 for 1 or 2 x HY50 **£9.32**
PSU 70 for 1 or 2 x HY120 **£15.85**
PSU 90 for one HY200 **£15.85**
PSU180 for one HY400 or 2 x HY200 **£26.47**

Information sheets on application. Use our FREEPOST service.

★ OUR VALUES REMAIN SUPREME!

Please supply

Total Purchase Price

I enclose Cheque Postal Orders Money Order

Please debit my Access/Barclaycard Account number.

Name and address

Signature

FP58

Ref. Bus. No. 1032630 Eng.



STRUMECH ENGINEERING ELECTRONICS DEVELOPMENTS


★★★ **BUSINESS** ★★★ **EDUCATION** ★★★

★★★ **RESEARCH** ★★★

32K-56K RAM - DUAL MINI DISKS | **56K RAM-DUAL 8" DISKS-10MgDISK**



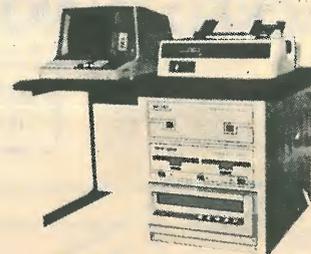seed system one
prices from £1500-£2500
NEW-FORTRAN £80



seed system 12
prices from £4500-£12000


Suppliers of equipment to: Leading Universities, H.M. Government, Hospitals, Schools, Colleges and Small Business

SEED - STRUMECH - PORTLAND HSE. - COPPICE SIDE - BROWNHILLS - WALSALL

WW - 091 FOR FURTHER DETAILS

If we told you the best way to talk to your staff... what would you say?

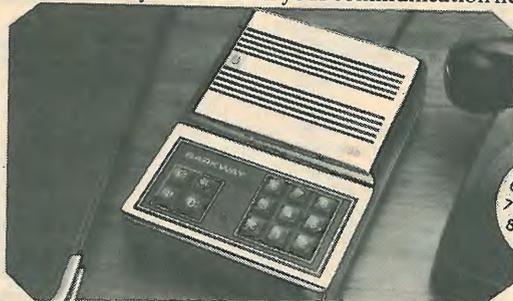We can tell you how to talk to your secretary, your accounts clerk, your foreman - or to all of them at once. We can now offer you the first really practical and economical duplex intercom system - for all your communication needs.



- The first 100% British designed and manufactured duplex intercom system
- Employs the smallest known control unit
- Offers paging facility as standard
- Conference facility up to 8 stations - also standard
- Uses less cable than competitive systems.

Easier to install - More standard facilities - *And* less expensive than most other systems




Barkway Electronics Ltd, Barkway, Royston, Herts SG8 8EE
Telephone Barkway (0763 84) 666
Telex 817651. Barcom G

WW-038 FOR FURTHER DETAILS

VORTEXION

a happy event...

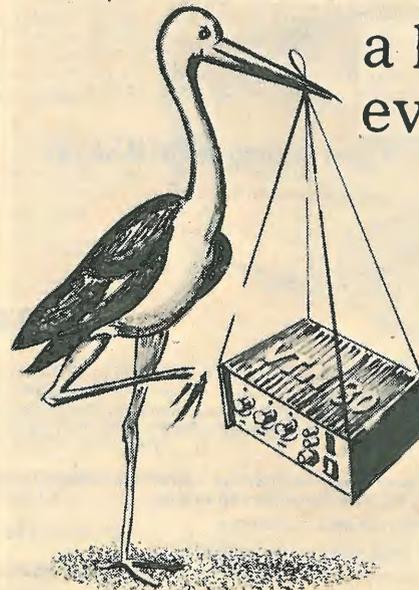

... a new addition to our family of amplifiers. The VTN 30. The new baby weighs in at 30 watts, and has a maximum of 3 inputs.

The other members of the Vortexion family are the system 2000, 50/70 watt and CP50 mains/battery amplifiers.

Contact Jennifer Hall - VORTEXION DIVISION.

Clarke & Smith Manufacturing Co. Ltd., Melbourne Works, Melbourne Road, Wallington, Surrey. Tel. 01-669 4411 Ext. 38.

Telex Casint G 22574; Telegrams: Electronic Wallington.

WW - 058 FOR FURTHER DETAILS

NOT EVERY CABLE HAS A LABEL


Everyone who works with electricity needs to know at some time or other what's going on inside the cable he's handling. What voltage. What current. What resistance. Not knowing the answers, or worse still having inaccurate answers, can make life difficult, even terminal.

Eagle Test Equipment gives the right answers


The range covers general multimeters, high voltage probes, clamp meters, insulation testers. Here are just four. Send the coupon for details of all the rest.



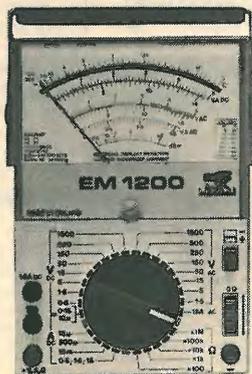
KEW 7 Multimeter
1000 OPV. DC volts up to 1000, DC amps up to 100 mA. AC volts up to 1000. Resistance up to 150 Kohms. Pocket size. "Off" damping. Complete with leads & battery. R.R.P. £6.95 ex. VAT.



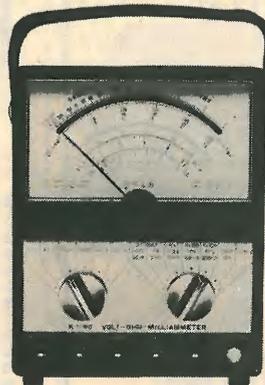EM 1200 Multimeter
100,000 OPV. Taut band movement. Overload protection. Reversible DC polarity. AC amps: 15, AC volts to 1500. DC amps up to 15, DC volts to 1500. Resistance up to 200 megohms. R.R.P. £49.95 ex. VAT.



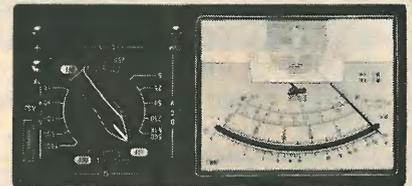K1400 Multimeter
20,000 OPV. DC and AC volts up to 5000. DC and AC amps up to 10. Resistance up to 20 megohms. "Off" damping. Overload protection. R.R.P. £79.35 ex. VAT.



EM10, 20 & 30 Multimeters
10, 20 & 30,000 OPV. All with antiparallax mirror scale. DC volts to 1000 (1200 for EM30). DC amps to 250 mA (600 for EM30). AC volts to 1000 (1200 for EM30). Resistance up to 6.5 and 60 megohms respectively. R.R.P.'s EM10 £13.50 EM20 £17.25, EM30 £20.75 ex. VAT.

Test Equipment: EAGLE



Please send me details of your complete range of Test Equipment.

Name _____ Company _____


Address _____

EAGLE INTERNATIONAL Precision Centre, Heather Park Drive, Wembley, Middlesex HA0 1SU.

ww9

NEW! from

OLSON

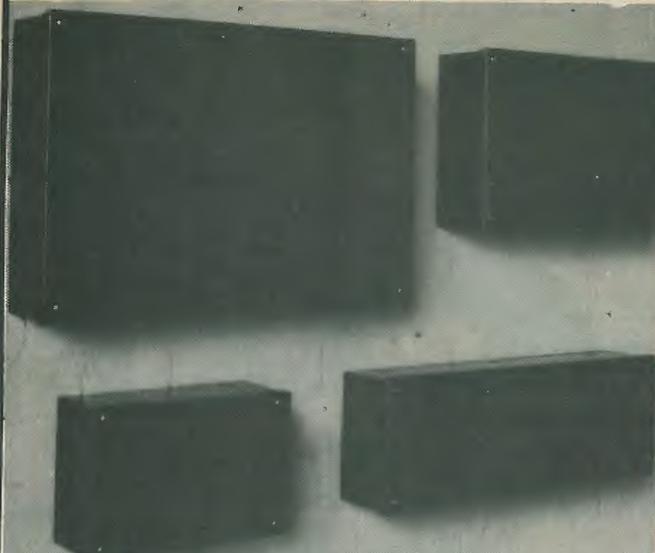

WALL MOUNTING CASES In four sizes.

Made from 18G M/S. In dark grey, hammer.

- Type 301 — 175mm x 250 x 110—**£7.25**
- 302—250mm x 350 x 110—**£9.50** + Post
- 303—175mm x 500 x 110—**£9.50** & VAT
- 304 — 350mm x 500 x 110—**£13.50**



low cost ultra violet eprom erasing lamp will erase up to 12 chips at one time.

PRICE £95.00 + VAT


**INSTANT TRUNKING SYSTEM!
4 FEET LONG FOR WALL OR BENCH MOUNTING**



- Ready to use. Internal wiring suitable for 30 amp
- TR6** — 6 sockets switched **£21.50** P&P **£1.85**
 - TR9** — 9 sockets switched **£25.50** + VAT

**PORTABLE POWER DISTRIBUTION
FOR INSTANT MAINS!**

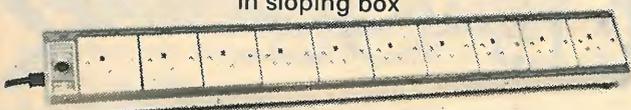**NEW! 10 sockets switched
in sloping box**



Type 13A/10SW **£27.50**. P&P **£1.85** + VAT

- COMPLETE WITH 6FT. CABLE AND 13 AMP. FUSED PLUG
- 4 sockets 13A **£12.15**
 - 6 sockets 13A **£14.30**
 - 4 sockets 13A switched **£13.75**
 - 6 sockets 13A switched **£15.95**
- + post 85p + VAT

ALL DISTRIBUTION PANELS ARE FITTED WITH MK SOCKETS & PLUG
Send for details of complete range
OLSON ELECTRONICS LTD., FACTORY NO. 8, 5-7 LONG ST., LONDON E2 8HJ
TEL: 01-739 2343


WW — 081 FOR FURTHER DETAILS

STOP IT!

Heyco Nylon Hole Plugs



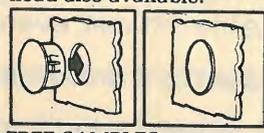seal unwanted holes neatly, quickly and easily. Snap-lock into panels with fingertip pressure. Low cost. 20 sizes for holes from 3/16" to 2".
Vent plugs with perforated head also available.



20 SIZES

FREE SAMPLES and catalogue showing our full range of bushings on request.

Heyco have got it made for cables



Heyco Manufacturing Co. Ltd.,
Uddens Trading Estate,
Nr Wimborne, Dorset BH21 7NL.
Tel: Ferndown (STD: 0202) 871411/2/3/4.
Telegrams: HEYCOMAN Wimborne.
Telex: 41408.

WW — 098 FOR FURTHER DETAILS

STEREO DISC AMPLIFIER 3

A reference amplifier for disc monitoring and transfer when replay signals of the highest quality are required.

Based on the Surrey Electronics Disc Amplifier 2 and manufactured under licence, two unbalanced outputs are provided enabling Line and DIN level inputs to be driven simultaneously. To facilitate cartridge matching, a wide range of switchable load capacitance and resistance values are provided, together with left and right 20 turn gain presets.

DYNAMIC INTERMODULATION DISTORTION

It is now widely recognised that two pieces of equipment may have the same Total Harmonic and Static Intermodulation distortion performance yet sound quite different. Remaining distortion is attributed to transient distortion effects and these can be quantified with a combined square wave and sine wave test signal. The signal used consists of a 3.18kHz square wave through



single pole —3dB at 100 kHz plus 15 kHz sine wave, 4:1 amplitude ratio. The signal before pre-emphasis is shown above. Distortion in the equipment under test will produce sum and difference products and the RMS sum of those below 15 kHz quoted relative to the amplitude of the 15 kHz sine wave is the Dynamic Intermodulation Distortion.
High (Line) output: Loaded with 10kΩ, 1kHz at —44dBV, 7 (5mV) set for OdBV, 7 output. Pre-emphasised input 500mV pk-pk. —70dB, 0.03% measurement limit.

Price: cash with order, UK postage and 15% VAT inclusive £169.

Dominus P.O. Box 1 Cranleigh, Surrey
Tel. 04866 6477

QUALITY REEL TO REEL & CASSETTE TAPE HEADS

SOME POPULAR UNIVERSAL CASSETTE TAPE HEADS	
B12-01 MONO PLAYBACK	£1.89
B12-02 MONO RECORD/PLAYBACK	£4.02
B24-01 STEREO PLAYBACK	£3.30
B24-02 STEREO RECORD/PLAYBACK	£6.66
B24-RP STEREO GLASS FERRITE REC/PLBK	£11.60
E12-09 MONO/STEREO ERASE	£1.85
B22-02 TWIN HALF TRACK RECORD/PLBK	£5.97
C44RPS02 QUAD QUARTER TRACK REC/PLBK	£9.37
C22ES02 TWIN HALF TRACK ERASE	£4.72

MAGNETIC TAPE HEADS CATALOGUE 25 PENCE
AUDIO AND HI-FI CATALOGUE (80 PAGE FULL COLOUR) 50 PENCE

MONOLITH


PLEASE ENCLOSE 20p P&P WITH ORDER

THE MONOLITH ELECTRONICS CO. LTD.
5/7 CHURCH ST., CREWKERNE, SOMERSET, ENGLAND. (0460) 74321

ALL PRICES INCLUDE VAT

YOUR COMPLETE RANGE OF ELECTRONIC HARDWARE...

BIMENCLOSURES

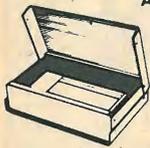


ALL METAL BIMCASES

Red, Grey or Orange 14swg Aluminium removable top and bottom covers. 18 swg black mild steel chassis with fixing support brackets.
BIM 3000
(250x167.5x68.5mm)
£15.52



MINI DESK BIMCONSOLES

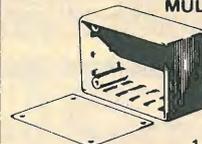Orange, Blue, Black or Grey ABS body incorporates 1.8mm pcb guides, stand-off bosses in base with 4 BIMFEET supplied. 1mm Grey Aluminium panel sits recessed with fixing screws into integral brass bushes.
BIM 1005 (161 x 96 x 58mm) £2.48
BIM 1006 (215 x 130 x 75mm) £3.48



MULTI PURPOSE BIMBOXES

Orange, Blue, Black or Grey ABS with 1mm Grey Aluminium recessed front cover held by screws into integral brass bushes. 1.8mm pcb guides incorporated and 4 BIMFEET supplied.
BIM 4003 (85x56x28.5mm) £1.34
BIM 4004 (111x71x41.5mm) £1.84
BIM 4005 (161x96x52.5mm) £2.48




ALL METAL BIMCONSOLES

All aluminium, 2 piece desk consoles with either 15° or 30° sloping fronts, sit on 4 self-adhesive non-slip rubber feet. Ventilation slots in base and rear panel for excellent cooling. See latest catalogue for new styles and sizes

	Colour Code	Top Panel	Base	
	A	Off White	Blue	
	B	Sand	Green	
	C	Satin Black	Gold	

15° Sloping Panel	30° Sloping Panel	
BIM7151 (102x140x51 [28] mm)	BIM7301 (102x140x76 [28] mm)	£11.36
BIM7152 (165x140x51 [28] mm)	BIM7302 (165x140x76 [28] mm)	£12.28
BIM7153 (165x216x51 [28] mm)	BIM7303 (165x183x102 [28] mm)	£13.43
BIM7154 (165x211x76 [33] mm)	BIM7304 (254x140x76 [28] mm)	£14.83
BIM7155 (254x211x76 [33] mm)	BIM7305 (254x183x102 [28] mm)	£16.36
BIM7156 (254x287x76 [33] mm)	BIM7306 (254x259x102 [28] mm)	£17.71
BIM7157 (356x211x76 [33] mm)	BIM7307 (356x183x102 [28] mm)	£18.83
BIM7158 (356x287x76 [33] mm)	BIM7308 (356x259x102 [28] mm)	£19.92

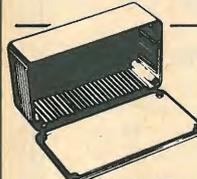


ABS & DIECAST BIMBOXES

6 sizes in ABS or Diecast Aluminium. ABS moulded in Orange, Blue, Black or Grey. Diecast Aluminium in Grey Hammetone or Natural. All boxes incorporate 1.8mm pcb guides, stand-off supports in base and have close fitting flanged lids held by screws into integral brass bushes (ABS) or tapped holes (Diecast).

	ABS	Diecast	Hammetone	Natural
(50x50x25mm)	N/A	BIM5001/11	£1.54	£1.23
(100x50x25mm)	BIM2002/12	BIM5002/12	£1.66	£1.32
(112x62x31mm)	BIM2003/13	BIM5003/13	£2.24	£1.70
(120x65x40mm)	BIM2004/14	BIM5004/14	£2.81	£2.11
(150x80x50mm)	BIM2005/15	BIM5005/15	£3.19	£2.72
(190x110x60mm)	BIM2006/16	BIM5006/16	£4.94	£3.96

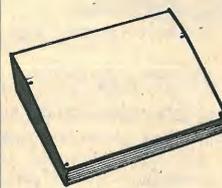
Also available in Grey Polystyrene with no slots and self-tapping screws
BIM 2007/17 (112x61x31mm) £1.06



LOW PROFILE BIMCONSOLES

Orange, Blue, Black or Grey ABS body has ventilation slots as well as 1.8mm pcb guides and stand-off bosses in base. Double angle recessed front panel with 4 fixing screws into integral brass bushes. 4 BIMFEET supplied.

BIM 6005 (143 x 105 x 55.5 [31.5] mm)	£2.76
BIM 6006 (143 x 170 x 55.5 [31.5] mm)	£3.58
BIM 6007 (214 x 170 x 82.0 [31.5] mm)	£4.83

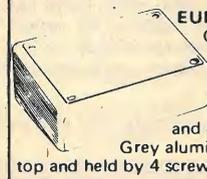


EUROCARD BIMCONSOLES

Orange, Blue, Black or Grey ABS body accepts full or 1/2 size Eurocards, with bosses in the base for direct fixing. 1.8mm wide pcb guides incorporated and 4 BIMFEET supplied. 1mm Grey aluminium lid sits flush with body top and held by 4 screws into integral brass bushes.

BIM 8005 (169x127x70 [45] mm)	£4.71
BIM 8007 (243x187x103 [66] mm)	£6.70

BIMTOOLS + BIMACCESSORIES

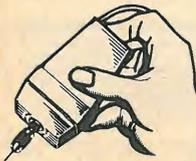

MAINS BIMDRILLS


Small, powerful 240V hand drill complete with 2 metres of cable and 2 pin DIN plug. Accepts all tools with 1mm, 2mm or .125" dia. shanks. Drills brass, steel, aluminium and pcb's. Under 250g, off load speed 7500 rpm. Orange ABS, high impact, fully insulated body with integral on/off switch £11.21

Mains Accessory Kit 1 includes 1mm, 2mm, .125" twist drills, 5 burrs and 2.4mm collet £2.64

Mains Kit 2 includes Mains BIMDRILL as above, 20 assorted drills, mops, burrs, grinding wheels and mounted points, 1mm, 2mm, 2.4mm and .125" collets. Complete in transparent case measuring 230x130x58mm £23.57

BIMDAPTORS

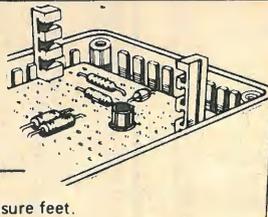Allows pcb's to be flat mounted sandwich fashion in BIMBOXES, BIMCONSOLES, and all other enclosures having 1.5mm wide vertical guide slots. One plastic BIMDAPTOR on each corner of pcb(s) enables assembly to be simply slid into place. 54mm long, 10 slots on 5mm spacing and can be simply snapped off to length. £1.15 per pack of 25.



BIMFEET

11mm dia. 3mm high, grey rubber self-adhesive enclosure feet.
£0.81 per pack of 24.




12 VOLT BIMDRILLS

2 small, powerful drills easily hand held or used with lathe/stand adaptor. Integral on/off switch and 1 metre cable.

Mini BIMDRILL with 3 collets up to 2.4mm dia. £ 8.62
Major BIMDRILL with 4 collets up to 3mm dia. £14.49

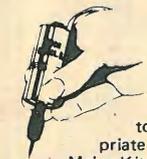Accessory Kits 1 have appropriate drills and collets as above plus 20 assorted tools. Mini Kit 1 - £16.10, Major Kit 1 - £20.70. Accessory Kits 2 have appropriate drills, collets plus 40 tools and mains-12V dc adaptor. Mini Kit 2 - £36.22, Major Kit 2 - £41.97. Accessory Kits 3 as appropriate Kits 2 plus stand/lathe unit. Mini Kit 3 - £48.30, Major Kit 3 - £54.05.




BIMPUMPS

2 all metal desoldering tools provide high suction power and have easily replaceable screw in Teflon tips. Primed and released by thumb operation with in-built safety guard and anti-recoil system.
BIMPUMP Major (180mm long) £8.51
BIMPUMP Minor (150mm long) £7.24




BIMIRONS

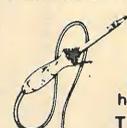Type 30 General Purpose 27 watt iron with long life, rapid change element, screw on tip, stainless steel shaft and clip on hook. Styled handle with neon. £4.37
Type M3 Precision 17 watt iron, quick change tip, long life element, styled handle with clip on hook. £4.71



BIMBOARDS

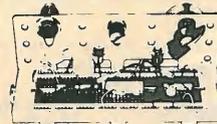

DIL COMPATIBLE BIMBOARDS



Accept all sizes (4-50 pin) of DIL IC packages as well as resistors, diodes, capacitors and LEDs. Integral Bus Strips up each side for power lines and Component Support Bracket for holding lamps, switches and fuses etc. Available as single or multiple

units, the latter mounted on 1.5mm thick black aluminium back plate which stand on non slip rubber feet and have 4 screw terminals for incoming power.

BIMBOARD 1 has 550 sockets, multiple units utilising 2, 3 and 4 BIMBOARDS incorporate 1100, 1650 and 2200 sockets, all on 2.5mm (0.1") matrix.

BIMBOARD 1	£ 9.40
BIMBOARD 2	£22.37
BIMBOARD 3	£31.83
BIMBOARD 4	£41.53

DESIGNER PROTOTYPING SYSTEM

1, 2, or 3 BIMBOARDS mounted on BIM 6007 BIMCONSOLE with Integral Power Supply (±5 to ±15Vdc @ 100mA and fixed +5Vdc @ 1A) All O/P's fully isolated. Short circuit and fast fold back protection. Power rails brought out to cable clamps that accept stripped wire or 4mm plug.

DESIGNER 1	£58.65
DESIGNER 2	£64.97
DESIGNER 3	£71.30

...FROM **BOSS**
INDUSTRIAL MOULDINGS LIMITED

All quoted prices are 1 off and include Postage, Packing and VAT. Terms are strictly cash with order unless you have authorised BOSS account. For individual data sheets or short form catalogue on all BOSS products send stamped, self addressed 4" x 8" envelope.

2, Herne Hill Road, London SE24 0AU
Telephone: 01 737 2383
Telex: 919693 Answer Back 'LITZEN G'
Cables & Telegrams: 'LITZEN LONDON SE24'

Ohio Scientifics

SUPERBOARD III

Now only

£188 + VAT

Full 8K basic and 4K user RAM
Power supply and R.F. Converter P.O.A.

Built and tested

(Delivery within 7 days)

Features

- Uses the ultra powerful 6502 microprocessor
- 8K Microsoft BASIC-in-ROM
- Full feature BASIC runs faster than currently available personal computers and all 8080-based business computers.
- 4K static RAM on board expandable to 8K
- Full 53-key keyboard with upper-lower case and user programmability
- Kansas City standard audio cassette interface for high reliability
- Full machine code monitor and I/O utilities in ROM
- Direct access video display has 1K of dedicated memory (besides 4K user memory), features uppercase, lower case, graphics and gaming characters for an effective screen resolution of up to 256 by 256 points. Normal TV's with overscan display about 24 rows of 24 characters, without overscan up to 30 x 30 characters.

Extras

- Available expander board features 24K static RAM (additional mini-floppy interface, port adapter for printer and modem and OSI 48 line expansion interface.
- Assembler/editor and extended machine code monitor available.

Commands

CONT	LIST	NEW	NULL	RUN
Statements				
CLEAR	DATA	DEF	DIM	END FOR
GOTO	GOSUB	IF...GOTO	IF...THEN	INPUT LET
NEXT	ON...GOTO	ON...GOSUB	POKE	PRINT READ
REM	RESTORE	RETURN	STOP	

Expressions

Operators
-, +, *, /, ↑, NOT, AND, OR, >, <, <>, >=, <=, =
RANGE 10⁻³² to 10⁺³²

Functions

ABS(X)	ATN(X)	COS(X)	EXP(X)	FRE(X)	INT(X)
LOG(X)	PEEK(I)	POS(I)	RND(X)	SGN(X)	SIN(X)
SPC(I)	SQR(I)	TAB(I)	TAN(X)	USR(I)	

String Functions

ASC(X\$)	CHR\$(I)	FRE(X\$)	LEFT\$(X\$,I)	LEN(X\$)	MID\$(X\$,I,J)
RIGHT\$(X\$,I)			STR\$(X)		VAL(X\$)

Plus variables, arrays and editing facilities.

Fully built and tested. Requires only +5V at 3 amps and a videomonitor or TV and RF converter to be up and running.



4 MORGAN STREET
LONDON E3 5AB

TELEPHONE: 01-981 3993
TELEX: 261426 ATN. LOTUS SOUND

WW — 104 FOR FURTHER DETAILS

the indispensable BIRD 43



THRULINE® WATTMETER
0.45-2300 MHz / 0.1-10,000 watts

The Standard of the Industry
What more need we say...

Exclusive UK representative

aspen electronics limited

2 KILDARE CLOSE, EASTCOTE, MIDDX. HA4 9UR
TELEPHONE: 01-868 1188 — TELEX 8812727

ASTRA-PAK

92 GOLFSTONE ROAD
WHYTELEAF SURREY CR3 0EB

All prices include V.A.T. Add 25p for P&P (Extra for overseas). Discounts over £10 less 5%, over £20 less 5%, over £20 less 10%, over £50 less 15%, over £100 less 20%. Sgnd SAE for complete list of components.

7400	0.12	7495	0.54	74190	1.05	74LS113	0.36	4007	0.16	4085	0.72
7401	0.12	7496	0.60	74191	0.99	74LS114	0.36	4008	0.82	4086	0.76
7402	0.12	7497	2.38	74192	0.99	74LS123	0.82	4009	0.46	4089	1.55
7403	0.12	74100	0.84	74193	1.05	74LS124	2.44	4010	0.48	4093	0.65
7404	0.13	74104	0.40	74194	0.90	74LS125	0.44	4011	0.15	4094	1.80
7405	0.13	74105	0.40	74195	0.50	74LS126	0.44	4012	0.18	4095	1.10
7406	0.28	74107	0.28	74196	0.90	74LS132	0.69	4013	0.42	4097	3.50
7407	0.28	74109	0.45	74197	0.90	74LS136	0.40	4014	0.80	4097	3.50
7408	0.14	74110	0.46	74198	1.48	74LS138	0.53	4015	0.77	4098	1.12
7409	0.14	74111	0.70	74199	1.48	74LS139	0.53	4016	0.42	4099	1.90
7410	0.13	74116	1.60	74221	1.50	74LS151	1.06	4017	0.87	4412	0.30
7411	0.18	74118	0.82	74273	2.15	74LS153	0.50	4018	0.42	4428	0.80
7412	0.21	74119	1.30	74279	1.25	74LS154	1.20	4019	0.92	4445	1.50
7413	0.25	74120	0.82	74283	1.70	74LS155	0.88	4020	0.92	4449	0.30
7414	0.54	74121	0.25	74284	6.85	74LS156	0.86	4021	0.82	4501	0.17
7416	0.27	74122	0.40	74293	1.35	74LS157	0.47	4022	0.82	4501	0.17
7417	0.27	74123	0.53	74298	1.92	74LS158	0.53	4023	0.15	4502	0.88
7420	0.13	74125	0.44	74390	0.27	74LS160	1.22	4024	0.68	4507	0.50
7421	0.28	74126	0.45	74393	2.12	74LS161	0.69	4025	0.15	4508	2.25
7422	0.17	74128	0.62	74LS00	0.18	74LS162	1.22	4026	1.28	4510	1.05
7423	0.25	74132	0.88	74LS01	0.19	74LS163	0.69	4027	0.50	4511	0.98
7425	0.20	74135	0.68	74LS02	0.19	74LS164	1.20	4028	0.67	4512	0.92
7426	0.25	74136	0.78	74LS03	0.19	74LS168	2.00	4029	0.88	4514	2.85
7427	0.25	74137	0.94	74LS04	0.20	74LS169	2.00	4030	0.48	4515	2.80
7428	0.34	74141	0.58	74LS05	0.20	74LS170	1.78	4031	2.34	4516	1.02
7430	0.13	74142	2.00	74LS08	0.19	74LS173	1.05	4033	1.25	4518	0.99
7432	0.24	74143	2.00	74LS09	0.19	74LS174	1.12	4034	2.00	4519	0.50
7433	0.32	74144	0.80	74LS10	0.19	74LS175	1.05	4035	1.00	4520	1.05
7437	0.24	74145	0.64	74LS11	0.19	74LS178	2.85	4036	2.40	4521	2.00
7438	0.24	74147	1.30	74LS12	0.19	74LS190	0.81	4037	0.99	4522	1.35
7440	0.13	74148	1.18	74LS13	0.48	74LS191	0.81	4038	1.00	4527	1.80
7441	0.52	74150	0.99	74LS14	1.10	74LS192	1.80	4039	2.80	4528	0.82
7442	0.55	74151	0.80	74LS15	0.19	74LS193	1.80	4040	0.88	4529	1.10
7443	0.90	74153	0.80	74LS20	0.19	74LS195	1.12	4041	0.77	4536	3.56
7444	0.90	74154	1.05	74LS21	0.19	74LS196	1.20	4042	0.72	4553	4.20
7445	0.70	74155	0.63	74LS22	0.19	74LS197	1.20	4043	0.82	4555	0.85
7446	0.70	74156	0.63	74LS26	0.24	74LS221	1.12	4044	0.82	4556	0.85
7447A	0.84	74157	0.63	74LS27	0.40	74LS247	0.97	4045	1.40	4558	1.25
7448	0.80	74159	1.70	74LS30	0.19	74LS248	0.97	4046	1.32	4566	1.40
7450	0.13	74160	0.80	74LS32	0.25	74LS249	0.97	4047	0.96	4583	0.75
7451	0.13	74161	0.80	74LS37	0.27	74LS251	1.00	4048	0.68	4585	0.85
7453	0.13	74162	0.80	74LS38	0.27	74LS253	1.05	4049	0.62	4585	0.85
7454	0.13	74163	0.80	74LS40	0.19	74LS257	1.05	4050	0.42	4588	1.25
7460	0.13	74164	0.89	74LS42	0.53	74LS258	1.05	4051	0.84	4588	1.25
7470	0.28	74165	0.89	74LS43	0.97	74LS266	0.39	4052	0.84	4588	1.25
7472	0.22	75166	0.99	74LS47	0.97	74LS273	2.80	4053	0.84	4588	1.25
7473	0.26	74167	2.70	74LS48	0.97	74LS279	0.50	4054	1.18	4588	1.25
7474	0.28	74170	1.68	74LS51	0.19	74LS283	1.00	4055	1.00	4588	1.25
7475	0.30	74172	4.00	74LS54	0.19	74LS289	2.85	4060	0.98	4588	1.25
7476	0.28	74173	1.18	74LS55	0.20	74LS293	0.90	4066	0.48	4588	1.25
7480	0.45	74174	0.89	74LS74	0.34	74LS298	1.00	4067	3.50	4588	1.25
7481	0.90	74175	0.68	74LS75	0.45	74LS352	0.92	4068	0.24	4588	1.25
7482	0.80	74176	0.88	74LS76	0.32	74LS353	1.05	4069	0.17	4588	1.25
7483	0.72	74177	0.88	74LS75	0.32	74LS365	0.50	4070	0.17	4588	1.25
7484	0.80	74178	1.20	74LS78	0.32	74LS366	0.50	4071	0.17	4588	1.25
7485	0.58	74179	1.10	74LS83	0.78	74LS367	0.50	4072	0.17	4588	1.25
7486	0.28	74180	0.80	74LS85	0.80	74LS368	0.50	4073	0.17	4588	1.25
7489	2.00	74181	1.92	74LS86	0.35	74LS386	0.37	4075	0.17	4588	1.25
7490	0.35	74182	0.75	74LS89	0.86	74LS670	2.00	4076	1.05	4588	1.25
7491	0.85	74184	1.20	74LS95	1.10	4000	0.14	4077	0.48	4588	1.25
7492	0.44	74185A	1.20	74LS107	0.36	4001	0.15	4078	0.22	4588	1.25
7493	0.40	74186	7.20	74LS109	0.36	4002	0.16	4081	0.17	4588	1.25
7494	0.80	74188	2.70	74LS112	0.38	4006	0.82	4082	0.20	4588	1.25

WW—040 FOR FURTHER DETAILS

Try our boots on for size



Highvol capacitor boots give complete insulation of the terminal. Slip-on assembly — no mess, no heat. 30 sizes ensure a snug fit, yet the terminal remains easily accessible. 3 types for Tantalum, Aluminium and Ceramic capacitors, all conforming to UL safety and flammability ratings. FREE samples and catalogue showing our full range of insulator covers on request.



HIGHVOL CONNECTORS LTD.
Uddens Trading Estate,
Nr. Wimborne, Dorset BH21 7NL.
Tel: Ferndown (STD 0202) 871411/2/3/4
Telex: 41408

WW — 083 FOR FURTHER DETAILS



747 UNIVERSAL COUNTER TIMER £175 + £3.50 p&p

DC-150MHz
8 DIGITS
8 FUNCTIONS
3 CHANNELS

Measures — A KHz, C MHz, Period A, Pulse Width A±, Time A± to B±, Count A, Count A (gated by B, reset by C)
Max. resolution 0.1Hz, 100pS.
Averages 1 to 1000 events.

Also available — Counter Timers, Frequency Meters, Filter Oscillators, Function Generators, Off-air Standards, Lab/Bench Power Supplies, Panel Meters & Bar Indicators.

OMB ELECTRONICS
Riverside, Eynsford, Kent DA4 0AE
Tel: Farningham (0322) 863567

Prices, which are CWO & ex-VAT, are correct at time of going to press and are subject to change without notice.

WW — 070 FOR FURTHER DETAILS

Measure Resistance to 0.01Ω ... At a Price that has no resistance at all

New **ELENCO PRECISION** Digital Multimeter M1200B
USA

ONLY £55 (£3 p&p + VAT £8.70 = £66.70)

*FULLY GUARANTEED FOR 2 YEARS

*METAL CASE

*EX STOCK DELIVERY



**THE ULTIMATE IN PERFORMANCE —
MEASURES RESISTANCE TO 0.01 OHMS,
VOLTAGE TO 100 MICROVOLTS, CURRENT
TO 1 MICROAMPS AT LOWEST EVER PRICE!**

FEATURES

- 3½ digits 0.56" high LED for easy reading
- 100μV, 1μA, 0.01Ω resolution
- High input impedance 10 Megohm
- High accuracy achieved with precision resistors, not unstable trim pots
- Input overload protected to 1000V (except 200mV scale to 600V)
- Auto zeroing, autopolarity
- Mains (with adaptors not supplied) or battery operation—built-in charging circuitry for NiCads
- Overrange indication
- Hi Low power ohms, Lo for resistors in circuit, Hi for diodes

SPECIFICATIONS:

DC Volts	Range 200mV, 2V, 20V, 200V, 1000V Accuracy 1% ± 1 digit, Resolution .1mV Overload protection 1,000 volts max
AC Volts	Range 200mV, 2V, 20V, 200V, 1000V Accuracy 1.5% ± 2 digits, Resolution .1mV Overload protection 1000V max, 200mV scale 600V
DC Current	Range 2mA, 20mA, 200mA, 2amp. Accuracy 1% ± 1 digit, Resolution 1 Microamp Overload protection — 2 amp fuse and diodes
AC Current	Range 2mA, 20mA, 200mA, 2 amp Accuracy 1.5% ± 2 digits, Resolution 1 Microamp Overload protection — 2 amp fuse and diodes
Resistance	Range 20, 200, 2K, 200K, 2 Meg. 20 Meg. Accuracy 1% ± 1 digit, Resolution .01 ohms
Environmental	Temp coefficient 0° to 30° C ± .025% C Operating Temp 0° to 50° C Storage — 20° to 60° C
General	Mains adaptor: 6 - 9 Volts @ 200mA (not supplied) 4C size batteries (not supplied) Size 8¼ x 5¼ x 2¼ Weight 2½ lbs.

To: Maclin-Zand Electronics Ltd
1st Floor, Unit 10, East Block
38 Mount Pleasant, London WC1X 0AP

Please send me DMM M1200B
@ **£66.70 inc. p&p + VAT (overseas £60)**
I enclose cheque/PO/Bank Draft for £

Name

Address

(BLOCK LETTERS PLEASE)

ELENCO PRECISION Sole UK Distributor



Maclin-Zand Electronics Ltd
38 Mount Pleasant, London WC1X 0AP

© N Zand **Tel. 01-837 1165**
Telex. 8953084 MACLING

WW — 076 FOR FURTHER DETAILS

we wondered why....

The B.B.C., British Rail, B.A.C., Decca Acoustics, Institute of Sound and Vibration Research, I.C.L., Post Office Telecommunications, Philips Research, U.K. Atomic Energy Authority, and many Universities were among our customers.

Maybe they liked the competitive prices of our modules, or the fact that all modules have a frequency response from 20Hz to 22kHz -0.2dB, a slewing rate of 8 volts per microsecond, input sensitivity of 0dB (0.775V), a damping factor greater than 400 to 1kHz and a total harmonic distortion less than 0.055% at 1kHz.

Or could it be that they want for the reliability and the comprehensive protection circuitry. Then there is the full 2 year guarantee which accompanies our range of modules.


OR PERHAPS THEY JUST LIKED THE SOUND OF US!

J.P.S. 60 : 60 Watt.
J.P.S. 100 : 100 Watt.
J.P.S. 150 : 150 Watt.




Power supplies available to suit all modules. Send for further information on our range of pre-amplifier modules. J.P.S. products are now stocked at the distributors shown below. Further information on all products available direct from J.P.S. Associates or via reader reply service.

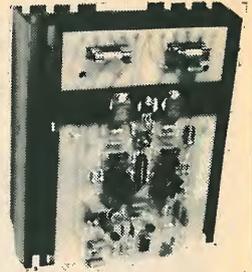All modules are made in the United Kingdom.



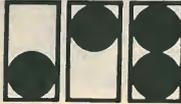J.P.S. ASSOCIATES
(ASTONKILN LTD.)
BELMONT HOUSE
STEELE ROAD
PARK ROYAL
LONDON NW10 7AR
Tel: 01-961 1274/5



BELGIUM
Sindiek Elektronika
Trompsstraat 290
3000 Leuven, Belgium
Tel. (016) 234554
Contact: Mr. Leo Swinnen

ENGLAND, Midlands
CROXFORD CUSTOM EQUIP.
64 London Road
Litchfield
Tel. 0533 339485
Mr. Phil Croxford

ENGLAND, West
SEVERNIDE AUDIO & LTD
29 The Promenade
Gloucester Road
Bristol BS7 9TZ
Tel. 0272 41066
Mr. Peter Hanney

ENGLAND, South
R.E.W. AUDIO VISUAL
128 Charing Cross Road
London
WC2
Tel. 01-436 2372
Mr. John Cowan

SCOTLAND
ATMOSPHERE LTD & SOUND
57 Nelson Street
Aberdeen
Scotland
Tel. 0224 572905
Mr. Keith Main

FRANCE
MUSIQUE & SON
1 Residence Bel-Event
95200, Comcais, France
Tel. (00) 00 67 77
Mr. Yves Jambic

WW-032 FOR FURTHER DETAILS

CAN YOUR BUSINESS
REALLY OPERATE SUCCESSFULLY
without a **MICROPROCESSOR**



STRUTT

Electrical and Mechanical
Engineering Ltd.

3c BARLEY MARKET STREET, TAVISTOCK,
DEVON. PL19 0SF.

TELEPHONE: TAVISTOCK 5439

TELEX: 45263

BUSINESS MICROPROCESSOR

The SEMEL 1. Microprocessor can be used for VAT, Wages, Invoices, Stock-Control, School Computer Studies, Wordprocessing, Sales, Purchasing, Addressing envelopes, Auditing, Estate Agents:(For listing all Properties in groups ie. Size, Cost, Area) For doing all Bookings: Coach Tour Operators, Travel Agents, Hotels, etc.

The SEMEL 1. Can also be used for operating Machines and Equipment.


The SEMEL 1. can be coupled, via suitable interface circuits, to a wide variety of external devices, such as Computers, other Microprocessors, Printers, Cash Registers, Tape Readers & Punches, Cassette Readers/Recorders, any input output Typewriter, and many more.

SEMEL Business System - this system consists of the Microprocessor unit with keyboard and VDU and one Floppy Disc Unit. This system contains a software package of Editor assembler and debug, and full file handling capabilities in Basic Language. Systems requiring high level language including an extended operating system and utilities and 64k of RAM can support Basic, Fortran and Cobol.

SEMEL-1

The **MICROPROCESSOR** is perhaps the most important development the electronics industry has seen for at least the last decade. It was introduced with the ever increasing demand for speed and efficiency required in industry and commerce, and because of its ability to perform a wide variety of different functions, whether in the office, stores, on the factory floor, in warehouses, schools, on ships, in vehicles and many more places of business.

WW-042 FOR FURTHER DETAILS

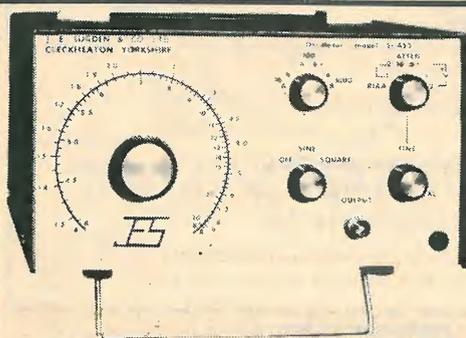

JES AUDIO INSTRUMENTATION

Illustrated the Si453 Audio Oscillator

SPECIAL FEATURES:

- ★ very low distortion content—less than 0.03%
- ★ an output conforming to RIAA recording characteristic
- ★ battery operation for no ripple or hum loop
- ★ square wave output of fast rise time

£70.00

also available

Si451 Millivoltmeter

- ★ 20 ranges also with variable control permitting easy reading of relative frequency response

£70.00

Si452 Distortion Measuring Unit

- ★ low cost distortion measurement down to 0.01% with comprehensive facilities including L.F. cut switch, etc.

£56.00

ALL PRICES PLUS VAT

J. E. SUGDEN & CO. LTD., CARR STREET, CLECKHEATON, W. YORKS. BD19 5LA.

Tel. 0274-872501

WW-026 FOR FURTHER DETAILS

THE NEW PIL SHOWROOM



**More to see...
more room to see it in.**

Pil are pleased to announce the official opening of their new 1500 sq. ft. showroom to the public.

Offering a range of some 350 electrical measuring instruments manufactured by around 60 manufacturers, both British and international.

Pil can cater for practically every electrical measurement problem for any user on an ex-stock/short delivery basis.

The showroom facilities and its technical back-up are available to everyone from export

Factory/Repairs 01-639 0155
North London Showroom 01-965 2352

houses and overseas users, buyers engineers, to do-it-yourself enthusiasts and hobbyists.

Instruments Electrical the service and calibration division can provide full guarantee facilities as well as offering their normal repair and calibration service.

For an immediate solution to your instrument problems, contact the Instrument Group at Instrument House.

Showroom/Sales/Export 01-639 4461
Open Mon. to Fri. (ring for Sat. opening times)

PIL

**AN IEC GROUP
COMPANY**

**INSTRUMENT HOUSE, 727 OLD KENT ROAD, LONDON SE15
TELEPHONE: 01-639 4461 TELEX: 8811854 (INTEL)**

fact: viscous-damping straightens out all your records



your favourite record may be a tangle of warps

Your pickup cartridge "sees" such records as twisted, heaving surfaces, jolting up and down 0.5 to 8 times a second. Even records that look flat have warps, and a warped record can change the cartridge-to-record distance, the tracking force, and the vertical tracking angle. Warps produce frequency "wow" and distortion, and can dangerously overload speakers and amplifiers.


What's more, somewhere between 5 and 15 Hz, every pickup arm-cartridge system has a resonance frequency—a frequency at which a warp will produce an exaggerated response that may result in mistracking and in extreme cases, cause serious damage to both the record and stylus.

The Shure V15 Type IV is the first cartridge in the world to incorporate effectively the principles of viscous damping. The Dynamic Stabilizer acts something like a "shock absorber," carrying the cartridge over surface irregularities without distortion, without bottoming out, and without risk of damage to records or stylus. It even protects the stylus should it be dropped accidentally onto the record.

the role of the Dynamic Stabilizer:

The V15 Type IV's Dynamic Stabilizer makes certain you hear the recorded information, not the warps. The viscous-damping system of the Dynamic Stabilizer resists rapid changes in the cartridge-to-record distance. This remarkable Shure innovation eases the stylus over warps without affecting the tracking force on warped or unwarped portions of the record. And the pickup arm-cartridge resonance is attenuated to a subaudible level. As further bonuses, the Dynamic Stabilizer cushions the stylus from accidental impacts, and the carbon fibres in the "brush" conduct static electricity from the record surface to earth!

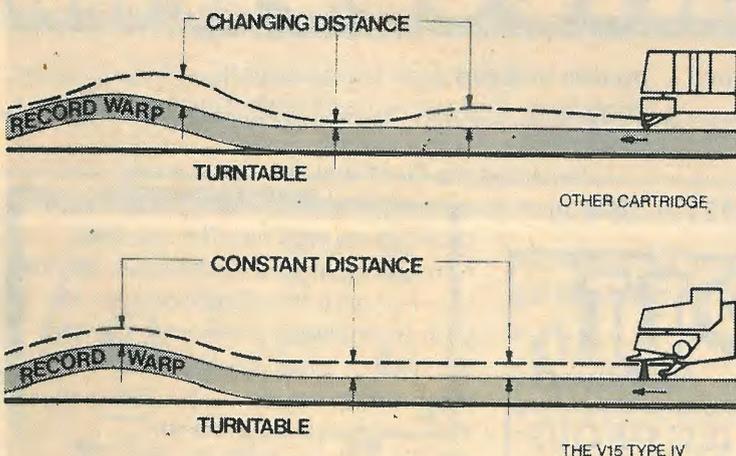For more information write for the V15 Type IV Product Brochure.



V15 Type IV
the viscous-damped cartridge by...



Shure Electronics Limited, Eccleston Road, Maidstone ME15 6AU Telephone: Maidstone (0622) 59881

wireless world

Good, clean fun

Editor:

TOM IVALL, M.I.E.R.E.

Deputy Editor:

 PHILIP DARRINGTON
 Phone 01-261 8435

Technical Editor:

 GEOFFREY SHORTER, B.Sc.
 Phone 01-261 8443

Projects Editor:

 MIKE SAGIN
 Phone: 01-261 8429

News Editor:

 RAY ASHMORE, B.Sc., G8KYY
 Phone 01-261 8043

Communications Editor:

 TED PARRATT, B.A.
 Phone 01-261 8620

Drawing Office Manager:

ROGER GOODMAN

Production & Design:

ALAN KERR

Advertisement Controller:

G. BENTON ROWELL

Advertisement Manager:

 BOB NIBBS
 Phone 01-261 8622

DAVID DISLEY

Phone 01-261 8037

BARRY LEARY

Phone 01-261 8515

Classified Manager:

 BRIAN DURRANT
 Phone 01-261 8508 or 01-261 8423

NEIL McDONNELL

 (Classified Advertisements)
 Phone 01-261 8508

JOHN GIBBON (Make-up and copy)

Phone 01-261 8353

Publishing Director:

GORDON HENDERSON

The Home Office — or, at least, that part of it which is concerned with the regulation of radio transmissions — is evidently one of the more inductive arms of central government and, in its unexplained opposition to any change in the current of public opinion, begins to exhibit slight, but unmistakable evidence of a belief in the philosophy of King Canute, though it is said that even he only sat there on the beach to show how ill-conceived an idea it was to try to curb the tide.

If, by chance, the good king left any family over there in Denmark, let it be known that a further demonstration of the futility of that approach is overdue, the need for it being occasioned by the remarkable blandness of replies to reasoned requests for the right to operate personal radio transceivers on a citizens' band.

It is possible that the unsympathetic response to such demands stems from the unnecessarily righteous arguments put to the government by the supporters of the c.b. lobby. The suspicion lurks that, while the use of such equipment in the USA may have been the means of saving innumerable, isolated old ladies from the attentions of escaped man-eating tigers and while, in the absence of c.b., the roads of the Mid-West would be made all but impassable by the dried-up skeletons of long-distance truck drivers, the real reason for wanting the c.b. facility is that it is quite good fun.

If it is this aspect of the cult that bothers the Home Office, then there is nothing at all for them to worry about. There are several precedents which provide a stable platform for the assertion that entertainment is respectable, even when it relies on the use of natural resources — renewable or not.

Television has effectively commandeered many hundreds of megahertz of the usable spectrum, with sound radio a more moderate but still fairly grasping tenant. Much of the spectrum occupied by broadcasting carries identical pro-

grammes being transmitted to different areas on different frequencies — hardly an economical use of the broadcast bands. But, allowing that this is necessary and pretending that cable transmission has never been thought of, it all becomes well worth while, since every person in the land is provided with first-class entertainment and instruction: a highly respectable endeavour.

Or is it? One evening's examination of the aforementioned entertainment and instruction will rapidly demolish any pretence of an effective use of bandwidth. The content of broadcasts is not normally the province of *Wireless World*, but insofar as the imported trash (and some homegrown material of the same standard) is responsible for the annexation of so much of the available spectrum, and is considered worthwhile by the powers that be, it considerably reduces the impact of any argument based on the premise that c.b. operation is merely entertainment and consequently not to be encouraged.

The supporters of c.b. have their other argument to fall back on when faced with the Home Office's blank and uncomprehending disapproval; one which ought to appeal to bureaucratic self-interest, if nothing else. James Bryant of the CB Association has expressed the view that there will soon be so many illegal, and therefore unlicensed operators working with 27MHz, a.m. sets that a free choice of the specification to be officially adopted will not be possible. Mr Bryant's figures cannot be checked and may seem somewhat excessive, but his argument does possess a certain force, and deserves a more considered reply than has so far been made public.

The official attitude that the need for c.b. has not been demonstrated is not even up to the standard of regulation Civil Service double-talk. Has anyone ever demonstrated the need for 'Sale of the century' or 'Wonderwoman'?

Logarithmic audio sweep generator


Unit for use with an oscilloscope to display l.f. response curves

by A. C. Ainslie

The log sweep generator to be described was developed primarily for the display of overall l.f. response curves on a conventional, d.c.-coupled oscilloscope. Sweeps are calibrated over a 10:1, 100:1 and 1000:1 range, with selectable start frequencies of 10Hz, 20Hz, 100Hz, 200Hz. This enables the "normal" audio band of interest of 20Hz-20kHz to be presented in a single sweep.

Linear sweep facilities enable the graticule divisions on the oscilloscope to indicate frequency directly without a law conversion, while an accurate "log" facility produces sweeps with a linear sweep on the c.r.t. for uniform brightness but with logarithmic frequency conversion.

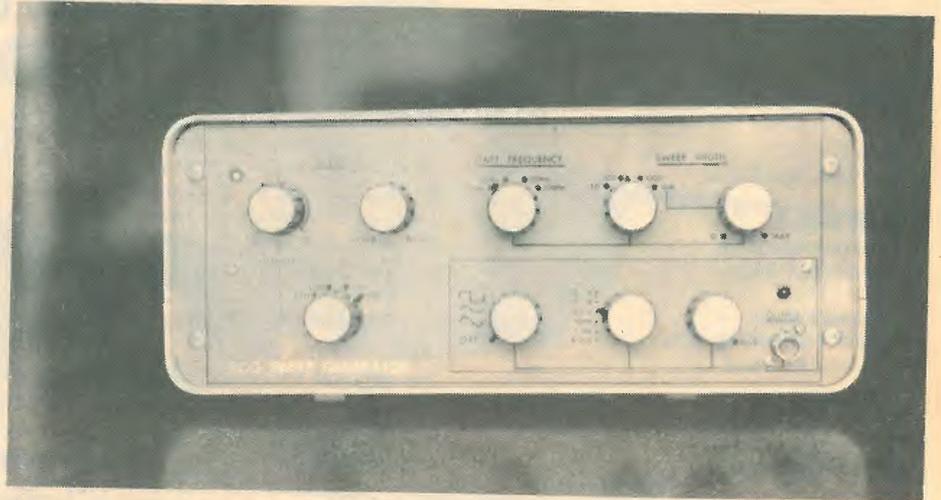Outputs up to 10V p-p are available into 600Ω loads from either sine, square or triangle sources. RIAA equalisation has been provided at a nominal 5mV 1kHz level for display of RIAA equalisation.



voltage-controlled oscillator. Low frequencies are arranged to be on the left hand side of the display, providing the c.r.o. conforms to the convention of an increasing positive voltage moving to the spot to the right.

An integrated logarithmic amplifier converts the linear sweep to a log. v.c.o. control voltage so that the rate of increase of frequency increases with frequency, enabling responses to be displayed conforming to the more common form of presentation.

Amplification of the v.c.o. output is necessary to drive loads as low as 600- with 10V p-p level. Clearly the output

amplifier must be flat. A consequence of the v.c.o. used is that square and triangle waves are available simultaneously with the sine wave which is used for response sweeping. Selection is provided to enable these outputs to be used, giving a swept function-generator facility.

Y deflection of the oscilloscope is from the output of the device under test. The result of a sweep will be to display an envelope on the screen, the top of which is representative of the response of the device under test. Normally the lower half of the display would be lowered below the lower datum of the graticule to give a less confusing display. Several refinements to the display of the envelope will be discussed later on as an aside.

Sweep generator

The v.c.o. used in this design has a linear relationship between control voltage and frequency. The requirement for the sweep generator is, therefore, a simple linear ramp with variable repetition rate and the possibility of manual setting to any point in the sweep to enable frequency to be manually set. In Fig. 2, an astable 555 timer is used with a constant current source, Tr_1 , to produce a linear sweep from the charging of C_1 . The 555 is used between +15V and earth with the internal comparator levels, resulting in a sweep from +5V to +10V. The charging current for C_1 and hence the sweep repetition frequency is

THE SIMPLIFIED block diagram of the unit in Fig. 1 shows the connexions to an oscilloscope and to the unit under test. Additionally, retrace blanking is provided to the c.r.o.

The ramp generator drives the X amplifier of the c.r.o., while simultaneously varying the frequency of the

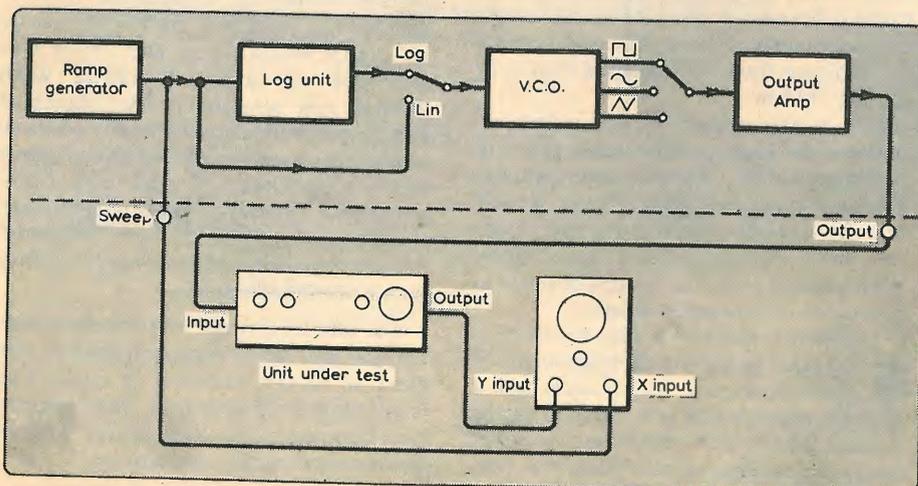


Fig. 1. Basic principle of swept-frequency investigation.

controlled by R_2 , a panel control labeled 'SWEEP'.

Switch S_{1a} selects either the automatic sweep or a manual tuning voltage from R_9 , 'MANUAL,' to be passed to various level shifters by follower, IC_2 . The combination of R_{12} and C_4 removes high frequency jitter on the ramp from the 555. Amplifier IC_5 converts the ramp from S_{1a} to a 10V excursion, centred around 0V, to drive the oscilloscope at 1V/division maximum. Level shifter IC_3 drives the log. conversion circuit, which requires the ramp to be presented inverted, running from about 2.5V to just above earth. A linear, inverted ramp is also obtained from IC_4 , sweeping from earth to -5V. The h.f. end of the ramp is set by R_{21} . Potentiometers R_{17} and R_{23} set the working levels of the two translators, establishing the h.f. end of the log. sweep and the l.f. point of the linear sweep.

Oscilloscope trace bright-up must be provided under control of the sweeper.

Pin 3 of the 555 rises to +15V during the sweep, falling to 0V during retrace. This signal is used to turn on Tr_2 during sweep; in the retrace period Tr_2 is off and 'B.U. output' rises to +20V, cutting off the oscilloscope. The R_6/C_3 combination prevents ripples getting onto the 20V line, passing through the 15V regulator and giving problems.

The convention used above, in which positive-going voltages reduce beam intensity, seems to be a fairly common requirement for most modern oscilloscopes: it is an easy matter to introduce an inverter should the need arise. If a greater bright-up voltage than 20V is needed, it would probably be better to build a high-voltage amplifier into the mainframe, using its internal


supplies and driving the amplifier with the bright-up output of the sweeper.

To produce a logarithmic change in frequency when displayed on a linear trace, an antilogarithmic distortion of the linear ramp is needed, which is provided in this case by an Intersil 8049, the principle being shown in Fig. 3.

The 8049 was used in this design because various discrete "textbook" designs proved too fussy in respect of temperature control or compensation over the requisite 10^3 range. This package is surprisingly inexpensive for its degree of precision and it is certainly simple to use. Setting up, once complete, is very stable.

The input presented to IC_6 is a ramp falling from 2.5V to about 0V, which must be turned into a 10^3 sweep voltage range. With a supply of 15V on the 8049, a maximum output of 10V seems reasonable, making the l.f. end of the sweep output 10mV. The scale factor of the device is approximately 1V per decade of output, actually trimmed during

Fig. 2. Ramp generator, logarithmic amplifier and sweep-width control. Letter code on connexions refers to author's p.c.b. layout. This may be made available if there is a demand.

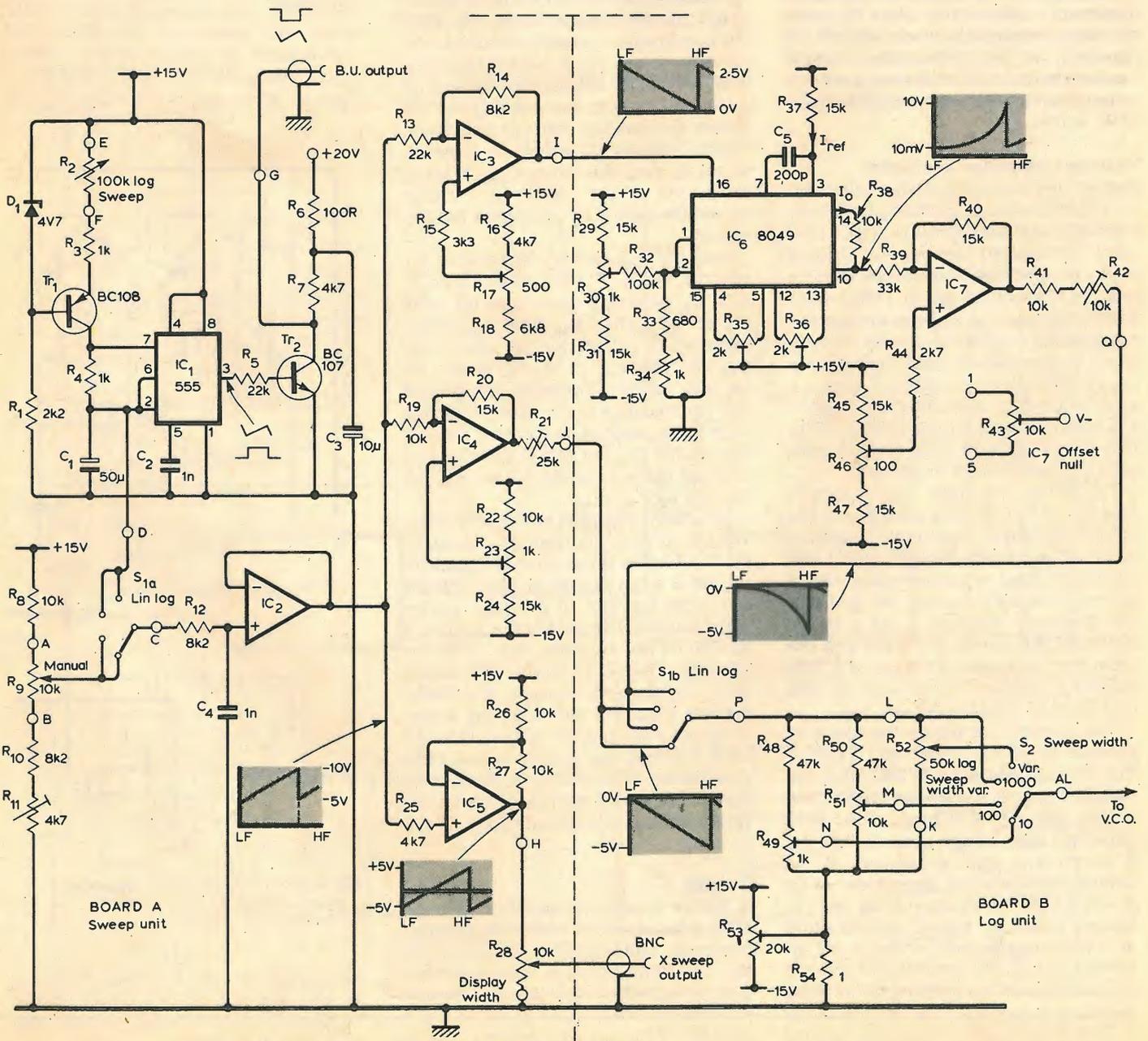

calibration to be less than this, and producing a 10^3 output range from the 2-5V input range. The 1mA reference current for the device is produced by R_{37} from the +15V rail.

The output from the package is obtained from one end of R_{38} — the external feedback resistor for the second internal op. amp. IC_7 is a level translator and inverter, putting the sweep into a 5V range, negative going, starting at 0V as is the case with the output of IC_4 , the LIN sweep. R_{46} trims the l.f. end of the log. sweep with R_{42} setting the h.f. end to be in line with that set by R_{21} .

Sweep width. Both lin. and log. sweeps as selected by S_{1b} are negative-going from 0V over a 5V range. The sweep width selector, S_2 , is connected to attenuators R_{48}/R_{49} , R_{50}/R_{51} and R_{52} to give control of the total sweep range, reducing the sweep to -50mV in the first instance for a 10:1 sweep and -500mV in the second for a 100:1 sweep. The variable sweep with control, R_{52} , gives continuous control up to a ratio of 1000:1; it is a log. component for maximum controllability. With R_{52} at its minimum setting, the v.c.o. should be running at its minimum sweep frequency. To trim this accurately, a pedestal voltage is applied to the bottom of R_{52} across R_{54} .

Voltage controlled oscillator

Rather than attempt to design a discrete v.c.o. (which would probably take the form of controlled astable with sine-wave conversion) the popular Intersil 8038 v.c.o. package was chosen for this unit. It is specified up to 1MHz with 1000.1 sweep and so appears to meet the requirements. However, even Intersil admit that operation with 1000.1 sweep range is full of problems and an application note breadboard certainly will not meet the intended specification. It is worth taking a little time to consider the operation of the device.

The 8038 contains two current sources, one producing a current I , the other, a current $2I$. The timing capacitor on pin 10 is initially charged with I and then discharged at a threshold by the $2I$ generator being switched on, giving a net discharge current, I . At a lower threshold the process reverses and the capacitor once again charges at I . The resulting symmetrical triangle is sine converted to yield the output.

The current I is set by the value of external resistors connected to pins 4 (for the constant source) and 5 for the switched source. Figure 4(a) shows the current generators internal to the 8038 which are also voltage controlled by pin 8, common to both generators. If the control voltage is $-V$, the emitter of Q_1 is $-(V + V_{be})$, the emitter of Q_2 and Q_3 , being a single V_{be} higher, are therefore at $-V$. Unfortunately, there is no inherent feedback over this current-control mechanism internal to the 8038, resulting in unpredictable compression at low frequencies when the control

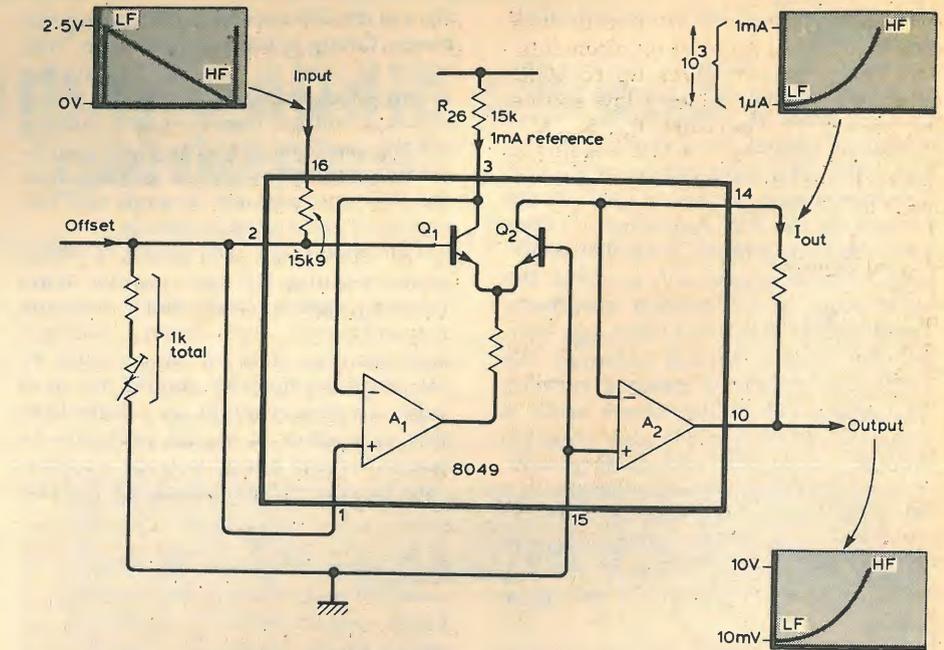


Fig. 3. Principle of Intersil antilog amplifier.

voltage is approaching the 0V rail.

By adding an op.-amp. round the internal current source; as in Fig. 4(b), this non-linearity is easily removed. The op.-amp. drives pin 8, taking feedback from pin 4, and forcing the voltage on pin 4, and current through R_{59} etc., to follow the control voltage precisely. Figure 5 shows D_2 which, in practice, serves to stop the control pin 8 being forced out of the linear v.c.o. range should the device be overswept for any reason.

Each of the four start frequencies are selected by S_3 , START FREQUENCY, with S_{3a} selecting capacitors for each range. Switches S_{3b} and S_{3c} select appropriate calibration presets, enabling the symmetry to be individually set on each range. Symmetry can be lost due to unbalance of the current sources at low frequencies as control voltage approaches 0V, but this is corrected by drawing current on pin 5 with R_{67} , adjustable by R_{68} .

Internally, the 8038 buffers capacitor voltage to give the triangle output on pin 3, while an uncommitted transistor on pin 9 is switched by the charge/discharge flip-flop to give the square wave output. The sine wave output is produced by feeding the buffered triangle through an active attenuator with increasing attenuation as the level departs from the mean, giving a surprisingly pure output of less than 1% t.h.d. A preset, R_{72} , is used to make this non-linear attenuation symmetrical about the mean, giving symmetrical positive and negative half cycles.

Output

A simple push-pull amplifier delivers 10Vp-p into loads of 600Ω with minimal distortion and excellent flatness over the frequency range. The function switch, S_4 , selects the appropriate output from the 8038, centred about a d.c. level of -7.5V, via appropriate resistors

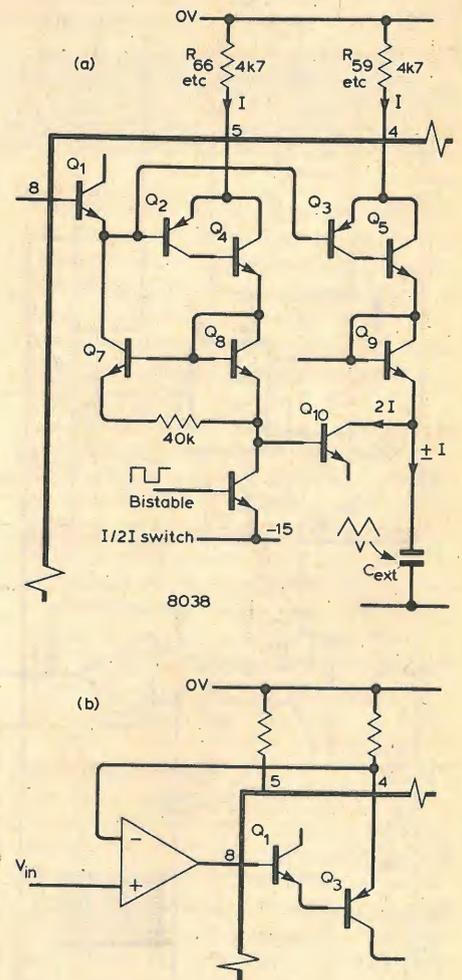


Fig. 4. Use of op.-amp. to linearize output of 8038 v.c.o.

to equalize the gain. Feedback from R_{110} is also applied at the input of the amplifier. R_{82} serves to correct any zero effect that may occur.

Attenuator. A simple attenuator was judged to suffice for most requirements. The design shown gives up to 60dB attenuation and provides a low source impedance. The network R_{91} , R_{92} , C_{12} , C_{13} and R_{98} compose a RIAA weighting network, which enables checks to be made on pickup equalizers, etc.

Power supply

The instrument requires $\pm 15V$ at around 125mA. Monolithic fixed voltage regulators are suitable, but the design shown uses two 723 packaged regulators with external pass transistors and with R_{101} and R_{107} setting the positive and negative rails respectively. A +20V supply is also provided for the b.u. amplifier. Clearly, any regulated power supply can be used but, since the calibration is very dependent on the supply rails, good long term stability is important. Hindsight makes the author favour monolithic regulators.

Construction

The prototype was built in a West Hyde 'Contil' case, approximately 10.5in \times 4.5in panel size. Doubtless, the more patient could build the design on Veroboard — there is nothing especially critical — but p.c.bs are to be recom-

mended. Five small boards were used in the prototype, as follows:

- Board A sweep 4.5 \times 3.5in
- Board B log. 5 \times 2.5in
- Board C v.c.o. 3.75 \times 2.5in
- Board D output amp. 4 \times 2in
- Board E p.s.u. 3.5 \times 3.25in

Care should be taken to avoid earth loops, which would give spurious output and affect v.c.o. control. A layout problem can occur with the edge of the squarewave breaking through to SINE or TRIANGLE and producing a small pip at top and bottom. Should this occur in individual instruments the easiest cure is to use a spare pair of contacts on S_4 to connect 100nF between the square signal lead at this switch to ground on all but the SQUARE setting of the switch.

It is recommended that all presets be cermet and resistors 5 per cent film types, 1/3W being adequate. However, in view of the extended l.f. range of a log. sweep, an error of perhaps only a fraction of a per cent of full sweep is shown as a considerable portion of the

X axis. To avoid errors here, it is essential to ensure low drift in IC_7 . Good quality resistors must be used, preferably the metal-film type for R_{45} and R_{47} . The preset R_{46} was a miniature 15-turn type in the prototype, stuck behind a small hole in the panel with Araldite. It is simple to set the low-frequency end of the sweep to the correct frequency with this preset, should the calibration drift.


Setting up

There are many preset adjustments in the instrument and the use of a digital voltmeter is a good idea during the setting-up procedure. Providing good-quality components are used, subsequent calibration should only rarely be needed, and any single adjustment can often be carried out on a working instrument without test equipment.

1. Set R_{53} particularly and all other presets midway. Switch on and set R_{101} to give +15V on the positive rail. R_{107} sets the -15V rail.

2. Switch S_1 to AUTO LIN sweep. Verify that IC_2 gives the waveform shown in Fig. 2 at its output. Leaving the oscilloscope connected, switch to MANUAL LIN. Adjust the manual frequency control, R_9 , anticlockwise and set R_{11} to give 5V at IC_2 output.

Fig. 5. Voltage-controlled oscillator and output circuitry.

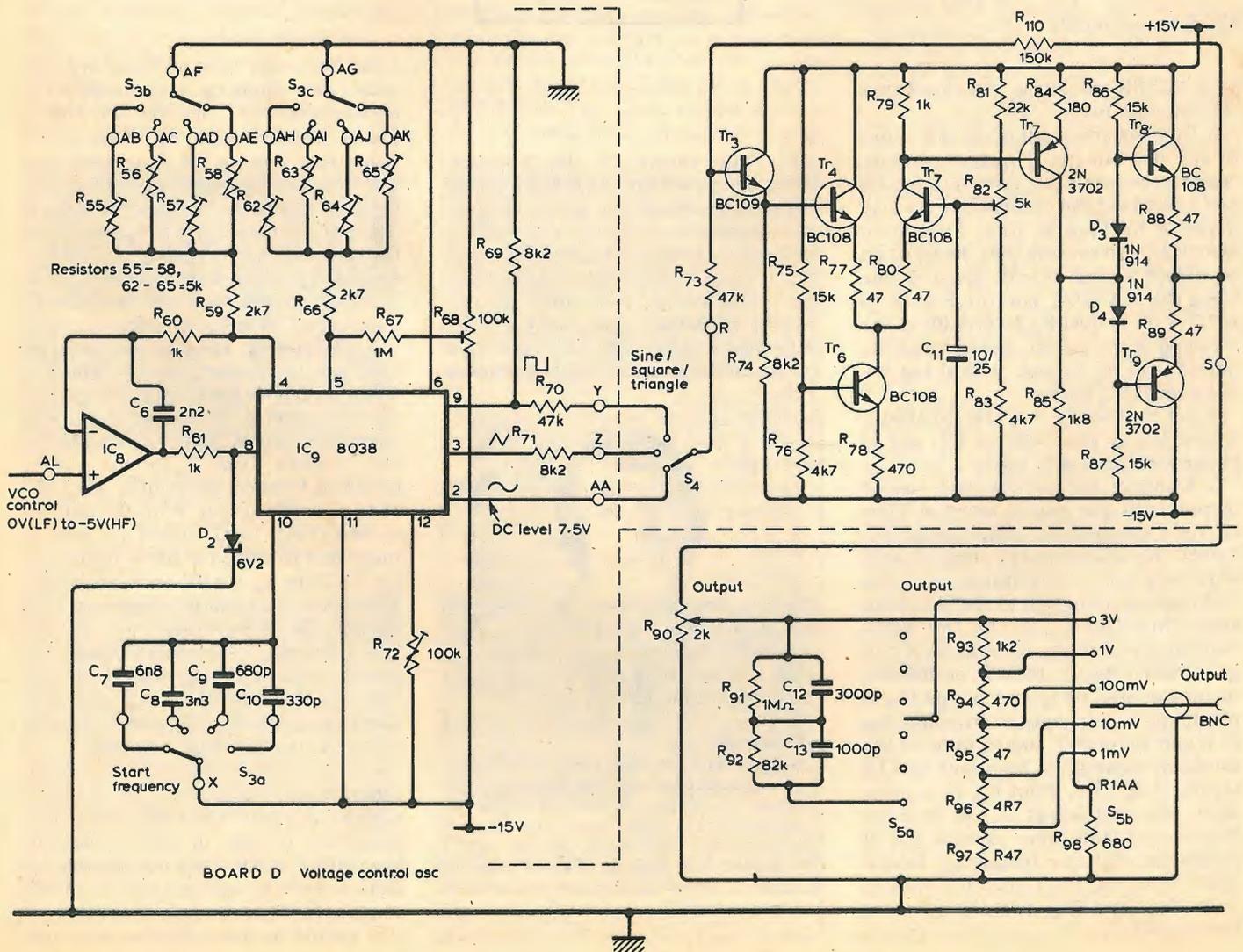

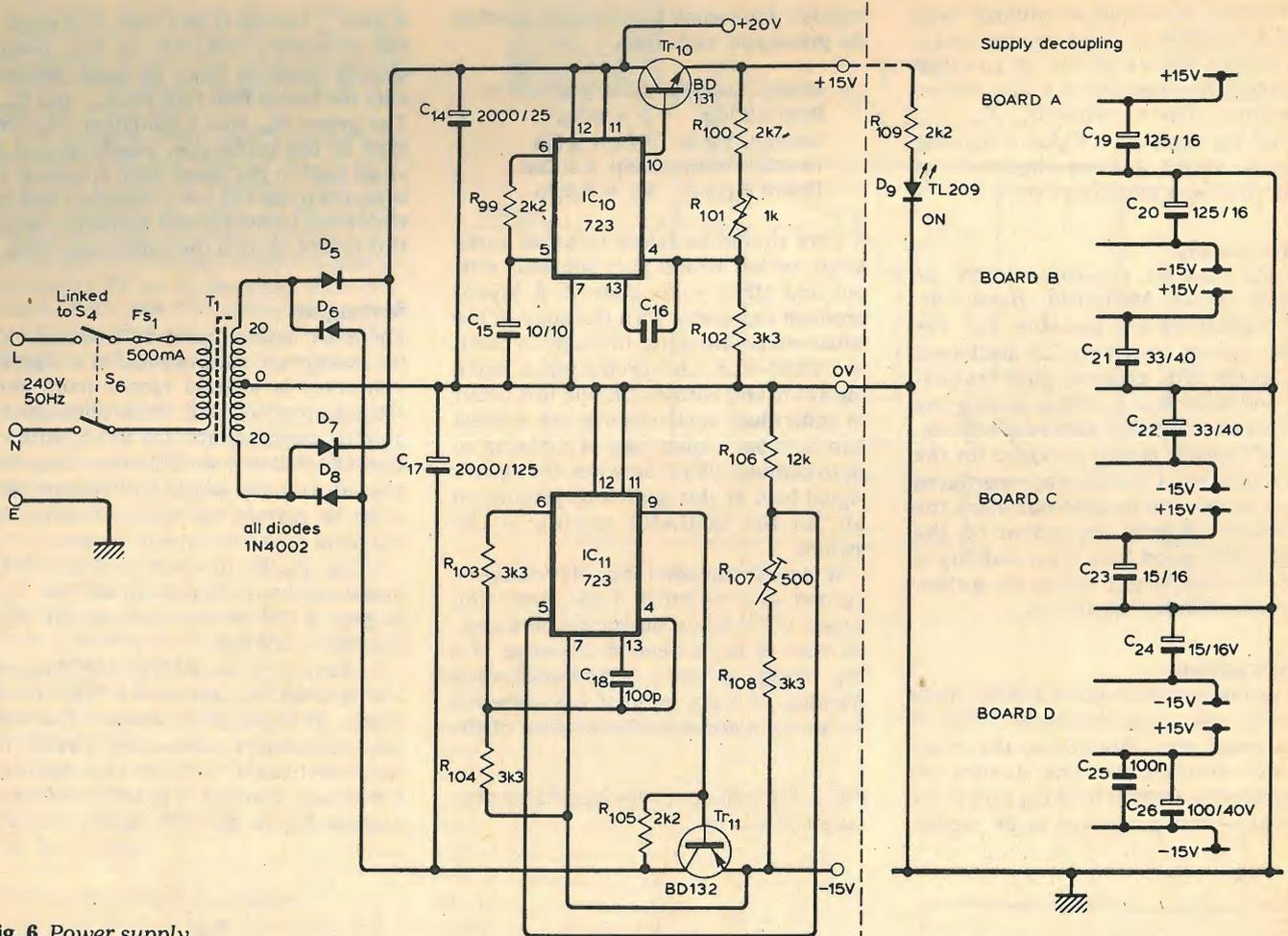


Fig. 6. Power supply.

Turn R_9 fully clockwise and check that IC_2 output is 10V.

3. Connect the oscilloscope's X input to the instrument X output socket, connect the bright-up, switch to AUTO LIN and adjust the oscilloscope for a 10 division horizontal line. Switch to MANUAL and confirm that the spot can be placed within the 10 division line using the MANUAL control. Switch to AUTO LIN. Adjust R_{23} to give 0V at the zero end of the sweep, measured at IC_4 output, and R_{17} to give zero at the h.f. end seen at IC_3 output.

4. Set S_2 , SWEEP WIDTH, to 1000:1. Adjust R_{21} to give -5V at h.f. end of sweep measured at S_2 wiper.

5. Connect the oscilloscope to the output, with sine output selected. Trim R_{82} for a symmetrical output about 0V. Select the square-wave output and, with R_{52} set a maximum, and the oscilloscope connected to the X output, select MANUAL LIN. At the high-frequency end of the ranges, set R_{21} to give 10kHz, 20kHz, 100kHz or 200kHz. At the low-frequency end, adjust R_{23} to obtain the correct output, trimming R_{68} to retain symmetry and to prevent the oscillator locking up. Approach this l.f. setting with care. Trim R_{52} to a minimum now and adjust R_{53} so that the frequency is the same as with R_{52} at maximum. Set the frequency to h.f. again, selecting 100.1 and 10.1 sweeps. Trim R_{51} and R_{49} for the correct frequencies.

6. Each range of the voltage-controlled oscillator has presets for the charging current.

10Hz	R_{55} and R_{62}
20Hz	R_{56} and R_{63}
100Hz	R_{57} and R_{64}
200Hz	R_{58} and R_{65}

Whichever range has been used for calibration this far is finally trimmed at



The author

Alan Ainslie studied electronic engineering at Sheffield Polytechnic and Brunel University, before forming an electronic design consultancy in the fields of audio and instrumentation. He has published over thirty articles and is engaged in writing two books on computer programming.

a mid frequency to be perfectly symmetrical (view single cycle of square wave on oscilloscope). Then the h.f. end is finally trimmed with R_{21} . Each other range now has its h.f. frequency and symmetry set by adjusting the relevant presets together. Finally R_{68} (low frequency symmetry) is checked. R_{72} is trimmed for best wave shape (+ and - symmetry) on pin 2 of the 8038. Repeat 3, 4 and 5, paying particular attention to accuracy of low frequencies.

7. The antilog. amplifier can now be trimmed. Disconnect pin 16 from IC_3 output. Connect pin 16 to +15V. Adjust R_{36} for exactly 0V out (use d.u.m.). Disconnect pin 16 from +15V and connect to earth. Trim R_{30} for 10V output on pin 10. Connect the antilog. amp. pin 16 back to IC_3 output. With the unit set to MANUAL LOG, select l.f. end of range and trim R_{34} for 10mV output on pin 10. Trim R_{46} for 0V on wiper of S_{1b} . Then select h.f. end of range and trim R_{42} for -5V on S_{1b} wiper.

8. Recheck 7. On MANUAL LOG check frequency of output at l.f. and trim R_{46} again so that LOG. and LIN. operation coincides. Similarly trim R_{42} so that h.f. end of range coincides.

Operation

Operation is quite self-explanatory. It is important to bear in mind, however, that high-Q circuits are not suitable for swift sweeps. It is always easy to switch to manual sweep to verify a display.

It should be quite obvious that only


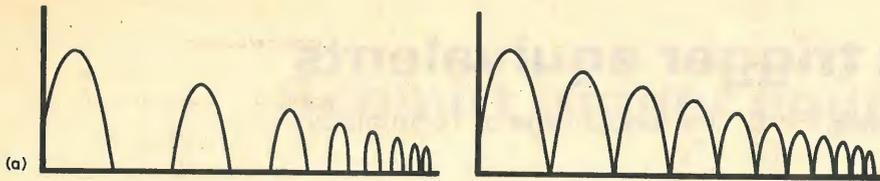
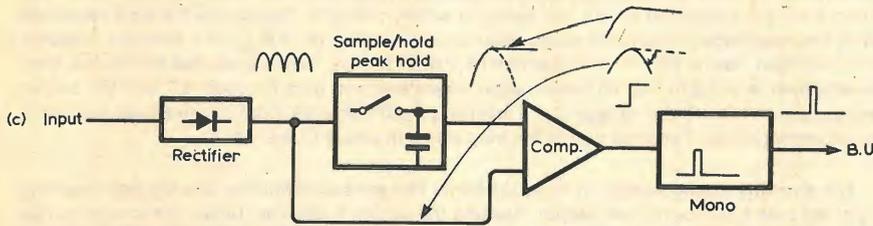


Fig. 7. Full-wave rectifier improves appearance and resolution at l.f. end of sweep, as at (a). Display at (b) shows trace obtained when bright-up is at peaks of response only, dots being extended to a continuous line by sample/hold arrangement of (c).

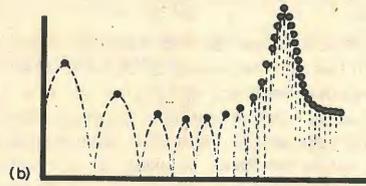

the sine wave output is suitable for sweeping to display a frequency response. It is important if sweeping a highly-sensitive filter, for example, to remember that the t.h.d. is worse than 0.1% (60dB down). This can lead to false rejection figures if a wide dynamic range, in the order of 60dB, is used in the display. Normally, however, the output signal purity is more than adequate.

Display

The simplest display technique is to use the top of the envelope displayed on the

oscilloscope as the frequency response plot. Photographic records can be particularly satisfactory if the exposure covers several sweeps, since the sweep and v.c.o. are not synchronous. However, there are several options open to improve the display which will be discussed below.

Precision full wave rectifier. This effectively doubles the number of points on the display, and improves resolution dramatically at the l.f. end of the display as seen in Fig. 7(a). However, the circuitry used has to accommodate the

dynamic range of the output of the unit under test and have a flat frequency response over the bandwidth in question: simple op.-amp. full-wave rectifiers run into the usual slew rate problems at higher frequencies.

Bright up at signal peaks. By generating the bright up from the output of the device under test, so that for each peak the c.r.o. is under bright up for a small period of time, the display is comprised of a series of dots representing the response curve. As above, a full-wave rectifier doubles the resolution of the display. The result is as in Fig. 7(b).

Unfortunately, due to unpredictable phase shifts through the unit under test, which will probably vary with frequency, it is not possible to generate bright up from the sweeper, only the output of the unit under test as in Fig. 7(c). It is possible, using this technique, to display phase on the c.r.o. by using a constant-phase bright up.

Sample hold. By using a sample-hold to retain peak value, modifying this level with each subsequent cycle, the c.r.o. can be made to display a continuous envelope of response. This is possibly the most attractive display method but has the dynamic range and speed problems mentioned earlier.

Phase-locked loop. A phase-locked loop can be used to cause an oscillator to track the output of the unit under test and may be then used to bright up peaks. An 8038 is suitable for this task with a phase comparator, since the squarewave phase is suitable for generating the bright up without modification, or driving a sample/hold.

An interesting aspect of this technique is that it is possible to record the sweep on tape for example and play back after a delay to drive the scope display.

Log. amplitude display. Audio responses are usually displayed with a logarithmic vertical scale. This can be easily arranged with the Intersil 8048 log. amplifier package. a 10^3 range is easily accommodated with no requirements for temperature compensation.

It is obvious from the above discussion that many possibilities exist for an additional unit to assist the display of the information. A possibility not mentioned above, but probably the most useful of all, would be a form of display storage for the slow sweeps. It is the author's intention to complete development of a complementary display and storage unit which will possibly be described at a later date. □

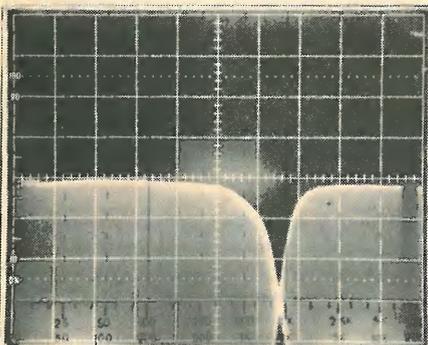


Fig. 8. Swept display of a t.h.d. meter, set to 1kHz. In the final stages of calibration, an accurately-calibrated notch filter is useful for setting the scale factors.

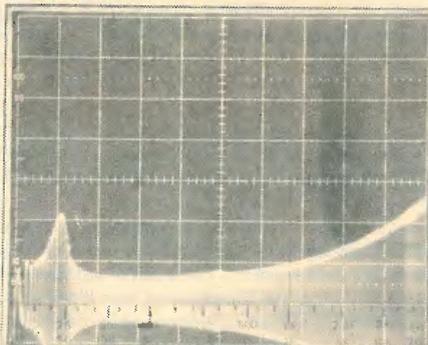


Fig. 10. Impedance sweep of 8in bass driver in free space. Resonance is at 50Hz.

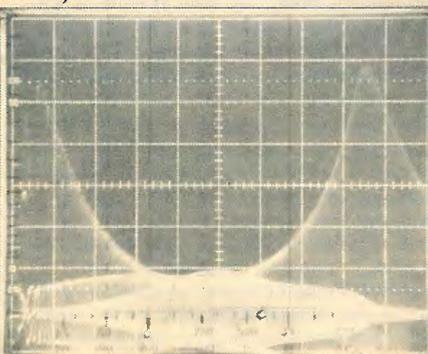


Fig. 9. Tone control and filter responses of an audio amplifier.


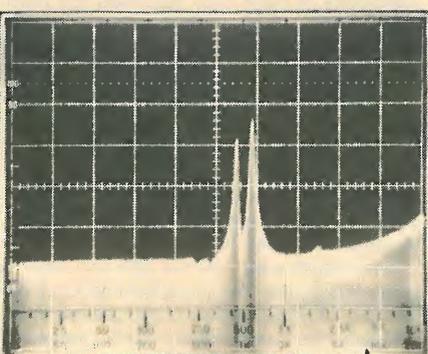
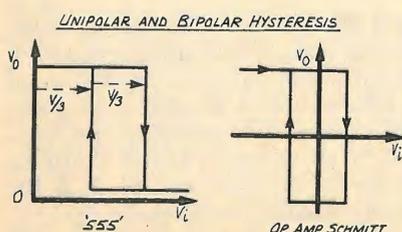
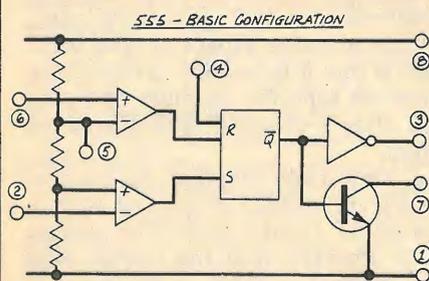
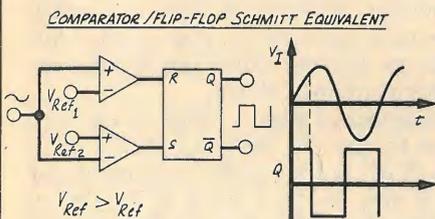
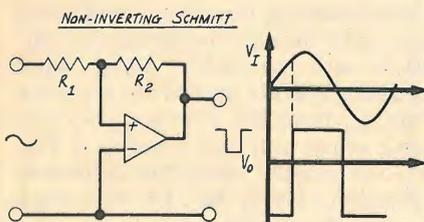


Fig. 11. Impedance sweep of small treble unit.

Schmitt trigger equivalents

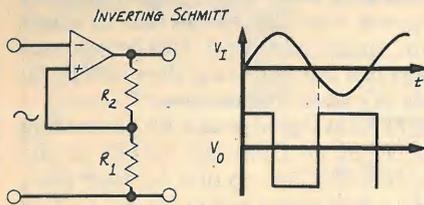by Peter Williams, Ph.D., Paisley College of Technology



The operational amplifier is used in linear circuits because of the precision with which it allows functions to be provided. It has a limited speed of response when internally compensated to ensure stability under all negative feedback conditions up to and including 100%. This constraint can be removed when using positive feedback to switch it through the linear region in the shortest possible time. Even simple amplifiers in their uncompensated state can have slow rates in excess of $10\text{V}/\mu\text{s}$. If series feedback is used, as is needed for maximum input resistance, then the input signal is taken to the inverting input i.e. the amplifier connections are the reverse of those for a series negative-feedback amplifier. With recent amplifiers having c.m.o.s. output stages the output can swing to within millivolts. Failing this the time switching levels become proportional to the output saturated levels $[R_1 / (R_1 + R_2)](\pm V)$. With the output at $+V_O$ the input has no effect if it is less than $[R_1 / (R_1 + R_2)]V_O$. When it reaches this critical level the amplifier is brought into its linear range where the loop gain exceeds $+1$ and the output swings negative (since the voltage at the inverting input becomes more positive than that at the non-inverting input). For large inputs the output is anti-phase to the input.

The alternate configuration, in form similar to the see-saw amplifier, has the non-inverting input fed from both source and output. Assume the output is positive; unless the source swings sufficiently negative the output remains in this saturated state. When the threshold is reached the non-inverting input becomes more negative than the inverting input, the output swings negative and regenerative switching ensues, forcing the output to its most negative value. The source has no further influence until it becomes sufficiently positive to overcome the negative contribution of the output. The threshold levels are obtained by applying superposition to determine when the non-inverting input is driven through zero. This gives threshold levels $(-R/R_2)(\pm V_O)$. Again for stability of switching levels the output swing must be well-defined: if this is not inherent in the amplifier output stage as is the c.m.o.s. types then breakdown diode or other clamping methods can be applied. In this circuit the current drawn from the source is significant and in particular experiences a sharp step as the output switches. This makes the inverting form more widely useful.

The same function can be performed by the Schmitt trigger and an appropriate combination of comparators and a set-reset flip-flop. Other advantages need to be established in return for the apparent increase in complexity; the word apparent is included because the number of elements in a complete i.c. using this method is surprisingly small. Each comparator contains far fewer components than an op. amp. as the output it has to provide is both smaller and better defined — just sufficient current to set or reset a simple flip-flop. The last-mentioned needs to be reasonably fast but has a defined input and is buffered by an output stage so that it has few components. Thus for comparable performance to the Schmitt trigger based on an op.amp., this form can be simpler. Compared with a single high-speed comparator used with positive feedback it is slower, but much more flexible in that the thresholds can be precisely set and controlled. When the input goes more positive than V_{REF1} , the output of the comparator 1 resets the Q output to logic 0. It remains in this condition until the input swings more negative than V_{REF2} when the second comparator sets the Q output to logic 1.

The first commercial i.c. embodying these ideas has since become the industrial standard. Designed by Signetics for mass production it is arguably the first universal successor to the operational amplifier — a circuit of sufficient flexibility to permit a very wide range of functions. In addition to the comparators and flip-flop it contains an inverting output stage which is t.t.l. compatible and an additional open-collector output. The inversion leads to the use of the Q connection of the flip-flop to retain the same overall phasing. By connecting the comparator inputs to tapings on a chain of equal resistors the reference levels are set at $V_S/3$ and $2V_S/3$ respectively. The top comparator input is brought out to a separate pin 5 for decoupling against transients on the supply for changing the threshold levels while retaining a 2:1 ratio, or for modulating the switching points. Another re-set terminal to the flip-flop 4 allows its timing cycle to be over-ridden, as for example when synchronizing to a higher-frequency source. The availability of these extra terminals has inspired a continuing stream of novel designs. It is a challenge to the ingenuity of designers, while because of its low cost it has to be considered for even the simplest of monostable and astable functions.

The similarity between the operational amplifier and comparator / flip-flop forms is sometimes obscured by the different voltage levels. The op-amp. normally functions from dual polarity supplies, while the 555 and similar circuits are designed for single-supply operation (for compatibility with logic circuits and battery powered systems where two batteries are inconvenient). The difference is illustrated by considering the hysteresis of each circuit. The graph of output against input is traced out as the input first increases through the upper threshold and then back through the lower threshold. The output takes up only one of two values in each case. For the 555 the lower value is close to zero and the upper is around 1V below the supply. The transitions occur as the input passes through the positive voltages $V_S/3$ and $2V_S/3$, independent of the precise output levels. If the op.amp. is adjusted for the same hysteresis the thresholds are spaced equally on either side of zero (assuming the output positive and negative saturation levels are equal).

Schmitt trigger equivalents

THEORY

● Let the saturated output voltages be V_A, V_B where $V_A > V_B$ and where $V_A \rightarrow +V_S, V_B \rightarrow -V_S$ for standard op-amps. The two values of voltage at the non-inverting inputs are thus

$$V_1 = \frac{V_A R_1}{R_1 + R_2} \text{ and } V_2 = \frac{V_B R_1}{R_1 + R_2}$$

These define the corresponding levels on the input wave at which the amplifier is driven into its linear region, raising the loop gain and initiating the switching action.

Typically

$$V_1 \approx \frac{R_1}{R_1 + R_2} \cdot (+13)$$

$$V_2 \approx \frac{R_1}{R_1 + R_2} \cdot (-13)$$

for a typical op.amp. operating from $\pm 15V$ supplies.

Certain comparators operating from a single-ended supply of say $+10V$ and have outputs capable of swinging between 0 and $+10V$, i.e. the thresholds are

$$V_1 = \frac{R_1}{R_1 + R_2} \cdot 10$$

$$V_2 = 0$$

In all cases

$$V_1 - V_2 = \frac{R_1}{R_1 + R_2} (V_A - V_B)$$

where $V_1 - V_2 = \Delta V_{in}$ referred to as the hysteresis is a defined fraction of the change in output.

$$\text{i.e. } \Delta V_{in} = \frac{R_1}{R_1 + R_2} \Delta V_{out}$$

● For the non-inverting Schmitt the thresholds again correspond to the points at which the amplifier is driven into its linear region i.e. when

$$\frac{V_1}{R_1} + \frac{V_B}{R_2} = 0$$

$$V_1 = -\frac{R_1}{R_2} V_B$$

$$V_2 = -\frac{R_1}{R_2} V_A$$

$$\Delta V_{in} = V_1 - V_2 = \frac{R_1}{R_2} (V_A - V_B)$$

Note that the input thresholds are of opposite polarity to the output voltage.

● The thresholds for the comparator/flip-flop combination are defined by a pair of independent threshold voltages

$$\text{i.e. } \Delta V = V_1 - V_2 = V_{Ref 1} - V_{Ref 2}$$

In certain cases it is convenient to apply the signal to one or both of the inputs via potentiometers so that $V_1 = k_1 V_{ref 1}, V_2 = k_2 V_{ref 2}$ of the signal transmitted by the potentiometers. This allows independent control of the hysteresis for fixed values of $V_{Ref 1}, V_{Ref 2}$.

● For this i.c. the reference levels are defined by a potential divider composed of three equal resistors, and the circuit normally operates from a single supply $+V_S$.

$$\therefore V_{Ref 1} = \frac{2V_S}{3}$$

$$V_{Ref 2} = V_S/3$$

$$\text{The hysteresis } \Delta V = V_S/3$$

Each of these terms is independent of any imperfections on the output stage that prevent the output swinging between 0 and $+V_S$.

EXAMPLES

1. A comparator has saturated output voltages V_A and V_B of $+12$ and $-11V$. For $R_2 = 20R_1$, in an inverting Schmitt determine the switching thresholds V_1 and V_2 and the hysteresis $V_1 - V_2$.

$$V_1 = \frac{R_1}{R_1 + R_2} \cdot 12$$

$$= \frac{1}{20+1} \cdot 12 = \frac{12}{21} = 0.57V$$

$$V_2 = \frac{R_1}{R_1 + R_2} \cdot (-11) = -0.52V$$

$$V_1 - V_2 = \frac{12 - (-11)}{21} = \frac{23}{21} = 1.09V$$

2. Find the corresponding figures for the non-inverting Schmitt.

$$V_1 = \frac{-R_1}{R_2} \cdot (-11)$$

$$= \frac{11}{20} = 0.55V$$

$$V_2 = -\frac{R_1}{R_2} \cdot 12 = -\frac{12}{20} = -0.6V$$

$$V_1 - V_2 = 1.11V$$

3. With the component values of Ex. 1 determine the phase angles at which switching occurs for an input sinusoidal wave of $1V$ r.m.s.

$$V_1 = \sqrt{2} \sin \theta$$

\therefore switching takes place at V_1, V_2 where


$$V_1 = 0.57 = \sqrt{2} \cdot \sin \theta$$

$$\therefore \sin \theta_1 = \frac{0.57}{\sqrt{2}}$$

$$\therefore \theta_1 = 23.8^\circ$$

$$\text{similarly } \sin \theta_2 = \frac{-0.52}{\sqrt{2}}$$

$$\theta_2 = 191.6^\circ$$

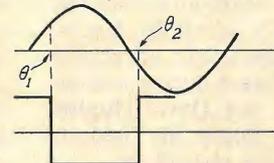

4. A comparator/flip-flop combination has switching thresholds defined by a potential divider of three equal resistors placed across the supply lines of 0 and $+10V$. The input waveform is sinusoidal and initiates the switching action at phase angles of 30° and 240° . Find the mean and peak-peak values of the waveform.

Let the input be $V_m + V \sin$

$$\text{The switch thresholds are } V_1 = \frac{2}{3}V$$

$$\text{and } V_2 = \frac{1}{3}V$$

because of the given resistor values.

$$\therefore V_{av} + V \sin \theta_1 = \frac{2V}{3}$$

$$V_{av} + V \sin 30 = \frac{20}{3}$$

$$\text{Similarly } V_{av} + V \sin 240 = \frac{10}{3}$$

Subtracting, $V (\sin 30 - \sin 240) = 10/3$

$$V = \frac{10}{3 \left(\frac{1}{2} + \frac{\sqrt{3}}{2} \right)} = 3.85V$$

\therefore Peak-to-peak value of sine wave = $7.7V$

$$V_{av} + 7.7 \sin 30 = 20/3$$

$$V_{av} = 6.67 - 3.85 = 2.82V$$

$$\text{Mean value of input} = 2.82V$$

Century of amateur radio?


Few people think of 1979 as the centenary of amateur radio, yet a good case could be advanced in support of the view (put forward in the late John Clarricoats, G6CL "World at their fingertips") that "Britain's first radio amateur" was London-born, American-educated David E. Hughes, one-time professor of music but also a noted inventor of microphones and mechanical telegraphy systems. In 1879 Hughes could have been found walking up and down Great Portland Street, London listening on a telephone ear-piece and a detector consisting of a steel needle in loose contact with a piece of coke to clockwork-interrupted signals from a transmitter some 500 yards away. His experiments were virtually a discovery of Hertzian waves before Hertz, of the coherer before Branley and of wireless telegraphy before Marconi, as the *Globe* newspaper was later to record.

Hughes was convinced that his signalling was due to "aerial electric waves" but he was profoundly discouraged by an inability to convince well-known scientists, claiming in February 1890 that his experiments were "pooh-poohed" in an "unpleasant discussion" which ended with the scientists departing "very coldly." Even earlier than Hughes had been the efforts of an American dentist Dr Mahlon Loomis who in 1865 claimed to have spanned a distance of 18 miles using a kite "aerial" (it was Loomis who first named the aerial). It was left to Marconi to turn the whole host of early work by Hertz, Lodge and many others, into a practical communications system during the decade 1894 to 1904. But David Hughes came very close to this in his "pedestrian mobile" operation in 1879-80.

Polar-loop ssb transmitters

At a 21st anniversary symposium organized by South Midlands Communications Ltd, V. Petrovic of the University of Bath suggested that radio amateurs could benefit from the recent development of the v.m.o.s. power f.e.t. form of polar-loop s.s.b. transmitters (*Electronics Letters*, May 10, 1979). This interesting approach appears to overcome many of the problems of designing and building linear amplifiers of high performance as well as making possible the use of more efficient Class C and Class D amplifiers for all stages of power amplification.

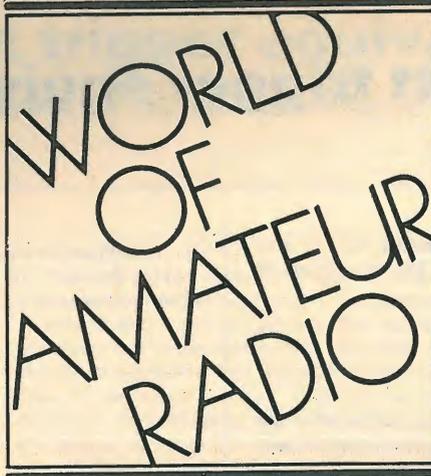The polar-loop technique is based on a form of s.s.b. transmission by envelope elimination and restoration originally proposed by Leonard Kahn in 1951 (*Proc IRE*, July 1952). However the team at Bath University has combined the Kahn approach of splitting the s.s.b. signal at low level into its phase-modulated



component and then restoring the amplitude envelope only in the final power amplifier stage with newly developed modulation techniques and the use of feedback to improve linearity. This has resulted in h.f. and v.h.f. (99.5MHz) s.s.b. transmitters with outputs of 20W and 13W respectively, with third-order intermodulation products typically over 50dB down on p.e.p. and power efficiency in excess of 55 per cent.

It is claimed that the r.f. circuits, using a combination of v.m.o.s. and bipolar devices are exceptionally simple, and can include Class C frequency multipliers. It is also suggested that the feedback arrangement makes the equipment unusually insensitive to power-supply variations, tuning, change of components and does not require critical setting up; all these are characteristics of particular interest to an amateur building his own equipment. While the system is the subject of a patent application, V. Petrovic made it clear that there is no objection to the use of these techniques in home-built equipment.

The use of v.m.o.s. r.f. devices is becoming much more attractive to amateurs with the appearance of relatively low-cost devices such as the Siliconix VN88AF and VN67AJ. Work at Bath has shown that while v.m.o.s. successfully overcomes many of the destructive problems associated with bipolar transistor power amplifiers, care is still needed to avoid, for example, destruction of devices by the use of too high bias resistors. The v.m.o.s. amplifiers however are extremely easy to bias and can also be neutralised using traditional valve neutralising circuits in either single-ended or push-pull form.

Spanning the bands

A.R.R.L., commenting recently on the continuing problem of the Russian 'Woodpecker' over-the-horizon radar interference to communications, stated: "despite numerous complaints to the FCC by the users of several radio services in the United States, and despite

the fact that the US State Department has been involved in this matter for nearly three years, the interference persists." The League suggests that American amateurs suffering from the interference should write to the Monitoring Branch of FCC at Washington DC.

During March a number of Australian amateurs worked N6CT and W6XJ in California on 52MHz, the first Australian-USA 50MHz contacts to be recorded in Solar Cycle 21. During January 7-11 many 144MHz and some 432MHz contacts were made across the Tasman sea between Australia and New Zealand. Late in June it appeared that the second of the four predicted peaks of Cycle 21 had been passed with the last two peaks expected in late-Autumn and early 1980.

The IARU Region 1 v.h.f. "records" suggest that it is becoming increasingly difficult to set up new "tropo" propagation records from the UK. Favoured stations would appear to be those along the Mediterranean where for example the 1977 144MHz contact between Israel and Malta spanned 1964km - and could conceivably be extended to the Tunisian coast or even Spain, comparable to the sea-path ducts that have occasionally occurred between Hawaii and California.

In brief

Listeners registered as members of the BBC World Radio Club have passed the 38,000 mark . . . The next Radio Amateurs' Examination will be held on Monday, December 3, 1979 . . . FCC has confirmed its decision not to issue special-event amateur station licences . . . Bill Leonard, W2SKE, has been named president of CBS-TV news . . . Amateurs in Spain, Balearic Islands, Canary Islands and Spanish Morocco have been granted permission to operate in the frequency band 1820-1835kHz while the USSR is opening the band 1850-1950kHz to amateurs . . . The Italian amateur, Fausto Minardi, I4EAT, has contacted 50 countries on 144MHz using tropo, moonbounce, meteor scatter, Sporadic-E and auroral modes . . . Angus McKenzie, the well-known blind amateur (G3OSS) and audio consultant, received an M.B.E. in the Queen's Birthday Honours List for his services to audio research, the blind and disabled . . . A Morse recording "ad astra per aspera" made by W. R. Schoppe, WB2FWS, was included on space probes Voyager 1 and 2 . . . There seems little likelihood of any further operation through the two Russian amateur satellites RS1 and RS2 following telemetry indications of battery troubles . . . Mobile rallies include: August 26 Torbay Mobile Rally at Paignton; September 9 Telford Mobile Rally; September 16 Peterborough; September 30 Harlow.

PAT HAWKER, G3VA

Sidebands as phasors

Depicting the mechanism of modulation: 1 — a.m., d.s.b. and s.s.b.

by J. M. Osborne, M.A., F. Inst.P., South London Science Centre

The phasor is a useful visual aid to understanding sidebands that bridges the gap between simple amplitude/frequency graphs, as seen on a spectrum analyser, and the rigorous mathematical expressions from which they come. This first article, dealing with amplitude modulation, outlines the principles of phasor representations of carriers and sidebands, then illustrates points such as why carrier re-insertion in s.s.b. is not critical while in d.s.b. it is near impossible. A second article will deal with phasor representation of sidebands in frequency modulation.

FOR MOST electronic engineers who have to deal with modulation, the structure of sidebands in a.m., s.s.b. and d.s.b. is well recognized. The direct mathematical approach is well within the (university or poly) student's grasp. The requisite manipulation of trig. functions is relatively elementary. The same cannot be said of frequency modulation. The consequences of rather involved mathematics (see later for Bessel functions) show that we have sidebands stretching to infinity. Text books tell us that in practice we need not have infinite bandwidth since the more remote sidebands are likely to be negligibly small.

If we frequency modulate a carrier by 50kHz above and below the unmodulated carrier frequency, intuitively we might suppose that 100kHz bandwidth would be required. The mathematicians tell us that this naive thinking could be quite erroneous; it happens to be the right approximation for large modulation indices but not true for narrow band f.m. They are right, since their approach is rigorous. Can we lesser mortals understand why? Let us start with a.m. Fig. 1 shows a typical a.m. signal of 1MHz carrier 100% amplitude modulated with a 1kHz audio note.

Such an illustration as Fig. 1(b) is used to give an elementary explanation of diode demodulation. This is valuable in, say, the "Beginners book of radio" or "How does a crystal set work?" Fig. 1(a) is more difficult for the beginner but is really the next step in sideband conception. It presents the mathematician's work in a form suitable for considering bandwidth and selectivity in practice. It is easy to visualize the extended form of


Fig. 1 when speech or music modulation is imposed on the carrier. I assume that the reader is familiar with the complex waveform seen on a c.r.o. when the y input is fed with an audio signal from a microphone or gramophone pickup; and that this complexity determines the required (audio) frequency response of associated amplifiers, loudspeakers etc. This is shown figuratively in Fig. 2(a) and (b). Here sidebands will be popping up and down like yo-yos. This may be used to discuss the hi-fi limitations of medium wave broadcasts.

What these figures fail to do, and what the mathematicians frequently fail to point out in their results, is the significance of phase. A plausible, though inadequate explanation is that each side band (in Fig. 1) heterodynes (beats with) the carrier to produce the difference frequency (1kHz); the two contributions add to give the required audio output. In particular the real problems of homodyne and synchrodyne reception are missing; the superficial explanations of such techniques along these lines are of little value.


It is at this stage that the phasor comes into its own. The phasor bridges the gap between the simple representation of Fig. 1 (a) and the pure rigorous maths from which it comes (see Appendix). It gives the electronic engineer a

visual picture which rationalizes the significance of phase in the more sophisticated techniques of demodulation; e.g. why carrier reinsertion in s.s.b. reception is not critical while in d.s.b. it is near impossible. It also explains why a.m. works without such considerations, since everything starts right (in terms of phase) from the transmitter. When we amplitude modulate the carrier nothing is changed (no synthesized carrier is generated and inserted at the reception end) throughout the communication link. We gloss over selective fading in short-wave reception and its consequent distortion. Not only do 'phasors' rationalize the foregoing but, and this is perhaps the main point of this article, 'phasors' explain in Part 2 'f.m. sidebands'.

The explanation is best started by considering a.m. (see Fig. 3). This also has the spin-off in clarifying the relevance of phase in the examples mentioned above. "The 1MHz sinusoidal (sine wave) carrier has its amplitude varied sinusoidally at the very much lower modulating frequency of 1kHz." Here is the catch for the unwary. The fallacy is in suggesting that the amplitude of a sine wave is changed. This is a nonsense statement. Look at Fig. 4(a) and (b), two sine waves of different amplitude (same

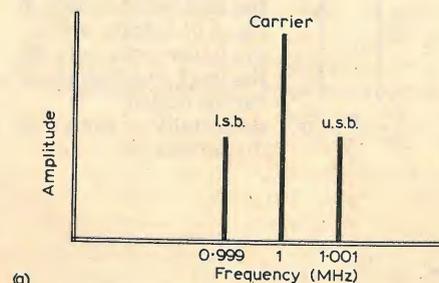


(a)

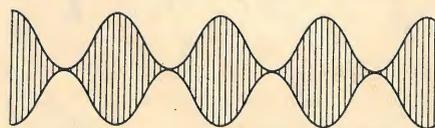


(b)

Fig. 1. (a) One way of representing the sidebands of an a.m. signal consisting of a 1MHz carrier modulated 100% by a 1kHz tone (b).

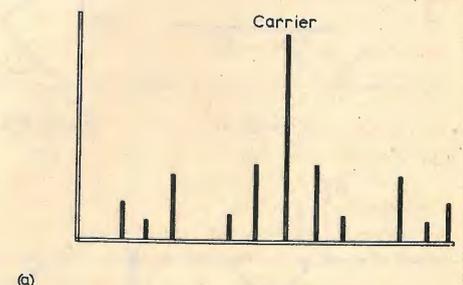

(a)

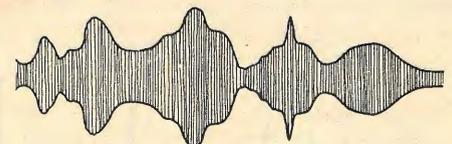

(b)

Fig. 2. (a) Typical pattern of sidebands when a carrier is amplitude modulated by an audio signal from a microphone or pickup (b).

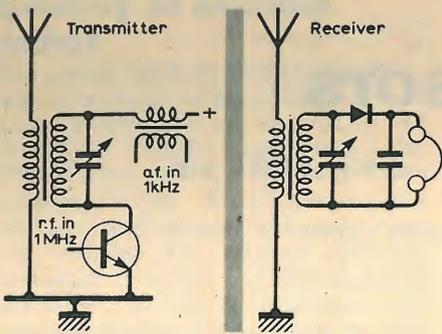


Fig. 3. Transmitter and receiver using amplitude modulation.

frequency). Now consider changing from one to the other as in Fig. 4(c), or for that matter in Fig. 1(b). (c) is neither (a) nor (b). At some stage, the shape or slope of (a) must change to get it to (b). While this change is taking place we have no simple sine wave, neither (a) nor (b). (c) is not part of an amplitude modulated "sine" wave.

When is a sine wave not a sine wave? Answer in this case - while it is changing amplitude.

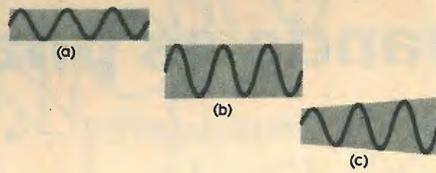


Fig. 4. During the change from a sine wave of amplitude (a) to a sine wave of amplitude (b), the transitional waveform (c) is not a pure sine wave.

To remind you of the sine wave, consider a radius, a , in Fig. 5 rotating at Ω_0 radians per second. ($\Omega_0 = 2\pi f_0$ is the revolutions per second or frequency in Hz). If the radius starts horizontally at time zero, rotating anticlockwise, then after t seconds, it makes an angle Ωt with the horizontal. The projection onto the vertical axis is given by $y = a \sin \Omega t$. If the graph of y against t is plotted we get the familiar sine wave of alternating voltage to y input of c.r.o., with linear (x) timebase, of amplitude a and time for one cycle $1/f_0$. y may represent

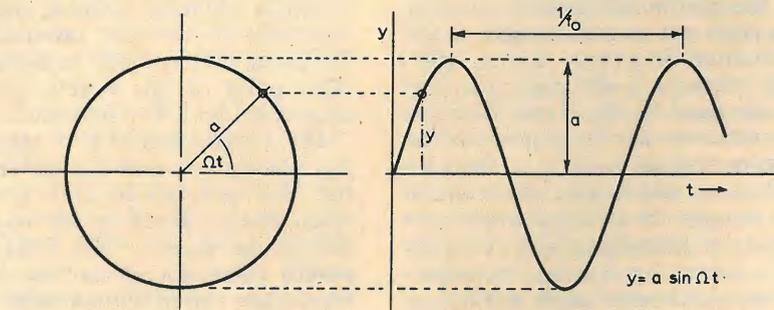


Fig. 5. Formation of a sine wave $y = a \sin \Omega t$ from a radius, a , rotating at Ω radians per second. Capital omega is used to denote a reference wave. In the Appendix, lower-case omega refers to the modulating wave.

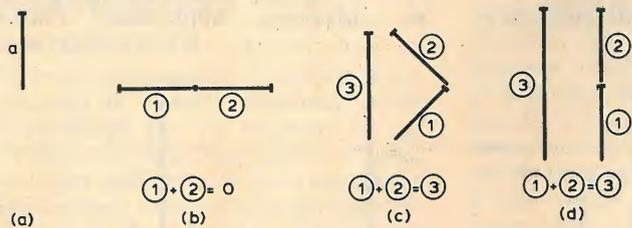


Fig. 6. At (a) is a phasor representing the sine wave shown in Fig. 5 (it rotates about the lower extremity of the line). Such phasors can be added vectorially as shown in (b), (c) and (d).


physical displacement, as in simple harmonic motion, or the instantaneous value of an alternating voltage or current. This is determined by the scale and label of the y axis. t along the x axis is usually chosen to show a few cycles.

The phasor representation of this is shown in Fig. 6(a). This shows a length a representing the generating radius which is supposed to be rotating anticlockwise at the frequency f_0 . The attractive feature of this notation is that it shows phase. For example, if two sine waves, equal in amplitude and frequency, of different phases are combined, the resultant can be found by adding vectorially the phasors. This is shown in the examples of Fig. 6(b), (c) and (d); in (b) the signals cancel (180° phase difference) whereas in (d) the amplitude of the resultant is the sum of the two components (in phase), and (c) is an intermediate state of phase difference.

If the two above phasors have differing frequencies f_1 and f_2 , instead of f_0 , their instantaneous resultant (that is amplitude) will change with their relative phase. Suppose we consider the two sine waves such that f_1 is greater than the reference f_0 , f_2 less by the same amount. This shown in Fig. 7 in a series of diagrams showing the time for f_1 to gain one cycle and f_2 to lose one cycle on the reference. Note the suggested modification to the phasor notation to show which way f_1 and f_2 phasors rotate with regard to the reference phasor, frequency f_0 . Row 1 shows the two components while row 2 shows successively the instantaneous resultant. Note another suggested notation (double bar) to identify the resultant.

If we now add these to the component of frequency f_0 and amplitude equal to

Fig. 7. Effect of vectorially adding two phasors representing equal amplitudes but different frequencies. Row 1 shows the two phasors separately at successive instants of time (moving right on the page) while row 2 shows the resultants at those instants. (Small bars on moving ends of phasors in row 1 are modified from Fig. 6 to show directions of rotation. The double bars in row 2 identify the phasors as resultants.)

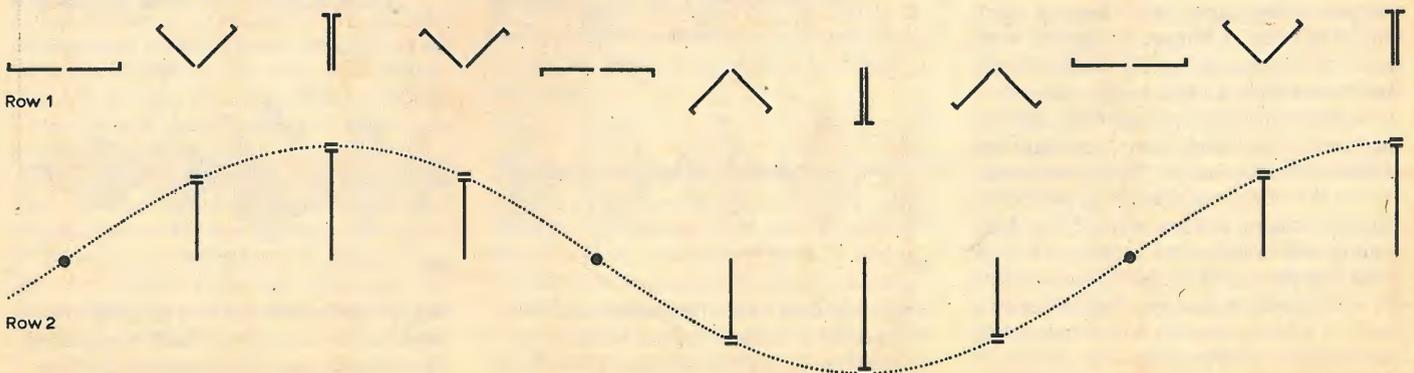

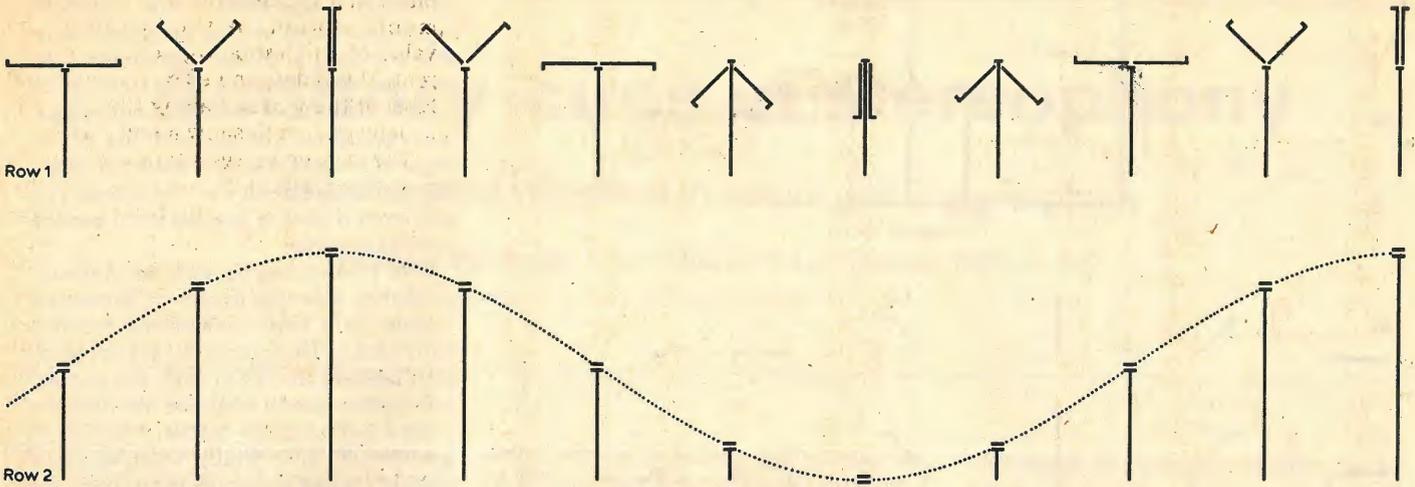


Fig. 8. The phasors in Fig. 7, representing upper and lower sidebands, are added to a phasor representing a carrier of constant amplitude and phase. Row 1 shows the separate phasors and row 2 the resultants. This demonstrates the carrier being amplitude modulated as a result of adding the sidebands to it.

the sum of the amplitudes of f_1 and f_2 , we obtain the resultant shown in Fig. 8. Note that the instantaneous resultant remains precisely in phase with the reference. What this shows is that if two sine waves f_1 and f_2 are added to the reference sine wave the resultant is of frequency f_0 and amplitude varying at a frequency $f_1 - f_0$ (which is the same as $f_0 - f_2$). Phasors show that an amplitude modulation of a carrier f_0 results from adding to it an upper sideband f_1 and lower sideband f_2 , all three being pure sine waves.

We can now see Fig. 1 (a) and (b) in terms of sine waves. Also it is not difficult now to visualize that imposing amplitude modulation on a carrier as in Fig. 3 distorts the 'pure' sine wave of the (c.w.) carrier to produce, in addition, the two sidebands.

The example chosen has been de-

liberately simplified to modulation by a single (audio) frequency. It is not difficult to visualize, say, speech or music modulation producing a complex of sidebands as in Fig. 2. What should now be clear is that, however complex the signal, it consists only of sine waves; the carrier f_0 remains unchanged; the sidebands occur only in pairs, equally above and below the carrier frequency and that the final resultant remains exactly in phase with f_0 varying only in amplitude.¹


The example of Fig. 8 (and Fig. 1) shows 100% modulation, the amplitude of the sidebands being half each the amplitude of the carrier. It is important not to over-modulate, which can easily happen if the transmitter of Fig. 3 is improperly adjusted. Not only does it become impossible to recover the modulation in the receiver, but the sudden discontinuities when the resultant falls to zero produce very high frequency sidebands (splatter), resulting in spurious signals, i.e. interference, over a very great bandwidth. In fact to accommodate speech and music modulation, the average amplitude of the sidebands must be kept very small to avoid over-modulation on peaks.

In terms of power and efficiency

amplitude modulation is very poor. Bear in mind that doubling the amplitude quadruples the power (doubling the voltage in a circuit doubles the current and hence quadruples the power). For 100% modulation, each sideband is a quarter of the power of the carrier so that two-thirds of the total power goes in the 'reference frequency' carrier and only one third in the information bearing sidebands. This is the best case of 100% modulation; the general case of a typical broadcast station would probably show that over an extended period the average efficiency, that is the energy of the information bearing sidebands to total energy radiated, is only a few percent.

The radiation of vast amounts of carrier power, often 10 to 100kW in the case of broadcasting stations, has led to suppressed carrier systems for other

Fig. 9. Phasor illustration of the effect of using a reinserted carrier in a receiver 90° out of phase with the suppressed carrier in Fig. 8. Row 1 shows this reinserted carrier phasor together with the sidebands, while row 2 shows the process of their vectorial addition (a) and the resultants (b) indicating changes in phase but little change in amplitude.

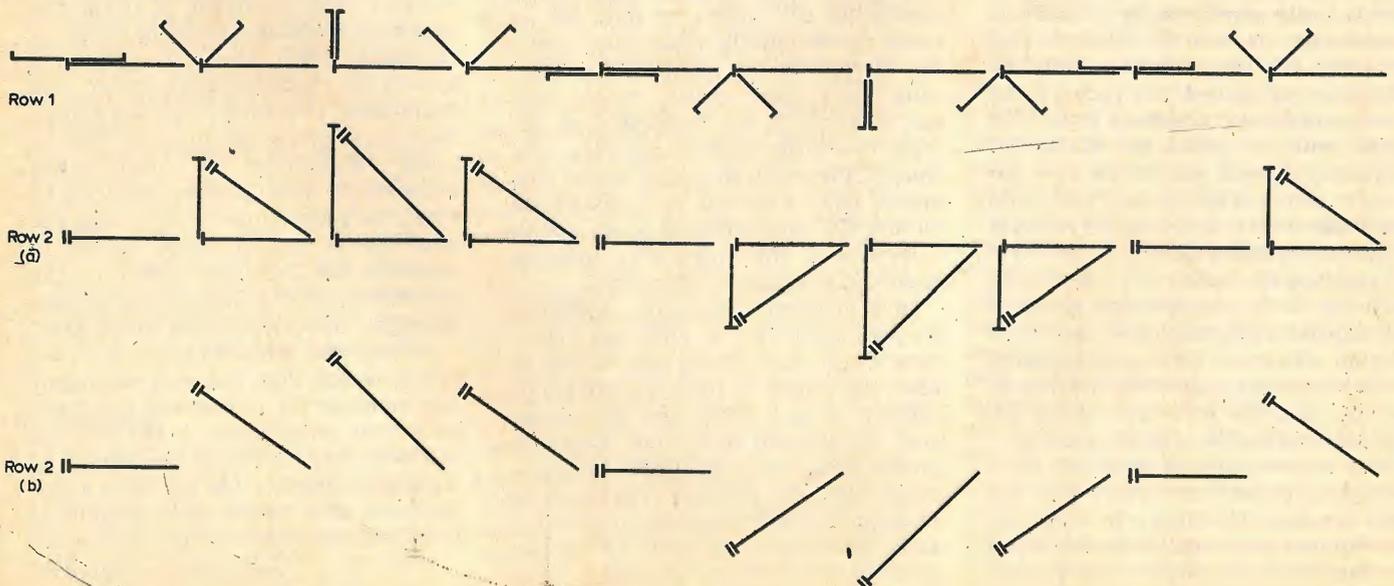

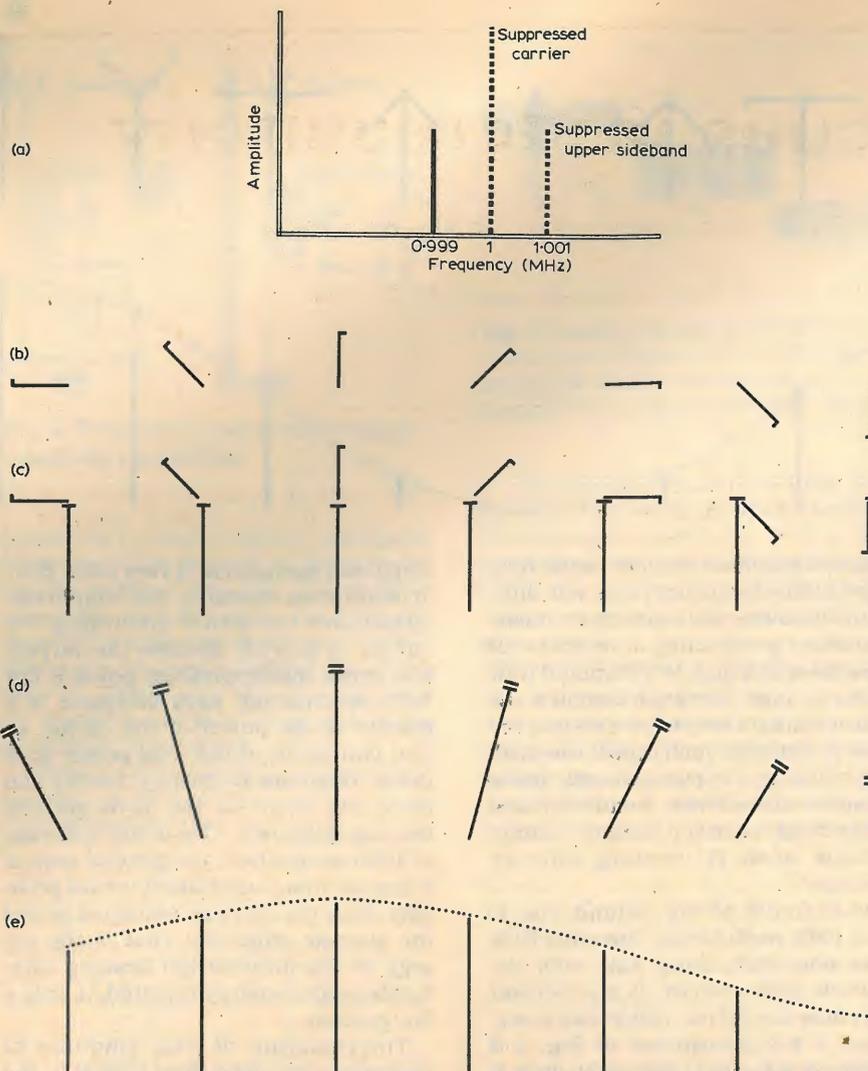


Fig. 10. Phasor illustration of s.s.b. communication. At (a) is the s.s.b. equivalent of the Fig. 1 (a) spectrum; (b) radiated (lower) sideband; (c) carrier re-inserted at the receiver; (d) resultants from (c); and (e) resultants plotted as amplitude values to show waveform of amplitude modulated signal.

communication, only the sidebands being radiated. Double sideband suppressed carrier (d.s.b.) is shown in Fig. 7. This is easily generated by a balanced modulator in which the carrier frequency is balanced out and only the sidebands produced. To receive the signal is, in theory, simplicity itself! One needs only a local oscillator of frequency f_0 and amplitude two (or more) times the peak sideband amplitude. This is added in the receiver (maybe a few milliwatts are involved) to the received sidebands and we proceed as in Fig. 8. The transmitted power is only sideband information so the transmission efficiency (effective radiated power) is theoretically 100% and only at the cost of a few milliwatts in the additional local oscillator in the receiver.

Such a system would obviously have come into general use years ago but there is a snag. The snag is in achieving the required performance specification for the local oscillator. The phasor

approach makes the problem clear. Consider a local oscillator of the right frequency f_0 added to the sidebands of Fig. 7 but 90° out of phase with that shown in Fig. 8. If we redraw this new situation in Fig. 9 we see that the amplitude of the resultant hardly varies at all (and incidentally the phase no longer remains the same as the reinserted carrier). This shows the tight specification of the local oscillator; not only does f_0 have to be the same frequency as the original suppressed carrier but if it differs by only 90° in phase the amplitude modulation virtually disappears. No practical free running oscillator could meet this specification. If the frequency of the local oscillator differed by only 1 Hz from f_0 the received signal would disappear twice a second, as it passed the 90° and 270° phase difference point with reference to the original f_0 , making meaningful reception impossible.

In a dispersive medium, different frequencies travel at different velocities. Only small effects are needed to alter the phase of received sidebands relative to each other and the carrier with consequent distortion. Likewise phasor additions of multipath propagations can give garbled results. A.m. propagation via ionospheric reflection (s.w. broadcasts) is liable to fall far below "entertainment" standards while

amateurs working long range v.h.f. by reflection of signals from the Northern Lights (aurorae), during periods of suitable sun spot activity, cannot use a.m. and use c.w. (morse code) for such communication. Variations in propagation conditions and the stability of the original transmitter f_0 would not allow the requisite stability of the whole system even if such a precise local oscillator was feasible.

The phenomenon can be demonstrated by listening to an a.m. broadcast station on a communications receiver with a b.f.o. The carrier is reinforced by zero beating the b.f.o. with the carrier. Intelligible speech might be obtained for even a few seconds before it begins to get 'rough' and finally unintelligible. Should results be better than predicted some form of pulling (i.e. tendency to lock) of the b.f.o. to the carrier frequency is almost certainly taking place. This would result in homodyne/synchrodyne reception² (by accident rather than design). The mode of operation of receivers intentionally using these techniques is easier to follow if the 'phasor fundamentals' are first digested.

One such system of a.m. demodulation available as an i.c. package is the phase locked loop (p.l.l.). The local voltage controlled oscillator (v.c.o.) locks onto the carrier frequency f_0 . The signal with its sidebands and local oscillator are mixed in a product detector to give the audio output. It so happens that the locked v.c.o. runs 90° out of phase, i.e. in quadrature, with the carrier. An external 90° shift has to be incorporated in the system to achieve the Fig. 8 rather than the Fig. 9 situation.

We can now, using the phasor reasoning, continue the argument to show the viability of s.s.b. as an efficient means of communication. Fig. 10(a) shows the s.s.b. as an equivalent of the Fig. 1(a) spectrum, taking the lower sideband. (Exactly the same argument would apply had we taken the upper sideband.) Fig. 10(b) shows the radiated sideband while Fig. 10(c) shows also the carrier f_0 (1 MHz) as reinserted at the receiver. The resultant is again the amplitude modulated signal as shown in Fig. 10(d). Only half a cycle is shown, as by now the reader will be familiar with the process. The resultant shows a small (spurious) phase modulation (hence phase distortion at modulating frequency). This can be reduced to negligible proportions by increasing the amplitude of the reinserted carrier. In practice the local oscillator in the receiver is so much more powerful than the signal that the problem solves itself.

As only one sideband is involved we can now see that the very stringent requirements for reinserting the d.s.b. carrier no longer apply. If the inserted carrier is, say, ± 10 Hz off the original f_0 , the consequence is that the 1 kHz audio tone is in error by the same amount. If the original modulation had been

continued on page 60

Auditory cues in stereophony

Importance of transients in nature and in stereophony

by Philip Vanderlyn, Central Research Laboratories, EMI Limited

Now that the spate of new multi-channel stereophonic reproducing systems has decreased to a trickle, it seems timely to look again at the physical and psychological bases that govern directional hearing to discover why nothing has so far emerged to displace the familiar two-channel arrangement hitherto widely accepted.

This article emphasises the time difference cue to direction and the role of transients as "time tags" both in natural listening and in stereophony. Some experimental evidence is put forward in support of the conclusions which largely explains the failure of quadraphonic and other systems to make good their claims to "all-round" localization and total realism.

OVER THE LAST TEN years or so multichannel stereophonic systems have proliferated. The proponents of most of these systems have so far largely failed to spell out the objectives that they are pursuing, still less the means by which they hope to succeed. Not all of the systems aim at increased naturalness of reproduction: the so-called "surround" category in particular were only designed to produce a (hopefully) pleasing effect. Mostly, however, the implication is that they are trying to recreate the natural listening situation to a greater extent than is possible with the now conventional two-channel arrangement. Efforts have met with varying degrees of success but none can claim to have said the last word on this complicated subject.

One cause of failure is surely the lack of awareness of the auditory cues that have to be provided if nature is to be effectively imitated. This article summarizes the generally accepted facts concerning directional hearing of which architects of stereophonic systems must take note if they hope to achieve realism.

The Pioneers

Tribute is due to the illustrious workers who have contributed so painstakingly and rigorously over a very long period to piece together the now considerable body of knowledge that exists concerning the ear and hearing. From the

pinna which receives the pressure variations that constitute an acoustic stimulus, through the transducing members comprising the eardrum, stapes, cochlea, basilar membrane and hair cells, the action potentials they generate, their coding and mode of transmission along the fibres of the eighth nerve and its pathways and interconnections between the higher centres of the brain where the semantic and other significant information is extracted and utilized, would be long enough in itself to fill an article. A short list might include Helmholtz, Rayleigh, Stewart, Banister, Firestone, Stevens, Newman, von Békésy, Fletcher, Snow, Wallach, Rosenzweig, de Boer, van Urk, Galambos, Davis, Jeffress, Wiener, Hirsch, Cherry, van Bergeijk and Deatherage, omitting many more, particularly of the most recent workers. Anyone who cares to follow the unfolding story through the medium of their published papers will find it a fascinating, if as yet incomplete one.

Before examining hearing in detail it is interesting to compare the sense of hearing with that of sight. Hearing, like sight, must have evolved primarily as a survival mechanism; the reaction to a sudden stimulus automatically posing the questions: "What is it?" and "Where is it?" In daytime the eye has a great advantage in that the geometrical laws of optics do a great deal of the work of locating and recognizing remote objects, a process employing large numbers of parallel channels which respond relatively slowly (fortunately for the cinema and tv). In the dark the ears become the first line of defence and by contrast provide only two channels, albeit capable of much more rapid response, and more processing is needed to extract meaningful information. From a complex sound stimulus the ears and brain together have to recognize which components cohere into groups identifying specific sources (the "gestalten" of Cherry¹), their pitch and timbre, in which directions these lie, a rough idea of their distance and perhaps, from their reflections, something of the unseen environment. The process is essentially time-oriented, the response of the auditory complex being much more rapid than that of the visual. less than 100 discrete samples per second give an

impression of visual continuity; to do the same aurally requires upwards of 20,000. At its most acute it can detect time differences of a few tens of microseconds.

Physical basis of localization

The simplest example of natural listening must be that of an observer exposed to sound from a single source a few metres distant, so that conditions in his vicinity approximate to plane wave propagation. If the direction of the source relative to the listener is arbitrary, i.e. it lies neither in the horizontal plane passing through his head nor in the median plane dividing his sphere of observation into left and right halves, the sounds reaching his eardrums will differ in time of arrival and will be modified spectrally by the effect of his own head as an obstacle in the sound field and by their passage through the convolutions of his pinnae. The spectral modifications depend on both frequency and direction of arrival and become increasingly large and complicated at high frequencies. The time difference, however, is invariant with frequency and depends only on the difference in length of the paths from the source to the two ears. This lack of dependence on frequency gives the interaural time difference an overriding importance in sound localization.

If the sound source emits a pure constant-amplitude sine wave the time difference manifests itself at low frequencies as a phase difference proportional to frequency. As frequency increases the phase difference becomes equal to π radians at about 700Hz for maximally left or right sources, when the path difference becomes half a wavelength. Above this, the phase shift in excess of π radians would lead to an ambiguous judgment were it not for the fact that at this frequency the head begins to be an obstacle in the sound field and introduces an amplitude difference that allows the ambiguity to be resolved² up to something like 1.2kHz. Above this point the only meaningful cue resides in this amplitude difference, which is by no means so precise an indicator of direction as the time difference, being subject to perturbations due to local obstacles or wax in the ears

or, in closed spaces, reflections from the boundaries. It is considered to be of secondary importance: the ear relies on it when it has to.

When the sound is complex as, for example, in the case of human speech it will contain many transients, i.e. identifiable singularities in the waveform: these restore the possibility of using at high frequencies the time difference cue that already provides a firm indication at low frequencies. Not only that, but the increased resolution possible at high frequencies permits increased accuracy of localization. Evidence from everyday life supports this argument: try, for example, to detect the position of a blackbird uttering its alarm call, consisting of long pulses of tone at about 3kHz with long onset and decay times. The studied avoidance of sudden transients at the start and finish added to the choice of a frequency resulting in an ambiguous phase difference for large predators, leaves only the rather inaccurate amplitude cue which is subject to the confusing effects of obstacles and reflections. By contrast, its territorial and other song is rich in transients and presents little difficulty in locating the source.

It is difficult to overestimate the importance of transients in sound localization: a reliable mechanism clearly exists at low frequencies, but without transients it cannot be employed in that part of the frequency spectrum where the ear is at its most sensitive — from 1 to 6kHz. With their aid the interaural time difference, the most important single parameter in sound localization, can be evaluated over the entire audible frequency range.

The interaural time difference alone, however, will not determine direction: what it does is to define a surface on which the source must lie. This surface is, strictly, a hyperboloid of revolution about the axis through the listeners two ears, but negligible error results in practice from considering it as the asymptotic cone, and it is the apical angle of this cone that the time difference defines.

At this stage what have so far been considered as secondary cues come into play. The amplitude difference reinforces the left/right impression given by the time difference, whilst at frequencies for which its dimensions constitute a half wavelength or more the characteristic shape of the pinna, with its narrow and highly individual polar characteristic introduces spectral changes that every proud owner of a pair of ears will have learnt subconsciously to interpret as an indication of direction of arrival. In this connection a recent paper by Butler and Belendui³ throws some light on the use of spectral variation for estimating elevation in the median plane. A characteristic irregularity in the frequency response around 6kHz is identified that varies systematically as the source elevation changes.

These cues to localization are available to the observer without any conscious action on his part. If, additionally, he is free to move his head he can learn more about the position of the source. By observing the change in its apparent position as he turns his head from left to right he can immediately tell whether it is in front of or behind him. He can also use the first derivative — the rate of change of interaural time difference as his head turns — to estimate its elevation (Wallach⁴, de Boer and van Urk⁵).

By these means the listener has localized the source to a unique direction in space. It only remains to estimate its distance.

This parameter is the one that he has the least satisfactory means of determining. Loudness is a possible cue, but postulates prior knowledge of the strength of the source: in the case of something familiar like a human voice a rough guess at distance can result. It has been suggested that the particle velocity/pressure ratio that increases during the approach to a small source could be instrumental — the difficulty here is that the ear has no obvious means of perceiving velocity. It is true that it could be done by the two ears acting in concert sensing it as pressure gradient, but the means by which the gradient could be derived from the pressures at the ears has not been disclosed. Moreover the method would be insensitive, the rise in particle velocity amounting to only 3dB for an approach to within one radian of the source frequency. At 50Hz a radian corresponds to about 1 metre, and at higher frequencies it is proportionately less. At one wavelength distant the rise is only 0.1dB and quite undetectable.

In a closed space such as a room, the ratio of direct to reverberant sound is a quantity that gives some idea of distance but it begs the question as to how the direct and reverberant components are differentiated. In view of the confusion caused by reflections the initial judgment of direction must rely almost entirely on transients of medium and high frequency since these are the only cues available in advance of the reflections. Perhaps the relative magnitude of transients to the total sound gives some idea of distance. Certainly these considerations give added emphasis to the importance of transients in localizing sound sources.

Having pinpointed the position of the source using the means outlined, the natural reaction — no doubt a relic of the primitive survival situation — is for the listener to turn and face it. This immediately brings it into the region of greatest perceptual acuity; all the asymmetries disappear and the accuracy of location is determined by the limiting angular discrimination in azimuth. Numerous investigators had experimented on this topic: typical results are those of Moir and Leslie⁶, who found that less than 2° was detect-

able. This corresponds to an interaural time difference of a mere 22μs or so.

Psychophysiology of hearing Nature of the Transducer

The foregoing describes the physical situation of a listener exposed to a sound source. If he is to be provided by artificial means with stimuli that affect him in the same way, it is necessary to discover something of the psychoacoustic processing that constitutes his response, so that a realistic impression may be created. We have to know what cues can be and must be provided.

It is not appropriate here to enter on a detailed discussion of the ear complex: there is a very extensive literature on the subject should any reader wish to search more deeply than the present article allows. A good starting point is Fletcher⁷.

In summary: the visible portion of the auditory mechanism, the pinna, plays a not very significant role in hearing. It probably performs an energy collecting function and from its convoluted shape introduces characteristic colorations that its owner has learned to interpret as front/back and/or up/down information. Its small size restricts these functions to high frequencies, say 4kHz and above.

Within the ear the sound impinges on a membrane — the eardrum — whose motion is transmitted by way of a linkage of small bones to a further membrane — the oval window — that in turn transmits the sound energy to a liquid-filled tapered canal known as the cochlea from its coiled configuration, similar to a snail shell. The small bones that form the linkage are so proportioned that they provide an impedance match between the eardrum and the cochlea.

Running centrally down the cochlea and dividing it into two parts lies the basilar membrane, narrow regions of which resonate in response to the different frequency components of the energy reaching the oval window, in a crude Fourier analysis. High frequency components cause resonance near the oval window at the basal end of the basilar membrane whilst progressively lower frequencies shift the activity down toward the apical end. There is thus a ready-made "place" mechanism of frequency discrimination, though the mechanical constants of the system are not in accord with the known discriminatory capability of a listener. If place alone were involved a "Q" of several hundred would be necessary instead of the value that actually obtains — about three. This low value is necessary to ensure a rapid response. One must therefore assume that critical frequency resolution results from neural processing higher in the chain.

Along the length of the basilar mem-

brane and cooperating with it to produce the initial response to a sound stimulus is the organ of Corti, comprising the hair cells that are thought to play an important part in originating this response.

Neural response

The processing that takes place in the brain is electrochemical in nature and is thus not suitable to operate on an electrical signal corresponding to the sound pressure waveform. That being so, there is no reason why an electrical analogue of the waveform should appear during stimulation. Such an analogue, however, can be detected by electrodes suitably placed on the head and neck. This response is called the "cochlear microphonic", but it is not believed to play any part in subsequent processing. Possibly it is instrumental in initiating those neural signals that the brain does process, and which carry in coded form all the information subsequently extracted and recognized.

The eighth nerve, concerned with the sense of hearing, comprises at the peripheral (cochlear) level, a bundle of between 20,000 and 30,000 fibres, evenly distributed along the length of the basilar membrane, where they originate in the region of the hair cells. When the excitation of the basilar membrane adjacent to a nerve fibre ending reaches a certain threshold an "action potential" is generated, supposedly through the intermediary of the hair cells. This action potential, which propagates electrochemically along the fibre, bears little relationship to the stimulus waveform, consisting of a short pulse of the order of 1ms long, of standardized amplitude, repeated at intervals if the stimulus is maintained, at a rate depending on the stimulus intensity, but not exceeding 300 to 400 pulses per second in any single fibre. As the stimulus intensity is raised beyond the threshold, the fibre responds to an increasingly wide range of frequency, so that further processing must take place if the known fine limits of pitch perception are to be achieved. The behaviour of neural fibres was studied, notably by Galambos and Davis⁸, who worked with cats: their results are therefore conditioned by the differences between cat and human physiology. The neural mechanisms, however, operate on the same principles.

The question inevitably poses itself — how can the brain, however cunningly organized, extract the detailed information that it does from signals that apparently bear so little relation to the incoming stimulus? We are here concerned mainly with the localization problem, so that it is proposed to discuss only those cues relevant to that purpose. For more general reading, an excellent review was written by Whitfield⁹ in 1957, most of which appears still valid today.

To return to the action potential; let

us examine some of its known characteristics in the light of the localization problem. It seems that although the rate of firing depends on stimulus intensity, successive firings of the same fibre are always separated by an integral multiple of the stimulus period. This strongly suggests synchronism, and in fact the firings relate to the zero-crossing times of the stimulus (in one direction only). As is usual in nature, things are not perfectly tidy, and there is a delay, known as "latency" between the onset of a stimulus and the generation of a spike action potential. The latency is least for strong stimuli and for high rates of zero-crossing, which suggests that a threshold has to be overcome — however the disturbance to synchronism is not great.

Additionally, it has been remarked already that transmission of the action potential impulses along the nerve fibres is not purely electrical, consequently we are not considering velocities of the same order as that of light. The process is more complex, involving ion exchange between the inside and outside of the fibre, and the speed is dependent on a number of factors, including the fibre diameter and the intensity of the original stimulus. It ranges from several hundred down to one or two metres per second in the fine fibres of the auditory cortex. This slow propagation is significant since it makes available the time delay parameter as one of the processing tools with which the brain can operate on the neural signals from the two ears. Significantly, innervation from both ears takes place quite early in the neural pathways, at the superior olivary complex. It is difficult to imagine any other purpose of such an arrangement than a close comparison of the two sets of neural signals.

Regrettably, at this point the trail peters out for the moment, and the processing that eventually results in localization itself is still a matter of conjecture. Models have been proposed by several workers, notably Jeffress¹⁰ and van Bergeijk¹¹ and although these are interesting as far as they go, they are incomplete. They do, however, rely on the interaural time difference cue which is coded into the total neural response by the near synchronism of the spikes of action potential, with the vibrations of the sound stimulus as they appear at the basilar membrane. It seems that for all intensity levels well above threshold there will be at least one action potential pulse generated for every individual cycle of the incoming waveform by virtue of the large number of fibres involved. This holds good up to the limiting frequency at which one period of the stimulus is comparable with the duration of the spike: say 1kHz or so.

Nature has taken too much care over the preservation of the interaural time difference in the transcoding of the linear input signal into the non-linear neural response for this to be the result of a happy accident. It must surely

indicate the importance of such a cue in the task of localization.

The stereophonic image

In the present context stereophony excludes systems that merely set out to make a pleasing effect, such as the quadraphonic class — some spatial correspondence between the sound sources in the recording studio and the images created in the reproducing room is implied. We have to consider how, and to what extent, the natural cues in directional listening can be provided artificially by stereophonic reproducing systems.

"Discrete" stereophony

As is well known, a minimum of two channels is needed to form any sort of sound image. The simplest arrangement envisages a pair of earphones driven through identical transmission channels from a pair of microphones mounted to simulate the ears on a dummy head. In this case the listener can be presented directly with the interaural time difference cues appropriate to the positions of the various sound sources around the dummy head. The arrangement does provide a good spatial impression, to which there are two main drawbacks.

First, because the headphones move with the head, those cues associated with head movement in a free field are absent, and although the time difference cue gives good directional information, listeners usually describe the sources as being "in the head" — which is, to say the least, unnatural. Second, the wearing of headphones is in itself unaesthetic: it is far preferable to receive the sounds through one's own two ears from freely propagating acoustic waves.

Free-field stereophony

When we consider reproduction from a pair of symmetrically spaced loudspeakers we have to take account of the fact that each loudspeaker communicates with both of a listener's ears. Thus, to produce an interaural phase difference it is not appropriate to drive the loudspeakers with signals differing in phase, as in the case of headphones. As Blumlein propounded in 1931¹², to produce phase differences at the ears, the loudspeakers must be driven by signals in-phase but of different magnitude. A recapitulation of his analysis can be found in a paper by Clark, Dutton and Vanderlyn¹³ of 1957.

As a phase difference proportional to frequency is equivalent to a constant delay, a realistic interaural time difference cue can be simulated. The analysis postulates that the wavelength is long compared with the ear spacing and thus that the attenuation at the further ear due to the shadowing effect of the head itself is negligible. This condition is met at low frequencies but starts to

break down at about 700 Hz, when the interaural path becomes half a wavelength: above this frequency it is necessary to seek some other mechanism of localization.

High frequency cues

Many workers in the field have, from the earliest days, looked to the interaural amplitude difference, which is most pronounced at high frequencies, to explain the undoubted directional capability of the ear in this region. Whilst a good impression of leftness or rightness in the horizontal plane can be produced by a simple amplitude difference there are two main difficulties in ascribing to it the entire mechanism of high frequency localization. First, stereo reproducing systems work much too well in the presence of room reflections and additionally they are much too sensitive to small displacements of the listener from the central position between the two loudspeakers. These considerations strongly suggest that transients play as important a role in stereo reproduction as they do in natural listening. Experiments carried out by Percival¹⁴ in 1957 confirm this, and suggest the following hypothesis.

Localization using transients depends on the integrating capability of the ear. The situation is illustrated in Fig. 1(a). The left and right ear responses are juxtaposed to show the relative timings. At an arbitrary time the left ear, for example, receives an impulsive signal L_L from the left loudspeaker and simultaneously the right ear receives a signal R_r from the right loudspeaker. This follows from the symmetry of the listening geometry. An image to the left of the sound stage is assumed; hence L_L is shown greater than R_r . After an interval equal to the extra time taken by these sounds to travel to the contralateral ears, which, for a $\pm 30^\circ$ loudspeaker spacing will be approximately 0.3ms, the left ear will receive R_l and the right ear L_r . This later pair of signals will be reduced in amplitude as a result of their diffraction round the head. It is now suggested that the integrating capability of the ear – that is, its failure to resolve two impulses monotonically presented at an interval of less than 2 to 3ms – will cause each ear to hear a single signal at a virtual time dependent on its component parts. The resultant summed signals S_L and S_r , shown in broken line in the diagram, will have virtual timings biased toward their larger components. The significant parameter is the equivalent interaural time difference Δt between S_L and S_r , which will determine the apparent direction when the ear-brain complex fuses them into a single stereophonic image at a direction determined by the loudspeaker amplitudes L and R .

The theory clearly holds for the central case when all is symmetrical, and for the limiting cases when one loudspeaker is silent and the delay corres-

ponds to the direction of the energized one. However, the signals shown in the diagram are over-simplistic, since they represent impossibly short impulses that would be severely mutilated in passing through filters and transducers, not to mention the peripheral mechanisms of the ear itself. The figure is really no more than a timing diagram, showing the fixed time relationship between the variable amplitude component sounds at the two ears. What it implies is that at some time after the onset of the partial stimuli indicated by the thick arrows of Fig. 1, the integral of the energy received by one ear will reach a threshold value before the other, depending on the relative amplitudes of these partial stimuli, and an action potential will be generated at that ear earlier than at the other, as though it had resulted from a single virtual stimulus with a timing indicated by the thick broken arrow.

In Fig. 1(c) the position of the virtual stimulus may seem strange, but remember that if the second pair of

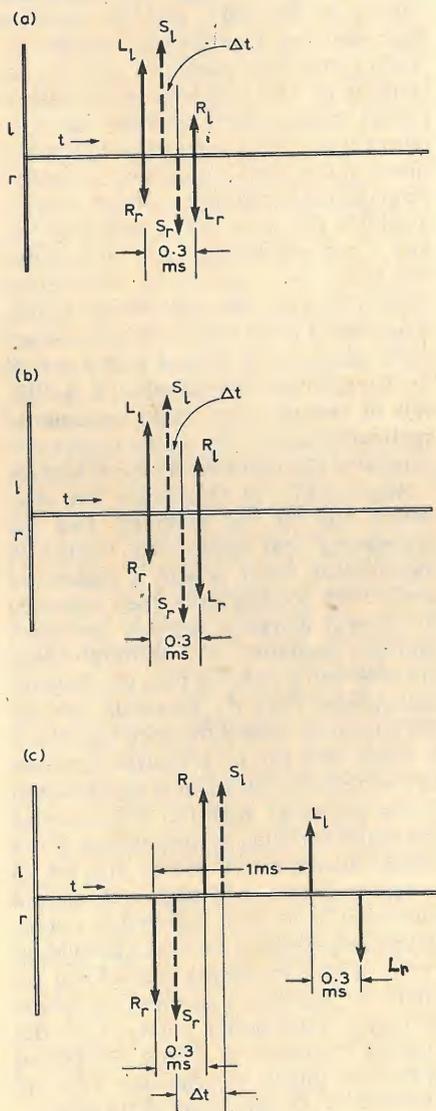


Fig. 1. Timing diagram, shows generation of a virtual time difference Δt from components fixed in time but of variable relative amplitude.

partial stimuli are significantly delayed, the response tends to separate into two parts associated with the two components, and the second partial stimulus will have little effect on the first. This could indicate a time-weighting in the integration, the running integral having an effective decay time of a few milliseconds: clearly the integral cannot be allowed to build up indefinitely.

Experimental evidence

Some light is thrown on this theory by an experiment in which an attempt is made to recentralize the perceived image by delaying the signals to one or the other ear. Two symmetrically placed loudspeakers, driven in-phase at different amplitudes, produce signals at a pair of non-directional pressure microphones spaced 20cm apart, representing the relative ear positions of a hypothetical listener. To eliminate any effects due to head shadowing, no dummy head is used: the only variable is the relative amplitude of the fixed time components of Fig. 1(b) as determined by the loudspeaker signals. The amplified microphone outputs are fed to delay networks arranged to produce a differential delay in either sense up to a maximum of 0.35ms, and thence to the left and right receivers of a pair of stereo headphones. Assuming that integration takes place independently in each ear it should be unaffected by the interposition of the delays in the microphone channels, and it should be possible to shift the signals of Fig. 1(b) relative to each other by an amount $-\Delta t$ until the summed signals S_L and S_r synchronize to produce a central image.

Denote $(L-R)/(L+R)$ by x , and call this normalized amplitude difference the calculated position of the source. Against this is plotted the normalized angle of incidence of a sound wave at the microphone position which would give rise to the interaural time difference Δt determined experimentally. The full-line curve of Fig. 2 shows there is good correspondence between the theoretical and experimental values, which represent the average of six observers' results.

These results were not obtained without difficulty. It was pointed out previously that the signals of Fig. 1 are fictitious, and it was proposed initially to ensure that vestigial low frequency cues were absent by using a high frequency tone pulse with rapid onset and slower decay time. Difficulties were encountered with interference fringes due to the tone which, with the unavoidable small asymmetries of the experimental set-up, produced spurious amplitude differences at the microphones. To overcome this, random noise, band-limited by a 2kHz high-pass filter was substituted for the tone and modulated with the same pulse waveform. This improved matters considerably but the final image produced

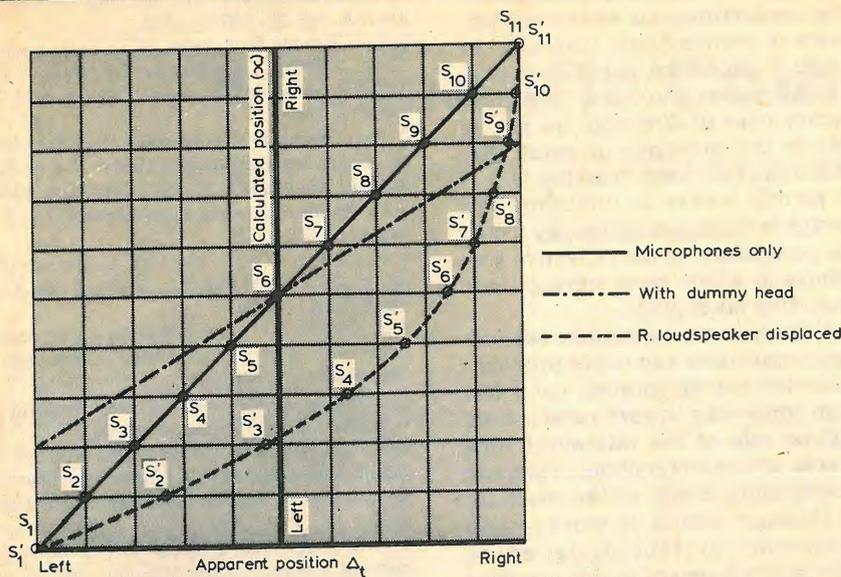


Fig. 2. Central listening results in linear stage geometry as virtual sources S_1 to S_{11} from equal increments of x , require equal increments of Δt to restore centrality. Asymmetric listening (broken curve) results in stage geometry distorted as the same virtual images are drawn towards the nearer loudspeaker. Dummy head (dot-dash curve) enhances the cue without affecting linearity.

in the headphones was still not so well defined as the actual image at the microphone position in the anechoic room. The results, nevertheless, are sufficiently clear cut to show that an effective interaural time difference cue is produced when the loudspeakers are driven with high frequency transient signals, in-phase but of different amplitude, without benefit of any head shadowing effects.

The effect of the head

Because diffraction round the head undoubtedly plays a significant part in live listening the experiment was made more realistic by introducing a dummy head between the microphones. This was made of plaster, but wrapped in polyurethane foam so as to simulate human flesh a little more closely. The result of this was to enhance the angular sensitivity of the arrangement, requiring more compensating delay for a given amplitude difference at the loudspeakers, as shown by the dot-dash curve of Fig. 2. This additional delay must represent a trade-off of time differences against the intensity differences introduced by head shadowing.

The enhanced angular sensitivity of the stereo listening arrangement at high frequencies was noted in ref. 13 as an empirical finding. In those early experiments the angular displacement of the image at low frequencies as the speaker amplitudes were varied agreed closely with that found in the present case in the absence of the dummy head, although two quite different mechanisms are involved. At high frequencies the excess sensitivity is now shown to be due to the presence of the head with its attendant diffraction pattern. The

magnitude of the increase is of the right order to account for the difference.

Before concluding the tests one further experiment of significance was performed to demonstrate the effect of asymmetrical listening. Reverting to the set-up without the dummy head, the right loudspeaker only was brought one foot nearer the microphones and the first experiment repeated. This is approximately the same as displacing the listener the same amount to the right of centre, but more convenient experimentally.

Fig. 1(c) shows how the timings are affected. The sound from the right loudspeaker clears both ears before that from the left reaches either, about 1ms later. By this time a fully right-handed cue is in course of establishment which the later sound from the left loudspeaker has difficulty in modifying. One can thus expect a strong bias to the right and this is indeed what happens, as is evident from Fig. 2. The broken curve shows that values of x corresponding to apparent sources S_1 and S_{11} for the central listening position, five to the left and five to the right of stage centre, now yield a distorted image with only two (S_1, S_2) to the left and eight (S_4 to S_{11}) on the right, crowding up toward the loudspeaker position.

Moreover, this effect is not one which scales up or down with the size of the reproducing set-up. The result of a foot of misalignment is the same whether we are operating in a domestic living room or the Albert Hall. It is one of the principal hazards in the way of mounting a large scale demonstration of stereophony, as anyone who has made the attempt will be only too aware.

The implications for quadrasonic systems are obvious, but their pro-



Philip Vanderlyn joined EMI in 1935, working under A. D. Blumlein and H. A. M. Clark from where he learned the facts of stereophonic life. Experience at EMI up to retirement in 1979 included work on stereophony, sound locators, radar, data transmission and the application of digital techniques to sound recording. Born in London in 1913, he was educated at Christ's Hospital and Northampton Polytechnic.

ponents seem never to have faced up to them. All two-channel systems have a locus on which it is possible for a listener to position himself equidistant from the loudspeakers. For three channels there will always be one point that meets this criterion, but four channels do not provide even this vestigial possibility unless great care is taken in siting the loudspeakers – errors must be small compared with a foot. Nevertheless this factor seems to be universally ignored: much effort is expended on analysing the energy distribution around a point-sized listener, tacitly assumed to be exactly equidistant from every reproducer. Yet a little matter of a foot of error in the placing of one of them can distort the image geometry out of all recognition. Consideration of the directional distribution of energy may perhaps be appropriate under steady-state conditions. Speech and music, however, together with most other everyday sounds conveying useful information to a listener do not fall in this category. In contrast they may be more realistically considered as a stream of connected transients.

It is more than probable that, given additional channels, better stereophony can be achieved than with the basic two which economic stringency has hitherto allowed us. However, before we adopt any alternative multichannel system as an industry standard we ought to be clearer than we are now about its psychoacoustic basis, its aims and objects and the means by which these are to be put into effect.

Conclusion

The practice of stereophony comprises two facets: the understanding of how a listener uses his ear/brain complex to locate the sources of sounds under natural conditions, and the engineering of means to reproduce en-

ough spatial cues from a multiplicity of loudspeakers to recreate an effective image at another place or time.

We are still a long way from writing a full description of the total mechanism of localization. What is clear is that nature employs all the auditory clues available at all times, but they vary in effectiveness according to circumstances. The present article is intended to highlight the important role played by transients in nature and in stereophony – in the last instance it might well form an addendum to reference 13.

The experiments described are not proof that an actual interaural time difference is generated by the method described. Because the cue derived in Fig. 1(b) can be compensated by the introduction of a contrary time differential it is not rigorous to assume it consisted of a time difference in the first place: many workers (e.g. ref. 15) have shown that time differences can be traded directly with, for example, intensity differences. But the fact that the compensating delay in the experiment trades off linearly against the differential cue provided, arriving at the precise value of intermicrophone delay in the fully left or right condition when only one loudspeaker is operating, suggests strongly that an effective interaural time difference is indeed created.

Obviously, the additional intensity difference cue resulting from the insertion of the dummy head has to be traded off against an additional time delay (see the dot-dash curve of Fig. 2).

The experiment on asymmetric listening underlines an everyday experience in stereophonic listening. In this case it should be noted that only transients are involved; the low frequency cues to direction are not so fragile in the presence of small displacements. This very fragility, however, merely serves to underline the powerful influence exerted by transients, particularly in the reflective surroundings in which most stereophonic reproduction takes place.

The experiments are neither exhaustive nor conclusive and could probably be extended and elaborated, but I feel they go some way toward establishing the prime role of the interaural time difference cue in stereophonic listening and unravelling some of the mechanisms through which it works. Any stereophonic system designed to operate without regard to this cue does so at its peril.

Acknowledgments

My thanks are due to many colleagues, in particular Dr W. S. Percival, for numerous day-to-day discussions, mostly of some fifteen years ago, that have been responsible, along with the personal experience of living with stereo since its inception, for distilling the material of this article. Acknowledgements are also due to the Directors of EMI Limited for permission to publish it.

References

1 E. C. Cherry & B. McA. Sayers, Mechanism

- of binaural fusion in the hearing of speech. *J.A.S.A.* vol. 29 (1957) p. 973.
 2 T. T. Sandel, D. C. Teas, W. E. Feddersen & L. A. Jeffress, Localization of sound from single and paired sources. *J.A.S.A.* vol. 27 (1955) p. 842.
 3 R. A. Butler & K. Belenduck, Spectral cues utilized in the location of sound in the median sagittal plane. *J.A.S.A.* vol. 61 (1977) p. 1264.
 4 H. Wallach, On sound localization. *J.A.S.A.* vol. 10 (1939) p. 270.
 5 K. de Boer & A. T. van Urk, Some particulars of directional hearing. *Philips Tech. Rev.* vol. 6 (1941) p. 359.
 6 J. Moir & J. A. Leslie, Stereophonic reproduction of speech and music. *J. Brit. I.R.E.* 1951 Radio Convention.
 7 Harvey Fletcher, Speech and Hearing in Communication. Van Nostrand, 1953.
 8 R. Galambos & H. Davis, Response of single auditory nerve fibres to acoustic stimulation. *J. Neurophysiology* vol. 6 (1943) p. 39.
 9 I. C. Whitfield, Coding in the auditory nervous system. *Nature* 25th Feb. 1957, p. 756 et seq.
 10 L. A. Jeffress, A place theory of sound localization. *J. Comp. Physiol. Psychol.* vol. 41 (1948) p. 35.
 11 W. A. van Bergeijk, Variation on a theme of Békésy. A model of binaural interaction. *J.A.S.A.* vol. 34 (1948) p. 1431.
 12 A. D. Blumlein, BP 394325.
 13 H. A. M. Clark, G. F. Dutton & D. B. Vanderlyn, The "Stereosonic" recording and reproducing system. *Proc. I.E.E.* vol. 104 part B (1957) p. 417.
 14 W. S. Percival, Stereophonic reproduction with the aid of a control signal. EMI Research Laboratories Report RN/108 (1957).
 15 L. L. Young & R. Carhart, Time-intensity trading functions for pure tones and a high frequency a.m. signal. *J.A.S.A.* vol. 56 (1974) p.605. □

Sidebands as phasors *continued from page 54*

speech or music, with a corresponding sideband structure as exemplified by the left-hand side of Fig. 2(a) the audio output from the receiver would be bodily shifted $\pm 10\text{Hz}$ from the original. This would still give good "communication" quality speech. When, in a live news broadcast, a reporter from some remote part of the world sounds a little "rough" or "artificial" the explanation is probably due to a difference in frequency between the original and reinserted carriers, over an s.s.b. link.

It is worth noting that in suppressing the carrier in transmission, a source of interference, heterodyning, by adjacent carriers, disappears. Further, in the case of s.s.b., only half the bandwidth is used, enabling greater receiver selectivity to be employed. The absence of heterodyne interference from adjacent stations, twice the number of stations in the band, 100% efficiency in terms of the information content of the radiated energy, has made s.s.b. very popular for commercial and amateur usage.

Amplitude modulation is still the only system for broadcasting between

200kHz and 20MHz. The broadcasting of the very wasteful reference signal is necessary to enable the listener to use an elementary receiver requiring no sophisticated local oscillator and no skilled operating in the adjustment of a local oscillator. The increasing problems of heterodyne interference would be reduced if broadcast stations could use reduced (pilot) carrier working. The cost of the receiver and its operation will no longer be a factor with the potential use of specially designed integrated circuits in the future.

(To be continued)

References

1. Scroggie, M. G., "Phasor diagrams", Iliffe (1966), p.18.
 2. Hawker, P., "Synchronous detection in radio reception-1". *Wireless World*, September 1972, pp. 419-422.

Appendix

Mathematical expression of a.m. (for 100% modulation of a carrier, amplitude a , frequency f_0 , (angular frequency Ω_0), the modulating frequency f (angular frequency ω) is

$$a(1 + \sin\omega t)\sin\Omega_0 t$$

or in terms of frequency

$$a(1 + \sin 2\pi ft)\sin 2\pi f_0 t$$

This shows that the amplitude of the $a \sin 2\pi f_0 t$ (carrier) term is rising and falling between $2a$ and zero at the modulating frequency f . Rewriting, we have $a \sin \Omega t + a \sin \omega t \sin \Omega t$. Expanding the left-hand term (using the trig relation $\sin x \sin y = \frac{1}{2} \cos(x-y) - \frac{1}{2} \cos(x+y)$), this becomes $a \sin \Omega_0 t + a/2 \cos(\Omega_0 - \omega)t - a/2 \cos(\Omega_0 + \omega)t$.

We are left with the unmodulated carrier (sine) and two cos terms of frequencies f below and above the carrier frequency – the lower and upper sidebands. There is of course no difference (except phase) between cos and sine. Hence we have three sinusoids – the carrier, amplitude a , and the lower and upper sidebands, amplitude $\frac{1}{2}a$ – as depicted in Fig. 1(a).

We should still arrive at Fig. 1(a) had we started with any other appropriate expression, e.g. $a \sin \omega t \cos \Omega_0 t$ and the corresponding trig formula for the expansion. It all depends on the time we start (i.e. when $t=0$) and the relative phases of the sidebands with respect to the carrier at any instant. The phasor diagrams in the main text explain clearly the significance of the sideband phase as related to the carrier. □

A Scientific Computer — 6

Final program examples, tv interface and radio teleprinter interface

By J. H. Adams, M.Sc.

THE FINAL TWO programs in Table 18 were used to ease the design of active filters for the teleprinter interface. The filters are based around the LM3900 quad Norton amplifier i.c. and a low-pass version is shown in Fig. 24. The display in Fig. 25 shows a run of the first program which computes the resistor values required for a given gain, Q and fixed capacitor values. The program will intervene if the ratio of the capacitors is too low for correct operation, and when presenting the results it uses two graphic characters to enhance the appearance. New values for C₁ and C₂ may be entered repeatedly until the resistors are near enough to preferred values for the accuracy required.

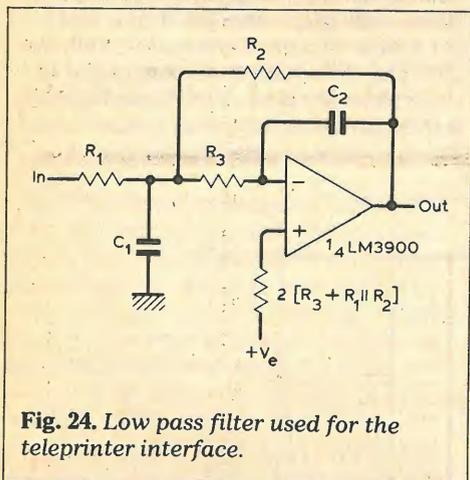


Fig. 24. Low pass filter used for the teleprinter interface.

```

002 PRINT " LOW PASS ANALYSIS"
003 PRINT " INPUT R1, R2, C1; C2 NOW . . . "
005 INPUT R S C D
006 AXIS 125 8
008 LET F=1
011 GOSUB 232
014 LET E=60 G -
017 GOSUB 232 -
020 LET G=G E +
023 IF G<0 THEN 32
024 LET Z=F LOG
026 PRINT "F ="F1, "HZ"
027 GRAPH G Z
028 LET F=F 10 RT *
030 GO 17
032 HALT
034 ERASE
036 GO 1
232 LET X=1E12 2 / PI / F / C /
235 LET Y=1E12 2 / PI / F / D /
238 LET A=X Y / R S * X / Y / - 1 - SQ
241 LET B=X R S + - Y / SQ - -
244 LET G=A B + ROOT REC LOG 20 *
247 RETURN


0000

004 PRINT " LOW PASS FILTER PROGRAM"
005 PRINT " INPUT GAIN + Q REQUIRED, CORNER FREQUENCY, C1 + C2"
020 LET W=2 PI * F *
023 LET C=C 1E12 /
026 LET D=D 1E12 /
029 LET S=1 K G / - ROOT 1 + 2 / Q / K / W / C / 1000 /
032 LET R=S A /
035 LET T=W C * SQ S * K * REC 1E06 /
038 PRINT "R1 ="R2, "k", R2 ="S, "k", R3 ="T, "k"
039 INPUT C D
040 GO 11
041 END
050 PRINT "REDUCE THE RATIO OF C2 TO C1. INPUT NEW VALUES NOW . . ."
051 GO 39
053 INPUT D
056 LET D=D 1E12 /
059 GO 29

00CB
    
```

Table 18. Two programs for designing active filters based on the LM3900.

Fig. 25. V.d.u. showing a computer run for the circuit in Fig. 24.

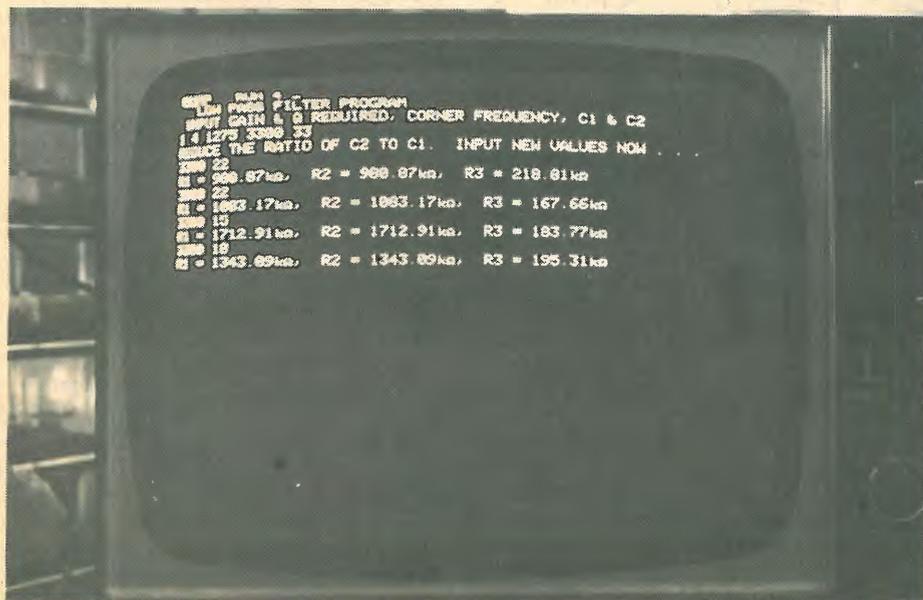

The second program can then be used to give a gain versus frequency plot of the filter's characteristics. In Fig. 24, R₃ is assumed to be equal to R₁. The program terminates when the gain falls below unity, but it may be re-run by pressing the space bar as described in part 4.

A specific tv interface

It was mentioned in part 2 that if a live tv chassis is used for the v.d.u., a mains isolation transformer is necessary. This expense can be avoided by using a television set such as the Ferguson or Ultra model 3845 which has a fully isolated power supply. A simple interface for this set is shown in Fig. 26. All of the connections are made to the tube base except for the sync. input. Resistor R₇₂ on the tv's p.c.b. is lifted at the end nearest to the back of the set, and a wire from the empty pad is taken to a changeover switch which connects the original sync, or that from the computer

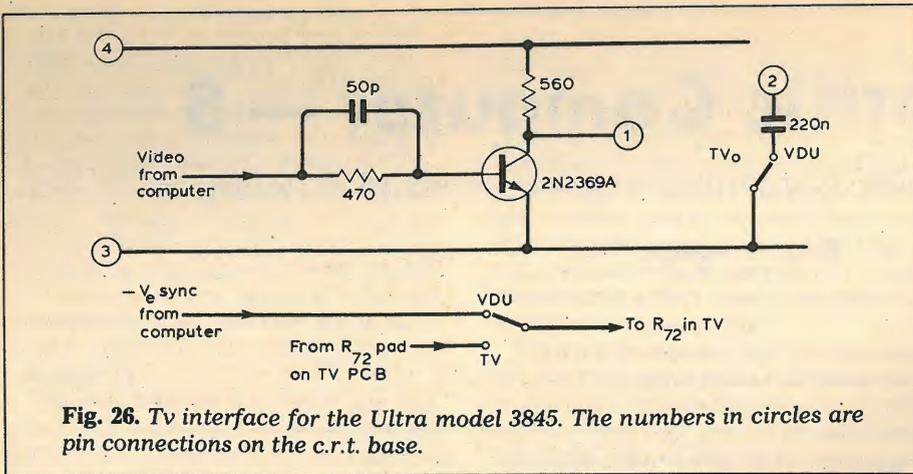


Fig. 26. Tv interface for the Ultra model 3845. The numbers in circles are pin connections on the c.r.t. base.

to the p.c.b. With negative going sync. supplied from the computer, a display should be obtained which, with the switch in the v.d.u. position, synchronises without any adjustment to either the horizontal or vertical holds. It is possible that the display will not completely fit onto the screen, but this can be rectified by the following alterations.

Loosen the polythene clamp which holds the scanning coils onto the neck of the tube and slide the plastic end of the width adjusting collar (this fits between the coils and the tube neck) to reduce the width of the picture. If the display is still too wide, connect a voltmeter between pins 3 and 4 on the tube base and adjust the preset resistor R_{69} which is just in front of the line time-base compartment. This sets the h.t.,

normally 11.3V, and should produce the required change with less than a one volt alteration. If the display is not horizontally centred, adjust the position of the core in the line oscillator coil (this can be found behind the line compartment nearer to the centre of the set than the "set h.t." preset). This must be done with a non-metallic tool.


If the television is tuned to a station whilst in use as a v.d.u., the tv picture may faintly modulate the display. This can be avoided by tuning off the station, unplugging the aerial or turning down the contrast control. If a brighter display is required, a higher supply voltage to the 2N2369A will be necessary. This can be supplied by the computer or from the 90V supply on pin 6 of the c.r.t. base. If the 90V is used, a potential divider must be connected because the maxi-

imum collector voltage of a 2N2369A is well below 90V. Whichever supply is chosen, the collector load should be increased proportionately from the 560Ω shown in this design.

Radio-teleprinter interface

One task for which this computer is well suited is the reception and transmission of radio teleprinter signals — RTTY. The system described here consists of hardware which converts f.s.k. (frequency shift keying) signals into digital levels, and software which is used to receive the serial stream of data, recognise the start of bytes and then frame, translate and display them. This software allows the Baud rate, the style of encoding and the code used to be controlled by the programmer.

The receiver should use a product detector or a b.f.o. so that the f.s.k. signals are available as two audio tones. The difference in frequency between the tones will depend upon the shift being used by the sender of the RTTY, but will usually range from 170 to 850 Hz. If the receiver's bandwidth can be reduced to this extent, the wanted/unwanted signal ratio will be improved and this will produce more reliable decoding. However, even with conventional bandwidths, the first two amplifiers in Fig. 27., which are connected as high and low-pass active filters with gains and Qs of one and a bandpass of approximately 1200 to 2100 Hz, will filter out the required tones to some extent. The filtered signal is then fed into a 565 phase locked loop. This i.c. compares the input signal with

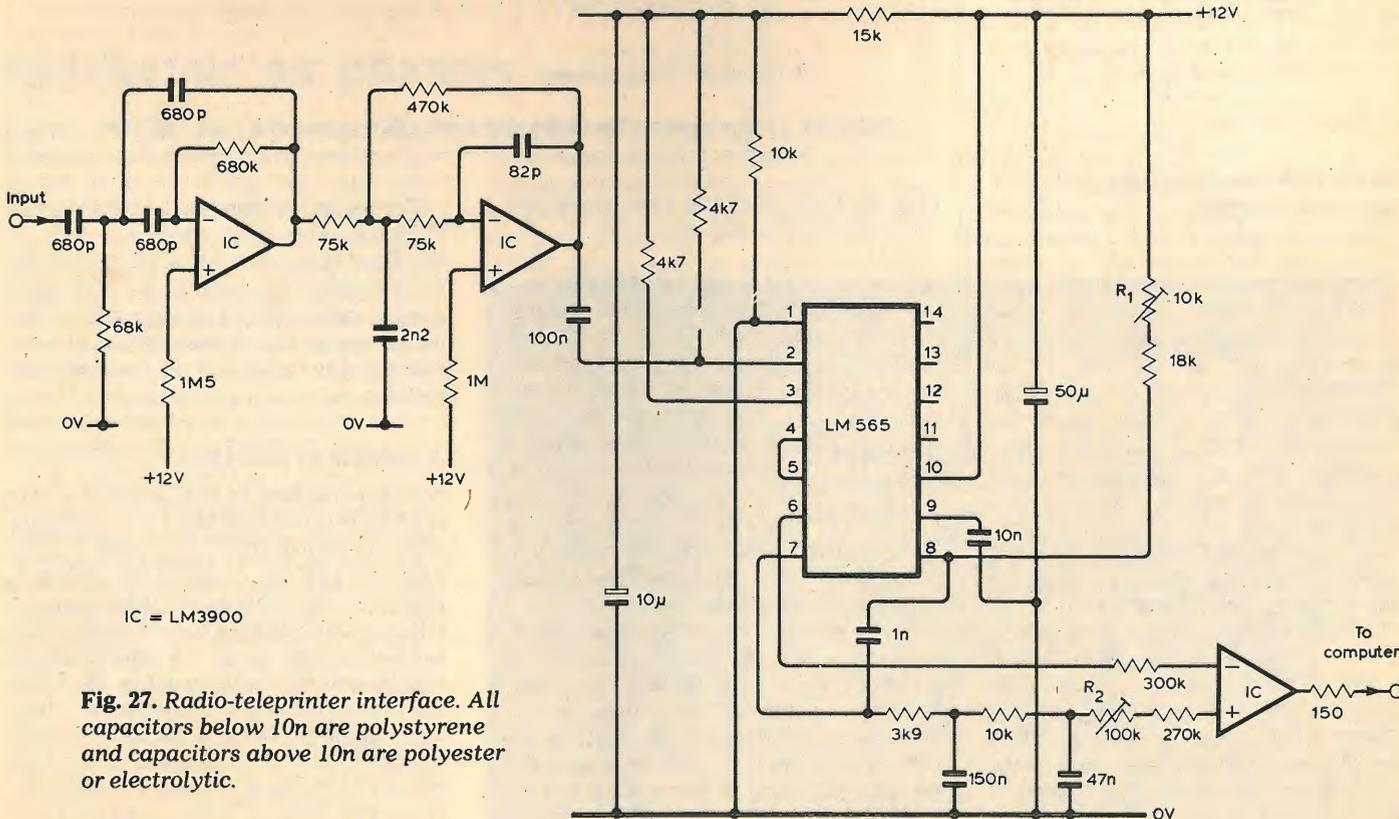

IC = LM3900

Fig. 27. Radio-teleprinter interface. All capacitors below 10n are polystyrene and capacitors above 10n are polyester or electrolytic.

1C00	11	4C	8D	21	8C	1C	DB	00	E6	04	2C	FA	CD	36	03	10
1C10	0B	0C	0E	04	2C	FC	0A	03	CD	36	03	5D	1C	F0	01	00
1C20	05	01	03	0C	34	10	17	4E	CD	36	03	6D	04	2E	03	10
1C30	10	EF	70	0F	0F	0F	2F	0C	1F	FE	05	2C	04	2E	03	10
1C40	C5	FE	04	20	04	2E	A0	10	BD	E5	95	6F	7E	E1	FE	EE
1C50	20	B4	FE	FF	2C	05	0C	04	03	1E	AD	12	13	FE	20	20
1C60	A5	7D	E6	3F	FE	37	D4	C4	03	7A	FE	88	2C	9E	CD	5D
1C70	03	1E	8D	FF												
1C80	EE	0B	11	15	EE	0A	17	01	18	06	19	13	02	04	1A	05
1C90	16	03	10	09	07	12	0C	EE	0D	0E	08	20	0F	EE	14	EE
1CA0	EE	2E	31	37	EE	EE	32	2D	2F	25	36	27	3F	EE	2B	39
1CB0	3D	3A	36	38	00	34	29	EE	2E	2C	64	2C	35	EE	35	EE

Table 19. RTTY software to be run at 1C00.

that of a v.c.o. which has been set at a frequency between the two tones. The result of this comparison will contain a low frequency component which after filtering is used to pull the oscillator to the frequency of the incoming tone. This voltage therefore switches in sympathy with the tones and is fed to a comparator which produces the digital output.

If reception only of RTTY is required, the oscillator's free-running frequency should be set at the midpoint of the active-filters pass band. Alternatively, when a complete terminal is used and standard frequencies are required, e.g. 1275 and 1445 Hz for a narrow shift, the oscillator is set to the midpoint of these frequencies. Before this adjustment is made, R₂ should be set so that with no input to the unit the output is on the point of changing state. With an input of 10mV at the required change-over frequency, R₁ should be set in the same way.

A 12V supply is available from the computer and the output of the unit should be fed, via the serial input buffer IC₅₃, to the line which feeds data bus line D₂.

A RTTY byte consists of a start bit, 5 data bits and 1½ stop bits. The software makes two checks 1ms apart for a start bit, to improve the noise immunity, and when it is successful in finding a start bit the data byte is read in, translated into ASCII and displayed. As there are two sets of characters in the RTTY, Murray code numbers and letters, the computer is set initially to letters and section 1C39 to 1C48 of the program, see Table 19, recognises and acts upon the Murray bytes to draw the correct ASCII byte for display. Because most teleprinters have more than the v.d.u.'s 64 characters per row, the section 1C5D to 1C72 ignores conventional carriage return and line feed bytes, but looks for spaces in the last eight character positions on a row. When one is found a new line is called which avoids the split words and short lines that occur with most v.d.u. systems. If this facility is not required, e.g. when receiving lines of tabulated data, alter 1C5F to 18, 1C9D and 1CBD to FF to obtain a new line with every carriage return received. Section 1C80 to 1CBF contains the look-up tables for converting letters (1C80 to 9F) and numbers (1CA0 to BF) from Murray to ASCII. Note that without the graphics option, the Murray £ appears as a \$. Tuning the receiver is most easily done by observing the output of the unit on an oscilloscope and

tuning for the cleanest display, although after some practice the ear is quite adept at picking out the correct point. If after correct tuning the display is random, this may be due to the transmission rate being other than 50 or 45.5 Baud. In this case the byte XX following the calling of the software time delay (CD 36 03 XX) must be altered to change the delay length, see part 4 for details of the sub-routine. The time delay has been set at 21ms as a compromise between 45.5 and 50 Baud by calling two delays with an XX of A0 between data bits, and three delays of 9B at the beginning to clear the start bit when recognised, and to return half way into the first data bit. Three times 9B plus the 10 time delay called between the two start bit checks equals 1½ times two A0 delays. If the code makes no sense when receiving at the correct Baud rate, it is probable that the sense of shift is reversed which causes the computer to read 1s as 0s and vice-versa. This can be corrected by changing sidebands on a receiver using a product detector, or by tuning the b.f.o. to the tones on the other side of zero beat. This problem is most easily recognised by characters appearing regularly but without spaces which suggests that the timing is correct, or if the test signals often transmitted by such stations are received as SYSSYSY . . . instead of RYRYRYRY. Narrow shift RTTY transmissions can usually be found between 14080 and 14100kHz during most of the day. □

Points arising

Unfortunately the following errors occurred in part 1 of the series. In the memory circuit of Fig.1. D₀-D₃ should read D₀-D₇. The 1k2 and 220Ω resistors on the base of Tr₁ in Fig. 2 should be transposed. For the kit, move R₂ to R₁ and fit a 220Ω in the R₂ position. Pin 15 of IC_{4,5} should be connected to 0V and to maintain the correct order for D₀-D₇, the two outputs from IC_{4,5} to IC₇ should be transposed. In the diagram on the left of Fig. 3, the NO arrow should be placed above the Read strobe box.

Two points have arisen from comments by constructors of the computer. Clock instability causing horizontal jitter on the picture can be eliminated by changing the 470Ω resistors at IC₂₈ to 1kΩ. Due to manufacturing tolerances in some 4528 monostables, the tape reader may not function.

If this occurs replace the 27kΩ resistor

connected to the 4528 with a 50kΩ preset, feed a 1V r.m.s. sine wave at 1800Hz into the tape reader and adjust the preset until the 4013 output which connects to the monostable is just changing state. The preset can then be replaced with the nearest preferred value resistor.

In conclusion

This section completes the scientific computer series. Due to a lack of space the firmware details have not been published but readers who wish to program their own r.o.ms can obtain a firmware list by sending a s.a.e. to this office.

We hope to support this design in the future with a floppy-disk drive and further practical programs. However, readers are invited to submit details of their own modifications or programs for publication.

We understand that John Adams is prepared to undertake the service or repair of computers built from a kit. Constructors experiencing difficulties should contact the author at 5 The Close, Radlett, Hertfordshire (Radlett 5723).

SIXTY YEARS AGO

After World War 1, amateur radio enthusiasts were left wondering for a time what was to happen to them. Then, as reported in the September 1919 issue, all pre-war licences were cancelled, preparatory to sweeping changes being introduced. In the present-day uncertainty about citizen's band, one hears remarks which could have applied to the situation of sixty years ago.

"... said an official of the General Post Office to a Daily Express representative, we are very careful to see that applicants are not simply out for amusement. Before the war we had a good deal of trouble with silly fools who apparently asked their best girls to tea and amused them by sending out 'S.O.S.' signals on their wireless sets. Now that there have been such improvements in the apparatus inanities of this kind will be very obstructive to messages of commercial importance."

All we have to say with regard to that statement is that any practical wireless man knows how the "fools" could be soon discovered and eliminated; no ban has been placed upon private motor cars simply because a "fool" occasionally runs over a pedestrian. As for amusement, we should like to know why people may not amuse themselves in any way they please, provided they do not infringe the liberties of other citizens or transgress against the law. The amateur is willing to be supervised and to conform to reasonable regulations; he is even willing to act as a policeman of the aether amongst his own class, but judging from the look of things there exists a desire to obliterate him altogether. America has bowed — stiffly, it is true — to Prohibition, but she did not agree to the proposal to stifle amateur wireless telegraphy. Why should you? What are the Wireless Clubs doing to defend their rights? It was the American amateurs themselves who won their day, though they interested their legislators in the matter. Have our Wireless Clubs knowledge of any Member of Parliament who will stand up for them in the House?

Selecting stabilizer thermistors for Wien bridge oscillators

by M. G. Salem Ph.D

Assessment of the output voltage of thermistor-stabilized Wien bridge oscillators very often depends upon cut-and-try methods. Similarly, the temperature coefficient relative to output amplitude is normally not effectively predicted. The general formula to determine these factors is provided here and is allied to a specific oscillator circuit. Selection details are also included, covering three "popular" thermistors.

In the Wien bridge oscillator shown in Fig. 1 an amplifier with two feedback loops is used, the feedback to the non-inverting input being in phase with the input only at the frequency $f_o = 1/(2\pi R_1 C_1)$. Negative feedback is independent of frequency but is arranged to increase as output increases, helping to maintain a constant output level. The final oscillator constitutes an amplifier with a gain of 3 and a constant amplitude sinewave output at a frequency determined as in the calculation above.

Amplitude stabilization is usually accomplished by making one of the negative feedback resistors sensitive to temperature and ensuring that the power dissipated by it is sufficient to raise its temperature well above the ambient level. Under such circumstances the resistance of the temperature-sensitive element will be determined by the oscillator output, with only slight dependence upon ambient temperature. The temperature-sensitive element may be a resistor or thermistor, in which case the

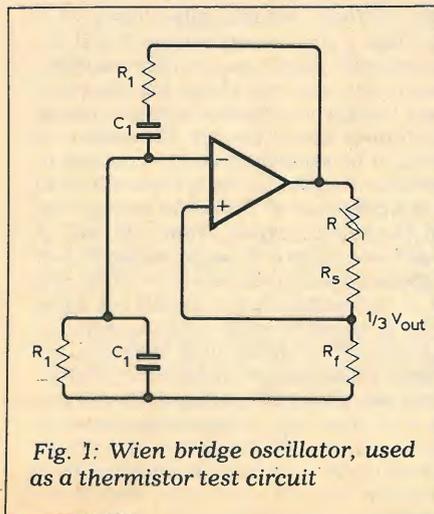


Fig. 1: Wien bridge oscillator, used as a thermistor test circuit

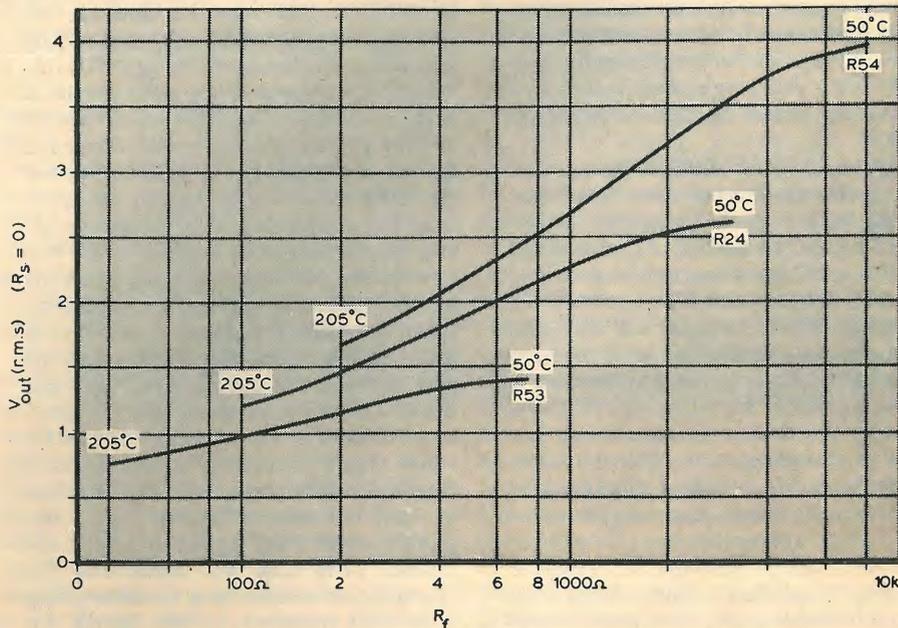


Fig. 2: graph showing V_{out} relative to R_f and operating temperature for three basic thermistor types

symbol R is used, indicating a negative temperature coefficient, or R_f indicating a positive temperature coefficient device or filament lamp.

If the open loop gain of such an oscillator is much larger than 3 the voltage fed back to the inverting input will be close to 1/3 of the output voltage, giving $R + R_s = R_f$. It is convenient to set R_s at zero. The resistance of a thermistor is given approximately by $R = A \exp(B/T)$ where A and B are thermistor constants and T is the thermistor temperature in degrees Kelvin. Temperature rise above the ambient level is approximately proportional to the power dissipated and it is usual for manufacturers to quote the dissipation coefficient, which we will term D, in mW/°C.

For a given value of R_f (and R_s if used) the steady-state resistance of the thermistor must be $R = 2R_f - R_s$. Temperature will be $T = B/\ln(R/A)$ degrees Kelvin and the temperature rise $\Delta T = T - T_a - 273$, where T_a is the ambient temperature in degrees C, typically 20°C. Power dissipated by the thermistor is $P = D\Delta/1000W$, current is $I = (P/R)$ in amps and output voltage is $3IR_f$. Combining these expressions gives V_o

Table 1: principal operating details of each thermistor.

Thermistors with low dissipation factor					
Type	R at 20°C	R at 220°C	I at 220°C	A	B
R53	5k	63	4.5mA	0.12	3100
R24	20k	150	7mA	0.17	3400
R54	50k	270	3.3mA	0.18	3650

All types: $T_{max} = 220^\circ C$ $P_{max} = 3mW$
 $D = 0.016mW/^\circ C$

$(r.m.s.) = 3R_f$

$$\sqrt{\left| \frac{D}{1000R} \left(\frac{B}{\ln(R/A)} - T_a - 273 \right) \right|}$$

$-T_a - 273$ where R is usually equal to $2R_f$.
 The relative temperature coefficient is $1/(2\Delta T)$ or $100/(2\Delta T)\%/^\circ C$, independent of thermistor or circuit. Such formulae should not prove daunting in these days of pocket calculators, but it may be worth remembering that $\ln(R/A) = 2.3 \log(R/A)$.

As a comparative test of the formula,

continued on page 95



When editing a message it helps to see what you're doing

. . . . and the Transtel VDU attachment does just that.

The operator can prepare messages on the VDU which acts as 'a window into the electronic memory' of the B315 ASR teleprinter. Messages can be altered instantly by deleting or inserting words or even whole paragraphs and the text re-justified to avoid broken words at the touch of a button.

The VDU can be used to prepare messages whilst previously recorded messages are sent to line, saving valuable time. The VDU can be used even when an incoming message is being received on the in-built printer.

- Microprocessor control.
- High quality dot matrix printout.
- Multicopy on standard paper
- Speeds up to 30 cps.
- 8000 character memory.
- Full word editing capability.
- Telex or Private Circuit operation.

TRANSTEL

Transtel Communications Limited

Mill Street, Slough, Berkshire SL2 5DD, England
Telephone: Slough (0753) 26955 Telex: 849384

8K ON BOARD MEMORY!

5K RAM, 3K ROM or 4K RAM, 4K ROM (link selectable). Kit supplied with 3K RAM, 3K ROM. System expandable for up to 32K memory.

2 KEYBOARDS!

56 Key alphanumeric keyboard for entering high level language plus 16 key Hex pad for easy entry of machine code.

GRAPHICS!

64 character graphics option — includes transistor symbols! Only £18.20 extra!

MEMORY MAPPED.

High resolution VDU circuitry using discrete TTL for extra flexibility. Has its own 2K memory to give 32 lines for 64 characters.

KANSAS CITY

low error rate tape interface.

2 MICROPROCESSORS

Z80 the powerful CPU with 158 instruction, including all 78 of the 8080, controls the MM57109 number cruncher. Functions include +, -, *, /, squares, roots, logs exponentials, trig functions, inverses, etc. Range 10^{-99} to 9×10^{99} to 8 figures plus 2 exponent digits.

EFFICIENT OPERATION

Why waste valuable memory on sub routines for numeric processing? The number cruncher handles everything internally!

RESIDENT BASIC

With extended mathematical capability. Only 2K memory used but more powerful than most 8K Basics!

1K MONITOR

Resident in EPROM

SINGLE BOARD DESIGN

Even keyboards and power supply circuitry on the superb quality double-sided plated through-hole PCB.

**COMPLETE
KIT**



Only
£275.00
+ VAT

Cabinet Size 19.0" x 15.7" x 3.3"

Television by courtesy of Rumbelows Ltd., price £58.62

POWERTRAN

**PS1 Comp 80.Z80 Based powerful scientific computer
Design being published in Wireless World — NOW!**

The kit for this outstandingly practical design by John Adams being published in a series of articles in Wireless World really is complete!

Included in the PS1 COMP 80 scientific computer kit is a professionally finished cabinet, fibre-glass double sided, plated-through-hole printed circuit board, 2 keyboards PCB mounted for ease of construction, IC sockets, high reliability metal oxide resistors, power supply using custom designed toroidal transformer, 2K Basic and 1K monitor in EPROMS and, of course, wire, nuts, bolts, etc.

**SYSTEM
EXPANSION
COMING
SHORTLY!**

e.g.
**8K RAM Board
8K ROM Board
Prom Programmer
Printer Interface
etc.
etc.**



Kit also available as separate packs; e.g. PCB, Keyboards, Cabinet, etc.

PCB size 16.0" x 12.5"

Value Added Tax not included in prices

PRICE STABILITY: Order with confidence! Irrespective of any price changes we will honour all prices in this advertisement until October 31st, 1979, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.

EXPORT ORDERS: No VAT. Postage charged at actual cost plus 50p handling and documentation.

U.K. ORDERS: Subject to 15% surcharge for VAT. NO charge is made for carriage. *Or current rate if changed.

SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.

UK Carriage FREE

POWERTRAN COMPUTERS

(a division of POWERTRAN ELECTRONICS)

PORTWAY INDUSTRIAL ESTATE
ANDOVER HANTS SP10 3NN

ANDOVER
(0264) 64455

Microcomputer interfaces

Connecting input and output equipment

by Ian H. Witten, M.A., C.Sc., Ph.D., M.I.E.E.

Department of Electrical Engineering Science, University of Essex.

THE SAME information can be represented in different ways, like marks on paper, or speech sounds. An interface is a connexion between one information representation and another. Computer interfaces convert between the computer's representation, namely electrical signals on the bus, and another representation – like dots of light on a display screen, or a musical note. There is an obvious distinction between input and output interfaces. (What is not obvious is which is which: it is conventional to look at things from the computer's point of view, so that "input" means from the outside world to the computer.)

Interfaces provide a means of communication between the outside world and the computer. Contrast this with buses¹ which provide communication within the computer system itself. Communication along a bus is entirely in the form of binary electrical signals. The information to be transmitted falls naturally into logically separate groups: address, data and control. The control part is the most interesting, and depends on the protocol which is adopted for information transfer. Each control line has a different purpose, and each is necessary if the protocol is to be observed. All in all, the subject of buses is well-defined and satisfyingly logical.

Interfaces are a different matter. They are closer to the real world, with all its variety and hazards. For a start, there is a multitude of different representations of information. To interface to a car engine, the throttle position, mixture control, engine speed and temperature, and ignition timing all need to be converted or controlled. Where does interfacing end and mechanical engineering begin? To interface to smells, we need to study chemistry. What about transmission of information between the computer and a remote device which converts it to another representation – is this part of the interface? There is no clean logical structure to the subject of interfacing; no neat division between the interface and the real world. Nevertheless, interfaces must be understood, designed, and built, and this is probably the most important single area in the application of microprocessors to man-machine communication. For example, lack of a cheap car engine interface and smell interface is the chief reason why automatic anti-pollution controls for

vehicle engines – which would benefit everyone by improving petrol consumption and reducing pollution – are not commonly used.

Simple i/p and o/p peripherals

The simplest output peripheral is a bank of on/off l.e.d.s (light-emitting diodes), which emit light when they conduct current. If eight l.e.d.s are provided, then one data word can be displayed. To keep the l.e.d.s alight, the data from the bus can either be latched into flip-flops, or periodically regenerated ("refreshed") by the processor. If l.e.d.s are refreshed twenty or more times a second for a millisecond or more each, an illusion of continuous illumination is achieved.

The input device corresponding to a bank of l.e.d.s is a row of switches, which are bi-stable devices, so latching is unnecessary. There is, however, a serious problem with contact bouncing. Figure 1 shows a typical waveform generated when a switch is changed from open to closed. The output does not change cleanly, as one might expect, but passes through a transition phase where it oscillates randomly. Unless appropriate precautions are taken, this will cause chaos if interfaced directly to a microprocessor. As with display refresh, the precautions can be taken in either hardware or software.


A hardware debouncing circuit is also shown in Fig. 1. It relies on a break-before-make switch action, so that no matter how unclean the switch output is as one contact is broken and as the

other is made, the "breaking" is completely finished before the "making" begins. Then, the first "make" spike which exceeds the threshold for logic 1 will activate the latch, and it will remain in the new state throughout the rest of the "making" disturbance. Software debouncing uses a different principle. The program waits for a specified time (usually around 20 ms) after a change in switch value is detected, before reading the switch and returning the new value.

A 7-segment display contains seven l.e.d. segments arranged so that the numerals can be shown, the lights being connected to the appropriate bits in the data word. Again, the data may either be latched, or refreshed by the processor. The problems of latching are highlighted when several banks of 7-segment displays are used. If there are six displays in a bank, $6 \times 7 = 42$ latches must be supplied for each. With several banks, a fair-sized store is needed to hold the latched bits. But the microcomputer already has a store – accessible to the processor – which can be used providing the processor is prepared to undertake to refresh the segments regularly. The input device corresponding to a 7-segment display is a thumbwheel.

Computer systems often need to communicate with devices with analogue electrical inputs and outputs. A d/a converter (digital-to-analogue) takes a binary signal and produces an output voltage whose size is determined by the input. Usually the relationship between output and input is linear, although non-linear (e.g. logarithmic) d/as do exist. Suppose the output range is 0-10V, and the input is 8 bits. Then an input of $\langle 00000001 \rangle$ will give $1 \times 10 / 256 = 0.04V$ output, $\langle 10000000 \rangle$ will give $128 \times 10 / 256 = 5V$ output, and so

Fig. 1 — Malformation of low-to-high edge produced by switch bounce, with anti-bounce circuit.

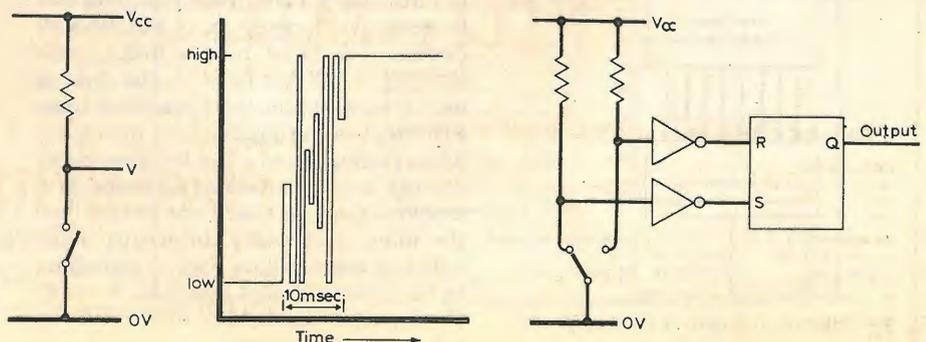

on. The use of an 8-bit input implies a precision of $1/256=0.4\%$. If more accuracy is required by the analogue signal, then more input bits must be used - 10 bits, 12 bits, or even 14 bits. An a/d converter (analogue-to-digital) performs the opposite conversion, taking as input an analogue voltage (say between 0 and 10V) and producing the corresponding binary value as output.

Figure 2 shows the circuit of a simple d/a. It works by converting each "1" bit in the input to a current with a weighting appropriate to the position of that bit in the word, summing the currents,

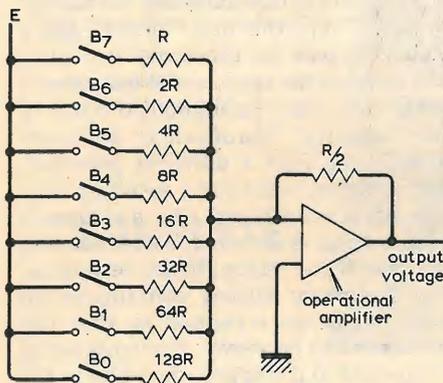


Fig. 2 - Principle of digital-to-analogue conversion, using weighted resistors.

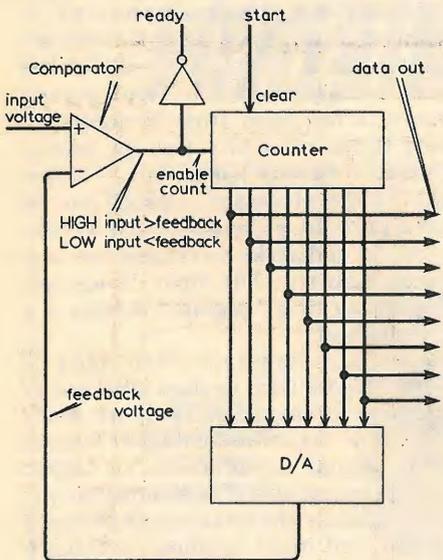


Fig. 3 - D-to-a converter in feedback loop makes a-to-d converter.

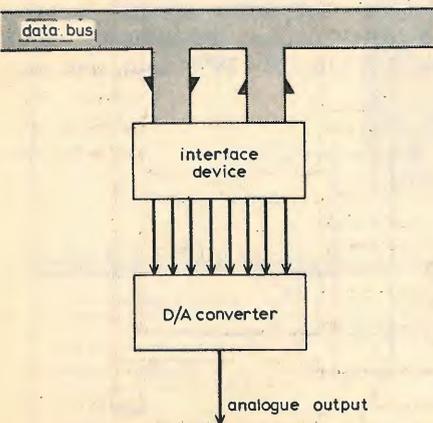


Fig. 4 - Interfacing d-to-a converter to a bus.

and converting the result back into a voltage. B_0 to B_7 are switches driven by the 8 bits of the input. When closed, they route the constant voltage E (say 10V) through a weighting resistor into an amplifier. The resistors are chosen to give each bit an appropriately large or small influence on the overall output. The operational amplifier sums the currents produced in the resistors, with the $R/2$ feedback resistor ensuring that the most significant bit (B_7) accounts for exactly half of the total analogue output range.

There are problems with the d/a of Fig. 2. Resistors do not come in binary-related values. Furthermore, if the overall accuracy is to be 0.4%, in accordance with the 8-bit input used, then the largest resistor must have 0.4% tolerance - a stringent requirement. There are better d/a circuits which circumvent these difficulties, but Fig. 2 shows the basic conversion principle.

The most common types of a/d converter are made from a d/a converter and a voltage comparator. Figure 3 shows one possibility, in which an 8-bit counter counts up from zero, its output being d/a converted continuously and compared with the input voltage. While it is smaller, the counter keeps counting. As soon as it exceeds the input voltage, counting is stopped and the "ready" line is activated to indicate that the conversion is finished.

Again, there are problems with the circuit. The inevitable transients during counting will produce terrible spikes on the d/a output. The most fundamental problem, however, is that the conversion takes a long time, especially if the input voltage is near the top of its range. Again, these difficulties can be overcome, but Fig. 3 illustrates one principle of a/d conversion.

Interface devices

The d/a converter in Fig. 4 is connected to a bus via an interface device. Since the bus is parallel, and the d/a converter needs a parallel input, why not connect it directly to the bus and dispense with the interface device? Consider the operations that must be performed:

- address decoding
- handling of read-write/address valid/ data accepted/reset lines
- data latching
- electrical buffering
- interrupt logic.

The first two operations were described in reference 1. (The "reset" control line is asserted at power-up, to initialise all devices attached to the bus.) Data latching is needed because the data is only present on the bus for a short time. Electrical buffering is often necessary when reading from a bus because many devices may be attached to it and precautions must be taken not to overload the lines electrically. Interrupt logic, which is essentially a way of signalling to the processor that new data is ready (for input) or needed (for output), is not covered in this course.

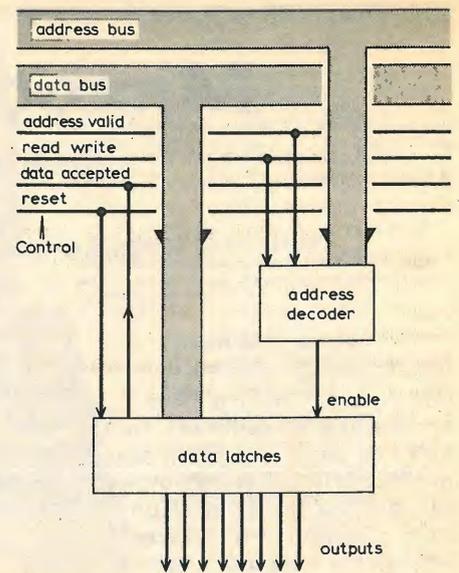


Fig. 5 - Simple output port.

An output interface that performs most of the tasks is shown in Fig. 5. The data latch assembly forms the basis of an interface device which goes under various names used by different manufacturers, such as "parallel output port", "PIA" (programmable interface adaptor), "VIA" (versatile interface adaptor), "PIO" (parallel input/output interface), "MILE" (microprocessor interface latch element). The address decoding function is not normally a part of the interface device, because with a 16-bit address bus, 32 extra pins would have to be provided on the integrated circuit - 16 for the address bus and 16 for the desired interface address - and circuits with lots of pins are difficult to manufacture and use.

Example. To drive a bank of six 7-segment displays, six separate parallel output ports could be used. A more elegant solution, which uses only two output ports, is shown in Fig. 6, where port 1 selects one of the six displays to be refreshed, while port 2 gives the data for the segments of that display. One of the six binary patterns

- 1000000
- 0100000
- 0010000
- 0001000
- 0000100
- 0000010

is written to port 1 to select just one of the displays, and the 7-segment code for that display is written to port 2. Care is taken to write zero to port 2 before changing the address, to prevent the transient appearance of the wrong pattern on the newly-selected display.

The simple output port of Fig. 5 is sometimes combined, on the same chip, with an input port. A more versatile interface allows each of the lines from the port to be programmed as an input or an output. A data direction register within the interface is used to indicate which are inputs and which are outputs. Each of the data direction register bits is

set to 0 if the corresponding line is to be an input and 1 if it is to be an output. For example, if the data direction register held <01010011> then lines L7, L5, L3, and L2 in Fig. 7 would be inputs while L6, L4, L1 and L0 would be outputs. The data direction register can be written by the processor at any time.

The interface device shown has three registers within it: each can be read or written by the processor. When the data register is written, the bits in it which correspond to outputs appear on their respective lines. When it is read, the states of those lines which are configured as inputs appear in their respective bits. The control and status register, when written, affects the functioning of the device and the state of the extra output bit shown in the figure. When read, it gives the status of the interface and of the extra input bit. These two extra bits can be used for a variety of purposes, including handshaking of data with the input/output device connected to the interface. The functions of the control and status register can be summarised as:

- [write] set/reset extra output bit
- enable/disable handshaking
- select data direction register or data register
- enable/disable interrupts (i.e. should the processor be informed automatically when new data is present?)
- [read] read extra input bit
- read interrupt status (i.e. is new data present?)

Fig. 8 shows the block diagram of a commercially available interface device, the Motorola PIA, which contains two separate, 8-bit input/output ports. This is a relatively simple device! The MOS Technology VIA has 16 registers and is more complex than many processor chips.

Serial transmission

Serial transmission is used with remote devices, in which case the data rate will be relatively low, because cramming all the data down one wire is inherently slower than using a parallel connexion with many wires. Such devices are usually character-oriented input/

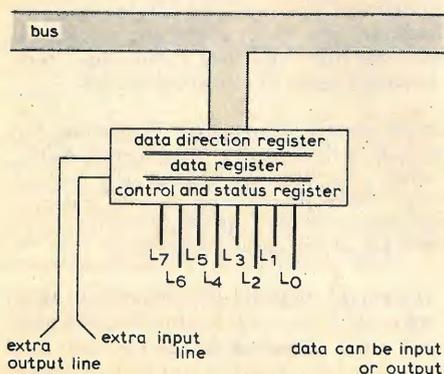


Fig. 7 - Input and output in same port.

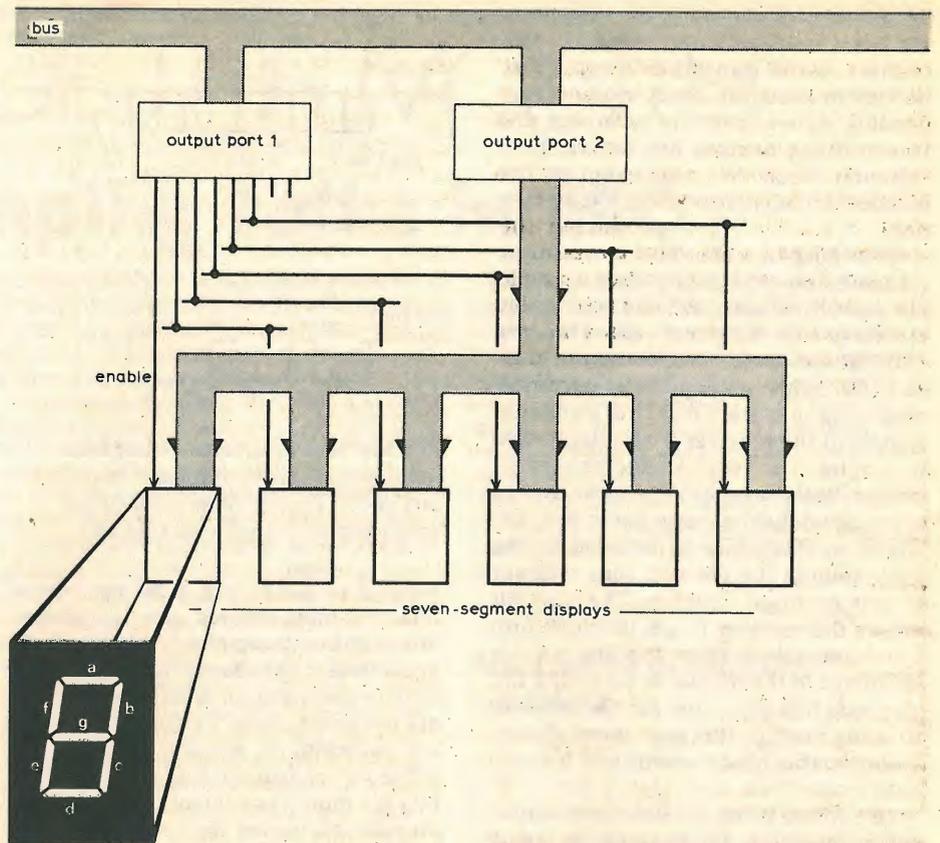


Fig. 6 - Enable line allows sequencing of 7-segment displays, using only two ports.

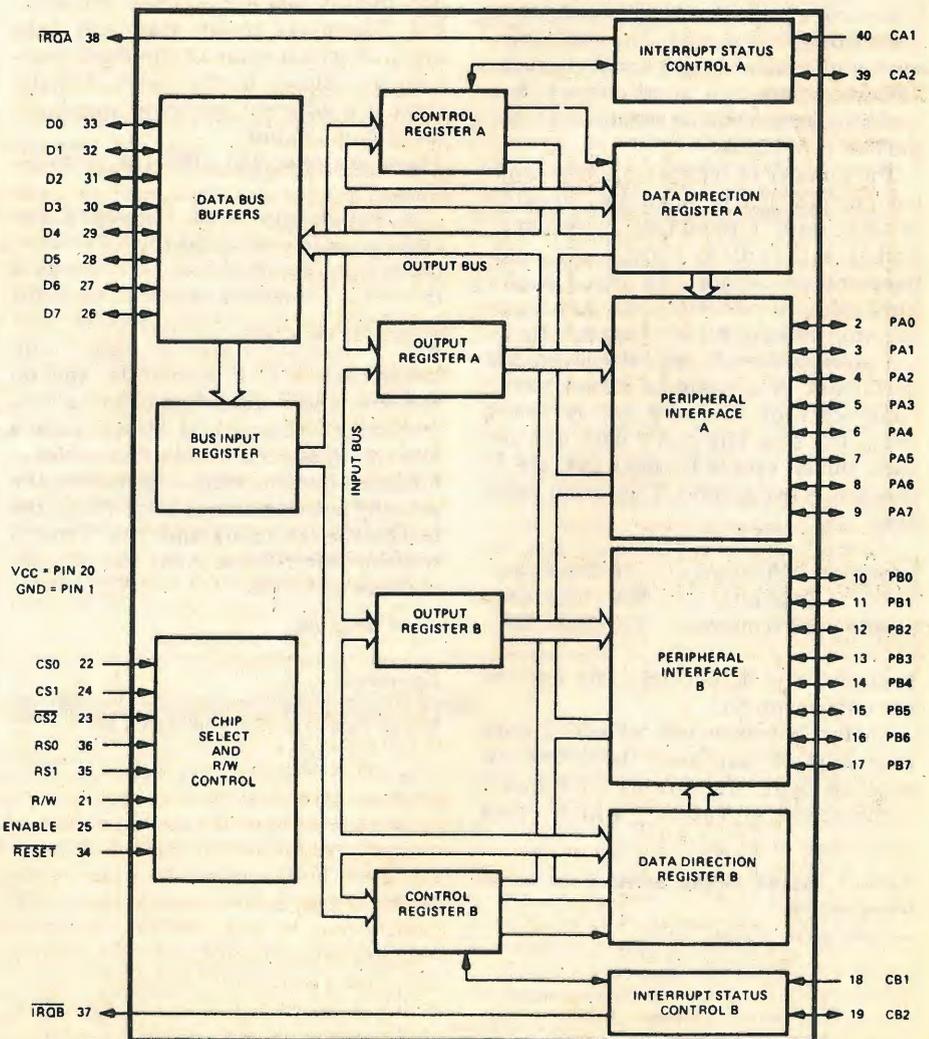


Fig. 8 - Specimen block diagram of p.i.a. - Motorola MC6820.

output terminals, such as teletypes, v.d.u.s (visual display units), and printers. Serial transmission can either be synchronous or asynchronous, depending on whether the receiving and transmitting devices are driven by a common clock. We will examine the protocol for asynchronous transmission only.

According to a standard convention, transmission of a serial data word is preceded by a "start bit" and terminated by one or two "stop bits". Start bits are LOW and stop bits HIGH, so a HIGH-to-LOW transition is guaranteed at the beginning of a start bit. This transition signals to the receiver that a data word is coming. The receiver and the transmitter will have clocks running at approximately the same rates but, because no clock line is included in the cable joining the devices, they will not be synchronised together. The start bit allows the receiver to get its clock into synchronisation. Then, the line state is examined in the middle of each data bit. The stop bits give time for the receiver to ready itself for the next word. Figure 9 shows the bits transmitted for one data word.

Of course, if the receiver gets out of synchronisation, for example by being switched on in the middle of a data word, it may mistake a HIGH-to-LOW transition between data bits for the beginning of the start bit. Then the first word would be misread. The same mistake could also occur subsequently; however, there is a good chance that synchronisation will be regained within the first few words.

The number of bits/second transmitted down the line is called the "bit rate" or "data rate". ("Baud rate" is also met, and is a technical term used with telecommunications systems. For the kind of transmission we are considering, the baud rate happens to be the same as the bit rate. However, the definition of a baud involves extra complications that are not relevant here.) If 2 stop bits and 8 data bits are used, the bit rate is 11 times the rate of characters per second. Typical bit rates are:

teletype	110 bits/sec	10 chars/sec
v.d.u.	9600 bits/sec	960 chars/sec
printer	1200 bits/sec	120 chars/sec

Note that the higher data-rate devices use only 1 stop bit.

So far, the principle of serial data transmission has been described. In practice there are various differences, summarised in Table 1, which often

Table 1. Some of the options for serial transmission.

stop bits	data bits	parity	bit rate	electrical
			110	
			300	
1	7	odd	600	voltage driven
			1200	
2	8	even	2400	current driven—20mA
			4800	current driven—60mA
			9600	

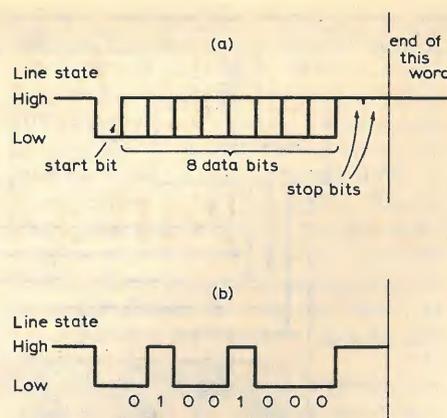


Fig. 9 - Serial transmission of 8-bit word, showing one start and two-stop bits at (a). Typical 8-bit word at (b) combined with start and stop bits.

confuse people trying to set up a serial link. We have already seen the alternatives of 1 or 2 stop bits. Similarly, there are different standards for the number of data bits used, of which 7 and 8 bits are the commonest. 7 bits (128 symbols) are sufficient to encode the alphabet, while for transmission of data words, 8 bits are more convenient. In either case an extra bit, called the "parity bit", can be added to make the parity (number of 1's in the transmission) even or odd, as an error-detection feature, so 8 or 9 information bits are actually transmitted. There are many standard data rates, of which some of the most common are shown in the Table. Finally, there are different electrical standards for driving the line.

There are over 150 different possibilities.

A commonly-used standard for coding alphabetic and numeric characters and symbols into 7-bit words is the ASCII (American Standard Code for Information Interchange) code. The ASCII characters include upper- and lower-case letters, numerals, special symbols, and a sprinkling of extra control codes with standard interpretations like "ht" (assists in formatting tables — horizontally tabulating — by moving the printing position along), "bel" (rings the bell on the terminal), and "etx" (end of transmission). These make the number of codes up to 128.

To be continued.

Reference

1. Witten, I. H., Computer buses, *Wireless World*, February 1979 and March 1979. □

LITERATURE RECEIVED

Report of study on workplace exposure to man-made mineral fibres, contains recommendations concerning inhalation of respirable fibres, etc. Report is available from HMSO, 49, High Holborn, London WC1V under title "Man-made Mineral Fibres" price 50p.

Catalogue of books on microcomputer matters called "Microdigital" from the "Microcomputer Bookshop", 25 Brunswick St., Liverpool L2 0BJ.

A general data booklet is available from IMF Electronics which is intended to explain the UHI surround-sound system, developed by the N.R.D.C. in collaboration with the BBC and IBA. Interested parties should write, requesting information on "Ambisonics" to IMF Electronics, Westbourne St., High Wycombe, Bucks HP112 2PZ.

A product summary of available "Glennite" piezoceramics can be obtained from Gulton Europe Ltd., The Hyde, Brighton, Sussex. This covers the company's range of lead zirconate titanate and lead metaniobate piezoceramics, which are available as thin sheets, bender elements, shaped elements and strain gauges.

Catalogue from H. A. Wainwright and Co. gives details of the full range of Fenwal temperature controls. H. A. Wainwright and Co. Ltd., 95 Farncombe St., Farncombe, Godalming, Surrey, GU7 3BA.

A brochure from Ferranti discusses the selection and use of the Uncommitted Logic Array (ULA). This is a family of bipolar l.s.i. chips, each containing an unconnected final stage. The brochure explains how the interconnection pattern can be arranged to convert the uncommitted chip into the required custom l.s.i. circuit. Ferranti Electronics Ltd., Fields New Rd., Chadderton, Oldham, OL9 8NP.

Illustrated catalogue of professional audio equipment from F.W.O. Bauch Ltd. Covers complete range of products under Studer, Revox, Neumann banners as well as many others. F.W.O. Bauch Ltd., 49 Theobald St., Borehamwood, Herts WD6 4RZ.

Latest technical information in the form of glossy brochures on the product range of Sony Broadcast, City Wall House, Basing View, Basingstoke, Hampshire RG21 2LA

Catalogue containing details of a range of products from abrasive paper to Zener diodes from Maplin Electronic Supplies Ltd., P.O. Box 3, Rayleigh, Essex. No price list supplied.

Shortform catalogue of microcomputer hardware plus list of books and software is available from New Bear Computing Store, 40 Bartholomew St., Newbury, Berks.

Information on transmitter "happenings" is contained in the IBA's "Engineering News" which covers activities in all UK regions. Engineering Information Service, Independent Broadcasting Authority, Crawley Court, Winchester, Hampshire SO21 2QA.

The Philips/Signetics data handbook, about 300 pages of technical information on bipolar and m.o.s. memories can be obtained from Mullard Ltd., Mullard House, Torrington Place, London, WC1E 7HD

NEWS OF THE MONTH

Anti-dumping talks in EEC

Mr John Nott, the Secretary of State for Industry, and Mr Cecil Parkinson, the Minister for Trade, visited Brussels on July 10 for talks with the EEC Commission on Community anti-dumping activities. At the meeting it was generally agreed that there was a need for streamlining the Community regulations and this would take place when they had implemented the changes recommended by the results of the recent world trade talks ** which included a modification of the General Agreement on Tariffs and Trade (GATT) dumping and subsidies code. The GATT anti-dumping code says that dumping occurs when a manufacturer sells goods at a lower price in an export market than in his home market.

Readers may remember that in the past the Japanese have been accused of dumping hi-fi and amateur radio equipment in UK markets (see p59, August 1977 issue — Amateur radio equipment survey) but this was apparently never proved — probably because of the problems encountered in obtaining the necessary facts and figures at the time (see

p68, September 1977 issue). Today, however, the Department of Trade has its own expert anti-dumping unit which advises UK industries on the formulation of anti-dumping cases to present to the Commission.

A spokesman for the D. of T., when asked about the Japanese export question, said that the Japanese were generally not identified as a source of dumping. Because their products had been cheap compared with British products of the same kind they had frequently been suspected of dumping, but investigators had to determine whether the reduced prices were due to dumping or manufacturing and other efficiencies. On the odd occasion when the Japanese had been found to be dumping, the price difference due to dumping was very much less than that due to efficiency. The figures used to assess whether dumping is occurring are obtained by taking into account all the normal price differences due to shipment, import duty, product style changes etc, but even then there are variations due to such things as exchange rates and material cost fluctuations.

Dumping which does occur involves only relatively small amounts of money and this can be and is normally controlled by a policy of import restraints. Government (counter-veil) subsidies are allowed on regional policy and unemployment grounds, but if these are applied only to export and not generally to the manufacturing industry, then these too can contribute to dumping.

** The talks have been taking place over the last five years but general agreement was reached shortly before the general election this year.

America to get British viewdata

An agreement between the US giant General Telephone and Electronics Corporation (GTE), and Insac Data Systems, the government-owned UK company, is expected to result in the US getting British viewdata later this summer. Under the terms of the agreement, GTE will initially be offering a limited public service for business users only but this is to be extended to residential users later.

Although Insac, which has a sole licence from the British Post Office to exploit Prestel-type systems in America, developed its viewdata service specifically to suit the US market, the end result is similar in operation to Prestel and therefore helps to encourage world-wide acceptance of the BPO standards. Exclusive US and Canadian rights to the Insac system have been granted to GTE and the company has also been given a US sub-licence to Prestel under Insac's Post Office licence. Initially, the aim is to test the market in the US. Publishing, finance, news and entertainment companies have already expressed interest in the service. GTE will concentrate on business and domestic markets while Insac offers the service to corporate and closed-user organisations who may have special software needs.

This news follows the successes earlier in the year when it was announced that the Post Office had sold its viewdata expertise to Switzerland, West Germany, the Netherlands and Hong Kong.

Electronics vital in transglobe expedition

On September 2 this year an expedition, headed by Sir Ranulph Fiennes, sets sail from London to start the first longitudinal circumnavigation of the globe — via the North and South Poles. As is usual in present-day expeditions of this kind, electronics is to play a vital role in ensuring the safety and comfort of the expedition team. Some 330 companies have sponsored the expedition and about 80% of these are British. Burndept, Racal, Ferranti and Sinclair are just a few of the electronics firms who have provided equipment for the journey.

The expedition team will use the latest pioneering equipment, ranging from shoes for walking on water, cardboard huts and motorised sledges to highly accurate watches, underwater cameras and diesel generators. Burndept Electronics (E.R.) have provided miniature ground-to-air emergency beacons which will be used for aircraft and supply drops and for pinpointing team positions in ice floes. Wherever possible they intend to use solar power equipment provided by Ferranti Ltd and in white-out conditions (when vision is impaired by weather and surroundings) they will use solar sensors made by Hawker Siddeley Dynamics Ltd.

Muirhead Data Communications Ltd have provided facsimile machines which will be operated both on the ship and at the ice bases and it is hoped that they will enable photographs to be sent back to the ship. R. H. Minns (Baluns) Ltd are supplying radio monitoring equipment for indicating imperfections in the antennae systems which the team will be relying upon. No man can go anywhere without a calculator these days so Sinclair Equipment International Ltd has supplied the team with pocket calculators

which are specially programmed for astro-navigation.

One of the most important aids that an exploration team can have is good communications and on this score the entire expedition will depend upon products produced by Racal. The group companies involved are Racal Communications Ltd, Racal Group Services Ltd, Racal Systems Ltd, and Racal Tacicom Ltd. They will provide communications equipment for use on land, with Land and Range Rovers, at sea, on the Benjamin Bowring, which is a polar research ship that will be used to transport the team, and in the air, from a De Havilland Twin Otter aircraft. Communications will also be provided on ice, between ice group members, and from ice bases back to a Royal Aircraft Establishment Cove. Most of this equipment will be expected to operate in temperatures as low as minus 80°F.

More home video machines at Berlin

Grundig will launch a new video cassette recording system at the Berlin Radio & Television Exhibition (24.8 to 2.9). Called video 2000, it has been jointly conceived with Philips as a European response to the recent Japanese video recorders, which now incidentally includes a new longitudinal machine from Toshiba.

Grundig say the cassettes, measuring 18.3×2.6×11cm, can be played both sides. They claim a substantial reduction in hourly tape cost and a total of eight hours playing time. Recording speed is 5.08 m/s with a tape speed of 2.44 cm/s.

The Toshiba system is a relative of the BASF longitudinal approach but whereas the original BASF proposal was to switch tape direction at the end of a longitudinal scan, the Toshiba machine uses an endless loop cartridge, the head stepping tracks after 100 metres of tape, travelling at 5.9 m/s. Toshiba say 200 tracks 40µm wide are contained on ½in wide tape, with a spacing of 10µm. The fixed-head approach of BASF, and now Toshiba, is expected to reduce mechanical complexity albeit with more complex though potentially cheaper signal processing circuitry.

The British exporter and the Japanese yen

As Britain joins the select group of petro-economies, spare a thought for the British exporter shouldering the burden of an increase in sterling of 31 per cent against the Japanese yen and 10 per cent against the deutschmark since the beginning of the year, according to the trade weighted index. The trade figures for the first five months of the year are witness to these deadening export pressures, showing a £1 billion deficit on the current account. Following this trend of undiluted pessimism, a Department of Industry Survey of the top UK exporting companies predicts a slowdown in export growth for the whole of 1979.

Imports have been rising in inverse proportion to exports as the strength of sterling continues to restrict volume growth. There are many advocates of the swings and roundabouts theory, who emphasize the beneficial effects of a strong currency in curbing inflation and lowering the prices of imported raw materials for end products. The larger companies and multi-nationals always have the advantage in this and most other situations, keeping trading within the privileged confines of the group, not having to bear the full brunt of competitors with weaker currencies.

Announcing Plessey's results for the year ended March 31, 1979, chairman Sir John Clark reported that the fall in other currencies relative to sterling had cost the Group more than £2 million in profits, and yet he still favours a strong currency. Over the same

period Racal reported that the upward movement in sterling had a £6 million impact on sales, but commenting on the military radio side of its operations a spokesman emphasized that though price was an important factor, it was by no means the only factor in determining sales. Asked about export expectations for the year, Pye of Cambridge stated that its first six months export turnover was up on the previous year but it was difficult to forecast the outcome of the second half with such variables as wages, fuel and currency fluctuations to consider. Centronics reported that exports were expected to stay at last year's level. Indications in the electronics industry are that export growth will be maintained over the year, though a decline is expected in many other industries.

Since 1977 Government has largely given up the attempt to give sterling some semblance of stability. In line with its ideal of a free market economy, the Conservative Government has stood behind or rather left alone the strong pound, quoting the example of other successful economies which have turned a strong currency to advantage. Indications are that the Government intends to follow through the relaxations in exchange control made in the budget. The dollar premium could go, freeing overseas investment, which might, though not necessarily, result in sterling declining against other currencies. Mrs Thatcher had also

indicated a willingness to consider membership of the European Monetary System, though this would be particularly awkward at a time when sterling is at such an unnatural level.

Britain is not alone in the currency battle. In June the New York Federal Reserve Bank and the West German Bundesbank spent \$2.5 billion to support the dollar against the deutschmark. Growth of the deutschmark has already severely distorted the European Monetary System particularly at the expense of the Belgian franc. Japan has been attempting to strengthen the yen, as inflation continues to bite into its growth rate. More recently the economy has been seeing a boom in domestic demand with the export benefits of a weaker currency taking time to filter through. The current level of advance orders from abroad indicates that there will be a sharp rise in exports over the remainder of the year, wiping out Japan's first quarter's current account deficit. This year has seen considerable pressure brought to bear on the Japanese to open up their markets to exporters. At the Tokyo Summit the right of UK telecommunications manufacturers to tender for Japanese contracts was due to be debated, since to date large contracts for corporations like the Nippon Telegraph and Telephone Corporation have only been open to Japanese manufacturers. The Inward Investment subgroup of the recent Japanese Import Promotion Mission are reported to have been impressed with the idea of manufacturing in the UK as a means of reducing exports without reducing the level of UK sales. The National Economic Development Council's report on the electronic consumer goods sector suggests that inward investment should be turned directly to the benefit of UK exporters by the formation of joint ventures, increasing the competitiveness of UK goods.

The response of British industry to low-price competition from abroad has been defensive so far, often withdrawing manufacture of those products threatened. The appreciation of sterling has made the problem more acute, but competition is not only fought on the price front, and the anti-inflationary force of a strong currency can be used to increase export volume.

Solar energy used in Nepal expedition

A team of explorers who have just returned from a four-month hovercraft expedition to open up the Kali Gandaka River in the West Nepalese Himalayas used solar-energy, battery-charging units to charge their film cameras, communications radios, engine starting, lighting and other electronics equipment. The films recorded were shown on the BBC2's World About Us programme on July 1.

Traditionally, the sun is the explorer's worst enemy but this time the solar cell units, supplied by Lucas Industries Ltd, enabled some of it, at least, to be tamed. Using the sun to recharge their batteries helped the exploration team to conserve valuable fuel. The

three Lucas panels shown in the picture, for example, are standard and supply a total of 13.6V at 650mA. Each panel contains 30 cells, each producing about 0.45V, and when connected in parallel their total current is almost 2 amps. In strong sunlight, such as exists in West Nepal, it takes about seven hours to completely recharge a typical car battery. Each panel weighs only about 2½kg and measures approximately 510 × 340 × 25mm.

The expedition's aim was to demonstrate that, using modern technology, a river route could open up to link remote communities with the medical facilities of the outside world.



Record firms not too worried about oil prices

Despite the fact that co-polymer, the petrochemical material used in the manufacture of records, has increased in price by about 400% over the last ten years, with large increases recently, record manufacturers do not appear to be too worried about the current increases in oil prices.

According to a spokesman at EMI, co-polymer cost £130 per ton in 1969, and at the end of June the same amount cost £500. Oil prices did have a direct effect on record production, he said, but manufacturers had to live with this. Mr Townsley, a director of Decca Records, held the same view but added that they had to be careful not to reduce the value of the product by making the record too thin. He did not know what the future held, as far as oil and record prices were concerned, but they were taking no special action at the present time. When asked whether record manufacturers would be looking for alternative materials for the product in the future, he said that this was "always on the books".

Houses discuss Post Office monopoly

The Post Office monopoly was the subject of discussion in both the House of Commons and the House of Lords recently.

In the House of Commons on June 25, the Industry Secretary, Sir Keith Joseph, said that he would not rule out the possibility of taking action to abolish the British Post Office's statutory monopoly, and during question time he joined MPs from both the Labour and Conservative parties in criticising PO efficiency. When Mr J. Bruce-Gardyne, Conservative MP for Knutsford, asked whether he would give his support in introducing a one-clause Bill to abolish the PO's statutory monopoly, Sir Keith said that he had "no plans for such initiative or response at the moment but would not like to rule it out".

At the House of Lords on May 23, Lord Torpichen raised a question relating to the Carter Report on the Post Office (see p51, September 1977 issue). His question was: "To

ask Her Majesty's Government whether any review of the Post Office telecommunications monopoly has taken place since the publication of the Carter Report in July 1977, and whether they plan to implement the recommendation in paragraph 63 of that report to relax the monopoly". The Minister of State for the Department of Industry, Viscount Trenchard, said in reply to this that the government were studying the scope for increasing competition in some areas now served by monopoly-nationalised industries. He confirmed that this included the Post Office telecommunications monopoly and the matter contained in the Carter Report. Thanking the minister for his reply, Lord Torpichen asked him if he could give the House some indication of when this would happen. Viscount Trenchard was unable to answer this question but said that the government regarded some of the matters in the Carter Report as having been outstanding for a long while. They were unaware of the need, both for morale and for other reasons, to clarify the atmosphere on these matters.

Lord Plant then asked the minister if he would bear in mind the urgent necessity to take into account the views of the workers in the telecommunications industry and the Post Office and to have consultations with them. Viscount Trenchard said that all concerned would be consulted.

Lord Wallace of Coslany, praising the Post Office's telecommunications system, suggested that it would be a most retrograde step to partially sell off such a prosperous organisation leaving "the not so remunerative parts to the postal services to stand at a loss with public expense involved and possibly higher charges". Despite interruption from several Lords, he then added, "It would be a damnable result for our British telecommunications system to be completely cast-rated, which is the policy of the Tory Party". To this Lord Trenchard said that the government was well aware of the dangers of taking parts away and leaving a part which was very difficult to run but he wished to assure Lord Wallace that because their object was efficiency this point would be taken into account. As the Carter Report had indicated, the Government believed that a little competition was able to be introduced.

When Lord Shinwell suggested that the transfer of Post Office liabilities should be considered as well as the transfer of assets, Lord Trenchard appeared to ignore the question at first and then added that he did not believe that efficiency was compatible with dogma. The Minister later agreed with Lord Orr-Ewing to bear in mind that a greater measure of competition amongst those who seek contracts from the Post Office would also be beneficial.

Returning to his original question, Lord Torpichen reminded the minister that the "so-called telephone interconnection industry is virtually denied to British firms by nature of the restrictions placed upon it by the British Post Office, and that quite a small liberalisation of this monopoly could possibly pay dividends both to Post Office workers and to British firms who would be able to export the products relating to the telephone system". The minister said that he would bear this in mind too.

US electronics sales up 15% in '78

American sales for electronic equipment, systems and components totalled \$64.9 billion (about £32.5 thousand million) in 1978, representing an increase of nearly 15% over the previous year, according to the 1979 Electronic Market Data Book***, which was published recently by the Electronic Industries Association. Over one third of the sales were for industrial electronic equipment, which had grown by 18% in the same period, and the consumer electronics, electronic components and communicating equipment sales had grown by about 15%, 14% and 12% respectively.

About 20% of the total sales of electronic products were exported during 1978, according to the EIA, which gave a trade surplus in these products of \$2.6 billion (about £1.3 thousand million) while the nation experienced an overall trade deficit of \$34 billion (about £17 thousand million). America's largest customer was Canada, which imported \$1.6 billion worth of electronic products, followed closely by the United Kingdom and West Germany who each imported \$1.2 billion. These three countries accounted for more than 30% of the US's electronic exports.

Forty-four percent of America's electronic

imports came from Japan who supplied the country with more than \$4.6 billion worth of electronic products. The second and third largest exporters of electronics to the US were Taiwan, with \$1.1 billion and Mexico, with almost \$800 million worth of products. Together, these three countries accounted for more than 60% of the electronic products brought into America.

Employment growth rate in the electronic industries was 99% in 1978, almost twice the growth-rate in overall US employment. This brought the total number of US workers in that field to more than 1.3 million.

***The Electronic Market Data Book may be obtained from the EIA Marketing Services Department, 2001 Eye Street, NW, Washington, D.C. 20006.

New s.s. radar for Irish airspace

Eurocontrol, the European Organization for the Safety of Air Navigation, has placed an order with Thomson-CSF for a secondary surveillance radar (s.s.r.) system to be installed at Woodcock Hill (Shannon), in Ireland. The contract, worth almost £640,000, covers the first phase of a programme to replace the dual-head 'SECAR' s.s.r. system installed by Eurocontrol in 1968, which supplies upper airspace radar data to Shannon Upper Area Control Centre (see p70, October 1978 issue).

The new secondary surveillance radar, which is expected to be bought into service in early 1981, will be the first of its kind to be used in Europe. For reliability, it will have duplicated electronics so that if one set should fail, the other can take over. In addition, the system has been designed for future use in the monopulse mode. To minimise problems arising from ground reflections, a new antenna with a sharp lower cut-off is to be fitted. An option in the contract covers the installation of a second s.s.r. head in a new building near Woodcock Hill.

Earth terminal brings Congress to American States

Earlier this year, the Cable Satellite Public Affairs Network (C-SPAN) in Georgia, inaugurated its first live television coverage of the US House of Representatives. A ten-metre diameter antenna, made by Scientific-Atlanta, at Fairfax, Virginia, has enabled television pictures and sound to be sent from the House chambers to 370 communities in 50 states. The signals are carried from the chambers to the earth terminal via a terrestrial microwave link and are then transmitted to the satellite for retransmission to the communities' cable tv systems.

International trade exhibition in Paris

A new international exhibition and forum, called Expansion Co-operation 1980-1990, is to be held at the Centre National des Industries et des Techniques, Paris, from June 9 to 15, 1980. Its purpose is to develop closer trade links between Western Europe, the Arab countries of the Middle East and member nations of the Organization of African Unity by helping in the search for outlets for agricultural and industrial products, consumer goods, works and services and to provide the contacts necessary for arranging financial and technical agreements for the development of local industries. Developing nations will also have the opportunity to

show off raw materials and other goods.

The exhibition is specifically Western European, and no exhibitors will be allowed from Eastern Europe or from Japan or the USA, though European branches of multinational companies will be permitted to exhibit. It is under the patronage of the French ministers of Foreign Affairs, Co-operation, Economy and External Commerce and of the presidents of the Federation of French Industries and the Paris Chamber of Commerce and Industry. IPC Business Press, publishers of *Wireless World*, will be ensuring a substantial British and German presence at the exhibition.


Fibre optic prices cut by almost 50%

Advances in cable manufacture and test techniques have resulted in Hewlett-Packard reducing the price of their 25 to 100m fibre optic connector and cable assemblies by as much as 47% on quantity orders. Even on small quantity orders, reductions range from 17 to 47%.

Hewlett Packard's components group manager, Ian Graham, pointed out that their new prices continue to include installed and tested connectors guaranteed to meet the

standard performance specifications. Another spokesman from the company told *Wireless World* that the price cuts partly reflected increased usage but were mainly the result of the improved techniques. He believed that Hewlett-Packard was one of the first companies to introduce such a deal but he assumed that other companies would also be offering a similar package. Cuts of this magnitude are likely to increase the use of optical fibres still further in some fields.

False alarms anger firemen because they tie up costly men and machines at times when lives could be endangered by a real blaze. Racal Recorders Ltd has introduced an advanced cassette recorder which will help to guard against this. Callstore cassettes, as they are called, have been installed at the Oxfordshire fire service headquarters, Kidlington, and can quickly replay an incoming telephone call at the same speed, or faster or slower, to make identification of the caller's voice much easier. The divisional officer at the Kidlington HQ, which has three Callstores, says that they will also help the monitoring of genuine calls because people in a panic have a tendency to speak too fast. Our picture shows the Callstore recorders installed in one of the HQ's control consoles. A 19in rack houses the drive unit (below the desk) which can take up to four cassette drives. Although the digital remote-control units are shown at the console they can be used up to 100m away from the drive unit. Tape speed is nominally 1½ in/s but this can be varied -50% to +20%. A message search facility is also included in the unit - at the beginning of each message an audio tone is recorded and these can be sensed on rewind and selected by reference to a seven-segment message counter.

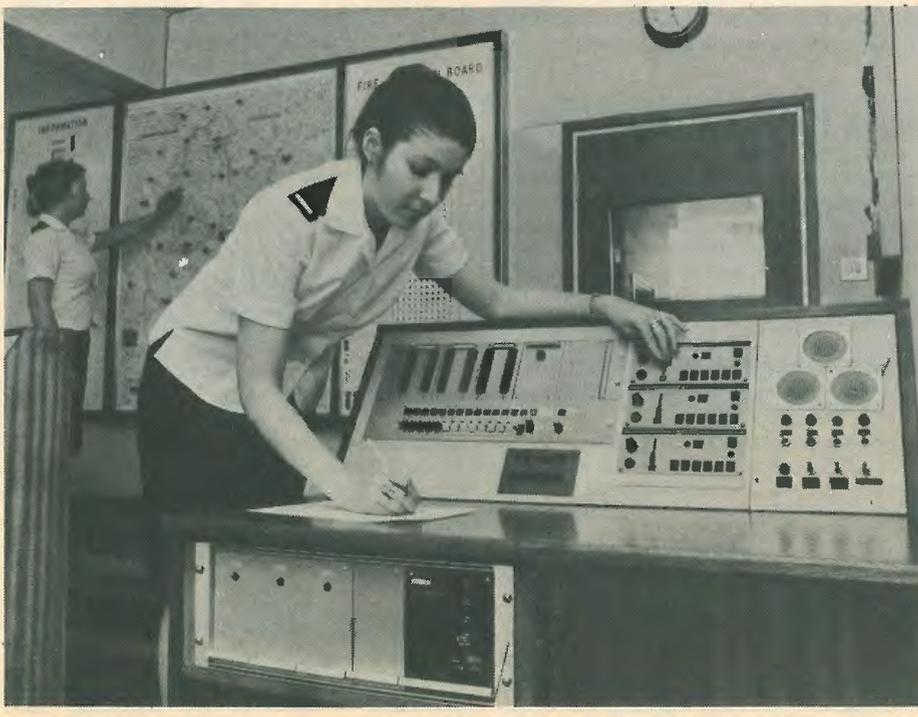

Israel solar heating for France

Miromit, an Israeli solar-heating equipment manufacturer, has been selected as "approved supplier" in France following a major international competition for the installation of sun-heating units in that country. The company was named as the only non-French firm among six, first prize winners in competition with 78 European solar equipment firms to supply solar energy for 3,000 residential units throughout France. Tests were conducted by the French Ministry of Environment with France's largest public building organization, L'Union Nationales des Federations De Organismes, H.L.M. Miromit will be awarded at least 500 of the solar installations. Users who purchase their collectors will receive subsidies from the French government, which is encouraging the use of solar energy for domestic hot water.

Radios protect wildlife from poachers

The Kenyan government's Ministry of Wildlife and Tourism, which is taking measures to stamp out poaching that is threatening some wildlife species with extinction, has placed a large order for v.h.f. communications equipment with Marconi Communication Systems Ltd.

The order, received through the Crown Agents for Oversea Governments and Administrations, is for sixteen base stations, fitted with RC730 transceivers, more than 350 outstations and mobiles, fitted with RC625 10-channel f.m. radiotelephones, and over 200 RC530 transportable lightweight radiotelephones. The portable transceivers will be used by foot patrols.

Marconi's contract is to completely re-equip and expand the country's present v.h.f. network to cover all their national parks and sanctuaries for both wildlife and fisheries.

NEWS IN BRIEF

Dr Thomas A. Mutch has been appointed (with effect from July 1, 1979) **NASA associate administrator for space science**. As professor of geological sciences at Brown University, Providence, R.I. he has been a major contributor to NASA science programs since 1969. Among other things he was a member of the Lunar Science Review Board from 1969 to 1973, leader of the lander imaging science team for the Viking project from 1969 to 1977, and is chairman of several NASA committees planning the post - Viking exploration of Mars.

Lionel Mudd, Head of the Engineering Support Department of the Research Division of Rediffusion Engineering Ltd, has been elected **President to the Society of Cable Television Engineers**, succeeding Chris Swires. Stanley Bell of the Radio Rentals' Relay Division is now Vice President. The society's Secretary is T. Hall, 10 Avenue Road, Dorridge, Solihull B93 8LD.

His Royal Highness, the Prince of Wales, has agreed to become **Vice-Patron of the Royal Institution**. There is a long tradition of Royal patronage going back to the foundation of the Institution in 1799, and past Princes of Wales have been Vice-Patrons since 1863.

CIRCUIT IDEAS


Differential rumble filter

A major problem with hi-fi reproduction from disc material is the large sub-audio signals known as rumble

A common solution to this problem is a steep cut filter below 50Hz, but unfortunately this also removes musical information.

Examination of the unwanted signals show that they are generated mainly by stylus movement in the vertical plane which produces stereo difference signals. Because purely vertical stylus signals will produce antiphase output voltages at the cartridge terminals, they can be removed by simply mixing the two channels. If the mixing is confined to frequencies below 100Hz, the mono bass output will have no effect on the stereo image.

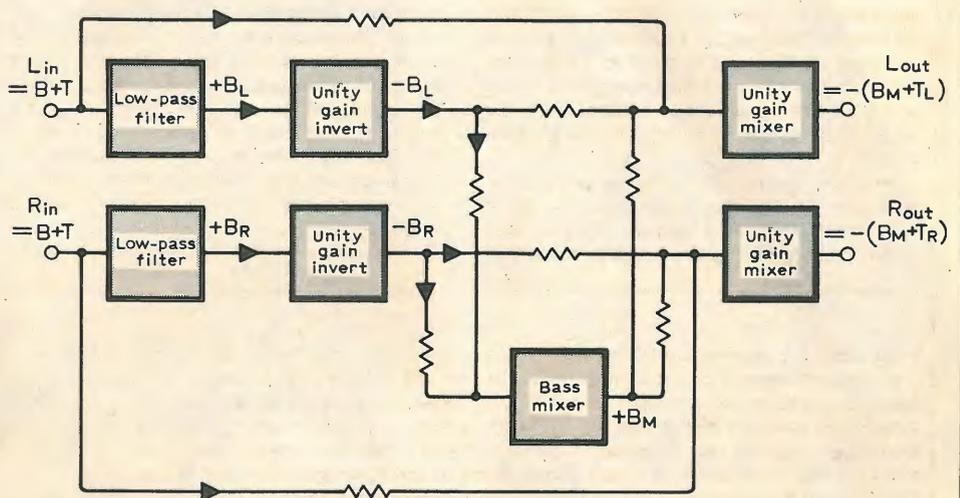The block diagram shows the basic system. The separate bass signals are simultaneously deducted from the



treble components, T_L and T_R , and the mono bass is also added to the treble components in the unity gain mixers, the outputs of which provide a stereo signal with a mono bass.


In the practical circuit the left channel, the filter and the inverter are in one stage around Tr_1 . A Butterworth filter with a 12dB/octave roll off is used, and the common bass mixer is formed by Tr_3 , R_{12} , R_{13} , R_{14} , and R_{15} .


Transistor Tr_2 forms the unity gain mixer and operates in the virtual earth mode. To minimise phase shift and reduce the component count, direct coupling is used throughout.

The circuit should be inserted between the pre-amp and power-amp, and should be driven from an impedance of not more than 10k Ω .

My prototype significantly reduces spurious low frequency signals, and has no effect on the musical bass. No difference can be detected in the level of bass with or without the unit in circuit, and the measured frequency response of the prototype extends from 15Hz to 30kHz at the -1dB points. Distortion measures less than 0.1% for outputs of less than 1V r.m.s.

J. P. Macaulay
Crawley
W. Sussex

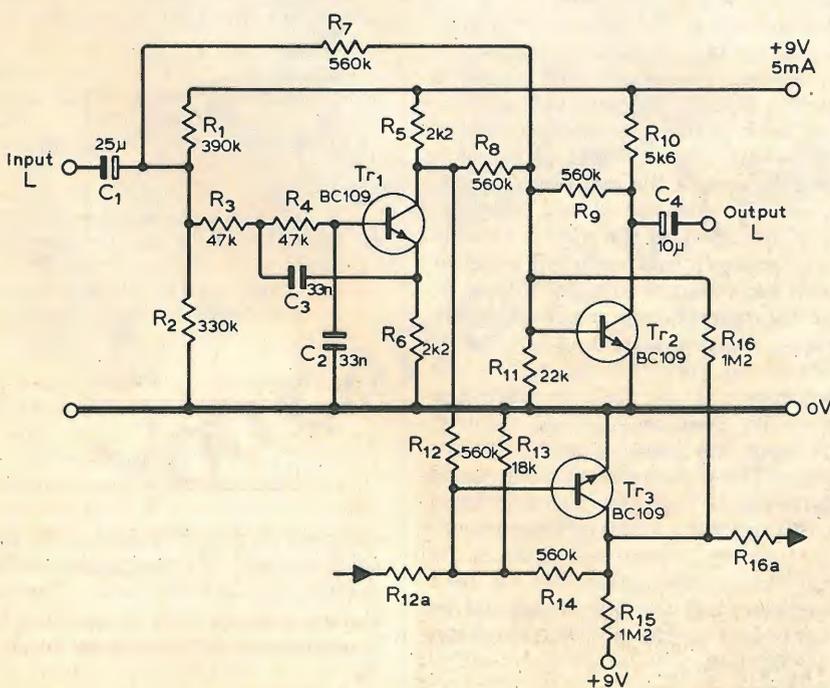

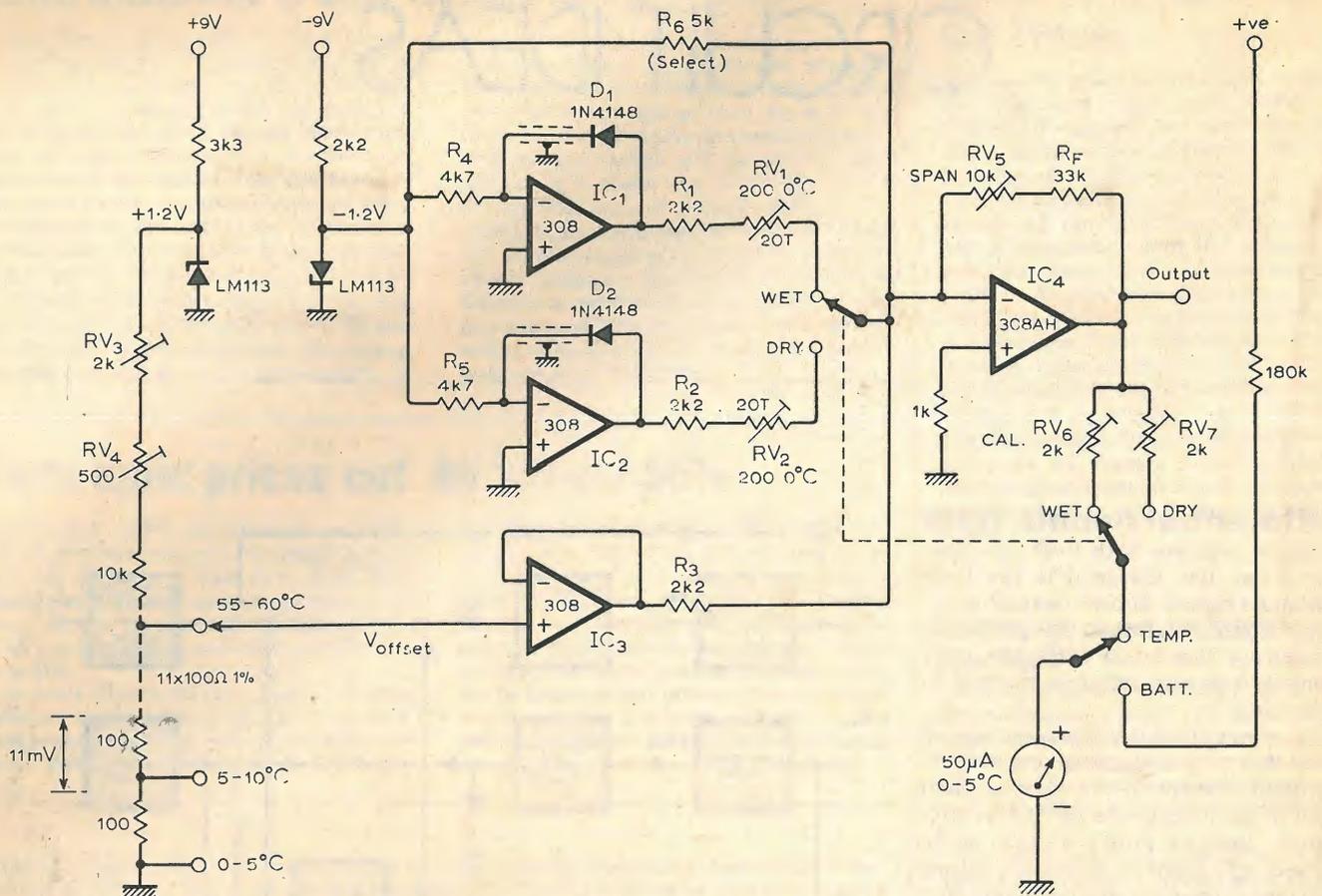

Portable wet and dry thermometer

By using two silicon diode sensors fed by a constant current source, this thermometer can make rapid temperature measurements from 0 to 60 deg C to within ±0.1 deg C. With the values shown the diode current is 1.2V/R₄ = 250µA. The output V is given by

$$-R_F \left[\frac{V_{OFFSET}}{R_3} + \frac{(V_{DO} - 2.2T)}{R_1} - \frac{1200}{R_6} \right] \text{mV}$$

and after calibration this reduces to

$$V_{OUT} = -\frac{R_F}{2k2} [2.2T - V_{OFFSET}] \text{mV}$$

where R_F is the total feedback resistance in kΩ, T is the temperature in deg C, V_{DO} is the diode voltage at 0 deg C in mV and V_{OFFSET} is the temperature range offset voltage in mV.


Diode D₁ is housed in a wet wick and aspirated by a small fan. To calibrate the circuit disconnect the meter and set RV₁ and RV₂ about midway. Adjust RV₃ and RV₄ so that 11 mV is developed across each of the 100Ω 1% resistors. Then, with the temperature offset switch in the 0 to 15 deg C position,

place both probes into an ice and water slurry. Connect a millivoltmeter to the output and adjust RV₁ and RV₂ for a null with the wet/dry selector switch in the appropriate position. If there is insufficient adjustment range replace R₆ with a slightly different value. Next, place both probes in an accurately known water temperature of about 4 deg C. Reconnect the meter and adjust RV₆ and RV₇ until the correct temperature is indicated on the meter. Finally, put the probes into a beaker of water of known temperature around 25 deg C, place the temperature range switch in the appropriate position and adjust RV₄ to obtain the correct reading. The last adjustment may be made in either the wet or dry position. Current drain is 4mA from the positive and negative supplies. The circuit maintains its stated accuracy if the batteries discharge from 9 to 6V, and if the ambient temperature rises to 45 deg C. High stability 1 or 2% metal oxide resistors should be used throughout and the circuit should be mounted in a case for protection against solar radiation.

K. D. Achleitner
Rondebosch
South Africa

L.e.d. flasher

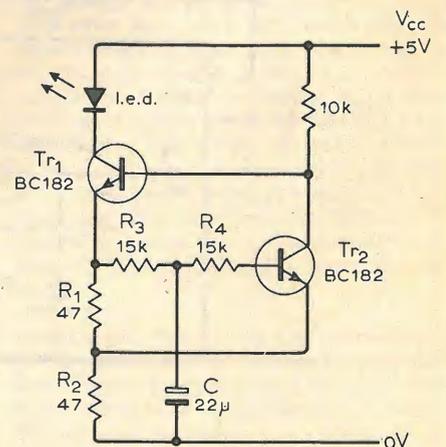If a flashing l.e.d. is required this circuit is simple and effective. A Schmitt trigger provides regenerative switching and R₁ gives the necessary charge/discharge bistable action as Tr₁ is



switched on and off. Resistors R₃ and R₄ set the on and off times respectively and the best ratio seems to be 2:1. The values shown achieve this at about 1.5 Hz. Brightness of the l.e.d. is set by R₁ and R₂.

W. C. Peaston
Gosta Green
Birmingham



You can see what you're doing


Telequipment's versatile CT71 Curve Tracer is the answer to your semiconductor testing problems. Insert two transistors into the test fixture, set the easy-to-use controls and you can make immediate comparison of characteristics at the flick of a switch. Display collector currents from 5nA to 200mA per division, and base or collector volts 0.1V to 100V/division. Test all types of transistors, FET's, diodes, thyristors and triacs easily, safely and accurately with the Telequipment CT71. Put it to the test, ask for a demonstration or our 36 page catalogue. It's quite free.

TELEQUIPMENT

Tektronix UK Ltd., PO Box 69, Coldharbour Lane, Harpenden, Herts. AL5 4UP.
Tel: Harpenden 63141.

For total Industrial Reaction

Visit the 12th
... and expanded ...

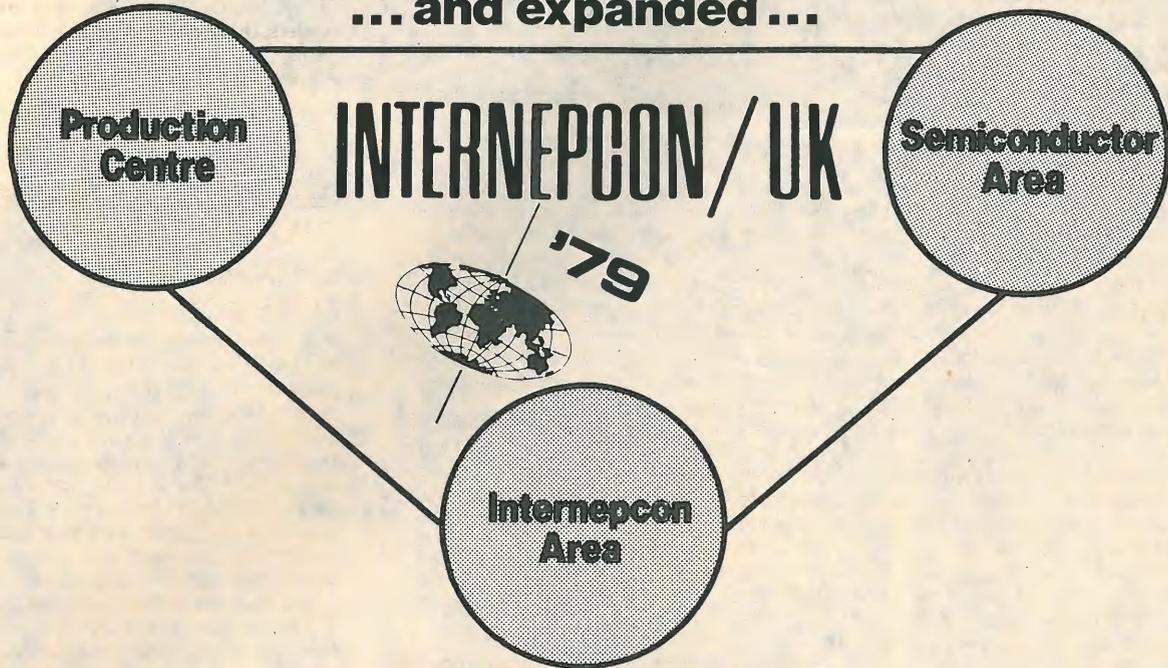

16-18 October 1979
Metropole Convention Centre & the Brighton Centre
Brighton, England

For the first time ... TWO NEW and separately situated display areas.

TWIN VENUES

Respected internationally for its professional service to the electronics industry, Internepcon takes on a new look this year by introducing two separately situated exhibition areas to cover all aspects of electronics production technology. More than 400 exhibits in the METROPOLE and BRIGHTON CENTRE will be displayed in three defined areas.

PRODUCTION CENTRE

Equipment for component insertion, milling, etching, drilling, soldering and cleaning will be displayed on large open stands in the BRIGHTON CENTRE.

SEMICONDUCTOR AREA

Devices, materials, test and production equipment, devoted to semiconductor development and production, occupying the ground floor of the METROPOLE HOTEL.

INTERNEPCON AREA

Six halls of components, materials, tools, hardware, PC's chemicals and production aids for the total electronics industry in the METROPOLE CONVENTION CENTRE.

CONFERENCE PROGRAMME

In addition to the Internepcon programme a special Semiconductor Conference will feature subject areas for Semiconductor Memories. Modern Packaging Methods. VLSI. Designing Systems with Microprocessors. LSI Testing. Semiconductors for Telecommunications. Static Elimination in Semiconductor Assemblies.

FOR ADVANCE INFORMATION COMPLETE AND RETURN THE COUPON - NOW

✂

Return to Kiver Communications S.A.
171/185 Ewell Road, Surbiton, Surrey, England
Telephone: 01-390-0281 Telex: 929837

Name _____

Company _____

Address _____

Please send FREE exhibition ticket
 Please provide conference programme

My prime interest will be Production Centre
 Semiconductor Area
 Internepcon Area

ENGINEERS ARE VICTIMS OF THE MARKET

Mr C. E. H. Benson ("The Solicitor's Lot", May letters) contrasts the "bellyaching" engineer with the professional outlook of solicitors, yet is very reticent about their status.

The Law Society, as the professional body for solicitors, provides its members with guidance on the fees to charge for professional work. It prohibits advertising for clientele, thus limiting competition*. A law graduate who aspired to qualifying as a solicitor, but was in temporary employment, recently explained to me that practical training in law was difficult to obtain because the permitted number of training positions with firms of solicitors was limited. Thus competition was further limited. Overall, The Law Society has resorted to the courts to protect its members from competition in legal work from outside the profession.

On the other hand, engineering is not a regulated profession. A qualified engineer has to have an aggregate of engineering education, training and responsible experience of not less than seven years to attain corporate membership of the Institution of Electrical Engineers, which has learned society status, and has to compete on the open market not only with other engineers but with many unqualified persons who trade and advertise as engineers. Because there is so much competition, skill and expertise cannot command economic rewards. Qualified engineers have to resort to the trade unions to prevent a continuing fall in living standards. Neither the engineer nor his institution can take action to prevent competition from unqualified persons.

The professional exercise of law differs from that of engineering. For example, last year The Law Society succeeded in obtaining a conviction (*The Guardian* 28 Jan. 1978) against Mr Barry Powell who runs a non-profit organisation called Assistance in Divorce. The complaint was that he had helped people prepare documents to get undefended divorces. The difference between the professional practice of engineering and law is that the former is subject to the caprices of market economics while the latter is the exercise of real power in the community.


R. E. George
Ilford
Essex

*But the Law Society itself advertises for the profession as a whole, pointing out, incidentally, that individual solicitors can be found in Yellow Pages. — Ed.

RELATIVITY AND TIME SIGNALS

Initially failing to grasp Dr Essen's point (October 1978 issue), I did not at the time give his article the attention it deserved. However, the "answers" to his problem which you have published, together with some inconsistencies in the recent BBC television programme "Einstein's Universe", have convinced me that it is high time we physicists awoke from our relativistic dreaming.

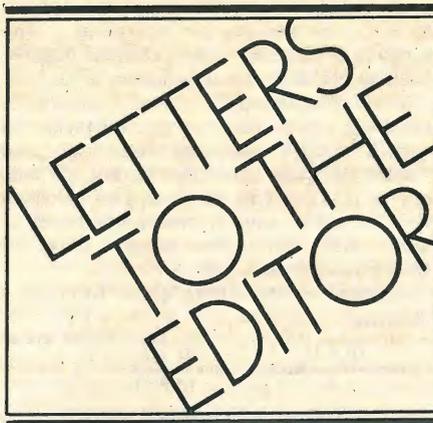It is implied in the April issue that this correspondence is regarded as being closed by Professor Fremlin's letter in that issue, but



I hope you will allow me space to pose the following extension to Professor Fremlin's scenario: consider a third party, "Observer", positioned along a line at right angles to that joining Sirius and Earth, far enough away that "Traveller" moves virtually at right angles to his line of sight. What is "Observer" to make of the proposed relativistic, or rather Lorentzian, caperings of "Traveller's" clock? Surely, he will see both "Traveller's" and "Stay at home's" clocks running always at the same rate.

A little more open-mindedness and a little less blind faith than has been revealed by this correspondence might reduce the present resemblance of physics to a moribund branch of theology.

W. T. Morris
Teddington
Middlesex

AUDIO KITS AND MODULES

I would most strongly like to endorse the comments of Ivor Abelson regarding reviews of kits and modules (May issue). Not one of the major electronics magazines even attempts to review such items, unless one absolutely pathetic attempt in April is to be counted (most of the samples never arrived so the magazine could not say very much).

The market in modules seems to be so cut-throat at present that unless the buyer wants something rather special which he is prepared to spend many hours building, it is pointless to build completely from scratch—designs and Veroboards etc. Hence anyone simply restoring disco units or building p.as (which I do for churches and halls etc.) naturally turns to the "module" or kit market. But although there are some excellent units, I've discovered, there are some very dodgy specimens as well and specifications are often misleading — especially when the figures only apply when the unit is chassis mounted with an elaborate p.s.u. (not supplied!). To take an example, the Klifco 30+30 amplifier module, if ordered with a stabilised p.s.u. comes complete with both mounted on a solid chassis which acts as heat sink. The BiPak modules do not. This, in practice, is a major consideration and makes a great difference to installation.

In more esoteric fields, kits are often the answer to component buying problems. I tried to build a magazine project recently just buying the parts from their cheapest sources and it took nearly 20 orders and cost a fortune in postage charges. I do, however, have the satisfaction of knowing that all the semiconductors are first grade,

that the capacitors in the power supply are computer grade and of recent manufacture, that the output and input socketry is both of the type I want (Standard jacks rather than DIN-plugs) and that the cabinet-work is very rugged. Some of the socketry supplied with kits that I have bought is better thrown away. With these kits it is not the electronics that form the bulk of the expense but the hardware, the socketry and the transformers and smoothing capacitors . . . and these can vary enormously in quality. In my opinion, there would be no greater service you could do for many of your non-professional readers, than reviewing and monitoring such items.

Hugh Bridge
Vauxhall
London SE11

OWNING CB SETS SHOULD BE AN OFFENCE

The mere mention of citizens' band radio in the technical press almost invariably precipitates heated correspondence. However, despite this, one fact seems to be generally overlooked — that certain people do use c.b. equipment within this country and as such are openly flouting the law of the land. Furthermore c.b. sets are both widely advertised and are readily available from several retailers, despite regulations which expressly forbid their importation. Unless action is taken soon it will be impossible to clear the 27MHz band if and when such a service is legally introduced on more suitable frequencies.

The activities of these c.b. pirate operators cannot possibly assist the efforts of many hardworking and responsible people who are at present campaigning for a recognised c.b. radio service within the United Kingdom. The apprehension of the 27MHz and other pirate operators is, however, seriously hampered by the present regulations, and I suggest that only by changing the law to make it an offence to possess radio transmitting equipment without the appropriate operating licences will the situation be readily brought under control.

J. Berry of Bristol (June letters) is mistaken in his belief that the "high and mighty" radio amateur is opposed to c.b. as such. The two services are fundamentally different and each has its part to play in a responsible society. The majority of radio amateurs do, however, take exception to the belief that c.b. should be introduced as an amateur band for unqualified operators, especially so since a radio amateur licence is readily available to any person who has sufficient interest to pass a simple examination.

W. B. Kendal G3GDU
Crawley
Sussex

RSGB TO CONTROL CB USERS?

I have no intention of entering into a discussion about the benefits that would result if we had a citizens' band in the UK; obviously very powerful financial interests are at work behind the scenes. But, as a member of the RSGB, I doubt the wisdom of compelling c.b. users to join this body as suggested by Mr

Berry in June letters. Although I feel that all radio amateurs should join the RSGB I would not dream of making it the law of the land that they should join.

And I do not follow Mr Berry's comment that if all c.b. users were members of the RSGB that body could ensure that they behaved properly on the air. The RSGB is not in my opinion the body to police either c.b. or the amateur bands. We have a government department charged with this task.

Of course the efficiency of the Home Office may fall soon as the Thatcher cuts take effect, but even then I would be loath to see the RSGB take over such jobs from the Government.

L. S. Chase
London SW2

ANOTHER CANADIAN ON C.B.

I felt it necessary to write in an effort to assure *Wireless World* readers that not all Canadians are cast in the same mould as Mr I. Switzer whose letter appeared under the heading "Ridiculous UK" in your May issue. Considering the rudeness of the opening paragraph one tends to suspect that the writer is at least to some extent lacking in manners and thus is hardly qualified to comment on what is socially desirable or acceptable.

Mr Switzer implies that as there are millions of citizens' band sets operating in North America it therefore must be a good thing and the rest of the world must follow. This theory that high numbers make anything desirable and good is a very interesting one. In North America we have millions of people with cancer, VD and all kinds of things that in my ignorance I thought were nasty.

One problem of c.b. is the tendency of some people to prattle away with no thought to logic or common courtesy; but then sometimes we get the same thing in a much older form of communication.

C. Henry
Pte Clare
Quebec, Canada

HAVERSINE FOR ANTENNA AIMING

Mr A. M. Stephenson (June letters) is in good company. It seems that few of my colleagues know what a haversine is. The haversine formula. $\text{hav } a = \text{hav } (b \sim c) + \text{hav } A \sin b \sin c$; together with its various rearrangements, is very useful for solving spherical triangles. ($b \sim c$) means the difference between b and c .

The angles of such a triangle might be referred to as A, B, and C and the sides opposite them as a , b and c . The sides are arcs of great circles and are expressed as the angles subtended by each arc at the centre of the sphere. If the radius of the sphere be known the distances along the arcs may be calculated. Since the geographical mile corresponds to one minute of arc along the equator it is convenient to leave a , b and c in angular form.

It might be thought that the haversine formula requires the use of a special calculator button but this is not so. $\text{Hav } \theta = \sin^2 \theta / 2$ and so any scientific calculator will do. The haversine is used to avoid ambiguity. $\text{Sin } 93^\circ$ entered on a calculator will offer 87° when arc

sin is pressed but $\text{sin } 93^\circ / 2$ squared and put through the reverse process returns one safely to 93° . The haversine is always positive because of this squaring process.

While considering the matter of haversines recently I realised that manipulation of $\sin^2 \theta / 2 = \frac{1}{2}(1 - \cos \theta)$ leads to an algorithm for finding square roots; that is, that $\sqrt{n} = \text{sin arc cos } (1 - 2n)$. This works well for values of $n < 1$. $\sqrt{375}$, say, is best considered as $100\sqrt{0.0375}$. Can anyone suggest a use for this amusing ornament?

Apropos of something quite different, I find that

$$\sqrt{n} = \frac{(n+1)}{2} \text{sin arc cos } \frac{(n-1)}{(n+1)}$$

This, apart from being a good party trick, is equally useless.

Perhaps it would be as well to state that the three points of the antenna aiming triangle are the points of transmission and reception and the north or south pole; whichever is convenient.

P. Wadham
Carshalton
Surrey

"SIMPLIFIED DISTORTION MEASUREMENTS"

The late Mr Butler's article on distortion measurements (April issue) emphasizes the need for great care in the theory and practice, particularly when the distortion is small. As an oldie with experience in the design of wideband feedback amplifiers at r.f. and a.f., I learnt in the difficult days of valves and transformers the value of single-point earths to avoid spurious feedback due to mutual impedances and also to use local feedback loops sparingly. Thirty years ago such techniques made possible stable wideband amplifiers with over 60dB loop feedback over portions of the passband, but in those days we had the advantage of using pin-boards and not printed circuits but lacked the simplification due to transistors and transformer-less designs. Can anybody suggest a better method for seeking trouble due to improper earthing than to provide input and output sockets that are mounted close together on a sheet of metal? Mr Moir has drawn attention to similar bad practices. Mr Butler almost insists on the use of an isolating transformer as a cure but surely this only prevents troubles in one section of the system and problems due to poor earth techniques may well be causing troubles in other sections, necessitating the use of more transformers. No, the real answer is to 'clean up' the earth connections and only use transformers when such cleaning up is impractical or the other advantages of transformers are utilized.

On our tv feedback amplifiers we used, and rejected, the self-oscillating method described because the additional feedback loop could produce instability and changes in performance. Consider Mr Butler's typical amplifier shown in Fig. 5. The feedback network has a gain of about 1/40 at the fundamental frequency and an effective Q of about 6, but as the author says "worse is to come". Assuming that the gain of the original amplifier was $40 \angle 0^\circ$ at the second harmonic frequency, the addition of the network will change this gain to about $40 - j5$. I think the amplifier designer would be justified in cal-

ling this a FB modification.

The RC parallel-T network is not strictly a three-terminal form of the Wien bridge since this bridge has two resistive arms. One can expect this T network to have a superior Q value — about twice — to the Wien bridge because in an equivalent bridge circuit all four arms contain RC combinations.

In the table associated with the bridged-T networks some of the information is wrong, as can be seen by applying Bartlett's Bisection Theorem to convert these networks to the lattice form. The sole reason for the presence of the resistance R is to compensate for the inductor loss resistance so that a complete null can be obtained. This is very important for low Q coils but the inclusion of these resistances alters the frequency of the null. In the case of the network using coupled coils the coefficient of inductive coupling is not unity and comes into the equation for the null frequency.

Thus from the foregoing and for other relevant reasons I think that it is more rewarding to spend effort on 'cleaning up' a driving oscillator than to use self-oscillating techniques. A useful network for nulling and the measurement of harmonics is as follows:

The use of a transformer can give a voltage gain which at low levels is always useful. The two halves of the centre-tapped winding are wound on together and high-permeability cores can be used. When $R = 5.6\omega_p L_1$ the relative output voltages are optimum and for the 2nd, 3rd, and 10th harmonics are respectively 0.5, 0.77, and 0.9. For spot frequency working this can easily be equalized. In practice the oscillator frequency and the variable resistor are trimmed to give the desired null. It is much easier to set this null than with a bridged-T network.

F. G. Clifford
Wynberg
South Africa

I fear that the article "Simplified distortion measurements" by the late Mr F. Butler (April issue) dismisses the Wien oscillator too hastily. It has many advantages — uncritical setting up, range changing etc. — so it deserves a second look.

The author gives the correct transfer function (with $K = 1$) for the network as

$$\frac{e}{E} = \frac{1}{3 + j(n - (1/n))}$$


but the oscillator takes the form of the Wien bridge, and the transfer function now becomes

$$H(n) = \frac{K}{2 + K + j(n(1/n))} \cdot \frac{K}{2 + K} = \frac{K}{2 + K} \cdot \frac{1}{1 + j(2 + K) \frac{n}{n_2 - 1}}$$

which is a notch filter with infinite attenuation at $n = 1$. Another form is

$$H(\omega) = \frac{S^2 + \omega^2}{S^2 + (2 + K)\omega S + \omega^2}$$

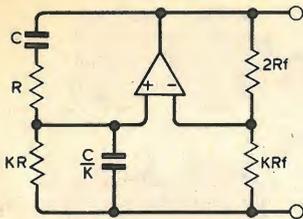and the position of the poles depends on the value of K . By a judicious choice of K the circuit could be used at the designed gain of the amplifier, or to make life easier at a high gain (e.g. with $K = 0.01$) which would result in amplified distortion and so easier measurements.



On the subject of the low cost digital frequency meter by Messrs Tooley and Whitfield (January and February) there may be difficulties for some constructors in a well thought-out design.

There is no specification of frequency response for most c.m.o.s. devices, only typical performances being given, and quite the slowest device I have met is the 4049 inverter which could, in one case, just manage 180kHz. The binary dividers also are suspect here. NAND or NOR gates are much quicker. Perhaps the easiest solution would be to change over to a crystal at 250kHz. Another point is the input capacitance of the device, which varies significantly with the rail voltage at 5V. Around this figure it is easy to trim the frequency by small variations to the rail voltage, whereas at about 12V the frequency becomes much less voltage dependent.

For a frequency meter I would recommend a separate voltage regulator for the oscillator circuit.

Tim Hartigan
Dublin 4
Republic of Ireland

SMALLER TELETXT RECEIVERS NEEDED?

I was interested to see the news item on the disappointing sales of teletxt tv receivers in the July issue and the editorial comment on this subject in the August issue.

I wonder if this is due to the fact that the manufacturers treat teletxt facilities as an exotic gimmick available only at the very top end of the market. I have enquired in several places about renting a set with teletxt but in order to have the decoder I would also have to lumber myself with an obscenely large 26-inch colour tv receiver, ultrasonic controls and a king's ransom in rental fees.

If teletxt were available on a compact tv set I would get one tomorrow and I'm sure a lot of other folk would too.

Charles G. Brewster
Brockley
London SE4

T.H.D. MEASUREMENT AND SOUND QUALITY

I was somewhat dismayed to see in your July issue, yet another article describing methods of measuring harmonic distortion of the order of 0.00001%. Mr Linsley Hood and the late Mr F. Butler (April issue) have produced two well thought-out methods of measuring t.h.d. but without questioning the validity and usefulness of the technique in the first place.

In the audio field percentages of distortion have very little relation to the purity of the perceived sound. Unless the figures are weighted in relation to the harmonic struc-

ture of the distortion, the results are misleading to say the least. An amplifier with a 'spikey' 1% crossover distortion will sound quite different from one with 1% second harmonic distortion. It is true that t.h.d. measurements at high frequencies can indicate problems of slewing - induced distortion but the correlation is not straightforward.

The present popularity of valve amplifiers, with their distortions in the 1% region, indicate that harmonic distortion alone is hardly a reliable criterion on which to judge the sonic performance of an amplifier. There are many other parameters in my estimation worthy of such detailed attention as is currently given to t.h.d., among which in power amplifiers are: dynamic power supply rejection; intermodulation with power supply ripple; variation of output impedance with (a) frequency, (b) output voltage; and dynamic shifting of the working point (dynamic offset).

I hope in future to see some designs that have a wider understanding of the mechanism of hearing.

Brian E. Powell
Crimson Elektrik
Leicester

involve stray capacitances and inductances in the vehicle's wiring loom. Clearly, then, the interference must be suppressed at source.

The problem in my case was quite severe and the cure was complete. The lead to the coil primary was screened, this being earthed inside the box containing the electronics. All the other leads leaving the box were decoupled with 0.1µF capacitors. The 12V supply to the coil and to the electronics was passed through a filter as shown in Fig. 2; this filter was housed in a separate die-cast box and mounted close to the coil.

The performance of this arrangement is excellent. Only a trace of impulse noise remains at the high frequency end of the medium-wave band, and this disappears when the aerial is retracted. A just audible trace of inverter noise (a rapidly modulated whistle) is apparent on weak long-wave signals.

The car radio used here is of the "cheap and cheerful" kind and is plagued by images and other spurious responses. The cure for this has been a two-section L-R low-pass filter at the base of the aerial, with a cut-off frequency of 1.8MHz. This also gives some relief from noise from other vehicles and neon display lighting.

T. H. Woolner
Harpenden
Herts

INTERFERENCE FROM ELECTRONIC IGNITION

Mr Whitehead does not describe the nature of the interference from which he suffers (May letters), but a note of my efforts may be of interest. My problem was both impulse noise from the discharging of the reservoir capacitor and whine from the inverter. My system is a home-built affair but is fairly representative in operation.

It is important to understand that the primary and secondary current in the ignition coil both pass through the wiring to the ignition switch and return to chassis through the battery (Fig. 1). Thus it is clear that a car radio will inevitably be connected to a noisy supply line. The actual route taken by the noise current may be quite complex and

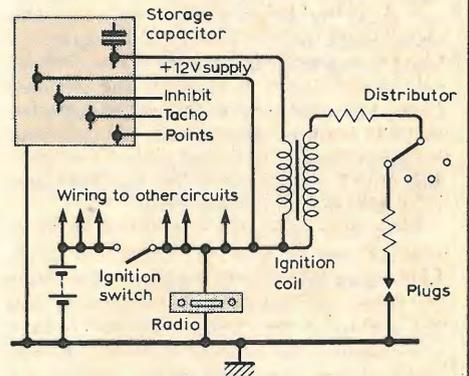


Fig. 1.

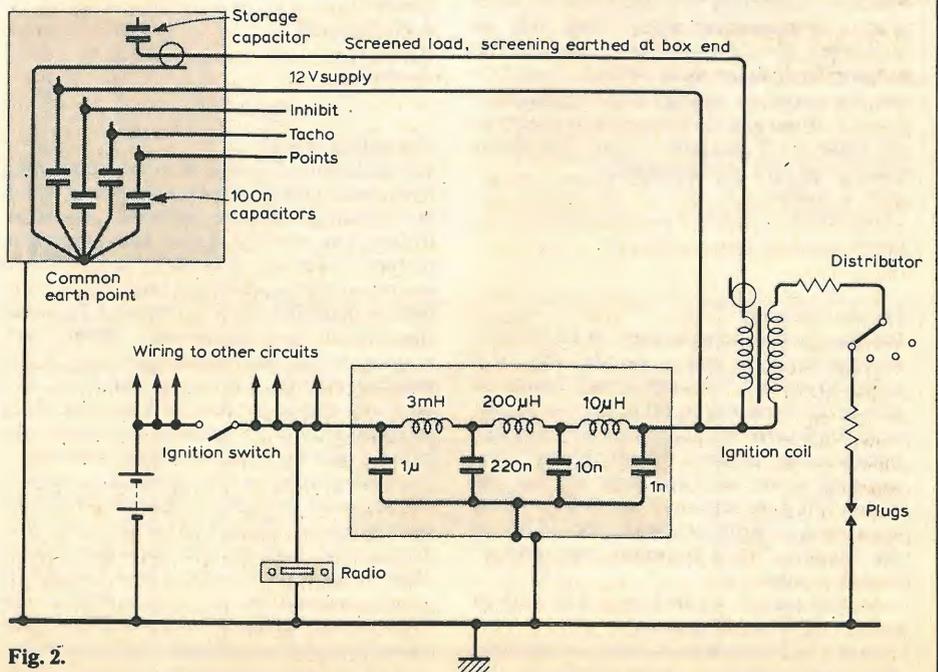


Fig. 2.

DISPLACEMENT CURRENT

Messrs Catt, Davidson and Walton are perhaps right to draw attention yet again to the importance the distributed nature of real capacitors can have in real circuits (December 1978 issue). Its significance in r.f. circuits is well-known and obviously it has some slightly unexpected subtleties in high-speed pulse circuits. But I cannot see how they can claim to have excised displacement current from Electromagnetic Theory – or in their case circuit theory – in any useful way.

To begin with, Kirchhoff's "Laws" apply to ideal circuits of zero physical extent described by simple mathematical relationships between their terminal voltages and currents. No assumptions are made about their physical nature, nor is the concept of "displacement current" necessary for the development of all the richness of modern circuit theory from these basic assumptions. Nor is there any doubt about the practical usefulness of the resulting theory, for example, in successfully designing high-performance filters.

If one must, for the sake of peace of mind, equate the terminal current of a capacitor with "... a mathematical manipulation of the electric field E between the capacitor plates" all well and good, and no harm will come provided the limits of the approximations necessary are always borne in mind; for example, that the dimensions of the capacitor must be small compared with the wavelength of the electrical disturbance being considered. But where is the conceptual improvement in equating the terminal current to what must in the end be a mathematical manipulation of the electric and magnetic fields associated with a transmission line? Especially when the manipulations involved are a lot more difficult.

If, as they claim, the concept of displacement current permits the retention of Kirchhoff's laws, does their "excision" of it throw out those too? And if so, what analytical tools are left to us for circuit analysis? If their transmission-line concept replaces displacement current, then how so? For there is still no closed path in which current can flow.

In short, are we to regard this article as a warning to beware of transmission-line effects in capacitors at frequencies (or pulse widths or risetimes) where they may be important, and can we therefore take the philosophical claims with a pinch of salt? Or are we asked to change the fundamental basis of circuit and electromagnetic theory as we know it? If the latter, I find the claims made to be very unconvincing.

John L. Haine,
Chelmsford,
Essex.

The authors reply:

We find the second paragraph of Dr Haine's letter ambiguous, and so cannot reply to it except to say that "modern circuit theory" is rich, in the same way as other tall stories are rich. High-performance filters are not designed using "modern circuit theory", because inductors and capacitors are not designed using theory; they are cobbled in a haphazard, experimental way. Try talking to the "experts" in a company "designing" chokes or capacitors.

As with para. 2, we find para. 3 is back to front, or at least ambiguous.

Para 4. The answer is, yes. Traditional analytical tools have been useful in the

setting and passing of examinations, but not in practical engineering problems; emphatically not in the interconnection of high speed (Ins) logic, where they have created havoc, leading to the abandonment of virtually all such projects.

Para. 5. You are asked to change the fundamental basis of circuit and electromagnetic theory as we know it. The need to successfully assemble high speed logic systems forces us to abandon the slovenly mess which has masqueraded as electromagnetic theory for fifty years, and build a sound theory from the ground up. The first casualty is displacement current, the bastard issue of a marriage between ignorance and nonsense. We must clear away the rubble before we begin to build.

"Our electrical theory has grown like a ramshackle farmhouse which has been added to, and improved, by the additions of successive tenants to satisfy their momentary needs, and with little regard for the future. We regard it with affection. We have grown used to the leaks in the roof. . . . But our haphazard house cannot survive for ever, and it must ultimately be replaced by a successor whose beauty is of structure rather than of sentiment." – Intermediate Electrical Theory, by H. W. Heckstall-Smith, Dent, 1932, page 283.

A lot more sludge has collected since 1935. We must dredge deep, through a century of sycophancy.

I. Catt, M. F. Davison, D. S. Walton.

DISAPPEARING MAGNET

May I take Epsilon's problem of the magnetic sphere (December 1978, page 69) a little further and ask what is the external field if the last plug is later removed? The answer is that the field remains zero! To see why, one simply considers the energy required to push the last plug into place. Since, after you have done this, there is no magnetic field inside or outside the sphere, the energy involved must be that required completely to demagnetize the whole structure. Consequently when it is disassembled, the pieces will no longer be magnets.

J. Middlehurst
Sydney
Australia

The author replies:

Mr Middlehurst poses a most interesting extension to the original problem, one which is difficult to discuss with any precision unless the coercivity of the magnetic material is known. (Coercivity is the H field in ampere turns per metre required to completely demagnetize a specimen.) To avoid this difficulty it is convenient to replace each magnet by an equivalent solenoid. If the original magnet were long and thin, this solenoid simply consists of a current sheet wrapped around the surface. The sphere can now be built up as in the original problem.

Starting with the first solenoid, as soon as the second is brought up against it there will be a repulsive force. Furthermore, the currents in the two sides that buck one another flow in opposite directions and completely cancel one another. This is illustrated in Fig. 1(a). As the sphere is assembled, it will be found that all the solenoids repel one another and all adjacent sides have opposite current

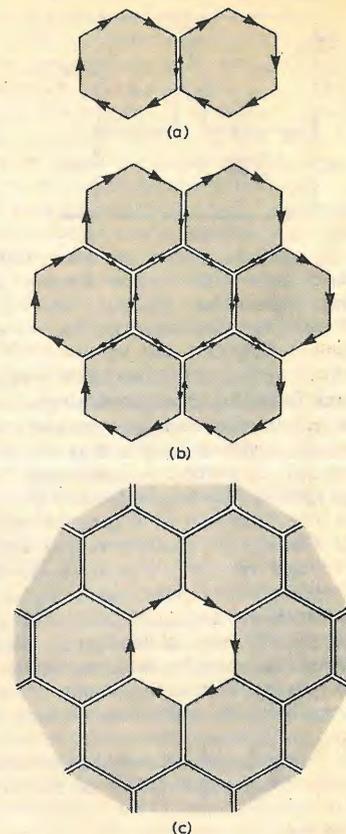


Fig. 1 Stages in the assembly of the sphere, showing current cancellation.

flows. In fact, only the current at the extreme periphery causes an external magnetic field, and this is the situation illustrated in Fig. 1(b).

The situation when the last solenoid is about to be fitted in is shown in Fig 1(c); the currents cancel everywhere except round the small hole. The external field at this time is quite small, and insertion of the last solenoid will completely cancel the remaining currents shown in the diagram. The magnetic field is zero everywhere and the stored potential energy is distributed evenly over all the solenoids in the form of the strain in the clamps required to hold the whole structure together. Note that potential energy and magnetic energy are gradually interchanged as the sphere is built up.

What happens when the solenoids are replaced by permanent magnets is not quite the same. For all practical materials the coercivity is such that there would be a progressive demagnetization as the sphere is built up, the edges of the shell having the greatest magnetic intensity. Under such assumptions the completed sphere might have residual magnetism, and it is no longer possible to discuss Mr Middlehurst's interesting supposition.

TECHNICAL WORDS

F. L. Devereux (December 1978 letters) has raised a point which has been aired in some technical publications in this country, namely the use, spelling and pronunciation of words used by technologists. While "expertise" is not strictly a technological word (it does not describe an item or situation specifically related to a science or engineering) it is typical of the changes emer-

continued on page 86

Passive notch filters — 2

How to design high and low impedance null filters

by G. Kalanit, B.Sc., M.I.E.E., Rediffusion Engineering Ltd.

Selecting the right type of filter for the particular job at hand from the literature is laborious and time consuming. And little information is provided about design procedure and hardware.

Three articles provide design procedure and simple formulae by way of examples as well as hardware details. To simplify description of the examples formulae and statements are given without theoretical proof; normally theoretical and mathematical development is treated separately in appendices.

THIS THREE-PART article concentrates mainly on null-type notch filters which are derived from a prototype lattice or Wheatstone bridge. At the notch frequency the arms of the bridge are made to resonate into four equal resistances which perform a null of the bridge and no output of the frequency

appears at the filter output. At all other frequencies the filter acts as an all-pass network.

The lattice which possesses four resonant arms is a balanced type of network. In most practical applications an unbalanced or grounded form that employs only two resonant arms is preferred, achieved with a hybrid transformer.

There are number of unbalanced configurations, all of which use the same hybrid transformer and the choice depends on the particular application at hand. The notations of the formulae refer always to the prototype lattice; thus the same set of formulae serve all the variations. A detailed description summarising all the configurations is given in a section about the hybrid transformer in part three.

Examples 3 and 4 are high and low impedance null-type filters.

dynamic impedance D of coil inductance $2L_a$. Thus

$$2R_a = D = Q_a \cdot \omega_0 2L_a$$

from equation 2-2 where Q_a is the Q value of coil $2L_a$.

The equivalent circuit at resonance is shown in Fig. 3-3. To have a null: $R_a = R_b$. Hence

$$R_b/2 = R_a/2 = 2R_a/4 = D/4 \quad 3-1$$

i.e., $R_b/2$ is adjusted to be a quarter the value of the dynamic impedance.

From appendix C, equations C-10 to C-12,

$$\omega_3 = \frac{(n+1)/n}{(C_a/2) \cdot 2R} \cdot M \quad 3-2$$

where n is the ratio of R_a to R ,

$$n = R_a/R = D/2R \quad 3-3$$

and
$$M = \frac{2(n+m)}{n+m(n+2)} \quad 3-4$$

where m is the ratio of R_s to R ,

$$m = R_s/R \quad 3-5$$

When the source and load resistance are equal, $R_s = R$, then $m = 1$ which results in $M = 1$. Hence

$$\omega_3 = \frac{(n+1)/n}{(C_a/2) \cdot 2R}$$

when $m = R_s/R = 1$. 3-6

Also
$$\omega_3 = \frac{1}{C_a/2} \left(\frac{1}{2R} + \frac{1}{D} \right) \quad 3-7$$

When $D \gg 2R$ ω_3 approximates to

$$\omega_3 = \frac{1}{(C_a/2) \cdot 2R} \quad 3-8$$

Notice that the larger the source, the load and dynamic impedances the narrower the notch becomes. In the example shown in Fig. 3-4, a notch is required at $f_0 = 24\text{MHz}$ with bandwidth of about 10kHz at notch depth of -40dB, i.e., $f_{40} = 0.01\text{MHz}$. Hence

$$f_3 = 0.01 \times 100 = 1\text{MHz}.$$

Example 3: High impedance null filter

A high impedance null type of filter provides a narrow notch in amplifier interstages where the impedances of the source and the load are comparatively high. The basic circuit is derived from Fig. 1-5 by the removal of the reactive components of arm 'b'. As with Fig. 1-5 it is possible to dispense with the hybrid transformer. The result is two possible

configurations shown in Figs 3-1 and 3-2, derived from Figs 1-9 and 1-10 respectively.

To minimize insertion loss in the pass band, the null resistance $R_b/2$ should be as high as possible, consequently $2R_a$ which is $4 \times R_b/2$ should also be maximal. Hence, no real $2R_a$ resistor is employed; resistance $2R_a$ represents the

Fig. 3-1

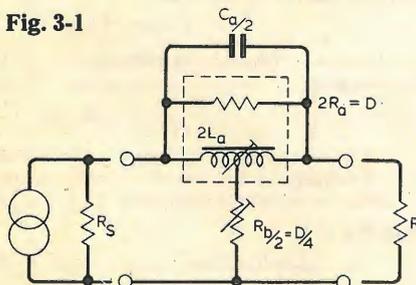


Fig. 3-2

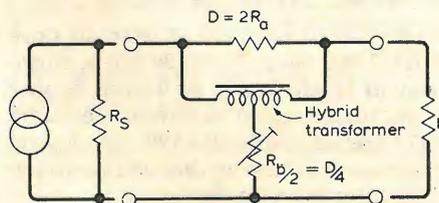
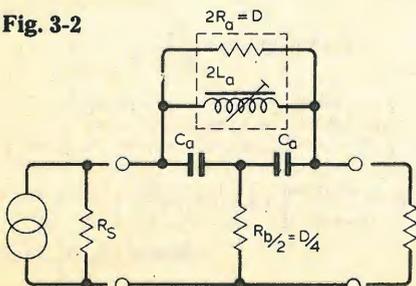


Fig. 3-3

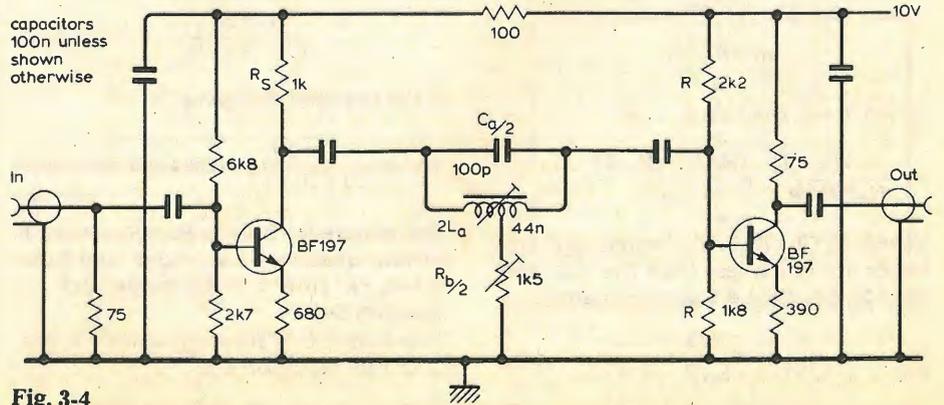


Fig. 3-4

$R_S = R = 1000 \text{ ohm}$ and $m = 1, M = 1$ (R is 2200Ω in parallel with 1800Ω is 1000Ω)
From equation 3-8

$$C_a/2 = \frac{1}{2\pi \cdot f_3 \cdot 2R} \approx 79.5\text{pF}$$

It is not possible to use equation 3-6 or 3-7 to compute $C_a/2$ more accurately because the dynamic impedance D of $2L_a$ is unknown. However if one assumes a Q value for the coil, it is possible to use the following equation

(appendix C equation C-17)

$$C_a/2 = \frac{1}{\omega_3 \cdot 2R(1-q)} \quad 3-9$$

where $q = \frac{Q}{Q_a} = \frac{f_o/f_3}{Q_a}$, 3-10

and Q_a is the Q value of the coil.
Assuming $Q_a = 100$ then

$$q = \frac{24/1}{100} = 0.24 \text{ and}$$

$$C_a/2 = \frac{1}{2\pi \times 2000 \times (1-0.24)} = 104\text{pF.}$$

Thus a 100pF capacitor was used. The coil was made of 0.2mm-diameter bifilar copper wire, 3 + 3 turns wound on $4 \times 0.5 \times 10\text{mm}$ core, Neosid, grade 900. Q_a was measured to be 106 at 25MHz. The notch width at -40 dB was measured to be $f_{40} = 11\text{kHz}$. Maximum attenuation of the notch was -62 dB . Resistance $R_b/2$ was 1500 ohm, which means $D = 4 \times 1500 = 6000 \text{ ohm}$. The introduction of $R_b/2 = 1500 \text{ ohm}$ gives an extra loss of 0.75 to the circuit. The general formula for extra insertion loss is

$$\frac{1}{\frac{1}{R_S} + \frac{1}{R}} + \frac{1}{\frac{1}{R_S} + \frac{1}{R} + \frac{1}{D/4}} \quad 3-11$$

To compute $C_a/2$ when $R_S \neq R$; estimate Q_a as above and hence q (equation 3-10); then calculate n ($m = R_S/R$) from appendix C, equation C-15.

From n and m compute M of equation 3-4. Then compute $C_a/2$ from equation 3-2.

Correction. Equation 1.4 in example 1 (August) should read as equation E-7, page 86.

Example 4: Low impedance null filter

The low impedance null filter suits networks where the source and load impedances are low. A common example of low impedance source is an emitter follower. The lower the impedances the narrower is the notch. The circuit is in a sense the inverse network of the high-Z notch of example 3.

The circuit is derived from Fig. 1-5 by the removal of the reactive components of arm 'a'. Unlike example 3, the hybrid transformer stays.

In an example where $R_S = R = 10 \text{ ohms}$ a notch is required at $f_o = 19\text{MHz}$ with bandwidth of 4kHz at notch depth of -40dB , i.e. $f_{40} = 0.004\text{MHz}$, thus $f_3 = 0.4\text{MHz}$. From equation 4-7

$$L_b/2 = \frac{R/2}{\omega_3} = \frac{10/2}{2\pi \times 0.4} \approx 2\mu\text{H}$$

As the coil losses are not known it is not possible to use equation 4-6 for more accurate computation. However, one may assume a coil Q and compute (from appendix D, equation D-12)

$$L_b/2 = \frac{R/2}{\omega_3} \cdot \frac{1}{1-q} \text{ when } m=1 \quad 4-8$$

where $q = \frac{Q}{Q_b} = \frac{\omega_0/\omega_3}{Q_b}$ 4-9

Assume $Q_b = 90$ for coil $L_b/2$. Then

$$q = \frac{\omega_0/\omega_3}{Q_b} = \frac{19/0.4}{90} = 0.53$$

and from equation 4-8

$$L_b/2 = \frac{10/2}{2\pi \times 0.4} \cdot \frac{1}{(1-0.53)} = 4.2\mu\text{H}$$

From equation 4-1

$$R_b/2 = \frac{\omega_0 \cdot L_b/2}{Q_b} = \frac{(2\pi \times 19) \times 4.2}{90} = 5.5\text{ohm}$$

Hence $2R_a = 4 \times 5.5 = 22 \text{ ohm}$.

Coil used was made of Neosid core CH1/7/900 wound with 20 turns, close-wound single layer, of 0.4mm copper wire, tinned nylon acetate. Measured Q of coil at 8MHz was 120. The hybrid coil was the same as that of example 1. Capacitor $2C_b$ was 18pF.

The extra insertion loss due to the notch circuit is

$$\frac{R_S + R}{R_S + R + 2R_a} \quad 4-10$$


In the example this gives

$$\frac{10 + 10}{10 + 10 + 22} = 0.48 \rightarrow 6.4 \text{ dB}$$

To compute $L_b/2$ when $R_S \neq R$; estimate q from equation 4-9 as above, and from $m = R_S/R$ find k from appendix D, equation D-10.

Then compute N from equation 4-3, and $L_b/2$ from equation 4-2.

Fig. 4-1

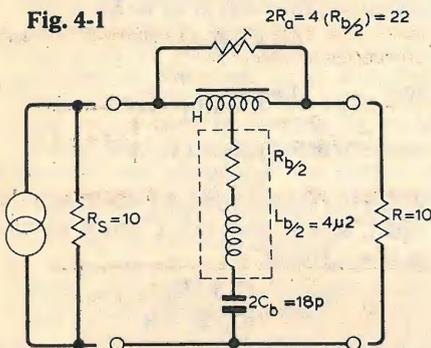

To minimize insertion loss in the pass band $R_a = R_b$ should be minimal, i.e. high Q_b value for inductance $L_b/2$.

$$Q_b = \omega_0 (L_b/2) / (R_b/2) \quad 4-1$$

From appendix D, equations D-4 to D-7,

$$\omega_3 = \frac{R/2}{L_b/2} \cdot \frac{k+1}{k} \cdot N \quad 4-2$$

where

$$N = \frac{2(1+mk)}{2+k(1+m)} \quad 4-3$$

$$k = \frac{R/2}{R_b/2} \text{ and} \quad 4-4$$

$$m = R_S/R.$$

When $m = 1, N = 1$ and

$$\omega_3 = \frac{R/2(k+1)}{(L_b/2) \cdot k} = \frac{(R/2) + (R_b/2)}{L_b/2}$$

When $R_b/2 \ll R/2$, i.e. when the coil losses are much less than the load resistance, equation 4-6 approximates to

$$\omega_3 = \frac{R/2}{L_b/2} \quad 4-7$$

Appendix C. Lattice of high Z notch

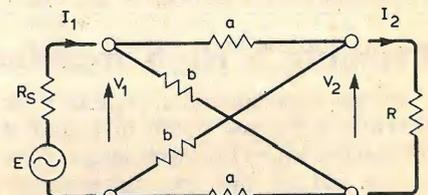


Fig. C-1

The lattice input impedance is not a constant at all frequencies, i.e. V_1 and I_1 are not constant, therefore the source resistance R_S has to be included in the calculation. From the matrix equation B-5,

$$V_1 = \frac{1}{b-a} \cdot [(b+a) \cdot V_2 + 2baI_2] \quad C-1$$

$$I_1 = \frac{1}{b-a} \cdot [2V_2 + (b+a)I_2] \quad C-2$$

From Fig. C-1

$$I_2 = V_2/R \text{ and} \quad C-3$$


$$E = V_1 + R_S \cdot I_1 \quad C-4$$

Insert I_2 from equation C-3 in C-1 and C-2, and then insert C-1 and C-2 in C-4 which gives

$$E = V_1 + R_S \cdot I_1 = \frac{V_2}{b-a}$$

$$\begin{aligned} & \left[(b+a) + \frac{2ba}{R} + 2 \cdot R_S + \frac{R_S \cdot (b+a)}{R} \right] \\ = E &= \frac{V_2}{1-a/b} \left[(1+a/b) \left(1 + \frac{R_S}{R} \right) + \frac{2a/R + 2R_S/b}{1-a/b} \right] \quad C-5 \end{aligned}$$

Fig. C-2

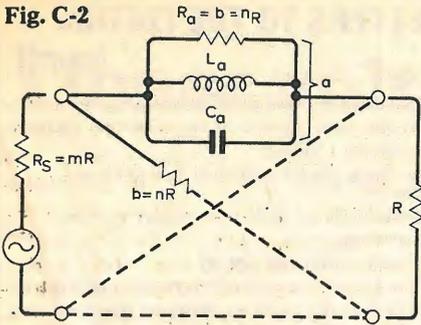

In the high Z notch, Fig. C-2, arm b is a resistor, and R_a is made equal to b for a null at $\omega_0 = 1/L_a C_a$.

Make 'b' a multiple n of R, thus $b = nR$ or $R = b/n$.

Also make $R_S = mR$, hence

$$E = \frac{V_2}{(1-a/b)} \times [(a/b)(1+m+2n) + (1+m+2m/n)]$$

and the voltage transfer is

$$\frac{V_2}{E} = \frac{(1-a/b)}{(a/b) \cdot (1+m+2n) + (1+m+2m/n)}$$

The voltage transfer in the pass bands V_{20}/E occurs when the impedance of arm 'a' is zero, i.e. $a=0$, thus

$$\frac{V_{20}}{E} = \frac{1}{(1+m+2m/n)}$$

which is the insertion loss in the pass bands. The voltage transfer function V_T is then the ratio of the transfer voltage to the insertion loss in the pass bands.

$$V_T = \frac{(V_2/E)}{(V_{20}/E)} = \frac{(1-a/b)}{(a/b) \cdot (1+m+2n) + (1+m+2m/n)} \quad \text{C-6}$$

From Fig. C-2

$$\frac{1}{a} = \frac{1}{b} + \frac{1}{pL_a} + pC_a = \frac{pL_a/b + 1 + p^2L_a C_a}{pL_a}$$

$$\text{Hence } a/b = \frac{pL_a/b}{(pL_a/b + 1 + p^2L_a C_a)}$$

Insert a/b in equation C-6

$$V_T = \frac{1 + p^2L_a C_a}{(pL_a/b) \cdot \left[\frac{1+m+2n}{1+m+2m/n} + 1 \right] + 1 + p^2L_a C_a}$$

Multiply numerator and denominator by $\omega_0^2 = 1/L_a C_a$ and replace b by $nR = b$ then

$$V_T = \frac{\omega_0^2 + p^2}{C_a \cdot nR \left[\frac{2(n+1)(n+m)}{n+m(n+2)} \right] + \omega_0^2 + p^2} \quad \text{C-7}$$

From comparison with equation A-4, the coefficient of p is

$$\omega_3 = \frac{(n+1)}{C_a R_n} \cdot \frac{2(n+m)}{n+m(n+2)} \quad \text{C-8}$$


where R is the load, $m = R_S/R$ and $n = b/R$. When the source and the load resistance are equal, $m = 1$ and equation C-8 reduces to

$$\omega_3 = \frac{1}{C_a \cdot R} \cdot \frac{n+1}{n} \quad \text{C-9}$$

Unbalanced high-Z notch

The unbalanced form of Fig. C-2 is shown in Fig. C-3

Fig. C-3

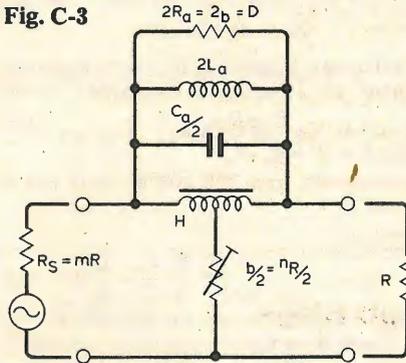

Re-write equation C-8

$$\omega_3 = \frac{1}{(C_a/2) \cdot 2R} \cdot \frac{n+1}{n} \cdot M \quad \text{C-10}$$

where

$$M = \frac{2(n+m)}{n+m(n+2)} \quad \text{C-11}$$

When $R_S = R$, $m = 1$; hence $M = 1$, and

$$\omega_3 = \frac{(n+1)/n}{(C_a/2) \cdot 2R} \quad \text{C-12}$$

To find $C_a/2$ in terms of Q_a of inductance $2L_a$

$$n = b/R = \frac{2b}{2R} = \frac{Q_a \cdot \omega_0 2L_a}{2R} = \frac{Q_a}{2R} \cdot \frac{1}{\omega_0 \cdot C_a/2} = \frac{Q_a}{2R \left(\frac{\omega_0}{\omega_3} \right) \omega_3 \cdot C_a/2}$$

$$n = \frac{1}{2Rq\omega_3 C_a/2} \quad \text{C-13}$$

where

$$\frac{1}{q} = \frac{Q_a}{\omega_0/\omega_3} = \frac{Q_a}{Q} \quad \text{C-14}$$

From C-10: $2RC_a/2n\omega_3 = (n+1)M$ and from equation C-13: $n2R\omega_3 C_a/2 = 1/q$.

Hence

$$\frac{1}{q} = [(n+1)M] = (n+1) \cdot \frac{2(n+m)}{n+m(n+2)}$$

$$\therefore n^2 \cdot 2q - n(1+m)(1-2q) - 2m(1-q) = 0.$$

The solution of n in terms of q and m; n =

$$\frac{(1+m)(1-2q) + \sqrt{(1+m)^2(1-2q)^2 + 16q(1-q)}}{4q} \quad \text{C-15}$$


$$\text{When } m=1, n = \frac{1-q}{q} \quad \text{C-16}$$

and from equation C-12

$$C_a/2 = \frac{(n+1)/n}{\omega_3 \cdot 2R} = \frac{1}{\omega_3 \cdot 2R(1-q)} \quad \text{C-17}$$

Appendix D. Lattice of low-Z notch

Fig. D-1

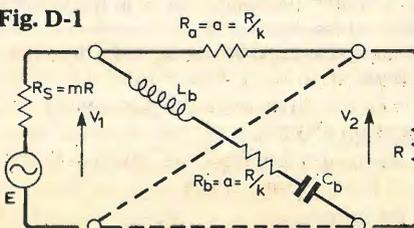

In a manner similar to appendix C arm 'a' is a resistor and R_b is made equal to a for a null at $\omega_0 = 1/(L_b \cdot C_b)$. Make R a multiple k of 'a', i.e. $R = ka$. From equation C-5 where $R_S = mR$, $E =$

$$\frac{V_2}{(1-a/b)} \left[(1+a/b)(1+m) + \frac{2a}{ka} + 2mk a/b \right] = \frac{V_2}{(1-a/b)} [(a/b)(1+m+2mk) + (1+m+2/k)].$$

Hence

$$\frac{V_2}{E} = \frac{1-a/b}{(a/b) \cdot (1+m+2mk) + (1+m+2/k)}$$

When arm 'b' is open circuit, $b = \infty$ and

$$\frac{V_{20}}{E} = \frac{1}{1+m+2/k}$$

$$V_T = \frac{V_2/E}{V_{20}/E} = \frac{1-a/b}{(a/b) \cdot (1+m+2mk) + (1+m+2/k)} + 1 \quad \text{D-1}$$

From Fig. D-1 (to simplify, use L and C instead of L_b, C_b)

$$b = a + pL + \frac{1}{pC} = \frac{pC \cdot a + p^2LC + 1}{pC}$$

Hence

$$a/b = \frac{pC \cdot a}{pC \cdot a + 1 + p^2LC}$$

Insert this expression in equation D-1 and proceed as in appendix C.

$$V_T = \frac{1 + p^2LC}{pC \cdot a \left[\frac{2(1+k) \cdot (1+mk)}{2+k(1+m)} \right] + 1 + p^2LC}$$

Multiply by $\omega_0^2 = 1/LC$ and replace 'a' by $a = R/k$

$$V_T = \frac{\omega_0^2 + p^2}{\frac{R}{kL} \left[\frac{2(1+k)(1+mk)}{2+k(1+m)} \right] + \omega_0^2 + p^2}$$

Thus by comparison with A-4, the coefficient of p is

$$\omega_3 = \frac{R(k+1)}{L_b \cdot k} \left[\frac{2(1+mk)}{2+k(1+m)} \right] \quad \text{D-2}$$


When $R_S = R$, $m = 1$

$$\omega_3 = \frac{R}{L_b} \cdot \frac{k+1}{k} \quad \text{D-3}$$

where $k = R/a$.

Unbalanced low-Z notch

Fig. D-2

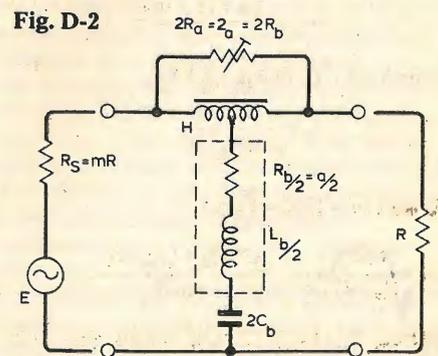

Re-write equation D-2 to suit configuration of Fig. D-2

$$\omega_3 = \frac{R/2}{L_b/2} \cdot \frac{k+1}{k} \cdot N \quad \text{D-4}$$

where $N = \frac{2(1+mk)}{2+k(1+m)}$ D-5

when $m=1, R_s=R, N=1$

$$\omega_3 = \frac{R/2}{L_b/2} \cdot \frac{k+1}{k}$$
 D-6

and $k = \frac{R}{a} \cdot \frac{R}{R_b} = \frac{R/2}{R_b/2}$ D-7

To find $L_b/2$ in terms of Q_b

where $Q_b = \frac{\omega_0 L_b/2}{R_b/2}$ or $\frac{1}{R_b/2} = \frac{Q_b}{\omega_0 L_b/2}$

$$k = \frac{R/2}{R_b} = \frac{R/2 \cdot Q_b}{\omega_0 \cdot L_b/2} = \frac{R/2 \cdot Q_b}{\omega_3 \cdot (L_b/2) \cdot \omega_0/\omega_3}$$

$$= k = \frac{R/2}{\omega_3 \cdot (L_b/2) \cdot q}$$
 D-8

where $\frac{1}{q} = \frac{Q_b}{Q} = \frac{Q_b}{\omega_0/\omega_3}$ D-9

From eq D-4 $\frac{k \cdot (L_b/2) \cdot \omega_3}{R/2} = (k+1) \cdot N$

From eq D-8 $\frac{k \cdot (L_b/2) \cdot \omega_3}{R/2} = 1/q$

Hence $\frac{1}{q} = (k+1)N = (k+1) \cdot \frac{2(1+mk)}{1+k \cdot (1+m)}$

$\therefore k^2 \cdot 2mq - k(1+m)(1-2q) - 2(1-q) = 0$
and thus $k =$

$$\frac{(1+m)(1-2q) + \sqrt{[(1+m)(1-2q)]^2 + 16mq(1-q)}}{4mq}$$
 D-10

When $m=1, k = \frac{1-q}{q}$ D-11

From equation D-6

$$L_b/2 = \frac{R/2}{\omega_3} \cdot \frac{k+1}{k} = \frac{R/2}{\omega_3} \cdot \frac{1}{(1-q)}$$
 D-12

Appendix E

Derivations. Given: resonance (equation 1-1), constant resistance (equation B-4) and 3dB bandwidth (equation B-9).

E.1 Equation 1-5

From equation B-9

$$L_b/2 = \frac{1}{\omega_3^2 \cdot C_a/2} = \frac{2}{\omega_3^2 \cdot C_a}$$
 E-1

From resonance equation 1-1

$$\frac{1}{C_a} = \omega_0^2 \cdot L_a$$

Substitute $1/C_a$ in equation E-1

$$L_b = \frac{2\omega_0^2 \cdot L_a}{\omega_3^2}$$

$$\frac{L_b}{L_a} = \frac{4\omega_0^2}{\omega_3^2}$$

or $\sqrt{\frac{L_b}{L_a}} = \frac{2\omega_0}{\omega_3} = (\text{equal by definition to}) = 2Q$ E-2

This confirms equation 1-5

E.2 Equation 2-3

Q factor of arm 'b' is

$$Q_b = \frac{\omega_0 \cdot L_b}{R_b} \therefore R_b = \frac{\omega_0 L_b}{Q_b}$$
 E-3

From resonance equation 1-1

$$\omega_0 \cdot L_b = \frac{1}{\omega_0 \cdot C_b}$$

thus $R_b = \frac{\omega_0 \cdot L_b}{Q_b} = \frac{1}{Q_b(\omega_0 C_b)}$ E-4

The dynamic impedance of arm 'a' equals R_a (where no resistor is employed), hence

$$R_a = Q_a \omega_0 L_a$$
 E-5

From B-4 $R^2 = R_a \cdot R_b$

Substitute R_a from E-5 and R_b from E-4 in above.

$$R^2 = R_a R_b = (Q_a \omega_0 L_a) \cdot \frac{1}{Q_b \cdot \omega_0 C_b} = \frac{Q_a L_a}{Q_b C_b} = \frac{Q_a}{Q_b} R^2$$
 E-5

as $\frac{L_a}{C_b} = R^2$ from B-4.

Hence $\frac{Q_a}{Q_b} = 1$ or $Q_a = Q_b$ E-6

which completes equation 2-3.

E.3 equation 1-4

For $Q_{b(\min)}$ where no extra coil resistor is employed in arm 'b', $R_b=R$. Similarly, for $Q_{a(\min)}$ $R_a=R$. Thus

$$\frac{R_b}{R_a} = \frac{R}{R} = 1$$

Substitute R_b from equation E-3 and R_a from equation E-5

$$1 = \frac{R}{R} \cdot \frac{R_b}{R_a} = \frac{\omega_0 \cdot L_b/Q_{b(\min)}}{\omega_0 \cdot L_a/Q_{a(\min)}}$$

$$= \frac{L_b}{L_a} \cdot \frac{1}{Q_{a(\min)} \cdot Q_{b(\min)}}$$

Substitute

$$\frac{L_b}{L_a} = (2Q)^2$$
 from E-2, thus


$$1 = \frac{(2Q)^2}{Q_{a(\min)} \cdot Q_{b(\min)}}$$

As $Q_{a(\min)} = Q_{b(\min)}$ from E-6

$$2Q = Q_{a(\min)} = Q_{b(\min)}$$
 E-7

which completes equation 1-4

Appendix F. Bartlett's bisection theorem

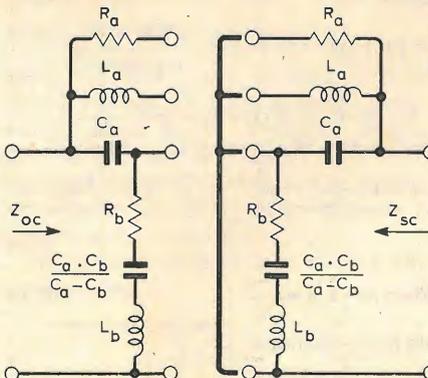

According to Bartlett's bisection theorem, if Fig. 1-10 is bisected the short-circuited half Z_{sc} forms one lattice arm and the open-circuit half Z_{oc} the other arm. Hence Z_{sc} becomes arm 'a' and Z_{oc} becomes arm 'b' in the lattice of Fig. 1-1 (see also ref. 2).

The two capacitors in series in Z_{oc} become C_b , thus

$$\frac{1}{\text{capacitance}} = \frac{1}{C_a} + \frac{1}{C_a \cdot C_b} = \frac{1}{C_b}$$

To be continued

LETTERS TO THE EDITOR (cont)

ging in the various English languages. In the 1976 edition of the Concise Oxford Dictionary I found:

expertise n. Expert opinion or skill or knowledge.

expertize, -ise v.i. & t. Give expert opinion (concerning)

So I ask - why not use it?

The broad issue I wish to raise in this letter is who has the right to allow or disallow use of words. Obviously a dictionary compiler will not create a word and list it as in common use, so that it must be in use before it is listed. At this stage people with an academic interest in the language complain, forgetting that for most users of the language it is but a tool.

Specifically, technologists must have the right to create their own words not only as they do in naming a new invention, discovery or parameter (charmed quark), but where a minor descriptive category becomes of special importance. Brevity and phonetic ease with an attempt at spelling rationality are of prime importance. That this "jargon" is unintelligible outside the field is unimportant. Mathematical formulae, biological classifications, chemical nomenclature, astronomical designations are meant as tools for people trained in their use and these people resent being told that they may not coin new words for their use.

For it is not just the present with words such as expertise, program(me), hex(a)/(i)decimal, microprocessor/microcomputer which are in question but all technological names and descriptions which have been coined over the centuries. It will be impossible to produce any technical publication, such as *Wireless World*, when only non-specialised words and abbreviations are permitted.

My suggestion is that a society which desires literacy for all its people rather than as a privilege of the wealthy must actively expedite this policy. Acceptance of the nature of language (it is a tool) will precede the optimization and rationalization of usage, which includes acceptance of new words. Three types of dictionary could be collated: Archaic - for words we may read but will never write.

Contemporary - for the words we see, hear, and use in everyday life.

Technical - a suitable criterion for inclusion would be frequency of occurrence in the media, as a measure of contemporaneity.

Our dynamic languages cannot be vitrified until our life styles do so. Countries which can alter currency and mensuration units can certainly regard their language with objectivity.

James Nolan
Sydney
Australia

MICROPROCESSOR USERS CLUB

It is proposed to set up a club in Britain for those people using the RCA 1802 microprocessor, Cosmac ELF, ELFII, Super Elf etc. The unofficial assistance of RCA and HL Audio has been promised. Would those interested please contact me at 7 Harrowden Court, Harrowden Road, Luton LU2 OSR. Please send a stamped addressed envelope.

James Cunningham
Luton

Linear voltage-controlled oscillator

LC circuit provides increased s/n ratio

by J. L. Linsley Hood

The author describes a technique for linearizing the characteristics of a varicap-tuned LC tuned circuit, which allows a frequency control of $\pm 5\%$, with a linearity of better than 0.5% over the range.

A NUMBER of circuit arrangements exist for the generation of a.c. signals whose frequency is a linear function of some direct control voltage. Of these, the majority in current use employ some form of RC relaxation oscillator,

which is usually an elaboration of the well-known cathode-coupled multivibrator.

There are three fundamental disadvantages in this type of circuit. These are that it is very difficult to make such circuits operate beyond some 20 or 30 MHz, because of the nature of the relaxation mechanism, and that the frequency stability is poor at this end of the operating range. Also, because of the way in which the circuit operates, the signal-to-noise ratio of the

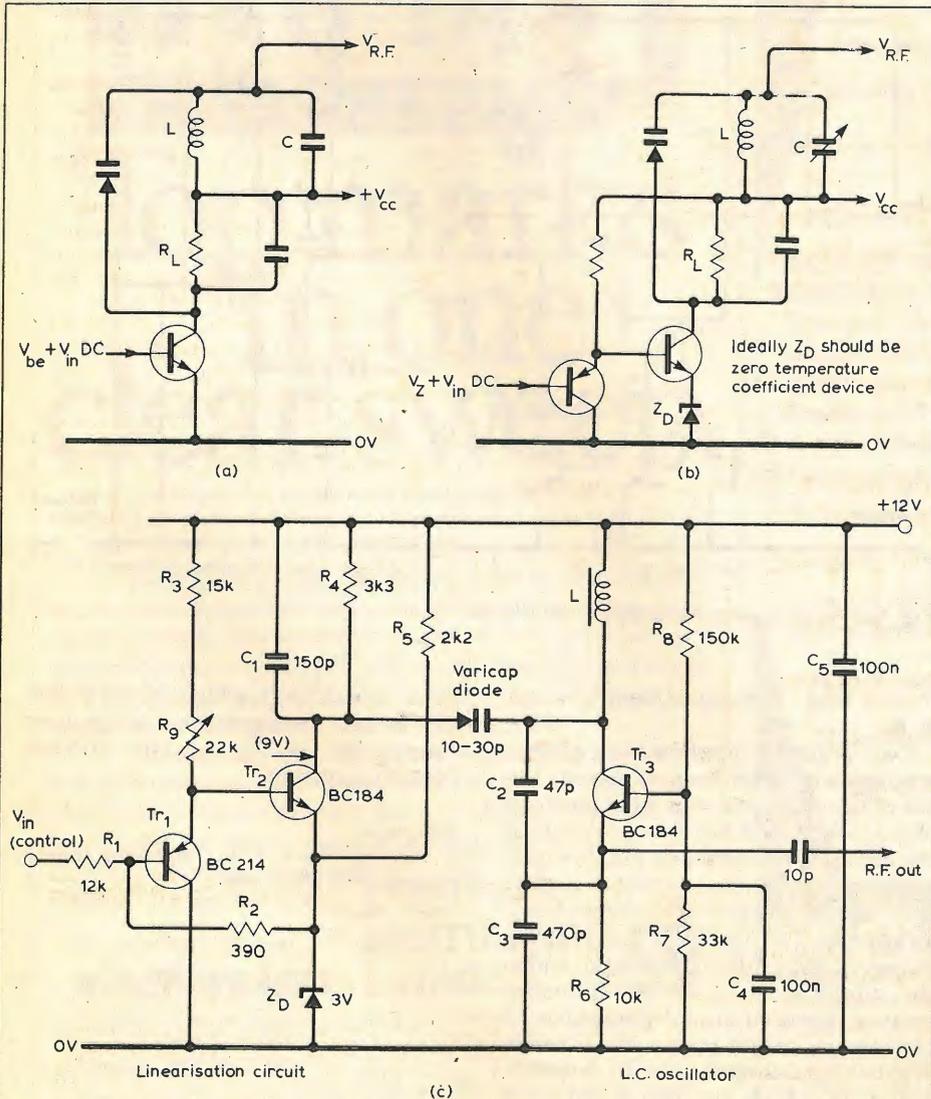


Fig. 1. Voltage/capacitance characteristic of Varicap and base voltage/collector current curve of transistor follow similar law in circuit at (a). Modification at (b) removes effect of base-emitter voltage of transistor. Practical circuit is shown at (c).

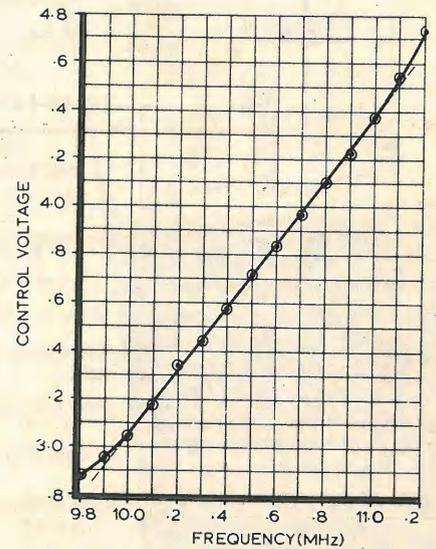




Fig. 2. Characteristic of circuit in Fig. 1(c).

generated signal may be some 20-30 dB less good than that of a comparable LC oscillator.

For some applications, the less good s/n ratio of the multivibrator circuit is relatively unimportant. However, it will be appreciated that this expresses itself as a 'jitter' in the turn-on and turn-off timings, and that the noise is therefore of an f.m. nature.

By analogy with the way in which the noise accompanying the h.f. bias signal in a tape recorder will be superimposed on the recorded input, with a resultant degradation in the overall s/n ratio, it can be seen that any f.m. noise present on the output of the voltage-controlled oscillator in a phase-locked-loop, f.m. demodulator will be superimposed on the incoming f.m. signal during demodulation. This difficulty may be a significant reason for the almost complete absence of this type of demodulator in commercial f.m. receivers.

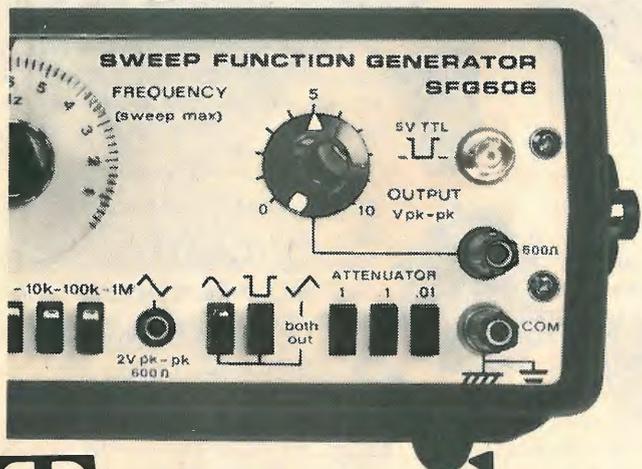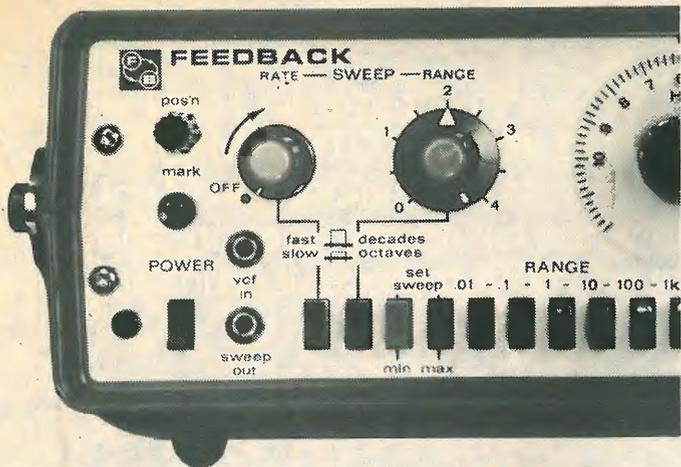Alternative types of voltage-controlled oscillator based on the combination of an LC circuit and some form of voltage-controlled reactance, such as a Blumlein integrator or a voltage variable capacitor or Varicap diode, are seldom used except in expensive and specialized equipment because of the complexity of the circuitry normally employed to obtain a linear relationship



Top marks in one clear sweep.

You'd expect a Sweep Function Generator from Feedback to contain a lot more features for your money. And you'd be right—the SFG606 with its crisp frequency marker does just that.

It sweeps up to 4 decades of frequency—bi-directionally. So you can avoid problems of transient effects. It maintains low signal distortion with absolute precision over the entire sweep range. It features a choice of decade or octave sweep—so it's ideal for narrow band analysis. It provides sine, square or triangle outputs over the frequency range 0.01Hz to 1MHz.

And with that beautifully sharp, fine line frequency marker that gives you accurate determination of spot frequency on the display, the SFG606 really does score top marks. Read all about the SFG606 and all its companion test instruments in the Feedback 600 range. Send to Feedback for literature today.

Or contact our distributors

electroplan

P.O. Box 19, Orchard Road, Royston, Herts. SG8 5HH. Telephone: Royston 45145.

Feedback Instruments Limited




Feedback Instruments Ltd., Park Road, Crowborough, Sussex TN6 2QR. Telephone: Crowborough (08926) 3322. Cables: Feedback Crowbr. Telex: 95255.

The new SFG606 passes even the testiest tester's test.

WW — 006 FOR FURTHER DETAILS

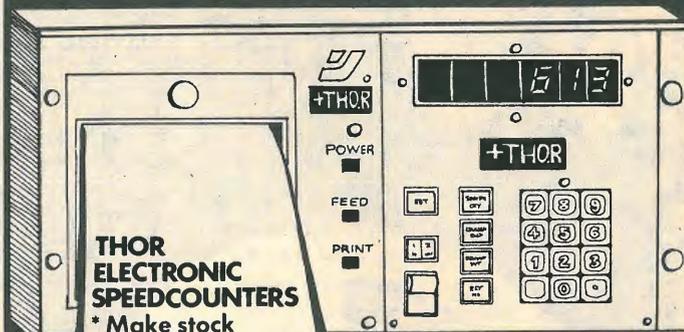This solid state parts counter saves you money 20 ways. For as little as £6.95 per week



THOR ELECTRONIC SPEEDCOUNTERS

- * Make stock checks easier
- * Save counting time
- * Control stock levels
- * Control parts issuing
- * Avoid stock shortages
- * Save operator training
- * Simplify record keeping
- * Save management time

No comparable product is as fast, accurate and simple to use. And we'll be happy to demonstrate actual proof of those claims. We'll listen to your particular counting problems and show you how to vastly increase efficiency, productivity and profitability. 20 ways. For as little as £6.95 a week.

THOR ELECTRONIC INDUSTRIAL SCALES

- * Optional print out
- * Weigh 0-2000 Kg
- * Push button taring
- * Counts to 999,999
- * Accurate from 0.01 gram
- * Leasing from £6.95 per week
- * Push button product reference
- * Platform sizes up to 150 x 120 cm
- * 24 hour service from factory trained technicians available
- * British made — spares always available
- * Comprehensive 5 year guarantee available
- * Ex-stock delivery available on most models

+THOR

To: Balance Consultancy, 35 Harford Street, Trowbridge, Wiltshire, BA14 7HL Telex 449128 Telephone (02214) 64461 and ask Karen York for our rapid leaflet service

- Please send me details of your money saving machines.
- Please ask your Area Manager to call. WW 7/9/79

Tick as appropriate,

NAME
COMPANY
ADDRESS


TEL:

WW — 011 FOR FURTHER DETAILS



"We've £150,000 worth of recording gear working 24 hours a day — all fed from the OTARI MX5050B. On a cost effectiveness basis alone the MX5050B is unbeatable, but when taking into account sheer professionalism and performance, it is unequalled by recorders three times the price."

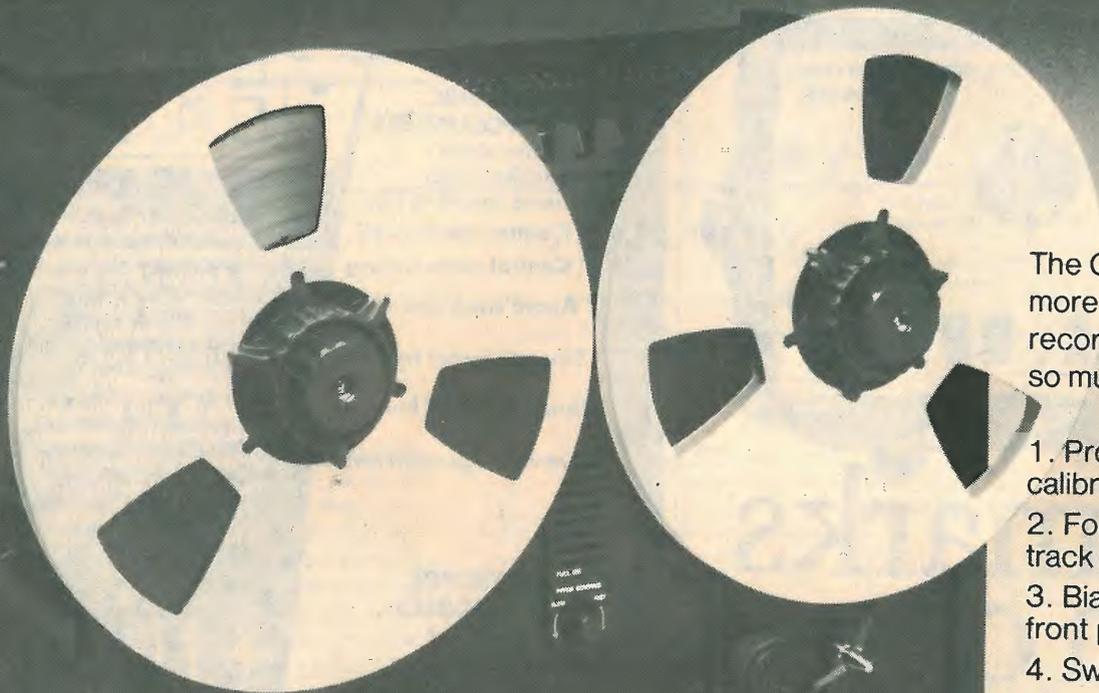Mike McLoughlin, Chief Engineer, Independent Tape Duplicators, Aylesbury.



The Otari MX5050B costs little more than modified domestic recorders. That little extra buys so much more.

1. Proper editing facilities with calibrated splicing block.
2. Four heads provide 2 or 4 track replay.
3. Bias and EQ adjustable from front panel.
4. Switchable NAB and IEC EQ.
5. XLR Connectors.
6. +28 dBm 600 ohm balanced output.
7. Direct drive capstan servo with varispeed.
8. Variable or preset output level.
9. 70 dB (weighted) signal/noise ratio.
10. Sel sync on each channel.



OTARI from ITA

1-7 Harewood Avenue, Marylebone Road, London NW1. Tel: 01-724 2497. Telex: 21879.

WW — 096 FOR FURTHER DETAILS

Video disc battle looms

Audio and video highlights from Chicago consumer electronics show

Introduced by Adrian Hope . . .

. . . and continued by George Tillet

Big news at this year's Consumer Electronic's Show in Chicago was the introduction of the long-awaited video discs and the Magnavision display created quite a sensation. So did the demonstration by Pioneer whose player also uses the Philips-MCA laser system. The MCA library now offers a choice of 200 disc titles ranging in price from \$6 for 30 minutes playback to \$16 for a two-hour movie.

PROBABLY THE MOST IMPRESSIVE demonstration was given by JVC with their VHD-AHD system, which superficially resembles the Philips/Magnavox video disc but is wholly incompatible with that system – and indeed every other video and digital audio system so far announced. Like the Philips disc, the JVC disc is of 30cm diameter, is pressed from vinyl plastics and has a spiral track pits on its smooth, ungrooved surface. But whereas the Philips system reads the pits optically (the Philips disc surface is coated with reflective material) the JVC system reads the pits electrically. The JVC vinyl plastics pressing mix contains a carbon additive and the disc is tracked by a relatively large sapphire stylus which embraces a small electrode. This electrode follows the spiral of programme pits under servo control derived from signals coded in a sequence of guidance pits alongside the programme pits. The track pitch is 1.4 μ m and information is coded as variations in both length and depth of the pits. The relatively large stylus spreads its load over several turns of the spiral to offer a claimed stylus life of 2,000 hours and a claimed disc life of 50,000 plays. JVC cite the physical contact area as 30 times greater than that of a needle-in-groove system, such as Matsushita's Visc or the RCA grooved capacitance system. Tracking force is 40mg but the servo system enables a player to track a disc on an uneven surface. The grooveless surface also enables random access (as with the Philips system) and (also as with the Philips system) there are facilities for trick play, such as freeze frame, multiplication or division of speed by 2, 4, 8 or 16 times, and coded frame-by-frame identification. For NTSC countries the rotational speed is 900 rev/min which offers up to one hour playing time per side with two full picture frames, i.e. four fields, per revolution. Picture quality and stereo sound for the video disc appears every bit as good as that

offered by the Philips laser system. Imperfections up to 10 μ m in size on the disc surface are simply sheared off and smoothed out by the tracking stylus and a drop-out compensator corrects for blemishes of up to 500 μ m on the disc surface. Main snag with this system appears to be susceptibility of the disc to surface containment. Any oil or grease from a human hand will upset tracking so discs must at all times be stored in protective caddies (similar to those used by RCA and Matsushita). The disc is automatically removed from the caddy when introduced into the player so the disc is never touched by hand.

The audio capability of the system using pulse code modulation was also demonstrated. JVC, unlike Philips, argue in favour of a single player to handle both video and p.c.m. discs. Philips of course argues in favour of one player for video discs and another tailored for digital audio. JVC use a 14-bit linear code with sampling at around 44kHz. This provides predictably impressive audio performance, e.g. signal-to-noise ratio of 90dB (presumably the extra 6dB is achieved with pre-emphasis). Unfortunately JVC's in-

Carver magnetic field amplifier claims an output of 400 watts at 94% efficiency.



tention, at least as stated in Chicago, is to tie p.c.m. coding standards to TV frame standards, for instance by marketing a 900 rev/min video-audio player for NTSC countries and a different speed (e.g. 750 rev/min) player for Europe. Although the world is now accustomed to the impossibility of playing NTSC video recordings on European players and vice-versa it would seem an absurdly retrogressive step to impose the same strictures on p.c.m. discs. Such strictures are as unnecessary as they are undesirable. For instance by the adoption of constant tangential rather than constant rotational velocity tracking, Philips will make Compact Discs world-wide compatible. Hopefully JVC will think again before any commercial launch of the disc system (promised for the end of 1980) and by divorcing tv and p.c.m. standards ensure that JVC p.c.m. audio discs bought anywhere in the world will play on similar system players anywhere else in the world. Otherwise the system will surely never fly. But whatever route JVC takes over pulse encoding, the basic incompatibility of the JVC capacitance and Philips laser systems seems assured. A potentially crippling battle between commercial giants with competitive systems of similar potential thus also seems assured.

While the video world waits for BASF to show LVR, the linear or fixed head recording system at Berlin, Toshiba has already shown its own LVR system. According to the BASF technique a length of tape shuttles rapidly backwards and forwards past a fixed recording head. According to the Toshiba technique the tape is in a continuous loop, contained in a cartridge similar to an eight-track audio cartridge. The Toshiba cartridge contains a 100 metre continuous loop of 12.5mm tape which traverses the head at 6 metres per second. As the loop finishes a full pass every 17 seconds the head steps fractionally across the tape width. Each step takes 22 milliseconds, and 220 tracks are laid across the tape width. This provides an hour of continuous recording with generally imperceptible transitions. Rapid access to any point on the tape loop is achieved by fast-stepping the heads across the tape width. Longer playing time and smaller units than the prototype on show in Chicago are promised for 1980.

RCA are very much pre-occupied with their SelectaVision video tape

recorders and now have quite a range. One model, the VDT 201 has a four-hour capacity and it comes complete with a digital clock timer that allows preset recording for seven days with a playing time of six hours.

Colour TV imports were down nearly 25% from last year's first quarter figures but black and white units were little affected at well over a million units. RCA are using a comb filter system with a memory to double process the picture, thus increasing the sharpness. The system is called a Dynamic Detail Processor and it involves a charge-coupled device that effectively increases the number of lines by about 25%. Sylvania, like several other manufacturers, have suddenly realized the importance of good TV sound and models use a two-way speaker system with tone controls — and a filter switch. Projection TV is slowly gaining in popularity and several new models were to be seen. Sony's one-piece models have 50- and 70-inch screens and the VIRS (vertical interval reference signal) is used for colour control. Advent also has a single-unit model and this one employs a five-foot diagonal screen.

Now for a brief look at the audio scene: here the main interest centred on the new cassette decks which had provision for metal tapes. Some firms, like Pioneer and Akai had more than four models with "metal tape compability", as the copywriters put it. One of the most interesting decks was the Nakamichi 680 which can play at half-speed (15/16th in/s) as well as 1½ in/s. The upper -3dB at the slow speed was quoted at 15kHz while the response is extended to 20kHz at 1½ in/s. The metal tape used at the demonstration was made by TDK but Nakamichi propose to market their own brand soon. The 680 has three motors, one for tape drive, one for hub control and the third for transport functions. It has a built-in calibration generator, azimuth head adjustment, monitoring capability, dual function (that is peak-average) fluorescent level indicators and provision for cable or wireless remote control. Many of the new decks are using bar-graph indicators of one kind or another instead of VU meters — some are LCD, others consist of a series of LEDs. Microprocessors are being used extensively now: for example one of the new BIC two-speed (1½ and 3¼ in/s) decks use one for program control with digital display while Phase Linear's Model 7000 employs a microprocessor for automatically setting the bias, equalisation and levels for nine operating parameters, including different kinds of tape.

Dolby Labs took Chicago in June as the opportunity to launch the new HX system which, as an addition to the basic Dolby B domestic noise reduction system, offers additional high frequency head room. This is achieved by varying the level of the record bias in dependence on the character of the pro-



Toshiba linear video recorder achieves tape speed of 6 m/s and a playing time of an hour with 220 tracks on continuous loop.

gramme being recorded. It is of course difficult, with even the most exotic cassette tapes and decks, to achieve accurate recordings of music which is particularly rich in high frequencies. The sound of percussion instruments, such as tambourines and cymbals, and synthesized music are particularly hard to record faithfully. This follows from the compromises necessary with a fixed bias system; the fixed level will often be too low for the optimal recording of mid and low frequencies and too high for optimally recording HF. The idea of varying the bias level according to signal content is not new but has so far foundered because bias variation also alters recorder sensitivity across the frequency spectrum and this produces a bumpy response. It was Dolby engineer Ken Gundry who recognized the need to vary the recorder sensitivity along with the bias. To achieve this a control signal is necessary and the new HX circuit derives this from the Dolby B circuitry which is already virtually standard in stereo cassette decks. Dolby is offering HX under free licence to all firms already licensed to use Dolby B. Headroom at 10kHz and over can be improved by around 10dB, regardless of tape type. This is of course in addition to the similar reduction of h.f. noise offered by the B system.

Tandberg's Dyneq system was also attracting a lot of attention and as used in the model TCD 440A it also reduces saturation effects and improves signal-to-noise. It works by automatically adjusting the record pre-emphasis to obtain the maximum high frequency response without distortion. The system is patented but the company is said

to be willing to consider licensing agreements. DBX (who prefer to be known as dbx) now have an ambitious encoded disc program with the co-operation of many well-known recording companies. Recordings that meet stringent technical and/or musical standards are re-mastered to produce dbx encoded discs. A simple playback decoder is required for playback but this is relatively inexpensive. So far, 25 records have been issued (re-issued?) and I for one was most impressed with the increased dynamic range and silent background.

One of the sensations at the January Show in Las Vegas was the Carver "magnetic field" amplifier which is claimed to be 94% efficient. Precise details are not available but the circuit involves a voltage or rather energy storage "in a relatively small lightweight and low cost magnetic field coil, thereby eliminating the need for a power transformer and electrolytic capacitors". The unit measures less than a 7 inch cube and weighs only 8¼lb. Rated power output is 200 watts per channel and I can confirm that heat dissipation is insignificant. One of the most interesting features of the design is the constant impedance output so parallel loudspeaker connections cause no problems. Since the Las Vegas show, minor circuit changes have been made and the amplifier should be available later this year.

Amplifiers with "Class A" output stages are still popular with some audio enthusiasts although most of them are low powered models. An exception is the Threshold model 4000 which as a rated output of 200 watts per channel. The power supply uses a 1 kilowatt transformer and the 48 output transistors have a dissipation reserve of 6 kilowatts. A class A cascode circuit is used throughout and a matching cascode preamplifier is now available. The input stage is a little unusual as the open-loop curve is shaped to complement the RIAA characteristic resulting in a constant amount of feedback over the audio range.

How to get bass from a small box is a problem that has long plagued loudspeaker designers and one method that has had a certain amount of success is the use of servo-feedback which involves a built-in amplifier. Now, KLH have come up with another variation — the use of a dynamic bass equalizer which is controlled by the signals present at the loudspeaker terminals. The unit is connected in the tape-in, tape-out circuit or between the preamp and power amplifier and low frequency lift is dynamically controlled so the maximum displacement of the speaker cone is not exceeded. The attack time of the processor is so fast, say KLH, that mechanical overload is most unlikely. There are three systems in the associated range of loudspeakers, the smallest measuring 12½ by 8½ by 6 inches and the -3dB point is at 40Hz.

Victorian microwaves

Millemetre transmissions before the Boer War

By K. L. Smith, Ph.D., University of Kent at Canterbury

By 1900, the fundamentals of microwave transmission, and quasi-optical analogue results were firmly established. The theoretical solutions of waveguide transmission and modes of oscillation on spherical and other conductors were nearly all established; but the subject died completely.

MANY SCIENCE and engineering students in higher education still make believe how modern and up to the minute their advanced courses in microwaves are. Mainly because of the way modern mass-media approach such matters, they feel at one with all those dishes that sprout on Post Office towers and the microwave systems now used for satellite links around the the world. It seems to be symbolic of being right there and 'with it' in high technology.

It seems to come as a considerable shock to these students when it is pointed out that such technology was nearly all spelled out sufficiently early on for Queen Victoria to have had the possibility of seeing and inspecting the hardware. As the author of *Ecclesiastes* put it,¹ "There is nothing new under the Sun".

Microwave physics was bound to be realised soon after Clerk Maxwell's equations predicted the possibility of long electromagnetic waves. In 1883, F. G. FitzGerald was already suggesting that Leyden jar discharges should emit Maxwellian radiation.² Then in 1888³, Heinrich Hertz, at Karlsruhe conclusively demonstrated that such waves existed. The apparatus he devised to generate the shorter of his various wavelengths was broadly resonant at 500MHz, and with it most of the properties of microwave optics were established. Hertz used a resonant dipole at the focal line of a cylindrical parabolic aerial, together with a short, parallel-wire transmission line to the detector from a similar dipole at the receiver. Working at the same time in Britain and very nearly establishing the space waves, Oliver Lodge was already well advanced in demonstrating powerful high-frequency waves on wires. Lodge, to quote a report of the time,⁴ ". . . got quantitative evidence of nodes and loops in wires when working with Mr. Chattock in the session 1887-8 (the Bath meeting of the BA) . . . the wires them-


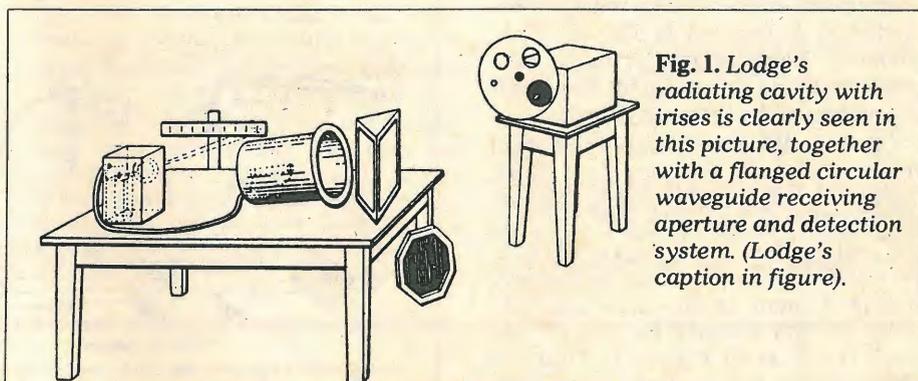



Fig. 1. Lodge's radiating cavity with irises is clearly seen in this picture, together with a flanged circular waveguide receiving aperture and detection system. (Lodge's caption in figure).

General arrangement of experiments with the Copper "Hat," showing Metal Box on a Stool, standing outside the Theatre. The Box is not exactly represented, but inside it the Radiators were fixed with a graduated series of apertures; the Copper Hat containing the Coherer is seen on the Table with the Metal Box on the left of the Table containing Battery and Galvanometer Coil connected to it by a compo pipe conveying the wires, as in Fig. 19c; the Lamp and Scale barely indicated at one side of the Table; a Paraffin Prism; and a Polarising Grid of copper wires stretched on a frame. [This figure is from a thumbnail sketch by Mr. A. P. Trotter, taken at the Lecture in 1894.]

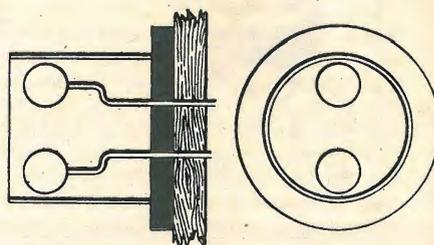

Dr. Lodge's Hollow Cylindrical Radiator, arranged horizontally against the outside of a Metal-lined Box containing the Spark-producing Apparatus. Half natural size. Emitting 3in. waves.

Fig. 2. Pictured are two of Lodge's oscillators, which would have generated predominantly TE_{11} mode radiation.

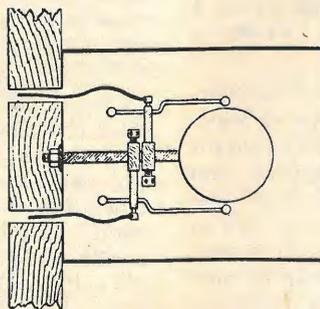

Spherical Radiator for emitting a Horizontal Beam, arranged inside a Copper Hat, fixed against the outside of a metal-lined Box, which contains induction coil and battery and key. One-eighth natural size. The wires pass into the box through glass tubes not shown.

selves becoming momentarily luminous . . . except at the nodes, thus enabling the waves to be actually seen, having been made stationary by reflection. . . . The wires . . . were very long

going five or six times round a large hall . . ."

The reports published on all these spectacular preliminary observations soon resulted in the near-exponential

growth of experimental work and the publication of papers, so well described by Derek De Solla Price in his book "Big Science, Little Science".⁵ Within five years, an identifiable "invisible college" existed on this subject – a socio-scientific phenomenon also described by Price. The members of this international group were described as "the Hertzians". Hertz died at this time, and leadership moved over more firmly to Lodge, A. Righi⁶ in Italy, and to J. Chunder Bose from Calcutta,⁷ whose millimetre wave experiments were quite remarkable. It was during Righi's public lectures that the young Marconi became acquainted with electromagnetic wave phenomena. Other workers included F. J. Trouton in Dublin, J. A. Fleming, Zehnder in Germany, and contributions from Lord Rayleigh strengthened the theoretical base.


Oliver Lodge demonstrated radiation from circular waveguides on 1 June, 1894 at the Royal Institution in London. To this end, he invented the radiating iris, and in effect also resonant cavities. He called them 'copper hats', and clearly intended them as directive aperture radiators and to raise the "Q" of the oscillators, as in Figure 1. Figure 2 clearly shows that he was exciting the TE_{11} modes in the transmitting guide. By placing his coherer detector crossways in the receiving guide he detected this mode, but he also stated that, "Sometimes the (coherer) tube is put lengthwise in the hat instead of crossways, which makes it less sensitive, and also has the advantage of doing away with the polarising, or rather analysing, power of a crosswise tube." This position of his detector can be seen in figure 1.

Clearly Lodge understood he was using the circularly polarised TM_{01} mode in this instance. This mode has a null along the axis, and we find Lodge writing about the receiver as, "... a copper hat with its mouth turned well askew to the source ..." thus receiving the TE_{11} mode radiation on one of the maxima to the side of the axis. Lodge's microwave demonstration operated at 4 GHz, his 7.5 cm waves were just above "S" band.

But it is to Bose we owe a considerable advancement in millimetre wave studies. He developed a semiconductor detector, rectangular waveguides and horn aerials (Figures 3 and 4). His microwave bench was put to use in measurements of refractive index, reflection from plane and curved surfaces and many experiments on polarisation.


Bose generated 5mm wave radiation near "E" band. His resonator consisted of a conducting sphere set oscillating across a diameter. This was the common form of transmitter employed by virtually all the experimenters. Bose seems to have refined his spherical resonator by partially enclosing it in capacitive cups each side, as

Fig. 3. This microwave bench enabled Bose to investigate polar diagrams, crystal lattice diffraction (or its analogue), total internal reflection, refractive indices and so on, all at 60 GHz. (Bose's caption in figure.)

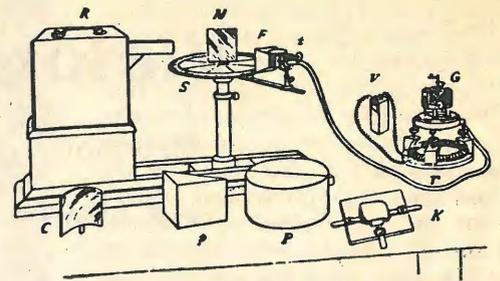

Arrangement of the Apparatus.

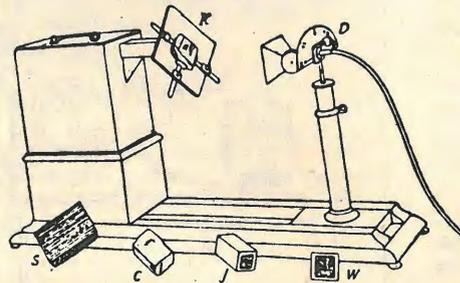
R, radiator; S, spectrometer-circle; M, plane mirror; C, cylindrical mirror; p, totally reflecting prism; P, semi-cylinders; K, crystal-holder; F, collecting funnel attached to the spiral spring receiver; t, tangent screw, by which the receiver is rotated; V, voltaic cell; r, circular rheostat; G, galvanometer.




Polarisation Apparatus.

K, crystal-holder; S, a piece of stratified rock; C, a crystal; J, jute polariser; W, wire-grating polariser; D, vertical graduated disc, by which the rotation is measured.

Fig. 4. It is clear that Bose had all the requisite motions to establish polarisation angles. He must have understood the effect of wire gratings placed parallel, perpendicular and in practice at any angle, to the E-vector of the 60 GHz beam of radiation. (Bose's caption in figure.)

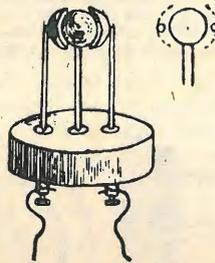

The Radiator.

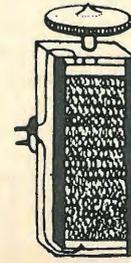

The Spiral-spring Receiver.

Fig. 5. Reproduced here are Bose's capacitively loaded spherical oscillator, and a curious two dimensional spring contact detector.

seen in his drawing reproduced as Figure 5. This must have increased the charge stored, therefore the energy, by capacitive loading. Also, the radiation must have been reduced by the partial screening effect, thus raising the "Q" of the system, which yielded many more cycles of oscillation per discharge than must have been usual. (The bandwidth of the radiation must have been reduced.) It had been reported elsewhere by other members of the "Hertzians" that the damping of an open oscillator of this type was such that normally only one or two complete oscillations were obtained.

The ingenious detector evolved by Bose is also shown in Figure 5. It most likely consists of a space-irradiated multicontact semiconductor (using the natural oxide of the springs) plus some cohering action. But from Bose's reports this action, unlike most coherers, appeared to be self-decohering.

One of his experiments involved Bradshaw's Railway timetable, inter-

leaved with sheets of tinfoil in the pages, as a cut off metal plate grating. Also, one of his millimetre aerials used a sulphur lens, shaped to the required curve by using the refractive index as measured on the bench at 60 GHz.

A most remarkable development carried out by Bose has already been mentioned. His use of microwave horn aerials occurred well before the turn of the century. No doubt he considered that the larger collecting area of a horn aperture would increase the energy incident on his detector – reasoning precisely in the same way as a microwave engineer now designing his receiving aerial for a communication, links or satellite ground station.

All these workers generated radio frequency powers of considerable magnitude, so they were not energy limited. Oliver Lodge estimated that one of the shock excited oscillators that were in popular use at the time developed a peak power of some 70 kW. He goes on to say that sparks could be drawn from

all sorts of metal pipe wires and fittings, and that fuses were regularly blown by the received power that was picked up by the electrical system of the building, when the sending apparatus was operating.

In 1896, Lord Rayleigh⁸ published a complete solution to Maxwell's equations yielding all the possible modes in rectangular and circular waveguides, complete with Bessel's functions and all. Thus the stage was set for point to point communications links with parabolic aerials, waveguide feeders, increasingly sensitive detectors – and even microwave Radio Astronomy of the Sun as Oliver Lodge proposed, and actually attempted.

Yet one of the most remarkable mysteries in science and technology is that none of this occurred. The subject faded rapidly from the scene. Hertz was dead, the others seemed to switch to new fields of work. Microwave electronics was before its time and had to wait half a century until just before the second world war for Southworth, Chu, Schel-

kunoff and others, to make the re-discovery and begin the applications.

Lodge, who was the outstanding British figure in this work, became increasingly involved in running a University, and took an increasing interest in the paranormal, becoming in fact President of the Society for Psychical Research. He continued to write many instructive articles on "wireless" in the journals such as the early editions of *Wireless World*, and was elected President of the Radio Society of Gt Britain for the year 1925.

Bose moved on to investigations of plant growth and the effects of e.m. radiation upon biological structures. All the other workers faded from view. Perhaps it was Guglielmo Marconi's great success in using extremely long Hertzian waves for telegraphy that swung all the young engineers away from microwaves. But whatever the historical cause of the moratorium in microwave science, nothing can detract from the lustre of these first pioneers of microwaves at the end of the 19th century.

References

1. Ecclesiastes, ch. 1 and 2. (the 'Tao' of the Old Testament.)
2. See, Joseph Larmor, ed. "The Scientific Writings of the Late F. G. FitzGerald." Longmans Green (London) 1902. Page 100 contains the details of comments FitzGerald made at the 1883 British Association meeting in Dublin.
3. H. Hertz. "Electric Waves." Macmillan and Co. 1893. (Reprint by Dover available.)
4. O. J. Lodge. "Signalling Through Space Without Wires". 'The Electrician' Printing and Publishing Co. 1898.
5. Derek De Solla Price. "Big Science, Little Science". New York, Columbia University Press, 1963.
6. A. Righi. "L'Ottica delle Oscillazioni Elettiche".
7. J. C. Bose. "Collected Physical Papers". Longmans Green, NY. 1927.
8. Lord Rayleigh. "On the Passage of Electric Waves Through Tubes . . ." *Phil. Mag.* vol. 43, pp 125 to 132, February 1897.

Oliver Lodge had a paper on the history of his own contributions to early radio science in "*Wireless World*," July 1st. 1922. He was President of the R.S.G.B. during the year 1925. □

Books Received

The latest offering in the Newnes Technical Books' "Master" series, in this case **Master Hi-Fi Loudspeakers and Enclosures**, by Dave Berriman, offers some interesting and attractive material covering the essentials of each element of the loudspeaker, both as individual items and in concert with the box. However, those who are observant will notice a tendency to gloss over the hairy areas, such as the power output losses incurred by passive filter networks. Active networks are not even mentioned, but the nice paper and intermittent two-colour presentation (blue type-face for captions on illustrations and silky white paper throughout), added to the fairly wide spread given to the subject, makes the book a good buy at £2.95 in limp back. One nasty inconsistency is that represented by the cover illustration. A confused shopper stands in front of a pile of speakers with the slogan "Special Offer", but as Mr Berriman provides no information at all on the efficiency/price relationship in the book, it could prove frustrating for some. Butterworth and Co. (Publishers) Ltd., 88 Kingsway, London, WC2B 6AB.

"**Starting and Running a Small Business**", first published in 1977, must be one of those books which (ideally) should help to swell anyone's profits from business. The author, Alan Sproxtton, outlines with admirable candour the main objection to the use of the book as an aid to money-making or the fractional reduction of the dole queue when he points out that he has so far managed to avoid making a fortune himself. Maybe fortunes aren't to be made in small business but it can't help circulation to act as your own devil's advocate. Nevertheless, the same general advice holds good in this up-dated version as did in the 1977 printing, though with more acid heaped upon Civil Service and government departments alike. A

humorous and handy volume on the whole. Hardback at £3.95 from United Writers Publications, Trevail Mill, Zennor, St. Ives, Cornwall.

The IEE has recently (March) issued a new edition of its "**Symbols and Abbreviations for Electrical and Electronic Engineering**", and there's not a great deal to say about this except that, as always, it provides the fundamental sign language of electronics as well as quantity symbols for mechanics, heat and illumination among other universal phenomena. It comprises a sixteen page booklet costing 75p from The Institution of Electrical Engineers, Marketing Dept., Station House, Hitchin, Hertfordshire SG5 1RJ.

"**Digital Hardware Design**", by the popular (for us!) team of Catt, Walton and Davidson, converts some of the contributions by Heaviside, S.P. Thompson and Hertz to solutions of digital problems. The ideas are well-explained, the maths fairly easy to handle and the drawings rather poor in places. Nevertheless, some half-forgotten ideas are given a fresh new treatment and appear at a high relevant moment, considering the development of high-speed digital techniques via ECL (emitter coupled logic) and Shottky t.t.l. £4.50 in limp-back from Macmillan Press, 4, Little Essex St., London WC2R 3LF.

"**A Guide to Amateur Radio**", by Pat Hawker, is a hard-back and up-dated version of the well-known booklet version of the 17th edition produced in 1978. This useful work contains two additional sections dealing with fundamentals of electronics and sample RAE examination questions. £5.40 from Butterworth and Co.

Yet another in the massive series of D.A.T.A.

books has appeared. This deals with **memory integrated circuits** and covers 9118 types spread across 51 manufacturers. The technical sections deal with r.a.ms, r.o.ms, character generators, code converters, shift registers and special memory devices including oddities such as trigonometric r.o.ms. — a.t.n, rhythm generators and transistor arrays. This is edition 16 and is, as usual, available from London Information (Rowse Muir) Ltd., Index House, Ascot, Berkshire SL5 7EU at a price of £32.65.

Thermistor stabilizers

continued from page 64

J. L. Linsley Hood's "Low Distortion Oscillator" (*Wireless World*, Oct. 1977 pp 69-70) can be examined. In this case $R_s = 220\Omega$, $R_f = 820\Omega$ and the thermistor is an STCR53. The quoted output is 1.5V and the calculated result is 1.60V. Calculated temperature coefficient is $-22\text{mV}/^\circ\text{C}$, which is equivalent to $-0.118\text{dB}/^\circ\text{C}$. With $R_s = 0$ and $R_f = 127\Omega$ the calculated voltage is 1.01V and the measured voltage 1.1V. The temperature coefficient is then $-4.5\text{mV}/^\circ\text{C}$ or $-0.039\text{dB}/^\circ\text{C}$.

One way to reduce amplitude dependence upon temperature is to operate the thermistor at higher temperatures, but this is not profitable as the instantaneous temperature can rise above the steady-state level even when settling.

In principle it is possible to provide compensation over a temperature "band" by replacing R_f with a thermistor of dissipation factor which is much larger than the output sensing thermistor, or by means of a thermistor/resistor combination.

NEW PRODUCTS

Cassette with die-cast frame

Claiming that its MA-R die-cast (zinc) framed cassette provides improvements in tape-to-head relationships, resulting in reduced levels of wow and flutter etc., TDK points to greater rigidity as the prime source of the improvements. The new cassette features a new type of tape anchorage within "truly circular hubs" which ensures "even, regular spooling." In addition to the new frame and tape anchorage, the cassette contains (C60 size) "metal alloy" tape and a table is provided giving details of the electrical properties of the new tape. Sensitivity figures for the three frequencies of 333Hz, 10kHz and 16kHz are given as 5dB, -0.5dB and 2dB respectively. No information is provided concerning comparative wow and flutter measurements. The main advantage of the "metal alloy" (particle) tape is improved coercivity and remanence. This cassette will be available in the UK in September 1979 and the C60 will retail at about £6. TDK Tape Distributor (UK) Ltd., 11th Floor, Pembroke House, Wellesley Rod., Croydon CR0 9XW.

WW 301

1W (max.) v.h.f. crystal oscillators

A range of fixed-frequency crystal oscillators covering the frequencies 5MHz to 300MHz, the CO-284W series, can deliver an output of up to 1W according to the distributors, Lyons Instruments. Those in the 300MHz to 500MHz range can deliver 0.5W, giving levels of 30dBm and 27dBm for the two range spreads respectively. Oscillators can be supplied as "standard stability" types at ± 20 ppm at temperatures between 0 and 50°C with options of stability to ± 3 ppm and operation over temperature extremes between -55°C to +125°C. Each oscillator is factory-set to within 10 ppm of the specified frequency but adjustment for setting within 1 ppm is available as an option and electronic tuning is available for phase-locking applications. Sup-



WW 301


ply requirements are +15V d.c. at 300mA and the dimensions are 51x76x19mm. The oscillators are manufactured by Vectron Laboratories and the distributors point out that the pricing system is complicated by differences for "standard" and "high" stability units, variations for differing frequency coverage and savings obtained by "bulk" ordering. As an example, an item which costs between £285-£490 as a "one-off" could easily be brought down to the £120-£195 range when ordered as a "100-off". Lyons Instruments, Hoddesdon, Herts.

WW 302

Sub-miniature rotary switch

Full dust-proofing and operation over the temperature range -45°C to +85°C are features of the PS613 series of sub-miniature rotary wafer switches which the manufacturer, Radiatron, claims

WW 302

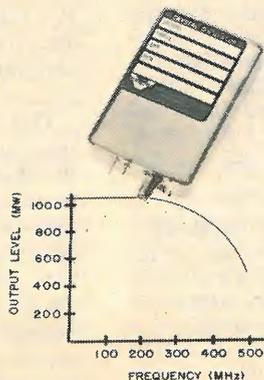


for its recently introduced range. The switches have been designed with miniaturized equipment in mind as well as long life. They may be specified with either silver or AuNi contacts and will switch loads at 110V d.c. or 125V a.c., both at 0.25A. Maximum load current is 1A and either 12 or 6 positions may be selected in both shorting and non-shorting configurations. Each wafer can have one or two poles and each switch can incorporate up to 4 wafers. The overall diameter of each switch is 12mm and a choice of p.c. board mounting or panel types is available. Radiatron Components Ltd, 76 Crown Rd., Twickenham, Middlesex.

WW 303

CW lasers

Two new injection c.w. lasers, offering a 5mW output with a typical beam divergence of 5

WW 303

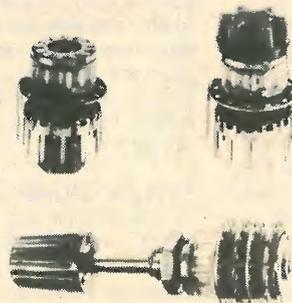

milliradians are now available from Laser Diode Laboratories, a subsidiary of the (American) Valtec Corporation. These devices, which are said to feature high c.w. power output and low beam divergence, are classified as the SCW-30 and SCW-31. Other significant characteristics include a threshold current of 85mA and a peak wavelength of 820 nm. Typical linewidth of the SCW-30 is 1nm and that of the SCW-31 is 0.1nm. Both lasers incorporate the SELFLOC lens and are housed in the LDL-9F package. A 10,000-hour warranty is offered for both items. Walmore Electronics Ltd., 9-15 Betteberton St., Drury Lane, London WC2H 9BS.

WW 304

Combined 5V regulator and bridge rectifier i.c.

A mains transformer, filter capacitor and an r.f. by-pass capacitor are all that is needed to turn a new i.c. from Fairchild (UK) into the central element of a self-contained 5V and 5A power supply. This is the SH1705 and contains the μ A 78H05A regulator in combination with a diode bridge circuit. The usual features of short-circuit protection, thermal shut-down, low drop-out voltage and internal current limiting are included, and if desired the regulator section can be used separately from the bridge rectifier. Absolute maximum ratings are 23V r.m.s. input, 50W internal power dissipation (at a case temperature of 25°C) and a regulator section input/output differential voltage of 25V d.c. (max.). Regulator input is via a separate pin, making it suitable for use in more complex supplies, using other devices. The retail price of the i.c. is £9.71 before v.a.t. Fairchild (UK) Ltd., Potters Bar, Herts.

WW 305

30W opto-isolated switchers

An efficiency level of 70% and remote sensing as a standard feature are two of the quoted points of interest relating to a new range of opto-isolated switchers recently introduced by

Farnell Instruments. These are an extension to the "G" range of switching power supplies and four current combinations can be employed, at 6, 12, 15 and 24V. A further claim is that they will tolerate wide variations in input voltage, i.e. in the range 176 to 264V (a.c.) or 92 to 132V (a.c.). The application of opto-isolation switching techniques has resulted in compact, lightweight power supplies housed in a case measuring 145x88x33mm and exhibiting an insulation tested breakdown point of 5.8kV d.c. input to output. That is, 2.9kV d.c. output to earth and 2.9kV input to earth. In keeping with the rest of the "G" range the unit output is designed to hold up for the duration of a missing mains cycle without the addition of external output capacitors. These switchers comply with the interference requirements of VDE 0875, curve N, CISPR (publication 2) curve N and BS800. Farnell Instruments Ltd., Sandbeck Way, Wetherby, LS22 4DH.

WW 306


Car stereo booster and graphic equalizer

Compensation for high noise levels inside the car can be obtained by boosting the output power of a car stereo system and the RE-482 Car Stereo Booster, in combination with the RE-484 graphic equaliser, can supply this extra feature. The makers, Ross Electronics, say that each unit provides an output of 20W per channel and is fitted with by-pass switches to re-connect the car stereo unit to the speakers direct. Each unit operates only with 12V negative earth systems and output impedance is 4 to 8-. The RE-482 is fitted with bass and treble controls providing, according to the makers, frequency control which can provide a response equivalent to home hi-fi systems. The graphic equalizer offers the same basic tonal variations but the five controls cover centre frequencies of 60Hz, 250Hz, 1kHz, 3.5kHz and 10kHz. The dimensions of the RE-482 are 115x40x150mm, the unit being priced at £27.90 plus v.a.t. while those for the RE-484 are 160x40x150mm, the price of this item being £50.40 plus v.a.t. Ross Electronics, 32 Rathbone Place, London W1P 1AD.

WW 307

Digital thermometer

Covering the range 0 to 400°C, a new digital thermometer offers more durable features than many previous items of a similar nature, according to the makers, DMS Electronics. For example, the probe is permanently wired to minimize errors and is fed with

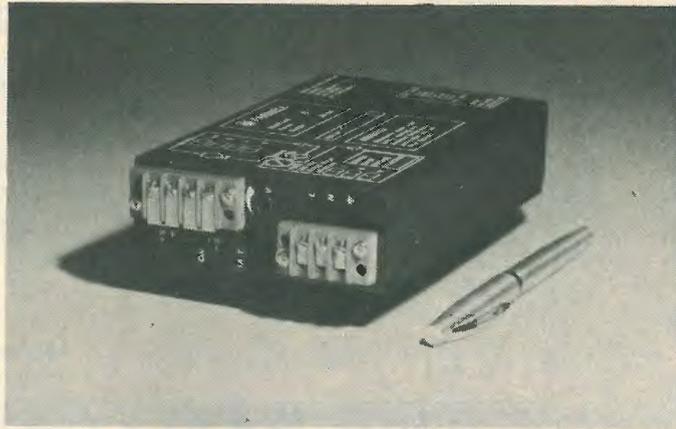

WW 306



WW 307




WW 308

"armoured" coaxial cable for hard wear. Error is ± 1 digit over the entire temperature range with a claimed fast response in changes of temperature. The display is l.c.d. (0.5in) and the low power consumption permits up to 100 hours continuous use from the self-contained rechargeable battery. The instrument is housed in a lightweight ABS case with a protective hinged lid. A carrying wallet is also supplied with the thermometer. DMS Electronics, Unit 10 Willow Close, South Anston, Sheffield S31 7GX.

WW 308

Suppression chokes

Radio frequency interference suppression chokes in a heavy-duty form are being made and marketed by Ashcroft Electronics. Intended for use in vehicles, aircraft and ships, these chokes operate within the range 150kHz to 200MHz (approx.) and are constructed from enamelled wire wound on a ferrite former and connexions are taken to axial lead-outs. A tough plastic outer sheath gives protection against vibration and moisture. Inductance range is 5.5 H to 70 H,

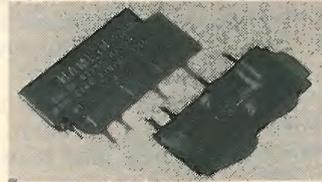

WW 310

tolerance is $\pm 20\%$ and the normal operating temperature range is -40°C to $+85^{\circ}\text{C}$. Ashcroft Electronics, Cirencester, Gloucestershire.

WW 309

Thick-film relays and drivers

Combination of several modern constructional techniques has given rise to a new range of solid state a.c. relays and thyristor drivers from Hamlin Electronics. Designated the 7580 series, the relays are constructed using thick-film technology and optical isolation methods and are formed as a compact single-in-line package occupying less than half a square inch (300mm²) of mounting area. Input/output isolation voltage (max.) is 1,500V. r.m.s. and the device features polarity-protected inputs, zero voltage switching and compatibility with i.c. logic. Load current rating is 2A r.m.s. at a control voltage of 3V d.c. and 1.75A r.m.s. at 32V d.c. Non-repetitive single-cycle surge current is 70A peak, and 1 second overload current is 35A peak. The driver units in this series are intended to interface with logic control circuits and power thyr-

istors operating on the a.c. line. Output current to the thyristor is 50mA r.m.s. (max.) or 150mA pulse current. Both relays and drivers are mounted in a package measuring 40x22x9mm and each weighs 7g. Hamlin Electronics Europe Ltd., Diss, Norfolk.

WW 310

Quick index machine

Rapid access to index details and a capacity of about 1,000 entries are features of an electrically-operated records index, the "Datax," which is available from Hadley Sales Services. Index cards slide in and out of plastic trays and the relevant details are quickly displayed behind a transparent plastic screen in response to the pressing of a button. The information stored could be telephone numbers, part numbers, prices, inventories, customer accounts, etc, and a 30 button keyboard (full alphabetical range) allows flexibility for combinations of letters and numerals. Each unit includes a supply of pre-cut index cards and keyboard tables. The "Datax" is portable and operates either from two HP2 cells or an a.c. mains adaptor. The price is £40 (plus 15% v.a.t.) for the TBX-30 and a smaller version, the TB-15, with a capacity of 360 entries, costs £18 plus 15% v.a.t. Hadley Sales Services, 112 Gilbert Rd., Smethwick, Warley, West Midlands B66 4PZ.

WW 311

Quad v.m.o.s. power f.e.t.

Four independently accessible v.m.o.s. power f.e.t.s. contained in a single 14 pin d.i.l. package and specified as the VQ1000 constitute one of the latest products from Siliconix. The manufacturer claims for this device advantages such as reduced component count, high switching densities and lower than usual assembly costs. Each individual f.e.t. within the package has a maximum switching capability of 60V and a continuous current rating of 0.5A or 1A in pulse applications. In higher power applications each f.e.t. can be connected in parallel externally to take advantage of the load-sharing capabilities of v.m.o.s. devices and typical switching times are as low as 5ns. Applications are various and include t.t.l./c.m.o.s. logic to high power interfacing, i.e.d. digit strobe drivers, high speed line drivers, stepping motor drivers and peripheral control driving circuits. Overall package power dissipation is 1.75W max. at 25°C and each VQ1000 will be available in either plastic or ceramic packages complete with Zener protection. Siliconix Ltd, Morriston, Swansea SA6 6NE.

WW 312

Softly, softly . . .

I would like all manufacturers of domestic audio equipment to pay attention for a moment. It's high time for some plain speaking, so just stop trying to decide which bit of planned obsolescence to build in next and listen to me.

Well, that's it, really. Built-in obsolescence. It never used to be like this. When my father bought us a gramophone, he was reasonably confident that he would have time to get it out of the box before we were made to feel under-privileged by "new technology." At the current frantic rate of innovation, it would barely be fully wound up for the first Gracie Fields record before a new model with oil-fired winding and a cast-iron needle was introduced.

Even motor cars seem to last for a year or two before petrol-pump attendants start sneering at them, and in the other gadget-conscious brotherhood of photography, it is positively not done to have shiny new equipment — not according to glossy ads. for Olympus, at any rate.

What I feel is that it would be rather nice to have time to get the 13A plug on my new cassette deck before the next one is launched (amphibious, are they?). Because that is what this is all about. I want to buy a cassette deck, but by the time these devices have been on the market long enough for the intelligentsia to tell me whether they are any good or not, they can't be found in the shops, having been replaced by new designs with slight and probably unimportant differences. One can't keep up the pace. So, look, chaps, can you hold it for a couple of months, please. I'd quite like to be up there with the cognoscenti for the first time in my life, even if it is only for a week or two.

Paper tigers

When television was young, and keeping up with the Joneses entailed knowing someone who'd been to Torquay instead of Blackpool for the annual fortnight, it was not unknown for the H aerial on a chimney to feed nothing but its own downfall. If the neighbours *thought* you had a television set, that was the main consideration.

That sort of ploy was understandable I suppose, from impecunious high livers, but to transfer the philosophy to the camera end takes a devious mind — the kind which impels people to put notices on the front gate implying that the Hound of the Baskervilles is in residence and praying for a chance to sink its teeth into the juicy bits.

Nevertheless, I do feel a little less threatened than I used to when doing the weekend shopping in the supermarket, because a note came from a firm which makes it its business to keep all us potential shoplifters in line to tell me that the latest line in c.c.t.v. cameras



aren't what they seem. Those devices that follow your every move aren't cameras at all. A new fitting lately on the scene consists of four dummy lenses, mounted on a sort of pudding basin affair and fixed to the ceiling. Red lights flash to make you think that the manager has his little button eyes on you and a sign says "c.c.t.v. pictures relayed to central monitors." The missing articles and verb avoid the accusation of a downright lie, but the message is certainly there.

This isn't the only one of its kind. The same firm do a wall-mounted one which darts quick glances about the shop in an apparently purposeful way. It doesn't have anything behind the "lens," either.

I don't know how long this has been going on, but it's made me feel a bit foolish. It means that all those funny faces I've been pulling at c.c.t.v. cameras have been wasted. I would also have thought that to tell everyone about it would rather tend to reduce the effectiveness of the operation.

Information gap

I'm pretty sure that the most certain way of indicating which gaps in one's education yawn wider than average is to look at the front covers of the IEEE Transactions on various subjects. The front cover is about as far as I usually get because, since the contents list is printed thereon, it is made painfully clear to me that I can't even understand the titles, much less the articles themselves. Faced with a title such as "Recursive implementation of a two-step non-parametric decision rule," I cannot claim that my heartbeat reacts at all dramatically. The effect of "An intrinsic dimensionality estimator from near neighbour information" on my pulse rate can best be described as unspectacular.

It is all very depressing and I was considerably cheered to see, on the first issue of a new Trans., the article "A family of similarity measures between two strings." Well, like most people, I had previously supposed that when you'd seen one piece of string, you'd seen the lot, but I was pleased that there was at least one word in the title that meant something to me. So I took the

not inconsiderable step of opening the journal to read this account, and found that the strings in question were strings of symbols which were either identical ($S=1$) or not like each other one little bit ($S=0$), with shades of similarity in between. Well, that's fine, as far as it goes, but it's the kind of article that does tend to leave me wondering if I've missed the punch line.

What I mean to say is, it's so difficult to obtain even a smattering of the whole field of electronic study. When I was a lad, just after the Flood, a well-rounded engineer was expected to work effectively in any branch of the discipline — from directly-coupled amplifiers to microwaves, from record players to guided weapons, from stabilised power supplies to stabilised platforms. The amount of information released in the last twenty years means that no one, or no one I know anyway, can even comprehend the whole field of interest.

It doesn't half make you feel old.


Les Miserables

As all good chess players know, the only thing to do when your king is pinned down and your queen is about to be abducted is to bend down to stroke the cat and accidentally knock the board on the way up again. In the ensuing argument, you can then maintain that the brilliant coup you were about to pull off would have enabled you not only to escape check, but to mate in the next four moves. When challenged to prove it, you can't, of course, quite remember where the pieces were.

Chess, so I'm told, is popular in France, which possibly explains the unreliability of their telephone system. You don't get the connexion? Well, no — neither did the Post Office Prestel exhibit at the Tele-informatics exhibition in Paris a few weeks ago. It seems that 'Prestel and Didon', a French viewdata system somewhat similar to Prestel, were on neighbouring stands. Comparison was thereby invited — at least, it would have been but for the fact that Didon wouldn't work. Prestel pressed on regardless, the Post Office people no doubt feeling distinctly chuffed by their unforeseen edge over Didon, until just after the relevant French Minister did his walkabout of the show, whereupon the Prestel decoder was left talking to itself. The telephone line had been cut off.

Urgent representations were naturally made, but in spite of the location of the exhibition — the French post office headquarters — the phone stayed dead. A token French engineer came round, said he'd have to get his screwdriver or something, and promptly disappeared into the hinterland. No one is saying anything. Not even why, out of all the telephone lines in use, only the three on the Prestel stand were out.

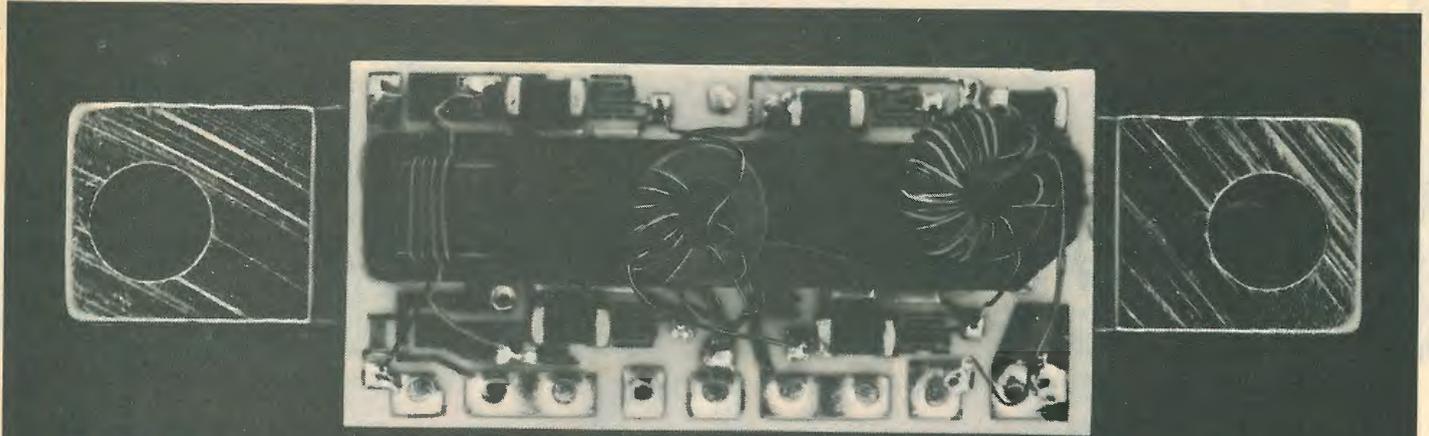
Still, these accidents will happen. Sometimes, it's the only way.



TRW wide bandwidth linear hybrid amplifiers.

All the advantages and reliability of thin-film circuitry and gold metalization techniques.

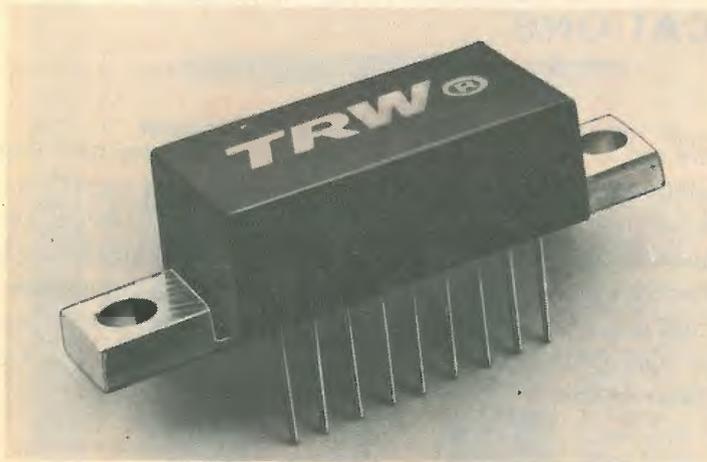The TRW CA2800 series is the perfect answer when you need really stable linear amplification from 10-400MHz. Applications will be IF amplifiers, local oscillator buffer amplifiers, fibre optic drivers, laser/LED diodes or drives for acousto-optic modulators — in fact just about any situation where wideband linear amplification is needed.



Just check opposite the module that suits your particular requirements, then contact MCP for the complete data.

GENERAL PURPOSE HYBRID AMPLIFIERS

PRODUCT SUMMARY

P/N	BANDWIDTH MHz	GAIN DB	OUTPUT POWER 1 DB COMPRESSION
CA 2800	10-400	17	800 mW
CA 2810	10-350	33	800 mW
CA 2818	1-200	18	800 mW
CA 2820	1-520	30	400 mW
CA 2830	5-200	34	1 W
CA 2832	1-200	35	2 W
CA 2833	5-200	34	1 W
CA 2840	30-300	22	1 W
CA 2842	30-300	22	1 W
CA 2850	40-100	17	250 mW
CA 2851	40-100	17	250 mW
CA 2870	20-400	34	400 mW
CA 2875	40-100	17	310 mW
CA 2876	40-100	22	100 mW
CA 2880	40-100	22	100 mW

WW 9/79



To M.C.P. Electronics Ltd.,
Station Wharf, Alperton, Wembley, Middx.
Tel: 01-902 5941.

Please send me full data on the TRW CA2800 wide bandwidth linear hybrid amplifier range.

Name _____

Company _____

Address _____

Tel.: _____

TRW® RF SEMICONDUCTORS

Soundstar

from Beyer Dynamic

- True supercardioid characteristic
- Well balanced, rising frequency response with low frequency roll-off and presence boost
- Built-in hum bucking coil to cancel electromagnetic hum
- Breath and "pop" filter
- On-off switch
- Professional three-pin audio connector




DESCRIPTION AND APPLICATIONS

The Beyer Dynamic model M 400 N (C) soundstar mk II is a unidirectional moving coil microphone, especially designed to meet the demand of musicians, singers and entertainers for an elegant and superb sounding microphone. It is also an excellent microphone for instrument pick up and well suited for a variety of broadcast, recording and stage applications. Its supercardioid pickup pattern minimizes background noise and other undesirable acoustic effects. A highly effective built-in burst filter controls explosive breath and "pop" noises. For boom, stand and hand use, indoor and out, the M 400 is unaffected by humidity and temperature extremes. Its rugged construction makes this microphone particularly suited to withstand the rigors of professional use. The microphone is fully fieldserviceable.

M 400 N (C)

soundstar mk II

Beyer
Dynamic

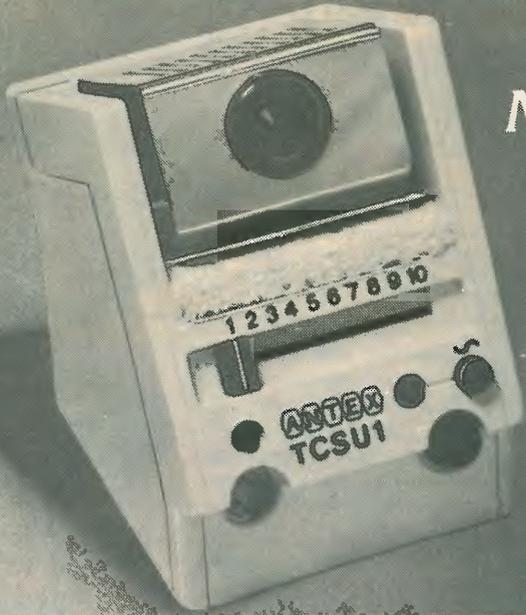

Micro-precision soldering !

ANTEX TCSU1 & CTC

... its the perfect kit

Model TCSU1 Soldering Station

The TCSU1 soldering station with either the XTC 50 watt—24/26 volt soldering iron or the CTC 35 watt—soldering iron for pin point precision and exceptionally fast recovery time. We have put at least twice as much power into irons which are already known for good recovery time. The temperature control stops them from over-heating: the "fail-safe" electronic circuit provides protection even if the thermocouple fails. TCSU1 soldering station with XTC or CTC iron. **£41.54** including VAT (Nett to industry). Postage extra.



Model XTC Priced at **£11.62** inclusive of VAT and P&P



Model CTC Priced at **£11.62** inclusive of VAT and P&P

Model SK3 Kit




Contains both the model CX230 soldering iron and the stand ST3. Priced at **£7.19** inclusive of VAT and P&P. It makes an excellent present for the radio amateur modelmaker or hobbyist.

Model SK4 Kit




With the model X25/240 general purpose iron and the ST3 stand, this kit is a must for every toolkit in the home. Priced at **£7.19** inclusive of VAT and P&P.

Model CX 17 watts

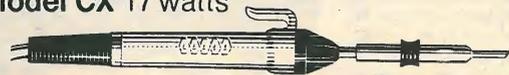

A miniature iron with the element enclosed first in a ceramic shaft, then in a stainless steel. Virtually leak-free. Only 7/8" long. Fitted with a 3/32" bit. **£5.18** inclusive of VAT and P&P. Range of 5 other bits available from 1/4" down to 3/64".

Model X25 25 watts

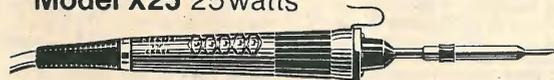

A general purpose iron also with a ceramic and steel shaft to give you toughness combined with near-perfect insulation. Fitted with 3/8" bit and priced at **£5.18** inclusive of VAT and P&P. Range of 4 other bits available.


Model MLX Kit

The soldering iron in this kit can be operated from any ordinary car battery. It is fitted with 15 feet flexible cable and battery clips. Packed in a strong plastic envelope it can be left in a car, a boat or a caravan ready for soldering in the field. Price **£5.69** inclusive of VAT and P&P.




Model SK1 Kit

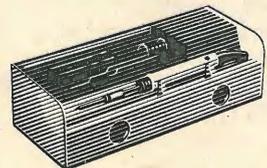This kit contains a 15 watt miniature soldering iron, complete with 2 spare bits, a coil of solder, a heat sink and a booklet, 'How to solder'. Priced at **£7.48** inclusive of VAT and P&P.



Model ST3 Stand

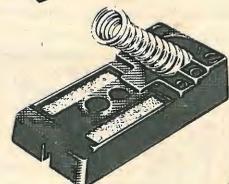A strong, chromium plated, steel spring screwed into a plastic base of high grade insulating material provides a safe and handy receptacle for all ANTEX models soldering irons. Priced at **£2.07** inclusive of VAT & P&P



Stocked by many wholesalers and retailers or direct from us if you are desperate


Please send me the Antex colour brochure I enclose cheque/P.O./Giro No.258 1000

Please send the following

Name

Address

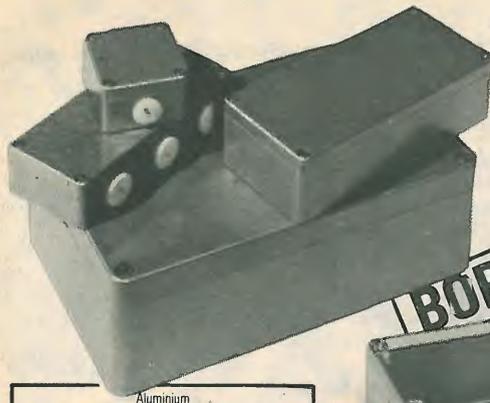Antex Ltd. Freepost, Plymouth PL1 1BR Tel. 0752 67377 www



WEST HYDE
Best Selling BOPLA range




The Bocon is a two-toned high impact polystyrene case to IP44. In dark/light grey, red/black, or clear covers (see cat.).

All the Bopla range, with the exception of BOCON are to IP65 standard, being very accurately made. Their lids are sealed by a recessed continuous ring gasket, which will also resist petrol and oil. Fixing screws are outside the sealed chamber, but inside the case. Bopla are aluminium and Boplast either polycarbonate or glass polyester. Certain sizes can have clear covers.

Aluminium					
L	B	H	L	B	H
A100	50	45	30	2.80	
A101	58	64	34	4.01	
A102	98	64	34	4.71	
A103	150	64	34	6.39	
A105	75	80	57	5.87	
A110	125	80	57	7.67	
A115	175	80	52	8.74	
A117	250	80	52	12.31	
A120	122	120	90	13.36	
A123	220	120	90	16.12	
A124	360	120	80	20.81	
A125	160	160	90	17.68	
A130	260	160	90	22.06	
A135	360	160	90	27.52	
A138	560	160	90	42.24	
A140	200	230	110	37.84	
A160	330	230	110	49.98	
A165	330	230	180	70.78	
A168	400	230	110	64.83	
A195	420	240	210	61.30	

Polycarbonate					
L	B	H	L	B	H
M205	52	50	35	2.31	
M206	65	50	35	3.22	
M210	82	80	55	4.25	
M215	120	80	55	4.84	
M217	122	120	85	6.44	
M220	160	80	85	5.67	
M221	200	120	75	9.61	
M223	200	150	75	10.21	
M225	82	80	85	4.84	
M226	120	80	85	5.67	
M227	122	120	85	7.33	
M228	122	120	110	8.78	
M230	120	80	90	5.67	
M231	160	80	90	6.32	
M235	160	80	90	6.32	
M240	250	160	90	11.60	
M2401	240	160	90	11.60	
M241	250	160	120	15.57	
M242	240	120	100	10.21	
M243	240	160	120	15.53	
M244	340	150	100	17.51	
M245	340	150	120	19.45	
M250	250	160	150	15.53	
M252	300	230	65	16.98	
M253	300	230	85	19.50	
M254	300	230	110	22.41	
M265	360	200	150	28.23	

Glass Polyester					
L	B	H	L	B	H
P305	80	75	50	7.21	
P311	110	75	50	7.88	
P316	160	75	50	8.98	
P319	190	75	50	9.82	
P322	230	75	50	10.65	
P323	55	55	58	6.31	
P324	110	75	75	8.86	
P325	160	75	75	9.65	
P326	80	75	75	7.90	
P327	230	75	75	12.59	
P328	190	100	90	16.50	
P330	160	160	90	21.23	
P333	260	160	90	26.28	
P334	360	160	90	32.76	
P355	400	250	120	61.11	

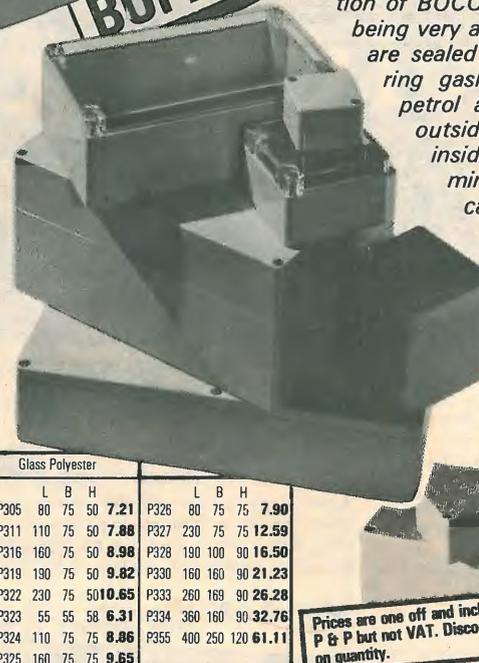

Bocon handles, mounting brackets and aluminium panel versions are also available.



Prices are one off and include P & P but not VAT. Discounts on quantity.

NOTE NEW PHONE NO. WEST HYDE DEVELOPMENTS LIMITED, Unit 9, Park Street Industrial Estate, AYLESBURY, BUCKS. HP20 1ET. Phone: Aylesbury (0296) 20441. Telex: 83570

WW-065 FOR FURTHER DETAILS

TRANSISTORISED DC TO AC INVERTERS

12v-24v-48v dc input models
110v or 240v AC off load
output models
Square-wave output or
optional filtered models
Frequency 50Hz or 60Hz models
(± 5% typical)



All silicon power transistors
Separate driver and output
transformers
Designed for cool continuous
operation
Aluminium ventilated cased units
DC input fused

12v dc inputs / 110v or 240v outputs
50Hz or 60Hz

N12/A—8"x6"x6" 40 watts	£18.00
N12/B—8"x6"x6" 60 watts	£23.20
N12/C—8"x6"x6" 100 watts	£28.10
N12/D—8"x6"x6" 150 watts	£34.50
N12/E—8"x6"x6" 200 watts	£42.00
N12/F—8"x6"x6" 250 watts	£50.60
N12/G—8"x6"x6" 300 watts	£58.00
N12/H—10"x8"x8" 400 watts	£69.80

Filtered waveform models available at 15% extra.

24v dc inputs / 110v or 240v outputs
50Hz or 60Hz

N24/A—8"x6"x6" 40 watts	£19.20
N24/B—8"x6"x6" 100 watts	£29.80
N24/C—8"x6"x6" 150 watts	£36.00
N24/D—8"x6"x6" 200 watts	£44.00
N24/E—8"x6"x6" 250 watts	£52.50
N24/F—8"x6"x6" 300 watts	£60.00
N24/G—10"x8"x6" 400 watts	£71.40
N24/H—10"x8"x6" 500 watts	£83.00
N24/I—12"x8"x8" 700 watts	£101.00
N24/J—12"x8"x8" 1000 watts	£150.00

Filtered waveform models available at 15% extra.

48v dc inputs / 110v or 240v outputs
50Hz or 60Hz

N48/A—8"x6"x6" 50 watts	£20.00
N48/B—8"x6"x6" 100 watts	£31.60
N48/C—8"x6"x6" 150 watts	£37.00
N48/D—8"x6"x6" 200 watts	£45.00
N48/E—8"x6"x6" 250 watts	£54.00
N48/F—8"x6"x6" 300 watts	£62.00
N48/G—10"x8"x8" 400 watts	£73.00
N48/H—10"x8"x8" 500 watts	£86.00
N48/I—12"x10"x8" 700 watts	£112.00
N48/J—12"x10"x8" 1000 watts	£160.00
N48/K—12"x10"x10" 1500 watts	£210.00


Filtered waveform models available at 15% extra.

Please add £5.00 carriage per unit U.K. overseas at cost
Delivery 10 to 21 days subject to availability — Cased sizes subject to variations
Callers strictly by appointment — Telephone enquiries 01-736 0685/01-748 5778

ELECTROVANCE

P.O. BOX 191, LONDON SW6 2LS

WW — 085 FOR FURTHER DETAILS

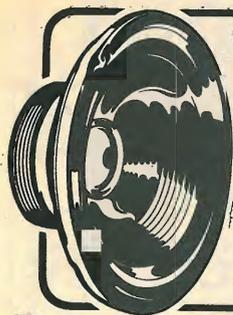

WILMSLOW AUDIO

The firm for Speakers

HI-FI DRIVE UNITS



Audax HD 12 9D25	£7.65
Audax HD13D34H	£12.75
Audax HP11P25EBC	£6.65
Audax HP20B25H4	£13.25
Audax HD24S45C	£20.50
Baker Superb	£25.00
Castle Super 8RS/DD	£12.65
Chartwell CEA205 8" bass, matched pairs only 8 ohm (pair)	£61.25
Coles 4001	£7.65
Coles 3000	£7.65
Celestion HF 1300 II	£8.45
Celestion HF 2000	£10.25
Dalesford D10 tweeter	£8.45
Dalesford D30/110 5in	£11.25
Dalesford D50/153 6½in	£12.25
Dalesford D50/200 8in	£12.25
Dalesford D70/250 10in	£22.25
Dalesford ABR 10in	£10.25
Dalesford D100/310 12in	£35.75
Decca London horn	£57.25
Decca DK30 horn	£43.75
Decca CO/1000/8	£10.25
EMI 14A/770 14in x 9in 8 ohm	£19.50
EMI 8in x 5in d/c, 10 watt, 4 ohm	£4.05
EMI Type 350 4 ohm	£9.45
Isophon KK8/8	£8.15
Isophone KK10/8	£8.45
Jordan Watts Module	£20.40
Jordan Watts HF kit	£9.15
Jordan 50mm unit	£24.50
Jordan CB crossover (pair)	£24.50
Jordan Mono crossover (pair)	£24.50
Kef T27	£9.45
Kef B110	£12.00
Kef B200	£13.25
Kef B139	£27.00
Kef DN13	£5.40
Kef DN 12	£8.65
Kef DN 22 (pair)	£40.85
Lowther PM6	£51.00
Lowther PM7	£88.45
Peerless KO10DT	£10.50
Peerless DT10HFC	£10.50
Peerless KO40MRF	£12.25
Radford BD25 II	T.B.A.
Radford MD9	T.B.A.
Radford MD6	T.B.A.
Radford FN8/FN831	T.B.A.
Richard Allan DT20	£8.95
Richard Allan DT30	£9.45
Richard Allan CG8T	£11.25
Richard Allan CG12T Super	£25.30
Richard Allan LP8B	£11.75
Richard Allan HP8B	£17.60
Richard Allan HP128	£28.40
Seas H107	£8.95
Shackman Electrostatic, c/w polar network and crossover (pair)	£130
Tannoy DC386 15in	£178.90
Tannoy DC296 10in	£107.35

PA GROUP & DISCO UNITS



Baker Group 35	£15.45
Baker Group 50/12	£23.45
Baker Group 50/15	£35.15
Celestion Powercell 12/150	£56.50
Celestion Powercell 15/250	£69.25
Celestion G12/50 Twin cone	£15.95
Celestion G12/80 Cambric edge	£20.25
Celestion G12/80 Twin cone	£19.75
Celestion G12/125 Cambric edge	£35.10
Celestion G15/100 Cambric edge	£31.95
Celestion G15/100 Twin cone	£32.25
Celestion G18/200	£53.25
Celestion MH1000	£15.95
Fane Pop 40	£12.50
Fane Pop 50H	£13.80
Fane Pop 75	£19.70
Fane Pop 65	£21.25
Fane Pop 80	£25.50
Fane Pop 100	£41.80
Fane Guitar 80L	£26.10
Fane Guitar 80B	£27.15
Fane Disco 80	£27.15
Fane PA80	£26.10
Fane Bass 85	£34.00
Fane Crescendo 12E	£57.50
Fane Crescendo 15E	£74.50
Fane Crescendo 18E	£94.75
Fane J44	£6.90
Fane J104	£14.85
Fane J73	£10.90
Fane HPX1/HPX/2	£3.45
Fane HPX3A	£5.60
Fane HPX3B	£4.55
Goodmans 8PA	£5.05
Goodmans 12P	£21.00
Goodmans 12PD	£23.95
Goodmans 12PG	£22.65
Goodmans 18P	£48.45
Goodmans Hifax 50HX	£21.85
Motorola Piezo horn 3½in	£8.50
Motorola Piezo horn 2in x 6in	£12.25
Richard Allan HD8T	£17.00
Richard Allan HD10T	£18.50
Richard HD12T	£24.45
Richard Allan HD15	£43.40
Richard Allan Atlas 15in	£75.00
Richard Allan Atlas 18in	£90.00

WILMSLOW AUDIO



KITS FOR MAGAZINE DESIGNS etc.

Kits include drive units, crossovers, BAF/long fibre wool, etc. for a pair of speakers.	£3.75
Practical Hi-Fi and Audio PRO9-TI (Rogers) Felt panels for PRO9-TL £6.72 plus £1.60 carriage	£138
Hi-Fi Answers Monitor (Rogers)	£146
Hi Fi News State of the Art (Atkinson)	£182
Hi Fi News Miniline (Atkinson) (carriage £2.66)	£48
Hi Fi for Pleasure Compact Monitor (Colloms) (carriage £5.25)	£115
Popular Hi-Fi Mini Monitor (Colloms)	£74
Popular Hi Fi Round Sound (Stephens) including complete cabinet kit	£71
Popular Hi-Fi (Jordan) plus (carriage £2.66)	£93
Practical Hi-Fi & Audio BSC3 (Rogers)	£65
Practical Hi-Fi & Audio Monitor (Giles)	£155
Practical Hi-Fi & Audio Triangle (Giles)	£99
Practical Hi-Fi & Audio Mini Triangle (Giles)	£108
Wireless World Transmission Line (Bailey) KEF	£122
Wireless World Transmission Line (Bailey) RADFORD	£184
Hi-Fi News Tabor (Jones) with J4 bass units	£60
Hi-Fi News Tabor (Jones) with H4 bass units	£66

CARRIAGE & INSURANCE

Tweeters & Crossovers	43p each
Speakers up to 10in.	80p each
Speakers up to 12in.	£1.60 each
Speakers up to 15in.	£2.66 each
Speakers up to 18in	£3.75 each
Speaker kits	£2.66 per pair
Magazine design kits	£3.75 per pair

SPEAKER KITS



Dalesford System 1	£54
Dalesford System 2	£57
Dalesford System 3	£104
Dalesford System 4	£110
Dalesford System 5	£142
Dalesford System 6	£95
Eagle SK210	£17.60
Eagle SK215	£32.60
Eagle SK320	£40.80
Eagle SK325	£68.50
Eagle SK335	£93.00
Goodmans DIN 20 4 ohm (special offer)	£27.60
LS3/5A equivalent kit	£71
Lowther PM6 kit	£105.30
Lowther PM6 Mk 1kit	£110.40
Lowther PM7 kit	£176.85
Peerless 1070	£124.70
Peerless 1120	£142.10
Peerless 2050	£51.10
Peerless 2060	£67.40
Radford Studio 90 kit	£184
Radford Monitor 180 kit	£218
Radford Studio 270 kit	£350
Radford Studio 360 kit	£440
Ram Kit 50 (makes RAM 100)	£71.50
Richard Allan Tango Twin kit	£49.00
Richard Allan Maramba kit	£69.00
Richard Allan Charisma kit	£101.20
Richard Super Triple kit	£81.70
Richard Allan RA8 kit	£52.65
Richard Allan RA82 kit	£83.30
Richard Allan RA82L kit	£89.90
Seas 223	£40.85
Seas 253	£63.10
Seas 403	£76.60
Seas 603	£122.60
Wharfedale Denton XP2 kit	£31.45
Wharfedale Shelton XP2 kit	£40.40
Wharfedale Linton XP2 kit	£56.20
Wharfedale Glendale XP2 kit	£69.00

PRICES CORRECT AT 1/7/79

ALL PRICES INCLUDE VAT @ 15%

Send 15p stamp for free 38 page catalogue 'Choosing a Speaker'


Telephone Speakers, Mail Order and Export 0625 529599
Hi-Fi: (Swift of Wilmslow) 0625 526213.

Lightning service on telephoned credit card orders!

SWIFT
OF WILMSLOW
The firm for Hi-Fi
5 Swan Street,
Wilmslow, Cheshire.

WILMSLOW
AUDIO
The firm for Speakers

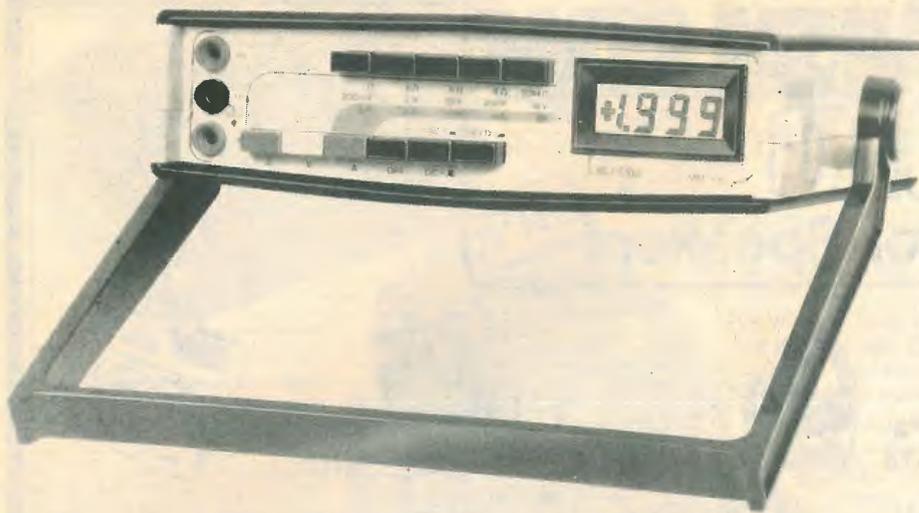Swan Works, Bank Square,
Wilmslow, Cheshire.



Portable Precision

LMM-100 Multimeter

0.1% Accuracy
WITH

Digital Hold

£69.95 + VAT

Crisp 0.5" LCD read-out gives up to 2,000 hrs. battery life with 'Battery Low' warning. Basic Accuracy 0.1%. Ten voltage (min. reading 0.1mV) ten current (min. reading 0.1µA) and five resistance (min. reading 0.1Ω) ranges. Unique 'digital hold' facility for easy data-logging. Auto-polarity and Auto-zero. Inputs protected against overload. Full 2 year warranty. A rugged ABS case with adjustable handle makes the LMM-100 the ideal instrument for bench or field use.

LMM-100 MULTIMETER £69.95. SUITABLE LEADS £1.95. P & P £1.50. ADD 15% VAT TO ALL PRICES.

LASCAR ELECTRONICS · BASILDON (0268) 727383
Unit 1, Thomasin Road, Burnt Mills, Basildon, Essex SS13 1LH

WW-089 FOR FURTHER DETAILS

You can get a lot out of our free catalogue



Future Film Developments

36/38 Lexington Street, London, W1R 3HR.

Tel: 01-437 1892/3

Tlx: 21624 ALOFFD G

WW - 056 FOR FURTHER DETAILS

Catronics FOR BEST VALUE IN THE FINEST SHORTWAVE RECEIVERS

Low SRX30 utilises a drift cancelling loop system to give performance plus 500KHz-30MHz coverage. USB/LSB/AM/CW. 240Vac/12Vdc supply. £179.

Trio R300 with dual conversion on higher frequency band (above 18MHz). 170KHz - 30MHz coverage. USB/LSB/AM/CW. 120Vac/240Vac/12Vdc supply or internal batteries. £189.

Both the above receivers are currently available from stock. Prices INCLUDE VAT but please add £4 for Securicor delivery

CATRONICS FOR THE FINEST AMATEUR RADIO EQUIPMENT

Trio TR2300 2m FM portable transceiver PLL with all 80 FM channels £199

Trio TR3200 70cm FM handy transceiver fitted 3 channels £190

AR240 2m synthesised FM hand-held transceiver in 5KHz channels £199

USED AMATEUR EQUIPMENT

Catronics always have a good selection of reliable used and secondhand equipment — all with 3 months' GUARANTEE, including TR2200G: £100-£120 and Liner 2 £100.

JAYBEAM AERIALS

Catronics stock the full range of VHF and UHF amateur aerials — send S.A.E. for list and special prices.

MICROWAVE MODULES

Converters and transverters for 2m & 70cm — send S.A.E. for illustrated leaflet and price list.

ALL OUR PRICES INCLUDE VAT

EASY TERMS available. Access and Barclaycards welcome

CATRONICS LTD. (Dept. 929) COMMUNICATIONS HOUSE
20 WALLINGTON SQUARE


WALLINGTON, SURREY SM6 8RG
Phone: 01-669 6700. Mon.-Fri. 9 a.m.-5.30 p.m. Sats. 1 p.m.

WW — 929 FOR FURTHER DETAILS


PCB's & CONTACTS CLEANED WITHOUT WATER OR POWDER USING FYBRGLASS BRUSHES

by
RUSH

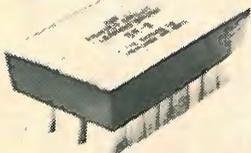Fybrglass PCB brush approx size 76mm x 50mm



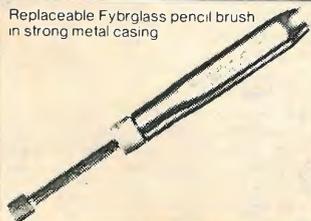Replaceable Fybrglass pencil brush in strong metal casing



ERASER INTERNATIONAL LTD.

Unit M, Portway Industrial Estate
Andover, Hants, SP10 3LU
Tel. 0264 51347

WW—071 FOR FURTHER DETAILS

J. L. Linsley-Hood High Quality Cassette Recorder



We are the Designer Approved suppliers of kits for this excellent design. The Author's reputation tells all you need to know about the circuitry and Hart expertise and experience guarantees the engineering design of the kit. Advanced features include: High quality separate VU meters with excellent ballistics. Controls, switches and sockets mounted on PCB to eliminate difficult wiring. Proper moulded escutcheon for cassette aperture improves appearance and removes the need for the cassette transport to be set back behind a narrow finger trapping slot. Easy to use, robust Lenco mechanism. Switched bias and equalisation for different tape formulations. All wiring is terminated with plugs and sockets for easy assembly and test. Sophisticated modular PCB system gives a spacious, easily built and tested layout. All these features added to the high quality metalwork make this a most satisfying kit to build. Also included at no extra cost is our new HS15 Sendust Alloy record/play head, available separately at £7.60 plus VAT, but included FREE as part of the complete kit at £81.50 plus VAT.

REPRINTS of the 3 articles describing this design 45p No VAT.

REPRINT of Postscript article 30p No VAT.

TEST CASSETTE TC1

Special Hart Copyright test tape makes it easy to set up VU level, head azimuth and tape speed, without test instruments. Suitable for any cassette recorder. Complete with instructions £2.70 inc. VAT.

LINSLEY HOOD CASSETTE RECORDER

Our new improved performance model of the Linsley Hood Cassette Recorder incorporates our VFL 910 vertical front mechanism and circuit modifications to increase dynamic range. Board layouts have been altered and improved but retain the outstandingly successful mother and daughter arrangement used on our Linsley Hood Cassette Recorder 1.

This latest version has the following extra features. Ultra low wow-and-flutter of .09% — easily meets DIN Hi-fi spec. Deck controls latch in rewind modes and do not have to be held. Full Auto stop on all modes. Tape counter with memory rewind. Oil damped cassette door. Latching record button for level setting. Dual concentric input level controls. Phone output. Microphone input facility if required. Record interlock prevents re-recording on valued cassettes. Frequency generating feedback servo drive motor with built-in speed control for thermal stability. All these desirable and useful features added to the excellent design of the Linsley-Hood circuits and the quality of the components used makes this new kit comparable with built-up units of much higher cost than the modest £94.90 + VAT we ask for the complete kit.


SUPER BARGAIN OFFER

LENCO FFR CASSETTE DECK

For those who missed our recent bargain CT4s, we now are delighted to be able to offer Brand New Lenco FFR decks complete with motor speed and solenoid control boards fitted and tested. This deck is almost identical to the CRV lacking only the pause control and record button.

A mono head is fitted but we can supply a stereo head, *bought at the same time*, for only £2 + VAT.

This deck would normally cost about £25, and we are offering it complete with a free escutcheon for the incredibly low price of £9.99 + VAT.

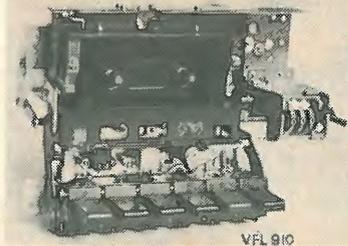

VFL 910. Vertical front loading Super Hi-fi deck, as used in our new Linsley-Hood Cassette Recorder 2. £31.99 + VAT. Set of knobs £1.46 + VAT.

LENCO CASSETTE MECHANISMS

We hold stocks of a range of Lenco tape transports for all uses, we can also supply spare parts. For example:

CRV Motors complete £4.00 plus VAT.

CRV Drive Belts 90p plus VAT.

CASSETTE HEADS

A large range of cassette heads for domestic, industrial and audio visual purposes is available from us. The very best stereo head that we can find is our HS15 Sendust Alloy Super Head. This has an even better high frequency response than our HS14 which it replaces. Unlike cheaper and ferrite types this excellent high frequency performance is combined with a high output, thus maintaining the best possible signal to noise ratio. Price £7.60 plus VAT.

4-TRACK Record/play head. Scans all 4 tracks on cassette tape. Suitable for auto-reverse mechanisms, film sync, quadrophonics and many other purposes. Standard impedance £7.40 plus VAT.

Full details of these and other heads are in our lists.

ALL UK ORDERS ARE POST FREE

Please send 9x4 SAE for lists giving fuller details and price breakdowns.

HART ELECTRONICS

Penylan Mill, Oswestry, Salop

Personal callers are always welcome
but please note we are closed all day Saturday

Instant easy ordering, telephone your requirements and credit card number to us on Oswestry (0691) 2894.

OSCILLOSCOPES — FREQUENCY COUNTERS — OFF-AIR RECEIVERS

**MODEL
S1500
15 MHz
Dual Trace
£280**



**MAINS/BATTERY
PORTABLE OSCILLOSCOPE**

A professional standard model dual trace DC to 15MHz. Usable to 25MHz with alternate, chop and single-channel A or B amplifier selection. 5mv/cm, accuracy 3%. Excellent triggering wide range time base. Natural anodised aluminium case with blue vinyl steel covers, retractable angled feet, carrying handle.

**SUPPLIERS TO: Ministry of Defence, G.P.O., B.B.C., Government
Depts., Crystal Manufacturers and Electronic Laboratories world-wide
for 18 years**



ELECTRONICS, 6 WOLSEY ROAD, ASHFORD, MIDDX. ASHFORD 53661

WW — 060 FOR FURTHER DETAILS



NewBear Books



NEWBEAR MAIL ORDER: 40 Bartholomew Street, Newbury, Berks. Tel: 0635 30505

NORTHERN SHOWROOM: Mersey House, 220-222 Stockport Road, Cheadle Heath, Stockport

Tel: 061 491 2290

GAMES

Chess & Computer	D. Levy	£ 7.16
Chess Skill in Man and Machine	P. Frey	£11.84
32 Basic Programs for the Pet		£ 9.95
Game Playing with Computers	D. Spencer	£10.20
Basic Computer Games	D. Ahl	£ 5.50
Star Ship Simulation		£ 5.10
Game Playing with Basic	D. Spencer	£ 4.10

BASIC

Learning Basic Fast	De Rossi	£ 6.30
Basic Basic	J. S. Coan	£ 5.00
Advanced Basic	J. S. Coan	£ 5.50
Illustrated Basic	D. Alcock	£ 2.25
The Basic Workshop	Hayden	£ 6.60
Basic with Business Applications	Hayden	£ 5.56
Introduction to Basic	J. Morton	£ 6.50
Beginning Basic	P. Gosling	£ 2.95
Introduction to Basic	P. Hartley	£ 1.95

NEW BOOKS

Fundamentals of Computer Algorithms		£15.00
Computer Mathematics		£ 8.58
Top-Down Structured Programming Techniques		£12.76
Microcomputer Design		£ 8.99
A Directory of Microcomputing		£10.00

Z80 BOOKS

Z80 Programming for Logic Design	A. Osbourne	£ 5.95
Z80 Technical Manual	Zilog	£ 4.00
Z80 P10 Technical Manual	Zilog	£ 2.75
Z80 Programming Manual	Zilog	£ 4.50
Z80 Microcomputer Handbook	W. Barden	£ 6.99
Practical Microcomputer Programming (Z80)	Weller	£23.96

"BY RETURN ORDER SERVICE"

6800 BOOKS

6800 Programming for Logic Design	A. Osbourne	£ 5.95
6800 Assembly Language Programming	A. Osbourne	£ 6.95
Using the 6800 Microprocessor		£ 5.65
77-68 6800 Microprocessor		£ 7.50
6800 Software Gourmet Guide Cook Book	Scelbi	£ 7.95
Practical Microcomputer Programming (6800)	Weller	£17.56
The 6800 Microprocessor		£ 3.60
D.N. 4 Definite description of the 6800 Instruction Set		£ 1.50

PASCAL

Pascal: User Manual & Report	Springer-Verlag	£ 5.52
Problem Solving Using Pascal	Springer-Verlag	£ 7.84
Programming in Pascal	P. Grogono	£ 7.50
A Practical Introduction to Pascal	A. Addyman	£ 3.50

6502

The Best of Micro 6502 Journal		£ 5.99
Sym Reference Manual		£ 7.50
Sym Programming Manual		£ 7.50
First Book of Kim		£ 7.00
6500 Hardware Manual		£ 7.50
6500 Programming Manual		£ 7.50
Programming the 6502 SYBEX	Zaks	£ 7.95

COOKBOOKS

Active Filter Cookbook	Lancaster	£10.45
CMOS Cookbook	Lancaster	£ 6.95
IC OP-AMP Cookbook	Jung	£ 9.50
IC Timer Cookbook	Jung	£ 7.50
TTL Cookbook	Lancaster	£ 6.95
T.V. Typewriter Cookbook	Lancaster	£ 7.50
Cheap Video Cookbook	Lancaster	£ 4.30

WW — 101 FOR FURTHER DETAILS

**QUARTZ
CRYSTALS
— FAST!**



AEL CRYSTALS LIMITED
Gatwick House, Horley, Surrey, England RH6 9SU
Telephone: Horley (02934) 5353 Telex: 871116 (Aerocon Horley)
Cables: Aerocon Telex Horley

WW—041 FOR FURTHER DETAILS

**KELSEY K102M TRANSFORMERS
BALANCED LINE MICROPHONE AMPLIFIERS**

Specifications	
Direct P.C.B. mounting	
Supply Voltage	+15V
Maximum Gain	43 dB
Gain Control Range	38 dB
Gain Reduction in Unbalanced Mode (Input to Terminal +)	10 dB
Maximum Input Level (Unbalanced Mode, Input to Terminal +)	+15 dBV
Input Impedance (Each Input Terminal to Ground)	5Kohm
Optimum Source Impedance	200 ohm
Maximum Output	+20 dBV
Frequency Response	+ 0.5dB Ref. 10Hz to 50KHz
Slew Rate	10 V microsec
Harmonic Distortion	Better than 0.03% Ref 1KHz
	Typically 0.02%
Common Mode Rejection Ratio	Better than 80 dB
Equivalent Input Noise (Unweighted)	Better than -125 dBV (Din Audio band weighted)
Recommended Output Loading	10Kohm
Dimensions	40mm x 40mm x 20mm
Weight	48 grams

KELSEY ACOUSTICS LTD 28 POWIS TERRACE, LONDON W11. TEL: 01-727 1046

WW — 106 FOR FURTHER DETAILS



NRDC-AMBISONIC UHJ



SURROUND SOUND DECODER

The **first ever** kit specially produced by Integrex for this British NRDC backed surround sound system which is the result of 7 years' research by the Ambisonic team. W.W. July, Aug., '77.
 The unit is designed to decode not only UHJ but virtually all other 'quadrophonic' systems (Not CD4), including the new BBC HJ 10 input selections.
 The decoder is linear throughout and does not rely on listener fatiguing logic enhancement techniques. Both 2 or 3 input signals and 4 or 6 output signals are provided in this most versatile unit. Complete with mains power supply, wooden cabinet, panel, knobs, etc.

Complete kit, including licence fee **£49.50 + VAT**
 or ready built and tested **£67.50 + VAT**

NEW S5050A STEREO AMP

50 watts rms-channel. 0.015% THD. S/N 90 dB, Mags/n 80 dB.

Tone cancel switch. 2 tape monitor switches.
 Complete kit only **£63.90 + VAT.**



Wireless World DolbyTM noise reducer

Trademark of Dolby Laboratories Inc.



Typical performance

Noise reduction better than 9dB weighted.
 Clipping level 16.5dB above Dolby level (measured at 1% third harmonic content)

Harmonic distortion 0.1% at Dolby level typically 0.05% over most of band, rising to a maximum of 0.12%

Signal-to-noise ratio: 75dB (20Hz to 20kHz, signal at Dolby level) at Monitor output

Dynamic Range >90db

30mV sensitivity.

Featuring:

- switching for both encoding (low-level h.f. compression) and decoding
- a switchable f.m. stereo multiplex and bias filter.
- provision for decoding Dolby f.m. radio transmissions (as in USA).
- no equipment needed for alignment.
- suitability for both open-reel and cassette tape machines.
- check tape switch for encoded monitoring in three-head machines.

Complete Kit **PRICE: £43.90 + VAT**

Also available ready built and tested **Price £59.40 + VAT**

Calibration tapes are available for open-reel use and for cassette (specify which) **Price £2.40 VAT**

Single channel plug-in DolbyTM PROCESSOR BOARDS (92 x 87mm) with gold plated contacts are available with all components **Price £9.00 + VAT**

Single channel board with selected fet **Price £2.75 + VAT***

Gold Plated edge connector **Price £1.75+VAT**

Selected FETs **65p** each + VAT, **110p** + VAT for two, **£2.10** + VAT for four.

Please add VAT @ 15%

We guarantee full after-sales technical and servicing facilities on all our kits, have you checked that these services are available from other suppliers?



INTEGREX LTD.


*Please send SAE for complete lists and specifications
**Portwood Industrial Estate, Church Gresley,
 Burton-on-Trent, Staffs DE11 9PT
 Burton-on-Trent (0283) 215432 Telex 377106**

INTEGREX

S-2020TA STEREO TUNER/AMPLIFIER KIT

SOLID MAHOGANY CABINET

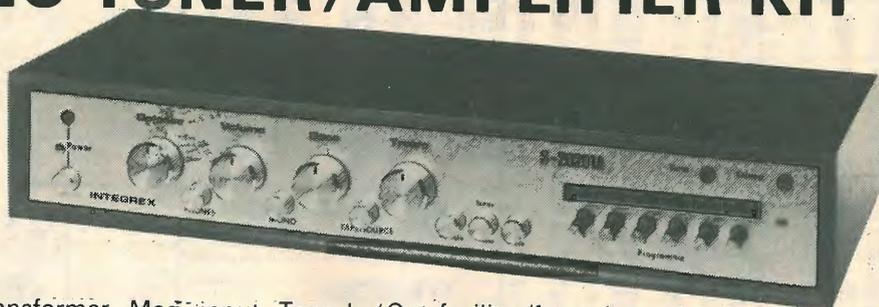A high-quality push-button FM Varicap Stereo Tuner combined with a 24W r.m.s. per channel Stereo Amplifier.




Brief Spec. Amplifier Low field Toroidal transformer, Mag. input, Tape In/Out facility (for noise reduction unit, etc.), THD less than 0.1% at 20W into 8 ohms. Power on/off FET transient protection. All sockets, fuses, etc., are PC mounted for ease of assembly. Tuner section uses 3302 FET module requiring no RF alignment, ceramic IF, INTERSTATION MUTE, and phase-locked IC stereo decoder. LED tuning and stereo indicators. Tuning range 88-104MHz. 30dB mono S/N @ 1.2µV. THD 0.3%. Pre-decoder 'birdy' filter. **PRICE: £59.95 + VAT**

NELSON-JONES MK.2 STEREO FM TUNER KIT Price: **£69.95 + VAT.**
Improved performance with linear phase IF and second generation IC decoder.

NELSON-JONES MK. I STEREO FM TUNER KIT

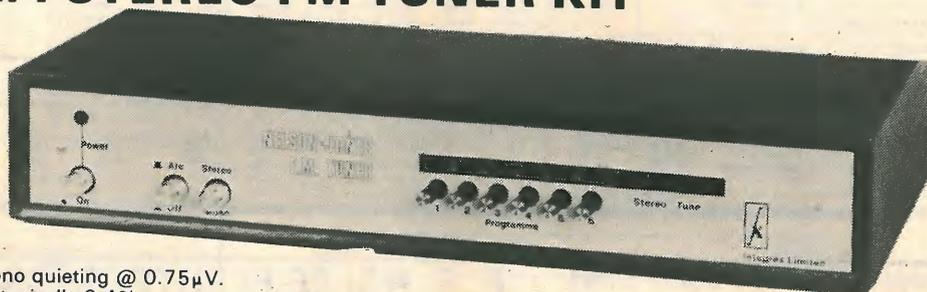A very high performance tuner with dual gate MOSFET RF and Mixer front end, triple gang varicap tuning, and dual ceramic filter / dual IC IF amp.



Brief Spec. Tuning range 88-104MHz. 20dB mono quieting @ 0.75µV. Image rejection - 70dB. IF rejection - 85dB. THD typically 0.4%. IC stabilized PSU and LED tuning indicators. Push-button tuning and AFC unit. Choice of either mono or stereo with a choice of stereo decoders.

Compare this spec. with tuners costing twice the price.

Mono £36.40 + VAT

With ICPL Decoder £40.67 + VAT

With Portus-Haywood Decoder

£44.20 + VAT



Sens. 30dB S/N mono @ 1.2µV
THD typically 0.3%
Tuning range 88-104MHz
LED sig. strength and stereo indicator

STEREO MODULE TUNER KIT

A low-cost Stereo Tuner based on the 3302 FET RF module requiring no alignment. The IF comprises a ceramic filter and high-performance IC Variable INTERSTATION MUTE. PLL stereo decoder IC. Pre-decoder 'birdy' filter Push-button tuning

PRICE: Stereo £33.95 + VAT



S-2020A AMPLIFIER KIT

Developed in our laboratories from the highly successful "TEXAN" design. PC mounting potentiometers, switches, sockets and fuses are used for ease of assembly and to minimize wiring. Power 'on/off' FET transient protection.

Typ Spec. 24+24W r.m.s. into 8-ohm load at less than 0.1% THD. Mag. PU input S/N 60dB. Radio input S/N 72dB. Headphone output. Tape In/Out facility (for noise reduction unit, etc.). Toroidal mains transformer.

PRICE: £35.95 + VAT

BASIC NELSON-JONES TUNER KIT	£15.70 + VAT	PHASE-LOCKED IC DECODER KIT	£4.47 + VAT
BASIC MODULE TUNER KIT (stereo)	£18.50 + VAT	PUSH-BUTTON UNIT	£6.00 + VAT
PORTUS-HAYWOOD PHASE-LOCKED STEREO DECODER KIT			£8.80 + VAT

B-I-P-A-Y

**SEMICONDUCTORS SEND YOUR ORDERS TO
DEPT. WW 9, PO BOX 6, WARE, HERTS.
VISIT OUR SHOP AT: 3 BALDOCK ST, WARE, HERTS.
TEL: 0920 3182. TELEX: 817861**

TRANSISTORS

AC126	£0.21	BC148	£0.08	BC549	£0.12	BU105	£1.84	ZTX109	£0.11
AC127	£0.21	BC149	£0.08	BC550	£0.12	BU105/02	£2.24	ZTX300	£0.13
AC128	£0.18	BC157	£0.12	BC556	£0.16	BU204	£1.81	ZTX500	£0.14
AC128K	£0.30	BC158	£0.12	BC557	£0.15	BU205	£2.58	2N1613	£0.23
AC132	£0.23	BC159	£0.12	BC558	£0.14	BU208/02	£2.58	2N1711	£0.23
AC134	£0.23	BC167	£0.14	BC559	£0.16	MJE2955	£1.04	2N1889	£0.51
AC137	£0.23	BC168	£0.14	BC560	£0.16	BD115	£0.58	MJE3055	£0.69
AC141	£0.25	BC169	£0.10	BD116	£0.92	BD121	£0.75	MJE3440	£0.60
AC141K	£0.35	BC169C	£0.12	BD121	£0.92	BD124	£0.81	MPF102	£0.32
AC142	£0.23	BC170	£0.10	BD124	£0.81	BD132	£0.40	MPF104	£0.32
AC176	£0.21	BC171	£0.10	BD131	£0.40	BD133	£0.40	MPF105	£0.40
AC176K	£0.30	BC172	£0.10	BD132	£0.40	BD135	£0.46	MPSA05	£0.23
AC178	£0.21	BC173	£0.10	BD135	£0.46	BD136	£0.40	MPSA55	£0.23
AC179	£0.29	BC177	£0.10	BD136	£0.40	BD137	£0.40	MPSA56	£0.23
AC180	£0.23	BC178	£0.18	BD137	£0.40	BD138	£0.41	OC22	£0.25
AC180K	£0.32	BC179	£0.18	BD138	£0.41	BD139	£0.41	OC23	£1.73
AC181	£0.23	BC180	£0.29	BD139	£0.41	BD140	£0.41	OC25	£1.15
AC181K	£0.32	BC181	£0.10	BD140	£0.41	BD155	£0.92	OC26	£1.15
AC187	£0.32	BC182	£0.10	BD155	£0.92	BD175	£0.69	OC28	£1.15
AC187K	£0.40	BC183	£0.10	BD175	£0.69	BD176	£0.69	OC29	£1.09
AC188	£0.21	BC183L	£0.10	BD176	£0.69	BD177	£0.78	OC35	£1.03
AC188K	£0.32	BC184	£0.10	BD177	£0.78	BD178	£0.78	OC36	£1.03
AD140	£0.69	BC207	£0.13	BD178	£0.78	BD179	£0.88	OC70	£0.27
AD142	£0.88	BC208	£0.13	BD179	£0.88	BD200	£0.92	OC71	£0.17
AD143	£0.88	BC209	£0.14	BD200	£0.92	BD201	£0.92	TIC44	£0.40
AD149	£0.69	BC210	£0.10	BD201	£0.92	BD202	£0.92	TIC45	£0.33
AD161	£0.40	BC212L	£0.10	BD202	£0.92	BDY20	£0.92	TIP29A	£0.46
AD162	£0.40	BC213	£0.10	BDY20	£0.92	BF457	£0.43	TIP29B	£0.48
AD161P	£0.81	BC213L	£0.10	BF457	£0.43	BF458	£0.43	TIP29C	£0.51
1P29MP	£0.81	BC214	£0.10	BF458	£0.43	BF459	£0.44	TIP30A	£0.46
AF124	£0.35	BC214L	£0.10	BF459	£0.44	BF591	£0.35	TIP30B	£0.46
AF125	£0.35	BC227	£0.10	BF591	£0.35	BF592	£0.35	TIP30C	£0.46
AF126	£0.35	BC238	£0.18	BF592	£0.35	BF593	£0.35	TIP30D	£0.46
AF127	£0.37	BC251	£0.17	BF593	£0.35	BFX30	£0.25	TIP30E	£0.46
AF139	£0.40	BC251A	£0.18	BF594	£0.32	BFX85	£0.28	TIP31A	£0.46
AF186	£0.58	BC301	£0.32	BF594	£0.32	BFX86	£0.29	TIP31B	£0.46
AF186K	£0.69	BC302	£0.32	BF595	£0.32	BFX87	£0.25	TIP31C	£0.50
AF239	£0.39	BC303	£0.33	BF595	£0.32	BFX88	£0.25	TIP31D	£0.50
AL102	£1.38	BC303	£0.33	BF596	£0.32	BFX89	£0.25	TIP31E	£0.50
AL103	£1.36	BC304	£0.44	BF596	£0.32	BFX90	£0.25	TIP32A	£0.46
AU104	£1.81	BC327	£0.18	BF597	£0.32	BFY50	£0.18	TIP32B	£0.48
AU110	£1.81	BC328	£0.17	BF597	£0.32	BFY51	£0.18	TIP32C	£0.48
AU113	£1.81	BC337	£0.17	BF598	£0.32	BFY52	£0.18	TIP32D	£0.48
BC107A	£0.09	BC407	£0.17	BF598	£0.32	BFY53	£0.18	TIP32E	£0.48
BC107B	£0.10	BC408	£0.17	BF599	£0.32	BFY54	£0.18	TIP41A	£0.50
BC107C	£0.12	BC441	£0.35	BF599	£0.32	BFY55	£0.18	TIP41B	£0.52
BC108A	£0.09	BC460	£0.44	BF599	£0.32	BFY56	£0.18	TIP41C	£0.55
BC108B	£0.11	BC461	£0.44	BF599	£0.32	BFY57	£0.18	TIP42A	£0.50
BC108C	£0.12	BC477	£0.23	BF599	£0.32	BFY58	£0.18	TIP42B	£0.52
BC109A	£0.09	BC478	£0.23	BF599	£0.32	BFY59	£0.18	TIP42C	£0.55
BC109B	£0.10	BC479	£0.23	BF599	£0.32	BFY60	£0.18	TIP42D	£0.55
BC109C	£0.12	BC547	£0.12	BF599	£0.32	BFY61	£0.18	TIP42E	£0.55
BC147	£0.08	BC548	£0.12	BF599	£0.32	BFY62	£0.18	TIP955	£0.69
				20MP	£0.92	TS147	£0.23	TIP956	£0.69
				BRY39	£0.51	ZTX107	£0.11	TIP957	£0.69
						ZTX108	£0.11	TIP958	£0.69

74 SERIES TTL

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
7400	£0.10	7427	£0.27	7472	£0.23	74105	£0.43	74163	£0.71
7401	£0.12	7428	£0.29	7473	£0.28	74107	£0.27	74164	£0.78
7402	£0.12	7430	£0.12	7474	£0.28	74110	£0.41	74165	£0.78
7403	£0.12	7432	£0.25	7475	£0.33	74111	£0.66	74166	£0.99
7404	£0.12	7433	£0.34	7476	£0.28	74118	£0.92	74174	£0.74
7405	£0.12	7437	£0.25	7480	£0.50	74119	£1.35	74175	£0.71
7406	£0.25	7438	£0.24	7481	£0.97	74121	£0.27	74176	£0.66
7407	£0.25	7440	£0.13	7482	£0.97	74122	£0.44	74177	£0.66
7408	£0.14	7441	£0.57	7483	£0.66	74123	£0.46	74180	£1.72
7409	£0.14	7442	£0.46	7484	£1.01	74136	£0.59	74181	£0.66
7410	£0.12	7443	£0.80	7485	£0.78	74141	£0.63	74182	£0.80
7411	£0.19	7444	£0.80	7486	£0.25	74145	£0.63	74184	£0.80
7412	£0.17	7445	£0.74	7489	£1.95	74150	£0.78	74190	£0.78
7413	£0.27	7446	£0.69	7490	£0.36	74151	£0.55	74191	£0.71
7414	£0.57	7447	£0.55	7491	£0.93	74153	£0.55	74192	£0.69
7415	£0.26	7448	£0.64	7492	£0.40	74154	£0.94	74193	£0.66
7416	£0.26	7450	£0.12	7493	£0.34	74155	£0.57	74194	£0.71
7417	£0.12	7451	£0.12	7494	£0.86	74156	£0.57	74195	£0.69
7420	£0.17	7452	£0.12	7495	£0.57	74157	£0.57	74196	£1.20
7421	£0.18	7453	£0.12	7496	£0.57	74160	£0.66	74197	£1.20
7422	£0.12	7454	£0.12	7497	£0.57	74161	£0.71	74198	£2.12
7423	£0.24	7460	£0.12	74100	£0.97	74162	£0.71	74199	£2.12
7425	£0.21	7470	£0.28	74104	£0.44				
7426	£0.26								

CMOS ICs

Type	Price								
CD4000	£0.16	CD4015	£0.87	CD4026	£1.38	CD4043	£1.01	CD4070	£0.19
CD4001	£0.17	CD4016	£0.48	CD4027	£0.57	CD4044	£0.94	CD4071	£0.19
CD4002	£0.18	CD4017	£0.88	CD4028	£0.78	CD4045	£1.61	CD4072	£0.19
CD4006	£1.05	CD4018	£0.97	CD4029	£0.97	CD4046	£1.49	CD4080	£0.19
CD4007	£0.19	CD4019	£0.48	CD4030	£0.55	CD4047	£1.00	CD4082	£0.20
CD4008	£1.05	CD4020	£1.03	CD4031	£2.30	CD4048	£0.48	CD4510	£1.13
CD4009	£0.51	CD4021	£0.94	CD4035	£1.15	CD4050	£0.48	CD4511	£1.09
CD4010	£0.55	CD4022	£1.94	CD4037	£1.09	CD4054	£1.26	CD4516	£1.15
CD4011	£0.17	CD4023	£0.17	CD4040	£1.01	CD4055	£1.15	CD4518	£1.15
CD4012	£0.18	CD4024	£0.17	CD4041	£0.87	CD4056	£1.55	CD4522	£1.15
CD4013	£0.48	CD4025	£0.74	CD4042	£0.82	CD4069	£0.19	CD4014	£0.92

LINEAR

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
CA3011	£1.95	CA3130	£1.06	MC1350	£1.38	UA710C	£0.46	SN76115	£2.18
CA3012	£1.55	CA3140	£0.80	MC1352	£1.61	UA710D	£0.34	SN7660	£0.66
CA3018	£0.74	LM301	£0.33	MC1468	£3.50	UA711C	£0.36	SL414	£2.24
CA3020	£1.95	LM304	£1.84	MC1496	£1.03	UA7211	£0.36	TA5508	£2.30
CA3028	£0.92	LM308	£1.15	NE536	£3.05	UA723C	£0.52	TA621A	£2.30
CA3035	£1.81	LM309	£1.72	NE550	£1.09	UA723D	£0.52	TA621B	£2.87
CA3036	£1.15	LM320-5V	£1.72	NE555	£0.27	UA741C	£0.27	TA661	£1.72
CA3042	£1.72	LM320-12V	£1.72	NE560	£0.69	UA741D	£0.27	TA610	£1.49
CA3043	£2.12	LM320-15V	£1.72	NE565	£0.57	UA741E	£0.23	TB450	£2.41
CA3046	£0.80	LM320-24V	£1.72	NE566	£1.38	UA747C	£0.69	TB4810S	£0.86
CA3052	£1.84	LM380	£0.97	NE567	£1.95	UA747D	£0.69	TB4810	£1.12
CA3054	£1.26	LM381	£1.66	UA702C	£0.52	UA748	£0.40	TB4820	£0.80
CA3075	£1.72	LM390	£0.66	72102	£0.52	72748	£0.40	TB4920	£2.87
CA3081	£1.72	LM1303L	£0.97	UA703	£0.28	748P	£0.40	TCA2705	£2.30
CA3089	£2.30	MC1304	£2.18	UA709	£0.28	SN75013N	£2.01	TB4800	£0.92
CA3090	£4.14	MC1310	£1.09	72709	£0.52	SN76023	£2.01		
CA3123	£2.18	MC1312	£2.18	709P	£0.28	SN76110	£1.72		

THYRISTORS

Volts No.	Price	Volts No.	Price	Volts No.	Price	Volts No.	Price
50 THY1A/50	£0.29	50 THY7A/50	£0.55	50 THY3A/50	£0.32	100 THY10A/50	£0.58
100 THY1A/100	£0.32	100 THY7A/100	£0.58	100 THY3A/100	£0.34	200 THY10A/100	£0.65
200 THY1A/200	£0.36	200 THY7A/200	£0.60	200 THY3A/200	£0.		

scope for recording

Video Images

The provision of permanent low cost records without delay from ultrasound equipment is useful both in the medical field, for cardiac and foetal imaging and in industry for non-destructive testing.


The wideband video modulation, high resolution and good grey scale makes the Fibre Optic Recorder an ideal read-out. Alpha-numeric data and time codes may easily be included in the hard copy. Fibre Optic Recorders now offer full video bandwidth and may be used on high speed facsimile systems and for the generation of pictorial records from weather satellite transmissions and from scanning electron microscopes.

Suitable papers in either 100mm or 200mm width, include dry direct print UV sensitive emulsions where limited grey scale is acceptable and similar chemically processed papers for good photographic quality. (Illustration shows Side Scan Sonar read-out)

Medelec Fibre Optic Recorders are also used for research and development in Digital Data, Noise and Vibration, Transients and many other fields.



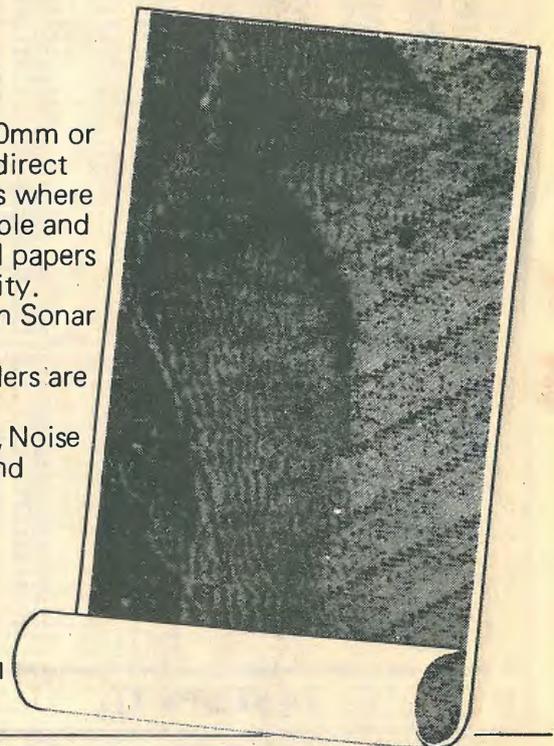MEDELEC LIMITED
Manor Way, Woking, Surrey
Telephone: Woking (04862) 70331
Telex: 859141 Medlec G



WW - 064 FOR FURTHER DETAILS

THE VALVE AND TUBE SPECIALISTS

Type No.	Price Ea.	Type No.	Price Ea.	Type No.	Price Ea.	Type No.	Price Ea.	Type No.	Price Ea.	Type No.	Price Ea.	Type No.	Price Ea.	Type No.	Price Ea.	Type No.	Price Ea.	Type No.	Price Ea.		
A2233	4.85	E55L	21.00	*EF95	4.19	M24-3025H	26.50	*PL84	1.00	*UBF80	1.10	*630L2	1.56	*6F66B	1.75	56TVP-03	466.70	5551A	73.25	6227	5.96
A2426	14.25	E80CC	5.00	*EF183	1.36	M24-302W	26.50	*PL95	1.20	*UBF89	1.10	*64B4	1.25	*6GAB	1.56			5552A	99.00	6252	26.75
*A34-510W	21.16	E80CF	7.00	*EF184	1.44	M31-3126H	33.00	*PL500	1.20	*UBL21	1.40	*6AJ8	2.32	*6GWB	1.58	75C1	1.80	5557	19.15	6267	4.40
AH205	38.68	E80F	6.32	*EH90	1.25	M31-3128	33.00	*PL504/505	2.00	*UCC85	1.10	*6AK5	2.44	*6J4	1.50			5559	36.45	6360	1.50
AH238	24.30	E81CC	2.40	*EL30	0.96	M31-3346H	33.00	*PL506	2.20	*UCB1	1.50	*6AK6	2.33	*6J6	6.58	85A1	7.00	5651	1.75	6574	15.66
AH2511	25.80	E82CC	8.51	*EL34	2.24	M31-334W	33.00	*PL509	3.15	*UCL81	0.75	*6AK7	4.80	*6J7	5.54	85A2	1.75	5654	2.50	6589	5.64
AT1038-40	62.50	E83CC	7.48	*EL36	1.94	M38-3126H	37.50	*PL802	2.95	*UCL82	1.66	*6AL5	0.88	*6L12	1.16			568	6.34	6622	4.98
*A231	9.15	E83F	4.50	*EL37	6.75	M38-312W	37.50	*PY33	1.00	*UFB0	0.75	*6AMS	6.00	*6L13	0.68	90AG	8.10	5696	2.60	6639	9.90
*A241	1.65	E84C	5.64	*EL38	10.50	M8079	9.60	*PY81	1.00	*UFB5	0.65	*6AM6	1.60	*6L16	1.19	90AV	8.10	5687	59.30	6673	3.70
*865	1.70	E88C	10.35	*EL41	2.25	M8081	7.79	*PY82	0.75	*UFB9	0.75	*6AJ5	1.12	*6L66A	1.44	90C1	1.62	5688	76.82		
*8309	0.80	E88CC-01	5.56	*EL41	1.90	M8082	3.00	*PY83	0.75	*UFB4	1.44	*6AJ6	2.52	*6L76T	3.00	90C6	13.68	5694	31.00	7062	5.87
*8319	0.84	E90F	4.92	*EL41	1.20	M8089	8.99	*PY88	1.36	*UVA1	0.95	*6AQ5	1.68	*6R12	0.88	90CV	13.30	5726	9.75	7082	150.95
*8329	0.68	E90F	6.35	*EL42	1.15	M8098	4.80	*PY500	2.24			*6AQ8	1.16	*6P15	1.15	92AG	7.96	5751	4.00	7527	62.67
B1153	109.98	E130L	20.33	*EL90	2.16	M8100	6.81	*PY500A	2.24	XG1-2500	58.35	*6AR3	6.40	*6R3	3.38	92AV	7.96	5753	3.12	7534	20.33
BK656	59.15	E180CC	5.87	*EL91	5.58	M8137	7.23	*PY801	1.26	XG2-500	45.87	*6AS7	1.95	*6S2	0.84					7643	9.90
BK448	73.25	E180F	6.48	*EL92	1.22	M8161	6.52			XG5-500	30.62	*6AT6	1.23	*6S7	2.44	108C1	2.36	6057	2.10	7788	10.07
BK484	99.00	E182CC	6.34	*EL90A	4.12	M8223	2.70	00V02-6	9.90	XR1-1600A	22.50	*6AW6	0.96	*6S7T	1.60			6058	2.10		
B75	36.00	E186CC	8.04	EL821	8.20	M8248	4.85	00V03-10	4.50	XR1-6400A	80.00	*6AV6	1.88	*6S7T	1.22	150B3	4.10	6060	1.00		
B759	26.70	E186CC	5.28	EL822	6.44	ME1400	4.85	00V03-20A	18.00	ZM1550	3.38	*6BA6	0.80	*6S7T	1.08	150C2	1.45	6064	1.65		
B717	55.05	E20F	21.43	EW10	15.00			00V06-40A	31.00	ZM1551	3.76	*6BA8	0.96	*6X4	1.08	150C3	1.92	6080	7.00		
B719	22.20	E283CC		EW32	15.86			00V07-40	9.50	ZM1552	3.76	*6BA9	0.96	*6X5GT	1.15	150C4	1.75	6084	6.32		
B795	78.05	E288CC	15.00	EN91	5.80	*N77	6.00	0S85-10	4.85	ZP1200	26.25	*6BA6	1.44					6085	5.76		
BT125	63.10	*EA91	0.88	EN92	5.85	*N309	2.22	0S95-10	4.85	ZP1230	32.13	*6BL8	1.36	7FC7	1.38	1913	96.00	6189	7.01		
BT127	69.10	*EABC80	1.15	*EY51	2.37	*N359	0.80	0S105-15	4.10	ZP1240	26.60	8B07A	1.55			2050A	4.84	6201	1.05		
BW1162J3	213.49	*EB91	0.88	*EY81	3.38	*PC86	1.45	Q81200	2.25	ZP1300	15.00	8B87	6.00	*12AL5	2.15						
B31081-01	165.00	*EBC90	1.25	*EY84	6.81	*PC88	1.55	Q81205	1.75	ZP1310	12.53	8B87	3.84	*12AT7	0.80						
B41981-01	225.00	*EBC90	2.20	*EY86	0.84	*PC89	1.15	Q81212	3.55	ZP1470	47.25	*6BW6	6.35	*12ATT WA	1.20						
		*EBC91	6.09	*EY87	0.84	*PC90	1.80	Q81215	1.80	ZP1481	31.50	*6BW7	1.40	*12A08	1.28						
		*EBC92	1.02	*EY88	1.05	*PC94	0.84	QW05-25	3.12	ZP1530	43.26	*6B7	1.40	*12A09	1.50						
D10-1606H	58.17	*ECC81	0.80	*EY91	2.25	*PC85	1.25	QW06-20	7.92	Z11011	22.50	*6C4	2.20	*12A07	0.68						
D13-266H-01	151.00	*ECC82	1.15	*EY80Z	0.91	*PC88	1.12	QY2-100	51.80	ZX1051	87.00	*6C5GT	1.10	*12A08	2.56						
D14-1706H	90.56	*ECC83	1.15	*EY85	1.15	*PC89	1.38	QY3-125	46.80	ZX1052	158.77	*6C6	1.02	*12B8A	0.80						
D14-1726H	90.56	*ECC84	1.19	*EY40	1.25	*PC89	1.38	QY4-250A	55.14	0A2	1.45	*6C6A	0.72	*12B87	1.50						
D14-1726M	106.82	*ECC85	1.16	*EY80	0.98	*PC89	1.60	QY5-100	62.67	0A2WA	2.55	*6CA7	2.24	*12B87A	1.45						
*DC491	1.00	*ECC86	1.90	*EY81	0.72	*PC82	0.95	QZ06-20	22.25	0B2	1.80	*6CB8A	0.75	*12B7A	1.54						
06A4-1000ED	26.72	*ECC88	6.58	*EY90	1.08	*PC86	1.58	*R12	2.37	0B2	2.36	*6CB6	1.76	12E1	10.17						
*DF61	1.50	*ECC91	1.12	GL5751	4.00	*PCF200	2.20	RG1-240A	21.80	0C2	2.96	*6CB6	1.60	12E1A	32.78						
*DF91	0.75	*ECC90A	9.32	GR31	8.95	*PCF801	1.28	RG3-250A	28.10	2D21	2.24	*6CK6	6.44	1303	5.60						
*DF92	0.85	*ECC90	1.36	GR31	8.95	*PCF802	1.28	RG3-250B	24.45	2K25	14.00	*6CM5	1.94	1308	3.75						
*DF31	47.25	*ECC93	1.04	GU50	12.00	*PCF808	1.44	RG4-1250	25.80	3B28	7.50	*6CS5	1.28								
PG1-32	47.25	*ECC94	1.32	GX1100	34.00	*PCF808	1.44	RG4-1250	25.80	3C45	8.25	*6C94	4.72	29C1	13.30						
PG13-2	21.00	*ECC81	2.32	GX1120	43.85	*PCL82	1.25	RG4-1250	25.80	3E29	8.25	*6C94	4.72								
PH3-91	40.29	*ECL80	1.32	GXP250	237.80	*PCL82	1.25	RG4-1250	25.80	3E29	8.25	*6C94	4.72								
*DH77	1.40	*ECL82	0.88	GU1	16.63	*PCL83	1.25	RG4-1250	25.80	3E29	8.25	*6C94	4.72								
*DH109	1.28	*ECL85	1.12	GU4	33.00	*PCL84	1.15	RG4-1250	25.80	3E29	8.25	*6C94	4.72								
*DH142	2.00	*ECL86	1.58	GU51	15.45	*PCL85	1.45	RG4-1250	25.80	3E29	8.25	*6C94	4.72								
*DH719	1.10	*E3F7A	3.35	GUS101	2.57	*PCL86	1.58	RG4-1250	25.80	3E29	8.25	*6C94	4.72								
*DK91	0.95	*E3F8	3.75	GUS102	1.12	*PCL88	1.68	RG4-1250	25.80	3E29	8.25	*6C94	4.72								
DL15	4.67	*E80	0.80	*GZ31	2.25	*PCL805/85	3.90	RG4-1250	25.80	3E29	8.25	*6C94	4.72								
DL316	10.50	*E82	0.91	*GZ32	1.65	*PCL84	1.15	RG4-1250	25.80	3E29	8.25	*6C94	4.72								
DR2000	4.45	*E86	1.44	*GZ34	1.90	*PCL85	1.45	RG4-1250	25.80	3E29	8.25	*6C94	4.72								
DR2010	4.85	*E89	1.77	*GZ37	3.50	*PCL86	1.58	RG4-1250	25.80	3E29	8.25	*6C94	4.72								
DR2100V1	5.70	*E91	3.99	GUX50	14.00	*PCL87	1.00	RG4-1250	25.80	3E29	8.25	*6C94	4.72								
*DY86	0.60	*E92	5.00	*K76	6.75	*PL36	2.05	RG4-1250	25.80	3E29	8.25	*6C94	4.72								
*DY87	0.60	*E93	0.80	*K78	8.72	*PL36	2.05	RG4-1250	25.80	3E29	8.25	*6C94	4.72								
*DY802	.04	*E94	0.80			*PL36	2.05	RG4-1250	25.80	3E29	8.25	*6C94	4.72								

RECEIVING, SPECIAL QUALITY, TRANSMITTING, DISPLAY, ELECTRO-OPTIC, CAMERA TUBES, GAS FILLED, ETC.


All valves guaranteed new & tested before despatch.

Cash with order. Postage & Packing: Order up to £2-30p, £5-50p, Over £5-85p. Add VAT: 12½% where marked, others 8%

Telephone for a quote for quantity requirements.

Account facilities available for established companies. Solid state replacements for certain types of obsolete valves.

Why Scopex?

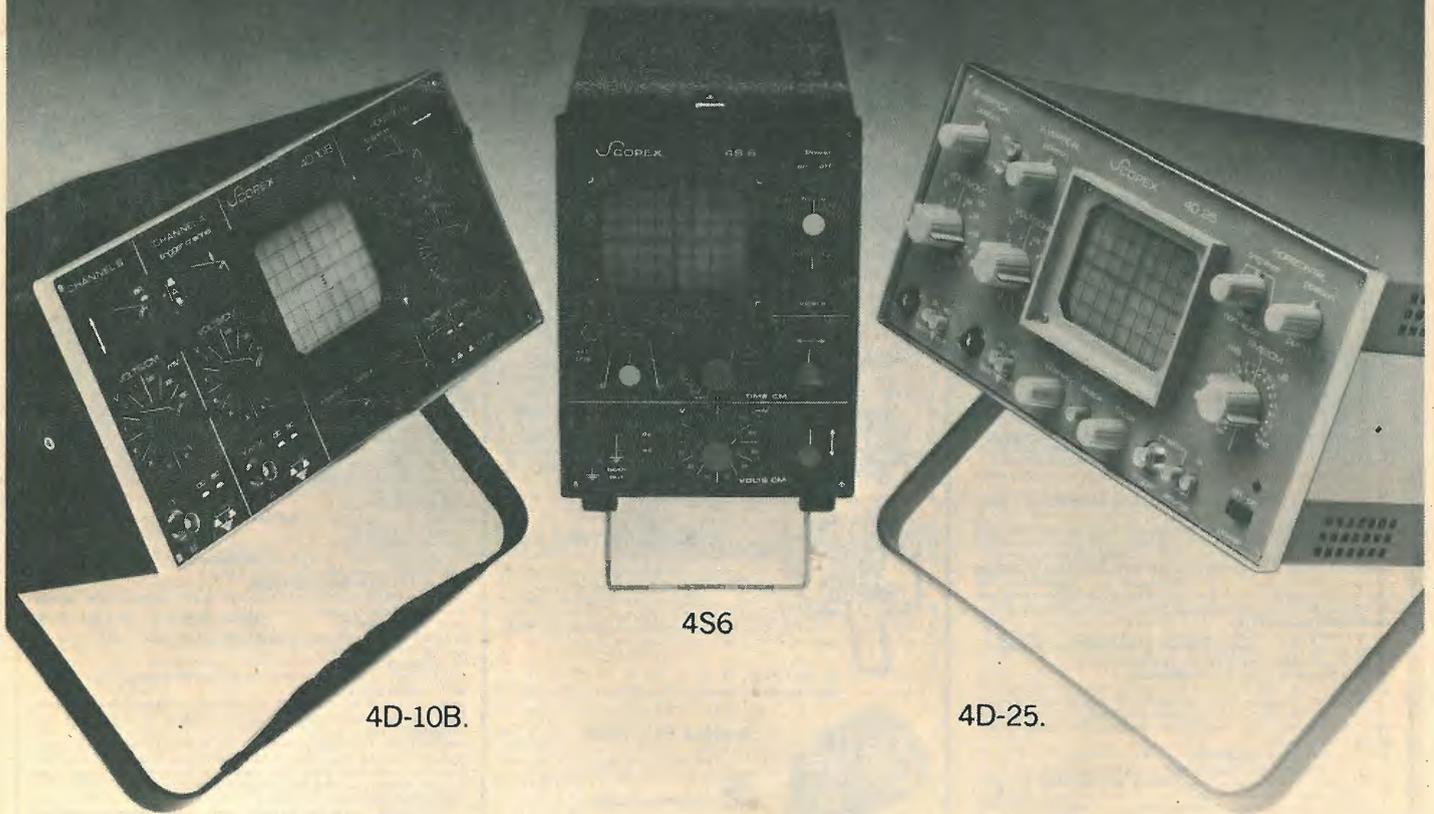

4D-10B.

4S6

4D-25.

There's a range of answers.

There's something every one of our scopes has in common. Great accuracy, tremendous reliability and keener pricing, plus free delivery on UK mainland.

Take the new 4D-10B. The fully stabilised power supply gives 3% accuracy. There's a full XY facility using CMOS ICs for extra reliability, Z modulation for brightening or dimming the trace, 10MHz scan at full bandwidth over the full screen area, trace locate and TV field trigger. At £210.00* it's astonishing value.

Or the 4D-25. A dual trace model with DC-25MHz bandwidth and 10mV/cm sensitivity. Signal delay allows you to trigger from and see the leading edge of any signal. Trigger level and slope are selected on one dual function control. 3% accuracy and still only £360.00*.

Plus the 4S6 single beam 6MHz bandwidth model with easy to use controls. 10mV sensitivity and timebase range of 1 us to 100ms/cm. Lightweight, compact and a very good price. £144.00*.

Return the coupon for full details of the range that gives you a lot more scope.

*UK list price excluding VAT.



Scopex Sales,
Pixmore Avenue, Letchworth, Herts SG6 1JJ.
Tel: (04626) 72771.

Please send me full details of the Scopex range.

Name _____

Company _____

Address _____

Tel: _____

ww 9 79

SERVICE TRADING CO

FT3 NEON FLASH TUBE

High intensity, multi-turn, high voltage, neon glow discharge flash tube. Design for ignition timing etc. £1.50 P&P 25p (£2.01 inc. VAT). 3 for £3. P&P 50p (£4.03 inc. VAT & P).

WHY PAY MORE?!

MULTI RANGE METERS TYPE MF15A. AC/DC volts 10, 50, 250, 500, 1000. Ma. 0.5-0.10, 0-100. Sensitivity 2000V. 24 ranges. Dimensions 133 x 93 x 46mm. Price £7.00 plus 50p P&P (£8.63 inc. VAT & P).



TRIAC.

Raytheon tag symmetrical Triac. Type Tag 250/500V. 10 amp 500 piv. Glass passivated plastic triac. Swiss precision product for long term reliability. £1.25 P&P 10p (£1.55 inc. VAT & P) (inclusive of date and application sheet). Suitable Diac 22p.

0 to 60 MINUTES CLOCKWORK TIMER.

Double pole 15 amp 230V AC. Contacts (no dial). £1.50. P&P 30p (£2.07 inc. VAT & P). N.M.S.

MERCURY SWITCH

Size 27m x 5mm, 10 for £5.00 P&P 30p, total including VAT £6.10. Min. quantity 10. N.M.S.



230 VOLT AC FAN ASSEMBLY

Powerful continuously rated AC motor complete with 5 blade 6 1/2" or 4 blade 3" aluminium fan. New reduced price £3.00 P&P 65p (£4.20 inc. VAT & P). N.M.S.



21-WAY SELECTOR SWITCH with reset coil

The ingenious electro mechanical device can be switched up to 21 positions and can be reset from any position by energising the reset coil. 230/240V AC operation. Unit is mounted on strong chassis. Complete with cover. Price £5.50 P&P 75p (£7.19 inc. VAT & P). N.M.S.



A.E.G. CONTACTOR

Type LS6/L11. Coil 240V 50Hz. Contacts — 3 make: 600V : 20 amp. 1 break: 600V : 20 amp. Price: £5.50 + 50p P&P (£6.90 inc. VAT & P) N.M.S.

TORIN BLOWER

Smith type FFB 1806 022 220/240V AC Aperture 10x4 1/2cm overall size 16x14cm. Price £3.75 P&P 75p (incl. VAT £5.18). Other types available. S.A.E. for details. N.M.S.



24V DC BLOWER UNIT

USA made 24V DC 0.8 amp blower that operates well on 12V 0.4 amp DC producing 30 cu ft min at normal air pressure. Maximum housing dia 110mm, depth inc motor 75mm, nozzle length 19mm, dia 22mm. Ideal for cooling mobile equipment, car, caravan, etc. £4.50 P&P 75p (£6.04 inc. VAT & P). N.M.S.

MINIATURE UNISELECTOR

12V 11 way 4 bank (3 non-bridging, 1 homing). £3.00 P&P 35p (£3.85 inc. VAT & P).


MICRO SWITCHES

Sub min. lever m/switch type MML46. 10 for £2.50 inc. VAT & P. Type 3 115M 906T 10 for £2.50 post paid (£2.88 inc. VAT & P). BF lever operated 20a. c/o. mf. Unimax USA. 10 for £4.00 plus 50p P&P (min. order 10) (£5.18 inc. VAT & P). D.P. C/O lever m/switch, mfg. by Cherry Co. USA. Precious metal, low resistance contacts. 10 for £2.50. P&P 30p. Total inc. VAT £3.22 (min 10). N.M.S.



HEAVY DUTY SOLENOID

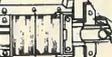Mfg. by Magnetic Devices. 240V AC. Intermittent operation. Approx. 20lb pull at 1.25in. Ex. equip. Tested. Price £1.00 P&P 75p (£8.33 inc. VAT & P). R & T.



PYE EYTHER

240V AC Solenoid. Approx 11lb pull, 1/4" travel, intermittent rating. Price £1.00 P&P 20p (£1.38 inc. VAT & P). N.M.S.

WESTOOL TYPE MMS MODEL 2

240V AC. Approx. 1 1/4 lb pull at 1/2 inch. Rating 1. Price £1.50 P&P 20p (£1.96 inc. VAT & P). N.M.S. 18-24V DC 70 ohm Coil Solenoid. Push or Pull. Adjustable travel to 3/16in. Fitted with mounting brackets and spark suppressor. Size: 100 x 65 x 25mm. Price: 3 for £2.40 + 30p P&P (min. 3 of) (£3.10 inc. VAT & P).

240V AC SOLENOID OPERATED FLUID VALVE

Rated 1 p.s.i. will handle up to 7 p.s.i. Forged brass body, stainless steel core and spring 1/2 in. b.s.p. inlet outlet. Precision made. British mfg. Price £3.50 Post 50p (£4.60 inc. VAT & P). N.M.S.



INSULATION TESTERS (NEW)

Test to I.E.E. spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L. 8 in. W. 4 in. H. 6 in., weight 6 lb. **500 VOLTS** 500 megohms £49.00 Post 80p (£57.27 inc. VAT & P)



1000 VOLTS 1000 megohms £55.00 Post 80p (£64.17 inc. VAT & P) SAE for leaflet.

YET ANOTHER OUTSTANDING OFFER New (MFD) 600V Dribbler wire ended capacitors, 10 for £1.50 P&P 50p. (£2.30 inc. VAT & P&P). (Min 10).

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230V AC 50/60 OUTPUT VARIABLE 0/260V AC BRAND NEW. All types.
200W (1 Amp) fitted A/C volt motor £14.50
0.5 KVA (Max. 2 1/2 Amp) £17.00
1 KVA (Max. 5 Amp) £22.50
2 KVA (Max. 10 Amp) £37.50
3 KVA (Max. 15 Amp) £45.50
5 KVA (Max. 25 Amp) £74.00
10 KVA (Max. 50 Amp) £168.00
17 KVA (Max. 75 Amp) £260.00

Carriage and VAT extra

LT TRANSFORMERS

0-10V-15V at 3 amp. (ex new equip) £2.50 P&P 50p (£3.45 inc. VAT)
 13-0-13V at 1 amp £2.50 P&P 50p (£3.45 inc. VAT)
 25-0-25V at 2 1/2 amp. £4.50 P&P 75p (£6.04 inc. VAT & P)
 0-4V/6V/24V/32V at 12 amp. £18.50 P&P £1.90 (£23.46 inc. VAT & P)
 0.6V/12V at 20 amp £14.70 P&P £1.50 (inc. VAT £18.63)
 0-12V at 20 amp, or 0-24V at 10 amp. £12.00 P&P £1.50 (£15.53 inc. VAT & P)
 0-6V/12V at 10 amp. £8.25 P&P £1.25 (inc. VAT £10.93)
 0-6V/12V/17V/18V/20V at 20 amp. £19.00 P&P £1.50 (£23.58 inc. VAT & P)
 0-10V/17V/18V at 10 amp. £10.50 P&P £1.50 (inc. VAT £13.80)
 Other types in stock; phone for enquiries or send sae for leaflet.

POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.

25 WATT 10, 25, 100, 150, 250, 500, 1k, 1.5k ohm £2.40 Post £2.09 inc. VAT & P) **50 WATT** 250 ohm £2.90 Post 25p (£3.62 inc. VAT & P) **100 WATT** 1/5, 10/25/50/100/250/3000/500/1k/1.5k/2.5k/5k ohm. £5.90 Post 35p (£7.19 inc. VAT & P). **Black Silver Skirted Knob** calibrated in Nos. 1-9, 1 1/2 in. dia brass bush. Ideal for Rheostats. 28p ea.

SPECIAL OFFER

BERCO type L RHEOSTAT
 85 ohm 300 watt 1.86 amp £7.50 P&P 50p (Total £9.20 inc. VAT). N.M.S.

BLOWER/VACUUM PUMP

3 phase AC motor, 220/250V or 380/440V, 1.425 rpm 1/4 hp cont. Direct coupled to Wilma Altec carbon vane blower/vacuum pump. 0.9 cm 8hg. Price £22.00 P&P £2.00 (£27.60 inc. VAT & P). N.M.S.

STROBE! STROBE! STROBE!

HY-LIGHT STROBE KIT Mk. IV

★ Latest type Xenon white light tube. Solid state timing and triggering circuit. 230/240V AC operation. Speed adjustable 1-20 f.p.s. ★ Designed for large rooms, halls, etc. Light output greater than many (so called 4 Joule) strobes. Price £19.00 post £1.00 (£23 inc. VAT & P). Specially designed case and reflector for Hy-Light £8.80 Post £1.00 (£11.27 inc. VAT & P).

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

★ 4ft. 40 watt £10.00. (Callers only £10 inc. VAT. 2ft. 20 watt £6.20. Post 75p (£7.99 inc. VAT & P) (for use in stan bi-pin fittings) Mini 12in. 8 watt £2.80. Post 35p (£3.62 inc. VAT & P). 9in. 6 watt £2.25. Post 35p (£2.99 inc. VAT & P). 6in. 4 watt £2.25. Post 35p (£2.99 inc. VAT & P). ★ Complete ballast unit for either 6", 9" or 12" tube 230V AC op. £3.50 plus P&P 45p (£4.54 inc. VAT & P). Also available for 12V DC op. £3.50 plus P&P 45p (£4.54 inc. VAT & P). ★ 400 watt UV lamp and ballast complete £31.50. Post £3 (£39.68 inc. VAT & P). 400 watt UV lamp only £11.25. Post £1.20. (£14.32 inc. VAT & P).

SQUAD LIGHT

A new conception in light control. Four channels each capable of handling 750 watts of spotlights or dozens of small mains lamps. Seven programs all speed controlled plus flash modulation, effective glowing displays. Makes sound-to-light obsolete. Completely electrically and mechanically noise free. Price only £80.70 (£89.61 inc. VAT & P). S.A.E. (Footscap) for further details. Post 75p



WIDE RANGE OF DISCO LIGHTING EQUIPMENT

S.A.E. (Footscap) for details

XENON FLASH GUN TUBES

Range of Xenon tubes available from stock. S.A.E. for full details.



RELAYS

Wide range of AC and DC relays available from stock. Phone or write in your enquiries.

230/240V AC Relays: Arrow, 2 c/o. 15 amp £1.50 (£1.96 inc. VAT & P). T.E.C. open type 3 c/o. 10 amp £1.10 (£1.50 inc. VAT & P). Omoron or Keyswitch 1 c/o. 7 amp £1.00 (£1.38 inc. VAT & P). **DC Relays:** Open type 9/12V 3 c/o 7 amp £1.00 (£1.38 inc. VAT & P). Sealed 12V 1 c/o 7 amp octal base. £1.25 (£1.67 inc. VAT & P). Sealed 12V 3 c/o 7 amp 11-pin. £1.35 (£1.78 inc. VAT & P). 24V. Sealed 3 c/o 7 amp 11-pin £1.35 (£1.78 inc. VAT & P) (amps = contact rating). P&P on any Relay 20p. Other types available — phone for details. N.M.S. **Very special offer.** 9-12V D.C., 2 make contacts, new ITT3 for £1.75 + 25p P&P (inc. VAT £2.30). Diamond H heavy duty AC relay 230/240V AC, two c/o contacts 25 amps res at 250V AC £2.50 P&P 50p. (£3.45 inc. VAT & P&P). Special base 50p.

METERS (New) — 90mm DIAMETER
 AC Amp. Type 62T2: 0-1A, 0-5A, 0-20A. AC Volt. 0-15V, 0-300V. DC Amp. Type 66C5: 0-2A, 0-10A, 0-20A, 0-50A. DC Volt. 0-15V, 0-30V. All types £3.50 ea. + P&P 50p. (£4.60 incl. VAT). 0-50A DC, 0-100A DC. Price £5.00 + 50p P&P (£6.33 inc. VAT).



GEARED MOTORS

100 R.P.M. 115 lbs. ins.!!

115 lb. ins., 110 volt, 50Hz, 2.8 amp, single phase, split capacitor motor. Immense power. Continuously rated. Totally enclosed. Fan cooled. In-line gearbox. Length 250mm. Dia. 135mm. Spindle Dia. 16.5mm. Length 115mm. Ex-equipment tested £12.00. Post £1.50 (£15.53 inc. VAT & P). Suitable transformer 230/240 volt £8.00 Post 75p (£10.06 inc. VAT & P). R&T



GEARED MOTORS

28 r.p.m., 20lb. inch 115V AC Reversible motor. 71 r.p.m. 10 lb. inch. 115V AC Reversible motor. Both types similar to above drawing. Price either type £4.75 + 75p P&P (£5.33 inc. VAT & P&P). Supplied with transformer for 240V AC operation £7.25 + P&P £1. (N.M.S. £9.49 inc. VAT & P&P). N.M.S.

FRACMO MOTOR

56rpm 50lbs inch 240V AC reversible, 0.7 amp, sharp-throw 35mm, dia. 16mm, weight 6 kilos 600 grams. Price £15.00 P&P £1.50 (£18.98). N.M.S.



FRACMO MOTOR

1400 rpm HP 1-30 continuously rated 115V AC fitted with anti-vibration cradle mounting. Supplied complete with transformer for 230-240V AC op. £10.00 P&P £1.00 (Total £12.65 inc. VAT). N.M.S.

PARVALUX MOTOR TYPE S.D.2

12V DC shunt 1/30th ph motor. Continuously rated 4.000 rpm. Price £10.00 P&P 75p (£12.36 inc. VAT & P). N.M.S.

PARVALUX 230/250V AC MOTOR

Type SD18 240V AC reversible 30 rpm 50lbs inch. Price £15.00 P&P £1.50 (£18.98 inc. VAT). N.M.S.



CITENCO

FHP motor type C 7333/15 220/240V AC 19 rpm reversible motor, torque 14.5 kg. Gear ratio 144:1. Brand new incl. capacitor, our price £14.25 + £1.25 P&P (£17.83 inc. VAT & P). N.M.S.



CRUZET — 230/240V AC 2 rpm synchronous geared motor £2.90 P&P 30p (Total £3.68 inc. VAT). N.M.S. **HAYDON** — 230/240V AC 1 rpm synchronous geared motor £2.90 P&P 30p (Total £3.68 inc. VAT). N.M.S.

REVERSIBLE MOTOR 230V AC

General Electric 230V AC, 1,600 r.p.m. 0.25 amp. Complete with anti-vibration mounting bracket and capacitor. O/A size 110mm x 90mm. Spindle 5/16 dia. 20mm long. Ex-equipment tested £3.00. Post 50p (£4.03 inc. VAT & P).

BIG INCH

Tiny precision built 3RPM USA motor size only 1 x 100 volt AC op supplied with resistor for 230 volt AC price £2, P&P 20p (inc. VAT & P £2.53). 4 for £5.00 post paid (inc. VAT £5.75).

12V DC GEARED MOTOR

Precision built miniature motor, 6/12V DC operation. Incredibly powerful for size. Approx speed at 6V 60 rpm 40 ma Approx speed at 9V 80 rpm 50 ma Approx speed at 12V 120 rpm 60 ma Size 27mm dia, 38mm length, weight 55 gram. Drive spindle 5 mm x 2 mm dia. Price: £2.50 post paid (£2.88 inc. VAT).

REDUCTION DRIVE GEARBOX

Ratio 1:1. Input spindle 1/4 x 1/8in. Output spindle 3/8 x 3in. long. Overall size approx: 120 x 98 x 68mm. All metal construction. Ex-equip. tested. Price: £2.00 + 50p P&P (£2.88 inc. VAT).

'VENNER TYPE' ERD TIME SWITCH

200/250V AC 3 amp. 2 on/2 off every 24 hrs. at any manually pre-set time. 36-hour spring reserve and day omitting device. Built to highest Electricity Board specification. Price £90.00 P&P 75p (£11.21). R & T.



SANGAMO WESTON TIME SWITCH

Type S251 200/250V AC 2 on 2 off every 24 hours. 20 amps contacts with override switch, diameter 4" x 3", price £48.00 P&P 50p (£8.78 inc. VAT & P). Also available with solar dial. R & T.

AEG TIMESWITCH

200/250V AC 1 on/1 off every 24 hours, 80 amp contact (ideal storage heaters). Spring reserve £10.00 P&P 50p (Total £12.08 inc. VAT). N.M.S.

AC MAINS TIMER UNIT

Based on an electric clock, with 25 amp, single-pole switch, which can be preset for any period up to 12 hrs, ahead to switch on for any length of time, from 10 mins. to 6 hrs. then switch off. An additional 60 min. audible timer is also incorporated. Ideal for Tape Recorders, Lights, Electric Blankets etc. Attractive satin copper finish. Size 135 mm x 130 mm x 60 mm. Price £2.25. Post 40p. (Total inc. VAT & Post £3.05). N.M.S.




2-CAM PROGRAMMER

Crouzet 1 rpm, 115V. A.C. Motor operating 2 Roller Micro switches (4 amp). Can be used on 240V AC with either 0.25 mfd 250V Condenser or 5 6k wirewound Resistor 7 watt (not supplied) Price £2.50 + 50p P&P (£3.45 inc. VAT & P).

MINIATURE 24-HOUR TIMSWITCH (German mfr.)

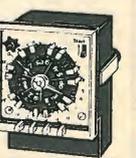240V. AC operation. Spring reserve. 10 amp contacts, one on-off every 24 hours. Calibrated in two-hour steps. Minimum on-off period 6 hours. Day Omission. Unusual feature with these switches is that trips may be removed at will enabling individual days to be programmed as required. Size only 3" x 4". Depth 2 3/4". Price £6.50 + 50p P&P (£8.05 incl. VAT & P).



N.M.S. — New Manufacturers' Surplus R & T — Reconditioned and Tested

SERVICE TRADING CO

57 BRIDGMAN ROAD CHISWICK LONDON W4 5BB 01-995 1560

ACCOUNT CUSTOMERS MIN. ORDER £10.00

All Mail Orders — Callers

— Ample Parking

Showroom open Mon-Fri.


PERSONAL CALLERS ONLY
 9 LITTLE NEWPORT STREET,
 LONDON, WC2H 7JJ

Tel: 01-437 0576

ELECTRONIC KITS OF DISTINCTION FROM **POWERTRAN**

DE LUXE EASY TO BUILD LINSLEY-HOOD 75W STEREO AMPLIFIER £99.30 + VAT

This easy to build version of our world-wide acclaimed 75W amplifier kit based upon circuit boards interconnected with gold plated contacts resulting in minimal wiring and construction delightfully straightforward. The design was published in Hi-Fi News and Record Review and features include rumble filter, variable scratch filter, versatile tone controls and tape monitoring whilst distortion is less than 0.01%.

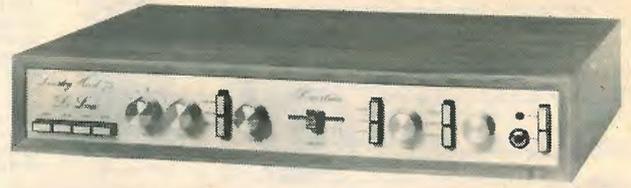


WIRELESS WORLD FM TUNER £70.20 + VAT

A pre-aligned front-end module makes this Wireless World published design very simple to construct and adjust without special instruments. Features include an excellent a.m. rejection push-button station selection as well as infinitely variable tuning and a phase locked loop stereo decoder, incorporating active filters for "birdy" suppression.



LINSLEY-HOOD CASSETTE DECK £79.60 + VAT

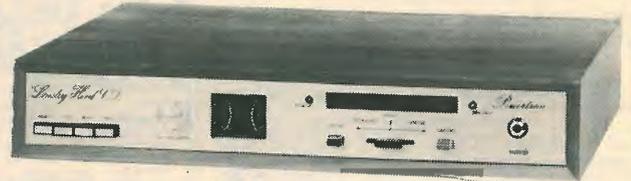This design, published in Wireless World, although straightforward and relatively low cost provides a very high standard of performance. There are separate record and replay amplifiers and switchable equalisation together with a choice of bias levels are also provided. The mechanism is the Goldring-Lenco CRV with electronic speed control.



TRANSCENDENT 2000 SINGLE BOARD SYNTHESIZER

As featured in Electronics Today International



Cabinet size 24.6"x15.7"x4.8" (rear) 3.4" (front)

The kit includes fully finished metalwork, fully assembled solid teak cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or 1/2% metal film!) and it really is complete — right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit — you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibre glass PCB printed with component locations. All the controls mount directly on the main board, all connections to the board are made with connector plugs and construction is so simple it can be built easily in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesizer comparable in performance and quality with ready built units selling for between £500 and £700!

**COMPLETE KIT
ONLY
£172.00 + VAT!**

Comprehensive handbook supplied with all complete kits! This fully describes construction and tells you how to set up your synthesizer with nothing more than a multi-meter and a pair of ears!

CHROMATHEQUE 5000 5-CHANNEL LIGHTING EFFECTS SYSTEM

This versatile system featured as a constructional article in ELECTRONICS TODAY INTERNATIONAL has 5 frequency channels with individual level controls on each channel. Control of the lights is comprehensive to say the least. You can run the unit as a straightforward sound-to-light or have it strobe all the lights at a speed dependent upon music level or front panel control setting or use the internal digital circuitry which produces some superb random and sequencing effects. Each channel handles up to 500W and as the kit is a single board design wiring is minimal and construction very straightforward.

Kit includes fully finished metalwork, fibreglass PCB, controls, wire, etc. — Complete right down to the last nut and bolt!


**COMPLETE KIT ONLY
£49.50 + VAT**



Panel size 19.0"x3.5". Depth 7.3"

MPA200 100W MIXER/AMPLIFIER

Featured as a constructional article in Electronics Today International the MPA 200 is an exceptionally low-priced but professionally finished general purpose, rugged, high-power amplifier which has an adaptable range of inputs such as disc, microphone, guitar, etc. There are 3 wide range tone controls and a master volume control. Mechanically the design is simplicity in the extreme with minimal wiring making construction very straightforward. Kit includes fully finished metalwork, fibreglass PCB's, controls, wire, etc. — Complete right down to the last nut and bolt!

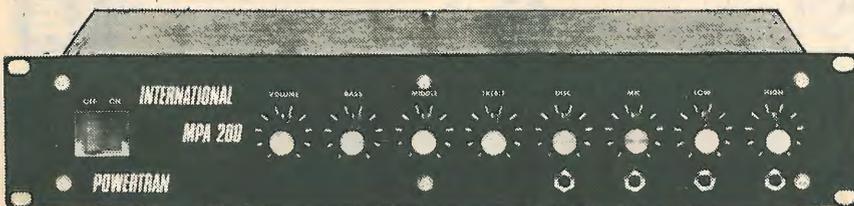

Panel size 19.0"x3.5". Depth 7.3"

**COMPLETE KIT ONLY
£49.90 + VAT**

All kits also available as separate packs (e.g. P.C.B. component sets, hardware sets, etc.). Prices in FREE CATALOGUE.


ASCENSION ISLAND YUGOSLAVIA UNITED STATES OF AMERICA JORDAN GREECE INDIA GUYANA PORTUGAL FALKLAND ISLANDS UNITED ARAB EMIRATES JAMAICA HOLLAND KENYA

EIRE GRENADA SAUDI ARABIA NEW ZEALAND NORWAY SINGAPORE ICELAND SWEDEN MALAYA INDONESIA BRAZIL SWITZERLAND ZAMBIA GIBRALTAR CHILE SPAIN


AUSTRIA CZECHOSLOVAKIA SOUTH AFRICA FINLAND NIGERIA LUXEMBOURG TUNISIA GERMANY NAURU HONG KONG GAMBIA AUSTRALIA DENMARK FRANCE MUSCAT & OMAN

NEW GUINEA ISRAEL GUERNSEY CYPRUS BELGIUM UGANDA BRUNEI TRINIDAD SOUTH WEST AFRICA ITALY JAVA SIERRA LEONE WINDWARD ISLANDS CANADA MALTA

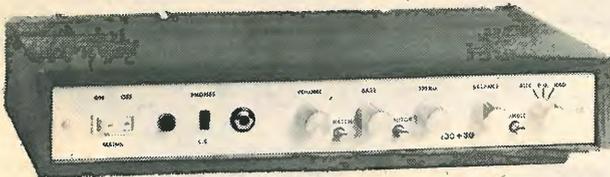T20 + 20 AND T30 + 30 20W, 30W AMPLIFIERS



WWII TUNER

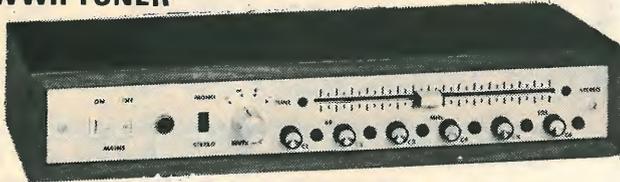

SPECIAL PRICE FOR COMPLETE KIT £47.70 + VAT
AVAILABLE AS SEPARATE PACKS — PRICES IN OUR FREE CATALOGUE

Following the success of our **Wireless World FM Tuner Kit** this cost reduced model was designed to complement the **T20+20** and **T30+30** amplifiers and the cabinet size, front panel format and electrical characteristics make this tuner compatible with either.

Designed by Texas engineers and described in *Practical Wireless*, the Texan was an immediate success. Now developed further in our laboratories to include a Toroidal transformer and additional improvements, the slimline **T20+20** delivers 20W rms per channel of true Hi-Fi at exceptionally low cost. The **easy to build** design is based on a single F/Glass PCB and features all the normal facilities found on quality amplifiers including scratch and rumble filters, adaptable input selector and headphones socket. In a follow-up article in *Practical Wireless* further modifications were suggested and these have been incorporated into the **T30+30**. These include RF-interference filters and a tape monitor facility. Power output of this model is 30W rms per channel.


SPECIAL PRICES FOR COMPLETE KITS

T20+20 KIT PRICE £33.10 + VAT

T30+30 KIT PRICE £38.40 + VAT

AVAILABLE AS SEPARATE PACKS — PRICES IN OUR FREE CATALOGUE

POWERTRAN SFMT TUNER

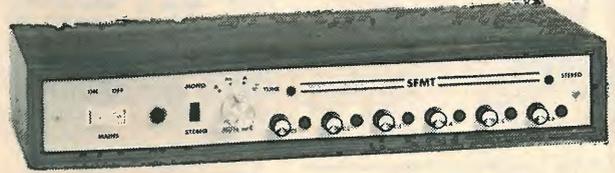

PRICE FOR COMPLETE KIT £35.90 + VAT

AVAILABLE AS COMPLETE KIT ONLY

This is a simple, low cost design which can be constructed easily without special alignment equipment but which still gives a first-class output suitable for feeding any of our very popular amplifiers or any other high quality audio equipment. A phase-locked-loop is used for stereo decoding and controls include switchable afc, switchable muting and push-button channel selection (adjustable by controls on the front panel). This unit matches well with the **T20+20** and **T30+30** amplifiers.

NEW!

Another superb design by synthesizer expert Tim Orr!

TRANSCENDENT DPX

As featured in *Electronics Today International* August, September October, 1977 issues

DIGITALLY CONTROLLED, TOUCH SENSITIVE, POLYPHONIC, MULTI-VOICE SYNTHESIZER

The Transcendent DPX is a really versatile new 5 octave keyboard instrument. There are two audio outputs which can be used simultaneously. On the first there is a beautiful harpsichord or reed sound — fully polyphonic i.e. you can play chords with as many notes as you like. On the second output there is a wide range of different voices, still fully polyphonic. It can be a straightforward piano or a honky tonk piano or even a mixture of the two! Alternatively you can play strings over the whole range of the keyboard or brass over the whole range of the keyboard or should you prefer — strings on the top of the keyboard and brass at the lower end (the keyboard is electronically split after the first two octaves) or vice versa or even a combination of strings and brass sounds simultaneously. And on all voices you can switch in circuitry to make the keyboard touch sensitive? The harder you press down a key the louder it sounds — just like an acoustic piano. The digitally controlled multiplexed system makes practical sensitivity with the complex dynamics law necessary for a high degree of realism. There is a master volume and tone control, a separate control for the brass sounds and also a vibrato circuit with variable depth control together with a variable delay control so that the vibrato comes in only after waiting a short time after the note is struck for even more realistic string sounds.



Cabinet size 36.3"x15.0"x5.0" (rear) 3.3" (front)
Also available as separate packs — prices in free catalogue

COMPLETE KIT ONLY £365.00 + VAT!

To add interest to the sounds and make them more natural there is a chorus/ensemble unit which is a complex phasing system using CCD (charge coupled device) analogue delay lines. The overall effect of this is similar to that of several acoustic instruments playing the same piece of music. The ensemble circuitry can be switched in with either strong or mild effects. As the system is based on digital circuitry data can be easily taken to and from a computer (for storing and playing back accompaniment with or without pitch or key change, computer composing etc., etc.) and an interface socket (25 way D type) is provided for this purpose. Although the DPX is an advanced design using a very large amount of circuitry, much of it very sophisticated, the kit is mechanically extremely simple with excellent access to all the circuit boards which interconnect with multiway connectors, just four of which are removed to separate the keyboard circuitry and the panel circuitry from the main circuitry in the cabinet. The kit includes fully finished metalwork, solid teak cabinet, professional quality components (all resistors 2% metal oxide), nuts, bolts, etc., even a 13A plug — you need buy absolutely no more parts before plugging in and making great music! When finished you will possess an instrument comparable in performance and quality with ready-built units selling for over £1200!

EXPORT A SPECIALITY!

Our Export Department can readily despatch orders of any size to any country in the world. Some of the countries to which we sent kits last year are shown in this advertisement. To assist in estimating postal costs our catalogue gives the same as for U.K. customers but no Value Added Tax charged. Postage charged at actual cost plus 50p documentation and handling. Please send payment with order by Bank Draft, Postal Order, International Money Order or cheque drawn on an account in the U.K. Alternatively for orders over £500 we will accept Irrevocable Letter of Credit payable at sight in London.

**Value Added Tax not included in prices
UK Carriage FREE**

PRICE STABILITY. Order with confidence! Irrespective of any price changes we will honour all prices in this advertisement until October 31st, 1979, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.

U.K. ORDERS. Subject to 15% surcharge for VAT. No charge is made for carriage. * Or current rate if charged.

SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.

SALES COUNTER: If you prefer to collect your kit from the factory, call at Sales Counter. Open 9 a.m.-4.30 p.m. Monday-Thursday.

QUALITY: All components are brand new first grade full specification guaranteed devices. All resistors (except where stated as metal oxide) are low noise carbon film types. All printed circuit boards are fibreglass, drilled roller tinned.

**FOR FURTHER INFORMATION PLEASE WRITE OR
TELEPHONE FOR OUR FREE CATALOGUE**

POWERTRAN ELECTRONICS


PORTWAY INDUSTRIAL ESTATE
ANDOVER HANTS SP10 3NN

ANDOVER
(0264) 64455

Z & I AERO SERVICES LTD.
 Head Office: 44a WESTBOURNE GROVE, LONDON W2 5SF
 Tel. 727 5641 Telex 261306

RETAIL SHOP
 85 TOTTENHAM COURT ROAD, W.1
 Tel. 580-8403

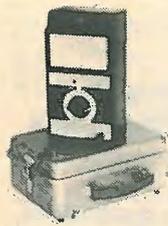SPECIAL OFFER OF BRAND NEW USSR MADE MULTIMETERS



TYPE	U4313	U4315
Sensitivity D.C.	20,000 o.p.v.	20,000 o.p.v.
Sensitivity A.C.	2,000 o.p.v.	2,000 o.p.v.
D.C. Current	60µA-1.5A	50µA-2.5A
A.C. Current	0.6mA-1.5A	0.5mA-2.5A
D.C. Volts	75mV-600V	75mV-1000V
A.C. Volts	15V-600V	1V-1000V
Resistance	1K-1M	300Ω-500kΩ
Capacity	0.5µF	0.5µF
Accuracy	1.5% D.C. 2.5% A.C.	2.5% D.C. 4% A.C.

Price complete with pressed steel carrying case and test leads
 Packing and postage

£10.50 £10.50
 £1.50 £1.50



TYPE U4324

D.C. Current:	0.06-0.6-60-600mA-3A
A.C. Current:	0.3-3-30-300mA-3A
D.C. Voltage:	0.6-1.2-3-12-30-60-120-600-1200V
A.C. Voltage:	3-6-15-60-150-300-600-900V
Resistance:	500Ω-5-50-500kΩ
Accuracy:	D.C. 2.5% A.C. 4% (of F.S.D.)

PRICE complete with test leads and fibreboard storage case **£9.50**
 Packing and postage £1.20

**TYPE U4323
 COMBINED WITH SPOT FREQUENCY OSCILLATOR**



Sensitivity:	20,000Ω/V
Voltage ranges	2.5-1000V A.C. / D.C.
Current ranges	0.05-500mA D.C. only
Resistance:	5Ω-1MΩ
Accuracy:	5% F.S.D.
Oscillator output	1kHz 50/50 squarewave 465KHz sinewave modulated by 1KHz squarewave

PRICE, in carrying case, complete with leads and manual **£8.00**
 Packing and postage £1.00



**TYPE U4341
 COMBINED MULTIMETER AND
 TRANSISTOR TESTER**

Sensitivity:	16,700Ω/V D.C., 3,300Ω/V A.C.
Current:	0.06-0.6-6-60-600mA D.C., 0.3-3-30-300mA A.C.
Voltage:	0.3-1.5-6-30-60-150-300-900V D.C. 1.5-7.5-30-150-300-750V A.C.
Resistance:	2-20-200kΩ-2MΩ
Transistors:	Collector cut-off current 60µA max D.C. current gain 10.350 in two ranges

PRICE, complete with steel carrying case, test lead, battery and instruction manual **£9.50**
 Packing and Postage £1.50

THIS OFFER IS VALID ONLY FOR ORDERS ACCOMPANIED BY REMITTANCE WHICH SHOULD INCLUDE DELIVERY CHARGES AS INDICATED AND 15% V.A.T. ON THE TOTAL

OUR 1978 CATALOGUE/PRICE LIST OF VALVES, SEMICONDUCTORS, PASSIVE COMPONENTS AND TEST EQUIPMENT IS AVAILABLE. PLEASE SEND P.O. for £0.30 FOR YOUR COPY

WW — 024 FOR FURTHER DETAILS

RADIO SHACK LTD for DRAKE



TR-7 Transceiver

Ham Bands with 1.5-30 MHz receive with built-in 150 MHz frequency counter plus option of 0-1.5 MHz receive and/or any transceiving application 1.8-30 MHz.

RADIO SHACK LTD

For Communications equipment including Trio products and Trio testgear.

We are situated just around the corner from West Hampstead Underground Station (Bakerloo line). A few minutes' walk away is West Hampstead Midland Region station and West End Lane on the Broad Street Line. We are on the following Bus routes: 28, 59, 159. Hours of opening are 9-5 Monday to Friday. Closed for Lunch 1-2. Saturday we are open 9-12.30 only. World wide exports.

DRAKE * SALES * SERVICE

RADIO SHACK LTD

188 BROADHURST GARDENS, LONDON NW6 3AY

Giro Account No. 588 7151. Telephone: 01-624 7174

Cables: Radio Shack, London, NW6. Telex: 23718

TV TUBE REBUILDING

Faircrest Engineering Ltd., manufacture a comprehensive range of equipment for processing all types of picture tubes, colour and mono. Standard or custom built units for established or new businesses. We export world-wide and have an excellent spares service backed by a strong technical team.

Full training courses are individually tailored to customers' requirements.

For full details of our service contact Neil Jupp

FAIRCREST ENGINEERING LTD.

Willis Road, Croydon, 01-684 1422, 01-689 8741
 CRO2XX. Tel: 01-689 8741

WW—035 FOR FURTHER DETAILS

At last...

A REALLY RELIABLE IN-CIRCUIT TRANSISTOR TESTER THAT WORKS!

Previous Testers have been too easily fooled by low shunt impedances resulting in false alarms on perfectly sound transistors. Designed for fast IN-CIRCUIT testing the new DATONG DATEST 2 tests transistors, FETs SCR's and Triacs even when shunted by resistors as low as 20 ohms!

Automatic NPN/PNP indication, foolproof three-LED display, and unique test probes allow a very high rate of testing even by unskilled users. Very competitive price includes probes and the DATEST 2 is available from stock. Full data sheet free on request.

ONLY £39.50 COMPLETE + 8% VAT

DATONG ELECTRONICS LIMITED
 Spence Mills, Mill Lane, Bramley
 Leeds LS13 3HE
 Telephone: Pudsey (0532) 552461

WW—037 FOR FURTHER DETAILS



The service organisation of the instrument manufacturer

When you get your test equipment serviced or maintained by the London Instrument Repair Centre, you get the same top quality work that made the instrument in the first place—and backed by a full year's warranty too.

Contact the address below for your nearest centre.



The service organisation of:



Archcliffe Road, Dover, Kent. Telephone: 0304-202620

Thorn Measurement & Components Division

WW — 005 FOR FURTHER DETAILS

ELECTROVALUE

Your leading direct suppliers for



NASCOM MICROCOMPUTERS AND FULL SUPPORTING RANGE OF ITEMS FOR WORKING TO PROPER PROFESSIONAL LEVELS

- ★ Widest possible range of ancillary Nascom items stocked
- ★ Information on request
- ★ Enquiries from trade, industrial and educational users invited

We are also Appointed Distributors for the fine products of:

SIEMENS, ISKRA, RADIOHM, VERO AND MANY OTHER FAMOUS MANUFACTURERS

It's a good deal better from



Dept. WW9, 28 St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB
 Phone: Egham 3603. Telex 264475.
 Northern Branch (Personal shoppers only), 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.

- We pay postage in U.K. on orders list value £5 or over. If under, add 27p handling charge.

- We give discounts as follows on C.W.O. orders except items marked Net or N in our catalogues.

5% on orders, list value £10 or more.

10% on orders list value £25 or more.

Not applicable to Access or Barclaycard orders

- We stabilise prices.

by keeping to our printed price lists which appear but three or four times a year.

- We guarantee all products brand new, clean and to maker's spec. No seconds, no surplus.

- WE WILL SEND YOU OUR 120-PAGE CATALOGUE NO. 9 FREE ON REQUEST.

Comprehensive, informative, very well produced. Write, phone or call for your free copy, together with latest list. (Available separately.)

TRANSFORMERS SAME-DAY DESPATCH

Please add VAT after P&P

MAINS ISOLATOR

Pri 120 or 240V Sec 120 or 240V Centre Tapped and Screened

Ref.	VA (Watts)	£	P&P
07*	20	4.40	.79
149	60	6.70	.96
150	100	7.62	1.14
151	200	11.16	1.14
152	250	13.28	1.50
153	350	16.43	1.84
154	500	20.47	2.15
155	750	29.06	OA
156	1000	37.20	OA
157	1500	51.38	OA
158	2000	81.81	OA
159	3000	86.66	OA

*115 or 240 sec only. State volts required. Pri. 0.220-240V.

VAT 15% 12 or 24-VOLT

Separate 12V windings Pri 220-240V

Ref.	Amps	12v	24v	£	P&P
111	0.5	0.25		2.20	.45
213	1.0	0.5		2.64	.78
71	2	1		3.51	.78
18	4	2		4.03	.96
85	5	2.5		5.00	.79
70	6	3		6.35	.96
108	8	4		7.42	1.14
72	10	5		8.12	1.14
116	12	6		8.99	1.32
17	16	8		10.72	1.32
115	20	10		13.98	2.08
187	30	15		17.93	2.08
226	60	30		36.74	OA

50 VOLT RANGE

Pri 220-240V. Sec. 0-20-25-33-40-50V. Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 25, 30, 33, 40 or 20V-0-20V and 25V-0-25V Screened

Ref.	Amps	£	P&P
102	0.5	3.41	.78
103	1.0	4.57	.96
104	2.0	7.16	1.14
105	3.0	8.56	1.32
106	4.0	11.41	1.50
107	6.0	15.06	1.64
118	8.0	20.26	2.08
119	10.0	24.98	OA
109	12.0	28.90	OA

30 VOLT RANGE

Pri 220-240V Sec. 0-12-15-20-24-30V. Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V and 15V-0-15V.

Ref.	Amps	£	P&P
112	0.5	2.64	.78
79	1.0	3.57	.96
3	2.0	5.77	.96
20	3.0	6.20	1.14
21	4.0	7.99	1.14
51	5.0	9.87	1.32
117	6.0	11.17	1.45
88	8.0	14.95	1.64
89	10.0	17.25	1.84
90	12.0	19.17	1.95
91	15.0	21.96	2.08
92	20.0	29.45	OA

60 VOLT RANGE

Pri 220-240V Sec. 0-24-30-40-48-60V. Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V or 24V-0-24V and 30V-0-30V

Ref.	Amps	£	P&P
124	0.5	3.88	.96
126	1.0	5.91	.96
127	2.0	7.60	1.14
125	3.0	11.00	1.32
123	4.0	12.52	1.84
40	5.0	15.84	1.64
120	6.0	18.06	1.84
121	8.0	25.56	OA
122	10.0	29.55	OA
189	12.0	34.06	OA

SCREENED MINIATURES

Primary 240V

Ref.	mA	Volts	£	P&P
238	200	3-0.3	2.57	.55
212	1A, 1A	0-6, 0-6	2.85	.78
13	100	9-0.9	2.14	.38
235	330, 330	0-9, 0-9	1.99	.38
207	500, 500	0-8-9, 0-8-9	2.77	.71
208	1A, 1A	0-8-9, 0-8-9	3.53	.78
236	200, 200	0-15, 0-15	1.99	.38
239	50MA	12-0-12	2.57	.38
214	300, 300	0-20, 0-20	2.80	.78
221	700 (DC)	20-12-0-12-20	3.41	.78
206	1A, 1A	0-15-20, 0-15-20	4.63	.96
203	500, 500	0-15-27, 0-15-27	3.99	.96
204	1A, 1A	0-15-27, 0-15-27	6.04	.96

AUTO TRANSFORMERS

Ref. VA (Watts) TAPS

Ref.	VA (Watts)	TAPS	£	P&P
113	15	0-115-210-240V	2.48	.71
64	75	0-115-210-240V	4.01	.96
4	150	0-115-200-220-240V	5.35	.96
67	500	"	10.99	1.64
69	250	"	7.04	1.14
84	1000	"	18.76	2.08
93	1500	"	23.28	OA
95	2000	"	34.82	OA
73	3000	"	59.21	OA
80s	4000	0-10-115-200-220-240	76.86	OA
57s	5000	"	89.50	OA

Step Up or Step Down

CASED AUTO TRANSFORMERS

240V cable input. USA 115V. Flat pin outlets. P&P Ref.

Ref.	VA (Watts)	£	P&P
20VA	59.95	.90	56W
75VA	67.73	1.14	64W
150VA	110.01	1.14	44W
200VA	110.92	1.45	65W
250VA	111.59	1.45	69W
500VA	118.17	1.64	67W
1000VA	127.88	2.30	84W
1500VA	128.02	OA	93W
2000VA	149.97	OA	95W

PANEL METERS

43mm x 43mm 82mm x 78mm

0-50µA	£6.20	0-50µA	£6.70
0-500µA	£5.95	0-500µA	£6.70
0-1mA	£5.95	0-1mA	£6.70
0-30V	£5.95	0-30V	£6.70

VU Indicator Edge 54mm x 14mm µA FSD £2.60
 VU Panel Ind. 48 x 45mm, 250µA FDS £2.60
 Carriage 65p VAT 15%

U4315 Budget Meter 20Ku/v Rangers to 1000v
 2.5A AC/DC 500Ku. Res in steel case £15.85 P&P
 £1.15. VAT 15%.

NEW RANGE TRANSFORMERS

Pri 0-120; 0-100-120; (120v or 220-240v) Sec. 0-36-48 twice to give 72v or 92v.

2A	£12.14	PP	£1.40	4A	£18.17	PP	£1.90
3A	£14.70	PP	£1.50	5A	£26.64	PP	£2.20

Full range of ElectroSil Resistors

PLUG-IN — SAVE BATTERIES

MVA30. 6, 7.5, 9v at 300mA plugs direct into 13A socket (fused). 4-way multi plug £4.00

3300-3-6-9-12v at 300ma plug straight to 13A socket (fused) with multiplug £4.60
 15% VAT. 55p P&P

Transformer Ref. 63 Pri 0-240V Sec 0-240 500VA
 £11.50 £2.15 P&P

Send 15p for catalogue Prices correct at 18/7/79

TEST METERS

AV08 Mk. 5 £88.10
 AV071 £36.00
 AV073 £48.70
 AV0MM5 MINOR £32.95
 WEE MEGGER £74.25
 TT169 (tests transistors in circuit) £39.53
 EM272 316KΩ/v... £57.80
 DA116 Digital £108.90
 Megger BM7 (Battery) £51.76
 Avo Cases and Accessories P&P £1.15 VAT 15%

BRIDGE RECTIFIERS

100v 25A+ £2.10
 200v 2A £45p
 400v 2A £55p
 200v 4A £65p
 400v 4A £80p
 400v 6A £1.40
 500v 12A £2.35
 P&P 15p. VAT 15%

MINIATURE TRANSFORMER

O-Centre Tapped-15V

Ref.	Amps	Price	P&P
171	500MA	2.09	.45
172	1A	2.96	.78
173	2A	3.59	.78
174	3A	3.75	.86
175	4A	5.73	.96

ABS PLASTIC BOXES

Inset brass nuts, slots to take PC cards (boards) flush fitting lid.
 PB1 80mm x 62 x 40 .65p
 PB2 100mm x 75 x 40 .73p
 PB3 120mm x 100 x 45 .87p
 PB4 215mm x 130 x 85 £2.54
 P&P 29p. VAT 15%

ANTEX SOLDERING IRONS

15W £3.95. 25W £3.95
 Stand for above £1.52. P&P 46p. VAT 15%.

ISOLATOR

Ref. 30 240V. 240V 200VA £4.54. P&P £1.04.
 M624 0-380V-110V @ 13.6A £12.70. P&P £1.04.
 ISOLATOR Ref. 62 240V. 240V 250VA £5.62. P&P £1.04

Barrie Electronics Ltd.
 3, THE MINORIES, LONDON EC3N 1BJ
 TELEPHONE: 01-488 3316/8
 NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.

YOU NEED NEVER BUY A COLOUR FILM AGAIN!

WIRELESS WORLD COLOUR PHOTO SERVICE



● **SUPER QUALITY HI-DEFINITION SHEEN COLOUR PRINTS**


● **FREE KODACOLOR FILM TO FIT YOUR CAMERA**

● **SEE YOUR PICTURES BEFORE YOU PAY!**



ROLLEI POCKETLINE 200 COMPACT CAMERA AND ELECTRONIC FLASH-GUN

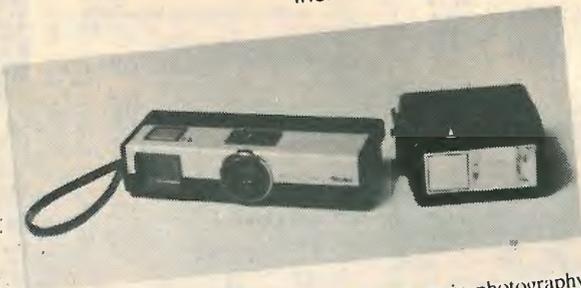RSP £31.18 **Our Price £20.45**
inc. VAT & P&P



From Rollei, one of the most respected names in photography. Precision made with a 3 element optical glass lens, colour corrected for quality colour photography. Supplied in gift box complete with wrist-strap. Fully guaranteed for 12 months. Finger-light push button shutter release • 2 brightness setting controls • Shutter speed 1/125 sec. reducing the possibility of camera shake • Clear view finder — easy to use even with spectacles • Drop-in 110 cartridge loading — simplicity itself • Detachable electronic flash — no complicated wires. 150 flashes from 2 pen-cell batteries (not supplied).

CAMERA ORDER FORM

To: Camera Offer, Freepost, Teddington TW11 8BR.
Please send me the Rollei Pocketline 200 Camera and Electronic Flash-gun.

I enclose cheque p.o. for £20.45 (payable to Wireless World Camera offer)

Name (please print)

Address

Registered in England No. 495406. Registered Office: 1 Throwley Way, Sutton, Surrey.

You get a special deal when you use our Colour Photo Service. Thousands of magazine readers are delighted with it. Because you save money on Kodak recommended prices — and you only pay for the prints you actually receive! So why not give it a try? You'll be delighted with our luxury borderless colour prints. Without borders you get as large a picture as possible — and our pictures have a hi-definition sheen for greater clarity.

HERE'S WHAT YOU DO

Send us any make of colour print film inside the envelope enclosed in this issue. Or fill in the coupon below and send it with the film in a strong envelope to: Wireless World Colour Photo Service, FREEPOST, Teddington TW11 8BR. No stamp is required. Send no money at this stage.

FREE KODACOLOR FILM

We'll send you a Kodacolor film, absolutely free, with your prints, together with an invoice for only the successful shots, eliminating the need for credit notes.

UNBEATABLE VALUE

You're probably paying around 18p a print plus £1.10 for developing. Well, our price is an amazing 16p per print plus only 90p to cover developing, administration, postage and packing! Our minimum charge is 90p (assuming no prints come out) inc. V.A.T. Offer limited to U.K. and Eire, C.I. and B.F.P.O.

Remember, you only pay for successful prints — no credit vouchers. And you only pay on invoice: a straight forward business transaction with the extra advantages of quality, reliability and convenience. Value for money — and a free Kodacolor film worth about £1.00.

Films accepted on Standard Terms of Business (available on request).

From Wireless World
COLOUR PHOTO SERVICE,
Freepost, Teddington, TW11 8BR

NAME (please print)

ADDRESS

Postcode

TTLs by TEXAS 7400 11p 74251 140p 4019 45p 7401 12p 74252 250p 4020 100p 7402 12p 74278 290p 4021 110p 7403 14p 74279 110p 4022 110p 7404 12p 74280 150p 4023 22p 7405 14p 74281 150p 4024 22p 7406 12p 74282 200p 4025 22p 7407 12p 74283 200p 4026 130p 7408 12p 74284 100p 4027 50p 7409 12p 74285 100p 4028 84p 7410 12p 74286 100p 4029 100p 7411 12p 74287 100p 4030 55p 7412 12p 74288 200p 4031 200p 7413 12p 74289 200p 4032 100p 7414 12p 74290 200p 4033 180p 7415 12p 74291 200p 4034 200p 7416 12p 74292 200p 4035 110p 7417 12p 74293 200p 4036 295p 7418 12p 74294 200p 4037 115p 7419 12p 74295 200p 4038 120p 7420 12p 74296 200p 4039 285p 7421 12p 74297 200p 4040 100p 7422 12p 74298 200p 4041 80p 7423 12p 74299 200p 4042 80p 7424 12p 74300 200p 4043 80p 7425 12p 74301 200p 4044 80p 7426 12p 74302 200p 4045 110p 7427 12p 74303 200p 4046 110p 7428 12p 74304 200p 4047 110p 7429 12p 74305 200p 4048 110p 7430 12p 74306 200p 4049 110p 7431 12p 74307 200p 4050 110p 7432 12p 74308 200p 4051 80p 7433 12p 74309 200p 4052 80p 7434 12p 74310 200p 4053 80p 7435 12p 74311 200p 4054 125p 7436 12p 74312 200p 4055 150p 7437 12p 74313 200p 4056 150p 7438 12p 74314 200p 4057 150p 7439 12p 74315 200p 4058 150p 7440 12p 74316 200p 4059 150p 7441 12p 74317 200p 4060 150p 7442 12p 74318 200p 4061 150p 7443 12p 74319 200p 4062 150p 7444 12p 74320 200p 4063 150p 7445 12p 74321 200p 4064 150p 7446 12p 74322 200p 4065 150p 7447 12p 74323 200p 4066 150p 7448 12p 74324 200p 4067 150p 7449 12p 74325 200p 4068 150p 7450 12p 74326 200p 4069 150p 7451 12p 74327 200p 4070 150p 7452 12p 74328 200p 4071 22p 7453 12p 74329 200p 4072 22p 7454 12p 74330 200p 4073 22p 7545 12p 74421 200p 4164 22p 7546 12p 74422 200p 4165 22p 		83 SERIES 9301 160p 9302 175p 9308 318p 9310 275p 9311 275p 9312 160p 9314 165p 9316 225p 9321 225p 9322 160p 9324 225p 9368 200p 9370 200p 9374 200p 		VEROBOARDS 0.1 (Copper clad) 2.5 x 3.75" 43p 2.5 x 5" 57p 51p 3.75 x 3.75" 7p 3.75 x 5" 64p 64p 4.75 x 17" 222p 184p 4.75 x 17" 222p 184p Pkt of 10 pins 50p Spot glue cutter 86p Pin insertion tool 118p Vero Writing Pen + 2 wire spoons + comb 370p Coxs 7p 		TRANSISTORS AC126 25p AC127/8 20p AC176 25p AF187/8 25p AF187/7 30p AF188 25p BF129 25p BF29 30p BF30 30p BF30A 30p BF30B 30p BF30C 30p BF30D 30p BF30E 30p BF30F 30p BF30G 30p BF30H 30p BF30I 30p BF30J 30p BF30K 30p BF30L 30p BF30M 30p BF30N 30p BF30O 30p BF30P 30p BF30Q 30p BF30R 30p BF30S 30p BF30T 30p BF30U 30p BF30V 30p BF30W 30p BF30X 30p BF30Y 30p BF30Z 30p 		MEMORIES 2102-2L 120p 2107H 500p 2111-2 225p 2112-2 300p 2114 525p 4027 375p 4116 511p 5101 510p 5910 350p 74201 510p 82516 325p 		ROM/PROMS 71901 700p 74518B 225p 74527 350p 74537 350p 74547 650p 74571 650p 74571 1100p 93427 400p 93427 400p 93427 400p 93446 650p 93448 1000p 		CPUs 1600 1600 6502 512 6800 900p 6802 1250p 8080A 800p Z80 1150p 		EPROMS 1702 500p 2516 3200p 2708 900p 2716 532 		SUPPORT DEVICES 3245 400p 4002 500p 6820 500p 6821 500p 6850 500p 8205 320p 8212 320p 8216 225p 8224 400p 8228 400p 8251 550p 8255 550p 8257 1100p 8259 1100p 280P10 650p Z80CT 850p MC14411 1100p MC14412 1100p 		KEYBOARD AY-3-1015P 500p AY-5-1013P 400p AY-5-1014P 400p TMS6011NC 400p 		CHARACTER GENERATORS 3257ADC 990p MCM6576 510p RO-3-2513 U.C. 600p RO-3-2513 L.C. 600p SN74S262AN 1350p 		TRANSFORMERS 6-0-6 100mA 85p 9-0-9 75mA 82p 12-0-12 100mA 85p 0-1-20 1250mA 280p 0-25V (5VA) 250p 9-0-9 1A 270p 12V 2A 380p 0-12-15 340p 20-24-30 1A 285p 15-0-15 1A 285p (Please add 50p p&p charge to all marked * above our normal p&p charge.) 		RESISTORS High 5% E12 500p Carbon Film 500p 1/4W 10R-1M 7p/5pcs one value 1/2W 10R-10M 5p/3pcs one value Miniature Presets 12p Hor/Vent 100R-1M 12p Carbon Track Pots 12p K-1M Log or Lin 225p Single 400p Single with Switch 30p Dual 72p 		LOW PROFILE DIL SOCKETS BY TEXAS 8 pin 10p 18 pin 22p 24 pin 30p 14 pin 11p 20 pin 25p 28 pin 38p 16 pin 12p 22 pin 28p 40 pin 48p 		WIRE WRAP SOCKETS BY TEXAS 8 pin 30p 18 pin 70p 28 pin 90p 14 pin 40p 20 pin 75p 28 pin 110p 16 pin 55p 22 pin 80p 40 pin 140p 		SUBMINIATURE SWITCHES Toggle 60p SPST 60p SPDT 65p DPDT 70p DPDT (centre off) 85p DPDT (make) 15p break 25p SLIDE DPDT 18p ROCKER SPST 28p 		ANTX SOLDERING IRONS C-15W 380p C-17W 380p CN-15W 380p X25 380p C/CX/CN 48p X25 50p 		SPARE BITS C/CX/CN 48p X25 50p 		SPARE ELEMENTS C/CX/X25 180p CN 200p 		ADCOLA IRONS K1000 550p K2000 550p 		VEROBOARDS DIP Breadboard 270p A.15 x 6.15 Suitable for 20 x 14 pin ICs 16 x 16 pin DIL ICs DIP Breadboard as above with tracks for 31 way connector 340p V-0 Boards for ICs 1085p (No track cutting) 		CONNECTOR PLUGS 31 way Plug 110p 31 way Socket 110p S-100 Busboard 512 		DIODES BY127 12p BY36-300 20p OA47 8p OA81 15p OA85 15p OA90 3p OA91 3p OA95 9p OA200 9p OA202 10p IN914 4p IN916 12A 400V 85p IN4148 4p IN4001/2 5p IN4003/4 6p IN4005 6p IN4006/7 7p IN4008/1/3 14p IN5404/7 14p IS920 9p 		TRIACS PLASTIC 60p OA30 3A 500V 85p OA31 3A 500V 85p OA35 6A 400V 70p OA36 6A 500V 88p OA40 8A 400V 75p OA45 8A 500V 95p OA50 12A 400V 85p OA55 16A 500V 100p OA60 16A 400V 110p OA65 16A 500V 130p 		THRISTORS 1A 50V 40p 1A 400V 65p 3A 400V 90p 8A 600V 140p 16A 400V 160p 16A 100V 180p 16A 600V 220p BT108 110p C106D 45p MCR101 36p 2N3525 12p 2N4444 140p 2N5060 34p 2N5064 40p 		HEAT SINKS For TO220 Volt- age Regs. and Transistors For TO5 22p 		BRIDGE RECTIFIERS 1A 50V 21p 1A 100V 22p 1A 400V 30p 1A 600V 30p 2A 50V 30p 2A 100V 35p 2A 400V 45p 3A 200V 60p 3A 600V 72p 4A 100V 95p 4A 400V 100p 6A 50V 90p 6A 100V 95p 6A 400V 120p 10A 400V 200p 25A 400V 400p 		LOUD-SPEAKERS Size 2 1/2" 64R 70p 2 1/2" 8R 70p 2" 8R 80p 1 1/2" 8R 80p 		ZENERS 2.7V 33V 400p 400V 7W 9p 1W 15p 	
--	--	--	--	---	--	---	--	--	--	---	--	--	--	---	--	---	--	--	--	---	--	--	--	--	--	--	--	--	--	--	--	--	--	---	--	---	--	---	--	---	--	--	--	--	--	---	--	---	--	--	--	---	--	--	--	--	--

PLEASE SEND SAE FOR LIST. Government, Colleges, etc. Orders accepted. CALLERS WELCOME. We carry a large stock of 74 and 74LS TTLs, CMOS, Linear, Memories, etc. and can normally offer ex-stock deliveries. We welcome inquiries for volume quantities both from local and overseas buyers.

TECHNOMATIC LTD.
17 BURNLEY ROAD, LONDON NW10
(2 minutes Dollis Hill tube station) (ample street parking)
Tel: 01-452 1500 Telex: 922800

AS SEEN IN
P.E. AUGUST, SEPTEMBER
OCTOBER 1979

EUROPE'S FASTEST SELLING ONE BOARD COMPUTER —
JUST CHECK THE SPEC'S.

SAMPLE TAPE
INCLUDING EXTENDED
MACHINE CODE MONITOR
INCLUDED FREE

COMPUKIT UK101

LOW COST SUPERBOARD IN KIT FORM

The CompuKit UK101 has everything a one board 'superboard' should have.

- * Uses ultra-powerful 6502 microprocessor.
- * 50Hz Frame refresh for steady clear picture (U.S.A. products with 60Hz frame refresh always results in jittery displays)
- * 48 chars by 16 lines — 1K memory mapped video system providing high speed access to screen display enabling animated games and graphs.
- * Extensive 256 character set which includes full upper and lower case alphanumerics, Greek symbols for mathematical constants and numerous graphic characters enabling you to form almost any shape you desire anywhere on the screen.
- * Video output and UHF Highgrade modulator (8Mz Bandwidth) which connects direct to the aerial socket of your T.V. Channel 36 UHF.
- * Fully stabilised 5V power supply including transformer on board.
- * Standard KANSAS city tape interface providing high reliability program storage — use on any standard domestic tape or cassette recorder.
- * 4K user RAM expandable to 8K on board £49 extra.
- * 40 line expansion interface socket on board for attachment of extender card containing 24K RAM and disk controller. (Ohio Scientific compatible)
- * 6502 machine code accessible through powerful 2K machine code monitor on board.
- * High quality thru plated P.C.B. with all I.C.'s mounted on sockets.
- * Professional 52 Key keyboard in 3 colours — software polled meaning that all debouncing and key decoding done in software.



*8K Microsoft Basic means conversion to and from Pet, Apple and Sorcerer easy. Many compatible programs already in print.

- SPECIAL CHARACTERS**
- @ Erases line being typed, then provides carriage return, line feed.
 - Erases last character typed.
 - CR Carriage Return — must be at the end of each line.
 - : Separates statements on a line.
 - CONTROL/C Execution or printing of a list is interrupted at the end of a line.
 - "BREAK IN LINE XXXX" is printed, indicating line number of next statement to be executed or printed.
 - CONTROL/O No outputs occur until return made to command mode. If an Input statement is encountered, either another CONTROL/O is typed, or an error occurs.
 - ? Equivalent to PRINT

Simple Soldering due to clear and concise instructions compiled by Dr. A.A. Berk, BSc.PhD

NO EXTRAS NEEDED JUST HIT 'RETURN' AND GO.

Build, understand, and program your own computer for only a small outlay.

KIT ONLY £219 + VAT including RF Modulator & Power supply. Absolutely no extras.

Available ready assembled and tested, ready to go for £269 + VAT

COMMANDS
CONT LIST NEW NULL RUN
STATEMENTS
CLEAR DATA DEF DIM END FOR
GOTO GOSUB IF_GOTO IF_THEN INPUT LET
NEXT ON_GOTO ON_GOSUB POKE PRINT REAC
REM RESTORE RETURN STOP

EXPRESSIONS
OPERATORS
+ * / % ^ NOT.AN.DR. >< <> >=< RANGE 10⁻³² to 10⁺³²

VARIABLES
A.B.C. ... Z and two letter variables
The above can all be subscripted when used in an array. String variables use above names plus \$.e.g. AS-

FUNCTIONS
ABS(X) ATN(X) COS(X) EXP(X)
LOG(X) PEEK(I) POS(I) RND(X)
SPC(I) SQR(X) TAB(I) TAN(X)
FRE(X) INT(X)
SGN(X) SIN(X)
USR(I)

STRING FUNCTIONS
ASC(X\$) CHR\$(I) FRE(X\$) LEFT\$(X\$,I)
RIGHT\$(X\$,I) STR\$(X)
LEN(X\$) MID\$(X\$,I,J)
VAL(X\$)

EXTRAS AVAILABLE IN 4 WEEKS

COLOUR ADD-ON enables you to choose your foreground and background colour anywhere on the screen. Flash any character on the screen at will. Full documentation and parts in kit form.

AD-A-RAM EXTENDER CARD provides up to 32K Dynamic RAM Expansion, 8 Eprom sockets for 2708's or 2716's. Parallel Port (electronics compatible) and an RS232C serial port.

WIN YOURSELF AN ANADEX DP8000 LINE PRINTER

There's never enough good software around. That's why COMPUKIT LTD. are sponsoring a software contest. There are 2 categories:

- 1) Business and Education
- 2) Fun and Games

One lineprinter will be awarded to the winner of each category. Send or bring along to the address shown below the following:

- 1) The program on cassette in the format used by the COMPUKIT UK101
- 2) Any documentation that you have for the program (source listing not necessary)
- 3) This coupon signed by you accepting the rules and conditions of the competition.

RULES:

- 1) Entries, including documentation, must be printed by computer or typed double spaced, with your name on every page.
- 2) Send or bring your entries to the address shown below.
- 3) Entries must be received by midnight on 29/2/80, any received after this time are void.

Winners will be notified by post before 31/3/80.

4) You warrant by your signature that all programs and documentation material included is entirely your own creation, and that no rights to it have been given or sold to any other party, and you agree to allow COMPUKIT LTD. to use, publish, distribute, modify, and edit it as it sees fit.

- 5) All entries become the property of COMPUKIT LTD. No entries will be returned nor any questions answered regarding individual entries.
- 6) Judging will be by a selected panel chosen by, and including representatives of COMPUKIT LTD. Judges may assign programs to any of the categories as they see fit. Decision of the judges is final.
- 7) Employees of COMPUKIT LTD, its dealers, distributors, advertising agencies and media are not eligible to enter.

Name _____

Address _____

I agree to abide by the above mentioned rules.

Signature _____

Please add VAT to all prices — Delivery at cost, will be advised at time of purchase. Please make cheques and postal orders payable to COMP, or phone your order quoting BARCLAYCARD, ACCESS, DINERS CLUB or AMERICAN EXPRESS number.

OPEN — 10am to 7pm — Monday to Saturday CREDIT FACILITIES ARRANGED



COMP COMPUTER COMPONENTS

14 STATION ROAD, NEW BARNET, HERTFORDSHIRE TEL: 01-441 2922 (Sales)

CLOSE TO NEW BARNET BR STATION — MOORGATE LINE 01-449 6596

OPEN — 10am to 7pm — Monday to Saturday

TELEX: 298755



All Products Ex-Stock Please check availability

(Part of the Compshop Ltd. Group)



SEE THE NEW VACANCIES WHILE THEY'RE STILL VACANT...

Electronics Weekly is the main job announcements medium for the industry, carrying the majority of the best electronics positions advertised in the UK.

But all good vacancies have one thing in common. They don't stay vacant long.

If you only get to see Electronics Weekly days after publication... if, in other words, you're way down the office pass-on list... then you're leaving yourself at the back of the queue for career opportunities.

But for only 10p a week you could move up front, and see Electronics Weekly ahead of everyone in your company. Fill in and post this coupon, and you'll be breakfasting with Opportunity every Wednesday morning from now on!

To: Subscription Department, IPC Business Press Ltd.,
 Oakfield House, Perrymount Road, Haywards Heath, Sussex.
 Please send me Electronics Weekly for a year. I enclose cheque/p.o.
 for UK £6 (inclusive of p. & p.) Overseas \$18.60, payable to
 IPC Business Press Ltd.

Name _____

Address _____

Electronics Weekly

TEK scope 545A with H plug-in **£125 ea.**
TEK scope 545A with CA plug-in **£175 ea.**
H.P. scope 175A 50MHZ Dual trace Single Trace **£125 ea.**
SOLARTRON CT316 6MHZ Single Beam **£47.50 ea.**
Ex-Ministry CT52 Small, Single Beam **£37.50 ea.**
WAYNE KERR Universal Bridge CT375 **£75 ea.**
MARCONI Wave Analyser TF2330 **£500 ea.**
MARCONI Audio Oscillator TF1101 20HZ-200KHZ **£45 ea.**
ADVANCE Signal Generator J1A (CT433A) **£35 ea.**
MARCONI Valve Voltmeter TF1041C **£30 ea.**
NOISE GENERATOR CT410 — covers audio to VHF **£8 ea.**
DIGITAL EQUIP. CORP. Disk Drives (Fixed) **£160 ea.**
TEK Transistor Curve Tracer **£225**
NAGARD Pulse Generator 5002C **£50 ea.**
MARCONI Carrier Deviation Meter TF791D **£75 ea.**
MARCONI Wave Analyser type TF455E **£50 ea.**
SOLARTRON DVM LM 1420 with AC unit LM1477 **£40 ea.**
HONEYWELL 1920 character Upper Case ASCII VDU with edit and block mode transmission; limited quantity. With data **£260 ea.**
CALCOMP Drum Plotter type 564 **£1,500**
MARCONI GEN. TF995 (CT402) **£170**
MARCONI Bridge TF868B **£120**
RANK Flutter Meters **£50 ea.**
HEWLETT PACKARD Signal Gen. 608D **£240**
AVO Signal Generator HF135 **£120 ea.**
 Carriage all units **£4 ea.**

10-Way Multi-Colour Ribbon Cable. New. **40p per metre.** P&P 50p.
SPEAKERS 2 1/2in. 50 ohm 0.2W. New **40p each.** P&P 50p.
STEPPING MOTORS 6/12 position with additional where the rota is coils. Devise can be used as a tach. Diagram supplied. Will actually work on 5 volts. 12 24 recommended. **£1.50 each.** P&P 75p. Reduction for quantity
RAPID DISCHARGE capacitors 8mfd 4kV. **£5 each.** P&P £1.50
GEC UHF 4-button tuner. **£2.50 each.** P&P 85p.
BIG INCH Motor 110V AC 3rpm 50 cycle — very small. **50p each.** P&P 50p.
CENTUAR 115V FANS. Brand New 4.5 x 4.5 x 1.5in. **£4.50 each.** P&P 75p.
Ex-Used Equipment — tested **80p each.** P&P 75p.
POTTER & BRUMFIELD TIMER RELAY 115V AC Heavy duty 2 pole c/o with 2-second delay. Change R & C for different timing. **50p each.** P&P 85p.
CONTACTORS Heavy Duty 24V/DC 5 make. **£1 each.** P&P 85p.
GEC UHF/VHF 6-button tuner. **£4.50 each.** P&P £1
SMITHS encapsulated transistorised AUDIBLE WARNING DEVICES 4V-12V. Can be driven from TTL. **35p each.** P&P 25p.
DIGITAL 24-HOUR CLOCK with built-in alarm as used in BRUAN Digital clocks. Silent running. Large illuminated numerals. AC mains. Size 6" x 2 1/2" x 2 1/4". **ONLY £3.75 each.** P&P 50p.
931A PHOTOMULTIPLIER in stainless steel container with window and built in resistor network. **£2 each.** P&P £1
SLIDER CONTROL 500K. Log Single track. Complete with knob. Length 3 1/2in. **25p each.** P&P 25p.
RANCO 250V 16A THERMOSTATS with Control knobs calibrated 50-200 degree F. **£2.50 each.** P&P £1.
SOLID STATE UHF TUNERS 38 mcs. **£1 each.** P&P 75p.
BRAND REX blue wire wrap. 30 metres for **£1.** P&P 25p.
Sin. SOLID RUBBER RINGS (1in. dia. rubber). Keep the kids (or dog) happy. **4 for £1.** P&P £1.25.
TRANSFORMERS
AUTO 240V input 115V 1 Amp output. **£1.25 each.** P&P £1.25.
240V input Sec. 6V 1.66A. Size 2 1/2" x 2" x 2in. Good quality. **£1.50 each.** P&P £1.
240V input Sec. 12V 0.92A. Size 2 1/2" x 2" x 2in. Good quality. **£1.50 each.** P&P £1.
240V input Sec. 12V 100MA. Size 60 x 40 x 42mm. **50p each.** P&P 75p.
240V input Sec. 12-0-12V 50MA. Size 53 x 45 x 40mm. **£1 each.** P&P 75p.

115V Input Secs. 23V. 15V. 10V all at 1.5A. Size 3 x 3 1/2 x 2 1/2in. **£1 ea.** P&P £1. Or **2 for £1.75.** P&P £1.50.
115V Input Sec. 5V 250MA. Size 1 11/16 x 1 5/16 + 1 1/2in. **2 for 50p.** P&P 75p.
SEMICONDUCTORS
AI 2p each.
 1N3063, 1S44, **AI 5p each.**
 BC147, BC148B, BC157, BC158, BC184L, BC237, BF197, 0A90, 0A91, BA154, BA243, **AI 25p each.**
 TIP31, TIP41A, TIP47, 2N5296, AF139, ZTX341, BY127 **10p**; BF181 **20p**; BD239 **40p**; BD241 **40p**; MJE340AT **40p**; BD222 **50p**.
 BD233 & BD234 Comp pair 25W — **80p per pair** or **50p each.**
 Regulator TBA625 8 to 20V in — 5V out 100MA T05 Can. **50p each.** BF256C — **20p**.
 FND10 7-segment display 0.15in. **40p each.**
 TV Amplifier TBA120 — **20p each.**

Integrated Circuits

7453	5p	74H74	12p	74154	70p
7451	5p	74S04	12p	75325	£1
7401	5p	74H51	7p	SN15862	4p
7402	12p	74S38	10p	MC4028	60p
7476	20p	74S02	12p	7417	14p
7495	35p	74S00	12p	7441	40p
709	15p				

MOTOROLA Dual in line 6-pin Opto Couplers. **30p each.** Gold pin-faster version **50p each.**
AM9140-4K RAMS STATIC 5 Volts, ceramic. **£4 each.**
TELEPHONES, 706 style Black or Grey. **£5.50 each.** 746 style Black or Grey. **£7.50 each.** Older style Black. **£2.50 each.** Postage £1 each.
HONEYWELL Humidity Controllers. **50p each.** P&P 40p.
THYRISTOR TIMER, Solid State. 15 secs adjustable (preset) in plastic relay case. Standard 7-pin base. Series delay. **50p each.** P&P 85p.
MINIATURE PC MOUNT SLIDE SWITCH. Single pole 3-way. **10p each.**
DIGITAL to ANALOGUE CONVERTOR, 8-bit, will fit standard TT1 socket. With data. **£2.50 each.** P&P 25p.
VARIACS 2 Amp. Standard 240 Volts, **£10 each.** P&P £1.50.
ELECTROSTATIC VOLTMETERS, 7.5KV. **£6 each.** P&P £1.
 Other ranges available — please enquire.
TRIMMERS Sub-min. 1-4.5 pf. **6p each.**

Minimum order £3 value of goods. P&P or Carriage and VAT at 15% on total must be added to all orders.
CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5pm Monday to Saturday incl.
BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome.

CHILTMHEAD LTD

NORWOOD ROAD, READING TELEPHONE NO. READING 669656

(2nd turning left past Reading Technical College in King's Road then first right — look on right for door with "Spoked Wheel")

Buy a System . . . Not just a "Pretty Box"

The SD System* — From about 97p per hour (40-hour week)

The SDS-200 TOTAL System features:

System Hardware

The SDS-200 give you features that are not found in systems costing thousands more. State-of-the-Art Engineering. Quality Production and Full Reliability testing make the SDS-200 a dependable, compact and easy-to-operate data processing system.

- Up to 256K Bytes RAM
- Full Keyboard with Special Accounting Key Pad
- Large 12in. Video Display Screen
- Full Cursor Control including Addressable Cursor
- Blinking, Underlining, Reverse and Protected Fields
- Uses 8in. Flexible Diskettes for Permanent Storage 2 Mbyte on-line
- Forward and Reverse Scrolling
- Capable of up to 160 Special Characters
- Expandable with Memory and Peripheral Equipment
- Will Operate as a Remote Batch Processor for Large Systems
- Industry Standards S-100 BUS/CPM
- 4 Spare S-100 Slots

System Software


A full range of Business Programs are available from CAP-CPP written in Microcobol.

The system will support all normal high-level languages including:

- Fortran
- Cobol
- Basic
- CP/M

AUTHORISED DEALERS

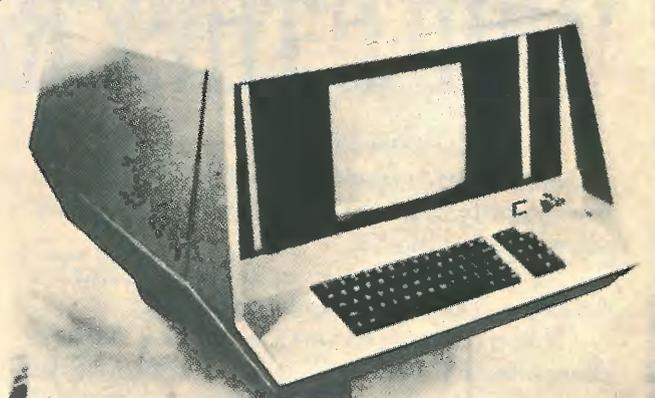- Apple Computer, Glenalmond, Perthshire. Tel. 073-888 267.
- Codified Computer Systems, 69 Calabria Road, London. Tel. 01-226 1319.
- Anglo American Computers Ltd., Milburn House, Dean Street, Newcastle-upon-Tyne. Tel. 0632 29593.
- Bell Computers, 62 Lowther Street, Carlisle. Tel. 0524 411271.



* The SD System includes—
 SDS-200 Microcomputer
 T.I. 810 Printer (or Equivalent)

Cash Price for SDS-200: £4750.00

U.K. DISTRIBUTOR:

AIRAMCO LTD

Unit A2, 9 Longford Avenue, Kilwinning Ind. Est., Kilwinning, Ayrshire, KA13 6EX

(0294) 57755. Telex 779808

Dealer enquiries invited



SOUTHEAST ENGLAND'S ELECTRONICS CENTRE

MINIATURE 24 HR TIME SWITCH



- ★ Only 2" square
- ★ Up to 32 on-offs
- ★ 16 amp contacts
- ★ Plug-in carrier

This amazing time switch enables the programming of up to 32 on-offs in a 24 hour period. This is achieved by inserting triggers into the dial in the appropriate time positions. Plug in carrier for easy time setting and 16 amp contacts make it suitable for most switching applications. Supplied brand new with fixing screws and 3 sets on-off triggers.

£8.50

OPTO SMASH!

TIL 302/MAN 7 7 segment LED readout common anode direct drive (via resistors) from 7447 £1.10 each
TIL 119/OC72 Darlington opto isolator 3 for £1.00.
SAVE THAT SPACE! THICK FILM RESISTOR NETWORK 7x100Ω resistor in DIL pack. Ideal for use with 7 seg. displays etc. 4 for £1.00.
TIL305 0.3" 7 x 5 matrix LED alphanumeric readouts £3.75 each.
PHOTO TRANSISTOR Fairchild FPT-100 NPN silicon 30v, 25ma. 4 for £1.00.

DISPLAY I.C. AND TRANSISTOR BARGAINS NEVER CHEAPER

All I.C.'s and Transistors by well known manufacturers and fully guaranteed. No fall outs. Comprehensive data on I.C.'s 15p per type.
2N4351 N channel MOS FET.
2N4352 P channel MOS FET.
 60p each £1.00 per pair.
HIGH VOLTAGE NPN POWER SWITCHING transistors BVcbo 600v BVceo 500v BVebo 15v 1c 5 amps Pc 125 watts HFE 60 typ ft 2.5 mhz ideal invertors, etc. TO3 £1.60 each 4 for £5.40.
BF258 NPN 250v @ 200ma 45p each 3 for £1.08.
I.R. BSB01 2.5 amp 100v bridge rec. P.C. mount long leads 35p each 4 for £1.08.
IN4998 4 amp 100v P.C. mount diodes long leads 14p each 10 for £1.10.
LM309K +5v 1.2 amp regulator £1.10 each 6 for £5.35.
2N1671B unijunction 450mw 30v 48p each 3 for £1.00.
IN4004 SD4 1 amp 400v diodes 7p each 18 for £1.00.
I.R. 12 amp BRIDGE RECS. 400 volt £1.25 each.
POWER DARLINGTON SCOOP!
MJ1000 NPN 60v 90w 8 amps T03 95p each
2N6385 PNP 80v 100w 10 amps T03 £1.25 each
MJ4030 NPN 60v 150w 16 amps T03 £2.25 each



4k x 12 RAM static Memory card

Complete 4K x 12 bit memory system on one PCB. This ex computer memory card contains all relevant decoding, read write and control logic for coupling to your M.P.U. or mini computer system. TTL in and out make interfacing a "cinch". We understand that by reading the outputs correctly, the memory can be organised as a 6K x 8! Features include fast 250ns max. access time. Standard +12v, -12v+5v power rails compact construction, non-volatile memory, data remains even when power switched off!
 Original cost over £800 each, supplied complete with full data and circuit manual, at an unbelievable price of **£39.95** P.P. £1.75
 Note: Memories are removed from working equipment but supplied untested, unguaranteed.

HOW TO GET HERE

Victoria, London Bridge or Holborn Viaduct to Thornton Heath. 1 minute from Thornton Heath Station.

MPU EXPERIMENTORS POWER SUPPLY

Once again we are very pleased to offer this superb Power Supply Unit, and hope to satisfy most of our previous customers who were disappointed when we sold out due to demand, last time they were advertised! These units may just have well been made for your lab., they consist of a semi-enclosed chassis measuring 160mm x 120mm x 350mm containing all silicon electronics to give the following fully regulated and short circuit proof outputs of:
 +5v @ 2 amps D.C. +12v @ 800ma D.C.
 -12v @ 800ma D.C. +24v @ 350ma D.C.
 and if that's not enough a fully floating 5v output @ 50ma D.C. which may be seriesed to give a host of other voltages. All outputs are brought out to the front panel via miniature jack sockets and are also duplicated at the rear on short flying leads. Units accept standard 240v AC mains input. They are ex GPO and may have minor scratches on the front panels, they are sold untested but in good internal condition. Our original price of £16.50 and the recent VAT increase makes these an absolute snip at only **£15.50** each + £2.25 P & P. Complete with circuit and component list.
HURRY WHILE STOCKS LAST!!

HY GRADE SMOOTHING CAPS
MULLARD - PLESSEY - MALLORY - SPRAGUE
 1500mf 100v 60p* 3300mf 40v 50p
 3300mf 63v 70p* 4500mf 25v 70p
 10,000mf 15v £1† 22,000mf 16v £1.10†
 87,000mf 7v £1† 2100mf 200v £2.50†
 *Ex equipment tested †P.P. 40p

SEMICONDUCTOR 'GRAB BAGS'

Amazing value mixed semiconductors, include transistors, digital, linear I.C.'s, triacs, diodes, bridge recs. etc. All devices guaranteed brand new, full spec. with manufacturers markings, fully guaranteed.
 50 + BAG £2.95 100 + BAGS £5.15

MUFFIN FANS

ideal equipment cooling etc. tested, ex-equipment
 240v 50-60 HZ **£6.15** + p.p. 45p
 110v 50-60 HZ **£5.05** + p.p. 45p

ELECTRONIC COMPONENTS & EQUIPMENT **66% DISCOUNT**

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s Transistors, Relays, Cap's., P.C.B.'s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads., we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME". Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay plus we always include something from our ads. for unbeatable value!! Sold by weight
 71b £ 5.25 141b £ 7.95
 281b £13.75 561b £22.00
 PLEASE ADD P + P £1.25

ISOLATED 240V 4 AMP & 10 AMP SOLID STATE RELAYS

Interface your MPU etc, with the outside world made by the famous "Astralux" Co. They consist of a miniature plastic module with mounting holes containing a reed relay for isolation, choke and triac. 12-20 volts D.C. at a few milliamps enable on/off control of A.C. loads up to 10 ampel! The 10 amp version should be mounted on a heatsink. 100's of uses including power control, lighting, etc, etc. Dimensions: 4 amp, 1 1/2" x 1" x 3/4"; 10 amp, 1 1/2" x 1 1/2" x 1". 4 amp £1.45 10 amp £2.10 complete with circuit

PLESSEY EDGE STACKABLE DECADE THUMBWHEEL SWITCHES. Gold plated contacts dimensions 2" x 2" x 1/8" 85p each 8 for £5.35.
AMPHENOL 50Ω BNC chassis socket single hole fixing 50p each.
AMPHENOL 50Ω BNC plug 50p. **50Ω BNC** plug right angled 60p.
C90 Audio Cassettes screw type construction 45p each 3 for £1.00.
Bulbs 24v 14 watt white frosted S.B.C. 8 for £1.00.
Bulbs 12v 100 watt clear, base similar S.B.C. 45p each.
S.B.C. Bulb Holders All steel cad. plated panel mount easily fixed via nut and round hole, ideal disco displays, scoreboards, etc. 4 for £1.10.
Xtal filters S.E. 1 QC11211/B miniature low insertion loss P.C. mount.
C.F. 10.7mhz with B.W. of 7.5khz 2000Ω imp in-out. Brand new @ £7.99.
Heavy Duty Flat Insulated Earth Braid 100-200 amp braided tinned copper in heavy clear PVC sheath 50p per metre. £6 for 15 metres + PP £1 per 15 metres.
BULGIN miniature 6 way male chassis mount socket and matching free plug 60p each, 2 for £1.10.
Red L.E.D.'s full spec. 0.2" 14p each. 10 for £1.25.
Dynamic Stick Mics 600Ω with built in on/off switch complete with lead and min. jack plug £1.15 each. 10 for £10.00.
TO5 HEATSINKS "Thermalloy" black anodised press on aluminium finned type 18p each. 8 for £1.00.

HARDWARE PACK Don't be stuck for the right nut and bolt for the job. Pack contains B.A. Metric, Unified, Self Tap, etc. Nuts, Bolts, Screws, Washers, etc. in Brass Bronze and Steel. All steel items plated. Average contents 400-600 pieces.
 Sold by weight, **£2.65** 21b bag.

MANY HUNDREDS OF TRANSFORMERS IN STOCK - SEND SAE FOR LIST
1 ONLY DEC PDP8M
 16k memory, auto restart, vk8 video set, serial/parallel, printer interface etc. Perfect order.
£850.00 + VAT + carriage.

IMPORTANT
 We have now moved to larger premises and whilst we are recovering! callers are welcome on Fridays and Saturdays between 9.30am and 5.30pm, and by appointment on other days.

FREQUENCY	CRYSTALS	PRICE
100 KHZ	B7G	£2.35
250 KHZ	HC8/U	£2.35
1.00 MHZ	HC8/U	£2.35
2.00 MHZ	B7G	£2.25
2.50 MHZ	HC18/U	£2.25
5.00 MHZ	HC18/U	£2.25
8.00 MHZ	HC18/U	£2.25
10.25 MHZ	HC18/U	£1.75
11.20 MHZ	HC18/U	£2.80
33.339 MHZ		
UART Xtal 3B 40 KHZ		
SAE for latest XTAL stock list.		

SCOOP OF THE YEAR HAZELTINE H1200 V.D.U. TERMINAL

Due to an even bigger purchase we are now able to pass our bulk buy savings direct to you!

960 characters 12 x 80, 55 key TTY keyboard, RS232 interface, scroll up, adjustable baud rate 75-9600 upgradable to 1920 (24 x 80) characters, lower case option, plus many other features.

Brand New and Boxed - at only

£250 + VAT + Carriage

FULL TECHNICAL MANUAL **£10.00**

POWER SUPPLY UNITS

5 VOLT 2.5 AMP T.T.L. P.S.U.
 Made for T.T.L. this compact ex computer systems unit features a 10 amp transformer with D.C. outputs of 5 volts @ 2.5 amps and 7.5 volts @ 5 amps. The 5 volt output is fully regulated and smoothed and has electronic current limiting. May be easily moded for 5 volts @ 7.8 amps, believed working but untested.
 Complete with circuit **£8.25** P.P. £1.60

KEYBOARD



A special bulk purchase enables us to offer the above Keyboard at a lowest ever price. 49 coded keys encoded into a direct TTL compatible 7 bit output. Features such as delayed strobe, 5 volt D.C. single rail operation and rollover protection make this an absolute must for the MPU constructor! Supplied complete with connection diagram and edge connector. at a secondhand price of only **£20.00** P.P. £1.60

UNIVERSAL TOROID TRANSFORMER

Just what you have been waiting for, made for a major electronics co. this miniature toroidal transformer accepts 240V AC input and gives AC outputs of 0-10v @ 1.8 amps and 2 x 0-20v @ 750ma. Intended for an MPU supply of +5 and -12v, its small physical size of only 2 1/2" x 1 1/2" and negligible hum field make it a snip at only **£4.25** + pp 60p.

HIGH EFFICIENCY SMITHS RADIAL BLOWERS

Are your hot parts sweltering? Then keep them cool with our high efficiency radial snail type blowers. Made by Smiths, designed for continuous use in expensive electronic equipment very powerful and quiet, gives massive air flow to prolong component life and reliability. Easily mounted, air aperture 2 1/2" x 3". Ideal linears etc.
BRAND NEW
£4.25 P.P. £1-10

ELECTRONICS
 64-66 Melfort Road, Thornton Heath, Surrey. 01-771 2027
MAIL ORDER INFORMATION
 Unless otherwise stated all prices inclusive of VAT. Cash with order. Minimum order value £2.00. Prices and Postage quoted for UK only. Where post and packing not indicated please add 30p per order. Bona Fide account orders minimum £10.00. Export and trade enquiries welcome. Orders despatched same day where possible. Access and Barclaycard welcome.

Electronic Brokers


49/53 Pancras Road London NW1 2QB Tel: 01-837 7781. Telex 29869

Our background

Electronic Brokers is Europe's largest specialist in quality, second user test equipment, mini-computers and associated peripherals. Established 11 years ago, we have pioneered the second user concept in Britain, and many overseas territories.

One reason for our success is the company's policy of continually

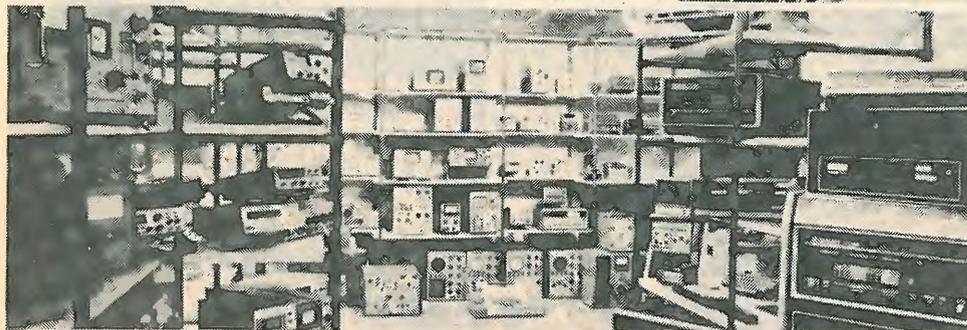
updating the type of equipment we sell. So from selling to private users, the business has rapidly developed, and today, our customer list includes leading international companies, research establishments, universities, colleges and government institutions throughout the world.



Back up

To support our growth we have a skilled team. This includes trained sales staff, whose role is not only to sell, but provide a helpful information service to our many customers. Backing this team is our own service laboratory where technicians monitor each item of equipment we sell. Our maxim is

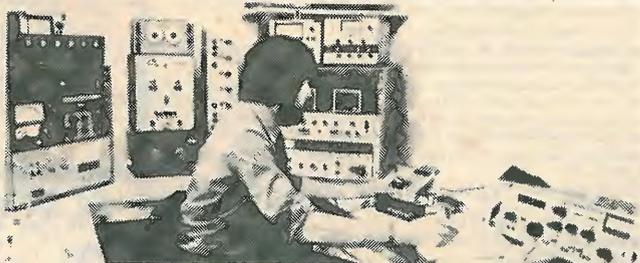service, and those who have dealt with us will know that we endeavour to always live up to our reputation. Equipment can be configured to customer's exact requirement, and a number of options can be made available — almost like custom-tailoring.



Refurbishing

Our own service laboratory checks each item that arrives at our Pancras Road headquarters. Electronic test equipment is then thoroughly cleaned and a schedule

prepared for any work which needs to be carried out to meet customer's requirements. Whether it is new test equipment or used, all items pass through the service

laboratory where they are given final tests to ensure they meet manufacturers' specifications, before delivery to the customer.

Unless otherwise stated all equipment offered in the Electronic Brokers 4 page advertisement is refurbished and in the case of Test Equipment also calibrated. Test equipment is guaranteed for 12 months; computer peripherals for 3 months.

Hours of Business: 9 a.m. - 5 p.m., Mon.-Fri. Closed lunch 1-2 p.m.

A copy of our trading conditions is available on request.

Add 15% VAT to ALL PRICES

Carriage and Packing charge extra on all items unless otherwise stated.

WW — 114 FOR FURTHER DETAILS

SEND FOR AUTUMN '79 CATALOGUE

Containing latest information on our stocks of Test Equipment, Minicomputers, Peripherals, Stroboscopes, Tachometers, etc. Airmail to overseas addresses £2.00.


SEE US AT E.M.I.X. '79 OCT. 9, 10 and 11 BLOOMSBURY CENTRE LONDON



PHILIPS

PM3261 Dual Trace Portable Oscilloscope.
DC — 120MHz, 5mV — 2/div
5nS — 1S/div Full delayed sweep.
5 digit LED event display
Auto. TTL triggering

£1250.00
current new price
£1990.00

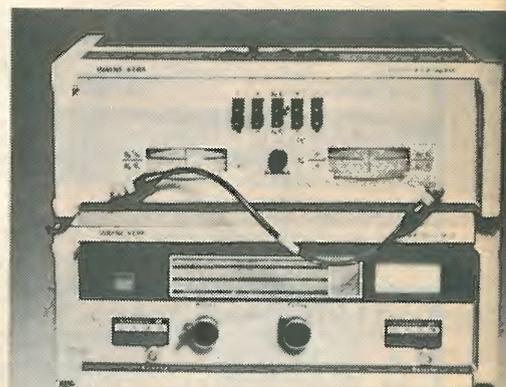

WAYNE KERR

Wayne Kerr B602 VHF Admittance Bridge
c/w SR268 source and Detector
Frequency Range 100kHz—100MHz
Ranges: 1pF—1mF, 100μΩ—100MΩ
1pH—10H, 10n mhos—10k mhos
Accuracy typically 1%

£1900.00




PHILIPS

PM2524 4 1/2 Digit D.M.M.
AC/DC voltage and current and resistance
Full autoranging.

£299.00
Current new price £435.00

No.1 in Second User Test Equipment

Add 15% VAT to all prices

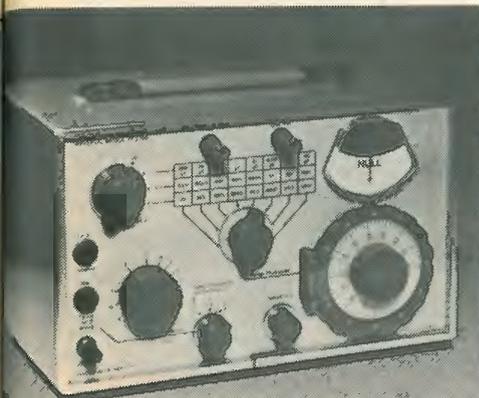

MARCONI INSTRUMENTS

TF2700 RCL Bridge
Ranges: 0.2 μ H—110H,
0.5pF—1100 μ F,
0.01 Ω —11M Ω . Accuracy typically 1%
Battery operated

£210.00




HEWLETT PACKARD

141T-8552A-8553B Spectrum
Analyser.
1kHz-110MHz Variable persistence
Display Sensitivity—140dBm

**THE MOST POPULAR
ANALYSER OF ALL TIME.**

£5100.00

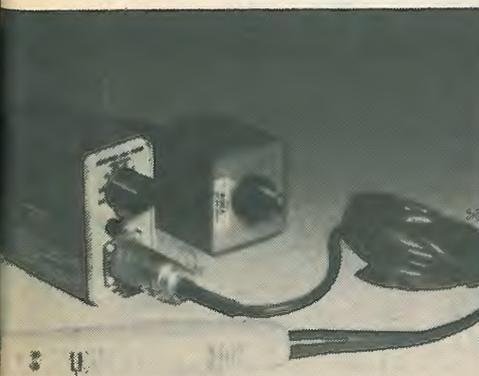

TEKTRONIX

P6046 Differential Probe
DC-100MHz
1mV-300mV/div
Complete with power supply.

£350.00



HEWLETT PACKARD

5% DIGIT D.M.M. 3490A
AC-DC volts
and resistance
Self check facility

only £550.00

Current new price
£1,679.00



MARCONI

TF1313A Universal Bridge
LC R. 0.1% accuracy

£790

Current new price **£995.00**

STOP PRESS!

Exclusive purchases of
outstanding Test Equipment
now arriving . . .


Save on the
best at Electronic Brokers!

AMPEX PR 2200 FM / DR Tape Recorder	£6500	PM 3262 100MHz Scope	£1300
BIOMATION 1650 16 Channel Logic Analyser	£4100	PM 3211 15MHz Scope	£450
BRUSH 816 High Speed Multipoint 8 Channel Chart Recorder	£695	PM 3212 25MHz Scope	£625
DATA LABS DL 905 Transient Recorder	£875	PM 3214 25MHz Scope	£700
DL 019 Power Line Disturbance Monitor	£300	PM 3243 50MHz Storage Scope	£2000
DATRON 1051 5 $\frac{1}{2}$ Digit D.M.M.	£995	PM 2517E D.M.M.	£120
DYMAR 1771 L.F. Wave Analyser	£375	PM 5127 Function Generator	£395
1785 AM / FM Mod. Meter	£300	PM 5108 Function Generator	£250
1765 L.F. Distortion Meter	£250	PM 6614 520MHz Counter	£450
FLUKE 8022A D.M.M. (Brand new)	£89	PM 2522A D.M.M.	£200
HEWLETT PACKARD 651B Oscillator	£415	RACAL 9081 FM / AM Synthesized Sig. Gen.	£1900
4204A Decade Oscillator	£750	Store 4 FM Tape Recorder	£2600
1703A Dual Trace Storage Scope	£1850	9915 8 Digit 520MHz Counter	£395
1600A 16 Channel Logic Analyser	£2050	SHANDON SOUTHERN F 10-650 6 Channel U/V Recorder	£725
8640A AM / FM Signal Generator	£1800	SYSTRON DONNER 6250 8 Digit 50MHz Counter Timer	£175
MARCONI INSTRS. TF 2102M / 1 A.F. Oscillator	£195	6220 L.F. Frequency Counter	£160
TF 2300A AM / FM Mod. Meter	£550	SOLARTRON 7055 Microprocessor Controlled D.M.M. Without Processor Option	£975
TF 2950 / 5 Mobile Radio Test Set	£1250	With Processor Option	£1300
TF 2950 / 8 Mobile Radio Test Set	£1500	7065 Microprocessor Controlled D.M.M. Without Processor Option	£1150
TF 144H / 4 Signal Generator (Late model)	£750	With Processor Option	£1450
TF 1066B / 6 Signal Generator (Late model)	£725	TEKTRONIX 5403 Scope (with 5A48 + 5B42)	£975
TF 2603 R.F. Millivoltmeter	£525	434 25MHz Split Screen Storage Scope	£1600
TF 2012 U.H.F. Sig. Gen.	£900	434 (option 01) Storage Scope	£1700
TF 2606 Diff Voltmeter	£725	P. 6042 Current Probe	£375
TF 2331 Distortion Factor Meter	£475	WAYNE KERR B 642 Autobalance Univ. Bridge	£695
TF 2330A Wave Analyser	£725	WATANABE MC 641 6 Channel Chart Recorder	£2250
TF 2300B Mod. Meter	£950	WAVETEK 131 Function Generator	£225
PHILIPS PM 2514 Autoranging D.M.M.	£125	135 Sweep Function Gen.	£275
PM 2527 Autoranging D.M.M.	£400	144 Sweep Function Gen.	£325
PM 3260 120MHz Scope	£1095	1801A R.F. Sweep Gen.	£435
		2001 R.F. Sweep Gen.	£650

REMEMBER!!
All equipment has a 12 month
Warranty, full specifications
are available on request.

Electronic Brokers

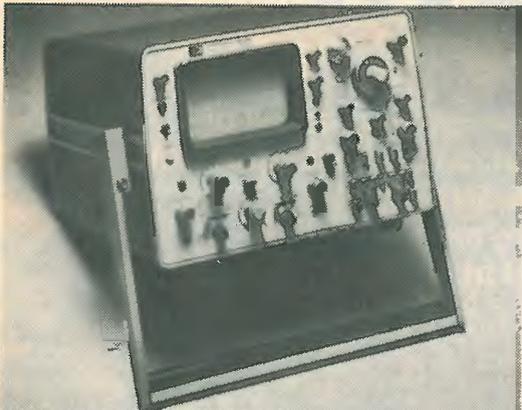
49/53 Pancras Road London NW1 2QB Tel: 01-837 7781. Telex 298694



HEWLETT PACKARD

DUAL TRACE PORTABLE
OSCILLOSCOPE 1707B
DC-75MHz. 10mV-10V sensitivity.
Delayed Sweep. Very
High Quality

£925.00

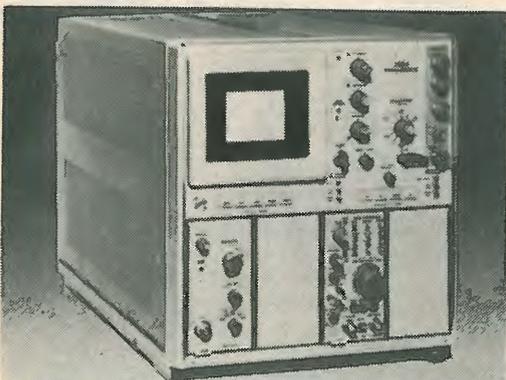

7904 Oscilloscope Main Frame
with 7A26 - 7A19 - 7A21 - 7892
Bandwidth: 350MHz with 7A26
500MHz with 7A19
1GHz with 7A21
Sweep speeds 0.5nS - 0.2S/div,
Full delayed sweep.

TEKTRONIX

SUPERB/QUALITY AT VERY SENSIBLE PRICE £6350

BRIDGES

GENERAL RADIO

Immittance Bridge 1607A £750
1608A LCR Bridge. Accuracy
typically .05% £1450

MARCONI INSTRS.

In Situ Univ. Bridge TF2701

Univ. Bridge TF1313 £395

WAYNE KERR £395

Univ. Bridge B221 (0.1%)

£275

Univ. Bridge B521 (1%) £120

Low Impedance Adaptor Q221

£75

CALIBRATION EQUIPMENT

HEWLETT PACKARD

DC Voltage Source & Differential

Voltmeter 740B £850

DC Voltage Source & AC/DC

Diff. Voltmeter 741B £975

FLUKE

883AB AC/DC Differential Volt-

meter £975

TEKTRONIX

Time Mark Generator 184 £275

Time Mark Generator 2901

£450

5nS Pulse Generator 2101

£525

Pulse Generator 109 £320

SOUND LEVEL METERS

GENERAL RADIO

Portable Sound Level Meter

1565B £225

Portable Sound Level Meter

1983 £190

1933 & 1935 Portable Sound

Level Meter with data cassette

recorder £2600

Portable Sound Level Meter

1981 £575

DIGITAL COUNTERS

GOULD ADVANCE

500MHz Counter TC15 + 15P1

£495

80 MHz Counter TC17 or TC17A

£195

FLUKE

125MHz Multi-Function Counter

1910A-01 £285

125MHz Multi-Function Counter

1910A £199

520MHz Communications

Counter 1920A-06 £490

125MHz Multi-Function Counter

1925A £405

520MHz Univ. Timer Counter

1953A-01 £675

125MHz Univ. Timer Counter

1953A-15-16 £850

PHILIPS

80MHz Timer Counter PM6612

£405

1GHz Timer Counter PM6615

£795

80MHz Freq. Counter PM6661

£185

512 MHz Freq. Counter

PM6645 £710

520MHz Automatic Freq.

Counters PM6664 £305

DIGITAL VOLTMETERS & MULTIMETERS

ADVANCE

True R.M.S. Voltmeter DRM6

£150

FLUKE

4½ digit D.M.M. 8040A-01

£220

4½ digit D.M.M. 8600A £290

4½ digit D.M.M. 8600A-01

£335

8800A D.M.M. 5½ digit £599

HEWLETT PACKARD

5½ digit D.M.M. 34702A +

34740A £295

PHILIPS

4 digit D.M.M. PM.2424 £300

4½ digit DC. D.V.M. PM2443

£430

3½ digit D.M.M. PM2513 £90

3½ digit D.M.M. PM2513A

£95

SCHLUMBERGER-

SOLARTRON

5½ digit Digital Multimeter

A243 £675

4½ digit D.M.M. 7050 £350

OSCILLOSCOPES

ADVANCE

OS2200 Dual Trace Storage with

delayed time base £745

COSSOR

35MHz Dual Trace CDU 150

£450

50MHz Dual Trace 4000 £495

4100 Dual Trace 75MHz £695

DYNAMCO

30MHz. Dual Trace. 7100

£350

PHILIPS

5MHz Miniscope Battery/Mains.

PM3010 £325

S.E. LABS

35 MHz D.T. Scope SM 113

£350

TEKTRONIX

24 MHz Dual Trace Bench. 543B

+ CA £350

50 MHz Dual Trace Bench. 647

+ 10A2 + 11B2 £600

24MHz D.T. Bench. 545B + CA

£425

50MHz D.T. Bench. 547 + 1A1

£775

80MHz D.T. Bench 585A + 82

£775

Four Trace Plug in M £275

Four Trace Plug in 1A4 £600

Dual Trace Plug in CA £60

Differential Comparator Plug in Z

£150

10MHz D.T. Battery Miniscope

326 £900

Spectrum Analyser Plug In 1L30

£1000

Spectrum Analyser Plug In 1L40

£1000

7D11 Digital Delay

£850

TELEQUIPMENT

50MHz Portable Scope D75

£675

HEWLETT PACKARD

Time Domain Reflect. System

Type 140A & 1415A £1200

High Sensitivity X-Y Scope 130C

£345

OSCILLOSCOPE PROBES

ELECTRONIC BROKERS

(NEW)

X1 Probe Kit EB90 £9

X10 Probe Kit EB91 £11

X1 X10 Probe Kit EB95 £15

SIGNAL SOURCES

ADVANCE

Low Dist. Oscillator SG68A

£120

FLUKE

Freq. Synthesiser 6160A/DX

£875

HEWLETT PACKARD

AM/FM. Generator 202H £495

VHF Sig. Generator 608D £495

VHF Sig. Generator 608E £675

Variable Phase Oscillator 203A

£495

612A UHF Signal Generator

540-1230 MHz £825

MARCONI INSTRS.

AM/FM Signal Generator

TF2015/1 £110

A.M. Sig. Generator TF801D/

from £40

A.M. Sig. Generator TF801D

8S £60

AM/FM Sig. Gen. TF995A/5

£47

AM/FM Sig. Gen. TF995B/2

£38

AM/FM Sig. Gen. TF2006

£875

Two Tone Source TF2005R

£350

A.F. Oscillator TF2000 £325

R.C. Oscillator TF1101 £120

A.F. Oscillator TF2100 £150

PHILIPS

AM/FM Signal Generator

PM5326X £735

AM/FM Signal Generator

PM5324 £450

Function Generator PM 5167

£795

SIGN/ROGERS

Low Distortion Oscillator S324

£90

MISCELLANEOUS

AVO/BPL

Component Comparator

CZ457/6 £235

Electronic Multimeter EA 113

£85

BRADLEY

D.C. Voltage Calibrator 126B

£275

E.N.I.

R.F. Power Amplifier 500L

£315

GERTSCH

Complex Ratio Bridge CR1B

£600

GENERAL RADIO

Vibration Analyser 1911A

£2100

HEWLETT PACKARD

310A Wave Analyser 1kHz-

1.5MHz £1200

True R.M.S. Voltmeter 3400A

£505

Microwave Freq. Converter

2590B £595

MARCONI INSTRUMENTS

A.F. Transmission Test

Set TF2332 £425

M.F. Transmission Test Set

TF2333 £600

Quantization Distortion Tester

TF2343 £400

Deviation Meter TF791D £195

Electronic Voltmeters TF2604

£250

Attenuator TF2162 £135

Sine Sq. Pulse & Bar Generator

TF2905 £450

Grey Scale Generator TF2909

£600

PHILIPS

Pulse Generator PM5712 £525

Pulse Generator PM5715 £575

Pulse Generator PM5775 £600

Pulse Generator PM5776 £700

Pattern Generator PM5501

£180

Wow & Flutter PM6307 £275



WESTON

4449 3½ Digit D.M.M.
AC-DC Voltage and current and resistance,
SUPERB VALUE AT ONLY
QUANTITIES AVAILABLE

£59.00

No.1 in Second User Minis & Peripherals



AZELTINE H-2000A NOW ONLY **£395**


Standard specification includes full edit capability, direct addressing, standard V.24 (RS232) interface. 90 days warranty.

Now available: Off-the-shelf delivery of the latest Azeltine Model 1510, Brand New and Boxed, at a discounted price of **£825.00**.



DEC PDP11/04 — SPECIAL PURCHASE

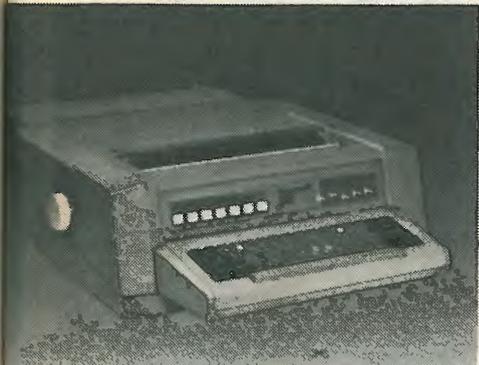PDP11/04-MD 9-slot 5 1/4" Processor with 28K core and DL11W Interface. **BRAND NEW SURPLUS — ONLY £4,500.00.**



TELETYPE TERMINAL 7075


Keyboard Send / Receive Impact Printer providing full upper and lower case character set, switch-selectable print speeds of 10, 15 and 30 cps. 118-column print line with pin-feed platen suitable for paper or continuous stationery (paper width 12.85"). Standard V.24 (RS232) Interface. **PRICE £575.00.**



TEXAS SILENT 700

Model 725KSR Terminal mounted in integral carrying case complete with built-in acoustic coupler. 64 ASCII character set with 5 x 7 dot matrix. 30 cps. Weight 35lbs. Dimensions 21 1/2" x 19" x 6 1/2".

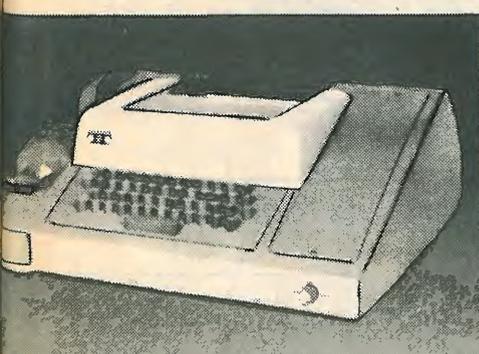Also available Model 733ASR keyboard terminal complete with twin cassette drive for high-speed ASR capability, and the 742 programmable data terminal. Prices from **£695.00.**



ASR33 and KSR33 TELETYPE

Input/Output terminals with 64 ASCII character set. 30 baud operation. Paper tape punch and reader (ASR33 only). Choice of interface (20mA or RS232). ASR33 — **£425.00**. ASR33 — **£650.00**. Pedestal **£100.00**.



NEW ASCII KEYBOARDS

KB756 ROM-encoded 56-station keyboards with full 128 ASCII character set. Standard TTL logic. Power requirements +5 — 12V. Supplied with full technical data and circuitry (see next column for prices).

DEC EQUIPMENT

- BA11-ES Expander Box **£750**
- DL11-B Serial Interface **£275**
- KW11P Programmable Clock **£345**
- MM11-LP 8K Add-on Core with backplane (11-05, 11-35) **£750**
- MS11-FP 8K Add-on MOS (11-04, 11-34) **£375**
- PDP8E — Series — Large stocks of add-on core and option modules.
- PR11 High-speed paper tape reader and control **£1,450**
- RK8E/RK05J Disk drive and control **£3,950**
- RK11D/RK05J Disk drive and control **£3,950**
- TA11/TU60 Twin Cassette drive and control **£1,500**
- TWE16-ED 9-track 800/1600 bpi. **BRAND NEW EX CANCELLED** **P.O.A.**
- ORDER
- TC11 TU56 DECtape drive and control **£1,395**
- H9602 Data system Cabinet, complete with power distribution unit (no side panels), as new condition **£750**

COMPUTER PERIPHERALS

- CENTRONICS 101 Matrix printer**
64SCII uppercase character set. 165 characters per second. 132 print columns. 5 x dot matrix. Parallel input.
PRICE: £750
- SCOPE DATA SERIES 200 PRINTER**
240 cps 80 column receive-only matrix printer. Full upper and lower case ASCII character set. Standard RS232 interface Electro-sensitive printing ensuring quiet operation. **BRAND NEW SURPLUS**. New low price **£495.**
- DEC LA30 DECWRITER**
80-column KSR terminal with selectable transmission speeds of 10, 15 and 30 cps. Upper case ASCII character set. Current loop interface. Integral pedestal **£575.**
- SEALCRO PATCH BOARDS**
Programme boards for switching and interconnecting input/output circuits. 11 + 20 XY matrix. Interconnection is by means of shorting. Skip and component holding pins (not included). Dimensions 7 1/2" x 5 1/4" x 1".
PRICE £12.50 (mail order total £14.58).

- CALCOMP 565 DIGITAL DRUM PLOTTER** Y-Axis 11". X-Axis 120". Maximum speed 300 increments 4.2" per second. Input Positive or negative polarity pulses, amplitude greater than 10V, rise time less than 10 microsec., minimum pulse with 4 microsec. Source impedance less than 500 ohms. **PRICE £1,250.**
- GE TERMINET 1200**
Receive only impact printer with switch selectable print speeds of 10, 30 and 120 cps. 120 print positions with adjustable pinfeed paper tractor. 94-character upper and lower case ASCII. Current interface.
PRICE £695.
- NEW SHUGART FLOPPY DISC DRIVES**
SA400 Minifloppy — 110KB capacity, 35 tracks, transfer rate 125-bit/sec. AV access time 550msec Power requirements + 5VDC + 12VDC. **PRICE £195.**
SA800 Floppy — 400KB capacity, 77 tracks, transfer rate 250K-bit/sec AV access time 280msec. Power requirements + 24VDC + 5VDC-5VDC. **PRICE £395.**

VIDEO TAPE — SPECIAL PURCHASE

Ampex type 162-3000 DD-20 1" x 3000' video tape on 9 1/4 reels. **BRAND NEW SURPLUS — ONLY £15.00** per reel (plus carriage and VAT).

NEW KEYBOARDS

- | | | |
|--|---------------|---------------|
| KB756 key-stations mounted on PCB | £49.50 | £58.65 |
| KB756MF, as above, fitted with metal mounting frame for extra rigidity | £55.00 | £64.98 |
| Optional Extras | | |
| KB15P Edge Connector | £3.25 | £4.31 |
| KB701 Plastic Enclosure | £12.50 | £15.24 |
| KB702 Steel Enclosure | £25.00 | £30.48 |
| KB710 Numeric Pad | £8.00 | £9.78 |
| KB2376 Spare ROM Encoder | £12.50 | £14.95 |
| DC512 DC-DC Converter | £7.50 | £9.20 |

LATEST ADDITION TO THE RANGE

KB771 71 Station keyboard incorporating separate numeric/cursor control pad and installed in custom-built steel enclosure with textured enamel finish. Case dimensions: 17 1/4" x 7 1/2" x 3 3/8". Total weight: 4Kg.
PRICE £95 (mail order total **£108**)
D25S Connector for KB771 **£4.25** **£5.46**
Quantity Discounts available

NEW KEYTOP/KEYSWITCH KITS — ACSII CHARACTER SET. BRAND NEW SURPLUS

Pack of 58 keytops and keyswitches comprising 49 "Qwerty" set, TTY format + 9 Edit/Function keys.
PRICE £15 (mail order total **£18.98**)

SURPLUS KEYBOARDS

KB3 ROM-encoded ASCII keyboard with 63 push-button key stations. TTL-compatible. Power requirements: + 5V-12V. Constructed on rugged PCB with metal mounting plate. Supplied with full technical data. Manufacturers surplus.
ONLY £35 (mail order total **£41.98**)

Electronic Brokers

ELECTRO-TECH COMPONENTS LTD.

364 EDGWARE ROAD, LONDON, W.2. TEL: 01-723 5667

TE20D R.F. SIGNAL GENERATOR



Accurately covers 120 KCS. To 500 MCS in 6 bands. Directly calibrated. Variable R.F. Attenuator 240v AC. Dimens. 140 x 215 x 170mm.

£52.95
P.&P £1.25

Y7206 EN 20,000 OPV



AC Volts: 0-10, 50, 250, 500, 1000. DC Volts: 0-0.5, 5, 25, 125, 250, 500, 1000. DC Current: 0-0.05, 5, 250 mA. Resistance: 0-3k ohms, 300k ohms, 3 meg ohms. Decibels: -20—+63 db. Dim: 127 x 90 x 32 mm.

£10.95 P.&P. 75p



IT 1/2 20,000 OPV

AC volts: 0 to 10, 50, 100, 500, 1000. DC volts: 0 to 5, 25, 50, 250, 500, 2500. DC current 0 to 50 uA. 2.5 ma, 250 ma. Resistance: 0 to 6K ohms, 6 meg ohms. Decibels: -20 to +22 db. Capacitance: 10 pf, 0.01 uf 0.1 uf. Size: 4 1/2 x 3 1/4 x 1 inch.

£10.95
P.&P. 75p



TMK500 MULTITESTER 30,000 OPV

A sturdy and reliable instrument. Has internal buzzer. AC volts: 0 to 2.5, 10, 25, 100, 250, 500, 1000. DC volts: 0 to 0.25, 1, 2.5, 10, 25, 100, 250, 1000. DC current: 0 to 50 uA, 5 ma, 50 ma, 12 amp. Resistance: 0 to 6K, 60K, 6 meg, 60 meg. Decibels: -20 to +56 db. Short test: Internal buzzer. Size: 160 x 110 x 55 mm.

£20.50 P.&P. 75p



TX17 TE15 GRID DIP METER "TRADIPER"

Covers 440 KCS to 280 MCS in 6 ranges. 6 coils supplied. Chief applications: (a) Measuring tuning frequencies. (b) Oscillating frequency circuit measured without oscillation. (c) Earphone monitoring - Heterodyne frequency meter. (d) Substitution as a test oscillator. (e) Relative field strength meter. Dim: 150 x 80 x 45 mm.

£32.50
P&P £1


ROTARY STUD SWITCH PLESSEY 30 way, 2 bank.

Single pole. Contacts 1 amp. 240v. AC/DC. .005Ω res. Make before break. Stop infinitely adjustable allowing for any desired arc of travel. Ideal for instrument and model switching. Size 2 1/4" dia overall x 2 1/4" deep plus 1 1/4" x 1/4" dia. spindle.

£3.25 P.&P. 50p

SOLENOIDS 240V A.C.

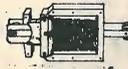MAGNETIC DEVICES LTD. 20lb. pull for 50% duty. 1 1/2" travel, push or pull. Shackle both ends. Size 1 1/4" wide x 3 1/4" high x 4" long plus 3" arm travel.



£6.75 + P.&P. £1.00


Please add 15% VAT to all orders

Callers welcome

We are open 9 a.m.-6 p.m. Mon.-Sat.

We carry a very large selection of electronic components and electro-mechanical items. Special quotations on quantities.

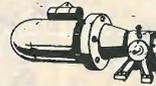1/8 H.P. reversible geared motor. 220/240V. 50 Hz. 1 Ph. cap. start cont. rating. Gearing 5:1. Final drive approx. 280 rpm. 3/4" dia. shaft. Size 1 1/4" inc. gearbox x 5 1/2" dia. plus cap. and base. New. Robust.




£23.95 Carr. £5.00

BENDIX MAGNETIC CLUTCH

Superb example of electro-mechanics. Main body in two sections, coil section fixed with 3/4" sleeve, drive section rotating on outer perimeter. Uniting plate has 3/4" ID bearing concentric with main section and 18-tooth cog wheel. Extremely powerful transmission. 24V D.C. 240 m/s.

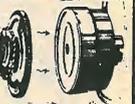Dozens of uses in Home, Farm, Workshops & Lab.



£4.75 P.&P. 75p

HERE IT IS! THE BRAND NEW 8022A HAND-HELD DMM

Consider the following features: 6 resistance ranges from 200 ohm - 20 mohm. 8 current ranges from 2mA-2A AC/DC. 10 voltage ranges from 200 mv - 1000v DC, 200 mc - 750V AC. Pocket size—weighing only 370 gms. Full overload protection—will withstand 6kv spikes. Rugged construction—virtually indestructible. Meets tough military specs—drop proof. In line push-button operation for single-handed useage. Incorporates low power CMOS chip for low power consumption. All this plus a 2-year full guarantee.

For only £89.00
Carriage and insurance £3.00



Even more sophisticated the Fluke 8020A. Identical in most respects to the 8022A but in addition incorporates a conductance range from 2mS-200nS.

£112.00

Carriage and Insurance £3.00

A handsome soft carrying case is available for the 8020A and 8022A at **£7.00**


OFF THE SHELF DELIVERY ON THESE



DIGITAL MULTIMETERS

The following accessories are in stock now

Y8008 Touch and Hold Probe	£18.00
80K-40 High Voltage Probe	£45.00
81RF RF Probe to 100 MHz	£32.00
80T-150C Temperature Probe (C)	£55.00
801-600 Clamp-on AC Current Probe	£50.00

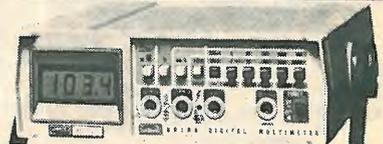

8010A AND 8012A BENCH MODEL D.M.M.s

The 8010A is a general purpose, bench/portable digital multimeter with more functions and features than ever offered for such a low price. Its companion, the 8012A, has identical characteristics except that it has two additional low resistance ranges, 2Ω and 20Ω to replace the 8010A's 10 ampere current range.

The 8010A and 8012A feature: 10 voltage ranges from 200mv - 1000v dc, 200mv - 75v ac. 3 conductance ranges from 2mS - 200 nS. 6 resistance ranges from 200Ω - 20MΩ - the 8012A has two additional resistance ranges 2Ω and 20Ω. 10 current ranges from 200μA - 2A AC/DC - the 8010A has two additional current ranges 10A AC and 10A DC.

8010A £159.00 8012A £179.00

Carriage and Insurance £3.00

The 8010A is also available with two rechargeable Nicad size C batteries installed in option -01 at **£179.00**.

AURA SOUNDS

THE WERSI SPECIALISTS

SOUTHERN SHOWROOM
at 14/15 ROYAL OAK SHOPPING CENTRE
PURLEY, SURREY
TEL. 01-668 9733

FOR

WERSI ORGANS D.I.Y. KITS LPs

Catalogues and Price Lists — £1.00

NORTHERN SHOWROOM
at 17 Upper Charter Arcade
Barnsley, Yorks.
Tel. Barnsley 5248

WW — 084 FOR FURTHER DETAILS

SEND FOR S I N T E L FREE CATALOGUE

S I N T E L

CD4015	0.83	CD4032	0.89	CD4049	0.50	CD4072	0.20	CD4099	1.85
CD4016	0.48	CD4033	1.25	CD4050	0.43	CD4073	0.20	CD4502	0.81
CD4017	0.79	CD4034	1.71	CD4051	0.82	CD4075	0.20	CD4510	1.01
CD4018	0.83	CD4035	1.06	CD4052	0.82	CD4076	1.17	CD4511	1.25
CD4019	0.50	CD4036	2.86	CD4053	0.82	CD4077	0.39	CD4514	2.47
CD4000	0.15	CD4020	1.11	CD4037	0.85	CD4054	1.04	CD4078	0.20
CD4001	0.17	CD4021	0.90	CD4038	0.96	CD4055	1.18	CD4081	0.20
CD4002	0.17	CD4022	0.82	CD4039	2.78	CD4056	1.18	CD4082	0.20
CD4006	1.04	CD4023	0.18	CD4040	0.97	CD4059	4.29	CD4085	0.64
CD4007	0.18	CD4024	0.70	CD4041	0.75	CD4060	1.00	CD4086	0.64
CD4008	0.87	CD4025	0.20	CD4042	0.69	CD4063	0.98	CD4089	1.39
CD4009	0.50	CD4026	1.55	CD4043	0.88	CD4066	0.55	CD4093	0.80
CD4010	0.50	CD4027	0.44	CD4044	0.84	CD4068	2.35	CD4094	1.89
CD4011	0.18	CD4028	0.77	CD4045	1.28	CD4069	0.20	CD4095	0.94
CD4012	0.20	CD4029	1.03	CD4046	1.20	CD4069	0.20	CD4096	0.94
CD4013	0.43	CD4030	0.50	CD4047	0.89	CD4070	0.46	CD4097	3.35
CD4014	0.83	CD4031	2.00	CD4048	0.50	CD4071	0.20	CD4098	0.98

ASSEMBLED LATCHED COUNTER MODULES



Our range of Industrial Latched Counter Module Kits is now available ready-built. These counters use both CMOS and TTL ICs and will save you considerable design, purchasing, building and de-bugging time. Each module uses a set of red LED displays and features a single in-line plug and socket. Instructions are provided. For full details please send for Catalogue.

	TTL			
	Part No.	Built	Part No.	Kit
2 digit	401-484	£13.22	526-412	£10.52
4 digit	715-484	£23.38	657-412	£17.98
6 digit	293-484	£33.76	721-412	£25.66
	CMOS			
	Part No.	Built	Part No.	Kit
2 digit	985-568	£13.12	548-470	£10.42
4 digit	512-568	£25.31	869-470	£18.11
6 digit	393-568	£33.95	191-470	£25.85


Our offices are at Chapel Street, Oxford, but please do not use this as a postal address. FAST SERVICE. We guarantee that Telephone Orders for goods in stock, received by 4.15 p.m. (Mon.-Fri.) will be dispatched on the same day by 1st Class Post (some heavy items by parcel post) and our stocking is good. Private customers should telephone and pay by giving their Access or Barclaycard number with a minimum value of £5. Official orders no minimum. Official orders, Companies, Govt., Natl. Inds., and Univa. ORDERS: C.W.O. add VAT at 8% + 35p p&p. TELEPHONE and CREDIT invoiced ORDERS add VAT at 8% + 50p p&p minimum charge (the balance will be charged at cost). Please send FAST SERVICE. EXPORT ORDERS welcome, no VAT but add 10% (Europe), 15% (Overseas) for Air Mail p&p. For export postage rates on heavy items — contact us first.



SEND YOUR ORDER TO
SINTEL
PO BOX 75C OXFORD
Tel: 0865 49791



Automatic component testing

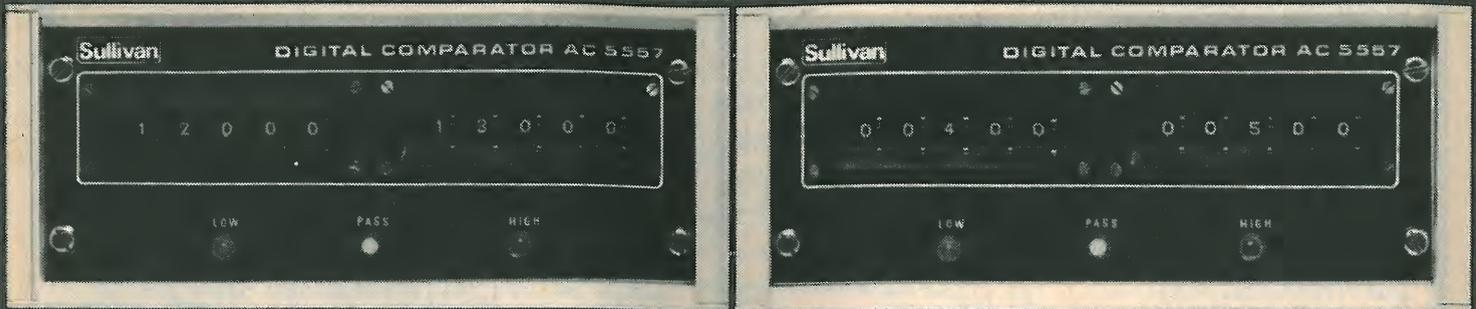

As a component analyser, the Sullivan AC5555 takes some beating. Simply slot the component into the jig and watch the equipment select the correct range and function and provide a read-out of the correct value...automatically. It's as simple as that.

However, couple the AC5555 with the AC5557 Digital Limit Comparator and you've got a ready made system for large batch testing of components. Just set the upper and lower limits and the equipment will indicate low, high or pass for the component.

Simplicity, accuracy and reliability
— no more than you would expect from Sullivan.

Get in touch with us today, and we'll tell you the full facts about our equipment for automatic component testing.

Sullivan

HW Sullivan Ltd
Archcliffe Road, Dover, Kent CT17 9EN.
Tel: (0304) 202620. Telex: 96283.

Thorn Measurement & Components Division

PRECISION DIAL GAUGES John Bull No. 6 series ↑. 0.1mm. £6 P.P. 50p.
COAXIAL CRYSTAL DETECTORS. (Marconi-Saunders), 200 MHz-12 GHz. £7.50
FIBREGLASS COPPER-CLAD BOARD
 9x4½x1/16in. 40p P&P 10p
 9x6x1/16in. 50p P&P 15p
 9x4½x1/16in. (double sided) 50p P&P 10p
 9x6x1/16in. (double sided) 65p P&P 10p
 15x15x1/16in. (double sided) £2.50 P&P 50p
OFF-CUT PACKS. 150 sq. ins. £1 P.P. 25p.
LOW PROFILE RELAYS (ZETTLER) P.C.
 Mounting. 6v or 12v. D.C.
 1 P. c/o 50p. P&P 10p.
 2 P. c/o. 75p. P&P 10p.
 4 P. c/o. £1. P&P 10p.
TRANSISTORISED BRIDGE MEGGERS (500v.)
 Ex P.O. Good condition. £20. P&P £2.
PLUG-IN (CRADLE) RELAYS 6/12/24/48V.W.
 2 P. c/o. 65p. P&P 10p.
 4 P. c/o. 85p. P&P 10p.
 BASES 10p each
P.A.R. BI-STABLE RELAYS. 24v d.c. 4 c/o £1 P.P. 15p.
U.H.F. COAXIAL CABLE (white) Double screened.
 Lab. quality 100m. drum £10 p.p. £1.50.

MULTICORE CABLES
10 CORE CABLE 10 x 7/76 (10 colours) P.V.C.
 O.D. 7m.m. 10m—£2.50m—£8.50. 100m—£16. P&P 2p per metre
10 PAIR RIBBON CABLE
 10 x 7/76 twisted pairs, p.v.c.
 Forming 18 m.m. wide loom. Polarised.
 10m. — £3; 50m — £13.50; 100m — £25.
16 PAIR RIBBON CABLE 16x2 core P.V.C.
 Double sheathed forming 2in wide strip
 10m—£3; 50m—£13.50; 100m—£25. P&P 2p per metre.
18 CORE SCREENED OVERALL, black p.v.c. outer.
 18 x 7/76 colour coded o.d. 7 m.m.
 10m — £4; 50m — £30; 100m — £50. P&P 2p/metre.
E.H.T. MODULES (resin encapsulated, in metal box)
 i/p 240x. 50hz. o/p 13.7 kv. @ 7 watts (150x95x72m.m.) £10 P.P. £1.
P.C. EDGE CONNECTORS
 32 way (.1 pitch) finished end 49p P&P 10p
 56 way (.1 pitch) cuttable 65p P&P 15p
 64 way (.1 pitch) cuttable 75p P&P 15p
 Mounting pillars for 56/64 way 15p per pair.
H.D. THYRISTORS on deep finned heat sink.
 65 amp @ 200 p.i.v. £3. P&P 50p.
'DRYFIT' RE-CHARGEABLE BATTERIES (Lead/Acid)
 Ex. Equip. Good condition, tested.
 6v @ 2.6 A.H. £2.50 P&P 50p
 6v @ 6 A.H. £3.50 P&P 75p
 6v @ 7.5 A.H. £5.00 P&P 75p
STEP-DOWN TRANSFORMERS. Double wound.
 Input 200/240v. Output 115v @ 20 amps.
 Fused output. £22.50. P&P £2.50.

J. B. PATTRICK
 191/193 London Road
 Romford, Essex RM7 9DJ
 Romford 44473

NEW Modern home study courses in electronics.

Complete Self-study training in:-

- 1) Basic practical electronics - circuit diagram masters - building oscilloscope and other test gear.
- 2) Training for Radio Amateur Licence.
- 3) Training for City & Guilds and other professional examinations.
 - a) Servicing and maintenance of Radio, T.V. and other electronic equipment.
 - b) Digital electronic and Computer technology.

Free! Brochure, without obligation to:- WWW/9
British National Radio & Electronic School P.O. Box 156, Jersey, Channel Islands

NAME _____

ADDRESS _____

(Block caps please).

Specialists in electronic training.
 Established over 40 years.

WW — 087 FOR FURTHER DETAILS

practical up-to-date SAMS BOOKS for radio enthusiasts

William I. Orr

RADIO HANDBOOK 21st Edition

This new edition of William Orr's famous communications handbook has been thoroughly revised. Among the new material in the twenty-first edition is a greatly enlarged section on semiconductors and IC circuit design.

£12.70 \$26.35 1,136 pages hardback 672-24034-3

REFERENCE DATA FOR RADIO ENGINEERS 6th Edition

A favourite with radio engineers since the first edition, the sixth edition of this comprehensive book contains three new chapters on active filter design, optoelectronics and optical communications.

£19.50 \$40.50 1,344 pages hardback 672-21218-8

Prices are correct at the time of going to press but may be subject to change.

Book orders and enquiries These titles are available from your usual bookseller. In cases of difficulty and for further information please contact the Marketing Services Department at the address below.

Prentice/Hall  International

66 Wood Lane End, Hemel Hempstead, Hertfordshire, England

RECHARGEABLE BATTERIES

TRADE ENQUIRIES WELCOME

Full range available to replace 1.5 volt dry cells and 9 volt PP type batteries, SAE for lists and prices. £1.25 for booklet. "Nickel Cadmium Power," plus catalogue.

Write or call at:

SANDWELL PLANT LTD.

2 Union Drive, Boldmere

Sutton Coldfield, West Midlands 021-354 9764

See full range at TLC, 32 Craven street, Charing Cross, London WC2.

WW — 043 FOR FURTHER DETAILS

SINCLAIR PRODUCTS. New 10MHz scope pos. PFM200 £52.69, case £3.40, adaptor £3.40, connector kit £11.27. Microvision TV UK model £91.44, mains adaptor £6.86, PDM35 £29.76, mains adaptor £3.40, case £3.40, DM350 £71.82, DM450 £102.17, DM235 £52.66, rechargeable batts £7.98, mains adaptor £3.94, case £9. Enterprise prog calculator with accessories £23.37.
COMPUTER GAMES Star Chess £62, Chess Champion 6 £84, Chess Challenger 7 £91, Chess Challenger 10 £152.80, Voice Challenger pos Checker Challenger 2 £46, Checker Challenger 4 £88, Atari video computer £147, cartridges £14.32.
COMPONENTS 1N4148 1.4p, 1N4002 3.1p, 741 18p, bc182b, bc183b, bc184b, bc212b, bc213b, bc214c 5p, resistors ¼W 5% E12 10R to 10M 1p, 0.8p for 50+ of one value, 18V electrolytics. 5/1/2/5/10/22uf 5p, 100uf 6p, 1000uf 10p, 1 lb FeCl £1.20, dalo pen 84p, 40 sq ins pcb 64p, polystyrene capacitors E12 63V 10 to 1000p 3p, 1n2 to 10n 4p, ceramic capacitors 50V E5 22pf to 47n 2p, zeners 400mW E24 2v7 to 33v 7p, preset pots submin 0.1W 100 to 4M7 7.2p.
TV GAMES AY-3-8500 + kit £9.53. Rifle kit £5.27. AY-3-8610 + kit £16.51. Stunt cycle chip + kit £16.72. AY-3-8603 chip £9.48.
TRANSFORMERS 6-0-6V 100ma 76p, 1½a £2.50, 6-3V 1½a £2.01, 9-9V 75ma 8p, 1a £2.12, 2a £2.77, 12-0-12V 100ma 82p, 1a £2.65.
IC AUDIO AMPS with pcb. JC12 6W £2.08. JC20 10W £3.14.

BATTERY ELIMINATORS 3-way type 7/7½/9V 300 ma £3.14, 100ma radio type with press-studs 9V £3.57, 9V+9V £4.79, Car converter 12v input, output 4½/6/7½/9V 800 ma £2.86.
BATTERY ELIMINATOR KITS 100ma radio types with press-studs 4½v £1.49, 6v £1.49, 9v £1.49, 4½V+4½v £1.92, 6+6v £1.92, 9+9v £1.92. Stabilised 8-way types 3/4½/6/7/4/9/12/15/18v 100ma 2-98, 1Amp £6.81, stabilised power kits 2-18v 100ma £2.98, 2-30v 1A £7.40, 2-30v 2A £11.86, 12v car converter 6/7½/9v 1A £1.44.
T-DEC AND CSC READBOARDS s-dec £4.05, 1-dec £4.28, u-dec £4.69, u-dec £7.16, 16 di adaptor £2.31, exp4b £2.64, exp300 £6.61, exp350 £3.62, exp325 £1.84.
BI-PAK AUDIO MODULES s450 £24.03, AL60 £4.97, PA100 £17.33, spm80 £4.57, bmt80 £6.08, stereo 30 £20.57, AL30 £4.04, PA12 £7.77, PS12 £1.42, MA60 £36.23.

SWANLEY ELECTRONICS

Dept. WW, 32 Goldsai Rd., Swanley, Kent.

Post 30p extra. Prices include VAT. Official and overseas orders welcome. Lists 20p post free.


YOUR LAST CHANCE to obtain Wireless World Circards.

We still have some copies of the original Wireless

World circuit cards, even though the companion bound volumes **Circuit Designs 1 & 2*** are out of print. Fill the gaps in your circuit files with these sets of 5 × 8in. (127 × 204mm) cards in plastic wallets — and at 1976 prices!

These unique circuit cards normally contain descriptions and performance data of 10 tested circuits, together with ideas for modifying them to suit special needs.

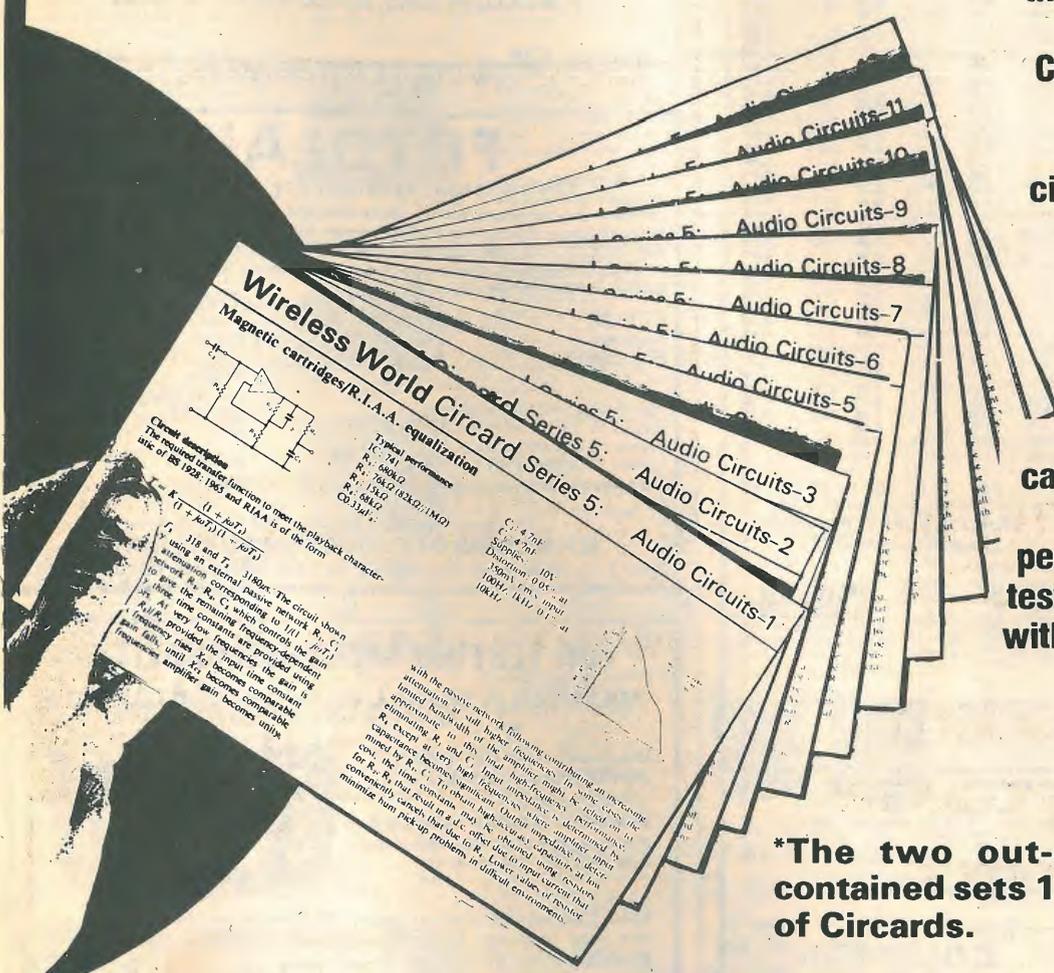***The two out-of-print volumes contained sets 1 to 10 and 11 to 20 of Circards.**



- Micropower circuits
- 12 Wideband amplifiers
- 14 Digital counters
- 16 Current differencing amplifiers-signal processing
- 18 Current differencing amplifiers — measurement and detection
- 25 RC oscillators — 1
- 27 Linear cmos — 1
- 29 Analogue multipliers
- 31 Digital multipliers
- 32 Transistor arrays
- 33 Differential and bridge amplifiers
- 34 Analogue gate applications — 1
- 35 Analogue gate applications — 2
- 11 Basic logic gates
- 13 Alarm circuits
- 15 Pulse modulators
- 17 Current differencing amplifiers-signal generation
- 19 Monostable circuits
- 20 Transistor pairs
- 21 Voltage-to-frequency converters
- 22 Amplitude modulation and detection
- 23 Reference circuits
- 24 Voltage regulators
- 26 RC oscillators
- 28 Linear cmos
- 30 Rms/log/power laws

- 1 Basic active filters
- 2 Switching circuits, comparators and Schmitts
- 3 Waveform generators
- 4 AC measurements
- 5 Audio circuits
- 6 Constant current circuits
- 7 Power amplifiers
- 8 Astable circuits
- 9 Optoelectronics
- 10

To: General Sales Department, IPC Electrical-Electronic Press Ltd., Room CP34, Dorset House, Stamford Street, London SE1 9LU.

Please send me the following sets of Circards:

£2 each, £18 for ten, inclusive.

I enclose cheque/money order for £
Make cheques payable to IPC Business Press Ltd.

Name

Address

Company registered in England. Registered address, Dorset House, Stamford Street, SE1 9LU, England. Registered Number 677128

VALVES			VALVES VAT IS INCLUDED		
£			Minimum Order £1.00		
A1065	1.40	EL82	0.70	PY80	0.70
A2293	8.50	EL84	0.90	PY81/800	0.85
A2900	8.00	EL86	1.05	PY82	0.55
AR8	0.70	EL90	1.45	PY83	0.60
AR3	0.70	EL91	1.80	PY88	0.75
ATP4	0.80	EL95	0.80	PY500	1.50
812H	3.35	EL504	0.90	PY809	6.45
CY31	1.15	EL802	0.70	PY807	1.70
DAF96	0.70	EL821	5.05	QV03-10	2.80
DET22	21.95	EL822	5.05	QV03-12	2.80
DF96	0.70	EM31	0.85	QV06-40A	6AK8
DK96	1.05	EM80	0.70		6AL5
DH76	1.00	EM81	0.70	QV03-12	2.80
DL92	0.80	EM84	0.45	SC1/400	4.50
DY86/87	0.65	EM87	1.15	SC1/600	4.50
DY802	0.65	EY51	0.55	SP61	0.95
E55L	8.45	EY81	0.55	TT21	12.65
EB8CC/01	1.50	EY86/87	0.65	U25	1.15
E180CC	1.50	EY88	0.65	U26	0.95
E190F	6.75	Z80	0.55	Z27	0.75
E182CC	3.95	Z81	0.70	U191	0.85
EA76	2.25	GY501	1.05	U281	0.60
EABC80	0.60	GZ32	0.75	U301	0.60
EB91	0.45	GZ33	3.95	U600	5.10
EB33	1.15	GZ37	2.25	U801	0.90
EBF80	0.60	GZ37	2.25	U8C80	0.70
EBF83	0.60	KT66	5.75	UAF42	0.85
EBF89	0.60	KT88	7.20	UBF80	0.65
EC52	0.45	MH4	1.15	UBF89	0.60
EC831	0.65	ML6	1.15	UBL1	1.15
EC832	0.60	NL24	10.15	UB21	0.85
EC833	0.65	OA2	0.85	UCC84	0.70
EC834	0.50	OB2	0.70	UCC85	0.75
EC885	0.60	PABC80	0.60	UCF80	0.90
EC886	1.40	PC85	0.60	UCH81	0.70
EC888	0.70	PC86	0.95	UCL82	0.85
ECC189	0.90	PC88	0.85	UF41	0.90
ECF80	0.80	PC900	1.40	U60	0.55
ECF82	0.55	PCC84	0.75	UF85	0.60
ECF801	0.90	PCC89	0.65	UL41	0.85
ECH34	1.15	PC3189	0.75	ULB4	0.85
ECH35	1.70	PCF80	0.90	UM80	0.70
ECH42	0.90	PCF82	0.45	UM84	0.70
ECH81	0.55	PCF84	0.75	UY82	0.55
ECH84	1.15	PCF86	0.75	UY85	0.60
ECL80	0.70	PCF200	1.05	VR105/30	2.05
ECL82	0.65	PCF201	1.05	VR150/30	1.40
ECL83	1.40	PCF801	1.15	Z66	1.05
ECL85	0.75	PCF802	0.75	X61M	1.70
ECL86	0.65	PCF805	2.05	Z800U	3.40
EF37A	1.80	PCF806	0.95	Z801U	3.90
EF39	3.30	PCF808	2.05	Z900T	2.50
EF40	0.80	PCH200	0.90	1A3	0.70
EF41	0.85	PCL81	0.70	1L4	0.50
EF80	0.45	PCL82	0.75	1R5	0.85
EF83	1.70	PCB84	0.80	1S4	0.45
EF85	0.45	PCL86	0.80	1S5	0.45
EF86	0.55	PCL805/85	1.74	1T4	0.45
EF91	0.65		0.85	1U4	0.80
EF92	0.75	PD500	3.65	1X28	1.25
EF95	0.85	PL30	2.50	2B21	0.65
EF183	0.65	PL36	0.90	2K25	12.95
EF184	1.80	PL81	0.85	2X2	0.90
EF804	2.25	PL82	0.60	3A4	0.70
FFL200	0.85	PL83	0.60	3D6	0.50
EH90	0.70	PL84	0.75	3D21	23.00
EL32	1.00	PL85	1.60	3S4	0.50
EL34	2.95	PL508	1.50	3V4	0.95
EL37	3.40	PL509	3.65	5B/254M	8.45
EL38	4.50	PL802	3.15	5B/255M	8.45
EL41	0.90	PL80	3.40	5B/258M	8.45
EL81	1.20	PY33	0.70	5R4GY	1.25
5U4G	1.05	6L6GT	1.75	20P5	1.15
6V4G	0.75	6L7G	0.75	25L6GT	0.90
5Y3GT	0.75	6L8	0.70	25Z4G	0.70
5Z3	1.15	6L20	0.70	30C15	1.15
5Z4G	0.80	607G	0.90	30C17	1.25
5Z4GT	0.85	65A7	0.65	30C18	
6A87	0.70	65G7	0.85	30F5	1.15
6A87	1.70	65J7	0.80	see PCF805	
6A87	0.60	65J7GT	0.60	30F12	1.35
6AK5	0.65	65K7	0.70	30FL2	1.60
6AK8	0.60	65L7GT	0.85	30FL14	2.05
6AL5	0.45	65N7GT	0.85	30L15	1.15
6AL5W	0.80	65Q7	0.85	30L17	1.15
6AM5	1.80	6V8GT	0.90	30P12	1.15
6AM6	0.75	6X4	0.70	30P11	1.15
6AN8	0.95	6X5GT	0.65	30P13	1.25
6AQ5	1.05	6Y6G	1.10	30P14	1.25
6AQ5W	1.45	6Z4	0.75	35L6GT	1.15
6AS6	0.90	6-30L2	1.95	35W4	0.80
6AT6	0.85	7B7	0.90	35Z4GT	0.80
6AU6	0.45	7V4	0.90	50C5	1.35
6AV6	0.60	9D2	0.70	50C6G	1.35
6AX4GT	0.90	9D6	0.85	75	0.90
6AX5GT	1.16	10C2	0.70	75C1	1.15
6B7	0.85	10F18	0.70	76	0.90
6BA6	0.45	10P13	0.70	78	0.90
6BE6	0.60	11E2	12.40	80	0.85
6BG6G	1.15	12A6	0.70	85A2	0.85
6BJ6	1.25	12AT6	0.55	723A/8	2.70
6BQ7A	0.70	12AT7	0.65	803	14.40
6BQ7	2.60	12AU7	0.60	805	0.75
6BW6	0.70	12AV6	0.80	807	20.25
6BW7	1.15	12AX7	0.60	813	1.15
6C4	0.70	12BA6	0.60	829B	11.85
6C6	0.70	12BE6	1.25	832A	7.35
6CH6	5.05	12BM7	0.70	866A	5.10
6CL6	1.70	12CB	0.65	931A	3.15
6CY5	1.00	12E1	4.80	954	6.75
6D6	0.85	12K5GT	0.90	955	0.60
6E8A	0.90	12K7GT	0.70	956	0.65
6E8B	0.85	12K8GT	0.80	957	0.60
6F8G	0.75	12Q7GT	0.60	1625	1.00
6F12	0.90	12SC7	0.65	1629	1.15
6F14	0.95	12SH7	0.80	2051	0.80
6F15	1.15	12SJ7	0.65	5763	1.15
6F17	1.15	12SQ7	0.65	5842	2.25
6F24	1.00	12Y4	0.45	5933	7.30
6F33	4.75	13D6	0.70	6057	3.45
6H6	1.05	14S7	1.15	6080	0.95
6J4WA	2.00	19A05	0.85	6064	0.80
6J4	1.35	19G3	11.25	6065	0.95
6J5GT	0.85	19G6	6.75	6067	1.35
6J6	0.60	19H5	19.15	6080	4.80
6J7	0.85	20D1	0.70	6146	4.95
6J7G	0.50	20F2	0.70	6146B	5.10
6K7	0.80	20L1	1.15	6360	2.25
6K7G	0.45	20P1	0.45		
6K8GT	0.65	20P3	0.60		
6L6M	2.15	20P4	1.25		

BRITISH MOTOROLA 6800-6809 COMPUTER SYSTEMS

6800S, the world's most powerful 6800/6809 computer kit. Basic kit has 16K ram, Mikbug type monitor, cuts + high-speed tape interface, power supply, full Query keyboard, mem. mapped VDU with u/I case, graphics, scrolling, spare ACIA and PIA. Addon 16K ram kit, disc available. All on a single board. For **£275.00**.

Mini 6800 System. A very versatile system based on several 100mm x 275mm PCBs. The basic kit contains the CPU + cuts card and VDU card and costs **£127.50**. Add to this: 8K RAM + 5EPROM card + calculator (MM57109) card + Errom programmer card + multifunction input-output card and you have a do anything system. Microcase: our own big ABS case to house a 6800S or Mini. **£29.00**.

All prices exclude VAT and postage. Send stamped addressed envelope, please, for leaflets.

HEWART MICROELECTRONICS

95 BLAKELOW ROAD, MACCLESFIELD, CHESHIRE

WW — 100 FOR FURTHER DETAILS

FOTOLAK

POSITIVE LIGHT SENSITIVE AEROSOL LAQUER

Enables YOU to produce perfect printed circuits in minutes!
Method: Spray cleaned board with lacquer. When dry, place positive master of required circuit on now sensitized surface. Expose to daylight, develop and etc.. Any number of exact copies can of course be made from one master. Widely used in industry for prototype work.

FOTOLAK	£1.50	Pre-coated 1/16" Fibre-glass board	
Developer	30p	204mm x 114mm	£1.50
Ferric Chloride	40p	204mm x 228mm	£3.00
		408mm x 228mm	£6.00
		467mm x 305mm	£9.00

Plain Copper-clad Fibre-glass.		Single-sided	Double-sided
Approx. 3.18mm thick sq. ft.		£1.25	£1.50
Approx. 2.00mm thick sq. ft.		£2.00	£2.25
Approx. 1.00mm thick sq. ft.		£1.50	£1.75
Clear Acetate Sheet for making master, 260mm x 260mm			12p

Postage and packing 65p per order. VAT 15% on total


G. F. MILWARD ELECTRONIC COMPONENTS LIMITED

369 Alum Rock Road, Birmingham B8 3DR. Telephone: 021-327 2339

FOR TESTING AMPLIFIER QUALITY

YOU NEED A SIGNAL WITHOUT DISTORTION

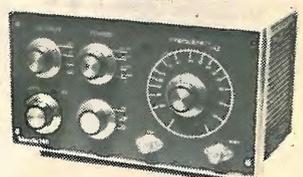We do not claim our Model A0146 Signal Generator is distortionless. However it is so low (.0015%) that only the most sophisticated Analyser can detect it.



Spec. Sine wave distortion below .0015% output lv rms. Freq. coverage 10hz-100kHz Coarse and fine attenuation into 600 ohms. Square wave alternative.

£36.00
Tax extra 15%
P.P. £1.50.

TELERADIO ELECTRONICS

325 FORE STREET, EDMONTON, LONDON N9 0PE
01-807 3719 Closed Thursdays. S.A.E. for lists.

WW — 105 FOR FURTHER DETAILS

WE CAN ACT AS YOUR CONSULTANTS for MICRO COMPUTERS & TEST EQUIPMENT

TELEROMETER MRA3 DISTANCE MEASURERS
LOW RESISTANCE HEADPHONES TYPE CLB
£1.50. 40p postage. VAT 12%.

WANTED AR 88 RECEIVERS

Phone for our exceptionally high offer.

36' AERIAL MASTS consisting of 6 sections 6' 8" x 2 1/4" dia. Complete with all accessories to erect and install.

FOR EXPORT ONLY
Mullard C11. High power installation, 1000W. Technical details and prices available on request.

COLOMOR (ELECTRONICS LTD.)

170 Goldhawk Rd., London W.12
Tel. 01-743 0899

Open Monday to Friday
9-12.30, 1.30-5.30 p.m.

POSTAGE: £1-£2 20p; £2-£3 30p; £3-£5 40p; £5-£10 60p; over £10 free.

VIDECON TUBE TYPE P863B

English Electric — £20

SPECIAL VALVES VALVES AND TRANSISTORS

Telephone enquiries for valves, transistors, etc., retail 749 3934; trade and export 743 0899.

HIGH VACUUM VARIABLE CAPACITORS — ceramic envelopes — UC 1000A/20/150 = VMMHC 1000 60-1000µF, 20kv-150A RF max = 27MHz.

TEST SET FT2 for testing Transceivers A40, A41, A42 and CPRC26.

UNIVERSAL WIRELESS TRAINING SET No 1 Mk 2
YA 8316 to train 32 operators simultaneously on key and phone. Complete installation consists of 3 kits packed in 3 special transit cases.

HARNESS "A" & "B" CONTROL UNITS "A" "R" "J1" "J2," Microphones No 5, 6, 7 connectors, frames, carrier sets etc.

HYDRATIONS GLASS ENVELOPE. MIL 5948/1754. Us 25KV. TA 1.25A P-12.5M.

IGNITION BK 484/5552A. Max 1200 KVA. Anode Current 140A.

PPM2: PEAK PROGRAMME METERS

- Approved by broadcasting authorities in the U.K. and overseas for critical programme monitoring.
- Reviewed *Studio Sound* September, 1976. Meets IEC268-10A, draft BS5428-9.
- Accurate law at and between all PPM marks with minimal preset adjustment. Marginal adjustment is retained to allow compensation for the tolerance in scale markings between meter manufacturers and different meters from the same maker.
- Decay matching of all boards allows use with twin movements without pairing.
- Flat frequency response at all PPM marks and also below minimum calibration point.
- Gold plated connector and floating input protected against mains or static voltages on the signal lines. Supply input protected against reverse polarity.
- Close tolerance components with excellent temperature and ageing characteristics used throughout.
- Soak tested bars. Ernest Turner meter movements 642, 643 and TWIN flush mounting adaptors and illumination kits from stock. Scalings available: 7, IEC268 10A Type 11a: —12T/TEST/+12 Type 11b used by EBU and conforming to CCITT recommendation N15 (1972) but not recommended by us except for EBU and measuring instruments.

Stereo Disc Amplifier 2 ★ 10 Outlet Distribution Amplifier 2 ★ Stabilizer ★ Peak Deviation Meter ★ Chart Recorders.

SURREY ELECTRONICS

The Forge, Lucks Green, Cranleigh, Surrey GU6 7BG. Tel: (04866) 5887

SIGHT for sore eyes



STICKIES are printed self-adhesive labels that stick to the top of ICs. They turn a board-full of ICs into a working circuit diagram! See at a glance where to place your soldering iron or test probe. Use STICKIES for building and de-bugging prototypes, fault-finding, experimenting, teaching — even designing PCB layouts.

STICKIES come in handy-size packs for 7400- or 4000-series ICs. Each pack contains a sensible mix of more than 60 different IC types.

120-label packs 80p.
480-label packs £2.80, 2-10 packs £2.50 each, 11+ £2.20 each.
Prices include 15% VAT and first-class postage.
Please state whether TTL or CMOS required.
Official orders welcome.

Let others suffer the sore eyes — try a pack of STICKIES and see the difference.

For your STICKIES by return of post, contact **CONCEPT ELECTRONICS**, 8 Bayham Road, Sevenoaks, Kent, TN13 3XA (0293 514110).

WW — 051 FOR FURTHER DETAILS

U.K. RETURN OF POST MAIL ORDER SERVICE, ALSO WORLDWIDE EXPORT SERVICE

BSR DE LUXE AUTOCHANGER

Plays 12", 10" or 7" records, Auto or Manual. A high quality unit backed by BSR reliability. Stereo Ceramic Cartridge. AC 200/250V. Size 13½-11¼in. 3 speeds. Above motor board 3¾in. Below motor board 2½in. with Ceramic Stereo cartridge.



£20.00 Post £1.60

HEAVY METAL PLINTHS ONLY

Cut out for most BSR or Garrard decks. Silver grey finish.

Post £1.60

Model "A" Size 14½ x 12½ x 3in.

£3.50

Model "B" Size 16 x 13¾ x 3in.

£4.50

TINTED PLASTIC COVERS ONLY

Sizes: 14½ x 12½ x 4¼in. **£3.50**

15¼ x 13½ x 4in. **£4.18** 13¼ x 4in. **£6.**

17¼ x 9½ x 3½in. **£3.18** 12½ x 3in. **£6.**

14½ x 14¼ x 2½in. Rosewood sides **£4.**

Post £1.60

BSR SINGLE PLAYER

Ideal replacement or disco deck with cueing device and stereo ceramic cartridge. 3 speeds. Large turntable, modern design

£21 Post £1.60



TWO-SPEED BUDGET MODEL £15.

BSR P182 3 speeds flared aluminium turntable "S" shape arm, cueing device, ceramic cartridge **£24.** Post £1.60 BSR MP60/P128 Stereo Ceramic, balanced arm, cueing device. Bias compensator **£26.** Magnetic **£5** extra.

GARRARD HI-FI AUTO CHANGER

Model 2025 3-speed stereo cartridge. Cueing devices Post £1.60



B.S.R. P163 BELT DRIVE QUALITY DECK

Manual or automatic play. Two speeds. Precision balanced arm. Slide in head, cueing device. Bargain price




£30 Post £1.60

Suitable magnetic cartridge **£6.50.**

ELAC HI-FI SPEAKER 8in. TWIN CONE

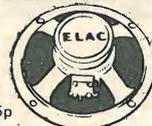Large ceramic magnet. 50-16,000 c/s. Bass resonance 40 c/s. 8 ohm impedance. 10 watts. RMS. **£5.95** Post 75p 20 watt woofer bass unit only **£7.95** Post 75p



LOW VOLTAGE POWER PACK for MODELS

Ready made. Famous make. Will supply 10 volts D.C. at 400mA. With terminals and mains lead. **£2.75** Post 50p

VOLUME CONTROLS

5KΩ to 2MΩ. LOG or LIN. L/S 35p. DP 60p. Stereo L/S 85p. DP £1. Edge Pot 5K. SP 45p.

80 Ohm Coax

FRINGE LOW LOSS 15p yd. PLUGS 10p. SOCKETS 10p. LINE SOCKETS 25p. OUTLET BOXES 80p. 300 ohm FEEDER 5p yd.

EMI 13½ x 8in. LOUDSPEAKERS

With tweeter and crossover. 10 watt. 3 or 8 ohm.

Bass woofer only 8 ohm. 15 watt.

£9.95 Post 75p

£10.95 Post 75p

Bass woofer only 15 ohm. 20 watt.

£11.95 Post 75p

Suitable Bookshelf Cabinet

Teak finish. For EMI 13 x 8 speakers. Size 16 x 11 x 8 inches approximately.

£8.50 Post £1.60

THE "INSTANT" BULK TAPE ERASER

Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S.A.E.

Will also demagnetise small tools

£6

Head Demagnetiser only **£5.00** Post 50p



RELAYS. 12V DC 95p. 6V DC 85p. 240V AC 95p.

BLANK ALUMINIUM CHASSIS. 6 x 4-95p; 8 x 6-£1.40; 10 x 7-£1.55; 12 x 8-£1.70; 14 x 9-£1.90; 16 x 6-£1.85; 16 x 10-£2.20. ANGLE ALI. 6 x ¾ x ¼in-20p.

ALUMINIUM PANELS. 6 x 4-24p; 8 x 6-38p; 14 x 3-40p; 10 x 7-54p; 12 x 8-70p; 12 x 5-44p; 16 x 6-70p; 14 x 9-94p; 12 x 12-£1; 16 x 10-£1.16.

PLASTIC AND ALI BOXES IN STOCK. MANY SIZES

VARICAP FM TUNER HEAD with circuit & connections. Some technical knowledge required **£4.95.**

TAG STRIP 28-way 12p.

TAPE OSCILLATOR COIL. Valve type. 35p.

BRIDGE RECTIFIER 200V PIV ½ amp 50p. 8 amp **£2.50.**

TOGGLE SWITCHES SP 30p. DPST 40p. DPDT 50p.

MANY OTHER TOGGLES IN STOCK. Please enquire.

PICK-UP CARTRIDGES ACOS. GP91 **£2.00.** GP94 **£2.50.**

SONOTONE 9TAHC Diamond **£3.75.** V100 Magnetic **£6.50.**

WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 15p

CASSETTE MOTOR. 6 volt **£1.00.**

CASSETTE MECHANISM. Mono heads, no motor **£3.00.**

MAINS OPERATED SOLID STATE AM/FM STEREO TUNER



200/240V AC Mains. F.M./A.M. Stereo Tuner. Covering M.W., A.M. 540-1605KHz V.H.F., F.M. 88-108MHz. Ferrite rod aerial for M.W. Full AFC and AGC on A.M. and F.M. Stereo Beacon Indicator. Built-in Pre-amps with variable output adjustable by pre-set control. Max. o/p Voltage 600mV R.M.S. into 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 8¼in wide, 4in. high x 9½in. deep approx.

£28 Post £1.60

RCS SOUND TO LIGHT KIT Mk. 2

Kit of parts to build a 3 channel sound to light unit 1,000 watts per channel. Suitable for home or disco. Easy to build. Full instructions supplied. Cabinet **£4.50** extra. Will operate from 200MV to 100 watt signal.

£18 Post 50p

RCS "MINOR" 10 watt AMPLIFIER KIT

This kit is suitable for record players, guitars, tape playback, electronic instruments or small PA systems. Two versions available: Mono. **£12.50;** Stereo. **£20.** Post 45p. Specification 10W per channel; input 100mV; size 9½ x 3 x 2in. approx. SAE details. Full instructions supplied. AC mains powered. Input can be modified to suit guitar.

R.C.S. STEREO PRE-AMP KIT. All parts to build this pre-amp.

Inputs for high, medium or low imp per channel. With volume control and P.C. Board **£2.95** Post 35p Can be ganged to make multi-way stereo mixers

MAINS TRANSFORMERS ALL POST 75p.

250-0-250V 70mA, 6.5V, 2A	£3.45
250-0-250V 80mA, 6.3V 3.5A, 6.3V 1A	£4.80
350-0-350V 80mA, 6.3V 3.5A, 6.3V 1A	£5.80
300-0-300V 120mA, 2x6.3V 2A C.T., 5V 2A	£8.50
220V 45mA, 6.3V 2A	£1.75
HEATER TRANSFORMER 6.3V ½ amp	£2.3 amp
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs available	
2 amp, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V	£3.60
1 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£6.00
2 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£9.50
3 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£12.50
5 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£16.00

12V, 100mA	£1.30	20V, 40V, 60V, 1 amp	£4.00
12V, 750mA	£1.50	12V, 3 amp	£3.50
10-0-10V 2amp	£3.00	10V, 30V, 40V, 2 amp	£3.50
30V, 5 amp and 17V-0-17V, 2 amp	£4.00	40V, 2 amp	£3.50
0, 5, 8, 10, 16V, ½ amp	£2.50	20V, 1 amp	£3.50
9V, 3 amp	£3.50	20V-0-20V, 1 amp	£3.00
25-0-25V 2 amp	£4.50	30V-0-30V, 2 amp	£8.00
30V, 2 amp	£3.50	2 of 18V, 6 amp, each	£11.00
30V, 1½ amp	£3.30	12-0-12V, 2 amp	£3.50
		9V, ¼ amp	£1.50

AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 150W **£7.00** 250W **£8.00** 400W **£9.00** 500W **£10.00**

FULL WAVE BRIDGE CHARGER RECTIFIERS. 6 or 12V outputs, 2 amp.....75p. 4 amp.....£1.25

CHARGER TRANSFORMERS: ½ amp.....£3.50. 4 amp.....£6.50. 25p

COMPACT SPEAKERS


Teak 4 or 8 ohm

White 4 ohm only

13 x 10 x 6in. approx.

50 to 14,000 cps. 10 watts.

£16 pair Post £1.60

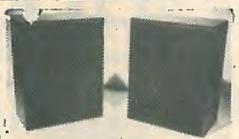

EXTENSION SPEAKERS £3.95 ea.

Globe shaped cases in high gloss mouldings of red or green, are finished with chrome frontal trim. In addition, 2½ metres of twin lead already fitted with phono plug is supplied.



Full Range Quality Frequency Response Impedance: 8 ohms Power Peak: 5 watts

LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.		
500mF 12V 15p; 25V 20p; 50V 30p; 420mF/500V £1.30.		
1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p.		
2000mF 6V 25p; 25V 42p;		
2500mF 50V 62p; 3000mF 25V 47p; 50V 65p.		
3900mF 100V £1.80. 4700mF 63V £1.20. 2700mF/76V £1.		
5000mF 35V 85p. 5600mF/76V £1.75		
HIGH VOLTAGE ELECTROLYTICS		
8/350V 22p	8+8/450V 50p	50+50/300V 50p
16/350V 30p	8+16/450V 50p	32+32/450V 75p
32/500V 75p	16+16/450V 50p	100+100/275V 65p
50/350V 50p	32+32/350V 50p	150+200/275V 70p

MANY OTHER ELECTROLYTICS IN STOCK

SHORT WAVE 100pf air spaced gangable tuner, 95p.

TRIMMERS 10pF, 30pF, 50pF, 5p. 100pF, 150pF, 15p.

CERAMIC, 1pF to 0.01mF, 5p. Silver Mica 2 to 5000pF, 5p.

PAPER 350V-0.1 7p; 0.5 13p; 1mF 150V 20p; 2mF 150V 20p; 500V-0.001 to 0.05 12p; 0.1 15p; 0.25 25p; 0.47 35p.

MICRO SWITCH SINGLE POLE CHANGEOVER 20p.

SUB-MIN MICRO SWITCH, 25p. Single pole change over.

TWIN GANG, 385 + 385pF 80p; 500pF slow motion 75p.

365 + 365 + 25 + 25pF, Slow motion drive 85p. 120pF 50p.

TRANSISTOR TWIN GANG, 50p.

NEON PANEL INDICATORS 250V. Amber or red 30p.

ILLUMINATED ROCKER SWITCH, single pole. Red 65p.

RESISTORS. 10Ω to 10M. ¼W, ½W, 1W. 20% 2p; 2W, 10p.

HIGH stability. ¼W 2% 10Ω to 1 meg., 12p.

5p. Ditto 5%. Preferred values 10 ohms to 10 meg., 5p.

ELECTRO MAGNETIC PENDULUM MECHANISM 95p


Post 30p. 1.5V DC operation over 300 hours continuous on SP2 battery, fully adjustable swing and speed. Ideal displays, teaching electro magnetism or metronome, strobe, etc.

BAKER SUPERB £24

12in 25 watt

Post £1.60

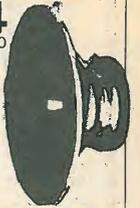Quality loudspeaker, low cone resonance ensures clear reproduction of the deepest bass. Special copper drive and concentric tweeter cone. Full range reproduction with remarkable efficiency in the upper register. Bass resonance 25 c/s Flux Density 16,500 gauss Useful response 8 or 16 ohms models 20-17,000 c/s



BAKER "BIG-SOUND" SPEAKERS. Post £1.60

Group 100	Disco 100	Group 50/15
12 inch 100 watt	12 inch 100 watt	15 inch 75 watt
£29	£29	£35
8 or 16 ohm	8 or 16 ohm	8 or 16 ohm

BAKER LOUDSPEAKER, 12 INCH. 60 WATT. GROUP 50/12, 4 OR 8 OR 16 OHM HIGH POWER.

FULL RANGE PROFESSIONAL QUALITY. RESPONSE 30-16,000 CPS. MASSIVE CERAMIC MAGNET WITH ALUMINIUM PRESENCE CENTRE DOME. **£23** Post £1.60

TEAK VENEERED HI-FI SPEAKER CABINETS

For 13x8in. or 8in. speaker **£9.50** Post £1.00 For 6½in. speaker and tweeter **£8.50** Post 75p

Many other cabinets in stock. Phone your requirements.

SPEAKER COVERING MATERIALS. Samples Large S.A.E.

LOUDSPEAKER CABINET WADDING 18in wide 20p ft.

R.C.S. 100 watt VALVE AMPLIFIER CHASSIS



Four inputs. Four way mixing, master volume, treble and bass controls. Suits all speakers. This professional quality amplifier chassis is suitable for all groups, disco, PA, where high quality power is required. 5 speaker outputs. AC mains operated. Slave output socket. Produced by demand for a quality valve amplifier. 100V line output to order £10 extra. Send for leaflet. Suitable carrying cab £21 Price **£105** carr. £6.00

GOODMANS TWIN AXIOM 8 inch dual cone loudspeaker. 8 ohm, 15 watt hi-fi unit £10.50.

CROSSOVERS. TWO-WAY 3000 c/s 3 or 8 or 15 ohm £1.90. 3-way 950 cps/3000 cps **£2.20.**

LOUDSPEAKERS PM 3 OHM 7x4in. £1.50; 6½in., £1.95; 8x5in., £1.90; 8in., £2.50.

SPECIAL OFFER: 8 ohm, 2¼in., 2¼in., 35 ohm, 3in., 25 ohm, 2½in., 3in., 5x3in., 7x4in. 8 ohm, 2½in., 3in., 3½in., 5in., 15 ohm, 3½in., 6x4in., 7x4in., 5x3in., 3 ohm, 2¼in., 2½in., 3½in., 5in. dia. £1.50 each.

PHILIPS LOUDSPEAKER, 8in., 4 ohms, 4 watts, £2.50.

RICHARD ALLAN TWIN CONE LOUDSPEAKERS 8in. diameter 4W £2.50. 10in. diameter 5W £3.50; 12in. diameter 6W £4.50. 3/8/15 ohms, please state.

MOTOROLA PIEZO ELECTRIC HORN TWEETER. £6.50

Handles up to 100 watts. No crossover required.

BLACK PLASTIC CONSTRUCTION BOX with brushed aluminium fascia. Sturdy job. Size 6¼ x 4¾ x 2in. **£1.50**

BAKER 150 WATT PROFESSIONAL MIXER AMPLIFIER



All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 4 8/16 ohms. A.C. Mains. Separate treble and bass controls. Master volume control. 100 watt line model **£99** £1.60 carr. **£85**

BAKER 50 WATT AMPLIFIER



Superior quality ideal for Halls/PA systems, Disco's and Groups. Two inputs with Mixer Volume Controls. Master Bass, Treble and Gain Controls. 50 watts RMS. Three loudspeaker outlets 4, 8, 16 ohm. AC 240V (120V available). Blue wording on black cabinet. **£63** Post £1.60

GOODMANS COMPACT 12-INCH BASS WOOFER

Standard 12in. diameter fixing with cut sides 12 x 10". 14,000 Gauss magnet. 20 watts R.M.S. 4 ohm imp. Bass resonance = 30 c.p.s. Frequency response 30-8000 c.p.s. **£9.95 each** Post £1.60



ALUMINIUM HEAT SINKS. FINNED TYPE.

Sizes 5" x 4" x 1" **95p.** 6½" x 2" x 2¼" **45p**

JACK PLUGS. Plastic 25p; Metal 30p.

JACK PLUGS Stereo Plastic 30p; Metal 35p.

JACK SOCKETS. Open 20p; Closed 25p.

JACK SOCKETS Stereo Open 25p; Closed 30p.

FREE SOCKETS - Cable end 30p.

2.5mm and 3.5mm JACK SOCKETS 15p.

2.5mm and 3.5mm JACK PLUGS 15p.

DIN TYPE CONNECTORS

Sockets 3-pin, 5-pin 10p. Free Sockets 3-pin, 5-pin 25p.

Sockets 3-pin 20p; 5-pin 25p.

PHONO PLUGS and SOCKETS ea. 10p.

Free Socket for cable end ea. 15p.

Screened Phono Plugs ea. 15p.

TV CONVERGENCE POTS


Values = 5, 7, 10, 20, 50, 100, 200, 2

Tecknowledgedgey for sale.

The Mark III FM Tuner

DIY Hi-Fi will never seem the same again. Ambit's Mark III tuner system is electrically & visually superior to all others. Some options available, but the illustrated version with reference series modules: £149.00 + £18.62 VAT

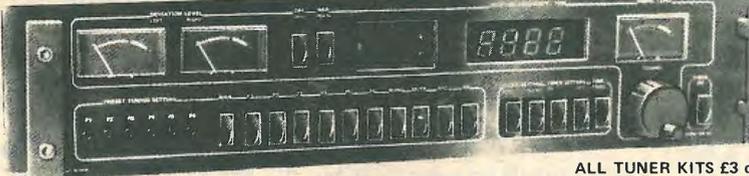With Hyperfi Series modules £185.00 + £23.12



Features of the system:

- * Precision construction & design of all parts
- * Time/frequency display
- * State of the art performance with facilities for updates, using modular plug in systems.
- * Deviation level calibrator for recording
- * All usual tuner features

PW SANDBANKS PI METAL LOCATOR

Maintaining our professional approach to home constructor kits, we offer the pulse induction 'Sandbanks'. Now with injection molded casing for greatly improved environmental sealing. £37.00+£5.55vat

VHF MONITOR RX WITH PLESSEY IC

4/9 channel version of the PW design - but using standard (fundx9) crystals, and TOYO 8 pole crystal filter with matching transformers. Coil sets from our standard range to cover bands from 40 to 200MHz. Complete module kit £31.25 +£3.90vat

MICROMARKET

OSTS overflow:	
6800P 650p	8212 230p 2102 170p
6820P 600p	8216 195p 2112 340p
6850P 275p	8224 350p 2513 754p
6810 400p	8258 478p 4027 578p
6852 365p	8251 2114 1000p
R80 630p	8255 540p +15% VAT

RADIO and AUDIO MODULES: Consistently the most advanced

FOR FM

- EF5801-3-4 series: 6 stage varicap tuning, all with oscillator output
- 5801 Dual gate MOSFET RF stages, bipolar mixer £17.45 + 2.61VAT.
- 5803 Dual gate RF/mixer stages, amplified LO out £19.75 + 2.96VAT.
- 5804 'Hyperfi' series, with internal PIN diode agc, and ultra wide range tuning system £24.95 + 3.74VAT
- EF5402 4 stage varicap tuner with TDA1062 and LO output. Uses FET/IC input. PIN agc £10.75 + 1.61VAT

FOR 30-200MHz

The EF series are available on special order to cover bands (usually approx 20% of the centre frequency) in the range described. Details in our price list.

FOR FM IFs at 10.7MHz

- 7030 single 6 pole linear phase filter IF with HA1137E10.95 + 1.64VAT
- 7130 two 6 pole linear phase filter IF with CA3189E £16.25 + 2.44VAT
- 7230 Hyperfi IF, switched bandwidth, AGC IF preamp, linear phase ceramic filters with diode switched narrow filter £24.95 + 3.74VAT

DECODERS for MPX (STEREO)

Various types, guaranteed the world's biggest and best ranges

LARSCHOLT FM TUNERS

- 7252 MOSFET front end combined with CA3089 IF £26.50 + 3.97VAT
- 7252 JFET front end, combined with IF and decoder £26.50 + 3.97VAT

FM/AM tuning synthesiser, see details elsewhere in this advertisement

ALL TUNER KITS £3 carriage

COMPONENTS FOR RADIO/COMMUNICATIONS/AUDIO/TV etc.

As usual, Ambit brings you the latest and best, a small selection of which is shown in this advertisement. The Ambit catalogues contain information on most of the devices mentioned here - and an order for the new part three will ensure you stay up with latest developments. Data photocopying service described in pricelist info.

RADIO ICs for FM vat		SL1600 series		Audio preamps vat	
CA3089E	1.94 29	SL1610	1.60 24	LM381N	1.81 27
CA3189E	2.45 37	SL1611	1.60 24	LM382N	1.65 25
HA1137W	2.20 33	SL1612	1.60 24	KB4436	2.53 38
HA11225	2.20 33	SL1613	1.89 28	KB4438	2.22 33
SN76660N	0.75 11	SL1620	2.17 33	TDA1028	3.50 53
		SL1621	2.17 33	TDA1029	3.50 53
		SL1623	2.44 37	TDA1074	3.75 56
		SL 624	3.28 49		
		SL1625	2.17 33		
		SL1626	2.44 37		
		SL1640	1.89 28		
		SL1641	1.89 28		
		SL6640	2.75 41		
		SL6690	3.20 48		
		MC3357	3.12 47		
		MC1496	1.25 19		
		NE544	1.70 25		

Current news: A PCB for the Mullard DC tone and volume control system is now available £3 + 0.45 VAT. HMOS PA modules for 60-100W - kit £14 + £2.10VAT, heatsink £4.10+0.61. FM radio control system crystals £3.75 pair inc VAT (Sept. on). MK50366N: static drive clock/timer IC £3.78 + 0.57 VAT. 12½kHz channel spacing 8 pole 10.7MHz XTAL filter by TOYO type H4402 £15.50 + £2.32VAT. A further updated pricelist is now available, and we would like to remind you that enquiries can only be answered if accompanied either by an official business letterhead, or an SAE. STOP PRESS: TOKO's new split-apart triple AM tuning diodes are in stock £2.45 + 37p VAT, (KV1215). S BL1 diode DBM 1-500MHz - £4.25+0.64p. Terms: CWO please. Account facilities for commercial customers OA. Postage 25p per order. Minimum credit invoice for account customers £10.00. Please follow instructions on VAT, which is usually shown as a separate amount. Overseas customers welcome - please allow for postage etc according to desired shipping method. Access facilities for credit purchases. Catalogues: Ambit. Part 1 45p. Part 2 50p 90p pair. TOKO Euro shortform 20p. Micrometals toroid cores 40p. All inc PP etc. Full data service described in pricelist supplements. Hours/phone: We are open from 9am -7pm for phone calls. Callers from 10am to 7pm. Administrative enquiries 9am to 4.30pm please (not Saturdays). Saturday service 10am to 6pm.

ambit international [®] 2 Gresham Road, Brentwood, Essex.

WW - 110 FOR FURTHER DETAILS

ELF 11 ELF 11



BUY A minicomputer only £79.95 + VAT for less than some TV games

ELF 11 BOARD WITH VIDEO OUTPUT

STOP reading about computer and get your "hands on" an ELF 11 and Tom Pitman's short course. ELF 11 demonstrates all the 91 commands which an RCA 1802 can execute, and the short course speedily instructs you how to use them. ELF 11's VIDEO OUTPUT makes it unique among computers selling at such a modest price. The expanded ELF 11 is perfect for engineers, business, industry, scientific and educational purposes.

SPECIFICATION

- *RCA 1802 8-bit microprocessor with 256 byte RAM - expandable to 64K bytes
- *RCA 1851 video IC to display program on TV screen via the RF Modulator
- Single Board with: Professional hex keyboard - fully decoded to eliminate the waste of memory for keyboard decoding circuits
- Load, run and memory protect switches
- 16 Registers
- Interrupt, DMA and ALU
- Stable crystal clock
- Built-in power regulator
- 5 slot plug in expansion bus (less connectors)

- * POWER SUPPLY (6.3v AC) for ELF 11 5.00
- * ELF 11 DELUXE STEEL CABINET (IBM Blue) £23.01
- * GIANT BOARD KIT System/Monitor, Interface to/cassette, TTY etc BS232, 35.00
- * 4K STATIC RAM board kits (requires expansion power supply) £69.44
- * Expansion power supply (required when adding 4K Rams) 19.00
- * ASC11 Keyboard Kits 96 printable characters, etc. 50.58
- * ASC11 D/lux steel cab (IBM Blue) 15.02
- * KLUGE prototype board (build you own circuits) 12.83
- * 86 pin Gold plated connectors (EA) 4.00
- * ELF Light pen writes/draws on TV screens 6.50
- * Video graphics board 32/64 characters by 16 lines on TV/monitor screens 69.95
- * ELF 11 Tiny basic on cassette 13.50
- * ELF 11 Bug/monitor powerful system monitor/editor 13.50
- * T PITMANS short course in programming manual (nil VAT) 4.00
- * T PITMAN short course on tony basic manual (nil VAT) 4.00
- * RCA 1802 users manual (nil VAT) 4.00
- * On cassette test editor assembler, disassembler (EA) 16.95

SAVE 10% AND BUY ALL THREE TOGETHER

All units can be supplied wired and tested
Send s.a.e. for comprehensive brochure

Add 15% VAT to all prices shown. Plus £2 P&P Over £20

Name _____
Address _____
Postmark _____
Barclaycard Access

To: NEWTRONICS
The Personal Computer Div.
of H. L. Audio Ltd.
138 Kingsland Road E2 8BY
Tel. 739 1582.

WW-101 FOR FURTHER DETAILS

YOU ARE INVITED TO THE WORLD'S FIRST PERMANENT ELECTRONICS EXHIBITION.

AND ADMISSION IS FREE.

On September the 25th the doors of the National Microprocessor and Electronics Centre will be opened to the public.

We know it will surprise you. And admission is free to all.

Beneath the historic walls of The Tower of London we have established a unique facility for engineers and buyers to examine the latest products - without any salesmen breathing down their necks!

Over the coming year we shall create comprehensive displays augmented by a regular series of single technology displays.

For example, our first features Oscilloscopes; our second, a general introduction to "Applying Microprocessors"; and then some 30+ other topics during the next twelve months.

It is our intention that each product area shall be **totally** reviewed. So that you can try out all those you are likely to consider in a single visit to a single location. (And, obviously, make comparisons on the spot.)

The World Trade Centre, which houses our own Centre, is easy to get to by train, car - or by boat (just moor at Tower Bridge!).

But we'd prefer that you completed the coupon or used our enquiry number so that we can send you full instructions, our programme for the first months of operation, and some more news about this unique service that is freely available.

Please make contact. Or else we'll have to put you next door...

**OPENING
TUESDAY 25th SEPTEMBER 1979**

Open thereafter each week day 10.00 a.m. until 4.00 p.m. with the permanent exhibition.

**First 'mini' exhibition:
OSCILLOSCOPES,**

September 25th to 27th.


**Second 'mini' exhibition:
APPLYING MICROPROCESSORS,**

October 9th to 11th.

**Third 'mini' exhibition:
MULTIMETERS,**

October 23rd to 25th.

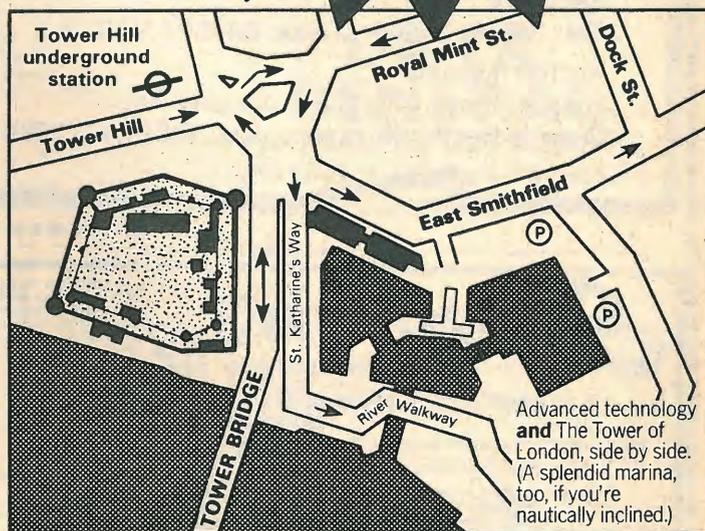All enquiries to 'The Centre,'
Telephone 01-488 2400,
Telex 884671.




Please register me as a prospective visitor to the new Centre and send me your full programme, the list of permanent exhibitors or participants, and all your latest news.

Just clip and post to 'The ME Centre,' The World Trade Centre, London, E1 9AA.

Name _____

Company _____

Address _____

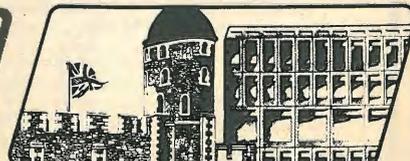

New Bear Systems



PRICES DOWN! at New Bear

Head Office: 40 Bartholomew Street, Newbury,
Berkshire
Tel: (0635) 30505 Telex: 848507 NCS
Northern Branch:
Mersey House, 220-222 Stockport Road,
Cheadle Heath, Stockport Tel: (061-491) 2290

CROMEMCO SYSTEMS

APPLE II

NORTH STAR HORIZON

Phone for Details

A wide range of Peripherals, Software and Literature

WW — 103 FOR FURTHER DETAILS

Samson's (ELECTRONICS) LTD.

9 & 10 CHAPEL ST., LONDON, N.W.1
01-723 7851 01-262 5125
ADJACENT TO EDGWARE ROAD MET. LINE STATION

PLEASE ADD 15% TO ALL ORDERS INC. CARR.

CURRENT RANGE OF NEW L.T. TRANSFORMERS OPEN TYPE TAG CONNECTIONS ALL PRIMARIES 220-240V

Type	Sec Taps	Amps	Price	Carr
1	24-30-40-48-60v	12	£31.48	£2.00
2	24-30-40-48-60v	10	£27.58	£2.00
3	24-30-40-48-60v	8	£23.48	£1.75
4	24-30-40-48-60v	5	£13.75	£1.75
5	24-30-40-48-60v	3	£10.35	£1.00
6	24-30-40-48-60v	2	£7.30	£1.00
6-8-10-12-16-18-20-24-36-40-48-60v CAN BE OBTAINED FROM THE ABOVE RANGE				
7	19-25-33-40-50v	10	£27.58	£2.00
8	19-25-33-40-50v	6	£16.75	£1.50
9	19-25-33-40-50v	3	£10.35	£1.25
10	19-25-33-40-50v	2	£7.35	£1.00
5-7-9-10-13-15-17-20-25-30-40-50v OR 25-0-25v OR 20-0-20v CAN BE OBTAINED FROM THE ABOVE RANGE				
11	12-15-20-25-30v	10	£16.45	£1.75
12	12-15-20-25-30v	5	£9.45	£1.25
13	12-15-20-25-30v	2	£5.35	£1.00
3-4-5-6-8-9-10-12-15-18-20-24-30v OR 12-0-12v OR 15-0-15v CAN BE OBTAINED FROM THE ABOVE RANGE				
14	12-24v	12v 60A, 24v 30A	£32.50	£3.00
15	12-24v	12v 30A, 24v 15A	£16.85	£2.00
16	12-24v	12v 20A, 24v 10A	£13.35	£2.00
17	12-24v	12v 10A, 24v 5A	£7.95	£1.00
18	12-24v	12v 4A, 24v 2A	£3.95	£1.00

HEAVY DUTY OP TRANSFORMERS

Type OT28EL 100 watts, 3.75v, 7.5v, 15v, 1.75K CT. 4 EL34.
2x250 m/a dc max. £13.85, pp £1.25. Type OT29EL 50 watts,
3.75v, 7.5v, 15v, 3.5K CT, rated 2x125m/a dc max. £8.75, pp
£1.

LOW POWER LT TRANSFORMERS CLAMPED OPEN FRAME. TAG CONNECTIONS. ALL PRIMARIES 240V

Type	Sec Taps	Amps	Price	Postage
1	15v twice	200 m/a ea.	£2.00	75p
2	6v twice	500m/a ea.	£2.00	75p
3	6v twice	4 amps ea.	£3.95	£1
4	6-9v twice	1 amp ea.	£2.75	75p
5	6v twice	1 1/2 amp ed.	£2.75	75p
6	12-0-12v	12VA	£2.00	75p
7	15-24-30v	2 amps	£4.75	£1
8	28v twice	1.3 amps ea.	£4.75	£1
9	15-0-15v	60VA	£3.75	£1
10	12v	4amps	£4.75	£1
11	12v	1 1/2 amps	£2.00	75p

AUTO STEPDOWN TRANSFORMERS FOR AMERICAN EQUIPMENT 240-110V 80-2250 WATTS

Fully shrouded, fitted with American two or three pin outlet and three core 240V mains lead. Send sae for latest price list. American plugs, sockets, adaptors also available. Open frame types. Tag connections by famous makes, fraction of list price, tapped 240-220-200-120-110-100V, 750 watts, £12.00 carr £2. 500 watts £8.25 carr £2. 80 watts 240-110V, wire ended £3.95 pp £1.

HEAVY DUTY ISOLATION TRANSFORMERS 240-240V OR 240-110V UPTO 15 AMPS

Large selection available, all by famous makers, fraction of list price. Please telephone us for further details.

E.H.T. TRANSFORMERS

CUMBERNAULD Pri. tapped 240-260-285-300-315-330-350-387V Sec. 2500V 0.11A. Open frame terminal board connections, fraction of maker's price £15 carr £3. PAR-MEKO potted type Pri. 220-240V Sec. 1875V 60 m/a and 500V 31 m/a £5.95 carr £2. GRESHAM open type terminal board connections Pri. 240V Sec. 2300V 10 m/a and 6.3V 1.5A £4.50 carr £1.50.

SPECIAL PURCHASE BY FAMOUS MAKERS

L.T. TRANSFORMERS IDEAL FOR UP-TO-DATE POWER SUPPLY CIRCUITS

No 1 GRESHAM Pri. 240v Sec. 43v 3 amps Fully tropicalised. Open type wire connections £3.95 pp 75p. No 2 HINCHLEY Pri. 240v Sec. 33v 5 amps and 18-0-18v 1A. Tropicalised open frame. Wire connections. Two in series will give 33-0-33v 5A and 18-0-18v 2A £3.95 each, pp 75p. No 3 FARMER Pri. 240v Sec. 30v 5A and 12v 2.2 amps. Table top connections £4.95 pp £1. No 4. AEG open type tag board connections Pri. 220-240v Sec. 10v 13.8A and 22.8v 10.5A £8.50 carr £2. No 5. 'C' core tag board connections Pri. 220-240v Sec. 27v, 3v, 3v, 1v separate windings. 10 amps each £6 carr £1.50. No 6 Pri. 120-240v Sec. 60-0-60v 10A open type cable lead connections, size 6x6x6in £19.50 carr £3. No 7 Pri. 220-240v Sec 36v 6A. Open type, tag board connections £7.50 carr £1.50, two will give 36-0-36v 6 amps Special offer for two £15 inc carriage.

L.T. TRANSFORMERS NEW SURPLUS FAMOUS MAKERS. FRACTION OF MAKER'S PRICE

Limited number £4 No 3 Pri. 115-220-240v. Sec. 9v 2A and 9v 1A open type terminal block connectors £2.50 pp £1. No 4 Pri. 230v Sec. 80v 1.1A open type tag board connections £3.00 pp £1. No 5 Pri. 120-240v Sec. 13v 3A and 15v 1A open type terminal block connections £3.00 pp £1. No 6 Pri. 240v Sec. 30v 5.5A and 12v 2.2A open type table top connections £5.75 carr £1.50. No 7 Pri. 230v sec. tapped 24-30-32v 2A potted type £3.00 pp £1. No 8 Pri. 220-240v. Sec. 6v 1A twice shrouded GPO type £2.00.

AEI 20 AMP CONTACTORS BRAND NEW BOXED FRACTION OF MAKER'S PRICE

Type	Coil voltage	Contacts	Price
0652	415vAC	3M 1B	£1.50
0655	415vAC	4M	£1.50
0648	110vAC	4M 4B	£1.50
0650	110vAC	6M 2B	£1.50
0653	110vAC	4M	£1.25
0654	110vAC	2M 2B	£1.25
0651	110vAC	3M 1B	£1.25
0649	42vAC	6M 2B	£1.50
0647	42vAC	4M 4B	£1.50

P&P 25p each

AC WKG BLOCK CAPACITORS BY FAMOUS MANUFACTURERS

MFD	Volts	Price
Q75	440vAC	50p
1	470vAC	60p
1.25	360vAC	65p
2	400vAC	75p
2.4	360vAC	75p
2.5	360vAC	75p
2.7+0.1	700vAC	£1.25
3	440vAC	£1.00
3.5	250vAC	£1.00
4	250vAC	£1.00
5	360vAC	£1.25
6	440vAC	£1.50
7.2	440vAC	£1.50
8.4	250vAC	£1.00
15	250vAC	£1.75

PP up to 2.5 MFD 25p, 2.7 to 15 MFD 50p +8% on total.

Oil Filled Paper Block Capacitors By Famous Makers. Unused

MFD	DC volts	Price
8	WKG 600v	£1
8	400v	75p
8	350v	65p
8	200v	50p
4	600v	65p
4	500v	50p
2	800v	65p
2	600v	50p
1	1500v	75p
1	1000v	60p
1	600v	50p
1	350v	35p
0.5	1000v	50p
0.1	300vAC	50p
6	300vAC	£1

Post 0.1 to 2 MFD 25p, 4 MFD to 8 MFD 50p.

STANDARD OPEN TYPE RELAYS SINGLE HOLE FIXING 7 AMP CONTACTS BY FAMOUS MAKERS

Coil voltage	Contact	Price
240vAC	3 CO	85p
240vAC	2 CO	75p
240vAC	1 CO	65p
110vAC	2 CO	65p
48vDC	3 CO	50p
24vDC	2 CO	75p
12vDC	2 CO	75p

P&P 10p per relay. Please add VAT 15% on total

L.T. SMOOTHING CHOKES

'C' core types 14 M/H 6A £3.75 pp £1. 10 M/H 25amps £8.50 carr £2. 4 M/H 12amps £3.75 carr £1.50. Swinging 'C' core type, 10 M/H 4A — 100 M/H 1/2A £4.50 carr £2. M/H 1.15A £1.50 pp 75p. Open types 4.8 13 M/H 1.15A £1.50 pp 75p. Open types 4.8 M/H 10A £3.50 pp 75p. 140 M/H 5A £4.80 carr £1.50. 50 M/H 2 1/2A £3.50 pp £1. 15 M/H 3 1/2A £3.50 pp £1.

H.T. SMOOTHING CHOKES

Potted types, 15H 75M/A £1.50 pp 75p. 50H 25M/A £1.50 pp 75p. 10H 75M/A £1.50 pp 75p. 1H 75M/A £1.50 pp 75p. 4.5H 280M/A £3 pp £1. 'C' core 10H 350M/A £4.50 pp £1.50. 40H 40M/A £2.25 pp £1.

CRESSALL RHEOSTATS

Built-in ventilated 6 inch metal surround with control knob, 101000, 0.15A, 9800, 0.48A, 32500, 0.24A £3.95 pp £1.25. 3 inch size 30000, 0.1A £2 pp 75p. ZENITH heavy duty fixed wire resistors, enclosed, size 18x5x3 1/2in, 1360 1.7A £3 carr £1.50.

HEAVY DUTY 'C' CORE L.T. TRANSFORMERS BY FAMOUS MAKERS. FRACTION OF LIST PRICE

ALL PRIMARIES £220-240V
No 1 12 volts 40 amps cont. £19.50 carr £3.
No 2 14+3+1 1/2V 40 amps cont £22.50 carr £3.
£3. Limit number.

HEAVY DUTY L.T. TRANSFORMERS BRAND NEW. FRACTION OF LIST PRICE

ALL PRIMARIES 220-240V
Open frame type, Sec. 17+2+1 1/2+1 separate windings, all at 20 amps £9.50 carr £2. No 2 as above, 10 amp rating £6.50 carr £1. No 3 65v 2.2A and 30-0-30v 100 m/a £3.95 pp £1. 'C' core types 12V 10A and 30-0-30v 1/2A £5.50 pp £1. 12V 5A and 30-0-30v 250 m/a £3.75 pp £1. Sec. 18-22-27V 250 m/a twice £2.75 pp 75p. Sec. 24V 480 m/a twice £2.75 pp 75p. Sec. tapped 3-9-12-27-30-36V 1.8A £3.75 pp £1.

H.T. TRANSFORMERS BY FAMOUS MAKERS. ALL PRIMARIES 240V

Type MT33 300-0-300V 1500VA 6.3v ct 4A 5.5 3v 2A £4.50 pp £1. MT12 Sec. 300-0-300V 120M/A 6.3v ct 4A 5.5 3v 2A £4.00 pp £1. MT11 Sec. 300-0-300V 100M/A 6.3v 3.5A 5v 2A or 6.3v 1A £3.75 pp £1. MT7 Sec. 350-0-350V 100M/A 6.3v 3.5A 5v 2A or 6.3v 1A £4.00 pp £1.

WODEN POTTED TRANSFORMERS

Pri. 230v sec. tapped 40-41-42-48-49-50v, very conservatively rated at 10 amps and 60v 100M/A. Size 9x7x6in callers £15 carr £3.

Hundreds of bargains for enthusiasts' Huge stocks of high capacity electrolytics. Heat sinks. Ex computer bits.

C.T. ELECTRONICS (ACTON) LTD.

Registered in England 1179820

267 & 270 ACTON LANE, LONDON W4 5DG. Telephone: 01-994 6275

9.30am-6.00pm
MON-SAT
CONTINUOUS

This advertisement represents a fraction of our stock. Please phone your requirements. Minimum mail order £5 plus carriage and packing charge. Add VAT at 15% to all prices. Government, colleges, trade and export welcome.

DATA GENERAL COMPUTERS

We have three complete systems left, each consisting of:
NOVA 820 main frame (including 240V 50Hz power supply)
NOVA 820 expansion chassis (including 240V 50Hz power supply)
CPU 1 (8206) with power monitor and restart (16 bit)
CPU 2 (8207) Multi/div. I/O interface for teletype (4007/4010)
32K core memory. Disk pack controller (4046)
General purpose interface board with data channel (4040/4047)
Diablo series 30 (type 4047A) moving head 2.5M byte disk drive.
240V 50Hz power supply for above, with adaptor and logic board (4047)
Computer control panel. Cabinet, including fans and mains filter.

OFFERS AROUND £5,000

FARRINGTON AUTOMATIC WRITING MACHINES:

We have two machines each consisting of: Heavy duty typewriter, photoelectric paper tape reader, paper tape punch and solid state logic control. The units together provide an automatic data processing system. **£750 + VAT.**

DATA DYNAMICS 390 ASR TELETYPE

Refurbished, full working condition. **£300 + VAT.**

Diablo series 30 DISK DRIVES: Type 4047A, 2.5M byte with psu. **£400 + VAT.**

BRANDENBURG Model 374 Photomultiplier power supply, 300V — 1KV at 5mA. Current limit; metered, 19 inch rack mounting. **£20 + VAT.**

TEXAS 4030JL DYNAMIC RAM (Eq. Intel 2107). **£3 + VAT.**

We have large stocks of spare parts for the Nova 820 series computers, eg, Memory boards, I/O interface boards, Disk pack controller boards, disk drive power supplies, etc. Many surplus bargains in our retail shop for callers only. Much of our stock is constantly changing and hence not practical to list. Please phone your requirements.

3 Centaur Fans 110/120V 12W (119/119/38mm). In 19 inch Vero case. **£12 + VAT.**

NEW SURPLUS OFFER HIGH SPEED 15MHz 8-BIT DIGITAL TO ANALOGUE CONVERTERS

by Micro-Consultants Ltd. 50ohm Cable-drive output. Linearity: 0.25% max; 0.125% typ. Settling time: 2volt step 70nS typ; 2mV step 50nS.

Colour Television Transmission Standard. Differential Gain 0.5%. Differential Phase Shift 0.5%.

TYPES RAD 802 AND MC2208/8 UNUSED, EX-MAKER'S PACK

ONE-OFF CURRENT LIST PRICE . . . OVER £250
SPECIAL OFFER PRICE NOW £50 + VAT

Berk Tek BTK-30-3CL 30 AWG 5mil wall Kynar cable (for computer back panel wiring) style 1423 105°C, red or white. Approx. 1/2 list price at £20 per 10,000 ft. reel.
Blues Macs RIBBON CABLE £20 + V.A.T. 25-way (150V, 105°C). 100ft. Reels per reel.
Thermosetting Silver Compound £20 + V.A.T. per 50g Tube.
Special offer Filmet SC 65 1MΩ 0.1% M. Film Resistors 20p each.
REED RELAYS OSMOR CD3182 6V 2PCO PCB MOUNTING (60 x 18 x 13mm), £1.00 + V.A.T.

7400	0.12	7451	0.20	74141	0.75	4000UB	0.17	4027B	0.44	4075B	0.20
7401	0.12	7453	0.20	74150	1.00	4001UB/B	0.17	4028B	0.77	4076B	0.20
7402	0.12	7454	0.20	74151	0.70	4002UB/B	0.17	4029B	1.03	4077B	0.39
7403	0.12	7460	0.20	74153	0.70	4006B	1.04	4032B	0.89	4078B	0.20
7404	0.12	7470	0.35	74154	1.00	4007UB	0.18	4034B	1.71	4081B	0.20
7405	0.18	7472	0.30	74155	0.70	4008B	0.87	4040B	0.97	4082B	0.20
7406	0.32	7473	0.30	74156	0.85	4011UB/B	0.18	4043B	0.88	4093B	0.80
7407	0.32	7474	0.30	74157	0.70	4012UB/B	0.20	4044B	0.84	40160B	1.19
7408	0.20	7475	0.45	74160	0.95	4013B	0.43	4049UB	0.50	40161B	1.19
7409	0.20	7476	0.35	74161	0.50	4014B	0.83	4050B	0.43	40162B	1.19
7412	0.20	7480	0.60	74162	1.00	4015B	0.83	4051B	0.82	40163B	1.19
7413	0.30	7481	1.00	74163	1.00	4016B	0.48	4052B	0.82	40174B	0.85
7414	0.70	7482	0.90	74164	1.00	4017B	0.79	4053B	0.82	40175B	0.86
7415	0.30	7483	0.90	74165	1.00	4018B	0.83	4066B	0.55	40194B	1.19
7417	0.30	7484	1.10	74166	1.00	4020B	1.11	4068B	0.20	4510B	1.01
7419	0.50	7485	0.90	74167	2.50	4021B	0.90	4069UB	0.20	4511B	1.25
7420	0.18	7486	0.30	74170	2.00	4022B	0.82	4070B	0.46	4512B	0.91
7421	0.20	7489	0.35	74174	0.95	4023UB/B	0.18	4071B	0.20	4516B	1.01
7422	0.35	7490	1.60	74175	0.80	4024B	0.70	4072B	0.20	4518B	0.97
7423	0.32	7491	0.50	74176	0.80	4025UB/B	0.20	4073B	0.20	4520B	0.80
7425	0.30	7492	0.45	74177	0.80	EDGE CONNECTORS					
7426	0.30	7493	0.40	74180	0.80	Single sided 0.1 pitch:					
7427	0.30	7494	0.90	74181	1.95	24-way (fixing holes 73mm)—UCL £0.70					
7428	0.40	7495	0.65	74182	0.95	40-way (fixing holes 118mm)—RS £1.20					
7430	0.18	7496	0.65	74184	1.50	78-way (length 204mm)—UECL £1.50					
7432	0.26	7497	1.90	74185	1.50	Single sided 0.15 pitch:					
7433	0.50	74100	1.40	74188	2.50	15-way (fixing holes 73mm). Gold plated EB £0.60					
7437	0.30	74104	0.70	74190	1.00	18-way (fixing holes 85mm) inc. locating pin £0.75					
7438	0.30	74105	1.70	74191	1.00	32-way (fixing holes 136mm). Gold plated, EB £1.50					
7440	0.18	74107	0.30	74192	1.00	27-way (fixing holes 122mm) £1.30					
7441	0.70	74109	0.55	74193	1.00	Double sided-0.1 pitch:					
7442	0.50	74110	0.55	74194	1.00	2 x 40-way (fixing holes 117mm). Gold plated £2.00					
7443	1.30	74118	0.95	74195	0.95	Double sided 0.15 pitch:					
7445	1.00	74119	1.30	74196	0.95	2 x 40-way (fixing holes 165mm). Gold plated £2.00					
7446	1.00	74121	0.28	74197	0.80	LEVER SWITCHES GPO BP1000 Type					
7447	0.75	74122	0.55	74198	1.60	4PCO, 8PCO with knobs £0.60					
7448	0.75	74123	0.55	74199	1.60	PUSHBUTTON SWITCHES by A. B. Electronics					
7449	1.00	74125	0.50	74200	1.60	4-way 2PCO £0.50 , 7w. 5x2PCO, 2x4PCO £0.80 .					
7450	0.20	74132	0.70								

TRANSFORMERS, all 240V primary
6-0-6 500mA (63 x 35 x 48) **£1.40**
0-11, 2A; 0-22, 1A (76 x 64 x 60) **£2.40**
12V 130mA (36 x 45 x 40) **£0.75**
17V 300mA (44 x 47 x 74) **£1.50**
18V 2A (80 x 55 x 70) **£2.80**
18V 2.5A (115 x 65 x 62) **£2.50**
28V 200mA (53 x 45 x 37) **£1.00**
32V 250mA (46 x 37 x 31) **£1.20**
0-2-4-6-8-10-12, 0-1-1, 5A **£6.00**

Aluminium Boxes	ins L	W	H	Retail price	+ VAT
AB7	5 1/4	2 1/2	1 1/2	0.70	0.80
AB8	4	4	1 1/2	0.70	0.80
AB9	4	2 1/2	1 1/2	0.70	0.80
AB10	4	5 1/2	1 1/2	0.70	0.80
AB11	4	2 1/2	2	0.85	1.00
AB12	3	2	1	0.70	0.80
AB13	6	4	2	1.00	1.15
AB14	7	5	2 1/2	1.20	1.38
AB15	8	6	3	1.55	1.78

Blue Rexine Covered	ins L	W	H	Retail price	+ VAT
AB16	10	7	3	1.75	2.00
AB17	10	4 1/2	3	1.45	1.66
AB18	12	5	3	1.75	2.00
AB19	12	8	3	2.40	2.76
RB1	6	4 1/2	2 1/2	1.45	1.66
RB2	8	5	3	1.70	1.95
RB3	9	5	3 1/2	1.00	1.15
RB4	11	6	4	2.30	2.64
RB5	11	7 1/2	4 1/2	2.70	3.10

DATA GENERAL PHOTO PAPER TAPE READERS 400 I.P.S. 8 BIT Part No. 6013-2 SPECIAL OFFER PRICE £150 + VAT

MAINS FILTERS

Potter 30A, 125V (184 x 51 x 70). Sealed **£3.00**
Erio 8A, 250V (61 x 120 x 47). Diecast box **£5.00**
BRIMAR CRT M17/15GV, with scan coils and Wallis power supply. Rectangular screen (96 x 130) **£20.00**

LARGE PANEL METERS (Clear view)

SIFAM 140-0-140microAmp (107 x 145), Calibrated 0-14 and 7-0-7. Boxed **£5.00**
ANDERS 1mA f.s.d. (145 x 115), Calibrated 0.15KV boxed. **£5.00**

KEYSWITCHES — HEAVY DUTY by Kraus & Naimer

2P (1PM-1PB) 12A 600VAC **£1.50** 49mm square
10P (4PM-6PB) 12A 600VAC **£3.00** fascia
By Baco: **£0.85**

8P (4PM-4PB) 10A 380VAC. By Baco **£3.00**

ILLUMINATED SWITCHES by Licon

Rectangular snap in (01-800 series). 10A contacts. Min. flange bulb holders
SPCO Momentary **£1.00**
2PCO Momentary **£1.50** Indicator only **£0.50**
Price includes lenses but not bulbs.
Red, yellow, blue, green and white lenses available.

VEROBOARDS

0.1" Pitch Copper Clad		0.15" Pitch Copper Clad	
2.5" x 5"	0.59	2.5" x 5"	0.53
2.5" x 3.75"	0.50	2.5" x 3.75"	0.44
2.5" x 17"	1.77	3.75" x 17"	1.98
3.75" x 5"	0.66	3.75" x 5"	0.74
3.75" x 3.75"	0.59	0.15" Pitch Plain Board	
3.75" x 17"	2.28	5" x 3.75"	0.47
4.7" x 17.9"	2.99	2.5" x 5"	0.30
2.5" x 11" (Sold in 5s)	0.70	New V-Q DIP Board	1.11
0.1" Pitch Plain Board			
3.75" x 17.9"	1.49		
3.75" x 2.5"	0.36		
3.75" x 5"	0.56		

SPECIAL OFFER
741 8 pin DIL **15p**


Cassette Erase Tape Heads 1/4" **£1.00 each**.
Cassette Monotape Heads 1/4" **£2.00 each**. Brand new.

Miniature Moulded Track Presets by Plessey. Screwdriver operation, 0.25W dissipation. PCB fixing, **15p each**.
Open Cermet Presets. Most values in stock. **15p each**.

ROTARY SWITCHES available in 30 different types, prices range from **45p-£1.20**
PREH Television Push-button Tuner Units, 4 and 6 button, brand new in original boxes **75p each**. Large quantity available.

SINE WAVE INVERTERS

120-300 VA. 50/60 Hz

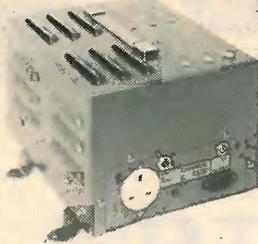

HIGH QUALITY A.C. POWER SUPPLIES FOR MOBILE, INDUSTRIAL, COMMUNICATIONS, MARINE AND MANY OTHER USES

- ★ Ruggedly built in welded steel cases
- ★ Stabilised low distortion output
- ★ Closely controlled frequency
- ★ Full overload and short-circuit protection
- ★ Battery protection by low voltage warning and automatic cut-out
- ★ Automatic standby and remote options

SERIES A: 12/24 V DC.I.P. 240, 220 or 115V. AC. O.P.

CARACAL ENGINEERING

42-44 SHORTMEAD ST., BIGGLESWADE, BEDS. Tel: 0767-81361

A complete High Quality 20AX System Colour Television Receiver Kit

The Forgestone 500

- 20AX Hi-Bri tube
- Full technical construction manual
- Modern cabinets
- Pin diode tuner
- Glass epoxy printed circuit panels
- Teletext option

Buy as you build. All Forgestone Kits are for the constructor of today. Sections of the Kit are available separately. Please send stamp for further details of these quality products.

Forgestone Colour Developments Limited

Ketteringham, Wymondham, Norfolk, NR18 9RY
Telephone: Norwich 810453 (STD 0603)
Telephone or Mail Orders accepted on Barclaycard/Access

WW — 108 FOR FURTHER DETAILS

KEYBOARD TERMINAL



The Newtronics Keyboard Terminal is a low cost stand alone Video Terminal that operates quietly and maintenance free. It will allow you to display on a monitor 16 lines of 64 characters or 16 lines of 32 characters on a modified TV (RF Modulator required).

The characters can be any of the 96 ASC11 alphanumerics and any of the 32 special characters, in addition to upper-lower case capability it has scroll up features and full X-Y cursor control. All that is required from your microcomputer is 300 baud, RS232-C or 20ma loop, serial data plus a power source of 8v DC & 6.3v AC. The steel cabinet is finished in IBM Blue-Black. And if that is not enough the price is only **£135.55 + VAT as a Kit, or £175 + VAT assembled and tested.** Plus £2 P&P (Monitor not included).

Dealer O.E.M. enquires invited
To order phone or write to:

Newtronics

138 KINGSLAND ROAD, LONDON E2 8BY
TEL: 01-739 1582

Access/Barclaycards accepted

WW — 094 FOR FURTHER DETAILS

BI-PRE-PAK

NICKEL-CADMIUM BATTERIES AT LESS THAN HALF-PRICE



BY A WORLD-FAMOUS MANUFACTURER IN 5 VALUABLE SIZES

BRAND NEW & GUARANTEED

Type	Capacity in mAh	Voltage	Charge Rate mA/12 hrs	Size in mm dia. x Thickness	Our price inc. 15% VAT
NC20	200	1.24	20	24.8 x 7.4	45p
NC28	280	1.24	28	34.4 x 5.3	60p
NC50	500	1.24	50	34.3 x 9.5	80p
NC90	900	1.24	90	50.5 x 8.3	£1.20
NC175	1750	1.24	175	50.7 x 14.9	£1.75

- High capacity for very small size.
- Wide temperature operating range.
- Low internal resistance.
- Very simple charging circuit required.
- INDEFINITE SHELF LIFE.

TO ORDER

Please send cash with order. Minimum order £3.00 plus 30p p/p in U.K. Orders over £10 cart. paid U.K. All prices inc. V.A.T.

Ideal for portable & emergency equipment, instruments, etc.

(WW) 222-224 West Road
Westcliff-on-Sea, Essex
SS0 9DF
Telephone 03708 5543

BI-PRE-PAK LTD.

APOLOGIES

With reference to advert on page 106 which is incorrect.

CORRECTED ADVERT APPEARS BELOW.

KELSEY K102M TRANSFORMERLESS BALANCED LINE MICROPHONE AMPLIFIERS

Specifications

Direct P.C.B. mounting	
Supply Voltage	+15V
Maximum Gain	43 dB
Gain Control Range	38 dB
Gain Reduction in Unbalanced Mode (Input to Terminal +)	10 dB
Maximum Input Level (Unbalanced Mode, Input to Terminal +)	+15 dBV
Input Impedance (Each Input Terminal to Ground)	5 Kohm
Optimum Source Impedance	200 ohm
Maximum Output	+20 dBV
Frequency Response	+ 0.5dB Ref. 10 Hz to 50 KHz
Slew Rate	Better than 10 V / microsec
Harmonic Distortion	Better than 0.03% Ref 1KHz
	Typically 0.027%
Common Mode Rejection Ratio	Better than 80 dB
Equivalent Input Noise (Unweighted)	Better than -125 dBV (Din: Audio band weighted)
Recommended Output Loading	10 Kohm
Dimensions	40mm x 40mm x 20mm
Weight	48 grams

KELSEY ACOUSTICS LTD 28 POWIS TERRACE, LONDON W11. TEL: 01-727 1046

WW — 106 FOR FURTHER DETAILS

Appointments

Advertisements accepted up to 12 noon Friday, August 31st for October issue, subject to space being available.

DISPLAYED APPOINTMENTS VACANT: £10.00 per single col. centimetre (min. 3cm).
LINE advertisements (run on): £1.50 per line, minimum three lines.

BOX NUMBERS: 70p extra. (Replies should be addressed to the Box Number in the advertisement, c/o Wireless World, Dorset House, Stamford Street, London SE1 9LU.)
PHONE: Neil McDonnell on 01-261 8508

Classified Advertisement Rates are currently zero rated for the purpose of V.A.T.

RADIO TECHNICIANS

At the Government Communications Headquarters we carry out research and development in radio communications and their security, including related computer applications. Practically every type of system is under investigation, including long-range radio, satellite, microwave and telephony.

Your job as a Radio Technician will concern you in developing, constructing, installing, commissioning, testing, and maintaining our equipment. In performing these tasks you will become familiar with a wide range of processing equipment in the audio to microwave range, involving modern logic techniques, microprocessors, and computer systems. Such work will take you to the frontiers of technology on a broad front and widen your area of expertise — positive career assets whatever the future brings.

Training is comprehensive: special courses, both in-house and with manufacturers, will develop particular aspects of your knowledge and you will be encouraged to take advantage of appropriate day release facilities.

You could travel — we are based in Cheltenham but we have other centres in the UK, most of which, like Cheltenham are situated in environmentally attractive locations. All our centres require resident Radio Technicians and can call for others to make working visits. There will also be some opportunities for short trips abroad, or for longer periods of service overseas.



You should be at least 19 years of age, hold or expect to obtain shortly the City and Guilds Telecommunications Technician Certificate Part I (Intermediate), or its equivalent, and have a sound knowledge of the principles of telecommunications and radio, together with experience of maintenance and the use of test equipment. If you are or have been in HM Forces your Service trade may allow us to dispense with the need for formal qualifications.

WORK IN COMMUNICATIONS R&D AND ADD TO YOUR SKILLS

You start at £3900 rising to £5530, and promotion will put you on the road to posts carrying substantially more. There are also opportunities for overtime and on call work paying good rate.

Get full details from our Recruitment Officer, Robby Robinson, on Cheltenham (0242) 21491, Ext. 2269, or write to him at GCHQ, Oakley, Priors Road, Cheltenham, Glos. GL52 5AJ. If you seem suitable we'll invite you to interview in Cheltenham — at our expense, of course.

(9106)

UNIVERSITY OF KEELE ELECTRONICS TECHNICIAN

in the

DEPARTMENT OF COMMUNICATION AND NEUROSCIENCE

Vacancies exist for an Electronics Technician or Trainee to work on laboratory instrumentation, including computers and peripherals, in a Department engaged in research into communication mechanisms of the brain. Experience in electronics and/or computer maintenance desirable. A suitably qualified and experienced applicant can be appointed in Grade V (salary range at present £3474-£4056 p.a.); but applications will be considered from less qualified persons willing to undergo training, with an initial appointment in a lower grade (salary range £1722-£3336 p.a.) Application forms and further particulars obtainable from the Registrar, The University, Keele, Staffs ST5 5BG. Forms should be returned by 20th August 1979. (9614)

NATIONAL VEGETABLE RESEARCH STATION

Instrumentation

and

Electronics Engineer

An Instrumentation and Electronics Engineer is required to provide a service for design, development and fabrication of electronic, electro-mechanical and mechanical apparatus and equipment.

Degree in electrical/electronic engineering or Council of Engineering Institutions Part II examination in an appropriate subject, or equivalent or higher qualification, with an aggregate of at least five years' recognised study, professional training or experience.

Salary scale: Professional and Technology grade P & TO II £4869 rising by 5 increments to £5739. (Salary under review from 1 April 1979).

Further particulars and application forms from Secretary, National Vegetable Research Station, Wellesbourne, Warwick CV35 9EF. (9646)

UNIVERSITY OF LIVERPOOL

EXPERIMENTAL OFFICER

(TWO POSTS)

(a) DEPARTMENT OF ELECTRICAL ENGINEERING & ELECTRONICS

(b) DEPARTMENTS OF MECHANICAL & CIVIL ENGINEERING

Post (a) involves assistance in the development and application of microprocesses and other digital systems to a wide range of undergraduate, postgraduate and industrial activities.

Post (b) involves responsibility for interfacing microcomputers with a wide variety of laboratory sensors and transducers used by these Departments in both teaching and research.

Expert advice on hardware and software is available. Candidates must possess a degree or equivalent qualification.

Salary within range up to £5604 p.a.

Application forms available from: The Registrar, The University, P.O. Box 147, Liverpool L69 3BX. Quote Ref: RV/709/WW. (9607)

Good Radio Systems Engineers are few and far between

So are opportunities like this

£5,500-
£7,500

Yet again we are adding personnel to our Systems Planning Team. We need male or female Engineers to take on the responsibility of designing and planning systems ranging from single channel HF to Broadband microwave links. Detailing performance estimates, writing specs and systems descriptions are all part of the job. Naturally technical expertise and experience are paramount in our developing world. We need experience in the latest state of the art as well as traditional technology.

In return for your services we offer a variety of tasks and early responsibility in a highly motivated team. Please do not waste your time or ours unless you are prepared to travel overseas from time to time and to put in that little extra that IAL expects as the norm.

As well as paying the salary noted above we have an excellent pension scheme - the usual company social club who will do their best to organise your off time - good holiday travel benefits are available and our staff catering facilities are second to none. If you have to relocate to join IAL we will pay you reasonable relocation expenses and provide accommodation for the employee during the first few weeks of employment.

Our offices are close to Heathrow which puts the residential areas of Wokingham, Reading, the Chalfonts and Harrow in easy commuting reach.

Write or 'phone quoting ref. 259/K to The Senior Recruitment Officer, IAL, Aeradio House, Hayes Road, Southall, Middlesex. 01-574 5134.

(9503)

IAL

Aviation and Communications Systems and Services - worldwide



ROYAL NORTHERN COLLEGE OF MUSIC

Applications are invited for the post of

SENIOR TECHNICIAN (SPECIAL PROJECTS)

Salary £3,732-£4,161 (under review)

Duties will include investigation into acoustic modifications, new recording techniques (quadrophonic and digital systems), design of equipment for electronic synthesis. Assistance will also have to be given to Academic Staff in respect of Aural Training and to the Recording Manager in the running of his Department. Qualifications should include HNC or HND in Electrical Engineering, appropriate degree or Corporate Membership of the IEETE. This should be combined with an exceptional understanding of electro-acoustics (theoretical and practical), of acoustic problems and design and an interest in music and experience in video/sound recording. Application forms and further details may be obtained from Administrative Registrar, Royal Northern College of Music, 124 Oxford Road, Manchester M13 9RD. Tel: 061-273 6283, Ext. 46. Closing date for return of application form 10 September, 1979.

(9496)

UNIVERSITY OF LONDON GOLDSMITHS' COLLEGE New Cross, London SE14 6NW

Psychology Department

The Psychology Department has two senior vacancies for technical staff to start as soon as possible.

(1) TECHNICIAN

(Grade 6) to work on the Department's extensive range of electronic and video equipment. Normal qualifications for this post will be HNC/HND.

Salary on the following scale: £3,984 - £4,104 - £4,236 - £4,365 - £4,497 - £4,626 - £4,758 plus £525 London Weighting Allowance.

(2) TECHNICIAN

(Grade 5) to work in the field of computer and microprocessor applications in psychological research. Normally technical qualifications/experience would be required for this post but applications for graduates in relevant fields will be welcome.

Salary on the following scale: £3,474 - £3,582 - £3,699 - £3,816 - £3,933 - £4,056 plus £525 London Weighting Allowance.

Write for further details to the Personnel Officer to whom applications should be sent by 31st August, 1979.

(9603)

THE CITY UNIVERSITY DEPARTMENT OF COMPUTER SCIENCE

SRC RESEARCH STUDENTSHIP

Applications are invited for an SRC Research Studentship to investigate braille translation. This project, in collaboration with the Royal National Institute for the Blind, aims to produce a low-cost office machine capable of accepting typewriter input, and forming braille on a refreshable braille display.

Candidates would normally be required to have a good Honours Degree in computer science or electronics.

Applications, together with the names of two referees should be submitted as soon as possible to Dr. G. R. Dowling, Department of Computer Science, The City University, Northampton Square, London EC1V 0HB, from whom further particulars may be obtained.

(9631)

Radio Communications Electronics Engineers and Software Designers

Mid-Sussex - S.W. London

Salaries up to £7,000

To join our expanding R&D Laboratories covering a wide range of R.F. spectrum, from L.F. to V.H.F. Equipments include transmitters and receivers for marine and land based use, radio nav aids and radio monitoring remote computer controlled systems.

Electronics Engineers should have experience in transmitter or receiver design, analogue or digital circuit design, microprocessor applications. Software Designers should be experienced Programmers with an interest in control, signal processing or navigational software.

Attractive salaries are complemented by excellent prospects and generous benefits.

Contact: The Personnel Manager, Redifon Telecommunications Limited, Broomhill Road, Wandsworth, London S.W.18. Phone: 01-874 7281 (reverse charges).

(9033)

Inner London Education Authority

HACKNEY COLLEGE

LECTURER I

Suitably qualified person required to teach theory and craft processes to ELECTRICAL AND ELECTRONIC ENGINEERING CRAFT AND TECHNICIAN APPRENTICES.

Applicants should hold a City and Guilds of London Institute Advanced Craft or Full Technological Certificate and have suitable industrial experience.


Salary on an incremental scale within the range £3,192-£5,334 (under review) plus £474 Inner London Allowance. Starting point will depend on qualifications and experience.

Applications obtainable from/returnable to Senior Administrative Officer, Hackney College, Dalston Lane E8 1LJ, Ext. 212 (01-985 8484).

Closing date 31 August, 1979.

(9604)

Electronics Engineers

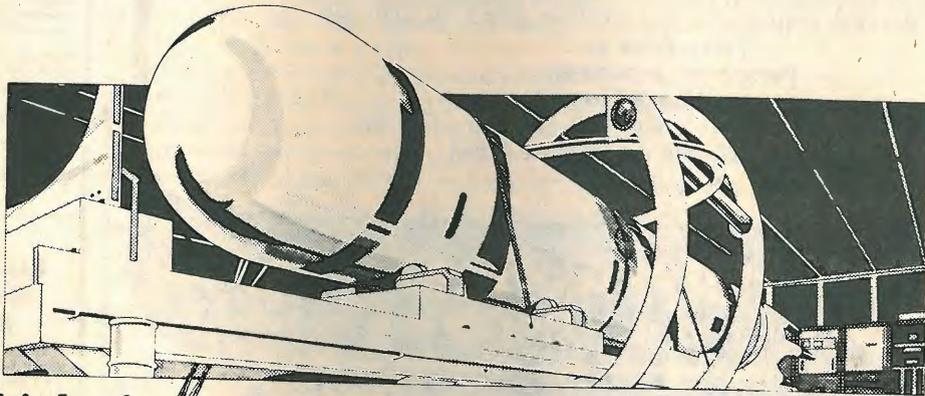

Can you think of a more testing environment for your test experience?

There can be few areas that present greater technical challenge than the project we have started. It involves the creation of entirely new torpedo-based defence systems flexible enough to counter threats as yet unknown and incorporating the latest advances in micro-processing control and guidance technologies.

We need hardly underline the importance of an accurate, flexible and, above all, reliable test and maintenance system for the torpedo's success. What we're offering you is the chance to make your own direct contribution - right from the start of the project.

As a vital member of a tightly-knit engineering team, developing the sophisticated ATE the system requires, you can expect full involvement. The scope of our work includes systems design, detail design and software applications of both manual and automatic test systems - integrating maintainability aspects of test logistics.

The men and women we're looking for are self-motivated Electronic Engineers, unafraid of applying innovative thought to ATE systems and design.

If you fit one of the following, we want to hear from you.

An ATE Manager

Concerned with the design and development of an Automatic Test System, you will supervise both in-house design and sub-contract control following the generation of the initial requirement specification.

A Section Leader

You will be responsible for the design of special to type test equipment, to support the development, production and in-service use of the weapon system. This will involve generation of the initial requirement specification - as well as the subsequent design and development.

Engineers-Test System Studies

Possible areas of involvement include depth of test calculations, tolerance tiering philosophy, diagnostic procedures and maintenance logistics. Some previous experience of servicing complete weapon systems, while not essential, would be an advantage.

Engineers-Detailed Design

You will be working on special to type test equipment, both manual and computer controlled. Your involvement will extend to the weapon system's commissioning and development trials.


ATE Software Manager

You will lead a group concerned with i) the programs associated with executive control of a computer controlled ATE, and ii) generating, in conjunction with Design Engineers, the test specifications for the weapon system.

If you can't see your precise area of work here, but have an interest in test equipment, we would still like to hear from you - as we have a number of projects under way.

Apart from the excitement of the work itself, we offer realistic salaries, excellent opportunities for career development and a range of fringe benefits - including financial help with relocating you and your family to our pleasant South Coast setting, where housing is readily available.

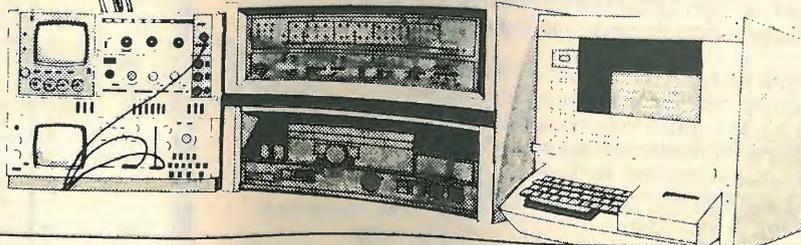For full details of career opportunities in our testing environment, complete the attached coupon. And get ready for your career to grow.



Name _____
 Address _____
 Area of interest _____

Jack Burnie, Applied Electronics Laboratory, Marconi Space & Defence Systems Ltd., Browns Lane, The Airport, Portsmouth. Telephone: Portsmouth 699 111 (Ref. 9610)

Marconi Space & Defence Systems (Portsmouth)

A GEC Marconi Electronic's Company

Closed Circuit Television Manager

The name of "Chubb" is synonymous with progress and expansion in the field of integrated security systems. Recently we have relocated part of our diverse operation to Woking, Surrey. It is here that we wish to appoint a high calibre Closed Circuit T.V. Manager. The person we are looking for will be a self-starter with both engineering and commercial experience plus a sound and up to date knowledge of CCTV systems and techniques.

Salas project management and support to our busy field force both at home and abroad are two of the main responsibilities of this demanding position. The successful applicant (male/female) can expect an attractive remunerative package with salary in the range of £6,500 to £8,500 per annum, Company car and a wide range of Company benefits. If you feel that you can meet the above requirements and would like to develop your career in a positive direction then call:

Terry Ainsley

Personnel Department
Chubb Alarms Limited

42/50 Hersham Road · Walton-on-Thames · Surrey
Telephone: Walton-on-Thames 43851

Relocation expenses will be paid where appropriate.

(9623)



Chubb Alarms

a member of The Chubb Electronics Group.

Systems Engineers

Collins Radio, a division of Rockwell International, are acknowledged leaders in the field of communication systems. As a result of recent contract awards our Operations Group is expanding.

Qualified Engineers, at all levels, are required to work as systems Engineers in our Ship Systems and Ground/Transportable Systems Groups. They will be required to evaluate and systemise complex communication requirements utilising HF/SSB, MF, VHF, UHF, microwave and data transmission techniques. Systems projects, in addition to radio equipment, typically include antennas, power sources, RTTY, voice/data scramblers; remote control/supervisory, radio telephone patch, selective calling, audio distribution/switching, antenna matrix and customised terminal/control equipment.

These positions would be of interest to qualified engineers currently employed as Radio Engineers, Radio Communication Engineers, Communications Engineers, System Test Engineers, Systems Engineers, Systems Designers, System Circuit Design Engineers, Electronic Engineers, Project Engineers, Applications Engineers, and Planning Engineers.

Ideally applicants should have a broad theoretical and/or practical background in communication methods, but training would be given to suitable engineers who are able to demonstrate an ability or willingness to undertake projects from inception to final system implementation. The positions will be based in Reading, Berkshire, and will involve some overseas travel.

We offer an attractive starting salary which is negotiable, assistance with relocation expenses and considerable Company benefits.

Please telephone Reading (0734) 61111 or write for application forms to: - Personnel Manager, Rockwell-Collins (U.K.) Ltd., Suttons Industrial Park, London Road, Earley, Reading RG6 1AZ.



Rockwell International

(9506)

INNER LONDON EDUCATION AUTHORITY
London College of Printing, Elephant and Castle, London SE1 6SB
DEPARTMENT OF PHOTOGRAPHY, FILM AND TELEVISION

TELEVISION TECHNICIAN/ENGINEER (ST1/2)

Applications are invited for the above post in the School of Film and Television, Department of Photography, Film and Television. Candidates should be conversant with 1/2", 3/4" and 1" black and white and colour equipment and be capable of electronic maintenance. Experience in professional broadcasting would be an advantage, as well as an interest in experimental video work. The successful applicant will be expected to assist in running studio productions, and video tape editing.
Salary within the scale £3688.44-£5401.44 inclusive. Progression up the scale to £4867.44 is by annual increments subject to satisfactory performance. Progression beyond that point is dependent on a positive assessment.

Application form, returnable within 14 days, obtainable from the Senior Administrative Officer at the College. Tel. No. 735 8484 ext 227. (9624)

LONDON BOROUGH OF HARINGEY - Education Service

PART-TIME ASSISTANT HEARING AND VISUAL AIDS TECHNICIAN

required at Blanche Nevile Special School, Philip Lane, N15, to work 15 hours per week x 52 weeks per annum to assist in the repair and maintenance of hearing and visual aids equipment.

Grade/Salary: Pro-rata to N.J.C. Technical Grade 2 - £3600 per annum rising to £3972 per annum inclusive, which equals £1542 per annum (under review).

Applicants should preferably have experience in maintaining electronic equipment and should hold one of the following qualifications.

Final City and Guilds Certificate for Electrical Technicians/Marine Shop Engineering/Mechanical Engineering, or other equivalent qualification.

OR a minimum of ten years' suitable experience in a school or industry.

Hours of duty: 9.30 a.m. to 12.30 p.m. Candidates will be welcome to contact Mr. J. H. Stanway, Headmaster (01-808 5744).

Application forms obtainable from: Chief Education Officer, Education Offices, Somerset Road, N17.

Forms returnable by: September 7, 1979. (9641)

UNIVERSITY OF EDINBURGH

DEPARTMENT OF CHEMISTRY ELECTRONICS SPECIALIST

£3,689 to £7,145 (Grade 1A/1B)

Electronic Engineers! You are invited to apply for this post of electronics specialist. It is a staff position, academically related and benefits include six weeks' holidays per annum. Applicants should have a broad spectrum of analogue and digital expertise which they will exercise on the very broad range of analytical instrumentation used for teaching and research. The successful applicant will be responsible to the Head of Electronic Services for the design and construction of new equipment and the maintenance of existing equipment which includes N.M.R., E.S.R., Mass Spectrometers, real time computer systems and peripheral devices, ultra high speed RF and digital equipment. Experience in RF and microprocessor techniques would be advantageous.

The appointment will be within the scale as shown commensurate with experience/qualifications.

Applications giving career history and the names of two referees should be made to: The Secretary, University of Edinburgh, Old College, South Bridge, Edinburgh.

Closing date for application 3rd September, 1979. Please quote reference 5034.(9489).

If you understand electronics...

Writing about electronic equipment is a fascinating and challenging career – especially when you're working with the sophisticated equipment that we produce at EMI.

Coming to EMI means joining one of our small informal, but highly professional teams, becoming totally involved in the development lifecycle of our major projects. With EMI training for this interesting and expanding field, you will be producing not only manuals, but the whole range of product literature both internal and external, and enjoying the opportunity to contribute your experience to our development activities.

You will therefore liaise with designers, engineers and draughtsmen on technical matters, and you should have developed considerable working experience in an electronics environment, ideally one connected with defence or industrial electronics utilising techniques such as micro-processor, miniature radar, infra-red and electro-optics. An ONC/HNC would be an appropriate qualification.

EMI offers excellent salaries dependant on your experience, and a full range of valuable benefits including relocation allowance where appropriate, and discounts off Group products and services.

Please telephone or send the coupon to K.D. Wilsher, Personnel Department, EMI Limited, FREEPOST (no stamp required), 135 Blyth Road, Hayes, Middlesex. Tel: 01-573 3888 or call Record-a-Call anytime on 01-573 5524.

...you've got something to write about as a Technical Author with EMI

To: K.D. Wilsher, Personnel Department, EMI Limited, FREEPOST, 135 Blyth Road, Hayes, Middlesex.

Name _____

Address _____

My experience includes _____

Ref: KDW

Hayes (Middx), Feltham, Woking, Camberley, Wells (Somerset)

EMI

EMI Electronics Limited

ONC? This is no ordinary maintenance job

The Philips Research Laboratories near Redhill in Surrey are one of Europe's most advanced electronics research establishments.

So it follows that our labs, benches and test areas are packed with advanced, professional equipment — oscilloscopes, pulse generators, digital equipment, recorders and so on. It also follows that maintaining and calibrating that equipment has to take a very high priority in an organisation such as ours.

If you're a man or woman who's reached at least Tech 3 or ONC and you've handled electronics repair work, moving to Philips Research would give you new and

interesting work experience, and bring you into an electronics environment where new things are happening all the time. Even if you already have full experience of our type of equipment, we can still give you plenty of fresh experience.

And of course, you'll enjoy all the benefits and future job opportunities you only find with an international organisation the size of Philips.

If you're looking for a maintenance job that's way above the ordinary, phone our Personnel Manager, Mr. Malpass, on Horley (029 34) 5544, or write to him at Philips Research Laboratories, Cross Oak Lane, Redhill, Surrey.



Research
Laboratories

PHILIPS

INSTITUTE OF PSYCHIATRY DEPARTMENT OF NEUROLOGY

Applications are invited for the post of Medical Laboratory

SENIOR SCIENTIFIC OFFICER

Duties will include designing new electronic equipment to expand a physiological laboratory and installing a PDP 11/34 computer to complement an existing PDP 12. Candidates are expected to have experience with computer programming and microprocessors. Involvement with research projects on the physiology of movement will be encouraged.

Whitley Council Terms and Conditions with starting salary, according to qualifications and experience, in the range £4701 p.a. - £6123 p.a. including London Weighting £354 p.a. (This salary range is under review.)

For application form please write to the Deputy Secretary, Institute of Psychiatry, De Crespigny Park, Denmark Hill, London SE5 8AF, or telephone 01-703 5411, ext. 214 quoting reference CDM/WW. (9626)

TOP JOBS IN ELECTRONICS

Posts in Computers, Medical, Comms, etc. ONC to Ph.D. Free service.

Phone or write: BUREAUTECH AGY, 46 SELVAGE LANE, LONDON, NW7. 01-959 3517. (8994)

Electronics Service Engineer

Imaging Instrumentation

Searle Medical, a Company within the G. D. Searle Group, markets a wide range of advanced electronic equipment having applications throughout the medical field.

A Customer Service Engineer, with an electronics/physics background, is now required to join a high technology imaging instrumentation group at the Company's headquarters in High Wycombe.

Responsibilities will include the commissioning and testing of new installations of nuclear and ultrasound imaging equipment, using state-of-the-art micro-computing techniques, and maintaining a high level of post-installation customer service engineering.

A good salary will be offered in line with experience and ability and benefits include a company car and expenses. Full product training will be given and the appointment is open to both men and women.

Write for an application form to Mr. J. N. Williams, G. D. Searle & Co. Ltd., P.O. Box 53, Lane End Road, High Wycombe, Bucks HP12 4HL.

(9496)



SEARLE



ROHDE & SCHWARZ

Independent concern

4,500 employees internationally represented in 80 countries require

SENIOR TEST AND CALIBRATION ENGINEERS

With a background in RF and microwaves, experienced in analogue, digital techniques, logic and microprocessor controlled ATE.

also vacancies exist for

TEST & CALIBRATION ENGINEERS

with knowledge on one or more of the above techniques.

We offer an exceptional salary ★ Performance related bonus scheme ★ Training abroad ★ Prospects of promotion ★ A wide variety of work ★ A happy atmosphere ★ Non-contributory pension scheme ★ Subsidised restaurant.

Please write or phone to:

Mr. Z. Eres (Technical Manager) extension 43.

Electronic Instruments & Communications Equipment

aveley
electric LTD



Roebuck Road, Chessington, Surrey KT9 1LP
Tel: 01-397 8771. Telex: 928479 Aveley (9492)

UNIVERSITY OF LEEDS

ELECTRONICS TECHNICIAN (Grade 3)

The person appointed would be required, under the supervision of the Electronics Engineer, to assist in the construction and maintenance of electronic equipment associated with the research and teaching of biological studies. Must be capable of working from circuit diagrams and sketches. Applicants should hold ONC or equivalent qualifications and relevant experience.

Salary on the scale £2931-£3336 (under review), according to age and qualifications.

Applications stating age, qualifications and full experience, together with the names and addresses of two referees should be addressed to: Mr. E. French, Departmental Superintendent, Department of Physiology, The Worsley Medical and Dental Building, University of Leeds, LEEDS LS2 9NQ. (9617)

Overseas Installations and Commissioning Staff

Vacancies exist for all levels of technical staff to work world-wide on strategic HF radio installations. All posts are permanent and are based in Bracknell, Berkshire.

Extensive overseas travel is necessary on unaccompanied tours of up to 90 days. Generous leave breaks apply, plus the opportunity for UK-based familiarisation and refresher training.

Installation/Commissioning Engineer vacancies up to **Principal Engineer** status.

All positions will require relevant academic qualifications, plus considerable field experience for the senior positions. A knowledge of modern circuit technology and HF/VHF experience is required.

Antenna Installation Supervisor

Previous rigging and mast experience is a necessity for this post, together with an ability to supervise field crews. Candidates should have extensive experience in modern HF antenna systems. (eg Log Periodic Antennas).

Customer Liaison/Commissioning Engineers

In addition to the requirements outlined above, candidates will also need the ability to liaise with customers

and represent the Company at a high level.

These posts require previous experience, ideally in a similar capacity, and a confident ability to work on one's own.

Installations Technicians

A craft apprenticeship or Forces experience would provide the ideal background. Good craft ability in prototype wiring and assembly of electronic equipments is required, together with the ability to use tools and work to high standards of modern installation practice.

All the above positions carry an excellent salary and benefits package, including overseas allowances and free overseas accommodation. Full medical insurance is also provided.

Please apply in writing, with brief career details to date, to:

Personnel Manager,
Racal Communications Limited, Western Road,
BRACKNELL, Berkshire.

or

Telephone for an application form to:
BRACKNELL (0344) 3244 Ext. 149.

Britain's fastest growing electronics group

RACAL

AUDIO + VIDEO LTD.



VTR ENGINEER

We require a VTR Engineer, preferably with broadcast experience, to service and maintain RCA and Ampex 2" Quad machines. A working knowledge of the Rank Cintel Mark III Telecine equipment would be an advantage.

Other in-house facilities include Marconi DICE Standards Converter, TBCs and a multitude of helical scan machines, and so the work can often be varied.

Please ring Mr. C. J. Carroll and have an informal chat about the work, salary and holidays, etc.

(9605)

ELECTRONICS PRODUCTION

ENGINEERS AND TECHNICIANS

Dolby Laboratories, the successful and progressive London manufacturers of professional audio noise reduction equipment, require production engineering staff. Duties will include the design and fabrication of test and assembly equipment, method study and application of techniques to maximise production from a limited area.

Qualifications: Several years' experience in electronics manufacture, appropriate academic qualifications and the ability to work projects through to successful conclusions without close supervision.

Competitive salaries and excellent employment conditions are offered.

For application form, contact:



Paul Garrard
DOLBY LABORATORIES, INC.
346 Clapham Road, London, S.W.9
01-720 1111

(9329)



MINNESOTA 3M RESEARCH LIMITED

CREATIVE ELECTRONIC EQUIPMENT DESIGNER

We have a vacancy in our Physics and Systems Research Group for a person with an interest in applying the latest electronic techniques in the design and construction of novel instrumentation for a wide variety of research projects. Current programmes include dielectric measurements, electrolytic processes, particle size measurement and methods of process control. The broad interests of this Laboratory require that the successful candidate show initiative and genuine creativity in developing the specialized equipment required. Some knowledge of and interest in Physics or Chemistry would be an advantage.

The attractive salary offered will reflect experience and academic qualifications. The Company operates generous pension, life assurance and sickness benefit schemes, and above all, offers good future prospects.

The 3M Company world-wide invests millions of pounds in research programmes each year. This has been, and will continue to be, a major factor in the Company's success.

Please apply in writing, giving brief details of qualifications and experience to:

**Administrative Manager
MINNESOTA 3M RESEARCH LIMITED
The Pinnacles, Harlow, Essex CM17 0HL**

(9638)

UNIVERSITY OF SURREY

ELECTRONICS TECHNICIAN

Grade 5

DEPARTMENT OF PHYSICS

A vacancy exists in the Electronics Workshop of the above Department. The Workshop is responsible for the development, construction, repair and calibration of analogue and digital equipment used for both research and teaching. Whilst qualification to HHNC or final year City and Guilds will be required, emphasis will be placed on a broad background experience. The post will offer an opportunity to help develop microprocessor systems. Further particulars and application form may be obtained from the Staff Officer, University of Surrey, Guildford, Surrey GU2 5XH, or telephone Guildford 71281 ext. 452. (9615)

CHELSEA COLLEGE
University of London
Electronics Workshop

DEPUTY SUPERVISOR

(Grade 6)

ELECTRONICS TECHNICIAN/ENGINEER (Grade 5) and ELECTRONICS TECHNICIAN (Grade 3) required for interesting work for Electronics and Physics Research and Teaching includes prototype instrument design, development and construction and the servicing and repair of commercial electronic equipment.

Experience and qualifications in Electronics at an appropriate level are essential. Generous holidays. Day release for approved further study can be arranged at Grade 3. Inclusive salaries (under review).

Grade 6 £4508 to £5282 p.a.
Grade 5 £3998 to £4580 p.a.
Grade 3 £3455 to £3860 p.a.

Further details and application forms from: Mr. M. E. Cane (E.W.), Chelsea College, Pulton Place, London SW6 5PR. (9642)

Royal Holloway College
(University of London)
Egham Hill, Egham, Surrey

TECHNICIAN

required by the departments of Computer Science and Computer Services. The technician will be in his early to mid-twenties with O.N.C. standard electronics or any similar training or experience and will undergo further in-house and day-release training, particularly in computer programming. The appointment will be on the University Technician Grade 4 or 5 depending on age and experience, that is £3500-£4300 including London weighting. Further details can be obtained from the Personnel Officer. (WW). (9497)

Electronic Test Engineers

TO £4800 p/a

We manufacture and market audio noise reduction equipment which is used by major recording companies, recording studios and broadcasting authorities throughout the world and have enjoyed successful growth since incorporation in 1968.

The increased demand for our equipment in the recording and cinema industries has necessitated the recruitment of experienced test engineers.

If you have practical knowledge and experience of electronic testing, think you can test, calibrate and troubleshoot our sophisticated equipment and enjoy the challenge of quality and delivery pressures telephone Tony Hill 01-720 1111.



Dolby Laboratories Inc
346 Clapham Road
London SW9 9AP
Telephone 01-720 1111

(9372)

BRIGHTON POLYTECHNIC

LEARNING RESOURCES



VTR ENGINEER

£4245-£5073 per annum
(plus 1979 salary award)

Unique opportunity to work in the forefront of helical vtr developments: using new 1" high band, broadcast 3/4" and all consumer formats: requiring a qualified engineer to work to broadcast standards but interested in working with all vtr formats.

Further details and application forms from Personnel Officer, Brighton Polytechnic, Moulsecomb, Brighton. BN2 4GJ. Tel: Brighton 693655 ext 2536. To be returned as soon as possible.

Electronics & Computer Test To £7,500

Use your C&G/ONC/HNC/Forces Training and good DIGITAL/ANALOGUE/RF experience to advantage. Working with state-of-the-art MINI/MICRO PROCESSOR; LASER; ATE; COMMUNICATIONS; NUCLEONIC; CCTV and similar equipment. Most UK areas; from Technician to Manager.

For free confidential counselling and practical career advice contact GRANT WILSON ref: GW470.

TECHNOMARK, 11 Westbourne Grove, London W2 4UA.
Tel: 01-229 9239 (01-229 4218 - 24 hrs).
Engineering Recruitment Consultants.

ICAO Seeks Aviation Specialists

THE CHALLENGE

Over the next six months we will be hiring more than 170 aviation specialists for short and medium-term assignments in Africa, Asia, Latin America and the Middle East.

We are looking for very expert, very experienced technical specialists who have good academic degrees or equivalent high professional qualifications, together with a minimum of ten years' practical aviation experience, at least half of it in the specific area of specialisation. Obviously with this experience requirement we don't expect applicants to be much below the age of 35. There is no upper limit as long as you are young in spirit and in good health.

THE ORGANISATION

We are the International Civil Aviation Organisation (ICAO), and we administer a technical assistance operation funded in main part by the United Nations Development Programme. Our expenditures this year will be close to (U.S.) \$50 million, and we shall be helping more than 75 developing countries.

THE JOBS

We are looking particularly for **electronics engineers** and **electronics technicians** (technical officers) who are highly qualified in one or more of the following fields:

- Aeronautical Communications
- Aeronautical Radar
- Aeronautical Navigation Aids

THE TERMS

We pay good salaries, ranging from (U.S.) \$28,000 to \$44,000 before taxes, depending upon the job. The cost-of-living allowance depends on the duty station. For example, currently for an expert with dependants: \$12,940 to \$17,730 in Jordan and Venezuela, \$7,470 to \$10,240 in Nigeria, \$6,370 to \$8,740 in Malaysia. Plus: Installation grants, travel for dependants, education grants and six weeks' leave per year with home leave after two years.

If you have the necessary experience and ability, and if you or your employer would like to help a country develop its citizens and resources—while you accumulate valuable international experience—send your résumé to:

**Technical Assistance Recruitment
International Civil Aviation Organisation
1000 Sherbrooke Street West
Montreal, Quebec, Canada H3A 2R2**



(9494)

Service Engineers

Greenford, Middlesex

Sansui manufacture some of the most sophisticated equipment, and are rapidly making inroads into the U.K. market. To keep in line with current expansion, they now need two Service Engineers for their new service department in Greenford.

You will be involved in the repair and maintenance of our product range which includes speakers, turntables, amplifiers etc. If you're qualified to City & Guilds or possess a similar qualification, so much the better. But experience will be considered as important.

Salary will very much be dependant on age and experience but will reflect the importance of the job. To find out more, telephone or write to:-

Peter Gibson, Sansui Audio Europe N.V.,
Unit 10A,
Lyon Industrial Estate,
Rockware Avenue,
Greenford, Middlesex,
UB6 0AA.

Only Hi-Fi, everything Hi-Fi.

(9602)

ELECTRONIC ENGINEERS

The BBC requires experienced electronic engineers to maintain Videotape equipment in its West London premises. These staff work a 7-day fortnight shift pattern.

In addition to possessing a degree in Electrical Engineering, Electronics or Applied Physics, HNC/HND (Electrical) or City & Guilds full Technological certificate in Telecomms., applicants, male or female, must have a thorough understanding of Television Broadcast Systems and be experienced in the maintenance of Videotape equipment.

Starting salary is between £6,350 and £6,913 (including shift allowance).

For further details and application forms, please ring Ray Bell 01-743 8000 extension 2308.

(9495)

ENGINEER

The BBC requires an Engineer in the Semiconductor Unit of its Valve Section, Mottspur Park, Surrey. The Engineer deals with technical enquiries and is involved in all aspects of the acquisition from manufacturers and the distribution throughout the Corporation of a wide range of solid state devices. Candidates, male or female, should have a Degree or H.N.C. and be experienced in the use of transistors, integrated circuits, etc. and/or be able to demonstrate an in depth knowledge of modern devices.

The salary will be in the range of £6955/£8405 per annum depending on experience. Other benefits include modern pension scheme, 23 days' annual leave, luncheon vouchers and assistance with removal expenses where appropriate.

Requests for application forms to the **Engineering Recruitment Officer BBC, Broadcasting House, London W1A 1AA**, quoting Reference Number 79.E. 2314/WW.



(9629/)

THE POLYTECHNIC, HUDDERSFIELD
COMPUTING AND AUDIO VISUAL SERVICES DIVISION

TECHNICAL OFFICER

(Audio Visual)
T3 £3732-£4146 Ref NT417 B/WW

A Technical Officer is required to take responsibility for all radio and TV work within the audio visual services. He/she will lead a small team of Technicians, involved in a variety of audio visual work. Experience of colour TV equipment, including vtr's and cameras is essential, as is C&G 101 or equivalent qualifications. Experience of TV studio and production work is also desirable.

Application forms, obtainable from The Personnel Office, The Polytechnic, Queensgate, Huddersfield HD1 3DH. Telephone Huddersfield 22288, ext. 2223, should be returned by 29th August, 1979.

(9488)

AMPEX

Ampex Corporation, a world leader in analogue and digital data recording technology, has been designated the official supplier of video recording and magnetic tape products to the 1980 Moscow Olympics. The Group's UK companies now seek:

... ENGINEERS

with broadcast television equipment experience, for their International Systems department which prepares proposals, designs and produces outside broadcast vans and television systems. Interest and challenge for dedicated engineers with possibility of travel overseas.

... CUSTOMER SUPPORT ENGINEERS

to maintain digital or analogue recording equipment throughout the United Kingdom.

These positions are based in Reading. The usual International Company benefits apply including Pension Plan and Life Assurance. Please contact **Joan Feaver, Ampex Great Britain Limited, Acre Road, Reading, Berks. Telephone 0734-85200.**

(9622)

CATV CHIEF ENGINEER

Canada's most advanced CATV manufacturer requires a chief engineer with a solid background in RF and CATV design or related electronic experience. An exciting career opportunity for a highly technical innovative person eager and willing to learn and adapt to new technology in an expanding and stimulating field. Related RF, Passive, Digital, Microwave experience would be valuable to us.

This is a senior position with commensurate salary and a wide range of company benefits.

Situated in Ontario we have beautiful mountains, excellent housing and schooling and superb recreational facilities. An ideal place to bring up the family in an unspoilt area of Canada.

Please forward resumé with salary history and expectations in confidence to:

**Mr. Thomas
LINDSAY SPECIALITY PRODUCTS**

50 Mary Street West
Lindsay, Ontario, Canada K9V4S7
Tel. Area Code 705 324 2196

(9648)

COME TO THE SUNNY SOUTH COAST

We require the following personnel in the areas: Hampshire, Dorset, Sussex, Somerset, Wiltshire and Berkshire.

**ATE Engineers
Control Engineers
Electronic Design Engineers
IC Development Engineers
Production Engineers
Microprocessor Engineers
Sales Engineers
Software Specialists
System Design Engineers
Test Engineers**

**Buyers
Electro Mechanical/
PCB Draughtsmen
Instrumentation Engineers
Physicists
Microwave Engineers
Service Engineers
Software Programmers
Technical Authors
Q.A. Engineers**

All these positions offer excellent salaries and in most cases relocation expenses.

Please write or ring: **CBS Appointments, 224 Old Christchurch Road, Bournemouth, Bournemouth 292155.** (24-hour Ansaphone Service—Agy.).

(9416)

**LEEDS CITY COUNCIL
Department of Education
Leeds Polytechnic
Educational Unit**

SENIOR TECHNICIAN

(ELECTRONICS)

Ref. 188/10 T 3/4 £3732-£4632 + Technicians qualification allowance. Required to service and maintain high grade electronics equipment used in the various schools of the Polytechnic in their teaching work to a wide range of courses. Knowledge of micro-electronics technology would be an advantage.

Application forms quoting reference number from the Administrative Services Officer, Leeds Polytechnic, Calverley Street, Leeds LS1 3HE. Closing date 14 days' after appearance of advert.

(9644)

CAPITAL APPTS.

FREE LISTS

101 Design/Development and Test Jobs
Permanent and Contract

To £6,000

(8782)

637 5551 day; 636 9659 eve.

ELECTRONICS ENGINEERS to £14,000, Microwave/RF design to £250 pw, microwave/RF test to £220 pw, digital, analogue, communications and computer engineers, design/test/service to £230 pw, for long (2 years) lucrative contracts at many sites throughout southern England. — Roger Howard, C.Eng, M.I.E.E., Cliveden Consultants (CRC), 99 St Leonards Road, Windsor (07533) 57818, answerphone. (9640)

APPOINTMENTS IN ELECTRONICS £5 - £10,000

Take your pick of the permanent posts in:

**MISSILES — MEDICAL COMPUTERS
RADAR — COMMS
MICROPROCESSOR
HARDWARE — SOFTWARE**

For free expert advice and immediate action on salary and career improvement, phone or write to, Mike Gernat@BSC.

Technomark

Engineering and Technical Recruitment

11 Westbourne Grove
London W2. 01-229 9239

(9257)



CAPITAL APPOINTMENTS LTD.

FREE JOBS LIST

for **FIELD SERVICE ENGINEERS**
BASIC SALARIES TO £7,000 + CAR

(8781)

30 Windmill Street, London. W1
01-637 5551

ARE YOU UP FRONT—

Technologically speaking? If not trust yourselves to the tender hands of "Charles Angels" (Judy, Anne and Dawn) and our buddy "EINSTEIN" (A compucolor II information retrieval system).

CURRENT VACANCIES INCLUDE

Design development engineers to join a new products group — a "thorn in the flesh" to an industrial giant working on the latest intelligent terminals for TV applications. Very sophisticated audio telephone techniques and a wide range of microprocessors (4 bit - 16 bit) in use. Salary to £9,000 area. Ring and find out.

Commercial-aware Boffin to research futuristic data channels, application of CAD techniques to real design, circuit synthesis, digital coding and researching into high density recording. Intellectual dexterity in physical sciences essential. Area: Middlesex. Salary: "Wot 'e's werf."

Technological Think Tank Boffs, i.e. pretty authoritative engineers to augment a team who have produced some of the most advanced satellite communications and radar systems of the century. To £10,000 for expertise in either computer controlled message switching, servo systems, Microwave systems or VHF/UHF equipment, Berks.

Young graduate to join a high powered firm of telecommunication consultants involved in: research, planning and information retrieval for public and private sector of industry. Intellectual dexterity essential. London. Excellent salary.

ALWAYS IN DEMAND

Electronic engineers for design, development, post design, production control, quality assurance, field trials, systems test, computer field service, test installation and commissioning. Note our success rate is between 70 and 80% of engineers placed.

For further details, please contact:

Charles Airey Associates

"PROBABLY THE BEST KNOWN SUPPLIER OF ELECTRONICS ENGINEERS IN THE COUNTRY"
FINANCIAL TIMES
155 KNIGHTSBRIDGE, LONDON, SW1. TEL: 01-581 0286

(9643)

TEST/QUALITY ASSURANCE ENGINEERS

Test/quality assurance engineers at senior and intermediate level wanted to work on our range of advanced broadcast television studio products including colour and monochrome television studio cameras.

Applicants should have an up to date knowledge of digital and linear circuit techniques gained from experience working on television studio equipment, radar equipment or similar sophisticated products, and qualified to HND, HNC or equivalent level.

Employment benefits include excellent salary, generous holidays, free life and health insurance, pension scheme, staff restaurant and relocation expenses.

Please apply for further details and application forms to Jean Smith at the address given below.



Advanced Broadcasting Equipment


LINK
ELECTRONICS

Link Electronics Limited,
North Way, Andover,
Hants, SP10 5AJ.

Telephone: (0264) 61345

(9601)

Professional Careers in Electronics

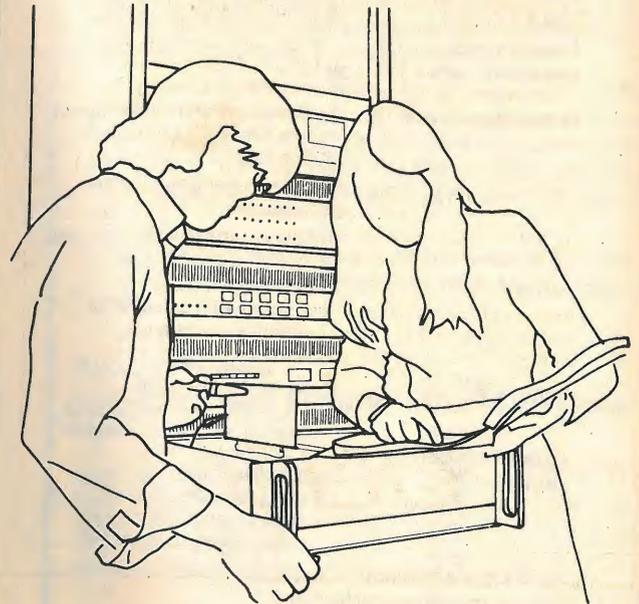

All the others are measured by us...

At Marconi Instruments we ensure that the very best of innovative design is used on our range of communications test instruments and A.T.E. We have a number of interesting opportunities in our Design, Production and Service Departments and we can offer attractive salaries, productivity bonus, pension and sick pay schemes together with help over relocation. If you are interested to hear more, please fill in the following details:-

Name _____ Age _____

Address _____

Telephone Work/Home (if convenient) _____

Years of experience 0-1 1-3 3-6 Over 6

Present salary £2,500- £3,500- £4,500- over
 3,500 4,500 5,500 £5,500

Qualifications None C & G HNC Degree

Present job _____

Return this coupon to John Prodger, Marconi Instruments Limited, FREEPOST, St. Albans, Herts, AL4 0BR. Tel: St Albans 59292

Marconi Instruments

A GEC MARCONI ELECTRONICS COMPANY

(9200)

Electronics Technicians

The job ? * Servicing and calibrating complex electronic equipment.

How much could I learn ? * £5600 plus per annum.

Overtime at premium rates ? * YES

Other benefits ? * Generous Holidays increasing with Service
* Sick Pay,
* Superior Pension Scheme
* Restaurant
* Relocation assistance, etc. etc.
* Assistance with Local Authority housing accommodation could, in certain circumstances, be made available.

Where ? * NEASDEN, N.W.10.
(Opposite the Underground Station, and close to the M.1.)

Qualification required ? * CONSIDERABLE practical knowledge and experience of electronic circuitry faults diagnosis and rectification.

For further information please telephone, call or write to
R. F. Honnor Personnel Manager
G & E Bradley Limited,
Electral House, Neasden Lane,
London NW10 1RR.
Telephone: 01-450 7811

Bradley Electronics

A Lucas Company

9649

ELECTROSONIC

PRODUCTION TEST / FAULT-FINDING ENGINEERS



c. £4,500

Electrosonic Ltd. is a leading company in the expanding fields of lighting control equipment and audio visual systems.

The Company, based at Charlton within easy reach of rural Kent, offers an attractive working environment and excellent conditions of employment.

PRODUCTION TEST/FAULT-FINDING ENGINEERS: Engineers are required for a small batch production line and system testing / fault finding on a wide range of electronic equipment employing some of the latest digital, analogue and audio circuitry.

Applicants should have either experience in the testing / fault finding of electronic equipment or academic qualifications to HNC or degree level. Suitable applicants will find opportunities for advancement to higher paid technical support positions in the Company's software or hardware design teams and project engineering section after a period in the Test Department.

SERVICE ENGINEERS/HIRE DEPT. ENGINEERS: Engineers are also required for fault finding and presentation work on the above equipment both in — company and on customer's premises.

Applications in writing, giving a resume of career to date, addressed to: **P. W. Way, Production Director, ELECTROSONIC LTD., 815 Woolwich Road, LONDON, SE7 8LT. Tel: 01-855 1101.**

(9651)

MID-CAREER RETRAINING

in Electronics Design

If you have substantial electronics design engineering experience but perhaps have not been working on the frontiers — don't despair. We can offer a thorough formal training scheme (fully paid) of twelve weeks duration to update you on some of the most recent developments in electronics. After successfully completing this, you would be working on the design and development of solid state analogue control systems, power converters, etc.

Sperry Gyroscope can offer the employment benefits expected of a successful major company operating in an advanced technology environment including realistic relocation expenses where applicable.

To find out more contact Viv Moss, Personnel Dept., Sperry Gyroscope, Downshire Way, Bracknell, Berks RG12 1QL. Telephone Bracknell (0344) 3222 ext. 512 or 199. Quote ref. WW 18779



(9611)

The Polytechnic of North London

Educational Development Service

EQUIPMENT TECHNICIAN

Grade 6

The Educational Development Service provides a comprehensive AV service throughout the Polytechnic. We require an experienced Equipment Technician to perform technical and administrative functions in the Service:—

To manage the physical resources of the Service and assist and deputise for the Chief Technician as required:

To establish a service routine for AV equipment and maintain service records:

To establish technical standards and assist production staff using AV equipment:

To help to train and supervise various staff using AV equipment:
To develop existing AV systems and advise on the purchase of new equipment.

An HNC or equivalent qualification is required and a minimum of nine years' relevant experience (including training period).
Salary Scale: £4509-£5283 inclusive of London Weighting.

Application forms can be obtained from the Chief Technician, Educational Development Service, The Polytechnic of North London, Holloway, London N7 8DB.

(9490)

Imperial War Museum

LONDON

Audio Technician

The Museum illustrates and records all aspects of the two world wars and all other military operations involving Britain and the Commonwealth since 1914. This post is in the Department of Sound Records, where the technical operations are based on a Sound Suite incorporating Leever's-Rich E200 and Revox tape machines, disc reproducers, a Neve BCM 10/2 mixing desk and ancillary facilities.

The technician appointed will be responsible for the control of studio recording, transfer operations, routine servicing and maintenance of all the audio equipment, some location recording, control of public listening facilities in the Museum and the provision and maintenance of certain archival lists and procedural records. In addition the successful candidate will work from old recordings and those produced on domestic equipment, and assist in the production of programme material for use in the Museum's public and educational services.

This post has been exempted from the Government's ban on recruitment.

Candidates must have an ONC in engineering TEC/SCOTEC Cert or C & G Pt II in a relevant subject or an equivalent or higher qualification, and an aggregate of at least 8 years' training (eg apprenticeships and/or full-time study) and experience. Practical experience of operating and maintaining audio equipment and a theoretical knowledge of sound recording essential.

Salary, starting at £4850 rises to £5390. **Salaries under review.** Non-contributory pension scheme.

For further details and an application form (to be returned by 5 September 1979) write to Civil Service Commission, Alencon Link, Basingstoke, Hants RG21 1JB, or telephone Basingstoke (0256) 68551 (answering service operates outside office hours). **Please quote ref: T/5127.**

(9498)

TELECOMMS TECHNICIANS/ENGINEERS

ABU DHABI

Al-Mariah United Company a fast growing telecommunications company has regular requirements for qualified and experienced personnel ranging from City and Guilds to Degree Level. Present requirements are for Telemetry Systems and VHF/UHF Radio Links CGLI Final and for a Senior Telecoms Engineer (married, accompanied or bachelors) of degree level.

Applications to Mr. George Fee, General Manager, 16 Hallview Grove, Darlington during August with copy to P.O. Box 206, Abu Dhabi with telephone contact. Full C.V. and if bachelor status interest. Usual expatriate terms and conditions.

(9636)

KINGSTON POLYTECHNIC TECHNICIAN

School of Electronic Engineering and Computer Science

The technician is required to support the work of the digital electronics laboratory. Duties include the servicing of electronic instruments and peripherals, and the development of digital sub-assemblies microprocessors experiments and digital experimentation.

Wide variety of interesting work in the forefront of digital techniques in both development and research. Applicants should have some knowledge of digital integrated circuits and preferably of logical techniques.
T2 grade £3600-£3972 inclusive (award pending).

Application forms from Assistant Registrar (Personnel), Kingston Polytechnic, Penrhyn Road, Kingston upon Thames KT1 2EE, 01-549 1366.

(9637)

Radio Officers

If you trade or training involves radio operating and you are no more than 35 years of age, you qualify to be considered for a Radio Officer post with the Composite Signals Organisation.

A number of vacancies will be available in 1979/80/81 for suitably qualified candidates to be appointed as Trainee Radio Officers. Candidates must have had at least 2 years radio operating experience or hold a PMG, MPT or MRGC certificate.

On successful completion of 40 weeks specialist training, appointees move to the Radio Officer Grade.

Salary Scales

Trainee Radio Officer	Radio Officer
Age	Age
19	20
20	21
21	22
22	23
23	24
24	25+
25+	

then by 5 annual increments to £6981 inclusive of shift working and Saturday, Sunday elements



for further details telephone Cheltenham 21491 ext 2269 or write to the address below

(9493)

GCHQ

Recruitment Office

Government Communications Headquarters

Oakley, Priors Road, Cheltenham GL52 5AJ

NATIONAL FILM SCHOOL

ELECTRONICS TECHNICIAN FOR VIDEO STUDIOS

Experienced in prototype construction, versed in analogue, digital and RF design, to assist video engineer in the establishment and operation of the new video production facility.

Knowledge of video an advantage but not essential.

Apply to Studio Manager for application form, Beaconsfield Studios, Station Road, Beaconsfield, Bucks.

TEL: BEACONSFIELD 71234 ext. 22

(9645)

SITUATIONS VACANT

Test Gear Engineer

Consumer Electronics

We have a vacancy for someone of HND/C (or equivalent) qualification in electronics, with a bias towards television and digital techniques, to join a team engaged in the design and construction of test gear for use in a manufacturing environment.

As well as a good theoretical and practical knowledge, the post demands the ability to apply the elements of circuit design and component technology to the production of test equipment to technical and commercial specification.

It is unlikely that we shall find someone with the necessary experience and creative flair outside the ranks of those already working in the field. Both men and women may apply.

The salary will reflect the job requirements and the calibre of person likely to fill it effectively. In addition, the situation affords a valuable opportunity to join a forward-looking company offering attractive conditions, including generous holiday entitlement, contracted-out pension arrangements, and the satisfaction of doing a technically interesting job located in a very pleasant part of the South Coast. (We will provide help to move here, where this is appropriate.)

Write, phone or call for application form: George Greaves, Senior Personnel Officer, ITT Consumer Products (UK) Ltd., Theaklen Drive, Hastings, Sussex. Tel: (0424) 437061.

ITT

World-wide Technology

The Royal Fleet Auxiliary requires Junior Radio Officers

Applications are invited for Junior Radio Officer vacancies which will be arising in the near future.

Applicants should possess MRGC and Radar Maintenance Certificate.

For further details and application form contact: The Careers Office, Royal Fleet Auxiliary DST (FMV) 74a, Room 705 Empress State Building, London SW6 1TR. Tel: 01-385 1244 ext 2192

Closing date for receipt of completed applications 5th September.

ROYAL FLEET AUXILIARY **RFA**

(9619)

ARTICLES FOR SALE

ANTIQUE MACHINES + CURIOSITIES

The world's first high quality glossy magazine devoted to mechanical and other collectables and curiosities of all types. Fifty-six page first issue out now price 95p including 16 pages in full colour and the unique collectors card index. Obtainable from your newsagent or direct from AM+C, 3 Heathcock Court, Strand WC2R 0PA. Telephone: 01-379 6025.

(9357)

THE SCIENTIFIC WIRE COMPANY

PO Box 30, London, E.4

ENAMELLED COPPER WIRE

SWG	1lb.	8oz.	4oz.	2oz.
10 to 19	2.65	1.45	.75	.60
20 to 29	2.85	1.65	.90	.70
30 to 34	3.05	1.75	1.00	.75
30 to 40	3.40	1.95	1.15	.84
41 to 43	4.55	2.55	1.95	1.30
44 to 46	5.05	3.05	2.15	1.70
47	8.00	5.00	3.00	1.80
48	15.00	9.00	6.00	3.30

SILVER PLATED COPPER WIRE

14 & 16	4.50	2.25	1.44	.90
20 & 22	5.00	2.85	1.74	1.06
24 & 26	5.70	3.31	2.00	1.22
28 & 30	6.67	3.86	2.35	1.44

Prices include P&P and VAT
S&E brings list of copper & resistance Wires
Dealer Enquiries Invited

(9063)

ARTICLES FOR SALE

NUMBER CRUNCHER KIT

Now you can add all the functions of a powerful calculator to your Z80 or SC/MP Microcomputer. Our MM57109 based kit includes quality PCB, all components, complete instructions and software. Only neat soldering is required to complete this kit. The kit as supplied interfaces to an unmodified Nascom 1.

Functions available include +, -, X, /, sine, arctang, logarithms and exponents. The design of the unit ensures that only a minimum amount of memory is required to perform complex calculations.

Complete Kit (inc. VAT) £38.75 + £1.25 p&p.

From:

Control and Electronic Developments, 719 Pinebank, Craigavon, Co. Armagh, N. Ireland. (9375)

FOR SALE: 24 band receiver RF8000 Super National Panasonic, unused, shop soiled only, value £2,000, will let go for £1,200. V.C.R. N.1700. Used, new cost £760, will let go for £350. Reusable 1 hour tapes available at £5 each. — Contact Morris 66455 (0223) office hours, 46274 after office hours. (9464)

SOLAR CELLS: bits, books and bargains. Send stamp for list or 95p for Solar Cell booklet and Data sheets. Edencombe Ltd 34 Nathans Road, North Wembley, Middlesex HA0 3RX. (8061)

Quartz Crystal Units
ACCURATE RELIABLE

Private enquiries, send 13p in stamps for brochure

THE QUARTZ CRYSTAL CO. LTD.
Q.C.C. WORKS, WELLINGTON CRESCENT
NEW MALDEN, SURREY. 01-942 0334 & 2985

8493

VALVES RADIO — T.V. Industrial-Transmitting. We dispatch valves to all parts of the world by return of post, air or sea mail, 2,700 types in stock 1930 to 1976. Obsolete types a speciality. List 20p. Quotation S.A.E. Open to callers Monday to Saturday 9.30 to 5.00. Closed Wednesday 1.00. We wish to purchase all types of new and boxed valves. Cox Radio (Sussex Ltd., Dept WW, The Parade, East Wittering, Sussex PO20 5BN, West Wittering 2023 (STD Code 024366). (9082)

INVERTERS High quality DC-AC. Also "no break" (2ms) static switch, 19" rack. Auto Charger.



COMPUTER POWER SYSTEMS
Interport Mains-Store Ltd.
POB 51, London W11 3BZ
Tel: 01-727 7042 or 0225 310916

(9101)

SCREEN PRINT SYSTEM. Prints labels, circuit boards, dials, front panels. Ready to operate, willing to train operator. About £200. — J. Waller, Dunstable Street, Ampt-hill, Beds. 0525 402279. (9635)

CM2506 DIGITAL CAPACITANCE meter 1pF-2uF, 5 ranges, 2 1/2 digits, 0.6in leds; acc. 0.5%. Assembled module only £20.75 plus VAT. — Precision Measurements, PO Box 70, 8 St Stephens Ct, Canterbury, Kent. (Callers by appointment). (9613)

PARTRIDGE ELECTRONICS

THE MIXER MANUFACTURERS OFFER

Electronics-panels-frames-etc. i.e. everything for high quality mixers, large or small, available as assembled and tested sub units or kits.

A. C. Partridge Limited
56 Fleet Road, Benfleet, Essex
Telephone (STD 03745) 3256
Access — Barclaycard

(9500)

G.W.M. RADIO LTD, 40/42 Portland Road, Worthing, Sussex. Tel. 0903 34897, for government and factory surplus second user and s/h equipment. Radio telephones for sale and wanted in large or small lots. Atlanta Marine Communication Receivers £115 plus carriage at cost. Avometers model 7 £31. Model 8 £43 inc. sound powered tele-phones with intrinsically safe circuits, unused. 40ft pneumatic masts by Scam Clark £321, in original unopened maker's box gross weight 4 cwt. Many one off items in stock. No lists, we are worth a visit. (9152)

SITUATIONS VACANT

SERVICE ENGINEERS

What's it to be...



Midnight in Moscow, or lunchtime in London?

That's the sort of choice you could be faced with at Linotype-Paul. We're a highly successful, high technology electronics company designing and manufacturing computer controlled phototypesetting systems for use by the world's printing and publishing industries.

As a service engineer you'll be called in to client locations almost anywhere in the world, it's a fact that our systems are used on Pravda, so the Moscow connection really does exist. What's more, you'll be responsible for repairing right down to component level on systems that are as sophisticated as they are varied - that means electronics, mechanical units, electrics, high precision optics, and computer peripherals, such as VDU's, tape readers and disc drives.

But don't worry, we'll give you full product and technology training and when an overseas assignment comes up, you'll be asked rather than told to go.

For the right men and women we're offering highly competitive salaries, first class benefits, a Cortina 1600 Saloon, plus excellent prospects for career advancement. Generous assistance with relocation will be available where necessary.

If you are qualified to HNC or above and have had several years relevant experience ring or write now to David Hilton, Personnel Manager, Linotype-Paul Ltd, Kingsbury Road, London NW9 8UT. Tel. 01-205 0123.

Linotype-Paul (9502)

ARTICLES FOR SALE

VERO 3E CARD FRAMES. Re-turbished, as new. Height 5U. Each with many extras: 15in, no case, £4; 19in inc case £10; 78-way W/W edge conns £1. — Details 048955355. (9612)

9 UNIT 7 SEGMENT CALCULATOR DISPLAYS 45p. Teleprinter 54s £35, and 75s £30. Spares etc. MKS, 27 Upper Stone Street, Maidstone, Kent. (9442)

LAB CLEARANCE: Signal Generators; Bridges; Waveform, transistor analysers; calibrators; standards; millivoltmeters; dynamometers; KW meters; oscilloscopes; recorders; Thermal, sweep low distortion true RMS, audio FR, deviation. Tel. 040-376236. (6250)

GENUINE original RGD radiogram. 1046 G, perfect working order. Offers: Jackson, 235 Winstanley Drive, Leicester. Tel 824405. (9625)

TV TUBE REBUILDING

Top quality professional plant and equipment, and leading consultants, for complete plant or upgrading and for training and all supplies.

**WESTERN WHYBROW
ENGINEERING**
TEL. (0736) 762265

TELEPRINTERS

5/Level Receive Only Creed Envoy's, seen working and purchased as viewed, mounted in sound proof metal cabinet. £85 each.

ASSOCIATED PRESS LTD.
83/86 Farringdon Street, London
EC4.
01-353 1515 Ext. 212

THE MESSAGE IS...

We are Europe's leading exporters of two-way radio communications systems and can offer you the opportunity to work on innovative, high technology projects, in some of the best equipped Development Laboratories in the country.

Development Engineers

We are looking for Degree or possibly HND level Electronic Engineers to work on sophisticated mobile radio equipment at our new headquarters in Cambridge. You would join teams working on fixed, portable, mobile or link products and sub-units, and you should have two years or more development experience on VHF/UHF communications equipment or low/medium capacity multiplex radio links.

LOUD AND CLEAR

Electronic Designer

With about ten years relevant design experience is also required, to make a major contribution to a project team developing low capacity FDM/PCM radio links.

Successful applicants (of either sex) will be offered attractive salaries, generous benefits and relocation expenses. Both the working and living environments are particularly good, and there are opportunities for career development within the Company and in the wider scope of the Philips Group.

For more information and an application form, contact: Alan Depauw, extension 305, at the address below.

(9499)



Pye Telecommunications Ltd

St Andrews Road Cambridge England CB4 1DP
Tel: Cambridge (0223) 61222 Telex: 81166PYE Telecom CAMBGE

A member of the Pye of Cambridge Group

ARTICLES FOR SALE

EXCLUSIVE OFFER

RACK MOUNTING CABINETS HIGHEST QUALITY 19"				
Ref	H"	Width"	Depth"	Price
PE	10	21	13	£10.00
LL10	54	21	18	£20.00
TT	64	25	26	£45.00
SL	71	25	26	£50.00
ST	85	22	24	£70.00

Racal cabinets for RA-17/117 £30.00
 Uniframe, single £30.00
 Uniframe, double £40.00
 Uniframe, triple £50.00

Over 60 types available from 12" to 90" high. Also bins, tripes and consoles. Above are only a few types. Please send for full list.

AUDIO AND INSTRUMENTATION-TAPE RECORDER-REPRODUCERS

- * Ferrograph YD 2 track 1/4"
- * Leavers-Rich 1/4" 2 track
- * Uher 1/4" 2 track
- * Ampex FR 1300
- * Plessey ID33 Digital Units, 7 track 1/2"
- * Plessey MS500 Digital Unit, 7 track 1/2"
- * Ampex FR-1100, 6 speeds, stereo 1/4"
- * Ampex FR600, 4 speeds, 7 track 1/4"
- * Ampex FR-1300 1/4" 7 track
- * Consolidated VR-3800 1/4" 7 track
- * Consolidated VR-3600 1" 14 track
- * D.R.J. RMI, 4 speeds, 4 track 1/4"
- * Minicom CMP-100, 6 speeds, 7 track 1/4", 1/2", 1"
- * Ampex 351 2 speed, 2 track 1/4"
- * 3M H, 4 speeds, 14 track 1"

Prices of above £70 to £500
Also Transport Decks only available

We have a large quantity of "bits and pieces" we cannot list - please send us your requirements, we can probably help - all enquiries answered.

RADIO RECEIVERS 0-4 G19/MCS by Marconi, Collins, Racal, T.M.C., G.E.C., Rhode & Schwarz, Polarad Eddystone, Nems Clarke, S.T.C., ETT. Lists available.

OSCILLOSCOPES TO 100 MHZ by Tektronix, Hewlett Packard, Telegroup, Solartron, Cossor, Rhode & Schwarz, Roband, etc. List available.

TEST EQUIPMENT by Rhode & Schwarz, Avo, Cintel, Dawe Bradley, Teleonic, Hewlett Packard, Racal, Saunders, Multihead, G.E.C., Mafaid, B & K, Solartron, Honeywell, Mesl, Airmec, Furze Hill, Plessey, etc.

SPECIAL MOBILE TOWER
80 feet high extended.
12 feet high closed.

Hydraulic operation with ladders and platform on top.

All mounted on Bedford 4-wheel-drive truck with self-levelling arrangements built in. Made to Ministry requirements.

MANUALS
We have a quantity of Technical Manuals of Electronic Equipment, not photostats, 1940 to 1960, British and American. No lists. Enquiries invited.

AERIAL EQUIPMENT ALL TO MINISTRY SPECIFICATIONS

- Lattice towers
- Lattice masts
- Sectional tubular masts
- Yagi arrays
- Log aperiodic arrays
- Aerial amplifiers
- Multi couplers
- Baluns
- Attenuators

LIST AVAILABLE

We have a varied assortment of industrial and professional Cathode Ray Tubes available. List on request.

PLEASE ADD CARRIAGE AND V.A.T.

P. HARRIS
ORGANFORD, DORSET, BH16 6BR
BOURNEMOUTH (0202) 765051

(9891)

ARTICLES FOR SALE

TO MANUFACTURERS, WHOLESALE & BULK BUYERS ONLY

Large quantities of Radio, T.V. and Electronic Components
RESISTORS CARBON & C/F 1/8, 1/4, 1/2, 1. 1 Watt from 1 ohm to 10 meg.

RESISTORS WIREWOUND. 1 1/2, 2, 3, 5, 10, 14, 25 Watt.

CAPACITORS. Silver mica, Polystyrene, Polyester, Disc Ceramics, Metalamite, C280, etc.

Convergence Pots, Slider Pots, Electrolytic condensers, Can Types, Axial, Radial, etc.

Transformers, chokes, hopts, tuners, speakers, cables, screened wires, connecting wires, screws, nuts, transistors, ICs, Diodes, etc., etc.

All at Knockout prices. Come and pay us a visit. Telephone 445 2713, 445 0749.

BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, N. Finchley, London, N.12. 5 mins. from Tally Ho Corner (9461)

Complete repair information, any requested T.V. £5 (with diagrams £5.50). Any service sheet requested for £1 plus S.A.E. S.A.E. brings newsletter and special offers - service sheets from 50p, bargain vouchers.

Unique Publications, Aus.(V), 76 Church Street, Larkhall, Lanarkshire.

TRANSFORMER PROBLEMS?

1VA-1KVA Prototypes in 7-10 days. Phone Vince Sellar on 06076-66716.

TRENT TRANSFORMERS LTD.

26 Derby Road
Long Eaton, Nottingham (8363)

SITUATIONS VACANT

Gallenkamp is a leading company in the laboratory equipment field, and a member of the Fisons Group.

We require two young

Electrical Test Engineers

to fill posts in our expanding Product Assurance Section

One post will involve the examination in detail of the apparatus which we sell and the specification of any modifications necessary to ensure that it meets our quality assurance requirements and United Kingdom and foreign electrical safety specifications.

Experience of electrical testing is essential and experience of testing to BS3456 or to similar international specifications would be an advantage.

The other post will primarily involve the measurement of radio interference levels and the specification of suitable suppression systems. Experience of electrical testing is essential and experience with BS800 or similar international specifications would be an advantage.

The work is in a modern, well equipped laboratory at our Head Office building near Moorgate Tube and Liverpool Street stations.

A good starting salary is offered, plus four weeks' holiday, subsidised staff restaurant and other benefits associated with a large company.

Please phone 01-247 3211 ext. 285 or write to Sarah Bramble, Recruitment Officer, A. Gallenkamp & Co. Ltd., P.O. Box 290, Technico House, Christopher Street, London EC2P 2ER.

Gallenkamp

(9478)

TELEVISION BROADCAST ENGINEER

We require an engineer to join the staff of a rapidly expanding video cassette duplicating facility. The candidate should have a minimum of three years' experience in broadcast television with specific knowledge of Quad and Helical Scan, VTRs, Flying Spot Telecines and related systems.

The candidate should be qualified to HNC, Full Technical Certificate, Degree or equivalent qualification. The job reports to the Technical Manager and the successful candidate will be responsible for maintenance of equipment, supervision of technical trainees and the installation of additional facilities.

High salary (level dependent upon experience and qualifications) plus normal benefits.

Please reply in confidence to:

Mr. Tony Owers



PERSONNEL & ELECTRONICS LTD.

Triumph House, 1096 Uxbridge Road, Hayes, Middlesex, UB4 8QH, England
Telephone: 01-573 8333 Telex: 934271

ARTICLES WANTED

WANTED!

all types of scrap and
**REDUNDANT
ELECTRONIC &
COMPUTER
MATERIALS**

with precious metal content

**TRANSISTORS
& PRINTED
CIRCUIT BOARDS
TO COMPLETE
COMPUTERS**

**THE COMMERCIAL
SMELTING &
REFINING Co. Ltd.**
171 FARRINGDON ROAD
LONDON, EC1R 3AL
Tel: 01-837 1475

Cables: COMSMELT, EC1
Works: FLECKNEY, Nr. LEICESTER

SPOT CASH

paid for all forms of electronics equipment and components.

F.R.G. General Supplies
550 Kingston Road, London
Tel: 01-404 5011
Telex: 24224 Quote Ref 3165
(8742)

WANTED RACAL ATTACHMENTS

MA350B and MA1350A Decade Frequency Generators.

MA259 Frequency Standard or Equivalent.

SA510 Frequency Standard.

RA66A or B Panoramic Adaptor.

RA137 or 237 LF Converter.

RA1218 Receiver plus associated attachments — RA337 — RA316 — RA298 —

RA366 — MA358 — MA397 —

MA350B — MA210

**ALL RACAL SPARES AND
EQUIPMENT WANTED**

JOHNS RADIO

424 Bradford Road, Batley, Yorks.
Tel: 0924 8159 (9.30 a.m. to 1 p.m.)
(9389)

WANTED

All your gold washed scrap. Plugs, sockets, edge connectors, P.C. boards, pins, etc.

We collect and pay cash for any amount from 1cwt.

Minimum price £100-£200 per cwt.

P. Skollern Metals, The Iron Yard (Est. 1935), Cutlers Green, Thaxted, Essex CM19 2PL. Telephone: Thaxted 830 862.

SPOT CASH for all types test equipment, receivers, transmitters, valves, components, cable and surplus electronic scrap. M. & B. Radio, 86 Bishopgate Street, Leeds LS1 4BB. 0532 35649. (8789)

STORAGE SPACE is expensive, why store redundant and obsolete equipment? For fast and efficient clearance of all test gear, power supplies, PC boards, components, etc., regardless of condition or quantities. Call 01-771 9413. (8209)

TURN YOUR SURPLUS Capacitors, transistors, etc. into cash. Contact COLES-HARDING & Co., 103 South Brink, Wisbech, Cambs. 0945-4188. Immediate settlement. We also welcome the opportunity to quote for complete factory clearance. (9509)

COIL WINDING

Large or small
PRODUCTION RUNS

AIRTRONICS LTD

GARDNER INDUSTRIAL ESTATE
KENT HOUSE LANE
BECKENHAM KENT BR3 1UG
01-659 1147
8936

PCB ARTWORK DESIGN SERVICE with component notation masters and assembly drawings. PADS Electrical Ltd, 01-850 6516, 45 Southwood Road, New Eltham SE9. (7905)

ELECTRONIC CIRCUIT Design and prototype construction production assembly. Test and PCB artwork design. Write: Powerline Electronics, High Street, Bognor Regis, Sussex PO21 1EZ or telephone STD 024-32 (Pagham) 66587 evenings. (8963)

SMALL BATCH productions wiring assembly to sample or drawings. Specialist in printed circuits assembly. Rock Electronics, 42 Bishopsgate, Harlow, Essex 0279 33018. (9094)

A COMPLETE SERVICE to manufacturers. Assembly, cable forming and testing. Also a prototype PCB service and component scheduling at competitive prices. Small or large runs with quick turn-round to high standards. Contact the professionals — Techtronic Services, Staincliffe Mills, Dewsbury, W. Yorks. Tel (0924) 409040 TX 556267. (9504)

CAPACITY AVAILABLE

I.H.S. SYSTEMS

Due to expansion of our manufacturing facilities we are able to undertake assembly and testing of circuit boards or complete units in addition to contract development.

We can produce, test and calibrate to a high standard digital analogue and RF equipment in batches of tens to thousands.

Telephone to arrange for one of our engineers to call and discuss your requirements, or send full details for a prompt quotation.

TEL. 01-253 4562

or reply to Box No. WW 8237
(8237)

MEKTON MINI BUS PCB strip. M822 — code 5-10-6, M823 — code 7-9-3, £25 per 100. Also thousands surplus 74 series IC's cheap. — Tel. (0329) 237362.

PRINTED CIRCUIT BOARDS: Complete service for manufacture of single and double sided boards. Design, artwork, photography, gold plating, drilling, screen printing. Assembly: P.C.B. assembly, wire wrapping. Complete construction, screen printing and engraving of panels. Design and development of electronic equipment. — Scope Advanced Systems Ltd., Dept A, 36 Singer Road, East Kilbride, Glasgow. 035-52-37112. (9474)

PRINTED CIRCUITS BOARDS. Quick deliveries, competitive prices. Quotations on request, roller thinning, drilling, etc. Speciality small batches. Larger quantities available. Jamieson Automatic Ltd., 1-5 Westgate, Bridlington, North Humberside. For the attention of J. Harrison (0262) 74738 or 77877. (9652)

ARTICLES FOR SALE

WORKSHOP CLEARANCE. Sale starts on August 27th-8th September. No correspondence please. Please phone 01-543 2515 or call in person. The store is at the rear of 550 Kingston Road, London SW20 8DR. Entrance from Edna Road, first alley left. Nearest tube station Wimbledon, Southern Railway Station, Raynes Park only 400 yards. Tektronix Oscilloscopes. 545B with CA unit plug-in, price £195; 544 with L plug-in unit £150; 545A with CA plug-in unit £175; 585 with 82 plug-in units £250; 585A with 82 plug-in units £350; Signal generator TF801D/8/S £195; R & S signal generator AM/FM type SMAF frequency 4-300 MHz £240; J-1A signal generator £15; 190A constant-Amplitude signal generator £50; Solartron digital voltmeter LM1420 £40; R&S UHF test receiver £75; HP 2410B AC/OHMS converter £50; HP 2539A digital comparator £50; HP 8875A differential amplifier (quantity 4) with main frame £50. Attenuator variable CT532 (TF2162) £45; Muirhead-Wigan decade oscillator type 890A, £85; HP oscilloscope 140B £275; Q-Meter TFI245 with TFI246 oscillator £395; 547 oscilloscope with 1A1 plug-in unit £375; 409 FM/AM modulation meter £170; TF2300A FM/AM modulation meter £350; TF791D deviation meter £95; Polyscop SWOB 1 wideband sweeper and display 0.5-2400 MHz 2 probes, handbook, £395; wave analyser 248 freq 5-300 MHz £45; 248A £150; 853 30 KHz-30 MHz £45; Cohu DC voltage calibrator type 303B £185; type 324A £295. Advance pulse generator PG52B £250; Constant voltage transformers 500W £15; 3 KW95, 5KW £120; Variac 8A £15; 3ph 20A £120; HP 606B HF signal generator 50 KHz 65 MHz £75; BNC to BNC50ohms cables length approx 7ft £1.50; Type N plug-in unit £60; Hewlett Packard electronic counter type 5245M with 2 frequency converters type 5253B, and 2590B, price negotiable; R&S noise generator freq. 3-1000 MHz £75; RF power meter TF1020A/5M1 50 ohms, 0-300 watts in two ranges £85; CT202 swept signal generator freq. approx 3-72MHz £15; Dynamic digital voltmeter DM20225 £60; 19in cabinet on castor wheels ht. approx 4in £50; as above but 4ft 11in approx £65; double pulse generator type 5002 £55; Solartron power supply 0-30v at 10A £75; HP type 624C x band signal generator £95; regulated high voltage power supply 0-3.4 KV £85; Philips power supply, type PE 1527, 0-150 volts, 3 amps, £195; Hughes travelling wave tube amplifier, L band, £250; Wayne Kerr Bridge Universal CT375 £25; CT530 with low impedance adaptor £75; UHF admittance bridge B801 with bridge sauce £50; Insulation tester (500V-15KV) CT318 £75; English Electric insulation tester 10 KV DC £45; Vacuum tube voltmeter TF1041B £19; Singer Spectrum analyser 10 MHz - 40 KMC £150; Variable delay unit, delay in nanoseconds (total 1110 ns) input 75 OHMS or 50 OHMS output 75 OHMS or 50 OHMS £95; pulse generator type GO 1101-2 £15; 24 MHz sweep signal generator TF1099/3S with probes £95, 180A time-mark generator £45. A parcel of glass envelope crystals qty. 3500 approx., price £350, or any individual freq. if available, £1 ea. Transistors BD121 30 ea, minimum order qty 100. Hp oscilloscope 140B with 1415A plug-in unit £550. HN to BNC adaptors £2 each. As this is a genuine clearance, on some units an offer will be considered. All prices exclusive of VAT and carriages. (9616)

COLOUR, UHF AND TV SPARES (miniature size 4 1/2 x 3 1/2 x 2 1/2). New Saw Filter IF Amplifier plus tuner (complete and tested for sound and vision, £28.50, p/p £1. TELETEXT, Ceefax and Oracle in Colour, Manor Supplies "easy to assemble". Teletext kit including Texas Tifax XM11 Decoder. External unit aerial input, no other connections to set. Wide range of facilities in colour include 7-channel selection, Mix, Newsflash and Update. (Price: Texas Tifax XM11 £130, Auxiliary Units £88, Case £14.80, p/p £2.50). Demonstration model at 172 West End Lane, NW6. Also latest Mullard Teletext 610LVM module available. Call, phone or write for further information. **COMBINED COLOUR BAR AND CROSS HATCH GENERATOR KIT** (MK 4) UHF aerial input type. Eight pal vertical colour bars, R-Y, B-Y, Grey scale etc. Push-button controls £35* p/p £1; Battery Holders £1.50*; Alternative Mains Supply Kit £4.80*; De Luxe Case £4.80*; Aluminium Case £2.60*. Built and tested (battery) in De Luxe Case £58*, p/p £1.20. **CROSS HATCH KIT**, UHF aerial input type, also gives peak white and black levels, battery operated £11* p/p 45p. Add-on Grey scale kit £2.90* p/p 35p; De Luxe Case £4.80*; Aluminium Case £2* p/p 85p. Built and tested in De Luxe Case £23.80* p/p £1.20. **UHF SIGNAL STRENGTH METER KIT** £16.80*, alum. Case £1.50*, De Luxe Case £4.80* p/p £1. **CRT TEST AND REACTIVATOR KIT** for Colour and Mono £20.80*, p/p £1.30; TV 625 IF Unit for Hi-fi amps or tape rec. £6.80, p/p 75p. Surplus Bush IF panels. A816 £2.80, TV312 (single IC) £5. BC5600 (Exp) £5, A823 (Exp) £2.80 p/p 85p. Bush A823 (A807) Decoder panel £7.50 p/p £1. A823 Scan Control panel £3.50, blue lat, 75p (Mullard also panel £3.80 p/p £1. Philips G6 single standard convergence unit £3.75 p/p 90p. GEC 2040 ex rental panels, Decoder £5, Time Base £5 p/p 90p. Thorn 3000 ex rental panels, Video, Decoder, frame, IF £5 p/p 90p. Colour Scan coils, Plessey £6, Yoke £3.50, blue lat, 76p (Mullard also available). Mono Scan coils Philips/Pye £2.80. Thorn £2.80 p/p 85p. Philips G8 Decoder panels, salvaged for spares £3.80 p/p 90p. Varicap UHF tuners gen. instr. £3.50, ELC 1043 £4.50, ELC1043/05 £5.50; Philips G8 £5.50 p/p 35p. Salvaged UHF Varicap tuners £1.50 p/p 35p. UHF/VHF ELC2000S Varicap tuner £8.50 p/p 65p. Varicap control units, 3 pos. £1.20, 4 pos. £1.50, 5 pos. £1.80, 6 pos. (special offer) £1.80, 7 pos. £3.80 p/p 45p. Touch Tune control unit Bush 6 pos. £5 p/p 75p. UHF transist tuners, rotary incl. slow motion drive £2.50, 4 pos. push button £2.50, 6 pos. push button £4.20 p/p £1. (Thorne, GEC, Bush, Decca, etc., special types available, details on request). Delay Lines DL20, DL5 £3.50, DL1 80p p/p 65p. Lumiance delay lines £1 p/p 40p. Helical pots 100K 4 for £1.20 p/p 30p. Remote Control Thorn-type Transmitter, receiver £2 pair p/p 45p. Large selection of lopts, trippers, mains droppers, and other spares for poplar makes of colour and mono receivers. **MANOR SUPPLIES, 172 WEST END LANE, WEST HAMPSTEAD, LONDON NW6, SHOP PREMISES, EASILY ACCESSIBLE, WEST HAMPSTEAD-BAKERLOO, JUBILEE TUBE, and BRITISH RAIL N. LONDON (RICHMOND-BROAD ST.) and ST. PANCRAS-BEDFORD. BUSES 28, 159, 2, 13. Callers welcome. Thousands of additional items available at shop premises not normally advertised. Open daily all week including Saturday (Thursday half-day). MAIL ORDER: 64 GOLDERS MANOR DRIVE, LONDON NW11 9HT. Tel. 01-794 8751. VAT. Please add 12 1/2% to ALL PRICES (EXCEPT WHERE MARKED * VAT 8%). (60)**

SOLAR CELLS 4in diameter, 2 amps, 4v \$6.75 each or 10 for \$65.00 plus shipping. — Kenneth Foster, 1742 Dowd St Louis, Missouri 63136, USA. (9621)

TELEPHONE ANSWERING machine available for outright purchase. — Telephone Burton-on-Trent (0283) 47427 (9609)

SOWTER TRANSFORMERS

WITH 37 YEARS' EXPERIENCE we have the expertise to design and manufacture ANY TYPE OF AUDIO TRANSFORMER AT THE RIGHT PRICE.

Whilst we specialise in every kind of transformer for audio control desks and mixers demands are increasing for **LOUDSPEAKER TRANSFORMERS** and **100 VOLT LINE AUDIO OUTPUT TRANSFORMERS** FOR MOST KINDS OF AMPLIFIERS FROM 30 WATTS TO 500 WATTS OR MORE. We can also supply multi-output transformers for **COLUMN LOUDSPEAKERS**. A recent tendency is the demand for **OUTPUT TRANSFORMERS FOR ULTRA LINEAR AMPLIFIERS** using **KT 88** and **KT 66 BEAM TETRODES** and for these we have standard designs with exceptional performance. We call your attention to our very successful **MICROPHONE SPLITTER TRANSFORMER** type 4079 with a high impedance 200 ohm primary and two 200 ohm secondaries. It will handle up to 2.3 volts rms at 30 Hz and has a frequency response of plus/minus 1/2dB from 20 Hz to 20 kHz. It is contained in a Mumetal Can 33 mm diam x 37 mm high and WORKING DETAILS OF THE CONSTRUCTION OF A SPLITTER ARE AVAILABLE ON REQUEST. We will supply single transformers, or any quantity, with short delivery times and, without obligation on your part, will quote price and exact dispatch on receipt of your requirements. **E. A. SOWTER LTD., Manufacturers and Designers, P.O. Box 36 IPSWICH IP1 2EG, ENGLAND. Tel. IPSWICH (0473) 52794 and 219390.** (8289)

ELECTRONIC TEST EQUIPMENT

SALES PURCHASES AND SERVICE

Tek. 526 Vectroscope	£395
Tek. 105 Generator	£60
Tek. 109 Generator	£100
Tek. 575 Curve Tracer	£100
Tek. 530 and 540 Mainframes from Feedback TWG 504 Function Gen.	£80
Marconi TF 801 D/I Generator	£195
TF 2410 120 MHz Counter	£120
Marconi TF 1020 A Powermeter	£55
Marconi TF 995 A/2 AM/FM Sig. Gen.	£150
Marconi TF 1073 A Attenuator	£60
Marconi TF 2091/2902 Noise System	£300
HP 5102 1MHz synthesizer	£250
HP 250B RX Meter	£200
R & S SLDLR High Power Sig. Gen.	£1000
Compariscope	£495
B & K 2005 Hetero Dine Volt Meter	£125
Teleguipmeter D52 10 MHz Scope	£150
Cosser CDU 150 35 MHz Scope	£350
Taylor 128 Meter	£20
Avometer Model 8 and 9	£50
Avometer Model 7 and 12. From Ampex VR 5003 Video Tape Recorder	£30
Lab. Gear Colour Bar Gen.	£225
Korting Colour TV Servicing Gen.	£95
HP5263A Time Interval Unit	£150
Belix 5v/4A PSU Modules, new	£45
Magnetic AB S410A 2/4 GHz AM Sig. Gen.	£22.50
ASC11 Keyboards	£150
Bradley 126B DC Calibrator	£20
Airmec 858 30 MHz Oscillator	£125
	£25

DUTCHGATE LTD.

Pyle Hill, Winchester Rd.
Fair Oak, Hampshire
Fair Oak 5252 (9486)

EQUIPMENT WANTED

TO ALL MANUFACTURERS AND WHOLESALE IN THE ELECTRONIC RADIO AND TV FIELD

BROADFIELDS & MAYCO DISPOSALS

will pay you top prices for any large stocks of surplus or redundant components which you may wish to clear. We will call anywhere in the United Kingdom.

21 LODGE LANE
NORTH FINCHLEY, LONDON N12 8JG
Telephone Nos. 01-445 0749/445 2713
After office hours 958 7624 (9123)

A.R. Sinclair

Electronic Stockholders
Stevenage 812193

We purchase all types of Mechanical and Electronic Equipment and Surplus stocks. (9206)

IC CONVERTER COOKBOOK

by W. G. Jung Price £8.90

A SIMPLE GUIDE TO HOME COMPUTERS

by S. Ditlea Price: £4.00

MICROCOMPUTER-BASED DESIGN

by J. B. Peatman Price £5.50

INTRODUCING MICROPROCESSORS

by G. L. Simons Price £7.00

OPERATIONAL AMPLIFIERS 2nd ed.

by G. B. Clayton Price £10.00

RADIO HANDBOOK 21st ed.

by W. I. Orr Price £13.50

MICROCOMPUTER DEVELOPMENT SYSTEMS & SUBSYSTEMS

by Motorola Set price £15.90

9900 FAMILY SYSTEMS DESIGN & DATA BOOK

by Texas Instruments Price £8.40

INTRODUCTION TO DIGITAL TECHNIQUES

by D. I. Porat Price £13.85

THE DESIGN & DRAFTING OF PRINTED CIRCUITS

by D. Lindsey Price £19.50

* ALL PRICES INCLUDE POSTAGE *

THE MODERN BOOK CO.

Specialists in Scientific & Technical Books

19-21 PRAED STREET
LONDON W2 1NP

Phone 723 4185
Closed Sat. 1 p.m. (8974)

SERVICES

ELECTRONIC DESIGN SERVICES.

Wide engineering experience available for the design of basic circuits to complete systems. Analogue DC to 1GHz and Digital. Write or phone Mr Anderson, Andertronics Ltd, Ridgeway, Hog's Back, Seale (Nr. Farnham), Surrey. Runfold 2639. (9140)

PRECISION SHEET METAL work,


chassis, panels, etc., steel, stainless or aluminium, long/short runs, good deliveries. EES Ltd., Clifford Road, Monks Road, Exeter 36489. Telex 42401. (8060)

DUST COVERS. Specialists in one-offs and batch production of high quality P.V.C. covers for test equipment, scopes and electronic devices. Send drawings for immediate quote. Design Covers, 7 Southcote Rise, Ruislip, Middlesex. Telephone Ruislip 30583.

ELECTRONIC COMPONENTS IN WEST GLAMORGAN BLUEBIRD ELECTRONICS

72 CRYMLYN ROAD
SKEWEN, NEATH
TELEPHONE SKEWEN 812103
Electronic Components available mail order or in the evenings 5 pm to 7 pm and at weekends: Sat., 9 am to 5 pm and Sun., 10 am to 1 pm.
Send S.a.e. for catalogue or call in and see us. (9618)

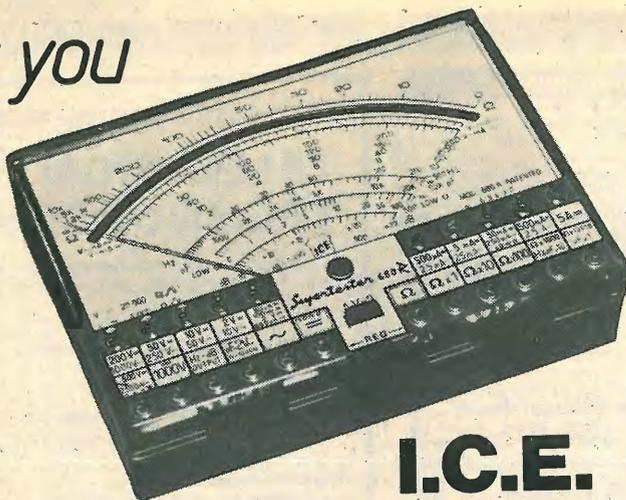Here's why you should buy an I.C.E. instead of just any multimeter



I.C.E.

WW - 111 FOR FURTHER DETAILS

- * Best Value for money.
- * Used by professional engineers, D.I.Y. enthusiasts, hobbyists, service engineers.
- * World-wide proven reliability.
- * Low servicing costs.
- * 20K/volt sensitivity and high accuracy.
- * Large mirror scale meter.
- * Fully protected against overload.
- * Large range of inexpensive accessories.
- * 12 month warranty, backed by a full after sales service at E.B. Sole U.K. Distributors:

Prices from £16.60 — £32.00 + VAT
Send for full colour leaflet and prices on whole range including accessories.

ELECTRONIC BROKERS LIMITED

49-53 Pancras Road, London NW1 2QB.
Tel: 01-837 7781. Telex: 298694.

INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 141-159

	PAGE		PAGE		PAGE
Acoustical Mfg. Co. Ltd	21	Gould Advance	11	Patrick, J. B.	132
AEL Crystals	106	Greenwood Electronics Ltd.	15	PBRA Ltd.	28
Airamco	124			Petalect Electronic Servicing	24
Ambit International	136			Plessey Controls	4
Antex	101	Harmsworth Townley & Co. Ltd.	16	Powertran Electronics	66, 116, 117
Aspen Electronics Ltd	36	Harris Electronics (London) Ltd.	15, 20	Pye Telecommunications Ltd.	6
Astra Elec. Comps.	36	Hart Electronics	105	Pye Unicom	17
Aura Sounds	130	Hewart Microelectronics	134	Precision Instruments	30, 39
Barkway Electronics Ltd.	32	Heyco MFG.	34	Prentice/Hall Int'l	132
Barrie Electronics Ltd.	119	Hivol Connectors Ltd.	37		
Beyer Dynamics	100	H.L. Audio	136	Quantum Electronics	26
Bi-Pak Semiconductors Ltd.	111			Racal Recorders	25
Bi-Prepak	140	I.L.P. Electronics Ltd.	31	Radio Components Specialists	135
Boss Industrial Mouldings Ltd.	35	Industrial Tape Applications	90	Radio Shack	118
Britec	30	Integrex Ltd.	108, 109	Ralfe, P.	110
Bull, J.	114	Intel Electronic Comps. Ltd.	112	R.C.S. Electronics	106
British Nat. Radio & Elec.	132	Interface Quartz Devices Ltd.	28	R.S.T. Valves	107
Cambridge Learning	7	International Civil Aviation	130		
Caracal Eng.	140	International Video Corp.	14	Sandwell Plant Ltd.	132
Carston Electronics Ltd.	23	Internepon	178	Scopex Instruments Ltd.	113
Catronics	105	Interport Mains Store	154	Sabtronics International	16
Chiltmead Ltd.	124	JPS Associates	38	Samsons (Electronics) Ltd.	138
Circards No. 5	133			Scott, J. (Elec. Eng.) Ltd.	8
Colomor (Electronics) Ltd.	134	KEF Electronics Ltd.	20	Service Trading	115
Compec '79	5	Kirkham Amplifier	2	Shure Electronics	40
Comp Computer Components	122	Kelsey Acoustic Ltd.	106, 140	Sintel	130
Concept Electronics	134			SME Ltd.	13
Clarke Smith (Vortexion)	32	Langrex	107	Southern Electronics	30
Colour Photo Service	120	Lascar Electronics	104	Special Products Ltd.	26
Continental Specialities	29	Leavers-Rich Equip. Ltd.	20	Sonimag 17	27
Crellon (Hewlett Packard)	9	Levell-Electronics Ltd.	3	Strumech End. Ltd.	32
Crellon (RCA Tubes)	28	London Inst. Repair Service	119	Strutt Electrical & Mech. Engrs. Ltd.	24, 38
Crimson Elektrik	12	Lotus Sound	36	Sugden, J. E. & Co. Ltd.	38
C. T. Electronics	139	Low Electronics Ltd.	18	Sullivan, H. W. Ltd.	131
Danavox (G.B.) Ltd.	22			Surrey Electronics	134
Datong	118	Maclin-Zand Electronics Ltd.	37	Swanley Electronics Ltd.	132
Display Electronics	125	Maplin Electronic Supplies	Cover iii	Technomatic Ltd.	121
Dominus	34	Marshall, A. & Sons (London) Ltd.	110	Tektronix (U.K.) Ltd.	Cover ii, 77
Eddystone Radio Ltd.	12	Martin Associates	10	Teleradio Electronics	134
Eagle/Carter Associates	18	MCP Electronics Ltd.	99	Transtel Communication Ltd.	65
Eagle International	33	Medelec	112		
Electronic Brokers Ltd.	126, 127, 128, 129, 160	Milward, G. F.	134	Valradio Ltd.	26
Electro-Tech Comps. Ltd.	123	Monolith Electronics Co.	34	Vero Electronics Ltd.	134
Electrovalue Ltd.	119	Multicore Solders Ltd.	Cover iv	Weighdata Ltd.	89
Electrovanace	102	Newbear Comp. Store	106, 138	West Hyde Developments Ltd.	102
Eraser International	105	Newtronics	136, 140	Wingrove & Rogers Ltd.	10
Faircrest Eng.	118	Olson Electronics	34	World Trade Centre	137
Farnell Insts. Ltd.	Readers Card 19	OMB Electronics	37	W.K. Electronics	5
Feedback Instruments	89			Wilmslow Audio	103
Field Tech	8			Z. & I. Aero Services Ltd.	28, 118
Forgestone Colour Dev's	140				
Future Film Developments	104				
Fylde Electronic Labs Ltd.	16				

OVERSEAS ADVERTISEMENT AGENTS:

- France & Belgium:** Norbert Hellin, 50 Rue de Chemin Vaat, F-92100, Boulogne, Paris.
- Hungary:** Mrs. Edit Bajusz, Hungexpo Advertising Agency, Budapest XIV, Varosliget Telephone: 225 008 — Telex: Budapest 22-4525 INTFOIRE.
- Italy:** Sig. C. Epis, Etas-Kompass, S.p.a. — Servizio Estero, Via Mantegna 6, 20154 Milan, Telephone: 347051 — Telex: 37342 Kompass.

- Japan:** Mr. Inatsuki, Trade Media — (BPA) (Japan), 8-212, Azabu Heights, 1-5-10 Roppongi, Minato-ku, Tokyo 106. Telephone: (03) 585-0581.
- UNITED STATES OF AMERICA:** Ray Barnes, IPC Business Press, 205 East 42nd Street, New York, NY 10017 — Telephone: (212) 689 5961 — Telex: 421710. Mr. Jack Farley Jr., The Farley Co., Suite 1584, 35 East Wacker Drive, Chicago, Illinois 60601 — Telephone: (312) 6 3074.
- Mr. Victor A. Jauch, Elmatex International, P.O. Box 34607, Los Angeles, Calif. 90034, USA — Telephone (213) 821-8581 — Telex 18-1059.

- Mr. Jack Mentel, The Farley Co., Suite 650, Ranna Building, Cleveland, Ohio 44115 — Telephone: (216) 621 1919.
- Mr. Ray Rickles, Ray Rickles & Co., P.O. Box 2008, Miami Beach, Florida 33140 — Telephone: (305) 532 7301.
- *Mr. Tim Parks, Ray Rickles & Co., 3116 Maple Drive N.E., Atlanta, Georgia 30305. Telephone: (404) 237 7432.
- Mike Loughlin, IPC Business Press, 15055 Memorial, Ste 119, Houston, Texas 77079 — Telephone (713) 783 8673.
- Canada:** Mr. Colin H. MacCulloch, International Advertising Consultants Ltd., 915 Carlton Tower, 2 Carlton Street, Toronto 2 — Telephone: (416) 364 2269. *Also subscription agents.

MAPLIN



This superb organ – build the first working section for just over £100. Full specification in our catalogue.



A range of highly attractive knobs is described in our catalogue. Our prices are very attractive too!



The 3800 synthesiser build it yourself at a fraction of the cost of one ready-made with this specification. Full details in our catalogue.



Touch operated rhythm generator, the 'Drumsette'. Construction details 25p. (Leaflet MES49). Specification in our catalogue.



Multimeters, analogue and digital, frequency counter, oscilloscopes, and lots, lots more at excellent prices. See cat. pages 106 and 183 to 188 for details.



61-note touch-sensitive piano to build yourself. Full specification in our catalogue.



A pulse width train controller for smooth slow running plus inertia braking and acceleration. Full construction details in our catalogue.



Speakers from 1½ inch to 15 inch; megaphone. PA horns, crossovers etc. They're all in our catalogue. Send the coupon now!

Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 37p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.07.

NAME _____

ADDRESS _____

WW 979




A wide range of disco accessories at marvellous prices. Our catalogue has all the details.



A very high quality 40W per channel stereo amplifier with a superb specification and lots of extras. Full construction details in our catalogue.



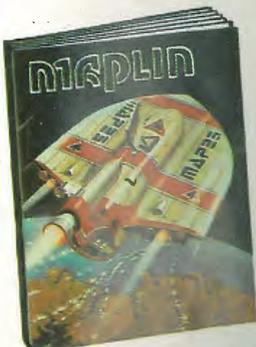A genuine 150W per channel stereo disco to build yourself. Full specification in our catalogue.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages – some in full colour – it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.

MAPLIN

ELECTRONIC SUPPLIES LTD

All mail to:—
P.O. Box 3, Rayleigh, Essex SS6 8LR.
Telephone: Southend (0702) 554155.
Shop: 284 London Road, Westcliff-on-Sea, Essex.
(Closed on Monday).
Telephone: Southend (0702) 554000.

high quality

Multicore solder helps Europe's OTS-2 satellite orbit at 23,000 miles

OTS-2, a forerunner of a European communications satellite, was launched from Cape Canaveral on May 11th 1978.

Now orbiting the equator at a height of 23,000 miles, OTS-2 was built for the European Space Agency by the MESH consortium, led by British Aerospace Dynamics Group, Stevenage.

In building OTS-2, complete precision was called for. Which is why Ersin Multicore solders were used for many of the soldering operations.

Quite simply, Multicore solders have *that* kind of reputation. For quality, toughness and reliability. That's why so many electronics manufacturers won't use anything else.

Next time you need solder of any kind, aim as high as OTS-2... and use Multicore.

Full details of Ersin Multicore solders, solder chemicals and high purity-bar solders for automatic soldering from



Multicore Solders Ltd

Maylands Avenue
Hemel Hempstead Herts HP2 7EP
Tel: Hemel Hempstead 3636
Telex: 82363

