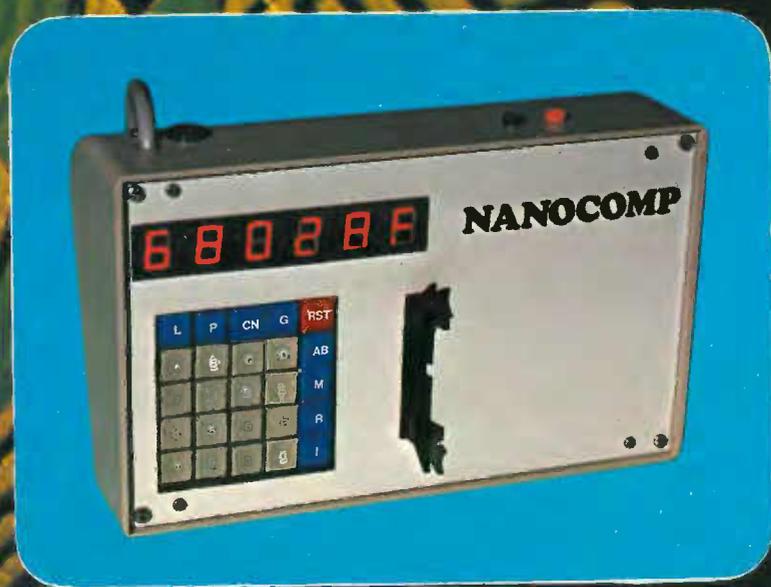


wireless world

JANUARY 1981 60p

Australia A\$ 2.00
Canada C\$ 3.15
Denmark Kr. 17.00
Germany DM. 5.00
Greece Dr. 87.00
Hong Kong Dfl. 5.75
Italy L. 2000
New Zealand N\$ 17.25
Singapore S\$ 4.50
Spain Ptas. 140.00
U.S.A. \$ 2.00

Microprocessor trainer
Off-air frequency reference
Multiplex organ keying





Biggest name in solder worldwide

Products that help you make a better job of it.



Arax Multicore Solder.
Economy pack for general non-electrical use. Replaces solid wire and stick solder. (B.S. 219 Grade L).
Econopak 200g reel of 3mm dia. Size 16A. £4.14 per reel.



Toolbox Reels.
Multicore 5-core solder for general use. Suitable for electrical joints (B.S. 219 Grade C).
0/60 tin/lead. 1.6mm dia. Size 3. £3.91 per reel.

Savbit.
Multicore 5-core solder for radio, TV and similar work. Reduces copper erosion. Suitable for service engineers and manufacturers using small quantities of solder.
2mm dia. Size 12. £3.91 per reel.



Multicore Wick.
Multicore solder-wick for removing solder from virtually any joint.
7mm dia. Size AB10. £1.38 per reel.




Aluminium Soldering.
Alu-Sol Multicore 4-core solder for soldering most types of aluminium. No extra flux needed.
6mm dia. Size 4. £6.90 per reel.

Hi-Fi Accessories Ltd., (Solder Division),
Key House, Wood Lane End,
Wellesbourne, Warwick, CV8 3JF.
Tel: 0442 61291.



| Product | Description | Per pack |
|---------|---|----------|
| PC115 | for printed circuits. | £1.15 |
| SV130 | for radio and TV repairs. | £1.61 |
| AR140 | for non-electrical applications, except aluminium for stainless steel and silver jewellery. | £1.38 |
| SS160 | for all electronic joints, non-corrosive. | £2.53 |
| 19A | for aluminium. | 96p |
| AL150 | solder cream for stainless steel, jewellery and household products (non-electrical). | £1.93 |
| BCA16 | solder cream for electronic and electrical use. | £3.22 |
| BCR10 | all purpose solder cream, non-electrical jointing and repairing. | £1.38 |
| BCA14 | | £1.38 |

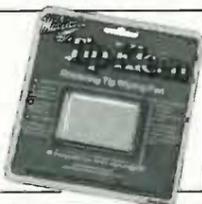Tip Kleen.
Multicore Tip Kleen. Soldering-iron tip wiping pad. Replaces wet sponges. (Should not be used above 350°C).
81p per pack.



Soldering Flux Pastes.
Multicore soldering flux paste. Extra fast, non-corrosive, rosin-flux for electrical and general purpose soldering.
Rosin R.F.10. 35g net. 69p per pack.
Multicore soldering flux paste for soft metals (except aluminium) and stainless steel. Non-electrical.
Arax A.F.14. 35g 69p per pack.



Econopak.
Ersin Multicore 5-core solder. Contains non-corrosive flux for electrical applications.
1.2mm dia. 200g Econopak. Size 13A. £4.14 per reel.



Metal Soldering.
Arax Multicore 4-acid-core solder for metal fabrication (not aluminium) and repairs.
40/60 tin/lead. 1.6mm dia. Size 11. £3.91 per reel.



TV and Radio Soldering.
Savbit Multicore for radio, TV and similar work. Reduces copper erosion.
1.2mm dia. Size 5. 90p per handy dispenser.

Econopak.
General purpose solder suitable for all electrical joints.
40/60 alloy. 1.2mm dia. Size 6. 58p per handy plastic dispenser.



Wire Stripper and cutter.
Wire stripper and cutter with precision ground and hardened steel jaws. Adjustable to most wire sizes. With handle locking-catch and easy-grip plastic covered handles.
Ref. 9. £2.69 per pair.

All recommended retail prices shown are inclusive of VAT. If you have difficulty in obtaining any of these products send direct with 40p for postage and packing. For free colour brochure send S.A.E.

WW-004 FOR FURTHER DETAILS


wireless world

JANUARY 1981 60p

Microprocessor trainer Off-air frequency reference Multiplex organ keying

Australia A\$ 2.00
Canada C\$ 3.15
Denmark Kr. 17.00
France Fr. 5.00
Germany DM. 87.00
Italy Lit. 5.75
Japan ¥ 2000
Norway Kr. 17.25
Singapore S\$ 4.50
Spain Ptas. 340.00
U.S.A. \$ 2.00

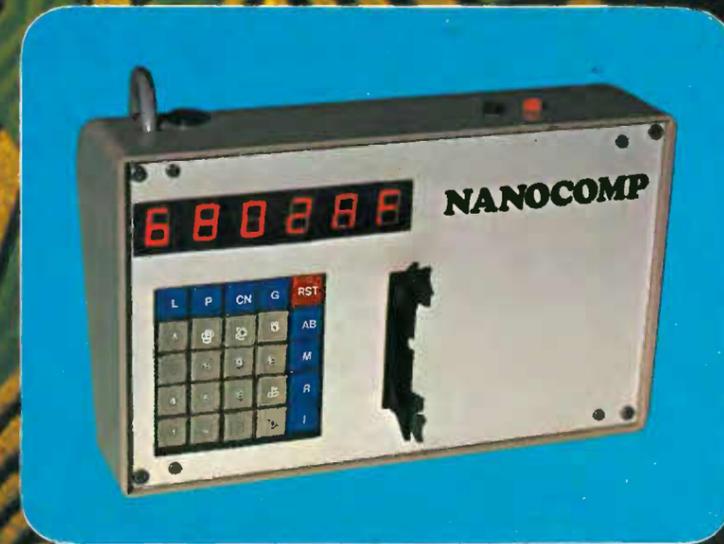WIRELESS WORLD JANUARY 1981 VOL 87 NO 1540



The DMM range that's
matched to
your requirements

1st place for
quality and value



With the introduction of two very low priced pocket-sized DMM's, Avo are now in a position to offer a team of digitals to meet your electrical and electronic testing requirements precisely. All feature accuracy, reliability and ease of use; and all are readily available through our 25 U.K. Distributors.

Get the backing of Team AVO. Call us today or talk to your local distributor for further details. Join the race for quality and value.

**Team
AVO**



Avo Limited, Archcliffe Road, Dover, Kent CT17 9EN
Telephone: 0304 202620 Telex: 96283

You'll never meet a better meter.


A Member of the
THORNEMI Group



WW 001

FOR FURTHER DETAILS

WIRELESS WORLD JANUARY 1981

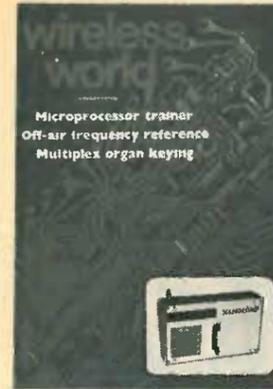

Front cover shows (inset) microprocessor trainer described in this issue with background of a Burr Brown thick film hybrid a-to-d converter photographed by Paul Brierley.

IN OUR NEXT ISSUE

Wind speed and direction indicator for the yachtsman digitally displays wind direction at the masthead to within 2° and speed from 1 to 100 knots.

Morse code decoding computer programme for the Wireless World scientific computer decodes Morse signals into normal text. Will identify and reject interference pulses.

'Just detectable' distortion. Signal characteristics which control the detectability of distortion to the ear and attempts made to determine what is 'just-detectable.'

Current issue price 60p, back issues (if available) £1.00, at Retail and Trade Counter, Units 1 & 2, Bankside Industrial Centre, Hopton Street, London SE1. Available on microfilm; please contact editor.

By post, current issue 96p, back issues (if available) £1.50, order and payments to EEP General Sales Dept., Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS.

Editorial & Advertising offices: Quadrant House, The Quadrant, Sutton Surrey SM2 5AS.
Telephones: Editorial 01-661 3500, Advertising 01-661 3129.
Telegrams/Telex: 892084 BISPRS G.

Subscription rates: 1 year £10.00 UK and \$33.80 outside UK.

Student rates: 1 year £5.00 UK and \$16.00 outside UK.

Distribution: 40 Bowling Green Lane, London EC1R 0NE. Telephone 01-837 3636.

Subscriptions: Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. Telephone 0444 59188. Please notify a change of address.

USA mailing agents: Expeditors of the Printed World Ltd, 527 Madison Avenue, Suits 1217, New York, NY 10022. 2nd-class postage paid at New York.

© IPC Business Press Ltd, 1981
ISSN 0043 6062

wireless world

ELECTRONICS / TELEVISION / RADIO / AUDIO

JANUARY, 1981 Vol 87 No 1540

31 A testing time f electronics

32 Nanocomp microprocessor trainer
by R. Coates

37 World of amateur radio

38 The first thousand transmitters
by Edward Trickett

42 Electronic combination lock
by Jan Hruska

44 Low speed differentiator
by L. Hayward

Wideband amplifier 46 Circuit ideas Simple s.c.r. oscillator
Visual fire effect

1980 Broadcasting Act 49 News of the month
Bus for omnibuses Faulty vision caused
by brewer's products

53 Multiplex keying system for organs
by A. W. Critchley

57 Technology versus fundamentals in education
by D. A. Bell

59 Multiphase low distortion oscillator
by A. D. Ryder

61 Letters to the editor
Microchips and megadeaths Audio kits The floating bridge

67 Artificial intelligence
by Malcolm Peltu

72 Off-air reference frequency
by D. I. Stansfield

77 F.m. detectors
by S. W. Amos

81 Improved parity checker
by N. Darwood

83 New products


- ORDER BY POST OR TELEPHONE WITH BARCLAYCARD/ACCESS
- ELECTRONIC TEST EQUIPMENT SPECIALISTS
- ALL PRICES INCLUDE VAT

AUDIO ELECTRONICS

- ALL MODELS ON DISPLAY
- RETAIL - MAIL ORDER - EXPORT - INDUSTRIAL
- OPEN SIX DAYS A WEEK
- CALL IN AND SEE FOR YOURSELF

SCOPES

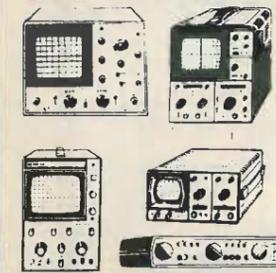A range of Scopes in stock from 5mHZ Single Trace to 50mHZ Dualtrace. Mains and Battery/Mains portables. Many on demonstration.



SINGLE TRACE (UK c/p etc £2.50)

Hm 307-3 10mHZ, 5mV, 6 x 7cm display plus component test **£170.00**
 CD1303D 5mHZ, 10mV, 7 x 7cm display **£109.25**
 SC110 10mHZ Battery portable, 10mV 3.2 x 2.8cm display (Optional case £8.80, Nicads £7.95, Mains unit £4.00) **£149.95**
 LBO12A 10mHZ, 10mV, 5" display **£195.00**
 CS1559A 10mHZ, 10mV, 5" display **£198.50**
 V151 15mHZ 1mV 5" display **£241.50**

OPTIONAL PROBES (ALL MODELS)
 X1 **£6.50**, X10 **£8.50**, X100 **£12.95**, X1-X10 **£10.95**

DUAL TRACE (UK c/p etc £3.50)

CS156A 10mHZ, 10mV, 5" display **£244.95**
 CS1575 5mHZ 1mV 5" display **£270.00**
 Hm 312-8 20mHZ, 5mV, 10cm display **£253.00**
 CS1566A 20mHZ, 5mV, 5" display **£323.15**
 LBO3085 70mHZ, 2mV, 5 x 6.3cm display. Battery/mains Portable, built-in Nicads **£482.00**
 HM412-4 20mHZ, 5mV, 8 x 10cm display plus Sweep Delay **£399.50**
 CS1577A 30mHZ, 2mV, 5" display **£455.40**
 CS1830 30mHZ, 2mV, 5" display plus sweep delay **£507.15**
 Hm 512-8 50mHZ, 5mV, 10 x 8cm display. Delay Sweep **£667.00**
 LBO514 10mHZ, 1mV, (5mV) 5" display **£294.00**
 V152 15mHZ, 1mV, 5" display **£326.00**
 V302 30mHZ, 1mV, 5" display **£447.35**
 V550 50mHZ, 1mV 10 x 8cm. Delay sweep + 3 channel display **£799.25**


All scopes now with free probe(s)

ALL PRICES INCLUDE VAT

HAMEG • TRIO • SINCLAIR • LEADER • HITACHI

GENERATORS

(UK c/p £1.75)

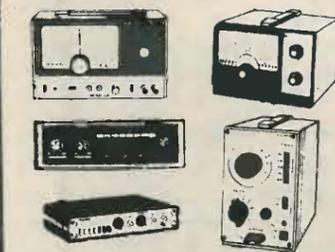

RF

SG402 100KHZ - 30mHZ with AM modulation **£64.40**
 LSG16 100KHZ (300mHZ on Harmonics) **£56.50**
 LSG231 100m HZ ± 1mHZ (adjustable) FM stereo generator and pilot and mod. **£195.00**

PULSE

2001 1HZ-100KHZ (function) **£86.00**
 TG105 5HZ-5mHZ **£92.50**
 4001 0.5HZ-5mHZ **£105.00**
 200P 0.002HZ-5.5mHZ **£253.00**
 200SPC as 200P plus built in freq. display/100mHZ counter **£437.00**

A range of Signal Generators to cover Audio, RF and Pulsing. Mains operated (TG series Battery).

LEADER • TRIO • NEWTRONICS • LEVELL

AUDIO (All sine/square)

AG202A 20HZ-200KHZ **£65.55**
 LAG26 20HZ-200KHZ **£69.00**
 AG203 10HZ-1mHZ sine/square **£120.75**
 LAG120A 10HZ-1mHZ **£137.00**

LEVELL (Battery Portables) ('M' with Meter)

152 SERIES 3HZ - 300KHZ Sine/Square **£92.00**
 200 SERIES 1HZ-1mHZ Sine/Square **£113.85**
 TG152D **£124.20**
 TG200D **£149.50**
 TG200DM **£155.25**
 TG200DMP

TV GENERATORS

LCG-393V PAL B VHF 6 patts. **£137.00**
 SCG-392U PAL B UHF 15 patts. **£217.00**

SWR/FS AND POWER METERS

Range in stock covering up to 150mHZ and up to 1K watt power. PL259 sockets. Also 250 UHZ Grid Dipmeter


SWR5 SWR/S 3-150mHZ **£9.50**
 SWR50 SWR/Power meter, 3/4-150mHZ 0-1000 watts **£13.95**
 110 SWR/Power 1/2-144mHZ 0/10/100 watts **£11.50**
 171 As 110 Twin meter plus F/S **£14.50**

Plus large range of BNC/PL259/ etc leads plus adaptors/connectors always in stock.

178 SWR/Power/FS 1/2-144mHZ 5-50 watt Plus 25-40mHZ ac match **£16.60**
 KDM6 Gnd Dip 1/2-250mHZ **£38.50**

DIGITAL MULTIMETERS

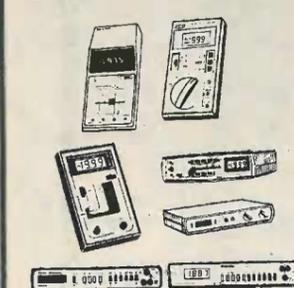A range of LED and LCD Bench and Hand DMM's battery operated with optional Mains Adaptors - some with optional Nicads. All supplied with batteries and leads.



HAND HELD (UK post etc. 85p)

TM352 3 1/2 Digit LCD plus 10 ADC and Hfe checker **£54.95**
 PDM35 3 1/2 Digit 16 range LED (no AC current) **£32.95**
 ME502 3 1/2 Digit LED plus 10A DC and Hfe checker **£43.95**
 LM2001 3 1/2 Digit LCD 2 amp AC/DC 0.1% **£51.70**
 6200 3 1/2 Digit LCD 0.2A AC/DC, Auto range **£39.95**
 6220 As 6200 plus 10A AC/DC **£49.95**
 6100 As 6200 plus Cont. test/range hold **£59.95**
 6110 As 6100 plus 10A AC/DC **£74.95**

BENCH PORTABLES (UK c/p £1.00)

DM235 3 1/2 Digit LED 21 ranges, 0.5% AC/DC 2A **£56.50**
 DM350 3 1/2 Digit LED 34 ranges AC/DC 10A **£78.50**
 TM353 3 1/2 Digit LCD AC/DC 2 amp **£86.50**
 TM351 3 1/2 Digit LCD AC/DC 10 amp **£107.95**
 LM100 3 1/2 Digit LCD AC/DC 2 amp **£86.50**
 DM450 4 1/2 Digit LED 34 ranges AC/DC 10 amp **£107.95**
 (DM series options. Carry case £8.50, NI-cads £7.95. Mains adaptor £4.00).

LOGIC PROBES/MONITORS

Logic probes indicating high/low etc states that scopes can miss. All circuit powered for all I.Cs.

LMI


LP3 50mHZ logic probe **£55.95**
 LP1 10mHZ logic probe **£35.50**
 LP2 1 1/2mHZ logic probe with case **£19.95**

Logic monitor **£33.00**. Also in stock range of Probe-board kits and breadboards.

LDP076 50mHZ logic probe with case **£51.00**

CHOOSE FROM UK'S LARGEST SELECTION

FREQUENCY COUNTERS

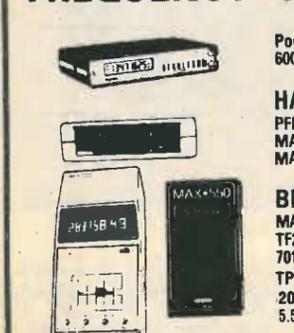

Portable and Bench LCD and LED Counters up to 600mHZ. Prices include batteries and leads.

HAND HELD (UK post etc 85p)

PFM200 20HZ to 200mHZ 8 Digit LED **£54.50**
 MAX50 100HZ to 50mHZ 6 Digit LED **£61.00**
 MAX550 30KHZ to 550mHZ 6 Digit LED **£106.00**

BENCH PORTABLES (UK c/p £1.00)

MAX100 8 Digit LED 5HZ to 100mHZ **£99.00**
 TF200 8 Digit LED 10HZ to 200mHZ **£158.95**
 7010A 9 Digit LED 10HZ to 600mHZ **£184.00**
 TP600 600mHZ Pre-Scaler for TF200 **£41.00**
 200SPC 6 Digit 100mHZ LED built into 0.002HZ to 5.5mHZ Pulse Generator **£437.00**

CLAMP METERS/INSULATION TESTERS

(All multirange except K2303)

K2303 30 AMPS 500 VAC **£21.95**

3101 300 AMPS 600 VAC 1K OHM **£32.95**
 K2803 300 AMPS 600 VAC 2K OHM **£53.95**
 K2903 900 AMPS 750 VAC 2K OHM **£77.95**
 K3103 Transistorised insulation/continuity tester, 100 MEG, 600 VAC, 0/2 1/2K **£95.00**
 M500 Insulation tester 100 MEG, 500 VOLT, 0/200 OHMS continuity **£87.50**

Also digital and DC types in stock

ELECTRONIC METERS

UK c/p

K200 38 range FET 10m OHM input 20Hz to 30mHZ multimeter **£95.00**
 TM11 120 range multimeter 3Hz to 200KHz **£172.50**
 TM3A Multirange AC micro voltmeter **£149.50**
 TM3B As TM3A larger size meter **£166.75**

'PRO' MULTIMETERS

UK c/p

M1200 100K/Volt 30 ranges plus AC/DC 15 amp **£120**
 M1200 100K/Volt 30 ranges plus AC/DC 15 amp **£67.00**
 K1400 20K/Volt 23 range large scale **£79.95**
 M1500 20K/Volt 42 range plus AC/DC 10 amp **£53.50**

CSC • SINCLAIR • OPTOELECTRONICS • NEWTRONICS

Stockists of electronic equipment, speakers/kits, PA equipment plus huge range of accessories • UK carriage/packing as indicated • Export - prices on request • All prices correct at 1.12.80 E & OE • All prices include VAT

AUDIO ELECTRONICS Cubegate Limited
 301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TELEPHONE 01-724 3564

OPEN SIX DAYS A WEEK



FREE CATALOGUE!
 Send large SAE (17 1/2p UK) Schools, Companies, etc. free on request.




DON'T GAMBLE WITH PERFORMANCE BUY LEVELL OSCILLATORS




FREQUENCY 1Hz to 1MHz in 12 ranges.
ACCURACY 0 to 1% fine control on TG200DMP. ± 1.5% ± 0.01Hz up to 100kHz. ± 2% up to 1MHz.
SINE OUTPUT 7V r.m.s. down to < 200µV with Rs = 600Ω.
DISTORTION < 0.05% from 50Hz to 15kHz, < 0.1% from 10Hz to 50kHz, < 0.2% from 5Hz to 150kHz, < 1% at 1Hz and 1MHz.
SQUARE OUTPUT TG200D, DM & DMP only, 7V peak down to < 200µV. Rise time < 150nS.
SYNC OUTPUT < 1V r.m.s. sine in phase with output
SYNC INPUT + 1% freq. lock range per volt r.m.s.
METER SCALES TG200M, DM & DMP only. 0/2V/0/7V & -14/+6dBm.
SIZE & WEIGHT 260 x 130 x 180mm. 4.3kg with batteries.

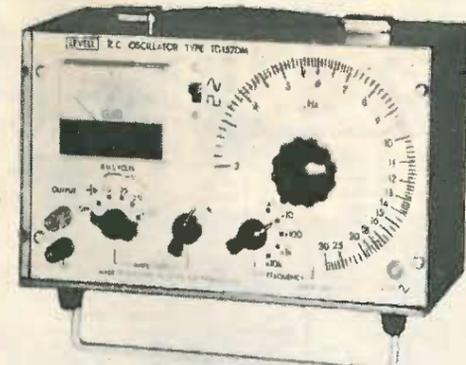TG200 **£99** TG200D **£108** TG200M **£125** TG200DM **£130** TG200DMP **£135**



FREQUENCY 3Hz to 300kHz in 5 decade ranges.
ACCURACY ± 2% ± 0.1Hz to 100kHz. Increasing to ± 3% at 300kHz.
SINE OUTPUT 2.5V r.m.s. down to < 200µV
DISTORTION < 0.2% from 50Hz to 50kHz.
SQUARE OUTPUT 2.5V peak down to < 200µV.
SYNC OUTPUT 2.5V r.m.s. sine
METER SCALES 0/2.5V & -10/+10dB on TG152DM.
SIZE & WEIGHT 260 x 130 x 180mm. 3.4kg with batteries.

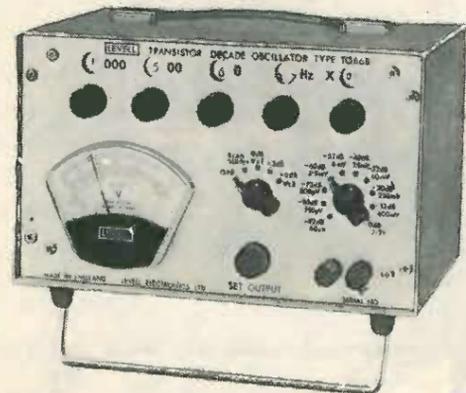TG152D Without meter **£80** With meter **£99**



FREQUENCY 0.2Hz to 1.22MHz on four decade controls.
ACCURACY + 0.02Hz below 6Hz. + 0.3% from 6Hz to 100kHz. + 1% from 100kHz to 300kHz. + 3% above, 300kHz.
SINE OUTPUT 5V r.m.s. down to 30µV with Rs = 600Ω.
DISTORTION < 0.15% from 15Hz to 15kHz.
METER SCALES < 0.5% at 1.5Hz and 150kHz. 2 Expanded voltage and -2/+4dBm
SIZE & WEIGHT 260 x 180 x 180mm. 5.4kg.

TG66B Battery model **£265** Mains & battery model **£280**

Prices are ex works with batteries. Carriage, packing and VAT extra. Optional extras are leather cases and mains power units. Send for data covering our range of portable instruments.

LEVELL ELECTRONICS LTD.

MOXON STREET, BARNET, HERTS., EN5 5SD. TEL: 01-449 5028/440 8686

AND THERE'S MORE WHERE THIS CAME FROM

It's a long time since one of our adverts was presented in 'list' form - but simply because we do not try to squeeze this lot in every time doesn't mean that it's not available. Our new style price list (now some 40 pages long) includes all this and more, including quantity prices and a brief description. The kits, modules and specialized RF components - such as TOKO coils, filters etc. are covered in the general price list - so send now for a free copy (with an SAE please). Part 4 of the catalogue is due out now (incorporating a revised version of pt.1).

LINEAR ICs - NUMERIC LISTINGS

| | | | |
|-----------|------|-----------|-------|
| TBA1205 | 1.00 | KB4413 | 1.95 |
| L200 | 1.95 | KB4417 | 1.80 |
| U237B | 1.28 | TDA4420 | 2.25 |
| U247B | 1.28 | KB4420B | 1.09 |
| U257B | 1.28 | KB4423 | 2.30 |
| U267B | 1.28 | KB4424 | 1.65 |
| LM301H | 0.67 | KB4431 | 1.95 |
| LM301N | 0.30 | KB4432 | 1.95 |
| LM308H | 0.96 | KB4433 | 1.52 |
| LM308N | 0.65 | KB4436 | 2.53 |
| LM339N | 0.66 | KB4437 | 1.75 |
| LM348N | 1.86 | KB4438 | 2.22 |
| LF351N | 0.38 | KB4441 | 1.35 |
| LF352N | 0.76 | KB4445 | 1.29 |
| LM374N | 3.75 | KB4446 | 2.75 |
| LM380N-14 | 1.00 | KB4448 | 1.65 |
| LM380N-8 | 1.00 | NE5044N | 2.26 |
| LM381N | 1.81 | NE5532N | 1.85 |
| ZM419CE | 1.95 | SD6000 | 3.75 |
| NE544N | 1.80 | SL6270 | 2.03 |
| NE555N | 0.30 | SL6310 | 2.03 |
| NE556N | 0.50 | SL6600 | 3.75 |
| NE560N | 3.50 | SL6640 | 2.75 |
| NE562N | 4.05 | SL6690 | 3.20 |
| NE564N | 4.29 | SL6700 | 2.35 |
| NE565N | 1.00 | IC180380C | 4.50 |
| NE566N | 1.60 | MSL9362 | 1.75 |
| NE570N | 3.85 | MSL9363 | 1.75 |
| SL624 | 3.28 | HAI1211 | 1.95 |
| TBA651 | 1.81 | HAI1223 | 2.15 |
| UA709HC | 0.64 | HAI1225 | 1.45 |
| UA709PC | 0.36 | HAI2002 | 1.45 |
| UA710HC | 0.65 | HAI2017 | 0.80 |
| UA710PC | 0.59 | HAI2402 | 1.95 |
| UA741CH | 0.66 | HAI2411 | 1.20 |
| UA741CN | 0.27 | HAI2412 | 1.55 |
| UA747CN | 0.70 | LF13741 | 0.33 |
| UA748CN | 0.36 | SN76660N | 0.80 |
| UA753 | 2.44 | | |
| UA758 | 2.35 | | |
| TBA810AS | 1.09 | | |
| TBA820M | 0.75 | | |
| TC940E | 1.80 | | |
| TDA1028 | 2.11 | SAAL056 | 3.75 |
| TDA1029 | 2.11 | SAAL058 | 3.35 |
| TDA1054 | 1.45 | IC1390C | 14.00 |
| TDA1062 | 1.95 | LM1232 | 19.00 |
| TDA1072 | 2.69 | LM1242 | 19.00 |
| TDA1074A | 5.04 | MSL2318 | 3.84 |
| TDA1083 | 1.95 | MSM5523 | 11.30 |
| TDA1090 | 3.05 | MSM5524 | 11.30 |
| HAI137 | 1.20 | MSM5525 | 7.85 |
| HAI196 | 2.00 | MSM5526 | 7.85 |
| HAI197 | 1.00 | MSM5527 | 9.75 |
| TDA1220 | 1.40 | MSM55271 | 9.75 |
| LM1303 | 0.99 | ICM7106CP | 9.55 |
| LM1307 | 1.55 | ICM7107CP | 9.55 |
| MCI1310P | 1.90 | ICM7216B | 19.25 |
| MCI1330 | 1.20 | ICM7217A | 9.50 |
| MCI1350 | 1.20 | SP8629 | 3.85 |
| HAI370 | 1.90 | SP8647 | 6.00 |
| HAI388 | 2.75 | 95H90PC | 6.00 |
| TDA1490 | 1.86 | HD10551 | 2.45 |
| MCI496P | 1.25 | HD4015 | 4.45 |
| SL1610P | 1.60 | HD12009 | 6.00 |
| SL1611P | 1.60 | HD44752 | 8.00 |
| SL1612P | 1.60 | | |
| SL1613P | 1.89 | | |
| SL1620P | 2.17 | | |
| SL1621P | 2.17 | | |
| SL1623P | 2.24 | | |
| SL1624C | 3.28 | | |
| SL1625P | 2.17 | | |
| SL1626P | 2.44 | | |
| SL1630P | 1.62 | | |
| SL1640P | 1.89 | | |
| SL1641P | 1.89 | | |
| TDA2002 | 1.25 | | |
| TDA2020 | 3.00 | | |
| U1A2242A | 3.05 | | |
| U1A2283B | 1.00 | | |
| CA3080E | 0.70 | | |
| CA3089E | 1.84 | | |
| CA3090AQ | 3.35 | | |
| CA3123E | 1.40 | | |
| CA3130E | 0.80 | | |
| CA3130T | 0.90 | | |
| CA3140E | 0.46 | | |
| CA3189E | 2.20 | | |
| MC3357P | 2.35 | | |
| LM3900N | 0.60 | | |
| LM3909N | 0.68 | | |
| LM3914N | 2.80 | | |
| LM3915N | 2.80 | | |
| KB4400 | 0.80 | | |
| KB4406 | 0.60 | | |
| KB4412 | 1.95 | | |

TTL N and LSN

| | | | |
|--------|------|---------|------|
| 7400N | 0.13 | 7445N | 0.94 |
| 74LS00 | 0.20 | 7446N | 0.94 |
| 7401N | 0.13 | 74LS47 | 0.89 |
| 74LS01 | 0.20 | 7448N | 0.56 |
| 7402N | 0.14 | 74LS48 | 0.99 |
| 74LS02 | 0.20 | 74LS49 | 0.99 |
| 7403N | 0.14 | 7451N | 0.17 |
| 74LS03 | 0.20 | 74LS51 | 0.24 |
| 7404N | 0.14 | 7453N | 0.17 |
| 74LS04 | 0.24 | 7454N | 0.17 |
| 7405N | 0.18 | 74LS54 | 0.24 |
| 74LS05 | 0.26 | 74LS55 | 0.24 |
| 7406N | 0.28 | 7460N | 0.17 |
| 7407N | 0.38 | 74LS63 | 1.24 |
| 7408N | 0.17 | 7470N | 0.28 |
| 74LS08 | 0.24 | 7472N | 0.28 |
| 7409N | 0.17 | 7473N | 0.32 |
| 74LS09 | 0.24 | 74LS73 | 0.38 |
| 7410N | 0.15 | 7474N | 0.27 |
| 74LS10 | 0.24 | 74LS74 | 0.28 |
| 7411N | 0.20 | 7475N | 0.38 |
| 74LS11 | 0.24 | 7476N | 0.37 |
| 7412N | 0.17 | 74LS76 | 0.38 |
| 7413N | 0.30 | 74LS78 | 0.38 |
| 7414N | 0.51 | 7480N | 0.48 |
| 74LS15 | 0.24 | 7481N | 0.86 |
| 7416N | 0.30 | 7482N | 0.69 |
| 7417N | 0.30 | 7483N | 1.04 |
| 7420N | 0.16 | 74LS85 | 0.99 |
| 74LS20 | 0.24 | 74LS86 | 0.40 |
| 7421N | 0.29 | 7489N | 2.05 |
| 74LS21 | 0.24 | 7490N | 0.33 |
| 7423N | 0.27 | 74LS90 | 0.90 |
| 7425N | 0.27 | 7491N | 0.76 |
| 7427N | 0.27 | 74LS91 | 1.10 |
| 74LS27 | 0.44 | 7492N | 0.38 |
| 7428N | 0.35 | 74LS92 | 0.78 |
| 74LS28 | 0.32 | 7493N | 0.32 |
| 7430N | 0.17 | 74LS93 | 0.99 |
| 74310N | 0.24 | 7494N | 0.78 |
| 7432N | 0.25 | 7495N | 0.65 |
| 7433N | 0.24 | 74LS95 | 1.14 |
| 7437N | 0.40 | 7496N | 0.58 |
| 7438N | 0.33 | 74LS96 | 1.20 |
| 74LS38 | 0.24 | 7497N | 1.85 |
| 7440N | 0.17 | 74LS107 | 0.38 |
| 74LS40 | 0.24 | 74109N | 0.63 |
| 7441N | 0.74 | 74LS109 | 0.70 |
| 7442N | 0.70 | 74110N | 0.54 |
| 74LS42 | 0.99 | 74111N | 0.68 |

VARICAP

| | | | |
|----------|------|---------|------|
| 74LS112 | 0.38 | 74LS169 | 2.00 |
| 74LS113 | 0.38 | 74170N | 2.30 |
| 74LS114 | 0.38 | 74LS170 | 2.00 |
| 74118N | 0.83 | 74LS174 | 1.20 |
| 74120N | 1.15 | 74175N | 0.87 |
| 74121N | 0.42 | 74LS175 | 1.10 |
| 74122N | 0.46 | 74176N | 0.75 |
| 74123N | 0.73 | 74177N | 0.78 |
| 74LS124 | 1.75 | 74181N | 1.65 |
| 74125N | 0.38 | 74LS181 | 3.50 |
| 74126N | 0.57 | 74LS183 | 2.10 |
| 74128N | 0.74 | 74184N | 1.35 |
| 74132N | 0.73 | 74185N | 1.34 |
| 74LS132 | 0.78 | 74LS190 | 0.92 |
| 74LS136 | 0.40 | 74192N | 1.05 |
| 74LS138 | 0.60 | 74193N | 1.05 |
| 74141N | 0.56 | 74LS193 | 1.80 |
| 74142N | 2.65 | 74194N | 1.05 |
| 74143N | 3.12 | 74196N | 0.99 |
| 74144N | 3.12 | 74LS196 | 1.10 |
| 74LS145 | 0.97 | 74LS197 | 1.10 |
| 74147N | 1.75 | 74198N | 1.50 |
| 74148N | 1.09 | 74199N | 1.60 |
| 74LS148 | 1.19 | 74LS247 | 0.93 |
| 74150N | 0.99 | 74LS257 | 1.08 |
| 74151N | 0.55 | 74LS260 | 1.53 |
| 74LS151 | 0.84 | 74LS279 | 0.52 |
| 74LS153 | 0.54 | 74LS283 | 1.20 |
| 74LS154N | 0.96 | 74LS293 | 0.95 |
| 74LS155N | 0.54 | 74LS365 | 0.49 |
| 74LS155 | 1.10 | 74LS366 | 0.49 |
| 74LS156N | 0.80 | 74LS367 | 0.43 |
| 74LS157 | 0.65 | 74LS368 | 0.49 |
| 74LS158 | 0.60 | 74LS374 | 1.80 |
| 74LS159 | 2.10 | 74LS377 | 1.95 |
| 74160N | 0.82 | 74LS379 | 1.30 |
| 74LS160 | 1.30 | 74LS393 | 1.40 |
| 74161N | 0.92 | | |
| 74LS161 | 0.78 | | |
| 74LS162 | 1.30 | | |
| 74163N | 0.92 | | |
| 74LS163 | 1.04 | | |
| 74164N | 1.78 | | |
| 74LS164 | 1.30 | | |
| 74165N | 1.05 | | |
| 74LS165 | 1.04 | | |
| 74167N | 2.50 | | |

TUNING DIODES

| | | | |
|---------|------|---------|------|
| BAL02 | 0.30 | BC237 | 0.08 |
| BAL21 | 0.30 | BC238 | 0.08 |
| ITT210 | 0.30 | BC239 | 0.08 |
| BB105B | 0.36 | BC307 | 0.08 |
| BB109 | 0.27 | BC308 | 0.08 |
| MVM125 | 1.05 | BC309 | 0.08 |
| BB212 | 1.95 | BC413 | 0.10 |
| KV1210 | 2.45 | BC414 | 0.11 |
| KV1211 | 1.75 | BC415 | 0.07 |
| KV1226 | 1.95 | BC416 | 0.08 |
| KV1225 | 2.75 | BC546 | 0.12 |
| KV1215 | 2.55 | BC556 | 0.12 |
| KV1225 | 2.75 | BC550 | 0.12 |
| BC640 | 0.23 | BC560 | 0.12 |
| BC639 | 0.22 | BC639 | 0.22 |
| 2SC1775 | 0.18 | 2SC1775 | 0.18 |
| 2SA872A | 0.14 | 2SA872A | 0.14 |
| IN6263 | 0.62 | 2SD666A | 0.30 |
| BA182 | 0.19 | 2SB646A | 0.30 |
| BA244 | 0.17 | 2SD668A | 0.40 |
| BA379 | 0.35 | 2SB648A | 0.40 |
| TDA1061 | 0.95 | 2SD760 | 0.45 |
| 2SB720 | 0.45 | 2SB720 | 0.45 |
| 2SC2546 | 0.19 | 2SA1084 | 0.20 |
| 2SA1084 | 0.20 | 2SC2547 | 0.19 |
| 2SC2547 | 0.19 | 2SA1085 | 0.20 |
| 2SA1085 | 0.20 | | |

TRANSISTORS

| | | | |
|---------|------|----------|------|
| IN4148 | 0.06 | IN4001 | 0.06 |
| IN4001 | 0.06 | IN4002 | 0.07 |
| IN5402 | 0.15 | OA91 | 0.07 |
| OA91 | 0.07 | AAL12 | 0.25 |
| AAL12 | 0.25 | BRIDGES: | |
| LA/50V | 0.35 | LA/50V | 0.35 |
| 6A/200V | 0.75 | 6A/200V | 0.75 |

CAPACITORS

| | | | |
|---------------------|-------|--------------------|-------|
| CERAMIC 50V | | 330P, 390P, 470P | 0.055 |
| 2P2, 3P3, 4P7, 6P8 | | 1N0, 2N2, 3N3, 4N7 | 0.06 |
| 8P2, 10P, 15P, 18P | 0.04 | 10N (0.01uF) | 0.05 |
| 22P, 27P, 33P, 47P | | 22N, 47N | 0.06 |
| 56P, 68P, 82P, 100P | 0.05 | 100N, 220N | 0.09 |
| 150P, 220P, 270P | | MONOLITHIC CERAMIC | |
| 330P, 390P, 470P | 0.055 | 10N, 100N | 0.16 |
| 1N0, 2N2, 3N3, 4N7 | 0.06 | | |
| 10N (0.01uF) | 0.05 | | |
| 22N, 47N | 0.06 | | |
| 100N, 220N | 0.09 | | |
| MONOLITHIC CERAMIC | | | |
| 10N, 100N | 0.16 | | |

FREQUENCY DISPLAY & SYNTHESIZER ICs

| | |
|-----------|-------|
| SAAL056 | 3.75 |
| SAAL058 | 3.35 |
| IC1390C | 14.00 |
| LM1232 | 19.00 |
| LM1242 | 19.00 |
| MSL2318 | 3.84 |
| MSM5523 | 11.30 |
| MSM5524 | 11.30 |
| MSM5525 | 7.85 |
| MSM5526 | 7.85 |
| MSM5527 | 9.75 |
| MSM55271 | 9.75 |
| ICM7106CP | 9.55 |
| ICM7107CP | 9.55 |
| ICM7216B | 19.25 |
| ICM7217A | 9.50 |
| SP8629 | 3.85 |
| SP8647 | 6.00 |
| 95H90PC | 6.00 |
| HD10551 | 2.45 |
| HD4015 | 4.45 |
| HD12009 | 6.00 |
| HD44752 | 8.00 |

VOLTAGE REGULATORS

| | |
|-----------|------|
| 78Series | 0.95 |
| 79Series | 1.00 |
| 78MSeries | 0.65 |
| 78LSeries | 0.35 |
| 79L5 | 0.85 |
| 78M2C | 1.75 |
| 79M2C | 1.75 |
| 723CN | 0.65 |
| L200 | 1.95 |
| TDA1412 | 0.75 |
| NE5553N | 1.25 |
| LM317MP | 1.48 |
| LM337MP | 1.48 |

CRYSTAL FILTER PRODUCTS

| | |
|-----------------------|-------|
| 10.7MHz 2 POLE TYPES: | |
| 10M15A 15KHz BW | 2.49 |
| 10.7MHz 8 POLE TYPES: | |
| 10M4B1 15KHz BW | 14.50 |
| H4402 7.5KHz BW | 15.50 |
| 10M22D 2.4KHz SSB | 17.20 |
| HF FIRST FILTER: | |
| B34F8A 34.5MHz HF | 32.00 |

RADIO CONTROL CRYSTALS

| | |
|-------------------|------|
| AM TX:- | |
| 3rd OT 30pF HC25U | 1.65 |
| AM/FM RX:- | |

Why the Sinclair ZX80 is Britain's best-selling personal computer.

Built: £99.95

Including VAT, post and packing, free course in computing, free mains adaptor.

Kit: £79.95

Including VAT, post and packing, free course in computing.

This is the ZX80. A really powerful, full-facility computer, matching or surpassing other personal computers at several times the price. 'Personal Computer World' gave it 5 stars for 'excellent value'. Benchmark tests say it's faster than all previous personal computers.

Programmed in BASIC – the world's most popular language – the ZX80 is suitable for beginners and experts alike. And response from enthusiasts has been tremendous – over 20,000 ZX80s have been sold so far!

Powerful ROM and BASIC interpreter

The 4K BASIC ROM offers remarkable programming advantages:

- * Unique 'one-touch' key word entry: the ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST, etc.) have their own single-key entry.
- * Unique syntax check. A cursor identifies errors immediately.
- * Excellent string-handling capability – takes up to 26 string variables of any length. All strings can undergo all relational tests (e.g. comparison).
- * Up to 26 single dimension arrays.
- * FOR/NEXT loops nested up to 26.
- * Variable names of any length.
- * BASIC language also handles full Boolean arithmetic, condition expressions, etc.
- * Randomise function, useful for games and secret codes, as well as more serious applications.
- * Timer under program control.
- * PEEK and POKE enable entry of machine code instructions.
- * High-resolution graphics.
- * Lines of unlimited length.

Unique RAM

The ZX80's 1K-BYTE RAM is the equivalent of up to 4K BYTES in a conventional computer – typically storing 100 lines of BASIC.

No other personal computer offers this unique combination of high capability and low price.



The ZX80 as a family learning aid. Children of 10 years and upwards are quick to understand the principles of computing – and enjoy their personal computer.

The Sinclair teach-yourself BASIC manual


If the specifications of the Sinclair ZX80 mean little to you – don't worry. They're all explained in the specially-written 128-page book (free with every ZX80). The book makes learning easy, exciting and enjoyable, and represents a complete course in BASIC programming – from first principles to complex programs.

Kit or built – it's up to you

In kit form, the ZX80 is pleasantly easy to assemble, using a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9V DC nominal unregulated. If not, see the coupon.

Both kit and built versions come complete with all necessary leads to connect to your TV (colour or black and white) and cassette recorder. Plug in and you're ready to go. (Built versions come with mains adaptor.)

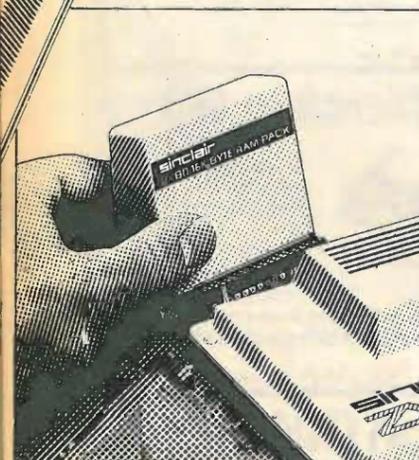Now available for the ZX80... New 16K-BYTE RAM pack



Massive add-on memory. Only £49.95.

The new 16K-BYTE RAM pack is a complete module designed to provide you – and your Sinclair ZX80 – with massive add-on memory. You can use it for those really long and complex programs – or as a personal database. (Yet it can cost as little as half the price of competitive add-on memory for other computers.)

For example, you could write an interactive or 'conversational' program to show people what your ZX80 can do. With 16K-BYTES of RAM, they could be talking to your computer for hours!

Or you can store a mass of data – perhaps in a fairly simple program – such as a name and address list, or a telephone directory.

And by linking a number of separate programs together into one giant, but modular, program, you can achieve the same effect as loading several programs at once.


We're also confident that it won't be long

before you can buy cassette-based software using the full 16K-BYTE RAM. So keep an eye on the personal computer magazines – and brush up your chess perhaps!

The RAM pack simply plugs into the existing expansion port on the rear of the ZX80. No wires, no soldering. It's a matter of seconds and you don't need another power supply. You can only add one RAM pack to your ZX80 – but with 16K-BYTES who could want more!

How to order

Demand for the ZX80 exceeds all other personal computers put together! So use the coupon to order today for the earliest possible delivery. All orders will be despatched in strict rotation. We'll acknowledge each order by return, and tell you exactly when your ZX80 will be delivered. If you choose not to wait, you can cancel your order immediately, and your money will be refunded at once. Again, of course, you may return your ZX80 as received within 14 days for a full refund. We want you to be satisfied beyond all doubt – and we have no doubt that you will be.

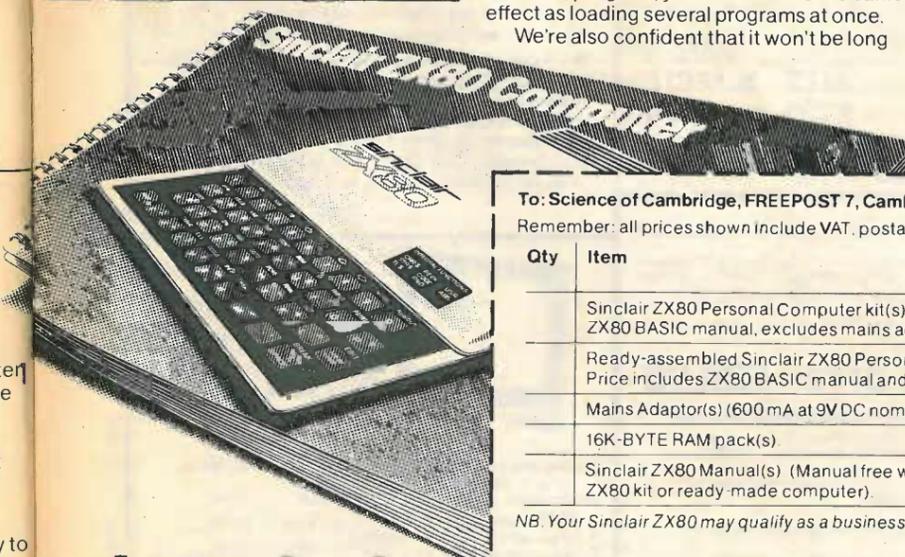

To: Science of Cambridge, FREEPOST 7, Cambridge CB2 1YY.

Remember: all prices shown include VAT, postage and packing. No hidden extras. Please send me:

| Qty | Item | Code | Item price £ | Total £ |
|-----|---|------|--------------|---------|
| | Sinclair ZX80 Personal Computer kit(s). Price includes ZX80 BASIC manual, excludes mains adaptor. | 02 | 79.95 | |
| | Ready-assembled Sinclair ZX80 Personal Computer(s). Price includes ZX80 BASIC manual and mains adaptor. | 01 | 99.95 | |
| | Mains Adaptor(s) (600 mA at 9V DC nominal unregulated) | 03 | 8.95 | |
| | 16K-BYTE RAM pack(s) | 18 | 49.95 | |
| | Sinclair ZX80 Manual(s) (Manual free with every ZX80 kit or ready-made computer). | 06 | 5.00 | |

NB. Your Sinclair ZX80 may qualify as a business expense.

TOTAL: £

I enclose a cheque/postal order payable to Science of Cambridge Ltd for £ _____
Please print

Name: Mr/Mrs/Miss _____

Address _____

FREEPOST – no stamp needed.

WRW 01

sinclair ZX80
Science of Cambridge Ltd.


6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Tel: 0223 311488.

WW – 014 FOR FURTHER DETAILS

From Newtronics

THE NEW EXPLORER/85 SYSTEM

EXPLORER/85 PROFESSIONAL COMPUTER KIT

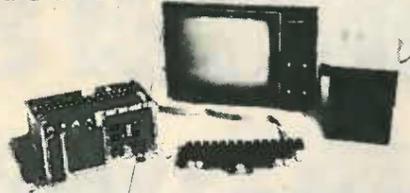

An inexpensive 8085, S100 Based Computer System designed for maximum flexibility. Now available with 8" Floppies

The EXPLORER/85 offers you real design flexibility — you can build the exact system you require. EXPLORER/85 can be your Beginners System, OEM Controller or IBM formatted 8" Disc System. You don't buy more than you need. Prices start from £85.

Here's the line up:

Intel 8085 microprocessor. 8355 as a really powerful 2K Monitor system. 8155 RAM I/O all on one single Mother board with room for RAM/ROM/PROM/EPROM and two S-100 pads (expands to six), plus plenty of prototype space.

The 8085 is 100% compatible with the 8080 but 50% faster. The 8355 ROM 2K monitor system includes cassette interface with tape control. Two 8-bit programmable I/O ports, automatic baud rate selection, labelling of cassette files, etc. 8155 RAM I/O features ¼K "scratch pad". Two programmable 8-bit and one programmable 14-bit binary counter-timer. Plus many other features which cannot be included due to lack of space.

You can purchase the EXPLORER/85 Mother board (level A) at this point for as little as £85 or we'll supply it with address decoding and data drives plus wait state generator and separate regulators (level B), 4K Workspace (level D), 8K Microsoft Basic in ROM for £233 in kit form of £293 assembled and tested.

If you don't possess a VDU you can add our Keyboard Terminal (less monitor) which features a full ASCII keyboard with upper and lower case with cursor control. Video Display board which is microprocessor controlled giving 64 or 32 (on TV) Characters by 16 lines adding up to a full computer system having 4K workspace at a special price of £299 (less P.S.U. and monitor/TV).

Compare these prices carefully and you'll find you are actually getting more for your money.

4K space not enough? Then it's "JAWS" for you (see below) and you can go up to 64K in 16K steps. We'll let you have a 16K EXPLORER/85 for only £399.

Like a Floppy Disc system? We now have an 8" Drive system with CP/M. We will quote you for a complete system either in kit form or assembled ready to go.

LET NEWTRONICS HELP YOU EXPAND YOUR SYSTEM 8" FLOPPY DISC SYSTEM

8" Control Data Corp Professional Drive
 * LSI Controller * Write protect * Single or Double density * Capacity 400K Bytes (SD) 800K Bytes (DD) unfur matted * Access time 25ns. Price £350.

DISC CONTROLLER I/O BOARD
 Controls up to 4 Drives * 1771 ALSI (SD) floppy disc controller * On board data separator (IBM compatible) * 2716 PROM socket included for use in custom applications * On board crystal controlled * On board I/O baud rate * Two serial I/O ports * Autoboot to disc system when system reset * Generators to 9600 baud * Double-sided PC board (glass epoxy). Price £150.

DISC DRIVE CABINET WITH POWER SUPPLY
 De Luxe steel cabinet to house single drive with power supply unit to ensure maximum reliability and stability. Price £79.

DRIVE CABLE SET-UP FOR TWO DRIVES
 Price £19.00

SAVE £30 by purchasing complete single drive system. One 8" drive, F.D.C. board, cabinet/PS.U. and cables. Regular price £598, Special price £568.

CP/M 1.4 £75 CP/M 2.2 £98. Extended Microsoft Basic £213 (Includes CP/M 2.2).

64K 'JAWS' S100 DYNAMIC RAM BOARD

We offer you Hidden refresh fast performance lower power consumption latched data outputs 200ns 4116 RAM's on board crystal 8K bank selectable fully socketed solder mask on both side of the board

Designed for 8080, 8085 and Z80 bus signals works in Explorer/85, Tuscan, Horizon, Sol, as well as all other well-designed S100 computers.

| WIRED KITS | | & TESTED | | WIRED KITS | | & TESTED | |
|------------|------|---------------|-----|------------|------|----------|--|
| 16K | £149 | £169 | 48K | £239 | £259 | | |
| 32K | £194 | £214 | 64K | £284 | £304 | | |
| | | 16K expansion | | £45 | | | |

ELF II



SPECIFICATION
 *RCA 1802 8 bit microprocessor with 256 byte RAM expandable to 64K bytes.
 *RCA 1861 video IC to display program on TV screen via the RF Modulator Single Board with Professional hex keyboard - fully decoded to eliminate the waste of memory for keyboard decoding circuits. Load, run and memory protect switches. 16 Registers, Interrupt, DMA and ALU Stable crystal clock. Built in power regulator 5 slot plug in expansion bus (less cabinet price).

SPECIAL XMAS OFFER £39.95

ELF II BOARD WITH VIDEO OUTPUT FEATURING THE RCA COSMAC 1802 cpu STOP reading about computers and get your "hands on" an ELF II and Tom Pitman's short course. ELF II demonstrates all the 91 commands which an RCA 1902 can execute, and the short course speedily instructs you how to use them.

ELF II's VIDEO OUTPUT makes it unique among computers selling at such a modest price. The expanded ELF II is perfect for engineers, business, industry, scientific and educational purposes.

ELF II EXPANSION KITS
 Once you've mastered your ELF II you can then expand it to a full 64K microcomputer with our range of ELF II expansion kits. — Hardware — Firmware — Software — Manuals.

NOW AVAILABLE BASIC LEVEL III with R.P.N. Maths package. Both cassette and EPROM versions.

SEND SAE FOR COMPREHENSIVE BROCHURE

Please add VAT to all prices. P&P extra Please make cheques and postal orders payable to NEWTRONICS or phone your order quoting BARCLAYCARD. ACCESS number

We are open for demonstrations and Sales Monday-Saturday. 9.30 a.m - 6.30 p.m. Near Highgate Underground on main A1 into London.

Oki Microline 80



Small, light, quiet matrix printer.

40, 80 or 132 cols. 6 or 8 lines per inch. 96 ASC II + 64 graphics character set with Centronics compatible interface £369

Epson MX 80

— the worlds first printer with disposable print head

*9 x 9 dot matrix * Logic Seeking * Bi-directional * 96 ASCII Characters * 64 Graphics and 8 International Characters * Centronics I/P with optional RS232 and IEEE 488 * Four print densities 40, 80, 66 or 132 columns * Multiple type fonts * Self Test * Self Diagnostics * Buzzer for end of paper and bell code error

ONLY £399



TVM-10 MONITOR

DUE TO BULK BUYING

£99.50 NOW £79.95

IDEAL FOR APPLE NASCOM U.K. 101, ETC.

- Designed for monitoring computers, closed circuit TV and Video Tape Recorders
 - 10" black and white video monitor
 - 10 MHz band width
 - High-quality metallic cabinet
 - Dimensions: 9" x 9" x 9½"
- Trade Enquiries Welcome



Newtronics
 255 ARCHWAY ROAD, LONDON, N.6
 TEL. 01-348 3325

WW — 047 FOR FURTHER DETAILS

NEW! DMM BREAKTHROUGH!


If you want an Autoranging, Auto Unit Display, 3½-digit LCD DMM. For only

£39.95

(inc VAT)

We've got to hand it to you!

The Incredible 6200

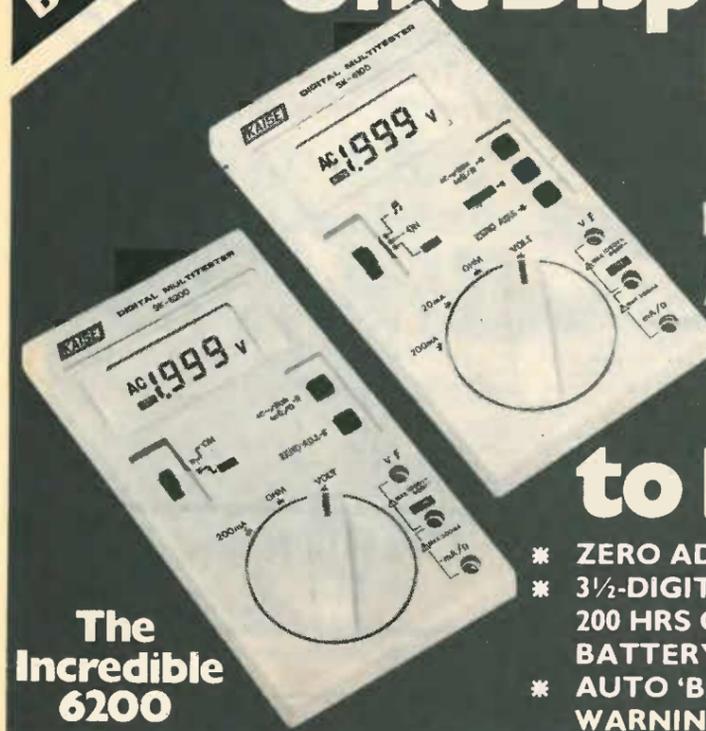

- * ZERO ADJUSTMENT
- * 3½-DIGIT LCD WITH 200 HRS CONTINUOUS BATTERY LIFE
- * AUTO 'BATT' WARNING
- * FULL AUTORANGING
- * AUTO UNIT DISPLAY
- * CONTINUITY TEST (6110 and 6100 only)
- * 10 AMP AC/DC (6110 and 6220 only)

Introducing the latest professional state-of-the-art 3½-digit DMM — at really old-fashioned prices! From just an unbelievable £39.95 inc. VAT, plus £1.15 p&p!

| | 6100 | 6110 | 6200 | 6220 |
|--------------------------------|--|--------------|--------------------|--------------|
| RESOLUTION | 1 mV, 10µA, 0.1 Ω | | 1 mV, 100µA, 0.1 Ω | |
| FULL AUTO RANGING | ✓ | ✓ | ✓ | ✓ |
| RANGE HOLD | ✓ | ✓ | ✓ | ✓ |
| UNITS OF MEASUREMENT DISPLAYED | mV, V, mA | mV, V, mA, A | mV, V, mA | mV, V, mA, A |
| FUNCTIONS DISPLAYED | Ω, KΩ, AUTO, BATT, ADJ, LO, — and AC | | | |
| MEASURES DC VOLTAGE TO | 1000V | 1000V | 1000V | 1000V |
| MEASURES AC VOLTAGE TO | 600V | 600V | 600V | 600V |
| MEASURES AC DC CURRENT TO | 200mA | 10A | 200mA | 10A |
| MEASURES RESISTANCE TO: | 2 Megohms | 2 Megohms | 2 Megohms | 2 Megohms |
| ZERO ADJUSTMENT | ✓ | ✓ | ✓ | ✓ |
| ACCURACY | 0.5% | 0.5% | 0.8% | 0.8% |
| LOW POWER OHM RANGES | For in-circuit resistance measurements on all models | | | |
| BUZZER — Continuity Test | ✓ | ✓ | ✓ | ✓ |
| BUZZER — Over Range Indicator | ✓ | ✓ | ✓ | ✓ |
| COMPLETE WITH | Batteries, pair of Test Leads, Spare Fuse, six months' guarantee | | | |
| PRICE | ONLY £64.95 | ONLY £74.95 | ONLY £39.95 | ONLY £49.95 |
| p&p | £1.15 | £1.15 | £1.15 | £1.15 |

Why such a low, low price? Because the A/D converter and display are custom built! This is a genuine top-spec DMM. Check these features for unbeatable value — you won't find a hand-held DMM with these features at these prices again!

I believe you! Please send me the DMM s as marked.

- _____ 6200 @ £41.10 each, inc. VAT, p&p. Total price £ _____
- _____ 6220 @ £51.10 each, inc. VAT, p&p. Total price £ _____
- _____ 6100 @ £66.10 each, inc. VAT, p&p. Total price £ _____
- _____ 6110 @ £76.10 each, inc. VAT, p&p. Total price £ _____

ACCESS orders taken. Please write card no: and signature.

ACCESS NO _____
 Name _____
 Address _____

Total cash cheque enclosed £ _____
 Cheques payable to
 Maclin-Zand Electronics Ltd., please.



Signed _____

38 Mount Pleasant, London WC1X 0AP.
 Tel. 01-278 7369 01-837 1165

Maclin-Zand

To: Maclin-Zand Electronics Ltd., 38 Mount Pleasant, London WC1X 0AP.
 For overseas orders, please add £5 to cost of total order package.

Making state-of-the-art affordable.

4WW

BUILT FOR RELIABILITY




Newport Range—

Sound reinforcement and public address amplifiers; 30, 60, 120 or 200 watts— with a range of 10 models for free standing and rack mounting use— engineered for reliability



Audix Limited, Station Road, Wenden, Saffron Walden, Essex CB11 4LG
Tel: Saffron Walden (0799) 40888; Telex: 817444

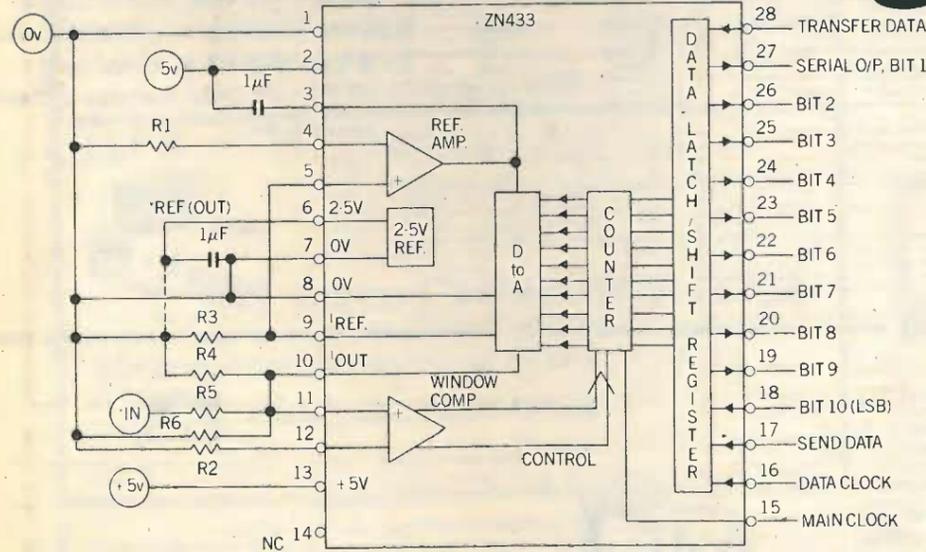ZN433. The world's first 10-bit tracking ADC.



ZN433 is a monolithic 10-bit tracking ADC with on-chip 2.5 volt precision reference and is ideal for continuous tracking of analogue signals. Using Ferranti monolithic ADC's will not only give you reliable performance but reduce your costs.

Send for data or contact IC Marketing, Ferranti Electronics Limited, Fields New Road, Chadderton, Oldham, OL9 8NP. Telephone: 061-624 0515 Telex: 668038

FERRANTI
Semiconductors

WW — 049 FOR FURTHER DETAILS



5 HZ TO 100 MHz

TOMORROW'S TOOLS TODAY

CONTINENTAL SPECIALTIES CORPORATION



C.S.C. (UK) Limited Dept. 7D
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex. CB11 3AQ
Telephone: Saffron Walden (0799) 21682
Telex: 817477

Instant frequency indication from 5Hz to 100MHz; no range selection problems; a brilliant 8-digit LED display; mains or battery operation; an accuracy of 4 parts per million ± 1 count; and totally automatic operation — all this for only £77.55* with CSC's new Max-100 frequency counter.

Just take a look at our spec. Where else could you find anything similar at the price?
*Frequency range 5Hz - 100 MHz *Input impedance 1M shunted by 10pF *Sensitivity 30mV from 1KHz up to 50MHz; 120mV r.m.s. over full frequency range *Timebase accuracy ± 4 parts in 10⁶ (from 5 to 45°C) *Maximum aging rate 10 parts in 10⁶ per year *Over-frequency indication *Low-battery-power alarm *Operates from dry or rechargeable cells, an external 7.5 to 10VDC supply, or a car battery (via an adaptor) *Dimensions: 45 x 187 x 143mm *Options: 12V adaptor; battery eliminator; r.f. antenna, low-loss r.f. tap, carrying case.

Fill in the coupon for further details . . . *price excludes post, packing and VAT

C.S.C. (UK) Limited, Dept. 7D, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

| | | | | |
|---------|---------------|----------------------------|--------|-----------|
| MAX 100 | FREQ. COUNTER | Unit price inc P&P 15% VAT | £90.91 | Only Rent |
|---------|---------------|----------------------------|--------|-----------|

Name _____
Address _____

I enclose cheque/P.O. for £ _____ or debit my Barclaycard/Access/American Express card no. _____ exp. date _____

FOR IMMEDIATE ACTION — The C.S.C. 24 hour, 5 day a week service. Telephone (0799) 21682 and give us your Barclaycard, Access, American Express number and your order will be in the post immediately.

For FREE catalogue tick box

MORE SPEC. FOR YOUR MONEY

TYPE 747 UNIVERSAL COUNTER TIMER

DC to 150MHz 8 DIGITS, 3 CHANNELS

MEASURES —

- FREQUENCY Ch A and Ch C
- PERIOD Ch A
- TIME \pm Ch A to \pm Ch B
- PULSE WIDTH Ch A + or —
- COUNT Ch A (may be gated and reset by B & C)



£175

AVERAGES 1 to 1000 events & 3.50 carriage, ins. etc.

TYPE 745 COUNTER TIMER

DC to 32MHz 5 DIGITS

MEASURES —

- FREQUENCY
- PERIOD
- TIME
- COUNT
- 6 GATE TIMES/TIME UNITS
- 10 μ S to 1S



£116.38

& £3 carriage, ins. etc.

TYPE 746 AUTORANGING FREQUENCY METER £84.88

1Hz to 99.9KHz

TYPE 615 OFF-AIR STANDARD £97.13

10MHz, 1MHz and 100KHz

OMB ELECTRONICS, RIVERSIDE, EYNSFORD, KENT DA4 0AE
Tel. Farningham (0322) 863567

Prices, which are CWO and ex-VAT, are correct at the time of going to press and are subject to change without notice.

FROM OMB ELECTRONICS
WW — 021 FOR FURTHER DETAILS

Rank Radio International
Watton Road Ware Hertfordshire England Tel. WARE 3966 Telex 81344
A DIVISION OF THE RANK ORGANISATION

The Service Engineers Guide to Teletext

Rank Radio International, first in the field with Teletext receivers, have prepared this hardback book especially for the engineer and the enthusiast.

Based on practical experience, the book is written in simple, easy to understand language and gives an introduction to the theory and design of the Teletext system as well as simple explanations of "gates" and digital theory.

SPECIAL OFFER £1.75+P&P WHILE STOCKS LAST

There are nine chapters as follows:

1. Introduction to Teletext
2. Teletext Transmission System
3. Decoders
4. Tifax Module Interfaces
5. The Teletext Receiver
6. Teletext Receiver Installation
7. Adding Text to typical mono/colour receivers
8. Remote Control Systems
9. Introduction to Digital Units

The hardback* concludes with a very useful glossary of the jargon used in this sphere of technology.

*This offer applies to United Kingdom only

ORDER FORM

Please send _____ copies of THE SERVICE ENGINEERS GUIDE TO TELETEXT at a special price of £2.00 (1.75 +25p P&P).

NAME _____
ADDRESS _____

Cheque/PO enclosed value _____

Please send orders to: Rank Radio International, Watton Road, Ware, Herts.
*This offer applies to United Kingdom only

WW — 055 FOR FURTHER DETAILS

SEMI-CONDUCTORS

High quality - good value



Extensive range of Germanium and Silicon semi-conductors. Quick delivery from stock. Exporters of international repute, established over 20 years. Direct supplies for OEM, industrial and rental users and wholesalers. Private and retail users please send for list of distributors. Overseas distributor enquiries welcomed. Write, ring or telex for details and prices:

Edicron

Edicron Ltd., Redan House, Redan Place, London W2 4SA
Telephone: 01-221 4717 Telex: 265531

Germanium and Silicon Semi-conductors • Valves • Tubes • TV tube guns
WW - 040 FOR FURTHER DETAILS

CB RADIO ACCESSORIES

THE LARGEST DISTRIBUTORS OF CB ACCESSORIES IN THE U.K. Come and see the biggest and best selection of CB Radio Accessories from all the leading manufacturers, including:

COMMUNICATION ANTENNAS

HA HARADA K40

WT

TELEX

Mura CORPORATION-SA

TELED CB PRODUCTS

SIRTEL

TURNER

CB by ARISTA

SWR METERS including RAMA, HANSEN etc.

THE ANTENNA SPECIALISTS CO.

Sole UK agents for:-

Mura Electronics (UK) Ltd., 79 Church Rd, Hendon, London NW4 Tel: 01 203 5277/8

THE CINTEC SINUSOIDAL FREQUENCY AND VOLTAGE STABILIZER



- ### APPLICATIONS
- * SOUND RECORDING
 - * VIDEO RECORDING
 - * MEDICAL
 - * MARINE
 - * COMPUTERS
 - * NAVIGATIONAL SYSTEMS

Applications for the use of CINTEC FREQUENCY & VOLTAGE STABILIZER are more numerous than can be listed. Therefore, if you have a supply problem, contact CINTEC LIMITED whose engineers will be only too pleased to assist.

The CINTEC FREQUENCY & VOLTAGE STABILIZER provides the answer to both these problems

- * 500VA OR 250VA
- * SOLID STATE
- * HIGH STABILITY
- * ROBUST
- * VERSATILITY
- * RELIABILITY
- * SINUSOIDAL

When the supply frequency is fluctuating wildly, between 45Hz and 65Hz and the voltage by more than 10% the output from the Stabilizer will not vary more than .01% from 50Hz or 1% in voltage, even when different loads are imposed.

Used by Government establishments, oil rigs, hospitals, police, video and electronic industry, shipbuilders etc, for a wide range of applications including video systems, medical, frequency conversion, navigational aids and sound recording systems.

Reliable Frequency & Voltage Stabilization

The efficient operation of sophisticated electrical and electronic equipment is, in many instances, dependent upon an electrical supply which is stable in both frequency and voltage.

In many countries and even in the United Kingdom during periods of heavy demand, the variation in the frequency and voltage is sufficient to introduce errors and the malfunction of such items as Recording equipment etc. Likewise, in certain areas, the only source of supply is from a Generator, the output of which can vary considerably when different loads are imposed. This has precluded the use of a wide range of equipment in many countries. Voltage Stabilizers are readily available but these do not stabilize the frequency of the supply which, in many instances, is essential.

The CINTEC FREQUENCY & VOLTAGE STABILIZER is also available for supplies of 100-125 volts, 45-65Hz with an alternative output of 50Hz or 60Hz at 115 volts or 230 volts and as a dual frequency model with a switchable output of 50Hz or 60Hz.

The Stabilizer may also be used as a frequency converter. For example, the supply to it can be any frequency between 45-65Hz and the output can be switched to either 50Hz or 60Hz.

Cintec Ltd., Wandle Way, Mitcham, Surrey CR4 4NB, England. Tel: 01-640 2241. Telex: 946177

SPECIFICATION

| | |
|---------------|--|
| INPUT | 105-125 volts or 210-250 volts at 45-65Hz. |
| OUTPUT | 115 volts or 230 volts |
| RATING | 500VA or 250VA |
| STABILITY | Voltage $\pm 1\%$ No load to full load— Frequency $\pm 0.01\%$ No load to full load |
| FREQUENCY | 50Hz or 60Hz. Single or dual versions |
| WAVEFORM | SINUSOIDAL |
| DISTORTION | Less than 2%. |
| AMB TEMP | -20°C to +40°C |
| COOLING | Fan cooled |
| DUTY | Continuous |
| DIMENSIONS | 432 (W) x 196 (H) x 508mm (D) (17" x 7 3/4" x 20") |
| WEIGHT | 45 or 30Kg unpacked |
| CONSTRUCTION | Cabinet or rack mounting |
| TERMINATION | Cannon Connectors at rear of case |
| NATO CODIFIED | 24V OC Inverter |

In addition to the A.C. operated models, a 24v D.C. INVERTER Stabilizer is available which operates from a heavy duty 24 volt battery and has output ratings similar to the A.C. models. This type of Stabilizer is particularly suitable for mobile operation.

Detailed Specification and Brochure - Available Post Coupon or Telephone/Telex

Name _____

Position _____

Company _____

Address _____

WW6

CINTEC LTD

Wandle Way, Mitcham, Surrey CR4 4NB. England. Telephone: 01-640 2241 Telex: 946177


WW-012 FOR FURTHER DETAILS

Join the Professionals...

Crimson modular audio amplifiers feature: ★Low values of transient and steady state distortions ★Envelope distortion (below 500 Hz) less than 0.05% ★on-board electronic protection ★P.C.B. pin and edge connector termination ★Full range of complimentary components, i.e. P.S.U.'s, heatsinks etc. available from Crimson.

The Crimson range of amplifier modules are built to very high standards and have earned an enviable reputation in every field to which they have been applied. The boards come ready built and tested (guaranteed for two years) and can be used to advantage where high quality signal amplification is required. The power amplifier modules range from 60WRMS to 310WRMS with up to twice this amount in bridge mode. All feature substantial heatsink brackets which can be bolted to any available heatsink or the Crimson purpose designed types. Input sensitivity is set at 775mV and power supply requirements are catered for by one of the three Crimson toroidal power supplies. The Pre-amplifier module (CPR1) is basically a phono amplifier with sophisticated circuitry incorporating R.I.A.A. equalisation. Also on-board is auxiliary amplification for tape and tuner inputs. A separate module (MC1) is also available and the required boost for low output moving coil type cartridges. External components required are potentiometers for volume and balance, switches for signal routing and a regulated ±15V D.C. power source (REG1). Complementary this range, are the electronic crossover modules XO2/XO3 which, with a special muting board (MU1) can be incorporated in all types of active speaker systems.

Numerous applications are possible with Crimson modules. For example, a complete Hi-Fi Pre & Power amplifier of 40-125WRMS/channel can be built using our Hardware kits (see Hobby Electronics review, August 1980). Alternatively, Mono or Stereo slave amps of up to 500WRMS can be built into proprietary flight cases, while other uses include active loudspeaker systems such as designed by R.I. Harcourt in Wireless World October/November 1980. Further details of how to use the modules are contained in the Users/Application Manual available at £0.50.

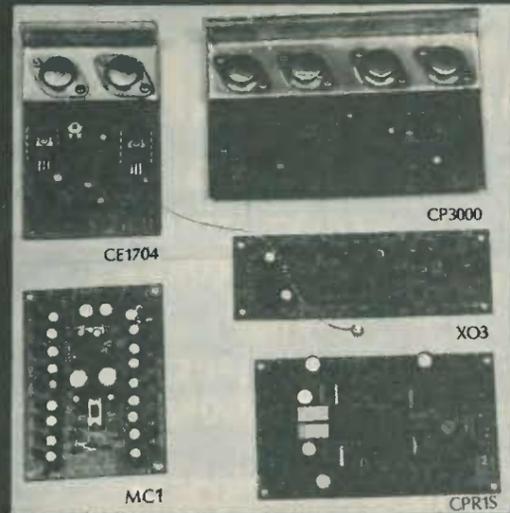

| SPECIFICATIONS | | | | | | | | | | |
|----------------|------------|-------------|------|-----------|--------|-------|-------------|--------------|-------------------------------------|----------------|
| Type | O/P/8ohms* | O/P/16ohms* | PSU | H/Sinks | Slew | S/N | Sensitivity | T.H.D. (typ) | F.R. | Size |
| CE 608 | 38 | | CPS1 | 50mm | 30V/μs | 110dB | 775mV | 0.0035% | 1.5Hz 50kHz/1 30dB | 80 x 120 x 25 |
| CE1004 | 44 | 70 | CPS2 | 100mm | 30V/μs | 110dB | 775mV | 0.0035% | 1.5Hz 50kHz/1 30dB | 80 x 120 x 25 |
| CE1008 | 66 | | CPS3 | 100mm | 30V/μs | 110dB | 775mV | 0.0035% | 1.5Hz 50kHz/1 30dB | 80 x 120 x 25 |
| CE1704 | 85 | 121 | CPS6 | 150mm/FM1 | 30V/μs | 110dB | 775mV | 0.0035% | 1.5Hz 50kHz/1 30dB | 80 x 120 x 25 |
| CE1708 | 125 | | CPS6 | 150mm/FM1 | 30V/μs | 110dB | 775mV | 0.0035% | 1.5Hz 50kHz/1 30dB | 161 x 102 x 25 |
| CP3000 | | 250 | CPS6 | FM2 | 30V/μs | 110dB | 775mV | 0.0035% | 1.5Hz 50kHz/1 30dB | 161 x 102 x 25 |
| CPR15i | Output | 77mV | REG1 | | 3V/μs | 70dB | 2.8mV/RMS | 0.008% | 20Hz 20kHz | 80 x 120 x 25 |
| MC1S | Output | 2mV | REG1 | | 3V/μs | 65dB | 70μV/150 | 0.008% | 20Hz 20kHz | 80 x 120 x 25 |
| XO2/XO3 | Output | 775 2500mV | REG1 | | 3V/μs | 90dB | 775mV | 0.01% | C over points see set 150 x 50 x 20 | |


*Power output is quoted WRMS and is given for two modules run off the same power supply. Higher powers are obtainable if using one module per P.S.U. or if using a stabilised P.S.U.

| PRICES - HELD FROM MAY - TO FEB 80 | | | |
|------------------------------------|----------------------|--------------|--------|
| Power Amplifier Modules | Power Supply Modules | Heatsinks | |
| CE 608 | £21.00 | CPS1 180V/A1 | £19.50 |
| CE1004 | £24.50 | CPS2 150V/A1 | £23.50 |
| CE1008 | £27.50 | CPS6 250V/A1 | £31.00 |
| CE1704 | £35.00 | REG1 | £9.30 |
| CE1708 | £35.00 | TR6 | £2.50 |
| Pre-Amplifier Modules | Active Crossovers | Hardware | |
| CPR1 | £34.00 | XO2 | £18.00 |
| CPR15 | £46.50 | XO3 | £28.25 |
| MC1 | £26.00 | MU1 | £7.50 |
| MC1S | £37.00 | | £1.90 |

EE Crimson Elektrik
9 CLAYMILL ROAD, LEICESTER LE4 7JJ, ENGLAND. Tel 0533 761920 Telex 34694 Chanco G CRIMLEK
WW-053 FOR FURTHER DETAILS

PLEASE SEND ME MORE DETAILS OF ALL CRIMSON ELEKTRIK AMPLIFIERS
Name _____
Address _____

Cushman

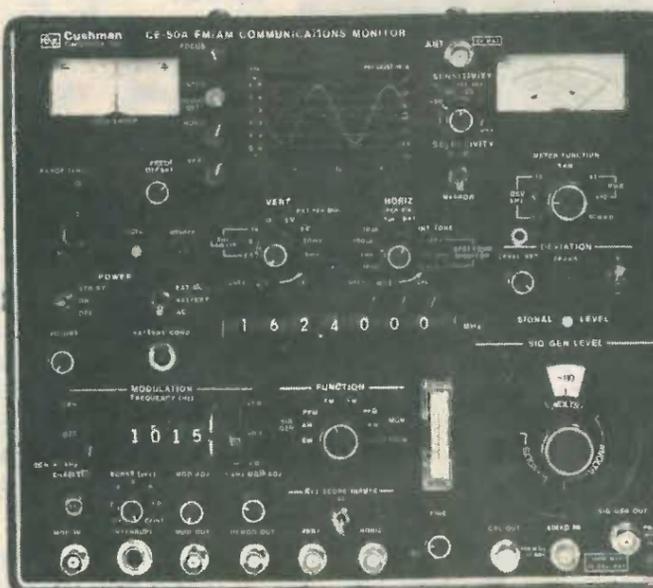

Compact, versatile field service monitors for two-way radio maintenance

CE-50A: FM/AM Field Service Monitor
CE-50A-1: FM/AM Field Service-Spectrum Monitor

Exclusive representative:
Aspen Electronics Limited
Communications Equipment and Components
2 Kildare Close, Eastcote, Ruislip, Middlesex HA4 9UR
Telephone: 01-868 1188
Telex: 8812727



WILMSLOW AUDIO

The firm for Speakers



HI-FI DRIVE UNITS



PA GROUP & DISCO UNITS



WILMSLOW AUDIO



SPEAKER KITS

- | | | | |
|---|-------------------|---|--------------|
| Audax HD12.9D25 | £8.25 | Celestion G12/50TC | £19.50 |
| Audax HD11P25EBC | £7.50 | Celestion G12/80CE | £24.50 |
| Audax HD20B25H4 | £14.95 | Celestion G12/80TC | £23.75 |
| Audax HD13D34H | £12.95 | Celestion G12/125CE | £42.00 |
| Audax HD24S45C | £21.95 | Celestion G15/100CE | £37.95 |
| Baker Superb | £25.00 | Celestion G15/100TC | £36.50 |
| Castle Super 8 RS/DD | £14.95 | Celestion G18/200 | £64.75 |
| Chartwell CEA205 | pairs only £81.25 | Celestion HF1300 | £12.50 |
| Coles 4001 | £7.65 | Celestion HF2000 | £12.50 |
| Coles 3000 | £7.65 | Celestion Powercell 12/150 | £86.00 |
| Celestion HF1300 II | £10.95 | Celestion Powercell 15/250 | £88.00 |
| Celestion HF2000 | £10.95 | Celestion MH1000 | £21.75 |
| Dalesford ABR 10" | £10.25 | Fane Classic 45 12" | £13.95 |
| Dalesford D30/110 | £11.25 | Fane Classic 55 12" | £15.50 |
| Dalesford D50/153 | £12.25 | Fane Classic 80 12" | £19.75 |
| Dalesford D50/200 | £12.25 | Fane Classic 85 15" | £26.00 |
| Dalesford D70/250 | £25.50 | Fane Classic 150 15" | £37.95 |
| Dalesford D100/310 | £35.75 | Fane Classic 125 18" | £43.95 |
| Dalesford D10 tweeter | £8.45 | Fane Classic 175 18" | £47.95 |
| Decca London Horn | £61.95 | Fane Disco 100 12" | £26.25 |
| Eiac BNC204 6 1/2" | £7.50 | Fane PARS 12" | £27.25 |
| Eiac BNC298 8" | £7.95 | Fane Bass 100 15" | £28.75 |
| EMI type 350, 13" x 8", 4 ohm | £9.45 | Fane Crescendo 12E | £26.25 |
| EMI 14A/770, 14" x 9", 8 ohm | £19.50 | Fane Colossus 15E | £74.50 |
| isophon KK10/B | £8.15 | Fane Crescendo 18E | £94.75 |
| Jordan Watts Module | £24.95 | Fane Colossus 18E | £99.95 |
| Jordan Watts HF kit | £10.50 | Fane Colossus 18E | £107.00 |
| Jordan 50mm unit | £24.50 | Fane J44 | £8.90 |
| Jordan CB crossover | £24.50 pair | Fane J73 | £15.95 |
| Jordan Mono crossover | £24.50 pair | Fane HPX1/HPX2 | £10.80 |
| Kef T27 | £9.45 | Fane HPX3A | £3.45 |
| Kef B110 | £12.25 | Fane HPX3B | £5.80 |
| Kef B200 | £13.50 | Goodmans 8PA | £4.55 |
| Kef B139 | £27.75 | Goodmans PP12 | £5.05 |
| Kef DN13 | £6.75 | Goodmans D112 | £22.50 |
| Kef DN12 | £9.40 | Goodmans GR12 | £24.95 |
| Kef DN22 | pair £42.00 | Goodmans 18P | £48.45 |
| Lowther PM6 | £69.00 | Goodmans Hifax 50HX | £21.85 |
| Lowther PM6 Mk I | £82.00 | McKenzie C12100GP | £24.45 |
| Lowther PM7 | £94.50 | McKenzie C12100TC | £24.45 |
| Peerless K010TD | £10.95 | McKenzie GP15 | £35.10 |
| Peerless DT10HFC | £10.50 | McKenzie TC15 | £35.10 |
| Peerless K04DMRF | £13.60 | McKenzie C15 bass | £59.60 |
| Radford BD25 Mk III | £36.95 | Motorola Piezo horn 3 1/2" | £8.50 |
| Radford MD9 | £14.85 | Radford FNB/FNB31 | £12.25 |
| Radford MD6 | £25.50 | Richard Allan CGBT | £13.50 |
| Radford FNB/FNB31 | £22.50 | Richard Allan CG12T Super | £29.50 |
| Richard Allan CGBT | £13.50 | Richard Allan HP88 | £20.75 |
| Richard Allan CG12T Super | £29.50 | Richard Allan LP88 | £14.50 |
| Richard Allan HP88 | £20.75 | Richard Allan HP12B | £33.50 |
| Richard Allan LP88 | £14.50 | Richard Allan DT20 | £9.95 |
| Richard Allan HP12B | £33.50 | Richard Allan DT30 | £10.75 |
| Richard Allan DT20 | £9.95 | SEAS H107 | £6.95 |
| Richard Allan DT30 | £10.75 | Shackman Electrostatic with polar network and crossover | £138.00 pair |
| SEAS H107 | £6.95 | Tannoy DC296 10" | £118.00 |
| Shackman Electrostatic with polar network and crossover | £138.00 pair | Tannoy DC316 12" | £159.00 |
| Tannoy DC296 10" | £118.00 | Tannoy DC386 15" | £199.00 |
| Tannoy DC316 12" | £159.00 | | |
| Tannoy DC386 15" | £199.00 | | |

- KITS FOR MAGAZINE DESIGNS, etc. KITS INCLUDE DRIVE UNITS, CROSSOVERS, BAF/LONG FIBRE WOOL, etc. FOR A PAIR OF SPEAKERS Carriage £3.95 unless otherwise stated**
- Practical Hi Fi & Audio PRO9-TL (Rogers) £148.00
As above but including felt panels £152.75 + £5 carriage
Hi Fi Answers Monitor (Rogers) £146.00
Hi Fi News State of the Art (Atkinson) £185.00
Hi Fi News Miniline (Atkinson) £48.00 + £3 carriage
Hi Fi For Pleasure Compact Monitor (Colloms) £116.00 + £5 carriage
Popular Hi Fi Mini Monitor (Colloms) £74.00
Popular Hi Fi Round Sound (Stephens) including complete cabinet kit £71.00
Popular Hi Fi Jordan System 1 £96.00 + £3 carriage
Practical Hi Fi and Audio BSC3 (Rogers) £65.00
Practical Hi Fi and Audio Monitor (Giles) £180.00
Practical Hi Fi and Audio Triangle (Giles) £120.00
Hi Fi News Tabor (Jones) with J4 bass units £66.00
Hi Fi News Tabor (Jones) with H4 bass units £70.00
Wireless World Transmission Line KEF (Bailey) £126.00
Wireless World Transmission Line RAD-FORD (Bailey) £179.00
Everyday Electronics EE70 (Stephens) £150 + £5 carriage
Everyday Electronics EE20 (Stephens) £29.80 + £3 carriage
- SMART BADGES FREE WITH ABOVE KITS (TO GIVE THAT PROFESSIONAL TOUCH TO YOUR DIY SPEAKERS!)**
- REPRINTS/CONSTRUCTION DETAILS OF ABOVE DESIGNS 10p EACH**
- CARRIAGE & INSURANCE**
TWEETERS/CROSSOVERS 60p each
SPEAKERS 4" to 6 1/2" 80p each
8" to 10" 12", 13" x 8", 14" x 9" £1.95 each
15" £2.95 each
18" £4.50 each
SPEAKER KITS £3.95 pair
MAG DESIGN KITS £3.95 pair unless otherwise stated
ALL PRICES CORRECT AT 1/2/80
- Prices per pair
Carriage £3.75 per
- | | |
|---------------------------------|-------------------------|
| Dalesford System 1 | £54.00 |
| Dalesford System 2 | £67.00 |
| Dalesford System 3 | £104.00 |
| Dalesford System 4 | £110.00 |
| Dalesford System 5 | £142.00 |
| Dalesford System 6 | £95.00 |
| KEF Reference 104a8 kit | |
| KEF Cantata kit | £133.00 + £5 carriage |
| LS3 Micro Monitor kit | £133.50 + £5 carriage |
| Lowther PM6 kit | £71.00 + £3.75 carriage |
| Lowther PM6 Mk I kit | £116.00 |
| Lowther PM7 kit | £122.00 |
| Peerless 1070 | £195.00 |
| Peerless 1120 | £157.00 |
| Peerless 2050 | £169.90 |
| Peerless 2060 | £59.95 |
| Peerless 2060 | £79.95 |
| Radford Studio 90 kit | £181.00 |
| Radford Studio 270 kit | £309.00 |
| Radford Monitor 180 kit | £243.00 |
| Radford Studio 360 kit | £450.00 |
| RAM 50 kit (makes RAM 100) | £76.25 |
| Richard Allan Maramba kit | £77.50 |
| Richard Allan Taho Twin kit | £55.80 |
| Richard Allan Maramba kit | £77.50 |
| Richard Allan Charisma kit | £111.00 |
| Richard Allan Super Triple kit | £102.50 |
| Richard Allan Super Saraband II | £158.95 |
| Richard Allan RAB kit | £82.75 |
| Richard Allan RAB2 kit | £96.75 |
| Richard Allan RAB2L kit | £108.00 |
| SEAS 223 | £42.50 |
| SEAS 253 | £67.00 |
| SEAS 403 | £79.95 |
| SEAS 603 | £134.95 |
| Wharfedale Denton XP2 kit | £31.45 |
| Wharfedale Sheltor XP2 kit | £40.40 |
| Wharfedale Linton XP2 kit | £56.20 |
| Wharfedale Glendale XP2 kit | £69.00 |

ALL PRICES INCLUDE VAT @ 15%

Send 50p for 56 page catalogue 'Choosing a Speaker' (or price list only free of charge)

SWIFT OF WILMSLOW
The firm for Hi-Fi
5 Swan Street, Wilmslow, Cheshire.

Tel: 0625 529599 FOR MAIL ORDER & EXPORT OF DRIVE UNITS, KITS, ETC.
Tel: 0625 526213 (SWIFT OF WILMSLOW) FOR HI-FI & COMPLETE SPEAKER SYSTEMS.

Lightning service on telephoned credit card orders!

WILMSLOW AUDIO
The firm for Speakers

35/39 Church Street, Wilmslow, Cheshire



AMCRON INDUSTRIAL MUSCLE



Model — M600

- ★ POWER RESPONSE DC — 20KHz ± 1dB.
- ★ OUTPUT POWER IN EXCESS OF 1.5kW INTO 2.75 Ohm LOAD (CONTINUOUS R.M.S.).
- ★ D.C. OUTPUT 20 AMPS AT 100 VOLTS OR 2KV_a.
- ★ HARMONIC DISTORTION LESS THAN 0.05% DC-20KHz AT 1kW INTO 6 OHMS
- ★ PLUG-IN MODULES: CONSTANT VOLTAGE/CURRENT, PRECISION OSCILLATORS ★ UNIPOLAR AND BIPOLAR DIGITAL INTERFACES, FUNCTION GENERATORS, AND MANY OTHERS.
- ★ OUTPUT MATCHING TRANSFORMERS AVAILABLE TO MATCH VIRTUALLY ANY LOAD.
- ★ FULL OPEN AND SHORT CIRCUIT PROTECTION GUARANTEED STABLE INTO ANY LOAD.
- ★ TWO UNITS MAY BE CONNECTED TO PROVIDE UP TO 4kW.
- ★ INTERLOCK CAPABILITY FOR UP TO EIGHT UNITS.
- ★ 3-YEAR PARTS AND LABOUR WARRANTY.

For full details on all Amcron Products write or phone Chris Flack




Kirkham Electronics

MILL HALL, MILL LANE, PULHAM MARKET, DISS, NORFOLK IP21 4XL
DIVISION OF K.R.S. LIMITED
TELEPHONE (037 976) 639/594

WW — 064 FOR FURTHER DETAILS

INSTRUMENT CASES AND BOXES

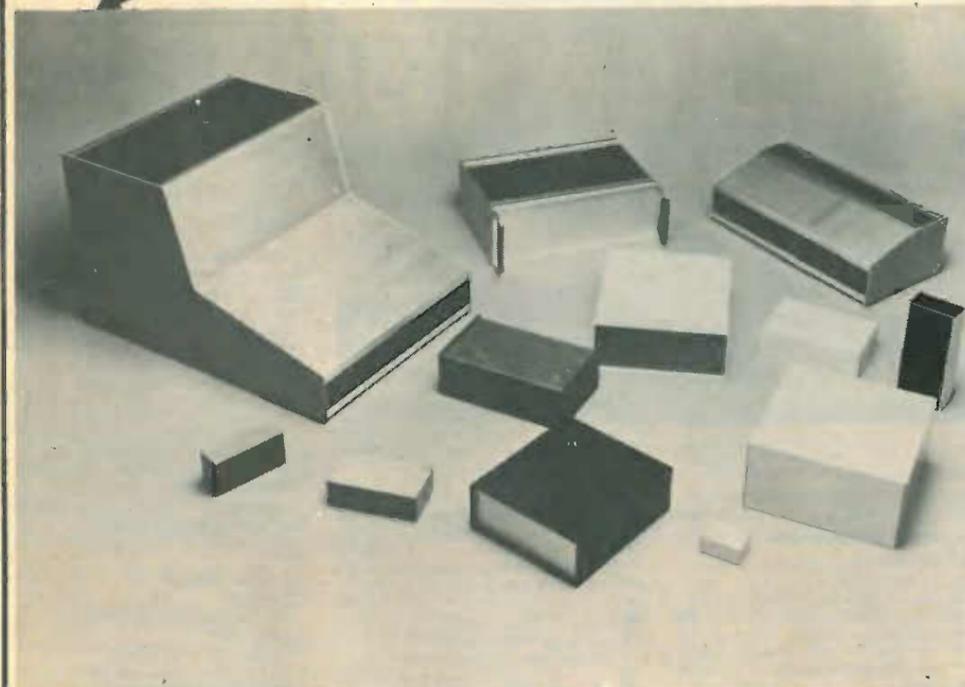

**Zaerix
Electronics
Limited**

46 Westbourne Grove
London, W2 5SF

**PROFESSIONAL
QUALITY**

Desk consoles, instrument cases and boxes which feature anodised aluminium extrusions and panels, with integral facilities to mount sub chassis and PCBs.

Telex: 261306
Tel. 01-221 3642

WW—031 FOR FURTHER DETAILS

MARTIN ASSOCIATES for the reliable Hire Service

LOGIC ANALYSER
Tektronix 308 Logic Analyser.

BRIDGES
Wayne Kerr B.224 Universal Bridge. Resistance Range 1μΩ - 100GΩ.
Wayne Kerr B.601 Bridge Freq. Range 15KHz-5MHz.

COUNTERS
Hewlett-Packard 5340A Counter 8 Digit 10Hz-18GHz.
Fluke 1910A Counter 7 Digit 5Hz-125MHz.

DIGITAL VOLTMETERS
Fluke 8010A 3.5 Digits. DCV, ACV, Ohms.
Solartron 7040 4½ Digit. DCV, ACV, DCI, ACI, Ohms.

SOUND LEVEL METER
Bruel & Kjaer 2209 Sound Level Meter.

METERS
Hewlett-Packard 3400A True RMS Voltmeter 10Hz-10MHz.


OSCILLOSCOPES
Telequipment D.83 DC-50MHz.
Tektronix D.34 DC-15MHz.
Tektronix 465B DC. 100MHz.
Tektronix T.935A DC-35MHz.

RECORDERS
Data Labs Transient Recorder DL905
J.J. Lloyd X-Y Plotters.
J.J. Lloyd CR.600 2 Pen Recorder.

OTHER EQUIPMENT AVAILABLE



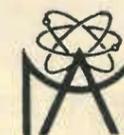Send for further details, catalogue available now.




Martin Associates (Electronics) Ltd.

34 Crown Street
Reading Berks RG1 2SE
Tel: Reading (0734) 595853/51074

Telephone Reading (0734) 595853/51074

WW — 071 FOR FURTHER DETAILS

Carston Electronics

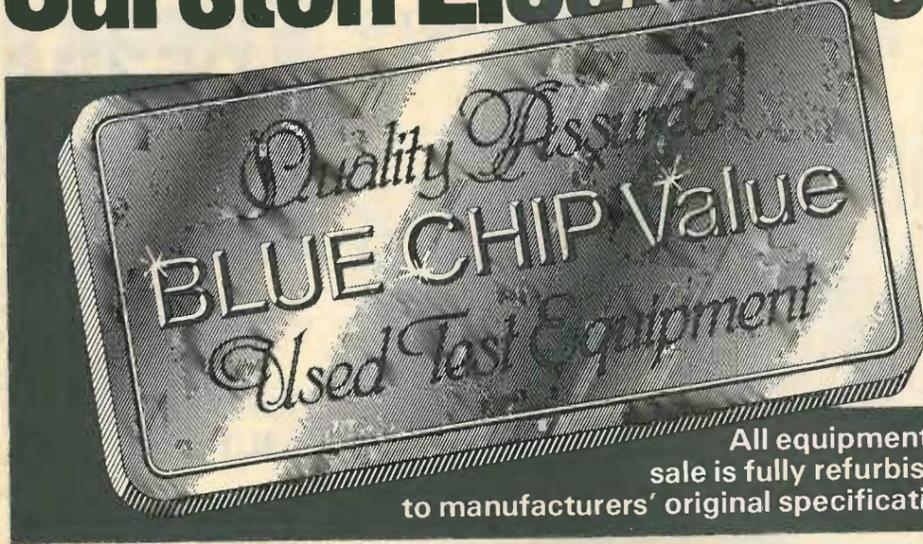

| Prices from £ | Prices from £ | Prices from £ |
|--|---------------|---------------|
| Bridges | | |
| GENRAD GR1657 Digibridge LCR, auto. LED display | 850 | |
| CINTEL 277 Measures iron core inductances 0.01H-1000H (with a Q value not less than 2) | 130 | |
| HEWLETT PACKARD 4342A 'Q' Meter QLC complete | 1250 | |
| MARCONI TF868A Universal Bridge | 250 | |
| TF1313A Universal LCR Bridge 0.1% | 375 | |
| WAYNE KERR B224 Wide range LCR Bridge | 475 | |
| B500 Log LCR Bridge | 225 | |
| B601 RF LCR Bridge (Detector and Oscillator not incl.) | 125 | |
| B641. Measures L/C/R/G Accuracy of 0.1% | 460 | |
| Q801. Y parameter test set. Plus transistor adaptor unit | 230 | |
| Cable Test Equipment | | |
| MARCONI TF2333 Transmission Test set | 575 | |
| HEWLETT PACKARD 3556A For psophometric measurements from 20 Hz-20kHz. 0.1mV-30V input level | 475 | |
| NEC TTS-37B. Noise, level and VU measurement. Sensitivity -80dBm up to +20dBm | 275 | |
| STC 74216A Noise Generator CCITT 74261A Psophometer CCITT | 240 | |
| TEKTRONIX 1502 Portable TDR Cable Tester | 2,725 | |
| WANDEL u. GOLTERMANN DLM-1. Send/receive system LDS-2. 200Hz-600kHz sender for measuring group delay and attenuation variations LDEF-2. Filters for DLM unit | 1500 | |
| Counter Timers | | |
| HEWLETT PACKARD 5300A/5303B DC-520 MHz 6 digits 5300A Display Module. 6 Digits. 3 x 10 ⁷ | 210 | |
| 5302A DC-50 MHz. 100mV sens. Time interval. Period. Ratio. Totalise. | 75 | |
| 5303B DC-520 MHz. 1Plug-on) 125mV sens. 50 Ω | 120 | |
| 5308A 0-75 MHz. Universal Module. 50mV sens. 1M Ω | 100 | |
| 5267A Time Interval Plug-in 10ns | 120 | |
| 5345 DC-500 MHz Time Int. Ave. Burst Total Ratio | 1225 | |
| 10590A Adaptor converts 5245 Plug-ins to 5345 | 225 | |
| RACAL 9024 10 Hz-600 MHz 7 + 1 digits 9835 6 Digit DC-20 MHz 10mV 9837 DC-80 MHz 6 digits | 250 | |
| 100 | | |
| 130 | | |
| SYSTRON DONNER 6053 9 Digit 20 Hz-3 GHz BCD O/P | 850 | |

| | |
|---|------|
| 6054A/04 11 Digit 20 kHz-18 GHz BCD O/P | 2800 |
| Function Generators | |
| INTER-STATE ELECTRONICS F51A Multi-Mode. + and - offset: 0.0005 Hz to 10 MHz. 10/15V/50 Ω F55A Multi-Mode. 0.0025 Hz-10 MHz. 10V/50 Ω . Ext. VGC. Burst O/P up to 100k bursts/sec | 250 |
| 350 | |
| PHILIPS PM5127. 0.1 Hz-1 MHz. Sine/Square/Triangular/Pulse outputs. External sweep facility 30Vp. p max output | 325 |
| Logic Analysers | |
| HEWLETT PACKARD 1601L Logic state analyser 12 channel display 1600A 16 channel 20 MHz clock MAP A & B store 1607 16 channel 20 MHz clock (Display scope required) | 250 |
| 1850 | |
| TEKTRONIX 7D01F 16 channel up to 50 MHz clock MAP | 2650 |
| Mains Monitors | |
| COLE T1007 200-260V. 35-65 Hz Thresholds 10V, 50V, 100V, 200V | 75 |
| DATALAB DL019 Power line interface for transient recording DL905 Digital Storage Unit DC-3 MHz 10mV | 350 |
| 1055 | |
| DRANETZ 606-3 Disturbance Analyser Avg. Sag/Surge | 2625 |
| GAY LDM Records +ve/-ve transients of 50ns on AC or DC Lines | 1250 |
| Modulation Meters | |
| AIRMEC 409 3-1500 MHz. AM/FM | 295 |
| MARCONI TF2300A 1-1000 MHz. AM/FM | 450 |

| | |
|--|------|
| Oscilloscopes | |
| ADVANCE OS1000A DC-20 MHz. dual trace 3300B Dual Trace DC-50 MHz 5mV/div. Dual Timebase | 600 |
| GOULD ADVANCE OS1000B DC-20 MHz Dual Trace X-Y TV Sync | 400 |
| HEWLETT PACKARD 1703A Storage 1000Div/ms. DC-35 MHz. Dual trace Mains/Ext DC | 1200 |
| 181A Storage 1000Div/ms DC-100 MHz Main frame only | 650 |
| 182C DC-100 MHz Mainframe, large screen | 525 |
| MEDELEC M-scope 4 channel DC-100 kHz U/V Chart | 1650 |
| PHILIPS PM3211 DC-15 MHz Dual Trace 2mV PM3233 Dual Beam DC-10 MHz 2mV/div. | 425 |
| 400 | |
| TEKTRONIX 475 Dual Trace DC-200 MHz 2mV 485 Dual Trace DC-350 MHz 50 Ω 1 M Ω 250 MHz | 1125 |
| 2100 | |
| 545B/1A1. DC-30 MHz. dual trace. Delayed timebase | 325 |
| 585A/82. DC-80 MHz. dual trace 10 mV sensitivity | 525 |
| 547/1A1. DC-50 MHz. dual trace DTB | 525 |
| 547/1A4. DC-50 MHz. four trace DTB | 625 |
| 7403N DC-60 MHz 3 Plug-in Mainframe | 450 |
| 7704A DC-200 MHz. CRT Readout. Mainframe for 4 Plug-in | 1200 |
| TELEQUIPMENT | |
| D34 Dual Trace DC-15 MHz 2mV Mains/Batt | 525 |
| D75 Dual Trace DC-50 MHz Dual Timebase | 600 |
| D83 DC-50 MHz. Dual trace. Large 6 1/2" CRT. Dual Time Base | 650 |
| Oscilloscope Plug-ins | |
| HEWLETT PACKARD 1804A DC-50 MHz Four channel 20 mV-10V/div. | 575 |

As New Ex Stock delivery

OSCILLOSCOPES

| | |
|---|-------|
| TEKTRONIX 465 DC-100 MHz Dual Trace 5mV-5V/Div 0.05 μ s-0.5s/Div Delayed T/B XY DC 4 MHz | £1250 |
| TEKTRONIX 475A DC-250 MHz Dual Trace 5mV-5V/Div 0.01 μ s-0.5s/Div Delayed T/B XY DC 3 MHz | £1950 |

These instruments sold with **ONE YEAR FULL GUARANTEE**

WIRELESS WORLD JANUARY 1981

| | |
|---|------|
| 1825A Dual Timebase 50ns-1s/div. 1805A Dual Trace DC-100 MHz 5mV. 1M Ω /50 Ω | 525 |
| 550 | |
| TEKTRONIX | |
| Type R. Transistor R.T. tester. Pulse rate 120 pulses/sec. R.T. Less than 5 nys | 100 |
| Type G. Differential amplifier. 100:1 CMR DC-20 MHz. 50 mV sensitivity Plug-ins for 500 series | 50 |
| 1A1 dual trace Plug-in DC-50 MHz | 225 |
| 1A2 dual trace Plug-in DC-50 MHz | 180 |
| 1A4 four trace Plug-in DC-50 MHz | 375 |
| 1A5 Differential Plug-in | 175 |
| Z Differential Plug-in | 140 |
| 81 Adaptor Plug-in 1A Series to 580 Series | 75 |
| 7A12 Dual Trace DC-105 MHz 5mV/div. | 410 |
| 7A22 High gain diff. amp. 0.1 Hz-1 MHz 10 μ V | 450 |
| 7A26 Dual Trace DC-150 MHz 5mV-5V/div. | 525 |
| 7B53A Dual Timebase 5ns-5s/div. | 550 |
| Oscilloscopes (storage) | |
| TEKTRONIX 549/1A1. DC-30 MHz. 5mV sensitivity. Dual trace. Storage scope. Writing speed: 5cm/ μ s with enhancement. Includes trolley 564B/3A6/2B67. DC-10 MHz. Dual trace 10mV sensitivity, split screen storage oscilloscope | 675 |
| 466 Storage 1350 cm/ μ s Variable Persist DC-100 MHz | 2225 |
| 7313 Split screen 4.9 cm/ μ s. DC-25 MHz (M/F for 3 Plug-ins) | 1650 |
| Phase Meter | |
| DRANETZ 301A 5 Hz-500 kHz. Z in 100k Ω . Accuracy \pm 1° to \pm 2°. Analogue O/P | 400 |
| Power Meters | |
| DYMAR 2081/100 True RMS. DC-500 MHz. 30mW-100W | 425 |
| HEWLETT PACKARD 478A Thermistor Mount for 432A 435A 0.3 μ W to 100mW 5 MHz-18GHz | 90 |
| 8481A Power Sensor for 435A | 475 |
| 200 | |
| MARCONI SANDERS 6460 10 MHz-40 GHz (Depending on Head) | 300 |
| 6420 10 MHz-12.4 GHz 10mW | 110 |
| MARCONI TF2512 DC-500 MHz 0.5-30w 50 Ω TF 893A 10 Hz-20 kHz. 20 μ W-10W. | 130 |
| 120 | |
| Power Supplies | |
| BRANDENBURG 475R 10-2100V 5mA DC Stab. | 150 |
| FARNELL L30B 0-30V 1A DC Stab. | 55 |
| FLUKE 415B 0.3-3100V 30mA 0.005% reg. Protected | 350 |
| ITT Power Lab. up to 30V Dual Supply | 90 |
| MARCONI TF2154/1 0-30V 1A. 0.2-15V 2A 0.7-5V 4A | 60 |
| SMITHS 4701 5-7V o/p Power Pack | 32 |
| SORENSEN DCR 300-2.5 0-300V 2.5A DC Stab. | 375 |
| Pulse Generators | |
| DB ELECTRONICS 150. I.C. pulse generator | 50 |
| EH RESEARCH 122. 1 kHz-200 MHz 5V/50 Ω RT 12ns | 220 |
| 1391L. 10Hz-50 MHz 10V/50 Ω RT 5ns | 175 |
| 1221. Timing Unit 6 Channel 0-10 MHz 5V/50 Ω RT 8ns | 50 |
| HEWLETT PACKARD 214A 100V/50 Ω . Double pulse O/P. W50ns-10ms. 10 Hz-1 MHz. 15ns RT | 360 |
| MARCONI TF2025 0.2 Hz-25 MHz \pm 10V/50V RT 7ns | 350 |
| Recorders and Signal Conditioning Equipment | |
| AMPEX PR2200 Instrumentation Recorder up to 16 channels. FM/DR. Record replay all speeds. 1" tape FM/DR I.R.I.G. DC-40 kHz FM. 100 Hz-300 kHz DR | 6500 |
| BRUNO WOELKE ME102B. Wow and flutter meter | 75 |
| ME102C. Wow and flutter meter | 90 |

Bigger stock investment greater equipment range means wider choice

| | |
|--|------|
| BRYANS SOUTHERN | |
| BS314 4 channel 1mV-10V 16 speeds | 1650 |
| BS316 6 channel 1mV-10V 16 speeds | 2350 |
| HEWLETT PACKARD | |
| 680M. 5 inch. Stripchart Single Pen 5mV-120V I/P 20cm/min 2.5 cm/hr | 275 |
| 7046A Two pen A3 0.25mV-5V/cm | 995 |
| KUDELSKI | |
| Nagra 4.2 LSP Professional Audio Recorder (Batt optd) | 1215 |
| PHILIPS | |
| PM 8251 Single pen 10in chart 10mV-5V | 450 |
| RACAL | |
| Store 4. Uses D/4 inch magnetic tape. Will record 4 F.M. channels. Operates at 7 different speeds. | 1675 |
| S E LABORATORIES | |
| 6150/6151 12 channel UV 1250 mm/s-25 mm/min 6 in chart 994 6 Channel Pre-Amp \pm 1% \pm V o/p | 1400 |
| 6008 25 Channel μ V 8 in 4m/sec to 25mm/min | 450 |
| 895 | |
| SMITHS INDUSTRIES | |
| RE541.20 Single Pen. 0.5mV-100V FSD. 3-60cm/min and hour | 350 |
| YOKOGAWA | |
| 3046. 10 inch Chart Single Pen. 0.5 mV-100 V I/P 2.60cm/min and/hr 3047. 2 Pen Version of 3046 | 360 |
| 425 | |
| Signal Sources and Generators | |
| BOONTON 102B 4-3.520 MHz Int/Ext FM/AM 0.1 μ V-1V 50 Ω | 1725 |

| | |
|---|------|
| DYMAR | |
| 1525 100 kHz-184 MHz Int/Ext AM/FM Batt/Mains | 525 |
| GENERAL RADIO | |
| 1362 UHF. 220-920 MHz | 450 |
| GOULD ADVANCE | |
| SG70 5 Hz-125 kHz 600 Ω 4w | 85 |
| HEWLETT PACKARD | |
| 204D 5 Hz-1.2 MHz. 600 Ω . 80dB att. O/P 5V RMS | 150 |
| 620B 7-11 GHz 50 Ω FM/PM 1mw 8614A 800 MHz-2.4 GHz + 10dBm to -127 dBm 50 Ω AM/FM 8616A 1.8-4.5 GHz Ext AM/FM/50V 10 mw | 1100 |
| MARCONI | |
| TF144 H/4S HF Generator 10 kHz-72 MHz AM | 550 |
| TF791. FM Deviation Meter 4-1024 MHz | 95 |
| TF801/D1. 10-470 MHz AM. FM. TF995A/2. 1.5-220 MHz AM. FM. TF2171 Digital Synchroniser for TF2015 | 255 |
| 350 | |
| TF2002/AS 10 kHz-72 MHz FM/AM 0.1-1V o/p | 625 |
| TF2012 UHF. FM 400-520 MHz. 0.03 μ V. Counter o/p | 650 |
| TF2012 UHF. 400-520 MHz. FM | 550 |
| RACAL | |
| 9081 5-520 MHz LED Display O/P - 130dBm AM/FM | 1875 |
| SCHAFFNER | |
| NSG330 Ignition Interference Attachment | 150 |
| NSG200B Mains Interference Simulator (Mainframe) | 250 |
| STC | |
| 74216 Noise Generator 20 Hz-4 kHz Flat/CCITT Wtg | 315 |

| | |
|---|------|
| Spectrum Analysers | |
| HEWLETT PACKARD | |
| 8443A Tracking Gene/counter 100 kHz-110 MHz | 850 |
| 8445A Automatic pre-selector 10 MHz-18 GHz | 1300 |
| 8555A RF Plug-in 10 MHz-18 GHz 1 kHz Res | 3000 |
| 851B/851B Display & RF Section | 1350 |
| NELSON ROSS | |
| 011. DC-20 kHz. 80dB dynamic range. Dispersion: 100 Hz-6 kHz | 350 |
| 022. DC-100 kHz. Dynamic range 60dB fits into various 500 series CRO's | 350 |
| TEKTRONIX | |
| 3L5. Plug-in unit fits into various 500B series CRO's. 50 Hz-1 MHz. Greater than 60dB dynamic range | 475 |
| Sweep Generators | |
| HEWLETT PACKARD | |
| 8690B Mainframe. Int/Ext AM. Ext FM | 600 |
| 8693B/100 3.7-8.3 GHz 5mW. PIN levelled 'N' connectors | 600 |
| 8699B/100 0.1-4 GHz 6mW. (20mW to 2 GHz). PIN levelled. 'N' connectors | 1200 |
| TEXSCAN | |
| 9900 Sweep Generator 10-30 MHz CRT Display | 525 |
| VS60 Sweep Generator 5-100 MHz Rate 60 Hz | 950 |
| TV Markers set of 5: 31.5, 32.5, 35, 39.5 & 41.5 MHz | 195 |
| LN40A Log Amplifier | 105 |


| | |
|--|-----|
| Temperature Measuring Equipment (NB Thermocouples not incl.) | |
| COMARK | |
| 1601BLS 87°C to 1000°C Type K Thermocouples | 75 |
| 1604BLS -80°C to +170°C Type K Thermocouples | 82 |
| 1625BLS -100°C to +300°C Type T Thermocouples | 90 |
| 1642BLS -120°C to +800°C Type J Thermocouples | 75 |
| Voltmeters-Analogue | |
| AVO | |
| 8 Mk IV AC/DC V.AC/DC Amps. Ω | 70 |
| BOONTON | |
| 92AD/01/09 10 kHz-1.2 GHz 1999 FSD 10 μ V Res | 525 |
| 92C 10 kHz-1.2 GHz 500 μ V-3V. 1% of FS | 350 |
| HEWLETT PACKARD | |
| 400E Millivoltmeter 10 Hz-10 MHz B/W 1mV FSS | 99 |
| 427A. AC/DC Ω multimeter 3406A. 10 kHz-1.2 GHz | 275 |
| 3400A 10 Hz-10 MHz 1mV-300V True RMS | 345 |
| 350 | |
| KEITHLEY | |
| 610C Electrometer DC 1mV-100V. Amps 10 ⁻¹⁴ Recorder o/p | 350 |
| LEVELL | |
| TM3B 5 μ V-500VAC 1 Hz-3 MHz + 50 to 100 dB | 80 |
| MARCONI | |
| TF2603. AC voltmeter to 1.5 GHz | 300 |
| PHILIPS | |
| PM2454B 1mV-300V. 10 Hz 12 MHz Z in 19M Ω . DC O/P | 300 |
| RACAL | |
| 9301 RMS Millivoltmeter 10 kHz-1.5 GHz with carry case | 475 |
| Voltmeters-Digital | |
| ADVANCE | |
| DMM 7A/01 1999 FSD AC/DC/ Ω /Current | 115 |
| FLUKE | |
| 8000A 1999 FSD AC/DC/OHMS/Current | 115 |
| HEWLETT PACKARD | |
| 34740A/34702A 9999 FSD AC/DC/OHMS | 180 |
| SOLARTRON | |
| LM1420.2. 2300 FSD DC only 0.05% True RMS/DC | 75 |
| LM1420.2BA. 2300 FSD AC | 110 |
| A200. 19999 FSD DC only | 160 |
| A203. 19999 FSD AC/DC/ Ω Sensitivity: (1 μ V DC, 10 μ V AC, 100m Ω resistance) | 300 |
| A205. 19999 FSD AC/DC/ Ω | 300 |
| A243. 119999 FSD AC/DC/ Ω Sensitivity: (1 μ V DC, 10 μ V AC, 10m Ω resistance) | 325 |
| 7050 99999 Auto AC/DC/ Ω | 350 |
| Voltmeters Vector/Phase | |
| DRANETZ | |
| 305B 9999 FSD Mainframe for PA 3001 module | 575 |
| HEWLETT PACKARD | |
| 3490A 100000 FSD 1 μ V-1000V DC 0.01% | 625 |
| 10 μ V-1000V AC θ | |

ALL PRICES LISTED ARE EXCLUSIVE OF VAT (Standard Rate).

Prime Equipment

| | |
|--|-------|
| HEWLETT PACKARD | |
| 8640B Precision AM-FM Signal Generator | £3550 |
| 141T Spectrum Analyzer - Mainframe | £1300 |
| 8552B Spectrum Analyzer - IF Section | £1650 |
| 8553B Spectrum Analyzer - RF Section | £4400 |
| 8555A Spectrum Analyzer - RF Section | £1650 |
| 8556A Spectrum Analyzer - LF Section | £2500 |
| 8558B Spectrum Analyzer (for 180 Mainframe) | £2150 |
| 1600A 16 Channel Display Logic Analyzer | |
| PHILIPS | |
| PM 3212 Dual Trace 25 MHz 2mV/Div Oscilloscope | £525 |
| PM 3214 Dual Timebase Dual Trace DC-25 MHz Osc. oscopce | £625 |
| RACAL | |
| 9081 5-520 MHz Generator 130 dBm AM/FM | £1975 |
| TEKTRONIX | |
| 485 Dual Trace 350 MHz Oscilloscope | £2995 |
| 7912 Dual Trace Storage Oscilloscope DC-10 MHz 250 cm/ms writing speed | £699 |
| 7313 Storage Oscilloscope Mainframe 4.9 cm/ μ s writing speed DC-25 MHz | £1900 |
| 7A22 Differential Plug-in. As new DC-1 MHz 10 μ V-10V/Div (12 month guarantee) | £670 |
| 7A26 Dual Trace Plug-in. DC-150 MHz 5mV-5V/Div. | £780 |
| 7B53A Dual Timebase 5ns-5s/Div CRT Readout | £650 |

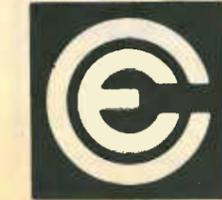Carston Prime Equipment brings you recent "State-of-the-Art" instruments at competitive prices, with fast delivery (2-4 weeks). Every "Prime" instrument carries the Carston 90 Day Full Guarantee covering parts and labour.



Carston Electronics


Contact Brian Hollingsworth or Noel Jennings
CARSTON ELECTRONICS LTD
 SHIRLEY HOUSE, 27 CAMDEN RD.,
 LONDON NW1 9NR Telex 23920

01-267 5311/2

PLEASE NOTE:
 LISTED HERE IS ONLY A SELECTION OF OUR WIDE STOCK OF EQUIPMENT - FOR SPECIALIST NEEDS OR FOR DETAILS OF OUR FULL STANDARD RANGE OF EQUIPMENTS - **RING US TODAY!**

Redundant Test Equipment
 Why not turn your under-utilized test equipment into cash? Ring us and we'll make you an offer.

METER PROBLEMS?

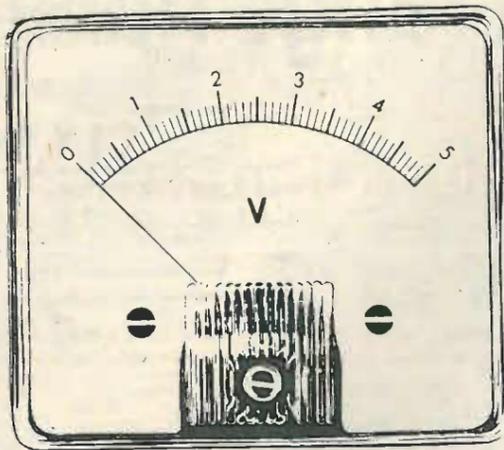

STRAIN GAUGE TRANSDUCER INSTRUMENTATION

The 2100 Series Conditioner/Amplifier is just one of a wide range of instruments we offer. For all your strain measurement requirements contact us first.

- We also offer the widest range of strain gauges and accessories.
- INPUTS: 1/2 and Full Bridge
- GAIN: 100 to 2100
- BRIDGE EXCITATION: 1 V to 12 V dc
- INTERNAL CALIBRATION: 2 step
- EACH CHANNEL FULLY INDEPENDENT

Full Information from: **HARRIS ELECTRONICS (London)**
138 GRAY'S INN ROAD, W.C.1
Phone: 01-837/7937
Telex: 892301


WW - 056 FOR FURTHER DETAILS

DISPLAY ELECTRONICS

Would like to wish all their customers and business associates a Very Merry Christmas and Prosperous New Year



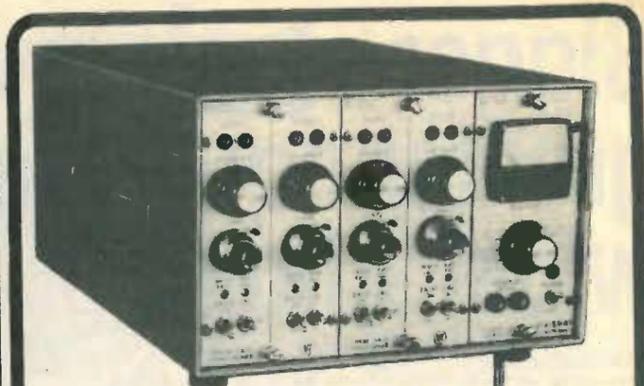Dept. W.W., 64-66 Melfort Rd., Thornton Heath, Surrey. Telephone: 01-689 7702



STRAIN GAUGE TRANSDUCER INSTRUMENTATION

The 2100 Series Conditioner/Amplifier is just one of a wide range of instruments we offer. For all your strain measurement requirements contact us first.

- We also offer the widest range of strain gauges and accessories.
- INPUTS: 1/2 and Full Bridge
- GAIN: 100 to 2100
- BRIDGE EXCITATION: 1 V to 12 V dc
- INTERNAL CALIBRATION: 2 step
- EACH CHANNEL FULLY INDEPENDENT

W.S.M. ARMSTRONG ROAD BASINGSTOKE RG24 0QA ENGLAND
Telephone: Basingstoke (0256) 62131

WW - 020 FOR FURTHER DETAILS

VERY SPECIAL OFFER OF FULLY GUARANTEED BRAND NEW SINGLE SIDE EUROPEAN MINIDISK DRIVES

EXCLUSIVELY TO WIRELESS WORLD READERS

Now really is the time to buy. New 5 1/4" drives will probably never again be so cheap. Ring the enquiry number for further details. This offer is exclusive to WW Readers and represents a saving of about £75 each on the normal RRP.

SPECIAL C.W.O. PRICE: £120 + £2 CARRIAGE + 15% VAT

Total CWO Price: **£140.30 per Drive**

Cheques and postal orders made payable to:

WW DISK OFFER
49 Milford Hill, Batford Harpenden, Herts.
Tel: 0582 429122

WW - 050 FOR FURTHER DETAILS

PRIME COMPONENTS LOW PRICES

All our microchips are at micro prices. Don't be fooled by low prices. We do not offer for sale surplus, sub-spec or rebranded devices. All our parts are guaranteed new, first quality, factory prime, full spec devices. It is also our policy to offer you the best of new devices that become available and these are featured regularly. Prices are exclusive of p&p and VAT - please refer to "Ordering Information" before ordering. Official orders from schools, colleges, universities and Gov. authorities accepted.


| | | | |
|-------|------|----------------------|-------|
| 7400 | 88p | 2114 300NS | 250p |
| 7401 | 11p | 2114 450NS | 225p |
| 7402 | 12p | 4116 200NS | 250p |
| 7403 | 13p | 4116 150NS | 375p |
| 7404 | 17p | 4116 200NS Caramic | 225p |
| 7409 | 15p | 6514 (TC 5514P) 1kx4 | 550p |
| 7410 | 18p | CMOS RAM 450NS | 550p |
| 7412 | 18p | 6502 | 895p |
| 7413 | 28p | 6504 | 750p |
| 7420 | 16p | 6505 | 750p |
| 7430 | 18p | 6800 | 645p |
| 7432 | 25p | 6802 | 825p |
| 7440 | 16p | 6809 | 2450p |
| 7442 | 68p | 8080A | 425p |
| 7448 | 75p | 8080SA | 1095p |
| 7473 | 32p | 8080 | 700p |
| 7474 | 32p | 8080A | 900p |
| 7476 | 40p | 8080SA | 1250p |
| 7490 | 35p | 8080 | 850p |
| 7492 | 50p | 8080SA | 950p |
| 7493 | 50p | 8080 | 850p |
| 7496 | 45p | 8080SA | 950p |
| 74121 | 35p | 8080 | 850p |
| 74123 | 45p | 8080SA | 950p |
| 74154 | 90p | 8080 | 850p |
| 74157 | 55p | 8080SA | 950p |
| 74122 | 45p | 8080 | 850p |
| 74125 | 50p | 8080SA | 950p |
| 74195 | 100p | 8080 | 850p |
| 74196 | 100p | 8080SA | 950p |
| 74203 | 140p | 8080 | 850p |
| 74290 | 120p | 8080SA | 950p |
| 74365 | 90p | 8080 | 850p |
| 74366 | 90p | 8080SA | 950p |

| | | | |
|---------|------|---------|------|
| 74LS | 40p | 74LS01 | 12p |
| 74LS02 | 13p | 74LS02 | 13p |
| 74LS03 | 13p | 74LS03 | 13p |
| 74LS04 | 13p | 74LS04 | 13p |
| 74LS08 | 20p | 74LS08 | 20p |
| 74LS10 | 19p | 74LS10 | 19p |
| 74LS11 | 20p | 74LS11 | 20p |
| 74LS12 | 30p | 74LS12 | 30p |
| 74LS13 | 35p | 74LS13 | 35p |
| 74LS14 | 60p | 74LS14 | 60p |
| 74LS15 | 38p | 74LS15 | 38p |
| 74LS20 | 18p | 74LS20 | 18p |
| 74LS21 | 30p | 74LS21 | 30p |
| 74LS22 | 38p | 74LS22 | 38p |
| 74LS26 | 45p | 74LS26 | 45p |
| 74LS27 | 45p | 74LS27 | 45p |
| 74LS30 | 18p | 74LS30 | 18p |
| 74LS32 | 23p | 74LS32 | 23p |
| 74LS37 | 35p | 74LS37 | 35p |
| 74LS38 | 35p | 74LS38 | 35p |
| 74LS40 | 25p | 74LS40 | 25p |
| 74LS42 | 60p | 74LS42 | 60p |
| 74LS47 | 75p | 74LS47 | 75p |
| 74LS48 | 85p | 74LS48 | 85p |
| 74LS49 | 90p | 74LS49 | 90p |
| 74LS73 | 30p | 74LS73 | 30p |
| 74LS74 | 30p | 74LS74 | 30p |
| 74LS75 | 42p | 74LS75 | 42p |
| 74LS85 | 98p | 74LS85 | 98p |
| 74LS90 | 35p | 74LS90 | 35p |
| 74LS93 | 70p | 74LS93 | 70p |
| 74LS96 | 160p | 74LS96 | 160p |
| 74LS107 | 40p | 74LS107 | 40p |
| 74LS112 | 75p | 74LS112 | 75p |
| 74LS123 | 63p | 74LS123 | 63p |
| 74LS125 | 60p | 74LS125 | 60p |
| 74LS126 | 60p | 74LS126 | 60p |
| 74LS132 | 78p | 74LS132 | 78p |
| 74LS138 | 68p | 74LS138 | 68p |
| 74LS148 | 75p | 74LS148 | 75p |
| 74LS151 | 75p | 74LS151 | 75p |
| 74LS153 | 75p | 74LS153 | 75p |
| 74LS155 | 95p | 74LS155 | 95p |
| 74LS157 | 74p | 74LS157 | 74p |
| 74LS160 | 115p | 74LS160 | 115p |
| 74LS161 | 78p | 74LS161 | 78p |
| 74LS163 | 90p | 74LS163 | 90p |
| 74LS164 | 90p | 74LS164 | 90p |
| 74LS165 | 100p | 74LS165 | 100p |
| 74LS168 | 180p | 74LS168 | 180p |
| 74LS173 | 100p | 74LS173 | 100p |
| 74LS174 | 95p | 74LS174 | 95p |
| 74LS175 | 95p | 74LS175 | 95p |
| 74LS181 | 280p | 74LS181 | 280p |
| 74LS190 | 110p | 74LS190 | 110p |
| 74LS195 | 87p | 74LS195 | 87p |
| 74LS196 | 100p | 74LS196 | 100p |
| 74LS221 | 110p | 74LS221 | 110p |
| 74LS240 | 210p | 74LS240 | 210p |
| 74LS241 | 200p | 74LS241 | 200p |
| 74LS242 | 220p | 74LS242 | 220p |
| 74LS244 | 175p | 74LS244 | 175p |
| 74LS245 | 220p | 74LS245 | 220p |
| 74LS251 | 120p | 74LS251 | 120p |
| 74LS253 | 120p | 74LS253 | 120p |
| 74LS257 | 110p | 74LS257 | 110p |
| 74LS260 | 90p | 74LS260 | 90p |
| 74LS273 | 78p | 74LS273 | 78p |
| 74LS290 | 95p | 74LS290 | 95p |
| 74LS293 | 120p | 74LS293 | 120p |
| 74LS366 | 87p | 74LS366 | 87p |
| 74LS373 | 170p | 74LS373 | 170p |
| 74LS374 | 170p | 74LS374 | 170p |
| 74LS375 | 140p | 74LS375 | 140p |
| 74LS393 | 138p | 74LS393 | 138p |
| 74LS490 | 140p | 74LS490 | 140p |
| 74LS870 | 260p | 74LS870 | 260p |

| | | | |
|---------|------|---------|------|
| 74LS | 40p | 74LS01 | 12p |
| 74LS02 | 13p | 74LS02 | 13p |
| 74LS03 | 13p | 74LS03 | 13p |
| 74LS04 | 13p | 74LS04 | 13p |
| 74LS08 | 20p | 74LS08 | 20p |
| 74LS10 | 19p | 74LS10 | 19p |
| 74LS11 | 20p | 74LS11 | 20p |
| 74LS12 | 30p | 74LS12 | 30p |
| 74LS13 | 35p | 74LS13 | 35p |
| 74LS14 | 60p | 74LS14 | 60p |
| 74LS15 | 38p | 74LS15 | 38p |
| 74LS20 | 18p | 74LS20 | 18p |
| 74LS21 | 30p | 74LS21 | 30p |
| 74LS22 | 38p | 74LS22 | 38p |
| 74LS26 | 45p | 74LS26 | 45p |
| 74LS27 | 45p | 74LS27 | 45p |
| 74LS30 | 18p | 74LS30 | 18p |
| 74LS32 | 23p | 74LS32 | 23p |
| 74LS37 | 35p | 74LS37 | 35p |
| 74LS38 | 35p | 74LS38 | 35p |
| 74LS40 | 25p | 74LS40 | 25p |
| 74LS42 | 60p | 74LS42 | 60p |
| 74LS47 | 75p | 74LS47 | 75p |
| 74LS48 | 85p | 74LS48 | 85p |
| 74LS49 | 90p | 74LS49 | 90p |
| 74LS73 | 30p | 74LS73 | 30p |
| 74LS74 | 30p | 74LS74 | 30p |
| 74LS75 | 42p | 74LS75 | 42p |
| 74LS85 | 98p | 74LS85 | 98p |
| 74LS90 | 35p | 74LS90 | 35p |
| 74LS93 | 70p | 74LS93 | 70p |
| 74LS96 | 160p | 74LS96 | 160p |
| 74LS107 | 40p | 74LS107 | 40p |
| 74LS112 | 75p | 74LS112 | 75p |
| 74LS123 | 63p | 74LS123 | 63p |
| 74LS125 | 60p | 74LS125 | 60p |
| 74LS126 | 60p | 74LS126 | 60p |
| 74LS132 | 78p | 74LS132 | 78p |
| 74LS138 | 68p | 74LS138 | 68p |
| 74LS148 | 75p | 74LS148 | 75p |
| 74LS151 | 75p | 74LS151 | 75p |
| 74LS153 | 75p | 74LS153 | 75p |
| 74LS155 | 95p | 74LS155 | 95p |
| 74LS157 | 74p | 74LS157 | 74p |
| 74LS160 | 115p | 74LS160 | 115p |
| 74LS161 | 78p | 74LS161 | 78p |
| 74LS163 | 90p | 74LS163 | 90p |
| 74LS164 | 90p | 74LS164 | 90p |
| 74LS165 | 100p | 74LS165 | 100p |
| 74LS168 | 180p | 74LS168 | 180p |
| 74LS173 | 100p | 74LS173 | 100p |
| 74LS174 | 95p | 74LS174 | 95p |
| 74LS175 | 95p | 74LS175 | 95p |
| 74LS181 | 280p | 74LS181 | 280p |
| 74LS190 | 110p | 74LS190 | 110p |
| 74LS195 | 87p | 74LS195 | 87p |
| 74LS196 | 100p | 74LS196 | 100p |
| 74LS221 | 110p | 74LS221 | 110p |
| 74LS240 | 210p | 74LS240 | 210p |
| 74LS241 | 200p | 74LS241 | 200p |
| 74LS242 | 220p | 74LS242 | 220p |
| 74LS244 | 175p | 74LS244 | 175p |
| 74LS245 | 220p | 74LS245 | 220p |
| 74LS251 | 120p | 74LS251 | 120p |
| 74LS253 | 120p | 74LS253 | 120p |
| 74LS257 | 110p | 74LS257 | 110p |
| 74LS260 | 90p | 74LS260 | 90p |
| 74LS273 | 78p | 74LS273 | 78p |
| 74LS290 | 95p | 74LS290 | 95p |
| 74LS293 | 120p | 74LS293 | 120p |
| 74LS366 | 87p | 74LS366 | 87p |
| 74LS373 | 170p | 74LS373 | 170p |
| 74LS374 | 170p | 74LS374 | 170p |
| 74LS375 | 140p | 74LS375 | 140p |
| 74LS393 | 138p | 74LS393 | 138p |
| 74LS490 | 140p | 74LS490 | 140p |
| 74LS870 | 260p | 74LS870 | 260p |

| | | | |
|---------|------|---------|------|
| 74LS | 40p | 74LS01 | 12p |
| 74LS02 | 13p | 74LS02 | 13p |
| 74LS03 | 13p | 74LS03 | 13p |
| 74LS04 | 13p | 74LS04 | 13p |
| 74LS08 | 20p | 74LS08 | 20p |
| 74LS10 | 19p | 74LS10 | 19p |
| 74LS11 | 20p | 74LS11 | 20p |
| 74LS12 | 30p | 74LS12 | 30p |
| 74LS13 | 35p | 74LS13 | 35p |
| 74LS14 | 60p | 74LS14 | 60p |
| 74LS15 | 38p | 74LS15 | 38p |
| 74LS20 | 18p | 74LS20 | 18p |
| 74LS21 | 30p | 74LS21 | 30p |
| 74LS22 | 38p | 74LS22 | 38p |
| 74LS26 | 45p | 74LS26 | 45p |
| 74LS27 | 45p | 74LS27 | 45p |
| 74LS30 | 18p | 74LS30 | 18p |
| 74LS32 | 23p | 74LS32 | 23p |
| 74LS37 | 35p | 74LS37 | 35p |
| 74LS38 | 35p | 74LS38 | 35p |
| 74LS40 | 25p | 74LS40 | 25p |
| 74LS42 | 60p | 74LS42 | 60p |
| 74LS47 | 75p | 74LS47 | 75p |
| 74LS48 | 85p | 74LS48 | 85p |
| 74LS49 | 90p | 74LS49 | 90p |
| 74LS73 | 30p | 74LS73 | 30p |
| 74LS74 | 30p | 74LS74 | 30p |
| 74LS75 | 42p | 74LS75 | 42p |
| 74LS85 | 98p | 74LS85 | 98p |
| 74LS90 | 35p | 74LS90 | 35p |
| 74LS93 | 70p | 74LS93 | 70p |
| 74LS96 | 160p | 74LS96 | 160p |
| 74LS107 | 40p | 74LS107 | 40p |
| 74LS112 | 75p | 74LS112 | 75p |
| 74LS123 | 63p | 74LS123 | 63p |
| 74LS125 | 60p | 74LS125 | 60p |
| 74LS126 | 60p | 74LS126 | 60p |
| 74LS132 | 78p | 74LS132 | 78p |
| 74LS138 | 68p | 74LS138 | 68p |
| 74LS148 | 75p | 74LS148 | 75p |
| 74LS151 | 75p | 74LS151 | 75p |
| 74LS153 | 75p | 74LS153 | 75p |
| 74LS155 | 95p | 74LS155 | 95p |
| 74LS157 | 74p | 74LS157 | 74p |
| 74LS160 | 115p | 74LS160 | 115p |
| 74LS161 | 78p | 74LS161 | 78p |
| 74LS163 | 90p | 74LS163 | 90p |
| 74LS164 | 90p | 74LS164 | 90p |
| 74LS165 | 100p | 74LS165 | 100p |
| 74LS168 | 180p | 74LS168 | 180p |
| 74LS173 | 100p | 74LS173 | 100p |
| 74LS174 | 95p | 74LS174 | 95p |
| 74LS175 | 95p | 74LS175 | 95p |
| 74LS181 | 280p | 74LS181 | 280p |

METER PROBLEMS?

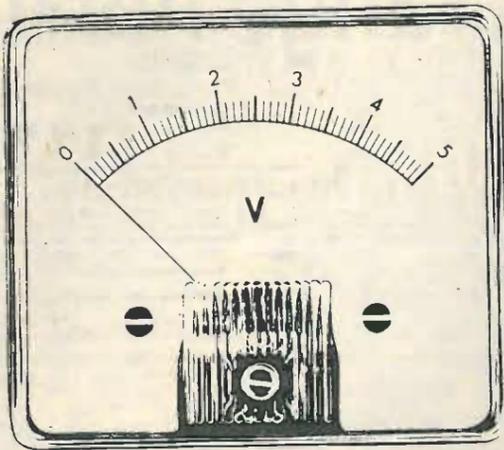

STRAIN GAUGE INSTRUMENTATION

The 2100 Series Conditioner/Amplifier is just one of a wide range of instruments we offer. For all your strain measurement requirements contact us first.

- We also offer the widest range of strain gauges and accessories.
- INPUTS: 1/2, 1 and Full Bridge
- BRIDGE EXCITATION: 1 V to 12 V dc
- GAIN: 100 to 2100
- INTERNAL CALIBRATION: 2 step
- EACH CHANNEL FULLY INDEPENDENT

Full information from: **HARRIS ELECTRONICS (London)**
138 GRAY'S INN ROAD, W.C.1 Phone: 01-837/7937
Telex: 892301


WW - 056 FOR FURTHER DETAILS

DISPLAY ELECTRONICS

Would like to wish all their customers and business associates a Very Merry Christmas and Prosperous New Year



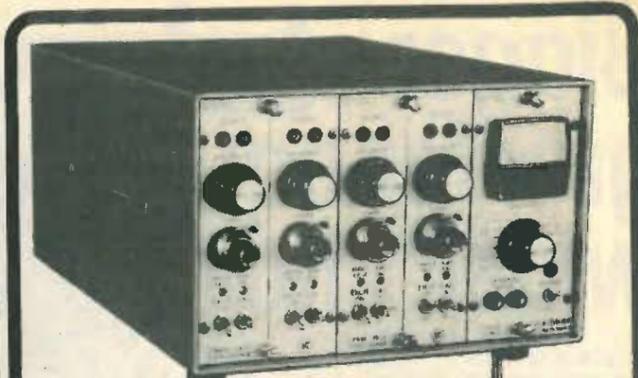Dept. W.W., 64-66 Melford Rd., Thornton Heath, Surrey. Telephone: 01-689 7702



STRAIN GAUGE INSTRUMENTATION

The 2100 Series Conditioner/Amplifier is just one of a wide range of instruments we offer. For all your strain measurement requirements contact us first.

- We also offer the widest range of strain gauges and accessories.
- INPUTS: 1/2, 1 and Full Bridge
- BRIDGE EXCITATION: 1 V to 12 V dc
- GAIN: 100 to 2100
- INTERNAL CALIBRATION: 2 step
- EACH CHANNEL FULLY INDEPENDENT

WSM ARMSTRONG ROAD BASINGSTOKE RG24 0QA ENGLAND
Telephone: Basingstoke (0256) 62 131

WW - 020 FOR FURTHER DETAILS

VERY SPECIAL OFFER OF FULLY GUARANTEED BRAND NEW SINGLE SIDE EUROPEAN MINIDISK DRIVES EXCLUSIVELY TO WIRELESS WORLD READERS

Now really is the time to buy. New 5 1/4" drives will probably never again be so cheap. Ring the enquiry number for further details. This offer is exclusive to WW Readers and represents a saving of about £75 each on the normal RRP.

SPECIAL C.W.O. PRICE: £120 + £2 CARRIAGE + 15% VAT

Total CWO Price: **£140.30 per Drive**
Cheques and postal orders made payable to: **WW DISK OFFER**
49 Milford Hill, Batford Harpenden, Herts.
Tel: 0582 429122

WW - 050 FOR FURTHER DETAILS

PRIME COMPONENTS LOW PRICES

All our microchips are at micro prices. Don't be fooled by low prices. We do not offer for sale surplus, sub-spec or rebranded devices. All our parts are guaranteed new, first quality, factory prime, full spec devices. It is also our policy to offer you the best of new devices that become available and these are featured regularly. Prices are exclusive of p&p and VAT - please refer to "Ordering Information" before ordering. Official orders from schools, colleges, universities and Gov. authorities accepted.

| | | | |
|-------|------|------|------|
| 7400 | 11p | 4023 | 88p |
| 7401 | 12p | 4024 | 50p |
| 7402 | 12p | 4025 | 20p |
| 7403 | 13p | 4026 | 130p |
| 7404 | 17p | 4027 | 45p |
| 7409 | 18p | 4028 | 75p |
| 7410 | 18p | 4029 | 80p |
| 7412 | 18p | 4030 | 50p |
| 7413 | 28p | 4031 | 195p |
| 7420 | 16p | 4032 | 145p |
| 7430 | 18p | 4033 | 104p |
| 7432 | 18p | 4034 | 290p |
| 7440 | 18p | 4035 | 105p |
| 7442 | 88p | 4036 | 110p |
| 7448 | 75p | 4037 | 290p |
| 7473 | 32p | 4038 | 98p |
| 7474 | 32p | 4039 | 73p |
| 7475 | 32p | 4040 | 73p |
| 7476 | 40p | 4041 | 86p |
| 7490 | 35p | 4042 | 86p |
| 7497 | 50p | 4043 | 86p |
| 7493 | 50p | 4044 | 86p |
| 7496 | 45p | 4045 | 160p |
| 74121 | 35p | 4047 | 99p |
| 74123 | 35p | 4048 | 56p |
| 74154 | 90p | 4049 | 38p |
| 74157 | 55p | 4050 | 40p |
| 74122 | 45p | 4051 | 69p |
| 74125 | 50p | 4052 | 75p |
| 74195 | 100p | 4053 | 73p |
| 74196 | 100p | 4054 | 111p |
| 7423 | 140p | 4055 | 121p |
| 74290 | 120p | 4056 | 121p |
| 74365 | 90p | 4059 | 560p |
| 74366 | 90p | 4060 | 112p |
| | | 4061 | 112p |
| | | 4062 | 92p |
| | | 4067 | 422p |
| | | 4068 | 19p |
| | | 4069 | 19p |
| | | 4070 | 28p |
| | | 4071 | 28p |
| | | 4072 | 25p |
| | | 4075 | 20p |
| | | 4076 | 20p |
| | | 4077 | 23p |
| | | 4078 | 23p |
| | | 4081 | 23p |
| | | 4082 | 25p |
| | | 4085 | 88p |
| | | 4086 | 68p |
| | | 4089 | 130p |
| | | 4093 | 68p |
| | | 4094 | 225p |
| | | 4095 | 99p |
| | | 4098 | 32p |
| | | 4098 | 110p |
| | | 4099 | 180p |
| | | 4501 | 25p |
| | | 4502 | 112p |

| | |
|---------|------|
| 74LS | 12p |
| 74LS01 | 12p |
| 74LS02 | 13p |
| 74LS03 | 13p |
| 74LS04 | 13p |
| 74LS08 | 20p |
| 74LS10 | 18p |
| 74LS11 | 20p |
| 74LS12 | 30p |
| 74LS13 | 30p |
| 74LS14 | 80p |
| 74LS15 | 38p |
| 74LS20 | 18p |
| 74LS21 | 30p |
| 74LS22 | 38p |
| 74LS26 | 48p |
| 74LS27 | 48p |
| 74LS30 | 18p |
| 74LS32 | 23p |
| 74LS37 | 38p |
| 74LS38 | 35p |
| 74LS40 | 25p |
| 74LS42 | 56p |
| 74LS47 | 78p |
| 74LS48 | 85p |
| 74LS49 | 99p |
| 74LS53 | 30p |
| 74LS74 | 30p |
| 74LS75 | 42p |
| 74LS85 | 98p |
| 74LS86 | 39p |
| 74LS90 | 15p |
| 74LS93 | 70p |
| 74LS96 | 160p |
| 74LS107 | 40p |
| 74LS112 | 75p |
| 74LS123 | 63p |
| 74LS125 | 50p |
| 74LS126 | 60p |
| 74LS132 | 79p |
| 74LS138 | 89p |
| 74LS139 | 75p |
| 74LS148 | 170p |
| 74LS151 | 75p |
| 74LS153 | 75p |
| 74LS155 | 55p |
| 74LS157 | 74p |
| 74LS160 | 115p |
| 74LS161 | 78p |
| 74LS163 | 90p |
| 74LS164 | 90p |
| 74LS165 | 150p |
| 74LS168 | 190p |
| 74LS173 | 100p |
| 74LS174 | 98p |
| 74LS175 | 98p |
| 74LS181 | 280p |
| 74LS190 | 110p |
| 74LS195 | 87p |
| 74LS196 | 100p |
| 74LS221 | 110p |
| 74LS240 | 210p |
| 74LS241 | 200p |
| 74LS242 | 220p |
| 74LS244 | 175p |
| 74LS245 | 220p |
| 74LS251 | 120p |
| 74LS253 | 120p |
| 74LS257 | 110p |
| 74LS260 | 90p |
| 74LS273 | 175p |
| 74LS290 | 85p |
| 74LS293 | 120p |
| 74LS366 | 87p |
| 74LS373 | 170p |
| 74LS374 | 170p |
| 74LS375 | 140p |
| 74LS393 | 135p |
| 74LS490 | 140p |
| 74LS670 | 260p |

| | |
|---------|------|
| 74LS01 | 12p |
| 74LS02 | 13p |
| 74LS03 | 13p |
| 74LS04 | 13p |
| 74LS08 | 20p |
| 74LS10 | 18p |
| 74LS11 | 20p |
| 74LS12 | 30p |
| 74LS13 | 30p |
| 74LS14 | 80p |
| 74LS15 | 38p |
| 74LS20 | 18p |
| 74LS21 | 30p |
| 74LS22 | 38p |
| 74LS26 | 48p |
| 74LS27 | 48p |
| 74LS30 | 18p |
| 74LS32 | 23p |
| 74LS37 | 38p |
| 74LS38 | 35p |
| 74LS40 | 25p |
| 74LS42 | 56p |
| 74LS47 | 78p |
| 74LS48 | 85p |
| 74LS49 | 99p |
| 74LS53 | 30p |
| 74LS74 | 30p |
| 74LS75 | 42p |
| 74LS85 | 98p |
| 74LS86 | 39p |
| 74LS90 | 15p |
| 74LS93 | 70p |
| 74LS96 | 160p |
| 74LS107 | 40p |
| 74LS112 | 75p |
| 74LS123 | 63p |
| 74LS125 | 50p |
| 74LS126 | 60p |
| 74LS132 | 79p |
| 74LS138 | 89p |
| 74LS139 | 75p |
| 74LS148 | 170p |
| 74LS151 | 75p |
| 74LS153 | 75p |
| 74LS155 | 55p |
| 74LS157 | 74p |
| 74LS160 | 115p |
| 74LS161 | 78p |
| 74LS163 | 90p |
| 74LS164 | 90p |
| 74LS165 | 150p |
| 74LS168 | 190p |
| 74LS173 | 100p |
| 74LS174 | 98p |
| 74LS175 | 98p |
| 74LS181 | 280p |
| 74LS190 | 110p |
| 74LS195 | 87p |
| 74LS196 | 100p |
| 74LS221 | 110p |
| 74LS240 | 210p |
| 74LS241 | 200p |
| 74LS242 | 220p |
| 74LS244 | 175p |
| 74LS245 | 220p |
| 74LS251 | 120p |
| 74LS253 | 120p |
| 74LS257 | 110p |
| 74LS260 | 90p |
| 74LS273 | 175p |
| 74LS290 | 85p |
| 74LS293 | 120p |
| 74LS366 | 87p |
| 74LS373 | 170p |
| 74LS374 | 170p |
| 74LS375 | 140p |
| 74LS393 | 135p |
| 74LS490 | 140p |
| 74LS670 | 260p |

| | |
|---------|------|
| 74LS01 | 12p |
| 74LS02 | 13p |
| 74LS03 | 13p |
| 74LS04 | 13p |
| 74LS08 | 20p |
| 74LS10 | 18p |
| 74LS11 | 20p |
| 74LS12 | 30p |
| 74LS13 | 30p |
| 74LS14 | 80p |
| 74LS15 | 38p |
| 74LS20 | 18p |
| 74LS21 | 30p |
| 74LS22 | 38p |
| 74LS26 | 48p |
| 74LS27 | 48p |
| 74LS30 | 18p |
| 74LS32 | 23p |
| 74LS37 | 38p |
| 74LS38 | 35p |
| 74LS40 | 25p |
| 74LS42 | 56p |
| 74LS47 | 78p |
| 74LS48 | 85p |
| 74LS49 | 99p |
| 74LS53 | 30p |
| 74LS74 | 30p |
| 74LS75 | 42p |
| 74LS85 | 98p |
| 74LS86 | 39p |
| 74LS90 | 15p |
| 74LS93 | 70p |
| 74LS96 | 160p |
| 74LS107 | 40p |
| 74LS112 | 75p |
| 74LS123 | 63p |
| 74LS125 | 50p |
| 74LS126 | 60p |
| 74LS132 | 79p |
| 74LS138 | 89p |
| 74LS139 | 75p |
| 74LS148 | 170p |
| 74LS151 | 75p |
| 74LS153 | 75p |
| 74LS155 | 55p |
| 74LS157 | 74p |
| 74LS160 | 115p |
| 74LS161 | 78p |
| 74LS163 | 90p |
| 74LS164 | 90p |
| 74LS165 | 150p |
| 74LS168 | 190p |
| 74LS173 | 100p |
| 74LS174 | 98p |
| 74LS175 | 98p |
| 74LS181 | 280p |
| 74LS190 | 110p |
| 74LS195 | 87p |
| 74LS196 | 100p |
| 74LS221 | 110p |
| 74LS240 | 210p |
| 74LS241 | 200p |
| 74LS242 | 220p |
| 74LS244 | 175p |
| 74LS245 | 220p |
| 74LS251 | 120p |
| 74LS253 | 120p |
| 74LS257 | 110p |
| 74LS260 | 90p |
| 74LS273 | 175p |
| 74LS290 | 85p |
| 74LS293 | 120p |
| 74LS366 | 87p |
| 74LS373 | 170p |
| 74LS374 | 170p |
| 74LS375 | 140p |
| 74LS393 | 135p |
| 74LS490 | 140p |
| 74LS670 | 260p |

| | |
|---------|------|
| 74LS01 | 12p |
| 74LS02 | 13p |
| 74LS03 | 13p |
| 74LS04 | 13p |
| 74LS08 | 20p |
| 74LS10 | 18p |
| 74LS11 | 20p |
| 74LS12 | 30p |
| 74LS13 | 30p |
| 74LS14 | 80p |
| 74LS15 | 38p |
| 74LS20 | 18p |
| 74LS21 | 30p |
| 74LS22 | 38p |
| 74LS26 | 48p |
| 74LS27 | 48p |
| 74LS30 | 18p |
| 74LS32 | 23p |
| 74LS37 | 38p |
| 74LS38 | 35p |
| 74LS40 | 25p |
| 74LS42 | 56p |
| 74LS47 | 78p |
| 74LS48 | 85p |
| 74LS49 | 99p |
| 74LS53 | 30p |
| 74LS74 | 30p |
| 74LS75 | 42p |
| 74LS85 | 98p |
| 74LS86 | 39p |
| 74LS90 | 15p |
| 74LS93 | 70p |
| 74LS96 | 160p |
| 74LS107 | 40p |
| 74LS112 | 75p |
| 74LS123 | 63p |
| 74LS125 | 50p |
| 74LS126 | 60p |
| 74LS132 | 79p |
| 74LS138 | 89p |
| 74LS139 | 75p |
| 74LS148 | 170p |
| 74LS151 | 75p |
| 74LS153 | 75p |
| 74LS155 | 55p |
| 74LS157 | 74p |
| 74LS160 | 115p |
| 74LS161 | 78p |
| 74LS163 | 90p |
| 74LS164 | 90p |
| 74LS165 | 150p |
| 74LS168 | 190p |
| 74LS173 | 100p |
| 74LS174 | 98p |
| 74LS175 | 98p |
| 74LS181 | 280p |
| 74LS190 | 110p |
| 74LS195 | 87p |
| 74LS196 | 100p |
| 74LS221 | 110p |
| 74LS240 | 210p |
| 74LS241 | 200p |
| 74LS242 | 220p |
| 74LS244 | 175p |
| 74LS245 | 220p |
| 74LS251 | 120p |
| 74LS253 | 120p |
| 74LS257 | 110p |
| 74LS260 | 90p |
| 74LS273 | 175p |
| 74LS290 | 85p |
| 74LS293 | 120p |
| 74LS366 | 87p |
| 74LS373 | 170p |
| 74LS374 | 170p |
| 74LS375 | 140p |
| 74LS393 | 135p |
| 74LS490 | 140p |
| 74LS670 | 260p |


| | |
|--------|-----|
| 74LS01 | 12p |
| 74LS02 | 13p |
| 74LS03 | 13p |
| 74LS04 | 13p |
| 74LS08 | 20p |
| 74LS10 | 18p |
| 74LS11 | 20p |
| 74LS12 | 30p |
| 74LS13 | 30p |
| 74LS14 | 80p |
| 74LS15 | 38p |
| 74LS20 | 18p |
| 74LS21 | 30p |
| 74LS22 | 38p |
| 74LS26 | 48p |
| 74LS27 | 48p |
| 74LS30 | 18p |
| 74LS32 | 23p |
| 74LS37 | 38p |
| 74LS38 | 35p |
| 74LS40 | 25p |
| 74LS42 | 56p |
| 74LS47 | 78p |
| 74LS | |

Guide to Broadcasting Stations

18th Edition

Around the world some thousands of radio stations are sending signals. If you're receiving, this standard guide will tell you who's where. It lists stations broadcasting in the long, medium, short wave and vhf bands, dealing with them by frequency, geographical location and alphabetical order. Sections are helpfully cross referenced. The Wireless World Guide to Broadcasting Stations is the eighteenth edition of a publication which has sold over 270,000 copies. In addition to the stations data, it includes much useful information on radio receivers, aerials, propagation, signal identifications and reception reports.

£3.25 inc. postage.

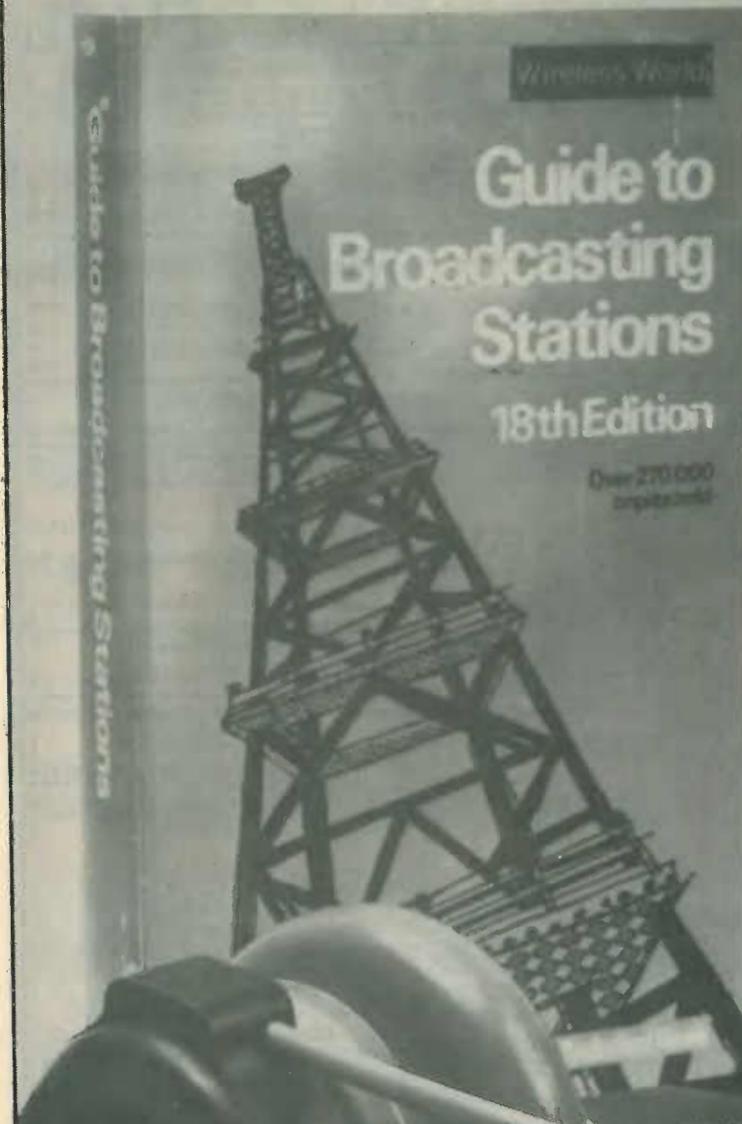

To: General Sales Dept., Room 205
Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS
Please send me _____ copy/ies of the Wireless World Guide to Broadcasting Stations (18th edition) @ £3.25 a copy inclusive, (U.K.), \$8 overseas, remittance enclosed. Cheque/P.O. payable to IPC Business Press Ltd.

Name _____
(please print)
Address _____

Registered in England No. 677128
Registered Office: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS


FAST ERECTING CLARK MASTS

For World-wide Telecommunications in the 1980's

Clark Masts Ltd. are specialists in the design and manufacture of telescopic and sectional mast systems. With over 25 years' experience in supplying masts to meet exacting military and civil specifications we have the expertise you can depend on.

Extended heights 4m-30 metres capable of lifting headload 1Kg-200Kgs, sectional or telescopic air operated for field or vehicle mounting. Write or phone us for details today.

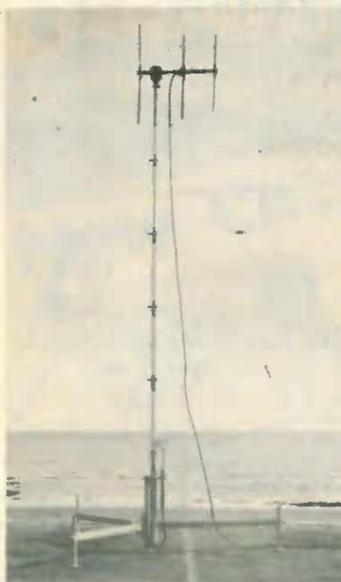Telescopic air operated Clark P.B. 29 Mast 4.5 metres mounted vertically within Volvo vehicle.



Telescopic air operated Clark Mast Type QT4m/HP mounted on portable tripod.

CLARK MASTS LTD.
Binstead,
Isle of Wight,
PO 33 3PA, England.

Telephone Ryde (0983) 63691,



Telex 86686

WW - 007 FOR FURTHER DETAILS

Telequipment S61 SINGLE TRACE LIGHTWEIGHT 5 MHz OSCILLOSCOPE

LARGE
5" DISPLAY
CRT

DIRECT FROM
MANUFACTURER SCOOP PURCHASE



NEW!

Unused, Ex-stock,
to manufacturer's
full specification

ONLY
£122 + VAT
90 DAY
GUARANTEE

This offer cannot be repeated.
Available only whilst stocks last.

- BANDWIDTH DC to 5MHz (-3dB)
- DEFLECTION 5mV/div to 20V/div
- SWEEP SPEEDS 500ms/div to 1µs/div
- TRIGGERING Variable control or Auto
- SOURCE Internal, External or Line
- C.R.T. 5" tube 8 x 10 divisions (each division nominally 1cm)
- DIMENSIONS 280mm High, 160mm Wide, 370mm Deep, Weight 6.0kg

For complete spec. of the Telequipment S61, or to order direct - complete and post coupon today. Personal callers welcome. Only 5 mins from Camden Town underground. Come and see our complete range of 'Blue Chip' Used Test & Measuring Equipment.

HOW TO ORDER

Fill in coupon and return with your cheque made payable to Carston Electronics Ltd. (Remember to include packaging & dispatch fee. U.K. mainland only.) Or we can debit your Barclay Card or Access Account - tick box as appropriate. Allow 21 days for delivery to your door.

To CARSTON ELECTRONICS LTD.

Shirley House, 27 Camden Road,
London NW1 9NR Telephone 01-267 5311
Please send me the Telequipment S61 scope - I enclose my cheque for £151.80 (which includes £10 net, packing and dispatch + VAT on total).
Please charge my ready-credit card Barclay/Access, account No. _____
Please send me further information on the S61 /and details of your complete range of 'second user' equipment

Signature _____

Name: Mr/Mrs/Miss _____
(BLOCK CAPITALS PLEASE)

Address for delivery _____

Post Code _____

Registered No. 890082 England. 1/WW



WW - 070 FOR FURTHER DETAILS

BULK EPROM PROGRAMMING

P4000 PRODUCTION EPROM PROGRAMMER



2-YEAR WARRANTY

This unit provides simple, reliable programming of up to 8 EPROMS simultaneously. It has been designed for ease of operator use — a single 'program' key starts the self check — blank check — program — verify sequence. Independent blank check & verify controls are provided along with mode, pass/fail indicators for each copy socket and a sounder to signal a correct key command & the end of a programming run. Any of the 2704/2708/2716 (3 rail) & 2508/2758/2516/2716/2532/2732 (single rail) EPROMS may be selected without hardware or personality card changes. **PRICE £545 + VAT.** Postage paid

BULK EPROM ERASING

EX-STOCK



MODEL UV141 EPROM ERASER

- 14 EPROM capacity
- Fast erase time
- Built-in 5-50 minute timer
- Convenient slide-tray loading of devices
- Safety interlocked to prevent eye and skin damage
- Rugged construction
- MINS & ERASE indicators
- Price £78 + VAT postage paid.

MODEL UV140 EPROM ERASER

Similar to Model UV141 but without timer. **Price £61.50 + VAT** post paid

BULK EPROMS

EX-STOCK

| | | | | | |
|----------------------------|-------|-------|-------|-------|--------|
| | 1-9 | 10-24 | 25-49 | 50-99 | 100 up |
| 2716 (450ns) (single rail) | £9.00 | £8.00 | £7.35 | £7.00 | £6.60 |
| 2708 (450ns) | £4.80 | £4.30 | £3.90 | £3.60 | £3.40 |

DEDUCT A FURTHER 5% FOR CASH WITH ORDER ON THESE EPROM PRICES.

Postage and Packing is included in all prices. ADD VAT at 15%. All our EPROMS are manufactured by leading companies and are fully guaranteed, branded and to full specification.

WRITE OR TELEPHONE FOR FURTHER DETAILS OR SEND OFFICIAL COMPANY ORDERS/CHEQUES TO:

PLEASE NOTE NEW ADDRESS & TELEPHONE NUMBER

GP INDUSTRIAL ELECTRONICS LTD.

Unit 6, Burke Road, Totnes Industrial Estate, Totnes, Devon
Telephone: Totnes (0803) 863360 sales, 863380 technical
DISTRIBUTORS REQUIRED - EXPORT ENQUIRIES WELCOME

WW - 029 FOR FURTHER DETAILS

PRODUCTION TESTING

DEVELOPMENT

SERVICING

POWER UNITS

Now available with 3 OUTPUTS



Type 250VRU/30/25

- OUTPUT 1: 0-30v, 25A DC
- OUTPUT 2: 0-70v, 10A AC
- OUTPUT 3: 0-250v, 4A AC

ALL Continuously Variable

Valradio

VALRADIO LIMITED, BROWELLS LANE, FELTHAM
MIDDLESEX TW13 7EN
Telephone: 01-890 4242/4837

WW-032 FOR FURTHER DETAILS

RUBBER DUCK CALLING LOGI BAIRD - "SAY MAC WHERE DO I GET R.F TRANSISTORS 2-30 MHZ, CIRCUIT BOARDS AND APPLICATION NOTES?"

GAILAN OF COURSE!! THEY'VE ALWAYS GOT WHAT I WANT, MOTOROLA M.R.F AND JAPANESE REPLACEMENT TYPES.

BURDETT ROAD, WISBECH CAMBS. PE13 2PS
TEL. 0945 63281 TELEX 32630

WW - 006 FOR FURTHER DETAILS


NEW FROM REDITRONICS

HERE'S HOW TO TALK TO ALL OF THE PEOPLE ALL OF THE TIME

with a communications system built up from the all-embracing, constantly expanding range of

REDITRONICS EQUIPMENT

The latest addition to that range -

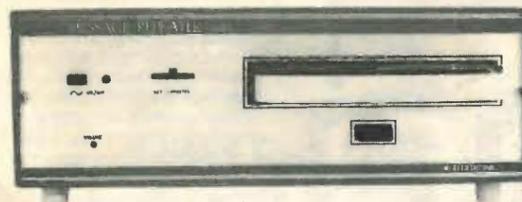

'SERIES TWO' MESSAGE REPEATER

with 4-TRACK CAPABILITY

for four-message or four-language simultaneous or selective tape playback through external amplifiers, plus one selected track through an internal amplifier. 'Add-ons' - slide-synchronizer, monitor loudspeaker, associated multi-channel amplifiers.

When it comes to SOUND communications, REDITRONICS EQUIPMENT does MORE FOR LESS. REDITRONICS is the one name that says it all.

Send for details of any item, and our full brochure, of a range of equipment that can provide every integrated link in the chain of a tailor-made sound communications system.

REDIFFUSION REDITRONICS LTD.,
La Pouquelaye, St Helier, Jersey, Channels Islands
Tel: Jersey (0534) 30321 Telex: 4192341
U.K. DEPOT: River View Road, Bitterne, Southampton, Hampshire, U.K.
Tel: Southampton (0703) 555566

DISTRIBUTORS FOR GREATER LONDON & HOME COUNTIES:
MUSITUNE LTD., 388 Green Lanes, London N4 1DW Tel: 01-802 1163

REDITRONICS

TOTAL SYSTEMS CAPABILITY



DORAM ELECTRONICS LTD

Fitzroy House, Market Place, Swaffham, Norfolk, PE37 7QH.

New Catalogue



40p

FREE competition entry with catalogue

to be refunded with first order

Please send me a copy of your new catalogue

REF. Dept.WW

NAME _____
ADDRESS _____

I enclose cheque/postal order for 40p

WW - 041 FOR FURTHER DETAILS

NEED ENCLOSING?

Now, CSC are really in the hardware business, with a series of plastic cases ideally suited to applications ranging from hand-held probes to hi-fi equipment. CSC cases are moulded in robust plastic and come with all the necessary screws, covers and, where appropriate, battery compartments, connectors and transparent panels for displays. And CSC can provide customer-specified variations for large-quantity orders. Fill in the coupon for more details.

CSC (UK) Ltd, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ. Telephone: (0799) 21682. Telex: 817477.

| | | |
|---|--|---|
| CTP- Probe Case (£2.30 Nett) £3.50 Qty. | DMC-2 Design-Mate Case (£3.85 Nett) £5.29 Qty. | CBP-1 Portable Case (£5.75 Nett) £7.76 Qty. |
| CTH-1 Handheld Case (£3.00 Nett) £4.31 Qty. | DMC-1 Design-Mate Case (£4.25 Nett) £5.75 Qty. | CTB-1 Bench Topper Case (£7.15 Nett) £9.37 Qty. |

Bold prices include P & P and 15% VAT. Please deduct £1 postage from each additional order.

I enclose cheque/PO for £.....
or debit my Barclaycard, Access, American Express card
No..... Exp. date.....
or Tel: (0799) 21682 with your card number and your order will be in the post immediately.

NAME _____
ADDRESS _____

CONTINENTAL SPECIALITIES CORPORATION
CSC FREE catalogue tick box

Continental Specialities Corporation (UK) Limited, Dept. 7MM
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

TOMORROW'S TOOLS TODAY

Eddystone at SONIC SOUND AUDIO

BRITAIN'S No.1 AUDIO STORE

The Leaders in Short Wave

SOLE U.K. RETAIL DISTRIBUTORS FOR EDDYSTONE

Sonic Sound, the premier home entertainment store have now added yet another big name in the field of sound equipment to further enhance their prestige in London's centre of the audio/visual and Hi-Fi field in Tottenham Court Road.

Eddystone, at the top of the tree since short wave began, have now appointed Sonic Sound Audio as sole retail distributors in the United Kingdom.

Anyone even contemplating purchasing short wave equipment, be they looking for the best possible available for their Embassy, press department or home use, should visit or contact Sonic where they will be able to view and listen to the most comprehensive range of the latest short wave equipment on the market today.

Listen and choose in comfort at Britain's most up-to-date air conditioned sound demonstration studios. Full ranges of Hi-Fi, Video equipment, In-car and portables, etc., from all leading manufacturers: B & O, Sanyo, Sony, Hitachi, Pioneer, J.V.C.

THE COMMUNICATION CENTRE

SONIC SOUND AUDIO Eddystone

248-256 TOTTENHAM COURT ROAD LONDON W1 TEL: 01-637 1908 A Marconi Group Company.

WW — 010 FOR FURTHER DETAILS

You Need Integrated Circuits? WE HAVE THEM!

(Even the "Difficult" ones!)

- Silicon Solar Cells? Solar Cell Arrays?
- Photovoltaic Solar Cell Panels?
- Solar powered Toys & Novelties?

Just Phone or Telex Bob Owen

TELEX 181-758 Answbk. "Calconsdg"

PHONE (714) 565 8303

CALCON LIMITED

9235 CHESAPEAKE DR. STE. F. S.D., CA 92123, USA

WW — 023 FOR FURTHER DETAILS

Self Instruction Courses

Microcomputers are coming - ride the wave! Learn to program.

Millions of jobs are threatened but millions will be created. Learn BASIC - the language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency, with a unique style of graded hints. In 60 straightforward lessons you will learn the five essentials of programming: problem definition, flowcharting, coding the program, debugging, and clear documentation.

BOOK 1 Computers and what they do well; READ, DATA, PRINT, powers, brackets, variable names; LET; errors; coding simple programs. BOOK 2 High and low level languages; flowcharting; functions; REM and documentation; INPUT, IF... THEN, GO TO; limitations of computers, problem definition. BOOK 3 Compilers and interpreters; loops, FOR...NEXT, RESTORE; debugging; arrays; bubble sorting; TAB BOOK 4 Advanced BASIC; subroutines; strings; files; complex programming; examples; glossary.



Also **THE BASIC HANDBOOK (BHB) £11.50** An encyclopaedic guide to the major BASIC dialects. A must if you use other peoples' programs

and: **ALGORITHM WRITER'S GUIDE (AWG) £4.00** Communicate by flow chart! Learn to use Yes/No questions for: procedures, system design, safety, legislation etc.

Understand Digital Electronics

Written for the student or enthusiast, this course is packed with information, diagrams, and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters, and simple arithmetic circuits; and finally to an understanding of the design and operation of calculators and computers.



BOOK 1 Decimal, Octal, hexadecimal, and binary number systems and conversion between number systems; negative numbers; complementary systems. BOOK 2 OR and AND functions; multiple-input gates; truth tables; De Morgan's Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic. BOOK 3 Half, full, serial, and parallel adders; subtraction; processors and ALUs; multiplication and division. BOOK 4 flip flops; shift registers; asynchronous, synchronous, ring, Johnson, and exclusive-OR feedback counters; ROMS and RAMS. BOOK 5 Structure of calculators; keyboard encoding; decoding display-data; register systems; control unit; PROM; address-decoding. BOOK 6 CPU; memory organisation character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming, assemblers; computers; executive programs; operating systems.

DIGITAL COMPUTER LOGIC & ELECTRONICS. (DCL) £7.50 A course covering the material in italics above, but at a slower pace. (4 vols)

GUARANTEE — No risk to you. If you are not completely satisfied your money will be refunded without question, on return of the books in good condition.

PLEASE SEND ME: — Quantity

- CPB (£10.00)
- BHB (£11.50)
- AWG (£4.00)
- DDS (£13.50)
- DCL (£7.50)

FOUR WAYS TO PAY:
 1) A U.K. cheque or a U.K. postal order (Not Eire or overseas)
 2) A bank draft, in sterling on a London bank (available at any major bank)
 3) Please charge my Access/M.Ch. Barclay/TrustC/Visa. Am. Exp. Diners.
 4) Or phone us with these credit card details: 0480 67446 (ansaphone) 24 hour service.

Card No. Signed
THESE PRICES COVER THE COST OF SURFACE MAIL WORLDWIDE. AIRMAIL:
 Eur. N.Af. Mid.E. add 1/2 to price of books: Jpn, Aus, N.Z, Pcfc add 3/4; elsewhere add 1/2

Name
 Address

U.K. Delivery: up to 21 days

Cambridge Learning Limited, Unit 38, Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs. PE17 4BR, England
 Reg. In Eng. No. 1328762

PM COMPONENTS LTD. VALVE & COMPONENTS SPECIALISTS

CONINGS HOUSE, WROTHAM ROAD, MEOPHAM, KENT. TEL. 0474 813225

| SEMICONDUCTORS | | | | I.C.s | | | | DIODES | | | | | | | |
|----------------|------|--------|------|-------|------|-------|------|--------|------|---------|------|----------|------|----------|------|
| AC126 | 0.22 | BC108A | 0.10 | BD116 | 0.52 | BF178 | 0.26 | BU500 | 1.75 | CA270CW | 1.00 | SN76644N | 1.35 | TBA810AS | 1.35 |
| AC127 | 0.22 | BC108C | 0.10 | BD124 | 0.52 | BF179 | 0.26 | BU520 | 0.40 | MC1307 | 1.00 | SN76650N | 1.05 | TBA820Q | 1.65 |
| AC128 | 0.28 | BC109B | 0.10 | BD131 | 0.32 | BF180 | 0.29 | MUE520 | 0.44 | MC1327 | 1.00 | SN76668N | 0.70 | TBA850 | 2.35 |
| AC141K | 0.34 | BC114 | 0.11 | BD133 | 0.40 | BF182 | 0.29 | R2088B | 1.70 | MC1349 | 1.30 | TAAS59 | 0.25 | TBA900 | 1.40 |
| AC142K | 0.30 | BC115A | 0.12 | BD135 | 0.30 | BF183 | 0.29 | R2540 | 2.45 | MC1350 | 1.00 | TAA61B | 1.20 | TBA900Q | 1.40 |
| AC176 | 0.22 | BC140 | 0.21 | BD136 | 0.30 | BF184 | 0.28 | TIP29C | 0.42 | MC1351 | 1.00 | TAA700 | 1.70 | TCA270Q | 1.10 |
| AC176K | 0.31 | BC141 | 0.25 | BD137 | 0.29 | BF185 | 0.28 | TIP29C | 0.42 | TBA120B | 0.70 | TCA280 | 2.15 | | |
| AC187K | 0.28 | BC142 | 0.21 | BD138 | 0.30 | BF186 | 0.28 | TIP30C | 0.42 | TBA120S | 0.70 | TCA90 | 1.65 | | |
| AC187K | 0.28 | BC143 | 0.24 | BD139 | 0.32 | BF194 | 0.11 | TIP31C | 0.42 | MC1352 | 1.00 | TDA440 | 2.85 | | |
| AC188 | 0.22 | BC147 | 0.09 | BD140 | 0.30 | BF195 | 0.11 | TIP32C | 0.42 | ML231B | 2.10 | TDA100A | 1.85 | | |
| AD146 | 0.70 | BC146 | 0.09 | BD144 | 0.29 | BF196 | 0.11 | TIP32C | 0.42 | ML232B | 2.10 | TDA1170 | 1.95 | | |
| AD161 | 0.30 | BC149 | 0.09 | BD144 | 0.29 | BF197 | 0.11 | TIP33B | 0.55 | TBA120U | 1.00 | TDA1190 | 2.15 | | |
| AD161 | 0.30 | BC149 | 0.09 | BD144 | 0.29 | BF198 | 0.10 | TIP42C | 0.47 | TBA120S | 0.70 | TDA1327 | 1.70 | | |
| AC181/2 | 1.04 | BC157 | 0.10 | BD203 | 0.78 | BF199 | 0.14 | TIP47 | 0.85 | SAS5705 | 1.80 | TDA1470 | 1.85 | | |
| AD162 | 0.30 | BC158 | 0.09 | BD204 | 0.70 | BF200 | 0.30 | TIP47 | 0.85 | SL917B | 0.25 | TDA2030 | 2.80 | | |
| AF124 | 0.34 | BC159 | 0.09 | BD222 | 0.46 | BF201 | 0.15 | TIP47 | 0.85 | SL1310 | 1.80 | TDA2522 | 2.40 | | |
| AF125 | 0.32 | BC160 | 0.29 | BD225 | 0.46 | BF202 | 0.26 | TIP47 | 0.85 | TBA306 | 1.10 | TDA2530 | 1.85 | | |
| AF126 | 0.32 | BC161 | 0.28 | BD237 | 0.30 | BF203 | 0.26 | TIP47 | 0.85 | TBA306 | 1.10 | TDA2532 | 2.40 | | |
| AF127 | 0.32 | BC170B | 0.10 | BD238 | 0.33 | BF204 | 0.15 | TIP47 | 0.85 | TBA306 | 1.10 | TDA2541 | 2.15 | | |
| AF139 | 0.42 | BC171 | 0.06 | BD238 | 0.33 | BF205 | 0.15 | TIP47 | 0.85 | TBA306 | 1.10 | TDA2541 | 2.15 | | |
| AF150 | 0.42 | BC171A | 0.10 | BD238 | 0.33 | BF206 | 0.15 | TIP47 | 0.85 | TBA306 | 1.10 | TDA2541 | 2.15 | | |
| AF229 | 0.42 | BC172 | 0.00 | BD238 | 0.33 | BF207 | 0.15 | TIP47 | 0.85 | TBA306 | 1.10 | TDA2541 | 2.15 | | |
| AU110 | 2.00 | BC172C | 0.10 | BD238 | 0.33 | BF208 | 0.15 | TIP47 | 0.85 | TBA306 | 1.10 | TDA2541 | 2.15 | | |
| AU113 | 1.48 | BC173B | 0.10 | BD238 | 0.33 | BF209 | 0.15 | TIP47 | 0.85 | TBA306 | 1.10 | TDA2541 | 2.15 | | |
| BC107 | 0.10 | BC174A | 0.00 | BD238 | 0.33 | BF210 | 0.15 | TIP47 | 0.85 | TBA306 | 1.10 | TDA2541 | 2.15 | | |
| BC107B | 0.10 | BC174A | 0.00 | BD238 | 0.33 | BF211 | 0.15 | TIP47 | 0.85 | TBA306 | 1.10 | TDA2541 | 2.15 | | |
| BC108 | 0.10 | BC182L | 0.10 | BD238 | 0.33 | BF212 | 0.15 | TIP47 | 0.85 | TBA306 | 1.10 | TDA2541 | 2.15 | | |

| NEW BRANDED VALVES | | | | WIREWOUND RESISTORS | | | | |
|--------------------|-------|--------|------|---------------------|--|------|-------|------|
| A1998 | 10.00 | EBF90 | 0.55 | 4 WATT | 4R7 5R6 6R8 10R 22R 33R 47R 68R 100R 150R 220R | 0.13 | 12AU7 | 0.60 |
| A2067 | 11.50 | EBF89 | 0.70 | 7 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 0.12 | 12AX7 | 0.65 |
| A2134 | 8.00 | ECC81 | 0.55 | 11 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 0.17 | 12AX7 | 0.65 |
| A2233 | 7.20 | ECC82 | 0.55 | 17 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 0.24 | 12AX7 | 0.65 |
| A2321 | 9.00 | ECC83 | 0.60 | 25 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 0.31 | 12AX7 | 0.65 |
| BT58 | 30.00 | ECC84 | 0.60 | 40 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 0.38 | 12AX7 | 0.65 |
| D3a | 18.00 | ECC85 | 0.60 | 60 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 0.45 | 12AX7 | 0.65 |
| DM160 | 2.10 | ECC86 | 0.65 | 80 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 0.52 | 12AX7 | 0.65 |
| DY86/87 | 0.55 | ECC91 | 0.65 | 100 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 0.59 | 12AX7 | 0.65 |
| DY802 | 0.90 | ECC189 | 0.78 | 150 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 0.66 | 12AX7 | 0.65 |
| EB00C | 4.75 | ECC204 | 0.46 | 200 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 0.73 | 12AX7 | 0.65 |
| EB00F | 0.25 | ECC207 | 1.30 | 250 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 0.80 | 12AX7 | 0.65 |
| EB1CC | 3.00 | ECCF80 | 0.65 | 300 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 0.87 | 12AX7 | 0.65 |
| EB2CC | 2.25 | ECCF82 | 0.60 | 350 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 0.94 | 12AX7 | 0.65 |
| EB3CC | 3.00 | ECH81 | 0.58 | 400 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 1.01 | 12AX7 | 0.65 |
| EB4CC | 3.00 | ECH83 | 0.78 | 450 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 1.08 | 12AX7 | 0.65 |
| EB5CC | 3.00 | ECH84 | 0.96 | 500 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 1.15 | 12AX7 | 0.65 |
| EB6CC | 3.00 | ECL80 | 0.66 | 550 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 1.22 | 12AX7 | 0.65 |
| EB7CC | 2.00 | ECL82 | 0.58 | 600 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 1.29 | 12AX7 | 0.65 |
| E130L | 13.00 | ECL83 | 1.13 | 650 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 1.36 | 12AX7 | 0.65 |
| E180CC | 4.00 | ECL84 | 0.74 | 700 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 1.43 | 12AX7 | 0.65 |
| E180F | 4.50 | ECL85 | 0.74 | 750 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 1.50 | 12AX7 | 0.65 |
| E182CC | 4.50 | ECL86 | 0.74 | 800 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 1.57 | 12AX7 | 0.65 |
| E180F | 8.25 | EF37A | 3.00 | 850 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 1.64 | 12AX7 | 0.65 |
| EAB00 | 0.56 | EF39 | 2.00 | 900 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 1.71 | 12AX7 | 0.65 |
| EAF90 | 1.40 | EF39 | 1.50 | 950 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 1.78 | 12AX7 | 0.65 |
| EB91 | 0.52 | EF80 | 0.48 | 1000 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 1.85 | 12AX7 | 0.65 |
| EB41 | 0.85 | EF85 | 0.48 | 1050 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 1.92 | 12AX7 | 0.65 |
| EB281 | 0.85 | EF86 | 0.70 | 1100 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 1.99 | 12AX7 | 0.65 |
| EB289 | 0.85 | EF89 | 0.65 | 1150 WATT | 1R 1R5 2R2 3R3 4R7 6R8 10R 15R 22R 33R 47R 56R | 2.06 | 12AX7 | 0.65 |

Many other types available. Please phone or send list for quotation Export & Trade Enquiries Welcome


WW — 073 FOR FURTHER DETAILS

TRUE AS AN Arrow

Professional Wire and Cable Fasteners for all installation requirements.

TELEPHONE — ELECTRONICS ALARM SYSTEMS, ETC.

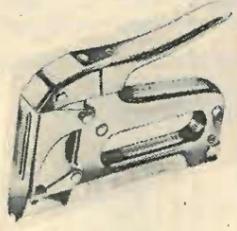4 Precision made models. 12 different staple sizes. Rugged all steel construction in chrome finish. Grooved guide. Grooved driving blade. Tapered striking edge. Jam-proof mechanism (patented). Short span easy compression handle.



Some of the features that make an Arrow cable fastener the outstanding tool for all installation engineers.

Illustrated literature and details of staple sizes available from: **SPECIAL PRODUCTS DISTRIBUTORS LTD.** 81 PICCADILLY, LONDON W1V 0HL TEL. 01-629 9554. Telex 265200 (A/B RACEN) Cables: Speciproduct London W1

WW — 069 FOR FURTHER DETAILS

You could do with a Helper on your test bench.

Helper low cost instruments are specially designed for 'fiddle-free', instant bench testing or mobile servicing of two-way radio equipment.

They'll make life easier for the busy technician whilst giving extremely reliable, lasting service.

The Autopeak Modulation Monitor..

For reading peak modulation and modulation density on any FM receiver whose 2nd I.F. is 400, 450 or 455KHz. Other frequencies may be accommodated on special order.

£280
exc. VAT & P




The Sinadder 3...

Ideal for bench or mobile service van use, with 3 functions in one. Automatic SINAD meter with audio monitoring plus a 1000Hz tone generator. Sensitive AC voltmeter, 1MΩ input impedance, with audio monitor for tracking down distortion and locating defective stages.

These are just two of our Helper range.

Write now for a product guide and free copy of the mobile radio desk reference.

£220
exc. VAT & P

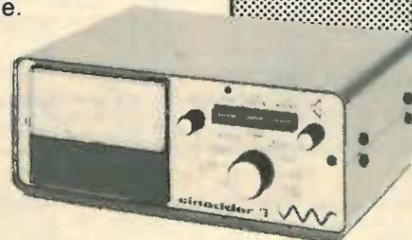


HELPER

LYONS INSTRUMENTS

Lyons Instruments Limited, Hoddesdon, Herts, EN11 9DX, England
Telephone 67161 Telex 22724 A Claude Lyons Company

WW — 013 FOR FURTHER DETAILS

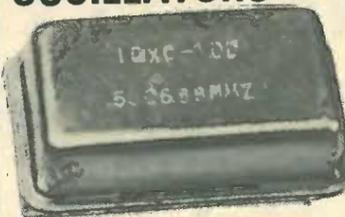IQXO-100 SERIES LOW PROFILE CRYSTAL CLOCK OSCILLATORS



- Hermetically sealed metal package
- DIL compatible
- 20.70L x 13.08W x 5.08H (mm)

The frequency range 600 Hz to 30 MHz is covered by both CMOS (600 Hz - 8 MHz) and TTL (150 KHz - 30 MHz) types having an overall tolerance of ±0.01% from 0 to +70°C. For more stringent requirements, ±0.01% from -55 to +125°C is available.


Many frequencies can be supplied from stock.



INTERFACE QUARTZ DEVICES LTD

29 Market Street, Crewkerne, Somerset TA18 7JU
Crewkerne (0460) 74433 Telex 46283 inface g

WW — 054 FOR FURTHER DETAILS

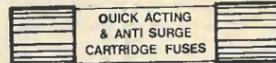

from **£2.80** per 100

Wirewound Power Resistors (Ceramic). 5w-17w 0R5-39K from **£9.35** 100.

Cable Sleeves and Markers from **£1.31** 1000.

Cf. Resistors. 1/4w-2w from **£4.00** 1000.

Crimp Terminals, Elma Knobs and Oials, Audible Warning Devices from **£1.14** each.

Catalogue available (state interests)

Cf. Resistors 1/4w 5%
£3.00 1000 (per value) + carr. and V.A.T. Following values only.

6E8 33E 100E 120E 360E 470E 560E 2K4 2K7 4K7 5K6 7K5 8K2 100K 120K 150K 220K 300K 390K 820K

PBRA LTD.
Golden Green, Tonbridge Kent, TN11 0LH
Hopfield (073274) 345
Member Crystalate Group

WW — 038 FOR FURTHER DETAILS



LOW VOLTAGE POWER DRILLS AND ACCESSORIES

Illustration shows Titan Drill and Stand (Price £27 inc. VAT and Postage) which is One of the combinations which can be purchased from our comprehensive range of Drills and Accessories.

Prices from **£8.34** (Reliant Drill only) inc. VAT and Postage.

Send 25p for Catalogue.

A. D. BAYLISS & SON LTD.
PFERA WORKS, REDMARLEY GLOUCESTER GL19 3JU

Access Welcome
Tel. Bromesbarrow (053 181) 364 or 273

WW — 027 FOR FURTHER DETAILS

DON'T HANG ABOUT!

Latch on to binding posts with the new HPA-1 package from CSC. Designed to provide a firm foundation for a variety of electronic interconnections, complete with insulating shoulder washers and mounting nuts. Versatile, too — they accept bare wires, banana plugs, alligator clips, spade connectors, and hook connectors. There are five red, five black posts, 20 insulating shoulder washers and 20 hex mounting nuts. And for large quantity orders, CSC can supply other colours. You won't find it a bind to post off the CSC coupon for more details — do it today!

CSC (UK) Ltd, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.
Telephone: (0799) 21682. Telex: 817477.

| | | | | |
|-------|---------------|------------|------------------------------------|-----------|
| HPA-1 | Binding Posts | Nett £2.50 | Unit price inc P & P 15% VAT-£3.73 | Div. Head |
|-------|---------------|------------|------------------------------------|-----------|

Please deduct £1 postage from each additional order.

I enclose cheque/PO for £.....
or debit my Barclaycard, Access, American Express card

No..... Exp. date.....
or Tel: (0799) 21682 with your card number and your order will be in the post immediately.

NAME.....

ADDRESS.....
CONTINENTAL SPECIALTIES CORPORATION

CSC FREE catalogue tick box

Continental Specialties Corporation (UK) Limited, Dept. 7SS
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

TOMORROW'S TOOLS TODAY

839 T2A1 239YT0TOR9 FAST PCB PROTOTYPES

SAME DAY DESPATCH

Prototype epoxy glass printed circuit boards up to 250mm x 200mm from your camera ready artwork.

Up to 125mm x 100mm — **£18 + VAT** per side etched only drilling **£5 + VAT**
Up to 250mm x 200mm — **£24 + VAT** per side etched only drilling **£10 + VAT**

Send your order with artwork cheque and instructions—orders received by 10 a.m. guaranteed despatched first class same day etched only (next day etched and drilled) or your money refunded—subject to acceptance of artwork

ACR AUSTERFIELD-CLARK RESEARCH. Tel. 0484 48016
42 Blackhouse Road, Huddersfield HD2 1AR (625)

WW — 051 FOR FURTHER DETAILS

METALFILM RESISTORS 1% Tolerance, 1/4 Watt

| | | | |
|------|-----|-----|------|
| 100R | 1k | 10k | 100k |
| 110R | 1k1 | 11k | 110k |
| 120R | 1k2 | 12k | 120k |
| 130R | 1k3 | 13k | 130k |
| 150R | 1k5 | 15k | 150k |
| 160R | 1k6 | 16k | 160k |
| 180R | 1k8 | 18k | 180k |
| 200R | 2k | 20k | 200k |
| 220R | 2k2 | 22k | 220k |
| 240R | 2k4 | 24k | 240k |
| 270R | 2k7 | 27k | 270k |
| 300R | 3k | 30k | — |
| 330R | 3k3 | 33k | 330k |
| 360R | 3k6 | 36k | — |
| 390R | 3k9 | 39k | — |
| 430R | 4k3 | 43k | — |
| 470R | 4k7 | 47k | 470k |
| 510R | 5k1 | 51k | — |
| 560R | 5k6 | 56k | 560k |
| 620R | 6k2 | 62k | — |
| 680R | 6k8 | 68k | 680k |
| 750R | 7k5 | 75k | — |
| 820R | 8k2 | 82k | 820k |
| 910R | 9k1 | 91k | 910k |

ONLY 4p EACH
Minimum order £10
Minimum 5 pcs per value
89 Values (E24)


Special Offer: 5 PCS OF EACH (445 RESISTORS) ONLY **£16.50**.
High Quality High Stability, High Strength.
VAT inclusive. Add £1.00 p&p all areas.

ORION SCIENTIFIC PRODUCTS LTD.
10 Wardour St., London W1

SPECIAL PURCHASE



OF TOP QUALITY LCD MULTIMETERS

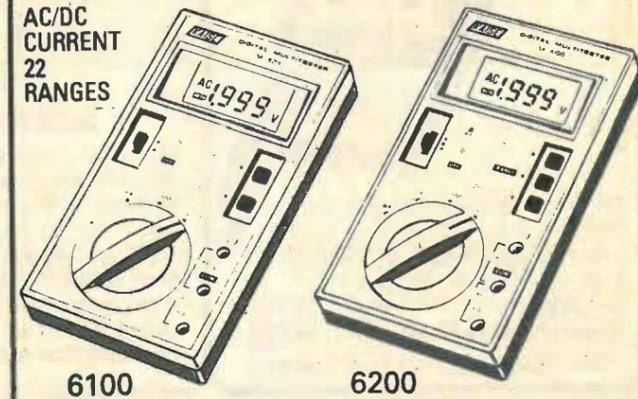

AC/DC CURRENT
22 RANGES

6100

6200

- CHOOSE FROM FOUR MODELS**
- ★ 3 1/2 digit autoranging (volts/Ohms)
 - ★ 200 hours battery life (2 pencils)
 - ★ 10 amp AC/DC (6220 & 6110) ★ 1000v DC 600v AC
 - ★ 200 mA AC/DC (6200 & 6100)
 - ★ Range hold facility (6100 & 6110)
 - ★ Unit and range sign (6110 & 6220)
 - ★ Continuity buzzer (6100 & 6110)

| RESOLUTION | | ACCURACY | |
|----------------------|-----------------|-----------------|-----------------|
| 100 μVDC, 1 mVAC | 6100/6110 | 0.5% DC Volts | 6200/6220 |
| 10 μA AC/DC, 0.1 ΩHM | 1.3% DC Current | 1.4% AC Current | 0.8% DC Volts |
| 10 mA on 10A, AC/DC | 1.2% AC Current | 0.8% Resistance | 1.3% DC Current |
| | 0.5% Resistance | | 1.4% AC Current |
| | | | 0.8% Resistance |
| 6200 | £39.95 | 6100 | £59.95 |
| 6220 | £49.95 | 6110 | £74.95 |

★ All prices include batteries/leads and UK VAT (UK 2/p 65p)
★ Order By Post or Telephone with Barclay or Access.

OR CALL IN AND SEE FOR YOURSELF

Prices correct at 1.12.80 E&EO

Cubegate Limited OPEN 9-6 SIX DAYS A WEEK

AUDIO ELECTRONICS
301 EDGWARE ROAD, LONDON, W2 1BN
TELEPHONE 01-724 3564

Send large SAE (17/p UK) Schools, Companies, etc. free on request.

(Block caps please) REF. (WW)

From: Mr. / Mrs. / Miss

ADDRESS

Please supply QTY

1/We enclose (inc. 65p post) Chq/PO Value

Or debit Barclay/Access No.

WW — 016 FOR FURTHER DETAILS

FREE PROJECT BOOK WITH APS NEW EBBO BREADBOARDS

WITH EACH EBBO IC-1 OR DC-1 STARTER PACK A FREE STEP BY STEP 10 PROJECT BOOKLET ANYBODY CAN BUILD ELECTRONIC PROJECTS WITH EBBO MONEY BACK GUARANTEE IF YOU CAN'T


POWERACE THE MOST EXPENSIVE BREADBOARD IN THE WORLD



Three poweraces that give you the ultimate in breadboarding. Built in power supplies and a FREE logic probe is built into MODEL 102

POWERACE 101 923221 £61.30
POWERACE 102 923222 £95.80
POWERACE 103 923223 £95.80

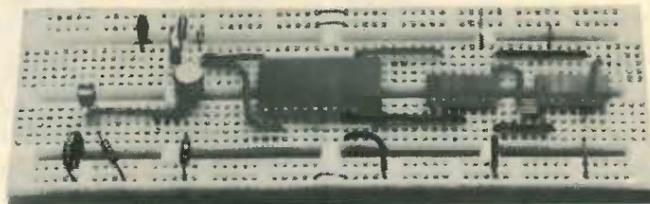
SUPERSTRIP SS2 THE BIGGEST SELLING BREADBOARD IN THE WORLD



When you buy a **SUPERSTRIP BREADBOARD** you buy a breadboard to last you for ever, we give you a **LIFETIME** guarantee. **SUPERSTRIP** is the most used breadboard by hobbyists, professionals and educationalists because it gives you more for you money ... With 840 contact points **SUPERSTRIP** accepts all DIP's and discrete components and with eight bus bars of 25 contact points each **SUPERSTRIP** will take up to nine 14-pin DIP's at any one time. You should only buy a breadboard once so buy the biggest seller with a lifetime guarantee.

SUPERSTRIP SS2 923252 PRICE INCL VAT £9.78

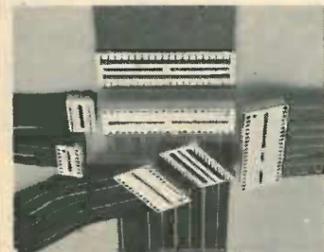DIP-DIP-DIP-DIP-DIP JUMPERS AP DIP JUMPERS ARE THE LOWEST PRICE IN THE UK




- EX-STOCK DELIVERY
- 5 STANDARD LENGTHS
6, 12, 18, 24, 36"
- WITH 14, 16, 24, 40 CONTACTS
- FULLY ASSEMBLED AND TESTED
- INTEGRAL MOULDED ON STRAIN RELIEF
- LINE BY LINE PROBEABILITY

| SINGLE-ENDED | | DOUBLE-ENDED all prices 1-9 off. Huge discounts for quantity | | | | | |
|--------------|-------|--|-------|-------|-------|-------|-------|
| CONTACTS | 24" | CONTACTS | 6" | 12" | 18" | 24" | 36" |
| 14 | £1.67 | 14 | £2.11 | £2.21 | £2.31 | £2.43 | £2.63 |
| 16 | £1.89 | 16 | £2.33 | £2.45 | £2.58 | £2.66 | £2.97 |
| 24 | £2.74 | 24 | £3.45 | £3.62 | £3.78 | £3.94 | £4.30 |
| 40 | £4.38 | 40 | £5.31 | £5.61 | £5.91 | £6.22 | £6.81 |

We can supply DIP, SOCKET, PCB, CARD-EDGE RS232, assemblies made-up, tested, ready for use, cheaper than you can buy the parts, ask for quote.


TEST-CLIP TEST-CLIP

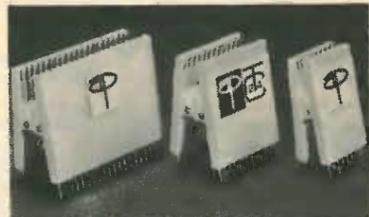

Clip an **AP TEST-CLIP** over an IC and you immediately bring up all the leads from the crowded board into an easy working level.

22 NEW AP TEST-CLIPS TO PICK FROM
examples: TC 14 923695 £2.76
TC 16 923700 £2.91
TC 24 923714 £8.50
TC 40 923722 £12.88

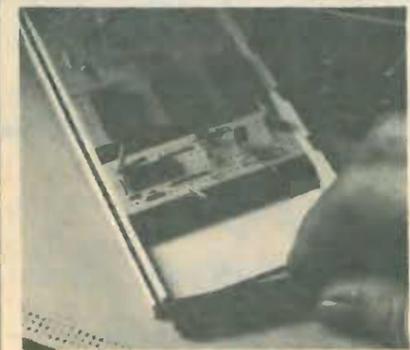NEW The NEW Modular Circuit Building System



Until now hobbyists had to buy professional solderless breadboards for their projects and pay professional prices. But now there's **EBBO** a brand new total breadboarding system that's not only economically priced but offers far more advantages to hobbyists and schools. At the core of the system are two starter packs, one for discrete component projects, the other for integrated circuit (IC) projects. Each starter pack comes with a number of **EBBO** system modules fitted into a tray and an illustrated booklet which guides you step by step in building ten projects. Building a project is simple because the modules are colour-keyed and letter/number indexed and because **EBBO** is expandable, you can add to your system as many of the available compatible modules. For schools and beginners we have a complete step by step approach to teach yourself electronics consisting of five basic electronics books and the discrete starter pack. So buy your **EBBO** Starter Pack, get your free step by step 10 project booklet and start building projects yourself. Free advice or money back guarantee.

BASIC INTEGRATED CIRCUIT STARTER PACK

The IC Starter Pack includes two terminal strips, two distribution strips and a spacer/support strip already in an **EBBO** tray, ready for use. A free project booklet containing ten IC projects with step-by-step instructions completes the pack.

IC-1 Starter Pack £4.24

BASIC DISCRETE COMPONENT STARTER PACK

This Starter Pack contains a tray, discrete component strip, battery holder and connector and project booklet with ten projects.

DC-1 Discrete Starter Pack £4.67



All prices shown are recommended retail incl. VAT. In difficulty send direct, plus 50p P & P. Send S.A.E. for a free copy of colour catalogues detailing our complete range.

AP PRODUCTS, PO BOX 19, SAFFRON WALDEN, ESSEX, (0799) 22036

WW - 048 FOR FURTHER DETAILS

wireless world

A testing time for electronics

Why would a British nationalized industry not wish to associate itself publicly with the work of one of its engineers in using microprocessors, quite properly, to improve its industrial performance? This is what happened with an article we published recently. The engineer was quite free to publish the work, but his employer, the nationalized industry, specifically asked for their name not to be revealed in the article. You would think they would be proud to show their owners, you and me, what they were doing in this up-and-coming technology. Could it be that, with a national background of economic recession and high unemployment, they felt it was not exactly the right time to admit responsibility for "new technology" which might mean a permanent reduction in their work force?

A few years ago the argument that the use of electronics in new products and manufacturing processes would create more jobs than it displaced was readily accepted because of the confidence engendered by the rapid expansion of the free-market economies in the 1950s and '60s and the resulting high level of employment. Today, although the argument could still be valid - because we can point to actual new jobs that have been created - it is beginning to look somewhat feeble against the scale of current events. In Britain we now have over two million unemployed. This fact has come to some people as a sudden shock. Even so they dismiss it as a temporary, though severe, effect of yet another of those swings in the recurring trade cycles we have known for a century or more. It must end, they say. But other, perhaps more discerning, observers see the present figure of two million unemployed as not merely a temporary freak but as part of a longer term "structural" change, as the economists call it. Up to about 1967

unemployment in the UK, running at about 300,000, was roughly matched by the number of job vacancies available. But after 1967 this situation no longer obtained. The unemployment curve began to "take off" upwards, leaving the "vacancies" curve much as it had been before. This trend has continued unmistakably for over a decade.

If these analysts are right and there is indeed a long-term structural increase in unemployment, then electronics and any other technologies being used to improve labour productivity will be scrutinized and tested as never before in the full glare of the public arena. If the higher labour productivity indicates a loss of jobs, rather than an increase of output with the existing level of employment, then the new technology will be opposed far more strongly than if we were living in an expanding economy. Those who introduce it will have to prove, under the most searching examination, that they are not bringing social disruption in its wake by adding even more people to that sad group which always bears the brunt of industrial change - the poor, the unemployed, the unskilled, the handicapped, the chronically ill and the inadequate.

One can only be glad that these new conditions are clearly understood by the central economic organization of the Western capitalist countries, the OECD. In a recent report "Technical change and economic policy" (written by a group including two men with an electronics background) this influential body states firmly that technical change can never be a goal in itself. It must be politically supported by the populations of these countries, and this social sanction "will be forthcoming only if there is a satisfactory balance between the generation of new employment and the loss of old jobs and if technical change is perceived to improve the quality of life."

Editor:
TOM IVALL, M.I.E.R.E.

Deputy Editor:
PHILIP DARRINGTON
01-661 3500 X3586

Technical Editor:
GEOFF SHORTER, B.Sc.
01-661 3500 X3590

Projects Editor:
MIKE SAGIN
01-661 3500 X3588

Communications Editor:
TED PARRATT, B.A.
01-661 3500 X3587

News Editor:
MARTIN ECCLES
01-661 3500 X3589

Drawing Office Manager:
ROGER GOODMAN

Technical Illustrator:
BETTY PALMER

Production & Design:
ALAN KERR

Advertisement Controller:
G. BENTON ROWELL

Advertisement Manager:
BOB NIBBS, A.C.I.I.
01-661 3130

DAVID DISLEY
01-661 3500 X3593

BARBARA MILLER
01-661 3500 X3592

Classified Manager:
BRIAN DURRANT
01-661 3106

JOHN GIBBON (Make-up and copy)
01-661 3500 X3561

Publishing Director:
GORDON HENDERSON

Using the 6802 microprocessor and only 8 other i.cs, this microcomputer design provides up to 4K of e.p.r.o.m., 1K of r.a.m., p.i.a., six digit display and up to eight monitor commands. Although ideal as a trainer, the Nanocomp is also a useful tool for general microprocessor applications. The unit can be built on one printed circuit board and housed with a power supply in a small case.

Two problems which prevent many electronic engineers from learning to use microprocessors are the complexity and cost of taking the first step. Constructing a unit can reduce the cost but may require some troubleshooting if it doesn't work. A simple unit that can be built easily may have limitations which restrict its use. With these points in mind, a microprocessor trainer has been designed which is suitable for a novice but provides sufficient facilities for use as a tool.

A block diagram of the design is shown in Fig. 1. Only 9 i.cs are used, which makes construction quite easy for anyone with the minimum of experience. The central processing unit is a Motorola 6802. Although not a particularly well known microprocessor, it is based on the popular 6800 device and includes clock generation and 128bytes of r.a.m. This reduces the cost and simplifies construction because only one crystal is required to complete the clock generation circuit. For programming, the 6802 is identical to the 6800 and is therefore well supported with software. Apart from the c.p.u. r.a.m., there are two other blocks of memory available. An e.p.r.o.m. permanently stores the monitor program, which takes care of the general "housekeeping" duties such as scanning the keypad, refreshing the display and providing debugging facilities to help with program development. The monitor occupies about 850bytes of the e.p.r.o.m. To improve flexibility, the unit has been designed to accept 1K, 2K and 4K e.p.r.o.ms so that the user can write programs and have them permanently stored for an application such as a dedicated controller. The second memory block is a 1K r.a.m. for developing and running programmes.



A versatile and simple microprocessor trainer

The final section of the block diagram contains the input/output (i/o) circuit which drives the keypad and display, and allows interfacing to other circuits.

The complete circuit is shown in Fig. 2. A clock reference is provided by the 3.2786 MHz crystal and C₁. However, other crystals between 400kHz and 4MHz can be used with an adjustment to C₁ for reliable oscillation. The 6802 clock circuit divides the oscillator frequency by 4 to provide an 819kHz system clock signal (Ø2 of the 6800) at E. This frequency leaves a small safety margin for the devices, which have a maximum operating frequency of 1MHz. A 74LS00 gates the E signal with VMA (valid memory address) to provide VMA.E which is used by the address decoder IC₉ to ensure that other devices on the bus are only accessed when a valid address is present on the address bus. The address decoder generates select lines for the memories and i/o chips by

decoding the three most significant address lines. This provides selection of 8 4K address blocks, of which Y₁, Y₄ and Y₇ are used. Note that the most significant address line, A₁₅, from the c.p.u. is not used because sufficient address space is available without it.

Data pins D₀ to D₇ of the c.p.u. are connected to the data bus. The control bus comprises E, VMA.E, read/write, reset (connected by a push switch and used to start the monitor program at switch-on, and to initialise the i/o chip for programming), IRQ and NMI interrupt lines which allow program execution to be interrupted or, in the case of NMI (non-maskeable interrupt), termination of a monitor command with the Abort key which returns the processor to the monitor switch on point. Both interrupts are connected to external pins for use by an external circuit if required.

As mentioned previously, three sizes of e.p.r.o.m. can be used. Although the 2708 is the cheapest device it will provide only a small amount of spare memory space, and it requires +5V, -5V and +12V supply rails. The 2516 and 2532 only require +5V and leave just over 1K and 3K respectively for expansion.

The main r.a.m. is provided by two 4-bit 2114 i.cs. With the 819kHz clock, slow


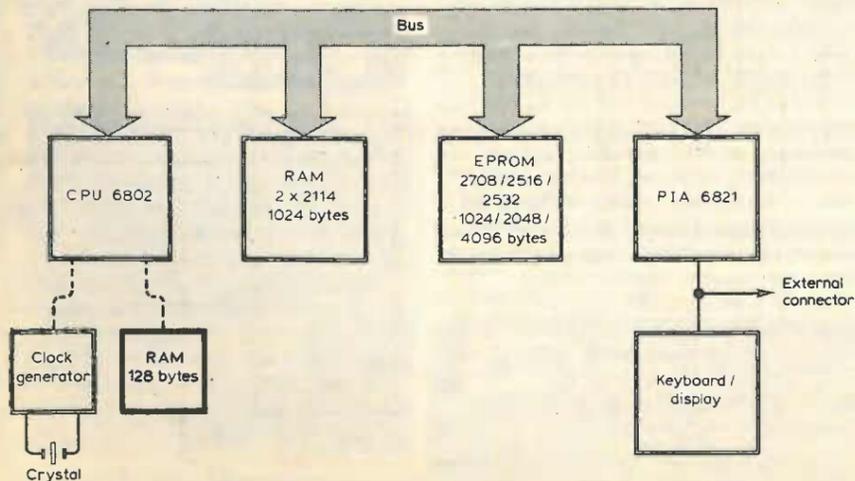


Fig. 1. Block diagram. The 6802 is similar to the 6800 but contains a clock generator and 128bytes of r.a.m.

Fig. 2. Complete logic diagram. Although the circuit can use a 1K 2708 e.p.r.o.m., 2 or 4K devices are recommended because they provide spare memory space and require only one supply rail. ▶

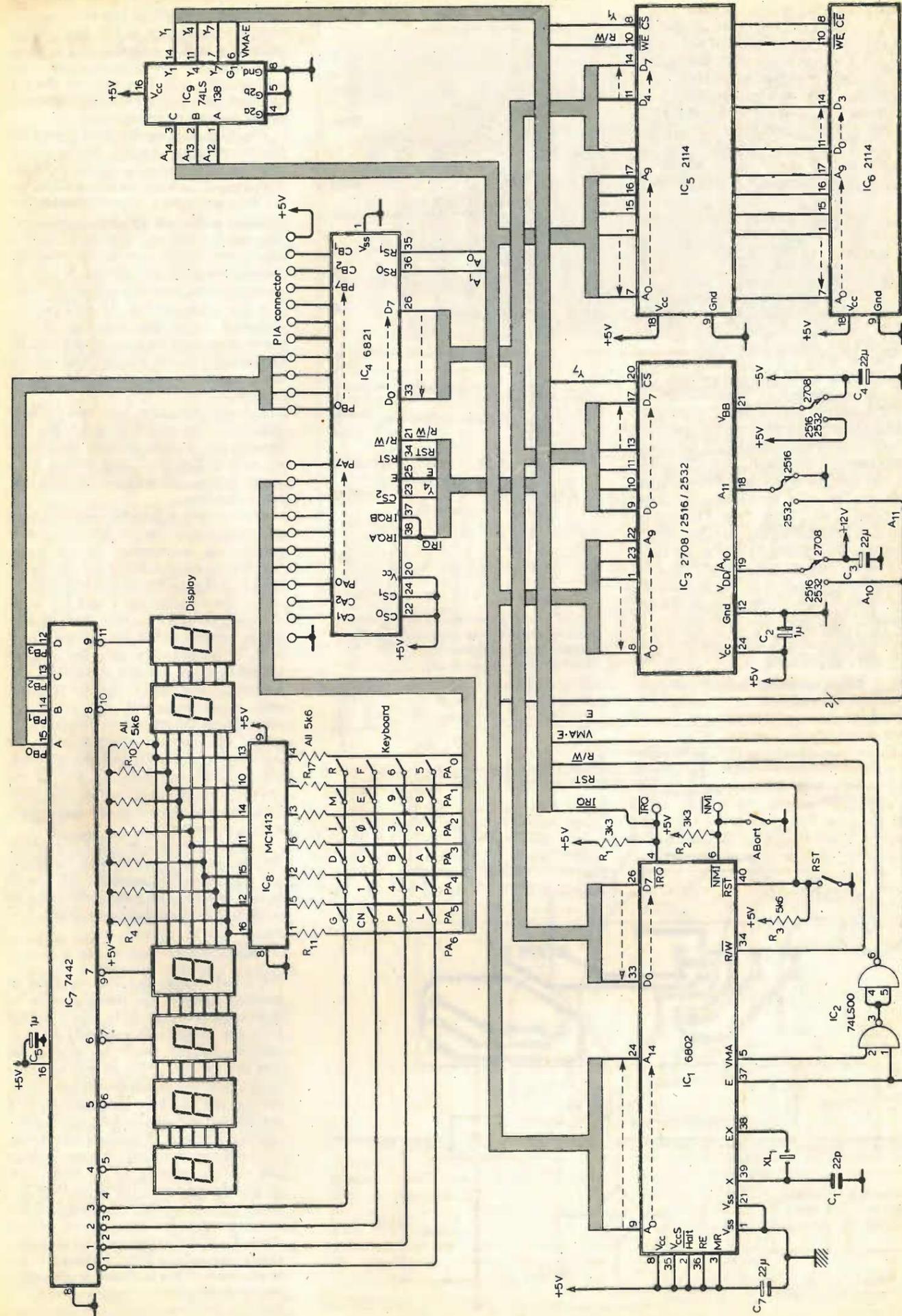

(450ns) devices will work without trouble. An input/output device, IC₄, the MC6821 peripheral interface adaptor (p.i.a.), provides two sets of 8 data lines for communicating with external circuits. One set of lines (PA) is t.t.l. compatible, and the other (PB) is m.o.s. compatible. The lines can be individually programmed as inputs or outputs and can for example, with suitable buffering, drive relays or read the states of microswitches. Also available are four control lines, two for each set of data lines, which can be used to control transfers of data between the p.i.a. and external devices. Two are inputs only, and two are inputs or outputs. The inputs can drive the \overline{IRQ} line so that the c.p.u. can service them immediately if required. All of these lines, together with ground and +5V, are available at a multiway connector.

Twelve of the p.i.a. data lines are also used to drive the display and keypad. The display comprises six common-cathode l.e.d. numerals which can show a 4-digit address and 2-digit data. The display data is not latched but multiplexed, so a constant refresh is required. This is achieved by the monitor which has a sub-routine that can be used to display data in a program. Data lines PB0-PB3 select which digit is to be refreshed, the binary numbers are decoded by IC₇ which sinks one of its outputs low. Six of the 7442 outputs are connected to the cathodes of the displays, thus the appropriate digit is selected. Segment drive information is provided by PA0-PA6. Resistors R₄ to R₁₀ turn the segments on, and the segments

Fig. 3. Single rail power supply. The p.c.b. measures 160 x 60 mm.

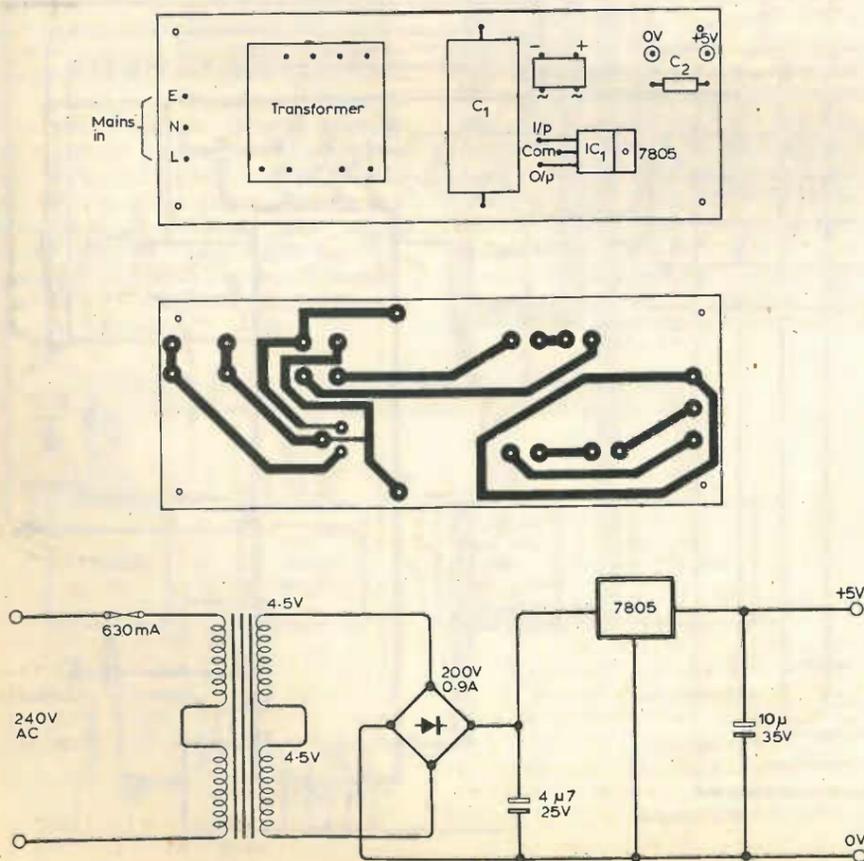


Table 1. Memory map.

| | | |
|---------------|-------------------|----------------------------------|
| e.p.r.o.m. | monitor | 7FFF |
| | user | 7C00 |
| | e.p.r.o.m. | 7800 |
| | | 7400 |
| | | 7000 |
| | p.i.a. | 4003 |
| | | 4000 |
| | program r.a.m. | 13FF |
| | | 1000 |
| c.p.u. r.a.m. | display buffer | 007F |
| | monitor workspace | 007A |
| | | 006A |
| | monitor stack | 0060 |
| | user stack | 0040 |
| | spare | 0000 |
| p.i.a. | 4000 | output/data direction register A |
| | 4001 | output/data direction register B |
| | 4002 | control register A |
| | 4003 | control register B |

are turned off by a logic 1 on the p.i.a. line which turns on one of the seven shunt transistors in IC₈. Although this arrangement is a little wasteful on power, (the consumption is highest with the display off) it provides a simple drive circuit which in this design is more important.

The p.i.a. lines are also used to read the keypad switches, but for this operation they are programmed as inputs. With no keys pressed, no loads are presented on the t.t.l. compatible inputs which are therefore pulled up by internal resistors. The keys are arranged in a matrix and IC₇ selects one of four rows in the same way that display digits are selected. If a key is pressed in that row, the appropriate PA0-PA6 input is pulled low. To read the keypad, each row is selected in turn and the inputs monitored for a low on one line. By identifying the row selected and the column pulled low, the pressed key can be determined.

Although the p.i.a. lines are available externally, they cannot be used to drive an external device while servicing the keypad or display. This is a small penalty for a simple design, and does not normally present a problem.

Construction is straightforward because all components, except for the power supply, can be mounted on one p.c.b. Sockets are recommended for the m.o.s. devices and pins for all external connections. The switches are a tight fit, but if the holes are drilled a little oversize they can be manoeuvred in place. If the circuit is to be housed in a box, the switches should be raised as much as possible. The legends on the switch caps are transfers such as Letraset. All components are mounted on the top side of the board together with four wire links to select the e.p.r.o.m. For a 2708 no links are used, for the 2516 and 2532, C₃ and C₄ are omitted and the two links from their positions inserted along with the link by the e.p.r.o.m. socket.

The power supply in Fig.3 is a simple 5V design intended for use with the single-rail e.p.r.o.m.s. The complete unit can be housed in a case, see component notes, or used on an open printed circuit board.

Testing

For initial testing, the r.a.m.s need not be inserted. Connect the power supplies to their respective pins (note that if a 2708 e.p.r.o.m. is used with separately switched supplies, the -5V should be switched on first and off last). After switch on, press Reset (RST) and a dash should light up on the far left display. This symbol is a prompt and indicates that the unit is waiting for a command. If it does not light with a correctly programmed e.p.r.o.m., check that power is reaching the i.cs. Next, with an oscilloscope connected to pin 38 of IC₁, check that the crystal is oscillating. If the crystal is alright but there is no oscillation, check C₁ and experiment with different values, particularly if the frequency is not as specified. If the oscillator is operating, test the E output of IC₁ which should be a square wave at one quarter of the crystal

frequency. This waveform will contain some ripple. If an oscilloscope is not available, a high-impedance voltmeter connected to pin 37 should read between 24 and 25V. If the fault still persists, it is likely to be a dry joint or a board fault. Because many of the tracks on the top side of the board are covered by components, it is advisable to carefully examine the board before the components are mounted.

Operation

The memory map for the unit is shown in Table 1. Note that the e.p.r.o.m. occupies 7000 - 7FFF, although the monitor program only occupies 7C00 - 7FFF. Addresses 7E63 to 7FE7 are unused because, in the original unit, routines for a paper-tape punch and load were stored there. This space can be used for load and dump routines to suit the users storage medium.

The reset button is used at switch-on, or if control of a program is lost, to run the monitor program. Sixteen hexadecimal keys enter data, and the remaining eight keys enter monitor commands. L and P are spare keys, used in the original for load and punch with the paper-tape unit, which can be used for extra facilities.

These do not need to be storage routines, but any routine the user wishes to write and include in the monitor. Locations 7DC4/5 should contain the 16-bit start address of the routine to be run on pressing the L key, and 7DCB/C the address for the P key. For testing the unit these keys can be ignored.

The memory (M) command allows a memory location to be examined and altered if required. This key is acknowledged by 17 in the far right display. A 4-digit hex address, when entered, appears on the left four digits, and the data in that location appears on the right two digits. To alter the contents of the location, enter two hex digits, which will be shifted into the data display from the right (if a mistake is made, keep entering appropriate digits until the correct data appears in the display). Next press the Increment (I) key, which stores the displayed data in the memory location and advances the display to the next memory location. If the memory contents do not need altering, press I to advance or Abort to terminate command and return to monitor start.

Register display (R) displays the contents of the various c.p.u. registers following a SWI instruction in a program. The command is automatically entered after a SWI, but may be re-entered with the R key. The condition code register contents are first displayed, the right two digits denote the register being displayed. $\overline{L} =$ condition code register, $\overline{I} =$ AccB, $\overline{7} =$ AccA, $\overline{1} =$ Index register, $\overline{2} =$ program counter, $\overline{5} =$ stack pointer position) and the left four digits show the register contents. The I key will increment through the various registers or AB will abort. After displaying SP, the unit will automatically return to monitor start.

Go (G) is used to go to a user program and A will acknowledge command. When


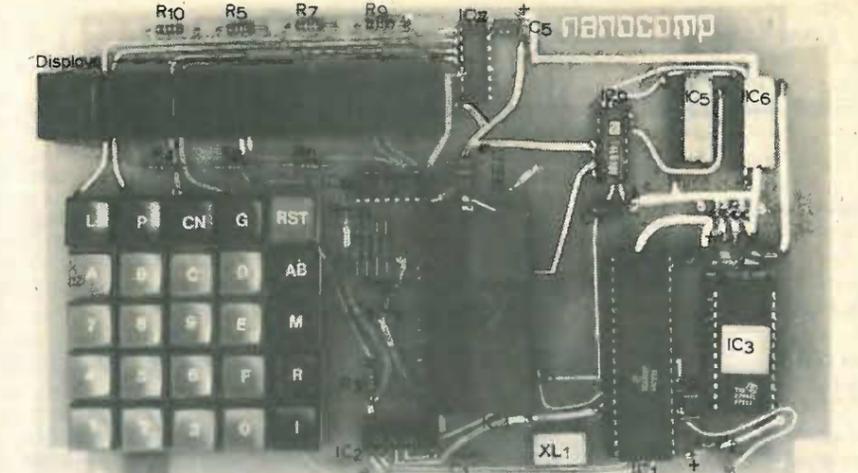


Fig. 4. Assembled printed circuit board and layout details. The board measures 200 x 120mm.

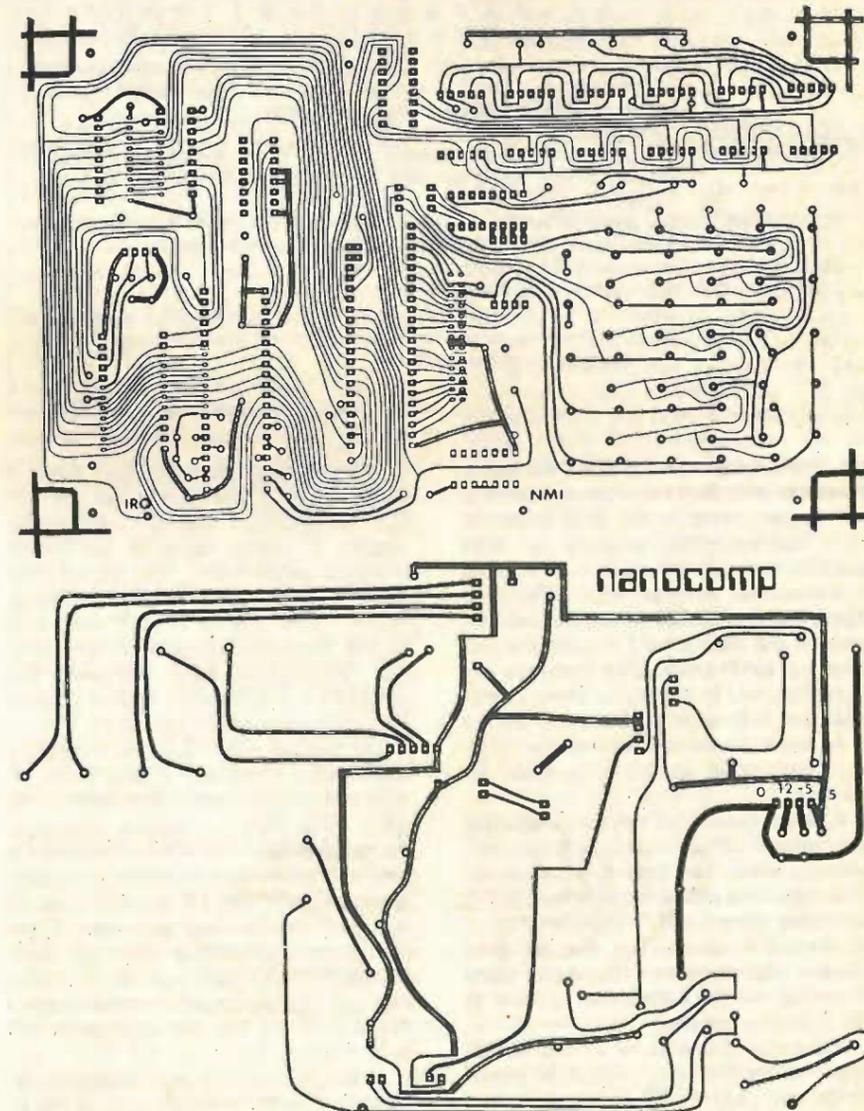

the 4-digit hex start address of the program is entered the program will run. If a program is interrupted by a SWI instruction, the continue (CN) key will run the program from the instruction following SWI. If a program is interrupted by the abort key, CN will make it continue from the interruption provided the abort key (NMI) has not been modified by the user program for a different purpose.

Abort (AB) stops the current com-


mand/program by operating the non-maskable interrupt line. The program then jumps to the location specified by memory location 0072/0073. These are set, during Reset operation, to the monitor start address but may be altered to use the NMI facility.

Programs

If one of the larger e.p.r.o.m.s is used, the programs at 7800 - 7BFF can be run immediately. Two of these are games and two

Table 2. Useful monitor subroutines.

7C7B DISPRESH Refreshes display with contents of display buffer (six locations of r.a.m., one for each display digit) which contains the seven segment information for the display. For a program to use the multiplexed display, the data must be written in locations 007A (left digit) to 007F (right digit) and DISPRESH continually accessed. Each segment of a digit is allocated to a bit in the data word, to turn a segment on set that bit to 1. The bit/segment allocation is

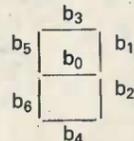

7C20 GETKEY Alternately scans keyboard and refreshes display until a key is pressed. It then waits for the key to be released, and returns with the key code in accumulator A. The codes for the keys are

0 1 2 3 4 5 6 7 8 9 A B C D E F L P C N G M R I
22 24 02 12 14 00 10 04 01 11 03 13 23 33 21 20 05 15 25 35 31 30 32

7CE7 HEXCON Converts a key code in Acc A into the hex equivalent for that key and returns with it in Acc A. If a non-hex (command) key code is entered, the routine defaults back to the monitor start.

7CE4 KEYHEX Combines GETKEY and HEXCON.

7CB5 BADDR Builds a 4-digit hex address entered from keyboard, refreshing display whilst doing so, and returns with that address in index register.

7CFF L7SEG Converts the left hex digit of a byte in Acc A to the seven segment code required by the display, and returns with it in Acc A.

7D03 R7SEG As above but for right hex digit of byte.

7D15 7TOHEX Converts a seven segment hex code in Acc A to that hex digit and returns with it in Acc A. Defaults to monitor start if code is not hex.

7CCC 7HEXIN Uses KEYHEX to accept two hex key entries, and combines the two hex digits into one byte in Acc A.

are useful programming aids. To run a program, press Reset to obtain a prompt in the display, press G and then enter the start address. The program at 7800 converts hexadecimal numbers to decimal and vice-versa. After pressing G 7800, the display will be blank. For a decimal to hex, press L and then enter a decimal number from 1 to 65535 followed by I, and the hex equivalent will be displayed. Press I again and enter L for another decimal to hex, or P for a hex to decimal conversion. After each conversion press I to prepare for another.

A tedious aspect of machine code programming is calculation of the two's complement offset for branch instructions. This task is simplified by the branch calculator program at 7A00. When the program is entered S appears on the far right display, which indicates that the program is waiting for the 4-digit start address of the branch instruction.

Enter this followed by I, and d will appear on the display to request the 4-digit destination address. When this is entered, the two's complement offset appears on the two far right displays. If two dashes appear, the branch is outside the range of a branch instruction. Press I to prepare for another calculation.

The two games programs are at 7A80 and 7930. The first is "Mastermind", and after entering, I will appear on the display. After a few seconds, required for generation of the secret code, press I and try to solve the 4-digit code using numbers 0 to

7. After entering the first 4-digit guess, a 2-digit number will appear on the two right hand displays. The first indicates the number of correct digits in the correct positions (called bulls). The second indicates the correct numbers in the wrong places (called cows). Press I and enter another number. The game finishes when four bulls have been deduced, and pressing I will indicate the number of tries. Pressing I again starts a new game.

The second game is called duckshoot and locations 0000 and 1 have to be set with a number to control the speed of the game. With 0020 as a starting point, run the program and two ducks will traverse the display. To shoot the ducks the display number (1 to 6 from left to right) must be entered when the duck is present. When hit, the duck disappears and the game finishes when no ducks are left. To terminate the demonstration programs, press AB or RST and the monitor program will be re-entered.

Although this unit was originally designed as a versatile training aid, it can be used as a desktop computer and as a software development tool. The spare e.p.r.o.m. space allows it to be used as a form of calculator or a controller. Useful programming information is available in the M6800 Microprocessor Instruction Set Summary from Motorola distributors, and an ideal book is the *6800 Programming Reference Manual* which gives details of the c.p.u. and p.i.a. devices together with a full description of the instructions. □

Component notes

Keyswitches

Grey RS 337-611
Blue RS 337-605
Red RS 337-598

Displays

FND500 or FND560

Case

RS 508-475

Connector plug

26 way insulation displacement type
RS 467-352

Software

A software listing for the Nanocomp can be obtained by sending a stamped addressed envelope to Wireless World, Room L303, Quadrant House, The Quadrant, Sutton, Surrey.

Printed circuit boards

A set of p.c.bs (1 double sided, 1 single sided) will be available for £9.00 inclusive of v.a.t and UK postage from M. R. Sigin, 23 Keyes Road, London N.W.2.



The Author

Bob Coates studied electronics at the Rolls-Royce Aero Engine Division where he gained a HND. In 1974 he joined a research & development establishment and is currently working on microprocessor systems design for industrial control and data acquisition. Apart from electronics, Bob's interests include amateur radio (G4DIH).

Component kit

We understand that Technomatic, 17 Burnley Road, London N.W.10, will be offering a kit of components including a programmed r.o.m. for the Nanocomp.

WORLD OF AMATEUR RADIO

A direct-conversion breakthrough

About two years ago, the Plessey Company demonstrated a novel "on-channel" form of low-power v.h.f. "repeater", developed primarily for military tactical radio networks. This attracted considerable interest among amateurs as offering a system which could extend the range of simple hand-held transceivers not equipped for 600 kHz off-set operation through the conventional amateur repeaters, and also offering the possibility of single-channel duplex operation on narrow-band-frequency-modulation if two such units were used. At the time the company, for reasons of commercial security, were unwilling to disclose even the principle on which this system worked.

At the I.E.E. recently, Chris Richardson, the inventor, revealed that the key feature lies in the use of a direct-conversion receiver in which the transmitted signal acts also as the local oscillator for the two-phase balanced mixer used to recover the signals in a form suitable for n.b.f.m. demodulation, enabling a deep rejection notch to accurately track the instantaneous outgoing frequency. Direct-conversion ("zero i.f.") receivers have been popularized and used by many amateurs during the past decade, and it is clear that the technique is being taken increasingly seriously by professional designers. Work at STL, Harlow, by Ian Vance, G3WMS, has shown that it is possible virtually to design a mobile v.h.f. radio on a single microchip by using direct-conversion techniques (*The Radio & Electronic Engineer*, April 1980). This design again uses two-phase (quadrature) techniques to facilitate demodulation of n.b.f.m. signals and allows "a measure of integration previously unobtainable in radio equipments", though further development is envisaged.

Here and there

Extensive tropospheric ducting during early October resulted in many contacts between amateurs in the south of England and Eastern Europe on the 144, 432 and 1296 MHz bands. The first-ever contacts between the U.K. and Czechoslovakia by means of 2300 MHz (13cm) ducting were made by several East Coast stations, including G4BYV and G3LQR.

The weekly "World Radio Club" programmes for short-wave listeners, radio amateurs and anyone interested in the radio sciences does not appear in the programme schedules of the BBC World Service for January 1981, though it is still not clear whether this will prove to be a temporary or permanent closure of the "club". Started in 1967, this programme has run

without breaks for more than 700 editions and more than 40,000 listeners in all parts of the world have written in to register themselves as members. Producers have included John Pitman, Joy Boatman and currently Reg Kennedy, while Henry Hatch, G2CBB, a retired BBC engineer, has been taking part in the programme since the start.

Richard Thurlow, G3WW, is currently installing in his Robot 400 slow-scan television equipment additional memory boards to convert his equipment into the form of colour s.s.t.v. developed by Don Miller, W9NTP. He reports that A.H.G. Waton, G3GGJ (19 New Road, Barton, Cambridge CB3 7AY, tel. Comberton (0220-26) 2129) is undertaking to supply amateurs on a non-profit basis with commercially printed boards, complete with 240 plated-through links and produced from the original W9NTP artwork, together with associated circuit data relating to the W9NTP and ZL1BLV designs.

Science Museum GB8SM

The Science Museum amateur radio station, GB2SM, has recently been using the callsign GB8SM to mark its 25th anniversary. The station, since 1955, has progressed from a simple table-top layout into one of the most elaborate amateur stations in regular operation anywhere in the world. The present equipment includes Collins, Racal, Eddystone, "KW" (Decca) and Trio units arranged to permit three separate operating positions to be manned simultaneously. Staff operator since 1955 has been Geoff Voller, G3JUL, assisted by volunteers. Over the years the station has had thousands of contacts world-wide and has been visited by many of the millions who come to the Science Museum.

RSGB's record year

The annual report of the Radio Society of Great Britain (to June 30, 1980) shows that the membership has reached an all-time high of 25,658, while total income of the Society from all sources for the first time exceeds £0.5 million, resulting in a surplus for the year (after tax) of over £24,000. The 1979 World Administrative Radio Conference is seen as "successful from an amateur point of view". The RSGB also "welcomes" the Home Office "Open Channel" proposals as "being in line with its own view" and feels that a 928 MHz frequency "should satisfy the large majority of users, while at the same time minimizing most potential interference problems."

Though the report does not mention it, 1981 also promises to provide a special footnote in the Society's history: wife of

the 1981 President, Mrs E. O'Brien, holds her own amateur callsign, G3WIO. Basil O'Brien, G2AMV is an amateur enthusiast of many years standing. He comes from outside the "electronics" field, being a retired bank manager.

An additional GB2RS news bulletin is now being transmitted on Sunday mornings at 9 a.m. local time on 7047.5 kHz from stations in Northern Ireland. These amplitude-modulated signals can be received on conventional "all-band" domestic receivers in many parts of the U.K. and supplement the 11 a.m. 7 MHz a.m transmissions from the West Midlands.

In brief

Doug Finlay, D.F.C., G3BZG, a former R.S.G.B. president (1957) and later (1970-74) general manager of the society died during September ... About 50 Dutch amateurs are now licensed to use c.w. between 1720 to 1740 kHz and 1830 to 1850 kHz with power limited to 10 watts d.c. input The A.R.R.L. are preparing a proposal to be submitted to F.C.C. advocating an amateur band at about 900 MHz. The League have recommended that the 10 MHz band, due to be released when the WARC 1979 Radio Regulations become established, should be used only for c.w./r.t.t.y. operation with a maximum power of 250 watts, but are advocating extra phone segments above 14,150 kHz and a new phone segment from 7075 to 7100 kHz... The amateur radio club of London Weekend Television now holds the callsign G4LWT ... Class B licences in the sequence G6AAA etc are due to be issued soon The F.C.C. have "deregulated" much of the American 50 MHz amateur band which extends from 50 to 50.4 MHz, retaining as compulsory band-planning only the segment 50 to 50.1 MHz allocated to c.w. and confining repeaters to the segment above 52 MHz.... A new proposal has been submitted to the R.S.G.B. Repeater Working Group for an experimental 145 MHz repeater capable of handling s.s.b. signals, initially to be located at the University of Sheffield. A previous proposal for a linear repeater ran into considerable opposition and was not implemented ... The Lincoln Short-Wave Club has now been allotted the callsign G5FZ, the callsign originally issued to the Lincoln Wireless Society in 1922 ... The most northerly beacon is a new 28.225 MHz station VE8AA located in the Canadian North West Territories on an island in Lake Contwoyto at latitude 65.5° North, longitude 102° West. It has been heard in the U.K. and should provide a valuable guide to propagation studies.

PAT HAWKER, G3VA

The first thousand transmitters

Britain's u.h.f. colour television reaches 98.7% coverage

by Edward Trickett B.Sc., Ph.D
BBC Engineering Information Department

On the seventh of November, 1980, Mike Neville, star of 'Look North', opened a small television transmitting station at Hedleyhope in the Deerness Valley, County Durham. The Hedleyhope relay contains the one thousandth u.h.f. television transmitter to be brought into service by the BBC.

In less than 17 years, 51 main stations and more than 450 relay stations have come into service. With the exception of two stations which do not carry BBC2 (Sandale provides BBC1 Scotland for Dumfries and Galloway, and Wrexham-Rhos offers BBC Cymru/Wales) all the stations have transmitters for BBC2 and BBC1 (or BBC Cymru/Wales).

Hedleyhope is a long way from Crystal Palace, where the United Kingdom's u.h.f. television service began in 1964, carrying the brand-new service, BBC2. Like its predecessors (the original BBC television service in 1936 and ITV in 1955) BBC2 was pioneering a new broadcasting band of higher frequency than any used before in the UK. But it was also using a new line standard destined to be the vehicle for colour transmissions.

The BBC's u.h.f. transmitter network is a major engineering achievement which stretches the length and breadth of the country, from Baltasound to St Helier, from Dover to Fermanagh and from the Scillies to Peterhead. The problem compared with v.h.f. is that more than 500 stations have been needed to reach the present 98.7 per cent coverage of the 55 million people in the UK. By comparison, the BBC's 405-line v.h.f. network needed only 110 stations to give 99 per cent coverage.

The u.h.f. network represents a great deal of co-operation between BBC and IBA engineers. The service has been planned using the computer at the BBC's research department in Kingswood, Surrey, where the transmitting parameters of all the u.h.f. stations in the UK plus those of the main stations in nearby countries in Europe, are held in memory. The Stockholm plan of 1961 allocated all main station channels and maximum powers, but the detailed planning of the relays is done with the computer. The proposed parameters are fed in to check for possible interference. Even though u.h.f. transmissions do not normally propagate over great distances, some 500 stations, each using 4 channels out of a possible 44, mean that

finding useful channels for new relays is getting difficult.



Where possible, existing v.h.f. sites doubled as u.h.f. transmitting stations although more main stations were needed and have been built, with the BBC responsible for site acquisition of half the sites and the IBA responsible for the other half. At each station one organisation is the tenant of the other. The landlord is responsible for the building, tower or mast, aerials and transmitters for its own services: the tenant organisation looks after its own transmitters.

The relay network also used existing

v.h.f. sites where possible but many more sites have been obtained on the same landlord/tenant relationship. The obstruction caused by terrain is much greater at u.h.f. than at v.h.f. and the relay stations fill in the gaps left by the main stations. The flat lands of eastern England need very few relays but the heavily-populated valleys of South Wales and industrial Yorkshire and Lancashire need very many. On the whole the relays serving larger populations have been built, and the number of people served by each new relay has fallen from half-a-million (Sheffield) down to between 500 and 1000 for most



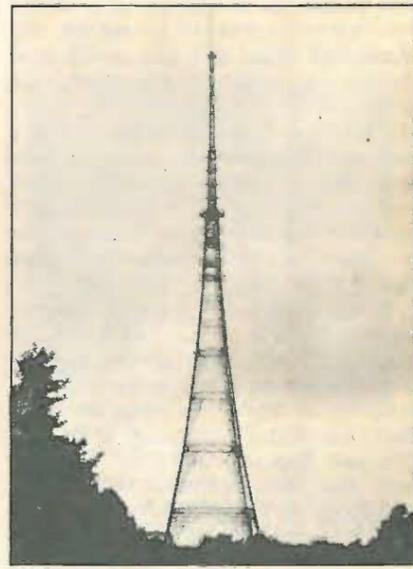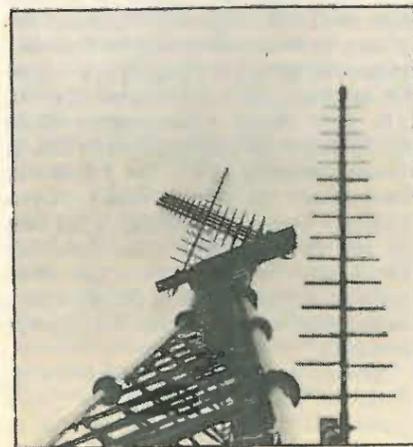Hedleyhope, the BBC's 500th u.h.f. station, with modular, 3-legged tower, log-periodic aerials and prefabricated building, all of BBC design.



The Crystal Palace tower where the country's u.h.f. services began in 1964. The u.h.f. aerials are in the white cylinder at the top.

Looking up at the mast at Hedleyhope. Log-periodic aerials are visible. That on the right is the receiving aerial. The transmitting aerial puts most power in the direction of the stack of four with a little at right angles to serve an odd few houses in that direction. Note the simple tower construction.

current stations. Hedleyhope serves 1000 people.

Deficiencies in coverage are measured during detailed surveys by the service planning section of the research department. Possible transmitting sites are investigated using the computer and ground profiles drawn from ordnance survey maps. Site tests are carried out with mobile test transmitters and aerials and to check for good received signals. These methods ensure that optimum coverage can be achieved in any area where deficiencies exist.

At this stage, either the BBC's site acquisition section or its IBA counterpart takes over. There has to be main power available within a convenient distance, and reasonable access. Then the landlord has to purchase the freehold or negotiate a lease on the site and obtain planning permission and air navigation obstruction clearance. In some areas there can be objections to even a small pole on environmental grounds but the broadcasters are at pains to erect the most discrete structure consistent with performing the necessary service. They have no power of compulsory purchase, and planning consent has to be obtained in the usual way.



Tötley Rise, Sheffield. One of the BBC's tiny, unobtrusive installations with wooden pole, log-periodic aerials and prefabricated building.

Providing the stations

The BBC's transmitter capital projects and architectural and civil engineering departments are responsible for turning the research department's specification for each station into reality. The specification includes transmitted power, channels, aerial radiation patterns and height. The most appropriate equipment, aerial support structure and building are all carefully selected to fulfil these requirements.

Most components are ordered in quantity and parts are allocated to each station while it awaits its turn to be built. At present the broadcasters are opening 70 new stations each year and it is vital to

maintain a steady flow of materials to meet this target.

On many small BBC sites the concrete tower base (which includes the building base) is laid by BBC staff. A BBC-designed pre-fabricated building is equipped at the Brookmans Park workshops. Building, tower components and aerials are taken by lorry to the site, where the rigging team puts the pieces together. The aerial engineer pays a brief visit to check that the transmitting aerial (which he assembled at the workshops) is a good impedance match when installed with its feeders. He checks the received signal and installs the combining and splitting filters. The relay engineer installs the transposers to complete the installation. The tenant's representatives install their transposer(s) and finally the manager of the transmitter maintenance team accepts the BBC equipment on behalf of the transmitter group, who will operate it. The station is now ready for switch-on and appropriate publicity is arranged through local papers, the 'Service Information' programme and the trade, a week ahead of the opening date. An engineer from the BBC's engineering information department visits the service area with a survey vehicle in the first week or two of

operation to check the performance of the station. He advises both dealers and members of the public on the spot about reception conditions as he finds them.

So far only the planning and provision of the stations have been considered, but the expansion of the networks has made huge demands on the ingenuity of our engineers. At several stages in the programme when there was no suitable commercial device, the equipment has been designed within the BBC. The Hedleyhope relay, for instance, has aerials, tower, transposers, amplifiers and channel-selection and combining equipment all of BBC design.

The programme has been a continuing story of smaller and smaller stations serving fewer and fewer people. Inevitably the cost per person served increased and the BBC has made considerable efforts to reduce complexity and expense. The Hedleyhope station has cost some £50 per viewer whereas a high-power station for a densely-populated area would cost 30 or 40p.

Transmitters

Crystal Palace was a test-bed for u.h.f. equipment for several years before it went into programme service in 1964 and the

The main stations in the BBC's u.h.f. transmitter network.



BBC also benefited from the experience of the West Germans who had already begun a u.h.f. service. We aimed to make all u.h.f. stations unattended, requiring maintenance rather than operational staff. So klystrons were used for the main station power amplifiers because of their reliability and long life. Recently the amplifier drives at these stations have been replaced and klystron amplifier efficiency has been improved by 50 per cent although we are still experimenting to obtain even higher efficiencies. Initially, parallel transmitters were used, with separate sound and vision amplifiers (i.e. four amplifiers) so that one half of the system could fail or be maintained whilst the other continued in service. Later, we used one klystron each for vision and sound with a 'cut-back' condition whereby one could carry both signals with a loss of 7dB in power output.

Transposers at the early relays used valves with klystron or travelling-wave-tube final amplifiers. Solid-state transposers came in early and were used initially with output valves or travelling-wave tubes but the most powerful amplifiers using solid-state techniques were 50W units. For most of the smaller stations, 2W and the occasional 10W amplifiers have been adequate. For that, out of the BBC designs department was rolled the 'Blue Streak' — not a rocket as the name suggests, but a transposer/amplifier unit with a very good specification and designed for ease of maintenance. Interconnections are the most likely source of problems in r.f. equipment, so all of the Blue Streak's interconnecting leads are visible and replaceable from the front.

Although this makes it an ugly duckling, the equipment has proved extremely reliable in service. For the future, the de-



Shatton Edge. The 'slimline' tower was originally developed for use in the Peak District National Park. The 'trough' receiving aeriels are just above the special stone building. The cantilevered cylinder contains a 'cardioid' transmitting aerial.

signs department has developed a new transposer, already nicknamed 'Silver Streak' which out-performs its predecessor at lower cost. In a very small space, four 2-watt units can be installed side-by-side and only one spare is necessary because the operating frequencies are determined in a separate unit.

Aerials

The most obvious feature of a u.h.f. main station is the white glass-reinforced plastic radome which appears as a cigarette-like cantilever on the masts and towers. The transmitting aeriels consist mostly of panels, normally four wavelengths high, arranged in stacks on three or four sides of the central spine. The aeriels are in two halves, fed by independent feeders and phasing is arranged to give an overall downward tilt to the main beam. At most stations one aerial carries all four services but there are a few where one is used for the BBC and one for the IBA services.


Most early relay stations used cardioid-pattern transmitting aeriels built to a BBC specification. Enclosed in a structural gap cylinder, they consisted of a pole with dipoles on one side. Later aerial systems were built using components designed by a team at the BBC's research department. The trough aerial (resembling a pig-trough) was used occasionally for transmitting and more often for receiving. The panel aerial, essentially two slots etched into a printed circuit board and panel and protected by a plastic cover, became the common building block of the Phase 1 stations serving populations down to 1000. The log-periodic aerial has since taken over and is the common component for

both reception and transmission at Phase II relays serving groups of people down to 500.

The early heavy-duty towers were not acceptable to the environment conscious planners for the Peak District National Park. A new, more elegant, tower was commissioned. Named the 'slimline', it appeared in the Peak Park and in every other part of the country from St Just in Cornwall to Fodderty in Easter Ross. Even this was too big for the smaller stations which use either simple poles or a light-weight, modular tower designed by the BBC's architectural and civil engineering department at a fifth of its predecessor's price. The tower was designed to be put up by the BBC teams who previously had only erected the aerial systems after contractors had erected the actual tower.

Distributing the signals

A number of main transmitters receive their feed by Post Office (British Telecom) link. This applies to at least one station in each region as there are regional opt-outs on BBC1. The remaining main stations take their picture by off-air reception using BBC-designed rebroadcast-quality receivers. Relay stations almost all use transposers to avoid the need for demodulation to baseband. In a number of cases the Post Office was unable to provide the necessary links and the BBC planned its own link systems to do the job. The three most obvious examples are in Scotland where the feeds to the Inner and Outer Hebrides and to the Shetland Islands are all carried by microwave links installed by the broadcasters. The relay at Torosay (Mull) receives its signal by link from the relay station at South Knapdale, above Loch Fyne in Argyllshire. The main station at Eitshal (Lewis) is fed by a 6-hop link from Rosemarkie on the Black Isle near Inverness. This network, which straddles northern Scotland, was planned and installed by staff in the communications and links unit of the BBC's transmit-

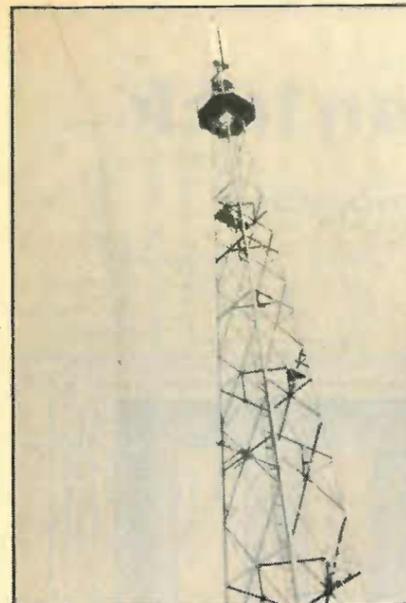

St Just. Another 'slimline' tower but with 'panel' transmitting aeriels.

ter capital projects department. The country that the route crosses is so rugged that two sites without electrical power are used for passive deflectors. The chain of links

carries the v.h.f. radio, as well as the television channels, to the Melvaig transmitter on the Wester Ross coast. The feasibility of a link to Shetland via Fair Isle was investigated by the BBC and the eventual installation was the responsibility of IBA staff. Both Torosay and Bressay (Shetland) are classed as relays but actually use klystron amplifiers for the BBC services and, of course, cannot employ transposers.

The way ahead

The current phase of the relay programme is taking in stations for as few as 500 people and last May the Home Secretary authorised a third phase for populations as low as 200, where practicable. The broadcasters are now looking towards even simpler and cheaper equipment, 'Silver Streak' being the first of this.

The Home Secretary has also given permission for people in communities of less than 200 to install their own cable systems or transmitters but, of necessity in collaboration with the broadcasters. Already more than 60 applications have been received by the BBC.

The 405-line transmissions in Bands I and III are to be phased out between the beginning of 1982 and the end of 1986. Not all of Band I will be available for

The author

Dr Trickett was educated at King Edward VII School Sheffield and University College Durham, gaining his doctorate under a BBC research scholarship. He began working for the Corporation in 1968. After a short time in the research department he joined the transmitter capital projects department. Three years ago he joined the engineering information department and is currently employed as a publicity engineer.

broadcasting after that, but the remainder and Band III are under consideration for 625-line area television or another near-national network.

So it would seem that we have exploited all the possibilities for terrestrial television broadcasting in the United Kingdom. It remains now to use the next group of broadcasting bands with satellites as discussed by my colleague Dr G. J. Phillips in his articles in this journal of October and November 1980.

I am indebted to the BBC's Director of Engineering for permission to publish this article. □

Smaller television cameras

There is a continuing pressure from broadcasters and industrial/commercial users to reduce the size and weight of television cameras. The broadcasters need them small for ENG (electronic news gathering) while the industrial users need them small to mount on machinery or to be unobtrusive for surveillance purposes. Soon, home video will be adding to this pressure (see News, December). Two recent responses from the electronics industry have been the c.c.d. (charge coupled device) image sensor and the single-gun photoconductive tube for producing colour pictures. New examples of these were presented at the International Broadcasting Convention, Brighton, in September, and also by Howard Steele, managing director of Sony Broadcast, in his October inaugural address as chairman of the IEE's Electronics Division.

The c.c.d. image sensor is claimed to be "the first commercially available sensor with the full 625-line tv capability." Developed by the GEC Hirst Research Centre, Wembley, it takes the form of a 14mm x 10mm polycrystalline silicon chip mounted in a 30-pin package (type number MA357). The incident light image is converted from a pattern of photons to a corresponding pattern of electric charge by an 8.5mm x 6.4mm image section on the chip, which contains 864 horizontal electrodes and 385 vertical charge transfer columns. This charge pattern is transferred, by a three-phase pulsing applied to the horizontal electrodes, line by line downwards into a storage section on the chip. The charge collection plus transfer time is equal to one field period (20ms in the 625-line standard) and the transfer takes place in the blanking interval.

At the bottom of the storage section each line is transferred in parallel into a line read-out section, from which it is read out sequentially in the time of an active tv line, 52µs. While each line is being read out a second pattern of charge is being collected in the image section. Although charge is collected from the whole image area in each field, the three-phase pulsing system causes the centres of charge collection to be shifted up and down between fields to give in effect a 2:1 interlace in the vertical direction. Thus the c.c.d. device is compatible with the 625-line tv standard, where 575 lines are displayed and the remaining 50 lines are used for field blanking periods.

Picture quality from the GEC device is not yet good enough for television broadcasting, but the present performance is claimed to be adequate for "a wide variety of industrial, professional and military applications."

The new single-gun colour tube, intended for ENG cameras and developed by the Sony Corporation, is only 3/8 inch in diameter. It is called the Trinicon because of its similarity to the well-known vertical-stripe Trinitron cathode-ray tv display tube made by the same company. The light image, in fact, is focused onto a colour filter array consisting of red, green and blue vertical stripes, each only 9 microns wide, which are integral with the face-plate of the tube. An unusual feature of the tube is the colour coding principle, which uses a phase reference carrier onto which the red, green and blue signals are modulated. This phase reference carrier is generated within the tube by the electron beam scanning an inter-digital electrode structure (rather like two combs) be-

hind the target, and is subsequently used in synchronous demodulators to obtain two quadrature modulated colour-difference signals.

In this system the incident light image is modulated by the striped colour filters to produce a three-channel pulse amplitude modulated signal containing the three colour components E_R , E_G and E_B . The base band and first harmonics are expressed as $E' = a_0 (E_R + E_G + E_B) + (E_R - (E_G + E_B)/2) a_1 \cos(\omega t + \phi) + \sqrt{3/2} (E_G - E_B) a_1 \cos(\omega t + \phi - \pi/2)$.

In this equation the first term is the luminance signal while the remaining two are the quadrature modulated colour-difference signals which are subsequently recovered in the synchronous demodulators.

The inter-digital electrode structure which produces the phase reference carrier is related to the spatial pattern of the red, green, blue colour filter stripes in that a pair of the interleaved "fingers" or digits occupies the same horizontal distance (27 µm) as one red-green-blue triad of filter stripes (each 9 µm). A small offset voltage is applied between the two comb-shaped elements forming this structure and is alternated at the television line rate, so producing the phase reference carrier onto which the red, green and blue signals are modulated. Outside the tube these phase-reference and colour-signal components are separated by a correlation system.

An ENG colour camera using this single new tube weighs 200g and occupies a volume of 80cc compared with the 1200g and 600cc of a corresponding three-tube ENG camera. The power consumption of the tube supplies (1.5W) is, as might be expected, about a third of the three-tube camera consumption.



Inside Hedleyhope. Gordon Bowhay, of the BBC's transmitter capital projects department, is putting the finishing touches to his 'Blue Streak' installation. The instruments at bottom left are test gear, not station equipment.

Electronic combination lock

Mains independent, with four digit code via keyboard

by Jan Hruska B.A.

This article describes how a key-operated mechanical lock can be converted to an electronic combination lock by the addition of a commercially available solenoid operated lock, a keyboard and some c.m.o.s. logic. In design, this lock is similar to the one published in the March 1980 issue of W.W. (Ref. 1.), but it has the following advantages: it is totally independent of the mains; it uses fewer integrated circuits. Although the author specifies a solenoid lock for use with the electronic system, the keyboard and accompanying circuit can be used for various applications.

The system consists of three parts, a keyboard, a processing unit with batteries and a solenoid operated lock. When the correct 4-digit code is entered via the keyboard outside the protected area the solenoid of the electric lock is activated for approximately two seconds by the timer section of the processing unit. The 4-digit code required for activation is predetermined in binary form by the settings on two 16 pin d.i.l. switches which may be mounted on the same p.c.b. as the rest of the logic and timing circuit. Binary code setting provides security against easy reading by a layman.

If a mortise type solenoid lock is used in conjunction with a standard Yale type lock, the door can be opened either by using a key or the keyboard code. The processing unit inside the protected area requires connection to the keyboard outside via an eight core cable and connection to the solenoid via a twin core cable. A 4x4 matrix encoded hexadecimal keyboard is used. Vandalizing of the keyboard or cutting of the wires leading to it do not cause activation of the lock.

The processing unit contains the logic necessary to identify the correct sequence of the four digits and operate the lock, the switches for setting the code and the 6V power source. A total standby current of 200µA is required for the c.m.o.s. logic i.cs and a short-burst current of 700mA while the solenoid is being activated. Since the lock activation time of two seconds is small compared with the standby time, four HP2 type batteries connected together will give operation for up to one year. If required, the processing circuit can be made up on a

piece of Veroboard measuring 107x54mm and housed, along with the batteries, in a plastic box measuring about 110x190mm.

One type of solenoid operated lock which can be used in the system is the 11K model from Baron Security Group (Ref. 2.) which costs around £13.90 plus v.a.t. This lock was used in the prototype and although the manufacturers specify 8V a.c. as the operating voltage, it worked reliably on 6V d.c.

System operation

The 4 digits are entered sequentially via the 4x4 matrix hexadecimal keyboard as shown in Fig. 1. Each digit is debounced and encoded by a 74C922 encoder. The resulting binary code is then fed to the four-stage shift registers for which two 4015 dual shift registers are used. Comparison between the four digits in the shift registers and the code set in binary in the 16 d.i.l. switches is then carried out by the four 4-bit comparators. If both sets of 16 bits correspond the A=B outputs of the cascaded 4063 comparators will go "high" and trigger the c.m.o.s. 555 timer which will in turn energize the lock through the buffer circuit for about two seconds.

When choosing a code, it is advisable not to use four identical digits as, due to the shift register logic, an intruder would only have to enter one correct digit to activate the lock if a correct code had been used previously. The system described has been in operation in the Medical Engineering Laboratory, Oxford, for more than six months and everybody found it convenient not having to fuss with keys in order to gain access to a busy room with restricted access.

References:

1. Alan Oakley, *Wireless World*, March 1980, p.65-67, "Electronic combination lock".
2. "Remote Control Electric Locking Systems" leaflet, Baron Security Group, 34/35 Dean Street, London W1V 5AP, Tel. 01-439 4536.

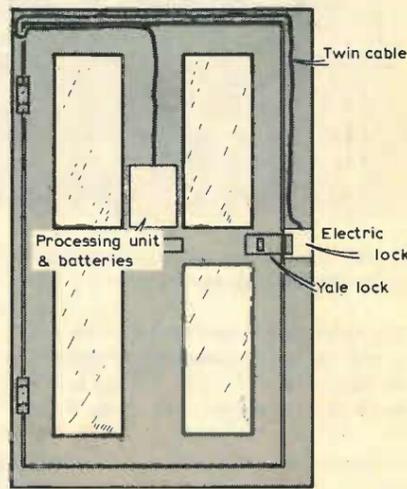


Fig. 1. Complete circuit diagram. The settings of the d.i.l. switches have been drawn so that a code of 3, 6, 9, 7 would be required to activate the solenoid. ▶

Components list

- 1 4x4 matrix encoded hexadecimal keyboard
- 1 74C922 keyboard encoder (c.m.o.s.)
- 2 4015 dual shift register
- 4 4063, 4-bit comparator
- 1 4011 quad 2-input NAND gate
- 1 555 c.m.o.s. timer
- 2 d.i.l. switch, 8-pole single-throw
- 1 ZTX300 or similar n-p-n transistor
- 1 TIP32A or similar p-n-p power transistor
- 1 1A diode
- 1 15Ω resistor
- 2 10kΩ "
- 16 1.5MΩ "
- 1 1nF capacitor
- 2 10nF "
- 1 100nF "
- 1 330nF "
- 1 4.7µF tantalum capacitor
- 1 47µF "

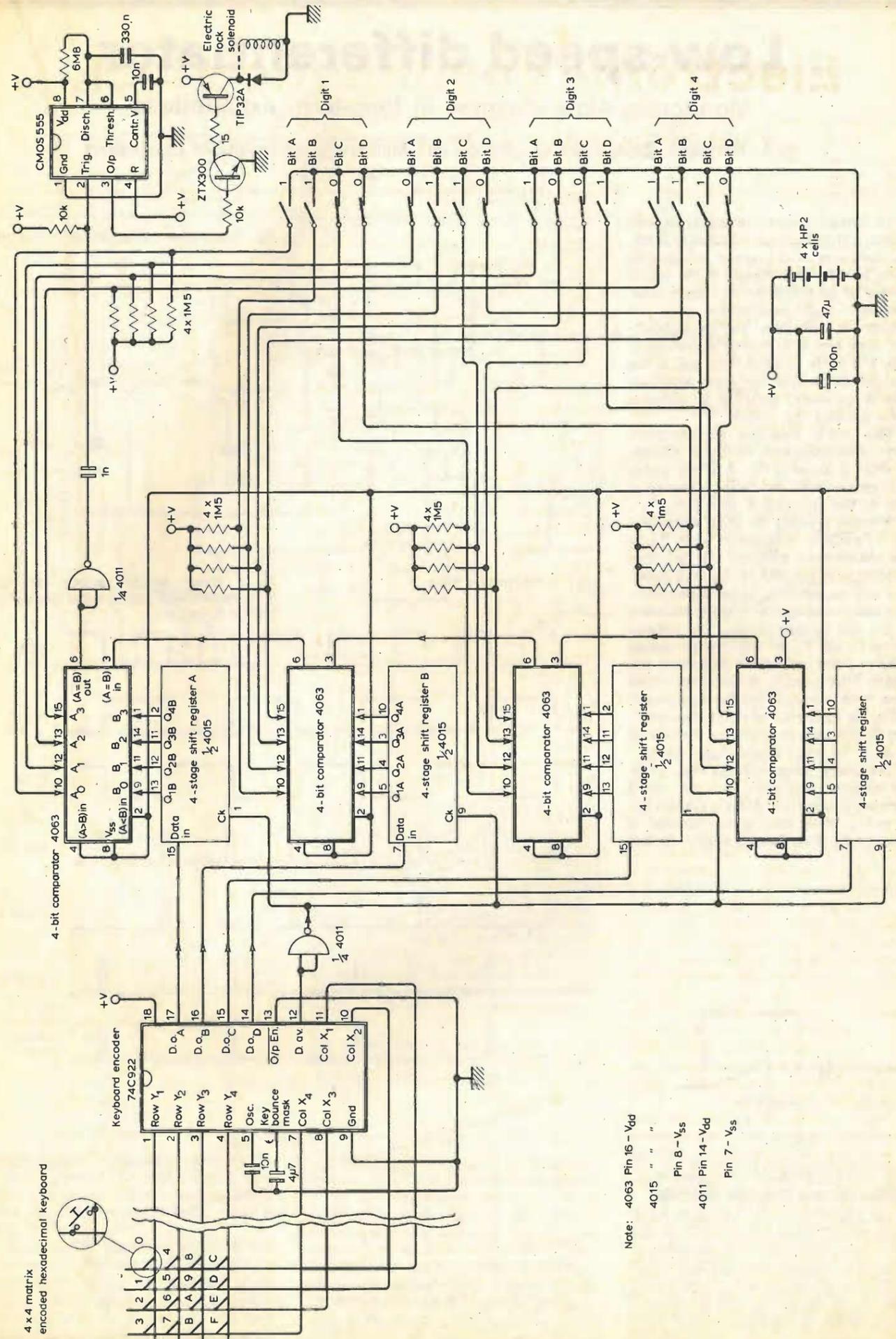


Fig. 2. If the Yale and solenoid locks are mounted as shown here, the door can be opened either by using the key or the combination-lock keyboard.

Note: 4063 Pin 16 - V_{dd}
 4015 " " "
 Pin 6 - V_{ss}
 4011 Pin 14 - V_{dd}
 Pin 7 - V_{ss}

Low-speed differentiator

Monitoring slow changes in long-term experiments

by L. Hayward, Department of Geology and Mineralogy, University of Queensland

With certain electro-chemical experiments, it often becomes desirable to obtain the derivative of the output voltage/time curve in order that changes in the rate of change of amplitude become more easily observed. Such experiments often last minutes or even days, and consequently the classic type of RC differentiator seen in Fig. 1 is likely to be of little use, as the changes are so slow that great amplification is necessary, resulting in excessive noise masking the output.

This article describes an alternative form of differentiator, the block diagram of which is shown in Fig. 2. When read in conjunction with the timing diagram of Fig. 3, the operation is as follows.

A buffer presents the input signal to a pair of c.m.o.s. transmission gates. These are alternatively switched on for short periods, as determined by the clock generator and the sampling period monostable. The sampled voltages at t_1 and t_2 are stored in C_1 and C_2 respectively. The voltages across C_1 and C_2 are buffered by voltage followers, and applied to a differential amplifier. After t_1 and t_2 , the resultant output from the differential amplifier is proportional to the difference of the charges on C_1 and C_2 that were set up during the interval t_1 to t_2 . In other words $V_{(out)} = \Delta v / \Delta t$.

The timing diagram shows that, whilst the samples t_1 to t_2 and t_3 to t_4 , etc., are of the same polarity, i.e. A-B, the periods t_2 to t_3 and t_4 to t_5 , etc., give a reversal of polarity, i.e. B-A. Consequently, a further

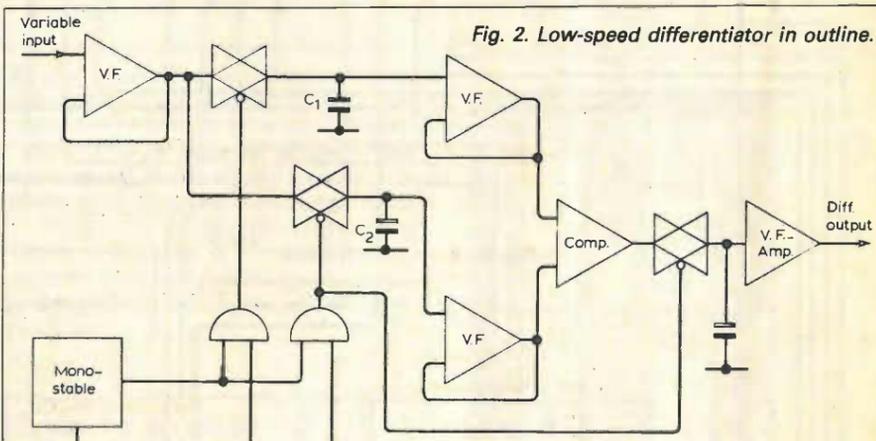


Fig. 2. Low-speed differentiator in outline.

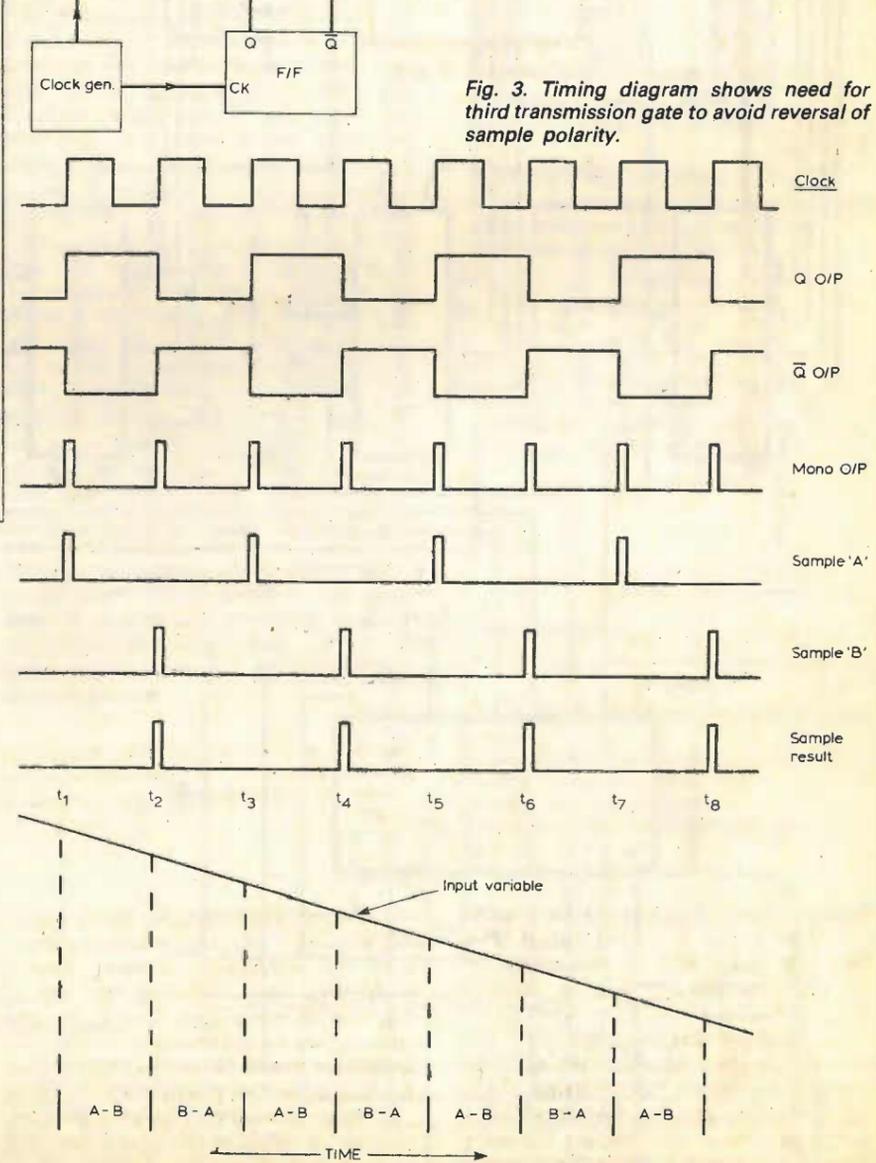


Fig. 3. Timing diagram shows need for third transmission gate to avoid reversal of sample polarity.

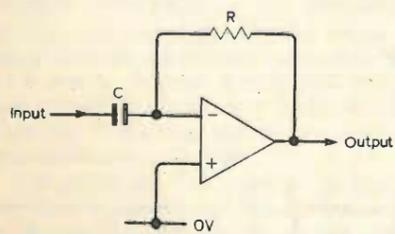


Fig. 1. Ordinary type of RC differentiator - useless for very long time intervals.

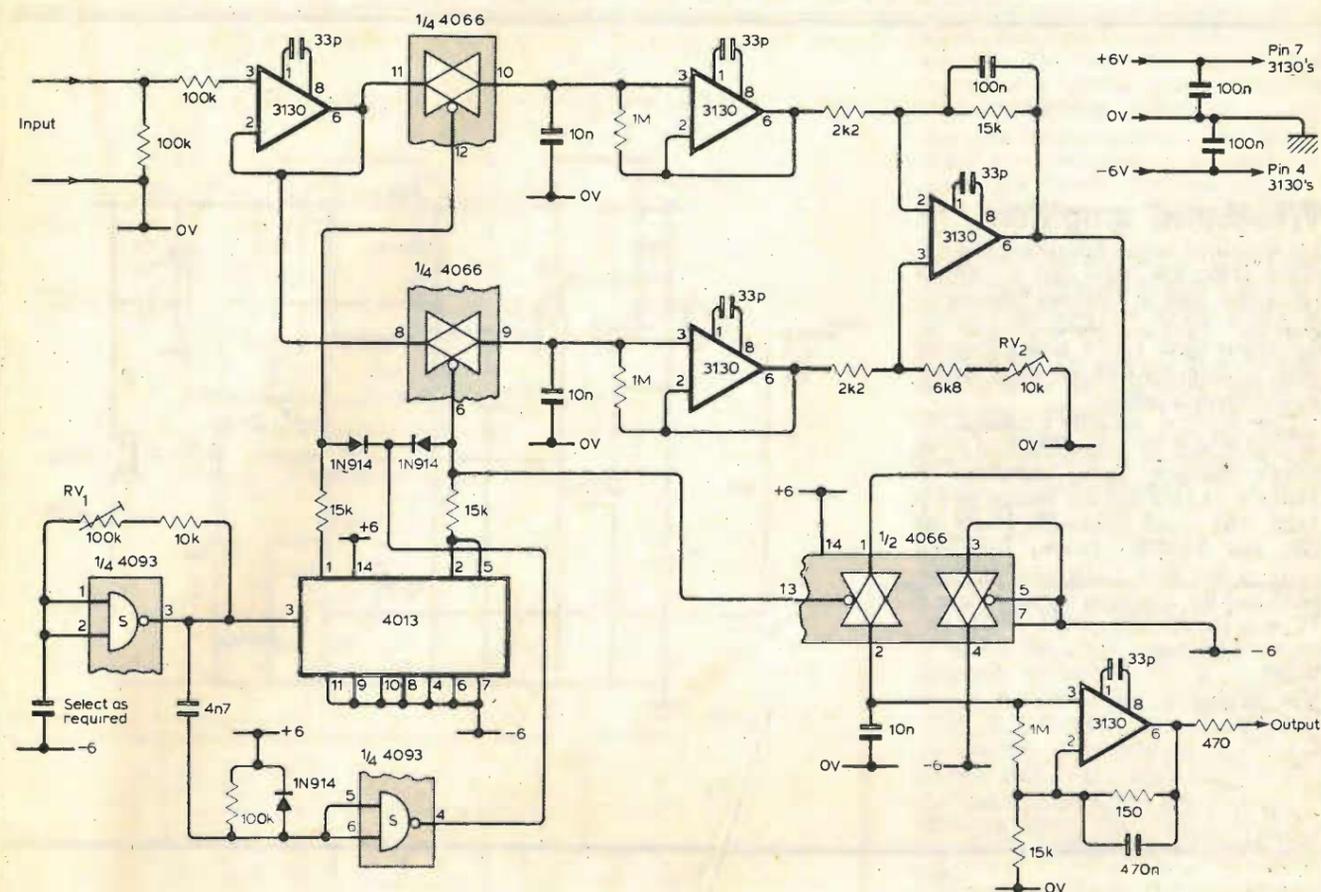


Fig. 4. Complete circuit diagram. 4013 is a dual, D-type flip-flop.

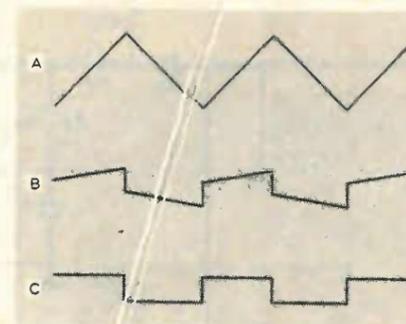


Fig. 5. The effect of adjusting RV_2 for differential balance. Triangular-wave input at (a) should produce square-wave output, as at (c).

sampling gate is required to eliminate the unwanted period. An output storage capacitor and output buffer complete the device, the complete circuit being shown in Fig. 4.

In operation, maximum sensitivity will be obtained when the clock frequency approaches the fastest rate of change of the signal. Clearly, the clock frequency should not be equal to, or less than this. The clock frequency is roughly adjusted by selection

of capacitor, and fine tuned by the potentiometer RV_1 . The only other adjustment is by RV_2 (differential balance). This is most easily set by observing the result of the triangle wave input (in Fig. 5). The output from the differentiator under these conditions should be a square wave, since we have a constant positive rate of change (gradient) followed by a negative gradient, and the amplitude of this square wave will be related to the input frequency. Set up

RV_2 for maximum flatness of the square-wave output.

The circuit described is useful where a trend, rather than absolute results, are required. Clearly, this simple design could be elaborated to reduce offsets, and to use rather than eliminate the alternative sampling period, by more complex switching. Considering these limitations, the differentiator performs well and produces consistent results. □


CIRCUIT IDEAS

Wideband amplifier

For low signal level applications, this amplifier offers low noise and a 9.8MHz bandwidth with a minimum amount of frequency selective peaking. As a result, the output signal has an almost constant phase relationship with the input signal, which improves stability.

The circuit is basically a cascode arrangement with the output buffered by an emitter follower. Input impedance at 2MHz is 18.5kΩ and the voltage gain is 32dB. The -3dB bandwidth points are 6Hz and 9.8MHz. Output amplitude ripple is less than 1.2dB over the pass-band, and the maximum output voltage is 3V pk-to-pk.

D. R. Wightman
Waihi
New Zealand

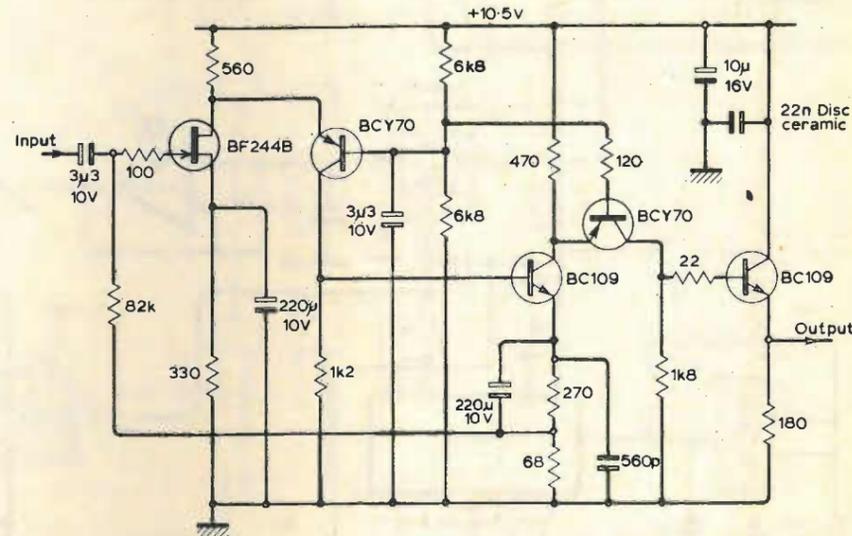


Dynamic noise reducer

This circuit was developed for use with a good quality cassette recorder, such as the Linsley Hood design, where the cost and complexity of a Dolby B or similar system was not justified. Noise from a replayed tape is most noticeable at low recorded signal levels, and the noise spectrum peaks in the 5 to 10kHz region. Reduction of the background noise is achieved by applying a progressive treble cut to signals which fall below about -35dB (relative to the nominal 0VU replay level), to roughly match the falling treble response of the ear.

A voltage controlled filter uses a diode as a variable resistance element which is modulated by the detected signal level. At high signal levels the gain is unity over the audio spectrum, but falls to -10dB at frequencies above 5kHz as the h.f. content of the input signal is reduced. The level-detector delay time and sensitivity are determined by R_d and R_f respectively. A stereo noise reducer can be built using one LM324 or similar quad op-amp. For recording, a complementary characteristic can be obtained by connecting D_1 in series with C_1R_2 instead of C_2R_3 .

G. C. Hammond
Nuneaton
Warwickshire


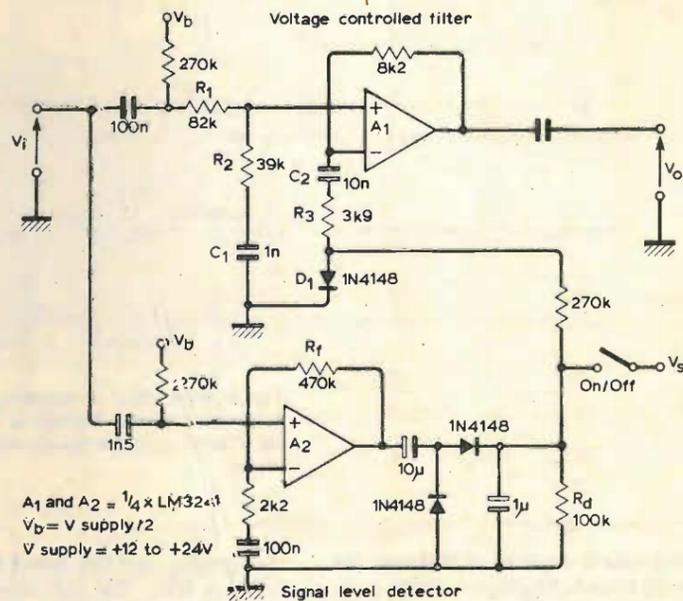


Phase synchronised monostable oscillator

Two monostables form an oscillator whose phase can be synchronised with an incoming pulse. The circuit was originally used to replace a damped resonant-amplifier clock regenerating circuit in a data recording system. Analogue data from the signal processing system was peak detected, and the write data was encoded to have a maximum of four clock periods between peak pulses.

The oscillator is started by the first peak pulse which occurs at the start of each data stream. Successive peak pulses update the phase of the oscillator and keep the clock in phase with the analogue data. If a peak pulse is early, M_1 is triggered and M_2 is reset, which effectively resets the phase to zero. If the peak pulse is late, M_1 is retriggered which extends its period by the amount the pulse is overdue.

E. M. Davies
Towcester
Northants

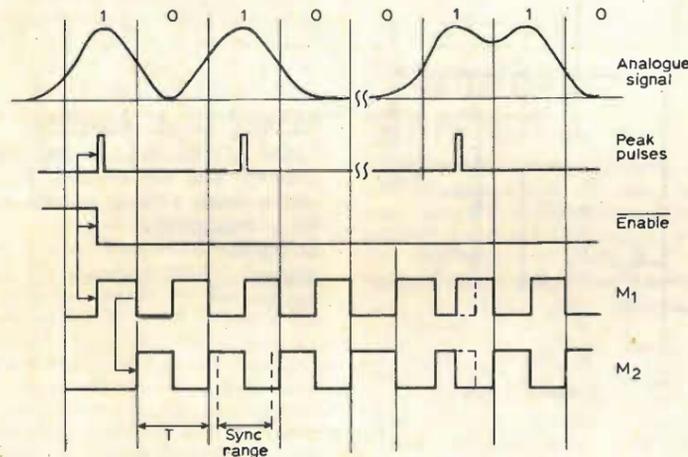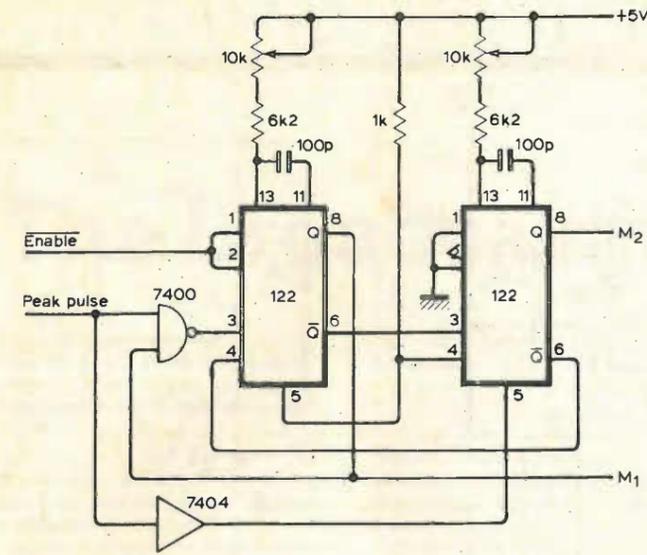


Visual fire effect

A realistic fire effect, suitable for amateur dramatics, can be achieved with the circuit shown. A wooden base carries three 60W bulbs, the two outer lamps are red and are permanently on to produce the effect of glowing coals. The middle bulb is yellow and flashes randomly to give the effect of flickering flames. The unit is covered by a log effect moulding taken from an electric fire.

A 4015 shift register and the exclusive-OR gates form a maximum length pseudo-random sequence generator. This is clocked at 10Hz by the oscillator using Schmitt trigger A. The pseudo-random pattern of ones and zeros at point X repeats every 25s, and gate E prevents the generator from locking up in the all-zeros state. Diodes D_1 , D_2 and D_3 provide a +10V supply for the circuit, and Tr_1 , Tr_2 generate a positive-going pulse at point Y each time the mains voltage passes through zero. These pulses are gated with the pseudo-random sequence by gate B. Gates C and D generate a negative-going pulse at point Z, whose width is determined by R_2C_1 , to trigger the triac just after the zero crossing point and eliminate interference.


J. A. H. Edwards
Leicester

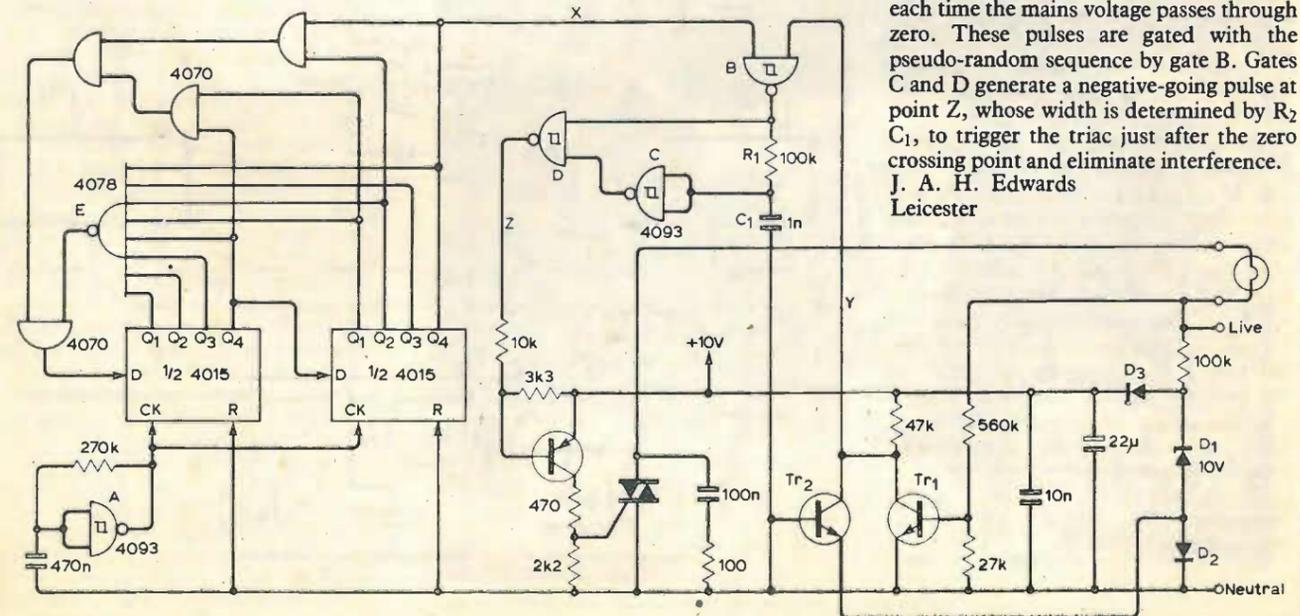

Simple s.c.r. oscillator

Fig. (a) shows a basic s.c.r. oscillator with a frequency of 7kHz. The voltage across the s.c.r. rises until there is sufficient gate current to switch it on. The anode resistor is chosen so that when the s.c.r. conducts, the current is below the minimum sustain current and the device switches off. A new cycle then starts. Supply voltage and temperature are critical and not every s.c.r. will oscillate. An improved circuit is shown in Fig. (b) where an inductor, such as a speaker coil, is connected in series with the capacitor to provide an output frequency from 100Hz to 10kHz. The components are not critical and the circuit will work with a wide range of supply voltages. Because the back e.m.f. of the inductor helps to switch the s.c.r. off, this principle can be used to control a d.c. load as shown in Fig. (c). Current through the load can be controlled between 25 and 90% with the potentiometer.



D. Di. Mario
Rome
Italy

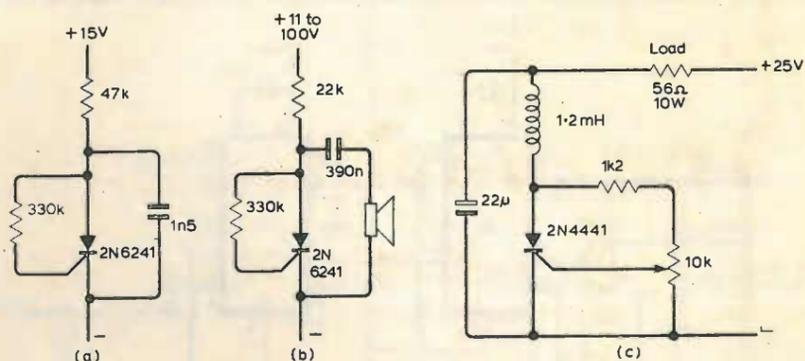

Tachometer indicates rotation sense

Rotation speed and sense can be detected by two phototransistors as shown. One monostable is triggered by the phototransistor which turns on first, depending on the direction of rotation. Tr₃ inhibits the remaining monostable and a RC combination produces a delay to permit triggering of the first monostable. The light sources must produce a V_{cc} of 300mV for Tr₁ and Tr₂, and Schmitt triggers are recommended to produce fast trigger edges, especially at slow rotational speeds.


S. Ion
Romania

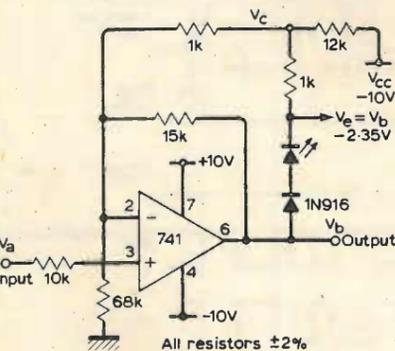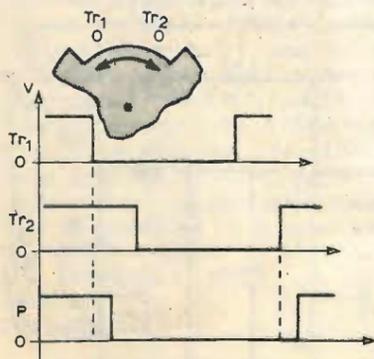

Linear l.e.d. control

Linear control of l.e.d. intensity can be achieved with one op-amp. The input is varied from +5.6 to -6.2V where the l.e.d. extinguishes.

P. Amin
Harlow
Essex

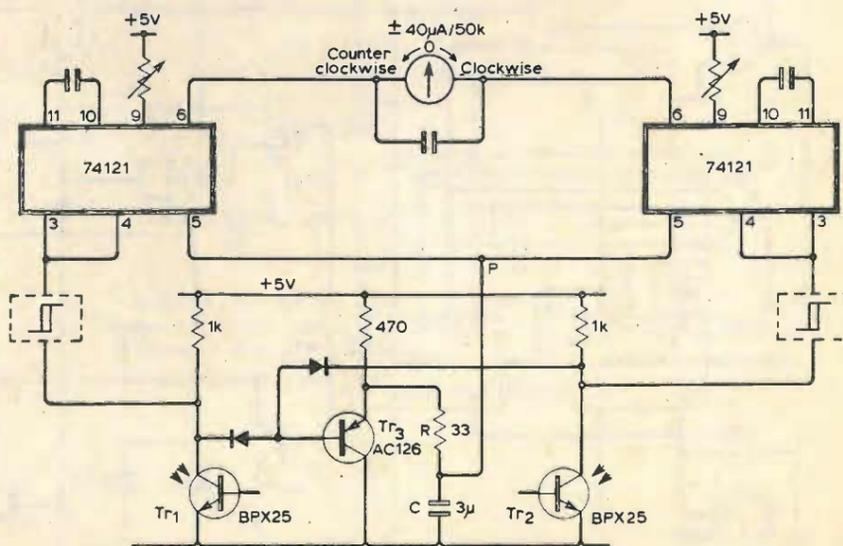

NEWS OF THE MONTH

The Broadcasting Act 1980

One of the main effects of the Broadcasting Act, which received the Royal Assent in November, is to extend the life of the IBA by fifteen years. Under previous legislation the life of the IBA was due to expire at the end of 1981. Now, as recommended by the Annan Committee on broadcasting, the Authority will go on until the end of 1996 - and this may be extended by statutory instrument for up to five years.

Another important effect of the Act is to hand over the fourth television channel to the IBA to provide a new service (other than in Wales). Here the IBA has to ensure that the fourth channel programmes contain a suitable proportion of matter calculated to appeal to tastes and interests not generally catered for on ITV; to ensure that a suitable proportion of programmes are of an educational nature; to encourage innovation and experiment in programming and generally to give the fourth channel a distinctive character of its own.

Programmes will be obtained and assembled into schedules by a subsidiary formed by the IBA for that purpose. Finance for engineering, transmitting and supervising the fourth channel, and for the purchase by the subsidiary of programmes for the service, will come from the ITV programme companies, who will have the right to sell advertising time among fourth channel programmes broadcast in their regions. The IBA will be required to include in its annual report information about the way the fourth channel service has differed from the ITV service, both in content and sources of programmes, and how innovation and experiment has been encouraged. Information will also be required about complaints received concerning the sale of advertising of either channel.

The Act provides for Welsh Language programmes to be concentrated on the fourth channel in Wales, with the possibility of changing to a two-channel solution after a period. A Welsh Fourth Channel Authority, consisting of a chairman and four members appointed by the Home Secretary, will have overall responsibility. A substantial proportion of programmes must be in Welsh. When Welsh programmes are not being broadcast programmes shown on the channel will normally be those being transmitted on the main fourth channel service at that time. The BBC will have to supply the Welsh Authority with Welsh language programmes free of charge and the IBA's Welsh contractor has to do so in return for payment. The last-mentioned contractor may sell advertising time on the fourth channel in Wales.

The Welsh Authority's expenses will be met by payments agreed between it and the IBA (or in default of agreement, fixed by the Secretary of State) which the IBA will raise from the ITV programme contractors.

A selection of the Act provides for new financial arrangements for independent local radio. Rental payments will be made to the IBA by the ILR contractors in respect of the Authority's cost in supervising and expanding the system,

and there will be a levy payable to the Exchequer on their profits. The rate of levy is set at 40 per cent, but this (like the 66.7 per cent levy on the profits of ITV contractors) could be varied by order. Also, the IBA will be able to make grants to local radio contractors. This will enable the Authority to help the expansion of independent local radio and to improve the quality of its service.

Under the Act, ITV and ILR contracts will run for a maximum of eight years (subject to a

transitional provision for independent local radio in existence before the introduction of the legislation). But a first ILR contract in an area previously unserved by ILR may run for a maximum of ten years. In addition, the IBA is required to re-advertise both ITV and ILR contracts when the contract periods comes to an end. The ILR will have to publish a notice of its intent to enter a contract and the date from which the contract will run and invite applications for that contract.

Ptarmigan takes off

Plessey, the prime contractor for the battlefield communication system, Ptarmigan, say that its total value will be "several hundred million pounds", and that it will provide over 400 new jobs. Sub-contractors include STC, Marconi, Airtel, BICC, Marshall of Cambridge and Membrain. Plessey's order book now stands at £1,200 million.

Ptarmigan is designed for the British Army and RAF in Germany, although it is meant to be compatible with older equipment such as Bruin, which it replaces, and other systems being developed in Europe. It is a trunk digital radio network with access for 'subscribers' and is described by General Sir Hugh Beach as "like System X with car radiophone, only more so".

A full range of facilities, such as abbreviated dialling, call transfer, hold, conference and storage, are available. In addition to speech, the system can handle telegraph, data and facsimile.

Development of Ptarmigan started in 1973, and first deliveries of equipment are expected around 1982, although there appears to be an element of uncertainty about this. The army seems to think that the second half of the decade is a more realistic expectation, and the mid-'80s has also been mentioned.

Both Plessey and General Beach (Master General of the Ordnance) find themselves unable to comment on the award of the production contract vis-à-vis the moratorium on new defence contracts introduced on August 8. It seems likely that the production contract is considered a continuation of the development contract and consequently immune to cancellation.



Ptarmigan mobile 'subscriber' terminal in a Land-Rover.

Two-year trial period for subscriptions tv

Following his consideration of a report submitted to the House of Commons in February, the Home Secretary, William Whitelaw, has decided to allow 12 pilot schemes in subscription tv (using cable systems) to begin operation in the UK, initially for a two-year period.

In a written answer to a question from Colin Shepherd (the MP for Hereford), he said that, since it "would not be practical nor appropriate for the Home Office to supervise the programmes shown nor to exercise the functions of a broadcasting authority", most of the broadcast material would consist of feature films. Licensees may not seek exclusive rights to show sporting and entertainment events of national importance. **Advertising will not be permitted.**

As well as being required to conduct research into public reactions to such a service, each licensee will be expected to monitor progress and submit reports to the Home Office from time to time.

The Home Secretary also said that he is considering a levy "for the benefit of the film industry, and . . . any additional safeguards needed to protect the cinema and television broadcasting services." Applications for licences will only be considered from existing licensees of broadcasting relay systems. The schemes will be conducted at the commercial risk of the operator who will also be required to provide details of the technical characteristics of the system and to comply with any licence conditions calling for the suppression of interference with other forms of broadcasting. The Depart-

ment of Trade will not charge a levy in respect of the showing of films in the pilot schemes, although a licence fee will be charged to cover the administrative costs incurred by the Home Office.

Licences have been granted for broadcast relay since the late 1920s, first to relay sound and then tv programmes. In 1965 an experiment was set up as a reaction to suggestions by several companies, resulting in three companies being issued with licences for an experimental service. However, two of these companies decided that the restrictive conditions imposed by the Post Office (which was the licensing authority in 1965) and the lack of commercial assurance for the future, were not acceptable, and surrendered their licences.

The third company, Pay-TV Ltd, mounted experiments in London and Sheffield and operated technically successful services from 1966 to 1968. The company was satisfied that the results showed the acceptability of the service and that commercial viability could be achieved if coverage could be extended from the experimental 12,500 to 250,000 homes. Permission to increase the coverage was refused, however, and the service closed down.

In contrast, many cable tv networks are in operation in the US and by 1976 there were 633,000 homes so equipped, most of the stations providing feature film and general sport programmes, in fact much like the system currently envisaged by William Whitelaw. Many of these US networks now receive their signals via satellites.

US local TV stations recommended

Hundreds of low-power local television stations may be set up in the USA as a result of a recent recommendation. With a power of about 1kW and covering areas with a radius of about 25km, they are intended for specialized services such as dealing with local community events. They have been planned not to interfere with the broadcasting of normal, high power commercial television stations, but the National Association of Broadcasters in the US is worried because they think the FCC may not have studied the problems thoroughly enough. Obviously, the proprietors of existing commercial TV stations will see the new service as a possible threat to their present advertising revenues.

On 7 Nov the BBC's 1000th colour tv transmitter was put into service (see Dr Trickett's article this issue). The transmitter is located at Hedleyhope in Co. Durham and will serve about 1000 homes in Waterhouses, Esh Winning and East Hedleyhope. The services and channels relayed are BBC1 (North-East) - ch.40, BBC2 - ch.46, ITV (Tyne-Tees) - ch.43 and the 4th channel (when operational) - ch.50. Polarization is horizontal.

A short course entitled **Thermal Design of Electronic Systems** will be presented at Cranfield Institute of Technology during the week 26-30 Jan 1981. It will consist of two three-day tuition blocks covering (1) fundamentals and applications of conduction, convection and radiation to temperature control (2) liquid pool boiling, heat pipes, phase change materials, fluidized beds and thermoelectric cooling. This section of the course will also deal with thermal imaging and laser Doppler anemometry. Apply to the Short Course Officer, Cranfield Institute of Technology, Cranfield, Bedford MK43 0AL.

ors) or similar high speed logic elements, is to be embarked on by the US, France, Germany the UK and Japan. A major target of the scheme will be to produce a computer which accepts not only the spoken word but pictures in various forms as well as designing its own (simple) programs and diagnosing its own faults.



Studios 7 and 8 at BBC Television Centre are now being lit by a microprocessor-controlled system developed by Thornlite in collaboration with the BBC's Capital Projects Department. The unit can control up to 500 studio lights and use nine Motorola 68000 microprocessors.

News in brief

More than 700 Japanese government officials, businessmen and technical personnel attended the second British Overseas Trade Board seminar on industrial energy saving and efficiency, held in Tokyo late in September. The seminar was held at the World Import Mart building and was the first such meeting in Japan sponsored by a foreign government organization.

Digital Communications Corporation, a member of the M/A-Com group of companies (US) has formed DDC Ltd, a British subsidiary. The new company's product range will include satellite ground station, terrestrial p.c.m. and data transmission equipment for private and national organizations. The company's head office will be located at Humphrys Rd, Dunstable, LU5 4SX.

Communications 82 will be held at the National Exhibition Centre, Birmingham, from Tuesday 20 until Friday 23 April 1982 (inclusive). This will be the sixth in a series of biennial international expositions dealing with communications equipment and systems.

The British Standards Institution has published a six-part delineation of *High Fidelity Audio Equipment and Systems; Minimum Performance Requirements*. For further information, contact the BSI, 2, Park St, London W1A 2BS or telephone 01-629 9000.

A ten-year collaboration project, aimed at producing a new generation of computers based on the use of Josephson junctions (superconduc-

SRC, inflation, Einstein and quasi stellar mirages

The continuing success of the Science Research Council in discharging its commitment to the social, technical and economic ramifications of industry and academia, in spite of the rigours of inflation, is given detailed support in its report for 1979-80, published early in November.

Alongside comparisons of expenditure of grants (£19 million in 1979 compared with £3½ million in 1970) the report records some "striking discoveries." The most notable of these is probably the confirmation of Einstein's prediction, made fifty years ago, that gravitational fields could act as "lenses". During a uniform survey of quasi-stellar objects (q.s.os) at the Nuffield Radio Astronomy Laboratory, Jodrell Bank, a radio source was identified with a close pair of q.s.os on a photograph. They were found in collaborative studies at Kitt Peak Observatory to have identical spectra and nearly equal brightness, coupled with identical large redshifts.

This is in fact only one q.s.o. and the most plausible explanation is that the light from this object is reaching us by alternative paths distorted by a strong gravitational field. Recently, workers at the Mount Palomar Observatory have detected a massive galaxy on a line of sight to this object and substantially nearer to us. The mass and position of the galaxy account for the observed effect and although the shift of

a stellar image seen near the Sun was an early confirmation of Einstein's prediction, this is the first occasion on which one stellar object has been seen as two.

In another area of its activity, the SRC reports on its involvement with the University of Essex and the Mullard Space Science Laboratory of University College in obtaining data from the GOES-2 satellite. This information provides confirmation of the linear instability theory of plasma physics and is especially significant because of the importance of plasma techniques in power generation by nuclear fusion.

During the conference to introduce the report, Sir Geoffrey Allen, Chairman of the SRC, said that the cut-backs in funding caused by the present government's policies had not been as serious as was expected when he gave last year's report. However, there is a "cashflow" problem, introduced by contractors (presumably worried about the chances of payment if left too late) putting in bills immediately.

Among the facilities introduced in the current year, the electron beam lithography units at Rutherford and Appleton Laboratories carry important implications for engineering in that they can provide a precision i.c. mask-making service, supplementing the device fabrication facilities already established at Edinburgh, Southampton, Surrey and Sheffield universities.

Also in this context, Sir Geoffrey hinted at the strong possibility that the name of the Council might soon be changed to read "Science and Engineering Research Council."

The report of the Science Research Council for the year 1979-80 is available from HMSO, price £7.10.

A JOB FOR LIFE

What British company is characterized by the following phrases, quoted from a recent speech? "When an individual joins a company operating a life-long employment system he does so with a tacit understanding that, in normal circumstances, he will remain an employee of the company until retirement. The company will not discharge the employee before he reaches retirement age unless an exceptional situation arises".

"It provides strong employment stability which the employees appreciate and rigidity in the workforce size which constrains the companies in times of business recession. For the company it also serves as a guarantee against future labour shortages".

"There is a very strong emphasis on group effort towards achieving a specific business target which is hardly present in the USA where the emphasis is on individual performance....".

"The system allows the employee to feel that he can place his trust in the company, he can rely on it and thereby obtains a deeper interest in its affairs than he might otherwise acquire. The company is encouraged to place its trust in the continuing co-operation and service of its regular employees. The result is collective dedication to achieving the company's objectives."

"Employees do not find it necessary to resist technical change and innovation even though it may mean assignment to other jobs because they recognize that such changes are unlikely to affect adversely either security of employment or income. Nevertheless, it would be wrong to assume that employees are servile. The emphasis is on a reasonable approach being made by both company and employees to issues of

common concern which allows the company to maintain a high level of productivity so that the status quo continues".

"Under the seniority wage system the income of an employee is directly related to length of service with the company. Such factors as individual ability, responsibility and the demands of the job itself play a smaller part in the determination of an employee's income within a group having similar tasks. It follows that there are no comprehensive company salary or wage structures. Job evaluation, as we know it, is also missing".

"Such a system ensures that income increases with time in much the same way as the demands on it increase for the greater proportion of a family man's career".

"Strikes are viewed generally as being more in the nature of demonstrations.....".

The speech was in fact the inaugural address of the new president of the IERE, John Powell, who is engineer-in-chief of Cable and Wireless. The subject was "Resource management: a key to immediate improvement in productivity" and a good deal of the address was about the success Cable and Wireless has had in the management of its work force. The quotations above were from Mr Powell's admiring description of Japanese industry, and it was clear he felt his own firm's success in management was because its methods had an "affinity to the employment pattern found in the large Japanese companies". Mr Powell concluded: "I believe that employment practices in British manufacturing industry tend towards those generally found in the USA and therefore differ considerably from those developed in Cable and Wireless. Would there be value in rethinking this whole issue of resource management? My answer is an unqualified yes."



A prayer modem in its assembly stage by a Tibetan operative at Lhasa. Each verse is assembled in hexadecimal form before being modulated and passed into a "loop" circuit where it is converted to analogue form and fed to the output stage at the standard monotone voice frequency.

Photo by courtesy of Advanced Prayer - Wheel Designs Inc. (and STCI)



Final testing of the SBS communications satellite at the Hughes Aircraft facility at El Segundo, California. This satellite, the first of three to be put into orbit so as to provide "secure" voice, video, data and facsimile traffic for US business, was launched on Nov 15 and is owned jointly by IBM, Comsat General Corporation and Aetna Life and Casualty.

Faulty vision caused by brewer's products



An example of tv "hash" on channel B3, photographed by Roger Bunney during v.d.u. business hours (0800 to 1700).

In view of the heavy fines imposed upon 27MHz c.b. users and the claims made by the Home Office that such illegal activity seriously interferes with established authorized services, Roger Bunney's reception experiences in the Romsey area force some interesting comparisons.

He works as a television technician and journalist, contributing articles on long-distance tv reception to the magazine Television (IPC Magazines) and a considerable part of his professional activity involves monitoring the broadcast bands 1 to V. Arriving in Romsey, Hampshire in 1972, he set about building a 50ft lattice mast to carry the necessary aerials. One of the most successful and active bands for DX is Band 1 (48-68MHz), where sporadic E combines with the favourable conditions of the F₂ layer to make reception up to 500 miles possible.

In September 1976 the entire Band 1 spectrum was disrupted by high level interference, which was eventually traced to a nearby industrial site. The Whitbread-Wessex brewing concern had established a distribution office about 60 yards away, equipped with six v.d.u.s and related equipment for receiving information by cable (Post Office) from the main brewery in Portsmouth. The disruption produced a whining "motor" effect, peaking at intervals of about 1.5MHz from 30MHz up to 100MHz.

Efforts were made to contact the makers of the equipment with a view to suppression but a solicitor was eventually engaged (after a severe

lack of response!) and the v.d.u. manufacturer eventually paid for a stacked aerial array. However, this had little effect and the Home Office subsequently made measurements using Mr Bunney's array and Post Office arrays mounted on a vehicle. Although the actual results were never provided, the Home Office eventually wrote pointing out that action would not be taken nor public funds used to terminate the nuisance.

The attitude of the Home Office seems unfortunate, to put it mildly. A source of interference which is producing a public nuisance has been allowed to continue for several years, despite acknowledgement that the problem exists and within a domestic broadcast band. This was also noted by another citizen, who laid a similar complaint based on interference to local f.m. radio reception, but who has since left the area. One criticism that could be levelled at the complainant is that he is necessarily seeking remote and weak signals and can therefore expect problems, but this seems to imply that domestic users and enthusiasts are relegated to a position where they must suffer interference from vested interests and commercial organizations.

Perhaps it's time for the statutory limits to interfering radiation to be reconsidered.

Shuttle will assist in closer look at Venus

One of Jimmy Carter's last official acts as President of the United States was to approve NASA's request for funding of a mission to map the surface of Venus, to begin in 1986.

After launch by the space shuttle, the Venus Orbiting Imaging Radar (VOIR) spacecraft would circle the planet for seven months taking pictures as well as making measurements of the surface and atmosphere.

Dr Robert Frosch, NASA's chief administrator, says that this scientific project will "reveal the true nature and geological history of our sister planet in the same way that Mariner 9 enabled us to see Mars." Venus is completely veiled in clouds. No permanent feature has ever been identified by telescope. The current plans provide for arrival of the vehicle in December 1986, at which point the spacecraft would be inserted into polar orbit at an altitude of about 180 miles.

The mapping activity would result in near-global coverage of the planet with moderate resolution imagery (corresponding to 2000 feet) and a smaller section in higher resolution (about 150m - 500ft).

News in brief

The first telecommunications equipment show and seminar ever held in China is to be staged at the Beijing (Peking) Exhibit centre from Nov 3 to 13 1981 by the Electronic Industries Association (US) and the National Council for US-China Trade. Approximately 100 American manufacturers are expected to exhibit equipment at the show.

The International Association of Broadcasters (IABM) has moved to new headquarters at Triumph House, 1096 Uxbridge Rd, Hayes, Middlesex. The telephone number is now 01 573 8333.

A bureau approach to viewdata, enabling small-scale users to exploit Prestel-like hardware in a private system, is to be set up by GEC Viewdata Systems. Pages of internal information are held on the organization's viewdata computer, which can be called up, modified, and new pages inserted by users of various departments of the organization. A typical system, holding about 30,000 pages, would cost about £50,000, excluding the cost of terminals.

Public payphones which use plastic cards instead of coins will be tried out by British Telecom next year in London, Birmingham and Manchester. They will be sited near conventional payphones, giving users a choice, although it will be necessary to buy the cards, which are erased automatically when inserted into the mechanism. Each card unit is priced at 5p and there will be two basic cards on sale - one of 40 units costing £2 and a 200 unit card at £10.

receiver responds and opens an input gate to receive five bits of command data. The controller then transmits inverted command data as a check for false instructions. When the receiver has verified the command, the output stages are switched accordingly and a reply is sent to the controller, which indicates the state of the outputs and hence the effectiveness of the command. This procedure is then repeated for the next receiver in the sequence. When all the receivers have been addressed, the cycle repeats with the controller re-reading the states of the driver-operated switches.

Each receiver incorporates a fail-safe circuit which switches the affected loads to a safe state if a failure occurs.

Leyland have also developed a diagnostic system which, via the bus, can quickly check the electrical circuits on the vehicle and provide a print-out. Although the multiplexed bus technique is by no means original, this appears to be the first instance of its use in a vehicle. Some bus operators have been sceptical about the reliability of parts that do not move, but the designers stress the more positive points of the system which include the claim that it will be no more expensive than an equivalent conventional wiring harness, will be far more flexible and, with the addition of vehicle condition monitoring and diagnostic systems, far more useful.

Bus for a bus

Lucas and Leyland have jointly developed a multiplexed bus system to replace most of the complicated electrical wiring in a passenger bus or other vehicle.

Although "critical loads" such as headlamps and stop lights will still be wired conventionally, all the control wires for door solenoids, internal lighting, horn, etc., can be replaced by the bus. The system comprises a three- or four-wire "ring main", a microprocessor-based controller and up to 30 local receiver units. The bus provides a common power rail, a single wire for the transmitted data and one wire for a synchronising clock. An optional fourth wire can be added to provide a noise-free return.

The controller reads the state of the driver-operated switches, sends sync pulses at 32kHz to set the receivers to stand-by and then transmits the 5-bit address of the first receiver in the sequence. Clock pulses synchronise the loading of this address into a memory in each receiver and, to overcome false addressing caused by noise, the same address is transmitted again and loaded into a second memory. Each receiver compares the two stored addresses which, if identical, are compared with the fixed address of the receiver. Consequently, only one

Multiplex keying system for organs

TDM system reduces complexity and cost, allows mixture stops, transposition and pizzicato effects

by A. W. Critchley, Dipl.El., M.I.E.R.E.

Home organ projects suffer from a high mortality rate perhaps principally as a result of their inflexibility and the time taken to get acceptable results; it is common to be overtaken by technology! This article presents the basis for a system intended to reduce the drudgery and cost of building an organ, whether pipe, electronic or hybrid. It shows that the resulting system is flexible enough to permit a wide range of organ features, many hitherto unobtainable on electronic organs, which can result in them being able to simulate pipe organs more closely at a fraction of the cost.

The principles can easily be adapted for microprocessor control at a much lower hardware cost and complexity. But for the experimenter or technician without microprocessor capability who likes to know how things are done and who wants to be able to change it around without too much effort, the microprocessor approach takes away a lot of the fun and relegates everything to a mystery black box.

The method of controlling the keying to be described is offered as a practical solution to the problem of multiple key contacts, whether the organ is a pipe or electronic, church or entertainment type. It has advantages over conventional wiring, not least being the cost, which can be paid for out of the saving in copper wire:

Cable size from the console is significantly reduced.

Circuitry is inexpensive and uses standard c.m.o.s. devices.

Single-pole contacts throughout of light current capacity - a milliamp or so just to keep the contacts clean.

Keyboard wiring is simple and can be standardised.

Octave coupling within manuals is simply a matter of incorporating delays. Inter-manual coupling is identically done using longer delays.

Any required pitch can be selected with ease.

Mutation and mixture stops are no problem.

Any kind of organ can be controlled - pipe or electronic.

No limit to the size of organ.

Extra consoles may be added. Second-touch keying is easily catered for.

All other switch information can be included if desired.

Only a handful of printed-circuit boards is required.

It is flexible to permit custom designing.

Coupler switches are not used, avoiding high-current supplies.

Disadvantages include complex circuitry in which a single failure could render the whole organ inoperative, a high level of servicing competence being necessary.

Key matrixing

The system basically comprises a matrix for the pedals and keys to minimise the number of wires that have to be connected to the keys. The contact information is then turned into a series of pulses by sequential scanning of the matrix, see Fig. 1. Data is passed over a single wire through various delay systems to demultiplexers which recover the keyed information to switch on and off the

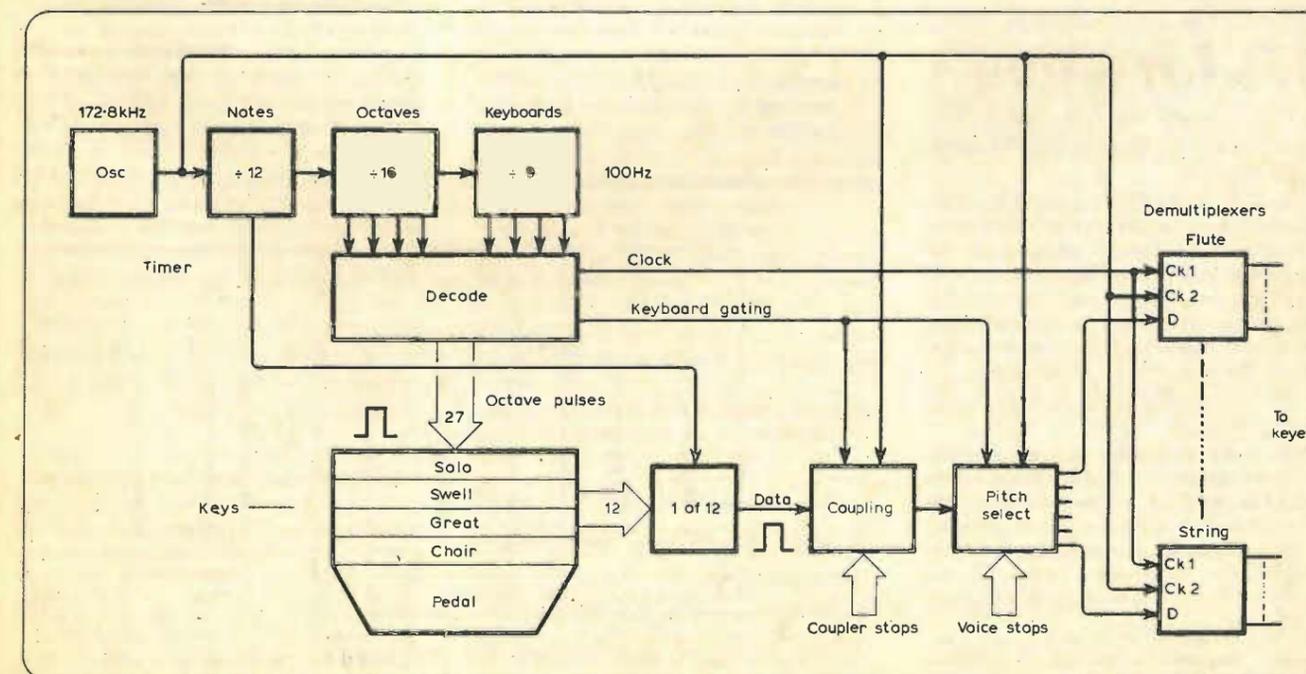


Fig 1. Sequential scanning of keyboard matrix in electronic or pipe organs reduces wiring by sending data over single wire.

appropriate musical notes in various pitches and tones. These may be made by pipes, oscillators, or any other means; this article does not discuss this part of the organ. The delays consist of shift registers and perform the tasks of pitch selection and coupling.

It is convenient to arrange the keyboard matrix in the form of manuals and octaves in one direction and notes in the other, although for a matrix with the minimum number of wires an 8 x 8 format would be optimum, and would lend itself to microprocessor control more readily. Each octave comprises the 12 notes C, C#, D, . . . A#, B. All identical notes are wired together resulting in twelve wires on one side of the matrix. On the other side of the key contacts each manual has all 12 notes in each octave wired together and every key has a series diode to prevent back-circuits (Fig. 2) resulting in six wires per manual plus three for the pedals (32 notes max.). For a four-manual organ, then only 39 wires are necessary. The whole organ is scanned sequentially note-by-note and octave-by-octave from the lowest pedal to the highest manual key such that the serial data output represents a series of rising pitches. Pulses occur only when the keys are pressed. The repetition rate of this scan has to be fast in order to permit fast playing such as trills and glissandos. A one-hundredth of a second is reasonable for this resulting in a pulse repetition rate of less than two hundred kilohertz for a four-manual organ.

Octave and manual coupling

As the serial keyboard data is in the form of one pulse per note it is clear that 12 pulses separate keys an octave apart in pitch. Therefore to couple an octave is simply a matter of delaying the data by 12 pulses and adding it to the data stream when whichever keys were played will also sound their octaves.

Sub-octave coupling is almost as simple. The data itself are delayed by 12 pulses and the undelayed data added instead. The output is of course delayed by 12 pulses but this is easily taken care of in the demultiplexers by delaying the decoding signals to match.

Fig. 3 shows the system for swell octave and sub-octave couplings together with a unison-off coupler which merely removes the normal pitch. Also shown is a choir octave coupler. This is possible with the same circuit by time-sharing as the data for this manual comes at a different time than that for the swell. Gating of the data has to be done in any case as we do not want to octave-couple all manuals at once. The gating pulse lasts only as long as that particular manual is being scanned and may be applied at the input, output or via the stops as shown. As the data are delayed by up to 24 pulses the scanning time per manual has to be increased by two octaves to prevent this data from intruding into the data for the next manual.

Coupling between manuals is simply a matter of lengthening the delays involved so that the delayed data turns up in the right place in the scan of the next manual.

The problem

One of the biggest problems in the manufacture of an organ, electronic or pipe but particularly electronic, is in the wiring of the key contacts and coupler stops. These affect which notes are played when keys are pressed on the manuals (keyboards). The traditional approach in the pipe organ is to wire one contact per key to the magnet (solenoid air-valve) which allows one pipe to speak from one rank of pipes. It is customary to be able to couple keyboards together in a variety of ways, so that for instance when the great-manual keys are played they perform the functions of the swell-manual keys as well, but not vice versa. The swell keys do not have to go down although in olden days they used to with mechanical actions.

Each coupling requires an extra contact on every key as well as a series switch to effect control. This last is operated by a solenoid action as 61 poles are required, one for each key per manual. Several hundreds of milliamps are required to operate the solenoid and almost as much to operate each pipe magnet.

On larger organs similar couplings can be selected so that the coupled manual can be played at a different pitch; usually an octave higher and/or lower. This coupling can be on the same manual too. If the swell manual is coupled to the great manual so that the swell plays an octave higher, then the coupler stop is called swell-to-great octave or swell-to-great 4 ft. The majority of organs can also couple the manuals to the footpedals, which are simply a large set of keys, but none of the couplings are

normally performed in the reverse direction.

Each key can therefore have many contacts. There is not room for more than perhaps eight without resorting to multi-pole relays. Consequently the number of wires involved with a large organ is colossal. Not only is it tedious to wire up, but it is also bulky and expensive as well as being inflexible in its requirements. There is a multiplicity of things that can go wrong; especially where contacts are involved at high currents.

Electronic organs usually require even more contacts per key but for different reasons. It is common to switch actual signals with the key contacts which are then arranged in isolated pairs. Each key requires, say, five pairs to control five harmonically-related frequencies such as the sub-harmonic, the fundamental, second, third and fourth harmonics. This means that inter-manual coupling must also have five pairs of contacts per key. This is just not practical. Most electronic organs that do have couplers couple either in another way altogether or else couple only the fundamental pitches. The classical organist generally does not like electronic organs and this lack of adequate coupling may be one reason why.

The system described in the article is capable of controlling any kind of organ in which the various pitches are turned on and off by remote means. This can be solenoid-operated pipes or electronic oscillators with transistor switches, etc., in any combination. It does not show how the switching is performed.

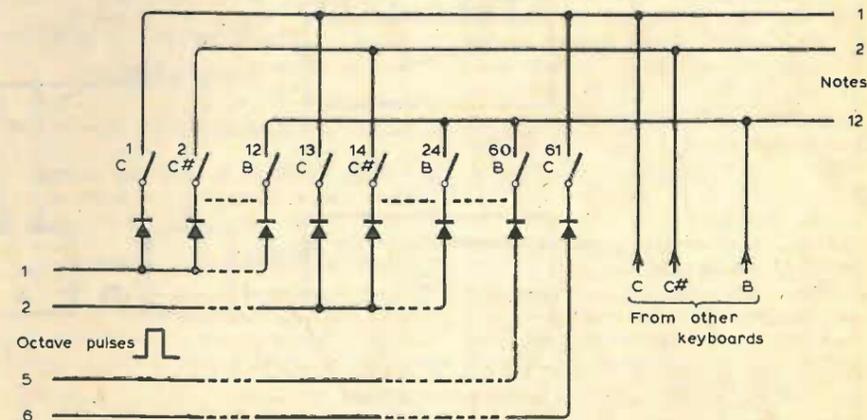


Fig. 2. Identical notes are wired together on one side of matrix, with all 12 notes in each octave wired together via diodes on the other side.

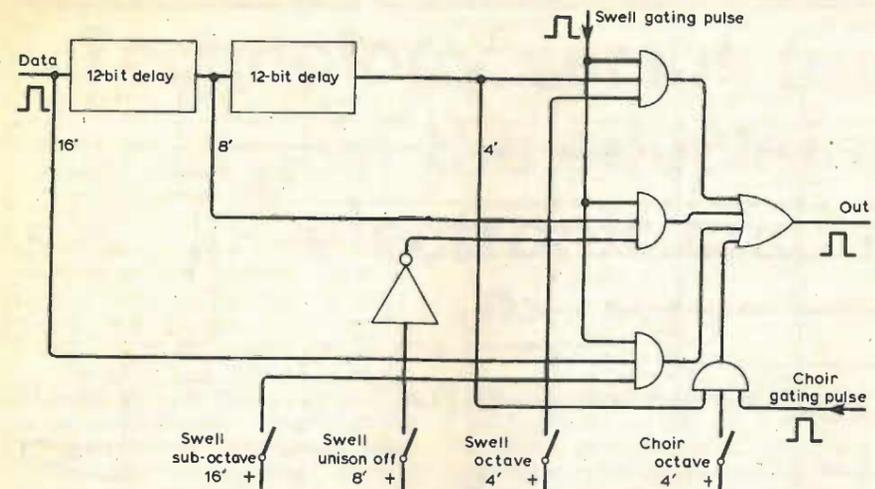


Fig. 3. As scanning is sequential note-by-note and octave-by-octave, 12 pulses separate keys an octave apart, and octave coupling is achieved using 12 pulse data delays.

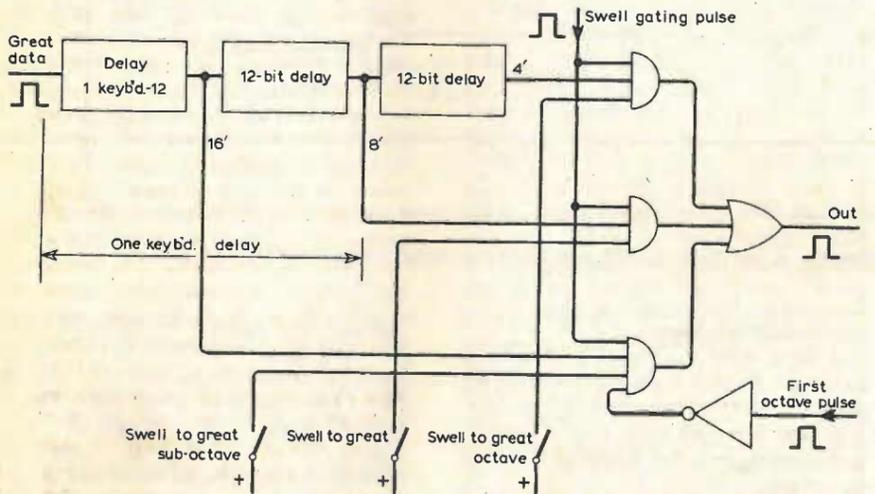


Fig. 4. Coupling between manuals is achieved by lengthening delays so that delayed data occurs at the right place in the scan.

This may also be done plus or minus an octave. Fig. 4 shows the system.

Any method of coupling octaves will involve the use of notes beyond the normal range of the keyboards. These are not normally coupled in a pipe organ because the pipes for them are not there. This results in the player running out of notes and can be a nuisance. On unit or extension organs the pipes are there for that reason among others, but it is not a bad idea to omit the lowest octave of an inter-manual sub-octave coupler in any case to avoid muddy sounds. In fact, some ranks of pipes stop at Tenor C anyway. The omission of the lowest octave in the system described is easily done by including the first octave gating pulse from the timing system - as shown.

There is a convention regarding which manuals may be coupled together on a large organ. The swell manual may be played from the choir or the great but not the other way around. Similarly, the choir may be played from the great. The solo manual (the top one) cannot couple to the other manuals whilst the pedals may only be coupled to manuals. Taking this into

account, the arrangement of the delay systems for inter-manual coupling may be optimized by scanning the matrix in a staggered manner. For a two-manual organ this would be pedal, great and swell whilst a four-manual organ might be pedal, great, choir, swell and solo.

Addition of extra manual delay periods for coupling means that extra manual periods are required in the scanning process to avoid intrusion of pulses into the next pedal scan period. A two-manual organ therefore requires five such periods in the scan.

Fig. 5 shows the complete coupling system for a two-manual church organ.

Multiple pitches

Even the simplest organ should have the ability to play notes at different pitches when a single key is pressed; electronic organs do this by keying up to five pitches per key into separate busbars where they are filtered to form five pitches of tones. Pipe organs solve the problem by having separate ranks of pipes for each type of sound so that, for instance, an 8ft flute

would have 61 pipes (one per key) and a 4ft flute would have another 61 and sound an octave higher. This is the brute force approach and a typical small church organ with, say, eight swell ranks, four great ranks and two pedal ranks would have 796 pipes. Clearly, a large pipe organ is going to have a colossal number of pipes and be cumbersome and difficult to keep in tune as well as having a lot of wire from the keys.

In 1891 Robert Hope-Jones devised the unit organ in which only a small number of ranks could be played at any pitch from any manual. Ranks were not duplicated in tone and six or eight could provide the tone range for the whole organ, provided that the ranks were extended and the voicing was altered to boost up the middle volume to compensate for the extra non-unison pitches. There was one drawback: it was no longer possible to have independent control of the volume levels of the different manuals. Hope-Jones also devised the electric action with which to control the unit system which is nowadays known as the extension system. Later manufacturers, notably the Wurlitzer company, improved on his ideas to make the giant cinema organs of yesteryear. Even some of the biggest of these had no more pipes in them than a small church organ but what sounds they could make. Of course, they had special effects such as xylophones, principally for the accompaniment of silent films and, incidentally, are marvellous examples of ergonomics in the layout of their console facilities; something from which church organs could benefit.

The extension principle requires each rank to be extended so as to provide extra upper and lower octaves; 97 pipes would be required to cover the range from 16 to 2ft. Nevertheless, fewer pipes are required than for a conventional organ. The availability of these extra pitches enables octave coupling to be properly carried out.

In electronic organs the extension principle is carried to the extreme in that a single rank of frequency generators is switched into a few busbars and the different voices obtained by filtering. The problem of lack of volume independence between manuals is overcome by controlling the volume of the entire organ by one control pedal. It is, however, possible to separate some voices for control by a second pedal after the manner of a cinema organ. By this means the resultant voicing may be varied without releasing any keys by cross-fading the two pedals, not an easy task with one foot!

Couplers were not often found on cinema organs because of the great variety of sounds that could be obtained without them due to the extended ranks. They are not often found on electronic organs either, not because they are not necessary but because they are difficult to incorporate. Now that the circuitry within electronic organs is becoming cheaper and simpler the extension principle is being rediscovered. A single rank of generators is still used but separate keying for different voices (ranks) is beginning to be

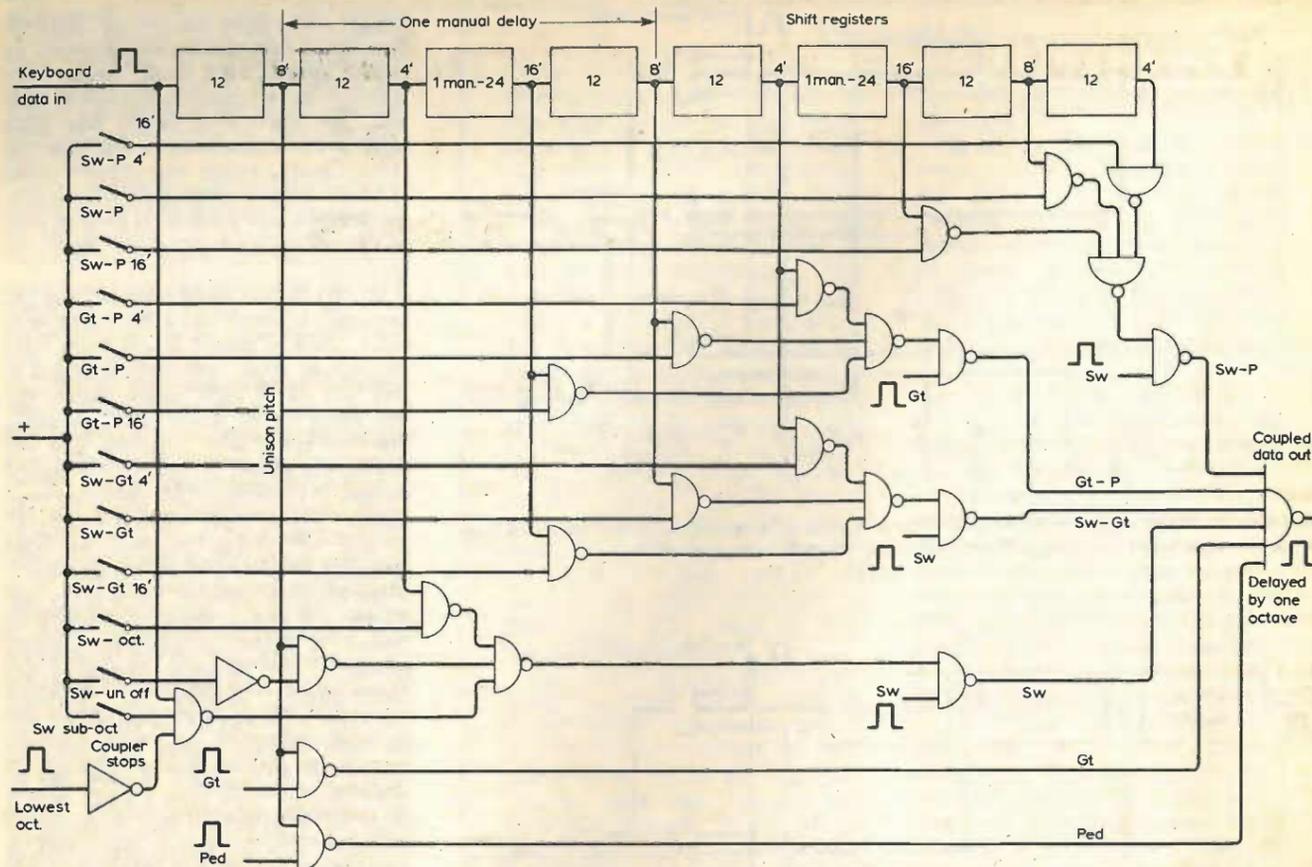


Fig. 5. Extra manual delays are required during scanning to avoid intrusion of pulses into next pedal scan period. Diagram shows coupling system for two-manual church organ.

employed. This enables more realistic sounds to be obtained as the voices can be balanced in level at different pitches by using several filters instead of just one. Also tricks like 'chiff' can be incorporated into a flute rank without affecting other ranks.

Extra ranks of generators are becoming popular, too; for instance, the celeste voice is tuned slightly sharp to give a wavering effect (not to be confused with tremolo or vibrato) and the unda maris is a flute tuned slightly flat. The same principle also provides the chorus effect by using two parallel generators with a slight frequency difference between them. The second generator is usually at a lower level.

The keying system described provides the ability to obtain keying for all pitches required in the extension principle - or

the conventional manner.

A long delay in the data stream is equivalent to inter-manual coupling and a delay of 12 pulses gives octave coupling. The same principle holds good for multi-pitch keying by using delays of less than one octave.

The selection of a shift register output only a few sections away from the normal 8ft output is equivalent to changing the pitch of the entire organ. For example, if the delay is made seven sections then an 8ft note C would result in a 5 1/2ft note G which is musically higher by a fifth in the diatonic scale. Logically then, one can tap the shift register at every necessary pitch increment and through simple gating by the stops can control the appropriate frequencies from the generators (or pipes). For a large organ many pitches are

required from 32ft for the pedals to 1ft or less, with various odd ones in between to cater for mutations or mixtures. Fig. 6 shows how this is achieved whilst Fig. 7 (part 2) shows a control system in which similarly-voiced stops are collected together. Each keyboard has its own gating pulses so that only one such shift register is necessary for the entire organ. Again, the length of the delay involved necessitates extra time in the scanning process.

At this point the traditional and extension organ principles diverge. The traditional one would use all the outputs to drive independent demultiplexers (one for each rank) whereas the extension type would further collect together all outputs of identical voicing to drive one demultiplexer per voice only. In Fig. 7 this results in three demultiplexers instead of six.

To be continued

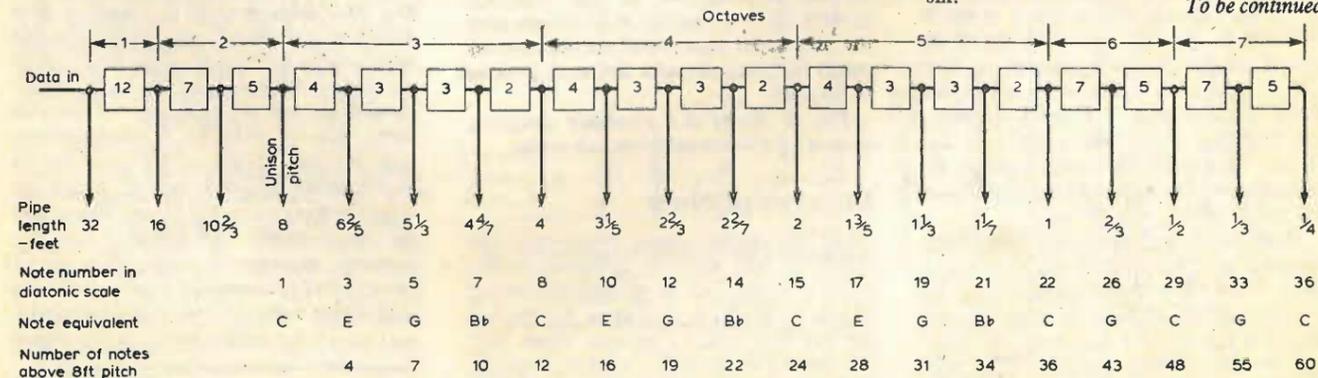


Fig. 6. Shift register can be tapped at necessary increments and simple gating controls appropriate frequencies from generators or pipes. (See part 2, Fig. 7, for simplified control system.)

Technology versus fundamentals in the education of electronic engineers

by D. A. Bell, F.Inst.P., F.I.E.E.

It has long been customary to speak of the education-and-training of engineers. The two aspects are combined in the French word *formation* and there is now a move to anglicize this French word to describe the process of turning a school boy/girl into an engineer. But in Britain there is an argument whether academic institutions (universities and polytechnics) should be responsible for training as well as education, since the 2-year graduate apprenticeship has been in decline since the outbreak of the second world war. There was a Greek legend that instead of being born in the usual way the goddess Athene sprang from the head of Zeus fully grown and fully armed. To expect an engineer to arise fully developed from the ceremony of conferring his degree may be just as irrational as the Greek legend: a degree course cannot include all the "know-how" of every firm by whom a graduate might be employed, and the employer must be prepared to provide some technical training, either formally or informally. But the employer can rightly expect the graduate to know basic matters and the problem in designing a degree course is to decide what is basic both in fundamentals and in current technology.

Which kind of engineer?

It has always been a major problem to cater adequately for those students whose university performance, whatever their A-level grades, suggests that they are not capable of the standard which universities describe as 'honours' and the professional institutions are now describing as that of 'innovative engineers'. It may be noted that the latter distinction arises because the institutions are now according professional status to technician engineers. At one time the distinction was between (innovative) professional engineers and (follow-the-beaten-path) technicians; but technicians now make such an important contribution to the progress and conduct of all branches of engineering that it seems only right that the more senior of them should be accorded professional status.

There is also a suggestion that innovative engineers should be produced only through 'enhanced' engineering courses. Apart from the certain objections of the majority of universities which will not have 'enhanced' courses* and which would therefore be condemned to producing only

technician engineers, this raises the question of whether students can be classified as 'innovative' or 'technician' types before entry to a university course. If university departments ran their own entrance examinations, with interviews, they could probably pick the few 'high fliers' (although psychologists maintain that interviews conducted by amateurs are useless); but when on average the number of applicants is at least ten times the number of places (x5 for UCCA choice and x2 for examination failures) individual examination is impracticable. Such statistical evidence as there is suggests that the correlation between A-level grade and degree class is positive but very weak; and since the applicants are already a selected group of about 20% of the age group, with complex selection criteria, further selection within this group is difficult. (Apart from intellectual ability, the selection of the 20% depends, amongst other things, on peer attitudes, parental attitudes, parental income, and the consequent ambitions of the individual.) Therefore a number of universities have adopted the policy that no students are admitted direct to the 'pass course' (the future technician engineers) but admissions are to the honours course with relegation to pass for those who prove unable to sustain the standard of the honours course. The discussion in this paper will be based on the assumption of this policy.

Educating the innovative engineer

Even within the 'innovative engineer' group there will be a considerable range of aptitudes, interests and consequent careers. But although the British system provides more individual care of students than do most others, it is not practicable to have as many distinct courses as there are students. Some compromise in course content is inevitable. (This is ruling out the unit course or 'cafeteria' system.)

A major problem is that of keeping the technological content of a university course reasonably up-to-date. From a fundamentalist view point this is not very important: the education which a student receives will have to set him up for a working lifetime of some forty years. Academics cannot foretell all the technological developments of the next forty years, so to a large extent they must teach fundamentals and leave it to graduates to continue their education, by reading and perhaps

'refresher' courses, and to re-interpret fundamentals in terms of the later developments in technology. An example of re-interpretation is that the development of waveguides, with longitudinal components of field, required the replacement of the over-simplified idea that "electromagnetic waves have fields transverse to the direction of propagation" by the more precise statement that "electromagnetic waves in free space are transverse, but in the neighbourhood of conductors the disposition of fields is governed by boundary conditions". Naturally courses should be kept reasonably up-to-date in technology. But apart from the general effort involved - e.g., the transition from thermionics to the solid state - one may have used a particular piece of technology to illustrate a particular principle and new technology will mean a search for a new illustration.

The technology is important to the technician engineer, but does it matter to the innovative engineer? The writer once complained to a former industrial colleague that an otherwise good book on communication did not contain any descriptions of hardware. He replied "Does it matter? We find we can design systems without reference to the hardware". Yet one must know the limits of the hardware: one could not design a satellite communication link without knowing what noise figures were attainable in the receivers and what radiated power to expect from the satellite. The low-noise capabilities of parametric amplifiers can either be introduced as part of a fundamental study, using the Manley-Rowe relationship, or merely stated as a fact.

When presenting Nyquist's formula for Johnson noise and noise figures, should one emphasise equipartition or the noise figures of current devices? A typical problem is how far one should teach solid-state physics. Most current devices can be explained in terms of band theory and Fermi level; but the Gunn diode requires an appreciation of effective mass, and who knows what the future will bring? On the other hand, does a graduate need to know all the detailed technology of m.o.s., c.m.o.s., n.m.o.s., v.m.o.s. as well as of s.o.s.* which introduces an important new angle? He ought at least to appreciate that devices of the m.o.s. family are in general

* s.o.s. stands for "silicon on sapphire"; and the sapphire substrate is chosen for its thermal conductivity, not for any electrical property.

* Hull has an enhanced course.

slower than bipolar devices and that the access time of r.a.m.s is now to be measured in nanoseconds: the idea of 1μs as a short time is as out of date as the 60 m.p.h. express train!

Mathematics

Mathematics often forms a practical barrier between the two types of courses. It is an interesting question whether British mathematics teaching is bad or mathematics forms an intellectual sieve of great discriminating power; but it is a fact that the mathematical content of honours degree courses in electrical/electronic engineering courses has tended to increase. Forty to fifty years ago the use of Heaviside's operational calculus was *avant garde*; today, the student is expected to use Laplace transforms at a fairly early stage. The digital computer is of course ubiquitous, sometimes in microprocessor form, and the trend towards digital handling of all data has made the z transform and the Fast Fourier transform essential tools. Autocorrelation (and cross correlation) are now familiar operations, and for some specializations one needs an acquaintance with Hadamard/Walsh functions and transform, a corner of group and field theory and now Fermions and Carmichael numbers (pseudo-primes). The engineer may need a nodding acquaintance with a far wider range of mathematics than is covered by any one academic mathematician. From the mathematician's point of view this 'nodding acquaintance' is nearer to technology than to a fundamental study; but from the engineer's point of view it is only the honours student (or graduate) who can be expected to take on so many new ideas. After all, mathematics is supposed to be the epitome of fundamental study, of universal application.

The 'tool kit'

But as far as engineering technology is concerned, the graduate should include in the 'tool kit' which he takes to his first job some up-to-date knowledge. (Without it, he would take a long time to earn the respect of the technicians on whom he will depend.) Most engineering honours courses now include a project, the successful completion of which requires a student to design and either construct or have constructed a specific piece of hardware. This requires some expertise in the handling of currently available devices and so contributes to the practical side of the 'tool kit'.

Educating the technician engineer

So much for the education of the honours graduate or innovative engineer, but what about the pass graduate or technician engineer? Clearly the one policy which is unsatisfactory is to allow the pass student to flounder in honours studies and award him a pass degree for a very poor performance in the honours examinations. The general principle is to take him out of the more mathematical and abstract courses and substitute partially with more practical

courses based on current technology. ('Partially' because the pass degree student generally cannot assimilate information as fast as the honours student can.) The lecturer who gives an honours course may be able to provide a 'mugs' guide' to the same subject: for example, one can give the bare fact that the radiation resistance of an aerial is proportional to $(h/\lambda)^2$ whereas for an honours course one would derive this from electromagnetic theory. One would need to supplement this with more descriptive material about current types of aerial.

Non engineering studies

The problem of fundamentals versus technology arises equally in the field of business studies and management which we are nowadays urged to include in the undergraduate curriculum. (There are really two branches, the one being finance and the other being largely personnel management.) There is no doubt that lack of either type of expertise can be disastrous: Rolls Royce is the best known example of lack of financial expertise, and it is probable that a significant number of strikes could be eliminated by wiser management. But in the larger firms these functions should be controlled by specialists; and if one takes the traditional I.E.E. view that the professional engineer starts on 90% technology and 10% administration, but in course of time reverses the proportions, then any graduate of honours or innovative pretensions should be able to acquire the appropriate skills when they are needed. It may be desirable to give undergraduates some exposure to these subjects by way of 'opening windows', but it is not necessary to treat them in depth. An exceptional case could be made out for the entrepreneur who founds his own business on some technological innovation, but one should not distort the main curriculum for the benefit of this exception! He must either learn fast or find a partner to look after the non-technical side of the business. The summary is that business topics should be taught on a technological rather than fundamental basis. (The meaning of 'fundamental' in this context was illustrated once by the sarcastic remark of a Professor of Economics to a Professor of Accounting: "You should not be teaching undergraduates the rules of accounting: you should be teaching them how to break the rules".)

The question of written (and spoken) communication has been left until last. It has recently been unfashionable to study language, particularly one's own language, fundamentally. The lack of inflections in English makes it particularly important to use a reasonable word order in order to establish the relationships between different parts of a sentence. (Though in the interest of emphasis, the present writer is prone to inverting the natural order of phrases on occasion.) Perhaps this should be regarded as the technological aspect of language, the fundamental aspects being linguistics and literature.

To summarize, the ancillary subjects


Professor Bell founded the Department of Electronic Engineering of the University of Hull in 1966 but retired in 1978. This article therefore presents his personal views, but in no way commits that Department. The importance of the subject has been enhanced by the publication of the report of the Finniston Committee on the Engineering Profession.

such as mathematics, language and business and management studies should certainly be taught as technology, but in professional topics there is a need to teach fundamentals, if only as an insurance against the effects of technological change during the following 40 years.

I believe that "engineering" is primarily an attitude of mind which may be hinted at by the phrase "enthusiasm for getting things done properly". This attitude of mind is not dependent on the academic and technical content of a course, enhanced or not, but it can be influenced by the way in which material is presented.

Since this was written, an article on "Training of Engineers in Japan" by H.A.J. Prentice has appeared in *Electronic and Power* (the Journal of the I.E.E.), April 1980, vol. 26, pp. 327-329. The attitude of Japanese industry appears to be an extreme case of the policy on industrial training which has been suggested above.

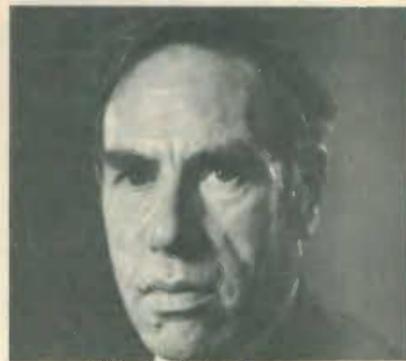This article is based on a paper presented at the conference on "Electronic Engineering in Degree Courses - Teaching for the 80's", Hull, 31st March to 3rd April 1980. Copies of the conference proceedings, covering all 43 papers, can be obtained from Mr K. A. Welsh, Department of Electronic Engineering, University of Hull, Hull HU6 7RX, price £12, plus post and packing (£1.25 in U.K.).



Professor David Bell, who joined the University of Hull in 1965 to set up its Department of Electronic Engineering, retired in September 1978. From 1949 to 1961 he was Reader in Electromagnetism in the electrical engineering department of Birmingham University, and thereafter till 1965 he was the director of AMF British Research Laboratory. He has contributed widely to the learned journals and has been writing for *Wireless World* throughout his career.

Multiphase low distortion oscillator

Sine wave generation with frequency independent amplitude control

by A. D. Ryder, M.A., Ph.D., F.I.E.E.

Linear oscillators, such as the well known Wien bridge, are easily constructed using op-amps, and have inherently low distortion provided the amplitude is kept within the linear range of the devices. The outputs are normally free from high-order harmonics, which can complicate the use of wave-shaping oscillators such as the 8038. This design is suitable for fixed or spot-frequency requirements, it will generate low-distortion signals of m phases where $m = 3, 5, 7$, etc. ($m = 2n + 1$) and, by adding inverters to the outputs, signals of $2m$ phases, i.e. 6, 10, 14, etc. The frequency range extends from zero to the limit of the op-amp characteristics.

The original application required a modulation source for multiple path f.m. of tone signals from an electronic organ, a technique used to enrich the sound by emulating a chorus of independent pipes. This requires frequencies down to 0.3Hz or below, ideally with some choice of frequency and modulation depth, i.e. oscillator amplitude. At such low frequencies a conventional thermal amplitude-control would need an intolerably long thermal time-constant to operate linearly. Unfortunately, the control-loop should introduce as little delay as possible because even a few extra oscillator cycles of settling time are inconvenient. This circuit is not frequency-dependent and, because it is repeatable, is preferable to thermal control even at high frequencies. The circuit in Fig. 1 comprises m stages, all identical except for the input connection of the first.

Each output phase P1 to P m has the same op-amp source resistance and voltage capability, and the phase balance depends primarily on the matching of R, R $_x$, and C. The simplest way to change frequency is by switching capacitors C. The vector diagram for the second stage, see Fig. 2, is typical. Feedback current p is the vector sum of $r = P2/R$ and $c = P2/X$, where X is the reactance of C, and the inverting connection maintains current p equal to the input current q , where $q = P1/R_x$. The stage gain is unity when

$$\sqrt{\frac{1}{R^2} + \frac{1}{X^2}} = \frac{1}{R_x} \text{ or } X = \frac{R}{\sqrt{R^2 + X^2}}$$

The stage produces a phase-shift of $180^\circ - \phi$ where $\tan \phi$ is equal to R/X (1), and the

condition for unity gain is $x = \cos \phi$ (2). From expression (1), $\tan \phi = 2\pi f RC$ or $f = \tan \phi / 2\pi RC$ (3). In a three-phase oscillator, each stage is required to produce unity gain at 120° phase-shift, $\phi = 60^\circ$, therefore $x = \cos 60^\circ = 1/2$. From (3), the corresponding frequency is $\sqrt{3}/2\pi RC$ or $0.276/RC$.

Because ϕ lies between 0 and 90° , the attainable shift per stage lies between 90° and 180° . To use five or more stages, the total loop phase-shift must be a multiple of 360° . The spoke diagram in Fig. 3 shows how this works for a 5-phase oscillator, $m = 5$, $n = 2$, where the phases are separated by 72° ($360^\circ/5$) but each stage generates 144° . In this case $x = \cos 36^\circ = 0.809$ and $f = 0.116/RC$. As $m = 2n + 1$, two steps of n phases will always produce an $(m - 1)$ shift around the diagram, and m such steps will visit all spokes. For m greater than 5 there may be more than one possible shift per stage, geometrically, within the 90 to 180° limits. For example, when $m = 7$, phase separation 51.4° , it is possible to visit either 102.8° in steps of two, or 154.2° in steps of three. However, it is necessary to design for the highest usable phase-shift, i.e. the mode for which the loop gain is highest, $360n/m^\circ$ per stage. The angle ϕ is then equal to half the phase separation. In general, the capacitive feedback discriminates against harmonics and, so far as d.c. is concerned, the loop feedback is negative because m is odd, which tends to stabilize the working point.

The oscillator loop is given 50% excess gain by making R_3 two-thirds of the basic value, which is offset by antiphase feedback via A_2 and R_4 . Amplifier A_2 is a multiplier, or a variable- μ device such as

the 3080, and its gain is controlled by the oscillation amplitude which is detected by a full-wave rectifier of two diodes per phase and differential amplifier A_1 . In the steady state, the balancing output of A_2 has $1/3$ of P m amplitude and just offsets the excess gain. The level at which the

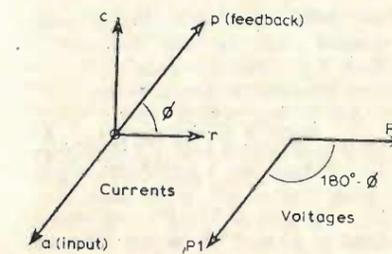


Fig. 2. Vector diagram for second oscillator stage.

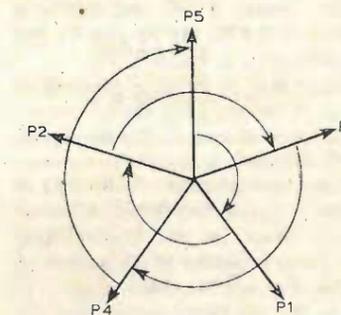


Fig. 3. Spoke diagram for a 5-phase oscillator, $m = 5$, $n = 2$. Phase separation is 72° and the sequence is P5-P3-P1-P4-P2.

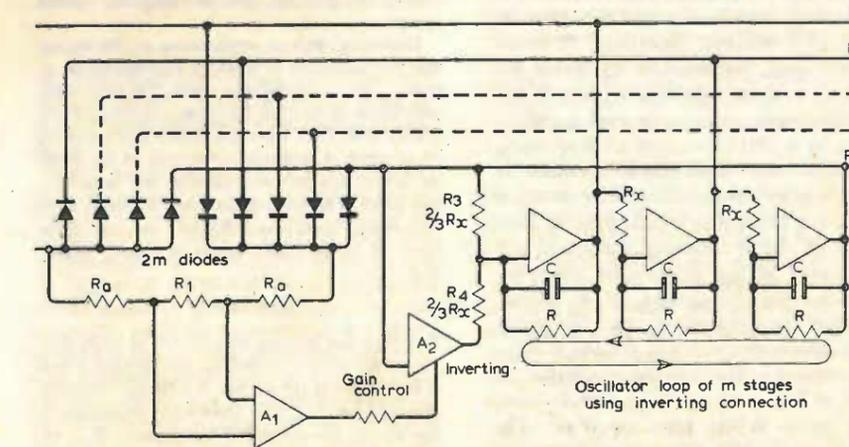


Fig. 1. Oscillator of m phases.

begin to end their serfdom to military/industrial empires, insisting that, instead, their knowledge and skills be applied to the task of making this planet a more congenial place. If they do not, they have at least the consolation that, unlike the physicists of Los Alamos, they will have scant opportunity for regret after their last great work has reached functional expression.

John G. McKenzie
Momieth
Dundee

Congratulations on your editorial in the November issue. It is gratifying to see that some people connected with electronic engineering are willing to make known their opinions on the matter of "defence". I only hope that your good example is contagious and that it spreads to others. Perhaps your editorial will help to make responsible people employed on "defence projects" reflect on the possible consequences of their endeavours.

It seems to me that governments are largely to blame for the excesses of the armaments industry in encouraging this trade. In fact the trade is referred to as one of Britain's successes in improving her balance of payments, GNP etc. Unfortunately the alternatives to the armaments industry do not appear to be so remunerative: witness medical electronics, medical research — it's a matter of demand presumably. Many other countries are guilty of the same crime. I feel that comments such as yours can only help here.

Incidentally, I am not a pacifist or keen on unilateral disarmament. I have been employed as an electronics technician since being trained by the Royal Air Force in the 1950s. Most of the work I have been connected with has been of a peaceful nature. I also usually vote Conservative, the concept of free enterprise being attractive.

B. Morton
Berkhamsted
Herts.

Please accept my warmest congratulations on a most courageous editorial in your November issue. I agree with every word; without the compliance and connivance of engineers the arms race would greatly diminish.

While reading about the candidates for reelection to the Council of the IERE in the latest journal I was interested to see how many worked for the military in one way or another and I wondered how much this is true of the whole Council and if the Institution is in the grip of the military-industrial complex. If this is so I see little hope of the Institution freeing itself from the self-perpetuating system you spoke of.

Wilfred Laycock
Abingdon
Oxfordshire.

Comment from the IERE

First, I would like to assure you that we are well aware of Mr Laycock's views on the merits of engineers who work in the military sphere of activity: we published one of his letters on this theme in the November 1979 issue of *The Radio and Electronic Engineer*. And second, concerning his thoughts on the occupations of the members of the IERE Council, I would suggest that he writes to me direct with some constructive comment when he has finished the 'wondering' he

The present 41-member Council of the IERE includes a retired air vice-marshal (the secretary), a brigadier, a colonel, a retired lieutenant-commander, a major-general, a Ministry of Defence director, a professor of the Royal Military College of Science and three senior engineers from companies well known in military electronics manufacturing. — Ed.

mentions in his second paragraph. No doubt by then he will be able to explain to me how he justifies his conclusion that the IERE is at present tied to "the self-perpetuating system you spoke of" in your editorial.

S. M. Davidson
Secretary, IERE
London WC1

THE "TWINS" PARADOX OF RELATIVITY.

The late Professor Dingle's simple question to the scientists (October issue) has never been answered because Special Relativity Theory (S.R.T.) is defended by the astute deployment of the proverbial red herrings.

S.R.T. speaks only of relative uniform straight line motion but the defenders of that faith invoke acceleration and gravity to account for the slower ageing of one of the twins. Please note that I am careful to avoid commitment as to which twin suffers what and for which reason; I have learned some lessons from the relativists.

It surely must be obvious to all that if the relative variation in the rate of clocks is to be justified by acceleration or gravity then that justification is tantamount to the admission that the clocks in pure S.R.T. (as taught in undergraduate texts) do not in fact run, physically, at different rates; they only appear to do so. That which applies to clocks must also stand true for measuring rods and mass, or so S.R.T. avers.

We are thus left with the fact, unpalatable though it may be, that all of the alleged experimental confirmations of S.R.T. are a result of accidental coincidence and not predictions of the theory at all.

Since Prof. Dingle did not himself provide an alternative explanation I now ask to be allowed to clean up the mess, an activity that is not without precedent in science. Let us start with mass.

In a letter in the November 1979 issue responding to Prof. Jennison's June 1979 article "What is an Electron", I postulated that mechanical force was radiation pressure and provided a completely new derivation of the Newtonian kinetic energy equation. As far as I am aware that derivation has been neither challenged nor refuted. In his article Prof. Jennison also used the radiation pressure of light as a mechanical force and I have not seen that factor of his argument questioned. Any refutation of either of these ideas must first, obviously, deny the experimental facts of radiation pressure.

In my derivation I allowed the effect of a force, related to a datum, to diminish linearly with the velocity of the affected mass between the limits zero and infinity. This accounted for the Newtonian view but in the real world the diminution occurs linearly between the limits zero and c .

We have two velocity contexts to contend with, that of real physical behaviour and that of our calculations. It is an unfortunate fact that our only method of measuring velocity happens to coincide with our calculations. Using a rigid measuring rod we can only measure velocities that are a fraction of the velocity scale zero to infinity because the measuring rod cannot of itself limit the distance that it might measure in unit time. It is linked firmly to the infinite scale of positive whole numbers and hence to our calculations. Knowing this we must say:

$$V.k = V$$

where on the left-hand side is behaviour, V as we measure and k the now experimentally deter-

mined Lorenz transform. This transform applies to the numerical ratio which we call velocity but *not* to its components.

We see just why M , L and T seem to be at variance with our velocity measurements and calculations. Using the equation it is possible to account for all of our experimental results leaving M , L and T invariant. It is interesting to note that Prof. Dingle himself expressed a fleeting doubt concerning the measurement of velocity in "Science at the Crossroads".

Finally, just to round things off, it is to be noted that if any of the justifications for the alleged null result of the Michelson and Morley experiment is true, then it must be concluded on grounds of pure logic that the experiment was a decisive demonstration of the existence of absolute space.

Alex Jones
Alderney
Channel Islands.

DOSIMETERS ADVERT

Your October issue included an advertisement by Dondene Ltd for dosimeters. The general information, principle and construction details are a word for word copy of our standard sales leaflet (copy enclosed). Furthermore, the sectional drawing has also been reproduced without our permission.

One of our staff purchased a dosimeter from Dondene. Briefly, it is of a different construction to that shown on the advertised drawing. The company that produced the purchased dosimeter ceased trading in this business some 15-20 years ago. The unit is not hermetically sealed and the charging mechanism is not compatible with available charging units.

R. A. Stephen is and has been for many years the UK's only designer and producer of dosimeters and we should like to make it clear that we are not in any way associated with this flip-pant advertisement.

R. W. Hawley
R.A. Stephen and Company Ltd
Mitcham
Surrey

DISPLACEMENT CURRENT

Dozens of people in this country, professors and Nobel Laureates, have gained financially from the subject of electromagnetic theory. Something is expected from them in return. It would be a great shame if Professor D. A. Bell, the only man among them who has bothered to contribute to the discussion in *Wireless World*, should suffer thereby. We should congratulate him for standing up to be counted.

Ivor Catt
St Albans
Herts.

AUDIO KITS

It is a long time since I have read such libellous piffle as that contained in the November letter from M. J. Evans on the subject of kits. It would appear that, through not having taken sufficient care when choosing his purchase, he is now publicly venting his spleen on all kit manufacturers and the kit-building public as well.

Mr Evans complains that the amplifier kit he bought was four times more powerful than he needed: it really is too bad of these wicked kit suppliers to let Mr Evans have the amplifier he ordered! He also complains that the kit took 100 per cent longer to build than he estimated: who got his estimate wrong then?

Certainly, the kit of which Mr Evans com-

plains was a bit of a rat's nest to build, but a photograph is included in that manufacturer's literature and it is up to the buyer to judge whether he wants to indulge in that kind of work. Should Mr Evans feel that any error of description was made, then his remedy is at law with the manufacturer concerned. If there is no error, then the fault must lie squarely on Mr Evans' shoulders.

Either way, the argument is a private one between an individual and a company and should not involve *Wireless World* or *Hi Fi News* readers, or other kit companies who give the public first-class products and designs. If Mr Evans' wish is purely to hurt the manufacturer with whom his argument lies, his missiles are a little tardy, since the offending kit became obsolete over a year ago, advertising was withdrawn from *Hi Fi News* before that, and he would now appear to be about to cease offering any hi-fi amplifier kits.

The further suggestion is made that the public should refrain from building anything so complex as a stereo amplifier. As a general principle, a good kit makes construction easier, provides a better standard of finish and design and has the additional benefit of a second group of engineers looking at the design in production terms after the circuit designer has finished with it. In the case of my company's products, careful design and attention to detail produces stereo amplifier kits that wouldn't cause a tea-drinking chimpanzee much trouble provided that he could read and hold a soldering iron! Stereo amplifiers are easy, Mr Evans, if you buy properly in the first place.

But is this public, of which Mr Evans is so dismissive, as incompetent as he suggests? Magazine readers have been building radio and electronic projects almost from the turn of the century. After the last war, people built television receivers from kits without the benefit of printed circuits: nowadays they build teletext decoders and microcomputers.

So please, Mr Evans, do not allow your silly vendetta to knock magazine readers and the trade which serves them: they are our future engineers, our customers and our friends and we do not like it. Without them, no magazine could exist and the world would be a poorer place.

A. H. Milligan
Hart Electronic Kits Ltd.
Oswestry

Having just given up, yet again, the construction of a disastrously bad "kit", I would like to add one or two observations to Mr Evans's letter in the November issue.

It would appear from the pages of the electronics press that there are kits available for almost any piece of apparatus you can imagine, supplied by an army of different manufacturers, if manufacturer is the right word. My own experience of kits has varied from the idiot-proof masterpiece of planning and instruction to the present bout of transistorised insanity. While I would disagree with Mr Evans's inclusion in his total costs of £300 plus for labour (surely he enjoys his hobby?), I object to the amount of rectification work that some kit suppliers subject us to.

The cassette deck kit which I am at present engaged upon should be held up to prospective manufacturers as an example of how not to go about it. The problems started before the kit even arrived, since I had sent my money with the order before I found out that no kits had actually been made at that time, and therefore, had a four month wait, at the end of which there appeared a half set of electronics with one p.c.b. missing. They still hadn't been made. Then the

case arrived. The advert in *W.W.* had painted glowing pictures of a beautiful satin anodised aluminium case with teak ends. What actually arrived were two pieces of pressed steel, stove enamelled battleship grey, with two pieces of Melamine covered chipboard, and no means of holding any of it together.

After a few irate phone calls, always taken by the shop assistant as the manager was never available, the remainder of the bits and the second p.c.b. arrived along with what can only be described as a few helpful clues as to the assembly procedure. I like to think of myself as resourceful, so on I went. The p.c.b. assemblies went together quite well, although some of the components were fiendishly difficult to identify, but the pile of spare resistors and capacitors left over at the end was a bit disconcerting. "What was missing?" I asked myself, and spent another hour deciding that they really were spare.

The hard part is still in progress. None of the mounting holes in the case is in the right position, the cassette transport has a record button but no switch mechanism, and the battleship grey is looking quite scarred by the attempts to make things fit. I now seem to be faced with either a transport which fits the case but can't be worked properly because it is too deeply recessed, or one that works but which won't allow the lid to fit.

The whole thing, excluding Mr Evans's £2 an hour labour charge, has so far cost me about £65. I noticed the other day in our local hi-fi shop a beautiful front-loading satin anodised cassette deck, with Dolby, and only £62!

My message is simple: if you are thinking of buying a kit (1) don't buy from anyone who is not well known for kits; (2) if a kit is advertised as being suitable for the experienced constructor, it is either too difficult for you or you could design a better one anyway; (3) wait a few months before you buy it, the chances of it arriving whole and with all the latest updates will be much higher; and (4) make sure you can't buy better and cheaper ready made.

Unless, of course, you enjoy your hobby!
P. B. Hodgson
Grantham
Lincs.

I think your correspondent M. J. Evans in the November issue is a little hard on kit suppliers and totally wrong in his opinion of those who buy them.

In recent years I have bought several kits from firms who advertise in this magazine. They have been at the least adequate mechanically, acceptable in appearance and used good quality components. I cannot say they have all been trouble-free initially but once commissioned have given reliable service and excellent performance. I have been building audio equipment since about 1947. In those days I used to buy all the components separately but today that is a very tedious task conveniently overcome by the kit.

People build their own equipment, I would have thought, largely out of the interest it gives them. To cost the time involved as if one would otherwise have been doing a paid job is, as with any other hobby, ludicrous. Does it matter if it takes 40 hours or 80 hours or as long as you enjoy taking? These people also, incidentally, usually finish up with a machine costing about half the price of a commercial unit of similar performance.

I do not think there are many people who will spend £100 or more on a kit if they do not either have confidence in their own ability or have ready access to competent assistance. Despite how some kits may be advertised it is extremely naive to think a sophisticated instrument can be

built from its individual components without some initial troubles. As your correspondent says, there are kits in which most of the assembly work is done to reduce this risk but to me that is little different from buying ready made equipment. But that is the point, the variety is there — you make the choice.


Finally, may I join the statistics "guessing game" even though I intend to cheat by using facts? From my own experience and that of colleagues the score is 100 per cent working and 100 per cent satisfied.

R. W. Hurst
Welwyn
Herts.

MULTISECTION TONE EQUALISER

I was interested to note that the authors of "Multisection Tone Equaliser" claimed that the equaliser was "primarily designed to cancel room resonances and equalise loudspeaker responses" (June/July 1980 issue). However, such a claim is rather a myth as an equaliser of the type described in the article is quite incapable of cancelling room modes even though many commercial units are now on the market bearing similar claims.

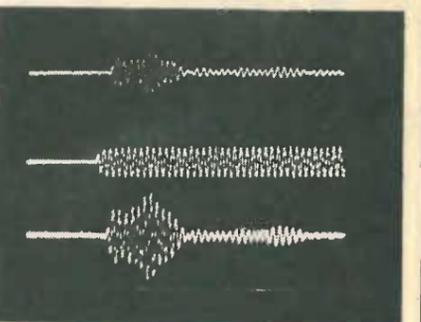The problem stems from a basic lack of understanding of the acoustics of listening rooms and the formation of standing waves and resonances. Standing waves/room resonances are in fact occurrences in the time domain which also manifest themselves as irregularities in the frequency domain, particularly when measured under the steady state conditions the electronics



Traces illustrating loudspeaker-room interaction with or without an equaliser. The middle trace is the input tone burst. At the bottom is the room response without an equaliser; at the top the response with an equaliser. Note how the equaliser fails to compensate for envelope distortion and hence timbre and character. (Timebase 20ms/div.)

and audio industries usually rely on. But when trying to equalise such frequency aberrations one is looking at the effect rather than the cause — and it is the cause, occurring in the time domain, which must be corrected for, rather than the symptom shown up in the frequency domain. Some recent investigations, reported elsewhere¹, clearly showed this. The investigations, using a number of commercially available units, showed that subjectively resonances could only be partially tamed — they certainly were not cancelled, as both oscilloscope and ear clearly testified.

Although the "loudness" of a resonance could be reduced with an equaliser, this is only half the story, as a resonance also affects the "attack" and "decay" of a note as well as its steady state response, and thus completely alters perceived timbre and character (see traces). The

equaliser, because of its mode of operation, just could not cope with such waveform distortions, which the ear clearly detected. The basic room resonance is still excited but at a lower level rather than true cancellation taking place.

Furthermore, the bandwidth of the equaliser filter circuits, unless very narrow, can also produce quite audible changes in the response at other frequencies. It was also noted that not all programme material excited room modes — but the equaliser filter is always in circuit, removing a "chunk" of the signal when not required to do so.

One possible solution to the problem might be to use a series of extremely narrow-band filters precisely tuned to the frequencies of the worst room resonances—apart from requiring a number of high Q tunable filters with their attendant phase shift problems in a stereo set up, this method still does not attack the problem in the right way. Compensation must take place in the time domain (3 dimensional) if room resonances are to be successfully "cancelled".

Peter Mapp
Department of Electrical Engineering Science
University of Essex.

Reference

1. Mapp, P.A., Graphic Equalisers Myth or Magic? *Hi-fi for Pleasure*, October 1980.

THE FLOATING BRIDGE

In his two articles on bridge amplifiers (September and October issues) Mr Brady presents many stimulating circuit ideas and practical suggestions. His analysis of the circuits is, however, presented mainly in the form of a plausibility argument and he leaves the potential designer without the necessary analytical tools. It is evident from the article that Mr Brady has carried out a small signal analysis of the circuits; perhaps this is not reproduced because of the obscurity lent by his choice of circuit representation. I believe I can improve on this.

The diagrams repeatedly include an amplifier symbol with its output connected to signal earth (Fig. 1). By this Mr Brady means that, since the power supply is left floating with respect to signal earth, this amplifier causes the signal which would have appeared at its output to appear inverted at the power supply lines A, B, C. Let us draw this explicitly (Fig. 2). In Fig 2 the amplifier behaves the way one is normally entitled to expect from this symbol. Its output voltage with respect to signal earth is proportional to the differential input voltage. Two important features of Fig. 2 are: (1) the inverting and non-inverting inputs have (apparently) been exchanged; (2) the relationship of the power supply to ground is explicit.

Terminals A, B, and C are equivalent in a small signal analysis where we may properly expect to ignore power supplies. The voltage swings available at the final output terminals can be determined later from the practical circuit diagram of the bridge output stages without the complication of including signal paths.

Finally, to demonstrate the utility of this transformation, I have re-drawn Fig 1 of the first article as my Fig 3. This circuit is amenable to the kind of analysis we all know and love. For the first amplifier we have:

$$\frac{V_i - \Delta V_1}{R_1 + 1/j\omega C_1} + \frac{y - \Delta V_1}{R_2} = 0 \quad (1)$$

$$V_A = G_1 \Delta V_1 \quad (2)$$

If we assume that the loop gain through both

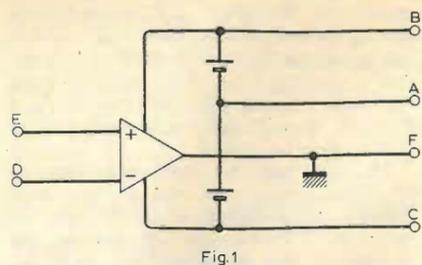


Fig. 1

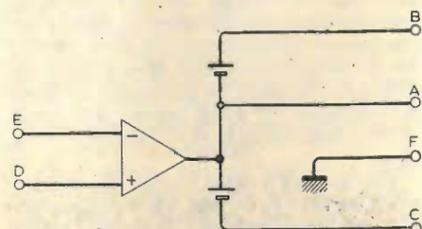


Fig. 2

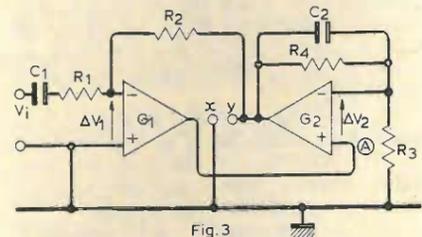


Fig. 3

amplifiers $y \rightarrow A \rightarrow y$ is negative so as to maintain stability and that G_1 is very large so that $\Delta V_1 \rightarrow 0$ (by equation (2)), we have:

$$\frac{V_i}{R_1 + 1/j\omega C_1} + \frac{y}{R_2} = 0 \quad (3)$$

and hence the gain of the total amplifier, which is insensitive to the nature of G_2 , the gain of the second amplifier. This justifies Mr Brady's comments about the relative quality of A_1 and A_2 at the top of page 42 of the first article.

J. Allen
Cheltenham
Glos.

The author replies:

The reason for the inclusion of an earth in the position shown in the article (e.g. my Fig. 1) is that in a simple design the input may be with respect to earth, which has great convenience. (If a 'change-of-origin' is included this is of course not necessary.)

I think Mr Allen's Fig. 3 will not work, for two reasons. First, where is the power supply? In his Fig. 2 the power supply has A as mid-point. If this is intended for Fig. 3, then when G_1 is driving current, the closed path is from the supply, through G_1 , into A, through the battery and back into the amplifier — which path does not drive current through the output at all.

Perhaps Mr Allen intends some other power supply arrangement.

Ignoring this problem, then the feedback loop controlling the G_1 in his Fig. 3 includes the characteristics of G_2 . Though there is negative feedback, the open-loop gain will be some horrendous problem to calculate unless the G_2 is of good-quality design. The two amplifiers are coupled together in this way — which the original design hoped to avoid.

R. M. Brady
Trinity College
Cambridge

DISPLACEMENT CURRENT

In order to avoid any suggestion of 'increasing the noise level' in this seemingly interminable correspondence (November letters) I will limit myself to one fact, one question and one comment.

(1) The fact. My reference to Hobbes' *Leviathan* was correct. I noticed it in 1943 and verified it in 1978.

(2) The question. A body continues in motion or at rest unless disturbed by some force. Electromagnetic radiation has momentum, so once launched it appears to behave according to Newtonian mechanics. If there be 'energy current' what force accelerates it (instantaneously?) to the velocity of light?

(3) The comment. L.H. Higgins says in November letters that Catt, Davidson and Walton "only need to define what they mean by energy current". But so far they have not done so and I do not believe they can.

D.A. Bell
Beverley, Yorkshire

PARALLEL TRACKING PICKUP ARM

I have just completed Rod Cooper's parallel-tracking arm system, as described in your December 1979 and January 1980 issues. It works beautifully and it is quite fascinating to watch the drive system adjusting the tracking speed of the arm. I used a Swiss made micro-motor with a 54:1 reduction gearbox in place of the suggested drive system as I was not very enthusiastic over the cross drive and dual belts, which would need rather careful assembly.

I do not know whether any of your readers actually managed to assemble the whole thing in the suggested 40 hours! I used the components already machined by the supplier (J. Biles), but found that a lathe and milling machine in my home workshop were needed for some operations, such as the forming of the nylon sliding block, motor pulley, cartridge clamp, etc.

Now that it is hardly worth attempting construction of home radio and hi-fi equipment it is very helpful to find designs such as this, and the conjunction of electronic and mechanical elements adds greatly to the interest of the project.

Frank Gutteridge
Corsier, Switzerland

P.R.B.S. GENERATORS.

Further to my letter (September) and the replies (November) concerning p.r.b.s. generators, may I thank Mr Hall and Dr Thackeray for their comments? The reference to Golomb is particularly useful.

The details I originally described were side products of some unrelated programming I was investigating on a Z80 system, and I must admit I did not delve deeply into the subject. I found no positive analysis, so I performed the negative one presented.

I have satisfied myself that generators a multiple of eight elements long do not produce the full sequence when simple feedback is used, but I have not found a reason for it (yet). Accordingly I have altered my Z80 routine, which I do not present here as it forms an interesting machine code exercise. The sequence previously produced was so long that I never noticed that it was shorter than expected.

Incidentally, a number of degenerate values for 'a' slipped into my table. Readers may find it instructive to locate them.

K. Wood
Ipswich, Suffolk

fact:
the SM63 looks
(and sounds) great
in front of people...
and cameras!



SM63
Omnidirectional
Dynamic
Microphone
(actual size)

Take it from the professionals

A top quality Shure microphone makes a measurable difference in upgrading sound. Now, Shure has added a new microphone designed to upgrade the appearance of your act, as well as the sound. The SM63 is a top-quality omnidirectional microphone with high output and clear, crisp sound quality — an innovative blending of smaller size, handsome appearance, and truly noteworthy broadcast-quality performance. Highly effective pop protection, low handling noise and very low profile (so it won't obscure the performer's face) make it the perfect choice for on-camera applications. The SM63 omnidirectional dynamic microphone measures just 5 11/16 in. long, 1 1/4 in. in diameter and weighs only 2.8 ounces with no compromise in Shure's standard of reliability. It offers twice the voltage sensitivity of our own SM61 (6 dB) and features a humbucking coil for superior rejection of electromagnetic hum (up to 20 dB better than competitive units) and an elastomer isolation shock mount for minimized handling noise. The new SM63 also features the Shure-developed VERAFLX® dent resistant grille and a smooth satin finish perfect for on-stage and on-camera applications. Send for complete literature on all Shure professional microphones — including the new SM63. (Please let us know your microphone application.)

SPECIFICATIONS


Frequency Response: 50 to 20,000 Hz
Polar Pattern: Omnidirectional
Impedance: 150 ohms
Output Level (at 1,000 Hz): Open Circuit Voltage (0db = 1 volt per microbar) —76.0db (0.16mV) Power Level (0db = 1 milliwatt per 10 microbars) —56.5db
Hum Pickup (typical at 60Hz): 13 db equivalent SPL in 1 millioersted field
Shock Mount: Patented internal vibration isolator
Case: Champagne finish aluminium with VERAFLX® grille
Dimensions and weight: 5 11/16 in. long, 1 1/4 in. in diameter; 2.8 ounces

professional microphones...by

SHURE

Shure Electronics Limited, Eccleston Road, Maidstone ME15 6AU — Telephone: Maidstone (0622) 59881

WW — 019 FOR FURTHER DETAILS

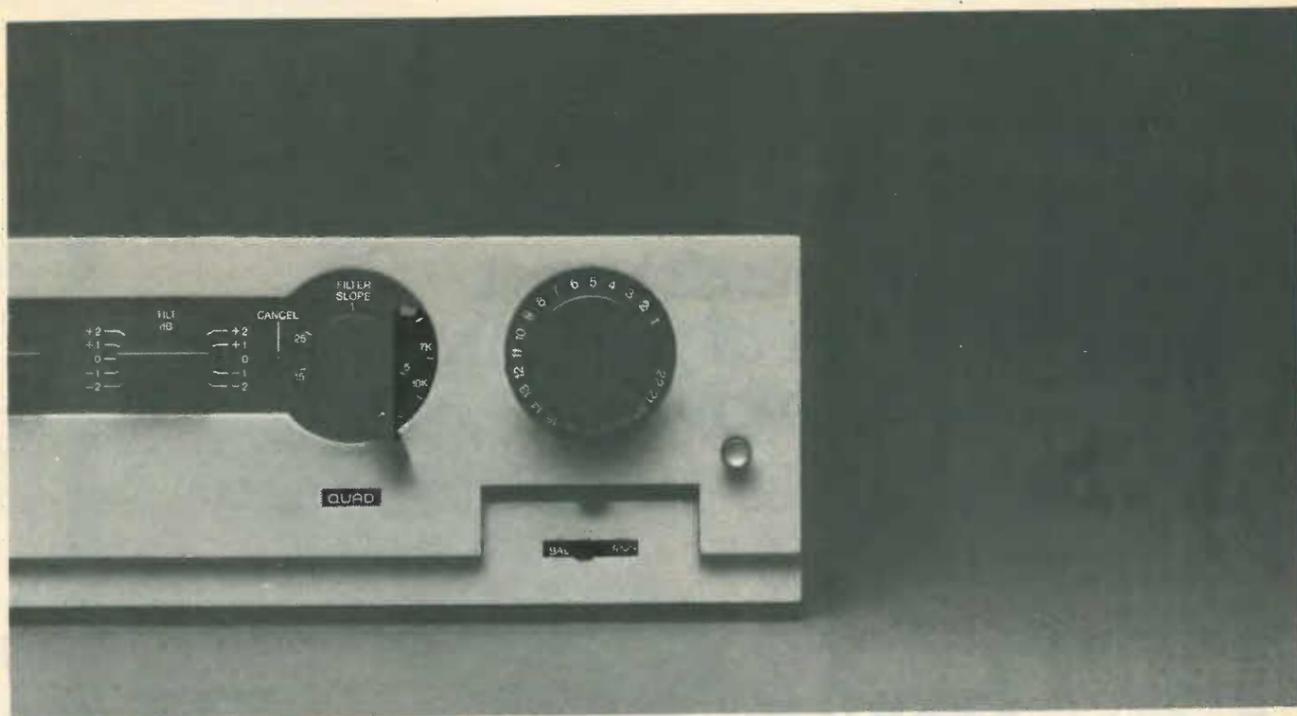

If everything were perfect...

Tilt, nothing to do with pinball wizardry, has a great deal to do with programme balance.

The recording or broadcast engineer attempts to capture the ambience of the studio or concert hall but what the listener perceives is the aggregate of this and the reverberation characteristics of his listening room.

If all listening rooms were equal the engineer could make due allowance, but since some listening rooms are more equal than others, the engineer has to assume some arbitrary norm, and the chances are that further correction and compensation will give improved results. Thus a reverberant recording reproduced in a 'live' listening room will sound overbright and a dry recording reproduced in an overdamped or 'dead' room will sound dull and bass heavy.

The tilt control on the Quad 44 cannot alter the reverberation characteristics of your room but by gently sloping the frequency response of your

system about a centre point, chosen to maintain a constant overall subjective level, it can produce a more natural programme balance, without introducing unwanted colouration.

If you are in any doubt that the listening room characteristics have a fundamental effect upon the final results try listening to the same record played on the same equipment in two different rooms.

To learn all about the Quad 44 write or telephone for a leaflet.

The Acoustical Manufacturing Co. Ltd., Huntingdon PE18 7DB.
Telephone: (0480) 52561.

QUAD

for the closest approach
to the original sound

QUAD is a registered trade mark.



WW - 025 FOR FURTHER DETAILS

Artificial intelligence

Computing techniques adapted for use in intelligent machines

by Malcolm Peltu

One British pioneer thinks that the most important use of artificial intelligence will be to save us all from the havoc likely to be caused by too much reliance on computers. Be that as it may, there is already a growing body of AI work on more specific problems such as in robotics, speech understanding, visual perception, automating reasoning procedures, understanding natural languages and man-machine communication. This article first takes a look at the history and politics of the subject in Britain then, through examples of research in computational vision, speech understanding and man-machine communication, gives an insight into the general nature of this developing cousin of computer science.

Computers were an essential aid to putting men on the moon; yet a small step for a man, like crossing a busy road, is still a giant and unbridged step for a computer. Computers can store vast libraries of information and play a pretty good game of chess; but no machine can match the ability of a child to learn a language or read a picture book. The ability of computers to perform many complex tasks, although they have immense difficulty in doing what comes naturally to humans, raises important and intriguing questions about the nature of human intelligence and the limits of machine or 'artificial' intelligence.

The techniques of computer science which underpin modern applications of computing power are based on mathematical and logical methods of analysing system functions and translating them into sequences of detailed instructions which program the computer into performing a pre-defined task. In the 1950s a new breed of computer scientist began to emerge — the artificial intelligentsia. Whereas conventional computer science was primarily concerned with tackling information processing tasks that could be analysed into clearly defined and unambiguous programs, the new subject of artificial intelligence (AI) was starting to explore the ambiguities and uncertainties involved in trying to understand the principles, and building working models, of intelligent behaviour.

For the past 25 years or so there has been a running battle between computer scientists and AI researchers, with the traditional computer specialists often com-

plaining that AI is too vague a subject to be regarded as a coherent discipline and that the artificial intelligentsia are a rather dilettante lot, drawing off valuable research resources from mainstream computing. There is, however, a growing and impressive body of AI work covering such diverse areas as robotics, speech understanding, visual perception, automating human reasoning procedures, understanding natural human languages, improving the methods used for communicating between people and machines — and for playing 'intelligent' games like chess.

One of Britain's most distinguished AI pioneers believes that the most important contribution from AI will eventually be to help save mankind from the havoc that could be caused by increased reliance on that potentially Frankensteinian invention, the digital computer. Professor Donald Michie, head of the Machine Intelligence Unit at Edinburgh University, thinks that AI can open a "human window" onto the way computers reach decisions which have a direct impact on human safety and prosperity. The Three

Mile Island nuclear incident in 1979, for example, nearly became a horrifying disaster because the operator could not "understand" the myriad of warning messages provided by the computer-controlled monitoring system. And last year the world was twice brought to the brink of a nuclear war because of computer failures in the US defence network.

If that nuclear war alert had gone as far as reaching the President, how could he have interrogated the computer to find out the validity of its warning? asks Professor Michie. Computer science, he says, has produced complex information processing machines which perform calculations and search through information at such speeds that it is often difficult, if not impossible, for humans to trace back the 'thought' processes used by the computer to reach a particular conclusion.

As AI is concerned as much with human intelligence and understanding as with computer processes Professor Michie believes that its development of what are known as *expert systems* will make computer systems more understandable by forcing designers of automation equipment to fit the machine procedures into "the human mental mould." When you remember that computers are already relied on for controlling the operation of and diagnosing faults in tasks such as air traffic control, factory automation, medical analysis and building environment control, as well as nuclear power stations and national defence systems, the importance of opening such a human window should not be underestimated.

Yet, in the UK at least, computer scientists continue to cast doubt on the validity of AI's right to exist as a research area in its own right and even on the integrity of some AI practitioners. Last September at an international seminar of computer scientists at Newcastle University sponsored by the computer manufacturer IBM, the scepticism of British and some European computer scientists to AI was evident, despite the presentation by speaker after speaker of an impressive body of research work in this field. It appeared that each concrete advance in AI, such as speech understanding by computers or automatic recognition of visual scenes, was regarded by the sceptics as an example of computer science, rather than AI. The scepticism culminated in an acid after-dinner speech at the end of the conference by Professor Euan Page, vice chan-



In robotics AI systems are needed for recognising objects. This mobile robot developed at Warwick University has sensory equipment enabling it to avoid obstacles and to seek out, approach and grasp an object such as the plastic bin shown.

cellor of Reading University and former head of the Newcastle computing laboratory. Although he accepted that some specific progress had been made, Professor Page still chose to turn to Roger's Thesaurus to point out that 'artificial' is a synonym for words such as "bogus, phoney, pseudo, meretricious and flash." He also blamed AI for creating the public fear of Big Brother computers and scare stories about incorrect computer gas bills because the artificial intelligentsia had given birth to the notion of super-intelligent machines that will control the world.

This kind of petty bickering would be of only passing interest in the cloistered halls of academia if it did not reflect an attitude which has contributed significantly to Britain's low level of advanced industrial automation. In 1972, applied mathematician and now vice-chancellor of University College, London, Sir James Lighthill was called in by the Science Research Council to look at AI, primarily because many computer scientists were worried that this dubious new subject was siphoning off funds that they should have been receiving. According to one computer scientist who was on the Council at the time, the real aim of the Lighthill report was "to do a hatchet job on AI."

Although his report said there was some signs of progress in aspects of what has been called AI (such as advanced automation), Sir James was generally dismissive of AI claims. As a result, AI funding — and in its wake robotics research which had been tarred with the AI brush — was drastically cut back, although in the early 1970s British research workers, such as Professor Wilf Hegginbotham at Nottingham University and Professor Michie at Edinburgh were in the forefront of developments. For almost a decade, according to Dr Mike Larcombe of Warwick University, a leading member of the British Robot Association, this "neglect and persecution" of AI and robotics work almost threw Britain out of the advanced automation race, the flag being carried by a few individuals and groups operating in a fragmented, unco-ordinated way. Earlier this year, however, the Science Research Council decided to invest £2.5 million over three years in industrial robotics research. According to Dr Larcombe this money came at the eleventh hour for the hardy band of research workers, like himself, who had struggled on in the 1970s. Otherwise the temptations of the more enthusiastic and plentiful environment of the US would have drawn the last life blood out of robotics research in Britain. In the US, AI is generally accepted as an important aspect of computer-related developments.

Dr Larcombe pointed out that in Britain it was the robot research academics who have lead the way in creating an awareness of and involvement in advanced industrial automation whereas there was, until recently, "a general level of ignorance in British industry" about the importance of automation. Although grateful for the new research funds for robots, he is cautious about the way the funds have been tied to



Fig. 1. A noisy visual scene, which can be interpreted by the human eye and brain with the aid of a large stored set of patterns. (If you can't see what the picture shows, refer to the main text.)

creating partnerships for research projects with industry. As British industry starts from such a backward international position, he fears that the aims of the projects funded in this way will be to catch up with past neglect rather than to forge ahead into new areas, such as mobile robots, which is his main interest.

Computational vision

The cold AI climate that set in after the Lighthill report did drive many researchers away from the UK. One of those was Dr Harry Barrow who worked on the Freddy project at Edinburgh University in the early 1970s. This was one of the first attempts to produce a robot that could see and intelligently manipulate objects. It had started to show inklings of success when the Lighthill blight fell. Now, robots that can see are recognised as one of the most significant advances in automation.

Dr Barrow went to the US and is currently working at the AI Centre at SRI International on computational vision. The attempt to give computers 'eyes', 'ears' and 'voices' has typified one stream of AI research which mixes analyses of physical and sensory properties with attempts to understand how people make sense out of a host of stimuli. The other main strain of AI work is concerned with purely 'intellectual' questions, such as natural language communications and the process of human reasoning. Dr Barrow described at Newcastle one of the most advanced artificial vision systems, called Hawkeye. US Defence and Highways Departments are thinking of using it to draw maps automatically and to monitor traffic flows. Using a television camera and a

video processing system which translates images into a digital code that can be fed into computers, Hawkeye is capable, for example, of recognising and counting ships going into and out of a harbour or vehicles on a road.

To a human being this is not a difficult task. For a computer, however, there are two main problems. First, it has to analyse a scene into quantifiable factors that could subsequently be used in interpreting the nature of the images, such as the length and position of boundaries between objects, illumination, reflectance and surface orientation of areas within the scene. And then it has to make sense out of that scene. There is an enormous amount of information in a given scene. A typical colour tv picture, for example, requires about 1Mbit of information to be transmitted in digital form. With computational vision, a scene is broken down into pixels (picture elements), with values being assigned at each point for a predetermined set of qualities, such as luminance and reflectance. A typical picture analysed by Hawkeye has about 2,000 to 4,000 pixels.

The problems that could be encountered in interpreting a picture are indicated in Fig. 1, which is a noisy visual scene in which it is difficult to pick out any meaningful shapes or objects. Somehow, however, the human eye and brain can detect that it is a spotted dog drinking water in a stone-strewn street (provided the picture is presented the right way up). To a computer, of course, it would be a meaningless jumble of black and white splodges. The aim of AI is to crack the mystery of how intelligent people can extract sense from such an apparently

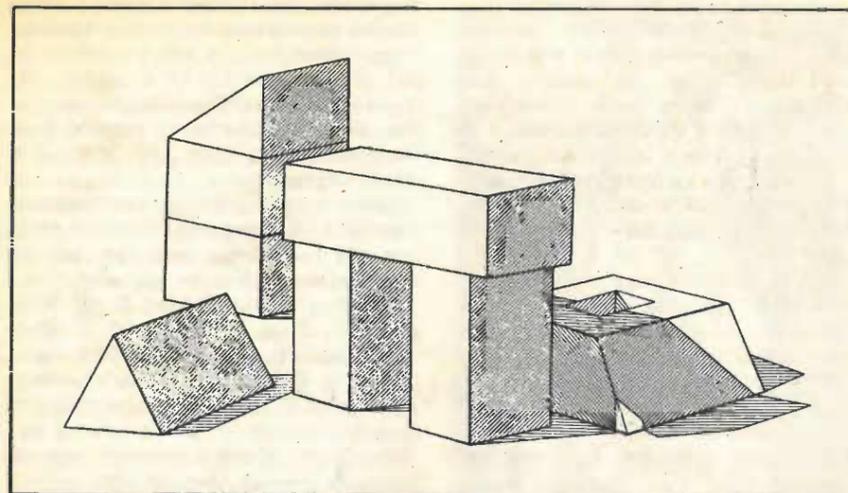


Fig. 2. A line drawing correctly interpreted by David Waltz's program for computer vision.

meaningless visual 'noise'.

According to Professor Michie, "The rate of input of visual information to the higher centres of the brain is not great enough to do more than give hints and prompts." From these partial stimuli, the brain constructs meaning, he says, from a large repertoire of stored 'models' of the real world held in the brain's memory.

The earliest AI experiments in vision, such as the Freddy robot at Edinburgh, reduced noise by being limited to simple 'block worlds' in which the only objects had simple, straight-line edges. The main task in the low level (noise reducing) analysis was to find, trace and segment boundaries defining homogeneous areas — in other words, to find the edges of blocks.

Even in a simple block world with a limited number of objects and specially lit to avoid shadows, this was a difficult task; for example, when blocks partially obscure each other so that the computer has to try to build up images of whole three dimensional objects from two-dimensional line drawings in which the edges of one block might be obscured in many places by other blocks. Any one object also obviously has different shapes when viewed from different angles. David Waltz of the University of Illinois developed a sophisticated computer vision system which could use lines (see Fig.2) to represent not only the edges of objects but also shadows, cracks and other physical attributes.

A great deal was learnt from working in the block world, although it was clearly too restricted to be of much use in a real world of irregularly-shaped objects which can be brought to the eye from an infinite number of view-points. Yet Hawkeye, which 'looks' into just such a variable real world, still employs similar basic principles in abstracting information from the noisy picture, although the interpretation is far more complex and subtle than just producing a two-dimensional frame representation.

An important problem at the low level end of sensory analysis is the speed with which information can be processed. Given that a visual scene could contain many thousands of picture elements with

many different measurements needed at each element, it is clear that the computer should be able to perform calculations on all elements very quickly. Traditionally, however, computers have been able to process information serially, i.e. only one calculation can be performed at a time. This has been satisfactory for most commercial and industrial data processing needs because the speeds of the processors (performing hundreds of thousands or even millions of instructions per second) have been satisfactory. Recently, however, new types of array processors have been developed. These consist of a network of many little processors which can operate independently of each other but within a co-ordinated plan. This technique is ideal for computational vision tasks which require the parallel processing of a variety of information.

Michael Duff at University College, London has developed a special computer language for the Clip-2 parallel array processor which is capable of carrying out low-level image analysis far more efficiently than by other means.

The professor of electronics at Brunel University, Igor Aleksander, is developing a pattern-recognition machine which exploits the recent availability of low cost microelectronics memory chips to store information. His machine will have a network of such memory chips, each of which contains a key piece of information that will be used to identify, say, an object in a scene. It will accept tv quality pictures as input; as the picture comes in, it will be analysed and compared with the 'keys' in the memory chips. The chips communicate with each other to indicate whether or not they have identified the object or an aspect of the object. Professor Aleksander believes that such a system is similar to the neural structures in the brain, where memories and information in the brain are linked by association in order to identify people, images, letters of the alphabet, etc.

The Hawkeye system, however, does not rely on any new types of computer processor. It also does not attempt to be totally automated and is designed to operate in interaction with people who can

help to supplement its intelligence. Hawkeye contains a computerised library of images relating to geometric and topological data found in the environment being viewed. It also contains 'intelligence' information needed to make sense out of the images, such as the fact that roads and rivers run under bridges, that buildings stand vertically or that, say, in a view of a dock area, ships move on the sea area and different types of ship have particular characteristics. Like most current AI developments, Hawkeye does not attempt to be a general purpose intelligence capable of instantaneous adaptation to any environment. For each task it is doing, it has to be given information about that particular slice of the world and it is intelligent only with that slice of life.

Much of the criticism levelled at AI in the past was aimed at some rather silly claims made by pioneer artificial intelligentsia, such as a statement by Herbert Simon and Allen Newell of the Carnegie-Mellon University in Pittsburgh in 1958 that: "There are now, in the world, machines that think, that learn and that create. Moreover, their ability to do things is going to increase rapidly until — in the visible future — the range of problems they can handle will be co-extensive with the range to which the human mind has been applied." This idea of the universal robot is still a long, long way over the horizon. But within particular areas — domains is the AI jargon word — machine intelligence is indeed flourishing. Given its library of background information and a simple language with which to communicate with an operator, Hawkeye is already able to automatically produce primitive maps, provided it is given guidelines, such as indications of landmarks near a road. It is also beginning to be able to monitor chip movements in the San Francisco Bay docks and motor traffic on a highway in California. It can answer questions like "What is this building?" and "How high is it?" when the user points to a particular part of an image with a special pointer.

Future work in computational vision is likely to develop the themes started in those early block worlds and now being developed in systems like Hawkeye. On the one hand, there is a lot of work going into low level analysis of sensory input to determine the appearance of the image and array processors could play a significant role in this. At the other end there is work into psychological understanding of human perception. In the middle, the AI expert 'engineer' is trying to produce working models of machines that can 'see'. In industry, the most obvious need is for robots that can recognise objects but, as Hawkeye has shown, computational vision has many other potential benefits.

Speech understanding

Speech understanding — computer 'ears' — poses a similar type of problem as computational vision. Brian Pay of the mar/computer research team at the National Physical Laboratory, Teddington, has said, "People are extremely inefficient at

speech recognition but brilliant at speech understanding."

Speech recognition is concerned with the receipt of aural stimuli and interpretation into sounds, words and sentences. This is equivalent to the low level visual analysis and is often literally a noisy jumble. At a party, for example, a person will be bombarded with a jumble of voices and noises yet is capable of picking out and understanding particular voices and conversations. Computer speech understanding started with low level speech recognition. There have been systems on the market for about a decade which can be trained to recognise individual words spoken in isolation by the person who trained the machine. When the computer is being trained, the operator repeats a set of words to the machine. The voice patterns of the operator for each word are analysed and stored. When the operator speaks them in a working situation, the input pattern is matched against those in the computer memory and, if found, the appropriate word is 'understood' and the computer responds accordingly.

The more difficult task which is only just beginning to be overcome is continuous speech understanding, where the computer can understand a stream of words spoken naturally. This is extremely difficult. At the physical level it is a complex task to identify particular words because people do not enunciate words clearly and crisply, words merge into each other, people swallow the ends of words and sentences, miss out words, etc. But even if the words are identified, the human processes of making sense out of them is still insufficiently understood, as with finding meaning in visual images.



Portable "turtle" drawing device built by the Department of Artificial Intelligence at Edinburgh University. It comprises a press-button box, a microprocessor and a mobile robot. The microprocessor runs a sub-set of the LOGO programming language. Each button on the box corresponds to a language instruction: for example, the "forward" button moves the turtle forward when given a numerical input for distance; the "right" button turns it on the spot clockwise when given a numerical input in degrees of rotation. The turtle carries a drawing pen and can leave a trace of its movement path - that is, it can make a line drawing. It is used to teach basic programming ideas to children and adult novices, using drawing as the context. With the device they can write programs for drawing simple regular shapes.

AI research has tackled the problem by analysing linguistic components, such as grammatical structures, syntax and other speech characteristics. In addition, the machine needs to be given information about the nature of the world in which it is functioning to help it understand speech, just as a centre forward at a football match would interpret the command "shoot!" in a different way from somebody at a rifle range.

Those continuous speech understanding computers that have begun to emerge from the research laboratories operate within clearly defined domains but they show sufficient progress to indicate that there is no insuperable barrier, although at present they are limited and slow. IBM, for example, has developed an automatic equipment which can understand words spoken from a vocabulary of the 1,000 most used words taken from words and sentences used by lawyers in submitting US patent applications in laser technology. Although it can recognise words with a 91 per cent accuracy and type them out automatically, a 30 second burst of speech takes about 100 minutes before it is typed out.

Computer controlled speech synthesizers

Although computers find it difficult to see or hear no evil (or anything at all), they find it relatively easy to speak. Ironically, the ability to talk is the main capability which seems to make computers intelligent, yet automatic speech requires relatively little intelligence compared with other AI tasks. Electronic sound synthesizers have been around for a long time and it is now

easy to generate an artificial voice. It is also possible to store recorded human speech in computerised form. A data base of words and phrases recorded by a person can therefore be stored in a computer and can then be joined together to respond to a particular enquiry under the control of a computer program.

Many companies already use computer controlled voice response systems to automatically answer enquiries and requests from dealers, salesmen and customers. The computer-based System X telephone exchanges being introduced by the Post Office (see News, November 1980 issue, p.52) will also use automatic voice response based on human speech recording to provide a variety of new automated services. There is also a growing range of consumer products that can 'speak', from the Texas Instruments Speak and Spell educational aid and an automatic language translator to cookers and ovens. From a computer programming point of view, however, voice output is no more difficult than putting out information in any other form.

The main problem with speech reproduction is making the artificial response sound natural. With synthesized speech this is difficult because voice quality is dependent on the physiological characteristics of the throat and breathing. When recorded voices are used, the problem is overcoming artificial pauses between words or phrases when they are 'spliced' together to form a particular response and to allow for the same word having a different emphasis or inflexion depending on its context in a sentence. This is being tackled more through patient study of human psychology and perception than by any technical breakthrough.

Man-machine communication

One of the important reasons for wanting computers to see, speak and listen is to assist in communication between people and computers. At present this communication typically takes place through a visual display unit. The information is keyed in and responses are presented on the screen. Although the words used in such a dialogue may be English, the 'language' available for the communication is usually extremely limited and inflexible - an error can be caused if a full stop is missed out in some cases or if a word is even slightly misspelt.

A vital area of AI research has been into natural language communication which allows all the flexibility and natural dialogue characteristics of ordinary human interaction. This is essentially a subset of the task being tackled with speech understanding systems except that there is no problem about recognising the words being put in. The question is how to understand the meaning of a sentence. Once again, AI work in this field is taking place within an acceptance of the need for defined domains. Typical person/computer dialogue systems assume a basic 'script' or 'scenario'. This typifies the particular interaction taking place in which there is a

certain number of objects and ideas being discussed and a particular pattern to the discussion, such as a doctor/patient relationship.

A milestone in natural language systems was a doctoral thesis in 1971 by Terry Winograd at the Massachusetts Institute of Technology. It was rooted in the block world that was then an intrinsic part of AI, robotics and computational vision work. The Winograd program displayed a block world scene on a screen containing a variety of blocks each with its colour printed on it as a word, together with a simulated robot arm. The user could then ask the 'robot' to carry out a variety of tasks in a natural language dialogue (see Fig.3). Here are some excerpts from a dialogue between a person and a simulated robot operating on such a set of toy blocks:

Person: How many blocks are not in the box?

Computer: Four of them.

Person: Is at least one of them narrower than the one which I told you to pick up?

Computer: Yes, the red cube.

Person: Can a pyramid be supported by a pyramid?

Computer: I don't know.

Person: Will you please stack up both of the red blocks and either a green cube or a pyramid?

Computer: O.K. (carries out the action on the display screen)

Person: Had you touched any pyramid before you put the green one on the little cube?

Computer: Yes, the green one.


Person: When did you pick it?

Computer: While I was stacking up the red cube, a large red block and a large green cube.

Person: Why?

Computer: To get rid of it.

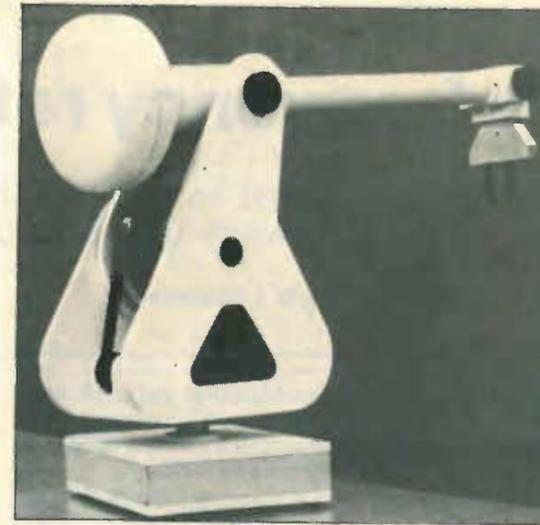Xerox Corporation has developed a system called GUS, as part of its work on new, more naturally human information systems, which foreshadows the kind of public information services that might eventually become widespread. For



This robot arm, for light assembly tasks, is a successor to the "Freddy" robot used by the Department of Artificial Intelligence at Edinburgh University for experiments in computer control of robots. The arm has joints, each actuated by an electric motor. Torque is transmitted between motor and joint by a gear train and in two cases by toothed belts. Angles of joints are measured by incremental shaft encoders. These are interrogated by a 16-bit microprocessor which computes the difference between where the joint is and where it ought to be and, allowing for the speed of the joint, issues a command signal to the corresponding motor.

example, a business executive specifies that he wishes to interact with a GUS computerised travel consultant. The dialogue goes like this:

Client: I want to go to San Diego on May 28.

GUS: What time do you want to leave?

Client: I must be in San Diego before 10 a.m.

GUS: Would you like P.S.A. flight 102 that arrives at 9:15 a.m.?

Client: What is the next flight?

GUS: Air California flight 310 that leaves at 8.30 a.m. and arrives at 10.00 a.m.

Client: I'll take the first one.

GUS: In what name should I make a reservation?

Client: Dan Bobrow.

GUS: I have confirmed the following flight: P.S.A. flight 102 on Wednesday May 28 from San Jose to San Diego which leaves at 7.30 a.m. and arrives at 9:15 a.m.

These kinds of dialogues are an important aspect of the AI development which comes closest to the core of real human intelligence - expert systems. The starting point of an expert system is an expert, called a 'domain specialist'. Expert

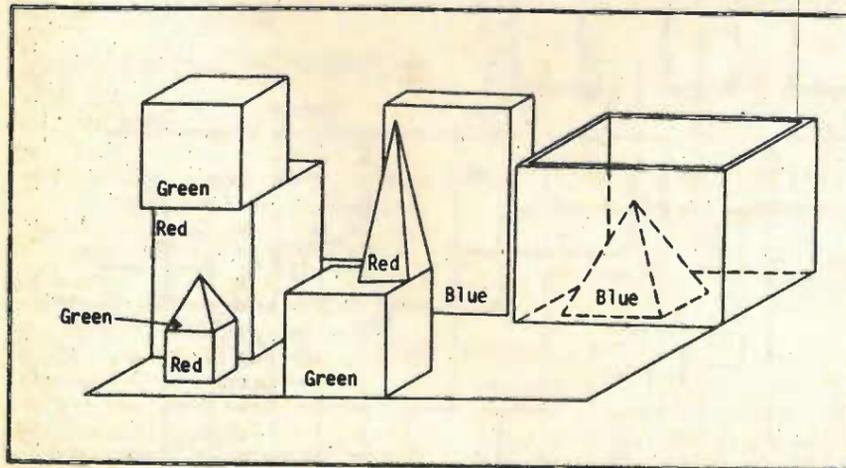


Fig. 3. Winograd's simple world for understanding natural language. A screen displays these blocks, each of which has a word printed on it indicating a colour.

systems exist in domains as varied as geology, biochemistry, medical diagnosis and applied mathematics.

The expert computer system holds the distilled knowledge of the domain expert, written by an AI specialist in a logical programming language using statements that are easy to interpret. The form of these statements might typically be: "IF condition x AND condition y BUT NOT condition z THEN there is a reasonable/poor/good chance that condition A is true/false." For example, "IF the temperature is over 80 degrees AND door 53 is locked THEN there is a reasonable (0.6) probability that a fire will break out."

Expert systems perform as well as—or sometimes better than—the domain specialists whose knowledge and experience formed their basis. What is more, the expert system program is written in understandable human reasoning terms so that anyone can understand the process used by a computer to reach a decision and the probabilities of various of its decisions being accurate. The expert system program can even be used as a tutor.

Expert systems are of practical use. B.P., for example, is currently working with Edinburgh University to produce an expert system for an oil rig which will be able to help identify any faults and explain the most appropriate course of action without having to immediately send for a Red Adair. And the multinational group Schlumberger is using an expert system to help find new oilfields!

The image created by science fiction writers of mankind being superseded by a race of superintelligent robots has been the image most associated in the popular mind with AI. The reality, however, could be that AI helps to turn the computer into a genuine workhorse and intellectual friend of people by removing the mystique of automation, simplifying and humanising the interaction between man and machine and providing a window into the "mind" of the computer. So when a computer is trying to warn us of something dangerous about to occur, we can question it and if necessary, heed its warning.

Off-air frequency reference

Seven outputs from 1Hz to 10MHz, phase locked to the Droitwich transmission

by D. I. Stansfield

Although i.s.i. techniques have simplified the construction of a frequency counter, accuracy depends on the stability and adjustment of the reference oscillator. Unless this oscillator is temperature controlled and adjusted in conjunction with a standard frequency source, even a quartz crystal will not provide better than 1 part in 10⁵ accuracy.

This unit provides a 10MHz signal, phase-locked to the BBC 200kHz Radio 4 transmission from Droitwich. The long term accuracy is that of the BBC standard and the error due to jitter is less than 0.1 cycles pk-to-pk over an ambient temperature range of 0 to 30°C.

The heart of the frequency reference contains a quartz crystal oscillating at 10MHz. Logic divides this output to produce a 200kHz signal which is compared in phase with the transmission as shown in Fig. 1. The resulting error signal is filtered by an active-loop filter and used to fine-tune the quartz crystal with a varicap diode. The active-loop filter enables the loop-lock conditions to be accurately specified, the static phase-error to be kept small and, in the event of interference being received, the oscillator frequency to be kept close to its locked frequency due to the memory action of the filter time constants. The 200kHz signal is received with a tuned ferrite-rod aerial, see Fig. 2, followed by a

two-stage tuned amplifier and a two-stage limiter. A buffered 200kHz output from the main divider chain is further divided to provide outputs down to 1Hz.

The main problem associated with using Radio 4 as a frequency standard is the removal of amplitude modulation. Even after full limiting, residual modulation appears as jitter on the phase detector output in Fig. 3, and if the detector output is

not sufficiently filtered, the jitter appears as phase modulation on the 10MHz signal. Because heavy filtering is necessary, a crystal oscillator is used to maintain the unlocked frequency within the narrow lock-up range of the p.l.l.

Loop consideration

Because the lock-up temperature range and amount of filtration are in conflict, it is necessary to specify the operating condition. For reliable lock-up over the ambient temperature range 0 to 30°C, and because

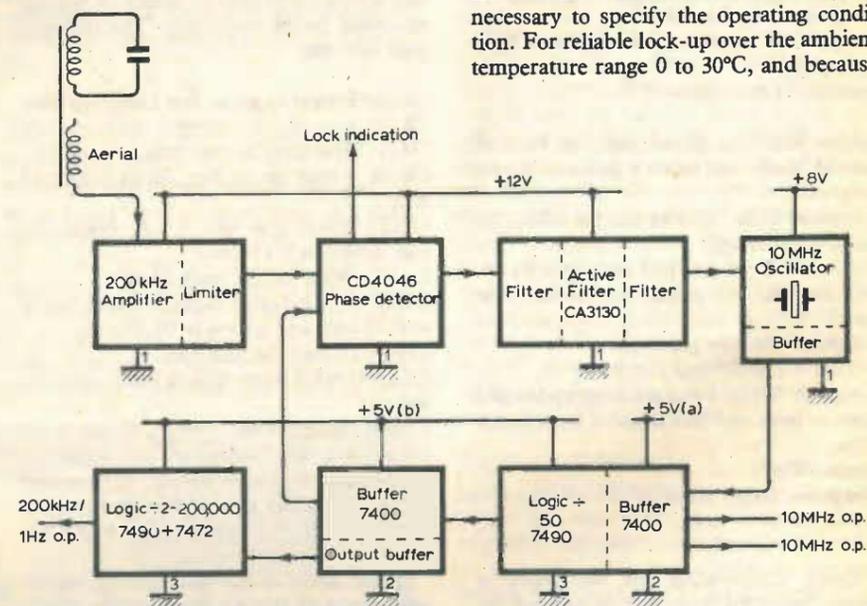


Fig. 1. Block diagram.

Fig. 2. 200kHz receiver and limiter.

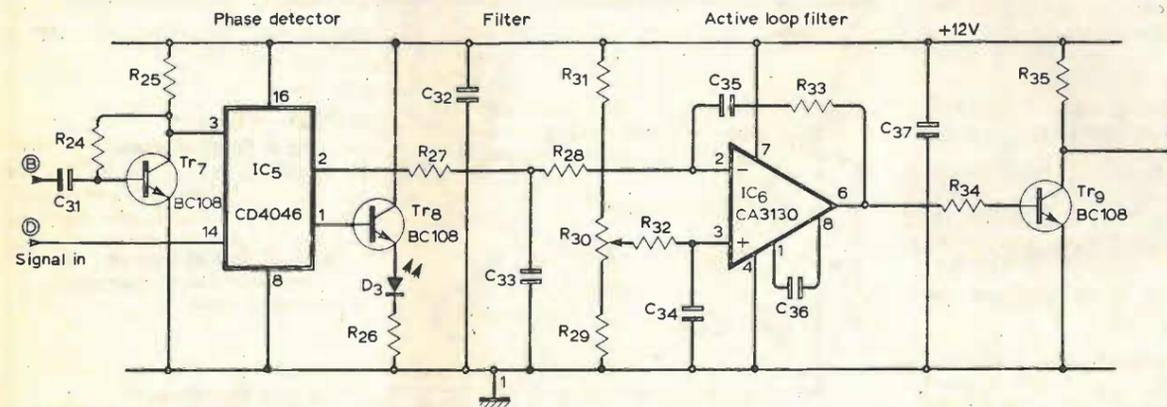
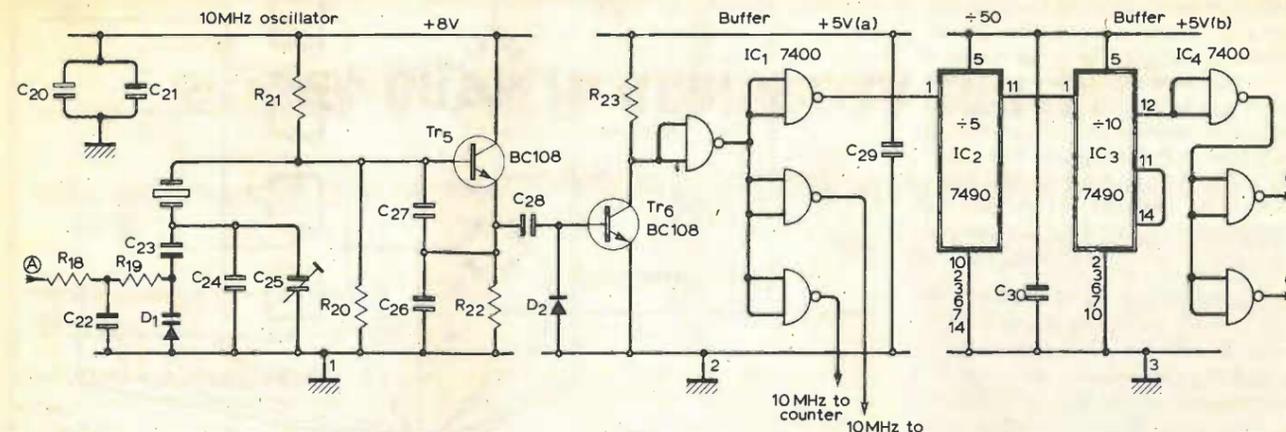
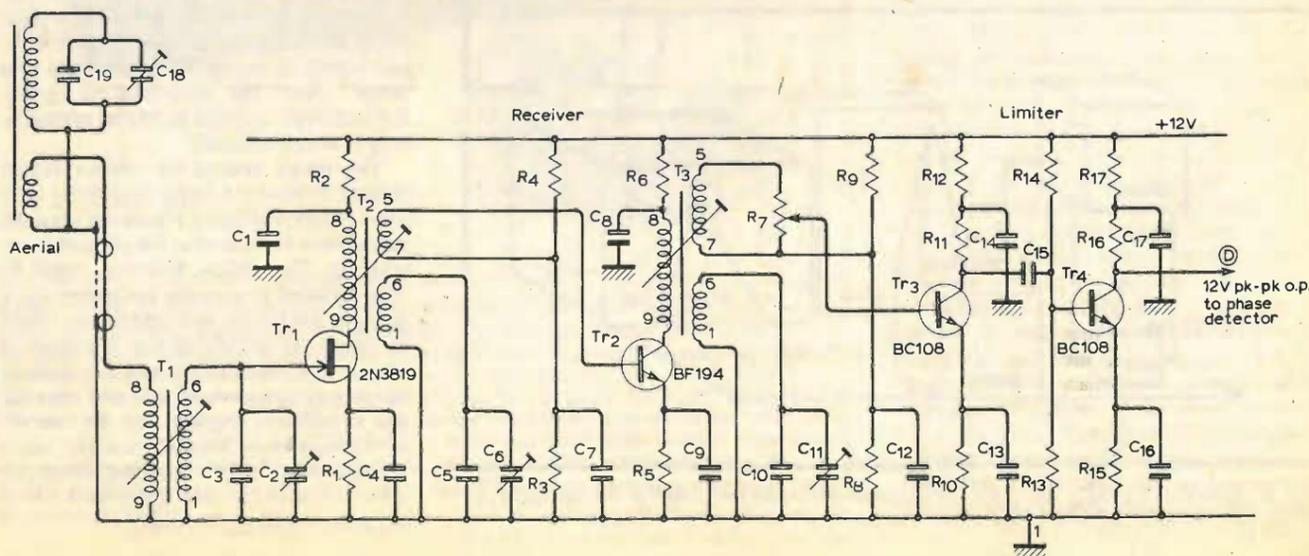


Fig. 3. Phase locked 10MHz oscillator.

Fig. 4. Active-loop filter.

Fig. 5. Divider chain with x2 switching.

crystal stability is about 20 p.p.m. above 90°C, the control range required is

$$20 \times \frac{30}{90} \times \frac{10^7}{10^6}$$

i.e. 66Hz at 10MHz.

This can be adjusted by C₂₃. For high-gain loops, the lock-up range is $2\sqrt{\zeta\omega_n K_v}$ (1) where $K_v = K_p K_o N$. For the 4046 in this configuration, K_p is 10V/rad, K_o by measurement is $93 \times 2\pi/10$ rad/V at 10MHz, and the division ratio N is 50. Therefore, K_v is $10 \times 93 \times 2\pi/50 = 11.68$.

For average conditions a loop damping factor ζ of 0.707 is satisfactory, therefore from (1)

$$\frac{66 \times 2\pi}{50} = 2\sqrt{0.707\omega_n 11.68}$$

$$\therefore \omega_n = 2.08$$



Considering the loop filter components in Fig. 4

$$T_1 = \frac{C_1 R_1}{K_v} = \frac{11.68}{2\zeta} = \frac{11.68}{2 \times 0.707} = 2.69$$

$$T_2 = \frac{C_1 R_2}{\omega_n} = \frac{2\zeta}{\omega_n} = \frac{2 \times 0.707}{2.08} = 0.679$$


Because $C_1 = 1\mu\text{F}$, $R_{1/2} = 1.3\text{M}\Omega$ and $R_2 = 670\text{k}\Omega$. To increase the loop filtration, C_2 can be included, but to avoid affecting loop performance $10(C_2 R_{1/2}) < C_1 R_1$, therefore $C_2 = 0.2\mu\text{F}$. Lock-up time is roughly $5/\omega_n \omega_{2s}$.

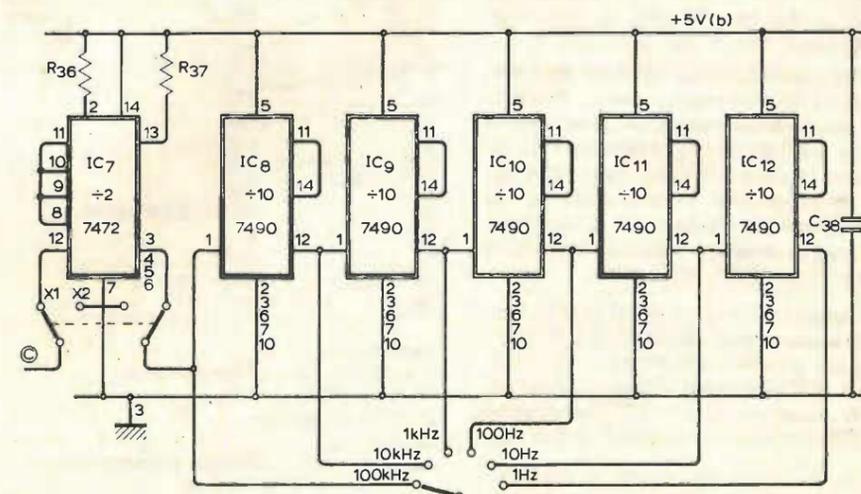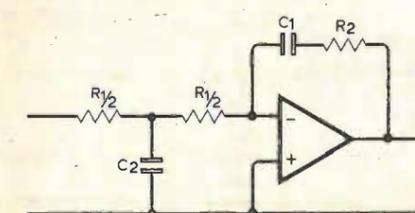Measurements of the voltage present across the tuning diode show less than 10mV pk-to-pk noise, which is equivalent to $93/10 \times 0.01 = 0.09\text{Hz}$ at 10MHz.



Construction

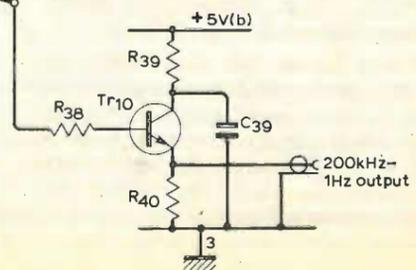The receiver is a conventional design and produces a 20mV output about 240km from Droitwich. A manual gain control is included for adjusting the limiting conditions. Because high gain is used, it is necessary to screen the receiver in a die-cast box and to locate the aerial 2m away



from the receiver. To minimize signal frequency and counter noise, buffers are included before and after the divider chain in Fig. 5, and separate earth and power supplies are provided. Double-sided printed circuit board is also important with one side used as an earth plane. The power supply in Fig. 6 uses 1A voltage regulators and smoothing capacitors to provide the low noise level necessary for a clean output signal.

Adjustment of the receiver should be carried out using an oscilloscope to observe the waveform before the limiting stages. The aerial trimmer and each tuned stage is set to resonance so that the a.m. envelope is at a maximum. If the envelope amplitude is unstable and does not exhibit normal modulation variations, the receiver is probably oscillating and the feedback source should be investigated. The gain control is adjusted to give 10V pk-to-pk free from amplitude variations.

Adjustment of the loop is carried out by observing the phase-lock l.e.d. as follows, with no input signal - l.e.d. extinguished, with input signal connected and loop close to lock - l.e.d. pulses at the beat frequency, with input signal connected and loop locked - l.e.d. on.

To adjust the loop set point, disconnect the input signal and apply +10V to pin 2 of IC₆, check output voltage to diode is >10V. Apply 0V to pin 2 of IC₆ and check output voltage to diode is <0.5V. Resistor R₃₄ can be adjusted if required. Next, adjust R₃₂ for 5V to the diode with no drift. Reconnect the input signal and set C₂₅ to obtain the lock indication. Finally, measure the ambient temperature and adjust the varicap voltage with C₂₅ as shown in Fig. 7.

Because indication of lock is provided, if the unit is connected to an 8-digit 10MHz counter, count rates up to 10⁷ per second or 10⁸ in ten seconds can be accurately achieved.

The current system used by the BBC employs satellite transmitters at Westerglen and Aberdeen which are phase locked to the main Droitwich transmitter. In locations where a subsidiary transmitter signal is comparable in magnitude to the Droitwich transmission, the cleanest signal may be obtained with the aerial rod in line with the second transmitter.

If greater short-term signal purity is required, the crystal oscillator can be temperature stabilized to allow a narrower lock range and additional filtration. Alternatively, a narrow band crystal filter centred at 200kHz can be included before the limiter to reduce the energy of the a.m. sidebands. These improvements would, however, increase the cost of the unit.

Within the next five years Radio 4 will be changed to 198kHz, although it will maintain the present accuracy. To lock onto 198kHz, the receiver must be modified to include a mixer and narrow-band crystal filter to pick out the required sideband as shown in Fig. 8.

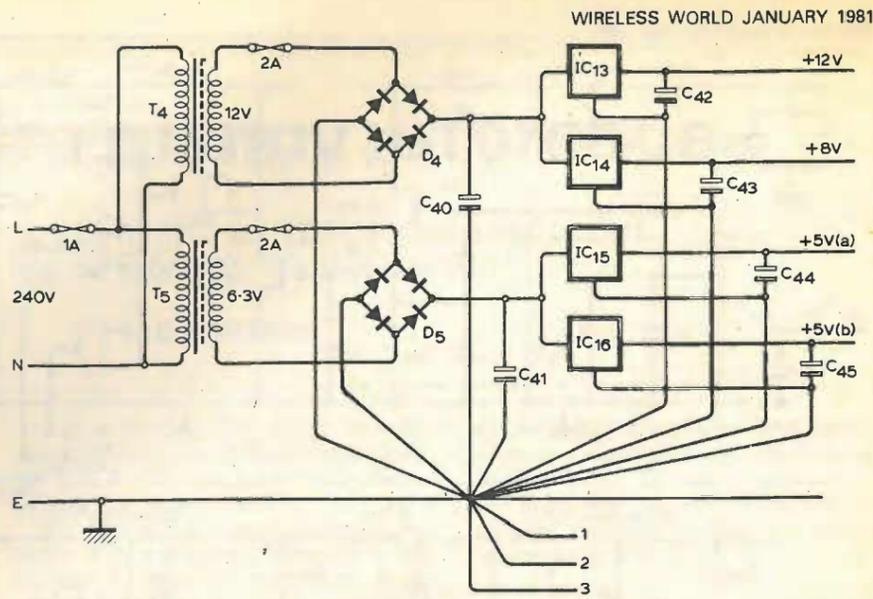


Fig. 6. Four rail power supply.

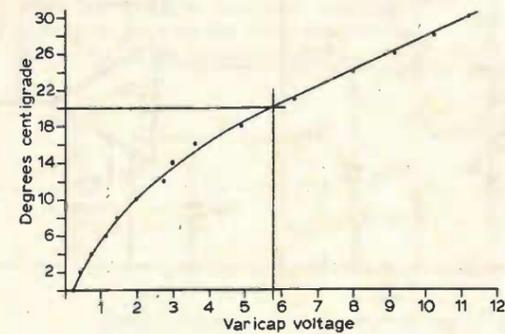


Fig. 7. Varicap voltage versus ambient temperature (loop locked).

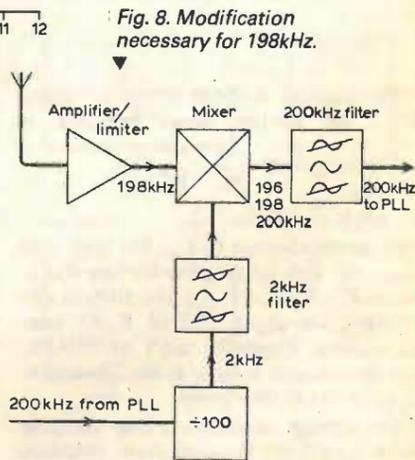


Fig. 8. Modification necessary for 198kHz.

COMPONENTS

| | |
|---|-----------------------------|
| Resistors 1/2W | |
| 1,36,37 | 5% |
| 2 | 1k |
| 3,13 | 330 |
| 4 | 8k2 |
| 5 | 39k |
| 6 | 870 |
| 7 | 4k |
| 8,10,22,35 | 10k preset |
| 9,18,19,29,31,38 | 2k2 |
| 11,16 | 4k7 |
| 12,17 | 5k6 |
| 14 | 100 |
| 15,26 | 56k |
| 20,21 | 470 |
| 23 | 27k |
| 24 | 560 |
| 25 | 620k |
| 27,28 | 10k |
| 30 | 1M |
| 32 | 1k 10 turn trimmer |
| 33 | 470k |
| 34 | 670k |
| 39,40 | 330k |
| | 51 |
| Capacitors | |
| 1,4,7,8,9,12,13,14,15,16,17,21,29,30,31,32,34,37,38,39, | 100n polyester |
| 2,6,11,18, | 30/80pF compression trimmer |
| 3,5,10 | 180pF mica |
| 19 | 300pF mica |
| 20 | 10µF electrolytic |
| 22,33 | 220n polycarbonate |
| 23 | 10pF mica |
| 24 | 27pF ceramic |
| 25 | 2/10pF rotary trimmer |
| 26,36 | 100pF mica |
| 27 | 220pF mica |
| 28 | 150pF mica |

| | |
|---|---------------------------|
| 35 | 1µF polycarbonate |
| 40,41 | 4000µF electrolytic |
| 42,43,44,45 | 100µF electrolytic |
| Transistors | |
| 1 | 2N3819 |
| 2 | BF194 |
| 3-10 | BC108 |
| Integrated circuits | |
| 1,4 | 7400 |
| 2,3,8,9, | 7490 |
| 5 | 4046 |
| 6 | CA3130 |
| 7 | 7472 |
| 13 | 7812 |
| 14 | 7808 |
| 15,16 | 7805 |
| Diodes | |
| 1 | OA81 |
| 2 | BA102B |
| 3 | l.e.d. |
| 4,5 | 2A 50V bridge rectifier |
| Transformers/coils | |
| 1 | Denco I.T. Blue |
| 2,3 | Denco I.T. Yellow |
| 4 | 12V 2A mains transformer |
| 5 | 6.3V 2A mains transformer |
| Ferrite rod aerial | |
| 8 x 3/8in with 200 turns of 36 s.w.g. spread wound over 6in, and 15 turns of 36 s.w.g. close wound at one end of the rod. | |
| Crystal - 10MHz | |

TOP QUALITY REBUILT TV TUBES

Rebuilt on the most modern equipment to original manufacturers' specifications

- ★ HIGH FOCUS
- ★ LONG LIFE
- ★ FULLY TESTED
- ★ FULLY GUARANTEED



These top-class rebuilders cover the country - phone your nearest one now for details and prices - and first-class service.

GLASGOW—RENUV Tubes
Tel: (041) 883 8272

COLERAINE—PE Tubes
Tel: (0265) 3397

BRADFORD—VISOR Tubes
Tel: (0274) 494340

OLDHAM—RE-LIFE Tubes
Tel: (061) 665 2668

NORTH SOMERCOTES—RETUBE
Tel: (0507) 85 300

DUBLIN—PE Tubes
Tel: 860547

STOKE-ON-TRENT—BAREX Tubes
Tel: (0782) 322744

NOTTINGHAM—TRENT TUBES
Tel: (0602) 813329

BIRMINGHAM—TUBESURE
Tel: (021) 558 7777

COVENTRY—TELETUBE
Tel: (0203) 610977

RUGBY—VISIONEX
Tel: (0788) 62626

NEWPORT—OMSPEC Tubes
Tel: (0633) 612556

SOUTHAMPTON—WECO Tubes
Tel: (0703) 36985

PENZANCE—WECO Tubes
Tel: (073 676) 2265

All these top-class rebuilders use plant and equipment manufactured by Western-Whybrow Engineering - acknowledged as the best available, and the product of more than twenty years' experience of rebuilding colour tubes in U.K. and U.S.A. There is a constant interchange of information to ensure the highest standard of rebuilt tube.

S-2020TA STEREO TUNER / AMPLIFIER KIT

NEW HIGH PERFORMANCE TUNER

A high-quality push-button FM Varicap Stereo Tuner with pilot cancel decoder combined with a 24W r.m.s. per channel Stereo Amplifier, using Bifet op. amps.

Brief Spec. Amplifier Low field Toroidal transformer, Mag. input. Tape In / Out facility (for noise reduction unit, etc.) THD less than 0.1% at 20W into 8 ohms. **High Slew Rate.** Low noise op. amps used throughout. Power on/off FET transient protection. All sockets, fuses, etc., are PC mounted for ease of assembly. Tuner section uses UM 1181 FET module requiring no RF alignment, ceramic IF INTERSTATION MUTE, and phase-locked IC pilot cancel, stereo decoder, LED tuning and stereo indicators. Tuning range 88-108MHz 30dB mono S/N @ 0.7 μ V. THD 0.3%.

PRICE: £69.95 + VAT



NELSON-JONES Mk. 2 STEREO FM TUNER KIT

A very high performance tuner with dual gate MOSFET RF and Mixer ready built front end, triple gang varicap tuning, linear phase I.F. and 3 state MPX decoder.

PRICE: £74.95 + VAT



NRDC-AMBISONIC UHJ SURROUND SOUND DECODER

The first ever kit specially produced by Integrex for this British NRDC backed surround sound system which is the result of 7 years' research by the Ambisonic team. W.W. July, Aug., '77. The unit is designed to decode not only UHJ but virtually all other 'quadrophonic' systems (Not CD4), including the new BBC HJ. 10 input selections. The decoder is linear throughout and does not rely on listener fatiguing logic enhancement techniques. Both 2 or 2 input signals and 4 or 6 output signals are provided in this most versatile unit. Complete with mains power supply, wooden cabinet, panel, knobs, etc.

Complete kit, including licence fee £57.70 + VAT or ready built and tested £76.95 + VAT



S5050A STEREO AMP

Very high performance kit

50 watts rms-channel. 0.015% THD. S/N 90 dB, Mags/n 80 dB. Output device rating 360w per channel. Tone cancel switch. 2 tape monitor switches. Metal case — comprehensive heatsinks.

Complete kit only £69.95 + VAT

(Also available our 20w/ch BIFET S2020 Amp)



INTRUDER 1 Mk. 2 RADAR ALARM

With Home Office Type approval

The original 'Wireless World' published Intruder 1 has been re-designed by Integrex to incorporate several new features, along with improved performance. The kit is even easier to build. The internal audible alarm turns off after approximately 40 seconds and the unit re-arms. 240V ac mains or 12V battery operated. Disguised as a hard-backed book. Detection range up to 45 feet. Internal mains rated voltage free contacts for external bells etc.

Complete kit £52.50 plus VAT, or ready built and tested £68.50 plus VAT.

Wireless World Dolby noise reducer

Trademark of Dolby Laboratories Inc.



Complete Kit PRICE: £49.95 + VAT (3 head model available)

Also available ready built and tested

Calibration tapes are available for open-reel use and for cassette (specify which)

Single channel plug-in Dolby (TM) PROCESSOR BOARDS (92 x 87mm) with gold plated contacts and all components

Typical performance
Noise reduction better than 9dB weighted.
Clipping level 16.5dB above Dolby level (measured at 1% third harmonic content)
Harmonic distortion 0.1% at Dolby level typically 0.05% over most of band, rising to a maximum of 0.12%
Signal-to-noise ratio: 75dB (20Hz to 20kHz, signal at Dolby level) at Monitor output
Dynamic range >90dB
30mV sensitivity

Price £67.60 + VAT

Price £2.75 + VAT

Price £10.50 + VAT

We guarantee full after-sales technical and servicing facilities on all our kits, have you checked that these services are available from other suppliers?



All kits are carriage free

INTEGREX LIMITED

Please send SAE for complete lists and specifications

Portwood Industrial Estate, Church Gresley,
Burton-on-Trent, Staffs DE11 9PT
Burton-on-Trent (0283) 215432 Telex 377106

F.m. detectors

A survey and a system of classification

by S. W. Amos, B.Sc. M.I.E.E.

An earlier article, in the April 1980 issue, was devoted to a survey and a classification of a.m. detectors. In this article the author similarly examines f.m. detectors.

The purpose of a detector is, of course, to abstract information from a modulated signal. Often the wanted information is a copy of the waveform of the modulation content but it is not always so. For example an f.m. detector may be required to give an output for a.f.c. purposes and here a filter is incorporated to eliminate modulation-frequency components from the output.

F.m. detectors are sometimes called discriminators or frequency discriminators but a discriminator differs from a detector in that it is required to produce an output substantially proportional to the deviation of the frequency (or phase) of an alternating input from some predetermined value (BS 301 5013). This suggests that the function of a discriminator is similar to that of a demodulator and is more specialised than that of a detector which is therefore a more general term. This distinction is not perfectly observed in the terminology of the circuits: for example two circuits with substantially the same performance and purpose are the Seeley-Foster discriminator and the ratio detector.

Frequency discriminators are sometimes called phase discriminators. The relationship between frequency modulation and phase modulation is simple: in frequency modulation, for a constant-amplitude modulating signal, the phase shift of the carrier is swept between limits which are inversely proportional to the modulating frequency: in phase modulation the limits are fixed. Similarly in phase modulation the limits are fixed. Similarly in phase modulation the limits are fixed. In practice this means that one form of modulation can be converted to the other by including a 6dB per octave filter in the modulating-signal path and, by use of such a filter, the same circuit can be used for the detection of f.m. or p.m. signals. For simplicity all the circuits mentioned in this article are referred to as f.m. detectors or discriminators.

An examination of the various types of f.m. detector suggests that they all belong to one of the following four categories: (a) those consisting essentially of an f.m.-

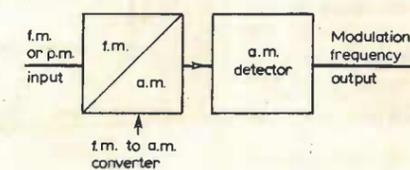


Fig. 1. Block diagram illustrating the form of a number of types of f.m. detector.

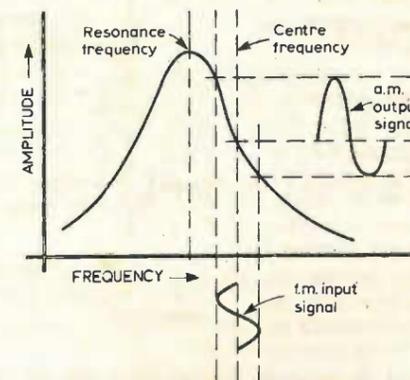


Fig. 2. Simple f.m. slope detector.

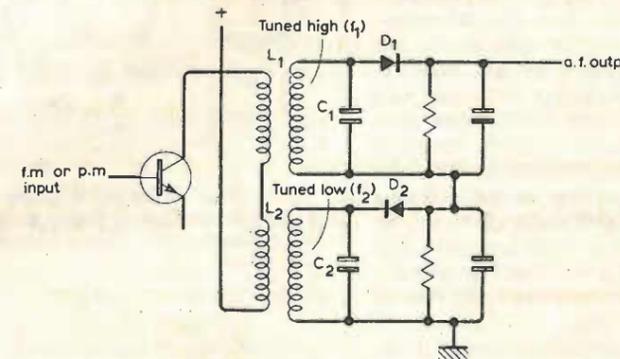


Fig. 3. Round-Travis f.m. detector.

to-a.m. converter followed by an a.m. detector, (b) those using phase comparators i.e. circuits in which the output is dependent on the degree of overlap of two sets of carrier-frequency pulses, (c) those using a counter circuit as a discriminator, (d) those using the locked-oscillator principle.

This classification will now be examined in detail.

F.m. detectors incorporating an f.m.-to-a.m. converter

Perhaps the most obvious way of detecting an f.m. signal is to convert the frequency variations into corresponding amplitude variations of the carrier which is then applied to an a.m. detector. A number of

types of f.m. detector operate on this principle which is illustrated in Fig. 1.

Slope detector. A simple way of achieving f.m.-to-a.m. conversion is to make use of the slope of the skirts of the amplitude/frequency characteristic for a tuned circuit. If the resonance frequency of the tuned circuit is so chosen that the centre frequency of the signal falls on a suitable part of the characteristic, as shown in Fig. 2, then the output is a signal which is amplitude-modulated and frequency-modulated by the same modulating signal. If this output is applied to an a.m. detector, the frequency modulation will be ignored but the amplitude modulation will give an output at the modulation frequency. The curvature of the skirts of the resonance curve causes harmonic distortion which can be minimised by choice of Q value and resonance frequency for the tuned circuit but the distortion is still serious.

Round-Travis detector. In this form of detector the distortion caused by curvature of the tuned-circuit characteristic is reduced by use of the push-pull principle. Two similar tuned circuits are used, one (L_1C_1), resonant at a frequency f_1 above the centre frequency and the other (L_2C_2) resonant at f_2 an equal amount below the centre frequency. The signals developed across L_1C_1 and L_2C_2 are detected by separate a.m. detectors, their outputs being connected in series opposition. One possible circuit diagram for a Round-Travis detector is shown in Fig. 3 in which simple sampling-type detectors are shown.

The operation of the detector is illustrated in Fig. 4. At the centre frequency equal outputs are received from the two diodes so that the net output is zero. At frequencies above the centre frequency D_1 gives a larger output than D_2 and the combined output is positive; at frequencies below the centre frequency D_2 gives a larger output than D_1 and the combined output is negative. Thus the net output indicates by its polarity whether the instantaneous frequency of the input is above or below the centre value and by its magnitude the extent of the deviation.

Fig. 4 shows that the complementary curvature of the characteristics for L_1C_1 and L_2C_2 yields a straighter overall amplitude/frequency relationship than is possible from a single tuned circuit. The overall relationship shown in Fig. 4 has the S-shaped form characteristic of that of many f.m. detectors.

The Round-Travis detector was at one time used in f.m. receivers but has long since been abandoned in favour of some of the alternative types described later. It has two main disadvantages:

- L_1C_1 and L_2C_2 must be so adjusted that their resonance frequencies f_1 and f_2 are symmetrically disposed about the centre frequency. Thus alignment of the detector circuit is more complicated than for a number of the alternative types which require alignment only at the centre frequency.
- It responds to any amplitude modulation of the input signal. To obtain maxi-

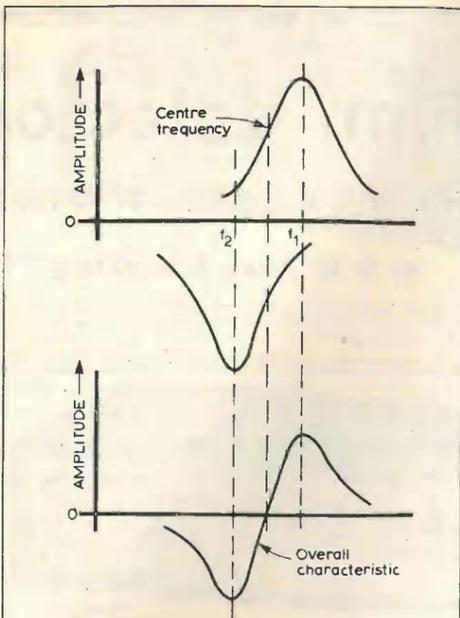


Fig. 4. Derivation of overall characteristic of Round-Travis f.m. detector.

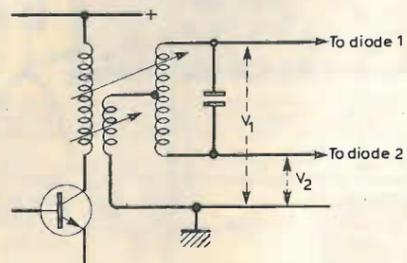


Fig. 5. Method of deriving the two diode inputs in Seeley-Foster and ratio detectors.


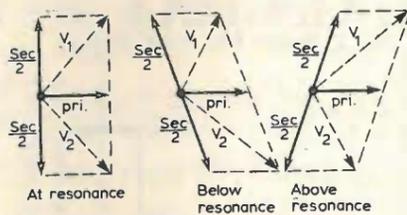


Fig. 6. Vector diagram for the circuit of Fig. 5 showing how the voltages V_1 and V_2 applied to the diodes vary with frequency.

Fig. 7. One circuit for a Seeley-Foster discriminator.

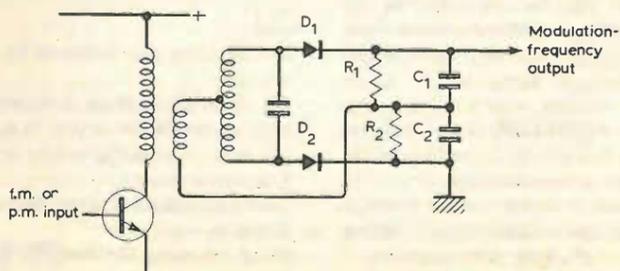

imum signal-to-noise ratio, an f.m. receiver should respond only to frequency modulation of the input signal and should ignore any amplitude modulation which may be present. Some f.m. detectors can be designed to have inherent a.m. rejection and these are naturally preferred.

Seeley-Foster discriminator. This f.m. detector uses an arrangement of diodes similar to that of the Round-Travis circuit but the method of providing the diode input signals is different. The method makes use of the phase relationship between the voltage across the tuned secondary winding of a transformer and that across the primary winding. Whether the primary winding is tuned or not, these two voltages are in quadrature when the applied signal is at the resonance frequency of the secondary winding. At frequencies above resonance the secondary voltage lags the quadrature condition to an extent dependent on the frequency deviation and at frequencies below resonance the secondary voltage leads on the quadrature condition to an extent depending on the deviation.

If therefore the secondary winding is centre-tapped and if a sample of the primary voltage is injected into the centre tap, as shown in Fig. 5, the voltages V_1 and V_2 at the two ends of the secondary winding vary with frequency in the same way as those from the two tuned circuits in the Round-Travis circuit. This is shown in the vector diagram of Fig. 6 which illustrates the relative magnitudes of V_1 and V_2 at resonance, above and below resonance. These diagrams apply when the primary voltage is equal to half the secondary voltage.

Thus a Seeley-Foster circuit could be made up from the circuit shown in Fig. 5 feeding into two simple diode circuits as shown in Fig. 7. An alternative circuit which simplifies the design of the transformer is to use a capacitive link between primary winding and secondary centre tap as shown in Fig. 8. By this means the whole of the primary voltage is injected into the secondary circuit.

The introduction of the capacitor C_p interrupts the diode circuit. Normally when a diode detector is fed via a series capacitor the diode and its load resistor are both shunt-connected to ensure that the capacitor can be charged once per cycle when the diode conducts and can discharge through the load resistor when the diode is cut off by the input signal. In the circuit of Fig. 8(a) the series capacitor can certainly charge when the diodes are driven into conduction by the input signal

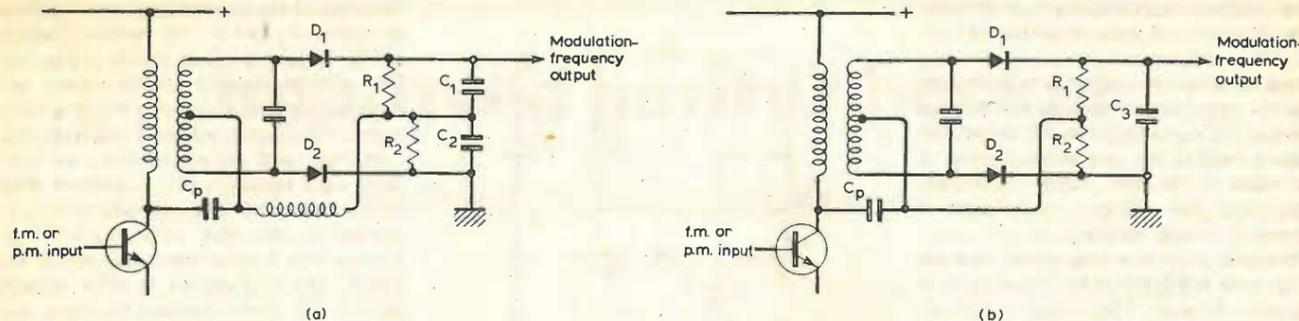


Fig. 8. Two forms of Seeley-Foster circuit using a capacitive link between primary and secondary windings.

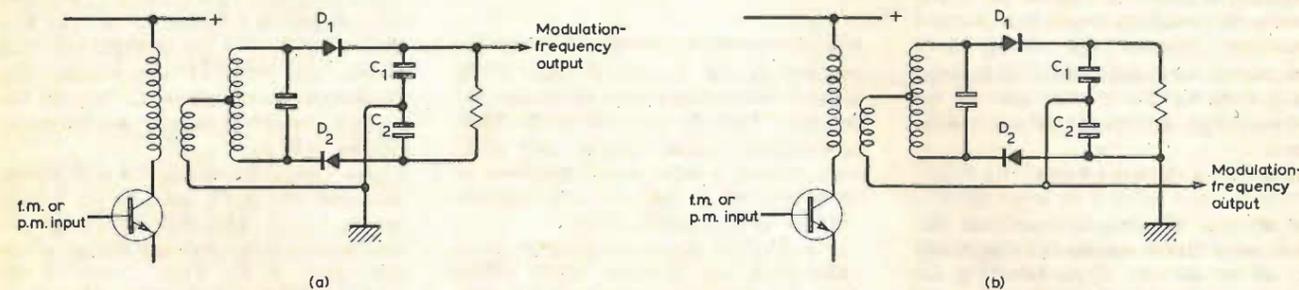


Fig. 9. Simplified circuits for (a) balanced and (b) unbalanced forms of ratio detector with no provision for a.m. rejection.

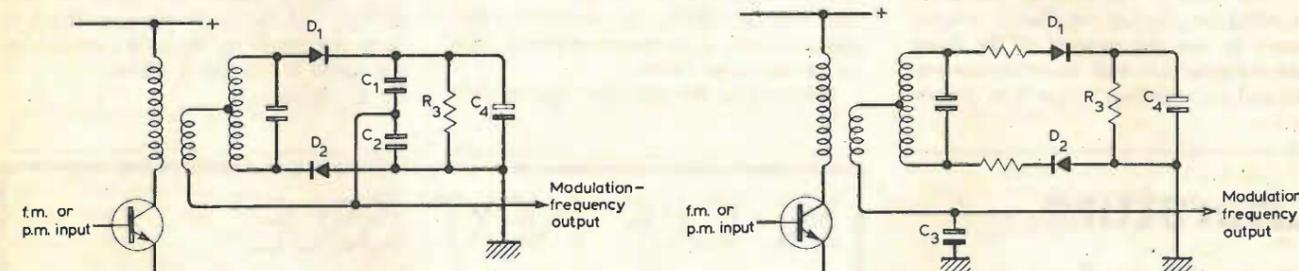


Fig. 10. The circuit of Fig. 9 (b) modified so as to give a measure of a.m. rejection. Fig. 11. An unbalanced ratio-detector circuit with a single reservoir capacitor C_3 .

but, for the periods when the diodes are cut off by the input signal, a discharge path must be provided between the right-hand plate of C_p and the junction between R_1C_1 and R_2C_2 . Moreover this path must not introduce significant damping of the primary circuit. There are two techniques which are commonly adopted to achieve this end:

- As shown in Fig. 8(a) an inductor can be introduced between the secondary centre tap and R_1R_2 junction. This should have an inductance such that its reactance is large compared with that of C_1 and C_2 at the operating frequency.
- If the link between R_1R_2 and C_1C_2 is cut a direct connection can be made between the coupling capacitor and R_1R_2 junction as shown in Fig. 8(b). Damping of the primary circuit can be minimised by using sufficiently large values for R_1 and R_2 . As shown C_1 and C_2 can be replaced by a single equivalent capacitor, C_3 .

The Seeley-Foster discriminator was extensively employed in early f.m. receivers. Alignment is straightforward, needing only a signal source at the centre frequency and linearity can be made acceptable. Its chief disadvantage, shared with the Round-Travis circuit, is that it responds to any amplitude modulation of

the input signal. Thus to obtain the high signal-to-noise ratio of which an f.m. receiver is capable it is necessary to precede the Seeley-Foster circuit by one or more amplitude-limiting stages to minimise any a.m. content in the received signal.

Ratio detector. By a simple modification the Seeley-Foster discriminator can be made capable of a useful degree of a.m. suppression. The detector circuit so produced is known as the ratio detector and it is not surprising that it rapidly displaced the Seeley-Foster discriminator. The way in which the ratio detector operates can be approached in the following way.

If one of the diodes in the circuit of Figs. 7 or 8(a) is reversed, the net output is the sum of the voltages across the individual diode loads (not the difference as in the Seeley-Foster circuit). Thus for an input to the circuit at the centre frequency there is a voltage at the combined output approximately equal to the sum of the peak input voltages to the diodes: this compares with zero output from the Seeley-Foster circuit.

If the frequency of the input is displaced from the centre value the output across one diode load increases whilst that across the other decreases as shown for V_1 and V_2 in Fig. 6 and the combined voltage output

tends to be independent of frequency and thus of frequency modulation. This combined output is proportional to input signal amplitude and can be used to operate a tuning indicator.

Even though the voltage across (C_1+C_2) is constant (for a given input amplitude) the voltages across the individual reservoir capacitors C_1 and C_2 vary with the frequency of the input signal and either capacitor can be used as the source of modulation-frequency output from the detector. In a balanced ratio detector circuit the junction of C_1 and C_2 is earthed and the detector output is taken from the non-earthed terminal of C_1 (as shown in Fig. 9(a)) or C_2 . In an unbalanced ratio detector one end of the combined diode load is earthed as shown in Fig. 9(b) and the detector output is taken from C_1C_2 junction. In both types of circuit the constant voltage across the series-connected reservoir capacitors C_1 and C_2 is divided in a ratio determined by the peak inputs to D_1 and D_2 : this is the origin of the name of the circuit.

To make the circuit capable of a useful degree of a.m. rejection the diode load resistor(s) are given low value(s) so that the tuned circuit feeding the detector is heavily damped. A large value capacitor is then connected across the load resistors to give a

time constant approaching one second. Fig. 10 illustrates these modifications applied to an unbalanced circuit. The voltage across the long-time-constant network is in practice approximately equal to the peak value of the input signal to the diodes and adjusts itself to any permanent change in the value of the peak input. As already mentioned this voltage can be used to operate a tuning indicator.

Suppose there is a momentary increase in the peak amplitude of the signal input to the ratio detector. The voltage across the diode load circuit cannot instantaneously adjust itself to equal the peak value of the spike and as a result the diodes are driven heavily into conduction and their forward resistance increases the already-heavy damping on the tuned circuit thus momentarily reducing the voltage gain of the previous stage, minimising the effect of the spike.

Similarly if there is a momentary reduction in the peak value of the input signal to the detector, the long-time-constant network again cannot register the change and the diodes are cut off so removing the damping imposed by the diode load on the tuned circuit. Thus the gain of the previous stage is momentarily increased, offsetting the effect of the change in input signal. In fact the removal of the diode load damping can result in overcompensation and a common technique is to include

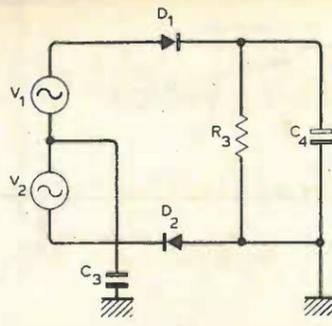


Fig. 12. Equivalent circuit of Fig. 11.

low-value resistors in series with the diodes as shown in Fig. 11, the resistance being adjusted empirically to give optimum a.m. rejection. Thus the inclusion of the long-time-constant circuit enables very short term changes in input signal amplitude to be minimised: in fact the ratio detector operates as a dynamic limiter.

Fig. 11 gives the circuit diagram of an unbalanced ratio detector which differs from that described earlier in that it contains only a single reservoir capacitor C_3 in place of the two shown in earlier circuits. The way in which the modulation-frequency output is developed across C_3 can be explained as follows.

If we replace the secondary and tertiary

windings of the transformer by equivalent generators V_1 and V_2 , the essential feature of Fig. 11 take the form shown in Fig. 12. Both diodes conduct together once per carrier cycle and, because of the long time constant R_3C_4 , the period of conduction is very brief and occurs as the combined diode input signal (V_1+V_2) reaches its peak value. As a result of this conduction C_4 is charged to the peak value of (V_1+V_2) . During this brief conduction period D_1 and D_2 can be regarded as short circuits and D_2 effectively connects C_3 across the generator V_2 . C_3 thus charges to the peak value of V_2 . For an input signal at the centre frequency V_1 is equal to V_2 and thus C_3 is charged to a voltage equal to one half that across C_4 . For the remainder of each carrier cycle when D_1 and D_2 are non-conductive the charge on C_3 remains except for a small leak through any resistor in parallel with it.

One cycle later, during the next period of conduction of D_1 and D_2 , the voltage across C_3 is adjusted by charge or discharge to agree with any change in the peak value of V_2 . Thus a copy of the changing value of V_2 is built up across C_3 and this is, of course, a representation of the changing phase relationship between primary and secondary voltages which, in turn, represents the frequency-modulated waveform of the input signal.

To be continued

Literature received

Switching diodes from Unitrode are listed and described in brochure (SSD-600D), which contains details of both commercial and JAN/JANTX devices. Unitrode (UK) Ltd, Deepdene House, Bellegrave Road, Welling, Kent DA16 3PY. WW401

Serck Controls have expanded the range of Lexor delay lines, which are the subject of a series of leaflets, covering various types with delays of 1ns to 1000ns. Leaflets available from Serck Controls, Rowley Drive, Coventry CV3 4FH. WW402

Colour brochure from SE Labs contains brief information on the company's range of multichannel oscilloscopes, signal conditioners and transducers. Frequency response equipment is also mentioned. Obtainable from The Instrumentation Division, SE Labs (EMI) Ltd, Spur Road, Feltham, Middx TW14 0TD. WW403

Application notes on the use of Exar devices as sine-wave converters, modems, and carrier detectors, with some general information on the use of op-amps is available from Rastra Electronics Ltd, 275-281 King Street, Hammer-smith, London W6 9NF. WW404

Radio Link is a radiotelephone message-handling system from Blick which is described, together with a radio pager, in a leaflet available from Blick International Systems Ltd, Blick House, Techno Trading Estate, Bramble Road, Swindon, Wilts. SN2 6ER. WW405

IN OUR NEXT ISSUE

Wind speed and direction indicator

Constructional design for the yachtsman displays digitally the wind direction at the masthead to within 2° and its speed from around 1 knot to 100 knots. There's also an analogue direction indicator. Powered by a 12V source, the instrument takes 290mA d.c.

Morse code decoding

A computer programme for the Wireless World scientific computer that will decode Morse code signals picked up on a radio receiver into normal language text. It will identify and reject interference pulses and will also cope with differences in senders' characteristics.

'Just detectable' distortion

This article examines signal characteristics which control the detectability of distortion to the ear and reviews attempts made to determine 'just-detectable' distortion. Also some actual examples of what the author considers to be 'just-detectable' distortion levels in audio equipment.

On sale 21 January

Improved parity checker

Moving check detects double errors

by N. Darwood

An improved method of parity checking is described, which avoids the difficulty of recognizing two errors.

Before proceeding with the suggested innovation, it may be helpful first to see what parity is and how conventional parity-checking systems work.

In the particular sense of error detection in a group of digits, the parity of a number is the sum of its digits. For example, the parity of 142 is odd, because the sum of its digits is 7, which is an odd number: 93 has even parity. Numbers in the binary notation are similarly assigned even or odd parity if the sum of the constituent 1s is even or odd: 1000100, for example, exhibits even parity, while 0110100 has odd parity.

Parity bits are used in both serial and parallel data channels, in which they are often called horizontal and vertical parity bits respectively, as indicated by Fig. 1. In either case an extra bit (the parity bit) is added to the number. It is made either a 1 or a 0 such that the total number of 1s overall (i.e. in the number plus the parity bit) is even. Some examples are shown below:

| Data | P |
|---------|---|
| 1000100 | 0 |
| 1110111 | 0 |
| 0110100 | 1 |
| 1101101 | 1 |
| 0110011 | 0 |
| 0100000 | 1 |

Data plus the parity bit is called a word in Fig. 1.

An error in transmission changes a 1 to a 0 or a 0 to a 1. On reception, each word (a horizontal row in the first method of Fig. 1; a vertical column in the second method) is checked by counting the number of 1s in each word. If odd, then an error has occurred. If two errors occur in a word the parity is not altered and they will pass undetected, but three can be detected as an error. The fact that two errors are not detected is a disadvantage of conventional parity checkers. This article remedies this disadvantage.

The new coding method came into being following a requirement for a check on a serial digital data channel, as in Fig. 1(a). Having reviewed the two methods of how a parity bit can be employed the obvious solution was to tack on a parity bit at the end of each word. Unfortunately, the data

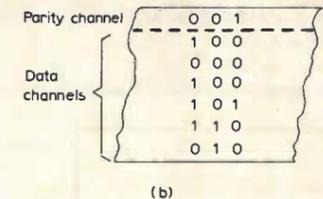
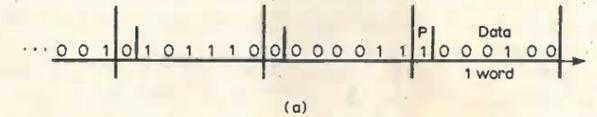


Fig. 1. Parity bits in serial (a) and parallel (b) data channels.

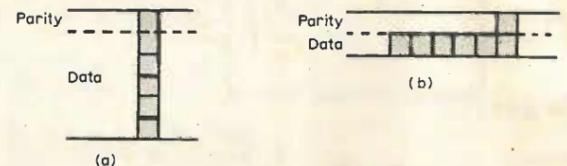


Fig. 2. Checking area of a parallel channel can be 'bent' to enable one parity bit to check serial data as in (b).

stream could not be interrupted to insert the parity bit, which meant that an extra channel, acting as a vertical parity bit, would have to be used. A first attempt at a solution is shown below, where each column is of even parity.

| | | | | | | | | | | | |
|--------|-----|---|---|---|---|---|---|---|---|---|---|
| Parity | ... | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 0 |
| Data | ... | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 0 |

Although this trial attempt at a solution will detect one error, two errors will pass undetected. But what is worse is that here there is 100% redundancy.

Figure 2(a) emphasizes that the 'checking area' of the parallel channel of Fig. 1(b) is a vertical column, so that, for a serial data channel, the checking area can be rotated through a rightangle as shown in Fig. 2(b). This forms a vertical parity bit which checks horizontal data bits. Any single error within the checking area will be detected because it will make the parity odd but, what is more, now two errors will be detected, as will any number of errors in a block of 12 (with one exception). To understand why this is so, assume only a two serial data bit checking area. The checking area is then depicted thus,



A typical sequence would be as shown below, with the checking area at one position

| | | | | | | | | | | | |
|-----|---|---|---|---|---|---|---|---|---|---|---|
| ... | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 |
| ... | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |

At the receiver, the parity-checking circuit will check for even parity over the 3-bit area. For this illustrative case, all single, double and treble errors (with one exception) will be detected, as will a block of four errors.

How the multiple errors are detected can be shown by passing the error pattern through the checking area, as in Fig. 3(a), where any odd number of errors in the checking area indicates an error.

The only pattern not detected is



As this pattern passes through the checking area, an even number of errors is counted at each position and no error is

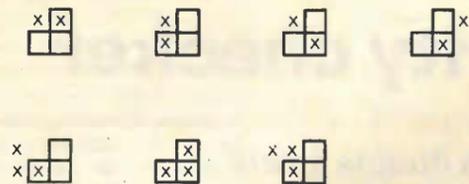


Fig. 3. Two, three and four errors, distributed as at (a) are detected, since the parity check gives an odd result at some point as the data stream passes the checking area. The pattern at (b) is not detected, because the parity remains even at any position.

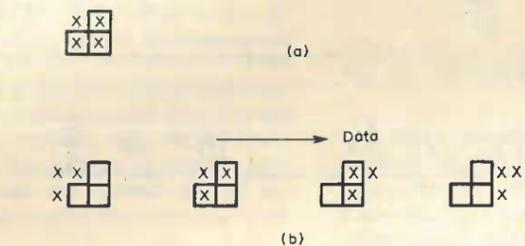


Fig. 4. Logic diagram of parity generation and checking.

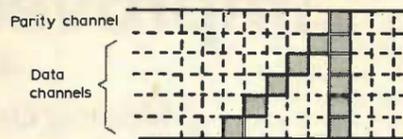


Fig. 5. Suggested checking area for parallel data channel.

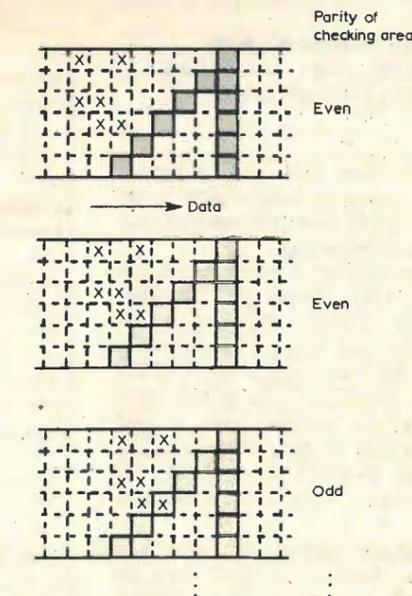


Fig. 6. Operation of the parity check of Fig. 5.

for the 8-channel system is

X X X X X X X X

The one combination of errors not detected is shown below

X X X X X X X X
X

Note that this error pattern is the checking area, rotated through 180°. Why it is not detected can be seen by passing it through the checking area.

The principle of moving parity, can be extended to embrace the parallel system shown in Fig. 1(b). Fig. 5 shows a checking area which is easy to implement in hardware. Even so, it is difficult to find an error pattern in a block of 36 that can pass undetected, other than the checking area rotated through 180°. An example of one attempt is shown in Fig. 6 to demonstrate how the checker works.

Further reading

Darwood N. 'A Moving Parity Check Method' *Electronic Engineering*, April 1979.

indicated. Fig. 3(b) shows why this is so. In a working parity checker, it is convenient to use eight channels because 8-bit i.c.s are readily available. At the transmitter, the parity-generating logic consists of a shift register, which forms the eight fictitious channels from which the parity bit is generated by an 8-bit-input parity-generating chip. Fig. 4(a) shows a typical arrangement.

At the receiver, shown in Fig. 4(b), the same circuit is used to form an 'assumed

parity' which is compared with the actual received parity bit. The comparison is shown below

| Assumed | Received | Error |
|---------|----------|-------|
| 0 | 0 | No |
| 0 | 1 | Yes |
| 1 | 0 | Yes |
| 1 | 1 | No |

This logic function is the final exclusive-Or in Fig. 4(b). Finally, the checking area

NEW PRODUCTS

Video recorder

Low weight is the main feature of the VT 7000 video recorder from Hitachi, as it weighs only 6.8kg, including its rechargeable battery pack. This v.h.s. recorder can be powered by its own batteries, a car battery or by the mains supply. There are two possible ways of operating the recorder: one can either use the touch buttons on the front of the unit, or the remote control keypad which is supplied as standard. Numerous sockets are provided for connexion to a monitor or other v.t.r., video camera, microphone, earphone, and for receiving audio and video signals from another v.t.r. or external sound equipment. To extend the scope of the VT 7000, the same manufacturers have also introduced a tuner, the VT TU 70, which is similar in style to the recorder. A time-control mechanism on the tuner can be set, with the aid of an inbuilt digital clock, to record programmes after a time interval of up to 10 days from any one of the 12 tv channels. An a.c. mains-powered charger for the batteries of the VT 7000 is built into the tuner. Both recorder and tuner are supplied with all the necessary connecting leads and their prices are £579 and £159 respectively, including v.a.t. Hitachi Sales (UK) Ltd, Hitachi House, Station Road, Hayes, Middx.

WW301

Linear test system

A large range of devices including d.-to-a. and a.-to-d. converters, can be tested by means of the LTS 2000 benchtop automatic test instrument from Analog Devices Inc. This system is designed for use in incoming inspection, device selection and grading and other such applications. At the heart of the system is a 16-bit microcomputer, backed up by 4Kbyte of e.p.r.o.m., 60Kbyte of r.a.m. and a 92Kbyte floppy-disk unit. Other main parts of the system are a 40-character dot-matrix display, a thermal printer and an alpha-numeric keyboard. Devices to be tested are interfaced to the test-unit via "family boards" which contain all the circuits necessary to measure a general class of components. In the simplest mode of operation of the LTS,2000, the operator needs only to press the 'START TEST' button to obtain a pass or fail message from the display. Setting up of the system is also relatively simple, since programming is carried out by a "fill-



WW301



WW302

in-the-blanks" method which gives complete prompting: programs can also be supplied by the manufacturer. Full editing facilities are provided for both types of programming. Among the other types of device which can be tested are op-amps, comparators, voltage regulators, isolation amplifiers and c.m.o.s. switches. Analog Devices Ltd, Central Avenue, East Molesey, Surrey KT8 OSN.

WW302

Thermometer

Conversion of the displayed temperature reading from °C to °F or vice versa, storage of maximum or minimum temperature values, and automatic calculation and display of

WW303




the probe temperature minus the value stored in the memory are some of the features made possible by the use of a microprocessor in the hand-held digital thermometer type KM10,000 from Kane-May Ltd. For temperatures from -200 to +200°C, the resolution of the reading is 0.1°C (outside this range, the resolution is 1°C), and from -213 to +1820°C the accuracy of the reading is ±0.2°C, ±0.1%. For °F, the resolution is 1°F for the full range. A backlit 10mm l.c.d. display is used to display the temperature and give indications as to the mode of operation, as well as providing numerically coded information in the event of a fault condition being discovered by the continuously running self-test. Warnings are also given for over and under-ranging of a particular thermocouple, a broken thermocouple and for incorrect execution of the temperature difference function. The unit is powered by rechargeable batteries. Kane-May Ltd, Burrowfield, Welwyn Garden City, Herts.

WW303

Crystal filters

Quartz crystal filters in a new range, designed for i.f. selection in u.h.f. and v.h.f. telephone systems, are available from Hy-Q Quartz Products Ltd. The QMF Series filters are for use in i.f. amplifiers with a centre-band frequency of 10.7MHz, and are obtainable in three basic types, for either 12.5kHz, 20kHz, 25kHz channel spacings. Each of these basic types is available in either 2,4,6 or 8 pole versions, which give stop bandwidths ranging from 18 to 90dB at the channel spacing frequency. An

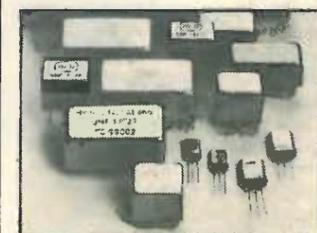

operating temperature range of between -40 and + 80°C is quoted for these filters which can have either hermetically sealed or epoxy-filled cans, and are said to be suitable for use in mobile and portable transceivers. Hy-Q Quartz Products Ltd, Station Rod, Whitllesford, Cambridge CB2 4NL.

WW304

Multi-colour display


One of the reasons why analogue-reading meters are still used extensively in control and inspection "go, no-go" applications is that they are less tiresome to read than their digital counterparts. However, Eureka Electronics Ltd have announced the availability of the MCDPM digital panel meter which could provide an answer to the aforementioned drawback in digital meters as the colour of its display indicates the range into which the input voltage falls. The levels at which the displayed digits change colour are adjusted by trimmer potentiometers. In the standard version three ranges are indicated by green, yellow and red digit colours and three c.m.o.s. compatible outputs are provided, one of which goes "high" when the relevant colour is displayed to allow such devices as audible warning units, etc., to be driven with the aid of a suitable buffer. Colouring of the digits is achieved by using filtered backlighting. The 0.5in high, 3½ digit l.c.d. display has a viewing angle of 150°, a contrast ratio of better than 20:1, and its decimal point position is selectable at the input connector. An input impedance of greater than 100MΩ is quoted for both the N311 and N111 types which differ slightly in accuracy and other electrical specifications. Both types also have f.s. resolutions of ±199.9mV or ±1.999V as standard, with two other ranges as options. Many variations on the standard versions can be provided on request, including up to five digit colours in one unit. Standard models are priced at around £68 each. Eureka Electronics Ltd, Castle House, 27 Castle Street, Brighton, East Sussex BN1 2HD.

WW305

Instrument cases

A manufacturing service for small batches of custom-made equipment cases can now be provided by Le Clair Precision, who claim that they can produce cases quickly, and to any design in most materials and finishes from a simple sketch. This service is expected to be of particular interest to companies manufacturing specialized equipment in small quantities and to research and development departments requiring prototype equipment cases. Costs are said to be generally competitive with those for adapted standard equipment cases, and will depend upon size and features required. Le Clair Precision, The Green, Theale, Reading, Berks.

WW306

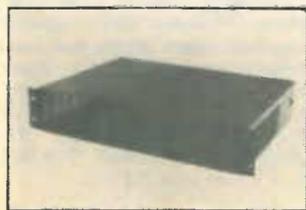

WW305

Power supplies

Recently introduced to the market is a range of 13.5V d.c. stabilized power supplies specifically designed for use with amateur radio equipment. The DRAE range from Davtrend Ltd consists of 3, 6, 12 and 24A output current versions all with fuse-protected outputs, current limiting, current foldback, thermal overload shutdown and crowbar overvoltage protection. Surge current ratings are typically twice as high as the continuous current ratings given above. Davtrend Ltd, 89 Kimbolton Road, Portsmouth, Hants.

WW307

Keyboard encoder

Up to 144 keys can be interfaced with a c.r.t. terminal using the n.m.o.s. MM57499 keyboard encoder from National Semiconductor, and a 4-12 line decoder. If interfacing of only 96 keys is required, no external components are needed, as this 28 pin i.c. provides direct interfacing, with serial transmit and receive, to a 12 x 8 matrix keyboard. The MM57499 also features a 400 word per minute burst rate and phrase storage, which allows the user to program in and store up to 14 key-strokes of data, which can be recalled using a single key. This data can be either a series of characters or control functions. Full upper and lower case ASCII, numeric and function encoding are "on-chip" and a "lock-out" feature is also provided to prevent two or more keys from being activated at the same time. National Semiconductor (UK) Ltd, 301 Harpur Centre, Horne Lane, Bedford.

WW308

Chopper op-amp

An input offset voltage of 1µV and an input bias current of 10pA maximum at 25°C are features of the ICL7650 chopper-stabilized op-amp from Intersil. Only two external capacitors are required for storing the correcting potentials on the chopper amplifier nulling inputs. Chopper drive and other control circuits are included on the chip, although the 14-pin package version also has provision for an


external clock if required. Chopping spikes at the input and output are said to be minimized due to a unique design approach. The gain bandwidth product is 2MHz, the slew-rate is 2.5V/µs and the common-mode and power supply rejection is 120dB. The 7650 is available in both T099 and 14-pin plastic or ceramic d.i.p. versions and is internally compensated for unity gain operation. In addition, the output clamp circuit reduces overload recovery problems so that the device may be used as a precision comparator. Intersil (UK) Ltd, Snamprogetti House, Basing View, Basingstoke, Hants RG21 2YS.

WW309

P.c.b. buzzers

Sound output levels of between 70 and 83 dB(A) at 22cm can be obtained from these miniature p.c.b.-mounting buzzers from Highland Electronics Ltd. Four types are available, in a range from 1.75 to 30V d.c., and the current consumption is 25mA maximum. The frequency of the tone produced is 400Hz. Both flat and right-angle-mounting versions can be obtained, all with dimensions of 22 x 15 x 10mm and weighing 7 gm each. Highland House, 8 Old Steine, Brighton, East Sussex. BN1 1EJ.

WW310

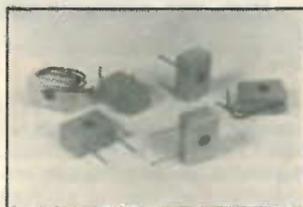

14-bit d-to-a



A signal to noise ratio of typically 85dB in the audio band is one of the features of the TDA1540 14-bit digital to analogue converter from Mullard Ltd. This converter is designed for use as a digital signal processor in sound recording and reproduction systems and includes "on-chip" data latches which eliminate the need for a deglitching circuit at the output. Other specifications for the TDA1540 are a non-linearity error of less than 3.10⁻³, a current settling time 1µs to 1/2 l.s.b. of the 4mA full scale output, 300mW power dissipation and t.t.l. compatible outputs. Mullard Ltd, Mullard House, Torrington Place, London WC1E 7HD.

WW311

Prototype wiring system

An interesting alternative to wire wrap point-to-point wiring has recently been launched in the UK. The system, known as Quick Connect, uses an insulation displacement technique originally developed by Bell Laboratories, and provides sockets or terminals which are compatible with standard p.c.b. holes. Each socket/terminal has an insulation displacement connection tine on the underside of the board, which can accept two 30 gauge solid wires to provide four connections. To make a connection the wire is simply pushed, with the pencil provided, into the tine which penetrates the insulation and forms a gas tight contact with a typical resistance of 10mΩ. Because no wire stripping is necessary the system is very quick, especially when "daisy chain" connections are required. An important advantage of Quick Connect is the re-usable tine, which allows wired boards to be modified or stripped and used again. Another advantage is the low profile, 6.35mm compared with 16.64mm for wire wrap. At present Quick Connect can be used in three ways. Sockets and terminals can be supplied in bandoleer strips for insertion by the user, customers' boards can be factory fitted with the contacts, or standard socket boards can be purchased for general prototyping work. Astralux Dynamics Ltd, Red Barn Road, Brightlingsea, Colchester, Essex.

WW312

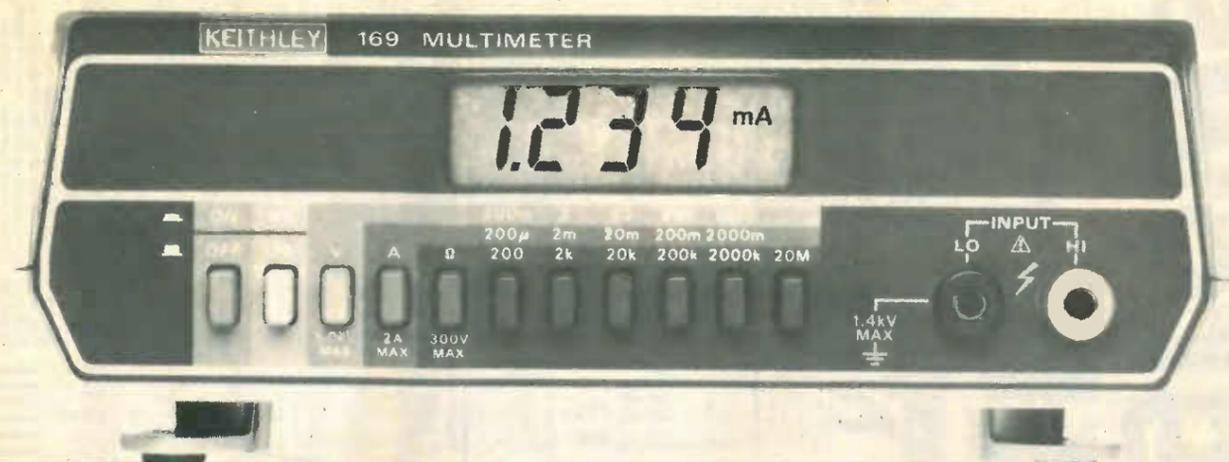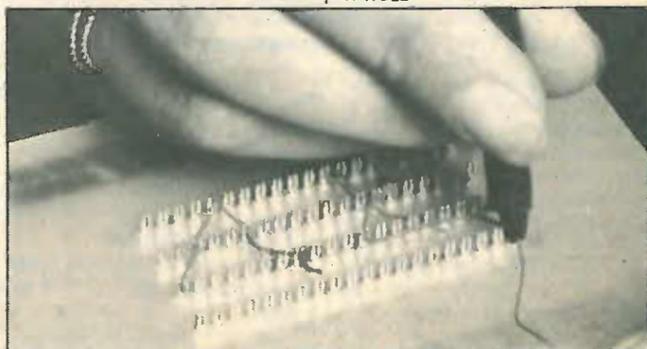

HIGH QUALITY



WIDE CHOICE

Keithley D.M.M. Test Equipment: Quality. With machines like the 169 shown above. 3½ digits; .25% accuracy. A no-nonsense five function D.M.M. at a no-nonsense price.

Choice. The Keithley range spans Pocket, 3½, 4½, 5½ digit D.M.M.'s; many with I.E.E.E. options. So we can be sure of having exactly the right product for your own requirements. Built to a standard that very few people can equal.

LOW COST

Cost. And at a price even fewer can match. From £79 + V.A.T., Keithley D.M.M. test equipment is backed by the resources of a specialist company with a formidable reputation. To find out more, just fill in the coupon, and get your free literature today.



KEITHLEY

Keithley Instruments Ltd
1 Boulton Road Reading Berkshire RG2 0NL
Telephone (0734) 861287
Telex 847047

WW - 083 FOR FURTHER DETAILS

I would like to know more about
Keithley D.M.M.'s. I am particularly
interested in: 3½ Digit Models
 4½ Digit Models 5½ Digit Models
 I.E.E.E. Position

Name _____
Company _____
Address _____
Tel _____

SIMPLY AHEAD
and staying there

The range grows bigger... better...

New Profile Amplifiers - Two New Series

MOSFET


CHOOSE AN I.L.P. MOSFET POWER AMP when it is advantageous to have a faster slew rate, lower distortion at higher frequencies, enhanced thermal stability, the ability to work with complex loads without difficulty and complete absence of cross-over distortion. I.L.P.'s exclusive encapsulation technique within fully adequate heatsinks has been taken a stage further with specially developed computer-verified 'New Profile' extrusions. These ensure optimum operating efficiency from our new MOSFETS, and are easier to mount. Connection is via five pins on the underside. **I.L.P. MOSFETS ARE IDENTICAL IN PERFORMANCE TO THE COSTLIEST AMPLIFIERS IN THIS EXCITING NEW CATEGORY BUT ARE ONLY A FRACTION OF PRICES CHARGED ELSEWHERE.**

| Model | Output Power RMS | Distortion Typical at 1KHz | Slew Rate | Rise Time | Signal/Noise Ratio DIN AUDIO | Price & VAT |
|--------|------------------|----------------------------|-----------|-----------|------------------------------|----------------|
| MOS120 | 60W into 4-8Ω | 0.005% | 20V/μs | 3μs | 100dB | £25.88 + £3.88 |
| MOS200 | 120W into 4-8Ω | 0.005% | 20V/μs | 3μs | 100dB | £33.46 + £5.02 |


BIPOLAR

CHOOSE AN I.L.P. BIPOLAR POWER AMP where power and price are first consideration while maintaining optimum performance with hi-fi quality and wide choice of models. From domestic hi-fi to disco and P.A., for instrument amplification, there is an I.L.P. Bipolar to fill the bill, and as with our new Mosfets, we have encapsulated Bipolars within our New Profile extrusions with their computer-verified thermal efficiency and improved mounting shoulders. Connections are simple, via five pins on the underside and with our newest pre-amps and power supply units, it becomes easier than ever to have a system layout housed the way you want it.


| Model | Output Power RMS | Distortion Typical at 1KHz | Slew Rate | Rise Time | Signal/Noise Ratio DIN AUDIO | Price & VAT |
|-------|------------------|----------------------------|-----------|-----------|------------------------------|----------------|
| HY30 | 15W into 4-8Ω | 0.015% | 15V/μs | 5μs | 100dB | £6.34 + 95p |
| HY60 | 30W into 4-8Ω | 0.015% | 15V/μs | 5μs | 100dB | £7.24 + £1.09 |
| HY120 | 60W into 4-8Ω | 0.01% | 15V/μs | 5μs | 100dB | £15.20 + £2.28 |
| HY200 | 120W into 4-8Ω | 0.01% | 15V/μs | 5μs | 100dB | £18.44 + £2.77 |
| HY400 | 240W into 4Ω | 0.01% | 15V/μs | 5μs | 100dB | £27.88 + £4.15 |

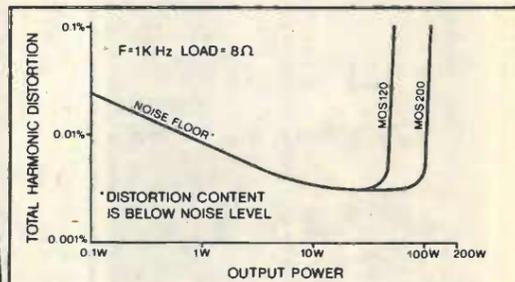

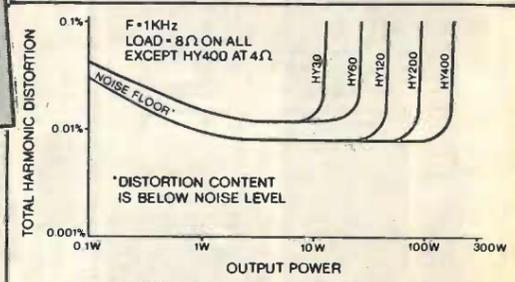Load impedance both models 4Ω - ∞ Input impedance both models 100KΩ
4Ω - ∞ Input sensitivity both models 500mV Frequency response both models 15Hz-100KHz - 3dB



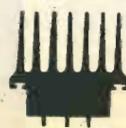Load impedance all models 4Ω - ∞ Input impedance all models 100KΩ
Input sensitivity all models 500mV Frequency response all models 15Hz-50KHz - 3dB



THE NEW PROFILE EXTRUSIONS
The introduction of standard heatsink extrusion for all I.L.P. power amplifiers achieves many advantages: - Research shows they provide optimum thermal dissipation and stability. Slotted shoulders allow easy mounting; standardisation enables us to keep our prices competitive. Surfaces are matt black, anodised for lower thermal conductivity. Extrusions vary in size according to module number.

I.L.P. POWER AMPS ARE ENCAPSULATED FOR THERMAL STABILITY AND LONGER LIFE



HY120




HY60

NEW PRE-AMPS

HY6 (mono) and HY66 (stereo) are new to I.L.P.'s range of advanced audio modules. Their improved characteristics and styling ensure their being compatible with all I.L.P. power-amps both MOSFET and BIPOLAR, giving you chance to get the best possible reproduction from your equipment. HY6 and HY66 pre-amps are protected against short circuit and wrong polarity. Full assembly instructions are provided. Mounting boards are available as below.
Sizes - HY6 - 45x20x40 mm. HY66 - 90x20x40 mm.
Active Tone Control circuits provide ±12dB cut and boost.
Inputs Sensitivity - Mag. PU. -3mV; Mic - selectable 1-12mV; All others 100mV. Tape O/P - 100mV; Main O/P - 500mV; Frequency response - D.C. to 100KHz - 3dB.

HY6 mono £5.60 + 84p VAT Connectors included
HY66 stereo £10.60 + £1.59 VAT Connectors included
B6 Mounting Board for one HY6 78p + 12p VAT
B66 Mounting Board for one HY66 99p + 15p VAT

COMPATIBLE WITH ALL I.L.P. MODULES

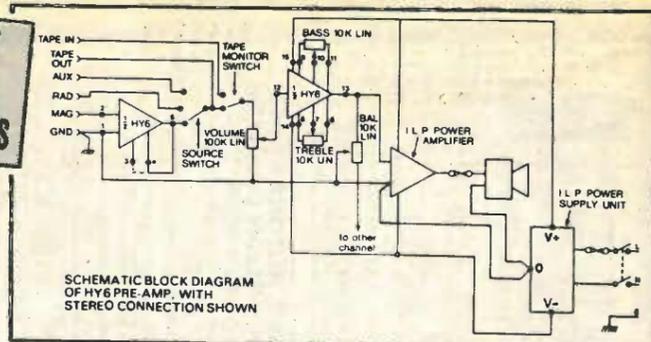

- DISTORTION TYPICALLY 0.005%
- S/N RATIO - 90dB (Mag. P.U. - 68 dB)
- 38 dB overload margin on Mag. P.U.
- LATEST DESIGN HIGH QUALITY CONNECTORS
- ONLY POTS, SWITCHES AND PLUGS/SOCKETS NEED ADDING
- NEEDS ONLY UNREGULATED POWER SUPPLY ±15 to ±60v

NEW POWER SUPPLY UNITS

Of the eleven power supply units which comprise our current range, nine have toroidal transformers made in our own factory. Thus these I.L.P. power supply units are space-saving, more efficient and their better overall design helps enormously when assembly building. All models in the range are compatible with all I.L.P. amps and pre-amps with types to match whatever I.L.P. power amps you choose.

- PSU30 ±15V at 100mA to drive up to 12 x HY6 or 6 x HY66 £4.50 + 0.68p VAT
- THE FOLLOWING WILL ALSO DRIVE I.L.P. PRE-AMPS
- PSU36 for use with 1 or 2 HY30's £8.10 + £1.22 VAT
- ALL THE FOLLOWING USE TOROIDAL TRANSFORMERS
- PSU50 for use with 1 or 2 HY60's £9.75 + £1.46 VAT
- PSU60 for use with 1 HY120 £9.75 + £1.46 VAT
- PSU65 for use with 1 MOS120 £9.75 + £1.46 VAT
- PSU70 for use with 1 or 2 HY120's £13.61 + £2.04 VAT
- PSU75 for use with 1 or 2 MOS120 £13.61 + £2.04 VAT
- PSU90 for use with 1 HY200 £13.61 + £2.04 VAT
- PSU95 for use with 1 MOS200 £14.75 + £2.21 VAT
- PSU180 for use with 1 HY400 or 2 HY200 £23.02 + £3.45 VAT
- PSU185 for use with 1 or 2 MOS200 £24.20 + £3.63 VAT

IN A RANGE OF 11 MODELS USING LATEST TOROIDAL TRANSFORMERS

1971-1980 TEN YEARS OF PLANNED PROGRESS

When, in 1971, Ian L. Potts founded his now world-famous company, he saw the need for a different and more rational approach to exploiting to the full, the potential that lay in modular construction. New thinking was badly needed. The result was a range of modules revolutionary in concept. The rightness of this new thinking is shown by the size of the company today, its vast exports, its acceptance by constructors as the modules to build with. The range grows bigger and better. Exciting new lines (in no way conflicting with existing ones) are well past drawing board stage. This is why I.L.P. are simply ahead and staying there.

BRITAIN'S FASTEST GROWING MODULE SUPPLIERS

To: I.L.P. ELECTRONICS LTD. CANTERBURY CT2 7EP

Please supply Total purchase price £.....

I enclose Cheque Postal Orders International Money Order

Please debit my Access/Barclaycard Account No.

NAME

ADDRESS

Signature

NO QUIBBLE 5 YEAR GUARANTEE
7-DAY DESPATCH ON ALL ORDERS
BRITISH DESIGN AND MANUFACTURE
FREEPOST SERVICE



ELECTRONICS LTD.

FREEPOST 5 Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP.
Telephone (0227) 54778 [Technical (0227) 64723] Telex 965780
Available also from MARSHALLS, WATFORD ELECTRONICS and certain other selected retailers

ALL UK ORDERS DESPATCHED FREE

HERE IT IS! THE BRAND NEW 8022A HAND-HELD DMM

Consider the following features:
 6 resistance ranges from 200 ohm-20 ohms
 8 current ranges from 2mA-2A AC/DC
 10 voltage ranges from 200 mv-1000v DC-200 mc-750V AC
 Pocket size — weighing only 370 gms.
 Full overload protection — will withstand 6kv spikes
 Rugged construction — virtually indestructible
 Meets tough military specs — drop proof
 In line, pushbutton operation for single-handed use
 Incorporates low power CMOS chip for low power consumption
 All this plus a 2-year full guarantee



For only £75 + VAT SOFT CARRYING CASE £7 extra
 Carriage and Insurance £3

Even more sophisticated the Fluke 8020A identical in most respects to the 8022A but in addition incorporates a conductance range from 2mS-200nS.

Price £112

Carriage and insurance £3.00


A handsome soft carrying case is included (this model only)



DIGITAL MULTIMETERS BRAND NEW FROM FLUKE!!! NOW AVAILABLE THE 8024A HAND HELD DMM

This model incorporates all the features of the 8020A but in addition has:
 A peak hold switch which can be used in AC or DC for volts and current functions.
 Audible continuity testing and level detection for sensing logic levels.
 A temperature (°C) range for use with a thermocouple. £135
 Carriage and Insurance £3

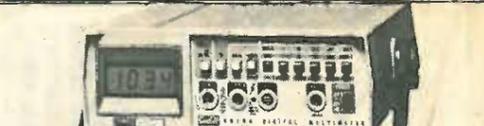The following accessories are in stock now
 Y8008 Touch and Hold Probe £18.00
 80K-40 High Voltage Probe £45.00
 81RF RIF Probe to 100 MHz £32.00
 80T-150C Temperature Probe (C) £55.00
 801-600 Clamp-on AC Current Probe £55.00



8010A AND 8012A BENCH MODEL D.M.M.s

The 8010A is a general purpose, bench/ponable digital multimeter with more functions and features than ever offered for such a low price. Its companion, the 8012A, has identical characteristics except that it has two additional low resistance ranges, 2Ω and 20Ω to replace the 8010A's 10 ampere current range.
 The 8010A and 8012A feature:
 10 voltage ranges from 200mv - 1000v dc, 200mv - 75v ac.
 3 conductance ranges from 2mS - 200 nS.
 6 resistance ranges from 200Ω - 20mΩ - the 8012A has two additional resistance ranges 2Ω and 20Ω.
 10 current ranges from 200μA - 2A AC/DC — the 8010A has two additional current ranges 10A AC and 10A DC.

8010A £159 8012A £199
 Carriage and Insurance £3
 The 8010A is also available with two rechargeable Nicad size C batteries installed in option 01 at £179.00.

LOW COST, AUTORANGING MULTI-FUNCTION COUNTER MODEL 1900A

- Autoranging in both frequency and period measurement modes
- Wide Frequency range — 5 Hz to 80 MHz
- High sensitivity — 25 mV, typically 15 mV
- Six digit LED display with leading zero suppression, automatic annunciation and overflow
- Optional internal battery pack providing 4 hours continuous operation
- Autoreset on all gate times, all function switches
- Four manually selected gate times providing resolution to 0.1 Hz
- Event counting to 10⁶ events with overflow indicator
- Signal input conditioning with switchable 1 MHz low pass filter and attenuator
- Rugged moulded case with convenient tilting/carrying handle
- Optional parallel data output with decimal point and annunciation
- Traditional high Fluke quality
- Self check

£195 Carriage and Insurance £3

Y7206 EN 20,000 OPV
 AC Volts: 0-10, 50, 250, 500, 1000
 DC Volts: 0-0.5, 5, 25, 125, 250, 500, 1000
 DC Current: 0-0.05, 5, 250 mA.

TMK500 30,000 OPV
 A sturdy and reliable instrument. Has internal buzzer.
 AC volts: 0 to 2.5, 10, 25, 100, 250, 500, 1000
 DC volts: 0 to 0.25, 1, 2.5, 10, 25, 100, 250, 1000. DC current: 0 to 50 μa, 5 ma, 50 ma, 12 amp.

PLEASE ADD 15% VAT TO ALL ORDERS EXCEPT WHERE ITEMS MARKED "VAT INCLUDED." CALLERS WELCOME
 We are open 9 a.m.-6 p.m. Monday-Saturday
 We carry a very large selection of electronic components and electro-mechanical items. Special quotations on quantities

ROTARY STUD SWITCH
 PLESSEY 30-way, 2 bank, Single pole. Contacts 1 amp 240v, AC/DC. 0.05Ω res. Make before break. Stop infinitely adjustable allowing for any desired arc of travel. Ideal for instrument and model switching. Size 2 1/4" dia. overall x 2 1/4" deep plus 1 1/4" x 1/4" dia. spindle.
£3.25 P&P 50p

BENDIX MAGNETIC CLUTCH
 Superb example of electro-mechanics. Main body in two sections, coil section fixed with 3/8" sleeve, drive section rotating on outer perimeter. Uniting plate has 3/8" IO bearing concentric with main section and 18-tooth cog wheel. Extremely powerful transmission. 24V D.C. 240 m/a.
£4.75. P.&P. 75p

Resistance 0-3k ohms 300k ohms, 3 meg ohms
 Decibels — 20 — +63 db.
 Dims 127 x 90 x 32 mm.
£10.95 P & P 75p


Resistance: 0 to 6K, 60K, 6 meg, 60 meg.
 Decibels: — 20 to +56 db.
 Short test: Internal buzzer.
 Size: 180 x 110 x 55 mm.
£20.50. P.&P. 75p

ELECTRO-TECH COMPONENTS LTD.
 364 EDGWARE ROAD, LONDON, W.2. TEL: 01-723 5667

elektor PRINTED CIRCUIT BOARDS

Did you know that Elektor is the only monthly electronics magazine to supply printed circuit boards for featured projects? At present over 300 different boards are available with designs covering many aspects of the hobby, ranging from microcomputers to electronics in the car. Disco and live music is the theme for the January issue and constructional articles include a versatile multichannel mixer, a 200 Watt power amplifier, a sound level meter and a very unusual VU meter.

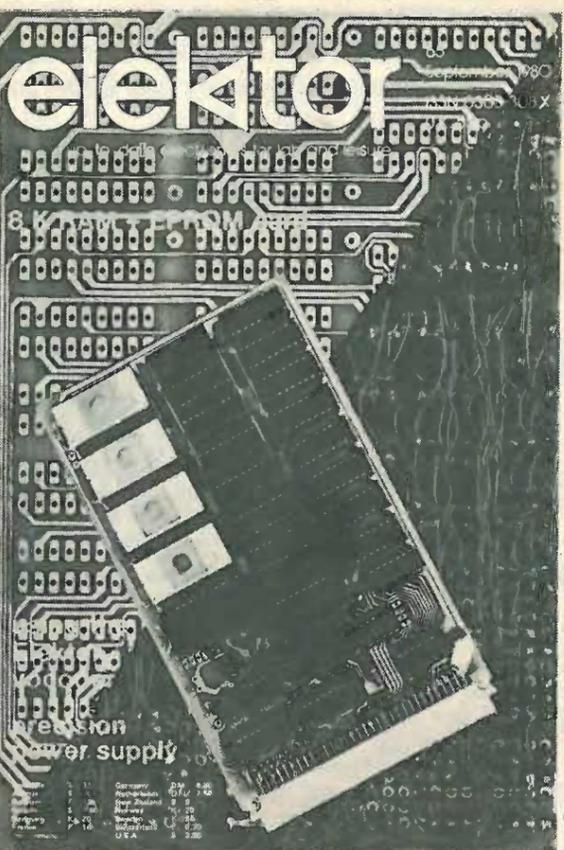Place an order with your newsagent or order direct from Elektor Publishers Ltd., 10 Longport, Canterbury, Kent. Price 60p (+20p postage and packing)



S 100

Do You Have All These Facilities On Your S 100 System, With Just Two Boards?

1. Z80A CPU-2 or 4 MHz Operation.
2. Z80A CTC — 4 Channels.
3. Z80A S10 — 2 RS-232.
4. Z80A P10.
5. Disk controller; Takes up to 4 disk drives, single or double density operation.
6. 64k Bytes of memory.
7. EPROM Programmer.
8. Real time clock.
9. Software; Standard 2k Monitor. CP/M Cold Start Loader. CP/M B10S (1.4).

Prices:
 FDC-1 Board **£495.50**
 Expandoram **£327.56**
 Mother Board **£42.00**
 All prices exclude VAT.

SEMEL
 MICROCOMPUTER - HARDWARE - SOFTWARE
 3c Barley Market Street, Tavistock, Devon PL19 0JF
 Tel. Tavistock (0822) 5247. Telex: 45263

Happy Memories

| | | |
|------|--------|--------------|
| 4116 | 200ns | £2.95 |
| 2114 | 200ns | £3.45 |
| 2708 | 450ns | £4.75 |
| 2114 | 450ns | £2.95 |
| 2716 | 5 volt | £7.95 |

Memorex Soft-sectored mini-discs for PET, TRS-80 etc. Supplied in FREE LIBRARY CASE, £19.95 per 100

Low Profile I.C. Sockets by 'Texas'

| | |
|-------|----------------------------|
| Pins | 8 14 16 18 20 22 24 28 40 |
| Pence | 10 11 12 16 17 20 21 28 37 |

Memory Upgrade Kits for Apple, 2020, TRS-80 etc: from £30, please phone. Quantity prices available on request. Government and Educational Orders welcome Trade accounts opened

All prices include VAT. Postage FREE on orders over £10, otherwise add 30p. Access & Barclaycard welcome

HAPPY MEMORIES, DEPT. W.W. GLADESTRY, KINGTON HEREFORDSHIRE HR5 3NY Tel. (054422) 618

CHILTERN ELECTRONICS

B.C.M. BOX 8085, LONDON WC1N 3XX TEL: 0494 714483

TERMINALS
 G.E. Terminet 300: Modern micro-controlled 30 cps terminal, RS232 ASCII with correspondence quality upper and lower case impact print. Ideal for word processors. With electronic keyboard Brand new **£400**
 Second-hand working **£300**
 QUME Q-30 Daisy wheel printer **£400**
 CENTRONICS 102A Printers, 330 ch/sec., perfect working order with stand **£350**
 LEAR SIEGLER 200 Series Ballistic printers, brand new. Cost over £1200 **£625**
 A.C.T. 165 cps Matrix Printers **£220**

DISKS
 Diablo Series 30 2.5 MByte exchangeable disk drives — fully compatible with DEC RK05 **£450**
 IBM 3470 Floppy Disk Drives, new **£350**
 Above prices exclude VAT

DEC PDP8/PDP11 COMPUTERS
 PDP LSI-11 System running RT-11: LSI-11 Processor + 32K Memory + Diablo 30 Disk Drive, takes RK05 Compatible 2.5 MByte disks. Disk Controller. Two DLV11 Serial Interface cards. Complete system **£2500**
 PDP8E Processor, full 32K Core memory, programmers console, teletype and DMA Interface cards. As new **£1150**
 PDP8F Computer, 16K Core, programmers console, teletype interface **£650**
 PDP8L Processors, with memory expansion unit, total 12K core, and teletype interface **£250**
 All above are compact table-top computers, working and ready to use. Software available includes all the major languages.

The above items are only a small selection of our second-user equipment; please telephone for a complete list. We hold a full range of spares for most DEC PDP8 and PDP11 computers.

WW — 082 FOR FURTHER DETAILS

READ ALL ABOUT IT — all the latest on home entertainment equipment and ideas in . . .


HI FI YEARBOOK AND HOME ENTERTAINMENT 1981

Published again in November, this new 1981 edition in larger magazine size means more comprehensive coverage of the whole range of home entertainment equipment, from aeriols to headphones, from microphones to video recorders and from radios to electronic organs.

Backed by authoritative articles on developments in the world of Hi Fi, plus details of stockists, Hi Fi Yearbook and Home Entertainment 1981 is essential reading for enthusiasts and buffs.

Available from leading newsagents and bookshops from 1st November 1980. Price £3.00.

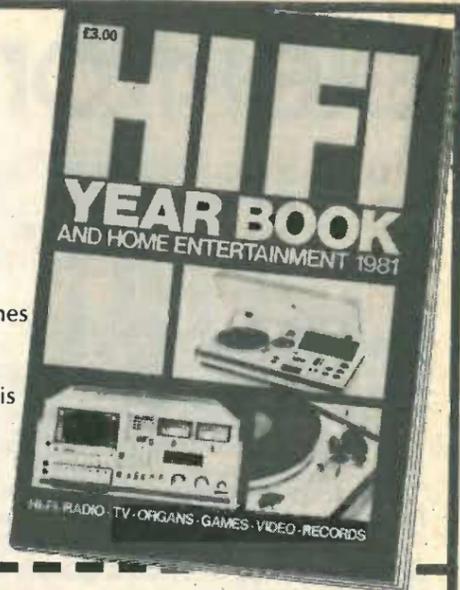If you have difficulty in obtaining your copy order direct from the publishers @ £3.50 inclusive.



ORDER FORM

To: General Sales Manager, Room 205, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS.

Please send me copy/copies of the Hi Fi Yearbook and Home Entertainment 1981 @ £3.50 including postage and packing. Cheque/postal order should be made payable to IPC Business Press Ltd.

Name _____
(please print)

Address _____

Registered in England No: 677128.

WW2

RADIO SHACK LTD for DRAKE



TR-7 Transceiver

Ham Bands with 1.5-30 MHz receive with built-in 150 MHz frequency counter plus option of 0-1.5 MHz receive and / or any transceiving application 1.8-30 MHz.

RADIO SHACK LTD

For Communications equipment including Trio products and Trio testgear.

We are situated just around the corner from West Hampstead Underground Station (Bakerloo line). A few minutes' walk away is West Hampstead Midland Region station and West End Lane on the Broad Street Line. We are on the following Bus routes: 28, 59, 159. Hours of opening are 9-5 Monday to Friday. Closed for Lunch 1-2. Saturday we are open 9-12.30 only. World wide exports.

DRAKE * SALES * SERVICE

RADIO SHACK LTD

188 BROADHURST GARDENS, LONDON NW6 3AY

Giro Account No. 588 7151. Telephone: 01-624 7174

Cables: Radio Shack, London, NW6. Telex: 23718

WW-035 FOR FURTHER DETAILS

HIBED

L.E.D.s .125 and .2

| | | | |
|----------|-----|------|-------|
| | 1+ | 100+ | 1000+ |
| RED | .08 | .069 | .058 |
| YELLOW | | | |
| OR GREEN | .11 | .10 | .09 |

1N4148 Diodes

| | | |
|--|-------|------|
| | 1+ | .02 |
| | 100+ | .016 |
| | 1000+ | .013 |

Prices per 100. Larger and Mixed. Quantity prices available.

CARBON FILM RESISTORS E12 SERIES

| | | |
|-------------------|------|------|
| | .25W | |
| 100 off one type | | .70p |
| 500 off one type | | .64p |
| 1000 off one type | | .58p |
| | .5W | |
| 100 off one type | | .90p |
| 500 off one type | | .80p |
| 1000 off one type | | .72p |

T.I. LOW PROFILE I.C. SOCKETS

| | | | |
|-------|-------|-------|------|
| | 1+ | 100+ | 500+ |
| 8pin | .075p | .068p | .06p |
| 14pin | .09 | .082 | .073 |
| 16pin | .10 | .096 | .085 |
| 18pin | .125 | .113 | .10 |
| 20pin | .14 | .126 | .113 |
| 22pin | .15 | .135 | .12 |
| 24pin | .15 | .135 | .12 |
| 28pin | .16 | .145 | .125 |
| 40pin | .24 | .215 | .19 |

Please add £1.50 handling charge and 15% V.A.T.

We also stock transistors, diodes, TTL, CMOS, capacitors, switches, connectors etc. Free catalogue available to trade customers only. Enquiries welcome.

Harrison Bros.

Electronic Distributors

22 Milton Road, Westcliff-on-Sea
Essex SS0 7JX England

Tel. Southend-on-Sea (0702) 32338

WW-044 FOR FURTHER DETAILS

MICROSYSTEMS '81

EXHIBITION & CONFERENCE

March 11-13, 09.30-18.00 daily

Wembley Conference Centre

Exhibition admission £1.00

A complete study of microprocessors in use.


Microsystems '81 consists of a wide ranging exhibition, together with a three day conference and three one-day microprocessor awareness courses. Together they comprise an invaluable opportunity for those interested in microprocessor applications and the latest developments in microelectronics technology.

Take advantage of this unique event to examine and discuss a comprehensive range of microprocessors, peripherals, memory products and personal computers together with the software which accompanies them.

For Conference details write to: The Conference Administrator IPC Conferences Ltd, Surrey House, 1 Throwley Way, Sutton, Surrey SM1 4QQ

For *advance exhibition tickets at £1 each, write to: Microsystems Tickets IPC Exhibitions Ltd, Surrey House, 1 Throwley Way, Sutton, Surrey SM1 4QQ

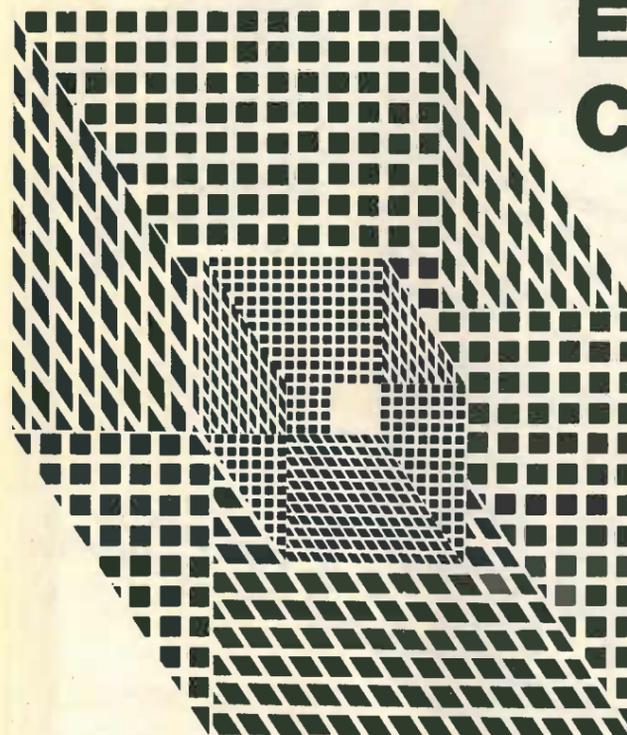*Please note applications for tickets cannot be accepted after February 23, although tickets will be available at the door price £1. Cheques should be made payable in UK sterling to IPC Business Press Limited.



CB -the countdown has begun!

Get ready for Citizens Band radio with a brand-new magazine that tells you everything you want to know. We show you how CB works and how to use it. We've got a full colour spread on customised American trucks. We offer special deals on CB World sweat shirts, T shirts, caps and badges. And we ask: should we use US Truck speak or create our own English jargon? And what about the radio amateur — and the aircraft modeller? Tell us what you feel. Get involved — and get this very first issue of **CB World!**

Published by IPC — the world's largest publisher of radio and electronic magazines.



RECHARGEABLE BATTERIES

TRADE ENQUIRIES WELCOME

Full range available to replace 1.5 volt dry cells and 9 volt PP type batteries, SAE for lists and prices. £1.45 for booklet, "Nickel Cadmium Power," plus catalogue.

★ New sealed lead range now available ★

Write or call at:

SANDWELL PLANT LTD.
2 Union Drive, Boldmere
Sutton Coldfield, West Midlands. 021-354 9764

TV TUBE REBUILDING

Faircrest Engineering Ltd., manufacture a comprehensive range of equipment for processing all types of picture tubes, colour and mono. Standard or custom built units for established or new businesses. We export world-wide and have an excellent spares service backed by a strong technical team.

Full training courses are individually tailored to customers' requirements.

For full details of our service contact Neil Jupp

FAIRCREST ENGINEERING LTD.

Willis Road, Croydon, CR02XX.
01-684 1422, 01-689 8741

WW-043 FOR FURTHER DETAILS

Anyway you look at it,



it's small.

Except in performance. Anders' new OEM-1 digital panel meter module is ultra-compact size. In OEM quantities, it is also ultra-low in price and power consumption — thanks to the latest micro-miniaturisation techniques. So OEM-1's high performance makes it especially suitable for new designs of hand-held, low-power multimeters, digital

thermometers, pH meters, moisture meters, resistance meters, etc. High performance plus large liquid crystal display also means it can replace many panel-mounting digital or analogue meters — at an analogue display price. OEM-1 is just one of Anders' modern range of digital and analogue panel meters. Send for details now.



Foremost in meters
Anders Electronics Limited, 48-56 Bayham Place,
Bayham Street, London NW1 0EU, Tel: 01-387 9092, Telex: 27364.

WW — 076 FOR FURTHER DETAILS

HART

SUPER BARGAIN OFFERS LENCO FFR CASSETTE DECK

For those who missed our recent bargain CT4s we now are delighted to be able to offer Brand New Lenco FFR Decks complete with motor speed and auto-stop control board fitted and tested. These will operate with any supply between 9 and 16 volts. This deck can be used for both record and playback applications and is fitted with an erase head. A mono record/play head is fitted and we can supply an extra stereo head, if ordered with the deck at the very special price of £2 plus VAT. We also supply, with each deck and completely FREE, one of our specially moulded escutcheons. This deck would normally cost about £25 but we are able to offer them, while they last, at only £9.99 plus VAT.



TOP LOADING HI FI CASSETTE DECK. Very limited quantity of British made Thorn 4499 top loading decks fitted with stereo R/P head, 3 digit re-settable counter, 12 volt electronic speed controlled motor and auto stop read.


Very special price £12.99 Complete with top cover and cassette door. Post etc. £1.50. VAT £2.34.

LINSLEY-HOOD PEAK DRIVE INDICATOR

A very useful device, connected to loudspeakers giving a 4 light readouts of peak power delivered for the protection of both the loudspeaker and the perceived quality of sound. Gives instant indication even for peaks of only 5 microseconds duration. Unit uses CMOS technology, is self-contained and battery powered. Complete Kit except batteries, only £17.40 plus VAT.

Reprint of Article 250. No VAT. Post Free.

LINSLEY HOOD CASSETTE RECORDER 1

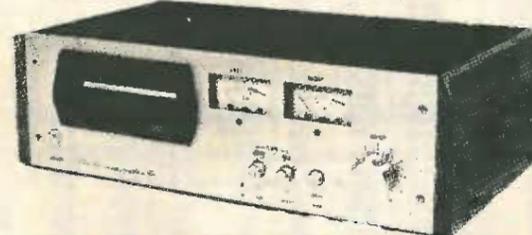

We are the Designer Approved suppliers of kits for this excellent design. The Author's reputation tells all you need to know about the circuitry and Hart expertise and experience guarantees the engineering design of the kit. Advanced features include: High-quality separate VU meters with excellent ballistics. Controls, switches and sockets mounted on PCB to eliminate difficult wiring. Proper moulded escutcheon for cassette aperture improves appearance and removes the need for the cassette transport to be set back behind a narrow finger trapping slot. Easy to use, robust Lenco mechanism. Switched bias and equalisation for different tape formulations. All wiring is terminated with plugs and sockets for easy assembly and test. Sophisticated modular PCB system gives a spacious, easily built and tested layout. All these features added to the high-quality metalwork make this a most satisfying kit to build. Also included at no extra cost is our new HS15 Sendust Alloy record/play head, available separately at £7.60 plus VAT, but included FREE as part of the complete kit at £75 plus VAT.

REPRINTS of the 3 articles describing this design 45p. No VAT.

REPRINT of Postscript article 30p. No VAT.

Part Cost of Post, Packing and Insurance.

Order up to £10 — 50p P&P Export Orders — Postage or shipping at cost plus
Orders £10 to £49 — £1 £2 Documentation and Handling
Over £50 — £1.50

Please send 9x4 SAE for lists giving fuller details and price breakdowns.

Instant easy ordering, telephone your requirements and credit card number to us on
Oswestry (0691) 2894

Personal callers are always welcome but please note we are closed all day Saturday



NEW NEW NEW

Linsley-Hood 35 and 45 Watt MOSFET Power Amplifiers

New. Latest hot-off-the-press design by John Linsley-Hood described in this month's issue of Hi Fi News. External appearance is identical to the 30 watt design but minor circuit changes and MOSFET output devices give lower distortion, audibly better sound and higher power output. The delicacy and transparency of tone quality enable this amplifier to outperform on a side-by-side comparison the bulk of amplifiers available today, even surpassing the Authors own 75watt design.

Complete Kit for fully integrated 35watt MOSFET amplifier £87.40. Plus VAT. Same but 45watt output £94.80. Plus VAT.

Conversion Kit with full instructions for use with existing 30-watt amplifiers £16.90. Plus VAT.

Reprints of MOSFET article. 25p. No VAT. Post Free.

LINSLEY-HOOD 30 WATT AMPLIFIER




The very latest amplifier design to be published and in our opinion the best yet. The concept was to produce an amplifier that sounded as good as the authors 75 watt design but which was cheaper and simple to build for applications where the higher power is not needed. This new kit is designed to match the Linsley-Hood Cassette Recorder 2 and a tuner will be available later to make a complete stackable system. A very advanced assembly system has been devised by us to make construction ultra simple and anyone who can solder components in a printed circuit board will find it great fun. Conventional wiring is at an irreducible minimum, only being needed to connect the mains transformer and pilot light. For an amplifier of this quality this kit represents incredible value for money.

All parts can be bought separately at a total cost of £79.12 but complete kits are available at a special introductory discount price of only £72 + VAT.

Reprints of original Articles from 'Hi Fi News' 50p. Post Free. No VAT.

LINSLEY HOOD CASSETTE RECORDER 2

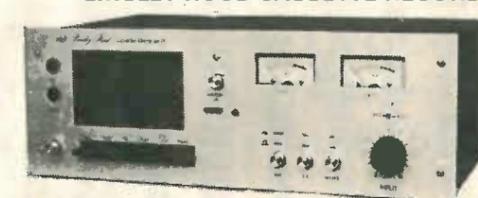

Our new improved performance model of the Linsley Hood Cassette Recorder incorporates our VFL 910 vertical front mechanism and circuit modifications to increase dynamic range. Board layouts have been altered and improved but retain the outstandingly successful mother and daughter arrangement used on our Linsley Hood Cassette Recorder 1.

This latest version has the following extra features. Ultra low wow-and-flutter of .09% — easily meets DIN Hi-Fi spec. Deck controls latch in rewind modes and do not have to be held. Full Auto stop on all modes. Tape counter with memory rewind. Oil damped cassette door. Latching record button for level setting. Dual concentric input level controls. Phone output. Microphone input facility if required. Record interlock prevents re-recording on valued cassettes. Frequency generating feedback servo drive motor with built-in speed control for thermal stability. All these desirable and useful features added to the excellent design of the Linsley-Hood circuits and the quality of the components used makes this new kit comparable with built-up units of much higher cost than the modest £94.90 + VAT we ask for the complete kit.

CASSETTE HEADS

| | |
|---|------|
| HS15 SENDUST ALLOY SUPER HEAD. Stereo R/P. Longer life than Permalloy. Higher output than Ferrite. Fantastic frequency response. Complete with data | 7.60 |
| HS16 Very latest Sendust Alloy Super Head with even better HF Response | 8.20 |
| HC20 Stereo Permalloy R/P head for replacement uses in car players, etc. | 4.25 |
| HM90 Stereo R/P head for METAL tape. Complete with data | 7.20 |
| HS61 Special Erase Head for METAL tape | 4.90 |
| HS24 Standard Ferrite Erase Head | 1.50 |
| 4-Track R/P Head. Standard Mounting | 7.40 |
| R4B4 2/2 (Double Mono) R/P Head. Std. Mtg. | 4.90 |
| ME151 2/2 Ferrite Erase. Large Mtg. | 4.25 |
| CCE/8M 2/2 Erase. Std. Mtg. | 7.90 |

All prices plus VAT

HART

HART ELECTRONIC KITS LTD
PENYLAN MILL OSWESTRY
SHROPSHIRE
phone (0691) 2894
Telex 35661
Hartel G

LANGREX SUPPLIES LTD


Climax House, Fallsbrook Rd., Streatham, London SW16 6ED

RST Tel: 01-677 2424 Telex: 946708 **RST**

| SEMICONDUCTORS | | | |
|----------------|------|-------|------|
| AA119 | 0.12 | AS215 | 1.38 |
| AA130 | 0.20 | AS216 | 1.27 |
| AA132 | 0.17 | AS217 | 1.15 |
| AA133 | 0.16 | AS220 | 2.84 |
| AA134 | 0.17 | AS221 | 2.88 |
| AA137 | 0.13 | AU113 | 2.88 |
| AC107 | 0.67 | AU110 | 2.88 |
| AC125 | 0.29 | BA147 | 0.15 |
| AC126 | 0.29 | BA148 | 0.15 |
| AC127 | 0.29 | BA149 | 0.15 |
| AC128 | 0.35 | BA150 | 0.12 |
| AC141 | 0.32 | BA151 | 0.13 |
| AC141K | 0.40 | BA152 | 0.12 |
| AC142 | 0.40 | BA153 | 0.12 |
| AC142K | 0.40 | BA154 | 0.12 |
| AC176 | 0.35 | BA155 | 0.13 |
| AC187 | 0.32 | BA156 | 0.12 |
| AC188 | 0.32 | BA157 | 0.12 |
| AC189 | 0.32 | BA158 | 0.12 |
| AC191 | 1.50 | BA159 | 0.18 |
| AC192 | 1.32 | BA160 | 0.17 |
| AC193 | 1.27 | BA161 | 0.17 |
| AC194 | 1.27 | BA162 | 0.17 |
| AC195 | 1.27 | BA163 | 0.17 |
| AC464 | 1.27 | BA432 | 0.17 |
| AC465 | 1.27 | BA433 | |

FYLDE

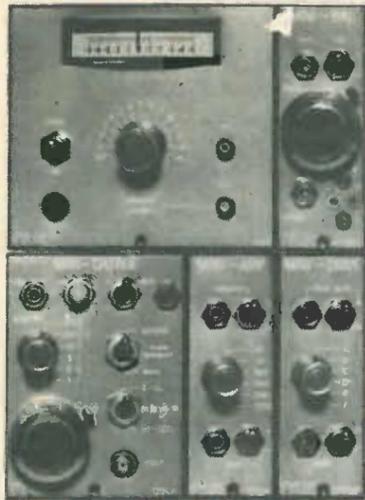TRANSDUCER and RECORDER AMPLIFIERS and SYSTEMS



reliable high performance & practical controls. individually powered modules—mains or dc option single cases and up to 17 modules in standard 19" crates small size—low weight—realistic prices.

FYLDE

Fylde Electronic Laboratories Limited.

49/51 Fylde Road Preston PR1 2XQ
Telephone 0772 57560

WW — 061 FOR FURTHER DETAILS

PRINTED CIRCUITS

FOR WIRELESS WORLD PROJECTS

| | |
|--|---------------------|
| U.h.f. television tuner—Oct. 1975—1 d.s. | £8.50 |
| Stripline r.f. power amp—Sept. 1975—1 d.s. | £5.00 |
| Audio compressor/limiter—Dec. 1975—1 s.s. (stereo) | £4.25 |
| F.m. tuner (advanced)—April 1976—1 s.s. | £5.00 |
| Cassette recorder—May 1976—1 s.s. | £5.00 |
| Audio compander—July 1976—1 s.s. | £4.25 |
| Time code clock—August 1976—2 s.s. 3 d.s. | £15.00 |
| Date, alarm, b.s.t. switch—June 1977—2 d.s. 1 s.s. | £9.50 |
| Audio preamplifier—November 1976—2 s.s. | £8.50 |
| Additional circuits—October 1977—1 s.s. | £4.00 |
| Stereo coder—April 1977—1 d.s. 2 s.s. | £8.50 |
| Morse keyboard and memory—January 1977—2 d.s. (logic board 10 1/4 in. x 5 in.) (keyboard and matrix 13 in. x 10 in.) | £14.00 |
| Low distortion disc amplifier (stereo)—September 1977—1 s.s. | £2.00 |
| Low distortion audio oscillator—September 1977—1 s.s. | £3.50 |
| Synthesized f.m. transceiver—November 1977—2 d.s. 1 s.s. | £12.00 |
| Morsemaker—June 1978—1 d.s. | £4.50 |
| Metal detector—July 1978—1 d.s. | £3.75 |
| Oscilloscope waveform store—October 1978—4 d.s. | £18.00 |
| Regulator for car alternator—August 1978—1 s.s. | £2.00 |
| Wideband noise reducer—November 1978—1 d.s. | £5.00 |
| Versatile noise generator—January 1979—1 s.s. | £5.00 |
| 200MHz frequency meter—January 1979—1 d.s. | £7.00 |
| High performance preamplifier—February 1979—1 s.s. | £5.50 |
| Distortion meter and oscillator—July 1979—2 s.s. | £5.50 |
| Moving coil preamplifier—August 1979—1 s.s. | £3.50 |
| Multi-mode transceiver—October 1979—10 d.s. | £35.00 |
| Amplification system—October 1979—3 preamp 1 poweramp | (£4.20 each) £16.00 |
| Digital capacitance meter—April 1980—2 s.s. | £7.50 |
| Colour graphics system—April 1980—1 d.s. | £18.50 |
| Audio spectrum analyser—May 1980—3 s.s. | £10.50 |
| Multi-section equalizer—June 1980—2 s.s. | £8.00 |
| Floating-bridge power amp—Oct. 1980—1 s.s. (12V or 40V) | £4.00 |

Boards are glassfibre, roller-tinned and drilled. Prices include V.A.T. and U.K. postage. Airmail add 20%, Europe add 10%, Insurance 10%.

Remittance with order to:
M. R. SAGIN, 23 KEYES ROAD, LONDON, N.W.2

WW—033 FOR FURTHER DETAILS

SWITCHCRAFT XLR CONNECTORS

| | | | |
|-----------------|-------|--------------------|-------|
| Line Female A3F | £0.99 | Chassis Female D3F | £1.25 |
| Line Male A3M | £0.88 | Chassis Male D3M | £0.71 |

4, 5 and 6 pin versions and large selection audio adaptors available

NEUTRIK XLR CONNECTORS

| | | | |
|------------------------------------|-------|----------------------------------|-------|
| Latchless Chassis Female NC3-FZ | £0.67 | Latchless Chassis Male NC3-MZ | £0.59 |
| PCB Mounting Chassis Female NC3-FD | £1.12 | PCB Mounting Chassis Male NC3-MD | £0.95 |

Please specify horizontal or vertical mounting PCB format.

BELCLERE AUDIO TRANSFORMERS

| | |
|--|-------|
| EN6422 Ratio 1 + 1:2 + 2. Freq. 40Hz-35KHz. PCB Mount. PRI 150/600Ω. sec. 600/2.4KΩ | £2.90 |
| EN6423 Ratio 1 + 1:6.45 + 6.45. Freq. 40Hz-25KHz. PCB Mount. PRI 150/600Ω. sec. 6.25K/25KΩ | £2.90 |
| SKT-723 MuMetal Screening can. 39dB reduction 50Hz ext. field | £0.95 |

Trade enquiries welcome, quality discounts available. All prices subject to VAT. Call, write or phone. Minimum order £10. Please add £1 postage. Access, AmEx, Barclaycard.

KELSEY ACOUSTICS LTD.

28 POWIS TERRACE, LONDON W11 1JH
01-727 1046

WW — 052 FOR FURTHER DETAILS

ELECTRONIC VALVES WANTED

All Types Receiving, Transmitting, Industrial

PL504 — PL802 — PCL805 — CV131 — CV136 — CV138 — CV329 — CV345 — CV450 — 805 — 807 — 813 — 2K25, Etc.

Phone/write to:
PYPE HAYES RADIO LTD.
606 Kingsbury Road
Birmingham B24 9PJ
021-373 4942

WW — 026 FOR FURTHER DETAILS

Memories

| | | |
|------------|--------------|--------|
| 2114-300ns | 1k x 4 SRAM | £2.25 |
| 4116-200ns | 16k x 1 DRAM | £2.61 |
| 2708-450ns | 1k x 8 EPROM | £3.60 |
| 2516-450ns | 2k x 8 EPROM | £7.92 |
| 2716-450ns | 2k x 8 EPROM | £7.92 |
| 2532-450ns | 4k x 8 EPROM | £23.40 |

Please add 50p for postage and VAT
Send SAE for price list

STRUTT LTD.

**ELECTRONIC COMPONENT DISTRIBUTORS
MANUFACTURERS & SUB-CONTRACTORS
to the ELECTRONIC INDUSTRY**

3c Barley Market Street
Tavistock
Devon, England PL19 0JF
Tel. Tavistock (0822) 5439/5548
Telex: 45263

TRANSCENDENT 2000 SINGLE BOARD SYNTHESIZER

Designed by consultant Tim Orr (formerly synthesizer designer for EMS Ltd.) and featured as a construction article in ETI, this live performance synthesizer is a 3 octave instrument transposable 2 octaves up or down giving sweep control, a noise generator and an ADSR envelope shaper. There is also a slow oscillator, a new pitch detector, ADSR repeat, sample and hold, and special circuitry with precision components to ensure tuning stability amongst its many features.

The kit includes fully finished metalwork, fully assembled solid team cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or 1/2% metal film), and it really is complete — right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit — you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibreglass PCB printed with component locations. All the controls mount directly on the main board, all connections to the board are made with connector plugs and construction is so simple it can be built in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesizer comparable in performance and quality with ready-built units selling for many times the price. Comprehensive handbook supplied with all complete kits! This fully describes construction and tells you how to set up your synthesizer with nothing more elaborate than a multi-meter and a pair of ears!



Cabinet size 24.6" x 15.7" x 4.8" (rear) 3.4" (front)

**COMPLETE KIT ONLY
£168.50 + VAT!**

NEW! TRANSCENDENT POLYSYNTH



Cabinet size 31.1" x 19.6" x 7.6" (rear) 3.4" (front)

**EXPANDABLE POLYPHONIC SYNTHESIZER
AS FEATURED IN
Electronics Today International
COMPLETE KIT from £320 + VAT**

By brilliant design work and the use of high technology components the Polysynth brings to the reach of the home constructor a machine whose versatility and range of sounds is matched only by ready-built equipment costing thousands of pounds. This latest addition to the famous Transcendent family is a 4 octave (transposable over 7 octaves) polyphonic synthesizer with internally up to 4 voices making it possible to play simultaneously up to 4 notes. An add-on unit permits expansion up to 8 voices. Each voice is a complete synthesizer in itself with 2 VCOs, 2 ADSRs, 1VCA and 1 VCF. Being voltage controlled all voices can be adjusted simultaneously by master controls yet their own pitch and gate signals mean each voice can be operated independently from the keyboard. Although using very advanced electronics the kit is mechanically very simple with minimal wiring, most of which is with ribbon cable connectors. All controls are PCB mounted and the voice boards plug into PCB mounted sockets. The kit includes fully finished metalwork, solid teak cabinet, professional quality components (resistors 2% metal oxide or 0.5% and 0.1% metal film), nuts, bolts, etc. Complete kit with 1 voice £320, 2 voices £368, 4 voices £464; expansion unit to extend to 8 voices £275 (all prices subject to V.A.T.). A mere fraction of what you would have to pay for a ready-built comparable instrument!

TRANSCENDENT DPX

MULTI-VOICE SYNTHESIZER

Another superb design by
synthesizer expert Tim Orr
published in
Electronics Today International

**COMPLETE KIT
ONLY
£299 + VAT!**



Cabinet size 36.3" x 15.0" x 5.0" (rear) 3.3" (front)

The Transcendent DPX is a really versatile 5 octave keyboard instrument. These are two audio outputs which can be used simultaneously. On the first there is a beautiful harpsichord or reed sound—fully polyphonic, i.e. you can play chords with as many notes as you like. On the second output there is a wide range of different voices, still fully polyphonic. It can be a straightforward piano or a honky tonk piano or even a mixture of the two! Alternatively you can play strings over the whole range of the keyboard or brass over the whole range of the keyboard or vice-versa or even a combination of strings and brass sounds simultaneously. And on all voices you can switch in circuitry to make the keyboard touch sensitive! The harder you press down a key the louder it sounds — just like an acoustic piano. The digitally controlled multiplexed system makes practical touch sensitivity with the complex dynamics law necessary for a high degree of realism. There is a master volume and tone control, a separate control for the brass sounds and also a vibrato circuit with variable depth control together with a variable delay control so that the vibrato comes in only after waiting a short time after the note is struck for even more realistic string sounds.

To add interest to the sounds and make them more natural there is a chorus/ensemble unit which is a complex phasing system using CCD (charge coupled device) analogue delay lines. The overall effect of this is similar to that of several acoustic instruments playing the same piece of music. The ensemble circuitry can be switched in with either strong or mild effects. As the system is based on digital circuitry digital data can be easily taken to and from a computer (for storing and playing back accompaniments with or without pitch or key change, computer composing, etc., etc.).

Although the DPX is an advanced design using a very large amount of circuitry, much of it very sophisticated, the kit is mechanically extremely simple with excellent access to all the circuit boards which interconnect with multiway connectors, just four of which are removed to separate the keyboard circuitry and the panel circuitry from the main circuitry in the cabinet. The kit includes fully finished metalwork, solid teak cabinet, professional quality components (all resistors 2% metal oxide), nuts, bolts, etc., even a 13A plug!

POWERTRAN

MANY MORE KITS ON PAGES 95 and 99. ORDERING INFORMATION ON PAGE 95

All projects on this page can be purchased as separate packs, e.g. PCBs, components sets, hardware sets, etc. See our free catalogue for full details and prices.

A PROGRAMMABLE THAT THINKS IT'S A COMPUTER

For the price of a good scientific

CASIO'S AMAZING NEW FX-3500P

Statistical regression and integrals. Non-volatile memories and stores.

38 functional (non-volatile) steps. 2 programme storage capability. Unconditional and conditional jumps. 7 (non-volatile) memories; one independent, 6 constant memories. 18 pairs of parentheses, nestable in 6 levels.

61 built-in functions, including: Integrals (Simpson's rule). Linear regression, logarithmic regression, exponential regression and power regression.

Hyperbolics, sexagesimal and co-ordinates conversions. 10 digit mantissa or 10+2 exponent. Two silver oxide batteries give approximately 1,000 hours continuous use with power-saving automatic cut-off, with data and memory protection.

Dims: 9/32 x 2 1/4 x 5 1/4 inches. Supplied with leatherette wallet.

ALL THIS FOR ONLY £22.95

CASIO FX-2700P

Similar to the FX-3500P but without regression analysis and integrals. Single program storage. 8 digit mantissa or 8 digit mantissa and 2 digit exponent. 50 built-in functions including cube root. RRP £22.95. **ONLY £19.95**



CASIO'S SUPERCALCS! FX-8100

Our best selling scientific

46 scientific functions, clock, calendar, alarm, countdown alarm, interval alarm timer, 1/100 second stopwatch with lap timing.

Clock. Hours, minutes, seconds, am/pm.

Calendar. Pre-programmed to 1999. Day, date, month and year.

Alarm. 24 hour alarm with hourly chimes.


Countdown alarm. Can be set up to 10 hours, or, interval alarm timer up to 10 hours, or,

Stopwatch. Measuring net, lap and first and second place times in units of 1/100 second to 10 hours.

Calculator. 8 digits or 8+2. 5 level parentheses, full access memory. Trigs, logs, hyperbolics, standard deviations, co-ordinates and sexagesimal conversions, fractions, %, cube roots, pi, sign change, register exchange, etc.

Two silver oxide batteries last approx. 1 year (continuous). Dims: 1 1/4 x 2 3/4 x 5 1/4 inches. Leatherette wallet.

ONLY £24.95. (RRP £22.95)

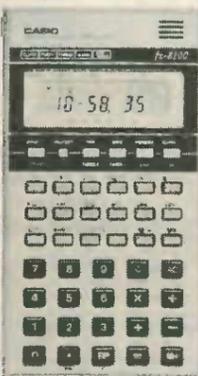

FX-6100.

Similar to the FX-8100 but without the calendar function, interval alarm timer, hyperbolics or fractions. 8 digit mantissa or 6+2 digit exponent. Powered by two AA size batteries. Dims: 1 1/4 x 3 1/2 inches. R.R.P. £22.95

£19.95

FX-7100.

Credit card version of FX-6100 with kiss-touch keys. Two silver oxide batteries give approx 1 year continuous use. 3/16 x 2 1/4 x 3 3/8 inches. Wallet. R.R.P. £27.95

£24.95

12 PRE-PROGRAMMED MELODIES


Clock, calendar, 11-note melody maker, calculator, square roots, %, Alarm 1; 7 tunes, one for each day. Alarm 2; a fixed tune.

Hourly chimes. Date memories; 4 anniversary tunes. **M-1200** (below) Desk or bedside. Built-in speaker. Volume control. Nightlight. Powered by three AA size batteries. 1 9/16 x 6 1/4 inches.

£19.95 (£22.95)

ML-90 (right) Kiss keys Stopwatch 7/32 x 2 1/2 x 4 1/2" (£22.95)

£19.95

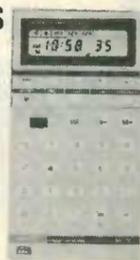

CASIOTONE KEYBOARDS NEW MODEL! CT-301

Provisional specifications: As CT201 below but with 14 instruments and 16 rhythm voices.

Provisional price; under £300

The revolutionary CT-201

A remarkable new concept in electronic keyboard instruments using a totally new technology to faithfully reproduce the pitch, timbre and harmonics of 29 instruments. A 4-sound memory function allows switching between any 4 pre-selected instruments. This polyphonic instrument can play full chords of up to 8 notes on its 29 white and 20 black keys spanning 4 octaves. Vibrato and tone switches. Foot volume and sustain pedal options. Echo jacks. 3x33 1/2 x 9 1/2 inches. Weight 15lb. Black or woodgrain finish. AC only.

M-10. Polyphonic playing of piano, organ, violin and flute. 19 white and 13 black keys span 2 1/2 octaves. 2x16 1/2 x 5 1/4 inches. Mains/battery. R.R.P. £79.

ONLY £69



Price includes VAT, P&P. Send your company order, cheque, P.O. or phone your ACCESS or BARCLAYCARD number to:

TEMPUS

Dept. WW, FREEPOST, 164-167 East Road, Cambridge CB1 1DB. Tel: 0223 312866

WW-077-FOR FURTHER DETAILS

Now Casio take a giant step forward in time with

THE ULTIMATE WATCHES

Send 12p for details of this amazing range of watches NOW!

Casio



AA81 Analogue Display



AA82 Digital Display

With around 40 functions LCD ANALOGUE/DIGITAL Alarm Chronograph with countdown

Analogue. Independent hours and minutes with synchronous digital seconds. Dual time ability. **Digital.** Hours, minutes, seconds, day and date. **Stopwatch.** 1/100 second to 12 hours. Net lap and 1st and 2nd place. Start/stop and 10 minute signals.

Alarm. For 30 seconds with carousel display. **Countdown Alarm.** Normal and net times to 1 hour with amazing "Star Burst" flashing display. **Time Signal.** Half-hourly and hourly chimes. Tone control. Lithium battery. Light. Water-resistant case. 8.65mm thick. Mineral glass.

AA81 Chrome plated £29.95

AA81G Gold plated £49.95

AA82 Stainless Steel £39.95

12 MELODY ALARM CHRONOGRAPHS Countdown alarm Date memories

Hours, minutes, seconds, am-pm, 12 or 24 hour. Day, date and month auto calendar.

Alarm. 7 melodies, one for each day of the week.

Hourly time signal. With "Big Ben" type tune.

Date memory. Select either "Wedding March" or "Trinkled" to be played.

Birthdays and Christmas Memory.

Countdown alarm. From 1 second to 1 hour. After zero count continues positively.

Stopwatch. 1/10 second to 1 hour. Net, lap, etc.

Picturesque moving display of notes played. Light. Lithium. Glass. Water-resistant cases.

M-12 resin, s/s trim. **M-1200** all s/s 9.0 mm thick.



£24.95



£29.95



£19.95



£32.50

For around 30 functions

100 METRE WATER RESISTANT

Alarm chronographs with countdown

Amazing 5-year lithium battery life. Hours, minutes, seconds, am/pm, day, date and month. 12 or 24 hour. Time is always visible regardless of display mode.

Stopwatch. 1/100 second to 1 hour. Net, lap and 1st and 2nd. Start/stop signal. 10 minute signal.

Alarm. Sounds for 30 seconds.

Countdown Alarm. Normal and net times to 12 hours. Start/stop and 10 minute signals.

Time signal. Half-hourly and hourly chimes.

W-100. All resin. **W-150B** All s/s. **W-150C** (not illustrated) s/s case/resin strap. **£29.95**

SEIKO Alarm Chronos from £37.50

JET 010 Duo display (far right). Independent analogue time. Digital time. Calendar, alarm, hourly chimes. 1/100th second stopwatch. Stainless steel

DFT 048 Alarm chrono (right). Full time and calendar display. Alarm and hourly time signal. Countdown alarm timer. Backlight. Stainless steel. Water resistant.

Many other models including solar powered and 100m water resistant.

SEND 25p for our illustrated catalogue.



£37.50




£62.50

PRICES

Include VAT and post and packing. Remember, we will beat any lower advertised price by 5% providing the advertiser has stocks and we still make a small profit!

MPA 200 100 WATT (rms into 8Ω) MIXER/AMPLIFIER

Featured as a constructional article in ETI, the MPA 200 is an exceptionally low priced — but professionally finished — general purpose high power amplifier. It features an adaptable input mixer which accepts a wide range of sources such as a microphone, guitar, etc. There are wide range tone controls and a master volume control. Mechanically the MPA 200 is simplicity itself with minimal wiring needed making construction very straightforward. The kit includes fully finished metalwork, fibreglass PCBs, controls, wire, etc. — complete down to the last nut and bolt.

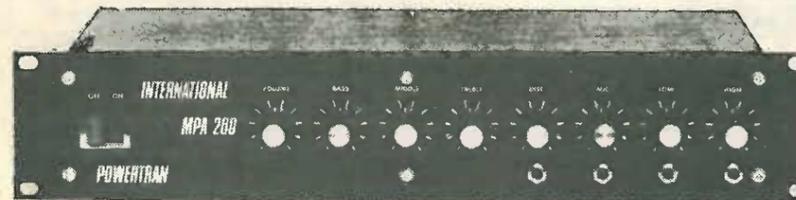

Panel size 19.0" x 3.5". Depth 7.3"

COMPLETE KIT ONLY **£49.90 + VAT!** MATCHES THE CHROMATHEQUE 5000 PERFECTLY!

CHROMATHEQUE 5000 5 CHANNEL LIGHTING EFFECTS SYSTEM

This versatile system featured as a constructional article in ELECTRONICS TODAY INTERNATIONAL has 5 frequency channels with individual level controls on each channel. Control of the lights is comprehensive to say the least. You can run the unit as a straightforward sound-to-light or have it strobe all the lights at a speed dependent upon music level or front panel control or use the internal digital circuitry which produces some superb random and sequencing effects. Each channel handles up to 500W and as the kit is a single board design wiring is minimal and construction very straightforward.

Kit includes fully finished metalwork, fibreglass PCB controls, wire, etc. — Complete right down to the last nut and bolt!




Panel size 19.0" x 3.5". Depth 7.3"

COMPLETE KIT ONLY **£49.50 + VAT!**

POWERTRAN

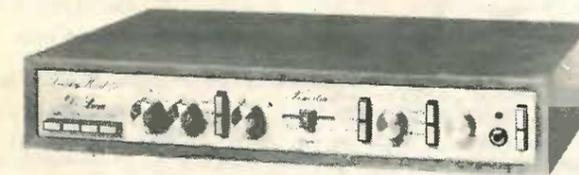SYNTHESIZER KITS ON PAGE 97; MORE KITS AND ORDERING INFORMATION ON PAGE 95



DE LUXE EASY TO BUILD LINSLEY HOOD 75W STEREO AMPLIFIER **£85.00 + VAT**

This easy to build version of our world-wide acclaimed 75W amplifier kit based upon circuit boards interconnected with gold plated contacts resulting in minimal wiring and construction delightfully straightforward. The design was published in Hi-Fi News and Record Review and features include rumble filter, variable scratch filter, versatile tone controls and tape monitoring while distortion is less than 0.01%.



T20+20 20W STEREO AMPLIFIER **£33.10 + VAT**

This kit, based upon a design published in Practical Wireless, uses a single printed circuit board and offers at very low cost, ease of construction and all the normal facilities found on quality amplifiers. A 30 watt version of this kit (T30+30) is also available for **£38.40 + VAT.** MATCHING TUNERS — See our FREE CATALOGUE!

Above 2 kits are supplied with fully finished metalwork, ready assembled high quality teak veneer cabinet, cable, nuts, bolts, etc. and full instructions — in fact everything!

BLACK HOLE


MUSIC EFFECTS DEVICE — AS FEATURED IN ELECTRONICS TODAY INTERNATIONAL!

The BLACK HOLE designed by Tim Orr, is a powerful new musical effects device for processing both natural and electronic instruments, offering genuine VIBRATO (pitch modulation) and a CHORUS mode which gives a "spacey" feel to the sound achieved by delaying the input signal and mixing it back with the original. Notches (HOLES), introduced in the frequency response, move up and down as the time delay is modulated by the chorus sweep generator. An optional double chorus mode, allows exciting antiphase effects to be added. The device is floor standing with foot switch controls, LED effect selection indicators, has variable sensitivity, has high signal/noise ratio obtained by an audio compander and is mains powered — no batteries to change! Like all our kits everything is provided including a highly superior, rugged steel, beautifully finished enclosure.

COMPLETE KIT ONLY **£49.80 + VAT** (single delay line system)

De Luxe version (dual delay line system) also available for **£59.80 + VAT**

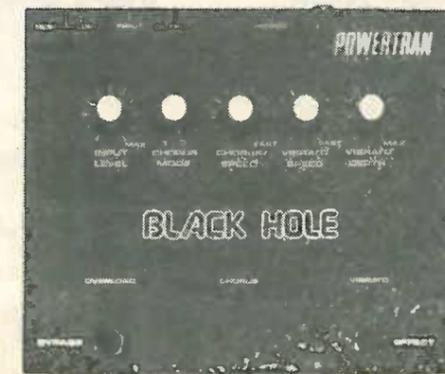Cabinet size 10.0" x 8.5" x 2.5" (rear) 1.8" (front)



SAFGAN presents **DT-400** series from **£159** + V.A.T.
HIGH-QUALITY DUAL TRACE OSCILLOSCOPES
A BRITISH PRODUCT EVERYONE CAN AFFORD

Model DT-410 DUAL TRACE 5mv/div 10MHz @ **£159** + VAT
 Model DT-412 DUAL TRACE 5mv/div 12MHz @ **£172** + VAT
 Model DT-415 DUAL TRACE 5mv/div 15MHz @ **£185** + VAT

SPECIFICATION FOR ALL MODELS

- * CH1, CH2: 5mv/div — 20v/div in 12 col 1-2-5-steps. Input impedance 1MΩ + 22pF
- * BANDWIDTH: 10MHz (DT-410), 12MHz (DT-412) 15MHz (DT-415)
- * TIME BASE: 0.5μs/div — 200ms/div in 18 cal steps X5 Expansion to 100 ns/div X5 Multiplier to 15/div
- * XY FACILITY: Matched Inputs X = CH1, Y = CH2
- * TRIGGER: Level Control, ± Slope, Bright Line AUTO, NORMAL, TV Triggering CH1, CH2 0.5 div, EXT Trig 100mv
- * Z Modulation
- * Cal output/probe compensation.
- * Graticule blue ruled 8 × 10 div (6.4 × 8cm²)
- * SIZE: H215mm W165mm D280mm Weight 4.5 kg.
- * PROBE (X1-REF-X10) **£11.50** + V.A.T.

Orders to: **SAFGAN ELECTRONICS LTD.** (Goods + 15% + £3 p. & p.)
56 Bishop's Wood, St. John's, Woking, Surrey, GU21 3QB Tel: Woking 69560 or Woking 66836
 Official Government and Educational Orders accepted. Distributors required — please enquire

DT-400 Series

WW — 057 FOR FURTHER DETAILS

3½ DIGIT LCD MULTI-METER KITS

BUILD YOUR OWN PROFESSIONAL QUALITY DMM AS ALREADY USED BY HUNDREDS OF LABORATORIES, RESEARCH UNITS, UNIVERSITIES ETC. THE LASCAR RANGE OF MULTIMETERS IS NOW ALSO AVAILABLE IN KIT FORM, CONTAINING ALL PARTS NEEDED TO CONSTRUCT THESE SUPERBLY STYLED MULTIMETERS—EVEN BATTERIES AND TEST LEADS. BOTH TYPES FEATURE FIVE FUNCTIONS (AC AND DC VOLTS, AC AND DC CURRENT RESISTANCE) WITH ABILITY TO CHECK DIODES. 0.5" LCD DISPLAY WITH 'BATTERY LOW' WARNING, AUTO-POLARITY, AUTO-ZERO, FULL PROTECTION AGAINST OVERLOADS AND TRANSIENTS, CAN WITHSTAND MAINS ON ANY RANGE. RUGGED ABS CASES AND A COMPREHENSIVE 1-YEAR WARRANTY.

The LMM 200 has been featured as a project in the July 80 Practical Electronics. It is a compact handheld multimeter with a 0.5% basic accuracy and 15 different ranges. It measures AC/DC voltage from 0.1mV to 500V, AC/DC current from 0.1μA to 2 Amps and resistance from 0.1Ω to 20MΩ. 200 hours battery life.

The LMM 100 is suitable for field or bench use. It has a basic accuracy of 0.1% and 25 different ranges. It measures AC/DC voltage from 0.1mV to 1Kv, AC/DC current from 0.1μA to 2 Amps and resistance from 0.1Ω to 20MΩ. Battery life is over 2,000 hours. It also features a unique 'digital hold' facility and adjustable carrying handle.

We also offer a calibration service (£5.00 + VAT = £5.75) and a trouble-shooting and calibration service (£7.50 + VAT = £8.62).

| | £ | P & P | VAT | TOTAL |
|--------------------------------------|-------|-------|-------|-------|
| LMM 200 KIT (PE DMM) | 32.95 | 1.00 | 5.09 | 39.04 |
| LMM 100 KIT | 58.95 | 1.75 | 9.10 | 69.80 |
| LMM 200 FULLY ASSEMBLED (INC. LEADS) | 39.70 | 1.25 | 6.14 | 47.09 |
| LMM 100 FULLY ASSEMBLED (INC. LEADS) | 77.50 | 1.75 | 11.88 | 91.13 |

Lascar Electronics Ltd., Unit 1, Thomasin Road, Basildon, Essex. Telephone No: Basildon (0268) 727383.

To: Lascar Electronics, Unit 1, Thomasin Road, Basildon, Essex.

Please send me Data LMM 200 Kit £39.04 LMM 100 Kit £69.80 Assembled LMM 200 £47.09 Assembled LMM 100 £91.13

Name _____
 Address _____
 Tel. No. _____

I enclose cheque/P.O. value _____

Orders may be phoned quoting your Access or Barclaycard No. Official orders accepted.

WW—084 FOR FURTHER DETAILS

Memories 8085 Series

| | | | | | |
|---|-------|-------|---------|-------|-------|
| 2716 | 1.24 | 25.99 | 8085A | 1.24 | 25.99 |
| 2732 | 7.00 | 4.73 | 8085A-2 | 6.80 | 4.10 |
| 2114L-3* | 15.65 | 13.65 | 8155 | 8.50 | 6.50 |
| 4116-3* | 2.99 | 2.75 | 8155-2 | 9.45 | 8.96 |
| *200 ns | 2.62 | 2.50 | 8251A | 11.81 | 11.20 |
| | | | 8253-5 | 5.60 | 5.40 |
| All components guaranteed new full specification devices. | | | 8255A-5 | 5.99 | 5.60 |
| | | | 8257-5 | 4.99 | 4.80 |
| | | | 8279-5 | 10.40 | 9.99 |
| | | | | 8.30 | 7.50 |

Please add VAT, and on orders under £15. p&p 30p

BDS Microsystem Designs Ltd.
 28 Pinewood Close, St Albans, Herts AL4 0DS
 Telephone St Albans (0727) 31831

WW — 017 FOR FURTHER DETAILS

MAINS INTERCOM NEW IMPROVED

£37.99 + VAT £5.70 per pair

NO BATTERIES, NO WIRES. Made to high Safety and Telecommunications Standard. The modern way of instant 2-way communications. Just plug into power socket. Ready for use. Crystal clear communications from room to room. Range ¼ mile on same mains phase with call buzzer and light indicator. On-off switch. Volume control. Useful as inter-office intercom between office and warehouse. Also useful as burglar alarm. 6 months' service guarantee. P&P £1.85. Also F.M. 2-channel model £49.95 + VAT £7.50 + P&P £1.95 per pair.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER

ONLY £18.95 + VAT £2.85

New improved battery operated Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates on/off switch for immediate two-way conversation without holding the hand-set. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for conference calls, leaves the user's hands free to make notes, consult files. No "holding on", save money and long-distance calls. Volume control. Model with conversation recording facilities. Price £20.95 + VAT £3.15, post and packing for either model £1.25.

10 days' price refund guarantee. Barclaycard and Access welcome.

WEST LONDON DIRECT SUPPLIES (WW)
 169 KENSINGTON HIGH STREET, LONDON W8 6SN

Here



NOW

ELECTROVALUE CATALOGUE '81

as included FREE with December issue of PRACTICAL ELECTRONICS

It's work-bench size for keeping alongside your favourite journal for instant reference to stock and technical data.

NEW LARGE FORMAT

With more to choose from than ever - all the items you have learned to depend on being obtainable from Electrovalue PLUS MANY NEW ONES to bring Catalogue '81 bang up to date. The V.A.T. inclusive price list that goes with it will hold for at least 4 months before the next one is issued.

Yes - you will enjoy dealing with Electrovalue - prices are keen - service is tops.

FREE FOR THE ASKING

Write, phone or call if you haven't yet got Catalogue '81 — and you will receive yours by return. (We pay postage.)

AND YOU GET BONUS DISCOUNTS AND FREE U.K. POSTAGE TOO, WHEN YOU BUY FROM ELECTROVALUE.

ELECTROVALUE LTD. (Dept. WW) 28 St Jude's Rd, Englefield Green, Egham, Surrey TW20 0HB. Telephone: (STD 0784) (London 87) 33603 Telex: 264475

Please send me my FREE COPY OF ELECTROVALUE CATALOGUE '81.

Name _____


Address _____

EXTENSIVE RANGE OF NEW FLUKE DMM'S FROM ELECTRONIC BROKERS

IMMEDIATE DELIVERY



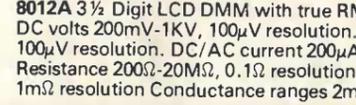8050A 4 ½ Digit LCD DMM with true RMS on AC volts and current DC volts 200mV-1KV, 10μV resolution AC volts. 200mV-750V, 10μV resolution. DC/AC current 200μA-2A, 0.01μA resolution resistance 200Ω-20MΩ, 0.01Ω resolution. Also reads dB direct referenced to 16 stored impedances. Conductance ranges 2mS and 200nS. **£199** mains model **£239** mains battery.



8012A 3 ½ Digit LCD DMM with true RMS on AC volts and current. DC volts 200mV-1KV, 100μV resolution. AC volts 200 mV-750V, 100μV resolution. DC/AC current 200μA-2A, 0.1μA resolution. Resistance 200Ω-20MΩ, 0.1Ω resolution Low resistance 2Ω and 20Ω, 1mΩ resolution Conductance ranges 2mS-20μS-200nS



£199.00 mains model **£219.00** mains battery.

8010A 3 ½ Digit LCD DMM Same spec as 8012A plus a 10Amp AC/DC current range, but no low resistance range. **£159.00** mains model **£179.00** mains battery.



8024A 3 ½ Digit hand held LCD DMM with peak hold Level Detector and continuity tester. DC volts 200mV-1KV, 100μV resolution.

AC volts 200mV-750V, 100μV resolution. DC/AC current 2mA-2A; 1μA resolution. Resistance 200Ω-20MΩ, 0.1Ω resolution. Conductance 200nS. Peakhold of AC or DC volts and current. Level detector operates around +0.8V reference. Audio tone on level and continuity. **£135.00** carrying case **£7.00** extra.

8020A 3 ½ Digit hand held LCD DMM. spec as per 8024A with extra conductance range of 2mS but no peak hold, level or continuity ranges. Complete with carrying case. **£112.00**

8022A 3 ½ Digit hand held LCD DMM. Spec as per 8020A but no conductance ranges and slight reduction on accuracy. Was **£89.00** now reduced to **£75.00** carrying case **£7.00** extra.



Also available a range of accessories including current shunts, EHT probe, rf probe, Temperature probe and touch and hold probe. Full details on request. The warranty period on all items shown is 1 year other than the 8020A which is 2 years.

Electronic Brokers


61-65 King's Cross Road London, WC1X 9LN
Tel: 01-278 3461 - Telex 298694
 Prices do not include carriage or VAT.

WW — 062 FOR FURTHER DETAILS

CS1830 FROM TRIO

Since its introduction, the CS1830 has been our top seller, and no wonder, when you glance at the comprehensive specification and the extremely attractive price which includes two matching X1/X10 probes. Add to that the fact that we can normally supply from stock and you have a winner. Some of the details are listed here but if you need further information, just contact us and we'll be happy to assist.

- C.R.T.:**
120 x 96 mm rectangular PDA with internal graticule
- Y Bandwidth:**
DC - 30MHz
- Sensitivity:**
5mV/div (30MHz)
2mV/div (20MHz)
- Input RC:**
1M/23pF
- Risetime:** 11.7nS
- Beam Switch:**
Chop/alternate
- Modes:**
CH1, CH2, Dual, Add, Subtract
- Time Base:**
Triggered, auto, or single shot
- Sweep Time:**
0.5S/div-200nS/div (40nS using X5 mag) 20 ranges in 1-2-5 sequence
- Sweep Delay:**
100mS-1uS adjustable with trace bright up for delay location
- Z Modulation:**
TTL compatible 10K impedance 5MHz bandwidth
- Trace Rotation:**
Electrical
- And the Price?**
£455 + VAT (includes 2 probes)

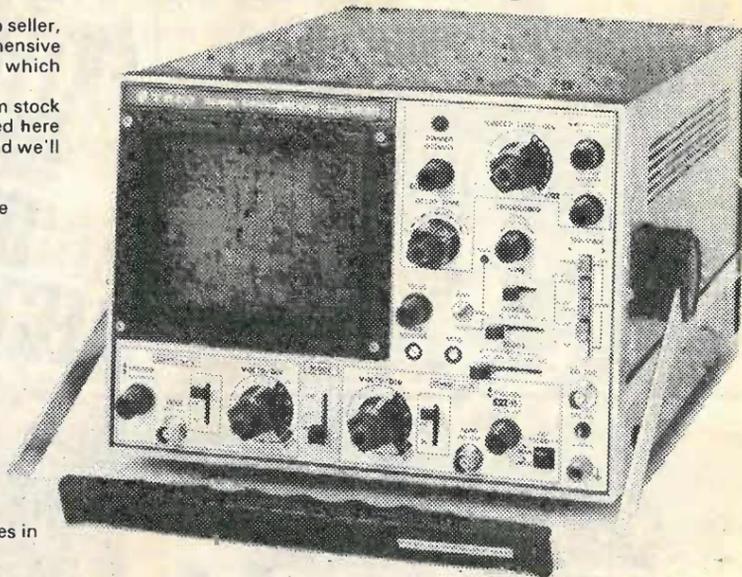

Also
CS1577A
Dual 30MHz/2mV Signal
Delay etc
£410 + VAT



NRD-515 receiving for the discerning few.



- NRD 515 SYNTHESISED HF MONITORING RECEIVER **£948.75 inc. VAT**
- NHD 515 MULTICHANNEL MEMORY UNIT **£161.00 inc. VAT**
- NVA 515 LOUDSPEAKER UNIT **£27.60 inc. VAT**
- CFL 260 600Hz CW FILTER **£34.50 inc. VAT**

The NRD 515 is a PLL-synthesised communications receiver of the highest class featuring advanced radio technology combined with the latest digital techniques. The new NRD 515 is full of performance advantages including general coverage, all modes of operation, PLL digital VFO for digital tuning, 24-channel frequency memory (option), direct mixing pass-band tuning, etc. JRC's 65 years of radio communications experience will give you "the world at your fingertips". The NRD 515 is but a single item from the JRC product range which extends all the way to full marine radio installations for supertankers.

LOWE ELECTRONICS Ltd.
CHESTERFIELD ROAD, MATLOCK, DERBYSHIRE DE4 5LE

TEL. 0629 2430/2817

WW - 079 FOR FURTHER DETAILS

OHIO SCIENTIFIC COMPUTERS. New series 2 Challenger C1P p.o.a. New Series 2 disc version Challenger C1PMF p.o.a. New Superboard 3 £199 + 15% VAT post free, with free power supply and modulator kit. Kits for use with old Superboard 2 (add 15% VAT).— Guard band kit £8. 4K extra ram £17.50. Display expansion kit approx 30 lines x 54 characters £20. Cass. Colour conversion board kit £45 or built £85. CEGMON improved monitor rom £29.50. Cassette recorder £18.

SINCLAIR PRODUCTS. SC110 10MHz Scope £145. PFM200 £81.95.

TV GAMES. AY-3-8600 + kit £12.95. Stunt cycle chip + kit £20.95.

IC AUDIO AMPS with pcb. JC12 6W £2.50. JC20 10W £3.54.

BATTERY ELIMINATORS. 3-way type 6/7 1/2/9v 300ma £3.50. 100ma radio types with press-studs 9v £4.77, 9 + 9v £5.99. Car converters 12v input, output 4 1/2/6/7 1/2/9v 800ma £3.04.

BATTERY ELIMINATOR KITS. 100ma radio types with press-studs 9v £1.54, 9 + 9v £2.30. Stabilized 8-way types 3/4 1/2/6/7 1/2/9/12/15/18v 100ma £3.12. 1 Amp £5.10. Stabilized power kits 2-18v 100ma £3.12. 1.30v 1A £3.30. 1.30v 2A £4.82. 12v car converter 6/7 1/2/9v 1A £1.82.

T-DEC AND CSC BREADBOARDS. S-dec £3.75, t-dec £4.59, exp-1 £2.84, exp-2 £2.84.

TRANSFORMERS. 6-0-6V 100ma 8p, 1 1/2 £3.32. 9-0-9V 75ma 8p, 1a £3.05, 2a £4.93. 12-0-12V 100ma £1.20, 1a £3.70.


SHARP COMPUTERS

Add 15% VAT to these prices. Sharp MZ80K Computer with Basic tape and a free tape of approx 50 programs.— 20K version £435, 48K version £485, MZ80 I/O £83. MZ80P3 £499. MZ80FD £772. PC1211 £83. CE121 £12.

PRINTERS. 800MST £359. Oki Microline 80 £349. Free interface and word processor for Superboard 2 included. Add 15% VAT.

SWANLEY ELECTRONICS
Dept. WW, 32 Colindale Road, Swanley, Kent
Telephone SWANLEY 64851. Please add 40p postage.
Prices include VAT unless stated. Lists 27p post free.
Overseas customers deduct 13%. Official credit orders welcome.

PEAK PROGRAMME METERS

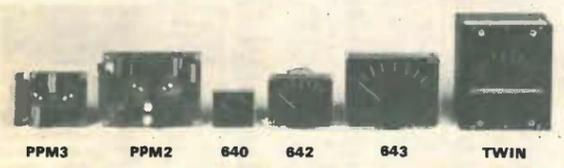

Manufactured under licence from the BBC the PPM2 drive circuit used with an Ernest Turner meter movement is the definitive Peak Programme Meter approved by broadcasting authorities in the U.K. and overseas for critical programming monitoring. Reviewed Studio Sound September 1976. PPM3 drive circuits have unbalanced inputs and may be used in equipment which will be required to pass IBA Code of Practice inspection. Drive circuits, meter movements, flush mounting adaptors and illumination kits from stock. Other level monitoring units are illuminated PPM Boxes, rack mounting Peak Deviation Meters and Programme and Deviation Chart Recorders for test purposes or making continuous record of levels in broadcasting.

Ring or write for full specification of these or Stereo Disc Amplifier 2 and 3 x 10 Outlet Distribution Amplifier * Stabilizer 4 * Frequency Shift Circuit Boards & Moving Coil Pre-amplifier.

SURREY ELECTRONICS, The Forge, Lucks Green, Cranleigh, Surrey GU6 7BG.
Tel. 04886 5997

Auto Transformers: Designed for USA equipment. Either open construction or cased with USA 3 pin sockets and cable input from 20VA to 6KVA. All continuous ratings.

| AUTO TRANSFORMERS | | | |
|-------------------|------|-------|------|
| Ref. | VA | £ | P&P |
| 113* | 15 | 2.73 | 0.81 |
| 64 | 80 | 4.41 | 1.10 |
| 4 | 150 | 5.89 | 1.31 |
| 53 | 350 | 10.08 | 1.31 |
| 67 | 500 | 12.09 | 1.91 |
| 84 | 1000 | 20.64 | 2.39 |
| 93 | 1500 | 25.81 | O.A. |
| 95 | 2000 | 38.31 | O.A. |
| 73 | 3000 | 65.13 | O.A. |
| 80S | 4000 | 84.55 | O.A. |
| 57S | 5000 | 98.45 | O.A. |

*0, 115, 220, 240 only.

| CASED AUTO TRANSFORMERS | | | |
|-------------------------|-------|------|------|
| VA | Price | P&P | Ref. |
| 20 | 8.55 | 1.03 | 56W |
| 75 | 8.50 | 1.31 | 64W |
| 150 | 11.00 | 1.31 | 4W |
| 250 | 13.39 | 1.67 | 69W |
| 500 | 20.13 | 1.89 | 67W |
| 1000 | 30.87 | 2.65 | 84W |
| 2000 | 54.97 | O.A. | 95W |

Transformer Winding Service. One-off prototype or batch production service available in addition to our standard range. Full specifications at keenest prices and quick deliveries. **Catalogue (send 20p stamps).**

NOW AVAILABLE
Radio Navigational Aids. Satellite Navigation Systems, eg Wherefinder II; 2900 series. Marine Receivers & Accessories. (Agents for P&O Radio Services.)

CONNECTORS
Thorn, Cannon, Plessey, Bendix, Greenper now available.

Soldering Iron — 25W to BS spec. **£1.75** + 30p P&P + VAT.

Solder Gun — 100W include bulb for spot-on vision and joints **£4.69** + P&P 70p + VAT.

De-solder Pumps. Spring loaded precision with quick action button release for one handed working. **Large £5.10.** P&P 35p + VAT. **Small £4.75** P&P 30p + VAT. Replacement tips... **Small 65p** + VAT. **Large 85p** + VAT.

Educational Meters. (Moving coil.) 0-10A, 0-15V, 0-30V. Free standing large scale easily read meters with top screw terminals for quick connections. Size 75x78 scale. **£4.50.** P&P 66p + VAT.

SPECIAL OFFER: Multimeter (20kΩ) with combined audio/i.f. test oscillator at 1kHz and 465kHz. AC/DC to 1000 volts. DC current to 500mA resistance to 1MΩ size 160x97x40mm **£8.50.** P&P £1 VAT 15%.

Barrie Electronics Ltd.
3 THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/7/8
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST

Other items available. Send 20p for Catalogue
Please add VAT after P&P

**Incredible Quality
Incredible Performance
Incredible Price!!!**



HM312 Dual Trace Oscilloscope.
DC-20MHz.
Sensitivity 5mV-20V/cm. Time base range 0.5uS-0.2S/cm with x5 horiz mag to 100nS/cm, with variable control uncalibrated to 40nS/cm. CRT screen 8 x 10cm. Full XY using ch1 as X input. Bandwidth 2.3MHz. TV trigger.

NOW BETTER VALUE THAN EVER AT

£220



HM512 Dual Trace Oscilloscope with delayed sweep.
DC-50MHz.
Sensitivity 5mV-20V/cm Time base range 0.1uS-2.0S/cm with x5 horiz mag to 20nS/cm. Delay ranges 7 decade steps 100ns-1S with fine control CRT screen 8 x 10cm. Full XY using ch 11 as x input, bandwidth 4 MHz. Z input. Delay line allows viewing of leading edge. Vertical overscan indicated by 2 LED's.

£580

World-beating Oscilloscope Offers
FROM
Electronic Brokers

61/65 Kings Cross Road,
London WC1X 9LN.
Tel: 01-278 3461. Telex 298694
Prices do not include carriage or VAT.

WW - 063 FOR FURTHER DETAILS

WW - 046 FOR FURTHER DETAILS

| | | | | | | | | | | | | | | | | | | | | | | | | |
|-------|------|---------|------|------|------|------|------|-------|------|--------|------|-------------|-------|----------|--------|----------|--------|----------|-------|---------|------|-----|------|------|
| 7400 | 11p | 74293 | 150p | 4020 | 100p | 9301 | 160p | 74500 | 60p | 745114 | 120p | TRANSISTORS | BFR40 | 25p | TIP30A | 48p | 2N3055 | 48p | 3N204 | 120p | 6A | 50V | 80p | |
| 7400 | 60p | 74298 | 200p | 4022 | 110p | 9302 | 175p | 74504 | 60p | 745124 | 300p | AC126 | 25p | BFR11 | 25p | TIP30C | 60p | 2N3442 | 140p | 40290 | 250p | 6A | 100V | 100p |
| 7401 | 12p | 74366 | 100p | 4023 | 27p | 9308 | 318p | 74505 | 75p | 745132 | 150p | AC176 | 25p | BFR80 | 25p | TIP31A | 62p | 2N3565 | 30p | 40361/2 | 75p | 10A | 400V | 200p |
| 7402 | 12p | 74368 | 100p | 4024 | 50p | 9310 | 275p | 74508 | 75p | 745133 | 75p | AC187/8 | 25p | BFR11 | 25p | TIP32A | 69p | 2N3584 | 250p | 40364 | 75p | 6A | 400V | 100p |
| 7403 | 14p | 74367 | 100p | 4025 | 20p | 9311 | 275p | 74510 | 60p | 745138 | 225p | BFX29 | 40p | BFR29 | 40p | TIP32C | 82p | 2N3637/4 | 48p | 40409/3 | 120p | 25A | 400V | 400p |
| 7404 | 14p | 74368 | 100p | 4026 | 130p | 9312 | 160p | 74520 | 60p | 745139 | 225p | AD149 | 40p | BFR30 | 34p | TIP33A | 90p | 2N3702/3 | 12p | 40409 | 100p | | | |
| 7405 | 18p | 74390 | 200p | 4027 | 50p | 9314 | 165p | 74530 | 60p | 745157 | 250p | AD161/2 | 45p | BFR34/5 | 40p | TIP33C | 114p | 2N3704/5 | 12p | 40410 | 100p | | | |
| 7406 | 36p | 74393 | 200p | 4028 | 84p | 9316 | 225p | 74532 | 90p | 745174 | 250p | AU107 | 200p | BFR37/8 | 30p | TIP34A | 115p | 2N3706/7 | 14p | 40411 | 300p | | | |
| 7407 | 36p | 74398 | 200p | 4029 | 100p | 9317 | 225p | 74537 | 90p | 745178 | 250p | BFR38 | 30p | BFR38 | 30p | TIP34B | 115p | 2N3708/9 | 12p | 40412 | 300p | | | |
| 7408 | 17p | 74451 | 150p | 4030 | 55p | 9322 | 150p | 74554 | 60p | 745194 | 350p | BF109 | 11p | BFR10 | 90p | TIP35C | 90p | 2N3773 | 300p | 40455 | 120p | | | |
| 7409 | 17p | 74450 | 14p | 4031 | 200p | 9334 | 360p | 74574 | 90p | 745241 | 450p | BF117 | 20p | BF105 | 30p | TIP36 | 290p | 2N3819 | 25p | 40673 | 75p | | | |
| 7410 | 15p | 74452 | 16p | 4034 | 200p | 9368 | 280p | 74585 | 300p | 745260 | 70p | BF117 | 20p | BF105 | 30p | TIP36A | 270p | 2N3820 | 50p | 40681 | 90p | | | |
| 7411 | 24p | 74453 | 18p | 4035 | 110p | 9370 | 300p | 74593 | 180p | 745373 | 500p | BF149 | 10p | BF105 | 30p | TIP36C | 340p | 2N3823 | 70p | 40681 | 90p | | | |
| 7412 | 24p | 74454 | 18p | 4036 | 110p | 9374 | 300p | 74512 | 120p | 745374 | 500p | BF159 | 11p | BF105 | 30p | TIP41 | 65p | 2N3866 | 90p | 40681 | 90p | | | |
| 7413 | 30p | 74455 | 25p | 4039 | 250p | | | | | | | BF169C | 12p | BSX19/20 | 20p | TIP42A | 70p | 2N3903/4 | 18p | 40681 | 90p | | | |
| 7414 | 40p | 74458 | 22p | 4040 | 100p | | | | | | | BF172 | 12p | BU104 | 225p | TIP42C | 82p | 2N3905/6 | 20p | 40681 | 90p | | | |
| 7414C | 90p | 74459 | 21p | 4041 | 80p | | | | | | | BF177 | 12p | BU105 | 190p | TIP54 | 180p | 2N4037 | 85p | 40681 | 90p | | | |
| 7416 | 17p | 744510 | 20p | 4043 | 90p | | | | | | | BF179 | 16p | BU108 | 250p | TIP120 | 120p | 2N4058/9 | 12p | 40681 | 90p | | | |
| 7417 | 27p | 744511 | 30p | 4044 | 90p | | | | | | | BF182/3 | 10p | BU109 | 225p | TIP122 | 130p | 2N4060 | 12p | 40681 | 90p | | | |
| 7420 | 17p | 744513 | 40p | 4044 | 90p | | | | | | | BF184 | 11p | BU126 | 180p | TIP142 | 130p | 2N4061/2 | 18p | 40681 | 90p | | | |
| 7421 | 40p | 744514 | 50p | 4046 | 110p | | | | | | | BF187 | 30p | BU180A | 120p | TIP147 | 130p | 2N4123/4 | 27p | 40681 | 90p | | | |
| 7422 | 22p | 744520 | 20p | 4047 | 100p | | | | | | | BF213 | 11p | BU205 | 200p | TIP255 | 75p | 2N4125/6 | 27p | 40681 | 90p | | | |
| 7423 | 36p | 744521 | 38p | 4049 | 45p | | | | | | | BF217 | 10p | BU208 | 70p | TIP440/1 | 72p | 2N4401/3 | 14p | 40681 | 90p | | | |
| 7425 | 36p | 744527 | 38p | 4049 | 45p | | | | | | | BF230 | 15p | BU406 | 145p | TIP543 | 45p | 2N4427 | 90p | 40681 | 90p | | | |
| 7426 | 40p | 744530 | 20p | 4050 | 45p | | | | | | | BF232 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7427 | 36p | 744532 | 27p | 4051 | 80p | | | | | | | BF237 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7428 | 36p | 744537 | 30p | 4052 | 80p | | | | | | | BF238 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7430 | 17p | 744538 | 30p | 4054 | 80p | | | | | | | BF238 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7432 | 30p | 744542 | 70p | 4054 | 150p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7433 | 40p | 744547 | 75p | 4055 | 125p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7437 | 35p | 744551 | 24p | 4056 | 135p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7438 | 35p | 744555 | 30p | 4059 | 60p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7440 | 17p | 744556 | 10p | 4062 | 115p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7441 | 70p | 744574 | 27p | 4063 | 120p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7442A | 60p | 744575 | 36p | 4066 | 50p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7443 | 112p | 744576 | 45p | 4067 | 45p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7444 | 112p | 744583 | 70p | 4068 | 27p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7445 | 100p | 744585 | 60p | 4069 | 25p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7446A | 93p | 744589 | 60p | 4070 | 30p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7447A | 75p | 744590 | 40p | 4071 | 25p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7448 | 80p | 744592 | 70p | 4072 | 25p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7449 | 17p | 744593 | 60p | 4075 | 25p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7451 | 17p | 744596 | 10p | 4078 | 25p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7453 | 17p | 7445107 | 45p | 4078 | 107p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7454 | 17p | 7445109 | 80p | 4081 | 27p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7460 | 17p | 7445112 | 40p | 4082 | 27p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7470 | 30p | 7445113 | 90p | 4083 | 150p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7472 | 30p | 7445121 | 90p | 4089 | 150p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7473 | 34p | 7445122 | 60p | 4093 | 70p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7474 | 30p | 7445123 | 60p | 4094 | 250p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7475 | 38p | 7445124 | 180p | 4095 | 95p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7476 | 32p | 7445125 | 50p | 4097 | 34p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7480 | 50p | 7445126 | 50p | 4097 | 34p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7481 | 100p | 7445132 | 60p | 4098 | 120p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7482 | 84p | 7445133 | 30p | 4099 | 200p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7483A | 90p | 7445136 | 55p | 4100 | 220p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7484 | 100p | 7445138 | 65p | 4102 | 180p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7485 | 110p | 7445139 | 65p | 4102 | 180p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7486 | 34p | 7445145 | 120p | 4103 | 180p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7489 | 210p | 7445147 | 220p | 4104 | 95p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7490A | 30p | 7445148 | 175p | 4105 | 120p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7491 | 80p | 7445150 | 100p | 4106 | 80p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7492A | 46p | 7445153 | 60p | 4107 | 60p | | | | | | | BF241 | 16p | E308 | 50p | TIP593 | 60p | 2N4871 | 60p | 40681 | 90p | | | |
| 7493A | 36p | 74 | | | | | | | | | | | | | | | | | | | | | | |



We use advanced winding technology to make our toroidal transformers. They have only half the weight and height of their laminated equivalents and are appreciably more efficient.

30VA 70mm dia. x 30mm Weight 0.45 Kg £4.71 (+£1.00 p.p. + 0.86 VAT)

Table with columns: TYPE, SECONDARY RMS VOLTS, SECONDARY RMS CURRENT. Lists transformer models like 1X010, 1X011, etc.

50VA 80mm dia. x 35mm Weight 0.9 Kg £5.19 (+£1.10 p.p. + 0.94 VAT)

Table with columns: TYPE, SECONDARY RMS VOLTS, SECONDARY RMS CURRENT. Lists transformer models like 2X010, 2X011, etc.

80VA 90mm dia. x 30mm Weight 1 Kg £5.76 (+£1.20 p.p. + £1.04 VAT)

Table with columns: TYPE, SECONDARY RMS VOLTS, SECONDARY RMS CURRENT. Lists transformer models like 3X010, 3X011, etc.

120VA 90mm dia. x 40mm Weight 1.2 Kg £6.72 (+£1.30 p.p. + £1.20 VAT)

Table with columns: TYPE, SECONDARY RMS VOLTS, SECONDARY RMS CURRENT. Lists transformer models like 4X011, 4X012, etc.

CHOICE OF 3 PRIMARY INPUTS

I.L.P. Toroidal Transformers are available in choice of 110V, 220V, 240V, coded as follows: (Secondaries can be connected in series or parallel)

For 110V Primary insert 0 in place of "X" in type number. For 220V Primary (Europe) insert 1 in place of "X" in type number. For 240V Primary (U.K.) insert 2 in place of "X" in type number.


Example - 120VA 240V 15 + 15V. 4A = 42013.

* CUSTOMER DESIGN ENQUIRIES INVITED. QUANTITY PRICE LIST AVAILABLE.

FREEPOST facility (U.K. only).

Simply address envelope to FREEPOST to address below. NO STAMP REQUIRED.

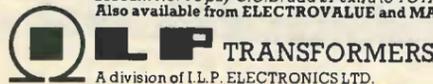TO ORDER Enclose cheque/Postal Order/Money Order payable to I.L.P. Electronics Ltd or quote your ACCESS or BARCLAYCARD account No. To pay C.O.D. add £1 extra to TOTAL value of order.



A division of I.L.P. ELECTRONICS LTD. FREEPOST T5 GRAHAM BELL HOUSE ROYER CLOSE CANTERBURY CT2 7EP

Phone (0227) 54778 Technical (0227) 64723 Telex 965 780

TELEVISION SOUND IS GOOD!

Yes it's true - but you'll need to listen through a Minim Television Sound Tuner to be convinced. Music, wildlife, even the news suddenly comes to life when you can hear all the detail that you expect from High Fidelity equipment.

Further information will only cost you 12p - stamp out poor television sound!

Name Address

Minim Audio Limited, Lent Rise Road, Burnham Slough SL1 7NY. Tel: Burnham 63724

MINIM AUDIO make a note of our name!

WW1

Get a great deal from Marshall's

The new Marshall's 80/81 catalogue is now available. A veritable treasure house of components, test gear, tools, etc.

Lots of old friends, but also many new products including Leader test gear, Crimson Hi Fi Modules, Rechargeable Ni Cad batteries and chargers (very competitive). More components including SN74ALS series, new tools etc.

We are franchised distributors for Arrow Hart switches; Mullard; National; Siemens; Sinclair (Thandor); Texas; Thomson; CSF etc.

Send for our latest catalogue. Free to industrial customers: 75p post paid to private individuals.

A. Marshall (London) Ltd., Kingsgate House, Kingsgate Place, London NW6. 4TA. Industrial Sales: 01-328 1009 Mail Order: 01-624 8582 24 hr service Retail branches: London: Glasgow: Bristol



NEW THE TUSCAN S100

A Z80 based S100 Computer System.



TUSCAN main board. The heart of the system with Z80, video, Ram, Rom, and I/O plus five S100 slots for expansion.

Available in Kit Form or Assembled. All components available separately.

Houses two 5 1/4" drives for a compact business system. Professional case will house the complete system. Two keyboard options. Hinged lid for easy access. Stylish finish ideal for office or home.

ex-stock

On Demonstration NOW

KITS from £235 + VAT Complete Business System 48K. Two 5 1/4" drives £1481.00

NASCOM PRODUCT LIST + VAT table listing various components like I/O board kit, UART + BAUD rate generator, etc.

nascom-2 MICRO-KIT COMPUTER WITH IMPROVED 16k B RAM Board



only £335 + VAT Full after sales service. Firmware & MOS ICs Software. Zeap Assembler (4, 1Kx8 EPROMS) £50. Nas Pen text editor (2, 1Kx8 EPROMS) £30. Expansion boards (in kit form) 48K RAM £210 16K RAM £140

EPROM CARD (NASCOM compatible) KIT. Suitable for 16 x 2708 or 16 x 2716 or mixed 1 x NASCOM 8k BASIC ROM £55.00. BASIC programmers aid. Self locating tape £14.95.

THE HENELEC DISK SYSTEM FOR NASCOM and any other Z80 8080 Microcomputer with an uncommitted P10

DISKS The Henelec controller card plugs direct into a Z80 P10 and controls up to 3 double-sided mini-floppy drives giving a maximum 480K system. General Purpose FDC control software for simple DOS or for CPM. Simple DOS software for NASCOM 1/2 under NAS-SYS. OR ROM CB10S for CPM on NASCOM 1/2 incorporating the major NAS-SYS features. Maximum 60K CPM system. New MD program supplied for N2/CPM TWO SYSTEMS. SIM-DOS "Floppy Tape Recorder" with 1 drive PSU firmware, etc. Double sided £380 plus VAT. CPM System with 1 drive, double sided PSU firmware, etc. £450 plus VAT. Additional Drives with PSU £205 plus VAT.

Professional ASCII Keyboards



The 'APPLE' Computer Keyboard. 52 key 7 bit ASCII coded. Positive strobe +5V -12V. Full ASCII characters. Parallel output with strobe. Power light on control. National mm 5740 chip. TTL output. Superbly made. Size 12x5.5x1.5ins. Black keys with white legends. Escape, shift, return and reset keys.

Complete with circuit and data. Ideal for use with Tangerine, Triton, Apple and most computers. Ex stock from HENRY'S. This is definitely the BEST BUY. Supplied Brand New in manufacturer's original jacking (anti-static). Just post remittance total £35.95 (incl. VAT and Post)

TANGERINE COMPUTER SYSTEMS

"MICRON" the latest line in superb products on demonstration from your London stockist. £395.00 inc. VAT BRITISH DESIGN

- 6502 based microcomputer. VDU alpha numeric display. Powerful monitor TANBUG. 8K RAM. 32 parallel I/O lines. 2 serial I/O lines. RS 232 C/20mA loop, with 16 programmable Baud rates. Four 16 Bit counter timers. CUTS cassette recorder interface. Data bus buffering. Memory mapping control. 71 Key ASCII Keyboard, including numeric keypad and with auto repeat. Including metal cabinets for both keyboard and modules. Including power supply. 10K Microsoft BASIC.

CENTRONICS QUICK PRINTER



List Price £459 incl. VAT. OUR PRICE plus VAT. EXCLUSIVE TO HENRY'S 50% OFF MAKER'S PRICE £195. Software selectable 20, 40 and 80 column using 120mm aluminium-ised paper. 1 roll supplied. 150 lines per minute. NASCOM Centronics parallel data interface for Nascom, Tandem, etc. 240 volt mains input. ASCII character set Paper feed, and on/off select switches. 'BELL' signal. Weight 10lbs. Size: 13" x 10 1/2" x 4 1/2".

MONITORS New and Reconditioned FROM £35

NASCOM-1 12" x 8" PCB carrying 5LSI MOS packages, 16 1K MOS memory packages and 33 TTL packages.

Nascom-1 Kit Price £125 Plus VAT + P&P £1.50

PLAIN PAPER £325 PRINTER

Fully built and housed in a stylish enclosure for just £325 plus VAT. INTERFACES WITH ALL MICRO COMPUTERS. The Nascom IMP (Impact Matrix Printer) features: 60 lines per minute. 80 characters per line. Bi-directional printing. 10 line print buffer. Automatic CR/LF. 96 character ASCII set (including upper/lower case, \$, £). Accepts 8 1/2" paper (pressure feed). Accepts 9 1/2" paper (tractor feed). Tractor/pressure feed. Baud rate from 110 to 9600. External signal for optional synchronisation of baud rate. IDEAL FOR WORD PROCESSING

Table listing Microtan 65 kit, Tanex assembled, Tanex lexpanded kit, Lower case option, Graphics option, 20 way keypad, Full ASCII keyboard, Tanex kit, Tanex assembled, Tanex lexpanded kit, Serial I/O option, Tanram kit, Tanram assembled, Tanram lexpanded kit.

SEND FOR COMPLETE COMPUTER BROCHURE

Table listing MEMORIES Discounts 10% for 4, 15% for 8, 20% for 16. ADD VAT. MK 3880 (NZ80), MK 3880-N4 (Z80A), MK 4116 16k x 1 dy RAM, MK 4027 4K x 1 dy RAM, 2102 1K x 1 static RAM, 4118 1K x 8 static RAM, Tanex assembled, Tanex lexpanded kit, Serial I/O option, Tanram kit, Tanram assembled, Tanram lexpanded kit.


TANGERINE LONDON STOCKISTS

Table listing MPS1 power supply, Mini Mother board, Mini Rack.

HENRY'S Official Export & Educational Orders Welcome

Computer Kit Division 404 Edgware Road, London, W2, England I.E.D. 01-402 6822

Quantum Electronics

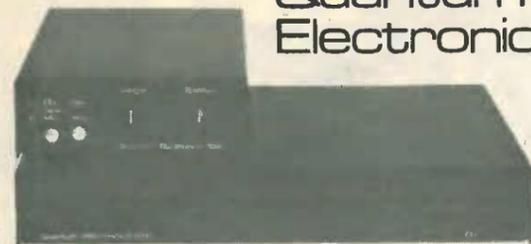

The 102, shown above, must be the most cost-effective pre-amp available, catering for auxiliary, 2 or 3 head tape and providing a perfect match for any cartridge, moving coil or magnetic, by using our unique low-cost matching card to define the sensitivity and cartridge loading. Prudent choice of components and elegant circuitry give outstanding objective and subjective performance (see Popular Hi-Fi August). The module used in the 102 is available separately, as are suitable mains supplies and moving coil head amp/modules. There are two matching stereo power amp kits which are supplied with built and tested circuit boards, requiring only straightforward assembly and point to point wiring. The new ready-built 'D' versions feature separate d.c. supplies for each channel and other refinements which elevate their performance into the super-fi class but which are not incorporated in the kits. Our power amp modules and supplies below enable an amp of high specification to be constructed.

*** COMING SOON: ACTIVE CROSSOVERS ***
102 pre-amp: module only £63.50; built £92

45W/channel: kit, P2, £100.50; built, 202D £151
110W/channel: kit, P4, £126; built, 204D £185

POWER AMP MODULES AND SUPPLIES

QE 1708, 1704, £31.96. QE 3003, £46.29*
QE 1004 (608) £20.69. QE 3008, £49.97*




M1504, 1508 £35.97. M3003 £50.28
M854 £26.00 M3008 £53.96
M4002, 5004 £82.60*

6 NEW MODULES ★ NOW UP TO 500W r.m.s.!

We offer a wide range of modules to suit virtually any application with an honest specification unbeatable at the price. They are available in both the popular medium duty 'L' bracket format for up to 300W r.m.s. (M3008, MS6, 8ohms) and also in high dissipation versions using various heatsink combinations. Correct choice of modules allows reliable continuous operation at up to 500W r.m.s. (M5004, MS6, 4ohms) without premature cut off or the need for external circuitry. Matching toroidal power supplies with single and double d.c. section are available. Exemplary specifications includes t.h.d. less than .01% at 1kHz; 30V/μs slew rate; noise below 110dB; integrally protected overload and high d.c. output offset: stable into any load.

★ EXCELLENT TRADE PRICES ★

NEW DELUXE SPEAKER KITS

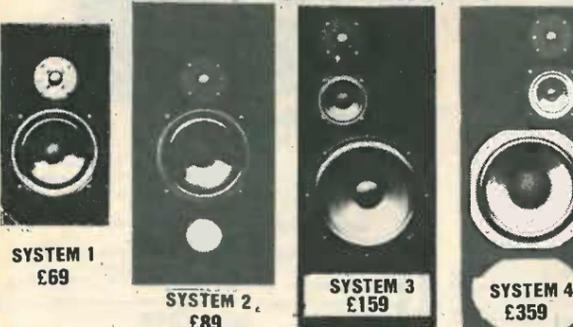

SYSTEM 1
£69

SYSTEM 2
£89

SYSTEM 3
£159


SYSTEM 4
£359

PRICES PER PAIR INC. BAFFLES

Have you wondered why the existing sources of speaker kits offer a bewildering choice of systems, particularly combinations of 200mm bass unit and tweeter? Don't they know which ones are best? If so, why bother with the rest! Well we have sorted out these super kits so you can order in confidence, knowing you get full endorsement of their performance and value. The kits incorporate professionally finished front baffles with the drive units already mounted so all the fiddly work is done for you. All that is left to do is to make a simple box. Crossover networks, foam and terminals are included. Systems 1 and 2 use a 200mm bass and 25mm dome tweeter from Son Audax. System 2 being a reflex design that we enthusiastically recommend. System 3 is a competitive 3-way I.B. using Seas bass and mid with a Son Audax tweeter, cleverly incorporating a stand at the bottom of the enclosure, as does System 4, undoubtedly the best kit on the market, using a Volt 250mm bass driver with a 250mm ABR on the rear baffle (also supplied), a modified Peerless mid and Son Audax tweeter. We will also be retailing selected drive units at competitive prices, e.g. Son Audax 200mm bass, 20B25J4 £13.50; 25mm tweeter, HD100D25, £9.
All our prices include V.A.T. and delivery. Export no problem — please send for a specific quote by return. All equipment can be wired for 110V mains. Please send a large S.A.E. or dollar bill for our full information and review reprints.

SWEDEN: BLN LUD HI-FI, SÖDRA KASERNGATAN 14 B, S291 33 KRISTIANSTAD
U.S.A.: DX DISCO, BOX 123, CLAYMONT, DELAWARE 19703
AUSTRALIA: COMPLETE AUDIO SYSTEMS PTY. LTD.
175 MCKEAN STREET, NORTH FITZROY, VICTORIA 3068
8 ALBION STREET, LEICESTER, TEL. 546198

Cut costs and speed trouble shooting

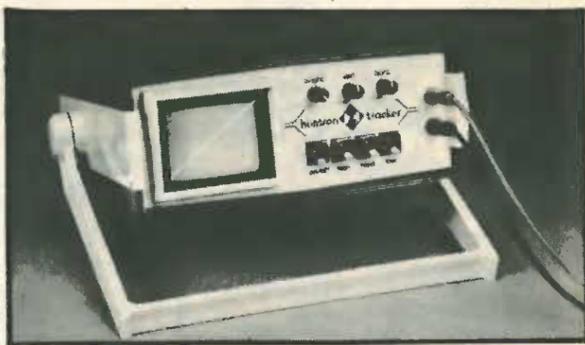

with the

Huntron Tracker

This easy to use test instrument displays shorts, opens, and leakage in solid state components. Check diodes, unijunctions, bipolars, Darlingtons, J-FET's, MOS FET's, LED's, electrolytics and IC's... IN CIRCUIT!
Test pure digital or analogue hybrid boards... WITHOUT CIRCUIT POWER!
Current limited to protect delicate devices in the MOS-CMOS family.
Save 20... 30... 40... even 50% of trouble shooting time and recover your investment fast! Exclusive 12 months warranty, available from—

MTL Microtesting Limited
1-15 Butts Road, Alton, Hampshire
Telephone: Alton (0420) 88022.



WW—072 FOR FURTHER DETAILS

FOTOLAK

POSITIVE LIGHT SENSITIVE AEROSOL LACQUER

Enables YOU to produce perfect printed circuits in minutes!
Method: Spray cleaned board with lacquer. When dry, place positive master of required circuit on now sensitized surface. Expose to daylight, develop and etch. Any number of exact copies can of course be made from one master. Widely used in industry for prototype work.

| | | |
|-----------------|-------|------------------------------------|
| FOTOLAK | £2.00 | Pre-coated 1/16" Fibre-glass board |
| Developer | 30p | 204mm x 114mm |
| Ferric Chloride | 50p | 204mm x 228mm |
| | | 408mm x 228mm |
| | | 467mm x 305mm |

| | | |
|--|--------------|--------------|
| Plain Copper-clad Fibre-glass. | Single-sided | Double-sided |
| Approx. 3.18mm thick sq. ft. | | £1.50 |
| Approx. 2.00mm thick sq. ft. | £2.00 | |
| Approx. 1.00mm thick sq. ft. | £1.50 | £1.75 |
| Clear Acetate Sheet for making master, 260mm x 260mm | | 12p |

Postage and packing 65p per order. VAT 15% on total
G. F. MILWARD ELECTRONIC COMPONENTS LIMITED
369 Alum Rock Road, Birmingham B8 3DR. Telephone: 021-327 2339

DO YOUR OWN ENGINE TUNING with the aid of our **AUTO ANALYZER** Test Meter. Sensitivity 2000G/V. D.C. Volts. 360 m/V. 3.2V. 8V. 18V. 32V. D.C. current 0.8A. 8A. 32A. 320A. Resistance Mid scale 200-2KΩ. Full scale 5000-50KΩ. Includes spark plug efficiency check. Capacitor efficiency check — Autodiodes Alternator check. Complete with full instructions. Test Leads & Heavy Duty plastic case. £22 + £1 p&p + VAT.

C.B. USERS. We have the perfect aerial for use on your vehicle, no holes to drill, it has a heavy duty magnetic base (fits kits anywhere on metal). Black matt & chrome finish, 5 metres of 500 cable terminating with a PL259 plug. Complete with loading coil & sprung antenna. £8.00 + £1 p&p + VAT.

BRAND NEW WASHING MACHINE WATER PUMPS. Suitable for most types of washing machines & dish washers. Manufactured by top Scandinavian Co. 220V 50Hz. 170 watt. Overall size: Length 180mm, width 95mm, height to top of pump outlet 120mm. Inlet & outlet bore 25mm. £15.00 + £1 p&p + VAT.

BRITISH MADE. "Versadrill" 1/4in. chuck 12V D.C. compact battery operated power tool. Powerful enough to perform all the tasks associated with a similar size 240V drill. Length 150mm x 50mm. Dia. £14.50 + £1 p&p + VAT.

PHILIPS 10 Button Universal Intercom Telephone. Attractive two tone grey and brown cradle type, complete with junction box. £7.50 + £1 p&p. Ideal for small offices.

PROTECT THAT EXPENSIVE EQUIPMENT with a resettable thermal overload cutout. Trip current 2.5A, 4A, 8A. Press to reset. £1.25 + VAT.

ELECTRONIC EQUIPMENT CO. LTD.
SPRINGFIELD HOUSE, TYSSEN STREET, LONDON E8 2ND
PHONE 01-249 5217
TELEX 895396 ECCO.G.

WE CANNOT ADVERTISE ALL WE SELL. For real bargains visit our warehouse and trade counter during the hours of 9 a.m. to 5 p.m. Monday to Friday. You will find us **BEHIND DALSTON LANE POLICE STATION.** All enquiries treated with prompt attention.

VALVES

Minimum Order £1.00

VALVES VAT IS INCLUDED

| | | | | | | | | | |
|----------|-------|-----------|-------|-----------|-------|--------|-------|--------|-------|
| A1065 | 1.40 | KT66 | 6.30 | X66 | 0.95 | 6H6 | 1.60 | 30PL14 | 2.45 |
| A2293 | 8.80 | KT88 | 13.80 | X61M | 1.70 | 6X4 | 1.35 | 35GT | 1.40 |
| A2900 | 12.80 | 9A2 | 9.20 | X61M | 1.70 | 6X4WA | 2.00 | 35W4 | 0.80 |
| ARR | 0.75 | MH4 | 2.50 | XR1-6400A | 82.90 | 6J5 | 2.30 | 35Z4GT | 0.80 |
| ARP3 | 0.70 | ML6 | 2.50 | | | 6J5GT | 0.90 | 40K6 | 3.15 |
| ATP4 | 0.80 | N78 | 9.90 | | | 6J6 | 0.65 | 50C5 | 1.15 |
| B12H | 3.80 | OA2 | 0.70 | Z800U | 3.45 | 6J6W | 0.90 | 50C66G | 1.35 |
| CV31 | 1.40 | OB2 | 0.60 | Z801U | 3.75 | 6J7 | 1.20 | 75B1 | 1.25 |
| DAF96 | 0.70 | PABCB0 | 0.80 | Z803U | 8.95 | 6J6EC | 2.95 | 75C1 | 1.70 |
| DET22 | 21.95 | PC85 | 0.75 | Z900T | 2.45 | 6S8C | 2.35 | 76 | 0.95 |
| DF96 | 0.70 | PC86 | 0.95 | 1A3 | 0.85 | 6K7 | 0.80 | 78 | 0.95 |
| DK96 | 1.20 | PC87 | 0.95 | 1A4 | 0.50 | 6L8M | 2.80 | 80 | 1.70 |
| DH16 | 0.75 | PC97 | 1.50 | 1R5 | 0.60 | 6L6G | 2.50 | 85A2 | 1.40 |
| DL92 | 0.80 | PC900 | 1.15 | 1S4 | 0.45 | 6L6GC | 2.10 | | 2.55* |
| DY86/87 | 0.85 | PCC84 | 0.50 | 1S5 | 0.45 | 6L6GT | 1.25 | 723A/B | 11.90 |
| DY802 | 0.70 | PCC89 | 0.85 | 1T4 | 1.50 | 6L7G | 0.65 | 805 | 20.70 |
| E55L | 14.90 | PC189 | 1.05 | 1U4 | 0.80 | 6L8 | 0.70 | 807 | 1.25 |
| E8RCC | 1.80 | PCF80 | 0.80 | 1X28 | 1.40 | 6L6 | 2.95 | 813 | 13.30 |
| E8RCC/01 | 3.10 | PCF82 | 0.70 | 2021 | 1.10 | 6L0D20 | 0.70 | 8298 | 14.00 |
| | | PCF84 | 0.75 | | 1.85 | 6K66A | 2.70 | 832A | 8.90 |
| E92CC | 1.20 | PCF86 | 1.50 | 2K25 | 1.15 | 607G | 1.30 | 886A | 3.80 |
| E180CC | 2.40 | PCF87 | 2.00 | 2X2 | 1.15 | 6S4T | 1.00 | 886E | 6.25 |
| E180F | 6.30 | PCF200 | 1.60 | 3A4 | 0.70 | 6S7 | 1.15 | 931A | 13.80 |
| E182CC | 4.95 | PCF201 | 1.65 | 3AT2 | 2.40 | 6S7J | 1.05 | 954 | 0.80 |
| E47E | 2.25 | PCF800 | 0.50 | 30B | 0.65 | 6K7 | 0.95 | 955 | 0.70 |
| EABC80 | 0.80 | PCF81 | 1.75 | 3D22 | 23.00 | 6S7GT | 0.85 | 957 | 1.05 |
| EB91 | 0.80 | PCF82 | 0.85 | 3E29 | 19.00 | 6SN7GT | 0.60 | | |
| EB33 | 1.15 | PCF85 | 2.45 | 3S4 | 0.80 | 6SR7 | 1.10 | 1625 | 1.80 |
| EB30 | 0.90 | PCF806 | 1.20 | 4B32 | 18.25 | 6S07 | 0.95 | 1629 | 1.85 |
| EBF80 | 0.80 | PCF808 | 2.05 | 5B/254M | 14.00 | 6V6G | 1.50 | 2051 | 2.90 |
| EBF83 | 0.80 | PC1200 | 0.95 | 5B/255M | 14.00 | 6V6GT | 0.95 | 5763 | 4.20 |
| EBF89 | 0.80 | PCL81 | 0.75 | 5B/255M | 14.00 | 6X4 | 1.75 | 5842 | 7.50 |
| EC52 | 0.85 | PCL82 | 0.95 | | 11.50 | 6X4WA | 2.10 | 5881 | 3.40 |
| EC91 | 3.40 | PCL84 | 0.90 | 58/258M | 8.80 | 6X5G | 0.65 | 5933 | 6.90 |
| EC92 | 0.85 | PCL86 | 1.05 | 5C2 | 29.90 | 6Y6G | 0.90 | 6057 | 2.20 |
| EC81 | 0.85 | PCL805/85 | 1.25 | 5U4G | 0.75 | 6Z4 | 0.70 | 6060 | 1.95 |
| EC82 | 0.80 | PD500/510 | 4.30 | 5V4G | 0.75 | 7Y4 | 1.25 | 6085 | 3.20 |
| EC83 | 0.85 | PLL200 | 1.10 | 5Y3GT | 0.80 | 902 | 0.70 | 6087 | 2.30 |
| EC84 | 0.80 | PL36 | 1.25 | 5Z4G | 1.05 | 10C2 | 0.85 | 6080 | 5.30 |
| EC85 | 0.80 | PL81 | 0.85 | 6/30L2 | 0.90 | 10F18 | 0.70 | 6146B | 5.20 |
| EC86 | 1.70 | PL82 | 0.70 | 6A87 | 0.70 | 10P13 | 1.50 | 6360 | 2.85 |
| EC87 | 0.85 | PL83 | 0.60 | 6AG5 | 0.60 | 11E2 | 1.50 | 6550 | 6.60 |
| EC88 | 0.85 | PL84 | 0.95 | 6AG6 | 0.80 | 12A6 | 0.70 | 6870 | 14.00 |
| EC89 | 1.05 | PL504 | 1.45 | 6AH6 | 1.15 | 12AT6 | 0.70 | 6872 | 8.20 |
| EC93 | 2.25 | PL508 | 1.95 | 6AK5 | 0.65 | 12AT7 | 0.65 | 6973 | 3.30 |
| EC94 | 1.70 | PL509 | 2.90 | 6AK8 | 0.60 | 12AU7 | 0.60 | 7199 | 2.85 |
| EC95 | 1.70 | PL519 | 3.20 | 6AL5 | 0.50 | 12AV6 | 0.95 | CRT | 18.50 |
| EC96 | 0.80 | PM33 | 0.70 | 6AL6 | 0.85 | 12AX7 | 1.65 | 1CP | 11.00 |
| EC97 | 0.70 | PM33 | 0.70 | 6AL7 | 1.30 | 12BA6 | 0.90 | 38P1 | 11.00 |
| EC98 | 0.80 | PM33 | 0.70 | 6AM5 | 4.25 | 12BE6 | 1.25 | 5FP7 | 18.00 |
| EC99 | 0.70 | PM33 | 0.70 | 6AM6 | 1.50 | 12BH7 | 1.10 | 4EP1 | 32.00 |
| EC100 | 0.75 | PM33 | 0.70 | 6AN8A | 2.50 | 12C8 | 0.65 | 88J | 14.00 |
| EC101 | 1.40 | PM33 | 0.70 | 6AD4 | 3.40 | 12E1 | 18.95 | 88L | 14.00 |
| EC102 | 0.85 | PM33 | 0.70 | 6A05 | 1.00 | 12E2 | 18.95 | 88M | 14.00 |
| EC103 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E3 | 18.95 | 88N | 14.00 |
| EC104 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E4 | 18.95 | 88P | 14.00 |
| EC105 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E5 | 18.95 | 88Q | 14.00 |
| EC106 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E6 | 18.95 | 88R | 14.00 |
| EC107 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E7 | 18.95 | 88S | 14.00 |
| EC108 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E8 | 18.95 | 88T | 14.00 |
| EC109 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E9 | 18.95 | 88U | 14.00 |
| EC110 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E10 | 18.95 | 88V | 14.00 |
| EC111 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E11 | 18.95 | 88W | 14.00 |
| EC112 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E12 | 18.95 | 88X | 14.00 |
| EC113 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E13 | 18.95 | 88Y | 14.00 |
| EC114 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E14 | 18.95 | 88Z | 14.00 |
| EC115 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E15 | 18.95 | 88AA | 14.00 |
| EC116 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E16 | 18.95 | 88AB | 14.00 |
| EC117 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E17 | 18.95 | 88AC | 14.00 |
| EC118 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E18 | 18.95 | 88AD | 14.00 |
| EC119 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E19 | 18.95 | 88AE | 14.00 |
| EC120 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E20 | 18.95 | 88AF | 14.00 |
| EC121 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E21 | 18.95 | 88AG | 14.00 |
| EC122 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E22 | 18.95 | 88AH | 14.00 |
| EC123 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E23 | 18.95 | 88AI | 14.00 |
| EC124 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E24 | 18.95 | 88AJ | 14.00 |
| EC125 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E25 | 18.95 | 88AK | 14.00 |
| EC126 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E26 | 18.95 | 88AL | 14.00 |
| EC127 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E27 | 18.95 | 88AM | 14.00 |
| EC128 | 0.85 | PM33 | 0.70 | 6A05W | 1.80 | 12E28 | 18.95 | 88AN | |



Decade Resistance Box 8000

- 0.1% ACCURACY
- 1Ω TO 100MΩ
- COLOUR CODED DIGITS



Decade Capacitance Box 9000

- 1% ACCURACY
- 100 pF-10 μF
- COLOUR CODED DIGITS

A compact 5 decade capacitance box. Coloured digits give nF in white, pF in yellow and μF in red. All contacts are gold plated.



Low Ohm Resistance Box 1041

- 0.01Ω TO 1KΩ
- IN LINE READ-OUT
- 1 WATT POWER RATING

Decade Resistance Boxes Type 1061/1062

- STABLE—(METAL FILM RESISTORS)
- FULLY SCREENED
- 2 VERSIONS 1Ω to 1.2MΩ (1061)
- 10Ω to 12MΩ (1062)
- IN LINE READ-OUT
- MECHANICALLY AND ELECTRICALLY ROBUST
- PRECISE

The 1061/1062 Decade Resistance boxes are designed to meet the standard required in both educational and industrial applications. Metal film resistors, with the advantages of stability and low temperature coefficient, are used throughout. The case provides complete electrostatic screening.

TIME ELECTRONICS LTD, Botany Industrial Est., Tonbridge, Kent, England TN9 1RS. Tel: (0732) 355993. Telex: 95481

WW — 081 FOR FURTHER DETAILS

FREQUENCY COUNTERS—OFF/AIR RECEIVERS

250MHz
801 B
£250
Crystal oven
3 parts 10"



OFF/AIR
RECEIVER
TYPE 103
PRICE £135

| | | |
|--------|----------------|------|
| 401A | 50MHz 6 Digit | £130 |
| 801B/M | 250MHz 8 Digit | £250 |
| 901M | 520MHz 8 Digit | £325 |
| 1001M | 1-2GHz 8 Digit | £550 |

20 models available including LED versions

RCS ELECTRONICS
WOLSEY ROAD
ASHFORD, MIDDX.
Phone 53661

WW—037 FOR FURTHER DETAILS



| | ADV 030 | ADV 025 |
|--|---|--|
| Model No. | ADV 030 | ADV 025 |
| Output Current | 5 Amp | 10 Amp |
| Output Voltage | 2.30 DC | 0.25 DC |
| Input Volts | 115-230-250 A/C | 115-230-250 A/C |
| Tolerated Mains Variation | 15% | 15% |
| Ripple On Load | 0.5% | 0.5% |
| Load Regulation | 0.5% | 0.5% |
| Better Than Protection | 0.5% | 0.5% |
| Both Models. Internal short circuit Protected. | Both Models. Internal Fold Back. Overload. Thermal and short circuit Protected. | |
| Both Models. 2 years Guarantee | Both Models. 2 years Guarantee | |
| Dimensions | Height. 130 M/M mm Width. 250 M/M mm Depth. 170 M/M mm | 177 mm 335 mm including handles 294 mm |

SOUTHERN ELECTRONICS

6 WESTCLIFF ARCADE, RAMSGATE, KENT TEL. THANET (0843) 57888

WW — 087 FOR FURTHER DETAILS

A PROFESSIONAL TOOLCASE FOR UNDER £40

For the TV or Electronics Engineer.



- Features**
- Multi-Purpose Tool Pallet
 - Document Area
 - Deep Base and Lid
 - Aluminium Frames
 - Locking Stays
 - Twin Handles
 - Toggle Locks

Dimensions 17" x 12" x 6" split

Tools NOT included. British Made. Money back guarantee. Allow 7-21 days for delivery

Order Form
Telman Products Ltd
Ermine House, Post St, Godmanchester, Cambs. PE18 8BA (0480) 65534

Please send TL99 Professional Toolcases at £39.90 each. inc. VAT (P&P £2.00 extra)

Enclosed my cheque for £.....

Name
Company
Address

TEKTRONIX STORAGE OSCILLOSCOPE. Type 434, as 'new. 12 months' warranty £1,950.

TEKTRONIX OSCILLOSCOPE. Type 647, with 10A2 and 3B11. £500

TEKTRONIX STORAGE OSCILLOSCOPE. Type 564 with 3A6 and 3B4 £350.

TELEQUIPMENT STORAGE OSCILLOSCOPE. Type DM53A £285.

TELEQUIPMENT OSCILLOSCOPE. Type D32. Portable. mains/battery. £275.

HAMEG OSCILLOSCOPE. Type 512 DB, 50MHz. £350.

TELEQUIPMENT OSCILLOSCOPE. Type 55A 5B 10MHz. £190.

SE LABS OSCILLOSCOPE. Type SM11 1 DB 20MHz. £325.

ADVANCE OSCILLOSCOPE. Type OS1000 DB 15MHz. £250.

TEKTRONIX OSCILLOSCOPE 547 with 1A1 plug-in Dual TB. 50MHz. £375.

TEKTRONIX OSCILLOSCOPE. Type 561A with 3A1 and 2B87 10MHz. £300.

TEKTRONIX OSCILLOSCOPE. Type 533A with CA. DB 24MHz. £140.

HEWLETT PACKARD AC CONVERTOR. Type 3461A £120.

MARCONI FM SIG. GEN. Type TF1066B/6S. £285.

G. S. E. BRADLEY LTD. R.F. MILLIVOLTMETER. Type 112 £75

ADVANCE A.C. VOLTMETER. Type VM77E £80

MARCONI WAVE ANALYSER. TF2330. Good condition. £150

AVO R.F. SIG. GEN. Model HF135. £75

MARCONI WIDE RANGE R.C. OSCILLATOR. TF1370. £85.

MARCONI AM/FM SIG. GEN. Type TF1066/1. £225.

MARCONI BENEFIT VALVE VOLTMETER. TF2600. £50.

MARCONI SIG. GEN. MK2. TF955A/3/S (CT402) £275.

TEKTRONIX type 1L30 SPECTRUM ANALYSER PLUG-IN. (works, slight corrosion) £325

AIRMEC SIGNAL GENERATOR. Type 204 AM/FM 320MHz £150

WAYNE KERN UNIVERSAL BRIDGE. Type B221 £50

ADVANCE R.F. Signal Generator E2 100KHz-100MHz £40

ADVANCE VHF MILLIVOLTMETER VM78 (No probe) £50

ADVANCE SIGNAL GENERATOR type B487 30KHz-30MHz £25

COBSON NOISE LEVEL METER CT484 (Ex-Military) £18

S.T.C. ATTENUATOR 0-1000B 500ohm £5

S.T.C. ATTENUATOR 0-1000B 75 ohm £5

AVO VALVE CHARACTERISTIC METER E20

E.H.T. UNIT 230V 50c 25VA 7.5V £22.50

BRANDENBURG HIGH VOLTAGE GENERATORS 10KV £60

BRANDENBURG HIGH VOLTAGE GENERATORS 30KV £80

VARIACS Ex-equipment. Good condition 8 amp £25

VARIACS Ex-equipment. Good condition 20 amp £35

CRC GENERATOR TBF6860. Sine/Square/Triangle. Very good £80

B&K AUTOMATIC VIBRATION EXCITER CONTROL. Type 1018 £50

B&K AUTOMATIC VIBRATION EXCITER CONTROL. Type 1019 £50

MARCONI UNIVERSAL BRIDGE. Type TFB68B £50

SOLARTRON TRUE RMS VOLTMETER. Type VM1484 £75

TAYLOR VALVE TESTER. Type 45D £85

ADVANCE LF OSCILLATOR. Type H1E £45

ADVANCE SIGNAL GENERATOR. Type SB28 150KHz-220MHz £60

MARCONI UNIVERSAL BRIDGE. Type TFB68A £50

TAYLOR METER MODEL 12S. £15

R&S SELEKTOMAT USWB BN 15221/2 £100

B&K LEVEL RECORDER. Type 2304 £50

RACAL HF SELECTIVE ANALYSER. Type 9056 £375

SCHLUMBERGER AUTO COUNTER. Type FB2602. £150

MARCONI F.E.T. MULTIMETER. Type TF2650 (new) £95

LEVEL MULTIMETER. Type TM11 £50

ICE MULTIMETER SUPERTESTER 890R £18

MARCONI SIGNAL GENERATOR. Type TF8010/1/S. £195

MARCONI SIGNAL GENERATOR. Type TF8010/1/S. £195

MARCONI UNIVERSAL BRIDGE. Type TF1313. £250

RACAL SIGNAL GENERATOR. Type 365A. 1 to 320MHz AM/FM. £175

R&S Z-g DIAGRAM BN3682 300-2400MHz £85

R&S POLYBROOK 1810B BN 4242/2. £80

WYNE KERR COMPONENT BRIDGE. CT375 (B521) £75

R&S UNBALANCED STANDARD ATTENUATOR 500hm. BN18942/50 £45

STODDART AIRCRAFT Radio Interference and Field Intensity Meter. type NM-52A 375-1000MHz (2 pieces) £328

MARCONI SIGNAL GENERATOR. Type TF801B £85

R&S DIRECT CAPACITANCE METER E80

B&K METEORODYNE VOLTMETER (RECEIVER) Type 2005 £250

MARCONI VARIABLE ATTENUATOR. TF1073A/2S £40

MARCONI DOUBLE PULSE GENERATOR. Type TF1400/S £50

RADIOMETER (RECEIVER) WAVE ANALYSER. Type FRA 2CT3A £50

SOLARTRON DIGITAL VOLTMETER. Type LM1867 £75

HEWLETT PACKARD DIGITAL RECORDER. Type 5050B £50

HATFIELD PHOPHOMETER. Type DRG 657167A £50

ADVANCE DUAL STABILISED D.C. SUPPLY PPS. 0-30V 1A £25

PICTURE MONITOR MODEL PM-52T (5in screen) As new £55

HEWLETT PACKARD POWER SUPPLY 6214A. 0-12V. 0-12A. new, boxed. £85.

H.P. DC POWER SUPPLY 62098. 0-320V. 0-0.1A. new boxed. £140

T.O.A. ELECTRONICS LTD Electronic Polystyrene EPR-21. Mains £120

THE JONES KING COMPANY FB-1100T FREQUENCY STANDARD £50

MARCONI CARRIER DEVIATION METER. Type TF891D £60

SOLARTRON PULSE GENERATOR. type G01101.2 £40

MI SANDERS LEVELLING AMPLIFIER. Type 6587 £175

SCOPE OSCILLOSCOPE. Type 4D10 DB 10MHz £170

ADVANCE OSCILLOSCOPE. Type T21 05240 DB 10MHz £75

COBSON OSCILLOSCOPE. Type CDU150 DB 35MHz £225

TELEQUIPMENT OSCILLOSCOPE. Type D61 DB 10MHz £185

HEWLETT PACKARD OSCILLOSCOPE. Type 1208 X-Y. From £55

FLUKE DIFFERENTIAL AC/DC VOLTMETER. Model 832A £60

ADVANCE AUDIO SIGNAL GENERATOR. Type H1. Sine/Square £25

R & S TUNABLE INDICATING AMP. BN 12121/2 45-600MHz £100

MURHEAD WAVE ANALYSER. Type 3460B £75

HEWLETT PACKARD DIGITAL VOLTMETER. Type 3460B £75

WAYNE KERN VOLTMETER. Type L100 with probe. £50

HATFIELD RADIO FREQUENCY BRIDGE. Type LE300A/1. £50

SOLARTRON OSCILLOSCOPE. Type CD1400. DB 15MHz. From £75

HAMEG OSCILLOSCOPE. Type HM412. £250

KNIGHT RF SIG. GEN. KG686 with Sweep Marker Gen. KG687 The Pair £100.

H.P. MEMORY DISPLAY 5480B with 5486A Control TB and 5488A Y System. £275

H.P. MEMORY DISPLAY 5480A with 5486A Control TB and 5485A two channel input. £225.

R&S UHF TEST RECEIVER 0-9.2GHz. BN1524 £150

EDDYSTONE RECEIVER. Type 9905 250-850MHz. £450

R&S UHF TEST RECEIVER. BN1523 280-940 MHz. £120

KEITHLEY REGULATED HIGH VOLTAGE SUPPLY. Type 241 £250

HEWLETT PACKARD D.C. CURRENT SOURCE. Type 6181B £175

MARCONI XY MEMORY Type TK2124. £140

R&S UHF SIGNAL GENERATOR. BN41022 300-1000MHz. £80

GPO DATED TESTER NO. IC. 1100

LEVEL BROADBAND VOLTMETER. Type TM68 £40.

DAWE AF ANALYSER. Type 1461A. £30

R&S UHF VHF FREQUENCY METER. BN4422 30-3000MHz. £60

R&S UHF MILLIVOLTMETER. BN1091. £70

GERROLD SWEEP FREQUENCY GENERATOR. Model 602. £40

TELEONIC SWEEP GENERATOR. Type SD-3 450-900 MHz. £75.

H.P. VHF SIGNAL GENERATOR. Type 6080. Case damaged hence £50

MARCONI VALVE VOLTMETER. Type TF1300. £15

SOLARTRON DIGITAL VOLTMETER. Type LM1420.2. £30

VIDEO CIRCUITS LTD TUBE TESTER. Type V33. £30

LABGAEUR COLOURMATCH 625 PATTERN GENERATOR. Type CM6004-PC. £30

R & S GREAT FREQUENCY OSCILLATOR. Type 1014. £175

ADVANCE OSCILLOSCOPE. Type OS1000A. DB 20MHz. £300

HEWLETT PACKARD
MICROWAVE SWITCH type 33124A SPST
up to 12.4 GHz. Brand new.
£140 each. Reduction for quantity.

ATTENUATOR
Type 6493A. 3db up to 12.4 GHz
£25 each

EDDYSTONE
RECEIVERS
Model 730-500KHz to 30MHz
£65 each
Model 770R-AM/FM
£95 each
Some models slight imperfections.
Phone for Special Price

INFRA RED IMAGE
CONVERTER Type 9606
(CV 144)
1 3/4in diameter. Requires single low current
3KV to 6KV supply individually boxed. With
data.
£12.50 each
Infra Red Lamps also advertised

GARRARD DIRECT DRIVE
TURNTABLE MOTORS
Made in Japan. With internal electronic
speed control. 24 volt. Connections supplied.
£3.50 each. P&P £1.50

EX-MINISTRY SOLID
STATE
400 HZ INVERTOR
28 VDC input. 115V output. Size 7 x 2 1/2 x
1 1/2in approx. Connection details supplied.
£18 each. P&P £2

TRANSISTOR INVERTOR
115V AC 1.7 Amp Input. Switching is at
20KHz. Output windings from Pot Core. Can
be returned to suit own purpose or unit can
be broken for host of components. Circuits
supplied.
£1.25 each. P&P £2.

CONVERT THIS UNIT TO A
SUPER BATTERY CHARGER
Attractive green ministry quality case with removable
top and bottom plates — heavy duty power switches,
high powered resistors to control current, good quality
centre mounted amp meter, strip of wing nut terminals
on front panel which can be used for connecting leads.
All this for £3.50. P&P £2. Four units £12. Carriage £5.

STEPPING MOTORS
6/12 position with additional where the rotor is coils.
Device can be used as a tach. Diagram supplied. Will
actually work on 5 volts. 12/24 recommended
£1.50 each P&P 75p
or 5 for £5 P&P £1.50.

STEPPING MOTORS
200 Steps. 20 oz/in. torque. 12/24 volt input 4-wire
£12 each. P&P £1.50

KEYBOARD PAD
Size 3x2 1/2x2 1/2" high with 12 Alma Reed Switches. Blue
keys marked in green 0-9 and a star with one blank.
£4 each. P&P £1, or 5 for £15 P&P £2.

MINIATURE KEYBOARD
Push contacts, marked 0-9 and A-F and 3 optional
function keys. £1.75 each.

CRYSTALS
Flat metal case — 19.2KHz. 844.8KHz. B7G — 10MHz. 50p each.

LOUHAILERS. Transistorised hand-held. no leads. Standard
internal batteries supplied. Howl Switch. £20 ea. P&P £2

INFRA RED QUARTZ LAMPS. 230V 620 Watts. Size 1 3/4" x
1 1/2" dia. £1.50 ea. 230V 1650 Watts. Size 2 1/4" x 1 1/2" dia. £3
ea.

BRIDGE RECTIFIER. 2 Amp 50p ea.

PHOTOIODE DETECTOR 4" fly leads. 25p ea.

AMPHEROL. 17-way chassis mount edge connectors 0.1
spacing. 15p ea.

I.E.C. Standard MAINS LEAD. Moulded (3 vertical flat pins centre
offset) 50p ea.

FANS. 115V 13 Watts. Size 3 1/4 x 3 1/4 x 1 1/2" BRAND NEW.
£4.50 ea. Second hand £2.50 ea.

DELAY LINE. 50 nanosec. 3 connections — ground-in-out Size 2
x 7/16 x 5/16" New 25p ea.

MOTOR 12V DC with pulley and integral semiconductor. Speed
Control. New £1 ea.

LEDEX ROTARY SOLENOIDS. 115V DC. No switch assembly.
15p ea.

DIAMOND H CONTROLS ROTARY SWITCH. Single pole
10-way. Printed Circuit Mount. New 10p ea. 100 for £7.50

SOME TEKTRONIX 500
range oscilloscopes
with Single Trace Plug-ins Working.
From £100. Phone for details

PULSE TRANSFORMER. Sub min. Size 1/2 x 5/16 x 1/4".
Secondary centre tapped. New 20p ea.

REMID TV TYPE MULTIPLIER. Two high voltage outputs and
focus. £1 each.

DON'T TAKE CHANCES. Use the proper EHT Cable. 10p per
metre or £7.50 per 100 metre/drum. P&P £2

PHOTOGRAPHIC LAMPS. Pearl 230V 500 watt. Screw cap
75p ea. Box of 12 £5.50. P&P £1.50.

RAPID DISCHARGE capacitors 8mf 4kV £5 each. P&P £2.

MYSTERY IC PACK. Some 4 pin — good mixture — all new
devices. 25 ICs for £1. P&P 50p.

DECOUPLING CAPACITORS
0.05mf 10V. 0.01mf. 0.047mf 250V. 33K. 330pf. All values
100 for £1.50.

E.H.T. Capacitor 500pf 8KV 20p each.

10-way MULTI COLOUR RIBBON CABLE. New 40p per
metre. 10 metres for £3.

GEC UHF 4-button tuner £1.50 each.

CENTAUR 115V FANS 4 1/2 x 4 1/2 x 1 1/2". £4.50 ea.

EX-USED equipment. tested. 80p each.

CONTACTORS. Heavy Duty 24V OC 5 make £1 each.

GEC UHF/VHF 6-button tuner £2 each.

831A PHOTO MULTIPLIER £2 each. P&P £1

RANCO 250V 15A THERMOSTATS with Control knobs
calibrated 50-200 degree C £2.50 each.

SOLID STATE UHF TUNERS. 30 ac £1 each.

BRAND REX blue wire wraps. 30 metres for £1. P&P 25p.

SLIDER CONTROL. 800K Log. Single track. Complete with
knob. Length 3 1/2". 25p each.

TRANSFORMERS
AUTO 240V input 115 V. 1 Amp output £1.25 each. P&P £1.25.
240V input. Soc. 6V. 1.86A. Size 2 1/2 x 2 x 2". Good quality.
£1.50 ea. P&P £1

240V input Soc. 12V 0.92A. Size 2 1/2 x 2 x 2". Good quality.
£1.50 ea. p&P £1

240V input 12V 100MA. Size 60 x 40 x 42mm. 50p each.

240V input. Soc. 12-0-12V 50MA. Size 53 x 45 x 40mm. £1
ea.

115V input. Soc. 5V 250MA. Size 1 1/2 x 1 1/2 x 1 1/2". 2 for
50p.

115V input. Soc. 10-0-10V1A. Size 2 1/2 x 2 x 2". 2 for £1.50.

SEMICONDUCTOR.
1N4005 — 5p; 1N4002 — 3p.

At 5p each:
BC147. BC148B. BC157. BC158. BC237. BF197. OA90. OA81.
BA154. BA243.

At 25p each:
TIP31. TIP41A. 2N5696. AF139. 2TX341
BY127 10p. BF181 20p; BO239 48p; BO241 40p; MA343AT
48p; BO228 50p; BO233 & BO234 Comp Pair 25W — 80p per
pr. at 50p each.

REGULATOR T9A625 8to 20V in — 5V out 100MA TOS Con.
50p each BF256C 20p.

TV AMPLIFIER TBA 120 20p each.

| Integrated Circuits | 74H74 | 12p | 75325 | £1 |
|---------------------|-------|-----|---------|-----|
| | 74H51 | 7p | SN15862 | 4p |
| | 74S13 | 5p | MC4028 | 60p |
| | 7402 | 12p | 74502 | 12p |
| | 7416 | 20p | 74154 | 70p |
| | 7495 | 35p | 74C02 | 16p |
| | 74122 | 12p | 74C04 | 18p |
| | 74C00 | 17p | 74C74 | 18p |

MOTOROLA DUAL in Line 6 pin Opto Coupler 30p each. Gold
plate test version 80p each.

EPROMS 2708 £5.50 each.

SMITHS encapsulated transistorised AUDIOIBLE WARNING
DEVICES 4V-12V. Can be driven from TTL 85p each.

ELECTROSTATIC VOLTMETER. 7.5KV £5. ea. P&P £1.50.
Other ranges available — please enquire

TRIMMERS. Sub min. 0.25 to 1.25 pf. 1 to 4.5 pf. 7 to 45 pf. All
at 5p each.

MONEYWELL humidity controllers 80p each.

THYRISTOR TIMER. Solid State. 15 secs adjustable (reset) in
plastic relay case. Standard 7-pin base. Series delay 80p each.

MINIATURE PC MOUNT SLIDE SWITCH. Single pole 3-way
10p each.

4 DIGIT 7 SEGMENT per digit plus a figure one to the left plus a
centre minus sign to the left of the figure one with decimal places
between digits. Good brilliance at 1.5V. 15 connections £2.50
each. Some E.H.T. Transformers and Capacitors available. Please
enquire.

TELEPHONES 706 style black; grey or blue £5.50 ea. 746 style
black or grey £7.50. Older style black £2.50 each. Oiscoloured
grey 706 £5 ea P&P £1.50 per telephone.

DC SERVO MOTOR 110V 2.5Amp continuous. Double shaft.
Brand new. 4 wire. 4 brush £25 ea. Plus carriage.

PC Mount POT. Wire wound with knob 200 ohm & 10ohm. 10p
ea.

MIN. RELAY 24V. 2 pole c/o. Brand new. 75p each.

TIME DELAY RELAY 0.1 to 10 secs. 115V AC. OPOT. £5 each.
CAPACITORS at 5p each. 0.1uf 400V. Small ec. block PC
Mount German class. 3300pf. 220nF 250V. 0.01mf 160V

IBERTY can be used as Microphone/Earpiece (Like used as insert
in telephone but superior quality) Ex-Min. Brand new wrapped 75p
each. or 10 for £5.

TOROIDAL TRANSFORMERS. Input 0-120-240 Volts. Output
0-12V. 0-2V. 10VA per winding. Encapsulated — identical to R.S.
Components at 85p. OUR SPECIAL PRICE £5 ea. P&P £1.50

TANTALUM CAPACITORS. All at 10p each — 100 off £7.50.
22mf 6V. 39mf 10V. 22mf 35V. 1mf 35V.

MINIATURE SLIDE SWITCHES. Single pole 2 way 10p each.
10 off 80p

HEAVY DUTY RHEOSTAT. 7.5ohm 5.5Amp. Diameter 5".
Standard 1/4" shaft £2.50 each. P&P £1.50

LARGE EX-MINISTRY SPEAKERS. OUTSIDE 15 ohm or
500 ohm. Tested £25 each or 5 for £100.

MINIMUM ORDER £3 VALUE OF GOODS. MINIMUM P&P £1 — where P&P not stated please use own discretion — excess refunded.
ES CARRIAGE ON ALL UNITS. P&P OR CARRIAGE AND VAT AT 15% on total MUST BE ADDED TO ALL ORDERS.
CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5pm Monday to Saturday inc.
BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome.

CHILTMHEAD LTD
NORWOOD ROAD, READING
(2nd turning left past Reading Technical College in King's Road then first right — look on right for door with "Spoked Wheel")
TELEPHONE NO. READING 669656

ELECTRONIC GILT-EDGED USED

A.C. VOLTMETERS

- BOONTON**
True R.M.S. Voltmeter 93A £375
- FLUKE**
AC/DC differential Voltmeter 883AB £975
- HEWLETT PACKARD**
Log-Voltmeter/Amplifier 7563A £325
- MARCONI INSTRUMENTS**
A.C. Voltmeter 400EL £225
Valve Voltmeter TF 2600 £175
Valve Voltmeter TF 2604 £250
R.F. Millivoltmeter TF 2603 £525
- PHILIPS**
A.C. Millivoltmeter PM2454B £225

ANALYSERS

- BIOMATION**
Logic Analyser 1650D £3600
- GENERAL RADIO**
Vibration Analyser 1911A £1750
- HEWLETT PACKARD**
Network Analyser System 8407A+8412A
c/w 8600A+8601A Sweep Marker
Generator 100KHz-110MHz range. £3500
- TEKTRONIX**
1L5 Spectrum Analyser Plug In £850

BRIDGES

- AVO**
Electrolytic Capacitance Bridge CB154/4 £500
- BOONTON**
VHF 'Q' Meter. 280AP. (210-610 MHz) £650
Inductance Bridge 63H £2750
- GENERAL RADIO**
Immitance Bridge 1607A £750
- MARCONI INSTRUMENTS**
'Q' meter TF1245 c/w TF1246 and TF1247 £950

RHODE AND SCHWARZ


- Inductance Meter LRT £475
Capacitance Meter KRT £475
- WAYNE KERR**
A.C. Testmatic A60 £900
Universal Bridge B221 (0.1%) £225

D.V.M.s AND D.M.M.s

- DATRON**
5 1/2 digit D.V.M. 1051 £995
- FLUKE**
5 1/2 digit D.M.M. 8800A £495
5 1/2 digit D.M.M. 8800A-01 £575
- HEWLETT PACKARD**
5 1/2 digit D.M.M. 1µV resolution 3490A £515
- PHILIPS**
Autoranging D.M.M. PM 2514 £125
4 digit D.M.M. PM 2524 £225
Autoranging D.M.M. PM 2527 £400
- SCHLUMBERGER**
5 1/2 digit D.M.M. A243 £425
Microprocessor D.M.M. 7065 £950
As above with processor option £1250
Microprocessor D.M.M. 7055 £850
As above with processor option £1150

FREQUENCY COUNTERS

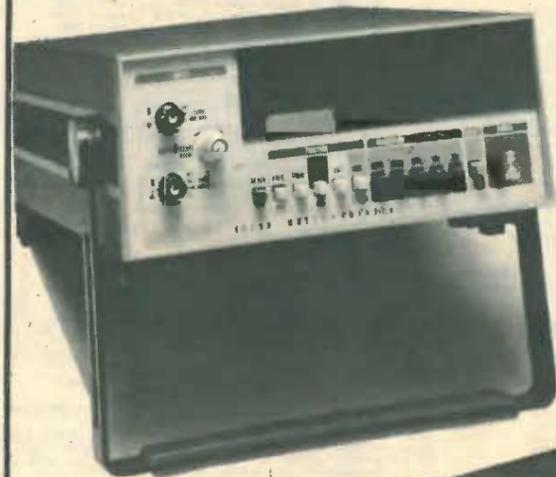- ADVANCE**
500MHz Counter TC 15 & TC 15 P1 £495
- FLUKE**
250MHz Multifunction Counter 1911A-01 £325
500MHz Multifunction Counter 1912A £395
125MHz Multifunction Counter 1925A £350
- PHILIPS**
520MHz Univ. Counter/Timer PM6614 £395
80MHz. Freq. Counter PM6664 £250



FLUKE

125MHz 9 Digit Frequency counter type 1925A EMI proof. 15mV Sensitivity to 100MHz. Variable trigger level


NEW PRICE £599
OUR PRICE £350



SOLARTRON

Microprocessor controlled 5 1/2 digit DMM type 7055 1µV resolution on AC and DC volts

NEW PRICE £1290
OUR PRICE £850

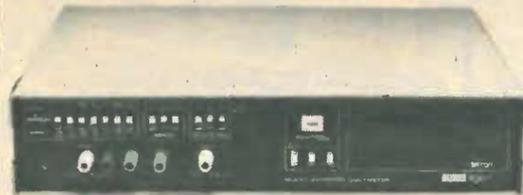

DATRON

True RMS 5 1/2 digit DMM. 0.1µV resolution on DC. AC measurement to above 100KHz. Auto ranging.

ONE ONLY £850



PHILIPS

Dual Trace Portable Oscilloscope PM3212 DC-25MHz. Signal delay. TV trigger

NEW PRICE £695
OUR PRICE £545

Electronic Brokers Ltd., 61-65 King's Cross Road, London WC1X 9LN. Tel: 01-278 3461. Telex: 298694

Unless otherwise stated all equipment offered in the Electronic Brokers advertisement is refurbished and in the case of Test Equipment also calibrated. Test equipment is guaranteed for 12 months; computer peripherals for 3 months.

BROKERS TEST EQUIPMENT

OSCILLOSCOPES

- COSSOR**
4100 75MHz Portable Dual Trace, Delayed Sweep. 30-day warranty Only £450
- HAMEG**
HM 312-7 DC — 10MHz Dual Trace (New) £200
- HEWLETT PACKARD**
75 MHz Dual Trace 1707A £600
High Sensitivity Single Trace 130C £250
1707B 75MHz Portable Dual Trace, Delayed sweep. 30-day warranty Only £650
- MARCONI INSTRUMENTS**
X-Y Display TF 2213/1 c/w Memory Unit TK 2214 £790
- PHILIPS**
25MHz Dual Trace PM 3212 £625
PM3260E 120MHz Dual Trace, Delayed Sweep 1 Only £975

S.E. LABS

- 6 Channel Monitor SM121 £395
- TEKTRONIX**
465 100MHz. Spec. similar to 465B but no alternate sweep. £1195
35MHz Dual Trace T932 £550
W. Diff. Plug In £295
1A6 Plug In £199

TELEQUIPMENT

- D75 50MHz Portable Dual Trace, Delayed Sweep £715
4 Trace Dual Beam Oscilloscope System D63 plus 2 V4 modules DC-15MHz. Supplied with Shackman Super 7 Camera £950.00
D67A Dual Trace 25MHz. Delayed Sweep £570.00

RECORDERS

- BRYANS SOUTHERN**
40000 12 channel UV Recorder plus 2 Off 40501 galvo amps. 6" chart width. Grid and timing lines. Superb condition £950
- PHILIPS**
Single Channel Recorder PM 8110 £195
- RACAL**
Store 4 FM Tape Recorder, 4 tracks DC-20KHz, 7 speeds. £1950
- S.E. LABS**
3006 12 channel UV Recorder. 6" chart width. Grid and timing lines £550
6012 50 channel UV Recorder 12" chart width. Servo paper drive up to 5 Mtr/Sec. Two event markers. Trace identification 1 Only £1100
- WATANABE**
6 Channel Chart Recorder MC 641 £2250
- YOKOGAWA**
Chart Recorder 3047 £450

SIGNAL SOURCES

- HEWLETT PACKARD**
H.F. Signal Generator 606B £1500
AM/FM Signal Generator 8640B (Opt. 002) 0.5-1024MHz £3650
Variable Phase, Sine and Signal Generator 203a £495
Oscillator 10Hz-10MHz 651B £415
V.H.F. Oscillator 3200B £400
U.H.F. Signal Generator 612A £850
V.H.F. Signal Generator 608F £450
Phase Lock Synchroniser 8709A £475
RF Sweeper/Marker Generator 8600A+8601A, 100KHz-110MHz. 5 marker frequencies. £1500
- KORTING**
TV Colour Pattern Generator 82515 £325.00

MARCONI INSTRUMENTS

- AM/FM Signal Generator TF 995B/2 (0.2 to 220MHz) £675
A.F. Oscillator TF 2100 £150
A.M. Signal Generator. TF801D/8S £550
L.F. Oscillator TF 2102/1M1 £195
U.H.F. Signal Generator TF1060/3 £650
Two Tone Source TF 2005R £295
H.F. Generator TF 144H/4 £750
TF2002B AM/FM Signal Generator. 10KHz-82MHz 1 Only £1200
- PHILIPS**
Function Generator PM 5108 £250
Function Generator PM 5127 £395
Function Generator PM 5167 £500
- RADIOME ER**
FM Stereo Generator SMG1c 100MHz carrier £445.00

TELONIC

- R.F. Sweeper 2003 c/w 3302, 3331, 3341, 3351, 3360, 3370 (1-300MHz) £1150

MISCELLANEOUS

- ADVANCE**
Constant Voltage Transformer CVN 1000A £65
Off Air Frequency Standard OFS 2B £95
- AVO**
Valve Tester VCM 163 £475
- BRADLEY**
AC Calibrator 125 B £475
DC Calibrator 126B £250
- BRUEL KJAER**
Sound Level meter 2203 & Microphone 4145 £395

FERROGRAPH

- Recorder Test Set +TS2 £345.00

FLUKE

- DC Differential Voltmeter 895A £950
332A DC Voltage Calibrator 0.003% Calibration Accuracy 0.1PPm resolution £1750
- GENERAL RADIO**
Sound Level Meter 1933 £1000
Cassette Recorder 1935
Recording Sound and Vibration Analyser 1911A £1250

HEWLETT PACKARD

- DC Microvolt-ammeter 425A £250
AC/DC Differential Voltmeter 741B £695
Vector Impedance Meter 4815A £1950
S Parameter Test Set. 8745A £2750
Insulation Resistance Meter 4329A £500
- MARCONI**
A.F. Power Meter TF 893A £185
Transmission Test SET TF 2332 £425
Transmission Test Set TF 2333 £600
P.C.M. Regenerator Test Set OA 2805A £2700
P.C.M. Multiplex Tester TF 2807A £1500
- RHODE AND SCHWARZ**
Stereocoder MSC £850
- S.E.I.**
Super 50 Selectest £77

SIEMENS

- Carrier-Freq. L.M.S. D2021/W2021/G2021 10KHz-25MHz £1700
Level Measuring System. D2074/W2074/G2006 £2600
Carrier Frequency Level Test Set W2007+D2007, 6KHz-18.6MHz. £175

TEKTRONIX

- Pulse Generator 2101 £420
TM515 Main Frame c/w FG504 0.001Hz-40MHz function generator. 2 Off PS503A Triple Power Supplies. £1250
TM515 Main Frame c/w SC502 15MHz Oscilloscope. FG503 1.0Hz-3MHz Function Generator. DM502 3 1/2 digit DMM. DC503 100MHz Counter £1495

WANDEL & GOLTERMAN

- Andimat (2MHz system) £9500
Pattern generator PFG-1 £995
Digital Error Detector PFM-1 £1495

WAVETEK

- Sweep Generator 135 £275
Programmable Phase Meter 755 £550

POWER SUPPLIES

- ADVANCE**
PMA47. 0-15V @ 3A (Presetable). £37
PMA 50. 0-15V @ 5A (Presetable). £45
MG 5-60 5V @ 60A (Switching). £160
MG 5-20 5V @ 20A (Switching). £120
MG 5-10 5V @ 10A (Switching). £95
MG24-12 24V @ 12A (Switching). £130

ONLY A SMALL SELECTION OF OUR VAST STOCKS ARE SHOWN HERE. IF THE EQUIPMENT YOU REQUIRE IS NOT LISTED, PLEASE PHONE OR CALL FOR FAST ATTENTION

12-MONTH WARRANTY

All Second User Test Equipment is fully guaranteed for 12 months unless otherwise stated.

Electronic Brokers Ltd., 61-65 King's Cross Road, London WC1X 9LN. Tel: 01-278 3461. Telex: 298694

Hours of Business: 9 a.m.-5 p.m., Mon.-Fri. Closed lunch 1-2 p.m. Add 15% VAT to ALP PRICES

A copy of our trading conditions is available on request. Carriage and Packing charge extra on all items unless otherwise stated.


ELECTRONIC USED

DEC EQUIPMENT



DEC MEMORY — BARGAIN OFFER

- MM11DP 16KW core (ex DEC-maintained 11 34 systems) ONLY **£395.00**
- H775-CB Battery Back-up **£525.00**
- KA8E Positive I/O (8E) **£95.00**
- KD8E Databreak (8E) **£145.00**
- KL8JA Asynchronous I/O (BE) **£275.00**
- KL8E Asynchronous I/O (8E) **£250.00**
- KP8E Power Fail (8E) **£95.00**
- LALI-PD 180 cps matrix printer **£1250.00**
- M7850 Parity Controllers **£185.00**
- MF11L 8KW Core including 9-slot system unit **£975.00**
- MM11LP 8KW Parity Core **£750.00**
- MM11YP 32KW Core Memory **£1750.00**
- MSV11C 16KW MOS Memory (LS111) **£495.00**
- MS11JP 16KW MOS Memory **£895.00**
- PDP 11/03-SD Processor 3 1/2 in chassis. 32KB MOS. BRAND NEW **£1495.00**
- PDP11/34 Processor, 10 1/2 in chassis. 128KW MOS, DL11W, KY11B **£6500.00**
- PDP11/40 Processor with 32KW parity core, KT11D Memory Management, DL11 Interface 6ft cabinet **£3600.00**
- PR11 High speed reader & control **£925.00**
- REV11 Bootstrap (LS111) **£75.00**
- PDP8E Series modules — large stocks of option modules, add-on core, CPU boards etc. all at reduced prices.

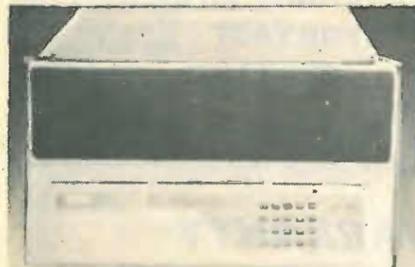

PDP11/04 PROCESSOR
10 1/2 in chassis. 16KW MOS DL11W. BRAND NEW **£4,500.00** (Can be enhanced to 28KW).

SCOOP BULK PURCHASE OF HAZELTINE VDUs

HAZELTINE H1000 VDU

12 x 80 Display Upper Case ASCII RS232 Interface Choice of Baud Rates
SUPER VALUE

£199
+ VAT
30-day warranty

HAZELTINE H2000 VDU


Superb spec including full XY Cursor Addressing and edit facility, 27 x 74 Display. Upper Case ASCII RS232 Interface Switch-Selectable Baud Rates

£299
+ VAT
90-day warranty

HAZELTINE MODULAR ONE VDU

Now with Upper/lower case, XY Cursor Addressing 24 x 80 line display. Upper/Lower Case ASCII. Detachable Keyboard. RS232 Interface. XY Cursor addressing.

£399
+ VAT
90-day warranty

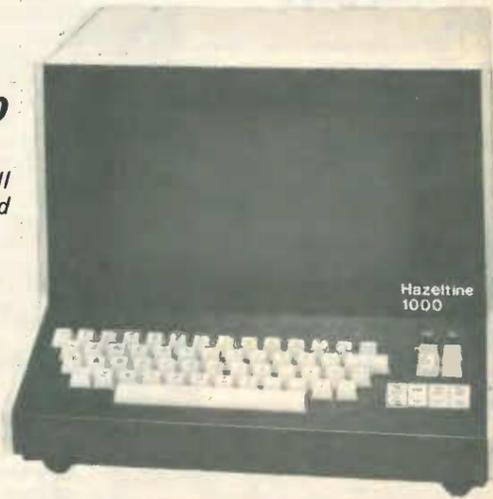

Electronic Brokers Ltd., 61-65 King's Cross Road, London WC1X 9LN. Tel.: 01-278 3461. Telex: 298694.

Unless otherwise stated all equipment offered in the Electronic Brokers advertisement is refurbished and in the case of Test Equipment also calibrated. Test equipment is guaranteed for 12 months; computer peripherals for 3 months.

BROKERS COMPUTER EQUIP

PRINTERS



CENTRONICS 101A

Heavy Duty Matrix Printer with 64 ASCII upper case character set. 165 cps operation. 132 print positions with adjustable tractor feed. 7 x 9 dot matrix, parallel input. Special Purchase enables us to offer the famous 101 series printer at **ONLY £495.00**

ASR 33 TELETYPE

Input/Output terminal incorporating paper tape punch and reader. 64 ASCII upper case character set. 110 baud operation, even parity keyboard choice of RS232 or 20mA interface. **NOW ONLY £595.00**. Options: ICL-type keyboard £50.00. 8th level marking £25.00. Remote reader control £50.00. Reader 'step' £20.00. Auto reader £25.00. Pedestal £30.00.

GE TERMINET 1200 RO Printer, 80 columns, tractor feed, upper/lower case, ASCII, 20mA Interface **£325.00**


HAZELTINE THERMAL PRINTER, 80 column 30 cps silent RO printer with parallel TTL input **£395.00**

TALLY 1602 MATRIX PRINTER, Parallel Input, Upper/lower case, Tractor feed, as new **£995.00**

TERMIPRINTER 7075 RO Impact Printer, Upper/lower case, pin-feed, RS232 **£275.00**

TEXAS 725 Portable Terminal with acoustic coupler **£625.00**

TEXAS 733 ASR Terminal **£1375.00**

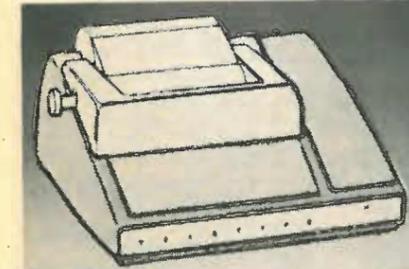

LOW COST PRINTER OFFER

Teletype 33 printer mechanism including case but no keyboard or electronics, 64 upper case ASCII 10 cps Pinfeed platen, ideal for the electronic hobbyist. **only £85.00**

MISCELLANEOUS

DIGITRONICS P135 paper tape punches. 35 cps. Solenoid device with 27VDC coil **£95.00**

NEW! NEW! NEW!
GP80 GRAPHICS PRINTER
80 column 30 cps matrix printer with full upper/lower case ASCII character set PLUS GRAPHICS FACILITY. Adjustable tractor feed. Standard Centronics parallel interface. **ONLY £249.00**
Optional interfaces also available for RS232, IEEE, Pet, Tandy and Apple.

NEW CATALOGUE OF COMPUTER EQUIPMENT JUST OUT—SEND FOR FREE COPY

HEWLETT PACKARD PROGRAMMABLE CALCULATOR MODEL 9830A



8K Memory. Extended I/O ROM. String Variables ROM 4. Peripheral interfaces (1 serial, 3 parallel). **PRICE £1995.00**

BALL MIRATEL TTL15

15in Diagonal green phosphor tube. Integral power supply. Requires separate horizontal and vertical video input. **BRAND NEW SURPLUS £75.00**




NEW ASCII KEYBOARDS — NEW LOW PRICES

KB 771 Superb 71-station ASCII Keyboard incorporating separate numeric/cursor control pad and installed in custom-built steel enclosure with textured blue enamel finish. Ideal for the VDU builder. Case dimensions 17 1/4" x 7 1/2" x 3 3/4". Total weight 4kg. **PRICE £85.00** (mail order total £101.20).



- KB756 56-station ASCII Keyboard mounted on P.C.B. **£39.50** £47.15
 - KB756MF As above, fitted with metal mounting frame for extra rigidity **£45.00** £53.48
 - KB710 10-key numeric pad, supplied with connecting cable **£8.00** £9.78
 - KB701 Plastic enclosure for KB756 or KB756MF **£12.50** £15.24
 - KB702 Steel enclosure for KB756 or KB756MF **£18.00** £23.00
 - KB2376 Spare ROM Encoder **£12.50** £15.24
 - KB15P Edge connector for KB756 or KB756MF **£3.25** £4.31
 - DC-512 DC converter to allow operation at 5V only (plugs in to P.C.B.) **£7.50** £9.20
 - DB25S Mating connector for KB771 **£4.25** £5.46
 - PERK 56-station ASCII Keyboard for PET complete with PET interface, built-in power supply and steel enclosure **£95.00** £112.70
- Discounts available for quantities

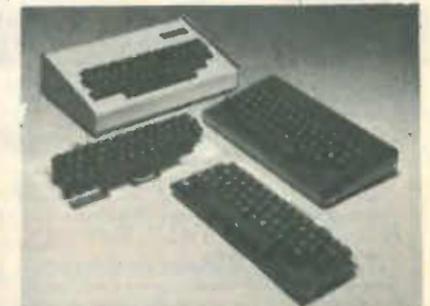

90-DAY WARRANTY
SECOND-USER PRINTERS AND TERMINALS ARE COVERED BY FULL 90-DAY PARTS AND LABOUR WARRANTY UNLESS OTHERWISE STATED.

All Prices subject to carriage and VAT

Electronic Brokers Ltd., 61-65 King's Cross Road, London WC1X 9LN. Tel.: 01-278 3461. Telex: 298694

Hours of Business: 9 a.m.-5 p.m., Mon.-Fri. Closed lunch 1-2 p.m. Add 15% VAT to ALL PRICES

A copy of our trading conditions is available on request. Carriage and Packing charge extra on all items unless otherwise stated.

WW — 059 FOR FURTHER DETAILS

ELECTRONIC TEST EQUIPMENT

DEC EQUIPMENT

DEC MEMORY OFFER

MM11DP 16KW
11 34 systems
H775-CB B
KA8E Pos
KD8E D
KL8J
KL8P
KL8R

NEW CATALOGUE OF COMPUTER EQUIPMENT JUST OUT—SEND FOR FREE COPY

ASCII KEYBOARDS—PRICES

71 station ASCII keyboard
rate numeric/cursor control
custom-built steel enclosure
metal finish. Ideal for the
home. 17 1/2" x 7 1/2" x
1 1/2". Price £85.00

RADIO/CB/TV TEST



CRT Testers · Pattern Generators · Signal Generators · Antenna Impedance Meters · RF Power Meters · C.B. Signal Generators · Stereo Signal Generators · Dip Meters · SWR/Wattmeters

LSG16 SIGNAL GENERATOR
A compact R.F. generator ideally suited to checking alignment of AM/FM and T.V. receivers.
*Frequency Range 100 kHz — 100 MHz
*Frequency Accuracy ± 1.5%
*Crystal Oscillator 1-15 MHz
*Modulation Internal 1kHz for A.M.
*Output Voltage 0.1Vrms or higher to 100 MHz

GENERAL TEST

Function Generators · Transistor Checkers · LCR Bridges · Power supplies · Millivoltmeters · Curve Tracers · Home Appliance Testers

LHM 80A H.V. METEDED PROBE

*Input Impedance 20KΩ per volt
*Range 40K Volts
*Accuracy ± 3% Full Scale

LDP 076 LOGIC PROBE

Fast servicing and analysis of digital circuits
*Input Impedance > 10MΩ
*Frequency Range DC to 50MHz
*Minimum Pulse Width 10nsec



AUDIO TEST

Audio Generators · Frequency Response Recorders
Audio Systems Analyzers · Wow & Flutter Meters
Speaker Analyzers · Audio Testers · Distortion Meters · Attenuators

LFR5600A FREQUENCY RESPONSE RECORDER

Designed to graphically record wow and flutter, drift, voltage, temperature and frequency response of Audio equipment.
*Frequency Range 20 Hz - 30 KHz
*Variable chart speed
*Voltage range 0.1V, 1V, 10V
*Sweep Oscillator *Pilot Signal *Cartridge pen
*Metered, Sweep frequency input/output voltage

£1395 plus VAT NEW



OSCILLOSCOPES

with more performance and reliability
models, single and dual trace, for bench or field use. All models offer comprehensive triggering controls, TTL compatible Z-AXIS modulation and convenient colour-keyed front panel layout. Probes are included with each model.



LB0508A OSCILLOSCOPE

With 20MHz bandwidth and 10 mV input sensitivity on a 5" screen this universal oscilloscope is suitable for a wide range of applications

- *5" Dual trace
- *DC-20 MHz bandwidth (vert amp)
- *10 mV Sensitivity
- *Sweep mode: chop - ALT, CH1, CH2, X-Y
- *Synchronisation: Auto, Norm, TV, Int., Ext., +, -
- *Timebase Sweep Speeds: 0.5 μs/cm - 200 ms/cm
- *X5 Magnification (max speed 100ns/cm)

| | | | | |
|----------|--------|-----------|--------------|--------------------|
| LBO 310A | 4 MHz | 20 mV | Single Trace | 3" |
| LBO 301 | 8 MHz | 10 mV | Single Trace | 3" |
| LBO 308S | 20 MHz | 2 mV | Dual Trace | 3.5" Mains/Battery |
| LBO 510A | 4 MHz | 20 mV | Single Trace | 5" |
| LBO 512A | 10 MHz | 10 mV | Single Trace | 5" |
| LBO 513 | 10 MHz | 5 mV/1 mV | Single Trace | 5" |
| LBO 514 | 10 MHz | 5 mV/1 mV | Dual Trace | 5" |
| LBO 552A | 10 MHz | 20 mV | Dual Trace | 5" Stereo Scope |
| LBO 506A | 15 MHz | 10 mV | Dual Trace | 5" |
| LBO 507A | 20 MHz | 10 mV | Single Trace | 5" |
| LBO 515B | 30 MHz | 5 mV | Dual Trace | 4.5" Sweep Delay |
| LBO 520A | 35 MHz | 5 mV | Dual Trace | 5.5" |
| LBO 517 | 50 MHz | 5 mV/1 mV | Quad Trace | 6" Sweep Delay |

For full technical details together with price list please contact:

LEADER

SINCLAIR ELECTRONICS LTD

London Road, St. Ives, Huntingdon, Cambs. PE17 4HJ.
Telephone: St. Ives (0480) 64646. Telex: 32250

Sinclair Electronics Ltd. reserve the right to alter prices and specifications on Leader equipment without prior notice.

SERVICE TRADING CO

FT3 NEON FLASH TUBE
High intensity multi turn high voltage, neon glow discharge flash tube. Design for ignition timing etc. £1.50. P&P 25p. (£2.01 inc. VAT) 3 for £3. P&P 50p (£4.03 inc. VAT & P).

WHY PAY MORE?
MULTI RANGE METERS Type MF15A. AC/DC volts 10, 50, 250, 500, 1000 Ma 0.5 0.10 0.100. Sensitivity 2000V 24 ranges dimensions 133x93x46mm. Price £7.00 plus 50p P&P (£8.63 inc. VAT & P).

VARIABLE VOLTAGE TRANSFORMERS
INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V

| | |
|--------------------------------|---------|
| 200W 1 amp inc. a.c. voltmeter | £14.50 |
| 0.5 KVA (2 1/2 amp MAX) | £16.00 |
| 1 KVA (5 amp MAX) | £24.00 |
| 2 KVA (10 amp MAX) | £39.00 |
| 3 KVA (15 amp MAX) | £47.00 |
| 5 KVA (25 amp MAX) | £76.00 |
| 10 KVA (50 amp MAX) | £168.00 |
| 17 KVA (75 amp MAX) | £260.00 |

All plus Carriage & VAT

SOLID STATE E.H.T. UNIT
Input 230V A.C. Fully isolated output. 10 mm spark. Approx. 15KV. Built-in 10 sec. Timer. Easily modified for 20 sec., 30 sec., to continuous operation. Designed for boiler ignition. Dozens of uses in the field of physics and electronics, e.g. supplying neon or argon tubes, etc. E.H.T. starter for lasers, xenons, C.S.I. lamps, Van de Graaff Generator, loss of vacuum detector, Ouidini coils, etc. etc.
Size: Lgth 155 mm. Wdth 85 mm. Ht 50 mm. Wt 530 gms. Price £5.00 + 85p p. & p. (Total incl. VAT £5.73) N.M.S.

230 VOLT AC FAN ASSEMBLY
Powerful continuously rated AC motor complete with 5 blade 6 1/2" or 4 blade 3" aluminium fan. New reduced price £3.50 P&P 65p (£4.77 inc. VAT & P.) N.M.S.

A.E.G. CONTACTOR
Type LS6/L11. Coil 240V 50Hz. Contacts - 3 make 600V 20 amp 1 break 600V 20 amp. Price £5.50 + 50p P&P (£6.90 inc. VAT & P.) N.M.S.

ARROW-HART MAINS CONTACTOR
Cat. No. 130A30
Coil 250V or 500V AC. Contacts, 3 make 50 amp up to 660V AC 20hp at 440V 3 phase 50Hz. Price £7.75 + P&P £1.00 (Total incl. VAT & P £10.06) N.M.S.

SMITH BLOWER
Type FFB.1706. Small quiet smooth running. 240V AC operation. Output aperture 45x40cm. Overall size 135x165mm. Flange mounting. Price: £4.25 P&P 75p. (£5.75 incl. VAT & P.) N.M.S. Other types available SAE for details

24V DC BLOWER UNIT
USA made 24V DC 0.8 amp blower to operate well on 12V 0.4 amp DC producing 30 cu ft min at normal air pressure. Maximum housing dia 110mm, depth inc motor 75mm, nozzle length 19mm, dia 22mm. Ideal for cooling mobile equipment, car, caravan, etc. £4.50 P&P 75p (£6.04 inc. VAT & P.) N.M.S.

CENTRIFUGAL BLOWER UNIT Airflow Development Ltd. powered by G.E.C. 230/250V. 2,850 rpm motor producing approx. 120 cfm. Aperture: 65x90mm. Overall size 222x225x195mm incl. starter capac. Price: £16.00 + P&P £2.00 (total inc. VAT £20.70). N.M.S.

MINIATURE UNISELECTOR
12V 11 way 4 bank (3 non-bridging, 1 homing) £3.50 P&P 35p (£4.43 inc. VAT & P)

MICRO SWITCHES ex. new equip.
Sub. Min. Honeywell Lever m/s type 3115M 906t, 10 for £3.50 post paid (£4.03 incl. VAT) These V3 types.

Barton Type (Pye) 10 for £3.00 (£3.45 incl. VAT)

Short Lever type 16amp. rating (Grouzet) £4.00 (£4.60 incl. VAT)

Roller Type (Bonnella) 10 for £3.50 (£4.03 incl. VAT) N.M.S.

HEAVY DUTY SOLENOID
Mfg by Magnetic Devices. 240V AC intermittent operation. approx. 20lb. pull at 1.25in Ex equip. Tested. Price £5.50 + 75p P&P (£7.19 inc. VAT & P) R&T

12V DC SOLENOID N.M.S.
12V DC heavy duty Solenoid 4 Kp pull. Easily removable from plate. Ali. chassis containing 4 x 24V DC Push Solenoids (1 1/2 lb approx). 5-fig. Counter. 6 min photo cells. Sub-min Microswitches etc. etc. Ex-equip London Transport Printer. Price: £9.00 + £1.00 p. & p. (total incl. VAT £11.50)

12V DC SOLENOID
Approx. 1lb pull. Price £1.40 + P&P 30p (£1.96 incl. VAT & P)

TYPE AG/TG
18-24V DC 70 ohm Coil Solenoid. Push or Pull Adjustable travel to 3/16in. Fitted with mounting brackets and spark suppressor. Size 100x65x25mm. Price 3 for £2.40 + 30p P&P (min 3 off) (£3.10 inc. VAT & P). Westool Series D6 Model A3. 24V D.C. Price £1.50 + 50p P&P (£2.30 incl. VAT). Westool Series D4 Model A 24V D.C. Price £1.00 + 30p P&P (£1.50 incl. VAT).

INSULATION TESTERS (NEW)
Test to I.E.E. spec. Rugged metal construction, suitable for bench or field work. constant speed clutch. Size L 8in, W 4in, H 6in, weight 6lb
500 VOLTS 500 megohms £49.00
Post 80p (£57.27 inc. VAT & P)
1000 VOLTS 1000 megohms £55.00
Post 80p (£64.17 inc. VAT & P). SAE for leaflet

YET ANOTHER OUTSTANDING OFFER
New 1MFD 600V Dubilier wire ended capacitors. 10 for £1.50 P&P 50p (£2.30 inc. VAT & P). (Min. 10) N.M.S.

3-PHASE VARIABLE VOLTAGE TRANSFORMERS
Dual input 200-240V or 380-415V. Star connected
3KVA 5 amp per phase max. £106.43
6KVA 10 amp per phase max. £159.37
10KVA 16 amp per phase max. £327.43

LT TRANSFORMERS
13-0-13V at 1 amp £2.50 P&P 50p (£3.45 inc. VAT)
0-15V at 12 amp 0-30V at 12 amp £20.40 P&P £2.30 (£26.11 inc. VAT & P)
0.6V/12V at 20 amp £16.20 P&P £1.00 (inc. VAT £19.78)
0-12V at 20 amp or 0-24V at 10 amp £14.90 P&P £1.50 (£18.86 inc. VAT & P)
0-6V/12V at 10 amp £9.10 P&P £1.50 (inc. VAT £12.19)
0-6V/12V/17V/18V/20V at 20 amp £20.80 P&P £2.00 (£26.34 inc. VAT & P)
0-10V/17V/18V at 10 amp £11.55 P&P £1.50 (inc. P&P £16.35)

CARRIAGE, PACKING & VAT EXTRA

POWER RHEOSTATS
New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.

25 WATT 10, 25, 100, 150, 250, 500, 1k, 1.5k ohm £2.80 Post 20p (£3.45 inc. VAT & P). 50 WATT 250 ohm £2.90 Post 25p (£3.62 inc. VAT & P). 100 WATT 1/5, 10/25/50/100/250/300/500/1K/1.5K/2.5K/5kohm £6.90 Post 35p (£8.34 inc. VAT & P). Black Silver Skirted Knob calibrated in Nos 1-9, 1 1/2in dia brass bush. Ideal for above Rheostats 24p ea.

STROBE! STROBE! STROBE!

SUPER HY-LITE STROBE KIT Mk. IV
Details on receipt of foolscap s.a.e.
Latest type Xenon white light tube. Solid state timing and triggering circuit 230/240V AC operation. Speed adjustable 1.20 f.p.s. Designed for large rooms, halls etc. Light output greater than many so called 4 Joule strobes. Price: £22.00 post £1.50 (£27.03 inc. VAT & P). Specially designed case and reflector for Hy-Lite £9.00 Post £1.00 (£12.08 inc. VAT & P).

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES
4ft 40 watt £8.70 (callers only £10.00 inc. VAT). 2ft 20 watts £6.20. Post 75p (£7.99 inc. VAT & P). (For use in standard bi-pin fittings.)

Mini 12in 6 watt £2.80. Post 35p (£3.62 inc. VAT & P). 9in 6 watt £2.25 Post 35p (£2.99 inc. VAT & P). 6in 4 watt £2.25 Post 35p (£2.99 inc. VAT & P).

Complete ballast unit for either 6", 9" or 12" tube 230V AC op £4.50 plus P&P 75p (£5.69 inc. VAT & P). Also available for 12V DC op £4.50 plus P&P 35p (£5.58 inc. VAT & P).

400W UV lamp and ballast complete £38.00 Post £3. (64.73 inc. VAT & P). 400 watt UV lamp only £14.00. Post £1.50 (£17.83 inc. VAT & P).

WIDE RANGE OF DISCO LIGHTING EQUIPMENT S.A.E. (Foolscap) for details.

XENON FLASH GUN TUBES
Range of Xenon tubes available from stock. S.A.E. for full details.

REED SWITCHES
Size 28mmx4mm dia. Price: 10 for £1.00 + P&P 20p (total incl. VAT £1.38). 100 for £8.00 + P&P 30p (total incl. VAT £9.55).

RELAYS Wide range of AC and DC relays available from stock. Phone or write in your enquiries

230/240V AC Relays:
Arrow 2 c/o 15 amp £1.50 (£1.96 inc. VAT & P). T.E.C. open type 3 c/o 10 amp £1.10 (£1.50 inc. VAT & P). 3 c/o sealed 11 pin base £1.25 P & P 25p (£1.73 incl. VAT) KNK1 Relay. 230V AC. 1c/o. Open type 10 amp contact, m.f. by "Keyswitch" 80p + 20p P & P (£1.15 inc. VAT). 5 for £3.75 post paid (£4.32 inc. VAT)

DC Relays: Open type 9/12V 3c/o 7 amp £1.00 (£1.38 inc. VAT & P). 11-pin £1.35 (£1.78 inc. VAT & P) 24V Sealed 3 c/o 7 amp 11 pin £1.38 (£1.78 inc. VAT & P) (amps=contact rating) P&P on any relay 20p.

Very special offer. 0-12V DC, 2 make contacts, new TT3 for £1.75 plus 25p P&P (inc. VAT £2.30). Diamond H heavy duty AC relay 230/240V AC, two c/o contacts 25 amps res at 250V AC £2.50 P&P 50p (£3.45 inc. VAT & P&P) Special base 50p.

HELLERMAN DEUTSCH. Hermetically sealed sub.-min. Relay. 12-24V. D.C. 2 c/o 850 ohm coil. 0.2 pitch. P.C. mounting. L. 20mm. W. 10mm. H. 12mm. Fraction of maker's price: £2.50 post paid (£2.88 incl. VAT). N.M.S.

METERS (New) — 90mm DIAMETER
AC Amp. Type 62T2: 0-1A, 0-5A, 0-20A. AC Volt, 0-15V, 0-300V. DC Amp. Type 65C5 0-2A, 0-10A, 0-20A, 0-50A. DC Volt. 0-15V, 0-30V. All types £3.50 ea plus P&P 50p (£4.60 inc. VAT) 0.50A DC, 0-100A DC. Price £5.00 plus 50p P&P (£6.33 inc. VAT).

GEARED MOTORS
7 1/2 rpm KLAXON motors approx. 25lb inch. 28 rpm WYNSCALE motors approx. 20lb inch. 71 rpm WYNSCALE motors approx. 10lb inch. Above four motors are designed for 110V AC supplied with auto transformer for 240V AC operation £9.25 (P&P 75p) Total incl. VAT & P £11.50, N.M.S.

18 rpm FHP 220/240 AC reversible torque. 14.5kg. Gear ratio 144-1. Brand new, including capacitors, mt. CITECO. Price £14.25 + £1.25 P&P (£17.83 inc. VAT) N.M.S.
30 rpm 23N/240V AC 50lb. in. mt. PARVA-LUX. Price £15.00 + £1.50 P&P (£18.98 inc. VAT) N.M.S.
68 rpm, 240V AC, 50lb. in. 50Hz 0.7 amp. Shaft length 35mm. Dia. 15mm. Wt. 6kg. 800g. Mt. FRACMO. Price £13.00 + £1.50 P&P (£18.98 inc. VAT) R.&T.

24V D.C. Reversible Motor
Parvalux type SD 12L, 24 D.C. shunt wound motor. 133rpm. 88lbs. in. Gearbox ratio 30-1. Current 6-8 amp. Rating continuous. Will operate on reduced power and speed at 9V D.C. or less. Size Dia. 16mm. Width 150mm. Shaft dia. 16mm. Price £16.00 plus p&p £2.00. (£20.70 inc. VAT) N.M.S.

100W Rheostat 1 ohm speed control £8.90 (£7.94 inc. V.A.T.)
100 rpm 110V AC 115lb. in. 50Hz. 2.8 amp. Single phase split capacitor. Immense power. Totally enclosed. Length 250mm. Dia. 135mm. Spindle dia. 15.5mm, length 145mm. Tested. Price £12.00 + £1.50 P&P (£15.53 inc. VAT) R. & T. Suitable Transformer for 230-240V op. Price £8.00 + 75p P&P (£10.65 inc. VAT).

200 rpm 35lbs in 115V 50Hz. Price £16.00 + £1.50 P&P (£20.13 inc. VAT) N.M.S.
Suitable Transformer for 230-240V AC Price £6.00 + £1.00 P&P (£10.35 inc. VAT) N.M.S.

1 rpm 230/240V AC synchronous geared motor. Mt. HAYDON 2 rpm 230/240V AC Synchronous geared Motor. Mt. CROUZET. Either type £2.50 + 30p P&P (£3.68 inc. VAT) N.M.S.

24V DC GEARED MOTOR
24V DC 200 rpm 10 lbs/ins continuously rated geared Motor mfg by either Parvalux or Carter. Easily removable from heavy all chassis containing 9 x 24V DC Solenoids, microswitches, friction clutch, precision gearing, etc. etc. Ex-equipment London Transport Ticket Printer. Price: £11.00 + £2.00 p. & p. (total incl. VAT £14.95).

ROTARY CARBON VANE VACUUM & COMPRESSOR
Direct coupled to 1/3 h.p. 110/115V AC. Motor 4.2 amp. 1380 rpm. Motor manuf. by A.E.I. Pump by Williams. Max. Vac. 25" H.G. Max. pressure cont. 10 p.s.i. 15 p.s.i. Max. airflow 3 c.f.m. at "0" H.G. Price £30.00 + P & P £4.00 (£37.95 inc. VAT) N.M.S.
Suitable transformer for 240V op. £10.00 P & P £2.00 (£13.80 incl. VAT) N.M.S.

REDUCTION DRIVE GEARBOX
Ratio 72:1 input spindle 1/4 x 1/2in. Output spindle 3/4 x 3in long. Overall size approx 120x98x68mm. All metal construction. Ex-equip tested. Price £2.00 + 50p P&P (£2.68 inc. VAT & P).

AC Wkg TUBULAR CAPACITORS
Fraction of maker's price. Motor start, etc.

| | | | | | |
|----------|---------|-------|---------|---------|---------|
| 1.5 mfd. | 440V AC | 60p | 14 mfd. | 400V AC | £3.00 |
| 2 mfd. | 250V AC | 60p | 15 mfd. | 250V AC | £1.50 |
| 2 mfd. | 450V AC | 75p | 19 mfd. | 280V AC | £2.00 |
| 2 mfd. | 440V AC | 75p | 20 mfd. | 250V AC | £2.25 |
| 3 mfd. | 440V AC | £1.00 | 50 mfd. | 370V | £5.00 |
| 4 mfd. | 440V AC | £1.00 | | | (block) |
| 5 mfd. | 400V AC | £1.25 | | | |
| 5.3 mfd. | 160V AC | 80p | | | |
| 5.4 mfd. | 280V AC | 75p | | | |
| 6.5 mfd. | 280V AC | £1.00 | | | |
| 7.5 mfd. | 200V AC | £1.00 | | | |
| 10 mfd. | 250V AC | £1.00 | | | |

P&P up to 2.5 mfd. 25p. 3 mfd. to 20 mfd. 50p. 50 mfd. £1.50. All plus VAT. N.M.S.

SPECIAL DISCOUNT FOR BULK ORDERS

'VENNER TYPE' ERD TIME SWITCH
200/250V AC 30amp 2 on / 2 off every 24 hrs at any manually pre-set time. 36-hour spring reserve and day omitting device. Built to highest Electricity Board Specification. Price £9.00. P&P 75p (£11.21 inc. VAT) R&T.

SANGAMO WESTON TIME SWITCH
Type S251 200/250V AC 2 on 2 off every 24 hours. 20 amps contacts with override switch. Diameter 4 1/4 x 3 1/4 price £8.50 P&P 50p (£10.35 inc. VAT & P). Also available with solar dia. R&T.

PROGRAMME TIMERS
12 Cam Programmer Timers. 240v. A.C. op. Each Cam individually adjustable. Price £7.50 plus 75p p&p (£9.49 inc. V.A.T.). R&T.
Ditto, 6 adjustable 6 fixed cams. Price £6.00 plus 75p p&p (£7.76 inc. V.A.T.) R&T.

MINIATURE PROGRAMMER
Crouzet 1 rpm 115V AC Motor operating 2 roller micro-switches (4 amp). Can be used on 240V AC with either 0.25 mfd 250V Condenser or 5.6K wirewound resistor 7 watts (supplied). Price £2.50 + 50p P&P (£3.45 inc. VAT & P). N.M.S.

800 WATT DIMMER SWITCH
Easily fitted. Will control up to 800W. of all lights except fluorescent at mains voltage. Price: £3.90 + 50p P & P (£5.06 incl. VAT).

N.M.S. — New Manufacturers' Surplus R.&T. — Reconditioned and Tested

Personal callers only
9 Little Newport Street
London WC2H 7JJ
Tel: 01-437 0576


All Mail Orders — Kp
Ample parking space
Showroom open Monday-Friday

SERVICE TRADING CO
57 BRIDGMAN ROAD CHISWICK LONDON W4 5BB 01 995 1560
ACCOUNT CUSTOMERS MIN. ORDER £10

Personal callers only
9 Little Newport Street
London WC2H 7JJ
Tel: 01-437 0576

LEADER TEST INSTRUMENTS

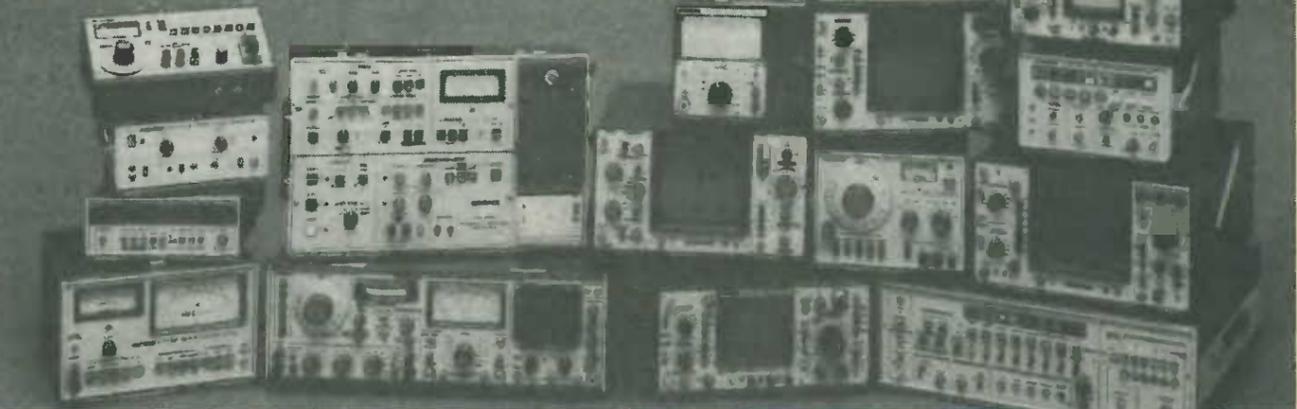- more performance and reliability than you ever thought possible



A Leader instrument for every need.

The full range of Leader Test Equipment, the first choice of engineers around the world, is now available in the U.K. Leader products, with a long history of high reliability, backed by a 1-year warranty, are engineered and built to the most rigid standards, and incorporate the latest technology. A complete technical and service facility is provided in the U.K. by Sinclair Electronics Ltd.

RADIO/CB/TV TEST



CRT Testers · Pattern Generators · Signal Generators · Antenna Impedance Meters · RF Power Meters · C.B. Signal Generators · Stereo Signal Generators · Dip Meters · SWR/Wattmeters
LSG16 SIGNAL GENERATOR
A compact R.F. generator ideally suited to checking alignment of AM/FM and T.V. receivers.
* Frequency Range 100 KHz - 100 MHz
* Frequency Accuracy ± 1.5%
* Crystal Oscillator 1-15 MHz
* Modulation Internal 1kHz for A.M.
* Output Voltage 0.1Vrms or higher to 100 MHz

GENERAL TEST

Function Generators · Transistor Checkers · LCR Bridges · Power supplies · Millivoltmeters · Curve Tracers · Home Appliance Testers
LHM 80A H.V. METERED PROBE
* Input Impedance 20KΩ per volt
* Range 40K Volts
* Accuracy ± 3% Full Scale
LDP 076 LOGIC PROBE
Fast servicing and analysis of digital circuits
* Input Impedance > 10MΩ
* Frequency Range DC to 50MHz
* Minimum Pulse Width 10nsch




AUDIO TEST



Audio Generators · Frequency Response Recorders · Audio Systems Analyzers · Wow & Flutter Meters · Speaker Analyzers · Audio Testers · Distortion Meters · Attenuators
LF5600A FREQUENCY RESPONSE RECORDER
Designed to graphically record wow and flutter, drift, voltage, temperature and frequency response of audio equipment.
* Frequency Range 20 Hz - 30 KHz
* Variable chart speed
* Voltage range 0.1V, 1V, 10V
* Sweep Oscillator *Pilot Signal *Cartridge pen
* Metered, Swept frequency input/output voltage

OSCILLOSCOPES

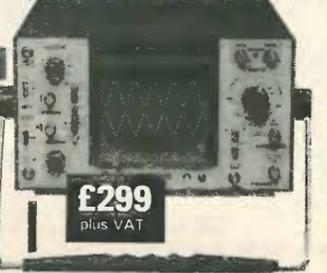4-50MHz Oscilloscopes with more performance and reliability for less cost. The Leader range of oscilloscopes includes 14 models, single and dual trace, for bench or field use. All models offer comprehensive triggering controls, TTL compatible Z AXIS modulation and convenient colour-keyed front panel layout. Probes are included with each model.



LB0508A OSCILLOSCOPE

With 20MHz bandwidth and 10 mV input sensitivity on a 5" screen this universal oscilloscope is suitable for a wide range of applications

£299 plus VAT
* 5" Dual trace
* DC-20 MHz bandwidth (vert amp)
* 10 mV Sensitivity
* Sweep mode: chop - ALT, CH1, CH2, X-Y
* Synchronisation: Auto, Norm, TV, Int., Ext., +, -
* Timebase Sweep Speeds: 0.5 μs/cm - 200 ms/cm
* X5 Magnification (max speed 100ns/cm)

| | | | | |
|--------------|--------|-----------|--------------|--------------------|
| LBO 310A | 4 MHz | 20 mV | Single Trace | 3" |
| LBO 301 | 8 MHz | 10 mV | Single Trace | 3" |
| LBO 308S | 20 MHz | 2 mV | Dual Trace | 3.5" Mains/Battery |
| LBO 510A | 4 MHz | 20 mV | Single Trace | 5" |
| LBO 512A | 10 MHz | 10 mV | Single Trace | 5" |
| LBO 513 | 10 MHz | 5 mV/1 mV | Single Trace | 5" |
| LBO 514 | 10 MHz | 5 mV/1 mV | Dual Trace | 5" |
| LBO 552A | 10 MHz | 20 mV | Dual Trace | 5" Stereo Scope |
| LBO 506A | 15 MHz | 10 mV | Dual Trace | 5" |
| LBO 507A | 20 MHz | 10 mV | Single Trace | 5" |
| NEW LBO 515B | 30 MHz | 5 mV | Dual Trace | 4.5" Sweep Delay |
| LBO 520A | 35 MHz | 5 mV | Dual Trace | 5.5" |
| NEW LBO 517 | 50 MHz | 5 mV/1 mV | Quad Trace | 6" Sweep Delay |

For full technical details together with price list please contact:

LEADER

SINCLAIR ELECTRONICS LTD

London Road, St. Ives, Huntingdon, Cambs. PE17 4HJ.
Telephone: St. Ives (0480) 64646. Telex: 32250

Sinclair Electronics Ltd. reserve the right to alter prices and specifications on Leader equipment without prior notice.

SERVICE TRADING CO

FT3 NEON FLASH TUBE

High intensity multi turn high voltage, neon glow discharge flash tube. Design for ignition timing etc. £1.50. P&P 25p. (£2.01 inc. VAT) 3 for £3. P&P 50p (£4.03 inc. VAT & P).

WHY PAY MORE?

MULTI RANGE METERS Type MF15A. AC/DC volts 10, 50, 250, 500, 1000 Ma 0.5 0.10 0.100. Sensitivity 2000V 24 ranges dimensions 133x93x46mm. Price £7.00 plus 50p P&P (£8.63 inc. VAT & P).

SOLID STATE E.H.T. UNIT

- Input 230V A.C. Fully isolated output. 10 mm spark.
- Approx. 15KV. Built-in 10 sec. Timer. Easily modified for 20 sec., 30 sec., to continuous operation. Designed for boiler ignition. Dozens of uses in the field of physics and electronics, e.g. supplying neon or argon tubes, etc.
- E.H.T. starter for lasers, xenons, C.S.I. lamps, Van de Graaff Generator, loss of vacuum detector, Oudin coils, etc. etc.
- Size: Lgh 155 mm. Width 85 mm. Ht 50 mm. Wt 530 gms. Price £5.00 + 85p p. & p. (Total incl. VAT £5.73) N.M.S.

230 VOLT AC FAN ASSEMBLY

Powerful continuously rated AC motor complete with 5 blade 6 1/2" or 4 blade 3" aluminium fan. New reduced price £3.50 P&P 65p (£4.77 inc. VAT & P) N.M.S.

A.E.G. CONTACTOR

Type LS6/L11. Coil 240V 50Hz. Contacts - 3 make 600V 20 amp 1 break 600V 20 amp. Price £6.50 + 50p P&P (£6.90 inc. VAT & P) N.M.S.

ARROW-HART MAINS CONTACTOR

Cat. No. 130A30
Coil 250V or 500V AC. Contacts, 3 make 50 amp up to 660V AC 20hp at 440V 3 phase 50Hz. Price £7.75 + P&P £1.00 (Total incl. VAT & P £10.06). N.M.S.

SMITH BLOWER

Type FFB.1706. Small quiet smooth running. 240V AC operation. Output aperture 45x40cm. Overall size 135x165mm. Flange mounting. Price: £4.25 P&P 75p. (£5.75 incl. VAT & P). N.M.S. Other types available SAE for details

24V DC BLOWER UNIT

USA made 24V DC 0.8 amp blower to operate well on 12V 0.4 amp DC producing 30 cu ft min at normal air pressure. Maximum housing dia 110mm, depth inc motor 75mm, nozzle length 19mm, dia 22mm. Ideal for cooling mobile equipment, car, caravan, etc. £4.50 P&P 75p (£6.04 inc. VAT & P) N.M.S.

CENTRIFUGAL BLOWER UNIT

Airflow Development Ltd. powered by G.E.C. 230/250V. 2,850 rpm motor producing approx. 120 cfm. Aperture: 65x90mm. Overall size 222x225x195mm incl. starter capac. Price: £16.00 + P&P £2.00 (total inc. VAT £20.70). N.M.S.

MINIATURE UNISELECTOR

12V 11 way 4 bank (3 non-bridging, 1 homing) £3.50 P&P 35p (£4.43 inc. VAT & P).

MICRO SWITCHES ex. new equip.

Sub. Min. Honeywell Lever m/s type 3115m 906t. 10 for £3.50 post paid (£4.03 incl. VAT) These V3 types.

BURTON TYPE (Pye) 10 for £3.00 (£3.45 incl. VAT)

Short Lever type. 16amp. rating (Grouzet) £4.00 (£4.60 incl. VAT)

HEAVY DUTY SOLENOID

Mfg by Magnetic Devices. 240V AC intermittent operation. approx. 20lb. pull at 1.25in Exgip. Tested. Price £5.50 + 75p P&P (£7.19 inc. VAT & P) R&T

12V DC SOLENOID N.M.S.

12V DC heavy duty Solenoid 4 Kp pull. Easily removable from plate. All. chassis containing 4 x 24V DC Push Solenoids (1 1/2 lb approx). 5-fig. Counter. 6 min photo cells. Sub-min microswitches etc. etc. Ex-gip London Transport Printer. Price: £9.00 + £1.00 p. & p. (total incl. VAT £11.50).

12V DC SOLENOID

Approx. 1lb pull. Price £1.40 + P&P 30p (£1.96 incl. VAT & P).

TYPE AG/TG

18-24V DC 70 ohm Coil Solenoid. Push or Pull Adjustable travel to 3/16in. Fitted with mounting brackets and spark suppressor. Size: 100x65x25mm. Price 3 for £2.40 + 30p P&P (min. 3 off) (£3.10 inc. VAT & P)

INSULATION TESTERS (NEW)

Test to I.E.E. spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L 8in, W 4in, H 6in. weight 6lb

500 VOLTS 500 megohms £49.00 Post 80p (£57.27 inc. VAT & P)
1000 VOLTS 1000 megohms £55.00 Post 80p (£64.17 inc. VAT & P). SAE for leaflet

YET ANOTHER OUTSTANDING OFFER

New 1MFD 600V Dabliuer wire ended capacitors, 10 for £1.50 P&P 50p (£2.30 inc. VAT & P). (Min. 10) N.M.S.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V

| | |
|--------------------------------|---------|
| 200W 1 amp inc. a.c. voltmeter | £14.50 |
| 0.5 KVA (2 1/2 amp MAX) | £18.00 |
| 1 KVA (5 amp MAX) | £24.00 |
| 2 KVA (10 amp MAX) | £39.00 |
| 3 KVA (15 amp MAX) | £47.00 |
| 10 KVA (50 amp MAX) | £76.00 |
| 17 KVA (75 amp MAX) | £260.00 |

All plus Carriage & VAT

3-PHASE VARIABLE VOLTAGE TRANSFORMERS

Dual Input 200-240V or 380-415V. Star connected

| | |
|-----------------------------|---------|
| 3KVA 5 amp per phase max. | £106.43 |
| 6KVA 10 amp per phase max. | £159.37 |
| 10KVA 16 amp per phase max. | £327.43 |

CARRIAGE, PACKING & VAT EXTRA

LT TRANSFORMERS

13-0-13V at 1 amp £2.50 P&P 50p (£3.45 inc. VAT)
0-15V at 12 amp, 0-30V at 12 amp £20.40 P&P £2.30 (£26.11 inc. VAT & P)
0.6V/12V at 20 amp £16.20 P&P £1.00 (inc. VAT £19.78)
0-12V at 20 amp or 0-24V at 10 amp £14.90 P&P £1.50 (£18.86 inc. VAT & P)
0-6V/12V at 10 amp £9.10 P&P £1.50 (inc. VAT £12.19)
0-6V/2V/17V/18V/20V at 20 amp £20.90 P&P £2.00 (£28.34 inc. VAT & P)
0-10V/17V/18V at 10 amp £11.55 P&P £1.50 (inc. P&P £15.35)

POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated

| | |
|--|----------------------|
| 25 WATT 10, 25, 100, 150, 250, 500, 1k, 1.5k ohm | £2.80 |
| Post 20p | (£3.45 inc. VAT & P) |
| 50 WATT 250 bhm | £2.90 |
| Post 25p | (£3.62 inc. VAT & P) |
| 100 WATT 1/5/10/25/50/100/250/300/500/1K/1.5k/2.5k/5kohm | £6.90 |
| Post 35p | (£8.34 inc. VAT & P) |

Black Silver Skirted Knob calibrated in Nos 1-9, 1 1/2 in dia brass bush. Ideal for above Rheostats 24p ea.

STROBE! STROBE! STROBE!

SUPER HY-LITE STROBE KIT Mk. IV

Details on receipt of foolscap s.a.e. Latest type Xenon white light tube. Solid state timing and triggering circuit 230/240V AC operation. Speed adjustable 1.20 f.p.s. Designed for large rooms, halls etc. Light output greater than many (so called 4 Joule) strobes. Price: £22.00 post 1.50 (£27.03 inc. VAT & P). Specially designed case and reflector for Hy-Lite £9.00 Post 1.00 (£12.08 inc. VAT & P)

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft 40 watt £8.70 (callers only £10.00 inc. VAT). 2ft 20 watts £6.20. Post 75p (£7.99 inc. VAT & P). (For use in standard bi-pin fittings)

Mini 12in 8 watt £2.80. Post 35p (£3.62 inc. VAT & P).
9in 6 watt £2.25 Post 35p (£2.99 inc. VAT & P).
6in 4 watt £2.25 Post 35p (£2.99 inc. VAT & P).
Complete ballast unit for either 6", 9" or 12" tube 230V AC op. £4.50 plus P&P 75p (£5.69 inc. VAT & P). Also available for 12V DC op. £4.50 plus P&P 35p (£5.58 inc. VAT & P).
400W UV lamp and ballast complete £38.00 Post £3 (£47.73 inc. VAT & P). 400 watt UV lamp only £14.00. Post £1.50 (£17.83 inc. VAT & P).

WIDE RANGE OF DISCO LIGHTING EQUIPMENT

S.A.E. (Foolscap) for details.

XENON FLASH GUN TUBES

Range of Xenon tubes available from stock. S.A.E. for full details.

REED SWITCHES

Size 28mm x 4mm dia. Price: 10 for £1.00 + P&P 20p (total incl. VAT £1.38). 100 for £8.00 + P&P 30p (total inc. VAT £9.55).

RELAYS

Wide range of AC and DC relays available from stock. Phone or write in your enquiry

230/240V AC Relays:

Arrow 2 c/o 15 amp £1.50 (£1.96 inc. VAT & P). T.E.C. open type 3 c/o 10 amp £1.10 (£1.50 inc. VAT & P). 3 c/o sealed 11 pin base £1.25 P & P 25p (£1.73 incl. VAT) KMK1 Relay. 230V AC. 1 c/o. Open type 10 amp contact, mf. by "Keyswitch" 80p + 20p P & P (£1.15 inc. VAT). 5 for £3.75 post paid (£4.32 inc. VAT).

DC Relays:

Open type 9/12V 3 c/o 7 amp £1.00 (£1.38 inc. VAT & P). 11-pin £1.35 (£1.78 inc. VAT & P) 24V Sealed 3 c/o 7 amp 11 pin £1.38 (£1.78 inc. VAT & P) (amps=contact rating) P&P on any relay 20p.

METERS (New) - 90mm DIAMETER

AC Amp. Type 62T2: 0-1A, 0-5A, 0-20A. AC Volt, 0-15V, 0-300V. DC Amp, Type 65C5 0-2A, 0-10A, 0-20A, 0-50A. DC Volt. 0-15V, 0-30V. All types £3.50 ea plus P&P 50p (£4.60 inc. VAT) 0.50A DC, 0-100A DC. Price £5.00 plus 50p P&P (£6.33 inc. VAT).

GEARED MOTORS

7 1/2 rpm KILAXON motors approx. 25lb inch. 28 rpm WYNSCALE motors approx. 20lb inch. 70 rpm WYNSCALE motors approx. 10lb inch. Above four motors are designed for 110V AC supplied with auto transformer for 240V AC operation £9.25 (P&P 75p). Total incl. VAT & P £11.50, N.M.S.

18 rpm FHP 220/240 AC reversible torque. 14.5kg. Gear ratio 144-1. Brand new, including capacitors, mf. CITENCO. Price £14.25 + £1.25 P&P (£17.83 inc. VAT). N.M.S.
30 rpm 230/240V AC 50lb. in. mf. PARVALUX. Price £15.00 + £1.50 P&P (£17.98 inc. VAT) N.M.S.

56 rpm 240V AC. 50lb. in. 50Hz 0.7 amp. Shaft length 35mm. Dia. 16mm. Wt. 6kg. 600g. mf. FRACMO. Price £15.00 + £1.50 P&P (£18.98 inc. VAT). R.&T.

24V D.C. Reversible Motor

Parvalux type SD12L, 24 D.C. shunt wound motor. 133rpm. 65lbs. in. Gearbox ratio 30-1. Current 6-8 amp. Rating continuous. Will operate on reduced power and speed at 9V D.C. or less. Size Dia. 16mm. Width 150mm. Shaft dia. 16mm. Price £18.00 plus p&p £2.00. (£20.70 inc. VAT). N.M.S.

60rpm 100lb in rating. Price as above.
100W Rheostat 1 ohm speed control £6.90. (£7.94 inc. V.A.T.)
100 rpm 110V AC 1.15lb. in. 50Hz, 2.8 amp. Single phase split capacitor. Immense power. Totally enclosed. Length 250mm. Dia. 135mm. Spindle dia. 15.5mm. length 145mm. Tested. Price £12.00 + £1.50 P&P (£15.83 inc. VAT). R. & T. Suitable Transformer for 230-240V op. Price £8.00 + 75p P&P (£10.05 inc. VAT).
200 rpm 35lbs in 115V 50Hz. Price £16.00 + £1.50 P&P (£20.13 inc. VAT). N.M.S.

Suitable Transformer for 230-240V AC. Price £8.00 + £1.00 P&P (£10.35 inc. VAT). N.M.S.
1 rpm 230/240V AC synchronous geared motor. Mf. HAYDON 2 rpm 230/240V AC Synchronous geared Motor. Mf. CROUZET. Either type £2.90 + 30p P&P (£3.68 inc. VAT). N.M.S.

24V DC GEARED MOTOR

24V DC 200 rpm 10 lbs/ins continuously rated geared Motor mfg by either Parvalux or Carter. Easily removed from heavy all chassis containing 9 x 24V DC Solenoids, microswitches, friction clutch, precision gearing, etc. Ex-equipment London Transport Ticket Printer. Price: £11.00 + £2.00 p. & p. (total incl. VAT £14.95).

ROTARY CARBON VANE VACUUM & COMPRESSOR

Direct coupled to 1/3 h.p. 110/115V A.C. Motor 4.2 amp. 1380 rpm. Motor manuf. by A.E.I. Pump by Williams. Max. Vac. 25" H.G. Max. pressure cont. 10 p.s.i. int. 15 p.s.i. Max. airflow 3 p.f.m. at 10" H.G. Price £30.00 + P & P £3.00 (£37.88 inc. VAT). N.M.S.

REDUCTION DRIVE GEARBOX

Ratio 72:1 input spindle 1/4 x 1/2in. Output spindle 3/4 x 3/16in. Overall size approx. 120 x 98 x 68mm. All metal construction. Ex-gip tested. Price £2.00 + 50p P&P (£2.88 inc. VAT & P).

AC Wkg TUBULAR CAPACITORS

Fraction of maker's price. Motor start, etc.

| | | | | | |
|----------|---------|-------|---------|---------|-------|
| 1.5 mfd. | 440V AC | 60p | 14 mfd. | 400V AC | £3.00 |
| 2 mfd. | 250V AC | 60p | 15 mfd. | 250V AC | £1.50 |
| 2 mfd. | 450V AC | 75p | 15 mfd. | 280V AC | £2.00 |
| 2.2 mfd. | 440V AC | 75p | 30 mfd. | 250V AC | £2.25 |
| 3 mfd. | 440V AC | £1.00 | 30 mfd. | 370V | £5.00 |
| 4.1 mfd. | 440V AC | £1.00 | | (block) | |
| 5 mfd. | 400V AC | £1.25 | | | |
| 6.3 mfd. | 160V AC | 60p | | | |
| 6.4 mfd. | 280V AC | 75p | | | |
| 6.5 mfd. | 280V AC | £1.00 | | | |
| 7.5 mfd. | 200V AC | £1.00 | | | |
| 10 mfd. | 250V AC | £1.00 | | | |

'VENNER TYPE' ERD TIME SWITCH

200/250V AC 30amp 2 on 2 off every 24 hrs at any manually pre-set time. 36-hour spring reserve and day omitting device. Built to highest Electricity Board Specification. Price £9.00. P&P 75p (£11.21 inc. VAT). R&T.

SANGAMO WESTON TIME SWITCH

Type S251 200/250 AC 2 on 2 off every 24 hours. 20 amps contacts with override switch. Diameter 4" x 3" price £8.50 P&P 50p (£10.38 inc. VAT & P). Also available with solar dia. R&T.

PROGRAMME TIMERS

12 Cam Programmer Timers. 240V. A.C. op. Each Cam individually adjustable. Price £7.50 plus 75p p&p. (£9.49 inc. V.A.T.). R&T.
Ditto, 6 adjustable 6 fixed cams. Price £6.00 plus 75p p&p (£7.76 inc. V.A.T.). R&T.

MINIATURE PROGRAMMER

Crouzet 1 rpm 115V AC Motor operating 2 roller micro-switches (4 amp). Can be used on 240V AC with either 0.25 mfd 250V Condenser or 5.6K wirewound resistor 7 watts (supplied). Price £2.50 + 50p P&P (£3.45 inc. VAT & P). N.M.S.

800 WATT DIMMER SWITCH

Easily fitted. Will control up to 800W. of all lights except fluorescent at mains voltage. Price: £3.90 + 50p P & P (£5.06 incl. VAT).
N.M.S. - New Manufacturers' Surplus R.&T. - Reconditioned and Tested

SERVICE TRADING CO

57 BRIDGMAN ROAD CHISWICK LONDON W4 5BB 01 995 1560
ACCOUNT CUSTOMERS MIN. ORDER £10

All Mail Orders - Callers
Ample parking space
Showroom open Monday-Friday

Personal callers only
9 Little Newport Street
London WC2H 7JJ
Tel: 01-437 0576

Appointments

Advertisements accepted up to 12 noon Monday, 22nd December, for February issue, subject to space being available.

DISPLAYED APPOINTMENTS VACANT: £12.00 per single col. centimetre (min. 3cm).
LINE advertisements (run on): £2.00 per line, minimum three lines.
BOX NUMBERS: £1 extra. (Replies should be addressed to the Box Number in the advertisement, c/o Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.
PHONE: Eddie Farrell, 01-661 3500, Ext. 8158.
Classified Advertisement Rates are currently zero rated for the purpose of V.A.T.

Check out your market value ✓

£5k (for starters) to £15k+ (high flyers)

and your potential for a bigger job with salary and prospects to match – that's our business. If you don't make the effort to check your market value, discreetly, with a leading consultancy, you will almost certainly miss the sort of opportunities you ought to go for. Are you in design/senior test/RF/micros/telecoms or computer service? Qualified to HNC/BSc?

Ring in confidence
Barry Barnett

01-491 4706

Knight Engineering People
14 Old Park Lane,
London W1Y 4NL



Recruitment Consultants within the BOC Management Consultancy Team

(849)

ONE IN A MILLION?

Among the million or so leaving school or university this year there is a chance that one – perhaps two – is destined to make a significant development in audio.

That person's first decision might well be to join QUAD in Huntingdon. At school, he or she will have realised that amplifier design is not just a matter of having a listen or a fiddle with standard circuits and their variations. Later will come an adolescent stage of great discoveries. "Increase the rise time to eliminate TIM". "Regulate the power supply for better imaging".

Following on from such childish things will have come an ability to distinguish between the characteristic impedance of the medium and the third row of the dress circle and between peak flux density and the rather gooey substance fed by spoon to small children. He or she will, nevertheless, be sufficiently down to earth to know that one newton is about the weight of the average apple.

1 in 10⁶?
Well, drop us a line anyway.

Mr. P. J. Walker
THE ACOUSTICAL MANUFACTURING COMPANY LIMITED
30 St. Peters Road, Huntingdon, Cambs. PE18 7DB

(403)

ELECTRONIC SERVICE ENGINEERS

Age 23-40 LONDON & GLASGOW

Our Company specialises in both sales and servicing of Professional Sound and Lighting equipment.

We are the UK's leading Company in this specialised field and due to continued expansion we now have vacancies in the above areas.

Applications are invited from Electronic Service Engineers who have had at least 3 years experience working with either Hi-Fi, Studio P.A. or similar equipment.

Good salary plus Service Commission (depending on age and experience).

Contact Max Randell for further details.

Roger Squire's

Roger Squire Limited
Barnet Trading Estate Park Road Barnet Herts EN5 5SA
Telephone: 01-441 1919


(876)

Appointments

Broadcast Transmission Engineering

To ensure that broadcasting services are of consistently high quality provides far greater challenge than you may have realised. It is essential that viewers and listeners can rely on good television and radio reception and at the IBA we have a firm commitment to achieving these superior standards. We operate a

network of over 570 transmission stations nationwide, servicing Independent Television and Local Radio, services which we are steadily expanding. An increasing number of transmitting stations and the addition of the fourth channel all mean that ours is the environment to assure your future – we can offer both security and scope. We rely greatly on the skills of our highly trained engineers to maintain our Transmitting Stations so that they are reliable in operation and transmit services of the expected high standard.

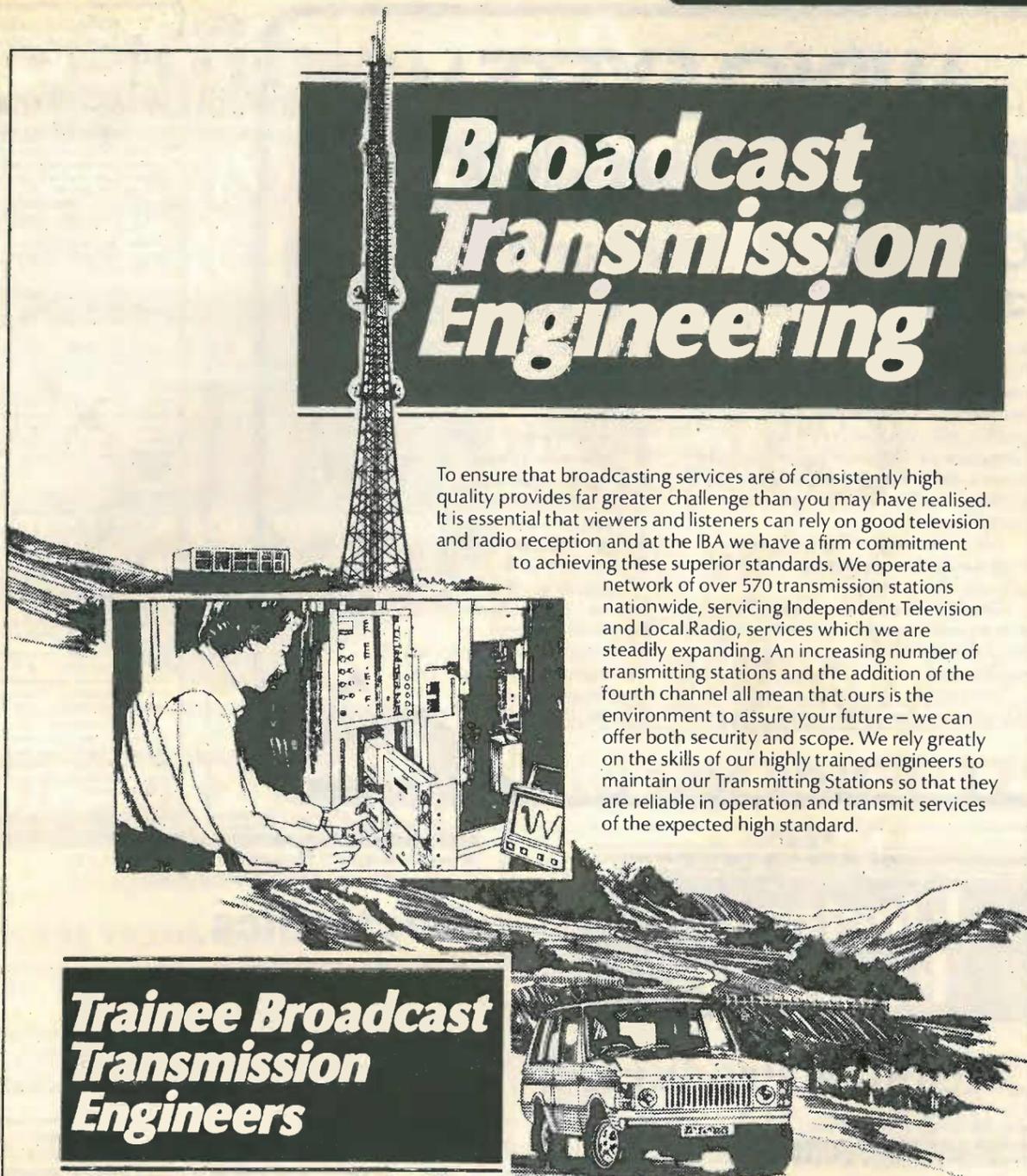

Trainee Broadcast Transmission Engineers

We have opportunities for Engineers (male or female) ideally at the HNC/HTC or equivalent level, to join us on our next training programme which commences this summer. Consideration will also be given to applicants at the City & Guilds Full Tech. to CNAA pass degree level. This comprehensive and carefully devised training, in collaboration with a leading Polytechnic, can result in a nationally recognised diploma, and is a step beyond traditional learning, combining theoretical and practical studies to give you a grounding in broadcast engineering that is second to none. During the course we will pay your fees, accommodation and meals and, if you do not already possess a full driving licence, we will arrange and pay for your instruction. Your salary, on satisfactory completion of the training, will be £6,752, and will then rise annually to £8,372 per

annum, with further progression to £9,433 per annum. Your initial salary while training will be in the range of £5,000/£5,400 per annum. Additionally we offer you a generous range of benefits, including free life assurance and personal accident schemes, a contributory pension scheme, generous relocation expenses and subsidised mortgage facilities.

To receive our illustrated information package and application form please write to or telephone Mike Wright, Personnel Officer – Engineering Regions, IBA, Crawley Court, Winchester, Hants, SO21 2QA. Telephone Winchester 822574 or 822273.



(841)

AUDIO SYSTEMS DESIGN ENGINEERS

Circa £8,000 ...join our Project Teams designing Professional Audio Equipment

Neve are leading designers and manufacturers of Professional Sound Control and Distribution Systems used throughout the world in Television, Film, Broadcasting and Recording Studios. We have immediate vacancies for Audio Engineers to work on the Design and Development of exciting New Products for the Professional Audio Industry.

We are looking for Senior Design Engineers with several years experience of audio system design.

Qualifications are Degree or HNC but, in exceptional cases, relevant experience may be acceptable instead of a formal qualification.

Neve employ over 400 people in the U.K. alone and are able to offer very good

career prospects in a growing and successful company. Engineers appointed could expect the following benefits where appropriate:-

- * Generous relocation package
- * Contributory Pension Scheme
- * Subsidised canteen
- * Company Transport to/from Royston/Cambridge
- * Four weeks paid holiday
- * Overtime paid

Telephone, call or write for application form to: Valerie Chapman, Personnel Manager, Neve Electronic Laboratories Ltd., Cambridge House, Melbourn, Royston, Herts. Tel: Royston (0763) 60776.

Neve

(840)

AGRICULTURAL RESEARCH COUNCIL LETCOMBE LABORATORY

ELECTRONICS ENGINEER

Required to develop research apparatus generally in support of the laboratory's programme in plant and soil science. The main duties at present involve the design, development, and construction of microprocessor systems for analysing, calculating and tabulating measurements recorded automatically or manually in the field and for controlling field and laboratory experiments.

Appointment as Professional and Technology Officer Grade II. Salary Scale £7,000 to £8,100. Non-contributory superannuation.

Qualifications required: degree or equivalent in appropriate field with at least five years' recognised study or professional experience.

Apply to the Secretary, Agricultural Research Council, Letcombe Laboratory, Wantage, Oxfordshire OX12 9JT for further details and application form. Closing date 5 January, 1981. Quote Ref. 80/9.

(870)

THE MIDDLESEX HOSPITAL W1

MEDICAL PHYSICS TECHNICIAN III

(Clinical Measurement Department) Salary: £5750-£7177 p.a.

The duties include the servicing, construction and modification of a wide range of medical electronic equipment and applicants will need experience of both analogue and digital circuit design.

We would welcome informal visits to the Department, and application form and job description are available from Mrs R Sutton, Personnel Officer, The Middlesex Hospital, Mortimer Street, London W1. Tel: 01-636 8333 ext. 7462.

(842)

Royal Liverpool Hospital
Prescot Street, Liverpool L7 8XP

Electronics Technician

(Medical Physics Technician Grade III)

To assist with the maintenance/development of equipment used in the Department of Nuclear Medicine at the above hospital. Applicants should ideally possess an appropriate O.N.C./H.N.C. or equivalent qualification or should have considerable experience in electronics servicing.

Salary Scale: £4605 to £5952 (pay award pending w.e.f. 1.4.80).

Application form and further details available from the Personnel Department at the above address.



(844)



CAPITAL APPOINTMENTS LTD.

THE UK'S No. 1 ELECTRONICS AGENCY

Design, Dev. and Test to £10,000
Ask for Brian Cornwell

SALES to £12,000 plus car
Ask for Ken Sykes

FIELD SERVICE to £10,000 plus car
Ask for Maurice Wayne

We have vacancies in ALL AREAS of the UK

Telephone: 01-637 5551 (3 lines)

CAPITAL HOUSE
29-30 WINDMILL STREET
LONDON W1P 1HG
TEL: 01-637 5551

Electronics R&D

Join us in the forefront of technology

Take your pick

HF-VHF-UHF-
Microwave Optics & Acoustics

A challenging and full career in Government Service.

Minimum qualification — HNC.

Starting salary up to £6,737 (under review).

Please apply for an application form to the Recruitment Officer (Dept. WW9)

H.M. Government Communications Centre, Hanslope Park, Milton Keynes MK19 7BH.

(589)



GLASGOW Sub-Region
STRATHCLYDE POLICE

WIRELESS TECHNICIAN

Wireless Workshop, Helen Street, Glasgow.
Salary Scale — Tech. 'D' — £5268-£5973.

Duties of the post will involve servicing V.H.F. and U.H.F. radio equipment. A City and Guilds Certificate in Telecommunications or equivalent is desirable but not essential. Applicants must have a current driving licence.

Application forms may be obtained from The Assistant Director of Manpower Services, Glasgow Sub-Region, Strathclyde House (8), India Street, Glasgow G2 4PF, to whom completed forms, quoting Ref. G3105, should be returned by 30th December, 1980.

R. M. O. McCulloch
Director of Manpower Services
(866)

SERVICE ENGINEER

required with at least 3 years' experience of audio equipment. A knowledge of audio visual systems would be advantageous. An excellent salary will be offered to the right person.

Please contact:

Tony Shawyer
Fraser-Peacock Associates Limited
94 High Street
Wimbledon Village
London SW19 5EG
Telephone: 01-947 7551

(865)



require
FIELD SERVICE ENGINEER CAR AUDIO

c. £7,000 + Car

Applicants should hold a C. & G. qualification in Radio and T.V. Electronics or Telecommunications or an H.N.C. in Electronics. It is envisaged that the applicant should have up to 5 years' experience, the specialist knowledge required to analyse and solve car suppression problems and have a wide, general knowledge of car audio equipment, together with a methodical approach to work and the ability to deal in a friendly, polite way with people. You should hold a clean driving licence.

BENCH SERVICE ENGINEERS

Applicants should hold C. & G. Radio and T.V., Electronics Technician or equivalent certificate with a minimum of two years' experience in the Audio field. Alternatively, five years of relevant experience with sound knowledge of electronics is acceptable.

Salary up to £7,500 per annum, according to age and experience. Luncheon vouchers, four weeks' annual holiday and pension scheme.

For further information, do not hesitate to contact:

Mrs. C. A. Burridge
PIONEER HIGH FIDELITY (GB) LTD.
Pioneer House, The Ridgeway, Iver, Bucks.
Tel. Iver (0753) 652222

(776)

Electronics Engineers

Consumer Products

Large American, multi-national company with extensive Far-East manufacturing and engineering facilities opening European headquarters office in London — Spring of 1981.

Excellent opportunity offered to dynamic, well experienced electronics engineer with flair for customer-relations and international business.

Will be required to coordinate technical requirements and specifications and liaise between OEM and private label customers and the company's Far East engineering.

A degree or C&G Full Certificate in Electronics/Radio Engineering and a number of years experience in designing Audio/Video consumer products — essential. Previous business/administrative experience and knowledge of an additional European language — advantageous. Preferred age group 35-50. Excellent salary and prospects for successful candidate.


Write — enclosing photograph and details of qualifications and experience to: Vice-President, Electronics, Amerex Group of Companies, Eldex Building, 21 Ma Tau Wei Road, Kowloon, Hong Kong, B.C.C.



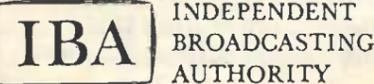(838)

Lines Transmission Engineer

We are looking for a young engineer qualified to HNC level in Electrical Engineering to monitor and test the performance of vision and sound networks rented from the Post Office for Television and Local Radio uses. This post involves liaison with the staff of the ITV and ILR Programme Companies and visiting their studios and IBA Transmitting Sites to undertake investigations. At least two years experience in the communications field is necessary together with a good knowledge of transmission systems. A current driving licence is essential in view of the travelling involved. Starting salary will be on a range from £6,775-£8,395 per annum. Generous relocation expenses will be paid where appropriate.



Applicants (male or female) should write or telephone for an application form quoting Ref: WW/512CC to: Glynis Powell, Personnel Officer, IBA, Crawley Court, Winchester, Hampshire SO21 2QA. Telephone: Winchester 822270.

(846)

LEEDS BRADFORD AIRPORT AIR TRAFFIC ENGINEER

Air Traffic Engineer required to undertake maintenance of all ground communications and navigational equipment including ILS, Radar and CRDF. Applicants should be experienced in ILS and Radar maintenance and hold appropriate technical qualifications. Salary in accordance with Local Government Grade T3 to T5 (4581 to £6381 p.a.). Commencing salary dependent upon experience and qualifications. In addition, the post attracts payment of 16% of basic salary for shift working and approximately 16% enhanced payments for weekend working. A salary award for 1980/81 is pending. National Joint Council conditions for Local Authorities apply to the position and in addition a car mileage allowance is payable for journeys to and from work, when public transport is not available.

Applications stating age, experience and details of educational and technical qualifications should be forwarded to the Airport Director, Leeds Bradford Airport, Yeadon, Leeds LS19 7TZ as soon as possible.

(839)

Leeds Bradford Airport



THE MIDDLESEX HOSPITAL MEDICAL SCHOOL SENIOR ELECTRONICS TECHNICIAN

Applications are invited from suitably qualified and experienced persons for the above post. The successful candidate will work with a wide range of electronic apparatus. Duties would include the use, maintenance and development of research, practical laboratory, video, sound and CCTV equipment. Salary, depending on qualifications and experience, within the range £6,657-£7,950 (inc. London Weighting). Please apply in writing to: **Chief MLSD, Department of Physiology, The Middlesex Hospital Medical School, London, W1P 6DB.** (777)

CHELSEA COLLEGE University of London DEPARTMENT OF ELECTRONICS

ELECTRONICS TECHNICIAN GRADE 5

is required for Electronics Workshop serving Electronics and Physics research and teaching. Interesting prototype instrument design, development and construction work using both digital and analogue techniques, and also the servicing of commercial electronic equipment. Salary (under review) £5556-£6357 p.a. inclusive. Generous holidays. Further details and application form from: **Mr. M. E. Cane (5EW), Chelsea College, Pulton Place, London SW6 5PR.** (780)

BRISTOL POLYTECHNIC DEPARTMENT OF ENGINEERING

Applications are invited to apply for the following post, duties to commence as soon as possible.

LECTURER II/SENIOR LECTURER IN DIGITAL SYSTEMS Ref. No. L52/56

Preference will be given to candidates with industrial experience in digital systems design, including computer architecture and micro-computer applications. A knowledge of LS1/VLS1 design techniques would be an advantage.

SALARY SCALE:
LII - £6012-£8952 (bar)-£9702 per annum
SL - £8952-£10539 (bar)-£11295 per annum

The appointment will be made on the appropriate scale according to relevant previous service/experience. (Progression from the LII scale to the SL SCALE is in accordance with the provisions of the Burnham Further Education Report).

For further details and an application form, to be returned by 30 January, 1981, please contact the **Personnel Office, Bristol Polytechnic, Coldharbour Lane, Frenchay, Bristol BS16 1QY.**

Please quote Reference Number L52/56 in all communications. (874)

DIGITAL EXPERIENCE?

FIELD, SUPPORT AND PRODUCTION. VACANCIES IN COMPUTERS, NC, COMMS, MEDICAL, VIDEO, ETC. Fore free registration ring 01-464 7714 ext. 502 24 HOURS



ELECTRONICS RECRUITMENT SERVICE HIGH ROAD, LOUGHTON, ESSEX 01-502 1589/01-464 7714, EXT. 502 (321)

Bedfordshire Education Service LUTON COLLEGE of Higher Education

LECTURER GRADE I in Physics

Applications are invited for the above post from suitably qualified persons normally holding at least a good Honours Degree in Physics.

The appointee will be required to teach and develop courses in Physics across a broad spectrum from T.E.C. I to Honours Degree level within the B.Sc (CNA) Combined Studies.

Application form and details from **Assistant Director, LCHE, Park Square, Luton, Beds., Tel: (0582) 34111 ext 216.** (843)

ROYAL MILITARY COLLEGE OF SCIENCE SHRIVENHAM, SWINDON, WILTSHIRE DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING

NEW CONCEPTS IN INTEGRATED MILLIMETRE WAVE COMPONENTS

Applications are invited for two research posts concerned with interesting innovative work on millimetre wave integrated circuit components and antennas. Applicants must hold a good honours degree in Physics, Mathematics or Engineering, or have equivalent qualifications and experience. For younger graduates the posts offer a good opportunity to join an active research group.

For Post 1 (sponsored by the US Army) the appointment will be for a period of two years with a possibility of extension to a third year, at Research Scientist/Higher Research Scientist according to qualifications and experience. Ability to carry out measurements is a requirement. An opportunity to study for a higher degree could be made available. Reference HQ 120/1/81.

For Post 2 (sponsored by SRC) the appointment will be for a period of three years at Higher Research Scientist/Senior Research Scientist level according to qualifications and experience. Possession of a higher degree could be an advantage but ability to carry out mathematical work is essential. Reference HQ 120/1/97.

Salary scales: Research Scientist £4809-£6480; Higher Research Scientist (minimum of 2 years' postgraduate experience) £6075-£7999; Senior Research Scientist (minimum of 4 years' postgraduate experience) £7644-£9619.

Accommodation for a single person may be available in a Hall of Residence and there is a possibility of housing for a married candidate.

Application forms and further information may be obtained from the Civilian Administration Office, Royal Military College of Science, Shrivenham, Swindon, Wilts SN6 8LA, telephone (0793) 782551, Ext. 421. Please quote relevant reference number(s).

CLOSING DATE FOR APPLICATIONS: 8th January, 1981. (863)

KINGSTON AND RICHMOND AREA HEALTH AUTHORITY

CHIEF ELECTRONICS TECHNICIAN

(Based at Kingston Hospital) For the maintenance of complex electronic equipment, mostly of a medical nature, also management of subordinate staff. H.N.C. (Electronics) or equivalent required. Previous hospital experience advantageous. Salary: £6291-£7845 p.a. plus £527 p.a. London Weighting. **Application form and job description from: Area Personnel Department, South Wing, Normansfield, Kingston Road, Teddington, Middlesex. Tel: 01-977 8833 Ext. 312.** Closing date: 15th January, 1981. (871)

TOP JOBS IN ELECTRONICS

Posts in Computers, Medical, Comms, etc. ONC to Ph.D. Free service.

Phone or write: **BUREAUTECH, AGY, 46 SELVAGE LANE, LONDON, NW7. 01-906 0251.** (8994)

Technicians in Communications

GCHQ We are the Government Communications Headquarters, based at Cheltenham. Our interest is R & D in all types of modern radio communications - HF to satellite - and their security.

THE JOB All aspects of technician support to an unparalleled range of communications equipment, much of it at the forefront of current technology.

LOCATION Sites at Cheltenham in the very attractive Cotswolds and elsewhere in the UK; opportunities for service abroad.

PAY Competitive rates, reviewed regularly. Relevant experience may count towards increased starting pay. Promotion prospects.

TRAINING We encourage you to acquire new skills and experience.

QUALIFICATIONS You should have a TEC Certificate in Telecommunications, or acceptable equivalent, plus practical experience.

HOW TO APPLY For full details on this and information on our special scheme for those lacking practical experience, write now to **Robby Robinson, Recruitment Office, GCHQ, Oakley, Priors Road, Cheltenham, Glos. GL52 5AJ,**

or ring **0242-21491 ext 2269.**



NORTHWICK PARK HOSPITAL & CLINICAL RESEARCH CENTRE

Brent and Harrow Area Health Authority - Harrow District
Watford Road, Harrow, Middlesex HA1 3UJ

ELECTRONICS TECHNICIAN (MPT GRADE III)

A technician is required to service and calibrate a wide range of equipment used for medical, surgical and engineering purposes. The successful applicant will work closely with medical and other professional staff. The major part of the work involves basic maintenance and repair of the equipment.


ONC, HNC or HND or Science Degree (or three years' previous experience as a Technician Grade IV) is a necessity.

Salary: £5223-£6750 plus £527 London Weighting Allowance.

For further details and application form please contact Personnel Department, Ext. 2001.

BRENT & HARROW HEALTH AUTHORITY (855)

Professional Careers in Electronics

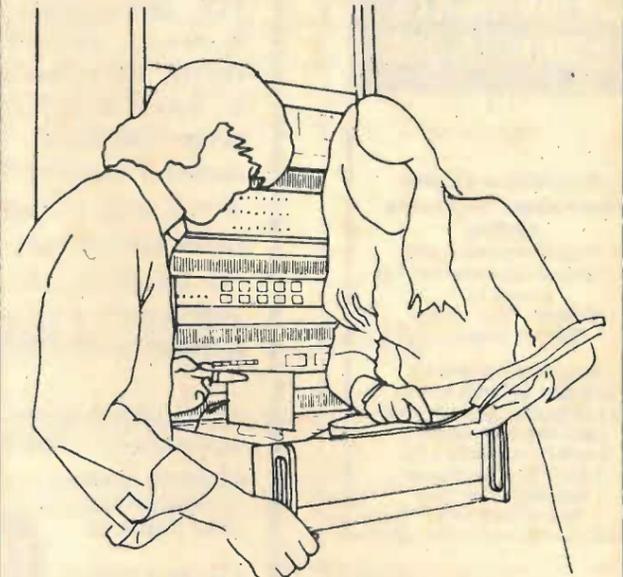

All the others are measured by us... At Marconi Instruments we ensure that the very best of innovative design is used on our range of communications test instruments and A.T.E. We have a number of interesting opportunities in our Design, Production and Service Departments and we can offer attractive salaries, productivity bonus, pension and sick pay schemes together with help over relocation. If you are interested to hear more, please fill in the following details:-

Name _____ Age _____
Address _____
Telephone Work/Home (if convenient) _____
Years of experience 0-1 1-3 3-6 Over 6

Present salary £3,500- £4,500- £5,500- over
£4,500 £5,500 £6,500 £6,500

Qualifications None C & G HNC Degree

Present job _____

Return this coupon to John Prodger, Marconi Instruments Limited, FREEPOST, St. Albans, Herts, AL4 0BR. Tel: St Albans 59292



A GEC MARCONI ELECTRONICS COMPANY (9200)

ELECTRONIC COMPUTER & MANAGEMENT APPOINTMENTS £5,000-£15,000

Use Your

Mini-Micro-Digital Hardware/Software Ability

100s of interesting and progressive opportunities at all levels in

Design - Test - Sales
Service - Support

Ring **MIKE GERNAT**
076-384 676 (24 hours)
**ELECTRONIC COMPUTER
AND MANAGEMENT
APPOINTMENTS LTD**
148/150 High Street
Barkway, Royston
Herts SG8 8EG (860)

Electronic Engineers - What you want, where you want!

TJB Electrotechnical Personnel Services is a specialised appointments service for electrical and electronic engineers. We have clients throughout the UK who urgently need technical staff at all levels from Junior Technician to Senior Management. Vacancies exist in all branches of electronics and allied disciplines - right through from design to marketing - at salary levels from around £4000 to £8000 p.a.

If you wish to make the most of your qualifications and experience and move another rung or two up the ladder we will be pleased to help you. All applications are treated in strict confidence and there is no danger of your present employer (or other companies you specify) being made aware of your application.

TJB ELECTROTECHNICAL
PERSONNEL SERVICES,
12 Mount Ephraim,
Tunbridge Wells,
Kent. TN4 8AS.



Tel: 0892 39388

Please send me a TJB Appointments Registration form:

Name

Address

(9238)

UWIST

University of Wales

DEPARTMENT OF
PHYSICS, ELECTRONICS
AND ELECTRICAL
ENGINEERING

MSc/DIPLOMA COURSE IN ELECTRONICS

Applications are invited for places in the full-time one-year MSc/Diploma course in Electronics, commencing 30 September 1981.

Further details and application forms (returnable as soon as possible) may be obtained from the Academic Registrar, UWIST, Cardiff CF1 3NU. (846)

ELECTRONIC ENGINEER

Established independent recording studio and recording company is looking for an Electronic Engineer with excellent knowledge of advanced transistor techniques and a degree of experience in the audio field.

High qualifications essential.

Phone Helen at Utopia Studios
on 01-586 3434



(846)

Radio Communications Electronics Engineers and Software Designers

Mid-Sussex - S.W. London Salaries up to £8,000

To join our expanding R&D Laboratories covering a wide range of R.F. spectrum, from L.F. to V.H.F. Equipments include transmitters and receivers for marine- and land-based use, radio nav aids and radio monitoring remote computer-controlled systems.

Electronics Engineers should have experience in transmitter or receiver design, analogue or digital circuit design, microprocessor applications. Software Designers should be experienced Programmers with an interest in control, signal processing or navigational software.

Attractive salaries are complemented by excellent prospects and generous benefits.

Contact: **David Bird, Redifon Telecommunications Limited,**
Broomhill Road, Wandsworth, London, S.W.18. Phone: 01-874
7281 (reverse charges).

(9938)

CENTRAL SERVICES DEPARTMENT OF THE SCOTTISH OFFICE WIRELESS TECHNICIANS (£5,300-£7,060)

Applications are invited for three posts of Wireless Technician in the Central Services Department of the Scottish Office. The posts are based in Inverness, Edinburgh and Montreathmont, Forfar. Candidates must hold an Ordinary National Certificate in Electronic or Electrical Engineering or a City and Guilds of London Institute Certificate in an appropriate subject or a qualification of a higher or equivalent standard and have three years' appropriate experience.

A clean current driving licence and ability to drive private and commercial vehicles are essential.

Application forms and further information are obtainable from Scottish Office Personnel Division, Room 110, 16 Waterloo Place, Edinburgh EH1 3DN (quote ref. PM(PTS) 2/13/80 (031-556 8400, Ext. 4317 or 8028).

Closing date for receipt of completed application forms is 11 February, 1981. (891)

UNIVERSITY OF PAPUA NEW GUINEA

Applications are invited for the post of **SENIOR TECHNICAL OFFICER IN THE DEPARTMENT OF HUMAN BIOLOGY**. Applicants should have a Diploma in Medical Technology or Science Laboratory Techniques or equivalent. Those with experience in the field of physiology will be given preference. A substantial part of the duties will consist of supervision and on-the-job training of junior technical staff, with emphasis on training in handling instrumentation. Salary: K14,050 p.a. (£1 sterling = K1.58). Three year contract; gratuity; rent-free accommodation; family passages; baggage allowance; leave fares after 18 months service; education allowance; salary continuation scheme for extended illness or disability.

Detailed applications (2 copies), including a curriculum vitae, a recent small photograph and naming 3 referees should be sent to the Secretary, Box 4820, University P.O., Papua New Guinea, to arrive no later than 19 December 1980. Applicants resident in U.K. should also send 1 copy to Inter-University Council, 90/91 Tottenham Court Road, London, W1P 0DT. Further details are available from either address. (801)

APPOINTMENTS IN ELECTRONICS £5 - £10,000

Take your pick of the permanent posts in:

MISSILES - MEDICAL
COMPUTERS
RADAR - COMMS
MICROPROCESSOR
HARDWARE - SOFTWARE

For free expert advice and immediate action on salary and career improvement, phone or write to **GRANT WILSON**

Technomark
Engineering and Technical Recruitment
11 Westbourne Grove
London W2. 01-229 9239 (9257)



Increased home and export orders for our broadcast TV products mean that we are looking widely to recruit staff to fill new vacancies and others created by promotion of engineers who have been with us some time.

SYSTEMS ENGINEERS - TELEVISION

Experienced engineers are needed to work on design and project management of Outside Broadcast vehicles and television studios. This is an opportunity for engineers to become involved in projects from their initial design concept, through manufacturing to delivery and installation.

Our custom built systems require a high degree of customer contact at engineering level, from the initial design stage to the necessary training of operational staff on completion of the contract, both within the UK and overseas.

You should have a knowledge of TV studio engineering gained from experience in this type of work or from experience in the operational side of television.

DESIGN AND DEVELOPMENT ENGINEERS - VIDEO

An experienced engineer who will be involved in the design of studio products, including a new range of colour cameras, using the very latest analogue and digital techniques. You will have the opportunity to see your designs made in volume production, fulfilling the high technology requirements of the '80s.

We are looking for engineers who are qualified to degree or HND level and who have at least four years' experience in the design of electronic equipment, with some knowledge of video engineering and microprocessor techniques.

TEST ENGINEERS

We require engineers at intermediate level to assist in the manufacture of our new range of products for the Broadcast studio television market.

You need to have an up-to-date knowledge of digital and linear circuit techniques gained from experience working on broadcast television, or similar sophisticated products, and be capable of faultfinding down to component level.

We are a young, successful Company, well known in international television circles, operating from our modern purpose-built factory in Andover. Salaries offered are very competitive, and supplemented by generous holidays, free life and health insurance, pension scheme, subsidised meals and relocation expenses.

PLEASE WRITE GIVING FULL DETAILS OR PHONE JEAN SMITH AT THE ADDRESS BELOW FOR AN APPLICATION FORM.

LINK
ELECTRONICS

Link Electronics Limited,
North Way, Andover,
Hants, SP10 5AJ.

Telephone: (0264) 61345

(800)

Communications Engineers and Technicians. Have you considered a career in Technical Publicity?

Our Central Publicity Department, based in the pleasant Berkshire town of Wokingham, has opportunities for Communications Engineers & Technicians (Male or Female) who wish to move into technical publicity by joining a team involved in the production of written copy for a wide range of sales literature and technical articles.

Even if you have never considered writing as a career, providing you have experience in communications, either data or radio, and an ability to express yourself clearly, we would very much like to hear from you.

Those people currently employed in telecommunications services or the electronics industry or those about to leave the HM forces would find the work varied, stimulating and creative. A

certain amount of travelling will be involved for which a generous mileage allowance is payable. Excellent prospects exist for promotion to more senior positions.

We can offer staff excellent salaries, Group pension scheme, free life assurance, five weeks' annual holiday and relocation expenses where applicable.

This is your chance to join the most successful electronics Company in the U.K. Apply in writing, or telephone, giving brief details of age, experience and qualifications to:

Manager Group Personnel Services,
Racal Group Services Ltd.,
Western Road, Bracknell, Berks
Tel: Bracknell (0344) 3244 Ext. 149

Britain's fastest growing electronics group



(B14)

ENGINEERING OPPORTUNITIES

Samuelson Sight & Sound Ltd. is a well established firm, which in the past few months has found, due to increasing business the need to take on both Video and Audio engineers.

VIDEO ENGINEERS

Well proven service background in all aspects of video, including television, television camera, video tape recorder both VHS and U-Matic formats.

Salary negotiable dependent on experience.

AUDIO ENGINEERS

Experience in all forms of audio equipment including sound mixing consoles, amplifiers, talk back systems etc. However if you have a good electronics background this would be considered.

Salary negotiable dependent on experience.

Please apply in writing, giving details of previous experience and training to:-

Mr. R.T.Morgan (Service Manager)
Samuelson Sight & Sound Ltd.
303/315 Cricklewood Broadway,
London NW2 6PQ



SALARIES UP TO £13,000

can be obtained despite the recession

CURRENT VACANCIES INCLUDE:

DESIGN ENGINEERS to work on counter measures for secure computers i.e. equip to detect interference from voice radio telex etc., up to 1.3GHz. Surrey to £13,000.

VERSATILE YOUNG ENGINEERS to join high flying design team engaged on new industrial instruments including: chart and data recorders, data acquisition and display products. Exp. low frequency instrumentation and mpu controls essential. South Coast to £10,000.

DESIGN ENGINEERS Digital video systems for security and document transmission over satellite and viewphone. Experience in digital signal processing essential. Berks to £1,000.

RF ENGINEERS & DIGITAL ENGINEERS for very advanced emergency services communication system. Berks to £10,000.

DEVELOPMENT ENGINEERS pcb's for control of mechanical peripheral equipment. Rural Cheshire to £8,000.

DEVELOPMENT ENGINEERS to work on a wide range of video cameras, video processing equipment — and sonar. South West Coast to £8,000.

PROJECT ENGINEER with drive and enthusiasm to develop analogue and digital modules for automotive industry. Rural Gloucs. c£9,000.

COMPUTER ENGINEERS Vacancies throughout U.K. in tech. support, field service, permanent site and systems test. Salaries range from exceptionally good to diabolical — but according to location and type of equipment.

WANTED URGENTLY — ANY HARDWARE OR SOFTWARE ENGINEERS, TEST ENGINEERS, SERVICE ENGINEERS, TRIALS ENGINEERS.

For further details, please contact:

Charles Airey Associates

8 Hammersmith Grove, London W6 0NA. Tel: 01-741 4011


PROBABLY THE BEST KNOWN SUPPLIER OF ELECTRONIC ENGINEERS IN THE COUNTRY

(532)

ELECTRONIC ENGINEERS



looking for a different image?

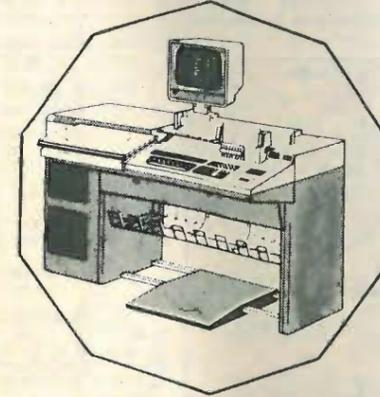

Competitive Salary + Car

In the field of Electronics, few areas offer such growth opportunities as that of Computing. Philips Data Systems is a division of Philips Business Systems, the pacesetter group that manufactures and markets one of the widest ranges of advanced business systems and equipment. We are looking throughout the UK for **Customer Engineers**, male or female, who wish to be part of that growth.

If you are experienced in dealing with customers' problems, skilled in electronics/electro-mechanics, then Philips will provide you with the training necessary to enter this technically exciting and challenging field.

We offer excellent conditions of employment, a competitive initial salary, which will be reviewed on completion of your first 6 months training period. Naturally, a company vehicle will be provided.

If you believe you have the ability/experience needed to take on this image, then why not telephone Alan Bowden, Senior Personnel Officer, on 0206 5115 or write to him at Philips Data Systems, Elektra House, 2 Bergholt Road, Colchester, Essex CO4 5BE.



Business Systems

Simply years ahead

PHILIPS

(809)

JUNIOR DEVELOPMENT ENGINEERS ELECTRONICS

John Player and Sons, a leading manufacturer of tobacco products, offer the opportunity to young electronics engineers to gain valuable practical experience in industrial electronics.

Vacancies exist for work in the Machinery Evaluation Section where new generation cigarette making and packing machines are undergoing pre-production trials. These machines are equipped with increasing numbers of modern electronic control circuits using the latest technological advances including microprocessors.

The successful applicants will undergo a period of familiarisation, look after specific machines during the evaluation period, be involved in the development of special features as well as devising evaluation aids and ultimately in the training of others in the maintenance of these machines on the production floor.

We are looking for men or women who are qualified to HNC or equivalent, and who have two years' experience in one or more of the following areas:

- a) electronic control and logic circuits
- b) process control systems
- c) microprocessors

A knowledge of the tobacco industry is not essential.

We offer a starting salary of £6,500 per annum together with other benefits associated with a large progressive company including relocation assistance where applicable.

Application forms can be obtained by telephoning Nottingham (STD 0602) 787711, Extension 345 or writing to:

Lorna Blayney

JOHN PLAYER & SONS

NOTTINGHAM NG7 5PY

(790)

ELECTRONICS ENGINEER

CENTRAL SCOTLAND

A vacancy exists in our engineering design and development department for an Electronics Engineer. Applicants should be qualified to HNC level or have the depth of industrial experience and ability to work on new designs with the minimum of supervision.

Apply for application form to:

Administration Manager
GR INTERNATIONAL ELECTRONICS LTD.
Inverlorn Industrial Estate, Perth PH1 3NY
Telephone: Perth 34771

(796)

When the ship comes home, why not settle down?

We're British Telecom Maritime Service and we have everything in a job that you'd want: the kind of work you're trained to do, good pay, job security and all the comforts of home where they really count — at home!

Radio Officers

Vacancies exist at several coast stations for qualified Radio Officers to carry out a variety of duties that range from Morse and teleprinter operating to traffic circulation and radio telephone operating. And for those with ambition, the prospects of promotion to senior management are excellent.

You must have a United Kingdom Maritime Radio Communication Operator's General Certificate or First Class Certificate of proficiency in Radio-telegraphy or an equivalent certificate issued by a Commonwealth Administration or the Irish Republic. Preferably you should have some sea-going experience.

The starting pay at 25 or over will be about £5,381; after 3 years service this figure rises to around £7,087. (If you are between 19 and 24 your pay on entry will vary between approximately £4,229 and £4,937). Overtime is additional, and there is a

good pension scheme, sick-pay benefits and at least 4 weeks' holiday a year.

For further information, please telephone Kathleen Watson on Freefone 2281 or write to her at the following address: IE Maritime Radio Services Division (WWA), IS8.1.1.2, Room 304, Landsec House, 23 New Fetter Lane, London EC4A 1AE.

British
TELECOM
PART OF THE POST OFFICE

(524)

ELECTROSONIC

PROJECTS DIVISION

The Projects Division of Electrosonic wish to recruit an experienced

PROJECT ENGINEER/MANAGER

to be responsible for a wide range of projects, both at home and abroad. The projects will include industrial and commercial dimming, TV and theatrical lighting, hotel and conference centre low voltage systems, audio and audio visual systems. The Company manufactures a wide range of lighting, audio and audio visual products, and has extensive manufacturing facilities capable of handling virtually every stage of the production for both standard and special products in-house. The successful applicant will probably be qualified to HND or Degree Level and will have experience in one or more of the above fields, but of more importance, is his or her drive and ability to take a project from the drawing board to final completion on site. The salary offered will depend upon experience, but will be in the range of £7,000 to £9,000 p.a. Other fringe benefits will include the use of a company car and overseas allowances.



Applicants should write giving a brief C.V. to: R. L. C. Stinton, C.Eng., M.I.E.E. Divisional Manager, Projects Division

ELECTROSONIC LTD.

815 Woolwich Road, London SE7 8LT. Phone: 01-855 1101

(899)

TEST AND COMMISSIONING ENGINEERS. We urgently require engineers to work on our latest range of Numerically Controlled Machine Tools. Suitable applicants should be fully conversant with T.T.L. and CMOS Logic and have had some experience with Micro Processors. Salary, Attendance Bonus, Sick Pay and Subsidised Canteen. For details and application form, contact Brian Warner, Toolmasters Controls Ltd., Perimeter Road, Woodley, Reading, Berks. Telephone: 0734-691918. (857)

POST SOUGHT. Radio comms/electronics tech (CEI) insert, excellent track record, 15 years UK, Africa, Middle East. Oil, military, civil — SSB/FM to 1 GHz, digital, process control, maintenance, commissioning, engineering, circuit design/mods, cal, operations, sales. Now managing telecomms facility in UAE, amateur radio country preferred, UK considered — based near London, 33 years, married, available February '81. — W.W., Box 873. (873)

TESTERS, TEST TECHNICIANS, TEST ENGINEERS. Earn what you're really worth in London working for a World Leader in Radio & Telecommunications. Phone Len Porter on 01-874 7281, or write: REDIFON TELECOMMUNICATIONS Ltd., Broomhill Road, Wandsworth, London, SW18. (9856)

ARTICLES FOR SALE

THINKING OF RENTING A TELEPHONE ANSWERING MACHINE? THEN STOP!

Did you know that for the equivalent of just one year's rental you could actually buy one outright?

For details write to: Javal Supplies Ltd. (Dept. 2C), 120 Alexandra Road, Burton-on-Trent, Staffs DE16 0JB or telephone (0283) 47427 any time. (337)

BRAND NEW Vero packs 19in x 5.2in, complete with 5 "D" range cannon connectors on back panel, guides for 21 cards, and fully stabilised +5 volt, 3 amp power supply. Complete unit £22, rack only £15, power supply only £10. VAT and 15 per cent extra. P&P £5 per unit. — Tel: (Rushmore Electronics Ltd) 0252 515373. (868)

LAB CLEARANCE: Signal Generators; Bridges; Waveform, transistor analysers; calibrators; standards; millivoltmeters; dynamometers; KW meters; oscilloscopes; recorders; Thermal, sweep, low distortion true RMS, audio FR, deviation. Tel. 040-376236. (8250)

ARTICLES FOR SALE

TOWERS' INTERNATIONAL MICROPROCESSOR SELECTOR

by T. D. Towers Price: **£15.70**
THE CP/M H/B WITH MP/M by R. Zaks Price: **£9.50**
YOUR FIRST COMPUTER by R. Zaks Price: **£6.40**

OPTICAL FIBRE COMMUNICATION SYSTEMS by C. P. Sandbank Price: **£18.60**
THE ACTIVE FILTER H/B by F. P. Tedeschi Price: **£4.85**
INFORMATION TRANSMISSION MODULATION, & NOISE by M. Schwartz Price: **£8.00**

OPERATIONAL AMPLIFIERS by B. G. Clayton Price: **£11.70**

DESIGN OF TRANSISTOR CIRCUITS WITH EXPERIMENTS by Dr. K. A. Pullen Jr. Price: **£9.15**

DIGITAL ELECTRONICS FUNDAMENTAL CONCEPTS & APPL. by C. E. Strangio Price: **£17.30**
RADIO & TELEVISION SERVICING 1979/80 MODELS by R. N. Wainwright Price: **£16.50**

★ PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.

Specialist in Scientific & Technical Books

19-21 PRAED STREET LONDON W2 1NP

Phone 402-9176

Closed Sat. 1 p.m. (8974)

Quartz Crystal Units
ACCURATE RELIABLE
Private enquiries, send 3p in stamps for brochure
THE QUARTZ CRYSTAL CO. LTD.
Q.C.C. WORKS, WELLINGTON CRESCENT, NEW MALDEN, SURREY. 01-942 0334 & 2982 (8493)

ARTICLES FOR SALE

TO MANUFACTURERS, WHOLESALERS & BULK BUYERS ONLY

Large quantities of Radio, T.V. and Electronic Components.
RESISTORS CARBON & C/F 1/8, 1/4, 1/2, 1. Watt from 1 ohm to 10 meg.
RESISTORS WIREWOUND. 1 1/2, 2, 3, 5, 10, 14, 25 Watt.
CAPACITORS. Silver mica, Polystyrene, Polyester, Disc Ceramics, Metalamite, C280, etc.
Convergence Pots, Slider Pots, Electrolytic condensers, Can Types, Axial, Radial, etc.
Transformers, chokes, hopts, tuners, speakers, cables, screened wires connecting wires, screws, nuts, transistors, ICs, Diodes, etc., etc.
All at Knockout prices. Come and pay us a visit. Telephone 445 2713, 445 0749.

BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, N. Finchley, London, N.12. 5 mins. from Tally Ho Corner (9461)

BUILD YOUR OWN LASERS. Full plans and instructions on how to construct three fully working lasers: Pulsed dye, Argon and Helium — neon, at a fraction of the cost of a commercially produced device. All parts available. Send £4.95 plus 25p P&P to A. V. Services, 10 Agcroft Road West, Prestwich, Manchester M25 8RL. Also Laser Scanning Systems. Send for literature. (647)

RACAL MA-259-G secondary frequency standard. New with test certificate. £595. — Nottingham 0602-397446 evenings. (703)

TEKTRONIX OSCILLOSCOPES in lptop condition, re-calibrated with handbooks 535A £135, 545B £180, CA £60, 1A2 £120. All prices inclusive, no extras. Bournemouth (0202) 291481. (854)

SERVICE MANUAL LIBRARY for sale. TV, Radio etc. Sensible offers considered. S.S. Radio Service, 726 Eastern Avenue, Ilford, Essex IG2 6PE. 01-554 9650. (858)

MAINS REGULATORS working on solid state triac controlled auto-transformer principle. 2KVA. Manufactured by Topaz Electronics. Brand new. 47 to 63 Hz. Mains voltage regulation range ± 7%. Load regulation less than 1% for full load. Response time 1 cycle. Less than 1% total harmonic distortion. £120. Tel. 01-200 7111 (Mr P. Irani). (856)

MARCONI SIGDEN TF 1060/3 470-950 MHTZ AM FM £300. Farnell digital measuring system plug in units £40. Advance standard of's 1 £40. Evenings 0822 85. (853)

CALIBRATOR, Bradley 156, good condition, calibrated, £200. — Phone M. Finch, 01-897 3759 (West Drayton). (875)

BARGAIN MEMORIES, SN7489 fast buffer 'scratch pad', £1.75 each, £8/5, £14/10. Full data 25p. — Computer Components, 1 Conifer Drive, Camberley, Surrey. (877)

PRINTED CIRCUITS. Make your own simply, cheaply and quickly: Golden Fotolok Light Sensitive Lacquer — now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibre-glass Board approx. 1mm thick £1.75 sq. ft. Post/Packing 60. — White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall. (714)

ENCAPSULATING, coils, transformers, components, degassing, silicone rubber, resin, epoxy. Lost wax casting for brass, bronze, silver, etc. Impregnating coils, transformers, components. Vacuum equipment low cost, used and new. Also for CRT regunning met alising. Research & Development. Barratts, Mayo Road, Croydon, CR0 2QP. 01-684 9917. (9678)

THE SCIENTIFIC WIRE COMPANY

P.O. Box 30, London, E.4

| ENAMELLED COPPER WIRE | | | | |
|-----------------------|-------|------|------|------|
| SWG | 1lb. | 8oz. | 4oz. | 2oz. |
| 8 to 29 | 2.76 | 1.50 | .80 | .60 |
| 30 to 34 | 3.20 | 1.80 | .90 | .70 |
| 35 to 40 | 3.40 | 2.00 | 1.10 | .80 |
| 41 to 43 | 4.75 | 2.60 | 2.00 | 1.42 |
| 47 | 8.37 | 5.32 | 3.19 | 2.50 |
| 48 to 49 | 15.96 | 9.58 | 6.38 | 3.69 |

| SILVER PLATED COPPER WIRE | | | | |
|---------------------------|------|------|------|------|
| 14 to 30 | 6.50 | 3.75 | 2.20 | 1.40 |

| TINNED COPPER WIRE | | | | |
|--------------------|------|------|------|-----|
| 14 to 30 | 3.38 | 2.36 | 1.34 | .90 |

Prices include P&P, VAT and Wire Data SAE for list. Dealer enquiries welcome. Reg Office: 22 Coningsby Gardens. (9063)

TIME EXACT?

MSE CLOCK is ALWAYS CORRECT — never gains or loses, self setting at switch-on, 8 digits show Date, Hours, Minutes and Seconds, larger digit Hours and Minutes for easy QUICK-GLANCE time, auto GMT/BST and leap year, also parallel BCD output and audio to record and show time on playback, receives Rugby 60KHz atomic time signals, built-in antenna, 1000Km range, £54.80. V.L.F. 7 10-150KHz Receiver £13.70. 60KHz RUGBY RECEIVER, as in MSF Clock, serial data output, £15.70. Each fun-to-build kit includes all parts, printed circuit, case, postage etc. Money back assurance so GET one NOW.

CAMBRIDGE KITS, 45 (WN) Old School Lane, Milton, Cambridge

INVERTERS

High quality DC-AC. Also "no break" (2ms) static switch, 19" rack. Auto Charger.



COMPUTER POWER SYSTEMS

Interport Mains-Store Ltd. POB 51, London W11 3BZ Tel: 01-727 7042 or 0225 310916 (9101)

BUILDING RAMS?

Why waste time hand-wiring RAMS? This 5.3 x 2.5 inch professional plated PCB mounts on your prototyping board, looking like an 8K byte TTL compatible static RAM. 13 address lines, 8 data I/O, write enable, 2 neg and 1 positive card selects.

Assembled with sockets, pins and caps, just plug in 16 2114's and 1 74LS138 £21. Bare board £15, no VAT, post paid.

Ibix Electronic Design 56H Norris Hill Drive Heaton Norris Stockport, Cheshire (850)

ARTICLES FOR SALE

TELETEXT, TV SPARES & TEST EQUIPMENT. TELETEXT. Latest MK2 external unit kit incl. Mullard Decoder 6101VML and infra-red remote control £258, p/p £2.50 (further details on request). Also MK1 external unit kit incl. Texas XM11 decoder, special offer price £188, p/p £2.50. Both kits incl. UHF modulator, and plug into TV set aerial socket. SPECIAL OFFER TEXAS XM11 Decoder, new and tested, limited quantity at a price, £65, p/p £1.40. Stab. power supply (5v) for Teletext decoders, £5.80, p/p £1. Thorn design XM11 interface unit, £1.80, p/p 80p. NEW SAW FILTER IF AMP PLUS TUNER (complete & tested for sound & vision), £28.50, p/p £1. COLOUR BAR & CROSS HATCH GENERATOR KIT (MK4) PAL, UHF aerial input type, 8 vertical colour bars, R-Y, B-Y, grey scale, etc. P/B controls £35. Batt holders £1.50 or stab. mains power supply kit £4.80. Deluxe case £5.20 or alum. case £2.90, p/p £1.40. Built & tested in De-luxe case (battery) £58, p/p £1.50. CROSS HATCH KIT UHF aerial input type also gives peak white & black levels, batt. op. £11, p/p 45p. Add-on GREY SCALE KIT £2.90, p/p 35p. De-luxe case £5.20. UHF SIGNAL STRENGTH METER KIT £17.50. Alum. case £1.80. De-luxe case £5.20, p/p £1.40. CRT TEST & REACTIVATOR KIT for colour & mono £22.80, p/p £1.70. THORN 9000 Touch Tune Remote control receiver unit plus transmitter handset £18, p/p £1.40. THORN 9000 Fascia incl. channel select. indicator, set controls, speaker, £5.80, p/p £1.60. TV SOUND IF TRANSTD. Tested, £8.80, p/p 85p. BUSH SURPLUS IF PANELS. A816 £1.80, TV312 (single I.C.) £5, 2718/BC6100 £5, A823 (Exp) £2.80, p/p 85p. BUSH 2718/BC6100 Line Time Base Panel Z904, incl. LOPT, EHT stick, Focus, etc., 18in or 22in, £15, p/p £1.60. BUSH 161 series TB panel A634 £3.80, p/p £1.20. DECCA colour TV Thyristor Power supply £3.80, p/p £1.40. GEC 2010 series TB panel £1, p/p 90p. GEC 2040 CDA panel £4.50, p/p £1.20. PHILIPS G6 S/S conv. panel £2.50, p/p £1.20. G8 Decoder panels for spares £1.80, p/p £1.20. G9 Signal panels for small spares £3.80, p/p £1.20. THORN 3500 Line TB panel £5, p/p £1. 3000 ex-external panels IF, VIDEO, DECODER, £5, p/p £1.20. 8000/8500 TB salvs/spares £4.80, p/p £1. 9000 Line TB (incl. LOPT) salvs/spares £7.50, p/p £1.60. COLOUR SCAN COILS (Mullard or Plessey) £6, p/p £1.80. Yoke £2.50, p/p £1. Blue Lat 75p, p/p 35p. Mono Scan Coils (Thorn, Philips, Pye) £2.80, p/p £1. VARICAP UHF TUNERS. Mullard U321 £7.80, ELC1043/05 £5.50. G.I. £3.50. Salv. (asstd) £1.50, p/p 45p. Varicap UHF/VHF ELC2000S £8.50. Bush (dual) £7.50, p/p 70p. TOUCH TUNE CONTROL units, Bush (6 pos) £4.50, p/p 80p. VARICAP CONTROL UNITS 3 pos. £1.20, 4 pos. £1.50, 5 pos. £1.80, 6 pos. £1.80, 6 pos. special offer £1, p/p 45p. UHF transtd. Tuners (rotary) incl. s/m drive £2.50, 4 pos. P/B £2.50, 6 pos. P/B £4.20, p/p £1.20. (Special types available, details on request). DL50 Delay Line £2.50, p/p 50p. Large selection of LOPTS, Triplers, Mains Droppers, and other spares for popular makes of colour & mono receivers. PLEASE ADD 15% VAT TO ALL PRICES. — MANOR SUPPLIES, 172 WEST END LANE, WEST HAMPSHIRE, LONDON, N.W.6. SHOP PREMISES. Tel. 01-794 8751. Easily accessible W. Hampstead Jubilee Tube & Brit. Rail N. London (Richmond-Broad St.) and St. Pancras-Bedford. Buses 28, 159, 2, 13. Callers welcome. Thousands of additional items not normally advertised available at shop premises. Open daily all week incl. Saturday (Thursday half day). MAIL ORDER: 64 GOLDERS MANOR DRIVE, LONDON NW11 9HT. PLEASE ADD 15% VAT to all prices. (60)

MINIATURE COAXIAL CABLE SOLDER IRON resistant dielectric and sheath 50 ohm £1.15, 75 ohm £1.75 per metre including P&P and VAT — Selbac, 65 Penrhyn Avenue, Litherland, Liverpool 21. (836)

OVER 600 ARCOLECTRIC SWITCHES and Bulgin panel lampholders for disposal. Offers invited. — Details: Weston-Super-Mare (0934) 417565. (835)

TEKTRONIX 546 oscilloscope complete with 1 A4, four beam plug in very good condition, £250 ono. — Phone 0302 742054. (837)

TEKTRONIX 535A + CA, brand new tube, recalibrated, probes, manuals and trolley. Buyer collects at £250. — 0603-20142 day time, 0603-28978 evenings. (834)

LAB CLEARANCE: Signal Generators; Bridges; Waveform, transistor analysers; calibrators; standards; millivoltmeters; dynamometers; KW meters; oscilloscopes; recorders; Thermal, sweep, low distortion true RMS, audio FR, deviation. Tel. 040-376236. (8250)

RADIO TELEPHONE system — VHF band, Marconi base RC1010 with remote control and talk-through (demo model) £1,600, new. Two Marconi RC625 Messenger mobiles £400 each. New KEE 2.5 watt handportable £450. — Phone 031 554 2591, Alexian Electronics Ltd, Edinburgh. (867)

CLEARANCE PARCELS: Transistors, resistors, boards, hardware, 10lbs only £5.80! 1,000 Resistors £4.25, 500 Capacitors £3.75. BC 108, BC 171, BC 204, BC 230, 2N 5061, CV7497 Transistors, 10-70p, 100-£5.80, 2N 3055, 10 for £3.50. S.a.e. lists: W.V.E. (3), 15 High Street, Lydney, Glos. (444)

SMALL BATCH PCB's produced from your artwork. Also DIALS, PANELS, LABELS. Camera work undertaken. FAST TURNAROUND. — Details: Winston Promotions, 9 Hatton Place, London EC1N 8RV. Tel. 01-405 4127/0960. (8794)

P.C.B. PROTOTYPE and small batch production. Design layout, assembly and testing. Fast, reliable service. Wye Valley Electronics, 15 High St, Lydney, Glos. Tel: Dean (0594) 41267. (865)

SHEET METAL WORK, fine or general front panels chassis, covers, boxes, prototypes. 1 off or batch work, fast turnaround. 01-449 2695. M. Gear Ltd., 179A Victoria Road, New Barnet, Herts. (812)

ELECTRONIC DESIGN SERVICES. MICROPROCESSOR HARDWARE and SOFTWARE design facilities have now been added to our established expertise and comprehensive test facilities previously available to you for ANALOGUE and COMMUNICATIONS designs. — For fastest results please phone Mr. Anderson, Andersons Ltd, Ridgeway, Hog's Back, Seale (nr. Farnham), Surrey. 02518-2639. (275)

COMPLETE ELECTRONIC SERVICES. Industrial and Audio Electronics, services include: Design and development, PCB design, prototype and batch production and assembly facilities. Consultancy and systems installation. RLW Developments, 833 London Road, Trent Vale, Stoke-on-Trent ST4 5NZ. Tel. (0782) 45907. (851)

EXACT TIME?

MSF CLOCK is ALWAYS CORRECT — never gains or loses, self-setting at switch-on, 8 digits show Date, Hours, Minutes and Seconds, larger digit hours and minutes for easy QUICK-GLANCE time, auto GMT/BST and Leap Year, also parallel BCD output and audio to record and show time on playback, receives Rugby 60KHz atomic time signals, built-in antenna, 1000Km range, ACCURACY £54.80. V.L.F. 7 10-150KHz Receiver £13.70. 60KHz RUGBY RECEIVER, as in MSF Clock, serial data output, £15.70. Each fun-to-build kit includes all parts, printed circuit, case, postage etc. Money-back assurance so GET one NOW.

CAMBRIDGE KITS, 45 (WM) Old School Lane, Milton, Cambridge (803)

PERSONAL

INFORMATION WANTED

Seeking information to re-establish contact with old friend Maurice V. Bradley, ex London, U.K., and Toronto, Canada. Last heard was U.K./Germany, servicing computers. Please write: C. Henry, 202 Lakeshore Road, Pointe Claire, Quebec, Canada. (864)

BOOKS

CB WORLD. The big one. Published by IPC end of November. Available from all usual newsgroups and bookshops 60p. Don't miss it. Insist on it. Be first, order it before it sells out. (786)

PULSE INDUCTION MADE EASY. The D.I.Y. constructor's dream. Complete information circuit diagrams waveforms component layout £2. Please to Robert Crone, 39 Woodlands Drive, Drumpeller, Coatbridge ML5 1LB Scotland. (859)

EX GOVT tape recorders, Ferrograph, Vortexion, etc. S.a.e. details. A. E. Wright, Sunningdale, Broadheath, Worcester. (885)

SERVICES

CIRCOLEC

THE COMPLETE ELECTRONIC MANUFACTURING SERVICE

Let us realise all or any part of your project from prototypes to production, from artwork design and component sourcing, through assembly and test to final quality assurance, packing and delivery. We also provide a test, repair and modification service to suit your individual requirement.

For competitive prices and fast turnaround contact:

CIRCOLEC, 1 Franciscan Road, Tooting, S.W.17

Telephone: 01-767 1233 (544)

PRINTED CIRCUIT MANUFACTURE. Very fast, reliable service. Lowest prices. Prototypes welcome. Inhouse photography. Phone 06474-573 for instant quote or write to AKTRONICS Ltd., 42/44 Ford Street, Moretonhampstead, Devon. (9857)

SMALL BATCH PCB's produced from your artwork. Also DIALS, PANELS, LABELS. Camera work undertaken. FAST TURNAROUND. — Details: Winston Promotions, 9 Hatton Place, London EC1N 8RV. Tel. 01-405 4127/0960. (8794)

P.C.B. PROTOTYPE and small batch production. Design layout, assembly and testing. Fast, reliable service. Wye Valley Electronics, 15 High St, Lydney, Glos. Tel: Dean (0594) 41267. (865)

SHEET METAL WORK, fine or general front panels chassis, covers, boxes, prototypes. 1 off or batch work, fast turnaround. 01-449 2695. M. Gear Ltd., 179A Victoria Road, New Barnet, Herts. (812)

ELECTRONIC DESIGN SERVICES. MICROPROCESSOR HARDWARE and SOFTWARE design facilities have now been added to our established expertise and comprehensive test facilities previously available to you for ANALOGUE and COMMUNICATIONS designs. — For fastest results please phone Mr. Anderson, Andersons Ltd, Ridgeway, Hog's Back, Seale (nr. Farnham), Surrey. 02518-2639. (275)

COMPLETE ELECTRONIC SERVICES. Industrial and Audio Electronics, services include: Design and development, PCB design, prototype and batch production and assembly facilities. Consultancy and systems installation. RLW Developments, 833 London Road, Trent Vale, Stoke-on-Trent ST4 5NZ. Tel. (0782) 45907. (851)

ARTICLES WANTED

TO ALL MANUFACTURERS AND WHOLESALERS IN THE ELECTRONIC RADIO AND TV FIELD

BROADFIELDS & MAYCO DISPOSALS

will pay you top prices for any large stocks of surplus or redundant components which you may wish to clear. We will call anywhere in the United Kingdom.

21 LODGE LANE NORTH FINCHLEY, LONDON N12 8JG Telephone Nos. 01-445 0749/445 2713 After office hours 958 7624 (9123)

STORAGE SPACE is expensive, why store redundant and obsolete equipment? For fast and efficient clearance of all test gear, power supplies, PC boards, components, etc., regardless of condition or quantities. Call 01-771 9413. (8209)

COURSES

SPECIALISED TUITION on microprocessors for design engineers to suit individual applications. — Call 01-452 8780 after 6.30 pm. (847)

EURO CIRCUITS

Printed Circuit Boards — Master layouts — Photography — Legend printing — Roller tinning — Gold plating — Flexible films — Conventional fibre glass — No order too large or too small — Fast turnaround on prototypes. All or part service available NOW. (9630)

EURO CIRCUITS LTD. Highfield House West Kingsdown Nr. Sevenoaks, Kent. WK2344

ALTRONIC SYSTEMS LTD. Alarm systems designed and manufactured to your requirements. Free estimates under no obligation. — Tel Ansafone 07073 30514. (715)


DESIGN AND DEVELOPMENT. ANALOGUE, DIGITAL, RF AND MICROWAVE CIRCUIT AND SYSTEM DESIGN. Also PCB design, mechanical design and prototype/small batch production. — Adenmore Limited, Unit 103 Liscombe, Bracknell, Berks. Tel: Bracknell 52023. (656)

DESIGN SERVICE. Electronic Design Development and Production Service available in Digital and Analogue Instruments, RF Transmitters and Receivers for control of any function at any range. Telemetry, Video Transmitters and Monitors, Motorised Pan

Secondhand Terminals Stock Clearance

ITEL Model 1051

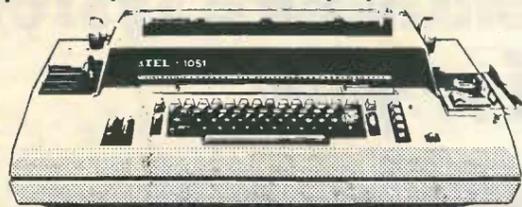IBM SELECTRIC (Golfball) typewriter with optical tape reader and tape punch in



compact desk-top unit with RS232 serial interface. EBCDIC coded. Reduced from £375 to £295. Also available a *limited number only* of machines untested, except for typewriter operation, at £195.

- *DI/AN Model 9030 Desk-top terminal similar to DECwriter LA36. Upper/lower case matrix printer, up to 300 Baud. Features switchable Baud rate, parity, keyboard and duplex options. Reduced from £225. **£190**
- *DATA DYNAMICS Model KSR 33 Teletype with keyboard and printer for 110 Baud operation. RS232 interface. In excellent condition. Reduced from £175. **£150**
- *DATA DYNAMICS Models ASR 33 and ASR 390 terminals with paper tape reader/punch also available from **£195**

VAT and carriage extra on all items

COMPUTER APPRECIATION 86 High Street, Bletchingley, Redhill, Surrey, RH1 4PA Godstone (0883) 843221

INDEX TO ADVERTISERS JANUARY

Appointments Vacant Advertisements appear on pages 122-134

| PAGE | PAGE | PAGE |
|---|--|--|
| Acoustical Mfg 66 | G.P. Industrial Elec Ltd 24 | Quantum 108 |
| Ambit International 4 | Guide to Broadcasting Stations 22 | |
| Anders Electronics Ltd 92 | | |
| Anglia Components 24 | Hall Electric 5 | Radio Components Specialists 111 |
| A.P. Products 30 | Happy Memories 88 | Radio Shack 90 |
| Aspen Electronics Ltd 14 | Harris Electronics (London) Ltd 20 | Rank Radio 11 |
| Audio Electronics 29 | Harrison Brothers 90 | R.C.S. Electronics 114 |
| Audix BB 10 | Hart Electronics 93 | Rediffusion Reditronics 25 |
| Austerfield Clark 29 | Henry's Radio 107, 110, 112 | |
| Avo Inst cover ii | Hi-Fi Y/Book 90 | |
| | | |
| Barkway Electronics Ltd 112 | ILP Electronics Ltd 86, 87 | Safgan Electronics 100 |
| Barrie Electronics Ltd 103, 109 | ILP Transformers Ltd 106 | Sagin 96 |
| Bayliss, A. D. 28 | Integrex Ltd 76 | Sandwell Plant 92 |
| BDS Micro Systems Ltd 100 | Interface Quartz 28 | Science of Cambridge 6, 7 |
| BIB Hi-Fi cover iv | | Scopex Instruments Ltd 130 |
| Bi-Pak 105 | Keithley Inst 85 | Service Trading 121 |
| | Kelsey Acoustics 96 | Shure Electronics 65 |
| Calcon 27 | Kirkham Amplifier 16 | Sinclair Elec 120 |
| Cambridge Learning 27 | Langrex 92 | Sonic Sound 26 |
| Carston Electronics Ltd 18, 19, 23 | Lascar 100 | Southern Elec 114 |
| CB World 92 | Levell 3 | Special Products Ltd 27 |
| Catronics 110 | Lowe 102 | Strutt Electrical & MSH Ltd 88, 96 |
| Chiltern 89 | Lyon Instruments 28 | Surrey Electronics Ltd 103 |
| Chiltmead Ltd 115 | | Swanley Electronics Ltd 103 |
| Cintec 13 | Maclin-Zand Elec. Ltd 9 | |
| Clark Masts Ltd 23 | Maplin Electronic Supplies cover iii | |
| Colomor 109 | Marshall A. (London) Ltd 106 | |
| Computer Appreciation 136 | Martin Associates 17 | Technomatic 104 |
| Continental Specialities 11, 25, 29 | Microcircuits Ltd 21 | Tempus 98 |
| Crimson Elektrik 14 | Microsystems 91 | Time Elec 114 |
| | Mills, W. 112 | |
| Display Electronics 20 | Milward, G. F. 108 | |
| Doram Elec 25 | Minim Audio 106 | Valradio Ltd 24 |
| | MTL 108 | |
| Edicron 12 | Multicore Solders Ltd cover iv | |
| Elector 89 | Mura Electronics 12 | |
| Electronic Brokers Ltd 101, 103, 116, 117, 118, 119 | | Newtronics (H.L. Audio) 8 |
| Electronic Equipment 108 | | OMB Electronics 11 |
| Electro-Tech Comps Ltd 88 | | Orion 29 |
| Electrovalue 101 | | P.B.R.A. Ltd 28 |
| Eraser 135 | | P.M. Components 26 |
| | | Powertran Electronics 95, 97, 99 |
| Faircrest Eng 92 | | Pype Hayes 96 |
| Ferranti 10 | | |
| Fyde 96 | | |

OVERSEAS ADVERTISEMENT AGENTS:
France & Belgium: Norbert Hellin, 50 Rue de Chemin Veat, F-9100, Boulogne, Paris.

Hungary: Mrs Edit, Bajusz, Hungexpo Advertising Agency, Budapest XIV, Varosliget. Telephone: 225 008 — Telex: Budapest 22-4525 INTFOIRE

Italy: Sig C. Epis, Etas-Kompass, S.p.a. — Servizio Estero, Via Mantegna 6, 20154 Milan. Telephone: 347051 — Telex: 37342 Kompass.

Japan: Mr. Inatsuki, Trade Media — IBPA (Japan), B.212, Azabu Heights, 1-5-10 Roppongi, Minato-ku, Tokyo 106. Telephone: (03) 585 0581.


United States of America: Ray Barnes, IPC Business Press, 205 East 42nd Street, New York, NY 10017 — Telephone: (212) 867-2080. Telex: 238327.

Mr Jack Farley Jr., The Farley Co., Suite 1584, 35 East Wacker Drive, Chicago, Illinois 60601 — Telephone: (312) 63074.

Mr Victor A. Jauch, Elmatex International, P.O. Box 34607, Los Angeles, Calif. 90034, USA — Telephone (213) 821-8581 — Telex: 18-1059.

Mr Jack Mentel, The Farley Co., Suite 650, Ranna Building, Cleveland, Ohio 44115 — Telephone: (216) 621 1919.
 Mr Ray Rickles, Ray Rickles & Co., P.O. Box 2028, Miami Beach, Florida 33140 — Telephone (305) 532 7301.
 Mr Tim Parks, Ray Rickles & Co., 3116 Maple Drive N.E., Atlanta, Georgia 30305. Telephone: (404) 237 7432.
 Mike Loughlin, IPC Business Press, 15055 Memorial Ste 119, Houston, Texas 77079 — Telephone (713) 783 8673.

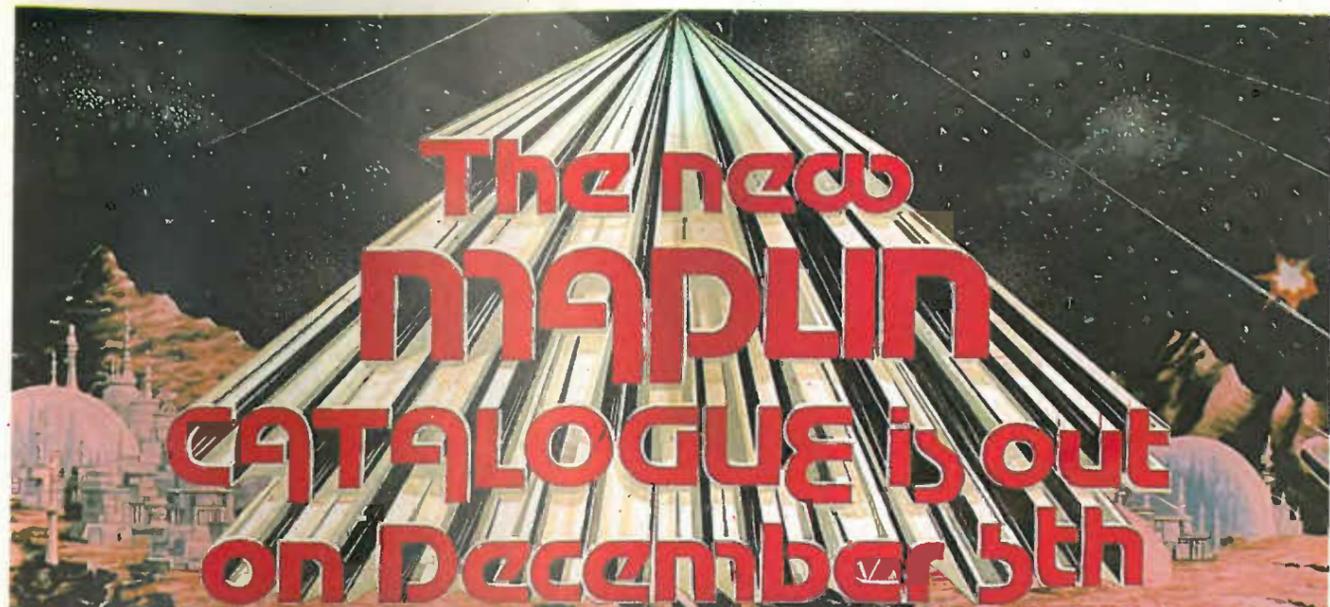Canada: Mr Colin H. MacCulloch, International Advertising Consultants Ltd., 915 Carlton Tower, 2 Carlton Street, Toronto 2 — Telephone (416) 364 2269.
 *Also subscription agents.



A massive new catalogue from Maplin that's bigger and better than ever before. If you ever buy electronic components this is the one catalogue you must not be without. Over 300 pages, it's a comprehensive guide to electronic components with thousands of photographs and illustrations and page after page of invaluable data. We stock just about every useful component you can think of. In fact, well over 5000 different lines, many of them hard to get from anywhere else. Hundreds and hundreds of fascinating new lines, more data, more pictures and a new layout to help you find things more quickly.



Maplin Electronic Supplies Ltd.
 All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR.
 Telephone: Southend (0702) 554155. Sales (0702) 552911.
 Shops:
 159-161 King Street, Hammersmith, London W6. Telephone: (01) 748 0926.
 284 London Road, Westcliff-on-Sea, Essex. Telephone: Southend (0702) 554000.
 Both shops closed Mondays.

On sale in all branches of W H Smith from Dec 5th price £1

PLUS LOW PRICES such as
 Resistors from 1p
 Multimeters from £4.25
 Ni-Cads from £1.15
 Stereo Headphones from £3.49
 Radios from £2.95
 Over 300 Books
 21 Different ranges of capacitors, etc., etc., etc.



Post this coupon now for your copy of our 1981 catalogue price £1.
 Please send me a copy of your 320 page catalogue. I enclose £1 (Plus 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the UK send £1.68 or 12 International Reply Coupons.
 I enclose £1.25
 Name _____
 Address _____



The biggest name in solder worldwide

Products that help you make a better job of it.




Arax Multicore Solder.
Economy pack for general non-electrical use. Replaces solid wire and stick solder. (B.S. 219 Grade L). Econopak 200g reel of 3mm dia. Size 16A. £4.14 per reel.



Handy Dispensers

| Product | Description | Per pack |
|---------|--|----------|
| PC115 | for printed circuits. | £1.15 |
| SV130 | for radio and TV repairs. | £1.61 |
| AR140 | for non-electrical applications, except aluminium | £1.38 |
| SS160 | for stainless steel and silver jewellery | £2.53 |
| 19A | for all electronic joints, non-corrosive. | 96p |
| AL150 | for aluminium. | £1.93 |
| BCA16 | solder cream for stainless steel, jewellery and household products (non-electrical). | £3.22 |
| BCR10 | solder cream for electronic and electrical use. | £1.38 |
| BCA14 | all purpose solder cream, non-electrical jointing and repairing. | £1.38 |

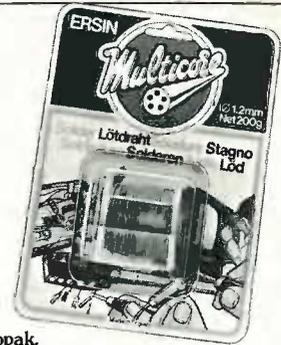Tip Kleen.
Multicore Tip Kleen. Soldering-iron tip wiping pad. Replaces wetsponges. (Should not be used above 350°C). 81p per pack.



Econopak.
Ersin Multicore 5-core solder. Contains non-corrosive flux for electrical applications. 1.2mm dia. 200g Econopak. Size 13A. £4.14 per reel.



Metal Soldering.
Arax Multicore 4-acid-core solder for metal fabrication (not aluminium) and repairs. 40/60 tin/lead. 1.6mm dia. Size 11. £3.91 per reel.



TV and Radio Soldering.
Savbit Multicore for radio, TV and similar work. Reduces copper erosion. 1.2mm dia. Size 5. 90p per handy dispenser.
Econopak.
General purpose solder suitable for all electrical joints. 40/60 alloy. 1.2mm dia. Size 6. 58p per handy plastic dispenser.



Multicore Wick.
Multicore solder-wick for removing solder from virtually any joint. 1.7mm dia. Size AB10. £1.38 per reel.



Aluminium Soldering.
Alu-Sol Multicore 4-core solder for soldering most types of aluminium. No extra flux needed. 1.6mm dia. Size 4. £6.90 per reel.



Soldering Flux Pastes.
Multicore soldering flux paste. Extra fast, non-corrosive, rosin-flux for electrical and general purpose soldering.
Rosin RF.10. 35g net. 69p per pack.
Multicore soldering flux paste for soft metals (except aluminium) and stainless steel. Non-electrical.
Arax A.F.14. 35g. 69p per pack.



Wire Stripper and cutter.
Wire stripper and cutter with precision ground and hardened steel jaws. A justable to most wire sizes. With handle locking-catch and easy-grip plastic covered handles. Ref: 9. £2.69 per pair.

Bib Hi-Fi Accessories Ltd., (Solder Division), Kelsey House, Wood Lane End, Hemel Hempstead, Hertfordshire HP2 4RQ. Telephone: (0442) 61291.

All recommended retail prices shown are inclusive of VAT. If you have difficulty in obtaining any of these products send direct with 40p for postage and packing. For free colour brochure send S.A.E.

WW-004 FOR FURTHER DETAILS