

wireless world


Australia A\$ 2.40
Canada C\$ 4.25
Denmark Dkr. 20.25
Germany Dm. 6.00
Greece Dra. 125.00
Holland Dfl. 5.00
Italy L 2300
Norway Nkr. 2.300
Singapore M\$ 5.50
Swain Pts. 180.00
U.S.A. \$3.75

APRIL 1981 60p

70 years of publication

Active cross-over networks

Low-noise amplification

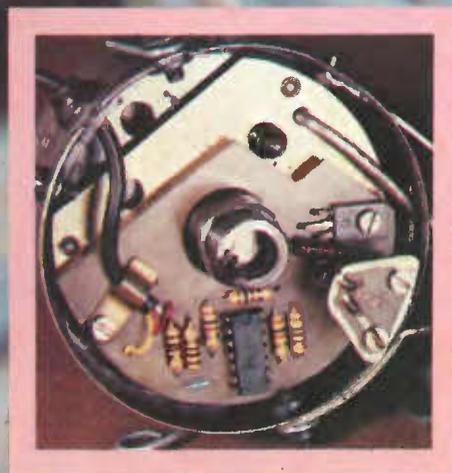

**Opto-electronic
contact breaker**



Soldering blind just burns up profit.

Given that some metallic substances are more easily soldered than others, and that there are significant differences both in the speed with which they can be soldered and in the strength of adhesion of the solder to their surfaces, it is clearly necessary to make absolutely sure that the procedure used to solder components is correct. Testing for solderability greatly reduces the risk of failed joints and that can mean appreciable savings on rejects.

Multicore, the world's leading authority on soldering, has developed a simple-to-use piece of equipment designed to assess solderability. It is called a MUST - Multicore Universal Solderability Tester - and it really is a must if you want to avoid the costly problems of inefficient soldering.

The built-in microprocessor takes the complex force/time curve and reduces it to just two values, making the application of the sophisticated test method to quality control particularly simple.



printed circuit boards and plated-through holes.

It can be used for the Edge Dip Test that appears in IPC-S-801, EIA RS-178 and EIA RS-319 Method 2 for evaluating quality of wetting, and for the Globule Test as described in many national and international standards including IEC 68-2-20, BS 2011: 2T and DIN 40046 to measure wetting speed.

This speed, together with the wetting force, may also be measured by the quick and easy addition of a wetting balance.

The Multicore Universal Solderability Tester could make a big difference to your soldering operations - and to your profits. For the eye-opening facts use the reader reply service, cut the coupon or contact Multicore direct.



The MUST can be used to evaluate the solderability of any plain or plated metal in sheet, strip or wire form. It is, however, ideal for use with electronic component terminations, metal clad laminate,



The biggest name in solder worldwide

Please send me full details on the MUST
 Please telephone me

Name _____
 Position _____
 Company _____
 Address _____
 Telephone _____
 Telex _____

WWI

Sales Department, Multicore Solders Limited, Maylands Avenue, Hemel Hempstead, Hertfordshire HP2 7EP. Telephone (0442) 3636. Telex 82363.

wireless world

APRIL 1981 60p

70 years of publication
Active cross-over networks
Low-noise amplification

Australia AS 2.40
Canada C\$ 4.25
Denmark Dkr. 20.25
Germany Dm 8.00
Greece Dra 125.00
Holland Dfl. 5.00
Italy L. 2300
Norway Nkr. 25.00
Singapore M\$ 5.50
Swain Pts. 180.00
U.S.A. \$3.75

WIRELESS WORLD APRIL 1981 VOL 87 NO 1543



Opto-electronic contact breaker



TESTING MOBILE RADIOS?

... catch this bus with Farnell

and arrive economically at an efficient ATE workstation.

Comprehensive testing under low cost desk computer control.

Manual systems too.



Farnell

INTERFACE WITH US NOW!

Ask for details from:



Front cover shows (inset) details of the opto-electronic contact breaker described in this issue on the background of a Marconi Space and Defence Systems hybrid microelectronic circuit.

IN OUR NEXT ISSUE

Digital capacitance meter uses the timed charge-injection method of measurement, with an input protection circuit, optimized to reduce errors.

Wien oscillator is a new design by Linsley Hood, using a different connexion of the standard Wien bridge to give a total harmonic distortion of 0.001%.

Active television deflector receives tv signal, amplifies and re-transmits it to viewers in no-signal reception areas.

Current issue price 60p, back issues (if available) £1.00, at Retail and Trade Counter, Units 1 & 2, Bankside Industrial Centre, Hop-ton Street, London SE1. Available on microfilm; please contact editor.

By post, current issue 96p, back issues (if available) £1.50, order and payments to EEP General Sales Dept., Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS.

Editorial & Advertising offices: Quadrant House, The Quadrant, Sutton Surrey SM2 5AS.
Telephones: Editorial 01-661 3500. Advertising 01-661 3129.
Telegrams/Telex: 892084 BISPRS G.

Subscription rates: 1 year £10.00 UK and \$33.80 outside UK.
Student rates: 1 year £5.00 UK and \$16.00 outside UK.

Distribution: 40 Bowling Green Lane, London EC1R 0NE. Telephone 01-837 3636.

Subscriptions: Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. Telephone 0444 59188. Please notify a change of address.

USA mailing agents: Expeditors of the Printed World Ltd, 527 Madison Avenue, Suits 1217, New York, NY 10022. 2nd-class postage paid at New York.

wireless world

ELECTRONICS/TELEVISION/RADIO/AUDIO

APRIL 1981 Vol 87 No 1543

37 The next seventy years

38 Opto-electronic contact breaker
by J. R. Watkinson

41 More on active cross-over networks
by David Read

44 News of the month
Flat c.r.t. from Sinclair. Custom-built I.s.i. Microcomputers in space

48 Circuit ideas
Pre-amp and multi-section control. Divide by $(2n - 1)$

51 Radio observation of the 'active' sun
by R. A. Ham

55 Letters to the editor
Artificial intelligence. Commercial broadcasting.
Designing with microprocessors.

59 Dividing by fractions
by Gilbert Pearson

62 Phase measurements with an oscilloscope
by I. D. MacArthur

65 Wireless World, 1911-1981

66 Designing with microprocessors - 7
by D. Zissos

70 World of amateur radio

71 Introduction to low-noise amplifier design
by A. Foord

74 Magnetic recording review - 2
by J. Moir

79 Surface acoustic wave devices - 2
by R. J. Murray and P. D. White

83 Multipath distortion
by Pat Hawker

86 Novatexts: amplitude sensing and control
by P. Williams

88 New products

90 Sidebands
by Mixer

Electronic Brokers - Europe's Premier Test Equipment Company offer SUPERLATIVE USED EQUIPMENT CALIBRATED TO ORIGINAL SPECS

The Electronic Brokers GUARANTEE

Unless otherwise stated, all test equipment sold by us carries a 12 month warranty; For VDUs and Teletypes we offer a 90 days warranty, and computers are offered with on site acceptance and diagnostic tests (which may qualify them for independent on-going maintenance). When you buy from Electronic Brokers you know the equipment is in 'top notch' condition. It is refurbished in our own service laboratories and checked to meet the original manufacturer's sales specifications. And it's serviced by our own highly qualified technicians.

A copy of our Trading Conditions is available on request.

..... April 1981..... Latest Test Equipment.....

- ANALOGUE VOLTMETERS AND MULTIMETERS**
- Bonton.**
93A True RMS Voltmeter. Bandwidth 10Hz-20MHz. 1mV-300 FSD. £375.00
- Fluke.**
883AB AC/DC Differential Voltmeter. 20Hz-100kHz. 1mV-1100V. Very high accuracy. £975.00
- 895A DC Differential Voltmeter. 0-1100V. Null sensitivity. 100 μ V-100V. Very high accuracy. £950.00
- Hewlett Packard.**
400E AC Millivoltmeter. 10Hz-10MHz. 1mV-300V DC o/p proportional to i/p. £235.00
- 7563A DC Log Voltmeter / Amplifier. Single i/p range 360 μ V-100V O/P 0-1.1V @ 10mV/dB. £250.00
- Marconi.**
TF2600 AC Millivoltmeter. 10Hz-5MHz. 1mV-300V. £175.00
- TF2604 Electronic Voltmeter. AC 20Hz-1.5GHz. 300mV-1KV. DC 10mV-1KV. 0.2 μ -500M Ω . £350.00
- TF2606 DC Differential Voltmeter. 1mV-1100V on 5 decade dials. £200.00
- Philips.**
PM2454B AC Millivoltmeter. 10Hz-12MHz. 1mV-300V. £195.00
- ANALYSERS**
- Biomation.**
1650D 16 Channel Logic Analyser. Displays Timing. Map, hex, octal. Clock rate upto 50MHz. Supplied with display formatter and a Hameg HM312-B oscilloscope. £3600.00
- Dymar.**
1771 LF Wave Analyser. 20Hz-50kHz. 30 μ V-300V. £275.00
- General Radio.**
1911A Sound and Vibration Analyser. CW Graphic level recorder. 4.5Hz-25kHz. 1/3 or 1/10 octave. £950.00
- 8407A/B412A Network Analyser. CW. 8600A/B601A Sweeper. 0.1-110MHz. £3500.00
- Hewlett Packard.**
141T-8552B-8554B Spectrum Analyser. 100kHz-1250MHz. +10 to -122dBm. Variable persistence display. £5400.00
- Marconi.**
TF2330 Wave Analyser. 20Hz-20kHz. 30 μ V-300V. £395.00
- Tektronix.**
1L5 Spectrum Analyser. 10Hz-1MHz. £750.00
- 491 Spectrum Analyser. 10MHz-2GHz direct. Up to 40GHz with optional mixers. £4150.00
- Wayne Kerr.**
RA200 Frequency Response Analyser. Frequency range 20Hz-30kHz or 200Hz-200kHz. 11 in. crt display. £850.00
- BRIDGES & COMPONENT TESTERS**
- AVO/BPL.**
CB15/4 Electrolytic Capacitance Tester. 0.1 μ F-1F. Accuracy 1% to 2%. £515.00
- Bonton.**
63H Inductance Bridge. 0-110mH. Bridge frequency 5-500kHz. £1250.00
- 280AP VHF O Meter. 0-20 to 25,000. 210-610MHz. £650.00
- General Radio.**
1607A Transfer Function and Immittance Bridge. 25-1500MHz. Direct reading. £750.00
- Marconi.**
TF1245-TF1246-TF1247 'O' Meter and Oscillators. 0.5 to 500. 40kHz-300MHz. £950.00
- TF1313/2M 0.25% LCR Bridge. 0.1 μ H-110H. 0.1pF-100 μ F. 3m Ω -110M Ω . 1 and 10kHz. £325.00
- Rohde & Schwarz.**
KRT (BN5100) Capacitance Meter. 1pF-100 μ F. 2.2-285kHz. £395.00
- LRT (BN6100) Inductance Meter. 1pH-100 μ H. 2.2-285kHz. £395.00
- Wayne Kerr.**
BZ21 0.1% LCR Bridge. 0.0002pF-1.1 μ F. 90-500G Ω . 0.9mH = 5MH. 2pu-111mv. £225.00
- B641 0.1% LCR Bridge. 0.002pF. 50.000 μ F. 200nH-5MH. 2m Ω -50.000M Ω . 20pu-500v. £445.00
- A60 Testmatic Dynamic Circuit Tester. Automatically checks upto 60 functions in 10 seconds on PCB's. £895.00
- CALIBRATION EQUIPMENT**
- Advance.**
OFS2B Off Air Frequency Standard. O/P 1 and 10MHz. £95.00
- Bradley.**
125B AC Calibrator. 0-511V in 0.1V steps @ 50-60-400Hz. £425.00
- Fluke.**
332A DC Voltage Calibrator. 0 to 1111.110V. 0.1ppm resolution. 0.003% calibration accuracy. £1495.00
- 760 Meter Calibrator. DC/AC Volts and current. £2150.00
- Hewlett Packard.**
741B DC Voltage Source and AC/DC Differential Voltmeter. £695.00
- Tektronix.**
191 Constant Amplitude Generator. 350kHz-100MHz. £350.00
- DVM's AND DMM's**
- Datron.**
1051 5 1/2 Digit DMM. AC/DC Volts, Resistance. True RMS. 0.1 μ V resolution. £750.00
- Fluke.**
8800A 5 1/2 Digit DMM. AC/DC volts, resistance. 1 μ V resolution. £450.00
- Hewlett Packard.**
34702A & 34740A 4 1/2 digit DMM. AC/DC volts, resistance. £225.00
- 3490A 5 1/2 Digit DMM. AC/DC volts, resistance. 1 μ V resolution. 30 day warranty. £375.00
- Philips.**
PM2513A 3 1/2 Digit DMM. AC/DC volts and current, resistance. £80.00
- PM2514 3 1/2 Digit Autoranging DMM. AC/DC volts and current, resistance. £95.00
- PM2517E 4 Digit Auto ranging DMM. AC/DC volts and current, resistance. £115.00
- PM2527 4 1/2 Digit DMM. AC/DC volts, current and resistance. 10 μ V resolution. True RMS. £400.00
- Solartron.**
A243 5 1/2 Digit DMM. AC/DC volts, resistance. 1 μ V resolution. 30 day warranty. £375.00
- 7055 Microprocessor DMM. Scale length 200,000. AC/DC volts, resistance. 1 μ V resolution. £850.00
- 7055 plus processor control and RS232 interface. £1150.00
- 7065 Microprocessor DMM. Scale length 1,400,000. AC/DC volts, resistance. £950.00
- 7065 plus processor control and RS232 interface. £1250.00
- Weston.**
4440 3 1/2 Digit DMM. AC/DC volts, DC current, resistance. £90.00
- FREQUENCY COUNTERS**
- Advance.**
TC15 & P1 Frequency Counter. DC - 500MHz. 9 digits. £275.00
- Fluke.**
1900A-01 Frequency Counter. 5Hz-80MHz. 6 digits. Mains / battery operation. £195.00
- 1911A-01 Frequency Counter. 5Hz-250MHz. 7 digits. Mains / battery operation. £325.00
- 1912A Frequency Counter. 5Hz-520MHz. 7 digits. £340.00
- 1925A Frequency Counter. 5Hz-125MHz. 9 digits. EMI proof case. £375.00
- Philips.**
PM6604 Timer Counter. DC - 50MHz. 6 digits. £150.00
- PM6614 Frequency Counter. 10Hz-520MHz. 9 digits. £450.00
- PM6615 9 digit 1GHz Frequency Counter. 10mV sensitivity. Period, ratio and totalizing. £695.00
- PM6664 Fully Auto Frequency Counter. 10Hz-520MHz. 8 digits. £250.00
- MULTIMETERS**
- Avo.**
8MK 5 Multimeter 20k Ω /volt. £70.00
- Full lead kit. £5.25
- Test Set Number 1. 20k Ω /volt, very robust. £75.00
- S.E.I.**
Super 50 Selectest. 20k Ω /volt. £77.00
- OSCILLOSCOPES**
- Cossor.**
4100 Dual Trace Portable Oscilloscope. DC - 75MHz Full delayed sweep. 30 day warranty. £450.00
- Hewlett Packard.**
1707A Dual Trace Portable Oscilloscope. DC - 75MHz Full delayed sweep. 30 day warranty. £450.00
- 1707B Dual Trace Portable Oscilloscope. DC - 75MHz. 10mV-5V/div. Full delayed and intensified sweep. Trigger hold off. £725.00
- Philips.**
PM3212 Dual Trace Portable Oscilloscope. DC - 25MHz. 2mV-10V/div. £575.00
- SE Labs.**
SM121 6 Channel Monitor. 12" crt. Internal sweep. £395.00
- Tektronix.**
432 Dual Trace Portable Oscilloscope. DC - 25MHz. 1mV sensitivity. 20ns-55. Auto setting mains input 100-250V. £510.00
- 464 Dual Trace Portable Storage Oscilloscope. DC - 100MHz. 5mV-5V/div. Full delayed sweep. Max writing speed 110 div/ μ s. £2250.00
- 465 Dual Trace Portable Oscilloscope. DC - 100MHz. 5mV-5V/div. Full delayed sweep. 3000div/ μ s. £2875.00
- 521A PAL Vectorscope. Measures Luminance Amplitude, Chrominance Phase, Chrominance Amplitude, Differential Phase and Gain. As new condition. £2650.00
- 7704A Main Frame CW 7A26. 7880. 7885. Dual Trace DC - 200MHz. £3550.00
- Telegquipment.**
D75 Dual Trace Portable Oscilloscope. DC - 50MHz. Full delayed sweep. £715.00
- VU-Data.**
PS940 Dual Trace Portable Battery Operated Oscilloscope. DC - 20MHz 10mV-20V/div. Weight 9.5lbs. £395.00

..... April 1981..... Latest Test Equipment.....

- OSCILLOSCOPE PROBES**
- EB90 X1 Probe. 1.2 mtr length DC - 20MHz. £9.00
- EB91 X10 Probe. 1-2 mtr length DC - 100MHz. £11.00
- EB95 X1, X10 Probe. 1.2 mtr length DC - 10MHz or DC - 100MHz. £15.00
- POWER SUPPLIES**
- Advance.**
PMA47 0-15V preset @ 3A. £37.00
- PMA50 0-15V preset @ 5A. £45.00
- MG5-60 5V @ 60A switching. £160.00
- MG5-20 5V @ 20A switching. £120.00
- MG5-10 5V @ 10A switching. £95.00
- MG24-12 24V @ 12A switching. £130.00
- RECORDERS**
- Bryans Southern.**
40000 12 Channel UV Recorder Plus 2 off 40501 Galvo Amps. 6" paper. £950.00
- Hewlett Packard.**
2FA XYY A3 Plotter. 2 Pens on Y axis. Infrared X sweep. Electric paper grip. £725.00
- S. E. Labs.**
3006/12 12 Channel UV Recorder. Grid and timing lines. 6" paper. £550.00
- 6012 50 Channel UV Recorder. Servo paper drive upto 5 metres/sec. 12" paper. £1100.00
- Watenabe.**
MC641 6 Channel Chart Recorder. 1mV-100V. 250mm scan width. £1495.00
- MC611 5-4L 4 Channel Chart Recorder. 100 μ V-2V. 400-800-1600mm/Hour/Minute. £595.00
- Yokagawa.**
3047 2 Channel Chart Recorder. 0.5mV-100V. 2cm/hr-60cm/min. £435.00
- SIGNAL SOURCES**
- Avo.**
HF135 AM Signal Generator. 100kHz-240MHz. 1 μ V-100mV into 75 Ω . AM 0-30% @ 1kHz. £190.00
- HF136 AM/FM Signal Generator. 4.0-120MHz. 0-100mV in 20dB steps plus fine control. O/P Z = 75 Ω . £410.00
- Hewlett Packard.**
203A Variable Phase Oscillator. 0.005Hz-60kHz. 0-360°. £450.00
- 4204A Decade LF Oscillator. 10Hz-1MHz. 1mV-10V into 600 Ω . £695.00
- 606B AM Signal Generator. 50kHz-65MHz. AM 0-95%. £850.00
- 612A AM/PM UHF Generator. 450-1230MHz. 0.1 μ V-0.5V. £775.00
- 616B UHF Signal Generator. 1.8 to 4.2GHz. Int. pulse Mod. £1000.00
- 651B Test Oscillator. 10Hz-10MHz. 0.1mV-3.16V. £415.00
- B600A + B601A RV Sweeper + Markers. 100kHz-1.0MHz. £1500.00
- B690B RF Sweeper Main Frame CW the following RF Modules: B698B 400kHz-1.0MHz. B699B 0.1-4GHz. B694A 8-12.4GHz. £2500.00
- Marconi.**
TF144H/4 AM Signal Generator. 10kHz-72MHz. 2 μ V-2V. £750.00
- TF144H/4S AM Signal Generator. 10kHz-72MHz. 2 μ V-2V. £550.00
- TF995B/2 AM/FM Signal Generator. 0.2 to 220MHz. 1 μ V-200mV into 50 Ω or 75 Ω . £675.00
- TF995B/5 AM/FM Signal Generator. 200kHz-220MHz. 1 μ V-200mV. Narrow deviation for mobiles. £695.00
- TF1370A Wide Range RC Oscillator. 10Hz-10MHz. Sine wave, square wave upto 100kHz. £275.00
- TF2002B AM/FM Signal Generator. 10kHz-88MHz. 0.1 μ V-1V. 20Hz-20kHz Mod frequency. £1200.00
- TF2005R 2 Tone Signal Source. 20Hz-20kHz. 0-11 dB in 0.1 dB steps. £295.00
- TF2100 AF Oscillator. 20Hz-20kHz. 0.05% distortion. £150.00
- Philips.**
PM5108 Function Generator. 1 Hz-1MHz. Sine, square and triangle. Triangle O/P. £250.00
- PM5127 Function Generator. 0.1Hz-1MHz. Sine, square and triangle. £395.00
- PM5167 Function Generator. 1MHz-10MHz. Sine, square, \pm pulse, ramp and triangle. £500.00
- PM6456 Stereo Generator. Separate L and R Signals. Carrier frequency 100MHz. RF O/P 1 μ V-100mV into 75 Ω . £375.00
- Schlumberger.**
4000C Frequency Synthesizer. 300Hz-520MHz. Max O/P 1V into 50 Ω . 0-139.9dB attenuator. £1250.00
- Tektronix.**
2101 Pulse Generator. 2.5Hz-25MHz. + and - O/P. £375.00
- Telonik.**
2003 RF Sweeper System. 1-300MHz. 5 and 10kHz markers. £950.00
- SOUND LEVEL METERS**
- Bruel and Kjaer.**
2203 Sound Level Meter. CW 4145 1" Microphone. A, B, C, weighting. £395.00
- General Radio.**
1933 Sound Level Meter CW 1935 Cassette Data Recorder. 10-130dB. ABC weighting. Octave band filters at 10 centre frequencies from 31.5Hz to 16kHz. £750.00
- 1981 Sound Level Meter. 70-120dB. Digital and analogue reading. Peak hold. A weighting. £300.00
- 1983 Sound Level Meter. 70-120dB. A weighting. £195.00
- TRANSMISSION MEASURING EQUIPMENT**
- Marconi.**
OA2805A PCM Regenerator Test Set. Composed of TF2801/2, TF2802/2 and TF2823. For use on systems at 1.536 and 2.048Mbits. £2700.00
- TF2807A PCM Multiplex Tester. Comprises Noise / Sinewave source and level meter. £1500.00
- TF2332 AF Transmission Test Set. 20Hz-20kHz. £425.00
- Siemens.**
D2040 Selective Level Analyser and Voltmeter. 10Hz-60kHz. -110dB to +50dB. 3 μ V-300V Lin and log indication. 5 digit frequency readout. £1200.00
- D2072 + W2072 Level Meter and Oscillator. 50kHz-100MHz. -110dB-0dB. Receive bandwidth 3.1 and 10kHz. £2200.00
- W2006 + D2006 Carrier Level Test Set. 10kHz-17MHz. -100 to +10dB. £1650.00
- W2007 + D2007 Carrier Level Test Set. 6kHz-18.6MHz. -120 to +20dB. £1800.00
- Wandel and Goltermann.**
PF-1 Digital Error Rate Measuring Set. Consisting of PPM-1 Digital Error Rate Meter and PFG-1 Pattern Generator. £2490.00
- PSO-5 and PMO-5 Level Measuring Set. 10kHz-36MHz. -110 to +20dB. CW AZD-1 Scale expander. £2050.00
- SPM-6 and PS-6 Level Measuring Set. 6kHz-18.6MHz. -110dB to +20dB. Mains / battery operation. £2150.00
- Andimat (PSM-4 2MHz Automatic PCM Testing System) composed of the following PCM-1 PCM Test Set, PDA-64 PCM Signalling Analyser, PMD-1 Digital Level and Noise Measuring System, PDG-1 Digital Signal Generator, PDA-1 PCM Digital Signal Analyser, PSM-4 Level Measuring Set, MU-4 Scanner, R1-1 computer interface. £6500.00
- MISCELLANEOUS**
- Avantek.**
UA101 RF Modular Amplifier. 5-500MHz. 10.5dB gain. £39.00
- UA103 RF Modular Amplifier. 10-500MHz. 10dB gain. £39.00
- UA301 RF Modular Amplifier. 1-400MHz. 7dB gain. £39.00
- UA305 RF Modular Amplifier. 2-500MHz. 13dB gain. £39.00
- Avo.**
VCM163 Valve Tester. £425.00
- Data Laboratories.**
DL905 Transient Recorder with Pre-Trigger facility. Ideal for viewing single shot voltage transients. £990.00
- Dymar.**
1581 RF Power Meter. DC - 500MHz. 30mW-100W. £350.00
- Ferroglyph.**
RTS2 Recorder Test Set Measures Wow & Flutter, Distortion, Gain. £345.00
- RTS2 + ATU2 Recorder Test Set. CW Auxiliary Test unit. Superb condition. £650.00
- General Radio.**
335E Programmable Attenuator. 0-12dB. DC - 10GHz. 50 Ω . £75.00
- 432A Power Meter with 478A Thermistor Head. 10MHz-10GHz. 100 μ V-10mV. £450.00
- 4329A Insulation Resistance Meter. Range 500k Ω to 2 x 10¹¹ Ω . £500.00
- 8745A S Parameter Test Set. Fitted with 11604A Universal Arms 0.1-2GHz. £2750.00
- Marconi.**
TF791D Deviation Meter. 4-1024MHz. £195.00
- TF893A AF Power Meter. 1mW-10W. £185.00
- TF2300 AM/FM Modulation Meter. 0.5-1200MHz. £375.00
- TF2337 Automatic Distortion Meter. Frequency range 400Hz and 1kHz 0-30% in 4 ranges. £245.00
- Rohde and Schwarz.**
MSC Stereo Coder. 30Hz-15kHz. £500.00
- Radiometer.**
BKF10 Automatic Distortion Analyser. 20Hz-20kHz. 0.02%-10%. £1100.00
- Rifa.**
EVV 300 Microprocessor Development Kit. Based on Motorola 6800 TTY interface. £235.00
- Tektronix.**
TMS15 Main Frame CW FG504. 0.001Hz-40MHz Function Generator and 2 off PS503A Power Supplies. £1250.00
- TMS15 Main Frame CW SC502. 15MHz oscilloscope. FG503 1MHz-3MHz Function Generator. DM502 3 1/2 digit DMM. DC503 100MHz counter. £1495.00

Electronic Brokers is Europe's largest specialist in quality, second user test equipment, computers and associated peripherals. Established 14 years ago we have pioneered the second user concept in Britain, and many overseas territories.

To support our growth we have a skilled team. This includes trained sales staff, whose role is not only to sell, but provide a helpful information service to our many customers. Backing this team is our own service laboratory where technicians monitor each item of equipment we sell. Our maxim is service, and those who have dealt with us will know that we endeavour to always live up to our reputation.

Wherever your business is - UK, Europe, in fact anywhere in the world, The Electronic Brokers Organisation is just a telephone or telex call away!

Hours of Business: 9 a.m. - 5 p.m. Mon-Fri.
Closed lunch 1.2p.m.
ADD 15% VAT TO ALL PRICES.
Carriage and Packing charge extra on all items unless otherwise stated.



WW-200 for further details

Electronic Brokers Limited
61/65 Kings Cross Road
London WC1X 9LN England
Telephone: 01-278 3461
Telex: 298694 Elebro G

Electronic Brokers - Europe's Premier Used Computer Company offer

SUPERLATIVE USED COMPUTER EQUIPMENT - AS

Electronic Brokers - Europe's Premier Used Computer Company offer

SUPERLATIVE USED COMPUTER EQUIPMENT - AS

April 1981 Latest Computer Equipment

PDP11 SYSTEMS

DEC
PDP11/34A System complete with 256KB MOS memory DL11W Asynchronous Interface / Line Clock, KY11-LB Programmers Panel, VT100 Terminal, 2 x RL01 5-meg Disk Drives, DZ11A 8-Line multiplexer, FP11A Floating Point, H960 Cabinet **£17,500.00**

PDP11/34A System complete with 256KB MOS memory, 2 x RK01 28-meg Disk Drives, TMB11 magnetic tape station, DZ11 16-line multiplexer, Data system cabinet and expander box, LA36 console terminal **£27,750.00**

PDP11/60 System with 2 RK07 Disk Drives, choice of console **P.O.A.**

PDP11/03 System (desk-mounted) 20KW MOS, RX11 dual floppy disk drive and control, 3 serial interfaces, LA180 Printer, VT100 Console terminal **P.O.A.**

PDP11 C.P.U.s

DEC
PDP11/03-SD Processor in 3 1/2" chassis complete with 16KW MOS memory and E15 option. **£1495.00**

PDP11/04 Processor in 10 1/2" chassis complete with 16KW MOS memory and DL11W Interface. **£4500.00**

PDP11/34 in 10 1/2" chassis complete with 64KB MOS memory. **£5500.00**

PDP11/34 Processor (non-A) in 10 1/2" chassis complete with 128KB MOS memory, DL11W Interface and programmers front panel. **£5900.00**

PDP11 MEMORY

DEC
MF11L 8KW core memory c/w 9-slot system unit **£975.00**

MM11L 8KW core memory **£795.00**

MM11LP 8KW parity core memory **£750.00**

MM11DP 16KW core (ex DEC-maintained 11/34 systems). **£395.00**

BARGAIN OFFER - ONLY
MM11UP 16KW Parity core memory complete with 9-slot system unit **£1500.00**

MM11UP 16KW parity core memory (pre-requisite MF11UP) **£1250.00**

MS11UP 16KW MOS memory **£675.00**

MSV11C 16KW MOS memory (LS11) **£495.00**

MJ11-BE 64KW 11/70 memory **£4500.00**

MK11-BE 64KW MOS memory for 11/70 **£3950.00**

MS11-MB 256KB ECC MOS memory for 11/44 (NEW) **£3942.00**

DISKS

DEC
RK05J add-on disk drive 2 1/2" meg. Exchangeable cartridge type. From **£1850.00**

RK06 Add-on disk drive 14 meg. Free standing. From **£3250.00**

RK07-ED Add-on Disk drive 28 meg. **P.O.A.**

RL01-AK Add-on Disk drive 5 meg. **£1975.00**

RP02 20 meg add-on disk drive **£1250.00**

RP04 add-on 88 meg disk drive **£8000.00**

RP06 add-on 176 meg disk drive **£15,950.00**

RX11-BD Dual floppy disk drive and control. **£1800.00**

Controllers usually available for above drives.

MAGNETIC TAPE

DEC
Available from time to time - TU10, TU45, TE16 TS03 etc.

PDP11 OPTIONS

DEC
AA11D VT01 Controller with 4-slot System Unit **£125.00**

DD11A 4-slot System Unit **£125.00**

DD11B 4-slot System Unit **£150.00**

DD11-DK 9-slot backplane **£465.00**

DL11 Serial Interface **£250.00**

DL11W/A/B Serial Interface/Line Clock **£395.00**

DR11C General Purpose Interface **£250.00**

DRV11B 16-bit Parallel Interface **£225.00**

DZ11A 8-line E1A MUX **£1395.00**

FP11A Floating Point **£1750.00**

KL11 TTY Interface **£150.00**

KW11L Real Time Clock **£150.00**

KW11P Programmable Clock **£345.00**

M105 Device Selector **£30.00**

M792 ROM Diode Matrix **£195.00**

M920 Unibus Connector **£12.00**

M9301-YB Bootstrap **£325.00**

POWER SUPPLIES

DEC
H720 Power supply for BA11 Expander Box, BRAND NEW SURPLUS **£175.00**

PDP8A C.P.U.

DEC
PDP8A Processors, systems and add-on memory usually available.

PDP8A MEMORY

DEC
MM8AA 8KW Core **£750.00**

MM8AB 16KW Core **£995.00**

PDP8E CPU, MEMORY, OPTIONS

DEC
DP8EB Communications Adaptor **£395.00**

KABE Positive I/O Bus **£95.00**

KDBE Databreak **£145.00**

KLBE Asynchronous Interface **£250.00**

KPBE Power fail/auto restart **£95.00**

MM8E 4KW Core memory stack **£350.00**

TABE Dual Cassette Drive and Controller **£525.00**

VT8E Set graphics Control Modules **£250.00**

TERMINALS

DEC
LA34 DECwriter 1V 30cps desk-top terminal, 132 columns, upper/lower case ASCII **£495.00**

LA36 DECwriter 11 Keyboard Printer Terminal. The Terminal that has become an industry standard, with 132 column upper/lower case printing and switch-selectable speeds of 10, 15 & 30cps. Available with either 20mA or RS232 interface. NOW ONLY **£595.00**

VT 52 SPECIAL PURCHASE of this outstanding Video Display Terminal featuring full upper/lower case ASCII character set, 24 x 80 display, auxiliary keypad, direct cursor addressing and tabulation, scroll or hold screen mode with X-off facility, 9 switch-selectable baud rates (75-9600 baud) choice of 20mA or RS232 interface. BRAND NEW SURPLUS. ONLY **£450.00**

VT100 - Also available from time to time, DEC's latest 132 column display terminal. Please enquire for latest price and delivery. **£750.00**

PRINTERS

Centronics 101.
Heavy Duty Matrix printer with 64 ASCII upper case character set, 165 cps operation, 132 print positions with adjustable tractor feed. Parallel input. ONLY **£495.00**

GP80 Graphics.

NEW
BRAND NEW - LOW COST MATRIX PRINTER IDEAL FOR MICROPROCESSOR USERS SUCH AS HOBBYISTS & EDUCATIONALISTS OR ANY LOW-BUDGET APPLICATION

- * Full upper/lower case ASCII PLUS GRAPHICS Mode
- * 80-column printing with adjustable tractor feed
- * Standard and double-width characters (12 cpi and 6 cpi)
- * 30 cps print speed with 1-line buffer
- * Standard parallel (Centronics-type) interface
- * Optional interfaces available for RS232, IEEE488, Tandy, PET, Apple II
- * ONLY **£199.00** (Mail order total **£240.35**)

GE Terminus 1200.
RO printer, 80 columns, tractor feed, upper/lower case, ASCII, 20mA Interface **£325.00**

Hazeltine.
Thermal printer, 80 columns, 30 cps silent RO with parallel TTL input **£395.00**

Tally 1602.
Matrix printer, parallel input, upper/lower case, tractor feed, as new **£995.00**

Teletype.
ASR 33 input/output terminal incorporating paper tape punch and reader, 64 ASCII upper case character set, 110 baud operation, even parity keyboard choice of RS232 or 20mA interface. NOW ONLY **£595.00**

Options.
ICL-type keyboard **£50.00**

8th level marking **£25.00**

Remote reader control **£50.00**

Reader step **£20.00**

Auto reader **£25.00**

Pedestal **£30.00**

Low Cost Printer Offer.
Teletype 33 printer mechanism including case but no keyboard or electronics, 64 upper case ASCII, 10 cps, pinfeed platen, ideal for the electronic hobbyist ONLY **£85.00**

Termiprinter 7075.
Impact printer, upper/lower case, pin feed, RS232 **£325.00**

Texas.
733 ASR terminal utilising high performance twin cassette drive for fast time-saving transmission and off-line storage.

- * Silent operation
- * Switch-selectable transmission speeds 10, 15, & 30 cps
- * Full tape editing capability
- * High-speed duplication and rewind
- * Standard RS232 interface **£1375.00**

745 Portable Data Terminal including keyboard, printer, integral acoustic coupler and carrying case. Total weight only 13 lbs **£750.00**

April 1981 Latest Computer Equipment

PAPER TAPE PUNCHES

Digitronics.
P120 paper tape punch. Solenoid-actuated unit capable of punching 5 to 8 channel tapes at speeds up to 35 cps. Pulse amplitude 27 VDC. Compact table-top unit. **£95.00**

Facit 4070.
The top quality punch that has become an industry standard. Asynchronous 75cps operation. Adjustable for punching 5, 6, 7 or 8 level tape. Self-contained desk-top unit incorporating supply and take-up spools, chad box, and TTL-compatible control logic. **£650.00**

KEYBOARDS

George Risk.
New ASCII Keyboards New Low Prices

NEW
KB771 Superb 71-station ASCII keyboard incorporating separate numeric/Cursor control pad and installed in custom-built steel enclosure with textured blue enamel finish. Ideal for the VDU builder. Case dimensions: 17 1/4" x 7 1/2" x 3 1/8". Total weight 4kg. PRICE **£85.00**

Mail Order Total **£103.50**

KB756 56-station ASCII keyboard mounted on P.C.B. **£39.50**

Mail Order Total **£47.15**

KB756MF as above, fitted with metal mounting frame for extra rigidity **£45.00**

Mail Order Total **£53.48**

KB710 10-key numeric pad, supplied with connecting cable. **£8.00**

Mail Order Total **£9.78**

KB701 Plastic enclosure for KB756 or KB756MF **£12.50**

Mail Order Total **£15.24**

KB702 Steel enclosure for KB756 or KB756MF **£8.00**

Mail Order Total **£23.00**

KB2376 Spare ROM encoder **£12.50**

Mail Order Total **£15.24**

KB15P Edge connector for KB756 or KB756MF **£3.25**

Mail Order Total **£4.31**

DC-51 2 DC converter to allow operation at 5V only (plugs in to P.C.B.) **£7.50**

Mail Order Total **£9.20**

DB25S Mating connector for KB771 **£4.25**

Mail Order Total **£5.46**

PERK 56-station ASCII keyboard for PET complete with PET interface, built-in power supply and steel enclosure. **£95.00**

Mail Order Total **£115.00**

Discounts available for quantities.

PROGRAMMABLE CALCULATORS

Hewlett Packard.
9830A with 8K Memory, Extended I/O ROM, String Variables ROM, 1 Serial and 3 parallel interfaces **£1695.00**

MODEMS

Racal Milgo.
Modem 26 ISI 1200/2400 baud, 2 or 4 wire, full/half duplex **P.O.A.**

GENERATORS

Mawdsley.
45KVA Generator system comprising AC Induction Motor, AC Generator, AC Exciter and Emerg Regulator. The alternator comprises of a screen-protected rotating field, complete with built-in over-hung exciter of the brushless pattern. It is wound for 415V, 3 phase, 50Hz, 4 wire and developing 45KVA at 018 P.F., when running at a speed of 1500 rpm. The alternator and exciter are used in conjunction with the automatic transistorised voltage regulator, incorporating 3-phase sensing. The regulator is so designed that when the alternator is on balanced 3-phase load and with one phase switched off or disconnected, the phase voltage will not vary more than ± 6% under any conditions **£1250.00**

VDUs

Hazeltine.
H1000 The low, low priced teletypewriter-compatible video display terminal, offering your choice of transmission speeds up to 9600 baud as well as parity generation and checking, 12 x 80 display upper case ASCII, RS232 interface, choice of baud rates SUPER VALUE **£199.00**

H2000 Superb spec. including full XY cursor addressing and edit facility, 27 x 74 display, upper case ASCII, RS232 interface, switch-selectable baud rates **£299.00**

H2000C NOW ALSO AVAILABLE with 25 x 80 line format and C-MOS logic **£375.00**

Modular One. Now with upper/lower case, XY cursor addressing, 24 x 80 line display, dual intensity detachable keyboard, choice of 8 transmission rates up to 9600 baud **£399.00**

MONITORS

Ball Miratel TTL15.
15in. diagonal green phosphor tube, integral power supply. Requires separate horizontal and vertical video input. BRAND NEW SURPLUS **£75.00**

FLOPPY DISK DRIVES

Shugart SA400.
5 1/4" MINI-FLOPPY

- * Capacity (unformatted): 110Kb (single density) 220Kb (double density)
- * Transfer rate: 125/250 kilobits/sec.
- * Average access time: 463ms.
- * Read/Write and Write Protect electronics
- * Power requirements + 5VDC + 12VDC Dimensions 5 3/4" x 3 3/4" x 8", weight 3lbs

Supplied complete with technical manual. Application notes are available on interfacing the SA400 to Intel 8080A, Motorola etc **£195.00**

Shugart SA450.
Double-sided, double density minifloppy providing 440KB unformatted storage capacity, yet the same compact size and weight as the SA400 **£299.00**

Shugart SA801.
8" FLOPPY (NEW)

- * Capacity (unformatted): 400Kb (single density) 800Kb (double density)
- * Transfer rate: 250/500 kilobits/sec.
- * Average access time: 211ms
- * Read/Write and Write Protect electronics
- * Power requirements + 24VDC + 5VDC - 5VDC Dimensions 4 1/2" x 9 1/2" x 14 1/4"

Supplied complete with technical manual **£395.00**

Hours of Business: 9 a.m.-5 p.m. Mon-Fri. Closed lunch 1-2p.m.
ADD 15% VAT TO ALL PRICES
Carriage and Packing charge extra on all items unless otherwise stated.

WW-201 for further details

Electronic Brokers is the largest specialist buyer and seller of used computers in Europe.

Our specialists deal daily in DEC, Data General and many of the numerous and well-known manufacturers of related systems and peripherals such as Teletype, Hazeltine, Texas, Hewlett Packard, Textronix. All computer equipment offered by Electronic Brokers is maintenance eligible by the original manufacturer.

Our customers come from the fields of industry, education, research government and general commerce. We have met their needs time and time again.

Whether your requirements are quick replacement, low cost development systems, additional capacity for existing equipment, or a cost effective used computer - we are only a phone call or telex away to one of our skilled sales specialists familiar with your equipment needs.



Electronic Brokers

Electronic Brokers Limited
61/65 Kings Cross Road
London WC1X 9LN England
Telephone: 01-278 3461
Telex: 298694 Elebro G



New! Sinclair ZX81 Personal Computer.

Kit: £49.⁹⁵ complete

Reach advanced computer comprehension in a few absorbing hours

1980 saw a genuine breakthrough – the Sinclair ZX80, world's first complete personal computer for under £100. At £99.95, the ZX80 offered a specification unchallenged at the price.

Over 50,000 were sold, and the ZX80 won virtually universal praise from computer professionals.

Now the Sinclair lead is increased: for just £69.95, the new Sinclair ZX81 offers even more advanced computer facilities at an even lower price. And the ZX81 kit means an even bigger saving. At £49.95 it costs almost 40% less than the ZX80 kit!

Lower price: higher capability
With the ZX81, it's just as simple to teach yourself computing, but the ZX81 packs even greater working capability than the ZX80.

It uses the same micro-processor, but incorporates a new, more powerful 8K BASIC ROM – the 'trained intelligence' of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays.

And the ZX81 incorporates other operation refinements – the facility to load and save named programs on cassette, for example, or to select a program off a cassette through the keyboard.

Higher specification, lower price – how's it done?

Quite simply, by design. The ZX80 reduced the chips in a working computer from 40 or so, to 21. The ZX81 reduces the 21 to 4!

The secret lies in a totally new master chip. Designed by Sinclair and custom-built in Britain, this unique chip replaces 18 chips from the ZX80!

Proven micro-processor, new 8K BASIC ROM, RAM – and unique new master chip.


Built: £69.⁹⁵ complete



Kit or built – it's up to you!


The picture shows dramatically how easy the ZX81 kit is to build: just four chips to assemble (plus, of course the other discrete components) – a few hours' work with a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9 V DC nominal unregulated (supplied with built version).

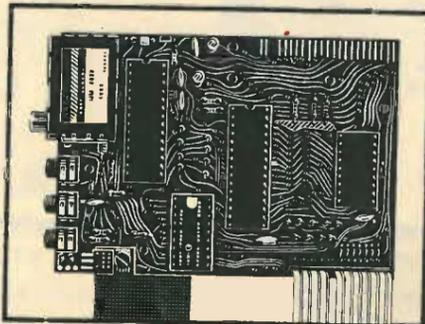Kit and built versions come complete with all leads to connect to your TV (colour or black and white) and cassette recorder.



New Sinclair teach-yourself BASIC manual

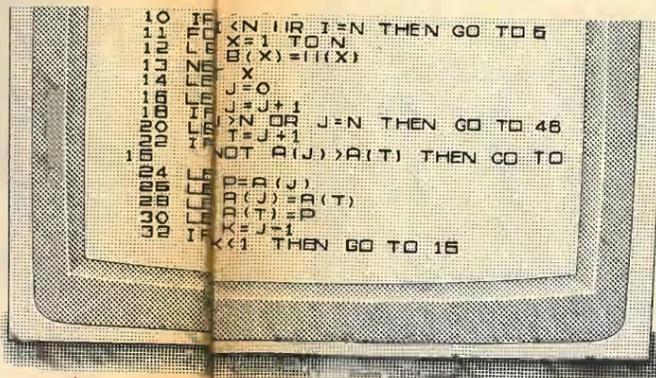Every ZX81 comes with a comprehensive, specially-written manual – a complete course in BASIC programming, from first principles to complex programs. You need no prior knowledge – children from 12 upwards soon become familiar with computer operation.



New, improved specification

● Z80A micro-processor – new faster version of the famous Z80 chip, widely recognised as the best ever made.

● Unique 'one-touch' key word entry: the ZX81 eliminates a great deal of tiresome typing. Key words (RUN, LIST, PRINT, etc.) have their own single-key entry.

● Unique syntax-check and report codes identify programming errors immediately.

● Full range of mathematical and scientific functions accurate to eight decimal places.

● Graph-drawing and animated-display facilities.

● Multi-dimensional string and numerical arrays.

● Up to 26 FOR/NEXT loops.

● Randomise function – useful for games as well as serious applications.

● Cassette LOAD and SAVE with named programs.

● 1K-byte RAM expandable to 16K bytes with Sinclair RAM pack.

● Able to drive the new Sinclair printer (not available yet – but coming soon!)

● Advanced 4-chip design: micro-processor, ROM, RAM, plus master chip – unique, custom-built chip replacing 18 ZX80 chips.

sinclair ZX81

Sinclair Research Ltd,
6 Kings Parade, Cambridge, Cambs.,
CB2 1SN. Tel: 0276 66104.
Reg. no: 214 4630 00

If you own a Sinclair ZX80...

The new 8K BASIC ROM used in the Sinclair ZX81 is available to ZX80 owners as a drop-in replacement chip. (Complete with new keyboard template and operating manual.)

With the exception of animated graphics, all the advanced features of the ZX81 are now available on your ZX80 – including the ability to drive the Sinclair ZX Printer.

Coming soon – the ZX Printer.

Designed exclusively for use with the ZX81 (and ZX80 with 8K BASIC ROM), the printer offers full alphanumeric across 32 columns, and highly sophisticated graphics. Special features include COPY, which prints out exactly what is on the whole TV screen without the need for further instructions. The ZX Printer will be available in Summer 1981, at around £50 – watch this space!



16K-BYTE RAM pack for massive add-on memory.

Designed as a complete module to fit your Sinclair ZX80 or ZX81, the RAM pack simply plugs into the existing expansion port at the rear of the computer to multiply your data/program storage by 16!

Use it for long and complex programs or as a personal database. Yet it costs as little as half the price of competitive additional memory.



How to order your ZX81
BY PHONE – Access or Barclaycard holders can call 01-200 0200 for personal attention 24 hours a day, every day.
BY FREEPOST – use the no-stamp-needed coupon below. You can pay by cheque, postal order, Access or Barclaycard.
EITHER WAY – please allow up to 28 days for delivery. And there's a 14-day money-back option, of course. We want you to be satisfied beyond doubt – and we have no doubt that you will be.

To: Sinclair Research Ltd, FREEPOST 7, Cambridge, CB2 1YY.				Order	
Qty	Item	Code	Item price £	Total £	
	Sinclair ZX81 Personal Computer kit(s). Price includes ZX81 BASIC manual, excludes mains adaptor.	12	49.95		
	Ready-assembled Sinclair ZX81 Personal Computer(s). Price includes ZX81 BASIC manual and mains adaptor.	11	69.95		
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	10	8.95		
	16K-BYTE RAM pack(s).	18	49.95		
	8K BASIC ROM to fit ZX80.	17	19.95		
	Post and Packing.				2.95

Please tick if you require a VAT receipt TOTAL £ _____

*I enclose a cheque/postal order payable to Sinclair Research Ltd, for £ _____

*Please charge to my Access/Barclaycard account no. _____

*Please delete/complete as applicable. Please print.

Name: Mr/Mrs/Miss _____

Address _____

FREEPOST – no stamp needed. WRW 04

WW – 047 FOR FURTHER DETAILS

FAST ERECTING CLARK MASTS


For World-wide Telecommunications in the 1980's Clark Masts Ltd. are specialists in the design and manufacture of telescopic and sectional mast systems. With over 25 years' experience in supplying masts to meet exacting military and civil specifications we have the expertise you can depend on.

Extended heights 4m-30 metres capable of lifting headload 1Kg-200Kgs, sectional or telescopic air-operated for field or vehicle mounting. Write or telephone us for details today.

SCAM Telescopic air-operated 12 metre mast kit shown in radio relay role for field or vehicle mounting 9-, 12-, 15- and 21-metre versions available



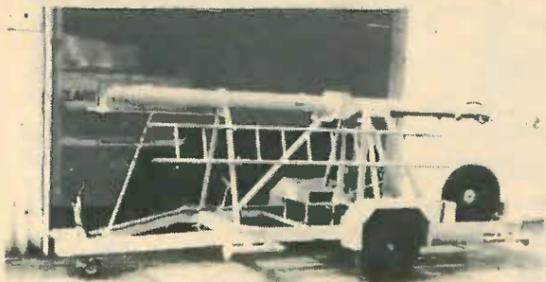Mobile air-operated 21-metre telescopic trailer mast. Horizontally stowed for transit, raised to vertical position for extension.



CLARK MASTS LTD.
Binstead,
Isle of Wight,
PO 33 3PA, England.



Telephone Ryde (0983) 63691,

Telex 86686

WW - 027 FOR FURTHER DETAILS

Make it for a Song!



The New Maplin Matinée

Amazing Value For Only **£299.95** + £99.50 for cabinet if required.

Easy to build. Latest technology — means less cost, less components and 80% less wiring. Comparable with organs selling for up to £1,000.00. Two 49-note manuals. 13-note pedalboard. All organ voices on drawbars. Preset voices: Banjo, Accordion, Harpsichord, Piano, Percussion. Piano sustain Sustain on both manuals, and pedalboard. Electronic rotor, fast and slow. Vibrato and Delayed vibrato. Reverb. Manual and Auto-Wah. Glide (Hawaiian Guitar Sound). Single finger chording plus memory. 30 Rhythms! 8-instrument voicing. Major, Minor and Seventh chords. Unique walking bass lines with each rhythm. Unique countermelody line with each rhythm. Truly amazing value for money. Full construction details in Electronics & Music Maker magazine.



The complete buyers' guide to electronic components. With over 300 pages, it's a comprehensive guide to electronic components with thousands of photographs and illustrations and page after page of invaluable data. Get a copy now — it's the one catalogue you can't afford to be without.

Post this coupon now for your copy of our 1981 catalogue price £1. Please send me a copy of your 320 page catalogue. I enclose £1 (Plus 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the UK send £1.68 or 12 International Reply Coupons. I enclose £1.25.

Name _____

Address _____

WW481

MAPLIN

Maplin Electronic Supplies Ltd.
All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR
Telephone: Southend (0702) 554155. Sales (0702) 552911.

Shops:
159-161 King Street, Hammersmith, London W6. Telephone: (01) 748 0926
284 London Road, Westcliff-on-Sea, Essex. Telephone: Southend (0702) 554000.
Both shops closed Mondays.



Catalogue now on sale in all branches of WHSMITH Price £1.00

WW - 023 FOR FURTHER DETAILS

Hilomast Ltd

HILOMAST SYSTEMS

PNEUMATIC TELESCOPIC MASTS

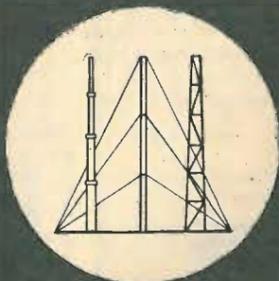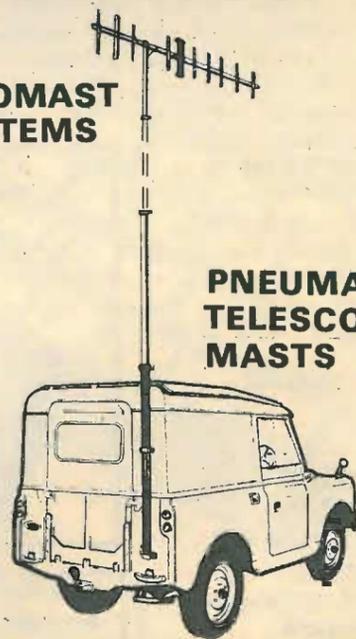

HILOMAST LIMITED

THE STREET HEYBRIDGE — MALDON
ESSEX CM9 7NB ENGLAND
Tel. MALDON (0621) 56480
TELEX NO. 995855

HAMEG

OSCILLOSCOPES

Top Performance
In Every Range



HM 307 £136
Y: Bandwidth 1-30MHz (-3dB) • Sensitivity 5mV-20V/cm (±3%)
X: Timebase 2s-20ns/cm incl. x5 Magn. • Trig. DC-30MHz (3mm)
Dual trace • Algebraic addition • X-Y Operation • Screen 8x10cm • 2kV

HM 312 £220
Y: Bandwidth DC-20MHz (-3dB) • Sensitivity 5mV-20V/cm (±3%)
X: Timebase 0.2s-40ns/cm incl. x5 Magn. • Trig. 3Hz-30MHz (4mm)
Dual trace • X-Y Operation • Calibrator • Screen 8x10cm • 2kV

HM 412 £350
Y: Bandwidth DC-20MHz (-3dB) • Sensitivity 2mV-20V/cm (±3%)
X: Timebase 2s-40ns/cm incl. x5 Magn. • Trig. DC-40MHz (5mm)
Dual trace • Algebr. addition • X-Y Operation • Screen 8x10cm
Sweep delay • Overscan, Trigger, Delay indications • Trigger filter
Z-Modulation • Calibrator • Graticule illumination • 2kV

HM 512 £580
Y: Bandwidth DC-50MHz (-3dB) • Sensitivity 5mV-50V/cm (±3%)
X: Timebase 5s-20ns/cm incl. x5 Magn. • Trig. DC-70MHz (5mm)
Dual trace • Algebr. addition • X-Y Operation • Screen 8x10cm
Delay line • Sweep delay • After delay triggering • Trigger filter
Single shot • Reset • Overscan, Trigger, Ready, Delay indications
var. Hold-off • Z-Modulation • Graticule illumination • 12kV

HM 812 £1,458
Y: Bandwidth DC-50MHz (-3dB) • Sensitivity 5mV-50V/div. (±3%)
X: Timebase 5s-20ns/div. incl. x5 Magn. • Trig. DC-70MHz (0.5 div.)
Dual trace analog storage with var. Persistence and Auto-Storage
Algebr. addition • X-Y Operation • Screen 8x10div. (7.2x9cm)
Delay line • Sweep delay • After delay triggering • Trigger filter
Single shot • Overscan, Trigger, Ready, Delay, AS indications
var. Hold-off • Z-Modulation • X-Guard circuit • Calibrator • 8.5kV



HM 812
Storage

For more information contact: **HAMEG LTD.** 74-78 Collingdon Street, Luton Bedfordshire LU1 1RX Telephone (0582) 413174 Telex 825484

Prices U.K. List Ex. VAT

The ^{exciting} new name in Linear I/Cs

Analog Systems, the fast growing linear I/C company of Arizona whose products are available from Pascall, offer a wide range of high performance linear integrated circuits.

Hi-Speed Amplifiers

- MA 207 - 1.5 GHz gain-bandwidth product. ± 800 V/μS slew rate.
- MA 401 ± 225 V/μS slew rate ± 20V swing.
- MA 324 ± 130 V/μS slew rate, 450 MHz gain-bandwidth product.
- MA 326-350 MHz gain-bandwidth product. 400ns settling time.

ANALOG SYSTEMS

Pascall

Send for full product listings of Analog Systems exciting product range

Pascall Electronics Limited, Hawke House, Green Street, Sunbury-on-Thames, Middlesex TW16 6RA Telephone: (09327) 87418 Telex: 8814536

Def Stan 05-31/BS9000/CECC approved

WW — 012 FOR FURTHER DETAILS

New KONTAKT Sprays



for the Electronics & Electrical Industries

KALTRON 601

A new cleaner for Magnetic Recording Units. Kaltron 601 has an extremely low surface tension thereby enabling the cleaning of magnetic sound heads leaving no deposit or other traces.

It is chemically pure (99.8%) — non conductive — non-flammable.

It can be used on energised electrical installations and electronic equipment, e.g. video units, tape recorders, data processing systems etc.

Also NEW

PRINTER 66

Spray cleaner for type wheel printers, matrix printers and chain printers. Can also be used for cleaning normal typewriters.

SCREEN 99

Specially for the cleaning of all types of screens, including data terminals and T.V. Screens.

VASELINE SPRAY 701

For use in communications engineering and construction of antennae. Proved successful as corrosion inhibitor for cable clamps, connecting screw joints etc. Application from spray can with capillary tube is clean and simple. Distributed by:

Special Products Distributors Ltd.
81 Piccadilly, London, W1V 0HL

Tel: 01-629 9556 : Cables: Speciproduct, London, W.1
Telex: 265200 (answerback RACEN)

WW — 025 FOR FURTHER DETAILS




**WE CUT THE PRICE.
WE CUT THE SIZE.
WE LEFT THE OMRON QUALITY.**

IMO can now offer you the high quality and reliability that you have come to expect in Omron relays, in their new series of low profile, printed circuit mounting subminiatures.

There's a tremendous range for every interface, communication and output application, suitable for mounting with sockets or directly onto printed circuit boards. There are low cost types like the LC1-NE, where price is a major consideration, and high reliability types like the LZN's with gold-clad, bifurcated crossbar contacts and card lift-off operation.

With contact ratings up to 10A and 240VAC and down to 10μA, all in a variety of housing styles and sizes, and up to four changeover contacts per relay, this range from IMO offers

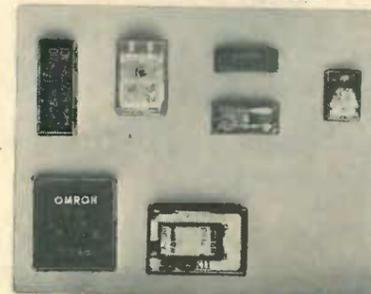you real design flexibility. All usual AC and DC coil voltages are available from stock.



With the increased requirement for complete reliability in electronic circuitry, you'll need relays at the right price and the highest quality.

In a word, Omron—from IMO.

IMO
Much more than you may know

IMO Precision Controls Ltd.,
349 Edgware Road, London W2 1BS.
Tel: 01-723 2251/4 or 01-402 7333/6.

HERE IT IS! THE BRAND NEW 8022A HAND-HELD DMM

Consider the following features:
 6 resistance ranges from 200 ohm-20 ohms
 8 current ranges from 2mA-2A AC/DC
 10 voltage ranges from 200 mv-1000v DC-200 mc-750V AC
 Pocket size — weighing only 370 gms.
 Full overload protection — will withstand 6kv spikes
 Rugged construction — virtually indestructible
 Meets tough military specs — drop proof
 In line, pushbutton operation for single-handed useage
 Incorporates low power CMOS chip for low power consumption
 All this plus a 2-year full guarantee



For only £75 + VAT SOFT CARRYING CASE £7 extra
 Carriage and Insurance £3

Even more sophisticated the Fluke 8020A
 Identical in most respects to the 8022A but in addition incorporates a conductance range from 2mS-200nS.

Price £125

Carriage and insurance £3.00

A handsome soft carrying case is included (this model only)



DIGITAL MULTIMETERS BRAND NEW FROM FLUKE!!! NOW AVAILABLE THE 8024A HAND HELD DMM

This model incorporates all the features of the 8020A but in addition has:
 A peak hold switch which can be used in AC or DC for volts and current functions.
 Audible continuity testing and level detection for sensing logic levels.
 A temperature (°C) range for use with a thermocouple.

£149

Carriage and Insurance £3

The following accessories are in stock now

Y8008 Touch and Hold Probe	£18.00
80K-40 High Voltage Probe	£45.00
81RF RF Probe to 100 MHz	£32.00
80T-150C Temperature Probe (C)	£55.00
801-600 Clamp-on AC Current Probe	£85.00



8010A AND 8012A BENCH MODEL D.M.M.s

The 8010A is a general purpose, bench/portable digital multimeter with more functions and features than ever offered for such a low price. Its companion, the 8012A, has identical characteristics except that it has two additional low resistance ranges, 20 and 200. The 8010A and 8012A feature:
 10 voltage ranges from 200mv - 1000v dc, 200mv - 75v ac.
 3 conductance ranges from 2mS - 200 nS.
 8 resistance ranges from 2000 - 20mΩ - the 8012A has two additional resistance ranges 20 and 200.
 10 current ranges from 200µA - 2A AC/DC — the 8010A has two additional current ranges 10A AC and 10A DC.

8010A £159 8012A £199

Carriage and Insurance £3

*The 8010A is also available with two rechargeable Nicad size C batteries installed in option 01 at £179.00.

LOW COST, AUTORANGING MULTI-FUNCTION COUNTER MODEL 1900A


- Autoranging in both frequency and period measurement modes
- Wide Frequency range — 5 Hz to 80 MHz
- High sensitivity — 25 mV, typically 15 mV
- Six digit LED display with leading zero suppression, automatic annunciation and overflow
- Optional internal battery pack providing 4 hours continuous operation
- Autostop on all gate times, all function switches
- Four manually selected gate times providing resolution to 0.1 Hz
- Event counting to 10⁶ events with overflow indicator
- Signal input conditioning with switchable 1 MHz low pass filter and attenuator
- Rugged moulded case with convenient tilting/carrying handle
- Optional parallel data output with decimal point and annunciation
- Traditional high Fluke quality
- Self check

£235 Carriage and Insurance £3



Y7206 EN 20,000 OPV
 AC Volts: 0-10, 50, 250, 500, 1000
 DC Volts: 0-0.5, 5, 25, 125, 250, 500, 1000
 DC Current: 0-0.05, 0.5, 250 mA

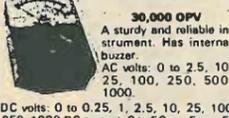Resistance: 0-3k ohms, 300k ohms, 3 meg ohms
 Decibels: -20 to +63 db
 Dims: 127 x 90 x 32 mm
£10.95 P & P 75p



TMK500 30,000 OPV
 A sturdy and reliable instrument. Has internal buzzer.
 AC volts: 0 to 2.5, 10, 25, 100, 250, 500, 1000.
 DC volts: 0 to 0.25, 1, 2.5, 10, 25, 100, 250, 1000. DC current: 0 to 50 uA, 5 mA, 50 mA, 12 amp.
 Resistance: 0 to 6K, 60K, 6 meg, 60 meg.
 Decibels: -20 to +56 db.
 Short test: Internal buzzer.
 Size: 160 x 110 x 55 mm.
£20.50, P & P 75p

PLEASE ADD 15% VAT TO ALL ORDERS EXCEPT WHERE ITEMS MARKED "VAT INCLUDED." CALLERS WELCOME
 We are open 9 a.m.-6 p.m. Monday-Saturday
 We carry a very large selection of electronic components and electro-mechanical items.
 Special quotations on quantities



PLESSEY 30-way, 2 bank
 Single pole. Contacts 1 amp 240v. AC/DC. 0050 res. Make before break. Stop infinitely adjustable allowing for any desired arc of travel. Ideal for instrument and model switching. Size 2 1/4" dia. overall x 2 1/4" deep plus 1 1/4" x 1/4" dia. spindle.
£3.25 P & P 50p



BENDIX MAGNETIC C. 17CH
 Superb example of electro-mechanics. Main body in two sections, coil section fixed with 3/8" sleeve, drive section rotating on outer penmeter. Uniting plate has 1/8" ID bearing concentric with main section and 18-tooth cog wheel. Extremely powerful transmission. 24V D.C. 240 m/a.
£4.75, P & P 75p

ELECTRO-TECH COMPONENTS LTD.

364 EDGWARE ROAD, LONDON, W.2. TEL: 01-723 5667

INSTRUMENT CASES AND BOXES



Zaerix Electronics Limited

46 Westbourne Grove
 London, W2 5SF

PROFESSIONAL QUALITY

Desk consoles, instrument cases and boxes which feature anodised aluminium extrusions and panels, with integral facilities to mount sub chassis and PCBs.

Telex: 261306
 Tel: 01-221 3642



WW - 041 FOR FURTHER DETAILS



Reality as seen by your ears

The sound of Spondor speakers has to be compared with the sound of live music to really appreciate its quality. It is the reality of reproduction that has made Spondor one of the most respected manufacturers of speaker systems in the country. The construction and finish too is the envy of any craftsman.

The Spondor Company is a self-contained unit of highly talented audio engineers who put quality before quantity. Currently over 2,000 Spondor speakers are used by professionals like the British Broadcasting Corporation, The I.B.A., W.D.R. Cologne and other selective organisations.

Reality as seen by your ears? Compare Spondor sound with live sound and see for yourself.

spondor
 Sound engineering


Spondor Audio Systems Ltd.,
 Station Road Industrial Estate,
 Hailsham, Sussex BN27 2ER
 Tel: Hailsham 843474

WW - 026 FOR FURTHER DETAILS

CS1830 FROM TRIO

Since its introduction, the CS1830 has been our top seller, and no wonder, when you glance at the comprehensive specification and the extremely attractive price which includes two matching X1/X10 probes. Add to that the fact that we can normally supply from stock and you have a winner. Some of the details are listed here but if you need further information, just contact us and we'll be happy to assist.

- C.R.T.:**
120 x 96 mm rectangular PDA with internal graticule
- Y Bandwidth:**
DC - 30MHz
- Sensitivity:**
5mV/div (30MHz)
2mV/div (20MHz)
- Input RC:**
1M/23pF
- Risetime:** 11.7ns
- Beam Switch:**
Chop/alternate
- Modes:**
CH1, CH2, Dual, Add, Subtract
- Time Base:**
Triggered, auto, or single shot
- Sweep Time:**
0.5S/div-200ns/div (40ns using X5 mag) 20 ranges in 1-2-5 sequence
- Sweep Delay:**
100ms-1µs adjustable with trace bright up for delay location
- Z Modulation:**
TTL compatible 10K impedance 5MHz bandwidth
- Trace Rotation:**
Electrical
- And the Price?**
£455 + VAT (includes 2 probes)

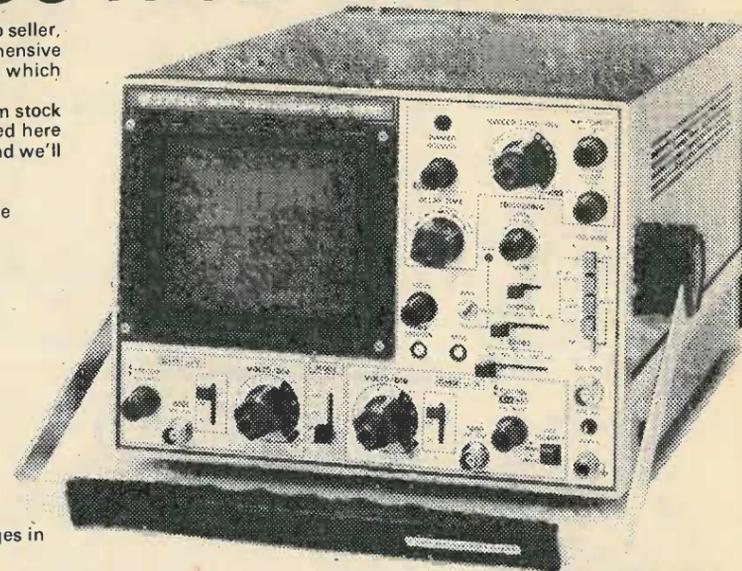

Also
CS1577A
Dual 30MHz/2mV Signal
Delay etc
£410 + VAT



NRD-515 receiving for the discerning few.



- NRD 515 SYNTHESISED HF MONITORING RECEIVER **£948.75 inc. VAT**
- NHD 515 MULTICHANNEL MEMORY UNIT **£161.00 inc. VAT**
- NVA 515 LOUDSPEAKER UNIT **£27.60 inc. VAT**
- CFL 260 600Hz CW FILTER **£34.50 inc. VAT**

The NRD 515 is a PLL-synthesised communications receiver of the highest class featuring advanced radio technology combined with the latest digital techniques. The new NRD 515 is full of performance advantages including general coverage, all modes of operation, PLL digital VFO for digital tuning, 24-channel frequency memory (option), direct mixing pass-band tuning, etc. JRC's 65 years of radio communications experience will give you "the world at your fingertips". The NRD 515 is but a single item from the JRC product range which extends all the way to full marine radio installations for supertankers.

LOWE ELECTRONICS Ltd.
CHESTERFIELD ROAD, MATLOCK, DERBYSHIRE DE4 5LE

TEL. 0629 2430/2817

WW - 046 FOR FURTHER DETAILS

- ORDER BY POST OR TELEPHONE WITH BARCLAYCARD/ACCESS
- ELECTRONIC TEST EQUIPMENT SPECIALISTS
- ALL PRICES INCLUDE VAT


AUDIO ELECTRONICS

- ALL MODELS ON DISPLAY
- RETAIL - MAIL ORDER - EXPORT - INDUSTRIAL
- OPEN SIX DAYS A WEEK
- CALL IN AND SEE FOR YOURSELF

ALL PRICES INCLUDE VAT

SCOPES

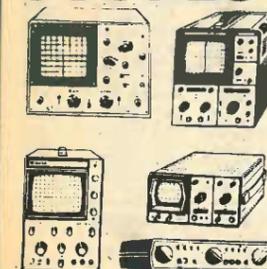A range of Scopes in stock from 5mHZ Single Trace to 50mHZ Dualtrace. Mains and Battery / Mains portables. Many on demonstration.



- SINGLE TRACE** (UK c/p etc £2.50)
- Hm 307-3 10mHZ, 5mV, 6 x 7 cm display plus component test **£158.78**
 - C01303D 5mHZ, 10mHZ, 7 x 7cm display **£109.25**
 - SC110 10mHZ Battery portable, 10mV 3.2 x 2.6cm display (Optional case) **£158.95**
 - HLB012A 10mHZ 10mV, 5" display **£195.00**
 - CS1559A 10mHZ 10mV, 5" display **£198.50**
 - W181 15mHZ 1mV 5" display **£241.50**
- *Price includes free Probe(s)
- OPTIONAL PROBES (ALL MODELS)**
X1 £8.50, X10 £8.50, X100 £12.95, X1-X10 £10.95
HAMEG ● TRIO ● SINCLAIR ● LEADER ● HITACHI

- DUAL TRACE** (UK c/p etc £3.50)
- CS156A 10mHZ, 10mV 5" display **£267.00**
 - CS1575 5mHZ 1mV 5" display **£284.00**
 - Hm 312-8 20mHZ, 5mV 10cm display **£253.00**
 - CS1566A 20mHZ, 5mV, 5" display **£339.00**
 - HLB03085 70mHZ, 2mV, 5 x 6.3cm display. Battery/mains. Portable built-in Nicads **£482.00**
 - HM412-4 20mHZ, 5mV, 8 x 10cm display plus Sweep Delay **£399.50**
 - CS1577A 35mHZ, 2mV, 5" display **£478.00**
 - CS1830 30mHZ, 2mV, 5" display plus sweep delay and delay line - new model **£569.00**
 - Hm 512-8 50mHZ, 5mV, 10 x 8cm display. Delay Sweep **£667.00**
 - HLB0514 10mHZ, 1mV, (5mV) 5" display **£294.00**
 - W182 15mHZ, 1mV, 5" display **£328.00**
 - W302 30mHZ, 1mV, 5" display **£447.35**
 - W550 50mHZ, 1mV, 10 x 8cm Delay sweep + 3 channel display **£799.25**

GENERATORS



- SG402** 100 KHZ 30mHZ with AM modulation **£68.00**
- LSG16** 100KHZ (300mHZ on Harmonics) **£63.25**
- LSG231** 100m HZ 1mHZ (adjustable) FM stereo generator, pilot and mod **£195.00**
- PULSE**
- 2001 1HZ 100KHZ (function) **£89.70**
 - TG105 5HZ 5mHZ **£92.50**
 - 4001 0.5HZ 5mHZ **£109.25**
 - 200P 0.00 2HZ 5.5mHZ **£253.00**
 - 200SPC as 200P plus built-in freq. display/100mHZ counter **£437.00**
 - TT100 (Function 10KHZ) **£90.85**
- AUDIO** (All sine/square)
- AG202A 20HZ-200KHZ **£69.00**
 - LAG26 20HZ-200KHZ **£73.60**
 - AG203 10HZ-1mHZ sine/sq **£126.50**
 - LAG120A 10HZ-1mHZ **£146.00**
- Also in stock range of Protoboard kits and breadboards.

- 'PRO' MULTIMETERS** (UK c/p £1.20)
- M1200 100K/Volt 30 ranges plus AC/DC 15 amp **£87.00**
 - K1400 20K/Volt 23 range large scale **£79.95**
 - M1500 20K/Volt 42 range plus AC/DC 10 amp **£53.50**
 - K200 38 range FET 10m OHM input 20Hz to 30MHz multimeter **£95.00**


SWR/FS AND POWER METERS

- Range in stock covering up to 150mHZ and up to 1K watt power PL259 sockets. Also 250 UHZ Grid Dipmeter. **SWR9 SWR/S 3-150mHZ £69.50**
- SWR6 SWR/Power meter.** 3½-150mHZ 0-1000 watts **£13.95**
- 110 SWR/Power 1½-144mHZ 0/10/100 watts **£11.50**
 - 171 As 110 Twin meter plus E/S **£14.50**
- Plus large range of BNC/PL259/ etc leads plus adaptors/connectors always in stock.
- 176 SWR/Power/FS 1½-144mHZ 5-50 watt plus 25-40mHZ ac match **£18.60**
 - KDM6 Gnd Dip 1½-250mHZ **£38.50**

- LOGIC PROBES/ MONITORS**
- Logic probes indicating high/low, etc., states that scopes can miss. All circuit powered for all ICs.
- LP3 50 MHz logic probe **£55.95**
 - LP1 10 MHz logic probe **£35.50**
 - LP2 1½ MHz logic probe **£19.95**
 - LM1 Logic monitor **£33.00**
 - LDP076 50 MHz logic probe with case **£51.00**

LEADER ● TRIO ● NEWTRONICS ● LEVELL

DIGITAL MULTIMETERS

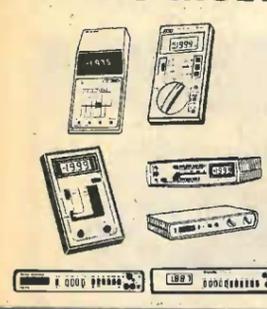

- A range of LED and LCD Bench and Hand DMM's battery operated with optional Mains Adaptors - some with optional Nicads. All supplied with batteries and leads.
- HAND HELD** (UK post etc 85p)
- GL35C 3½ Digit LCD in AC/DC with case **£37.50**
 - TM352 3½ Digit LCD plus 10A DC and Hfe checker **£54.95**
 - ME502 3½ Digit LED plus 10A DC and Hfe checker **£43.95**
 - LM2001 3½ Digit LCD 2 amp AC/DC 0.1% **£51.70**
 - 6200 3½ Digit LCD 0.2A AC/DC. Auto range **£45.95**
 - 6220 As 6200 plus 10A AC/DC **£55.95**
 - 6100 As 6200 plus Cont. test/range hold **£69.95**
 - 6110 As 6100 plus 10A AC/DC **£85.95**
 - TM354 3½ Digit LCD 2A DC with case **£45.95**
- BENCH PORTABLES** (UK c/p £1)
- DM235 3½ Digit LED 21 ranges, 0.5% AC/DC 2A **£60.38**
 - DM350 3½ Digit LED 34 ranges AC/DC 10A **£83.38**
 - TM353 3½ Digit LCD AC/DC 2 amp **£96.60**
 - TM351 3½ Digit LCD AC/DC 10 amp **£113.85**
 - LM100 3½ Digit LCD AC/DC 2 amp **£86.50**
 - DM450 4½ Digit LED 34 ranges AC/DC 10 amp **£113.85**
- (DM series options. Carry case £8.86 Ni-cads £8.63 Mains adaptor £4)
- 1503 4½ Digit LCD 28 range AC/DC 10 amp includes mains adaptor **£159.95**

MULTIMETERS (UK c/p 75p)

- KRT101 1K/Volt 10 range pocket **£4.60**
- ATM1/LT1 1K/Volt 12 range pocket **£5.98**
- NH55 2K/Volt 10 range pocket **£6.50**
- ATI 2K/Volt 12 range pocket de luxe **£7.75**
- NH56 20K/Volt 22 range pocket **£11.95**
- YN360TR 20K/Volt 19 range pocket plus hfe test **£13.50**
- AT1020 20K/Volt 19 range de luxe plus hfe test **£16.95**
- 7081 50K/Volt 36 range plus 10 amp DC **£20.80**
- TR303TR 20K/Volt plus 12A DC plus hfe test **£15.95**
- AT20 20K/Volt 21 range de luxe plus 10A DC and 5KV DC **£21.95**
- AT205 50K/Volt 21 range de luxe plus 10A DC **£24.95**
- 7080 20K/Volt 26 range large scale, 10A DC plus 5KV AC/DC **£26.95**
- AT2050 50K/Volt 18 range de luxe plus hfe test **£28.50**
- AT210 100K/Volt 21 range de luxe 12A AC/DC **£29.95**
- 360TR 100K/Volt 23 range plus hfe checker and AC/DC 10 amps **£34.95**

FREQUENCY COUNTERS



- Portable and Bench LCD and LED Counters up to 600mHZ. Prices include batteries and leads.
- HAND HELD** (UK post etc 85p)
- PFM200 20HZ to 200mHZ 8 Digit LED **£52.27**
 - MAX50 100HZ to 50mHZ 6 Digit LED **£61.00**
 - MAX550 30KHZ to 550mHZ 6 Digit LED **£106.00**
- BENCH PORTABLES** (UK c/p £1)
- MAX100 8 Digit LED-5HZ to 100mHZ **£89.00**
 - TF200 8 Digit LCD 10HZ to 200mHZ **£166.75**
 - 7010A 9 Digit LED 10HZ to 600mHZ **£169.00**
 - TP600 600mHZ Pre-Scaler for TF200 **£43.13**
 - 200SPC 6 Digit 100mHZ LED built into 0.002HZ to 5.5 MHz Pulse Generator **£437.00**
 - TF040 8 Digit LCD 20mHZ **£126.50**

CLAMP METERS/ INSULATION TESTERS

(All multirange except K2303)

- K2303 30 AMPS 500 VAC **£21.95**
 - 3101 300 AMPS 600 VAC 1K OHM **£32.95**
 - K2803 300 AMPS 600VAC 2K OHM **£53.95**
 - K2903 900 AMPS 750 VAC 2K OHM **£77.95**
 - K3103 Transistorised insulation/continuity tester. 100 MEG. 600 VAC 0.2½K **£95.00**
 - M500 Insulation tester 100 MEG. 500VOLT. 0/200 OHMS continuity **£87.50**
- Also digital and DC types in stock

CHOOSE FROM UK'S LARGEST SELECTION

- TV GENERATORS**
- LCG-393V PAL 8VHF 6 patts **£137.00**
 - SCG-392U **£217.00**
 - PAL B UHF 15 patts **£217.00**

CSC ● SINCLAIR ● OPTOELECTRONICS ● NEWTRONICS

Stockists of electronic equipment, speakers/kits, PA equipment plus huge range of accessories ● UK carriage/packing as indicated ● Export - prices on request ● All prices correct at 1.2.81 E & OE ● All prices include VAT

AUDIO ELECTRONICS Cubegate Limited
301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TELEPHONE 01-724 3564

OPEN SIX DAYS A WEEK

FREE CATALOGUE!

Send large SAE (20p UK) Schools, Companies, etc. free on request.

WW - 009 FOR FURTHER DETAILS

PM COMPONENTS LTD. VALVE & COMPONENTS SPECIALISTS

Table listing various electronic components including Semiconductors, I.C.s, Diodes, New Branded Valves, Video Tapes, and Wound Resistors. Includes part numbers, descriptions, and prices.

WW - 045 FOR FURTHER DETAILS

a special 24-page supplement in Elektor

THE 16-BIT PROCESSOR

The new generation of 16-bit microprocessor systems can equal or even better the performance of present day minicomputers. This means that a 'real' computer is now within the reach of any enthusiast.

The April issue of Elektor contains a special 24 page supplement giving a brief survey of the field, concentrating in particular on the following types:

Table listing manufacturers (Intel, Motorola, National Semiconductor, Texas Instruments, Zilog) and their corresponding processor types (8086, 68000, 16000 family, 9900, 8001).

Comparisons are given of the basic capabilities, register sets, addressing modes, instruction sets, memory maps and support chips. The article has been checked for technical accuracy by specialists from the respective manufacturers.

elektor


April issue on sale now, price 60p. Or direct from address below, price 80p (inc. 20p P&P) Elektor Publishers Ltd., 10 Longport, Canterbury, Kent CT1 1PE. Tel. (0227) 54439/0

WW - 029 FOR FURTHER DETAILS


Chokes, block filters, ceramic filters, resonators, IFTs, oscillator coils, audio filter blocks etc.

LOW PASS FILTERS

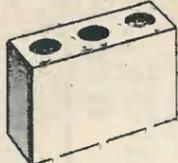Now from 10kHz to 20MHz TOKO's recently expanded LPF series covers from the audio spectrum through to 20MHz in a series of LPFs for mpX, video, radio etc.



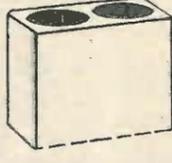The LPFs are based on 7&10mm formats with up to 4 LC tuned elements per block. Many stock types available.



HELICAL FILTERS 2 & 3 elements available for VHF and UHF:



Featuring low insertion losses, -80dB at the +/- 21.4MHz points. Ask for details.


CERAMIC RESONATORS & PIEZO SOUNDERS



Audio buzzers now down to 1kHz - low cost 400-600kHz crystal replacements for MPUs, RCs etc. Low cost - wide range.

VIDEO FRAME STORES

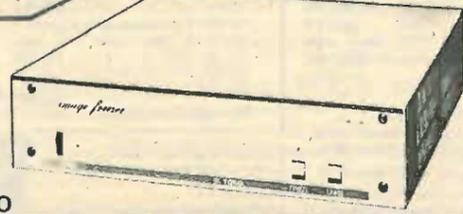- ★ 525/625 operation
★ 512 pixell/line
★ Local or remote control
★ Top/bottom & L/R reverse
★ Models available with digitized I/O



Video frame stores are a new addition to TOKO's memory product range. They permit easy analysis of low dose X-Ray pictures, digital processing of picture information (including the VFM10D with 8" disk drive) with much better resolution than available from VTR

TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

AMBIT international 200 North Service Road, Brentwood, Essex

WW - 049 FOR FURTHER DETAILS

Large table listing various electronic components including Linear ICs, Crystals, Radio Control, and Micromarkets. Includes part numbers, descriptions, and prices.

ALL PRICES EXCLUDE VAT - CURRENTLY AT 15% POSTAGE 50p ORDERS UNDER £12 - FREE OVER £12 Terms and conditions of sale: CWO please, MA available for schools, colleges, industrial users etc. Please ask for details. ACCESS/BARCLAYCARD may be used for mail or phone orders (Mastercharge/Visa overseas). Please add enough for overseas airtel (inc catalogues pse) since the airmail rates have been dramatically increased in January.

AMBIT international 200 North Service Road, Brentwood, Essex

WW - 050 FOR FURTHER DETAILS

Carston Electronics



Category	Model	Price from £
Bridges	GENRAD GR1657 Digitbridge LCR, auto, LED display	850
	CINTEL 277 Measures iron core inductances 0.01H-1000H (with a Q value not less than 2)	130
HEWLETT PACKARD	4342A "Q" Meter QLC complete	1250
	MARCONI TF868A Universal Bridge	250
WAYNE KERR	8224 Wide range LCR Bridge	475
	8500 Log LCR Bridge	225
HEWLETT PACKARD	8601 RF LCR Bridge (Detector and Oscillator not incl.)	125
	8641. Measures L/C/R/G Accuracy of 0.1%	450
Cable Test Equipment	MARCONI TF2333 Transmission Test set	575
	HEWLETT PACKARD 3566A For psophometric measurements from 20 Hz-20kHz. 0.1mV-30V input level	475
NEC	TTS-37B Noise, level and VU measurement. Sensitivity -80dBm up to +20dBm	275
	STC 74216A Noise Generator CCITT	240
TEKTRONIX	1502 Portable TDR Cable Tester	2,725
	WANDEL u. GOLTERMANN DLM-1. Send/receive system	1500
GAY	LDM Records +ve/-ve transients of 50ns on AC or DC Lines	1250
	LDEF-2. Filters for DLM unit	250
Counter Timers	HEWLETT PACKARD 5300A/5303B DC-520 MHz 6 digits	210
	5300A Display Module. 6 Digits. 3 x 10 ⁷	90
RACAL	5302A DC-50 MHz. 100mV sens. Time interval. Period. Ratio. Totalise.	75
	5303B DC-520 MHz (Plug-on) 125mV sens. 50Ω	120
SYSTRON DONNER	6053 9 Digit 20 Hz-3 GHz BCD O/P	850

Category	Model	Price from £
Function Generators	6054A/04 11 Digit 20 kHz-18 GHz BCD O/P	2800
	INTER-STATE ELECTRONICS F51A Multi-Mode + and - offset: 0.0005 Hz to 10 MHz. 10/15V/50Ω	250
PHILIPS	PM5127. 0.1 Hz-1 MHz. Sine/Square/Triangular/Pulse outputs. External sweep facility 30Vp. p max output	325
	HEWLETT PACKARD 1601L Logic state analyser 12 channel display	250
Mains Monitors	1600A 16 channel 20 MHz clock MAP A & B store	1850
	1607 16 channel 20 MHz clock (Display scope required)	1500
DATA LAB	DL019 Power line interface for transient recording	350
	DL905 Digital Storage Unit DC-3 MHz 10mV	1055
DRANETZ	606-3 Disturbance Analyser Avg. Sag/Surge	2625
	606-4 Disturbance Analyser Avg. Sag/Surge	2625
Modulation Meters	AIRMEC 409 3-1500 MHz. AM/FM	295
	MARCONI TF2300A 1-1000 MHz. AM/FM	450

Category	Model	Price from £
Oscilloscopes	ADVANCE OS1000A DC-20 MHz. dual trace	200
	3300B Dual Trace DC-50 MHz 5mV/div. Dual Timebase	600
HEWLETT PACKARD	1703A Storage 1000Div/ms. DC-35 MHz. Dual trace Mains/Ext DC	1200
	1703A Storage 1000Div/ms DC-100 MHz Main frame only	650
MEDELEC	M-scope 4 channel DC-100 kHz U/V Chart	1650
	PHILIPS PM3211 DC-15 MHz Dual Trace 2mV	425
TEKTRONIX	475 Dual Trace DC-200 MHz 2mV	1125
	485 Dual Trace DC-350 MHz 50Ω 1 MΩ 250 MHz	2100
FLUKE	545B/1A1. DC-30 MHz. dual trace. Delayed timebase	325
	585A/82. DC-80 MHz. dual trace 10 mV sensitivity	525
ITT	547/1A4. DC-50 MHz. four trace	625
	7403N DC-60 MHz 3 Plug-in Mainframe	450
TELEQUIPMENT	7704A DC-200 MHz. CRT Readout. Mainframe for 4 Plug-in	1200
	D34 Dual Trace DC-15 MHz 2mV Mains/Batt	525
HEWLETT PACKARD	D75 Dual Trace DC-50 MHz Dual Timebase	600
	D83 DC-50 MHz. Dual trace. Large 6 1/2" CRT. Dual Time Base	650
HEWLETT PACKARD	1804A DC-50 MHz Four channel 20 mV-10V/div.	575
	TEKTRONIX 465 DC-100 MHz Dual Trace 5mV-5V. Div 0.05μs-0.5s. Div Delayed	£1250
TEKTRONIX	475A DC-250 MHz Dual Trace 5mV-5V. Div 0.01μs-0.5s. Div Delayed	£1950
	T B XY DC 4 MHz	£1250

As New Ex Stock delivery

OSCILLOSCOPES

These instruments sold with **ONE YEAR FULL GUARANTEE**

Model	Price from £
1825A Dual Timebase 50ns-1s/div.	525
1805A Dual Trace DC-100 MHz 5mV. 1MΩ/50Ω	550
TEKTRONIX	
Type R. Transistor R.T. tester. Pulse rate 120 pulses/sec. R.T. Less than 5 μs	100
Type G. Differential amplifier. 100:1 CMR DC-20 MHz. 50 mV sensitivity	50
Plug-ins for 500 series	
1A1 dual trace Plug-in DC-50 MHz	225
1A2 dual trace Plug-in DC-50 MHz	180
1A4 four trace Plug-in DC-50 MHz	375
1A5 Differential Plug-in	175
Z Differential Plug-in	140
81 Adaptor Plug-in 1A Series to 580 Series	75
7A12 Dual Trace DC-105 MHz 5mV/div.	410
7A22 High gain diff. amp. 0.1 Hz-1 MHz 10μV	450
7A26 Dual Trace DC-150 MHz 5mV-5V/div.	525
7B53A Dual Timebase 5ns-5s/div.	550
Oscilloscopes (storage)	
TEKTRONIX 549/1A1. DC-30 MHz. 5mV sensitivity. Dual trace. Storage scope. Writing speed: 5cm/μs with enhancement. Includes trolley	675
564B/3A8/2B67. DC-10 MHz. Dual trace 10mV sensitivity. split screen storage oscilloscope	750
466 Storage 1350 cm/μs Variable Persist DC-100 MHz	2225
7313 Split screen 4.9 cm/μs. DC-25 MHz (M/F for 3 Plug-ins)	1650
Phase Meter	
DRANETZ 301A 1 Hz-500 kHz. Z in 100kΩ. Accuracy ±1° to ±2°. Analogue O/P	400
Power Meters	
DYMAR 2081/100 True RMS. DC-500 MHz. 30mW-100W	425
HEWLETT PACKARD 478A Thermistor Mount for 432A	90
435A 0.3μW to 100mW 5 MHz-18GHz	475
8481A Power Sensor for 435A	200
MARCONI SANDERS	
6460 10 MHz-40 GHz (Depending on Head)	300
6420 10 MHz-12.4 GHz 10mW	110
MARCONI	
TF2512 DC-500 MHz 0.5-30w 50Ω	130
TF893A 10 Hz-20 kHz. 20μW-10W.	120
Power Supplies	
BRANDENBURG 475R 10-2100V 5mA DC Stab.	150
FARNELL L30B 0-30V 1A DC Stab.	55
FLUKE 415B 0-3100V 30mA 0.005% reg. Protected	350
ITT Power Lab. up to 30V Dual Supply	90
MARCONI	
TF2154/1 0-30V 1A. 0-15V 2A 0-7.5V 4A	60
SMITHS	
4701 5-7V o/p Power Pack	32
SORENSEN	
DCR 300-2.5 0-300V 2.5A DC Stab.	375
Pulse Generators	
DB ELECTRONICS 150. I.C. pulse generator	50
EH RESEARCH	
122. 1 kHz-200 MHz 5V/50Ω	220
RT 12ns	220
139(L). 10Hz-50 MHz 10V/50Ω	175
RT 5ns	175
1221. Timing Unit 6 Channel 0-10 MHz 5V/50Ω RT 8ns	50
HEWLETT PACKARD	
214A 100V/50Ω. Double pulse O/P. W50ns-10ms. 10 Hz-1 MHz. 15ns RT	350
MARCONI	
TF2025 0.2 Hz-25 MHz ±10V/50V RT 7ns	350
Recorders and Signal Conditioning Equipment	
AMPEX PR2200 Instrumentation Recorder up to 16 channels. FM/DR. Record replay all speeds. 1" tape FM/DR I.R.I.G. DC-40 kHz FM. 100 Hz-300 kHz DR	6500
BRUNO WOELKE	
ME102B. Wow and flutter meter	75
ME102C. Wow and flutter meter	90

Bigger stock investment greater equipment range means wider choice

Model	Price from £
BRYANS SOUTHERN	
BS314 4 channel 1mV-10V 16 speeds	1650
BS318 6 channel 1mV-10V 16 speeds	2350
HEWLETT PACKARD	
680M. 5 inch. Stripchart Single Pen 5mV-120V I/P 20cm/min 2.5 cm/hr	275
7046A Two pen A3 0.25mV-5V/cm	995
KUDELSKI	
Nagra 4.2 LSP Professional Audio Recorder (Batt opt)	1215
PHILIPS	
PM 8251 Single pen 10in chart 10mV-50V FS	450
RACAL	
Store 4. Uses D/4 inch magnetic tape. Will record 4 F.M. channels. Operates at 7 different speeds.	1875
S E LABORATORIES	
6150/6151 12 channel UV 1250 mm/s-25 mm/min 6 in chart 994 6 Channel Pre-Amp ±1% ±1V o/p	1400
6008 25 Channel μV B in 4m/sec to 25mm/min	450
SMITHS INDUSTRIES	
RES41.20 Single Pen. 0.5mV-100V FSD. 3-60cm/min and hour	895
YOKOGAWA	
3046. 10 inch Chart Single Pen. 0.5 mV-100 V I/P 2.60cm/min and/hr	350
3047. 2 Pen Version of 3046	425
Signal Sources and Generators	
BOONTON	
102B 4.3-520 MHz Int/Ext FM/AM 0.1μV-1V 50Ω	1725

Model	Price from £
DYMAR	
1525 100 kHz-184 MHz Int/Ext AM/FM Batt/Mains	525
GENERAL RADIO	
1362 UHF. 220-920 MHz	450
GOULD ADVANCE	
SG70 5 Hz-125 kHz 600Ω 4w	85
HEWLETT PACKARD	
204D 5 Hz-1.2 MHz. 600Ω. 80dB att. O/P 5V RMS	150
620B 7-11 GHz 50Ω FM/PM 1mw	1100
8614A 800 MHz-2.4 GHz + 10dBm to -127 dBm 50Ω AM/FM	1950
8616A 1.8-4.5 GHz Ext AM/FM/PM 10 mw	925
MARCONI	
TF144 H/AS HF Generator 10 kHz-72 MHz AM	255
TF995A/2. 1.5-220 MHz AM. FM.	350
TF2171 Digital Synchroniser for TF2015	525
TF2002/AS 10 kHz-72 MHz FM/AM 0.1-1V o/p	625
TF2012 UHF. FM 400-520 MHz. 0.03μV. Counter o/p	650
TF2012 UHF. 400-520 MHz. FM	550
RACAL	
9081 5-520 MHz LED Display O/P - 130dBm AM/FM	1875
SCHAFFNER	
NSG330 Ignition Interference Attachment	150
NSG200B Mains Interference Simulator (Mainframe)	250
STC	
74216 Noise Generator 20 Hz-4 kHz Flat/CCITT Wtg	315

Model	Price from £
Spectrum Analysers	
HEWLETT PACKARD	
8443A Tracking Gene/counter 100 kHz-110 MHz	850
8445A Automatic pre-selector 10 MHz-18 GHz	1300
8555A RF Plug-in 10 MHz-18 GHz 1 kHz Res	3000
851B/8551B Display & RF Section	1,350
NELSON ROSS	
011. DC-20 kHz. 80dB dynamic range. Dispersion: 100 Hz-6 kHz	350
022. DC-100 kHz. Dynamic range 60dB fits into various 500 series CRO's	350
TEKTRONIX	
3L5. Plug-in unit fits into various 500B series CRO's. 50 Hz-1 MHz. Greater than 60dB dynamic range	475
Sweep Generators	
HEWLETT PACKARD	
8690B Mainframe. Int/Ext AM. Ext FM	600
8693B/100 3.7-8.3 GHz. 5mW. PIN levelled 'N' connectors	600
8699B/100 0.1-4 GHz. 6mW. (20mW to 2 GHz). PIN levelled. 'N' connectors	1200
TEXSCAN	
9900 Sweep Generator 10-30 MHz CRT Display	525
VS60 Sweep Generator 5-100 MHz Rate 60 Hz	950
TV Markers set of 5: 31.5, 32.5, 35, 39.5 & 41.5 MHz	195
LN40A Log Amplifier	105

Model	Price from £
Temperature Measuring Equipment (NB Thermocouples not incl.)	
COMARK	
1601BLS 87°C to 1000°C Type K Thermocouples	75
1604BLS -60°C to +170°C Type K Thermocouples	82
1625BLS -100°C to +300°C Type T Thermocouples	90
1642BLS -120°C to +800°C Type J Thermocouples	75
Voltmeters-Analogue	
AVO	
8 MK IV AC/DC V. AC/DC Amps. Ω	70
BOONTON	
92AD/01/09 10 kHz-1.2 GHz 1999 FSD 10μV Res	525
92C 10 kHz-1.2 GHz 500μV-3V. 1% of FS	350
HEWLETT PACKARD	
400E Millivoltmeter 10 Hz-10 MHz B/W 1mV FSS	99
427A. AC/DC/Ω multimeter	275
3406A. 10 kHz-1.2 GHz	345
3400A 10 Hz-10 MHz 1mV-300V True RMS	350
KEITHLEY	
610C Electrometer DC 1mV-100V. Amps 10 ⁻¹¹ Recorder o/p	350
LEVELL	
TM3B 5μV-500VAC 1 Hz-3 MHz + 50 to 100 dB	80
MARCONI	
TF2603 AC voltmeter to 1.5 GHz	300
PHILIPS	
PM2454B 1mV-300V 10 Hz 12 MHz 2 in 19MΩ. DC O/P	300
RACAL	
9301 RMS Millivoltmeter 10 kHz-1.5 GHz with carry case	475
Voltmeters-Digital	
ADVANCE	
DMM 7A/01 1999 FSD AC/DC/Ω/Current	115
FLUKE	
8000A 1999 FSD AC/DC/OHMS/Current	115
HEWLETT PACKARD	
34740A/34702A 9999 FSD AC/DC/OHMS	180
SOLARTRON	
LM1420-2. 2300 FSD DC only 0.05%	75
LM1420. 2BA. 2300 FSD AC True RMS/DC	110
A200. 19999 FSD DC only	160
A203. 19999 FSD AC/DC/Ω. Sensitivity: (1μV DC. 10μV AC. 100mΩ resistance)	300
A205. 19999 FSD AC/DC/Ω	300
A243. 119999 FSD AC/DC/Ω. Sensitivity: (1μV DC. 10μV AC. 10mΩ resistance)	325
7050. 99999 Auto AC/DC/Ω	350
Voltmeters Vector/Phase	
DRANETZ	
305B 9999 FSD Mainframe for PA 3001 module	575
HEWLETT PACKARD	
3490A 100000 FSD 1μV-1000V DC 0.01%	
10μV-1000V AC & Ω	625

ALL PRICES LISTED ARE EXCLUSIVE OF VAT (Standard Rate).

Prime Equipment

HEWLETT PACKARD	
8540B Precision AM-FM Signal-Generator	£3550
141T Spectrum Analyzer - Mainframe	£1300
8552B Spectrum Analyzer - IF Section	£2200
8553B Spectrum Analyzer - RF Section	£1650
8555A Spectrum Analyzer - RF Section	£4400
8556A Spectrum Analyzer - LF Section	£1650
8558B Spectrum Analyzer (for 180 Mainframe)	£2500
1600A 16 Channel Display Logic Analyzer	£2150
PHILIPS	
PM 3212 Dual Trace 25 MHz 2mV/Div Oscilloscope	£525
PM 3214 Dual Trace Dual Trace DC-25 MHz Oscilloscope	£625
RACAL	
9081 5-520 MHz Generator 130 dBm AM/FM	£1975
TEKTRONIX	
485 Dual Trace 350 MHz Oscilloscope	£2995
T912 Dual Trace Storage Oscilloscope	£699
DC-10 MHz 250 cm/ms writing speed	
7313 Storage Oscilloscope Mainframe 4.9 cm/μs writing speed DC-25 MHz	£1900
7A22 Differential Plug-in. As new DC-1 MHz 10μV-10V/Div (12 month guarantee)	£670
7A26 Dual Trace Plug-in. DC-150 MHz 5mV-5V/Div.	£780
7B53A Dual Timebase 5ns-5s/Div CRT Readout	£650

Carston Prime Equipment
brings you recent "State-of-the-Art" instruments
at competitive prices, with fast delivery (2-4 weeks). Every "Prime"
instrument carries the Carston 90 Day Full Guarantee covering parts and labour.

Carston Electronics

Contact: Noel Jennings
CARSTON ELECTRONICS LTD.
SHIRLEY HOUSE, 27 CAMDEN ROAD
LONDON NW1 9NR. Telex 23920


01-267 5311/2

WW - 019 FOR FURTHER DETAILS

PLEASE NOTE:
LISTED HERE IS ONLY A SELECTION OF OUR WIDE STOCK OF EQUIPMENT - FOR SPECIALIST NEEDS OR FOR DETAILS OF OUR FULL STANDARD RANGE OF EQUIPMENTS - RING US TODAY!

Redundant Test Equipment
Why not turn your under-utilized test equipment into cash? Ring us and we'll make you an offer.

Cushman

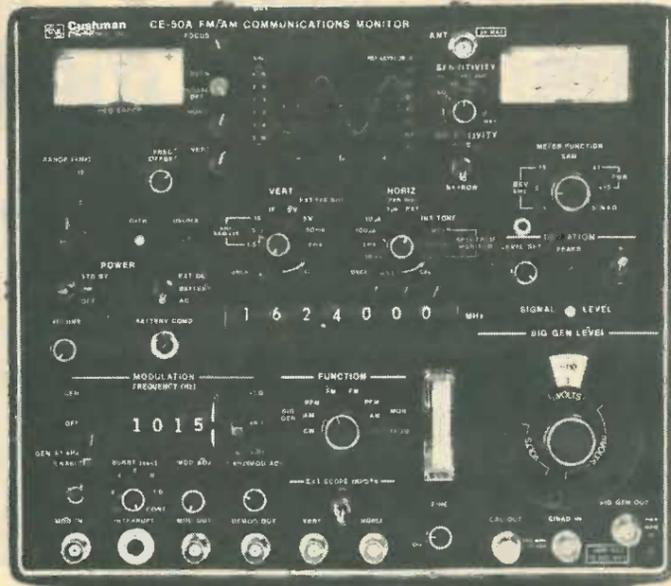

Compact, versatile field service monitors for two-way radio maintenance

**CE-50A: FM/AM Field Service Monitor
CE-50A-1: FM/AM Field Service-Spectrum Monitor**

Exclusive representative:

Aspen Electronics Limited

Communications Equipment and Components

2 Kildare Close, Eastcote, Ruislip, Middlesex HA4 9UR
Telephone: 01-868 1188
Telex: 8812727

WW - 034 FOR FURTHER DETAILS



NOW

DOUGLAS TRANSFORMERS FROM TITAN

NEW FRANCHISE AT FANTASTIC PRICES - EX STOCK

WE GUARANTEE THESE PRICES TO BE UNBEATABLE ANYWHERE !!

12/24V RANGE PRI 220/240V SEC. 0 12V 0V 12V				15/30V RANGE PRI 220/240V SEC. 0 12V 15V 0V 5V 8V 15V VOLTS AVAILABLE 3 → 15 → 0 → 15				25/50V RANGE PRI 120/220/240V SEC. 0 25V 50V 0V 25V 15V 15V VOLTS AVAILABLE 3 → 15 → 0 → 15				30/60V RANGE PRI 120/220/240V SEC. 0 30V 60V 0V 30V 30V 30V VOLTS AVAILABLE 3 → 15 → 0 → 15			
TYPE	AMPS	PRICE	P/P	TYPE	AMPS	PRICE	P/P	TYPE	AMPS	PRICE	P/P	TYPE	AMPS	PRICE	P/P
242	12v 24v	1.70	0.40	112	1 0.50	2.47	0.95	102	1.0 50v	2.88	1.43	124	1 0.5	2.92	1.43
213	0.3 0.15	2.32	0.70	79	2 1.0	3.16	0.95	126	2 1.0	3.60	1.43	127	4 2	7.13	1.73
71	2 1	2.51	0.90	3	4 2	5.64	1.43	104	4 2	7.04	1.73	125	6 3	10.73	1.90
18	4 2	3.24	1.43	20	6 3	6.59	1.73	105	6 3	8.33	1.90	123	8 4	12.28	2.20
68	3 1.5	3.15	1.43	21	8 4	7.80	1.73	106	8 4	11.18	1.90	40	10.5	15.55	2.20
85	5 2.5	5.52	1.43	51	10 5	9.68	1.90	107	12 6	14.79	2.20	120	12 6	17.72	2.95
70	6 3	6.26	1.43	117	12 6	10.97	2.05	89	20 10	15.93	2.35	121	16 8	25.09	2.65
108	8 4	7.36	1.73	88	16 8	14.85	2.20	90	24 12	18.84	2.55	122	20 10	29.07	4.00
72	10 5	8.05	1.65	99	30 15	21.56	2.65	119	20 10	24.52	2.55	189	24 12	33.51	4.60
116	12 6	8.57	1.90	92	40 20	30.08	3.50								
17	16 8	10.53	2.05												
115	20 10	13.69	2.05												
187	30 15	17.72	2.45												
232	40 20	25.16	3.50												
226	60 30	35.35	4.00												

AUTOTRANSFORMERS 240/220-115V 0V 115V 220V 240V				CASED AUTOTRANSFORMERS 240V LEAD IN: 115V 2PIN SOCKET OUT				LINE ADJUSTMENT AUTOTRANSFORMERS 0 200 210 220 230 240 250			
TYPE	VA	PRICE	P/P	TYPE	VA	PRICE	P/P	TYPE	VA	PRICE	P/P
25	65	3.82	1.10	56W	20	5.52	0.58	415C	50	2.13	0.58
64	80	4.40	1.10	64W	80	7.63	1.43	416C	100	3.13	1.10
4	150	5.84	1.43	4W	150	9.83	1.73	417C	200	3.65	1.43
69	250	7.13	1.73	69W	250	11.98	1.90	418F	350	5.63	1.43
53	350	8.97	1.90	67W	500	18.87	2.20	419F	500	6.13	1.73
67	500	11.09	2.20	84W	1000	26.90	2.65	420E	750	7.60	1.90
83	750	12.42	2.20	95W	2000	48.45	7.00	421F	1000	10.55	2.05
84	1000	16.88	2.65	73W	3000	69.18	8.00				
95	2KVA	31.26	4.00								
73	3	61.27	4.75								
57	5	87.42	6.60								
101	10	159.45	13.00								

MAINS ISOLATORS (SAFETY SCREEN)				MAINS ISOLATORS (SAFETY SCREEN)				MAINS ADAPTORS				
TYPE	VA	PRICE	P/P	TYPE	VA	PRICE	P/P	TYPE	VA	mA	PRICE	P/P
149F	60	7.35	1.73	243F	60	7.35	1.43	277PI	750			
105F	100	8.61	1.73	244F	100	8.61	1.73	279PI	1500	50.60	7.00	
151F	200	12.15	2.05	245F	200	12.15	2.05	280PI	2250	68.26	7.00	
152F	250	14.75	2.20	246F	250	14.75	2.20					
153F	350	18.22	2.55	247F	350	18.22	2.55					
154F	500	22.70	2.65	248F	500	22.70	2.65					
155F	750	32.08	7.00	249F	750	32.08	7.00					
156F	1000	41.26	7.00	250F	1000	41.26	8.00					

SEND TODAY 50p (REFUNDABLE WITH FIRST ORDER) FOR CATALOGUE
TITAN TRANSFORMERS AND COMPONENTS
CENTRAL HALL CHAMBERS GRIMSBY S. HUMBERSIDE
MAIL ORDER ONLY - PRICES INCLUDE 15% VAT


WW-018 FOR FURTHER DETAILS

ONE UP ON THE COMPETITION.

Introducing the first 4½ digit handheld DMM in a market that's been the exclusive domain of 3½ digit models. Until now...
The new Keithley 135.
Combining outstanding specification with impeccable performance. And confirming Keithley's position as a major innovator in D.M.M. technology:

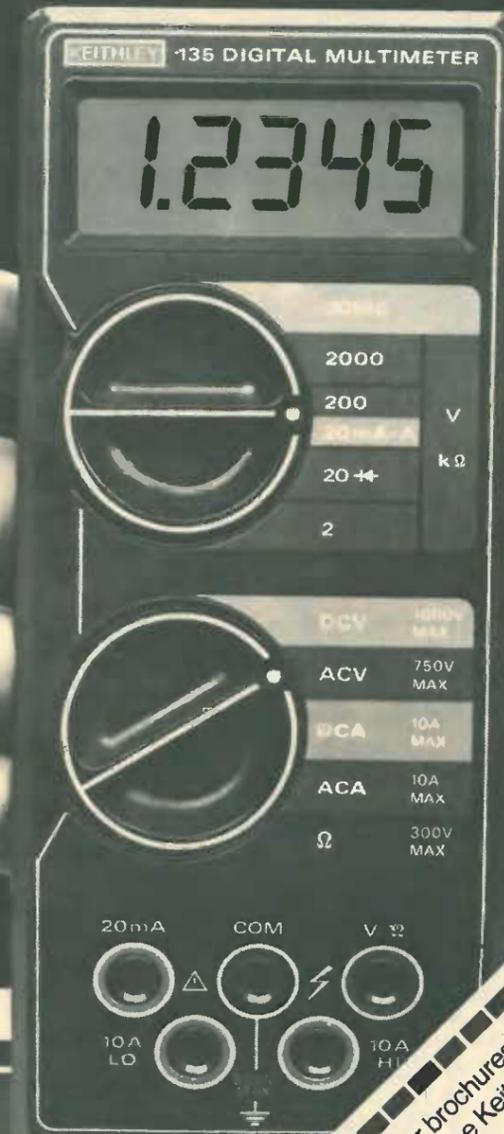- 0.05% DCV accuracy
- Five functions
- Low battery indicator
- Full overload protection:
 - 1000V max DCV
 - 1000V peak ACV
 - 300V max Ohms
- 10 amp range
- ACV bandwidth to 20 kHz

The price - only £139 + VAT
Need a bench unit? Then take a look at the new Keithley 176. Five functions, 4½ digits, ±0.05%, DCV accuracy, and full function annunciators. Built up to a standard - not down to a price. Yet at only £179 + VAT, the 176 gives quality, 4½ digit performance at a cost some 3½ digit manufacturers would dearly love to match. To find out more, fill in the coupon. And see what keeps Keithley one step ahead.



KEITHLEY

Keithley Instruments Ltd
1 Boulton Road Reading Berkshire RG2 0NL
Telephone (0734) 861287
Telex 847047

WW - 43 FOR FURTHER DETAILS

I'm interested. Please send me your brochures on
 The Keithley 135 The Keithley 176 The Keithley Range
 Name _____ Position _____
 Company _____
 Address _____
 Tel _____

WW3

How to get your hands on a signal success.



320 pages worth of the latest & best in signal processing components.

Write to Pascal for this new M80 catalogue which covers the complete Merrimac range of signal processing components and integrated networks from DC to 4GHz. It also provides reliability data in the form of MTBF calculations for each product area.

Merrimac is one of the World's most technically advanced companies specialising in low frequency lumped element components and integrated networks; microwave stripline components, subsystems, high power ferrite isolators and circulators.

So write to Pascal today for your copy of the M80 on your company's notepaper (or phone if you prefer) indicating your area of interest - we guarantee you'll find it one of the best.



Pascal

Pascal Electronics Limited
Hawke House, Green Street,
Sunbury-on-Thames,
Middlesex TW16 6RA
Telephone: (093271) 87418 Telex: 8814536

the best in electronics

WW - 042 FOR FURTHER DETAILS

PRODUCTION TESTING
DEVELOPMENT
SERVICING

POWER UNITS

Now available with 3 OUTPUTS



Type 250VRU/30/25

OUTPUT 1: 0-30v, 25A DC
OUTPUT 2: 0-70v, 10A AC
OUTPUT 3: 0-250v, 4A AC


ALL Continuously Variable

Valradio

VALRADIO LIMITED, BROWELLS LANE, FELTHAM
MIDDLESEX TW13 7EN
Telephone: 01-890 4242/4837

WW - 039 FOR FURTHER DETAILS

Quartz Crystals

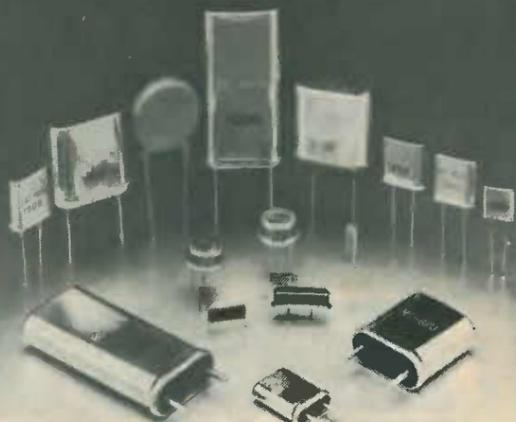

Stocks of standard items exceed a quarter of a million. Individual units to the tightest specification made to order.

Interface Quartz Devices Limited

This technology is available now from



29 Market Street
Crewkerne
Somerset TA18 7JU
Crewkerne (0460) 74433
Telex 46283 inface g

WW - 016 FOR FURTHER DETAILS

Oscilloscopes 5650 2CH/50MHz, 5mV at 50MHz, 1mV at 10MHz. Dual time base. Sweep delay. Signal delay. from £865	R.C. Oscillators 418B 10Hz to 1MHz. Sine and square outputs. Low distortion. £90	Voltmeters 1631A High Sensitivity: 100 micro volt (FS). RMS, dBm and dBv scale. Low-pass filter. High input impedance: 10MHz. from £175	Attenuator 9801A Low cost. DC to 50kHz. Unbalanced 'in' and 'T'. £97
5531 2CH/35MHz, 5mV at 35MHz, 1mV at 15MHz. Dual time base. Sweep delay. Signal delay. from £525	417B 5Hz to 500kHz. Sine and square outputs. Low distortion. £210	1831A 2 identical channels. 2 needle pointers. RMS, dBm and dBv scale. from £184	Voltage Tester 865AZ 0 to 5kV AC. Adjustable current limit. Manual, automatic modes. £295
5520 2CH/20MHz, 5mV at 20MHz, 1mV at 10MHz. One touch X-Y T.V. sync separator. from £230	Function Generators 459 0.01Hz to 1MHz. Sine, triangular and square outputs. Output voltage > 20V p-p. (459L 0.0005Hz to 1MHz) from £235	107B Volt ohmmeter. All solid state. AC or battery power. £99	Power Supplies Wide range of power supplies covering dc voltages up to 500 volts and currents up to 200 amps. £82-£124
538A Low cost. 5MHz bandwidth. 3" screen. from £85	457A 0.01Hz to 100kHz. Sine, triangular and square output. V.C.G. mode (FM) 1000:1 V.C.A. mode (AM). £555	Wow-Flutter Meter 6702 0.002% wow-flutter capability. High sensitivity. 100mV. JIS, NAB, CCIR, DIN standard. Sigma memory function. £625	PAB Series Economy series. Constant voltage continuously variable. Series/parallel operation. £82-£124
Alignment Scopes 5091 X-Y display. 9" screen. 1mV/DIV and 10V/DIV sensitivity. from £200	458A 0.01Hz to 100kHz. Sine, triangular and square output. V.C.G. mode (FM) 1000:1. Trigger and gate mode. £432	Frequency Counters 255 Frequency, time, rpm modes. 10Hz to 150MHz 0.01, 0.1 and 1.0 and 10.0 secs gate time. from £200	PAD Constant voltage, constant operation with automatic cross over. No overshoot on turn-on, turn-off. Remote programming, remote sensing, auto parallel operation. from £226

Just some of the extensive range of
KIKUSUI HIGH QUALITY ELECTRONIC TEST INSTRUMENTS
Post the coupon for your full, informative catalogue now

KIKUSUI

Please send me the full, informative Kikusui catalogue and price list.

All prices exclude VAT and are correct at time of supplying copy to publication

Name

Barclaycard and Access credit cards accepted



Address


Company Telephone No.

TELONIC/BERKELEY U.K

2, Castle Hill Terrace, Maidenhead, Berkshire SL6 4JR
Telephone: Maidenhead (0628) 73933 Telex: 849131 Telber G

WW - 053 FOR FURTHER DETAILS

100,000,000,000,000 Ohms

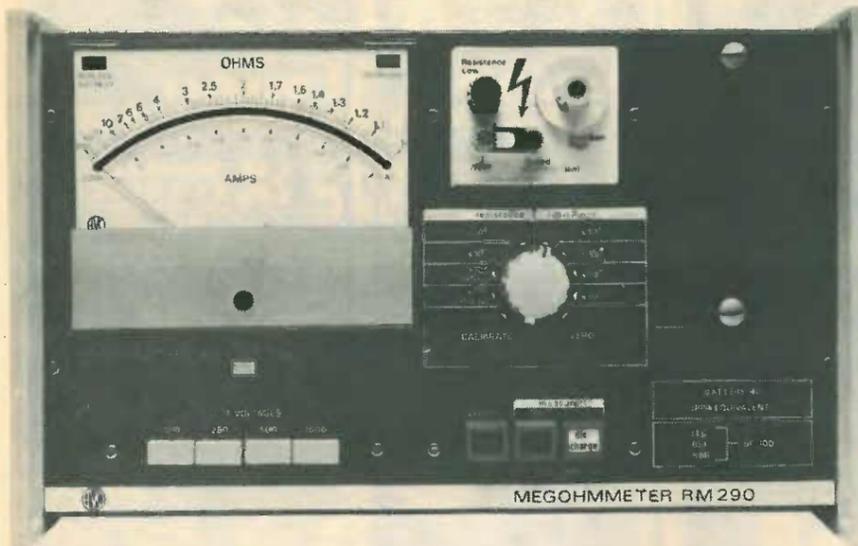

The AVO RM290 is a bench type megohmmeter with a resistance range that goes up to $10^{14} \Omega$ making it ideal for those applications where there is a need to measure the electrical resistance of non-conducting materials...accurately!

You can use the RM290 for tests on insulating components in electronic assemblies or on capacitor dielectrics. Resistance measurements can be made at test voltages of 100, 250, 500 or 1000 V. Readout from the single resistance scale on the meter is direct, irrespective of the test voltage selected.

You'll find the AVO RM290 a great asset. Get in touch with us today and we'll let you have the full facts.

You'll never meet a better meter

WW - 060 FOR FURTHER DETAILS



AVO Limited, Archcliffe Road, Dover, Kent, CT17 9EN
Tel: 0304 202620 Telex: 96283

Thorn Measurement & Components Division

CB RADIO ACCESSORIES

THE LARGEST DISTRIBUTORS OF CB ACCESSORIES IN THE U.K. Come and see the biggest and best selection of CB Radio Accessories from all the leading manufacturers, including:

Logos for HI HARADA, K40, LUMP, SIRTEL, TURNER, CB by ARISTA, WT, TELEX, NV-RAMA CORPORATION-SA, Mura Electronics (UK) Ltd.


Sole UK agents for: NV-RAMA CORPORATION-SA, the antenna specialists co.

SWR METERS including RAMA, NANSEN etc.

Mura Electronics (UK) Ltd., 79 Church Rd, Hendon, London NW4 Tel: 01 203 527718



AMCRON INDUSTRIAL MUSCLE

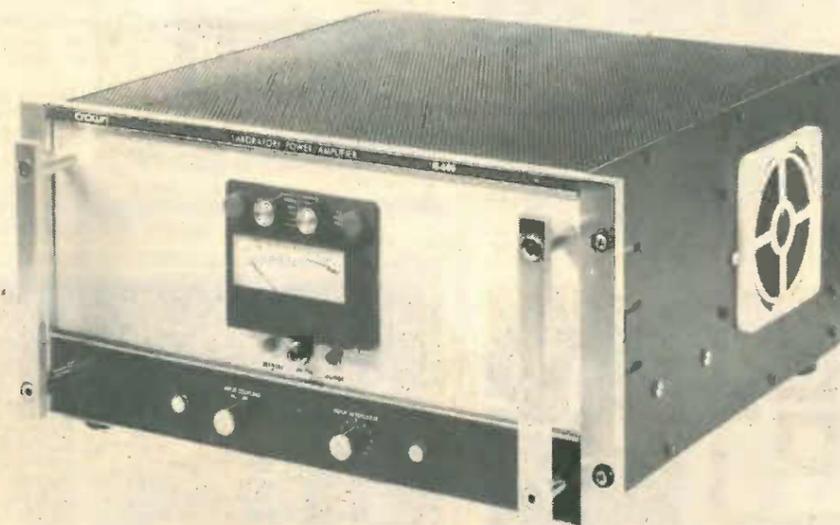

Model — M600

- ★ POWER RESPONSE DC — 20KHz ± 1dB.
- ★ OUTPUT POWER IN EXCESS OF 1.5kW INTO 2.75 Ohm LOAD (CONTINUOUS R.M.S.).
- ★ D.C. OUTPUT 20 AMPS AT 100 VOLTS OR 2KV_a.
- ★ HARMONIC DISTORTION LESS THAN 0.05% DC-20KHz AT 1kW INTO 6 OHMS
- ★ PLUG-IN MODULES: CONSTANT VOLTAGE/CURRENT, PRECISION OSCILLATORS ★ UNIPOLAR AND BIPOLAR DIGITAL INTERFACES, FUNCTION GENERATORS, AND MANY OTHERS.
- ★ OUTPUT MATCHING TRANSFORMERS AVAILABLE TO MATCH VIRTUALLY ANY LOAD.
- ★ FULL OPEN AND SHORT CIRCUIT PROTECTION GUARANTEED STABLE INTO ANY LOAD.
- ★ TWO UNITS MAY BE CONNECTED TO PROVIDE UP TO 4kW.
- ★ INTERLOCK CAPABILITY FOR UP TO EIGHT UNITS.
- ★ 3-YEAR PARTS AND LABOUR WARRANTY.

For full details on all Amcron Products write or phone Chris Flack



Kirkham Electronics

MILL HALL, MILL LANE, PULHAM MARKET, DISS, NORFOLK IP21 4XL
DIVISION OF K.R.S. LIMITED
TELEPHONE (037 976) 639/594

WW - 059 FOR FURTHER DETAILS

Toroidal

TRANSFORMERS
IN A RANGE OF
76
TYPES

We use advanced winding technology to make our toroidal transformers. They have only half the weight and height of their laminated equivalents and are appreciably more efficient. Our toroids cost virtually the same as the older types which they are rapidly replacing. Induced hum is reduced by a factor of ten. Supplied with rigid mounting kit with centre bolt, steel and neoprene washers.

30VA 70mm dia. x 30mm Weight 0.45 Kg **£4.71**
(+£1.20 p.p. + 0.89 VAT)

160VA 110mm dia. x 40mm Weight 1.8 Kg **£8.88**
(+£1.80 p.p. + £1.60 VAT)

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
1X010	6+6	2.50
1X011	9+9	1.66
1X012	12+12	1.25
1X013	15+15	1.00
1X014	18+18	0.83
1X015	22+22	0.68
1X016	25+25	0.60
1X017	30+30	0.50

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
5X012	12+12	6.66
5X013	15+15	5.33
5X014	18+18	4.44
5X015	22+22	3.63
5X016	25+25	3.20
5X017	30+30	2.66
5X018	35+35	2.28
5X028	110	1.45
5X029	220	0.72
5X030	240	0.66

50VA 80mm dia. x 35mm Weight 0.9 Kg **£5.19**
(+£1.30 p.p. + 0.97 VAT)

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
2X010	6+6	4.16
2X011	9+9	2.77
2X012	12+12	2.08
2X013	15+15	1.66
2X014	18+18	1.38
2X015	22+22	1.13
2X016	25+25	1.00
2X017	30+30	0.83
2X028	110	0.45
2X029	220	0.22
2X030	240	0.20

225VA 110mm dia. x 45mm Weight 2.2 Kg **£10.59**
(+£1.90 p.p. + £1.87 VAT)

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
6X014	18+18	6.25
6X015	22+22	5.11
6X016	25+25	4.50
6X017	30+30	3.75
6X018	35+35	3.21
6X026	40+40	2.81
6X028	110	2.04
6X029	220	1.02
6X030	240	0.93

80VA 90mm dia. x 30mm Weight 1 Kg **£5.76**
(+£1.50 p.p. + £1.09 VAT)

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
3X010	6+6	6.94
3X011	9+9	4.44
3X012	12+12	3.33
3X013	15+15	2.66
3X014	18+18	2.22
3X015	22+22	1.81
3X016	25+25	1.60
3X017	30+30	1.33
3X028	110	0.72
3X029	220	0.36
3X030	240	0.33

300VA 110mm dia. x 50mm Weight 2.6 Kg **£12.27**
(+£2.00 p.p. + £2.14 VAT)

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
7X016	25+25	6.00
7X017	30+30	5.00
7X018	35+35	4.28
7X026	40+40	3.75
7X025	45+45	3.33
7X028	110	2.72
7X029	220	1.36
7X030	240	1.25

120VA 90mm dia. x 40mm Weight 1.2 Kg **£6.72**
(+£1.60 p.p. + £1.25 VAT)

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
4X010	6+6	10.00
4X011	9+9	6.66
4X012	12+12	5.00
4X013	15+15	4.00
4X014	18+18	3.33
4X015	22+22	2.72
4X016	25+25	2.40
4X017	30+30	2.00
4X028	110	1.09
4X029	220	0.54
4X030	240	0.50

500VA 140mm dia. x 60mm Weight 4 Kg **£16.35**
(£12.10 p.p. + £2.77 VAT)

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
8X017	30+30	8.33
8X018	35+35	7.14
8X025	40+40	6.25
8X025	45+45	5.55
8X033	50+50	5.00
8X028	110	4.54
8X029	220	2.27
8X030	240	2.08

CHOICE OF 3 PRIMARY INPUTS

1 L.P. Toroidal Transformers are available in choice of 110V, 220V, 240V, coded as follows: (Secondaries can be connected in series or parallel)

For 110V Primary insert 0 in place of "X" in type number.
For 220V Primary (Europe) insert 1 in place of "X" in type number.
For 240V Primary (U.K.) insert 2 in place of "X" in type number.


Example - 120VA 240V 15+15V, 4A = 42013.

* CUSTOMER DESIGN ENQUIRIES INVITED.
QUANTITY PRICE LIST AVAILABLE.


FREEPOST facility. (U.K. only).

Simply address envelope to **FREEPOST** to address below. NO STAMP REQUIRED.

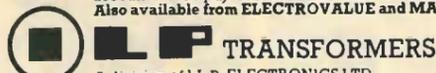TO ORDER Enclose cheque/Postal Order/Money Order payable to I.L.P. Electronics Ltd or quote your ACCESS or BARCLAYCARD account No. To pay C.O.D. add £1 extra to TOTAL value of order. Also available from ELECTROVALUE and MARSHALLS.



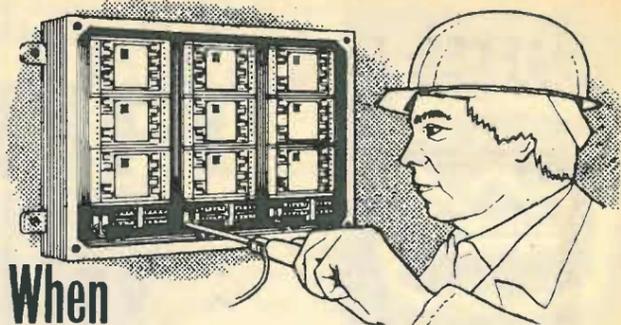A division of I.L.P. ELECTRONICS LTD.
FREEPOST T5, GRAHAM BELL HOUSE, ROPER CLOSE
CANTERBURY CT2 7EP
Phone (0227) 54778 Technical (0227) 64723 Telex 965 780



When SAFE ELECTRICAL INSTALLATIONS are your concern



you need the new



low resistance test set

FARNELL INDUSTRIAL CONTROL · WETHERBY · WEST YORKSHIRE LS22 4DH · TEL. (0937) 61961 · TELEX 557294 FARIST G
WW - 062 FOR FURTHER DETAILS

Measures earth resistance from equipment to distribution board earth up to 100m apart

Measures contact resistance of circuit breakers, switches, bus bar joints, crimps, fuses etc.

Also a boon to manufacturers of transformers, chokes and coils, wire and cables etc.

Test current up to 5A ensures contact 'wetting'

Resolution 1 milliohm

Smaller and lighter than alternative instruments

Costs a lot less too... only £210 UK ex VAT

Good range of optional accessories

Wholesaler enquiries welcomed

Detailed brochure and price list from:

How to become a SUCCESSFUL CONSULTANT in your own field.

Have you ever wished you could quit your job and start working for yourself?

Well, maybe you can! Many people are amazed when they discover the tremendous amount of professional experience and specialized knowledge they've accumulated; experience and knowledge that others will gladly pay for. Literally thousands of people who made that discovery are now prospering as independent consultants, full and part time.

The way to begin is by reading *How to Become a Successful Consultant in Your Own Field*, by Hubert Bermont.

Clear, straightforward, packed with solid information and advice, this authoritative manual tells you everything you need to know to establish your own independent consulting practice. Here's a sampling of the contents:

- What does it take to be a successful consultant? (See Chapter 1)
- How to get started. (See Chapter 3)
- How to operate your business - a collection of "tricks of the trade." (See Chapter 5)
- What to charge your clients - plus five helpful rules on fees. (See Chapter 6)
- Why you should never work on a contingency (speculative) basis. (See Chapter 7)
- Ingenious ways to promote yourself, and make people want your services. (See Chapter 9)
- Contracts: why you should avoid them at all cost. (See Chapter 10)

© CHARTSEARCH LTD., REG. NO. 953026, 11 Blomfield Street, London EC2M 7AY.


To: CHARTSEARCH LTD., 11-12 Blomfield Street, London EC2M 7AY. Please send me, postpaid, my copy of "How to Become a Successful Consultant in Your Own Field", for which I enclose my payment of £12.50.

Name _____
Address _____

Overseas orders, add £3 per order for airmail shipment. Please allow 14 days for delivery.

WW/A

METER PROBLEMS?

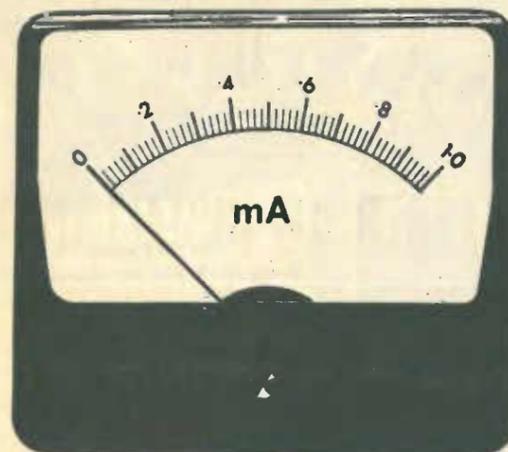

137 Standard Ranges in a variety of sizes and stylings available for 10-14 days delivery. Other Ranges and special scales can be made to order.

Full information from:

HARRIS ELECTRONICS (London)
138 GRAYS INN ROAD, W.C.1 Phone: 01/837/7937
Telex: 892301 HARTRO G

WW-061 FOR FURTHER DETAILS

PAGING... PAGING... PAGING...



SEQUENTIAL TONE GENERATOR - A PARAGON WITH MANY VIRTUES

This single instrument provides all the signals necessary for testing Pocket Pagers, Selective calling systems, C.T.C.S., Tone Burst Systems as well as R.C.C. systems using PTMF, MTS, IMTS, Interrupt and F.S.K.

The memory also has additional capacity for tomorrows communications needs.

For further information contact Mike Taylor




FieldTech Ltd.
Heathrow Airport
London
Hounslow TW6 3AF
Tel: 01-759 2811
Telex: 23734
FLDTEC G

PARAGON ELECTRONICS

WW - 015 FOR FURTHER DETAILS

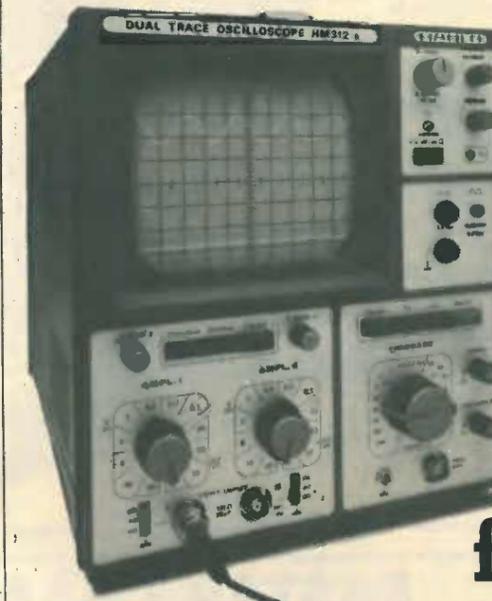
Incredible Quality Incredible Performance Incredible Price!!!



HM312 Dual Trace Oscilloscope.
DC-20MHz.
Sensitivity 5mV/20V/cm. Time base range 0.5uS-0.2S/cm with x5 horiz mag to 100nS/cm, with variable control uncalibrated to 40nS/cm. CRT screen 8 x 10cm. Full XY using ch1 as X input. Bandwidth 2.3MHz. TV trigger.

NOW BETTER VALUE THAN EVER AT

£220

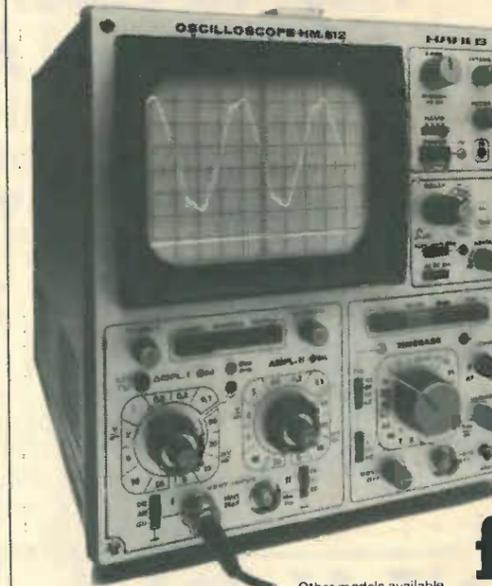

HM512 Dual Trace Oscilloscope with delayed sweep.
DC-50MHz.
Sensitivity 5mV/20V/cm Time base range 0.1uS-2.0S/cm with x5 horiz mag to 20nS/cm. Delay ranges 7 decade steps 100ns-1S with fine control CRT screen 8 x 10cm. Full XY using ch 1 as x input, bandwidth 4 MHz. Z input. Delay line allows viewing of leading edge. Vertical overscan indicated by 2 LED's.

£580

Other models available.
HM307 10MHz plus component tester. £138.00
HM412 20 MHz with sweep delay. £350.00
HM812 50 MHz storage. £1458.00

All scopes can be fitted with a long persistence CRT at extra cost.

World-beating Oscilloscope Offers

FROM

Electronic Brokers

61/65 Kings Cross Road,
London WC1X 9LN.
Tel: 01-278 3461. Telex 298694

Prices do not include carriage or VAT.

WW - 036 FOR FURTHER DETAILS

A PROFESSIONAL TOOLCASE FOR UNDER £40

Designed for the professional Electronics, T.V or Instrument Technician who needs to carry a large number of specialist tools.

The TL99 sets a standard as a low cost alternative to more expensive cases. It offers strength with a practical use of space and many other features.



Features

- 2 sided Reversible Multi-purpose tool pallet
- Document area
- 90° opening lock back stays
- 3" deep ABS lid and base
- Twin handles with 8 fixing points on aluminium frames
- Burst proof toggle locks with keys
- Moulded adjustable tray in base
- Heat sink for hot soldering iron


Dimensions TL 99 17" x 12" x 6" split (shown)
also available TL100 19" x 14" x 6" split

Tools NOT included. British made.
Money back guarantee. Allow 7-21 days for delivery.

Order Form
Telexman Products Ltd
 Ermine House, Post St, Godmanchester, Cambs. PE18 8BA (0480)65534
 Please send TL99 Professional Toolcases at £39.90 each.
 also available TL100 Professional Toolcases at £43.70 each.
 Both inc. VAT (P&P £2.60 extra)
 Enclosed my cheque for £
 Name
 Company
 Address

FASTER THAN A SCOPE— SAFER THAN A VOLTMETER

LOGIC MONITOR LM-1

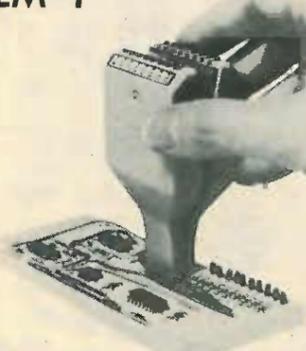

Instant - simultaneous monitoring of the logic state of all IC nodes

Just clip it over your IC.

- LM-1 Instantly and accurately shows both static and dynamic logic states on a bright 16 LED display.
- LM-1 finds its own power.
- LM-1 cuts out guesswork, saves time, and eliminates the risk of short circuits.
- LM-1 is suitable for all dual-in-line logic ICs. LED on = logic state 1 (high), LED off = logic state 0 (low), and each LED is clearly numbered 1 to 16 in the conventional IC pattern.

ONLY £31

plus 15% VAT, plus post and packing
Total £37.37 including box and instruction manual.



GLOBAL SPECIALTIES CORPORATION
 Europe, Africa, Mid-East: GSC UK LTD., Dept. 75
 Unit 1, Shire Hill Industrial Estate
 Saffron Walden, Essex, CB11 3AQ
 Telephone: SAFFRON WALDEN 21682
 Telex: 817477

GSC
GLOBAL SPECIALTIES CORPORATION, DEPT. 75
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex.

Name

Address

QUANTITY REQUIRED	FREE catalogue Tick box <input type="checkbox"/> I enclose cheque/PO for
LM1. £37.37 inc. p & p and VAT	£

Phone your order with Access, Barclaycard or American Express
 Card No. Expiry date.

SOUND INVESTMENT



Replacement tape heads from Monolith could mean a big improvement in sound quality from your tape recorder. A full catalogue is available, price 50p, which features a wide range of heads for cassette and reel to reel machines, as well as replacement motors, tape transports, etc.

Universal cassette heads to EIAJ standard, hole centres 17mm apart, 12mm from head face:

B12-02	Mono record/playback	£ 4.62
B24-01	Stereo playback	£ 4.62
B24-02	Stereo r/p	£ 7.66
B24-07	Stereo r/p for Dolby systems	£ 9.05
C42RPH20	Stereo r/p sendust head, suitable for chrome & metal tapes	£10.67
C42RPH04	Stereo r/p glass ferrite, the ultimate long life, high performance head	£13.34
C42RPS18	Stereo twin gap r/p long life head for record monitoring	£28.99
C21ES18	Mono/Stereo erase head	£ 2.13
C44RPH03	Four channel/track r/p	£15.15
C22ES04	Twin half track erase	£ 5.43

Ex stock deliveries, all prices include VAT. Post and packing 40p.

MONOLITH electronic products

The Monolith Electronics Co. Ltd., 5/7 Church Street, Crewkerne, Somerset TA18 7HR. Tel: 0460 74321. Telex: 46306 MONLTH G.

COMMUNICATION TUBES — EX STOCK

4-65A	5763	QQV06-40A
4-125A	6080	QQV07-50
4-250A	6146/A/B	QV08-100
4-400A	6155	QY4-125
4-1000A	6156	QY4-250
4CX250B	7527	QY4-400
4CX350A	8042	QY5-3000A
4CX1500A	QQV03-10	& MORE
4CX1500B	QQV03-20A	

R/F POWER TRANSISTORS — EX STOCK

2N3375	2N5102	BLY33	BLY88
2N3553	2N5590	BLY34	BLY89
2N3632	2N5591	BLY36	BLY91
2N3733	2N5641	BLY53A	BLY92
2N4040	2N5642	BLY55	BLY93
2N4127	2N5643	BLY83	BLX13
2N4128	2N6080	BLY84	BLX14
2N5070	2N6081	BLY85	BLX67
2N5071	2N6082	BLY87	BLX68
2N5090	2N6083		& MORE



LEADING EXPORTER

SEND FOR DETAILS TO:
 AERO ELECTRONICS (AEL) LTD
 GATWICK HOUSE
 HORLEY, SURREY, ENGLAND
 TEL: (02934) 5353
 TELEX 87116 (AERO G)
 CABLES AERO G TELEX HORLEY

EXTENSIVE RANGE OF NEW FLUKE DMM'S FROM ELECTRONIC BROKERS



8050A 4 1/2 Digit LCD DMM with true RMS on AC volts and current DC volts 200mV-1KV, 10µV resolution AC volts. 200mV-750V, 10µV resolution. DC/AC current 200µA-2A, 0.01µA resolution resistance 200Ω-20MΩ, 0.01Ω resolution. Also reads dB direct referenced to 16 stored impedances. Conductance ranges 2mS and 200nS.
£245 mains model
£285 mains battery



8012A 3 1/2 Digit LCD DMM with true RMS on AC volts and current. DC volts 200mV-1KV, 100µV resolution. AC volts 200 mV-750V, 100µV resolution. DC/AC current 200µA-2A, 0.1µA resolution. Resistance 200Ω-20MΩ, 0.1Ω resolution Low resistance 2Ω and 20Ω, 1mΩ resolution Conductance ranges 2mS-20µS-200nS
£199.00 mains model
£219.00 mains battery.



8010A 3 1/2 Digit LCD DMM Same spec as 8012A plus a 10Amp AC/DC current range, but no low resistance range.
£159.00 mains model
£179.00 mains battery.



8024A 3 1/2 Digit hand held LCD DMM with peak hold Level Detector and continuity tester. DC volts 200mV-1KV, 100µV resolution.
 AC volts 200mV-750V, 100µV resolution. DC/AC current 2mA-2A, 1µA resolution. Resistance 200Ω-20MΩ, 0.1Ω resolution. Conductance 200nS. Peakhold of AC or DC volts and current. Level detector operates around +0.8V reference. Audio tone on level and continuity, **£149.00**, carrying case **£7.00** extra.

8020A 3 1/2 Digit hand held LCD DMM. Spec as per 8024A with extra conductance range of 2mS but no peak hold, level or continuity ranges.
 Complete with carrying case. **£125.00**.

8022A 3 1/2 Digit hand held LCD DMM. Spec as per 8020A but no conductance ranges and slight reduction in accuracy. **£75.00** carrying case **£7.00** extra.

Also available a range of accessories including current shunts, EHT probe, rf probe, Temperature probe and touch and hold probe. Full details on request. The warranty period on all items shown is 1 year other than the 8020A which is 2 years.

Electronic Brokers

61-65 King's Cross Road
 London, WC1X 9LN
 Tel: 01-278 3461 - Telex 298694
 Prices do not include carriage or VAT.

**AUDIO/VIDEO
SERVICE EDITION**

**IMMEDIATE DELIVERY
ON ALL SERVICE EQUIPMENT**



UNBEATABLE PM 5519- FROM PHILIPS, OF COURSE

PM 5519 I CTV pattern generator

- * Over 20 colour and b/w test patterns carefully selected for maximum versatility
- * RF signals available in bands, I, III, IV and V
- * Variable video output (with 1 volt fixed position)
- * External video and sound modulation facility
- * Composite sync output for triggering — includes the line frame and blanking pulses to the local TV standard
- * Versions available for non-British TV systems

Reader inquiry number 220

SIGNAL SUCCESS

PM 5326 RF signal generator

- * 100 kHz — 125 MHz in nine overlapping ranges with 5 digit display
 - * Built-in 5 digit counter displays external frequencies.
- Two versions available: 100 MHz (1 kHz resolution) — PM 5326X or

- 1 MHz (10 Hz resolution) — PM 5326
 - * 50 mV RF output at 75Ω can be attenuated to over 100 dB
 - * Electronically stabilized output level
 - * Wobulator facility for IF amplifiers, AM/FM radio and TV receivers
- Reader inquiry number 221**



WIRELESS WORLD APRIL 1981

LOW-COST, HIGH-VALUE OSCILLOSCOPE

PM 3207 dual trace oscilloscope

- * Ideal for service and general-purpose applications
- * 15 MHz/5 mV
- * Triggering from either channel or external input
- * Auto TV triggering
- * Same sensitivity on X and Y channels
- * B-invert facility

* Full 8 x 10 cm screen
Reader inquiry number 222



PM 2505 electronic analogue multimeter

- * 62 measuring ranges
 - * High V and A sensitivity
 - * 10 MΩ input impedance
 - * Continuity check by sound signal
 - * Linear resistance ranges to 30 MΩ
 - * Automatic polarity indication
 - * Unique movement for high accuracy and repeatability
- Reader inquiry number 223**

PM 2502 passive analogue multimeter

- * Accuracy at a low price
 - * Comprehensive measuring ranges
 - * Highly shock-resistant meter system
 - * Common linear scale for AC and DC
 - * Continuity check by sound signal
 - * 250 V overload protection on all ranges
- Reader inquiry number 223**

...AND THREE COUNTERS

PM 6661 80 MHz automatic frequency counter

- * One control — ON/OFF
- * Automatic triggering, noise suppression and leading zero blanking
- * High 20 mV RMS sensitivity
- * 8-digit LED display

Reader inquiry number 224

NEW



CHOOSE FROM THREE METERS

PM 2517 digital multimeter

- * Full four digits
 - * Choice of LED or LCD display
 - * True RMS AC readings (AC coupled)
 - * Autoranging with manual override
 - * Current up to 10 A
 - * Options include temperature and data hold probes
- Reader inquiry number 223**

PM 6667 and PM 6668 high resolution counters

- * 1 GHz (PM 6668) or 120 MHz (PM 6667)
 - * Reciprocal technique giving fast high resolution measurements down to 10 Hz
 - * Auto triggering on all waveforms and duty cycles
 - * 15 mV RMS sensitivity
 - * High stability X-tal oscillators: 10⁻²/month
 - * Microprocessor control
- Reader inquiry number 225**

SOME OTHER STARS FROM THE RANGE

PM 5501 colour bar pattern generator

- * Ideal for mobile maintenance
 - * 5 test patterns for colour and b/w
 - * RF signal switchable between VHF, Band III, and UHF Band IV
 - * 1 kHz tone for sound checks
- Reader inquiry number 226**

PM 5107 low distortion LF generator

- * Frequency range 10 Hz — 100 kHz
 - * Distortion 0.02%
 - * Sine and square wave signals
 - * Separate TTL output
- Reader inquiry number 227**

PM 6307 wow and flutter meter

- * X-tal controlled oscillator
 - * High accuracy and frequency stability
 - * 3150 Hz or 3000 Hz switchable
 - * Separate 'drift' and 'flutter' indication
- Reader inquiry number 228**

PM 6456 stereo generator

- * Complete stereo signal with low crosstalk
- * Separate L and R signals
- * External modulation facility
- * X-tal controlled pilot
- * Adjustable multiplex signal and tunable 100 MHz RF signal

Reader inquiry number 229

WHERE TO BUY YOUR PHILIPS AUDIO AND VIDEO SERVICE EQUIPMENT

The entire range is available from the Philips Electronic Instruments Department (see address below) or from Philips Service Centres (phone 01-686 0505 for the address of your nearest branch). In addition, the PM 2517 and PM 3207 can be obtained from Wessex Electronics Ltd, 114-116 North Street, Downend, Bristol BS16 5SE. Tel (0272) 571404.

INPUT
FROM PHILIPS TEST & MEASURING INSTRUMENTS

Use the inquiry service to obtain information about the products which interest you. Alternatively, phone Cambridge (0223) 358866 and speak to our Commercial Office on extension 145 or 148. Inquiry No

PM 5519 CTV pattern generator	220
PM 5326 RF signal generator	221
PM 3207 oscilloscope	222
PM 2517, 2505, 2502 multimeters	223
PM 6661 80 MHz frequency counter	224
PM 6667/6668 high resolution counters	225
PM 5501 colour bar pattern generator	226
PM 5107 LF generator	227
PM 6307 wow and flutter meter	228
PM 6456 stereo generator	229

Pye Unicam Ltd
Philips Electronic Instruments Dept
York Street, Cambridge CB1 2PX, England
Tel. Cambridge (0223) 358866. Telex 817331

PHILIPS

PHILIPS Test & Measuring Instruments

BULK EPROM PROGRAMMING

4000 PRODUCTION EPROM PROGRAMMER


2-YEAR WARRANTY ON SHOW AT MICROSYSTEMS 81



This unit provides simple, reliable programming of up to 8 EPROMs simultaneously. It has been designed for ease of operator use — a single 'program' key starts the self check — blank check — program — verify sequence. Independent blank check & verify controls are provided along with mode, pass/fail indicators for each copy socket and a sounder to signal a correct key command & the end of a programming run. Any of the 2704/2708/2716 (3 rail) & 2508/2758/2516/2716/2532/2732 (single rail) EPROMS may be selected without hardware or personality card changes. **PRICE £545 + VAT.** Postage paid

BULK EPROM ERASING

EX-STOCK

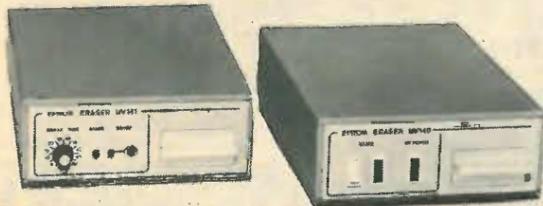

MODEL UV141 EPROM ERASER

- 14 EPROM capacity
- Fast erase time
- Built-in 5-50 minute timer
- Convenient slide-tray loading of devices
- Safety interlocked to prevent eye and skin damage
- Rugged construction
- MINS & ERASE indicators
- Price £78 + VAT postage paid.

MODEL UV140 EPROM ERASER

Similar to Model UV141 but without timer. **Price £61.50 + VAT** post paid

BULK EPROMS

EX-STOCK

	1-9	10-24	25-49	50-99	100 up
2716 (450ns) (single rail)	£6.00	£5.50	£5.00	£4.50	£4.20
2708 (450ns)	£3.90	£3.50	£3.10	£2.90	

Postage and Packing is included in all prices. ADD VAT at 15%. All our EPROMS are manufactured by leading companies and are fully guaranteed, branded and to full specification.

WRITE OR TELEPHONE FOR FURTHER DETAILS OR SEND OFFICIAL COMPANY ORDERS/CHEQUES TO:

PLEASE NOTE NEW ADDRESS & TELEPHONE NUMBER

GP INDUSTRIAL ELECTRONICS LTD.

Unit 6, Burke Road, Totnes Industrial Estate, Totnes, Devon
Telephone: Totnes (0803) 863360 sales, 863380 technical
Telex: 42596

DISTRIBUTORS REQUIRED - EXPORT ENQUIRIES WELCOME

WW-064 FOR FURTHER DETAILS

Get a great deal from Marshall's

The new Marshall's 80/81 catalogue is now available. A veritable treasure house of components, test gear, tools, etc. Specially interesting to the radio amateur are the following Leader instruments available from stock:

- Antenna Coupler LAC895 3.5 to 28 MHz Price: £88.00
- Antenna Coupler LAC896 50MHz Price: £44.00
- Antenna Coupler LAC897 144-148 MHz Price: £44.00
- TRDIP Meter LDM 815 1.5 MHz to 250 MHz Price: £45.00
- Antenna Impedance Meter LDM 870A 1.8 MHz to 150 MHz Price: £44.00
- RF Power Meter LPM 880 0.5 to 120W Price: £73.00
- SHR/Watt-meter LPM 885 1.0W to 100W Price: £47.00




Send SAE for details or phone Richard Kaiser 02407 3568 for specialist advice.

Send for our latest catalogue. Free to industrial customers, 75p post paid to private individuals.

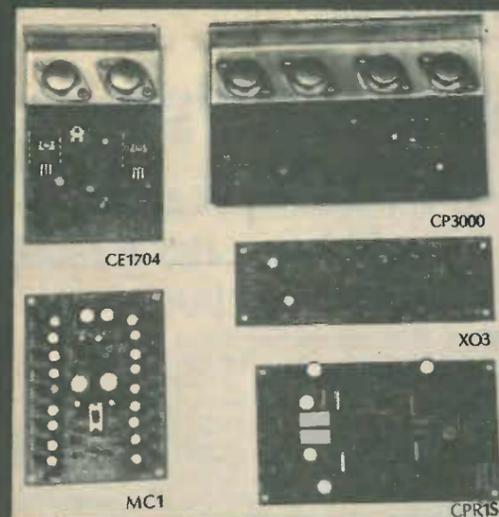A. Marshall (London) Ltd., Kingsgate House, Kingsgate Place, London NW6 4TA.
Industrial Sales: 01-328 1009
Mail Order: 01-624 8582 24hr service
Retail branches: London; Glasgow; Bristol.

Join the Professionals...

Crimson modular audio amplifiers feature: ★ Low values of transient and steady state distortions ★ Envelope distortion (below 500 Hz) less than 0.05% ★ on-board electronic protection ★ P.C.B. pin and edge connector termination ★ Full range of complimentary components, i.e. P.S.U.'s, heatsinks etc. available from Crimson.



The Crimson range of amplifier modules are built to very high standards and have earned an enviable reputation in every field to which they have been applied. The boards come ready built and tested (guaranteed for two years) and can be used to advantage where high quality signal amplification is required. The power amplifier modules range from 60WRMS to 310WRMS with up to twice this amount in bridge mode. All feature substantial heatsink brackets which can be bolted to any available heatsink or the Crimson purpose designed types. Input sensitivity is set at 775mV and power supply requirements are catered for by one of the three Crimson toroidal power supplies. The Pre-amplifier module (CPR1) is basically a phono amplifier with sophisticated circuitry incorporating R.I.A.A. equalisation. Also on-board is auxiliary amplification for tape and tuner inputs. A separate module (MC1) is also available and gives the required boost for low output moving coil type cartridges. External components required are potentiometers for volume and balance, switches for signal routing and a regulated ±15V D.C. power source (REG1). Complementary to this range, are the electronic crossover modules XO2/XO3 which, with a special muting board (MU1) can be incorporated in all types of active speaker systems.

Numerous applications are possible with Crimson modules. For example, a complete Hi-Fi Pre & Power amplifier of 40-125WRMS/channel can be built using our Hardware kits (see Hobby Electronics review, August 1980). Alternatively, Mono or Stereo slave amps of up to 500WRMS can be built into proprietary flight cases, while other uses include active loudspeaker systems such as designed by R.I. Harcourt in Wireless World October/November 1980. Further details of how to use the modules are contained in the Users/Application Manual available at £0.50.

Type	O/Pohms*	O/P4ohms*	PSU	H/Sinks	Slew	S/N	Sensitivity	T.H.O. (typ)	F.R.	Size
CE 608	38	44	CPS1	50mm	30V/μs	110dB	775mV	0.0035%	1.5Hz 50kHz 3dB	80 - 120 - 25
CE1004	44	70	CPS3	100mm	30V/μs	110dB	775mV	0.0035%	1.5Hz 50kHz 3dB	80 - 120 - 25
CE1008	65	121	CPS3	100mm	30V/μs	110dB	775mV	0.0035%	1.5Hz 50kHz 3dB	80 - 120 - 25
CE1704	85	121	CPS6	150mm PM1	30V/μs	110dB	775mV	0.0035%	1.5Hz 50kHz 3dB	101 - 102 - 35
CE1708	125	250	CPS6	150mm PM1	30V/μs	110dB	775mV	0.0035%	1.5Hz 50kHz 3dB	80 - 120 - 25
CP3000	250	250	CPS6	FM2	30V/μs	110dB	775mV	0.0035%	20Hz 20kHz	138 - 80 - 35
CPR1(S)	Output	775mV	REG1	3V/μs	70dB	2.8mV/RMS	0.008%	20Hz 20kHz	80 - 120 - 35	
MC1(S)	Output	2mV	REG1	3V/μs	90dB	775mV	0.01%	X over points	150 - 50 - 20	
XO2 XO3	Output	775-2000mV	REG1	3V/μs	90dB	775mV	0.01%	X over points	150 - 50 - 20	

Power Amplifier Modules	Power Supply Modules	Heatsinks	Price
CE 608	£21.00	CPS1 (50VA)	£19.50
CE1004	£24.50	CPS3 (150VA)	£23.50
CE1008	£27.50	CPS6 (250VA)	£33.00
CE1704	£35.00	REG1	£13.30
CE1708	£36.00	TR6	£2.50

Pre Amplifier Modules Active Crossovers Hardware
CPR1 £34.00 XO2 £19.00 Pre Amp £39.80
CPR1S £44.50 XO3 £28.35 Power Amp. £38.00
MC1 £28.00 MU1 £7.50 Thermal Cutouts £1.90
MC1S £37.00

GE Crimson Elektrik

9 CLAYMILL ROAD, LEICESTER LE4 7JJ, ENGLAND. Tel. 0533 761920. Telex 34694 Chamco G CRIMLEK

PLEASE SEND ME MORE DETAILS OF ALL CRIMSON ELEKTRIK AMPLIFIERS
Name _____ Address _____

MORE SPEC. FOR YOUR MONEY

TYPE 747 UNIVERSAL COUNTER TIMER

DC to 150MHz 8 DIGITS, 3 CHANNELS
MEASURES —
FREQUENCY Ch A and Ch C
PERIOD Ch A
TIME ± Ch A to ± Ch B
PULSE WIDTH Ch A + or —
COUNT Ch A (may be gated and reset by B & C)
AVERAGES 1 to 1000 events

£175 & 3.50 carriage, ins. etc.

TYPE 745 COUNTER TIMER

DC to 32MHz 5 DIGITS
MEASURES —
FREQUENCY
PERIOD
TIME
COUNT
6 GATE TIMES/TIME UNITS
10 μs to 1S

£116.38 & £3 carriage, ins. etc.

TYPE 746 AUTORANGING FREQUENCY METER £84.88

1Hz to 99.9KHz

TYPE 615 OFF-AIR STANDARD £97.13

10MHz, 1MHz and 100KHz

OMB ELECTRONICS, RIVERSIDE, EYNSFORD, KENT DA4 DAE
Tel. Farningham (0322) 863567

Prices, which are CWD and ex-VAT, are correct at the time of going to press and are subject to change without notice.

FROM OMB ELECTRONICS
WW-011 FOR FURTHER DETAILS



Now, the hand-held 50MHz counter. For £49.00 + 15% VAT AND P&P £58.08

It's true. Our new, diminutive frequency counter, the *Max 50 costs a mere £49.00. Which, when you consider its totally automatic performance, is quite outstanding.

Well, what would you normally expect to pay for a guaranteed frequency range of 100Hz to 50MHz; 6-digit LED display; auto-ranging, polarity, slope trigger and input level; and built-in overvoltage protection?

And there's even more. The high reliability of LSI circuitry; sensitivity of 30MV trigger threshold; 3ppm accuracy; choice of battery or a.c. mains operation, and optional antenna.


True value, and yours for the asking. Just call us on Saffron Walden (0799) 21682 right away. Your own *Max 50 could be hand-held tomorrow!

Dealer enquiries also welcomed. *For a while, supplies will be labelled 'Mini-max'.

GLOBAL SPECIALTIES CORPORATION G.S.C. (UK) Ltd., Dept 7F
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.
Telephone: Saffron Walden (0799) 21682
Telex: 817477

WW-006 FOR FURTHER DETAILS

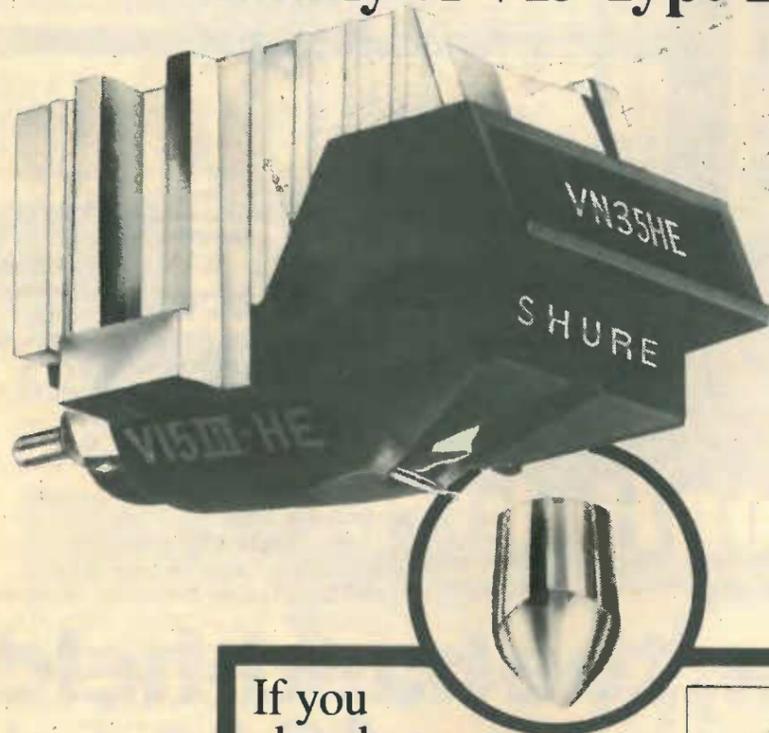fact:
we've put a **NEW plus**
into the **Super-Track Plus**
family of **V15 Type III Cartridges**




**Hyperelliptical tip for
audibly greater freedom
from distortion**

One of the critically acclaimed developments introduced in Shure's incomparable V15 Type IV pickup cartridge is its revolutionary distortion-reducing Hyperelliptical nude diamond tip. It established a new standard of sound purity through a dramatic reduction of both harmonic and intermodulation distortion. Now, the Hyperelliptical tip is also available in the world-famous V15 Type III Super-Track Plus Cartridge, bringing together the sound purity and flat response of the IV at an eminently affordable price. It is truly second only to one other cartridge in the world—the V15 Type IV.

V15 TYPE III-HE
Stereo Dynetic® Pickup Cartridge

**If you
already own a
V15 Type III
you can upgrade it!**

If you are one of the thousands of audiophiles who already own a V15 Type III, you too can benefit from the new freedom from distortion offered by the Hyperelliptical stylus. Simply replace your present stylus with the new VN35HE improvement stylus. It will give your Type III cartridge the same specifications as the new V15 Type III-HE. Takes only seconds to install (see illustration), requires no tools whatsoever.

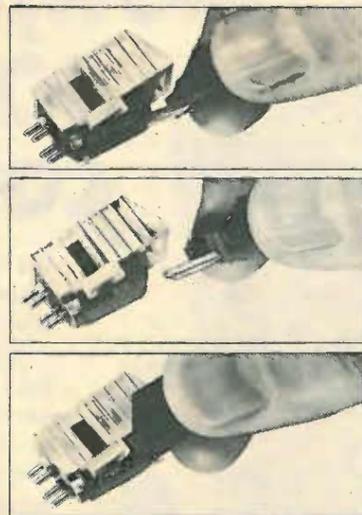

V15 TYPE III-HE IMPROVEMENT STYLUS



Shure Electronics Limited, Eccleston Road, Maidstone ME15 6AU—Telephone: Maidstone (0622) 59881

WW - 028 FOR FURTHER DETAILS

wireless world

The next seventy years

The artist Pablo Picasso once said: "Age only matters when one is ageing. Now that I have arrived at a great age, I might just as well be twenty." *Wireless World* feels much the same. Being the oldest radio journal in the world and having reached this month the Biblical age of three score years and ten, we can justly consider ourselves — in terms of electronics journalism — to have arrived at a great age. And we might just as well be twenty because it is in the nature of a periodical publication to renew itself with each issue. It doesn't matter whether one has produced 1,500 or only 15 previous issues, the next edition is always a completely new book — a new product belonging uniquely to its own moment in history and reflecting its own world at that moment. We did our reminiscing about the past on our 50th and 60th birthdays. Now, already 15 years into the era of the integrated circuit, we are as curious about the future and what it holds for us as any young person just starting to look at electronics as a possible career.

If we survive the next 70 years, what could we be looking back on in 2051 AD? Here a little humility is called for. If the periodical survives (and not necessarily on paper) it may well be a very different animal from what it is now. Electronics may no longer exist as a definable area of technology and industry. Just as radio spawned electronics, which then proceeded to absorb its parent, the same thing may happen again — several times over. On this principle one might look at other branches of science and technology with which electronics is already conjoined and speculate if they are capable of such absorption. Optics, perhaps, chemistry, biology . . . ? Or one might even consider the complete fragmentation of electronics into a variety of other technologies and interdisciplinary activities, some of which don't yet exist.

Extrapolation from present trends does take us a little way — greater complexity and higher performance in electronic products, more devices on a silicon chip, changes in microprocessor architecture and so on. This is the gadgeteering approach which envisages a world increasingly full of clever robots, wrist-

watch radios, flat tv screens and information centres in the home. But it doesn't allow for the possibility that a completely new, seminal device will be invented that will transform the technology — just as the valve transformed radio communication and the transistor opened the way to integrated circuits. Several laboratories are now exploring the possible use of biological structures as transducers and energy converters. Could this lead perhaps to a stochastic, rather than deterministic, principle of information processing and transmission, analogous to that in the animal central nervous system?

But it is unrealistic to consider a technology in isolation from the society which produces it. You can say with truth that scientists and engineers discover and invent things which change our lives. These individuals, however, are part of society and subject to its pressures. You can say with equal truth that the technology we have is a symptom of the kind of society we are: it develops in particular directions in response to our material, emotional and spiritual needs. Broadcasting, hi-fi and other electronic diversions are technological responses to the needs of the "nuclear family" for entertainment and even "company" in homes that are becoming socially isolated from communities. As in the past, technology will continue to be both cause and effect.

1911, in which we were founded, was the fateful year when Rutherford did the historic experiments that led him to postulate the atomic nucleus and the picture of the atom we have now. Since then our physicists have been discovering ever more fundamental particles and our view of matter and energy has been greatly elaborated. During the next 70 years there could be a discovery or insight that would unify our observations and even depart from the traditional line of thinking started by Democritus. Such an event would not immediately alter the practice of electronic engineering but would certainly affect profoundly the work of the applied scientists who research into physical processes to create new devices.

Editor:
TOM IVALL, M.I.E.R.E.

Deputy Editor:
PHILIP DARRINGTON
01-661 3500 X3586

Technical Editor:
GEOFF SHORTER, B.Sc.
01-661 3500 X3590

Projects Editor:
MIKE SAGIN
01-661 3500 X3588

News Editor:
MARTIN ECCLES
01-661 3500 X3589

Drawing Office Manager:
ROGER GOODMAN

Technical Illustrator:
BETTY PALMER

Production & Design:
ALAN KERR

Advertisement Manager:
BOB NIBBS, A.C.I.I.
01-661 3130

DAVID DISLEY
01-661 3500 X3593

BARBARA MILLER
01-661 3500 X3592

Classified Manager:
BRIAN DURRANT
01-661 3106

JAYNE PALMER
01-661 3033

JOHN GIBBON (*Make-up and copy*)
01-661 3500 X3561

Publishing Director:
GORDON HENDERSON

Opto-electronic contact breaker

Compact and maintenance free switching for electronic ignition systems

by J. R. Watkinson, B.Sc., M.Sc.

The conventional automotive contact breaker is still widely used in modern petrol engines despite its shortcomings. Superior alternatives have been available for several years, but car manufacturers have been slow to remove the weak link in the ignition system. This design is simple, cheap, reasonably easy to install, and provides a maintenance free unit which will drive almost all electronic ignition systems which operate with mechanical contacts.

Although many electronic ignition units are available, and several well designed constructional circuits have appeared, most of them are triggered by the existing contacts and use either inductive or capacitive discharge to improve the spark and extend contact life. Some designs claim to eliminate the effect of contact bounce, but the effects of contact heel wear and timing scatter still remain.

The circuit in Fig. 1 provides an output which, for low currents, simulates the contact breaker and can trigger an electronic ignition unit without modification. The existing centrifugal and vacuum advance mechanisms are retained, and the only mechanical part which must be constructed with any precision is a chopper disc.

The light source is an infra-red l.e.d. with a lens to give a well defined beam, which is received by a spectrally and physically matched phototransistor. Light passing between the two devices is interrupted by a chopper disc which produces a rough square wave. This waveform is cleaned up before it is used for timing because electronic ignition circuits generally require a sharp edge to trigger an s.c.r. A conventional two transistor Schmitt-trigger was not used because the regenerative

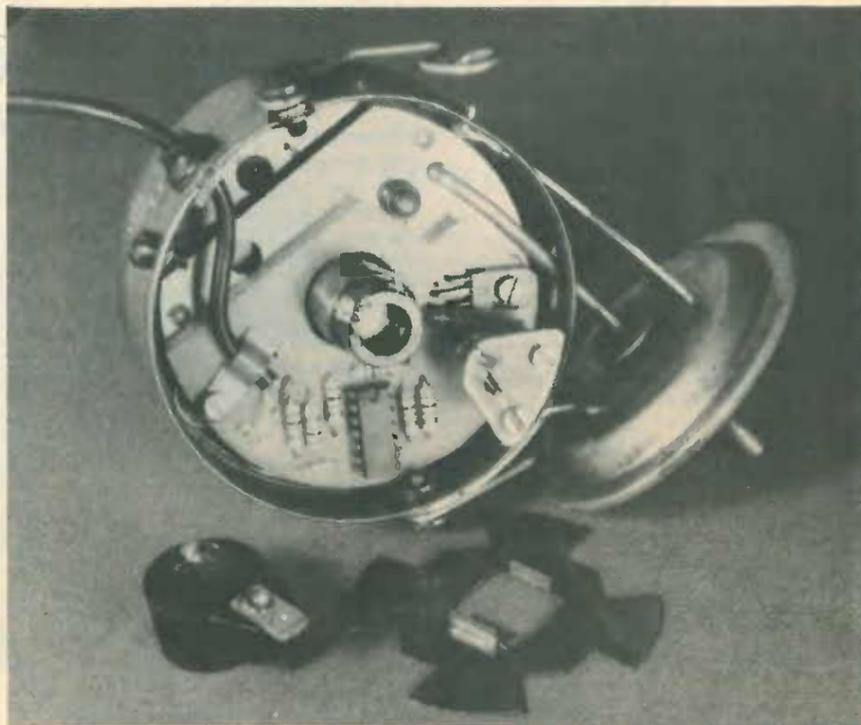


Fig. 2. Printed circuit board mounted on the action plate of a distributor. In the prototype Tr₁ was mounted underneath the board.

action only occurs if the input has a low source impedance and, in this design, the phototransistor is a current source. Instead, an open collector t.t.l. i.c. with two gates connected as a set - reset bistable is used. The inputs are driven in a complementary mode by using a third gate as an inverter, and the remaining gate is used as a buffer. The regenerative action of this circuit gives fast switching, and a conservatively rated series regulator provides reliable operation.

The complete circuit can be built on a glassfibre p.c.b. and mounted inside the

distributor as shown in Fig. 2. The prototype fits a Delco distributor as fitted to many G.M. vehicles, but the layout can be modified to fit most other types. Some foreign vehicles use very small distributors, and for these it is best to house the circuit in a small metal box beside the distributor. Installation is much easier if a replacement distributor is used. Also, the second unit is useful to carry as a spare.

The phototransistor is mounted directly on the p.c.b. and the l.e.d. is mounted about 2.5mm away on a small board supported by 3mm tapped pillars which also carry the l.e.d. current. The main p.c.b. is mounted with spacers on the action plate in the distributor with 3mm screws which must have holes drilled and tapped. As the action plate is rotated by the vacuum advance mechanism, it must not be ob-



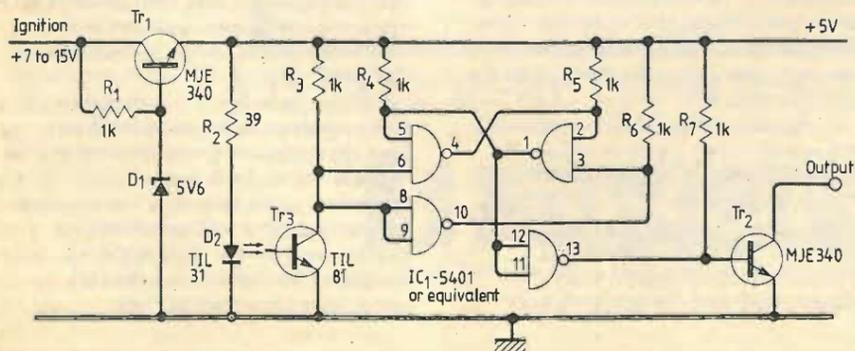


Fig. 1. Switching circuit and regulator. Tr₁ and Tr₂ do not require heatsinks, but should be secured with the screws that hold the p.c.b. in place. Note that IC₁ must be a ceramic type to ensure reliable operation during large temperature changes.

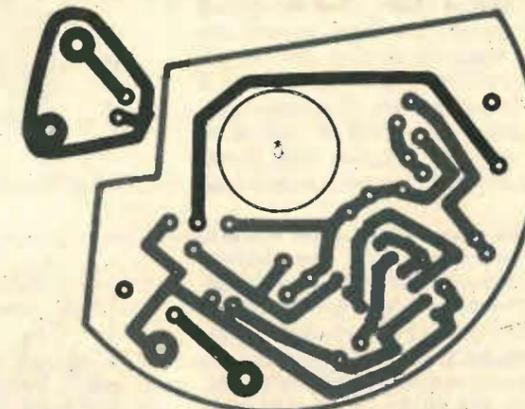

A set of shaped p.c.bs based on these layouts will be available for £4.00 inclusive from M. R. Sagin, 23 Keyes Road, London N.W.2.

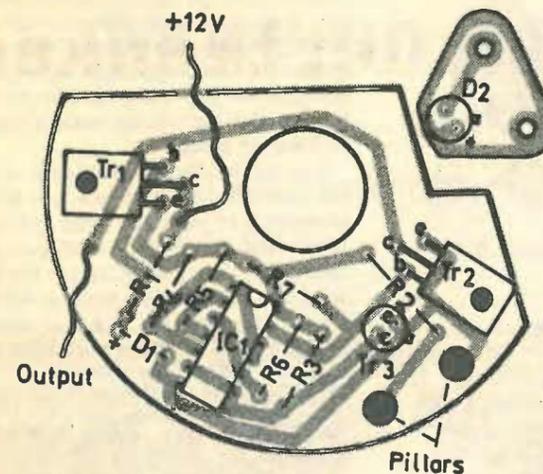

Fig. 4. Phototransistor and l.e.d. mounting. The two pillars must be metal types to carry the l.e.d. current.

▲ Fig. 3. Printed circuit boards and component locations for a Delco distributor.

structed by the board or swarf, and the manufacturer's recommended lubricant should be restored. If the existing contact pivots on a pillar rivetted to the action plate, the pillar must be removed before the p.c.b. can be installed. Care must be taken to ensure that the small board does not foul the rotor arm or the inside of the distributor cap. When installed, the p.c.b. is connected to the ignition unit by a length of good quality miniature three core stranded cable. The cable should be supported by a small P clip fixed by one of the mounting screws, and by the existing grommet in the distributor body. Remember to leave enough cable loose so that the action plate can revolve.

The circuit can be tested by connecting +12V to the supply lead, and a low power bulb from +12V to the output lead. The lamp should remain on until the light beam is interrupted. Note that the specified device does not emit visible light. If the circuit switches the lamp correctly, connect it to the electronic ignition unit and take the h.t. lead from the coil directly to one spark plug. This will avoid coil breakdown if the rotor arm is not pointing at a segment of the distributor cap. Check that a spark is generated every time the light beam is interrupted and not when it is re-established.

When the circuit has been tested, a chopper disc should be constructed to suit the distributor. The accuracy of this disc affects the overall performance of the system, and the most important parameter is the angle between the leading edge of the blade and the line joining the mainshaft axis with the centre of the rotor arm sector. It is imperative that this angle causes the leading edge of a blade to just obscure the l.e.d., i.e. the point of firing, when the end

Why replace the contact breaker?

A conventional contact breaker consists of a cam, rotated by the engine, which opens and closes a moving contact held in place by a stiff spring. As the contacts are forced open by the cam and closed by the spring, the cam has an alternating torque acting upon it. The cam is turned about the mainshaft by centrifugally operated weights which reach equilibrium with restoring springs to give different spark advance angles for different speeds. Therefore, there are two mass compliance systems which cause a wide distribution of timing. This problem is made worse by manufacturing tolerances in the cam and general wear in the contact breakers. Although a new distributor with correctly adjusted contacts operates fairly well, this peak performance rarely lasts for more than 2000 miles, and most petrol engines spend a significant proportion of their working life with a sub-standard ignition system.

The two most common replacements for the contact breaker are a magnetic pickup, where a lobed rotor varies the flux through a coil, and an optical system, where a light beam is interrupted by a chopper disc. The magnetic system is attractive to a mass producer because magnetic components and coils are familiar, but the optical system is more attractive for conversion of an existing unit because fewer mechanical parts are required.

Both types use the existing centrifugal and vacuum advance systems and, as the amount of energy extracted from the shaft is small in either case, the torsional excitation of the advance mechanism is negligible. Both systems do, however, exhibit a slight hysteresis between acceleration and deceleration as the rotor advances to take up any backlash when the engine slows. This is a small penalty and is normally of little consequence.

of the rotor arm is directly opposite a segment inside the distributor cap, with the vacuum advance at mid-travel. If this condition is not achieved the engine may not run. Another important requirement is that the chopper blades are evenly spaced to avoid scatter. The angle between the blades is found by dividing 360° by the number of cylinders. Although this unit is suitable for any number of cylinders, the greatest improvement will be noticed on engines with six cylinders and above, where multi-lobed cams cause more timing scatter.

The disc does not need great strength, and the prototype was cut from tinplate. The centre hole has tabs which are alternately bent up and down to grip the cam as shown in Fig. 5. To construct the disc make a centre punch mark and scribe a straight line through the centre mark. Using a large transparent circular protractor with 0 and 180° marks on the line, mark the position of the blade edges and scribe lines to the centre. If an inductive discharge system is used, the angle between the chopper blades becomes the dwell angle, the angle through which the points remain closed, and must be the same for all cylinders. With a conventional contact breaker the dwell angle has to be short so that the points can open a reasonable distance. Unfortunately, a short dwell angle limits the time available for primary

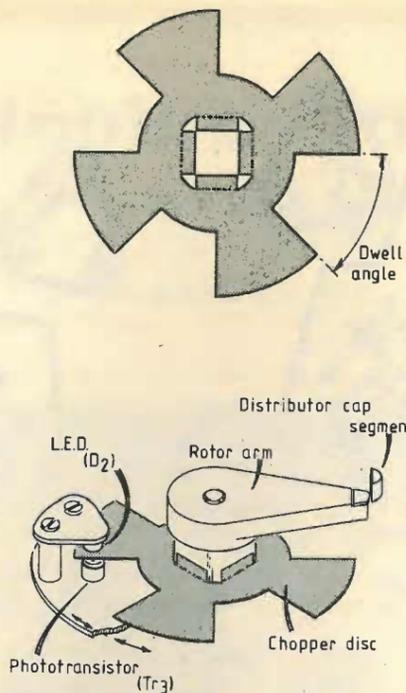


Fig. 5. Typical shape and mounting for the chopper disc. It is imperative that, when the disc just interrupts the light beam, the rotor arm is directly opposite a distributor segment with the vacuum pushrod at mid travel.

current build-up at high revolutions. With this design, the dwell angle can be increased from the manufacturers specification to increase spark energy at high revolutions. If the unit is used with a c.d. ignition system, the angle between the blades is not important because the spark is controlled only by the leading edges of the chopper blades.

Cutting the disc shape is made easier if the tinplate is clamped to a thin sheet of aluminium or plywood. After drilling the centre hole and filing it to shape, cut the disc to the correct diameter, cut the blades to shape and finish with a fine file. Finally, bend the tabs for a good central fit on the cam. The disc is then fixed to the cam with epoxy resin after checking that all the parameters are correct and that the disc revolves freely. When installation is complete, the distributor can be mounted in the engine and adjusted for correct timing with a strobe light.

Although this unit will not produce a dramatic increase in performance from a correctly tuned engine, the firing at high revolutions should be smoother and tick-over should be very steady even when cold, which permits sparing use of the choke. However, the main benefit is a maintenance free ignition system. The prototype has now been in use for five years and the distributor cap is only removed to show disbelievers.

BOOKS

Beginner's Guide to Digital Electronics,
by Ian R. Sinclair.
146pp., paperback.
Newnes Technical Books, £3.25.

Only a limited knowledge of electronics is assumed here. The author's intention is to explain the basics of digital technique to those who have no training in electronics, but who may have accumulated information on the active and passive components used in and around integrated circuits. He deals briefly with digital elements from switching devices, through small-scale systems such as counters, to microprocessors, though the chapter on micros, which occupies only fifteen pages, is rather too cursory to be of much practical value.

A complete beginner may find the lack of information on application a little worrying: elements are well described, but with little explanation of what their role in a system might be. A microprocessor, for example, is presented as a device whose program is capable of carrying out the action of a truth table as an alternative to a set of gates and registers, with no explanation of the advantages gained thereby.

The Prestel Business,
by Roger Nicholson and Guy Consterdine.
104pp., hardback.
Northwood Books, £4.95.

This is not a technical approach to Prestel, but an explanation, primarily for business people, of what a viewdata system is, how information is provided and used, some costings and some of the background. This would be a good introduction to the service for those who know little more than the name and who suspect that it could be of assistance in their work. There is no technical description whatever.

More on active crossover networks

Using electrostatic loudspeakers with a common bass unit

by D. C. Read, B.Sc.Hons (Elec. Eng.)

Modifications to David Read's 1974 active filter crossover design provide for Quad electrostatic loudspeakers or Isophon tweeters, with appropriate alterations in crossover frequencies.

An article in the November 1974 issue of *Wireless World* showed how some economies could be achieved in a stereo system using active cross-over networks. One such economy was to have a mixed mono/stereo arrangement using a single bass unit working in that part of the audio band where sounds are non-directional. Sounds in the mid and upper ranges were, in the system suggested, produced by smaller speakers fed via the amplifier/active-filter crossover units as described earlier (*Wireless World*, December 1973). This economy arrangement worked well, with the added flexibility of the active filters enabling best use to be made of the five conventional cone units — one bass, two

mid-range, two upper-frequency speakers — variously selected for best operation in the chosen ranges.

Given greater financial freedom in the choice of the output units, it seemed an attractive idea to apply such a mixed mono/stereo arrangement to a three-speaker system, using a single cone bass

unit working between a pair of Quad electrostatic radiators. An obvious benefit of band-sharing in this way was that the use of the single bass speaker relieved the electrostatic units of having to produce possibly loud sounds in that part of the audio spectrum where they are at their lowest efficiency and where, especially at

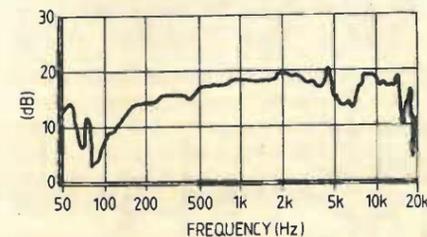


Fig. 1. Basis of modified design is this on-axis speaker response curve.

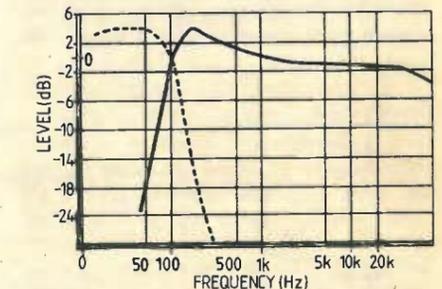


Fig. 2. New crossover frequency of 100Hz is chosen for dual electrostatic + common bass combination.

IN OUR NEXT ISSUE

Digital capacitance meter

This is a charge-injection capacitance meter, which is provided with a well thought out input-protection circuit to guard any initial charge on the capacitor to be measured. Sources of error in the protection circuit and elsewhere are analysed.

New Wien-bridge oscillator

John Linsley Hood describes an alternative way of using the Wien network to design low-frequency oscillators. The typical total harmonic distortion of a simple oscillator of this type is about 0.001%, instead of 0.01% in the conventional configuration. There is also an optoelectronic amplitude stabilizer.

Active television deflector

Constructing a device to help people who live in deep valleys or other places where u.h.f. television broadcasts can't be received normally. Placed on a vantage point nearby, it picks up the tv signal, amplifies it and re-transmits it to the viewer's house on the same frequency.

On sale 18 March

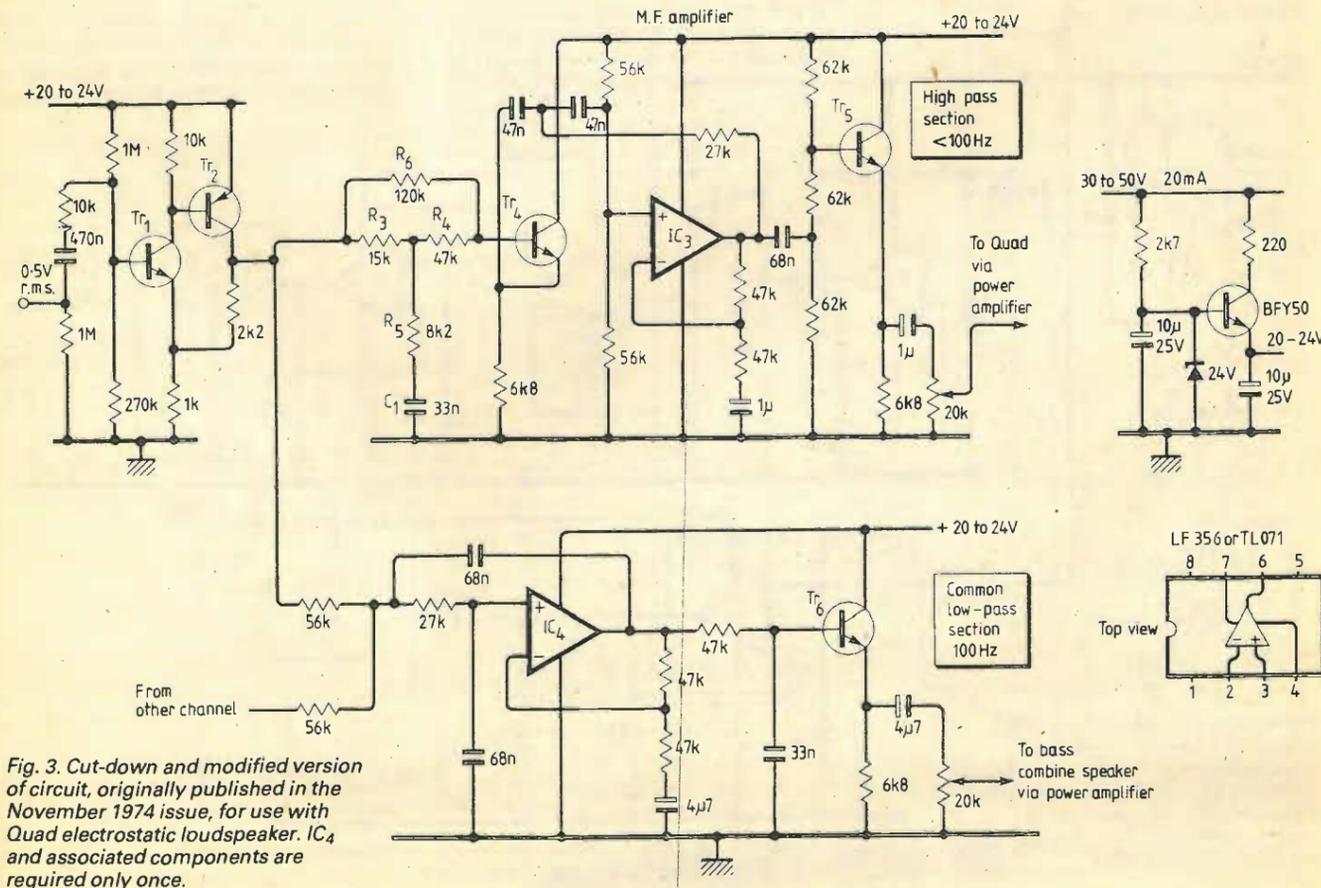


Fig. 3. Cut-down and modified version of circuit, originally published in the November 1974 issue, for use with Quad electrostatic loudspeaker. IC4 and associated components are required only once.

NEWS OF THE MONTH

Microcomputers in space

British Aerospace. Space and Communications Division is developing a spacecraft microcomputer module (SMM) as a standard unit suitable for general application in satellite systems. In addition to the hardware, the Division is also developing the necessary computer programs which includes all the basic executive routines needed to control an SMM system.

Eash SMM is a totally self-contained microcomputer. One of the design aspects of particular note is that of flexibility in choice of microprocessor used. The SMM development system at the Space and Communications Division currently comprises a Ferranti F100-L, three Texas Instrument 9900's and a DEC PDP11/34 mini computer, all running with compatible software and common hardware interfaces.

The F100-L which has been selected for use with SMM in the immediate future, is a bipolar microprocessor with low-power dissipation, manufactured by Ferranti as an LSI circuit on a single chip encapsulated in a 40-pin dual-in-line package. Military standard F100-L microprocessors are subjected to additional special testing and screening before being nominated for service in space.

A method of interconnecting up to 64 SMMs has been developed such that not only can their processing capabilities be shared for complex computations, but tasks may be transferred to other units should faults arise in individual devices. Input/output functions are performed by non-intelligent modules which are linked in an SMM system by a two-wire serial data bus designed by the Space and Communications Division.

An addressable serial bus interface circuit (ASBIC) is used as the standard interface for connecting a module to the bus.

Data and control instructions are transferred as 32-bit long words via the bus at 500 kilobits per second. The ASBIC performs all data synchronisation, module address detection and the serial-to-parallel and parallel-to-serial conversions necessary when transferring information between a module and the bus.

An ASBIC comprises a single 40-pin ceramic dual-in-line package. It is an LSI circuit manufactured by Ferranti using collector diffusion isolation and the uncommitted logic array technology developed by that company. It is TTL compatible, and importantly, operates at very low power levels from a single 5v source, an advance over similar circuits using hybrid and discrete technologies. It contains a 16-bit parallel data highway ideally suited to microprocessor applications and is manufactured to full military specifications. Utilising ASBIC, non-intelligent terminals can be adapted for connection to the data bus with the minimum of additional circuitry.

The configuration of the SMM and the selection of the military version of the Ferranti F100L microprocessor is the outcome of an engineering study carried out over the last 18 months by the Space and Communications Division to assess the operational characteristics required of microprocessors for prolonged service in space, aboard satellites. The F100-L was selected because its bipolar technology renders

it inherently more resistant to radiation damage, with the added merit that it is the only 16-bit microprocessor wholly designed, developed and manufactured within Europe. Throughout the study, liaison was maintained with the European Space Agency (ESA) to ensure the technical solutions proposed were compatible with data handling requirements for satellites specified by ESA.

Before the study began, British Aerospace Dynamics Group had already acquired considerable knowledge of the factors likely to influence computer operations in space as a result of previous privately-funded technical evaluations. The Group is continuing to invest money in the current research and development work, the cost of which is being shared by the Department of Industry as part of the UK Space Technology Programme.

The Space and Communications Division will be incorporating SMMs in the next generation of satellite systems they build and have begun evaluating the device with its supporting components to qualify it for use in the space environment. In addition to space, it is envisaged that SMMs will be eminently suited for a wide variety of data handling applications.

Computer in case

Intended for the 'globe trotting' reporter, salesman, engineer, programmer, auditor etc, model 8400 computer is fitted into a briefcase.

Produced by Microdata Computers Ltd, in Hayes, Middlesex, the computer incorporates many features to make it not only portable but also of practical use: it may be connected to a wide range of power supplies' voltages and frequencies and so may be used almost anywhere



An early prototype of the Microdata model 8400 briefcase computer, now going into production.

China standardizes in Industry

From a previous policy of self-reliance, China has embarked on a comprehensive programme of modernisation including a number of product standards and a building and civil engineering code. Details are included in a report, *Exporting to China*, prepared by the Standards Association of New Zealand and available from the British Standards Institute's Technical Help to Exporters service.

Chinese standards are divided into three grades - national, ministerial and enterprise - and the policy for each grade is explained. Details are given of the types of products covered by the mandatory National Standards. There are two Chinese standards covering labelling requirements for shipped goods and the labels are clearly illustrated. The report includes full addresses of all relevant organisations, corporations and embassies.


As if to underline that such trade is not necessarily one-way, Hitachi have announced the signing of a contract for the establishment of a joint venture company in Fujian Province, China for the production of television sets. Intended for domestic sales and for export, the company expects to be producing 200,000 colour and 180,000 black-and-white tv sets per year.

in the world; it incorporates a real time clock which can display GMT and local time; it includes acoustic couplers for transmission and reception of programmes or data through the telephone network. There is a full ASCII keyboard, a fold-away dot matrix gas plasma screen with a capacity of 480 characters; there is full text processing capability and the magnetic bubble memory does not lose data when the power is removed.

Integrated circuits to your own design

Isolated oxide CMOS, or ISO-CMOS, can be used to produce integrated circuit devices of higher speed, lower power consumption, lower propagation delays, higher densities and lower cost per function, according to the new GEC company, Marconi Electronic Devices Ltd which has been set up to combine ISO-CMOS with the established Cellmos computer-aided integrated circuit design service, the combined service to be known as ISO-Cellmos. By the addition of bigger and better computers and improvements in software, the service can now take a logic design, feed it into the computer which can analyse the circuit and can demonstrate the output response to any given input waveform. It can then select the appropriate gates from its own library and place them automatically in relation to each other to produce an optimal layout. The interconnect tracking is also laid out automatically. The layout is then analysed with capacitance measurements and checking for the effects of possible transients. It is also checked against the design rule book.

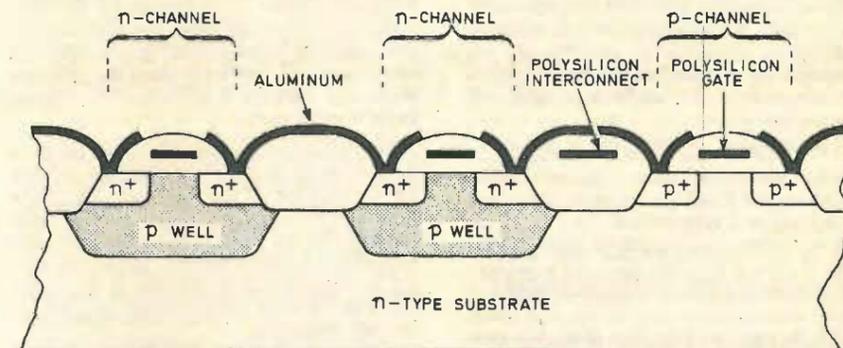All this has taken place within seconds of entering the original design into the computer. Two plots are produced; one of the proposed layout with pad positions etc. The other is a diagram of the chip in logic diagram form, allowing the customer to check it against his original circuit. At this stage, changes to the circuit may be made to correct any errors or to



This cross section illustrates the basic principle of ISO-CMOS

add modifications.

Once the layouts are accepted by the customer, they can be simply translated into magnetic tape format for the automatic preparation of production masks. At the same time test tapes are generated for the automatic testing of the finished integrated circuits.

A simpler and even more rapid approach is suitable for those circuits which can be adapted to the ISO-CMOS uncommitted logic array. The Cellmos system can generate a layout for the interconnection pattern which can be added

to ULAs available from stock. As these have fixed connection pad positions a testing facility is instantly available.

Thus the Cellmos system can design and layout a circuit in seconds - a job that would take a competent design engineer at least three months.

The new company, Marconi Electronic Devices Ltd, as well as providing the Iso-Cellmos service, has also taken under its wing the microwave, power and hybrid component divisions of the GEC/Marconi group.

Keyboard research

It has long been known that the 'qwerty' keyboard is not the most efficient way of arranging the letters. In fact it was originally designed to slow down the typist so that the primitive mechanics of early typewriters could cope with the task and not suffer from entanglements. The European Commission is inviting tenders for a unified keyboard layout suitable for the many languages based on the Latin alphabet. The keyboard layout will be used within the Commission and other European or international organisations who need to deal with many languages. Whether the research will lead to a major re-design of keyboard layout or just a tidy-up exercise of the comparatively minor differences in the various nationality keyboards remains to be seen.

Authors recognise technical writers

The Society of Authors (a professional society representing over 3000 writers) has under consideration a plan to form a Technical Writers' Group within the Society, to cater for the needs of technical and scientific authors. Those who write about technology are themselves much affected by the introduction of new technology in publishing and printing, and by rapid changes occurring in this field of writing.

The formation of a special Group would provide technical writers, in addition to the normal services of the Society, with the benefit of a core of expertise in this expanding area of writing and the opportunity to discuss problems common to technical and scientific writers.

These matters were discussed by Stanley Lyons in a special article in *The Author* recently. Copies of this - and further details about the Society - may be obtained gratis from the Society.

Centre to study effects of technology on society

The interaction of electronic systems such as computers and data processing equipment with society at large may well be one of the subjects to be studied by a new research centre now being set up in the UK. Called the Technical Change Centre, it is mainly concerned with the relationship of technology to economic well-being in the UK: it will develop "a major programme of research on the choice, management and acceptability of technical change relevant to the advancement of the national economy" in the words of its official statement. But it will also study changes in society and the economy which act as pressures influencing the course of technical innovation. A related area of research will be "trade-offs" between economic advance and social loss (in such matters as pollution and conservation) and the way technical change could be planned so as to reduce the inevitable disruption it causes in people's social and occupational lives.

The economic bias of the TUC is reflected in the choice of its director, who is an economist, Professor Sir Bruce Williams. Among many other appointments he was economic adviser to the Minister of Technology in 1967. Electronics interests are represented by the organizing committee having as one of its members Philip Hughes, who is managing director of Logica, the well-known software and electronics company. Funding comes from the Leverhulme Trust, which will contribute £1.5m over the first five years, and from the Science Research Council and the Social Science Research Council, each of which will provide £525,000 over the same period. Eventually the Centre is expected to have an annual budget of £750,000, with some of its revenue coming from commissioned research.

To some extent the TCC resembles the Office of Technology Assessment (OTA) which was established in the USA in 1972 - but by law. It is intended to be of practical help to those technocrats in government, industry and elsewhere who have the task of shaping public policies to respond to technological development and the changing position of the UK in the world economy.

Gallium arsenide invades Silicon Valley

The Harris Corporation is moving ahead on its first semiconductor operation in San Francisco's famed 'Silicon Valley' area by approving construction of a \$4 million facility in Milpitas, near San José.

The company is making the investment on behalf of an 80-per-cent-owned new company, Harris Microwave Semiconductor, Inc. The firm was established last June by Harris and a group of local semiconductor executive, specialising in the new field of gallium arsenide technology.

Gallium arsenide is a compound of two elements, gallium and arsenic. As a base material for integrated circuits, it offers significant advantages over silicon in applications requiring very good speed, high frequencies and extreme miniaturisation. Harris will use this technology to produce gallium arsenide transistors, microwave components and integrated circuits to support their communications and information processing equipment now under development.

Flat c.r.t from Sinclair

Clive Sinclair of Sinclair Research Ltd has recently announced the successful development of a flat cathode ray tube which will be incorporated into a miniature t.v. set. The set will include v.h.f./f.m. radio and may be switched to most international t.v. standards, making it of universal use.

The Sinclair tube measures about $4 \times 2 \times \frac{3}{4}$ in. and is three times brighter, requires between one quarter and a tenth of the power and is half the volume of a conventional c.r.t. with the same size screen. It is assembled from just two sheets of glass, a flat front plate and a vacuum-formed backing plate. The phosphor screen is coated on the inside of the backing plate and is viewed through the front face from the same




side that the electrons strike. This gives a brightness of more than double that of a conventional c.r.t. with the same beam energy. In addition to the horizontal and vertical deflection plates there is a third set between the phosphor screen and the front face to bend the electron beam on to the screen.

To correct for distortion the screen height is reduced by as much as half while the width is kept constant. This narrows the angle subtended by the electron beam and the picture height is restored optically by using a horizontal Fresnel lens to give an effective picture size with a 3 in. diagonal. Other distortion is eliminated by careful attention to the modulation applied to the deflection plates.

The tube has been produced in Sinclair's pilot production plant at St Ives, Cambridge but it has just been announced that a full production plant is to be commissioned in Dundee by the Timex Corporation. Timex were awarded the contract by Sinclair because of their expertise in automatic production. It is expected that at the end of the first phase the capacity will exist to produce the tubes at the rate of a million a year.

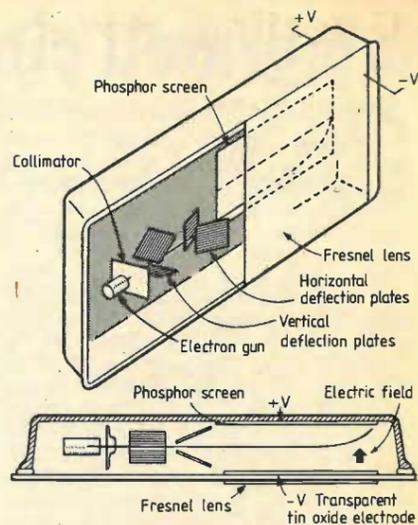The Microvision t.v. set which will incorporate the tube is also to be produced by Timex and should be on the market by mid-1982. Although the exterior design of the set has not been completed, some design models have been produced to show that the set will be about $6 \times$



4×1 in. or about the size of a paperback book. It will retail for about £50.

Further developments for the tube depend upon the extremely high brightness which may be achieved. This leads to its suitability for use in projection systems. A monitor for the Sinclair personal computer is high on the applications list, as is a colour projection t.v. which would incorporate three of the tubes and the associated electronics in a projector about the size of a shoe box to produce a picture on a wall screen with a 50 in. diagonal.

Electronics bosses disagree on industry's priorities

Opposing views on the future of the British electronics industry were expressed recently by two of its prominent figures, Mr Ernest Harrison, chairman and chief executive of Racal, and Mr Frank Chorley, deputy chairman and managing director of Plessey Electronic Systems. Mr Harrison believes that rationalisation will be necessary in the UK industry to meet foreign competition effectively. In a speech to stockbrokers, industrialists and financial journalists he said: "If we are to survive as a nation in professional electronics, or indeed in any of the electronics industries, we have got to do something about our resources and getting together. We are going to face in the 'eighties the might of Japan and America and these two countries are determined to dominate the world. They spend huge sums on research and development the like of which we cannot imagine. . . . The competition is going to be intense and it cannot be avoided". Referring to the rationalisation that had already taken place - Racal taking over Decca and Thorn taking over EMI - Mr Harrison claimed that "many more people now agree with what I have been saying for a long time".

One exception, however, is Frank Chorley. "I certainly don't agree with Ernie on that," he said, in reply to a question at a press lunch. "It's a good idea to scrap it out, because it makes us all more efficient." Companies in the UK industry were well able to look after themselves. Racal, Marconi and Plessey were all highly successful, though they were perhaps not good in all areas. There was no benefit to be gained by bringing them together.

A further difference of attitude emerged on the two companies' involvement in military electronics. Despite the fact that a large proportion of Racal's business has always been in this field (about 38% recently), and is likely to continue so with the acquisition of Decca, Mr Harrison declared: "We are too much in Defence.

This is much too large a proportion of our total business. What about the many applications for electronics in the old manufacturing industries in the UK? Who's going to do them?" He gave one example of a civil application which was fairly new to Racal - electronic funds transfer. A new company was doing a lot of development in this area and it had a good product but things were moving slowly because "the banks cannot make their minds up".

Mr Chorley's attitude about his own company, however, was that "The Defence industry is very successful in the UK. From time to time Socialist MPs have complained to me that we

ought to make calculators and other such products, but we have got to do what we are good at. We have got to exploit the market that already exists for us. The UK has a significant lead in this field - so why not exploit it?"

One matter on which both men were agreed was that the UK electronics industry should be supported by the government. Referring to the billions of pounds that the present administration is now pouring into steel and motor cars, Mr Harrison commented enviously "Just imagine what you could do in this business if you were given a billion pounds to invest in electronic projects".

Fourth TV channel signal monitoring

The quality of the transmitted signal of the new fourth television network due to go into service in the autumn of 1982 (News, January issue) will be monitored by automatic equipment. Instruments will be provided for the complete network of main stations. Each of these is under the supervision of a station controller which in turn is linked back to a computer at a regional operations centre. The automatic monitoring equipment, based on a Marconi Instruments

Alternatives for society

Appropriate technology, community communications, alternatives to nuclear energy and self-regulating education are among the alternatives to existing centralized institutions to be discussed in 30 small forums at the First Assembly of the Fourth World, London, July 29-31. According to its convener, John Papworth, "Human survival now depends on the swiftness with which our political, social and economic institutions can be made small enough for them to be manageable and more adequately responsive to human control." The education forum will be guided by Dr K. L. Smith of the

insertion signal analyser, operates under software control. All parameters important in the maintenance of picture quality can be monitored and the results compared with limits stored in the equipment. Warnings can then be given and executive action taken if any parameter falls outside its defined limits.

The monitoring equipment is being provided for the IBA by Marconi Instruments under a contract worth over £500,000.

Electronics Laboratories, University of Kent at Canterbury. Details from Fourth World, 24 Abercorn Place, London NW8 (tel: 01-286 4366).

More news from Sinclair


To be launched at the Microsystems '81 exhibition is a new Sinclair personal computer. It will incorporate a new, British, custom-built master chip, have a 'significantly higher specification' than the successful ZX80 and yet will be marketed at a 'substantially reduced price'. Details are also to be announced of a low cost printer and supporting software libraries.

Detecting drivers' behaviour

An electronic indicator which can be laid simply and quickly on a road surface to spot faulty driving has been developed by engineers and psychologists working in the School of Automotive Studies at the Cranfield Institute of Technology.

Although its most obvious use is to alert police to drivers who are drink-impaired, the Speed and Alignment Indicator can also be used to monitor speed alone. It could play a part in studies of driver behaviour too - a field in which there are many opinions, much speculation, but few certain ways of finding out precisely how drivers drive their cars.

When laid on the road the indicator looks like the rubber tubing used to count passing vehicles. Two tubes are laid parallel to one another across the carriageway and six feet apart. Beyond them is another set of tubes arranged like an arrowhead pointing in the same direction as the traffic flow. Each tube has a transducer which converts the pressure of vehicle wheels passing over them into an electronic signal to a micro-computer by the roadside. The micro converts the signals into the speed of the vehicle and its alignment on the road.

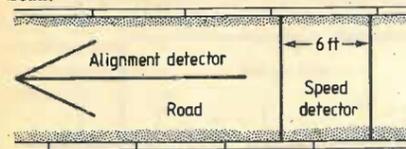

Vehicle speed is computed from the interval in time between the wheels passing over each of the two parallel tubes. Alignment is computed by the driver first of all driving along a straight

line laid up the centre of the carriageway. This line ends at the arrow's tip, from which two rubber arms slope away - the shape of an arrowhead. If the driver has aligned the two arms of the arrowhead simultaneously. If one wheel strikes its arm ahead of the other, the vehicle must be off the centre line.

The micro-computer is both 'Intelligent' and versatile, making a decision in milliseconds on whether a driver has passed or failed each of the two tests set by the operator. He/she can pre-programme the device with the speed limit of the road and can also decide on the margin of error allowed to a driver on the alignment test. British or metric units can be chosen and the indicator will give separate decisions on speed and alignment. The micro's decisions are flashed on a screen in front of the operator as 'pass' or 'fail' together with the figures for speed and the number of inches or centimetres by which the car is veering from the centre line. The decisions are also printed out, and a warning buzzer sounds when the error limits are exceeded. The indicator can be set to record every vehicle passing, or it can print out for failures only - whichever mode the operator chooses.

The equipment is compact and easy to use. It can be carried round in the smallest of cars. The Speed and Alignment Indicator is a prototype only at the moment, but it can be made and marketed easily if there is a demand for it. If police forces were interested in using it, the indicator could be set up on a road with a warning sign telling motorists that they were about to be tested. Drivers would then align with the guide line to the arrowhead and drive along it: if the indicator showed a driver to be

Approval and dis-approval for telephones

Although, under the policies of the present Government, British Telecom is to lose its monopoly of providing telephones and other attachments for use on telephone lines, it is very much concerned that there will not be a free-for-all. At present the only equipment permitted is that certified by British Telecom as suitable for use as an attachment. This ensures that the equipment is technically compatible with the British

network; it presents a minimal risk of injuring people or damaging the system; it does not interfere with other customers' use of the network; and it is correctly connected, to help in diagnosing faults. Even when British Telecom lose the monopoly, they will still be the sole supplier of the first telephone connected to the exchange line entering a person's home or office, under new arrangements proposed by the

out of alignment he could be stopped further down the road and asked to take a breath test.

At the moment police can stop a motorist and test him if they have 'reason to believe' he might have drunk too much alcohol, but there is no objective test of this and motorists have always opposed random testing.

The indicator could also be used to study driver behaviour by being set up to show, for example, how people take corners, road position, etc. There is no objective, accurate and easy way of obtaining this information at the moment.

C.b. to become legal with f.m.

Mr William Whitelaw, the Home Secretary, has announced that Citizen's Band, officially still known as Open Channel, radio is likely to become legal in the autumn of 1981. Two wavebands are to be allocated, 27MHz and 930MHz both to be frequency modulated. Amplitude modulation is to remain illegal and f.m. operators will require a licence. No details are available as to the maximum permissible signal strength or the number of channels but a draft specification will be issued to potential manufacturers.

The European Communities Commission is attempting to produce a harmonised set of technical regulations covering c.b. sets and are studying French proposals for a 27MHz service with a maximum strength of two watts and fewer than 22 channels.

Wireless World will be publishing a series of constructional articles for those wishing to build a c.b. set.



Government. Certification of the suitability of attachments will continue but will be no longer carried out by British Telecom but by an independent Government approved body which will establish and publish standards for privately supplied attachments and then test and certify that the attachments conform to the standards.

British Telecom warns that most telephone equipment now on sale in shops and department stores is not specially designed or modified for use on the British network, despite various claims that it 'meets British Post Office standards'. It is nearly all made and designed for use abroad. If connected to the British network, it may not work properly. Phones designed for overseas use are frequently insufficiently sensitive for satisfactory operation on all lines in the U.K. Mains-powered equipment can be electrically unsafe. Not only do the owners of such equipment suffer, but also the callers whose calls are made ineffective if the apparatus does not respond correctly, or gives poor quality reception. British Telecom are threatening, regretfully, to disconnect the telephone lines of customers who persist in using uncertified equipment.

To counter the sales of such illicit phones, British Telecom are continuing their programme of offering a wider range of telephones to be supplied direct to the customer. Two additions to the range are illustrated. On the left is Dawn. Intended for the boudoir, it has a low, sculptured profile on a circular base and is available in pale yellow, avocado green and white. The one-piece Eiger telephone, with a press-button keypad, includes a memory to store the last number called. It can call again automatically, if required to. The colours are more business-like; red, stone or two-tone brown.

CIRCUIT IDEAS

Divide by (2n-1)

Fig. 1(a) shows a divide-by-(2n-1) circuit which generates an equal mark-to-space ratio output if a divide-by-2 circuit is used in the final stage as shown in Fig. 1(b). With this arrangement, a divide-by-(n-1/2) output is available from the divide-by-n counter, but not with an equal mark-to-space ratio. Fig. 2 shows a divide-by-3 circuit, based on Fig. 1, where the divide-by-4 counter is clocked by a positive edge of the input waveform and then by a negative edge. During one complete output cycle the divide-by-4 counter receives four clocking pulses for three cycles of the input waveform. A divide-by-(n-1/2), i.e. divide-by-1 1/2, output is available from QA.

With the basic circuit of Fig. 1(a) it is easy to build other odd value counters by inserting the desired divide-by-2n circuit. Also, by combining divide-by-(2n-1) and divide-by-2n circuits, a counter can be designed to divide by any value of (2n-1). Some examples are shown in Fig. 3. Note that inputs and outputs between the various exclusive-OR gates must be separated by a counter.

A. J. Ewins
Harrow
Middx

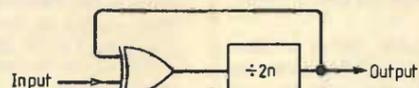


Fig 1(a) Divide-by-(2n-1)

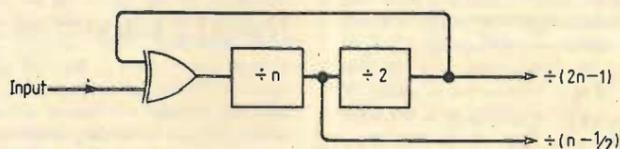


Fig 1(b) Divide-by-(2n-1) with (n-1/2) output

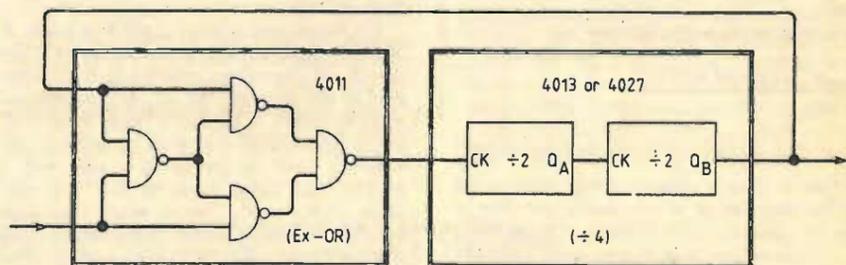


Fig 2(a) divide-by-3 circuit



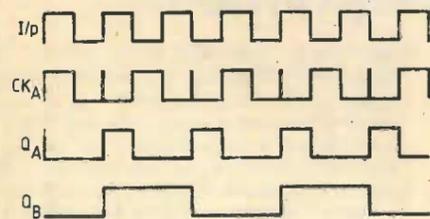


Fig 2(b) Waveforms of divide-by-3 circuit

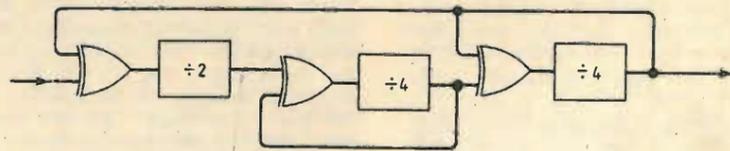


Divide-by-17

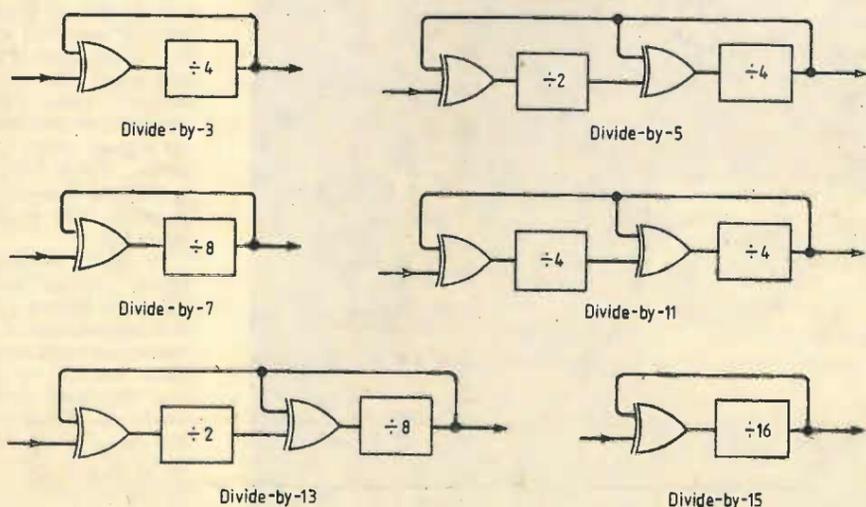

Pre-amp with multisection tone control

The input stage of this preamp, which originates from a studio mixer, will handle signal levels from 500µV to 5V r.m.s. For optimum performance the preset control should feed 5mV to Tr₂ which, with A₁, amplifies the signal to 3V r.m.s. The filters around gyrators A₃ to A₇ provide low-impedance paths to ground for five frequency bands, and attenuation or gain for these bands is achieved by controlling the low-impedance paths towards the voltage dividers around A₂. Balancing the filter potentiometers gives unity gain at A₂ because the input and feedback voltage-dividing networks cancel each other. The open-loop gain of the op-amps determines the maximum number of gyrators that can be used. At 15kHz the paralleled gyrator series resistors, 180Ω and 330Ω, which are boot strapped by the open-loop gain, should still be greater than the divider source impedances, 2k7, and prevent unexpected dips or peaks at high frequencies.

H. Riegstra
Amsterdam
Holland

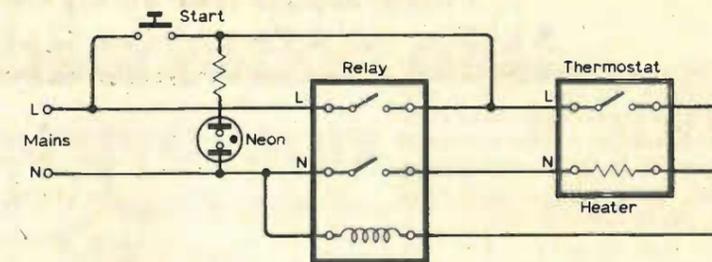


One-shot control of immersion heaters

A conventional immersion heater requires two operations, switching on and later switching off. Although simple, the second step is inconvenient and costly if forgotten. This simple circuit is easy to install and obviates the need to manually switch off the heater. A relay forms a one-shot monostable which is thermally rather than electrically controlled. A trigger is provided by the start button which energizes the relay coil, and the heater is powered until the thermostat cuts out and de-ener-

gizes the coil. Water temperature, and therefore the duration of the on period, can be adjusted via the thermostat setting. Apart from the relay connections, only one extra low-current wire is required between the start button and the thermostat.

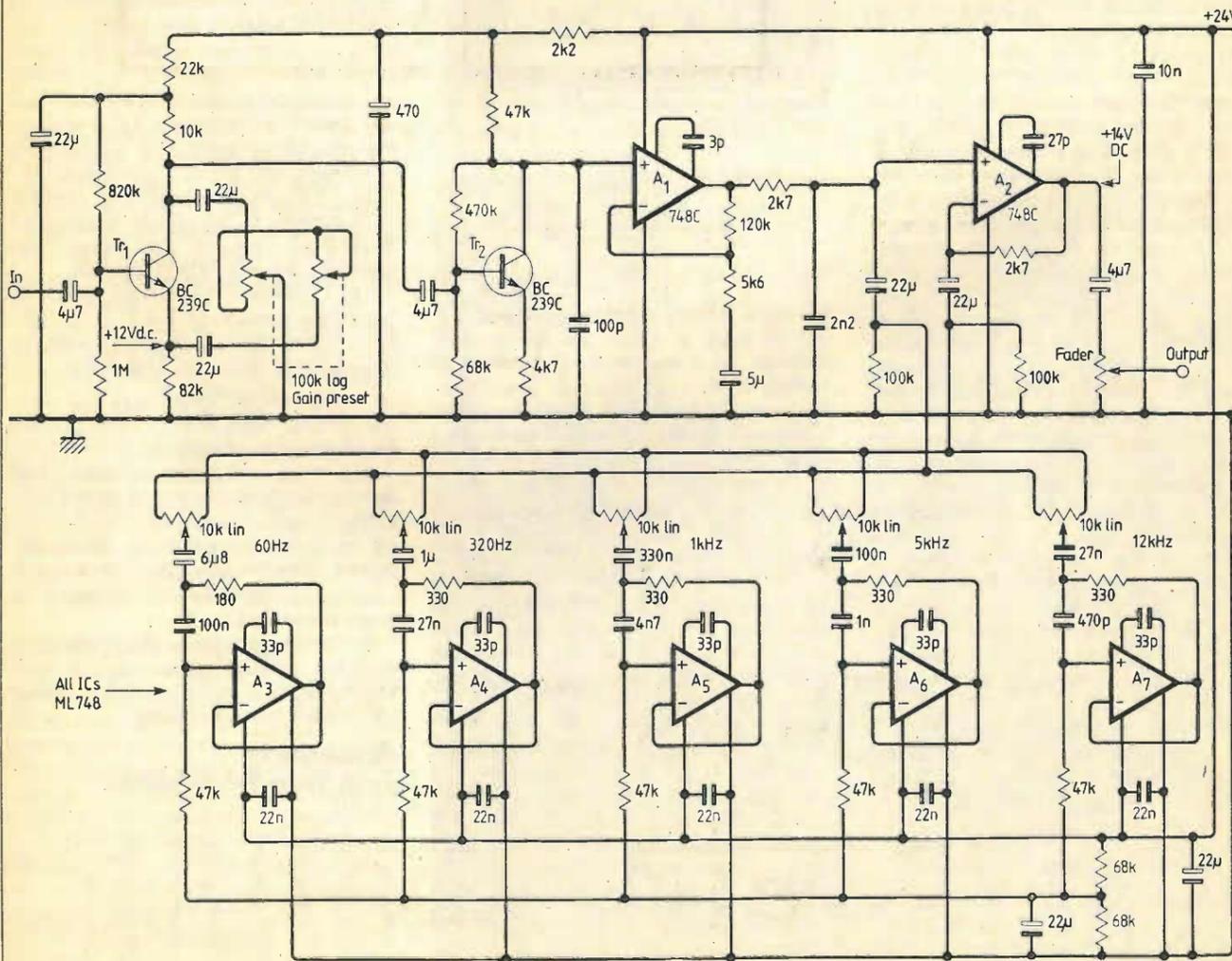This circuit can also be used to isolate equipment from the mains after a power failure.
S. Ho and
D. Wibberley
Manchester




Power supply with stable current limit

One problem with power supply current limits, which use the V_{BE} drop of a transistor, is their drift with temperature variation. A simple solution is to use a programmable Zener diode for current sensing, which offers less than 50 p.p.m./°C variation in V_{ref} . In the circuit shown

$$I_{limit} = \frac{V_{ref} - aV_{ref}}{R_{Sc}}$$

When the voltage at the R terminal of TL431 switches it on, base drive for the output transistors is removed and the output current is limited. However, if the output terminals are shorted, the TL431 is turned on but the voltage across it is 2.5V. Therefore, to take the output voltage to zero, V_z is required which can be any low voltage Zener diode above 2V.

M. S. Suresh
Bangalore
India

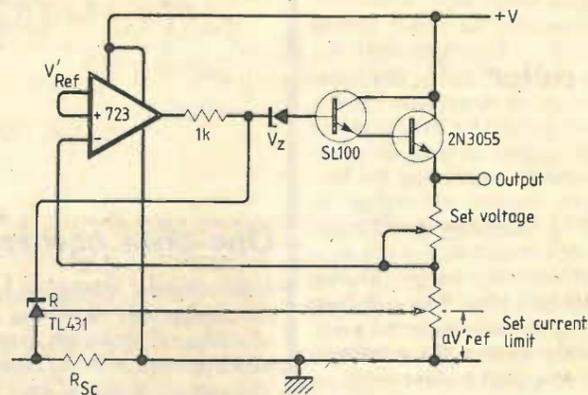

"Test your knowledge"


Answers to the December issue multiple-choice quiz

None of the entries received for Test Your Knowledge was completely correct, and the best entries had at least three of the answers wrong. That was one result of the quiz compiled by R. W. Ellingham and B. L. Hart and published in last December's issue. The stiff test was based on 40 questions, each with multiple answers, given to electronics students at the North East London Polytechnic. We offered prizes of Circuit Designs 3 or a subscription to *Wireless World* for ten correct entries opened after 5 January for UK readers and 2 March for overseas.

The answers provided by the authors are given in the panel. As almost all entrants gave the incorrect answers to questions 3, 24 and 34 (no-one got this last right), here are their solutions.

Question 3. The assertion is not true. A bipolar junction transistor comprises two p-n junctions both of which are forward biased when the device is saturated. By suitable biasing it is possible to arrange for the two junction drops to be equal in magnitude.

The reason is a true statement. Operation of the b.j.t. depends on the existence of both electrons and holes. Therefore (d) is the correct answer. Most thought (b).

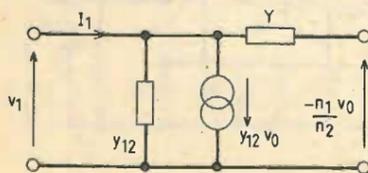

Question 24. See diagram. For neutralization $I_1 = 0$ when $v_1 = 0$.

$$y_{12}v_0 = -\frac{n_1}{n_2}v_0Y$$

$$Y = -\frac{n_2}{n_1}y_{12}$$

$$= -2(-j0.2) = j0.4mS \quad (d)$$

Question 34. Upper trip level corresponds to the level at which the comparator switches for a positive-going input. Assuming $V_0 = -12V$, the p.d. across the $8k\Omega$ resistor keeps the + input of the comparator below +4V, hence the output stays at -12V, until i_g increases to $i_g = (+4 - (-8))/8k\Omega$ which is 1.5mA, so (b) is correct, but everyone gave (c).

About half the entrants gave incorrect choices for questions 8, 9, 18, 36 and 37. In Q8, $I_c = ((I_b/I_b) + 1)I_b = 110mA$ and in Q9 zener current varies between 1mA ($I_b = 9mA$) and 10mA so the mean dissipation is $5V \times 5.5mA$. In Q18, the solution is found by equating the increase and decrease in charge first across the input C, to give $v = -E/3$ then across the output C to give $E_0 = Mv/3$. Those who got Q36 wrong gave (e) as the answer but the correct frequency is 50kHz. The period is obtained from $2 \times (CAV/D)$, due to current mirror action, giving 50kHz. Most entrants realised that the 150kHz printed for (d) was intended to read 50kHz. The minimum frequency, Q37, is one tenth of that.

Other answers were less frequently wrong, but more consistently so. In the answers to question 11, emitter current

was invariably given where collector current wasn't. For question 23, it appears that the transformation ratio was taken to be the square of X_{C1}/X_{C2} rather than $(X_{C1} + X_{C2})/X_{C2}$. As the amplifier of question 27 is matched to the source, actual noise power is twice the ideal noise power. That makes the noise figure 3dB, not 0dB.

The Thévenin equivalent circuit is needed for question 33. For V_0 to be high, the + input at the comparator must be more positive than -1V. This means

$$\frac{R_2(10/3) + 2}{R_2 + (R_1/3)} > 1,$$

from which the answer follows.

Only a few got question 22 wrong, but one that did, Jeffrey Borish of Santa Clara, California, wrote to correct his answer saying the question could be a "deliciously wicked trick," depending on whether c.m.r.r. was taken for the differential or single-ended output.

At the time of going to press the cut-off date for overseas readers hadn't been reached but prizes for the best UK entries have already been despatched. □

Answers to Test Your Knowledge

1	C	11	D	21	B	31	B
2	B	12	E	22	B	32	D
3	D	13	A	23	B	33	B
4	B	14	B	24	D	34	B
5	B	15	D	25	C	35	B
6	C	16	E	26	B	36	D(50kHz)
7	C	17	D	27	D	37	A
8	C	18	B	28	A	38	C
9	C	19	E	29	B	39	C
10	E	20	A	30	C	40	D

Radio observation of the 'active' sun

Solar effects on propagation recorded on home-made apparatus

by R. A. Ham

Since 1968 the author has used a simple radio telescope constantly to monitor the effects of solar activity on radio frequencies. This article is a brief history of sunspotters followed by a chronicle of solar events and outlines of the equipment used to make the recordings.

Until the advent of radio it was not realized that the sun, and indeed other stars, emitted radio waves. However, suspicions were aroused very early in radio's history as Sir Oliver Lodge tried to detect radio waves from the sun using a receiver with a coherer detector, and the editor of the *Scientific American* called upon radio enthusiasts to listen carefully during the total eclipse of the sun on 24 January 1925 and report any strange happenings to radio signals.

Short-wave bands

Throughout the pioneering days of the short-wave bands for broadcasting both amateurs and professionals were trying to explain why the propagation of radio signals varied between day and night and was often subject to echoing, fading and sudden blackouts.

Scientists such as Oliver Heaviside, Arthur Kennelly and Professor (later Sir) Edward Appleton had shown how the existence and structure of the ionosphere reflected short-wave signals around the world. But as more evidence was gathered by astronomers, physicists and radio engineers it was soon realized that streams of particles from a solar event, Fig. 1, could disrupt the prevailing state of the ionosphere and consequently upset the normal paths of terrestrial radio signals.

Solar radio astronomy

Signs of radio being used as an astronomer's tool date back at least to 1935 when Karl Jansky first detected radio waves coming from the sun in the Milky Way. Later in the same year Denis Heightman heard a hissing noise in the 10m band which was later confirmed as being caused by radio waves coming from a solar event. Between 1936 and 1939 this same noise was reported by no less than 24 amateurs using the same frequency, and by Miss Barbara Dunn while using a frequency of 56MHz.

Early in 1942 British wartime operators using similar frequencies recorded an



Fig. 1. Solar prominence photographed from the 'spectroheliograph' by Cmdr Hatfield on 10 February 1976.

extraordinarily high level of noise which was also found to be the result of a large sunspot group and soon after the war research into solar radio waves and their effects on radio was stepped up.

Simple radio telescope

Having heard the effects of solar noise, the author decided to build a simple radio telescope*, to find out more about the 'active' sun and its effects on terrestrial radio communications. The radio waves from the sun at 143MHz are collected by four 4-element yagis mounted on a wire mesh reflector, Fig. 2, which has a head amplifier mounted on its frame. The amplified signal passes along a coaxial cable to a 2m converter, where the observational frequency, having been changed to 27MHz, is tuned on an FRG-7 communications receiver which in turn drives a

* The author's radio telescope was featured in 'Tomorrow's World' by the BBC and in a scientific film made by Yorkshire Television and networked by the IBA.



Fig. 2. Four 4-element yagis used to collect radio waves from the sun.

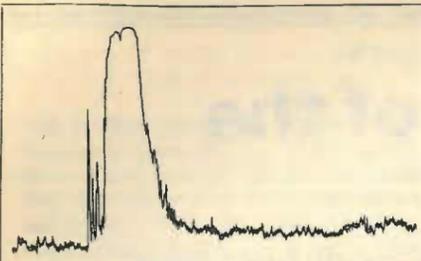


Fig. 3. Chart recording of a typical short duration solar flare.

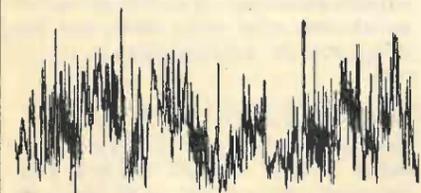


Fig. 4. A ten minute recording of a solar noise storm which occurred on 30 October 1973 at 136MHz.

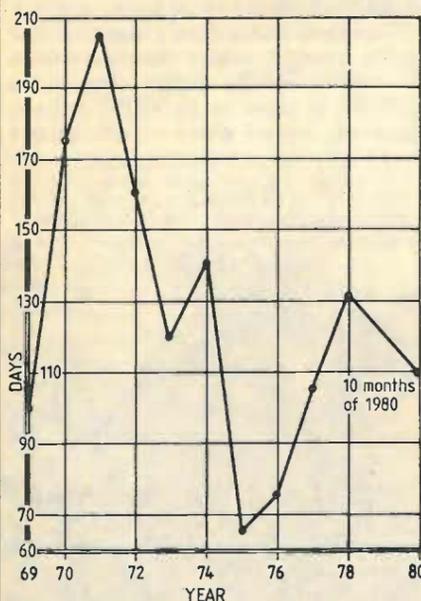


Fig. 5. Solar activity as recorded by the author originally at 136MHz and later at 143MHz (see text). Note that the peak in '71, the low in '75/'76 and the rise thereafter correspond with the recognized cycles.

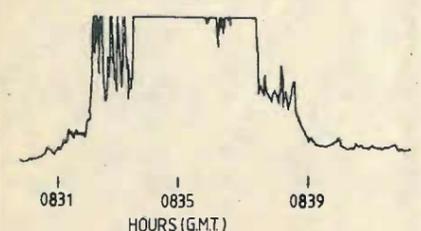


Fig. 6. One of the more memorable solar bursts from 3 July 1974 in which the recorder pen was sent off the scale.

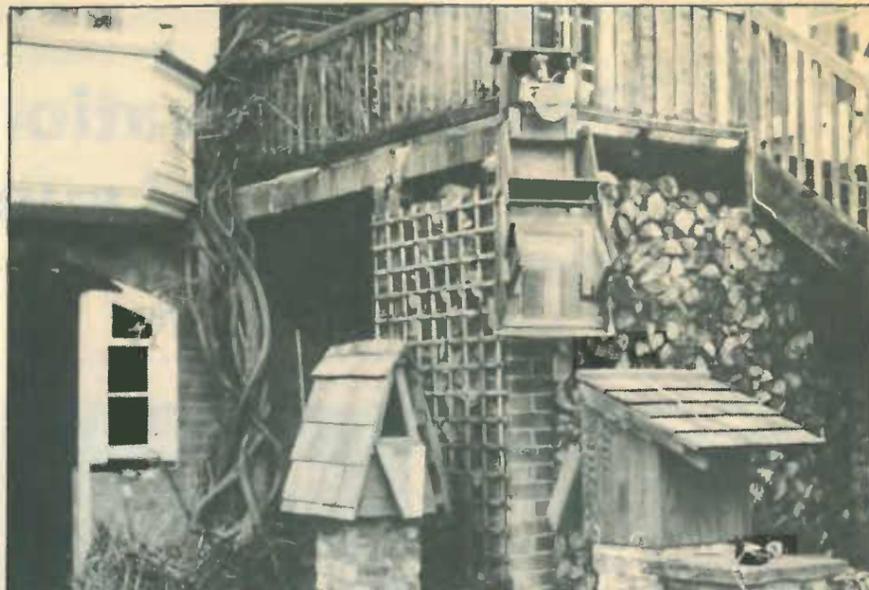


Fig. 7. The spectroheliograph. A mirror (top centre) follows the sun and reflects light towards the second unit (bottom right) which in turn passes through the garden room door off to the left via the lens housing (bottom left).

d.c. amplifier and pen recorder.

This instrument, although originally using a slightly different frequency and receiver, was brought into operation in 1968 and has operated for three hours daily ever since. Using a chart recording speed of 7cm/h, short-lived solar bursts are easily identifiable.

Sunspots – briefly

When a long-life sunspot, or group of sunspots, appears on the east-limb of the sun it can be visible for about 13 days before leaving on the western limb. The sunspots themselves are stationary but, because the sun revolves once every 27 days, they appear to move across the surface.

Constant observations have shown that when sunspots are present there are two main features of the associated solar r.f. noise, the individual burst, Fig. 3, which may last for several minutes, and the continuous noise storm which may last for days, Fig. 4. These radio waves are often generated by solar flares or prominences, Fig. 1, but the nuclear waste ejected by the event can take up to 50 hours before it reaches the earth and causes some form of atmospheric disturbance.

Sunspot cycle No. 20

The author's observations began on the rising side of sunspot cycle No. 20 (1965 to 1976 approx.) in June 1968. After a quiet start, a large burst of activity from a group of sunspots on 13 August and a noise storm from the 18th to 21st were recorded. Another period of quiet ended on 17 October with a 5-minute burst from a period of solar activity which lasted until 4 November. The main feature of this event was a noise storm which began on the 29th and ended on 1 November: shortly after its termination an aurora borealis manifested and deflected v.h.f. signals from amateur radio stations in northern Eng-

land, Northern Ireland and Scotland towards the south of England, proving to the author the connection between the 'active' sun and terrestrial radio disturbance.

The number of days on which solar noise was recorded increased towards a peak in 1971 and then decreased until the new cycle began, Fig. 5. One of the largest noise storms recorded began on 11 November 1970 and raged until the 22nd, during which time the solar-noise level was apparently constant as the output from the fixed azimuth aerial increased daily as a large sunspot group approached central meridian and gradually decreased thereafter.

This was an example of following the rotation of the sun using radio. The telescope's recording pen was at full scale throughout the observations on the 15th and 16th, which was not surprising because the *Daily Telegraph* newspaper reported on 17 November that there were four separate sunspot groups at the time and the biggest passed through the central meridian on the 16th. This solar event upset h.f. communications and one unusual feature was the high atmospheric noise level that was heard on the h.f. bands after sunset. Another major storm, associated with a large sunspot group between 3 and 13 March 1972 was the subject of a special report to the British Astronomical Association (BAAJ June '72) with a special emphasis on the flares which were recorded by radio on the 5th.

Of the many individual bursts recorded during the past decade, a large solar burst at around 08.35hr on 3 July 1974 was the most memorable. The telescope had been recording the radio waves from a severe noise storm on the two previous days so the author decided to check the rising sun by using a 2m beam and some auxiliary equipment. Suddenly the noise increased at 136MHz and other receivers in use at the time emitted noise at 70.5 and 30MHz.

At this point a communications receiver and a long-wire aerial were used to follow the noise and for six minutes it overpowered all terrestrial signals down to 8MHz before it slowly faded away back to 136MHz, Fig. 6. Solar noise was also heard at 28.5 and 70MHz on 3, 6 and 28 July.

At 07.45hr on 22 August 1976 strong bursts of solar noise were heard at 28MHz and later at 11.58hr while the author was using a low-band mobile radiotelephone another big burst occurred and blotted out the channel for 16 minutes. This burst was also recorded by the author's radio-telescope at 136MHz.

The sun often produces the unexpected and having been quiet, apart from two tiny bursts, for 18 days it suddenly emitted a 28 minute burst which covered 50MHz of the v.h.f. spectrum at 13.16hr on 29 July 1973. Another notable burst began on 1 August at 11.46hr and for eight minutes the solar noise was strong enough to

overpower static from a local thunderstorm.

Auroral observations

Briefly, an aurora manifests when a stream of particles from the sun collides with the gases of the earth's polar atmosphere causing a temporary ionisation which affects terrestrial radio signals. An auroral reflected signal can be identified by the following characteristics: an s.s.b. transmission sounds like a ghostly whisper, a c.w. signal becomes a low-pitched rasp and the main image on a television screen is accompanied by many distorted images, all frequently changing as the aurora ebbs and flows. Throughout the past decade Mr C. Newton, Auroral Co-ordinator for the RSGB, has organized a large network of radio amateurs who monitor the effects of signals bouncing off aurora.

Following a period of large solar bursts an aurora manifested in two phases on 8

March 1970. During the first phase, 16.00 to 16.47hr, auroral signals were heard in southern England from amateur stations located in parts of Ireland, Scotland, Wales and Holland in the 2m band. The second phase, 18.15hr to 23.30hr, was more intense and auroral signals from many east-European broadcast stations operating between 65 and 73 MHz were received in addition to the amateur stations heard during the first phase.

A large sunspot group was responsible for the noise storm which began on 2 August 1972 and became very intense on the 3rd. At sunrise on the 4th the solar noise was heard at several radio frequencies and by mid-day it had reached large proportions. It was not surprising that from midnight on the 4th until about 03.00hr on the 5th a spectacular aurora manifested which not only had an umbrella effect on v.h.f. radio signals, but its full glory was visible from southern-Eng-



Fig. 8. The yagi used in conjunction with the spectroheliograph.



Fig. 9. Sunspots photographed at 14.50hr on 11 February 1978.



Fig. 10. Clouds of gas from an active region of the sun.



Fig. 11. Solar activity near sunspots recorded on 3 May 1978.



Fig. 12. Sunspots and solar activity from 25 May 1978.

Recorded noise storms of 1971

7 to 14 and 19 to 23 Jan.
28 Jan. to 3 Feb.
10 to 17 Apr.
9 to 12 May.
14 to 19 and 24 to 28 Jul.
18 to 26 Aug.
16 to 19 Nov.
4 to 9 Dec.

land. Although less intense, the prevailing solar storm continued through the 5th, 6th and 7th. At 15.00hr on the 5th another aurora manifested but this time it could only be 'seen' by radio. Without radio both these events may have gone by unrecorded, the first could have been screened by cloudy skies and the second was obscured by daylight.

A special watch was kept on the 4m band during the solar activity from 28 March to 2 April 1973. At 16.00hr on the 1st observers in southern England were rewarded with auroral reflected signals from the Polish broadcast station at Gdansk, 70.31 MHz, and during the following hour auroral signals from 14 European broadcast stations were heard between 49 and 71 MHz.

The auroral events on 15 September and 13 October 1974 were expected because of the prevailing solar activity around these two dates. The September event lasted most of the afternoon and evening and although the October aurora was much shorter, 14.00hr to 17.15hr, the first warning came earlier as signals from the OSCAR-6 satellite crossing the north-pole were affected by the aurora.

At 08.41hr on 23 March 1976 a large solar burst was also recorded by the radio-telescope which Cmdr Henry Hatfield uses at his home in Kent in conjunction with a spectrohelioscope. At noon, Cmdr Hatfield noted that one of the legs of an arched prominence on the east-limb of the sun was very bright, indicating the presence of a new sunspot. This spot later proved to be very active because from 24 March to 1 April a solar noise storm was recorded and auroral propagation was reported during the afternoons of 26 March, 1 and 3 April.

The spectrohelioscope

By the beginning of sunspot cycle 21 Cmdr Hatfield, with his spectrohelioscope†, had introduced another tool for the study of solar activity. This instrument consists of two wave collectors, one a mirror, Fig. 7, and the other a 4-element yagi aerial, Fig. 8, which both follow the path of the sun. The sunlight is passed through a series of mirrors and lenses to an observatory in the garden room below the house. At the same time radio waves collected by the yagi are fed to a radio telescope in the same room.

The output stage of the radio telescope amplifier is used to drive an alarm bell when solar bursts are detected.

Sunspot cycle No. 21

It is understood that cycle 21 began in 1976 when sunspots of the new cycle were seen along the tail ends of cycle 20. From the author's observation cycle 21 got off to a slow start because solar radio noise was only recorded on 47 days out of 304 between 1 November 1976 and 31 August 1977. A marked increase in the daily rate of noise began in September 1977 and was still high at the end of July 1978. Out of

† Cmdr. Hatfield's spectrohelioscope was the subject of the BBC television programme 'The Sky at Night'.

the 212 days from 1 January to 31 July solar noise was recorded on 108 days compared with 34 for the same period in 1977, 35 days in 1976, 34 days in 1975 and around 124 days for the same period in the peak year, 1971. From present records 1978 appears to be the peak year, Fig. 5, of cycle 21 therefore it is worth taking a more detailed look at some of the special events which took place.

On 11 February 1978 the first clear sky for several days enabled Cmdr Hatfield to use his spectrohelioscope and in view of the high level of radio noise which had been coming from the sun on previous days he was not surprised to see some large sunspots. At 14.25hr he watched an explosion take place near the upper sunspot in Fig. 9 and soon after recorded a massive six minute long burst of radio noise at 136MHz. On 6 March at 12.31hr Cmdr Hatfield managed to photograph the solar activity, Fig. 10, responsible for the noise storm which was in progress using the spectrohelioscope.

Around 12.00hr on 9 April a burst of radio noise lasting six minutes was heard sweeping across the spectrum from 1.8 on 144MHz and during the severe noise storm from the 14th to the 17th, solar bursts were frequently heard at 28.5 and 136MHz. The sun was relatively quiet from the 19th to 27th when suddenly at 13.29hr on the 28th an enormous burst of noise lasting 32 minutes occurred which almost instantaneously blacked out the h.f. bands for a couple of hours. Some 50 hours later during the afternoon of the 30th an aurora took place which, with the help of another noise storm on 1 May, rolled around until the early hours of the 4th, Fig. 11. On 25 May Cmdr Hatfield again photographed solar activity around a group of sunspots, Fig. 12, which was causing a radio noise storm and it is possible that these spots were responsible for the solar flare at 10.45hr on 31 May and the sudden ionospheric disturbance that went with it.

Records show that aurora and/or ionospheric disturbance occurred during solar noise storms which manifested on six days in September, 10 in October, eight in December 1977, seven in January, 19 in February, six in March, five in April, six in May, five in June, six in July 1978, two in April, five in August 1979 and nine in April 1980. After 12 years of consistent observation the author has come to the conclusion that the 'active' sun is very unpredictable. □

Transient intermodulation distortion

We are sorry that the tutorial article on transient intermodulation distortion intended for this issue (see note in March issue p. 1) has had to be postponed. We hope to be able to go ahead with it later this year.

Literature received

Mallory alkaline and mercury batteries, and Multiplex NiCad rechargeable types are described in a leaflet from Intel Electronic Components Ltd, Henlow Trading Estate, Henlow, Beds. WW401

Brochure on Controlox, a multi-plane, plug-board programming system can be obtained from Oxley Developments Company Ltd, Priory Park, Ulverston, Cumbria LA12 9QG. Controlox is individually designed to undertake multi-programme circuit switching or sequencing. WW402

Data recorders SR-30 and SR-50 by TEAC are sold and serviced in the UK by International Recorders Ltd, 92 High Street, Berkhamsted, Herts. HP4 2BL, who can provide a brochure on these 7- and 14-channel instruments. WW403

Toroidal transformers in the OT series are based on stock core sizes to reduce manufacturing time and reduce costs. These custom-built units are described in a leaflet by Avel-Lindberg Ltd, South Ockenden, Essex RM15 5TD. WW404

The use of the input l.e.ds of an optical isolator to protect the inputs of an operational amplifier is described in a design note from Norbain Electro-Optics Ltd, Norbain House, Arkwright Road, Reading, Berks. RG2 0LT. WW405

Ancom's range of temperature measuring sensors and assemblies are illustrated and characterized in a leaflet, which can be obtained from Ancom Ltd, Devonshire Street, Cheltenham GL50 3LT. WW406

Unilab, makers of science teaching equipment, produce a set of booklets on the use of their equipment which can also be used in their own right as experimenter's guides. A variety of subjects in physics is covered; microwaves, microelectronics, geophysics, for example, the booklets costing, on the average, around £1.50. A list of 'Notes for Use' can be had from Unilab Ltd, Clarendon Road, Blackburn BB1 9TA. WW407

More on active cross-over networks

continued from page 43

ricated absorber boxes may provide an improvement. These involve membranes of bituminous roofing felt with mineral wool in hardboard panels 15 cm deep, the sound entering through perforated fronts with 4 mm holes on a 4 cm grid, and approximately 1 m square for the overall panel. The panels, of which several could be needed, are normally mounted on battens attached to the wall and ceiling. This is however a specialized subject involving reverberation time measurements and is a separate topic, discussed for example in BBC engineering division report RD1958/28, available in most university libraries or from the BBC for £1.50. □

LETTERS TO THE EDITOR

ARTIFICIAL INTELLIGENCE

In your January issue Malcolm Peltu presents a spirited and cogent defence of artificial intelligence as an important area of study. His already-strong case can be strengthened even further by the observation that a great deal of what is now presented as computer science has its origins in work carried out under the banner of artificial intelligence.

The contribution of AI to computer science is perhaps most readily illustrated by reference to early work. The programming language LISP was devised by McCarthy and his group to aid their work in AI, and this has had a profound influence on computer science. The value of recursion in programming was clearly shown by McCarthy's work as well as by that of Newell, Shaw and Simon on their General Problem Solver. The LISP language is also a paradigm for all the other languages (including PASCAL and ALGOL 68) which allow the construction of trees and other special data structures. Chomsky's pioneering work on the formal representation of syntax was undoubtedly stimulated by the attempts to make computer programs which would manipulate natural language, whether for mechanical translation or question-answering systems.

In more recent times, interest in distributed array processors has stemmed, at least in part, from the development of pattern recognition techniques and their potential application to specific tasks such as the automatic analysis of bubble-chamber photographs. The special programming languages developed at MIT and referred to as "LISP extensions" certainly embody features which will find their way into future data-base schemes with applications in science and commerce.

I am surprised that there now seems to be a tendency for computer scientists to dissociate themselves from AI. This is surely short-sighted in view of the fact that part of today's AI becomes tomorrow's computer science.

A. M. Andrew
Department of Cybernetics
University of Reading

MULTIPLEX KEYING FOR ORGANS

With reference to the article "Multiplex keying system for organs" by A. W. Critchley in the January and February issues, may I draw your attention to the fact that this company has marketed a multiplexing system for pipe organs for nearly four years.

The system is applicable to organs of any size, transmitting all the organ facilities over a single coaxial pair between console and organ. The system includes the necessary correlation between stops, keyboards and pipes of all ranks at any pitch and between keyboards and couplers at any pitch, thus avoiding the need for multi-contact relays and playing keys or the equivalent multiple gates. The customers' requirements are programmed into r.o.m., which controls the standardised modules. A solid-state piston capture system is also available.

We also have a solid-state recording system

which records some ten minutes or more of unrestricted organ playing in 32Kbytes of r.a.m. — a full performance of the well-known Widor Toccata uses just over the capacity. Tape back-up allows permanent retention of an unlimited library, with a C60 cassette holding several hours' playing time.

The transmission system has been installed on many organs, large and small, throughout this country and has been exported to the USA and South Africa.

L. W. Ellen
Christie Music Transmission Systems Ltd
Colchester
Essex

THE DEATH OF ELECTRIC CURRENT

My thanks to Ivor Catt for giving me a good laugh at myself for nearly being duped. I read his article "The death of electric current" (December 1980 issue) carefully, and then came to the analogies. Memorable things analogies (witness that damned mutual impedance somewhere in the hot water system), but so dangerous.

The theory C analogy succeeded in giving me a vivid picture of Catt's travelling wave packets going out into the world along what I used to think were insulators, but which I now see are the very opposite. But just a minute, isn't that the philosophical point from which I started: something travelling along the easiest path? It's just back to the wave-particle duality. They're in different places, that's all. I honestly don't know which to call correct and I should like to hear if Catt will swear that nothing that exists is a particle. The trouble with theoreticians is that they can begin to speak as if their self-consistent mathematics were the fact. OK Catt, your maths may be right, and I don't doubt that it is more helpful in your field of practical endeavour, but for me the AVO meter theory of electrical current has more deductive and predictive power. My money goes on Sprague, but when I need you, Catt, I'll gladly acknowledge it. In the meantime please don't put me down as a fool because I tend to live my life close to one side of the duality only. (I never got a shock from an insulator yet.)

The reference to the phlogiston theory was a red herring; that was proved by experiment to be untenable.

J. H. J. Dawson
Amsterdam
Netherlands

The author replies:

The duality (Theories N and H) inherent in classical electromagnetism is not the same thing as wave-particle duality. (See for instance D. A. Bell, *Wireless World* Sept. 1980, page 50, first para.) As to "They're in different places, that's all," my reply is that the location of a thing is one of its most important characteristics. As to "... nothing that exists is a particle," it depends what you mean by 'particle'. I have no sympathy for the billiard ball idea, and no sympathy for the notion of wave-particle duality. The idea of wave-particle duality could probably only have been concocted by people who did not know Heaviside's concept of a slab of energy current, now called the Heaviside signal

(see *Wireless World*, July 1979). In these particular matters my view coincides with Einstein's;

"... We all of us have some idea of what the basic axioms in physics will turn out to be. The quantum or the particle will surely not be amongst them; the field, in Faraday's and Maxwell's sense, could possibly be, but it is not certain."

"Quantum Mechanics and Reality. In what follows I shall explain briefly and in an elementary way why I consider the methods of quantum mechanics fundamentally unsatisfactory." (Max Born, "The Born-Einstein letters", pub. Macmillan 1971, pp. 164, 168.)

The most prominent feature of the maths of "OK Catt" is its virtual non-existence. E-m theory was buried in nonsensical, complex maths a long time ago, and I am extricating it. (See "Maxwell's equations revisited", *Wireless World*, March 1980, pp 77-78.)

(I would get a real shock if I got a shock from a conductor.)

Ivor Catt
St Albans

COMMERCIAL BROADCASTING

It is silly to speak of freedom of choice where the main criterion of choice is advertising revenue. It is equally silly to pretend that the best of anything is that which is desired by the majority, who clearly desire pools, dirt as represented by the *News of the World* etc, and pop-tune after pop-tune regardless of quality; good, bad or indifferent. This morning's paper says that peak viewing is soap-opera. And presumably the finest wartime musical work was "Roll out the Barrel" if popularity is the criterion.

It was as long ago as Hume or J. S. Mill that it was first pointed out that rigid democracy led as surely as any other system to suppression of minority interests. Certainly if longer hours mean more dreary episodes of Coronation Street and the like, more samey westerns and American cop-and-robber sagas and long-since-dated films, then they can have my licence duplicate.

And when is it all for? To try to dupe more people into buying, at ridiculously inflated prices, cosmetics, cancer-sticks, and beer which tastes, as Lawrence Durrell so admirably put it, like a urine sample from a mule. To make matters worse you would think from their attitudes that the advertisers were transmitting the word of God. In fact we would all be much better off if they were all strangled.

F. V. Bale
Maidenhead, Berks

With reference to your leader of the December 1980 issue I feel that I must pass comment on a number of salient points.

First, you state that the BBC has already started a course of competing for large audiences on terms set by the commercial broadcasting networks. It is not — it is competing on the same terms as always, but using material which is supposedly more suited to the changing tastes and opinions of the present day. That some find this material displeasing is a consequence of the more depressed financial state of the country as a whole, not just of the BBC itself. There may not exist a desirable level

of funds in the Corporation for new developments and the expansion of the network, but on a national level in a period of depressed outlook the discontent with most public services tends to increase anyway.

Secondly, you voice the opinion that, "British life will be impoverished without a good, strong-voiced public service broadcaster, independent of the state, creative and risk-taking . . .". Certainly I agree with most of your underlying sentiments, but I would venture to propound that, with respect to the BBC, the commercial networks have been just as strong-voiced on some important national issues and have demonstrated equal amounts of creativity and willingness to take risks. I would also say it is tenable fact that today they are generally as praiseworthy as the BBC, and state categorically that by definition (and in their *modus operandi*) they are much more independent of the state.

This brings me to my third point, being your statement that commercial broadcasting "is not independent at all . . ." and does not "sell programmes directly to the public, in the manner of theatres or book publishers . . .". Frankly, I do not follow this line of argument at all, especially as you carry on to say that "It is in the game for profit, and the service which it provides is incidental . . .". Theatres and book publishers produce plays and sell books that in some cases make a significant contribution to our culture, but they are still mainly 'in the game' for the primary purpose of taking money from our pockets.

Perhaps your leader writer might not have noticed that plays which are box-office disasters (=financial loss) do not tend to stay too long on the stage. Maybe, as a writer, he only has the slightest suspicion that authors receive a warmer welcome at the publisher's office if it is thought that their books may become best-sellers (=financial gain).

The commercial broadcast networks do indeed produce programmes that they calculate will receive the highest audience figures, and they appear to do so quite successfully so that their calculations cannot be too far awry. Therefore the public is paying, albeit indirectly through advertising revenue, mostly for what it wants to receive from these networks: if it were not, advertising revenue would plummet, the networks would go out of business, and the BBC would achieve higher audience ratings. (Somehow, though, I think that previously-advertised products would not be reduced in price; and maybe then the BBC would start to complain about competition from theatres and cinemas?).

The service that the commercial networks provide is anything but incidental; it is their very bread and butter, for if it did not meet the majority of the viewing and listening public's demands it would not receive the revenue income it needs to survive.

Finally, lest I be branded a 'public-sector-basher' or a 'capital extremist', let me wish for the BBC, and our country, better times: let me also ask that we remember that in our time of depression the horns must be drawn in, and that no solution exists in discrediting a service simply because it is not public-sector.

F.C.T. Gale, G8FH
Hengelo
Netherlands

Congratulations on your editorial "Save our public service broadcasting". One has only to view the American broadcasting situation to realise what would happen here if commercial broadcasting got the upper hand. The only reason why it produces good programmes now is because it must compete with the BBC. Had ITV-ILR arrived first, there would have been

no BBC and our programmes would have been at the American level.

The BBC operates two television services and an extensive sound broadcasting service at a lower cost than ITV-ILR operates one television service and a skeleton sound broadcasting service. But the greatest danger facing the public in the event of the demise of the BBC lies in the field of news broadcasts. It is generally believed that most people obtain their news via tv. Those of us who are old enough to remember the so-called "news-reels" of pre-war and just post-war days shudder to think of the type of "news" that would be presented to us by a commercial news-handling monopoly.

Roy C. Whitehead
Sutton
Surrey

MAIL ORDER BUSINESS

For many years people have bought magazines like *Wireless World* as a source of up to date information on component prices and availability. In any technical magazine the advertising is as much a service to the reader as is the editorial content. Increasingly, however, the material advertised for mail order is not available. Mail order firms are increasingly banking cheques and delaying months before sending goods either because they are grossly undermanned or because they get interest on the banked money. Alone of your advertisers, Sinclair are honest in admitting that goods will not be supplied from stock. It has been a long tradition in the electronics industry that small orders of components came by return of post. Unless this tradition is restored, I, for one, will no longer order by post. Those firms operating from the West Country are particularly remiss.

I am beginning to wonder if the people Roger Cook pursues have decided to move into the fraudulent component supply racket. Thus far I have not heard of any fraud in the area of electronic supply but the field is wide open. Advertise cheap memory and you could expect at least a thousand cheques for between twenty and thirty pounds. That is a lot of money. Electronics has traditionally been a field where people trusted each other, firms rarely bothering to wait for cheques to clear before sending goods. If criminals are going to move into this area, either by selling kits and data that won't make up into working devices, by sending for goods with bouncing cheques or advertising non-existent goods, a multi-million pound industry could just vanish.

Fred Allen
Cambridge

ELECTRONICS AND UNEMPLOYMENT

Though your magazine is not the place for an essay in economics, some comment on the January editorial may be in order.

First consider the overall effect of 'automation', a term which I use as short-hand for any procedure which uses sophisticated capital equipment - whether electronic or mechanical - to reduce the labour content of manufacture. One of the objectives of automation is to reduce manufacturing cost. A large part of the cost of robots, computers etc. is the cost of highly skilled labour employed in their design and manufacture (and marketing). Since there is an overall reduction in cost there must be an overall reduction in labour employed. This is on the basis of constant volume of output; and

there are arguments on grounds of limitation of material resources and 'quality of life' against the older idea of continual expansion of volume of output. Equally important as the reduction in total employment is the upgrading and change in type of skills required.

A reduction in working hours is often demanded. Over the course of history, working hours have been reduced from all the hours of daylight in six days to 60, 50, 40 per week and some further reduction would not be out of line. At constant hourly productivity and constant total output this would require more employees and so reduce unemployment; but in these terms it would be a form of work-sharing and require a reduction in weekly wage - probably not acceptable.

There are many detailed ifs and buts to be added. For example, if morale is improved by shortening the working week, production per man will not be reduced pro rata with hours. Volume of production may be limited by natural resources, but what about the sophistication factor? Automation may reduce cost of manufacture, but this is not the only motive for its introduction. One cannot just say whether or not "chips" will cause unemployment of millions: one must examine each sector of industry in detail and then the interactions between sectors. The one thing which does seem clear, however, is that training in appropriate skills is going to be of supreme importance.

D. A. Bell
Beverley
North Humberside

MICROCHIPS AND MEGADEATHS

Your editorial of last November, 'Microchips and megadeaths', and some of the letters in reply, remind me almost irresistibly of the words of 'Shooby' in the 'Hitch-hikers' guide to the galaxy: "I don't go round gratuitously shooting people and then bragging about it in seedy space-ranchers' bars. I go around gratuitously shooting people and then agonising about it afterwards to my girlfriend."

May I suggest that any electronics engineer who really agrees with your editorial should resign his job and live on the dole. Thus not only would he avoid the risk of inventing anything that might have a military application, but he would use up funds which could otherwise be spent on arms.

J. S. Linford
Oxford

By profession I am an artist; my hobby, since the early 1950s has been electronics. *Wireless World* has always been of great interest to me, keeping me up to date. Your articles and projects have always been on the highest level. I have built many projects - from Dinsdale, Linsley-Hood, Nelson-Jones, Baxandall etc. - and have received much pleasure from them, although I think the designers would be shocked with the look of some of my efforts. I bend wires instead of using p.b.cs, though, believe it or not, most work extremely well.

The other side of the electronics profession disturbs me very much and, like you, I wonder how highly intelligent, highly skilled electronics engineers can be so blind as to continue to invent and to use their ingenuity with modern circuitry, not to give pleasure and ease the burdens of life alone, but to destroy everything they and every creative person has ever worked for on this planet - including themselves and us!

Your excellent leading article and some letters from engineers in the industry in the No-

vember 1980 issue prompts me to write and congratulate you on your courage and foresight in printing these. Having travelled broadly, I know your magazine is read in many countries, so I hope engineers in the industry will take inspiration from you and stop supporting the industrial and political maniacs around the globe in their blind drive to destroy so much of the work of the Creator.

Please carry on the good work.
Ken Evans
Shaftesbury
Dorset

ELECTRONIC COMBINATION LOCK

I have read with interest the article describing an electronic combination lock (January issue), but what I feel Jan Hruska ought to have developed is a lock that opens to a pre-determined rhythmic operation of a conventional door bell press button. This would save any need for a keypad, and would be of use in situations already equipped with an electric striker, such as buildings with controlled access by "entry-phone" type systems, for example blocks of flats.

H. T. Wynne
Glasgow

The author replies:

I would like to make the following points in favour of my original design:

1. The hexadecimal code used in my design is equivalent to a combination of 16 dots and dashes, which would be a considerably greater burden of information for a non-user of Morse to learn.
2. Input of code in this form would take longer.

However, I had already considered constructing such an alternative device and have built a battery operated prototype using an Intel stand-alone microcomputer.

Jan Hruska
University of Oxford

PICKABACK SPARKS

John T. Lloyd, writing in November 1980 letters, mentions the phenomenon where a third electrode at high voltage initiates a discharge in air between two electrodes connected to a charged capacitor. I can confirm his observation and would add that a high frequency Tesla coil source may not be necessary.

I first observed the effect as a child, when I built an electronic flash gun. Having no xenon tube at the time, I decided to attempt an air discharge. The capacitor was about 200µF charged to 350 volts, and a miniature ignition coil was used (from a model aircraft). At first I was only able to obtain the weak high voltage spark, but by moving the electrodes progressively closer, I was rewarded by the bang and blue flash which discharged the capacitor. I found that a bare copper wire, freshly cut on a diagonal gave the best result.

Much later in life, I suggested the idea of a third electrode to Unilever Research in connection with an explosibility test apparatus. Originally two pointed electrodes were connected to a bank of capacitors which were gradually charged. The gap was sized to fire at a pre-determined voltage. Unfortunately, the voltage at which breakdown occurred was not accurately reproducible. Some of the reasons will be apparent from "Sparks gaps" by J Dearden in your November 1980 issue.

Using a third electrode allowed "ignition" of the discharge which then almost completely emptied the main capacitor bank. The signifi-

cance of this method is that although a high voltage spark is used to ignite the discharge, the energy in the high voltage spark can be minute by comparison with that in the capacitor bank. This discharge starts at a very predictable voltage (that of the capacitor bank itself) and a negligible disturbance is caused by the third electrode.

This idea worked very well in practice. I do not know whether Unilever has used this work or published it since I left. However, I would certainly like to lay claim to the invention; although I would be very surprised if no-one realised that this effect could happen before I discovered it for myself as a child.

A. R. Churchley
Sara Ltd
Warrington
Lancs

OPPORTUNITY LOST?

While in course of conducting research in the technological history of disc sound recording I browsed through a volume of the defunct German scientific journal *Akustische Zeitschrift*. On the last page of the July 1941 issue there is a review of a demonstration that took place in Berlin on June 10, 1941. The object in question was the "new Magnetophon" which boasted noiseless playback. The paragraph which is of the greatest interest, historically, is the following (translated by me into English):

"In recent research H. J. von Braunmühl and W. Weber (RRG) succeeded in improving the quality considerably, particularly the dynamic range, because they used high frequency magnetization in the recording head instead of d.c. magnetization. Thereby practically all noises originating from the tape disappear."

Now what does this prove? It proves to me that a fact which was not discovered by the Allied powers until 1945 and which explained certain feats of radio transmission during the 1939-45 war, was in fact publicly disclosed in Germany as early as 1941. The technical description was adequate, i.e. a person skilled in the art would have been able to fathom the advantages, had he read that particular review.

The war was a great obstacle, but surely there was at least a trickling distribution of scientific journals in the Allied countries (possibly through the neutral states Sweden or Switzerland). It seems rather a case of too few readers with sufficient fluency in reading German, because none of the standard accounts of the history of magnetic recording mentions this very early publication (e.g. Basil Lane's extremely thorough "75 years of magnetic recording" in *Wireless World* in 1975). It also proves that research into the history of technology (as any other historical discipline) cannot do without access to every page of an original publication and cannot be done by means of abstracting services or the like.

I hope to be corrected by any of your readers who may know about previous publication of the above reference.

George Brock-Nannestad
Genotfe
Denmark

DESIGNING WITH MICROPROCESSORS

R. M. O'Connor, writing in October 1980 letters, raises a number of important matters which deserve further discussion.

Firstly, there is no one "best" way of learning about microprocessors and their application. A

method aimed at recent graduates with a formal training in logic design may be completely inappropriate for a practising designer with many years of experience, and now faced with using this new device. Similarly, a programmer with a background in mini-computers is likely to need a quite different approach. I hope that *Wireless World* will cover these aspects too in due course.

O'Connor makes the point that what the designer needs to know is what micros can do. It is equally important that he also knows those things that micros can't do economically. There has been far too much talk about the wonders of the mighty micro, and far too little about the cold, hard facts of the hidden costs of using them.

On the question of machine independence, neither O'Connor nor Zissos and Valan have said whether they are talking about a single chip controller, a small industrial controller, or a system such as a TRS-80 or an Apple with a large capacity hard disc, line printer, etc. Perhaps it is best summed up by J. L. Alty in his introduction to Professor Zissos's "System Design with Microprocessors" in which he says:

"It is important to realize that the new technology will permeate society in two ways - the high volume/low cost and low volume/high cost categories. The former type will be produced in millions and will be very cheap indeed. They will often be single chips dedicated to one application and, as such, will not even be recognisable as computers.

Computer systems do not however consist of hardware alone. The software required to operate the new technology will also be provided in the same two categories - high volume/low cost and low volume/high cost, and each category will tend to run on the equivalent category of hardware. The software in the single purpose chips for example will also be single purpose, relatively fault free, and very cheap if only because of the large volume of sales. It will be unalterable by the user, and will not be maintained. It will simply have to work."

In the high volume applications, the cost of the hardware is likely to be the deciding factor. A \$1.00 microprocessor is going to face stiff competition from another costing 99c, no matter which language each uses. For these applications it won't make much difference which language is used - so long as the final code will fit in the memory space available, will do what has to be done in the time available, and is highly reliable.

The major part of the cost of software for microprocessor applications is in preparing the detailed specifications, then deciding the program logic and verifying the flow charts. The cost of coding these flow charts is then fairly small, so that if it is necessary to use a different microprocessor at some stage, the conversion cost could well be fairly small - particularly if the original programs have been kept free of sneaky tricks designed to save the odd byte of code by using a special feature of the original microprocessor.

At the other end of the scale, in the one-off and specials, the lowest total system cost will usually be obtained by using "off-the-shelf" standard hardware and software, with the absolute minimum of additions. In these cases, it often pays to modify the requirements to suit what is available to keep the costs down. Although the system may well turn out to be much more powerful than really necessary, does this matter if the costs are reduced?

For small production runs, it is probably better to design the system around a range of "off-the-shelf" modules. In this case, the particular microprocessor used is not as important as the range of modules available, and whether the hardware modules each have any necessary driver software supplied with them. Each module should be supplied with its own service

manual, so that the system documentation can be prepared by assembling the manual for each module, and adding a section on the complete system.

O'Connor raises the question of the disappearing micro. Now although it is true that many microprocessors have appeared, then disappeared just as rapidly, there are three families that have been with us for many years, and look like being around for a long time to come. These are the 6502, the 6800/6809 and the 8080/8085. Not only have the manufacturers taken care to see that it is a simple matter to change the software for new members of each family, but there is considerable support in the form of hardware and software, both from the semiconductor manufacturer and also from a large number of independent suppliers. I have deliberately left out the Z80 for two reasons — there is little software available specifically for the Z80 and in most applications they run 8080 code and so do not make use of all the extra facilities, and their future is likely to depend very much on how fast the Z8000 is accepted. The Z80 might simply be phased out and replaced by the 40-pin version of the Z8000.

The moral from this would seem to be — if you are going to make your product in millions then do what you would do for any other product, i.e. specify an interface that is independent of the type of microprocessor used, place an order for the cheapest components from one or two reliable suppliers, and make sure you buy enough for future spares. If the product sells so well that you have to make another 10 million, then it won't matter if new software is needed. After all, a black box is a black box is a black box is a black box to misquote Stein, and if you can't get inside it to repair or change it, does it matter whether it is a microprocessor, a state machine or random logic? What is important is the original unit cost, the reliability, and the replacement unit cost.

On the other hand, if you are only going to produce small quantities you had better stick to one of the above three families, and design around the one which has the best overall hardware and software support available to you locally, and which has a range of readily available modules which meet your needs. Although these modules look expensive at first they turn out to be far cheaper than rolling your own. You have to make a large quantity to recover the development and proving costs, even if you follow the recommended practices and get it right the first time. Designing a unit which works correctly is straightforward — designing a unit which works correctly and can be produced economically requires considerable extra skill and experience.

This leads me to comment on the design steps used by Zissos and Valan in part 5 (October, 1980). They advocate designing the hardware first then the software, then repeating these steps until a satisfactory design is obtained. In each of the failed designs that I have investigated the designers have followed this approach. I cannot stress too strongly that these two steps must be carried out concurrently, and in fact that there are four separate but strongly interwoven areas that must be considered in parallel. These are: 1. Hardware design. 2. Software design. 3. Design for testing. 4. Design for production.

The last two areas are often left till the prototype is completed, and then it's back to the drawing board for some very expensive changes. We should follow the Smallpiece philosophy of "Get it right the first time." Test points, both for production testing and field servicing must be built into the hardware and software during the original design. There is a lot to be said for making a commitment to including signature

analysis in every product. Similarly, what is the point of designing a system that can't be produced economically without redesign and the consequent delays in getting your product into the market place? After all, one of the big incentives to using microprocessors is that their use can substantially reduce the development time for the product.

As O'Connor said "Microprocessors are only cheap if they are cheap to use; if the way in which they are used brings crippling costs, they are extraordinarily expensive."

Alan M. Fowler
North Balwyn
Victoria, Australia

DESIGNING WITH MICROPROCESSORS

I would like to thank D. M. Vaidya for his letter in the March issue (p.62) pointing out the error in our Table 3 (p.73) of Part 6 of our series "Designing with microprocessors" in the December 1980 issue. We understand that the editor hopes to publish a corrected version in the next available issue.

Regarding the second point, we must disagree on this. We have written numerous programs using different microprocessors which show the generality of the approach that can be achieved with these different devices. This will be demonstrated in detail in an article which will follow later in our current series. Meanwhile, any readers who would like to have this information in advance are welcome to write to us at the address below.

D. Zissos and L. Valan
Department of Computer Science
University of Calgary
Calgary, Alberta T2N 1N4
Canada

THE TWINS PARADOX OF RELATIVITY

Alex Jones's letter (January) contains a fundamental flaw which I feel should be corrected.

The relative ageing in the Twins Paradox is not dependent on the accelerations at the start and finish of the journey, because the theory has it that, with the same accelerations, doubling the spatial distance of the trip doubles the age



Hugh Pocock, writer of the above letter (centre), with two later editors of *Wireless World*, H. F. Smith (right) and F. L. Devereux (left), on the occasion of the journal's 50th anniversary.

difference at the end (with short acceleration durations compared to total journey duration).

This is certainly the impression Einstein wished to impose on the world, and it is backed up by the whole series of text-books since. The effect is quite clearly one of Special Relativity, not of General Relativity.

If, as he suggests, the results of SRT are only "apparent", but the Twins Paradox experimentally resolves in Einstein's favour, as numerous text-book writers would have us believe, then Jones's "coincidence" is not only remarkable, but miraculous.

L. J. Higgins
Swindon Wilts

WIRELESS WORLD'S 70th ANNIVERSARY

If I give a brief record of my association with *Wireless World* it will explain how much pleasure it has given me to be invited by the present editor to say a few words on the 70th anniversary.

Looking for a career in journalism I answered an advertisement by the Marconi Company for an editorial assistant which stated "some knowledge of wireless would be an advantage". As I already had a Post Office Experimental Licence and had read all I could on the subject I had no difficulty in securing the job. I found myself on the editorial staff of the *Wireless World* with the launching of the first number. With a commission in the Royal Engineers, the 1914-18 war took me to Mesopotamia and Persia engaged on interception and direction finding. The Marconi Company kindly kept open the editorship of *Wireless World* for me on my return after demobilisation and I continued with the journal as editor and then as director and managing editor until my retirement in 1962.

With a career which has been so intimately wrapped up with the story of the *Wireless World* I welcome with enthusiasm its achievement of 70 years and, under the control of our present editor, we can look forward with every confidence to the future. I am proud to have been associated with a staff which has created *Wireless World* over the years.

Congratulations and every good wish for the future.

Hugh Pocock
London NW3

Dividing by fractions

Digital frequency synthesis using non-integral frequency division

by Gilbert Pearson, Australian Broadcasting Commission

This circuit allows a direct division from PAL/625 sub-carrier frequency to twice-line frequency, or a direct multiplication from twice-line to sub-carrier frequency. This is achieved in both cases using only digital counters and a single, phase-locked loop. Present methods require additions or subtractions in the frequency domain, which in turn require linear stages.

The unit to generate sub-carrier frequency from line frequency has been built and found to work satisfactorily. The greatest use for the circuit may well be found in synchronizing pulse generators, where its low cost and reliability should prove an advantage. But the principles described are applicable to any frequency synthesis problems where fractional divisions or multiplications are required.

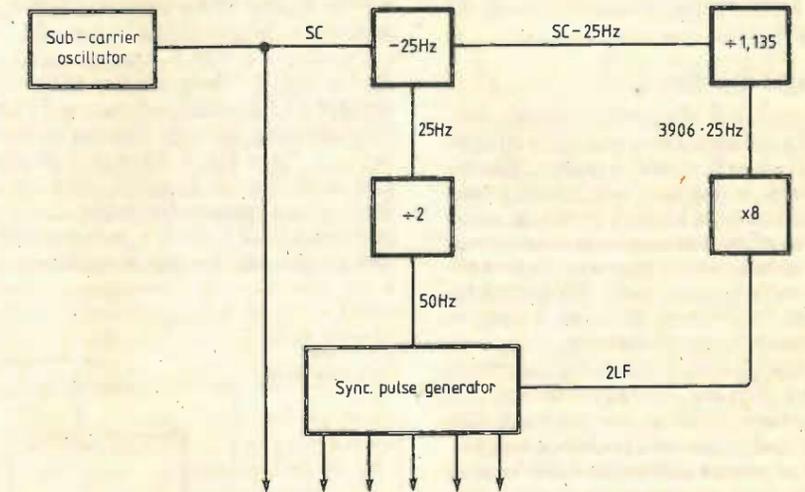


Fig. 1. Typical synthesizing technique.

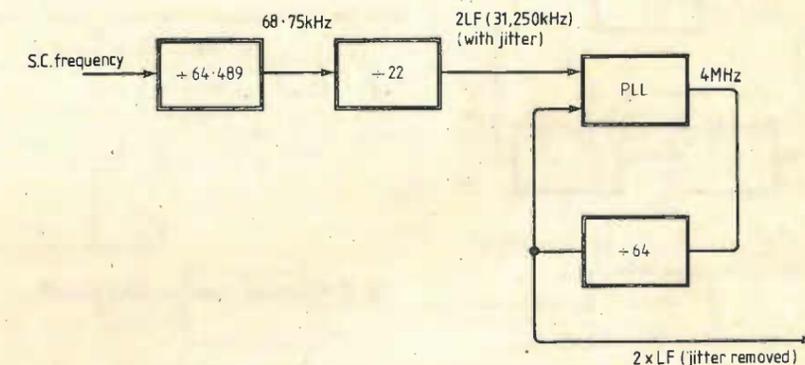


Fig. 2. Twice-line frequency (2LF) derived from sub-carrier frequency.

The colour sub-carrier frequency as used in the 625/PAL colour television system is 4,433,618.75Hz. It is derived from the relationship —

$$283\frac{3}{4} \times \text{line frequency} + 25\text{Hz}$$

$$\text{i.e. } 283\frac{3}{4} \times 15,625 + 25\text{Hz}$$

The addition of the 25Hz makes synthesis of one frequency from the other difficult. While straight divisions or multiplications can be done simply, with integrated-circuit dividers and phase-locked loops, the addition or subtraction of frequencies, such as 25Hz, requires precision phase shifters and tuned stages.

A common technique used in the generation of twice line frequency (2LF) from sub-carrier (SC) in a sync. pulse generator is shown in Fig. 1.

New method

The two frequencies can be broken into lower multiples, as shown below.

$$\text{SC} = 4,433,618.75\text{Hz}$$

$$= 11 \times 25 \times 25 \times 644.89\text{Hz}$$

$$2\text{LF} = 31,250\text{Hz} = 2 \times 25 \times 25 \times 25\text{Hz}$$

$$\text{Thus, } \frac{\text{SC}}{11 \times 25 \times 25 \times 644.89}$$

$$= \frac{2\text{LF}}{2 \times 25 \times 25 \times 25} = 1\text{Hz}$$

$$\text{i.e. } 2\text{LF} = \text{SC} \frac{25 \times 2}{11 \times 644.89}$$

$$= \text{SC} \frac{5}{11} \times \frac{1000}{64,489}$$

It must be pointed out at this stage that 64,489 is prime number and thus cannot be broken up further. From the above, it would seem that we could divide by 64,489, multiply by 1,000, divide by 11, multiply by 5 to generate twice line frequency. The problem with this, however, is that SC divided 64,489 gives 68.75 Hz and it is extremely difficult to stabilize a phase-locked loop (p.l.l. hereafter) with an input frequency which is so low. An ideal solution would be a divider which somehow achieved a fractional division.

$$\text{i.e. } 2\text{LF} = \frac{\text{SC}}{2.2 \times 64,489}$$

A reasonable first reaction is that this is impossible, and strictly this is correct. However it is possible, using programmable counters, to achieve on average a fractional division by dividing by two or more numbers in an appropriate ratio. For example a division of 4.5 could be performed by dividing alternately by 4 and 5. A division of 4.333 could be performed by dividing by 4 and 5 in the ratio of 2:1 respectively. Of course, the problem with such an arrangement is that the output exhibits a large amount of jitter. This can, for our requirements, be eliminated by a phase-locked loop and will be dealt with later.

If we assume for the moment that both 64,489 and 2.2 dividers are possible, arrangements as shown in Fig. 2 and 3 can

be used to generate 2LF from SC and vice-versa. In the schematic in Fig. 2, 2LF is derived directly from the two dividers in cascade. However, this output has large amounts of jitter, so the p.l.l. and divide-by-64 is included to remove this. This circuit would seem particularly useful in a sync. pulse generator where a suitable p.l.l. is often included anyway for the purpose of genlocking.

In Fig. 3, the p.l.l. serves two functions. Firstly, in conjunction with digital circuitry, it provides the means of multiplication. Secondly, by selecting the time constants of the p.l.l., it serves to prevent the jitter of the dividers being reflected on the SC output.

64.489 divider

As described in the previous section, fractional divisions are obtained by dividing by two numbers in a suitable ratio. In the case of 64.489, a solution is to divide by 64 and 65 in the ratio of 511:489. There are many ways in which such a ratio can be achieved, but the best one is that which gives the least low frequency jitter. To do this the divisions by 64 and 65 must as near as possible be evenly distributed.

Before moving to a detailed description of the divider, background on the programmable counters is necessary. The 9310 is such a counter, in which it is possible to arrange a division of any number from 1-10 by programming on pins 3 to 6. It is further possible to cascade the coun-

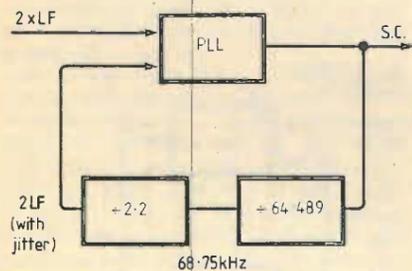


Fig. 3. Sub-carrier frequency (SC) derived from twice line frequency.

Fig. 5. Complete 64.489 divider.


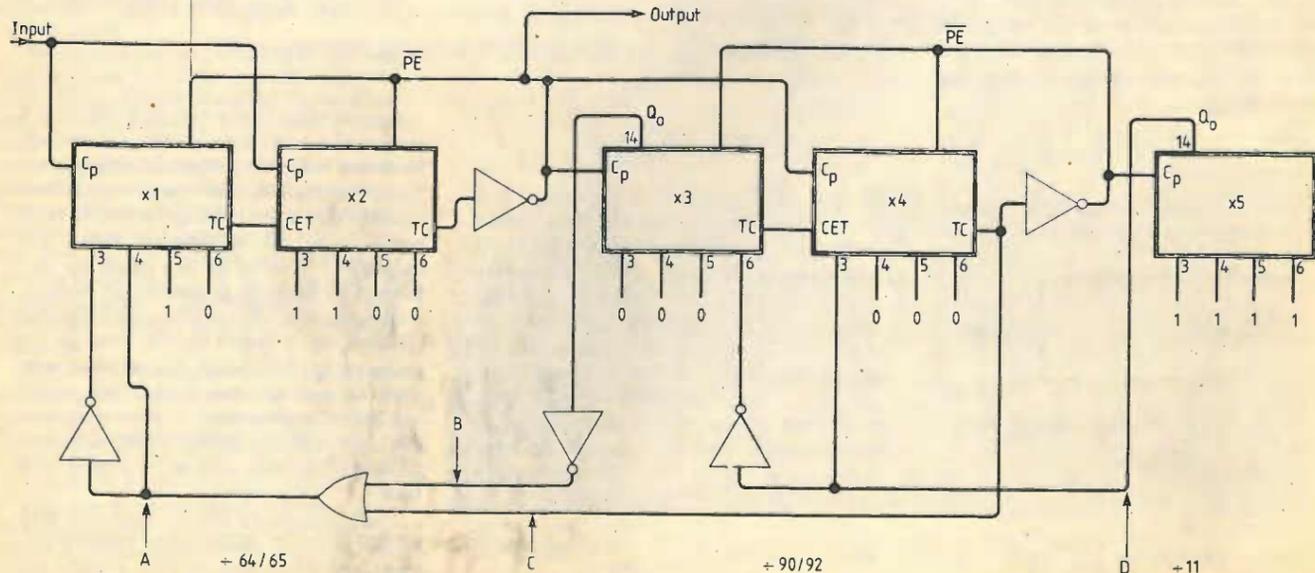


Fig. 4. Alternate divisions of 64 and 65.

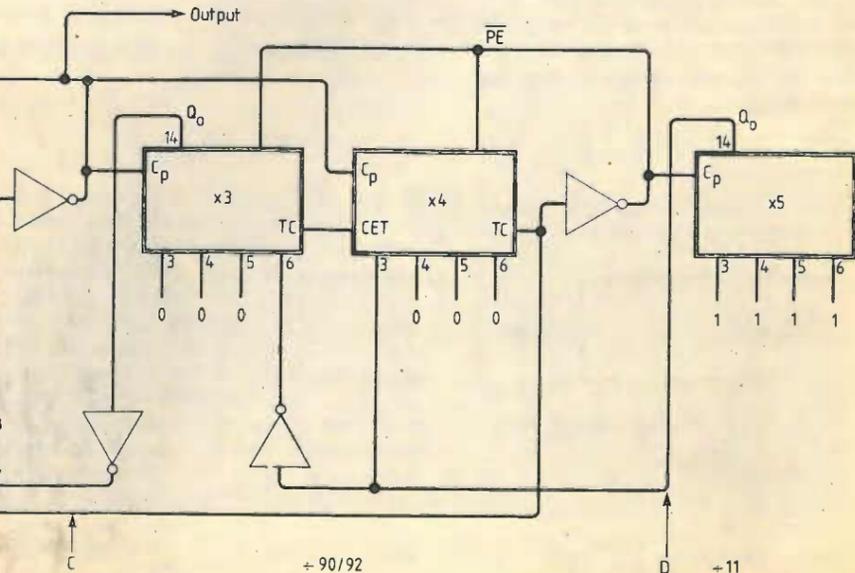

divide by 90 and 92 and, since both are even numbers, the Q₀ output of X3 will, regardless of which division is performed, always alternate between 0 and 1.

As stated previously a division of 64.5 is performed by the circuit shown in Fig. 4. This is close to the required division of 64.489. If 11 of the divide-by-65s ("÷65s") in 1,000 are changed into "÷64s" the correct ratio of 511:489 is obtained. This occurs in the circuit of Fig. 5. X3 and X4 divide by 90 and 92 in the ratio of 6:5. This means that they divide by 90.9090... or 1,000/11, and point C will thus have eleven pulses for 1,000 occurring at the clock of X3. Furthermore, these pulses derive from the terminal count of X4, and thus at a time when Q₀ of X3 is high and when B would be low, normally giving a ÷65 instruction. The 'high' on C thus overrides this through the OR gate and forces a "÷64" instead. The correct ÷90, ÷92 ratio is obtained from X5. A 9310 is not usually used to divide by 11, but it was used in this case to make all the types standard. When X5 is programmed

as shown, it will divide by 11 and its Q₀ output will oscillate between 0 and 1, except at the maximum count, when it will give two consecutive 1s. Q₀ will thus be high and low in the ratio of 6:5. It is this point, point D, that is used to command the ÷90/92 counter.

To summarize, X1 and X2 divide by 64 or 65, depending upon the command appearing at point A. This point will go high ("÷64") when either B or C are high. B alternates between low and high and thus, taken in isolation, would alternately command division by 64, 65. Point C goes high for just 11 of 1,000 pulses appearing at the output and it does this when B is low, instructing a "÷65". On these 11 occasions in 1,000 then, a "÷65" is converted to a "÷64" making the ratio of the two divisions 489:511 instead of 500:500 or 1:1.

Jitter. If the divider is given an input of sub-carrier frequency it has the following jitter components:

Frequency	Jitter (ns-pp)
34.375kHz	226
756.25 Hz	111
378 Hz	1.24
68.75 Hz	1.13

The first can be easily understood, since the divider for most of the time divides alternately by 64 and 65, meaning that the output phase oscillates about a true mean with a period of two output cycles. Since with a SC input the output will be 68.75kHz, this first jitter frequency must be half this, 34.375kHz. Its peak to peak excursions are 226ns, one period of the input frequency (T hereafter).

The remaining components are best des-


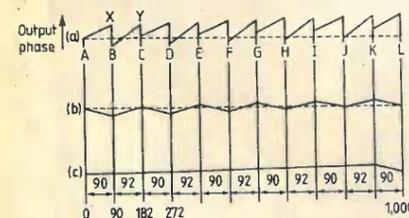


Fig. 6. 756.25 Hz, 378 Hz, and 68.75 Hz jitter components.

Fig. 8. Complete 2.2 divider.

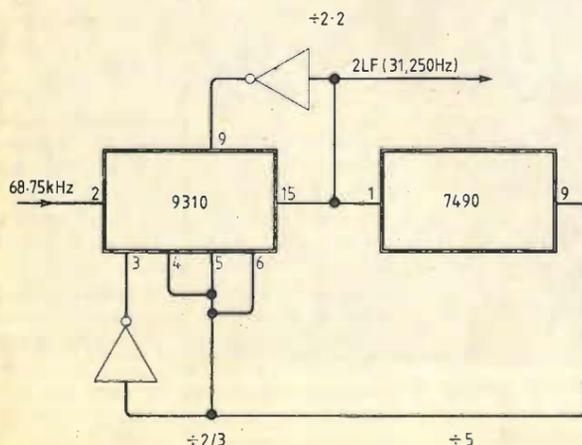

cribed with reference to Fig. 6(a). The horizontal axis is calibrated in periods of the output of the divider (1-1,000) and the vertical in its output phase, such that a mean line would be horizontal. The 34.375kHz component has been ignored. Beginning at point A, the divider divides alternately by 64 and 65 and since this is not quite the required division the output phase steadily deviates from the mean as seen by the slope of line A X. Referring to the previous section, instead of the 89 and 90th divisions being 64 and 65 as before, they are both "÷64s" resulting in an abrupt correction in the output phase (X-B). The count sequence from B-C is similar, except that the 91st and 92nd divisions are altered to both be "÷64s". Thus A-B and B-C give slightly different average divisions. The counts from C-D, E-F, G-H, I-J, and K-L are identical with A-B, while the alternate ones, D-E, F-G, H-I and J-K are identical to B-C. It must be noted that there are six of the former sequences and five of the latter, as described in the previous section. After point L, the entire sequence A-L repeats itself. By a quantitative examination of the plot of Fig. 6(a) it is possible to calculate the various jitter components, their waveforms and peak to peak values.

Alternate divisions of 64 and 65 clearly give an average of 64.5. This differs from the final required average by 64.5-64.489. That is 0.011 of an input period (T). This


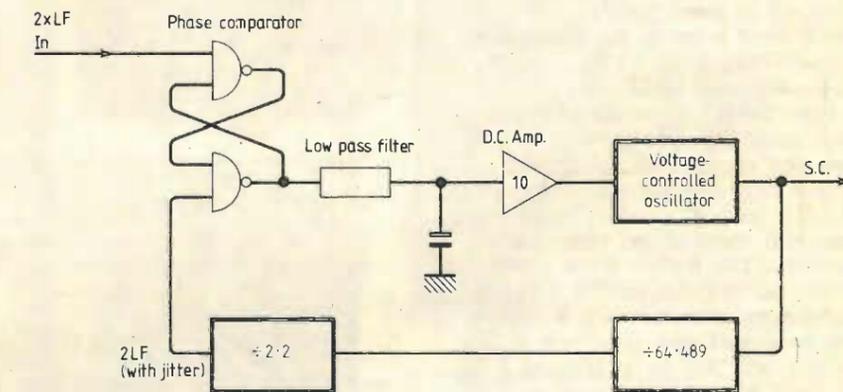


Fig. 7. Phase-locked loop used for synthesis of sub-carrier from twice line frequency.

Fig. 9. Complete 4.4 divider.

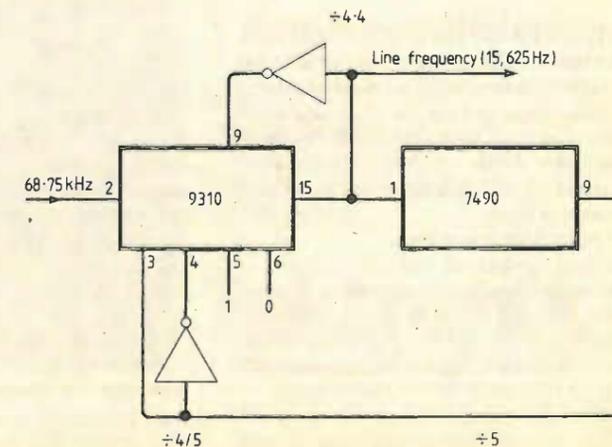

$$\frac{68,750 \times 11}{1,000} = 756.25 \text{ Hz}$$

Its peak to peak excursions will be 0.489T, i.e., with a SC input - 0.489 × 226ns = 111ns

An error of +0.484T accumulates to point X and a correction is made (X-B) of -0.484T when a double division by 64 takes place. The correction therefore "overshoots" by an amount of 0.005T. As the counter proceeds from B to Y, an error of 45 × 0.011 = 0.495T accumulates. A double division of 64 occurs from Y to C bringing a correction of -0.489T. In this case, the correction is insufficient and "undershoots" by an amount of 0.006T. Since C-D is identical to A-B and D-E is identical with B-C, the process of "overshoot", "undershoot" continues, the jitter waveform of Fig. 6(b) being the result. It is

continued on page 76

Phase measurement with an oscilloscope

Avoiding the difficulties of Lissajou figures and time estimation

by I. D. MacArthur

A method of measuring phase angle between two sine waves of the same frequency is described, using a double-beam oscilloscope, which is easy to use up to the full vertical bandwidth of the oscilloscope.

The classical method of measuring phase is by Lissajou figures, as in the example of Fig. 1, a method which suffers from a number of drawbacks. The centre of the ellipse must be accurately aligned with the cross wires of the graticule and then measurements made against the graduations, which are usually on the centre lines themselves. This is tricky and prone to error. Accuracy is poor when the phase angle is near 90° or 270°, and the gain of the horizontal amplifier is usually limited, making it impossible to "open out" the ellipse with small signals. The maximum frequency at which measurements can be made is also restricted by the horizontal amplifier — even a very good modern oscilloscope may be limited to about 200kHz before the relative phase shifts in the vertical and horizontal channels become unacceptable.

It must be stated though, that the Lissajou figure has one big advantage in that it is very useful for checking zero (or 180°) phase shift when the ellipse is closed and any small departures are easily visible.

Another method, shown in Fig. 2, is to measure the times of zero crossing of the waveforms. This method is still probably the best for "a quick look" but has the disadvantages that the two waveforms must be aligned with the centre of the graticule, and that the oscilloscope time base must be accurately triggered. One must also choose between the chopped and alternate modes, which both have disadvantages. On some oscilloscopes it is necessary to provide an external trigger.

Sum-and-difference method

Here the two signals are displayed as in the zero-crossing time-interval method, but it is unnecessary to have the timebase accurately triggered, or even synchronized in some cases. Measurements can sometimes be made in the presence of significant amounts of noise.

The procedure is as follows:

- Adjust the gain of the two channels to give equal-amplitude signals approximately half the screen height (to allow for displaying a 2x signal). The exact amplitude and gain settings are unimportant and the time base need not be synchronized.
- Switch the channel selector to A+B (algebraic add) and record the peak to peak

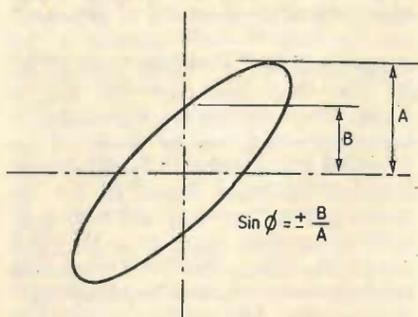


Fig. 1. Phase measurement by the Lissajou figure method. This is difficult, since the graduations on the cursor are usually on the centre line.

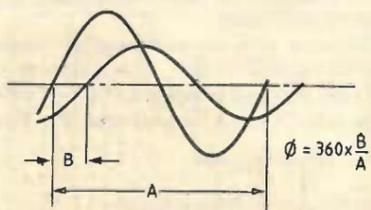


Fig. 2. The zero-crossing method, which can be tricky to set up symmetrically on the screen.

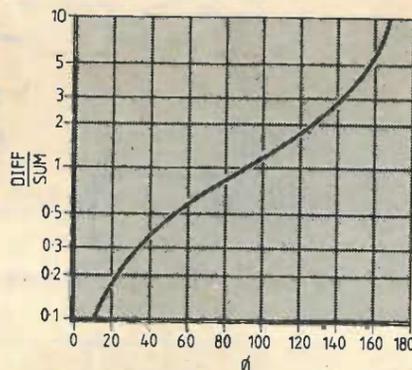


Fig. 3. Graph of diff./sum plotted against phase.

amplitude of the resulting sine wave (the sum voltage).


- Switch the channel selector to A-B (or invert one channel) and record the peak to peak amplitude of the resulting sine wave (the difference voltage).
- Calculate the phase angle from

$$\Phi = 2 \tan^{-1} \frac{\text{difference}}{\text{sum}}$$

or use the graph in Fig. 3.

When using this method one must understand its limitations. When making high-frequency measurements it is vital that probes are equally compensated —

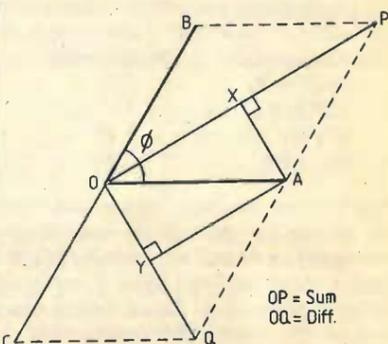Theory
In the phasor diagram, OA and OB represent the two signals being compared, with a phase difference of Φ between them, shown for convenience in the first quadrant. OC represents the OB signal shifted in phase by 180°, OP is the vector sum of OA and OB, and OQ is their vector difference. OB, OA and OC have been made equal.



AX and AY are perpendiculars from A to OP and OQ and AOP and AOQ are isosceles triangles.

angle AOP = angle APO = $\Phi/2$
and $OX = XP$
Hence $OX = AO \cos \Phi/2$
and $OP = 2AO \cos \Phi/2$
Similarly, $OQ = 2AO \sin \Phi/2$

Now, $\frac{2AO \sin \Phi/2}{2AO \cos \Phi/2} = \frac{\text{difference}}{\text{sum}}$
 $= \tan \Phi/2$

Hence $\Phi = 2 \tan^{-1} \frac{\text{diff}}{\text{sum}}$

Fig. 3 plots this result graphically.

best done by connecting both probes to one signal and adjusting for equal amplitudes. The accuracy of the method deteriorates as Φ approaches 0° or 180°. If the voltage measurement accuracy is $\pm 5\%$ then accuracy will be about 6.3% at $\Phi = 90^\circ$, reducing to about 10.5% at $\Phi = 12^\circ$ or 168° . Accuracy will also be impaired if significant distortion of either sine wave exists: it is useful to synchronize the time base and check the waveforms.

While the sum-and-difference method of phase measurement will never replace an accurate phase meter or vector voltmeter in the eyes of those who can afford them, it does offer a useful technique which can sometimes out-perform these instruments, particularly when the signals are noisy. I have used the technique on a switching regulator to measure 10mV signals in the presence of 100mV of noise.

"Tektronix understands" Value for money.

We sell the finest low cost oscilloscopes in the world.

The complete range of low-cost oscilloscopes available from Tektronix offers more choice and more value for money.

Because everyone needs a slightly different performance in either band-width/sensitivity or extra control functions, we offer a range with different specifications. There are 4 dual-trace oscilloscopes to choose from in the

Telequipment D1000 Series family, with 10 or 15 MHz bandwidths.

And there are 5 different Tektronix T900 Series oscilloscopes ranging from a 15 MHz single trace oscilloscope to a 35 MHz dual-trace oscilloscope with Delayed Sweep.

All our oscilloscopes are thoroughly pre-tested to meet

the high standards that go with our name. The result is solidly built oscilloscopes which are not only easy to operate and maintain but also represent the most reliable buys on the market.

The T900 Series is supported by a full range of accessories including battery power packs, cameras & scope stands.



Most oscilloscopes are sold & serviced worldwide by Tektronix.

Please send me more information on Telequipment Oscilloscopes T-900 Series Oscilloscopes

Name _____
Position _____
Company _____
Address _____

Telephone _____
Tektronix International Inc.
European Marketing Centre
Postbus 827, 1180 AV Amstelveen
The Netherlands

Tektronix
COMMITTED TO EXCELLENCE


TOP QUALITY REBUILT TV TUBES

Rebuilt on the most modern equipment to original manufacturers' specifications

- ★ HIGH FOCUS
- ★ LONG LIFE
- ★ FULLY TESTED
- ★ FULLY GUARANTEED



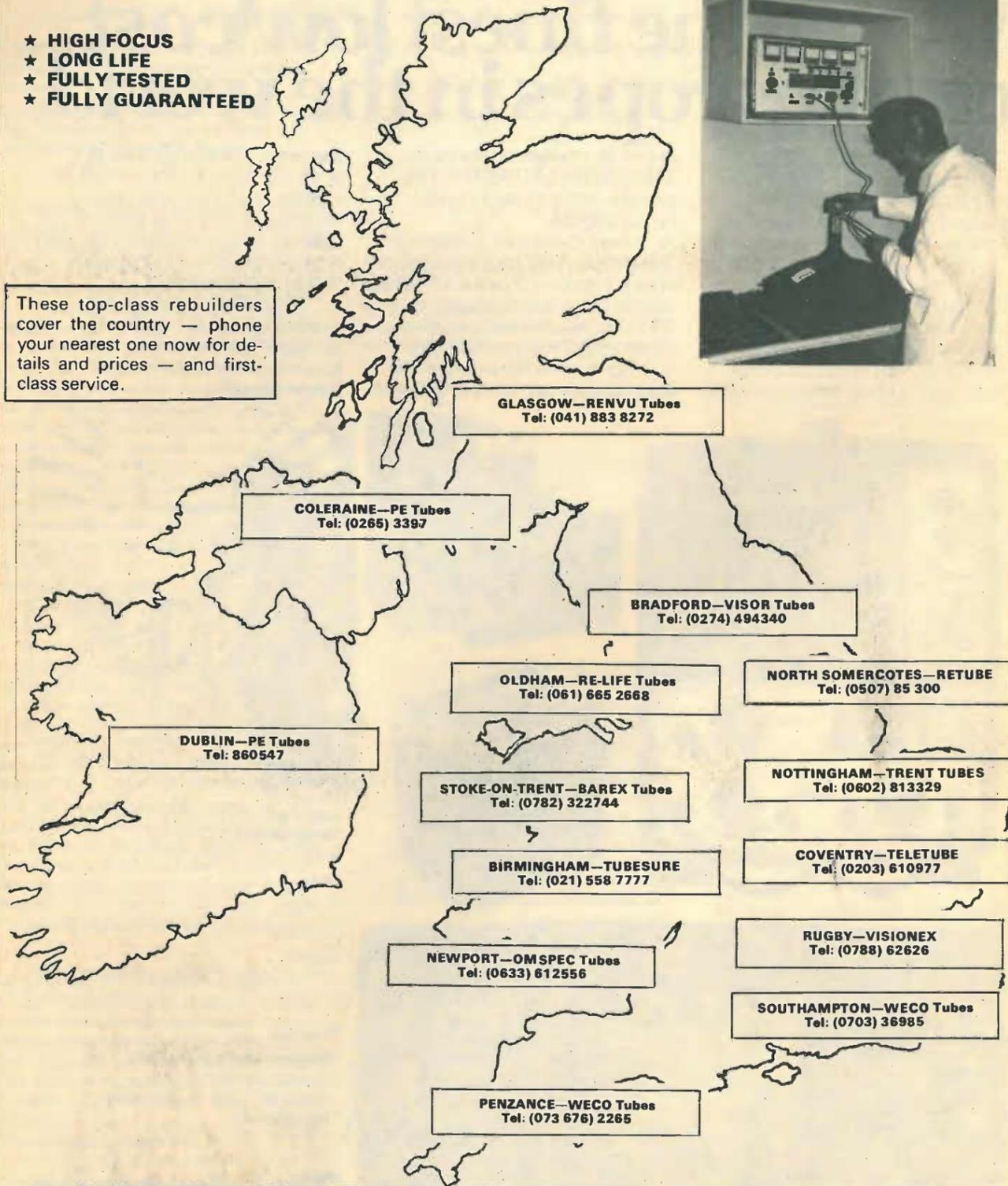These top-class rebuilders cover the country — phone your nearest one now for details and prices — and first-class service.



All these top-class rebuilders use plant and equipment manufactured by Western-Whybrow Engineering — acknowledged as the best available, and the product of more than twenty years' experience of rebuilding colour tubes in U.K. and U.S.A. There is a constant interchange of information to ensure the highest standard of rebuilt tube.

THE MARCONIGRAPH

No. 1.

April, 1911.

Subscription,
3 - per annum,
post free.

Price 2d.
Post Free 3d.

In 1911, the name of Marconi was almost synonymous with 'wireless': marine wireless operators were, as often as not, referred to as 'Marconi operators'. The growing profession of operating Marconi stations on board ship demanded a magazine, and the Marconi company responded in April 1911 with *The Marconigraph*, which carried news of the company, of operators scattered worldwide and of developments in wireless technique. Two years later, for reasons which have been aired before by writers more directly concerned with the event, *The Marconigraph* became *The Wireless World* and embarked on its declared life's work of being "of use and interest" to a rather wider fraternity than had been the case in its previous existence. Sticklers for detail may, with some justification, point out that *WW* is not 70 this month, but 68. We feel, however, that the two larval years should count towards the total for, while laying no claim to be roseate, we think *WW* quite as sweet as *The Marconigraph*.

While the new science and technology was at first naturally associated with ships' communications, there is a remarkably close parallel to be drawn between the development of radio (and later electronics) and aviation. Both technologies were emergent in 1911 (Bleriot had landed at Dover only two years earlier and Fleming's two-electrode valve was only seven years old), both were to advance rapidly in the two wars and have each, over the years, called for specific development in the other. In the beginning, communication was all, but even in the early days, direction finding and even radio landing aids were seen. The emergence of radar techniques and navigation systems changed the ways in which both civil and military aircraft were operated and even the design of some of them. Looking at it the other way round, the demands imposed on radio and electronics by military aviation in two wars and by an enormous expansion in civil air travel have hastened the development of avionics to a degree where only marginally-

stable aircraft become docile, but agile, and where landing aids are capable, in theory at least, of not only landing an aircraft in zero visibility, but getting it to the terminal building as well. Electronics and aviation are now so inextricably interwoven that airliners could hardly be operated without electronic assistance, and military aircraft would be unrecognizably different.

Wireless World, 1911-1981

From crystal detectors to microcomputers in 70 years

Wireless World has always reflected this use of electronics, beginning with the wireless sets used for gunnery spotting in 1916, reporting Lorenz instrument landing systems in 1935, gathering a whole mass of newly released radar information immediately post-war and continuing to report on air communication and navigation when the information is "of use and interest" to readers.

Our two enduring interests over the years have been radio and television broadcasting and reception, and the high-quality reproduction of sound. A great many of the leading figures in high fidelity have written in *WW*, and continue to do so, on theory and practice — an aspect perhaps best demonstrated by the publication of designs for D. T. N. Williamson's valve amplifier just after World War II, which set a standard to judge the rest by. People still write in to ask for reprints of these articles.

The Williamson standard was and is upheld by writers such as Jack Dinsdale, Arthur Bailey, Laurie Nelson-Jones, John Linsley Hood and many others on the

practical side of our content, and contributors of the calibre of Peter Baxandall, Professor David Bell, Thomas Roddam and the immortal Marcus Scroggie (Cathode Ray) have educated thousands of readers in the art of electronics.

Coverage of television began with Baird's first crude experiments, although the tone of some of our reports was a little bemused. It reached peaks in 1947 and 1968 with the publication of one of the first designs for a home-constructed monochrome television receiver (deflection yoke and line-output transformer both being home made) and the colour receiver by Walter Cocking, who made an enormous contribution to the standard of our practical articles over many years. The two receiver designs illustrated some of the reasoning behind *WW* projects, in that they were not necessarily the cheapest way of acquiring the receiver, or whatever was being built. One of the reasons for publishing them was that such a series of articles is undeniably the best way of explaining the operation of equipment. Even if one does not undertake the construction, the text is valuable in its own right.

In those days, of course, there were no integrated circuits. Circuit design was not the cost-effective deployment of the vast range of modules one can now select from, but the basic design that still goes on behind closed doors, its outcome being encapsulated in plastic. Integrated circuits have brought with them enormous opportunities for technical progress, but an unfortunate effect from a journal's point of view is that an article describing a piece of digital equipment often reads a little like a knitting pattern. It is not as easy as it used to be to read such articles in isolation.

Nevertheless, we have no intention of abandoning the ground rules laid down 70 years ago, that *Wireless World* should entertain, educate and be of use to the new generation, as well as their elders. It is doubtful that G. Marconi would recognize his grown-up brainchild, but we do hope he would approve. □

Designing with microprocessors

7 - Wait/go systems

by D. Zissos, Department of Computer Science, University of Calgary, Canada

Previous articles have described the synchronization problem and the most widely used solution involving software wait loops. In this article the wait/go concept is explained and step-by-step procedures for the design and implementation of wait/go systems are described. The design steps are illustrated by means of a fully worked out example.

The synchronization problem of microprocessors and the most widely used solution involving software wait loops have been described in previous articles. In this article we shall describe a hardware solution which involves keeping the microprocessor in animated suspension while the peripheral is responding. Systems using this solution are easy to design, program, implement and maintain.

The wait/go concept

Let us assume that we have a microprocessor which automatically enters the wait state when an i/o instruction is being executed. Let us further assume that when in the wait state it generates a logic 1 on wait terminal w , and that it exits the wait state when the signal on go terminal is pulled high ($g:=1$). The block diagram and state diagram of such a microprocessor are shown in Figs. 1 and 2. If we were to activate the peripheral with the 0 to 1 transition of the wait signal w and keep the microprocessor in the wait state until the peripheral had fully responded, we would clearly have no synchronization problems. Furthermore, if the peripheral is an action/status device¹, the interface reduces to two wires, as we show next.

The two-wire interface

Our starting point is the block diagram of a wait/go system shown in Fig. 3. The signals w , g , a and r have the following meaning:
Signal w : A '1' on this terminal (the wait line) indicates that the microprocessor has entered the wait state.
Signal g : A signal transition from 0 to 1 on this terminal (the go line) puts the microprocessor out of the wait state.
Signal a : A signal transition from 0 to 1 on this line triggers the peripheral into action.
Signal r : While the peripheral is responding $r=0$. When the peripheral has fully responded r changes to 1. No activation is possible when $r=0$.

Fig. 1. Block diagram of a wait/go microprocessor.

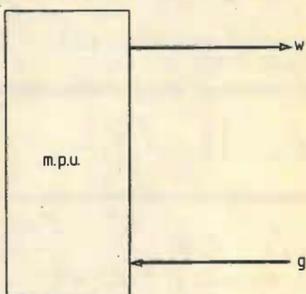


Fig. 2. State diagram of a wait/go cycle.

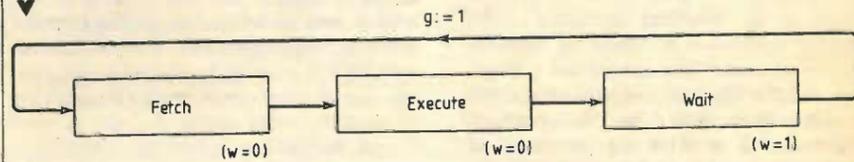


Fig. 3. Block diagram of a wait/go system.

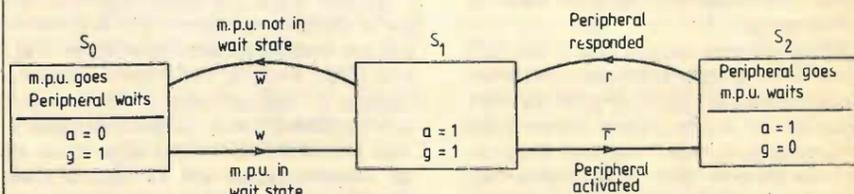
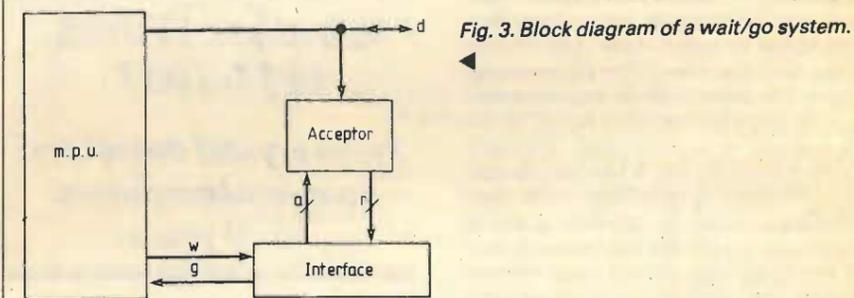


Fig. 4. Internal state diagram of a wait/go interface.

Fig. 5. State tables of the wait/go interface in Fig. 4.

wr	00	01	11	10
S ₀		(S ₀) a,g=0,1	S ₁ ∅,1	
S ₁		S ₀ ∅,1	(S ₁) 1,1	S ₂ 1,∅
S ₂			S ₁ 1,∅	(S ₂) 1,0

(a)

wr	00	01	11	10
S ₀₁₂	(S ₀₁₂) ∅,∅=0,0	(S ₀₁₂) a,g=0,1	(S ₀₁₂) 1,1	(S ₀₁₂) 1,0

(b)

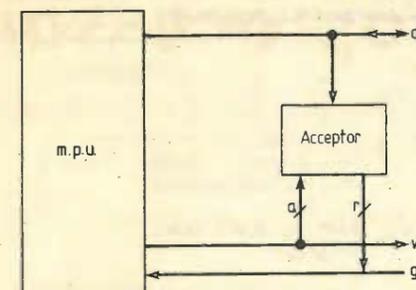


Fig. 6. The two-wire wait/go interface.

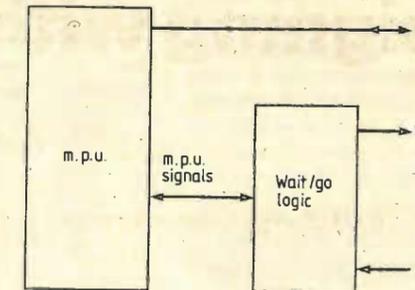


Fig. 7. Block diagram of the wait/go logic.

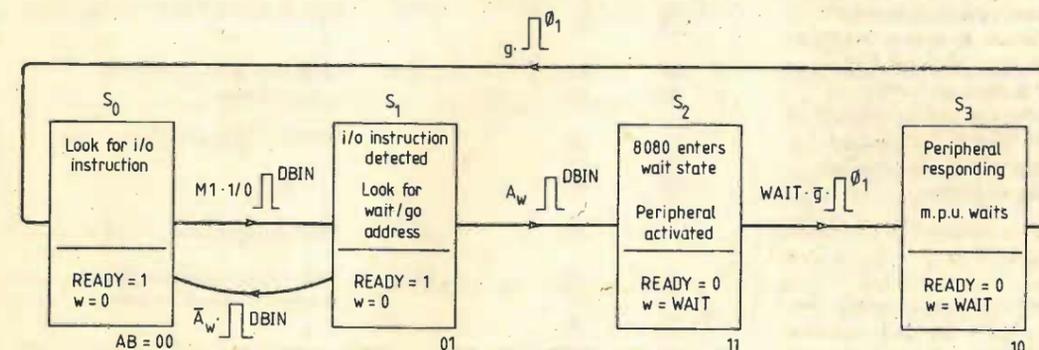


Fig. 8. State diagram of the wait/go logic for the Intel 8080.

A suitable internal-state diagram of a circuit to implement the above interface is shown in Fig. 4. Applying the reduction steps to its equivalent state table in Fig. 5 (a) allows its three rows to merge into one, as shown in Fig. 5 (b).

By direct reference to the reduced state table, we obtain the following equations
 $a = wr + w\bar{r} + (\bar{w}\bar{r}) = w$
 $g = \bar{w}r + wr + (\bar{w}\bar{r}) = r$

The corresponding circuit implementation consisting of two wires is shown in Fig. 6.

Advantages

- Wait/go systems are:**
- Easy to understand.** The 'wait' and 'go' are everyday concepts, not requiring specialist knowledge.
- Easy to design.** The hardware is straightforward and presents no difficulty. Specifically, in the case of action/status devices it consists of two wires.
- Easy to implement** - because of uncomplicated hardware.
- Easy to program.** Software overheads are minimal.
- Easy to maintain** - because of their reliability.

Wait/go logic

Although present-day microprocessors are not designed to operate in the wait/go mode, they can be made to do so by means of a relatively simple logic circuit, the **wait/go logic**, the block diagram of which is shown in Fig. 7. Its function is to look for i/o instructions with wait/go addresses, denoted by A_w , and to put the microprocessor automatically into a wait state when such an instruction is detected. At this point it passes exit control to the go terminal, that is to the outside world.

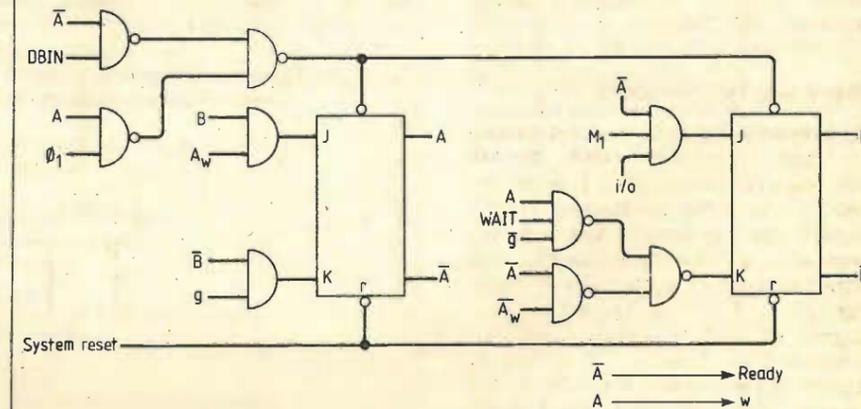


Fig. 9. Circuit implementation of the wait/go logic for the Intel 8080.

The design and implementation of wait/go logic is straightforward, as we demonstrate by means of the following example.

Wait/go logic for the Intel 8080

The m.p.u. signals of the Intel 8080 were described in the first article (May 1980 issue). Reference to these signals shows that the op code and i/o address are loaded into the m.p.u. registers in timeslots $M1 \cdot DBIN$ and the following $DBIN$ respectively. It follows that we can identify an i/o instruction by simply determining whether the signals on the data bus in time slot $M1 \cdot DBIN$ are 11010011 or not - 11011011 and 1101011 are the op codes for IN and OUT². Similarly, the wait/go addresses are identified by looking at the data bus with the following $DBIN$ signal. A suitable state diagram is shown in Fig. 8.

By direct reference to it, we obtain

$$S_A = S_1 \cdot A_w$$

$$= A \cdot B \cdot A_w \text{ therefore, } J_A = B \cdot A_w$$

$$R_A = S_3 \cdot g$$

$$= A \cdot \bar{B} \cdot g \text{ therefore, } K_A = \bar{B} \cdot g$$

$$S_B = S_0 \cdot M1 \cdot I/O$$

$$= \bar{A} \cdot \bar{B} \cdot M1 \cdot I/O$$

therefore, $J_B = \bar{A} \cdot M1 \cdot I/O$

$$R_B = S_1 \cdot \bar{A}_w + S_2 \cdot WAIT \cdot g$$

$$= A \cdot B \cdot \bar{A}_w + A \cdot B \cdot WAIT \cdot g$$

therefore, $K_B = \bar{A} \cdot \bar{A}_w + A \cdot WAIT \cdot g$

$$\text{Clock} = (S_0 + S_1) \cdot DBIN + (S_2 + S_3) \cdot \phi 1$$

$$= (\bar{A} \cdot \bar{B} + \bar{A} \cdot B) \cdot DBIN + (A \cdot B + A \cdot \bar{B}) \phi 1 = \bar{A} \cdot DBIN + A \cdot \phi 1$$

$$\text{Ready} = S_0 + S_1$$

$$= \bar{A} \bar{B} + \bar{A} B = \bar{A}$$

$$w = S_2 + S_3$$

$$= AB + \bar{A} B$$

$$= A$$

The corresponding circuit implementation is shown in Fig. 9.

A design problem: PRINT

The problem is to design and implement a wait/go system that would allow the programmer to produce a hard copy of data, which is stored in consecutive memory locations.

Solution

As explained in the previous article the first three design steps are independent of the microprocessor and therefore common to both solutions.

Step 1: aim of the design. The aim of the design is to expose the reader to wait/go systems.

Step 2: device characteristics. As specified.

Step 3: system design. The block diagram of our solution is shown in Fig. 10. Its step-by-step operation is flowcharted in Fig. 11. As in the case of the test-and-skip solution described in the previous article, we shall use index addressing. Addressing modes were described in Part 3 in the August issue.

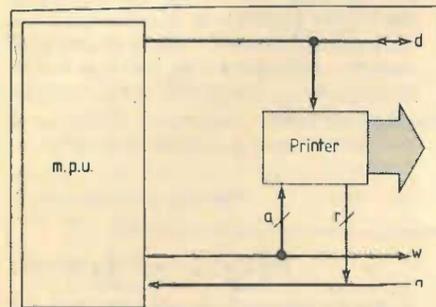


Fig. 10. Block diagram of the PRINT problem.

Table 1: Hex listing of the PRINT problem when implemented using the wait/go mode and the Motorola 6800.

Hex address	Hex listing	Mnemonics	Comments
0300	CE	LDX	Load index register with line 40 on page 20 - location of the first byte to be printed.
01	20		
02	40		
03	86	LDA A	Load acc. A with block length (n)
04	n		
05	97	STAA	Copy acc. A (n) into memory location (line 10 on page 20) to be used as a counter
06	20		
07	10		
M1: 08	27	BEQ	Branch to M2, if n=0 - forward 11
09	0B		
0A	A6	LDA A	Copy into acc. B next byte to be printed
0B	00		
0C	B7	STAA	PRINT - printer address 1000
0D	10		
0E	0D		
0F	08	INX	Point to next byte
10	7A	DEC	Decrement byte count (held) in memory location 2010
11	20		
12	10		
13	20	BRA	Branch to M1 - back 13
14	F3		
M2: 15	3E	WA1	Stop

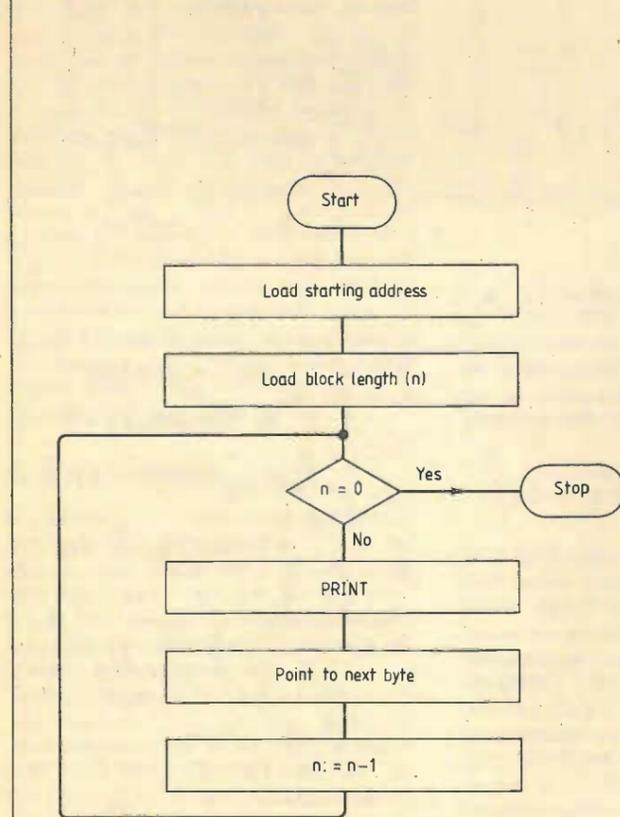


Fig. 11. Step-by-step operation of a wait/go system used to PRINT.

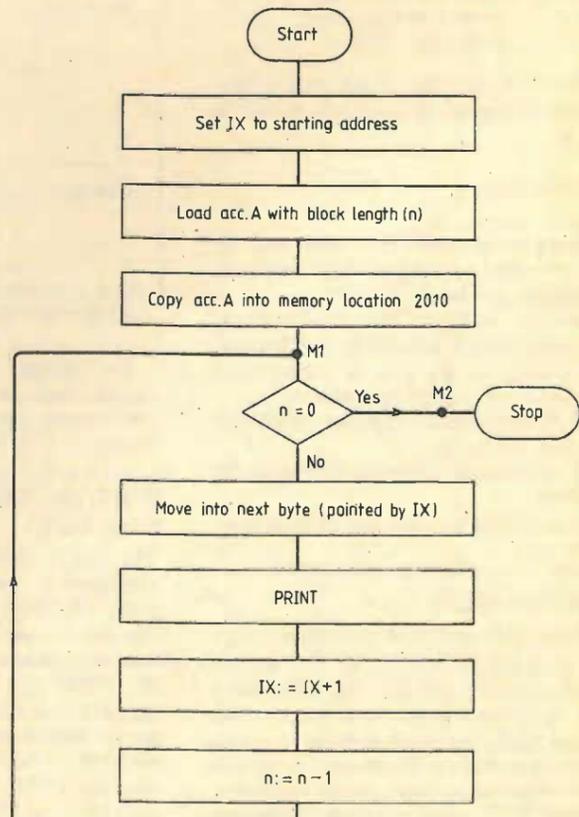


Fig. 13. Programming chart of the PRINT problem using wait/go and the M6800.

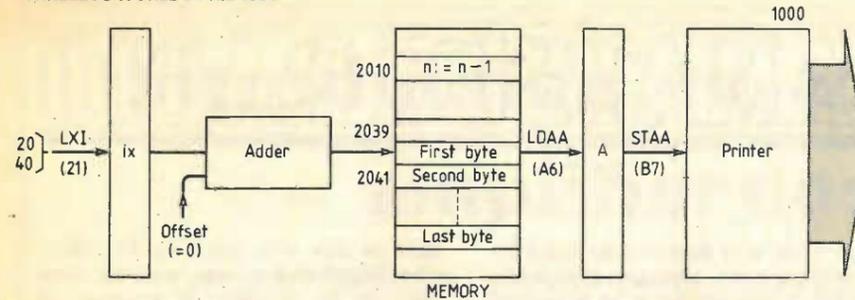


Fig. 12. Programming model for the PRINT problem using the M6800.

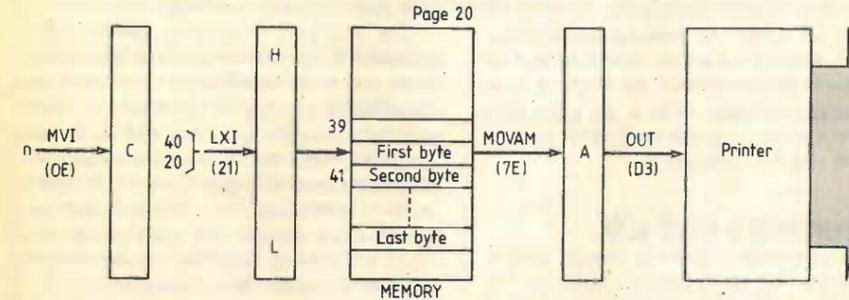


Fig. 14. Programming model for the PRINT problem using the Intel 8080.

Table 2: Hex listing of the PRINT problem when implemented using the wait/go mode and the Intel 8080.

Hex address	Hex listing	Mnemonics	Comments
1000	21	LX1 HL	Set memory pointer to line 40 on page 20 - location of the first byte to be printed
01	40		
02	20		
03	0E	MV1 C	Load register C with block length (n)
04	n		
05	0C	INRC	Increment C-sets flags
L2: 06	0D	DCRC	Decrement C
07	CA	JZ	Jump to L1, if n = 0 - that is if the zero flag is set
08	11		
09	10		
0A	7E	MOV A,M	Move into A next byte to be printed
0B	D3	OUT	PRINT
0C	06		
0D	23	INX H	Point to next byte in the block
0E	C3	JMP	Go to L2
0F	06		
10	10		
L1: 11	76	HLT	Stop

Demetrius Zissos is Professor of Computer Science and Adjunct Professor of Electrical Engineering at the University of Calgary, Canada. Educated in Britain, he has been associated with industry on both sides of the Atlantic for the past twenty years. He has written five books and numerous articles, including a series (with Brian Holdsworth) on logic design in Wireless World. He is currently writing two further books, one on logic design and the other on distributed systems.



6800 Solution

Step 4: hardware design. No interface hardware is required.

Step 5: software design. Our programming model and programming flowchart are shown in Figs. 12 and 13. Memory location 10 on page 20 is used as a counter and the first byte is stored in line 40 of the same page. Note that the programming model is the same as the one used for test-and-skip systems.

By direct reference to our programming model and to the M6800 instruction set³, reproduced in Part 4 (September issue), we obtain the hex listing of our wait/go software - see Table 1.

8080 Solution

Step 4: hardware design. As in the case of the 6800, no hardware is required.

Step 5: software design. Our programming model in the case of the Intel 8080 and programming flowchart are shown in Figs. 14 and 15. An m.p.u. register is assumed to be available for use as a counter. The first byte is stored in line 40 of page 20 in memory.

By direct reference to our programming model in Fig. 10 and to the Intel 8080's instruction set reproduced in the previous article, we derive the hex listing of our wait/go software. It is shown in Table 2.

References

1. Zissos, D., "System Design with Microprocessors", Academic Press, 1980.
2. Intel 8080 Microprocessor User's Manual, September 1975.
3. M6800 Microprocessor User's Manual, Motorola, 1976.

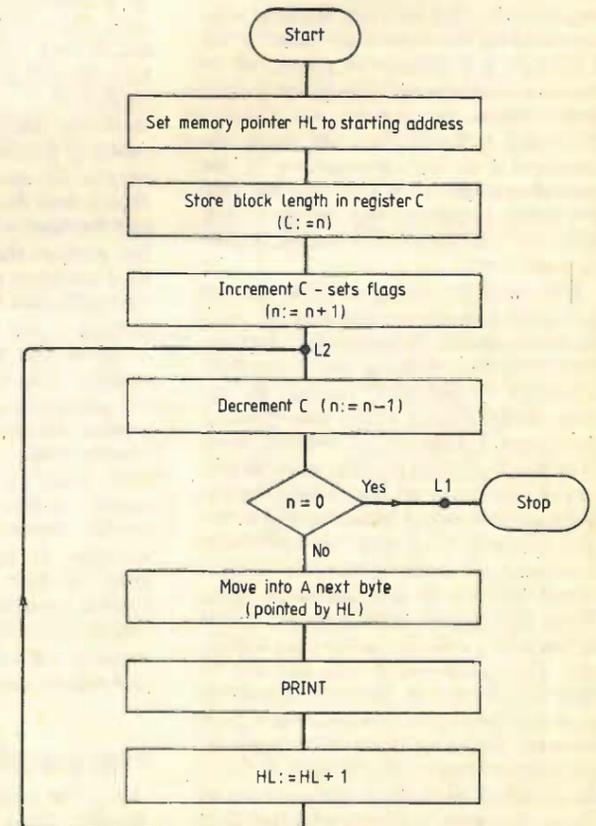


Fig. 15. Programming chart of the PRINT problem using wait/go and the Intel 8080.

WORLD OF AMATEUR RADIO

The earth-less vertical

In one of his series of classic papers on transmitting aeriels, Dr George Brown of RCA (*Proc IRE*, June 1937) analysed the efficiency of monopole radiators in terms of their use with 0.4λ buried radials, showing that typically an efficiency of up to 88 per cent can be achieved with 113 radials, reducing to only 12.4 per cent with just two radials. It is on this work that amateur use of the popular "ground plane" and "vertical" aeriels has largely been based for over 40 years, while the standard medium-wave broadcast aerial still tends to use 72, 120 or even 144 radials buried a couple of feet below the surface of the earth by means of mole ploughs, resulting in radiation efficiencies of the order of 75 to 90 per cent. More and more, in recent years, amateurs using verticals on 7MHz and below have been persuaded that an extensive earthing system or "mat" is a vital essential. Since such an earthing system cannot be fitted into the average garden, the h.f. monopole is generally accepted as not providing the sort of performance at long-distances of which it should be theoretically capable.

Recently, Leslie Moxon, G6XN, who has built up a considerable reputation for tilting at the many myths that are part of the "aerial lore" of many amateurs (and professionals), has been investigating what one could call the "cult of the radial" to see if effective h.f. directional arrays can be based on quarter-wave radiators at ground level without the use of any physical connection to earth. In doing so he has paralleled a similar investigation by the Australian amateur VK3AM who has been developing compact but efficient h.f. aeriels for use in confined spaces, including small boats.

This work is tending to show that, in fact, good efficiency is possible by using the once-popular "counterpoise" arrangement, but that this can be successfully shortened by inductive loading. In one form, G6XN is using with a base-insulated quarter-wave radiator, a 14MHz counterpoise a few inches above ground, consisting of a 7ft length of dural tubing parallel to the ground, with a linear loading inductance of about 11ft of wire. Such monopole (or dipole?) elements can be readily used as driven elements or as reflectors or directors (a two-element array however should be based on a reflector rather than a director). The counterpoise rods can also be used effectively to increase capacitive coupling between the array elements. Such elements can be easily moved to prepared positions to change the direction of fire of the array and taken down when not in use. The performance of an array formed from such elements would appear to be equivalent

to those of a similar array using an extensive earth mat, although, as might be expected, a little inferior to an equivalent horizontal array at moderate height. The vertical array, however, has many advantages of cost and convenience since it requires no tower, no rotating mechanisms and is not a permanent structure and so presumably falls outside the scope of local authority planning, while at the same time offering plenty of scope for further investigation and development.

Amateurs and c.b.

More and more it looks as though British amateurs will soon have to learn to live with, even if some of them may find it difficult to love, c.b. or Open Channel on frequencies additional to the proposed 928MHz. Indeed by the time these notes appear the die may well have been cast, although the package is likely to be so wrapped as to absolve the Home Office from any suggestion that they have been forced into making a "U-turn". But it is much to be hoped that amateurs will not allow themselves to be provoked into open hostility. Some of the common complaints made by some amateurs against c.b. could easily be represented as "sour grapes". For example, that amateurs always have to pay for licences, pass examinations, adhere to tight regulations, keep accurate logs etc, etc, so why should so many people have been allowed to "get away" with 27MHz operation? . . . and that sort of thing. But there are other, more seriously abrasive, causes of friction. Amateurs fear they will have to take the blame for interference and abuses since the media often fail to distinguish between c.b. operators and "hams". But perhaps the most serious problem of all is that many of the thousands of 27MHz c.b. units now being used in the UK will operate - and indeed often are operated - within the internationally "exclusive" amateur band 28 to 29.7MHz. Since most c.b. units are channelised it is possible that some of this intrusion is accidental, though in other cases it appears to be quite deliberate. Since the c.b. operators make no attempt to abide by "band-planning" or similar conventions, amateurs in many countries are seeing a virtual take-over of parts of their band. Unlike the radio control modellers they are not being offered alternative frequencies! C.b. enthusiasts would be well advised to play it cool and not stray above 28MHz.

Here and there

Australian amateurs are now permitted to handle "third party traffic" subject to three main exceptions. International traffic

must be only with countries that themselves permit such message handling; there must be no question of payment or material compensation, either tangible or intangible, direct or indirect; and no business traffic must be involved.

The problems of electromagnetic compatibility become ever more complex as more and more interference-producing or interference-susceptible electronics comes into use: interference from and to home computers and microprocessor-based appliances; automobile electronics; switched-mode power units (even the common or garden diode rectifier can emit hash); virtually all forms of electronics for entertainment or business. American amateurs are reporting yet another growing problem: transmitters causing false triggering of "smoke detector" alarms. The r.f. can be mains-borne and gets into the detector units unless protected by suitable r.f. bypassing. This requires care if the capacitors are not to interfere with the operation of the units.

An increasing problem for mobile operators, particularly since the public interest in c.b., has been the widespread theft of radio equipment from unattended vehicles. Most weeks, amateurs report the loss of several expensive transceivers (presumably when 27MHz units are stolen the illegal operators are reluctant to report the loss to the police). Recently, the West London 144 MHz repeater equipment of the UK FM Group was stolen and the Group has since taken out insurance on its other repeaters.

In brief

The G-QRP club, founded in 1975 to encourage interest in low-power operation, now has more than 1000 members in 24 countries, including over 200 in the USA the traditional home of the "Californian Kilowatt" . . . The Radio Amateurs Invalid and Blind Club now has a membership of over 600, including more than 300 licensed amateurs . . . PY2AA is the callsign of a new 50.055MHz beacon transmitter, with 25 watts power, located at Sao Paulo, Brazil. A South African multi-band beacon, ZS5VHF transmits on 28.2025, 50.005 and 144.925 MHz, the 28 MHz signals have been received well in the U.K. . . The British Amateur Television Club has just published an all-new "Amateur Television Handbook" with over 100 pages devoted to practical and up-to-date designs of amateur television equipment (Non-members £1.50 plus 35p postage from BATC Publications, 14 Lilac Avenue, Leicester LE5 1FN.).

PAT HAWKER, G3VA

Introduction to low-noise amplifier design

How to optimize collector current and calculate noise figure

by A. Foord

Many constructors still settle for more noise in their amplifiers than necessary because of the complexity of a full mathematical treatment and because manufacturers often fail to specify their transistor parameters in a convenient form. This article shows how to calculate the optimum collector current for a given source resistance and the minimum noise figure at that current, and gives practical circuits for instrumentation use and sound reproduction.

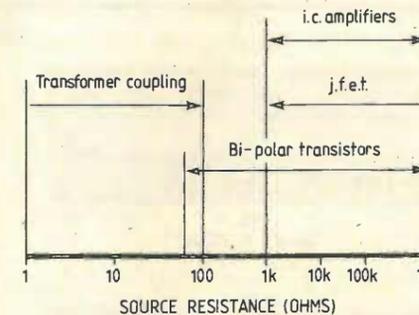


Fig. 1. Choice of input amplifying device depends on source resistance.

Once the basic design requirement of optimum collector current has been satisfied, the remaining amplifier parameters can be determined from the normal design relationships. For example, as the noise figure is independent of the transistor configuration and overall feedback, the usual feedback pair arrangements are practicable. Therefore the transistor and its operating point can be selected to meet the circuit noise requirements and the configuration or feedback can be determined to meet gain, bandwidth and impedance requirements. This approach allows the noise and other circuit constraints to be optimized independently.

The selection of a suitable input device depends mainly on the source resistance and bandwidth requirements. At the lowest values of source resistance it is necessary to use transformer coupling at the input to match the source resistance to the optimum for the amplifier, Fig. 1. Unfortunately transformers introduce extra losses and degrade the basic noise figure of the amplifier. For example, an amplifier designed for a 5kohm source might have a noise figure of less than 1dB. When matched with a transformer to a 30 ohms dynamic microphone this noise figure could be degraded to 2.7dB.

If integrated circuits are used their parameters are well specified by the manufacturer, but their noise levels are in general about two to five times that of a discrete transistor circuit. This makes them more suitable as second and succeeding stages. Fortunately bipolar transistors can be used for most audio front-end applications and this article is restricted to their use.

There is a slight difference between p-n-p and n-p-n transistors. A p-n-p transistor can have a lower base spreading resistance due to a higher carrier mobility in its base

region, while an n-p-n transistor often has a slightly larger current gain and bandwidth. This makes the p-n-p type more useful with low source resistances, with the n-p-n transistor useful at the higher end of the resistance range. For this reason, and also for direct coupled circuits, it is desirable to have information on a range of p-n-p and n-p-n devices.

A table of suitable low-noise transistors and their parameters is shown in Table 1. These are measured values and may not agree with those obtained from the manufacturers' specification sheets. Details of

some low-noise i.c.s are included for comparison.

Some noise mechanisms are process-dependent and result from faults such as surface defects, surface contamination, defective contacts, impurities, dislocations, and irregularities at the base-emitter junction. For this reason transistors with the same type number may vary from maker to maker. This is particularly true for low frequency noise below 1kHz where poor processing techniques become more apparent.

Any source unavoidably generates an amount of thermal noise power which depends on its temperature, Boltzmann's constant, and the system's noise bandwidth. Noise factor, as a ratio, is defined as

$$F = \frac{\text{total available output noise power}}{\text{portion of output power caused by source only}}$$

Noise figure is simply this noise factor expressed in decibels. $NF =$

$$10 \log \frac{\text{total available output noise power}}{\text{portion of output power caused by source only}}$$

or $NF = 10 \log F$. The noise figure is a measure of the signal-to-noise degradation attributed to the amplifier. For a perfect

Table 1. Measured values of low-noise device parameters may not agree with manufacturers data

		β at I_c of			r_{bb} (Ω)	Application
		1mA	100 μ A	10 μ A		
2N930	n-p-n	300	200	130	700	High source resistance
2N4124	n-p-n	300	200	110	100	Low source resistance
BC109	n-p-n	350	300	200	400	General purpose
2N3707	n-p-n	350	250	200	200	General purpose
2N4403	p-n-p	200	140	80	40	Low source resistance
2N4125	p-n-p	150	120	90	50	Low source resistance
2N3964	p-n-p	350	310	260	150	Low broadband noise
2N4250	p-n-p	350	310	260	150	Low broadband noise

IC type	V_n (nV/Hz ^{1/2})	I_n (pA/Hz ^{1/2})	R_s (k Ω)	f (Hz)	NF at R_s (dB)
TDA1034N	9.0	3.0	3.00	10	6.41
	3.5	0.4	8.75	1k	0.70
RM4739	20.0	4.0	5.00	10	10.41
	10.0	0.5	20.00	1k	2.11
LM201A	22.0	0.74	29.73	10	4.82
	16.0	0.20	80.00	1k	1.46
OP10EY	10.3	0.32	32.19	10	1.50
	9.6	0.12	80.00	1k	0.58
AD517	35.0	0.05	700	10	0.86
	20.0	0.03	667	1k	0.31
ZN460	0.8	1.0	0.800	5k	0.41

amplifier, one which adds no extra noise to the thermal noise of the source, the noise factor is unity, and the noise figure zero. Usually there is not a great deal of value in reducing the noise figure much below 3dB. A noise figure of 3dB is equivalent to saying that the amplifier and source are contributing an equal amount of noise to the wanted signal. Even if the amplifier noise could be reduced to 0.1 of the source noise, the total system noise is now about 0.7 of the 3dB condition. However it must be remembered that an amplifier with a noise figure of 0.5dB at 1kHz with a source resistance of 5kΩ will have a higher figure at low frequencies and at source resistances away from the optimum.

The normal procedure is to design the amplifier for a minimum noise figure at the desired source resistance. The optimum collector current for the transistor depends on the driving source resistance R_s and the direct current gain β .

Optimum collector current

$$I_c = \frac{(\beta)^{1/2}}{40R_s}$$

For example, determine the optimum current for a 2N4403 transistor with a source resistance of 400 ohms. Initially β can be taken as 200.

$$I_c = \frac{(200)^{1/2}}{40 \times 400} = 0.88\text{mA}$$

As shown in Table 1 a β of 200 at 0.88mA is possible. If the formula had given a much lower optimum collector current, say 50μA, then the β would have to be reduced to about 100 and the optimum collector current recalculated. This procedure is repeated if necessary until the β is believable for the calculated collector current.

The procedure is not too critical because of the wide variations in β between one transistor and the next and because the optimum collector current is proportional to the square root of β .

The minimum noise factor F at the optimum collector current can be calculated from the source resistance R_s , the current gain β , and the intrinsic base spreading resistance r_{bb} .

$$F = 1 + \frac{r_{bb}}{R_s} + \left(\frac{1}{\beta}\right)^{1/2}$$

For the conditions previously discussed for the 2N4403 transistor

$$F = 1 + \frac{40}{400} + \left(\frac{1}{200}\right)^{1/2} = 1.17 \text{ times}$$

Then the minimum noise figure is

$$NF = 10 \log F = 10 \log 1.17 = 0.68\text{dB}$$

Microphone preamplifier example

Many dynamic microphones have impedances of 200 or 600 ohms. The previous examples suggest that a 2N4403 transistor run at a collector current of about 1mA could be used for this application, and a suitable circuit is shown in Fig. 2.

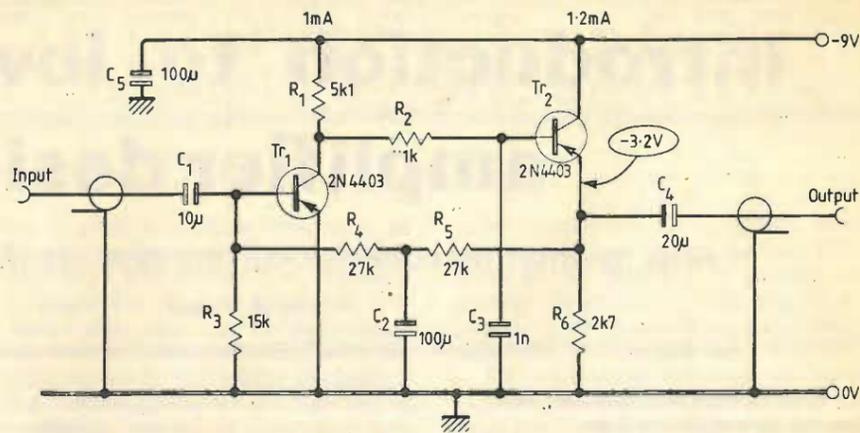


Fig. 2. Instrumentation preamplifier is suitable for microphone use.


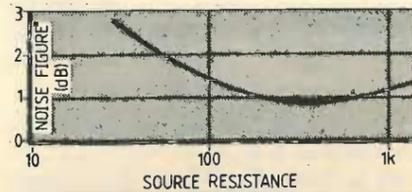


Fig. 3. Noise figure plotted against source resistance for the microphone preamplifier (top), and against frequency (bottom).

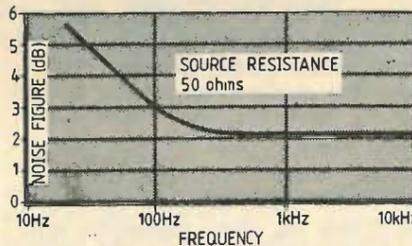

A common-emitter amplifier is followed by an emitter follower. The dc conditions are determined by the bias chain from Tr_2 emitter to Tr_1 base, but this does not provide negative feedback at signal frequencies because of C_2 . The low frequency response is determined mainly by the input and output coupling capacitors at 10Hz, while the high frequency response is determined by C_3 at 26kHz. If C_3 is not included the high frequency response would extend to 1MHz, which is undesirable.

The first transistor is essentially an unloaded common-emitter stage, and its gain at room temperature is

$$\frac{V_o}{V_i} \approx 40R_1 I_c = 204 \text{ times or } 46\text{dB}$$

Measured results on two amplifiers gave gains within 1dB of the calculated value. The input resistance was 2.7k ohms. As

Table 2. Comparison of several transistors for a 6kohm source.

	β	I_c (μA)	r_{bb} (Ω)	F	NF
2N930	150	51	700	1.198	0.79
2N4124	150	51	100	1.098	0.41
BC109	250	65.9	400	1.130	0.53
2N3707	220	61.8	200	1.101	0.42
2N4403	100	41.7	40	1.107	0.44
2N4125	100	41.7	50	1.108	0.45
2N3964	280	69.7	150	1.085	0.35
2N4250	280	69.7	150	1.085	0.35

Tr_1 has a high gain the noise contribution by Tr_2 is negligible. Fig. 3 shows the noise figure plotted against the source resistance, while Fig. 4 shows the noise figure plotted against frequency for a fixed source resistance; in this case the non-optimum value of 50 ohms.


These results confirm the theory, and show that the 2N4403 transistor is particularly suitable for both low source resistances and low frequency applications where noise is important.

Measurements on several 2N4403 transistors suggested that about one quarter of them had excess noise at low frequencies, but mid-frequency results were consistently low. For critical applications the amplifier input should be terminated with a 390-ohm wirewound resistor and Tr_1 selected for a minimum amount of noise. This noise can be measured at the output of the amplifier chain with an oscilloscope or a.c. voltmeter. An oscilloscope is particularly valuable because any low frequency or burst noise can be observed. If the preamp does not dominate the noise generated from succeeding stages (with the gain control at a maximum) then these stages need to be examined!

The full design of a general-purpose audio preamplifier can be quite a problem, and a magnetic pickup may be the most difficult source to match. Its impedance rises with frequency, the amplifier has an equalization curve which gives 20dB boost below 50Hz and 20dB cut at 20kHz, and the basic amplifier noise may be increasing at low frequencies.

The theoretically correct approach is to allow for all these factors and design for the lowest total noise over the complete audio bandwidth. This really demands an exact model for the circuit and a good computer program. In practice a reasonable answer can be obtained by designing for a source impedance of about 6k ohm.

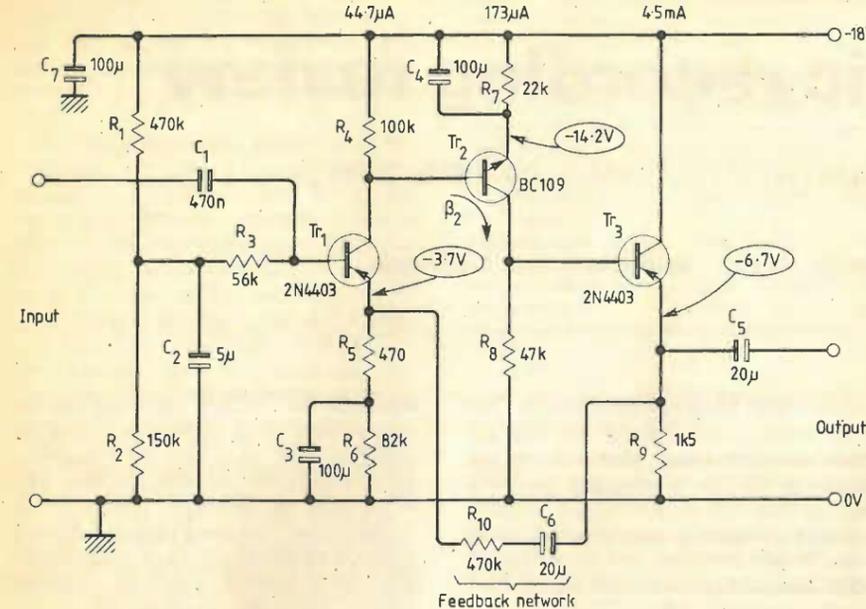In Table 2 several transistors are compared for this source impedance. All of these transistors appear to be suitable,



apart from the 2N930. The 2N4403 transistor has been chosen for the practical circuit, and the examples.

$$I_c = \frac{(\beta)^{1/2}}{40R_s} = \frac{(100)^{1/2}}{40 \times 6 \times 10^3} = 41.7\mu\text{A}$$

$$F = 1 + \frac{40}{6000} + \left(\frac{1}{100}\right)^{1/2} = 1.107$$

$$NF = 10 \log 1.107 = 0.44\text{dB}$$

One practical circuit might be similar to that shown in Fig. 5, where two common-emitter stages are followed by a common collector stage to drive the feedback network and the next stage. When Tr_1 is biased from a potential divider as shown, the only bias component which contributes noise is R_3 . The actual voltage drop across R_3 is small and therefore any excess noise generated by the resistor, due to the current flowing through it, is also small. The amount of thermal noise it generates is attenuated by the source. The value shown will provide the load resistance required for most magnetic cartridges, and can be shunted if necessary for other inputs.

The approximate open-loop gain for this type of circuit is

$$\frac{\beta_2 R_8}{R_5 + \frac{1}{40I_{c1}}} = \frac{320 \times 47 \times 10^3}{470 + \frac{1}{40 \times 44.7 \times 10^{-6}}} = 14,600 \text{ times} = 83\text{dB}$$

A practical measurement of this circuit gave an open-loop gain of 80dB, which is perhaps more realistic.

Unlike the first circuit, where the gain was well defined by the collector current, the gain of this circuit depends on the β of the second transistor. Overall negative feedback is therefore essential to accurately define the closed-loop gain. In Fig. 5 the closed-loop gain is 60dB and the frequency response is 3dB down at 8Hz and 45kHz.

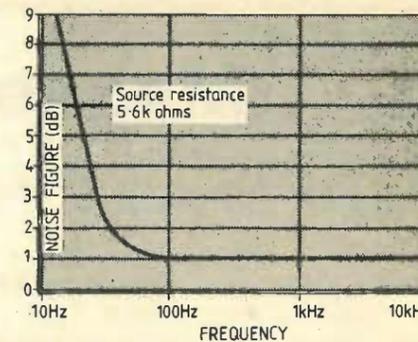


Fig. 5. Noise figure plotted against frequency for the general-purpose preamplifier of Fig. 4.

The closed-loop gain is defined at

$$G = 1 + \frac{R_{10}}{R_5} \text{ times.}$$

Resistor 5 is required so that the closed-loop gain can be defined by overall negative feedback. It also provides series local feedback for Tr_1 and reduces the open-loop gain by about 7dB. However the open-loop gain of 80dB which was measured is adequate to provide a reasonable amount of feedback at low frequencies even though the equalization curve demands a 20dB gain boost (below 50Hz) above the mid-band gain. The value of R_5 cannot be made too low as this will force a reduction in the feedback impedance, reducing the available output voltage swing at high frequencies where the equalization curve falls at 6dB per octave.

Although negative feedback does not alter the amplifier's noise figure, R_5 is effectively in series with the source and can contribute an amount of thermal noise, the effect of which depends on the source resistance. It should be made much smaller than the source resistance. Noise factor with R_5 is

$$F_r = F + \frac{R_5}{R_s}$$

In the example

$$F_r = 1.107 + \frac{470}{6000} = 1.185 \text{ times}$$

$$\text{thus } NF_r = 10 \log 1.185 = 0.74\text{dB}$$

Although this appears to be a significant degradation the resultant noise figure is still less than the 3dB level considered to be a reasonable value. It does indicate why an approach like Fig. 2 is valuable for critical applications, because the gain can be closely determined by the circuit parameters without using emitter degradation.

Further reading

Low-noise Electronic Design, by C. D. Motchenbacher and F. C. Fitchen (Wiley, 1973) gives many practical examples which are fully specified in terms of gain, bandwidth, and noise for up to four different values of passive components.

Fig. 4. Preamplifier as shown has flat frequency response; for use with magnetic pick-up replace feedback network with appropriate equalization network. Author recommends metal film or metal oxide resistors, as wirewound ones are bulky and expensive. Tantalum electrolytics are preferred over aluminium because of their lower leakage.

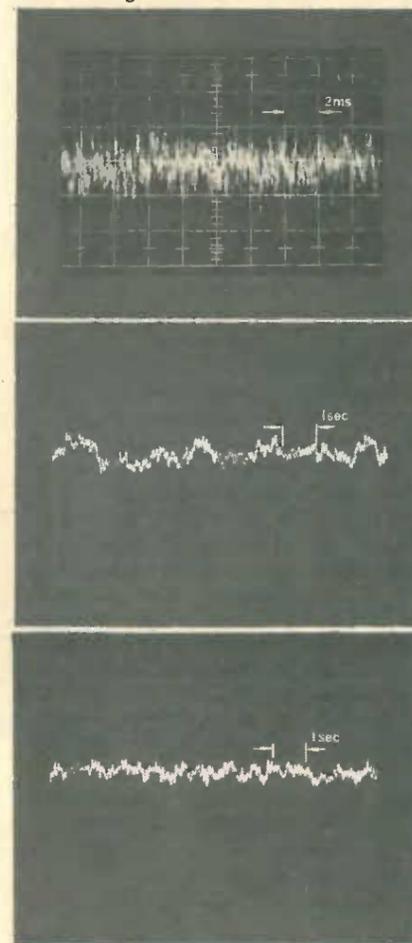


Fig. 6. Broadband noise from a 2N4403 transistor (top), low frequency noise from a poor 2N4403 transistor over 5 to 36Hz (middle), and low frequency noise from a typical 2N4403 transistor over 5 to 36Hz (bottom).

Magnetic recording review

2 - Performance of modern cassette tapes

by J. Moir, F.I.E.E., James Moir and Associates

Mr Moir continues his survey of magnetic recording technology and materials with an examination of modern cassette tapes. A brief look at possible future developments concludes the article.

Equalization

The limited frequency response of the early ferric coated tapes led to the extensive use of electronic equalization, a shaping of the frequency response of the record and replay amplifiers to improve both the frequency response and the s/n ratio. The correction required to achieve a flat overall record/replay response was divided between the record and replay system in a way that eliminated the need for variable equalization in the user's equipment. Standard replay calibration tapes were produced, having a closely specified response curve, and the recording engineer, having equalized his replay equipment to ensure that these standard tapes played with a flat frequency response, was required to vary the equalization of his recording system until the overall record/replay system response gave the same flat overall response.

However, the performance of tape coatings and our knowledge of record and replay head design has so far improved that the equalization originally specified is not only unnecessary but actually degrades the achieved performance of many of the recent types of tape.

The equalization to be applied to the system was specified indirectly as the relation between the signal voltage at the input of the recording chain and the resultant surface induction (now the short-circuit flux) on the tape. It was defined as the combination of two curves, one being the response of an RC circuit with a time constant of 1590 microseconds, defining the low-frequency performance, and a second RC circuit with a time constant of 120 microseconds defining the performance at frequencies above about 800Hz. The combined frequency response can be read from

Table 1: Standard time constants

Tape Speeds	Time Constant	
	t ₁	t ₂
76.2 cm/s (30in/sec) and 38.1 cm/s (15in/sec)	35	Infinity
19.05 cm/s (7½in/sec)	70	Infinity
9.53 cm/s (3¾in/sec)	90	3 180
4.76 cm/s (1¾in/sec)	120	1 590


Fig. 9, using the appropriate curves. The low-frequency signal is boosted and the high-frequency signal attenuated in the recording process to minimize distortion arising from the limited signal handling capacity of magnetic tape at high frequencies. Table 1 provides data on the agreed correction curves for all the current standard tape speeds.

To obtain a flat overall record/replay response, the replay chain must have the inverse response, but to achieve this some additional high-frequency equalization must be included to compensate for the high-frequency losses in the replay head.

The standard replay calibration tapes are recorded with a carefully calibrated, surface short-circuit flux/frequency relation that follows the specified recording curve. When these tapes are used to obtain a flat replay system frequency response the losses in the replay system are automatically corrected and the desired flat response is obtained for the whole record/replay chain.

During the few years following the standardizing of the 120µs equalization, the high-frequency signal-handling capacity of

Fig. 9. Recording characteristics (BS1568)

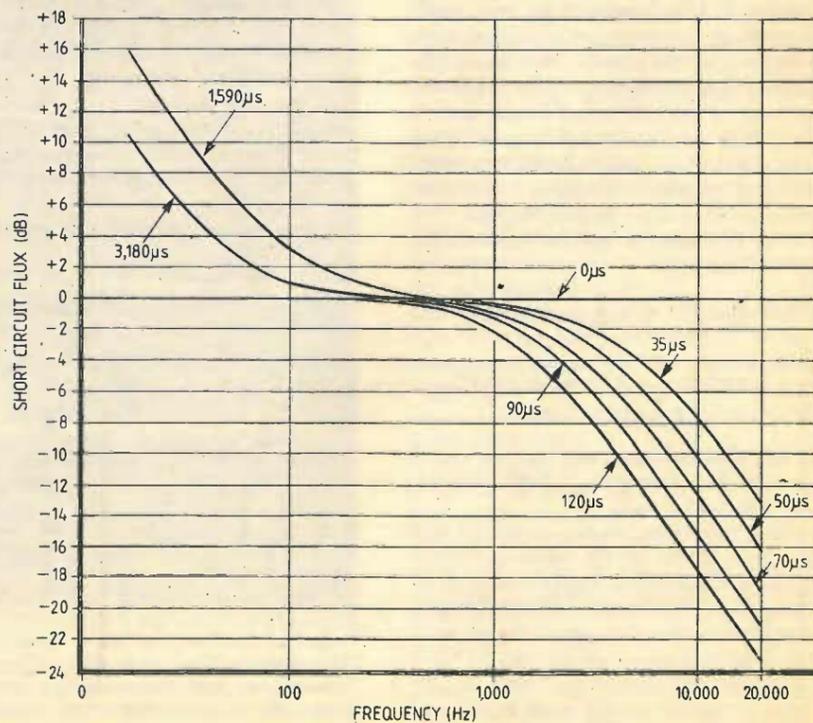

tapes has been greatly improved and designers have taken advantage of this by changing the recommended recording equalization time from 120µs to 70µs. This necessitates an equivalent change in the replay system frequency response, usually achieved by providing two or three alternative switch-selected frequency response curves. The 120µs equalization curve is used for all the ferric tapes and some of the early chromium and cobalt modified tapes, the 70µs equalization curve being employed with the later chromium and pure metal tapes.

Current semi-professional machines and the better domestic units now provide both bias and equalization adjustment, generally using separate controls. Used with understanding, this ensures near-optimum performance with most tapes. Professional and semi-professional machines usually provide a step-less control of bias.

Current tapes

At this point it appears appropriate to change from outlining simple theory to looking at some examples of current practice in tape production. About 100 samples of current cassette tapes from 25 suppliers were examined, using a Nakami-

chi 582 discrete-head machine, which is a good modern machine, with facilities for bias and equalization adjustment, and which is capable of handling metal tapes without saturating the recording head cores.

The bias settings were chosen using the Nakamichi facilities for equalizing the signal outputs at frequencies of 400Hz and 15kHz and with the equalization set to 120µs for the ferric tapes and 70µs for the ferrichrome, chromium dioxide and metal tapes. The bias settings are quoted in dB with respect to the appropriate DIN reference tape, but since there are as yet no metal reference tapes, the bias setting employed for these tests are quoted with reference to the Nakamichi metal tape.

The data for all the examples of each type of tape coating are averaged and these are the values in Table 2. The limits given in the 'Frequency Response' column should only be taken as being generally indicative of the results, the complete curves being used for any more detailed comparison.

The advantage possessed by the metal-particle tape of high saturation values at high frequencies is not immediately obvious from the data in the Table, being masked by the reduction of the high-frequency replay pre-emphasis from 120µs to 70µs. The higher levels of high-frequency signals that the metal tapes accept allows a reduction in the high-frequency attenuation of the standard recording amplifier and this in turn necessitates a reduction in the replay-amplifier high-frequency boost, with a corresponding improvement in the overall signal/noise ratio.

Typical response curves are provided for each type of tape in Fig. 10. Five separate bias levels are needed to enable optimum performance from every type of tape. However, the person who buys budget and 'special offer' tapes is unlikely to be interested in paying for a wide range of bias adjustment on his machine, so three levels of bias are probably adequate for the majority. Few of the cheap machines provide bias adjustments so the best performance is likely to be secured from the simple ferric tape.

The penalty for buying 'special offer' and 'advertisement-by-postal circular' types of tape is illustrated by the frequency response of Fig. 11. This is measured fre-

Fig. 10. Typical frequency response curves

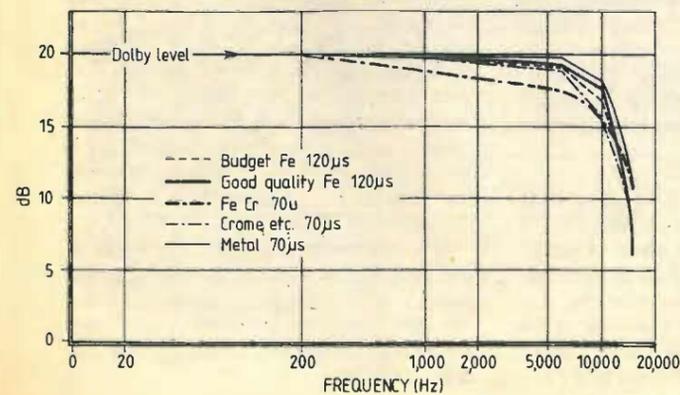


Fig. 11. Cheap tape performance

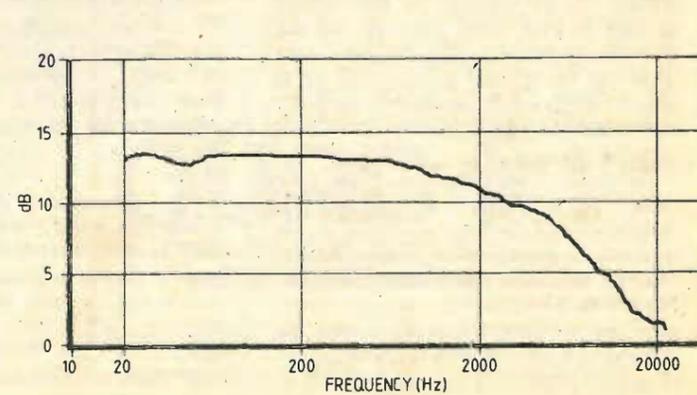


Table 2: Typical performance characteristics of cassette tapes

	Bias level	333Hz MOL	Sensit.	10kHz sat.	Noise (CCIR/ARM)	Print through	Freq. Resp. 10kHz-10dB (n.b. see also Fig. 10)
Budget quality Ferric tape	+0.39	+1.98	-1.38	-5.86	-50.65	-55.1	-1.65dB
Good quality Ferric tape	+1.26	+5.14	+0.03	-4.14	-50.76	-53	-1.34dB
FeCr tapes @ CrO ₂ *	+3.13	+7.3	-0.7	-6.38	-54.75	-49.5	-3.53dB
pseudo-chromes	+6.33	+5.09	+0.67	-6.12	-54.32	-47.85	-0.83dB
Metal tapes*	+11.3	+6.82	+0.6	-3.56	-54.48	-56.56	-0.2dB

* FeCr, CrO₂ and metal tapes all tested with 70µs equalization. Ferric tapes tested with 120µs equalization.

Notes

1. CrO₂ sensitivity quoted with respect to DIN CrO₂ sensitivity on optimum bias setting (+6dB)
2. FeCr sensitivity quoted with respect to DIN Fe sensitivity.
3. Metal sensitivity quoted with respect to Nakamichi ZX metal tape.
4. @ Equalization problem on Nakamichi with FeCr tapes.
5. All figures quoted with respect to Dolby level unless otherwise stated.
6. From an initial inspection of the Table it would appear that the high-frequency saturation level of metal tapes is little better than that of good-quality ferric tapes. However, the tests carried out on the metal tapes were with 70µs equalization whilst those in the ferric tapes were done using 120µs equalization. In absolute terms, the performance of the metal tape in this respect is at least 4dB better than the ferric tapes but, because the manufacturers have chosen to use a different equalization arrangement, the benefits of improved high-frequency saturation are not realized by the user. As far as the average user is concerned, the main advantage of using a metal tape would be an improvement of 4dB in background noise level.

quency response of a tape widely advertised under the name of, but having no connexion with, a very well known company. Not all such budget tapes are equally bad, however, and some of the very cheap ferric tapes may well be perfectly satisfactory in a machine bought for a youngster. At an intermediate price level, many own-name tapes from Boots and other well known multiple stores are excellent value for money.

The ferrichrome, two-layer tapes produced an unexpected response curve with a 'step' of about 4dB at frequencies in the region of 2kHz, presumably due to the magnetic discontinuity at the boundary between the chromium dioxide and ferric layers. This step would appear to require a special equalization curve to achieve the optimum performance.

With the bias optimized as described for

each type of tape, the metal tapes are seen to have the highest m.o.l. at 330Hz, the highest saturation level at 10kHz, the lowest noise level and currently the highest price, but note the qualification about optimizing the bias. A less well appreciated limitation to the use of metal tapes and even some of the CrO₂ tapes is the inability of many machines to fully modulate the tape at high frequencies, head design and circuit limitations being the apparent cause.

The performance of metal tapes used in machines incapable of providing the optimum bias is generally much worse than that of an intrinsically inferior ferric or ferric-chrome tape.

Some comment about the material employed for the tape base is probably interesting. The original tapes were all pvc-based, but in recent years tensilized poly-

ester has captured the market because of its superior mechanical properties and its relative freedom from the effects of humidity. Polyester has only a slightly greater tensile strength than pvc tapes, but is some eight times less susceptible to the effects of moisture, a great advantage in ensuring good spooling with a freedom from 'cupping' and variation in the tightness of wind. The pvc base is rather smoother than the polyester base but not significantly so. A smooth base is advantageous in reducing noise modulation effects due to the variation in coating thickness that results from changes in the thickness of the backing tape.

The nominal thickness of the tapes varies somewhat between suppliers but bases about 18µm, 12µm and 6µm thick are usually used for the three common lengths of tape, the C60, C90 and C120 types, the coating thickness being around 6, 4 and 3µm respectively. The C90 size tape is probably the best compromise between playing time and tape strength, the C120 type requiring more care in handling and gentler treatment in machines than is usual.

The use of a thick tape base has the obvious disadvantage of reducing the amount of tape that can be stored in a cassette or on an open spool, but it has advantages in reducing 'print through', the transfer of signals from one layer of tape to adjacent layers. These result in pre and post echoes that are obvious when they occur in the middle of quiet passages. The transfer is accelerated by storage of the tape in a warm environment and by long-term storage without replaying. Some tape coatings are more susceptible to the trouble than others, probably because of their increased temperature dependence.

The future

It is interesting to consider possible further improvements. The cassette format is here to stay, for its convenience clearly outweighs the residual deficiencies in performance. Its mechanical performance is not perfect, but is probably commercially adequate. Tape jamming is rare but still occurs, so the mechanics will be improved in this respect.

Tape saturation at high frequencies produces amplitude compression and harmonic-type distortions that do not occur in reel-to-reel recorders running at higher speeds. There is, therefore, some opportunity for improvement, but in most other respects the performance of the existing coatings is more than adequate for the commercial market. This suggests that achieving the present performance or at least a commercially acceptable performance at half the present tape speed is likely to be the next step.

Development in tape coatings that have contributed so greatly to improvements in performance of the cassette format do not appear to be applicable to 1/4 in tape, or at least do not have the same advantages. Most of the limitations in coating performance are wavelength-dependent and not frequency-dependent effects. An adequate frequency response for all professional re-

quirements can be secured from 1/4 in tape running at the present standard speeds and, in consequence, there appears to be no application for the new coatings in this field.

This situation does not hold for tapes used for tv and data recording, so the half-inch and wider tapes used for these applications are likely to benefit from coating developments that permit lower tape speeds.

Further reading

Daniel and Axon, The Reproduction Of Signals Recorded on Magnetic Tape, Part 3, May 1953.
Axon, Overall Frequency Characteristic in Magnetic Recording, *B.B.C. Quarterly*, No. 5, pp. 46, 1950.
Westmijze, W. K., Studies on Magnetic

Dividing by fractions

continued from page 61

triangular in form, has a frequency of half the last component, that is 378Hz, and a peak-to-peak amplitude of 0.0055 of an input period or, for a s.c. input,

$$226\text{ns} \times 0.0055 = 1.24\text{ns}$$

The final component is sketched in Fig. 6(c). The sequence A-B results in a phase error of $-0.005T$ and B-C in an error of $+0.006T$. B-C has thus over-corrected for A-B by an amount of $0.006 - 0.005 = 0.001T$. The sequence A-C is repeated by C-E, . . . etc and each time an additional error of $0.001T$ accumulates. This is repeated five times to point K, when the accumulated error reaches $0.005T$. Since the sequence K-L is identical to that of A-B, a correction of $-0.005T$ occurs, exactly eliminating the error. The steady accumulation of this error and its final elimination gives the jitter component seen in Fig. 6(c). It is nearly sawtooth in form, has a frequency of 68.75 Hz and a peak to peak amplitude of

$$226 \times 0.005 = 1.13\text{ns}$$

It has already been mentioned that removal of these jitter components is done with a phase-locked loop. The count of the divider has been so arranged that the low-frequency components of jitter are smallest in amplitude, as these are the most difficult to remove. If we set a specification of 1ns on the jitter, then both the final two components require little attenuation. The 756.25Hz component is the most difficult as its frequency is relatively low and amplitude high. At this frequency, we require 41dB attenuation, and this can be readily achieved in the phase-locked loop shown in Fig. 7.

The 111ns of jitter in a period of 65µs would give a p-p voltage perturbation of 7mV at the output of the phase comparator. For the moment ignoring any attenuation in the low pass filter, after the d.c. amplifier, 70mV jitter will appear at the input of the v.c.o. It can be shown that for a sawtooth variation at the input of a v.c.o.

Recording, Philips Research Laboratories Reprint R213-R214-R217-R222. (Originally in Philips Research Reports, Vol. 8, pp. 148-157, 161-183, 245-269, 343-366, 1953).
Daniel, E., A Preliminary Analysis of Surface-Induced Tape Noise, *IEEE Trans. on Comm. and Electr.*, V. 83, No. 72, May 1964.
Daniel, Eric D., and P. E. Axon, Accidental Printing in Magnetic Recording, *B.B.C. Quarterly*, Vol. 5, pp. 241-253, 1950.
Wallace, R. L., Reproduction of Magnetically Recorded Signals, *Bell System Technical Journal*, Vol. 30, Pt. 2, Oct 1951.
Review of Progress in Recording Materials, *IEEE Trans. on Magnetics*, September 1978.
Bate, G., Survey of Recent Advances in Magnetic Recording Materials, *IEE Trans. on Magnetics*, July 1978.
British Standard 1568 Magnetic Tape Recording Equipment. □

the output phase variation will be

$$\text{delta } \phi = \frac{1}{2} V K / f$$

where

delta ϕ = p-p phase deviation at the output
V = p-p voltage deviation at the input
f = frequency of sawtooth waveform
K = sensitivity of the v.c.o. in Hz/volt.

If the sensitivity of the v.c.o. is 100Hz/volt, the output phase jitter will be
 $\text{delta } \phi = \frac{1}{2} \times 0.07 \times 100 / 756$
= 0.0046 of an output period


If the input frequency is SC, then the jitter will be 1.05ns. Thus, only a small amount of attenuation need be provided by the low-pass filter to meet specification.

The circuit of Fig. 7 was the one used in the laboratory. If, as in an s.p.g., twice-line or line frequency were being generated from SC (Fig. 2) a phase-locked loop with similar time constants could be used.

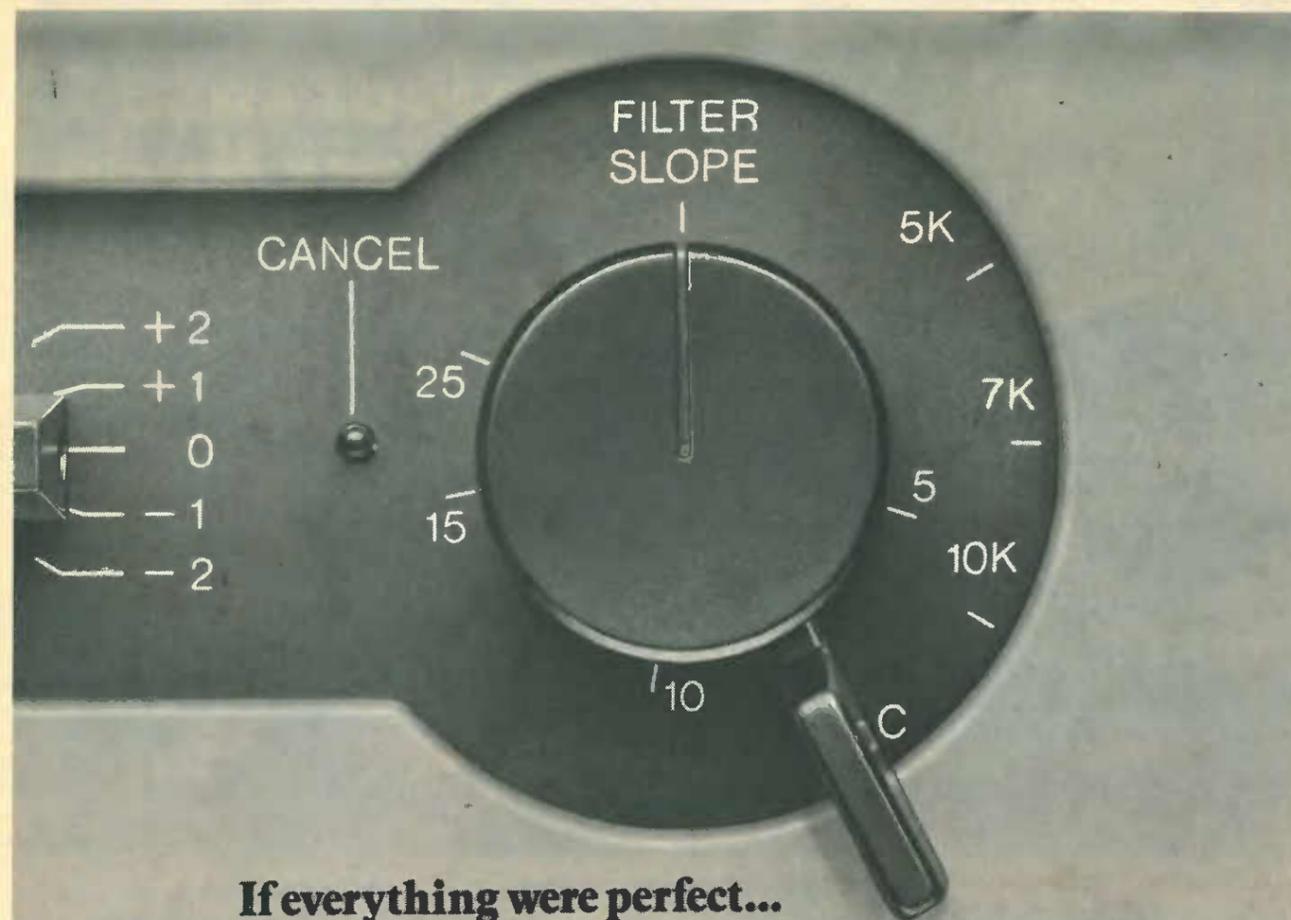2.2 divider

Performing this division is far simpler than that of the previous section. The division is performed by dividing by 2 and 3 in the ratio of 4:1. By taking the output of the last flip-flop within the 7490 as in Fig. 8, we obtain a waveform which is low and high in the ratio of 4:1. This waveform is fed to the programming of the 9310, where it instructs a division of 2 and 3. The output then, as appearing on pin 15, has an average frequency of 2LF, if the input is 68.75kHz. The jitter components present at the output will be 68.75kHz/5, i.e. 13.75kHz. Recalling the jitter analysis done in section 3, it will be clear that this is above that which would cause jitter with the filter and v.c.o. chosen; even though its amplitude is high.

If a division from SC to LF is required, the circuit shown in Fig. 9 would be suitable. This may be preferred, as it avoids the need for an extra flip-flop. The jitter frequencies would be similar to those for the 2.2 divider. □



If everything were perfect...

... a control unit would consist of a volume control and a programme selector switch.

In practice, correctly designed tone controls can make a significant contribution.

For a constant sound level, replay from a gramophone record produces distortion which increases very rapidly at high frequencies — doubling in fact for every major third increase in pitch.

There comes a point when the contribution of this distortion is increasing at a greater rate than the

musical content and this is what decides the optimum setting of the comprehensive Quad filter system, an essential and integral part of every Quad pre-amplifier.

The rate of attenuation can be set anywhere between 0 and 25dB per octave starting at one of three frequencies 5k, 7k, or 10kHz and an appropriate setting can be found for each record to provide more of the music and less of the distortion.

To learn all about the Quad 44 write or telephone for a leaflet.

The Acoustical Manufacturing Co. Ltd.,
Huntingdon PE18 7DB.
Telephone: (0480) 52561.



QUAD 
for the closest approach
to the original sound

QUAD is a registered trade mark.

WW — 008 FOR FURTHER DETAILS

A clear case for West Hyde

Hoseproof cases in aluminium and polycarbonate—two high quality ranges from West Hyde. Both sizes are manufactured in a large range of sizes to VDE requirements and offer protection to standard IP65.

Either type can easily be machined to accept our new range of glass-filled nylon Cable Glands.* The 'BOPAL' aluminium cases are competitively priced and give an extremely high strength to weight ratio. The 'BOPLAST' polycarbonate housings afford the same high degree of protection in an insulating material, and give the option of a transparent lid... clearly a case for specifying West Hyde.

***Cable Glands**
Cable diameter from 4mm-26mm
Option of flared skirt to prevent cable chafe.

WEST HYDE

West Hyde Developments Ltd., Unit 9,
Park Street Industrial Estate, Aylesbury, Bucks.
Telephone: Aylesbury (0296) 20441 Telex: 83570 W HYDE G

WW - 035 FOR FURTHER DETAILS

SAW devices from Mullard.

Backed by many years of research and development at Philips Research Laboratories, surface acoustic wave devices are now available as production components.

- * RF front end and IF filters
- * Oscillators * Delay lines * TV IF filters

Choose from a range of standard devices or let us make a customised design to your requirements.

For further details contact:
Brian Buckingham ext 2679 or Jack McIlravey ext 2767.

Mullard

MULLARD LIMITED, MULLARD HOUSE, TORRINGTON PLACE, LONDON WC1E 7HD. TELEPHONE: 01-580 6633. TELEX: 264341. Mullard manufacture and market electronic components under the Mullard, Philips and Signetics brands.

WW - 065 FOR FURTHER DETAILS

Surface acoustic wave devices

2 - More on bandpass filters, delay lines and oscillators

by R. J. Murray and P. D. White Philips Research Laboratories

This second part gives fuller information on the specification, operation and performance trade-offs of bandpass filters, delay lines and oscillators.

Bandpass filters

There are two types of s.a.w. bandpass filters. The first is the transversal filter, which consists of two or more interdigital transducers (see "principles") and is a travelling wave structure. These filters are wideband, with bandwidths of 0.2% to 100% of centre frequency. Centre frequencies in the range 10MHz-500MHz are readily achievable with a projected upper limit in excess of 1.5GHz. Design procedures are similar to those used for digital filters. The second type of bandpass filter is the resonator kind, which consists of one or more i.d.t.s in a cavity formed by two surface wave reflectors. This structure supports a standing wave. Bandwidths of 0.01% to 1% of centre frequency are feasible, with centre frequencies currently in the range 50-500MHz and ultimately greater than 1.5GHz. Design procedures are similar to those of conventional LC filters.

Transversal filters. Fig. 7 (a) shows a s.a.w. transversal bandpass filter, which consists of two i.d.t.s on a piezoelectric substrate. An electrical signal is fed into one transducer, converted to a surface acoustic wave, reconverted to electrical energy at the other i.d.t. and emerges as a filtered signal. An alternative structure is shown in Fig. 7 (b) which incorporates in the s.a.w. propagation path a multistrip coupler consisting of a series of parallel unconnected metal strips. This acts to transfer the surface wave from one track to another, providing discrimination against unwanted bulk waves which are also launched by i.d.t.s.

If two i.d.t.s have individual frequency responses $H_1(f)$ and $H_2(f)$, where f is the frequency, then the overall filter transfer function $H(f)$ is given by:

$$H(f) = H_1(f) \cdot H_2^*(f) e^{-j2\pi\tau} \quad (1)$$

where $\tau = L/v_0$, L is the geometric centre-to-centre separation of the i.d.t.s, v is the s.a.w. velocity and * denotes complex conjugate.

The filter amplitude response $A(f)$ is given by:

$$A(f) = |H_1(f)| \cdot |H_2(f)| \quad (2)$$

and the phase $\theta(f)$ by:

$$\theta(f) = -2\pi f\tau + \tan^{-1} \left\{ \frac{\text{Im}\{H_1(f) \cdot H_2^*(f)\}}{\text{Re}\{H_1(f) \cdot H_2^*(f)\}} \right\} \quad (3)$$

If $(H_1(f) \cdot H_2^*(f))$ is wholly real or wholly imaginary, the phase variation $\theta(f)$ in equation (3) becomes a linear function of frequency. This generally desirable property may be achieved by making each of the i.d.t.s symmetrical or antisymmetri-

cal about its geometric centre. S.a.w. transversal filters are usually non-minimum phase filters. This means that the amplitude and phase responses may be designed virtually independently of each other. In particular a very precisely defined amplitude response (e.g. with steep sides, a flat or even equi-ripple passband and good stopband level) can be achieved whilst maintaining a linear phase response i.e. constant group delay, τ . Typical delays are in the range 1 to 5 μ s.

In general, spurious signals will arrive at the output transducer with a different time delay from that of the main signal. These cause ripples in the amplitude, phase and

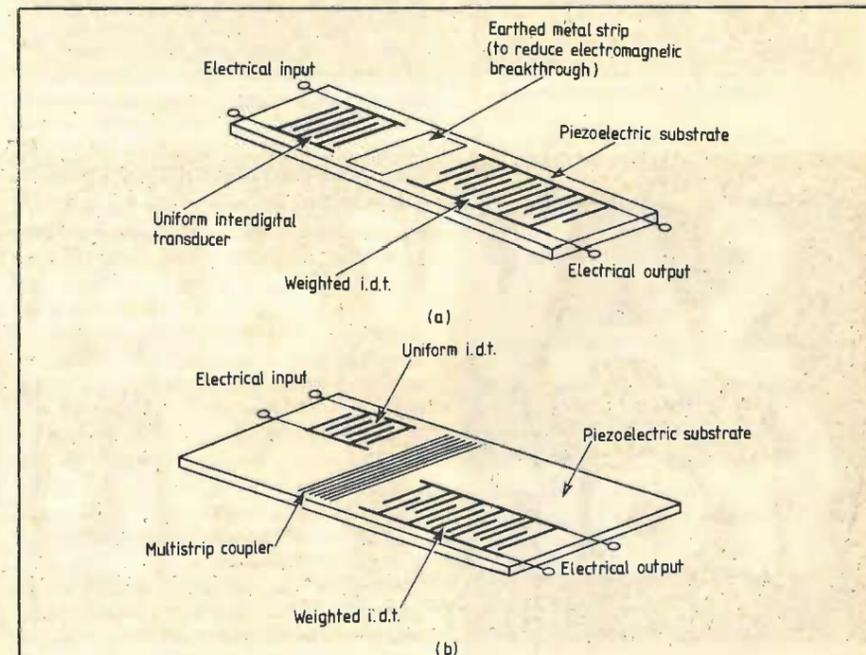


Fig. 7. (a) S.a.w. transversal filter geometry; (b) s.a.w. transversal filter incorporating multistrip coupler to suppress unwanted bulk waves.

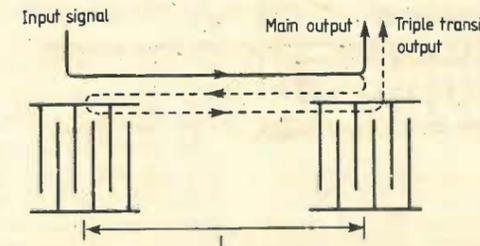


Fig. 8. Triple transit mechanism in s.a.w. devices. The triple transit signal results from successive electrical reflections from the output and input transducers before detection.

group delay responses of the filter. These spurious signals can cause quite large deviations from the ideal response and appropriate steps are usually taken to minimize them.

The most serious unwanted response is usually the triple transit signal which is illustrated in Fig. 8. This is caused by successive reflections from the output and input transducers before detection. If the main signal delay is τ , then the triple transit signal is delayed by 3τ i.e. 2τ more than the main signal. The period of ripples in the frequency response is thus $1/2\tau$.

The major contribution to the reflections which cause the triple transit signal is electrical and is a consequence of the three port structure of the i.d.t. The i.d.t. has two acoustic ports and one electrical port as shown in Fig. 9. When used for launching surface waves an electrical input

signal causes acoustic signals to be launched at both of the acoustic ports. If the electrical port is perfectly matched then half of the available power is delivered to each acoustic port. Conversely, if surface waves are incident on one acoustic port with the electrical port perfectly matched then half of the energy is delivered at the electrical port and one quarter is delivered at each acoustic port. This, for a filter consisting of two perfectly matched (electrically) conventional i.d.t.s, the minimum theoretical insertion loss is 6dB (never quite achievable in practice) and the triple transit signal is only 12dB below this level, which would result in an amplitude ripple of approximately 4dB peak-to-peak and a phase deviation from linear of approximately 25° peak-to-peak.

For most applications ripples of this magnitude are totally unacceptable. The simplest technique for reducing the triple transit signal, and the most widely used in practice, is to operate the filter with a mismatched source and/or load impedance. This increases the insertion loss but drastically reduces the level of the reflected signals. Using this technique a typical insertion loss is 20dB with peak-to-peak ripples of less than 0.3dB in amplitude and less than 2° from linear in phase. Therefore, when a filter has been designed to operate with mismatched terminations it is important to remember that any attempt to improve the match and thereby reduce the filter insertion loss will cause increased amplitude and phase ripple. Other, more complicated, methods of suppressing triple transit responses are available for use in filters with particularly difficult specifications.

There are several other spurious signals in s.a.w. devices which can be substantially reduced by suitable design of the i.d.t.s and substrate. Reflections from substrate ends are reduced by bevelling and applying acoustic absorber behind the i.d.t.s as shown in Fig. 10. Reflections within i.d.t.s are reduced by replacing each single electrode (a quarter of a wavelength wide) by a pair of like polarity 'double' electrodes (each an eighth of a wavelength wide) as in Fig. 11. Spurious bulk wave responses can be attenuated by the use of a track changing multistrip coupler on high coupling materials and/or by treatment of the lower surface of the substrate.

Resonator filters. A surface wave resonator consists of one or more i.d.t.s suitably positioned in a cavity between two efficient reflectors of surface waves as shown in Fig. 12. Unlike the more familiar bulk acoustic waves employed in bulk wave resonators, surface waves cannot be efficiently reflected by an abrupt discontinuity (e.g. a substrate edge) because this would cause a significant proportion of the energy to be mode converted into bulk waves. S.a.w. reflectors consist of a large number of small impedance discontinuities in the form of metal strips or grooves spaced by half a wavelength. This results in bandpass filters with peak amplitude reflection coefficients of typically 99% or higher. The resonant cavity will generally be capable of supporting several standing waves, and the required mode is selected by careful design of the reflectors and the i.d.t.

The electrical equivalent circuit of a

one-port s.a.w. resonator is shown in Fig. 13(a). This is similar to that of the familiar 'quartz crystal' bulk wave resonator, consisting of an LCR resonant section (the cavity) and a shunt capacitance due to the i.d.t. Two or more of these elements may be connected together to produce a coupled resonator. The equivalent circuit of a two port resonator is shown in Fig. 13(b). The capacitor C_c is defined by the coupling transducer and is given by:

$$C_c = 2C_o \frac{N_T}{N_C} \quad (4)$$

where N_T is the length of the input/output i.d.t.s and N_C is the length of the coupling i.d.t.s.

Normal coupled resonator behaviour is observed as N_C is changed, as illustrated in Fig. 14. By appropriate choice of structure, including in some cases inductive tuning, various standard filter types may be realised (Butterworth, Chebyshev, etc). In general, any number of resonators may be coupled together to form a multipole filter. A third-order filter is shown in Fig. 15.

S.a.w. resonator filters are low loss narrowband filters and are temperature stable if a quartz substrate is used. In the frequency range of application (50-1500MHz) there are very few suitable alternative filtering techniques and so the s.a.w. resonator allows narrowband filtering to be implemented at frequencies at which it has previously not been feasible. This has many implications in the design of modern systems where the filters may be included at the front end of communication systems and in the high frequency section.

Design procedures for s.a.w. resonator filters are similar to those for LC filters and the filters are minimum phase. Unlike transversal filters, the phase response achieved for a given amplitude response is uniquely defined.

Further details of delay lines

S.a.w. delay lines consist of two i.d.t.s suitably placed on a piezo-electric substrate. If each i.d.t. is geometrically symmetric or antisymmetric (about its geometric centre) then the delay line frequency response is band-pass with a linear phase characteristic. Identical uniform transducers are usually used and the amplitude response is, therefore, $(\sin x/x)^2$ (see section on "Principles"). Alternatively, with a suitable asymmetric design of the i.d.t.s the delay line can be made to be dispersive (i.e. the delay varying as a controlled function of frequency).

Linear phase delay lines can be made with bandwidths of up to 100% of centre frequency over the frequency range of 10MHz -1.5 GHz. Delays ranging from 400 nanoseconds to 30 microseconds or more can be achieved. Relative delays of less than 400 ns can be achieved directly if electromagnetic breakthrough is not a problem, or as the differential delay between two delay lines. The most attractive feature of s.a.w. delay lines is that rela-

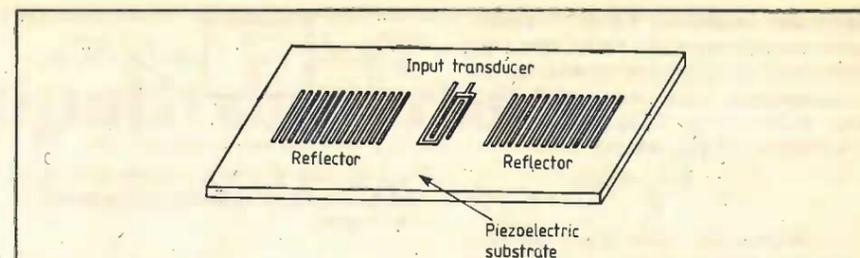


Fig. 12. One-port s.a.w. resonator geometry showing the transducer located between two reflectors.

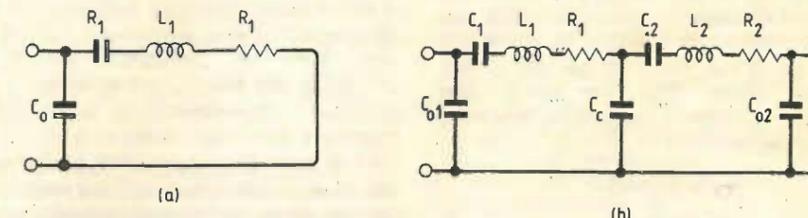


Fig. 13(a) Equivalent circuit of one-port s.a.w. resonator; (b) equivalent circuit of two-port s.a.w. resonator.

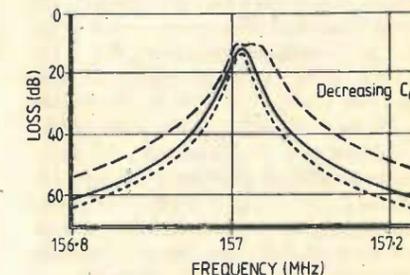


Fig. 14. The effect of varying coupling on s.a.w. resonator response. Note that decreasing the value of the capacitance C_c increases the coupling and results in a broader bandwidth and lower loss as with conventional filters.

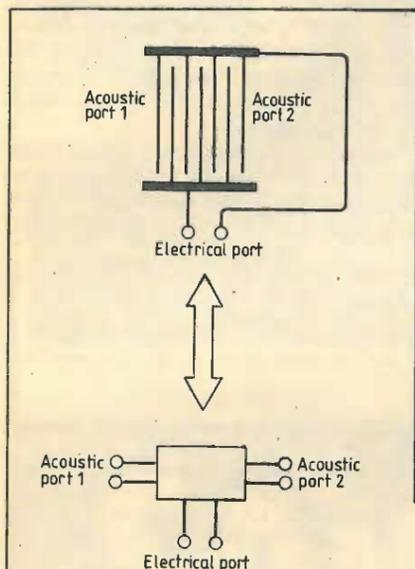


Fig. 9. Three-port nature of the interdigital transducer.

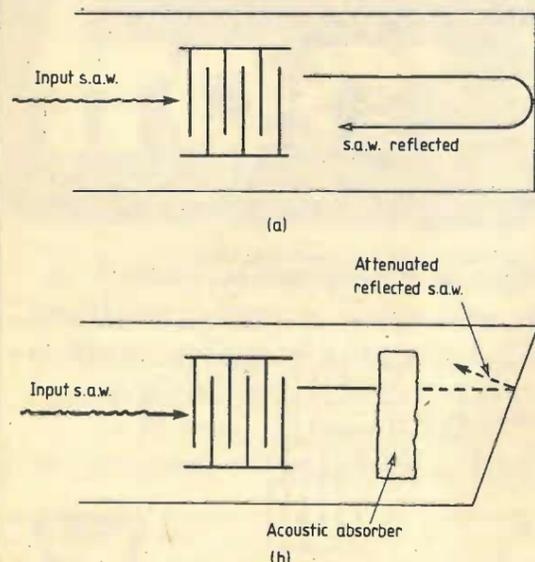


Fig. 10. (a) Spurious s.a.w. reflections from substrate end; (b) suppression of reflections from substrate end. These reflections cause distortion of the filter amplitude and phase responses.

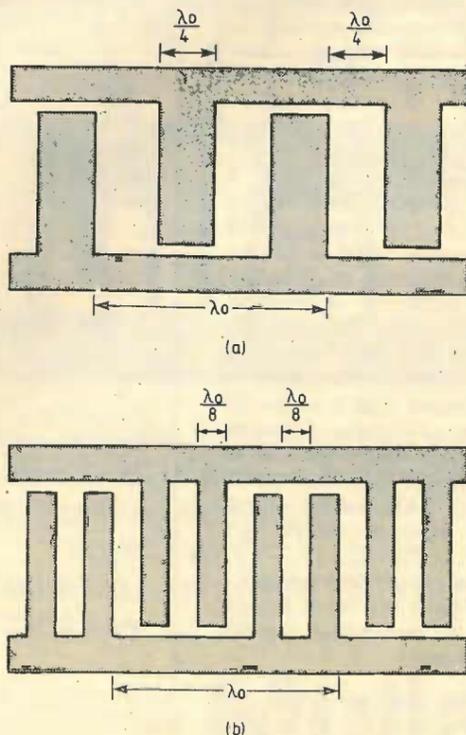


Fig. 11. (a) Conventional 'single electrode' interdigital transducer; (b) equivalent 'double finger' interdigital transducer used to suppress mechanical reflections.

tively large delays can be achieved in a small volume. For an ST-X (temperature compensated) quartz substrate, a delay of 1 μ s can be obtained with an acoustic path length of 3.2mm.

Applications include radar systems, electronic countermeasure systems and target simulators. S.a.w. delay lines can also be used in discriminator circuits such as that shown in Fig. 16 where a signal is fed to a double balanced mixer via two paths, one direct and the other through a s.a.w. delay line. Provided the delay line has a linear phase response the d.c. voltage output from the mixer is a cosine function of the input frequency and is approximately linear over a reasonable bandwidth. Linearity can be achieved over a wider bandwidth by limiting the signals at the mixer inputs to square waves.

Further details of s.a.w. oscillators

There are two distinct types of low noise, stable s.a.w. oscillators. The delay line oscillator employs a conventional s.a.w. delay line in the feedback loop of an amplifier; the frequency may be linearly modulated by typically 0.1%. The one-port s.a.w. resonator can be used in essentially the same oscillator circuits as conventional bulk wave resonators, or two port resonators can be used in an amplifier feedback loop. Resonator oscillators can only provide very narrowband linear frequency

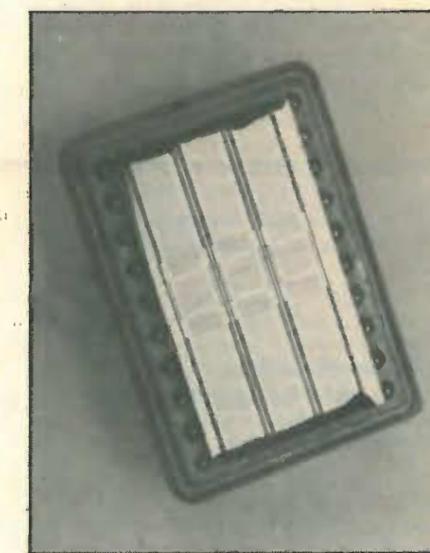


Fig. 15. A third order s.a.w. resonator filter (package size 28mm x 20mm). The central transducers and end absorber are clearly visible.

modulation but can provide better noise performance. Both types of oscillator can work at fundamental frequencies in the range 10MHz-1.5GHz without additional multiplying circuitry. The devices are considerably smaller, cheaper and lighter than conventional oscillator techniques.

Delay line oscillators. Fig. 17 is a schematic representation of a s.a.w. delay line oscillator. The delay line consists of two i.d.t.s separated by a distance L , with a delay of L/v corresponding to a phase shift at a frequency of ϕ_{DL} , where:

$$\phi_{DL} = \frac{2\pi Lf}{v} \text{ radians}$$

Oscillation will occur when the total phase shift around the loop is equal to an integer (n) multiple of 2π , i.e.

$$\phi_E + \phi_S + 2\pi \frac{Lf}{v} = n2\pi$$

where ϕ_E is the electrical phase shift around the loop (excluding delay line and phase shifter but including the amplifier) and ϕ_S is the phase change due to the phase shifter. The loop would thus support a comb of frequencies separated by Δf , where:

$$\Delta f = \frac{v}{L}$$

The required mode (at f_0) is selected by suitable design of the i.d.t.s so that frequency f_0 is passed but frequencies $f_0 \pm n\Delta f$, where n is a non-zero integer, are located at nulls of the response of the delay line. One simple way to achieve this is for one i.d.t. to be a uniform transducer with N periods where $N = (L/v)/\Delta f$; this makes the centre frequency f_0 with traps of the $\sin x/x$ response at frequencies $f_0 \pm n\Delta f$. This technique is illustrated in Fig. 18. Transducers with a proportion of electrodes removed (thinned i.d.t.s) are often used to increase frequency reproducibility and to reduce internal reflections.

The frequency of the oscillator loop may be modulated by variation of the phase in the phase shift circuit which usually incorporates one or more varicap diodes. The output signal can be taken at any point around the loop (but not usually immedi-

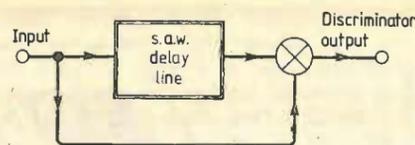


Fig. 16. Delay line discriminator using the good linear phase characteristics of the delay line.

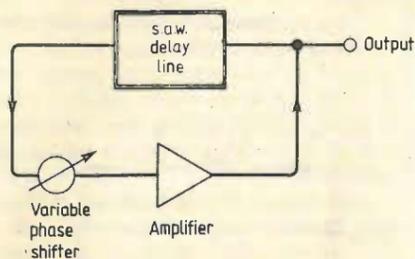


Fig. 17. Delay line oscillator. The circuit will oscillate at a frequency where the total phase shift around the loop is an integral multiple of 2π .

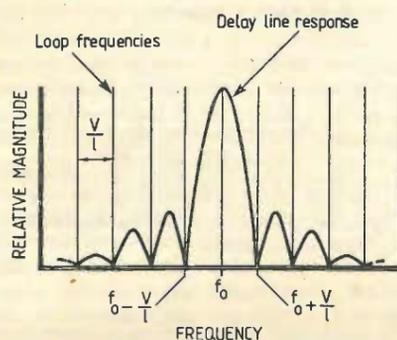


Fig. 18. Loop frequencies and transducer response of s.a.w. delay line oscillator, showing the comb of loop modes, one of which (f_0) is selected by the transducer response.

ately after the modulator). For maximum power this would normally be immediately after the amplifier; for minimum noise, immediately after the delay line is best.

The gain of the amplifier used must be greater than the loss around the loop and it is common to operate the loop with the amplifier saturated. The delay line loss will typically be 10-20dB, depending on the electrical matching.

Resonator oscillators. S.a.w. resonators (see earlier) are high Q components operating at frequencies of 50MHz and above. Unloaded Qs in excess of 20,000 can be achieved at 250MHz. This makes it possible to use these devices as oscillator control elements to provide stable sources at fundamental frequencies in the range 50MHz to 1.5GHz.

A s.a.w. resonator may be used in an oscillator as either a one-port or two-port device. If a two-port configuration is used then the circuit becomes similar to that used for delay line oscillators, i.e. an amplifier and a s.a.w. device in a feedback loop. The advantage of a resonator over a delay line in this case is that the amplifier need only provide 4 to 5dB of gain since the resonator has a lower insertion loss than the delay line. However, because the frequency response of a resonator is not linear phase, except over a very narrow range (approximately 0.02%), there is less potential for linear frequency modulation.

If the resonator is used as a one-port device then the circuit would be similar to that used for bulk wave crystal oscillators (e.g. Colpitts, Pierce), and because of the higher frequency (at u.h.f.) the construction could be based on a cavity or resonator stabilized microwave oscillator. A single transistor can be used in some cases, giving a very compact oscillator. □

Multipath distortion

— does polarization matter?

by Pat Hawker, Independent Broadcasting Authority

Many broadcasting authorities have introduced, or are planning to introduce, vertical or circular polarisation in the transmitted signal to help reception on vertical aerials in cars or on domestic receivers. However, there is some correlation between polarisation and an increase in distortion caused by receiving the signal from more than one source. Research in Japan and Germany has helped to analyse the problem.

A recent survey article — "How serious is multipath distortion?" (Ref 1) — drew attention to the lack of recognition in the UK that multipath propagation is probably the most serious cause of the degradation of quality when v.h.f./f.m stereo broadcasts are reproduced in the home through good quality equipment, even when reasonably careful regard has been paid to aerial installation.

The article stressed that over 25 years after the start of regular v.h.f./f.m mono broadcasting in the UK (May 2, 1955) and about 15 years after the gradual introduction of pilot-tone stereo, there was still widespread lack of knowledge about the extent, and methods of mitigating multipath effects, induced to some degree by the reluctance of broadcasters, long concerned with the problem of encouraging more listeners to use v.h.f./f.m rather than m.f./a.m, to draw attention, except in the most simplistic terms, to this problem.

Since that article was written, several developments have taken place that deserve serious consideration by those interested in high-quality reproduction of broadcasting.

(1) While the original article drew attention to the work carried out by NHK in Japan, the information then available was limited to a short English-text summary. Full details of this valuable investigation have since been published by Mitsuo Ohara in *IEEE Transactions on Broadcasting* (Ref 2). This paper makes it clear that multipath distortion is "far greater" on stereo than on mono transmissions and also reduces stereo separation (although the early investigations in the US and UK between 1940-1960 were of course confined to mono). Additionally it shows that multipath can be the cause of serious crosstalk into the broadcast programme of information carried on additional sub-carriers, including the SCA (subsidiary authorization channel) system widely used in the USA and, by implication, the

ultrasonic tone signalling systems used in the UK, and the experimental 'programme labelling' systems, etc.

(2) Investigations carried out in the Cologne area of West Germany, including 212 site tests carried out from five specially equipped vehicles, and reported in *EBU Review-Technical Part* (Ref 3) indicate that the addition of a vertical component to horizontally polarized transmissions, that is any form of mixed polarization, significantly increases rather than decreases the extent of multipath distortion, even for listeners with good, outdoor horizontally polarized aerials. This report emphasises that from both the economic and purely technical points of view, the adoption of circular polarization in West Germany would be undesirable. This report has been published shortly after the BBC announced its intention (Ref 4) of adding a vertical component to the main BBC national v.h.f./f.m networks of Radio 1-4 (with Wrotham to be modified in 1981), on the grounds of providing a better service for listeners using car radios, although the German investigators question even this assumption.

(3) The vulnerability of digital systems (including teletext) to short as well as long term echoes was noted in the earlier article. Since then it has become clear that British Telecom are experiencing more problems than they anticipated in the planning of high-speed digital networks (140 Mbit/s etc) even on strictly line-of-sight microwave links. *The Post Office Research Review 1979* (Ref 5) notes that: "Analogue f.m (link) systems are relatively tolerant of the signal distortions produced by multipath propagation which will cause an increase in intermodulation noise... in digital systems, the signal components arriving by alternative paths cause intersymbol interference... errors in the phase of the recovered carrier and timing signal which result in a more severe degradation in system performance". To overcome multipath propagation and deteriorations in cross-polar discrimination, both phenomena which in this context vary rapidly with time, British Telecom are considering such remedies as aerial height diversity, adaptive spectrum shape equalization, adaptive decision feedback, etc — all systems of some complexity, particularly when, as appears likely, it was initially expected that the 'ruggedness' of digital transmission would not require these added costs.

It is now clear that even well-planned

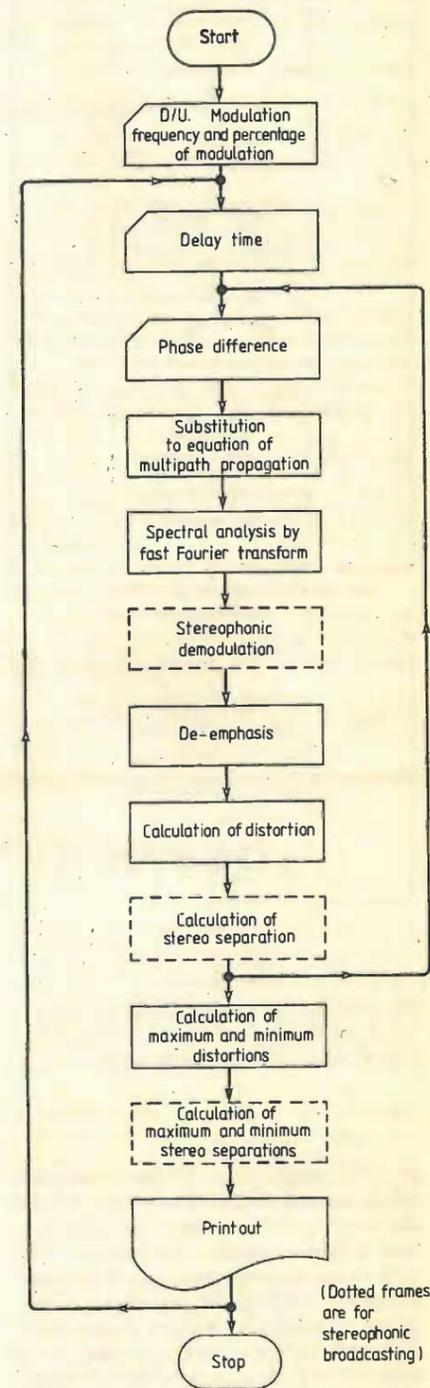


Fig. 1. The procedure used by Mitsuo Ohara (NHK) for computing multipath distortion of monophonic or stereophonic broadcasting.

BOOKS

Frequency Synthesizers, Theory and Design, by Vadim Mannasewitsch. 582pp. hardback. John Wiley, £19.25.

This is the second edition of a book, first published in 1976, which thoroughly describes a vast number of techniques, both practical and theoretical, for the generation of highly stable multiple frequencies using one reference — a subject which has only been seriously studied for around twenty years. It is written at a level suitable for graduate engineers.

Chapter 1 prepares the ground for the succeeding sections, covering in outline a large number of techniques and circuit blocks used in frequency generation, and being followed immediately by a chapter on the problems of spurious modulation and frequencies, and phase noise in practical synthesizers. Two 'practical' sections provide advice on screening against electric and magnetic fields and on fault-finding, and the three core chapters are concerned with analogue and digital phase-locked

loops and the basic circuits (mixers, amplifiers, dividers, etc.) needed for synthesizer operation. A further two chapters illustrate the techniques described earlier by reference to commercial synthesizers and frequency-reference sources. Important additions for the second edition are descriptions of direct digital synthesis and fractional-N, phase-locked loops.

Mannasewitsch has produced a clearly written treatise on this complex subject, which should be well suited to the needs of a working engineer who needs to acquaint himself quickly with the large number of techniques now in use. It is suggested by the author that the book would serve as a text for a course on the subject.

Handbook for Radio Engineering Managers by J. F. Ross. 947pp., hardback. Butterworth, £35.00

The role of a manager in technical and economic planning, safety engineering, environmental consideration and the operation and mainten-

ance of large and small radio stations is well covered, in all its aspects, in this enormous book. It is organized in six sections, on management and organization, engineering economy, safety practice, fires in radio installations, environmental aspects and specifications and contracts.

While management theory takes up a good deal of the book it is, in the main, a practical text, clearly the fruit of much experience. It is extremely comprehensive, treating not only the larger considerations of economics and planning, but minutiae such as precautions against the depredations of termites. Many photographs and drawings illustrate the text and it is pleasing to see a chapter on the engineer's obligation to the environment. Of particular interest to the British reader (the author is Australian) is an account of the collapse of the Emley Moor television mast in 1969, complete with photographs.

A very valuable work for anyone involved with planning, installing or running a radio station or network, whatever its size.

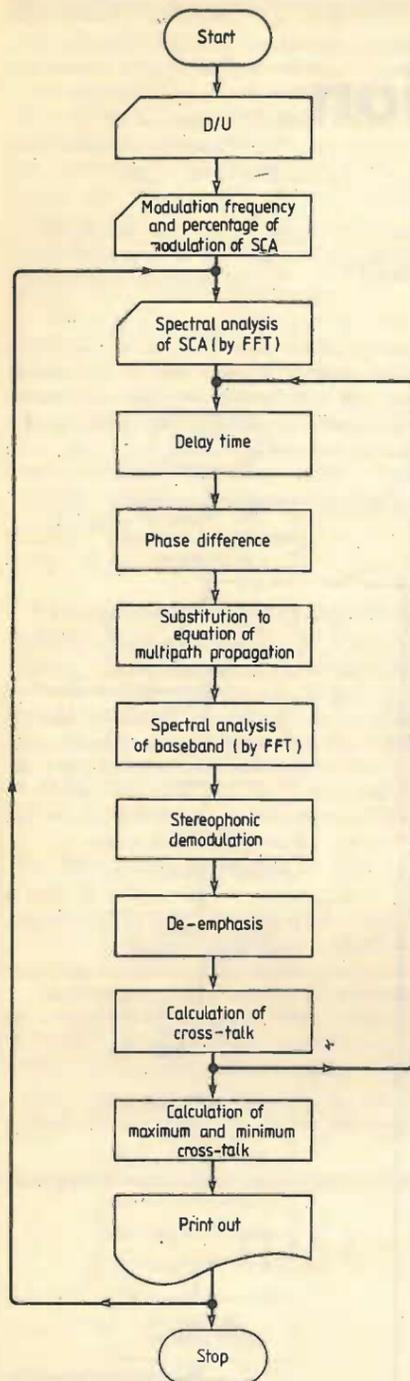


Fig. 2. Procedure for computing crosstalk into a stereo programme channel from 67-kHz (SCA) sub-carrier transmission.

microwave links can suffer from multipath effects causing increased error rate, intense short-duration error bursts or unacceptable adjacent channel interference. The IEE E8 professional group (Radio Communications Systems) are planning a *Colloquium on Multipath Problems* in May 1981. Although current thinking tends, for a variety of reasons, to favour digital systems it has to be recognised that there are circumstances where the gradual fall-off in performance of analogue systems is preferable to the 'go/no-go' characteristics of digital.

NHK multipath study

The NHK work on distortion and crosstalk caused by multipath propagation in v.h.f./f.m sound broadcasting constituted the first computer-assisted theoretical analysis of the relationship between multipath distortion and the relevant parameters. It provided a clearer picture of the characteristics of multipath distortion for both mono and stereo transmissions. It also included laboratory tests using a multipath simulator. Subjective listening tests were carried out using the simulator to investigate the relationship between the distortion and the reproduced sound quality under the influence of multipath distortion. It should be appreciated that the Japanese and American pre-emphasis time-constant is 75 microseconds, whereas the European figure is 50 microseconds: this means that multipath distortion effects may be rather different in Europe than elsewhere. Nevertheless too much should not be made of this difference, since with both time-constants the effects of multipath tend to show up intermittently and selectively rather than as continuous distortion. Mitsuo Ohara shows that distortion increases with low percentages of modulation, particularly where there are long delay times on the reflected signals. A few examples of the results of this work are shown in Figs 3-4 and also in (Ref 1).

Crosstalk - 'monkey chatter' from a 67 kHz-subcarrier SCA system is shown to reach peak values for delay times of about 10 microseconds and about 20 microseconds. There is little doubt that a multiplexed SCA channel can result in severe crosstalk to those listening on the main stereo programme channel; this was the experience noted by the BBC when experiments were carried out several years ago. The significance of the NHK work is that this can now be ascribed partly to multipath effects. Similarly it would not be unreasonable to suppose that the type of interference from the experimental programme labelling signals reported by R. Camp in *Wireless World* (Ref 6) could arise either from receiver design or from multipath effects, though no indication of this could be gathered from the BBC comments.

Polarization and multipath

The work carried out jointly by the Institut für Rundfunktechnik and Westdeutscher Rundfunk is particularly important in view of the increasing use being made in the UK of mixed polarization. In the form of "slant" polarization this was initially adopted by the BBC for their v.h.f./f.m local radio stations, and virtually all the ILR stations have used circularly polarized signals (although it is recognized that true circularity is not necessarily maintained throughout the service area). The main motivation for this was the 7 dB or so increase of signal strength when the signals are received on vertically polarized car radio aerials (or on portable receivers with telescopic rod aerials used out of doors in circumstances where there is little depolarization of the

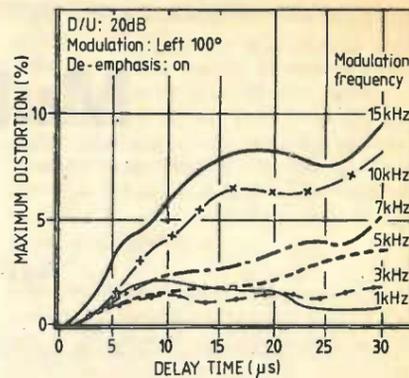


Fig. 3. An example of the relationship between the delay time of an echo and maximum distortion with an aerial direct/unwanted (D/U) ratio of 20 dB for different audio frequencies.

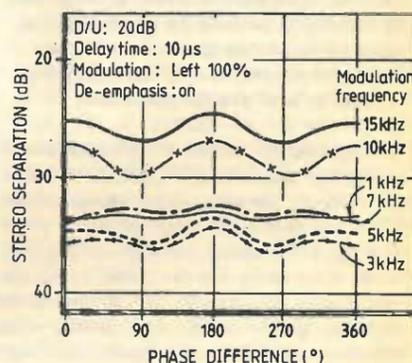


Fig. 4. An example of the relationship between phase difference of an unwanted signal and stereo separation for a D/U ratio of 20dB.

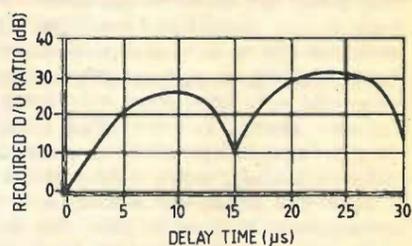


Fig. 5. Relationship between the delay time of an echo and the required D/U ratio if "monkey chatter" crosstalk from an SCA transmission into the main programme is to remain below -55dB (just perceptible). Note that crosstalk into the SCA-programme from the main programme, due to multipath effects, is greater than crosstalk into the main channel.

signals). There have also been some suggestions that cp may provide more homogeneous coverage and possibly some reduction of multipath distortion.

The German work confirms that close to the transmitter cp transmissions result in 4-6 dB more received car-radio aerial voltage, even where the total power of the cp transmissions is unchanged from that of the normally horizontally polarized transmissions. However, it emphasises that vertically polarized v.h.f signals are not

propagated as well as horizontally polarized signals: but in addition it strongly indicates that in normal terrain, there are many more (typically three times as many) long-term 'echoes' with vertically polarized signals than with purely horizontally polarized signals. Unlike most previous studies, the German work was not confined to the sole criterion of received field-strength, but also the quality of reception. The results are a surprisingly vehement rejection of the value of mixed polarization applied to broadcasting.

The tests appear to have been conducted with typical German thoroughness. If one assumes that the methodology contains no hidden flaws, then the results of these trials would seem sufficiently convincing as to suggest that the BBC should reconsider its decision to adopt mixed polarization for its main networks. It is not my purpose, as a member of the 'other' broadcasting organization, to make a partisan point. Indeed if the German work cannot be 'shot down' then there would appear to be every reason why both IBA and the BBC should at least reconsider future policy on local radio, though (as noted later) on lower-power transmissions a more convincing case for cp can be made on behalf of the v.h.f./f.m car radio listeners. For the quality-conscious domestic listener, the key finding in the German experiment is that "it has been seen that the vertical component excites long-range reflections which are so intense as to affect even reception with a horizontally-polarized aerial. It should be noted that this effect is apparent even with a very directional transmitting aerial. If the transmission is omnidirectional the long-range reflections may be even more severe".

The German study also points out that when a vertical component is introduced, there will be problems of compatibility with existing domestic reception. A certain number of new listeners may be gained "at the expense of others who will lose their service". Existing gaps will not be filled to any great extent.

While the German study indicates that a slightly inclined plane of polarization would help listeners with vertically-polarized receiving aerials, it does not even wholeheartedly support such a compromise. But did the German trials 'prove' only what those concerned wished to prove?

IBA engineers commenting in 1975 on the performance of the early ILR circularly polarized transmissions (Ref 7) noted that "the effects of multipath propagation on stereo broadcasts are well-known but often under-estimated. These effects occur far more often than is generally realised. During the off-air loop tests we have found on occasions that the system performance measured at the studio was severely affected by these phenomena. It has been the case that two aerials, on the same building, often very close together, have had very different multipath performance". It was also noted that although multipath distortion is caused by the fundamental mechanisms brought about by the reflected signals, the actual amount of

distortion above this figure is likely to vary greatly between different receivers, depending mainly on the amount of limiting applied to the sub-carrier.

Several years ago EBU Working Party K undertook a study of the work done by individual broadcasters on choice of optimum polarization for v.h.f./f.m sound broadcasting. Their report (Ref 8) summarised by F. Wise (formerly IBA) differentiated between: (a) "services intended primarily for high-quality receiving installations, probably with stereo, with no improvement to reception conditions for portable or car sets envisaged"; and (b) "primarily to reach the largest audience, especially those using portable or car sets. Account to be taken of those installations equipped to receive any existing transmissions". For (a) the report came out firmly in favour of retaining horizontal polarization for existing and new services in all types of terrain where existing services use horizontal polarization. For (b) the corresponding choice was 'mixed' polarization for 'flat or rolling terrain', but 'horizontal' for 'rugged' terrain. The report noted that reflections from the side of the direct signal path where the reflecting object may be a man-made structure, trees, hills or mountains will generally be of significantly greater magnitude for vertically-polarized transmissions, and that such transmissions are more likely to be affected by multipath. The evidence for increased reflections from behind the receiving point was then considered less convincing and the EBU Panel considered polarization unimportant, though noting that in Germany some evidence existed that buildings tend to reflect vertically-polarized Band II signals more than those which are horizontally polarized". The decision to convert BBC network transmissions to mixed polarization would appear to run contrary to the 1976 EBU report.

To conclude, it is necessary to stress that these comments are not intended as criticism of the BBC for playing down the multipath issue or even for their decision to add a vertical component to their network transmissions. Rather it is a plea that, as listeners or as broadcasters, we should be more aware of the effects multipath radio propagation and polarization have on the transmission of high-quality analogue or high-speed digital signals. Only if we recognise the problem are we likely to overcome the worst effects, or at least minimise them. We are still all in the learning stage, but it is important for quality-conscious listeners to discover whether the results of the German tests can be accepted as correct.

References

1. Pat Hawker, "How serious is multipath distortion?" *Wireless World*, April 1980, pp 46-48.
2. Mitsuo Ohara, "Distortion and crosstalk caused by multipath propagation in frequency-modulation sound broadcasting", *IEEE Transactions on Broadcasting*, Vol BC-26, No 3, September 1980, pp 70-81.
3. T. Bossert and A. Lau, W. Blobel and D. Hoff, "Comparison between horizontal and circular polarization for v.h.f./f.m reception in the home and in motor vehicles" *EBU Review - Technical Part*, No 182, August 1980, pp 175-187.
4. P. E. Lonsdale, Letter to *Electronics & Power*, October 1980, p 795.
5. P. James (Ed), "Microwave Radio Digital Links", *The Post Office Research Review* 1979, pp 42-60.
6. R. Camp, Letter to *Wireless World*, with comments by D. P. Leggatt, October 1980, p49.
7. D. S. Chambers and J. R. Edwards, "The specification and performance of ILR v.h.f. transmitting systems". IBA internal report: SD&C No R3/75, pp8-10.
8. F. Wise, "Choice of polarization for new Band II services" *EBU Review - Technical Part*, No 155, February 1976, pp 21-24.

Literature received

A leaflet on the Japanese Izumi range of motor-driven timers, which can switch up to 7A, is available from Appliance Components Ltd, Cordwallis Street, Maidenhead, Berks. SL6 78Q. WW407

Analog Devices has produced a brochure to explain specifications and applications of a-to-d and d-to-a converters, sample-and-hold amplifiers and v-to-f converters. It can be obtained from AD at Central Avenue, East Molesey, Surrey KT8 0SN. WW408

The FCC 180 series of D-subminiature connectors is made by Alpha for use with flat cables. A copy of their leaflet can be had from Alpha Wire, Ltd, Alpha House, Central Way, North Feltham Trading Estate, Feltham, Middx. WW409

Engineering Recommendation G22/1, published by the Electricity Council, is concerned with the use of devices which use the mains wiring to conduct signals. A copy can be obtained from the Distribution Engineering Branch, the Electricity Council, 30 Millbank, London SW1P 4RD at a cost of £1.


Prolog is a portable, multi-channel data acquisition and replay system, with dual microprocessor control over all operational functions. It is described by Microdata, the manufacturers, in a colour brochure, which can be obtained from the company at Monitor House, Station Road, Radlett, Herts. WD7 8JX. WW410

Verospeed's new catalogue is now available, containing 2500 items of hardware, components and instruments. The company will supply one off orders. Copies of the catalogue are available from Verospeed Ltd, Stansted Road, Boyatt Wood, Eastleigh, Hants. SO5 4ZY. WW411

The IEC have issued an international standard to achieve compatibility in the sub-systems and combination of sub-systems used in satellite earth receiving stations. The publication sets conditions for the measurement of return loss, input and output levels, amplitude and frequency characteristics, static a.g.c. characteristics, dynamic a.g.c. characteristics, and the group-delay/frequency characteristic. International Electrotechnical Commission, 1 Rue de Varembe, 1211 Geneva 20 Switzerland.

Amplitude sensing and control

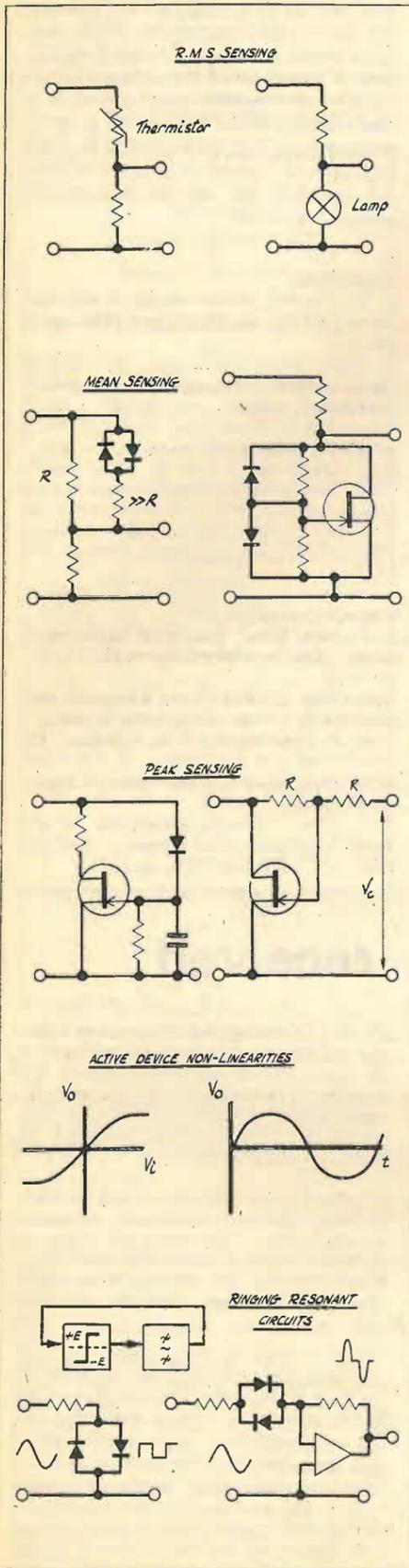by Peter Williams, Ph.D. Paisley College of Technology



There are two reasons for controlling the amplitude of a sinusoidal generator. The obvious one is where that amplitude affects the behaviour of some associated circuit or where its value is involved in consequent calculations. Less obviously any increase in amplitude changes the waveform because the output traverses more of the non-linear range of the active devices. The harmonics resulting are returned to the input where intermodulation due to the non-linearities produces new components at the fundamental frequency. These are equivalent to a phase-shift in the fundamental and have the same effect in shifting the frequency of oscillation as would any other phase shift. The amplitude control mechanism is essentially a negative feedback system in which some property of the output amplitude is sensed, used to modify the feedback and hence to set the amplitude to a desired level. The first two networks contain elements whose resistance is temperature- and hence dissipation-sensitive. Their time constant is made long compared with the oscillation frequency. Amplitude then settles to a value at which the heating effect (r.m.s. dependent) brings the element resistance to a level at which the oscillation is self-sustaining.

The r.m.s. methods involve elements that consume power and have of necessity a slow response. When to these factors the relatively high cost and possible temperature dependence are added, alternative solutions become increasingly attractive. The condition for sustained oscillation at constant amplitude is that the loop gain be identically unity. When a non-linear network is included in the feedback loop then the loop gain can exceed the critical value at low amplitude ensuring that oscillation build up. As amplitude increases the signal forces the non-linear elements into regions of their characteristics where the loop gain falls to less than unity. The amplitude stabilizes such that the mean value of the loop gain is at the critical level. Stabilizing action is instantaneous in that there are no time-constants involved other than strays. Disadvantage of the method is that it achieves its effect by deliberately distorting the feedback signal, though the remainder of the circuit may attenuate the harmonics as they pass through the frequency dependent network. The most common technique places a symmetrical pair of diodes (or series connected back-to-back zener diodes) so as to increase the feedback at higher amplitudes. A field-effect transistor having a low dynamic impedance at low voltages and then going into current limit would have the same effect placed in the other limb.



A third method combines some of the advantages of the previous two. It uses only electronic devices, consumes negligible power and can introduce negligible distortion. It has the disadvantage that a deliberate time constant has to be introduced into the sensing action, though this time constant can be varied to suit the oscillation frequency (a property not shared by thermistors or lamps whose thermal time constants must be long compared with the period of the lowest desired oscillation frequency). The output is peak-rectified and the direct voltage is applied to the gate of a field-effect transistor. The on-resistance of the drain-source path is varied and can form part of a potential-divider feedback loop. As shown the positive peaks generate a positive voltage that reverse biases the p-channel f.e.t. The value of r_{on} increases and with it the feedback. Because the f.e.t. characteristic is non-linear it can only be used directly with very small voltage swings - preferably $<V_p/10$ where V_p is the pinch-off voltage. With additional direct feedback across the f.e.t. as shown it is found that the linearity is markedly improved. The resistance across the capacitor is a compromise between speed of response and distortion; increased ripple worsens the second and is caused by attempting to improve the first.

The methods above have the amplitude sensing mechanism in the passive network, the assumption being that the amplifier is perfectly linear. It is equally feasible to incorporate the non-linearities in the forward path i.e. in the amplifier. The disadvantage is that the harmonics are then fully present at the output, the filtering due to the RC network only being effective in reducing the distortion present at the input. In both cases the distortion is minimized by arranging the loop-gain for small signals to be only slightly greater than that required to sustain oscillation. This reduces the non-linear excursions needed to bring the overall gain back to unity and hence reduces the distortion. If the non-linearities are symmetrical about the quiescent point then even harmonics are suppressed.

None of the above examples demand high-Q passive networks as the distortion introduced via the non-linearities or the sensing mechanisms need not be large. These methods are thus acceptable for simple RC oscillators even though the attenuation of harmonics offered by these networks is relatively small. With LC oscillators or certain RC oscillators based on high-Q active filters the constraint is removed. If a high-Q band-pass circuit is driven by a square wave whose fundamental frequency is the filter centre frequency, then the harmonics are so reduced at the output that an almost pure sine-wave results. It is difficult to maintain the drive frequency at the filter centre frequency since each is subject to the usual tolerances. If instead the filter output is passed through a squaring circuit then its input is a square-wave of the appropriate frequency and constant amplitude. Provided the filter gain at the centre-frequency is constant then the constant amplitude square wave ensures an equally stable sinusoidal output. The square wave can be obtained either by a simple diode limiter or with greater accuracy using a comparator with precision clipping. Antiphase feedback with diodes in the forward path of an amplifier are also found.

Amplitude sensing and control

THEORY

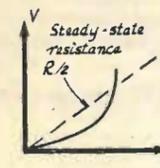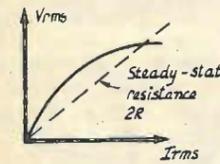

● Networks are used as amplitude-controlled negative feedback. At low amplitudes the steady-state resistance is $>2R$ for the thermistor or $<R/2$ for the lamp. Hence feedback $<1/3$ and for standard Wien type oscillators the amplitude increases. Conversely at high amplitudes the feedback $>1/3$ and amplitude decays, stabilizing at the steady state level where the negative feedback just balances the positive feedback.

● These methods are mostly used where only approximate amplitude limiting is required, though they are instantaneous in their action while using little power. The non-linearity makes analysis difficult.

● The f.e.t. drain current $I_D = k[(V_{GS} - V_p)V_{DS} - V_{DS}^2/2]$ For $V_{DS} \rightarrow 0$, $I_D \rightarrow k(V_{GS} - V_p)V_{DS}$ i.e. conductance

$$\frac{I_D}{V_{DS}} \rightarrow k(V_{GS} - V_p)$$

and is a linear function of the gate-source voltage. Hence varying the gate-source bias varies the conductance and hence the feedback.

For the second circuit

$$V_{GS} = \frac{V_{DS} + V_C}{2}$$

Substituting for V_{GS} in the expression for I_D above

$$I_D = k \left[\left(\frac{V_{DS} + V_C}{2} - V_p \right) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$= k \left[\frac{V_C}{2} - V_p \right] V_{DS}$$

Hence the conductance

$$\frac{I_D}{V_{DS}} = k \left(\frac{V_C}{2} - V_p \right)$$

and is linear for all values of V_{DS} while being a linear function of the new control voltage V_C . This modification allows control of the feedback without introducing any additional distortion into the system.

● For a second-order transfer function $v_o = k_0 + k_1 v_i + k_2 v_i^2$ and a sinusoidal input $v_i \sin \omega t$ the output becomes

$$v_o = k_0 + k_1 v_i \sin \omega t + k_2 v_i^2 \sin^2 \omega t$$

$$= k_0 + k_1 v_i \sin \omega t + \frac{k_2 v_i^2}{2} (1 - \cos 2\omega t)$$

Hence there is a second harmonic term in the output which expressed as a percentage of the fundamental term is proportional to the amplitude of the latter. Similarly higher-order terms result in higher harmonics, the absence of the nth harmonic in the output indicating the absence of the nth order term in the transfer function. Symmetrical transfer functions are preferred in that the even-order harmonic terms are thereby cancelled so that the lowest harmonic is the third harmonic.

EXAMPLES

1. A thermistor has a maximum permitted dissipation of 3mW and sets the output of a Wien bridge oscillator to 1V r.m.s. Choose a suitable value of resistor to complete the bridge.

With 1V r.m.s. total voltage, thermistor has p.d. of $\approx 2/3V$ r.m.s. assuming a high gain amplifier.

$$\therefore I = \frac{3 \cdot 10^{-3}}{2/3} = \frac{9 \cdot 10^{-3}}{2} = 4.5 \text{mA r.m.s.}$$

$$\therefore \text{Series resistor } R = \frac{1/3}{4.5 \cdot 10^{-3}} = \frac{10^3}{13.5} = 74\Omega$$

A suitable resistor might be 100Ω, to keep the thermistor well below its maximum dissipation.

2. At what output voltage does diode conduction commence in the simple diode amplitude control circuit?

Diode voltage at which current flow commences $\approx 0.5V$. But diode voltage is 2/3 of peak output

$$\therefore \text{Output voltage} \approx \frac{3}{2} \times 0.5V$$

$$\therefore \text{R.m.s. output voltage} = \sqrt{2} \cdot \frac{3}{4} = 1.08V \text{ r.m.s.}$$

In practice higher values are required since this level corresponds to only slight conduction, barely modifying the amplitude response and requiring critical resistor adjustments.

3. The peak sensing circuit has $R=1M\Omega$. If the frequency of oscillation is 1kHz, and the ripple across the capacitor is not to exceed 2% peak-peak, choose the corresponding capacitance.

For small ripple, then as in simple rectifier theory linear discharge is a reasonable assumption

$$\therefore \frac{\Delta V}{\Delta t} = \frac{I}{C} \quad \text{and } I \approx \frac{V}{R}$$

$$\therefore \frac{\Delta V}{V} = 0.02 = \frac{t}{CR} = \frac{10^{-3}}{C \cdot 10^6}$$

$$C = \frac{10^{-9}}{0.02} = 50 \text{nF.}$$

4. The ringing resonant circuit uses a filter with $Q=10$ a centre-frequency gain of 20 and an approximate square-wave of 1.2V peak-peak. Determine the % 3rd harmonic at the filter output.

For square-wave of amplitude 1.2V peak-peak, the fundamental and 3rd harmonic amplitudes are

$$\frac{4}{\pi} \times 0.6 \quad \text{and} \quad \frac{4}{3\pi} \times 0.6$$

$$\therefore \text{Fundamental output } 20 \times \frac{4}{\pi} \times 0.6$$

$$T_v = \frac{Hs}{s^2 + \frac{\omega_n^2}{Q}s + \omega_n^2}$$

with $Q=10$ and $\frac{HQ}{\omega_n} = 20$, i.e. $H=20\omega_n$

At $\omega=3\omega_n$

$$T = \frac{2\omega_n \cdot j \cdot 3\omega_n}{-9\omega_n^2 + \frac{3j\omega_n^2}{10} + \omega_n^2}$$

$$= \frac{6j}{-8+0.3j} \approx 0.75j$$

$$\left| \frac{T_{\omega=\omega_n}}{T_{\omega=3\omega_n}} \right| = \frac{20}{0.75} \approx 27$$

$$\therefore \% \text{ 3rd harmonic} = \frac{1}{27} \times \frac{1}{3} \times 100 \approx 1.2\%$$

NEW PRODUCTS

Cassette deck

Parts subject to wear have been kept to a minimum by eliminating belt drives, pulleys, friction clutches and mechanical brakes in a cassette recorder, designed by Revox, called the B710. These parts are avoided by using four direct-drive motors, two Hall commutated magnetic-disc drive motors with inductive tachogenerators for the capstans and two optical tachometer-controlled tape-hub motors. Separate p.l.l. circuits with a common, crystal-based reference are used to control the capstan motor speeds. Damped solenoids engage the Sendust/ferrite heads and lock the cassette in position, and the whole drive mechanism is co-ordinated by a microprocessor to afford maximum protection to the tape. A four-digit display doubles as time-clock/timer readout and tape-position indicator, and has provisions for electronic set, cancel and recall of values for both functions. Bar-type l.e.d. indicators display the peak recording level. This recorder is designed for professional use and switching for equalization, changeover, bias, muting and Dolby is electronic to avoid noise. F.W.O. Bauch Ltd, 49 Theobald St, Borehamwood, Herts.

WW301

Data conversion kit

A data conversion evaluation kit for engineers wishing to assess analogue-to-digital and digital-to-analogue converters for a certain application is offered by Celdis. This kit, designed by Ferranti, costs £28 and comprises two 10-bit a-to-ds, six 8-bit d-to-as, two 8-bit a-to-ds and two 8-bit d-to-a/a-to-ds with all the relevant data in folder form. The latter devices require only a comparator and a gate and clock signal to change their operation from d-to-a to a-to-d. Celdis, 37 Loverock Rd, Reading, Berks RG3 1ED.

WW302

Colour printer

Printouts in seven colours can be produced using the CX80 matrix printer from Integrex. Each of these colours, four of which are produced by mixing the three primary colours of the ribbon, is selected by one of seven control codes. In addition to 96 ASCII and 64 graphics characters in r.o.m. there are 15 characters which can be programmed by the user and facilities for producing elongated and reversed characters. Line and form feed are also programmable. Nee-

de addressing allows graphs, logos, teletext and other graphics to be printed in colour. The CX80 uses tractor feed paper up to 10in wide and can produce 80 columns, 60 dots/in and print rates of 150ch/s max. Normal characters have a 5x7 dot matrix and graphics characters a 6x7 matrix. A Centronics interface is standard, but other interfaces are available for the TRS-80, Apple II and for RS-232C, 20mA and IEEE 488. The price is £895 + v.a.t. Integrex Ltd, Church Gresley, Burton on Trent, Staffs DE11 9PT.

WW303

Fibre-optic interfaces

A pair of small fibre-optic interfaces called SEC10-1 can be used to transmit digital data optically over distances in excess of 1km and at data rates of up to 15Mbit/sec. These modules, one a transmitter and one a receiver, are manufactured by Lightdata and measure 30x20x15mm without the fibre-optic connector. The transmitter module operates on a 5V supply, but the receiver can be operated on 4.5 to 12V, to give a t.t.l., d.t.l. or c.m.o.s.-compatible output. Connection is by four wire-wrap pins in d.i.l. formation on the base of each module. Fibre-optic cable can also be supplied by this company to provide a complete data transmission system with a bit error rate of better than 1 in 10⁹. Lightdata Fibre Optic Communications, 129 Lindsey St, Epping, Essex CM16 6RE.


WW304

Computer interfacing a-to-d

Analogue input data from sensors is processed to provide digital I/O data, for use with any computer or terminal which has a 20mA or RS-232C port, by the μ MAC-4000 measurement and control system from Analog Devices. This system consists of a single 241x330mm board which provides sensor-signal conditioning, analogue multiplexing, analogue-to-digital conversion, digital I/O, serial communications and a p.s.u. Up to four of these boards, each of which accepts 4, 8 or 12 analogue inputs, can be used together to provide 48 channels: expansion boards can be used to allow up to 384 channels. A variety of isolating and non-isolating signal-conditioning modules which plug directly into the p.c.b. are available for voltage and current sensing and for direct connection to thermocouples, r.t.ds (resistance




WW301

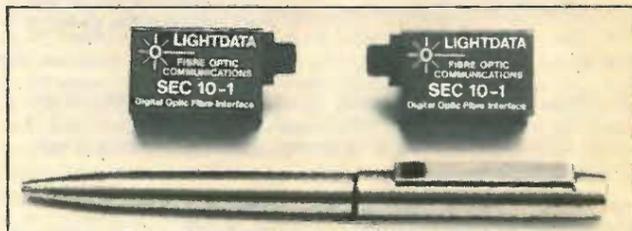

WW304



WW302

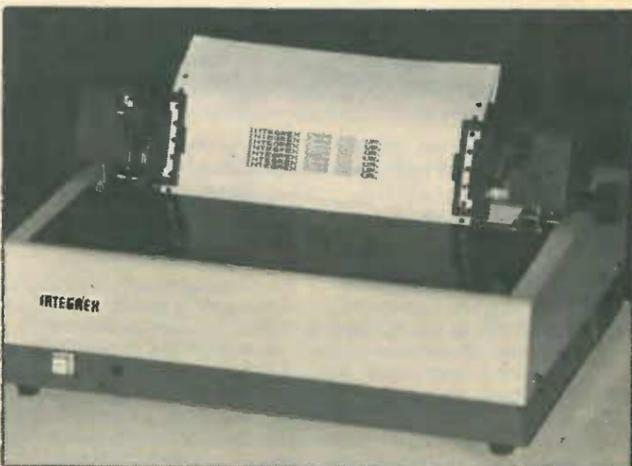

WW303

temperature detectors), strain gauges, etc. For control functions, eight t.t.l.-compatible outputs and eight t.t.l. or optically isolated inputs are provided on each board. Conditioned signals are processed by a low-drift, programmable-gain amplifier and 13-bit, integrating a-to-d converter. An 8085 processor with 6K r.o.m. and 1K r.a.m. are used to scale, linearize, convert into engineering units and store the converted input data. The data updating rate can be either 15 or 30 channels per second. A full duplex u.a.r.t. receives and transmits data at the serial i/o port over distances of up to 10,000ft from the host computer, using 20mA loops (for baud rates under 600). Baud rates of up to 9600 and odd or even parity are switch selectable and the 20mA interface is isolated to 300V d.c. The two ASCII-based protocols are compatible with assembly and high-level languages. Analog Devices Ltd, Central Avenue, East Molesey, Surrey KT8 0SN.

WW305


15in oscilloscope

Various face-plates and phosphors are available for the 15in c.r.t. of the 1530 data oscilloscope from Robel Electronics Ltd. This oscilloscope, with its small spot size and high writing speed, can be used in a number of applications, including the monitoring of waveforms from computer-based analysers, radars, sonars and most processing systems, including a.t.e. Slew rates of 0.5 μ s/cm and one degree phase shift up to 25kHz are quoted for the identical X and Y amplifiers. An internal three-step attenuator, an external continuously variable attenuator, and input impedance selectors are provided for these amplifiers. The Z amplifier, with a rise-time of 30ns, has differential inputs, with voltage ranges from 1 to 10V. A gain/contrast control is also provided. The photo shows the oscilloscope displaying data from an f.f.t. spectrum analyser. Robel Electronics Ltd, Rose Industrial Estate, Cores End Rd, Bourne End, Bucks SL8 5AS.

WW306

Tunable bandpass filters

This series of filters from March Microwave Ltd has octave tuning ranges with direct frequency readout, accurate to $\pm 0.5\%$. A total frequency range from 30 to 3000MHz is covered by 14 models and a choice of either 2 or 5% relative bandwidth between 3dB points is offered. Insertion loss at any tuned centre frequency is 2.5dB maximum for a 2% unit at 30MHz, and 1dB maximum for a 5% unit at 3000MHz. Attenuation is a minimum of 45dB at two bandwidths away from the centre frequency, and the power-handling

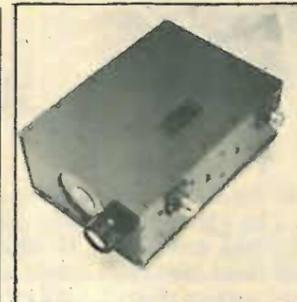

capability ranges from 35 to 60W. A single knob with slow-motion gearing is used for tuning and the readout dial is connected directly to the main shaft to avoid backlash. Special models can be constructed with different tuning ranges or steeper attenuation curves if required. March Microwave Ltd, 112 South St, Braintree, Essex.

WW307

Ceramic resonators



In applications where a timing element is required, cost can often be reduced by using a ceramic resonator instead of a quartz-crystal. Ambit CRM and CFE ceramic resonators are available in the range 200 to 600kHz and drift approximately 0.3% in frequency from -20 to +80°C, with 0.5% drift over 10 years. The CRM type is intended for use as a parallel resonator and the CFE type as a series element for use in bypass and trap applications. Both types are analogous to a quartz-crystal. Prices are 32p each or 19p for 100-up quantities. Ambit International, 200 North Service Rd, Brentwood, Essex CM14 4SG.

WW308


L.e.d. arrays

L.e.d. arrays with five or six elements and rectangular faces are manufactured by Impetron Ltd for use as level meter readouts, front panel indicators or simple graphic displays. Each element, measuring 4.5x2mm, is rated at 50mA peak forward current and 2V maximum forward operating voltage, so the GL series arrays can be driven by t.t.l. outputs without buffering. Three one-colour versions, red, yellow or green, and one version with four green and two red elements are available. Luminous intensity varies between 0.2 and 1.7mcd, depending on the colour selected. These l.e.d.s are also available in single form. IBR Electronics Group Ltd, Foundry Lane, Horsham, W. Sussex RH13 5PX.

WW309

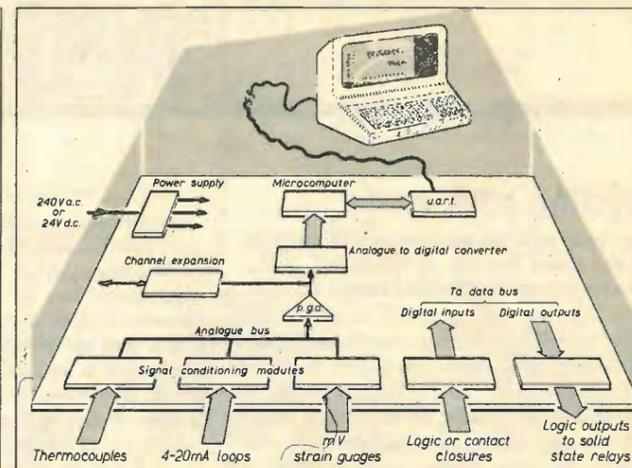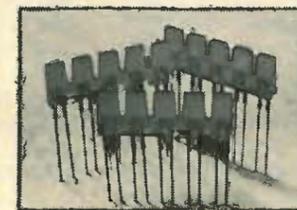

WW305

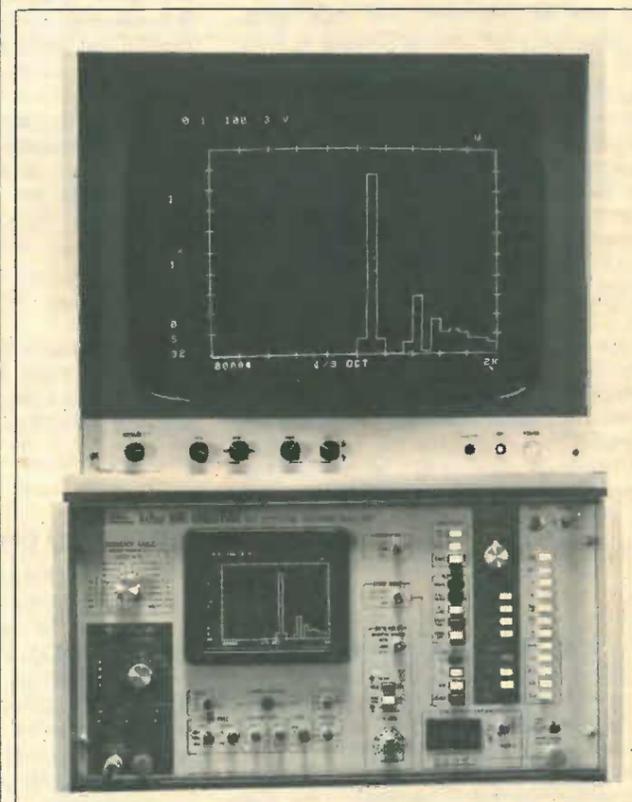

WW306

Zero insertion force sockets

Under conditions where occasional field replacement of i.c.s is unavoidable the Econo Zip from BFI Electronics can be used. These zero-insertion-force i.c. sockets are designed for production rather than test applications and the usual locking lever is replaced by a screw head. Otherwise, the socket is similar to other such devices on the market but the cost per unit has been kept low. Six versions are available to take 16, 24, 28, 40, 48 or 64 pin i.c.s, and the contacts are gold-plated to 100 μ m thickness. BFI Electronics Ltd, 516 Walton Rd, West Molesey, Surrey.

WW310

Magnet machining

Permanent magnets from stock or supplied by the customer can be machined by Magnet Developments Ltd. Their factory, they say, is equipped with slitting, slicing and spark-erosion machines, geared to machine and cut permanent magnets accurately for prototypes or short production runs. The range of magnets stocked by the company include sintered and bonded rare-earth types, sintered and flexible ferrites and cast-alnico types. A design advisory service is also available to customers. Magnet Developments Ltd, Unit 7, Headlands Trading Estate, Swindon, Wilts SN2 6JQ.

WW311

SIDEBANDS

By Mixer

Cycling stille hertz

My heart-rending experience with the bike (Feb. issue) did not go unnoticed. Keith Matthews, of the Wessex District Cyclists' Touring Association, writes to tell me not to be so lily-livered and to have another go (although he is much too polite to put in those words). It's all my fault, it seems — something to do with my not being "bike fit" and not having anything better to ride than a Moulton. Well, I'm quite ready to agree with him about my not being in shape for this sort of thing, but I always thought Moultons were nice little bikes. Maybe that's the trouble: I ought to have one of those spidery contraptions with a saddle like an emaciated razor blade and handlebars bent down to somewhere near the front hub.

I am considerably encouraged, however, by Mr Matthews' assertion that most car drivers will give way to a bikie (I am informed that I cannot be a cyclist until I graduate — maybe by riding the three miles without my feet touching the ground or being provoked to personal abuse) because they realise that if they hit you, you will probably bleed all over the paintwork, which will mean a visit to the car wash, a matter of some inconvenience and expense.

The real point of his letter was not, however, all the above, but was contained in the last sentence. He assumes that I shall take up my cycling career again after its disastrous start, and will want to try the bike computer this all started with in the February issue. When I do, he says, I shall discover that it is unreliable *above 30m.p.h.* (my italics). That, I think, adequately demonstrates the gulf that separates us bikies from real cyclists. Thirty miles an hour! Come now, Mr Matthews, I had in mind a rather more sedate progress than that. They used to say that people would suffocate and die at speeds over 20m.p.h., and for all I know, they could be right. No, as long as I go fast enough to avoid the danger of falling off sideways, I reckon that's enough for anyone. I have no ambition to achieve the yellow jersey to go with the plaster and bandages that would be the certain result of my travelling at 30m.p.h.

Thing-um-a-jig

O frabjous day! Calloo! Callay! The dual snubberless Schottky is with us!

I do beg your pardon — I was so overcome by the arrival of a bit of paper announcing the availability of the d.s.S. that I felt a little outraging of the old momerath was permissible. But it's all right — I'll stop now, or Ed. will vortal the page right here.

Isn't it lovely, though? Anyone whose imagination is untouched by a chance to use a dual snubberless Schottky must be a cold fish indeed, I should think. Not just one, mark you, but a dual package of the frumious little beasts. Now that they're here, and not before time, if you ask me, we've got to find something really beamish to do with them, before some dreadful old square writes in to say they're intended as rectifiers, or some such earthbound fate.

It doesn't need much thought to see that a dual snubberless Schottky is not a device you can tie down to anything too specific. It needs a free rein — to be allowed to breathe and develop in an atmosphere of (Oh, look, is there going to be a lot more of this? Ed.)

You have no idea how frustrating this job can be sometimes. I was only going to say that a d.s.S. could be the very thing for one of those electronic games, maybe Hunting the Snark, each player being armed with a paddle-controlled vortal blade. Every time a v.b. went 'snickers-nack' the d.s.S. would light up, or something.

Well, it's only a thought. You can't give a device a name like dual snubberless Schottky and expect people to use it for anything too serious.

Spoilt by choice

I've been watching the domestic television recording scene for some time now (video, it appears to be called, for some reason) with the kind of feelings I would expect Neanderthal Man to have experienced when confronted by an array of arrow heads down at the stonemonger's. All he wanted was a couple of dozen plain, ordinary arrowheads for the start of the bronto-shooting season and here was this character offering him umpteen models to fit different shaft sizes: all equally well chipped, mind you, but totally incompatible. Manners were fairly elementary then, of course, and for such an act of thoughtlessness, Neanderthal was quite likely to split the stonemonger down the middle and use his skin for trousers, appeals to his better nature notwithstanding. Headstrong, they were, in those times, and direct to the point of rudeness.

Time has had its effect on *Homo sapiens* and I'm not sure that a bit more directness wouldn't be a bad thing, particularly when dealing with all these clever people who keep on inventing video tape recorders and video disc players that do more or less the same job but are just different enough to prevent you using the software from one machine on another. I don't for a moment think that they are deliberately contemptu-

ous of the public's needs and wishes: in fact, I don't even think they give much thought to the public's needs and wishes, apart from the need to 'create' a market and persuade people to buy their wares. If they happen to think that their electronic equivalent to the arrow shaft should be 1/4in in diameter, they'll go ahead and make millions of arrows to fit, regardless of the fact that someone else is making them 3/8in in diameter, and has been for years.

It's no good at all saying that it's up to the buyer to make his mind up: how many people who simply want to record the television Shakespeare canon or transfer *Nationwide* to a more convenient time are in a position to make a difficult technical choice between the different v.c.rs? And how many will be able to decide between the three methods of reading a video disc, or realise that you can't play Philips discs on a JVC player, while all the time considering the claims of several firms to have the best disc library?

Quiet, please! It's breakfast time

When I was a bit younger, I used to have a finely tuned timetable in the morning. Everything was worked out to the nearest couple of microseconds, and a few seconds spent in putting a new blade in the razor, or a serious lapse in concentration resulting in the soap getting itself lost in the bathwater could cause havoc. Many's the time I've been ejected from the house without a second cup of coffee.

I've relaxed a bit, now. For one thing, I don't have to drive my wife to school since she gave up teaching and, for another, I've learned more sense. The move to Sutton has helped, too. I now take my mornings very gently, luxuriating over a leisurely bath, savouring a proper breakfast and invariably having a second cup of coffee.

Even so, taking all this gracious living into account and making due allowance for the need to keep abreast of world affairs, I can see no possibility of television getting a look in at that time in the morning. There are many things I want from life, but television with my crispy bacon and scrambled eggs is not one of them. As far as I am concerned, thanks, but no thanks, particularly if there are to be any of those indecently vivacious commercials for orange juice, or Snappafakes, or whatever. And what of the news itself? Most of it is quite bad enough when printed in a newspaper, but spoken right out loud, just like that, by a television person — well, it's enough to curdle the milk.

WILMSLOW AUDIO

The firm for Speakers

HI-FI DRIVE UNITS



AUDAX HD12.9D25	£8.75
AUDAX HD11P25EBC	£7.50
AUDAX HD20825H4	£14.95
AUDAX HD13D34H	£12.95
AUDAX HD24S45C	£21.95
AUDAX WFR15S	£23.95
CHARTWELL CE2A05	pair £81.25
COLES 4001	£7.65
COLES 3000	£7.65
COLES 3100	£7.95
COLES CE2000 6 1/2"	£14.95
CELESTION HF1300 II	£12.50
CELESTION HF2000	£12.50
DALESFORD D10 tweeter	£8.45
DALESFORD D10 ferrofluid	£6.95
DALESFORD D30/110	£11.25
DALESFORD D50/153	£12.25
DALESFORD D50/200	£12.25
DALESFORD D100/250	£29.95
DALESFORD D300	£35.75
DECCA London Horn	£79.95
ELAC 6NC204 6 1/2"	£7.50
ELAC 8NC298 8"	£6.95
EMI type 350, 13" x 8", 4 ohm	£9.45
EMI 14A/770, 14" x 9", 8 ohm	£19.50
ISOPHON KK8/8	£8.45
ISOPHON KK10/8	£8.45
JORDAN WATTS Module	£24.95
JORDAN WATTS Module Mk II	£28.50
JORDAN WATTS HF kit	£10.50
JORDAN 50mm unit	£33.50
JORDAN crossover	£34 pair
KEF T27	£9.45
KEF B110	£12.25
KEF B200	£13.50
KEF B139	£27.75
KEF DN12	£9.40
KEF DN13	£6.75
LOWTHER PM6	£63.00
LOWTHER PM6 Mk I	£67.75
LOWTHER PM7	£99.00
PEERLESS KO10DT	£10.95
PEERLESS DT10HFC	£10.50
PEERLESS KO40MRF	£13.80
RICHARD ALLAN CG8T	£13.50
RICHARD ALLAN CG12T Super	£29.50
RICHARD ALLAN HP8B	£20.75
RICHARD ALLAN LP8B	£14.50
RICHARD ALLAN HP12B	£33.50
RICHARD ALLAN DT20	£10.75
RICHARD ALLAN DT30	£9.95
SEAS H107	£10.95
SEAS H211 ferrofluid	£10.95
SHACKMAN ES units	£136 pair
SHACKMAN ES units with cabs.	£170 pair

PA GROUP & DISCO UNITS



CELESTION G12/50TC	£19.50
CELESTION G12/80CE	£24.50
CELESTION G12/80TC	£23.75
CELESTION G12/125CE	£42.00
CELESTION G15/100CE	£37.95
CELESTION G15/100TC	£36.50
CELESTION G18/200	£64.75
CELESTION Powercel 12/150	£66.00
CELESTION Powercel 15/250	£66.00
FANE CLASSIC 45 12"	£13.95
FANE CLASSIC 55 12"	£15.50
FANE CLASSIC 80 12"	£19.75
FANE CLASSIC 85 15"	£26.00
FANE CLASSIC 150 15"	£37.95
FANE CLASSIC 125 18"	£43.95
FANE CLASSIC 175 18"	£47.95
FANE GUITAR 80L 12"	£26.25
FANE GUITAR 80B/2 12"	£27.25
FANE DISCO 100 12"	£26.75
FANE PA85 12"	£26.75
FANE BASS 100 15"	£39.00
FANE CRESCENDO 12E 12"	£27.50
FANE CRESCENDO 15E 15"	£24.50
FANE CRESCENDO 18E 18"	£94.75
FANE COLOSSUS 15E 15"	£99.95
FANE COLOSSUS 18E 18"	£107.00
FANE J44	£6.90
FANE J73	£10.90
FANE J104	£15.95
FANE J105	£23.95
GAUSS 3181A 10" 150 watts	£115.00
GAUSS 4281 12" 300 watts	£146.00
GAUSS 4581 15" 300 watts	£162.00
GAUSS 4583A 15" 400 watts	£162.00
GAUSS 4882 18" 400 watts	£220.00
GOODMANS 8PA	£5.05
GOODMANS PP12	£22.50
GOODMANS D112	£25.50
GOODMANS GR12	£24.95
GOODMANS 18P	£48.45
GOODMANS HIFAX 50HX	£21.65
GOODMANS HIFAX 100HX	£24.50
McKENZIE C12100GP	£24.45
McKENZIE C12100TC	£24.45
McKENZIE C12100 bass	£24.45
McKENZIE C12125GP	£39.95
McKENZIE C12125TC	£39.95
McKENZIE GP15	£35.10
McKENZIE TC15	£35.10
McKENZIE C15 bass	£59.60
MOTOROLA PIEZO HORN 3 1/2"	£8.50
MOTOROLA PIEZO HORN 2" x 6"	£12.25
RICHARD ALLAN HD8T	£20.25
RICHARD ALLAN HD10T	£21.75
RICHARD ALLAN HD12T	£29.75
RICHARD ALLAN HD15	£52.75
RICHARD ALLAN HD15P	£52.75
RICHARD ALLAN 15"	£77.00
RICHARD ALLAN 18"	£96.00

WILMSLOW AUDIO



KITS FOR MAGAZINE DESIGNS

Kits include drive units, crossovers, BAF/long fibre wool, etc. for a pair of speakers

Carriage £3.95 unless otherwise stated

Practical Hi Fi & Audio PRO9-TL including felt panels and level controls £152.75 carriage £5

Hi Fi Answers Monitor £46.00

Hi Fi News State of the Art £169.00

Hi Fi News Midline £99.75

Hi Fi News Miniline £49.90

Hi Fi News Tabor with J4 bass units £66.00

Hi Fi News Tabor with H4 bass units £70.00

Hi Fi for Pleasure Compact Monitor £116.00

Hi Fi for Pleasure E.C.M. (including felt panels, foam etc) £77.50 carriage £5

Popular Hi Fi Jordan System 1 £126.00

Popular Hi Fi Mini Monitor £77.00

Popular Hi Fi Round Sound including complete cabinet kit £74.00

Practical Hi Fi and Audio BSC3 £65.00

Practical Hi Fi and Audio Monitor £180.00

Practical Hi Fi and Audio Triangle £120.00

Practical Hi Fi and Audio DBS4 £85.00 carriage £5

Everyday Electronics EE20 £29.50

Everyday Electronics EE70 £150.00 carriage £5

Wireless World T.L. KEF £125.00

Wireless World T.L. RADFORD £180.00

Smart badges FREE with all the above kits (to give that professional touch to your DIY speakers). Reprints/construction details of the above designs 10p each.

WILMSLOW AUDIO BA1 sub bass amplifier/crossover kit £37.95 plus £1 carriage

ALL PRICES INCLUDE VAT @ 15% and are correct at 1/2/81

SEND 50p FOR 56-PAGE CATALOGUE 'CHOOSING A SPEAKER' (or price list only free of charge) Export Catalogue £1 or \$3 U.S.

Tel. 0625 529599 for speaker drive units, kits, PA equipment, mail order enquiries, and all export enquiries.

Tel: 0625 526213 for Hi-Fi equipment and complete speaker enquiries.

Lightning service on telephoned credit card orders!

SWIFT
OF WILMSLOW
The firm for Hi-Fi
5, Swan Street
Wilmslow, Cheshire

EVERYTHING IN STOCK FOR THE SPEAKER CONSTRUCTOR!

BAF, LONG FIBRE WOOL, FOAM, CROSSOVERS, FELT PANELS, COMPONENTS, SPEAKER STANDS, BRACKETS, ETC. LARGE SELECTION OF GRILLE FABRICS.

(Send 22p in stamps for grille fabric samples)

SPEAKER KITS



PRICES PER PAIR CARRIAGE £3.95 UNLESS OTHERWISE STATED

COLES NIMBUS KIT (mounted on baffle)	£69.00
DALESFORD SYSTEM 1	£54.00
DALESFORD SYSTEM 2	£57.00
DALESFORD SYSTEM 3	£104.00
DALESFORD SYSTEM 4	£110.00
DALESFORD SYSTEM 5	£142.00
DALESFORD SYSTEM 6	£95.00
DALESFORD 'D' KIT (including cabinet)	£79.95
KEF Reference 104aB kit	£133.00 plus £5 carriage
KEF Cantata kit	£199.00 plus £5 carriage
LS3 Micro Monitor kit	£76.00
LOWTHER PM6 kit	£132.75
LOWTHER PM6 Mk 1 kit	£139.95
LOWTHER PM7 kit	£189.00
RADFORD Studio 90	£161.00
RADFORD Studio 180	£243.00
RADFORD Studio 270	£309.00
RADFORD Studio 360	£450.00
RICHARD ALLAN Tango Twin	£55.50
RICHARD ALLAN Maramba	£77.50
RICHARD ALLAN Charisma	£111.00
RICHARD ALLAN Super Triple	£102.50
RICHARD ALLAN Super Seriband II	£159.95
RICHARD ALLAN RA8 kit	£62.75
RICHARD ALLAN RA82 kit	£96.75
RICHARD ALLAN RA82L kit	£106.00
SEAS 223	£42.50
SEAS 253	£67.00
SEAS 403	£79.95
SEAS 603	£134.95
WHARFEDALE DENTON XP2 kit	£31.45
WHARFEDALE SHELTON XP2 kit	£40.40
WHARFEDALE LINTON XP2 kit	£56.20
WHARFEDALE L80 kit	£52.50
WHARFEDALE L80 kit	£75.00
WHARFEDALE L100 kit	£67.00
WHARFEDALE E50 kit	£129.00
WHARFEDALE E70 kit	£160.00
WHARFEDALE E90 kit	£249.50

CARRIAGE & INSURANCE
Tweeters/Crossovers 70p each
Speakers
4" to 6 1/2" 90p each
8" to 10" £1.10 each
12", 13" x 8", 14" x 9" £2.00 each
15" £3.00 each
18" £5.00 each
Speaker Kits £3.95 pair
Mag. Design Kits £3.95 pair unless otherwise stated

WILMSLOW AUDIO
The firm for Speakers

35/39 Church Street
Wilmslow, Cheshire

DOMESTIC PROBLEMS?

Look in our magazine - maybe we have the quick answer.

Every month we present designs that are useful both around the home and for leisure - including motoring, music, photography and games.

THIS MONTH:



Digital Ruler
INCHES

DIGITAL RULE

Uses ultrasonic pulses to determine distance. Handy for taking approximate measurements between awkward points.

ELECTRONIC SWITCH FOR MOTORS

A modern triac design to eliminate the troublesome centrifugal starting switch. Suitable for single phase induction motors, reversible or non-reversible.

DON'T LET YOUR GOODS GO BAD...

A simple design to alert you to a mains power failure and avert the possibility of ruined food.

INTERCOM

Mains powered two-station system. Can be used as a doorbell with speech communication to identify unknown visitors.

Everyday ELECTRONICS

APRIL ISSUE OUT NOW 60p

RUBBER DUCK CALLING LOGI BAIRD- "SAY MAC, WHERE DO I GET R.F. TRANSISTORS?"

ANGLIA OF COURSE!! THEY'VE ALWAYS GOT WHAT I WANT, MOTOROLA MRF AND JAPANESE REPLACEMENT TYPES.

BURDETT ROAD, WISBECH, CAMBS. PE13 2PS.
TEL. 0945 63281 TELEX 32630

WW - 058 FOR FURTHER DETAILS

PURE GOLD!

Top-quality, low-profile, gold-plated contacts,

IC SOCKETS	
8 pin	8p
14 pin	14p
16 pin	16p
18 pin	18p
20 pin	20p
22 pin	22p
24 pin	24p
28 pin	28p
40 pin	40p

Unbeatable value!

Minimum Order £10. Add £1 P.&P.
500 + and one type less 5%. 1,000 + any mix less 10%.
Special offer 10 x 8 pin, 20 x 14 pin, 20 x 16 pin. 5 x all others £11.50

ORION

Orion Scientific Products Ltd., 10 Wardour St., London, W.1

10. 15. 20

WORLD RANGER TRIBANDER TRIBANDER

'par excellence'

AERIAL £135 Plus VAT	BALUN £12.50 Plus VAT
----------------------	-----------------------

BARNET METAL & CAR CO. LTD.,
Tewin Road, Welwyn Garden City
Herts. AL7 1AG
Telephone: Welwyn Garden 24327
Telex: 38125 Cable: BARMECO

TRANSCENDENT 2000 SINGLE BOARD SYNTHESIZER

Designed by consultant Tim Orr (formerly synthesizer designer for EMS Ltd.) and featured as a construction article in ETI, this live performance synthesizer is a 3 octave instrument transposable 2 octaves up or down giving sweep control, a noise generator and an ADSR envelope shaper. There is also a slow oscillator, a new pitch detector, ADSR repeat, sample and hold, and special circuitry with precision components to ensure tuning stability amongst its many features.

The kit includes fully finished metalwork, fully assembled solid teak cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or 1/2% metal film), and it really is complete - right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit - you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibreglass PCB printed with component locations. All the controls mount directly on the main board, all connections to the board are made with connector plugs and construction is so simple it can be built in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesizer comparable in performance and quality with ready-built units selling for many times the price.

Comprehensive handbook supplied with all complete kits! This fully describes construction and tells you how to set up your synthesizer with nothing more elaborate than a multi-meter and a pair of ears!



Cabinet size 24.6" x 15.7" x 4.8" (rear) 3.4" (front)

COMPLETE KIT ONLY
£168.50 + VAT!

NEW! TRANSCENDENT POLYSYNTH

EXPANDABLE POLYPHONIC SYNTHESIZER AS FEATURED IN ELECTRONICS TODAY INTERNATIONAL

By brilliant design work and the use of high technology components the Polysynth brings to the reach of the home constructor a machine whose versatility and range of sounds is matched only by ready-built equipment costing thousands of pounds. Designed by synthesizer expert Tim Orr and published in Electronics Today International, this latest addition to the famous Transcendent family is a 4 octave transposable over 7 1/2 octaves polyphonic synthesizer with internally up to 4 voices making it possible to play simultaneously up to 4 notes, whereas conventional synthesizers handle only one at a time.

The basic instrument is supplied with 1 voice and up to 3 more may be plugged in. A further 4 voices may be added by connecting to an expander unit, the metalwork and woodwork of which is designed for side-by-side matching with the main instrument. Each voice is a complete synthesizer in itself, with 2 VCOS, 2 ADSRS, a VCA and a VCF (requiring only control voltages and power supply, the voice boards are also very suitable for modular systems). One of these voices is automatically allocated to a key as it is operated. There are separate tuning controls for each VCO of each voice. All other controls are common to all the voices for ease of control and to ensure consistency between the voices.




Cabinet size 31.1" x 19.6" x 7.6" (rear) 3.4" (front)

Although using very advanced electronics the kit is mechanically very simple with minimal wiring, most of which is with ribbon cable connectors. All controls are PCB mounted and the voice boards fit with PCB mounted plugs and sockets. The kit includes fully finished metalwork, solid teak cabinet, professional quality components (resistors 2% metal oxide or metal film of 0.5% and 0.1%), nuts, bolts, etc.

COMPLETE KIT ONLY £320 + VAT (Single Voice)
Extra voices, £52 + VAT or £48 + VAT if ordered with kit.
EXPANDER, COMPLETE KIT £295 + VAT

TRANSCENDENT DPX MULTI-VOICE SYNTHESIZER

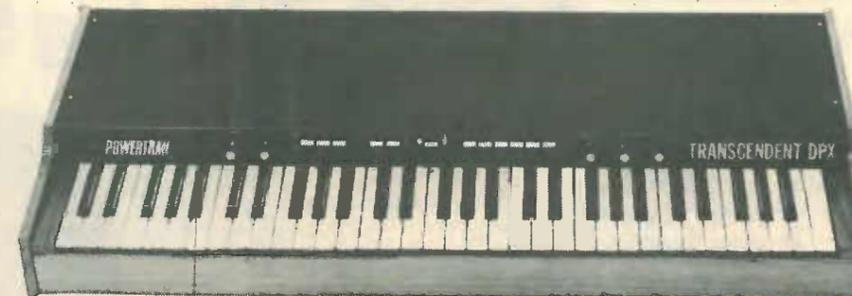Another superb design by synthesizer expert Tim Orr published in Electronics Today International



Cabinet size 36.3" x 15.0" x 5.0" (rear) 3.3" (front)

COMPLETE KIT ONLY
£299 + VAT!

The Transcendent DPX is a really versatile 5 octave keyboard instrument. These are two audio outputs which can be used simultaneously. On the first there is a beautiful harpsichord or reed sound—fully polyphonic, i.e. you can play chords with as many notes as you like. On the second output there is a wide range of the keyboard or whole range of the keyboard or should you prefer - strings on the top of the keyboard and brass as the lower end (the keyboard is electronically split after the first two octaves) or vice-versa or even a combination of strings and brass sounds simultaneously. And on all voices you can switch in circuitry to make the keyboard touch sensitive! The harder you press down a key the louder it sounds - just like an acoustic piano. The digitally controlled multiplexed system makes practical touch sensitivity with the complex dynamics law necessary for a high degree of realism. There is a master volume and tone control, a separate control for the brass sounds and also a vibrato circuit with variable depth control together with a variable delay control so that the vibrato comes in only after waiting a short time after the note is struck for even more realistic string sounds.

To add interest to the sounds and make them more natural there is a chorus/ensemble unit which is a complex phasing system using CCD (charge coupled device) analogue delay lines. The overall effect of this is similar to that of several acoustic instruments playing the same piece of music. The ensemble circuitry can be switched in with either strong or mild effects. As the system is based on digital circuitry digital data can be easily taken to and from a computer (for storing and playing back accompaniments with or without pitch or key change, computer composing, etc., etc.).

Although the DPX is an advanced design using a very large amount of circuitry, much of it very sophisticated, the kit is mechanically extremely simple with excellent access to all the circuit boards which interconnect with multiway connectors, just four of which are removed to separate the keyboard circuitry and the panel circuitry from the main circuitry in the cabinet. The kit includes fully finished metalwork, solid teak cabinet, professional quality components (all resistors 2% metal oxide), nuts, bolts, etc. even a 13A plug!

POWERTRAN

MANY MORE KITS AND ORDERING INFORMATION ON PAGE 93

All projects on this page can be purchased as separate packs, e.g. PCBs, components sets, hardware sets, etc. See our free catalogue for full details and prices.



All stations GO!

Soldering equipment designed by specialists for professionals.

ADCOLA 101 Soldering Unit

FEATURES

- no moving parts
- no magnetic effect
- no tip voltage
- no mains interference
- no real maintenance costs (bit/tip changes only)
- variable lockable temperature 120°C — 420°C
- total 50 watt electronic control (±2%)
- simple plug-in bits/tips
- electrical safety approved 240V 24V
- easy tool interchangeability from one Unit to another

~or complete 2001 Soldering Station

Soldering tool and control unit as Unit 101 but with the additional features

- filtered two speed fume extraction
- built in bench lighting
- solder reel dispenser
- clear bench area
- Adiron® long life bits/tips the same range as that for Unit 101




ADCOLA ADIRON® long life bits/tips simple plug-in type suitable for both Unit 101 and Unit 2001



ADCOLA PRODUCTS LIMITED Gauden Road London SW4 6LH Telephone Sales (01) 622 0291 Telex 21851 Adcola G

For full details contact

WW - 051 FOR FURTHER DETAILS

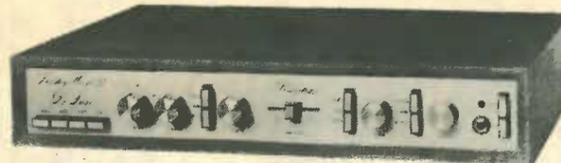

DE LUXE EASY TO BUILD LINSLEY HOOD 75W STEREO AMPLIFIER £85.00 + VAT


This easy to build version of our world-wide acclaimed 75W amplifier kit based upon circuit boards interconnected with gold plated contacts resulting in minimal wiring and construction delightfully straightforward. The design was published in Hi-Fi News and Record Review and features include rumble filter, variable scratch filter, versatile tone controls and tape monitoring while distortion is less than 0.01%.



T20 + 20 20W STEREO AMPLIFIER £33.10 + VAT

This kit, based upon a design published in Practical Wireless, uses a single printed circuit board and offers at very low cost, ease of construction and all the normal facilities found on quality amplifiers. A 30 watt version of this kit (T30 + 30) is also available for £38.40 + VAT. MATCHING TUNERS — See our FREE CATALOGUE!

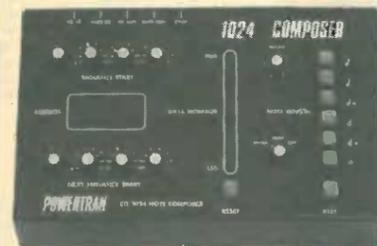Above 2 kits are supplied with fully finished metalwork, ready assembled high quality teak veneer cabinet, cable, nuts, bolts, etc. and full instructions — in fact everything!



1024 COMPOSER READ ALL ABOUT IT! COMPLETE KIT ONLY £89.50 + VAT! IN ELECTRONICS TODAY INTERNATIONAL

Programmed from a synthesizer, our latest design to be featured in ELECTRONICS TODAY INTERNATIONAL the 1024 COMPOSER controls the synth. with a sequence of up to 1024 notes or a large number of shorter sequences e.g. 64 of 16 notes all with programmable note length. In addition a rest or series of rests can be entered. It is mains powered but an automatically trickle charged Nickel-Cadmium battery supplying the memory, preserves the program after switch off. The kit includes fully finished metalwork, fibreglass PCB, controls, wire, etc. — Complete down to the last nut and bolt!

BLACK HOLE CHORALIZER



The BLACK HOLE designed by Tim Orr, is a powerful new musical effects device for processing both natural and electronic instruments, offering genuine VIBRATO (pitch modulation) and a CHORUS mode which gives a "spacey" feel to the sound achieved by delaying the input signal and mixing it back with the original. Notches (HOLES), introduced in the frequency response, move up and down as the time delay is modulated by the chorus sweep generator. An optional double chorus mode allows exciting antiphase effect to be added. The device is floor standing with foot switch controls, LED effect selection indicators, has variable sensitivity, has high signal/noise ratio obtained by an audio compander and is mains powered — no batteries to change! Like all our kits everything is provided including a highly superior, rugged steel, beautifully finished enclosure.

COMPLETE KIT ONLY £49.80 + VAT! (single delay line-system)
De Luxe version (dual delay line system) also available for £59.80 + VAT

Cabinet size 10.0" x 8.5" x 2.5" (rear) 1.8" (front)

CHROMATHEQUE 5000 5 CHANNEL LIGHTING EFFECTS SYSTEM

This versatile system featured as a constructional article in ELECTRONICS TODAY INTERNATIONAL has 5 frequency channels with individual level controls on each channel. Control of the lights is comprehensive to say the least. You can run the unit as a straightforward sound-to-light or have it strobe all the lights at a speed dependent upon music level or front panel control or use the internal digital circuitry which produces some superb random and sequencing effects. Each channel handles up to 500W and as the kit is a single board design wiring is minimal and construction very straightforward. Kit includes fully finished metalwork, fibreglass PCB controls, wire, etc. — Complete right down to the last nut and bolt!



MPA 200 100 WATT (rms into 8Ω) MIXER / AMPLIFIER Panel size 19.0" x 3.5", Depth 7.3"

Featured as a constructional article in ETI, the MPA 200 is an exceptionally low priced — but professionally finished — general purpose high power amplifier. It features adaptable input mixer which accepts a wider range of sources such as microphone, guitar, etc. There are wide range tone controls and a master volume control. Mechanically the MPA 200 is simplicity itself with minimal wiring needed making construction very straightforward. The kit includes fully finished metalwork, fibreglass PCBs, controls, wire, etc. — complete down to the last nut and bolt.

MATCHES THE CHROMATHEQUE 5000 PERFECTLY! COMPLETE KIT ONLY £49.50 + VAT!

All kits also available as separate packs (e.g. PCB, component sets, hardware sets, etc.). Prices in our FREE CATALOGUE.



SP2-200 2-CHANNEL 100W AMPLIFIER — NEW KIT! Panel size 19.0" x 3.5", Depth 7.3"

The power amplifier section of the MPA 200 has proved not only very economical but very rugged and reliable too. This new design uses two of these amplifier sections powered by separate power supplies fed from a common toroidal transformer. Input sensitivity is 775mV. Power output is 100 rms into 8 ohm from both channels simultaneously. The kit includes fully finished metalwork, fibreglass PCBs, controls, wire, etc. — complete down to the last nut and bolt!

COMPLETE KIT ONLY £64.90 + VAT!

Panel size 19.0" x 3.5", Depth 7.3"



MANY MORE KITS ON NEXT PAGE!

OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!

POWERTRAN ELECTRONICS
PORTWAY INDUSTRIAL ESTATE ANDOVER
ANDOVER HANTS SP10 3NN (0264) 64455

Value Added Tax not included in prices

PRICE STABILITY: Order with confidence! Irrespective of any price changes we will honour all prices in this advertisement until May 31st, 1981, if this month's advertisement is mentioned with your order. Errors and VAT rate change excluded.
EXPORT ORDERS: No VAT. Postage charged at actual cost plus £1 handling and documentation.
U.K. ORDERS: Subject to 15% surcharge for VAT. NO charge is made for carriage. Or current rate if changed.
SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.
SALES COUNTER: If you prefer to collect your computer from the factory, Call at Sales Counter. Open 9 a.m.-12 noon, 1-4.30 p.m. Monday-Thursday.



SIMPLY AHEAD
and staying there

The range grows bigger... better...

New Profile Amplifiers - Two New Series



HY120



HY60

MOSFET

CHOOSE AN I.L.P. MOSFET POWER AMP when it is advantageous to have a faster slew rate, lower distortion at higher frequencies, enhanced thermal stability, the ability to work with complex loads without difficulty and complete absence of cross-over distortion. I.L.P.'s exclusive encapsulation technique within fully adequate heatsinks has been taken a stage further with specially developed computer-verified 'New Profile' extrusions. These ensure optimum operating efficiency from our new MOSFETS, and are easier to mount. Connection is via five pins on the underside. **I.L.P. MOSFETS ARE IDENTICAL IN PERFORMANCE TO THE COSTLIEST AMPLIFIERS IN THIS EXCITING NEW CATEGORY BUT ARE ONLY A FRACTION OF PRICES CHARGED ELSEWHERE.**


Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
MOS120	60W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£25.88 + £3.88
MOS200	120W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£33.46 + £5.02

(Standard O-P Transistors)


BIPOLAR

CHOOSE AN I.L.P. BIPOLAR POWER AMP where power and price are first consideration while maintaining optimum performance with hi-fi quality and wide choice of models. From domestic hi-fi to disco and P.A., for instrument amplification, there is an I.L.P. Bipolar to fill the bill, and as with our new Mosfets, we have encapsulated Bipolars within our New Profile extrusions with their computer-verified thermal efficiency and improved mounting shoulders. Connections are simple, via five pins on the underside and with our newest pre-amps and power supply units, it becomes easier than ever to have a system layout housed the way you want it.


Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
HY30	15W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£7.29 + £1.09
HY60	30W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£8.33 + £1.25
HY120	60W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£17.48 + £2.62
HY200	120W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£21.21 + £3.18
HY400	240W into 4Ω	0.01%	15V/μs	5μs	100dB	£31.83 + £4.77

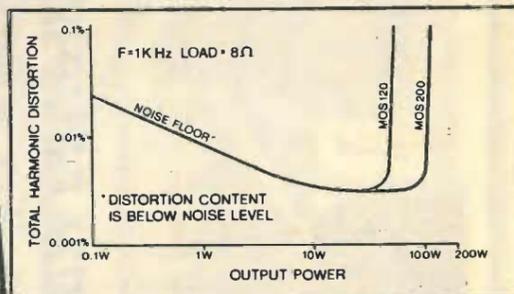

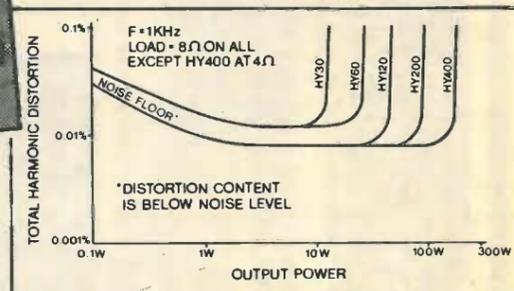Load impedance both models 4Ω - ∞ Input impedance both models 100KΩ
Input sensitivity both models 500mV Frequency response both models 15Hz-100KHz - 3dB



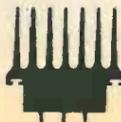Load impedance all models 4Ω - ∞ Input impedance all models 100KΩ
Input sensitivity all models 500mV Frequency response all models 15Hz-50KHz - 3dB



THE NEW PROFILE EXTRUSIONS

The introduction of standard heatsink extrusion for all I.L.P. power amplifiers achieves many advantages. Research shows they provide optimum thermal dissipation and stability. Slotted shoulders allow easy mounting; standardisation enables us to keep our prices competitive. Surfaces are matt black, anodised for higher thermal conductivity. Extrusions vary in size according to module number.



NEW PRE-AMPS

HY6 (mono) and HY66 (stereo) are new to I.L.P.'s range of advanced audio modules. Their improved characteristics and styling ensure their being compatible with all I.L.P. power-amps both MOSFET and BIPOLAR, giving you chance to get the best possible reproduction from your equipment. HY6 and HY66 pre-amps are protected against short circuit and wrong polarity. Full assembly instructions are provided. Mounting boards are available as below.

Sizes - HY6 - 45x20x40 mm. HY66 - 90x20x40 mm. Active Tone Control circuits provide ±12dB cut and boost. Inputs Sensitivity - Mag. PU. - 3mV; Mic - selectable 1-12mV; All others 100mV. Tape O/P - 100mV; Main O/P - 500mV; Frequency response - D.C. to 100KHz - 3dB.

HY6 mono £6.44 + 97p VAT Connectors included
HY66 stereo £12.19 + £1.83 VAT Connectors included

B6 Mounting Board for one HY6 78p + 12p VAT
B66 Mounting Board for one HY66 99p + 15p VAT

NEW POWER SUPPLY UNITS

Of the eleven power supply units which comprise our current range, nine have toroidal transformers made in our own factory. Thus these I.L.P. power supply units are space-saving, more efficient and their better overall design helps enormously when assembly building. All models in the range are compatible with all I.L.P. amps and pre-amps with types to match whatever I.L.P. power amps you choose.


PSU30 ±15V at 100mA to drive up to 12 x HY6 or 6 x HY66	£4.50 + 0.68p VAT
● THE FOLLOWING WILL ALSO DRIVE I.L.P. PRE-AMPS	
PSU36 for use with 1 or 2 HY30's	£8.10 + £1.22 VAT
● ALL THE FOLLOWING USE TOROIDAL TRANSFORMERS	
PSU50 for use with 1 or 2 HY60's	£10.94 + £1.64 VAT
PSU60 for use with 1 HY120	£13.04 + £1.96 VAT
PSU65 for use with 1 MOS120	£13.32 + £2.00 VAT
PSU70 for use with 1 or 2 HY120's	£15.92 + £2.39 VAT
PSU75 for use with 1 or 2 MOS120	£16.20 + £2.43 VAT
PSU90 for use with 1 HY200	£16.20 + £2.43 VAT
PSU95 for use with 1 MOS200	£16.32 + £2.45 VAT
PSU180 for use with 1 HY400 or 2 HY200	£21.34 + £3.20 VAT
PSU185 for use with 1 or 2 MOS200	£21.46 + £3.22 VAT

★ Freepost facility

When ordering or writing about I.L.P. products, you do not need to stamp the envelope. Mark it FREEPOST plus the code shown in the address below. We pay the postage for you.

★ **TO ORDER** Send cheque or money order payable to I.L.P. Electronics Ltd and crossed. Or pay by ACCESS or BARCLAYCARD. Cash payments must be in registered envelope; if C.O.D. payment is wanted, please add £1.00 to TOTAL value of order.

COMPATIBLE WITH ALL I.L.P. MODULES

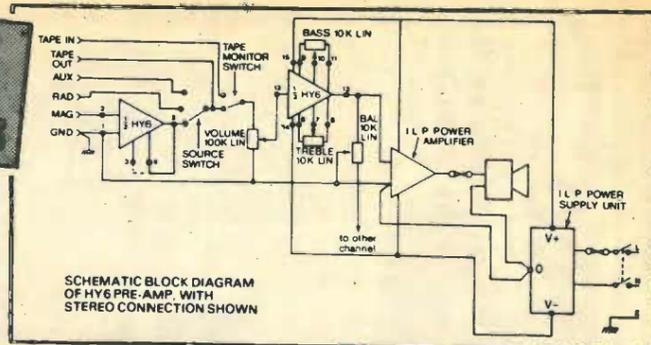

- DISTORTION TYPICALLY 0.005%
- S/N RATIO - 90dB (Mag. P.U. - 68 dB)
- 38 dB overload margin on Mag. P.U.

- LATEST DESIGN HIGH QUALITY CONNECTORS
- ONLY POTS, SWITCHES AND PLUGS/SOCKETS NEED ADDING
- NEEDS ONLY UNREGULATED POWER SUPPLY ±15 to ±60v

IN A RANGE OF 11 MODELS USING LATEST TOROIDAL TRANSFORMERS

1971-1980 TEN YEARS OF PLANNED PROGRESS

When, in 1971, Ian L. Potts founded his now world-famous company, he saw the need for a different and more rational approach to exploiting to the full, the potential that lay in modular construction. New thinking was badly needed. The result was a range of modules revolutionary in concept. The rightness of this new thinking is shown by the size of the company today, its new factory, its vast exports, its acceptance by constructors as the modules to build with. The range grows bigger and better. Exciting new lines (in no way conflicting with existing ones) are well past drawing board stage. This is why I.L.P. are simply ahead and staying there.

NO QUIBBLE 5 YEAR GUARANTEE
7-DAY DESPATCH ON ALL ORDERS
BRITISH DESIGN AND MANUFACTURE
FREEPOST SERVICE

BRITAIN'S FOREMOST QUALITY MODULE SUPPLIERS

To: I.L.P. ELECTRONICS LTD, CANTERBURY CT2 7EP

Please supply

..... Total purchase price £


I enclose Cheque Postal Orders International Money Order

Please debit my Access/Barclaycard Account No.

NAME

ADDRESS

Signature

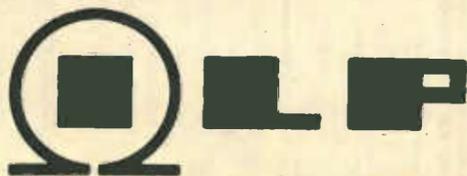

I.L.P. ELECTRONICS LTD.

FREE POST 6 Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP.
Telephone (0227) 54778 [Technical (0227) 64723] Telex 965780

Available also from MARSHALLS, WATFORD ELECTRONICS and certain other selected retailers

ALL U.K. ORDERS DESPATCHED POST FREE

GMT FreePost F Birmingham B19 1BR 021-233-2400

FREEPOST ON ORDERS • ACCESS
VAT INCLUSIVE PRICES • VISA
ADD 30p P&P • CASH
• CHEQUE
24 HR PHONE ANSWERING SERVICE

ALL PRICES IN PENCE EACH UNLESS OTHERWISE STATED

C-MOS			LINEAR			SEMICONDUCTORS					
HEF4006	22	HEF4006	105	HEF4512	138	CA3046	94	IN614	5	BC182L	12
HEF4001	22	HEF4046	133	HEF4516	127	CA3080E	77	IN4001	5	BC184	12
HEF4002	22	HEF4047	109	HEF4517	478	CA3130E	99	IN4002	5	BC184L	12
HEF4006	119	HEF4049	57	HEF4518	116	CA3140E	48	IN4004	7	BC212	11
HEF4007	22	HEF4050	57	HEF4519	69	CA3190E	293	IN4007	9	BC212L	12
HEF4008	100	HEF4051	87	HEF4520	118	LM301AN	34	IN4148	4	BC214	11
HEF4011	22	HEF4052	90	HEF4521	235	LM339N	78	IN5402	15	BC214L	12
HEF4012	22	HEF4053	90	HEF4522	124	LM339N	104	2N2369	21	BC567	13
HEF4013	57	HEF4056	62	HEF4522	150	LM381AN	198	2N2946	46	BC548	11
HEF4014	105	HEF4057	475	HEF4524	638	LM3900N	75	2N2926G	13	BC549	12
HEF4015	100	HEF4058	22	HEF4529	138	MC3403P	156	2N3053	19	BC557	15
HEF4016	57	HEF4059	22	HEF4535	122	NE531	131	2N3054	55	BC558	15
HEF4017	100	HEF4070	22	HEF4724	214	NE538T	259	2N3055	55	BCY70	15
HEF4018	100	HEF4071	23	HEF4077	113	NE555N	28	2N3702	9	BCY71	15
HEF4019	58	HEF4072	23	HEF4078	92	NE558N	66	2N3704	9	BD131	39
HEF4020	113	HEF4073	23	HEF4079	78	NE56N	171	2N3705	10	BD132	39
HEF4021	107	HEF4075	23	HEF4080	149	NE570N	485	2N3773	297	BD139	39
HEF4022	103	HEF4076	100	HEF4081	149	NE571N	505	2N3819	22	BD140	39
HEF4023	22	HEF4077	22	HEF4082	23	NE571N	505	2N3820	39	BF900	33.3
HEF4024	74	HEF4078	22	HEF4083	23	TA8120S	88	2N3904	9	BF905	29
HEF4025	22	HEF4081	23	HEF4084	23	TA8120S	88	2N3904	9	BF950	17
HEF4026	244	HEF4082	23	HEF4085	23	TA8120S	88	2N3904	9	BF951	17
HEF4027	37	HEF4083	23	HEF4086	23	TA8120S	88	2N3904	9	BF952	17
HEF4028	89	HEF4084	23	HEF4087	23	TA8120S	88	2N3904	9	BF953	17
HEF4029	113	HEF4085	23	HEF4088	23	TA8120S	88	2N3904	9	BF954	17
HEF4030	58	HEF4086	23	HEF4089	23	TA8120S	88	2N3904	9	BF955	17
HEF4031	230	HEF4087	23	HEF4090	23	TA8120S	88	2N3904	9	BF956	17
HEF4032	136	HEF4088	23	HEF4091	23	TA8120S	88	2N3904	9	BF957	17
HEF4033	107	HEF4089	23	HEF4092	23	TA8120S	88	2N3904	9	BF958	17
HEF4034	94	HEF4090	23	HEF4093	23	TA8120S	88	2N3904	9	BF959	17
HEF4035	83	HEF4091	23	HEF4094	23	TA8120S	88	2N3904	9	BF960	17
HEF4036	83	HEF4092	23	HEF4095	23	TA8120S	88	2N3904	9	BF961	17
HEF4037	83	HEF4093	23	HEF4096	23	TA8120S	88	2N3904	9	BF962	17
HEF4038	83	HEF4094	23	HEF4097	23	TA8120S	88	2N3904	9	BF963	17
HEF4039	83	HEF4095	23	HEF4098	23	TA8120S	88	2N3904	9	BF964	17
HEF4040	83	HEF4096	23	HEF4099	23	TA8120S	88	2N3904	9	BF965	17
HEF4041	83	HEF4097	23	HEF4100	23	TA8120S	88	2N3904	9	BF966	17
HEF4042	83	HEF4098	23	HEF4101	23	TA8120S	88	2N3904	9	BF967	17
HEF4043	83	HEF4099	23	HEF4102	23	TA8120S	88	2N3904	9	BF968	17

CAPACITORS		ELECTROLYTIC AXIAL		POLYESTER RADIAL LEADS		ELECTROLYTIC RADIAL LEADS	
1.0	10	10	10	10	10	10	10
2.2	22	22	22	22	22	22	22
3.3	33	33	33	33	33	33	33
4.7	47	47	47	47	47	47	47
10	100	100	100	100	100	100	100
15	150	150	150	150	150	150	150
22	220	220	220	220	220	220	220
33	330	330	330	330	330	330	330
47	470	470	470	470	470	470	470
100	1000	1000	1000	1000	1000	1000	1000
150	1500	1500	1500	1500	1500	1500	1500
220	2200	2200	2200	2200	2200	2200	2200
330	3300	3300	3300	3300	3300	3300	3300
470	4700	4700	4700	4700	4700	4700	4700
680	6800	6800	6800	6800	6800	6800	6800
1000	10000	10000	10000	10000	10000	10000	10000
1500	15000	15000	15000	15000	15000	15000	15000
2200	22000	22000	22000	22000	22000	22000	22000

RESISTORS		SKELETON PRESETS, MINIATURE	
0.25W, E24 Values	100-100k, 5% Tol.	0.1W, E3 Values	100R-1M, Lin. Vertical Mounting
0.5W, E24 Values	100-100k, 5% Tol.	0.1W, E3 Values	100R-1M, Lin. Horizontal Mounting
1W, E24 Values	100-100k, 5% Tol.	0.5W, E3 Values	100R-4M7, Lin. Vertical Mounting
2W, E24 Values	100-100k, 5% Tol.	0.5W, E3 Values	100R-4M7, Lin. Horizontal Mounting
5W, E24 Values	100-100k, 5% Tol.	1W, E3 Values	100R-4M7, Lin. Horizontal Mounting
10W, E24 Values	100-100k, 5% Tol.	2W, E3 Values	100R-4M7, Lin. Horizontal Mounting
25W, E24 Values	100-100k, 5% Tol.	5W, E3 Values	100R-4M7, Lin. Horizontal Mounting
50W, E24 Values	100-100k, 5% Tol.	10W, E3 Values	100R-4M7, Lin. Horizontal Mounting
100W, E24 Values	100-100k, 5% Tol.	25W, E3 Values	100R-4M7, Lin. Horizontal Mounting
250W, E24 Values	100-100k, 5% Tol.	50W, E3 Values	100R-4M7, Lin. Horizontal Mounting
500W, E24 Values	100-100k, 5% Tol.	100W, E3 Values	100R-4M7, Lin. Horizontal Mounting
1000W, E24 Values	100-100k, 5% Tol.	250W, E3 Values	100R-4M7, Lin. Horizontal Mounting
2500W, E24 Values	100-100k, 5% Tol.	500W, E3 Values	100R-4M7, Lin. Horizontal Mounting
5000W, E24 Values	100-100k, 5% Tol.	1000W, E3 Values	100R-4M7, Lin. Horizontal Mounting

MAINS TRANSFORMERS		D.I.L. SOCKETS	
0.5W, E24 Values	100-100k, 5% Tol.	8 Pin Low Profile Socket Tin	12 DIL SKT 8
1W, E24 Values	100-100k, 5% Tol.	14 Pin Low Profile Socket Tin	14 DIL SKT 14
2W, E24 Values	100-100k, 5% Tol.	16 Pin Low Profile Socket Tin	16 DIL SKT 16
5W, E24 Values	100-100k, 5% Tol.	18 Pin Low Profile Socket Tin	18 DIL SKT 18
10W, E24 Values	100-100k, 5% Tol.	20 Pin Low Profile Socket Tin	20 DIL SKT 20
25W, E24 Values	100-100k, 5% Tol.	24 Pin Low Profile Socket Tin	24 DIL SKT 24
50W, E24 Values	100-100k, 5% Tol.	28 Pin Low Profile Socket Tin	28 DIL SKT 28
100W, E24 Values	100-100k, 5% Tol.	32 Pin Low Profile Socket Tin	32 DIL SKT 32
250W, E24 Values	100-100k, 5% Tol.	36 Pin Low Profile Socket Tin	36 DIL SKT 36
500W, E24 Values	100-100k, 5% Tol.	40 Pin Low Profile Socket Tin	40 DIL SKT 40
1000W, E24 Values	100-100k, 5% Tol.	44 Pin Low Profile Socket Tin	44 DIL SKT 44
2500W, E24 Values	100-100k, 5% Tol.	48 Pin Low Profile Socket Tin	48 DIL SKT 48
5000W, E24 Values	100-100k, 5% Tol.	52 Pin Low Profile Socket Tin	52 DIL SKT 52


VERO ELECTRONICS PRODUCTS		SWITCHES	
2.5" x 5" 1" pitch Veroboard	71	Miniature Toggle - Honeywell	Order Code
3.75" x 5" 1" pitch Veroboard	79	SPDT	67 SW 8A1011
2.5" x 1" 1" pitch Veroboard (S)	85/Pack	SPDT C/O/H	81 SW 8A1021
3.75" x 5" 1" pitch Plain Board	88	SPDT Double Bias To Centre	90 SW 8A1041
5.82" x 2.9" 1" pitch V-DIP Board	135	DPDT C/O/H	111 SW 8A2011
Spot Face Cutter	107	Miniature Push - C & K	62 SW 8531
Pin Insertion Tool for .040 type pin	147	Push To Make, Momentary	62 SW 8533
DS Print 040 (100)	44/Pack	Push To Break, Momentary	62 SW 8533
SS Print 040 (100)	44/Pack		
Veronica Kit (11-pin, 2-wire, 25-comb)	456/Kit		
Veronica Combs (25)	109/Pack		
Veronica Wire (2)	109/Pack		

GMT ELECTRONICS PROJECTS	KIT	BUILT UP
FREE-STANDING COMPLETE TELETEXT UNIT - FULL SPEC	£199-90	£275-00
TELETEXT DECODER BOARD + REMOTE HAND CONTROL	£135-90	£160-00
TELETEXT COMPATIBLE TUNER AND P. S. U.	£ 46-90	£ 57-00
TELETEXT COMPATIBLE PAL ENCODER + MODULATOR	£ 22-90	£ 35-00
F. E. T. OUTPUT 100W MONO POWER AMPLIFIER MODULE	£ 27-50	£ 35-00
X-BAND DOPPLER RADAR ALARM MODULE - MARK II	£ 35-90	£ 44-00
ONE AMP P. S. U. MODULE (SPECIFY 5 OR 12 VOLTS)	£ 7-50	£ 10-00
SIMULATED INERTIA MODEL TRAIN CONTROLLER	£ 22-50	£ 35-00
SIMULATED INERTIA SLOT RACER CONTROLLER	£ 27-50	£ 40-00
MODEL TRAIN STEAM SOUND SIMULATOR MODULE	£ N/A	£ 5-00

WW - 069 FOR FURTHER DETAILS

S 100

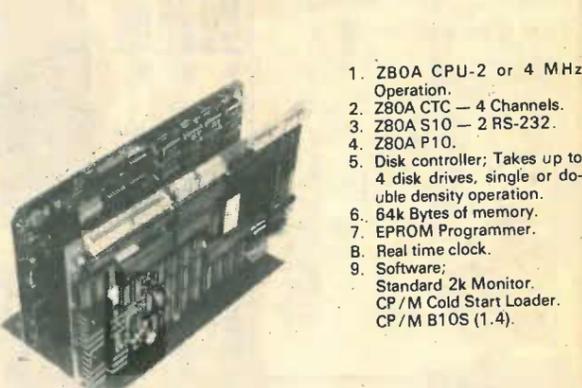Do You Have All These Facilities On Your S 100 System, With Just Two Boards?



1. ZBOA CPU-2 or 4 MHz Operation.
2. ZBOA CTC - 4 Channels.
3. ZBOA S10 - 2 RS-232.
4. ZBOA P10.
5. Disk controller; Takes up to 4 disk drives, single or double density operation.
6. 64k Bytes of memory.
7. EPROM Programmer.
8. Real time clock.
9. Software; Standard 2k Monitor. CP/M Cold Start Loader. CP/M B10S (1.4).

SEMEL

MICROCOMPUTER - HARDWARE - SOFTWARE

3c Barley Market Street, Tavistock, Devon PL19 0JF
Tel. Tavistock (0822) 5247. Telex: 45263

CLEF ELECTRONIC MUSIC

PIANOS SPECIALISTS SINCE 1972 DOMESTIC & STAGE TYPES KITS OR MANUFACTURED

MASTER RHYTHM User Programmable. Twenty-four patterns. Eight parallel tracks. Twelve instruments sequence operation.

£79 KIT

£114 Built

The most advanced form of Touch Sensitive action simulating piano key inertia by patented technique.

Four mixable voices for serious tone variation plus electronic chorus and flanger effects. See lists for Cabinets, P.A. and Manufacture.

CLEF PRODUCTS (ELECTRONICS) LIMITED
Dept. W, 44a Bramhall Lane South
Bramhall, Stockport, Cheshire SK7 1AH
061-439 3297

WW - 044 FOR FURTHER DETAILS

HIGH PERFORMANCE BUT LOW COST - AUDIO SIGNAL GENERATORS SINE/SQUARE WAVE

Model 146-9. Distortion .0015% (at 1 KHz). Range 10Hz-100KHz. Output 1v RMS (600 ohms).

Prices:
Assembled, battery model £36 (+ UK Tax £5.40)
Kit of Parts £31 (+ UK Tax £4.65)
Mains version, Assembled £46 (+ UK Tax £6.90)
UK P/P £2. Overseas from £5.50.

Model A0113
Distortion .02% (1 KHz) otherwise as 146.9.
Battery version £29.50 (+ UK Tax £4.40)
Mains version £36.00 (+ UK Tax £5.40)
Kit, battery £23.00 (+ UK Tax £3.45)
P/P £1.50.

TELERADIO ELECTRONICS
325 Fore Street, Edmonton, London, N9 0PE Tel: 807 3719

Also available: R.F. Sig. Gen. P.S.U. T.H.D. Analyser, Frequency Meter, MVM.T. Function (Sweep) Generators. SAE for full lists. (190)

PORTABLE RADIO CASE
Size: 11 x 8 x 3 1/2 ins approx. Made from plywood, pleasingly covered. Suitable for any normal radio circuit. Has studs for mounting 5" speaker and the front is drilled to take a tuning condenser in the centre and normal controls either side. £2.30 + £1.50 post.

LAST MONTH'S SNIP - STILL AVAILABLE
And it still carries a free gift of a desoldering pump, which we are currently selling at £6.35p. The snip is perhaps the most useful breakdown parcel we have ever offered. It is a parcel of 50 nearly all different computer panels containing parts which must have cost at least £500. On these boards you will find over 300 IC's. Over 300 diodes, over 200 transistors and several thousand other parts, resistors, capacitors, multi-turn pots, rectifiers, SCR, etc. etc. If you act promptly, you can have this parcel for only £8.50, which when you deduct the value of the desoldering pump, works out to just a little over 4p per panel. Surely this is a bargain you should not miss! When ordering please add £2.50 post and £1.27 VAT.

MAINS MOTORS Precision made as used in record players, blow heaters, etc. Speed usually 1,400. All have ample spindle length for coupling fan blade, pulley, etc. Power depends on stack size. 5/8" stack £2.00, 3/4" stack £2.50, 7/8" stack £3.00, 1" stack £3.50, 1 1/8" stack £4.50. Add 25% to motor cost to cover postage, and then add 15% VAT.

YOUR LAST CHANCE FOR THIS BARGAIN
100 twist drills, regular tool shop price over £50, yours for only £11.50. With these you will be able to drill metal, wood, plastic, etc. from the tiniest holes in P.C.B. right up to about 1/4". Don't miss this snip - send your order today.

MAGNET

Cotswold Electronics Toroidal Power Transformers

Budget range for the amateur and professional



Type	VA	Secondary Volts	Current	RMS	RMS	Dimensions Dia.	Height	Weight Kg	Price
C1000	30	6+6	2.50	70mm	30mm	0.45			£4.55 (+£1.10 p.p. + 0.84 VAT)
C1001	30	9+9	1.67	70mm	30mm	0.45			
C1002	30	12+12	1.25	70mm	30mm	0.45			
C1003	30	15+15	1.00	70mm	30mm	0.45			
C1004	30	18+18	0.83	70mm	30mm	0.45			
C1005	30	22+22	0.68	70mm	30mm	0.45			
C1006	30	25+25	0.60	70mm	30mm	0.45			
C1007	30	30+30	0.50	70mm	30mm	0.45			

Type	VA	Secondary Volts	Current	RMS	RMS	Dimensions Dia.	Height	Weight Kg	Price
C1010	60	9+9	3.33	87mm	33mm	0.75			£4.88 (+£1.43 p.p. + 0.94 VAT)
C1011	60	12+12	2.50	87mm	33mm	0.75			
C1012	60	15+15	2.00	87mm	33mm	0.75			
C1013	60	18+18	1.67	87mm	33mm	0.75			
C1014	60	22+22	1.36	87mm	33mm	0.75			
C1015	60	25+25	1.20	87mm	33mm	0.75			
C1016	60	30+30	1.00	87mm	33mm	0.75			
C1017	60	110	0.56	87mm	33mm	0.75			
C1018	60	220	0.27	87mm	33mm	0.75			
C1019	60	240	0.25	87mm	33mm	0.75			

Type	VA	Secondary Volts	Current	RMS	RMS	Dimensions Dia.	Height	Weight Kg	Price
C1020	100	12+12	4.17	88mm	40mm	1.00			£5.70 (+£1.43 p.p. + £1.07 VAT)
C1021	100	15+15	3.33	88mm	40mm	1.00			
C1022	100	18+18	2.78	88mm	40mm	1.00			
C1023	100	22+22	2.27	88mm	40mm	1.00			
C1024	100	25+25	2.00	88mm	40mm	1.00			
C1025	100	30+30	1.57	88mm	40mm	1.00			
C1026	100	110	0.91	88mm	40mm	1.00			
C1027	100	220	0.45	88mm	40mm	1.00			
C1028	100	240	0.42	88mm	40mm	1.00			

• A budget range of Toroidal transformers from the people backed by 25 years of experience supplying the high technology industries of avionics, telecommunications, electro-medical etc. - Transformers constructed from highest grades of grain oriented silicon steel to give operation at high flux density with very low iron losses resulting in high efficiency. • A reduction of up to half the weight and volume and radiated field as low as one tenth when compared with laminated conventional equivalents. • Each transformer supplied with fixing kit and technical information sheet.

Cotswold Electronics Ltd Cheltenham GL51 9NX

Type	Mains Voltage	Secondary Volts	VA	Qty

I enclose Cheque P.O. Money Order

Access/Barclaycard No.

Name

Address

Postal Code

Telephone No.

NOTE: All types normally supplied with 240 V primary 110 V, 220 V or other voltage supplied on request.

24 hour answering service: You may telephone your order throughout 24 hours quoting your Access or Barclaycard number. Phone number 0242-41313.

WW - 030 FOR FURTHER DETAILS

Type	VA	Secondary Volts	Current	RMS	RMS	Dimensions Dia.	Height	Weight Kg	Price
C1030	160	18+18	4.44	108mm	42mm	1.5			£8.40 (+£1.73 p.p. + £1.52 VAT)
C1031	160	22+22	3.64	108mm	42mm	1.5			
C1032	160	25+25	3.20	108mm	42mm	1.5			
C1033	160	30+30	2.57	108mm	42mm	1.5			
C1034	160	35+35	2.29	108mm	42mm	1.5			
C1035	160	110	1.46	108mm	42mm	1.5			
C1036	160	220	0.73	108mm	42mm	1.5			
C1037	160	240	0.67	108mm	42mm	1.5			

Type	VA	Secondary Volts	Current	RMS	RMS	Dimensions Dia.	Height	Weight Kg	Price
C1040	230	25+25	4.80	115mm	50mm	2.2			£10.20 (+£1.73 p.p. + £1.79 VAT)
C1041	230	30+30	3.83	115mm	50mm	2.2			
C1042	230	35+35	3.29	115mm	50mm	2.2			
C1043	230	40+40	2.88	115mm	50mm	2.2			
C1044	230	110	2.09	115mm	50mm	2.2			
C1045	230	220	1.05	115mm	50mm	2.2			
C1046	230	240	0.96	115mm	50mm	2.2			

Type	VA	Secondary Volts	Current	RMS	RMS	Dimensions Dia.	Height	Weight Kg	Price
C1050	330	25+25	6.60	130mm	52mm	2.8			£11.90 (+£1.90 p.p. + £2.07 VAT)
C1051	330	30+30	5.50	130mm	52mm	2.8			
C1052	330	35+35	4.71	130mm	52mm	2.8			
C1053	330	40+40	4.13	130mm	52mm	2.8			
C1054	330	45+45	3.67	130mm	52mm	2.8			
C1055	330	110	3.00	130mm	52mm	2.8			
C1056	330	220	1.50	130mm	52mm	2.8			
C1057	330	240	1.38	130mm	52mm	2.8			


Type	VA	Secondary Volts	Current	RMS	RMS	Dimensions Dia.	Height	Weight Kg	Price
C1060	530	30+30	8.83	145mm	60mm	3.8			£15.80 (+£2.06 p.p. + £2.88 VAT)
C1061	530	35+35	7.57	145mm	60mm	3.8			
C1062	530	40+40	6.83	145mm	60mm	3.8			
C1063	530	45+45	5.89	145mm	60mm	3.8			
C1064	530	50+50	5.30	145mm	60mm	3.8			
C1065	530	110	4.82	145mm	60mm	3.8			
C1066	530	220	2.41	145mm	60mm	3.8			
C1067	530	240	2.21	145mm	60mm	3.8			

FREEPOSTUK only: We pay postage on all enquiries and orders. Address your envelope: Dept W Cotswold Electronics Ltd, FREEPOST, Cheltenham Glos. GL51 1BR (No stamp required)

WW - 032 FOR FURTHER DETAILS

OTARI

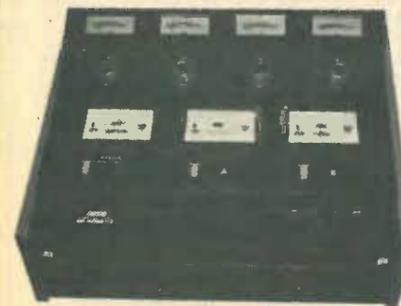World Leader in Duplicating & Tape-loading Equipment



C2 In-cassette Copier
High quality at low cost. Stereo. Expandable to 11 copies. Ferrite heads. DC servo motors.



DP4050 OCF
Reel to cassette copier. 6 slaves, DC Servo motors and ferrite heads. 2 speed master.

DP2700 Audio Tape-loader
A precision loader at a budget price. Compressor not required. Easy to operate and reliable. 100 C-60 per hour.



Video tape loaders also available

Sole UK Distributor:
ITA, 1-7 Harewood Avenue, Marylebone Road, London NW1. Tel: 01-724 2497. Telex: 21879.

WW - 077 FOR FURTHER DETAILS

MODERN LABORATORY TOOL HOUSED IN ATTRACTIVE STEEL CASE


- ★ HOLD SIX EPROMS
- ★ SAFETY INTERLOCKED EPROM TRAY
- ★ SEPARATE ERASE INDICATOR
- ★ MONEY BACK GUARANTEE

LOW COST EPROM ERASURE

£38.50 POST FREE
Including VAT

Send cash with order to:
NORTHERN ELECTRONICS
51 ARUNDEL STREET
MOSSLEY, LANCS. OL5 0LS
Tel: 04575 4119

WW - 031 FOR FURTHER DETAILS

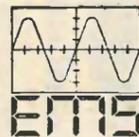

Electronic Measurement Services

REPAIR & CALIBRATION SPECIALISTS OF TEST & MEASURING INSTRUMENTS

- ★ Fast turn around time
- ★ High quality backed by warranty
- ★ Competitive rates
- ★ Certification if required
- ★ Nationwide collection and delivery service

Stockport Road, Longsight, Manchester M13 0LF

061-273 4653

WW No. 032

WW - 032 FOR FURTHER DETAILS

DT-400s are designed and manufactured by SAFGAN in UK


SAFGAN presents **DT-400** series from **£169 + VAT**

HIGH-QUALITY **DUAL TRACE** OSCILLOSCOPES
A BRITISH PRODUCT EVERYONE CAN AFFORD

Model DT-410 DUAL TRACE 5mv/div 10MHZ @ **£169 + VAT**
Model DT-412 DUAL TRACE 5mv/div 12MHZ @ **£175 + VAT**
Model DT-415 DUAL TRACE 5mv/div 15MHZ @ **£188 + VAT**

SPECIFICATION FOR ALL MODELS

- ★ CH1, CH2: 5mv/div — 20v/div in 12 col 1-2-5 steps. Input impedance 1MΩ + 22pF
- ★ BANDWIDTH: 10MHz (DT-410), 12MHz (DT-412), 15MHz (DT-415)
- ★ TIME BASE: 0.5µs/div — 200ms/div in 18 cal steps
X5 Expansion to 100ns/div
X5 Multiplier to 15/div
- ★ XY FACILITY: Matched Inputs X = CH1, Y = CH2
- ★ TRIGGER: Level Control, ± Slope, Bright Line AUTO, NORMAL, TV Triggering CH1, CH2 0.5 div, EXT Trig 100mv
- ★ Z Modulation
- ★ Cal output/probe compensation.
- ★ Graticule blue ruled 8 × 10 div (6.4 × 8cm²)
- ★ SIZE: H215mm W165mm D280mm Weight 4.5 kg.
PROBE (XI—REF—X10) **£11.50 + V.A.T.**

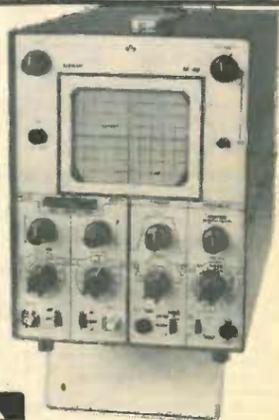

DT-400 Series

Orders to: **SAFGAN ELECTRONICS LTD.** (Goods + 15% + £3.50 P&P). Or £6.50 parcel service
56 Bishop's Wood, St. John's, Woking, Surrey, GU21 3QB Tel: Woking 69560 or Woking 66836
London Stockist: Audio Electronics, Edgware Road, London. Tel. 01-724 3564

WW - 038 FOR FURTHER DETAILS

Happy Memories

Memory	Capacity	Price
4116	200ns	£2.25
2114	200ns	£2.95
2708	450ns	£3.95
2114	450ns	£2.20
2716	5 volt	£5.25

Memorex Soft-sectored mini-discs for PET, TRS-80 etc. Supplied in FREE LIBRARY CASE, £19.95 per 10

Low Profile I.C. Sockets by "Texas"

Pins	Price
8	14
16	18
20	22
24	28
28	40
40	50
50	60
60	70
70	80
80	90
90	100

Memory Upgrade Kits for Apple, 2020, TRS-80, etc.: from £18, please phone. Quantity prices available on request. Government and Educational Orders welcome. Trade accounts opened.

All prices include VAT. Postage FREE on orders over £15, otherwise add 30p
Access and Barclaycard welcome

HAPPY MEMORIES, DEPT. W.W.
GLADESTRY, KINGTON
HEREFORDSHIRE HR5 3NY
Tel. (054422) 618


Memory	Price
2114L-300ns	£2.10
4116-200ns	£1.89
2708-450ns	£3.15
2716-450ns	£4.99

74LS series	Price
74LS240	£1.54
74LS243	£1.54
74LS244	£1.54
74LS245	£1.70

Bridge Rectifiers	Price
25 Amp 50 volt	£0.74
25 Amp 100 volt	£0.94
25 Amp 200 volt	£1.26
25 Amp 400 volt	£1.68
25 Amp 600 volt	£2.10
25 Amp 800 volt	£2.63

Please add 50 pence for carriage.
All prices EXCLUDE VAT
Please send s.a.e. for price list.

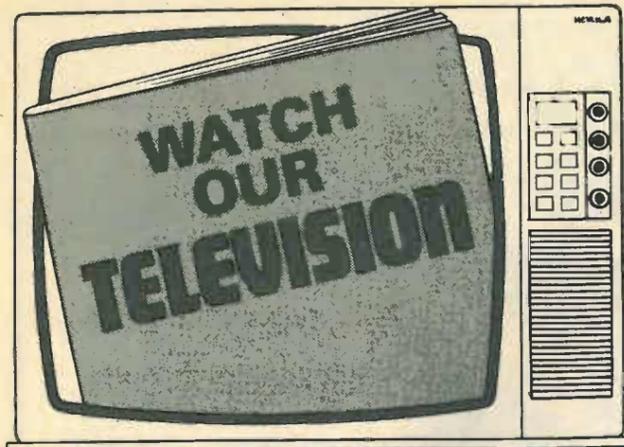STRUTT LTD.
ELECTRONIC COMPONENT DISTRIBUTORS
ETC.
3c BARLEY MARKET STREET, TAVISTOCK
DEVON, ENGLAND PL19 0JF
Tel. Tavistock (0822) 5439/5548. Telex: 45263



... the only magazine in Britain that gives the amateur enthusiast and professional engineer alike a comprehensive up-to-date coverage of TV technology. Coverage includes the latest developments in circuitry, video and long distance television ... with a special emphasis on servicing and fault finding.

Regular construction articles have included test equipment, mono-chrome/colour receivers, monitors and video cameras.

THIS MONTH

Construction
An 'Arrow' Generator

A special joystick control unit for inclusion between camera and monitor ... drawing attention to points on a TV display by use of a moveable arrow.

Servicing

Greatly increased reliability of modern TV sets means intermittent faults are accounting for a much larger proportion of the servicing workload. We offer guidance on tracking down these, often difficult to locate, faults.

Review

THORN TX10 Chassis

We review the latest Thorn chassis probably the equal of any in the world.

TELEVISION
The monthly magazine that keeps you in the picture!

60P

Sowter Transformers

With 40 years' experience in the design and manufacture of several hundred thousand transformers we can supply:

AUDIO FREQUENCY TRANSFORMERS OF EVERY TYPE YOU NAME IT! WE MAKE IT! OUR RANGE INCLUDES

Microphone transformers (all types), Microphone Splitter/Combiner transformers. Input and Output transformers, Direct Injection transformers for Guitars, Multi-Secondary output transformers, Bridging transformers, Line transformers, Line transformers to G.P.O. Isolating Test Specification, Tapped impedance matching transformers, Gramophone Pickup transformers, Audio Mixing Desk transformers (all types), Miniature transformers, Microminiature transformers for PCB mounting, Experimental transformers, Ultra low frequency transformers, Ultra linear and other transformers for Valve Amplifiers up to 500 watts, Inductive Loop Transformers, Smoothing Chokes, Filter, Inductors, Amplifier to 100 volt line transformers (from a few watts up to 1,000 watts), 100 volt line transformers to speakers, Speaker matching transformers (all powers), Column Loudspeaker transformers up to 300 watts or more. We can design for RECORDING QUALITY, STUDIO QUALITY, HI-FI QUALITY OR P.A. QUALITY. OUR PRICES ARE HIGHLY COMPETITIVE AND WE SUPPLY LARGE OR SMALL QUANTITIES AND EVEN SINGLE TRANSFORMERS. Many standard types are in stock and normal dispatch times are short and sensible. OUR CLIENTS COVER A LARGE NUMBER OF BROADCASTING AUTHORITIES, MIXING DESK MANUFACTURERS, RECORDING STUDIOS, HI-FI ENTHUSIASTS, BAND GROUPS, AND PUBLIC ADDRESS FIRMS. Export is a speciality and we have overseas clients in the COMMONWEALTH, E.C., USA, MIDDLE EAST, etc. Send for our questionnaire which, when completed, enables us to post quotations by return.

E. A. Sowter Ltd.

Manufacturers and Designers
E. A. SOWTER LTD. (Established 1941), Reg. No. England 303990
The Boat Yard, Cullingham Road, Ipswich IP1 2EG, Suffolk
P. O. Box 36, Ipswich IP1 2EL, England
Phone: 0473 52794 & 0473 219390

WW - 050 FOR FURTHER DETAILS

SWITCHCRAFT		XLR CONNECTORS	
Line Female A3F.....	£1.07	Chassis Female D3F.....	£1.34
Line Male A3M.....	£0.93	Chassis Male D3M.....	£0.77

4, 5 and 6 pin versions and large selection audio adaptors available			
NEUTRIK		XLR CONNECTORS	
Latchless Chassis NC3-FZ.....	£0.87	Latchless Chassis Male NC3-MZ.....	£0.59
Line Female NC3-SC.....	£1.34	Line Male NC3-MC.....	£1.15

XLR LINE SERIES			
XLR LINE 11C.....	£3.87	XLR LINE 12C.....	£3.76
XLR LINE 32.....	£2.89	XLR LINE 31.....	£4.14

BELCLERE AUDIO TRANSFORMERS	
EN6422 Ratio 1.2 + 2, Freq. 40Hz-35KHz, PRI 150/600Ω, sec. 600/2.4KΩ.....	£3.30
EN6423 Ratio 1 + 1:6.45 + 6.45, Freq. 40Hz-25KHz, PRI 150/600Ω, sec. 6.25K/25KΩ.....	£3.30
SKT-723 MuMetal Screening can, 39dB reduction 50Hz ext. field.....	£1.05

KELSEY ACOUSTICS LTD.
28 POWIS TERRACE, LONDON W11 1JH
01-727 1046

WW - 066 FOR FURTHER DETAILS

Wirewound Ceramic Resistors 5w-17w OR5-39K from £9.35 per 100	QUICK ACTING & ANTI SURGE CARTRIDGE FUSES from £3.15 per 100.
--	--

Carbon Film Resistors 1/4w 5% £2.50 per 1,000, per value, carriage and VAT extra. 6R8 33R 100R 120R 360R 470R 560R 2K4 2K7 4K7 5K6 7K5 8K2 100K 120K 150K 220K 300K 390K 820K.	Lists available of other wattages and values on special offer.
--	--

Cable Sleeves and Markers from £1.38 per 1,000. Crimp Terminals from £9.60 per 1,000. Audible Warning Devices. Buzz-tone, Bleep-tone, Banshee, Bedlam, etc. from £1.14 each. Self-adhesive Pcb guides from £5.04 per 100.	PBRA LTD. Golden Green, Tonbridge Kent TN11 0LH Hopfield (073274) 345 Member Crystalate Group
--	--

WW - 074 FOR FURTHER DETAILS

L. J. ELECTRONICS LIMITED

MICROELECTRONIC AND MICROPROCESSOR SYSTEMS FOR EDUCATION



Send for details of our:-

- ★ Microprocessor Systems
- ★ Peripheral Hardware
- ★ Test Equipment
- ★ Digital Patching Systems
- ★ Analogue Patching Systems
- ★ Laboratory Power Supplies

L. J. ELECTRONICS LTD.,
9, Francis Way,
Bowthorpe Ind. Est.,
Norwich.
NR5 9JA.
Tel: Norwich 746340
Telex: 975504

WW - 051 FOR MORE DETAILS

★ VIDEO
MONITOR BARGAIN ★

Due to a large purchase of surplus equipment, we are able to offer these superb professional 12in. green phosphor monitors at a fraction of their usual cost -

- ★ Manufactured by US Inco term Corporation, imported by large mainframe manufacturer.
- ★ Standard composite video in - just plug into your micro.
- ★ 230v mains. Additional PSU to supply keyboard included.
- ★ Extremely attractive anodised aluminium case.
- ★ 600 line resolution - P39 Phosphor - anti-reflective screen.
- ★ Ideal for graphics or alphanumeric display.
- ★ Complete with mains lead, long video cable and manual.
- ★ Guaranteed brand new in original boxes.

We believe these are the finest monitors available at any price. Trade enquiries invited. Only £75 each + VAT. Carriage £7.50.

KEYBOARDS

84 Key ASCII with numeric cluster and control keys. LED Status indicators. In very smart case, with all encoding circuitry and on-board regulators, brand new and unused. No circuit available, so only £27 each. We also have some keyboards, as above, but without indicators and case for only £15. Add VAT and £2.50 postage.

OTHER BARGAINS

Diablo series 30 disk drives, 2.5 MByte.....	£500
Fixed 5 Megabyte disk and controller for 8080.....	£400
IBM standard floppy drive and controller for 8080.....	£200
TEXAS Silent 700 ASCII 30 cps Terminals (KSR).....	£175
KSR33 Teletypes, 20mA loop ASCII.....	£100
Terminet 300 ASCII cps letter quality term.....	£300
Pertec Industry standard 9-track Magtape drives.....	£450
BASF 12-Sector Disk Cartridges, RK05 type, NEW.....	£30 ea.
DECTAPES, for TU55/56 drives.....	£20 for box 12 reels
TALLY high speed tape readers.....	£75

Many other items plus full range of PDP8/11 modules in stock - please telephone for latest list. VAT and carriage extra.

CHILTERN ELECTRONICS
B.C.M., Box 8085, London WC1N 3XX. Tel. 0494 714483

WW - 72 FOR FURTHER DETAILS

COME TO SPILTH ELECTRONICS FOR ALL YOUR CB NEEDS

- ANTENNAS, COAX
- CONNECTORS MIKES
- SWR METERS BOOKS
- 40 & 80 CH RECEIVERS

SPILTH ELECTRONICS

3D Barley Market Street
Tavistock, Devon
Phone 0822 5865
Telex 45236

Guide to Broadcasting Stations

18th Edition

Around the world some thousands of radio stations are sending signals. If you're receiving, this standard guide will tell you who's where. It lists stations broadcasting in the long, medium, short wave and vhf bands, dealing with them by frequency, geographical location and alphabetical order. Sections are helpfully cross referenced. The Wireless World Guide to Broadcasting Stations is the eighteenth edition of a publication which has sold over 270,000 copies. In addition to the stations data, it includes much useful information on aeriels, propagation, signal identifications and reception reports.

£3.25 inc. postage.

Guide to Broadcasting Stations
18th Edition

Over 270,000 copies sold

To: General Sales Dept., Room 205
Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS
Please send me _____ copy/ies of the Wireless World Guide to Broadcasting Stations (18th edition) @ £3.25 a copy inclusive, (U.K.), \$8 overseas, remittance enclosed. Cheque/P.O. payable to IPC Business Press Ltd.

Name _____
(please print)
Address _____

Registered in England No. 677128
Registered Office: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS

U.K. RETURN OF POST MAIL ORDER SERVICE, ALSO WORLDWIDE EXPORT SERVICE

BSR DE LUXE AUTOCHANGER

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability. Stereo Ceramic Cartridge. AC 200/250V. Size 13 1/2" x 11 1/4". 3 speeds. Above motor board 3 1/4". Below motor board 2 1/2". with Ceramic Stereo cartridge.



£20 Post £2

HEAVY METAL PLINTHS

Cut out for most BSR or Garrard decks. Silver grey finish with tinted plastic cover. Size 16 x 14 x 6in.

Post £2
£10.50

PIONEER and J.V.C. TEAK VENEERED PLINTH

19 x 14 1/2in. with Plastic Cover

Post £2
£10.50

TINTED PLASTIC COVERS

Sizes: 14 1/2 x 12 1/2 x 3in. £4.
18 x 13 1/2 x 4in. £6.
17 1/2 x 9 1/2 x 3 1/2in. £3. 18 x 12 1/2 x 3in. £6.

Post £1.50

BSR SINGLE PLAYER DECKS

BSR P200 2 speeds flared aluminium turntable "S" shape arm, cueing device.
Less cartridge £30
Belt drive Post £2



Ready cut mounting board. Only £1 extra.

BSR P172 RIM DRIVE QUALITY DECK

Manual or automatic play. Three speeds. Precision ultra slim arm.
Cueing device. Bargain price

£20 Post £2

With stereo ceramic cartridge
BSR P207 BUDGET SINGLE PLAYER ideal for disco or small two-speed Hi-Fi system with stereo cartridge and cueing device. £17 Post £2

GARRARD 6-200 SINGLE PLAYER DECK

Brushed Aluminium Arm with stereo ceramic cartridge and Diamond Stylus, 3-speeds. Manual and Auto Stop/Start. Large Metal Turntable. Cueing Device and Pause Control. Ready cut mounting board £1 extra.

£22 Post £2

ELAC HI-FI SPEAKER

10in. TWIN CONE

Large ceramic magnet. 50-16,000 c/s. bass resonance 40 c/s. 8 ohm impedance. 10 watts RMS.

£7.95 Post 99p



POTENTIOMETERS Carbon Track

5kΩ to 2MΩ. LOG or LIN. L/S 50p. DP 90p. Stereo L/S £1.10. DP £1.30. Edge Pot 5K. SP 45p. Sliders Mono 65p. Stereo 85p.

EMI 13 1/2 x 8in. LOUSPEAKERS

With tweeter and crossover. 10 watt. 8 ohm. 15 watts, 3 or 8 ohm.

£9.95 Post 99p
£10.95 Post 99p

SUITABLE BOOKSHELF CABINET

£10.50. Post £2.50

THE "INSTANT" BULK TAPE ERASER

Suitable for cassettes, and all sizes of tape reels. AC mains 200/250V. Hand held size with switch and lead.

Will also demagnetise small tools
Head Demagnetiser only £5
£8 Post 99p

RELAYS. 12V DC £1.25p. 6V DC 85p.

BLANK ALUMINIUM CHASSIS. 6 x 4—£1.20; 8 x 6—£1.50; 10 x 7—£1.90; 12 x 8—£2.20; 14 x 9—£2.50; 16 x 6—£2.40; 16 x 10—£2.70.

ANGLE ALI. 6 x 3/4 x 3/4in—25p.
ALUMINIUM PANELS. 6 x 4—24p; 8 x 6—38p; 14 x 3—40p; 10 x 7—54p; 12 x 8—70p; 12 x 5—44p; 16 x 6—70p; 14 x 9—84p; 12 x 12—£1; 16 x 10—£1.16.

PLASTIC AND ALI BOXES IN STOCK. MANY SIZES
ALUMINIUM BOXES. 4 x 4 x 1 1/2 £1. 4 x 2 x 2 £1. 3 x 2 x 1 80p. 6 x 4 x 2 £1.30. 7 x 5 x 2 1/2 £1.45. 8 x 6 x 3 £2.20. 10 x 7 x 3 £2.50. 12 x 5 x 3 £2.30. 12 x 8 x 3 £3.

BRIDGE RECTIFIER 200V PIV 4 amp £1.50. 8 amp £2.50.
TOGGLE SWITCHES SP 30p. DPST 40p. DPDT 50p.
RESISTORS. 10Ω to 10M. 1/4W. 1/2W. 1W. 1p. 2W 10p.

HIGH STABILITY. 4w 2% 10 ohms to 1 meg. 8p.
Ditto 5%. Preferred values. 10 ohms to 10 meg. 3p.
PICK-UP CARTRIDGES SONATONE 9TAHC £2.50.
BSR Stereo Ceramic SC7 Medium £2. SC8 High £2.
PHILIPS PLUG-IN HEAD. AU1020 (G306 - GP310 - GP233 - AG3306 - AG3310) £2.
LOCKTITE SEALING KIT DECCA 118. Complete £1.
SOLDERING IRON 240V 40W £2.75.
VALVE OUTPUT Transformers (small) 90p.

CAR SPEAKERS on Baffles 7 x 4 1/2 x 1 1/2in deep, 4 ohms. Twin Units Bass and Treble 10 watts RMS. Door Mounting. Stereo pair £14.

IN-CAR GRAPHIC EQUALISER. Power Booster. Stereo 20 watts RMS per channel. 5 sliders Graphic Equalisation 5 1/2 wide x 7 1/2 deep x 2 in. high. 12 volt D.C. suitable for Car Radio or Cassette £30.




MINI-MULTI TESTER

Deluxe pocket size precision moving coil instrument, jewelled bearings—2000 o.p.v. Battery included. 11 instant ranges measure: DC volts 10, 50, 250, 1000. AC volts 10, 50, 250, 1000. DC amps 0-100mA. Continuity and resistance 0-1 meg ohms in two ranges. Complete with Test Prods and instruction book showing how to measure capacity and inductance.

£6.50 Post 65p

PANEL METERS £4 each

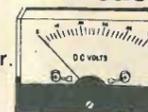50µa 100µa 500µa, 1ma, 5ma, 50ma, 25 volt, 50 volt, VU Meter. Facia 2 3/4 x 1 3/4 x 1 1/2in. Fixing hole 1 1/2in. dia. Lighting kit 6 or 12v 90p extra. 1ma (240° scale) 2 1/4in. sq. £5 Post 65p



RCS SOUND TO LIGHT CONTROL KIT

Kit of parts to build a 3 channel sound to light unit 1,000 watts per channel. Suitable for home or disco. £18 Easy to build. Full instructions supplied. Cabinet Post 65p £4.50 extra. Will operate from 200MV to 100 watt signal. 200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights, Edison Screw. 6 for £4, or 12 for £7.50. Post 65p.

"MINOR" 10 watt AMPLIFIER KIT £14

This kit is suitable for record players, guitars, tape playback, electronic instruments or small PA systems. Two versions available: Mono, £14; Stereo, £20. Post 65p. Specification 10W per channel; input 100mV; size 9 1/2 x 3 x 2in. approx. SAE details. Full instructions supplied. AC mains powered. Input can be modified to suit guitar.

RCS STEREO PRE-AMP KIT. All parts to build this pre-amp. Inputs for high, medium or low imp per channel, with volume control and PC Board £2.95 Can be ganged to make multi-way stereo mixers Post 65p

MAINS TRANSFORMERS

250-0-250V 70mA, 6.5V, 2A £4.50 £2.00
250-0-250V 80mA, 6.3V, 3.5A, 6.3V, 1A £5.00 £2.00
350-0-350V 250mA, 6.3V, 4A, 4A, CT, 5V, 2A £9.50 £2.00
300-0-300V 120mA, 2x 6.3V, 2A, CT, 5V, 2A £12.00 £2.50
220V 45mA, 6.3V, 2A £2.50 £1.00

GENERAL PURPOSE LOW VOLTAGE

Tapped outputs available
2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V £6.00 £2.00
1 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £6.00 £2.00
2 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £9.50 £2.00
3 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £12.50 £2.50
5 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £16.00 £2.50
12V, 100mA £1.30 80p
12V, 750mA £2.00 80p
10-0-10V 2a £3.00 £1
30V, 5a and 17V-0-17V, 2a £4.00 £2
0.5, 1, 10, 16V, 1/2a £2.50 80p
9V, 3a £3.50 £1
25-0-25V 2a £4.50 £1
30V, 1 1/2a £3.50 £1
6V 1/2a £2.00 £1
15-0-15V, 2a £3.75 £1
20V, 40V, 60V, 1a £4.00 £2
12V, 3a £3.50 £1
10V, 30V, 40V, 2a £3.50 £1
2 of 28 volt 1a £5.00 £2
20V, 1a £3.00 £1
20V, 0-20V, 1a £3.50 £1
9-0-9 volt 50mA £1.50 80p
2 of 18V, 6a £11.00 £2.50
12-0-12V, 2a £3.50 £1
9V, 1/2a £1.50 80p
32-0-32V, 6 1/2a £11.00 £2.50
500W £12 £2.50

AUTO TRANSFORMERS. 115V to 40V 150W £8 Post £2.50

CHARGER TRANSFORMERS RECTIFIERS
6-12 volt 3a £4.00 £2 6-12 volt 2a £1.10 80p
6-12 volt 4a £6.50 £2 6-12 volt 4a £2.00 80p

OPUS COMPACT SPEAKERS

FLUTED WOOD FRONTS

TEAK VENEERED CABINET

11 x 8 1/2 x 7in
50 to 14,000 cps. 15 watts 8 ohm

£20 pair Post £2

LOW VOLTAGE ELECTROLYTICS

ALL 10p
1 mfd, 2mfd, 4 mfd, 8 mfd, 10 mfd, 16 mfd, 25 mfd, 30 mfd, 50 mfd, 100 mfd, 250 mfd. All 15 vgts. 22 mfd/6v/10v; 25 mfd/6v/10v; 47 mfd/10v; 50 mfd/6v; 68 mfd/6v/10v/16v/25v; 100 mfd/10v; 150 mfd/6v/10v; 200 mfd/10v/16v; 220 mfd/4v/10v/16v; 330 mfd/4v/10v; 500 mfd/6v; 680 mfd/6v/10v/16v; 1000 mfd/2.5v/4v/10v; 1500 mfd/6v/10v/16v; 2200 mfd/6v/10v; 3300 mfd/6v; 4700 mfd/4v. ALL 10p.
500mF 12V 15p; 25V 20p; 50V 30p.
1000mF 12V 20p; 25V 35p; 50V 50p; 100V 70p.
2000mF 6V 25p; 25V 42p; 40V 60p; 1200mF 76V 80p.
2500mF 50V 70p; 3000mF 50V 85p; 2000mF 100V £1.
4500mF 64V £2. 4700mF 63V £1.20. 2700mF/76V £1.

HIGH VOLTAGE ELECTROLYTICS

8/450V 45p 8+8/450V 75p 32+32+16/350V 90p
16/350V 45p 8+16/450V 75p
32/500V 75p 20+20/450V 75p 100+100/275V 65p
10/500V £1.20 32+32/350V 50p 150+200/275V 70p
8/800V £1.20 32+32/500V £1.80 220/450V 95p
32/350V 50p 50+50/300V 50p 80+40/500V £2

TRIMMERS 10pF, 30pF, 50pF, 5p, 100pF, 150pF, 15p.
CAPACITORS 1pF to 0.01mF, 5p, Polystyrene 2 to 5000pF, 5p.
PAPER 350V 0.1 7p, 0.5 12p; 1mF 150V 20p; 2mF 150V 20p; 500V 0.01 to 0.05 12p, 0.1 15p; 0.25 25p; 0.47 35p.
MICRO SWITCH SINGLE POLE CHANGE OVER 20p.
SUB-MIN MICRO SWITCH, 25p. Single pole change over.
TWIN GANG, 120pF 50p; 500pF £1.
GEARED TWIN GANGS 25pF 85p, 365pF £1.
GEARED 365 + 365 + 25 + 25pF £1.
TRANSISTOR TWIN GANG, Japanese Replacement 50p.
NEON PANEL INDICATORS 250V 30p.
ILLUMINATED ROCKER SWITCH, Single pole, Red 65p.
WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 15p
CASSETTE MOTOR, 6 volt £1
CASSETTE MECHANISM, 12v Stereo Playback only £5
U.H.F. COAXIAL CABLE SUPER LOW LOSS, 25p yd.
COAX PLUGS 20p. COAX SOCKETS 20p.

BAKER LOUSPEAKERS

"SALE PRICES"

MODEL	INCHES	OHMS	WATTS	TYPE	PRICE
MAJOR	12	4-8-16	30	HI-FI	£12
DELUXE MK II	12	8-16	15	HI-FI	£12
SUPERB	12	8-16	30	HI-FI	£20
AUDITORIUM	12	8-16	45	HI-FI	£20
AUDITORIUM	15	8-16	60	HI-FI	£34
GROUP 45	12	4-8-16	45	PA	£12
GROUP 75	12	4-8-16	75	PA	£20
GROUP 100	12	8-16	100	PA	£20
GROUP 100	15	8-16	100	PA	£28
DISCO 100	12	8-16	100	DISCO	£20
DISCO 100	15	8-16	100	DISCO	£28

BAKER 50 WATT AMPLIFIER

£69 Post £2
Ideal for Halls/PA systems, Discos and Groups. Two inputs. Mixer, Volume Controls, Master Bass, Treble and Gain Controls. 50 watts r.m.s. Three loudspeaker outlets 4, 8, 16 ohms.



BAKER 150 WATT MIXER/POWER AMPLIFIER

Professional 4 inputs with volume controls. Will mix mics, decks, musical instruments, etc. £89 Slave version available £75 100 Volt Line £14 extra. Post £2.



FAMOUS LOUSPEAKERS

"SPECIAL PRICES"

MAKE	MODEL	SIZE	WATTS	OHMS	PRICE
SEAS	TWEETER	4in	50	8	£7.50
GOODMANS	TWEETER	3 1/2in	25	8	£4.00
AUDAX	TWEETER	3 1/2in	60	8	£7.50
SEAS	MID-RANGE	4in	50	8	£10.50
SEAS	MID-RANGE	5in	80	8	£10.50
SEAS	MID-RANGE	4 1/2in	100	8	£12.50
GOODMANS	FULL-RANGE	5 1/2in	15	8	£6.50
GOODMANS	FULL-RANGE	8in	30	8	£9.50
GOODMANS	AUDIOM 8p	8in	15	15	£8.50
GOODMANS	AUDIOM 8p	8in	15	15	£8.00
SEAS	WOOFER	8in	30	8	£14.00
RIGONDA	GENERAL	12in	50	8	£20.00
GOODMANS	AUDIOM PG	12in	60	8	£24.50
GOODMANS	PP12	12in	75	8/15	£20.00
GOODMANS	AUDIOM P	12in	50	8/15	£20.00
GOODMANS	GR12	12in	50	8/15	£27.50
GOODMANS	AUDIOM P	15in	50	15	£25.00

BATTERY ELIMINATOR MAINS TO 9 VOLT D.C.

Stabilised output, 9 volt 400 m.a. U.K. made in plastic case with screw terminals. Safety overload cut out. Size 5 x 3 1/4 x 2 1/2in. Transformer Rectifier Unit. Suitable Radios, Cassettes, models, £4.50. Post 65p

DELUXE SWITCHED VOLTS

MODEL STABILISED
3-6-7 1/2-9 volt 400ma DC max. Universal output plug and lead. Pilot light, mains switch, polarity switch £7.50. Post 65p.

TEAK VENEERED HI-FI SPEAKER CABINETS

For 13x8in. or 8in. speaker £10.50 Post £1.50
For 6 1/2in. speaker and tweeter £9.50 Post £1.50
Many other cabinets in stock. Phone your requirements
SPEAKER COVERING MATERIALS. Samples Large S.A.E.
LOUDSPEAKER CABINET WADDING 18in wide 25p ft.

CROSSOVERS. TWO-WAY 3000 c/s 3 or 8 or 15 ohm

£1.90. 3-way 950 cps/3000 cps. £2.20.
LOUDSPEAKER BARGAINS
3 ohm, 4in, 5in, 7x4in, £1.50; 6 1/2in, 8x5in, £3; 8in, £3.50.
8 ohm, 2 1/2in, 3in, 5in, £1.50; 6 1/2in, £3; 8in, £4.50; 12in, £6.
15 ohm, 3 1/2in, 5x3in, 6x4in, £1.50.
25 ohm, 3in, 5x3in, 7x4in, £1.50.
120 ohm, 3 1/2in dia, £1.50.

MOTOROLA PIEZO ELECTRIC HORN TWEETER

£6.50
Handles up to 100 watts. No crossover required. 4 or 8 or 16 ohm

BLACK PLASTIC CONSTRUCTION BOX

with brushed aluminium fascia. Sturdy job. Size 6 1/4 x 4 1/4 x 2in. £1.50

ECHO CHAMBER

Good quality unit with endless play tape cartridge. Stationary play heads ensure good reproduction and echo variance is achieved by changing tape speed. Input imp: 50k and 600 ohms. Power: 240 volts A.C. £68. Post £2 Spare tape £5.



ALUMINIUM HEAT SINKS. FINNED TYPE.

6 1/2" x 2" x 2 1/4" 65p.
JACK PLUGS Mono Plastic 25p; Metal 30p.
JACK PLUGS Stereo Plastic 30p; Metal 35p.
JACK SOCKETS. Mono Open 20p; Closed 25p.
JACK SOCKETS Stereo Open 25p; Closed 30p.
FREE SOCKETS - Cable end 30p.

FREE SOCKETS - Cable end 30p.
2.5mm and 3.5mm JACK SOCKETS 15p.
2.5mm and 3.5mm JACK PLUGS 15p.
DIN TYPE CONNECTORS
Sockets 3-pin, 5-pin 10p. Free Sockets 3-pin, 5-pin 25p.
Plugs 3-pin 20p; 5-pin 25p.

PHONO PLUGS and SOCKETS ea. 10p.
Free Socket for cable end ea. 15p.
Screened Phono Plugs ea. 15p.
TV CONVERGENCE POTS 15p each
Values = 10, 20, 50, 100, 200, 250, 470, 2000 ohms.

DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy to build kit. Controls up to 480 watts AC mains £3. Post 65p.
DE LUXE MODEL READY BUILT 800 watts plus Photo Electric Sunset "On" feature. Front plate fits standard box £4.

TELEPRINTER TYPE 7B: Pageprinter 24v. d.c. power supply. Speed 50 bauds per min. S/hand, good cond. (no parts broken), £28.75. OR G.P.O. MODEL, as above except motor, 110/230v. a.c., £34.50. Carriage either type £9.50. Send S.A.E. for list of Teleprinter spares available.

TS.147 RADAR TEST SET Combination Sig. generator and frequency meter and power meter. Provides C.W. and F.M. signals, 115v. a.c., £225. Carr. £7.

HEWLETT PACKARD Signal Generator HP608B. Freq. 10-400MHz C.W. and A.M. Output 1 microvolt to 8v. 50. Mod. 400-1000Hz. 230v. a.c., £225. Carr. £10.

TRANSISTORISED 3cm. RADAR AMPLIFIER SWITCH: with 24v. waveguide switch, 9 x 4cm ins. with crystal CV.2355 and spark gap VX 1046, £17.95 + £1 post.

INSULATION TEST SET 0 to 10KV, negative earth, with Ionisation Amplifier, 100/230 volts a.c., £48.87 + carr.

BC-221 FREQUENCY METER: 125-20,000kc/s, complete with original calibration charts, £24.15 + carr.

ROTARY INVERTER TYPE: PE218E: Input 24-28V DC, 80 amps, 4,800r.p.m. Output 11v AC, 13 amp 400 c/s. 1Ph. P.F. 9. £23 + carr.

RESONATOR PERFORMANCE CTC 424 8.5 to 9.0 kmc/s 3 cm, £80.50 + post £2.

INVERTER 24v. DC input 400 cycles IpH 6600 r.p.m. 200v, peak, £8.05 + £2 post.

OXYGEN BOTTLE 1800lb, w.p. £11.50 + carr.

NOISE SOURCE UNIT with CV.1881 noise source mount. Produces thermal noise 15.5dB 200/250v. AC. £80.50.

HS33 HEADSET. Low imp. £5.35 + 75p post.

MURHEAD DECADE OSCILLATOR TYPE 890D, £92 + carr. £5.

SIEMENS POWER METER REL3U/84/AB: 0-12kHz 1mw 500mw 6 ranges. 0.17dB 50 ohms, £92 + carr.

CV.1596 CATHODE RAY TUBE: (09D, 09G), 4in. screen, green electrostatic base B12B, HT1200 volts, heater 4 volts, £11.50.

VACUUM AND PRESSURE DEAL TEST EQUIPMENT: complete with 2 x 4in. gauges indicating 0.20lb. p.s.i. 0.30lb. vacuum. With stand, hand pump, etc., £34.50 + carr.

TELEPRINTER MODEL 75, available with perforator attachment, £74.75 + £10 carriage.

DIGITAL CLOCKS MODEL 304 with automatic recorder. Printout system model 301. £86.25 + £10 carriage.

SPERRY TRANSISTORISED SERVO-AMPLIFIERS TYPE C1 with circuit diagram, £11.50 + £1.50 post.

X-Y PLOTTER, £74.75 + £7 carriage.

BARGAIN MAPS
Large stocks of unused U.S.A.F. surplus maps, weather charts, etc. including:

ONC-E1 — U.K. in full and part N.W. Europe. Scale 1:1,000,000.
JNC-9N — N. Europe, U.K., Scandinavia. Scale 1:2,000,000.
JN-21N — Europe (Mediterranean). Scale 1:2,000,000.
SIZE 58" x 42" colour. Many others. Please send S.A.E. for list.
Price each 75p (inc. P&P)
25 x Maps (either same type OR assorted), £10 + £1.60 P&P.
10 x Maps (either same type OR assorted), £6.50 (in. P&P).

All prices include VAT at 15%
Carriage quotes given are for 50-mile radius of Herts.

W. MILLS

The Maltings, Station Road
SAWBRIDGEWORTH, Herts.
Tel: Bishop's Stortford (0279) 725872

ELECTRONIC VALVES WANTED

All Types Receiving, Transmitting, Industrial

PL504 — PL802 — PCL805 — CV131 — CV136 —
CV138 — CV329 — CV345 — CV450 — 805 —
807 — 813 — 2K25, Etc.

Phone/write to:
PYPE HAYES RADIO LTD.
606 Kingsbury Road
Birmingham B24 9PJ
021-373 4942

WW — 070 FOR FURTHER DETAILS



LOW VOLTAGE POWER DRILLS AND ACCESSORIES

Illustration shows Titan Drill and Stand (Price £27 inc. VAT and Postage) which is One of the combinations which can be purchased from our comprehensive range of Drills and Accessories.
Prices from £8.34 (Reliant Drill only) inc. VAT and Postage.
Send 25p for Catalogue.

A. D. BAYLISS & SON LTD.
PFERA WORKS, REDMARLEY
GLOUCESTER GL19 3JU
Barclaycard, Access Welcome
Tel. Bromesberrow (053 181) 273

PRINTED CIRCUITS FOR WIRELESS WORLD PROJECTS

- | | |
|--|---------------------|
| U. h. f. television tuner—Oct. 1975—1 d.s. | £8.50 |
| Stripline r.f. power amp—Sept. 1975—1 d.s. | £5.00 |
| Audio compressor/limiter—Dec. 1975—1 s.s. (stereo) | £4.25 |
| F.m. tuner (advanced)—April 1976—1 s.s. | £5.00 |
| Cassette recorder—May 1976—1 s.s. | £5.00 |
| Audio compander—July 1976—1 s.s. | £4.25 |
| Time code clock—August 1976—2 s.s. 3 d.s. | £15.00 |
| Date, alarm, b.s.t. switch—June 1977—2 d.s. 1 s.s. | £9.50 |
| Audio preamplifier—November 1976—2 s.s. | £8.50 |
| Additional circuits—October 1977—1 s.s. | £4.00 |
| Stereo coder—April 1977—1 d.s. 2 s.s. | £8.50 |
| Morse keyboard and memory—January 1977—2 d.s. (logic board 10 1/4 in. x 5 in.) (keyboard and matrix 13 in. x 10 in.) | £14.00 |
| Low distortion disc amplifier (stereo)—September 1977—1 s.s. | £2.00 |
| Low distortion audio oscillator—September 1977—1 s.s. | £3.50 |
| Synthesized f.m. transceiver—November 1977—2 d.s. 1 s.s. | £12.00 |
| Morsemaker—June 1978—1 d.s. | £4.50 |
| Metal detector—July 1978—1 d.s. | £3.75 |
| Oscilloscope waveform store—October 1978—4 d.s. | £18.00 |
| Regulator for car alternator—August 1978—1 s.s. | £2.00 |
| Wideband noise reducer—November 1978—1 d.s. | £5.00 |
| Versatile noise generator—January 1979—1 s.s. | £5.00 |
| 200MHz frequency meter—January 1979—1 d.s. | £7.00 |
| High performance preamplifier—February 1979—1 s.s. | £5.50 |
| Distortion meter and oscillator—July 1979—2 s.s. | £5.50 |
| Moving coil preamplifier—August 1979—1 s.s. | £3.50 |
| Multi-mode transceiver—October 1979—10 d.s. | £35.00 |
| Amplification system—October 1979—3 preamp 1 poweramp | (£4.20 each) £16.00 |
| Digital capacitance meter—April 1980—2 s.s. | £7.50 |
| Colour graphics system—April 1980—1 d.s. | £18.50 |
| Audio spectrum analyser—May 1980—3 s.s. | £10.50 |
| Multi-section equalizer—June 1980—2 s.s. | £8.00 |
| Floating-bridge power amp—Oct. 1980—1 s.s. (12V or 40V) | £4.00 |
| Nanocomp—Jan. 1981—1 d.s. 1 s.s. | £9.00 |
| Logic probe—Feb. 1981—2 d.s. | £6.00 |

Boards are glassfibre, roller-tinned and drilled. Prices include V.A.T. and U.K. postage.
Airmail add 20%, Europe add 10%, Insurance 10%.
Remittance with order to:
M. R. SAGIN, 23 KEYES ROAD, LONDON, N.W.2

WW — 040 FOR FURTHER DETAILS

Digital Video Noise Measurement System

The Digital D4066 Noise Measurement System offers an accurate and economical method of measuring video signal to noise ratio on broadcast or industrial TV systems.



£580 + vat

Accurate to ± 1.5dBs from 20dBs to 80dBs

- Measures signal to noise ratio down to 65dBs SNR
- Field interval SNR measurements are possible with the D4060 option 01
- SNR measurement is possible in the presence of sync pulses, some test signals or free running
- Visual display on oscilloscope ensures measurement confidence
- Full CCIR weighting filter sets are available

DIGI-TEL ELECTRONICS 20 Trenches Road
Crowborough, Sussex
Tel: Crowborough 5069

WW — 075 FOR FURTHER DETAILS



Communications 82

National Exhibition Centre
Birmingham, England
20-23 April 1982

Your Opportunity to Sell Communications Equipment and Systems

Communications 82 will be the sixth in a biennial series of expositions - now recognised as the World's leading international events for selling communications equipment and systems. It comprises a major international exhibition and integral conference plus a programme of social events with guest speakers of international stature.

Communications 82 will be a total communications exposition, covering all systems, equipment and components used in communications, including transmission, switching and terminal equipment as well as associated products and services for recording, testing and maintenance.

Communications 82 will be total also in user appeal, spanning the boundaries between civil and military, public and private, industry and commerce, fixed and mobile, in the same way as do the technologies involved.

Communications 82, therefore, offers a unique opportunity for you to sell your products to potential customers from all over the world - at Communications 80 there were well over 16,000 visitors from 70 countries.

If you manufacture or sell communications equipment and systems nationally or internationally, you cannot afford not to participate in Communications 82 - the total communications exposition.

- + PUBLIC TELEPHONE EQUIPMENT
- RIVATE TELEPHONE EQUIPMENT
- + LASERS + FIBRE OPTICS
- TELETEXT + SATELLITES + MICROWAVE
- + GENERATORS + COMPUTERS
- MOBILE RADIO + RADIO PAGING + WAVEGUIDES
- + FACSIMILE +
- BATTERIES + ANTENNAS
- CABLES + TERMINAL EQUIPMENT
- POINT-TO-POINT RADIO
- DATA COMMUNICATIONS
- TELEVISION TRANSMISSION + SWITCHING AND ROUTING
- ... AND MUCH, MUCH, MORE

Complete, detach and post to:

Terry Brandon, Sales Manager
Industrial and Trade Fairs Limited
Radcliffe House, Blenheim Court
Solihull, West Midlands B91 2BG
England

Tel: 021-705 6707 Telex: 337073

Communications 82 is organised by
Industrial and Trade Fairs Limited for
Tony Davies Communications

I am interested in exhibiting at Communications 82.
Please send me the full Data Pack.

Name

Position

Company

Address

Tel: Telex:



Professional ASCII Keyboards



ONLY £29.95
ADD P&VAT
SCOOP

THE 'APPLE' COMPUTER KEYBOARD

- 52 key 7-bit ASCII Coded
- Positive Strobe, +5v -12v.
- Full ASCII Characters
- Parallel output with Strobe.
- Power Light on Control
- National MM5740 Chip, TTL Output
- Superbly made, size 12x5.5x1.5in.
- Black keys with white legends
- Escape, shift, return and reset keys Complete with Circuit and Data

Ideal for use with TANGERINE, TRITON, TUSCAN, APPLE and most computers.

Ex-stock from Henry's.

This is definitely the BEST BUY. Supplied BRAND NEW in manufacturer's original packing (ANTI-STATIC). Just post remittance, total £35.95 (incl. VAT & Post).



Henry's

Computer Kit Division

404 Edgware Road, London W2 1ED, England I.E.D. 01-402 6822

FACTORY CLEARANCE SERVICES CO.

A GRAND CLEARANCE SALE OF NEW COMPUTER SPARES WILL BE HELD AT OUR CODICOTE WAREHOUSE ON SATURDAY, 4th APRIL AND SATURDAY, 11th APRIL

COMPRISING OF:

- Keyboards from £10
- Teletype Printers Type 35
- Power Supply units, 5v, 10v, 12v, 18v, 24v, 1-amp to 20-amp from £7.50
- 10-Tonne of Electric Motors from 50p ea.
- Fans and Blowers from £2
- 5-Tonne of Transformers from £1

Plus: Resistors, Capacitors, Semiconductors, Rectifiers, Solenoids, Relays and thousands of electrical and mechanical assemblies. Jumbo bags of mixed components £5

Come along and browse, bring your own sandwiches!

A. R. DAVIES (FACTORY CLEARANCE)

28 ST ALBANS ROAD, CODICOTE
NR. OLD WELWYN, HERTS

TEL: STEVENAGE (0438) 833417-820686

WW-074 FOR FURTHER DETAILS

B. BAMBER ELECTRONICS

Dept. WW, 5 STATION ROAD, LITTLEPORT, CAMBS, CB6 1QE
Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

Type	Price	Type	Price	Type	Price	Type	Price
AC107	0.25	BC207	0.15	BFX84	0.24	T1534	0.35
AC126	0.33	BC208	0.15	BFX85	0.24	T1720	0.10
AC128	0.34	BC212	0.10	BFX86	0.25	T1762	0.47
AC141	0.25	BC212A	0.15	BFX87	0.25	T17270	0.30
AC142K	0.32	BC213	0.10	BFX88	0.25	T17853	0.30
AC185	0.62	BC214	0.12	9LY36	9.99	TX107	0.10
AC188	0.32	BC239	0.10	9SV64	0.89	TX108	0.10
AC177	0.94	BC237	0.18	9SV68	0.40	TX109	0.10
AC178	0.72	BC337	0.15	9SX20	0.25	TX196	0.20
AC179	0.80	BC360	0.35	9SX21	0.25	TX212	0.15
AC220	0.65	BCW35	0.25	9SY27	0.27	TX300	0.14
AC221	0.78	BCX32	0.24	9SY38	0.20	TX312	0.39
AC244	0.32	BCY90	1.34	9SY95A	0.24	TX313	0.39
AD143	0.35	BF151	1.34	9SY248	0.33	TX314	0.43
ADY23	1.82	BCY33	1.34	9SX384	0.84	TX320	0.76
ADY25	7.60	BCY34	1.60	BUI05	1.84	TX321	0.76
AF114	4.50	BCY70	1.18	BUI08	1.84	TX302	0.18
AF124	3.38	BCY71	0.20	MP3731	3.29	T6210	0.46
AF211	5.57	BCY72	1.18	OC10	2.52	T6220	0.46
AF212	5.57	OCY87	5.35	OC15	2.52	T6221	0.46
ASYS2	0.80	BCY88	3.99	OC20	2.52	T6371	0.97
ASZ15	2.15	OCY99	3.99	OC22	2.52	T6404	0.81
ASZ16	2.12	BO116	0.82	OC23	2.52	T6441	7.60
AV10	1.29	BO121	1.85	OC24	2.52	T6456A	3.60
BC107	0.10	BO144	1.40	OC25	2.52	T6696	0.35
BC107B	0.12	BOY11	0.87	OC28	2.52	T6697	0.35
BC108	0.12	BOY60	2.90	OC29	2.52	T6706	0.21
BC108A	0.12	BF150	0.25	OC35	1.99	T6798	0.48
BC109	0.12	BF152	0.25	OC42	0.30	T6711	0.35
BC109B	0.12	BF158	0.20	OC44	0.35	T6711A	0.86
BC113	0.18	BF159	0.20	OC45	0.40	T6918	0.80
BC115	0.17	BF160	0.20	OC70	0.56	T6930	0.32
BC125	0.18	BF164	0.20	OC71	0.47	T61100	3.21
BC136	0.14	BF173	0.27	OC74	0.47	T61302	0.78
BC143	0.24	BF178	0.27	OC75	0.47	T61303	0.89
BC147	0.10	BF185	0.27	OC76	0.35	T61304	0.67
BC147B	0.10	BF191	0.10	OC77	0.58	T61307	0.90
BC153	0.15	BF196	0.10	OC81	0.37	T61495	0.80
BC154	0.15	BF200	0.28	OC82	0.60	T61531	7.41
BC157	0.12	BF248B	0.32	OC83	0.60	T61554	8.59
BC158	0.12	BF251	0.25	OC84	0.60	T61555	8.62
BC171	0.12	BF258	0.25	OC89	2.05	T61613	0.25
BC171A	0.16	BF259	0.32	OC170	1.26	T62082	9.25
BC172B	0.12	BF263	0.32	OC171	1.35	T62193	0.55
BC177	0.18	BF276	0.60	OC200	2.60	T62219	0.43
BC179	0.18	BF300	0.22	OC201	2.60	T62220	0.14
BC179A	0.20	BFY10	0.80	OC202	2.60	T62222A	0.22
BC179	0.20	BFY50	0.25	OC203	2.60	T62366	0.65
BC182A	0.12	BFY51	0.25	OC204	2.60	T62369	0.18
BC183	0.13	BFY52	0.25	OC271	0.55	T62476	0.56
BC183B	0.12	BFY57	0.40	OP951	0.55	T62643	0.35
BC184	0.12	BFY70	1.59	SE3001	0.29	T62804	0.35
BC184	0.10	BFY90	0.80	SE4001	0.40	T62904A	0.35
BC186	0.29	BFX13	0.48	TIP36	1.28	T62905A	0.35
		BFX29	0.29				

CAMPORE LONG TERM DISPOSABLE ELECTRODES

Packed in boxes of 100, size 4mm, approx 80,000 in stock. **Any Offers**

MONITOR CATHODE RAY TUBES

M2B-233 GH, M3B-100LG, M2B-13W. All brand-new and boxed. **£10 each**

MAINS ISOLATING TRANSFORMERS

500VA 240v in 240v C.T. Output. Enclosed in metal boxes, used but in good condition. **£15 each**

MAINS TRANSFORMERS

240v in 24v at 25A output. Ideal for soldering iron bench supply. **£15 each**

COLOUR T.V. MAINS INPUT FILTER CHOKES

Approx 1,000 **Any offers**

HELLERMAN HEAT SHRINK SLEEVING

Size LVR95 10mm. Colour black, length 150M reel. **£10**

LARGE QUANTITY OF USED LIN BINS

All sizes. **Half Normal Price.**

PYE ATU4 AERIAL TUNER UNIT

2.9mhz, tapped coil, input via SO239. Totally enclosed in metal box 13in x 5in x 7in. BRAND NEW. **Only £8 each**

FERRANTI MICROSPOT CATHODE RAY TUBES

Type 3H/1010, suitable for photographic multi-channel recorder systems. Fitted with a mounting collar and prism cemented to the faceplate, screen aluminised, Phosphor P. The tubes are also fitted with mounting units type MU1053 and deflection coil type SC48A. **Few only at £55 each**

AVO 8 MOVEMENTS COMPLETE WITH SCALE

Ex. Equipment Ministry type. **£8 each**

RIBBON CABLE

10 way decimal coded, 5 metres for **£1.25**

TELESCOPIC RADIO AERIALS

9 section, extends to 24in long, collapses to 4 1/2in. **Price £1 each**

VIDICON SCAN COILS

(Transistor type, but no data) To fit 1in tube, complete with vidicon base. **£3.50 each**

PYE WESTMINSTER

W30AM, low band, sets only, no control gear, complete and in good condition. **£45 each**

PYE WESTMINSTER

W15AM low bands, sets complete and in good condition but are less speakers, mikes, cradles and LT leads. (Sets only.) **£70 each**

PYE BASE STATION

F30AM low band. **Prices from £220 each**

A.C. ADAPTOR (Battery Charger)

120vac input, 5.8 vdc at 200mA output. USA type mains plug to 3.5mm jack plug, brand new and boxed. **£1.25 each**

A.C. ADAPTOR (Battery Charger)

117 vac input, 4.5 vdc at 150mA output. USA type mains plug to 2.5mm jack plug. Brand-new and boxed. **£1 each**

ISEP SLOTTED HORIZONTAL RAIL

Available in 9ft lengths. **£4 each**

WATCH STRAPS

Black stainless steel, 50p each. Black plastic 25p each, watch spring bars 10p each. **Discount for quantity.**

DATA DYNAMICS MODEL ASR 390

240v operation, complete with punch and reader, good condition. **£350**


CB ACCESSORIES

S.a.e. for catalogue and price list.

TERMS OF BUSINESS: Cheques or P.O. with order, made payable to B. Bamber Electronics, or phone your Access or Barclaycard No. Please add 15% VAT on all goods advertised after adding postage as applicable
CARRIAGE: Orders under £5 nett invoice add 75p. Orders over £5 but less than £20 add 50p. Orders over £20 at cost. **Callers welcome.**
Tues-Sat. 9.30 a.m.-5.30 p.m.

WW-063 FOR FURTHER DETAILS

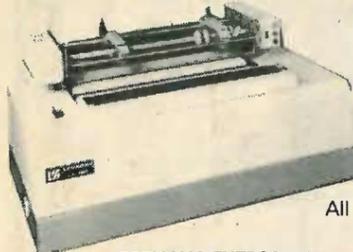THE PRINTER SCOOP OF THE YEAR, SAVE OVER £1400 THE LOGABAX Z80 MICROPROCESSOR CONTROLLED LX 180L MATRIX PRINTER



A massive bulk purchase enables us to offer you this superb professional printer at a fraction of its recent cost of over £2000. Utilising the very latest in microprocessor technology, it features a host of facilities with all electronics on one plug in PC.B. Just study the specification and you will instantly realise it meets all the requirements of the most exacting professional or hobbyist user.

STANDARD FUNCTIONS ★ Full ASCII character set ★ Standard ink ribbon ★ RS232C/V24 serial interface - 7 xtal controlled baud rates up to 9600 ★ Parallel ports interface ★ Handshakes on serial and parallel ports ★ 4 Type fonts, italic script, double width, italic large, standard ★ Internal buffer ★ Internal self test ★ 170 CPS ★ Variable paper tractor up to 175" wide ★ Solid steel construction ★ All software in 2708 eeproms easily reconfigured for custom fonts etc.


All this and more, **not** refurbished but BRAND NEW

At Only **£525** + carriage and ins. **£18.00 + VAT**

OPTIONAL EXTRAS ★ Lower case £25.00 ★ 16K buffer £30.00 ★ Second tractor for simultaneous dual forms £85.00 ★ Teak finished floor stand £35.00 (+£8.50 carriage) ★ Logabax maintenance P.O.A. All prices subject to VAT - AVAILABLE ONLY FROM:

ELECTRONICS 64-66 Melfort Rd, Thornton Heath Croydon, Surrey, 01-689 7702/6800 Telex 27924 Ref Fisher & **COMPUTER APPRECIATION** 86 High Street, Bletchingley Surrey 0883 843221

MAINS INTERCOM

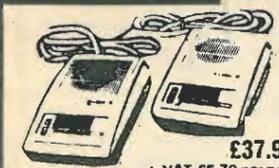

£37.99

+ VAT £5.70 per pair

NO BATTERIES, NO WIRES. Made to high Safety and Telecommunications Standard. The modern way of instant 2-way communications. Just plug into power socket. Ready for use. Crystal clear communications from room to room. Range 1/4 mile on the same mains phase with call buzzer and light indicator. On-off switch. Volume control. Useful as inter-office intercom between office and warehouse, in surgery and in homes, between house and garage. Also useful as burglar alarm. 6 months' service guarantee. P&P £1.95. Also F.M. 2-channel model £55.95 + VAT £8.40 + P&P £2.15 per pair.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



ONLY £18.95

+ VAT £2.85

+ P&P £1.65

New improved battery operated Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates on/off switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increases efficiency in office, shop, workshop. Perfect for conference calls, leaves the user's hands free to make notes, consult files. No "holding on", save money and long-distance calls. Volume control. Model with conversation recording facilities. Price £20.95 + VAT £3.15, post and packing for other model £1.65.

10 days' price refund guarantee. Barclaycard and Access welcome. **WEST LONDON DIRECT SUPPLIES (WW)** 169 KENSINGTON HIGH STREET, LONDON W8 6SN. TEL. 01-937 5548

TV TUBE REBUILDING

Faircrest Engineering Ltd., manufacture a comprehensive range of equipment for processing all types of picture tubes, colour and mono. Standard or custom built units for established or new businesses. We export world-wide and have an excellent spares service backed by a strong technical team.

Full training courses are individually tailored to customers' requirements.

For full details of our service contact Neil Jupp

FAIRCREST ENGINEERING LTD.

Willis Road, Croydon, CRO2XX. 01-684 1422/01-684 0246


WW - 073 FOR FURTHER DETAILS

READ ALL ABOUT IT - all the latest on home entertainment equipment and ideas in . . .

HI FI YEARBOOK AND HOME ENTERTAINMENT 1981

Published again in November, this new 1981 edition in larger magazine size means more comprehensive coverage of the whole range of home entertainment equipment, from aerials to headphones, from microphones to video recorders and from radios to electronic organs. Backed by authoritative articles on developments in the world of Hi Fi, plus details of stockists, Hi Fi Yearbook and Home Entertainment 1981 is essential reading for enthusiasts and buffs. Available from leading newsagents and bookshops from 1st November 1980. Price £3.00.

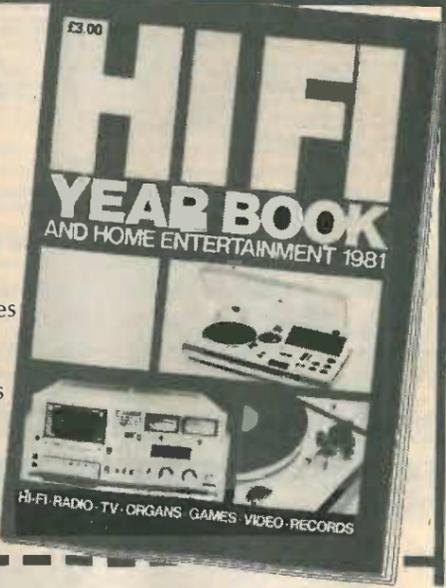If you have difficulty in obtaining your copy order direct from the publishers @ £3.50 inclusive.



ORDER FORM

To: General Sales Manager, Room 205, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS.

Please send me copy/copies of the Hi Fi Yearbook and Home Entertainment 1981 @ £3.50 including postage and packing. Cheque/postal order should be made payable to IPC Business Press Ltd.

Name _____ (please print)

Address _____


Registered in England No. 677128.

WWW

RADIATION DETECTORS

BE PREPARED WITH THIS DETECTOR

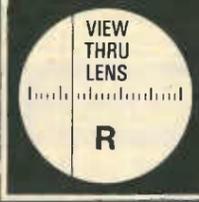Recommended for General use. CIVIL DEFENCE • FIRE SERVICES • MEDICAL



- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS.
- UNIT IS SIZE OF FOUNTAIN PEN AND WILL CLIP IN TOP POCKET.
- PRECISION INSTRUMENT, METAL CASED, WEIGHT 2oz.
- CONTAINS 3 LENSES. ■ RUGGED CONSTRUCTION.
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH.

COMPLETE WITH DATA

British design and manufacture. Tested, calibrated and guaranteed. Ex-stock delivery by return.

Standard model 0-5 or 0-50R ONLY

£6.95 inc. VAT Post & Packing 60p

Be prepared, buy whilst available.

HENRY'S

404 EDGWARE ROAD, LONDON W2 1ED



The larger catalogue that means

- FREE POSTAGE IN U.K.
- ADDITIONAL DISCOUNTS
- KEEN PRICES
- GUARANTEED SATISFACTION
- GOOD STOCKS - GOOD DELIVERY
- We pay postage

68 LARGER PAGES

Semi-Conductors • I.C.s • Opto-devices • Rs and Cs in great variety • Pots • Switches • Knobs • Accessories • Tools • Materials • Connectors

FREE FOR THE ASKING

ELECTROVALUE LTD.

(WW2), 28 St. Jude's Road, Englefield Green, Egham, Surrey (London 87) ST0 0784. Phone: 33603 (London 87) ST0 0784. Telex 264475
 NORTHERN BRANCH (Personal Shoppers Only): 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945

ALWAYS - A CHANGING RANGE OF OSCILLOSCOPES, COMPUTERS, TERMINALS ETC.

- Item No.
- 1 TEKTRONIX STORAGE OSCILLOSCOPE Type 434. Current Model. As new. 12 months warranty (No warranty £1,400) £1,850
 - 2 TEKTRONIX STORAGE OSCILLOSCOPE type 564 with 3A6 & 3B4 £250
 - 3 HAMEG OSCILLOSCOPE type 412. Dual Trace 10MHz £200
 - 4 TELEQUIPMENT OSCILLOSCOPE type D61A. Dual Trace 10MHz £200
 - 5 SCOPEX OSCILLOSCOPE type 4D10. Dual Trace 10MHz £170
 - 6 HEWLETT PACKARD OSCILLOSCOPE type 120B (X-Y) £120
 - 7 MARCONI WAVE ANALYSER TF2330. Good condition £150
 - 8 AVO UNIVERSAL BRIDGE B150 with adaptor A151 £80
 - 9 ADVANCE SIGNAL GENERATOR type E2 100KHZ-100MHZ £40
 - 10 B & K AUTO VIBRATOR EXCITER CONTROL type 1018 £50
 - 11 SOLARTRON Digital Voltmeter type LM1450 £20
 - 12 SOLARTRON PULSE GENERATOR type G0101.2 £40
 - 13 ADVANCE V.H.F. Millivoltmeter type VM79 - No probes £35
 - 14 ADVANCE A.F. SIGNAL GENERATOR type J2 £25
 - 15 KNIGHT RF Sig Gen KG686 with Sweep Marker Gen KG687. The Pair £90
 - 16 ADVANCE Audio Signal Generator HIE 15HZ to 50KHZ £45
 - 17 BELLAH VIDEO MONITOR £90
 - 18 LYONS PULSE GENERATOR type PG-2E £45
 - 19 COSSOR SINE-SQUARE WAVE GENERATOR 20HZ-1MHZ £40
 - 20 AVO UNIVERSAL BRIDGE Type 1 £75
 - 21 P.S.I. RMS VOLTMETER type A1301 £90
 - 22 LABGEAR 825 COLOUR MATCH GENERATOR CM 6004-PG £30
 - 23 ADVANCE LF OSCILLATOR type SG65A £75
 - 24 TAYLOR AM/FM SIGNAL GENERATOR type 62A Mk II £125
 - 25 MARCONI UNIVERSAL BRIDGE type TF1313 1/4% £200
 - 26 MARCONI WIDE RANGE OSCILLATOR type TF1370 10HZ-10MHZ £30
 - 27 SOLARTRON TRUE RMS VOLTMETER type VM1484 £75
 - 28 RANK V.H.F. SIGNAL STRENGTH INDICATOR £25
 - 29 RACAL COUNTER ELECTRONIC FREQUENCY 32MHZ type 836 £75
 - 30 WAYNE KERR CAPACITANCE BRIDGE type 8541C £40
 - 31 WAYNE KERR COMPONENT BRIDGE type B121 £45
 - 32 HEWLETT PACKARD DC CURRENT SOURCE type 6181B 0-100V; 0-250MA £175
 - 33 MARCONI SAUNDERS LEVELLING AMPLIFIER type 6587 £175
 - 34 TEKTRONIX PRE TRIGGER PULSE GENERATOR type 111 £85
 - 35 RACAL H.F. SELECTOR ANALYSER type 9056 £375
 - 36 MARCONI STANDARD SIGNAL GENERATOR type TF144H 10KHZ-72MHZ £225
 - 37 SCHULMBERGER/SOLARTRON AUTOMATIC COUNTER type FB2602 £150
 - 38 BRANDENBURG PHOTOMULTIPLIER POWER UNIT 0-2500Volts £90
 - 39 SCHULMBERGER/SOLARTRON COMPUTING VOLTMETER type JM1776 £90
 - 40 HEWLETT PACKARD AC CONVERTOR type 3461A £90
 - 41 MURHEAD W.K.134-A 30-310HZ £50
 - 42 PHILIPS COMPARATOR 278KHZ £50
 - 43 HEATHKIT CAPACITOR CHECKER IT-28 £25
 - 44 HEWLETT PACKARD DIGITAL VOLTMETER type 3440A £60
 - 45 HEWLETT PACKARD FREQUENCY CONVERTOR type 8729A £130
 - 46 RACAL AUTO FREQUENCY CONVERTOR type 803R 500MHZ £70
 - 47 AIRMEC ELECTRONIC VOLTMETER type 314A £75

- 48 VARIAN RUBIDIUM FREQUENCY STANDARD 100KHZ/1MHZ/5MHZ £600
- 49 KEITHLEY INSTRUMENTS REGULATED HIGH VOLTAGE SUPPLY TYPE 241 Accuracy +/- 0.55% or 1mm £250
- 50 T.O.A. ELECTRONIC POLYRECORDER type EPR-2T £90
- 51 STODDARD AIRCRAFT Radio Interference and Field Intensity Meter type NM-52A 375-1000MHZ (2 pieces) £275
- 52 TAYLOR VALVE TESTER type 45D £45
- 53 RHODE & SCHWARZ UHF TEST RECEIVER BN1523 280-940MHZ (4600MHZ) £120
- 54 R & S Z-g DIAPHRAGM 300-2400 MHZ BN3562 £85
- 55 R & S Unbalanced Standard ATTENUATOR BN18042/50 £45
- 56 R & S VHF-ET CAPACITANCE METER 30-3000MHZ BN442 £60
- 57 R & S DIRECT CAPACITANCE METER BN5201 £50
- 58 WAYNE KERR UNIVERSAL BRIDGE type B521 (CT375) £75
- 59 B & K HETERODYNE VOLTMETER type 2005 £250
- 60 HEWLETT PACKARD CLIP ON DC MILLIAMPMETER type 428A with probe £70
- 61 SOLARTRON DIGITAL VOLTMETER type LM1420.2 £30
- 62 SOLARTRON DIGITAL VOLTMETER type 1420.2 with Mean AC Unit £35
- 63 SOLARTRON DIGITAL VOLTMETER type 1967 £55
- 64 MARCONI SIGNAL GENERATOR type TF935A/3/S (CT402) £225
- 65 JARROLD SWEEP GENERATOR 20-112 MHZ £40
- 66 HEWLETT PACKARD VALVE VOLTMETER type 412A £35
- 67 HATFIELD SELECTIVE LEVEL METER type 1001 £90
- 68 COSSOR NOISE LEVEL METER CT454 £18
- 69 HEATHKIT DECADE RESISTANCE BOX DR1U £10
- 70 MARCONI VARIABLE ATTENUATOR type TF1073A/S (CT421) £40
- 71 ROCHAR UNIVERSAL COUNTER TIMER type A1149 £40
- 72 WAYNE KERR UNIVERSAL BRIDGE type B221 £50
- 73 WAYNE KERR AF SIGNAL GENERATOR type S121 10HZ-120KHZ £60
- 74 SIGNAL GENERATOR type Q103B £20
- 75 CLARE FLASH TESTER type CT344 0.1HZ-10MHZ £15
- 76 MARCONI RF ATTENUATOR type TF1073A £35
- 77 HEATHKIT VALVE MILLIVOLTMETER AV-3U £15
- 78 TELONIS SWEEPER 450-900MHZ £55
- 79 COSSOR SWEEP OSCILLATOR type CT202 £20
- 80 WEIR DIGITAL VOLTMETER type 500 Mk 3 £20
- 81 AIRMEC AM/FM SIGNAL GENERATOR type 204 1-320MHZ £130
- 82 HATFIELD TRANSISTORISED SELECTIVE LEVEL METER SPO 7820 £90
- 83 S.T.C. LEVEL MEASURING SET type 74309B £90
- 84 AVO TRANSISTOR ANALYSER type CT446 £20
- 85 SIEMENS SUPERHER RECEIVER 30HZ-1MHZ £35
- 86 R & S MICROWAVE POWER METER BN2412/50 0-3200MHZ £60
- 87 ADVANCE SIGNAL GENERATOR B4B 100KHZ-100MHZ £25
- 88 HEWLETT PACKARD DIGITAL RECORDER type 5050B £225
- 89 BRYANS X-Y PLOTTER - No pen £60
- 90 ADVANCE X-Y RECORDER type HR100 - No pen £50
- 91 MARCONI DOUBLE PULSE GENERATOR type TF1400/S £50
- 92 RADIOMETER WAVE ANALYSER type FRA 2C13A 30HZ-16KHZ £70
- 93 R & S RESONANCE FREQUENCY METER BN43122 30-300MHZ £70
- 94 S.T.C. OSCILLATOR type 74308A £70
- 95 WAYNE KERR VIDEO OSCILLATOR type 022B 10KHZ-10MHZ £30
- 96 HATFIELD PSOPHOMETER Drg 657167A £50
- 97 TEKTRONIX SAMPLING OSCILLOSCOPE type 661 with: 4S1 Yamp & 57A TB £275
- 98 HEWLETT PACKARD MEMORY DISPLAY 5480A with 5486A Control TB and 5485A two channel input £225
- 99 E.H.T. Unit 230 Volts 50cs 25VA 7.5KV £18
- 100 AVO VALVE CHARACTERISTIC METER £20

PLEASE CHECK AVAILABILITY BEFORE ORDERING

CREED MODEL 75

Printer with keyboard. Late model Still the cheapest way to get a printout from your microprocessor. Basic data and connections supplied.

Used, good condition ONLY £25 each

As new, Ministry boxed £40 each

RACAL SA520

Frequency counter. Small compact unit. £15 each

INFRA RED IMAGE CONVERTER Type 9606 (CV 144)

1 1/4in diameter. Requires single low current 3KV to 6KV supply individually built. With data.

£12.50 each
Infra Red Lamps also advertised

FERRET A.T.E. £650 Phone for details

VARIAN RUBIDIUM STANDARD Model R20. 5mhz, 1mhz, 0.1mhz £600

EX-MINISTRY SOLID STATE 400 HZ INVERTOR

28 VDC input, 115V output. Size 7 x 2 1/2 x 1 1/2in approx. Connection details supplied. £18 each. P&P £2

TRANSISTOR INVERTOR

115V AC 1.7 Amp Input. Switching is at 20Khz. Output windings from Pot Core. Can be rewound to suit own purpose or unit can be broken for host of components. Circuits supplied. £1.25 each. P&P £2.

CONVERT THIS UNIT TO A SUPER BATTERY CHARGER

Attractive green ministry quality case with removable top and bottom plates - heavy duty power switches, high powered resistors to control current, good quality centre mounted amp meter, strip of wing nut terminals on front panel which can be used for connecting leads. All this for £3.50. P&P £2. Four units £12. Carriage £5.

STEPPING MOTORS

6/12 position with additional where the rotor is coils. Device can be used as a tach. Diagram supplied. Will actually work on 5 volts. 12/24 recommended. £1.50 each P&P 75p or 5 for £5 P&P £1.50.

STEPPING MOTORS

200 Steps. 20 oz/in. torque. 12/24 volt input 4-wire. £12 each. P&P £1.50

KEYBOARD PAD

Size 3x2 1/2x2 1/2" high with 12 Alma Reed Switches. Blue keys marked in green 0-9 and a star with one blank. £4 each, P&P £1, or 5 for £15 P&P £2.

MINIATURE KEYBOARD

Push contacts, marked 0-9 and A-F and 3 optional function keys. £1.75 each.

- CRYSTALS 50p each. Flat metal case - 19.2KHZ; 844.8KHZ; B7G - 10MHZ.
- LOUDHAILERS. Transistorised hand-held. No leads. Standard internal batteries supplied. Howl Switch £20 ea. P&P £2
- INFRA RED QUARTZ LAMPS. 230V 620 Watts. Size 1 1/2" x 1/8" dia. £1.50 ea. 240V 1650 Watts. Size 2 1/4" x 1/2" dia., £3 ea.
- BRIDGE RECTIFIER. 2 Amp 50p ea.
- PHOTODIODE DETECTOR "A" fly leads, 25p ea.
- AMPHENOL. 17-way chassis mount edge connectors 0.1 inch spacing. 15p ea.
- I.E.C. Standard MAINS LEAD. Moulded (3 vertical flat pins centre offset) 60p ea.
- FANS. 115V 13 Watts. Size 3 1/4 x 3 1/4 x 1 1/2" BRAND NEW. £4.50 ea. Secondhand £2.50 ea.
- DELAY LINE. 50 nanosec. 3 connections - ground-in-out Size 2 x 7/16 x 5/16" New 25p ea.
- MOTOR 12V DC with pulley and integral semiconductor. Speed Control. New £1 ea.
- LEDEX ROTARY SOLENOIDS. 115V DC. No switch assembly. 15p ea.
- DIAMOND H CONTROLS ROTARY SWITCH. Single pole 10-way. Printed Circuit Mount. New 10p ea. 100 for £7.50

SOME TEKTRONIX 500 RANGE OSCILLOSCOPES with Single Trace Plug-ins. Working. From £100. Phone for details

From £100. Phone for details

DIODES All new full spec. devices IN3063 BAX 13. 1S44. 1N4148; 1N3470; 1N4151. 100 off £1.50, 1,000 off £10

100 off £1.50, 1,000 off £10


- PULSE TRANSFORMER. Sub min Size 1/2 x 5/16 x 1/4". Secondary centre tapped. New 20p ea.
- REMO TV TYPE MULTIPLIER. Two high voltage outputs and focus. £1 each.
- DON'T TAKE CHANCES. Use the proper EHT CABLE. 10p per metre or £7.50 per 100 metres/drum. P&P £2.
- PHOTOGRAPHIC LAMPS. Pearl 230V 500 watt. Screw cap 75p ea. Box of 12 £5.50. P&P £1.50.
- RAPID DISCHARGE capacitors 8mf 4KV £5 each. P&P £2.
- MYSTERY IC PACK. Some 40 pin - good mixture - all new devices. 25 ICs for £1. P&P 50p.
- DECOUPLING CAPACITORS 0.05mf 10V; 0.01mf; 0.047mf 250V; 33K, 330pf. All values 10p for £1.50.
- E.H.T. Capacitor 500pf 8KV 20p each.
- 10-way MULTI COLOUR RIBBON CABLE. New 40p per metre. 10 metres for £3.
- GEC UHF 4-button tuner £1.50 each.
- CENTRAL 115V FANS 4 1/2 x 4 x 1 1/2" £4.50 ea.
- EX-USED equipment. tested, 60p each.
- CONTACTORS. Heavy Duty 24V DC 5 make £1 each.
- GEC UHF/VHF 6-button tuner £2 each.
- 931A PHOTO MULTIPLIER £2 each. P&P £1.
- RANCO 250V 18A THERMOSTATS with Control knobs calibrated 50-200 degree C £2.50 each.
- SOLID STATE UHF TUNERS. 30 acs £1 each.
- BRAND REX blue wire wraps. 30 metres for £1. P&P 25p.
- SLIDER CONTROL 500K Log. Single track. Complete with knob. Length 3 1/2". 25p each.
- TRANSFORMERS
- AUTO 240V input 115 V. 1 Amp output £1.25 each. P&P £1.25.
 - 240V input. Sec. 6V. 1.86A. Size 2 1/2 x 2 x 2". Good quality. £1.50 ea. P&P £1.
 - 240V input Soc. 12V 0.92A. Size 2 1/2 x 2 x 2". Good quality. £1.50 ea. P&P £1.
 - 240V input 12V 100MA. Size 60 x 40 x 42mm. 50p each.
 - 240V input. Soc. 12-0-12V 50MA. Size 53 x 45 x 40mm. £1 ea.
 - 115V input. Soc. 5V 250MA. Size 1 1/16 x 1.5 x 1 1/4". 2 for 50p.
 - 115V input. Sec 10-0-10V1A. Size 2 1/2 x 2 x 2". 2 for £1.50.
- SEMICONDUCTORS
- 1N4005 - 5p; 1N4002 - 3p.
 - At 5p each: BC147, BC148, BC157, BC158, BC237, BF197, OA90, OA81, BA154, BA243.
 - At 25p each: TIP31, TIP31A, 2N5696, AF139, 2TX341.
 - BY127 10p. BF181 20p; B0239 49p; BD241 40p; MA343AT 49p; BD228 50p; BD233 & BD234 Comp Pair 25V - 80p per pr. at 50p each.
 - REGULATOR TBA825 8to 20V in - 5V out 100MA TO5 Con. 50p each. BF256 20p.
 - TV AMPLIFIER TBA 120 20p each.
- Integrated Circuits
- | | | | | | |
|-------|-----|-------|-----|---------|-----|
| 7453 | 5p | 74H51 | 7p | 75325 | £1 |
| 7451 | 5p | 74538 | 10p | SN15862 | 4p |
| 7402 | 12p | 74502 | 12p | MC4028 | 69p |
| 7476 | 20p | 74154 | 70p | 7417 | 14p |
| 7495 | 35p | 74C02 | 16p | 7441 | 40p |
| 74C00 | 17p | 74C04 | 18p | 74C86 | 50p |
| 74H74 | 12p | 74C74 | 18p | 74C161 | 24p |
- MOTOROLA DUAL in Line 6 pin Opto Coupler 30p each. Gold plate tester version 50p each.
- EPROMS 2708 £5.50 each.
- ELECTROSTATIC VOLTMETER. 7.5KV £8 ea. P&P £1.50.
- Other ranges available - please enquire.
- TRIMMERS. Sub min. 0.25 to 1.25 pf. 1 to 4.5 pf. 7 to 45 pf. All at 60p each.
- HONEYWELL humidity controllers 50p each.
- THYRISTOR TIMER. Solid State. 15 secs adjustable (reset) in plastic relay case. Standard 7-pin base. Series delay 50p each.
- MINIATURE PC MOUNT SLIDE SWITCH. 2 pole 2 way 10p each.
- 4 DIGIT 7 SEGMENT per digit plus a figure one to the left plus a centre minus sign to the left of the figure one with decimal places between digits. Good brilliance at 1.5V. 15 connections £2.50 each. Some E.H.T. Transformers and Capacitors available. Please enquire.
- TELEPHONES 706 style black; grey or blue £5.50 ea; 746 style black or grey £7.50. Older style black £2.50 each. Discoloured grey 706 £4 ea P&P £1.50 per telephone.
- DC SERVO MOTOR 110V 2.5Amp continuous. Double shaft. Brand new. 4 wire. 4 brush £25 ea. Plus carriage.
- PC Mount POTS. Wire wound with knob 200 ohm & 10ohm. 10p ea.
- MIN. RELAY 24V. 2 pole c/o. Brand new. 75p each.
- TIME DELAY RELAY 0.1 to 10 secs. 115V AC. DPDT. £5 each.
- CAPACITORS at 5p each. 0.1uf 40V. Small rec. block PC Mount German class; 3300pf; 220nf/250V; 0.01mf/160V. INSERT can be used as Microphone/Earpiece (Like used as insert in telephone but superior quality) Ex-Min. Brand new wrapped 75p each. or 10 for £6.
- TOROIDAL TRANSFORMERS. Input 0-120-240 Volts. Output 0-12V; 0-12V. 10VA per winding. Encapsulated - identical to R.S. Components at £8.90. OUR SPECIAL PRICE £5 ea. P&P £1.50.
- ALUMINUM CAPACITORS - All at 10p each - 100 off £7.50.
- 22mf 6V; 39mf 10V; 22mf 35V; 1mf 35V.
- MINIATURE SLIDE SWITCHES. Single pole 2 way 10p each. 10 off 90p.
- HEAVY DUTY RHEOSTAT. 7.5ohm 5.5Amp. Diameter 5". Standard 1/4" shaft £2.50 each. P&P £1.50.

LARGE EX-MINISTRY SPEAKERS. OUTSIDE 15 ohm or 500 ohm. Tested. £25 each or 5 for £100.

MINIMUM ORDER £3 VALUE OF GOODS. MINIMUM P&P £1.50 - where P&P not stated please use own discretion - excess refunded. £5 CARRIAGE ON ALL UNITS. P&P OR CARRIAGE AND VAT at 15% on total MUST BE ADDED TO ALL ORDERS. CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5pm Monday to Saturday inc. BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome.

CHILTHEAD LTD

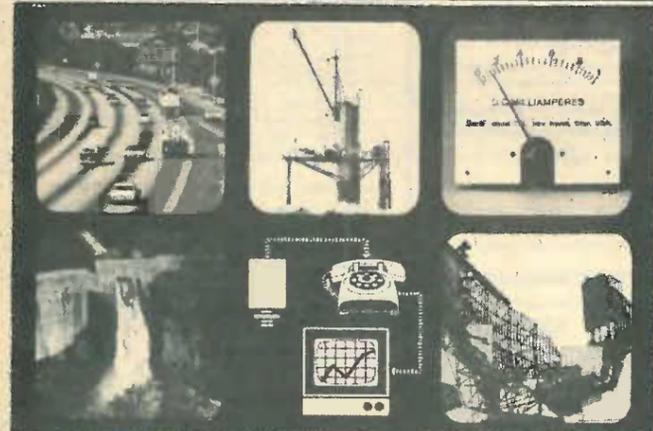NORWOOD ROAD, READING
TELEPHONE NO. READING 669656
(2nd turning left past Reading Technical College in King's Road then first right - look on right for door with "Spoked Wheel")



Visual monitoring of anything, anywhere, by phone, in seconds, with Robot Phoneline TV.

Robot's Phoneline TV systems provide a low-cost, efficient solution to the problem of visually monitoring remote installations, meters, gauges, traffic, weather, water levels, or any subject, large or small. The Phoneline TV equipment works well with standard CCTV equipment and converts the broadband video signal from the camera to narrow band audio tones for transmission via the dial telephone network or voice grade radio, then to a video signal again for display on a monitor at the receiving end. The entire process takes as little as 8.5 seconds and costs only the amount of the phone call. Since one or more cameras can be fed to one or more monitoring stations for viewing sequentially or simultaneously, and since the system can be fully automated, there is an almost infinite number of PLTV system configurations possible. Permanent storage is available by recording the transmissions on audio cassette tapes. For fast, uncomplicated, inexpensive visual monitoring of any subject anywhere, Robot Phoneline TV is the answer. Write or call for more information and descriptive literature.

Robot (UK) Ltd., Building 33, East Midlands Airport, Castle Donington, Derby DE7 2SA. Tel: (0332) 812446. Telex: 37522

ROBOT RESEARCH INC
World Leaders in Phone Line Television and Image Processing Systems



Close Encounters of the Capacitor kind

The Eurofarad close tolerance Capacitors are worthy of your close examination and consideration. They are quality precision components made for the professional market. (Eurofarad is a CECC approved manufacturer) and Pascall, as UK agent, offers the full Eurofarad range of professional capacitors.

Send for details today to:

- Range includes:
- Multilayer ceramic capacitors
 - Ceramic chip capacitors
 - Microwave chip capacitors
 - Polypropylene capacitors
 - Mica capacitors
 - Teflon capacitors
 - Polyester capacitors
 - Polycarbonate capacitors
 - Polysulphonate capacitors

Pascall the best in electronics

CECC approved stockist

UK agent for:

Eurofarad

Pascall Electronics Limited
Hawke House, Green Street, Sunbury-on-Thames, Middlesex TW16 6RA
Telephone: (09327) 87418 Telex: 8814536

WW - 083 FOR FURTHER DETAILS

VALVES

Minimum Order £1 VALVES VAT IS INCLUDED

Table listing various valve types (A1065, A2293, A2300, etc.) with their respective prices and specifications.

VALVES AND TRANSISTORS

Telephone enquiries for valves, transistors, etc. retail 749 3934, trade and export 743 0899.

COLOMOR (ELECTRONICS LTD.) 170 Goldhawk Rd., London W.12

FIELD TELEPHONES TYPE "J"


Tropical, in metal cases. 10-LINE MAGNETO SWITCHBOARD. Can work with every type of magneto telephones.

Image of electronic components with text: SURREY ELECTRONICS The Forge, Lucks Green, Cranleigh Surrey GU6 7BG. Tel. 04866 5997

PPM3 drive circuit to IEC268-10A, BS4297, draft BS5428-9. Unbalanced input. May be used in equipment which will be required to pass IBA Code of Practice inspection.

METALFILM RESISTORS

1% Tolerance, 1/4 Watt

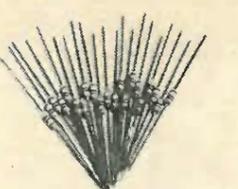

ONLY 3p EACH Minimum order £10 Minimum 5 pcs per value 89 Values (E24)

Table listing resistor values from 100R to 910R with prices.

ORION SCIENTIFIC PRODUCTS LTD. 10 Wardour St., London W1

Memories

Table listing memory types (2708, 2716, 2732, etc.) and prices.

8085 & Z80

Table listing microprocessors (8085A, 8085A-2, etc.) and prices.

BDS Microsystem Designs Ltd. 28 Pinewood Close, St. Albans, Herts., AL4 0DS Telephone: St. Albans (0727) 31831

Belle Vue Radio and Electronics Exhibition

in the LANCASTER HALL on SUNDAY, MARCH 29, 1981. Doors open at 11 a.m. The North's Premier Amateur Radio and Electronics Event

FREQUENCY COUNTERS—OFF/AIR RECEIVERS

Image of frequency counter with text: 250MHz 801 B £250 Crystal oven 3 parts 10" OFF/AIR RECEIVER TYPE 103 PRICE £135

Appointments

Advertisements accepted up to 12 noon Monday, 23 March, for May issue, subject to space being available.

DISPLAYED APPOINTMENTS VACANT: £12 per single col. centimetre (min. 3cm) LINE advertisements (run on): £2 per line, minimum three lines.

ECM ELECTRONIC OPPORTUNITIES £5,000-£15,000 Microprocessors - Minicomputers - Digital - Analogue - HF - VHF - UHF - Microwave

THE PAPUA NEW GUINEA UNIVERSITY OF TECHNOLOGY DEPARTMENT OF ELECTRICAL AND COMMUNICATIONS ENGINEERING PRINCIPAL OR SENIOR TECHNICAL OFFICER

A division of SOS Bureau Ltd The SOS Group Trading as: SOS Staff Bureau SOS Industrial Staff SOS Senior Appointments

Applications are invited for the above-mentioned position in the Department of Electrical and Communications Engineering. Applicants will be required to have appropriate qualifications and to be experienced in the fields of digital electronic equipment.

The following are a selection of the many vacancies currently on file: FIELD SERVICE TECHNICIAN! £6,000! CAR! COMPUTER SYSTEMS! W. LONDON! A.T.E. ENGINEER! £8,000!

Company Communications Controller

c. £10,000

As a major name in aviation and communication services for the world, maintaining and upgrading our own lines of communication is vital; customers and suppliers, for instance, are constantly in contact through telex, telephone, data transmissions and post. The task of our Company Communications Controller is to supervise both the technical and human aspects of the existing network and to advise on the introduction of new computer based information handling systems throughout the group.

He or she will work from Southall, liaising with suppliers and with service staff on maintaining equipment. There is also a large amount of advisory and analytical work involved, in order that existing systems may be improved.

Candidates should possess an HNC in telecommunications engineering and should have worked for at least five years with a manufacturer, major telecomm. user, or in Post Office telecommunications. They should understand business communication problems, and ought to be capable of expressing technical solutions clearly to non-technical management.

Benefits include a staff restaurant, a pension and life assurance scheme, relocation expenses where applicable and 5 weeks' holiday plus bonus.

Please apply, in writing, to John Callow, IAL, Aeradio House, Hayes Road, Southall, Middx, quoting Ref.K/024. Tel: 01-843 2411.

IAL HEAD OFFICE
TEL. NO. CHANGED TO
01-843 2411
ON 2ND MARCH
1981

IAL THE HIGH TECHNOLOGY TASK FORCE
COMMUNICATIONS SYSTEMS
COMPUTER SYSTEMS AND SERVICES
AVIATION SYSTEMS AND SERVICES - WORLDWIDE

(1001)

UMIST

EXPERIMENTAL OFFICER FOR SILICON DEVICE MANUFACTURE

REF: EEE/25. A new facility is being assembled in the Solid-State Electronics Group of the Department of Electrical Engineering and Electronics, for the manufacture and testing of semiconductor components in ultra-clean conditions. Within a large clean area there will be a total of 60 linear feet of ultra-clean bench housing a wide range of equipment. The Experimental Officer will be responsible for the day-to-day running of this facility, overseeing its use by undergraduate and postgraduate students, and will be responsible for the maintenance of the equipment, including the air filtration plant. He/she may also be required to assist staff of the Solid-State Electronics group in any research which involves semiconductor processing. A wide range of skills is required, together with the necessary experience and confidence to allow unsupervised working.

Salary will be in range of £4795-£9595 per annum (under review).

Requests for application forms, quoting the above reference, should be addressed to the Registrar, Room B6, UMIST, PO Box 88, Manchester M60 1QD. The closing date is March 31, 1981. (973)

TOP JOBS IN ELECTRONICS

Posts in Computers, Medical, Comms, etc. ONC to Ph.D. Free service.

Phone: 01-906 0251

(8994)

ELECTRONIC SERVICE ENGINEERS

NORTH LONDON - ILFORD

Our company specialises in both sales and servicing of Discotheque Sound and Lighting Equipment. We currently have vacancies for engineers who have had previous experience of either HiFi, Studio PA or similar equipment. Good salary, plus Commission and Bonus.

Please telephone or write to Janet Findlay for further details.

Roger Squire's

Barnet Trading Estate Park Road Barnet Herts EN5 5SA
Telephone: 01-441 1919

(963)

NORTHERN REGIONAL HEALTH AUTHORITY ELECTRONICS TECHNICAL ASSISTANT (2 POSTS)

Required for Regional Engineer's Division, based at Walkergate, Newcastle-upon-Tyne.

The appointments will be at Technical Assistant Grade 1. Salary £6,633 - £7,824 per annum.

The posts offer technologically interesting and varied work, with excellent working conditions and well-equipped laboratories, and involve visits to hospitals throughout the Region, for which financial reimbursement is made.

Applicants must be of high calibre and have had considerable and broad experience with modern electronic equipment.

Minimum qualifications: HNC or City and Guilds Full Technological Certificate in Electronic Engineering or equivalent.

Application form and job description available from the Regional Personnel Officer, Northern Regional Health Authority, Benfield Road, Newcastle-upon-Tyne NE6 4PY.

Closing date: 1 April, 1981.

(971)

PHILIP DRAKE ELECTRONICS LTD.

Manufacture Audio and Intercommunication Equipment for the broadcast industry and have vacancies for the following staff:

PROJECT ENGINEER

to work in the Project Department. The job includes project discussion with customers, the detail design of systems, test supervision, and the compilation of system handbooks. Experience in the broadcast audio industry is essential and a formal qualification is desirable.

ASSISTANT TEST ENGINEER

to test primarily the custom-built products, mainly intercommunication systems, along with the standard product range. Some experience in the testing of audio and digital circuits and in the design of test jigs is desirable.

DRAUGHTSPERSON/TRACER

to work primarily in the Project Department, to prepare handbook drawings and design system metalwork, and also to prepare circuit diagrams and standard products. Experience in control panel layouts and broadcast audio requirements is desirable.

The company offers a 37 1/2-hour week with 20 days' holiday minimum. Experience in the broadcast industry and/or suitable qualifications are desirable for all positions. Salary negotiable dependent on experience.

Apply by telephone or writing to:

ALAN BRILL, PHILIP DRAKE ELECTRONICS LTD.
23 REDAN PLACE, LONDON, W2 4SA - Tel: 01-221 1475

(1014)



CAPITAL
APPOINTMENTS LTD.

THE UK's No. 1 ELECTRONICS AGENCY

Design, Dev. and Test to £10,000
Ask for Brian Cornwell

SALES to £12,000 plus car
Ask for Ken Sykes

FIELD SERVICE to £10,000 plus car
Ask for Maurice Wayne


We have vacancies in ALL AREAS of the UK

Telephone: 01-637 5551 (3 lines)

CAPITAL HOUSE
29-30 WINDMILL
STREET
LONDON W1P 1HG
TEL: 01-637 5551

Sony Broadcast success story means even more career opportunities!

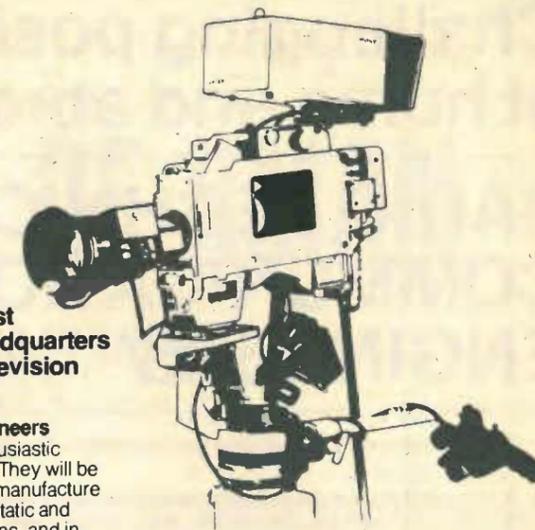Tremendous growth and success has created the need for even more first class staff at the Basingstoke International Headquarters of one of the world's leaders in professional television broadcast equipment.



UK Sales Manager/ess - TV Production Houses

£ neg + car

This is a new position created as part of our planned expansion programme. The successful candidate should possess experience of either Production or Engineering Operations within a broadcast television environment. A knowledge of professional VTR's, editing systems and cameras is necessary whilst previous sales experience is desirable, though not essential.

Sales Engineers/Technical Support Engineers for Western Europe

Competent engineers experienced in video cameras and/or VTR's are sought to join our sales team. Successful candidates are likely to be in the age range 25-35 and should be highly motivated and able to work on their own initiative. Experience in dealing with customers would be an advantage as would knowledge of a second European language. Travel within the western European area will be necessary.

Engineers - Commercial/Sales Applications

Openings exist, at various levels for engineers with a wide experience of the TV Broadcast Industry, to utilize their knowledge in a dynamic commercial environment.

The selected candidate will be self motivated, capable of working with a minimum of supervision, and will be appointed to our Proposals/Quotations section. He or she will have the ability to prepare detailed and concise customer presentations/quotations complete with pricing information.

Previous commercial/sales experience desirable, however not considered essential.

Systems Project Engineers

For our young and enthusiastic Special Projects Team. They will be involved in the design, manufacture and commissioning of static and mobile television systems, and in modifications and accessories. The successful applicants will have a thorough knowledge of sound and television principles. Ideally, he or she should have experience in operational television or its allied manufacturing industry.

Product Specialists

Opportunities exist for young engineers from a broadcast television background to be involved in all aspects of development, marketing and support of our entire product range.

We would be particularly interested to hear from you if you are currently working with professional VTR's/VCR's, cameras or microprocessor controlled post production systems and would like to further develop your technical and commercial skills in a challenging environment.

Field Service Engineers

Currently, openings exist at Engineer and Senior Engineer levels for personnel with experience of working on professional VTR's and cameras probably in a Broadcasting organisation or TV Broadcast Equipment Manufacturer. The Engineer level position should appeal to applicants with limited relevant experience who are now seeking a progressive environment in which to broaden their careers. Both positions offer the opportunity for some UK and overseas travel.

R & D Engineers

Sony is now established as the world leader in digital video recording technology. Development is still in the

formative stages but rapidly progressing to the new era of the 'All Digital Studio'. The R & D Section is involved in long term investigations into the application of high speed digital techniques to video processing, and in conventional product design. Being part of an international R & D team, the successful applicant may expect occasional opportunities for overseas travel. Applications are invited from engineers offering experience in high speed digital processing or video engineering. Alternatively, a well qualified recent graduate could be considered.

Lecturer

The Lecturer will join our training team and after a suitable familiarisation period will be required to conduct theoretical and practical training courses on our major products, and/or write circuit descriptions and produce training manuals with lucid block diagrams. Ideally, candidates should have had experience of video tape recorders, digital circuits and a practical up-to-date knowledge of the broadcast industry. Knowledge, or an ability to master the techniques of video cameras, digital audio equipment and the application of microprocessors to broadcast equipment will be an advantage although we are prepared to provide the necessary additional training. Promising young graduates may also apply for consideration as a Trainee Lecturer.

If you like the thought of enjoying the success of world leadership then write in strict confidence to Barry White, Personnel Manager, Sony Broadcast, now! And please don't forget a CV.

SONY
Broadcast



Sony Broadcast Ltd.

City Wall House
Basing View, Basingstoke
Hampshire RG21 2LA
United Kingdom

(968)

Challenging positions at home and abroad

RADIO TECHNICIANS COMMUNICATIONS ENGINEERS

EAE Limited install and maintain communications systems for the oil industry, at home and abroad.

Due to rapid and continuing expansion in our activities, we constantly require Radio Technicians, with experience of HF, MF, VHF and UHF, and Engineers (preferably qualified to HNC level or above) in the fields of Microwave, Multiplex and Tropospheric Scatter.

In the North Sea, earnings are in the range £9,000 to £12,000 p.a. Overseas earnings could be up to £20,000 - plus tax concessions and generous home leave.

The work is demanding, but rewarding, offering you the chance to use your skills and your initiative to the full.

The company is based in Great Yarmouth, with offices in Aberdeen and Lerwick - but where relocation is necessary, we will give generous assistance with removal, legal and temporary accommodation expenses.

Please apply, with details of your career to date, to: Personnel Manager, EAE Limited, Dept WW, Offshore House, 284/285 Southtown Road, Gt. Yarmouth, Norfolk NR31 0JB Telephone 0493 58541

EAE Limited

(935)

INNER LONDON EDUCATION AUTHORITY

Learning Materials Service
Television Centre, Thackeray Road, London, SW8

MOBILE SECTION ENGINEER ST3

The mobile section operates colour broadcast standard television facilities including a three camera (Link 120) mobile control room and battery portable equipment (Sony BVP, BVU). The main function of the section is to make observational classroom recordings for use in teacher education both in London and nationally. All members of the crew share rigging duties and driving of vehicles. A current driving licence is highly desirable and training will be provided leading to an HGV test.

The engineer will join a team of three other engineers who are jointly responsible for the operation and maintenance of the section's equipment. This involves lighting, vision control, microphone rigging, sound mixing and V.T. operation. Experience in one of the fields is essential; however as training in others will be given, it is important that candidates have appropriate academic qualifications and a thorough knowledge of current broadcast engineering practices. Candidates must also possess good health and normal colour vision.

Hours of work will be in accordance with the requirements of the service (the normal working week being 35 hours).

Further details available from the Mobile Videorecording Section, telephone 622 9966.

Salary within the scale £8,115 - £8,709 (plus an irregular hours allowance of £156 per annum).

Application forms available from the Education Officer (EO/Estab 1c), Room 365, County Hall, London, SE1. Telephone 633 7456/7546. Closing date: 14 days from appearance of advert.

(964)

ITN

SENIOR ENGINEER

ENG/OB Maintenance
Salary: £11,406 p.a.

Independent Television News Limited has vacancies for two Senior Engineers in their expanding ENG/OB Maintenance Section at ITN House, London, W.1

The successful candidates would be members of a small team responsible primarily for the maintenance of ENG equipment including Sony BVU series U-matics, RCA Tk76C and Sony BVP330 cameras, TBCs and associated portable equipment. The section is also responsible for the long-term maintenance of our two camera Outside Broadcast Unit.

The work would occasionally involve travel with ENG teams to remote locations.

Previous maintenance experience with U-matic equipment and/or lightweight cameras is essential.

Generous pension scheme, free life insurance.

Please telephone the Personnel Office on 01-637 3144, quoting reference number 30301 for an application form.

(966)

The following personnel are required by a radio manufacturer in South Africa. Successful applicants will need to be stable and have a desire to emigrate. This is not short term contract work.
Radio development engineers, with experience of domestic radio. Salary R1500 per month.
Radio technicians, preferably with factory experience. Salary R1000 per month.
Draughtsmen, preferably with radio cabinet design experience. Salary R1000 per month.
Radio or cabinet assembly line foreman or chargehands. These applicants must be prepared to train operators. Salary dependent on experience.
Injection moulding machine setters. Salary R1000 per month. Must be prepared for shift work.

PHOTO - STAFF CONSULTANTS LIMITED

133 OXFORD STREET
LONDON W1R 1TD

Telephone: 01-439 1821 (10 lines)
Telex 263 231 FOSTAF G

(990)

DIGITAL EXPERIENCE?

FIELD, SUPPORT AND PRODUCTION. VACANCIES IN COMPUTERS, NC, COMMS., MEDICAL, VIDEO, ETC.

For free registration ring 01-290 0267

LOGEX

ELECTRONICS RECRUITMENT SERVICE
HIGH ROAD, LOUGHTON, ESSEX
01-290 0267

(321)

SULTANATE OF OMAN

RADIO AND TV BROADCAST ENGINEERING VACANCIES

The Sultanate of Oman operates a modern colour television and radio broadcasting service with studio centres situated in the North and South of the country, the two centres being linked by satellite. High power VHF and low power UHF transmitters are employed to provide a 625 PAL TV service to various populated areas of the Sultanate. The radio broadcasting service uses HF, MF and VHF transmitters of various powers. Both services are managed by the Ministry of Information and Youth Affairs.

Due to expansion of the service vacancies for a variety of posts have arisen and applications are invited from suitable qualified persons.

TRANSMITTER ENGINEERS

For maintenance of high power VHF TV transmitters and low power UHF transposers, high power MF, HF and VHF FM sound transmitters. The work will involve travel and in some cases overnight stops away from base. The transmitters operated within the Sultanate are manufactured by Siemens, Philips, Marconi and Continental Inc., U.S.A.

STUDIO ENGINEERS

For maintenance on cameras, vision mixers, S.P.G.S., vision distribution systems, telecine machines and video monitors, etc. There will also be operational work, particularly on outside broadcasts.

The equipments employed are Philips LDK15 cameras, Bosch Fernseh KCU40 and KCP cameras, vision mixer units by C.D.L. and Bosch Fernseh, telecine by Rank Cintel and Bosch Fernseh.

SOUND MAINTENANCE ENGINEERS

To maintain a wide range of high quality sound broadcasting equipment.

VTR ENGINEERS

For maintenance on Ampex VR1200B and Bosch Fernseh BCM40 machines. There will also be some operational work. During the forthcoming year it is intended that 1in. "C" Format VTR machines will be installed.

PLANNING AND PROJECT ENGINEERS

To carry out planning for a wide range of transmitter installations for both TV and radio. Planning and Systems Engineers are also required for work on new radio studios to be constructed over the next few years.

Successful applicants will be expected to be directly involved with the nuts and bolts of the installation work, in some cases in remote areas. Applications are also invited for a number of senior positions in the transmitter, studio groups and electro-mechanical services groups. If you feel you can apply your knowledge and expertise to the efficient running of these groups we will be pleased to hear from you.

Applicants should be qualified to degree or HND level and have not less than six years' relevant experience. The senior positions require considerably more years of varied but relevant experience. In most cases a knowledge of Arabic - although not essential - would be useful.

Salaries, which are paid in Rials Omani, are fully remittable and tax-free and range from pounds sterling 1100 to 1300 per month upwards. The senior positions start at pounds sterling 1500 to 1700 per month (depending upon current rate of exchange).

Married accommodation is provided together with free air passage at beginning and end of contract for family. Air tickets are also provided for leave after the first year of service.

Applicants should write stating age, nationality, qualifications and full details of experience to:

Ministry of Information and Youth Affairs, Post Box 600, Muscat, Sultanate of Oman, marking the envelope "Technical Office" in top left-hand corner.

Development Engineers in Digital Electronics

We have an important client in the Cambridge area who is about to embark upon a major development programme incorporating projects valued at several million pounds. Over the last few years they have been developing and exploiting a specialised area of telecommunications, and to complete the highly specialist and skilled teams which are involved in breaking new ground in digital development, two experienced Engineers are needed immediately.

They will ideally have experience of both hardware and software gained in a development environment where high standards and imminent deadlines are the norm. A Degree standard of education is less important than experience on design and development and they will have the opportunity of seeing a prototype design right through to manufacture.

Our client offers in return the opportunity to become involved in a thriving organisation which offers excellent terms and conditions of employment, good career prospects and, most important, an opportunity to take digital electronics to new frontiers.

Please apply in confidence,
quoting Ref. KR77, to:

Andrew Millhouse
Ketchum Recruitment Limited
52 Bedford Row, London, WC1R 4LX.
01-405 1260



(972)

**NORTH-EAST
LONDON POLYTECHNIC**
FACULTY OF ENGINEERING -
BARKING PRECINCT
LONGBRIDGE ROAD
DAGENHAM, ESSEX

SCHOOL OF CHEMICAL
& SYSTEMS ENGINEERING

SENIOR TECHNICIAN

T5 REF: 83/E/80

required to control and supervise technicians working within the microprocessor laboratory, under the supervision of the Principal Technician. Other duties will include planning and progression of technician work, maintenance of progress and financial reports, and development, including design assistance, of equipment within the laboratory. Candidates should hold a full technological certificate and/or HNC/HND qualifications, and have had 5-10 years' experience in a technical environment.

The inclusive annual salary will be on a scale from £7,233 to £7,695 according to age, qualifications and experience.

For further details and application forms please contact the Personnel Office (R), North East London Polytechnic, Asta House, 156/164 High Road, Chadwell Heath, Romford, Essex, RM6 6LX. Telephone 01-590 7722, Ext. 3121 or 3135, quoting the above reference number.

CLOSING DATE FOR RECEIPT OF APPLICATIONS: April 3, 1981.

(992)

THE LEADING TELEVISION FACILITIES COMPANY

REQUIRES

DIRECTOR OF OPERATIONS

**EXCELLENT SALARY
+ CAR + PENSION + BUPA +
PROFIT SHARE**

The position of DIRECTOR OF OPERATIONS requires a person with drive, initiative and clear thinking, to be able to deal with the day-to-day demands of this high technology Television Facilities Company providing Studio, VTR and O.B. services to its Clientele.

Loyalty, hard work and the ability to lead, will be rewarded by a career in the fast-moving TELEVISION SERVICE and the Operations Director and his/her colleague Directors will have the opportunity of long-term future career development. The Company will be looking forward to one of the senior Directors becoming the next Managing Director.

The applicant must have Engineering ability and have worked or be working in a Broadcasting organisation and have high level Management experience plus that special "something" of being able to lead and drive for the achievement of the Company's policies.

The position of Director of Operations will be a Company Board appointment.

Please apply to the Sole Recruitment Agents in the strictest confidence quoting "OPS DIR 1981":



PERSONNEL & ELECTRONICS LTD.

Telephone: 01-573 8333 Telex: 934271
Triumph House 1096 Uxbridge Road Hayes Middlesex UB4 8QH England UK

(1005)

IF THIS IS RECESSION WE LIKE IT

AT LAST ELECTRONIC ENGINEERS ARE BEING PAID WELL AND THEIR WORK IS APPRECIATED ...

We have hundreds of vacancies which include:

SYSTEMS ENGINEERS: for new company specialising in secure computers based on DEC 11/23 and Z80. Knowledge of image processing and pattern recognition an advantage. To £13,000. SURREY.

RESEARCH ENGINEER/MANAGER: for a group providing support to an international company engaged in research on precious metal refining, cancer research, pollution monitoring, etc. Broad based experience. To £12,000. BERKS.

R.F. ENGINEERS: for small dynamic company engaged on telemetry and remote monitoring instruments for the off-shore industry - tankers, gas rigs, etc. To £10,000. LONDON.

HARDWARE AND SOFTWARE ENGINEERS: to work on a new generation of Printers and Data Terminals based on Z80 Intel 8080 and 8008. To £11,000. BERKS.

PRINCIPAL AND SENIOR MICROWAVE ENGINEERS: for development of V.C.O.s, frequency multipliers, amplifiers and fitters. Good salary but confidential. MIDLANDS.

YOUNG ENGINEER: with 8085 HW/SW experience to join a high flying team working on novel controls for the automotive industry. To £8,500. WEST COUNTRY.

DESIGN ENGINEER: broadcast TV equipment including character generators and teletext terminals. To £8,000. SURREY/HERTS. BORDER.

SENIOR ENGINEER: to design and develop special modules for users of a large international computer network based on ICL 1900 and PDP11. To £8,500. LONDON.

DESIGN ENGINEER: mini and micro computer based control equipment and systems for the heavy mechanical electro mechanical industry. Z80 HW/SW experience essential. To £8,000. NORTH-EAST ENGLAND.

COMPUTER ENGINEERS: vacancies throughout UK in systems test, field service permanent site and technical support.

For further details, please contact:

(1003)

Charles Airey Associates

4 Hammersmith Grove, London W6 0NA. Tel: 01-741 4011

PROBABLY THE BEST-KNOWN SUPPLIER OF ELECTRONIC ENGINEERS IN THE COUNTRY. Financial Times

ONE IN A MILLION?

Among the million or so leaving school or university this year there is a chance that one - perhaps two - is destined to make a significant development in audio.

That person's first decision might well be to join QUAD in Huntingdon. At school, he or she will have realised that amplifier design is not just a matter of having a listen or a fiddle with standard circuits and their variations. Later will have come an adolescent stage of great discoveries. "Increase the rise time to eliminate TIM". "Regulate the power supply for better imaging".

Following on from such childish things will have come an ability to distinguish between the characteristic impedance of the medium and the third row of the dress circle and between peak flux density and the rather gooey substance fed by spoon to small children. He or she will, nevertheless, be sufficiently down to earth to know that one newton is about the weight of the average apple. 1 in 10⁹?

Well, drop us a line anyway.

Mr. P. J. Walker

THE ACOUSTICAL MANUFACTURING COMPANY LIMITED

30 St. Peter's Road, Huntingdon, Cambs. PE18 7DB

(403)

DEPARTMENT OF NUCLEAR PHYSICS

ELECTRONICS TECHNICIAN (Grade 5)

Salary £5249-£6129 rising wef July, 1981, to £5695-£6650

Applications are invited for the post of electronics technician in the Department of Nuclear Physics for interesting and challenging work. The post involves assisting in the development and maintenance of a variety of equipment incorporating fibre-optic data links, 8 and 16-bit and bit-slice microprocessors, as well as some analogue circuitry. Some experience is essential, as are willingness and ability to learn quickly.

Applications in writing together with the names of two referees should be sent as soon as possible to the General Administrator, Department of Nuclear Physics, Keble Road, Oxford OX1 3RH. (967)

Can you develop our potential?

Ultra manufacture highly sophisticated communications equipment and are Europe's leading suppliers of Sonobuoys. Our Test Equipment Department has been extensively reshaped with new laboratories being built with a view to expansion. We can now offer Test Equipment Development Engineers and Technicians a real opportunity to become involved in the latest technology coupled with positive career development.

Test equipment development engineer £6500-£7500

Working closely with our Senior Engineers and outside companies you will primarily assist the Design Engineers in developing Test Equipment Design. In addition, you will develop systems and units from outline specifications through to building prototype units.

As the department is still in its early stages you will have the opportunity to make a positive contribution to its formation and you will also be expected to attend comprehensive training seminars and exhibitions.

Test equipment technicians £5500-£6000

With a minimum of 2 years practical experience in a repair environment and an HNC or C&G in Electronics, you will undertake the repair and calibration of Proprietary and Purpose-Built Test Equipment and Main Units.

In addition to 5 years practical experience in repair and calibration, you should have the ability to communicate with Senior Engineers.

For both positions we offer outstanding career prospects with a company that is looking to the future. Apart from competitive salaries, we offer a sports & social club, 23 days holiday, contributory pension scheme and a subsidised restaurant. For further information, please telephone Julie Foreman on 578 0081 or write to her at:



Electronic Communications Ltd.
 Ultra Electronic Communications Ltd
 419 Bridport Road Greenford Trading Estate
 Greenford, Middlesex. (999)




Technicians/Junior Engineers (Broadcasting Coverage)

If you like an outdoor life with plenty of travel all over the UK and are qualified to ONC/TEC level in electrical engineering (or a related subject), we may have just the career opportunity for you.

Working as a member of a small team, you would be involved in carrying out tests and surveys for our future television and local radio transmitter sites.

A current driving licence is essential. Previous working experience should have involved testing or taking measurements.

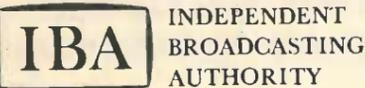Starting salary will be within the range £4,280-£5,980 per annum, according to experience. Further progression to a maximum of £7,360 per annum is possible after a period of experience.



Please write or telephone for an application form quoting Ref: WW/575cc to Glynis Powell, IBA, Crawley Court, Winchester, Hampshire, SO21 2QA. Telephone: 822270.

(These posts are open to men and women.)

(985)

THE OPEN UNIVERSITY FACULTY OF SCIENCE



Electronics Technician

Applications are invited for a technical vacancy in the Chemistry Discipline. The main duties of the post will be to maintain and upgrade spectroscopic instruments and other apparatus, including mini-computers, and to take responsibility for the operation of a Varian Electron Resonance Spectrometer. An ability to contribute to the design, particularly in the computer interface area, of electronic equipment would be an advantage.

Candidates should possess HNC (Electronics) or equivalent qualification and have 9-10 years' relevant experience.

Starting salary will be within the Grade VI Technician salary scale £6020-£7191 p.a. (£6,532-£7,802 p.a. from 1st July, 1981).

Further details and application forms are available from the Assistant Secretary Science (3440/1), The Open University, Watton Hall, Milton Keynes MK7 6AA, or telephone Milton Keynes (0908) 653481: there is a 24-hour answering service of 653868.

Closing date for applications: 14th April, 1981. (962)

TELEPHONE ENGINEER ABU DHABI

A Telephone Engineer is urgently required with experience on Siemens ESK 3000E or similar crosspoint exchange.

TELECOMMUNICATIONS TECHNICIANS

We also have vacancies for Radio Techs. able to take up appointments at short notice.

Comprehensive c.v.s should be airmailed immediately to:

Mr. George Fee, General Manager
 AL MARIAH UNITED CO.
 P.O. Box No. 206, Abu Dhabi U.A.E.

Telex: 22323 Phone 326017 giving contact U.K. telephone (1008)

UNIVERSITY OF SURREY Audio Visual Aids Unit Television Engineers ONCE IN A DECADE CHANCE!

Join a small and lively team providing television services for teaching and research. Now converting to high quality Video 80 colour system, studio based but versatile and mobile. Photography, film, graphics and instrument workshop services available within the Unit. Salaries according to experience and qualifications on scales between £4,870 and £7,873. Further training available where appropriate. Write or telephone now: Staff Officer, University of Surrey, Guildford GU2 5XH. Telephone Guildford 71281, ext. 776 for full information, quoting reference (16) WW. (960)

T.V./Video Engineers

Media Librarian

*Salary range
 5230-5625 Saudi Riyals per month

for the King Faisal Specialist Hospital and Research Centre Riyadh, Saudi Arabia

If you are well qualified in either of these areas, here is an excellent opportunity to make a break for 2 years and work in one of the world's most advanced Hospital and Research Centres. Working conditions are first class and all equipment and systems are the most modern available.

We need experienced T.V./Video Engineers to help maintain the hospital's sophisticated television network (mostly Sony equipment). You will be working with a five channel closed circuit system which is used for patient monitoring, training and medical/surgical recording, and in addition provides entertainment programmes for the hospital's surrounding residential and services complex.

Applicants should be able to operate test equipment and be familiar with PAL, SECAM and NTSC systems. Some previous experience of studio production (television and electronic editing systems) would be an advantage.

We also need a male Media Librarian to take overall control of the hospital's film and photographic library and operate the a/v equipment lending pool.

These are married status posts and successful applicants will be offered a 2 year contract (extendible by mutual agreement) with generous leave periods, air conditioned accommodation, subsidised meals and education assistance for eligible dependants. There are excellent facilities for sport and recreation.

*Sterling exchange rate at the time of going to press 8.0 Saudi Riyals to the £.

Please apply in writing with career details, quoting ref. no. KFSH 008, to:

Jim Hawkins
 Hospital Corporation International
 49 Wigmore Street
 London W1H 9LE
 Employment Agency reg. no. SE(A) 4698
 (1010)



UNIVERSITY POST GRADUATE STUDY


ELECTRONICS RESEARCH AT THE UNIVERSITY OF ESSEX

Graduates who have (or final year students who expect to obtain) a first or upper second-class honours degree are invited to apply for research leading to a higher degree (M.Sc., M.Phil. or Ph.D.) in the following areas:

Audio (high quality audio systems, music synthesis), Circuit Design (computer-aided design, filters), Computer Systems (architectures, languages, man-computer interaction, microprocessor systems), Optical Communications, Acoustic Noise and Vibration Cancellation, Satellite Communication Systems, Microwave and Millimetre Wave Propagation, Telecommunications Transmission (data transmission, filters, PCM, DPCM), Telecommunications Switching Systems and Software (computer control, traffic studies, network configurations), Visual Displays and Television Engineering (computer graphics, 3-D and colour TV), Picture Coding and Processing (feature extraction, digital filtering, perception).

Further information and application form available from: Professor K. W. Cattermole, Department of Electrical Engineering Science (Ref. JAN/2), University of Essex, Wivenhoe Park, Colchester CO4 3SQ. (961)

Professional Careers in Electronics

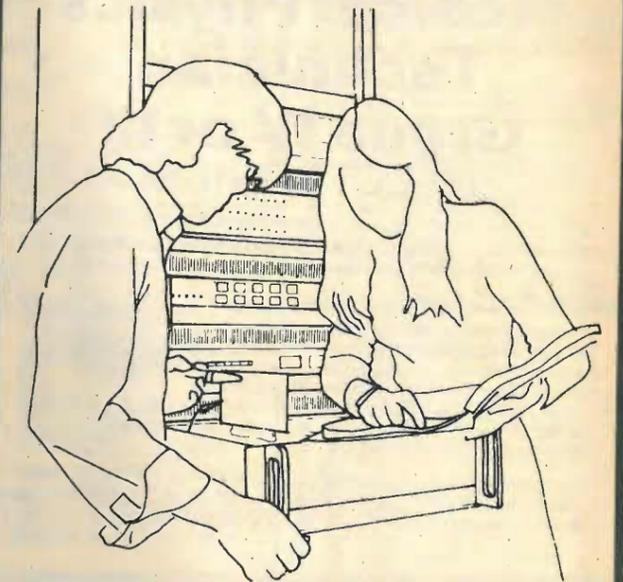

All the others are measured by us...

At Marconi Instruments we ensure that the very best of innovative design is used on our range of communications test instruments and A.T.E. We have a number of interesting opportunities in our Design, Production and Service Departments and we can offer attractive salaries, productivity bonus, pension and sick pay schemes together with help over relocation. If you are interested to hear more, please fill in the following details:-

Name _____ Age _____
 Address _____
 Telephone Work/Home (if convenient) _____
 Years of experience 0-1 1-3 3-6 Over 6

 Present salary £3,500- £4,500- £5,500- over
 £4,500 £5,500 £6,500 £6,500

 Qualifications None C & G HNC Degree

 Present job _____

Return this coupon to John Prodger, Marconi Instruments Limited, FREEPOST, St. Albans, Herts, AL4 0BR. Tel: St Albans 59292



A GEC MARCONI/ELECTRONICS COMPANY (9200)

SITUATIONS VACANT

National Heart and Chest Hospitals
Brompton Hospital

Medical Physics Technician
Grade IV or III (ELECTRONICS)

We require a technician to work in a small but busy department which provides a comprehensive medical electronics/physics service to this leading cardio-thoracic hospital.

For application forms and job description contact Personnel Manager, Miss J. A. Jenks, Brompton Hospital, Fulham Road, London, SW3. Tel. 01-352 8121 ext. 4357.

(1004)

ARTICLES FOR SALE

TO MANUFACTURERS, WHOLESALERS & BULK BUYERS ONLY

Large quantities of Radio, T.V. and Electronic Components. RESISTORS CARBON & C/F 1/2, 1/4, 1/8, 1/16. 1 Watt from 1 ohm to 10 meg.

BROADFIELDS & MAYCO DISPOSALS
21 Lodge Lane, N. Finchley, London, N.12. 5 mins. from Tally Ho Corner (9461)

RACAL COMMUNICATIONS RECEIVERS. 500kc/s 30mc/s in 30 bands 1MHz wide. RA17 £1.50. RA17L £200. Or a few as now £250.

MARCONI R.F. RADIATION & POWER METER. OA1430 (CT477), as new, in grey metal case with full manual, power meter FX range, 10mc/s to 10gc/s, complete with X-S-L band aerials, £50.

MUIRHEAD FACSIMILE EQPT. TX D901 D/S £50. RX D900 D/S or P/D £75 each.

WEATHER SATELLITE. RX D900 S/1A or S/2A £125 each with manual.

EXTEL TRANSEL MATRIX PRINTERS. 5 level Baudot Code. Accepts speeds up to 300 bauds. Supplied set to 50 and 75 bauds switched. Tested with manual, £165.

All items are bought direct from H.M. Government, being surplus eqpt. Price is ex-works. A.E.E. all enquiries. Phone for appointment for demonstration of any item. JOHNS RADIO, 424 BRADFORD ROAD, BATELEY, YORKS. TEL: 0924 478159 (9.30 a.m.-1 p.m.). (848)

TEKTRONIX 465 oscilloscope, mint condition, calibrated, other test equipment. — Phone 0582-425721.

DIGITAL WATCH TESTER. Placing a digital watch on the sensor pad gives immediate readout of time-keeping. Accurate, attractive instrument uses. Built-in off-air frequency standard. Offers invited for full manufacturing data, including presentable prototype. 073 088 317. (986)

GRUNDIG SATELLIT 2100. Multi band radio, £180. — Telephone Southend-on-Sea 588359. (976)

ASR 33 data terminal, good condition including paper tape I/O, stand and all operator manuals, £240. — Telephone 01-948 3464. (998)

6800 PARTS: 6802 MPU £6.50; 6821 PIA £2.50; 6845 CRT Cont. £13.50; 6850 ACIA £2.50; 2716J-8 UV £5.00. All to full spec. Postage £0.40. — M. S. Alexander, 83 Strachan Avenue, Dundee DD5 1RF. (994)

ADVANCE SWITCH MODE SUPPLIES, unused 5V at 40A £175. 24V at 15A £225. 5V at 20A £135. Teletype 33 keyboard punch reader £250. Prowest 24in 5A B/W monitor £150. — Telephone Chesham (02405) 71432 evenings. (986)

COSSOR 75MHz PORTABLE DUAL TRACE SCOPE, delayed sweep, excellent condition with handbook, £295. — Phone (02556) 6540. Frinton. (989)

BREAKER BREAK. Build your own CB rig (27 MHz transceiver), full circuit diagram and parts list. All components available in UK. Send a large SAE and £2.95 to P. Sherwood, 89 Avlestone Walk, Manchester M10 9NU. I'm on the side. (991)

GET INTO TELEPHONE ANSWERING SERVICING. Telstor (old model) operational manual, £4.50. Autophone manual £3.75. Old model Telstor spares available. SAE enquiries. G. Hay, 189 West Hendon Broadway, London NW9. 01-202 3344 (Callers by appointment please).

VACUUM EQUIPMENT. Edwards 12in coating unit. Also 140 L/S. Ion pump and chamber. Ion gauge. Fleet 3266. (1012)

NEW 1981

MODERN ELECTRONIC CIRCUITS REFERENCE MANUAL

by Markus Price: £32.50

RADIO AMATEUR HANDBOOK by ARRL 1981 ed. Price: £8

THE ART OF ELECTRONICS by P. Horowitz Price: £13.50

WORLD RADIO TV HANDBOOK, 1981 edition Price: £10.50

ELECTRONIC PRINCIPLES 2nd ed. by A. P. Malvino Price: £4.35

MANUAL OF ELECTRONIC SERVICING TESTS AND MEASUREMENTS by R. Genn Price: £10

INTRO. TO DIGITAL FILTERS by T. Terrell Price: £6.95

MICROPROCESSORS AND MICROCOMPUTERS FOR ENG. STUDENTS AND TECHNICIANS by B. Wollard Price: £5.65

USING CP/M A SELF-TEACHING GUIDE by J. Fernandez Price: £6.75

* ALL PRICES INCLUDE POSTAGE *

THE MODERN BOOK CO.

Specialist in Scientific & Technical Books

19-21 PRAED STREET LONDON W2 1NP

Phone 402-9176

Closed Sat. 1 p.m. (8974)

G.W.M. RADIO LTD, 40/42 Portland Road, Worthing, Sussex. Telephone 34897 for surplus, wholesale and retail. Ex-Government and Marine Communications receivers for callers. Changing stocks of test equipment, part exchanges, etc. Radio telephone equipment supplied to the trade. Model 7 Avometers £32 incl. Some Avometer movements available for selection by callers. Dashboard watches by Golay £35 each incl. WANTED end lots and runs for shop and mail order. Test equipment. Large or small lots of factory surplus. R/T sets and systems. (1007)

VIDEO FOR SALE. Philips N1700 VCR LP plus six tapes 2 1/2 hours each. Excellent condition. Little used. £245. Private sale. Tel: office hours 01-460 6174. Also, 5C/450A valves. Two for sale. Any offers.

TELETEXT TEXAS XM11 decoder module complete with infra red, remote control and data, £65. Phone Mirfield 499298 evenings. (983)

MANUFACTURER has surplus test equipment and components for sale, large SAE for list. R. Dutton, 80 Wheatland Lane, Wallasey, Merseyside L44 7EH. (970)

ARTICLES FOR SALE

EXCLUSIVE OFFER

Table with columns: Ref, Ht, width, Depth, Price. Lists rack mounting cabinets and other electronic components.

AUDIO AND INSTRUMENTATION-TAPE RECORDER-REPRODUCERS. Ampex FR1300 7 track 1/2" UHER 4000 1/4" Consolidated 3800 7 track 1/2" Plessey ID33 Digital Units, 7 track 1/2" Plessey M5500 Digital Unit, 7 tracks 1/2" Ampex FR-1100, 6 speeds, stereo 1/4" Ampex FR600, 4 speeds, 7 track 1/2" D.R.I. RC-1, 4 speeds, 4 tracks 1/4" Min-com CMP-100, 6 speeds, 7 tracks 1/4", 1/2", 1" 3M. H. 4 speeds 14 track 1"

Prices of above £70 to £500 Also Transport Decks only available

We have a large quantity of "bits and pieces" we cannot list - please send us your requirements. We can probably help - all enquiries answered.

All our aerial equipment is professional MOD quality

- Collins 5114 Receivers £220.00
Plessey PV245 Panoramic Receivers £190.00
Grainger H-F Log Applier Aerials P.U.R
Racal RA 117 Complete stations £390.00
Leak Stereo 20 Amplifiers £30.00
GEC TT-100 Valves £48.00
Int Jax Receivers £180.00
Racal MA-796 Drive Units £180.00
Optron Optical Encoders £80.00
Ampex Bulk Erasers £95.00
Eimas 6156 Valves £21.00
Clare Flash testers £50.00
Advance Signal Generators H1E-J1 £30.00
Bradley CT 471B VT Multi Meters £60.00
Westrex Multi Cellular H.F. lens Horns £40.00
General Electric 200/600 KHz 500 watt transmitters £245.00
Plessey PR-1556 filter Modulators £45.00
Marconi HR-23 ISB Receivers £220.00
K.B. Discomatic Domestic Juice Boxes £90.00
SCR-625 Mine Detectors in chests £21.00
Clare Flash testers £50.00
Hewlett Packard 400H VTVM Meters £95.00
Hewlett Packard 211A Sq. Wave Gen £80.00
Astrodata & Kor Meteorological Equipment
Ion Pump E.H.T. Power Supplies £60.00
Haynes D.V. 500W Casced Transformers £14.00
G.B. Kalee Flutter Meters, Model 17400 £60.00
Tektronix 551 Scopes £160.00
Tektronix 555 Scopes £180.00
Teleonic VFD Multiplexers £40.00
Hell Schriber RC-28 £75.00
Lenkurt Model 26D Data Sets £90.00
Aerial Multicouplers from £25.00
Marconi TF 1168 Disc Oscillators £90.00
Hughes Memorex Receivers £40.00
Nems Clarke 1306 VHF Receivers £260.00
Telefunken Surveillance Receiver £175.00
Helix Aerials 11" & 18" and Reflectors £18.00
Tektronix 543A Oscilloscopes £90.00
Tektronix 551A Oscilloscopes £150.00
Simon Mobile 80 foot Tower Hydraulic 80ft extended, 12" closed. Mounted on 4-wheel drive Bedford Truck, self levelling, raised and lowered in 10 minutes. Used for servicing dish aerials. £750.00
Racal RA-17 P Receivers £750.00
Collins KWT 6 Transmitter Receivers SSB P.U.R. £90.00
B & K 2407 Electronic Voltmeters £90.00
Winston "5" Band Spectrum Analysers P.U.R. £120.00
Airmac 352 Sweep Generators D £130.00
Advance Transistor Testers TT-15 £30.00
Marconi TF 329 Magnification Meters £140.00
Marconi TF 801/D/1 AM Signal Generators £160.00
Ferranti 25kV Auto Voltage Regulators £150.00
Manson TF 101 Multiplier £100.00
Servomax 2kw Auto regulators £100.00
125ft. Lattice masts, 24" sides P.U.R. £115.00
10ft Light Lattice Sections, 6" sides £18.00
EMI 12" Audio Tape 3600ft 10 1/2" nab. New. £4.50
D.R.I. Model RC-1 Professional Tape Recorder-Reproducers, 4 tracks 1/4" 4 speeds. 1 1/8", 3/4", 7/2" & 1 1/2", 4 amplifiers Monitor Scope All rack mounting & transistorised £250.00
SE4/28 C.R.I. £14.00
Racal 3 & 6 KCS S.S.B. filters £14.00
AVO CT 471A Electronic Multimeters £60.00
Stonorette L Tape Recorders £29.00
Uniselectors, 10 Bank 25-way £35.00
Multi-purpose Trolleys with Jacks 19 x 17" £18.00
Advance 3KVA CV Transformers £120.00
Metal V.D.U. Tables 30" x 36" x 30" £24.00

We have a quantity of Technical Manuals and Periodicals of Electronic Equipment, not photostats. 1940 to 1960, British and American. No lists. Enquiries invited.

- Data Efficiency Respoolers 240v £28.00
Belling Lee 100 Amp Interference Filters £76.00
Oscilloscope Trolleys from £18.00
Racal MA1978 pre-Selectors £85.00
Rack Mounting Operator Tables £10.00
75ft. Aluminium Lattice Masts, 20" sides £400.00
Racal MA-175 L.S.B. Modulators (new) £45.00
Tally 5/8 Track Tape Readers track spooling £65.00
Racal RA-535 SSB Adaptors, new £70.00
Racal RA-298 S.B. Transistorised Adaptors (new) £120.00

We have a varied assortment of industrial and professional Cathode Ray Tubes available. List on request.

PLEASE ADD CARRIAGE AND V.A.T. P. HARRIS ORGANFORD, DORSET BH16 6BR (0202) 765051 (8981)

TELETEXT, TV SPARES & TEST EQUIPMENT. TELETEXT. Latest MK2 external unit kit incl. Mullard Decoder 6101VML and infra-red remote control £258, p/p £2.50 (further details on request). Also MK1 external unit kit incl. Texas XM11 decoder, special offer price £168, p/p £2.50. Both kits incl. UHF modulator, and plug into TV set aerial socket. SPECIAL OFFER! TEXAS XM11 Decoder, new and tested, limited quantity at £ price, £65, p/p £1.40. Stab. power supply (5v) for Teletext decoders, £5.80, p/p £1. Thorn design XM11 interface unit, £1.80, p/p 80p. NEW SAW FILTER IF AMP PLUS TUNER (complete & tested for sound & vision), £28.50, p/p £1. COLOUR BAR & CROSS HATCH GENERATOR KIT (MK4) PAL, UHF aerial input type, & vertical colour bars, R-Y, B-Y, grey scale, etc. P/B controls £35. Batt holders £1.50 or stab. mains power supply kit £4.80. De-luxe case £5.20 or alum. case £2.90, p/p £1.40. Built & tested in De-luxe case (battery) £58, p/p £1.50. CROSS HATCH KIT UHF aerial input type also gives peak white & black levels, batt. op. £11, p/p 45p. Add-on GREY SCALE KIT £2.90, p/p 35p. De-luxe case £2.90. UHF SIGNAL STRENGTH METER KIT £17.50. Alum. case £1.80. De-luxe case £5.20, p/p £1.40. CRT TEST & REACTIVATOR KIT for colour & mono £22.80, p/p £1.70. THORN 9000 Touch Tune Remote control receiver unit plus transmitter handset £18, p/p £1.40. THORN 9000 Fascia incl. channel select. indicator, set controls, speaker, £5.80, p/p £1.60. TV SOUND IF TRANSTD. Tested, £6.80, p/p 85p. BUSH SURPLUS IF PANELS. A816 £1.80, TV312 (single I.C.) £8, Z718/BC6100 £5, A823 (Exp) £2.80, p/p 85p. BUSH Z718/BC6100 Line Time Base Panel Z904, incl. LOPT, EHT stick, Focus, etc., 18in or 22in, £15, p/p £1.60. BUSH 181 series TB panel A634 £3.80, p/p £1.20. DECCA colour TV Thyristor Power supply £3.80, p/p £1.40. GEC 2010 series TB panel £1, p/p 90p. GEC 2040 CDA panel £4.50, p/p £1.20. PHILIPS. G8 S/S conv. panel £2.50, p/p £1.20. G8 Decoder panels for spares £1.80, p/p £1.20. G9 Signal panels for small spares £3.80, p/p £1.20. THORN 3500 Line TB panel £5, p/p £1.3000 ex-rental panels IF, VIDEO, DECODER, £5, p/p £1.20. 8000/8500 TB saly/spares £4.80, p/p £1.9000 Line TB (incl. LOPT) saly/spares £7.50, p/p £1.60. COLOUR SCAN COILS (Mullard or Plessey) £6, p/p £1.80. Yoke £2.50, p/p £1. Blue Lat 75p, p/p 35p. Mono Scan Coils (Thorn, Philips, Pye) £2.80, p/p £1. VARICAP UHF TUNERS. Mullard U321 £7.80, ELC1043/05 £5.50. G.I. £3.50. Salv. (assd) £1.50, p/p 45p. Varicap UHF/VHF ELC2000S £8.50. Bush (dual) £7.50, p/p 70p. TOUCH TUNE CONTROL units, Bush (6 pos) £4.50, p/p 80p. VARICAP CONTROL UNITS 3 pos. £1.20, 4 pos. £1.50, 5 pos. £1.80, 6 pos. £1.80, 6 pos. special offer £1, p/p 45p. UHF transtd. Tuners (rotary) incl. s/m drive £2.50, 4 pos. P/B £2.50, 6 pos. P/B £4.20, p/p £1.20. (Special types available, details on request). DL50 Delay Line £2.50, p/p 50p. Large selection of LOPTS, Triplers, Mains Droppers, and other spares for popular makes of colour & mono receivers. PLEASE ADD 15% VAT TO ALL PRICES. — MANOR SUPPLIES, 172 WEST END LANE, WEST HAMPSREAD, LONDON. N.W.6. SHOP PREMISES. Tel. 01-794 8751. Easily accessible W. Hampstead Jubilee Tube & Brit Rail N. London (Richmond-Broad St.) and St. Pancras-Bedford. Buses 28, 159, 2, 13. Callers welcome. Thousands of additional items not normally advertised available at shop premises. Open daily all week incl. Saturday (Thursday half day). MAIL ORDER: 84 GOLDERS MANOR DRIVE, LONDON NW11 9HT. PLEASE ADD 15% VAT to all prices. (80)

THE SCIENTIFIC WIRE COMPANY
P.O. Box 30, London, E.4
ENAMELLED COPPER WIRE
SWG 1lb. 8oz. 4oz. 2oz.
8 to 29 2.76 1.50 .80 .60
30 to 34 3.20 1.80 .90 .70
35 to 40 3.40 2.00 1.10 .80
41 to 43 4.75 2.60 2.00 1.42
47 8.37 5.32 3.19 2.50
48 to 49 15.96 9.58 6.38 3.69
SILVER PLATED COPPER WIRE
14 to 30 6.50 3.75 2.20 1.40
TINNED COPPER WIRE
14 to 30 3.38 2.36 1.34 .90
Prices include P&P. VAT and Wire Data SAE for list. Dealer enquiries welcome. Reg Office: 22 Comingsby Gardens. (9063)

INVERTERS
High quality DC-AC. Also "no break" (2ms) static switch, 19" rack. Auto Charger.
COMPUTER POWER SYSTEMS
Interport Mains-Store Ltd.
POB 51, London W11 3BZ
Tel: 01-727 7042 or 0225 310916 (9101)

VIDEO CONVERSIONS
5-hour dual speed conversion to Philips N1700 VCR now available. Excellent picture and sound quality in kit version, £65; fitted £83.
1500-01-02 LP conversion tool!
Video in-out modifications
Evans Video Services
Video Engineering Specialists
Tel: 061-435 8696 (943)

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolack Light Sensitive Lacquer — now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibre-glass Board approx. 1mm thick £1.75 sq. ft. Post/Packing 60. — White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall. (714)

EQUIPMENT WANTED
TO ALL MANUFACTURERS AND WHOLESALERS IN THE ELECTRONIC RADIO AND TV FIELD
BROADFIELDS & MAYCO DISPOSALS
will pay you top prices for any large stocks of surplus or redundant components which you may wish to clear. We will call anywhere in the United Kingdom.
21 LODGE LANE
NORTH FINCHLEY, LONDON N12 8JG.
Telephone Nos. 01-445 0749/445 2713
After office hours 958 7624 (9123)

CAPACITY AVAILABLE
PRINTED CIRCUIT BOARDS. Conventional double and single sided PCBs. Fast prototype and production runs. Contact John Ritchey, Phototechnique, 11 Old Wincey Road Eynsham, Oxford. Telephone Oxford (STD - 0865) 880645. (9123)

CAPACITY AVAILABLE
PCB ASSEMBLY
CAPACITY AVAILABLE
Low or high volume, single or double sided, we specialise in flow line assembly of printed circuit boards.
Using the Zevatron flow soldering system and on line lead cutting, we are able to deliver high quality assemblies on time, and competitively priced. Test facilities available.
Find out how we can help you with your production. Phone or write. We will be pleased to call on you and discuss your requirements.
TW ELECTRONICS LTD.
120 NEWMARKET ROAD
BURY ST. EDMUNDS, SUFFOLK
TEL: 0284 3931
Sub-contract assemblers and wirelers to the Electronics Industry (9068)

I.H.S. SYSTEMS
Due to expansion of our manufacturing facilities we are able to undertake assembly and testing of circuit boards or complete units in addition to contract development.
We can produce, test and calibrate to a high standard digital analogue and RF equipment in batches of tens to thousands.
Telephone to arrange for one of our engineers to call and discuss your requirements, or send full details for a prompt quotation.
TEL. 01-253 4562
or reply to Box No. WW 8237 (8237)

SMALL BATCH PRODUCTIONS wiring assembly to sample or drawings. Specialist in printed circuits assembly. Rock Electronics, 42 Bishopsfield, Harlow, Essex 0279 33018. (8094)

ELECTRONIC DESIGN SERVICE. Immediate capacity available for circuit design and development work, PC artwork, etc. Small batch and prototype production welcome. — E.P.D.S. Ltd., 93b King Street, MAIDSTONE, Kent. 0622-677916. (9667)

PCB ARTWORK DESIGN SERVICE with component notation masters and assembly drawings. PADS Electrical Ltd, 01-850 6516, 45 Southwood Road, New Eltham SE9. (7905)

PRINTED CIRCUIT BOARDS. Quick deliveries, competitive prices. Quotation on request, roller tinning, drilling, etc. Speciality small batches. Larger quantities available. Boardraven Ltd, Lancaster Road, Carnaby Industrial Estate, Bridlington, North Humberside, YO15 3QY. For the attention of Mr J. Harrison. Tel: (0262) 78788. (443)

P.C.B. DESIGNS on circuit diagrams, etc. Competitive hourly rates, quotes free, cheaper hourly rates for solder resists and legends. — Helstead Designs Ltd, Helstead, Tel: 0787-477408. (869)

COMPARE our charges, quality and turnaround for printed board artworks assembly, test and prototype manufacture. Please phone Sharon Halfhide on Chelmsford 357935 or write to H.C.R. Artwork Designs, 1 Bankside, off New Street, Chelmsford, Essex. (557)

P.C.B.s WIRING assembly looms, coils, instruments, quality design prototype and production service in house or on site. — Batvale Ltd, Ely (0353) 778756. (982)

MANCHESTER POLYTECHNIC
Department of Communication Arts and Design
SENIOR TECHNICIAN
required for the School of Film and Television. Experience required in operation and maintenance of electronic equipment, preferably CCTV and/or sound equipment. An appropriate qualification such as ONC or City and Guilds would be an advantage. A Union Membership Agreement is in operation under which new employees are required to join a recognised union. Salary scale: T3/4 £5,268-£6,851. For further particulars and application form (returnable by 3 April 1981) send a self-addressed envelope marked A/353 to the Secretary, Manchester Polytechnic, All Saints, Manchester, M15 6BH. (988)

TESTERS, TEST TECHNICIANS, TEST ENGINEERS. Earn what you're really worth in London working for a World Leader in Radio & Telecommunications. Phone Len Porter on 01-874 7281, or write: REDIFON TELECOMMUNICATIONS Ltd., Broomhill Road, Wandsworth, London, SW18. (9858)

EXACT TIME?
MSF CLOCK is ALWAYS CORRECT - NEVER GAINS OR LOSES, SELF SETTING AT SWITCH-ON, DIGITS SHOW Date, Hours, Minutes and Seconds, auto GMT/BST and leap year, also parallel BCD output for computer or alarm and audio to record and show time on playback, receives Rugby 60KHz atomic time signals, built-in antenna, 1000KHz range, ABSOLUTE ACCURACY, £54.80.
V.L.F. 7.10-15KHz Receiver £13.70.
60KHz RUGBY RECEIVER, as in MSF Clock, serial data output, £15.70.
Each fun-to-build kit includes all parts, printed circuit, case, postage etc money-back assurance so GET yours NOW.
CAMBRIDGE KITS, 45 (WR) Old School Lane, Milton, Cambridge (965)

BUILDING RAMS?
Why waste time hand-wiring RAMS? This 5.3 x 2.5 inch professional plated thru PCB mounts on your prototyping board, looking like an 8K byte TTL compatible static RAM. 13 address lines, 8 data I/O, write enable, 2 neg and 1 positive card selects.
Assembled with sockets, pins and caps, just plug in 16 2114's and 1 74LS13B £21. Bare board £15, no VAT, post paid.
Ibix Electronic Design
56H Norris Hill Drive
Heaton Norris
Stockport, Cheshire (850)

ENCAPSULATING, coils, transformers, components, degassing, silicone rubber, resin, epoxy. Lost wax casting for brass, bronze, silver, etc. Impregnating coils, transformers, components. Vacuum equipment low cost, used and new. Also for CKT regunning metalising, Research & Development, Barratts, Mayo Road, Croydon, CR0 2QP. 01-684 9917. (9878)

MEMORY BARGAINS. Low price guaranteed devices. Eprom programming service. SAE for information, T.D.S., 57 Westmead, Woking, Surrey, GU21 3BS. (907)

CLEARANCE PARCELS: Transistors, resistors, boards, hardware, 10lbs only £5.80! 1,000 Resistors £4.25, 500 Capacitors £3.75, BC 108, BC 177, BC 204, BC 230, 2N 5081, CV7497 Transistors, 10-70p, 100-£5.80, 2N 3055, 10 for £3.50, S.a.e. lists: W.V.E. (3), 15 High Street, Lydney, Glos. (444)

LAB CLEARANCE: Signal Generators; Bridges; Waveform, transistor analysers; calibrators; standards; millivoltmeters; dynamometers; KW meters; oscilloscopes; recorders; Thermal, sweep, low distortion true RMS, audio FR, deviation. Tel. 040-376236. (8250)

BAND NEW VERO RACKS 19in x 5 1/2in, complete with 20 off 40 way edge connectors (only 6 used), 20 card slides and locking front panel (12in long). P.S.U. insitu on card slides having 110/240v input, on/off switch and power on indicator. Output is +5v at 5 amps and -10v at 5 amps, fully stabilised. (Can be converted to +12v at 5 amps). Price £35 P/P and VAT inclusive. Rushmore Electronics Ltd, 43 Queens Road, Farnborough, Hants. Telephone 0252 515373. (975)

AIRCRAFT BAND Xtal controlled Receiver Type Lowe AP-12. 95s. — Telephone Derby 768080. WANTED. Sweep generator in HF range. (980)

AVELEY CYBERVOX reel to reel language laboratory. Type AERC4 recorders, various items control unit, headsets, desks, offers invited for whole or part. Further details, Language Centre, Exeter University, Exeter EX4 4QH. Telephone Exeter 77911, extension 775. (981)

TELETYPE KSR33 with stand £100. Scopex 4D10A dual 10 MHz oscilloscope with probes, £150. — Telephone Cambridge 46504. (987)

SERVICES

P.C.B. MANUFACTURE AND ASSEMBLY

Wave Soldering and inspection. High quality PCBs from your artwork. Prototype design. Artwork from your circuit. Fast turnaround.

Endean Communications Services Ltd., Baileys Mill, The Cliff, Matlock, Derbys. (0629) 4929. Tlx. 378267 ECS G. (859)

SMALL BATCH PCB's produced from your artwork. Also DIALS, PANELS, LABELS. Camera work undertaken. FAST TURNAROUND. Details: Winston Promotions, 9 Hatton Place, London EC1N 8BV. Tel. 01-405 4127/0960. (0794)

P.C.B. PROTOTYPE and small batch production. Design layout, assembly and testing. Fast, reliable service. Wye Valley Electronics, 15 High St. Lydney, Glos. Tel: Dean (0594) 41267. (385)

SHEET METAL WORK, fine or general front panels chassis, covers, boxes, prototypes. 1 off or batch work, fast turnaround. 01-449 2695. M. Gear Ltd., 179A Victoria Road, New Barnet, Herts. (812)

ELECTRONIC DESIGN SERVICES. MICROPROCESSOR HARDWARE and SOFTWARE design facilities have now been added to our established expertise and comprehensive test facilities previously available to you for ANALOGUE and COMMUNICATIONS designs. For fastest results please phone Mr. Anderson, Anderson Ltd, Ridgeway, Hog's Back, Seale (nr. Farnham), Surrey. 02518-2639. (275)

CIRCOLEC

THE COMPLETE ELECTRONIC MANUFACTURING SERVICE

Let us realise all or any part of your project from prototypes to production, from artwork design and component sourcing, through assembly and test to final quality assurance, packing and delivery.

We also provide a test, repair and modification service to suit your individual requirement.

For competitive prices and fast turnaround contact:

CIRCOLEC, 1 Franciscan Road, Tooting, S.W.17

Telephone: 01-767 1233 (544)

DESIGN DEVELOPMENT MANUFACTURE. We can offer a high quality, professional service, covering all aspects from original design to small batch production. Digital/Analogue prototypes welcome. For competitive pricing and quick delivery phone Mr. Flower, Digitalis Ltd., 9 Milldown Road, Goring-on-Thames, Oxfordshire. Tel: 0491 873162. (936)

P.C.B. WIRING undertaken at a competitive rate. Can pick up and deliver. Write to Mr D. Pitt, 29 Bridgewood Close, Penge, London SE20 or phone 01-778 1374. (979)

TURN YOUR SURPLUS Capacitors, transistors, etc. into cash. Contact COLES-HARDING & Co., 103 South Brink, Wisbech, Cambs. 0945-4188. Immediate settlement. We also welcome the opportunity to quote for complete factory clearance. (9509)

DESIGN AND DEVELOPMENT. ANALOGUE, DIGITAL, RF AND MICROWAVE CIRCUIT AND SYSTEM DESIGN. Also PCB design, mechanical design and prototype/small batch production. Adenmore Limited, Unit 103 Liscombe, Bracknell, Berks. Tel: Bracknell 52023. (656)

PRINTED CIRCUIT BOARDS

Manufactured, any quantity, competitive prices, roller tinned, photographic and artwork services available.

MAYLAND PCB CO. LTD. 4 The Drive Maylandsea, Chelmsford, Essex Tel: 0621 741560 (937)

P.C.B. INDIGESTION? Investigate cost of using hybrid modules to ease assembly problems and improve reliability. Contact D. L. Brady, 43 Montague Road, Slough. Phone 38030. (969)

2716 (-5V) PROGRAMMING. From HEX: 4. Duplication: £1. SAE to J. Adamson, The Rectory, Oulton, NR32 3JX. (978)

SMALL BATCH PRODUCTION of your designs. PCB and circuit design, analogue, digital, software design for microprocessor based systems. Basingstoke 52451. (1006)

ARTICLES WANTED

SPOT CASH

paid for all forms of electronics equipment and components.

F.R.G. General Supplies 550 Kingston Road London SW20 8DR

Tel: 01-404 5011 Telex: 24224. Quote Ref. 3165 (8742)

WANTED

Test equipment, receivers, valves, transmitters, components, cable and electronic scrap, any quantity. Prompt service and cash. Member of A.R.R.A.

M & B RADIO 88 Bishopgate Street Leeds LS1 4BB 0532-35649

STORAGE SPACE is expensive, why store redundant and obsolete equipment? For fast and efficient clearance of all test gear, power supplies, PC boards, components, etc., regardless of condition or quantities. Call 01-771 9413. (8209)

RHODE & SCHWARZ

Selective UHF V/Meter. Bands 4 & 5. USVF Selectomat Voltmeter USWV £450. UHF Sig. Gen. type SDR 0.3-1GHz £750. UHF Signal Generator SCH £175. XUD Decade Synthesizer & Exciter. POLYSKOPS SWOB I and II. Modulator/Demodulator BN1 7950/2. UHF Sig. Gen. type SCR. 1-1.9GHz.

MARCONI

TF2360R TV Transmitter Sideband Analyser. TM6936R UHF Converter for above. TF1101 RC oscillators £65. 6551 SAUNDERS. 1400-1700MHz. FM. TF1066B/1. 10-470MHz. AM/FM. TF1152A/1. Power meter. 25W. 500MHz £50. TF1370A RC Oscillator £135. TF791D Carrier Deviation Meter.

U.H.F. SIGNAL GENERATORS

TF1066B/2 400-555MHz. Deviation to 300KHz. TF1060/2 450-1250MHz. TF1058 1.6-4000MHz.

BECKMAN TURNS COUNTER DIALS

Miniature type (22mm diam.). Counting up to 15 turn "Helipots." Brand new with mounting instructions. Only £2.50 each.

PRINTED CIRCUIT MOTORS

'Printed Motors Ltd' type G16M4. 60V DC. 5.5 amps. Continuous torque 140oz. in. 2350 rpm. Diameter 7.5". Depth 2.5". Shaft diam. 1/2 & 3/4". Price from Printed Motors is now over £150 ea. Supplied in good, used condition, tested & guaranteed £25 each (postage £3).

AUDIO & RF SIGNAL GENERATORS

ADVANCE types H1, H1E, C2, SG62B, J4A. TAYLOR 62A (AM/FM). AVO HF134. AIRMEC 352 Sweep Generator. MARCONI TF1066B/1 (AM/FM 10-470MHz).

LABORATORY OVENS.

Gallenkamp 3 cu. ft. £145. Also Morgan Grundy 1 cu. ft. £55. 20-WAY JACK SOCKET STRIPS. 3 pole type with two normally closed contacts £2.50 each (+25p pp). Type 316 three pole plugs for above - 20p ea. (pp free).

P. F. RALFE ELECTRONICS

10 CHAPEL STREET, LONDON, NW1 TEL: 01-723 8753



RANK KALEE 1742 Wow & Flutter Meter. AIRMEC 314A Voltmeter. 300mV (FSD)-300V. AIRMEC Wave Analysers types B53 & 248A. DERRITRON 1KW Power Amplifier with control equipment for vibration testing, etc. HEWLETT-PACKARD 8551B/851B Spectrum Analyser. 10MHz-40GHz. HEWLETT-PACKARD tuned amp & null detector. TF2600 Voltmeter 1mV-300V ftd. RADIOMETER Distortion Meter BKF6 £125.

LABGEAR T.V. PATTERN GENERATORS 625-line cross-hatch/dot/grey scale £45 (£1 post). RANK SIGNAL STRENGTH METERS UHF Channels 20-60. Battery operated £30 (£1 post).

TELEVISION TEST EQUIPMENT

TEXSCAN VS-60B Sweep Generator. 0-1000MHz £250. TEXSCAN DU-88 X-Y Display units £95. TELONIC 2003 Sweep Generator System £225. TELONIC 101 X-Y Display units £75. TELONIC 1204 Sweepers 0-500MHz £150. TELONIC 121 X-Y Display units £95.

OSCILLOSCOPE SALE

SOLARTRON CD1400. D/Beam 15MHz £150. HEWLETT-PACKARD 1707A. 75MHz £450. TELEQUIPMENT D75. TELEQUIPMENT DM64 Storage scope. DYNAMCO D7100. HEWLETT-PACKARD 122A SB. Audio. AIRMEC 279. 4 Beam Display Scope. TEKTRONIX 581A. 545A & B. 544, 661, 515A.

NOTICE. All the pre-owned equipment shown has been carefully tested in our workshop and reconditioned where necessary. It is sold in first-class operational condition and most items carry our three months' guarantee. Calibration and certificates can be arranged at cost. Overseas enquiries welcome. PLEASE ADD 15% VAT TO ALL PRICES.

DC POWER SUPPLIES

*APT 10459/8, 12-14V @ 5 Amps £25 (£2 p.p.) *APT 10459/8, 24V @ 5 Amps £25 (£2 p.p.) *We can supply the above power supply at any fixed voltage between 5V and 36V at 5A £25. *Mullard Dual Neg 12V at 1A and 0.4A respectively. Dimensions 9x4x5ins. £10 + 1 p.p.) *FARNELL Current limited. Dimensions 7x5x4ins. Following types available: 13-17 Volts @ 2A £15. 27-32 Volts @ 1A 5V £15. 5V @ 3A £15. (pp £1.50).

SPECIAL PURCHASE LAMBDA POWER SUPPLIES

Excellent LX5 Series DC power units at less than a tenth of new price. The snag? - they're all 110V AC input. Prices as follows: 5V at 24A. LX5 D5 0V R. £25. (List £350). 15V at 12A. LX5 D15 R. £20. (£339). 5V at 14A. LX5 CC 5V. £20. (£258). 24V at 3.1A. L5C 24. £15. (£223). Carriage each £2.50 extra

MODULATION METERS

AIRMEC 210 3-300MHz. AM/FM. £125 RADIOMETER AFM/1 3.5-320MHz. AM/FM. £145 RACAL 409 3-600MHz. AM/FM.

ROTRON INSTRUMENT COOLING FANS

Supplied in excellent condition, fully tested: 115V, 4.5 x 4.5 x 1.5" £4.50. 230V ea. 115V, 3 x 3 x 1.5" £4 + postage ea. 35p.

CT212 RF Signal Generators. 85KHz-32MHz £55.

BELL & HOWELL MICROFICHE VIEWERS

Type SR5. Screen size 9 x 5" New condition £75.

DIGITAL MULTI-METERS

DE FOREST ELECTRONICS TYPE MM200. DC V 0-1KV. AC V 0-700. DC 1.0-1A. AC 1.0-1A. Each in 4 ranges. Resistance 0-19.99 Mohms. 5 ranges. LED Display 1999. BRAND NEW. SPECIAL REDUCED PRICE OF £39, INCLUDING VAT & P.P.

CLASSIFIED ADVERTISEMENTS

Use this Form for your Sales and Wants

PLEASE INSERT THE ADVERTISEMENT INDICATED ON FORM BELOW

To "Wireless World" Classified Advertisement Dept., Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS

- Rate £2 PER LINE. Average six words per line. Minimum £10 (prepayable). Name and address to be included in charge if used in advertisement. Box No. Allow two words plus £1. Cheques, etc., payable to "IPC Business Press Ltd." and cross "& Co."

NAME..... ADDRESS.....

Table with 4 columns: Type, Sec Taps, Amps, Price, Carr. Contains various electronic component listings.

REMITTANCE VALUE..... ENCLOSED

PLEASE WRITE IN BLOCK LETTERS. CLASSIFICATION..... NUMBER OF INSERTIONS.....

Samson's (ELECTRONICS) LTD.

9 & 10 CHAPEL ST., LONDON, NW1 01-723 7851 01-262 5125 ADJACENT TO EDGWARE ROAD MET. LINE STATION

PLEASE ADD 15% TO ALL ORDERS INC. CARR.

CURRENT RANGE OF NEW LT. TRANSFORMERS

OPEN TYPE TAG CONNECTIONS ALL PRIMARIES 220-240V

Table with 4 columns: Type, Sec Taps, Amps, Price, Carr. Lists various transformer models and prices.

HEAVY DUTY LT C CORE TRANSFORMERS. PRI 110-220-240V sec. 12V 40A £22.50. Carr. £4. PRI 110-220-240V secs 14V 3V 1 1/2 1V. Separate windings 40A each, 14-15-15/2-17-18-18/2-19-19/2V at 40A £25. Carr. £4. PRI 220-240V sec. 140V CT (70-0-70V) 10A size 7 x 7 x 7ins. top panel connections £23.50, Carr. £5.

HEAVY DUTY ISOLATION TRANSFORMERS 240-240V ex-computer equipment. Large selection available 10-15 amps. Fraction of maker price. Telephone for further details.

HEAVY DUTY MULTITAPPED TRANSFORMERS. Ex-computer equipment. Top panel connections. PRI 220-240V, secs. 36V 21A, 19.5V 23A, 47.5V 5A, 31.75V 9A, 19.5V 13A, 47.5V 5A, 36V 4A, 11.5V 12A, 36V 1A seven times. All separate windings, £35 carr.

HEAVY DUTY C CORE LT TRANSFORMERS. PRI 220-240V sec. 18V 27A, 40V 10A, 40V 4A, 25V 4A, 52V 1A. All separate windings. £27.50. Carr. £5.

PARMEKO CASED TRANSFORMERS. PRI 240V sec. 50V CTE 250 watts conservatively rated. Fitted mains on/off switch £10. Carr. £3. PRI 240V sec. 25V 60VA, fitted output sockets, mains on/off switch and fuse. £8.50. P&P £2. PRI 240V sec. 12V 50VA, fitted input and output sockets. On/off switch and fuse. £7.50. P&P £2. Above transformers are designed for low voltage lighting. Supplied brand new at a fraction of maker's price.

GARDNERS UNIVERSAL LT TRANSFORMERS. Open frame top panel connections. PRI 120-240V secs 1v twice, 3v twice, 5v twice, separate windings, all at 6.4amps. Conservatively rated. The following voltages can be obtained 1-13v, in steps of one volt twice and 1-0.1v-13-0-13v in one volt steps, and 1-13v 12.8A £9.75 P&P £2

SPECIAL OFFER OF HIGH GRADE EX-COMPUTER AUTO TRANSFORMERS Conservatively rated by famous makers, perfect condition, fraction of list price Open frame construction top panel connections. 4000 watts tapped 0-105-115-125-135-200, 215-230-240-260V £45. Carr. £4. 3000 watts £39.50. Carr. £4. 500 watt tapped 0-90-115-125-200-210-230-240-250 Volts. Conservatively rated 500 watts £8.75. P&P £2.

LATEST PURCHASE. COMPUTER GRADE LT TRANSFORMERS. Conservatively rated. All Primaries 220-240V. No. 1 Secs. 27V 10A, 9V 3A, 15V 1/2A x 2. Separate windings. £8.50. P&P £2. No. 2 sec. tapped 26-31-36V, 11.2A £12. P&P £2.

LT CHOICES. Potted types 100 M/H 2A £4.50, P&P £2. 130 M/H 1.15A £2.50, P&P £1.50. Open types 12A M/H 10A £3.95, P&P £1.75, 2+2 M/H 4.2A £4.50, P&P £2. 50 M/H 4.4A £4.50, P&P £2. Other types up to 40 amps available. Let us know your requirements.

PARMEKO HT CHOKES. Potted types 15H 250 M/A £4.50, P&P £2. 10H 180 M/A £3.75, P&P £2. 10H 120 M/A £3. P&P £1.50. 50H 50 M/A £1.50, P&P £1. 15H 75 M/A £1.50, P&P £1. 50H 25 M/A £1.50, P&P £1. Swinging type, 5H 40 M/A-4H 250 M/A £3.75, P&P £2. C-Core type 20H 180 M/A £3.75, P&P £2. Open types 25H 60 M/A £2. P&P £1. 25H 25 M/A £1.50. 180H 24 M/A £4, P&P £2.

AEI 20 AMP CONTACTORS. BRAND NEW BOXED FRACTION OF MAKER'S PRICE. Type Coil voltage Contacts Price 0652 415VAC 3M 18 £1.50 0655 415VAC 4M 4M £1.50 0648 110VAC 4M 4M £1.50 0650 110VAC 6M 28 £1.50 0653 110VAC 4M 4M £1.25 0654 110VAC 2M 28 £1.25 0651 110VAC 3M 18 £1.25 0649 42VAC 6M 28 £1.50 0647 42VAC 4M 48 £1.50 P&P 25p kg

HEAVY DUTY HT TRANSFORMERS. PRI 220-240V sec. tapped 150-168V. Conservatively rated at 3 amps, top panel connections, £4.95, P&P £2. C-Core PRI 220-240V, sec. 250-0-250V £7.50, P&P £2. 60 M/A 2.8-0-2.8V 28A, 5V 2A, 6.3V 3A, 24V 3A £7.50, P&P £2.

PARMEKO LT SAFETY TRANSFORMERS. Totally enclosed, fitted with mains on/off switch, spring type output terminals, mains 240V mains lead. Output 6 or 8V 8A. Ideal bench transformer. Brand new. Fraction of maker's price. £5.50. P&P £1.50.

AC WKG BLOCK CAPACITORS BY FAMOUS MANUFACTURERS

Table with 3 columns: MFD, AC Volts wkg, Price. Lists various capacitor models and prices.

DC WKG BLOCK CAPACITORS. 10 MFD 600V DC WKG £2, P&P 35p. 4 MFD 350V DC WKG 75p, 5 MFD 350V DC WKG £1, P&P 35p, 2 MFD 800V DC WKG 50p, 1 MFD 800V DC WKG 50p. Please add 20p per cap postage.

SPECIAL OFFER 12V DC CAR. Five sections, 1 metre fully extended. Complete with dashboard control switch, leads and mounting brackets. These aerials all need slight attention. But motors are runners, £3.95, inc. postage, plus VAT.

PARMEKO OUTPUT TRANSFORMERS. 10 watts. PRI 80000 ct. Sec. 4-8-16! for 2 E184 valves. Atlantic potted series £4.95. P&P £1.50. Farnell multi-tapped Opt Transformers, type MRT/3 7 watts max. DC60 M/A 2/3/7.5! 15!. Data sheet supplied £2.25, P&P 75p.

ARROW HEAVY DUTY SWITCHES. 2 Pole make and 2 Pole break 250V AC 30 amp contacts, recessed, panel-mounting, £1.25, P&P 50p.

METWAY BAKELITE TERMINAL BLOCKS. 12-wire 30 amps packs of ten £4.50, P&P £1.50. Cinch 37-way cable socket ex-computer equipment £1.50. Post paid.

CRESSALL RHEOSTATS. Type S150 4 inch dia. 850! 150 watts, new and boxed £3.50, P&P 75p. Berco 1 1/2in. dia. 1500! 25 watt £1, P&P 50p, 500! 25 watt £1, P&P 50p.

HEAVY DUTY 240V DC CONTACTORS. Single pole make 100 amp contact £2.50, P&P £1. Two pole make 10 amp contacts and 2 pole make 5-amp contact £1.75, P&P 75p. Standard open type relay single-hole fixing AC240V 3 CO 7-amps £1, 2 CO 7-amp 85p, AC 110V 3 CO 7-amps 85p, 48V DC 3 CO 85p. Plug-in type AC 12V 1 CO £1, P&P 25p per relay.

AC240V BLOWERS. Ex-computer equipment, perfect condition, robustly housed in metal frame, overall size 11x7x7ins. Ir outlet size 4x3ins. Motor spec. 1300 rpm cont. rated, cap. start, cap. inc. with motor, quiet running £4.95 carr. £2.

sales



ANALYSERS
 TEKTRONIX 1L5 L.F. Spectrum Analyser Plug In. 50Hz-1MHz £700.00
 TEKTRONIX 1L10 Spectrum Analyser Plug In 1MHz-36MHz £700.00
 PARAMETRON 477 L.F. Spectrum Analyser 1MHz-50MHz £800.00

BRIDGES
 GEN-RAD 1607A Transfer Function and Immittance Bridge, complete in wooden box £300.00
 MARCONI 868B Universal Bridge 1KHz-10KHz Source 1% £175.00
 MARCONI 1313 Universal Bridge 0.25% £350.00
 WAYNE KERR B.641 Auto Balance Bridge 0.1% £275.00

COUNTERS
 HEWLETT-PACKARD 5245L + 5253B 8 Digit 500MHz £350.00
 MARCONI TF.2411 7 Digit DC-50MHz £85.00

DIGITAL MULTIMETERS
 KEITHLEY 130 3 1/2 Digit D.M.M., NEW £78.00
 Case for above £7.00
 FLUKE 8100A 3 1/2 Digit DC/AC Volts and Resistance £95.00



MARTIN ASSOCIATES
 71 Basingstoke Road
 Reading, Berks.
 Tel. Reading (0734) 868109

WW - 071 FOR FURTHER DETAILS


METERS
 HEWLETT-PACKARD 3400A RMS Voltmeter 10Hz-10MHz £295.00
 DYMAR 711 Millivoltmeter £65.00
 MARCONI TF.791D Carrier Deviation Meter 4MHz-1024MHz £100.00
 MARCONI TF.1020A R.F. Power Meter 250 MHz 100W 50 Ohms £100.00
 MARCONI TF.2600 Sensitive Valve Voltmeter 10Hz-5MHz £130.00
 MARCONI TF.1245/46/47 "Q" Meter and 2 Oscillators 1KHz-300MHz £750.00
 HEWLETT-PACKARD 130 L-C Meter 1uH-300uH and 1pF-300pF £125.00
 SIEMENS 3U84alb Thermal Milliwattmeter 1-500mW 12.5GHz £120.00

OSCILLOSCOPES
 COSSOR CDU.150 D/Beam DC-35MHz 5mV/cm £300.00
 HEWLETT-PACKARD 141A D/Beam DC-20MHz Storage £350.00
 NEW Oscilloscope Kikusui 5520 DC-20MHz Sens. 1mV/10MHz £230.00
 TEKTRONIX 432 Oscilloscope DC-25MHz Sens 10mV/div £400.00
 TELEQUIPMENT D.83 D/Beam DC-50MHz £850.00
 TEKTRONIX 603 Storage Monitor £600.00

PROBES
 TEKTRONIX P.6105 X10 DC-100MHz £40.00
 TEKTRONIX P.6056 X10 DC-3.5GHz £60.00
 TEKTRONIX P.6057 X100 DC-1.4GHz £60.00
 TEKTRONIX P.6075A X10 200MHz £50.00
 TEKTRONIX P.6430 Temperature Probe -85°C to +150°C £75.00

SIGNAL SOURCES
 ADVANCE PG.52B Pulse Generator c/w P6:P1A:P2A:P3A Plug Ins £550.00
 AIRMEC 304 Power Oscillator 50KHz-100MHz 10V into 50 Ohms £100.00
 AIRMEC 365A AM/FM Generator 1-320MHz 50 and 75 Imp £225.00
 HEWLETT-PACKARD 606B H.F. Oscillator 50KHz-65MHz 50 Ohms £500.00
 HEWLETT-PACKARD 8443A Tracking Generator 100KHz-110MHz 500hms £900.00
 MARCONI TF.801D/8S AM Signal Generator 10MHz-485MHz £300.00
 MARCONI TF.1101 R-C Oscillator 20Hz-200KHz £95.00
 MARCONI TF.6700A Sweep Oscillator 8-12GHz £1200.00
 DECCA EP685AGB Pal Colour Bar Generator £250.00
 LABGEAR CM.6052/CB Pal Colour Bar Generator £110.00

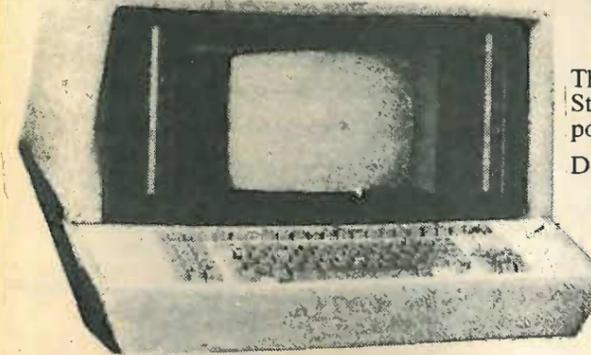The AIRAMCO Mikro 1000 -The Scottish Solution.



The Mikro 1000 is a Scottish built micro-computer which combines State of Art technology with simplicity and durability to give a powerful small business system at a very competitive price.

Driven by a 2.5 MHz or 4 MHz Z80 processing unit constructed around Industry Standard S100 Bus, the Mikro 1000 is designed to provide the ease of expansion necessary in a modern growing business or industry - memory is expandable from 32K to 256K, with up to 4 Megabytes of on-line disk storage.

The integral VDU has an 80 cols. x 24 lines screen, and incorporates a green phosphor CRT, while the 117 key keyboard can be used remotely from the main body of the machine, and may be programmed for user functions such as word processing commands.

As well as supporting all CP/M based languages, the Mikro 1000 has a full range of business software, including Sales, Purchase and Nominal Ledger, Inventory Control, and Payroll, as well as Word Processing (which is available at even lower cost as a separate system on the Mikro 1000 WP).

For further information on either Mikro 1000 system, please contact:



Unit A2, Longford Avenue, Kilwinning Ind. Est.,
 Kilwinning, Ayrshire, KA22 8NP.
 Tel: 0294 57755 Telex: 779808

WW - 076 FOR FURTHER DETAILS

FERRITE MAGNETS?

STANDARD
OR SPECIAL SIZES
FOR PROTOTYPE
WORK OR PRODUCTION
AVAILABLE AT SHORT
NOTICE **ALL OTHER
PERMANENT MAGNET
MATERIALS HELD
IN STOCK.**

UNIT 7, HEADLANDS TRADING ESTATE, SWINDON, WILTS. SN2 6JU

TELEPHONE: 0793 33212/3. TELEX: 444407 MAGDEV

MAGNET DEVELOPMENTS LIMITED

WW - 079 FOR FURTHER DETAILS

FLOPPY DISK DRIVES

New Low Prices!
Unbelievable but True!
Read On!

SIEMENS FDD - 100-8/FDD - 200-8

Fully Shugart Compatible Siemens 8" single and double sided disk drives are available now with unbeatable prices at single unit pricing.

Note these specifications:

★ TRACK 00 SENSING	★ WRITE PROJECT CIRCUITRY
★ ACTIVITY INDICATION	★ AUTO DISK EJECTION
★ MECHANICAL END STOPS AT TRACKS 00 AND 76	★ FAIL SAFE INTERLOCK WHICH PREVENTS THE COVER FROM CLOSING ON A PARTLY INSERTED DISKETTE
★ AUTO WRITE CURRENT SWITCHING AT TRACK 43	

FD100-8	SINGLE DENSITY	DOUBLE DENSITY
Capacity per disk unformatted	400 K Bytes 3.2MBit	800 KBytes 6.4Mbits
Bit Density inner track	3268 BPI innertrack	6536 BP1 inner track
Recording Method	FM	MF
Transfer Rate	250KBit/sec	500 KBits/sec
Head Engine Time	25 MS	
Access Time, Track to Track	3 MS	
Settling Time	12 MS	
Number of Recording Surfaces	1	
MTBF	6000 hrs	
MTTR	20 mins	
Power requirements		
AC-Power	240V, 50HZ	
DC-Power	+24V @d 1.8 amps	
DC-Power	+5V @ 1.3 amps	
Weight	5.9kg	
FD200-8		
Same as above except		
Capacity per disk unformatted.	800 KBytes 6.4MBIT	1600 KBytes 12.8 Mbits
Number of Recording Surfaces	2	

PRICING FDD-1008 FROM £249.95 EACH
FDD-200-8 FROM £360.00 EACH

IRVINE BUSINESS SYSTEMS

P.O. BOX 5 IRVINE, Ayrshire TEL: (0294) 75000 TELEX: 777582

*Reference Number 2235

WW - 088 FOR FURTHER DETAILS

Who's Who and What's What in the Electrical Industry

PUBLISHED
MARCH 1981
Price £6.00
incl. postage

Famous for its total coverage, detail and accuracy, the **ELECTRICITY SUPPLY HANDBOOK** usually sells out fast - so ensure your copy and post the coupon below, today!

- Over 2,000 names and locations of executive personnel in the Electricity Council, C.E.G.B., Area Boards and other organisations.
- Major authorities, government departments associated with the electrical industry.
- U.K. power stations, Area Board statistics, electricity tariffs, electrical associations.
- Pull out map of C.E.G.B. Regions, power stations and transmission lines.
- Bound in maps of Area Boards.

To: General Sales Department, Room 205, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS.

Please send me.....copy/ies of **ELECTRICITY SUPPLY HANDBOOK 1981**

Name _____

Address _____

Company registered in England No. 677128. Reg. Office: Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS.

www.americanradiohistory.com

COMPUTER APPRECIATION

86 High Street, Bletchingley, Redhill, Surrey RH1 4PA. Tel: Godstone (0883) 843221

- TELETYPE Model ASR 33** with 20 mA current loop or RS232 interface. 110 Baud, remote reader control (which may be disabled by insertion of a jumper), paper tape reader/punch & stand (when available) from £195 to £150
- TELETYPE Model KSR 33**. As above, but without paper tape facility..... £150
- DATA DYNAMICS Model ASR 390**. Mechanically identical to ASR 33 but with addition of 240v operation, motor cut out feature, reader single stop, stand and silencing cover. RS232 interface. With low hours and in immaculate condition..... £376
- DATA DYNAMICS Model KSR 390**. As above, but without tape reader and punch. RS232/V24. 110 Baud..... £150
- DATA DYNAMICS Model RO 390**. As above, but printer only..... £120
- DI/AN Model 9030**. Desk-top terminal similar to DECwriter LA36. Upper/lower case matrix printer, up to 300 Baud. Features switchable Baud rate, parity, keyboard and duplex options..... £190
- TEXAS SILENT 733 KSR terminal**. 30 cps dot matrix terminal using thermal paper. With 20 mA current loop interface..... £275
- TEXAS INSTRUMENTS Model 743 portable terminal** with V24 & 20 mA interface. Dated 1979 and with BURROUGHS printhead..... £475
- BRAND NEW printhead**..... £175
- TEL Model 1051**. IBM SELECTRIC (Golfball) typewriter based terminal. With standard RS232/V24 serial interface and optical paper tape reader and punch. EBCDIC coded..... £295
- TEL Model 1051**. As above but tested only so far as typewriter operation. Ideal for those users who wish to substitute their own electronics..... £195
- GENERAL ELECTRIC Terminal Model 30**. Upper/lower case matrix terminal with full ASR facility using twin Philips-type cassette units. V24 interface. Ex-demonstration..... £675
- SPERRY-REMINGTON Word Processor**. Incorporating IBM I/O typewriter with twin magnetic card stations. Operating stand-alone; or suitable for conversion to on-line use..... £280
- SCRIBONA Word Processor** with cassette tape unit and golfball typewriter..... £280
- OLIVETTI Model 318 ASR Terminal**. 110 Baud printer with papertape reader/punch and keyboard. One only available. In excellent condition..... £110
- CENTRONICS Model 101A** 165 cps matrix printer. With parallel and serial interface options..... £275
- POTTER Model LP-3000** High Speed (300 lpm) line printer..... £255
- BCL Matrix printer**. 120 cps with dual tractor and long platen (in excess of 300 col.). Unused..... £225
- ODEC Model 4000** belt printer. 65 lpm. Parallel TTL interface. Manufactured 1980..... £195
- DIABLO SERIES 30 DISC DRIVES**. These are offered fully refurbished and may be viewed operating on-line at our premises prior to purchase. 2.5 mByte removable cartridge version is directly compatible with the DEC RK05 drive for PDP/LS11..... £900
- As above, but with cartridge removable by engineer rather than operator..... £475
- WANGO Model T 1222** disc drive. 10 mByte capacity with one fixed and one top loading platter. 2400 rpm, 200 tpi and 2200 bpi. These drives are complete with documentation and have the industry standard interface. IOMEC are no longer in business, nevertheless, electronic components are standard and we can supply incomplete drives free of charge to buyers. Service is, in any case, apparently available for IOMEC drives. BRAND NEW in original boxes..... £350
- WANGO Model T 1222** disc drive. With one fixed and one top loading platter of 5 mByte capacity total. 2500 rpm, industry standard interface..... £500
- (One only BRAND NEW)..... £750
- BURROUGHS disc drives**. 2 x 2.5 mByte front loading cartridge in cabinet. Will interface to most controllers. Schematics available..... £175
- DEC Model CR11** 285 cps CARD READER. Without controller..... £325
- PERTEC Model 6840-9-25** 9-track PE and NRZI tape drives usually available from stock..... £475
- WANGO Model 1025** 9-track NRZ tape drives. 2 drives mounted in cabinet (Please enquire for one-off)..... £1,100
- TREND Model HSR 350**. 350 cps optical reader with TTL interface..... £225
- DATA DYNAMICS Model 1114** high speed tape punch. With parallel TTL interface. With low hours and recently serviced by DATA DYNAMICS. Price includes all documentation..... £325
- Please note:
 * VAT and carriage extra all items
 * Visitors welcome, but by appointment please
 * We are keen to bid competitively for all good used equipment

INDEX TO ADVERTISERS APRIL

Appointments Vacant Advertisements appear on pages 121-132

PAGE	PAGE	PAGE
Acoustical..... 77	Global Spec..... 30, 35	Northern Elec..... 103
Adcola..... 94	GMT Elec..... 98	Northern Radio..... 120
Aero..... 31	GP Industrial Elec. Ltd..... 34	OMB Electronics..... 34
Airamco..... 135	Guide to Broadcasting Stations..... 106	Orion..... 92, 120
Ambit International..... 18, 19	Hameg..... 12	Pascal Electronics..... 12, 24, 118
Anglia Components..... 92	Happy Memories..... 102	PBRA Ltd..... 104
AP Products..... cover iii	Harris Electronics (London) Ltd..... 29	PM Components..... 18
Aspen Electronics Ltd..... 22	Hart Electronics..... 116	Powertran Electronics..... 93, 95
Audio Electronics..... 17	Harwin..... 111	Pye Unicam..... 32, 33
Avel Lindberg..... 102	Henry's Radio..... 114, 118	Pype Hayes..... 108
Avo Inst..... 26	Hi-Fi Year Book..... 115	Radio Compozif Specialists..... 107
Bamber Electronics..... 115	Hilomast..... 10	Ralfe, P. F..... 133
Barnet Metal..... 92	House of Instruments..... 6	RCS Elec..... 120
Barrie Electronics Ltd..... 111	ILP Electronics Ltd..... 96, 97	Rediffusion Reditronics..... 112
Bayliss, A. D..... 108	ILP Transformers Ltd..... 28	Robot (UK)..... 118
BDS Microsystems Ltd..... 120	IMO..... 13	Safgan Electronics..... 102
BIB Hi-Fi..... cover iv	Integrex Ltd..... 100	Sagin..... 108
Bull, J..... 99	Interface Quartz..... 24	Samson..... 133
Carston Electronics Ltd..... 20, 21	International Trade Fair..... 109	Sawter, E. A..... 8, 9
Chiltern Elec..... 105	Irving Design..... 134	Science of Cambridge..... 113
Chilthmead Ltd..... 119	ITA..... 103	Scopex Instruments Ltd..... 36
Clark Masts Ltd..... 10	Keithey Instruments..... 23	Shure Electronics..... 12
Clef Products..... 98	Kelsey Acoustics..... 104	Special Products Ltd..... 12
Colomor..... 120	Kirkham Amplifier..... 27	Spender Audio..... 15
Computer Appreciation..... 114, 136	Langrex..... 101	Strutt Electrical & Semel..... 98, 103, 105
Court Search..... 28	Levell Electronics..... 7	Surrey Electronics Ltd..... 120
Crimson Elektrik..... 35	LJ Elec..... 105	Technomatic..... 110
Davies, A. R..... 114	Lowe Electronics..... 16	Tektronix (UK) Ltd..... 63
Digital..... 108	Magnet Design..... 134	Teleconic Berkley..... 25
Display Electronics..... 117	Maplin Electronic Supplies..... 11	Teleradio..... 98
Elec. M/Services..... 103	Marshall, A. (London) Ltd..... 34	Television..... 104
Electricity Supply Hand Book..... 135	Martin Associates..... 134	Teloman Products Ltd..... 30
Electronic Brokers Ltd..... 2, 3, 4, 5, 29, 31	Mills, W..... 108	Thurby Electronics..... 116
Electro-Tech Comps Ltd..... 14	Minster, J..... 112	Titan Transformers..... 22
Electrovalue..... 118	Monolith..... 31	Valradio Ltd..... 24
Elektron Publishers..... 19	Mullard..... 78	Western-Whybrow Engineering..... 64
Everyday Electronics..... 92	Multicore Solders Ltd..... cover iv	West Hyde Developments Ltd..... 78
Faircrest Eng..... 114	Mura Electronics..... 26	West London Direct Supplies..... 114
Farnell Instruments..... cover ii, 28	Japan: Mr. Inatsuki, Trade Media - IBPA (Japan), B.212, Azabu Heights, 1-5-10 Roppongi, Minato-ku, Tokyo 106. Telephone: (03) 585 0581.	Wilmslow Audio..... 91
Field Tech..... 29	United States of America: Ray Barnes, IPC Business Press, 205 East 42nd Street, New York, NY 10017 - Telephone: (212) 867-2080. Telex: 238327.	Zaerix..... 14
	Mr Jack Farley Jr., The Farley Co., Suite 1584, 35 East Walker Drive, Chicago, Illinois 60601 - Telephone: (312) 63074.	
	Mr Victor A. Jauch, Elmatex International, P.O. Box 34607, Los Angeles, Calif. 90034, USA - Telephone: (213) 821-8581 - Telex: 18-1059.	
	Mr Jack Mentel, The Farley Co., Suite 650, Ranna Building, Cleveland, Ohio 44115 - Telephone: (216) 621 1919.	
	Mr Ray Rickles, Ray Rickles & Co., P.O. Box 2028, Miami Beach, Florida 33140 - Telephone: (305) 532 7301.	
	Mr Tim Parks, Ray Rickles & Co., 3115 Maple Drive N.E., Atlanta, Georgia 30305. Telephone: (404) 237 7432.	
	Mike Loughlin, IPC Business Press, 15055, Memorial Ste 119, Houston, Texas 77079 - Telephone: (713) 783 8673.	
	Canada: Mr Colin H. MacCulloch, International Advertising Consultants Ltd., 915 Carlton Tower, 2 Carlton Street, Toronto 2 - Telephone: (416) 364 2269.	
	* Also subscription agents.	

OVERSEAS ADVERTISEMENT AGENTS:
 France & Belgium: Norbert Hellin, 50 Rue de Chemin Veat, F-9100, Boulogne, Paris.
 Hungary: Mrs Edit, Bajusz, Hungexpo Advertising Agency, Budapest XIV, Varosliget. Telephone: 225 008 - Telex: Budapest 22-4525 INTFOIRE
 Italy: Sig C. Epis, Etas-Kompass, S.p.a. - Servizio Estero, Via Mantegna 6, 20154 Milan. Telephone: 347051 - Telex: 37342 Kompass.


Printed in Great Britain by QB Ltd., Sheeps Place, Colchester, and Published by the Proprietors IPC ELECTRICAL-ELECTRONIC PRESS LTD., Quadrant House, The Quadrant, Sutton, Surrey SM25AS, telephone 01-661 3500. Wireless World can be obtained abroad from the following: AUSTRALIA and NEW ZEALAND: Gordon & Gotch Ltd. INDIA: A. H. Wheeler & Co. CANADA: The Wm. Dawson Subscription Service Ltd, Gordon & Gotch Ltd. SOUTH AFRICA: Central News Agency Ltd. William Dawson & Sons (S.A.) Ltd. UNITED STATES: Eastern News Distribution Inc., 14th floor, 111 Eighth Avenue, New York, N.Y. 10011.

ADVENTURES ON THE IC'S


A SPECIAL £6 OFF INTRODUCTORY OFFER FOR:-
 THE HOBBYIST For everyone who is keen on electronics
 THE STUDENT A sound practical work programme for examination
 THE SERVICE ENGINEER To understand and keep up with modern progress
 THE BUSINESS MAN Basic electronics to help understand the subject

ANYBODY CAN BUILD ELECTRONIC PROJECTS WITH EBBO BOARDS HERE'S HOW TO BUILD AN ELECTRONIC ORGAN.

Here's the Circuit Diagram

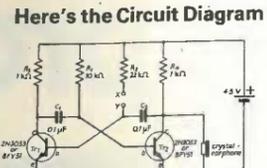

Here's how to build it on EBBO

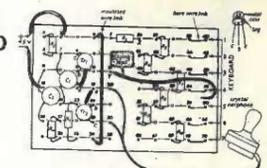


16 PROJECTS INCLUDE
 PARKING LIGHT
 BURGLAR ALARM
 TWO TRANSISTOR RADIO
 CHIP RADIO
 COMPUTER COUNTER
 And many others

COMPONENTS INCLUDE
 1 loudspeaker
 1 variable capacitor
 1 midget potentiometer
 1 ferrite rod
 2 npn transistors (2N3053 or BFY51)
 1 pnp transistor (ZTX500)
 1 field effect transistor (2N3819)
 1 integrated circuit (ZNA14)
 1 photocell, e.g. ORP12
 1 thermistor, e.g. TH3
 ... and many others

COMPLETE PACK OF COMPONENTS TO BUILD ALL 16 PROJECTS Normal Price £17.25

Start with the resistors take resistor 1 (R1) and push it into hole numbers E23 and G5, take resistor 2 (R2) and push it into hole numbers A9 and A11 and do the same with all the other resistors. Then take transistor 1 (TR1) and push it into hole number B8, C13 and D18, do the same with all the other components and you have a full working electronic organ. We even give you tunes to play.

What do you need

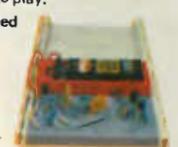

EBBO DISCRETE STARTER PACK Normal Price £6.67




ADVENTURES WITH ELECTRONICS Normal Price £2.30

Total Price Normally £25 SPECIAL INTRO PRICE ONLY £19 inclusive of VAT and Post & Packing. Available from Watford Electronics, BI-PAK and all good component stockists.

DIP-DIP-DIP-DIP-DIP JUMPERS

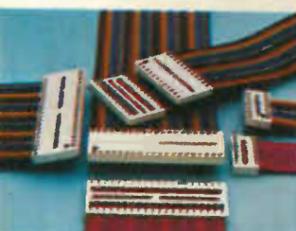AP DIP JUMPERS ARE THE LOWEST PRICE IN THE UK




- EX-STOCK DELIVERY
- 5 STANDARD LENGTHS
6, 12, 18, 24, 36"
- WITH 14, 16, 24, 40 CONTACTS
- FULLY ASSEMBLED AND TESTED
- INTEGRAL MOULDED ON STRAIN RELIEF
- LINE BY LINE PROBEABILITY

SINGLE-ENDED		DOUBLE-ENDED all prices 1-9 off. Huge discounts for quantity					
CONTACTS	24"	CONTACTS	6"	12"	18"	24"	36"
14	£1.67	14	£2.11	£2.21	£2.31	£2.43	£2.63
16	£1.89	16	£2.33	£2.45	£2.58	£2.66	£2.97
24	£2.74	24	£3.45	£3.62	£3.78	£3.94	£4.30
40	£4.38	40	£5.31	£5.61	£5.91	£6.22	£6.81

We can supply DIP, SOCKET, PCB, CARD-EDGE RS232, assemblies made-up, tested, ready for use, cheaper than you can buy the parts, ask for quote.

TEST-CLIP TEST-CLIP

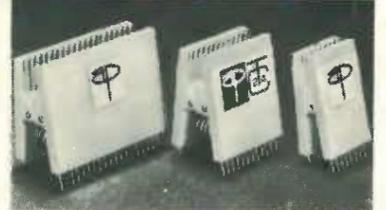

Clip an AP TEST-CLIP over an IC and you immediately bring up all the leads from the crowded board into an easy working level. 22 NEW AP TEST-CLIPS TO PICK FROM

examples:

TC 14	923695	£2.76
TC 16	923700	£2.91
TC 24	923714	£8.50
TC 40	923722	£12.88


POWERACE THE MOST EXPENSIVE BREADBOARD IN THE WORLD



Three poweraces that give you the ultimate in breadboarding. Built in power supplies and a FREE logic probe is built into MODEL 102

POWERACE 101	923221	£61.30
POWERACE 102	923222	£95.80
POWERACE 103	923223	£95.80

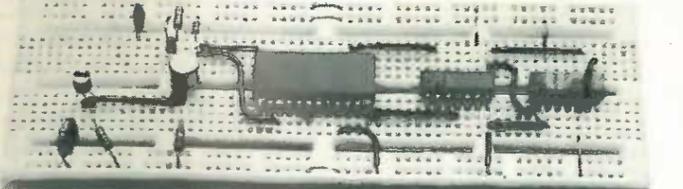SUPERSTRIP SS2 THE BIGGEST SELLING BREADBOARD IN THE WORLD



When you buy a SUPERSTRIP BREADBOARD you buy a breadboard to last you for ever, we give you a LIFETIME guarantee. SUPERSTRIP is the most used breadboard by hobbyists, professionals and educationalists because it gives you more for your money... With 840 contact points SUPERSTRIP accepts all DIP's and discrete components and with eight bus bars of 25 contact points each SUPERSTRIP will take up to nine 14-pin DIP's at any one time. You should only buy a breadboard once so buy the biggest seller with a lifetime guarantee. SUPERSTRIP SS2 923252 PRICE INCL VAT £9.78

All prices shown are recommended retail incl. VAT. In difficulty send direct, plus 50p P & P. Send S.A.E. for a free copy of colour catalogues detailing our complete range.

AP PRODUCTS, PO BOX 19, SAFFRON WALDEN, ESSEX, (0799) 22036



The biggest name in solder worldwide

Products that help you make a better job of it.



Arax Multicore Solder.
Economy pack for general non-electrical use. Replaces solid wire and stick solder. (B.S. 219 Grade L). Econopak 200g reel of 3mm dia. Size 16A. £4.14 per reel.



- | Handy Dispensers | | Per pack |
|------------------|--|----------|
| PC115 | for printed circuits. | £1.15 |
| SV130 | for radio and TV repairs. | £1.61 |
| AR140 | for non-electrical applications, except aluminium. | £1.38 |
| SS160 | for stainless steel and silver jewellery. | £2.53 |
| 19A | for all electronic joints, non-corrosive. | 96p |
| AL150 | for aluminium. | £1.93 |
| BCA16 | solder cream for stainless steel, jewellery and household products (non-electrical). | £3.22 |
| BCR10 | solder cream for electronic and electrical use. | £1.38 |
| BCA14 | all purpose solder cream, non-electrical jointing and repairing. | £1.38 |



Econopak.
Ersin Multicore 5-core solder. Contains non-corrosive flux for electrical applications. 1.2mm dia. 200g Econopak. Size 13A. £4.14 per reel.



Toolbox Reels.
Multicore 5-core solder for general use. Suitable for electrical joints (B.S. 219 Grade G). 40/60 tin/lead. 1.6mm dia. Size 3. £3.91 per reel.

Savbit.
Multicore 5-core solder for radio, TV and similar work. Reduces copper erosion. Suitable for service engineers and manufacturers using small quantities of solder. 1.2mm dia. Size 12. £3.91 per reel.



Metal Soldering.
Arax Multicore 4-acid-core solder for metal fabrication (not aluminium) and repairs. 40/60 tin/lead. 1.6mm dia. Size 11. £3.91 per reel.



Multicore Wick.
Multicore solder-wick for removing solder from virtually any joint. 1.7mm dia. Size AB10. £1.38 per reel.

Tip Kleen.
Multicore Tip Kleen. Soldering-iron tip wiping pad. Replaces wet sponges. (Should not be used above 350°C). 81p per pack.



TV and Radio Soldering.
Savbit Multicore for radio, TV and similar work. Reduces copper erosion. 1.2mm dia. Size 5. 90p per handy dispenser.
Econopak.
General purpose solder suitable for all electrical joints. 40/60 alloy 1.2mm dia. Size 6. 58p per handy plastic dispenser.



Aluminium Soldering.
Alu-Sol Multicore 4-core solder for soldering most types of aluminium. No extra flux needed. 1.6mm dia. Size 4. £6.90 per reel.



Soldering Flux Pastes.
Multicore soldering flux paste. Extra fast, non-corrosive, rosin-flux for electrical and general purpose soldering.
Rosin R.F.10. 35g net. 69p per pack.
Multicore soldering flux paste for soft metals (except aluminium) and stainless steel. Non-electrical.
Arax A.F.14. 35g. 69p per pack.



Wire Stripper and cutter.
Wire stripper and cutter with precision ground and hardened steel jaws. Adjustable to most wire sizes. With handle locking catch and easy-grip plastic covered handles.
Ref. 9. £2.69 per pair.

Bib Hi-Fi Accessories Ltd., (Solder Division), Kelsey House, Wood Lane End, Hemel Hempstead, Hertfordshire HP2 4RQ. Telephone: (0442) 61291.

All recommended retail prices shown are inclusive of VAT. If you have difficulty in obtaining any of these products send direct with 40p for postage and packing. For free colour brochure send S.A.E.

WW-004 FOR FURTHER DETAILS

www.americanradiohistory.com